

60c MAY 1970

Radio-Electronics



BUILD
"The Ultimate"

R-E's NEW
STEREO FM TUNER

EXPERIMENT WITH
Computer logic circuits
10 Emitter-follower
circuits


BONUS FEATURES
Kwik-Fix™ transistor agc
Photography 1970

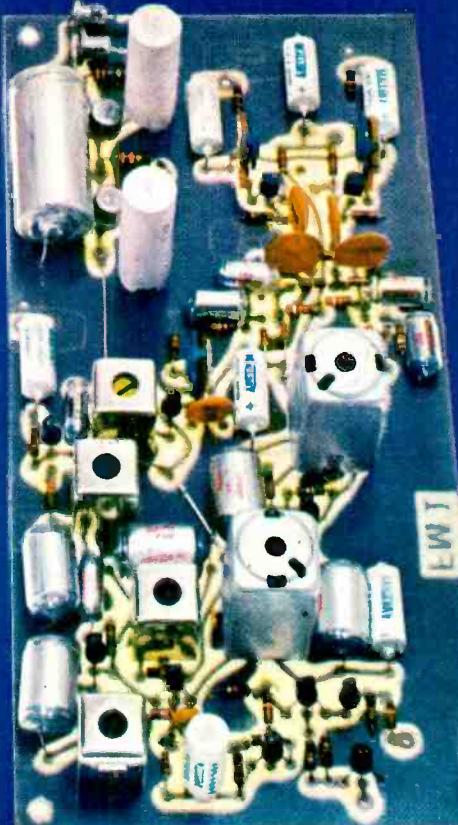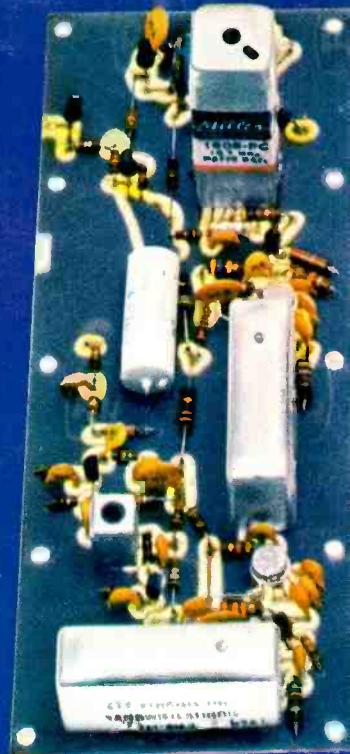BUILD ONE OF THESE
Electronic flash tester
Pulsed darkroom timer
Horizontal efficiency tester



A GERNSEY
PUBLICATION

Dazzle your friends with lightworks.

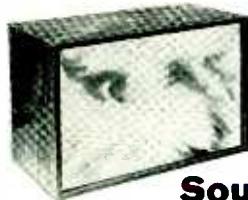

Sound n' Color®

The new dimension to music pleasure. EICO All Electronic Solid-State Audio-Color Organs transform sound waves into moving synchronized color images. Connect easily to speaker leads of hi-fi or radio. From \$29.95.



Translators

The electronics you need to create audio-stimulated light displays to your own imagination. Actuates: Light Display Units, Strobe Lites, any lamp configuration (Xmas trees, patio lights, etc.). From \$24.95 kit, \$39.95 wired.




Strobe Lites

High-intensity bursts of white light from Xenon tube flash in cadence with each beat of audio. From \$24.95 kit, \$39.95 wired.

Build the Stereo Kits praised by experts.

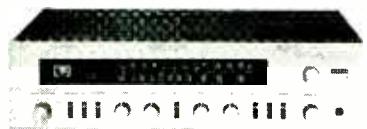All amplifier power ratings according to IHF standards. Cortina® designed and manufactured in U.S.A. and guaranteed by EICO.



70-Watt AM/FM Stereo Receiver including cabinet. Cortina 3770, \$189.95 kit, \$279.95 wired.

70-Watt FM Stereo Receiver including cabinet. Cortina 3570, \$169.95 kit, \$259.95 wired.



150-Watt Silicon Solid-State Stereo Amplifier, including cabinet. For the audio perfectionist. Cortina 3150, \$149.95 kit, \$225 wired.

70-Watt Silicon Solid-State Stereo Amplifier, including cabinet. Cortina 3070, \$99.95 kit, \$139.95 wired.



FM Stereo Tuner including cabinet. Cortina 3200, \$99.95 kit, \$139.95 wired.



EC-1100
FM WIRELESS MIKE \$9.95


Build for fun and use with Eicocraft jiffy project kits.

The newest excitement in kits. 100% solid-state and professional. Expandable, interconnectable. Excellent as introductions to electronics. No technical experience needed. Finest parts, pre-drilled etched printed circuit boards, step-by-step instructions. 36 kits to select from, \$2.50 to \$9.95. Just released: EC-2600 "Super Snoop" \$8.95; EC-2700 Police & Fire Converter



(lo band) \$7.95; EC-2800 Aircraft Converter \$7.95; EC-2900 Police & Fire Converter (hi band) \$7.95; EC-3100 2-Station Intercom (with cases) \$10.95; EC-3200 "Do-It-Yourself" PC Etching Kit \$4.95; EC-2300 Audio Preamplifier \$8.95; EC-2400 Bullhorn \$8.95; EC-2500 Fuzzbox \$8.95.

EC-1900 TREASURE FINDER \$9.95

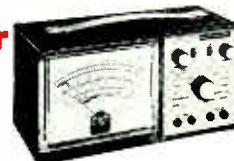


Shape up your own car/boat with EICO Engine Analyzer

For all 6V/12V systems; 4, 6, 8-cyl. engines. Now you can keep your car or boat engine in tip-top shape with this solid-state, portable, self-powered universal engine analyzer.

Completely tests your total ignition/electrical system. Complete with comprehensive Tune-up & Trouble-shooting Manual. EICO 888, \$49.95 kit, \$69.95 wired.

The first and only solid-state test equipment guaranteed for 5 years.

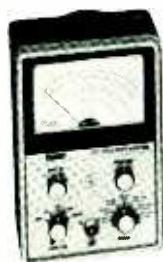
Only EICO brings you laboratory precision and long life at lowest cost.




EICO 240 Solid-State
FET-TVOM
\$59.95 kit; \$79.95 wired



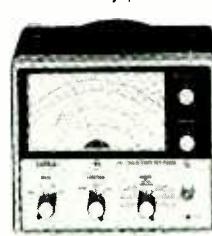EICO 379 Solid-State
Sine/Square Wave Generator
\$69.95 kit, \$94.50 wired



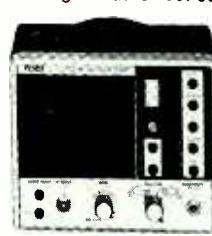EICO 242 Solid-State
Deluxe FET-TVOM
\$69.95 kit, \$94.50 wired



EICO 150 Solid-State
Signal Tracer
\$49.95 kit, \$69.95 wired



EICO 330 Solid-State
RF Signal Generator
\$59.95 kit, \$34.50 wired

You save up to 50% with EICO Kits. Since 1945. Best Buys in Electronics. Over 3 Million EICO Instruments Now in Use.

FREE 1970 CATALOG

Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer.



EICO Electronic Instrument Co., Inc.
283 Malta Street, Brooklyn, N.Y. 11207
Available In Canada

Name _____

Address _____

City _____ State _____ Zip _____

GRANTHAM GRADUATES STEP UP!



High School Diploma
and
Experience in Electronics



First Class FCC License
and
Radar Endorsement

Try thinking of the School as an escalator. Because in a way, that's what it is! The home-study* Associate Degree Program elevates you from electronics technician to associate engineer. *In one easy step?* No. Is anything worth accomplishing ever easy? GRANTHAM would like to see you reach the top, but the School also would like to see you remain at the top without faltering. The only way that you may accomplish *this* is by learning to really understand electronics.

By the time that you've completed approximately a third of the Associate Degree Program, you should be more than capable of passing the FCC Examinations for your *first class radiotelephone license and radar endorsement*. You'll have progressed beyond that level. But don't get the idea that this is

a crash course. GRANTHAM doesn't teach you simple gimmicks that are designed just to *get you by*.

When the Degree of Associate in Science in Electronics Engineering is conferred upon you, it will be because you've *earned* it. You'll have a knowledge and understanding of electronics that won't fail you. You'll know *what* you're doing, and *why* you're doing it. And what's more — your associates will know that you know what you're doing. You'll be proud to say that you're a GRANTHAM man. The pride that the School takes in its graduates is reflected in this simple statement: GRANTHAM graduates are men who have learned to step up!

If you're an electronics technician who has an earnest desire to become an electronics engineer, then you must realize that you'll need more education. But that realization, although it's im-

ACCREDITATION

GRANTHAM School of Engineering is accredited by the Accrediting Commission of the National Home Study Council, and is authorized under the laws of the State of California to grant academic degrees.

GRANTHAM SCHOOL OF ENGINEERING
"the college that comes to you"
1505 N. Western Av., Hollywood, CA 90027

Telephone:
(213) 469-7878



ASEE
DEGREE

portant, will get you nowhere unless you're really prepared to do something about it.

The first step that you take in that direction is more important than merely thinking about it. However, it's a very simple step. Just fill out the coupon at the bottom of this page, and mail it back to GRANTHAM. You'll receive a free bulletin which explains this unique home-study program in detail. Most of the questions that you may want answered about the School — *are answered* in the bulletin. You needn't worry about a salesman calling on you — none will.

Should you decide to enroll with the School, and your enrollment application is accepted, then you'll have taken a first step toward reaching the top in electronics. From that point on, GRANTHAM will work with you toward the fulfillment of your ambition — earning your degree in engineering!

G. I. BILL

The Associate Degree Program is approved for servicemen and veterans under the G. I. Bill.

*As a final requirement for the Degree of Associate in Science in Electronics Engineering, you must go to the School in Hollywood for two weeks of review and examination.

Grantham School of Engineering

RE-5-70
1505 N. Western Ave., Hollywood, Cal. 90027

Gentlemen:

Please mail me your free Bulletin which explains how the Grantham educational program can prepare me for my FCC license and Associate Degree in Electronics Engineering. I understand no salesman or counselor will call.

Name _____

Address _____

City _____ State _____ Zip _____

Circle 9 on reader service card

← Circle 8 on reader service card

NEW & TIMELY

Volume 41 Number 5

RADIO-ELECTRONICS

May 1970

ON THE ROAD: RADAR BRAKING, ELECTRONIC SHIFT

IC- and radar-controlled shifting and braking units for cars are in the news.

An automatic braking system may appear next year in trucks, buses and cars that uses an Impatt-diode microwave oscillator to beam a 10.525-GHz signal at obstacles on the road. The radar signal can be beamed from a horn antenna concealed near a headlight; another antenna near the other headlight receives reflections. A phase-sensitive detector senses Doppler frequency shift, feeding the signal eventually to accelerator and braking controls. Manufactured by Bentley Associates of Chelmsford, Mass., the units will cost \$800.

In Japan, an electronically controlled automatic transmission is being included in Toyota's Corona models. The electronic computer used in the car replaces almost 50% of the hydraulic parts needed in regular automatic transmissions with 12 hybrid and monolithic IC's. The electronic controls enable the shift range in second gear to be varied for conventional or sport-type driving. Cost is about \$60 over conventional automatic.


UHF FOR 'GHOSTS'

NEW YORK—When the twin 110-story towers of the World Trade Center rise above lower Manhattan in 1973, TV transmitters located in the Empire State Building will be moved to the trade center. Meanwhile, to prepare for possible ghosts from the partially completed towers, TV stations here are planning to operate secondary uhf transmitters to cover a pie-shaped wedge North of the city.

LOOKING AHEAD

In this issue the regular feature column by David Lachenbruch is on page 4.

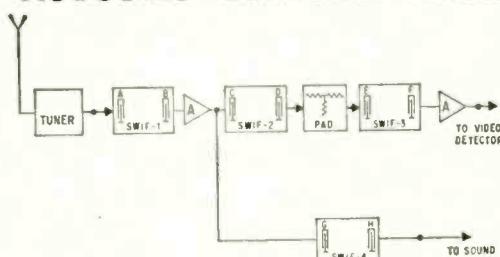ACOUSTIC SURFACE WAVE FILTERS FOR COLOR TV



Three SWIF combs are combined into single unit shown in photo. Center comb, with about 20 fingers, serves as transmitter; two outer combs are series or parallel connected. Diagram above is of SWIF i.f. unit formed on a 2 x 1-inch substrate with IC amplifiers.



CHICAGO—Transistors for tubes, IC's for discrete transistors, varactor and computer diodes for mechanical tuners . . . what's next on the replacement list in TV receivers? Zenith has their sights on the bulky, drift-prone LC filters needed for the i.f.

The exotic fixed-bandpass replacements are called SWIFs (Surface Wave Integrable Filters) by their developer, and are made with lead zirconate, a piezoelectric ceramic. The rf input to one


comb on an interdigital transducer pair (see drawing) exerts stress near the substrate. The transmitter comb propagates acoustic surface waves to the receiver comb, which detects electric fields generated by the waves. Spacing between comb fingers determines bandpass frequency.

To obtain the 40-MHz bandpass response for color TV, Zenith can cascade four SWIFs on a 2 x 1-inch thick-film substrate, along with IC amplifiers to boost losses

between SWIFs. One of the devices substituted for a standard i.f. produced a good color picture.

In the experimental SWIF, section 1 provides out-of-band rejection and attenuates the sound carrier; filters 2 and 3 provide a notch at 41.25 MHz, and with section 1, the proper bandpass with a notch at 47.25 MHz. Section 4, with part 1, provides the correct level between sound and picture carriers. The SWIFs are still under development.

COMPOSITE TRANSISTORS

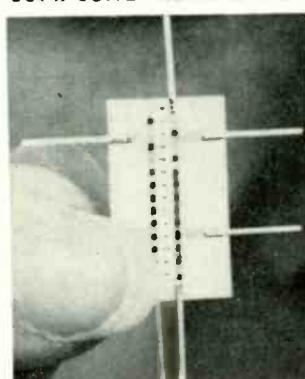

MURRAY HILL, N.J.—By combining a score of tiny transistor chips into a single power transistor, Bell Labs has greatly boosted the amount of information it can handle in comparison with other 17-watt devices.

A new technique used for the experimental transistors eliminates emitter circuit parasitic inductance, which has limited the power output/gain-bandwidth combination from power transistors. The devices have produced linear power gains of 15 dB from dc to 500 MHz with 60-70% efficiencies.

CBS OFFERS STATIONS NEW COLOR CORRECTOR

NEW YORK—If CBS Television network performers have been less colorful in recent months, it's the fault of CBS Labs. R. H. McManus, Jr. of CBS Labs developed a color corrector that keeps color variations between live, film and videotape programs to a minimum.

The network has been using a computer-regulated prototype, and a \$3000 version was made available to individual stations last month by CBS Labs.

Engineers can now adjust color variations after encoding or at any point during transmission. Color differences can be balanced by adjusting all three primary colors instead of one, which might upset the balance.

The source signal is split into two parts, and a correction vector added to the red, blue and green signals in one decoded signal. After remodulation, the combined signals produce an error voltage which is summed with the original signal to cancel the error. ■


(N & T continued on page 6)

Radio-Electronics

May 1970 • Over 60 Years of Electronics Publishing

ELECTRONICS IN PHOTOGRAPHY

Photographic Electronics—'70	41	John R. Free
Automatic focusing with infrared light		
Half-Hour Darkroom Timer	57	Frank Tooker
FET circuit provides long-interval timing		
Electronic Flash Tester	66	W. G. Eslick

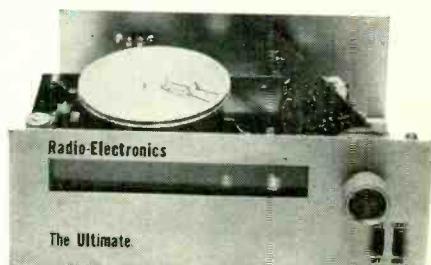

Radio-Electronics

The Ultimate.

Stereo FM tuner you'll be proud to own. Unbeatable performance . . . use the three PC patterns and instructions.


. . . see page 36

BUILD THIS ONE

'The Ultimate' Stereo FM Tuner	36	Kenneth E. Buegel
State-of-the-art performance		

TELEVISION

In The Shop	24	Jack Darr
Divide up for efficiency		
Kwik-Fix™ Troubleshooting Charts	53	Forest H. Belt
Transistor-keyed agc		
Horizontal Efficiency Tester	67	Homer L. Davidson
Meter readout saves your eyes		
Service Clinic	84	Jack Darr

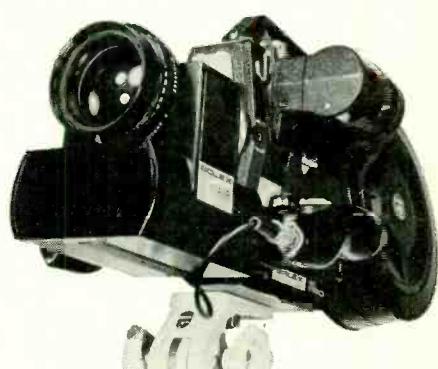


Sophisticated electro-optical system added to this movie camera uses modulated light beam to focus it.

. . . see page 41

GENERAL ELECTRONICS

Looking Ahead	4	David Lachenbruch
Current happenings with future overtones		
Equipment Report	26	Jack Darr
Hickok Digital Instrument System		
Emitter-Coupled Oscillators	33	Ken Maynard
Practical experiments with E-C circuits		
Easy-Build Computer Logic Circuits	44	Matthew Mandl
Get to know the basic logic circuits		
All About Tools	48	Thomas R. Haskett
Soldering equipment (conclusion) and nutdrivers		
Technical Topics	59	Robert F. Scott
FM with a swept i.f. circuit		

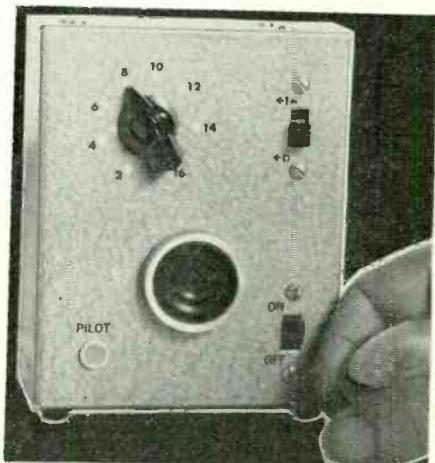

Half-hour interval timer can be used in the darkroom for accurate exposures—or anywhere in the house.

. . . see page 57

DEPARTMENTS

Coming Next Month	89	New Literature	79
Correspondence	16	New Products	75
New & Timely	2		

Reader Service	73
Technotes	88
Try This One	90

RADIO-ELECTRONICS, MAY 1970, Vol. 41, No. 5
Editorial, Advertising, and Executive offices: 200 Park Ave. S., New York, N.Y. 10003. Subscription Service: Boulder, Colo. 80302.
Second-class postage paid at Concord, N.H. Printed in U.S.A. One-year subscription rate: U.S. and possessions, Canada, \$6.
Pan-American countries, \$7. Other countries, \$7.50. Single copies 60¢. © 1970 by Gernsback Publications, Inc. All rights reserved.
POSTMASTER: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302.



Radio-Electronics is indexed in
Applied Science & Technology Index (formerly *Industrial Arts Index*)

LOOKING AHEAD

Volume 41 Number 5

RADIO-ELECTRONICS

May 1970

by DAVID LACHENBRUCH
CONTRIBUTING EDITOR

Standardizing VTR's

Standards adopted in Japan for video tape recorders using $\frac{1}{2}$ -inch tape may become worldwide standards—mainly because hardly any country outside Japan produces any quantity of $\frac{1}{2}$ -inch vtr's, and certainly no other country has given any thought to standardizing.

At the time the standards were adopted in Japan last August, no two makes of machine had compatibility or tape interchangeability. Now Sony, by far the biggest manufacturer of $\frac{1}{2}$ -inch vtr's, has announced that all of its new models will be "standard," giving virtual assurance that all future Japanese recorders will meet the same specifications. Earlier, Matsushita (Panasonic) had announced "standard" machines, and versions were understood to have been designed by seven other manufacturers—General, Hitachi, Mitsubishi, Sanyo, Sharp, Toshiba and Japan Victor.



Compact vtr by Panasonic uses standard $\frac{1}{2}$ -inch tape, and can record NTSC color. Automatic-control circuit corrects phase and frequency fluctuations. It will be available this year.

Highlights of the Japanese specs: (1) Full-field, 2-head, diagonal-scan video recording (FM); single-track fixed-head audio recording. (2) 7.5-ips tape speed. (3) Maximum recording time of more than 60 minutes on 7-inch reels. (4) Video frequency bandwidth of 2.5 MHz. (5) Video signal-to-noise ratio of more than 40 dB. (6) Cylinder diameter of 115.92 mm. (7) Video pitch of 173 microns. (8) Video track angle of 311° . (9) Control track width at 0.8 mm. (10) Audio track at 1 mm.

TV sets and fires

Completing its investigation of fire and smoke incidents in television receivers, the National Commission on Product Safety issued a widely publicized (and widely assailed) report on 13 TV manufacturers and their "problem" models which attempted to "rate" brands and models for fire safety on the basis of information submitted by the manufacturers themselves. There were immediate charges that manufacturers were penalized for their cooperation, and that those set makers with the best record-keeping procedures (particularly those with their own service companies) were charged with the greatest incidence of fires.

On the basis of records said to cover nearly 22 million color sets produced from 1965 through 1969, the Commission found that reported fire and smoke incidents worked out to 120 cases per million sets. It also determined that the large majority of identified part failures connected with these incidents involved transformers (mostly flybacks). Other parts responsible, to a considerably lesser degree, in diminishing order of importance—

high-voltage components, yoke, ac switch.

The Commission requested that set makers undertake a nationwide inspection and free parts replacement campaign covering so-called "problem models"—those models involved in two or more reported fire or smoke incidents. Some manufacturers—notably RCA and Olympic—announced immediate programs to locate, inspect and repair, if necessary, all cited models. Others, including Magnavox and Sears Roebuck, said they had already located and repaired most or all sets with potentially defective components.

The Commission's report concentrated on color sets because its study showed that they were 40 times more likely to have fire or smoke problems than black-and-white sets. Arithmetically, this would indicate only three fire or smoke incidents per million monochrome sets (based on the Commission's figures of 120 incidents per million color sets).

'Comparable' vhf-uhf tuning

Television set manufacturers were completely unprepared when the FCC issued its ruling requiring that uhf and vhf tuners in any receiver be mechanically and electronically "comparable." In fact, among set manufacturers there was the virtually unanimous view that the Commission had acted without knowledge of the true facts and that if the order were allowed to stand it would seriously hamper television production.

The controversial rule, adopted on the basis of petitions by uhf broadcasters who felt that tuning difficulties was costing them audiences, provides that all TV sets manufactured or imported into the U.S. after April 30, 1971 must have "comparable" tuning systems. An exception is made for sets with screens smaller than nine inches in diagonal measurement; these must be brought into compliance by May 1, 1973. The FCC made clear what it meant by "comparability": If the vhf tuner has detents to make it click into position, the uhf tuner must have them. If vhf tuning is done by pushbutton, uhf tuning must be accomplished the same way. If an electronic tuning system is used, it must be used on both bands.

The FCC did make a few qualifications. It said that uhf tuners need have only six detent positions or pushbuttons, provided that these can easily be set to any uhf channels by the set owner.

Set makers, who normally plan their new models three or more years in advance, said the target dates just couldn't be met. Some tuners may be available, but there was the feeling that the supply would be nowhere near the number needed. More importantly, the new types of uhf tuners won't fit, physically, the majority of cabinets already designed, requiring complete redesign and retooling. And even if target dates could be met, manufacturers were worried about the hefty cost increases involved—some put the retail price hike at \$12 to \$25 to cover the added costs of new tuners.

Though basically happy with the rule, some uhf broadcasters felt it didn't go far enough. They objected to the FCC's willingness to accept six uhf detents or pushbuttons as "comparable" when, in fact, some areas can receive more than six uhf channels. Some felt that 12 uhf positions would be truly comparable with a 12-position vhf tuner.

895
COMPLETE

WE'VE MOVED
IN THE EAST*

130-01 89th. Road., JAMAICA, N.Y. 11418

Castle, the pioneer of television tuner overhauling, offers the following services to solve ALL your television tuner problems.

● **OVERHAUL SERVICE** — All makes and models.
(1960, or later)

VHF or UHF tuner	\$9.95
UHF-VHF combination (one piece chassis)	\$9.95
TRANSISTOR tuner	\$9.95
COLOR tuner (Guaranteed color alignment . . . no additional charge)	\$9.95

Overhaul includes parts, except tubes and transistors.

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

Remove all accessories . . . or dismantling charge will apply.

● **CUSTOM REPLACEMENTS**

Exact replacements are available for tuners that our inspection reveals are unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

● **UNIVERSAL REPLACEMENTS**

Prefer to do it yourself?

Castle universal replacement tuners are available with the following specifications.

STOCK No.	HEATERS	SHAFT		I.F. OUTPUT		PRICE
		Min.*	Max.*	Snd.	Pic.	
CR6P	Parallel 6.3v	1 3/4"	3"	41.25	45.75	8.95
CR7S	Series 600mA	1 3/4"	3"	41.25	45.75	9.50
CR9S	Series 450mA	1 3/4"	3"	41.25	45.75	9.50
CR6XL	Parallel 6.3v	2 1/2"	12"	41.25	45.75	10.45
CR7XL	Series 600mA	2 1/2"	12"	41.25	45.75	11.00
CR9XL	Series 450mA	2 1/2"	12"	41.25	45.75	11.00

* Selector shaft length measured from tuner front apron to extreme tip of shaft.

These Castle replacement tuners are all equipped with memory fine tuning, UHF position with plug input for UHF tuner, rear shaft extension and switch for remote control motor drive . . . they come complete with hardware and component kit to adapt for use in thousands of popular TV receivers.

Order universal replacements out of Main Plant (Chicago) only.

CASTLE TV TUNER SERVICE, INC.

MAIN PLANT: 5715 N. Western Ave., Chicago, Illinois 60645

* EAST: 130-01 89th Rd., Jamaica, N.Y. 11418

Circle 10 on reader service card



New & Timely


BELL SETS TRIALS FOR WAVEGUIDE TUBES



Test "word" similar to PCM pulses to be beamed at high frequencies through waveguides is displayed on oscilloscope.

MURRAY HILL, N.J.—By the late 1970's, your telephone conversation may be beamed at 40-110 GHz through 2-inch circular waveguides throughout the country. 1974 field trials for northern New Jersey are being planned by Bell Labs.

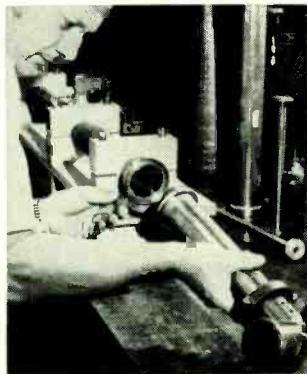One of the wrist-size copper waveguides is capable of carrying a quarter of a million telephone conversations. Bell will use PCM (pulse code modulation) since it is relatively unaffected by energy-mode variations that would be produced from slight bends in the copper tubes. PCM would cause only one error per billion pulses from one repeater to the next, and conversations



A length of copper-lined steel pipe is readied for tests at Bell Labs. When buried, conduit protects pipe.

and data transmission could be easily mixed with Picture-phone service.

Devices such as Impatt diodes, which generate millimeter waves (between microwaves and infrared in frequency), will be used as transmission sources, according to Bell.

At 20-mile intervals, repeater filters will divide the mm waves into 120 component channels, which will deliver 282 million-pulse-per-second streams to separate repeaters. After amplification and regeneration, the pulse streams will be recombined by additional filters and beamed the next repeater station along the pipe line.

RCA TO ORGANIZE NEW SERVICE CHAIN

NEW YORK—RCA is establishing a new servicing company, independent from the RCA Service Co., to repair all makes of TV sets and home-entertainment products. The first centers will open in Philadelphia and San Francisco by October.

The subsidiary is being established, according to an RCA executive, because of "an expanding need for service in the entire consumer products industry."

TV REPAIR BILL CALLS FOR BONDING

ALBANY, N.Y.—A bill that would require licensing of television repairmen has been introduced in the state legislature.

New York City, meanwhile, is preparing a similar bill with additional requirements. Repairers would be required to post \$2500 bonds to guarantee payment of customer judgments against them. Technician license fees would be \$25 annually, and dealers would be required to have at least one licensed technician unless the dealer was licensed.

The city bill would cover some 1100 TV, radio and phonograph repair shops.



International wiring: Engineers from British Aircraft Corp. help prepare a test panel rack, part of a complete system of test equipment, that will check out the Intelsat 4 series of communications satellites. BAC is one of 12 foreign firms participating with Hughes Aircraft Co., builder of the satellites, under a \$72 million contract from Comsat Corp. as agent for the 68-nation Intelsat organization. The test center, one of three to be built, is used to test satellites at the California factory, then shipped to Cape Kennedy to again test the satellites.

(N & T continued on page 12)

IN THIS ISSUE

"The Ultimate" stereo FM tuner described on page 36 has crystal filters and IC's in its i.f. section for a clean, steep-skirted bandpass. The rf front end uses forward-agc transistors for excellent performance on weak signals.

Radio-Electronics

HUGO GERNSBACK (1884-1967)
founder

M. HARVEY GERNSBACK,
editor and publisher

LARRY STECKLER, managing editor

Robert F. Scott, W2PWG
senior technical editor

John R. Free, associate editor

Jack Darr, service editor

I. Queen, editorial associate

Matthew Mandl, contributing editor

David Lachenbruch, contributing editor

Frances McDowell, editorial assistant

Vincent P. Cicenia, production manager

Barbara Rosefelt, production assistant

H. Matysko, circulation

Cover by Harry Schlack

RADIO-ELECTRONICS is published by Gernsback Publications, Inc.
200 Park Ave. South
New York, N.Y. 10003
(212) 777-6400

President: M. Harvey Gernsback
Secretary: Bertina Baer

ADVERTISING SALES

EAST
John J. Lamson, Eastern Sales Mgr.
N.Y.C. (212) 777-6400

MIDWEST

Ralph Bergen,
6319 N. Central Ave.
Chicago, Ill. 60646
(312) 792-3646

W. COAST/Texas/Arkansas/Okl.
J. E. Publishers Representative Co.,
8560 Sunset Blvd., Suite 601
Los Angeles, Calif. 90069
(213) 659-3810

420 Market St. San Francisco, Calif.
94111, (415) 981-4527

SOUTHEAST

E. Lucian Nefi Associates
25 Castle Harbor Isle
Fort Lauderdale, Florida 33308
(305) 566-5656

SUBSCRIPTION SERVICE: Send all subscription orders and correspondence to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302.

MOVING? For change of address, allow six weeks, furnishing both the old and new addresses and if possible attaching label from a recent issue below. Otherwise please print clearly your name and address exactly as it appears on your label.

ATTACH LABEL HERE

name _____ (please print)

address _____

city _____ state _____ zip code _____

Mail to: RADIO-ELECTRONICS
SUBSCRIPTION DEPT., BOULDER, COLO. 80302

RADIO-ELECTRONICS

Special introductory offer to new members of the ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

	A042/500 NUMERICAL CALCULATIONS AND ALGORITHMS by Beckett & Hurt Pub. price, \$10.50 Club price, \$8.95		A494/754 ENGINEERING MANUAL, 2/e by R. H. Perry Pub. price, \$12.50 Club price, \$9.95
	A101/094 MICROELECTRONIC CIRCUITS AND APPLICATIONS by J. M. Carroll Pub. price, \$12.00 Club price, \$10.25		A523/401 CHARACTERISTICS AND OPERATION OF MOS FIELD-EFFECT DEVICES by P. Richman Pub. price, \$10.00 Club price, \$8.50
	A286/507 SOLID-STATE ELECTRONICS by R. G. Hibberd Pub. price, \$9.50 Club price, \$7.95		A037/604 DIGITAL LOGIC AND COMPUTER OPERATIONS by Baron & Piccirilli Pub. price, \$14.50 Club price, \$11.95
	A287/457 SUCCESSFUL ENGINEERING MANAGEMENT by T. G. Hicks Pub. price, \$8.95 Club price, \$7.25		A423/814 PULSE, DIGITAL AND SWITCHING WAVEFORMS by Millman & Taub Pub. price, \$18.00 Club price, \$15.30
	A347/506 ELECTRONIC DIGITAL TECHNIQUES by P. M. Kintner Pub. price, \$12.50 Club price, \$10.65		A565/031 AMPLIFIER HANDBOOK by R. F. Shea Pub. price, \$37.50 Club price, \$29.50

ANY ONE
of these great professional books
for only \$1.00

VALUES FROM \$8.95 to \$37.50

Special \$1.00 bonus book
comes to you with your
first club selection

	A637/377 TRANSISTOR CIRCUIT DESIGN by Texas Instruments, Inc., Staff Pub. price, \$16.50 Club price, \$14.05		A126/070 PRINTED CIRCUITS HANDBOOK by C. F. Coombs, Jr. Pub. price, \$17.75 Club price, \$14.95
	A610/037 MODERN COMMUNICATION PRINCIPLES by Stein & Jones Pub. price, \$15.00 Club price, \$12.75		A259/607 COMMUNICATION SYSTEM ENGINEERING HANDBOOK by D. H. Hamsher Pub. price, \$29.50 Club price, \$24.95

Save time and money by joining the
Electronics and Control Engineers' Book Club

HERE is a professional club designed specifically to meet your day-to-day engineering needs by providing practical books in your field on a regular basis at below publisher prices.

How the Club operates: Basic to the Club's service is its publication, the *Electronics and Control Engineers' Book Club Bulletin*, which brings you news of books in your field. Sent to members without cost, it announces and describes in detail the Club's featured book of the month as well as alternate selections which are available at special members' prices.

When you want to examine the Club's feature of the month, you do nothing. The book will be mailed to you as a regular part of your Club service. If you prefer one of the alternate selections—or if you want no book at all for that month—you notify the Club by returning the convenient card enclosed with each *Bulletin*.

As a Club member, you agree only to the purchase of four books over a two-year period. Considering the many books published annually in your field, there will surely be at least four that you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

MAIL THIS COUPON TODAY

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB
330 West 42nd Street, 18th fl., New York, N. Y. 10036

Please enroll me as a member of the Electronics and Control Engineers' Book Club and send me the two books indicated below. I am to receive the bonus for just \$1.00, and my first selection at the special Club price shown. These books are to be shipped on approval, and I may return them both without cost or further obligation. If I decide to keep the books, I agree to purchase as few as four additional books during the next two years at special Club prices (approximately 15% below list).

Write Code No. of
bonus book
here

Write Code No. of
first selection
here

Name _____


Address _____

City _____

State _____ Zip _____

E33127

Circle 11 on reader service card

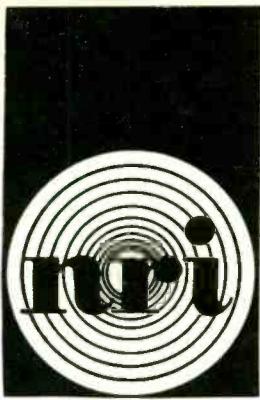

Learning electronics at home is faster, easier, more interesting with new achievement kit


Only NRI offers you this pioneering method of "3 Dimensional" home-study training in Electronics, TV-Radio... a remarkable teaching idea unlike anything you have ever encountered. Founded more than half a century ago—in the days of wireless—NRI pioneered the "learn-by-doing" method of home-study. Today, NRI is the oldest, largest home-study Electronics school. The NRI staff of more than 150 dedicated people has made course material entertaining and easy to grasp. NRI has simplified, organized and dramatized subject matter so that any ambitious man—regardless of his education—can effectively learn the Electronics course of his choice.

DISCOVER THE EXCITEMENT OF NRI TRAINING

Whatever your reason for wanting knowledge of Electronics, you'll find the NRI "3 Dimensional" method makes learning exciting, fast. You build, test, experiment, explore. Investigate NRI training plans, find out about the NRI Achievement Kit. Fill in and mail the postage-free card. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016

GET A FASTER START IN THE COURSE YOU CHOOSE WITH NRI'S REMARKABLE ACHIEVEMENT KIT

When you enroll with NRI we deliver to your door everything you need to make a significant start in the Electronics field of your choice. This remarkable, new starter kit is worth many times the small down payment required to start your training. And it is only the start... only the first example of NRI's unique ability to apply 50 years of home-study experience to the challenges of this Electronics Age. Start your training this exciting, rewarding way. No other school has anything like it. What do you get? The NRI Achievement Kit includes: your first set of easy-to-understand "bite-size" texts; a rich, vinyl desk folder to hold your training material in orderly fashion; the valuable NRI Radio-TV Electronics Dictionary; important reference texts; classroom tools like pencils, a ball-point pen, an engineer's ruler; special printed sheets for your lesson answers—even a supply of pre-addressed envelopes and your first postage stamp.

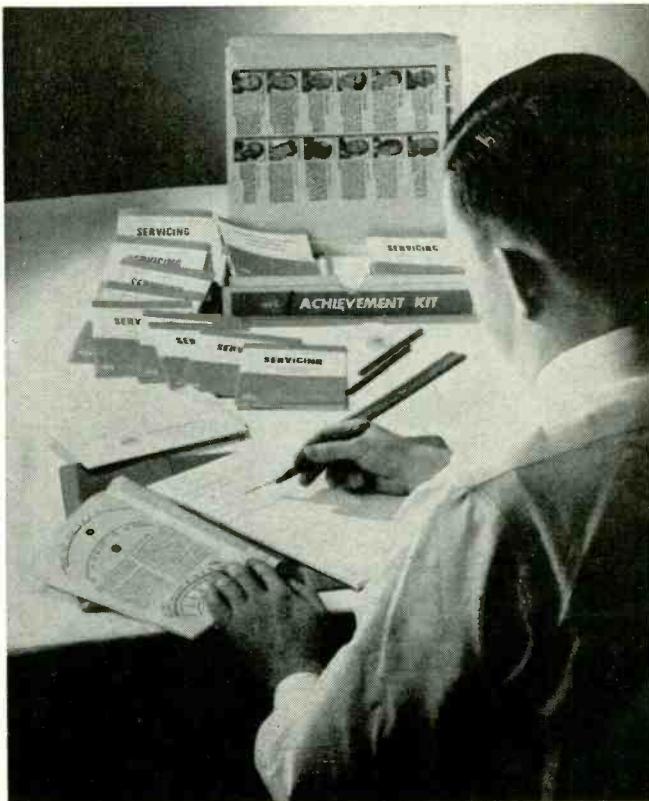

ELECTRONICS COMES ALIVE AS YOU LEARN BY DOING WITH CUSTOM TRAINING EQUIPMENT

Nothing is as effective as learning by doing. That's why NRI puts so much emphasis on equipment, and why NRI invites comparison with equipment offered by any other school, at any price. NRI pioneered and perfected the use of special training kits to aid learning at home. You get your hands on actual parts like resistors, capacitors, tubes, condensers, wire, transistors and diodes. You build, experiment, explore, discover. You start right out building your own professional vacuum tube voltmeter with which you learn to measure voltage and current. You learn how to mount and solder parts, how to read schematic diagrams. Then, you progress to other experimental equipment until you ultimately build a TV set, an actual transmitter or a functioning computer unit (depending on the course you select). It's the practical, easy way to learn at home—the priceless "third dimension" in NRI's exclusive Electronic TV-Radio training method.



SIMPLIFIED, WELL-ILLUSTRATED "BITE-SIZE" LESSON TEXTS PROGRAM YOUR TRAINING

Lesson texts are a necessary part of training, but only a part. NRI's "bite-size" texts are as simplified, direct and well-illustrated as half a century of teaching experience can make them. The amount of material in each text, the length and design, is precisely right for home-study. NRI texts are programmed with NRI training kits to make things you read come alive. As you learn, you'll experience all the excitement of original discovery. Texts and equipment vary with the course. Choose from major training programs in TV-Radio Servicing, Industrial Electronics and Complete Communications. Or select one of seven special courses to meet specific needs. Check the courses of most interest to you on the postage-free card and mail it today for your free catalog.

Available Under **NEW GI BILL**

If you served since January 31, 1955, or are in service, check GI line in postage-free card.

custom training kits "bite-size" texts

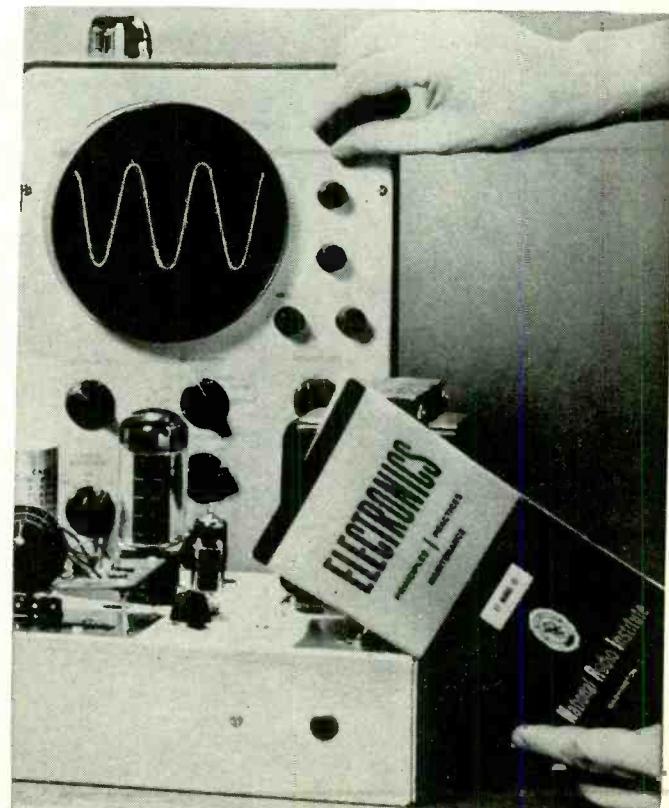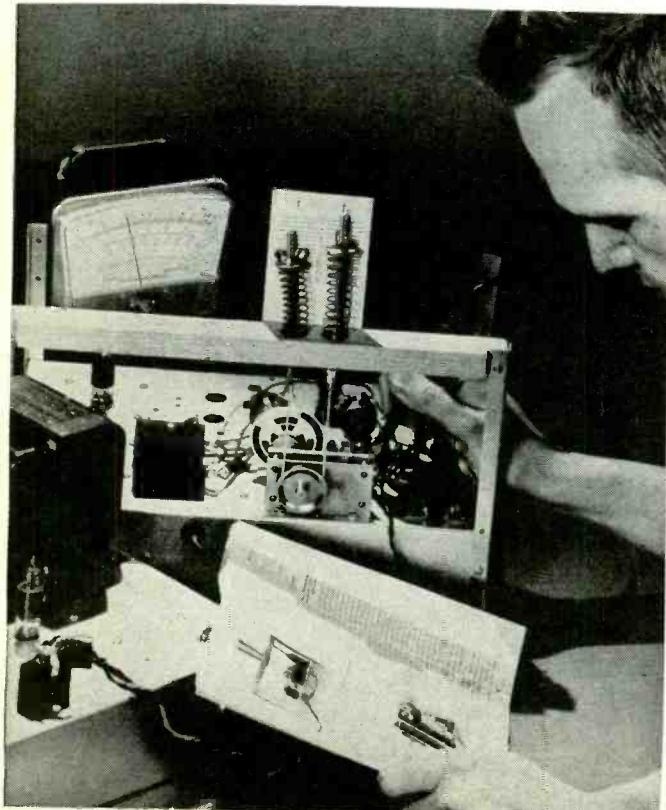

(continued from page 6)



Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this

Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?



Available through your local distributor, or write to:

RYE INDUSTRIES INC.
130 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.
Circle 12 on reader service card

\$147

POLICE CARS LINKED TO COMPUTER CENTER



SAN FRANCISCO—Twenty police patrol cars here have been linked to a computer through data transmission techniques. In addition, a computerized dispatcher communication system is now undergoing tests.

A command and control unit (above) displays the location and priority of incidents, also showing the status of patrol cars in the area. Magnetic tape stores all events for later analysis.


An important feature of the mobile transmission equipment will be "unjamming" crowded police frequencies. The car units can handle 100 data transmissions in the time required for one voice transmission.

button on his radio lets an officer instantly request assistance or an ambulance, for example.

Requests for license veri-



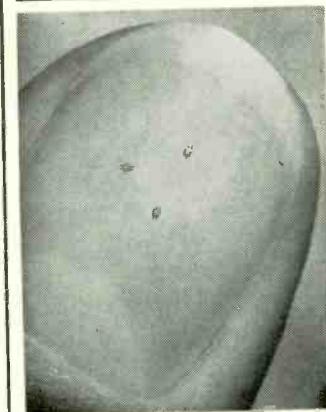fication can be cranked into a control panel (photo) and digitally transmitted by pressing the transmit button. A central computer can instantly acknowledge the signal on an illuminated dashboard display. The system is built by Sylvania.



Microminiature package made by Western Electric for Bell telephones contains four diodes for controlling the volume of signals for Touch-Tone calling. The 4-pin devices are part of an IC used in new tone generators, and replace larger diodes.

It's yours free

for the asking!

1970 FULL LINE ANNUAL RADIO-TV ELECTRONICS CATALOG

GIANT 274 PAGE 1970 RADIO-TV ELECTRONICS CATALOG

YOUR BUYING GUIDE FOR . . .

TV's, Radios, Recorders, Phonos, Amateur and CB equipment, electronic parts, tubes and test equipment . . . featuring B-A's famous big bargain packed section!

Write to:

BURSTEIN-APPLEBEE CO., DEPT. RE-5 3199 MERCIER ST., KANSAS CITY, MO. 64111

Name _____

Address _____

City _____

State _____ Zip Code _____

Circle 13 on reader service card

NEXT MONTH

If you've been worried about burglars, don't miss R-E's "radar" intruder alarm in June. The device will protect your home or shop.

Also coming is a detailed look at careers in aviation electronics.

Triacs are being used widely these days. Learn how they work next month.

The big difference in TV Alignment instruments: Ours Works.

The B & K Model 415 Sweep/Marker Generator not only works, but it makes alignment jobs faster and more accurate.

Why? Because it eliminates the need for a separate marker generator, sweep generator, marker adder, and bias supply. You get it all in one compact instrument.

And it's so easy to use. The IF and chroma bandpasses are simulated on the front panel for constant reference. Lights tell you which of the crystal-controlled markers are in use and where they should be located. And the exclusive marker tilt feature lets you place the markers either horizontally or vertically, so you can always identify their exact positions.

Put the B & K Model 415 Sweep/Marker Generator to work for you.

Ask your distributor for complete details.




Product of
DYNASCAN CORPORATION
1801 W. Belle Plaine
Chicago, Illinois 60613



Model 415:
\$399.95

Circle 14 on reader service card

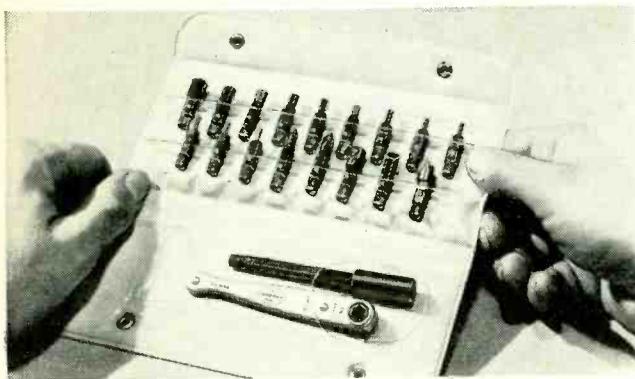Here's A Little Item That Will Get You Out Of Many A Tight Spot



HANDLE ONLY 3 3/4" LONG—
18 Degree Working Arc.

Stainless steel Midget Ratchet handle, 17 Drivers, 3 3/8" extension, two slotted and two Phillips bits, 12 hexagonal bits from 0.050 to 5/16", one square adapter for 1/4" wrench sockets—all in pocket-sized vinyl case.

You may purchase from your local Supply-House or direct from


THE CHAPMAN MANUFACTURING CO.

Manufacturers of Midget Ratchet Offset Screwdrivers for over 25 years.

30 Saw Mill Road, Durham, Conn. 06422

Circle 15 on reader service card

Kit #4320
complete \$10.00

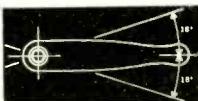

New Products From THE PHASE CORPORATION

TEST OSCILLATOR

\$34.95

THREE FUNCTIONS IN ONE SMALL PACKAGE
GENERATES PULSE, SAWTOOTH, AND SQUARE



Test your Audio Circuits

FET and
Unijunction Circuitry
All Solid-State

Trigger your
Logic Circuits
Overlapping Ranges
Portable and Compact

Specifications:


Frequency: Saw and Pulse	0.1 HZ—100 KHZ	Model O1K (kit with custom case) \$34.95
Square	0.05 HZ—50 KHZ	
Rise Time Square and Pulse	0.5 μ Sec.	Model O1W (wired and tested) \$54.95

FOUR TRACE PRE-AMP

\$34.95

CONVERTS ANY SINGLE TRACE SCOPE TO
DISPLAY UP TO FOUR SIGNALS AT THE SAME TIME

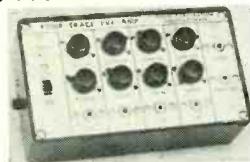Use as Dual Trace,
Three Trace, or
Four Trace
All Solid-State
Sync. Output



Uses Time Sharing Techniques

Transition Time: 5 μSec.
Input Impedance/Channel: 1 meg. ohm

Model A1KC (kit with custom case)	\$34.95
Model A1W (wired and tested)	\$54.95

Specifications:
Bandwidth: 1 megahertz/channel
Maximum Input Volts per Channel:
50 Volts p-p
Maximum Output Volts per Channel:
0.5 Volts p-p
Display Time: 50 μSec.

SEND CHECK, MONEY ORDER OR ASK US TO BILL YOUR
BANKAMERICARD OR MASTER CHARGE


We Pay Postage to USA Destinations • Dealer Inquiries Invited

THE PHASE CORPORATION, Dept. 37
ELECTRONICS DIVISION, MEDFORD, MASS. 02155

Circle 16 on reader service card

New & Timely

WILL DOLBY + CASSETTES = HI-FI?

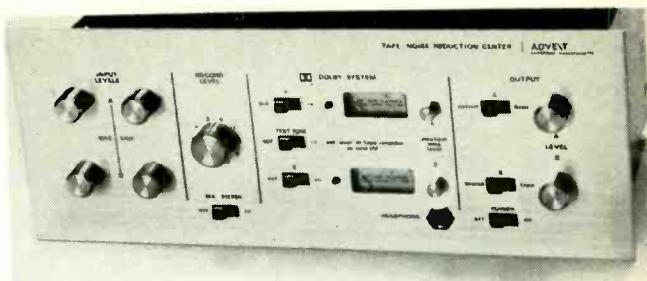

NEW YORK—A demonstration of a simplified version of the Dolby noise reduction system here indicates the audio quality of cassettes can approach that of records.

The noise-reduction unit, made by Advent Corp., was demonstrated as a separate unit (photo) for use with any open-reel, cartridge or cassette recorder, and in a cassette deck. The Dolbyized cassette machine will be available soon for \$250 and the separate tape unit is already on the market at the same price.

Both units use the "B-type" noise-reduction circuitry from the four-band professional system. The consumer version has a range from about 2 kHz upward, and pro-

vides a 10-dB noise reduction above about 4 kHz.

The Dolby system does not reduce noise already in the source material. Instead it boosts low-level signals above the background tape hiss level and compresses the recorded signal during playback. This returns the signal to its original level, pushing tape hiss down at the same time.

In addition to input- and master-level controls, the tape-center unit has calibration facilities to optimize the system to recorders, a test-tone oscillator and multiplex filter switch.

The Dolby units do not work with prerecorded tapes, currently on the market.

MODULE EXCHANGE



CONSUMER DOLBY— HOW DOES IT SOUND?

Advent conducted a series of A-B tests with and without Dolby. The basic cassette player used was a Wollensak. The only modification to the tape player was a readjustment of the bias for chromium dioxide tape (bias was turned up about 25% higher than in the original unit).

Sampler tape that came with the machine produced pronounced hiss. Dolby in—hiss almost completely gone.

High-density tape (Bell & Howell UHD and TDK) had lower hiss than standard tape. With Dolby hiss was absent.

Chromium dioxide tape had lower hiss to start. With Dolby in, no audible hiss remained.


Opinion? Dolby can take the hiss out of low tape speeds. Fidelity is another matter.

Plug-in modules in new H. H. Scott gear can be exchanged for \$10 if they become defective. Scott's regular parts & labor 2-year warranty remains in effect. Regular module cost is \$30-\$50.

Regular cost of the 342C's quartz crystal FM i.f. amplifier, for example, is now listed at \$48.88.

R-E

RADIO-ELECTRONICS

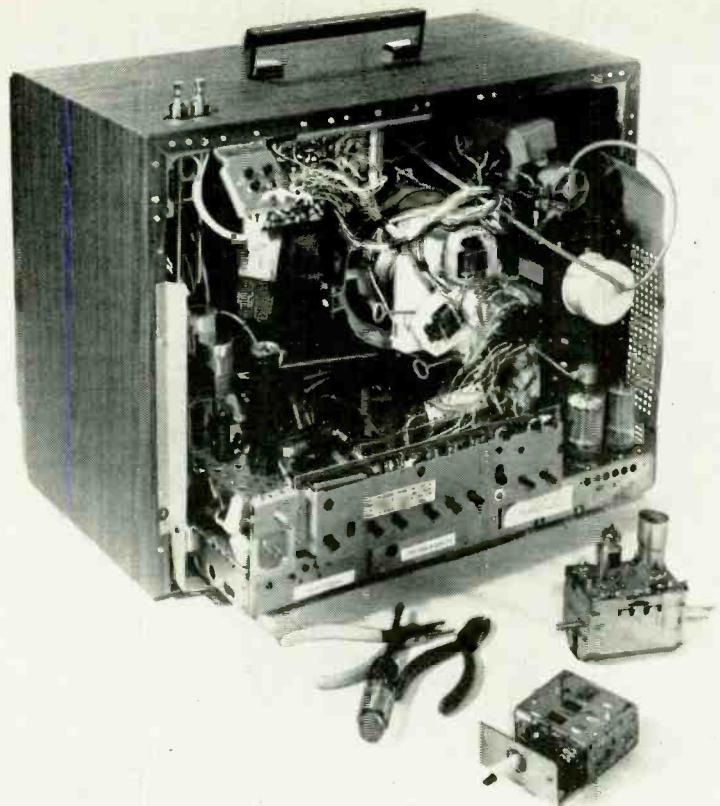

We guarantee the CRT... the rest is your business

Channel Master Opti-Vue Color CRT's with the new three year guarantee not only deliver perfect color pictures, but keep your customers coming back for all their servicing needs.

After all, you've earned their confidence by giving them the finest deal in color tubes...so who else is better qualified to fix the set when something else goes wrong?

Once your customers see the value in Opti-Vue — they're sold! It's a higher profit sale ... and you've got a satisfied customer.

We guarantee Opti-Vue for 3 years so you'll get more CRT profits ... and more servicing business.

OPTI-VUE®
The line with the 3 Year Warranty
CHANNEL MASTER

DIVISION OF AVNET, INC., ELLENVILLE, NEW YORK 12428

Circle 17 on reader service card

NOW— CHECK ALL TRANSISTORS IN OR OUT OF CIRCUIT...

Flick function switch to left to check all regular transistors.

Flick function switch to right to check any FET.



... plus
the new
**FIELD EFFECT
TRANSISTORS
too!**

You won't be stopped when you run into the new FETs that are wired into the latest hi-fi, newest TV receivers and nearly every other new device coming on the market. For the very first time, you can check them all, in or out of circuit. The TF151 works every time using tried and proven signal injection techniques. New, improved tests on special RF transistors and the latest high power transistors, mean that the TF151 is the only up-to-date transistor tester on the market. A new, exclusive setup book in rear compartment guides you to every test for over 12,000 transistors and FETs. The book is not needed for general service troubleshooting. Regular transistors are checked for beta gain and I_{CEO} leakage. FETs are checked for transconductance and I_{DSS} leakage. **only \$129⁵⁰**

NEW SENCORE TF17 compact in and out of circuit transistor FET tester. Same as TF151 except in new Sencore Handi case and with 4-1/2" meter. . . **\$109.50**



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 18 on reader service card



IS NEW, NEW?

I am an electronics technician and have been a reader of your magazine for 20 years. Many times I have read of the discovery of a new device or principle. Some have been genuinely new or unique, others have been those "why didn't I think of that before" kind. Recently, I have been seeing a high percentage of the latter.

Remember when Acoustic Research caused a sensation with their "new" principle? Does anyone remember that, long before, Bell (or Westrex) sold a speaker with very low natural resonance to be used in a closed box? It seems to me that there was also an English speaker.

Why is everyone so snowed and awed by the Dolby system of recording? If you do research (i.e., the Radiotron Designer's Handbook), you find that the principles have been known for a long time. Combine well known compression/expansion techniques with something like the Scott Dynaural and the Olson Noise Suppressor and you have Dolby. There are differences, but the Dolby circuit is an obvious conclusion.

The Scheiber 4-channel recording method is also an obvious conclusion. I have known how to do this for years. In fact, I once tried to get a local company interested. The details have not yet been released for legal reasons, but if Schreiber's method is what I think it is . . . a great many people are going to be upset. Schreiber's use of such phrases as "Analog Computer Techniques" is designed to snow everybody until he gets his patent.

There is a theory in psychology that such discoveries will frequently occur to a great many people at approximately the same time. These people have no knowledge of each other. It is not ESP (as some have suggested), but is simply a logical conclusion to be drawn from available facts in time of need. Whoever makes money is whoever gets to the Patent Office first!

CLYDE E. WADE, JR.

6200 Asher #143

Little Rock, Ark. 72114

(continued on page 22)



THE CALECTRO SUPERMARKET



EVERYTHING IN ELECTRONICS!



VARIABLE BALANCE STEREO HEAD PHONE

Unique "Sound Level" control on each earpiece permits adjustment. Frequency range: 20 to 20,000 + cps. 6½" cord with stereo plug. Impedance: 4 to 16 ohms.

Cat. No. Q4-132 \$17.95 Net

MINIATURE LAMPS



Type PR2 - 2.5 volt - 0.50 amp.
Cat. No. E2-430 - Pkg. of 2 \$2.29 Net
Type PR3 - 3.6 volt - 0.50 amp.
Cat. No. E2-431 - Pkg. of 2 \$2.29 Net



TAPE RECORDER MICROPHONE

Outstanding performance on music and speech for the price. Low impedance matches late model solid state recorders. Removable desk stand; 4½" cord with dual plugs that fit most models. Freq. Response: 100-8k Hz. Output: -77 dB. Impedance: 200 ohms.
Cat. No. Q4-144 \$4.95 Net



AUDIO ADAPTOR

"V" Audio Adaptor has a phono pin jack on one end and dual phono pin plugs on the other.

Cat. No. Q4-288 \$1.95 Net



HOBBYIST'S SOLDERING AND TOOL KIT

Diagonals, long nose pliers, soldering iron and solder, solder aid tool, heat-sink, and screwdriver. An ideal gift item.

Cat. No. H3-378 \$7.95 Net



EXPERIMENTER'S CIRCUIT BOARD KIT

Contains a 3¾" x 4" perforated board, 15 terminals (No. J4-636) and 4 mounting feet w/screws. Build small circuits, hobby and science projects, etc.

Cat. No. J4-660 \$1.98 Net

RESISTORS

Attractively packaged 2 per pack, showing values, color codes and formulas.

Type	Rating	Available Values	Price	Unit
Carbon	½ Watt	10 Ohm. —10%	.19	Pkg. of 2
Carbon	1 Watt	10 Ohm. —10%	.19	Ea.
Carbon	2 Watt	10 Ohm. —10%	.25	Ea.
Wire Wound	10 Watt	10 Ohm. —10%	.36	Ea.
		100K		
		15K		

STANDARD 1000 VOLT CAPACITOR

High quality, compact and reliable. Minimum capacity change with varying temperature. Rating: 1000 volts; tolerance: 20%.

Cat. No.	Description	Net	Unit
A1-060	220pF	\$.25	Pkg. of 2
A1-061	330pF	\$.25	Pkg. of 2
A1-062	470pF	\$.25	Pkg. of 2
A1-063	680pF	\$.25	Pkg. of 2
A1-064	0.001uF	\$.19	Ea.
A1-065	0.005uF	\$.19	Ea.
A1-066	0.01uF	\$.19	Ea.

STANDARD 1000 VOLT CAPACITOR

High quality, compact and reliable. Minimum capacity change with varying temperature. Rating: 1000 volts; tolerance: 20%.

Cat. No.	Description	Net	Unit
A1-060	220pF	\$.25	Pkg. of 2
A1-061	330pF	\$.25	Pkg. of 2
A1-062	470pF	\$.25	Pkg. of 2
A1-063	680pF	\$.25	Pkg. of 2
A1-064	0.001uF	\$.19	Ea.
A1-065	0.005uF	\$.19	Ea.
A1-066	0.01uF	\$.19	Ea.



The "GC Calectro Hobbyist Handbook" is available at your nearest Calectro Electronic Supermarket. One is located near you. WRITE TODAY and we'll rush you the name and address of your nearest Calectro Supermarket.



TWO STATION WIRELESS INTERCOM


Just plug into an electrical outlet. Completely portable. Expand system anytime with additional units. Two unit system complete in display pack. Cat. No. H4-110 \$34.95 Net

CALECTRO
G-C ELECTRONICS
400 SO. WYMAN ST. ROCKFORD, ILLINOIS 61101



A DIVISION OF
HYDROMETALS, INC.

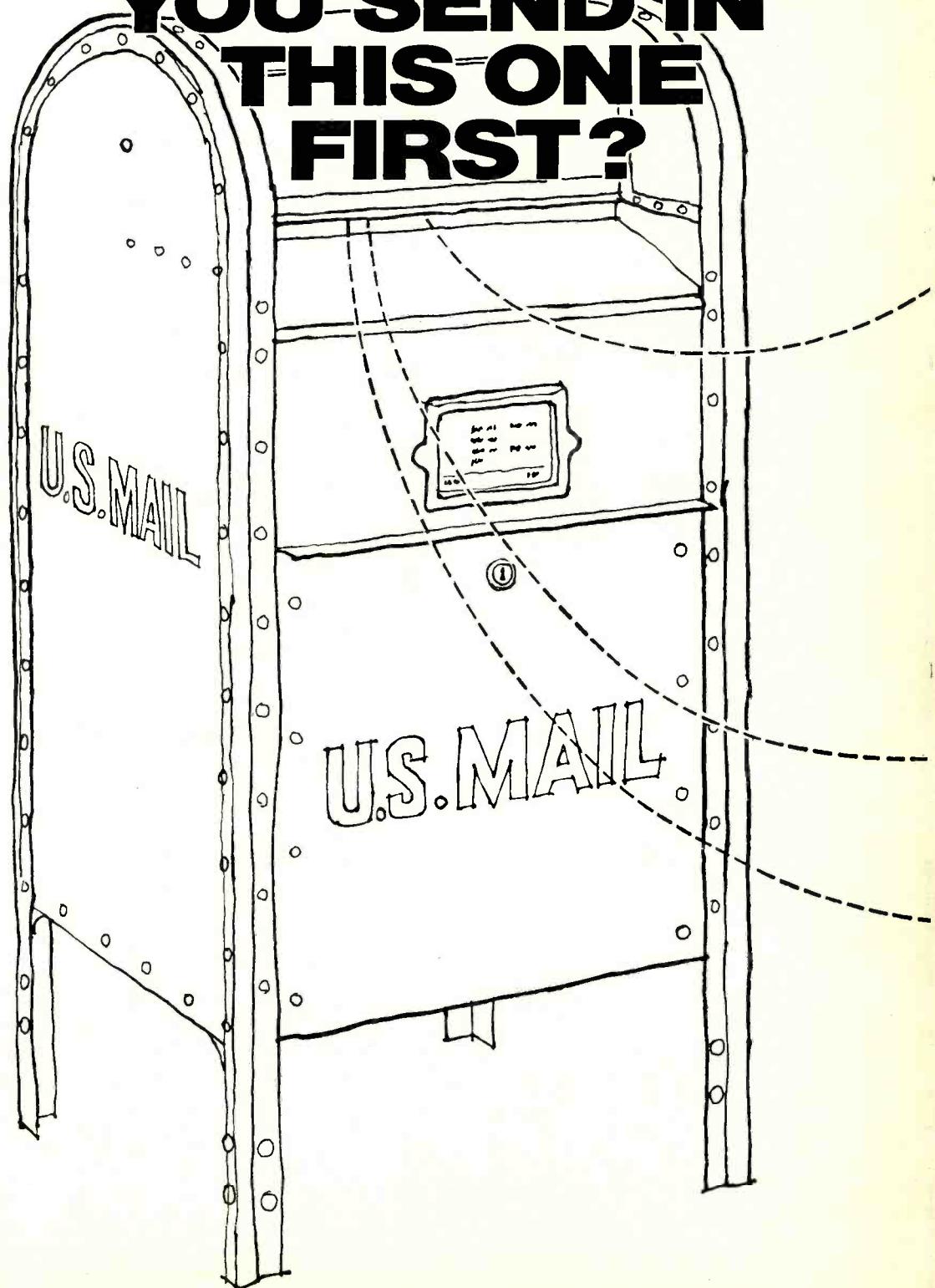**WITH ALL
THE POSTCARDS
IN THIS BOOK,
WHY SHOULD
YOU SEND IN
THIS ONE
FIRST?**



Because RCA Institutes home study training in electronics can get you started faster, easier to a bright job future and higher earnings!

Check these RCA Institutes benefits:

- You get Hands-On Training with most RCA Institutes electronics programs! (up to 25 kits with some!)
- You get RCA's exclusive "Autotext" method—individual programmed instruction, the *easy, faster* simplified way to learn!
- You get the widest choice of electronics courses and programs!
- You get a selection of low-cost tuition plans (including the exclusive "Pay As You Order" Plan!)

Pave your way to higher pay—mail the postcard today to RCA Institutes for the free illustrated catalog, "Your Career in a World of Electronics."

All courses approved under the new G.I. Bill. Accredited Member National Home Study Council. Classroom training also available, in New York City.



If reply card is detached, send this coupon today.

RCA Institutes, Inc.

Home Study Dept. 758-005-9
320 West 31st Street
New York, N.Y. 10001

Veterans:

Check Here

Age _____

Please send me free illustrated catalog,
"Your Career in a World of Electronics."

Name _____
(please print)

Address _____

City _____ State _____ Zip _____

Introducing the world's only \$339 triggered scope.

Before you say you don't need a triggered scope, look what's happening to TV servicing: tubes are out, transistors and IC's are in.

With tubes you could play hit-or-miss, knowing the tube would take the overload. Try the same thing now, and good-bye transistors.

For new-era circuitry, Leader introduces a new-era troubleshooter. A triggered scope, just like the ones the TV designers use.



Now the wave shape is locked in and continuously displayed. Now you can look at a waveform containing high and low frequency components. Now you can determine voltage directly and instantly.

Before you say \$339 is a lot of bread, look what it buys: Leader's LBO-501 5-inch triggered scope, with a bandwidth of DC to 10MHz and a solid state package.

Going like hotcakes at your Leader distributor.

Seeing is believing.

LEADER INSTRUMENTS

37-27 27th Street, Long Island City, N.Y. 11101, (212) 729-7411

Circle 20 on reader service card

Clever Kleps



Test probes designed by your needs—Push to seize, push to release (all Kleps spring loaded).

Kleps 10. Boathook type clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4 1/4" long. \$1.19

Kleps 20. Same, but 7" long. \$1.39

Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.47

Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 1/4" long. \$2.39

Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. \$.99

Pruf 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribbling tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. \$.79

All in red or black — specify.

For additional information, write for our complete catalog of — test probes, plugs, sockets, connectors, earphones, headsets, and minia-ture components.

Available through your local distributor, or write to:

RYE INDUSTRIES, INC.
130 Spencer Place, Mamaroneck, N.Y. 10543

CORRESPONDENCE
(continued from page 16)

ARTICLES I'D LIKE TO READ

I am a constant reader of your magazine and like it very much—especially the transistor circuits you suggest building. I build most of these circuits you publish, and would like to see more of them.

How about publishing some of the following articles in some of your future issues:

1. Low-voltage transistor capacitor tester (test of quality).
2. TV transistor camera (closed-circuit rf).
3. FET transistor quality tester.
4. Transistor audio oscillator.
5. Transistor signal generator.
6. Transistor multiband receiver.
7. Control rectifier quality tester.
8. Triac quality tester.

C. P. ARMENTROUT
Titusville, Fla.

KWIK-FIX™ WORKS!

I recently repaired a Zenith 20X1C38 chassis that had color stripes and turned to the March issue of Kwik-Fix™ for help.

It was a particularly difficult case because I had multiple troubles—the control voltage was inadequate and the 3.58 mHz oscillator was unstable, with the result that sometimes there were stripes and sometimes not.

Although the Kwik-Fix™ guide did not point to the defective parts, I found the circuit description and the troubleshooting guide in the text to be invaluable in isolating the intermittent components.

Although schematics are generally available, there is a real need for brief descriptions of their operation and I appreciate the thoroughness and tersity of Forest Belt's articles.

MONTY HUCKLE
Tahoe City TV Service
Tahoe City, Calif. 95730

PULSE-GENERATOR FOLLOW-UP

The author reports that if you use PC boards to construct the pulse generator (February 1970, page 37) you will do OK. But, if you wire directly from the main schematic (Fig. 2) or try to compare it with the PC pattern on page 38, you'll run into a little trouble. On the schematic, there should be a dot indicating a connection between the top end of R33 and the lead from R32 and the emitter of Q3. Resistor R33 is the common emitter resistor for Q12 and Q13.

Too, there should be a connection between the collector of Q5 and the top end of R18 in the base circuit of Q6.

R-E

Circle 22 on reader service card ➤



Stereo You Can Feel

It begins even before you've heard a note from the new Sony TA-1144 Stereo Amplifier and ST-5100 FM Stereo/FM-AM Tuner. Pleasure.

The switches flick firmly. The pushbuttons push back just enough before locking in smartly. Continuous controls (like tuning, volume, balance), feel almost viscous-damped. Your fingers are guided to function swiftly, effortlessly. You've experienced a feeling of quality that is a hint to the performance you'll enjoy once you turn on these Sony components.

Take the ST-5100. The combination of two tuning meters, a 2.6uV IHF sensitivity, and 1.5dB capture ratio zero in on your first station. FM stereo you can feel.

Now the TA-1144 Stereo Amplifier. More stereo you can feel. Rich (the TA-1144 puts out 50 watts IHF per channel into 8 ohms, both channels operating). Clean (less than 0.03% IM, 0.05% harmonic, at 1 watt). And just the way you like it (thanks to those subtly-detented bass and treble sliders on each channel).

So now you're wondering, of course, about the prices. Just \$219.50* each; \$439* the pair. You'll hardly feel that at all.

Sony Corporation of America, 47-47 Van Dam St., Long Island City, N.Y. 11101. **NEW SONY® AMPLIFIER AND TUNER**


*Suggested List



Use Aerovox capacitors available from your local AEROVOX DISTRIBUTOR

He's your best "one-stop" source for virtually every replacement capacitor you require. He carries the complete Aerovox line which includes: ceramics, micas, electrolytics, papers, film and interference filters. So no matter what your replacement requirement, you're sure to find it at an Aerovox Distributor.

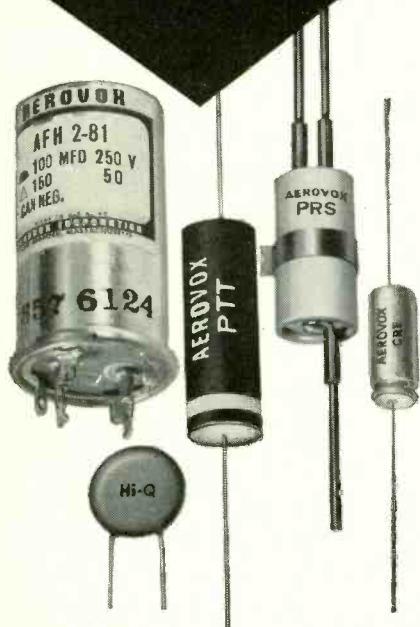*service it
FAST
with
components
that
LAST!*



AEROVOX
CORPORATION

DISTRIBUTOR SALES, New Bedford, Mass. 02741
Visit AEROVOX at New Show, Booth 4110 &
Indistribution Center Room 557
Circle 23 on reader service card

In the Shop . . . With Jack

By JACK DARR
SERVICE EDITOR

DIVIDE UP FOR EFFICIENCY

WHILE I WAS WORKING ON A TV SET the other day, I noticed that I did a lot of getting up and running back and forth. Not that the exercise wasn't good for me; I just seemed to spend most of my time "on the road." This might be healthy, but it isn't too darn efficient. This started me thinking about our shops, and their efficiency. In other words, what can we do to get more done in less time, and with less trouble?

I remembered a discussion I'd had with a friend about his shop layout. I took a long hard look at my own indoor pig pen, and decided that it fell a good deal short of being 100% efficient! Out came the scratchpad, and I started to see if I could work up some ideas.

I believe that for maximum efficiency we should divide the shop into three "primary areas," each one set up for a certain type of work— instruments, tools, etc. The first one would be the "starting point"; this should have the measuring test equipment— voltmeters, ohmmeters, high-voltage voltmeter, scope, etc. These are the test instruments you use *first* on every job to read "quantities": dc voltages, resistance, and so on.

A good percentage of service jobs will be finished right in this primary area. As you know, most jobs call for replacement of bad resistors, dead tubes, broken wires and that kind of thing. So, this position should have test equipment for making basic tests within easy reach.

Next to this position should be No. 2 area. This should have parts testers for capacitors, transistors, tubes, flybacks, and the parts-substitute boxes—resistors, electrolytic capacitors, etc. This area should *adjoin* No. 1 so you'll have to move only a short distance to get any of these instruments.

Next to No. 2 should be No. 3, with the equipment that we use least often. This would include color-bar and TV pattern generators, rf signal generators and the sweep and marker generators for alignment work. This

area should be accessible, but out of the "main stream" of traffic flow to areas 1 and 2. When this isn't being used for alignment, it can be used as a "cooking area," with the signal generators, bar-dots, etc. to provide steady test signals.

There's one more question, and this depends entirely on how *you* like to work. Might say that the question is "fixed or mobile?" In other words, should the test equipment be set on the bench, on a shelf above it, or on carts so that it can be rolled up to the job? The best way to find is to try it and see.

For example, I use a combination: scope under the shelf on the bench, small transistorized voltmeter on the bench, and a big capacitor tester, flyback tester and transistor tester on a roll-around cart.

Run an experiment for yourself. Make a tentative instrument setup, and try it out on a few actual service jobs. See how many times you have to get up and go get an instrument that's not within easy reach; also, see if your *most-used* instruments can be reached without moving too far. With me, this is the tvm and the scope; yours may be different.



So, step back and take a long, hard, honest look at the operation and layout of YOUR shop. Then, see if you can't find some way to shuffle things around so that it will be much more efficient. As another example, I put a new transistor tester on the shelf at the far end of the bench from my favorite working position. I found myself jumping up and running the length of the shop to get the transistor tester. So, onto the cart it went with the rest of the parts testers, where it belonged.

I think you'll be surprised at the results. If you can make only a 10% saving of time on most jobs, it will amount to a tidy bundle of bread at the end of a month! If you have a fixed minimum bench charge, as most of us do, the quicker you can get a job out, the more you make per day. And, that's the name of the game! R-E

don't miss this opportunity

**If You Have What It Takes
to Qualify for Training in Electronics
We'll Not Only Train You...**

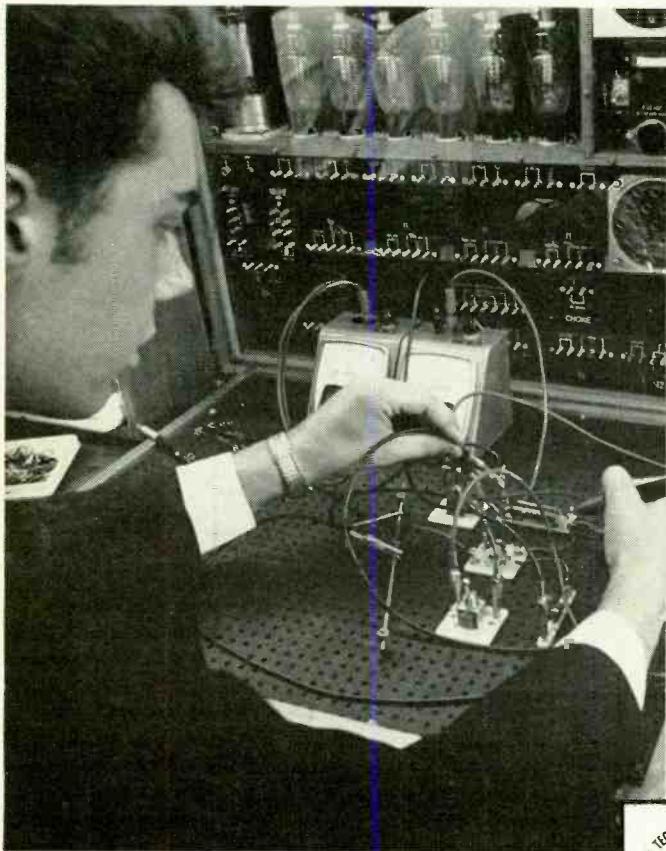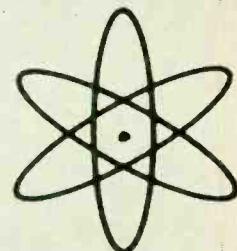**We'll Help You Finance
Training and Help Place You
In the Job You Want!**



Just a few short years ago, who could have imagined electronic marvels like the micro-miniaturized printed circuit, no larger than the head of a pin . . . battery-powered heartbeat regulators . . . computers that make split-second calculations it would take the human brain years to duplicate! This is the amazing world of technology.

The demand for trained Electronics Specialists and Draftsmen is increasing every year! These are well-paid, prestige positions with practically unlimited opportunities for advancement. In 12 months or less, United Technical Institute can prepare you to take your place in this dynamic, expanding field. You can study right at home, in your spare time and at your own pace — or attend a UTI resident school near you.

Because UTI is an eligible institution under the Federally Insured Student Loan Program, you may attend the Institute on a government-guaranteed educational loan. And after you finish your training, we can help you find your first position!

Accredited Member of National Association of Trade and Technical Schools. Approved for Veteran Training.

Get the facts now! Just clip the coupon and send today for a FREE, fact-filled book describing the exciting opportunities in electronics, and how you can qualify for them. We'll rush your book by return mail so you can read it and decide for yourself. No obligation, of course. But don't delay — clip the coupon for your free book today!



United Technical Institute

division of Career Academy

125 W. Wells St. Milwaukee, Wis. 53203 Dept. N215200

Please rush me your free 28 page booklet
with all the details on your Electronics course

Name _____ Age _____
(Please print)

Address _____

City _____ State _____ Zip _____

Phone _____

I am interested in: Classroom Study Home Study Facts on GI Bill


Circle 24 on reader service card

ARROW AUTOMATIC STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

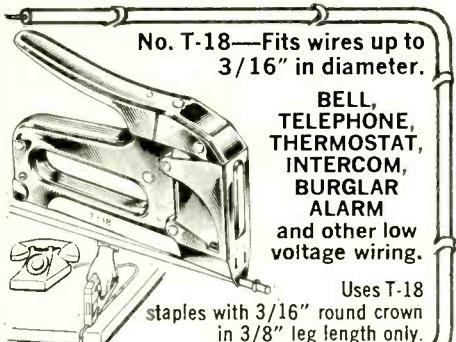SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!




No. T-18—Fits wires up to 1/4" in diameter.

Same basic construction and fastens same wires as No. T-18.

Also used for RADIANT HEAT WIRE


Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths.

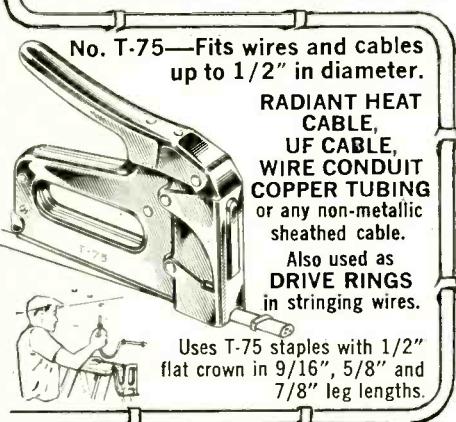T-18 and T-25 staples also available in Monel and with beige, brown and ivory finish at extra cost.



Arrow Automatic Staple Guns save 70% in time and effort on every type of wire or cable fastening job. Arrow staples are specially designed with divergent-pointed legs for easier driving and rosin-coated for greater holding power! All-steel construction and high-carbon hardened steel working parts are your assurance of maximum long-life service and trouble-free performance.

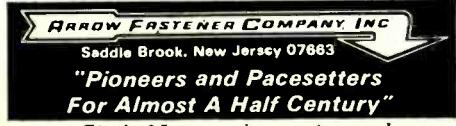Ask your Electrical Supply Dealer or write for further details.



EQUIPMENT REPORT

Hickok DMS-3200

For manufacturer's literature, circle No. 67 on Reader Service Card.

HICKOK'S NEW DIGITAL MEASURING System, the DMS-3200 Main-Frame, is the mother-unit of what promises to be a pretty large family. There are 12 plug-in units which can make the main-frame display unit into an ac or dc voltmeter, ohmmeter, capacity meter, event counter, current meter, frequency meter, and even a multimeter. Hickok will add new plug-in units from time to time, as the need arises.

The main frame includes the sequential counting and display circuits, their control circuitry, and an extremely well regulated power supply for main-frame circuitry and the plug-ins as well. The digital readouts are Burroughs Corp. Nixie tubes—special neon tubes which light up actual figures over an inch high. Three digits are displayed, but the system has a very wide coverage. This is made possible by range-switching of the plug-ins. The decimal point moves automatically.

The main-frame circuitry is basically a pulse counter. This is done by three cascaded decade scalers; five RTL JK flip-flops, interconnected as switch-tail-ring counters. These are computer circuits designed to count up to 10, then pass along one pulse

for every 10 pulses fed in. If there are any odd pulses left over, it saves them up and displays them on its own Nixie tube. (Each decade scaler stage controls one of the tubes).

For example, if 467 pulses are fed in, the first counter will save the odd "7," and pass on 46 pulses to the next stage. This stage will pass on four pulses and save the "6." The final stage gets only four pulses; each stage will display the figure it has left over, and the display then reads "467." The "first" stage, by the way, is the "units" or right hand digit; this works from right to left. This is actually a "mini-computer." "Mini" only in physical size; it uses a total of 18 integrated circuits and 43 transistors. The pulses that it counts come from the plug-in unit.

In the ac voltmeter plug-in, for example, an ac voltage of any frequency up to 1 MHz is fed to the input. It reads rms values, at a rated accuracy of $\pm 0.1\%$ of the indicated reading plus or minus one count. It will also read square or sawtooth waveforms with the same degree of accuracy. Correction tables are provided for use with other waveforms, if needed.

To get the pulses which are actually counted, the ac voltmeter takes the input ac voltage, passes it through a very closely calibrated attenuator network, and feeds it to an ac pre-amplifier.


From this stage, it goes to an ac/dc converter, where it is rectified to a dc voltage directly proportional to the rms value of the input. This is compared to a closely regulated reference voltage from a Zener diode. The differences voltage is split, and gated through a control flip-flop, with pulse shapers in its outputs. Our ac voltage has now become a squared-off and carefully calibrated pulse; this pulse triggers and times a gated oscillator circuit, working at about 10 kHz.

So, for a given value of ac input voltage, a very accurate "burst" of oscillator signal is generated and fed to the pulse counters in the main frame. These actually count the number of cycles, and display them on the Nixie tubes. In the example given before, the input voltage pulse "chops out" 467 cycles of oscillator signal and sends it along to be counted.

It's very interesting to watch this thing at work! The Nixies light up (continues on page 80)



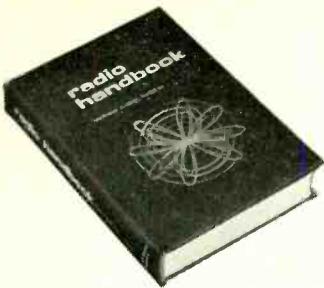New SAMS Books for every electronics interest




New 18th Edition of the famous E & E RADIO HANDBOOK

by WILLIAM I. ORR, W6SAI. Completely updated edition of the famous communications handbook which is the electronics industry standard for engineers, technicians and advanced amateurs. Explains in authoritative detail how to design and build all types of radiocommunications equipment. Includes SSB design and equipment, RTTY circuits, latest semiconductor circuits and IC's, as well as special-purpose and computer circuitry. Order 24020, only \$13.50

New 13th Edition of the famous TUBE SUBSTITUTION HANDBOOK

Lists over 12,000 direct substitutions. A complete guide to substitutions for receiving, picture tube, miniature, industrial, and communications types; also includes foreign tubes. Tells how and when to make proper substitutions.

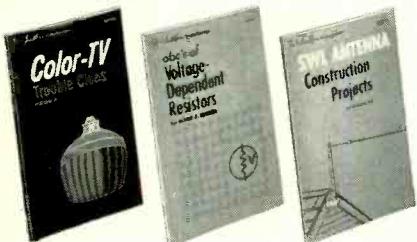Order 20769, Twin-Pak (regular size for bench use; pocket-size for caddy) both for only \$2.25
Order 20768, shop edition, only \$1.75



Color-TV Trouble Clues, Vol. 3

by HOWARD W. SAMS EDITORIAL STAFF. Helps speed diagnosis of color-TV troubles. Tells how to get right to the heart of the problem, how to make positive checks, how to use meaningful clues for quick troubleshooting. Supplements popular earlier volumes, but contains all-new material, especially on late-model color chassis. Order 20762, only \$3.50

ABC's of Voltage-Dependent Resistors


The Voltage-Dependent Resistor (VDR) is relatively unknown, and its advantages have gone largely unrecognized and unused. This book explains in simple language the principles of VDR's, and describes the many types available, and how they are used in a variety of applications. Order 20771, only \$2.95

SWL Antenna Construction Projects

Provides detailed information on how to construct 35 different antennas for improved short-wave reception. Explains basic antenna principles and then presents the construction projects which fall into six basic classes of design. Order 20766, only \$2.95

Auto Radio Servicing Made Easy

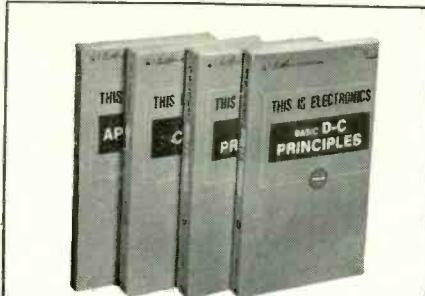2nd Ed. Explains the circuitry of both new and old auto radios, covering each of the tube and transistor stages. Provides step-by-step troubleshooting and repair details; explains how to eliminate noise and interference, and how to make proper adjustments. Order 20719, only \$3.95



THIS IS ELECTRONICS Series

by ITT EDUCATIONAL SERVICES, INC. These books provide a remarkable introduction to electronics, imparting to any reader a clear understanding of the basics of this vital technology. All topics are covered and readily mastered.

Vol. 1. Basic D-C Principles

Covers electronics—past and present; electronic components and symbols; matter and electricity; current, voltage, and resistance; series and parallel circuits; conductors, semi-conductors, and insulators; resistors; and sources of d-c power. Order 20657, only \$5.95

Vol. 2. Basic A-C Principles

Covers alternating voltage and current; capacitors and capacitive reactance; magnetism and electromagnetism; electrical measuring instruments; and inductors and inductive reactance. Order 20727, only \$6.95

Vol. 3. Circuits

A-c and d-c principles and components are used to illustrate how vacuum tubes and semi-conductors operate. Various amplifier and oscillator circuits of both tube and transistor types are fully described. Order 20759, only \$6.95

Vol. 4. Applications

This volume explains how amplifier and oscillator circuits are used in actual applications. Explains principles of modulation, broadcast receiver fundamentals, a-m and f-m receiver circuits, etc. Order 20760, only \$5.95
4-Vol. Set. Order 20761, only \$23.50

Record Changer Servicing Guide

Provides a complete understanding of record changers, how they operate, and the various systems employed. Provides detailed instructions on how to track down troubles encountered in record changers and how to repair them in the fastest and most effective way. Order 20730, only \$3.95

Electronic Organs—Vol. 2

Explains the fundamental principles of electronic organs, including theory, development, features and operation. In block diagram and schematic illustrations, the book shows what is inside an organ. Order 20754, only \$5.50

HOWARD W. SAMS & CO., INC.

Order from any Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. RE-5
4300 W. 62nd St., Indianapolis, Ind. 46268

Send books checked at right. \$____ enclosed.

Send FREE 1970 Sams Book Catalog

Name _____
PLEASE PRINT

Address _____

City _____ State _____ Zip _____

- | | |
|--------------------------------|--------------------------------|
| <input type="checkbox"/> 24020 | <input type="checkbox"/> 20760 |
| <input type="checkbox"/> 20769 | <input type="checkbox"/> 20761 |
| <input type="checkbox"/> 20768 | <input type="checkbox"/> 20730 |
| <input type="checkbox"/> 20762 | <input type="checkbox"/> 20754 |
| <input type="checkbox"/> 20771 | <input type="checkbox"/> 20763 |
| <input type="checkbox"/> 20766 | <input type="checkbox"/> 20765 |
| <input type="checkbox"/> 20719 | <input type="checkbox"/> 20753 |
| <input type="checkbox"/> 20657 | <input type="checkbox"/> 24004 |
| <input type="checkbox"/> 20727 | <input type="checkbox"/> 20756 |
| <input type="checkbox"/> 20759 | <input type="checkbox"/> 20755 |



Color-TV Waveform Analysis

This book provides both the theoretical and the practical knowledge of waveform analysis essential for profitable and efficient color TV servicing. It begins with the rf and i-f sections, and proceeds through the video-amplifier, bandpass-amplifier, color-sync, color-demodulator, and matrix circuits. Also includes a full discussion of vectorgrams. Order 20763, only \$3.50

ABC's of Thermistors

Explains in detail this simple, but extremely useful solid-state device with which many technicians are unfamiliar. Discusses thermistor fundamentals, instrument applications, control and alarm applications, amplifier and oscillator applications, thermistors in communications, and supplementary circuits. Order 20765, only \$2.95

101 Questions & Answers About Hi-Fi and Stereo

A practical and useful reference book explaining the essential facts about hi-fi and stereo, with important help on troubleshooting and maintenance. The six sections of the book cover: high-fidelity systems; amplifiers; tuners; record and tape players; maintenance and troubleshooting procedures. Order 20753, only \$3.50

Amateur Radio Incentive Licensing Study Guide

Fully explains the new incentive licensing which affects both newcomers and old-timers. Covers all the new FCC Regulations and band allocations. Includes sample exams for Novice, Technician, Conditional, and General- Advanced- and Extra-Class licensing. Order 24004, only \$2.75

Space-Flight Simulation Technology


Presented as a primer covering the contributions, capabilities, and future potentialities of a very rapidly expanding industry. Deals in detail with simulation and the simulator—a training innovation without which manned space flight would be impossible. Order 20756, only \$4.95

How to Use Integrated Circuit Logic Elements


Written for the engineer or technician who has not previously used or designed digital logic circuits. Also, electronic hobbyists will find this book interesting and understandable and will appreciate the fascinating logic circuits dealt with in the material. Order 20755, only \$3.95

**"Get more
education
or
get out of
electronics**

...that's my advice."

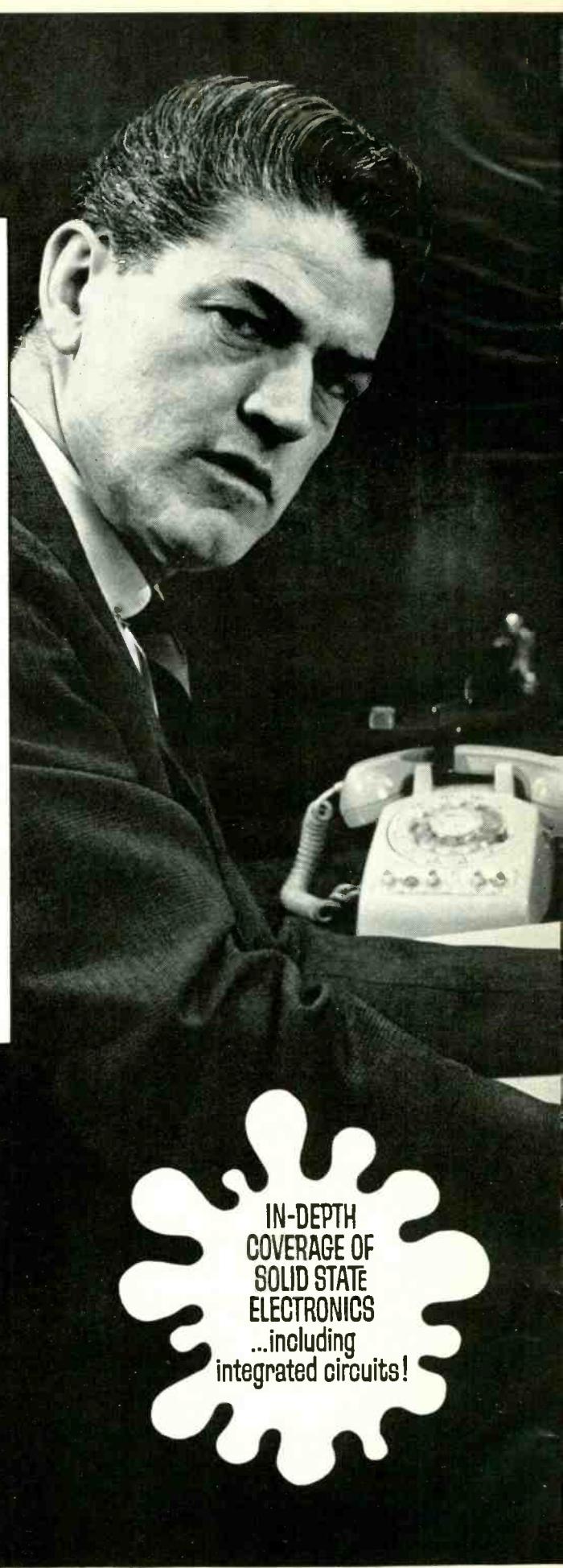

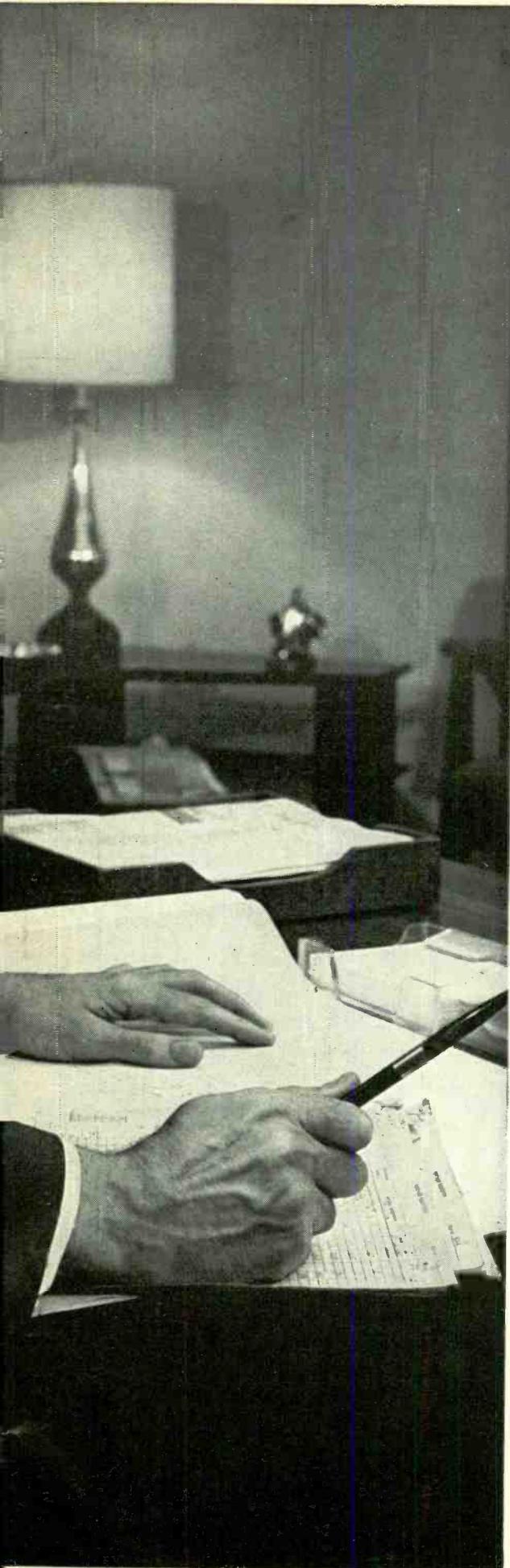**IN-DEPTH
COVERAGE OF
SOLID STATE
ELECTRONICS
...including
integrated circuits!**



Ask any man who really knows the electronics industry.

Opportunities are few for men without advanced technical education. If you stay on that level, you'll never make much money. And you'll be among the first to go in a layoff.

But, if you supplement your experience with more education in electronics, you can become a specialist. You'll enjoy good income and excellent security. You won't have to worry about automation or advances in technology putting you out of a job.

How can you get the additional education you must have to protect your future—and the future of those who depend on you? Going back to school isn't easy for a man with a job and family obligations.

CREI Home Study Programs offer you a practical way to get more education without going back to school. You study at home, at your own pace, on your own schedule. And you study with the assurance that what you learn can be applied on the job immediately to make you worth more money to your employer.

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Mail postpaid card for your copy. If card is detached, use coupon below or write: CREI, Dept. 1405A, 3224 Sixteenth Street, N.W., Washington, D.C. 20010.



**CREI, Home Study Division
McGraw-Hill Book Company
Dept. 1405A, 3224 Sixteenth Street, N.W.
Washington, D.C. 20010**

Please mail me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____


EMPLOYED BY _____

TYPE OF PRESENT WORK _____ G.I. BILL

I am interested in

- Electronic Engineering Technology Computers
- Space Electronics Nuclear Engineering Technology
- Industrial Automation NEW! Electronics Systems Engineering

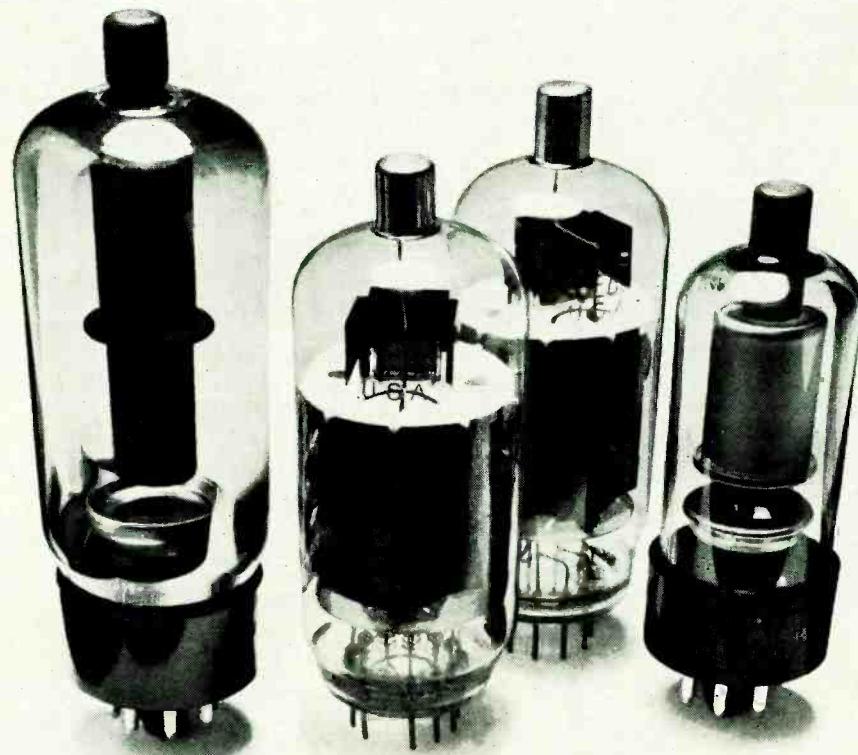APPROVED FOR TRAINING UNDER NEW G.I. BILL



Our hot ones are the last to go.

The last thing you need is to be called back a day or two after you've replaced the sweep or high voltage tubes in somebody's color TV.

But, they're usually the first to go. Because they get so hot.

So we figured out how to cool them.

Now, they last a lot longer.

Take our 6JE6C/6LQ6, for example. It's the horizontal deflection tube that takes such a beating when the set gets hot.

Well, we've given it special patented radiator fins that first absorb the heat and then radiate it out of the tube.

Now it runs cooler and lasts longer. Same for our 6JS6C.

Or take our 6BK4C/6EL4A. That's the shunt regulator that eliminates runaway high voltage. We gave this one a whole new anode and shield design to improve heat transfer and stability.

Now it also runs cooler and lasts longer.

Or take our 3A3B high voltage rectifier. This one's got leaded glass for added protection. And it lasts longer too.

So next time you have to replace any of the hot ones, just cool it. You'll both last longer.

SYLVANIA
GENERAL TELEPHONE & ELECTRONICS

RADIO-ELECTRONICS

For the experimenter

10 Emitter-Coupled Oscillator Circuits

- 1 Basic emitter-coupled circuit
- 2 Basic R-C oscillator
- 3 R-C oscillator to 30 kHz
- 4 Simple musical instrument
- 5 R-C oscillator with feedback

by FRED MAYNARD

THE Emitter-COUPLED AMPLIFIER IS a most useful configuration in logic, switching and vhf circuits. It can also be used in a series of very simple and interesting oscillators. Eight such circuits are shown here.

The basic E-C amplifier

The basic emitter-coupled amplifier consists of the two-transistor, three-resistor configurations shown in Fig. 1. The base of Q1 is the input, and the collector of Q2 is the output. Transistor Q1 is an emitter follower, and Q2 a grounded (common)-base voltage amplifier. The emitters of Q1 and Q2 are tied together and connected to a common, unbypassed emitter resistor, R2. Resistor R1 is a normal load resistor.

In the circuit in Fig. 1-a, the bases of both transistors are at ground potential, and a split supply of +3 volts and -6 volts is required. A more convenient circuit requiring a single 6- to 9-volt supply is shown in Fig. 1-b. Here the intermediate base bias level is obtained from voltage divider R3 and R4. Resistor R4 is bypassed to ground. In all the applications shown in this article, a version of Fig. 1-b is used, but the split-supply version of Fig. 1-a can also be used.

Gain and phase relationships

As a voltage amplifier, the E-C amplifier is not outstanding. The configuration in Fig. 1-b provides a voltage gain of about 4. A well-designed, common-emitter, single-transistor amplifier can provide voltage

- 6 L-C oscillator variations
- 7 Capacitive feedback circuit
- 8 Carrier insertion oscillator
- 9 Intruder detector
- 10 Emitter-coupled amplifier

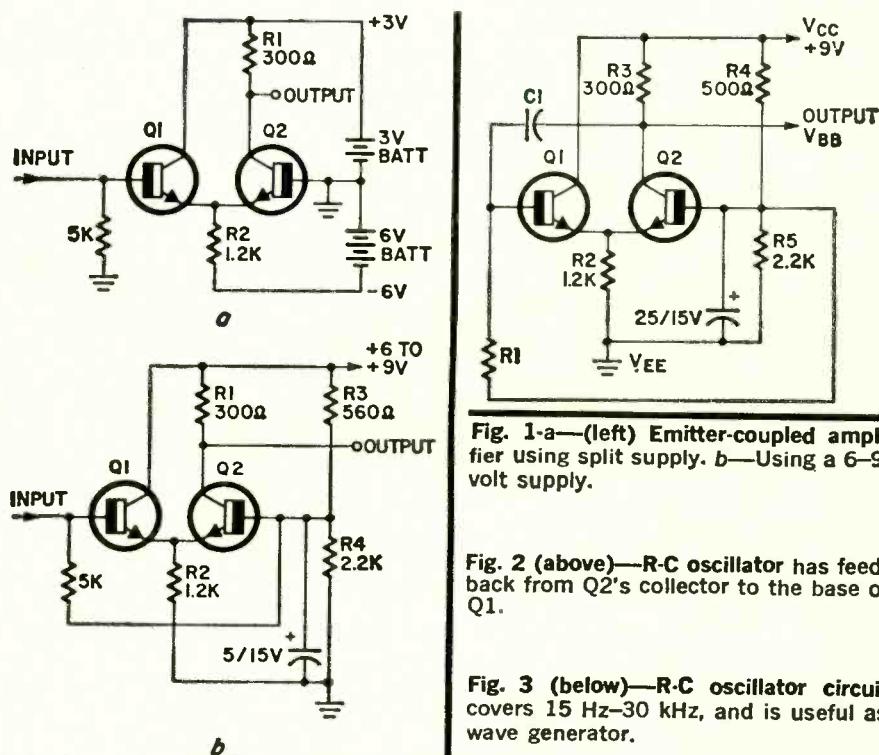


Fig. 1-a—(left) Emitter-coupled amplifier using split supply. b—Using a 6-9-volt supply.

Fig. 2 (above)—R-C oscillator has feedback from Q2's collector to the base of Q1.

Fig. 3 (below)—R-C oscillator circuit covers 15 Hz-30 kHz, and is useful as a wave generator.

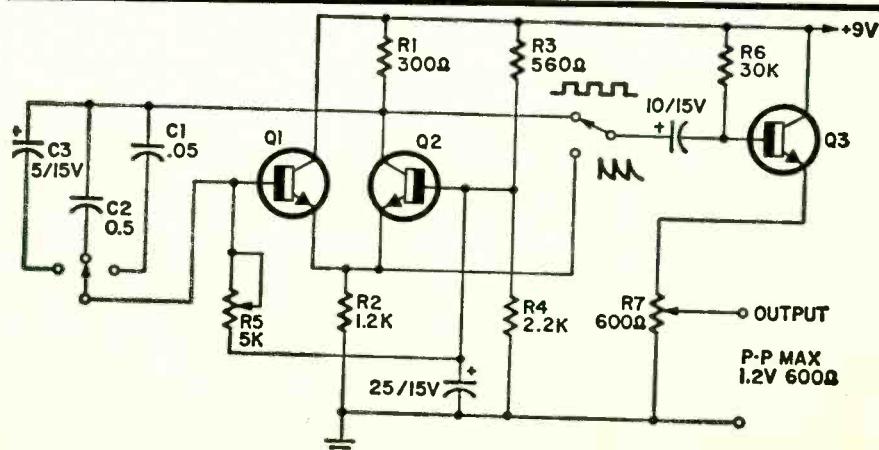


Fig. 4—Trim pot series can turn Fig. 3 circuit into a simple musical instrument covering C scale. R1 value varies vibrato.

Fig. 5—Variations of L-C oscillator can be used for useful R-C circuits.

gains of 10 to 20. On the other hand, the E-C amplifier has a much higher input impedance than the common-emitter version, and provides a much higher power gain.

The most interesting and useful thing about the E-C amplifier is that the input and output are in phase. Suppose a negative-going signal is applied to the input base of Q1. The emitter of Q1 will follow and go negative by the same amount. This pulls the emitter of Q2 negative, causing Q2 to conduct harder. Hence, the collector of Q2 is also pulled negative.

This in-phase relationship provides for the implementation of several very simple oscillators.

Basic oscillator circuit

A basic R-C oscillator is shown in Fig. 2. In this circuit the V_{BB} bias is obtained from voltage divider R4, R5, or may be from a split power supply, as described earlier. Feedback is provided from the collector of Q2 to the base of Q1, and the base bias (to Q1) from the V_{BB} bias through R1. The oscillator frequency depends basically on the R_1C_1 time constant, as well as other shunting or capacitive effects in the oscillator circuit.

This circuit will oscillate over a range of nearly two decades. Over a substantial part of this range, an approximate formula for frequency in terms of the values of C_1 and R_1 may be written as:

$$f_o = 0.32 \frac{1}{R_1 C_1}$$





where f_o is in kHz, R_1 in $\text{k}\Omega$, and C_1 in μF .

The measured deviation from this relation may be as much as $\pm 10\%$, depending on circuit conditions, transistor parameters, etc.

Simple wide-range R-C oscillator

A wide-range R-C oscillator is shown in Fig. 3. This oscillator is implemented with feedback capacitors C_1 , C_2 or C_3 from the collector of Q2 to the base of Q1, and variable resistor R5, which returns to the base point on the divider. With the constants shown the circuit will oscillate from about 15 Hz to 30kHz in three decade ranges.

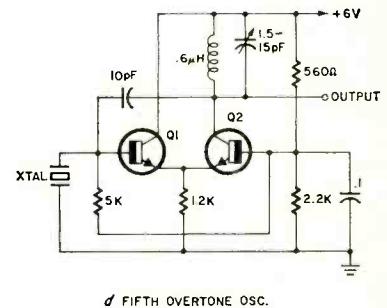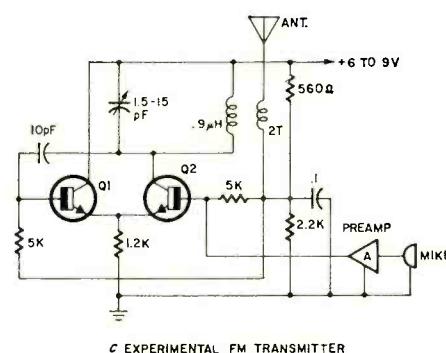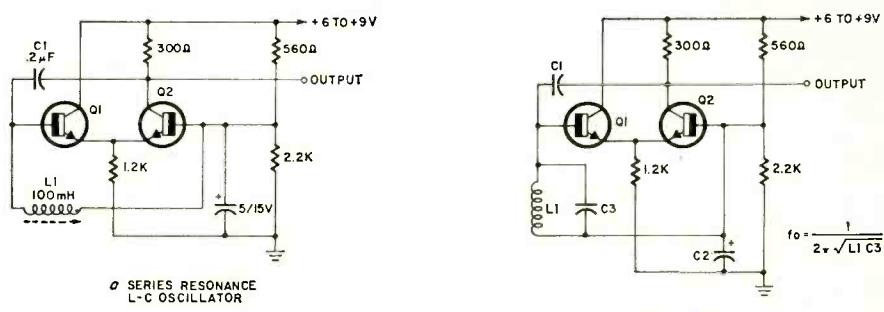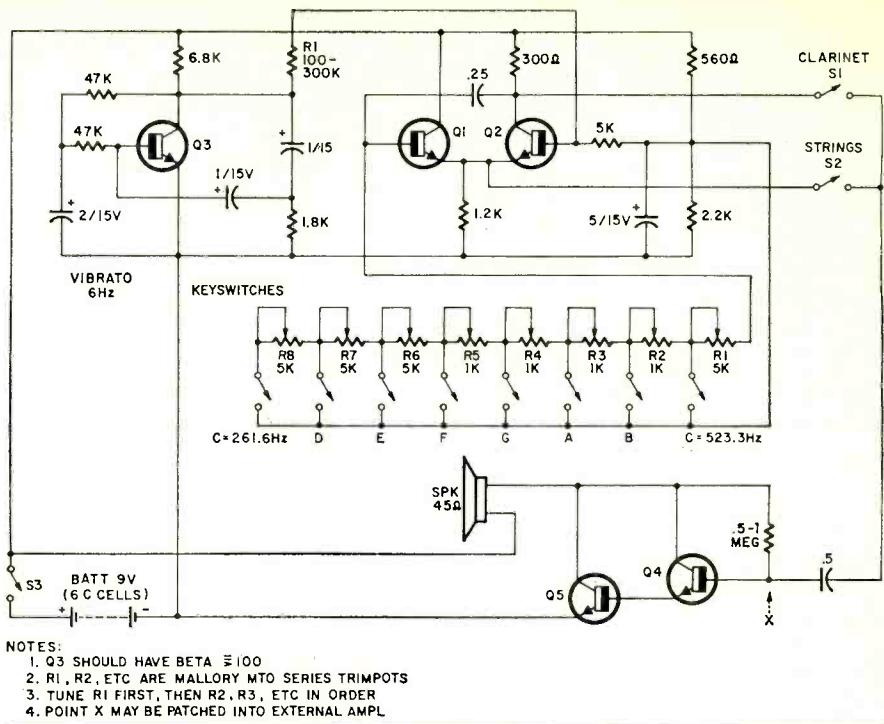The output of this oscillator at the collector of Q2 is a square wave with fast rise and fall times. It may, however, be quite asymmetrical over




part of the tuning range. A rather good sawtooth wave appears at the common-emitter junction. The follower, Q3, prevents loading.

I have used this circuit as a calibrated test generator and as a simple musical instrument. The latter is shown in Fig. 4. The oscillator is tuned to a musical scale with series-connected resistors, preferably adjustable low-cost trimming potentiometers. These resistors are adjusted to tune the oscillator to notes in a musical scale, such as the scale in C shown. If desired, a much longer scale can be used, and the half tones (sharps and flats) can be inserted.


Simple keyswitch contacts on the keys make contact to a bus that goes to the divider. The 5,000-ohm resistor between the base of Q2 and the divider allows the injection of a 6-Hz vibrato circuit (Q3). The instrument may be played with any external amplifier or the simple Darlington amplifier shown can be used to obtain moderate room volume. The vibrato depth can be adjusted to the most pleasing level by varying the value of resistor R1.

L-C oscillators

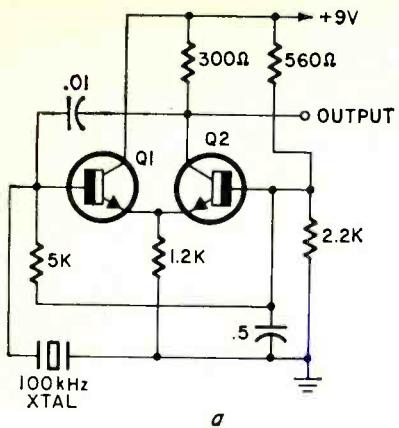Four L-C oscillator forms based on the emitter-coupled amplifier are in Fig. 5. The version shown in Fig. 5-a



a

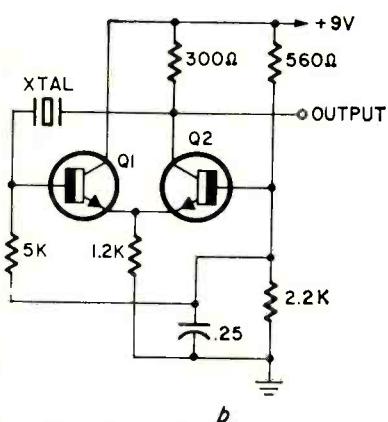

b

Fig. 6-a—Capacitive-feedback crystal oscillator. b—Using crystal for feedback.

is almost identical to the R-C version described earlier, with inductor L1 substituted for the resistor. This circuit has a series resonance between L1 and C1, but not at exactly the theoretical resonance.

In Fig. 5-b, a capacitor is added to the same circuit to form a tank circuit. Here the formula for series resonance for a good approximation is

$$f_o = \frac{1}{2\pi \sqrt{LC}}$$

Feedback capacitor C1 should be about a tenth the value of C3.

In Fig. 5-c, the L-C tank circuit

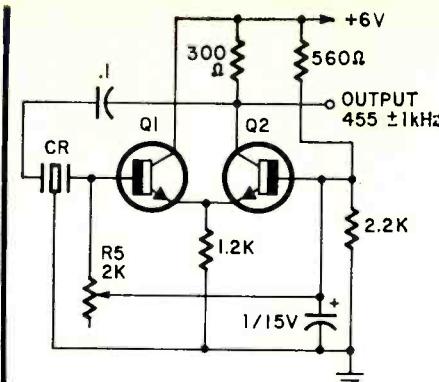


Fig. 7—Carrier insertion oscillator is one use for this ceramic-filter circuit.

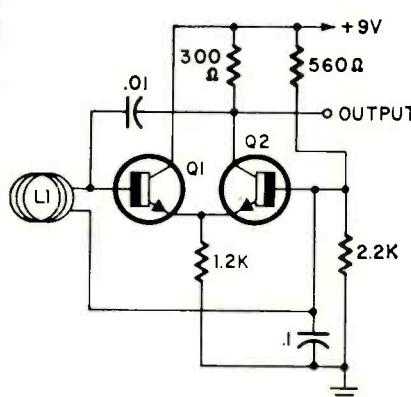


Fig. 8—Coil L1 varies 7–30-MHz oscillation when someone approaches the loop.

is placed in the collector leg of Q2. In this position the circuit develops substantially more power than in the version shown in Fig. 5-b. I used this circuit in an experimental FM transmitter at about 96 MHz. The FM is obtained by driving the base of Q2 with a microphone preamplifier signal. The voice quality obtained is quite good.

A crystal-controlled version of Fig. 5-c is shown in Fig. 5-d. This circuit was used as the local oscillator in a fixed-tuned vhf receiver with good results. The oscillator tank was locked in on the fifth crystal overtone.

Crystal-controlled oscillators

One overtone crystal oscillator was described above because it fits in with the L-C circuit versions. Two fundamental-mode crystal oscillators are in Fig. 6. In Fig. 6-a, capacitance feedback is used with the crystal across the base load of Q1. In Fig. 6-b, the crystal itself forms the feedback element.

An interesting oscillator is shown in Fig. 7. The part labeled CR is a 455-kHz ceramic filter used instead of a transformer in some transistor receivers. By varying R5, the crystal frequency can be "pulled" about ± 1 kHz from its center resonance frequency. This oscillator serves very effectively as a carrier-reinsertion oscillator in a solid-state single-sideband receiver. It provides excellent stability in the reinsertion stage, where very good stability is needed.

A "big loop" oscillator

During the experimental work with the E-C amplifier, when it appeared that the circuit would oscillate under almost any conditions, a "fun" circuit was set up. It may have an element of usefulness. In Fig. 8, L1 is a loop of 10 to 20 turns of insulated wire.

Several loops were tried, varying in diameter from about 4 inches to 4 feet. In all cases oscillation was obtained at some fairly high frequency (7 to 30 MHz). It was noted that the frequency shifted substantially when a person came near or into the loop. This oscillator together with a resonant detector might make a very good antipersonnel alarm.

Transistor requirements

Transistor gain does not appear to be critical in the E-C amplifier and the oscillator circuits. This is probably due to the fact that the critical gain in an emitter-coupled amplifier gain is alpha, rather than beta. Low-cost (40¢ each) Motorola MPS2926 units work satisfactorily. **R-E**

CONVENIENT TAPE-REEL STORAGE

A good way to hold tape reels in pairs is to use spring-type garment-holding clamps. These clamps are in pairs with a center pivoting rod. Large manila envelopes make excellent holders for single reels of tape with incomplete programs if you cut off the top of the envelope or fold it over to make it the proper size for the reel of tape. Jot the contents of the reel on the outside of the envelope, noting starting and stopping point of a particular program. There is plenty of space for making all required entries, and erasures can be made easily.

Discarded envelopes will serve this purpose as well as unused ones.—*Glen F. Stillwell*

COAX CONNECTOR HINT

When installing rf connectors on coaxial cable, excess heat can warp, melt or disfigure the polyethylene insulation covering the center conductor. You can prevent this and minimize the possibility of shorts by slipping a short piece of shrinkable tubing between the braid and the dielectric. The heat from the soldering operation shrinks the tubing

uniformly so the insulation holds its shape and does not melt.—*Richard Mollentine, WAOKKC*

MORE HEAT AT THE TIP

A stubborn soldering gun that requires frequent tightening of the nuts to maintain sufficient heat in the tip may be cured by tinning the back ends of the tip that fit into the body of the iron. The tinning will give improved electrical connections between the barrels and tip, and slow down oxidization at these points.—*Robert E. Kelland* **R-E**

THE "ULTIMATE"

R-E's NEW FM

by KENNETH E. BUEGEL

FM TUNERS FOR STEREO RECEPTION have steadily improved in quality. Today's audiophile can select a solid-state unit with specifications which were never achieved before.

All tube designs, all the older transistor designs, and the present FET designs use an agc technique known as reverse bias in which a negative bias is applied to either a grid or base to reduce the output current (and gain) of the device. While reverse bias works well with devices such as tubes and certain FET's, which can operate at zero or negative bias, it fails when used with ordinary transistors which must always have some forward bias to maintain operation.

Strictly speaking, the forward bias on the transistor was only reduced until the gain decreased at some very low collector current. Unfortunately, this meant that the base-emitter junction could be a very good rectifier for the same strong signal

that was producing the bias. Thus this biasing technique was a failure in operation and the setting was ripe for the introduction of FET's.

The use of a different type of transistor, however, solves the overload problem. This transistor is known as the "forward agc" type—one in which gain reduction is caused by an increase in the forward bias applied to the transistor as shown by the curve of Fig. 1. Note that at collector currents of only 2-3 mA the power gain of the device is maximum, but when the current has increased to a higher value the power gain may even become negative, with less output than input.

Of course, since the base-emitter junction is heavily biased, a strong signal cannot be rectified at this point. Thus, in the FM-1 tuner described here, we can apply a signal of 0.2V rms to the antenna terminals without degrading performance.

Although forward-agc transistors can successfully compete with FET's under extremely strong signal conditions, they deliver superior performance when handling very weak signals. We get this kind of performance by close impedance matching between the coupled circuits, which implies maximum power transfer. With an antenna impedance of 300 ohms it is simply not possible to transform this upwards to the higher values required for field-effect transistors. Circuit configurations capable of this transformation such as transmission lines and tuned cavities are bulky and of prohibitive size.

The transistors used in this design present a much lower input impedance and consequently more use-

ful power is transferred. The result is a tuner with high sensitivity and an extremely important side benefit—no shielding is required in the rf section. Whereas a stray coupling capacitance as low as 0.1 pF (16,000 ohms @ 100 MHz) can couple a considerable amount of power between two high-impedance circuits, the same stray capacitance effects little power transfer between impedances nearer 1200 ohms.

Remember also that any electrostatic shield placed over an inductance must be much larger than the coil diameter to prevent drastic reduction of Q values and inductance since the shield acts as a single shorted turn coupled to the inductor.

The crystal filter impedances in the FM-1 are closely matched to reduce phase non-linearity and preserve good stereo separation.


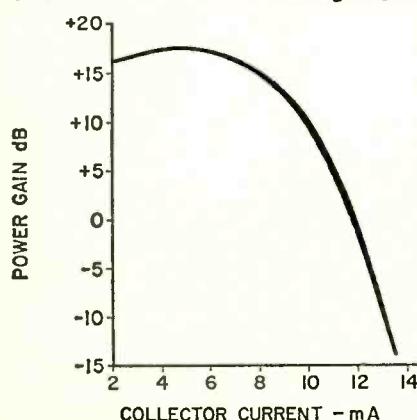


Fig. 1—Curve of foward-agc transistor. Low collector currents yield high gain.

FM-1

Using the detailed alignment procedure that appears on these pages, the reader should be able to achieve or improve the

20 db Quieting Sensitivity	1 μ V
30 db Quieting Sensitivity	1.4 μ V
50 db Quieting Sensitivity	3.9 μ V
Capture Ratio	1 dB
AM Suppression	60 dB
Harmonic Distortion	0.5% (measured at detector output)
Hum and Noise	less than -70dB
Spurious Response	less than -90dB
Image Rejection	less than -90dB
Half i.f. Response	less than -80dB
Adjacent Channel Selectivity	-70 dB
Overload Sensitivity (for 1% distortion)	0.2V rms

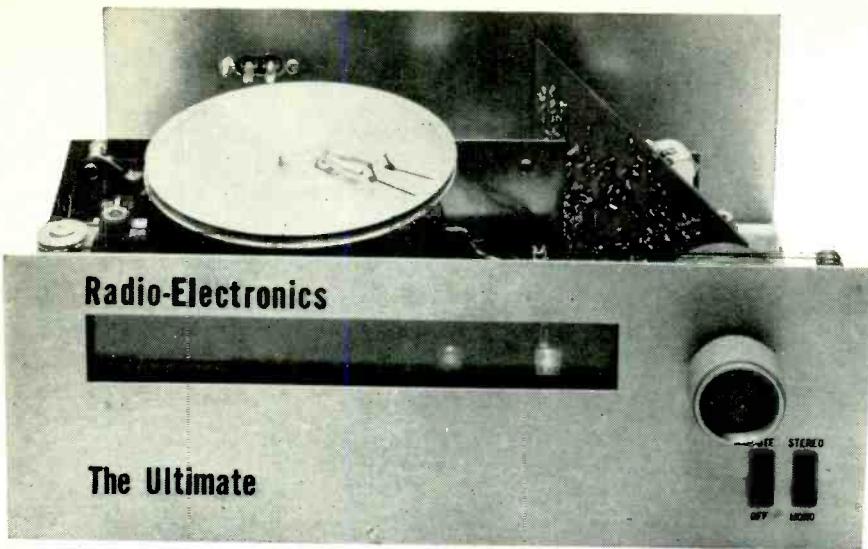

STEREO TUNER

On weak signal reception, forward bias to Q1 and Q2 (Fig. 2) is supplied through R22 and R24 from the junction of R21 and R25. Adjusting R25 sets the bias for highest sensitivity. As signal strength increases, the base voltage on Q5 becomes more positive until, at a higher signal level, Q5 is providing bias to Q1 and Q2.

The resistance in the collector circuits of Q1 and Q2 is low to prevent saturation at these higher collector currents. The base connections to L2 and L3 provide maximum power transfer from the tuned circuits. Q3 is a dual-gate FET mixer with the rf signal applied to gate 1 and the local oscillator signal to gate 2.

Transistor Q6 is arranged to provide a low distortion oscillator signal to the mixer. An additional Zener regulator prevents frequency variation while the R28-C24 combination re-

moves any Zener noise. The base of Q4 is matched to the mixer output by a tap point formed by the capacitive division of C14 and C15.

Transistor Q4 provides the 500-ohm output impedance for the first crystal filter. Each filter requires about 5 pF at the IN terminals to give the specified bandpass. For F101 (Fig. 3) this capacitance is the length of shielded cable connected to Q4. For the second filter it is the output capacitance of IC101.

Transistor Q101 amplifies the signal and applies it to Q103 and IC101. The gain of Q103 and Q104 is just enough so that the i.f. voltage rectified by D101-D102 will provide further bias to the transistors only when the signal is well past the point of maximum noise reduction, but long before the signal level reaches the overload level. The design gain of the Q103 and Q104 stages is centered within this range.

All i.f. transistors are of a special type with the emitter lead placed between the base and collector leads. This lead arrangement prevents unwanted coupling (and phase shift) between output and input of each stage.

The ratio detector, T102, has a linear bandwidth of 500 kHz and contains the diodes within the housing. Because of T102's bandwidth, alignment is simple, and can be done almost as well with off-the-air signals as with a signal generator.

The tune indicator lights when the signal is tuned correctly. The voltage at R125 will be about 1.1 V positive without a signal and rises to nearly 1.3 volts when even a weak signal is tuned in. R126 provides an adjustment for this voltage discrimina-

tion. When the voltage at R125 rises in the presence of a signal, Q105 is turned on, in turn saturating Q106 and Q107. LM101 in the collector circuit of Q107 lights to indicate correct tuning. A S202 contact (Fig. 4) is wired to the turn-on bias for Q107. If S202 is set to the stereo position this bias will be clamped to ground by Q207 unless the 19-kHz pilot signal has resulted in turning on the stereo indicator, LM201. Thus if the MUTE switch is on, and S202 is set to the stereo position, only stereo signals will be heard.

Since Q107 saturates at this time, a contact on S201 may return source resistors of Q210 and Q211 to ground, allowing the audio to appear at the output jacks.

The collector voltage at Q106 also saturates Q208 in the stereo indicator circuit, allowing an indication only when stereo is tuned in.

The detected composite signal feeds the high-impedance input of Q201. T201 and C203 present a high impedance in the emitter circuit of Q201. The output voltage appearing across R201 is low in 19-kHz components. T202 and C202 are tuned to 67-kHz to eliminate SCA interference at the stereo outputs. The 19-kHz pilot signal appearing across T201 is amplified by Q203. T203 and T204 are tuned to the 19-kHz signal. The input to emitter follower Q204 is a very pure 19-kHz signal which provides superior lock-in of the oscillator even on extremely weak signals. Since the voltage at the emitter of Q204 is a low impedance it is used to drive the pilot detectors, D201 and D202, as well as synchronizing Q209.

The rectified pilot signal satur-

Specifications

following figures. The specifications will be explained further next month.

Multiplex Separation 45 db mid-frequency
35 dB @ 50 Hz
30 dB @ 10 kHz

Output Level adjustable up to 1Vrms
Output Impedance approx. 20,000 ohms
Distortion 1%, 1000 Hz, 75 kHz deviation

SCA Suppression 48 dB
Hum and Noise 45 dB

—60 dB (below reference IV output with 19 and 38 kHz components notched out)

ates Q205, which in turn provides a turn-on bias to Q206, the stereo lamp driver. The emitter of Q206 is in series with Q208. Therefore, the indicator will not light unless Q208 is also turned on. Q208 is driven by the voltage appearing at the collector of Q106, and this voltage will bias Q208 only when a signal is received. The stereo indicator lights only when a stereo signal is received. There are no false indications between stations.

Locked oscillator Q209 can only operate when pin 6 of T205 is returned to ground by the saturation of Q206. T206 in the collector circuit is

tuned to 38kHz and drives the balanced detectors D203-D205 and D204-D206. Balanced detection reduces the 38-kHz components which can appear across the de-emphasis networks, R224-R225-C219 and R226-R227-C220.

The gates of output amplifiers Q210 and Q211 are returned to ground potential. Source resistors R230 and R231 are switched to ground to turn on and to +12 volts to mute. In muting, the audio output is reduced over 50 db. This switching voltage is taken from the collector of Q107, the TUNE lamp driver. The out-



put of each channel may be adjusted to any voltage up to 1V rms by the output controls in the drain circuits of Q210 and Q211.

Resistor R204 selects the amount of composite signal, minus 19-kHz and 67-kHz components, applied to the switched detectors. This composite output contains the L + R signal at 50-Hz to 15-kHz, as well as the L - R sidebands at 23-kHz to 53-kHz. These sidebands may be attenuated by multi-path reception as well as phase distortion in the i.f. strip. The detector transformer used in the FM-1 has a linear bandwidth of 500-kHz to minimize this distortion. However the tuner alone is not able to compensate for all possible causes of L - R sideband attenuation. Therefore C204 should be installed on the following basis: use the .02- μ F unit if this multiplex board is *not* used with the remainder of the FM-1, or if all your useable signals originate more than 30 air miles from your receiving location. Use the .05- μ F capacitor when the multiplex is used with the FM-1 and the stations are both local and distant.

The power supply provides +14.6V for LM101 and LM201 and regulated 12V for all other circuits. Q212 functions as a capacitance multiplier; the +14.6V has less than 5 mV p-p ripple. D210 provides a regulated output from Q213. If there is excessive Zener noise you can add a simple R-C network to eliminate it.

Diode D209 serves only one function; to prevent destruction of Q213 in case of a wiring error or accidental short during testing. Without D209 any short would cause the charge in C232 to be placed directly across the base-emitter junction of Q213. The resulting current flow would destroy this transistor. With D209 in place any short drains C232 of its charge at the cost of only a momentarily increased dissipation in Q213.

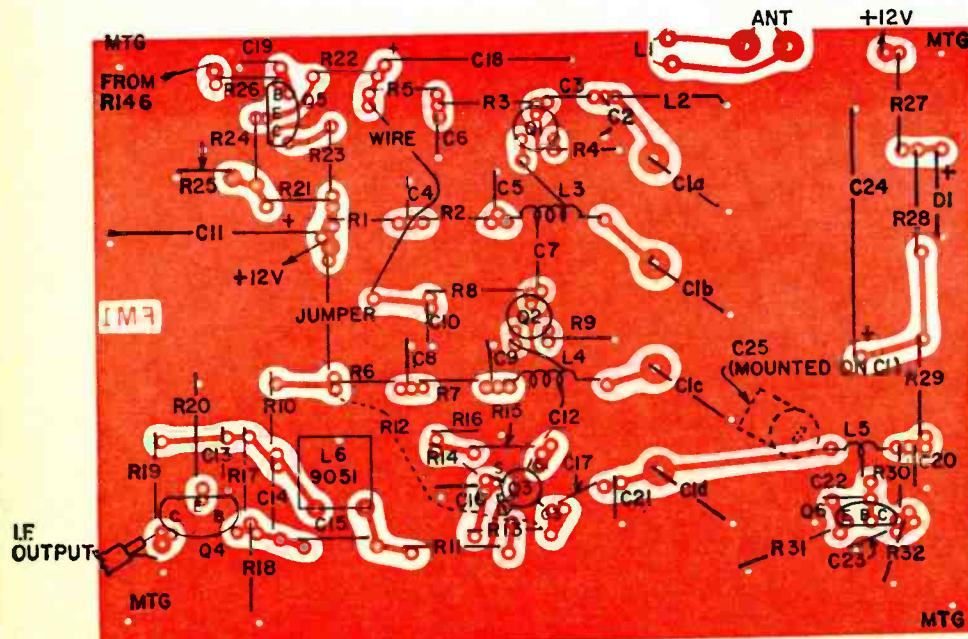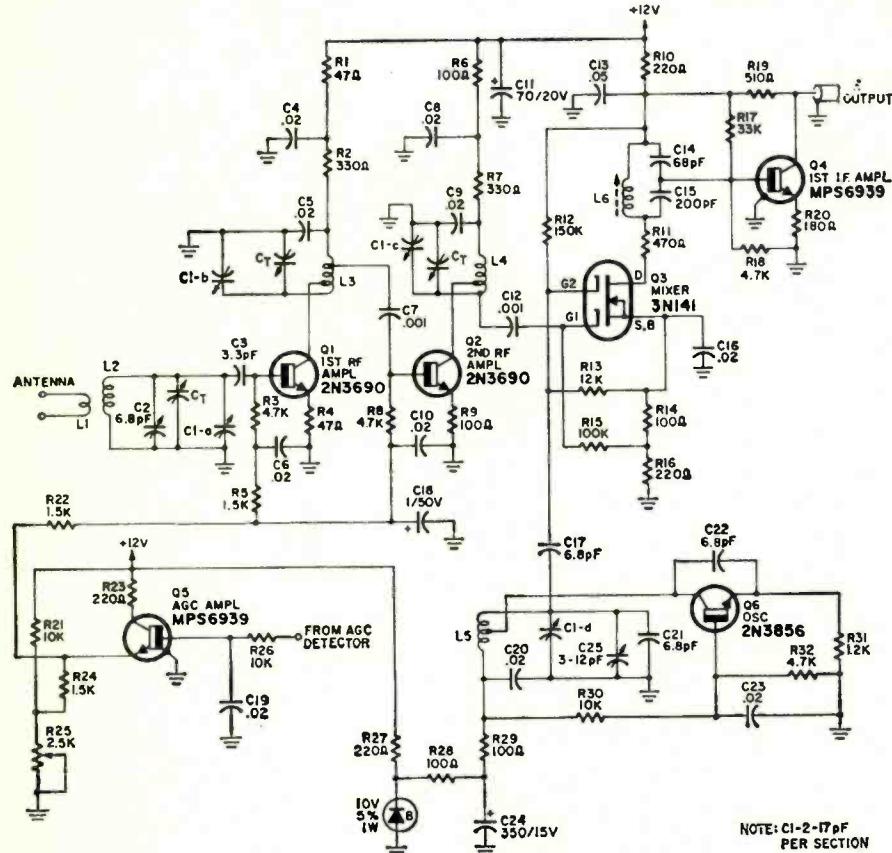Three circuit boards are used in the tuner. These boards are the rf head, i.f. strip, and multiplex and power supply boards. Each board is completed according to the sequence shown. When all boards are wired,



they are temporarily mounted in the chassis for alignment. After alignment is complete, the dial panels are mounted and the unit is ready for final wiring and assembly.

Alignment procedure

Set dial to 88 MHz. Loosen the dial drum set screws and slide the drum off the shaft. Using small pieces of masking tape, tape the dial cable in place so it cannot become tangled.

L.F. STRIP

1. Set generator for a sweep width of about 300 kHz, centered

about the 10.7 MHz. If possible, use post marker adding to set two markers; one at 10.6 and the other at 10.8 MHz. Set the generator output level to about 200 μ V. Connect the output cable ground to the edge of the i.f. strip near the input to F101. Clip the "hot" lead to the insulated cable jacket leading to F101; DO NOT tie the hot lead directly to the input pin of F101.

2. Set the bottom (primary) slug of T102 for a symmetrical response with the top slug tuned off resonance.

The scope vertical input should be connected to the output lead from R121, and the horizontal input should be fed from the sweep voltage in the generator. Follow the generator instructions for connections and phasing procedures.

3. Next adjust the top slug (secondary) of T102 for best linearity between the 10.6 and 10.8 MHz markers. Do not retune the bottom slug.

4. Connect a dc vtm set on the lowest range between ground and the top end of R119. Slowly adjust the


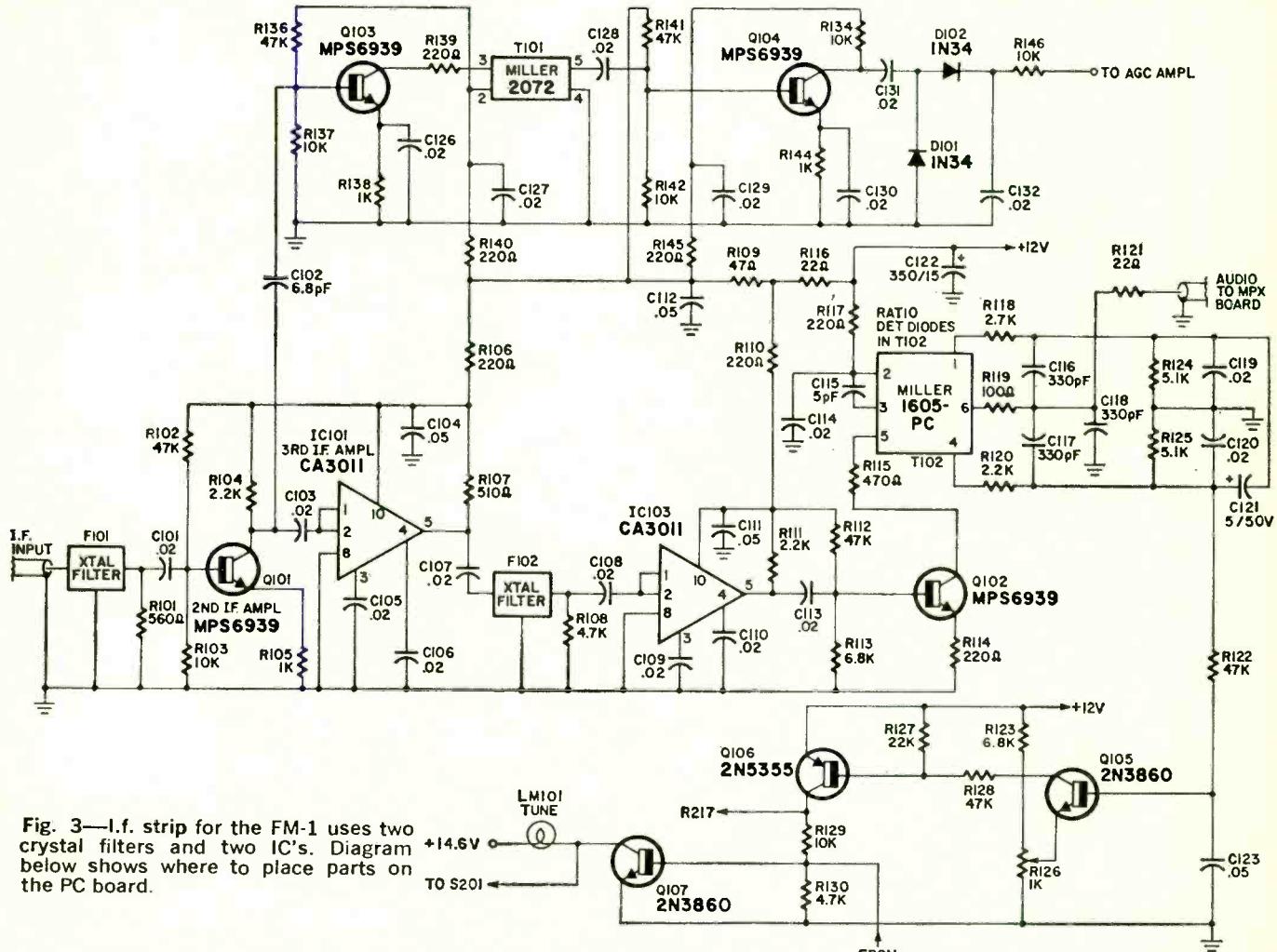


Fig. 3—I.f. strip for the FM-1 uses two crystal filters and two IC's. Diagram below shows where to place parts on the PC board.

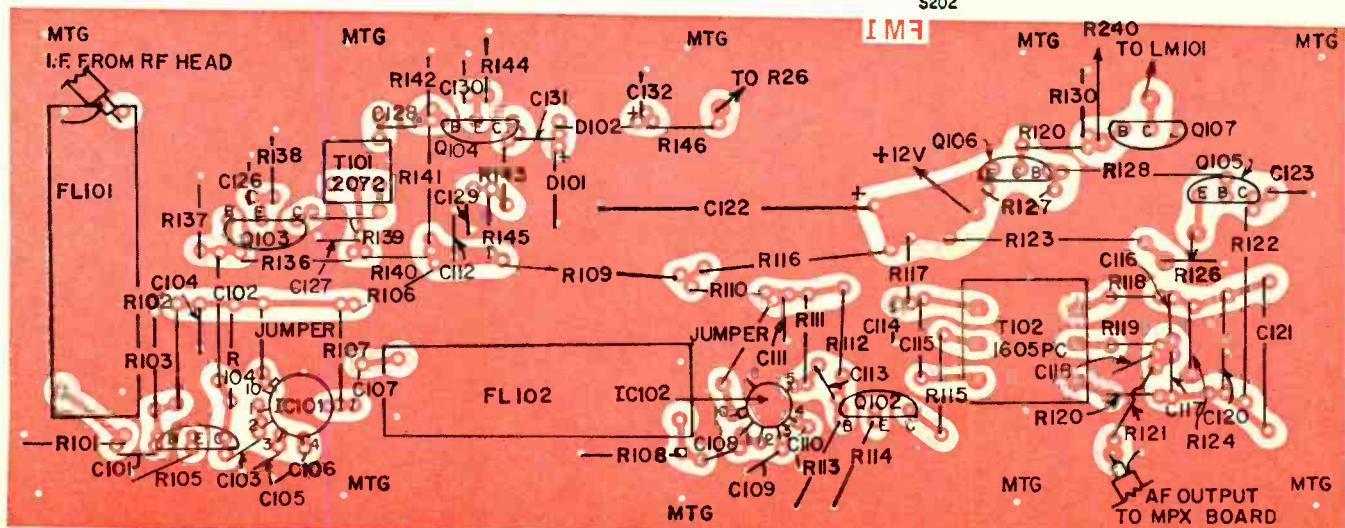

top slug of T102 for exactly zero volts. This should be a very small part of a turn.

5. Connect the vtm to the output lead from R146 and increase the generator output until you can read some voltage above zero. Tune T101 for a maximum reading. Reduce the

generator output and repeak T101.

6. Place a small ceramic-disc capacitor in series with the output lead of the generator and connect the capacitor to L4. Leave the vtm on R146. Increase the generator output and tune L6 for a maximum reading. Reduce the output and repeak L6



This completes the i.f. alignment.

RF HEAD

1. Set R25 to mid-position; connect a small amplifier and speaker to the output lead from R121. Set the generator output to 88 MHz with enough deviation so that an audio sig-

(continued on page 70)



Fig. 4—Multiplex decoder for the tuner and the power-supply components are mounted on the same PC board as shown below. D209 is a 40267 diode (mislabeled). Oscillator coil is T205.

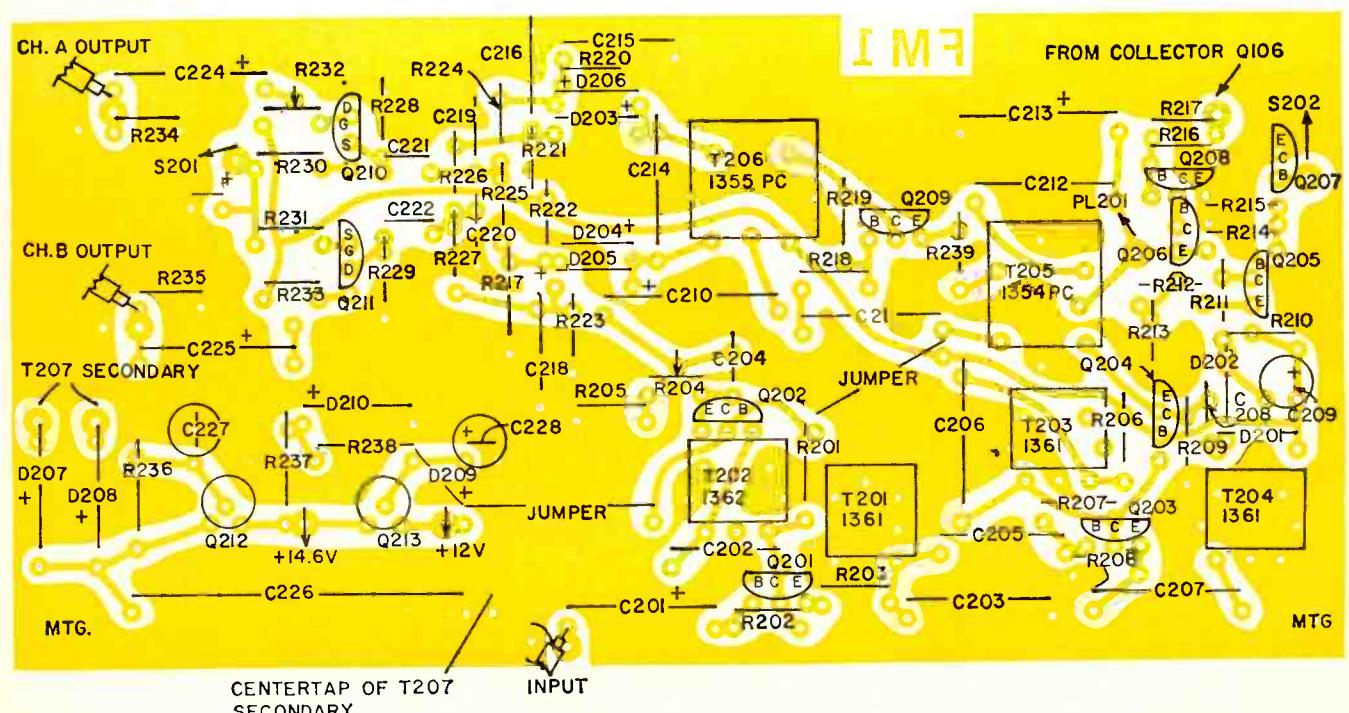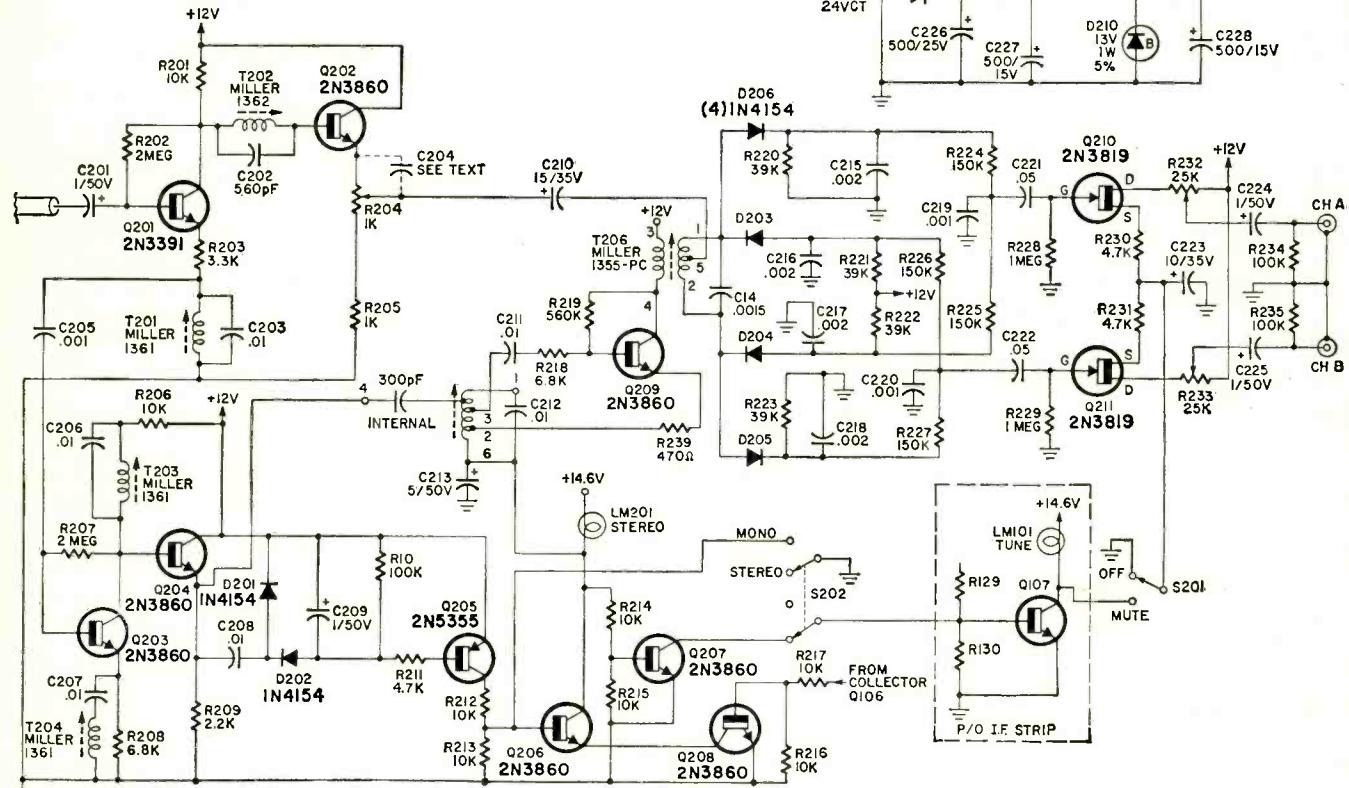

PHOTOGRAPHIC ELECTRONICS-'70

by JOHN R. FREE
Associate Editor

A narrow, invisible beam of modulated light penetrated the twilight near the United Nations building. Aimed through a group of reporters clustered around the ambassador's limousine, the beam caught him squarely in the chest as he stepped to the sidewalk. He paused; then, dodging questions, strode rapidly toward the UN. Now the beam was fixed on his back. Inside the small AIR unit pointed at him, computer circuits hummed . . . a servomotor whirred faintly, tracking him. . . .

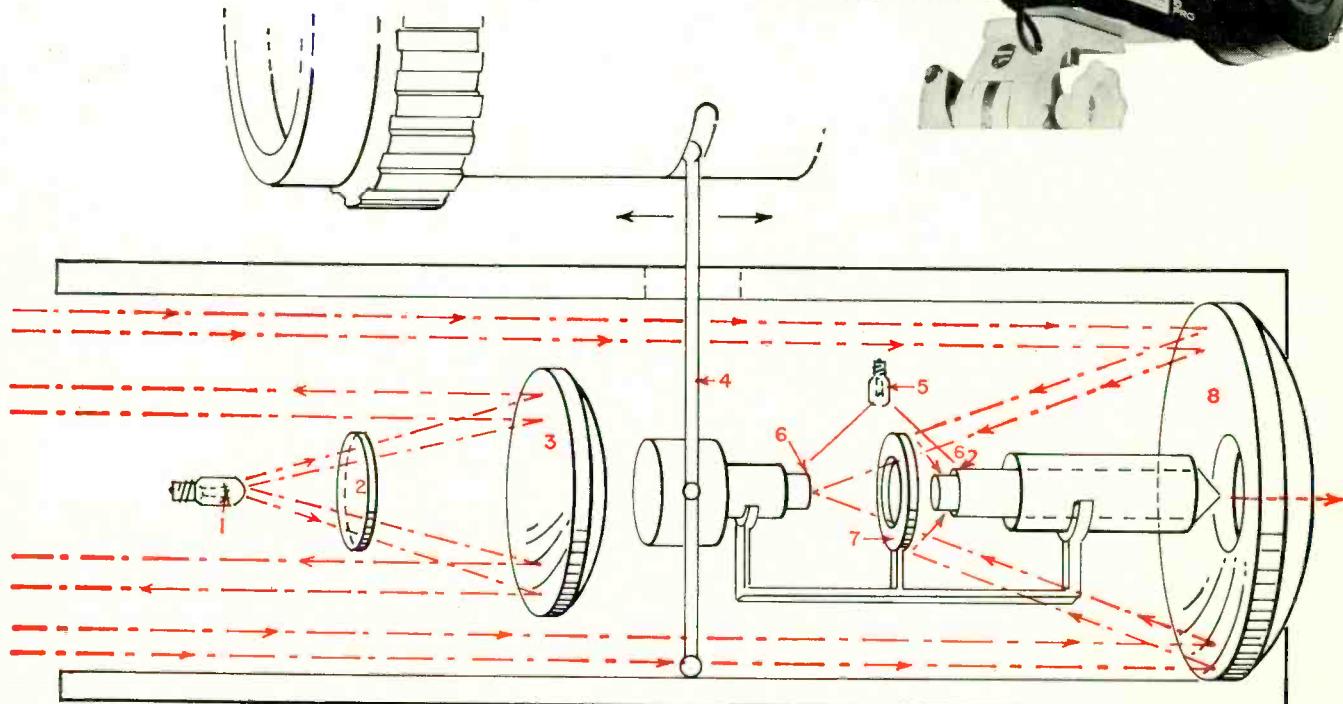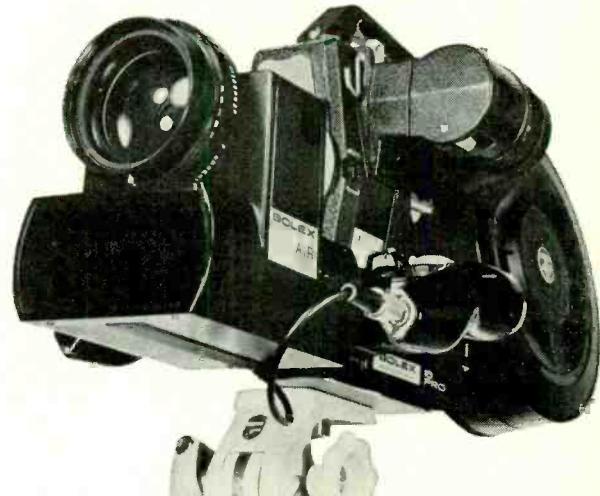

SOUND LIKE THE SCENARIO FOR A Hollywood science/spy thriller? Within a year, VIP's around the world may be "zapped" with invisible beams. The source of this international intrigue is Yverdon, Switzerland, where the Bolex AIR (Automatic Infrared Rangefinder) is being made.

The harmless beam comes from a 2-watt, 12-volt bulb in the AIR, whose function is to help newsreel cameramen keep their subjects in focus automatically. Variations of the AIR system may eventually be used for non-professional cameras.

The Bolex-made system, pre-

viewed at several photographic shows, will cost about \$700 when it reaches the market. The AIR shown in the photo is fitted to the Bolex 16 Pro, a newsreel camera with built-in power focusing. The 4 x 4 x 8-inch electronic and optical package guarantees accurate focusing between 5 and 80 feet. A 12-volt battery powers both the camera and AIR.

Projector and detector

To hit the camera subject with a narrow beam of modulated infrared light and receive the reflected radiation, the optical system shown in the diagram is used. A Schott glass infrared

filter (2) absorbs most of the visible light from the projector lamp (1), which is positioned at the focal point of a Mangin mirror (3). (This is a concave lens with a reflective coating on its rear surface.) The mirror curvature is designed so the infrared spot on a target 30 feet away is only 3 inches in diameter.

Part of the infrared light reflected from the subject strikes the larger receiving Mangin mirror (8). This light may be an extremely faint 10^{-14} watt, and of course is mixed with other light wavelengths—unwanted for AIR operation, but necessary to expose ordinary film. The

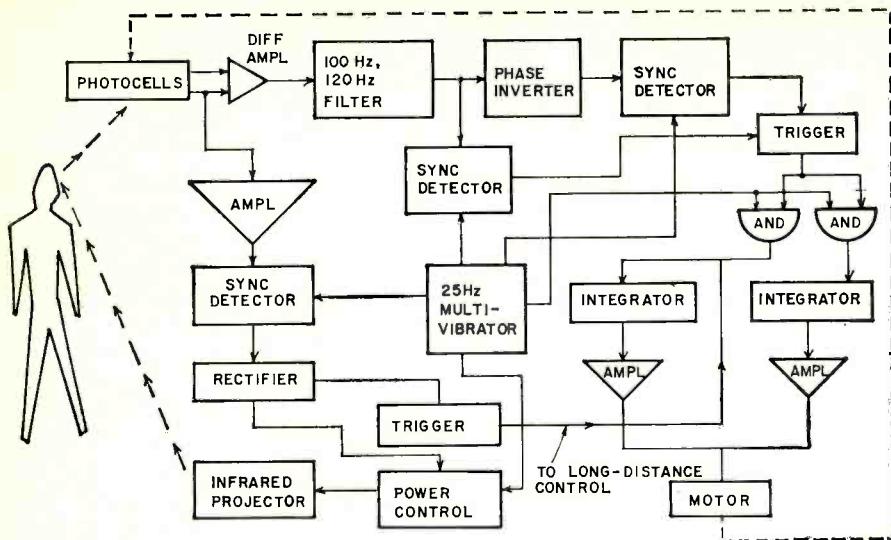


Fig. 1—Servoloop is formed by subject, mirror/photocell assembly and the circuit. Long-distance control sets lens to infinity when signal disappears.

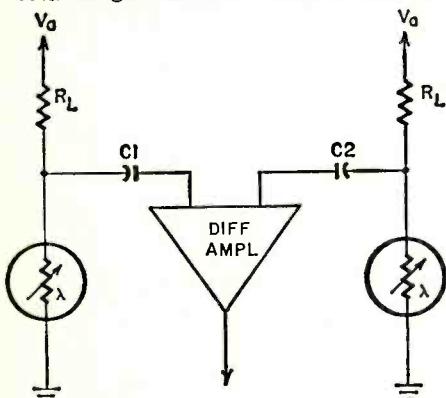


Fig. 2—Dc voltage in photocell circuit from sunlight is blocked by C1 and C2.

This image is directed toward a ring-shaped separator mirror (7) positioned between two infrared-sensitive photocells (6). The separator mirror/photocell assembly can move along the receiving mirror's axis, tracking the moving image.

When a camera-shy ambassador hurries away from the AIR, his image moves down the mirror axis, passing through the hole in the separator mirror and falling only on the left photoresistor. This unbalances the photoresistor/servo circuit (described later), which sends a signal to

camera lens into focus (4).

When the separator mirror moves into the correct plane with the image, some light passes through the separator mirror to the left photodiode and some is reflected to the right photodiode. With both photodiodes illuminated, the servomotor does not receive a drive signal. If the cameraman moves closer to the ambassador, or vice versa, only the right photodiode will be illuminated, and the mirror/photocell assembly will move toward the receiving mirror until equilibrium is achieved again.

Electronic servo circuit

Everything a cameraman points the AIR at emits infrared light, so the advantage of modulating the infrared projector is obvious: it makes the AIR's radar-like beam stand out from the infrared "chaff." Bolex selected 25 Hz as the central multivibrator frequency (Fig. 1) since at higher frequencies the lamp filament would not dim enough between pulses to provide a well-modulated beam.

Voltage generated in the photodiode circuits due to continuous light (sunlight, car headlights, etc.) is eliminated by capacitors C1 and C2 between the differential amplifier and photoresistor voltage divider (Fig. 2). Interfering illumination of 120 Hz (100 Hz in Europe) is filtered after the signal voltage is amplified. To operate the photoresistors in a fixed region of their response curve, a small "bias" lamp (5) shines on them. This lowers sensitivity, but improves accuracy.

Depending on which photodiode is illuminated, the differential amplifier output will be in or out-of-phase with the multivibrator. A phase inverter insures the sync detectors receive out-of-phase signals, so only one conducts when it receives in-phase 25-Hz pulses from the multivibrator.

After shaping in the trigger circuit, the signal turns on the proper AND gate. The pulses are then integrated, the voltage is amplified and, depending on its polarity, operates the servomotor to drive the mirror/photocell assembly forward or backward.

Incoming light to the photodiodes may vary at a ratio greater than 1:1000. The reflected 25-Hz signal, as we've mentioned, is a very small portion of the light reaching the photodiodes. But to keep this 25-Hz signal fairly constant, an automatic gain control circuit is used.

Bolex hasn't described this part of the AIR, but it appears that part of the return signal from the right photodiode is fed to this circuit when the subject is near and highly reflective. After detection and rectification, it is

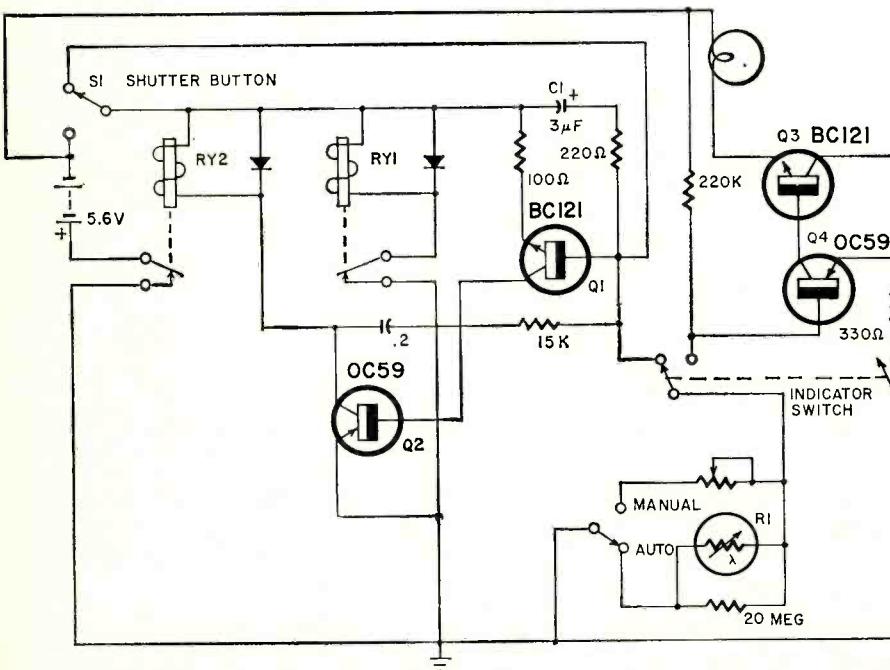


Fig. 3—Minox C works when S1 energizes RY1, opening shutter. C1 charges through photoresistor R1 until Q1 conducts, turning on Q2, which activates RY2.

larger Mangin mirror focuses light from the camera subject into a ring-shaped image that shifts along the mirror axis slightly as the subject moves away from or toward the AIR.

a servomotor telling it to move the mirror/photocell assembly down the mirror axis and "hunt" for the image missing on the right photodiode. Simultaneously, the motor moves the

used to control the light output of the projector lamp.

The servoloop formed by the mirror/photocell assembly, circuit and dc motor may look familiar if you've read about or used the autofocus slide projectors on the market. They usually use a mirror/lens arrangement to reflect a beam of light from the front of the slide to a spot between two photocells. If heat "pops" the slide slightly out of focus, the beam is deflected onto one of the cells, whose output operates a servomotor to drive the projector lens or slide holder into proper focus.

Minox C exposure control


Automatic electronic exposure control for 35 mm and other cameras is now old hat, but packing all the gadgetry necessary for the job into a $4\frac{3}{4} \times 1\frac{1}{8} \times \frac{5}{8}$ -inch ultraminiature camera—without using IC's—is no simple task. To squeeze all the hardware into their model C, Minox had to extend its length about $\frac{3}{4}$ inch beyond the B model. The miniature PC board for the Minox C requires very little space, but the 5.6-volt battery and electromagnets to operate the sliding double-blade shutter occupy about one-quarter of the case (see photo). The shutter-control circuit works with a fixed f/3.5 lens to expose the film from 7 secs to 1/1000 sec.

Despite its miniaturization, the exposure-control circuit is conventional, charging a timing capacitor through a cadmium-sulphide photocell (Fig. 3). When the shutter button (S1) is closed, electromagnet RY1 is energized, opening the shutter. Power is removed from RY1 an instant later when its normally closed contact opens. The shutter remains open.

Light falling on photoresistor R1 then begins charging C1 until a voltage level is reached where Q1 begins to conduct. This turns on Q2, which energizes RY2 and closes the shutter. RY2's contact opens and resets the circuit.

Like most electronically operated cameras, the Minox C also has a circuit to indicate when lighting conditions are too poor for a hand-held shot. To get this reading, the indicator switch is pressed and the lamp lights (through Q3 and Q4) if the exposure time would be long enough to require camera support.

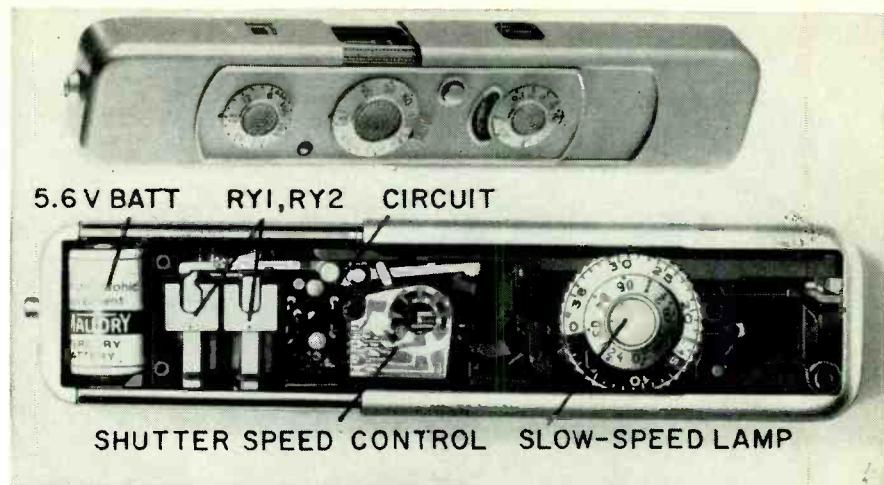A special miniature cadmium-sulphide photocell was specially designed by Clairex for the Minox. The cell was the only type available with an adequate slope of the conductance-vs-light curve at low resistance to be used linearly. A center-weighting effect is achieved with the photocell



by positioning it in a light well.

Oscillating shutter blades

A new circuit being used by Nikon in their movie cameras operates in conjunction with a photocell circuit to keep the diaphragm blades of a camera constantly in motion—although the motion does not register on the film.

Automatic exposure control for movie and TV cameras generally uses a photocell circuit that controls the current through the moving coil of a galvanometer. The diaphragm blades are mechanically linked to the moving coil. A problem with moving the diaphragm blades rapidly to compensate for changes in light has always been static friction between them. Also, since the galvanometer exerts little force, the blades can easily

Miniaturized electronic shutter control for Minox C fits in $4\frac{3}{4} \times 1\frac{1}{8} \times \frac{5}{8}$ " case.


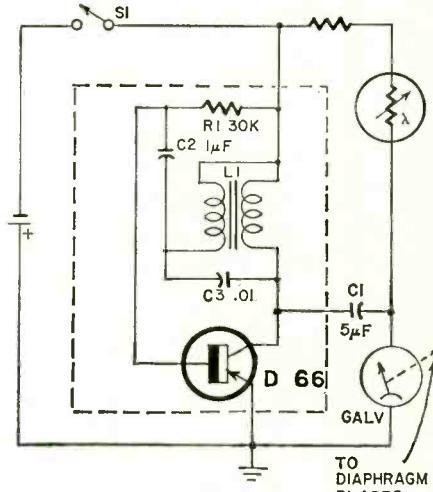


Fig. 4—Oscillator circuit puts ac current on galvanometer, vibrating blades.

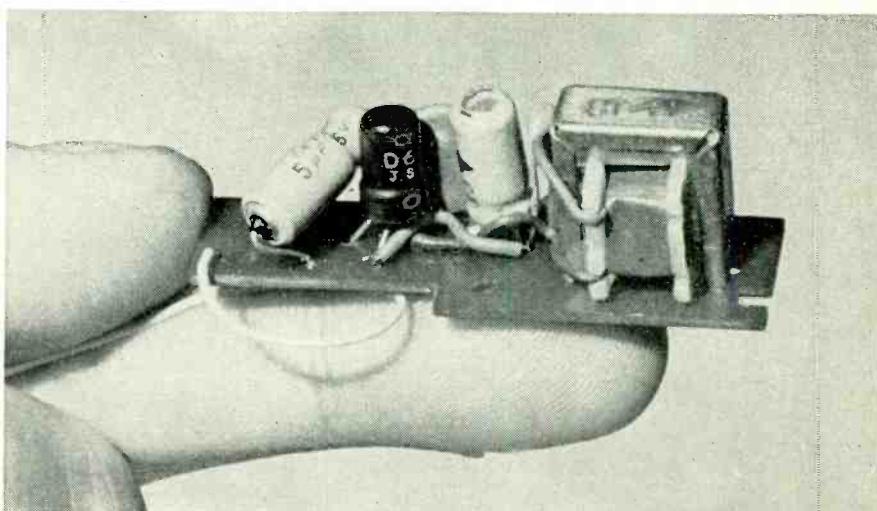

be jammed if foreign particles increase the friction between them.

The circuit used by Nikon (Fig. 4) provides an oscillating current that is superimposed on the direct current passing through the galvanometer. Component values in the circuit produce an oscillation frequency of about 200 Hz, and the circuit, minus the galvanometer and photocell, is mounted on a miniature PC board

Components shown in dashed-line portion of circuit above and C1 are on this small PC board.

(see the photograph above).

At 200-Hz, the oscillation of the moving coil cannot register on the film, and the frequency is greater than the natural frequency of the diaphragm blades. As a result, jerky movement of the blades is eliminated and jamming is prevented.



WHILE MODERN DIGITAL COMPUTERS use thousands of transistors, diodes and other components, the number of circuit types are few. Logic functions are performed by repeatedly using certain circuits, in series or parallel combinations, to perform the required tasks of counting, sorting and routing signals, and of modifying binary representations as needed.

Since logic circuits are not complex, they are easily assembled. Thus, if you build your own you not only learn the over-all circuit function, but get better acquainted with the function of individual components and the logic which applies to their use. With chips and modules it is almost impossible to acquire a true understanding of complete circuit makeup and its various functions.

Switches and gates

Most computer logic circuitry has switching functions. Signals are gated and routed to conform to preset conditions. Since a switch is either closed or open the two states are related to 0 and 1 (the binary system). Steady-state or pulse-type signals can be used to represent logic 0 or logic 1. If a positive voltage is selected as representing logic 1, then the absence of a voltage, or a negative voltage, represents logic 0. Similarly, if a negative voltage represents 1, logic 0 is either a positive voltage or no voltage. In the initial design of a computer, either a positive or negative signal is selected to represent logic 1.

Diodes have the advantage of forming simple and inexpensive logic circuitry, though transistors provide signal gain where needed and can also alter logic by phase inversion, as shown later. If you construct the circuit shown in Fig. 1 you can observe the function of two basic, and important, logic gates. Diodes other than 1N34 types can be used as long as they have a good front-to-back ratio. Use a vtv or a 20,000-ohms-per-volt meter for output signal observations.

While pulse-type signals would normally be used for this circuit, its function can be readily observed with steady-state signals. The type logic obtained with this circuit depends on whether we select a negative or a positive signal to represent 1. Initially, let's assume that a positive signal is logic 1 and a negative signal (ground) is 0. Set both spdt switches so inputs A and B to the diodes are at ground-voltage level. This now represents 0 input at A and B.


Now throw the A input switch to the positive-signal input. Note that a reading is obtained at the output, representing a 1 output (positive voltage). Place the A switch at ground again and repeat the procedure for the B switch. Note that an output is obtained again. Note also that an output is obtained when both switches engage a positive input.

You have now observed the function of what is known as an OR gate (or switch). The logic is: If either A or B or both inputs are ap-


Easy-to-Build Computer Logic Circuits

by MATTHEW MANDL
CONTRIBUTING EDITOR

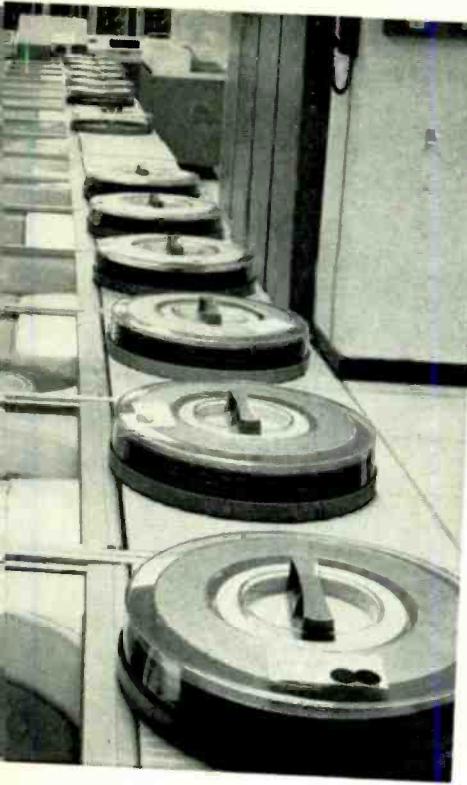All photos on these pages are of the RCA Spectra 70 computer system. Courtesy of RCA.



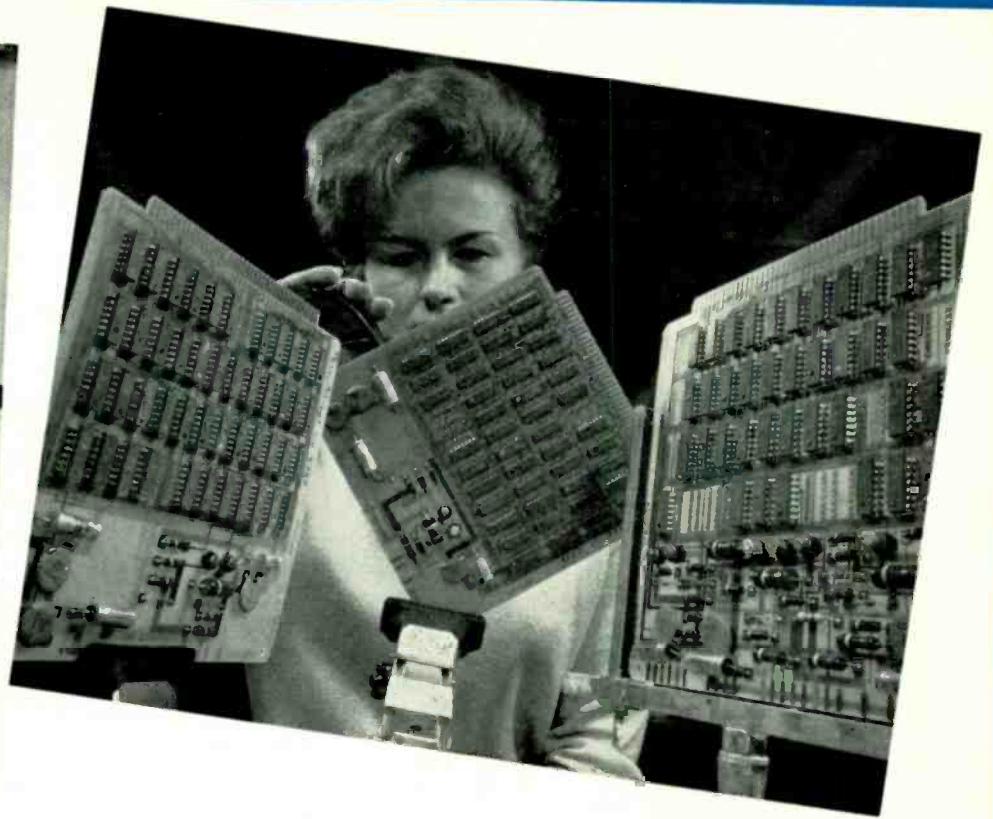Logic circuits are the basic elements of a computer.
Discover how they work by making your own—it's easy!



plied, an output is obtained. This OR circuit has a special symbol which is also shown in Fig. 1.


If we invert the logic 1 representation, we form an entirely different logic gate. Assume negative voltages represent logic 1 and place each spdt switch to the plus position for an initial logic 0 input at both A and B. The meter at the output reads a steady-state positive voltage, now representative of logic 0. Since a positive voltage appears at the input to each diode, both conduct.

If either the A or B input is changed for a logic 1 input (switching from positive- to negative-ground input), no appreciable voltage change is felt at the output, because one diode will still conduct. If, however, both A and B inputs have a negative voltage applied (logic 1's) both diodes stop conducting and the output voltage drops to the ground (negative) level, representing a logic 1 output of the circuit.

Thus, for this gate to produce an output when negative voltages represent logic 1, both the A and B inputs must be applied. Hence, this is called an AND gate or switch. Its special symbol is also shown in Fig. 1. This is sometimes also called a coincidence gate, because simultaneous inputs must be applied to obtain an output signal.

For more thorough understanding of the OR and AND functions

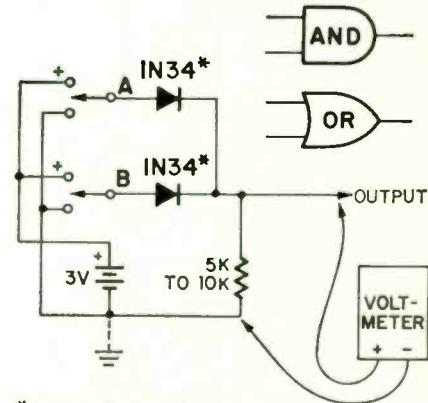reverse the diodes and the battery potential of Fig. 1. Now if you repeat the same test procedures you will find that an OR gate is formed when negative signals are used for logic 1's and



* OR EQUIVALENT


Fig. 1—OR function is shown when A or B or both inputs (switch to +) provide an output. AND function, or coincidence gate, requires both A and B switches in negative position for an output signal (negative voltages for a logic 1).

an AND gate function is obtained for conditions where positive signals are logic 1's.

In-depth analysis of factors relating to switching-circuit logic is done by using a special math known as Boolean algebra. In this system the OR and AND functions are indicated by using a plus sign (+) for the OR logic and a multiplication sign (\cdot)

for the AND logic. These signs are called *logical connectives* and if the circuit shown in Fig. 1 is used as an OR gate, the Boolean expression is: $A+B$, where the plus sign is read as OR (A or B). For the AND function, we can show it as $A \cdot B$, or use the algebraic method for displaying the multiplication, by placing the variables close together as AB .

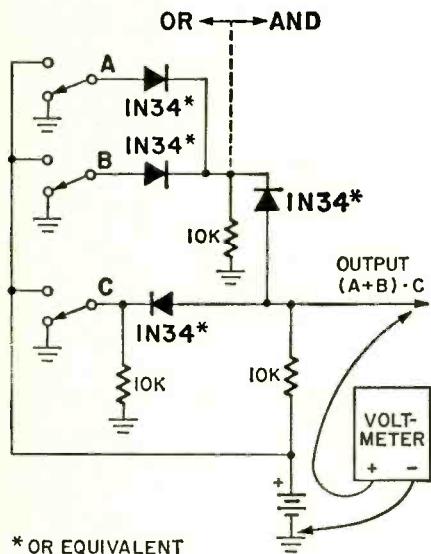More than two inputs can be used in the OR and AND gates of Fig. 1. If three inputs are used, for instance, the OR expression would be $A+B+C$ (assuming our third input is designated as a C). Other designations can, of course, be used. If we have a three-input AND circuit, with X, Y, Z inputs, the expression that



* OR EQUIVALENT

Fig. 2—Two-level circuit: two-input OR followed by two-input AND. Output requires A and B or both, plus the C input.

would be used is $X \cdot Y \cdot Z$, or XYZ .

Tables and levels

The logic of the OR and AND switches can be shown in "truth table" form, indicating the output obtained for given inputs:

OR gate		AND gate	
$A+B+C$	Output	$A \cdot B \cdot C$	Output
0 0 0	0	0 0 0	0
0 0 1	1	0 0 1	0
0 1 0	1	0 1 0	0
0 1 1	1	0 1 1	0
1 0 0	1	1 0 0	0
1 0 1	1	1 0 1	0
1 1 0	1	1 1 0	0
1 1 1	1	1 1 1	1

These tables show that an output is obtained for any one or more inputs to the OR switch, but an output is obtained from the AND gate only when all inputs are present.

One logic gating system can follow another to obtain specific functions, as shown in Fig. 2. This circuitry is a *two-level* type and could also consist of an AND circuit feeding an OR circuit. For the one shown we have a two-input OR gate followed by a two-input AND switch. Thus, since coincidence must occur at the AND gate inputs, we must have the C input and at least one or both of A and B. In this system we are using positive voltages for the logic 1's. Again, 1N34 diodes (or equivalent) are used.

Two-level logic in symbolic form is shown in Fig. 3. The OR-AND combination which produces an output of $(A+B)C$ applies to Fig. 2, and a C input must be present with either A

$(A+B)C$	Output
0 0 0	0
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

This table shows that only three input combinations produce an output: A and C, B and C, or all three inputs.

Transistor logic

Transistors, while more costly than diodes, provide amplification as well as additional logic functions not obtainable with diodes. For the circuit

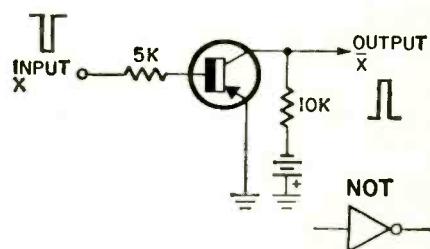
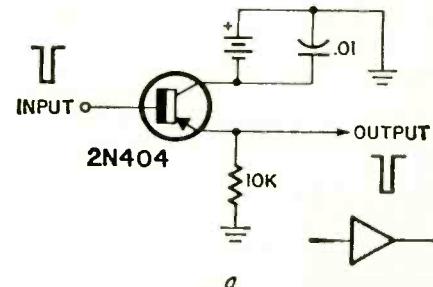


Fig. 3—OR-AND two-level logic symbol (top), AND-OR (middle) and the AND-AND-OR (bottom). Text shows $(A+B)C$ truth table.

Fig. 4-a—(right) Emitter-follower circuit keeps input signal phase and has no voltage gain. b—NOT circuit inverts phase.

or B (or both) for an output. The single AND gate feeding the OR circuit with an output of $(AB)+C$ is obtained if we reverse the diodes of Fig. 2 and also the battery potential, while still using positive voltages to represent logic 1. Now, C alone will produce an output, or A and B in coincidence, as well as all three inputs at the same time.

For Fig. 2 the C input could be replaced by another OR circuit to produce the logic $(A+B) \cdot (C+D)$, where at least one input from each OR circuit must be used to produce an output. With reversed logic we have the two AND gates feeding an OR circuit, as also shown in Fig. 3. Now the logic is $(AB)+(CD)$. Now either A and B or C and D will give an output.

Truth tables can also be constructed for these circuits, showing the logic which applies. The following example applies to the $(A+B)C$ system:

In Fig. 4-a, the output is obtained from the emitter resistor, hence the circuit is called an *emitter follower* (and compares to the tube-type cathode follower). If a negative signal (pulse or dc voltage) is applied to the base input line, the necessary forward bias is applied to permit the transistor to conduct.

Now, electron flow is from the negative terminal of the battery to the collector and emitter and down through the output resistor. Thus, a negative signal is developed at the output. While such a circuit has no voltage gain, there is signal current amplification. Note that the phase of the output signal "follows" that of the input—hence the term "emitter follower." The triangular symbol for amplifier is used as shown.

For the circuit in Fig. 4-b the output is taken from across the collector resistor. Electron flow is up through this resistor, producing a positive-signal output as shown. When we have such a phase reversal of the signal between input and output, the

logic which applies relates to the output signal *not* being in phase with the input signal. Hence this is known as a NOT circuit.

A line over a letter indicates the NOT function, as \bar{A} for "NOT-A" and $\bar{X} + \bar{Y}$ for NOT-X OR NOT-Y. A triangular symbol is used as with the amplifier, but a small circle denotes the NOT function. This logic function is useful when it is necessary to change a logic 1 to logic 0 or vice versa in computer circuitry design.

Diodes can be combined with transistors as shown in Fig. 5. Two diodes provide an OR gate input to an emitter follower in Fig. 5-a. Additional diodes could be included to provide more input lines. Such circuitry is known as diode-transistor logic and sometimes referred to as a DTL

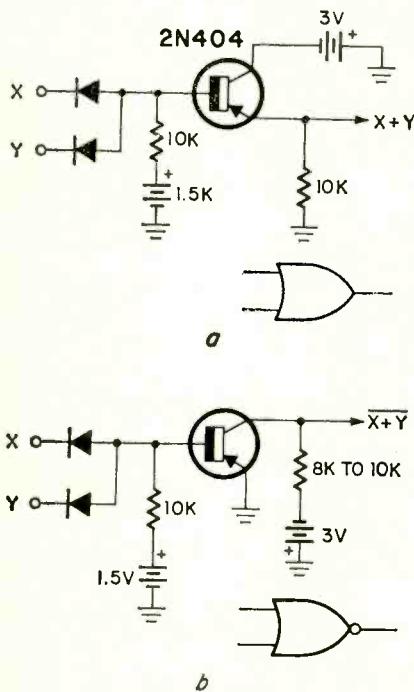


Fig. 5-a—DTL (diode-transistor logic) OR circuit. b—NOT-OR (NOR) circuit.

circuit. For the circuit in Fig. 5-b the output is from the collector and hence a NOT function is also obtained. Now we have the logic condition of NOT-OR, is commonly termed a NOR circuit. Note the OR-circuit symbol now has the small circle denoting the logic inversion function.

For the circuits in Fig. 5, a reverse bias is applied to the base circuit, thus cutting off transistor conduction. A negative signal above $-1.5V$ applied at either (or both) the X and Y inputs overcomes the reverse bias and causes conduction. Electron flow up through the collector resistor (Fig. 5-b) develops a voltage drop across it, producing a positive-signal output. The diodes could be replaced with re-

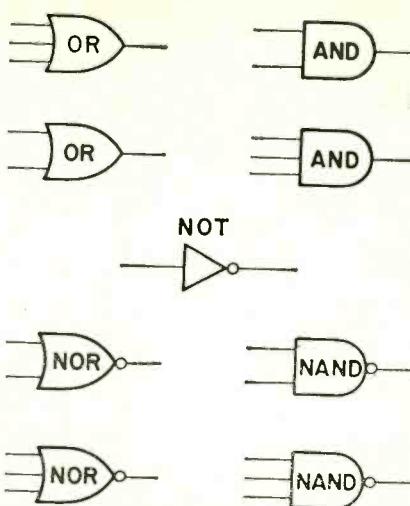


Fig. 6—Symbols for two- and three-input OR, NOR, AND, NAND gates.

Fig. 7—Below is a bistable flip-flop, which produces output only with input.


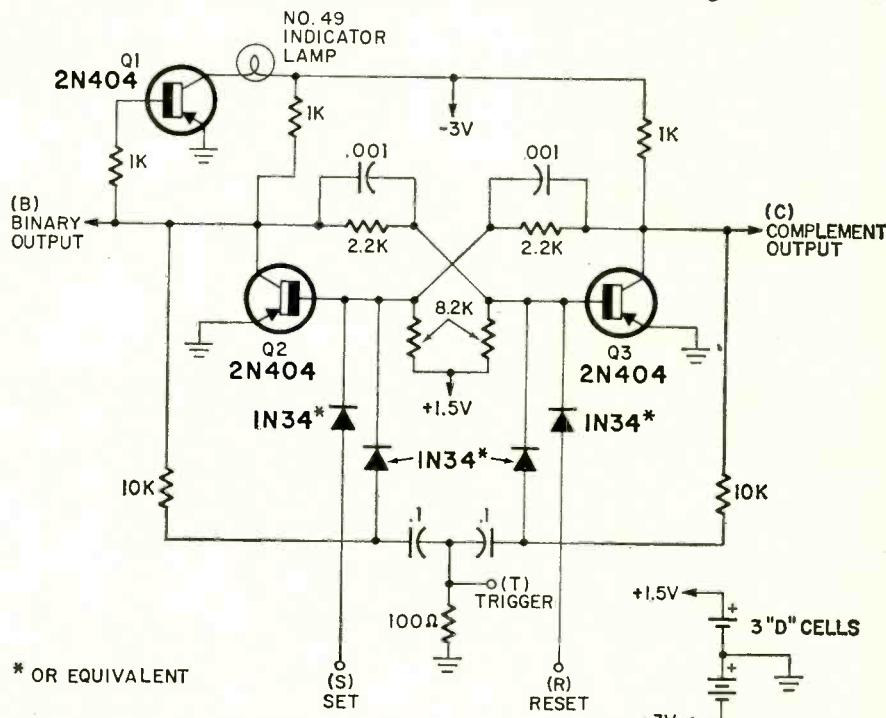


Fig. 8 (below)—Practical way to lay out circuit above on a small perf board.

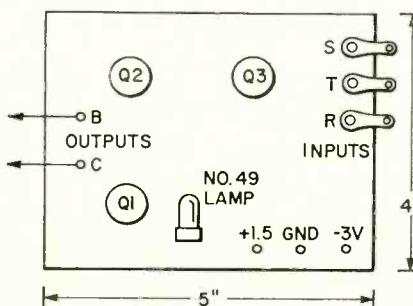

sitors for resistor-transistor logic (RTL) though diodes work better.

As with the diode logic gates discussed earlier, the AND function can also be obtained from these circuits. For Fig. 5-b the result is a NOT-AND

logic function, known as a NAND circuit. The symbol for the NAND circuit is shown in Fig. 6, where others are also shown for comparison.

The flip-flop

The flip-flop circuit performs many functions in a digital computer. A string of flip-flop circuits forms counters, temporary storage registers, accumulators (accumulating counts as basic addition), scalers (a form of binary division), and switches (providing "on" and "off" conditions as needed).

The flip-flop is a *bistable* device with one state representing logic 0 and the other logic 1. It is not a free-running oscillator and produces an output signal change only when an input signal is applied.

The flip-flop shown in Fig. 7 uses medium-switching 2N404 transis-

tors and operates with only three D-cells as shown. It has an extra transistor to drive the indicator lamp to show the logic 1 state of the flip-flop. The circuit can be built on a 4 x 5-inch panel as shown in Fig. 8. The output lines should be at the left so when several flip-flops are connected in series they will show binary magnitudes from right to left to conform to the arithmetic place system.

Note the polarity of the base diodes. These restrict the signals to positive voltages for representing logic 1. When the flip-flop is in the logic 0 state, transistor Q2 conducts while Q3 does not. At this time the binary (B) output line is less negative than the complement (C) output line, hence it can be considered positive with re-

spect to the other.

When power is first applied to a flip-flop it may assume either the 0 or 1 state, depending on which transistor conducts initially. Hence all computers reset all flip-flop stages to 0 immediately after power is applied. If your flip-flop indicator light goes on after you connect batteries you will have to reset it.

Use a jumper connected to the positive terminal of the battery and apply a voltage momentarily to the reset (R) input line. If the circuit has been assembled properly, the indicator light will go out. The positive voltage applies a reverse bias to the base of Q3 and causes it to stop conducting. Now the high negative potential at the collector of Q3 is felt at the base of Q2, permitting the latter to conduct.

Apply the positive voltage to the set (S) line and Q2 will stop conducting. Now the indicator light goes on, indicating the second state (logic 1) has been reached. Note that additional applications of positive signals to the set line have no effect.

Now apply the voltage to the reset line to change the stage to logic 0 again. Now note that additional voltages applied to the reset line have no effect. Voltages applied to the trigger (T) input should successively turn the flip-flop to the 1 and 0 states. (It may be necessary to apply the positive voltage quickly to imitate a pulse input for proper triggering.)

When two or more such flip-flop stages are connected so one feeds the other (Fig. 9-a) a counter is formed. Make sure the signal output from the B line is coupled to the T input of the next stage through a coupling capacitor as shown. (Ground connections must be common for each stage.)

Positive voltages applied to the trigger input of the first flip-flop (FF1) will cause the stages to count in ascending order in binary form. Thus, one signal entry into the first flip-flop will set the first stage to 1, with the indicator light on, represent-

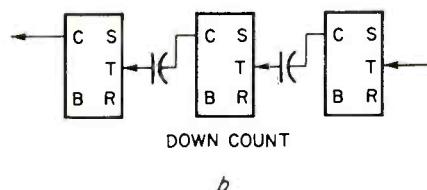
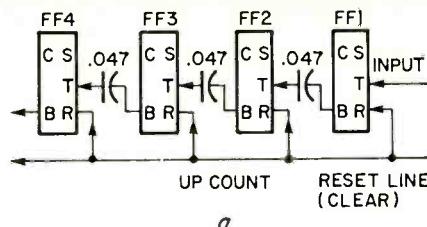


Fig. 9-a—Connecting flip-flop for count up. b—Count-down flip-flop circuit.

ing 0001. Another pulse entry at FF1 shuts off the indicator light of the first stage and the second stage goes into the 1 state, representing number 2 in binary: 0010. The third entry into FF1 sets the counter to 0011 for 3. The fourth shows 0100, the fifth 0101, the sixth 0110, etc. up to the maximum count, which is limited by the number of stages used. Four flip-flops will count up to 15 (binary 1111).

A down counter is formed by taking the complement (C) outputs and feeding them to the T inputs of successive stages as shown in Fig. 9-b. If each flip-flop is set to 1, successive inputs to the first flip-flop will reduce the count progressively. (In some diagrams the C and B outputs are designated as 1 and 0.)

The use of AND and OR gates with a counter is shown in Fig. 10-a. This combination forms a *decade counter* that will count only up to 9 and will trigger to 0 at the count of 10. Also, at the count of 10 the next stage is triggered to its logic 1 state. Decade counters are useful in data processing and each counter accumulates counts in base-10 fashion but still operates in basic binary mode. At the count of 9 the stages hold 1001

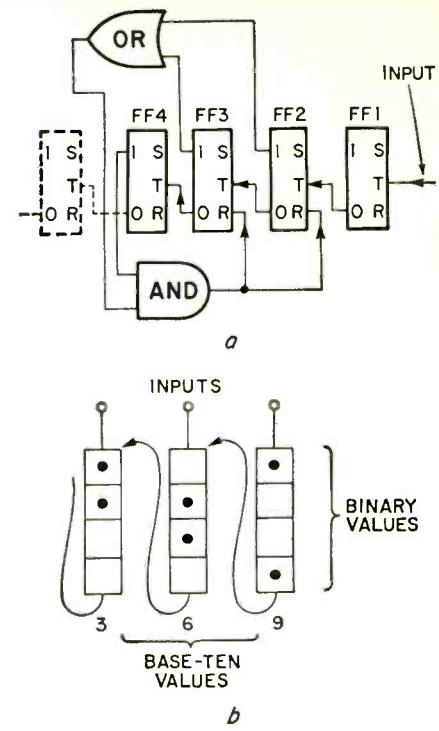


Fig. 10-a—Decade counter triggers at 10 count. b—Three decades set on 369. (binary). Normally the entry of another logic 1 input to the counter would result in the binary number 1010 (10_{10}). The on circuit, however, feeds the AND circuit and resets the second stage from the right to 0 and is also instrumental in clearing the fourth stage which, in turn, trips the next decade count to the 1 state.

In Fig. 10-b three decade counters are shown, holding the number 369. Note the first counter (at the right) holds binary 1001 which represents 9. The next counter holds binary 0110 (6) and the left counter contains 0011 (3). If another pulse were entered in the right-most counter, it would trip to 0 and send another pulse to the center counter, changing the latter to 7. Now the count would be 370 and the system would have added an additional 1 which was entered to the existing number.

R-E

TOOLS FOR ELECTRONICS

by TOM HASKETT

This issue, starting on the facing page, concludes our series of articles on soldering tools for electronics. It is the third part of our description of soldering tools. This month we will also start a series on nutdrivers. We believe you will find all of this material a handy, practical addition to your R-E Reference Manual.

If you wish, you can purchase a special hardcover binder to keep your Reference Manual pages together. It has a dark blue fabric cover and is gold stamped Radio-Electronics Reference Manual. The cost is \$1.00, postpaid. Order from N. Estrada, 17 Slate Lane, Central Islip, L.I., N.Y. 11722.

Iron and pencil accessories

You cannot simply lay an iron or pencil down on the work surface, for it can burn something or injure someone. Most people use a **holder** (also called a **stand** or **cradle**), as shown in Fig. 12. Some have a solder cup at the bottom, so the tip stays tinned.

Keeping the tip of a pencil or iron clean is another continuing task. You can use a rag, but if you do a lot of soldering it's convenient to use a **tip cleaner**, shown in Fig. 13. It's merely a wet sponge in a water well, and requires only one hand to clean the tip.

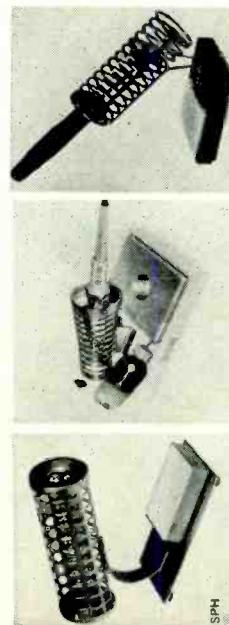


Fig. 12—*Three soldering iron holders that help make life a little easier. Left, Wall SPH. Center, Hexacon 890. Right General Electric 1197.*

SPH

cup at the bottom, so the tip stays tinned.

Keeping the tip of a pencil or iron clean is another continuing task. You can use a rag, but if you do a lot of soldering it's convenient to use a **tip cleaner**, shown in Fig. 13. It's merely a wet sponge in a water well, and requires only one hand to clean the tip.

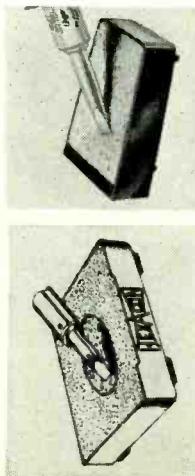


Fig. 13—*Two ways to keep soldering iron tips clean. Left is Hexacon model 812. Right is Ungar 400, Kleen-Tip.*

Other techniques

One very unusual soldering tool—a gun which contains a coil of solder which you can feed out into the joint—is very useful for one-hand jobs.

If you have to do some soldering in the field, away from an ac power line, you have a problem. The answer is a field iron, clamped across an auto battery. Models are available (Fig. 14) to work on 12 or 24 volts, and they come with battery clamps.



Fig. 14—*When you have to solder away from any ac outlets try a battery powered iron. The Weller TCP. 12 is shown.*

current to the probes. Sometimes a single probe is used together with a ground return connection.

Other specialized soldering methods are used in production work: high-frequency induction soldering, dip soldering, oil-path soldering, ultrasonic soldering and oven soldering. These highly specialized techniques are seldom used in the electronics fields covered here. R-E

NUTDRIVERS

The tool used for turning a hexagonal or square bolthead or nut is called a **wrench**. In electronics, many machine screws have hexagonal heads, and turning them with a right-angle wrench is tedious. Most people use a **nutdriver** (sometimes called a **socket wrench**) to turn hex-head screws and nuts up to about 3/4 inch in diameter. You can work a nutdriver much faster than a right-angle wrench. (Drivers for square nuts are made, but seldom used in electronics. This article will concentrate, then, on hex-socket nutdrivers.)

The common nutdriver is almost identical to the screwdriver; it consists of the **tip** (or **socket**), the **blade** (or **shaft**), and the **handle**, as you can see in Fig. 1. The socket and blade are forged from tool steel,



Fig. 1—*Common nutdriver is adequately described as a screwdriver wrench. Chan-nellock unit (left) and Crescent driver right are typical examples of available nutdriver types.*

and the socket is made to a precise size. The nutdriver operates, like the screwdriver, in the same plane as the bolt it's turning. The only difference is the tip, which fits over the bolthead or nut being worked. The tip, or socket, must fit very closely with the nut, or you can't turn it. Thus you must use a separate nutdriver for each size of nut (with one exception, which you'll learn about later).

Socket sizes and the color code

Hex nutdrivers are available with sockets from 3/32 inch to 7/8 inch in steps of 1/32 inch, measured between parallel faces. Each

A miniature torch—like that shown in Fig. 15—is useful for soldering, brazing and welding small parts, because it furnishes high, controllable heat in a small place. Models are available using oxygen and some sort of fuel gas (butane, acetylene, hydrogen, LP gas or natural gas).

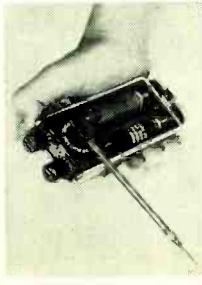


Fig. 15—Miniature torch is useful for soldering, brazing and welding small parts. Microflame unit uses butane and oxygen. Makes a neat handful in use.

For really large jobs, the only thing to use is a standard size torch, as shown in Fig. 16. This tool uses propane gas as fuel, and comes with several nozzles which allow you to do various jobs.

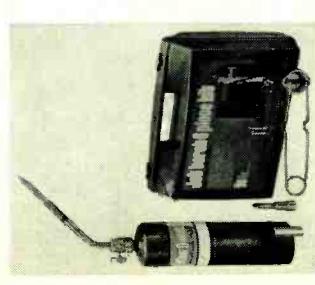


Fig. 16—Bigger soldering jobs require a larger torch. The Bernzomatic JT-50 Jet Torch Kit is illustrated.

driver is known by a number which is the number of 32's of an inch its socket measures. Thus a **No. 3** driver has a socket measuring **3/32 inch**; a **No. 28** has a **28/32-inch**, or **7/8-inch** socket.

Few manufacturers make drivers all the way from No. 3 to 28. Most make sizes from No. 6 (3/16 inch) to No. 20 (5/8 inch), as these are the nut and bolthead sizes most often encountered. A few 32-inch sizes are omitted in this range, though.

To make things easier for you, many manufacturers follow the same color code with their nutdrivers. Hence you can tell by the handle color what the socket size is. It goes like this:

No.	Socket size	Handle color
6	3/16"	Black
7	7/32"	Brown
8	1/4"	Red
9	9/32"	Orange
10	5/16"	Amber or yellow
11	1 1/32"	Green
12	5/8"	Blue
14	7/16"	Brown
16	1 1/2"	Red
18	9/16"	Orange
20	5/8"	Amber or yellow

You'll note that the colors are repeated; both the Nos. 8 and 16 drivers have red handles. However, the No. 16 is larger than the No. 8, so you can easily tell them apart. After you've worked with a set of drivers for a while, you can grab the right one after a glance at a nut. The two most common sizes of nuts and hex-head screws and bolts used in electronics are 1/4 inch and 5/16 inch, and therefore the two most useful nutdrivers are Nos. 8 and 10.

There are also **miniature-socket** drivers, with sockets usually of 5/64 inch, 3/32 inch, 7/64 inch, 1/8 inch, and 5/32 inch. These drivers usually come in a set of 5 or 7 (Fig. 2).

For working on European-made equipment, Xcelite has **metric-size** nutdrivers, with sockets from 3 to 17 mm. Models are available with either solid or hollow shafts.

Blade types

Nutdrivers are available with several types of blades (or shanks), depending on the job they're intended for. Most common is the **standard** size shown in Fig. 1. The blade is about 3 inches long, which means the overall driver length is about 6 inches.

The standard nutdriver has a solid blade, but more useful is the **hollow-shaft** type (Fig. 2). It has a hollow blade which slips over a

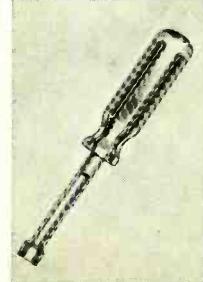


Fig. 2—Hollow-shaft nutdrivers are extra useful as they can slip right over a protruding bolt. Unit shown here is Vaco model S8.

protruding bolt, allowing you to work the nut far down the bolt. Another variation is the long-hollow-shaft type (Fig. 3), about 9½



Fig. 3—Long hollow shafts are needed in some special applications. Especially useful in chassis wells or recesses. Xcelite 8 MM is illustrated.

inches overall length. It's useful when you have to work a nut in a chassis well or recess. Obviously there are times when a regular-length nutdriver won't fit the work space; then you use a **stubby** (Fig. 4) which has a thick handle

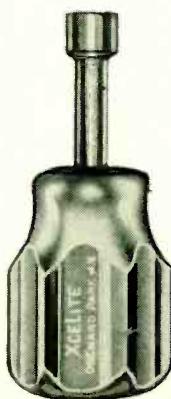


Fig. 4—Stubby nutdrivers have large handles, short blades, and get into tight corners. Left, Xcelite model S10. At right is Vaco stubby nutdriver.

of regular nutdrivers. More handy for field work is a **handle-and-blade** set (Fig. 7), which includes one handle and five or six interchangeable

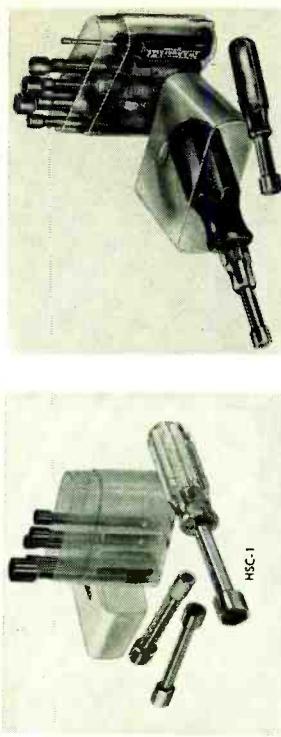



Fig. 7—Nutdrivers come in sets too. They include all of the more common sizes and usually a torque-amplifier large-diameter driving handle too. Left is Xcelite HSC-1. At right is Channellock set.

blades. The set is compact; you can slip it in your pocket. Some such kits include screwdriver blades. Another feature often found in a torque-



Fig. 8—T-handle is excellent torque amplifier to boost turning power. Xcelite 99-4 shown.

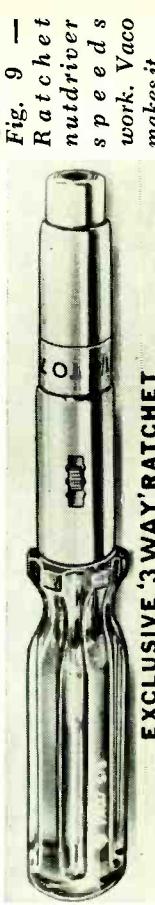multiplying **T handle** (Fig. 8). There are also **stubby** handles. And Vaco has a **ratchet-handle** nutdriver kit (Fig. 9), which speeds up the work.



EXCLUSIVE '3 WAY' RATCHET

Back panel service controls sometimes feature a locknut around a slotted adjustment shaft. It can be a nuisance to loosen the locknut with a nutdriver, set the control with a screwdriver, and then retighten the nut, sometimes unscrewing the control. Xcelite's unique and useful HSC-1 nutdriver set consists of eight hollow-shaft interchangeable driver blades and a mating **hollow handle** (Fig. 7 & 11). Thus you can pass a screwdriver completely through both handle and driver shaft, and use both hands simultaneously to make locknut and control-shaft adjustments.

and an overall length of about 3½ inches.

The **midget** nutdriver (Fig. 5) is also small—about 3½ inches overall—but has a slim handle. Most come with a clip so you can carry them in your pocket. They're useful for field work.

Occasionally you may have to work a nut in a live circuit, where the metal shaft could short out something. The answer is Klein's **insulated-blade** driver (Fig. 6) whose shaft is covered with plastic. This driver is available in socket sizes from No. 6 to No. 20.

Nutdriver handles

Few nutdrivers are made with wooden handles anymore, since plastic is a better insulator for electronics use. In addition, nutdrivers are available with **rubber handle grips** (Fig. 8). The rubber is more comfortable than plastic, and this makes the driver easier to use and reduces fatigue.

Almalt's **swivel-top-handle** nutdriver is a speed-increasing device. You simply apply pressure to the handle end and turn the body with the other hand.

Because the handle of a midget nutdriver is small, you cannot obtain much torque with it. An **auxiliary slip-on** handle is available that goes right over the midget-driver handle. The result is greater turning power. The auxiliary handle usually comes with a set of five or six midget drivers. These don't have pocket clips, which would get in the way of the slip-on handle.

Handle-and-blade kits

You can, of course, buy a set of the five or six most common sizes

P8

Fig. 10—*Hole through the handle speeds locknut and control-shaft adjustments. Ace-lite makes it.*



Fig. 5—*Midget nutdriver is short, but unlike stubby, has slim handle. Often has pocket clip too. Unit shown here is Xcelite model P8.*



Another Xcelite innovation is the type 600 **4-way driver** (Fig. 12) The handle contains a ¼ inch nutdriver at one end and a 7/16 inch nutdriver at the other. The reversible blade has a #1 Phillips screwdriver at the top.

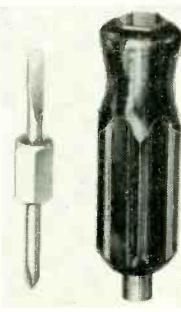


Fig. 11—*Four-way driver has two-way nutdriver bit and 2-way screwdriver bit. Handy pocket toolkit. Xcelite model 600.*

Nutdriver handles

Few nutdrivers are made with wooden handles anymore, since plastic is a better insulator for electronics use. In addition, nutdrivers are available with **rubber handle grips** (Fig. 8). The rubber is more comfortable than plastic, and this makes the driver easier to use and reduces fatigue.

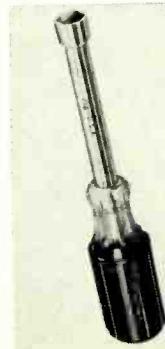


Fig. 6—*Rubber handles on a nutdriver don't add insulation, but do add drive power by giving user a better grip. Klein model 630 shown.*

Almalt's **swivel-top-handle** nutdriver is a speed-increasing device. You simply apply pressure to the handle end and turn the body with the other hand.

Because the handle of a midget nutdriver is small, you cannot obtain much torque with it. An **auxiliary slip-on** handle is available that goes right over the midget-driver handle. The result is greater turning power. The auxiliary handle usually comes with a set of five or six midget drivers. These don't have pocket clips, which would get in the way of the slip-on handle.

Handle-and-blade kits

You can, of course, buy a set of the five or six most common sizes

overall—but has a slim handle. Most come with a clip so you can carry them in your pocket. They're useful for field work.

Occasionally you may have to work a nut in a live circuit, where the metal shaft could short out something. The answer is Klein's **insulated-blade** driver (Fig. 6) whose shaft is covered with plastic. This driver is available in socket sizes from No. 6 to No. 20.

Few nutdrivers are made with wooden handles anymore, since plastic is a better insulator for electronics use. In addition, nutdrivers are available with **rubber handle grips** (Fig. 8). The rubber is more comfortable than plastic, and this makes the driver easier to use and reduces fatigue.

Almalt's **swivel-top-handle** nutdriver is a speed-increasing device. You simply apply pressure to the handle end and turn the body with the other hand.

Because the handle of a midget nutdriver is small, you cannot obtain much torque with it. An **auxiliary slip-on** handle is available that goes right over the midget-driver handle. The result is greater turning power. The auxiliary handle usually comes with a set of five or six midget drivers. These don't have pocket clips, which would get in the way of the slip-on handle.

Another Xcelite innovation is the type 600 **4-way driver** (Fig. 12) The handle contains a ¼ inch nutdriver at one end and a 7/16 inch nutdriver at the other. The reversible blade has a #1 Phillips screwdriver at the top.

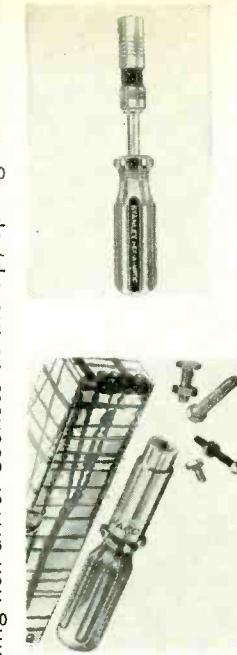


Fig. 11—*Four-way driver has two-way nutdriver bit and 2-way screwdriver bit. Handy pocket toolkit. Xcelite model 600.*



Another Xcelite innovation is the type 600 **4-way driver** (Fig. 12) The handle contains a ¼ inch nutdriver at one end and a 7/16 inch nutdriver at the other. The reversible blade has a #1 Phillips screwdriver at the top.

A recent development is the **multiple-size-socket** nutdriver (Fig. 13). It has telescoping hex-driver sockets at the tip, spring loaded. Thus

NEW R-E EXCLUSIVE

**Transistor Keyed Agc
with dc amplifier**

Kwik-Fix™ picture and waveform charts

by Forest H. Belt & Associates™

SCREEN SYMPTOMS AS GUIDES

SYMPTOM PIC	DESCRIPTION	VOLTAGE	WAVEFORM	WHERE TO CHECK FIRST	PART
	Whiteout; no video, no sound	Check all Q1 voltages	WF3		All in Q1 stage
	Overload darkout; no video, but sound okay	No specific voltage	WF3		Too many to be specific
	Agc control range reduced; can't whiteout more than this	Q1 emitter	No help		R4
	Bends and flagwaving	Q1 base Q1 collector	WF3		T1 reversed
	Right side of raster blacked out; sync poor; sound okay	Q1 emitter Q2 base	WF3		C3

*an Easy-Read™ feature by FOREST H. BELT & Associates © 1970

NOTES:

Use this guide to help you find which key voltage or waveform to check first.

Study the screen and the action of the agc control. Note sound.

Most helpful clues to the fault are found at the key test points indicated in Voltages or Waveform column.

THE STAGES

This agc system is a popular one in transistor and hybrid color receivers and in many black-and-white sets. Pulses from the flyback winding key the transistor agc stage. A distinguishing characteristic is the use of the winding as dc conductor for the agc voltage that is developed.

There is almost always a protective diode at the collector of the keyed stage. (It is at the emitter in some versions, because the keying pulse is applied there.)

This particular agc system develops a dc output that goes more positive as station-signal input increases. For a vhf tuner that uses an npn transistor rf amplifier, this is *forward agc*. (The normally forward-biased rf transistor is biased further forward by the agc as the signal gets stronger.) Most agc-controlled i.f. stages use npn transistors. For them,

make the voltage or waveform checks indicated for symptoms you see on the screen.

Use the Voltage Guide or Waveform Guide to analyze results.

For a quick check, test or substitute the parts listed as the most likely cause of the symptoms.

this is forward agc if the positive agc voltage is applied to the base; if it is applied to the emitter, it is ordinary reverse-bias agc.

In other versions, the dc amplifier stage is phase-reversing. That is, it converts a positive-going agc change to a negative-going one. But not in this version. The dc input is at the base, and dc output is at the emitter. A voltage change at the base produces the same polarity of change at the emitter.

SIGNAL BEHAVIOR

A video signal from the emitter of the first video amplifier is the input for the agc keyer stage. The amplitude of the sync pulses "tells" the stage how strong the station signal is. (Video level changes from scene to scene, but sync doesn't.)

DC VOLTAGES AS GUIDES

voltage change	to zero	very low	low	slightly low	slightly high	high
Key-point-A Normal 1.6 V. Varies with video, from 1.3 to 1.8 volts. Main source is emitter of video amplifier (dc connection).	R4 open R5 open R6 low **C2 shorted C3 shorted **D1 shorted D1 open T1 open		T1 reversed	R7 low C3 open		R1 open R2 low R3 open R4 low C1 shorted
Q1-base Normal 1.6 V. Varies with video, from 1.3 to 1.8 volts. Chief source is same as key-point-A.	R4 open C1 shorted C2 shorted	R6 low C3 shorted	R1 open R2 low R5 open D1 open, shorted T1 open	T1 reversed		R3 open R4 low
Q1-emitter Normal 1 V. Varies with setting of agc control, from zero to almost 4 volts. Is almost unaffected by signal.	R4 open C2 shorted			C1 shorted		R3 open R4 low C3 open
Q1-collector Normal -2.3 V. Varies with signal level at base. Goes as far as -14 volts with no station signal.	*R1 open *R3 open *R4 low *R5 open C1 shorted C2 shorted *C3 open *D1 open *T1 open, reversed	R4 low	R2 low D1 shorted	R6 low R7 low C3 shorted		R4 open
Q2-base Normal 5.5 V. Varies with signal level. With no station signal, goes down almost to zero. Is developed across R6 by Q1 conduction.	R4 open R5 open R6 low C2 shorted C3 shorted D1 open D1 shorted T1 open		C3 open	R7 low		R1 open R2 low R3 open R4 low C1 shorted
Q1-emitter Normal 5 V. Changes some with signal level. With no station signal, drops to about 3 volts. Is developed by Q2 conduction through R7.	R7 shorted		R4 open R5 open R6 low C2 shorted C3 shorted D1 open D1 shorted T1 open	R4 open R7 low		R1 open R2 low R3 open R4 low C1 shorted
	*goes positive **goes negative					

NOTES:

Use this guide to help you pinpoint the faulty part.

Do not clamp the agc line. This guide was prepared without external bias voltages.

Measure each of the six key voltages with a vtvm.


For each, move across to the column that describes the

change you find.

Finally, notice which parts are repeated in whatever combination of voltage changes you find.

Test those parts individually for the fault described.

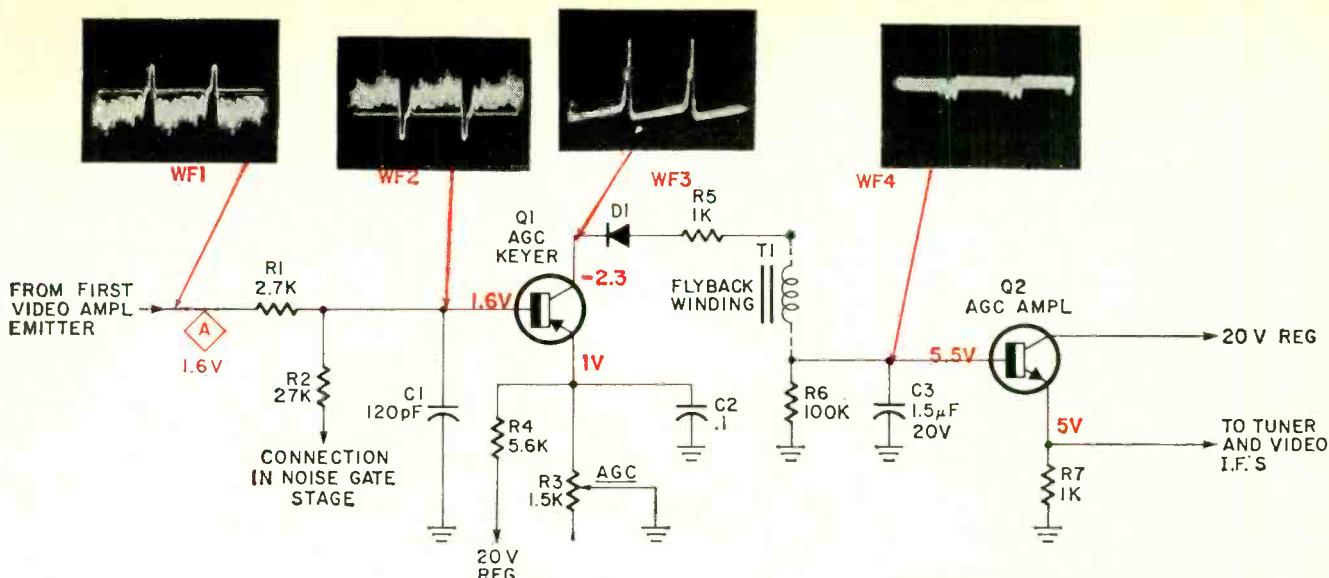Look for additional clues in the Waveforms Guide.



NOTE: VOLTAGES AND WAVEFORMS ARE TAKEN WITH LOCAL STATION TUNED IN

The sync pulses in WF1 and WF2 are negative-going. They drive the pnp transistor bias forward, setting its ability to conduct in proportion to the amplitude of the sync pulses.

But transistor Q1 isn't able to conduct constantly. It takes a high negative collector voltage (it's a pnp, remember) to make it conduct. That is supplied periodically by a strong negative pulse from a winding on the flyback transformer. The pulse occurs during horizontal retrace and is therefore timed just right to coincide with each horizontal sync pulse that arrives at the base of Q1.

Thus the time when Q1 conducts is determined by the keying pulse; the amount Q1 conducts is determined by the amplitude of horizontal sync.

Video is wiped out completely in Q1 because the transistor can't conduct at all between horizontal pulses.

Capacitor C3 keeps the "cold" end of the flyback winding (T1) at signal ground. From there on through Q2, there is no signal (WF4 is exhibited only to help spot trouble—it normally is zero).

DC DISTRIBUTION

A high negative dc voltage develops at the collector of Q1 when there's no station signal and therefore no video at the base. It is the average developed by the keying pulse. A small dc bias through R4 lets the transistor conduct slightly. When video is present, the transistor conducts much more during those keying pulses. Increased conduction lowers the negative dc average at the collector. That's a positive-direction dc voltage shift. That shift is, in effect, the basic agc voltage.

Emitter voltage on Q1 is controlled mainly by the agc control. The source is the regulated 20-volt line. R4 and R3 divide it to deliver a steady emitter bias.

Conduction in Q1 sets up a dc path that includes R6, the T1 winding, R5, D1, Q1 and R3. A dc voltage is developed across R6 that is positive at the base of Q2. It is an average dc that depends on conduction of Q1. It is very slight when lack of video keeps Q1 conducting very little; it goes up when the signal is stronger.

More positive voltage at the base of Q2, which is an npn transistor, increases its conduction. That develops a higher

positive voltage across R7. This positive voltage is what is fed to the tuner and to the video i.f.'s.

SIGNAL AND CONTROL EFFECTS

The station signal obviously affects practically every dc voltage in both stages. That's their function in the set.

However, signal has very little effect on one dc voltage and on one waveform. The emitter voltage of Q1 is relatively unaffected by anything except the agc control. And the keying waveform (WF3) is unaffected by station signal or by video input to Q1.

Turning the agc control when no signal is present doesn't change much other than the emitter voltage of Q1. However, if a station is tuned in, the agc control affects voltages throughout the agc amplifier (Q2) stage. But it affects them only a little bit as long as there's no video whiteout or overload darkout. When either of those happens, voltages change rather noticeably in the circuit.

For servicing, if the effects of turning the agc control can't be seen in the picture, just set the control at the center of its range.

QUICK TROUBLESHOOTING

Don't clamp the agc line to hunt trouble in this agc system. That works well with some, but the voltage and waveform guides in this *Kwik-Fix™* are prepared without external clamping bias. It confuses troubleshooting.

Know the difference between **whiteout** and **overload darkout**. The whiteout is from *too much* agc voltage: i.f. stages are cut off. It takes sound out, too. Darkout is caused by signal overload with *not enough* agc voltage. Sound stays during darkout. The screen (with dc-coupled video sections) gets darker. **Washout** is weak video caused by a little too much agc voltage cutting down i.f. gain.

Using scope waveforms WF2 and WF3: If WF2 is bad, momentarily clamp the agc line (at the emitter of Q2, in this version) to be sure the fault is not in the video or i.f. stages. But remove the clamp voltage to use the Guides. Polarity of WF3 is important. Wiring a new flyback transformer in backward is a common error that causes agc trouble.


R-E

WAVEFORMS AS GUIDES


WF 1 Normal 2 V p-p

This waveform is included for reference only. Sync pulses here are negative-going. The signal source is the emitter of the first video amplifier. It's the video input to the agc section. If it isn't present, clamp the agc line (at Q2 emitter) for a moment. If the waveform appears, the video or i.f. stages are okay. Remove the clamp voltage while troubleshooting the agc stages.

(Turn page for more waveforms)

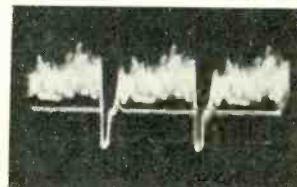


WF 2 Normal 2 V p-p

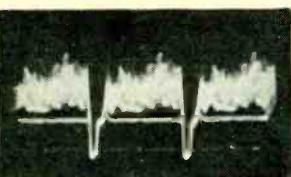

This waveform at the base of Q1 is about the same as WF1. Sync pulses are negative-going. This waveform reveals quite a few defects that occur in the stage. Notice especially its shape, and compare with the symptom photos below. Amplitude doesn't change much, even when there's a fault. The amplitude of these horizontal sync pulses determines the amount of agc.


V p-p low R2 low	V p-p high	V p-p zero R2 low R5 open C1 shorted D1 open	 2 V p-p R1 open	 0.6 V p-p R3 open	 1.8 V p-p D1 shorted	 1.2 V p-p T1 reversed
			 1 V p-p R4 low R6 low R7 low C3 shorted T1 open	 0.2 V p-p R4 open C2 shorted	 2.4 V p-p C3 open	

WF 3 Normal 15 V p-p

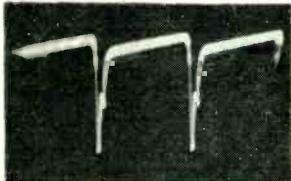

This is the negative-going keying pulse, taken at the collector of the keying transistor. The pulse comes from a winding on the flyback transformer. Resistor R5 and diode D1 sharpen it up before it reaches the transistor collector. This pulse keys the transistor on during each horizontal sync pulse, so the sync amplitude can set the average conduction of transistor Q1. Amplitude of the keying pulse is constant regardless of signal conditions; but a fault can foul that up quite a bit—as witness the symptoms pictured below.

V p-p low T1 open	V p-p high R6 low R7 low C3 shorted	V p-p zero R5 open D1 open T1- open	 0.6 V p-p R3 open	 1 V p-p R4 low	 25 V p-p D1 shorted	
			 12 V p-p R4 open C2 shorted	 3.5 V p-p T1 reversed	 18 V p-p C3 open	

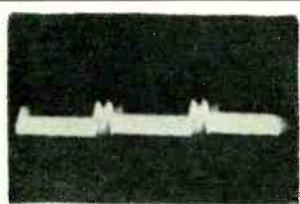

WF 4 Normal 0 V p-p

It's hardly fair to call this a waveform at all. If the stage is working properly, it isn't a waveform. In fact, it's virtually zero. However, it's included—taken at the base of Q2—to show its effect when C3 is open. Almost no other faults affect it.

V p-p low	V p-p high		 30 V p-p C3 open			
-----------	------------	--	-------------------------	--	--	--

Use this guide and the Voltages Guide to help you pin down fault possibilities.

Clamping the agc line is not necessary. Waveforms in this guide are taken without external bias voltages.

With the direct probe of the scope, check the four key waveform points. (Only two of them give most of the trouble

clues.) The scope sweep should be set at H or about 5 kHz, to show three cycles of the waveform.

Note amplitude. If it's missing, low, or high, check parts under those columns.


Note waveshape. If there's a change from normal, despite amplitude, check the parts indicated.

For Your Darkroom

HALF-HOUR INTERVAL TIMER


by FRANK H. TOOKER

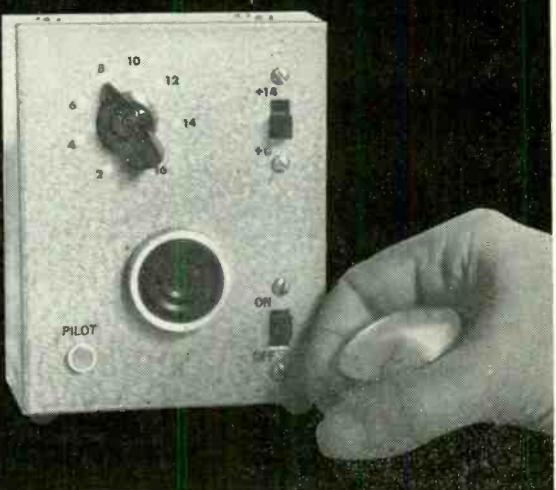Accurate long-term darkroom timing is a past problem once you build this electronic timer. Measures time intervals as long as 30 minutes, accurately



C1—220- μ F, 10V, low-leakage tantalum capacitor
 C2—0.01- μ F, 100V, Mylar capacitor
 C3—0.022- μ F, 100V, Mylar capacitor
 C4—500- μ F, 25V, electrolytic capacitor
 All resistors $\frac{1}{2}$ W, 10% unless noted
 R1—1-megohm linear potentiometer (Ohmite CU1052 or equal)
 R2—5-megohm linear potentiometer (Ohmite CU5052 or equal)
 R3—Two 10-megohm resistors in parallel (see text)
 R4, R5—100 ohms
 R6—47,000 ohms
 R7—15,000 ohms
 R8—3000-ohm wirewound potentiometer
 R9—10,000 ohms

R10—470 ohms
 R11—220 ohms, 1 watt
 D1—10V, 1-watt, Zener diode
 D2—15V, 1-watt, Zener diode
 D3, D4—rectifier diodes (1N3754 or similar)
 Q1—2N5457 field-effect transistor
 SCS1—3N84 silicon controlled switch
 S1—dpdt slide switch
 S2—spst slide switch
 T1—30V ct, 50-mA power transformer
 LM1—120V ac neon pilot lamp (Leecraft 36N2315 or similar)
 Mallory Sonalert type SC628
 MISC.—5 x 4 x 3-inch aluminum cabinet, power cord & plug, pointer knob, rubber feet, 3-lug terminal strip, small L-brackets, rubber grommet, hardware

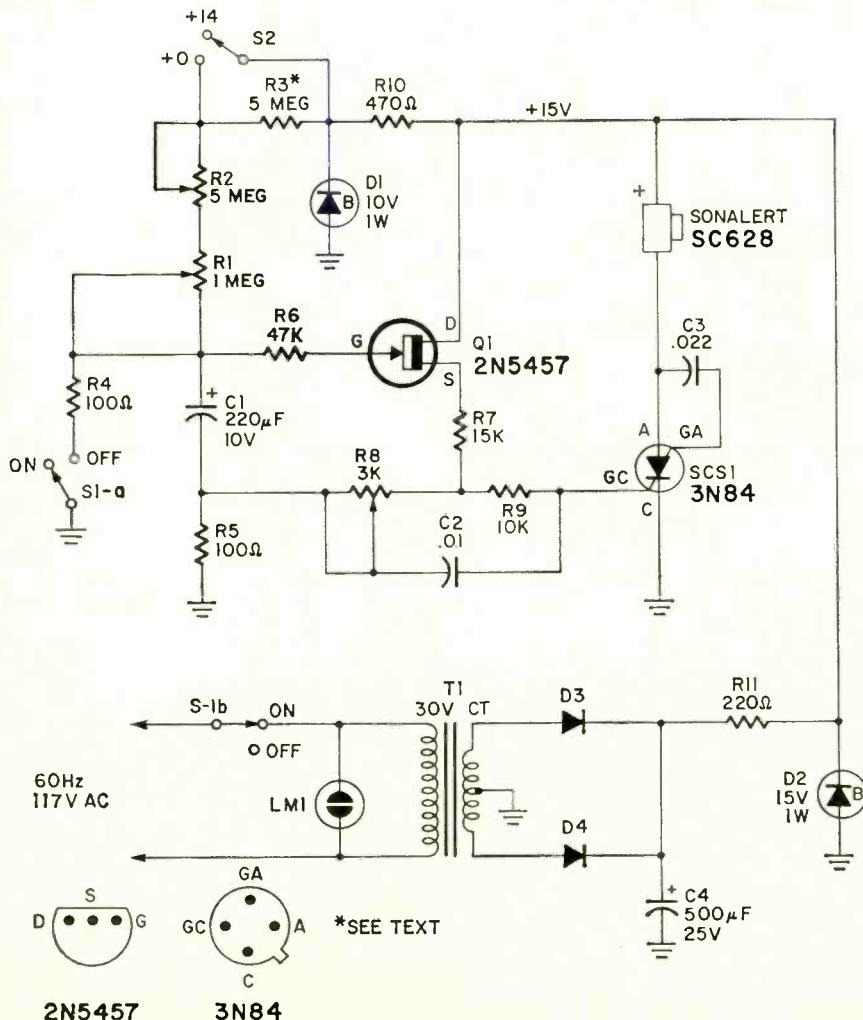

RC ELECTRONIC INTERVAL TIMERS usually have a maximum time lapse of about 10 minutes. Beyond this delay, timers have been costly to build, have required relatively hard-to-get parts or have been inexpensive but inaccurate.

The timer described here is different. It's not cheap to construct, but it won't flatten your wallet either. All components are available from catalog sources. The unit has two timing intervals, the longer is $\frac{1}{2}$ hr. Accuracy is $\pm 5\%$ for the low range; $\pm 10\%$ for the upper range.


You can use a timer such as this to get your breakfast eggs just right or for timing long-distance telephone calls. In the winter it will tell you when you've been under the sun lamp long enough; in the summer it tells you when to move the lawn sprinkler to another location. If you're a photography enthusiast, it will let you know—even in total darkness—when your negatives are developed, fixed and washed. You'll find a host of other uses once you have the instrument built.

How it works


A schematic of the $\frac{1}{2}$ -hour interval timer is in Fig. 1. Potentiometers R1, R2 and resistor R3, together with tantalum capacitor C1, determine the timing interval. Resistor R5 has much too small a value to affect the intervals significantly.

The voltage slowly developed across C1 is fed to the gate of field-effect transistor Q1 via R6. The FET is connected as a dc source follower. Gate junction leakage in the FET is very low—perhaps 1 nA at room temperature. Thus, loading of the RC timing components is negligible. Leak-

Fig. 1—Timer circuit is relatively simple. It uses an FET transistor and a silicon controlled switch (SCS) to do the hard work.

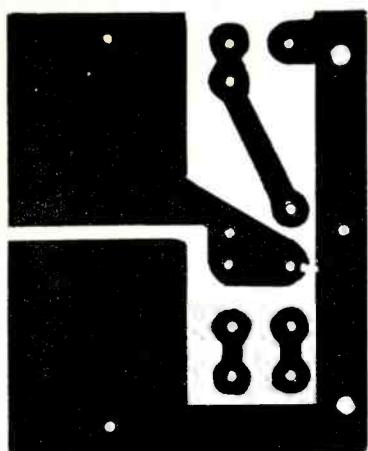

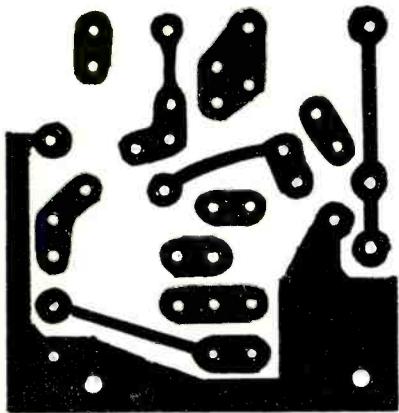Foil pattern for the power supply circuit board. This is actual-size drawing.




Foil pattern of the timer circuit board. Drawing is actual-size pattern.

age resistance of the timing capacitor is the only significant loss in this part of the circuit.


The dc potential at the source junction of Q1 rises as the voltage across C1 rises. This potential appears across voltage-divider resistors R7 and R8. The potential across R8 is fed to the cathode gate of the silicon controlled switch via R9. When this potential rises to the triggering level of the SCS (silicon controlled switch) (about 0.5 volt), the SCS turns on, applying voltage to the Sonalert unit.

The power supply uses a center-tapped transformer, a pair of rectifier diodes and a fairly large filter capacitor, C4. The dc output across C4 is fed through resistor R11 and regulated at 15 volts by Zener diode D2. On the timer PC board, this potential is regulated to 10 volts by R10 and Zener diode D1 before being applied to the sensitive RC timing circuit. Rigid control of the timing-potential supply is thereby maintained. The remainder of the timer is supplied at the regulated 15-volt level.

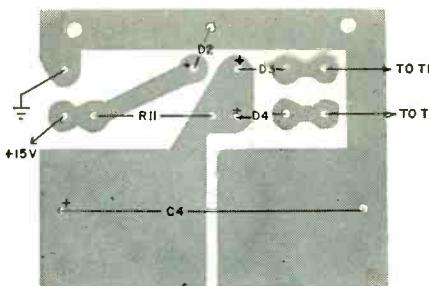When the Sonalert sounds, and the instrument is switched off, section S1-b of the ON-OFF switch opens the



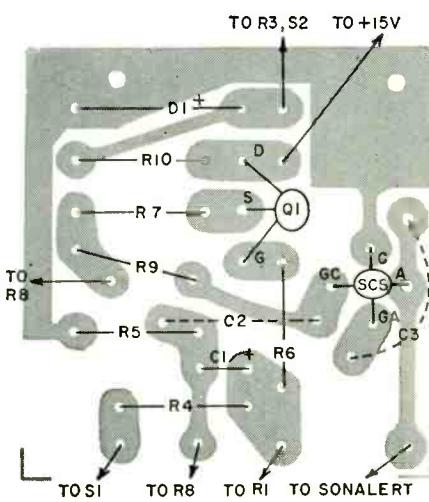Parts layout on the power supply board. Phenolic board material is ok here.



Parts layout for the timer board. For accuracy use a glass-epoxy board.

transformer primary circuit, while section S1-a discharges timing capacitor C1 by short-circuiting it through R4 and R5. The negative pulse that appears across R5 at the instant of discharge is fed to the cathode gate of the SCS via C2, triggering the SCS off. Without this feature, the Sonalert would continue to sound, even though the timer is switched off, until filter capacitor C4 becomes nearly discharged.

Capacitor C3 reduces the sensitivity of the SCS to line-voltage transients. The circuit, however, may at times be triggered by a strong transient pulse, when the potential at the cathode gate is raised near the firing level.

The instrument is equipped with a neon pilot lamp to indicate when the unit is on and timing. (It's discouraging to wait for a ½-hour interval and discover you've forgotten to plug the power cord into a wall receptacle!)

With S2 closed, any time interval between 2 minutes and 16 minutes may be obtained by setting potentiometer R2. When switch S2 is opened, a fixed 14 minutes is added to

the timed interval. The calibrated settings of R2 then cover a 16-30-minute range.

The setting of R8 determines the voltage level across capacitor C1 at which SCS1 turns on. This adjustment is made to obtain the 16-minute interval, when switch S2 is closed and potentiometer R2 is set at maximum resistance in the circuit. Potentiometer R1 is adjusted to obtain the 2-minute interval, when switch S2 is closed and potentiometer R2 is set at minimum resistance in the circuit.

The setup exhibits some variation in the timed intervals as a result of variations in room temperature. Over the range of 65-90°F, these variations fell within the specified tolerances. A variation of 3 min in ½ hr represents a 10% tolerance.

Building a timer

The timer shown in the photos is constructed in a 5x 4x 3-inch utility cabinet. Two PC boards are employed: one for timing circuit components, the other for power supply components. The timer-circuit PC board is preferably of glass-epoxy base material. The power supply board may be phenolic.

Be particularly careful not to overheat timer components when soldering this board. Even slightly excessive heat applied to C1 or the FET can materially affect circuit performance. If the timer cannot be calibrated as described later, or if the calibrated points appear to shift without reason or are otherwise erratic, and all solder joints are clean and properly made, then component overheating should be suspected.

The parts list calls for two 10-megohm resistors in parallel for R3. Using two parallel resistors like this allows the value of one of them to be adjusted slightly higher or lower to bring the longer range of timed intervals within the 10% tolerance. This adjustment is desirable because, as the timing extends beyond 16 minutes, the leakage resistance of C1 begins to have a slight but increasing influence on the timed intervals. As a result of this influence, R3 will appear to have a somewhat larger value when R2 is set at the 16-minute calibration point than when it is set at the 2-minute point. Thus, without compensation, all this effect could appear at the upper end of the range of the longer timed intervals. By carefully adjusting the value of R3 the effect can be divided between the high and low settings of R2, providing a more reasonable tolerance over the entire range.

(continued on page 82)

WHEN WE STARTED THIS COLUMN about a year ago, I suggested we make it *our* column. I asked you to tell me what you want to see in it and to contribute original or condensed material from foreign-language electronic publications. Well, I've received complements on Technical Topics but no suggestions on contents of future columns. You are really going all out in telling us what you like and want to see in R-E. Perhaps we can insert a few Tech Topics questions in a future questionnaire. But, I can't wait. Fellows, let me hear from you.

A real swinging i.f.

The receiver section of the new Signal/One model CX7 transceiver has, in addition to two cascaded 8-crystal lattice filters, a new patented *i.f. shift* circuit that lets you shift the i.f. carrier plus or minus 2 kHz within its extremely steep-skirted i.f. passband to eliminate QRM. You can attenuate a 500-Hz heterodyne by 50 dB without affecting the desired signal.

The CX7 is full of new and interesting circuit innovations and we plan to cover many of them for you later. In the meantime, let's take a look at a Magnavox circuit that does much the same thing for FM. It appears that it can be adapted for AM as well.

The FM Signal Sentry is what Magnavox calls its swept FM i.f. circuit designed to minimize noise and undesirable sidebands from strong adjacent-channel stations, to prevent the AFC from locking in on these undesired stations and to improve selectivity and signal-to-noise ratio. To do this, the engineers use a sharp 10.7-MHz interstage coupling network with VVC's (voltage-variable capacitance diodes) to vary the instantaneous i.f. resonant frequency above or below the nominal 10.7-MHz point in step with the audio output from the FM detector.

A simplified schematic of the AM-FM i.f. strip in the R223 series AM-FM tuner is shown in Fig. 1. The 10.7-MHz FM i.f. from the mixer is

developed across the broadband first FM i.f. transformer. The response of the i.f. signal at the base of Q1 is shown in Fig. 2-a. The first and second FM i.f. amplifiers are coupled through transformers T1 and T2 connected back-to-back by a 0.39-pF capacitor.

The high-impedance windings of T1 and T2 are tuned by 20-pF capacitors shunted by VVC diodes D1 and D2 in series with 150-pF capacitors. A fixed negative bias voltage is applied to the anodes of D1 and D2 so T1 and T2 are tuned for a 6-dB bandwidth of 100 kHz (Fig. 2-b) at the base of Q2.

Wideband resistance-capacitance coupling is used between the second, third, and fourth i.f. amplifiers and between the fourth stage and the limiter. Transformer coupling is not needed between these stages because adequate selectivity is provided between the first and second stages.


When a signal is tuned in, a portion of the audio output from the FM detector is fed back to the VVC diodes through the 20- μ F capacitor. The audio signal, impressed on the fixed dc bias, causes the effective capacitance of the VVC's to increase and decrease, depending on the polarity and strength of the applied audio. Thus, the frequency of T1 and T2 deviates about 10.7 MHz in step with the audio signal variations. The *apparent* overall bandpass for an incoming signal (indicated by dashed lines in Fig. 2-c) is approximately 250 kHz, while the actual bandpass at any given instant is only 100 kHz.

Since the apparent i.f. bandpass is determined by the amplitude of the recovered audio, we see that higher amplitude audio signals develop a proportionately wider bandpass. At the same time, the narrow (100 kHz)

TECHNICAL TOPICS

by ROBERT F. SCOTT
SENIOR TECHNICAL EDITOR

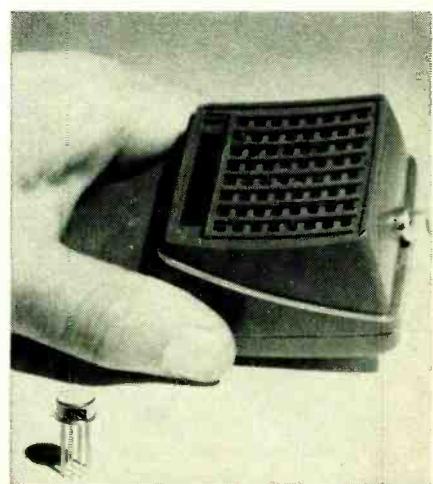Magnavox's FM Signal Sentry with VVC diodes for a swept i.f. circuit . . . applications of a new monolithic IC agc and squelch amplifier (applied to Shure's 401-A microphone) . . . a blocked-grid keyer



Mike with automatic-squelch added.

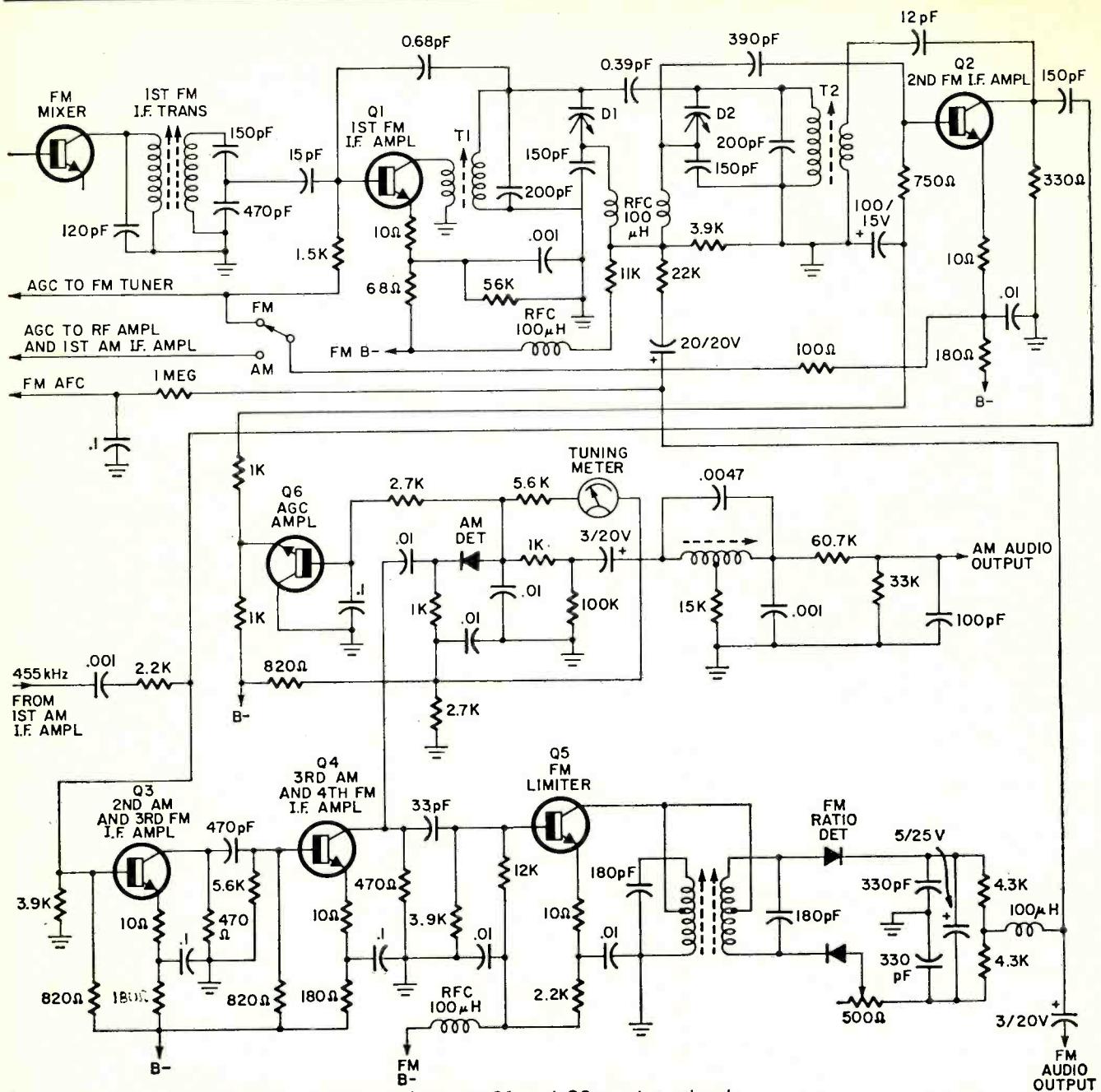


Fig. 1—VVC-diode/transformer combination between Q1 and Q2 receives signal from detector, so T1/T2 tuned frequency swings about 10.7 MHz with the audio.

instantaneous bandpass reduces noise and splatter from strong adjacent channels.

A portion of the dc output of the FM detector is filtered by a 1-meg resistor and 0.1- μ F capacitor and fed to the VVC used for afc in the tuner.

AM detector for FM agc

AM and FM i.f. signals at the collector of Q4 are rectified by the AM detector diode. The detector output, negative at the anode end, is coupled to the base of Q6, an emitter follower used as the agc amplifier. This transistor is normally conducting and its collector-emitter current drops as the detector output increases. The

emitter of Q6 is direct coupled to the base of Q2 to reverse-bias this stage.

As conduction in Q2 is decreased, its emitter goes more negative. This negative-going voltage is used for reverse-bias agc for the first FM i.f. amplifier, the FM rf amplifier during FM reception and for the AM rf amplifier and first AM i.f. amplifier on AM reception. The tuning meter—connected across the AM detector output—works on AM and FM.

Blocked-grid keying with transistor

The usual blocked-grid keying scheme for CW transmitters has two disadvantages. You either risk a shock

from the blocking bias on the key or you have to use an expensive—and often noisy—keying relay. A novel solution to this problem was presented by DM2BLJ in *Funkamateur*, a German ham magazine.

In the circuit (Fig. 3) blocked-grid keying is applied to the vfo. Normal operating grid bias is developed by grid current flowing through R1. This resistor is returned to -25 volts on a voltage divider (R2 and R3) across a -100-volt source. A transistor is shunted across R3. The transistor base is connected through the key to -1 volt on voltage divider R4-R5. When the key is up, the transistor is cut off and the tube is biased

off by the -25 volts at the low end of R1. When the key is closed, the transistor is biased on so it short circuits R3 and effectively grounds the low end of R1 so the tube operates normally.

The transistor selected for the job should have a collector-to-emitter breakdown (base open) rating (BV_{CEO}) higher than the drop across R3, and should be capable of carrying the normal operating grid current. R2 and R3 should be selected to provide cutoff bias for the tube being keyed.

IC for communication systems

Quite a few circuits and projects designed around IC's have been described in this magazine, but few have impressed me as much as some of those in Application Note AN-11 covering the use of National Semiconductor's LM170/LM270/LM370 monolithic agc and squelch amplifier. The LM170 (-55 to 125°C); LM270 (-25 to 75°C) and LM370 (0 to +70°C) combine a preamplifier whose gain can be controlled by an external dc voltage, two agc detectors and a squelch threshold detector. The IC's, housed in 10-lead TO-5 packages, operate with supply voltages up to 24. Typical current drain is 4 mA at 4.5 volts and 8 mA at 12 volts. Typical voltage gain is 40 dB at 1 kHz.

The principal applications of these IC's are in squelch and agc circuits, but they can be used for alc (automatic load control) in SSB transmitters, remote-controlled audio preamplifiers, automatic squelch-controlled microphones, constant-amplitude audio oscillators and other applications.

Fig. 4 is the circuit of a squelched microphone preamp that may be used to suppress background noise between pauses in speech. The LM170 series can be driven directly from a low-resistance dynamic or controlled magnetic microphone. The IC and suitable 4.5- or 6-volt batteries can be fitted inside the case of some of the smallest commercial microphones.

The 10,000-ohm SQUELCH THRESHOLD control can be adjusted so squelch opens at any desired input level. The release time constant is determined by the values of R1 and C1. The values of R2 and R3 are selected so C1 charges to about 3 volts from a 12-volt supply. The squelch has an extremely fast attack and gain fades to zero following a release time varying from around 200 msec to several seconds. Capacitor C1 may be any value between 5 and 50 μ F. The release time can be adjusted by varying the value of C1 or by using a selected value for C1 and replacing R1 with a potentiometer.

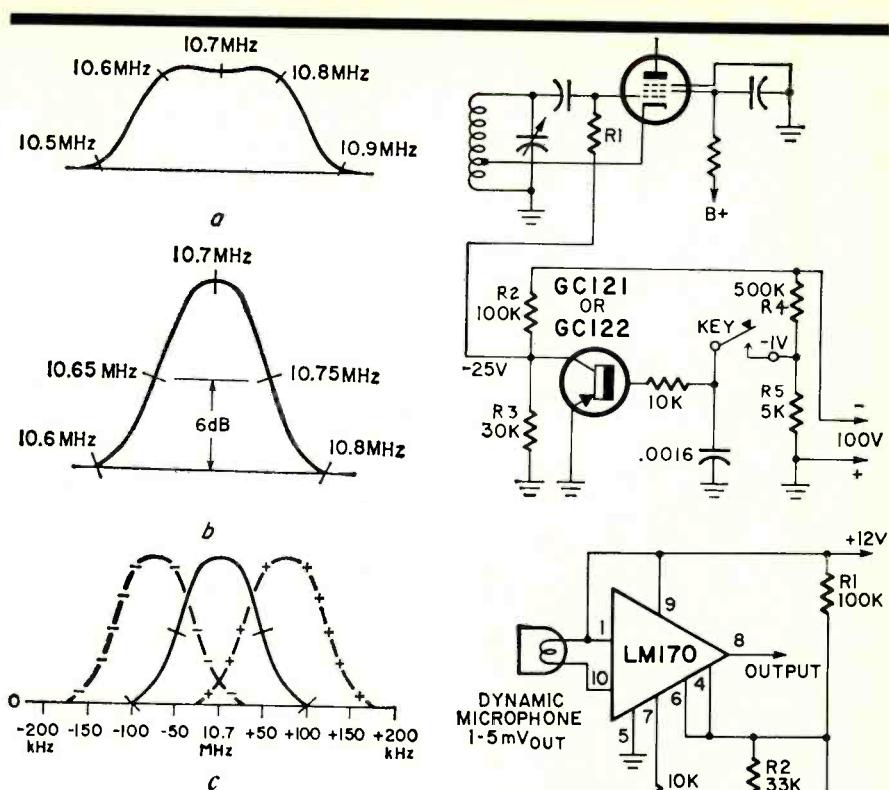


Fig. 2-a-c—I.f. variations: from Q1's base, to Q2's base, with modulation shifts.

Fig. 3 (top right)—Blocked-grid keying applied to the grid of the vfo tube.

Fig. 4 (right)—Squelched-mike circuit.

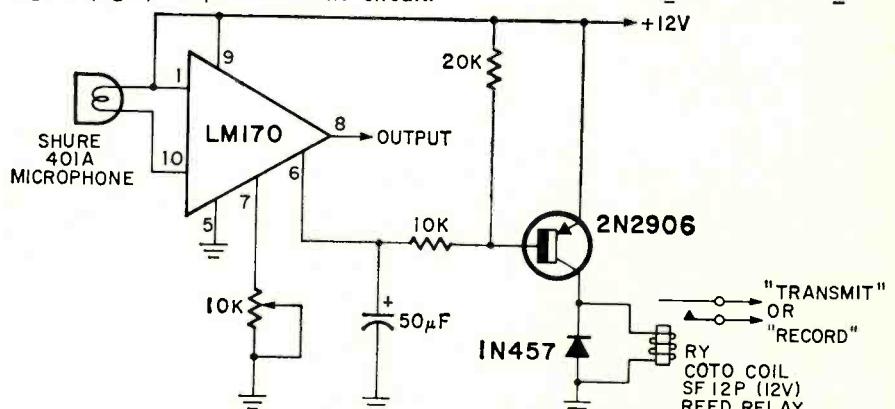



Fig. 5—Squelched voice-operated (vox) circuit application of the LM170 IC. Transmitter or tape recorder is turned on with speech through fast-acting relay.

Individual mikes are often used for panel discussions, conferences, in court rooms, etc. to permit all persons random access to the PA system. In a system of this type, all mikes can be fitted with automatic squelch and their outputs (pin 8 of the LM170 series IC) connected to a common input on the PA amplifier. The background noise at each mike position is suppressed, while close talking permits one or more of the speakers to be heard.

The LM170 can be connected (as in Fig. 5) as a vox (squelched voice-operated transmission) circuit for a transmitter or tape recorder. The recorder or rig is turned on with the

first syllable of speech and is turned off when the speech is turned off or drops below a preset level. A small pnp transistor drives a fast-acting relay such as the Coto Coil type SF12P reed relay. If the circuit tends to oscillate or hunt, connect a large electrolytic across the power supply. The relay contacts, number and form as needed, are used to control the transmitter, or recorder motor and other auxiliary circuits. The photo shows a Shure 401A converted to an automatic squelch-controlled microphone. The indicator lamp, controlled by auxilliary contacts on the relay, signals the speaker that he has turned on the transmitter or recorder.

R-E

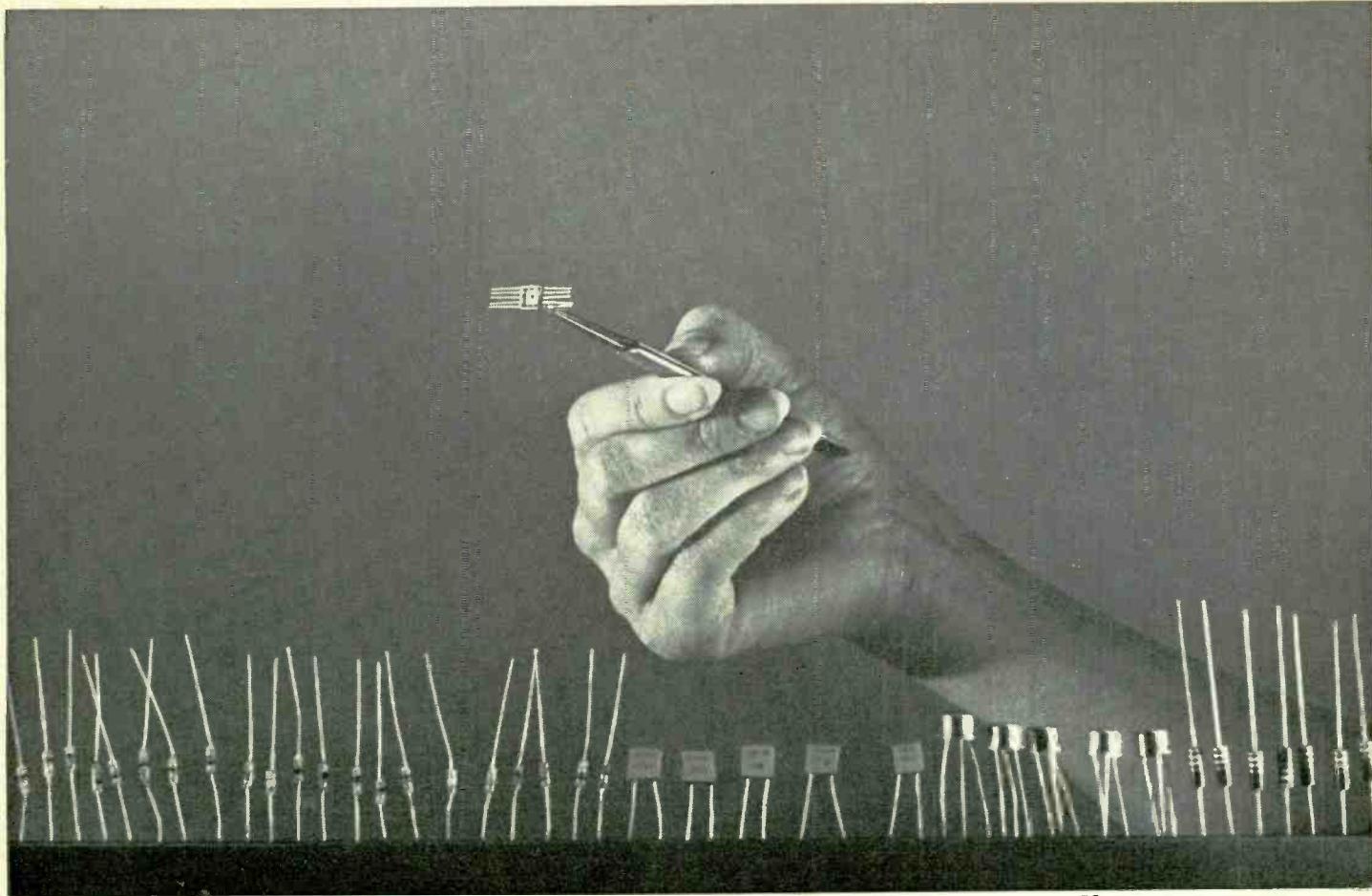

50 functions in a single chip. The functions of 50 separate transistors, diodes, resistors and capacitors can now be performed by the tiny dot in the center of the integrated circuit held by the tweezers.

The "Chip" ...will it make or break your future job?

THE DEVELOPMENT OF INTEGRATED CIRCUITRY is the dawn of a new age of electronic miracles. It means that many of today's job skills soon will be no longer needed. At the same time it opens the door to thousands of exciting new job opportunities for technicians solidly grounded in electronics fundamentals. Read here what you need to know to cash in on the gigantic coming boom, and how you can learn it right at home.

TINY ELECTRONIC "CHIPS," each no bigger than the head of a pin, are bringing about a fantastic new Industrial Revolution. The time is near at hand when "chips" may save your life, balance your checkbook, and land a man on the moon.

Chips may also put you out of a job...or into a better one. "One thing is certain," said *The New York Times* recently. "Chips will unalterably change our lives and the lives of our children probably far beyond recognition."

A single chip or miniature integrated circuit can perform the function of 20 transistors, 18 resistors, and 2 capacitors.

Yet it is so small that a thimbleful can hold enough circuitry for a dozen computers or a thousand radios.

Miniature Miracles of Today and Tomorrow

Already, as a result, a two-way radio can now be fitted inside a signet ring. A complete hearing aid can be worn entirely inside the ear. There is a new desk-top computer, no bigger than a typewriter yet capable of 166,000 operations per second. And it is almost possible to put the entire circuitry of a color television set inside a man's wristwatch case.

And this is only the beginning!

Soon kitchen computers may keep the housewife's refrigerator stocked, her menus planned, and her calories counted.

Money may become obsolete. Instead you will simply carry an electronic charge account card. Your employer will credit your account after each week's work and merchants will charge each of your purchases against it.

When your telephone rings and nobody's home, your call will automatically be switched to the phone where you can be reached.

Doctors will be able to examine you internally by watching a TV screen while a pill-size camera passes through your digestive tract.

New Opportunities for Trained Men

What does all this mean to someone working in Electronics who never went beyond high school? It means the opportunity of a lifetime—if you take advantage of it.

It's true that the "chip" may make a lot of manual skills no longer necessary.

But at the same time the booming sales of articles and equipment using integrated circuitry has created a tremendous demand for trained electronics personnel to help design, manufacture, test, operate, and service all these marvels.

There simply aren't enough college-trained engineers to go around. So men with a high school education who have mastered the fundamentals of electronics theory are being begged to accept really interesting, high-pay jobs as engineering aides, junior engineers, and field engineers.

How To Get the Training You Need

You can get the up-to-date training in electronics fundamentals that you need through a carefully chosen home study course. In fact, some authorities feel that a home study course is the best way. "By its very nature," stated one electronics publication recently, "home study develops your ability to analyze and extract information as well as to strengthen your sense of responsibility and initiative." These are qualities every employer is always looking for.

If you do decide to advance your career through spare-time study at home, it makes sense to pick an electronics school that specializes in the home study method. Electronics is complicated enough without trying to learn it from lessons designed for the classroom instead of correspondence training.

The Cleveland Institute of Electronics has everything you're looking for. We teach only Electronics—no other subjects. And our courses are designed especially for home study. We have spent over 30 years perfecting techniques that make learning Electronics at home easy, even for those who previously had trouble studying.

Your instructor gives your assignments his undivided personal attention. He not only grades your work, he analyzes it. And he mails back his corrections and comments the same day he gets your lessons, so you read his notations while everything is still fresh in your mind.


Always Up-to-Date

Because of rapid developments in Electronics, CIE courses are constantly being revised. Students receive the most recent revised material as they progress through their courses. This year, for example, CIE students are receiving exclusive up-to-the-minute lessons in Microminiaturization, Logical Troubleshooting, Laser Theory and Application, Single Sideband Techniques, Pulse Theory and Application, and Boolean Algebra. For this reason CIE courses are invaluable not only to newcomers in Electronics but also for "old timers" who need a refresher course in current developments.

ENROLL UNDER NEW G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box on reply card for G.I. Bill information.

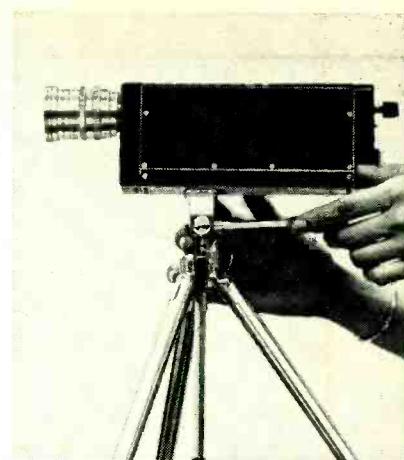Tiny TV camera for space and military use is one of the miracles of integrated circuitry. This one weighs 27 ounces, uses a one-inch vidicon camera tube, and requires only four watts of power.



Get FCC License or Money Back

No matter what kind of job you want in Electronics, you ought to have your Government FCC License. It's accepted everywhere as proof of your education in Electronics. And no wonder—the Government licensing exam is tough. So tough, in fact, that without CIE training, two out of every three men who take the exam fail.

But better than 9 out of every 10 CIE graduates who take the exam pass it.

This has made it possible to back our FCC License courses with this famous Warranty: you *must* pass your FCC exam upon completion of the course or your tuition is refunded in full.

Mail Card for Two FREE Books

Want to know more? The postpaid reply card bound in here will bring you a FREE copy of our school catalog describing today's opportunities in Electronics, our teaching methods, and our courses, together with our special booklet on how to get a commercial FCC License. If card is missing, use the coupon below.

CIE Cleveland Institute
of Electronics

1776 East 17th Street, Cleveland Ohio 44114

NEW COLLEGE- LEVEL COURSE IN ELECTRONICS ENGINEERING

for men with prior experience in Electronics. Covers steady-state and transient network theory, solid state physics and circuitry pulse techniques, computer logic and mathematics through calculus. A college-level course for men already working in Electronics.

Cleveland Institute of Electronics
1776 East 17th St., Cleveland, Ohio 44114

Please send me without cost or obligation:

1. Your 44-page book "How To Succeed In Electronics" describing the job opportunities in Electronics today, and how your courses can prepare me for them.
2. Your book on "How To Get A Commercial FCC License."

I am especially interested in:

- | | |
|--|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering | <input type="checkbox"/> Industrial Electronics and Automation |
| <input type="checkbox"/> First-Class FCC License | <input type="checkbox"/> Electronics Engineering |

Name _____ (please print)

Address _____

City _____

State _____ Zip _____ Age _____

Check here for G.I. Bill Information.

Accredited Member National Home Study Council
A Leader in Electronics Training... Since 1934

RE-74

Circle 27 on reader service card

BUILD . . .

Electronic Flash Tester

by W. G. Eslick


LATELY, I'VE HAD TO DO SOME REPAIR work on electronic photoflash units. To make the job easier, I built this tester from scrap parts. The jacks for the coil and *lite* test are insulated phone tip jacks. I picked up flash tubes and electrolytic capacitors from a camera shop. On my unit I mounted two flash tubes under a glass window

and inserted an extra toggle switch to select the desired one. One flashtube is a single turn xenon and the other is a two turn lamp.

Since there isn't any load on the transformer the capacitors charge to about peak voltage. The transformer I used is a small 640 volt CT unit (use $\frac{1}{2}$ of secondary). I installed a

PARTS LIST
 S1, S6—spst toggle switches
 S2, S3—dpdt toggles, good insulated types
 S4, 5—push button switches

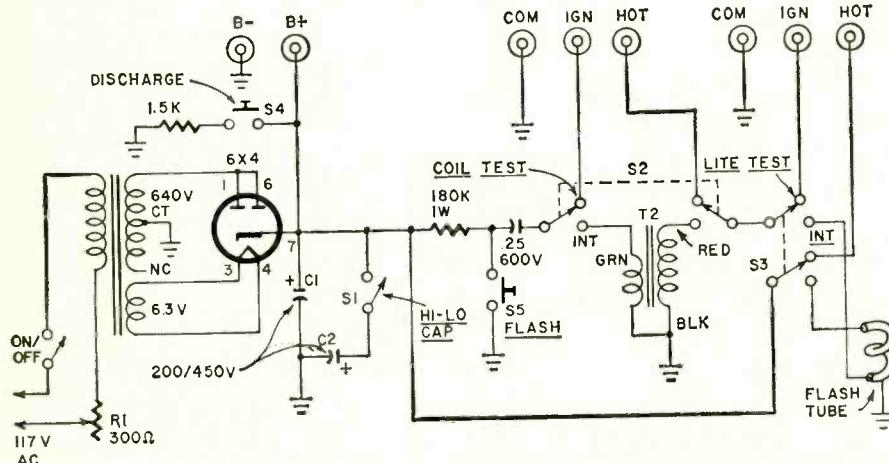C1, C2—200 μ F/450 V photoflash capacitors
 T1—power transformer, 640 ct, 40 mA
 T2—Heiland flash transformer
 Other parts from old flash units.



300-ohm pot salvaged from an old tube tester to adjust the open voltage.

The unit is quite flexible and is used to substitute parts in flash units being repaired by connecting test leads between tester and flash unit.

To test an electronic flash, disconnect the hot wire and the ignition wire from tube in the unit. Connect the three wires from the tester *lite* jacks to tube in flash unit. Set S3 to *LITE TEST* position, S2 to *internal* and S1 to *HiCap*. Turn the unit on and wait a few seconds for all capacitors to charge. Then press flash test push button (S5). The tube in the unit will fire if it is good.

To test the coil in the flash unit disconnect all leads from coil (transformer) in the unit. Connect lead from coil to the transformer in the flash unit. Make sure the hot and ignition leads are right. With S2 in *coil test* and S3 in *internal*, turn the tester on and wait a few seconds for all capacitors to charge. Then push flash push button. If the coil in the flash unit being tested is good, the strobe light in the tester will flash.

Like most service shops, a little extra work will help in slack times and most small camera shops cannot repair the flash units. A voltmeter and ohm-meter will go a long way to find the troubles, but the ignition coil and flash bulb must be tested under operating conditions.

Camera shops usually have some old trade-ins that you can get cheaply and your scrap box will furnish most of the other parts. There won't be enough work to spend a lot on test units, but for a few jobs each month, this tester will do.

R-E

BUILD . . .

Lights-on Reminder

Many arrangements have been made to warn the motorist when he turns the ignition off but inadvertently leaves the headlights on. Most attempts to provide this warning signal have used relays, but they are large, expensive, and subject to mechanical failure. For this reason, the following adaptation of a standard all semiconductor circuit was used. It is small, dependable and very inexpensive. In fact, it can be built from all new parts for around two dollars and the average hobbyist will have all the necessary items on hand.

A look at the schematic will reveal the simplicity of operation. The unit is basically a flasher which draws its operating voltage from the taillight circuit and the car's ground (points B

and C). The unit will go on or off with the light switch. However, if a connection is made between the base of Q2 and the accessory terminal on the ignition switch (point A) the unit will be turned off whenever the ignition switch is on.

Because almost any transistors can be used for Q1 and Q2, it would be best to breadboard the circuit to find the most suitable combination of parts to provide the rate of flash desired. Transistor Q1 may be any small-signal npn type and Q2 is a pnp


powered device such as a 2N301. The values on the schematic are only starting points.


Diodes D2 and D3 are necessary because these points go negative when the respective switches are in the OFF position. Diodes D1 and D2 can be any small current devices or even defective transistors that still have one good junction. However, D3 must be capable of carrying the current drawn by the lamp.

The whole unit can easily fit into a small plastic case smaller than a king-sized cigarette box and can be mounted anywhere under the dashboard away from excessive heat. Mount the signal lamp where it will most easily catch your eye as you begin to leave a car.

If your car has a positive ground, use a small-signal pnp type for Q1 and an npn power type for Q2 and reverse the polarity of the diodes and capacitors.

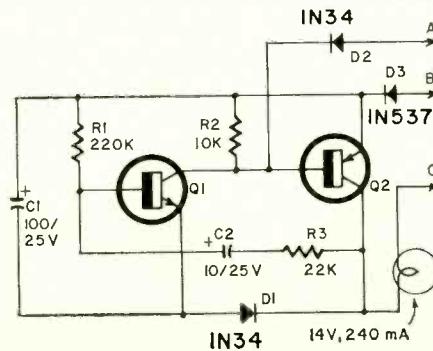Good luck and long live your battery.—Ronald F. Zollweg R-E



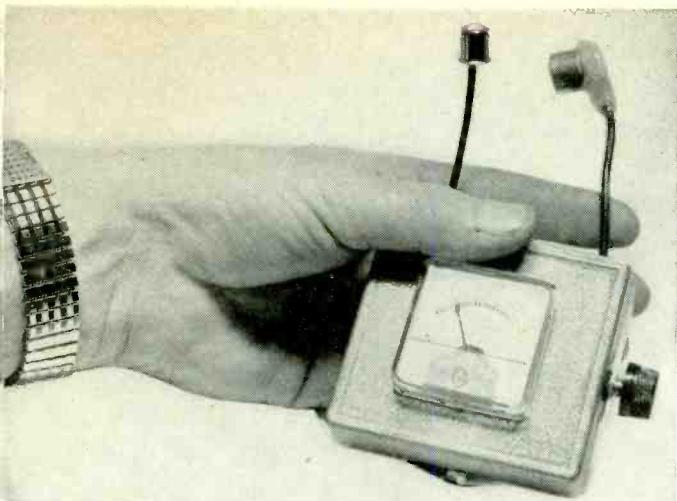

Completed unit is compact, easily fitting tube caddy. Plug goes to lead wire from horizontal output tube; cap goes on tube.

by HOMER L. DAVIDSON

HAVE YOU NOTICED A CERTAIN COLOR receiver popping 6JE6's right and left? Is that warranty tube box filling up with 6JE6 and 6DQ6 horizontal output tubes?

Correct adjustment of the horizontal efficiency coil is a key requirement in color TV repair. Improper efficiency coil settings will shorten the life of horizontal output tubes.

The horizontal efficiency coil is adjusted so the flyback transformer will run cool with minimum current. With properly controlled current through the flyback winding, the transformer lasts longer. Also, the horizontal output tube will not be driven too hard to get the correct amount of circuit efficiency.

Adjusting the hard way

The efficiency coil is adjusted with a 0-300-mA meter connected in series with the cathode of the horizontal output tube. You can also check this current in the plate circuit of the damper tube. The horizontal efficiency coil is adjusted for minimum dip on the meter.

Most color chassis in the 23- and 25-inch class have a horizontal efficiency coil in the high-voltage circuit. Generally, the coil is found on the rear apron of the color chassis. On RCA color chassis the coil is mounted upright on the etched circuit board, close to the damper and horizontal output tubes (see photo).

To insert a current meter in the horizontal output tube cathode circuit, the color chassis usually must be removed from the cabinet, or be pulled part way out.

Then someone came up with the idea of inserting a pilot lamp with two alligator clips in the plate lead of the horizontal output tube. On a dark day

HORIZONTAL EFFICIENCY COIL CHECKER

Simple solar-cell circuit makes a compact, portable checker for your shop

or in a dark corner the efficiency coil can be adjusted to a minimum brightness dip with a No. 39 pilot lamp. But if the service tech is working in a lighted room, the dip of the pilot lamp is sometimes hard to see.

Build a coil checker


It's much easier to see the needle movement of a current meter. The horizontal efficiency coil checker consists of a No. 39 pilot lamp, solar cell and 0-1-mA meter (see Fig. 1). A female plug and male cap are inserted in series with the pilot lamp. The brightness change of the pilot lamp registers on a B3M solar cell. The solar cell generates a voltage when light strikes it, which is indicated on the meter. A 5K pot will control the voltage from solar cell to meter.

When the horizontal efficiency coil is adjusted there will be a definite

point or dip indicated at the correct current setting. As a result, dim light applied to the solar cell will generate less as voltage than when more current flows through the pilot light. The pilot lamp brightness fluctuation controls the reading on the current meter.

A 3 1/4 x 2 3/4-inch plastic box was used to house the small components. A metal container is a shock hazard.

Mount the meter on the top lid of the box. Go slow when drilling holes—to eliminate cracked areas. The pilot-light assembly is mounted on the solar cell (Fig. 2). Remove the regular pilot-light bracket and wrap No. 14 copper wire around it. Bend the wire at right angles, so the pilot light is centered over the solar cell. Place the copper wire underneath the solar cell plastic framework. Push the heavy wire into the plastic solar cell

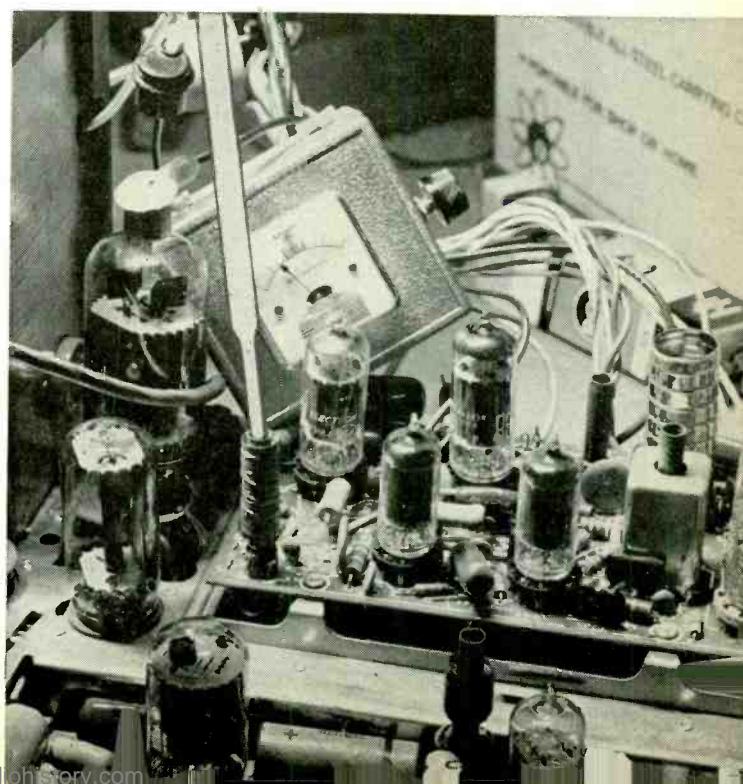

Horizontal efficiency coil location on an RCA chassis. Coil is on a PC board.

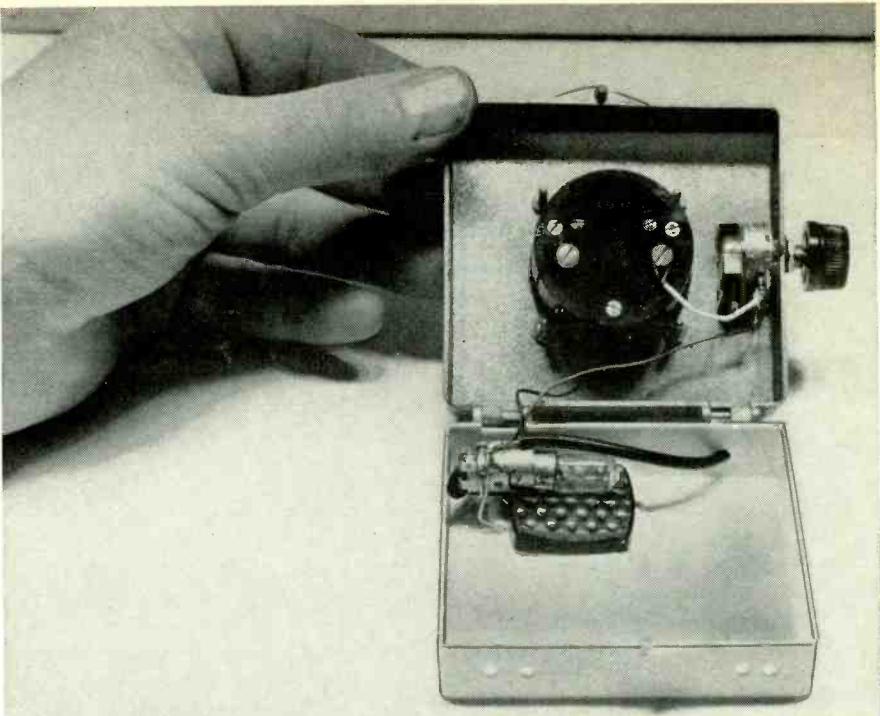
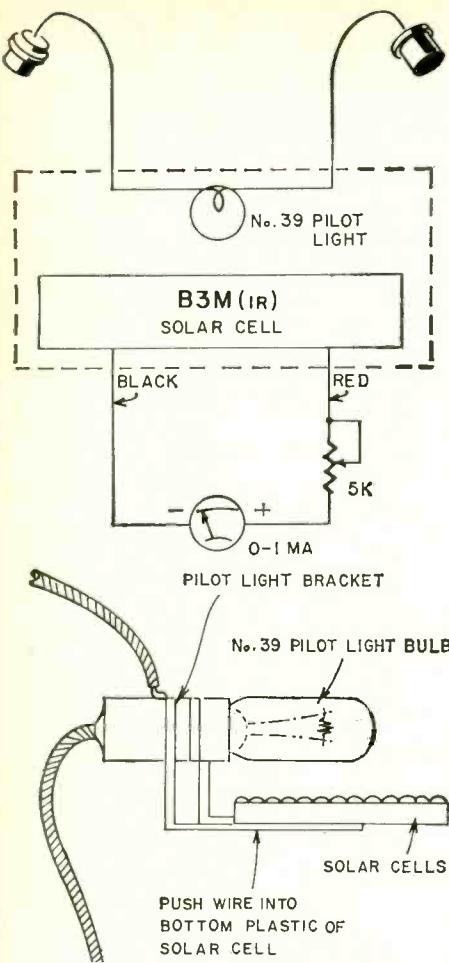


Fig. 1—(left top) Checker circuit converts hard-to-see light from No. 39 lamp into easy readout on current checker. Another version uses voltmeter in place of 0-1-mA meter. **Fig. 2—**Mount the pilot-light bracket directly on the plastic solar cell case. Meter and potentiometer can be mounted on lid of plastic box and the solar-cell assembly on the bottom. Spray the case to block light from the cell.

base while heating it with a hot soldering gun.

Run the internal lead from the pilot-light socket through a hole in the case for the male lead cap. To prevent erroneous readings from outside light, spray the inside of translucent cases with black paint. Glue the pilot-light assembly into a corner of the box. Run the black lead from the solar cell to the negative terminal of the current meter. The red or positive wire is soldered to the pot. Connect a piece of hookup wire from the other lug to meter positive.

Remove the plate cap from a defective 6DQ5 tube and solder it to the lead from the lamp socket. After soldering the plate cap in place, fill it with rubber silicone cement. A female high-voltage lead wire and plastic cap is soldered to the pilot-light assembly.

Check operation by placing a bench light over the solar cell. Adjust pot to full scale.

Unplug the lead wire from the horizontal output tube on a color chassis. Insert the male plug from the checker, and place the female cap over the horizontal output tube.

With the set on, the meter will at first shoot upwards. Don't adjust the linearity coil until the color chassis has warmed up for a few minutes. When the meter has stabilized, locate the horizontal efficiency coil on the TV chassis. Adjust the pot on the

checker so the meter reads full scale. Insert an alignment tool into the efficiency coil and turn the core until the meter dips to the lowest point or towards zero. Adjust a little farther and the meter will start to rise again. Set coil for lowest meter reading.

In the RCA CTC17 through CTC25X series chassis, adjust the core of the efficiency coil even with the bottom of the coil winding. Then adjust the core CCW to obtain a minimum meter dip. Continue to turn the core in the same direction until the cathode current increases 10 mA beyond the minimum-dip reading. Here's how the checker can be calibrated to read current.

By replacing the potentiometer with a trimmer-type pot, the horizontal efficiency checker can indicate comparative current values. Hook up the efficiency checker as described, and place a calibrated 0-300-mA meter in series with the cathode (to ground) of the output tube.

When the set warms up adjust the efficiency coil slug for maximum current on the calibrated meter in the cathode circuit. Adjust the trimmer pot for a full-scale reading on the checker meter. Mark the current on the calibrated meter dial or on a sheet of paper for reference. Remove the meter from the cathode circuit and see if there is a great change in the reading on the efficiency checker meter. You will notice a change of 0.25 mA or none at all.

Reinstall the calibrated meter in the cathode circuit and gradually decrease the current reading by adjusting the horizontal efficiency coil. Stop at 5 mA and observe the meter reading on the efficiency coil checker. Adjust for the minimum dip on the efficiency coil checker meter.

On most color receivers the best spread of current readings from adjusting the horizontal efficiency coil is 180-250 mA. Some color chassis will show only a slight change on the meter scale. Most color receivers will not pull over 220 mA; these readings are noted on the high-voltage schematic.

Another meter version

The vtm or vom will measure the voltage generated by the solar cell. For this coil checker, a smaller box may be used since the 0-1-mA meter is not used. On the vtm use a 0-2.5V dc voltage scale; on the vtv use the 0-5V dc scale.


Two small phone jacks can be used to plug in the meter probes. Construct the horizontal efficiency coil tester as shown in Fig. 1, but wire the leads that would go to the 0-2-mA meter to the phone jacks mounted on the case. Again, adjust the coil for minimum dip.

Both horizontal efficiency checkers are small enough to fit into the tube caddy for house calls. You may save several call backs and expensive 6JE6 or 6DQ5 horizontal output tubes.

R-E

The New 1970 Improved Model 257

A REVOLUTIONARY NEW TUBE TESTING OUTFIT

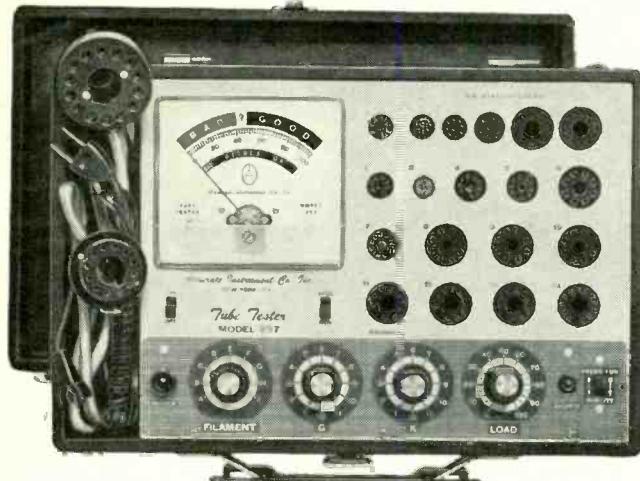

**COMPLETE WITH ALL
ADAPTERS AND ACCESSORIES,
NO "EXTRAS"**

STANDARD TUBES:

- ✓ Tests the new Novars, Nuvistors, 10 Pins, Magnovals, Compactrons and Decals.
- ✓ More than 2,500 tube listings.
- ✓ Tests each section of multi-section tubes individually for shorts, leakage and Cathode emission.
- ✓ Ultra sensitive circuit will indicate leakage up to 5 Megohms.
- ✓ Employs new improved 4½" dual scale meter with a unique sealed damping chamber to assure accurate, vibration-less readings.
- ✓ Complete set of tube straighteners mounted on front panel.

The Model 257 is housed in a handsome, sturdy, portable case. Comes complete with all adapters and accessories, ready to plug in and use. No "extras" to buy. Only

\$52.50

NOTICE

We have been producing radio, TV and electronic test equipment since 1935, which means we were making Tube Testers at a time when there were relatively few tubes on the market, way before the advent of TV. The model 257 employs every design improvement and every technique we have learned over an uninterrupted production period of 34 years.

Accurate Instrument Co., Inc.

SEND NO MONEY WITH ORDER PAY POSTMAN NOTHING ON DELIVERY

Pay Cash or in EASY MONTHLY PAYMENTS AFTER 15 Day Trial!

Try it for 15 days before you buy. If completely satisfied remit \$52.50 plus postage and handling charge. (If you prefer you may PAY MONTHLY ON OUR EASY PAYMENT PLAN.) If not completely satisfied, return to us, no explanation necessary.

ACCURATE INSTRUMENT CO., INC.

Dept. 741

2435 White Plains Road, Bronx, N. Y. 10467

Please rush me one Model 257. If satisfactory I agree to pay at the terms specified at left. If not satisfactory, I may return for cancellation of account.

Name _____

Address _____

City _____


Zone _____

State _____

Save Money! Check here and enclose \$52.50 with this coupon and we will pay all shipping charges. You still retain the privilege of returning after 10 day trial for full refund.


Circle 28 on reader service card

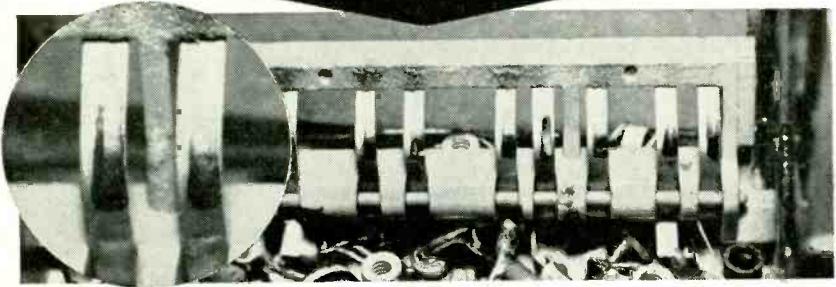HERE'S PROOF TUN-O-FOAM KEEPS TUNERS WORKING BETTER, LONGER!



**THIS TUNER
WAS USED AS IT
CAME FROM THE MANUFACTURER**

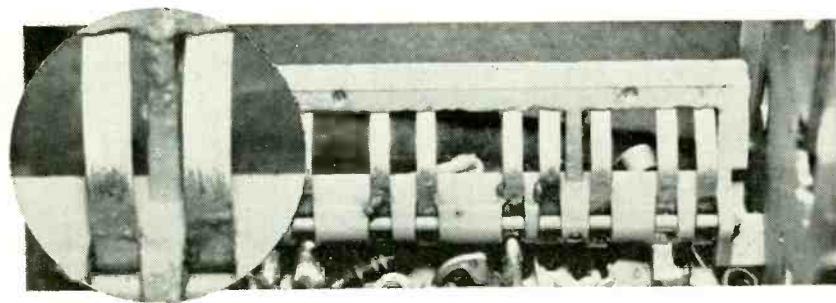After 36,000 revolutions, the silver has been worn away. The tuner does not function on any channel.



**THIS TUNER
WAS SPRAYED WITH TUN-O-FOAM**

After 36,000 revolutions there is no sign of wear. The tuner brings in all channels, sharp and clear.

THE PROFESSIONAL'S TV TUNER CLEANER

Foams into the tightest places. Won't cake up, dry out or detune. Keeps cleaning and lubricating contacts each time channel is changed. Guaranteed to be the best tuner lubricant cleaner you've ever used, or money refunded. Six-month no-callback guarantee.



1260 RALPH AVENUE,
BROOKLYN, N.Y. 11236

For export: ROBURN AGENCIES INC., NEW YORK, N.Y. 10014
In Canada: MAGNASONIC CANADA LTD., MONTREAL 9, CANADA

Circle 29 on reader service card

ULTIMATE STEREO TUNER

(continued from page 40)

nal can be heard from the speaker.

2. With the plates of C1 fully meshed adjust L2, L3, L4, and L6 for maximum quieting of the received signal. Reduce the generator output as needed so that the signal is always slightly noisy. Use a small nylon or fiberglass tool to move the coil turns.

3. Set the generator output to 107.8 MHz and set C1 so its plates are at minimum capacitance. Peak each trimmer capacitor on C1 for maximum quieting, as well as C25.

4. Repeat steps 2 and 3.

5. Set generator output frequency to a quiet spot near the upper end of the dial, around 105 to 106 MHz. Tune the receiver to this frequency and repeat the trimmer on L4 for best quieting. "Rock" C1 about this point while adjusting this trimmer since there is some interaction between peaking this trimmer and the local oscillator frequency. If you do not rock C1 you may only succeed in "fine-tuning" the oscillator frequency and sensitivity will be reduced from optimum.

6. Repeat steps 2, 3, and 5.

7. Tune C1 to a quiet spot near the bottom of the dial and adjust R25 for maximum quieting on a very weak input signal. At this time you may wish to check the sensitivity. It should be 20 dB quieting at less than 1 μ V input. L1 should be spaced about 1/8 inch below L2. If sensitivity is too low, carefully push L1 closer to L2 and repeat the antenna trimmer capacitor at 107.8 MHz and adjust the turns on L2 at 88 MHz. Ten sets of transistors were tried in the prototype unit and sensitivity varied between 0.95 to 0.55 μ V for 20 dB quieting.

MULTIPLEXER

You will need an oscilloscope and a multiplex generator to align this section. An ac vtm is also helpful when making separation measurements.

1. Connect the scope vertical input to the wiper of R204 and inject a 67-kHz input at the input to the multiplex board at C201. Tune the slug in T202 for a minimum output as seen on the scope.

2. Connect the scope to the Q202 end of C202. Inject a 19-kHz pilot signal at a 25-mV rms level and tune T201 for maximum trace height.


3. Connect the scope to the collector end of C206 and set S202 to the MONO position. Tune T203 and T204 for maximum trace height. Reduce the input level of the generator and carefully repeak the tuning of

transformers T201, T203 and T204.

4. Connect the scope to either channel A or B output and inject a 19-kHz signal at 25 mV rms. Tune oscillator transformer T205 for zero beat as observed on the scope. S202 must be in the STEREO position.

5. Connect the scope to either end of C214 and tune T206 for maximum 38-kHz trace height.

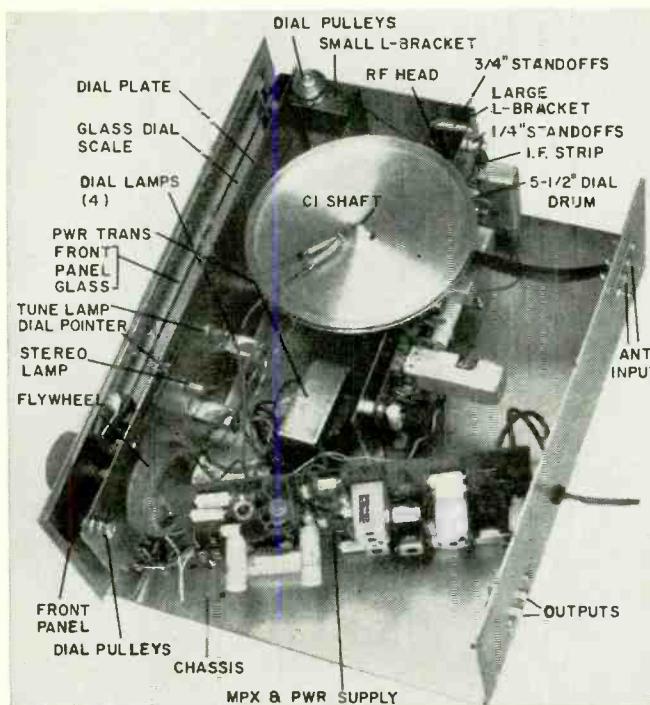6. Set up the generator to deliver a 0.25V rms L-only or R-only composite signal to the input. Connect the scope vertical input to channel A



Chassis layout of tuner sections used by the author. A large L-bracket supports i.f. and rf boards. C1 is mounted on rf board, concealed by dial drum here.

PICK UP MORE STATIONS - ON ANY RADIO WITH



This Radio Antenna Booster will pull in distant radio signals never received before, and will boost weak reception in remote areas. Great for campers, trailers, motor homes. No batteries or electrical hook up—lasts indefinitely. *Dealer inquiries invited.*

\$8.50

postpaid plus tax where applicable


RUSSELL PRODUCTS
3651 Oakley, Riverside, Ca. 92506

Circle 30 on reader service card

99.99% reliable

Every now and then, one of our tubes fizzles—and somehow it's the one you install. Even we don't know how you happen to receive that particular tube. But we do know that it doesn't happen more than once in thousands of times. Raytheon receiving tubes—including Raytheon Tubes for Imported Sets—have to be extra reliable. Because, Raytheon is the leading independent supplier of receiving tubes to independent servicemen. We don't have competing service trucks or retail outlets. So, we depend on you just as much as you depend on us.

RAYTHEON

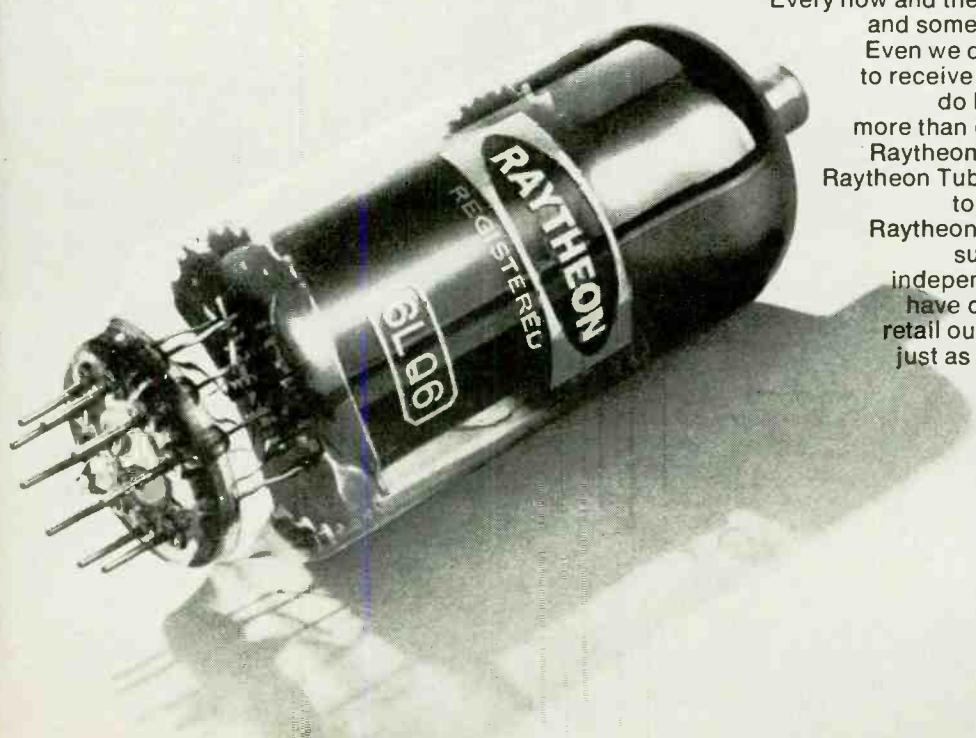

Circle 31 on reader service card

and the horizontal input to channel B. Slowly tune T205 until the scope is displaying either a vertical line or a horizontal line. One of the settings of T205 will be very unstable; use the setting which is the most stable and connect the scope so that an L-only input gives a vertical line.

7. Repeak T201 for the most vertical line and adjust R204 for the best vertical line. Switching to an R-only input should result in a horizontal line on the scope.

8. Inject an L plus R signal, with pilot, and set R232 and R233 for equal outputs from each channel. **R-E**

SPECIAL TUNER PARTS

The following special parts are needed for the construction of the tuner. All are available from Transitek, P.O. Box 98205, Des Moines, Washington.

Tuning capacitor C1	\$7.50
Miller coil No. 9051	\$2.04
Miller coil No. 2072	\$2.58
Miller coil No. 1354PC	\$2.61
Miller coil No. 1355PC	\$2.61
Miller coil No. 1361	\$1.80
Fairchild 2N3690	\$1.25
Crystal filter	\$13.50
Rf printed circuit	\$5.90
If printed circuit	\$7.20
Mx and power supply printed circuit	\$9.20

COMPLETE TUNER PARTS LIST

PARTS LIST RF HEAD

All resistors are $\frac{1}{4}$ W, 5% unless noted as $\frac{1}{2}$ W.

R1, R4	—47 ohms
R2, R7	—330 ohms
R3, R8	—4700 ohms
R5, R22, R24	—1500 ohms
R6, R9, R14, R29	—100 ohms
R10, R16, R23	—220 ohms
R13	—12,000 ohms
R15	—100,000 ohms
R21, R26, R30	—10,000 ohms
R25	—2500 ohms, $\frac{1}{4}$ -watt trimmer
R31	—1200 ohms
R32	—4700 ohms
R11	—470 ohms, $\frac{1}{2}$ watt
R12	—150,000 ohms, $\frac{1}{2}$ watt
R17	—33,000 ohms, $\frac{1}{2}$ watt
R18	—4,700 ohms, $\frac{1}{2}$ watt
R19	—510 ohms, $\frac{1}{2}$ watt
R20	—180 ohms, $\frac{1}{2}$ watt
R27	—220 ohms, $\frac{1}{2}$ watt
R28	—100 ohms, $\frac{1}{2}$ watt

Capacitors

*C1	—4 gang FM tuning capacitor, (2-17 pF per section. Trimmer range 0.5 to 12 pF. Only three trimmers are used. Local oscillator section uses separate trimmer.
C2, C17, C21, C22	—6.8 pF, NPO ceramic
C3	—3.3 pF, NPO ceramic
C4, C5, C6, C8, C9, C10, C16, C19, C20, C23	—.02 μ F, 25V cer.
C7, C12	—.001 μ F, ceramic
C11	—70 μ F, 20V electrolytic (Mallory MTA-70E20 or equiv.)
C13	—.05 μ F, 25V ceramic
C14	—68 pF polystyrene
C15	—200 pF polystyrene
C18	—1 μ F, 50V electrolytic (Mallory MTA-1D50 or equiv.)
C24	—350 μ F, 15V electrolytic (Mallory MTA-350 F 15 or equiv.)
C25	—3-12 pF ceramic trimmer (Centralab 822FZ or equiv.)
C ₁	trimmers on C1

Semiconductors, coils

Q1, Q2	—2N3690 (Fairchild)
Q3	—3N141
Q4, Q5	—MPS 6939
Q6	—2N3856
D1	—10V Zener diode, 1W, 5%
L1	—2T, #26 enamel, next to ground end of L2
L2	—4T, #18, $\frac{1}{4}$ " dia, 7/16" long
L3	—4T, #18, $\frac{1}{4}$ " dia, 7/16" long, tap at 1T and 3T
L4	—same as L3 but tap only at 3T
L5	—2T, #18, 5/16" dia, $\frac{1}{4}$ " long, tap at $\frac{3}{4}$ T from C1d
L6	—J.W. Miller 9051

IF Strip (101 to 199 series)


C101, C103, C105, C106, C107, C108, C109, C110, C113, C114, C119, C120, C126, C127, C128, C129, C130, C131, C132	—.02 μ F, 25V ceramic
C102	—6.8 pF, NPO ceramic
C104, C111, C112, C123	—.05 μ F, 25V ceramic
C115	—5 pF, polystyrene
C116, C117, C118	—330 pF ceramic
C121	—5 μ F 50V electrolytic (Mallory 5D50 or equiv.)
C122	—350 μ F 15V electrolytic (Mallory 350 F 15 or equiv.)
C124, C125	—omit due to design change

Resistors all $\frac{1}{4}$ watt 5% unless noted

R101	—560 ohms, $\frac{1}{2}$ watt
R102, R112	—47,000 ohms, $\frac{1}{2}$ watt
R103	—10,000 ohms, $\frac{1}{2}$ watt
R104, R111, R120	—2200 ohms, $\frac{1}{2}$ watt

(continued on page 91)

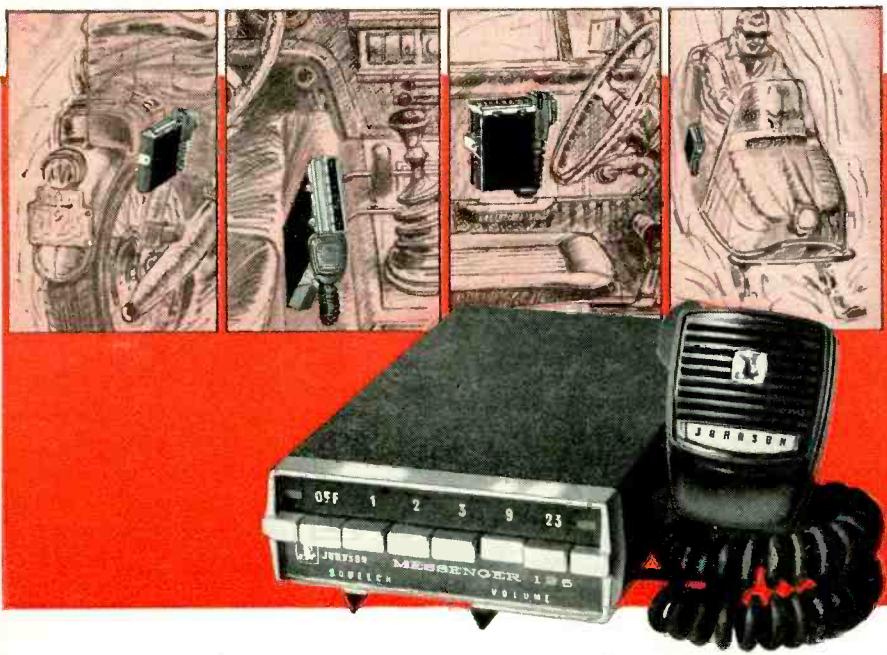Try these installations with any other five watt unit!



At \$99.95 the Messenger 125 fits anywhere...including your budget.

Best of all, even with its mini-size and price, the Messenger 125 is *big* on performance. Its 5-watt transmitter, with high level class B modulation and speech compression, gives it all the "talk power" you'd expect from a full-size radio. Half-a-microvolt receiver sensitivity pulls in the weak ones. Automatic threshold noise limiting, IF clipping, and special AGC circuitry means less noise—better quieting. Full 2-watt audio lets you hear even in noisy vehicles. And the Messenger 125 looks great, too. Not a single knob—push-buttons select up to 5 channels, slide-levers adjust squelch and volume. Installs between bucket seats, in door pockets, on trail bikes—or over your shoulder with its optional rechargeable battery pack.



Dimensions: $1\frac{1}{8}$ " High x $4\frac{1}{8}$ " Wide x 7" Deep • 4-watts output at 13.8 VDC•FCC type accepted, DOC approved • All solid state—draws just 0.2 amperes on squelched stand-by • Optional portable pack available with rechargeable battery, charger, antenna, and leather carrying case



E. F. JOHNSON CO.
WASECA, MINN. 56093

Circle 32 on reader service card

NEW PRODUCTS

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card at the left and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.

MINI-SPEAKER, Minimus 0.5, 10 watts to 8 ohms through screw terminals or phono jack. Surprisingly heavy, the extra weight is due to materials that



minimize effects of small size. $4\frac{1}{4} \times 6\frac{1}{2} \times 4\frac{1}{4}$ ". Walnut case; die-cast aluminum frame. Catalog No. 40-1995. \$9.95. Radio Shack, 730 Commonwealth Ave., Boston, Mass. 02215

Circle 46 on reader service card


CIRCUIT BREAKER. Sans-A-Fuse is color-coded in 12 models for temporary or permanent replacement of blown TV chemical or amp fuses. Fits chassis sockets; can help find cause of breakdown.



Can be left in set when repair is made.—Workman Electronic Products, Inc., Sarasota, Fla.

Circle 47 on reader service card

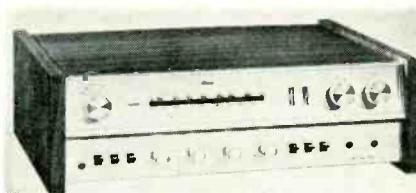MULTIPLEX RECEIVER, model RA-195, solid-state, 175-watt IHF, FM-AM-FM Stereo, uses two IC's and FET. Has FM sensitivity of $1.5 \mu V$ for 30 dB



quieting, over 30 dB stereo separation, 30-20,000 Hz, ± 3 dB frequency response. Loudness compensation +13 dB @ 50 Hz +4 dB @ 10 kHz. Hum and noise, -55 dB (mag phono). Output impedance, 4, 8, and 16-ohm. 25 transistors plus 14 diodes. $18\frac{1}{16} \times 5\frac{1}{8} \times 14\frac{1}{4}$ ". Uses 110-120 volts ac, 50/60 cps. \$249.98. Olson Electronics, 260 So. Forge St., Akron, Ohio 44308

Circle 48 on reader service card

SCHOOL INTRUD-ALARM changes building's PA speakers into microphones that detect noises in 1,000-to 5,000-Hz range using CA-21 Intrusion Detector. Inherent sounds such as heaters, clocks or compressors, outside noises such as car horns or backfires, and natural sounds such as lightning and thunder will not set off alarm. Internal audible



alarm can be triggered to scare intruder, or remote alarm (CA-22) may be sent over telephone wires to police station. CA-22 panel allows up to 9 school buildings to be monitored by same unit. System can be switched to battery supply in case of ac power failure. Can use magnetic detector switches on windows and doors, if desired. Bogen Communications Div., Lear Siegler, Inc., PO Box 500, Paramus, N. J. 07652


WIRELESS SMOKE AND FIRE ALARM, model SW-440. Features solid-state circuitry. Equipped with sensitive smoke and heat detectors, emergency pull chain, extra ac outlet for additional signal devices, and provisions for adding external heat sensor. Heat sensor activates



at 135°F . Powerful buzzer. $5\frac{1}{2} \times 7 \times 2\frac{1}{2}$ in. 110-120V ac, 50/60 cps. \$59.98. Olson Electronics, Inc., Akron, Ohio.

Circle 49 on reader service card

PLASTIC FOAM CUTTER, Model Machine, makes rip cuts, cross cuts, freehand, angle, circular, arc and filigree cuts up to 6 in. deep. Makes dovetails, miters and interlocking joints. Cutting wire works by melting fine cut. No batteries. Low-voltage transformer gives high or low heat for change of speed and width of cut. Ruled grid on base and sliding platform and adjustable fence lock in all positions for accuracy,

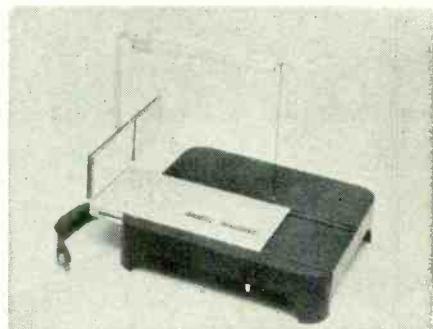

$3\frac{1}{2}$ lb. Uses 117-volt outlet, 8 watts. Guaranteed against all defects for 1 year. \$44. High-density foamed polystyrene comes in standard packs or custom-cut large blocks. Tightly packed closed cells are good for precision work. 400 cu. in. of assorted high- and low-density foam supplied with order. Waterproof and weather-resistant. Order details for additional foam come with order. Technical Devices, 1402 Norman Firestone Rd., Goleta, Calif. 93017.

Circle 50 on reader service card



TAPE STORAGE ALBUM, Stor-A-Pac, holds 6, 8 or 12 cassettes or 8 cartridges. Bookstyle, rigid construction prevents damage and keeps tapes dust-free. High-

AT LAST . . .

TRANSITEK'S CATALOG
IS READY!

MANY NEW UNPUBLISHED
PROJECTS COMPLETE DE-
SCRIPTIONS GIVEN.

NEW KITS . . .

4 CHANNEL PREAMP
4 CHANNEL POWER AMP.

STUDIO QUALITY TAPE
ELECTRONICS

PROFESSIONAL PREAMPLIFIER

LEGAL CORDLESS PHONE —
WITH DIALING

RADAR TYPE ALARM SYSTEM
— COMPLETE

plus TUNERS, TESTGEAR —
MANY OTHERS

Send 25¢ in coin for
catalog & supplements to:

TRANSITEK

PO Box 98205, Des Moines, Wash.
98016

Circle 106 on reader service card

**MILLIONS ARE
SPENT TO FIX
2-WAY RADIOS.
WHAT'S YOUR
CUT?**

If you'd like to get into a top-paying job, maybe FM 2-way radio is for you. Each year, more and more businesses are buying 2-way. That means service. And service means money. We can train you to get in on the action. Our special home study course is the place to start. We teach you FM 2-way radio servicing, and prepare you for an FCC license.

- Send me FREE Evaluation Examination
- Send details on Home Study Course on FM 2-way radio servicing.
- Send details on how you can prepare me for an FCC license.

Name _____ Occupation _____

Address _____

City _____ State _____ Zip _____

MOTOROLA
TRAINING INSTITUTE

1301 Algonquin Road, Schaumburg, Ill. 60172




Circle 107 on reader service card

gloss warm blue, hot red and black embossed leatherette. From \$3.49 to \$4.98 each. Modern Album and Finishing Co., Inc., 119-01 22 Ave., College Point, N.Y. 11356.

Circle 51 on reader service card


MUSIC SYSTEM, *Landmark 100*, includes AM/FM stereo tuner, record changer, *Acoust-Array* speakers, *Servo-Linear* motion feedback circuit in amplifier, *Garrard* automatic turntable. Speakers use 3 full-range loudspeakers and tweeter in small truncated cube enclosure. One faces forward; others placed asymmetrically at back of cabinet. Multi-directional radiation enlarges sound. Since speakers are angled, stereo aspect can be varied by placing speaker on its sides. Walnut-finished cabinets with dark brown grille cloths. 10 x 10 x 10". *Servo-*

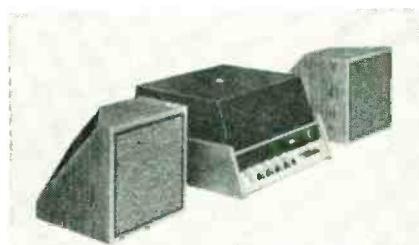

Linear motion feedback corrects any distortion from loudspeakers. Circuits sample actual movement of speaker cone compared to input signal and correct any difference through negative feedback. Amplifier has all-silicon transistor cir-


cuitry; is rated at 100 watts music power (± 1 dB), 80 watts IHF. AM/FM stereo tuner uses all-silicon transistor circuitry with FET front end for picking up weak signals without interference. Four integrated circuit chips perform functions of AM/IF, FM/IF, and multiplex. *Garrard* turntable has *Stereo-V* magnetic cartridge using dual magnets, one for each channel. High stereo separation, low mass, and excellent tracking ability. Moving system resonance above 20,000 Hz. \$399.95. Plastic dust cover, \$14.95. *Electro-Voice*, Inc., Buchanan, Mich. 49107.

Circle 52 on reader service card

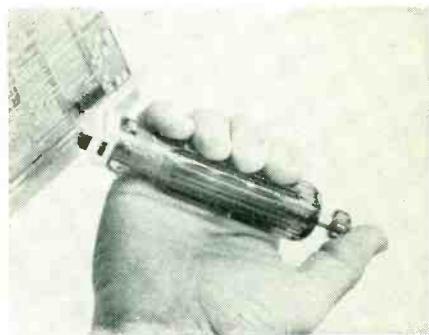

IC INSERTION TOOL, spring-loaded, designed for inserting D.I.P.'s into printed circuit boards. Picks up and squeezes D.I.P.'s to fit hole pattern, then ejects them when firmly placed in circuit board. \$8.90. #52. *Hunter Tools*, 9851 Albertus Ave., Santa Fe Springs, Calif. 90670.

Circle 53 on reader service card

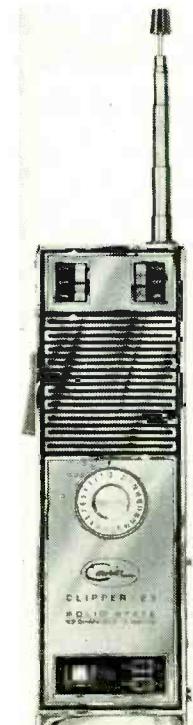

CB TRANSCEIVER, "Clipper 23", 23 channel and all solid state, includes 19 transistors, 4 diodes, 2 varistors, and 2 thermistors. Power input: 5 watts at 100% modulation with an effective inland range of 10 miles. Sensitivity: 0.25 μ V. Equipped with a full complement of jacks for PA systems, external earphone, a 2- $\frac{3}{4}$ " speaker, antenna, mike and power connection. \$159.95 complete with a leather carrying case. — *Courier Communications Inc.*, Newark, N.J.

Circle 54 on reader service card

RADIO ANTENNA BOOSTER, designed for campers, motor homes and trailers will last indefinitely (no batteries). For use in remote areas where reception is weak and where radio signals





COLOR ORGAN, Knight-Kit model KG-338. Solid-state 3-channel circuitry separates high, middle, low frequencies into blue, green and red lights giving 3-dimensional display through prismatic screen. Connects to speaker terminals of any receiver, amplifier or console. \$34.95 complete with vinyl-clad wood case, simulated walnut veneer. 8 $\frac{1}{4}$ x 14 $\frac{1}{4}$ x 5 $\frac{1}{4}$. Allied Radio Corp., 100 N. Western Ave., Chicago, Ill. 60680.

Circle 56 on reader service card

are not normally received. Clip short wire with alligator clip to metallic object such as window screen, door frame or water pipe. Long wire goes through window or door to outside. String it out full length and lay it on ground. Place unit behind radio and move unit to find maximum volume. 4 $\frac{1}{2}$ x 1" x $\frac{1}{2}$. **Russell Products**, 3651 Oakley St., Riverside, Calif. 92506.

Circle 55 on reader service card

STEREO RECEIVER, KR-7070, features AM, FM or FM multiplex tuning system and auto-tuning circuit that selects only FM stations, giving instant pinpoint tuning. Its 4 IC's and crystal filter FM i.f. stages provide selectivity and 1.5 dB capture ratio; 3-FET, 4-gang tuning capacitor FM front-end delivers 1.5 μ V sensitivity and spurious response ratio. FET mechanical filter AM tuner section. Dynamic amplifier section with power bandwidth of 10 to 30,000 Hz (IHF)

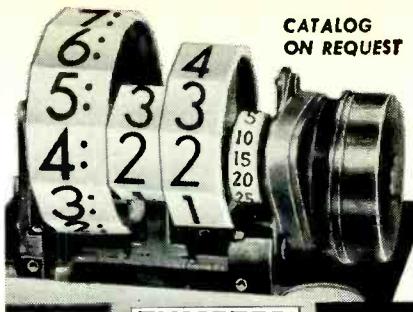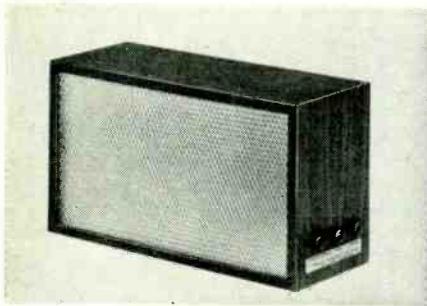

CATALOG
ON REQUEST



CLOCK MOVEMENTS

DIGITS RESETTABLE INDIVIDUALLY

Available in 50, 60 cyl., all voltages, AC, UL approved motor, cord. One Year Guarantee.

#130...12-HOUR #131...24-HOUR



Made in U.S.A.

Complete Line: Delay, Interval and Cycle Timers, Digital Computers

PENNWOOD NUMECHRON CO.
TYMETER ELECTRONICS

7249 FRANKSTOWN AVE., PITTSBURGH, PA. 15208

Circle 108 on reader service card

SELECT FROM TWO OF THE MOST USEFUL ELECTRONICS PRODUCTS AVAILABLE TODAY

THE MARK TEN CAPACITIVE DISCHARGE IGNITION SYSTEM

is time tested to give your car added performance. Carefully engineered, the Mark Ten electronic ignition system incorporates the advantages of capacitive discharge with those of solid state electronics. The largest selling unit of its type on the market today, the Mark Ten out performs all other known ignition systems regardless of price.

Compare these advantages:

Up to 20% increase in gasoline mileage • Installs in only 10 minutes on any car or boat without rewiring • Points and plugs last 3 to 10 times longer • Instant starts in all weather • Dramatic increase in acceleration and overall performance • Virtually eliminates ignition tune-ups.



Only \$44.95 ppd.
Assembled / \$29.95 ppd.
Kit Form



DETALENT, the all new ultrasonic silent sentry, is a total motion detection, intrusion and monitoring alert system. The system plugs into any wall outlet. It also features variable sensitivity control and adjustable timing which provides the most advanced sentry system on the market.

Specifications:

Ultrasonic Frequency: 35 KHZ △ Area Coverage: 15-30 feet (depending on shape of area)
△ Controls: On-Off Switch; Built in Timer; Variable Sensitivity Control △ Output: 110-130V at 1 Amp. △ Power Requirements: 110-130V, 60 Hz AC △ Dimensions: 10 $\frac{1}{4}$ "W x 3 $\frac{1}{4}$ "H x 3 $\frac{1}{4}$ "D △ Complete with 110-130V Drop Cord △ Walnut designer finish.

For Complete Unit, Ready to Use.....ONLY \$59.95 ppd



DELTA PRODUCTS, INC.

DP 70-3

P.O. Box 1147 RE/Grand Junction, Colo. 81501

Please send me literature immediately.

Enclosed is \$ _____ Ship ppd. Ship C.O.D.
Please send Mark Tens (Deltakit®) @ \$29.95; (12 Volt Positive or Negative Ground Only); Mark Tens (Assembled) @ \$44.95; Volt: Negative Ground only. 12 Volt: Specify. Positive Ground; Negative Ground; DeltAlert.


Car Year _____ Make _____

Name _____

Address _____

City/State _____ Zip _____

Circle 109 on reader service card

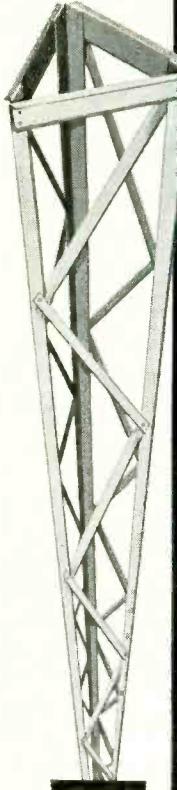

AL SERIES ALUMINUM TOWERS for uhf - vhf

Ideal for mounting industrial, commercial, citizens band, amateur, or television receiving antennas. Exceptional strength in proportion to weight qualities. Easy access to equipment mounted on the Microflect top mast extension. Other features are:

- To 120 feet high in easy to erect 10 foot sections.
- Available factory assembled or in kit form.
- Lightweight, all aluminum, 10 foot sections weigh only 12½ lbs.
- Low maintenance, will never rust or require painting.
- Staggered ladder treads for easy climbing.
- Can be used for direct radiator at HF.
- Wide variety of mounting brackets and accessories available.

DISTRIBUTOR INQUIRIES INVITED


MICROFLECT

3675 25TH STREET
SALEM, OREGON 97302
AC 503-363-9267 TWX 510-599-0107

Circle 110 on reader service card

Play Ball with Perma-Power

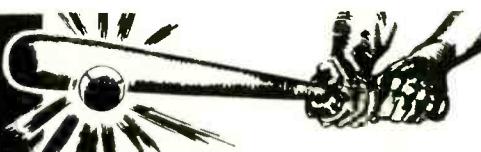an official Rawlings League Baseball
is your gift from Perma-Power
when you buy
three Color Briteners at the
lowest price ever!



You get these top selling Color Briteners that put back brightness to fading color pictures.

two Perma-Power Color Brite Model C-511 (Parallel wiring 90° small-button diheptal base) (Rectangular Color Tubes)
Regular Price \$5.85

one Perma-Power Color Brite Model C-501 (Parallel wiring 70° shell neodiheptal base) (Round Color Tubes)
Regular Price \$5.65

Regular price for all three is \$17.35. With this limited time offer you pay only \$15.50 and the baseball is FREE.

FREE!

"Always rely on Perma-Power Briteners to extend useful picture tube life for months, preserve excellent customer relations for years!"

Perma-Power®

Chamron Electronics
845 Larch Avenue, Elmhurst, Illinois 60126

Circle 111 on reader service card

and main input frequency response from 5 Hz to 120,000 Hz (± 1.5 dB) drives low-efficiency speakers. 2 pairs of phono input jacks, 2 pairs of stereo speaker output terminals and separate preamp outputs and main amp inputs permit unlimited system expansion. Automatic Protection Circuit (U.S. Pat.) protects power transistors from blowouts. Has individual 2 dB step-type tone controls for bass and treble, new presence control, which gives effect of changing proximity to sound, and 20 dB audio muting switch for temporary pause for quiet, such as phone call. \$549.95. KENWOOD, Dept. P, 15711 So. Broadway, Gardena, Calif. 90247.


Circle 57 on reader service card



ALIGNMENT SET for color TV-FM-/AM consists of 7 glass-filled polymer plastic tools. Three come in a hexstopper type shank and two in hex through type with diameters of 0.078" and 0.101". One 0.101" nonmagnetic metal-tipped insulated oscillator screw adjustment tool withstands 10" oz. torque. Also, a nonmetallic trimmer adjuster with a conical point probe measures 0.025 x 0.156".—JW Electronics, Plastic Div., Bloomington, Ind. 47401.


PORTABLE VOLTMETER, Master Volt-Ohmyst, RCA WV-510A, all solid-state, measures dc voltage from 0.01 to 1,500V, dc from 0.01 mA, to 1.5 amps, ac voltage from 0.2 to 1,500V, ac peak-to-peak voltage of complex waveforms from 0.5 to 4,200V, and resistance values from 0.2 ohms to 1,000 megohms. 7 overlapping ranges given for ac, resistance, and current measurements, and 8 ranges for dc voltage measurement. Accuracy: $\pm 3\%$ of full-scale reading. Zero stability and linearity, low current drain. Battery test function provided. Input resistance of 21 megohms on most critical low-impedance

Circle 58 on reader service card

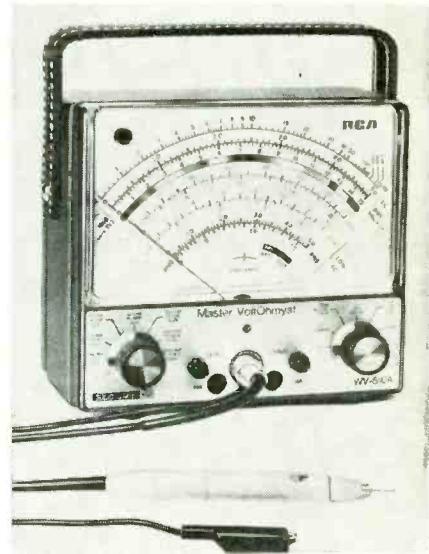

circuits. Has large, easy-to-read, 2-color meter with mirror scale. 6 $\frac{1}{2}$ x 5 $\frac{1}{4}$ x 3 $\frac{1}{2}$ in. 3 $\frac{1}{2}$ lb. Comes with dc/ac-ohms probe with flexible shielded input cable (type WG-401A) with BNC connector, slip-on alligator clip, current test leads, one RCA VS036 battery and instructions book. \$128. Accessories available: WG-301A crystal-diode slip-on probe for measuring rf from 50 kHz to 250 kHz; WG-411A high-voltage slip-on probe for measuring up to 50,000V dc; WG-436A multiplier resistor. Commercial Engineering, RCA Electronic Components, Harrison, N. J. 07029.

Circle 59 on reader service card

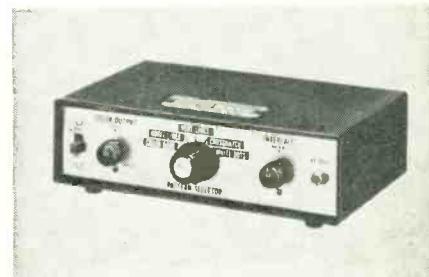

MINI COLOR GENERATOR, the Caddy Bar, Model CG19, generates color bars, crosshatch, white dots, vertical and horizontal lines. Features reduced circuit drain and, full voltage regulation on all circuits, increases battery life. Timer range doubled. Nearly impossible to have timer jump at any time. Timer controls are screwdriver adjustments. \$84.50. 2 lb. Sencore, Addison, Ill. R-E

Circle 60 on reader service card

NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader's Service number are free for the asking. Turn to the Reader's Service Card facing page 75 and circle the numbers of the items you want. Then detach and mail the card. No postage required!

COMPONENT SELECTOR CATALOG features resistors, rheostats/potentiometers, trimmers, tap switches, variable transformers, capacitors, relays, power controls (solid-state), light dimmers, rf chokes, meter saver, and design aids. 35 pages. Catalog 300A. Free from **Olmite Mfg. Co.**, 3660 Howard St., Skokie, Ill. 60076.

Circle 61 on reader service card

SCOTT STEREO COMPONENTS AND SPEAKERS CATALOG covers AM/FM stereo receiver and stereo cassette recorder, tuners and amplifiers, controlled impedance speakers, compact systems, stereo kits and stereo consoles. Free. **H. H. Scott, Inc.**, Dept. P, Maynard, Mass. 01754.

Circle 62 on reader service card

1970 CATALOG OF ELECTRICAL AND HOBBYIST BOOKS available free covers schematic/servicing manuals, broadcasting, basic technology, CATV, electric motors, electronic engineering, reference; television, radio and electronics servicing; audio and hi-fi, hobby and experiment, test instruments, and transistors in over 125 current and forthcoming books. Features newly revised 1970 edition of *Popular Tube/Transistor Substitution Guide* and, scheduled for publication March 15th, *Small Appliance Repair Guide*. **Tab Books**, Blue Ridge Summit, Pa. 17214.

Circle 63 on reader service card

Write direct to the manufacturers for information on items listed below:

1970 TELEVISION PARTS REPLACEMENT GUIDE. Stancor color and monochrome parts lists 500 transformer and deflection components, and replacement parts for 200 TV manufacturers in part-to-part cross-reference guide. Added section covers flybacks, deflection yokes, vertical outputs, power and output transformers and filter chokes, plus several pages of schematics. For free copy. **Essex International, Inc.**, Controls Div., Stancor Products, 3501 W. Addison St., Chicago, Ill. 60618.

PANEL INSTRUMENTS CATALOG features over 1,500 stock ranges, sizes and types. Includes quick-reference index on cover for getting ranges and types in desired case style. Introduces new Century series with rugged phenolic and glass construction; Model 2800 digital panel instruments with advanced IC design, nonblinking readouts which change only when measured value changes; accuracy $\pm 0.1\%$, with resolution of 1 part in 1000. Bold-Vue 3-hole mount instruments, contactless controllers and illuminated Designer series VU instruments. Catalog has panel instrument characteristics chart and glossary of terms. All items "off the shelf" delivery. **Bulletin 2801**. **Simpson Electric Co.**, 5200 W. Kinzie St., Chicago, Ill. 60644.

POWER SUPPLIES CATALOG features dc power supplies intended for use in DTL, TTL and MOS logic circuits; SR modular supplies from 3.6V to 48V with currents up to 35 amps. Militarized modular power supplies from 3.6V to 48V with current to 20 amps in 5V package meet all requirements of MIL-E-16400, MIL-T-21200, and MIL-E-4158 basic equipment specs with full power ratings to 71°C. Also has high-performance flat-pack military modular and ultraminiature power supply units. Powertec Div. **Airtronics, Inc.**, 9168 DeSoto Ave., Chatsworth, Calif. 91311. **R-E**

Now it costs less to own the best oscilloscope you need.



The New RCA WO-505A Solid-State Oscilloscope

RCA

*Inexpensive Quality

†Optional Distributor Resale Price

The best you need is the new 5-inch RCA WO-505A, all solid-state oscilloscope. It makes yesterday's general-purpose 'scopes look old-fashioned.

At just \$298.50[†] the WO-505A offers an unmatched list of features usually found only in more expensive, laboratory type instruments. For example there's the all solid-state circuitry...an illuminated graph screen calibrated directly in volts, and a deep-lip bezel for exceptional clarity. The regulated power supply minimizes trace bounce and provides excellent stability. And the camera mounting studs offer still more evidence of the functional value built into the new WO-505A.

But you've got to see this new RCA 'scope in operation—see the sharp, clean trace it provides—to appreciate it. Some statistics:

- High-frequency response, usable to 8 MHz.
- High Sensitivity (.05 V p-p range).
- DC vertical amplifier; DC/AC input.
- Return trace blanking...Trace polarity reversal switch...Phase control.
- High-frequency horizontal sweep; solid lock-in on 5 MHz.
- Preset TV "V" and "H" frequencies for instant lock-in.
- Built-in square-wave signal for calibrating P-P voltage measurements.
- Provision for connection to vertical deflection plates of CRT.

Some statistics! For complete details, contact your RCA Distributor.

RCA|Electronic Components|Harrison, N. J. 07029

Circle 112 on reader service card

World's Number One Trusted Name Brand

"NO NOISE"

TECHNICIANS' FIRST CHOICE OVER CHEAPER SUBSTITUTES!

- VOLUME CONTROL & CONTACT RESTORER
- TUNER-TONIC with PERMA-FILEM
- EC-44 FOR ELECTRICAL CONTACTS
- TAPE-RECO HEAD CLEANER
- / FRIGID-AIR CIRCUIT COOLER

All Guaranteed Non-Flammable, No Carbon Tet, Non-Toxic, Non-Drift Tuner Cleaner And Guaranteed Not To Affect Plastics.

The Only Brand Perfect For Color TV and Black & White

FREE extender assembly for pinpoint application supplied with ALL NO-NOISE PRODUCTS.

Electronic Chemical Corp.
813 Communipaw Ave. / Jersey City, N. J. 07304

Circle 113 on reader service card

Build this pipelike Schober Recital Organ for only \$1850!*



* Includes finished walnut console. (Only \$1446 if you build your own console.) Amplifier, speaker system, optional accessories extra.

Circle 114 on reader service card

EQUIPMENT REPORT (continued from page 26)

instantly when it's turned on, flicker between figures for a split second, then go to all zeros. When you feed an ac voltage into it, the reading is displayed instantly. If you're on one of the lower ranges, you'll probably notice that the last digit keeps changing about every half-second or so.

After a little while, you realize what is going on. The thing is actually taking a series of instantaneous readings of the varying values of the ac input, and telling you about it!

Here's what is actually happening: the counter and plug-in are "sampling" the input voltage, at very short intervals. If the instantaneous value of the voltage has changed even a tiny bit, a different reading is sent to the display. The time of this sampling can be controlled by a knob on the front panel, from about 0.8 sec up to about 4.0 secs. So, you can read very small variations in the input voltage much faster and more accurately than with a conventional-type meter movement.

Another valuable feature of this instrument is controlled by the same knob. If you're making a test, and you want to know "how much output for so much input?", set up the instruments, get the reading, and then pull the timing knob out. This locks

You couldn't touch an organ like this in a store for less than \$4,000—and there never has been an electronic instrument with this vast variety of genuine pipe-organ voices that you can add to and change any time you like! All four families of formal pipe tones are present in variety to delight players of classic and religious music. Yet you can change the entire organ for popular and theatrical sounds, or plug in special voices for baroque, romantic, or modern repertoires. If you've dreamed of the sound of a large pipe organ in your own home, if you're looking for an organ for your church, you'll be more thrilled and happy with a Schober Recital Organ than you could possibly imagine—kit or no kit.

You can learn to play it—and a full-size, full-facility instrument is easier to learn on than any cut-down "home" model. And you can build it, from Schober Kits, world famous for ease of assembly without the slightest knowledge of electronics or music, for design and parts quality from the ground up, and—above all—for the highest praise from musicians everywhere.

Send right now for the full-color Schober catalog, containing specifications of all five Schober Organ models, beginning at \$499.50. No charge, no obligation. If you like music, you owe yourself a Schober Organ!

Schober Organ Corp., Dept. RE-78
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog and free 7-inch "sample" record.
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

the reading at that instant; the display will then "remember" it for as long as you want!

The ac voltmeter plug-in, the DP-130, has six voltage ranges, from 10.0 mV volts up to 1000 volts, all rms. One very useful feature is the automatic location of the decimal point. For example, on the 10.0 mV range, it will be placed after the left-hand digit.

You might wonder how a 10-mV reading can be shown with only one digit to the left of the decimal point. The display is actually showing "9.99 mV" at full scale. On this range, you can actually read a variation of 10.0 microvolts on the last (right) digit. If the input goes above 10.0 mV, an "Overrange" light on the panel glows to warn you that the input has gone above 10.0 mV. The same principle is used on all ranges: the 1000 volt scale reads 999 volts, and so on.

The ac voltmeter input has a tremendously high input impedance: 1000 megohms shunted by about 25 pF. Despite this it is protected against accidental overload. A special fuse is used in the input that will blow within 100 microseconds. Its main use is protection of the lower ranges—10.0 mV, 100 mV, and 1000 mV.

On the 10V, 100V and 1000 V ranges, the capacitive divider used in the attenuator has capacitors with very high working voltage. Their values are chosen so that 99.9% of the input voltage is dropped across the divider; only 0.1% is actually applied to the preamplifier input. The instrument is practically immune to damage from overload, on the higher ranges, up to 1500 volts peak.

The construction of these units is beautiful. Epoxy boards are used, and the overall construction is rugged. Operation is simple; the number of controls have been kept to a minimum, and the display is simple and "positive." For lab work, production-line testing or any kind of measurements application, this system should be very useful indeed. The versatility of the "plug-in" system will make it a most desirable member of any instrumentation setup. Prices are well below those of similar units in the past, which is another good point today.—Jack Darr

R-E

DID YOU MISS . . .

If you're not sure how a flip-flop logic circuit is used in modern digital circuits, take another look at Matt Mandl's do-it-yourself circuits starting on page 44.

Ever hear of a swept i.f.? If you don't know what it is, turn back to page 59.

NEW METAL-CAN TRIACS

A new line of high-performance metal-can triacs with ratings up to 15 amps rms has been designated as the TIC 220, 230 and 240 series by Texas Instruments. The devices are designed for controlling ac power for motor, heat and light controls, and can be used with or in place of electromechanical relays and contactors.

The triac series will handle currents of 6, 10 and 15 amps, respectively. Each is available in voltage rat-



ings of 200, 400 and 500 volts at 125°C. Package configurations are: standard press-fit, stud mounted and an isolated stud providing electrical isolation from the chassis or heat sink.

In lots of 100, prices range from \$1.70 for a 6-amp, 200-volt device to \$4.15 for a 15-amp, 500-volt isolated-stud unit. For further information, write Texas Instruments, Inc., Inquiry Answering Service, P.O. Box 5012, M/S 308, Dallas, Texas 75222. Request data on TIC 220 triacs. R-E

IF YOU ARE A TV REPAIR MAN YOU NEED

TV TECH AID!

TV TECH AID is the best trouble shooting guide available today. It takes all the guess-work out of TV repair and is designed to help you solve your problems quickly and economically.

Each month you receive updated information on up to 40 different trouble-shooting cases. This important information is supplied to us by technicians, field reps and all the leading TV manufacturers.

You will find every symptom pictured with a clearly marked schematic of the particular faulty stage. The faulty components and corrections will also be listed to aid in repair. You go right to the source of the trouble without guesswork. In addition you get valuable information on current models as well as older models along with circuit changes and modifications as they occur.

TV TECH AID is the best investment you can make in your own business. The cost to you is only \$7.95 for a full years subscription. Send for it now . . . You'll be glad you did!

TV TECH AID
P.O. BOX 603
KINGS PARK, L. I.
NEW YORK 11754

ENCLOSED IS A CHECK OR M.O. FOR
\$7.95 PLEASE SEND 12 ISSUES OF TV
TECH AID
TO:

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

Circle 115 on reader service card

MAY 1970

Now it costs less to own the best VOM you need.



The New RCA WV-510A Solid-State Master VoltOhmyst®

The best you need is the new solid-state RCA WV-510A Master VoltOhmyst®. The most functional VOM we've ever produced, the 510A has all the features you'll ever need no matter what your requirements may be.

And we've added some extra features you won't find in any competitive VOM, at any price . . . features designed to make your work easier, help you get the job done faster.

For example: The RCA WV-510A operates from batteries or AC. Remove the detachable AC line cord while you're taking a measurement and the batteries take over immediately without a flicker of the pointer. And you'll get maximum life from the batteries because they're always on trickle charge during AC operation. Stability? Switch from range to range and watch a whole series of measurements without constantly having to zero-adjust the meter. Some statistics:

Current:

0.01 milliamperes to 1.5 amperes in 8 ranges.

Resistance:

0.02 ohm to 1000 megohms in 7 ranges.

DC Volts:

0.01 volt to 500 volts in 8 ranges.

AC Volts:

0.2 to 1500 rms AC volts in 7 ranges plus peak-to-peak voltages of complex waveforms.

21 megohm resistance on all DC ranges.

And it's only \$128.† complete with DC/AC ohms probe and flexible shielded input cable with BNC connector, and removable AC line cord.

Some statistics! For complete details, contact your local RCA Distributor.

RCA Electronic Components | Harrison, N. J. 07029

Circle 116 on reader service card

RCA

*Inexpensive Quality

†Optional Distributor Resale Price

There's no substitute for SUCCESS...



JAMES WONG—Research Engineer
Heald Engineering College Graduate

or IN-CLASS INSTRUCTION!

In electronics, it's the training that makes the difference. Employers require well-trained men and the first thing checked is where you gained your knowledge.

HEALD GRADUATES have many job offers with starting salaries often in excess of \$10,000 per year. AND advancement is rapid.

GET STARTED NOW. Be a
DRAFTSMAN—12 months
TECHNICIAN—15 months
ENGINEER (B.S. Deg.)—36 months
ARCHITECT (B.S. Deg.)—42 months
YOU are eligible for HEALD ENGINEERING COLLEGE if you have a high school education or the equivalent.

Increased income starts with success—success starts with your move to Heald. Send now for FREE brochures with more information on Heald in San Francisco and your future in Engineering.

FREE LIFETIME PLACEMENT SERVICE
VETERAN APPROVED



WRITE TODAY FOR DETAILS

HEALD Engineering College

1215 Van Ness Ave., San Francisco, California 94109

Please send me information about:

- ARCHITECTURE
- ENGINEERING: Civil Electrical
Electronic Mechanical
- TECHNOLOGY: Electronic Engineering
Technician (FCC)
- Radio-Television Technician (FCC)
- DRAFTING: Mechanical Electrical
Structural

I am interested in Day Evening courses
Also send an application.

NAME _____ AGE _____
ADDRESS _____
CITY _____
STATE _____
ZIP _____ PHONE _____


Circle 117 on reader service card

INTERVAL TIMER (continued from page 58)


The setting of potentiometer R8 determines the duration of the *longer* timed intervals, while the setting of potentiometer R1 determines the duration of the *shorter* timed intervals. Before turning the timer on initially, set R1 to put about two-thirds of its resistance in the circuit, and set R8 to just a little below midposition.

With R1 and R8 set as described, set potentiometer R2 in its maximum clockwise position (maximum resistance in the circuit). Make sure switch S2 is closed, shorting R3. Then move S1 to On. Using an accurate electric clock with a sweep second hand, check the duration of the timed interval. It should be 16 minutes. If it is less, switch the timer off and adjust R8 to put a little less resistance in the circuit. Then check the timed interval again. Try to set R8 so that the interval is accurate to within ± 10 sec. Check the interval several times, to make sure of the best setting of R8, and to determine the repeat accuracy.

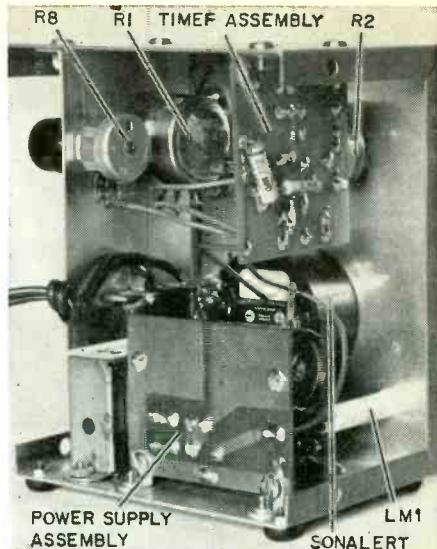With R8 properly adjusted, turn potentiometer R2 to its maximum counterclockwise position (minimum resistance in the circuit), and check the timed interval. It should be 2 min. If it is less than this, adjust potentiometer R1 to put a little more resis-



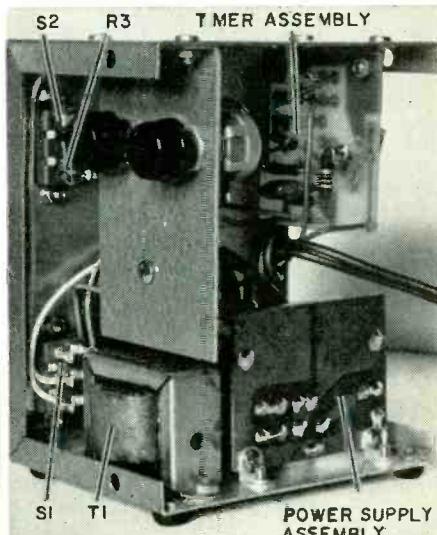Inside the timer case you get a close look at parts placement. Note the positions of the two circuit boards.



Another internal view shows parts locations from a different vantage point. Follow this arrangement closely.

tance in the circuit, and check the interval again. With R1 properly adjusted, go back and recheck the 16-minute interval. Readjust R8 slightly, if necessary. Then recheck the 2-minute interval, and readjust R1 slightly, if necessary. Go over these checks and settings several times.

Calibrating the settings of R2 consists of locating the pointer knob positions for the 4-, 6-, 8-, 10-, 12- and 14-minute intervals, and of making a tiny mark on the cabinet front at each position, using a sharp scriber. This can take time, especially when the exact settings for the longer intervals are involved. Having a good book to read during the interim each time will make the task seem less tedious. Be sure to make a mark at the extreme settings of R2 to locate the 2- and 16-minute intervals.

The optimum value for R3 may now be determined, as described previously. When this has been done, the timer is ready for use.

R-E



Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS Fantastic Value Packed Catalog — Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME _____

ADDRESS _____

CITY _____ STATE _____


GIVE ZIP CODE _____

If you have a friend interested in electronics send his name and address for a FREE subscription also.

OLSON ELECTRONICS
Dept. LE 260 S. Forge Street
Akron, Ohio 44308

Circle 118 on reader service card

stack these up against the others . . .

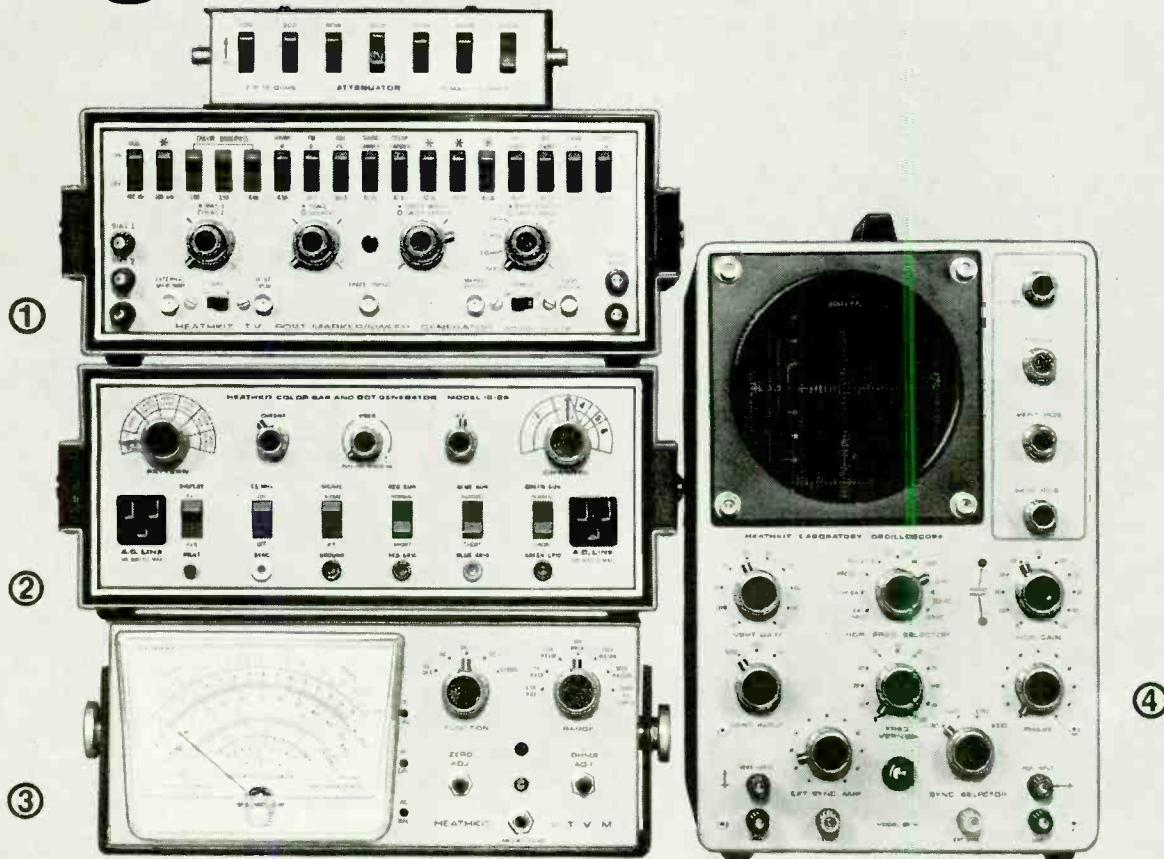

**for just the price of other sweep-marker generators,
you can get a bench full of Heathkit® color test gear**

Stack These Up Against The Others . . . a high performance Sweep-Marker Generator, an accurate Color Bar-Pattern Generator, a versatile VTVM and a rugged, dependable Scope . . . all for only \$347.40* . . . \$50 less than the cost of other sweep-marker generators alone. At Heath, we still believe that you should be able to get a stack of gear without spending a pile of money.

① Heathkit IG-57A Solid-State Sweep-Marker Generator . . . \$135.00*. 15 crystal controlled markers for color band-pass, TV sound, IF, picture & sound carriers for channels 4 & 10, FM IF . . . new Video Sweep Modulation allows injection of chroma-sweep directly into IF amplifiers or thru antenna terminals . . . two built-in variable bias supplies . . . 400 Hz modulated or CW output of any individual marker . . . exclusive external attenuator . . . stable, linear sweep signals for the five most used frequency ranges . . . complete scope matching controls . . . quick disconnect BNC connectors . . . complete with all probes, test leads & terminated cables. 14 lbs. Assembled IGW-28, 8 lbs. . . . \$199.00*

② Heathkit IG-28 Solid-State Color Bar-Pattern Generator . . . \$79.95*. Produces 12 patterns plus clear raster . . . dots, cross-hatch, vertical & horizontal bars, color bars and shading

bars in 9x9 or exclusive 3x3 display . . . all solid-state using computer-type integrated circuitry . . . variable front-panel tuning for channels 2 thru 6 . . . variable front-panel positive and negative video output . . . front panel negative going sync output . . . built-in gun shorting circuit with lead piercing connectors . . . switchable crystal-controlled sound carrier. 8 lbs. Assembled IGW-28, 8 lbs. . . . \$114.95*

③ Heathkit IM-28 "Service Bench" VTVM . . . \$39.95* Measures RMS DC & AC Volts from 1.5 — 1500 . . . AC P-P from 4 — 4000 V . . . resistance from 0.1 ohm — 1000 megohms . . . easy-to-read 6" meter . . . 10-turn vernier controls for zero & ohms . . . single test probe for all measurements . . . ±1 dB 25 Hz — 1 MHz response. 7 lbs. Assembled IMW-28, 7 lbs. . . . \$59.95*

④ The Heathkit IO-18 5" Wide-Band Scope . . . \$92.50* 5 MHz band-width . . . five sweep ranges from 10 Hz — 500 kHz . . . + or — internal, line or external sync . . . two extra, presettable sweep positions . . . front panel 1 V P-P reference . . . Z-axis input . . . retrace blanking . . . 0-135° phasing control . . . frequency-compensated vertical attenuation. 24 lbs. Assembled IOW-18, 23 lbs. . . . \$149.95*

Compare Heathkit performance and value . . . you'll see the others just don't stack up.



NEW

FREE 1970 CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, guitar amplifiers, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 20-5
Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model(s)

Please send FREE Heathkit Catalog.

Please send Credit Application.

Name _____

Address _____

City _____

 **HEATHKIT**

a Schlumberger company

*Mail order prices; F.O.B. factory.

Prices & specifications subject to change without notice.

TE-220

FAST

COMPLETE SERVICE ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(WE SHIP C.O.D.)
YOU PAY SHIPPING
\$9.95



UV Combo's \$16.50

Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. When sending tuners for repair, remove mounting brackets, knobs, indicator dials, remote fine tuning arrangements and remote control drive units.

All tuners must have remote control units and/or mounting brackets removed before tuner can be cleaned and repaired. Please remove these accessories before shipping as we will not be responsible for loss or damage.



All tuners are serviced by FACTORY TRAINED TECHNICIANS with years of experience in this specialized field. All tuners are ALIGNED TO MANUFACTURER'S SPECIFICATION on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

GEM CITY TUNER REPAIR SERVICE

Box 6E Dabel Station
2631 Mardon Drive
Dayton, Ohio 45420

Circle 120 on reader service card

Service Clinic

By JACK DARR
SERVICE EDITOR

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.


If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, New York 10003.

White Line in Raster After Flyback Replacement

I replaced the flyback in a Curtis-Mathes 12A1 with a Thordarson FLY-165. Works, but I get a vertical white line in the middle of the picture, about $\frac{3}{4}$ inch wide. Doesn't seem to be a drive line, for the picture is linear horizontally; no fold-over at that point. Can't get rid of it.

Does this flyback match this chassis?
—J. G., De Queen, Ark.

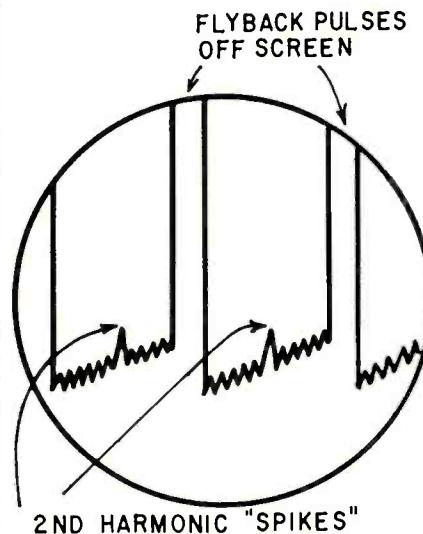Yes, it does. This may be due to the new flyback actually being a little



more efficient than the original! This is a little bit of second-harmonic ringing. If you'll look at the yoke voltage waveform (put the scope probe on one of the yoke wires) you'll see a tiny "pip" in the forward-sweep portion between the spikes (see diagram)!

The cure for this is a drive ad-

justment. This chassis doesn't have a drive control; reduce the size of the 330-pF horizontal-output coupling capacitor to 200 pF, and the line will go away.

More "push" needed in antenna

I've got a set, located about 75 miles from channels 4, 5 and 8. The antenna is a conical, about $\frac{1}{2}$ mile up on a hill, with open-wire transmission line. Low band stations are pretty good but channel 8 is pretty snowy. What would help this out?—L. M., Knoxville, Tenn.

I believe your best bet would be more gain in the antenna. Conicals are fine, but the maximum gain is about 4–5 dB. Try one of the later all-band Yagi types; these have gains up to 12–14 dB all the way across the band, and might help.

Also, you're losing that high-channel station in the transmission line, most likely. Losses are much higher in highs than lows. Might try a small antenna-booster, either at the antenna site or cut into the line say about half-way up. This length of line is okay. Be sure to put a good lightning arrester at the antenna.

Line-noise TVI

On a G-E M5 chassis (at the home) I get a band of dots and flashes about 2–3" high that slowly crawl up and down the screen. Sometimes there are two equally spaced smaller bars. It's worst on channel 2, sometimes present on 4–5, and hardly visible at all on 7, 9, 11 or 13. I've tried high-pass and ac-line filters with no help. It stops when the antenna is removed, and also when the rf amplifier tube is pulled. What is it?—H. F., Gardena, Calif.

It's ac power-line noise. This sounds like hardware noise—tiny arcs from the hot lines to any of the metal mounting hardware on a power pole. This can often be eliminated by tightening all hardware for three or four blocks.

Report this to your local power company. Or you can check it out with an auto radio. Listen for a roaring interference near certain poles.

Hash on screen

I get a sort of "hash" and flicker-

3 New Action-Packed Kits From Heath

NEW Heathkit "Spectre" 1/8 Scale R/C Car

Join The Most Exciting New Hobby In America . . .

building and racing radio-controlled Grand Prix cars up to scale speeds of 200 mph. The Heathkit "Spectre" R/C car reaches that speed and has already proven itself a winner. And no wonder; its design is unique. It has a chrome plated steel chassis, adjustable caster and toe-in, specially formulated rubber tires that lock onto the cast nylon wheels, independent front suspension for excellent cornering and a 5.5:1 gear ratio for maximum torque at all speeds. The snap on, 1/8 scale car body (length: 19 1/4") is of high impact plastic — almost indestructable. Suspension is by real coil springs. The radio equipment compartment is dirt and oil proof. The Heathkit "Spectre" is the only complete car kit available. You get the body, chassis, wheels & tires, 4 oz. fuel tank & tubing, equipment case & protective foam, centrifugal clutch & gears, axles, servo linkages & mounting tape, all hardware, decals, numbers and a comprehensive manual. The "Spectre" accepts any .15 to .23 cubic inch R/C engine and any proportional R/C electronics system. It requires only two servos to operate the steering, brake and throttle. Get in on all the thrills of R/C car racing at the lowest possible price . . . order a Heathkit "Spectre".

Kit GD-101, R/C car only, 8 lbs.....\$49.95*
Assembled GDA-101-1, Veco® .19 R/C engine, 1 lb.....\$19.95*




Heathkit GD-101

\$49 95*



Transmitter

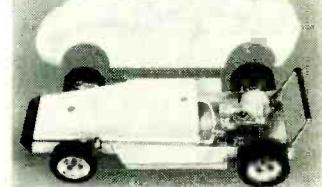


Heathkit GD-57

\$129 95*



Battery Pack

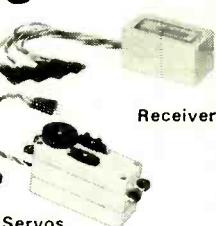

Servos



Heathkit Siren & Speaker


\$99 95*



Amplifier & Controls



Exterior Horn

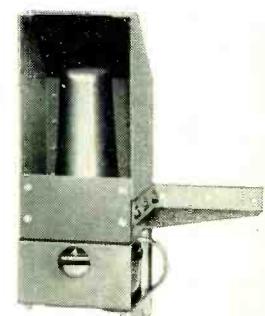

Concealed Horn

NEW Heathkit 3-Channel Digital Proportional R/C System For Planes, Gliders, Cars And Boats

Ideal for use with the new Heathkit "Spectre" R/C car to give you total control . . . ease of handling. Here's what the Heathkit GD-57 R/C system includes: Transmitter with assembled, factory aligned RF circuitry; new 2 oz. miniature receiver that needs no IF alignment, in a tough nylon case; you also get two servos; all plugs; connectors; cables; charging cord; new flat-pack rechargeable nickel-cadmium transmitter and receiver batteries . . . and a special soldering iron. You can have your choice of five operating frequencies in each of three bands . . . 27, 53 or 72 MHz. This is the most value ever offered in a 3-channel rig.

Kit GD-57, transmitter, receiver, 2 servos, batteries, charging cord, switches and soldering iron, (specify freq. desired), 11 lbs.....\$129.95*

Kit GDA-57-1, transmitter, battery, charging cord, (specify freq. desired), 5 lbs.....\$54.95*

Kit GDA-57-2, receiver only, (specify freq.), 1 lb.....\$34.95*

NEW Heathkit Siren/PA

For Licensed Emergency Vehicles Only

Hey Chief! Save up to 60% on a new electronic siren/PA system by ordering the low cost Heathkit GD-18. The siren gives both "wail" and "yelp" warnings at 55 watts output power, and you can adjust the pitch. As a public address it will amplify your voice with a full 20 watts of power, and it's practically immune to acoustical feedback. (Either PA or siren can be interrupted to use the other.) Incoming radio calls can be channeled through the GD-18 so you can hear them when away from your vehicle. Use it on any 12-volt auto electrical system with either positive or negative frame ground. It will operate from -20° to 150° F conditions. Control panel is lighted. Comes with gimbal bracket mounting. Take your choice of speakers . . . concealed or exposed.

Kit GD-18, Siren/PA Amplifier, 7 lbs.....\$54.95*

Assembled GDA-18-1, Exterior Horn, 9 lbs.....\$49.95*

Assembled GDA-18-2, Concealed Horn, 4 1/2 x 4 1/2 x 13", 9 lbs.....\$49.95*

System GD-18A, (includes GD-18 plus exterior horn), 16 lbs.....\$99.95*

System GD-18B, (includes GD-18 plus concealed horn), 16 lbs....\$99.95*



NEW FREE 1970 CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, guitar amplifiers, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 20-5
Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model(s).

Please send FREE Heathkit Catalog.

Please send Credit Application.

Name _____

Address _____

City _____

*Mail order prices; F.O.B. factory.

State _____


Zip _____

Prices & specifications subject to change without notice.

CL-385

FOR THE FINEST
RECEPTION AVAILABLE

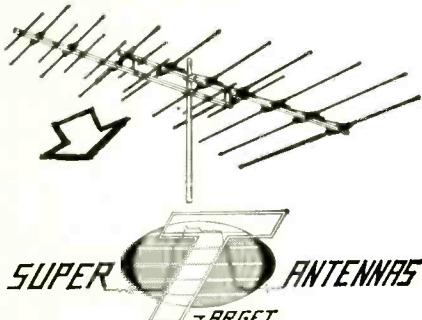NEW SUPER "T" VHF-FM-COLOR TARGET ANTENNA SERIES



ELIMINATE THE NEED
FOR TWO ANTENNAS.

The best features of Log-Periodic and Yagi type arrays are combined for outstanding performance in Super Target Antennas. New, tougher aluminum alloy used for all elements. Rugged square boom construction. Unique construction features reduce installation time.

S & A ELECTRONICS INC.

210 W. Florence Street • Toledo, Ohio 43605

Circle 122 on reader service card

BIG BUYS FOR THE VALUE WISE!

FREE \$1 BUY WITH EVERY 10 YOU ORDER

Only applies
to "\$1" Buys

FREE GIFT WITH EVERY ORDER

MARKET SCOOP COLUMN

<input type="checkbox"/> 12" UNIVERSAL SPEAKER. Top \$4 Quality ... Large Magnet	<input type="checkbox"/> 10" PHILCO SPEAKER \$2.69 Top Quality ... Large Magnet	<input type="checkbox"/> 8" UNIVERSAL SPEAKER - \$1.94 Large Magnet—Special Buy	<input type="checkbox"/> 6"-ECONOMY SPEAKER Top \$1.94 quality 2.15 Mag.	<input type="checkbox"/> 5" UNIVERSAL TWEETER \$1.29 1 Oz. ... Magnet	<input type="checkbox"/> UNIVERSAL 5 1/2" PM SPEAKER \$1 Alnico 5 magnet, quality tone	<input type="checkbox"/> UNIVERSAL 4" PM SPEAKER \$1 With 50L6 Output Transformer	<input type="checkbox"/> UTAH 8" - 3 WAY CO-AX SPEAKER 30 Watts, 8 Ohm \$18.95 Special	<input type="checkbox"/> UTAH 12" - 3 WAY CO-AX SPEAKER 45 Watts, 8 Ohm \$29.95 Special	<input type="checkbox"/> 2 1/2" x 4" SPEAKER \$6.95 Special Buy	<input type="checkbox"/> 3 1/2" - ROUND SPEAKER \$5.95 Special Buy	<input type="checkbox"/> 25 - 3900-OHM-7w RESISTOR \$1 10% Corning glass	<input type="checkbox"/> 20 - .47-600V CONDENSERS \$1 White Ceramic C.D.-American	<input type="checkbox"/> SPECIAL TUBE BUY 3CR6, 3DT6, 4CS6, 12AU7, 12BH7. Each \$49	<input type="checkbox"/> 10 - AST. RADIO & TV TUBES \$1 Every Tube a good number	<input type="checkbox"/> 3-PRINTED CIRCUIT IF TRANS- \$1 FORMERS 4-Lug, 456 KC
---	--	--	--	--	---	--	---	--	--	---	---	--	---	---	---

IMMEDIATE DELIVERY ... Scientific light packing for safe delivery at minimum cost.
HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box, place letter
F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping.
Tear-sheets will be returned as packing slips in your order, plus lists of new offers.

Minimum Order \$3.00

Please specify refund on shipping overpayment desired: CHECK POSTAGE STAMPS MERCANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N. Y. 10024

212-874 5600
TELEPHONE

RADIO-ELECTRONICS

ing effect on the left side of the screen on low channels only. It's worst on channel 2. What causes this kind of stuff?—R. W., Rego Park, N. Y.

Any interference on the left half of the screen should be caused by something in the damper, boost, or boosted-boost circuits. They supply the scan for that side. Try new tubes in the damper, high-voltage rectifier, and voltage regulator sockets. Also try a new horizontal output tube.

Make sure all shields, covers, etc., are in place and tight. This kind of problem is often caused by radiation from the horizontal sweep getting into the tuner or i.f. circuits. Yoke cables can cause it, which accounts for its positioning on the screen. The problem is often mistaken for yoke ringing. Could be a small arcing in the yoke. Check for corona.

Capacitors that squint

Question: you've got two identical capacitors, say 0.1 μ F. One makes the "eye" on a capacitor tester open wide, and the other opens the eye at the same place, but only about half as much, or less. Does this mean the narrow-eye capacitor is bad?—B. R., East Chicago, Ind.

Not necessarily, but maybe. The capacitor with the "squint" may have just a tiny bit more leakage than the

other. They both have the same capacitance, since you get the reading at the same point on the dial.

I seldom check paper capacitors for capacitance, but always check them for leakage. If I were working on a hi-fi amplifier, I'd certainly use the one with the wide eye in coupling applications, and the squint in non-sensitive applications such as cathode bypassing.

Multicolored bars on right

In a Zenith 25MC33 chassis, there are multicolored vertical bars on the right side of the screen—sometimes one, sometimes two. They look like Barkhausen oscillation, but why the colors?—R. D. H., Little Rock, Ark.

They are Barkhausen bars, most likely, especially if they have all the other typical symptoms. Change the horizontal output tube.

The multicolored effect is natural; Barkhausen oscillation is a pretty high frequency, and not too "pure" a sine wave! You've got harmonics, and the harmonics have harmonics, and somewhere in there you've got little bits and pieces of all kinds of frequencies, many of them in the range of the color signals. Very similar to the "fringing" seen when fine tuning is mistuned.

<input type="checkbox"/> COLOR-TV RECTIFIER — Used in most color sets—6500 kv ... 3 for \$1.95	<input type="checkbox"/> 300 - ASST. 1/2 W RESISTORS Top Brand, Short Leads, Excellent Selection \$1
<input type="checkbox"/> 15 - ASST. ROTARY SWITCHES \$1 all popular types \$20 value	<input type="checkbox"/> 100-ASST 1/4 WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> 15 - G.E. #NE-2 TUBES \$1 Neon Glow Lamp for 101 uses ...	<input type="checkbox"/> 100-ASST 1/2 WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> 150' - BUSS WIRE #20 tinned for hookups, special circuits, etc.	<input type="checkbox"/> 70 - ASST 1 WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> 50 - .0033 DISC CERAMIC \$1 CAPACITORS C.R.L.	<input type="checkbox"/> 35 - ASST 2 WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> STANDARD TV TUNER 21mc— with schematic Popular type for many TV's	<input type="checkbox"/> 50 - PRECISION RESISTORS \$1 asst. list-price \$50 less 98%
<input type="checkbox"/> 12-MINIATURE ELECTROLYtic CONDENSERS For Transistor & miniature work	<input type="checkbox"/> 20 - ASSORTED WIREWOUND \$1 RESISTORS, 5, 10, 20 watt
<input type="checkbox"/> 10 - MINIATURE 456KC IF TRANSFORMERS Exceptional value \$1 PC-1/2" x 1/4"	<input type="checkbox"/> 4 - TOGGLE SWITCHES \$1 SPST, SPDT, DPST, DPDT
<input type="checkbox"/> HEAVY DUTY COLOR FOCUS \$1 RECTIFIER 14,000 PIV @ 1 ma ..	<input type="checkbox"/> 10-ASSORTED SLIDE SWITCHES \$1 SPST, SPDT, DPDT, etc.
<input type="checkbox"/> 50 - OIL IMPREGNATED TUBULAR CAPACITORS Por- celain. Axial Leads—Most popular values	<input type="checkbox"/> TRANSISTOR RADIO asst type \$1.50 good, bad, broken, as-is, potluck ..
<input type="checkbox"/> 2 - COLORBURST QUARTZ- CRYSTAL REPLACEMENT For most Color TV Sets - 3579.545 \$1.49 KC	<input type="checkbox"/> TAPE RECORDER - assorted types \$4 good, bad, broken, as-is, potluck ..
<input type="checkbox"/> TV TUNER - asst. all new \$1 standard makes. Less tubes	<input type="checkbox"/> 32' - TEST PROD WIRE \$1 deluxe quality, red or black
<input type="checkbox"/> TV TUNERS asst. all new standard makes, including Tubes	<input type="checkbox"/> HEARING AID AMPLIFIER \$1 incl. 3 Tubes. Mike, etc. (as is) ..
<input type="checkbox"/> WESTINGHOUSE STANDARD TUNER #470V122H01-(3GK5- 6JC8) Tubes) \$4.95	<input type="checkbox"/> COLOR POWER TRANS- \$6.95 FORMER - Good for most sets 26R150 List Price—\$36.75
<input type="checkbox"/> UHF TUNER - TRANSISTOR \$3.95 TYPE Used in all TV Sets	<input type="checkbox"/> 6 - TRANSISTOR RADIO EAR- \$1 PIECES wires complete with plug \$20 - SHURE M70 DIAMOND \$3 NEEDLE exact replacement
	<input type="checkbox"/> 100' - FINEST NYLON DIAL \$1 CORD best size, .028 gauge ..
	<input type="checkbox"/> 10 - SETS PHONO PLUGS & \$1 PIN JACKS RCA type
	<input type="checkbox"/> 50 - ASSORTED PRINTED CIR- \$1 CUIT SOCKETS best types

Cost of
goods

Shipping

estimated

TOTAL


CATV "Leakage?"

We have a community antenna system here. It's causing a lot of interference to homes that use antennas. Is this normal?—H. J., Uhrichsville, Ohio

No it isn't, not if it's definitely cable leakage. A *properly installed* CATV system must hold its rf leakage down to a very low level. The most common problem is running line amplifiers too high, (or someone forgetting to put the shielding lids on amplifier boxes).

There's a good test you can make. Turn an antenna so that it points toward the TV station and a line-amplifier box as well, if you can. Now, look for a TV screen symptom something like that in the drawing.

WHITE OR LIGHT BAR IN CENTER OF SCREEN

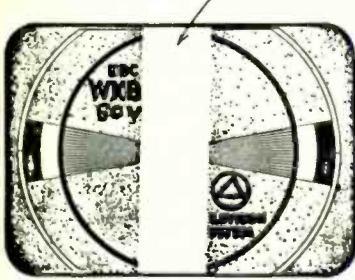

If the CATV amplifier is radiating, you'll see what we used to call a cable bar. It's the horizontal blanking bar from the same signal, delayed a few

microseconds in passing through the coaxial cable.

Check 2: Find a house with an antenna and rotator, so that you can aim the antenna *directly away* from a given TV station but directly at a suspected line-amplifier box. If you get a good picture by aiming at the box, it's radiating. For a better test, put the TV station at right angles to the front of the antenna. Some antennas have a poor front-to-back ratio, but very few have much pickup directly to one side.

Notify the CATV engineering staff. If they won't take care of the interference, yell to the FCC.


Low brightness after CRT conversion

I've converted a CTC5 RCA chassis from the original 21AXP22 to the newer 21FPB22. Works fine, but I've got some problems. When I turn the brightness up I get a bad blooming, a drop in the HV and loss of focus. Is there a further modification that should be made to get better brightness?—B. S., Denver, Colo.

I'd recommend a thorough going-over of the HV supply circuits. RCA's service data call for only 19,500 volts of HV in the original circuit. Your focus voltage is (and should be) a percentage of the HV,

(continued on page 95)

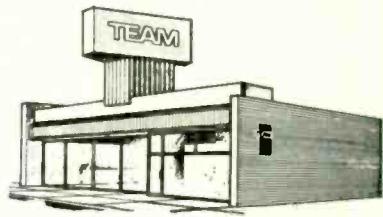own this home electronics center in your community ...



and make 3 profits!

Grow with the "fun" electronics market of hi-fi and stereo, color TV, tape and auto music accessories with a Team Electronics Center—retail, wholesale and systems sales. Over 50 Team stores—**ALL INDIVIDUALLY OWNED**—are now operating in Midwest States. Full franchises and "Partnerships in Profit" available. Team provides training, assistance in all areas. Investment range from \$12,000 to \$37,500. Partial financing available.

Dean Terry, Dir. of Franchising

TEAM CENTRAL, INC.

Suite 16, 720 29th Ave., S.E.
Minneapolis, Minnesota 55414
(612-331-8511)

Circle 123 on reader service card

SHANNON MYLAR RECORDING TAPE

2½"	225' ..	\$.17
3"	225' ..	.19
3"	300' ..	.27
3½"	600' ..	.58
5"	600' ..	.62
5"	900' ..	.80
5"	1200' ..	.97
5"	1800' ..	1.49
7"	1200' ..	.77
7"	1800' ..	1.12
	7" — 2400' ..	\$1.79
	7" — 3600' ..	2.95
	CASSETTE 60 minutes ..	.89
	CASSETTE 90 minutes ..	1.54
	CASSETTE 120 minutes ..	1.97
	2½" TAPE REEL ..	.04
	3" TAPE REEL ..	.05
	3½" TAPE REEL ..	.06
	5" TAPE REEL ..	.12
	7" TAPE REEL ..	.14

MOTOROLA HEP KIT—INTEGRATED CIRCUITS INCLUDES One JK flip flop, One Dual Buffer, One 4-input Gate, Two Dual 2-Input Gates. All Five \$3.95

MOTOROLA EXPERIMENTER KIT HEK-2—9 Projects, Instructions enclosed. Includes 2-FET, 2-Transistors, "Tips on using FETS" & Cross-references Guide. \$3.95

2-MOTOROLA HEP-170 RECTIFIER 2½ AMPs and 1000V(PIV) Covers all 600MA to 2500MA Units Voltage ranging from 50PIV to 1000 PIV \$1

4-TV ALIGNMENT TOOLS most useful assortment #1 \$1

4-TV ALIGNMENT TOOLS \$1.49 For Color TV #2

3-TOP BRAND 35W4 TUBES \$1

UNIVERSAL MICROPHONE regular/remote/single & dual plug \$2

CRYSTAL LAPEL MICROPHONE high impedance, 200-6000 cps \$59

STEREO HEADPHONES Hi-Fi Quality Complete \$5.95 with Stereo plug

50-TUBE CARTONS (colored) \$1 assorted sizes for Popular Tubes

4-36" Hi-Fi CABLES RCA Molded Phone plug at one end stripped and tinned leads on other \$1 end

3' JUMPER CABLES Male RCA \$1.19 Type Plug on Both Ends. 2 for

50-ASST. TERMINAL STRIPS \$1 all types, 1-lug to 6-lug

CANADIANS: Ordering is easy — we do the paperwork — try a small order

WESTINGHOUSE ALL TRANSISTOR HOME/OFFICE MESSAGE CENTER

Leaves messages for other for replay . . . Built in speaker/microphone for talk-into convenience . . . Records up to 3 minutes of messages . . . Illuminated signal shows when a message is waiting. Control adjusts playback volume without affecting recording volume . . . Capstan Drive! BRAND NEW SOLD AS IS \$10 10% off in lots of 3

RCA 110° FLYBACK TRANSFORMER

We scooped the Market Latest type—standard for all 110° TV's RCA's design of large Coil produces 18KV—assuring adequate width Incl Schematic Diagram application for any TV List price \$13.00 Your price \$3 10% off in lots of 3

110° TV DEFLECTION YOKE

for all types TV's incl schematic \$3

"COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE

\$5

90° FLYBACK TRANSFORMER

for all type TV's incl schematic \$2

90° TV DEFLECTION YOKE

for all type TV's incl schematic \$2

70° FLYBACK TRANSFORMER

for all type TV's incl schematic \$2

70° TV DEFLECTION YOKE

for all type TV's incl schematic \$2

2-TV CIRCUIT BREAKERS

Rated 4.2 TO 5.0 AMPS, etc. \$1.19

70° COLOR YOKE

For all round color CRT's \$10.95

90° COLOR YOKE


For all Rectangular 19 to 25" Color CRT's \$10.95

IBM COMPUTER SECTIONS

8 Assorted Units we sell for \$1 are loaded with over 150 valuable parts.

Incl.—Transistors, Condensers, Resistors, Heat Sinks, Diodes, Etc.

8 for \$1
100 for \$10

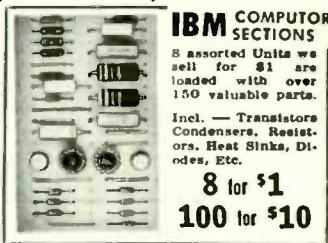

WESTINGHOUSE FM TUNER
#470-V-006H01 (12DT8 \$1.99
Tube) #470-V-015D01 Transistor \$3.99

300-ASSORTED HEX NUTS \$1
2/36, 4/40, 5/40, 6/32, 8/32 ..

250-ASST. SOLDERING LUGS \$1
best types and sizes ..

250-ASST. WOOD SCREWS \$1
finest popular selection ..

250-ASST. SELF TAPPING \$1
SCREWS #6, #8, etc. ..

150-ASST. 6/32 SCREWS \$1
and 150 6/32 HEX NUTS ..

150-ASST. 8/32 SCREWS \$1
and 150-8/32 HEX NUTS ..

150-ASST. 2/56 SCREWS \$1
and 150-2/56 HEX NUTS ..

150-ASST. 4/40 SCREWS \$1
and 150-4/40 HEX NUTS ..

150-ASST. 5/40 SCREWS \$1
and 150-5/40 HEX NUTS ..

500-ASSORTED RIVETS \$1
most useful selected sizes ..

500-ASSORTED WASHERS \$1
most useful selected sizes ..

100-ASST. RUBBER BUMPERS \$1
for cabinet bottoms & other uses ..

100-ASSORTED RUBBER GROMMETS \$1
best sizes ..

Circle 124 on reader service card

How to cool off hot-headed customers...



Install Admiral Super-Brite replacement color picture tubes with the 3-year warranty.

Admiral is the only replacement color picture tube with a 3-year warranty. That's a full year more protection for your customers.

Admiral Super-Brite replacement color picture tubes aren't rebuilts. They're brand new. And they're available in the U.S.A. and Canada. From Admiral, producers of more rectangular color picture tube sizes than anyone in the world.

Now, watch your customers warm up to you for steering them right.

Admiral
Mark of Quality

Admiral Corporation warrants this picture tube to be free from defects in material or workmanship for 3 years after date of sale to the customer. Admiral's obligation is limited to supplying a suitable replacement picture tube. This warranty is effective if the picture tube is registered with Admiral within 10 days after date of sale to the consumer.

Circle 125 on reader service card

TECHNOTES

NO COLOR WITH AFT IN

A common complaint is that, on certain channels, color is received with aft off but not when the aft switch is set to the **AFT ON** position. The service technician may attribute this to misalignment or other trouble in the aft circuits.

Almost invariably, the trouble can be traced to the color-killer control being set too high. This results from using the older method (setting the color killer to eliminate colored show on an unused channel) of setting the color-killer control. Use the following procedure on receivers with aft:

1. Set the killer control fully counterclockwise.
2. Turn the aft off.
3. Tune in a color transmission and adjust all controls for best color picture. The color control probably will be turned up about halfway.
4. Switch to a channel transmitting b/w and adjust fine tuning for slight sound interference. This causes false color in the picture.
5. Turn the killer control slowly clockwise, to just eliminate the false color.
6. Check the setting of the killer control by tuning to all channels transmitting color. If the color drops out on any channel when aft is switched on, back slightly on the killer control until color appears.—*DuMont Field Service Bulletin*

OLYMPIC CTC 30

Some early-production chassis have poor color-killer action. This is due to an incorrect connection of C170—a 0.01- μ F disc capacitor. A few chassis have one end of C170 connected to the junction of R189 and diode SR109. The correct connection for this capacitor lead is to the junction of resistors R188 and R189.—*Olympic Service Bulletin*

OLYMPIC MA-100 AND SA-100

Complaint: Insufficient volume when the tone control is turned counterclockwise.

Remedy: 1. Remove four Phillips-head screws from the changer board and remove entire assembly from the case.
2. (MA-100) Connect a 470,000-ohm $\frac{1}{2}$ -watt resistor, across the tone control terminals on the bottom of the amplifier PC board as shown in the diagrams.

3. (SA-100) Install two 470,000-ohm $\frac{1}{2}$ -watt resistors, one each from the center lug to the high side of the tone control in each stereo channel. The high side of the tone control can be identified by the brown lead running to the phono pickup.

4. Reinstall changer board in the case and test the tone control operation.—*Olympic Service Bulletin*

R-E

A LOOK AHEAD IN R-E

If you like the construction and special interest features you've been reading, you won't want to miss what we've planned for coming months.

- **July**—Sound reinforcement is the special feature. One article provides valuable tips on microphone types and techniques.
- **August**—TV cameras and vtr's are up front. Find out about the latest color cameras and equipment.
- **September**—TV antennas will be featured. R-E takes a close look at the uhf types and how they work.

COMING NEXT MONTH

JUNE 1970

■ Build R-E's "RADAR" Burglar Stopper

Dual-function alarm uses ultra-high frequency to fill rooms with an invisible protective shield. Auxiliary circuit protects doors and windows. Permits connecting sensors for fire, smoke, cold, etc.

■ Stereo In Your Car

8-track cartridge or 4-track cassette — both are ready for your car now. Pros and cons of both systems are presented and a rundown of current equipment too.

■ Careers In Aviation Electronics

Fast-growing aviation industry has a large number of openings for electronic technicians. See what you must know and how you can get started in this new electronics industry.


■ The Amplified Zener

Combine a diode with a transistor and get an effective Zener diode that handles real power. An interesting new technique.

■ Plus these regular features

Kwik Fix™
Service Clinic
In The Shop
Tools Report

Join the Admiral S&H book club.

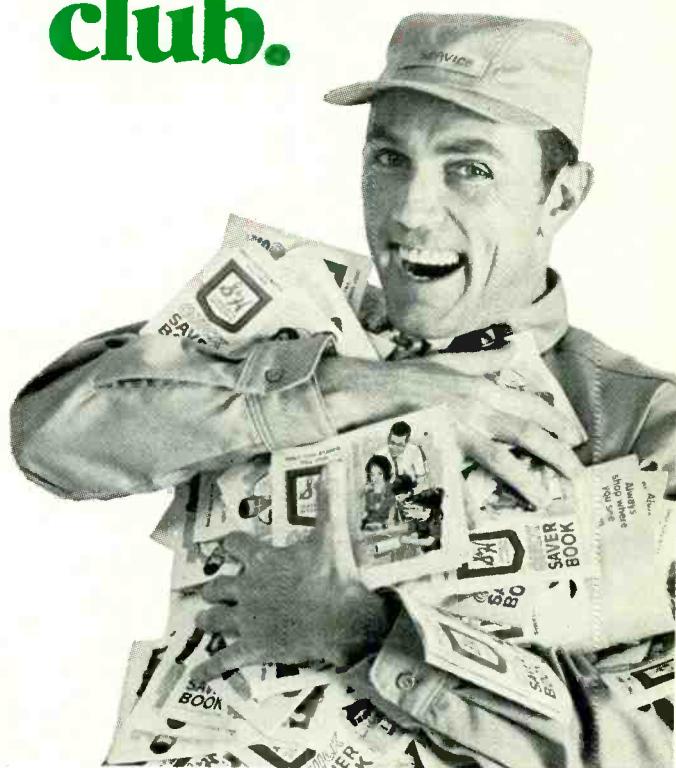

Get a free book of S&H Green Stamps with every Admiral Super-Brite color picture tube purchase.

Get a certificate worth 600 stamps ($\frac{1}{2}$ book) with every Magna-Brite color picture tube you buy.

Every book puts you closer to owning a set of luggage, a pool table, or any other item in the 180-page S&H Gift Catalog, including a 14-foot sailboat.

Register now with your Admiral Distributor and learn all the details about "A Brighter Year Ahead." Or use the Reader Service card.



Admiral Corporation,
3800 Cortland Street, Chicago, Illinois 60647.

Admiral
Mark of Quality

Circle 126 on reader service card

Who needs a tuner wash? Save your money and use

QUIETROLE

The product that cleans while it lubricates. Zero effect on capacity and resistance. Harmless to plastics and metals. Keeps color and black and white on the beam. Non-flammable.



manufactured by
QUIETROLE CO.
Spartanburg, South Carolina

Circle 127 on reader service card

TRY THIS ONE

SIMPLE CABLE STRIPPING

An easy way to cut through the insulation on all types of plastic-coated TV lead-in, microphone cable, etc. is to bend wire into a loop, then press a sharp knife into the insulation. The insulation separates before the blade has cut all the way through to the braid or inner conductors and they will not be nicked by the knife blade. Strip the insulation off by pulling with pliers.—*H. Josephs*


PERFECT REPAIR TOOL FOR BROKEN ANTENNAS

Most broken telescoping radio and TV antennas can be quickly and rigidly repaired with a common tubing cutter. The soft, thin metal scores easily before cutting, which is the secret of this repair. First, use the tool to cut off both tips of the broken pieces. This leaves both edges knurled inward. The lower piece is then stretched to its original size by rotating the tip of long-nose pliers inside. The upper section will then slide inside the lower one, after which the tubing cutter is used again to make a

couple of scores, crimping the doubled area. Depending on where the antenna is broken, it will sometimes continue to telescope fully, and in other cases be only slightly restricted. In either case, this is a real confidence builder among customers who might feel an expensive replacement is more than their set deserves. The smallest, cheapest tubing cutter does the job.—*B. M. Carrie*

FLAT-PACK HOLDER

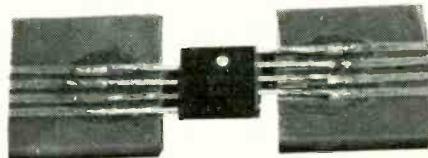
You can make inexpensive holders for flat-pack IC's. Take 2 pieces of $\frac{1}{2}$ -inch square copper-clad board, cut masking tape (or equivalent) into $\frac{1}{32}$ -inch strips and space them on the



copper clad to pick up each tab on the flat pack. Place the taped squares in some etching solution to remove the excess copper. Remove the tape and you're ready to mount your flat-pack.—*A. E. Plavcan*

IC MOUNTING TECHNIQUE

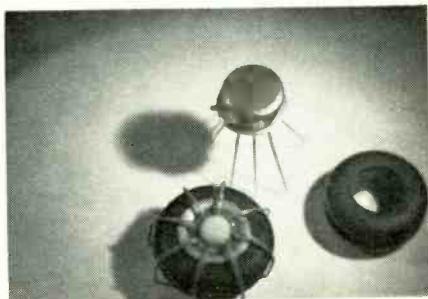The photograph illustrates a method of mounting TO-5-case IC's that is particularly well suited for experimental breadboards and prototypes.



The major advantage of this method is that each lead of the IC is easily accessible. Clipleads and probes are readily attached to any lead for waveform or voltage checks and measurements.

A rubber grommet of the proper size is pressed over the IC case and used as a form for bending the leads (photo). The grommet is removed and the IC is inserted into eyelets that have been set in perforated board. This method works well with any multilead TO-5 device—*Royland Pettersen*

R-E

The brand for all reasons



BSR McDONALD 600

Every BSR McDonald automatic turntable is precision made in Great Britain to the most exacting specifications. Upon their arrival in the U.S., every model is unpacked and re-tested under actual playing conditions. That's why BSR service calls are the lowest in the industry—and perhaps that also explains why BSR sells more turntables than anyone else in the world.



MCDONALD

Circle 128 on reader service card

BSR (USA) LTD.
BLAUVELT, N.Y. 10913
Please send FREE detailed literature
on all BSR McDonald automatic turntables.

Name
Address
City
State
Zip

ULTIMATE TUNER

(continued from page 72)

R105, R138, R144—1000 ohms
 R106, R110, R117, R139, R140, R145—220 ohms
 R107—510 ohms, $\frac{1}{2}$ watt
 R108—4700 ohms, $\frac{1}{2}$ watt
 R109, R121—22 ohms, $\frac{1}{2}$ watt
 R113—6800 ohms, $\frac{1}{2}$ watt
 R114—220 ohms, $\frac{1}{2}$ watt
 R115—470 ohms, $\frac{1}{2}$ watt
 R116—47 ohms, $\frac{1}{2}$ watt
 R118—2700 ohms, $\frac{1}{2}$ watt
 R119—100 ohms, $\frac{1}{2}$ watt
 R122—47,000 ohms
 R123—6800 ohms
 R124, R125—5100 ohms
 R126—1000 ohms, $\frac{1}{4}$ -watt trimmer
 R127—22,000 ohms
 R128, R136, R141—47,000 ohms
 R129, R137, R142, R143, R146—10,000 ohms
 R130—4700 ohms
 *F101, F102—XTAL FILTER, \$13.75 ea.

Specifications for F101 and F102:

Center frequency—10.7 MHz
 Bandwidth—1.5db, 200 kHz min., 3db, 240 kHz min., 20db, 500 kHz max., 50db, 1100 kHz max.
 Ultimate attenuation—50dB minimum
 Maximum insertion loss—5dB
 Phase linearity—Within plus or minus three degrees of best straight line over 200 kHz minimum bandwidth
 Input to filter—500 ohms plus 4.2 pF
 Load on filter—500 ohms plus 7.5 pF
 Size—51mm long, 18mm wide, 33mm high
 Operating temperature—45 to 110 degrees F.
 T101—J. W. Miller 2072
 T102—J. W. Miller 1605 PC
 Q101, Q102, Q103, Q104—MPS 6939
 Q105, Q107—2N3860
 Q106—2N5355
 D101, D102—IN34
 LM101—12-14V, 25-40 mA

Multiplex and Power Supply (201-299 series)

C201, C209, C224, C225— $1\mu\text{F}/50\text{V}$, electrolytic (Mallory MTA 1D50 or equiv.)
 C202—560 pF polystyrene
 C203, C206, C207, C211, C212— $0.1\mu\text{F}$ polystyrene
 C204— $.02\mu\text{F}$ or $.05\mu\text{F}$, disc ceramic; see text
 C205— $.001\mu\text{F}$ polystyrene
 C208— $.01\mu\text{F}$ disc ceramic
 C210— $15\mu\text{F}$, 35V, electrolytic (Mallory MTA 15E35 or equiv.)
 C213— $5\mu\text{F}$ 50V, electrolytic (Mallory MTA 5D50 or equiv.)
 C214— $.0015\mu\text{F}$, polystyrene
 C215, C216, C217, C218— $.002\mu\text{F}$ temp. stable ceramic
 C219, C220— $.001\mu\text{F}$ temp. stable ceramic
 C221, C222— $.05\mu\text{F}$, disc ceramic
 C223— $10\mu\text{F}$, 35V, electrolytic (Mallory MTA 10D35 or equiv.)
 C226— $500\mu\text{F}$, 25V, electrolytic (Mallory TC-2505B or equiv.)
 C227, C228— $500\mu\text{F}$, 15V, electrolytic (Mallory MTV 500DN15 or equiv.)

All resistors $\frac{1}{4}\text{-W}$, 5% unless otherwise noted

R201, R206, R212, R213, R214, R215, R216, R217—10,000 ohms
 R202, R207—2 megohms
 R203—3300 ohms
 R204—1000 ohms, $\frac{1}{4}$ watt trimmer
 R205—1000 ohms
 R208, R218—6800 ohms
 R209—2,200 ohms
 R210, R234, R235—100,000 ohms
 R211, R230, R231—4700 ohms
 R219—560,000 ohms
 R220, R221, R222, R223—39,000 ohms
 R224, R225, R226, R227—150,000 ohms
 R228, R229—1 megohm
 R232, R233—25,000 ohms, $\frac{1}{4}$ -watt trimmer
 R236—220 ohms, $\frac{1}{2}$ -watt
 R237—100 ohms, $\frac{1}{2}$ -watt
 R238—56 ohms, $\frac{1}{2}$ -watt
 R239—470 ohms
 T201, T203, T204—J.W. Miller 1361
 T202—J.W. Miller 1362
 T205—J.W. Miller 1354-PC

(continued on page 93)

It takes
 a
 good
 head
 to get good sound
 from your recorder.

KEEP YOURS CLEAN.
 CHECK REGULARLY FOR WEAR.
 REPLACE WHEN NECESSARY.



Your Nortronics distributor has the right replacement for almost any recorder, domestic or imported, open-reel, cassette or cartridge type.

ASK FOR FREE HEAD CARE BULLETIN NO. 7260

Nortronics
 COMPANY, INC.

6140 Wayzata Boulevard
 Minneapolis, Minnesota 55416
 Phone: (612) 544-0381

Circle 136 on reader service card



AMAZING OFFER RADIO & TV SERVICE DATA

Your best, complete source for all needed RADIO and TV diagrams and helpful servicing data. Most amazing values. Only \$2.50, \$3, \$4 per giant volume. Cover all important makes, models of all periods. Use this entire ad as your no-risk order form.

NO-RISK ORDER COUPON

TELEVISION SERVICE MANUALS

Supreme TV manuals are best for faster, easier TV repairs. Lowest priced. Factory data on practically all sets. Complete circuits, all needed alignment facts, wiring-board diagrams, waveforms, voltages, production changes, and double-page schematics. Only \$3 and \$4 per large annual manual. Check volumes wanted, send entire advertisement as your order form.

- New 1969 COLOR TELEVISION Manual, only \$4.
 1968 B-W TV, \$4. 1968 TV, \$4. 1967 TV, \$4.
- 1966 TV, \$3. Additional 1965 TV, \$3.
- 1965 TV, \$3. 1964 TV, \$3. 1963 TV, \$3.
- Additional 1962 TV, \$3. Early 1962 TV, \$3.
- 1961 TV Manual, \$3. 1960 TV Manual, \$3.
- Additional 1958 TV, \$3. Early 1959 TV, \$3.
- 1958 TV Manual, \$3. Additional 1957 TV, \$3.
- 1955 TV, \$3. 1954 TV, \$3. 1951 TV, \$3.
- Master Index to all TV & Radio Manuals, 25¢

RADIO DIAGRAM MANUALS

Get these low-priced radio manuals and simplify all repairs. Cover everything you may need from recent radios to pre-war old-timers; all type radios, stereo, combinations, transistor portables, FM-AM, and auto sets, Large schematics, all needed alignment facts, printed boards, voltage data, dial stringing hints. Volumes are big, 8-1/2" x 11", about 190 pages, each....

- 1966, 1965, 1964, 1963, 1962, 1961,
- 1960, 1959, 1958, 1956, 1955, 1954,
- 1953, 1952, 1951, 1950, 1949, 1948,
- 1942, 1941, 1940, 1926-38, EACH, \$2.50
- 1965 AUTO RADIOS, RADIO COURSE, \$2.50
- Also New 1967-1969 Combined Radio Volume, \$4.00.

SUPREME PUBLICATIONS

1760 Balsam Road, Highland Park, ILL, 60035


Rush today TV and Radio manuals checked in no-risk order form of this ad. Send postpaid, I am enclosing full price. You guarantee my complete satisfaction or my money back.

Name: _____

Address: _____

City: _____ State: _____

Circle 129 on reader service card

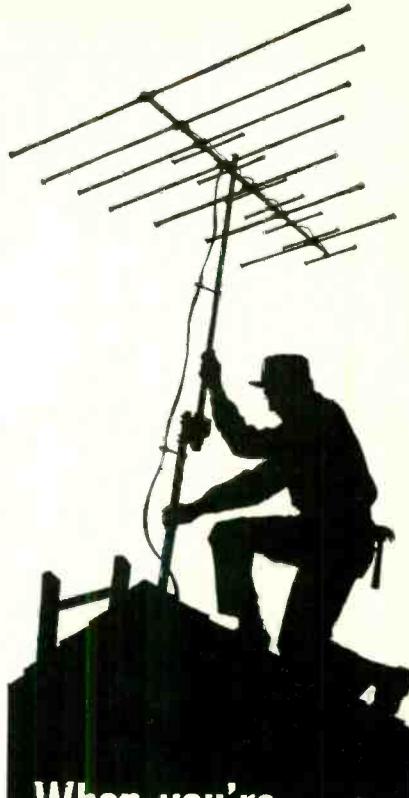

When you're
 putting up an
 antenna,
RCA supports it.
With a complete
line of hardware.

Chimney, wall, and roof mounts.
 Masting, Guy wires, fittings . . .
 and stardoffs, too. Whatever your
 requirements . . . RCA meets
 them with a complete line of
 Antenna Installation Hardware.

Every item in the line has been
 given that special attention to
 design and quality that you've
 come to expect from RCA.

Ask your RCA Distributor about
 the RCA antenna hardware line,
 and about his special deal on
 a hardware merchandiser for
 profitable "do-it-yourself" sales.
 Sell the hardware line with built-in
 consumer acceptance—RCA.

Parts and Accessories,
 Deptford, N.J. 08096


RCA
 Antenna
 Installation Hardware

MOST ADVANCED IGNITION SYSTEM ON THE MARKET

JUDSON'S ELECTRONIC MAGNETO

Provides Better Performance. Reduces Fuel Consumption. Increases Plug and Point Life. Prevents High Speed Miss and Plug Fouling. You'll feel the difference right from the start.

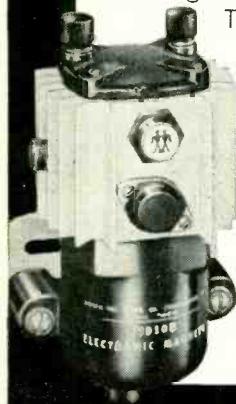The accepted standard in electronic ignition.



EASILY INSTALLED

Write Today
For Free
Literature

JUDSON
RESEARCH & MFG. CO.
CONSHOHOCKEN, PA. 19428

Circle 130 on reader service card

QUALIFY FOR YOUR RADIOTELEPHONE LICENSE!

ICS has successfully trained thousands. Study at home, at your own speed, with the detailed personal attention of your highly qualified instructor. No time lost commuting to classes, or waiting for a class to catch up.

Course material includes detailed information on various FCC examinations and typical FCC examination questions, with answers explained in detail. Covers preparation for First, Second and Third Class tickets. Study one... or all three.

Your tuition refunded—or additional instruction provided—if you fail to pass your FCC exam after completing ICS instruction.

Don't wait—or full information send the coupon today.

ICS, Scranton, Pa. 18515

ICS International Correspondence Schools
Division of Intext D7942D

Mail to ICS, Scranton, Pa. 18515

Rush me free details on your warranted Radiotelephone License qualifying program.

Name _____ Age _____
(please print)

Address _____

City _____ State _____ Zip _____

Occupation _____

I am a veteran; tell me how I qualify for tuition refund under the new GI Bill.

Circle 132 on reader service card

MOST ADVANCED IGNITION SYSTEM ON THE MARKET

JUDSON'S ELECTRONIC MAGNETO

Provides Better Performance. Reduces Fuel Consumption. Increases Plug and Point Life. Prevents High Speed Miss and Plug Fouling. You'll feel the difference right from the start.

The accepted standard in electronic ignition.

EASILY INSTALLED

Write Today
For Free
Literature

JUDSON
RESEARCH & MFG. CO.
CONSHOHOCKEN, PA. 19428

Circle 130 on reader service card

Stk. No.		Transistors	
B4002	2N1204	Motorola PNP Germanium	
B4003	2N231	General Purpose 5/1.00	
B4018	2N1907	PNP Germanium General Purpose 5/1.00	
B4022	2N1546	Texas Inst. PNP Germanium Power 1.75	
B4023	#108	Motorola MP 1546 High Reliability 90 Watts 1.00	
B4024	2N3567	Motorola or Deco Similar 3/2.00	
B4025	MADT	Fairchild NPN Silicon General Purpose 5/1.00	
B4028	2N1011	Sprague 4/1.00	
		Motorola PNP Germanium Power 35 Watts 3/2.00	
		Diods	
B4005	IN629	Hughes PIV 175, 30 ma 8/1.00	
B4006	IN1200	Sylvania PIV 100, 70 ma 8/1.00	
B4007	IN2326	RCA Rectifier PIV 200, 100 ma 5/1.00	
B4008	IN3195	RCA Rectifier PIV 600, 500 ma 10/1.00	
B4009	IN3255	RCA Rectifier PIV 600, 500 ma 10/1.00	
B4030	IN541	Motorola Silicon Rectifier 50 Volts, 15 Amps 3/1.00	
B4032	IN3208	RCA 600, 750 ma 8/1.00	
B4034	IN4785	Sylvania Bullet Diode PIV 600, 750 ma 8/1.00	
B4050	IN2071	Zener Diodes	
B4010	IN751A	5.1 Volts, 400 mw 5/1.00	
B4011	IN3039A	6.2 Volts, 1 Watt 3/1.00	
B4012	IN3822	3.6 Volts, 1 Watt 5/1.00	
B4013	IN3000B	62 Volts, 10 Watts 2/1.00	
B4014	IN3048B	150 Volts, 1 Watt 3/1.00	
B4015	1/2M3.0	3 Volts, 1/2 Watt 4/1.00	
B4029	IN429	5.6 Volts, 1 Watt 4/1.00	
B4038	IN961B	150 Volts, 1.7 ma 75	
B4040	IN3048	(Matched pair) 75	
		Integrated Circuits	
Stk. No.	Type	Case Function	Price
B3000	907	TO-5 Four input gate	.75
B3001	914	TO-5 Dual 2 input gate	1.00
B3008	914	FP Dual 2 input gate	1.00
B3002	915	TO-5 Dual 3 input gate	1.00
B3003	923	TO-5 JK Flip Flop	1.00
B3007	3M4-923	JK Flip Flop	1.00
B3005	1M4-925	FP Dual 2 input gate exp.	1.00
B3004	926	Buffered JK Flip Flop	1.00
B3006	926	FP Buffered JK Flip Flop	1.00
		(FP—Flat Pack)	

Lots of other items—send for free flier; all merchandise fully guaranteed. Please include postage, excess will be refunded.

DELTA ELECTRONICS CO.
BOX 1, LYNN, MASSACHUSETTS 01903

Circle 131 on reader service card

U.S. GOV'T ELECTRONIC SURPLUS

• Nationally Known—World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

BURGLAR-FIRE ALARM SYSTEM
• (ITEM #1135-A) - - Brand new burglar-alarm system. Operates on 115-VAC. Control unit, 2-Kelie flash fire, 2-microphone column, 3-door window actuators, alarm bell, 100 ft. wire, instructions. 8 1/2" x 7 1/2" x 3 1/2" (7 lbs.) \$29.95

POCKET SIZE MULTI-RANGE TESTER
• (ITEM #A107) - - Compact, 20,000-ohm-dial multimeter is excellent unit for testing electrical and electronic equipment, especially for servicing transistorized equipment. Has precision standards for extra accuracy. 20mm ammeter, 0-15mA. D'Arsonval movement, 30° scale with superior readability in low ranges. Spec.: AC Volts, 0-10, 30-25, 1000, 10C Volts, 0.5-2.5-10-50-250, DC Current, 0-250 mils, 0.5-5 microamps. Ohms: 0-10,000 and 1 Meg (expanded low ohm scale). D.C.: 20 to 200 milli. Overall size 4 1/2" x 3 1/2" x 1 1/2". Complete with leather case, 36" test leads, instructions. (2 lbs.) \$8.98

EXPANDED SCALE 0 - 15 DCVM
• (#21-900) - - Brand new, expandable voltmeter reads 9.5 to 160 millivolts. Very useful for automotive and aircraft battery charge indicator, etc. Has D'Arsonval movement, black plastic case. 7 1/2" x 3" x 2 1/2" (3 lbs.) \$12.95

RUNNING TIME METER
• (#0X-104) - - Use to record number of operating hours of electric lights and electrical devices such as refrigerators, furnaces, etc. Records total hours, tenths and hundredths up to 9,999.99 hours. For 115-volt, 50-cycles. Size 4 1/2" x 3" x 2 1/2". Shipping weight 2 lbs. \$5.69 Cost Over \$29.00

COMPUTER TRANSISTORS ON HEAT SINKS
IBM Computer Quality Units

• (#22-228) - - Unit consists of one 150-watt power transistor on heavy, ribbed, aluminum heat sink. Many experimental uses. (1 lb.) \$1.99

• (#22-915) - - Unit consists of two 150-watt power transistors, 2 pots, several diodes, capacitors, resistors, etc. on heavy, ribbed aluminum heat sinks. Ideal for use as motor speed control. (4 lbs.) \$4.91

ORDER FROM AD—WRITE FOR FREE CATALOG
Include Money For Postage Money Back Guarantee

SURPLUS CENTER

DEPT. RE-059 LINCOLN, NEBR. 68501

PHOTOCELLS FROM TRANSISTORS

Recently, I needed some photocells for an experiment. Recalling that the diode junctions of most transistors are photosensitive, I decided to investigate the possibility of using defective transistors in my experiment.

These transistors, in TO-3 cases, were opened up by using a carbondum wheel to grind away the top. Of two of the units I opened, one was a GM with the base connection made to a ring around a piece of crystalline material. The other, an unknown type and brand, had a grid-like emitter visible on the top layer of the transistor.

The emitter connections were removed and then tests were made on the photosensitive base-collector junction. Using the R × 10,000 scale of a multimeter, the B-C junction of the GM unit read about midscale when the diode was reverse biased and much lower when forward biased. With reverse bias, a resistance range of about 2 to 1 was obtained when light intensity was increased by moving closer to a 40-watt lamp. Thus, this device was not a good photoresistor. However, when used as a photoemissive cell connected to the 80-μA range of the meter, it would drive the needle off scale when close to the 40-watt lamp.

The second transistor with the grid-type emitter made an excellent photoresistor. Reverse biased, its resistance was more than 10 megohms in complete darkness. Resistance dropped rapidly as light intensity was increased. Stronger light caused the needle to drop below zero resistance. This indicates the diode resistance ranges from near infinity to a very low value and that with strong light, it also generates a voltage that augments the 7.5-volt battery in the ohmmeter—to drive the pointer off scale.


The voltage output is nearly constant for medium and high illumination, at around 0.2 volt for the GM transistor and 0.4 volt for the unknown type.—D. Dlitz





"If he had a gripe about working conditions why didn't he come directly to me?"

ULTIMATE TUNER
(continued from page 91)

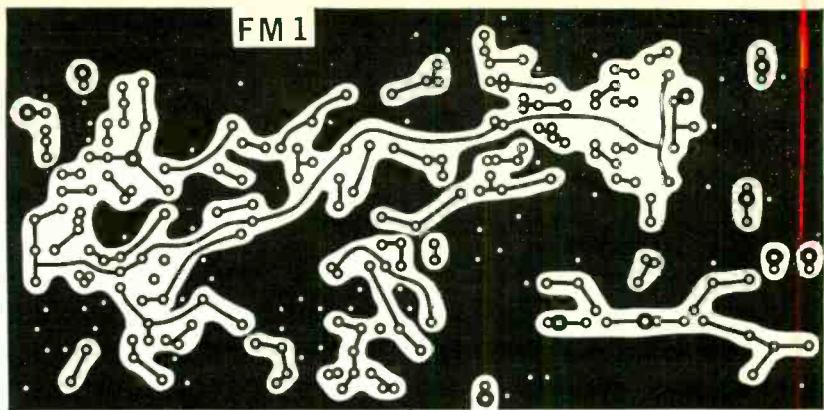T206—J.W. Miller 1355-PC
T207—117V pri., 24V CT secondary, 1A power
xfmr.
D201, D202, D203, D204, D205, D206—1N-
4154
D207, D208, D209—40267
D210—13V Zener diode, 1W, 5%
Q201—2N3391
Q202, Q203, Q204, Q206, Q207, Q208, Q209—
2N3860
Q205—2N5355
Q212—40408
Q213—40407
S201, S202—rocker switches
LM201—12-14V, 25-40 mA pilot bulb



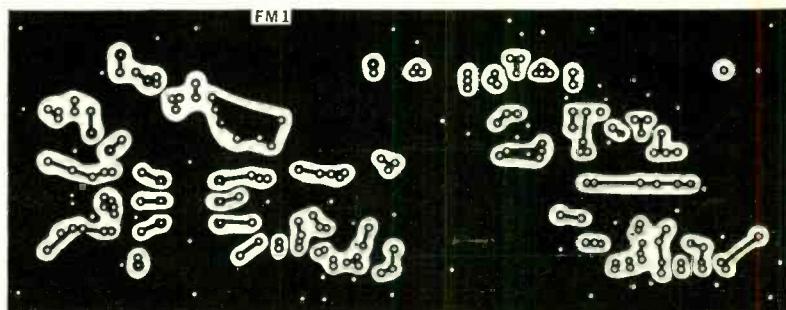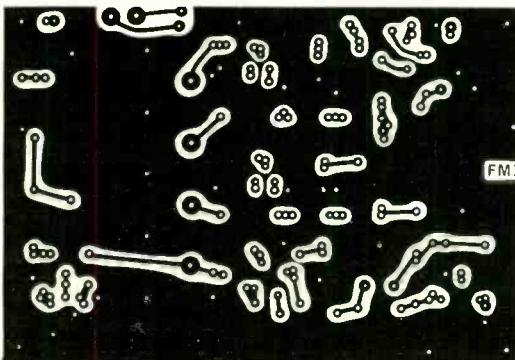Here are the printed circuit patterns used for the FM-1. They are shown one-half actual size and must enlarged photographically. The multiplex/power supply is above, the rf head below (left) and the i.f. strip is below.




Work is something
the handicapped
can do.

Hire them.

The President's Committee on Employment of the Handicapped
Washington, D.C. 20210

EIGHT INSTRUMENTS IN ONE

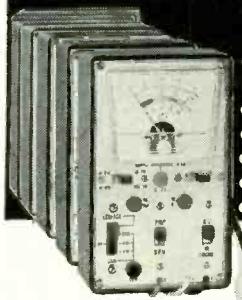

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212

Factory W red & Tested — \$21.50
Easy-to-Assemble Kit — \$14.50

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:

Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N.Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

NAME _____ RE-5

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York 12, New York

Export: Pan-Mar Corp., 1270 B'way, N.Y. 1

MARKET CENTER

ELECTRONICS

Ultra-sensitive and powerful METAL DETECTORS join the many who are finding buried coins, minerals, relics and artifacts. Don't buy till you see our free catalog of new models. Write JETCO—Box 132-RE, Huntsville, Texas 77340

TUBES—LOWEST WORLD PRICES. Foreign-American. Obsolete, current. Receiving, Special purpose, transmitting tubes. Send for tube and parts catalog. UNITED RADIO COMPANY, 56-R Ferry St., Newark, N.J. 07105

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL 4217-E University, San Diego, California 92105

RECEIVING & INDUSTRIAL TUBES, TRANSISTORS. All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request FREE Giant Catalog and SAVE! ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501.

CONVERT any television to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. RELCO-A25, Box 10563, Houston, Texas 77018

INTEGRATED CIRCUITS / RECTIFIERS SEMICONDUCTORS / TRIACS

TRIACS

PRV	10A
100	1.20
200	1.75
300	2.25
400	2.75
500	3.25

10,000 PRV 50 ma rectifiers \$2.00 ea.
ER900 TRIGGER DIODES. These bidirectional trigger diodes are one of the best and cheapest methods to trigger SCR's and triacs 3/\$1.00

UNIJUNCTIONS!

Similar to 2N2419. RBB of 5-7 stand off ratio of .6 and 1p of 12 with data sheet \$1.00
SE 161 ONE SHOTS \$3.50
US 908 FULL ADDERS \$1.50
US 913 REGISTERS \$1.50
US 940 OK FLIP FLOP \$1.00

MOUNTING HARDWARE KITS.

These kits are used to mount our SCR's Zeners and Rectifiers etc.
6x32 stud (3, 12 amp rectifiers, 7A SCR's) 6 sets/\$1.00

1/4x28 stud (30 amp. rectifiers, 20 amps SCR's) 4 sets/\$1.00

Send for our latest catalog featuring Transistors and Rectifiers; 325 Elm St., Cambridge, Mass.

N-CHANNEL FET'S TO-18 plastic units, low noise, low leakage. 25 volts source to gate, 50 ma gate current Gain to 9000 μ ho's. \$.80
 NEON LIGHT OR NIXIE TUBE DRIVERS. An NPN, TO-18, SI Transistor. With a VCEO of 120 3/\$1.00
9030 8 BIT MEMORIES \$3.95

NEW TTL IC SERIES
DECade DIVIDER \$5.95
RF 112 Dual JK Flip Flop \$2.50
MC 415 JK Flip Flop 1.50
MC 400 Dual 4 input NAND/NOR gate 1.50
4 Bit Storage Register 2.50
MC 403 Exclusive OR gate with COMP 1.50
9301 MSI ONE-OF-TEN DECODER 4.95

Silicon Power Rectifiers
PRV | 3A | 12A | 30A
100 | .09 | .24 | .50
200 | .16 | .35 | .80
400 | .20 | .45 | 1.20
600 | .30 | .70 | 1.50
800 | .40 | .85 | 1.80
1000 | .50 | 1.10 | 2.20

Terms: FOB Cambridge, Mass. Send check or Money Order. Include Postage, Average Wt. per package $1\frac{1}{2}$ lb. No C.O.D.'s. Minimum Order \$3.00

WE LEAD THE WAY
IN SERVICE AND QUALITY

OLID

Post Office Box 74D

TATE

Somerville, Mass. 02143

ALES

Tel. (617) 547-4005

Circle 134 on reader service card

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

READER SERVICE CARD NO.

28	Accurate Instrument Co., Inc.	69
125	Admiral Corp.	88
126	Admiral Corp.	89
23	Aerovox Corp.	24
25	Arrow Fastener Co., Inc.	26

14	B&K (Division of Dynascan Corp.)	13
124	Brooks Radio & TV Corp.	86-87
128	BSR USA Ltd.	90
13	Burstein-Applebee Co.	12

10	Castle TV Tuner Service	5
17	Channel Master	15
15	Chapman Mfg. Co.	14
29	Chemtronics	70
27	Cleveland Institute of Electronics	62-65
141	Cornell Dubilier	Cover III
	CREI, Home Study Division of McGraw-Hill Book Co.	28-31

131	Delta Electronics	92
109	Delta Products	77

113	Electronic Chemical Corp.	80
8	EICO, Electronic Instrument Co. Inc.	Cover II
	EMC, Electronic Measurements Corp.	93

19	G-C Electronics	17
120	Gem City Tuner Repair Service	84
9	Grantham School of Electronics	1

117	Heald Engineering College	82
119	Heath Co.	83
121	Heath Co.	85

132	International Correspondence Schools	92
140	International Crystal Mfg. Co.	98

32	E. F. Johnson Co.	72
130	Judson Research & Mfg. Co.	92

20	Leader Instrument Co.	22
11	McGraw-Hill Book Co.	7
110	Microlect	78

107	Motorola Training Institute	76
-----	-----------------------------	----

136	Nortronics	91
118	Olson Electronics, Inc.	82

108	Pennwood Numechron Co.	77
111	PermaPower	78
16	Phase Corp.	14

127	Quietrole Co.	90
-----	---------------	----

26	RCA Electronic Components	Cover IV
122	Tubes	79
114	Test Equipment	81

112	RCA Institutes	18-21
116	RCA Parts & Accessories	91
	Raytheon	71

31	Russell Products	71
12	Rye Industries, Inc.	12
21	Rye Industries, Inc.	22

26	Sams & Co., Inc. Howard W.	27
122	S & A Services Corp.	86
114	Schober Organ Co.	80

18	Sencore	16
22	Sony	23
129	Supreme Publications	91

123	Surplus Center	92
106	Team Central	87
115	Transiek	76

24	United Technical Institute Division of Career Academy	25
----	--	----

137	Arcturus Electronics Corp.	94-97
135	Bele Electronics	
	Edmund Scientific Co.	

138	Musica Associated	
139	Park Electronic Products	
134	Poly Paks	
	Solid State Sales	

134	Terado Corp.	
-----	--------------	--

SCHOOL DIRECTORY

Tri-State College

Valparaiso Technical Institute

SAVE OVER 33 1/3 on a pair of one of The World's Best Speaker Systems. Shipped direct to you from factory. Try them in your home for thirty days. KGLL INC., Water St., Lewiston, Maine 04240

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, RFD #3, Route 7, Brookfield, Conn. 06804

TAPE RECORDER SALE. Brand new nationally advertised brands, \$10.00 above cost. Amazing discounts on stereo components. ARKAY ELECTRONICS, 1028-E Commonwealth Avenue, Boston, Mass. 02215

RENT 4-TRACK OPEN REEL TAPES—all major labels—3,000 different. Free brochure. STEREO-PARTI, 55 St. James Drive, Santa Rosa, Cal. 95401

WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! BARRY, 512 Broadway, New York, N.Y. 10012, 212 WALKER 5-7000.

GENERAL

JAPANESE NEW PRODUCTS MONTHLY! \$1.00. Refundable. DEERE, 10639 Riverside, North Hollywood, Calif.

SCHEMATICS, DIAGRAMS, OLD RADIOS, \$1.50 TVs, \$2.50 GORDIE'S TV, Hustisford, Wis. 53034

RADIO-TELEVISION DIAGRAMS Service Material. 40-pound carton, \$19.95; postpaid. HARTFORD BEITMAN, 1760 Balsam, Highland Park, Illinois 60035

DIRECTORY of JAPANESE ELECTRONICS Companies, \$2.00 Today JAGO RE5, 120 South First Ave., Highland Park, New Jersey 08904

LATEST ARCTURUS SPECIALS

- Color focus rectifiers, 14,000 P.I.V. at 1 MA, 99¢ each. 6.5 KV—79¢
- Color TV yokes 70° & 90° types. Fit almost all sets \$10.95.
- 1700 Transistor types—39¢
- DS-501, 2N278 power transistor types. Cat. #349, 69¢
- HEP170, Motorola HV/CURRENT epoxy silicon rectifiers, 2.5 amps at 1,000 PIV, 49¢
- Fully transistorized UHF tuners. Fit most sets. Cat. #UHF567, \$4.95 each.
- UHF tuners, 1 tube type. Fit most sets. Cat. #UHF3, \$3.95 each.

Complete listings of electronic items at similar bargain prices are available. Write for our latest catalog. Minimum order \$5.00, plus postage.

ARCTURUS ELECTRONICS CORP.

502-22nd St., Union City, N.J. 07087
Dept. M.R.E.
Phone: 201-864-5568

Circle 137 on reader service card

POLY PAKS SMASHES "IC" PRICES!

GE PA-237 2-WATT AUDIO AMPLIFIER

*Lowest Prices *Brand New! \$2.95

2 watts continuous 9 to 27 volt supply, 8 mV sensitivity, includes 11 circuits, for phono, tape recorders, dictating, TV, FM, movie.

Westinghouse WC334 one watt audio amp, TO-5 case

198



How's your "MEMORIES" for 1970?

Guaranteed! With Spec. Sheets!

<input type="checkbox"/> Fairchild 1128 8 bit	\$2.49
<input type="checkbox"/> Fairchild 9033 16 bit	\$4.95
<input type="checkbox"/> Philco PL5R100 Dual 50 bit	\$12.50
<input type="checkbox"/> 4000 Bit Core Planes	\$8.50

TEXAS! NATIONAL! FAIRCHILD COUNTING "IC's"

Guaranteed! W/Spec Sheets Any 3 — 10% Discount!

- 958 Decade Counter \$4.95
- 959 Quad Latch 3.95
- 960 BCD Decoder 5.95
- SN7490 Decade Counter 5.50
- SN7475 Quad Latch 4.50
- SN7441 BCD Decoder 6.50
- 9301 I-to-10 Decoder 4.50
- 9306 BCD Up/Down Counter 8.95
- 9300 4 Bit Univ. Shift Register 2.98
- 9304 Dual Full Adder 4.95
- SN7493 4 Bit Binary Counter 4.95

LINEAR AMPLIFIERS

\$1.69 each, 3 for \$4.75

- 702C DC Amplifier
- 709C Operational Amp
- 710C Differential Comp.
- 711C Sense Amplifier

TERMS: add postage. Rated: net 30, cod's 25%. Phone Orders: Wakefield, Mass. (617) 245-3829. Retail: 211 Albion, St., Wakefield, Mass.

POLY PAKS

P.O. BOX 942 R
LYNNFIELD, MASS
01940



198

BRAND NEW! RTL-TTL 'ICS'

ALL GUARANTEED! With Spec Sheets!

Description	• Low! Low Prices!
<input type="checkbox"/> SG43SD Dual 4 Input Nand/Nor Gate ... TTL	
<input type="checkbox"/> W215F JK Flip Flop DTL	
<input type="checkbox"/> W266F Quad 2 Input Gate DTL	
<input type="checkbox"/> 320T JK Flip Flop (fastest logic) ... ECL	
<input type="checkbox"/> 900FF Buffer RLT	
<input type="checkbox"/> 908TU Full Adder RLT	
<input type="checkbox"/> 909TU Buffer RLT	
<input type="checkbox"/> 912TU Half Adder RLT	
<input type="checkbox"/> 913TU Shift Register RLT	
<input type="checkbox"/> 914TF Dual 2 Input Gate RLT	
<input type="checkbox"/> 923TF JK Flip Flop RLT	
<input type="checkbox"/> 960TU Dual Buffer RLT	
<input type="checkbox"/> 7470FX JK Flip Flop (35mhz) TTL	
<input type="checkbox"/> 7302FX Dual JK Flip Flop DTL	
<input type="checkbox"/> 84 00UF Quad 2 Input Gates TTL	

CODE: S=Sylvania, F=Fairchild, W=Westinghouse, X=Texas, F=Flat Pack, D=Dual Inline, T=TO-5 case, metal. U=unable to name maker. Give 1st, 2nd, and 3rd choices on case styles,

10 for \$1
 1 AMP 800 PIV RECTIFIERS



Circle 139 on reader service card

SERVICE CLINIC (continued from page 87)

about 4000–4200 volts. It sounds like your HV regulator is overdoing it.

Check the cathode current of the 6BK4. I like to set this so that at high brightness levels (with the CRT drawing its maximum beam current) it is drawing a very small current, not more than about 40–50 μA. At a dark-screen setting, this should go up to not more than 1.0–1.2 mA. HV then should be close to 22,000 volts.

Put a 0–500 dc milliammeter in the cathode circuit of the 6CB5 horizontal output tube, and "tune up" the horizontal efficiency coil for a dip in this current. Maximum current should be around 210–220 mA. The HV output should increase slightly at the dip, since this is the point of maximum efficiency or the whole horizontal output stage. Check the damper tube, since this depends on boost voltage. If the damper is down a little it will reduce output of the circuit.

Tape bars on color TV

I've had a color set for about 6 months. Every so often, I get horizontal red and green bars about an inch or so high across the screen. I complained about this, and they told me it was prob-

SOLID STATE 1970 WINNERS

<input type="checkbox"/> Philco SC1600 Dual Mosfets	\$3.98
<input type="checkbox"/> Fairchild 9601 Mono Vibrator	\$2.98
<input type="checkbox"/> Fairchild 741 OP. Amplifier*	\$2.98
*frequency compensated 709	
<input type="checkbox"/> Westinghouse Voltage Regulator	
<input type="checkbox"/> 10¢ BUYS BARGAIN CATALOG	
□ 0 to 40 VDC Positive	\$1.19
Shockley Diodes, 4 layers	3 for \$1.19
Neon & Nixie Driver 2N4410	4 for \$1.00
SCR/Triac Trigger Diodes	4 for \$1.19
9989 4 Bit Binary Counters	4.95
9997 4 Bit Shift Registers	4.95

ably the TV station equipment. Are they pulling my leg?—A. R., Pontiac, Mich.

No. The symptom you describe is typical of a color videotape reproducer with trouble in one or more of the heads. It will normally make horizontal bars (actually 16 lines high) across the screen. These seem to be red and green for some reason.

The problem can take different forms: if one head is bad or dirty, you may see a single red bar about every 5" down the screen. In bad cases, the whole picture may tear up into sawtoothed bars every 16 lines. This effect is most visible on commercials with solid color backgrounds.

Tape recorder belt trouble

I'm having a problem with a Concord 120 tape recorder. The take up belt keeps slipping up until it hits the upper part of the drive-shaft groove. This tears off bits of rubber (continued on page 97)



Rebuild Your Own Picture Tubes?
With Lakeside Industries precision equipment, you can rebuild any picture tube!

For complete details, mail coupon.
Lakeside Industries
5234 N. Clark St.
Chicago, Ill. 60640
Phone: 312-271-3399
NAME: _____
ADDRESS: _____
CITY: _____
STATE: _____
ZIP: _____

MAY 1970

SCHOOL DIRECTORY

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology & Electronic Technology curricula both available. Associate degree in 90 months. B.S. degree obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Sept., Feb. Dorms, campus. High school graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL
INSTITUTE**

Dept. C, Valparaiso, Indiana 46383



distinguished graduates

hold important engineering and management posts throughout U.S. Professionally-oriented college with outstanding placement record. Four-quarter year permits degree in three years. Dedicated faculty. Modern labs. Small classes, 400-acre campus. Accredited. Approved for vets. Moderate total costs. Enter June, Sept., Jan., March. For Catalog, write Admissions.



TRI-STATE COLLEGE

2450 College Avenue, Angola, Indiana 48703

**Help your Post Office to give
you the best possible service
— Mail early in the day!!**

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). 70¢ per word . . . minimum 10 words.

NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items) 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for July issue must reach us before May 10.

CLASSIFIED ADVERTISING ORDER FORM

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .30 Non-Commercial Rates } = \$ _____
{ @ .70 Commercial Rate }

Total Enclosed \$ _____

Insert _____ time(s)

Payment must accompany order unless placed through accredited advertising agency

Starting with _____ Issue

28

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SIGNATURE _____

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT.,
200 PARK AVE. SOUTH, NEW YORK, N.Y. 10003

MARKET CENTER

EDUCATION/ INSTRUCTION

FCC First Class License in six weeks—nation's highest success rate—approved for Veterans Training. Write: ELKINS INSTITUTE, 2603E Inwood Road, Dallas, Texas 75235

MATHEMATICS, ELECTRONICS. Satisfaction guaranteed. Free brochure, INDIANA HOME STUDY, Dept. RE, Box 1189, Panama City, Florida 32401

MEMORIZE, STUDY: "1970 Tests-Answers" for FCC First and Second Class License—plus "Self-Study Ability Test." Proven. \$5.00. COMMAND, Box 26348-E, San Francisco 94126.

ELECTRONICS ENGINEERING. Day or evening classes. Bachelor of Science Program evenings. Associate in Science Program day or night. If you are married or if you must work for a living while obtaining your education, this is the college for you. Approved for Veterans. WESTERN STATES COLLEGE OF ENGINEERING, 970 West Manchester Avenue, Inglewood, California 90301

INVENTIONS & PATENTS

FREE "Directory of 500 Corporations Seeking

New Products." For information regarding developments, sale, licensing of your patented/unpatented invention. Write: RAYMOND LEE ORGANIZATION, 230-U Park Avenue, New York City 10017.

INVENTORS: protect your ideas! Free "recommended procedure". WASHINGTON INVENTORS SERVICE, 422X Washington Building, Washington, D.C. 20005

INVENTIONS WANTED. Patented; Unpatented. GLOBAL MARKETING, 2420-AE 77th Ave., Oakland, Calif. 94605

GOVERNMENT SURPLUS

JEEPS Typically from \$53.00 . . . Trucks From \$78.40 . . . Boats, Typewriters, Airplanes, Multimeters, Oscilloscopes, Transceivers, Electronics Equipment, Used, 100,000 Bid Bargains Direct From Government Nationwide. Complete Sales Directory and Surplus Catalog \$1.00 (Deductible First \$1.00 Order). SURPLUS SERVICE, Box 820-REL, Holland, Michigan 49423

HOBBYISTS, EXPERIMENTERS; BLACK AND WHITE TELEVISION CONVERTED TO COLOR BY MEANS OF A NEW PATENTED COLOR CONVERTER ADAPTOR. INSTALLATION ALL DO IT YOURSELF. WRITE FOR FREE BROCHURE. BELE ELECTRONICS CORP., 111 N.E. SECOND AVE., MIAMI, FLORIDA 33132.

COLOR T.V. IS TERRIFIC with TERADO VOLTAGE ADJUSTERS

ACCURATE
A.C. VOLTMETER

RECTS HIGH OR LOW
VOLTAGE TO NORMAL CAP. 300 to 500 watts
SATURN (shown) Model no. 50-172 List \$26.95
POLARIS (w/o meter) Model no. 50-204 List \$16.50

FULL DEALER DISCOUNTS
See your Electronics Parts Jobber, or write

terado CORPORATION
1053 Raymond Ave., St. Paul, Minn. 55108

ENJOY THE "MUSIC ONLY" FM PROGRAMS

M. A. D.

MUSIC ASSOCIATED'S DETECTOR
for continuous, commercial-free music
with ANY FM tuner or receiver



Kit \$49.50 Wired \$75.00 Cover \$4.95 List of FM stations with SCA authorization \$1.00. For complete information write or call:

MUSIC ASSOCIATED
65 Glenwood Rd.,
Upper Montclair, N.J. 07043
phone 201-744-3387

SERVICE CLINIC

(continued from page 95)

that get into everything. What causes this? The shafts seem to be aligned.—
E. H., Washington, D. C.

The two shafts may seem to be aligned, but they're probably not. You can't "eyeball" this, but you can tell the minute you start them running. If the belt "climbs" or drops, it will mean that they are not parallel, as they must be.

Many tape recorders use flexible suspension on the motors: a set of soft rubber grommets or pads, with the mounting bolts going through the holes. You can align the motor by tightening or loosening these bolts. Better still, by adding more padding or a new grommet. If one of these grommets has gotten old, fallen out or become compressed, this will throw the whole thing out of line.

Replace them with new grommets, and try a test run to see which way the belt wants to travel. R-E

PEP'S Dollar Sale

\$1 Money Back guarantee \$1

1 Amp Silicon Rectifier
choice of package
Bullet—Miniature Glass-Metal

5-800V units \$1.00
 4-1000V units \$1.00
 3-1200V units \$1.00

3 AMP Epoxy Package
 10-1000V units \$1.00
 5-400V units \$1.00
 2-1000V units \$1.00

5 AMP Epoxy Package
 8-1000V units \$1.00
 6-2000V units \$1.00
 3-800V units \$1.00

SILICON STUD MOUNT
12 AMP
 5-1000V units \$1.00
 2-800V units \$1.00
 1-1000V units \$1.00

SILICON STUD MOUNT
20 AMP
 3-1000V units \$1.00
 1-1000V unit \$1.00

SILICON STUD MOUNT
15 AMP
 2-1000V units \$1.00

SILICON STUD MOUNT
60 AMP
 2-500V units \$1.00
 1-1000V unit \$1.25

SPECIAL
INTEGRATED CIRCUITS
Dual 4 Input Nand Gate
Digital \$1.50
Quad 2 Input Nand Gate
Digital \$1.50
JK Flip Master Slave
Digital \$1.75
Linear I C Operational
Amp 709C Type \$1.75

SCR
Silicon Controlled
Rectifier
TO-5 Package

5-50V units \$1.00
 4-100V units \$1.00
 3-200V units \$1.00
 2-400V units \$1.25

7 AMP SCR
 4-50V units \$1.00
 3-100V units \$1.00
 2-200V units \$1.00
 1-500V unit \$1.00
 1-800V unit \$1.50

20 AMP SCR
 2-50V units \$1.00
 1-300V unit \$1.00

Gen Purpose PNP
Germ Transistor Similar
to 2N404
 8 For \$1.00

ZENER DIODES
3 Watt
10 Volts

3 units \$1.00

ZENER DIODES 1 Watt
1 EA 4V-6V-8V-10V
 4 units \$1.00

GERM GLASS DIODES
D07 GEN PURPOSE
 20 Units \$1.00
Replaces 1N-34 1N-60
1N-64 1N-295

Zener Diodes 250 to 400
Milliwatt
1 EA 2V-4V-6V-8V-10V
 5 units \$1.00

16 Bit Memory Cell
\$4.25

14 Lead Dual In-Line Pkg
NO SALES TAX
WE PAY POSTAGE

FULL WAVE BRIDGES
PRV | 2Amp | 3Amp | 5Amp | 10Amp

50V | 1.25 | 1.35 | 1.50 | 1.70

100V | 1.50 | 1.60 | 1.75 | 1.95

200V | 1.75 | 1.85 | 2.00 | 2.20

400V | 2.00 | 2.10 | 2.25 | 2.45

600V | 2.50 | 2.60 | 2.75 | 2.95

800V | 3.00 | 3.10 | 3.25 | 3.45

PARK ELECTRONIC PRODUCTS

P. O. Box 78 N. Salem, N. H. 03073
Tel. (603) 893-0276

Circle 138 on reader service card

MAY 1970

1000's OF UNUSUAL SCIENTIFIC BARGAINS including...

SPECIAL UNIQUE PSYCHEDELIC LIGHTING for Fun, Profit, Effects!

GET YOUR OWN 4'7" SLAVE



Really spectacular 4-channel color organ translates every note, beat and vibration of sound into dazzling, throbbing, crisscross patterns of vibrant color. Individual gain controls—super-sensitive master adjustable to pick up faintest music with bright response. Easily attached to amplifier, stereo, etc. for Master and identical "slave" unit listed below. Ideal for Bands, Discoteques, Night Shows. Uses reg. house current. 55" H x 19" W x 8" D. Stock No. 85.18BEH (57 lb. Shpg. Wt.) \$249.50 FOB
"SLAVE" UNIT (Works in Tandem w/ Master) Stock No. 85.18EH (57 lb. Shpg. Wt.) \$149.50 FOB

PSYCHEDELIC LIGHTING HANDBOOK




100 information packed pages! Fully explains latest in psychedelic lighting equipment, techniques, developments. Covers all facets of psychedelic light-show production including strobes, black lights, projectors, crystals, organic slides, mirrors, color organs, polarized color, light boxes. Music, Vision, etc. 8 1/2" x 11" looseleaf paper for 3 ring binder. Stock No. 910EH \$3.00 Ppd.

LONG-WAVE BLACK LIGHT FIXTURE



Extremely versatile, compactly designed, long wave (3200-4000 angstroms) black light (ultraviolet) fixture—eliminates harmful shorter wave ultraviolet rays. Use to identify minerals, fungi, bacteria—check for surface flaws, oil and gas leakage—perfect for displays with fluorescent paper, paints, chalk, crayons, trace powder. Incl. adjustable aluminum reflector, push-pull switch, connecting plug. Mount vert., horiz., or on corner. 10" L, 1 1/2" W, 1 1/4" H. Stock No. 70.364EH \$12.50 Ppd.
No. 60.124EH REPLACEMENT BULB \$4.50 Ppd.

A COOL ADVENTURE . . . WITH LIGHT!

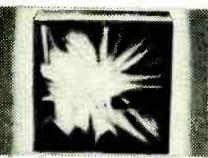

The almost hypnotic spell of ever changing firelight has been captured in a cool-light display box! With the liquid motions of a rising and cascading fountain blowing in the wind, psychedelic colors appear, intermingling and vanish to rise again in new patterns and drift away. This soothing light show housed in a handsome 11 1/2" square by 7" deep, walnut finished humia light box is an effective addition to any room—your living room, bedroom, rec-room, doctor's office. Especially effective among a wall picture group. Modern as tomorrow—available today! Stock No. 71.18EH . LUMINA LIGHT BOX \$29.95 Ppd.

TUNE IN AND TURN ON YOUR OWN

Psychedelic Light Show Take one bookshelf sized conservative looking oiled walnut finished light box—with its built-in kicker, an indiv. controlled 3-channel color organ. Activate by attaching to hi-fi or stereo speaker. Plug in and switch on! Music fills the room and magic fills the room and square by 7" deep, walnut finished humia light box is an effective addition to any room—your living room, bedroom, rec-room, doctor's office. Especially effective among a wall picture group. Modern as tomorrow—available today! Stock No. 71.18EH . LUMINA LIGHT BOX \$29.95 Ppd.

NEW! PROJECTION KALEIDOSCOPE



A low-cost unit with easily interchangeable 9" diam. liquid wheel. Projects variety of color patterns which do not repeat. Specially designed wheel, 3" projection lens and Edmund Visual Special Effects Projector make it all possible. Easily operated. Large screen image at short projection distance perfect for photo backgrounds. Dous current! Stock No. 80.126EH (18" Wx12" Hx9" D) \$49.95 Ppd.

MULTI-COLORED GLASS WHEEL

Shows, parties, dances, etc. Front or rear projection. Incl. 1 RIM 115V Motor, motor bracket, instructions. Stock No. 71.121EH \$94.50 Ppd.
Stock No. 71.122EH (9" diam.) \$15.00 Ppd.

NEW \$99.50 HELIUM-NEON LASER!

Completely assembled, instant-starting w/three times power output of comparable models. Steady, ripple-free light of moderate (safe) power. Excellent collimation. Particularly useful for studies, experiments in holography, interferometry, diffraction, optical alignment. Simple and safe to use—just plug in, switch on. The 4 1/2 lb. unit reaches 75% power in 2 sec.; full power typically 0.5 milliwatt (0.3 mW minimum) in 3 mins. Beam divergence only 2 milliradians (far ahead of competition); beam only 2 eams at 10 feet. Stock No. 79.004EH \$99.50 Ppd.

ORDER BY STOCK NUMBER • SEND CHECK OR MONEY ORDER • MONEY-BACK GUARANTEE

EDMUND SCIENTIFIC CO. 300 EDSCORP BUILDING BARRINGTON, NEW JERSEY 08007

Circle 135 on reader service card

3-CHANNEL COLOR ORGAN BARGAIN!

Create tremendous variety of unusual & beautiful lighting effects with this low-cost top-unit 1500-Watt unit (500 W. per channel). Compare with others selling for twice the price. Has pilot light, plus individual sensitivity controls and channel indicator lights. Can operate ten 150 W. "spots" or 200 Christmas lights. Uses reg. house current—attaches to audio source w/RCA-type phone plug. 5 1/4" x 6 3/4" x 2 1/2". 2 1/2 lbs. Thermal setting plastic case. 6-ft. cord. Including complete instructions. Stock No. 71.223EH \$34.95 Ppd.

AMAZING "TRICK" PHOTOGRAPHY KIT

Now any amateur can produce a variety of weird, wild, way-out photo effects. No special knowledge or equipment required. Unique kit enables you to turn friends into monsters, show house with water to 2nd floor, make psychedelic slides, kaleidoscopic photos, impressionistic photo-art . . . unlimited possibilities. Instructions reveal the secrets . . . includes all accessories needed. Stock No. 71.229EH \$10.50 Ppd.

ROTATING MULTI-COLORED LIGHT

Dazzling colors stream endlessly from constantly rotating light. Faceted, transparent globe is lowered drum inside with red, green, blue & yellow stars. Built heat rotates drum which projects flickering star points on walls, ceilings, etc. while individual globe facets present constantly changing ray of brilliant color. 9 1/2" star—approx. 12" high, bell-shaped base. Surprisingly light. Easily placed on table, TV, fireplace, or Xmas tree top. Stock No. 71.000EH \$6.00 Ppd.

SPECIAL VISUAL EFFECTS PROJECTOR SET

Fantastic variety. Incredibly beautiful. Create floating, exploding, fiery bursts of color like "Symphony of Spheres", "Chronatic Starbursts", "Crystal Starburst". Features 35mm, 500 W. fan cooled projector, produces big image at short distance. Accepts two 9" diam. wheels (Dry Kaleidoscope & Hexidoscope). 2 cylindrical accessories (6" Cloud & 5" Hexidoscope w/six internal mirrored walls). Complete instructions. Stock No. 71.212EH \$79.50 Ppd.

FIND BURIED METAL TREASURE!

Detect individual coins, rings as deep as 12"; metal coins, tools to 3'; metal chest, safes to 6 feet! Best fully transistorized, induction-balance loop detector at moderate price. Rugged, lightweight (3 1/2 lbs.) battery powered. Perfect for treasure hunters, collectors, explorers, beachcombers. Has visual and audible indicators, adjustable soil conductivity knob, on-off switch control, 144-sealed solid state circuitry. 32" overall, adj. 11" diam. loop. Includes 9 Volt (150 hr.) battery. Stock No. 80.119EH \$147.50 Ppd.

STEREO MICROSCOPE—Great Buy!

American made. High power. Direct measurement. Up to 3" working distance—wide 3-dimensional field. 2 sets of objectives on rotating turret. Standard pair of wide field 10X Kellner eyepieces give 23 power and 40 power clear, sharp, erect image. Interpupillary distance adjustable. 10-day free trial. Stock No. 85.056EH \$99.50 FOB

MAIL COUPON FOR GIANT FREE CATALOG

148 PAGES—1000's OF BARGAINS

Completely new edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Endless selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Trisms. Many war surplus items: for hobbyists, experimenters, workshop, factory. Mail coupon for catalog "EZ".

EDMUND SCIENTIFIC CO.
300 EDSCORP BUILDING
BARRINGTON, N.J. 08007

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____



**MXX-1 Transistor
RF Mixer \$3.50**

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range.

Lo Kit 3 to 20 MHz

Hi Kit 20 to 170 MHz

(Specify when ordering)




**SAX-1 Transistor
RF Amplifier \$3.50**

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output.

Lo Kit 3 to 20 MHz

Hi Kit 20 to 170 MHz

(Specify when ordering)

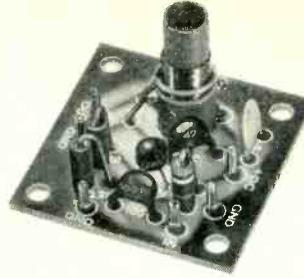

**PAX-1 Transistor RF
Power Amplifier \$3.75**

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency, 3,000 to 30,000 KHz.



**BAX-1 Broadband
Amplifier \$3.75**

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur.

For The Experimenter!

International EX Crystal & EX Kits

OSCILLATOR / RF MIXER / RF AMPLIFIER / POWER AMPLIFIER



Type EX Crystal

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is $\pm .02\%$ when operated in International OX circuit or its equivalent. (Specify frequency)

\$3.95



OX Oscillator

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz
Hi Kit 20,000 to 60,000 KHz
(Specify when ordering)

\$2.95

Write for complete catalog.



CRYSTAL MFG. CO., INC.

10 NO. LEE • OKLA. CITY, OKLA. 73102

Circle 140 on reader service card

The Re-Place



Capacitor Replacements for
Color and B/W TVs, Radios,
Stereo, Hi-Fi



"These capacitors practically sell themselves, like in a supermarket!"



Says Alexander Wellington, owner of Sylvan-Wellington, Inc., New York City, in speaking about The Re-Place, Cornell-Dubilier's new capacitor replacement center. "I am amazed at the increase in turnover, and the ease of selling."

A pioneer in electronic servicing, Mr. Wellington was also one of the first of those alert distributors who have installed The Re-Place in their stores.

The Re-Place is both a showcase and a self-service


store within a store, all in a compact 5' x 2' area. It organizes capacitor inventory and makes it easy for customers to select and to buy from a complete stock of twist-prong aluminum electrolytics, tubular electrolytics, miniature electrolytics, ceramic discs and mica capacitors.

You can provide instant service to your customers with The Re-Place—and profitably increase your turnover, too. Call your CDE Representative today. Or write for full information about The Re-Place.™




CORNELL-
DUBILIER

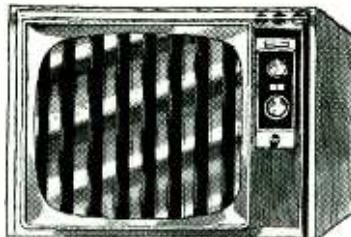When you don't have time to
take it back to the bench...



take this book to the home.

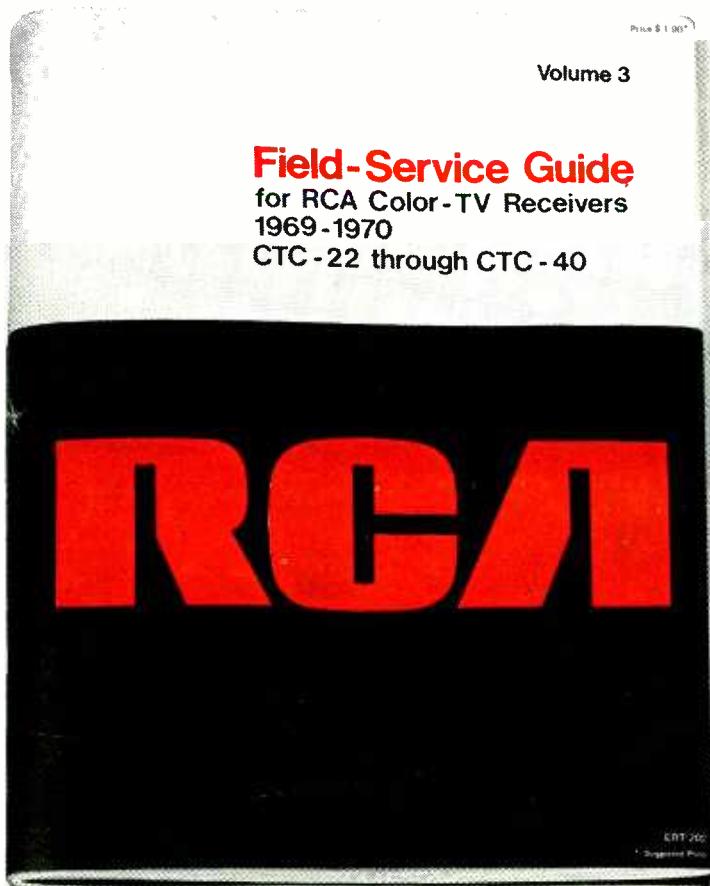

Tells all, shows all, for in-the-home
circuit adjustments on latest RCA color TV's

Here's Volume 3 of the renowned Field Service Guide—the most complete TV service reference of its kind! Add this new edition to Volumes 1 and 2 and you're ready for every RCA color TV dating back to 1955. Seven sections in easy-to-understand form, schematics, plus waveforms and illustrated adjustment procedures:

1. **General Field Service Adjustments.** Step-by-step procedures and illustrations for adjusting purity, black-and-white setup, static and dynamic convergence, and AFPC.
2. **RCA Receiving Tubes for Color TV.** Lists all the type numbers used in RCA color receivers.

3. **Chassis Section.** Specific procedures for adjustment of each chassis series, top-and-rear views, tube removal directions, etc.

4. **Parts List.** Includes major components and their replacement part numbers.

5. **Tuner Section.** Schematics, transistor and electrical control parts lists.

6. **Remote Tuner Section.** Schematics of transmitters and receivers in tuners used in Chassis Series CTC-22 to CTC-40.

7. **Index.** Cross-references for all receivers by model numbers, set names and chassis numbers.

ONLY \$1.90*

*Optional Price

See your RCA Tube Distributor for details on how you can get this valuable Guide.

RCA Electronic Components Harrison, N.J.

