

# Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

**NEW CIRCUITRY**  
Lets You Tell  
The Time On The  
Screen Of Your TV

**40 COSMOS**  
**CIRCUITS**  
IC Projects For  
Experimenters

**WHAT'S A RAM?**  
New Technology  
Report

**LEN FELDMAN TELLS**  
How To Test  
HI-FI Amplifiers

**PLUS**  
Step-By-Step  
Troubleshooting Charts

R  
T  
L  
S  
309196 DRK 6450M090 JUN75 1 A  
LLOYD DARKNELL  
6450 MYRTLEWOOD DR  
SAN JOSE CA 95129  
Jack Darr's Service Clinic



## SPECIAL REPORT

**SOMETHING ELSE TO FIX**  
New Opportunities For  
The Service Technician

# PTS ELECTRONICS

## Precision Tuner Service



now available near you

<b>ALABAMA:</b> 524 32nd ST., SOUTH BIRMINGHAM, ALA. 35222 TEL. 205. 323-2657	<b>CALIFORNIA—NORTH:</b> 4611 AUBURN BLVD. SACRAMENTO, CALIF. 95841 TEL. 916. 482-6220	<b>CALIFORNIA—SOUTH:</b> 5111 UNIVERSITY AVE. SAN DIEGO, CALIF. 92105 TEL. 714. 280-7070	<b>COLORADO:</b> 4958 ALLISON ST. ARVADA, COLO. 80001 TEL. 303. 423-7080	<b>FLORIDA—NORTH:</b> 1918 BLANDING BLVD. JACKSONVILLE, FLA. 32210 TEL. 904. 389-9952	<b>FLORIDA—SOUTH:</b> 12934 N.W. 7TH AVE. MIAMI, FLA. 33168 TEL. 305. 685-9811	<b>HOME OFFICE—INDIANA:</b> 5233 S. HWY 37 BLOOMINGTON, INDIANA 47401 TEL. 812. 824-9331	<b>KANSAS:</b> 3116 MERRIAM LAR KANSAS CITY, KANSAS 66100 TEL. 913. 831-1222
<b>TEXAS—EAST:</b> 4324-26 TELEPHONE RO HOUSTON, TEX. 77032 TEL. 713. 644-6793						<b>LOUISIANA:</b> 2914 WYTCWOOD OR METAIRIE, LOUISIANA 70033 TEL. 504. 885-2349	
<b>TEXAS—NORTH:</b> MOPAC LANE LONGVIEW, TEX. 75601 TEL. 214. 753-4334						<b>MARYLAND:</b> 1105 SPRING ST. SILVER SPRING, MD. 20910 TEL. 301. 565-0025	
<b>TENNESSEE:</b> 3614 LAMAR AVENUE MEMPHIS, TENNESSEE 38118 TEL. 901. 365-1918						<b>MASSACHUSETT:</b> 191 CHESTNUT ST. SPRINGFIELD, MASS. 01103 TEL. 413. 734-2737	
<b>PENNSYLVANIA—WEST:</b> 257 RIVERVIEW AVE W. PITTSBURGH, PA. 15202 TEL. 412. 761-7648						<b>MICHIGAN:</b> 13709 W. 8 MILE RD. DETROIT, MICH. 48223 TEL. 313. 862-1783	
<b>PENNSYLVANIA—EAST:</b> 1921 S. 70TH ST. PHILADELPHIA, PA. 19142 TEL. 215. 724-0999	<b>MINNESOTA:</b> 815 LAKE ST. MINNEAPOLIS, MINN. 55408 TEL. 612. 824-2333						
<b>OREGON:</b> 5220 E. SANDY BLVD. PORTLAND, OREGON 97213 TEL. 503. 282-9636	<b>OKLAHOMA:</b> 3007 N. MAY OKLAHOMA CITY, OKLA. 73106 TEL. 405. 947-2013	<b>OHIO—SOUTH:</b> US TUNER SERVICE CINCINNATI, OHIO 45215 TEL. 513 821-2298	<b>OHIO—NORTH:</b> 5682 STATE RD. CLEVELAND, OHIO 44134 TEL. 216. 845-4480	<b>NORTH CAROLINA:</b> 724 SIEGLE AVE CHARLOTTE, N.C. 28205 TEL. 704. 332-8007	<b>NEW JERSEY—NEW YORK CITY:</b> 158 MARKET ST. E. PATERSON N.J. 07407 TEL. 201. 791-6380	<b>NEW YORK:</b> 993 SYCAMORE ST. BUFFALO, N.Y. 14212 TEL. 716. 891-4935	<b>MISSOURI:</b> 8456 PAGE BLVD. ST. LOUIS, MO. 63113 TEL. 314. 428-1299

... NEW PTS PRODUCTS ... STOP ... PTS 4001 ...  
 ... PORT-A-ANALYST ... STOP ... NOT JUST A SUBBER ...  
 ... THE CADILLAC OF ALL ANALYZERS ... STOP ... PTS 4001 GIVES  
 82 CHANNELS OF HIGH GAIN RECEPTION ... STOP ...  
 ... UHF AND VHF ... STOP ... USE AS AN ANALYST  
 OR PART-A-TUNER ... STOP ... COMPLETELY  
 SAFE ... STOP ... ELECTRICALLY ISOLATED ...  
 ... 115V AC/18V DC ... STOP ...

... \$59.95 ...

... SEE YOUR DISTRIBUTOR OR  
 WRITE THE PTS SERVICE  
 CENTER NEAR YOU FOR  
 MORE INFORMATION  
 ... STOP ...

PTS ELEX.

## LET US TAKE CARE OF YOUR TUNER PROBLEMS. . .

PTS will repair any tuner—no matter how old or new—black & white or color—transistor or tubes—varactor or electronically tuned—UHF. 8 hour service is a must!


### ...THIS IS THE SERVICE WE OFFER:

1. Fastest Service—8 hour—in and out the same day. Overnight transit to one of our strategically located plants.
2. Best Quality—Your customers are satisfied and you are bothered with returning tuners for rework.
3. PTS uses only ORIGINAL PARTS! No homemade or make-do, inferior merchandise (this is why we charge for major parts!). You get your tuner back in ORIGINAL EQUIPMENT condition.
4. PTS is recommended by more TV Manufacturers than any other tuner company.
5. PTS is overhauling more tuners than all other tuner services combines.

VHF, UHF \$10.05  
 UV-COMBO 17.95  
 IF-SUBCHASSIS 12.50

Major parts and shipping  
 charged at cost.  
 (Dealer net!)

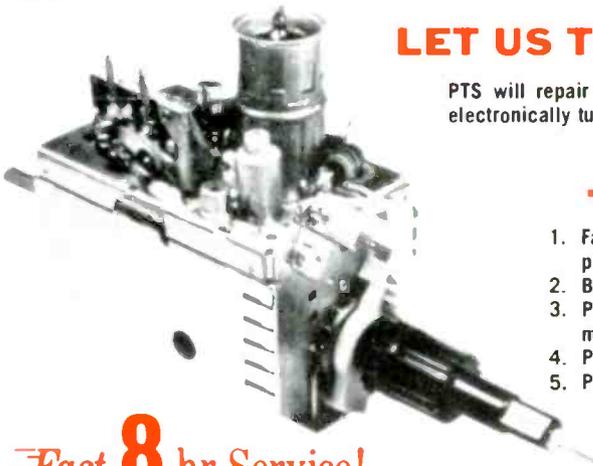Over 4000 exact tuner replace-  
 ments available for \$14.95 up  
 (new or rebuilt).



Fast **8** hr. Service!

We offer you finer, faster...

## 1 YEAR GUARANTEE


... Precision  
 Tuner Service



ELECTRONICS, INC....

...Number ONE and still trying harder!  
 (Not a Franchise Company)

Circle 1 on reader service card

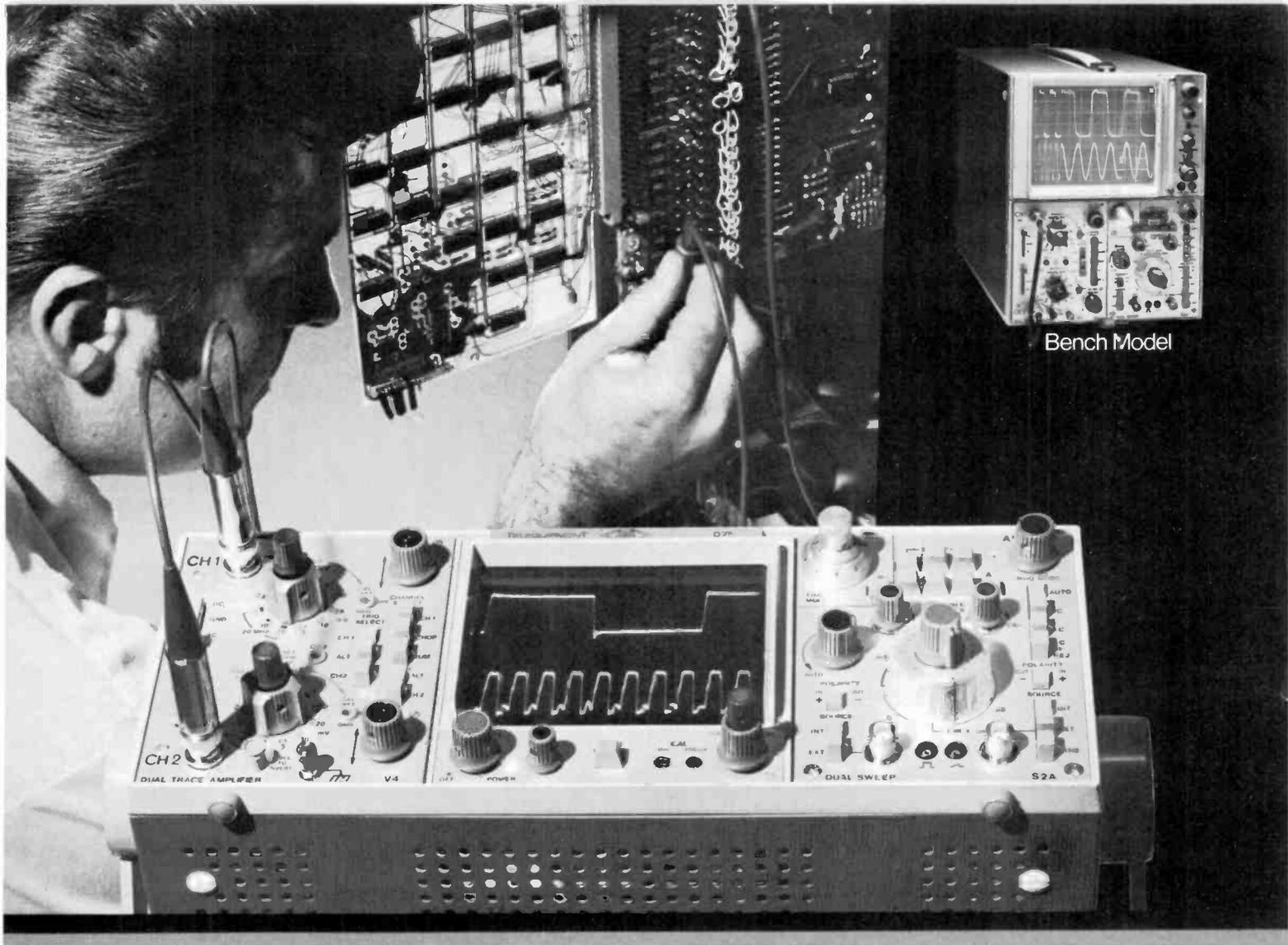

Bench Model

## the Demand is so Great.....

### We put one on the road

The demand is so great for low-cost 50 MHz dual-trace oscilloscopes that we offer two... the D83 Plug-in Oscilloscope and the D75 Portable.

The Telequipment D75 was designed with the electronic serviceman in mind. It trades the D83's plug-in changeability for easy portability. It's lightweight, rugged, and easy to hand-carry onto an airplane. The tilt handle snaps to thirteen different angles to conveniently position the instrument. The D75 costs only \$1375 with the same dual-trace amplifier and dual time base as the D83.

If you like the concept of plug-in selectability, choose the Telequipment D83 for only \$1495. Plug-ins include a differential amplifier (deflection factor 50  $\mu$ V/div to 10 V/div), dual-trace amplifier (deflection factor


5 mV/div to 10 V/div), and dual time base.

Both have large CRT displays, plus delayed, single and mixed sweep. With the mixed sweep mode, you can view the delayed sweep portion simultaneously with the main sweep. Until now, you could only get this feature in more sophisticated scopes. Sweep speeds range from 100 ns/div to 2 s/div with accuracies within 3%. A magnifier (X10) extends the maximum sweep rate to 10 ns/div.

Tektronix backs all its Telequipment OSCILLOSCOPES with its one-year warranty.

D75 Oscilloscope .....	\$1375
D83 Oscilloscope (without plug-ins) .....	\$ 800
V3 Differential Plug-in Amp .....	\$ 295
V4 Dual-Trace Plug-in Amp .....	\$ 295
S2A Dual Time Base .....	\$ 400

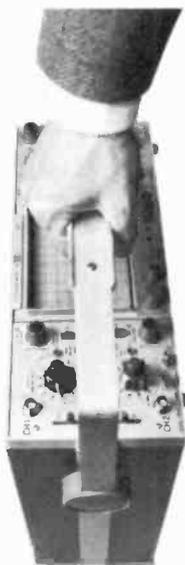Demos and models for sale are ready for immediate shipping. Call your field engineer, or mail this coupon to Tektronix, Inc., P.O. Box 500, Beaverton, Oregon 97005.



Circle 2 on reader service card

Name \_\_\_\_\_  
 Company \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

- I would like a demonstration.
- I would like more information.
- Enclosed is my letterhead/purchase order for immediate shipment.



Circle 15 on reader service card for demonstration 1

# New life for the old test jig.



## Make it a solid-state tester with our new Sylvania Rig-A-Jig™ CK1900X.

The old test jig you used with tube-set chassis can work full time again. Connect the new Sylvania Rig-A-Jig CK1900X to it and *presto*—you have a test jig for solid-state and hybrid TV as well.

The Rig-A-Jig CK1900X has a self-contained anode voltmeter, a complete set of yoke programmers, and an internal focus supply.

And, it will give you a close impedance match in receiver deflection circuits for almost any hybrid or solid-state sets you might have to service. And these connections are easy to make with up-front, highly accessible receptacles.

With simple modifications, you can give new life to your old test jig so it can handle sets with 350 to 500  $\mu$ H SCR sweep, 1 and 3 mH for transformer sweep, or tube and hybrid sets with yoke inductances from 7, 12, and 16 mH. Instruction sheets and set-up manual are also included.

Ask your Sylvania distributor for more information.

Rig-A-Jig CK1900X. The newest addition to the versatile family of Chek-A-Color™ Test Equipment.

**GTE SYLVANIA**

GTE Sylvania, Electronic Components Group,  
100 First Avenue, Waltham, Mass. 02154.

# Radio-Electronics


THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

More than 65 years of electronics publishing

SEPTEMBER 1974 Vol. 45 No. 9

<b>SPECIAL REPORT</b>	43	<b>New Opportunities for Service Technicians</b> There's more than just TV sets that need fixing. And the other consumer electronics repairs are just as profitable. <i>by Larry Steckler</i>
<b>BUILD ONE OF THESE</b>	33	<b>Put The Time On Your TV Screen</b> Take the BCD output of any electronic clock, add this revideo circuitry, and see the time in a 6-digit readout on your TV screen. <i>by Don Lancaster</i>
	47	<b>Op-Amp Tester</b> Easy-to-make device gives both visible and audible indication of op-amp condition. You need one on your bench. <i>by Sol D. Premsky</i>
<b>GENERAL ELECTRONICS</b>	4	<b>Guest Editorial</b> Does servicing have a future. <i>by Robert Adler</i>
	6	<b>Looking Ahead</b> Tomorrow's news today. <i>by David Lachenbruch</i>
	80	<b>Appliance Clinic</b> Using the vom around your car. <i>by Jack Darr</i>
<b>SOLID-STATE ELECTRONICS</b>	26	<b>Equipment Report</b> Continental Specialties Proto-Board Model 103
	50	<b>What's a RAM?</b> Random-Access-Memory, of course! But if you still don't know very much about it, this story will fill the gaps in your knowledge. <i>by Don Lancaster</i>
	58	<b>40 COSMOS IC Projects</b> This new series starts off with a careful examination of how COSMOS IC's work. It's just an introduction to the 40 practical working IC projects that will follow. <i>by R.M. Marston</i>
	66	<b>R-E's Transistor Replacement Directory</b> 2N3939 to 2N4151. <i>compiled by Elizabeth &amp; Robert F. Scott</i>
<b>AUDIO HI-FI STEREO</b>	61	<b>Measuring Audio Amplifier Performance</b> It takes the best equipment and you must use it properly. <i>by Len Feldman</i>
<b>TELEVISION</b>	26	<b>Equipment Report</b> Winegard CableMate Model CTS-1
	64	<b>Step-By-Step Troubleshooting</b> Always look at the CRT first. <i>by Stan Prentiss</i>
	69	<b>Service Clinic</b> The transistor — that imprecise device. <i>by Jack Darr</i>
	76	<b>Reader Questions</b> R-E's service editor solves reader problems.
<b>DEPARTMENTS</b>	106	<b>Advertising Index</b>
	86	<b>New Products</b>
	99	<b>Books</b>
	93	<b>Next Month</b>
	24	<b>Letters</b>
	109	<b>Reader Service Card</b>
	12	<b>New and Timely</b>
	96	<b>Technotes</b>
	91	<b>New Literature</b>
	97	<b>Try This</b>

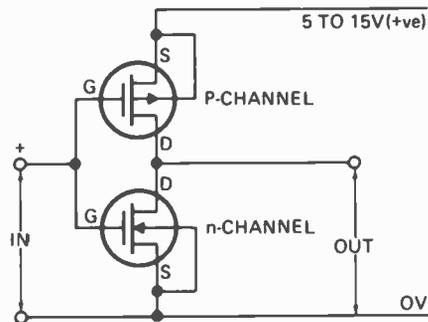**ON THE COVER**  
Here's the working heart of a new Sharp EL-805 calculator. The liquid-crystal readout and the circuit board are all on a single sheet of glass. For more details, see the article "New Opportunities For Technicians." It starts on page 43



40 COSMOS IC PROJECTS for the experimenter are here. They're part of a new series starting in this issue. The circuit shown here is a basic COSMOS digital inverter.

...turn to page 58

Hugo Gernsback (1884-1967)  
founder

M. Harvey Gernsback, editor-in-chief and publisher

Larry Steckler, CET, editor

Robert F. Scott, W2PWG, CET, technical editor

Jack Darr, CET, service editor

I. Queen, editorial associate

Leonard Feldman, contributing high-fidelity editor

David Lachenbruch, contributing editor

Barbara Schwartz, editorial assistant

Vincent P. Ciconia, production manager

Sarah Martin, production assistant

Harriet I. Matysko, circulation director

Arlene R. Bailey, advertising coordinator

Cover photograph by Walter Herstatt

Cover design by Louis G. Rubsamem

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.



Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York City 10003. Second-class postage paid at New York, N.Y. and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$7. Pan-American countries, \$8. Other countries, \$8.50. Single copies 60c. © 1974 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**Subscription Service:** Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, Colo. 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

---

# guest editorial

## *does servicing have a future?*

Many electronic service technicians are uneasy about the future and with apparent good cause. All manufacturers of consumer electronic products are trying hard to design their products for 100% reliability. If they achieve that level, service of course would no longer be required.

Then is the service industry about to become another victim of the technology? Should it prepare to go out of business?

The answer to both of these questions is *no*. There are good reasons why service will be around for a long time to come. For one thing, it is difficult to close our eyes to the fact that products in the home have become more and more complicated through the years. To keep our customers coming back, Zenith—like all other successful manufacturers—must continually add new features and conveniences to its products. Television for example has progressed from black-and-white to color, and the color TV set is the most complex electronic device ever mass-produced. Radio too has progressed from the simple five-tube AM set to FM, and FM stereo. Stereo is of course merely a duplication of channels with a balancing network. But now, multi-channel devices are coming into use which include quite complicated decoding systems. Quadriphonic FM broadcasting will be especially complex.

And this trend will continue. Extrapolating from experience, new products such as the video disc player will involve some fairly precise and complex mechanical equipment. Also, the product may have optics which have never before played a role in consumer electronics, and the design is quite likely to involve some little tricks that are completely different from anything done in the past.

And speaking of new products, when flat-panel television comes on the market, the panel itself, like the present picture tube, probably will not be serviceable. However, the peripheral electronics promise to be a relatively complicated array of a great many circuits arranged on circuit boards, or in some other integrated form. These will require occasional servicing.

So products have become more complex, and this trend to greater complexity will continue. This means that servicing will continue to be in demand to keep those complicated devices operating. But along with complexity, reliability has also increased greatly.

Reliability per active device in a solid-state circuit is quite a bit better than with vacuum-tube circuits. On the surface, it may not seem that way, but instead of a simple radio set with four or five vacuum tubes, we are likely to be faced with a complicated product equipped with many integrated circuits each containing dozens of active devices. In a flat-panel TV display system, that number could increase to several hundred IC's corresponding to thousands of individual transistors. So it has become a race between the reliability of individual components and

the complexity of the assemblies of those components. Each containing dozens of active devices. In a flat-panel TV display system, that number could increase to several hundred IC's corresponding to thousands of individual transistors. So it has become a race between the reliability of individual components and the complexity of the assemblies of those components.

It is well that reliability has increased. If it had not, the situation would be hopeless, for these complicated new products would never operate.

How will all this affect servicing? Fundamentally, the job of the electronic service technician is not going to change. But I think that the job will become more challenging in that he will have to be much more of a detective to find out what is wrong. The technician is going to be faced with many types of products; no two will be exactly alike, nor exactly like what he saw last week. He will have to use his brain and his education and his training to find the trouble quickly—he won't be able to spend all day plugging in one board after another. Rather than such a machine-like approach, he will have to rely on his experience, intuition, and his ability for intelligent deduction. The job of servicing is definitely going to become more intellectual and less physical—that is, less tinkering, less soldering will be needed.

And as equipment gets more complex, it will be necessary for the technician to learn how these complex devices operate. It will not, however, be necessary for him to learn everything in complete detail. Take a very complicated IC, for example—understanding its operation is a real challenge for almost anyone. The technician won't have to understand the theory of that IC; he will, however, have to know its function in the circuit and its effect on the entire system if it develops a fault. Learning these facts alone is a big challenge, for there are a great many IC's, and the number is steadily increasing.

Fortunately, most technicians will try to understand as much as they can. That's built into the nature of the man who makes a career of electronics—that curiosity about how things operate is what brings him into the field. If he doesn't have that inborn curiosity, he won't go very far in the technical end of the business.

Servicing is here to stay. The number of service calls per product per year may decrease due to increased reliability. This factor, however, will be offset by the increase in the number of products that will require servicing, and their greater complexity.


The services of the electronic technician will continue to be in demand as long as electronic equipment is manufactured.

—by Robert Adler, Vice President of Research, Zenith Radio Corporation, Chicago, Ill.


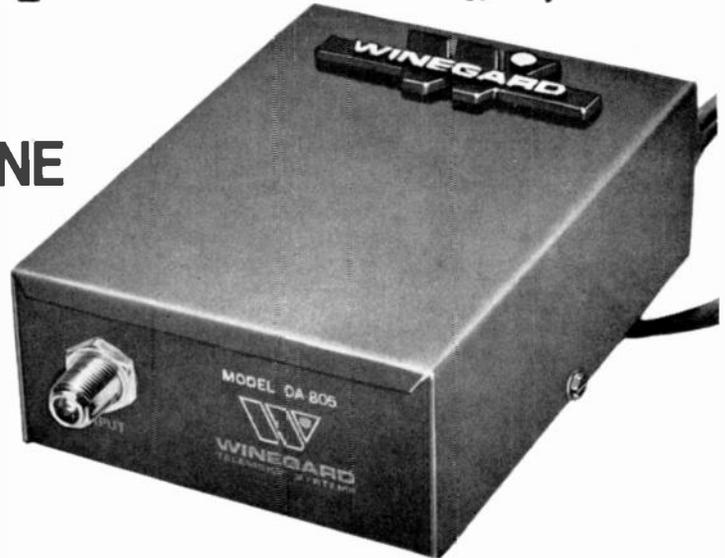
# Announcing the WINEGARD METRO-LINE TV-FM DISTRIBUTION AMPLIFIERS

...the first high input,  
high output, low-cost  
MATV system amplifiers  
for strong signal areas



Winegard's new Metro-Line amplifiers are specifically engineered to accommodate strong signals and eliminate overload economically and efficiently. Because they have the same commercial quality construction and circuitry as the DA-830, DA-825B and DA-815, they are ideal for home, hotel, apartment and office building systems.

Check these other important performance features:

- High output capability makes a Metro-Line your best db buy
- High input solves distortion and overload problems common in strong signal areas
- Lightning protection diode
- 82 channel models have separate VHF and UHF amplifier stages
- Extended band pass (54 to 300MHz) includes mid and super band coverage making Metro-Line approved for CATV use
- Eliminates multiple outlet charge for extra sets or MATV systems on cable TV
- UL listed
- Easy for any competent TV service dealer to install
- Choose from 3 VHF-FM and 2 VHF-UHF-FM models; suggested list prices from \$30.85 to \$47.30

		DA-203	DA-205	DA-215	DA-803	DA-805
OUTPUT PER CHANNEL*	VHF	46dbmv	46dbmv	53dbmv	43dbmv	45dbmv
	UHF	NA	NA	NA	35dbmv	35dbmv
INPUT PER CHANNEL*	VHF	31dbmv	31dbmv	40dbmv	31dbmv	31dbmv
	UHF	NA	NA	NA	26dbmv	26dbmv
GAIN	VHF	15db	15db	13db	12db	14db
	UHF	NA	NA	NA	9db	9db
IMPEDANCE		300 ohm	75 ohm	75 ohm	300 ohm	75 ohm
Bandpass	VHF	54 to 300MHz				
	UHF	NA	NA	NA	470 to 810MHz	470 to 810MHz
NOISE FIGURE	VHF	4.2db	3.3db	4.8db	4.3 db	3.3db
	UHF	NA	NA	NA	10.0db	7.3db
POWER REQUIREMENTS		117VAC, 60Hz, 2.3 watts	117VAC, 60Hz, 2.3 watts	117VAC, 60Hz, 2.3 watts	117VAC, 60Hz, 3.5 watts	117VAC, 60Hz, 3.5 watts

\*7 channels VHF, 5 channels UHF      0.5% Cross Modulation

For additional information and sample system layouts, request New Product Bulletin No. 24.



**WINEGARD TELEVISION SYSTEMS**  
Winegard Company / 3000 Kirkwood Street  
Burlington, Iowa 52601

Circle 3 on reader service card

# looking ahead

## RCA drops audio

Next year will be the end of an era which started in 1922 when RCA marketed its first radio. The RCA Corporation (whose name was changed in 1969 from "Radio Corporation of America") in 1975 will discontinue marketing audio products — radios, tape equipment and phonographs — to concentrate on television and such "video-related products" as home VTR's and videodisc systems. RCA's radio career ends as it began—its last and its first radio products were made by others. Its radios now are all made overseas to its specifications. Its first home radio introduced in Jan. 1922 was a GE-made crystal set at \$18 list (antenna \$7.50 extra). The first Victor phonograph was made at the dawn of the 20th century, and RCA absorbed the Victor Talking Machine Co. in 1929. With Victor, it inherited Nipper, the famous "His Master's Voice" dog trademark. Poor Nipper! Do you remember him?

Another pioneer is also dropping out of radio. Philco, whose name was synonymous with radio, particularly in rural America of the 1920's, will also discontinue radio marketing, and drop compact stereo systems as well (but remain in the stereo console business). The change in the mass-market audio business has also affected Warwick Electronics, long-time supplier to Sears Roebuck, which has discontinued stereo manufacturing to concentrate on color TV.

## Super-fi cassette

Uniset, a completely new tape cassette system designed for the professional and audiophile market, is expected to make its debut next year. Designed by BASF, German tape and equipment manufacturer, it's expected to be introduced simultaneously by several manufacturers. The new cassette uses high-

performance quarter-inch tape which can travel at 1 $\frac{1}{2}$ , 3 $\frac{3}{4}$  or 7 $\frac{1}{2}$  ips. The cassette is about the size of a paperback book, is designed so that all transport functions are accomplished by the recording and playback system and aimed at performance equal to that of open-reel recorders. The first such recorders are expected to retail at about \$400.

## The real cost

To find the real cost of a new color TV set today—the amount it will set you back over its lifetime—just multiply the retail price by two. A set selling at about \$400 will cost you \$800 over its expected 10-year lifetime, including purchase price, electricity and service. These are conclusions reached in a two-year study entitled "Consumer Appliances: the Real Cost," made by MIT under the sponsorship of the National Science Foundation.

The study found that the purchase price of the average 1972-model television set was about 53% of its "life-cycle cost," service was 35% and power 12%. Among other findings: (1) A typical modern color set fails approximately once a year as opposed to three times a year for a set built in 1960 and six times a year for a 1954 model. (2) The one-year parts-and-labor warranty now standard on most solid-state color sets costs the manufacturer about \$25 per set, as compared with \$3 for the 90-day parts-only warranty which once was standard. (3) Fully 30% of all warranty service calls are caused by consumer ignorance rather than set failure. (4) From 1965 to 1972, the average service call cost rose from \$20 to \$30 and is expected to reach \$50 by 1980. (5) TV technicians spend about 42% of total repair time scheduling calls and traveling to customers' homes. (6) TV carry-in service is expected to rise from 57% of all service in 1970 to 74% in 1980. Since the total number of technicians is expected to decline by 1980,

while the number of calls a technician can make per day stays the same, the report concludes that continued improvement in reliability is one of the best ways to meet service problems. It also recommends that manufacturers inform consumers of life-cycle costs.

## New videotape

3M is quietly distributing to equipment manufacturers a new type of videotape which it believes is so revolutionary that it could lead to tiny hand-held video cameras with built-in recorders and make practical other home videotape devices. A 3M spokesman said the new tape had six times the magnetic strength of today's tapes, but declined to elaborate. Such an increase in signal strength theoretically, at least, could make possible videotape transports running at one-sixth the speed of today's units. The tape is so radically different that it requires the development of special heads and other hardware. The production of both the tape and the equipment is several years off.

## Quasar by Matsushita

Over the years, Motorola has developed Quasar into a major brand name. And now it's no longer "Quasar by Motorola" but Quasar by Matsushita, as the result of the first purchase of an American television manufacturer by a Japanese firm. Matsushita, which probably is the world's largest television manufacturer, also makes Panasonic television for sale in the U.S. It will continue to manufacture Quasar TV in the U.S. and will continue to sell Panasonic sets here as a separate line (although it may make some Panasonics in Quasar's plants). The sale of Motorola's television business to the Japanese giant culminated two years of unprofitable operation, after which Motorola

decided to concentrate on its highly profitable semiconductor, communications and automotive electronics businesses. Zenith and Magnavox attempted to halt the sale on anti-trust grounds at the zero hour. Matsushita is now operating Quasar and it will spend many millions of dollars on plant-modernization.


## Dolbyized FM

The FCC has ruled that FM stations are free to process their signals with a combination of Dolby B-type noise-reduction unit and reduced pre-emphasis of 25 microseconds instead of 75. For listeners without Dolby units, it's claimed that this move will reduce high-frequency distortion and/or increase the program level. With a Dolby unit in the receiver and proper pre-emphasis, the move should result in improved S/N ratio, better dynamic range, better fringe area reception and reduced susceptibility to interference, says Dolby Labs. Existing Dolby B home units would require modification to realize the full benefits of Dolbyized transmissions. Several FM stations are already broadcasting under the new standards, and new Dolby units with the proper pre-emphasis are expected on the market soon.
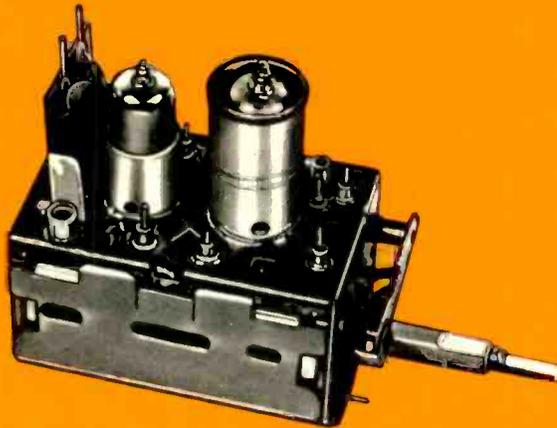
## Exit Packard Bell

After a rough-and-tumble, turbulent year which saw the television business of Admiral, Motorola and Philco offered for sale, one of America's pioneer TV manufacturers — Packard Bell — has decided to call it quits. A West Coast television brand since 1948, Packard Bell's parent company, Teledyne, is now in the process of shutting down its plants in Los Angeles and Nogales, Mexico, and selling off its inventory. The decision was obviously a sudden one. The company had already started producing its 1975 line.

by DAVID LACHENBRUCH  
CONTRIBUTING EDITOR



# \$995

ALL PARTS INCLUDED

except tubes and transistors

ONE YEAR GUARANTEE

## TUNER SERVICE CORPORATION

**PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.**

### REPAIR

VHF Or UHF Any Type \$9.95.  
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged extra.

Fast efficient service at our conveniently located service centers. This price does not cover mutilated tuners.

All tuners are cleaned ultrasonically, repaired, realigned and air tested.

### REPLACE

Universal Replacement (In Canada \$14.95)

This price buys you a complete new tuner built specifically by SARKES TARIAN INC. for this purpose.

All shafts have a maximum length of 10" which can be cut to 1 1/2".

Specify heater type parallel and series 450mA or 600mA.

### CUSTOMIZE

Customized tuners are available at a cost of only \$15.95. (In Canada \$17.95/\$15.95)

Send in your original tuner for comparison purposes to:

## TUNER SERVICE CORPORATION

Backed by the largest tuner manufacturer in the U.S.—SARKES TARIAN, Inc.

HEADQUARTERS	BLOOMINGTON, INDIANA 4701	537 South Walnut St.	Tel: 812-234-0411
ARIZONA	TUCSON, ARIZONA 85713	1528 S. 6th St. (P.O. Box 4534)	Tel: 502-791-9243
CALIFORNIA	BURLINGAME, CALIFORNIA 94010	1324 Marsten Road	Tel: 415-347-5728
CALIFORNIA	MODESTO, CALIFORNIA 95351	123 Phoenix Ave.	Tel: 209-521-8051
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91691	10654 Magnolia Blvd.	Tel: 213-769-2720
FLORIDA	TAMPA, FLORIDA 33606	1505 Cypress St.	Tel: 813-253-0324
GEORGIA	ATLANTA, GEORGIA 30310	938 Gordon St., S.W.	Tel: 404-758-2232
ILLINOIS	CHAMPAIGN, ILLINOIS 61820	405 East University St.	Tel: 217-356-6400
ILLINOIS	CHICAGO, ILLINOIS 60621	737 W. 55th St.	Tel: 312-73-5556-7
ILLINOIS	SKOKIE, ILLINOIS 60076	5110 W. Brown St.	Tel: 312-675-0230
INDIANA	INDIANAPOLIS, IND. 46204	817 N. Pennsylvania St.	Tel: 317-632-3493
INDIANA	HAMMOND, INDIANA 46323	6833 Grand Ave.	Tel: 219-845-2676
KENTUCKY	LOUISVILLE, KENTUCKY 40208	2920 Taylor Blvd.	Tel: 502-634-3334
LOUISIANA	SHREVEPORT, LOUISIANA 71104	3025 Highland Ave.	Tel: 318-861-7745
MARYLAND	BALTIMORE, MD. 21215	5505 Reisterstown Rd. (P.O. Box 2624)	Tel: 301-358-1186
MISSOURI	ST. LOUIS, MO. 63132	10530 Page Ave.	Tel: 314-429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Ave. #1	Tel: 702-384-4235
NEW JERSEY	JERSEY CITY, NEW JERSEY 07307	547-49 Tonnole Ave. (U.S. Highway 1 & 9)	Tel: 201-792-3730
NEW JERSEY	TRENTON, NEW JERSEY 08638	901 N. Olden Ave.	Tel: 609-393-0999
OHIO	CINCINNATI, OHIO 45216	7450 Vine St.	Tel: 513-821-5080
OHIO	CLEVELAND, OHIO 44109	4597 Pearl Road	Tel: 216-741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Ave.	Tel: 503-222-9059
TENNESSEE	GREENVILLE, TENNESSEE 37743	1215 Snapps Ferry Rd.	Tel: 615-639-8451
TENNESSEE	MEMPHIS, TENNESSEE 38111	3158 Barron Ave.	Tel: 901-458-2355
TEXAS	DALLAS, TEXAS 75218	11540 Garland Rd.	Tel: 214-327-8413
VIRGINIA	NORFOLK, VIRGINIA 23513	3295 Santos Street	Tel: 804-855-2518-9955
CANADA	TUNER SERVICE CORP., QUEBEC	Write headquarters office for address.	

Franchises available-Contact headquarters for information.

Circle 4 on reader service card



WATCH US GROW

# Compare what you get training and you'll

## Compare costs

Only NRI offers complete TV/ Audio Servicing Courses from \$312 to \$955 . . . with terms as low as \$10 down and \$22 monthly. In the Master Course in color TV servicing, with a 25" diagonal solid state color TV, you save \$800 or more over other comparable courses. And NRI provides you with a handsome TV cabinet and other equipment at no extra charge.

NRI saves you money because our costs are lower. We pay no salesmen, and we design our own kits and equipment. We don't buy "hobby kits" from others. Nor do we penalize you with big interest charges for time payments. We pass the savings on to you.

## Compare training

NRI is one of the few home study schools that maintains its own full-time staff of technical writers, editors, illustrators, development engineers and publications experts. The people who design the kits also design the lessons . . . so that theory and practice go hand in hand. The lessons aren't "retro-fitted" to an outside-source "hobby kit". The NRI set is designed exclusively for training. The fact that it is also a superb receiver for your personal use is an added plus.

## Compare choices

Most schools offer one course in color TV servicing, period. Only NRI offers you five different courses to match your needs and budget. The 65-lesson basic course, complete with 7 kits, costs as little as \$312. Or you can step up to a \$425 course that includes a 12" diagonal black & white portable TV for hands-on experience. Then there's the 19" diagonal solid-state color TV course for \$695; the advanced color TV course for trained technicians with the same 19" TV for \$535; and finally, the magnificent 25" diagonal solid-state color TV course, complete with console cabinet, oscilloscope, TV pattern generator, and digital multimeter, for \$995. Other schools charge you up to \$800 more for an equivalent course.



# in TV/Audio home choose NRI.

## Compare equipment    Compare schools

NRI has engineered the widest variety of professional electronic lab equipment ever designed entirely for training at home. When you enroll in the master course in TV/Audio Servicing, for instance, you receive kits to build a wide band, solid-state, triggered sweep, service type 5" Oscilloscope; color pattern generator; solid-state radio; and a digital multimeter.

Before you settle on any home training course, compare the over-all program. See if you are getting kits engineered for experimentation and training . . . or merely "hobby kits". Count the experiments . . . compare the components. Don't just count kits. (Some schools even call a slide rule a kit.)

Home study isn't a sideline with NRI. We've been its innovating leader for 60 years. Ask any of the hundreds of thousands of NRI graduates. They'll tell you . . . you can pay more but you can't buy better training.

Along with each course, NRI provides bite-size, fully-illustrated lessons; personally graded tests; and the kind of person-to-person teaching that makes learning easier and faster.

Send for the free NRI full-color electronics catalog and discover why so many choose NRI. You'll find courses offered in TV/Audio Servicing, FCC License, Complete Communications Electronics, Digital Computer Electronics, Marine and Aircraft Electronics, Mobile Communications, etc.

**MAIL  
THIS CARD  
FOR YOUR  
FREE NRI  
CATALOG**



NO SALESMAN WILL CALL.

**AVAILABLE UNDER GI BILL**

Check the GI Bill Box on the card for information.



**NRI SCHOOLS**  
McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue,  
Washington, D.C. 20016



# new & timely

## Second 1974 Scholarship Award won by David C. Greene

The winner of the Second 1974 Hugo Gernsback Scholarship Award—a \$125 grant made annually to an outstanding student in each of eight leading electronics home-study schools—is David C. Greene, 26, of Knoxville, TN. He is a home-study student of the Grantham School of Engineering, Los Angeles, CA.

After a short period as an instrumentation technician for an Oak Ridge firm in 1966, Mr. Greene got a job as transmitter engineer on the local radio station, WATE. Having much free time on watch, and an interest in two-way FM radio, he took a training course from a two-way radio manufacturer, supplementing this training by buying parts from the local distributor and setting up interesting circuits he saw in the manuals, running tests on them and making measurements, to improve his understanding of their action.

Discovering that he needed more theory and mathematics, Greene wrote to several of the schools advertising in the electronic magazines, and selected the Grantham School of Engineering as the one likely to be best suited to his needs. He is continuing with Grantham toward an Associate degree in Science in Electronic Technology.



David C. Greene


Sale of the station — now renamed WETE — resulted in promotion to chief engineer — with the side effect that the many duties of the new job cut down on time available for study.

In 1972, he was able to put his new knowledge to work. He joined Ultra Electronics, Inc., of Knoxville, manufacturers of scanning FM monitors, and is now engaged in designing multi-channel FM scanning receivers. In a letter to Gran-

tham, he thanks the dean of students for allowing him so much time on the fifth semester of his studies, since his time is still limited. Mr. Greene holds a First Class FCC license and an Advanced Class amateur license. •
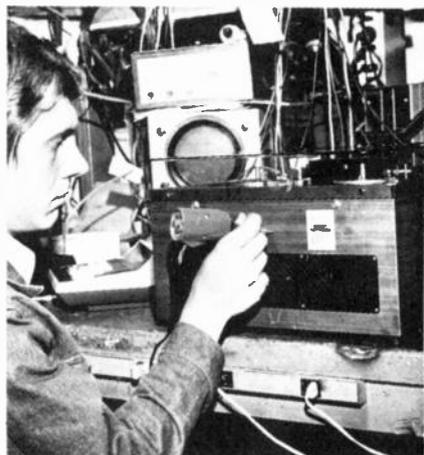
## Do something extra

Identification programs are among the more effective approaches in the spreading citizens' campaigns against crime. In such programs, an identification number — car license, social security number or



**IDENTIFYING A PIECE OF EQUIPMENT** with an engraving tool is almost as easy as writing down one's name with a fountain pen. The tool writes on metals, plastics, glass and ceramics. Writing is not easily removed.

other identification — is engraved on valuables most likely to be stolen. Since no experienced thief will knowingly steal a marked item, identification is a significant deterrent.

In areas where such programs have been put into effect — usually by block groups with police cooperation — thefts and burglaries have dropped substantially. But the programs are not as widespread as they might be, due in many cases, to lack of information, as well as lack of engraving equipment on the part of most home owners. Neighborhood groups, who could often borrow the tools from local police departments, are slow to organize, and in many areas the police themselves have not been active in identification programs.

Now a Wisconsin manufacturing concern, Dremel Division of Emerson Electric, has a plan to change all that. Briefly, the proposal is that electronic service technicians take the lead in promoting identification projects, thereby building up a positive image for their own concerns and the profession, and good-will with their customers, as well as a modest source of supplementary income from

identifying valuables for homeowners. The electronic service technician is a natural for this work, since the burglars' most common targets by far are electronic entertainment appliances.

The technician can offer the service as a good-will benefit to his customers, or make a special charge for identifying valuable items. Either way, he's providing an important service to his customer, for TV's, recorders and expensive audio equipment are the first things a burglar will look for — as long as they're not engraved.

As Dean Peel, Dremel's project theft-guard coordinator, sees it, the project has three basic elements:

**1. The engraver.** (Dremel naturally suggests their model 290, a rugged and long-lived device with a carbide or diamond tip that will mark indelibly any material the service technician is likely to encounter.)

**2. Theft-Guard stickers.** These are posted in conspicuous spots to warn off potential thieves. An ideal place is on the glass panes with which most exterior doors are provided. There, the warning may even forestall an attempt to enter.

**3. Inventory of protected property.** All engraved items should be listed, and where local police participate, a copy furnished to them. In some cases, police with such lists have restored stolen property before the owner missed it!

And there is no question that the technique works! Mr. Peel tells of an incident



in San Antonio, Texas, where two neighbors had their valuables engraved the same day. Burglars broke in that night, before the homeowners had got around to posting the warning stickers, and took

(continued on page 16)

# Radio Shack / Realistic 82 Watt Receiver Sale!



Reg. 249<sup>95</sup>

Sale 159<sup>95</sup>

SAVE \$90 on the magnificent STA-80 during this sale. Hurry — it's one of our best Realistic® sellers.

It'll make the heart of a great stereo system — a tape monitor lets you record like a "pro" and a switch lets you select main and/or remote speakers. For great sound we gave the STA-80 wideband AM, FET/IC FM, a hi-filter, FM muting, signal strength and center-channel meters, exclusive Perfect Loudness® for natural bass even at low volume and unique Glide-Path™ volume/balance controls. For beauty we gave it a blackout dial, a lighted dial pointer that doubles as a stereo beacon and a 29.95-value walnut veneer case. There's only one place you can find it... Radio Shack! #31-2046.

## Complete Realistic STA-80 System

save 119<sup>95</sup>  
regular 469.90  
**349<sup>95</sup>**

- Realistic STA-80 Receiver
- Two Solo-3B Speaker Systems
- LAB-36A Changer, Base, \$22.95-Value Elliptical Cartridge



Master Charge or  
Bank Americard at  
participating stores.

# Radio Shack®

A TANDY CORPORATION COMPANY

OVER 3000 STORES • 50 STATES • 8 COUNTRIES

Retail prices may vary at individual stores.

## FREE New 1975 Radio Shack Catalog

OVER 2000 PRODUCTS  
EXCLUSIVES ON EVERY PAGE  
BEAUTIFUL FULL COLOR

Stereo • Quadraphonic • Phonographs  
TV Antennas • Radios • Citizens Band  
Kits • Recorders • Tape • Tools  
Auto Tune-Up • Electronic Parts  
Test Instruments • More!



164 pages of the finest in home and hobby electronics. Respected names like Realistic, Micronta, Archer, Science Fair — and they're available only at Radio Shack stores and dealers nationwide! See what's really new in electronics.

SEND FOR YOURS TODAY!  
FILL OUT COUPON BELOW

1975 Catalog Mall to Radio Shack, P. O. Box 1052, Ft. Worth, Texas 76101. (Please print.) 431

Name \_\_\_\_\_ Apt. No. \_\_\_\_\_

Street \_\_\_\_\_


City \_\_\_\_\_

State \_\_\_\_\_ ZIP \_\_\_\_\_

# RCA's Free & Easy
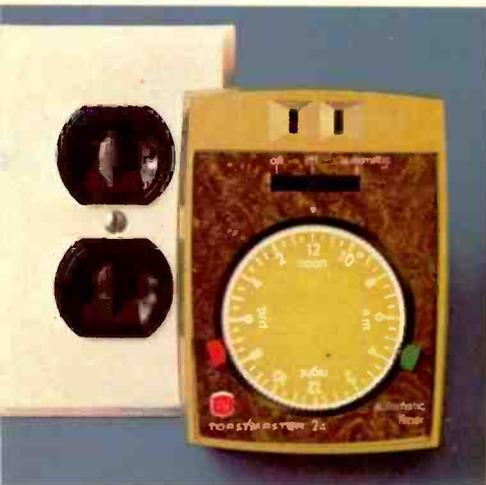
## Dealer Awards

**RCA** Electronic Components Harrison, New Jersey 07029



### Toastmaster Plug-in Automatic Timer for Lamps and Appliances

Cordless timer plugs directly into outlet. Time cycle extends from 90 minutes to 22½ hours. Turns lamps and appliances on or off any time of day or night and repeats the operation every 24 hours without resetting.

**FE-630**



### Polaroid Colorpack 5 Land Camera and Kit. Enjoy Instant Photography in Color and Black and White

• Big 3¼ x 4¼ color pictures in one minute • Black and white pictures in seconds • 3-element lens and unique face-in-the-square viewfinder

**FE-687 Value: \$44.95**



### Canon Palmtronic LE-83 Calculator

Slender enough to put in your pocket, the Canon Palmtronic LE-83 combines convenience with precision. • Adds, subtracts, multiplies, divides, performs mixed calculations, calculations with a constant and n-th power calculations. • Comes with an AC adapter or can be used with 4 penlight batteries. • Smooth key touch, easy to read LED indication panel.


**FE-LE-83 Value: \$44.95**



### Schick Styling Driers, Man's & Lady's Models

For Women: Quick drying with more natural styling  
For Men: Dries fast while it styles and grooms  
• 2 Speeds, 2 Heats • Dry setting — high airflow and high heat • Style setting — low airflow and low heat • Professional styling brush and styling comb • Air concentrator nozzle

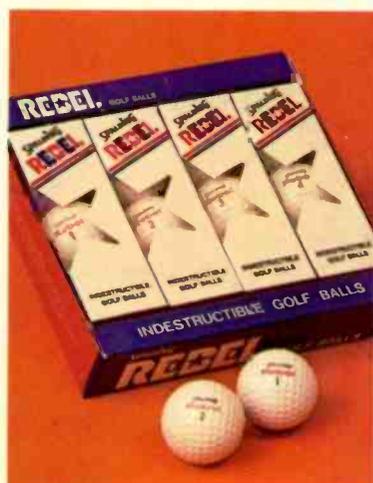
**Man's FE-336 Lady's FE-338 Value: \$15.98**



### Spalding "Rebel" Golf Balls (One Dozen)

Spalding is the premier distance ball with indestructible Surlyn cover. Two-piece construction gives you extra yards for the power you pack into your drive.

**FE-11117 Value: \$14.90**

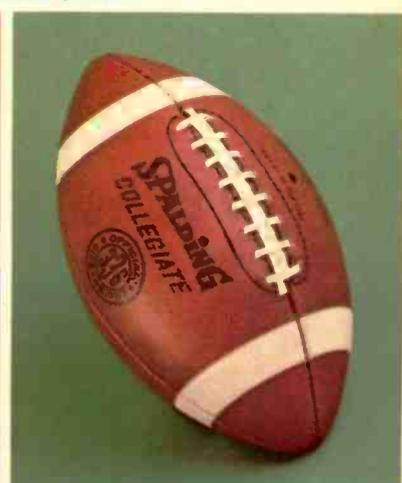

### Spalding "Collegiate" Football

The best value you'll find in a full-grain leather football. Tough butyl rubber bladder. Triple fabric lining with lockstitch construction.

**FE-61448 Value: \$17.00**

When you buy RCA tubes from your participating RCA tube distributor, he delivers the goods the easy way. No muss, no fuss, no constant cutting of carton flaps, no torn cartons on your shelf or in your caddy. Just give your tube order to your RCA distributor and get your premium the free and easy way. The bigger your tube order, the more valuable your gift. So visit him soon and select your Free and Easy RCA award with your purchase of RCA tubes. *(The values are really extra special.)*



**No Muss • No Fuss • No Torn Tube Cartons.**  
**Visit Your Participating RCA Tube Distributor.**  
**Place Your RCA Tube Order**  
**and Select Your "Free and Easy" RCA Award!**

**Remember, the Award Values Are Extra Special!**



**Omaha Steaks** Ten RCA "Steak-out '74" certificates can be redeemed for one package of tender, succulent Omaha steaks as follows:  
 6 (11 oz.) Boneless Strip Sirloins 1 1/8" thick or  
 8 ( 6 oz.) Filet Mignons 1 1/4" thick or  
 8 ( 8 oz.) Top Sirloins 1 1/8" thick or  
 6 ( 8 oz.) Filets of Prime Rib 1" thick  
 Choice cuts, generous portions and outstanding flavor!  
**1A2116**



**BULOVA... The watch you wear with pride. Bulova... synonymous with quality, craftsmanship, precision and style.**

**Oceanographer** — Highly contemporary 17 jewel, automatic instant change day/date calendar; depth tested to 333 feet. **FE-12604 Value: \$110**  
**La Petite** — Stunning feminine timepiece with 23 jewels, 4 diamonds, 10K rolled gold plate case. Adjustable mesh bracelet. **FE-55775 Value: \$110**



**Sea King** — Stalwart Bulova Sea King, 17 jewel precision timepiece, water-resistant with luminous dial. **FE-12280 Value: \$65**  
**Concerto** — Prettily sculptured model with 17 jewels, 10K rolled gold plate, stainless steel back and silver dial. **FE-63628 Value: \$65**




**Compass Binoculars**

Perfect for use at the track, at the stadium, in the woods. Field of view is a large 367 Feet at 1000 yards. Hard-coated optics. Complete with case and strap.  
**FE-3022 Value: \$44.95**



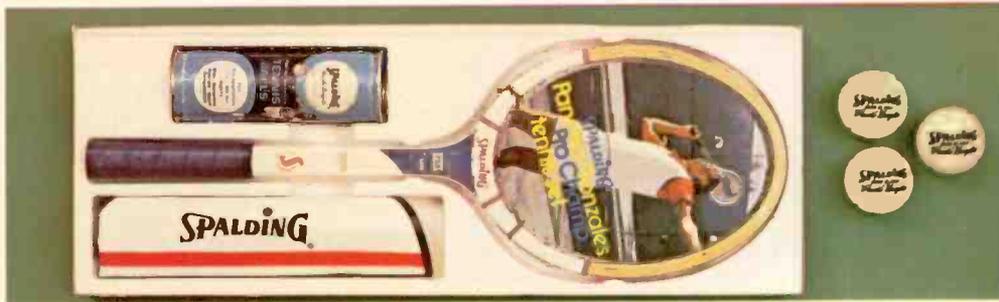**Shakespeare Deluxe Spinning Combo Balanced Tackle Set**

Shakespeare #2210 Marina Green spinning reel, matching Shakespeare SP-160 6' 6" Wonderod, 200 yards 6-pound monofilament, box of stainless steel hooks and spinning lure. For fresh and light salt-water fishing. **FE-S460 Value: \$42.00**



**Spalding Pancho Gonzales "Pro Champ" Tennis Set**

Pancho Gonzales "Pro Champ" racket, water-proof racket cover, plus three Pancho Gonzales tennis balls.  
**FE-531063 Value: \$18.65**

a number of TV's, a quantity of audio equipment and a tape recorder. The burglars apparently spotted the markings as they were loading the stuff, for the owners found their property stacked in the driveway between the two houses when they came home.


Such dramatic instances are not needed to demonstrate the method's effectiveness; police statistics show significant drops in burglaries in neighborhoods where they have promoted identification programs.

And, of course, when using the project to help him in his business, the technician can take time out and mark his own equipment! He has plenty of expensive test equipment, plus ordinary business machines. And the stickers may prompt customers to ask questions! ●
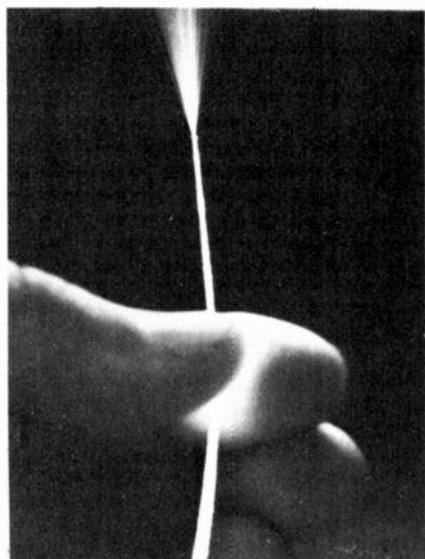
### "Most transparent glass fibers" set new 1.2 dB/km loss record

The world's most transparent glass fibers have been made by scientists of the Bell Laboratories. Their achievement represents an important step toward practical long-distance communications circuits using light, where the fantastic bandwidth, independence of losses from frequency, light weight and immunity from electrical interference of glass light conductors offer many advantages.

The new fibers are made by a vapor-deposition method. The materials that compose the fiber are heated to the vapor



LIGHT SPOUTING FROM THIS FIBER has traveled a half mile inside the glass tube.

form and deposited on the inside of a quartz tube. The tube is then collapsed by heating and the glass drawn into a thin fiber. A ten-inch section of collapsed tube

may be drawn into a tube a mile long.

The new fibers are also made to combat dispersion, or smearing of light pulses in transmission. Some of the light in a pulse travels straight down the center of the fiber; some of it may follow a zig-zag path, with repeated reflections from the boundaries, thus traveling farther and reaching the end of the fiber later than the light that went straight down the center. This makes the pulses longer and gives them smeary trailing edges. If pulses are closely spaced and the transmission distance great enough, pulses can run into each other and make the signals unintelligible.

This can be remedied by making the center of the fiber out of a glass with a lower speed of light conduction and the outer portion of a glass that lets the light travel faster. Thus the light that goes farthest goes fastest and tends to arrive at the same time as light that went straight down center.

The vapor-deposition technique makes it easy to construct such fibers. In Bell's best fiber, borosilicate was first evaporated against the inside of the quartz tube, and the center core was formed of fused silica. It was fiber so made that showed, under certain conditions of excitation at a wavelength of 1.06 millionths of a meter, a loss as low as 1.2 dB. ●

### New communication system "works under water"

A self-contained underwater communications system enables sports divers, underwater photographers, and diving instructors and students to communicate with ease under water. The device uses straight audio frequency. A transmitter only is needed, the listener picking up the audio-frequency pressure waves by direct conduction through the skull, aided slightly by the ears.

The D.U.C.S. (Divers Underwater Communication System) as it is called by its manufacturer, Micro-Tech Electronics, of St. Louis, consists of a throat microphone feeding into a speech-processing network that eliminates the distorted low-frequency sound waves from the larynx, improving the intelligibility. This inputs to an audio amplifier, also tailored for greater speech intelligibility and elimination of breathing and other extraneous noises. The final unit is a transducer which converts the electric signals into pressure waves. No volume control is needed, but a feedback control — which is adjusted just below the level of feedback squeal — is provided.

The D.U.C.S. is designed to work well with the almost universal demand regulator and half-face mask. A certain amount of skill must be developed, since

lip movement is hampered by the demand regulator and mouthpiece. Once this difficulty is mastered, intelligibility is greatly enhanced. Special microphones are available for use with the less common full-face mask.

Range of the D.U.C.S. is up to 165 feet, depending on water conditions and ambient noise. The equipment can be used down to 300 feet. Output power is 3.5 watts. ●



UNDERWATER COMMUNICATION IS EASY with the units shown strapped to the air tanks. Voice communication is feasible up to 165 feet.

### Radio may affect human health at lower levels than thought

Radio waves may affect the nervous system and behavior, and normal development and growth processes "at lower levels than anticipated in the past," the government Office of Telecommunications Policy stated in a report to Congress. The Office warns, however, that the tentative findings are based on a small number of experiments on a limited number of subjects, and that "casual relationships between the electromagnetic fields and observations are not yet clearly established."

High-intensity radio-frequency radiations are known to cause adverse biological effects by generating heat in the tissues. The thermal effects are well understood, and it has been fairly well established that power densities of less than 10 mW per cm<sup>2</sup> are harmless to human beings, as far as their heating effects are concerned.

Less is known of other effects of rf radiation, though they have been suspected to exist for some time, especially in the microwaves. (In the 1940's, de Forest suggested a study of "the non-thermal effects of higher radio frequencies.") Some effects of radio waves are rather sharply

(continued on page 22)

# In basic electronics or the newest in solid state...Sams has the latest.

Six of the books described below are brand new '74 releases. One is a new 2nd edition, and one is a new 3rd edition. Here is a wealth of new information and help for anyone interested in electronics. Look them over. No doubt several will be of real value to you.

## SOLID-STATE IGNITION SYSTEMS

by R. F. Graf and G. J. Whalen

Anyone who works with gasoline engines will find this new book an invaluable aid to understanding the now widely accepted solid-state ignition systems. It covers the operation of the semiconductor devices used in the new systems; the various systems now in use as original equipment or offered for replacement; and troubleshooting and servicing of the many types now in use. 136 pages, softbound.

No. 21049 \$4.50




## Solid-State Components

## SOLID-STATE COMPONENTS

by Rufus P. Turner

This new book is a handy encyclopedia of the many solid-state components now in use in modern electronics. It provides clear, concise descriptions of solid-state components used in devices ranging from the af transistor to the zener-protected MOSFET, and explains what these components are, what they do, and how they work. 96 pages, softbound.

No. 21099 \$3.95

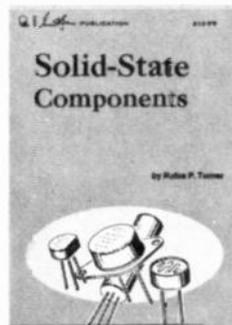


## LINEAR IC Principles, Experiments, and Projects

by Edward M. Noll

The integrated circuit, an essential part in many electronic systems, has paved the way to systems miniaturization and even more complex functions. Understanding of the structure and operation of ICs is essential for today's electronic technician. This new book provides that understanding. 384 pages, softbound.

No. 21019 \$8.95

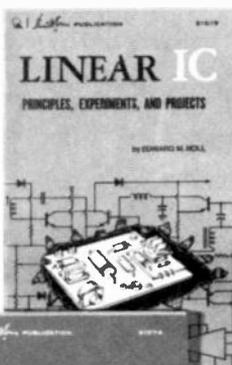

## DIODE APPLICATIONS

by Courtney Hall

Covers typical applications of the versatile diode in electronic circuits, and explains how diodes function in each case. All types of diodes, from the basic diode to zener diodes, LEDs, tunnel diodes, varactor diodes, and semiconductor lasers are explained and discussed. 96 pages, softbound.



No. 21033 \$3.50

## CB RADIO SERVICING GUIDE (3rd Edition)

by Leo G. Sands

A complete and practical guide for servicing all types of CB equipment. Includes tuning, testing and troubleshooting of both tube and transistor equipment, covers FCC regulations, and presents step-by-step analysis of transmitter circuits. 160 pages, softbound.

No. 21074 \$4.95

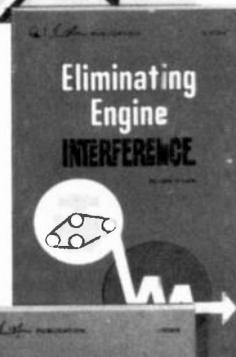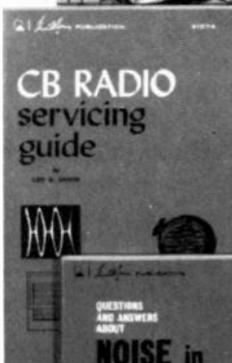

## ELIMINATING ENGINE INTERFERENCE (2nd Edition)

by John D. Lenk

Practical instructions on how to solve a major problem common to all communications equipment. Shows how to install shields and noise-suppression equipment, how to identify and isolate the specific components that create interference and generate noise. 128 pages, softbound.



No. 21004 \$4.50

## QUESTIONS AND ANSWERS ABOUT NOISE IN ELECTRONICS

by Courtney Hall

The simple Q. and A. format of this instructive book provides the reader with a basic understanding of noise characteristics and eliminates the need for performing complex mathematical operations to measure electronic noise. 96 pages, softbound.

No. 21022 \$3.95

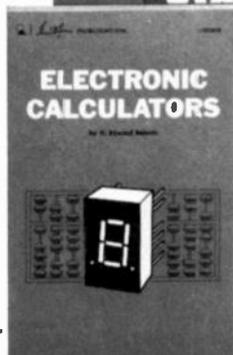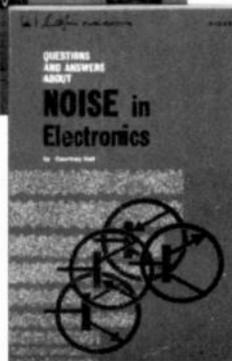

## ELECTRONIC CALCULATORS

by H. Edward Roberts

This new book is the first complete source for information on calculator design, fabrication, and repair. Covering calculator memories, displays, interfacing with hard-copy equipment, and servicing, it is a valuable aid for all who must understand and service the rapidly growing field of miniature electronic calculators. 176 pages, softbound.

No. 21039 \$5.95



Howard W. Sams & Co., Inc.  
4300 West 62nd Street, Indianapolis, Indiana 46206

RE 094

Order from your Electronics Parts Distributor, or mail to Howard W. Sams & Co., Inc.

Send books checked at right. \$\_\_\_\_\_ enclosed. Please include sales tax where applicable. Canadian prices slightly higher.

Send FREE 1974 Sams Catalog 007146.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

- 21049
- 21019
- 21074
- 21022
- 21099
- 21033
- 21004
- 21039

# Sylvania goes

TV reception simulated



# one better.

## We give you two TVs instead of one.



With Sylvania's Master TV Career Program you get not just one but two TV sets to build. Color and Black & White. Both Solid State.

With all Sylvania Career Programs you get our exclusive Autotext method of instruction, a modern, step-by-step approach to learning, which gets you through the basics of electronics quickly and easily.

An optional Cassette System, a technique that adds an extra dimension to learning. It's almost like having an instructor right in your own home. As you play the tapes, he'll guide you through your lessons, explaining as you read, going over schematics and reinforcing everything you learn!

Plus a choice of Programs that can lead to any number of career goals. In TV, communications, automation, digital and solid-state electronics. And in fields you haven't even dreamed of.

Plus specialized advanced training and carefully-engineered Project Kits for that "hands-on" training you need to make it in the world of electronics.

Throughout your training, Sylvania makes that extra effort to go one better

Send the card or mail in coupon today for our FREE Catalog. And go with Sylvania.

**SYLVANIA** Technical Schools  
Home Study Division 758-409-0  
Sylvania Technical Systems, Inc.  
909 Third Avenue  
New York N.Y. 10022

Please send me FREE illustrated career catalog. I understand that I am under no obligation.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_

Veterans: Check here

**GTE SYLVANIA**

# THE PROBLEM SOLVER



## DC300A

This is the totally new commercial super amp that is going to make your sound installations easier and your bank account fatter. It is the *only* dual channel high power low distortion amp specifically designed for portable and house systems, with the features you need.

The DC300A is rated at 150 watts per channel continuous into 8 ohms, 300 w/ch continuous into 4 ohms (both channels driven) or 500 watts continuous into 2.5 ohms (single channel driven). Each channel has *eight* 150-watt output transistors! For 600 watts continuous 8-ohm output, it converts easily to a mono amp, so you can drive a 70-volt line directly without a matching transformer.

With separate level controls and circuitry for each channel, the DC300A is almost *two* amps in *one*. Great for bi-amping or for driving two separate systems.

The exclusive new DC300A output protection circuitry practically eliminates servicing. Even better, it can drive *any* speaker load, resistive or even totally reactive, with *no* protection spikes, thumps or flyback pulses.

A fantastic new IC front end sets new world's records for low distortion and noise. Stringent factory testing brings you one step closer to install-and-forget field dependability. The price is under \$700, and as two amps in one, it will probably give you a surprising cost-break on your next multiple amp system.

To discuss your special application or request detailed technical data, phone (219) 294-5571 or write CROWN, Box 1000, Elkhart, Ind. 46514.



# CROWN

MADE ONLY IN AMERICA

# new & timely (continued from page 16)

tuned: ants align their antennas parallel to an electromagnetic field at 9 MHz; emissions at 29 MHz have been used to kill bugs in bread, and radiations at 388 MHz have killed monkeys. On the other hand, radiation at 21 MHz increases the germination of gladiolus bulbs. These phenomena cover wide frequency bands.


### EASAC elects officers

The Electronic & Appliance Service Associations Council of the State of New York elected Henry Wawryck, of Henry's Radio & TV, Hicksville, president of the Council for the 1974 season.

Thomas Delaney, Elgot Service, Long Island City, was elected executive vice president, Hy Latman, Flatbush Park Washer Service, vice president, appliances, and Warren Baker, Baker Electronics, Albany, vice president, electronics. The recording secretary is Phillip Holt, Holt & McLamb TV Service, Bayshore, and the corresponding secretary John Organist, Ganmar Electronic Co., Glen Cove. Hy Sheffron, Factory Servicenter, Brooklyn, is treasurer and Robert Plunz, Bob's Radio and TV Service, Scotia, Sergeant-at-Arms.

The officers are also members of the board of directors. They have selected

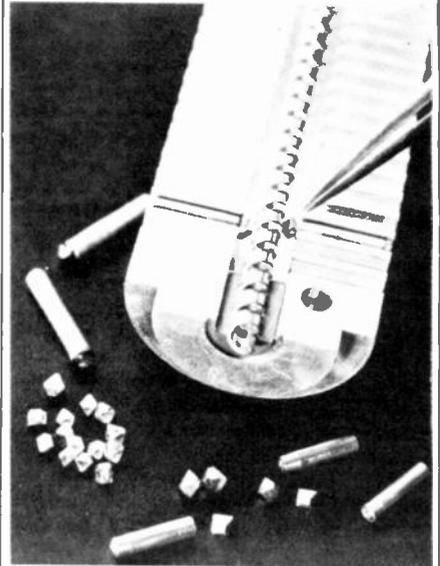Warren Baker as Chairman of the Board and Robert Plunz as secretary. **R-E**



**AUTHENTIC DIAMONDS SEPARATE** the tiny helix rings from the outer shell of this traveling-wave microwave tube, made at the Waltham, MA, plant of the Raytheon Co. Total weight of the diamonds, used because they are excellent heat conductors as well as electrical insulators, is about four carats per tube.

**Radio-Electronics** is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, N.Y. 10003 (212) 777-6400  
President: M. Harvey Gernsback  
Secretary: Bertina Baer

### ADVERTISING SALES

#### EAST

Stanley Levitan, Eastern Sales Mgr.  
Radio-Electronics  
200 Park Ave. South  
New York, N.Y. 10003  
(212) 777-6400

#### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
The Ralph Bergen Co.  
6319 N. Central Ave.  
Chicago, Ill. 60646  
(312) 792-3646

#### PACIFIC COAST/Mountain States

Jay Eisenberg  
J.E. Publishers Representative Co.,  
8560 Sunset Blvd.,  
Suite 601,  
Los Angeles, Calif. 90069  
(213) 659-3810  
420 Market St.,  
San Francisco, Calif. 94111  
(415) 981-4527

### MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print)

address

city state zip code

Mail to: Radio-Electronics  
SUBSCRIPTION DEPT., BOULDER, COLO.  
80302

# MARK TEN B, THE GAS SAVING, PLUG SAVING, TUNE-UP SAVING, ELECTRONIC IGNITION FROM DELTA. NOW AS LOW AS \$49.95.



Years of testing and use by race car drivers in all categories have proven Delta's Mark Ten B the most advanced ignition system on the market today.

Prove it to yourself. Give your car vroom! With a Mark Ten B Capacitive Discharge Ignition System under the hood of your car great things will happen...like reducing costly tune-ups by as much as 75%. Further, you get better all-weather starts, quicker acceleration and better mileage.

Many operational problems caused by emission control devices, poor manifolding or improper fuel mixtures disappear. Delta's Mark Ten B even improves the performance of brand-new factory installed electronic ignitions (Chrysler and Ford). Factory systems merely eliminate points and condenser, but the Delta Mark Ten B combines the advantages of capacitive discharge with solid state

electronics to give real performance and increased energy.

Are you a do-it-yourselfer?

Build your own Mark Ten B...it's available in low-cost

kit form. Or, if you prefer, get the complete ready-to-install unit. Either way, you can install it

yourself in minutes with no rewiring, even over Chrysler and Ford systems.

Mail the coupon today and discover how to enjoy happy motoring with Delta's Mark Ten B. The do-it-yourselfer's dream that really pays off.

**DELTA PRODUCTS, INC.**  
P.O. Box 1147, Dept. IRE Grand Junction, Colo. 81531  
303-242-3000

Please send me free literature.

Enclosed is \$ \_\_\_\_\_  Ship ppd.  Ship C.O.D. Please send: \_\_\_\_\_ Mark Ten B assembled @ \$64.95 ppd. \_\_\_\_\_ Mark Ten B Kit @ \$49.95 ppd. (12 volt negative ground only) \_\_\_\_\_ Standard Mark Ten assembled, @ \$49.95 ppd. \_\_\_\_\_ 6 Volt: Neg. Ground Only \_\_\_\_\_ 12 Volt Specify \_\_\_\_\_ Pos. Ground \_\_\_\_\_ Neg. Ground \_\_\_\_\_ Standard Mark Ten Deltakit® @ \$34.95 ppd. (12 Volt Positive or Negative Ground Only)

Car Year \_\_\_\_\_ Make \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_ Zip \_\_\_\_\_



been an issue from which I did not profit in some way.

JAMES D. TUCKER  
Knob Noster, Mo.


### MINICOMPUTER PC BOARD PRICES

Somehow, the prices listed for the PC boards for the Minicomputer in the July issue were transposed. The prices are right but were not matched to the proper items. The correct pricing should be:

Input multiplexer board	.....\$ 7.50
Memory board	.....10.50
CPU board	.....9.50
Output ports board	.....8.45
Address latch board	.....8.45
LED register display board	.....8.50
Complete set of boards (one of each)	.....47.50

LARRY STECKLER  
Editor


### TV TYPEWRITER COMMENTS

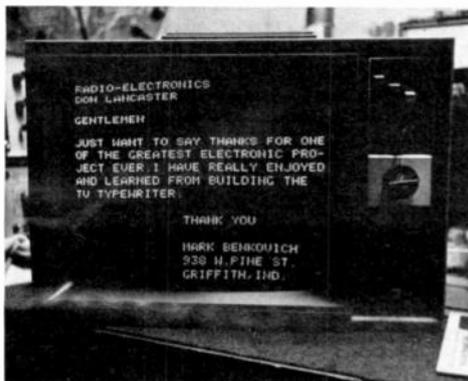

**"RAAACK"**  
**"HACCKK"**  
**"AHHEM"**  
**"COUGH"**

**"I HEAR  
YOU'RE STILL  
SMOKING"**

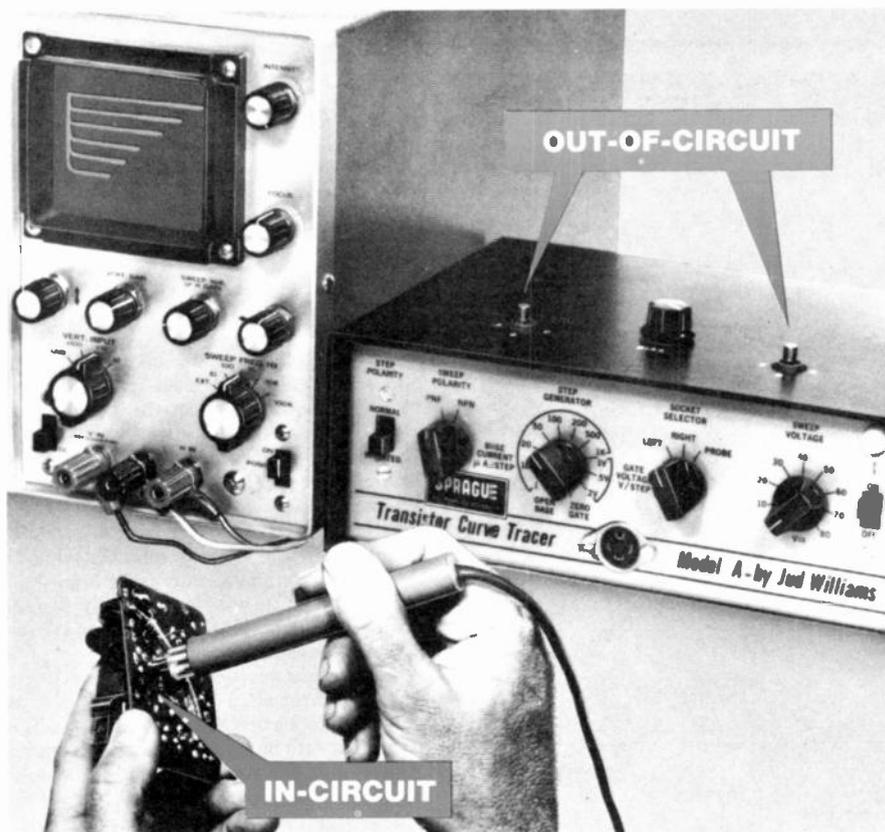**AMERICAN CANCER SOCIETY**  
THIS SPACE CONTRIBUTED BY THE PUBLISHER



## The fastest, easiest, most-reliable, least-expensive way to test transistors

### Sprague's Model A Transistor Curve Tracer by Jud Williams Incorporates Dynamic Signature Pattern™ Servicing Technique

**Eliminate transistor damage.** Did you ever unsolder a transistor to test it, find it defective, then wonder if it was ruined in removal? Or, if the device tested OK, how about the ticklish job of resoldering without damage to either transistor or board? The solution to such problems is in-circuit testing with the "Signature Pattern" technique.

**What are Signature Patterns?** They are scope readouts of the dynamic impedance of in-circuit transistors. With this unique test method, the transistor under test is actually turned on, not merely made to oscillate, as with conventional techniques. The "Signature Pattern" method of trouble-shooting has these definite advantages: (1) Quick, decisive, "good-or-bad" tests of suspect transistors; (2) Discovery of defective components within transistor circuits even when transistors are good; (3) Elimination of damage to transistors and other components; (4) Safe testing with system power removed.

**Quick, accurate tests.** By observing the family of curves, you can determine at a glance such parameters as gain, linearity, saturation, avalanche point, and leak-

age. No zeroing or balancing is necessary. The Model A also performs the all-important breakdown voltage test. It will identify a transistor type as either silicon or germanium. In addition, it will analyze an FET as either junction-type or insulated gate, as well as determine the pinch-off voltage.

**Service modules profitably.** With more and more set-makers switching to modular circuitry, it becomes economically difficult for service shops to stock a variety of plug-in panels in quantity . . . not to mention excessive costs to your customers when panel replacements are made. Also, you waste valuable time processing paper work and preparing modules for shipment to the factory for repair or credit. The practical solution is to quickly and economically repair defective modules in your own shop with the "Signature Pattern" test technique.

**Low-cost testing.** When the Sprague Model A Curve Tracer is connected to any general-purpose scope, you have the most complete semiconductor testing facility possible at a budget price . . . only \$149.50.

Get the Sprague Model A Transistor Curve Tracer from your Sprague distributor now. Or, ask him for Brochure M-957. If his supply of brochures is depleted, write to Sprague Products Co., 81 Marshall St., North Adams, Mass. 01247.

Circle 10 on reader service card

**SPRAGUE**  
THE MARK OF RELIABILITY

65-3128

# equipment report

## Winegard Cablemate Model CTS-1



Circle 97 on reader service card

MOST CABLE TV (CATV) SYSTEMS OFFER a greater variety of programs than is generally available to the viewer with a single fixed TV antenna. Too, signal strength is greater and more constant than with the usual unamplified antenna. Thus, when CATV is available, it offers the viewer a chance for improved reception and greater enjoyment from his TV set.

Often when the home owner subscribes to CATV service, he may find that he no longer gets one or more stations from an adjacent service area. This doesn't matter when the more distant stations carry network programs duplicated on local channels. But, he is out of luck when the distant station originates educational programs and local athletic events that he wants to view. Also, with the rapid expansion of uhf TV into the suburbs, the average CATV system (12 channels) does not have the capacity to provide the viewer with all the uhf channels available from his vhf/uhf antenna on the roof. Therefore, if the viewer wants access to all available TV channels, he must use a separate antenna for those stations not sent over the cable.

Uncoupling the cable and its balun from the TV set's antenna terminals and connecting the antenna lead-in is an inconvenience that soon discourages the viewer from watching programs not on the cable. The job of disconnecting and connecting the cable and TV lead-in—a real chore if the set is a console or a large color model—can now be easily overcome by installing Winegard's model CTS-1 Cablemate TV Signal Selector.

This handy gadget is a switch that allows the cable TV subscriber to select either CATV or his own antenna with the flick of a switch. It mounts on the back of the TV set where its selector switch lever is within easy reach.

There are three type "F" coaxial cable connectors and two parallel-screw non-strip twin-lead connectors on the switch box. One coax connector is the input for the CATV cable, one is for a 75-ohm antenna lead-in (if needed) and the third is for a TV set or multi-set coupler for 75-ohm lines. One of the twin-lead terminal strips is for connecting a TV set or coupler designed for 300-ohm lines and the other is the input from a 300-ohm antenna lead-in. Two slide switches match the Cablemate to 75- and 300-ohm impedances.

For several years I have used a roof-top vhf/uhf antenna with a rotator and an amplifier-splitter to distribute the signals to three TV sets in my home on Long Island. The rotator control box sits atop the color set in the living room. Invariably, when the antenna is pointed west so my wife can watch a network program from Manhattan, I want to watch wrestling or roller derby on a Connecticut station to the north and my teen-age son and his gang want to watch local high-school news or events telecast on a uhf channel to the east of us. We needed three separate antennas with rotators—a very impractical arrangement, particularly when all available roof space was needed for my quad and Yagi hamband antennas. My solution was to subscribe to CATV service with three taps.

This was satisfactory for a while but we soon missed programs that we had formerly watched on vhf and uhf channels in outlying areas. I resisted pleas from my wife and son to reconnect the old MATV system because of the inconvenience of disconnecting and properly terminating the unused signal cable each time we switched from one system to the other.

When Winegard announced the Cablemate, I thought that they had something. After using one for several weeks, I know that they have really come up with a useful TV accessory. I can now connect the main TV set to the antenna or CATV cable with the flick of a finger. As soon as I can get two more Cablemates, we'll have the same convenience on the den and bedroom.

### What's inside

The diagram is a simplified circuit of the Cablemate CTS-1. A dpdt rotary switch with a long lever-type handle selects the signal source to be connected to the set and provides a 75-ohm termination for the cable and TV lead-in when not in use. Two broad-band balun transformers with toroidal ferrite cores can be switched into the circuit to match 75-ohm unbalanced coax to 300-ohm balanced twin-lead lines.

### Enter Casper

As soon as the MATV system was returned to service, we began noticing odd types of interference on most channels.

Sometimes, there were faint floating venetian-blind type lines resembling co-channel interference. More often, there was a real crazy ghost (we named him Casper) that was displaced about half the screen width to the left or right of the main image. The weird thing about Casper is that he wouldn't stay put. When a camera switches or moves in for a close-up, Casper races smoothly from one side of the screen to the other—passing either in front of, or behind the main image. And sometimes, Casper appeared as a *negative* ghost.

### The exorcist

This problem was so unusual and intriguing that I had to lay this ghost to rest. It was finally traced to radiation from *both* the MATV and CATV cables inside the house. I tried separating the coax feeder cables and even rearranged them so they were at right angles as much as possible without any noticeable reduction in Casper's activities. Attenuator pads at the input and output of the MATV amplifier/splitter didn't help either. I haven't completely exorcised Casper but he is not as noticeable now that I've moved the amplifier/splitter and mounted it on a convenient cold-water pipe for good ground and replaced the three branch lines with *shielded* 300-ohm twin lead.

The CTS-1 Cablemate is a TV accessory that the cable TV subscriber will really appreciate. The choice of 75- and 300-ohm antenna input and output connections makes the device easy to attach to any existing antenna or MATV system. Installation takes only a few minutes. The model CTS-1 costs \$14.95. If yours is a multi-set family of avid TV watchers, be prepared to add one Cablemate to each set—you'll need them. I can hardly wait for my Winegard dealer to get them in so I can get two for the bedroom and den. **R-E**

## Proto Board by Continental Specialties

FOR THOSE OF US PROFESSIONAL AND AMATEUR circuit designers who have spent many exhausting hours wiring and rewiring complex breadboards, and have sometimes succumbed to the relative crudeness of our methods, Continental Specialties Proto-Board may well be a panacea.

The Model 103, third in a four model series, is 6" x 9" x 1/8" solderless breadboarding system mounted on a heavy gauge, black anodized aluminum ground plane with rubber feet. It is an assemblage of sockets, bus strips, and 5-way binding post. A double horizontal bus spans its width and four double vertical bus strips run along its length, arranged to distribute a pair of supply leads. An external power supply is connected to

(continued on page 30)

# free



**IT'S THE ONLY NATIONALLY DISTRIBUTED  
FULL-LINE CATALOG WITH A MAJOR  
SHOWING OF THE NEWEST NAME-BRAND  
ELECTRONICS PRODUCTS  
FOR 1975!**

**SEND FOR IT  
TODAY!**

## The "NEW LOOK" 1975 LAFAYETTE RADIO ELECTRONICS CATALOG

If you're interested in electronics you **NEED** this catalog! Completely re-designed for ease-of-than-ever ordering, with the finest and best Lafayette and national-brand products for '75. And you get the same quality and service that has made Lafayette a leader for 55 years. Iron-clad guarantees! Lowest Prices! Professional Service! State-of-the-art Equipment! Pick and choose from over 18,000 quality electronics products! Now, more than ever, we're your "Single-trip" shopping center for everything in electronics.

### SAVE ON EXCLUSIVE LAFAYETTE PRODUCTS PLUS THE BEST MAJOR BRAND NAMES

- Stereo and 4-Channel Music Systems
- Tape Recording Equipment • Car Stereo and Accessories • CB and Ham Gear • Police/Public Service Receivers • Car Stereo and Accessories • Antennas • Cameras • TV • PA and Test Equipment • Music Instruments and Amplifiers • Books • Electronic Calculators • Security Systems • PLUS PARTS, TUBES, BATTERIES, HARDWARE — ALL YOU NEED FOR QUALITY LIVING THROUGH ELECTRONICS

# Lafayette

Listen to us, you can't go wrong.

STORES COAST TO COAST Check Your Yellow Pages or Shop by Mail

**NEW!** Bigger Pages  
**NEW!** More Full Color  
**NEW!** Easier-to-Read Type

**free**  
**MAIL TODAY!**

Lafayette Radio Electronics  
111 Jericho Tpke., Syosset, L.I., N.Y. 11791

17094

Send me your FREE 1975 Catalog.

Send a 1975 Electronics Catalog to my friend.

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Street \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

# EXPERTS AGREE

## The TV of the future is here... in the Heathkit Digital-Design GR-2000 TV



At **ELEMENTARY ELECTRONICS** they said: "The fact is, today's Heathkit GR-2000 is the color TV the rest of the industry will be making tomorrow . . . there is no other TV available at

any price which incorporates what Heath has built into their latest color TV."

The **FAMILY HANDYMAN** reviewer put it this way: "The picture quality of the GR-2000 is flawless, natural tints, excellent definition, and pictures are steady as a rock. It's better than any this writer has ever seen."

**POPULAR SCIENCE** pointed out "more linear IC's, improved vertical sweep, regulators that prevent power supply shorts, and an industry first: the permanently tuned I.F. filter."

The **RADIO-ELECTRONICS** editors said the Heathkit Digital TV has "features that are not to be found in any other production color TV being sold in the U.S.:

*"On-screen electronic digital channel readout . . . numbers appear each time you switch channels or touch the RECALL button . . . On-screen electronic digital clock . . . an optional low cost feature . . . will display in 12- or 24-hour format . . . Silent all-electronic tuning. It's done with uhf and vhf varactor diode tuners . . . Touch-to-tune re-programmable, digital channel selection . . . up to 16 channels, uhf or vhf . . . in whatever order you wish . . . there's no need to ever tune to an unused channel. LC IF amplifier with fixed ten-section LC IF bandpass filter in the IF strip . . . eliminates the need for critically adjust-*

ed traps for eliminating adjacent-channel and in-channel carrier beats. No IF alignment is needed ever. *Touch volume control . . . when the remote control is used . . . touch switches raise or lower the volume in small steps."*

**POPULAR ELECTRONICS** took a look at the 25-in. (diagonal) picture and said it "can only be described as superb. The Black (Negative) Matrix CRT, the tuner and IF strip, and the video amplifier provide a picture equal to that of many studio monitors . . ."

Furthermore, the Heathkit GR-2000 is an easier kit-form TV to build. **POPULAR ELECTRONICS** pointed out that "Each semiconductor has its own socket and there are 12 factory-fabricated interconnecting cables . . . The complete color adjustments can be performed in less than an hour."


To sum up, **POPULAR ELECTRONICS** concluded its study by stating, "In our view, the color TV of the future is here — and Heath's GR-2000 is it!"

Why not see what the experts have seen? The Heathkit Digital Design Color TV — without question the most remarkable TV available today.

Mail order price for chassis and tube, \$659.95. Remote Control \$89.95 mail order. Clock, \$29.95 mail order. Cabinets start at \$139.95. (Retail prices slightly higher).


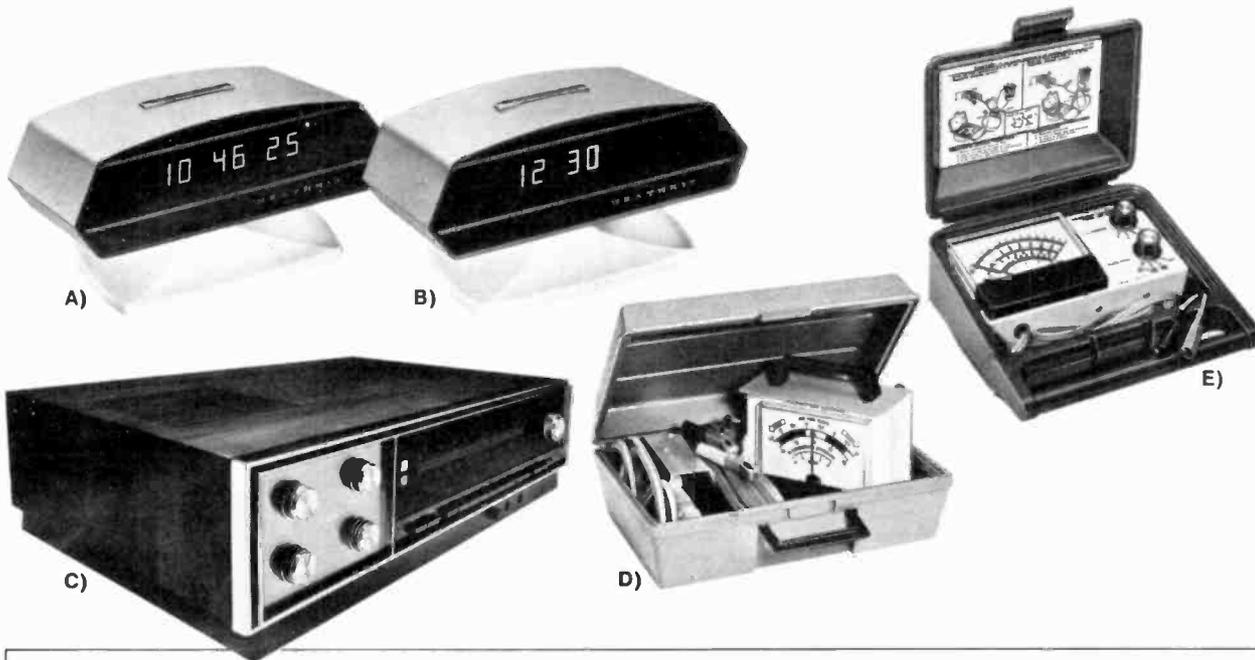
# TOMORROW'S PRODUCTS are in kit-form today- with Heathkit electronics



**(A) New Heathkit Digital Electronic Alarm Clock.** Like no other clock you've ever owned... with features as new as tomorrow! Wakes you with an electronic "beep" and shuts off at a touch — no fumbling for knobs or switches. And if the power goes off, you still get to work on time — the clock has its own emergency battery supply. Other features are a 24-hour alarm cycle with AM indicator light to aid in setting; 7-minute repeatable snooze cycle; 12 or 24-hour time format; automatic brightness control. Kit GC-1092A, 79.95\*. Shipping weight, 5 lbs.

**(B) New Heathkit Digital Electronic Calendar/Clock.** In this unique timepiece, we swapped the alarm feature for the date — and held the same low kit price featured in its alarm clock twin. Reads out the time in hours, minutes & seconds, with big orange digits. Plus, it gives you the month and day, either automatically for 2 seconds out of every 10, or anytime at the touch of an electronically activated control. It also features 12 or 24-hour time format, automatic brightness control, and built-in fail-safe reserve battery supply. Kit GC-1092D, 79.95\*. Shipping weight, 5 lbs.

**(C) New Heathkit AR-1500A, 180-Watt AM/FM Stereo Receiver.** Sequel to the famed "AR-1500" — now with these important new performance & kit-building improvements: a new Phase Lock Loop (PLL) multiplex demodulator with only one simple adjustment — gives maximum separation, drift-free performance, long-term stability; improved AGC circuit for better AM performance; improved output protection for today's wider range of speaker impedances; separate check-out meter & factory-installed cable connectors for even easier kit assembly. Precedent-setting specs are retained: 180 watts (1HF) per channel into 8 ohms, both channels driven with less than 0.25% harmonic distortion; 90 dB FM selectivity, 1.8  $\mu$ V sensitivity. Kit AR-1500A, 399.95\* less cabinet. Shipping weight, 53 lbs.

**(D) New Heathkit Exhaust Gas Analyzer.** A timely kit for the week-end mechanic and the professional alike.

Checks exhaust gas of cars for pollution level and measures air/fuel mixture to help you tune for top economy. Also a great training aid in automotive mechanics classes for demonstrating results of proper anti-pollution system adjustments. Easy to assemble, simple to use. Kit CI-1080, 59.95\*. Shipping weight, 6 lbs.

**(E) New Heathkit Tune-up Meter.** Successor to the popular Heathkit ID-29 — now with new, extended 0-20 VDC range. Checks dwell on 4-cycle, 3,4,6 & 8 cylinder engines with conventional ignition. Two rpm ranges. Reads voltage from 0-20 VDC. Use on 6 or 12V systems, either ground. No batteries required. Kit CM-1073, 29.95\*. Shipping weight, 5 lbs.

#### HEATHKIT ELECTRONIC CENTERS — Units of Schlumberger Products Corporation. Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis; NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho, L.I., Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; WASH.: Seattle; WIS.: Milwaukee.



#### FREE 1975 HEATHKIT CATALOG

350 easy-to-build kits in all price ranges. Send for your free copy today!

Heath Company  
Dept. 20-9  
Benton Harbor, Michigan 49022

- Please send my free 1975 Heathkit Catalog.  
 Enclosed is \$\_\_\_\_\_, plus shipping.  
Please send model(s)\_\_\_\_\_

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

\*Prices & specifications subject to change without notice.  
\*Mail order prices; F.O.B. factory

HEATH


Schlumberger

CL-526
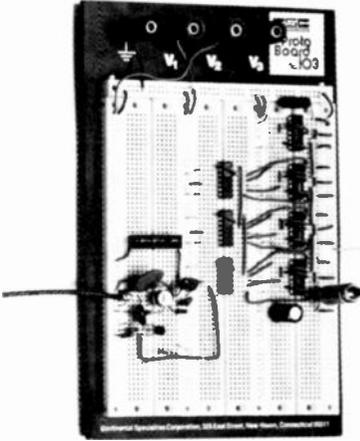
## EQUIPMENT REPORT

(continued from page 26)

two of the binding posts, one of which, the ground post, is electrically connected to the aluminum ground plane. Jumpers connect the binding posts to the horizontal buses which are then jumpered to the vertical bus strips. By using these dual buses, the bread-



Circle 98 reader service card

board power is distributed among three double columns of interconnected terminals, interlocked with the buses. The remaining binding posts, which are insulated from the ground plane, can be used for input and output connections.

The contacts are connected in groups of five with spacing on a 0.1-inch grid meant to accommodate dual-inline integrated circuits spaced across the insulated separating gap between the sides of the dual terminal strips. Twenty-four 14-pin or twenty-one 16-pin IC's will fit on the 103, and since the five terminal clusters radiate laterally from the plugged in IC's, wider devices such as 40-pin DIP's also work. In all there are a total of 2250 terminal contacts in the 103. Transistors, diodes, resistors, capacitors, and other integral lead components are simply plugged into the terminal grid after bending and cutting the leads to reach their proper terminations. Switch and potentiometer like components are managed by soldering No.22 bus wire to their terminals. Interconnections are made with No.22 solid jumper wires, a collection of which rapidly accumulates. Individual terminals can be removed to retrieve jumper ends that break off at or below the terminal surface level.

With this system circuits of moderate complexity can be wired on a single board, and very complex circuits wired by a combination of Proto-Boards. Wiring errors and design changes are easily handled with a minimum of component attrition because there is no repeated soldering of component leads, with the resulting heat and flexure damage. Circuit sections are isolated for debugging by selectively disabling the various supply buses by disconnecting jumpers. The end result is that a circuit design can be carried to completion in a fraction of the time burned up by more traditional methods.

We used the Proto-Board 103 to lash together some fairly complex linear and digital systems using IC's and transistors, and

found it to be really effective. The layouts were unusually neat for designs in such early stages of development. Neatness cuts troubleshooting time and makes it unnecessary to rewire a half-completed nightmare that has become unmanageable and useless. Snipped component leads when inserted in the contacts formed test points to clip test instrumentation onto. We preferred this breadboarding system to the less expensive pre-patterned printed circuit boards, because of its reusability. However, it is desirable to transfer a completed design to one of these printed boards to free the Proto-Board for its next assignment.

The one limitation of the system is working at high frequencies. Relatively long signal paths will generally cause the method to be impractical. There may be exceptions when only small parts of the overall design operates at high frequency, so these components can be confined to a small breadboard area.


The 101-104 Proto-Board series are priced from about \$30 to \$80. The model 103 sells for \$59.95. If your breadboarding requirements are more modest the QT (Quick Test) socket and bus strips are available unmounted in a variety of sizes. Units with the same lengths are agglomerated by their interlocking 'Snap Lock' design. Cylindrical protrusions at each end of the strips slide into matching blind cylindrical slots on the companion part.

R-E

### OCTOBER IS HI-FI MONTH

For all the latest dope on the world of hi-fi make sure you get the October issue of **Radio-Electronics**. It goes on sale September 19.

# Raytheon's Declaration To Independents

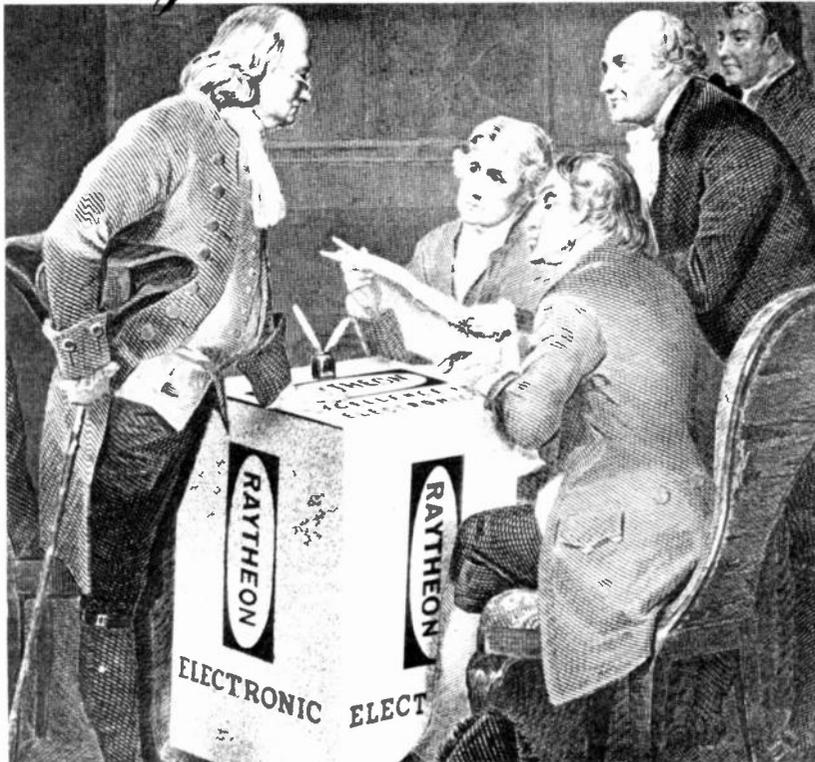

"We're declaring that 1974 will be another banner year for you, the independent service man. And, as the largest independent supplier of replacement tubes, we're also declaring that you will get the same dependable, profitable support that has made you and Raytheon the No. 1 team in the industry for over 40 years."

"Financial independence to the independents."

*Robert P. Knight*  
National Sales Manager

If you're not already on the No. 1 team, call (617) 272-6400 for the name of your nearest Raytheon receiving tube distributor. Or write Raytheon Company, Distributor Products Operation, Dept. KC, Fourth Avenue, Burlington, Mass. 01803.

# A POCKET-SIZE MULTIMETER TO GO.



## MODEL 245, ACTUAL SIZE

This rugged, truly miniature, lab-quality 4½ digit multimeter measures DC volts, AC volts, DC current, AC current and resistance with .005% resolution.

**\$295.00**  
COMPLETE

Data Precision's Model 245 is the smallest, lightest and most accurate 4½ digit multimeter you can buy.

It's a revolutionary instrument with basic accuracy of ±0.05%.

Rechargeable battery and line operated. Model

245 provides fast, reliable and incredibly precise measurements in the lab, on-site or anywhere else an accurate reading is essential.

Small enough to fit in the palm of your hand, big enough to do whatever you want it to do, here's a meter that will meet your most exacting needs.

If all you're looking for is a reliable bench DMM — a low cost instrument that's actually price competitive with analog meters — then Data Precision's Model 134 is probably just what you've been looking for.

Big, bright, easy to read, ½" high, 3-½ digit display.

Model 134 measured DC and AC volts, DC and AC current and resistance through a total of 22 range scales. No interpolations are necessary. And the specs speak for themselves: basic accuracy of ±0.2% reading ±0.2% f.s. with autopolarity, auto-decimal positioning and 100% overrange.

Optional High Voltage Probe available for both 245 and 134.

Data Precision Corporation  
Audubon Road, Wakefield, MA 01880  
Phone (617) 246-1600

**DATA PRECISION**  
...years ahead

## A Full Range 5-Function 3-1/2 Digit Multimeter




**\$189.00**  
with standard probe

**\$199.00**  
with standard probe and special isolation probe

To get your hands on these meters, simply contact the representative nearest you for immediate delivery.

AL (205) 533-5896	MA (617) 273-0198	NY (S) (516) 482-3500
AZ (602) 994-9519	MD (301) 552-2200	OH (N) (216) 725-4560
CA (N) (408) 733-9000	MI (313) 482-1229	OH (S) (513) 885-4471
CA (S) (714) 540-7180	MN (812) 781-1611	OR (503) 238-0001
CO (303) 449-5294	MO (W) (816) 737-0086	TX (N) (214) 234-4137
CT (203) 525-7647	MO (E) (314) 731-2331	TX (S) (713) 461-4487
FL (813) 294-5815	NC (919) 787-5818	UT (801) 268-3181
GA (404) 457-7117	NJ (S) (215) 525-8711	WA (206) 763-2210
HI (808) 262-6286	NJ (N) (201) 663-5660	CAN (W) (416) 787-1208
IL (312) 593-0282	NM (505) 265-6471	CAN (W) (613) 772-5874
IN (317) 293-9827	NY (N) (315) 446-0220	CAN (E) (514) 731-9328

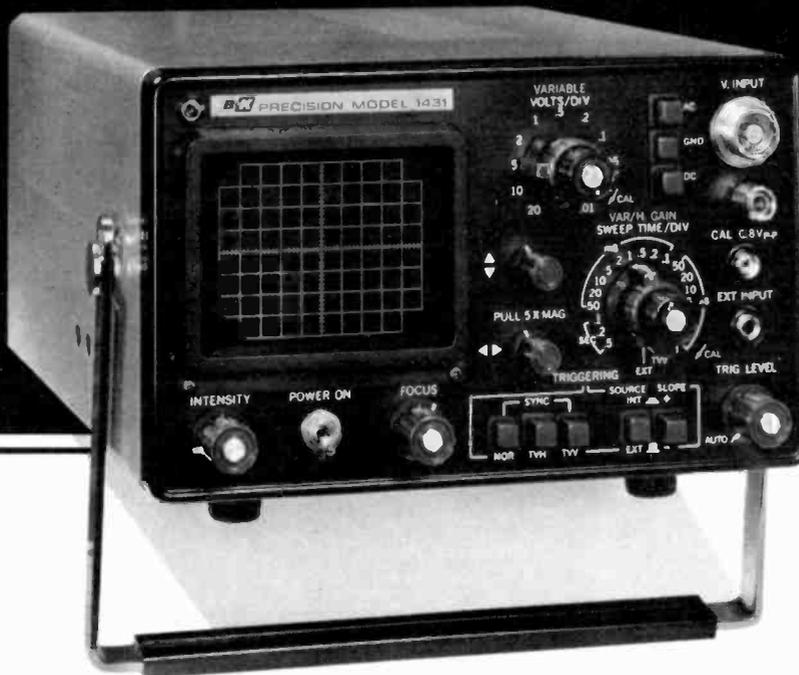**This 10 MHz Triggered Scope  
is 1/3 the size  
of comparably  
performing scopes.**



**MODEL 1431 \$399.00**

It's a lightweight 13 pounds in your hand and a heavyweight performance wideband scope with a 35 nanosecond rise time on your bench or jobsite. Whether you're servicing or designing industrial equipment or TV, there's the right sweep speed and sync for easiest operation. If you know our Model 1460, the leader in wideband 5" CRT scopes, you know our new 3" Model 1431 which gives you the same high performance in one third the size. (Only 4 $\frac{3}{4}$ "Hx7 $\frac{7}{8}$ "Wx12 $\frac{1}{8}$ "L)


Servicing, production, inspection, quality control and lab applications are all easier with this versatile all solid-state instrument. Triggering is accomplished with only 0.5V peak-to-peak. Ten millivolts per division sensitivity, 0.5 usec/cm to 0.5 sec/cm automatic and triggered sweep in 19 calibrated ranges, and external trigger input are just a few of the reasons you'll like it.

If you have been waiting to buy a portable scope until you could get all the features you'll ever need at a price you want to pay, you've been waiting for Model 1431. Contact your distributor or write Dynascan Corporation.



Shown with optional carrying cover and probe pouch.

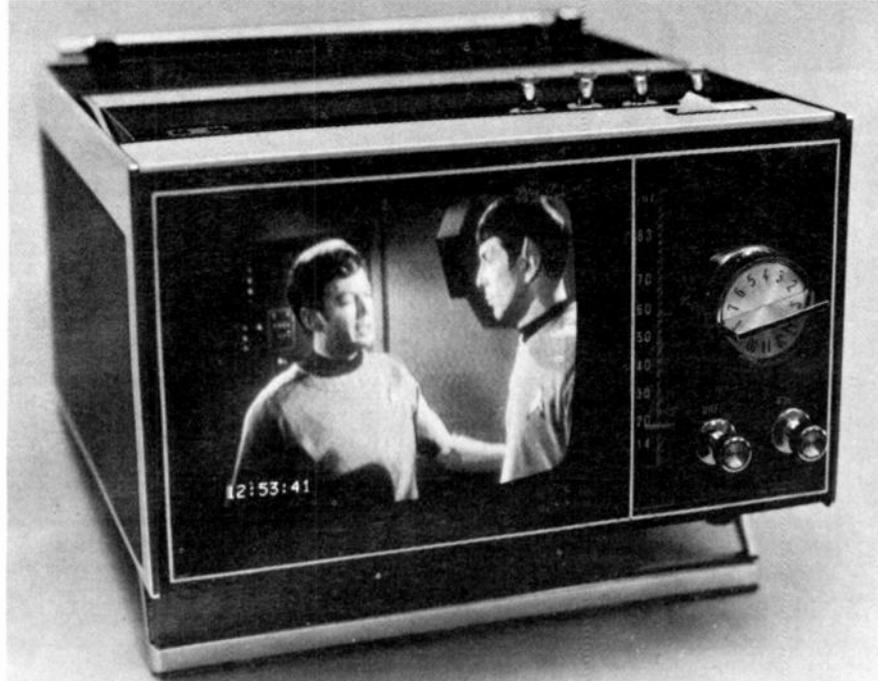**B&K** PRODUCTS OF  
**DYNASCAN**  
1801 W. Belle Plaine Ave.  
Chicago, IL 60613 • (312) 327-7270



Get the exact time on your TV screen without interfering with the picture

## Put the TIME on your TV screen



MANY RADIO-ELECTRONICS READERS HAVE asked for a way to connect their Superclock II (R-E, July and August '72) or other digital clocks to their TV set, so they can display time directly on top of an existing TV program. This eliminates the high cost of the self-decoding LED readouts from your Superclock design and is the ultimate in convenience for the discriminating TV viewer. When and if it is approved, the NBS (National Bureau of Standards) TV timing system is a natural source of self-resetting, always accurate signals for your Superclock, and the Revideo unit is the ideal output display.

You can also use the unit to transmit plant-wide or school-wide time, or to add time to a video recorder, cable TV system, or industrial recorder. While the unit was intended to give you an 08:18:36 style time display of any reasonable size positioned anywhere you want on the TV, it can be made to display any combination of eight letters, numbers, punctuation, or blanks. For instance, you could display the calendar date, the TV channel number, the temperature, the weather "CLOUDY"; "WARMER"; "RAIN"; etc. Or you can use it as a security monitor, a calculator readout, or anywhere else you want to display a changing, limited amount of alphanumeric information on a TV set or oscilloscope. The unit gives you complete control of presence, size, position, and contrast.

The Revideo unit consists of 14 IC's on a  $4\frac{1}{2} \times 6\frac{3}{4}$ -inch PC board and needs 5 volts dc at 200 mA and -12 volts dc at 25 mA. This is picked up from the clock, a lab supply, or from a small custom supply. The cost of the IC's come-to around \$23, buying from the back ads in *Radio-Electronics*, and a complete kit of all other parts is available, as are individual PC boards—see parts list.

The TV Revideo unit will interface with

the "1-2-4-8" counter outputs of any digital clock provided it uses the BCD code.

If you are using a one-chip or multiplexing clock circuit, you have to make sure a BCD output is available and then add suitable simple latches so that all the outputs (1, 2, 4, 8, 10, 20, 40 minutes, and 1, 2, 4, 8, 10, (20?) hours are available all at once in parallel form.

The final outputs must be TTL compatible. Regardless of what type of clock you use, you have to end up with these parallel BCD outputs. Since these rarely already exist as output terminals or pins, you usually add a short piece of multi-conductor flat cable to the respective pins on the counters in the clock.

Before you begin—note two important things: The TV set *must* be modified to bring out horizontal and vertical trigger pulses and a video input. If done properly, this is easy and cheap, and only adds to the value of the TV. In no way will it hurt normal operation. Secondly, if the receiver is a hot-chassis type, you'll have to either use an isolation transformer or else run the entire clock "hot-chassis" and properly safely-isolated as well. A schematic of the TV you're going to use is a must; a good scope will also be essential to modify the TV.

### Understanding TV scanning

A TV set has a raster scan. Once every  $1/60$ th of a second, a spot starts at the upper left hand corner and rapidly scans to the right and slowly downward, generating a series of 262  $1/2$  lines. Video is produced by controlling the brightness of, or *modulating*, the spot. During the next  $1/60$ th of a second, the TV generates another 262  $1/2$  lines, putting these *between* the ones it did on the previous go-around. The two *interlaced*  $1/60$ th second *fields* make up a  $1/30$ th second *frame*, the time needed to display one com-

plete, stationary picture of 525 lines. By presenting 30 stationary frames per second, the pictures appear to move, since the eye cannot respond to each individual frame, but can only average them out for a final result. The fancy interlace scheme is used to reduce the apparent flicker.

The horizontal scan time, or the time to generate one line, is around 62 microseconds, of which 50 microseconds is spent in the actual scan and the rest in returning the *blanked* or turned off beam to the left side of the picture. A horizontal *synchronizing* pulse of some 5 microseconds is centered in the return blanking interval. It is used to lock the TV's horizontal scan to the scan at the TV camera. Obviously, the camera has to be looking at the same place the TV set is at the same time if we don't want a rolling or scrambled picture.

The vertical scan time lasts the entire  $1/60$ th of a second. About 800 microseconds of this time is reserved for retrace. A vertical sync pulse 180 microseconds wide is centered in the blanking interval to lock the TV's vertical scan to that of the camera and the transmitter.

We can't change what the TV scan is doing or where it is at any particular time. This means we can't use stroke or segment style numerals on our time display. We have to use a bunch of dots, getting the dots to crop up at the right place and the right time to present a final numeral or character in a stationary and recognizable place.

We can easily sum an output signal from the Revideo unit right into the TV's video amplifier and present a composite time-on-picture display. The problem is to get the right dots in the right place at the right time. Fortunately, there is a stock MOS computer-on-a-chip that does most of the work for us.

To generate the dots, we have to derive a

horizontal trigger pulse and a vertical trigger pulse from the working TV and use these to synchronize and control the number generator. The vertical pulse is easily obtained from the vertical output stage and is attenuated to logic levels with external resistors and a coupling capacitor. While we could also use the horizontal output signal, this is usually a bit too strong and could detune the TV's flyback transformer. So, we have to find an equivalent positive-going horizontal pulse, such as off the plate or collector of the agc keyer. This signal is also attenuated with external resistors and capacitors to present a logic-level-sized, positive-going output pulse.

Fig. 1 is a block diagram of the TV Revideo unit, while Fig. 2 takes you through the timing sequence of a single field. The Revideo unit has two parts—the *timing* portion and the *signal processing* portion. The signal processing portion picks the right input number and converts it to the proper dot sequence at the proper place in the picture. The timing tells the signal processor when to do what, and locks things into the TV's vertical and horizontal scanning.

### Choosing a character

We could get by with a numeral 3 dots wide by 5 dots high, but it wouldn't be very pretty, and there's no standard IC that will do the job. Instead, we use a computer standard 5-dot-high number or letter that we can get out of a standard ASCII alphanumeric character generator IC. To keep the timing simple and to still allow enough circuit setup time, we use three blank "udots" between each character. We also let the timing run for an eighth line at the bottom, generating all blank undots. This gets us by with a standard divide-by-eight counter.

While a seven-line-high character would do the job, it would be very small. It would also mean that you would have all sorts of interlace problems. So, we go to 14 lines of character height, putting identical information on both fields and solving both problems at once. Now, if you want the same thing to seven pairs of lines on each field, and end up with a 28-line-high character. Thus you have a choice of two possible character heights.

Now, we somehow have to get the right part of each numeral in the right place at the right time. This is what the Revideo unit is all about.

At the beginning of a field, a vertical trigger pulse trips a monostable delay that sets the vertical position of the numeral display. (Step 1, Fig. 2). Since the monostable could end up anywhere on the screen, it tells a *synchronizing* circuit to pick up the *next* eight whole horizontal lines and to allow a video output only during those lines. We use the first seven lines for numeric output; the final line is a blank. If, instead, we are using the double height characters, the *next* sixteen whole horizontal lines are picked, presenting 14 lines of numeral and 2 lines of blanks.

As we adjust the vertical position, the entire display moves up or down the screen to where we want it. Since the line counter is always working on whole horizontal lines, the vertical position control does not affect the side-to-side numeral positions, and the start of each numeral takes place on each field exactly the same distance from the side

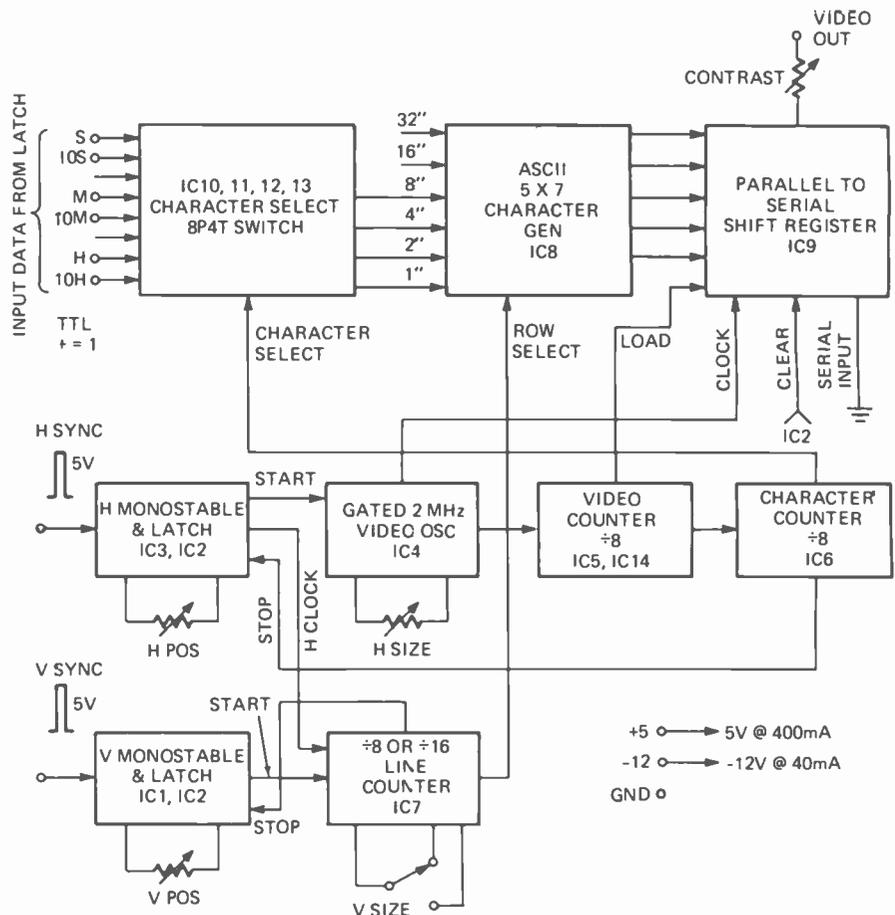


FIG. 1—REVIDEO UNIT for digital clocks, showing input and output connections.

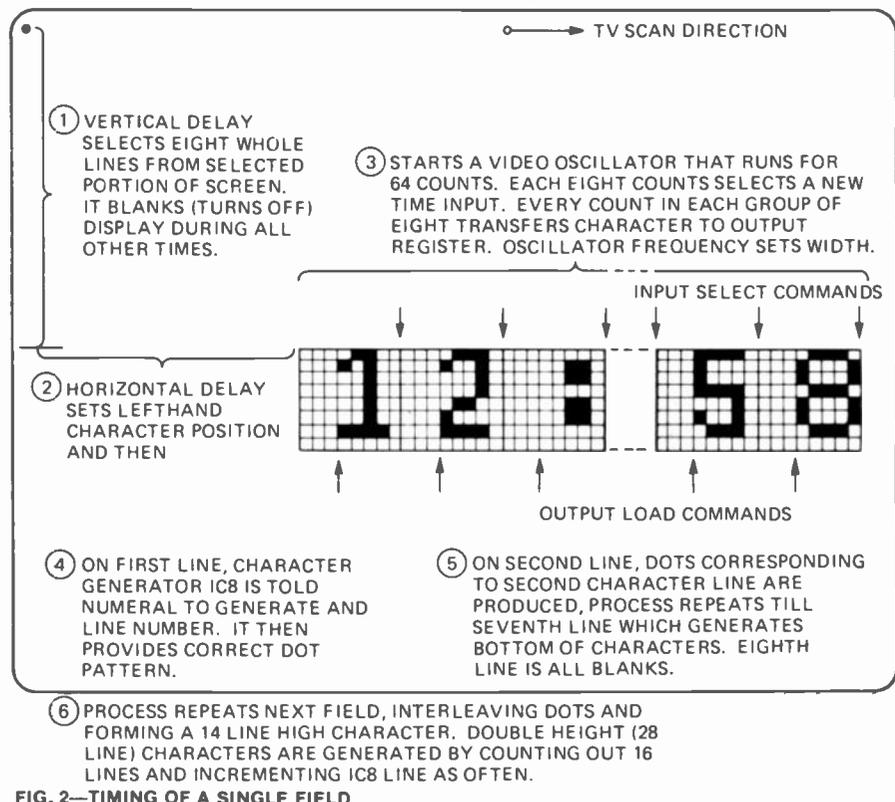


FIG. 2—TIMING OF A SINGLE FIELD

of the screen.

So much for the vertical action. Now (Step 2, Fig. 2) once each horizontal line, we start a delay monostable that tells us how far over to the right the display is going to be—this is our horizontal position control. After the delay is complete, a *video*

*oscillator* is started and counts out exactly 64 counts and then shuts down. The *frequency* of the video oscillator determines the spacing between counts, and thus determines the horizontal size of each numeral. The 64 counts are grouped into eight groups of eight counts each. The first group

is for the ten hours, the second for the hours, the third for a colon, and so on, out to the final eight, which are for the seconds information. The first three counts of each group is for the three blank-between-numeral undots and for settling time. The numeral undots and for settling time. The final five counts of each group are for the five possible numeral dots in each line.

The read-only memory computer character generator is the heart of the circuit. It has three input lines that tell it what line of the numeral it is working on, and six input lines that tell in which of 64 possible letters, numbers punctuation, or blanks to work on. When it is told which line of what character to generate, it outputs a group of five dots or undots that are needed for that part of that character. These five bits of information are then loaded into a shift register and marched out as video, nicely putting the right thing in the right place at the right time.

An eight-position selector switch precedes the character generator and picks the right input for each of the eight slots across the screen. The character generator combines this with an input from the line counter to decide what pattern of dots to produce. A three-count delay is allowed between the time we change the input to the character generator and load its output—this lets things settle down and gives the character generator a chance to operate. Thus, the output of the character generator is loaded into the shift register on the falling edge of the *third* count in each group of eight video oscillator pulses: the input selector is changed on the beginning of the *first* count in each group.

The character generator starts with the tops of all eight numerals on the first horizontal line. On the next line, its line counting input changes, and it puts the second row of dots down for each numeral. It continues this way down to the seventh line when it puts down the bottoms of all the numerals. The next line is a bunch of blanks, and after that, the circuit shuts down till the next field.

### The ASCII character code


The input code for the character generator is shown in Fig. 3. The 64 possible inputs are represented by six lines. For numerals, the bottom four lines are simply the BCD or binary coded decimal representation of the numbers, exactly the same code used in the Superclock and the majority of digital clocks. If we wanted to have all the letters and numbers, we'd need a six-pole input selector. But for just numbers, we can hard-wire 1's (+5 volts) to the two most significant inputs, and we get by with only four poles worth of input selector. A colon is nicely a BCD "ten," or 1010.

If we brought all the leads out, there would be 32 of them on the input. It turns out we can save on input wires by hardwiring what we aren't going to change or don't need. For instance, we can put the colons in permanently in positions three and six. We don't need the 80 hours and 40 hours inputs, so we can make these permanently zero or ground. We don't need the 20 hours input if we are using only a 12-hour display, but we do need it for the 24-hour version. Similarly, we don't need the 80 minutes and 80 seconds inputs; these can also be zeros. This reduces the input leads to 19 or 20. These can be a small flat cable (or two) a foot long

ASCII CHARACTER CODE			
fedcba		fedcba	
000000	@	100000	BLANK
000001	A	100001	!
000010	B	100010	"
000011	C	100011	#
000100	D	100100	\$
000101	E	100101	%
000110	F	100110	&
000111	G	100111	'
001000	H	101000	(
001001	I	101001	)
001010	J	101010	*
001011	K	101011	+
001100	L	101100	COMMA
001101	M	101101	DASH
001110	N	101110	PERIOD
001111	O	101111	/
010000	P	110000	0
010001	Q	110001	1
010010	R	110010	2
010011	S	110011	3
010100	T	110100	4
010101	U	110101	5
010110	V	110110	6
010111	W	110111	7
011000	X	111000	8
011001	Y	111001	9
011010	Z	111010	:
011011	[	111011	;
011100	\	111100	<
011101	]	111101	=
011110	^	111110	>
011111	UNDERLINE	111111	?

a = a<sub>0</sub> = WEIGHT "1" = PIN 17 OF IC8 (FIG. 1)  
 b = a<sub>1</sub> = WEIGHT "2" = PIN 18 OF IC8  
 c = a<sub>2</sub> = WEIGHT "4" = PIN 19 OF IC8  
 d = a<sub>3</sub> = WEIGHT "8" = PIN 20 OF IC8  
 e = a<sub>4</sub> = WEIGHT "16" = PIN 21 OF IC8  
 f = a<sub>5</sub> = WEIGHT "32" = PIN 22 OF IC8  
 "1" = +3 TO +5 VOLTS  
 "0" = GROUND

FIG. 3—ASCII CODE (The American Standard Code for information Interchange).

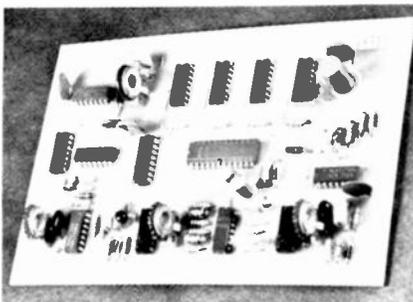

THE REVIDEO UNIT, carefully constructed, works as well as it looks.

that plugs directly into the readout sockets on the Superclock.

### The circuit

With these operating principles in mind, let's turn to the actual circuit and parts lists of Figs. 4 and 5. The H and V inputs are conditioned with Q1-D4 and Q2-D5 respectively and then fed to monostables IC3 and IC1 for the horizontal and vertical position delays. At the end of their delay times, the pair of latches in IC2 are respectively set. The vertical latch (pins 8-12) releases the clear on a divide-by-eight or a divide-by-sixteen counter IC7 that counts out the horizontal lines used for the active portion of the display. The *v* size control jumper

lets you pick a normal or double height character.

Once each horizontal line, the horizontal latch (pins 1 to 16 on IC2) releases a clearing clamp on the video oscillator IC4, the divide-by-eight video counter (IC5) and the cascaded divide-by-eight character counter (IC6). The video oscillator is a free running astable multivibrator when it is not being clamped by IC2. Its frequency is coarsely controlled by C11 and finely adjusted by R24, the horizontal size control. After exactly 64 counts, the H latch is cleared, the counters are clamped to 0000 and the video oscillator is stopped to await the next horizontal line.

The video counter goes around eight times and controls the output loading and spacing. It changes the input selector address just before its *first* count, and provides a shift register IC9 (Fig. 5) load count on the falling edge of its *third* count. This automatically transfers the contents of the character generator IC8 to the output register after a three-count settling delay. Three undots, or the space between numerals is generated during the three-count settling time. The final five counts of each numeral sequence are for the actual numeral video.

The character counter goes around only once per line, stepping a four-pole, eight-position input data selector IC10-13 once around as needed, routing the report inputs to the character generator in the right time slots. Character generator IC8 receives this data, along with a what-line-is-it? command from the line counter IC7. The character generator then outputs the proper dot combination to the output register IC9 which in turn marches the dots out as video.

### Building it

PC boards are commercially available for this project, as are parts kits—see the parts list. If you are building and etching your own board instead, a full size replica appears in Fig. 6. Components are located as shown in Fig. 7.

Start assembly with the jumpers and the smaller components, followed up by the IC's and finally the control pots. Use a small iron and fine solder and be sure to observe which IC goes where and the code notch and dot on each one. Also, watch out for diode and electrolytic capacitor polarities. Chances are you'll want to start with the larger character size, so jumpers the two upper "28" holes in the *v* size box. Do not unwrap IC8 or remove it from its protective foam until you have modified the TV suitable and have *completely* tested the rest of your circuit.


### Modifying your television

You'll need three modifications on your TV. One is to provide a new video input to sum the time on top of the existing program. One is to derive a narrow, positive-going, vertical sync pulse of 3 to 5 volts amplitude across a 10,000-ohm resistor. Finally, you have to derive a suitable narrow positive horizontal sync pulse of 3-5 volts across a 10,000-ohm resistor. *Any* method you use that doesn't obviously affect the TV operation and still gets the job done is acceptable, and the best way varies from brand to brand and model to model.

Before you modify your television, sit down carefully with a complete schematic or *PhotoFact* set and locate suitable tie-in


# CREI—the only home-study college-level training

## and now

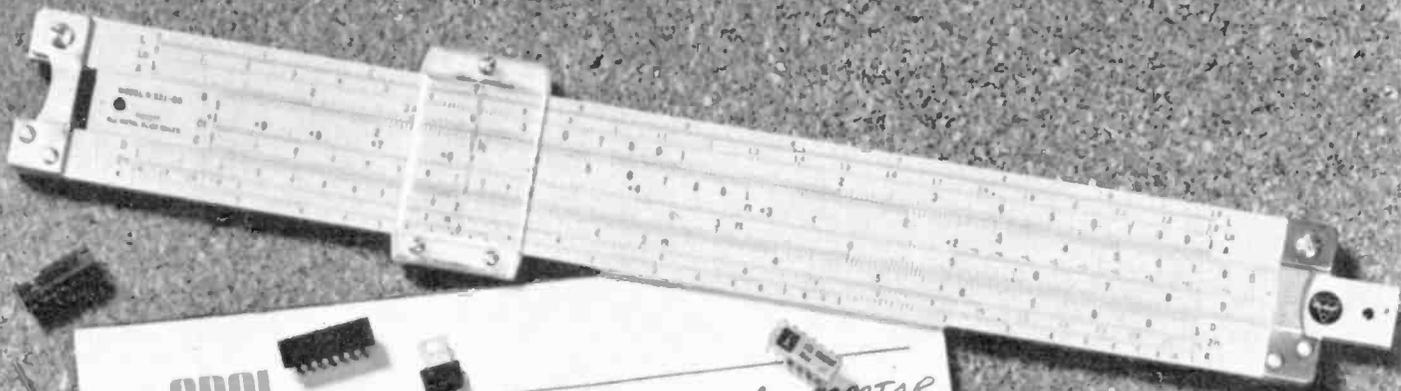

CREI


COMPARATOR  
CONTROLLED  
CLOCK

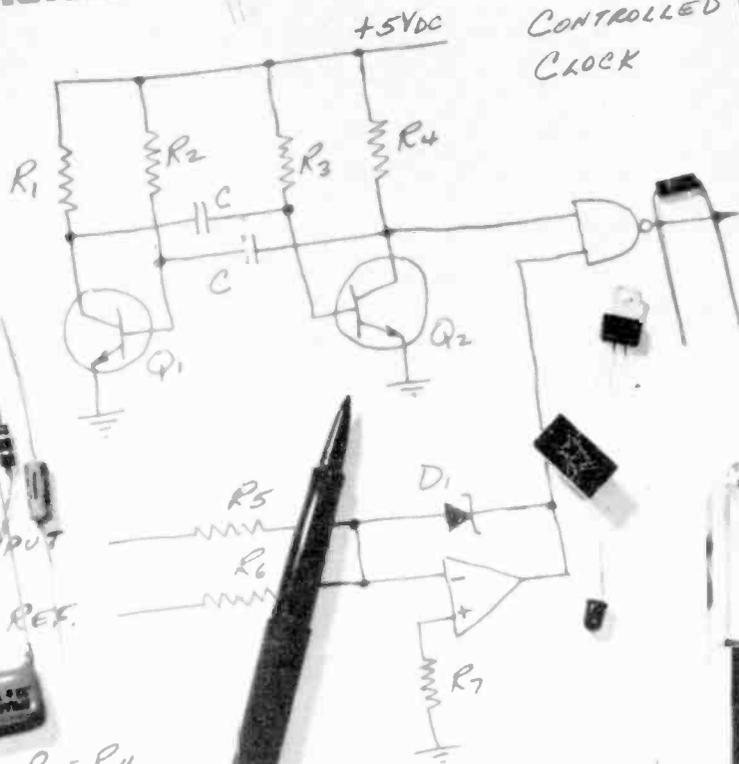

$$R_1 = R_4$$
$$R_2 = R_3 = R$$

$$T = .7RC$$

$$f = 1/2T$$

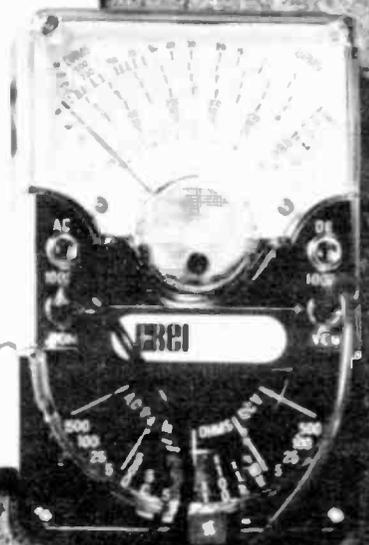

# program which gives you in electronic circuit design

# only CREI offers you a complete college-level Electronic Design Laboratory to speed your learning

**Electronic circuit design**—source of all new development in the application of electronics to new products and services. Without this skill, we would be unable to monitor the heartbeat of men in space. Without it, the computer revolution would never have occurred. And we would have yet to see our first TV show. *Yet, only CREI teaches electronic circuit design at home.*

## ELECTRONIC CIRCUIT DESIGN

A key skill which paces our nation's progress in countless fields—from pollution control to satellite tracking to modern medicine to exploring the ocean's depths. And beyond. A skill which you must have to move to the top in advanced electronics.

## CREI programs open up new worlds of opportunity for you.

In addition to electronic circuit design, CREI provides you with a full advanced electronics education in any of thirteen fields of specialization you choose. Communications, computers, space operations, television, nuclear power, industrial electronics—to mention just a few of the career fields for which CREI training is qualifying. With such preparation, you will have the background for a career which can take you to the frontiers of the nation's most exciting new developments. And around the world.

## This free book can change your life. Send for it.

If you are a high-school graduate (or equivalent) and have previous training or experience in electronics, then you are qualified to enroll in a CREI program to move you ahead in advanced electronics.




Send now for our full-color, eighty page book on careers in advanced electronics. In it, you will find full facts on the exciting kinds of work which CREI programs open up to you. And full facts on the comprehensive courses of instruction, the strong *personal* help, and the professional laboratory equipment which CREI makes available to you. All at a surprisingly low tuition cost.

## And when you have it, talk with your employer about it.

Tell him you're considering enrolling with CREI. He'll undoubtedly be happy to know you are planning to increase your value to him. *And he may offer to pay all or part of your tuition cost.* Hundreds of employers and government agencies do. Large and small. Including some of the giants in electronics. *If they are willing to pay for CREI training for their employees, you know it must be good.*

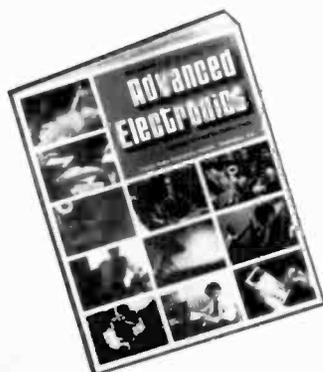**Send for Advanced Electronics today. You'll be glad you did.**



CREI Dept. E-1409-E  
3939 Wisconsin Avenue  
Washington, D.C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

If you have previous training in electronics, check here

Employed by \_\_\_\_\_

Type of Present Work \_\_\_\_\_

Veterans and servicemen, check here for G. I. Bill information

# CREI

**CAPITOL  
RADIO  
ENGINEERING  
INSTITUTE**

WASHINGTON, D.C. 20016

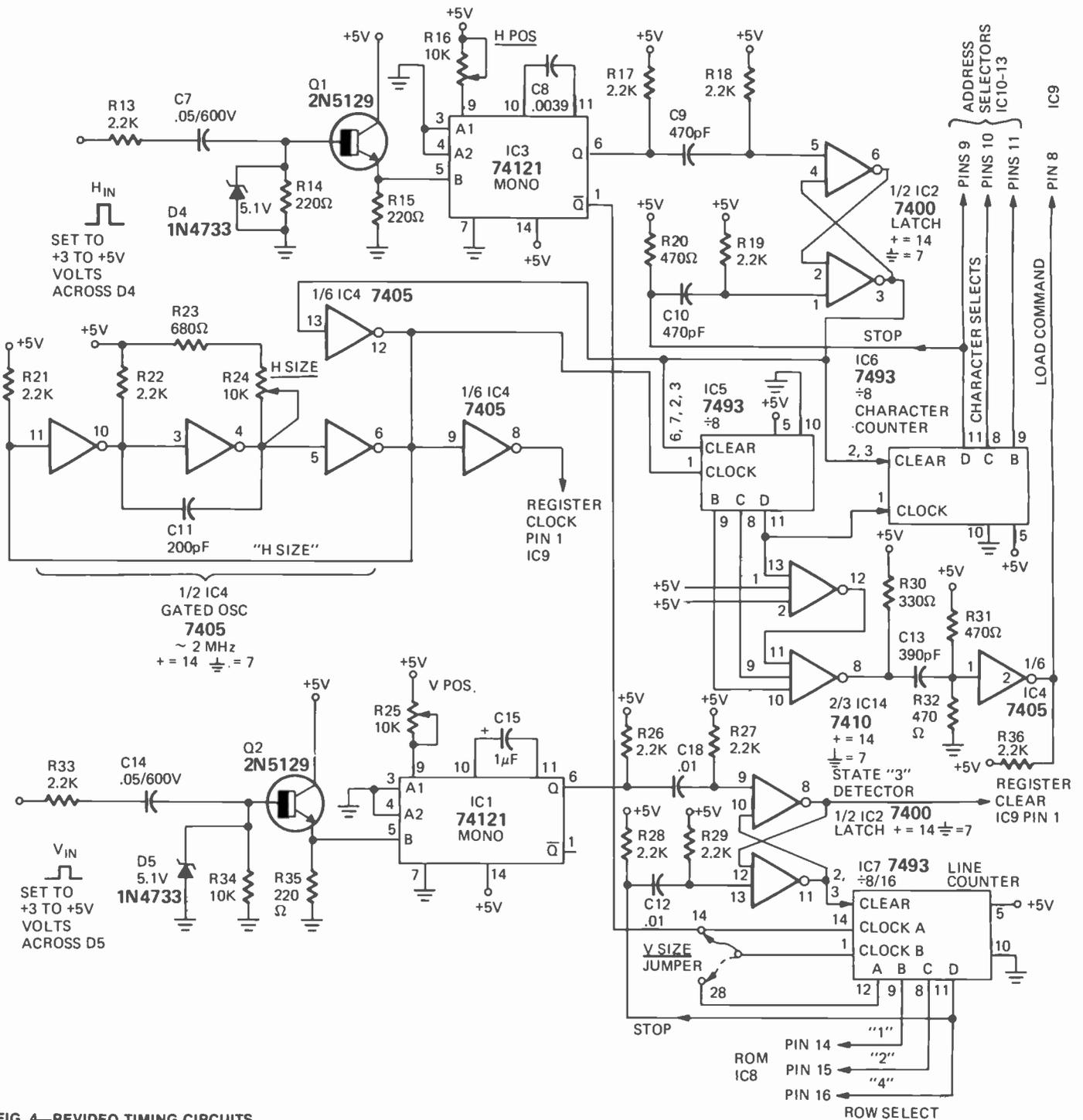


FIG. 4—REVIDEO TIMING CIRCUITS.

points. An oscilloscope is almost essential for this, even if you have extensive electronics experience. Fig. 8 suggests some possible interface points.


Let's start with the video. This can usually be injected into the grid or base of the first video amplifier stage, most likely through a 3,300-ohm series resistor and 0.1- $\mu$ F coupling capacitor. The optimum network here is one that doesn't degrade the normal picture response, yet at the same time provides enough numeral contrast. Be sure to pick a point that gives you *white* numerals. This means a point in the circuit where more positive means *whiter*. Adjust the value of R12 for the desired numeral contrast.

On a tube TV, a whole bunch of attenuation will be required to bring the trigger signals down to size. One good place to et the vertical trigger signal is the plate or col-

- C1, C2—10- $\mu$ F, 15-volt electrolytic
- C3—30- $\mu$ F, 6-volt electrolytic
- C4, C5, C16, C17, C18—0.1- $\mu$ F, 10-volt disc ceramic
- C6, C7, C14—0.05- $\mu$ F, 600-volt mylar
- C8—.0039- $\mu$ F polystyrene
- C9, C10—470-pF poly, mica, or disc
- C11—200-pF polystyrene or mica
- C12, C16—0.01- $\mu$ F, 10-volt disc ceramic
- C13—390-pF polystyrene or mica
- C15—1- $\mu$ F, 15-volt tantalum electrolytic
- D1—1N4001 or equivalent silicon power diode
- D2, D3, D4, D5—5.1-volt, 1-watt Zener diode, 1N4733 or equivalent
- IC1, IC3—72121 TTL monostable
- IC2—7400 TTL quad two-input gate
- IC4—7405 TTL open collector hex inverter

- IC5, IC6, IC7—7493 TTL divide by sixteen
- IC8—2513 ASCII character generator (Signetics)
- IC9—7496 TTL five-bit shift register
- IC10 to IC 13—74151 TTL one-of-eight selector
- IC14—7410 TTL triple three-input gate
- Q1, Q2—2N5129 transistor
- R1—27-ohm, carbon
- R2—150-ohm 1/2-watt carbon
- R3, R6, R9, R13, R17, R22, R26, R29, R33, R36—2.2K, carbon
- R7—1K upright mounting PC potentiometer
- R8—1K, carbon
- R14, R34—10K, carbon
- R16, R24, R25—10K upright mounting PC potentiometer
- R23—680-ohm carbon

COMPLETE

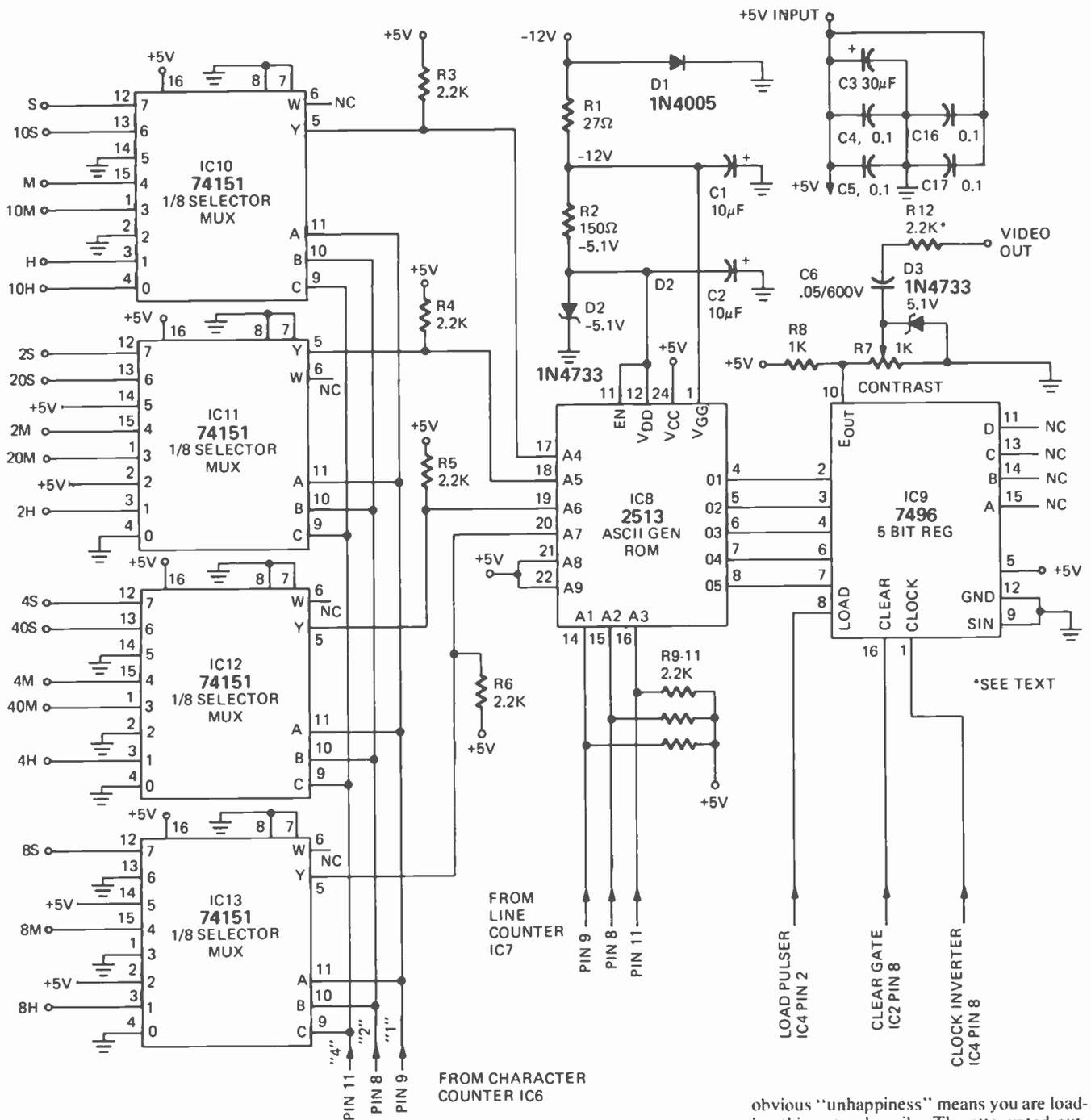

## PARTS LIST

R29—4.7K, carbon  
 R30—330-ohm, carbon  
 R20, R26, R31, R32—470-ohm, carbon  
 R15, R35—220-ohm, carbon

All resistors 1/4-watt unless noted

### Miscellaneous

PC Board, 4×6½ inches; PC terminals, optional (25); No. 24 wire jumpers and sleeving; mounting hardware; Flat 16-conductor input cable (2 lengths); solder; TV interface connector and lead kit (optional); gating switch (optional);

NOTE: The following is available from Southwest Technical Products, 219 West Rhapsody, San Antonio, Texas,

78216; Circuit Board, etched and drilled No. RV-1, \$2.85

(IC's are considerably cheaper from surplus and volume suppliers listed in **Radio-Electronics** ads than could be offered as part of a kit—the kit is thus split to give the **Radio-Electronics** reader the lowest possible unit price.)

lector of the vertical output stage. This will be several hundred volts high and a suitable narrow, positive going spike. Cut it down to size with two series 470K, 1-watt resistors and a 0.05-μF, 600-volt coupling capacitor. Use two series capacitors if the voltage is higher. When the network is added to the TV, nothing drastic should happen. A slight change in picture height or hold setting might occur, but any tearing, breakup, or

obvious "unhappiness" means you are loading things too heavily. The attenuated output has to drive a TTL monostable. It should stay below 0.8 volts most of the time; the narrow positive portion of the output should be 3 to 5 volts high with the Revideo unit connected. Unconnected, the signal should be *twice* as great (6-10 volts).

Don't try using the horizontal output stage as a trigger point—besides being lethal we could detune the flyback and cause all sorts of problems. So, look around for another, tamer narrow horizontal trigger pulse. On older tube TV's the plate of the agc keyer should have a several-hundred-volt narrow positive pulse suitable for our needs. Attenuate it down to the same size as the vertical trigger is—mostly below 0.8 volts except for a narrow, 3 to 5-volt positive pulse with the Revideo unit connected, 6-10 volts on open circuit.

Which transistor TV's, the voltages generally will be lower and somewhat less attenuation (lower value resistors) will be

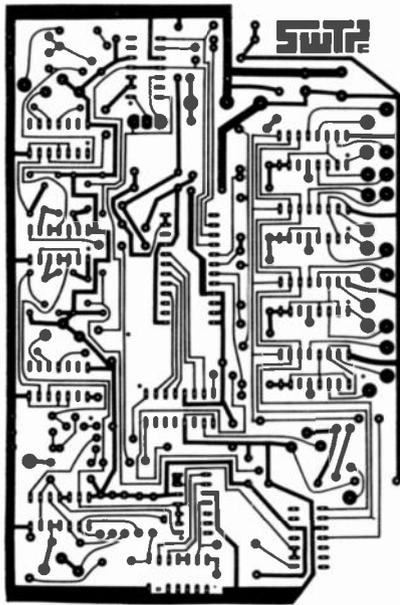


FIG. 6—LAYOUT OF THE PRINTED CIRCUIT BOARD, one-half actual size.

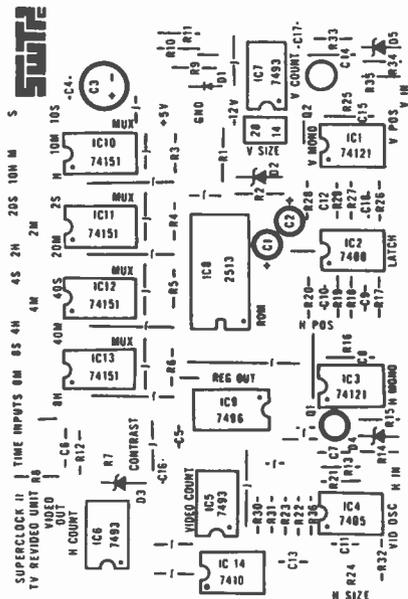


FIG. 7—THE COMPONENTS LAYOUT.

needed. Since the total energy you need for triggering is negligible compared to the normal circuit needs of the TV, you should have no problem after a try or two. Above all, work with the schematic and the scope when you're modifying the TV and don't connect the Revideo unit up until you are sure you have safe and reasonable trigger signals. Remember that connecting the Revideo unit will cut the trigger amplitude in half—from 6-10 volts to between 3 and 5 volts.

### Preliminary checkout

You'll also need a ground lead between the TV and the Revideo unit. A complete set of system interconnections is shown in Fig. 8. Remember that if the TV has a hot chassis you'll have to use an isolation transformer or live with a completely "hands off" system!

Leave IC8 uninstalled and the clock unconnected for the initial checkout. Apply suitable supply power and complete the television set to Revideo unit connections.

SAFETY WARNING: IF TV IS HOT CHASSIS, USE ISOLATION TRANSFORMER OR COMPLETELY INSULATE ENTIRE CIRCUIT!

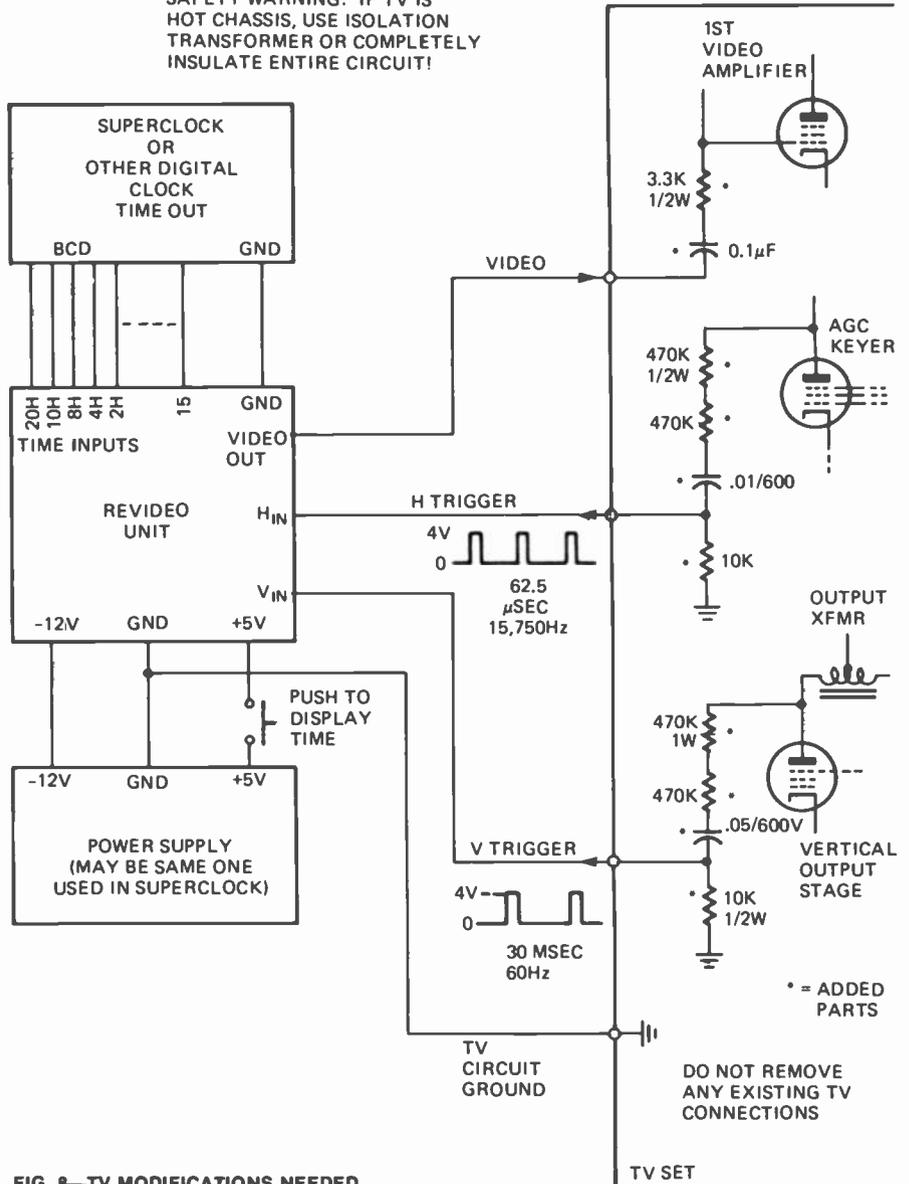


FIG. 8—TV MODIFICATIONS NEEDED.

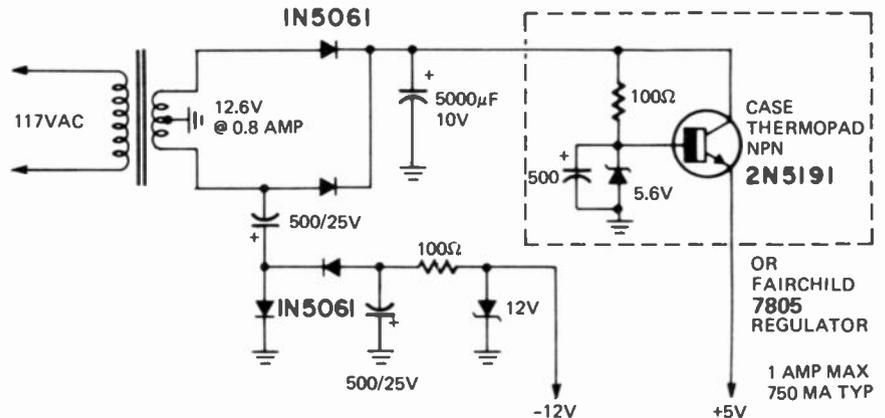


FIG. 9—OPTIONAL POWER SUPPLY

(An optional power supply is shown in Fig 9; use it only if you can't get power from the clock, the TV or a handy bench supply.)

If everything is working right, you should have eight white boxes where the numerals are to go, and you can move them around and change their size as you want to.

If you don't have the boxes, use a scope

to debug. Check first for proper trigger pulses on IC1 and IC3, followed by proper operation of the video oscillator and the three counters, finishing up with the output register and the stage-three decoder IC14. Usually trouble is caused by the input networks being wrong or crossed on the wrong inputs. (continued on page 94)

# SPECIAL REPORT

## *New Opportunities for the Service Technician*

*There's much more than just TV's and radios that require the services of today's technician. He can and should also be repairing electronic ovens, calculators, hi-fi gear, PA systems, burglar and fire alarms, videotape and electronic controls*

by **LARRY STECKLER**  
EDITOR

FOR THE PAST SEVERAL YEARS, I HAVE HAD THE GOOD fortune to meet with and talk to electronic service technicians from all parts of the United States. And to me, the most remarkable thing is how much alike they are. For whether they come from New York City; Des Moines, Iowa; Bath, Maine; Houston, Texas or Hot Springs, Arkansas they are all performing the same kinds of tasks and they all have the same kinds of problems, the same needs, the same aims and the same pressing desire to earn a better living this year than they did last year.

But the one thing that does not seem to make too much sense is the vast number of shops that repair only TV or only TV and radio. With the huge amount of consumer electronic equipment that is in every home these days, it seems to me that the technician who limits himself to servicing only TV or only TV and radio is letting a tremendous amount of other business go to someone else. Because you can be sure that someone is making money repairing calculators; someone is making money working on hi-fi equipment; someone is putting dollars into the bank from work he did on alarm systems. So let's take a look at these other products and see how and where they might fit into the service technician's capabilities and work patterns.

### **Hi-fi components and systems**


Next to the TV set, you will probably find more hi-fi

equipment in your customer's home than any other product. And if he's an average person, he's spent from \$250 to \$1000 or more for it. And when it isn't working properly he'd like to get it fixed. And you can fix it for him! We all know there was a day when you could repair a simple phono amplifier with little more than a voltmeter and perhaps, in an extremely difficult case, an audio oscillator. Well, those days are gone. If you are serious about doing hi-fi repair work you're going to have to invest in some \$2000 worth of test gear. Because today when a hi-fi amplifier stops working, the consumer wants you to do more than just restore the sound. He wants you to restore the original performance levels the manufacturer built into that equipment.


What does that really mean? It means that he wants the full 20, 40 or 60-watts per channel that the amplifier delivered when it was new. He wants that less than 0.5% distortion. He wants the original high sensitivity and selectivity of his tuner restored. You just can't do this kind of job with a voltmeter and audio oscillator. If you want to see what kind of equipment you really need for hi-fi service turn to Len Feldman's article in this issue (page 61) and find out.
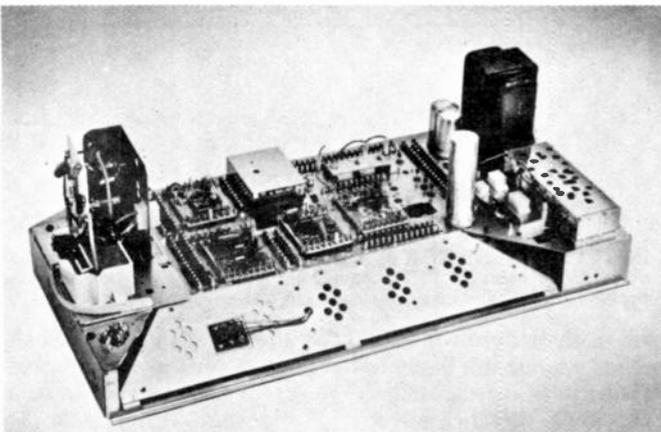
### **Take a look at calculators**

One of the hottest new electronic products on the market today is the electronic calculator. Ranging in price from as little as \$19.95 to as much as \$800 and more, they seem to be




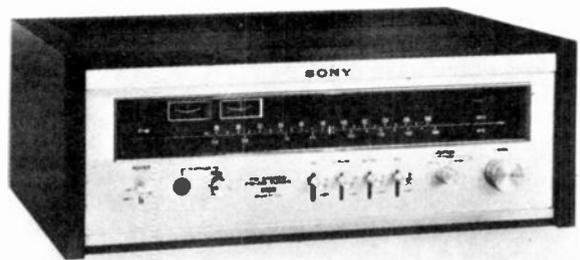**MODULAR TV CHASSIS IS WHAT MOST TECHNICIANS** are servicing today. But it represents only a small portion of the total number of consumer electronic devices in use today.



**TYPICAL HI-FI COMPONENTS LIKE THIS ONE** need service too. It takes some special test equipment and some additional service literature, but is a natural "extra" to try.

## ELECTRONIC OVENS

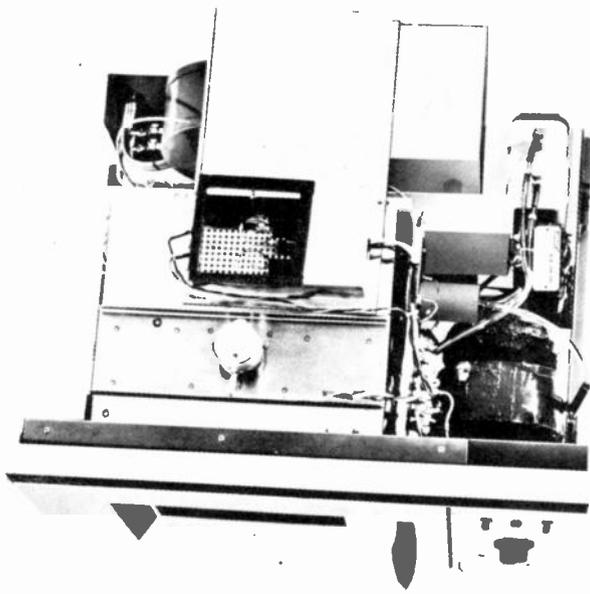

Foods are heated in the microwave oven by the absorption of microwave power. All food is constructed of many millions of molecules per cubic inch. These molecules react to the microwave field in much the same manner as a compass needle reacts to a magnet. If you place a magnet to one side of the compass, the needle will then point to the magnet. If you then move the magnet to the other side of the compass, the needle will turn and again point to the magnet. When this process is repeated quickly and many times, eventually the friction in the bearing that supports the needle will heat the bearing.

The molecules in food react in a very similar manner to the changing microwave field; that is, the molecules tend to align themselves with the field. The molecules that make up the food which is cooked in the microwave oven are rotated from their starting position to 180° from their starting position and back to their starting position 2,450 million times a second. This rate depends upon the operating frequency of the oven and can vary from oven-to-oven. This constant and rapid rotation causes the food to get hot. As the microwaves penetrate the food, power is lost to each successive layer of molecules. The center molecules, therefore are not rotated a full 180° and less heat is generated towards the center of the food than at the outside of the food.

Contrary to popular belief, food prepared in a microwave oven is not cooked from the inside out, but is cooked all the way through at the same time with more cooking being performed on the exterior of the food. It is, therefore, possible to prepare a rare, medium or well done roast in a microwave oven.

The fact that food is heated throughout makes it possible for the microwave oven to cook food fast. Time required to cook an item in the microwave oven is solely dependent upon how much heat is required, and in turn the amount of heat required of the food and the weight of the food. In conventional cooking, only the surface of the food is heated directly by the oven or grille. The heat required to cook the inside portion has to be conducted from the surface.

everywhere these days. Now obviously, you are not going to find too many people who want their \$19.95 machine repaired, but if they have \$150 or more invested and that machine breaks down, they are not going to run out and buy a replacement. And there is no reason why you can't get in on those repairs.

You don't need any special equipment. You do need some special knowledge. The technical end you can get from an article that has already appeared in *Radio-Electronics*. It's "How to Keep Electronic Calculators Running" and it appeared in the August 1973 issue. You will also have to do a bit of homework—find out who makes calculators, get the necessary service data, find out where to get the special parts you will need, and then let your customers know that you repair calculators.

## Electronic ovens

The electronic oven (microwave oven, radar oven, etc.) is really an electronic device. Yes it is an appliance. But basically it is electronic and compared to a TV set or hi-fi equipment or even a calculator it is a simple device. The only special equipment you will need, if you intend to service this equipment is a leakage detector. Your regular vom will take care of everything else. Again, some special briefing is needed, schematics are a must, and a look into sources of replacement parts must precede any announcement that you accepting these devices for repair. For a little more information on electronic ovens see the story on page 44.

## Don't overlook PA

Public-address systems go sour too; and when they do, the customer's usual concern is how soon can I get it back? So the prime service you must be able to offer your PA customer is speed. Fortunately, PA systems are not difficult to troubleshoot. For the most part you face a relatively ordinary amplifier, some elaborate speaker wiring and systems, plus a microphone. Again, no special techniques or equipment are needed. Even most of the replacement parts you



**VIDEOTAPE RECORDERS MAY SOON BECOME everyday fixture as common as color TV in the home. Are you ready to start servicing them? Do you know how they work and how to repair them?**

are likely to need will already be in your inventory. The only items you are not likely to have are the line-matching transformers. But these seldom require replacement so you can pick them up when needed. By the way, a PA system is a great item to cover on an annual maintenance contract. It can not only bring you some income without having to do any repairs—you may have years without having to do any

repairs—you may have years with no service requirements at all—but it locks the customer into your shop for service.

### Alarm systems

Here's an electronic system that suffers more from mechanical problems than electronic ones. The most common failures turn out to be window switches that don't work, a broken foil or a gap in the wiring somewhere. Yes, there are electronic faults that develop too but they are rare.

A good stock of normally open and normally closed switches plus a variety of transducers for special purposes will probably complete your extra parts inventory. One special word of warning however, before you run out and start repairing burglar or fire alarms. In some communities a special license is required. If you need one in your area, get it before you start repairing alarm systems.

### MATV and CATV

You are probably already installing master antenna systems right now. If you are, why don't you go on to the next section of this article. If you aren't, you really should be. How many customers do you now have, who own two or more TV's plus a hi-fi system, and *do not have* a MATV system in their homes? You're right! More than 90% of them.

By installing a MATV system you not only earn some extra dollars for yourself, you make it possible for your customer to have the best possible TV and FM reception. You can minimize interference between sets and insufficient signal strength to drive two or more sets simultaneously, etc.

And once you've done several home installations you may want to look at hotel and motel work. For a complete breakdown of what this kind of job entails, see "What's New In MATV", by Forest H. Belt, in the May 1974 issue of *Radio-Electronics*.

Cable television another story. In most instances the cable company uses its own personnel to handle all installations. However, if you could subcontract the installations, you might be able to get some new customers for the repair TV work out of it. You could also offer to install an MATV system in your customer's home that he could then hook up to the cable TV incoming line. If you are going to do very much of this work you'll need a truck equipped with a "cherry picker" to reach to the top of the utility poles. Also, watch out for power lines.




**MODERN DIGITAL TEST EQUIPMENT** will be a big help if you move into new servicing areas. Improved accuracy and easy reading are just two of the advantages.

### TV tape recorders

Here's an area of electronic equipment that is practically untouched. It is still so new that there is very little equipment in the consumer's home. The reason is simple—it costs too much. But the price is coming down and there are definite signs that the TV disc player is close at hand too (see "Here Come The Videodiscs" by David Lachenbruch,

### NEW SHARP CALCULATOR

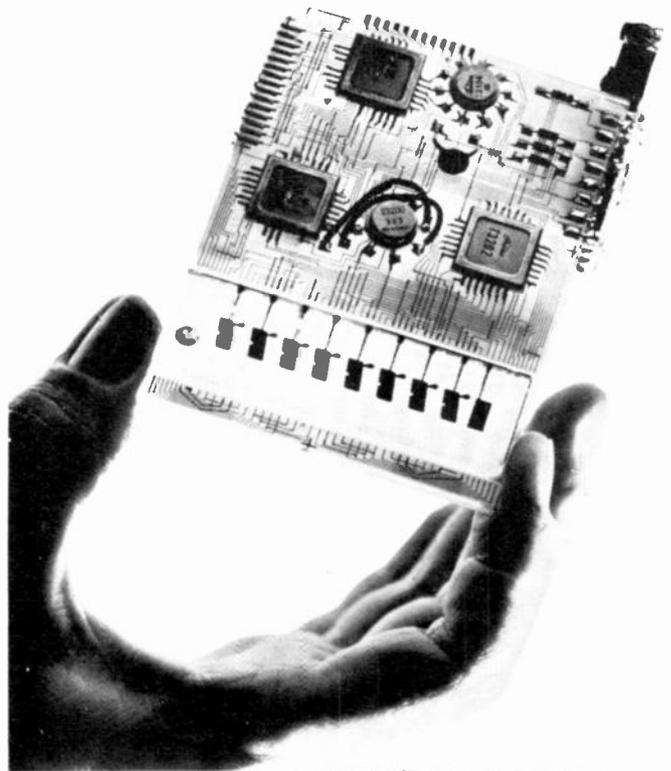

Here's a calculator that has a special feature in its construction that rates being called a technological innovation. As you can see on the cover of this issue of *Radio-Electronics* and in the photograph above the calculator is built on a glass substrate. On this substrate are all the LSI IC's, capacitors, liquid-crystal display and wiring for the main calculator section. One small circuit board with some additional components clips onto one side of the board. The result is a neat efficiently built unit with the extra bonus of very low power consumption. A single 1.5-volt penlight cell provides operating power for 100 hours of use.

The shirt-pocket calculator is 3 $\frac{1}{8}$  inches wide, 4 $\frac{3}{4}$  inches high on 1 $\frac{1}{16}$  inches deep. It has an 8-digit floating decimal display with leading zero suppression.

As the circuit board is a sheet of glass and not an epoxy-fiberglass compound, it is not as easy to work with. Bonding components and soldering wiring must be done at low temperatures to keep from distorting the glass panel. Also high temperatures could damage the liquid crystal display which is an integral part of the board. So special technology was developed to make the construction possible.

How important is the result? That depends on how important the cost of operating a calculator is. Compared to some calculators, the savings in battery cost could make it possible for this calculator to pay for itself in a five year period. How important is that feature to you?

**Radio-Electronics** August 1974 and "Videotape-Videodisc" by Fred Petras **Radio-Electronics** June 1974).

The circuitry in these new devices is very much like that of a TV receiver with some added complications thrown in. Again manuals and parts supply sources are first, but as this equipment has not saturated the consumer market yet, there's time to develop sources.

A training course in VTR repair might be a wise move. Work it in now if you can, before the rush begins and open classes become hard to find.

### Electronic musical instruments

This too sounds like a natural. In practice you'll find that it isn't. The special requirements of the musician are not for you and you will probably do best to leave this kind of repair work to the specialist.

### Industrial controls

Here's a place you can really shine. While large plants usually have their own electronic maintenance staffs, the smaller industrial plants usually rely on their regular plant maintenance people for this kind of work. The run-of-the-mill stuff they can handle but real troubleshooting is often beyond their capabilities.

One way to get some of this work is to visit local plants, find out what kind of electronic gear they have that needs maintenance and let them know that you can handle it. Then you can start off by suggesting that they call you the next time a problem comes up and eventually lead them into an annual maintenance contract.



**COMMUNICATIONS TEST BENCH** could look like this one. You'll note that much of the test gear is familiar and only a few unfamiliar instruments are to be seen.

In industrial work, there is one vital point to remember, speed of repair is pressing. Every minute equipment is down, out of service, is a minute of lost production. So if you plan on trying to do industrial work, it must be done on a rush basis.

### Communications equipment

Here's another growing market. The numbers of CB gear as well as commercial communications equipment is growing rapidly. You do need some special equipment here, but in


particular, you will need an FCC second class license. Without one you are not permitted to adjust frequency determining sections of this gear.

Here again, speed of service is important. If a person or a company depends upon radio communications they won't like being without equipment for long periods. And lest we forget there's lots of marine communications gear around too.
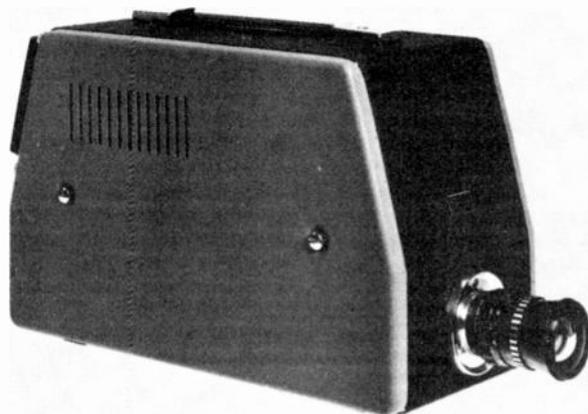
### Car stereo

As more and more people add FM and FM stereo radios to their car and as still others add 2 and 4-channel tape players and sometimes even recorders (both add-on and factory installed) more and more of them look for service once the warantee is over. This is a natural. Again you will need some special equipment—a 12-volt power supply to operate the unit on your bench and some acquired knowledge on how to get these things out of the car. By the way, the removal and reinstallation are likely to be the major problems. The electronics just isn't that difficult. One other requirement especially in cold climates, is a warm, indoor place to work while removing or installing equipment.

Installing tape decks in cars that don't have one can be profitable too. You can either make arrangements with a dealer that sells them to do his installation work or you might even consider carrying a line of your own that you could sell and install.



**CLOSED-CIRCUIT TV CAMERAS** ARE GROWING MORE COMMON too. You'll see them as a part of VTR systems as well as part of surveillance systems. And they do break down too.

### TV cameras

More and more low-cost units are appearing. You find them in catalogs of just about every electronics mail-order house. They are used with video tape recorders of course, to see who's at the front door, as a check on shoplifters and in dozens of other applications. But this means that there are plenty of TV camera repair jobs around too. How much of this work are you getting?

### Wrapup


In this article we've only tried to touch upon the more common possibilities that are open to the technician. We are certain that many readers are already doing these kinds of electronic service as well as others that we have not mentioned. In this direction you can help. If you've come across another area of electronic service that can be profitable, drop us a line and let us know. We'd like to pass it along. Address your letters to Editor, Radio Electronics, 200 Park Avenue South, New York, N.Y. 10003. And please accept our thanks in advance.

**R-E**

# BUILD THIS OP-AMP TESTER

*The knowledge that you are using a good IC is essential as you begin to work or experiment with op-amps. This go-no-go tester will give the assurance that you need.*

by SOL D. PRENSKY\*

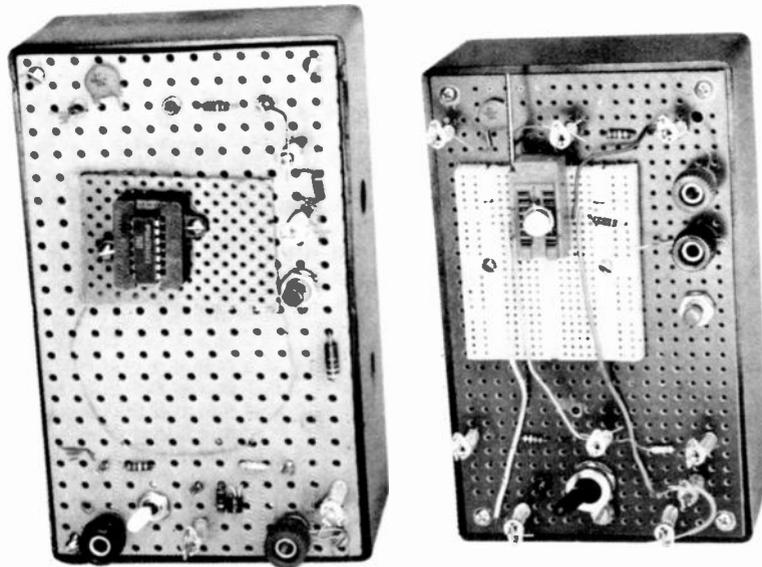

A SIMPLE AND PRACTICAL METHOD for rapidly testing the condition of integrated-circuit operational amplifiers (op-amps) is especially desirable now that these versatile devices are becoming more and more available. "Standardized" type numbers (such as the 709, 741, 101A and others) have emerged as low-cost, general-purpose op-amps that are attractive for all sorts of experimental construction projects. Moreover, they now can be conveniently obtained from retail stores and often, in untested condition, from surplus houses.

A major drawback for the experimenter, however, is the lack of any practical way of testing them inexpensively. There are formidable obstacles against arriving at even a fairly complete test for these useful devices. \*\*When dealing with these popular op-amps, the experimenter is confronted first by a variety of packages, [e.g., the 8-pin types in metal-can (TO-5) form, or the dual-in-line packages (DIP) in both 8-pin and 14-pin configurations]. Additionally, he is faced with a long list of refined specifications on the data sheet—all making it seem that it is necessary to use very special equipment, to perform a valid functional test—even if the experimenter is only interested in quickly finding out whether the op-amp in question is in good operating condition or not.

The test method described here gets around these complications, and quickly answers the "Go-No-Go" question for all three common packages of the popular op-amp series from the various manufacturers. It uses a unique arrangement for quick-and-easy insertion and extraction of the unit in question. Then, by concentrating only on the ability of the op-amp to function

\* Fairleigh Dickinson Univ.; adapted by the author from his "Manual of Linear Integrated Circuits" (in press), Reston Publishing Co., Reston, VA.

\*\* See "Text IC's 11 Ways With Your VTVM," which analyzes the internal components of only a single IC transistor array, (HEP590); *Radio-Electronics* (June 1973 issue).

satisfactorily, this test method rapidly determines the operating condition of the op-amp by just two strategic readings on a multimeter; (preferably a FET-VM, but also usable with a vtvm or even an ordinary vom).

## Theory of test operation


The test circuit of Fig. 1 shows the device under test (DUT) arranged in an oscillator (or multivibrator) configuration that produces a square-wave output for practically any of the widely-used "standard-type" op-amps. With the battery power turned on (S1); the multimeter set to read ac volts and connected across the output, first read the value of this square-wave output, with the op-amp in a nominally unloaded condition, (with the frequency-determining RC values set for a frequency around 1 kHz, and with a nominal 2K across the output, as specified for typical operation). Then, on pressing push-button switch S2, the circuit is loaded by the built-in miniature loudspeaker (in series with) the 330-ohm current-limiting resistor, and thus gives the second output-voltage reading, under the more heavily-loaded loudspeaker combination. The resulting audible output, plus the two readings of the voltmeter, provide the indications for the satisfactory working condition of the op-amp under both the nominally-unloaded condition; as well as with the op-amp delivering current to the load, (roughly here, around  $\pm 10$  mA). Thus, these two readings, accompanied by the audible tone, establish these two essential conditions:

1. The ability of the op-amp to provide a satisfactory oscillator-voltage output (and consequently sufficient voltage amplification), and,
2. The ability to deliver sufficient current output.

(Note: The interpretation of "Go-No-Go" values can be made either by comparison with a device of that type known to be good, or alternatively, from the summary of test results given in a later paragraph).

## Build your own

A choice of two breadboard arrangements

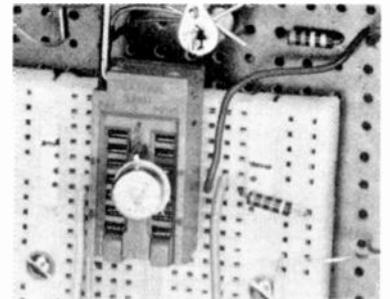

THE TEXTOOl DIP SOCKET for testing IC's. See text for details on how it works.

for the tester is shown in the photos. One arrangement uses the unique "ZIP-DIP" (zero-insertion-pressure) DIP adapter, which allows blissfully-easy insertion and extraction of the IC to be tested without any of the ordinary nuisance of straightening or aligning the pins of any of the three packages. The op-amp is simply dropped into the Textool adapter in its open (lever-up) condition, and the multiple leads of the unit are then firmly clamped into their proper contact by turning the closing lever down to its horizontal position.

The choice of sockets is given between the ordinary, inexpensive DIP socket version which requires soldering the DIP pins to respective "flea-clips" on a Vector perf-board, and a slightly more expensive "universal" breadboard arrangement that is made from a strip of the EL 5K-10 socket that requires no soldering. Here, the connections to the multiple pins of the DUT are made by simply inserting the bare end of the connecting wire (No. 20 or No. 22) into any one of the four receptacle holes that are already wired in parallel with each of the pins of the unit.

When these connecting wires are connected to the Vector spring clips (which also require no soldering), the rest of the components required for the circuit can be externally connected to the spring clips. As a result, since none of the connections are soldered, components can be clipped and unclipped to change the circuit at will, result-

ing in a truly "universal" breadboard. (More of this "universal" arrangement later.)

In any case, whichever form of breadboard is chosen, the test arrangement is greatly simplified by the fact that the circuit requires only five active leads for its operation—and these five leads are fortunately all in the same (or equivalent position in all of the three packages). Because of the fortunate "standardization" of practically all of the most-popular op-amp types, this comes about in the following way:

The 8-pin arrangement is shown in Fig. 2-a for the Mini-DIP package, and in Fig. 2-c for metal-can (TO-5) type with "formed leads" (as can easily be formed by hand in accordance with the "DIL-can" form used by RCA units). For either of these 8-pin arrangements, we use only the two input leads (numbered 2 and 3, the number 6 output lead, and the two split power-supply leads: 7 as V+ and 4 as V-.

The pin numbers for the 8-pin packages align identically with the corresponding active leads of the 14-pin package, by the simple expedient of inserting the 8-pin package two holes down from the index point of the 14-pin socket as shown in dotted lines of Fig. 2-b. Since the top two pins (on either side of the 14-pin socket) are NC (no connection), as is the lowest-pin on either side, we find that remaining 8 pins in the middle of the 14-pin socket have identically the same function as in the 8-pin arrangement. Thus as seen in Fig. 2-b corresponding DIP pins are as follows:

	<b>14-pin</b>	
Input leads	4	corresponds to
	5	corresponds to
Neg. Supply	6	corresponds to

Output 10 corresponds to  
Pos. Supply 11 corresponds to

#### 8-pin

two = INV (-)  
three = NON-INV (+)  
four = V-  
six = Output  
seven = V+

As a result, the identical connections are made, either when we insert the first pin of the 8-pin package into the third hole of the 14-pin socket, or, as obtained from inserting the 14-pin package into its socket in the usual way—and thus all three packages can be accommodated in the one simple 14-pin socket. The Textool adapter, as previously stated will plug into either the conventional, relatively-inexpensive 14-pin DIP socket, or the EL socket strip. (The recently announced SK-20 socket — also with solderless receptacles — is similar to the long SK-10 but is made to accommodate only a single 14/16-pin DIP. This SK-20 is convenient for a more compact tester, and at \$12.75, is much less expensive. Depending on your needs, you may prefer to use one-third of a SK-10 which will accommodate two 14/16-pin DIP's or four 8-pin mini-DIP's. However, the SK-20 will suffice for testing or using a single op-amp IC. This new device is the basis for a simplified EL Starter Kit, see parts list.)

Whichever socket you chose, the main point is that the plug-in Textool adapter makes it extraordinarily convenient to drop in any one of dozens of different types of "standardized" Op Amps for this test — and, in the case of the EL socket, with the added advantage of being able to quickly set

up any other desired op-amp circuit by simply changing components between the Vector spring clips.

In the arrangement used here some soldered connections were made for convenience in this test (but without necessarily destroying the "universal" aspect of the unit using the EL socket. The miniature (2 or 2¼ inch), 8-ohm loudspeaker is cemented to the board, and just a few soldered connections are made for the switch, LED pilot light, and the common-ground connections. The two square-bottomed (NEDA 1602) 9-volt batteries are easily fitted into the bottom of the plastic box as a ±9 volt split-supply; (these are used for extended life, although the common transistor-type 9-volt batteries can also be used to provide the limited current used by the tester). An extra Vector spring-clip is mounted next to and strapped to the V+ terminal; this strap can be removed if it is desired to monitor the current drawn from V+ by the op-amp in both the loudspeaker-load and the nominally-loaded conditions. Adding an LED as pilot indicator is optional, and its 10-20 mA current should not be an excessive drain on the batteries.

#### Test results

A number of popular makes of op-amps were tried on the tester, including both good and inoperative units. The tester found every defective op-amp. Of course, where a good op-amp of a particular type is available, it is a simple matter of compare its readings with that of the unknown unit of the same type. Otherwise, as a starting point, a rough "rule-of-thumb" range is given below, to illustrate the general order of magnitude of values that might be expected.

#### Rule of thumb limits


In general, the p-p value of the nominal-loaded square-wave output should roughly approach the value of the ±9-volt supply. Then, taking into account design variations of different makes of general-purpose op-amps, and figuring on the safe side, we can set a range of p-p values to exceed 2/3 of the total 18-volt dc supply, or, in this case, from 12 volts p-p up, to indicate a good unit for the first reading. When delivering current to the loudspeaker, we should expect at least half of the first reading, or greater than 6 volts (p-p) for the second indication.

#### Using the meter

The peak-to-peak readings given here are all based on using an FET-VM or a vtvm. It is also possible to use a non-electronic vom on its ac range, but because of the different rectifier arrangement in the vom, its values for a square-wave output will not agree with the p-p values of the FET-VM. When using a vom on its ac range, a rough but workable correction factor can be used by doubling the so-called "rms" vom reading (instead of the usual 2.8 for sine-waves), to approximate the equivalent p-p value of the FET-VM, for the square-wave output.
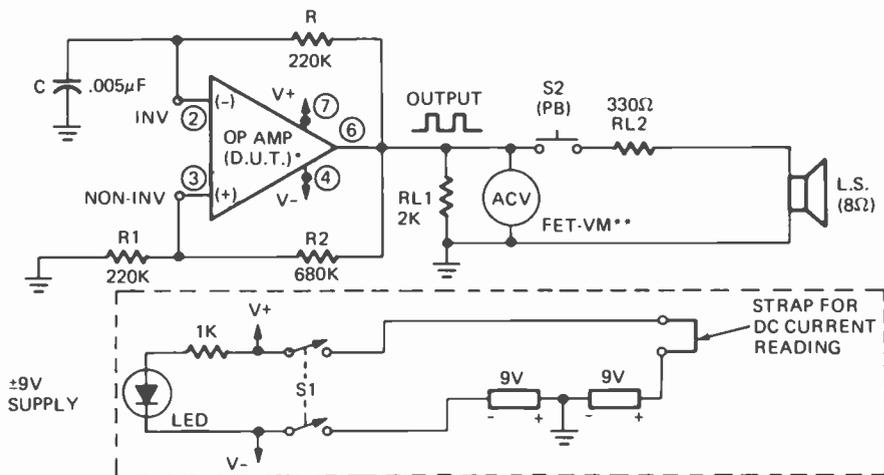
#### Sample results

Without attempting to discuss the many Case, plastic, to fit board.  
A kit containing all the breadboard and all necessary parts for the tester except batteries and S1 is available from EL Instruments, 61 First St., Derby, CT 06148. Order as EL Starter Kit. \$10.95 plus 50¢ for postage and handling.



\*CIRCLED PIN NOS. APPLY TO 8-PIN PACKAGES; SEE TEXT FOR 14-PIN PACKAGE.  
\*\*FET-VM PREFERRED FOR P-P READINGS; SEE TEXT FOR USE OF VOM.

FIG. 1—OP-AMP TESTER schematic. The instrument has spring clips so wiring and components can be changed as needed. Jacks are provided for plugging in a multimeter.

#### PARTS LIST

All resistors ½ watt

R, R1—220,000 ohms

R2—680,000 ohms

RL1—2000 ohms

C—.005 µF

BATT 1, BATT 2—9 volts each (for long life I suggest Eveready 246, Burgess 2N6 or equal NEDA 1602 type)

S1—dpst or dpdt

S2—push button, normally open

SPEAKER—2 or 2¼-inch, 4, 8 or 16 ohms

Perf board—with .093 holes, 3½×6 in.


Socket—standard type (requires soldering) dip, 14-pin (Cinch, Cambion, Barnes, GC Electronics or equal). Universal type (solderless) EL SK-10 (1/3 strip) or SK-20see text. (Available from EL Instruments, 61 First St., Derby, CT 06418)

JACKS—to fit meter test leads
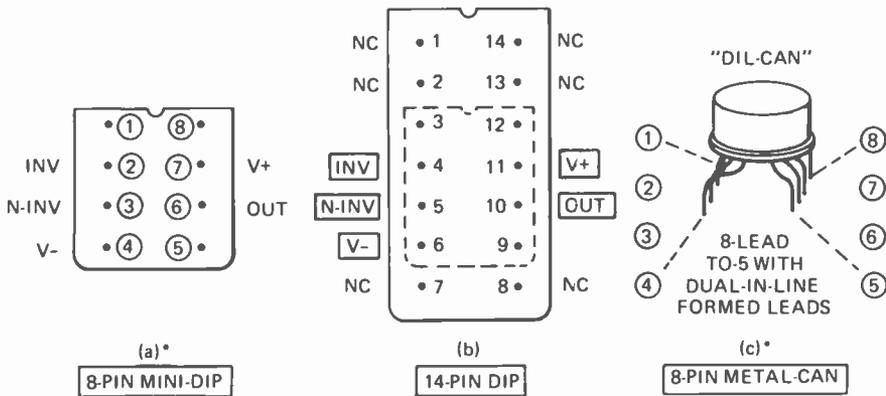
#### OPTIONAL

IC TEST SOCKET—Zip-Dip, 14-pin polycarbonate (available from Textool Products Inc.) 1410 W. Pioneer Dr., Irving, TX 75061)

LED pilot lamp—1.6 V, 20 mA and 1000-ohm series resistor



\*CIRCLED NOS. APPLY TO BOTH 8-PIN PACKAGES (a) AND (c).  
**FIG. 2—THE TEST SOCKET is a 14-pin DIL type that can be used for 8-pin mini-DIP and TO-5 can 8-pin DIL devices. Drawing (b) shows how 8-pin devices are inserted.**

types of op amps that are available for special purposes, here is a brief sampling of the results obtained from op amps I had on hand at the time. These samples include both *internally and externally compensate* types. Both types can be tested in this types of open-loop circuit without bothering with frequency-compensation. As a third class of

"standardized" op amps, samples of the FET-input type are included. (The "standardized" type number, which also reappears in "second-sourced" models by other manufacturers — is shown in italics). The following op-amps, (with standardized pin-numbers) all produced a clear tone and easily exceeded the arbitrary limits (12 volts

p-p unloaded and 6-volts p-p loaded), as "good" units on an FET-VM for the peak-to-peak readings:

*Internally-compensated units:*  
 CA3100S (RCA) MC1556 (Motorola)  
 LM107 (National) SN52771 T.I.)  
 $\mu$ A741 (Fairchild) HEP, C6052P,  
 similar to MC1741;


*Externally-compensated units used without compensation:*  
 LM101A SN52770  
 $\mu$ A709 HEP, C6053P,  
 similar to MC1539  
 $\mu$ A748

*FET-input units:*  
 $\mu$ A740 (Fairchild) NE536 (Signetics)  
 ICL8007 (Intersil) AD503 (Analog  
 Devices)

This list could be broadened to include op amps that do not have the "standardized" pin numbers by the use of the solderless "universal" form of breadboard. In that case, it is a simple task of only minutes to change the pin connections to the Vector spring clips, and thus be able to accommodate dual op amps (such as the 747 type) and many other special types, as desired. **R-E**
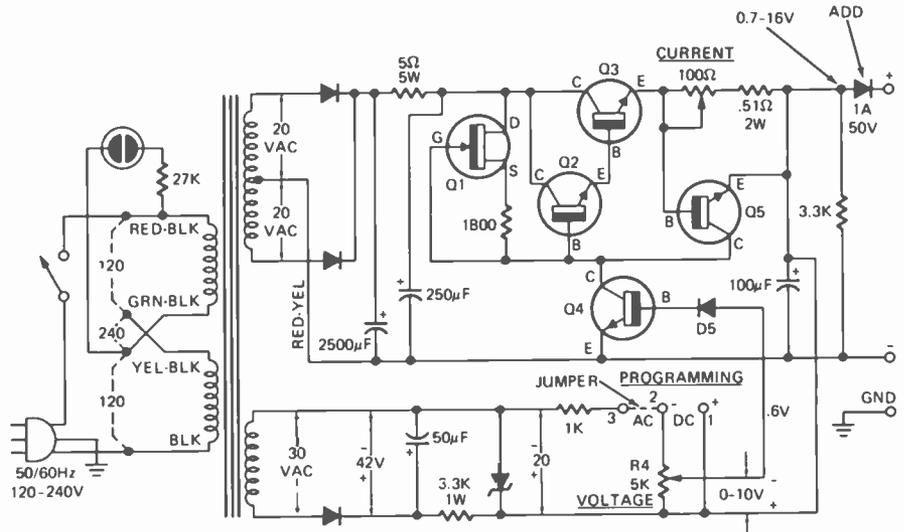
### HEATHKIT IP-18 POWER SUPPLY

This type of power supply is extremely susceptible to damage from reverse voltage applied to its output. If voltage control R4 is turned down when a Ni-Cad battery is connected, for example, excessive current may flow through D5 and Q4. Depending upon the failure mode of Q4 and the length of time power is left on, Q2 and Q5 may also fail. The solution is to connect a 1-ampere silicon diode at the output as shown. Simply remove the blue wire from the "+" terminal on the circuit board and connect it instead to the cathode of the new diode. Solder the anode of the diode into the "+" terminal of the board and the job is complete. — Donald R. Hicke



### POOR MAN'S BINDING POSTS

Binding posts are expensive these days and they take up lots of space, particularly when you are working with small components like IC sockets.

Here is how you can make your own binding posts for an IC test socket. Drill holes to pass 4-40 screws where you want a binding post. Fig. 1 shows

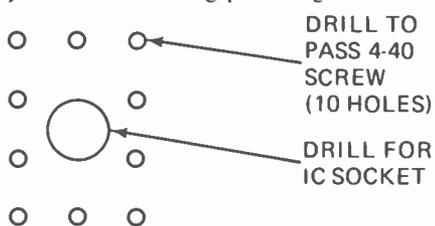


FIG. 1

the square pattern I use for a round 10-pin IC socket. It is easier to start with perforated board and simply widen existing small holes. Also, you

will need a larger hole at the center (S) into which the IC socket fits. Cement the socket in place.

Now cement a 4-40 nut under each hole as in Fig. 2. Use any good epoxy.

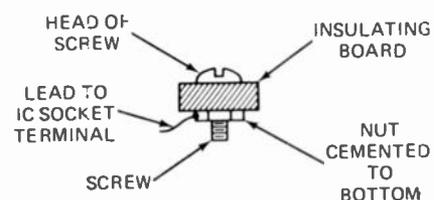


FIG. 2

When the glue is tacky enough to hold the nut fairly well, insert the screw from the top and tighten it. This holds the nut in the correct spot under pressure until the epoxy hardens. Make sure the screw is free to turn within the nut; don't let glue get inside the nut.

When finished, solder a lead between the nut and a terminal of the IC socket.

To use the binding posts, simply raise the screw, insert a lead under the head and tighten. If desired, you may use an open type lug instead of just a wire. This method is far more convenient than soldering and unsoldering wire during an experiment. — I. Queen



# What's a RAM?

The vocabulary of engineers or experimenters working with computers, synthesizers, electronic calculators and similar digital devices is replete with acronyms you should know. RAM is one, read on to find out what it is and how it's used.

by DON LANCASTER

ANY MEMORY IS A STORAGE DEVICE THAT is given some information at some time and hopefully will return that identical information at a later date for reuse at least once. The most elemental unit of a memory storage system is the *cell* which can store one *bit* consisting of a "1-0" or "Yes-No" simple decision. Memory cells are often grouped into *words* of several bits each. These words can represent the number in a calculator, an instruction command in a computer, a tone and its duration in an electronic music composer, an alphanumeric character in a TV Typewriter and so on.

Memories can range from one bit to many billions of bits. The equivalent of the human memory is sometimes suggested as 10 billion bits while the longest memory you can buy in a single off-the-shelf integrated circuit is 4096 bits.

There are several different types of memories. You usually classify them by when, how and how often you put information in them. A *Read Only Memory* (See "What is a Read Only Memory?", *Radio-Electronics*, February 1974) has information put into it only *once*. It keeps the information inside it more or less permanently. Read only memories are often used for such things as square root, log and trig instruction *microprograms* in a calculator, for time-zone conversion in a digital clock and for many other situations where you always want the same response to your system. Some read-only-memory systems are called "table lookup" systems, for they provide an "answer" in the same way you would get it from a math handbook. A few read-only-memory systems *can* be altered, but not rapidly. This is done by erasing them with intense ultraviolet light and reprogramming them; others are altered with special voltage or current pulses. Sometimes these are called *Read Mostly Memories*.

We could also theoretically have a *write only memory* that would accept information but never return it. Contrary to some misguided and uninformed industry jokes about WOM's, these DO exist and have a very specialized use in computer programming, particularly in data stripping and formatting. Still, nobody really manufactures WOM's. When you want a WOM function, you use one location of a read-write memory over and over again instead, never bothering to read it.

The most versatile memory is one that you can *write* (put information into) and *read* (receive information from) rapidly and in any sequence. Magnetic cores are typically this type of memory, although by eliminating or not using the write current generators, we can also obtain a read only function. Most cores are *destructively* read

out, meaning that the information is lost the first time you use it. You then have to perform a *rewrite after read* operation and then put the information *back* into the memory cells if you are going to use the information again.

Most semiconductor memories are *non-destructively* read out in that you can accept information without physically altering the memory contents.

If you *must* put the information in and get it back in one specified sequence, you have a *sequential* memory. Long MOS shift registers can make a sequential memory. These have traditionally been lower in cost than true read-write memories, but have disadvantages of being noisier and having to wait a long time for the information you need to come out.


The more versatile read-write memory is one that you can read or write in any location at any time. This is called a *Random Access Memory*, or RAM for short. RAM's can be made sequential simply by deciding that you want to access or *address* things in order.

A memory is *non-volatile* if you can remove the supply power or stop moving the data around inside the memory and still hold the information. Magnetic core is usually non-volatile. Semiconductor read only memories are, of course, non-volatile. Most reasonable or available semiconductor RAM's are volatile and you must keep the supply power up or you will lose information. Many RAM's offer a reduced power mode where you can keep information for long times on battery power. In a few years, we can expect true non-volatile semiconductor RAM's, but for now, you have to design your memory application in such a way that the information is either no longer needed or stored somewhere else than in a semiconductor RAM during power down times. This really isn't nearly as bad as it seems for usually you can easily get around the problem one way or another. Often a mixture of ROM's and RAM's in a single system does the job.


There are two basic types of semiconductor RAM's. These are the *static* RAM and the *dynamic* RAM. *Both* of these are volatile and will lose information during power down times. The difference is that static RAM's will keep their information so long as power is applied without reshuffling or *refreshing* the data while a dynamic RAM has to have its internal storage moved around occasionally, often at a 500-hertz rate or faster. Static RAM's usually have a flip-flop cell for data storage. Once set or reset, it will stay in that state until power is removed or it is retriggered. Dynamic RAM's usually use a capacitor for data storage. The

capacitor will eventually discharge and thus the data must be moved or *refreshed* before it is lost. Dynamic RAM's are normally far cheaper as you can pack a lot more bits onto a given size chip, but they add to the external circuit complexity and may take some elaborate timing to reliably get them to work. Thus, dynamic RAM's are more suited for very large memory systems, those over 50,000 bits or so.

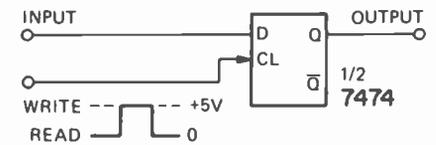
Today, you can buy a 256-bit surplus static RAM for \$2.56 and get the same thing new for under \$6.00. A 1024-bit dynamic



a ONE-BIT MEMORY

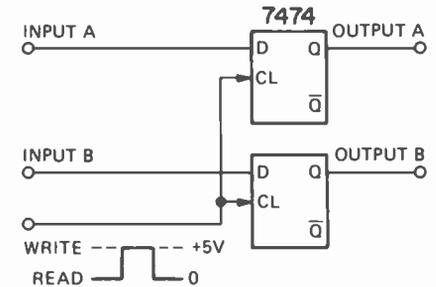


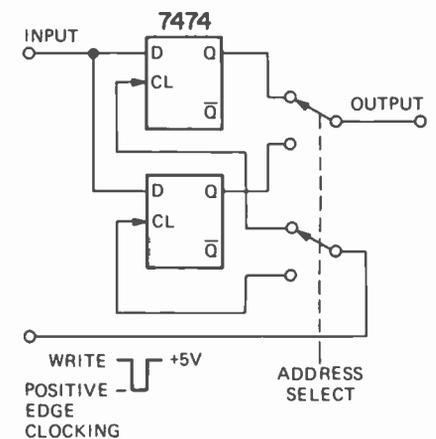b TWO-BIT MEMORY,  
ONE WORD OF TWO BITS (1 X 2)



c TWO-BIT MEMORY,  
TWO WORDS OF ONE BIT EACH (2 X 1)

FIG. 1—SOME VERY SIMPLE RAM circuits using the TTL 7474 dual-D flip-flop.

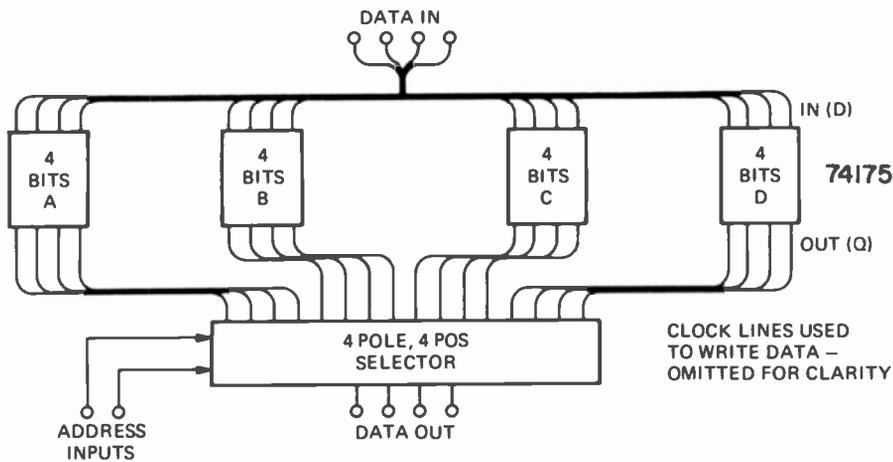

a 4-WORD, 4-BIT-PER-WORD MEMORY USING FOUR 74175's

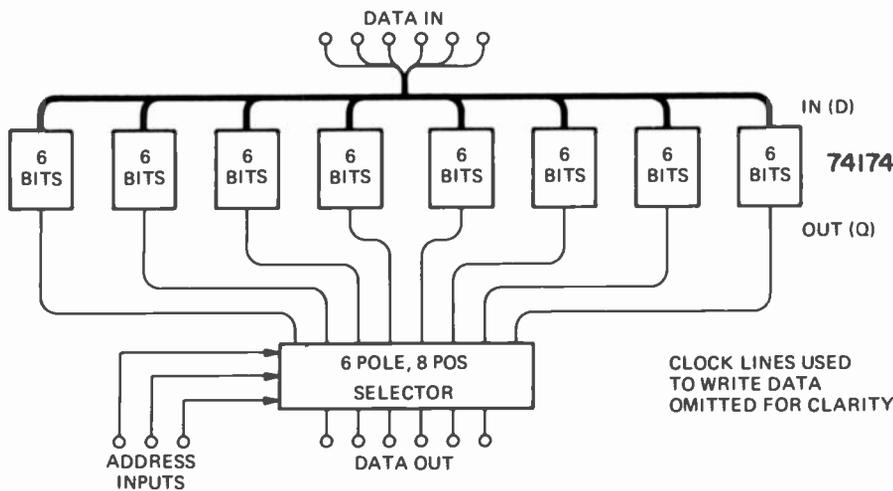


FIG. 2—TTL RAM CIRCUITS using quad and hex latches as memory IC's.

RAM runs around \$5.00 surplus and under \$12.00 new. Thus, we are talking prices *right now* of a penny per bit and under and projected pricing runs as low as *one-tenth* of a penny per bit. At this projected pricing, a minicomputer computer memory big enough to speak Basic or Fortran could be built for a memory component cost of \$64.00 for 64,000 bits, perhaps arranged as 4000 words of 16 bits each. Simpler memory systems for things like terminals, electronic locks, music composers and a whole bunch of things nobody has thought up yet today should cost well under \$20.00 and eventually should come down to \$2.00. So, now is the time to start becoming familiar with these exciting new devices.

### A simple semiconductor RAM

Let's start with a rather small RAM and see what we can do with it. We'll use the 7474 TTL dual type D flip-flop as shown in Fig. 1. We'll start with a one-bit memory and then double it to two bits by using both halves of the package.

In Fig. 1-a, we use half the 7474. This stage can store a "1" (often a high state around 3.3 volts) or a "0" (usually a low state around 0.5 volt). The stored value appears at the "Q" output. The opposite or *complement* of the stored value appears at the Q output. We have a data or D input and a clock or CL input. Information present on the D line gets loaded into our memory at

the time the clock goes from ground to a positive value. To enter information into our memory, we put the information on the D line. At that time, it does NOT go into the cell. At the instant we bring the clock line from ground to a positive level or from a TTL positive logic 0 to a positive logic 1, we actually load or write the information into our flip-flop cell. Whatever was on D at the instant of positive edge clocking gets loaded into the memory and appears at the Q output.

This is a random access memory as we always can get to the memory cell (trivial, as we only have one cell) anytime we want. It is static as it will keep the loaded information for as long as we apply power. It is volatile as the information will go away if we ever shut off the +5-volt power supply. And our simple memory is *organized* as "one word of one bit each."

We can watch or *read* our memory any time we like, but since a change may be produced during clocking, we shouldn't be using or reading at that particular instant. We call the clocking interval the *write cycle*. Time spent looking at this particular cell's output is called the *read cycle*. Normally, you don't read and write simultaneously. You either *execute* a read cycle where you monitor and use the output of the memory cell or you execute a write cycle where you place new information into the cell. The 7474 will do a write or a read cycle in under

50 ns. Since nothing physically changes internal to the 7474 during reading, the read-out is non-destructive and we can reuse the stored information hundreds or even millions of times if we like.

A one-bit, one-word memory by itself isn't too useful, although you can think of an alarm system as a one-bit memory and there are numerous other trivial applications. To do any really useful function, we most often need quite a few more bits of storage.

Figure 1-b shows how you can use both halves of a 7474 to build a memory of one word of two bits. This is done by simultaneously clocking each half of the package and using both outputs at once. Thus we have two data input lines, two output lines and one write line. This organization is *one word of two bits*. In 1-c, we have the opposite, a memory of *two words of one bit each*. Now something new has been added. We have to *combine* or *select* which of the two memory bits is going to appear as an output. We also have to decide which of the two cells is going to have data written into it at any given time. This decision is called *addressing*. We now have to address cell A (a 0 on the address line) or cell B (a 1 on the address line). By controlling the address line, we select which memory cell is to be acted upon or read.

The more cells we have, the more complicated the addressing will become. Note that we needn't alternate memory cells if you don't want to. You can address either cell in any sequence you want. Hence the name *random access*.

### Adding more bits

We could use as many 7474's as we like to build up any memory, but even at surplus prices, the 25¢ or so per bit and the large supply power and size will eventually get to us. The next step up is to use packages with more than two D flip-flops. Quad and hex latches, the 74175 and 74174 are a good choice. Figure 2 shows some memory circuits using these components.

In Fig. 2-a, we have a 16-cell memory arranged as four words of four bits each. We have four data lines, four output lines and *two* address lines. These two address lines are binarily decoded (00, 01, 10 and 11) to get at the *four* possible memory cell locations. We might use this memory to store four BCD numbers as part of a computer or calculator.

In Fig. 2-b, we use eight 74174's to build a 48-bit memory organized as eight words of six bits each. This time, we have six data input lines, six output lines, and *three* address lines. The three address lines are decoded (000, 001, 010, 011, 100, 101, 110 and 111) to get at the *eight* possible locations of six cell groups. Since we can represent a letter, number, space or punctuation with six bits of the standard ASCII code, this memory could be used to store an eight character message.

### Which organization?

Suppose we had a 64-cell memory. How could we group the cells to obtain different combinations of bits-per-word and numbers of words? Figure 3 shows some possibilities. While each of these memories is 64 bits total capacity, the *organization* of each is different.

In Fig. 3-a, we have one word of 64 bits each. We need zero address lines since we are always looking at the same word, but we

need 64 input lines and 64 output lines. In Fig. 3-b, we have two words of 32-bits each. We now need *one* address line to select which half of the memory is to be written into or read from. There are 32 input leads and 32 output leads. The next combination of Fig. 3-c would be four words of 16 bits each. Here we need *two* address lines binarily decoded to select which quarter of the memory is to be active and there would be 16 input leads and 16 output leads.

You can rapidly run down the other organizations. Figure 3-d gives us eight words of eight bits each. There are three address lines needed that are decoded one-of-eight to pick one-eighth of the memory for use and we have eight input lines and eight output lines. In Fig. 3-e, we have four words of 16 bits each. Four address lines decode one of sixteen and there are four input and output lines. Two words of 32 bits each take two input lines, two output lines and five address lines, the latter decoded one-of-32 as shown in Fig. 3-f. Finally, in Fig. 3-g, we have 64 words of one bit each. There is one input line, one output line and six address lines which are binarily decoded one-of-64 to pick which of the individual memory cells is to be interrogated.

So, we have a wide choice of organizations to any memory. The more the bits, the more the choices. Which do we use?

This depends on you if you are working with a large system and depends on the integrated circuit manufacturer if you are trying to get the job done with only one or two stock integrated circuits. Obviously, you organize the memory to suit the information you are trying to put into it. Four-bit words are common for BCD (binary coded decimal) number storage in calculators. Six-bit words are often used to store ASCII characters. If the full ASCII code, including transparent control commands and lower case and error detection is to be used, we have to up to eight bits per word. Or, we might like to use the remaining two bits to select a color on a color display. We could get one of four with two bits. Minicomputers tend to use 8-, 9-, 12-, 13-, 16-, 17-, 18-, 24- or 25-bit words depending on the manufacturer and the task the computer is aimed at. So, for system's use, you pick the number of bits needed to do the job.

On the other hand, if you are a integrated circuit manufacturer, you want to have the most reasonable package in your system. The majority of semiconductor memories only have ONE input line and ONE output line and address lines for one-of-N decoding, giving you organizations such as 256 one-bit words 1024 one-bit words, 4096 one-bit words, and so on. Occasionally a smaller memory may have four bits per word, to make working with BCD numbers easier. Other arrangements are rarely used and you usually add packages to pick up the total number of bits you want.

### Decoding

All organizations in Fig. 3 have binary to one-of-N decoders on the address lines. If this decoder is internally provided in the integrated circuit as it almost always is, we have an *internally decoded* memory. If we must provide external address decoding as is common with magnetic cores, we need *external decoding*. External decoding is also needed when you have several memory packages that you are combining for a total storage. In this case, you use *output enable*

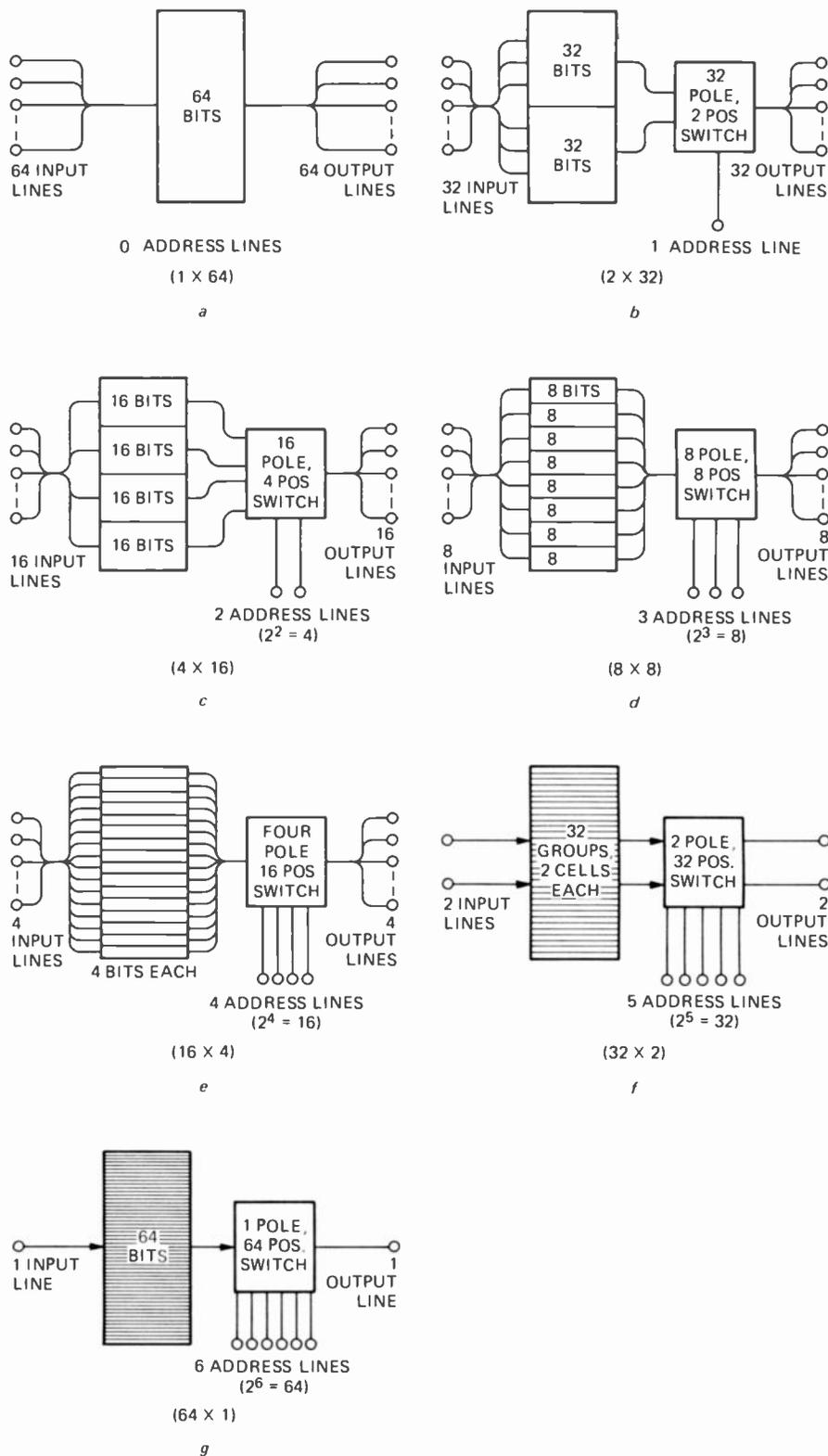


FIG. 3—WAYS OF ARRANGING or organizing a 64-bit memory.

or *chip select* lines to pick which package is to be used. Once selected, each individual package then goes on to provide internal decoding. For instance, with two IC's we could simply tie their inputs and outputs together and drive the first memory's chip select as an address line and drive the second memory's chip select from the *complement* of that line. Thus, we pick one-of-two memory IC's and the chip selects give us a new form of addressing. If we tie four memories together, we use two new address lines, one-of-four decode them


and then chip select only one memory at a time. Figure 4 shows how you can expand memories using the chip select system.

Unlike magnetic cores and many older memory systems, the data input and output lines are completely separate with most new semiconductor RAM's. This eliminates amplifier recovery problems, steering networks, "single port" problems and things like this.


### Who makes what?

Figure 5 is a list of my choice of the best

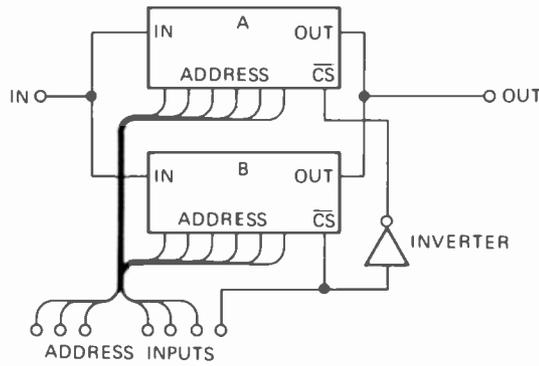HERE WE USE A NEW ADDRESS LINE AND AN INVERTER TO SELECT ONE OF TWO MEMORY IC'S. IF A AND B ARE ORGANIZED AS 64 X 1, NEW MEMORY IS 128 X 1.



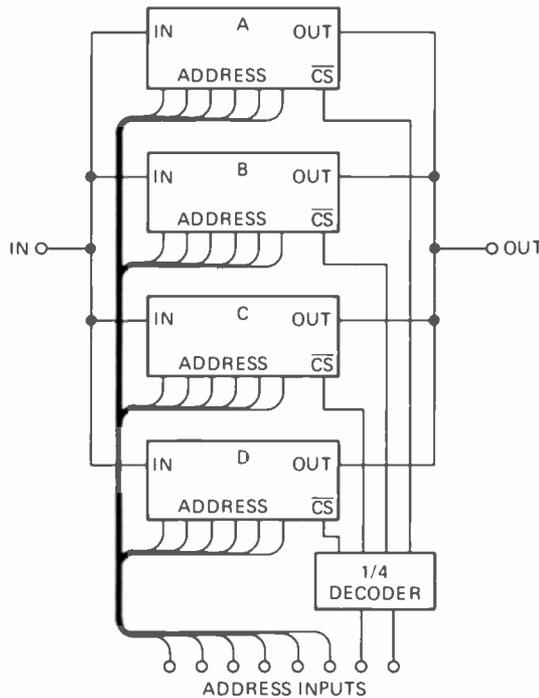WITH TWO NEW ADDRESS LINES AND A ONE-OF-FOUR DECODER, WE CAN QUADRUPLE A MEMORY BY USING FOUR IC'S. ONLY ONE MEMORY IS ENABLED AT A TIME. IF A, B, C, AND D ARE 64 X 1 MEMORIES, SYSTEM IS A 256 X 1 MEMORY.



ANY NUMBER OF IC'S CAN BE USED BY ADDING NEW ADDRESS INPUTS AND 1-OF-N DECODING THEM.

FIG. 4—MORE THAN ONE IC can be used in a memory by using the chip-select as a new address input. Everything is connected in parallel, but only one IC is enabled at any time.

NUMBER	BITS	TECHNOLOGY	ORGANIZATION	SUPPLY	MANUFACTURER*
7474	2	TTL	2x1 OR 1x2	+5.0	TEXAS INSTS.
74175	4	TTL	1x4	+5.0	TEXAS INSTS.
74174	6	TTL	1x6	+5.0	TEXAS INSTS.
7489	64	TTL	64x4	+5.0	TEXAS INSTS.
25L01	256	P MOS	256x1	+5,-12	SIGNETICS
2102	1024	N MOS	1024x1	+5.0	INTEL

\*PARENT COMPANY—MANY SECOND SOURCES  
FIRST NUMBER IN ORGANIZATION IS NUMBER OF WORDS; SECOND IS NUMBER OF BITS PER WORD.

FIG. 5—SIX IC's and their basic specifications.

ADVANCED MEMORY SYSTEMS 1276 Hammerwood Avenue Sunnyvale, California, 94086	INTERSIL MEMORY CORPORATION 10900 North Tantau Avenue Cupertino, California, 95014	NATIONAL SEMICONDUCTOR 2900 Semiconductor Drive Santa Clara, California, 95051
AMERICAN MICROSYSTEMS INC. 3800 Homestead Road Santa Clara, California, 95051	MICROSYSTEMS INTERNATIONAL Box 3529-C Ottawa, Canada, K1Y4J1	SIGNETICS 811 East Arques Avenue Sunnyvale, California, 94086
ELECTRONIC ARRAYS 501 Ellis Street Mountain View, California, 94040	MOSTEK 1215 West Crosby Road Carrollton, Texas, 75006	TEXAS INSTRUMENTS Box 5012 Dallas, Texas, 75222
INTEL CORPORATION 3065 Bowers Avenue Santa Clara, California, 95051	MOTOROLA SEMICONDUCTOR Box 20912 Phoenix, Arizona, 85036	

FIG. 6—IC MEMORY MAKERS. Write for information you need.

current bets for experimental memory use. These are easy to use, widely available and low in cost. Leading memory manufacturers are shown in Fig. 6. As with any semicon-

ductor work, always have the exact data sheet and as much as you can get in the way of applications information before you begin any work with semiconductor RAM's.


There are lots of different ways to classify semiconductor RAM's. One grouping is based on the process used. Bipolar RAM's include TTL and ECL logic. MOS versions include P-channel (metal and silicon gate), N-channel, and CMOS types. In the past, MOS devices have almost always been slower and much cheaper. Some MOS memories are now as fast as TTL and most MOS devices will continue to be cheaper than bipolar for some time to come.

MOS memories are further broken down into static and dynamic versions. Dynamic versions are much cheaper and much harder to use, particularly in experimental or very small system applications.

Let's take a closer look at some specific IC's:
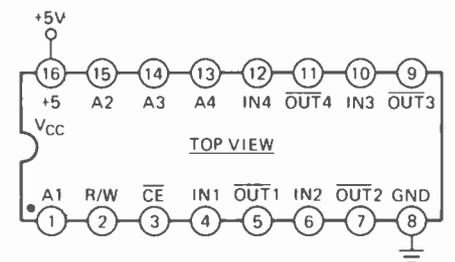
### 7489

The 7489 is a good choice for initial experiments with RAM's. It is TTL and works off a single 5-volt supply. Organization is 16 words of four bits each as shown in Fig. 7.



CHIP ENABLE LOW ENABLES MEMORY  
CHIP ENABLE HIGH INHIBITS MEMORY  
R/W LOW WRITES  
R/W HIGH READS

FIG. 7—THE 7489 IS A 64-BIT TTL memory organized as 16 x 4 or 16 words of 4 bits each (16 4-bit words). It needs a single +5-volt supply. Output information is a compliment of the input.

There are four data inputs and four data outputs along with four address lines. The address lines are four-line-to-one-of-sixteen decoded internally. Internal circuitry is arranged so that you store and read out the compliment of the input information.

To read this memory, you apply a four-bit address to pick the slot you want to look at and then bring the memory enable line low. For instance, address 0101 selects the fifth group of four cells. Data appears at the output shortly after the address is stable.

To write into the 7489, pick an address, input the compliment of the data you want to store and then briefly bring the write enable low. This loads the memory.

One thing you have to watch very carefully in any semiconductor memory is that the address cannot be changed immediately before, during or immediately after a write command. (The definition of "immediately" varies with the IC—carefully consult the data sheets!) As a memory address changes, certain locations are "flushed" by in the decoding process. It is possible to write, erase or physically move data around if you aren't careful. ALWAYS PULSE THE WRITE COMMAND ON ANY SEMICONDUCTOR MEMORY. NEVER CHANGE ADDRESSES DURING WRITE PULSING! Put another way, always leave the memory in a disable or a read mode. Don't put into write mode until after the address is stable.

This particular memory cycles in under 50  
(continued on page 78)

Hunting for  
a better job?

CIE will  
help you get  
the license  
you need



**A Government FCC License can help you qualify for an exciting, rewarding career in ELECTRONICS, the Science of the Seventies. Read how you can prepare for the license exam at home in your spare time — with a passing grade assured or your money back.**

**I**F YOU'RE OUT TO BAG A BETTER JOB in Electronics, you'd better have a Government FCC License. It will help you track down the choicest, best-paying jobs in the growing field of Electronics.

Demand for people with technical skills is growing twice as fast as any other group, while jobs for the untrained are rapidly disappearing. Right now there are thousands of new openings every year for electronics specialists. And you don't need a college education to qualify!

But you *do* need knowledge, knowledge of electronics fundamentals. And there is only one nationally accepted method of measuring this knowledge . . . the licensing program of the FCC (Federal Communications Commission).

**Why a license is important**

An FCC License is a legal requirement if you want to become a Broadcast Engineer, or get into servicing any other kind of transmitting equipment — two-way mobile radios, microwave relay links, radar, etc. And even when it's not legally required, a license proves to the world that you understand the principles involved in *any* electronic device. Thus, an FCC "ticket" can open the doors to thousands of exciting, high-paying jobs in communications, radio and TV broadcasting, the aerospace program, industrial automation, and many other areas.

So why doesn't everyone who wants a good job in Electronics get an FCC License?

It's not that simple. You must pass a Government licensing exam. A good way to prepare for your FCC exam is to take a licensing course from Cleveland Institute of Electronics.

Our training is so effective that, in a recent survey of 787 CIE graduates, better than 9 out of 10 CIE grads passed the Government FCC License exam. That's why we can offer this famous Money-Back Warranty: when you complete any CIE licensing course, you'll be able to pass your FCC exam or be entitled to a full refund of all tuition paid. This warranty is valid during the completion time allowed for your course. You get your FCC License — or your money back!

And with CIE, you learn at home in your spare time. With AUTO-PROGRAMMED\* Lessons, you'll pick up the facts, figures and electronics theories you

**CIE HAS CAREER COURSES TO FIT YOUR BACKGROUND**

**ELECTRONICS TECHNOLOGY with LABORATORY** . . . teaches you the fundamentals. With a 161-piece laboratory you apply the principles you learn by analyzing and trouble-shooting electronics equipment.

**ELECTRONICS ENGINEERING** . . . A college-level course for men already working in Electronics. Covers steady-state and transient network theory, solid-state physics and circuitry, pulse techniques, computer logic and mathematics through calculus.

may have considered "complicated" . . . even if you've had trouble studying in the past.

**CIE Grads get licenses . . . better jobs**

The value of CIE training has been demonstrated time and again by the achievements of our thousands of successful students and graduates.

An outstanding example is Ed Dulaney of Scottsbluff, Nebraska. He passed his 1st Class FCC License exam soon after completing his CIE course. Today, he owns two companies . . . one to manufacture and distribute two-way radio equipment, the other to maintain and repair such equipment along with home radio, TV and stereo sets. He says: "In the last three years we sold more than \$1,500,000 worth of equipment through dealers in every state plus Canada, South America and Europe."

Richard Kihn, Anahuac, Texas, worked in the engine room of a tugboat when he started his CIE training. He reports, "Before finishing, I got my FCC License and landed a job as broadcast engineer at KFDM-TV in Beaumont, Texas. I was able to work, complete my CIE course and get two raises . . . all in the first year of my new career in broadcasting."

**Send for FREE books**

If you'd like a chance to succeed like these men, send for our FREE book, "How To Get A Commercial FCC License." It tells you all about the FCC License . . . requirements for getting one . . . types of licenses available . . . how the exams are organized and what kind of questions are asked . . . where and when the exams are held, and more.

With it, you will also receive a second FREE book, "Succeed in Electronics." For your convenience, we will try to have a representative call. Send for both books today.

**APPROVED UNDER G. I. BILL**

All CIE career courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.

**CIE Cleveland Institute of Electronics, Inc.**

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

**Cleveland Institute of Electronics, Inc.**

1776 East 17th Street, Cleveland, Ohio 44114

Please send me your two FREE books:

1. Your book on "How To Get A Commercial FCC License."
2. Your school catalog, "Succeed in Electronics."

I am especially interested in:

- |   |  |
|---|--|
| <input type="checkbox"/> Electronics Technology                 | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering                  | <input type="checkbox"/> Industrial Electronics    |
| <input type="checkbox"/> First Class FCC License                | <input type="checkbox"/> Electronics Engineering   |
| <input type="checkbox"/> Electronics Technology with Laboratory |  |

Name \_\_\_\_\_  
(PLEASE PRINT)

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Age \_\_\_\_\_

**Veterans and Servicemen:**

- Check here for G.I. Bill information.

RE-34

# Using COSMOS

Are you up on COSMOS, the latest in solid-state technology?

DIGITAL INTEGRATED CIRCUITS HAVE BEEN available for a good many years now and most readers will be familiar with common family logic names like RTL (Resistor-Transistor Logic), DTL (Diode-Transistor Logic), TTL (Transistor-Transistor Logic) and ECL (Emitter-Coupled Logic). Each of these families offers its own particular advantages when compared to the other types, but all the families share a number of common disadvantages.

The chief disadvantages of the more common logic families are, (1), high quiescent current requirements (typically 5 mA per gate), (2), tight power supply requirements (power supplies typically have to be regulated to  $\pm 10\%$ ), (3), low input impedances (typically a few hundred ohms per gate) and (4), poor noise immunity (meaning that gates can be easily triggered by spikes on the supply lines).

Recently, a new and rather amazing type of digital IC has appeared on the scene and seems set to push all the other families into rapid obsolescence in low- to medium-speed applications. This new family of devices are known as COSMOS or CMOS (Complimentary Metal Oxide Silicon) digital IC's and suffer from none of the disadvantages of the earlier families.

Typically, COSMOS draws the incredibly low quiescent current of only 0.001  $\mu$ A per gate and can be used with unstabilized power supplies giving voltages anywhere in the range 5 to 15 volts (special versions of COSMOS can operate as low as 1.3 volts). Each COSMOS logic gate has an input impedance of about a million megohms, but is fully protected against damage by static charges via built-in safety circuitry.

COSMOS has inherently good noise immunity and can safely tolerate input spikes up to nearly 50% of the supply voltage without being upset. Finally, COSMOS has excellent thermal characteristics: low-cost "commercial" types of COSMOS are designed to operate over the temperature range  $-40^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ , while the more expensive military versions can operate from  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ .

The performance of COSMOS is so unbelievable that we have decided, in this series of articles, to PROVE just how good it really is by presenting forty practical projects that you, the reader, can build around a single low-cost COSMOS digital IC. These projects range from simple pulse inverters to high-output multi-input burglar alarms, etc. The IC that forms the basis of these forty circuits is a quad 2-input NOR gate and is available from a number of advertisers in this magazine at a cost of less than one dollar.

Before going on to look at the first of these practical projects, however, let's digress a little and find out just why COSMOS is so good. You might also check the article "All About CMOS" by Don Lancaster in *Radio-Electronics* December 1973.

## Understanding COSMOS IC's

The simplest type of digital circuit that you get in any logic family is the inverter or NOT gate. The symbol for a NOT gate is in Fig. 1-a and its resistor-transistor equivalent is in Fig. 1-b. Circuit operation is quite sim-

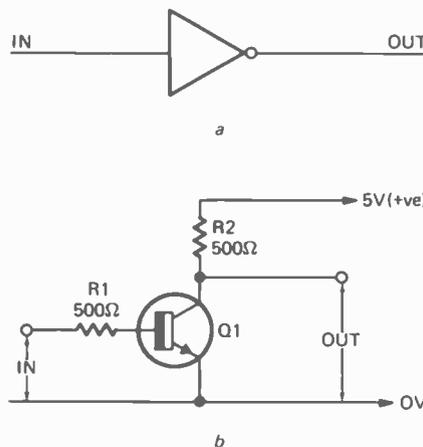


FIG. 1-a—THE SYMBOL of a digital inverter or NOT gate. b—RESISTOR-TRANSISTOR equivalent circuit.

ple. Input and output are always either low (grounded or at logic 0) or high (at positive supply voltage or logic 1). Suppose that the input to the circuit is at logic 0. In this case, zero base drive is applied to transistor Q1, so the transistor is cut off and the output is at logic level 1. In this case, the quiescent current of the circuit is equal to the leakage current of the transistor and is virtually zero.

Suppose now that the input to the Fig. 1 circuit is set to the high or logic 1 level. In this case, heavy base drive is applied to Q1 via R1, so the transistor is driven to saturation and the output falls to logic level 0. Under this condition, the quiescent current of the circuit rises to about 10 mA. Also note that the output of this simple circuit is always inverted relative to the input.

A simple manually-triggered 'memory' circuit can be made up from two NOT gates by cross-coupling them as shown in Fig. 2. If we press S1, we set the input of Q2 to logic 0 so the output of Q2 goes to logic 1 and drives Q1 on and thus reduces the Q1 output to logic 0. Because of the cross-coupling, the circuit stays locked in this state once S1

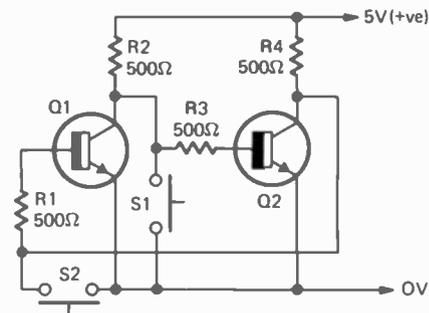


FIG. 2—SIMPLE MANUALLY TRIGGERED resistor-transistor "memory" circuit draws a quiescent current of 10 mA.

is released so the circuit acts as a simple memory. The state of the memory can be changed, if required, by momentarily closing S2, in which case the output of Q1 goes to logic 1 and the output of Q2 goes to logic 0. The important point to note here is that one or other of the transistor NOT gates is switched hard on (saturated) at all times, irrespective of the state of the memory, so the circuit draws a constant quiescent current of 10 mA.

So much for resistor-transistor logic. Let's now go on and see what happens in its COSMOS equivalent.

Figure 3 shows the basic circuit of a COSMOS inverter or NOT gate. The circuit

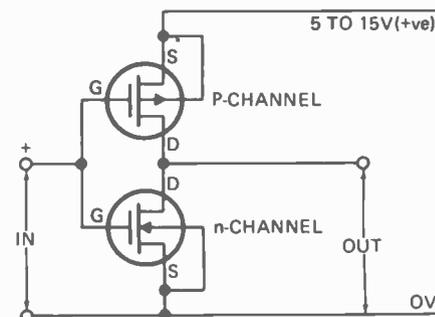


FIG. 3—BASIC COSMOS digital inverter or NOT gate.

consists simply of one p-channel and one n-channel insulated-gate field-effect transistor (IGFET), wired in series between the two supply lines, with the IGFET gates tied together at the input terminal and with the output taken from the junction of the two devices.

Essentially, an IGFET can be regarded as a 3-terminal voltage-controlled variable resistance. The variable resistance appears between the two terminals known as the source and the drain, and the control voltage is applied between the source and the third

# Digital IC's

If not, learn what its about with these simple circuits.

terminal, known as the gate. The gate typically presents an impedance of about a million megohms to incoming voltages or signals, so the IGFET can be regarded as a voltage (rather than current) controlled device.

When a very low (near-zero) voltage is applied to the IGFET gate, the drain-to-source path of the device acts like an open-circuit resistance and typically presents an impedance in the order of thousands of megohms. Near-zero current thus flows through the device under this condition. If the gate voltage is steadily increased, a point is reached where the drain-to-source resistance just starts to fall: this point is known as the THRESHOLD and threshold voltages are usually between 2 and 3 volts in COSMOS IGFET's.

As the gate voltage is increased beyond the threshold, the drain-to-source resistance falls further and eventually falls to a minimum effective value of about 400 ohms: the resistance cannot fall below this value no matter how much further the gate voltage is increased, so a safe limit is automatically set on the maximum current that can flow through the device.

Let's go back to our Fig. 3 circuit in which we are concerned mainly with input signals that are *low* (below the threshold of the n-channel IGFET but above that of the p-channel device) or *high* (above the threshold of the n-channel IGFET but below that of the p-channel device).

Suppose first that we have a logic 0 (low) input to the circuit. In this case, the n-channel (lower) IGFET is cut off and is acting like a virtual open-circuit resistor with an impedance of about 10,000 megohms, but the p-channel (upper) IGFET is biased hard on and acts like an impedance of only 400 ohms.

This situation is clearly illustrated in the

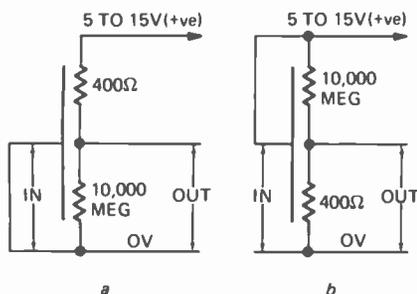


FIG. 4—EQUIVALENT CIRCUIT OF COSMOS NOT gate circuit with (a) logic 0 input and (b) logic 1 input.

equivalent circuit of Fig. 4-a where it can be seen that the two IGFET's act like a resistive voltage divider in which the output is high

(at logic 1) and is essentially strapped to the positive supply line via the 400-ohm resistance and in which the quiescent current of the divider is limited to the nanoamp region by the high value of the 10,000-megohm resistor.

Suppose now that the input voltage is slowly increased in a positive direction. The device current is virtually zero until the input voltage exceeds the threshold of the n-channel IGFET, at which point the effective resistance of the n-channel device starts to decrease and that of the p-channel IGFET starts to increase. Under this condition, the device current is dictated by the larger of the two resistances and is of measurable proportions.

When the input voltage is appreciably *less* than half of the supply volts, the resistance of the n-channel IGFET is much greater than that of the p-channel device, so the output of the circuit is high or at logic level 1: when the input voltage is appreciably *more* than half of the supply volts, the resistance of the n-channel IGFET is much less than that of the p-channel device, so the output of the circuit is low or at logic level 0.

When the input voltage is at approximately half-supply volts, a point is reached where both IGFET's attain the same value and at this point the output voltage starts to switch from one logic level to the other and a current of several milliamps may flow through the circuit: in practice, a semi-regenerative switching action takes place at this point and the output switches abruptly from one state to the other.

The value of input voltage needed to initiate this switching action is known as the TRANSITION voltage and is usually specified as a percentage of the supply voltage. Transition voltages vary between 30% and 70% of the supply voltage in COSMOS devices.

Finally, consider the case where the input to the Fig. 3 circuit is high or at logic 1. In this case, the p-channel IGFET is cut off and acting like a virtual open circuit while the n-channel IGFET is biased hard on and is acting like a 400-ohm resistor. This situation is shown in Fig. 4-b where it can be seen that the two IGFET's again act like a voltage divider, but in this case the 400-ohm resistor is at the low end, so the output is low (at logic 0) and is essentially strapped to ground via 400 ohms. The quiescent current of the network is again limited to the nanoamp region by the larger of the two resistors.

Thus, the Fig. 3 circuit acts as a conventional digital inverter or NOT gate, but has the following unique properties:

1. An exceptionally high input impedance (about a million megohms).

2. It draws negligible quiescent current from the supplies (about one nanoamp), irrespective of its logic state.

3. It can be operated from a wide range of supply voltages (typically 5 to 15 volts), since its minimum voltage requirement is limited only by the threshold characteristics of its IGFET's and the maximum is limited only by the breakdown characteristics of the devices.

4. Its output can swing from zero to the full positive supply rail voltage since no potentials are lost in the circuit as a result of saturation voltages or forward biased junction voltages.

5. The device cannot be damaged by shorts at its output since the maximum current of the device is automatically limited by the 400 ohms minimum impedance of its ON IGFET.

Figure 5 shows how two COSMOS NOT

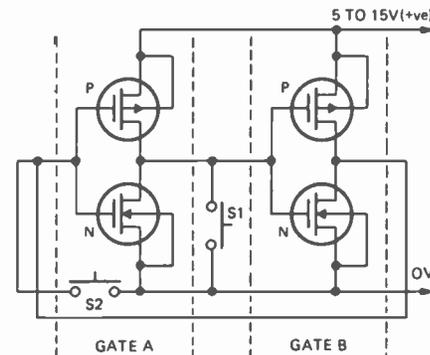


FIG. 5—MANUALLY TRIGGERED COSMOS "memory" circuit draws a quiescent current of .002  $\mu$ A.

gates can be cross-coupled to form a simple manually-triggered memory circuit. This circuit operates in a similar way to that of Fig. 2. When S1 is momentarily closed, the input to gate B is set at logic 0, so the output of gate B goes to logic 1 and in turn drives the output of gate A to logic 0.

The circuit remains in this state when S1 is released due to the cross-coupling between the two gates, so the circuit acts as a simple memory. The state of the memory can be changed by momentarily closing S2, in which case the output of gate A goes to logic 1 and the output of gate B goes to logic 0.

The most important practical difference between the resistor-transistor memory circuit of Fig. 2 and the cosmos circuit of Fig. 5 is that the resistor-transistor circuit draws a quiescent current of 10 mA while the cosmos version draws a quiescent current of only 0.002  $\mu$ A. Thus, the resistor-transistor version draws five million times

more quiescent current than its COSMOS equivalent.

The reader may at this stage be thinking that this notion of a logic circuit drawing virtually zero supply current sounds too good to be true and that there must be a catch in this COSMOS business somewhere. The simple answer to that is that a COSMOS circuit does in fact draw a significant current, but only as it is going through the actual motion of changing logic states and not when it is in the quiescent condition.

Each time COSMOS changes state, it draws a pulse of current from the supply. The more often it changes state in a given time, the greater are the number of current pulses that it takes from the supply and the greater is the MEAN current that it consumes. Thus, the mean current that it takes is directly proportional to the frequency of its operation.

At frequencies of 5 MHz, COSMOS logic draws roughly the same current as its TTL equivalent: at 5 kHz, it draws only one-thousandth of the current of TTL. Consequently, COSMOS is best suited to low- or medium-speed applications, although it is capable of operating as high as 10 MHz when needed.

Having cleared up these basic points, let's go on and look at a practical COSMOS digital IC.

### The CD4001

Several manufacturers produce ranges of COSMOS digital IC's. Leaders in the field are RCA, and one of the most useful and versatile IC's in their range is a quad 2-input NOR gate which is known as the CD4001: Motorola produces an identical device under the coding of MC14001.

Figure 6 shows the logic circuit and pin

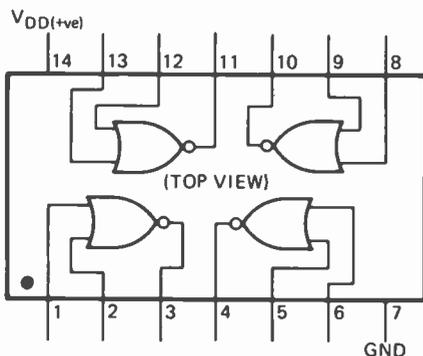


FIG. 6—LOGIC DIAGRAM and pin connections of the CD4001 quad 2-input NOR gate.

connections of the CD4001 IC which is encapsulated in a 14-pin dual-in-line plastic or ceramic package. As you can see, two of the pins are used for supply connections (pin 7 goes to ground and pin 14 goes to the positive supply line) and the rest of the pins connect to the input or output terminals of the NOR logic gates. There are four identical 2-input NOR logic gates in each IC package.

Figure 7-a shows the actual circuit that is used in each of the 2-input NOR gates. Here, two series-connected p-channel IGFET's are wired in series with two parallel-connected n-channel IGFET's: each of the two input terminals is connected to the gates of one of the p- and n-channel IGFET pairs. Circuit operation is as follows.

Suppose first that both input terminals are grounded or at logic level 0. In this case, both of the n-channel IGFET's are biased

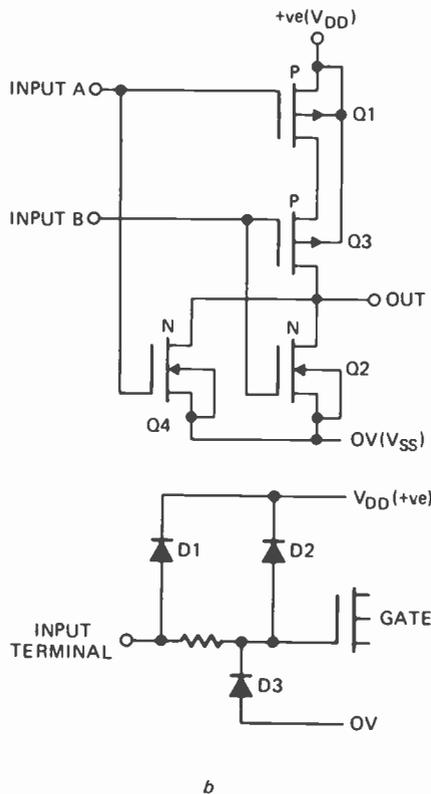


FIG. 7-a—CIRCUIT OF EACH of the four gates of the CD4001. b—COSMOS GATE INPUT protection circuit that is connected to each of the eight input terminals of the CD4001.

below their threshold points and act like open-circuit resistors and both of the p-channel IGFET's are saturated and act like 400-ohm resistors. The output of the circuit is thus high and at logic level 1 under this condition. The output is thus inverted relative to the inputs.

Suppose now that input A is at logic level 1 and that input B is at logic 0. Now Q2 acts like an open-circuit resistor and Q3 acts like 400 ohms due to the 0 input on terminal B, but Q1 acts like an open-circuit resistor and Q4 acts like 400 ohms due to the 1 input on terminal A. Since Q1 is in series with Q3 and Q2 is in parallel with Q4, the result is that the top half of the circuit acts like an open circuit and the lower half acts like 400 ohms. Consequently, the output of the circuit is low and at logic 0 under this condition.

Suppose next that input A is at logic level 0 and input B is at logic 1. This situation is similar to that outlined above except that in this case, Q3 and Q4 act like open circuits and Q1 and Q2 act like 400-ohm resistors. The net result is the same, however, and the top half of the circuit acts like an open circuit and the lower half acts like 400 ohms, so the output of the circuit is again at logic 0 under this condition.

Finally, suppose that both inputs are at logic level 1. In this case, both upper IGFET's act like open circuits and both lower IGFET's act like 400-ohm resistors, so the output is again low at logic level 0.

Thus, the output of the NOR gate goes to logic 1 only when both inputs are at logic 0. Note that the circuit can be made to function as a simple logic inverter or NOT gate by shorting inputs A and B together.

All input terminals of the CD4001 NOR gate IC (and all other digital IC's in the

COSMOS family) have input impedances of about a million megohms, but are fully protected against damage from static charges via the input safety circuit shown in Fig. 7-b. Each of the eight input terminals of the CD4001 are protected by one of these diode-resistor safety circuits.

The CD4001, like all COSMOS digital IC's, is an extremely rugged device and can withstand considerable abuse without suffering permanent damage. Its output, for example, is fully short-circuit proof. There are in fact only three ways in which you can damage a COSMOS circuit and one of these is to connect the supply lines in the wrong polarity, in which case heavy current will flow through the D2 and D3 protection diodes and damage the substrate.

One other way you can damage the device is to connect a very low impedance input signal to it when its power supplies are switched off and the remaining way is to connect the device to a very low impedance input signal that has such a large amplitude that it goes above the positive supply line voltage. In either case, a heavy current will flow through protection diode D1 and the substrate will again be damaged. Both of these potential sources of damage can be eliminated by simply wiring a 1000-ohm resistor in series with each input terminal so that any current that does flow is limited to a safe value of a few milliamps.

### Using the CD4001

The CD4001, like all other COSMOS digital IC's, is a very easy device to use, providing you obey the following basic rules.

1. Always make sure that power lines are in the correct polarity before you apply power to the IC.
2. Never connect very low impedance energy sources (including storage capacitors) directly to the device input terminals: always connect them via a 1000-ohm or greater current-limiting resistor.
3. Always tie unused input terminals directly to ground or to the positive supply line, depending on the logic requirements.
4. Never let used inputs float: always take them to ground or to the positive line via a high value resistance.

When you buy your first CD4001 IC, you'll find that it has a one-or-two-letter suffix added at the end of its basic code number. This suffix relates to the style of packaging of the device and to its voltage and temperature operating ranges. Details of the meanings of the five available suffix codes are shown in Table 1. Thus, the CD4001AD is a quad 2-input NOR gate housed in a ceramic dual-in-line package and can operate over the supply range 3 to 15 volts and the temperature range  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ , while the CD4001E is in a plastic DIL package and can only operate over the supply range 5 to 15 volts and the temperature range  $-40^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ .

Most of the forty practical projects described in the remaining sections of this series of articles are designed to operate with supply voltages in the range 5 to 15 volts and can thus be used with any types of CD4001 IC. In most cases, however, the circuits can be made to operate with supply voltages as low as 3 volts by simply using them with CD4001 IC's that have suffix numbers AD, AE or AK.

Next month we will go on and look at the first of our 40 IC projects. RE

# HOW TO

## Measure Hi-Fi Amplifier Performance

*Checking hi-fi component performance is a job that requires precise measurements with lab-grade test equipment. Our audio consultant describes his test gear and how it's used.*

by **LEN FELDMAN**  
CONTRIBUTING HIGH-FIDELITY EDITOR

HIGH-FIDELITY COMPONENTS HAVE reached a level of perfection which would have seemed impossible even for so-called professional sound equipment just a few years ago. Frequency response of audio amplifiers extends well below and above human audibility. Recognized forms of distortion such as IM and harmonic have been reduced in modern solid-state amplifiers to percentages so low as to defy measurement using the very best test equipment available just a few years ago. Power output of solid-state amplifiers is fast approaching kilowatt levels.

Whether or not you agree that these last orders of refinement are worth the money the consumer pays for them is secondary. Admittedly, there are experts in the field who steadfastly maintain that harmonic distortion of less than 0.5% contributes no further improvement to audible fidelity and that the ability of an amplifier to reproduce frequencies below 20 Hz or above 20 kHz is equally academic. Still, in the real world of the knowledgeable audiophile, there *are* consumers who are willing to pay for the ultimately low distortion figures and the wideband response. More important, these same consumers want continued assurances that their equipment is performing as well as when it was purchased. The fully equipped audio service center or laboratory of a few years ago is just not capable of accurately measuring and reporting on the important audio parameters of a modern hi-fi amplifier or preamplifier, however heavy the initial investment in test equipment many have been.

Take my own case. In addition to engaging in fundamental audio and rf design from time to time, I regularly test and report on a variety of audio products and occasionally am commissioned to confirm the performance of new prototype products which manufacturers submit to my laboratories.

### Distortion measurements

Up until recently, the measurement of harmonic distortion or power output capability of an amplifier on my lab bench involved the use of at least four

separate pieces of equipment, arrayed in the photo of Fig. 1. These included a Hewlett-Packard 650A signal generator, an HP 330A harmonic distortion analyzer, a Tektronix dual trace wideband oscilloscope, model 533, a pair of Ballantine ac vtvm's and, of course, suitable non-inductive loads of proper 8-ohm or 4-ohm impedances. The block diagram of Fig. 2 illustrates the usual setup. Since line voltage invariably affects power output capability of an audio amplifier, a variable voltage transformer and an accurately calibrated ac line voltmeter are also part of this elaborate measurement setup.

Since a fully equipped high-fidelity laboratory must also be capable of measuring the performance of FM tuner sections, a variety of additional equipment is arrayed across the test bench as shown in Fig. 3 and additional items are detailed in Figs. 4, 5 and 6. The inherent distortion of the HP 650A audio generator was known to be just under 0.1%, but there are amplifiers on the market today which boast THD figures of 0.02% and even lower at nominal power output levels. In addition, to perform a series of THD measurements over the entire audio spectrum involved tedious repeated voltage readings, resetting of frequency at both generator and distortion analyzer and repeated nulling and balancing of the null filter in the analyzer. At best, readings were subject to errors based upon meter and load accuracies. Particularly at maximum power output of an amplifier where an error of 3% in voltage can result in significant power errors, it was difficult to get two successive read-

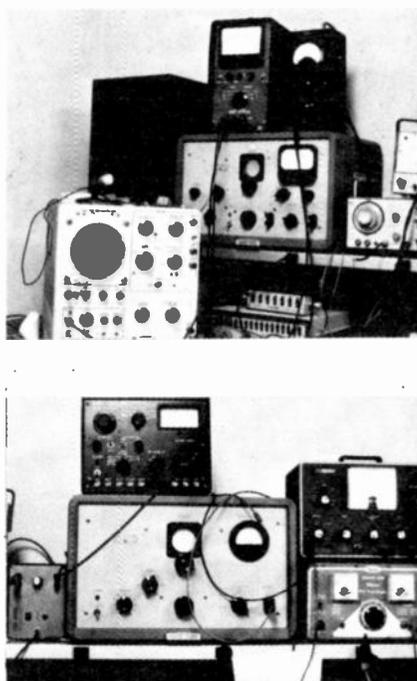


FIG. 1—PHOTOS SHOW MAJOR pieces of equipment used to check audio amplifier performance.

ings to agree. Suppose for example that a given amplifier is rated at 50 watts, driving 8-ohm loads, for less than 0.5% distortion. The amplifier output voltage should be set to 20 volts for this measurement.

$$(W = E^2/Z = 20^2/8 = \frac{400}{8} = 50 \text{ watts}).$$

If the ac vtvm reads 3% too low, a reading of 20 volts would really correspond to an actual output of 20.6 volts which would correspond to an actual power output of 53.05 watts at which output the distortion produced by the amplifier might well exceed several percent. To compound the error, if the loads are on the low side of 8 ohms by 3%, actual power produced would be  $(20.6)^2/7.76 = 54.69$  watts with an even higher distortion reading. Conversely, a high reading meter and a "plus" discrepancy in load resistors would result in an overly optimistic THD reading since the amplifier would then not be driven to its actual full rated output.

### The McAdam audio analyzer

McAdam Electronics of San Diego, California has assembled an "audio lab" in a single box" known as their model 2000A, a front view of which is shown in Fig. 7. The most important innovation of this combination instrument is its digital readout circuitry. In use, even the power line voltage can be monitored digitally and set, by means of the self-contained variable voltage transformer to precisely 120 volts.

In addition to a triggered sweep oscilloscope with maximum vertical sensitivity of .02 volts/cm., a series of high-power Dale load resistors are affixed to the back of the cabinet and are switchable to provide four channel loads at 4, 8 or 16 ohms. Loads of 600 ohms or open circuit are also available from a front panel switch. One of the high-power load resistors can be seen in the photo of Fig. 8. The three major modules developed by McAdam Electronics include the digital readout module (Fig. 9), the distortion analyzer module (Fig. 10) and the audio oscillator module (Fig. 11). This last module produces signals at selected frequencies from 20 Hz to 100 kHz and, in addition to the low-distortion sine waveform (less than .02% THD), square wave signals at each frequency can be generated as well as the 4:1 combination of 60 Hz and 7000 Hz required for IM distortion testing.

The signal is distributed to four jacks, each with its own amplitude trim pot so that quadriphonic amplifiers may be driven uniformly through all four channels. A master volume control permits varying the audio signal from less than 1 mV (for phono or microphone preamplifier input testing) to over 3 volts. Exact amplitude is read on the digital display. Outputs from the

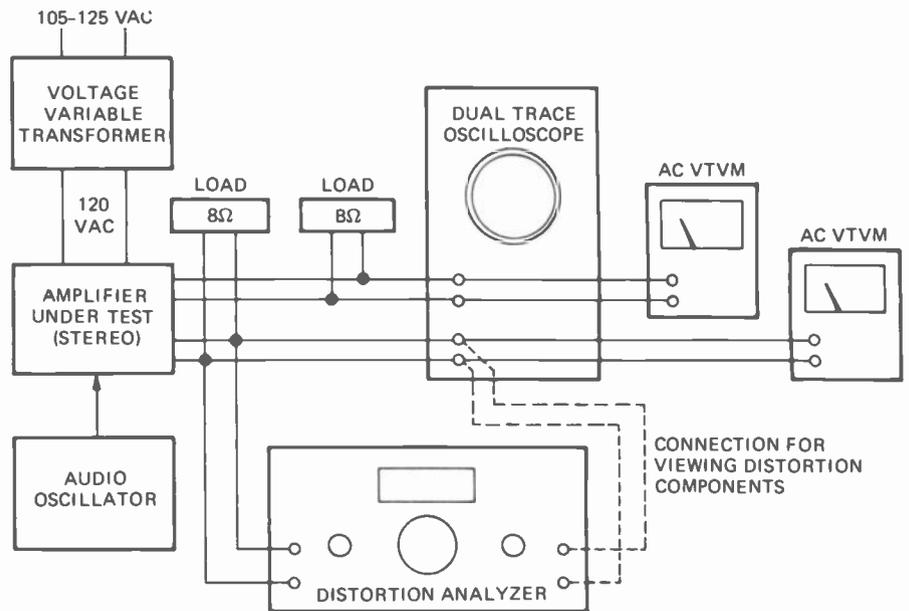


FIG. 2—BLOCK DIAGRAM OF SOME OF THE EQUIPMENT used to check audio amplifier performance specifications.



FIG. 3—OVERALL VIEW OF PORTION OF LAB TEST BENCH suggests amount of test gear required for audio equipment testing.

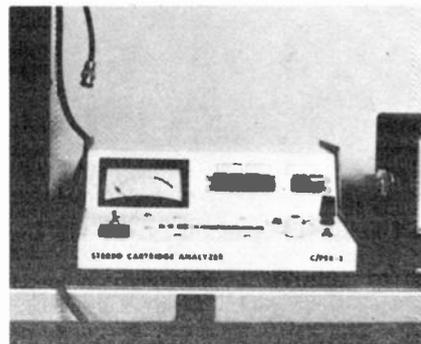


FIG. 4—SHURE CARTRIDGE ANALYZER is helpful in evaluating phono cartridge tracking and performance.

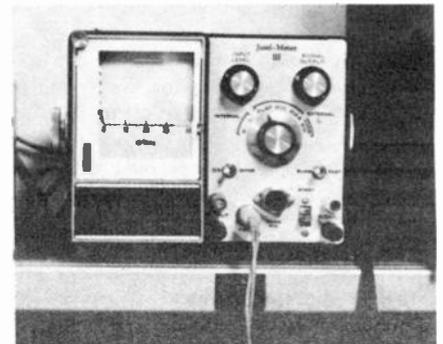


FIG. 5—AUDIO TECHNICA MARKETS COMBINATION graphic recorder useful in making frequency-response plots.

amplifier under test are connected by means of supplied cables to the output terminals on the analyzer. All other connections and interconnections to scope, etc. are accomplished internally and by means of front panel switches. For example, when the selector switch is set to "source," the scope face displays the input and its amplitude is digi-

tally displayed. When "amp" is selected, the output waveform is displayed on the scope and its value may be read directly in watts on the digital readout.

When THD is read, not only does the digital display indicate its value in percent (after 100% reference has been established) but the harmonic distor-

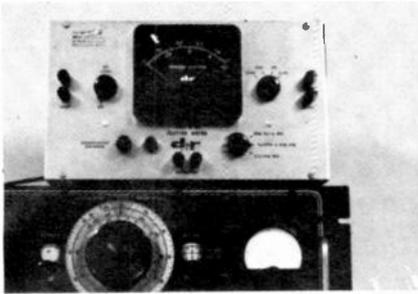


FIG. 6—WOW AND FLUTTER METER used for checking tape decks and turntables shown mounted above a second FM-AM generator.

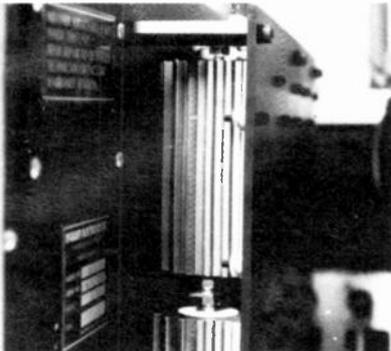


FIG. 8—ONE OF EIGHT high-power precision load resistors mounted on rear of McAdam analyzer.


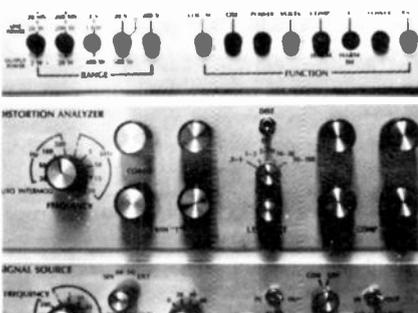


FIG. 10—DISTORTION ANALYZER SECTION has fixed frequency selection which simplifies nulling procedure.

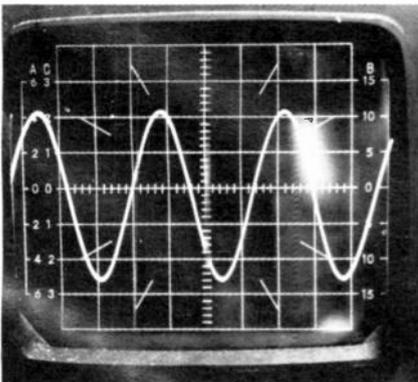

tion content of the waveform being analyzed is shown on the scope as well. Because fixed frequencies are available from the generator, corresponding fixed frequency settings on the distortion analyzer make filter nulling much more rapid than would be the case with continuously variable oscillators and separate distortion analyzers. Two types of nulling are available for making THD readings. The first uses a

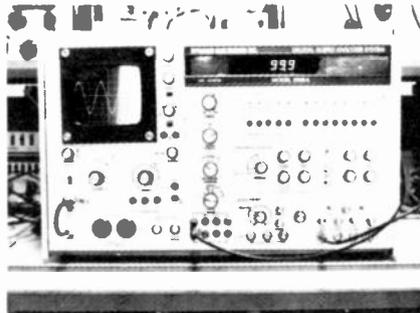


FIG. 7—OVERALL VIEW OF McADAM digital audio analyzer system.

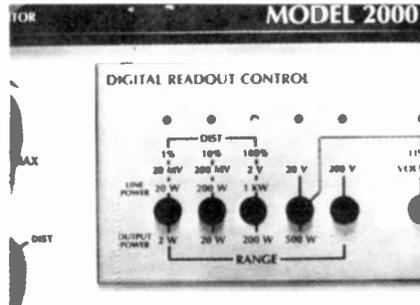


FIG. 9—PUSHBUTTONS ON DIGITAL READOUT control module determine readout range for all digital functions.

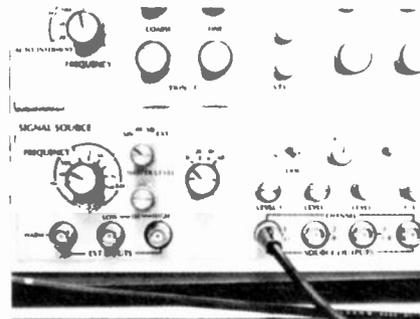


FIG. 11—FIXED FREQUENCIES of oscillator section range from 20 Hz to 100 kHz.

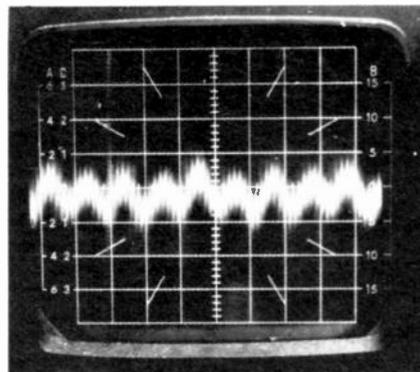


FIG. 12—BJILT-IN SCOPE is switched to view signal source preamplifier output (a, left) or to view actual distortion content of output waveform (b, above).

sharp twin-T nulling network and is nulled in a matter of seconds by means of the four adjustments knobs on the front panel. This filter will permit THD readings down to .02% or better. A more critical-to-adjust nulling system which cancels the signal source's own minute distortion permits readings down to as low as .002% or better and is intended for use with "super spec" equipment under test.

IM distortion readings are almost instantaneous and require no nulling. Percentages are read directly on the digital display module. The makeup of the IM distortion component is also displayed on the scope face when these measurements are made. An example of two scope displays is shown in Fig. 12. Figure 12-a is the output waveform from a high quality amplifier under test at a power output well below chipping. Figure 12-b displays the harmonic distortion of this waveform which, in this case, was just about 0.02% and consisted primarily of 3rd harmonic distortion with lesser amounts of higher order harmonics clearly in evidence despite their virtually unmeasurable amplitude. The presence of the visual display of total harmonic distortion on the scope makes nulling extremely rapid since one can quickly adjust the nulling controls for the smallest amplitude display.

#### Other audio measurements


Input sensitivities, residual hum and signal-to-noise capability of an amplifier product are all easily and directly readable on the digital module. There is even provision for converting the input signal to an RIAA equalized recording curve by means of a switch which hardly attenuates the input signal by 43 dB and also proportions the amplitude of the spot frequencies in accordance with prescribed RIAA bass attenuation and treble emphasis. Thus, when checking a playback preamplifier circuit, flat output response automatically corresponds to correct RIAA equalization while deviation from flat response denotes deviation from RIAA directly.

#### dB's and percentages

The digital readout facility of the analyzer is, of course, strictly an amplitude form of readout. Thus, such readings as involve dB ratios, such as signal-to-noise, hum and even frequency response must be translated from voltage or power amplitudes to decibel notations, if desired. Happily, our lab is equipped with a Hewlett-Packard model 45 pocket calculator which makes these transformations almost instantaneously, but we have also found that by calibrating any reference reading in terms of 100%, as if we were going to make a distortion measurement, it is simpler to "read down" on the digital scales in terms of percentage and translate the residual noise and hum readings to dB from a 100% reference. Thus, 1% equals -40 dB, 0.1% equals -60 dB, etc. Since the lowest or most sensitive scale will read down to 0.001% in this manner, that gives the instrument a potential reading capability down to -100 dB.

(continued on page 94)



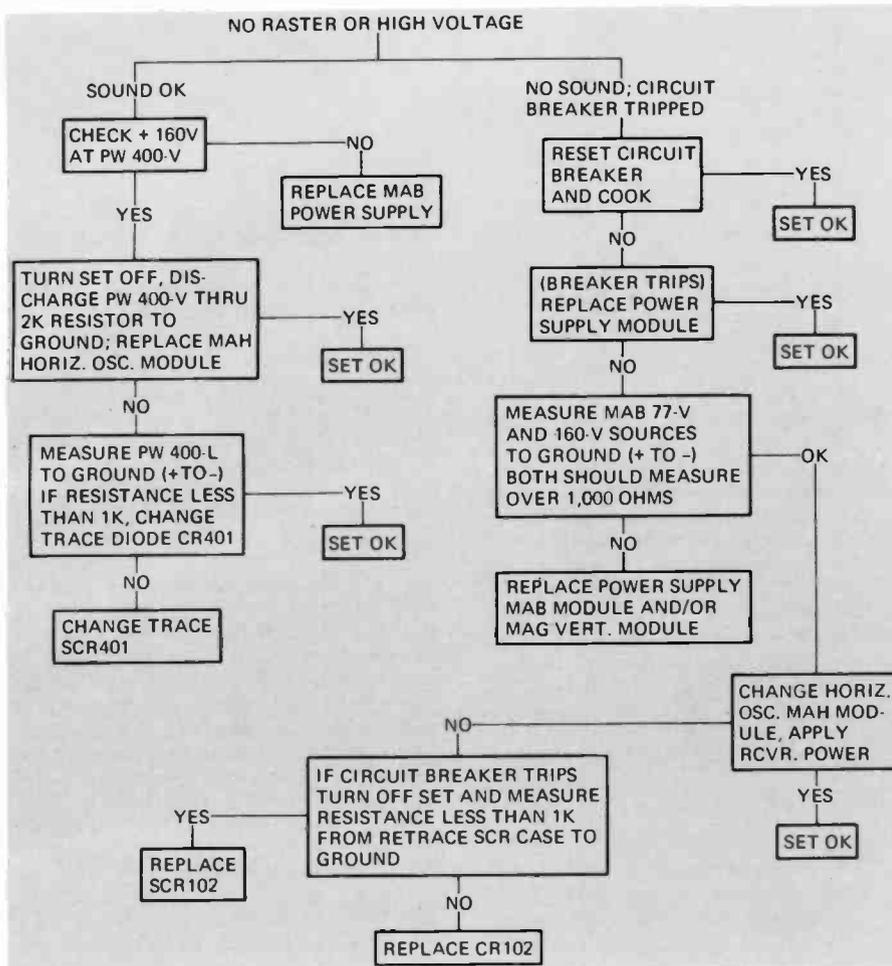

TRUBLESHOOTING CHART (Horizontal Deflection Circuits)

following the sequenced procedure, with and without sound. For if there is sound, the i.f. strip is obviously operating to some extent, even though there may not be adequate because of nonexistent flyback keying. Without sound, a good OFF/ON switch, and a tripped circuit breaker, both 160-volt and 77-volt power supplies are suspect, as well as certain modules. In any event, simply follow directions. The chart and its terminal designations apply to all XL-100 receivers, including the CTC 46, 48, 49, 54, & 59 chassis. The only exception is that PW400-U turns out to be numbered PW400-X on the portable RCA CTC 49 and 59 color television chassis.

Note that in making the resistance measurements indicated on the chart, that the positive ohmmeter test probe is always contacted to the test point and the meter adjustment is always on the R $\times$ 1 scale. Negative test lead is grounded.

#### Other facets

There is also an oscillator hold-down circuit in the later CTC 46 and regular CTC 54 and 48 chassis that can be serviced with this chart method, although the procedure's too short to require a formal drawing. If the horizontal oscillator is out of sync, short TP-2 to ground and adjust the horizontal hold so the oscillator can be brought momentarily into sync—but not held. If this can be done, the sync problem is actually excessive high voltage, and must be remedied by repairing the high-voltage circuit. When TP-1 and TP-2 are shorted together

with the oscillator in sync, it should fall out of sync, and the number of diagonal lines on the screens should change slightly with variations of the brightness control. These are the immediate problems of the moment, and will be illustrated with an oscilloscope following the usual theory of operation.

#### How SCR deflection operates

The trace portion of this SCR horizontal deflection sub-system (Fig. 1) includes the yoke, C120 and C121 in parallel, T405 pincushion transformer, primary turns of flyback T403, and SCR101 or CR401, depending on which is conducting. The retrace portion consists mainly of flyback windings, yoke, pincushion transformer, C120, C121, C406, C403, L108, C122 and R126, and SCR102-CR402. The resonant frequency of the trace circuit is about 10 kHz, and so a 20-kHz half cycle ( $T=1/F$ ) roundly equals the 52.4- $\mu$ s forward scan time. Retrace, then must typically have a resonance of 45 kHz so that its 90-kHz half cycle can equal the 11.1- $\mu$ s recovery time. Power input circuit is then composed of T402, T401, CR403, C404, R403, and SCR101, CR401. The voltage at the junction of L108 and T402 must then rise to maximum during the scan period and even begin decay, depending on the action of the voltage regulator, which senses the high-voltage output and increases or decreases its collector current, saturating or unsaturating T402. This action increases or decreases T402's resonance, causing retrace SCR102 to operate faster or slower and compensate for variations in

high voltage. Output from the retrace SCR, of course, is coupled through T401 and L401 to the gate input of trace SCR101, and turns it on after SCR102 completes conduction.

The two SCR's and their twin diodes are actually bidirectional switches in parallel, but inverse connections. During trace, diode CR401 actually conducts when yoke current is most negative. As this current passes through zero from negative to positive, CR401 (CR101 on some receivers) turns off and SCR101 draws current, discharging capacitors C120 and C121 and supplying energy to the yoke in the second half of forward trace, linearly deflecting the trace to the right edge of the CRT. As this period comes to an end, commutating (retrace) SCR102 gates ON from horizontal oscillator pulses and C406 discharges through L108. Discharge current increases until yoke current is exceeded, turning on CR401 which back-biases trace SCR101 so it can turn off. As the discharge pulse decreases below yoke current, CR401 opens and the yoke now has the current to charge C406 and C407, plus C122 during the initial half of retrace. In the second portion of retrace (or ringing period), CR402 (CR102 in other receivers) conducts, allowing the retrace SCR to turn off, and so begins a new cycle. CR104 is the screen control voltage supply positive rectifier, while CR403 will conduct when voltages on its anode exceed dc or rms 160 volts.

#### Problems & waveforms

The problem RCA technicians can have is not with the SCR circuit itself, but with shotgun parts substitutions by people who are careless. For instance, begin disturbing time constants in this circuit by swapping C406 for C404, and you'll have a slower CR401 turn off, a quicker pulse couple for SCR101, and the circuit begins to see all sorts of problems.

The waveform, at a time base of 20  $\mu$ s per divisor, illustrates approximately three cycles of conduction and non-conduction of these trace and commutator retrace SCR deflection units. In dealing with a pnp semiconductor switch, its ON time is inevitably the point of lowest resistance. Consequently, the trace dc period at 20  $\mu$ s begins at the second vertical line and continues just past line 4, for a total time of about 50  $\mu$ s— $52.4 \times 10^{-6}$  is normal line trace time. For the better part of trace conduction, the retrace (commutator) SCR is off, Y2(W1), and comes on for 25  $\mu$ s— $11.1 \times 10^{-6}$  is standard retrace time.

Now when test points TP-1 and TP-2 in the horizontal oscillator disable circuit are shorted together, the 10 volts potential difference between them across a 2% resistor is nullified, the disable transistor has full forward bias potential applied and conducts, drawing current from the oscillator and kicking it off frequency. Instead of 50  $\mu$ s for trace time as in W1, the conduction period of the trace SCR now amounts to 56  $\mu$ s, Y1'(W1') (Fig.3), and the resonant frequency drops from 20 kHz to 17.9 kHz, as the oscillator slows down and falls out of sync. The commutator portion, Y2'(W1') also reacts with a jittery shift around 25  $\mu$ s that really defies precise counting, although it, too, should be greater in time but less in frequency. If you're overly analytical and wonder about the 12.5  $\mu$ s that results from

(continued on page 66)

# equipment report

## Lafayette SQ-W 4-Channel Decoder



THE BASIC SQ MATRIX DECODER HAS little inherent center-front to center-rear separation. The separation that does exist is dependent on psycho-acoustic effects. The center-front (mono) program information appears in both rear outputs 180° out of phase with each other. If the listener is precisely positioned in relation to the speakers, the rear spill from the center-front information cancels in the listener's brain. Obviously, this idea does not work out in practice too often.

Several techniques have been used to increase the apparent center-front-center-rear (CF/CR) separation. One inexpensive method is to electrically blend some of the out-of-phase rear signals so part of the common rear output is cancelled before it gets to the speakers. Generally, 6 to 8 dB of blend is used for minimum reasonable degree of separation. Unfortunately, blending reduces the left-to-right separation, with 8-dB blend giving the most practical total surround separation. (Not great, but reasonably good.)


To achieve even greater separation, later SQ decoders used something termed "logic," actually a gain riding of either the center-front information, or the center-front and center-rear, depending on the decoder's complexity. When predominant center information was detected, the decoder's gain was increased (unbalanced) accordingly to expand the apparent CF/CR separation.

Something termed "wavematching" was added to the gain riding technique to expand the corner information. When predominant corner information was sensed, the corner gain was increased to enhance the spatial effect.

The wavematching full-logic decoder produced almost optimum results, characterized by many critics as "close to discrete." Depending on the type of program material, however, it was sometimes possible to actually sense the gain-riding, which appeared as a mild "pumping"—similar to the "pumping" heard on older movie sound tracks.

To eliminate "pumping" of the full logic decoder—which some users found

objectionable—Lafayette's SQ-W decoder features a Variblend in addition to the wavematching full-logic. When the decoder senses primarily corner information—front or rear—the separation is expanded through the wavematching circuits. But the spill from the center-front into the rear outputs appears equally in both rear channels, though out of phase. The Variblend senses this equal but out of phase information, and automatically increases the rear channels blend factor to electrically attenuate the signals before they get to the speakers. In this manner, the CF/CR separation is enhanced without using a high amount of gain

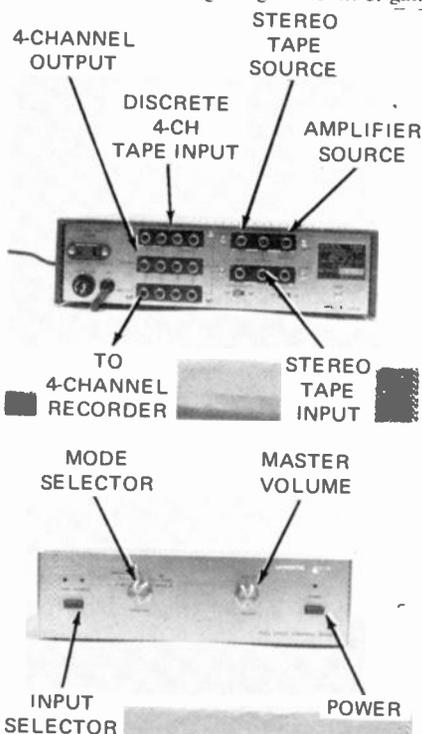

THOUGH THE SQ-W DECODER will normally use an amplifier's tape jacks, the recorder connections are not "lost" because they are available on the decoder. A stereo recorder can be used to record the stereo signal from the amplifier; a discrete 4-channel recorder connection(s) is handled directly by the decoder.

riding and without noticeable loss of left-to-right separation.

Since the blend factor is constantly changing in relation to the program information, the circuit was logically termed Variblend.

The Lafayette SQ-W decoder is an add-on accessory intended for 4-channel amplifiers and receivers which might or might not have a built-in matrix decoder. Its signal

(continued on page 100)

## STEP-BY-STEP (continued from page 65)

halving the commutator's 25- $\mu$ s retrace period, instead of the usual 11.1- $\mu$ s interval, this is just a slight time constant change from the original circuit. The proof that it works can be evaluated from the half power 3-dB down point of the OFF 400-volt trace pulse, Y1(W1), which measures just about 11  $\mu$ s on the button. Logically, then, if good trace, then sufficient retrace.

To aid service technicians, RCA in the CTC 48 series has now connected its pin-cushion transformer across the primary of the flyback instead of in series with the yoke so that an open in the yoke circuit is not as likely to occur and blow SCR101 or CR401. When checking one of these sub-systems after repairs, Variac the ac line current supply up to about 40 or 45 volts and see if the high voltage (it must be metered) is still increasing. If it is, there are probably no SCR or diode shorts, and you may continue to apply additional potential up to the normal 120 volts. If high voltage rise stops abnormally or decreases at some point below regular input voltage, check your circuits again for shorts. In this way, you'll save lots of SCR's—both yours and RCA's. R-E

## R-E's Substitution guide for replacement transistors PART XIX

compiled by

ROBERT & ELIZABETH SCOTT

- ARCH—Indicates the Archer brand of semiconductors sold only by Radio Shack and Allied Radio stores Allied Radio Shack, 2725 W 7th St., Ft. Worth, Texas 76107
- DM—D M Semiconductor Co., P.O. Box 131, Melrose, Mass. 02176
- G-E—General Electric Co., Tube Product Div., Owensboro, Ky. 42301
- ICC—International Components, 10 Daniel Street, Farmingdale, N.Y. 11735
- IR—International Rectifier, Semiconductor Div., 233 Kansas St., El Segundo, Calif. 90245
- MAL—Mallory Distributor Products Co., 101 S. Parker, Indianapolis, Ind. 46201
- MOT—Motorola Semiconductors, Box 2963, Phoenix, Ariz. 85036
- RCA—RCA Electronic Components, Harrison, N.J. 07029
- SPR—Sprague Products Co., 65 Marshall St., North Adams, Mass. 01247
- SYL—Sylvania Electric Corp., 100 1st Ave., Waltham, Mass. 02154
- WOR—Workman Electronic Products, Inc., Box 3828, Sarasota, Fla. 33578
- ZEN—Zenith Sales Co., 5600 W. Jarvis Ave., Chicago, Ill. 60648

Radio-Electronics has done its utmost to insure that the listings in this directory are as accurate and reliable as possible, however, no responsibility is assumed by Radio-Electronics for its use. We have used the latest manufacturers material available to us and have asked each manufacturer covered in the listing to check its accuracy. Where we have been supplied with corrections, we have updated the listing to include them. The first part of this Guide appeared in March 1973.

	ARCH	DM	G-E	ICC	IR	MAL	MOT	RCA	SPR	SYL	WOR	ZEN
2N3939	NA	SR-1245	NA	ICC-R1245	NA	NA	HEP-R1245	NA	NA	NA	NA	NA
2N3940	NA	SR-1246	NA	ICC-R1246	NA	NA	HEP-R1246	NA	NA	NA	NA	NA
2N3945	NA	TS-3010	NA	ICC-S3010	NA	PTC 144	HEP-S3010	NA	NA	NA	NA	ZEN 207
2N3946	NA	T-713	GE-20	ICC-713	NA	PTC 136	HEP-713	NA	NA	NA	NA	NA
2N3947	NA	T-713	GE-20	ICC-713	NA	PTC 136	HEP-713	NA	NA	NA	NA	NA
2N3948	RS276-2009	T-75	GE-28	ICC-75	IRTR-87	NA	HEP-75	SK 3024	RT-114	ECG 128	WEP 243	NA
2N3953	NA	T-709	NA	ICC-709	NA	NA	HEP-709	NA	NA	NA	NA	ZEN 105
2N3959	RS276-2013	T-730	NA	ICC-730	NA	NA	HEP-730	NA	NA	NA	NA	ZEN 116
2N3961	NA	NA	GE-28	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N3962	NA	T-708	GE-67	ICC-708	NA	NA	HEP-708	SK 3114	RT-115	ECG 159	WEP 717	NA
2N3963	NA	T-708	GE-21	NA	NA	NA	NA	SK 3114	RT-115	ECG 159	WEP 717	NA
2N3964	NA	T-715	GE-21	ICC-715	NA	NA	HEP-715	SK 3114	RT-115	ECG 159	WEP 717	ZEN 106
2N3965	NA	T-715	GE-21	ICC-715	NA	NA	HEP-715	SK 3114	RT-115	ECG 159	WEP 717	ZEN 106
2N3966	NA	T-801	GE-FET-1	ICC-801	NA	PTC 152	HEP-801	NA	NA	NA	NA	NA
2N3967	NA	T-801	GE-FET-1	ICC-801	NA	PTC 152	HEP-801	SK 3112	NA	ECG 133	NA	NA
2N3968	NA	T-801	GE-FET-1	ICC-801	NA	PTC-152	HEP-801	SK 3112	NA	ECG 133	NA	NA
2N3969	NA	T-801	GE-FET-1	ICC-801	NA	PTC 152	HEP-801	SK 3112	NA	ECG 133	NA	NA
2N3973	NA	TS-0004	GE-20	ICC-S0004	IRTR-64	PTC 123	HEP-S0004	SK 3122	RT-102	ECG 123A	WEP 735	ZEN 127
2N3974	NA	TS-0004	GE-20	ICC-S0004	IRTR-64	PTC 123	HEP-S0004	SK 3122	RT-102	ECG 123A	WEP 735	ZEN 127
2N3975	NA	TS-0004	GE-20	ICC-S0004	IRTR-64	PTC 123	HEP-S0004	SK 3122	RT-102	ECG 123A	WEP 735	ZEN 127
2N3976	RS276-2009	T-736	GE-20	ICC-736	IRTR-64	PTC 123	HEP-736	SK 3024	RT-102	ECG 123A	WEP 735	ZEN 120
2N3977	NA	T-739	GE-22	ICC-739	NA	PTC 103	HEP-739	SK 3114	RT-115	ECG 159	WEP 717	ZEN 122
2N3978	NA	T-739	GE-22	ICC-739	TR-20	PTC 103	HEP-739	SK 3114	RT-115	ECG 159	WEP 717	ZEN 122
2N3979	NA	T-739	GE-21	ICC-739	TR-28	PTC 103	HEP-739	SK 3114	RT-115	ECG 159	WEP 717	ZEN 122
2N3980	NA	T-310	NA	ICC-310	NA	NA	HEP-310	NA	NA	NA	NA	ZEN 129
2N3981	NA	NA	GE-63	NA	TR-25	PTC 144	NA	NA	NA	NA	NA	NA
2N3982	NA	NA	GE-63	NA	TR-25	PTC 144	NA	NA	NA	NA	NA	NA
2N3983	RS276-2011	T-56	GE-60	ICC-56	NA	PTC 121	HEP-56	SK 3039	RT-113	ECG 108	WEP 56	ZEN 104
2N3984	RS276-2011	T-56	GE-60	ICC-56	NA	PTC 115	HEP-56	SK 3018	RT-113	ECG 108	WEP 56	ZEN 104
2N3985	RS276-2011	T-56	GE-60	ICC-56	NA	PTC 115	HEP-56	SK 3018	RT-113	ECG 108	WEP 56	ZEN 104
2N3993	NA	T-803	NA	ICC-803	NA	NA	HEP-803	NA	NA	NA	NA	NA
2N3994	NA	T-803	NA	ICC-803	NA	NA	HEP-803	NA	NA	NA	NA	NA
2N3995	NA	T-2	NA	ICC-2	TR-17	NA	HEP-2	NA	NA	ECG 160	WEP 637	ZEN 300
2N4000	NA	T-714	GE-18	ICC-714	NA	PTC 144	HEP-714	NA	NA	NA	NA	NA
2N4001	NA	T-714	GE-18	ICC-714	NA	PTC 144	HEP-714	NA	NA	NA	NA	NA
2N4006	NA	NA	GE-22	NA	TR-20	PTC 103	NA	NA	NA	NA	NA	NA
2N4007	NA	NA	GE-22	NA	TR-20	PTC 103	NA	NA	NA	NA	NA	NA
2N4008	NA	NA	GE-21	NA	TR-28	PTC 103	NA	NA	NA	NA	NA	NA
2N4012	NA	NA	GE-28	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N4013	NA	T-736	GE-20	ICC-736	NA	NA	HEP-736	SK 3122	RT-102	ECG 123A	WEP 735	ZEN 120
2N4014	NA	TS-0005	GE-20	ICC-S0005	NA	NA	HEP-S0005	SK 3122	RT-102	ECG 123A	WEP 735	NA
2N4015*	NA	T-716	NA	NA	NA	NA	NA	NA	NA	NA	NA	ZEN 107
2N4016*	NA	T-716	NA	ICC-716	NA	NA	HEP-716	NA	NA	NA	NA	ZEN 107
2N4017*	NA	T-716	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4019*	NA	T-715	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4020*	NA	T-715	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4021*	NA	T-715	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4022*	NA	T-715	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4023*	NA	T-715	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4024*	NA	T-715	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4025*	NA	T-715	NA	ICC-715	NA	NA	HEP-715	NA	NA	NA	NA	ZEN 106
2N4026	NA	T-708	GE-67	ICC-708	IRTR-88	NA	HEP-708	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4027	NA	TS-3003	NA	ICC-S0003	IRTR-88	NA	HEP-S0003	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4028	NA	T-708	GE-67	ICC-708	IRTR-88	NA	HEP-708	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4029	NA	TS-3031	NA	ICC-S3031	IRTR-88	NA	HEP-S3031	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4030	NA	TS-3001	GE-67	ICC-S3001	IRTR-88	PTC 141	HEP-S3001	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4031	NA	TS-3003	NA	ICC-S3003	IRTR-88	NA	HEP-S3003	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4032	NA	TS-3001	GE-67	ICC-S3031	IRTR-88	NA	HEP-S3031	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4033	NA	TS-3031	NA	ICC-S3031	IRTR-88	NA	HEP-S3031	SK 3025	RT-115	ECG 129	WEP 242	NA
2N4034	NA	T-52	GE-21	ICC-52	NA	NA	HEP-52	NA	RT-126	ECG 106	WEP 52	NA
2N4035	NA	T-715	GE-21	ICC-715	NA	NA	HEP-715	NA	RT-126	ECG 106	WEP 52	ZEN 106
2N4036	NA	TS-3031	GE-29	ICC-S3031	NA	PTC 141	HEP-S3031	SK 3025	NA	ECG 129	NA	NA
2N4037	RS276-2025	TS-3012	GE-67	ICC-S3012	NA	PTC 141	HEP-S3012	SK 3025	NA	ECG 129	NA	NA
2N4040	NA	TS-3005	GE-28	ICC-S3005	NA	NA	HEP-S3005	NA	NA	NA	NA	NA
2N4041	NA	TS-3005	GE-28	ICC-S3005	NA	NA	HEP-S3005	NA	NA	NA	NA	NA
2N4046	NA	TS-3008	NA	ICC-S3008	NA	NA	HEP-S3008	NA	NA	NA	NA	NA
2N4047	NA	TS-0005	NA	ICC-S0005	NA	NA	HEP-S0005	NA	NA	NA	NA	NA
2N4048	NA	NA	NA	ICC-G6002	NA	NA	HEP-G6002	NA	NA	NA	NA	NA
2N4051	NA	NA	NA	ICC-G6002	NA	NA	HEP-G6002	NA	NA	NA	NA	NA
2N4054	NA	T-244	GE-27	ICC-244	NA	PTC 104	HEP-244	SK 3103	NA	ECG 157	WEP 244	ZEN 201
2N4055	NA	T-244	GE-27	ICC-244	NA	PTC 104	HEP-244	SK 3103	RT-135	ECG 157	WEP 244	ZEN 201
2N4056	NA	T-244	GE-27	ICC-244	NA	PTC 104	HEP-244	SK 3103	RT-135	ECG 157	WEP 244	ZEN 201
2N4057	NA	T-244	GE-27	ICC-244	NA	PTC 104	HEP-244	SK 3103	RT-135	ECG 157	WEP 244	ZEN 201
2N4058	RS276-2023	T-52	GE-67	ICC-52	IRTR-52	PTC 127	HEP-52	SK 3118	RT-126	ECG 106	WEP 52	NA
2N4059	RS276-2023	T-52	GE-67	ICC-52	IRTR-52	PTC 127	HEP-52	SK 3118	RT-126	ECG 106	WEP 52	NA

NA=NOT AVAILABLE

(turn page)

	ARCH	DM	G-E	ICC	IR	MAL	MOT	RCA	SPR	SYL	WOR	ZEN
2N4060	RS276-2023	T-52	GE-21	ICC-52	IRTR-52	PTC 103	HEP-52	SK 3118	RT-126	ECG 106	WEP 52	NA
2N4061	RS276-2023	T-52	GE-67	ICC-52	IRTR-52	PTC 127	HEP-52	SK 3118	RT-126	ECG 106	WEP 52	NA
2N4062	RS276-2023	T-52	GE-21	ICC-52	IRTR-52	NA	HEP-52	SK 3118	RT-126	ECG 106	WEP 52	NA
2N4063	NA	NA	NA	NA	NA	NA	NA	SK 3045	NA	ECG 123A	NA	NA
2N4064	NA	NA	GE-32	NA	NA	NA	NA	SK 3045	NA	ECG 123A	NA	NA
2N4068	NA	TS-0005	GE-18	ICC-S0005	NA	PTC 125	HEP-S0005	SK 3045	RT-110	ECG 154	WEP 712	NA
2N4069	NA	T-714	GE-32	ICC-714	NA	NA	HEP-714	NA	NA	NA	WEP 56	NA
2N4070	NA	TS-5004	NA	ICC-S5004	NA	NA	HEP-S5004	NA	NA	NA	NA	NA
2N4071	NA	T-707	NA	ICC-707	NA	NA	HEP-707	NA	NA	NA	NA	ZEN 204
2N4072	RS276-2011	T-718	GE-17	ICC-718	NA	PTC 121	HEP-718	SK 3018	RT-113	ECG 108	WEP 56	NA
2N4073	RS276-2009	T-75	GE-18	ICC-75	NA	NA	HEP-75	SK 3018	RT-113	ECG 108	WEP 56	NA
2N4074	RS276-2009	T-55	GE-64	ICC-55	NA	PTC 123	HEP-55	SK 3122	RT-102	ECG 123A	WEP 735	ZEN 103
2N4077	NA	NA	NA	NA	NA	NA	NA	NA	NA	ECG 155	NA	NA
2N4078	RS276-2006	T-643	GE-30	ICC-643	TR-50	NA	HEP-643	SK 3052	RT-127	ECG 131	WEP 642	NA
2N4079	NA	NA	NA	NA	NA	NA	NA	NA	RT-127	ECG 131,155(CP)	WEP 6742	NA
2N4080	NA	T-752	GE-21	NA	NA	NA	NA	SK 3118	RT-126	NA	WEP 52	NA
2N4081	NA	NA	GE-60	NA	NA	NA	NA	NA	NA	NA	NA	ZEN 127
2N4086	RS276-2009	T-55	GE-62	ICC-55	NA	PTC 139	HEP-55	SK 3124	RT-102	NA	WEP 735	ZEN 103
2N4087	RS276-2009	T-55	GE-62	ICC-55	NA	PTC 139	HEP-55	SK 3124	RT-102	NA	WEP 735	ZEN 103
2N4088	NA	TF-1035	NA	ICC-F1035	NA	NA	HEP-F1035	NA	NA	NA	NA	NA
2N4089	NA	TF-1035	NA	ICC-F1035	NA	NA	HEP-F1035	NA	NA	NA	NA	NA
2N4090	NA	TF-1035	NA	ICC-F1035	NA	NA	HEP-F1035	NA	NA	NA	NA	NA
2N4096	NA	SR-1002	NA	ICC-R1002	NA	NA	HEP-R1002	NA	NA	NA	NA	NA
2N4097	NA	SR-1003	NA	ICC-R1003	NA	NA	HEP-R1003	NA	NA	NA	NA	NA
2N4098	NA	SR-1005	NA	ICC-R1005	NA	NA	HEP-R1005	NA	NA	NA	NA	NA
2N4100*	NA	TS-0007	GE-63	ICC-S0007	NA	PTC 121	HEP-S007	NA	NA	NA	NA	NA
2N4101	NA	NA	NA	NA	NA	NA	NA	SK 3502	NA	NA	NA	NA
2N4103	NA	SR-1223	NA	ICC-R1223	NA	NA	HEP-R1223	NA	NA	NA	NA	NA
2N4104	NA	NA	GE-20	NA	NA	NA	NA	SK 3124	NA	NA	NA	NA
2N4105	NA	NA	GE-8	NA	TR-08	NA	NA	SK 3010	RT-122	NA	WEP 724	NA
2N4106	RS276-2006	T-238	GE-2	ICC-238	TR-05	NA	HEP-238	SK 3010	NA	NA	WEP 630	ZEN 329
2N4107	NA	NA	GE-54	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N4108	NA	SR-1002	NA	ICC-R1002	NA	NA	HEP-R1002	NA	NA	NA	NA	NA
2N4109	NA	SR-1003	NA	ICC-R1003	NA	NA	HEP-R1003	NA	NA	NA	NA	NA
2N4110	NA	SR-1005	NA	ICC-R1005	NA	NA	HEP-R1005	NA	NA	NA	NA	NA
2N4111	NA	T-704	GE-19	ICC-704	NA	NA	HEP-704	NA	NA	NA	NA	NA
2N4112	NA	NA	GE-19	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N4113	NA	T-704	GE-19	ICC-704	NA	NA	HEP-704	NA	NA	NA	NA	NA
2N4114	NA	NA	GE-19	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N4117	NA	NA	GE-FET-1	NA	NA	NA	NA	SK 3112	NA	ECG 133	NA	NA
2N4118	NA	NA	GE-FET-1	NA	NA	NA	NA	SK 3112	NA	ECG 133	NA	NA
2N4119	NA	NA	GE-FET-1	NA	NA	NA	NA	SK 3112	NA	ECG 133	NA	NA
2N4121	RS276-2023	T-52	NA	ICC-52	TR-30	NA	HEP-52	SK 3118	RT-126	NA	WEP 52	NA
2N4122	RS276-2021	T-715	GE-21	ICC-715	NA	NA	HEP-715	SK 3118	RT-126	NA	WEP 52	ZEN 106
2N4123	RS276-2009	T-724	GE-20	ICC-724	IRTR-53	PTC-136	HEP-724	SK 3124	RT-102	NA	WEP 735	ZEN 106
2N4124	RS276-2009	T-53	GE-20	ICC-53	IRTR-53	PTC 136	HEP-53	SK 3124	RT-102	NA	WEP 735	ZEN 112
2N4125	RS276-2023	T-52	GE-21	ICC-52	IRTR-54	PTC-103	HEP-52	SK 3114	RT-115	NA	WEP 717	ZEN 102
2N4126	RS276-2024	T-57	GE-67	ICC-57	NA	NA	HEP-57	SK 3114	RT-115	NA	WEP 717	NA
2N4127	NA	NA	GE-66	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N4128	NA	NA	GE-66	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N4130	NA	T-247	GE-14	ICC-247	NA	NA	HEP-247	SK 3036	NA	NA	NA	NA
2N4131	NA	TS-5004	NA	ICC-S5004	NA	NA	HEP-S5004	NA	NA	NA	NA	NA
2N4133	NA	T-714	NA	ICC-714	NA	NA	HEP-714	NA	NA	NA	NA	NA
2N4134	NA	T-709	GE-60	ICC-709	NA	PTC 121	HEP-709	SK 3039	NA	ECG 108	WEP 56	ZEN 105
2N4135	NA	T-709	GE-60	ICC-709	IRTR-64	PTC 121	HEP-709	NA	NA	NA	NA	ZEN 105
2N4136	NA	NA	GE-54	NA	NA	NA	NA	NA	NA	NA	NA	NA
2N4137	NA	TS-0004	NA	ICC-S0004	NA	NA	HEP-S0004	NA	NA	NA	NA	ZEN 127
2N4138	NA	T-733	GE-61	ICC-733	IRTR-51	PTC 139	HEP-733	NA	NA	NA	NA	NA
2N4140	RS276-2009	T-50	GE-20	ICC-50	IRTR-53	PTC 136	HEP-50	SK 3122	RT-102	NA	WEP 735	ZEN 100
2N4141	RS276-2009	T-55	GE-20	ICC-55	IRTR-53	PTC 136	HEP-55	SK 3122	RT-102	NA	WEP 735	ZEN 103
2N4142	RS276-2023	T-52	GE-21	ICC-52	NA	PTC 103	HEP-52	SK 3114	RT-115	NA	WEP 717	NA
2N4143	RS276-2024	T-57	GE-67	ICC-57	NA	PTC 127	HEP-57	SK 3114	RT-115	NA	WEP 717	NA
2N4144	NA	SR-1001	NA	ICC-R1001	NA	NA	HEP-R1001	NA	NA	NA	NA	NA
2N4145	NA	SR-1001	NA	ICC-R1001	NA	NA	HEP-R1001	NA	NA	ECG 5400	NA	NA
2N4146	NA	SR-1002	NA	ICC-R1002	NA	NA	HEP-R1002	NA	NA	NA	NA	NA
2N4147	NA	SR-1003	NA	ICC-R1003	NA	NA	HEP-R1003	NA	NA	NA	NA	NA
2N4148	NA	SR-1004	NA	ICC-R1004	NA	NA	HEP-R1004	NA	NA	NA	NA	NA
2N4149	NA	SR-1005	NA	ICC-R1005	NA	NA	HEP-R1005	NA	NA	ECG 159	NA	NA
2N4150	NA	TS-3002	GEMR-4	ICC-S3002	NA	NA	HEP-S3002	NA	NA	NA	NA	NA
2N4151	NA	S-620	GEMR-4	ICC-620	NA	NA	HEP-620	NA	NA	NA	NA	NA

\*Indicates a dual transistor for high-speed switching, diff amplifier etc. Likely to be a matched pair. Use two of the type specified, matching when necessary, on a curve tracer or lab-type transistor checker.

NA=NOT AVAILABLE

(continued next month)

# R-E's Service Clinic

## The transistor — that imprecise device!

*How to select replacements for hard-to-find types.*

by JACK DARR  
SERVICE EDITOR

THE INVENTION OF THE TRANSISTOR, 25 years ago, started something. For one thing, it opened the floodgates for a simply tremendous stream of literature written about it. The mathematicians had a field day! They happily poured out a flood of formulas and then developed more, and more, and more—the h-parameters (hybrid parameters), the y-parameters (admittance parameters) in addition to the few *simple* formulas that we need to determine the performance of the thing in a given circuit.

Besides this, they came up with the incomprehensible concept of "holes." This may be valid, but it served mainly to bring about a state of total and utter confusion in the minds of those of us who must work with the things. I can attest to this, not only from my own personal experience, but from thousands of letters we get at **Radio-Electronics** in the Service Clinic mailbag.

Unfortunately, this kind of math is based on the premise that these devices are precision instruments! In other words, they're all alike. Later thinking contradicts this. In the words of one authority, "The system of stability factors is too complex to be used easily in practical design situations without computer aid or an impractical amount of human effort!"\*

To be practical (meaning to work as predicted), transistors would have to be capable of precision reproduction. In plain English, this means that every device of a certain number would have precisely the same characteristics; gain, leakage, current-rating, and on and on. This is simply untrue. A group of 6CG7's all have identical characteristics; a group of 2Nxxx's do not.

You *can* get a group of transistors with almost identical characteristics. You *can't* build them that way, though. You make them, and then you *select* those with almost identical characteristics. All you have to do to verify this statement is to read the spec sheet on any transistor. You'll find that they show a minimum, maximum and typical value for every parameter of the device. For beta, as an example, you may find it varying from 50 to 150. This is called "parameter spread," as well as other names, some not nearly so polite. Even these must be read at a fixed temperature, 25°C. All parameters vary wildly with temperature; leakage, beta, breakdown voltage, and on and on.

In a large transistor factory which I visited some time ago, the final-test machine was a monster almost 100 feet long. The transistors were plugged into little adapters, and traveled down a track on the top. At each stop, they were tested. The first few were for shorts, opens, etc. Later, they

were checked for all other parameters. I asked the friendly soul who was giving me the guided tour "What's that last station, the one on the very end?" He grinned and said "When they get there, we raise the price three dollars and mark 'em MIL-SPEC!"

The transistors that were kicked out into bins in the middle of the machine were those that weren't precisely on spec, but within a given percentage *variation*. For example, if the bogey value of beta was 100, the machine could be set to kick out all that fell within a variation of +50 to -50 (except for those that read *precisely* 100; these went on to the Last Stop).

You can verify this, too. Just buy 100 commercial transistors and check them for beta. One of my friends has shown me this. Out of 100 identical transistors, 50 will be right on the typical, 25 above, and 25 below.

The wide tolerance of these things is amazing. When we were in radio school, we worked things out to four decimal places (which I always thought a bit unnecessary.) When we got out into actual service work, we found tolerances of 10% and even 20%, and felt that this was being a little slack. Normal tolerances in transistors are really something; one authority gives the figure of +100%; -50% for the beta alone.

From the preceding gloomy statements, you may begin to wonder how they could *ever* build anything with such inconstant devices. (So do they, at times.) However, there is a way. Later thinking has worked out means of compensating for the variations. To make a practical transistor circuit (one that works), the design engineer simply *designs the transistor out of the circuit*.

He does this by choosing his circuit constants so that the variation in parameters is simply *swamped out*. If this transistor has a normal leakage current of 500  $\mu$ A, he sets his normal resting current at say, 2.0 mA. This is so much greater than 50  $\mu$ A that the leakage-current variation won't cause too much change.

The next step in this process is the liberal use of feedback, both current-mode and voltage-mode. By doing this, he can swamp out the effects of any beta variation, and hold the overall gain of the circuit constant under worst-case conditions.

The final step is "derating." (Remember this.) This is simple; we've been doing it for years; we called it "safety factor." Example; if he needs a transistor with a maximum collector voltage breakdown of 50 volts, he uses one with a breakdown rating of 100 volts, or even 200 volts (if Production Control will let him). By derating voltage and

\*J.R. Pierce: "Transistor Circuit Theory and Design" Chas. E. Merrill Books, Columbus, Ohio 1963

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included, we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, New York 10003.

current ratings, the junction will run as cool as possible. This eliminates the worst single cause of parameter variation; a rise in the *junction temperature*. This makes every parameter of the transistor vary tremendously.

Right about now, most of you are probably saying "What's this all got to do with me? I'm not designing the stuff; I just fix it." That's the point, brethren. To make *practical* repairs on this stuff, we have to know how it works, and above all, the working *limits* of the devices. If you understand these, you can make substitutions and in most cases come up with a circuit that works better than it did before it failed. All you need to do this is a copy of any one of the Transistor Replacement Guides, which give the ratings for the whole line of general replacement transistors. I have six of these on my desk now, and there are several others. They're the most consulted reference books I have. All of the data you need is there.

You know that one of our worst problems is locating replacement transistors. We never open up a piece of equipment that we don't see a whole new set of numbers, if the things have any numbers at all on 'em. The makers of general replacement transistors claim that only 50-60 of their transistors will replace thousands of OEM numbers. This is quite true.

There simply isn't all that much *difference* in transistors. For example, if you need an i.f. or tuner transistor in a TV set, one general replacement transistor, such as RCA's SK-3018 or Motorola's HEP-728, can be used to replace any one of literally

thousands of OEM types. There are several others, of course, in other lines; I just picked those at random.

All common transistors could be lumped into a very few classes, with a very small set of the really important parameters. The *least* important to us is the beta. (More on this later.) The most important, in my mind, is the collector breakdown voltage and maximum collector current rating.

A properly designed transistor stage will be amply derated, as I said before. My pet authority on the subject recommends that a transistor should never be used at a collector current that is more than 40% of its maximum current rating. The same thing would apply to the collector voltage breakdown, though I like to double this, at least, and have used a factor of four.

The most controversial statement that I've made so far is probably the one about the beta being the least important parameter. Like everything else in our business, this isn't unqualified. I did say that in a *properly designed* circuit, it wasn't too critical! This is due to the fact that the beta of all transistors is far from being a constant thing. It will vary wildly with temperature, current, applied voltage, leakage, and you name it. In the properly designed circuit, these variations will be swamped out so that wide variations of voltage, current and even junction temperature will have only a small effect on the overall *gain* of the stage. (For a full discussion of this, read Gerald Williams' "Practical Transistor Circuit Design and Analysis," McGraw-Hill 07-070398-1.)

Besides these things, we have the wide parameter spread; often as high as 75% ±

the bogey value. So, even if you are using an Exact Factory Replacement, it's possible to get one with a beta that differs quite a bit from the original. (You may get one that's precisely the same, but then you may not. I've checked a few "matched pairs," and found them highly un-matched!)

In actual service work, and in a long series of experiments using general replacement transistors, I've found that this will work. I have substituted as many as five different GR types into TV sets, and found no trouble at all. In most cases, if you can "get in the ball-park," OK. If you can find a number on the thing, and it's listed in the Replacement Guide, the chances are it will work very well. The only time I've ever run into trouble is with the occasional typographical error.

There is one case where you may run into some problems. This is in the multi-stage direct-coupled audio amplifiers. If you replace an output transistor, and the resting current is incorrect, try replacing the driver transistor. The original driver may not have precisely the correct beta. (Although, as said before, if the designer swamped the circuit out, this won't upset it.) Try using types with either a higher or lower beta, and see. Sound like K&T? (Kut and Try.) It is. It may be the way the stage was designed in the first place! To check, read the resting current of the output transistors.

You can make your own experiments. The next time you get a TV set with plug-in transistors, try a few from your general replacement stock. Try picking one that *looks* as if it would work. The chances are that it will.

R-E

## Introducing the expensive curve tracer that doesn't cost a lot.

The B&K Model 501A.

It hooks up to any scope, old or new. (Like our Model 1460 triggered-sweep scope.)

And it analyzes all semi-conductors including J-FET's, MOS-FET's, signal and power bipolar transistors, SCR's, UJT's and diodes. Fast and easy.

Constant current and voltage steps with 3% accuracy make the Model 501A an exceptional value. In fact, it performs like \$2,000 units. Yet you can afford one on each engineer's bench. And another for incoming quality control.

Call your B&K distributor. Or write Dynascan Corporation.

In stock at your parts distributor.



**\$163<sup>00</sup>**



Product of Dynascan Corporation  
1801 West Belle Plaine Avenue, Chicago, Illinois 60613


You'd probably expect a portable oscilloscope as rugged and reliable as this one to cost a lot.

You'd be wrong.

Introducing the B&K Model 1403 3" Solid-state oscilloscope. It's so compact, reliable, and inexpensive that it's the perfect scope for most on-the-line monitoring applications. Look at its specs: DC to 2MHz bandwidth at 20mV/cm. Recurrent sweep speeds from 10Hz to 100k Hz. New wide-angle CRT to reduce case depth to a minimum. Direct-deflection terminals for waveforms up to 150 MHz. Weighs only 8½ pounds. And has a smoked acrylic graticule for trace sharpness and easy reading. All the reliability and accuracy you need in a monitor scope—at a surprisingly low price.

Contact your distributor, or write Dynascan Corporation.

**\$189<sup>00</sup>**

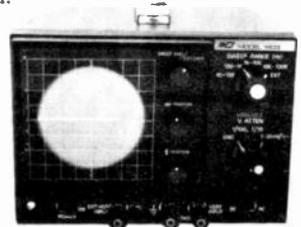

**B&K** Very good equipment at a very good price.  
Dynascan Corporation.  
1801 West Belle Plaine Avenue, Chicago, Illinois 60613


# new breadboard test equipment

... with power for the professional... with economy for the hobbyist!

Fresh, from the laboratories of Continental Specialties, whose QT Sockets and Proto-Boards have taken the electronics market by storm... here are exciting NEW ideas to make your circuit design and testing faster, safer, easier and less expensive!
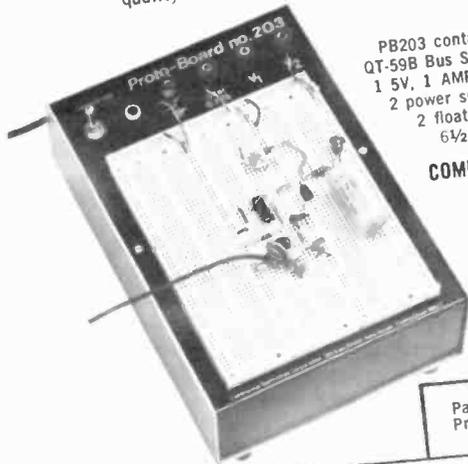
## NOW... PROTO POWER! NEW PROTO BOARD-203

New Proto Board 203 with built-in regulated short-proof 5V, 1AMP power supply. Ready-to-use. Just plug-in and start building!  
2 extra floating 5-way binding posts for external signals. Completely self-contained with power switch indicator lamp and power fuse. 24-14 pin DIP capacity. All metal construction... no chipping or cracking like plastic cases. Two-tone gold/black quality case makes PB203 asthetically, as well as technically, pleasing.



PB203 contains: 3 QT-59S Sockets; 4 QT-59B Bus Strips; 1 QT-47B Bus Strip; 1 5V, 1 AMP regulated power supply; 2 power supply 5-way binding posts; 2 floating binding posts; 9 3/4" L x 6 1/2" W x 2 3/4" H. Weight: 5 lbs.

COMPLETE  
**\$75**  
ORDER TODAY!

Patents Pending • Made in U.S.A.  
Prices subject to change

## For the economy-minded student or experimenter... NEW PROTO BOARD-100

Here's a low cost, big 10 IC capacity breadboard kit with all the quality of QT Sockets and the best of the Proto-Board series... complete down to the last nut, bolt and screw. Includes 2 QT-35S Sockets; 1 QT-35B Bus Strip; 2 5-way binding posts; 4 rubber feet; screws, nuts, bolts; and easy assembly instructions.




COMPLETE KIT...

**\$19<sup>95</sup>** ORDER YOURS TODAY!
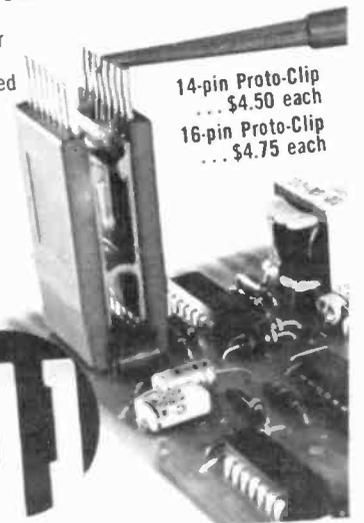
## NEW! PROTO-CLIP for power-on, hands-off signal tracing. Eliminates shorting leads... and costs under \$5!

Bring IC leads up from pc board for fast signal tracing and trouble-shooting. Inject signals. Wire unused circuits into boards. Scope probes and test leads lock onto D-nagrip (see circle) inset for hands-off testing. New plastic construction eliminates springs, pivots. Non-corrosive nickel/silver contacts for simultaneous low resistance connections. Narrow throat for high density pc boards.




14-pin Proto-Clip ... \$4.50 each  
16-pin Proto-Clip ... \$4.75 each

Build and test circuits as fast as you can think without soldering or patch cords with NEW
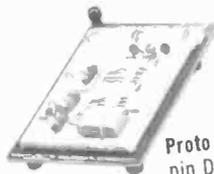
## Proto Board Breadboard Assemblies


Here are four versatile new Continental Specialties' Proto Boards, made from convenient combinations of QT Sockets and Bus Strips, that let you make all circuit and power interconnections with common solid #22 wire, while power distribution busses make wiring a snap. Aluminum base plates offer solid work surfaces and perfect ground plane. Rubber feet prevent scratching. Each Proto Board features one or more 5-way binding posts to tie into system or power supply ground. And all are compatible with digital and linear ICs, in T05s, DIP packs and discrete components. Each is assembled and ready-to-use.



Proto Board 102. Compact. 12-14 pin DIP capacity. 7" x 4 1/2". **39<sup>95</sup>**

Proto Board 101. Compact. Inexpensive. 10-14 pin DIP capacity. 5.8" long x 4.5" wide. **29<sup>95</sup>**

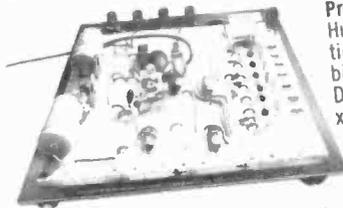Proto Board 103. 2,250 solderless tie points. (4) 5-way binding posts. 24-14 pin DIP capacity. 9" x 6". **59<sup>95</sup>**



Proto Board 104. Huge. 3,060 solderless tie points. (4) 5-way binding posts. 32-14 pin DIP capacity. 9 1/2" long x 8" wide. **79<sup>95</sup>**

**FREE!** Metric-to-English SLIDE RULE. Convert lengths, area, weight, volume instantly. Yours FREE with a minimum \$5.00 order!

Available off-the-shelf at your local distributor or order directly from Continental Specialties. Phone charges accepted for BankAmericard, Master Charge, American Express. Write for Free catalog. Dealer inquiries invited.



**Continental Specialties Corporation**  
325 East St., Box 1942, New Haven, CT 06509  
Telephone: (203) 624-3103

CANADA:  
Available thru Len Finkler, Ltd.  
Downsview, Ontario

# The better the the better you'

SOLID STATE  
OSCILLOSCOPE

COMPU-TRAINER

TUBE & TRANSISTOR  
TESTER

DIGITAL  
MULTIMETER

ELECTRO - LAB

NTS DIGITAL GR-2000 SOLID STATE  
COLOR TV WITH 315 SQ. IN. PICTURE  
AND VARACTOR DIGITAL TUNING

TROUBLESHOOTER  
VOM

As an NTS student, you'll acquire the experience and know-how that comes with first hand training on NTS "pro" equipment. Equipment you'll build and keep. Our courses include equipment like the 5" solid-state oscilloscope, a transistor and tube-tester, a vector monitor scope, 74 sq. in. B&W TV, or a solid-state stereo AM-FM receiver. The unique new **NTS Digital GR-2000 Color TV** with first-ever features like silent varactor diode tuning; digital channel selection, digital clock, an option at additional cost; and big 315 sq. in. ultra rectangular

screen. This is just a sampling of the kind of better equipment that get you better equipped for the electronics industry.

By following the easy-to-read NTS lessons, you learn the theory behind these tools of the trade. You'll learn and develop skill and confidence fast

**Choose from 12 NTS Electronics Courses**, including Color TV and B&W TV Servicing, Electronics and Computer Technology, Electronics Communications & FCC, and Industrial & Automation

# equipment will be equipped.



Electronics. All courses can provide you excellent opportunities to expand your career in the exciting world of electronics! So get started right now by checking the coupon and mailing it today.

**COMPARE WHAT WE OFFER IN KITS AND LESSONS. COMPARE OUR TUITION.**

**Classroom Training at Los Angeles.** You can take classroom training at Los Angeles in sunny Southern California. NTS occupies a city block with over a million dollars in facilities devoted exclusively to

technical training. Check box in coupon.

**Approved for Veteran Training.** Accredited Member: National Association of Trade & Technical Schools; National Home Study Council

**NATIONAL TECHNICAL SCHOOLS**

TECHNICAL-TRADE TRAINING SINCE 1905  
Resident & Home Study Schools  
4000 South Figueroa St., Los Angeles, Calif. 90037

# reader questions

## HUM-BARS FROM TRANSLATOR???

"In regard to the 'Hum-Bars in The Color' question, in the August 1973 issue, if the reader is getting his signal from a translator station, this is normal! I've seen this on about 20 sets in my area, on translators!"—R.J., Franklin, N.C.

Excuse me for differing with you, but

hum-bars in translator signals are definitely *NOT* normal! (In color, or anything else.) Not if the translator station is operating up to FCC standards. If you see them on more than one set, this should be reported to the Chief Engineer of the TV station using the translator. If this doesn't get action, write to your nearest FCC office.

## LOCAL STATION "BLOCKS" RADIO

Here's a problem! In a small clock radio, it'll get the local station, 50 kW, 540 kHz, about a mile away, and that's it. From about 590 on the dial, nothing. All transistors check out.—L.F. Wa-

trous, Sask, Canada.

You *do* have a problem. And when I get through you'll probably still have it. This is common. The signal from a 50-kilowatt at only a mile is tremendous, and I'm afraid that it's simply blocking the mixer-oscillator stage. The field strength is so great that the transistor is cut off.


About the only thing you could do is try a "suckout" trap tuned to the frequency of the local.

## HV PROTECTION CIRCUIT

Hey! I'm in hot water again. This time it's an almost new RCA CTC-63XC with brightness problems. If I turn the brightness control or contrast control down, the raster will cut off. Won't come on again until I turn the set off and on. Everything I check seems normal; waveforms, etc. HALP!—C.C., Baton Rouge, La.

Well, you know what they say; stay in hot water long enough and you get pretty hard-boiled. Let's see. This sounds familiar.

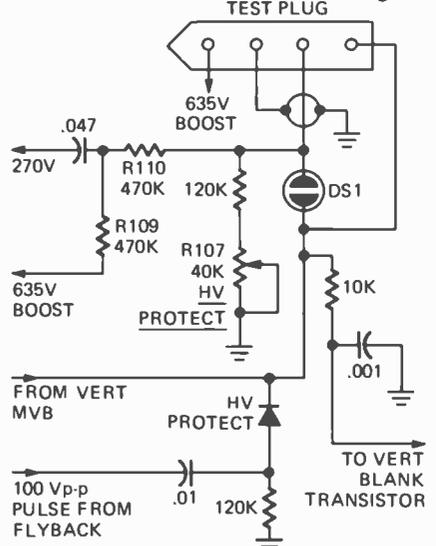Many late model sets have "protection circuits" built into them, to comply with some HEW regulation or other. This one does, too. The diagram



shows the high-voltage circuitry. RCA's service data says "With a synced picture, connect a 5-megohm precision resistor across R109-R110. The neon bulb DS1 should fire, and produce a blank or no-raster condition." The variable resistor, R107, is the control for this circuit, I'm almost certain. Seems to be able to set the threshold for the cutoff action (which cuts off the raster by biasing the video, through the vertical blanker).

Check this; if the neon lamp is firing, the circuit is getting just a little too eager about protecting you! You should be able to adjust it, with R107, to a point where it won't trigger on normal brightness or contrast changes. If not, the neon lamp may be defective; some of these will get erratic and fire at different voltages. Replace it. R-E

# CHANNELLOCK

Gives You More In Hand Tools Including

FULL POLISH FINISH

(quality you can SEE)

The honest gleam of drop forged steel, fine polished end to end. No plating, no black handles, no "good enough" compromise anywhere. Craftsmanship in every detail. Quality you see, not just hope for. CHANNELLOCK'S bonus to you at no extra cost.

HERE'S MORE. Our catalog gives you an arm-chair review of our complete line. It's yours for the asking.



TOOLS BY  
**CHAN NEL LOCK**  
MEADVILLE, PA. 16335

# SWTC - POWER FROM -25 TO 250 WATTS

No matter what your power requirements. No matter what your budget. Now there is a Southwest Technical power amplifier that will fit your requirements.

NEW— #215 Stereo Amplifier



Now those who don't need the power output of our famous "Tiger .01" can have the same super low distortion in a 25 Watt per channel amplifier. This amplifier has all of the features of "Tiger .01". Our unique cross coupled, complementary differential input system; an output triple and IM distortion of less than .01% up to rated output. It also has the same beautiful bronze anodized chassis with a perforated metal cover and two meters to indicate the output level. Frequency response is -3.0 dB at 0.1 Hz and 250 KHz. Rise time is less than a microsecond. As usual nothing but first quality parts and fibreglass circuit boards are used in the kit. Wiring pictorials and step-by-step instructions are provided.

# 215 Stereo Amplifier Kit \$69.50 PPD

The first of the super low distortion amplifiers, our famous "Tiger .01". The first amplifier to be designed with our complementary differential input system. Rated at 60 Watts continuous sine wave output into either 4.0 or 8.0 Ohms, "Tiger .01" is 3.0 dB down at 0.1 Hz and 250 KHz. Power bandwidth is 10 Hz to 75 KHz; and IM distortion is of course less than .01% up to rated output. The circuit is housed in a bronze anodized chassis and has an output meter, overheat indicator

lamp and power switch on the front panel. Parts are our usual name brand first quality stuff. In this kit you will find things like RCA, and Motorola transistors, Sprague capacitors and like that. The kit comes with the usual pictorial wiring diagrams, wiring tables and step-by-step instructions.

#207 Amplifier Kit \$77.50 PPD



New—#275 Tiger B

Our latest version of the amplifier that started it all, the faithful old "Universal Tiger". We have switched to our new complementary differential input circuit and put him in a fancy new chassis, but this is still the most economical, low distortion power you can get. Rated at 75 Watt with an 8.0 Ohm load, or 90 Watts with a 4.0 Ohm load with IM distortion less than 0.1% up to rated output. Typically less than .02% at low power levels. Frequency response is -3.0 dB at 0.1 Hz and 250 KHz and rise time is less than 1.0 microsecond. "Tiger B" is the ideal BASIC amplifier for all type of applications Hi-Fi system, public address, instrument amplifier; you name it. As in all of our amplifiers, we have provided all of the protection that we know how to put into a circuit. The outputs stages have volt-amp limiting systems, there are two supply fuses, a line fuse, a speaker fuse and a thermal cutout. "Tiger B" comes in the same chassis as our # 207, but the finish is alodine instead of anodize. For those of you who insist on guilding the lilly, we will have an accessory kit to add an

output level meter, input level control, etc.

# 275 Amplifier Kit \$64.50 PPD



Tigersaurus is our answer to those who want, or need tremendous amounts of power, but insist on it being clean. This amplifier uses the same basic circuit as "Tiger .01", but uses stacked parallel output devices and of course a higher supply voltage. This amplifier can supply 200 Watts continuous sine wave power into 8.0 Ohms and 250 Watts into 4.0 Ohms at less than .05% distortion. Below 100 Watts distortion is typically less than .01%. Output at clipping is typically 300 Watts. Bandwidth is the same as our other amplifiers. The eight output transistors are mounted on over 500 square inches of heat sink for cool reliable operation even at these power levels. There is a large illuminated meter to indicate power output on the front panel and the entire case is finished in a bronze anodized finish for durability and scratch resistance. If you need "beastly" amounts of power this is the amplifier for you.

# 210 Tigersaurus

Amplifier Kit

\$154.50 PPD



## SOUTHWEST TECHNICAL PRODUCTS CORPORATION

219 W. RHAPSODY — SAN ANTONIO, TEXAS 78216

# "Quick 'n Easy" Channel Scanning with ((P)) Pace Scanning Monitors!

## SCAN 10-4 SERIES



New compact design scanner for mobile or base. UHF model covers 450-470 MHz. VHF model covers 144-174 MHz. LF covers 25-50 MHz. Each of the 4 crystal channels is tunable. Either 110 VAC or 12 VDC. Local/distant function switch, lockout switches for each channel, jack for a remote speaker, power cords, mounting bracket and antenna. All of this in an extremely compact size—4 1/2" x 1 1/4" x 6".

## SCAN 150

Rubber antenna shown is optional.



PACE Engineers introduce the revolutionary "SCAN-MATE 150." Only 4 3/4" high, 2" wide and 3/4" thick. SCANMATE 150 scans 4 channels in a 10 MHz band spread within the VHF/hi/FM band. The 4 internal AA Nicad batteries can be charged with optional charger. External or rubber antenna jacks provided. Lockout controls are provided for each channel.

## ((P)) PACE COMMUNICATIONS

Division of PATHCOM INC., 24049 South Frampton Avenue, Harbor City, California 90710  
Export: 2200 Shames Drive, Westbury, New York 11590. Available in Canada.

Circle 23 on reader service card

(continued from page 53)

ns. If you are running any memory very fast, times will occur when the old information or wrong information will be put out until the answers settle down. If this "garbage" time is too great for your application, you can add a latch to the output (perhaps a 74174) to sample the output only during instants when you know the data is good. A very few new memory IC's include internal latches and eliminate this problem.

By the same token, if you are running fast, the ripple and gate times on address changes may cut into your cycle time significantly. Again, if you are running fast, it pays to either use fully synchronous timing or else latch the addresses to get them all changing at once. Some semiconductor mainframes get around the problem by using emitter coupled logic (ECL) and its very high speeds for addressing.


The 7489 has a few obvious and apparently untapped electronic music applications. For instance, you can use sixteen four-bit words to completely specify one cycle of a music waveform, the attack-sustain-decay envelope of a note or a melodic sequence. These run around \$3.50 surplus and under \$11.00 new.

### Other TTL memories

There's quite a few other TTL memories available, some as long as 1024 bits. The 7481 is a very old design arranged as sixteen words of one bit each. The 74170 is called a 4 x 4 file, meaning it is a 16-bit memory arranged as four words of four bits each. The 74200 and faster 74S200 are a 256 x 1 memory or 256 words of one bit each. There's also a bunch of "non-7400" TTL memories. The *Signetics* 8225 is a pin-for-pin replacement for the 7489.
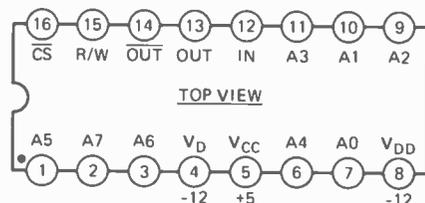
### 1101

The 1101 is a MOS static memory arranged as 256 words on one bit each. It's shown in Fig. 8. MOS memories are gener-



CHIP ENABLE LOW ENABLES OUTPUT  
CHIP ENABLE HIGH DISABLES OUTPUT  
R/W HIGH WRITES  
R/W LOW READS

FIG. 8—256-BIT MOS MEMORY takes +5 and -12-volt supplies. Typical devices are *Signetics* 25L01 and *Mostek* MK4007-4P. Older 1101 devices use same pinout but run hotter and take -9-volt supplies.

ally much cheaper and often much slower than TTL ones. The 1101 works on +5, -9 supplies and runs quite hot. There is TTL compatibility on inputs, addresses and outputs. There are seven address lines, internally decoded to pick one of the 256 bits. There is one input line and two output lines, a normal one and its complement.

To read, you make the chip select low and the read/write low after applying the selected address. The output data will be valid within a microsecond or so afterward.

## the Audio Amateur

A quarterly for the craft audio buff  
FUTURE FARE: A tonearm, pre-amp, a custom Dyna Stereo 70, Hiss filter, Synthesizer, Transmission Line Speakers, A variable inflection 3-way tone control—and much more.

PROJECTS PUBLISHED: a 9 Octave equalizer, Dyna PAT-4 update, power amps and preamps, a simple mixer, two 4-channel decoders and two encoders, 9 octave electrostatic speaker with a matching 900 W., Direct coupled tube amplifier. . . plus much more.

"Absolutely top quality...the only U.S. publication completely devoted to the really serious audiophile constructor."  
—Craig Stark, Columnist, Stereo Review

For a free prospectus & full details:

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
ZIP \_\_\_\_\_

Quarterly: \$7 yr.; 3 years \$20.  
P.O. Box 30R  
Swarthmore PA 19081

## FREE CATALOG of over 1500 unusual tools



A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.

**National Camera**  
2000 West Union Ave., Dept. GBC  
Englewood, Colorado 80110  
(303) 789-1893

Circle 25 on reader service card

high  
quality  
without  
high cost



IN A CONTROLLED  
OUTPUT  
SOLDERING IRON

BY **Weller**<sup>®</sup>

Model W-60. Versatile 60-watt, pencil-type tool with automatically controlled temperature and output. Only 7¼" long. Weighs but 2½ oz. Quick-change, anti-oxidation-coated ¼" screwdriver tip. Several other sizes available with choice of temperature outputs. Use with or without optional, mounted or free-standing bench stand PH-60.

Ask your local distributor or write...

**Weller-Xcelite  
Electronics Division**



**The Cooper Group**

P. O. BOX 728  
APEX, NORTH CAROLINA 27520

Circle 26 on reader service card

To write, you select your address, wait 300 ns, bring the read/write line high for at least 400 ns and then wait at least 100 ns after the write line goes low before changing addresses. As usual, NEVER change the address during, before or immediately after writing.

The 1101 is widely available and costs as little as \$2.56 for probably good surplus units and as little as 50¢ for questionable surplus units. New cost is under \$6.00. One possible application would be using six of them in a data terminal or programmable calculator to store a 256-word message using the ASCII code.

#### Improved 1101's

The original 1101's were rather slow and could take as long as 1.5 ms to read. They are very hot running and the -9 supply is usually a rather weird thing to have to provide. Improved devices are now available. An 1101A1 cycles in one microsecond maximum. The *Signetics* 25L01 and the *Mostek* MK4007-4P are second-generation, pin-identical, versions that cycle in under a microsecond, consume much less supply power and work on standard +5, -12 supplies.

#### CMOS RAM's

One new type of 1101 replacement is the CD4061, a CMOS device made by RCA. This is a pin-for-pin replacement, but being CMOS, it takes only one supply and draws utterly negligible supply power if you aren't writing or changing the address. Thus, you can use this with a very small battery for power down storage and still hold the information. You can also run on incredibly lower currents than the 1101 style devices and much faster as well—several hundred nanoseconds. This makes the 4061 ideal for hand-held data equipment and calculators, as well as meter readers and things like this. The only hitch—it's a new device and still costs \$40.00. Maybe next year.

Other CMOS memories include the *Motorola* 14505 (64 × 1), the *Solid State Scientific* SCL5554 (256 × 1) and the *Inselek* A5503 (256 × 1).

#### 1103

The main reason we include the 1103 here is as a warning NOT to try and use it—unless you have lots of fancy equipment and considerable experience. This is especially true of surplus 1103's.

The 1103 is a 1024-word x 1-bit dynamic shift register. It is very low in cost. It ranks as the all time most successful single integrated circuit and it toppled "king core" from the computer world. The device trades a very simple and very dense internal circuit for quite a bit in the way of outside support circuitry. This IC needs critically controlled clocks, usually needs an output sense amplifier, and has a complex timing sequence so elaborate that a 30-ns overlap error in the wrong place will cause information dropout. The 1103 is eminently suited for large memories of at least 50,000 bits (this is tiny by mainframe computer standards) or so, where all the critical support circuitry is easily worked with and may be offset by the savings you get by cramming 1000 bits in each package.

The 1103 uses capacitors for internal data storage. The data must be moved around or refreshed at least 500 times per second.

(continued on page 98)

pliers  
pliers  
pliers

BY **Xcelite**<sup>®</sup>

ALL THE TYPES  
YOU NEED IN A  
FULL RANGE OF SIZES

From 4" miniature electronics to 10" utility. Precision made in U.S.A. Forged alloy steel construction. Cleanly milled, perfectly aligned jaws. Hand-honed, mated cutting edges. Most with Cushion Grip handles.



#### INCLUDING

- 5" Bent Thin Chain Nose. For handling fine wires in close quarters. No. 79CG
- 5½" Thin Needle Nose. For firm gripping and looping of wires. No. 57CG
- 4" Full Flush Cutting Diagonals. Snap cuts to the extreme tip. No. 84CG
- 5" Midget Slip Joint. Narrow jaws for close quarters. 3 openings to ½". No. 50CG

Ask your local distributor or write...

**Weller-Xcelite  
Electronics Division**



**The Cooper Group**

ORCHARD PARK, N.Y. 14127

Circle 27 on reader service card

# We're too British to boast. So here's what the experts say about us.

Rather than appear immodest, we'll let the experts who write for the audio publications tell you about an automatic turntable we're quite proud of—our 810QX Transcription Series model.

## High Fidelity magazine says:

"The new cam system in the 810QX is credited with providing smoother and quieter operation than in past models. Average flutter was very low at 0.05%; total audible rumble by the CBS-APLL method was -52db. The arm has negligible friction laterally and vertically, and requires a 0.3 gram stylus force for automatic trip. Taking it all together—performance, features, styling—the BSR 810QX moves into ranking place among the best automatics we know of."

## Stereo Review magazine says:

"The BSR 810QX has an unusually complete array of operating controls and adjustments, yet is simple to use. The wow and flutter were very low—respectively 0.03 and 0.045% at 33 $\frac{1}{3}$  rpm and 0.05 and 0.04% at 45 rpm. The BSR 810QX, undeniably a well-constructed and attractively styled record player, was also a very easy one to operate. The controls had a smooth, positive feel and action."

This is a modest way to tell you how good our 810QX Transcription Series turntable really is. We would be pleased to send you detailed specifications. Just drop us a note.

BSR (USA) Ltd., Blauvelt, N.Y. 10913



McDONALD  
BSR (USA) Ltd.  
Blauvelt, N.Y. 10913



Circle 28 on reader service card

## USING THE VOM AROUND THE CAR

by JACK DARR  
SERVICE EDITOR

HERE ARE A FEW HANDY TRICKS AND TESTS you can make with a standard volt-ohmmeter (vom), around a car, boat, motorhome or anything with a dc power supply system. The primary source of power here is a storage battery with a recharging system. These systems are about as simple as you'll get, electrically speaking. There will be a hot wire from the battery to all devices, and the frame of the vehicle itself serves as the return or ground. When the engine is running, the battery is being recharged by a generator or alternator. That's all she wrote.

Whenever you have any kind of electrical trouble, you need some way to get a handle on the problem. The first thing to check is the condition of the battery. Using the 0 to 15 or 0 to 20-volt dc range of the vom, check this at any convenient point, usually at the battery itself. Normal voltage of a fully charged battery should be 12.6 volts. Simple test for condition of charge: switch on a medium load, like the headlights. The voltage shouldn't drop more than a fraction

# TeleMatic

## TUNER-MATE

KT-730  
MADE IN USA

TUNER—ANTENNA  
TROUBLE  
DETECTOR



ZEROS IN ON THE PROBLEM  
... SAVES HOURS!

- Instant Tuner Check
- Antenna Performance Test
- Pinpoint I.F. Signal Loss
- Shielded—Metal Case

Exclusively Thru Distributors

# TeleMatic

FREE Reference Charts. Telematic, Brooklyn, N.Y. 11207

Circle 29 on reader service card

Everything you wanted to know about CD Ignition Systems but didn't know whom to ask.

Send for FREE Tiger booklet (20 pages) which answers all your questions.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

CLIP OUT THIS AD AND SEND TO—

**TRI-STAR CORP.**  
P. O. Box 1727 Dept. H  
Grand Junction, Colo. 81501

Circle 30 on reader service card

# appliance clinic

of a volt. If it goes down to 8 to 10 volts, the battery needs recharging.

For the simplest check on whether the recharging system is working, start the engine and then read the voltage across the battery. Of course, if the battery won't turn the engine over, that answers your question. If it does start, the voltage should go up to about 14.5 volts. This shows that the generator or alternator is trying to charge the battery, anyhow. Unfortunately, this won't tell you whether the battery will take a charge or not. The voltage regulation of the system is very good, and it won't let the voltage go higher than 14.5 volts, even on a battery with a bad cell.

You can start the engine with jumper cables from another car. There is a right and wrong way to do this, too. WATCH the POLARITY! All US made cars, and a great many foreign cars, have a negative ground connection.

Connect the black cable from ground to ground on each car. Any good clean bolt, etc. makes a good contact. Now hook the red cable to the positive battery post of the good one, and to the positive battery post of the dead one. Start the engine of the helper car. NOW try to start the engine of the dead one. This lets the generator of the helper car carry the load. (In some British cars, such

as MGB's, if you raise the bonnet, which is the tin thing covering the motor, you'll see a little label saying "This vehicle wired negative earth." Same thing.)

## Cable testing

If the car starts slowly, there may be other things wrong besides a low battery. Bad contact between the battery cable terminals and the battery posts is one. To check for this, put one prod of the vom on the end of the battery post itself, and the other on the cable terminal. Push hard to make a good contact, and then hit the starter. If you see any *voltage reading* at all, this contact is dirty. Use the lowest scale on the vom for this, for accuracy. If you see even 1.0-volt reading on this test, take the terminal off, and clean both post and inside of the terminal, and bolt it back on very tightly. Recheck.

Second check: put one prod of the vom on each post of the battery (not on the terminals; the post itself). Note the reading, then crank the car. The voltage should not drop below about 9 or 10 volts. If it does, the battery may be low.

If you don't get much voltage drop on the battery itself, take the same reading from the terminals. A drop here indicates a dirty contact between post and terminal; clean it

up. If the voltage stays up at this point, but the starter cranks slowly, put one prod on the negative terminal of the battery and the other on a good clean bolt on the engine itself. Hit the starter. If you get any voltage reading, even on the lowest scale, the battery's ground cable isn't making good contact somewhere. You're reading a voltage drop across what should be practically a zero resistance. Loading it with the heavy current of the starter will show it up instantly.

## Dim lamps

In some cases, lamps on the car or motorhome will be mysteriously dim, though the battery checks good. This is usually due to corrosion or a dirty contact at the lamp socket. Take the bulb out, and scrape the terminals and shell clean. Check the socket for dirt or foreign matter.

If it's still dim, connect the negative vom lead to the frame, and check the voltage on the hot wire at the lamp socket. If this reads the full normal voltage, take another reading, this time from the negative (shell) of the lamp socket to the nearest ground. This, of course, should be zero, if the ground connection is good. If you see a 2 to 3-volt reading here, connect a jumper wire

(continued on page 90)

## INTERNATIONAL Frequency meter FM-2400CH

MOBILE

The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz. The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability:  $\pm .0005\%$  from  $+50^\circ$  to  $+104^\circ\text{F}$ .

Frequency stability with built-in thermometer and temperature corrected charts:  $\pm .00025\%$  from  $+25^\circ$  to  $+125^\circ$  (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

WRITE FOR CATALOG!

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation



FM-2400CH (meter only).....	\$595.00
RF crystals (with temperature correction).....	24.00 ea.
RF crystals (less temperature correction).....	18.00 ea.
IF crystals.....	catalog price



CRYSTAL MFG. CO., INC.  
10 NO LEE • OKLA CITY OKLA 73102

Circle 61 on reader service card


# If you can use any of these tools...



**You could build  
this Bell & Howell  
25-inch diagonal  
color TV with  
digital features!**

# It's just part of a fascinating learn-at-home program in electronics from Bell & Howell Schools!

Simulated TV picture

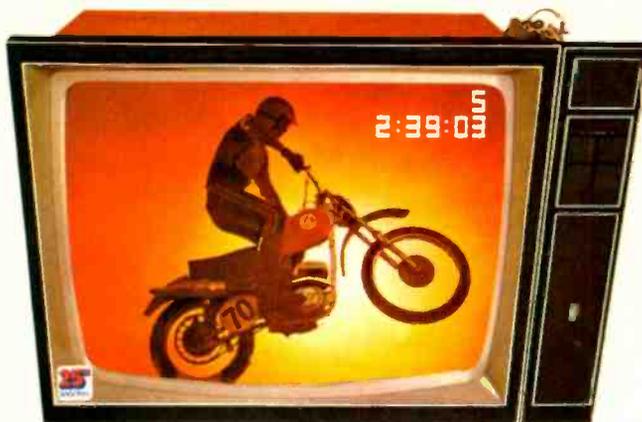

If you're handy with a set of tools, you may already have some of the skills you'll need to build Bell & Howell's color TV... the TV with digital features! This program is the perfect way to discover the exciting field of digital electronics... and best of all, you can do it all at home, in your spare time. Get free information now about this first-of-a-kind learn-at-home program prepared for you by skilled instructors at Bell & Howell Schools.

## Discover a new way to spend your spare time hours on evenings and weekends

Even if you have no prior background in electronics, you'll find digital electronics a fascinating world to explore. You'll enjoy spending hours reading about the systems of digital circuitry, performing experiments to test what you learn, and building this advanced color TV. It's completely absorbing, and you're spending your spare time learning something new that could open up extra income opportunities for you.

## Find out all about electronics equipment and how it works

Once you complete this learn-at-home program, you'll have the specialized skills to service color TV's plus the knowledge that you can apply to repair a variety of home electronic equipment. And because this Bell & Howell Schools' program includes the study of digital circuitry, you'll be among the first with professional home training in digital electronics, a field that's growing in importance every day.

## No electronics background necessary

We start you off with the basics. You'll receive a special Lab Starter Kit with your first lesson so that you can get immediate "hands on" experience to help you better understand newly-learned electronics principles. Later, you'll use your knowledge and learn valuable skills as you build the color TV. You can take full advantage of our toll-free phone-in assistance service throughout the program and also our in-person "help sessions" held in 50 cities at various times throughout the year where you can "talk shop" with your instructors and fellow students. You learn valuable skills in electronics through experiments and testing as you build this advanced-design color TV.

## You build and work with a revolutionary color TV

Discover the technology behind such extraordinary features as channel numbers that flash on the screen, an on-screen digital clock that flashes the time in easy-to-read numbers, and an automatic pre-set channel selector that allows intermixing of VHF and UHF channels in any sequence. You'll enjoy probing into advanced performance features like silent all-electronic tuning,

Black Matrix picture tube, "state of the art" integrated circuitry, and the 100% solid-state chassis that makes possible a brighter sharper picture with long life and dependability.

## You also build Bell & Howell's exclusive Electro-Lab® electronics training system

You get valuable experience performing experiments and later testing your TV with a digital multimeter, solid-state "triggered sweep" oscilloscope, and design console you build yourself.

## The skills you learn can lead to part-time income or a new career in a business of your own

While many of our students do not ask for employment assistance, it is available. We will help you look for a job in a field of electronics that best fits your interests and abilities. Of course, no assurance of income opportunities can be offered. One thing you can be certain of: no better or more practical at-home training in electronics is available anywhere.

## Channel numbers that flash on the screen

## Digital clock that flashes on the screen

## Automatic pre-set channel selector



Find out more about this fascinating program... mail the card today for full details, free!

This Bell & Howell Schools' program is approved by the state approval agency for Veterans' Benefits. Please check the box on the card for free information.

If card has been removed, write:  
An Electronics Home Study School  
DEVRY INSTITUTE OF TECHNOLOGY

668R2




ONE OF THE  
**BELL & HOWELL SCHOOLS**

4141 Belmont, Chicago, Illinois 60641
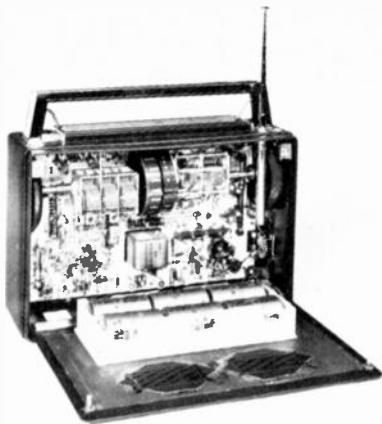
# new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.


**PORTABLE SHORTWAVE RECEIVER, model XCR-30.** All solid-state set features direct frequency readout. Uses multiple heterodyne circuit (interpolation and crystal oscillators); provides precision no-gap tuning from 500 kHz to 30 MHz. A 1-MHz crystal — in conjunction with the Wadley Loop circuit (Racal) — stabilizes received frequency and eliminates drift. Tuned frequency is displayed mechanically as a com-



posite function of two dials; the whole number (in MHz) shown on one dial drum and the decimal portion (in kHz) shown on the second. Reception modes include AM, CW and switchable (LSB or USB) single sideband. There are provisions for an external 9-12 volt dc supply, ear-phone reception and an external antenna (there is a built-in collapsible whip antenna). 11-1/2 x 7-1/2 x 3-7/8 in.; 9 lbs. 2 oz.; about \$260.00—Giffler Associates, Inc., 52 Park Avenue, P.O. Box 239, Park Ridge NJ 07656.

Circle 31 on reader service card

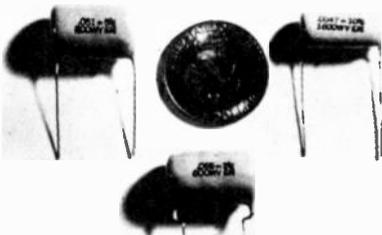**CAPACITORS.** El-Menco polypropylene dielectric capacitors are used in the audio to ultrasonic frequency range. Dissipation factor at 1 kHz is not greater than 0.1 percent and insulation resistance is greater than 10 gigohms. Capacitance drift after a temperature cycle from -55°C to +85°C is less than 0.5 percent.



Temperature coefficient is  $-200 \pm 150$  ppm/degree C. Features: film and extended foil construction, radial leads securely attached and fire retardant encased.

Type PPD series covers range of values from .0018 to .47  $\mu$ F at dc rated voltages of 200, 400 and 600. Type PPDS series covers range of values from .001 to .1  $\mu$ F at 600, 1000 and 1600 volts dc. Tolerances for both types are  $\pm 2$ ,  $\pm 5$ ,  $\pm 10$  and  $\pm 20\%$ . — International Electronics Corp./El Menco, 316 South Service Road, Melville, N.Y. 11746.

Circle 32 on reader service card

**QUADRIPHONIC RECEIVER, model 434** features 64 watts (4 x 16) rms continuous, all channels driven into 8 ohms at rated power bandwidth (28—22,000 Hz). FM sensitivity: 1.8 mV. Has front/rear SQ logic circuitry; CD-4 demodulator; "joystick" channel balance control.



Amplifier strapping combines power output of all channels for stereo operation.

There are two tuning meters — center-of-channel, signal strength; loudness contour with automatic shut-off when level is raised; illuminated mode indicators; Baxandall-type bass and treble controls; FM muting, jacks for 2- or 4-channel headphones; 4-channel recorder output jacks and tape monitor circuit.—Fisher Radio, 11-40 45th Road, Long Island City, NY 11101.

Circle 33 on reader service card

**MIXER POWER AMPLIFIERS** feature low distortion, extended and linear frequency response, low noise content and continuous wattage output. Model UPD-120T offers 20 watts  $\pm 1.5$  dB at less than two percent THD from 50 to 15,000 Hz. Model UPD-60T provides 60 watts and UPD-30T has 30-watt power output




with same specifications. All three models incorporate straight-line fader controls for mixing, equalization and mastering.

Master bass and treble controls,  $\pm 10$  dB at 80 Hz (bass control) and  $\pm 10$  dB at 8000 Hz. Master gain control provides simultaneous regulation of all six input channels. Other features: pre-installed transformers for balanced 150-ohm mic level inputs; input and output jacks for signal processing from external equalizer or compressor, tape/booster output that produces maximum of plus 30 dBm for use with tape recorders or bridging additional power amps; signal-to-noise is 75 dB — University Sound, 1515 South Manchester, Anaheim, Calif. 92803.

Circle 34 on reader service card

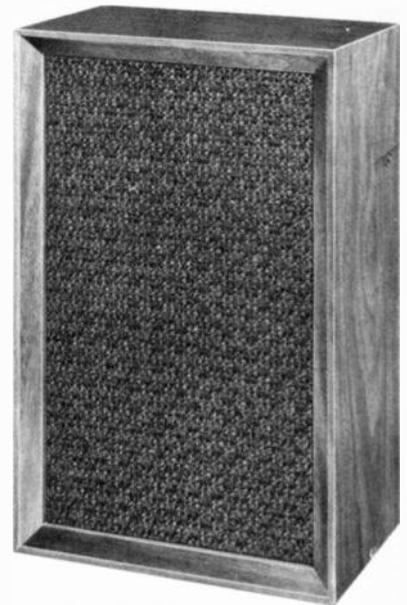**3-WAY LOUDSPEAKER SYSTEM, model AS-5.** Features a 10-inch high-compliance woofer that uses a 4-layer high temperature copper voice coil and 35-Hz resonance; 6-inch mid-range driver that uses damped cloth suspension and



sealed chassis; 3-1/2-inch direct radiator tweeter. Electrical crossovers provide frequency division within the system's range of 40 Hz to 18 kHz. Power capacity is 25 watts program, 50 watts peak. Nominal impedance is 8 ohms. 12-1/2 x 22 x 9 in.; 27 lbs.; finished in deep walnut with brown-and-black tweed grille fabrics; \$69.95—Utah Electronics, 1124 East Franklin Street, Huntington, Ind. 46750.


Circle 35 on reader service card

**MARINE CB ANTENNA, Lancer style 4039** requires no ground plane—works equally well on fiberglass, wood or metal boats. Features end-fed half-wave design and impedance-matching cable with thread base for ratchet folding mount (style 366). All antenna fittings are corrosion-proof nickel-chrome plated brass. 10-1/2 feet; complete with harness \$33.95.—Shakespeare Co., Industrial Fiberglass Div., P.O. Box 5806, Columbia, S.C. 29250.

Circle 36 on reader service card

**AMPLIFIER, model 4070** is rated at 70 watts total continuous power. Unit produces more than 15 watts per channel in *Quadradial* mode. Compatible with stereo with bridging circuits

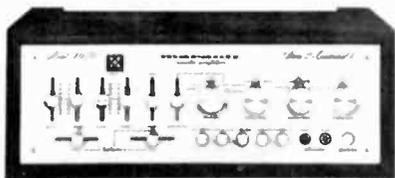producing full stereo power of more than 35 watts per channel. Total harmonic distortion at rated power is 0.5%. Pre-out/main-in facilities are provided on rear panel, allowing preamplifier section and output amplifiers to be used independently. Four-channel facilities include



decoder pocket on bottom panel that accommodates optional SQ-decoder or any advance in 4-channel matrix technology.


Built into amplifier is exclusive Vari-Matrix, a synthesizer that derives 4-channel sound from both stereo and matrix-encoded sources. A dimension control is provided for fine tuning 4-channel effect. Unit incorporates facilities to accommodate discrete demodulator for reproducing 4-channel sound from CD-4 discs and discrete tape sources. Other features include separate slide-type front-to-rear and left-to-right balance controls, separate professional slide-type bass and treble controls, loudness compensation, low and high filters and tape/source monitoring. \$299.95 — Marantz Co., Inc., P.O. Box 99, Sun Valley, Calif. 91352.

Circle 37 on reader service card

**PROGRAMMER** can program any MITS desktop calculator to do long or often used calculator operations. Instead of repeatedly entering into calculator a formula in which only certain variables change, a formula can be entered once into programmer and then be stored at will. Automatically executes all steps of program until it sees a location within the formula where a variable is to be entered. It then halts execution, but once the variable is entered into
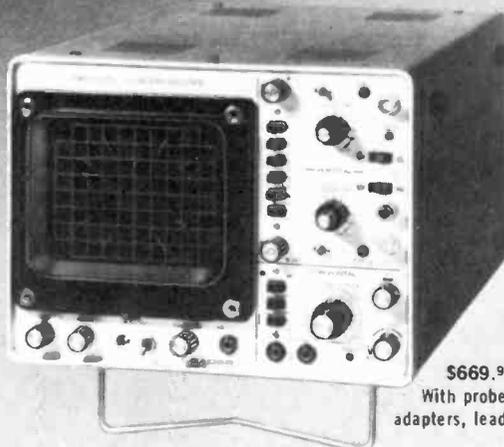
# LEADER... outduals them all!

LBO-505  
5" DUAL TRACE  
DUAL CHANNEL  
TRIGGERED SCOPE



Compact, economical, solid state accuracy. For prod'n, field maintenance, quality control, lab, design & testing.

**Features —**

- 15MHz bandwidth
- Trig. & auto. sweep — from 100 nanosec/cm (10X mag.) to 0.5sec/cm, 17 steps calibr'd.
- AC/DC coupling per chan.
- Separate or simultaneous sweep display of ch 1 & 2 — alternating, chopped, algebraically added & vector (X-Y).
- 10mVp-p/cm vert sensitivity.
- Cont. scale illumination w/front panel control.
- 7<sup>3</sup>/<sub>8</sub>" H x 9<sup>7</sup>/<sub>8</sub>" W x 15" D, 14 lbs.

\$669.<sup>95</sup>

With probes, adapters, leads.

"Put us to the test"

**LEADER**  
INSTRUMENTS CORP.

151 Dupont St., Plainview, L.I., N.Y. 11803 (516) 822-9300

Circle 62 on reader service card



THOUSANDS OF BARGAINS — TOP VALUES IN Electronic Parts

Transistors, Modules, Speakers, Stereo, Hi-Fi, Photo Cells and thousands of other Electronic Parts. Send for **FREE** Catalog




ELECTRONIC DISTRIBUTORS INC.  
Dept. TA-2, 4900 Elston  
Chicago, Ill. 60630

RUSH CATALOG

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

Circle 64 on reader service card

## Assemble this digital clock and calendar in just one evening... get continuous readout of hour, minute and second, plus month and day.

This new Digital Concepts electronic digital clock and calendar indicates the hours, minutes and seconds... or the month and the day... or alternates between time and date at 10 second intervals. Glowing orange digital readout (a continuous character .55 inch high) is visible from almost any viewing angle, no matter how light or dark the room.



Operation is totally silent, with accuracy to within seconds a month; life expectancy is an incredible 100,000 hours.

**CHOICE OF DISPLAY MODES**

You can decide to display time only, date only, or a continuous 10-second cycle in which time alternates with date. You can operate on a 12-hour or 24-hour international time sequence. And you can change all display modes instantly — any time you wish — by flicking simple controls.

**BEAUTIFUL, AND BEAUTIFULLY EASY TO ASSEMBLE**

The contemporary hand rubbed oiled walnut cabinet is ideal for home, office or place of business. And a very memorable gift. All components of the kit mount on two interlocking printed circuit boards, for easy assembly in one evening, using only a soldering iron and a pair of diagonal cutters. The only wire in the kit is the line cord. Accuracy is assured by one MOS/LSI integrated circuit "chip" and top quality electronic components throughout.

The Digital clock and calendar is also available factory assembled.

**ORDER NOW FOR IMMEDIATE DELIVERY**

Send this coupon with your check or money order for fast delivery anywhere in the world. Money back guarantee if not fully satisfied.

## digital concepts

Digital Concepts 249 Route 46, Saddle Brook New Jersey 07662/(201) 845-7101

Enclosed please find my check or money order for \$ \_\_\_\_\_ or charge my Mastercharge account number \_\_\_\_\_, expiration date \_\_\_\_\_ to cover the following order:

- \_\_\_\_\_ kit(s) of electronics only, Model CK-100 @ \$68.00 each
- \_\_\_\_\_ cabinet(s), with face and mounting hardware, Model C-31 @ \$18.00 each
- \_\_\_\_\_ factory assembled calendar/clock(s), Model EC-102 @ \$108.00 each

Add \$3.00 to cover costs of postage and handling. New Jersey residents add 5% Sales Tax

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 63 on reader service card

calculator, the continue key is pressed again and all remaining steps of formula are executed



until programmer sees another variable entry or end of program command.

Each key of calculator is represented by special alphanumeric programmer code. Code is entered into programmer by depressing ap-


propriate programmer keys associated with each code. Once a complete program has been entered, user can return to beginning address and either run program from start to finish or step through each instruction, executing them one at a time. Features 256 programming steps with optional expandability to 512 steps, constant power to RAM's to preclude destruction of stored programs, 16-key array to enter the address or instruction in hexadecimal. Kit form \$199.95; assembled unit \$299.95 — MITS Inc., 6328 Linn, N.E., P.O. Box 8636, Albuquerque, N.M. 87108.

Circle 38 on reader service card

**CAR STEREO & SPEAKER SYSTEMS, Chameleons.** Three models feature a removable, exchangeable front panel that can be modified, mixed or matched to suit the consumer's mood and the car's stereo. Sound from the stereo speakers emanates from both around and through the fabric or graphics display

panel. All panels have the tilt-up look.

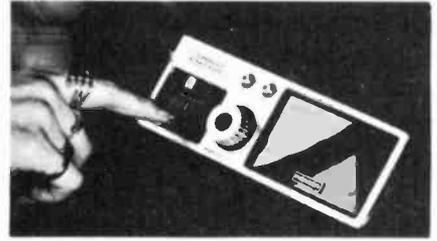6½ inch speakers fit into a variety of locations



three 8-track under-dash units: TP801 features an AM/FM radio; TP800 has an FM radio and TP828 is the 8-track unit alone. — Pioneer Electronics of America, 1555 East Del Amo Blvd., Carson, Calif. 90746.

Circle 39 on reader service card

**CASSETTE DECK, model CD-1000** is designed as a stereo component with front loading. Front panel contains headphone jacks, two VU meters, microphone jacks and tape counter with



memory rewind. Tape motion and direction is visually indicated.

Features solenoid assisted piano key controls for play, stop, rewind and fast forward; Dolby noise reduction system which eliminates tape noise and hiss; tape selector switch for regular, low-noise and chromium dioxide tapes; built-in illumination for head cleaning. Also contains a locking pause control, separate clutch-coupled

**1159 TUBE BONANZA!**  
20  
Assorted tubes for \$1.00  
Untested (some will be good, some bad).  
TAKE A CHANCE FOR \$1.00

**SLIDE SWITCHES**  
12 for \$1.00  
All types, SPDT, DPDT, etc. 1106

**TRANSISTOR REPAIR KIT**  
\$1.00  
Includes resistors, condensers, transistors, transformers and various & sundry parts used to repair transistor radios, walkie-talkies, tape recorders, etc. 1107

**PRECISION RESISTORS**  
60 for \$1.00  
All 1%, ½ watts & 1 watt. From low to high ohmages. 1113

**DUAL POTENTIOMETERS**  
25 for \$1.00  
Assorted ohmages. Originally for Hi-Fi, Stereo and TV. 1123

**TIE LUGS**  
50 for \$1.00  
From 2 lugs up to 14 lugs. 1143

**MISCELLANEOUS MINIATURE TUNING METERS.**  
2 for \$1.00 1190

**MONEY BACK GUARANTEE**  
Terms: Minimum order \$4.00. Include postage. Either full payment with order or 20% deposit, balance C.O.D.  
**FREE CATALOG**

**BARGAIN BONANZA OF EDLIE HIGHEST QUALITY KITS ONLY NEW PRODUCTS EXCELLENT MIXTURE**

**1188 GIANT PACK OF ASSORTED TRANSISTORS**  
Silicon Planar  
Untested, NPN & PNP  
Power, Audio, RF  
100 for \$1.98

**LED's in working condition**  
3 green or 3 yellow 3 for \$1.00 1101  
10 LED's asst. in working conditions \$1.00 1102  
7 segment \$1.25 each readouts 1103

**VOLUME CONTROLS**  
20 for \$1.00  
Wire wounds & carbons, up to 1 meg, some with switches. 1126

**10 SHIELDED WIRE ASSEMBLIES for \$1.00**  
With RCA molded plug at one end & tinned wire at the other. 1145

**WRITE FOR FREE VALUE PACKED CATALOG**  
**BONUS FREE CAPACITOR KIT**  
With Every \$5 Purchase

**DISC CAPACITORS**  
60 for \$1.00  
Assorted capacitances from .0001 to .1. Different voltages, mostly 600 volts N.P.O. N750. 1140

**MINIATURE TRANSISTOR ELECTROLYTES**  
13 for \$1.00  
Some axial leads, some vertical mount, mixed capacitances and mixed capacitances and mixed voltages. 1159

**MINIATURE POTS**  
12 for \$1.00  
Used in transistor and miniature applications. 1141

Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year. Most are of such standard makers as RCA, GE, etc.  
**RADIO & TV Receiving**  
Any 3 for \$1.19

114, 1S5, 3CB6, 3DG4, 3EH7, 3EJ7, 3KT6, 3S4, 3Q4, 4BC5, 4BN6, 4BU8, 5CZ5, 5J6, 5T8, 5U4, 6AC7, 6AB4, 6AF4, 6AG5, 6AJ8, 6AK5, 6AK6, 6AL5, 6AQ5, 6AU6, 6AX4, 6BA6, 6BA11, 6BL8, 6BN4, 6BQ6, 6BS3, 6BU8, 6BW4, 6BZ6, 6CB6, 6CD6, 6CF6, 6CG7, 6CG8, 6CM3, 6CQ4, 6DA4, 6DE4, 6DG6, 6DK6, 6DN7, 6DT6, 6DW4, 6EA7, 6EH5, 6EHB, 6FD7, 6FM7, 6FG7, 6GF7, 6GHB, 6GK6, 6GL7, 6GM6, 6GN8, 6GU7, 6GV5, 6HE5, 6HJ7, 6HJ8, 6HS8, 6J6, 6JN6, 6JW8, 6K7, 6K11, 6KY8, 6LF8, 6LY8, 6SA7, 6SH7, 6SN7, 6SV7, 6TB, 6T10, 6V4, 6W4, 6X4, 7GS7, 8CM7, 8CN7, 8EB8, 8SN7, 12AD6, 12AE7, 12AU7, 12AT7, 12AU6, 12AV5, 12AX4, 12BA6, 12BE6, 12BH7, 12BY7, 12CB, 12CN5, 12DS7, 12R5, 12SC7, 12SN7, 18FW6, 19T8, 2.EZ7, 22BW3, 35Y4, 36AM3, 50B5.

**25 ASSORTED POLYSTYRENE TOP GRADE CAPACITORS**  
Used by Hi-Fi manufacturers in most sets 1175

**Electronics Bench Manual**  
"EBM"

**WHAT'S AN "EBM"???**

Over 1,000 Illustrations and Tables, high-density text equivalent in content to a whole collection of other books, arranged in specific sections on:

- BENCH PLANNING & LAYOUT...BASIC BENCH SUPPORT FACILITIES...HAND SOLDERING...CONSTRUCTION & ASSEMBLY...SEMICONDUCTORS...ELECTRON TUBES...RESISTORS, POTENTIOMETERS & RHEOSTATS...CAPACITORS & ELECTROSTATIC DEVICES...INDUCTORS & ELECTROMAGNETIC DEVICES...SWITCHES & RELAYS...WIRE & CABLE...DISPLAYS, INDICATORS & METERS...ENERGY SOURCES...HARDWARE, FINISHES & HOUSINGS...MECHANICAL DEVICES, MOVEMENTS & ACTUATORS...DEVICE & COMPONENT DATA...GENERAL TABLES & FORMULAS...TIME & FREQUENCY SERVICES...APPLICATIONS & CIRCUITS.

Each as a separately bound book section, which can be detached for use on the bench, or used right in the rugged solid polyethylene binder supplied.

**ORDER YOURS TODAY!**

Check, Money Order, BANKAMERICARD or MASTERCARD  
(Write or Call with Account #)  
**STILL ONLY \$17.95** TECHNICAL DOCUMENTATION  
BOX 340  
CENTREVILLE, VA 22020  
703-830-2535

rotary record and output controls and an input line/mic selector switch. \$299.95. — Benjamin Electronic Sound Co., 40 Smith Street, Farmingdale, N.Y. 11735.

Circle 40 on reader service card

**MICROPHONE, Trucker model 555.** Noise-cancelling power microphone for CB application has been field tested on actual hauls by truckers. Sound waves of speech about 1/4 inch from lips are curved and accepted by special microphone cartridge and diaphragm. After traveling from distances beyond 1/2 inch, sound waves start to flatten out and microphone cartridge is insensitive to waves in this flat form.



Has high impact charcoal grey Cylolac case, three-conductor (one shielded) coiled cable that extends to eight feet, press-to-talk switch that springs to off position when released and a mounting bracket for vertical or horizontal mounting. Solid-state amplifier and piezo elec-

tric ceramic element resist temperature and humidity extremes. Factory wired for electronic type operation, it converts if relay type switching is required. Output is adjustable over 40 dB range with control knob furnished or with small screwdriver. Output impedance is under 5000 ohms and recommended load is 100 ohms and up to open circuit. 3-3/8 x 2-3/8 x 1-19/32 in.; 10-3/4 oz with cable. — Astatic Corp., Box 120, Conneaut, Ohio 44030.

Circle 41 on reader service card

**OSCILLOSCOPES, models 37 & 27.** Model 37 is a 3-inch scope, that operates over a bandwidth from 5 Hz to 2.5 MHz; in either 110-120 V or 220-240 V models for either 50 or 60 Hz. Input impedance: 1 meg-ohm shunted by 30 pF; maximum input: 400 V; synchronization: internal plus or minus and external; external band-



width: 5 Hz to 300 kHz; draws 25 watts; 4 x 8-1/4 x 10-3/4 in.; 11 lbs.; \$165.00.

Model Systems 27 is a 5-inch scope, has 5-inch CRT and operates over bandwidth from dc to 2.5 MHz; in either 110-120 V or 220-240 V models for either 50 or 60 Hz. Additional application is television line and field synchronization. Input impedance: 1 megohm shunted by 30 pF; maximum input: 400 V; synchronization: internal plus or minus, external, TV line and field; external bandwidth; dc to 300 kHz; 7 x 10-1/2 x 17 in.; 15 lbs.; \$280.00.—Systems Electronics, Inc., 9727 Inglewood Avenue, Inglewood, CA 90301. R-E

Circle 42 on reader service card

The Ultimate in Ignition Systems!

★ **ELIMINATES BREAKER POINTS.**  
Perfect Timing and Dwell never change!

★ **Eliminates Tune-ups.**  
Never wears out or needs any Maintenance.



★ **The Most Advanced**  
"OPTO-ELECTRIC SYSTEM"

● The Allison Breakerless System eliminates the Points and Condenser, replacing them with an Opto-Electronic Trigger, using a Light-Emitting Diode and Phototransistor. Also completely eliminates wiper-arm "friction" wear. The only "TRUE" Electronic Ignition ... that you can install for under \$100. Gives 40-times more Timing Accuracy than ANY system using mechanical Breaker-Points! Unlimited RPM. Smoother running. (No timing fluctuation as with Magnetic units). Unaffected by Temperature, Moisture, or Vibration! All Solid-State Components. Easier Starting under any condition! Increased Horsepower. Sparkplugs last longer. Perfect timing increases engine Efficiency and Gas Mileage up to 30%!

● **Quick and Easy Installation!**  
★ **Tested and Proven reliability.**

Only \$49.95 ● **SATISFACTION GUARANTEED!**

● Complete ● **1-YEAR FACTORY WARRANTY.**

(State Make, Year, Engine Size). (Calif. Res. add Tax)

● **CONVERT YOUR "C-D" UNIT TO BREAKERLESS!**  
"TRIGGER-UNIT" ONLY \$34.95


★ **Send Postcard for FREE BROCHURE Today.**

**ALLISON AUTOMOTIVE CO.**


P.O. Box 881-L, TEMPLE CITY, CAL. 91780

Circle 67 on reader service card
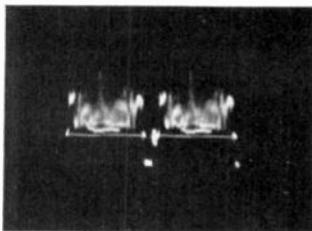
## RCA's new 3-inch scope...an entire servicing system for only \$229.\*



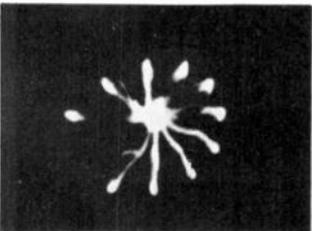1. It's an 8 MHz general-purpose scope. Typical sine-wave display.



3. It's a Vectorscope for color TV AFPC alignment. Color bar generator used for test signal.


For fast delivery and full information on the new WO-33B, contact any one of the more than 1,000 RCA Distributors worldwide. Or write: RCA Electronic Instruments Headquarters, Harrison, N.J. 07029.

Specialists demand the best tools of their trade.




**RCA** Electronic Instruments

Circle 68 on reader service card

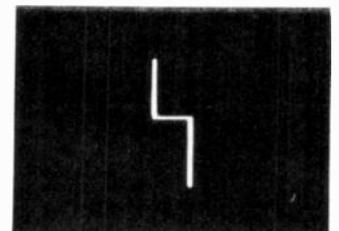

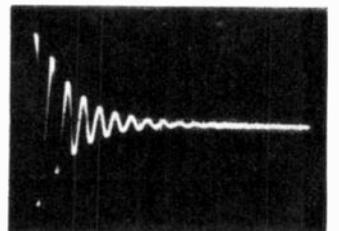2. It's a "Quicktracer" Transistor/Diode and Component Tester. Typical junction waveform.



4. It's a "ringing" tester for coils, yokes, transformers. Typical ringing test pattern.

5. It includes the WG-400A Direct/Low-Capacitance Switch Probe and Cable with BNC type connector, and a special "Quicktracer" probe.

\*Optional price

# WAHL® QUICK CHARGE CORDLESS SOLDERING IRON

We couldn't make the best better.  
So we made it three times faster.

Our original 'Iso-Tip' had all the features that people need: complete portability; soldering heat in 5 seconds; up to 125 electronic joints or more per charge; battery operated to eliminate AC leakage and the need for grounding; and "lock off" switch to prevent accidental heating. Complete with separate 'drop in' recharging stand.

We use premium quality nickel cadmium batteries that recharge in 1/3 the time of the standard Wahl iron — one to two hours for a partially discharged unit, four and a half hours for completely discharged battery. It still gives tip performance up to 50 watts and over 700° temperature.

So don't think of our new orange "Quick Charge" cordless soldering iron as a better iron. It's already the best. It's just three times faster.



Circle 69 on reader service card

**WAHL® CLIPPER CORPORATION**  
Sterling, Illinois 61081•815-625-6525

"Manufacturing Excellence Since 1919"

## APPLIANCE CLINIC (continued from page 81)

from the socket to a ground. If this brings the lamp to normal brightness, take the original ground connection off and clean it. These are generally pigtailed from the socket to a nearby bolt on the frame. Many tail-lamps, etc. on modern cars are mounted in plastic. So, they must have a pigtail to ground to make the lamp light.

If you get a low voltage under load, at the lamp socket, take the lamp out and repeat the test. If you now get the full battery voltage, the chances are that you have a wire somewhere with almost all of the strands broken. The low loading of the vom will show you the full battery voltage, while the load current of the lamp causes a high voltage drop in the wire. Cure; trace the wire, looking for a place where it has been almost cut in two, or bent very sharply. In some cases, such as tail or stop-lights inside the trunk, you can run another wire from the bad socket to a good one; tape the new wire to the cable, and that's all you need.

### Leaks

One of the most annoying things in the world is to go out on a cold morning and find your battery so dead that it won't even grunt. If there is a small current leakage anywhere in the system, it will drain the battery overnight. If you get it going, the next morning it could be dead again. This can be the battery itself; the only way to tell is with a "load-tester" at the service station. If the battery checks good, then you have a leakage.

If your vom has a dc amperes scale, preferably up to 10.0 amps, you can use it for the next test directly. If you have only a dc volts scale, get a 1.0-ohm wirewound resistor, and connect the vom prods across this, on a low dc volts scale. You'll read 1.0 volt dc for each 1.0A of current flowing through the resistor. Now you're ready to find the leakage.

Take one of the battery terminals off the post (either one). Connect the vom on the dc amps scale, or the 1.0-ohm resistor, *between* battery post and cable. Be sure that every normal load on the car is turned off, and the doors closed to turn off the dome lights. You should see zero current. If there is any leakage current, you'll read it on the meter. In my own car, some years ago, I had a steady reading of about 2.0 A. This may not sound like too much, but it pulled a perfectly good battery down so far that it wouldn't even pull in the starter solenoid!

To locate the leaky device, just start disconnecting things. When you pull the wire off the guilty part, you will see the leakage current disappear. In my car, it was the stop-light switch. A new one fixed it up. The push-on terminals used in so many places in modern cars makes this a lot easier.

R-E

Now...the most enjoyable do-it-yourself project of your life—A Schober Electronic Organ!



You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.

You need no knowledge of electronics, woodworking or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models with kit prices from \$500 to around \$2,000, each an authentic musical instrument actually superior to most you see in stores, easy for any musically minded adult to learn to play, yet completely satisfying for the accomplished professional. And there are accessories you can add any time after your organ is finished—lifelike big auditorium reverberation, automatic rhythm, presets, chimes, and more.

Join the thousands of Schober Organ builder-owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives — first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!

The Schober Organ Corp., Dept. RE-130  
43 West 61st Street, New York, N. Y. 10023

Please send me Schober Organ Catalog.  
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Circle 70 on reader service card

GIVE...  
so more will live  
**HEART FUND**



Contributed by the Publisher

# new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

**INTRODUCTION TO MATV.** 22-page booklet contains chapters on television signal, antennas, ghosting, cable preamplifiers, main power amplifier, splitters (combiners), tapoff (TV outlets), matching transformer, special applications, overall system, cost factors and a glossary of terms. Includes many diagrams. — **Blonder-Tongue Laboratories, Inc.**, 1 Jake Brown Road, Old Bridge, NJ 08857.

Circle 43 on reader service card

**TEST & MEASUREMENT INSTRUMENTS CATALOG.** 10-page catalog describes the TM 500 series which includes counters, power supplies, multimeters, signal sources, signal processors and CRT monitors. Contains many illustrations. — **Tektronix, Inc.**, P.O. Box 500, Beaverton, OR 97005.

Circle 44 on reader service card

**1974 ELECTRONIC TEST ACCESSORIES CATALOG.** 68-page catalog contains more than 500 products, 17 of which are new. Products introduced in this edition include a "Grabber" test probe fitted with 6-32 threads, a 36 kV test probe, seven adapters, three banana jacks with wire wrap terminals, four patch cords and one molded breakout. Provided illustrations and complete engineering information on all products—including dimension drawings, schematics, specifications, features and operating ranges.—**Pomona Electronics**, 1500 East Ninth Street, Pomona, CA 91766.

Circle 45 on reader service card

**SYSTEMS EQUIPMENT CATALOG** contains 75-ohm installations, 300-ohm installations, MATV systems diagrams, antennas, splitters, matching transformers, couplers, attenuators, tap-on wall plates, tap-off wall plates, hook-up cables, coaxial cables, uhf connectors, cable connectors, cable clips and clamps grounding blocks, tools, stapling equipment, parts master and how to sketch and plan a system. The second half of the catalog contains 19 systems project worksheets.—**RMS Electronics, Inc.**, 50 Antin Place, Bronx, NY 10462.

Circle 46 on reader service card

**TOOL KITS CATALOG.** 12-page catalog describes 18 different stock, fully equipped tool kits and shows 13 tool cases that can be ordered empty or custom filled with a choice of tools, meters, parts containers, etc. Tool kits are designed for maintenance, assembly and repair in the electronic, electrical, vending, computer, relay, appliance, office machine and similar industries. Catalog also provides listing of all tools that are most useful to installers, technicians and maintenance personnel. —**Electronic Tool Co.**, 15 Bertel Avenue, Mt. Vernon, NY 10550.

Circle 47 on reader service card

**AEROSOL PRODUCTS CATALOG.** 6-page catalog includes the company's aerosols available and also depicts, with line drawings, their application. Describes high-purity cleaners, special cleaners and solvents, mold releases, protective materials and aerosol accessories for special applications. Also includes a "Typical Maintenance Problems" chart that lists the equipment to be maintained, the cleaning problem, remedy and aerosol product that will solve the problem. —**Miller-Stephenson Chemical Co.**, P.O. Box 628, Danbury, CT 06810.

Circle 48 on reader service card

**STEREO SOUND SHEET** demonstrates PAIA's line of electronic music synthesizer kits. The record features the synthesizers at work in live performances and studio environments with pieces ranging from structured melodic works to "Sound Collages." Included with the record is a booklet that shows the patching connections for each piece and musical scores where applicable. A second booklet, "A Schematic Symbology for Synthesizer Patching Arrangements" is also included. Record and booklets as a set \$1.00—**PAIA Electronics, Inc.**, 1020 West Wilshire Blvd., Oklahoma City, OK 73114.

R-E

## If You Work In Electronics:

# GRANTHAM OFFERS YOU College-Level Training and a college degree.

**Electronic Circuit Design, Engineering Analysis (including mathematics thru calculus), Classical and Solid-State Physics, Engineering Design, etc., etc., are all part of the Grantham home-study degree program in Electronics Engineering.**

## PUT PROFESSIONAL RECOGNITION IN YOUR CAREER.

By adding college-level home training and a college degree to your experience, you can *move up* to greater opportunities in electronics.

Grantham offers the A.S.E.T. degree by correspondence. After earning this degree, you may continue with additional correspondence plus a 3-day residential seminar and certain transfer credits, to earn the B.S.E.T. degree. Then, the B.S.E.E. is available through further study.

## GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 90025

● Telephone (213) 477-1901 ●

Worldwide Career Training thru Home Study

Mail the coupon below for free bulletin.

**Grantham School of Engineering** RE 9-74  
2000 Stoner Ave., Los Angeles, CA 90025

I have been in electronics for \_\_\_\_\_ years. Please mail me your free bulletin which gives details concerning your electronics degree programs.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 71 on reader service card



# SUPER SPECIALS

## CONDENSERS CANS

300 Mfd. 200 Volts	4 for \$2.19
400 Mfd. 200 Volts	4 for \$2.39
500 Mfd. 50 Volts	3 for \$2.19
200 Mfd-80 Mfd.-350 Volts	3 for \$1.79
250 Mfd.-40 Volts*	5 for \$1.00
25 Assorted Filters	\$4.95

## ANTENNA EQUIPMENT

6-Ant. Clothespins	\$1.19
RMS-2 Set Coupler	\$1.89
RMS-4 Set Coupler	\$2.79
6-Coaxial "F" Connectors	\$1.19

## SPEAKERS

6X9	\$ .99
8" Round	\$2.29
6" Round	\$1.79
4" Square	\$ .89

## CONTROLS-RESISTORS

50 Asst'd Controls	\$2.98
50 Asst'd W.W. Res.	\$2.69
100 Asst'd Carbon Resistors	\$1.69
1 Meg. V.C./Sw.—P.P.	3 for \$1.19
66 Meg. HV res.	4 for \$2.00
70% Conv. Assembly	\$1.00
CRT BOOSTER 70%	\$4.29 (COLOR)
CRT BOOSTER 90%	\$4.59 (COLOR)
10 HV Anode Leads	\$1.00
25 Asst'd Plate Caps	\$1.00
Audio Output Xfmrs	2 for \$1.00
DELAY LINES	2 for \$1.19
25 Terminal Strips	\$1.00
Shunt Reg. Hoods	2 for \$1.00
10 Asst'd Align. Tools	\$1.98
TUNER CLEANER-8 Oz. Spray	\$1.00
50 Asst'd IF Xfmrs	\$2.49
20 Asst'd Tube Sockets	\$1.00

## COLOR FLYBACKS

RCA 136640	\$7.95
RCA 137545	\$7.95
EMERSON 738229A	\$3.95
PHILCO	.32-10132-1 \$3.95

## DIODES—SEMI-CONDUCTORS

25 IR 2.5 A-1000 PIV	\$4.95
100 IR 2.5 A-1000 PIV	\$14.95
6500 PIV Focus Rect.	4 for \$2.00
13.5 KV Focus Rect.	5 for \$3.00
3.58 Mhz. Crystals	3 for \$2.00
25—1N34A Crystal Diodes	\$2.00
5—Boost Rectifiers	\$2.00

## COLOR YOKES

EQUIV. DY 95AC-Y109 (Univ)	\$6.95
JAP COLOR YOKE	\$4.95
Y-133—Adm.—Mag.	\$3.95
SILVERTONE 80-56-4G	\$5.95
70% (21" CRT ROUND)	\$8.95

## TUNERS—NEW

Sylv. Trans. 54-29331-3	\$6.95
Sylv. Trans.—54-35055-2	\$6.95
PHILCO Trans. 76-14296-2	\$6.95
GEN. ELECT. Trans. 86X15	\$6.95
G.I. Parallel 6GS7-6HA5	\$3.95
Philco Series 5GJ7-3HQ5	\$3.95

BSR CHANGER-STEREO	\$15.95
CASSETTE TAPE—c-60	2 for \$1.19
CASSETTE TAPE—C-120	2 for \$2.29
10 RCA Phono Plugs	\$1.00

## CONDENSERS—AXIAL LEADS

100 Mfd.-150 Volts	10 for \$1.98
10 Mfd.—450 Volts	6 for \$1.49
10 Mfd.-600 Volts	3 for \$1.00
25 Assorted Condensers	\$4.95

## TUBES—ICC—RAYTHEON

25-6GH8	\$17.50
5—2AV2	\$4.50
5—6FQ7	\$4.25

MINIMUM ORDER \$15.00  
SEND FOR FREE CATALOG  
TUBES UP TO 80% OFF

SEND CHECK OR  
MONEY ORDER

## TV TECH SPECIALS

P.O. Box 603  
Kings Park, L.I., N.Y. 11754

## EQUIPMENT REPORT (continued from page 30)

source is usually taken from the amplifier's tape output jacks or directly from a stereo recorder, as determined by a front panel switch. Discrete 4-channel inputs (such as for a quad recorder) are also provided. There are front and rear (quad) outputs at line level for the amplifier and a tape recorder. A front panel selector determines either matrix decoding or direct feed from the 4-channel discrete tape input.

Three decoders are built into the SQ-W. In addition to the wavematching full-logic Variblend SQ decoder, there is also a basic SQ decoder with a moderate degree of blend (for A/B comparisons) and a "composer," Lafayette's term for a decoder that extracts "ambient sounds" from a standard stereo record or tape.

Two front panel controls are provided: one selects the decoder and discrete tape modes, the other serves as a master volume control for the quad system. Two switches serve for the power and amplifier/tape sound source.

The measured (not manufacturer's specs) level of performance of the Variblend decoder proved excellent, somewhat exceeding Lafayette's claims. The corner-to-corner separation was nominally 20 dB, while the CF/CR separation was 18 dB. This contrasts to the basic (blended) SQ decoder's CF/CR separation of 6 dB. The amplifier's frequency response was within 1 dB from 20 to 20 kHz, at a distortion no higher than 0.1% THD at any frequency.

Most important, using several different types of programs, no trace of gain-riding pumping was evident, yet the degree of separation was so high it was possible to hear musical effects moving from corner to corner, as originally orchestrated. A listener would be hard pressed to tell the difference between the SQ-W and a discrete system.

## Invite



## World Into Your Home

Write for information on how a high school student from another culture can make your life more exciting, rewarding—and fun.

American Field Service  
International Scholarships  
313 E. 43rd St., N.Y., N.Y. 10017

# PAIA

EXPANDS their line of  
**SYNTHESIZER  
KITS**  
from the  
**GNOME  
micro-synthesizer**

to  
modular systems  
all at affordable prices

demonstration record,  
including explanatory manual,  
patch charts and scores  
now available — \$1.00 ppd.  
catalog - free

PAIA ELECTRONICS  
BOX R14359, OKLAHOMA CITY, OK 73114

Circle 73 on reader service card

# FREE!

## TOOL CATALOG

2000 items - 112 packed pages

- ✓ instruments
- ✓ relay tools
- ✓ wire strippers
- ✓ tool kits
- ✓ cases bags
- ✓ tweezers
- ✓ soldering irons
- ✓ drivers
- ✓ metric tools
- ✓ optics
- ✓ wrenches

**SEND FREE CATALOG 674 TO:**

Name \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

JENSEN TOOLS and ALLOYS  
4117 N. 44th Street, Phoenix, Arizona 85018  
A ILLIS & LAUGHLIN industry

Circle 74 on reader service card

# next month

OCTOBER 1974

It's hi-fi time again, and here's the chance to get completely up-to-date on the latest developments in the world of high-fidelity sound.

## ■ Build A Full-Logic IC SQ Decoder

Latest circuitry includes wave-matching. Three new IC's make construction easy. This is probably the first time this circuit has been made available to the constructor.

## ■ CD-4 — How It Works

Take a look at what's behind the way discrete 4-channel records work. It's an up-to-the-minute report of where this system stands today.

## ■ Many Roads To Four Channel

Don't be afraid to buy new stereo gear now. It all can be used for 4-channel later.

## ■ 4-Channel Record Reviews

Radio-Electronics' editorial staff rates the 4-channel effectiveness of recent 4-channel record releases.

## ■ More COSMOS IC Projects

Part II of this series presents a group of circuits that are practical to build with COSMOS IC's.


**PLUS:**

**Step-By-Step Troubleshooting Charts**  
**Radio-Electronics' Replacement Transistor Guide**  
**Jack Darr's Service Clinic**  
**Appliance Clinic**


October issue on sale September 19

# GIANT Wall Chart of

## Electronic Symbols

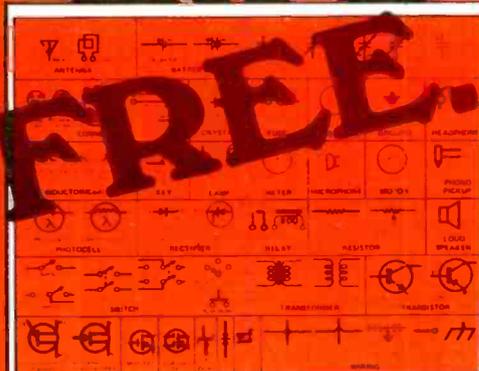

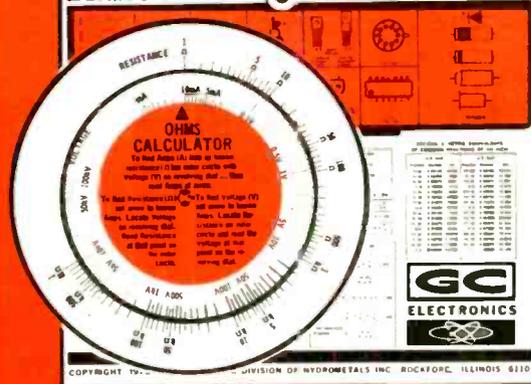**ELECTRONIC SYMBOLS**  
— DATA CHART — CALECTRO HANDBOOK



with every CALECTRO HANDBOOK! Available from your CALECTRO distributor!



**GC ELECTRONICS**

DIVISION OF HYDROMETALS, INC.  
ROCKFORD, ILLINOIS 61101 U.S.A.

Circle 75 on reader service card

## ELECTRONIC TECHNICIANS!

Raise your professional standing  
and prepare for promotion! Win  
your diploma in

### ENGINEERING MATHEMATICS

from the Indiana Home  
Study Institute

We are proud to announce two great  
new courses in Engineering Mathematics  
for the electronic industry.

These unusual courses are the result of  
many years of study and thought by the  
President of Indiana Home Study, who  
has personally lectured in the classroom  
to thousands of men, from all walks of  
life, on mathematics, and electrical and  
electronic engineering.

You will have to see the lessons to ap-  
preciate them!

NOW you can master engineering  
mathematics and actually enjoy doing it!

WE ARE THIS SURE: you sign no  
contracts—you order your lessons on a  
money-back guarantee.

In plain language, if you aren't satis-  
fied you don't pay, and there are no  
strings attached.

Write today for more information and  
your outline of courses.

You have nothing to lose, and every-  
thing to gain!

### The INDIANA HOME STUDY INSTITUTE

Dept. RE-974, P.O. Box 1189, Panama City, Fla.  
32401

Circle 76 on reader service card

## FREE ALARM SYSTEM CATALOG



Full line of professional burglar  
and fire alarm systems and sup-  
plies. 96 pages, 450 items. Off-the-  
shelf delivery.



mountain west alarm  
4215 n. 16th st.  
phoenix, az. 85016  
(602) 263-8831

Circle 77 on reader service card

## TIME ON TV SCREEN

(continued from page 42)

Once you have the eight white boxes,  
carefully measure the voltages where IC8 is  
to go—+5 on pin 24; -5 on 11 and 12; and  
finally -12 on pin 1. *Reverse supply voltage  
will instantly ruin IC13, so even with the  
idiot-proofing network D1, R1 be careful!*

IC8 is a MOS integrated circuit, and ex-  
ceptionally careless handling could damage  
it. Leave it in the case and protective foam  
till you are ready to use it, then quickly sol-  
der it in place with a small soldering iron,  
watching to get the code dot and notch cor-  
rect. After it is soldered in place, the circuit  
will protect the IC from most damage.

Reapply supply power, and the eight  
boxes should now read 1?:7?:7? if you have  
a 12-hour system and 3?:7?:7? if you have a  
2400-hour one. The unconnected inputs are  
"read" as digital "1"s, as are +5 signals.  
Only a ground is read as "0". Do not con-  
nect anything to your clock until you have  
the exact display called for above. Once you  
are certain all is well, connect up the mul-  
ticonductor cable to the proper place in your  
Superclock (either the inputs to the readouts  
or the 1-2-4-8 outputs of the various coun-  
ters). Keep these short, preferably under 15  
inches. The TV interconnects can be  
reasonably long, but avoid running across  
the room with them. When the clock is con-  
nected, you should have the correct time to  
your TV set and the project is complete.

### Using it

Remember, you can turn the time display  
off and on by applying or removing the +5,  
by breaking the video line, or by breaking  
the vertical trigger line. If you experience  
some character breakup at the minimum  
horizontal width settings of the display, you  
can increase the -12V supply by a volt to  
-13, or, if you're real brave, you can short  
out R1. Should you want a bigger than the  
largest available time display, increase C11.  
For a very small display, decrease C11 and  
you can go down to the breakup point. With  
the circuit we've shown you, the *minimum*  
display size will be slightly *wider* than  
shown in the lead photo. You should be able  
to use the available controls to move the  
display most anywhere you want to place it  
on the screen and almost any size, within  
reasonable limits.

If you want to display something besides  
the time, you can rework the input data  
selectors and perhaps add two more to pick  
up the total alphanumeric capability of this  
circuit.

Should you want lots more than 8 numer-  
als at a time and want internal storage as  
well, a much more elaborate TV  
ALPHABETIZER system is in the works here  
at RADIO-ELECTRONICS. We'll be telling you  
about it shortly. In the meantime, good luck  
on this project. R-E

## MEASURE HI-FI PERFORMANCE

(continued from page 63)

### Additional measurements

Another convenient pushbutton on  
the analyzer permits the user to di-  
rectly measure and read the wattage  
consumed by any audio product from  
the power line source. There is also an  
eternal input to the digital readout  
module which lets you read the am-  
plitude of any sinusoidal waveform up to  
250 volts rms.

External inputs are provided through  
which signals may be fed into the in-  
strument in the event that audio fre-  
quencies other than those built in are  
required for any reason. Such signals  
will, of course, have their amplitudes  
read directly by the digital module and  
are fully controllable by the switches  
and multum attenuation potentiomet-  
ers of the analyzer.

The acquisition of the McAdam  
audio analyzer has, of course, sim-  
plified many of the audio measure-  
ments which I am called upon to make  
almost daily and I have found that it is  
relatively easy to interface this equip-  
ment with the rf equipment which is  
used for AM and FM measurements.  
For example, the Sound Technology  
FM generator model 1000A, shown  
standing atop my now displaced audio  
generator in Fig. 1, has provisions for  
external modulation. By modulating it  
with the available audio tones from the  
McAdam analyzer and connecting  
tuner or receiver under test to the out-  
put terminals of the analyzer, full use  
can be made of the distortion meas-  
urement facilities of the analyzer and  
THD as well as S/N readings can be  
made digitally as well. By continuing to  
use the internally supplied stereo com-  
posite signal generating facilities of the  
FM generator, separation measure-  
ments can also easily be made using the  
generator in combination with the  
McAdam analyzer.

The McAdam analyzer is not inex-  
pensive, retailing for \$3450.00, but  
even in the short time we have had an  
opportunity to use it in our daily lab  
work it has begun to pay off in terms of  
time saved and increased accuracy and  
reliability of measured results. R-E

## Life Share!

Share your life with a  
high school student from  
another culture.

American Field Service  
International Scholarships  
313 E. 43rd St., N.Y., N.Y. 10017

# VALUE . . . PLUS PERSONALIZED SERVICE

FREE \$1 BUY WITH EVERY 10 YOU ORDER Only applies to "\$1" Buys FREE GIFT WITH EVERY ORDER

CANADIANS: Ordering is easy — we do the paperwork — try a small order

SHANNON MYLAR RECORDING TAPE

## RCA 110° FLYBACK TRANSFORMER



We scooped the Market Latest type — standard for all 110° TV's  
 RCA's design of large Coil produces 18KV, assuring adequate width Incl. Schematic Diagram application for any TV  
 List price \$13.90  
 Your price . . . \$3.95  
 10% off in lots of

110° TV DEFLECTION YOKE for all type TV's incl schematic \$4.95

"COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE \$6.95

90° FLYBACK TRANSFORMER for all type TV's incl schematic \$2.95

90° TV DEFLECTION YOKE for all type TV's incl schematic \$2.95

70° FLYBACK TRANSFORMER for all type TV's incl schematic \$2.95

70° TV DEFLECTION YOKE for all type TV's incl schematic \$2.95

SHARP 110° FLYBACK & YOKE COMBINATION #HFT-592 Good for most portable TV \$6.95

90° COLOR YOKE For all Rectangular 19 to 25" Color CRT's \$10.95

70° COLOR YOKE For all round color CRT's \$10.95

SPECTRO-V.D.M. — MODEL THL-33 2 1/2" Accuracy — 1/2" Precision Resistors — Mercury Protection Full Range — Complete with test leads & Manual \$9.95


SONY UHF TUNER TRANSISTOR TYPE exact replacement, complete w knobs \$3.95

4 — TV ALIGNMENT TOOLS most useful assortment #1 \$1.95

4 — TV ALIGNMENT TOOLS For Color TV #2 \$1.95

6 — TV COLOR ALIGNMENT TOOLS Most popular type \$2.95

## SARKES TARZIAN TUNER

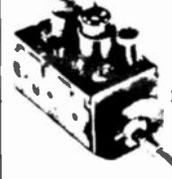

4mc  
 Latest Compact Model good for all 41 mc TV's.  
 BRAND NEW

Best TUNER "SARKES TARZIAN" ever made—last word for stability, definition & smoothness of operation. An opportunity—to improve and bring your TV Receiver up-to-date. \$7.95  
 COMPLETE with Tubes

WESTINGHOUSE FM TUNER #476-V-01500 Transistor \$3.99

WESTINGHOUSE FM TUNER #12D7N5 Tube \$1.00

UHF TUNER—TRANSISTOR TYPE Used in all TV sets \$3.95

STANOID TUNER—TRANSISTOR (GUIDED) 4 Channel closed circuit \$1.95

PHILCO TV TUNERS Model #76-13579-6 (5GJ7-3HQ5) \$4.95

WELLS GARDNER TUNER Part #7A120-114G572HA7 Tubes \$7.95

GE TUNER — EP 86X11 (2GK5 — 41J8) \$7.95

2—ELECTROLYTIC CONDENSERS 100/75 mfd-300 V, 70 mfd-25 V \$1.95

2—ELECTROLYTIC CONDENSERS 300 mfd-200 V, 300 V, 300/60 mfd-150 V \$1.95

PHILCO UHF/MF TUNER Transistorized \$9.95

GE TV TUNER FT 86X196 (6GK5-6B1R) \$5.95

5 — AC LINE CORDS Approved 6' \$1.95

UNIVERSAL TV ANTENNA Rack of set mounting 5 section rods \$2.99

BLUE LATERAL MAGNET ASSY Replacement for most color TV's \$1.99

COLOR CONVERGENCE ASSEMBLY Universal type—good for most sets \$2.49

COLOR TV RECTIFIER — Used in most color sets—6500 kv 3 for \$1.95

2 COLOR-TV CRT SOCKETS Wired leads, for all color TV's \$1.95

3 — RCA 110° CRT SOCKETS Wired leads, for all color TV's \$1.95

8 — MINIATURE PILOT BULBS 8" Leads —6.3 V, 30MA (5000Hrs) \$1.95

8 — MINIATURE PILOT BULBS 12" Leads—6.3V, 140MA (5000Hrs) \$1.95

IMMEDIATE DELIVERY . . . Scientific light packing for safe delivery at minimum cost.

HANDY WAY TO ORDER . . . Send check or money order, add extra for shipping. Lists of new offers will be returned in your order.

Please specify refund on shipping overpayment desired:  CHECK  POSTAGE STAMPS  MERCHANDISE (our choice) with advantage to customer

## WESTINGHOUSE ALL TRANSISTOR HOME/OFFICE MESSAGE CENTER

Leaves messages for other for replay . . . Built in speaker/microphone for talk-into convenience . . . Records up to 3 minutes of messages . . . Illuminated signal shows when a message is waiting. Control adjusts playback volume without affecting recording volume . . . Capstan Drive;  
 BRAND NEW SOLD AS IS \$7.95

## TEST EQUIPMENT SPECIAL DISCOUNT PRICES



MATCHED PAIRS TRANSISTORS NPN & PNP (2N4252-2N2904) (2N2222-2N2907) \$1.95 Each set

## KNOB SPECIAL

- 100 — ASSORTED RADIO KNOBS All standard types \$20 value \$1.95
- 50 — TV KNOBS — POPULAR TYPES Mostly Selector & Fine Tuning \$1.95
- 20 — VERTICAL LINEARITY KNOBS Long shank Front mount assortment \$1.95
- 20 — VERTICAL LINEARITY KNOBS Side mount Standard sizes \$1.95
- 25 — KNURLED SHAFT KNOBS Hard to get Best selection \$1.95
- 25 — CLOCK & RADIO KNOBS most popular types ANY 6 KITS FOR \$5

TRANSISTOR RADIO *asst type good* had, broken, as-is, potluck \$1.50

TAPE RECORDER—assorted types good, had, broken, as-is, potluck \$4.95

TUBE SPECIAL (61)W4 - 12DQ6 - 12BD6 - 17/3 - 25 EH5 \$1.75 ea

200 ASST. 1/2 W RESISTORS Short Leads Excellent Selection \$1.95

75 — ASST 1/4 WATT RESISTORS stand. choice ohms, some in 5% \$1.95

100 — ASST 1/4 WATT RESISTORS stand. choice ohms, some in 5% \$1.95

70 — ASST 1 WATT RESISTORS stand. choice ohms, some in 5% \$1.95

35 — ASST 2 WATT RESISTORS stand. choice ohms, some in 5% \$1.95

50 — PRECISION RESISTORS *asst list* \$50 list \$9.95

20 — ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt \$1.95

10 — ASSORTED SLIDE SWITCHES SPST, SPDT, DPDT, etc \$1.95

25 — SYLVANIA HEAT SHIMS For Transistors \$1.95

20 — ASSORTED TV COILS (F, VIDEO, sound, radio, etc) \$1.95

1 — ELECTROLYTIC CONDENSERS 300 300/100/100 MFD — 25 V \$1.95

1 — ELECTROLYTIC CONDENSERS 100 MFD-400V \$1.95

3 — ELECTROLYTIC CONDENSERS 20/20 MFD-450 V \$1.95

5 — 9 VOLT MOTORS Excellent for hobbyist \$1.95

1—8" x 9" HEAVY DUTY 10 OZ. SPEAKER Ceramic Type — 8 Ohm \$4.50

10—ASSORTED DIODE CRYSTALS 1N34, 1N48, 1N60, 1N64, etc \$1.95

8 — TOP BRAND SILICON RECTIFIERS 1 amp 1000 PIV \$1.95

5 — PNP TRANSISTORS general purpose, TO-5 case \$1.95

5 — NPN TRANSISTORS general purpose, TO-5 case \$1.95

25 — ASSORTED TRANSISTORS big factory scoop—sold as-is \$1.95

TV TWIN LEAD-IN 300 ohm 500' — \$7.100' — \$1.50 \$1.95

10—MINIATURE ELECTROLYTIC CONDENSERS For Transistor & miniature work \$1.95

4" SPEAKER — ROUND 8 Ohm large magnet \$1.95

4—ELECTROLYTIC CONDENSERS 75/30mfd-150v \$1.95

8 ELEMENT COLOR OUTDOOR ANTENNA Big shot Jr List \$11.95 \$5.95

4 — POLARIZED CHEATER CORDS Grey \$1.95

70° COLOR TUBE BRIGHTNER \$3.95

90° COLOR TUBE BRIGHTNER \$4.95

2 — COLORBURST QUARTZ-CRYSTAL For Most Color TV sets 3579 545 KC \$1.95

5 ASSTD GLOBAL VARISTOR Popular replacements for most COLOR TV \$1.95

250 — ASST SOLDERING LUGS best types \$1.95

250 — ASST WOOD SCREWS finest popular selection \$1.95

250 — ASST SELF TAPPING SCREWS #6, #8 etc \$1.95

100 — ASST. 6/32 SCREWS \$1.95

100 — ASST. 8/32 SCREWS \$1.95

100 — ASST. 8/32 HEX NUTS \$1.95

100 — ASST. 2/56 SCREWS \$1.95

100 — ASST. 2/56 HEX NUTS \$1.95

100 — ASST. 4/40 SCREWS \$1.95

100 — ASST. 4/40 HEX NUTS \$1.95

100 — ASST. 5/40 SCREWS \$1.95

100 — ASST. 5/40 HEX NUTS \$1.95

500 — ASSORTED RIVETS most useful selected sizes \$1.95

300 ASSORTED WASHERS most useful selected sizes \$1.95

100 — ASST RUBBER BUMPERS for cabinet bottoms — other uses \$1.95

100—ASSORTED RUBBER GROMMETS best sizes \$1.95

2—SPRAGUE ELEC CONDENSERS 40 30 4 Mfd — 475 V \$1.95

2 — ELECTROLYTIC CONDENSERS 300 300/100 V, 50 mfd-75 V \$1.95

8-TRACK TAPE PLAYBACK DECK Compact design fits anywhere \$27.50

3—ELECTROLYTIC CONDENSERS 100 mfd-100 V, 50 mfd-75 V \$1.95

32 — TEST PROD WIRE DELUXE QUALITY, red & black \$1.95

DELMONICO NIVICO COLOR FLYBACK Part #A20411-B \$10.95

15 — MINIATURE 458K IF TRANSFORMERS PC by X 1/2" — good value \$1.95

2 — 12B7 RCA TUBES \$1.95

ELECTROLYTIC CONDENSERS 300 300/100 Mfd — 25V \$1.95

2 — ELECTROLYTIC CONDENSERS 150 150/100 Mfd — 35V \$1.95

1 — 5" SPEAKER with output transformer \$1.39

12" UNIVERSAL SPEAKER Top Quality Large Magnet \$5.89

10" PHILCO SPEAKER Top Quality Large Magnet \$2.99

8" UNIVERSAL SPEAKER — Large Magnet—Special Buy \$2.99

4" UNIVERSAL TWEETER 1 oz. Magnet \$1.29

UNIVERSAL 4" PM SPEAKER Top Quality \$1.95

2 1/2" x 4" SPEAKER Special Buy 10 For \$5 \$6.95 ea

4" x 8" "QUAM" 16 OHM SPEAKER Large magnet Special BLY (10 for \$1.79) \$15.00

RONETTE STEREO CARTRIDGE latest dual sapphire fidover type \$2.95

STEREO HEADPHONES Hi-F. Quality Complete with Stereo plug \$5.95

10 — STANDARD TRANSISTORS NPN & PNP 2N2404, 2N414, etc \$1.95

UTAM 8" — HEAVY DUTY 10 OZ SPEAKER Ceramic Type — 8 Ohm \$4.50

VARCO STEREO CARTRIDGE-CN-72 With mounting bracket, fidover needle \$2.95

ELECTROLYTIC CONDENSER 300 Mfd — 300V \$1.95

15 — DIPPED MYLAR CAPACITORS .01 600 V \$1.95

15 — DIPPED MYLAR CAPACITORS .033-600 V \$1.95

15 — DIPPED MYLAR CAPACITORS .0033-1000 V \$1.95

15 — DIPPED MYLAR CAPACITORS .01 47-400 V \$1.95

15 — MOLDED TUBULAR CAPACITORS .068-400 V \$1.95

10039-400V \$1.95

TACHMETER 2 1/2" SQUARE PANEL METER 1-VDC, full scale, 33 Ohm coil resistance 0-6000 R.P.M. \$2.95

CASSETTE TYPE DYNAMIC MICROPHONE with universal plugs—300 Ohms \$2.99

10 — SETS PHONO PLUGS & PIN JACKS RCA type \$1.95

8—PRINTED CIRCUIT IF TRANSFORMERS 4-Lug, 456 KC \$1.95

STEREO TONE ARMS Most popular type—turn over cartridge \$2.95

## MARKET SCOOP COLUMN

ZENITH COLOR DEMODULATOR CMP PART #221-89 (Sprague Eqv. TVC-M) \$3.95

CO-AX CABLE RG59U (BLACK) 250' — \$10, 100' — \$4.50, 50' — \$2.69

1C4 AND 1C5 INTEGRATED CIRCUIT Used in Scott — Fisher etc. \$1.95

15 — ASSORTED IC'S For Experimenters \$1.95

SILICON NPN HV TRANSISTOR RCA — SK-3021 — Hep-240 \$1.69

RCA — SK-3026 — Hep-241 \$1.69

TRANSISTOR SPECIALS — YOUR CHOICE SK3006, SK3018, SK3020, SK3122, SK3124 \$1.25

TRANSISTOR SPECIALS—YOUR CHOICE SK3009—SK3025—SK3040 \$1.98

OUTDOOR/INDOOR MINI SPEAKER 4" — 1 Oz Magnet — 8 Ohms — Audio level control \$5.50

CONVERGENCE RECTIFIER — FOR COLOR TV 4 Cell — Used in RCA — Philco — Zenith, etc. \$1.00

TV DAMPER DIODE Single — Replace RCA part #120R18 \$2.29

RCA — RCA Part #135932 \$4.95

TOSHIBA CASSETTE STEREO DECK MODEL KT-403DC Record & Play Back \$79.95

TELEMTIC TUNER-MATE KT-730 Portable "Substi-Luner" — Instant Tuner Check \$38.50

TELEMTIC TEST JIG MODEL — EJ-190 Master Rigs—Combo Rigs — Econo Rigs \$49.95

3 SPEAKER — 7 WAY SELECTOR SWITCH Wall Mount \$1.69

STEREO MICROPHONES 1 — 1979/01 Made in Holland \$6.50 set

25' SHIELDED MICROPHONE CABLE Grey 25' \$1.95

50 — ASSORTED FUSES Popular assid. ampere ratings \$1.95

50 — RADIO & TV SOCKETS all type 7 pin, 8 pin, 9 pin, etc \$1.95

1 — 5"x7" UNIVERSAL SPEAKER (10-20-40 OHM Imped.) \$2.95

25' — MICROPHONE CABLE Deluxe, 2 conductor, shielded \$1.89

COLOR POWER TRANSFORMER — Good for most sets 26R150 \$6.95

LIST PRICE—\$36.75

TUBE & CONTINUITY CHECKER Model FT425 (Tests fuses, heaters, lamps, etc) \$1.99

## KLEPS "CLEVER" TEST PRODS

"Third-hand" test prods, reach into out of way places — Insulated — cannot slip — accommodates bare wire or banana plug—no soldering

PRUF 10 — VERSATILE TEST PROBE \$1.39

KLEPS 10 — BOATHOOK CLAMP 4 1/2" long \$1.49

KLEPS 20 — BOATHOOK CLAMP 7" long \$1.49

KLEPS 30 — FLEXIBLE-FORKED TONGUE 8" long \$1.79

KLEPS 40 FLEXIBLE-PC BOARD TERMINALS 6 1/2" long \$2.59

KLEPS 1-ECONOMY KLEPS-BOARD LIGHT WORK \$1.99

ASTATIC PICKUP MODEL 700-89T Contains 89T ceramic cartridge LIST PRICE \$17.00 \$2.95

4-50' HAWKS HOOR-UP WIRE assorted colors \$1.95

100'—SPOOL SPEAKER WIRE 2 cond 52 mini zip, clear, 10' uses \$1.95

10 — ASST. RADIO & TV TUBES Every Tube a good number \$1.95

5 — AUDIO OUTPUT TRANSFORM Sub-min for Trans Radios \$1.95

5 — IF COIL TRANSFORMERS 456-kt for Transistor Radios \$1.95

8" UNIVERSAL SPEAKER Top quality Special buy \$2.95

ALL AMERICAN TUBE KIT (12AV6-12BE-12BA6-35W4-50C3) \$2.95

VU 1" PANEL METER 0-200 div Scale \$1.29

2 - ELECTROLYTIC CONDENS

# NOW A PROFESSIONAL BURGLAR-FIRE ALARM SYSTEM YOU CAN INSTALL YOURSELF.



ONLY 149.95

Save hundreds of dollars in alarm installation and monthly service charges. The EICO SS-500 "install-it-yourself" burglar-fire alarm system offers you the kind of professional protection you have been looking for, at a price you can afford. The SS-500 has been designed on the EICO "Expandability Concept" that enables you to "add-on" protection to meet your own special needs. Before you purchase any security system, we suggest you read the EICO Security Handbook and see how easy EICO makes it to "Do-it-Yourself."

## FREE EICO CATALOG/SPECIAL OFFER!

Security handbook (Reg. \$2.95) only \$1.50 with this ad. Includes a catalog on EICO Security Systems, Test Instruments, Stereo, Hobby Kits and name of nearest distributor. For catalog only, check reader service card or send 50c for first class mail service.

EICO, 283 Malta Street, Brooklyn, N.Y. 11207



Circle 80 on reader service card

# need belts?



We've thousands in stock

Ready for immediate shipment! Belts for over 1800 makes and models of tape recorders, projectors, dictating machines, video recorders . . . and our simplified cross reference system makes it easy for you to order. Drive tires, wheels, phono idlers also listed. On most items we can ship the same day. Call or write today for your free catalog/cross reference chart.

PROJECTOR-RECORDER BELT CORP.

316 Whitewater St., Whitewater,  
Wisconsin 53190 414/473-2151

96 Circle 81 on reader service card

For  
faster  
service


USE  
ZIP  
CODE

on  
all  
mail

# circuits
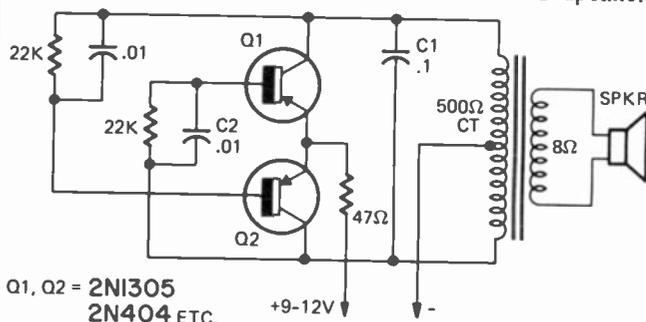
## BUILD OUR BARGAIN BASEMENT BEEPER!

If you are like most of us there must be many times when you need some sort of an alarm for a project, yet a decent buzzer or alarm isn't handy. Well here's an answer to your problems! Our Beeper is super simple, yet packs an audio wallop! It puts out almost 300 mW of power at a frequency that is certain to grab your attention! The circuit is simple, but yet it outperforms buzzers and alerts costing many times as much. You should be able to get the parts from your junkbox—see if you can find an old transistor radio: most radios can supply all the parts. But if you prefer to buy everything, there's no problem. All of the parts are available and they won't set you back but a few dollars. So let's get busy and build it! I constructed mine around a 2½" speaker.



Q1, Q2 = 2N1305  
2N404 ETC.

First I cut a doughnut of perforated board to fit over the speaker magnet and then I mounted all the parts on the board, wired them up, and slipped the board back over the speaker magnet, securing it with epoxy. I just finished up by connecting the speaker, and bringing out long wires for the power. To test it out I connected it up to a 9-volt transistor battery—voilà, it worked! You get an ear splitting beep of about 5 kHz, but if you want a different frequency, change the value of C1. Current drain is on the order of 50mA, so use a heavy-duty battery if you plan to use it much. By the way our beeper makes a terrific continuity checker, burglar alarm, and car seatbelt alarm. What sort of applications can you find? — Gary McClellan

R-E

## EASY-TO-HANDLE EPOXY

Epoxy cement is generally sold in tubes. Invariably it seems, they leak after several applications. They become so sticky that they may have to be discarded after 5 or 6 times of use.

Recently, a new brand of epoxy made its appearance. It is sold in small jelly-bean size containers that come in 2 colors, red and yellow. The directions call for cutting off the ends of one yellow and one red container, emptying their contents onto a flat surface, blending thoroughly for maximum strength and then using.

For my arts-and-crafts, and probably for your radio repairs, only a few drops of epoxy may be needed. I pierce the ends of the containers, squeeze out a few drops of each (equal quantity, of course) mix and use. I find that the "jelly bean" containers seal themselves at once, and you can use them over again. You must pierce them each time you use them, so keep a pin handy.

No fuss, no waste, no sticky fingers. — Lillian Queen R-E

# try this

## ICE CUBE TRAYS FOR HARDWARE STORAGE


Inexpensive plastic ice cube trays may be used in your work area to keep nuts, bolts, washers and other hardware organized. These trays are also handy to keep small parts from getting lost during construction of electronic kits. These




trays are often purchased by the happy homemaker in search for a tray that readily releases ice cubes . . . and when they do not, are usually found in or getting near the trash pile waiting to be rescued for use in your shop.—Kent Mitchell, W3WTO
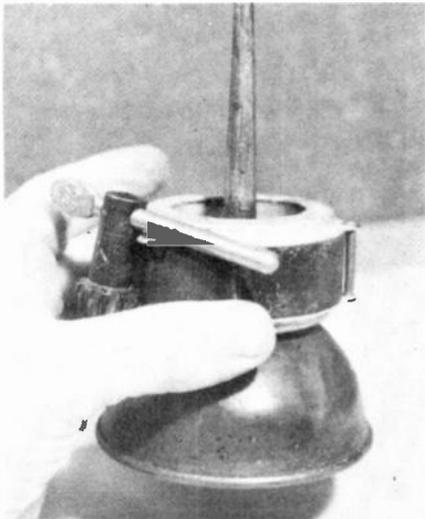
## MAGNET FROM TV RECEIVER

If you salvage parts from an old TV set; don't fail to save the heavy-duty ring magnet that encircles the picture tube neck. This type of collar — called a focus ring — is a powerful permanent magnet that will hold large hand tools firmly. Fasten it to the wall or at any convenient spot and use it to



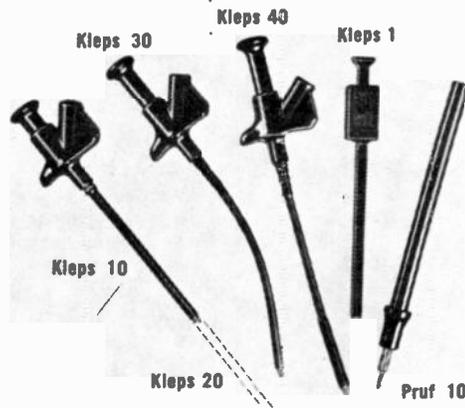hold an assortment of metal items. It is especially useful to hold squirt cans — usually made of copper-plated sheet iron — since the spout of the can may be inserted through the center of the ring from the bottom where it will be held securely until needed. For greater security spring-mount the magnet in some way to resist shock and vibration. — Glen F. Stillwell



## Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¼" long. \$1.39
- Kleps 20.** Same, but 7" long. \$1.49
- Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.79
- Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼" long. \$2.59
- Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long. \$ .99
- Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. \$ .89

All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.


Available through your local distributor, or write to:



**RYE INDUSTRIES INC.**  
130 Spencer Place, Mamaroneck, N.Y. 10543  
In Canada: Rye Industries (Canada) Ltd.  
Circle 82 on reader service card



# EIGHT INSTRUMENTS IN ONE

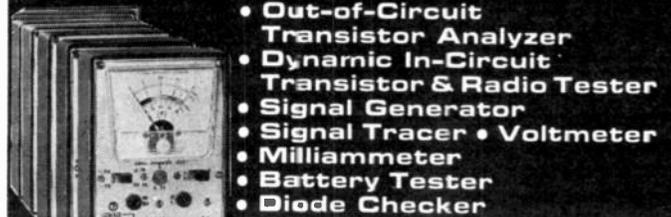

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

## Transistor Analyzer Model 212

Factory Wired & Tested—\$26.95  
Easy-to-Assemble Kit—\$17.95

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

**Features:**  
Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

NAME \_\_\_\_\_ RE-9

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

# EMC

ELECTRONIC MEASUREMENTS CORP.  
625 Broadway, New York, N.Y. 10012

# BURGLARS BEWARE

Instantly alert the police, yet avoid the expense of a central alarm system. This innovation in electronic security systems automatically contacts the police, or anyone else you choose, the instant your home or business is invaded by any intruder.

A simple connection to any existing alarm—contact, ultrasonic, laser, microwave or capacitive—will enable our system to automatically dial any desired number. The number you wish our system to dial can be any number you choose: the police, a security company, a neighbor, your home or business, etc. Once dialed, the recipient at the number reached will hear a pre-recorded message giving your name, phone number and the information that your location has been burglarized.

Provide yourself with immediate response to any intrusion.

Complete money-back guarantee. If you are not satisfied with our system, return within sixty (60) days and we will refund your entire remittance.

Enclose your check or money order for \$149.95 to:

**INSTANT SERVICE SYSTEMS**  
1650 EAST 18th STREET  
TUCSON, ARIZONA 85719  
(602) 623-2149

Circle 83 on reader service card

## DISCOUNT TEST EQUIPMENT SPECIALISTS

HICKOK

B&K EICO

SENCORE

Leader RCA

QUOTATIONS ON REQUEST

COMPLETE LINE OF  
ELECTRONIC SUPPLIES  
ICC/Mullard & Raytheon Tubes  
Telematic Test Rigs  
TV Tuner Subber

## FREE CATALOG

FORDHAM

Radio Supply Co., Inc.  
558 Morris Ave., Bronx, N.Y. 10451  
Tel: (212) 585-0330

## WHAT'S A RAM?

(continued from page 79)

The 1103 is obsolete today. There are some significantly improved devices available today that are much easier to use, but they still are a rather tough design problem if you do not have elaborate equipment and considerable digital know-how. Improved versions include the Intel 1103-A, the Mostek MK4006 and MK4008, the Electronic Arrays EA1500 1501 and 1502 and the American Microsystems S3103.


### 4096 bits

The big race today is to build an improved 1103-style integrated circuit with 4096 bits. At least one has been announced by TI at a 100-lot price of \$26.00, or around 0.6¢ per bit. The other manufacturers aren't taking this sitting down and the race is on. Pinouts have pretty much been standardized and some should be available as you read this. Competitive products include the *Electronic Arrays* 1504, the *Intel* 2107A, *Standard Microsystems* 4412, *Texas Instruments* 4030, *Microsystems International* 7112, *Mostek* 4096, *Motorola* 6605 and probably a bunch more. Only eight of these integrated circuits are needed to build a decent minicomputer main memory.
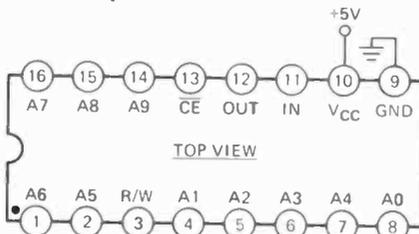
### +5-volt, single supply MOS memories

A number of new, very easy to use and interchangeable MOS memories are now available that use an n-channel static technology. They have no clocks and are entirely and absolutely TTL compatible. There are no clocks or sense amplifiers needed. These include the *Signetics* 2602, the *Intel* 2102, *Intersil* 1M7552, *Motorola* MCM6602 and the *Microsystems International* MF 2102. Cost in single quantities is around 2¢ per bit as of this writing. They are far too new to crop up surplus. Organization is 1024 × 1, or 1024 words of one bit each.

These integrated circuits cycle in a microsecond and screened 0.5-ms devices are also available. There are ten input address lines, a data in and a data out. Figure 9 shows the pinouts.



CHIP ENABLE LOW ENABLES OUTPUT  
CHIP ENABLE HIGH DISABLES OUTPUT  
R/W HIGH READS  
R/W LOW WRITES

FIG. 9—1024-BIT N-CHANNEL memory works off a single +5-volt supply and is very easy to use. Typical devices include Intel 2102, Signetics 2602, Motorola MCM6612, Intersil IM7552 and Microsystems International MM2102.

To read, you pick your address with the chip select low and the read-write high. The output data appears within a microsecond or so of an address change. To write, apply your input data, select your address, wait

400 ns, bring the write line low for at least 500 ns, send it back high again and wait at least 100 ns before changing the address. Once again, don't change the address immediately before, during or immediately after the write line is active low. The chip select can be used to expand the memory by several IC's. Six of these in parallel are ideal for a data terminal or TV typewriter memory. Prices should drop well under a penny per bit by next year.

What good are semiconductor memories? Calculators, programmable computers, teaching machines, terminals, TV typewriters, electronic games, minicomputers, full-blown computers, electronic music and hundreds of other applications exist now. What can you do with them? Let us know. R-E

## COLLECTORS!

We've just added the 1927 Radio Encyclopedia to your growing library—

**S. GERNSBACK'S 1927 RADIO ENCYCLOPEDIA** is your technical book on wireless and early radio. Deluxe illustrated reprint of the original. 175 pages. \$12.95 hard-cover, \$9.95 soft-cover.

**VINTAGE RADIO** is the fascinating photo reference for collectors and historians, 1887-1929. 263 pages, over 1,000 photos. \$6.95 hard-cover, \$4.95 soft-cover.

**RADIO COLLECTOR'S GUIDE** is the data book for collectors, 50,000 facts, 1921-1932. 264 pages, \$3.95 soft-cover.



And now while they last—  
Most-Often-Needed  
1926-1950 Diagrams

The original Supreme Publications books. Schematics of over 3,000 radio models from 1926 thru 1950. Restore those old sets, or use your books for valuable historical information.

- 1926-1938 Volume, 600 models, \$7.00.
  - 1940, 41, 42, 46, 48, 49, 50, \$4.00 each.
  - All eight volumes, special price \$31.50.
- Quantities of original books are limited. Order now and avoid a wait for reprints.



SEND TODAY to Vintage Radio, Dep't R,  
Box 2045, Palos Verdes Peninsula, CA., 90274.  
Postage Paid. California residents add 6% tax.

\_\_\_\_\_ \$  
\_\_\_\_\_ \$  
\_\_\_\_\_ \$  
\_\_\_\_\_ \$  
\_\_\_\_\_ \$  
TOTAL \_\_\_\_\_ \$

NAME \_\_\_\_\_  
STREET \_\_\_\_\_  
CITY \_\_\_\_\_ ST. \_\_\_\_\_ ZIP \_\_\_\_\_

## COLLECTORS!

# new books

**RADIO COLLECTOR'S GUIDE** by Ralph H. Langley. Edited and expanded by Morgan E. McMahon. Vintage Radio, Box 2045, Palos Verdes Peninsula, CA. 90274. 8 1/4 x 5 1/4 in. 264 pp. Softcover \$3.95.

This book fills the need for information on radio sets made from 1929 through 1932. It is an ideal aid to the collector, historian and dealer. It lists key information on over 9000 radio receivers made by some 1200 companies. It lists the manufacturer, year introduced, original price, cabinet type and technical notes for each of the sets listed.

**WORLD RADIO & TV HANDBOOK — 1974** Distributed in U.S.A by Gilfer Associates Inc., Box 239, Park Ridge, NJ 07656 6 x 9 in. 408 pp. soft cover \$7.50.

This is the 28th annual edition of this world-famous directory of short-wave, medium-wave, and long-wave radio broadcasting stations of the world. It also includes call signs, schedules, languages used, station power, etc.

In addition to radio station listings, the Handbook also includes world TV FM stations by frequency and power.

If you are a SWL or medium-wave DX'er, you will surely want this book.

**QUESTIONS & ANSWERS ABOUT TAPE RECORDINGS**, by Herman Burstein. TAB Books, Blue Ridge Summit, PA 17214. 264 pp. 8-1/2 x 5-1/4 in. Hardcover \$8.95; Softcover \$5.95.

Whether it's head alignment, bias adjustment or selection of the right tape, this book has all the answers plus all the circuits, sketches and wiring diagrams a tape recorder enthusiast is ever likely to need. Of importance to everyone who owns or services tape recorders or players, this book covers just about any problem that one might ever encounter or servicing recording playback equipment.

**TRANSISTOR CIRCUITS & APPLICATIONS**, Second Edition, by Laurence G. Cowles. Prentice Hall, Inc., Englewood Cliffs, NJ 07632. 365 pp. 9 x 6 in. Hardcover \$17.25.

An updated second edition of a highly practical description of junction and field effect transistor circuits. By using only those parameters that are truly important, the author succeeds in simplifying circuit calculations. The new edition has more examples of single- and multi-stage gain calculations. The explanations of feedback have been expanded to include loop feedback and the control of amplifier stability and there are new sections on an improved single stage amplifier, integrated circuits, CMOS switching and memory circuit, computers and memory control.

**SOLID-STATE DEVICES: ANALYSIS AND APPLICATION**, by William D. Cooper. Reston Publishing Co., Inc., Box 547, Reston, VA 22090. 453 pp. 9 x 6 in. Hardcover \$14.50.

Here is a logically organized treatment of all major solid-state devices. It includes integrated circuits and thoroughly describes and analyzes solid-state devices as circuit elements. The behavior of solid-state devices and practical circuit applications is well covered using both graphic and mathematic methods of circuit analysis. Many detailed and practical circuit examples including amplifiers, power supplies, oscillators and industrial circuits are provided in this book. Problems and questions at the end of each chapter assist in the retention of the material.


**ROLLING STONE GUIDE TO HIGH-FIDELITY SOUND**, by Len Feldman. Straight Arrow Books, 625 Third St. San Francisco, CA 94107. 159 pp. 7-3/4 x 4-3/4 in. Softcover \$4.95.

Ever since Tom Edison bellowed "Mary had a little lamb" into his first wax cylinder record-making machine back in 1877, people have been explaining and extolling the virtues of good sound reproduction in the home. Time and technology have improved the quality of reproduced sound, but most books on the subject have followed a rather dreary pattern of trying to make audio engineers out of the readers. This book is designed to rescue the audio neophyte from the mire of technical jargon, hard-to-understand specifications, myths and hi-fi folklore. Instead, it concentrates on how to put together a fine hi-fi system. This guide will help hi-fi enthusiasts make the distinction between a good hi-fi component product and a piece of junk parading itself as hi-fi equipment. The author begins with an introduction into audio dynamics, moves into the debate over components and then goes into further nuts and bolts considerations: turntables, speakers, amplifiers, receivers — including your room as a part of the sound system. From mono to stereo to quad-riphonic, it's all here — including a comprehensive glossary of hi-fi terms, many useful diagrams, schematic drawings as well as vintage turn-of-the-century illustrations.

R-E

## WINEGARD AMPLIFIED PRODUCTS PROVEN IN OVER 1,000,000 INSTALLATIONS.
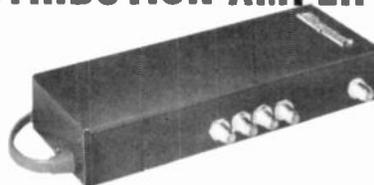
### CASE IN POINT: WINEGARD DISTRIBUTION AMPLIFIERS.



For quality and dependability in distribution amplifiers, look to Winegard. You know they're good. Because our distribution amplifiers have specs you can count on and the best reliability in the industry today.

When you install an MATV system you want it to work right . . . and keep on working that way. You want a headend amplifier that won't give you headaches. No matter what size systems you install Winegard offers the most trouble-free circuitry around . . . and at the most reasonable cost around.

On your next commercial system start out with a Winegard distribution amplifier. There's a model just right for every size and type of installation. We invite comparison!

*Best TV products for Best TV reception*

**WINEGARD**  
TELEVISION SYSTEMS

Winegard Company • 1000 Kirkwood Street • Burlington Iowa 52601

*Circle 85 on reader service card*

# mitScope

**FOUR CHANNEL DIGITAL HANDHELD MEMORY SCOPE**

MS-416 is a valuable tool for circuit analysis:

TV - stereo receivers - electronic calculators - digital clocks - digital auto electronics and more. • The MITS MS416- digital pocket scope is a four-channel, digital logic oriented, handheld scope with full memory capability. • The clock time-base is from .5 sec. to 200 m sec. • The scope may be operated in two modes, selected by another switch. Besides the normal mode, there is a store mode which enables the scope to remember the information on all four channels within the time-base range and display it continuously.

MS-416 regular price \$189.50

order now for . . . . . \$161.50

Prices, specifications and delivery/subject to change without notice. WARRANTY: 1 year

SPECIAL OFFER

MS-416 regular price \$189.50

order now for . . . . . \$161.50

Prices, specifications and delivery/subject to change without notice. WARRANTY: 1 year

SPECIAL OFFER

MS-416 regular price \$189.50

order now for . . . . . \$161.50

Prices, specifications and delivery/subject to change without notice. WARRANTY: 1 year

SPECIAL OFFER

MS-416 regular price \$189.50

order now for . . . . . \$161.50

Prices, specifications and delivery/subject to change without notice. WARRANTY: 1 year

SPECIAL OFFER

MS-416 regular price \$189.50

order now for . . . . . \$161.50

Prices, specifications and delivery/subject to change without notice. WARRANTY: 1 year

SPECIAL OFFER

MS-416 regular price \$189.50

order now for . . . . . \$161.50

Prices, specifications and delivery/subject to change without notice. WARRANTY: 1 year

SPECIAL OFFER

MS-416 regular price \$189.50

order now for . . . . . \$161.50

Prices, specifications and delivery/subject to change without notice. WARRANTY: 1 year



**MITS INC.**  
"Creative Electronics"

Enclosed is a Check for \$ \_\_\_\_\_

or  BankAmericard # \_\_\_\_\_

or  Master Charge # \_\_\_\_\_

Credit Card Expiration Date \_\_\_\_\_

Include \$5.00 for Postage and Handling

MS-416

Please send information on Entire MITS Line.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE & ZIP \_\_\_\_\_

MITS / 6328 Linn, N.E., Albuquerque, New Mexico 87108 505/265-7553 Telex # 660401

RE-9-74

*Circle 86 on reader service card*



### 7-SEGMENT READOUT 12-PIN DIP

- Three digits with right-hand decimal
- Plugs into DIP sockets
- Similar to (LITRONIX) DL337
- Magnified digit approximately .1"
- Cathode for each digit
- Segments are parallel for multiple operation
- 5 - 10 MA per segment
- EACH \$3.00 4 (12 Digits) \$11.00

### RCA 2010

- Numitron Digital Display Tube, incandescent 5-volt 7-segment:
- .6" High numeral visible from 30 ft
- Standard 9-pin base (solderable)
- Left-hand decimal point
- EACH \$5.00 5 FOR \$20.00

- CT5005** A single MOS chip with all the logic necessary for a 12-digit four-function calculator with an extra storage register for constant or memory applications.
- .28 Lead DIL package.
  - Standard 9-pin base (solderable).
  - Left-hand decimal point.
  - COMPLETE w/DATA \$14.95; DATA ONLY (Refundable with purchase of chip) \$1.00

### 40-PIN SINGLE CHIP

- Add, subtract, multiply, and divide
- 12-Digit display and calculate
- Chain calculations
- True credit balance sign output
- Automatic overflow indication
- Fixed decimal point at 0,2,3, or 4
- Leading zero suppression
- DATA ONLY (refundable with purchase of chip).....\$1.00
- COMPLETE WITH DATA.....\$9.95

### CD-2 COUNTER KIT

- Unit includes board, 7490, 7475, quad latch, 7447 seven-segment driver, and RCA DR2010.



- COMPLETE KIT only \$11.25; FULLY-ASSEMBLED \$15.00; boards can be supplied separately at \$2.00 per digit.

### KEYBOARD ASSEMBLY

- TRW Data Systems unit; 10 keys 0-9; 3 (or 4) 2.4V lamps; printed circuit board w/14 1N4001 diodes, capacitors, transistor, and resistors. All mounted in an attractive case approx. 4 1/2 x 4 1/2 x 2 1/2". These are used; no schematic is available. EACH \$6.95

### LM703

- RF-IF amp epoxy TO-5.
- EACH \$.45 TEN FOR \$3.50

### LINEARS

- |                      |        |             |        |
|----------------------|--------|-------------|--------|
| NE540.....           | \$2.00 | 747.....    | 1.00   |
| NE555.....           | 1.50   | 748.....    | \$1.00 |
| NE560.....           | 3.25   | CA3018..... | 1.00   |
| NE561.....           | 3.25   | CA3026..... | 1.00   |
| NE565.....           | 3.25   | CA3045..... | 1.00   |
| NE566.....           | 4.00   | LM100.....  | 1.00   |
| NE567.....           |        | LM105.....  | 1.25   |
| TO-5.....            | 3.00   | LM302.....  | 1.25   |
| NE555B.....          | 1.00   | LM308.....  | 2.00   |
| 709.....             | .45    | LM311.....  | 1.75   |
| 710.....             | .75    | LM370.....  | 2.00   |
| 711.....             | .40    | LM703.....  | .45    |
| 723.....             | 1.00   | LM309H..... | 1.00   |
| 741.....             | .55    | LM309K..... | 2.00   |
| LM1595 4-quad. mult. |        |             | 2.00   |

### LED's

- MV-50 Red Emitting 10-40 MA @ 2V \$ .20; 10/\$1.25 100/\$10.00
- MV5024 Red TO-18 High Dome @ 2V \$ .35; 10/\$2.95
- MV-10B Visible Red 5-70MA @ 2V \$ .30; 10/\$2.50

- MAN-3 Seven-segment readout: EACH ONLY.....\$1.25 TEN OR MORE, EACH.. 1.00
- MAN-1 LED Display..... 3.25
- MAN-4 Seven-segment DIP.....\$2.75

### SEND FOR FREE FLYER!

All ICs new and fully-tested; leads plated with gold or solder. Orders for \$5 or more are shipped prepaid; smaller orders add 55c. California residents add Sales Tax. ICs shipped within 24 hours.

**BABYLON ELECTRONICS**

C.O.D. PHONE ORDERS ACCEPTED--\$10 MINIMUM

P. O. Box 41727  
Sacramento, CA 95841  
(916) 334-2161

### 7400 DIP

- |             |
|-------------|
| 7400 \$ .25 |
| 74H00 .35   |
| 7401 .20    |
| 7402 .35    |
| 74H01 .35   |
| 7403 .30    |
| 7404 .28    |
| 74H04 .35   |
| 7405 .28    |
| 7406 .70    |
| 74H05 .35   |
| 7408 .35    |
| 74H08 .35   |
| 7410 .25    |
| 7413 1.25   |
| 7417 .40    |
| 7420 .25    |
| 74L20 .35   |
| 74H20 .35   |
| 74H22 .35   |
| 7430 .25    |
| 74H30 .35   |
| 74L30 .40   |
| 7440 .25    |
| 74H40 .35   |
| 7441 1.25   |
| 7442 1.20   |
| 7447 1.50   |
| 7450 .25    |
| 74H50 .35   |
| 7451 .25    |
| 74L51 .30   |
| 74H51 .35   |
| 7453 .20    |
| 7454 .25    |
| 74L54 .35   |
| 74L55 .35   |
| 7460 .20    |
| 74L71 .30   |
| 7472 .40    |
| 74L72 .50   |
| 7473 .60    |
| 74L73 .75   |
| 7474 .65    |
| 74H74 .80   |
| 7475 1.40   |
| 7476 .60    |
| 74L78 .80   |
| 7480 .65    |
| 7483 1.00   |
| 7489 4.00   |
| 7490 1.20   |
| 7492 .90    |
| 7493 1.15   |
| 7494 1.15   |
| 7495 1.15   |
| 74L95 2.00  |
| 74107 .70   |
| 74121 1.25  |
| 74154 2.30  |
| 74180 1.25  |
| 74193 1.50  |
| 74195 1.00  |

### Power Supply SPECIAL!

- 723 DIP variable regulator chip 1-40V, + or - output @ 150 MA 10A with external pass transistor--With diagrams for many applications.
- EACH.....\$1.00
- 10 FOR.....\$8.95

### TRIAC

- 2N6344 600V 8A TO-220.....\$ .75

### CMOS

- CD4002.....\$ .75
- CD4001......75
- 74C20......75
- 74C160..... 3.25

### CA3065

- 1F Amplifier-Limiter, FM Detector, Electronic Attenuator, Audio Driver all in one DIP \$7.75

# market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). \$1.15 per word . . . minimum 10 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 70c per word . . . no minimum.

FIRST WORD AND NAME set in bold caps at no extra charge. Additional bold face at 10c per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

### WANTED

QUICK cash . . . for electronic equipment, components, unused tubes. Send list now! BARRY, 512 Broadway, New York, NY 10012, 212 WALKER 5-7000

### ELECTRONIC ENGINEERING & INSTRUCTION

TV tuner repairs—Complete course details, 12 repair tricks. Many plans. Two lessons, all for \$2. Refundable. FRANK BOCEK, Box 3236 (Enterprise), Redding, CA 96001.

DEGREE program in Electronics Engineering. Our 29th year! Free literature. COOK'S INSTITUTE, Dept. 14, Box 20345, Jackson, MS 39209.

### EDUCATION & INSTRUCTION

SHORTCUT to success: Highly effective, profitable short courses (75 courses). Study at home. Diploma awarded. Our 29th year! Free literature. CIEE-E Box 20345, Jackson, MS 39209.

FASTEST and easiest way to a top paying engineering career. Free literature. TECHNOLOGY INTERNATIONAL, 933 Kifer Drive, Sunnyvale, CA 94086.

### BUSINESS OPPORTUNITIES

START small, highly profitable electronic production in your basement. Investment, knowledge unnecessary. Postcard brings facts. BARTA-AI, Box 248, Walnut Creek, CA 94597

### COLUMBIA 4 CHANNEL SQ

Solid state SQ 4 channel adapter, 2 amps built in. Decodes 4 channel or synthesizes 4 channel. . . . \$35.00

### AM-FM RADIO \$15.00

For console installation, w/face plate, no knobs.

Stereo amps for tape or turntable playback. . . . \$15.00

Pair of matching speakers w/wfms for above . . . . . \$ 5.00

### PHOTO STROBE

For use with most Instamatic cameras. With nicad battery and built-in charger. Never buy flash cubes again. . . . . \$9.95

### CALCULATOR CHASSIS

Fully assembled pocket calculator chassis with calculator chip. Uses LED readouts, not included . \$5.00

### POWER AMP XFMR 380 WATT

115 volt input, 64VCT 6 amp output. \$11.95 each, 2/\$22, 5/\$50

### BOOKSHELF SPEAKERS

Completely finished, 9x12x5 inches. 16 ohm, with extension cord. . . . . \$15/pair

All above material plus shipping. 96 page catalog free.


JOHN MESHNA JR. PO Box 62  
E. Lynn Mass. 01904

### OWN YOUR OWN PICTURE TUBE REBUILDING BUSINESS

With Lakeside Industries rebuilding equipment you can rebuild any picture tube!

For complete details send name, address, zip code to

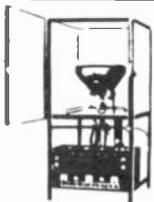LAKESIDE INDUSTRIES  
3520 W. Fullerton Ave.  
Chicago, Ill. 60647  
Phone: 312-342-3399



### ULTA DIGITAL CROSSHATCH

GIVES PROFESSIONAL, ACCURATE COLOR T.V. CONVERGENCE. DIGITAL IC'S COUPLED WITH A

CRYSTAL TIMEBASE OSCILLATOR PROVIDE SYNC FOR PRECISE HORIZONTAL & VERTICAL LINES

ACCURATE 8\*7 DOT OR CROSSHATCH PATTERN ACPower 2\*3 1/2\*6 IN. WT 240Z FITS IN TOOL KIT.

COMES COMPLETE WITH ALL PARTS, CASE CRYSTAL AND GUIDE TO ASSEMBLY & USE

KIT \$31.95 COMPLETELY ASSEMBLED \$41.95

SHIPPING PREPAID IN USA & CANADA NY STATE AOD

PHOTOLUME CORP.  
118 E 28 ST. NEW YORK, N.Y. 10018

DIGITAL:THEORY,DESIGN, CONSTRUCTION

### LOGIC NEWSLETTER

SAMPLE COPY \$ 1.00  
LOGIC NEWSLETTER  
POB 252  
WALDWICK,N.J. 07463

TELEPHONE ANSWERING SYSTEM 3 basic patents, pending applications for major developments. Bistable switching means, ring responsive circuit, first two cassette machine, simplified controls, automatic, recording, etc. Many firsts. No interference with service. No infringement. Low cost to reach \$40 million annual market. TODD 424 W. 119th St. New York 10027 212 865-3435.

# INTERNATIONAL ELECTRONICS UNLIMITED

## DIGITAL INTEGRATED CIRCUITS

	Ea.		Ea.		Ea.
7400	\$.19	7447	\$1.15	74141	\$1.23
7401	.19	7448	1.22	74145	1.15
7402	.19	7450	.24	74150	1.09
7403	.19	7451	.27	74151	.89
7404	.22	7453	.27	74153	1.29
7405	.22	7454	.39	74154	1.59
7406	.39	7460	.19	74155	1.19
7407	.39	7464	.39	74156	1.29
7408	.25	7465	.39	74157	1.29
7409	.25	7472	.36	74161	1.39
7410	.19	7473	.43	74163	1.59
7411	.29	7474	.43	74164	1.89
7413	.79	7475	.75	74165	1.89
7415	.39	7476	.47	74166	1.65
7416	.39	7483	1.11	74173	1.65
7417	.39	7485	1.39	74176	1.09
7420	.19	7486	.44	74177	.99
7422	.29	7489	2.75	74180	1.09
7423	.35	7490	.76	74181	3.65
7425	.39	7491	1.29	74182	.89
7426	.29	7492	.79	74184	2.69
7427	.35	7493	.79	74185	2.19
7430	.22	7494	.89	74190	1.59
7432	.29	7495	.89	74191	1.59
7437	.45	7496	.89	74192	1.49
7438	.39	74100	1.65	74193	1.39
7440	.19	74105	.49	74194	1.39
7441	1.09	74107	.49	74195	.99
7442	.99	74121	.57	74196	1.09
7443	.99	74122	.53	74197	.99
7444	1.10	74123	.99	74198	2.19
7445	1.10	74125	.69	74199	2.19
7446	1.15	74126	.79	74200	7.95

## LOW POWER TTL

74L00	.33	74L51	.33	74L90	1.69
74L02	.33	74L55	.33	74L91	1.45
74L03	.33	74L71	.33	74L93	1.69
74L04	.33	74L72	.49	74L95	1.69
74L06	.33	74L73	.69	74L98	2.79
74L10	.33	74L74	.69	74L164	2.79
74L20	.33	74L78	.79	74L165	2.79
74L30	.33	74L85	1.25		
74L42	1.69	74L86	.69		

## HIGH SPEED TTL

74H00	.33	74H21	.33	74H55	.39
74H01	.33	74H22	.33	74H60	.39
74H04	.33	74H30	.33	74H61	.39
74H08	.33	74H40	.33	74H62	.39
74H10	.33	74H50	.33	74H72	.49
74H11	.33	74H52	.33	74H74	.59
74H20	.33	74H53	.39	74H76	.59

## 8000 SERIES TTL

8091	.59	8214	1.69	8811	.69
8092	.59	8220	1.69	8812	1.10
8095	1.39	8230	2.59	8822	2.59
8121	.89	8520	1.29	8830	2.59
8123	1.59	8551	1.65	8831	2.59
8130	2.19	8552	2.49	8836	.49
8200	2.59	8554	2.49	8880	1.33
8210	3.49	8810	.79		

## 9000 SERIES TTL

9002	.39	9309	.89	9601	.99
9301	1.14	9312	.89	9602	.89

Please specify data sheets required with order. Add \$.50 per data sheet for items priced less than \$1.00 each.

## CMOS

74C00	.39	74C74	1.15	74C162	3.25
74C02	.55	74C76	1.70	74C163	3.25
74C04	.75	74C107	1.50	74C164	3.50
74C08	.75	74C151	2.90	74C173	2.90
74C10	.65	74C154	3.50	74C195	3.00
74C20	.65	74C157	2.19	80C95	1.50
74C42	2.15	74C160	3.25	80C97	1.50
74C73	1.55	74C161	3.25		

## 4000 SERIES RCA-EQUIVALENT

CD4001	.55	CD4013	1.20	CD4023	.55
CD4009	.85	CD4016	1.25	CD4025	.55
CD4010	.85	CD4017	2.95	CD4027	1.35
CD4011	.55	CD4019	1.35	CD4030	.95
CD4012	.55	CD4022	2.75	CD4035	2.85

## MEMORIES

1101	256 bit RAM MOS	1.75
1103	1024 bit RAM MOS	4.95
5260	1024 bit RAM Low Power	3.95
7489	64 bit RAM TTL	2.75
8223	Programmable ROM	4.95

SEPTEMBER - OCTOBER

## BACK TO SCHOOL SPECIALS

Substantial Price Reductions Throughout

Plus an Additional \$5.00 Merchandise Credit for Each \$50.00 Order or Invoices Totalling \$50.00 Within 6-Month Period.

(SEND INVOICES OR COPIES TO OBTAIN CREDIT)

### CALCULATOR CHIPS

5001 LS (40-Pin) Add, subtr., mult. & div., 12-dig. Data supplied with chip \$3.95 ea. Data only — Refundable with purchase 1.00
5002 LS similar to 5001 exc. des. for battery operated - Data supplied with chip 7.95 ea. Data only — Refundable with purchase 1.00
5005 LS (28 pin) Full 4 funct. mem. 12-dig. d/spl. & calc. 7 seg. mltplx. outp. Data suopl. w/chip 8.45 ea. Data only — Refundable with purchase 1.00
MM573E 18 Pin, 6-dig., add, subtr., mult., div. 3.95 ea.

### DIGITAL CLOCK CHIPS

MM 5311 28-pin any readout 6-dig. BCD mux with spec. sheet 9.95 ea.
MM 5312 24-pin any readout 4 digit pps output BCD mux with spec. sheet 6.95 ea.
MM 5313 28-pin any readout 6 digit lpps BCD mux with spec. sheet 7.95 ea.
MM 5314 24-pin LED-Incandescent readout mux 6-digit with spec. sheet 8.95 ea.
MM 5315 40-pin norm. alarm set snooze alarm-timer 12 or 24-hr. operat. with spec. sheet 12.95 ea.

### LED's

MV108 Visible red TO 18 .25 ea. .25 ea.
MV50 Axial leads micromini dome .25 ea. 5/1.00
MV5020 Jumbo clear dome visible red .35 ea. 3/1.00
ME4 Infra red (Invisible) diff. dome .60 ea.

### DISPLAYS

MAN1 Red, 7 seg., .270" \$2.50 ea
MAN2 Red alpha numeric, .32" 4.95 ea
MAN3A Red, 7 seg., .127" in line leads .79 ea
MAN3M Red, 7 seg., .127" staggered leads 1.15 ea
MAN4 Red, 7 seg., .190" 2.15 ea
MAN5 Green, 7 seg., .270" 2.95 ea
MAN7 Red, 7 seg., .270" 1.50 ea
MAN8 Yellow, 7 seg., .270" 3.95 ea
MAN6E .75" high direct viewing LED 4.65 ea
DL707 Red, 7 seg., .3" 2.15 ea

### OPTO ISOLATORS

MCD2 Diodes \$1.09 ea.
MCT2 Transistor .69 ea.

### PHASE LOCKED LOOPS

560 Phase Locked Loop DIP 2.75 ea.
561 Phase Locked Loop DIP 2.75 ea.
562 Phase Locked Loop DIP 2.75 ea.
565 Phase Locked Loop DIP 2.65 ea.
566 Function Generator MINI DIP 2.75 ea.
567 Tone Generator MINI-DIP 2.95 ea.

### LINEAR INTEGRATED CIRCUITS

380 Pos V Reg (super 723) TO-5 \$ .79 ea.
381 Hi performance AMP MINI-DIP, TO-5 .32 ea.
382 Voltage Follower TO-5 .79 ea.
384 Negative Voltage Regul. TO-5 .89 ea.
385 Positive Voltage Regul. TO-5 .95 ea.
387 Op AMP (super 741) MINI-DIP, TO-5 .35 ea.
388 Micro Power Op Amp MINI-DIP 1.10 ea.
389 5 V Regulator 200 ma TO-5 1.10 ea.
389K 5 V 1A Regulator TO-3 1.65 ea.
390 Voltage Follower Op Amp TO-5 1.19 ea.
391 Hi perf. Volt. Compartr. MINI-DIP, TO-5 1.05 ea.
399 Hi-Speed Dual Compartr. DIP 1.29 ea.
390 Neg. Reg. 5.2, 12, 15 TO-3 1.35 ea.
394 Quad Op Amp DIP 1.95 ea.
399 Quad Comparator DIP 1.69 ea.
39T Pos. Volt. Reg. (6V-8V-12V-15V-18V-24V) TO-220 1.95 ea.
390 AGC/Squelch AMPL TO-5 or DIP 1.15 ea.
392 AF-IF Strip-detector DIP .79 ea.
393 AM/FM/SSB Strip DIP 3.25 ea.
396 Pos. Volt. Regulator MINI-DIP .59 ea.
397 2W Stereo amp DIP 2.69 ea.
398 2 Watt Audio Amp DIP 1.49 ea.
398-8 .6W Audio amp MINI-DIP 1.25 ea.
391 Low-Noise Dual Pre-Amp DIP 1.79 ea.
392 Low-Noise Dual Pre-Amp DIP 1.79 ea.
590 Prec. Voltage Regulator DIP .79 ea.
595 Timer MINI-DIP .99 ea.
793 RF-IF AMP MINI-DIP .45 ea.
799 Operational AMPL TO-5 or DIP .29 ea.
791 Dual Different. Compar. DIP .29 ea.
793 Voltage Regulator DIP .59 ea.
799 Dual Hi Perf. Op AMP DIP 1.19 ea.
791 Comp. Op AMP MINI-DIP, TO-5 .35 ea.
797 Dual 741 Op Amp TO-5 or DIP .79 ea.
798 Freq. Adj. 741 MINI-DIP .39 ea.
193 Stereo Pre-Amp DIP .89 ea.
194 FM MulpX Stereo Demod DIP 1.19 ea.
197 FM MulpX Stereo Demod DIP .82 ea.
198 Dual Comp. Op. Amp. MINI-DIP .69 ea.
LM211 Dual LM 211 Volt. Comp. DIP 1.95 ea.
3965 TV-FM Sound System DIP .69 ea.
3975 FM Det.-LMTR & Audio Pre-Amp DIP .79 ea.
3900 Quad Amplifier DIP .59 ea.
3905 Precision Timer DIP .65 ea.
724 Core Mem Sense AMPL DIP 1.89 ea.
725 Core Mem Sense AMPL DIP .89 ea.
734 Core Mem Sense Amp DIP 2.59 ea.
735 Core Mem Sense Amp DIP 1.15 ea.
848 Function Generator DIP 4.95 ea.
7451 Dual Peripheral Driver MINI-DIP .39 ea.
7452 Dual Peripheral Driver MINI-DIP .39 ea.
7453 (351) Dual Periph. Driver MINI-DIP .39 ea.
7491 Quad. seg. driver for LED readout DIP 1.55 ea.
7492 Hex digit driver DIP 1.69 ea.

Please specify which data sheets are required with order. Add \$.50 per data sheet for items priced less than \$1.00 each.

### TRANSISTOR SPECIAL

Hi Voltage Power Transistors — Prime Quality Typically 40 Beta at 50 MHz. 10W, 1A max TO-5
MPN 400 VOLT \$2.45 ea. With combined
MPN 300 VOLT 1.20 ea. total of 100
MPN 200 VOLT .75 ea. trans — 15% Off

All items are new, unused surplus parts—tested functional. Satisfaction is guaranteed. Shipment will be made via first class mail — postage paid — in U.S., Canada and Mexico within three days from receipt of order. Minimum order — \$5.00. California residents add sales tax.

INTERNATIONAL ELECTRONICS UNLIMITED  
P.O. BOX 1708 MONTEREY, CALIF. 93940 USA

(408) 659-4773

# Quality Electronic Components

## MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS — AXIAL LEAD TYPE —

Temp range: 40°C plus 85°C Tolerance: ±10 plus 50% (greater than 4.7 UFD) -10 plus 75% (4.7 UFD or less)

Value	1	10-90°	240°	Value	1	10-90°	240°
1 UFD/50V	14c	12c	11c	100 UFD/16V	19c	15c	14c
2.2 UFD/50V	14c	12c	11c	100 UFD/25V	24c	18c	17c
3.3 UFD/35V	14c	12c	11c	220 UFD/16V	24c	18c	17c
4.7 UFD/35V	14c	12c	11c	220 UFD/25V	35c	25c	24c
10 UFD/16V	14c	12c	11c	330 UFD/16V	35c	25c	24c
10 UFD/25V	14c	12c	11c	330 UFD/25V	44c	35c	32c
22 UFD/16V	14c	12c	11c	470 UFD/16V	37c	30c	27c
22 UFD/25V	15c	13c	12c	470 UFD/25V	49c	39c	35c
33 UFD/16V	15c	12c	11c	1000 UFD/16V	49c	39c	35c
33 UFD/25V	17c	13c	12c	1000 UFD/25V	75c	60c	55c
47 UFD/16V	17c	14c	13c	2200 UFD/16V	75c	60c	55c
47 UFD/25V	19c	15c	14c				

\* 10 pcs. per capacitance value

### Ultronic 1100 Calculator



PRICE \$29.95

### IC SOCKETS

8 Pin DIP Solder	35c	10/\$ 3.00
14 Pin DIP Solder	45c	10/\$ 4.30
16 Pin DIP Solder	50c	10/\$ 4.75
24 Pin DIP Solder	\$1.25	10/\$11.00
8 Pin DIP WW	35c	10/\$ 3.00
14 Pin DIP WW	50c	10/\$ 4.75
16 Pin DIP WW	60c	10/\$ 5.50
24 Pin DIP WW	\$1.25	10/\$11.00

Also available are Linear IC's, Transistors, Diodes, LED's, Relays, Switches, Displays and more.

### ½ & ¼ WATT CARBON COMP. RESISTORS

5 each of the 85 standard 10% values (2.2-22M) ½ W Resistors (425 pcs.) Sorted by value \$12/set 2-4 are \$11/set 5-9 are \$10/set.

5 each of the 70 standard 10% values (10-5.6M) ¼ W Resistors (350 pcs.) Sorted by value \$12/set 2-4 are \$11/set 5-9 are \$10/set.

Resistors also available individually, in other assortments or in boxes of 1000 pcs. per value. ¼ W are hot molded MIL-R-11F specification types.



### DIGITAL TTL

1-99°	100-999°	1-99°	100-999°	1-99°	100-999°
7400N	32c	28c	7446N	\$1.30	\$1.10
7401N	32c	28c	7447N	\$1.30	\$1.10
7402N	32c	28c	7448N	\$1.35	\$1.15
7403N	32c	28c	7450N	32c	28c
7404N	35c	31c	7451N	32c	28c
7405N	35c	31c	7453N	32c	28c
7406N	52c	46c	7454N	32c	28c
7407N	52c	46c	7459N	32c	28c
7408N	36c	32c	7460N	32c	28c
7409N	36c	32c	7470N	36c	32c
7410N	32c	28c	7472N	40c	35c
7411N	35c	31c	7473N	52c	45c
7413N	63c	56c	7474N	52c	45c
7416N	50c	44c	7475N	85c	72c
7417N	50c	44c	7476N	60c	55c
7418N	35c	31c	7480N	74c	65c
7420N	32c	28c	7482N	\$1.02	91c
7423N	75c	67c	7483N	\$1.58	\$1.40
7426N	36c	32c	7486N	60c	55c
7430N	32c	28c	7489N	\$4.50	\$4.00
7437N	51c	46c	7490N	85c	72c
7438N	51c	46c	7491N	\$1.37	\$1.22
7440N	32c	28c	7492N	85c	72c
7441N	\$1.45	\$1.27	7493N	85c	72c
7442N	\$1.20	\$1.07	7494N	\$1.20	\$1.07
7445N	\$1.62	\$1.44	7495N	\$1.20	\$1.07

1 AMP SILICON RECTIFIERS			
IN4001	50 PIV	12/\$1.00	100/\$ 6.00
IN4005	600 PIV	8/\$1.00	100/\$ 9.00
IN4007	1000 PIV	6/\$1.00	100/\$11.00

### Send for Free Catalog or Mail Readers Service Card

COD ORDERS ACCEPTED FOR SAME DAY SHIPMENT CALL 218-681-6674

Orders Less than \$10.00 add 50c Service Charge—Others Postpaid "Only Quality Components Sold!"

### DIGI-KEY CORPORATION

P.O. Box 126 Thief River Falls, MN 56701

## FOR SALE

**TWENTY** disc. or 10 bar magnets. \$1.00. **MAGNETS**, Box 192-E, Randallstown, MD 21133

**GIANT** 126 page Canadian surplus catalog. \$1.00. **ETCO ELECTRONICS**, Dept. RE, Box 741, Montreal, Canada.

**DIGITAL electronics!** Complete schematics, parts lists, theories—Discrete component digital clock, \$3.00. Increase technical competence, hobby skills—Complete course in Digital Electronics is highly effective, \$10.00. Free literature. **DYNASIGN**, Box 60R2, Wayland, MA 01778

**RADIO & TV tubes** 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL**, 4217-E University, San Diego, CA 92105

**SURPRISE!** Build inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free! **GBS**, Box 100B, Greenbank, WV 24944

**SEMICONDUCTOR** and parts catalog. **J. & J. ELECTRONICS**, Box 1437, Winnipeg, Manitoba, Canada

**MANUALS** for Govt. surplus radios, test sets, scopes. List 50¢ (coin). **BOOKS**, 7218 Roanne Drive, Washington, DC 20021

**LOW noise resistors** - ¼W, 5%, carbon film from 10 to 3.3M ohms for 3.5¢ each. Fifty of one value for \$1.25. Specifications upon request. 75¢ postage and handling charge. Deduct 10% on orders over \$50.00. **COMPONENTS CENTER-RE**, Box 134, New York, NY 10038.

**JAPANESE transistors**, wholesale prices, free catalog. **WEST PACIFIC ELECTRONICS**, Box 25837, W. Los Angeles, CA 90025.

**LEARN design techniques**, Electronics Monthly Newsletter. Digital, linear construction projects, design theory and procedures. Sample copy \$1.00. **VALLEY WEST**, Box 2119-A, Sunnyvale, CA 94087

**LASER diode**, 6W, GaAs: \$10.25; liquid xtal (Illico) 3½ digit, .4": \$9.75; 8038 vco: \$5.95 intel 1103: \$3.00. Catalog: 10¢. **ELECTRONIC DISCOUNT SALES**, 138 N. 81st St., Mesa, AZ 85207

**HYBRID touch-tone generator**, MH8913J \$18.00. Matching Chometrics keyboard #ER21624 \$9.25. Full catalog 25¢ or free with order. **KA ELECTRONIC SALES**, Dept RE, 1220 Majesty, Dallas, TX 75247

**NEW Canadian Magazine**, "Electronics Workshop", \$5.00 yearly, sample \$1.00. **ETHCO**, Box 741 "A", Montreal, Canada

**DELTA Mark Ten-B**, 12 volt, negative ground, \$37.50 post paid. Send: **BERCOM ELECTRONICS**, P.O. BOX 237, Bergenfield, NJ 07621

**ELECTRONIC surplus 1974 catalog** — 25¢. Refundable w/order. **ATLANTIS**, Box 12654/4E, Tucson, AZ 85711

**ELECTRONIC Ignition**: Capacitor, transistor, pointless. Auburn sparkplugs. Information 10¢. **ANDERSON ENGINEERING**, Epsom, NH 03234

**CANADIAN'S** free catalog. IC's Semi's, parts. **CORNET ELECTRONICS**, 649A Notre Dame W., Montreal, Que. Canada, H3C-1H8

**BIG switch** lets little kids operate lights \$4. Telephone answering machines \$69.95. **LO COMPANY**, 13-B Fairview, Millbrae, CA 94030

**MELLOTRONS** — ARP Synthesizers. Low prices. **DAN KEEN**, Dept. R, 219 19th Street, Avalon, NJ 08202

**DIAGRAMS**, servicing information, television-radio, \$1.95. **PUBLICATIONS**, 1760 Balsam, Highland Park, IL 60035.

**EXCEPTIONAL 5-acre ranch**. Lake Conchas, New Mexico. Only \$995 per acre. Vacation paradise. Good long-term investment. Easy terms. Free brochure. **RANCHOS**, Box 2004RE, Alameda, CA 94501

**PARANOID???** ... Surveillance countermeasure equipment catalog \$1.00. **SECURITY BOX 671RE**, Westwood NJ 07675.

**UHF AFC TV tuner**, six channel memory selection. Send for details and useful converter applications. **VERSITRONICS COMPANY**, Box 872 — 582 Roger Williams, Highland Park, IL 60035

**FLYBACK checker**, scope adaptor. Easy to operate. Removal from circuit not necessary. \$10.95 post paid. **E.P. ELECTRONICS**, 17 East El Vado, Tucson, AZ 85706

**DIGITAL, Analog Electronics**. Theory, design, construction. Wide variety of topics. Lots of circuit ideas. All projects tested. Send \$1.00 for complete information and sample monthly issue. **SYNTEC CORP.**, P.O. BOX K, Bellingham, WA 98225

**LIQUID crystal digital wristwatch display**. Includes instructions for building your own. Identical display used in high-priced wristwatches. Could also be used in projects requiring 4-digit display. \$12.95 each. Limited quantity. **TRICOUNTRY WINSLOW**, Box 5885, Grand Central Station, New York, NY 10017

**CANADIANS** — We stock a broad line of electronic parts, including most solid-state devices — Send for free flyer. **DARTEX ELECTRONICS**, Dept. R, Box 2460, Dartmouth, Nova Scotia

## PLANS & KITS

**ELECTRONIC organ kits**, keyboards and many components. Independent and divider tone generators. All diode keying. IC circuitry. Supplement your Artisan Organ. 35¢ for catalog. **DEVTRONIX ORGAN PRODUCTS**, Dept. B, 5872 Amapola Dr., San Jose, CA 95129

**FREE catalog**. Most unusual electronic kits available. Music accessories, surf, wind synthesizers, wind chimes, many others. **PAIA Electronics**, Box B14359, Oklahoma City, OK 73114.

**CONVERT** any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **SANDERS**, Dept. A-25, Box 92102, Houston, TX 77010

**ELECTRONIC Lock Plans**. Advanced circuits, pick proof, push button, frequency key, analog key. \$2.50 ea. 3/\$6.50. **DIGILOCK**, 7901 SW 64 Ave., # 13, South Miami, FL 33143.

## TUBES

**RECEIVING & industrial tubes**, transistors. All brands-biggest discounts. Technicians, hobbyists, experimenters—request free giant catalog and save! **ZALYTRON**, 469 Jericho Turnpike, Mineola, NY 11501

## Make BIG Profits In YOUR OWN ONE-MAN ELECTRONIC FACTORY!

Start home, spare time. A postcard with your name & address, will bring you Free Illustrated Literature about this unusual opportunity! Write TODAY!

**BARTA-BI**, Box 248, Walnut Creek, Calif. 94597

### F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize study — Tests-Answers for FCC First and Second Class Radiotelephone Licenses Newly revised multiple-choice questions and diagrams cover all areas tested in FCC exams — plus Self-Study Ability Test \$9.95 postpaid Moneyback guarantee

COMMAND PRODUCTIONS P.O. BOX 26348 — E. RADIO ENGINEERING DIVISION • SAN FRANCISCO, CALIF. 94126

### PARTS! CORNELL TUBES!

FREE Send For FREE CORNELL'S New Color Catalog 48 Pgs. New Items IN LOTS OF 100

33¢ per tube

36¢ per tube

ORDER FREE IF NOT SHIPPED IN 24 HOURS!

4215 E. UNIVERSITY AVE. SAN DIEGO, CALIF. 92105

# GIVE AMERICAN CANCER SOCIETY

# Poly Paks 1st in Opto & Calculator Components!


## GIANT SALE ON LED'S LIGHT EMITTING DIODE GaAs INDICATORS

- 1-MV2, TO-18, dome, green, visible ..... \$1.00
  - 1-MV2, green small dome, green diff. lite ..... 1.00
  - 2-MV3, clear small plastic dome, green diff. lite ..... 1.00
  - 2-MV3, micro-mini "pin head" dome, TO-18, green lite ..... 1.00
  - 2-MV3, visible, "coax pin pak", red, mini dome lens ..... 1.00
  - 1-MV4, stud, high power, red, 2-watts ..... 3.95
  - 5-MV10B, visible, red, clear dome lens TO-18 ..... 1.00
  - 5-MV10C, visible, red, diffused, dome lens, TO-18 ..... 1.00
  - 5-MV50, axial leads, micro-mini dome, clear, red, TO-18 ..... 1.00
  - 1-MV52, micro-mini, axial green lens, green lite ..... 1.00
  - 1-MV53, micro-mini, axial yellow lens, yellow lite ..... 1.00
  - 5-MV54, micro-mini, axial leads, red lens, red lite ..... 1.00
  - 5-MV55, micro-mini, axial leads, red lens, red lite ..... 1.00
  - 5-MV5012, red small dome lens, red lite, TO-18 ..... 1.00
  - 5-MV5013, sm. dome, 2 hi red dome, soft red diff. lite, TO-18 ..... 1.00
  - 5-MV5020, jumbo clear dome, visible, red, TO-18 ..... 1.00
  - 1-MV5040, 4-LED red array, with 5-lead pak ..... 1.49
  - 5-MV5054, red jumbo dome lens, TO-18 red lite, upright ..... 1.00
  - 5-MV5080, TO-18, micro-mini red dome, red lite ..... 1.00
  - 5-MV5090, TO-18, micro-mini flat clear dome, red lite ..... 1.00
  - 1-MV5094, red bi-polar, solid state lamp V to 110-115VAC-DC ..... 1.98
  - 2-MV5222, green jumbo dome, green lite, panel snap-in ..... 1.00
  - 2-MV5282, micro-mini, green lens TO-18, green lite ..... 1.00
  - 2-MV5322, yellow jumbo dome, yellow lite, panel snap-in ..... 1.00
  - 1-MV5491, jumbo, Tri-State, RED, GREEN, OFF, special ..... 1.49
  - 2-MT2, photo transistor, light sensor, TO-18 ..... 1.00
- COUPLERS**
- 2-MCT2, 1500V isolation photo transistor ..... 1.00
  - 2-MCD2, 1500V isolation photo diode ..... 1.00



## 7-SEGMENT LED Readouts (All "LED" TYPES)

Type	Char.	Each	Special
MAN-1	.27	\$3.75	3 for \$9.
MAN-3	.12	1.49	3 for \$3.
MAN-4	.19	2.50	3 for \$6.

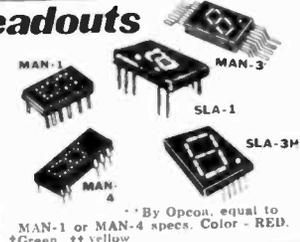

### REFLECTIVE BAR TYPES

SLA-1**	.33	2.10	3 for \$5.
SLA-3**	.70	4.95	3 for \$13.
SLA-11**	.33†	3.50	3 for \$10.
SLA-21**	.33††	3.95	3 for \$10.

## LED MITY DIGIT "DCM'S" \*Your choice of 5 red LED readouts!

Scientific Devices "Digital Counting Modules" outperform any other DCM on the market today. More features than ever before! Not gaseous, not incandescents, not noisy but the modern LED. Choose from such famous manufacturers as Monsanto's MAN-1, MAN-4, Litronics 707 and 704, Opcos's SLA-1 (the last 4 having character heights of 0.33 at no extra charge). Each kit includes 3x2" p.c. board with fingers for a FREE edge connector, side-mounting dip socket, LED readout of your choice, resistors, 3 IC's, and Molex connectors (this ELIMINATES SOLDERING YOUR IC'S) and booklet. INCLUDES P.C. EDGE CONNECTOR — FREE!

**Only \$9.99**

Buy 3 take 10%.

Model	Char.	Maker
MAN-1	27 h.	Monsanto
MAN-4	19 h.	Monsanto
707	33 h.	Litronics
704	33 h.	Litronics
SLA-1*	33 h.	Opcos

\* Pin-for-pin MAN-1. \*\* Pin-for-pin MAN-4, elec. char. same

## 9 "MINI" DIGITS Only \$6.95 ON A SUBSTRATE

Made by ANTEX No. DA1099. This Numarray is a GAASP numeric LED DISPLAY designed for calculators, miniature equipment — it's the latest in calculator construction. MEASURES ONLY: 3/4 x 2 3/4 x 1/32" on a ceramic substrate, internally multiplexed, providing 8 x 110 character digits each with its own decimal point and an extra-digit located in left hand position displaying a minus sign or overflow. All anode segments of each digit are connected in parallel reducing number of connections to 17 for a 9-digit display. Each digit contains its own BUBBLE MAGNIFIER MAX. SPEEDS: 60msec, 10 mils per segment, 3 volts, brightness 125-ft./l. With spec sheet.

### MUX'D DIGITAL CLOCK PC BOARD

Each board properly multiplexed for 6 digits, to hold MAN-1's, MAN-3's, MAN-4's, Litronics 707 (MAN-1), and 704's (MAN-1), and Opcos's SLA-1 (MAN-1). Board 6 7/8" long with spec sheets.

MAN-1	Litronics 707 (MAN-1*)
MAN-3	Litronics 704 (MAN-4**)
MAN-4	Opcos SLA-1 (MAN-1*)

\* Elec char. same as MAN-1 or 4.

**Only \$2.50**

## KRONOS WITH "TIME BASE" \*\*

Cabinet is 6" x 5 1/2" x 6".

**CHOOSE YOUR READOUT**

Type	LED	Charac.
KR-101	MAN-3	.12
KR-103	MAN-4	.33
KR-105	707†	.33
KR-106	704†	.33
KR-107	SLA-1† Red	.33
KR-108	SLA-1† Green	.33

• 12 or 24-hr clock

† "MAN" LED readouts are "all LEDs" but the Litronic 707 and Opcos SLA-1, like the MAN-1, are of the reflective bar segment technique, the 704 is the reflective bar version of the MAN-4.

**\$39** Any Type Clock less time-base

**NEW FOR 1974!**

• with TIME BASE \$54.95

Scientific Devices introduces the new any LED Kronos digital clock. That's right, you can choose the "ALL-LED" Man-1, Man-3, and Man-4, and the new reflective bar types with the larger digits, at only one price, \$39. This is a Scientific Device first! We even have the GREEN LED readouts at a slightly extra cost. We have more for \$19.95 we have available as an extra option to Naval Observatory your clock, or (\*) extra option to Naval Observatory your clock, or making it an all-purpose allduty unit. For indoor and outdoor activity. This "TIME BASE" is the simplest on the market today with the help of one of the largest time-base manufacturers for the famous digital wrist watches. Therefore, current drain is negligible, not like other cumbersome types. It's easy to construct, easy to slip into the Kronos of your choice and connect with easy instructions. Its overall design is simple and easy to construct. The kit is complete with famous black-and-white TEN-TEC cabinet, plus all accessories with booklets. Features include 3 setting controls, 1-hour per second, 1-minute per second, and hold button. KR100 series is a Scientific Device exclusive!

**CRYSTAL TIME BASE FOR ANY KRONOS\***

**\$19.95**

Includes precision crystal, time-base IC, pc board & accessories with info.

## WRIST WATCH Only \$19.95 LIQUID CRYSTAL DISPLAY

• 3-1/2 digit, 7 segment  
• Only 1-1/16 x 11/16 x 1/4"

See POPULAR ELECTRONICS (Jan., 1974) for building your own electronic digital wristwatch using the Liquid Crystal Display (LCD) as its basic. Easy to see, 3 1/2 digit display, requires less than 1/1000 of power as LED'S. Visibility increases with ambient light. Difficult reading of LED'S in light. Features SECONDS in center of display. NO NEED OF TRANSISTOR-RESISTOR interface, as LED'S, thus smaller package. Chip contains holder, tiny connecting terminals, and "slide-in-place chrome spring face plate". Size of display in holder: 1-1/16 x 11/16 x 1/4". Operating freq. 32 hertz. 45-microwatts of power. Operates from 1.5V hearing aid cell. Use the new and latest CMOS micro-circuitry. We include copy of write up from PE magazine.



## Calculator Basics

MAKE YOUR OWN CALCULATORS WITH OUR LOW PRICED Your Choice

**6 & 8 DIGIT POCKET CALCULATOR BASIC KITS**

**BASIC KIT #1** — includes case, all-function Flex Key Keyboard, Cal Tech CT6002 calculator chip, 9-digit Antex display with built-on individual magnifiers, plus sheets.

**BASIC KIT #2** — same as Basic #1 except calculator chip is National 8-digit MM5725.

**BASIC KIT #3** — same as Basic #1 except calculator chip is National 6-digit MM5736 and 75492.



**POLY PAKS BLUE RIBBON Policy** INCLUDES

- 20-Years of Business INTEGRITY
- 20-Years of Money-Back GUARANTEES
- 20-Years of Economy! LOWEST PRICES!

**48-HR. SERVICE**

**CRYSTAL OSCILLATOR** Rare buy of these popular precision modules that are used by hams, clock enthusiasts, hobbyists. By Monitor, Type 860. Freq: 4,000 MHz. Accuracy to .001. Requires 6VDC. Generates a square wave on output. 1 1/4 x 1 x 1/2".

**\$4.95**

**POCKET CALCULATOR CASE**

**Only \$2.50**



## LOWEST PRICES ON NATIONAL "CALCULATOR CHIPS"

- CT5001 12-Digits, 40 Pin ..... \$5.95 3 for \$17.
  - CT5002 12-Digit version of 5001 7.77 3 for \$21.
  - CT5005 12-Digits, 28-Pin ..... 8.99 3 for \$27.
- with 3-function memory.
- MM5725 8-Digits, 4-Funct. LED 6.95 3 for \$18.
  - MM5736 6-Digits, 28-Pin. 9V 4.95 3 for \$12.
- 3 for \$6.00

**THREE QUARTER INCH DIGITS**

Any color **\$4.95**

RED — GREEN — YELLOW

3 for \$13.

**POCKET CALCULATOR KEYBOARD**

For hand-held units, properly multiplexed for chip CT-5001, 2, 12 or Motek 5010-12, 18 feather-touch keys, by FLEX-KEY.

**Only \$6.95**

3 for \$18.

**BY OPCOA**

• 7 Segments, 30 mils  
• 0.7 character • 0 to 9

Order by type number

Type	Color
SLA-3H	RED
SLA-4**	RED
SLA-13	GREEN
SLA-14*	GREEN
SLA-23	YELLOW
SLA-24*	YELLOW

\* Plus or Minus one

**OAK FEATHER-TOUCH SWITCHES**

• For RTTY Switches  
• Printed Circuits Mtd. by OAK (Ham's note, No. 0\* 8\*  
• For Unique Panel RTTY, too) data systems. 1\* 0\* CE†  
same as used in Keyboard. 2\* 0\* CE†  
Calculator, SPST. Normally Open. 24V 1 amp contacts. 3\* 0\* CE†  
Characters and letters easily changed. 4\* 0\* CE†  
Printed circuit. 5\* 0\* CE†  
Blue top, white characters. 6\* 0\* CE†  
White top, black numbers. 7\* 0\* CE†

3 for \$1 39¢ ea

## "BRIGHTEST LED READOUT AROUND" BY XCITON

**Only \$2.95**

Buy 3 take 10%.

Will outperform Opcos's, Monsanto, Hewlett Packard, etc. MORE BRILLIANT, LESS CURRENT DRAIN (only 10 mils, others 20 to 30 mils). New low price! 0 to 9 numerals, with left decimals. Fits into 14-pin IC sockets. Character height 0.33. Order by type number

Type	Color
XAN-72	RED
XAN-52	GREEN

**CALCULATOR KEYBOARD SWITCH KITS**

**Kit of 17 for \$4.95**

• 10-pc. kit, 0-to-9 only 2.50  
• Same type as above.

Each switch made by Oak 2415, SPST normally open, 24V 1 amp contacts. Kit includes 0-to-9 (10 switches) white with black numerals) decimal, white with black dot, and CE, CL and 4 functions blue with white characters.

**"ULTRA BRITE" XCITON LED'S**

9-pc. kit **\$2.50**

One of Poly Paks exclusive ultra-brite offers at "dull" prices. Kit includes: 3 REDS, 3 GREENS, 3 YELLOWS, each including JUMBO'S, MEDIUM and MICRO'S.

**CLOCK CHIPS as Low as \$7.77 ON A "DIP"**

MM5311	6-digit 28-Pin	\$7.77
MM5312	4-digit 24-Pin	7.77
MM5313	6-digit 28-Pin	7.77
MM5314	6-digit 24-Pin	7.77
MM5316	4-digit 40-Pin, Alarm	9.95

• 1-MM5316, DIGITAL ALARM CLOCK  
FACTORY FALLOUT — \$1.00 EA

**4-FUNCTION MEMORY "CALCULATOR KIT" ONLY \$49.95**

Pocket type, the lowest price 4-function memory with all arithmetic. Complete with all parts, instruction booklet.

Terms: add postage. Rated: net 30  
Phone Orders: Wakefield, Mass. (617) 246-3829  
Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

• 2hc CATALOG on Fiber Optics, IC's, Semi's, Parts  
MINIMUM ORDER — \$4.00

**POLY PAKS**  
P.O. BOX 942R, LYNNFIELD, MASS. 01940

## MAGNUS TONE GENERATOR BOARD



These MAGNUS Model 1700 tone generator boards contain 12 separate oscillators, which produce a total of 37 notes. In addition, 3 additional oscillators are for chords, plus a power output stage of about 5 watts. A great basic start for your electronic organ. Boards are new, but as is, since some of the spring contacts may be bent, or a part broken. Board measures 27 1/4" x 4 1/2". Value of parts alone worth many times our price. With data sheet.  
**STOCK NO. J5200 Wt. 2 lbs. \$14.94 2/27.00**



## 12 VOLT AM AUTO RADIOS

These radios were removed from new cars as having minor defects, and since the cars were under warranty, they were repalced rather than repaired. Some work as is. Some have knobs missing.  
**STOCK NO. J5201 \$7.95 ea. 3/20.00**



## RADIATION METER

VICTOREEN Model 710, brand new radiation meter. Sensing element is hermetically sealed ionization chamber. Uses 2 "D" cells, and 2 22 volt hearing aid batteries. 3 scales, reads from .1 to 50 roentgens per hour. Designed by government for CD units. Usefull anywhere radiation is present, With manual and Instr.  
**STOCK NO. J5202 \$5.95 ea. 2/10.00**

## HI-CURRENT TRANSFORMER

10 volts @ 10 A., 18 volts @ 6 A., 17 volts @ 6 A. Conservatively rated. Wt. 6 lbs. 2 1/2 x 2 1/2 x 3 3/4 x 3  
**STOCK NO. J9906 \$8.95 2/15.00**

Include sufficient postage. Excess refunded. Send for new catalog No. 11, just out. **MINIMUM ORDER \$5.00**



# DELTA ELECTRONICS CO.

BOX 1, LYNN, MASSACHUSETTS 01903  
 Phone (617) 388-4705

Circle 90 on reader service card



**GREGORY ELECTRONICS**  
*The FM Used*  
**Equipment People.**  
 Send for New Catalog

## GENERAL ELECTRIC T.P.L. SOLID STATE TWO-WAY RADIOS



(Specify frequency range)

FE/RE 52, JA1, 2, or 3 series, 25-50 MHz, 12 volts, 35 watts, front or rear mount, fully solid state receive. 3 tubes in transmitter, fully narrow band, complete with accessories

**\$178.00**

FE/RE 53, JA6 series, 150-174 MHz, 12 volts, 35 watts, front or rear mount, fully solid state receive. 3 tubes in transmitter, fully narrow band, complete with accessories

**\$198.00**

(Specify frequency range)

FE/RE 72, JA1, 2, or 3 series, 25-50 MHz, 12 volts, 100 watts, front or rear mount, fully solid state receive. 4 tubes in transmitter, fully narrow band, complete with accessories

**\$288.00**

FE/RE 73, JA6 series, 150-174 MHz, 12 volts, 80 watts, front or rear mount, fully solid state receive. 3 tubes in transmitter, fully narrow band, complete with accessories

**\$298.00**

**R.C.A.**

CMFT50, 25-54 MHz, 12 volt, 50 watts, transistorized power supply, partially transistorized receiver, fully narrow band with accessories

**\$128.00**



## GREGORY ELECTRONICS CORP.

251 Rt. 46, Saddle Brook, N. J. 07662  
 Phone: (201) 489-9000

# VALU-PAK

LED 7 SEGMENT READOUTS		EACH		10 PAK		CMOS		EACH		10 PAK	
MAN-3	.115" w/RR decimal (claw)	\$ .90	\$ 8.00	CD 4016	Analog Switch	\$1.20	\$10.00				
MAN-3	.115" w/RR decimal (flat leads)	.80	7.00	74C74	Dual D FF	1.20	10.00				
MAN-4	.19" w/RR decimal (DIP)	2.00	17.50	74C76	Dual JK FF	1.30	11.00				
DL 33	.1" 3 digits in one 12 pin DIP	2.50	22.00	74C195	4 bit Shift Register	2.30	20.00				
LED DISCRETE DEVICES		EACH		10 PAK		TTL		EACH		10 PAK	
MV50	axial micro-mini red	\$ .15	\$ 1.00	7400 HN	\$ .22	\$ 1.80	7492	1.20	10.00		
MV5021	diffused dome red	.25	2.00	7401	.28	2.50	74107	.50	4.50		
MV4	2 WATT hi-pwr red (STUD)	2.25	20.00	7402	.28	2.50	74153	1.35	12.00		
MV4H	2 WATT hi-pwr red (hi-dome)	2.50	22.00	7403	.28	2.50	74193	1.40	12.00		
ME5	2 WATT hi-pwr INFRA-RED	2.50	22.00	7404	.22	1.80	74H00	.30	2.50		
				7404 HN	.28	2.50	74H04	.30	2.50		
				7405	.28	2.50	74H10	.30	2.50		
				7406	.40	3.50	74H53	.30	2.50		
				7408	.30	2.60	74L00	.38	3.50		
				7410	.28	2.50	74L36	.38	3.50		
				7411	.40	3.50	74L71	.35	3.00		
				7416	.45	3.80	74L74	.75	6.00		
				7420	.28	2.50					
				7426	.35	3.00					
				7430	.22	2.00					
				7441	1.25	10.00					
				7445	1.10	9.00					
				7450	.22	1.80					
				7460	.22	1.80					
				7473	.50	4.50					
				7474	.50	4.50					
				7483	1.00	9.00					

## CT5001 CALCULATOR CHIP SPECIAL!

Forty-pin calculator chip will add, subtract, multiply and divide; 12-digit display and calculate; chain calculations; true credit balance sign output; automatic overflow indication; fixed decimal point at 0, 2, 3, or 4; leading zero suppression.  
**\$5.95 EACH 10 FOR \$49.00**

## Memory IC 74S206

1X256 BIPOLAR TTL RAM  
**\$3.49 EA. 10 FOR \$29.00**

ALL MERCHANDISE IS NEW UNUSED SURPLUS AND IS SOLD ON A MONEY BACK GUARANTEE.

## OPTO ISOLATOR SPECIAL!

MONSANTO MCT26 6 PIN MINI-DIP  
**\$1.25 EACH 10 FOR \$10.00**

## FLIP FLOP SPECIAL!

Dual low power RST flip Flop-DIP package similar to SIGNETICS #8424. With data & application notes. -----10 FOR \$2.50

FIVE DOLLAR MINIMUM ORDER. FREE FIRST CLASS POSTAGE ON ALL ORDERS. CALIFORNIA RESIDENTS PLEASE ADD SALES TAX.

SEND STAMP FOR FREE FLYER. WRITE TO:  
**VALU-PAK box AF Carmichael, Ca. 95608 VALU-PAK**



## LED RIOT

LED Starter Kit \$3.50

- 8 Lg. Red LEDs 1 Red Bullet
- 2 Lg. Green LEDs 1 Green Bullet
- 2 Lg. Yellow LEDs 10 Resistors
- 1 Lg. Multicolor Exp. Book

- LARGE RED LED's 12 \$2 50/ \$7
- LARGE GREEN LED's 5 \$2 30 \$10
- LARGE YELLOW LED's 5 \$2 30/ \$10
- MULTICOLOR LED's 2 \$1 12/ \$5

(Color changes with Voltage)

## LED Experimenter's Kit \$6.75

- 15 Lg. Red LED's 2 Red Bullets
- 2 Lg. Green LED's 2 Gn. Bullets
- 2 Lg. Yellow LED's 10 Lim. Res.
- 2 Multicolor LED's 1 Book Exp.
- 4 SLA-1's missing 1 Segment
- 1 SLA-17-seg READOUT w/d.P.

## READOUTS

- SLA-1 .33" Red 3 \$5 10 \$15
- SLA-11 .33" Green 2 \$5 10 \$20
- SLA-21 .33" Yellow 2 \$5 10 \$20
- (above in Epoxy 14 Pin DIP)
- SLA-3H .77" Red 3 \$10 10 \$30
- SLA-13H .77" Green 3 \$12 10 \$35
- SLA-23H .77" Yellow 3 \$12 10 \$35
- SLA-1's with 1 seg. Missing (Ideal for signs, exp.) 2 \$1 10 \$4 30 \$10

**SATISFACTION GUARANTEED**  
**ELECTRONICS UNLIMITED**  
 P. O. BOX 91 OLNEY, MD. 20832  
 Circle 96 reader service card

# \$1 ECONOMY PAKS

## PARTS

- 30 POWER RESISTORS, 3 to 25w. sq. vit. asst. values ..... \$1
- 6 MINI REEDS, switches in glass 1 1/4" long spat ..... \$1
- 10 TRANSISTOR SOCKETS, for pnp, npn transistors ..... \$1
- 25 SURPRISE PAK, includes wide asst. of parts ..... \$1
- 50 TERMINAL STRIPS, includes 1 to 8 solder lug types ..... \$1
- 40 RADIO & TV KNOBS, asst. shapes, colors, sizes ..... \$1
- 30 SQUARE DISCS, space savers, 85 mmf. to .01 mf ..... \$1
- 75 PREFORMED RESISTORS, for printed ckt use, 1/2 w ..... \$1
- 10 RCA PHONO PLUGS AND JACKS, turners, amps, doubles too ..... \$1
- 10 KODAK LENSES, piano convex, concave, mirror, rd. & sq. .... \$1
- 50 TUBE SOCKETS, 4 to 9 types includes recept. plugs too ..... \$1
- 60 PREFORMED DISCS, asst. values to .01 mf p.c. use ..... \$1
- 20 DIPPED MYLARS, includes dipped silver mica too, asst. val ..... \$1
- 50 COILS & CHOKES, 1/2, 1, 2 watt bobbins too ..... \$1
- 50 PRECISION RESISTORS, 1%, 1/2, 1, 2 watt bobbins too ..... \$1
- 50 TUBULAR CONDENSERS, includes dipped, mylar, upright, asst ..... \$1
- 50 "DOG BONE" CONDENSERS, includes NPO, N-750, hi-q, etc. .... \$1
- 10 SUBMINIATURE IFS, 65Kcs, 1 x 1 x 1". For transistor ckt's ..... \$1
- 10 TRANSISTOR ELECTROLYTICS, axial & upright .5 to 100 mf ..... \$1
- 10 NE-2 BULBS, less resistor for 100's of neon ckt's ..... \$1
- 30 POLYSTYRENE CAPACITORS, finest caps made, C thru case ..... \$1
- 10 PANEL SWITCHES, 110vac, rotary, thermal, slide ..... \$1
- 10 VOLUME CONTROLS, single, double, 300 ohm, 500 ohm, etc. .... \$1
- 40 "WORLD'S SMALLEST CAPACITORS", Aerovox cerofol, to 1mf ..... \$1
- 40 "MICRO MINIATURE RESISTORS", 1/8, 1/4, 1% too ..... \$1
- 30 MOLDED CAPS, includes plastic, poly, dipped, ceramic ..... \$1
- 50 ONE WATERS, 1% and 5% cool 100 ohm to 20 meg ..... \$1
- 10 ELECTROLYTICS, includes FT'S, 5 types for AC ckt's ..... \$1
- 6 TRIMMER POTS, 100, 200, 250, 500, 2k, 5k, s.d. adj. .... \$1
- 80 MICA CONDENSERS, to .01 mf 1KV silvers too, asst. .... \$1
- 35 TWO WATERS, includes carbon & Corning, 1% and 5% too ..... \$1
- 3-8-ft. SPT, 100' roll, with switch attached, 600' ..... \$1
- 40-PC WIRE SPECIAL, includes asst. lengths, sizes, colors, .... \$1
- 6 TRIM POTS, 50K, 100K, 500K, 2 meg, 5 meg, etc. s.d. adjust ..... \$1
- 10 CRYSTAL CAN RELAYS, unmarked Babcock Leach, 6, 12, 25v ..... \$1
- 30 METAL FILM MINI resistors, 1/2 watt, 1%, finest made, 100's ..... \$1
- 10 pc's. HI-TENS, SHRINK, for protecting connecting wires 100 uses ..... \$1
- 75 MOLEX SOCKETS, most pop connectors for integrated circuits ..... \$1
- 15 LAMPS, for ac sets, flashlights, includes 2.25v, 2.3v, & 6 v ..... \$1
- 10 RESISTOR NETWORKS, for 100's of electronic ckt use ..... \$1
- 10 KODAK MINI CAMERA, 1/16" crystal, used in Instamatic, relay, ..... \$1
- 10 HEAT SINKS, for increasing amps of TO5 transistors, scr's ..... \$1
- 1000-PC FIBER OPTIC SURPRISE, the wire that "LIGHTS UP" ..... \$1
- 10 SLIDE SWITCHES, asst. SPST, DPST, DPDT, for pc, etc. use ..... \$1
- 20 TRIMMER CAPACITORS, mica compression type, asst. values ..... \$1
- 50 CORNING GLASS ONE WATERS, 1% 5% metallic film, axial ..... \$1
- 40 CORNING GLASS TWO WATERS, 1% 5% metallic film, axial ..... \$1
- 30 CORNING GLASS TWO WATERS, 1% 5% metallic film, axial ..... \$1
- 4 IBM BOARDS, by Control Data, loaded with parts ..... \$1
- 10 pc MAGNET KIT, asst. flat, square, round for 100's of uses ..... \$1
- 3 SOLENOIDS, 12v, 24v, asst. shapes, sizes and plunger ..... \$1
- 2 BUZZER ALARMS, energize buzzer sets alarm off, 3-6v ..... \$1
- 10 PRINTED CIRCUIT BOARDS with pre-etched circuits for ..... \$1
- PRINTED CIRCUIT BOARD, G-10, 6x6 with conner, clean ..... \$1
- 25 VITAMIN Q CAPACITORS, 0.1mf to 100mf up to 600v ..... \$1
- 4 TRANSISTOR TRANSFORMERS 500 to 3.2 ohms, 1/2 x 3/8 x 1/2 ..... \$1
- 100 FEET SPAGHETTI TUBING, #16 for bare wire and fiber optics ..... \$1

## WORLD FAMOUS Dollar Stretchers

- 2-2N5296 35-WATT NPN PLASTIC TRANSISTORS, for NE-540 ..... \$1
- 2-2N6109 40-WATT PNP PLASTIC TRANSISTORS, for NE540 ..... \$1
- 10-1N82 GERMANIUM UHF diode, clip-in type ..... \$1
- 5-SCRs 7-AMP TO220, 6-12-24 prv, power tab ..... \$1
- 10-MOS FETS, 2N7000, 2N7002, TO-18, Fairchild ..... \$1
- 5-SCRs & TRIACS up to 25 amps, 6-12-24 prv, studs too ..... \$1
- 2-2N3819, Texas, N channel, 6500 umho TO-18 ..... \$1
- 2-2N2848 UNIUNIONS, plastic transistors, Texas ..... \$1
- 50-SILICON, glass rectifiers, computer, axial leads ..... \$1
- 50-GERMANIUM, glass rectifiers, signal, axial leads ..... \$1
- 8-subminiature, 100mA, rectifiers, axial leads ..... \$1
- 30-500MW ZENERS, axial 4, 6, 9, 10, 12V rectifiers ..... \$1
- 4-2N3055, HOBBY, 40W npn silicon transistors, TO-3 ..... \$1
- 30-3-AMP RECTIFIERS, silicon, epoxy, assorted V, axial ..... \$1
- 2-EPOXY 2-AMP SILICON BRIDGE RECT, 1000 V "comb. type" ..... \$1

- 1- PHOTO TRANSISTOR, with darlington amp filter, ..... \$1
  - 2- PHOTO TRANSISTORS, with darlington amp, 2N5777, GE ..... \$1
  - 4- PHOTO CELLS, Clairex, pancake, 30K-70 ohms ..... \$1
- 2-Sylvania 18,000V Matchstick TV rectifier, 4" x 1/2" with leads ..... \$1
  - 8- ER900 TRIGGER DIODES for SCRs & Triacs ..... \$1
  - 5-FET'S 2x57 N channel 5000 umhos, TO-32 plastic ..... \$1
  - 10-1N914 fast switch diodes, silicon, 4 nanoseconds ..... \$1
  - 2-6 AMP TRIAC 200 PRV, TO-6 ..... \$1
  - 40-ITT MICRO MINI RECTIFIERS silicon porcelain to 1KV ..... \$1
  - 30-WORLD'S SMALLEST RECT, & zeners, 1/2 W, assorted volts ..... \$1
  - 2-2N4269 Nixie tube driver transistors, 1000 npn ..... \$1
  - 2-6000 PIV 50 mill epoxy rectifiers, axial leads ..... \$1
  - 10-BENDIX 25 WATT "pellet" power transistors, silicon ..... \$1
  - 4-80 WATT, 2N1488, silicon, TO3, 60 Vcc, npn ..... \$1
  - 1-2N5036 HI-PWR plastic trans 100 vceo, 7 amp 85 watts ..... \$1
  - 4-2N5228 HOBBY, 35 watts, plastic power, NPN ..... \$1
  - 4-2N6109 HOBBY, 40 watts, plastic power, PNP ..... \$1
  - 5-PLASTIC 35W powers, npn, silicon, hobby 2N6121 ..... \$1
  - 5-PLASTIC 35W powers, npn, silicon, hobby 2N6124 ..... \$1
  - 2-MOS FETS, N channel 10K umos 3N128, TO-18, RCA ..... \$1
  - 1-MOS FETS, DUAL GATE, N chan, 3N187, TO-18, RCA ..... \$1
  - 2-MOS FETS, DUAL GATE, N chan, 3N140, TO-18, RCA ..... \$1
  - 4-RCA 2N3600 NPN, UHF transistors, tv-fm, TO-18, 1000mc ..... \$1
  - 2-MPF-1000, Motorola MOS dual gate "The Claw" ..... \$1
  - 2-2N5655 200 hfe, 250 vceo, power tab 51 ..... \$1

## I.C. & LED HOBBY-ONICS

- 4-DUAL 709, dip pak, op amps, untested ..... \$1
- 10-RCA CA-3000 OP AMPS, TO-5 case ..... \$1
- 4-PHASE LOCK LOOPS, hobby 566, 560, 561 ..... \$1
- 10-TO-5 Case 536, 540, 566, 567, 741 ..... \$1
- 10-LINEAR OP AMPS, 709, 711, 301, 307, hobby ..... \$1
- 3-1-WATT AUDIO AMPLIFIERS, Westinghouse, TO-5 ..... \$1
- 5-HOBBY MEMORY CELLS, SN7481, up to 16-cell, DIP ..... \$1
- 5-MOS REGISTERS, 601 to 6017, TO-5, Mini-DIP's ..... \$1
- 10-IC'S MOS IC's, 74C and CD4000 series, DIP pak ..... \$1
- 10-MINI DIP OP AMPS, 709, 711, 301, 307, hobby ..... \$1
- 10-SIGNALIC OP AMP, 531, 533, 536, 538, 550, 555, DIP's, TO-5 ..... \$1
- 1-5311-14 CLOCK ON A CHIP, 4-or-6 digit, 24-or-28-pin ..... \$1
- 1-CALCULATOR ON A CHIP, hobby, exp. 40-pin, specs ..... \$1
- 1-2516 CHARACTER GENERATORS, hobby, for MAN-2 ..... \$1
- 1-2513 CHARACTER GENERATOR, Hobby for MAN-2 ..... \$1
- 5-IBM IC's with pc board, many parts, from computers ..... \$1
- 1-AM RADIO-ON-A-CHIP, by Sprague, DIP, test 'em ..... \$1
- 1-DUAL 2-WATT "Stereo-AM-On-A-Chip", fallout/Sprague, u-test ..... \$1
- 1-OPCOA SLA-11\*, like MAN-6, green, 1-or-more segs gone, ..... \$1
- 1-OPCOA SLA-30\*, 0.7 charac, readout, 1-or-more segs missing, ..... \$1
- 5-MONSANTO opto isolators, no test, 1500V ..... \$1
- 10-LED HOBBY SURPRISE, asst. types, factory rejects, no test ..... \$1
- 2-OPCOA SLA-1\*, MAN-1, red, .33" charac, 1-or-more segs gone ..... \$1
- 2-MONSANTO MAN-4, .19" charac, 1-or-more segs missing, red ..... \$1
- 5-MONSANTO MAN-3, .12" charac, red, 1-or-more segs missing, ..... \$1
- 2-3-DIGIT OPTICAL READOUTS, some digits good ..... \$1
- 10-SPRAGUE DIPS, LINEAR OP AMPS, 709, 711, 301, 307, hobby ..... \$1
- 1-MAN-3, "THE CLAW", one dot missing, 100% perfect ..... \$1
- 2-MMS736 6-Digit Calculator on a Chip, hobby ..... \$1
- 10-FAIRCHILD-NATIONAL, 9000 Series ICs, dips, hobby ..... \$1

## 8-TRACK PROFESSIONAL \$15.95 TAPE TRANSPORT

FOR HOME USE


Same type unit found in the most expensive home tape players. It's a complete 8-track player system with BUILT-IN PREAMP. Just plug into any stereo amplifier (see some of our low-priced units). Excellent replacement unit, or you can design your own high-quality stereo tape system. It's the type you insert a cartridge to turn-on deck, then enjoy up to 80 minutes of non-stop, non-repeat, stereo. Remove cartridge and trols in preamp. Features: 4 PROGRAM INDICATOR LIGHTS, automatic or manual program change, plays your car tapes at home. WOW-FREE precision fan-cooled motor, which operates off 115Vac. Requires external 12Vdc supply, for the electronics. With diagrams.



8-Watt Stereo Amplifier, 8-Track Tape Transport and hook-ups both. **\$19.95**
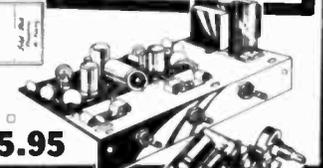
## 8 WATT STEREO AUDIO AMP

The factory "snipped" most of the cables to this compact 8 watt stereo unit with aluminum escutcheon plate. It's easy to use because we have all the cables marked ready to use. With power supply, 115vac, 3 controls, LEFT and RIGHT VOLUME control for two speakers for balancing and center TONE control. With knobs, 7 x 3 1/2 x 3 1/2. Hookup spec sheets.



**\$5.95**

## 4 WATT GUITAR AMP AMPEREX


Musical instrument amplifier at low, low price! Peak power output 10 watts. Two input circuits are equalized for normal or solo guitar. The four controls are VOLUME, TONE, TREMOLO INTENSITY and TREMOLO SPEED. There are terminals on board for normally open foot switch connection. Supply voltage 18Vdc. Output to 8 ohm hi-quality speaker, input impedance 23,000 ohms. Current drain 20 mls. External power supply required. Wt. 1 lb. With instructions, hookups and diagrams. Size 8 x 2 1/2 x 3.



**\$7.95**
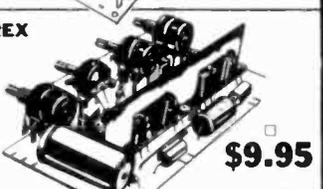
## 8 WATT STEREO AMP AMPEREX

Type PCA-3C-18. Provides 4 watts per channel. May be used as stereo tuner tool! Unit has 4 controls: VOLUME, BALANCE, BASS and TREBLE. Circuitry 3 stage DC coupled amplifier with thermostat for temperature stabilization. Each channel has separate PREAMP. Input imp 1 meg, for use with ceramic or crystal cartridges. Requires external power supply. Supply voltage 18VDC. Outputs to 8 ohm speakers. Freq. response 40 Hz to 30 kHz. Current per channel 340 mls. Size 7 x 3 1/2 x 3 1/2. **SOLID STATE**



**\$9.95**

## \$2.50 DIGITS FOR \$6.

## GIANT SALE ON 3-DIGIT READOUTS

Made by National, their Type NSN-33. With red lens. Multiplied. Three digits size of filter. Driver SN7448, 10 mls. Case only 9/16 x 3/8 x 1/16". 12-pins. For pc boards, or fits into standard IC socket. Includes 300 ohm resistor. Price is lowest we have seen! 100% perfect. Buy all good digits, not rejects as the Hewlett Packard's advertised by others.

- All 6 VDC 250 ohm coil
  - 1/2 x 1/2 x 5/16"
  - when energized 2 pole sets normally open, 2 poles N.C. Reverse the voltage polarity to the opposite takes effect thru built-in "magnet bias".
- Type
- MR2MF-1006
  - MR3MF-1006
  - MR4MF-1006

## "AEROSPACE" BABCOCK & LEACH CRYSTAL CAN RELAYS

All hermetically sealed Submini, 1/8", half, and full crystal can types in 6-12-24V in asst contacts up to 4PDT, 1 amp up to 10 amp, 1000's types. \$12 for 41, 10, 44, 16, 24, etc. **\$3.50**



## FIBER OPTIKS By POLY PAKS

### STAR LITE 3-LEVEL DISPLAY

Only **\$9.95**

- COLORFUL
- 18" HIGH LAMP

First multi-level 115 VAC fiber optic lamp display - in kit form far less than \$10. Colorful acrylic designed base structure. Versatile multi-color disc control changes 125 white lighted fiber tips to a splashing optical array of color. New design eliminates messy adhesives, 12" high. Kit includes: 125 pre-shaped 20-mil plastic fibers, black acrylic base, interlocking designed colorful cylinder, 6-ft. 115 VAC lamp cord, booklet, color disc control, all accessories.

## FILAMENT TRANSFORMERS

Input all 115/60 cycles. Open frame and metal encased.	Output	Sale
<input type="checkbox"/> 5.0V	@ 120A	\$1.00
<input type="checkbox"/> 6.3V	@ 3A	2.95
<input type="checkbox"/> 12.0VCT	@ 3A	2.95
<input type="checkbox"/> 18.0VCT	@ 2A	2.50
<input type="checkbox"/> 150.0V	@ 50MA.	
<input type="checkbox"/> 7.0V	@ 1A*	2.95

\*Nixie tube transf.

## 2 TRANSISTOR AM TUNER

Only **\$3.50**

Includes carefully matched transistors, A high Q lite wire loopstick matches the autodyne converter in stage #1 followed with an IF stage with age control. Audio output comes from transformer coupled detector thru and 2 of filter. Matches any audio amp with 50 mV sens. With 2 gang variable capacitor. Covers 630 to 1620 KHz. Power requirements 9V @ 6 ma. 2 x 4 1/2 x 2 1/2. Use with our Sanken amplifiers, Wt. 8 oz.



**POLY PAKS BLUE RIBBON**

*Policy*

INCLUDES

- 20-Years of Business INTEGRITY
- 20-Years of Money-Back GUARANTEES
- 20-Years of Economy! LOWEST PRICES!

**48-HR. SERVICE**

## CELESTIAL LIGHT KIT

3-LEVEL DISPLAY

Only **\$4.95**

- 1400 multi-color fibers
- 18" high of brittle filtes
- Cordless light source
- Variable color control
- Variable Level Control
- Blinks, Winks, Twinks

Advanced version! SELF-POWERED, multi-tiered fiber optic kit displaying colorful marvels, splashing, shimmering "sprays" of light from 1400 magical fibers, 18" high, includes "BLINK" variable color control (3-pc. kit). Telescopic stem gives instant level control (3 stems). Safe! Educational! Fun! Easy! RE-DO PROCESS to re-make your LIGHTS over again. 16-page booklet. Accessories include: "O" rings, adhesive, 1400 optically perfect glass fibers, 12" long.

Terms add postage. Rated: net 30. Phone Orders: Wakefield, Mass. (617) 246-3829. Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

20c CATALOG on Fiber Optics, IC's, Semi's, Parts. MINIMUM ORDER - \$4.00

## POLY PAKS

P.O. BOX 942R LYNNFIELD, MASS. 01940

# ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

## READER SERVICE CARD NO. PAGE

67	Allison Automotive	89
24	Audio-Amateur	78
	Bell & Howell Schools	82-85
14		
17, 18	B & K Division of Dynascan Corp.	32-70
79	Brooks Radio & TV Corp.	95
28	BSR USA Ltd.	80
88	Castle TV Tuner Service, Inc.	Cover IV
20	Channellock, Inc.	76
16	CIE, Cleveland Institute of Electronics	54-57
19	Continental Specialties Corp.	71
	CREI, Division of the McGraw-Hill Continuing Education Center	36-39
7	Crown International	22
13	Data Precision Corp.	31
8	Delta Products, Inc.	23
63	Digital Concepts	87
65	Edlie Electronics	88
22	Edmund Scientific Co.	108
80	EICO, Electronic Instrument Inc.	96
64	Electronic Distributors, Inc.	97
	EMC, Electronic Measurement Corp.	97
84	Fordham Radio Supply Co.	98
75	GC Electronics	93
71	Grantham School of Electronics	91
	GTE Sylvania Electronic Components	2
100	Heath Co.	28, 29
76	Indiana Home Study Institute	94
61	International Crystal Mfg. Co.	81
83	Instant Service System	98
74	Jensen Tool & Alloy	92
11	Lafayette Radio Electronics	27
62	Leader	87
9	Lectrotech, Inc.	24
86	MTS, Micro-Instrumentation Telemetry Systems, Inc.	99
77	Mountain West Alarm Supply Co.	94
25	National Camera Co.	78
	National Technical Schools	72-75
	NRI Training	8-11
23	Pace, Division of Pathcom, Inc.	78
73	PAIA Electronics	92
81	Projector Recorder Belt Co.	96
1	PTS Electronics	Cover II
5	Radio Shack	13
12	Raytheon Co.	30
	RCA Electronic Components	
	Picture Tubes	14, 15
68	Test Equipment	89
82	Rye Industries	97
6	Sams & Co. Howard W	17
70	Schober Organ	90
87	Shure Bros.	Cover III
21	Southwest Technical Products	77
10	Sprague Products Corp.	25
	Sylvania Technical School Home Study Division	18-21
66	Technical Documentation	88
2, 15	Tektronix, Inc.	1
29	Telematic	80
30	Tri-Star	80
4	Tuner Service Corp.	7
72	TV Tech Specials	92
	Vintage Radio	98
69	Wahl Clipper Corp.	90
26, 27	Weiler-Xcelite Electronics Division	79
3, 85	Winegard Co.	5, 99

## MARKET CENTER

## READER SERVICE CARD NO. PAGE

89	ATV Research Corp.	106
	Babylon Electronics	100
	Baria	102
	Cornell Electronics	100
	Command Productions	100
90	Delta Electronics	104
91	Digi-Key	102
96	Electronics Unlimited	104
	Gregory Electronics Corp.	104
92	International Electronics Unlimited	101
	Lakeside Industries	100
	Lesco Electronics	106
	Logic Newsletter	102
93	Meshna Electronics, John Jr.	100
	Photolum Corp.	100
94	Polypaks	103, 105, 107
	Solid State Sales	106
	Todd	102
95	Valu-Pak	104

# How to make friends and influence history. (Join Us.)



The American Red Cross. The Good Neighbor.

A Member of The American Red Cross

**BUILD A "SPACE-AGE" TV CAMERA!**

ONLY KNOWN SOLID-STATE CAMERA IN KIT FORM! Also available factory assembled. Ideal for experimenters, industry, education, etc. High quality performance backed by over seven years of job and field testing. Fully Guaranteed. Completely self-contained. Connects to any TV set without modification. Easy-to-follow assembly manual. Model XT-1A, Series D complete with vidicon \$189.99. PP anywhere in USA & Canada (less vidicon tube \$116.99pp). Many other kits, parts and plans also available.

PHONE or WRITE for CATALOG... DIAL 402-987-3771

BOX 453-RE **ATV Research** DAKOTA CITY, NEBR. 68731

**A NEW INSTRUMENT TO USE WITH YOUR SCOPE MULTITRACER**

Use with your present Oscilloscope to trace Resistors, Capacitors, Transistors, Diodes, Transistors, Tubes, Triodes, most Semiconductors, IC's, etc. Also shows continuity, in circuit and go/no-go checks. Complete with diagrams and instructions. No internal scope connections. For hobbyist, experimenter, engineer or ham.

ONLY \$19.95—CHECK OR MONEY ORDER W/PAY MORE?

BOX 14, **LESCO ELECTRONICS**, SKOKIE, ILL. 60076

SLA-37 segment LED readouts .77" numbers. 45 M/seg., red or yellow \$7.50

MINIATURE TRIM POTS 5K, 10K, 20K, 25K, 50K, 100K, \$7.5 3/\$2.00

MULTI-TURN TRIM POTS Similar to Bourns 3010 style 3/16" x 5/8" x 1 1/4" 50, 100, 500, 2000, 5000, 10,000 and 20,000 ohms. \$1.50 ea. 3/\$4.00

PRINTED CIRCUIT BOARD 4 1/2" x 6 1/2" single sided fiber glass board, 1/16" thick, unetched \$4.00 ea. 5/\$1.75

NIXIE TUBES Similar to Raytheon 8650 tubes, with socket & data sheet \$2.25 3/\$6.00

NSN 33 — 3 DIGIT LED ARRAY, MAN-3 SIZE (.12") INTERNALLY MULTIPLEXED AND DRIVEN BY 7448. \$1.95 EA.

**VERIPAX PC BOARD** This board is a 1/16" single sided paper epoxy board. 4 1/2" x 6 1/2" (standard veripax). DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with busses for power supply connections. Is also etched for 22 pin connector \$5.25

FLV 100 VISIBLE LED \$5.50  
ME-4 IR LED \$5.50  
MCD-2 OPTO-ISOL \$9.90  
GREEN GAP OSL-16 LED \$9.90  
RED GAP OSL-3 LED \$6.60  
14 PIN DIP SOCKETS \$4.40

10 WATT ZENERS 3.9, 4.7 OR 5.6 V \$7.5 EA  
4 WATT ZENERS 3.9, 5.6, 6.8 OR 12 V \$3.0 EA

**Silicon Power Rectifiers**

PRV	1A	3A	12A	50A
100	.06	.11	.30	.80
200	.07	.16	.35	1.15
400	.09	.20	.50	1.40
600	.11	.25	.70	1.80
800	.15	.35	.90	2.20
000	.20	.45	1.10	2.60

**REGULATED MODULAR POWER SUPPLIES**  
+ 15VDC AT 100 ma, 115VAC INPUT \$19.95  
5VDC AT 1A, 115VAC INPUT \$19.95  
IN 4148 14/\$1.00

Terms: FOB Cambridge Mass. Send check or Money Order. Include Postage. Minimum Order \$3.00

### TRANSISTOR SPECIALS

2N256 PNP GE TO-3	\$ .50
2N404 PNP GE TO-5	4/\$1.00
2N1137B PNP GE TO-3	\$ .95
2N1016A NPN Si TO-82	\$ 1.95
2N2226 NPN Si TO-82	\$ 2.50
MPS3393 NPN Si TO-92	4/\$1.00
2N3866 NPN Si TO-5	\$ .75
2N2369 NPN Si TO-18	5/\$1.00
2N3767 NPN Si TO-66	\$ .70
2N2222 NPN Si TO-18	5/\$1.00
2N3055 NPN Si TO-3	\$ 1.00
2N5296 NPN Si TO-220	\$ .50
2N6109 PNP Si TO-220	\$ .55
2N4898 PNP Si TO-66	\$ .60
MJ2252 NPN Si TO-66	\$ .90
2N3638 PNP Si TO-5	5/\$1.00
2N2218A NPN Si TO-5	4/\$1.00

**CAPACITORS**

6V 30UF TANT. 5/31	\$1.00
20V 4.7UF TANT. 5/31	\$1.00
12V 10UF ELECT. 5/31	\$1.00
50V 100UF ELECT. 5/31	\$1.00
25V 30UF ELECT. 4/31	\$1.00

**MAN-1, RED OR YELLOW LED READOUT \$3.25**

**MAN-3 LED READOUTS \$1.75**

**MAN-4 LED READOUTS \$2.50**

1103 1024 bit RAM	\$6.25
NEC 6003 2048 bit RAM	\$9.50
1101 256 bit RAM	\$2.75
8225 64 bit-write RAM	\$2.75
8223-PROGRAMMABLE ROM	\$6.25

Conductive Elastometer low profile calculator keyboard. A 2 3/4" x 3 1/4" x 1/2" flex key. 19SK-6 keyboard having 0-9, ., x, =, -, +, K + C buttons with off, on switch. \$6.00

**TTL IC SERIES**

74100	50	7474	48
7400	24	7475	80
7401	24	7476	52
7402	24	7480	60
7403	24	7483	110
7404	26	7485	150
7405	26	7486	48
7406	43	7489	300
7407	50	7490	83
7408	27	7491	130
7410	24	7492	85
7411	30	7493	85
7412	45	7495	99
7413	85	7496	95
7416	48	74107	50
7417	48	74121	60
7420	24	74123	100
7422	30	74125	140
7426	30	74126	140
7427	55	74150	115
7430	24	74151	95
7432	30	74153	110
7437	60	74154	165
7438	50	74157	125
7440	24	74163	160
7441	15	74164	205
7442	100	74165	205
7445	115	74173	180
7446	125	74176	180
7448	130	74177	180
7450	24	74181	395
7451	30	74192	150
7472	40	74193	145
7473	48	74195	100
		74451	100

Similar to 8038C IC Voltage controlled oscillator, as featured in Oct. 73 P.E. they have sine, square and triangular outputs good to 1MHz. Two of them can be used to make an FM generator. \$5.95

### C/MOS (DIODE CLAMPED)

74C 02	\$7.75
74C 10	\$6.65
74C 157	\$2.15
74C 165	\$3.50
CD 4001	\$6.65
CD 4002	\$6.65
CD 4009	\$1.50
CD 4010	\$6.65
CD 4011	\$6.65
CD 4012	\$6.65
CD 4013	\$1.60
CD 4016	\$1.25
CD 4022	\$2.25
CD 4023	\$6.65
CD 4025	\$1.50
CD 4027	\$1.35
CD 4030	\$6.65

**Full Wave Bridges**

PRV	2A	6A
200	1.95	1.25
400	1.15	1.50
600	1.35	1.75

5311—CLOCK CHIP 6 DIGIT BCD HOLD COUNT, OUTPUT STROBE \$8.50  
5314—CLOCK CHIP 6 DIGIT HOLD COUNT, OUTPUT STROBE \$8.50  
5316—ALARM CLOCK CHIP \$13.95

2513—64x7x5 CHARACTER GEN \$11.50  
2516—64x6x8 STATIC CHARACTER GEN \$11.50

**SANKEN AUDIO POWER AMPS**  
Si 1010 Y 10 WATTS \$7.95  
Si 1025 E 25 WATTS \$18.88  
Si 1050 E 50 WATTS \$29.95

TIS 73 N FET \$5.50  
2N4891 UJT \$5.50  
ER900 TRIGGER DIODES 4/\$1.00

### LINEAR CIRCUITS

LM 309K 5V 1A REGULATOR	\$1.80
723 — 40 +40V REGULATOR	\$7.75
LM 300H REGULATOR POSITIVE	\$9.90
LM 320 — 5 or —15V REGULATOR	\$1.75
LM 376 — V to 37V POS REG.	\$1.25
741A or 741C OP. AMP.	\$4.1
709C OPER AMP	\$4.1
DUAL 709 DUAL OP. AMP.	\$1.25
101 OPER. AMP., HI PERFORM.	\$7.75
LM 308 OPER. AMP., LOW POWER	\$1.15
301/748 — Hi Per. Op. Amp	\$4.1
536—FET INPUT OPER. AMP.	\$2.90
537—PRECISION OP. AMP.	\$2.50
LM 3900—QUAD OP. AMP.	\$7.75
LM 324—QUAD 741	\$2.20
560—PHASE LOCK LOOP	\$2.95
561—PHASE LOCK LOOP	\$2.95
565—PHASE LOCK LOOP	\$2.95
567—TONE DECODER	\$2.95
703—RF-IF AMP.	\$6.65
LM 370—AGC SQUELCH AMP.	\$1.15
555—2 μs — 2 HR. TIMER	\$1.20
3822—TRANSISTOR ARRAY	\$9.95
LM 380—2W AUDIO AMP.	\$1.75
LM 377—2W STEREO AUDIO AMP	\$3.25
LM 381—STEREO PREAMP	\$1.75
LM 382—DUAL AUDIO PREAMP	\$1.95
LM 311—HI PER. COMPARATOR	\$1.15
LM 319—DUAL HI SPEED COMP.	\$1.50
LM 339—QUAD COMPARATOR	\$1.95

**TRIACS**

PRV	1A	10A	25A	1.5A	6A	35A
100	.40	.70	1.30	.40	.50	1.20
200	.70	1.10	1.75	.60	.70	1.60
400	1.10	1.60	2.60	1.00	2.0	2.20
600	1.70	2.30	3.00			

325 Elm St., Cambridge, Mass.



## SOLID STATE SALES

P.O. BOX 74A  
SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

RELIABLE  
EAST COAST SEMICONDUCTOR  
PRODUCTS

**WITH GLASS ESCUTCHEON**

• 20-watt Solid State Amplifier!  
• All Solid State, Printed Circuitry!  
• Slide Rule Dial!  
• All Purpose, All Family System!

The most unusual HI-FI stereo buy of 1974. A unit that has so many unique and different functions, makes it the finest system of its kind at the usual Poly Pak economy prices. Features: built-in FM antenna, record player jacks on separate panel. Another external panel consists of provisions for "right" and "left" speaker jacks, for external FM ground, jacks for connecting a tape recorder to radio tuner or phono systems to record. Lower inputs for connecting tape deck that will play back thru the internal amplifier for systems. Includes red indicator on front panel for STEREO indicator. Another jack for plugging in a pair of stereo headphones.

Only **\$39.95**

**20-WATT STEREO AM-FM-MULTIPLEX**

Has the following controls on front panel. PHONO-STEREO-AM-FM, MONO, FM STEREO, TAPE, master control switch. LOUDNESS, BALANCE, TREBLE, BASS controls, with power ON-OFF rocker switch. Designed for all audio-phones to use as wall unit in DEN or FAMILY ROOM, or control unit by easy chair in family room, or for those who wish to design their own console or modular system, with 6 ft. 1 1/2 VAC cord and plug. Only 13 x 7 x 3 1/2" plus diagram, Shpg. wt. 3 lbs. With knobs.

**60-WATT AM-FM-MULTIPLEX 2 for \$19.95**

Same as above except amplifier heavy-duty stereo 60 watt unit. **\$59.95**

Same as item 21 except reject parts may be missing.

Brand New OVER 1,000,000-PC INVENTORY

# Inflation-Fighting ECONOMY IC PRICES

Buy 3 or more, 10% discount!

Factory Marked Order by type number! Spec sheets on request "ONLY"

Type	Sale	Buy 100 - Take 20%
SN7400	\$0.24	SN74108 .95
SN7401	.24	SN74112 .95
SN7402	.24	SN74113 .95
SN7403	.24	SN74114 .95
SN7404	.26	SN74121 .61
SN7405	.26	SN74122 .69
SN7406	.45	SN74123 1.05
SN7407	.49	SN74125 1.45
SN7408	.27	SN74126 1.55
SN7410	.24	SN74140 2.50
SN7411	.31	SN74141 1.95
SN7416	.89	SN74145 1.19
SN7420	.24	SN74148 4.50
SN7421	.55	SN74150 1.00
SN7422	.31	SN74151 1.00
SN7423	.50	SN74153 1.39
SN7426	.50	SN74154 1.69
SN7430	.24	SN74155 1.29
		SN74156 1.49
		SN74157 1.45
		SN74158 1.45
		SN74200 2.95

SN74732 .35  
SN74737 .49  
SN74738 .52  
SN74740 .24  
SN74741 1.19  
SN74742 1.12  
SN74743 1.12  
SN74744 1.25  
SN74745 1.19  
SN74746 1.29  
SN74747 1.29  
SN74748 1.35  
SN74749 .49  
SN74750 1.29  
SN74751 1.35  
SN74752 .35  
SN74753 .31  
SN74754 .31  
SN74755 .31  
SN74756 .31  
SN74757 .31  
SN74758 .85  
SN74759 .85  
SN74760 .65  
SN74761 1.25  
SN74762 .99  
SN74763 1.15  
SN74764 .85  
SN74765 1.19  
SN74766 1.19  
SN74767 1.19  
SN74768 1.19  
SN74769 1.19  
SN74770 1.19  
SN74771 1.19  
SN74772 1.19  
SN74773 1.19  
SN74774 1.19  
SN74775 1.19  
SN74776 1.19  
SN74777 1.19  
SN74778 1.19  
SN74779 1.19  
SN74780 1.19  
SN74781 1.19  
SN74782 1.19  
SN74783 1.19  
SN74784 1.19  
SN74785 1.19  
SN74786 1.19  
SN74787 1.19  
SN74788 1.19  
SN74789 1.19  
SN74790 1.19  
SN74791 1.19  
SN74792 1.19  
SN74793 1.19  
SN74794 1.19  
SN74795 1.19  
SN74796 1.19  
SN74797 1.19  
SN74798 1.19  
SN74799 1.19  
SN74800 1.19

"DIP" Packages

**60-WATT STEREO HIGH FIDELITY AMPLIFIER**

Wall "Slim-Line" Type! Tape, Record Player, PA & Musical Instruments!

The most amazing audio offer for the hi-fi-ers, PA men, and an ideal unit for the family den, or any room in the house, office, etc. Comes complete with hookup, escutcheon, and knobs. 5 separate controls: LOUDNESS, BALANCE, TREBLE, BASS, circuits switch for PHONO, TUNER, TAPE, MIKE, AUX. 3 switches for SCRATCH FILTER, HUMBLE FILTER, and POWER ON-OFF with built-in lite 4-output transistors, each 30 watts. Separate accessory mounting panel for 4 speaker attachment, mike and musical instrument jack, tape, tuner, and power jacks. 6-ft. cord set for 115VAC, 60 cycles. Measures only 13 x 7 x 3 1/2" Wt. 3 lbs. With attractive multi-color escutcheon. Made by leading US maker.

Only **\$39.95**

• 20-20,000 Cycles Resp • 4-Channel Spkr. Systems!

**IC'S FOR EXPERIMENTERS**

Money Back Guarantee! Factory Marked **\$1.00**

SN7400	20 for \$1.	SN7490	5 for \$1.
SN7401	20 for \$1.	SN74107	10 for \$1.
SN7402	20 for \$1.	SN74121	10 for \$1.
SN7403	20 for \$1.	SN74123	10 for \$1.
SN7404	20 for \$1.	SN74150	5 for \$1.
SN7405	20 for \$1.	SN74181	5 for \$1.
SN7406	20 for \$1.	SN74189	5 for \$1.
SN7407	20 for \$1.	SN74192	5 for \$1.
SN7408	20 for \$1.	SN74193	5 for \$1.
SN7410	20 for \$1.	SN74199	3 for \$1.
SN7411	20 for \$1.		
SN7416	20 for \$1.		
SN7420	20 for \$1.		
SN7421	20 for \$1.		
SN7422	20 for \$1.		
SN7423	20 for \$1.		
SN7426	20 for \$1.		
SN7430	20 for \$1.		

Includes factory stock rejects & defects, who knows at these prices!

**INTEGRATED CIRCUIT SOCKETS**

Buy Any 10 - 14-Pin, DIP \$45  
Take 10% off - 16-Pin, DIP \$50  
Discount! TO-5, 8 or 10-Pins \$29

14-Pin, Wire Wrap .69c  
16-Pin, Wire Wrap .89c

**NATIONAL READ ONLY MEMORIES**

Buy 3 take 10%  
Order by type number

THREE-QUARTER INCH 4-DIGIT KRONOS Using OPCOA SLA-3H Choose: Red \$54. Green

Type	Description	Sale
MM3501	1024 bit static ROM	\$3.95
MM4213	1024 bit ROM	3.95
MM4220	1024 bit static ROM	3.95
MM4230	2048 bit static ROM	3.95
MM4231	2048 bit static ROM	3.95
MM4232	4096 bit static ROM	3.95
MM4233	4096 bit static ROM	3.95
MM4241	3072 static charac. gen ROM	3.95

**NATIONAL LINEAR OP AMPS**

Buy any 3 - Take 10% (A) TO-5, Dip or mini Dip

LM-300	POS V.R. (super 723) TO-5	\$.91
LM-301	Hi-performance op amp (A)	.91
LM-302	Vol. follower TO-5	.91
LM-305	Pos. Voltage Reg. TO-5	1.19
LM-307	Super 741 op amp (A)	.41
LM-308	Hi-Q full-tye op amp TO-5	1.19
LM-309H	SV Volt-Regulator TO-5	1.19
LM-310	5V Volt. Reg. 1 Amp TO-3	1.25
LM-310	Voltage-Follower TO-5	1.19
LM-311	Hi-perf. Volt. Comp. (A)	1.19
LM-319	Hi-speed Dual Comp. DIP	1.50
LM-320	MINUS 5, 12 or 24V V.R. TO-3	1.50
LM-339	Dual Comparator, DIP	2.50
LM-342	Quad (4 741's) in DIP	2.50
LM-350	Dual peripheral driver	.41
LM-370	AGC Squelch op amp, TO-5	1.19
LM-371	R-F, I-F, op amp	1.25
LM-372	AM-FM 55B I.A.B. TO-5	3.50
LM-374	AM-FM 55 IVAD TO-5	3.50
LM-377	Dual 2-watt audio amp	3.00
LM-380	2-watt audio amplifier TO-5	1.69
LM-381	Low noise dual pre amp DIP	1.95
LM-382	Low noise dual pre amp DIP	1.95
LM-703	RF-IF, op amp, TO-5	1.50
LM-709	Operational amplifier (A)	.36
LM-710	Differential amplifier (A)	.45
LM-711	Dual Differential Amp (A)	.36
LM-741	Vol. Follower, 741C	.45
LM-742	Vol. Follower, 741C	.45
LM-743	Vol. Follower, 741C	.45
LM-748	Freq. adjustable 741C (A)	.44
LM-1303	Stereo pre amp DIP	.95
LM-1304	FM Stereo Multiplexer	1.25
LM-1307	FM Multit. Stereo Dem. DIP	1.91
LM-1308	Differential RF amp	.95
LM-3900	Quad "curtant mirror" amp	.95
LM-4250C	Programmable op amp	2.50
LM-75451	Dual peripheral driver	.44
LM-75453	Dual peripheral driver	.44
LM-75491	Quad neg. driver, LEO (DIP)	1.85
LM-75492	Hex digit driver, 250ma, DIP	1.85

**EXPERIMENTAL op amps**

Money Back Guaranteed!

Type	Sale	Buy 4 for \$1.
300	5 for \$1.	565
301	10 for \$1.	567
307	10 for \$1.	592
308	5 for \$1.	703
309K	4 for \$1.	709
380	3 for \$1.	710
381	3 for \$1.	711
516	5 for \$1.	723
556	4 for \$1.	733
		741

**MALLORY SOLID STATE ALARM 'SONARLERT'**

Only 3 for \$12 **\$4.50**

1000's of circuits where the voltage is 6 to 28 VDC. Responds to 3 milli with a sound output of 70 db. Mounts in 1-9/16" holes in panels up to 1/4" thick. Type SC628 with color-coded leads. 2.8KHz. minus 10° to 85°C. Size: 1 1/2" x 1 1/2"

Never before offered at these low prices. This unique intrusion alarm device may be used for

**LINEAR Op Amps**

FACTORY GUARANTEED

531	Hi slow rate op amp (TO-5)	\$2.50
532	Micro power 741 (TO-5)	2.50
533	Micro power 709 (TO-5)	2.50
536	FET input op amp (TO-5)	2.95
536	Precision 723 voltage reg. (DIP)	1.17
555	Timer 2 u Seconds to 1 hr. (A)	1.25
556	5 Times faster than 741C	2.10
558	Dual 741 (DIP)	1.00
560	Phase lock loops (DIP)	2.95
561	Phase lock loops (DIP)	2.95
562	Phase lock loops (DIP)	2.95
565	Phase lock loops (A)	2.95
567	Tone decoder (A)	2.95
702C	Hi-gradn. DC amp (TO-5)	1.49
704	TV sound IF system	1.50
711C	Dual diff. comp (A)	.33
723C	Voltage regulator (A)	.69
741CV	Freq. comp 709 (Mini DIP)	.44
748C	Freq. adj. 741C (A)	.44
753	Gain Block	1.75
739-739	Dual stereo preamp	1.98
741-741	Dual 741C (TO-5)	.89
PA265	5-Watt voltage regulator	1.00
UM-2300M	Op amp with SCR	1.00
CA3065	Video audio system	1.00
RC4195	Dual 15V Tracking V.R.	2.50
4136	Quad 741's (DIP)	2.50
RC-2556	Dual 555's	2.25
TVR-2000	Super 723, TO-5	\$1.

(A) TO-5 or DIP BUY ANY 3 - TAKE 10%

BRAND NEW LOWEST PRICES

**INDUSTRIAL SPEED CONTROL \$4.95**

A \$30 item from G.E. Model 633A (made for Xerox) that controls home, shop and industrial lighting too! A very elaborate circuit for controlling many electrical and electronic devices. Easily controls speeds of electric drills, brush type motors, etc. 115vac, rated at 1160 watts. With variable speed or dimming control in heavy-duty aluminum case. 3 x 2 1/4 x 2. With diagram and hookups.

**SCRS! TRIACS! QUADRACS!**

10-Amp Power Tab Plastic Units

PRV Sale	50 \$ 7.75
	100 10.95
	200 1.25
	300 1.50
	400 1.98
	500 2.25
	600 2.50

SAME PRICE SALE!

**NEW! TO-3 NATIONAL LM-340 VR's**

Your Choice **\$2.95**

TO-3 Case \* 1 Amp \* POSITIVE VOLTAGE

Type	Volts
LM-340-05	5 v
LM-340-06	6 v
LM-340-08	8 v
LM-340-12	12 v
LM-340-15	15 v
LM-340-18	18 v
LM-340-24	24 v

**GENERAL ELECTRIC 3-WATT AUDIO AMP \$2.50**

Delivers 10 watts continuous, 100 watts peak. With heat sink, micro-mini size, 3 pin, 1/2" x 9" to adv supply. High sensitivity. 8 to 16 ohms.

**SANKEN HYBRID AUDIO POWER AMPS**

Model	Watts	Sale
SI-1010Y	10	\$ 8.88
SI-1025E	25	18.88
SI-1050E	50	29.95

Used extensively in hi-fi systems, tape decks, FM tuners, record players, stereo components, musical instruments, P.A., etc. All amplifiers, flat within 1/2 db from hz to 100,000. Each unit properly heat-sinked, with heavy-duty connecting tie lug connections. Single-ended pushpull output. Power supply required 24VDC. Output to 8 ohms. Order by Stock No.

**20-WATT STEREO AMP**

Featuring solid state circuitry throughout, with printed circuit construction. 10 watts "peak" audio power per channel. Handsome walnut veneer grain with chrome trim escutcheon. With provisions for separate escutcheon mounting items as STEREO HEADPHONES, TREBLE, BASS, BALANCE, VOLUME controls, separate PHONO AND AUXILIARY with separate OFF-ON POWER switches. Chassis size 11 1/2" x 3" x 2". Separate rear plate has right and left speaker phono type jacks, with convenience power outlet for tape of phono and Auxiliary inputs, for using amplifier with tape decks, and other equipment. Separate external cables for stereo phono connections, 6-ft. power cord, separate ON-OFF light indicator, and automatic turntable power plug with handsome set of knobs. Wt. 2 lbs.

**16.95**

**48-HR. SERVICE**

**"MEMORY LANE"**

Buy Any 3 - Take 10%

1101	256 Bit RAM MOS	\$2.50
2513	1024 Bit RAM MOS	6.95
2516	Character Gen. ROM	6.95
7489	Character Gen. ROM	12.50
8223	64 Bit RAM TTL	2.95
8223	Programmable ROM	2.95
MMS220	64 bit read & write RAM	6.50
MMS260	1024 Bit RAM	2.95
MMS262	1024 Bit RAM	6.50
	2048 Bit RAM	9.95

**PLASTIC VOLTAGE REGULATORS**

L-129	5V 600ma	\$2.10
L-130	12V 500ma	2.10
L-131	15V 450ma	2.10

\*TO-136 Package

Terms: add postage - Rated: net 10  
Phone Orders: Wakefield, Mass. (617) 245-3829  
Retail: 18-18 The Garden St. Wakefield, Mass.  
(off Water Street) C.O.D.'S MAY BE PHONED

20c CATALOG Fiber Optics, IC's, Sem's PARTS

MINIMUM ORDER - \$4.00

**POLY PAKS**


P.O. BOX 942R, LYNNFIELD, MASS. 01940

# LIVE IN THE WORLD OF TOMORROW...TODAY!

## A BETTER LIFE STARTS HERE

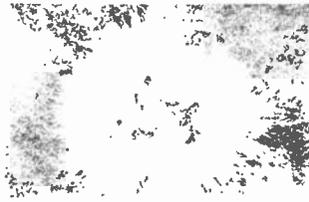
### NEW! KIRLIAN PHOTOGRAPHY KIT!

Experiment in the fascinating new field of "Kirlian" electrophotography — images obtained on film without camera or lens by direct recording of electric charge transmitted by animate & inanimate objects. Each "aura" differs — animate aura said to change corresponding to physical changes. Kit incl. portable darkroom, double transformer isolated from power source; instrs.



Stock No. 71,938EH .....\$49.95 Ppd.  
 "HIGH VOLTAGE PHOTOGRAPHY" by H.S. Dakin  
 No. 9129EH. (60-PG. PPBK BK.) .....\$5.00 Ppd.

### ON-TIME BIOFEEDBACK MONITOR

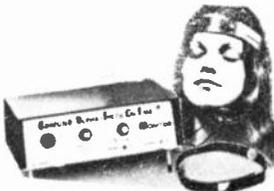

New—measures & records % of time spent producing alpha/theta! Electronic scoring device to observe exact degree of progress in alpha-theta prod'n. for greater relaxation, concentration. Deluxe sensitive instrument gives reliable audio & visual feedback of alpha/theta brainwaves. Tracking time (0-20 min.) of alpha or theta rhythm generated is switch-controlled. Other innovative features incl. artifact inhibitor (no muscle interference). 12 lb.

No. 1652EH . . . (15x10x6") .....\$349.50 Ppd.

### 3-CHANNEL COLOR ORGAN KIT


Easy to build low-cost kit needs no technical knowledge. Completed unit has 3 bands of audio frequencies to modulate 3 independent strings of colored lamps (i.e. "lows"-reds, "middles"-greens, "highs"-blues. Just connect hi-fi, radio, power lamp etc. & plug ea. lamp string into own channel (max. 300w ea.). Kit features 3 neon indicators, color intensity controls, controlled individ SCR circuits; isolation transformer; custom plastic housing; instr.



Stock No. 41,831EH .....\$17.50 Ppd.

(And our FREE CATALOG is packed with exciting and unusual ecological & physical science items—plus 4,500 finds for fun, study or profit . . . for every member of the family.)

### GET A CHARGE FROM THE SUN!

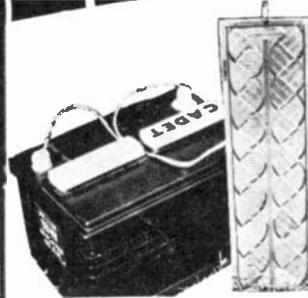

Our 12V Solar Battery Charger allows direct conversion of light-to-electricity. Compact panel put on a boat can automatically charge its 12V battery over entire daylight period. Use anywhere for a trickle charge. Big value, it comprises 30 1/2" silicon solar cells in series w/ diode.

(AB. 30 W-HRS./WK.)  
 No. 71,971EH .....\$89.95 Ppd.  
 9x18" HI CURRENT MODEL (6W, 12V 500MA)  
 (AB. 150 W-HRS./WK)  
 No. 72,010EH .....\$420.00 Ppd.  
 6x6" LO VOLTAGE MODEL (1.5V, .38W, 250 mA)  
 No. 42,172EH .....\$49.95 Ppd.

### PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18-3/4" reflecting shield & 2 I.C.'s in amplifier magnifies signals 100X that of omnidirectional mikes. Catch a songbird 1/2 mile off; QB's huddle strategy; sounds never before heard. Super directivity gives highest signal to noise ratio poss. Safe: auto. cuts off ear damaging noises. Earphones, tape recorder output, tripod socket. Req. two 9v trans. batt. (not incl).



No. 1649EH . . (5-1/2 LB) .....\$299.00 Ppd.  
 BIG EAR "TOY" MODEL #80, 176EH .....\$32.25 Ppd.

### 12v WIND-POWERED GENERATOR



Cheapest continuous source of electricity available! Attach to 12v truck batt. (not incl) and get free electricity from the wind. Needs only 7 mph wind — 15 amps output in 23 mph wind; double the wattour output of ordinary radio chargers. Perfect remote area and alternate energy source. Big 6' propeller

(Albers Air-Foil princ.) turns 200w generator; governor prevents overcharging/action. Price includes packing & shipping.

No 19,189EH . . (10'-145 LB.) .....\$425.00 Ppd.



## MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4,500 UNUSUAL BARGAINS!

Completely new '75 Catalog. Packed with huge selection of telescopes, microscopes, binoculars, magnets, magnifiers, prisms, photo components, ecology and Unique Lighting items, parts, kits, accessories — many hard-to-get surplus bargains. 100's of charts, illustrations. For hobbyists, experimenters, schools, industry.

**EDMUND SCIENTIFIC CO.**  
 300 Edscorp Building, Barrington, N. J. 08007  
 Please rush Free Giant Catalog "EH"

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_ Zip \_\_\_\_\_



## COMPLETE & MAIL WITH CHECK OR M.O.


**EDMUND SCIENTIFIC CO.**  
 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total

PLEASE SEND  GIANT FREE CATALOG "EH" MERCHANDISE TOTAL \$ \_\_\_\_\_  
 ADD HANDLING CHARGE—\$1.00 ON ORDERS UNDER \$5.00; 50¢ ON ORDERS OVER \$5.00



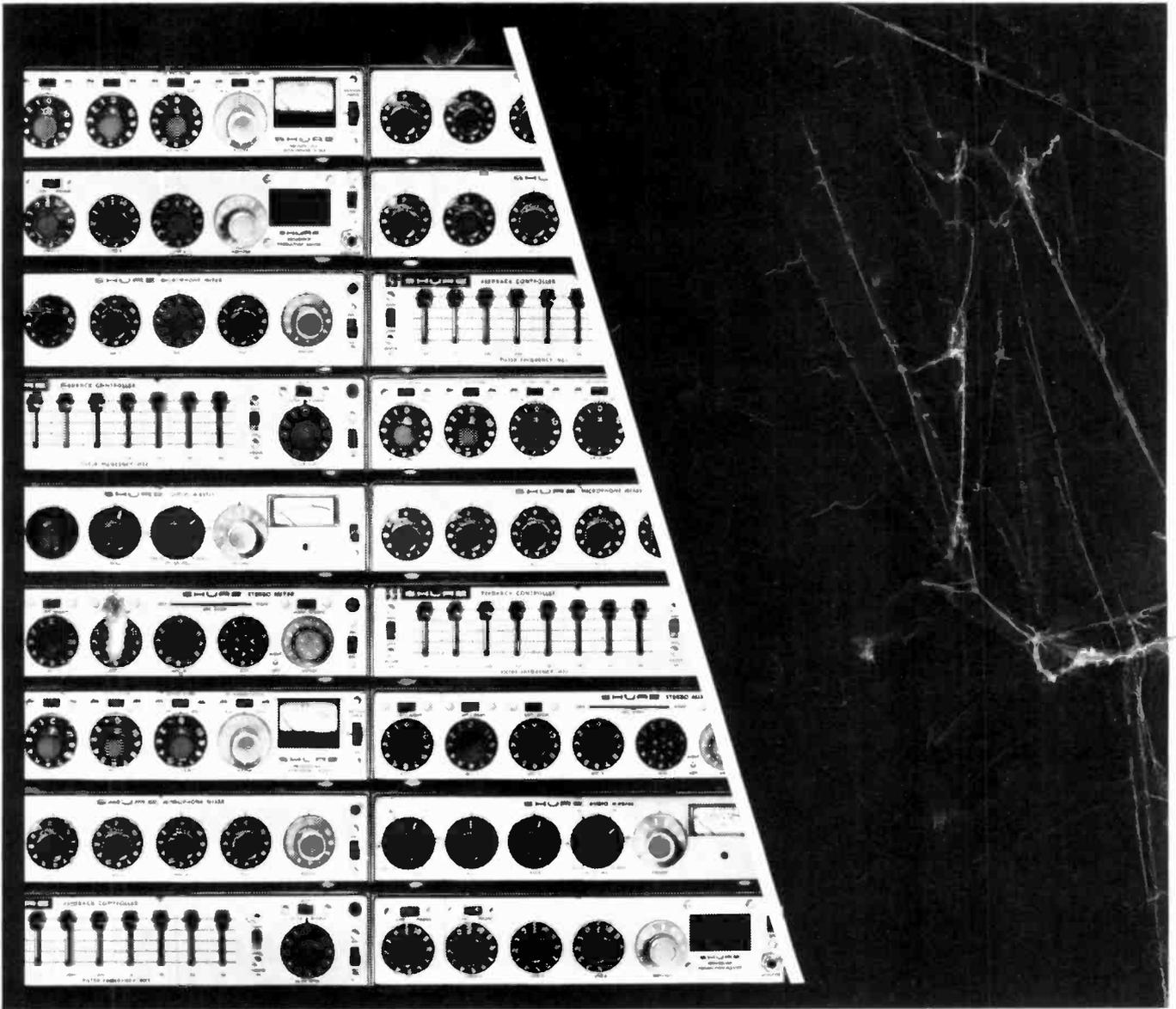I enclose  check  
 money order for \$ \_\_\_\_\_  
 NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



## It's a mod. mod. modular world.



Simplify, simplify! Instead of paying more for bigger, bulkier audio control components, pay less for compact Shure modular components that—singly or in combination—handle critical functions flawlessly. Cases in point: (1) the M67 and M68 *Microphone Mixers*, the original high-performance, low-cost mixers; (2) the M610 *Feedback Controller*, the compact component that permits dramatically increased gain before feedback; (3) the M63 *Audio Master*, that gives almost unlimited response shaping characteristics; (4) the M688 *Stereo Mixer*, for stereo recording and multi-source audio-visual work; (5) the M675 *Broadcast Production Master*, that works with our M67 to create a complete production console (with cuing!) for the cost of conventional consoles; and (6) the SE30 *Gated Compressor/Mixer*, (not shown above) with the memory circuit that eliminates "pumping." For more on how to "go modular," write for the Shure Total Communications Components Catalog No. AL280.

Shure Brothers Inc.  
222 Hartrey Ave., Evanston, Ill. 60204  
In Canada: A. C. Simmonds & Sons, Limited

Circle 87 on reader service card



# **SUBBER**<sup>TM</sup> TV Service Instruments for signal circuit analyzing.



When Castle introduced the TV Tuner SUBBER\* analyzing instrument a couple of years ago it became the first practical way to easily test the VHF tuner, UHF tuner and i.f. amplifier system of any TV receiver. Being lightweight, self contained and battery powered the TV Tuner SUBBER\* Mk. IV is the first such instrument which may be carried on service calls and used with ANY color or black and white TV receiver . . . at \$45.95 for the battery powered Mk. IV, or \$54.95 for the a.c. plus battery powered Mk. IV-A the instruments have been known to pay for themselves in **TIMESAVING** in the first two weeks of use!

Now we have introduced the Mk. V Master SUBBER\*, an instrument which is absolutely unique . . . there is nothing else like it anywhere! It is completely portable and battery powered, practically foolproof in its simplicity of operation when testing ALL the signal stages of any color or black and white TV receiver. The substitution signals available allow tests of the following stages: VHF tuner, UHF tuner, each video i.f. amplifier, video detectors, video amplifiers, 4.5 MHz sound i.f. amplifiers, sound limiter, sound detector and audio amplifier. It includes a signal level meter for testing the antenna signal. Inbuilt telescopic antenna makes the meter adaptable for true field strength measurements. Inbuilt monitor loudspeaker ensures foolproof substitution tests . . . every time!

At \$169.95 the Master SUBBER\* instrument is the best bargain in an analyzer that has ever been available. It will save oodles of time in the hands of a professional troubleshooter . . . and help advance the novice to professional status.

All SUBBER\* instruments come complete with batteries, connecting cables and comprehensive instruction manual. The Master SUBBER\* and Mk. IV-A TV Tuner SUBBER\* come complete with wall plug-in transformer for 120vac 60 Hz operation.

As an added bonus, all SUBBER\* instruments enable use of the high speed agc system analyzing procedure invented by Castle . . . the first practical method for analyzing agc system defects without confusion.

trademark of Castle TV Tuner Service, Inc.



These instruments boast the extra features of all Castle products — advanced technology — modern styling — and they work!

if you need to save some analyzing time . . . you need a SUBBER\* instrument!

See your stocking distributor . . . or write for more details and complete specifications.

**CASTLE TV TUNER SERVICE, INC.**

5715 N. Western Ave., Chicago, Illinois 60645 Phone: (312) 561-6354

In Canada: Len Finkler Ltd., Ontario