

48783

# Radio - ALL ABOUT CELLULAR TELEPHONE

\$2.25 SEPT. 1987  
IN CANADA \$2.75

# Electronics®

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE


**BUILD R-E's VIDEO PALETTE**  
It generates special video effects

**BUILD AN SCA RECEIVER**  
Find hidden signals on the FM band

**SCR's AND TRIACS**  
A circuit cookbook

**R-E ROBOT**  
Put it into action!

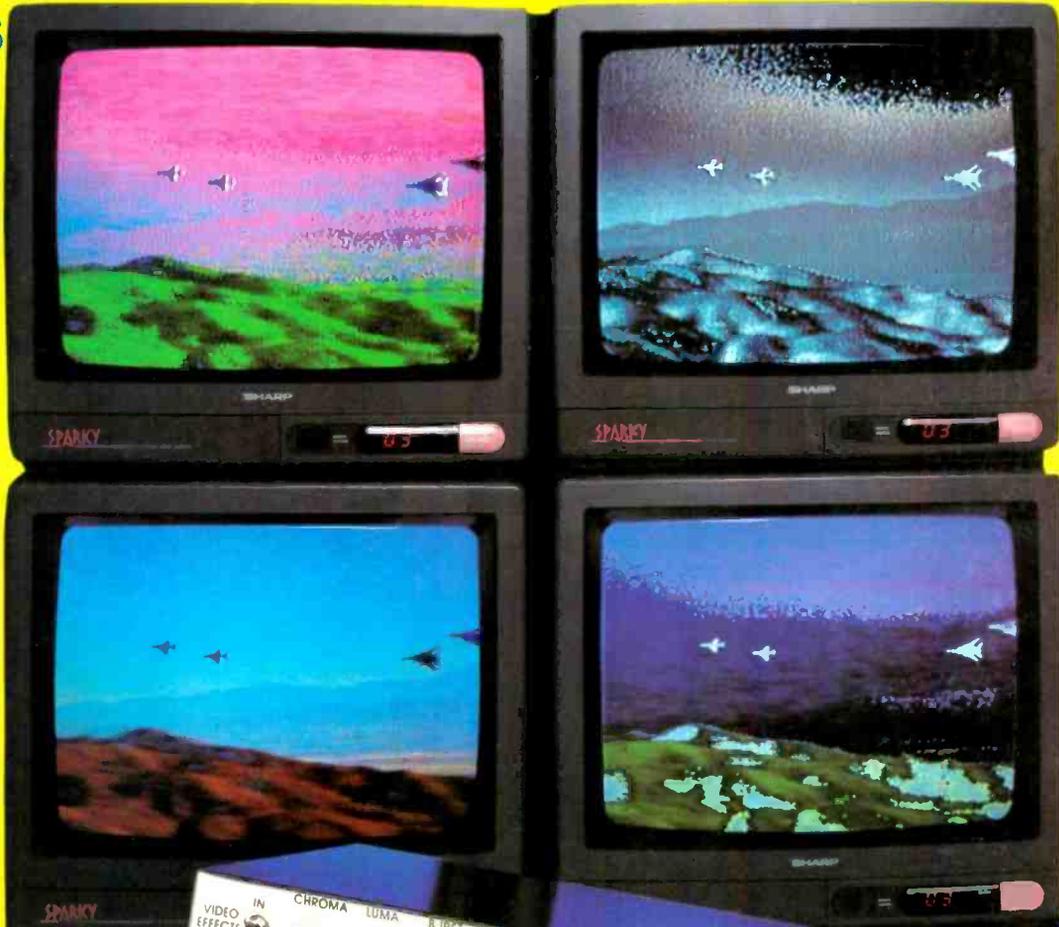**COMPUTER DIGEST**  
Hands-on tests of seven hot portables



**PLUS:**

- ★ Video News
- ★ Satellite TV
- ★ New Products



A  
**GERNSBACK**  
PUBLICATION

# NEW FROM TEK AT JUST \$995!

**Light weight** makes the 2225 easy to carry even to remote servicing sites.


**Fully segmented graticule lines** ease the way for quick, accurate voltage and time measurements.

**Bright, full-size CRT** with minimal geometric distortion and crisp, small spot size delivers sharp trace definition.

**One-button beam finder** locates off-screen signals, even when intensity is turned down.

**Proven design and rugged construction** offer reliability at its best. And the Tek reputation for meeting rigid environmental requirements means confidence in your measurements — and in knowing that this scope is built to last.

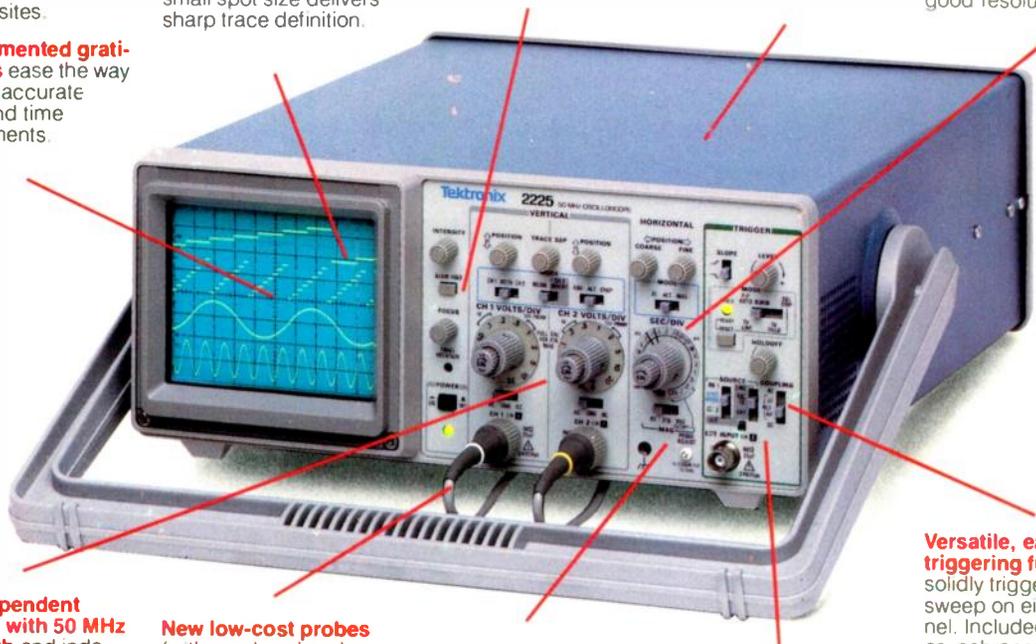**Sweep speeds to 5 ns/div** are fast enough for making accurate pulse and timing measurements on most digital logic families, with good resolution.



**Two independent channels with 50 MHz bandwidth** and independent bandwidth limiting on each channel to 5 MHz, 500  $\mu$ V/div sensitivity for low-level signal measurements and differential applications.

**New low-cost probes** (with nearly unbreakable tips) complement the rugged scope design. Compensation adjustments in the probe body itself eliminate the bulky compensation box at the front panel. Scope and probes are a perfect match!

**Fast, accurate alternate horizontal magnification** lets you choose any of three expansion levels to magnify any part of the normal waveform display — including the trigger point and end of sweep.

**Now for the first time! Two vertical-channel inputs and an external Z-axis input all on the front panel.** An excellent combination for manufacturing test stations and rackmount applications. And at the simple flip of a switch you can trigger on the Z-axis signal.

**Versatile, easy-to-use triggering functions** solidly trigger the sweep on either channel. Included are asynchronous triggering capability; flexible coupling via DC, AC, HF and LF reject filtering; hands-free triggering from virtually any signal; plus independent selection of either TV line or TV field triggering regardless of time-base setting.

**Now, the professional quality and performance you expect from Tektronix... at an unexpected price: \$995 for scope, probes, 3-year warranty and 30-day free trial on approved credit.** No portable in its class can match the Tek 2225 for features, versatility, convenience and value. It's the easy, economical answer to scope needs at bench and field sites, on the manufacturing floor and in the classroom. Call Tek to order, for application assistance or to get the name of your nearest Tek representative or distributor.



Call Tek direct: 1-800-426-2200  
In Oregon, call collect: 627-9000



**Tektronix**  
COMMITTED TO EXCELLENCE

## BUILD THIS

- 41 VIDEO EFFECTS GENERATOR**  
Tailor your video like a pro.  
**Rudolf Graf and William Sheets**
  
- 46 SCA RECEIVER**  
Part 2. Building, aligning, and using the receiver.  
**Rudolf Graf and William Sheets**
  
- 56 R-E ROBOT**  
Part 10. The first application.  
**Steven E. Sarns**
  
- 69 PC SERVICE**  
Direct-etch foil patterns for the SCA receiver.

## TECHNOLOGY


- 53 INSIDE CELLULAR TELEPHONE**  
The inside story on those remarkable mobile telephones.  
**Josef Bernard**

## CIRCUITS AND COMPONENTS


- 61 TESTING SEMICONDUCTORS**  
Part 6. Testing op-amp parameters.  
**TJ Byers**
  
- 64 USING TRIACS AND SCR'S**  
Practical applications for those versatile components  
**Ray Marston**

## DEPARTMENTS

- |  |  |
|--|--|
| <ul style="list-style-type: none"><li><b>6 VIDEO NEWS</b><br/>What's new in this fast-changing field.<br/><b>David Lachenbruch</b></li><br/><li><b>26 EQUIPMENT REPORTS</b><br/>Onkyo Unifer<br/>Universal Remote Control</li><br/><li><b>30 SERVICE CLINIC</b><br/>Troubleshooting the unusual ones.<br/><b>Jack Darr</b></li></ul> | <ul style="list-style-type: none"><li><b>32 NEW IDEAS</b><br/>An audible logic probe</li><br/><li><b>34 DESIGNER'S NOTEBOOK</b><br/>Simple delay circuits<br/><b>Robert Grossblatt</b></li><br/><li><b>87 SATELLITE TV</b><br/>International politics.<br/><b>Bob Cooper, Jr.</b></li><br/><li><b>94 STATE OF SOLID STATE</b><br/>A micropower op-amp<br/><b>Robert F. Scott</b></li></ul> |
|--|--|

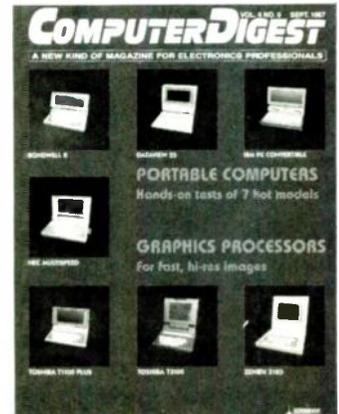

**PAGE 71**

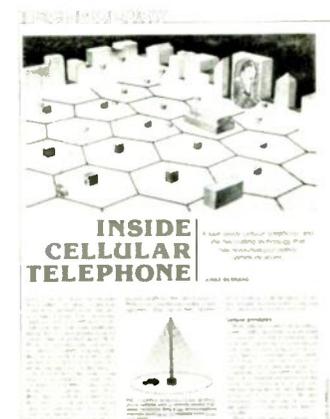

**PAGE 53**

## AND MORE

- 114 Advertising and Sales Offices**
- 114 Advertising Index**
- 115 Free Information Card**
- 16 Letters**
- 95 Market Center**
- 31 New Lit**
- 28 New Products**
- 4 What's News**

## ON THE COVER



If you have ever wanted to take complete control over the appearance of your video productions, this month's cover story is for you. It's a video-effects generator that will let you tailor a signal's tint, color, and brightness to create a custom look or to add special effects such as solarization, and posterization.

Some of the actual effects you can create with the Video Palette are shown on the screens of Sharp's model 3MM67 TV's. Sharp's digital VCR model VC-D75U was used to obtain the excellent still-frame images. We'd like to thank everyone at Sharp Electronics Corporation for their help and cooperation.

## COMING NEXT MONTH

### THE OCTOBER ISSUE IS ON SALE SEPTEMBER 1

#### BUILD THE LASER BUG

This laser receiver let's you use laser light to hear what's going on.

#### BUILD THE VIDEO PALETTE

Part 2 features circuit details, construction, and more.

#### TRIACS AND SCR's

Twenty-eight practical circuits from a zero-voltage line switch to a smart lamp-dimmer.

#### HOW TO SERVICE SWITCHING POWER SUPPLIES

A practical guide.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

**RADIO-ELECTRONICS, (ISSN 0033-7862) September 1987.** Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735 Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$16.97, Canada \$22.97, all other countries \$25.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$1.95. © 1987 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**POSTMASTER:** Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

## Radio-Electronics®

Hugo Gernsback (1884-1967) founder  
M. Harvey Gernsback,  
editor-in-chief, emeritus

Larry Steckler, EHF, CET,  
editor-in-chief  
and publisher

#### EDITORIAL DEPARTMENT

Art Kleiman, editorial director  
Brian C. Fenton, managing editor  
Carl Laron, WB2SLR, associate editor  
Jeffrey K. Holtzman,  
assistant technical editor  
Robert A. Young, assistant editor  
Julian S. Martin, editorial associate  
Byron G. Wels, editorial associate  
M. Harvey Gernsback,  
contributing editor  
Jack Darr, CET, service editor  
Robert F. Scott,  
semiconductor editor  
Herb Friedman,  
communications editor  
Bob Cooper, Jr., satellite-TV editor  
Robert Grossblatt, circuits editor  
Larry Klein, audio editor  
David Lachenbruch,  
contributing editor  
Richard D. Fitch,  
contributing editor  
Teri Scaduto, editorial assistant

#### PRODUCTION DEPARTMENT

Ruby M. Yee, production director  
Robert A. W. Lowndes,  
editorial production  
Andre Duzant, technical illustrator  
Karen Tucker, advertising production  
Marcella Amoroso, production traffic

#### CIRCULATION DEPARTMENT

Jacqueline P. Cheeseboro,  
circulation director  
Wendy Alanko,  
circulation analyst  
Theresa Lombardo,  
circulation assistant

Typography by Mates Graphics  
Cover Foto by Nick Koudis

Radio-Electronics is indexed in  
*Applied Science & Technology Index*  
and *Readers Guide to Periodical Literature*.

Microfilm & Microfiche editions are  
available. Contact circulation department  
for details.

Advertising Sales Offices listed  
on page 114.





#### \$75 DMM MEASURES CAPACITANCE, TRANSISTOR HFE, MORE...

B&K-PRECISION'S new 2905 is a more-than-full-feature 3½ digit DMM, at a surprisingly low price. Features include 0.5% VDC accuracy; 100 µV, 0.1 µA, 0.1 Ω, resolution. Measures capacitance to 20mF with up to 1pF resolution. Audible continuity and diode junction tests are built in. For field survivability, it features a drop resistant case, reverse polarity and overload protection and high-energy fusing. Contact: B&K-PRECISION, 6460 W. Cortland Street, Chicago, IL 60635 (312) 889-9087.

B&K-PRECISION'S new 2905 is a more-than-full-feature 3½ digit DMM, at a surprisingly low price. Features include 0.5% VDC accuracy; 100 µV, 0.1 µA, 0.1 Ω, resolution. Measures capacitance to 20mF with up to 1pF resolution. Audible continuity and diode junction tests are built in. For field survivability, it features a drop resistant case, reverse polarity and overload protection and high-energy fusing. Contact: B&K-PRECISION, 6460 W. Cortland Street, Chicago, IL 60635 (312) 889-9087.

*RT Check out these features + prices. WOW! FL*

#### 4½ DIGIT TRMS DMM READS FREQUENCY AND TEMPERATURE

The new 2945 is well suited for both the analog and digital worlds. DCV accuracy is 0.05%, with 10µV, 10nA, 0.01Ω resolution. Data hold freezes voltage and current readings. °C and °F temperature readings are from -20° to +1000°C frequency from 20 Hz to 200kHz. AC voltage and current are read in true RMS. Also checks continuity and diodes. \$250.00 Contact: B&K-PRECISION, 6460 W. Cortland Street, Chicago, IL 60635 (312) 889-9087.



#### FREQUENCY COUNTER AND DATA HOLD HIGHLIGHT NEW 4½ DIGIT DMM

For engineers in need of a high-accuracy 4½ digit DMM and a low range frequency counter the 2940 is made to order. DC voltage accuracy is 0.05%. Resolution is 10µV, 10nA, and 0.01Ω. Frequency measurements span from 20Hz to 200kHz with up to 1Hz resolution. The 2940 features a drop resistant case with full internal circuitry protection. \$155.00 Contact: B&K-PRECISION, 6460 W. Cortland Street, Chicago, IL 60635 (312) 889-9087.



#### HAND-HELD TEST BENCH READS VOLTAGE, RESISTANCE, CURRENT, HFE TEMPERATURE AND LOGIC.

The new 2906 3½ digit DMM from B&K-PRECISION is virtually a hand-held test bench, with a remarkable range of functions. °C and °F temperature measurements cover from -20C to 1000°C. The logic capability is ready for TTL and CMOS circuits. Other features include drop resistant case, reverse polarity and overload protection; plus high-energy fusing. DC accuracy, 0.25% VDC. \$95.00 Contact: B&K-PRECISION, 6460 W. Cortland Street, Chicago, IL 60635 (312) 889-9087.



#### TRUE RMS DMM OFFERS PEAK HOLD, CAPACITANCE, AND LOGIC

3½ digit true RMS handheld DMM featuring 0.1% DC accuracy. Housed in an ergonomic, drop-resistant case, the 2907 offers many functions and a low price. Resolution is 100µV, 0.1µA and 0.1Ω. Capacitance to 20µF with 1pF resolution. Peak hold feature freezes transient readings. Fully protected. Also checks logic, continuity and diodes. \$190. Contact: B&K-PRECISION, 6460 W. Cortland Street, Chicago, IL 60635 (312) 889-9087.



# THE BEST DMM BUY? NOW IT'S B&K-PRECISION

- ✓ Better specs
- ✓ Lower prices
- ✓ More features
- ✓ More capabilities
- ✓ More circuit and safety protection
- ✓ Ruggedized case with safety test leads

Five all-new models step ahead of the competition with better specs and higher performance per dollar. We've also packed more features than ever into every model.

All five instruments measure voltage, current and resistance, check continuity and diodes, and feature a new ergonomic case with angled LCD readout. Depending on model, additional capabilities include logic level, capacitance measurement, transistor gain, true RMS, frequency measurement, high-current measurement, data hold, peak hold and even temperature.

Like all B&K-PRECISION instruments, these new meters are made for the real world. They offer a drop-resistant case and the triple protection of reverse polarity protection, overload protection, and high-energy fusing.

Best of all, the B&K-PRECISION DMM you want is already in stock at your local distributor. Call today for full details.



**BK PRECISION**  
DYNASCAN CORPORATION

6460 West Cortland St. • Chicago, IL 60635 • 312-889-9087

International Sales: 6460 W. Cortland St., Chicago, IL 60635

Canadian Sales: Atlas Electronics, Ontario

South and Central American Sales: Empire Exporters, Plainview, NY 11803

# WHAT'S NEWS

## New chips to have more accurate spacing

Using a new technique known as mask-proximity correction, researchers at General Electric have made it possible for exposure systems that now can make chips with structures as small as 1.5 microns to be used for making next-generation devices with structures as small as 0.7 micron.

The new technique will greatly extend the effectiveness and hence the useful life of the million-dollar-plus optical lithography systems used in chip patterning.

The main problem experienced when pushing present-generation optical-exposure systems to make chips with sub-micron structures is that of proximity effects. Light from the exposure systems diffracts as it passes through the tiny openings in the masks. Because of

that, areas of dense patterning tend to be underexposed. To compensate, exposure times must be lengthened, but doing that overexposes the isolated features, causing them to be undersized.

GE's proximity-correction technique solves the problem by causing the features on the masks to be enlarged slightly in isolated areas of patterning. A special software routine analyzes the spacing between features and then causes selected dimensions in the masks to be enlarged.

The routine can specify a continuous correction range, from none, for the most dense areas, to heavy, for the most isolated features. Then when exposed, isolated features can be brought to within 0.05 micron of the target width.



A GE RESEARCH PHYSICIST, Dr. Yoav Nissan-Cohen, examines a computer-generated plot of a 0.8-micron chip, the first to be fabricated using mask-proximity correction.

## Spray painting solves problems of brittle superconductors

Scientists at IBM's Research Center at Yorktown Heights, NY report that they have found a way to circumvent the problem of brittleness in the new ceramic superconductor materials.

The IBM scientist's solution is to use a plasma-spraying technique—heating the material until it is ionized, then spraying it on a suitable surface and cooling it. After annealing, the painted surface is again completely superconductive at 68 degrees Kelvin. The researchers have even coated preformed wires, and painting traces like those found in printed circuitry is comparatively simple.

## New optoelectronic chip increases speed 10 times

Honeywell has developed an integrated GaAs monolithic receiver chip with a density speed about 10 times faster than that of any presently known circuit. The new chip contains a photodetector and 200 gates on the same GaAs substrate. It was demonstrated at 1-gigabit clock frequencies.

Measuring about  $2 \times 2$  cm, the chip contains an optical detector, preamplifier circuit, and 1:4 demultiplexer. It was designed to decode a 1-gigabit optical signal input into four parallel 250-megabit electrical outputs. Its high data rates make the chip particularly useful for optical interconnects between computer chips.

That second-generation device is compatible with current manufacturing processes using direct ion implantation and metal organic vapor deposition for epitaxial growth. It provides greater power and capability than earlier devices because of its greater complexity and true integration of gallium-arsenide microelectronics and optical components.

# TEST EQUIPMENT THAT MEASURES UP TO YOUR SPECIFICATIONS



**DMM-300 \$79.95**  
5 DIGIT DMM / MULTITESTER

Our best model. A highly accurate, full function DMM loaded with many extra features. Audible continuity, capacitance, transistors, temperature and conductance all in one hand-held meter. Temperature probe, test leads and battery included.

- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mv — 1000v, 5 ranges
- AC voltage: 200mv — 750v, 5 ranges
- Resistance: 200 ohms — 20M ohms, 6 ranges
- AC/DC current: 200uA — 10A, 6 ranges
- Capacitance: 2000pf — 20uf, 3 ranges
- Transistor tester: hFE test, NPN, PNP
- Temperature tester: 0° — 2000° F
- Conductance: 200ohms
- Fully over-load protected
- Input impedance: 10M ohm



**DMM-200 \$49.95**  
3.5 DIGIT FULL FUNCTION DMM

High accuracy, 20 amp current capability and many range settings make this model ideal for serious bench or field work. Tilt stand for hands-free operation. 2000 hour battery life with standard 9v cell. Probes and battery included.

- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mv — 1000v, 5 ranges
- AC voltage: 200mv — 750v, 5 ranges
- Resistance: 200 ohms — 20M ohms, 6 ranges
- AC/DC current: 200uA — 20A, 6 ranges
- Fully over-load protected
- Input impedance: 10M ohm
- 180 x 86 x 37mm, weighs 320 grams



**DMM-700 \$49.95**  
3.5 DIGIT AUTORANGING DMM

Autorange convenience or fully manual operation. Selectable LO OHM mode permits accurate in-circuit resistance measurements involving semi-conductor junctions. MEM mode for measurements relative to a specific reading. Probes and battery included.


- Basic DC accuracy: plus or minus 0.5%
- DC voltage: 200mv — 1000v, autoranging or 5 manual ranges
- AC voltage: 2v — 750v, autoranging or 4 manual ranges
- Resistance: 200 ohms — 20M ohms, autoranging
- AC/DC current: 20mA — 10A, 2 ranges
- Fully over-load protected
- Audible continuity tester
- Input impedance: 10M ohm
- 150 x 75 x 34mm, weighs 230 grams



**DMM-100 \$29.95**  
3.5 DIGIT POCKET SIZE DMM

Shirt-pocket portability with no compromise in features or accuracy. Large, easy to read .5" LCD display. 2000 hour battery life with standard 9v cell provides over two years of average use. Probes and battery included.

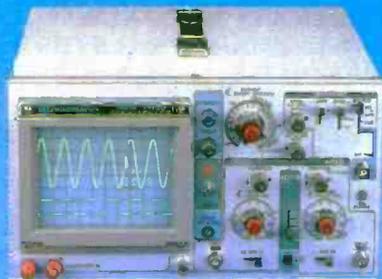- Basic DC accuracy: plus or minus 0.5%
- DC voltage: 2v — 1000v, 4 ranges
- AC voltage: 200v — 750v, 2 ranges
- Resistance: 2k ohms — 2M ohms, 4 ranges
- DC current: 2mA — 2A, 4 ranges
- Fully over load protected
- Input impedance: 10M ohm
- 130 x 75 x 28mm, weighs 195 grams



**MODEL 2000 \$349.95**  
20 MHz DUAL TRACE OSCILLOSCOPE

Model 2000 combines useful features and exacting quality. Frequency, calculation and phase measurement are quick and easy in the X-Y Mode. Service technicians will appreciate the TV Sync circuitry for viewing TV-V and TV-H as well as accurate synchronization of the Video Signal, Blanking Pedestals, VITS and Vertical/Horizontal sync pulses.

- Lab quality compensated 10X probes included
- Built-in component tester
- 110/220 Volt operation
- X-Y operation • Bright 5" CRT • TV Sync filter



**MODEL 3500 \$499.95**  
35 MHz DUAL TRACE OSCILLOSCOPE

Wide bandwidth and exceptional 1mV/DIV sensitivity make the Model 3500 a powerful diagnostic tool for engineers or technicians. Delayed triggering allows any portion of a waveform to be isolated and expanded for closer inspection. Variable Holdoff makes possible the stable viewing of complex waveforms.

- Lab quality compensated 10X probes included
- Delayed and single sweep modes
- Z Axis intensity modulation
- X-Y operation • Bright 5" CRT • TV Sync filter



**DPM-1000 \$54.95**  
3.5 DIGIT PROBE TYPE DMM

Autoranging, pen style design for the ultimate in portability and ease of use. Custom 80 pin LSI chip increases reliability. Audible continuity tester and data hold feature for added convenience. Case, test leads and batteries included.

- Basic DC accuracy: plus or minus 1%
- DC voltage: 2v — 500v, autoranging
- AC voltage: 2v — 500v, autoranging
- Resistance: 2k ohms — 2M ohms, autoranging
- Fully over-load protected
- Input impedance: 11M ohm
- 162 x 28 x 17mm, weighs 75 grams

**2 YEAR WARRANTY ON ALL MODELS**



**JDR INSTRUMENTS**  
110 Knowles Drive, Los Gatos, CA 95030  
(408) 866-6200 • FAX (408) 378-8927 • Telex 171-110

**ORDER TOLL FREE 800-538-5000**

OR VISIT OUR RETAIL STORE  
1256 SOUTH BASCOM AVE.  
SAN JOSE, CA. (408) 947-8881  
CIRCLE 59 ON FREE INFORMATION CARD

COPYRIGHT 1986 JDR MICRODEVICES  
THE JDR INSTRUMENTS LOGO IS A REGISTERED TRADEMARK OF JDR MICRODEVICES.  
JDR INSTRUMENTS IS A TRADEMARK OF JDR MICRODEVICES.

---

---

# VIDEO NEWS



DAVID LACHENBRUCH,  
CONTRIBUTING EDITOR

● **Video numbers.** As of June 1, 98% of all U.S. households had TV sets of some type. Breaking that figure down further, a color TV-set could be found in 93% of all U.S. households, projection TV-sets in 4%, LCD TV-sets in 2%, and some 7% of all U.S. households owned color TV-sets with multichannel (stereo) sound. Also, VCR's could be found in 45% of U.S. homes, camcorders in 3%, and 36% owned pre-recorded videocassettes.

Those estimates are from EIA, which also forecast that 18,300,000 color TV-sets will be sold this year. Of those, 4,300,000 will be stereo and 325,000 will be projection sets. Americans will also buy 13,725,000 VCR's, of which 12,000,000 will be table-model decks and 1,600,000 will be camcorders. Of the total VCR sales, the EIA predicts 2,500,000 will be equipped to receive and record stereo TV.

● **CD-Video Bows.** The CD has now formally been introduced in video form. Compact Disc-Video (or CDV, as it's expected to become known) has now been embraced by a sizeable number of hardware manufacturers, record companies, and movie firms. Although the audio CD is a digital medium, the visual part of the CDV is analog and uses the same record and playback principles as the *Laservision* videodisc.

The little 4<sup>3</sup>/<sub>4</sub>-inch CDV disc—the same size as an audio CD, but distinguished by its gold color—carries five minutes of video and up to 20 minutes of audio. The principal proponent of CDV, Phillips, has proposed changing the name of all *Laservision* players and discs to Compact Disc-Video, and several manufacturers have agreed to make players that will accommodate 4<sup>3</sup>/<sub>4</sub>-inch CDV's and audio-CD's, as well as 4<sup>3</sup>/<sub>4</sub>-, 8-, and 12-inch *Laservision* discs. Also in the works are mini-players that will play only the smaller discs; a little further down the line are possible CDV "boomboxes", portable audio-video systems with LCD displays.

Sales of CDV players and discs are scheduled to start this year. Many hardware and software manufacturers are standing aside for now, watching very closely to see if it is possible to

reincarnate the optical videodisc as a mass-market item via the magic of Compact Disc.

● **Super-VHS bargains.** When the first SVHS (Super-VHS) recorder was announced by JVC in Japan, the suggested list price was set at more than \$1,500, based on the yen-to-dollar exchange rate at the time. That led to speculation that the price of an SVHS recorder in the United States would be about \$2,000, effectively pricing the new medium out of the market. But consumer-electronics pricing can be full of surprises, and when Hitachi announced the first SVHS recorder for the American market, it was priced at about \$1,300. When JVC unveiled its model, it carried a U.S. suggested list price of just under \$1,200, although essentially the same model bore a list price of about \$1,550 in Japan. Facing that pricing challenge, other manufacturers are quoting \$1,100 for their units for the American market. Therefore, even before the first SVHS had reached the market in the U.S., prices had already come down by almost one-half.

By press time, SVHS decks had been announced for sale this year by Hitachi, JVC, Magnavox, Mitsubishi, Panasonic, Quasar, RCA, Sharp, Toshiba, and Zenith. JVC forecast that SVHS would soon replace standard VHS, but most other manufacturers disagree, arguing that there would be dual standards for some time to come.

One of the problems of SVHS currently is the lack of pre-recorded cassettes. Because cassettes recorded in the SVHS mode can't be played on standard VHS recorders (although VHS cassettes can be played on SVHS recorders), it will be some time before pre-recorded cassette makers will be willing to release much pre-recorded material in the new high-resolution format.

On another front, there is surprising interest in SVHS in the industrial and broadcast fields. Both JVC and Panasonic are preparing industrial models of SVHS, and there are forecasts that the new system could take over from the standard <sup>3</sup>/<sub>4</sub>-inch U-matic format in industrial video. And it is also felt that the format has potential for use in broadcast newsgathering.

R-E

# MAKE MONEY



# IN ELECTRONICS


You say you're *already* trained in electronics but that you're *not* making enough money??? Well then, maybe you don't have an accredited bachelor's degree to prove that your education is *up to snuff!* Check out the Grantham Independent-Study B. S. Degree Program. It could make a *dollars and sense* difference in your electronics career.

Grantham offers this program, complete but without laboratory, to electronics technicians whose objectives are to upgrade their level of technical employment. Since the field of electronics is so enormous, opportunity for advancement is always present. Promotions and natural turnover make desirable positions available to the man who is ready to *move up*.

**Grantham College of Engineering**  
10570 Humbolt Street  
Los Alamitos, California, 90720

**This booklet  
FREE!**

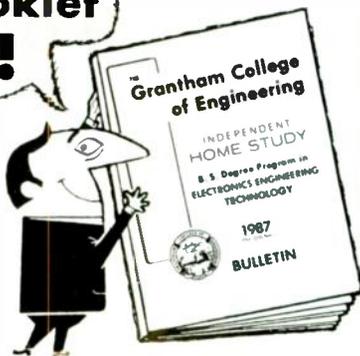This free booklet explains the Grantham B.S. Degree Program, offered by independent study to those who work in electronics.



for **FREE**  
**Booklet**  
**CLIP**  
**COUPON**  
and mail in  
envelope or  
paste on  
postal  
card.

## *Do You REALLY Want to Make More Money?*

Yes it does take *work* and a few sacrifices to climb up the electronics ladder to where the bigger money is. But, if that's where you want to be, then that's what you must do — *work* harder at learning and getting the right credentials, even if it takes a few sacrifices. A *B. S. degree* and the knowledge that rightly goes along with it can give you powerful ladder-climbing equipment in your search for *success in electronics*.

The accredited Grantham non-traditional B.S. Degree Program is intended for mature, fully-employed workers who want to upgrade their electronics careers.

## *Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through Independent Home Study*

Study materials, carefully written by the Grantham College staff for independent study at home, are supplied by the College. Your technical questions related to these materials and the lesson tests are promptly answered by the Grantham home-study teaching staff.

## *Recognition and Quality Assurance*

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council, as a degree-granting institution.

All lessons and other study materials, as well as communications between the college and students, are in the English language. However, we have students in many foreign countries; about 80% of our students live in the United States of America.


**Grantham College of Engineering** R-9-87  
10570 Humbolt Street, Los Alamitos, CA 90720

Please mail me your free catalog which explains your B.S. Degree independent-study program.


Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

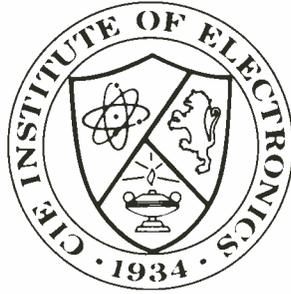City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



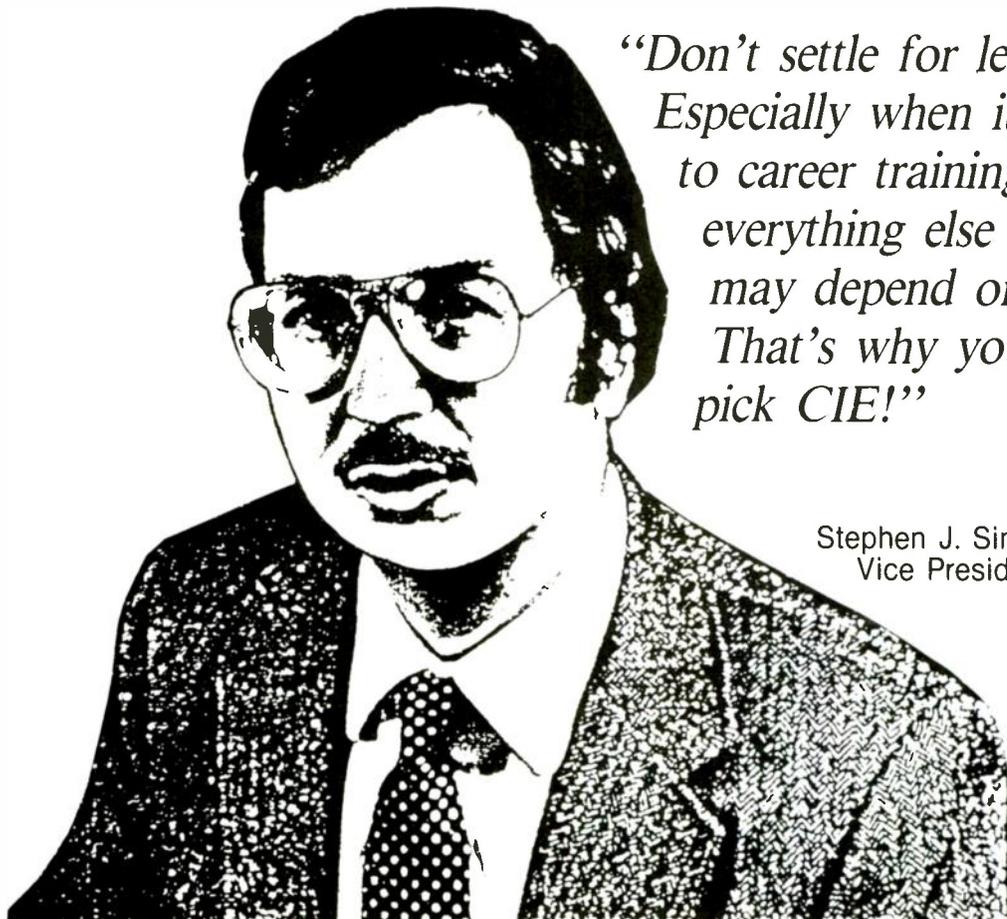“If you’re going to learn electronics, you might as well learn it right!”



*“Don’t settle for less.  
Especially when it comes  
to career training...because  
everything else in your life  
may depend on it.  
That’s why you ought to  
pick CIE!”*

Stephen J. Simcic  
Vice President, Academic Affairs

**Y**ou've probably seen advertisements from other electronic schools. Maybe you think they're all the same. They're not!

CIE is the largest independent home study school in the world that specializes exclusively in electronics.

### Meet the Electronics Specialists.

When you pick an electronics school, you're getting ready to invest some time and money. And your whole future depends on the education you get in return.

That's why it makes so much sense to go with number one . . . with the specialists . . . with CIE!

### There's no such thing as bargain education.

If you talk with some of our graduates, chances are you'd find a lot of them shopped around for their training. Not for the lowest priced but for the best. They pretty much knew what was available when they picked CIE as number one.

We don't promise you the moon. We do promise you a proven way to build valuable career skills. The CIE faculty and staff are dedicated to that. When you graduate, your diploma shows employers you know what you're about. Today, it's pretty hard to put a price on that.

### Because we're specialists we have to stay ahead.

At CIE, we've got a position of leadership to maintain. Here are some of the ways we hang onto it . . .

### Programmed Learning

That's exactly what happens with CIE's Auto-Programmed Lessons. Each lesson uses famous "programmed learning" methods to teach you important principles. You explore them, master them completely, before you start to apply them. You thoroughly understand each step before you go on to the next. You learn at your own pace.

And, beyond theory, some courses come fully equipped with electronics gear (the things you see in technical magazines) to actually let you perform hundreds of "hands-on" experiments.

### Experienced specialists work closely with you.


Even though you study at home, you are not alone! Each time you return a completed lesson, you can be sure it will be reviewed, graded, and returned with appropriate instructional help. When you need additional individual help, you get it fast and in writing from the faculty technical specialist best qualified to answer your question in terms you can understand.

### Pick the pace that's right for you.

CIE understands people need to learn at their own pace. There's no pressure to keep up . . . no slow learners hold you back. If you're a beginner, you start with the basics. If you already know some electronics, you move ahead to your own level.
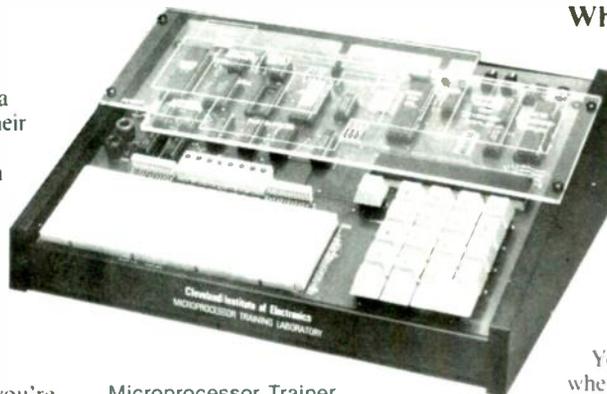
### Enjoy the promptness of CIE's "same day" grading cycle.

When we receive your lesson before noon Monday through Saturday, we grade it and mail it back the same day. You find out quickly how well you're doing!



Microprocessor Trainer

### State-of-the-art Laboratory Equipment

Some courses feature the CIE Microprocessor Training Laboratory. An integral part of computers, microprocessor technology is used in many phases of business, including service and manufacturing industries.

The MTL gives you the opportunity to program it and interface it with LED displays, memory devices, and switches. You'll gain all the practical experience needed to work with state-of-the-art equipment of today and tomorrow.

### CIE offers you an Associate Degree.

One of the best credentials you can have in electronics — or any other career field — is a college degree. That's why CIE gives you the opportunity to earn an Associate in Applied Science in Electronics Engineering Technology. Any CIE career course can offer you credit toward the degree — more than half of the number needed in some cases.

*"Cleveland Institute of Electronics is the only accredited institution of higher learning offering an Associate Degree program with tuition based on actual study time used. The faster you complete your degree assignments, the less your overall tuition."*

Steve Simcic  
Vice-President Academic Affairs

### Which CIE Training fits you?

Beginner? Intermediate? Advanced? CIE home study courses are designed for ambitious people at all entry levels. People who may have:

1. No previous electronics knowledge, but do have an interest in it;
2. Some basic knowledge or experience in electronics;
3. In-depth working experience or prior training in electronics.

You can start where you fit and fit where you start, then go on from there to your Diploma, Associate Degree, and career.

### Today is the day. Send now.

Fill in and return the postage-free card attached. If some ambitious person has removed it, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail in the coupon below or, if you prefer, call toll-free 1-800-321-2155 (in Ohio, 1-800-523-9109).

CIE

**Cleveland Institute of Electronics, Inc.**  
 1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

ARE-68

YES...I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program... plus my FREE package of home study information.

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_/\_\_\_\_\_


Check box for G.I. Bill bulletin on Educational Benefits:  Veteran  Active Duty

**MAIL TODAY!**


**CIRCLE 60 ON FREE INFORMATION CARD**




Components and Adaptors

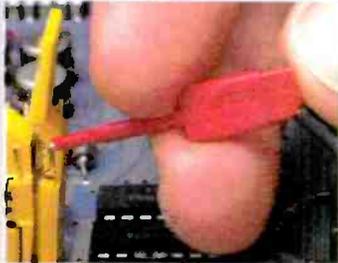



P-2E Plug-On Pico Hook

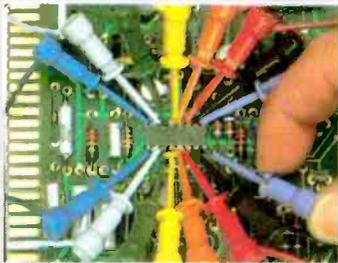

Micro-Hook

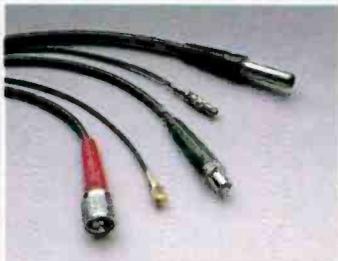

Coax Cable/Patch Cord Assemblies

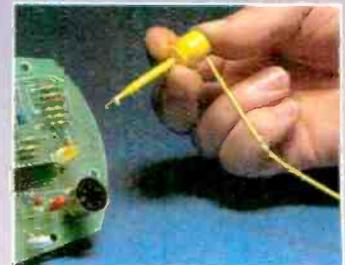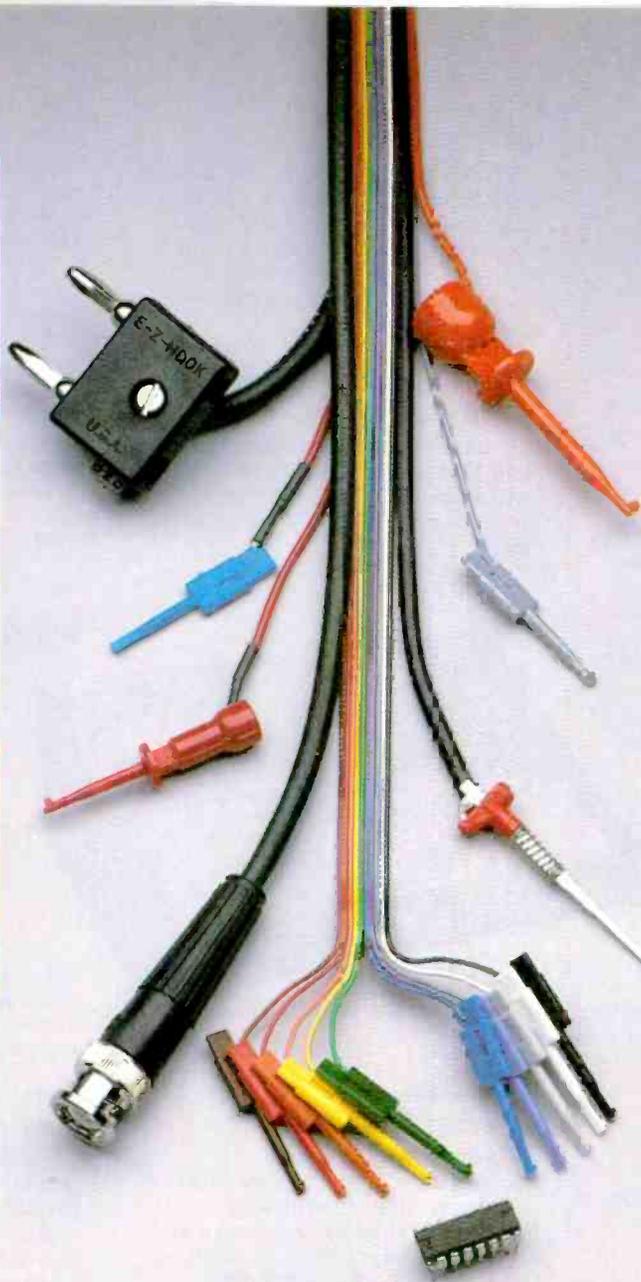


MP-I-Hook Test Leads



Pico-Hook, Narrow IC



Nail-Clip, Harnessing

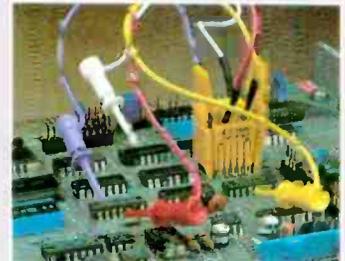

Tap-A-Dip 14 & 16 Pin Test Connectors

# SIGNAL ACCURACY.

## 12,000 Reasons Why Industry Relies on E-Z HOOK.

Choose from over 12,000 standard test accessory products for an immediate solution to your application. They're engineered to assure a reliable contact or connection for any testing, hook-up or assembly task. And E-Z HOOK can ship what you need in 48 hours or less.

For a quick, economical answer to your testing needs, ask for our 112-page catalog of Electronic Test Accessories. It's free. And reliable.

# E-Z-HOOK®

E-Z HOOK, A Division of Tektest, Inc., 225 North Second Ave., Arcadia, CA 91006  
P.O. Box 450, (818) 446-6175. TWX 910-582-1614.

CIRCLE 215 ON FREE INFORMATION CARD

WE MAKE SPECIALS  
SEND US YOUR REQUIREMENTS!

# LETTERS



## COMPONENT NUMBERING SYSTEMS

I enjoy reading your department, "Antique Radios." It's brought back memories of our first Atwater-Kent, and how I first began in radio around 1938.

Some of the history of those days is, I fear, becoming lost. One of the things that distresses me is when I hear someone refer to a diode, such as a 1N914 as an "eyen" 914.

Did you know that the XN (1N, 2N, 3N, 4N) system of numbering

semiconductor devices was actually invented before there were transistors? Before there were transistors (prior to 1948) there were tubes and solid-state "crystal" diodes. During World War II solid-state diodes, the venerable 1N21, 1N23, 1N23A, and 1N23B among them, were used as mixers in radar receivers. Their function was to downconvert the incoming RF energy so that it could be amplified at a lower frequency.

The tube-numbering system most in favor at the time was of the

form nXn; for example a 6L6. The first number indicated the nominal filament or heater voltage. The letter indicated whether the device was an amplifier or a rectifier. Letter designations in the first half of the alphabet were amplifiers; letter designation in the second half of the alphabet were rectifiers. (From that, we see that the L in the tube number indicated that the 6L6 was an amplifier.) The final number indicated the number of active electrodes.

With CRT's, the first number in-

## HAMEG Instruments

### HM 205-2

the new Digital Storage Oscilloscope with 5 MHz sampling rate and 2 x 1024 / 8 bit storage realtime bandwidth DC-20 MHz **\$ 888.00**

### HM 8148

the new intelligent Graphic Printer firmware for time, date, interval, linear interpolation zooming function **\$ 788.00**

### DSO Software

with 13 programs incl. IEEE BUS card **\$ 480.00**


call toll free

(800) 247-1241

HAMEG, Inc.

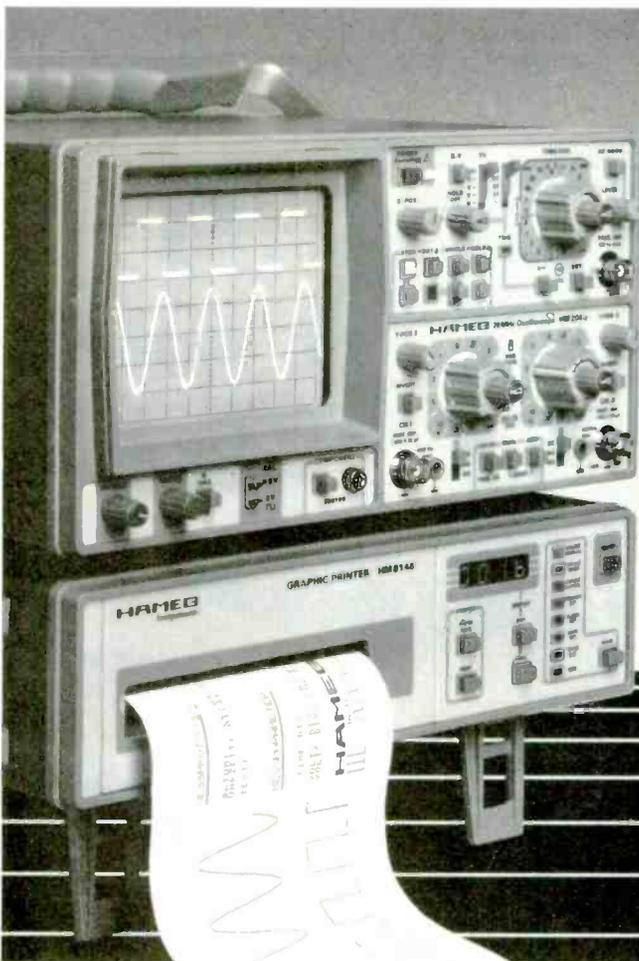88-90 Harbor Road · Port Washington, N.Y. 11050

Phone (516) 883-3837 · Telex (023) 497.4606



# Pride, quality,


When you unpackage a Heathkit product, you open up a special world, a world providing a unique blend of achievement and fun. ■ With your Heathkit product, you'll enjoy the pride of building it yourself, and the confidence that it's built right. Along with the convenience and assurance of knowing how to keep it running at peak performance. ■ Plus you'll learn about new and emerging technologies. For knowledge that gives you that added edge in your field. ■ But most important, with a Heathkit product you're buying from a company whose name is synonymous with quality and enjoyment. From our easy-to-follow documentation to our renowned technical support, we make sure your kitbuilding experience is fun and relaxing – as well as rewarding.

■ And when you're done, your pride will be matched by the satisfaction of owning a product that you know inside out. And that will last a long time. ■ Thousands of people

have discovered this unique dimension in product ownership. We'd like you to discover it, too.

For information on all our quality kits, send NOW for your FREE four-color Heathkit Catalog.

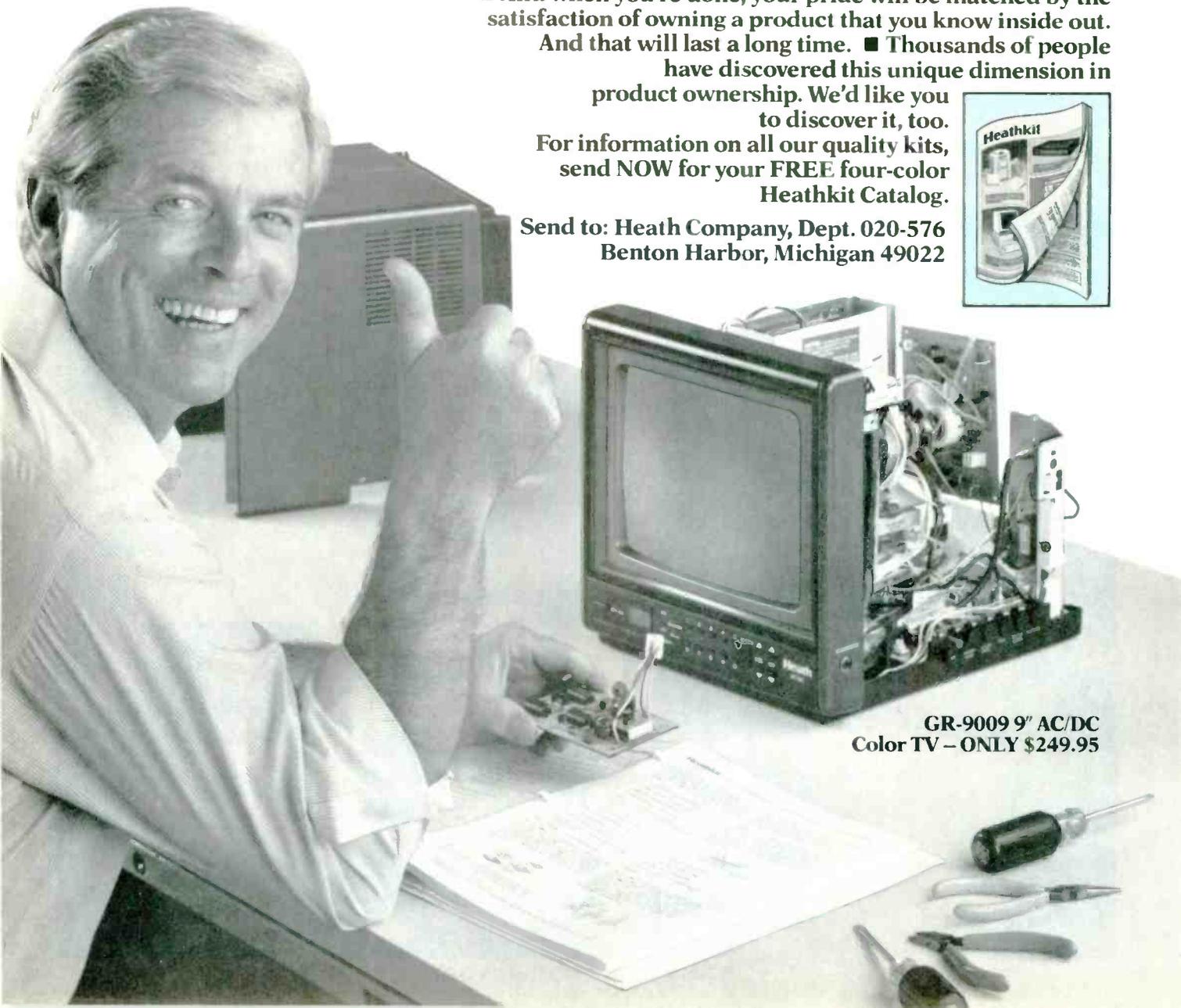Send to: Heath Company, Dept. 020-576  
Benton Harbor, Michigan 49022



GR-9009 9" AC/DC  
Color TV – ONLY \$249.95

# fun... Heathkit®

Enter the Heathkit world with...



## The Heathkit ID-4001

**Weather Computer**, which puts weather information at your fingertips. With the press of a button, you can instantly know temperature, wind speed and direction, and barometric pressure for the exact location in which you live. For planning outdoor activities with greater assurance than ever.

And it's all done with unsurpassed accuracy. Long life IR LED's act as sensors to make both the wind speed cups and the wind direction vane as sensitive and as accurate as a costly laboratory instrument. While active solid state devices reliably measure indoor and outdoor temperatures, all stored by a microprocessor for later recall.

Attractively designed, the ID-4001 will give you extraordinary performance unheard of at such a reasonable price, **\$399.95.**

## The IC-1001 Logic

**Analyzer** is the perfect answer for transforming a PC-compatible computer or standard terminal into a versatile logic analyzer.

A top-grade troubleshooter and design aid, the compact Logic Analyzer includes 16 data lines plus clock and two qualifier lines, checksum capability, and state and timing displays with hex, octal and ASCII equivalents. You can even use it in circuits with clock speeds up to 10 MHz, trigger on any digital word and view events 2,000 pulses before trigger and up to 50,000 pulses after. High impedance inputs virtually eliminate circuit loading.

And it's easy to use! The highly intuitive user-friendly software makes the IC-1001 fully keyboard-configurable and menu-driven. All in one portable unit.

Put this most advanced technology to work for you – for only **\$269.00.**

**To order, call toll-free 1-800-253-0570.**

**Ask for Operator 39.**

**We also have 66 Heath/Zenith Computers & Electronics stores in North America.**

**Call 616-982-3614 for the store location nearest you.**

Heathkit is a registered trademark of Heath Company, a subsidiary of Zenith Electronics Corporation

Prices, product availability and specifications are subject to change without notice.

**Heathkit®**

**Heath  
Company**

KB-103

CIRCLE 193 ON FREE INFORMATION CARD

licated the maximum screen dimension in inches instead of the heater (or filament) voltage. Thus 5BP1 was a tube with a 5-inch screen. The final "P1" indicates the phosphor type. That numbering system for CRT's is still used today, by and large, for both oscilloscope and TV CRT's.

Because solid-state diodes had no filament or heater, a different numbering system was called for. Using a zero designation would not work because there were tubes that had no filament or heater; the 0Z4, for example.) Although the specific origins of the nNxxxx numbering system are obscure (at least to this writer), the following seems clear:

The prefix 1N was chosen to be distinctive from the tube designations. The initial 1 indicated one less than the number of electrodes or contacts; even though, at the time, all semiconductor devices had only two contacts. Perhaps the numbering system was chosen with an eye to a possible future where more contacts would be

added. In any event, it was a fortuitous choice, because when the transistor came along, a ready-made numbering system was already in place!

It is true that as far back as 1925 (some would say even earlier) researchers had dreamed of transistor-like devices. However, the fact remains that there were no such devices generally available until sometime after the work of Shockley, Bardeen, and Brattain that culminated in the invention of the transistor in 1948. Nor was it generally believed, prior to that time, that such a device was even possible.

HOMER B. TILTON  
Tucson, AZ

### FM COMMERCIAL KILLER

Here's another idea for the FM commercial killer that works on at least one station in my area:

Subtract the left and right channel from each other using a differential amp. When the station is broadcasting anything but music, the left and right channels will be

identical (mono), and that can be used to kill the audio output.

There are several ways to find out if that will work with a particular station. One is to connect one side of a speaker to the positive terminal of the left-channel output and the other to the positive terminal of the right-channel output. The signal produced will be the difference between the two channels. Adjust the balance control for no output with a mono signal, and then listen for while. If the commercials can't be heard, the technique will probably work. A more traditional way to see if the technique will work is to examine the the left and right outputs with a dual-channel oscilloscope to see if the commercials are mono or to measure the voltage between the center conductors of the left and right tape-output jacks; for a mono signal, the voltage seen on an AC voltmeter during commercials should be near zero.

STUART ENGELKE

Whitehouse Station, NJ

*continued on page 92*

# NEW RUGGEDIZED SCOPE PROBES

Just a phone call away.

**\$35** P6103

50 MHz 10x  
Compensation Range  
15 to 35 pF

**\$58** P6109

150 MHz 10x  
Compensation Range  
18 to 22 pF


These new passive voltage probes can be used with any oscilloscopes having matching compensation ranges.

Screw in tips mean easy repair, no downtime.

To order call toll free **1-800-426-2200**

In Oregon, call collect (503) 627-9000.

VISA and MasterCharge accepted.

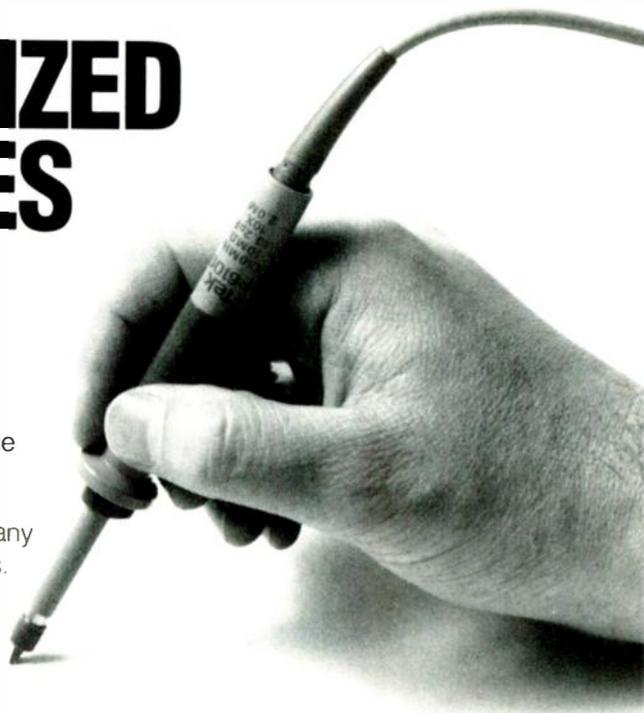

**Tektronix**  
COMMITTED TO EXCELLENCE


# Oops Proof. Now Even Better.

*Industry's Most Popular Heavy-Duty DMMs...  
Now Even Better With Dual-Fuse Protection  
And A Tougher Case.*

**The tough just got tougher.** When Beckman Industrial introduced heavy-duty DMMs tough enough to withstand accidental drops, input overloads and destructive environments, they quickly became the industry's most popular.

Now they're even tougher, thanks to the best dual-fuse protection you can buy and a new case. Covered by a one-year, no-fault guarantee against damage to the meter other than gross abuse.

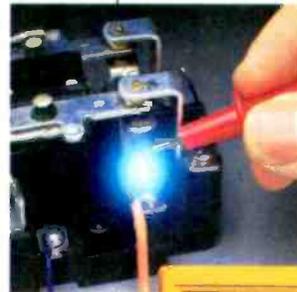For overloads, all voltage ranges can withstand transients up to 6KV. Resistance ranges are protected to 600 volts. Current ranges are protected by a 2 amp/600 volt fuse. The 10 amp range is protected by a 15 amp, 600 volt high energy fuse with 100,000 amp interrupt rating.



Our heavy-duty DMMs can withstand accidental drops, literally bouncing back for more, thanks to a new case made of Valox<sup>®</sup>, one of the most impact and corrosive chemical resistant thermoplastics around. Sensitive components are shock mounted for impact protection.

Even oil, water and industrial grime can't keep our heavy-duty DMMs away from the action. *Everything* is sealed with o-rings for maximum protection.

Of course, even the toughest DMM isn't much good if it can't deliver accuracy and the right combination of capabilities at the right price.

Check the HD DMM specs for yourself: Maximum voltage rating of 1500 volts DC, 1000 volts AC; tested to 40KHz; diode test function; and exclusive INSTA-Ohm<sup>®</sup> capability, now with an audible beeper, to make your HD even easier to use.

What's more, you can select just the model you need without paying extra. Start with the economical HD-100 at \$169.00 for solid, all-around meter performance. Choose the HD-110 with continuity beeper. Or, the HD-110T that lets you select Fahrenheit or Celsius temperature measurement with a simple field adjustment, accurately measuring from -4°F to +1999°F, and works with any K-type thermocouple. It also has a measurement range of 32°F to 392°F with the thermocouple provided.

You can even get the true RMS capability on the HD-130,



or with a 4 1/2 digit display required by the HD-140's accuracy.

HEAVY DUTY DMMS	HD100	HD110	HD110T	HD130	HD140
Digits			3 1/2		4 1/2
Accuracy (Vdc)		0.25%		0.1%	0.05%
Input Impedance		22 Megohms			10 Megohms
AC Conversion Type		Average		True RMS	True RMS
Bandwidth (AC Volts)		10KHz		40KHz	10KHz
Current Range		0.1µA			0.01µA
Min. Reading					
Max. Reading	2A	10A (20A for 30 Seconds)			
Continuity Beeper		✓			
Battery Life (Alkaline type)		2000 Hours			100 Hours

Visit your local Beckman Industrial distributor today. Compare. And discover why the toughest are tougher than ever.

*In-Service Instruments,  
We're The One.*

**Beckman Industrial™**

Beckman Industrial Corporation Instrumentation Products Division  
A Subsidiary of Emerson Electric Company  
4885 Ruffin Rd. San Diego, California 92123-1898  
(619) 565-4415 • FAX (619) 268-0172 • T1X 240031

© 1987 Beckman Industrial Corporation

# Train with NRI for a servicing

**NEW!**


Train with the newest Sanyo 880 Series Computer—it's fully IBM-compatible and runs almost twice as fast as the IBM PC!

## Get started now by building this fully IBM PC compatible computer

Now you get it all... training for America's fastest growing career opportunity... training to service all computers... training on the newest total computer system, the Sanyo 880. Only NRI can give you the well-rounded training you need, because only NRI gives you a complete computer system... computer, monitor, disk drive, software, even test instruments like a digital multimeter and logic probe to work with and keep. It all adds up to training that builds the knowledge, competence, and ability you need to succeed as a computer service specialist.
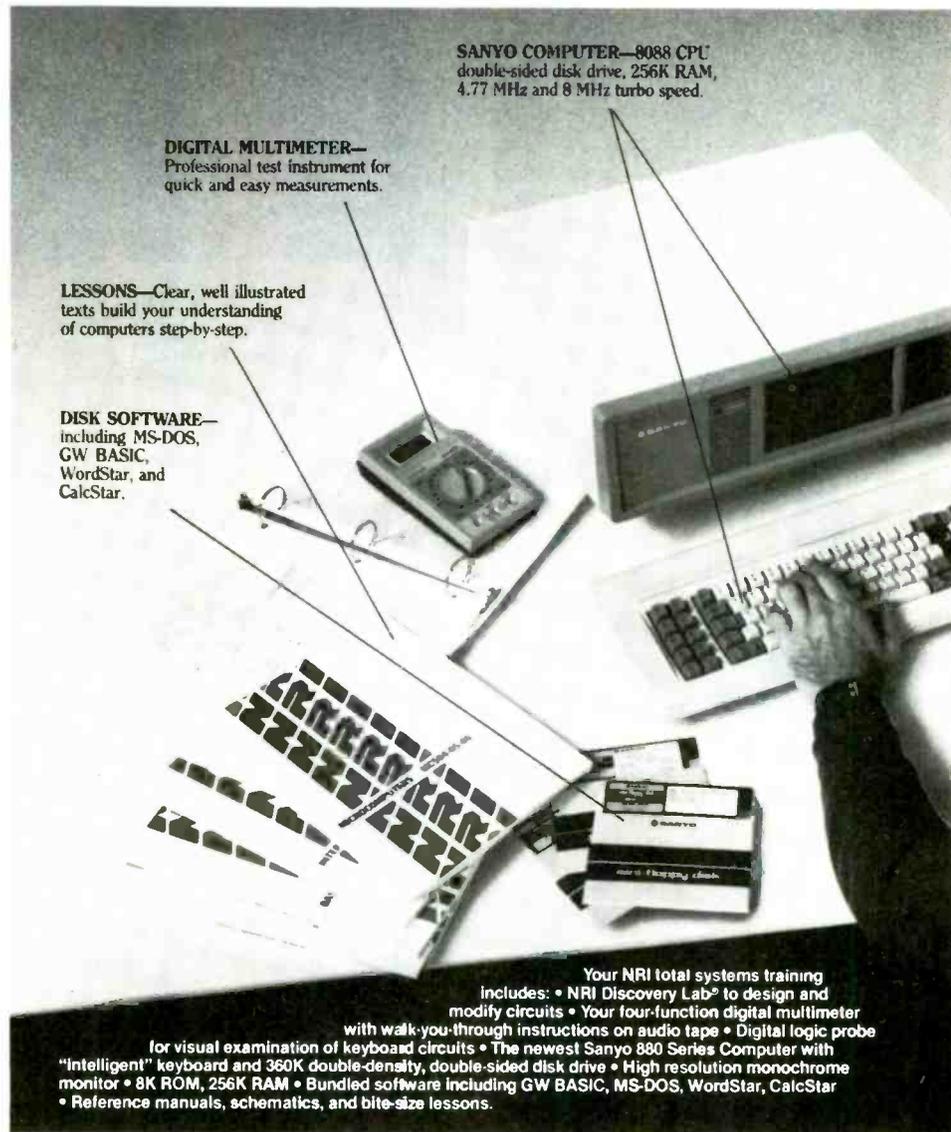
### Get inside the newest, fully IBM PC compatible Sanyo Microcomputer


As an NRI student, you'll get total hands-on training



as you actually build your own latest model Sanyo 880 Series computer from the keyboard up. It's fully IBM PC-compatible and, best of all, it runs programs almost twice as fast as an IBM PC. As you assemble the Sanyo 880, you'll perform

demonstrations and experiments that will give you a total mastery of computer operation and servicing techniques. You'll do programming in BASIC language—even run and interpret essential diagnostic software.

# high paying career computers

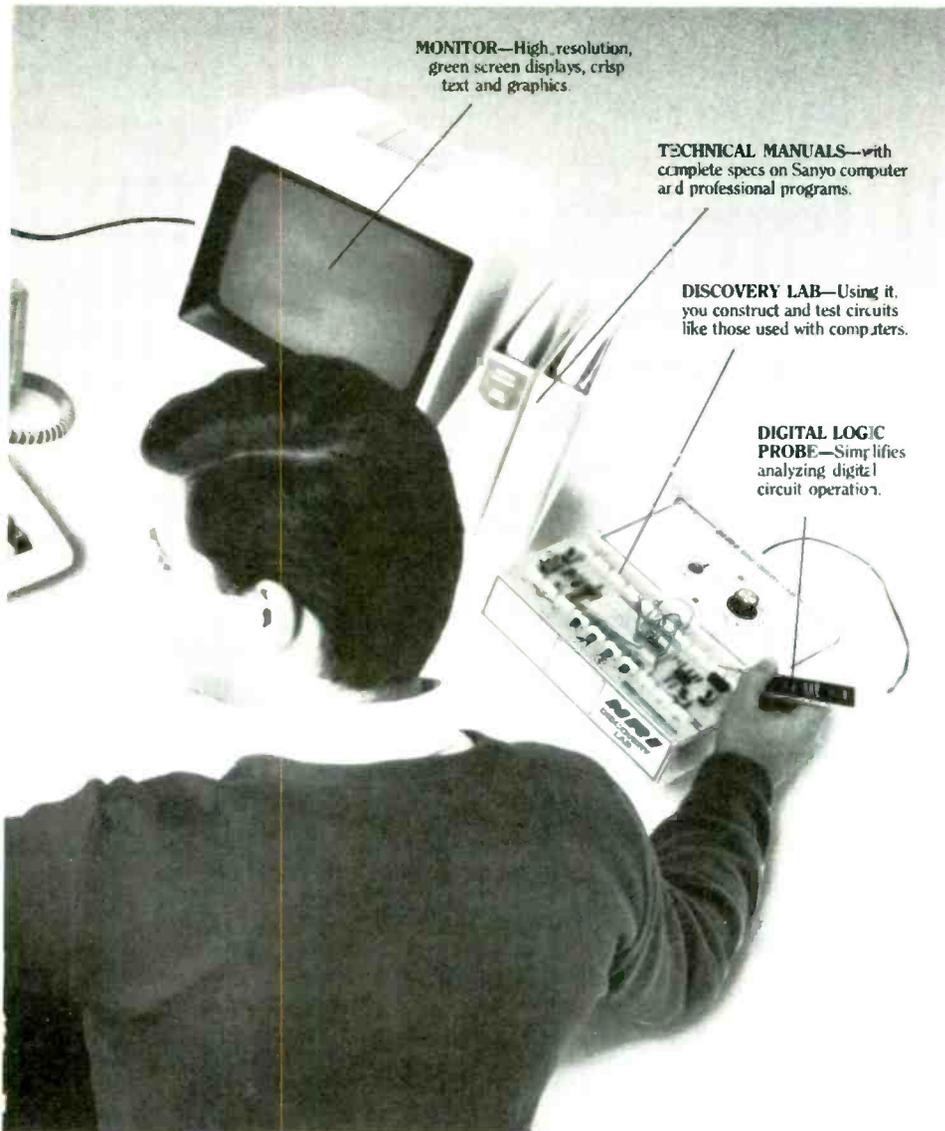

**MONITOR**—High resolution, green screen displays, crisp text and graphics.

**TECHNICAL MANUALS**—with complete specs on Sanyo computer and professional programs.

**DISCOVERY LAB**—Using it, you construct and test circuits like those used with computers.

**DIGITAL LOGIC PROBE**—Simplifies analyzing digital circuit operation.

at your own convenience, backed at all times by your own NRI instructor and the entire NRI staff of educators and student service support people. They're always ready to give you guidance, follow your progress, and help you over the rough spots to keep you moving toward your goal.

## 100 page free catalog tells more... send today

Send the postage-paid reply card today for NRI's 100 page catalog that gives all the facts about computer training, plus career training in robotics, data communications, TV/ audio/video servicing, and many other fields. If the card is missing, write to NRI at the address below.



## Understanding you get only through experience

You need no previous knowledge to succeed with NRI. You start with the basics, rapidly building on the fundamentals of electronics with bite-size lessons. You perform hands-on experiments

with your NRI Discovery Lab and then move on to master advanced concepts like digital logic, microprocessors, and computer memories.

## Learn at home in your spare time

You train in your own home

**NRI** SCHOOLS  
McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue  
Washington, DC 20016  
We'll give you tomorrow



# EQUIPMENT REPORTS

## Onkyo Unifier Universal Programmable Remote Control

A single handheld remote control for all your audio and video needs.

CIRCLE 12 ON FREE INFORMATION CARD



It makes sense that an audio manufacturer has come up with a solution to having too much of a good thing, because the new remote-controlled CD players, stereo tuners, and amplifiers have added their share to the growing clutter of handheld remote controls on consumers' coffee tables. But the *Unifier* does more than simply remove some coffee-table clutter—it is a device that can unite audio and video functions in a single control. And the marriage of audio and video equipment is sure to sell a great many systems over the next few years.

The *Unifier* is an infrared remote control with a memory capacity of more than 100 functions. Despite the array of 35 buttons, 5 LED's,

IN MARCH 1986, WE LOOKED AT THE FIRST programmable remote control, G-E's *Control Central*. Since that time, several other companies have manufactured similar prod-

ucts. The latest entry is the model RC-AVIM, better known as the *Unifier*, from Onkyo (Onkyo U.S.A. Corporation, 200 Williams Drive, Ramsey, NJ 07446).

## CONNECTION PROTECTION

SWITCHES & RELAYS

EDGE CONNECTORS

PLUGS & SOCKETS

POTENTIOMETERS



CONNECTING CABLES

TERMINAL STRIPS

GOLD PLATED CONNECTORS

BATTERY CONTACTS

### CRAMOLIN®

Even the finest equipment in the world cannot guarantee noise-free operation. One "dirty" connection anywhere in the electrical path can cause unwanted noise or signal loss.

### "MORE THAN A CONTACT CLEANER"

**CRAMOLIN®** is a fast-acting, anti-oxidizing lubricant that cleans and preserves all metal surfaces, including gold.

When applied to metal contacts and connectors, **CRAMOLIN®** removes resistive oxides as it forms a protective molecular layer that adheres to the metal surfaces and maintains maximum electrical conductivity.

**CRAMOLIN®** - USED BY THOSE WHO DEMAND THE BEST:

Bell & Howell	Hewlett Packard	MCI(Sony)	Nakamichi
Boeing	John Fluke Mfg.	Motorola	RCA
Capitol Records	McIntosh Labs	NASA	Switchcraft


SINCE 1956

**CAIG LABORATORIES** SINC

1175-O Industrial Ave., (P.O. Box J) - Escondido, CA 92025-0051 U.S.A. \* (619) 743-7143

CIRCLE 184 ON FREE INFORMATION CARD

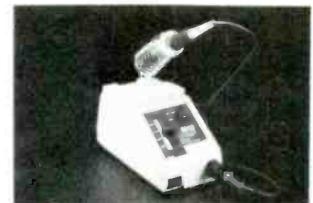W.S. Jenks & Ungar bring you temperature controlled, anti-static soldering with a 2-year warranty and a great price!



**\$115.95**

This soldering system can be tailored to fit your job requirements by means of interchangeable handles and tips. With a variable temperature range of 450 to 850°F, it features electronic control and 24 volt at the handle. Handles have quick disconnect plugs. A 2-position switch on the power base matches the correct calibration to the proper handle. Meets MIL-S-45743E, WS 6536E and DOD-STD-2000-1B, and is ESD safe.

Model 9920AS includes a traditional macro-size handle and heater barrel which is well suited for general electronic and standard soldering applications. Call TOLL-FREE for other handles and tips to expand this versatile soldering system.

TOLL-FREE  
1-800-638-6405

**W.S. JENKS & Son**



1933 Montana Ave. NE Washington DC 20002  
(202) 529-6020 TELEX: 89-2667 FAX: (202) 832-3411

CIRCLE 66 ON FREE INFORMATION CARD

and a 3-position slide switch on the front panel, the remote is surprisingly easy to program, and even easier to use.

The *Unifier* incorporates three major modes: AUDIO, VIDEO, and AUXILIARY; the front-panel slide switch determines which mode the unit is in. Each key can be programmed with a separate function for each mode.

The keyboard layout consists of 5 major key groupings: AMP/TV, PHONO, TUNER, TAPE/VCR, and CD/CATV and each button has one or two color-coded labels. For example, the AMP/TV section has keys labeled in white for CD, PHONO, TUNER, TAPE, etc. Those same keys are labeled in blue with the numerals 1 through 4. The white labels, of course, correspond to the audio mode, while the blue labels correspond to the video mode.

The function of each key, however, depends not on its label, but on how you program it. A keypad template is provided for any changes you make, as well as incorporating any additional auxiliary functions.

### Programming the *Unifier*

Teaching the *Unifier* the codes of your current remote units is almost as easy as using the remotes themselves. Its 5 LED's guide you through the process.

The first step is to put the *Unifier* in the learn mode by flipping a small, recessed switch on the back of the unit to the LEARN position. Once you flip the switch, an LED labeled PRESS MATCHING FUNCTION KEYS lights. You then place the unifier head-to-head with your remote and do what you're prompted to—you simply press the matching function keys. After the *Unifier* recognizes the code, the LEARNING RELEASE LED lights, prompting you to release the keys. Immediately after doing so, you're prompted by the INPUT AGAIN LED to repeat the process for that key—a great double-check. Assuming everything is OK, the FUNCTION LEARNED/SENDING LED lights to verify that the key is set. If, for any reason, the two codes don't match, or if anything else goes wrong, the ERROR LED lets you know.

*continued on page 29*

## HITACHI SCOPES AT DISCOUNT PRICES!

20MHZ



Model V212 \$475

Model V-212 20MHZ Dual Channel (1mV Sens.) \$475  
 Model V-422 40MHZ Dual Channel (1mV Sens.) \$699  
 Model V-425 40MHZ Dual Channel (with cursor) \$795  
 Model V-660 60MHZ Triple Channel (Delayed Sweep) \$990  
 Model V-1060 100MHZ Quad Channel (Delayed Sweep) \$1,340  
 All above scopes have a 3 year guaranty on parts and labor


100MHZ



Model V1060 \$1,340


15-25%  
OFF LIST  
PRICE

## ELENCO PRODUCTS AT DISCOUNT PRICES!

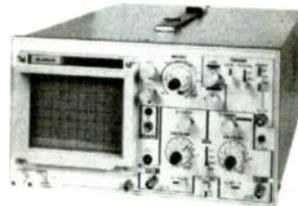

20MHz DUAL TRACE OSCILLOSCOPE  
\$359 MO-1251

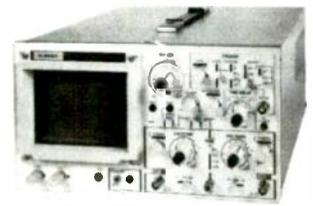TWO  
100MHZ  
SWITCHABLE  
PROBES  
INCLUDED



35MHz DUAL TRACE OSCILLOSCOPE  
\$498 MO-1252

Top quality scopes at a very reasonable price. Contains all the desired features. Elenco's 2 year guarantee assures you of continuous service. Two 1x, 10x probes, diagrams and manual included. Write for specs.

100MHZ test probes, switchable 1x, 10x, Ref. (Complete W/ 5 accessories) Fits most scopes \$22



MULTIMETER with CAPACITANCE AND TRANSISTOR TESTER  
Model CM-1500A \$58  
Reads Volts, Ohms, Current, Capacitors, Transistors & Diodes W/Case



TRUE RMS 4 1/2 DIGIT MULTIMETER  
Model M-7000 \$135  
.05% DC Accuracy  
.1% Resistance with Freq. Counter & Deluxe Case



Auto Ranging plus Manual Ranging 3 1/2 Digit Meter 28 Functions Fully protected  
M-1180 .7% Acy \$36.95  
M-1182 .25% Acy \$39.95  
M-1181 .1% Acy \$42.95




GF-8016 FUNCTION GENERATOR with Freq. Counter \$239  
• Sine, Square, Triangle  
• Pulse, Ramp, .2 to 2MHz  
• Frequency .1 thru 10MHz  
GF-8015 without Freq. Meter \$179



10MHZ OSCILLOSCOPE \$199  
Model S-3000  
• 10MHz DC or AC  
• Triggered Sweep  
• Calibrated Vert & Hor  
• Reads Volts & Freq



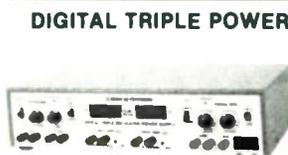BREADBOARD  
Model 9438 Shown  
9430 1,100 pins \$15  
9434 2,170 pins \$25  
9436 2,860 pins \$35



DIGITAL TRIPLE POWER SUPPLY Model XP-785 \$195  
0-20V @ 1A  
0-20V @ 1A  
5V @ 5A  
Fully Regulated, Short Circuit Protected with 2 Limit Cont. 3 Separate Supplies  
XP-680 with Analog Meters \$159.50




DIGITAL LCR METER \$148  
Model LC-1800  
Measures Inductors, Capacitors, Resistors



50MHZ LOGIC PROBE 20 nsec with memory LP-700 \$23  
Logic Pulsar LP-600 \$23



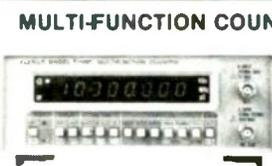DIGITAL 3 AMP POWER SUPPLY Model XP-750 \$165  
0-40V @ 1.5A  
0-20V @ 3A  
Fully regulated, short circuit protected current limit control  
XP-650 with Analog Meters \$129.50



MULTI-FUNCTION COUNTERS  
F-1000 1.2GH \$245  
F-100 120MH \$169  
Frequency, Period, Totalize, Self Check with High-Stabilized Crystal Oven Oscillator, 8 Digit LED Display

C&S SALES INC., 8744 W. North Ter., Niles, IL 60648 800-292-7711 (312) 459-9040 ASK FOR CATALOG

2 Year Limited Guarantee! Add 5% for Postage (\$10 max), IL Res., 7% Tax

CIRCLE 109 ON FREE INFORMATION CARD



V-209

**DC to 20MHz, Dual Channel Mini-Portable Scope**

- 3.5" CRT with 1.5kV Potential
- 3-WAY Power Supply- AC, DC and Built-in Battery Pack
- Vertical Deflection: CH1, CH2, ALT, CHOP, ADD (DIFF)
- Max Sensitivity: 1mV/div at x10 Mag.
- X-Y Operation: 3° from DC to 100kHz

**\$822. Save \$175!**

V-212



**\$440. Save \$175!**

**DC to 20MHz, Dual Channel**

- 6" CRT with 2kV Potential
- Vertical Deflection: CH1, CH2, ALT, CHOP, ADD (DIFF)
- Max Sensitivity: 1mV/div at X5 Mag.
- X-Y Operation 3° from DC to 50kHz

**V-222 Same as above, but**

with CH1 output and DC offset voltage monitor outlet available for external counter or DVM.

**\$515. Save \$200!**



**WM. B. ALLEN SUPPLY COMPANY**

**ALLEN SQUARE**

300 Block North Rampart  
New Orleans Louisiana 70112

NATIONWIDE 800 535-9593

LOUISIANA 800 462-9520

NEW ORLEANS 504 525-8222

FAX ORDER LINE 504 525-6361

• American Express • Visa • MasterCard •

CIRCLE 103 ON FREE INFORMATION CARD

# NEW PRODUCTS



CIRCLE 24 ON FREE INFORMATION CARD

**POWER BOOSTER** for infrared remote controls, *Zapit* attaches to the front of the handheld remote, where it receives the infrared signals, and re-transmits them at a higher power. The high-power infrared output of *Zapit* bounces off

walls and ceilings so that it is not necessary to carefully point the handheld remote unit at the device you want to activate. *Zapit* has a suggested retail price of \$24.95—**Monster Cable**, 101 Townsend Street, San Francisco, CA 94107.

**CURRENT CLAMP**, the model *80i-1010* clamp-on probe is an accessory for digital multimeters that accurately measures AC current to 700 amperes, and DC current up to 1000 amperes. The probe clamps

around a conductor and senses the magnetic field produced by current flow, allowing safe, accurate measurements without breaking into the circuit.

A special feature of the model *80i-1010* is a thumbwheel **ZERO** control that allows the user to compensate for residual core magnetism in the clamp, thereby improving the accuracy of DC measurements down to 1 ampere.

The model *80i-1010* has a suggested U.S. list price of \$229.00.—**John Fluke Mfg. Co., Inc.**, P.O. Box C9090, Everett, WA 98206.



CIRCLE 25 ON FREE INFORMATION CARD

**ELECTROSTATIC INTERFERENCE SIMULATOR**, the model *2600* is designed as a complete and field-portable ESD (spark discharge)

# Cable TV

## DESCRAMBLER ARTICLE PARTS

### February 1984 Issue

We stock the parts, PC Board and AC Adaptor for an article on building a cable TV descrambler appearing in *Radio-Electronics*.

**#701 Parts Package\*** ..... **\$29.00**

Includes all the original resistors, capacitors, diodes, transistors, integrated circuits, coils, IF transformers (Toko BKAN-K5552AXX).

**#702 PC Board\*** ..... **\$8.95**

Original etched and drilled silk-screened PC Board used in the article.

**#704 AC Adaptor** ..... **\$7.95**

Original (14 volts DC @ 285 ma) AC Adaptor used in the article.

**FREE reprint with Purchase Above**

**#708 Toko Coil Set** ..... **\$6.95**

Includes (2) BKAN-K5552AXX, (1) E520HN-300023, (1) 144LY-120K and BFQ-85 Replacement 2SC2369.

### February 1987 Issue

We stock the parts, PC Board and AC Adaptor for an article on a tri-mode cable TV descrambler appearing in *Radio-Electronics*.

**#301 Parts Package\*** ..... **\$39.00**

Includes all the original resistors, capacitors, diodes, potentiometers, transistors, integrated circuits, LED's, Toko coil (E520HN-300023) and Plessey Saw Filter (SY-323).

**#302 PC Board\*** ..... **\$8.95**

Original 5 x 8.8 etched and drilled silk-screened PC Board used in the article.

**#304 AC Adaptor** ..... **\$7.95**

Original (14 to 18 volt DC @ 200 ma) AC Adaptor used in article.

**Free Reprint with Purchase Above**

**#308 Plessey & Toko Set** ..... **\$6.95**

Includes (1) Plessey SY323 Saw Filter plus (1) Toko E520HN-300023 Coil.

Add \$2.50 Shipping & Handling; \$4.50 Canadian Orders

72-CHANNEL

MC-702 CONVERTER

## CABLE CONVERTER

**\$79.95**

WITH INFRA-RED REMOTE CONTROL



- 72-channel capability
- Wireless, Infra-Red remote control
- Channel output 2 or 3 switchable
- Microprocessor controlled PLL operation
- Skip channel memory eliminates unused channels
- Parental control for all channels
- Last channel recall
- Fine tune memory
- UL listed/FCC approved
- Simple installation with any TV
- Includes battery and 3 foot coax cable

Add \$3.50 Shipping and Handling  
\$4.50 on Canadian Orders

**ORDER TOLL FREE**  
**1-800-227-8529**

Inside MA: 617-695-8699

VISA, MASTERCARD OR C.O.D.



\*Not available to Massachusetts residents due to state law.

**J & W**  
**ELECTRONICS, INC.**

P.O. BOX 800 • MANSFIELD, MA 02048

©copyright 1987 by J&W Electronics, Inc.

CIRCLE 65 ON FREE INFORMATION CARD

## GREAT SAVINGS ON LEATHER ATTACHES



**FACTORY NEW!  
FIRST QUALITY!**

Unsnaps for an extra 1/4" depth!

### E-X-P-A-N-D-A-B-L-E LEATHER BRIEFCASES

Make a bold, new impression at your next business meeting. Order this set of TWO cases for the look and feel of designer attaches...without the high price, due to our special arrangements.

- TWO Factory New, First Quality Cases for ONE Low Liquidation Price.
- Rich Pigskin-Like Interior, Plus Generous Organization Pockets.
- Combination Locks Offer Security.
- Choose Burgundy or Black.

**Large Case.** It's 13" H x 18 1/4" W x 4 1/2" D and easily expands an extra 1/4" in depth if you need more room.

**Banker's Case.** Perfect for meetings where you need only a few documents. 11" H x 16 1/2" W x 2 1/2" D.

Shop and compare! You'll discover this is a great buy for TWO cases!

Compare At ..... **\$229.00**

Liquidation Price  
For Set of TWO ..... **\$59**

Burgundy: Item H-2802-7037-518 S/H: \$5.75/set  
Black: Item H-2802-7072-648 S/H: \$5.75/set

Credit card customers can order by phone. 24 hours a day, 7 days a week.

**Toll-Free: 1-800-328-0609**

Sales outside the 48 contiguous states are subject to special conditions. Please call or write to inquire

SEND TO: Item H-2802

COMB Direct Marketing Corp.  
1405 Xenium Lane N/Minneapolis, MN 55441-4494

Send **Leather Briefcase(s)** at \$59 per set, plus \$5.75 per set for ship, handling. (Minnesota residents add 6% sales tax. Sorry, no C.O.D. orders.)

Send **Burgundy**, Item H-2802-7037-518

Send **Black**, Item H-2802-7072-648

My check or money order is enclosed (No delays in processing orders paid by check.)

PLEASE CHECK  VISA  M/C  D/C  DISC

Acct No \_\_\_\_\_ Exp \_\_\_\_\_

PLEASE PRINT CLEARLY

Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. # \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ ZIP \_\_\_\_\_

Phone (\_\_\_\_) \_\_\_\_\_

Sign Here \_\_\_\_\_

test system, consisting of an analog controller, a separate high-voltage test head, and application modules. A series of plug-in tips, in conjunction with the various operating modes available on the




CIRCLE 26 ON FREE INFORMATION CARD

controller, provide a range of functions that include spark discharge, current injection, ion generation, corona generation, and electric field propagation and collapse.

The model 2600 is a complete system, with no additional hardware or calibrators needed. It is priced at \$4195.00.—IMCS Corporation, 1300 Spacepark Way, Mountain View, CA 94043.

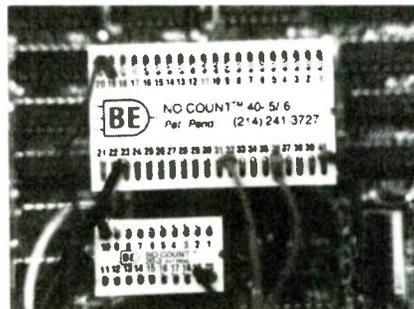**PIN LOCATOR**, the *No Count*, slips over the pins of an IC test clip and remains with the clip. When the



CIRCLE 27 ON FREE INFORMATION CARD

test clip is attached to the IC, each pin is easily identified, eliminating time-consuming pin counting.

*No Count* is available in 14 configurations from 14 to 64 pins; prices range from \$3.50 to \$6.50.—L. J. Broder Enterprises, Inc., 11105 Shady Trail, Suite 115, Dallas, TX 75229.

**AUDIO TAPE DECK CLEANER**, *Standard System II*, combines Discwasher's Perfect-Path Cassette Head Cleaner and the Capstan Pinch Roller Cleaner to provide complete tape-deck care in one cassette shell. A deluxe version

with a carrying case is also available.

The Perfect Path Cassette Head Cleaner is designed to clean audio-cassette heads on car or home cassette decks quickly and safely. It uses no fluid and contains no alcohol that can damage cassette




CIRCLE 28 ON FREE INFORMATION CARD

mechanisms, nor are there any abrasive polishing compounds to cause excessive wear.

The Capstan Pinch Roller Cleaner is based on a special fluid formula that will not extract vital rubber stabilizers. The *Standard System II* is priced at \$11.95; the deluxe version is \$2 higher.—Discwasher, 4309 Transworld Road, Schiller Park, IL 60176.

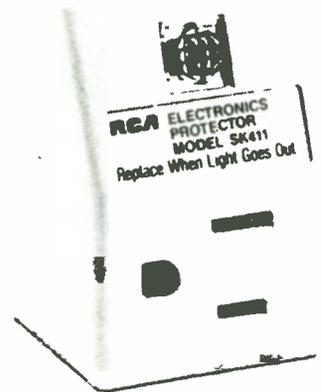**SURGE SUPPRESSORS**, the model *SK411*, (shown) the model *SKM411*, the model *SK416*, all contain metal-



CIRCLE 29 ON FREE INFORMATION CARD

oxide varistors and feature an indicator lamp that offers assurance that the equipment is being protected continuously.

The model *SKM411* is a single-outlet electronics protector, and is priced at \$22.15.

The model *SKM411* is a single-outlet microwave protector, and is priced at \$26.20.

The model *SK416* is a six-outlet electronic protection center surge suppressor and is a corded power center with ON/OFF switch. It is priced at \$73.80.

The model *SKF416* is a six outlet protection center. In addition to suppressing surge, it also filters out radio interference noise, with 35 dB noise attenuation at 1 MHz. It has an ON/OFF switch. It is priced at \$86.75.—RCA, 2000 Clements Bridge Road, Deptford, NJ 08096.

**TEMPERATURE AND HUMIDITY METERS**, the model *HT-410* (°C), shown in photo, and the model *HT-411* (°F) are designed to aid in the control of both parameters in



CIRCLE 30 ON FREE INFORMATION CARD

applications such as pharmaceutical, chemistry, agriculture, forestry, food, electrical/electronics, and building environments.

Among the features provided by those state-of-the-art digital temperature and relative-humidity meters are excellent water resistance, enabling measurements for long periods of time, even when the main unit, sensor, and probe are subjected to condensation, and instant switching between temperature and humidity displays. Simultaneous analog outputs for temperature and humidity facilitate use in environmental control and monitoring applications.

The model *HT-410* and the model *HT-411* both have the same price: \$450.00 each.—North American Soar Corporation, 1125 Cornell Ave., Cherry Hill, NJ 08002.

Call 1-800-843-3338 today to start thoroughly analyzing and pinpointing any trouble in any TV-RF distribution system, automatically to FCC specifications . . .

**New**



with the All New  
**FS74 CHANNELIZER SR™ TV-RF Signal Analyzer**  
Patents Pending \$3495

IEEE - 488

Does your success in servicing RF distribution systems depend on locating problems quickly and accurately? If so, here's why your all new Sencore FS74 CHANNELIZER SR. will mean success for you . . .

Quickly tune in all TV/FM channels from 5 MHz to 890 MHz. Exclusive all channel, microprocessor-controlled digital tuner checks every standard and cable channel with better than FCC accuracy to fully analyze any system.

Exclusive 5 microvolt sensitivity to bring in even weak signals. Autoranged attenuator automatically selects the best sensitivity for simplifying your VHF, UHF, or FM signal measurements like never before possible.

Automatic hassle-free S/N ratio, A/V ratio, and hum level tests. Exclusive on-channel signal-to-noise ratio test eliminates time-consuming signal comparison and chart reading. Exclusive audio-to-video ratio test measures directly in dB for easy comparison to specifications.

Exclusive checks for ghosts, co-channel interference, line reflections, and other signal quality checks. Portable 4 MHz wideband battery-operated monitor lets you finally check the quality of your cable or MATV system and stop annoying callbacks.

Built-in autoranging AC/DC volt/ohmmeter makes troubleshooting a snap. Exclusive all-weather design holds tighter than FCC specifications from -4°F to +104°F. Truly portable, field-tested tough for dependable ease of use.

Begin successfully locating TV-RF signal problems more quickly and accurately than ever before possible, with the new FS74 CHANNELIZER SR. Call WATS Free 1-800-843-3338 today for a free Product Guide or an industry exclusive "Try before you buy" 15 Day Self Demo.

"CHANNELIZER SR." is a trademark of Sencore, Inc.



WATS Free 1-800-843-3338 In Canada WATS Free 1-800-851-8866

**SENCORE**

Means Success In Electronic Servicing

3200 Sencore Drive, Sioux Falls, South Dakota 57107  
Call Collect 605-339-0100 In SD & AK

CIRCLE 187 ON FREE INFORMATION CARD

# Sterling™

## precision drills

variable or constant speed... from the Maxi to the Mini!



Crafted in West Germany, the high-speed, low-voltage, hand-held drills are extremely quiet, lightweight and cool running with a very low vibration level. Speeds range from 0-21,000 RPM with a universal chuck to accommodate accessories up to .125 in size.

### Accessories for any application!

Adapt your drill to all your exacting needs with over 100 high quality drill bits, grinding stones and wheels, saws, cutting wheels, sanders, brushes, polishers and other accessories. Available in "kits" or as separate items.

Your exacting standards demand Sterling quality.

WAHL CLIPPER CORPORATION  
2900 Locust Street, Sterling, IL 61081  
(815) 625-6525

CIRCLE 216 ON FREE INFORMATION CARD

**MINIATURE ADHESIVE MOUNT, ABMIM** is an adhesive-backed mount  $\frac{1}{2} \times \frac{1}{2}$  inches, designed to meet the needs of limited-space applications. It is used with sub-miniature or miniature cable ties



CIRCLE 32 ON FREE INFORMATION CARD

to provide secure mounting of wire and cable. Four-way entry design (of cable ties to mount) saves orientation time.

No hole-drilling or special fasteners are required. The user peels off the mount and then applies it. Four mounts are supplied on a common release liner for easy handling.

The miniature mount supports a maximum load of .13 lb. It can be used in applications with continuous temperatures up to 120°F with rubber foam-tape backing or up to 180°F with acrylic foam-tape backing. It is priced at \$24.49 per 100 pieces.—**Panduit Corporation**, 17301 Ridgeland Ave., Tinley Park, IL 60477-0981.

**CABLE DESIGNATOR**, the model 525, is designed for identifying individual cables in a common bundle. It can transmit through taps and a splitter, and is therefore able



CIRCLE 33 ON FREE INFORMATION CARD

to identify individual cables that are already in place, with all components installed.


The model 525 is useful in various construction applications including CATV or SMATV in

apartment buildings, local-area networks and other computer systems, schools, hospitals, offices, high-rise buildings, and ships.

The model 525 "SIX PAK," consists of one receiver, five transmitters, an operator's manual, and a carrying case; it is priced at \$395.00.—**Riser-Bond Instruments**, 505 16th Street, P.O. Box 188, Aurora, NB 68818.

**OSCILLOSCOPE**, the model 7934, is a screen-storage oscilloscope that takes over where digital storage leaves off.

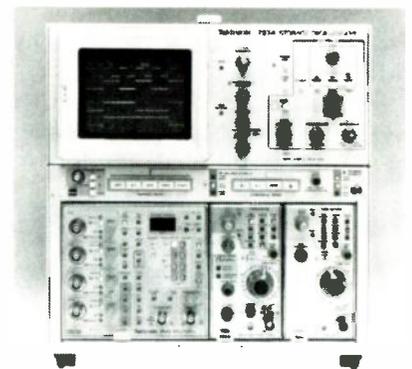Speed begins in the model 7934 with a high bandwidth—500 MHz—and a fast single-shot



CIRCLE 34 ON FREE INFORMATION CARD

risetime—700 picoseconds. The real speed advantage, however, is in the model 7934's 4-cm/nanosecond stored writing rate.

Along with fast storage, the model 7934 also offers the flexibility of multiple-storage modes and controls to meet changing application needs. A bistable storage feature provides long viewing times, which allows time-lapse displays of changing events, which is ideal for checking pulse jitter or digital timing margins. Fast variable persistence with reduced scan captures fleeting events, such as arcing or plasma discharge. A SAVE mode gives the user up to 30 times longer viewing time; and storage level adjusts writing rate, which is useful in suppressing storage of random noise on low-level signals.

The model 7934 is priced at \$20,355.00. That price includes the 7934 mainframe, a 7A29 vertical-amplifier plug-in for a 500-MHz bandwidth, and a dual time-base plug-in for 500-MHz triggering.—**Tektronix, Inc.**, PO Box 500, Beaverton, OR 97077. R-E

## EQUIPMENT REPORTS

continued from page 23

### Using the *Unifier*

The *Unifier* is no more difficult to use than any standard remote control—once you get used to it. It has more keys than most remotes, so finding the key you're looking for can be difficult. The unit can be difficult to handle, as well, because it weighs about ½ pound and measures about 7 × 3 inches, with a thickness that ranges from about ¾ to 1⅛ inch. What those numbers translate to is this: One-handed operation is possible for those with long fingers, but it's not easy to find a single grip that will let your thumb comfortably reach every key. For users with small hands, one-handed operation will be very clumsy. On the positive side, however, the most-used keys are grouped within easy reach, and the keys are large and spaced well enough that you won't hit a key you don't mean to.

Unfortunately, the labels used for the video functions are printed in blue, on a black background. If you keep your lights low in your media room, you may have a hard time finding the right key. Of course, searching for the VCR PLAY key on the *Unifier* can certainly be easier than trying to find the play key on your VCR's handheld remote unit—especially when it's buried somewhere on your coffee table between the remote for your TV, CD player, tuner, and maybe your cable box!

One problem that plagues some remotes is limited range. That's not the case here. The infrared power output from the *Unifier* is probably more powerful than the remotes you're currently using.

The *Unifier* is powered by 4 "AAA" alkaline batteries. You'll know when it's time to change the batteries thanks to a low-battery indicator. When you do change the batteries, what happens to the 100 functions that you programmed? Fortunately, a charged-capacitor backup system gives about one hour of memory retention. After that, you'll have to re-program the unit.

The *Unifier* has a suggested retail price of \$119.95. R-E

## Walk "tough dog" troubles out of any TV & VCR in half the time . . . or your money back



with the exclusive, patented,  
VA62 Universal Video Analyzer . . . \$3,295

### Would you like to?

**Reduce analyzing time:** Isolate any problem to one stage in any TV or VCR in minutes, without breaking a circuit connection, using the tried and proven signal substitution method of troubleshooting?

**Cut costly callbacks and increase customer referrals** by completely performance testing TVs & VCRs before they leave your shop? Own the only analyzer that equips you to check all standard and cable channels with digital accuracy? Check complete, RF, IF, video and chroma response of any chassis in minutes without taking the back off the receiver or removing chassis plus set traps dynamically right on CRT too? Simplify alignment with exclusive multiburst pattern?

**Reduce costly inventory from stocking yokes, flybacks, and other coils and transformers, for substitution only,** with the patented Ringing Test. Run dynamic proof positive test on any yoke, flyback, and integrated high voltage transformer . . . in- or out-of-circuit?

**Protect your future** by servicing VCRs for your customers before they go to your competition? Walk out "tough dog" troubles in any VCR chrominance or luminance circuit — stage-by-stage — to isolate problems in minutes? Have proof positive test of the video record/play heads before you replace the entire mechanism?

**Increase your business** by meeting all TV and VCR manufacturers' requirements for profitable warranty service work with this one universally recommended analyzer?

To prove it to yourself, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE Self Demo . . . or learn how the VA62 works first by calling for your free simplified operation and application instruction guide, worth \$10.00.



Call Today Wats Free 1-800-843-3338

**SENCORE**

3200 Sencore Drive

Sioux Falls, SD 57107

605-339-0100 In SD Only


*innovatively designed  
with your time in mind.*

CIRCLE 188 ON FREE INFORMATION CARD
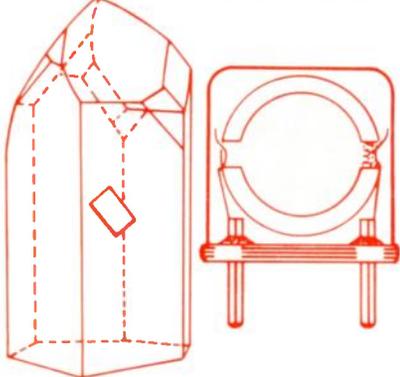
# CRYSTEK

The pulse of dependable communications

Reliability & Quality  
From Start To Finished Product



QUARTZ  
CRYSTALS/OSCILLATORS  
FOR  
ELECTRONIC — INDUSTRIAL

- Micro-Processor Control
- Computers/Modems
- Test/Measurement
- Medical

#### COMMUNICATIONS-REPLACEMENT

- Mobile/2-way/Channel Elements
- Pagers
- Marine
- Aircraft
- Telemetry
- Monitors/Scanners

AMATEURS

- CB
- Hobbist
- Experimenter

- COST EFFECTIVE
- MODERATE PRICING
- FAST DELIVERY



**The Pulse of Dependable Communications**

Crystek Crystals offers their new 16 page FREE catalog of crystals and oscillators. Offering state-of-the-art crystal components manufactured by the latest automated technology. Custom designed or "off the shelf." Crystek meets the need, worldwide. Write or call today!

**CRYSTEK CRYSTALS**

2351/2371 Crystal Dr. • Ft. Myers, FL 33907  
P.O. Box 06135 • Ft. Myers, FL 33906-6135

**TOLL FREE 1-800-237-3061**  
(813) 936-2109 • TWX 510-951-7448

CIRCLE 198 ON FREE INFORMATION CARD

# SERVICE CLINIC

## Quirks and queerities

THE TERM "QUEERITY" IS A SNIGLET meaning something queer and unusual. I've found my share of queerities when working on radios and TV's, so let's look a few of the tougher ones that I've had the (dis)pleasure of troubleshooting over the years.

One of my first queerities was a boat-anchor TV chassis having a queer sound. It wasn't actually oscillating, but it sounded as if it were on the verge of breaking into shrieks and whistles. Bridging all the filter and bypass capacitors didn't accomplish anything, but bridging the powerline bypass capacitor (which had nothing to do with the signal circuits) cured the problem. So I replaced the cabinet and sent it back to the customer. Although I never did figure out why the line bypass caused the instability there was no doubt that it did and the set was still working years after I made the "repair."

That case is typical of the hundreds that I've worked on since, where some component that can't possibly be the problem turns out to be the culprit. Of course, it's really impossible for unrelated components to affect circuit operation. Usually, if you trace a circuit carefully enough you'll eventually locate the feedback path: There must be one or the circuit wouldn't be oscillating.

### Bad bypasses

In general, most of the queerities I've run across were caused by open or leaky bypass capacitors, which are often difficult to locate because they don't necessarily create the same problems and conditions each and



JACK DARR,  
SERVICE EDITOR

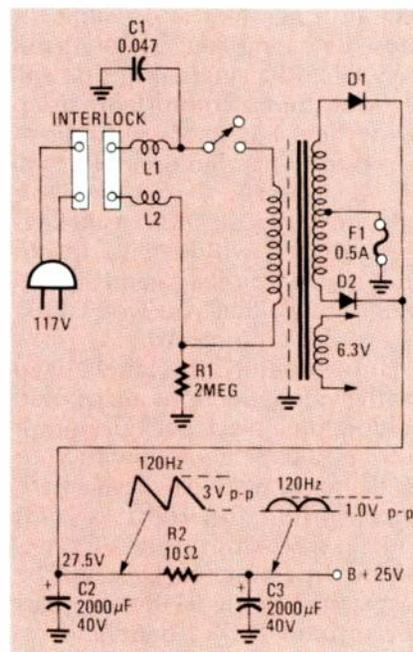


FIG. 1

every time. Bypass capacitors are in effect filters, whose job it is to remove unwanted signals from wiring before they can flow into other circuits. A defective bypass can allow signals to flow where they don't belong, resulting in mysterious oscillations, squeals, gurgles, or other strange sounds, and possibly video disturbances. For example, an open AGC bypass capacitor can cause oscillation if it permits signals to get into the grid or base circuit of the following amplifier stage.

Video problems caused by defective bypass capacitors are handled somewhat differently because you usually can see the problems they cause right on the TV screen. One of the easiest and

*continued on page 89*

# NEW LIT

**TEST EQUIPMENT CATALOG**, is a letter-sized, two-color, 377-page book, addressed to all new and used test-equipment needs. It includes amplifiers, distortion analyzers, avionics, telecommunication, filters, signal and sweep generators, transistor and tube testers, logic analyzers, calibration equipment, phase/synchro/resolvers, signal conditioning, microwave components, environmental test, and many others. Photos of the equipment offered are sharp and clear. The catalog is available upon request from **Tucker Electronics Company**, 1717 Reserve, Garland TX 75042.

CIRCLE 20 ON FREE INFORMATION CARD

**QUARTZ CRYSTAL CATALOG #30**, is 5½ × 8½ inches, 11 pages, and covers crystal units in both fundamental and high-frequency overtone modes, microprocessor crystals, scanner crystals, marine crystals, sockets, holders, amateur-band crystals, and CB crystals—both standard and non-standard. It is available on request from **Jan Crystals**, 2400 Crystal Drive, P.O. Box 06017, FL 33906-6017.

CIRCLE 21 ON FREE INFORMATION CARD

**FULL-LINE CATALOG**, letter size, includes the latest in instruments for testing video, audio, components, and cable systems. Also waveform analyzers, IEEE instruments, and a complete line of instrument accessories. Complete specifications are given for all products, along with application information on each product, including nine all-new instruments exclusively designed with the technician's precious time in mind. Available free from **Sencore Electronics**, 3200 Sencore Dr., Sioux Falls, SD 57107.

CIRCLE 22 ON FREE INFORMATION CARD

## Exclusive, triple patented dynamic cap and coil analyzing . . . guaranteed to pinpoint your problem every time or your money back



with the all new LC75 "Z METER 2"  
Capacitor Inductor Analyzer  
Patented \$995

The "Z METER" is the only LC tester that enables you to test all capacitors and coils dynamically — plus, it's now faster, more accurate, and checks Equivalent Series Resistance (ESR) plus small wire high resistance coils.

**Eliminate expensive part substitution and time-consuming shotgunning** with patented tests that give you results you can trust every time. Test capacitor value, leakage, dielectric absorption, and ESR dynamically; with up to 600 volts applied for guaranteed 100% reliable results — it's exclusive — it's triple patented.

**Save time and money** with the only 100% reliable, in- or out-of-circuit inductor tester available. Dynamically test inductors for value, shorts, and opens, automatically under "dynamic" circuit conditions.

**Reduce costly parts inventory** with patented tests you can trust. No more need to stock a large inventory of caps, coils, flybacks, and IHVTs. The "Z METER" eliminates time-consuming and expensive parts substituting with 100% reliable LC analyzing.

**Turn chaos into cash** by quickly locating transmission line distance to opens and shorts to within feet, in any transmission line.

**Test troublesome SCRs & TRIACs easily and automatically** without investing in an expensive second tester. The patented "Z METER 2" even tests SCRs, TRIACs, and High-Voltage Diodes dynamically with up to 600 volts applied by adding the new SCR250 SCR and TRIAC Test Accessory for only \$148 or FREE OF CHARGE on Kick Off promotion.

To try the world's only Dynamic LC Tester for yourself, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

**SENCORE**  
3200 Sencore Drive  
Sioux Falls, SD 57107  
605-339-0100 In SD Only

*innovatively designed  
with your time in mind.*

CIRCLE 189 ON FREE INFORMATION CARD

# NEW IDEAS

## Audible logic tester

A LOGIC TESTER WITH AN AUDIBLE INDICATOR can be handy when troubleshooting or testing a crowded circuit board. It allows you to keep your eyes on the circuit, rather than on an LED on the tester. The project described in this article is just such a tester. It provides an audible indication of the logic level of the signal presented to its input. A logic high is indicated by a high tone, a logic low is indicated by a low tone, and oscillation is indicated by an alternating tone. The input is high impedance, so it will not load down the circuit under test. It can be used to troubleshoot TTL or CMOS logic.

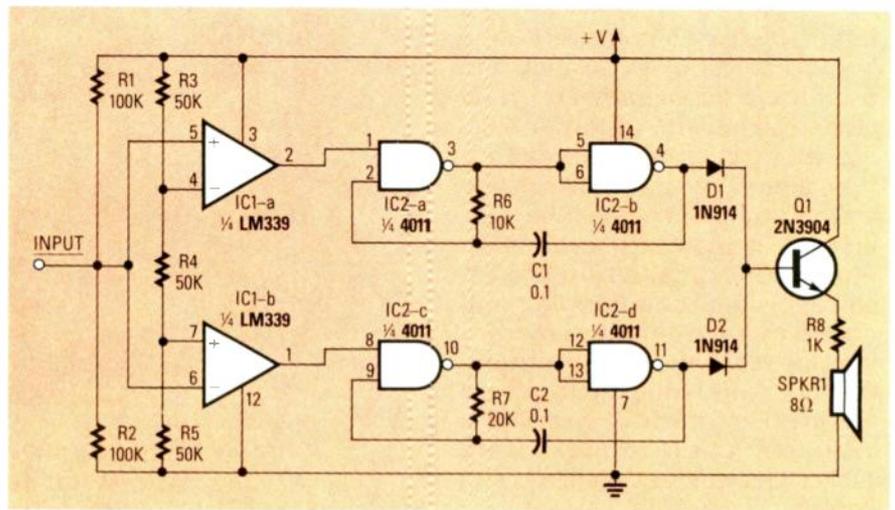


FIG. 1

## Choose from 30 Career Opportunities

Get Your Specialized Associate Degree or Career Diploma at Home in Spare Time

Without attending college and with no previous experience, you can train for a money-making career. Send for free facts and color brochure on employment opportunities in the field that interests you most. See how easy it is to train at home for a great new career or advancement on your present job.



**CALL TOLL FREE 1-800-228-5300** Dept. DES87  
CALL ANYTIME—Operators to take your call 24 hours a day, 7 days a week. No cost. No obligation. No salesman will visit you.

OR MAIL COUPON TODAY! 495ZA

**ICS** International Correspondence Schools  
Dept. DES87, Scranton, PA 18515

Please send me free facts, color brochure and full information on how I can study at home for the career I have chosen.

CHECK ONE BOX ONLY!

### ASSOCIATE IN SPECIALIZED BUSINESS DEGREE PROGRAMS

- Business Management
- Accounting
- Business Management with option in Finance
- Business Management with option in Marketing

### ASSOCIATE IN SPECIALIZED TECHNOLOGY DEGREE PROGRAMS

- Civil Engineering Technology
- Mechanical Engineering Tech
- Electrical Engineering Tech
- Electronics Technology

### CAREER DIPLOMA PROGRAMS

- High School
- Auto Mechanics
- Surveying & Mapping
- Drafting
- Air Conditioning & Refrigeration
- Wildlife/Forestry Conservation
- Police Sciences
- Diesel Mechanics
- Electrician
- Small Business Management
- Gun Repair
- Electronics
- Microcomputer Repair
- Bookkeeping
- Art
- Motorcycle Repair
- Catering/Gourmet Cooking
- Computer Programming
- Fitness & Nutrition
- TV/VCR Repair
- Photography
- Journalism/Short Story Writing

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. # \_\_\_\_\_

City/State \_\_\_\_\_ Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

A Subsidiary of National Education Corporation

CIRCLE 197 ON FREE INFORMATION CARD



THE MOST POPULAR WIRE-WOUND CB ANTENNAS IN THE WORLD

Because...they perform!

### FACT

"When CB was legalized in England, 'Firestik' antennas were barred from sale because the emitted signal was too strong. Fortunately, no other country, including the U.S., limits antenna efficiency."

YOU CAN HAVE SECOND BEST OR, 'Firestik'!

Call or Write for FREE Catalog

'Firestik' Antenna Company  
2614 East Adams  
Phoenix, Arizona 85034  
(602) 273-7151

MILLIONS OF SATISFIED OWNERS

CIRCLE 100 ON FREE INFORMATION CARD

ELECTRONIC COMPONENTS CATALOG  
... yours FREE by dialing

1-800-992-9943

In Texas: 817/ 483-4422

Call Today for your FREE subscription to the 1987 Mouser Electronics Catalog. Contains 176 pages featuring over 16,000 in-stock, quality electronic components.

..PLUS..Mouser's proven service and prompt delivery. (Outside U.S.A., Send \$2.)



MOUSER ELECTRONICS  
2401 Hwy 287 North  
Mansfield, Texas 76063

DISTRIBUTION CENTERS NATIONWIDE

CIRCLE 117 ON FREE INFORMATION CARD

## The circuit

A schematic of the circuit is shown in Fig. 1. The input section determines whether the logic level is high or low, and enables the appropriate tone generator; it consists of two sections of an LM339 quad comparator. One of the comparators (IC1-a) goes high when the input voltage exceeds 67% of the supply voltage. The other comparator goes high when the input drops below 33% of the supply. Resistors R1 and R2 ensure that neither comparator goes high when the input is floating or between the threshold levels.

The tone generators consist of two gated astable multivibrators. The generator built around IC2-a and IC2-b produces the high tone. The one built around IC2-c and IC2-d produces the low tone.

Two diodes, D1 and D2, isolate the tone-generator outputs. Transistor Q1 is used to drive a low-impedance speaker.

The tester can be built on a small piece of perforated construction board; a PC board could also be used, if desired. Layout is not critical. The completed board should be mounted in a case. The size of its case will most likely be determined by speaker's size.

Two notes on the IC's: The 4011 is a CMOS device. As with all other CMOS devices, extra care should be exercised in handling to avoid subjecting the IC to damaging static electricity. Also, all unused inputs on the LM339 should be tied to ground.

The tester is designed to draw its power from the circuit under test. Therefore, the power and ground leads should be terminated by small alligator clips. Connect a spare multimeter probe to the tester's input and you are all set.

Connect the power-supply lead to the positive supply rail of the circuit under test. Connect the ground lead to the circuit-under-test's ground rail. At this point, the tester should be silent. Now, touch the probe tip to the circuit's positive supply rail. The tester should produce a high-pitched tone. Next, touch the probe to the ground rail. The tester should produce a low-pitched tone. If all is well, your tester is ready for use.

—Philip L. Kane

## Analyze defective waveforms faster, more accurately, and more confidently — every time or your money back



with the SC61 Waveform Analyzer  
Patented \$2,995

If you value your precious time, you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you. 10 times faster, 10 times more accurate, with zero chance of error.

**End frustrating fiddling with confusing controls.** Exclusive ultra solid ECL balanced noise cancelling sync amplifiers, simplified controls, and bright blue dual trace CRT help you measure signals to 100 MHz easier than ever.

**Accurately and confidently measure waveforms from a tiny 5 mV all the way to a whopping 3,000 V without hesitation** with patented 3,000 VPP input protection — eliminates expensive "front end" repairs and costly equipment downtime.

**Make only one circuit connection and push one button for each circuit parameter test:** You can instantly read out DC volts, peak-to-peak volts and frequency 100% automatically with digital speed and accuracy. It's a real troubleshooting confidence builder.

**Confidently analyze complex waveforms fast and easily.** Exclusive Delta measurements let you intensify any waveform portion. Analyze glitches, interference signals, rise or fall times or voltage equivalents between levels; direct in frequency or microseconds.

**Speed your digital logic circuit testing.** Analyzing troublesome divide and multiply stages is quicker and error free — no time-consuming graticule counting or calculations. Simply connect one test lead to any test point, push a button, for test of your choice, for ERROR FREE results.

To see what the SC61 can do for your troubleshooting personal productivity and analyzing confidence, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

**SENCORE**

3200 Sencore Drive  
Sioux Falls, SD 57107  
605-339-0100 In SD Only

*innovatively designed  
with your time in mind.*

CIRCLE 190 ON FREE INFORMATION CARD

Get A Complete Course In

# ELECTRONIC ENGINEERING

8 volumes, over 2000 pages, including all necessary math and physics. 29 examinations to help you gauge your personal progress. A truly great learning experience.

Prepare now to take advantage of the growing demand for people able to work at the engineering level.

Ask for our brochure giving complete details of content. Use your free information card number, or write us directly. **\$99.95**, Postage Included. Satisfaction guaranteed or money refunded.



**Banner  
Technical  
Books, Inc.**

1203 Grant Ave.  
Rockford, IL 61103

CIRCLE 191 ON FREE INFORMATION CARD

## Be an FCC LICENSED ELECTRONIC TECHNICIAN!

Earn up to \$30 an hour and more!

Learn at home in spare time. No previous experience needed.

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS** - You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

### COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept 90  
P.O. Box 2223, San Francisco, CA 94126

Please rush **FREE** details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

# DESIGNER'S NOTEBOOK

## Very simple delay circuits

**ROBERT GROSSBLATT,**  
CIRCUITS EDITOR

I'VE GOTTEN SEVERAL LETTERS ASKING for a simple circuit that will accept a trigger pulse, wait a specified length of time, and then output another pulse. Now, there are almost as many ways to design delay circuitry as there are uses for it; how you go about such a design depends on the particulars of your application. But if precision is

- What clock frequencies do you have available?
- What degree of accuracy do you want?

Once you know exactly what your circuit needs, you can figure out which of those IC's, or some similar one, will work best for your particular application.

The 4017 Johnson counter will

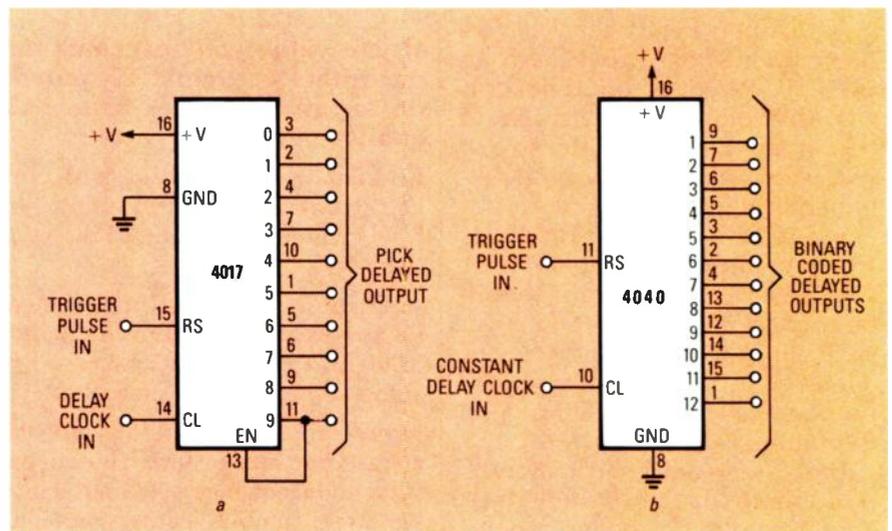


FIG. 1

what you have in mind, nothing works better than a stand-alone counter.

Two stand-alone counter "circuits" are shown in Fig. 1. Actually, we are being generous in calling them circuits because there is nothing to them aside from the IC itself. Figure 1-a is a 4017 Johnson counter; Figure 1-b is a 4040 binary counter. The choice of which one to use for your delay circuit depends on your answers to three interrelated questions:

- How much of a delay do you want?

give you a very accurate time delay for up to 10 clock pulses. All you have to do to create a delayed pulse is tie the ENABLE input to the 9 output, and your clock to—you guessed it—the CLOCK input. When you first apply power, the counter will advance and as soon as the 9 output goes high, it will freeze the count. The 4017 will stay in that condition until your trigger pulse comes along to zap the RESET pin (pin 15). That pulse will reset the counter, which will then count up to 9 and freeze again. Once the count starts you can pick off your

delayed pulse from any of the other output pins; the choice of pins is determined by the amount of delay needed.

By using a binary counter like the 4040, you can generate a much longer delay. Since there's no enable pin available, things have to be done a bit differently. The IC is set up to start counting as soon as power is applied. The trigger pulse will cause the device to reset to zero and you can pick off your delayed pulse at any of the device's output pins.

The price you pay for simplicity is that the circuit you hang on the output has to be set to ignore pulses until the trigger pulse is generated. That is because the 4040 will always be counting through its full range and your selected output will be high once per complete count. That problem can be solved with some additional gating, but the idea here is to keep the circuit as simple as possible.

In any event, those suggestions are just that—suggestions. More than likely you can think of lots of

simple alternatives that are even more flexible than these.

### Product of the month

Every so often I run across a product that's not only reasonably priced and extremely handy, but helps eliminate all kinds of hassles as well. From now on, when I find one of those things, I'll be awarding it the soon-to-be-famous "Silver Soldering Iron."



FIG. 2

I probably won't be bestowing that honor too often, because there's a lot of junk out there; but when I find something that's really worth honoring, I'll let you know about it.

The winner of the first Silver Soldering Iron is the *Portasol* from

The Boardworks (1077 East Edna Place, Covina, CA 91722). See Fig. 2. It's a butane-powered, pocket-sized soldering iron. Imagine, no batteries, no static electricity, no grounding problems, etc. At a list price of \$25.00, it is a really neat and inexpensive alternative to battery-powered portable soldering irons, and you don't have to worry about running out of power before you get to the last connection.

The *Portasol* can be refilled with any ordinary cigarette-lighter butane cartridge and gives about an hour of operation per charge. There are several different tips available for the unit, and the heat can be adjusted with a twist valve in much the same way a cigarette-lighter flame is regulated.

I've been using my *Portasol* for a few months and it works perfectly. It's a well-built realization of a good idea. I owe my living to electricity, but this is one time when gas is better. If you're in the market for a portable iron, get one of those. They're cheaper, faster, and much more convenient. **R-E**

Send Purchase Order  
 Check, Money Order, or C.O.D.  
 or Call Toll Free  
**800-223-0826**  
 in N.Y. State (212) 865-5580

#1 IN CABLE BOXES  
 SPECIAL!

### JERROLD CORDLESS CABLE TV CONVERTERS

MODEL STARCOM-460

\$99<sup>95</sup>

ANY QUANTITY

- Instant channel recall
- Programmable to go on at a particular channel and off automatically
- Compatible with descramblers

MODEL DRX3-105/400

\$69<sup>95</sup>

- Volume control
- 68 channels
- Mute control
- Automatic line tuning

MODEL JRZ/450

\$69.95/10 lot

\$79.95 ea

- 66 channels
- Automatic line tuning
- A/B switch option

VOLUME CONTROL

\*ADD \$5.00 FOR VISA OR MASTER CARD

JERROLD CORDLESS CABLE TV CONVERTER

MODEL DRX3-105/400

\$69<sup>95</sup>

- 58 channels
- Remote channel changing
- Remote on/off switch
- Remote line tuning

JERROLD CORDLESS CABLE TV CONVERTER

MODEL JRZ/450

\$69.95/10 lot

\$79.95 ea

- 66 channels
- Automatic line tuning
- A/B switch option

JERROLD CORDED CABLE TV CONVERTER

MODEL JRX3-105

\$29.95/10 up

\$39.95/6-9  
\$49.95/1-5

"THE RABBIT"

VIDEO MULTIPLYING SYSTEM

TR-7000

\$51<sup>95</sup>

\$59.95/6-11  
\$69.96/1-5

12 up

IT'S LIKE HAVING A VCR IN EVERY ROOM

OMNITRON

ELECTRONICS

770 Amsterdam Ave., New York, NY 10025

SHIPPING CHARGES

For Orders	Add
\$25-100	\$6.50
\$100-500	\$8.50
\$500-750	\$10.50
\$750 and up	\$20.00

Write for  
FREE CATALOG  
 136 Pages


MASTER CARD    VISA

CIRCLE 110 ON FREE INFORMATION CARD

SEPTEMBER 1987

35
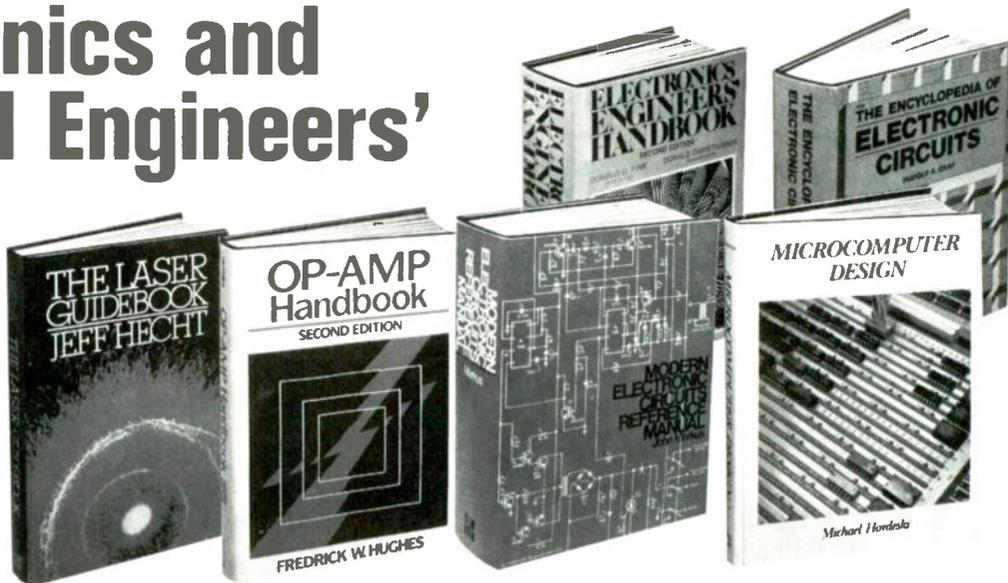
# Join the Electronics and Control Engineers' Book Club®



**ADVANCED DIGITAL COMMUNICATIONS: Systems and Signal Processing.** Edited by K. Feher. 768 pp., 436 illus. Emphasizes the newest advances and developments in telecommunications systems and networks. Chapters on subjects such as ISDN, speech coding algorithms, digital speech interpolation systems and interference are all written by international authorities to give you on-the-job expertise.  
583801-X Pub. Pr., \$59.95 Club Pr., \$42.50

**ELECTRONICS ENGINEERS' HANDBOOK, Second Ed.** Edited by D. G. Fink & D. Christiansen. 2,272 pp., 2,189 illus. This updated and enlarged edition covers all the latest knowledge in the field, including new advances in integrated circuits, pulsed and logic circuits, laser technology, telecommunications, and much more.  
209/812 Pub. Pr., \$89.00 Club Pr., \$61.50

**MICROCONTROLLERS IN PROCESS AND PRODUCT CONTROL.** By A. A. Berk. 211 pp., 68 illus. A practical guide filled with design information on a variety of microcontrollers used in process control, it will help you choose the right technology for a given application. There is comprehensive coverage of the basics along with many examples and new ideas.  
049/009 Pub. Pr., \$39.95 Club Pr., \$29.95

**THE LASER GUIDEBOOK.** By J. Hecht. 368 pp., 109 illus. This book covers the operating principles, characteristics and applications of all commercially available lasers. It will help you find the specific laser that best meets your requirements.  
277/338 Pub. Pr., \$49.50 Club Pr., \$37.50

**TROUBLESHOOTING ELECTRONIC EQUIPMENT WITHOUT SERVICE DATA** By R. G. Middleton. 303 pp., 162 illus. and tables. Packed with charts, diagrams, and case histories, this practical handbook shows you how to pinpoint defective electronic circuitry when no service data is available.  
583134-1 Pub. Pr., \$27.95 Club Pr., \$19.95

**ANTENNA ENGINEERING HANDBOOK, Second Ed.** Edited by R. C. Johnson and H. Jasik, with contributions by 57 recognized authorities. 1,408 pp., 946 illus. This widely acclaimed Handbook gives you the guidance you need to solve problems in antenna design and application.  
322/910 Pub. Pr., \$110.00 Club Pr., \$68.00

**AUTOMATIC CONTROL SYSTEMS, Fifth Ed.** By B. C. Kuo. 736 pp., illus. Provides an overview of automatic control systems, including in-depth coverage of classical control techniques, optimal control theory, and analog and digital control system design. This updated edition discusses the latest ideas on the use of computers to design control systems and as components of such systems.  
583706-4 Pub. Pr., \$48.00 Club Pr., \$33.50

**OP-AMP HANDBOOK, Second Ed.** By F. W. Hughes. 320 pp., 231 illus. Organized for on-the-job reference, this handbook covers all facets of op-amps, from stability and protection to signal processing using op-amps. Includes a collection of over 60 practical circuits for a variety of applications, procedures, and experiments.  
583651-3 Pub. Pr., \$36.35 Club Pr., \$27.50

**CHOOSING AND USING CMOS.** By M. J. Walsh. 304 pp., 155 illus. Offers a comprehensive overview of the semiconductor technology used . . . gives practical advice on circuit techniques to make your job easier. Specifications, characteristics and applications are included.  
679/576 Pub. Pr., \$35.50 Club Pr., \$24.95

**McGraw-Hill Concise Encyclopedia of Science and Technology.** Editor-in-Chief S. P. Parker and the Staff of the McGraw-Hill Encyclopedia of Science and Technology. 2,065 pp., 1,600 illus. This volume serves every need for understanding today's science and technology. Written by over 3,000 of the world's topmost experts, including 19 Nobel Prize winners, it covers 75 disciplines from Acoustics to Zoology.  
454/825 Pub. Pr., \$98.50 Club Pr., \$63.99

**MICROPROCESSORS IN INSTRUMENTATION AND CONTROL.** By S. A. Money. 246 pp., 148 illus. Provides the design procedures and applications data you need to create effective, high quality microprocessor-based systems. There is thorough coverage of programming, arithmetic and logic operations, parallel input-output, serial input-output, hardware design, analog digital conversion and much more.  
427/070 Pub. Pr., \$39.50 Club Pr., \$29.50

**AMERICAN ELECTRICIANS' HANDBOOK, Eleventh Ed.** By T. Croft and W. Summers. 1,824 pp., 1,560 illus. This newly updated handbook shows you how to select, install, maintain, and operate all the latest electrical equipment and wiring. It includes the most recent code requirements, basic formulas, and a wealth of circuit diagrams and illustrations.  
139/326 Pub. Pr., \$64.50 Club Pr., \$46.50

**POWER ELECTRONIC CONVERTERS: AC/DC Conversion.** By G. Segui. 362 pp., 144 illus. Provides a clear overview of rectifier circuits, which convert ac power to dc power. All types of rectifiers are covered, including half-wave diode, diode bridge, half-wave thyristor, thyristor bridge, and combinations, with over a hundred useful circuit diagrams, waveform diagrams, and reference tables.  
560/811 Pub. Pr., \$34.95 Club Pr., \$25.95

**MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL.** By J. Markus. 1,264 pp., 3,666 circuit diagrams. Complete with values of components and suggestions for revisions—plus the original source of each circuit in case you want additional performance or construction details.  
404/461 Pub. Pr., \$82.50 Club Pr., \$61.50

New Members!  
Take any one of these great professional books for only **\$289** as a premium with your first selection!

Spectacular values up to **\$110.00**

**HANDBOOK OF ELECTRONIC TABLES AND FORMULAS**  
Sixth Edition  
256 pages, illustrated. 583804-4

Up-to-date mathematical tables and electronic formulas in a convenient desk reference that you'll find indispensable. Included are basic formulas, constants, government industry standards, symbols and codes, service data, and more. The handbook also has new sections describing how to do your calculations on a computer, and complete computer programs.

**A \$19.95 Value — Yours ABSOLUTELY FREE when you join!**

**TELEVISION ENGINEERING HANDBOOK.**—By K. B. Benson. 1,478 pp., 1,091 illus. Packed with the technical information and know-how you need to design, operate and maintain every type of TV equipment in current use.

047/790 Pub. Pr., \$89.50 Club Pr., \$62.50

**STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, Twelfth Ed.**

By D. G. Fink and H. W. Beaty. 2,248 pp., 1,863 illus. and tables. Written and compiled by 115 leading experts, this is the essential reference for electrical engineers. It covers the basics including circuits, telecommunications, power distribution, and electrical standards, as well as the latest technology.

209/758 Pub. Pr., \$86.50 Club Pr., \$59.50

**THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS.** By R. Graf. 760 pp., 1,256 illus.

This large volume provides circuits for virtually every type of application in 98 different categories. Each has a clear and concise explanatory text accompanying it.

583265-8 Pub. Pr., \$60.00 Club Pr., \$43.50

**ELECTRONIC SPEECH RECOGNITION: Techniques, Technology, and Applications.** Edited by G. Bristow. 395 pp., 117 illus.

A complete sourcebook providing an introduction to voice recognition, an overview of the devices and systems now available, a list of vendors, and a collection of applications examples from companies that have used speech recognition technology.

079/137 Pub. Pr., \$48.50 Club Pr. \$35.50

**INTRODUCTION TO RADAR SYSTEMS.** By M. I. Skolnik. 2nd Ed. 698 pp., 244 illus.

Covering every radar: fundamental and all important changes this EE text exposes you fully to the systems themselves—and to their applications! Topics include radar equation CW and frequency-modulated radar MTI, pulse doppler, tracking radar, receivers, displays, duplexers, noise, and more.

579/091 Pub. Pr., \$51.95 Club Pr., \$38.95

**MICROCOMPUTER DESIGN.** By M. Hordeski. 406 pp., illus.

Emphasizes the most current, cost effective methods for developing, debugging and testing all types of microprocessor products, including software and hardware

583683-1 Pub. Pr., \$42.67 Club Pr., \$29.95

**DESIGNING ELECTRONIC CIRCUITS.** By R. G. Middleton. 351 pp. 192 illus.

Covers virtually every category of circuits commonly used. This practical manual provides the basic design procedures, tables and formulas vital to effective electronic circuit design. Plus over 60 start-to-finish procedures are featured along with scores of computer programs to help you design and analyze electronic circuits.

583673-4 Pub. Pr., \$36.95 Club Pr., \$27.50

**Be sure to consider these important titles as well!**

**OPERATIONAL AMPLIFIERS AND LINEAR INTEGRATED CIRCUITS, Third Ed.** By R. F. Coughlin and F. F. Driscoll

583754-4 Pub. Pr., \$34.95 Club Pr., \$25.95

**68000 MICROPROCESSOR: ARCHITECTURE, SOFTWARE & INTERFACE TECHNIQUES.** By W. A. Triebe & A. Singh.

583683-1 Pub. Pr., \$42.67 Club Pr., \$29.95

**DESIGNING DIGITAL FILTERS.** By C. S. Williams

583627-0 Pub. Pr., \$43.67 Club Pr., \$30.95

**APPLICATIONS IN ARTIFICIAL INTELLIGENCE.** By S. J. Andriole.

583715-3 Pub. Pr., \$49.95 Club Pr., \$34.95

**THE FOURIER TRANSFORM AND ITS APPLICATIONS, Second Ed., Revised.** By R. N. Bracewell

070/156 Pub. Pr., \$48.95 Club Pr., \$33.95

**DIGITAL FILTERS AND SIGNAL PROCESSING.** By L. B. Jackson.

583710-2 Pub. Pr., \$35.95 Club Pr., \$26.95

**MICROPROCESSOR SUPPORT CHIPS.** By T. J. Byers

095/183 Pub. Pr., \$44.50 Club Pr., \$35.25

**INDUSTRIAL ROBOTICS.** By M. P. Groover, R. N. Nagel and N. G. Odrey

249/89X Pub. Pr., \$39.95 Club Pr., \$28.95

**THE MCGRAW-HILL COMPUTER HANDBOOK.** By H. Helms

279/721 Pub. Pr., \$86.50 Club Pr., \$54.50

**MICROLITHOGRAPHY: PROCESS TECHNOLOGY FOR IC FABRICATION.** By D. Elliott

193/045 Pub. Pr., \$42.00 Club Pr., \$29.50

**RC ACTIVE FILTER DESIGN HANDBOOK.** By F. W. Stephenson

583350-6 Pub. Pr., \$44.95 Club Pr., \$33.75



**FOR FASTER SERVICE IN ENROLLING CALL TOLL-FREE 1-800-2-MCGRAW**

**MAIL THIS COUPON TODAY**

**McGraw-Hill Book Clubs  
Electronics and Control Engineers'  
Book Club®**

PO Box 582 Hightstown, NJ 08520 9959

Please enroll me as a member and send me the two books indicated plus the HANDBOOK OF ELECTRONIC LABELS AND FORMULAS. I am to receive one book for just \$2.89, the other at the discounted member's price plus local tax, shipping and handling charges. I agree to purchase a minimum of two additional books during my first year of membership as outlined under the Club plan described in this ad. I understand that a shipping and handling charge is added to all shipments.

Your FREE Handbook	
583804-4	
Write Code No. of the \$2.89 selection here	Write Code No. for the First selection here
<input type="text"/>	<input type="text"/>

Signature \_\_\_\_\_

Name \_\_\_\_\_

Address Apt. # \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. Foreign member acceptance subject to special conditions. E-33891

**Why YOU should join now!**

■ **BEST AND NEWEST BOOKS IN YOUR FIELD** — Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

■ **BIG SAVINGS** — Build your library and save money too! Savings ranging up to 40% or more off publishers' list prices.

■ **BONUS BOOKS** — You will immediately begin to participate in our Bonus Book Plan that allows you savings up to 70% off the publishers' prices of many professional and general interest books!

■ **CONVENIENCE** — 12-14 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and Alternate Selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an Alternate Selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three books (including your first selection) during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the first selection plus two additional books.

**Other McGraw-Hill Book Clubs:**  
Architects' Book Club • Byte Book Club • Chemical Engineers' Book Club  
• Civil Engineers' Book Club • Mechanical Engineers' Book Club

For more information, write to:  
McGraw-Hill Book Clubs, P.O. Box 582, Hightstown, New Jersey 08520-9959

# ARM YOURSELF AGAINST STATIC



# WITH NTE'S PATENTED FIELD SERVICE KIT.

LOOK FOR THE FULL LINE OF QUALITY NTE  
REPLACEMENT PARTS AND PRODUCTS:

Static electricity is a real hazard to sensitive electronic equipment. Now you can protect valuable components in the field and in the plant with NTE's new Field Service Kit.

Our Kit includes everything you need to keep your equipment free of static — a 24" x 24" table top work mat, wrist strap with 8' coil cord, 15' clip-on grounding line and anti-static component storage bags. Both the wrist strap cord and grounding cord contain integral current limiting resistors.

Unlike other kits currently on the market, NTE's patented\* three-



- Transistors
- Thyristors
- Integrated Circuits
- Rectifiers and Diodes
- High Voltage Multipliers and Dividers
- Optoelectronic Devices
- Zeners
- Microprocessors and Support Chips
- Memory ICs
- Thermal Cut-Offs
- Bridge Rectifiers
- Unijunctions
- RF Transistors
- Microwave Oven Rectifiers
- Selenium Rectifiers
- Flameproof Resistors
- Wire Ties
- Electrolytic Capacitors
- Static Control Products

layer construction produces controlled static drain, eliminating the danger of sparking and the chance of additional component failure during the repair operation. The static-dissipative, vinyl work surface is durable and its bright green color enhances visibility. The entire Kit folds down into a compact unit and comes with its own zip-close bag.

Look for NTE's new Field Service Kit and our other static control products — including our anti-static foam, for shipping and storing equipment, and separately packaged wrist straps — at your local NTE distributor.

\*Patent issued November 8, 1983.  
U.S. Patent No. 4,414,260.



**NTE ELECTRONICS, INC.**

44 FARRAND STREET • BLOOMFIELD, NEW JERSEY 07003  
(Outside N.J.) 1-800-631-1250 • (N.J. only) 1-800-624-2624

For more information or the name of your local distributor, call or write NTE.

CIRCLE 71 ON FREE INFORMATION CARD

# BUILD THIS

THERE ARE MANY INSTANCES IN VIDEO work when it is desirable or necessary to modify a video signal in one way or another. In the home, modifying a video signal usually means a simple color correction attained by adjusting the TV's tint and color controls. But for professional or artistic video-signal control, a much-wider range of signal modification must be available. For example, there must be a way to correct contrast when the color is OK but the signal's luminance component is weak. Another modification might include deliberate distortions of the signal

many applications, and is also great fun—it can be more fun than a video game. Some of its serious applications are:

1. **Video Recording**
  - a. Tint correction
  - b. Chroma boost/cut
  - c. Luminance/synch boost and cut
  - d. Additions of special effects to recordings
  - e. Posterization and solarization for effects and titling
2. **Photographic Uses**
  - a. Viewing color negatives as positives (a separate camera is required)

(0–4 MHz) 75-ohm source impedance NTSC video signal having a nominal amplitude of 1 volt peak-to-peak with negative sync is applied to the system via the VIDEO IN jack. A BYPASS SWITCH is provided to bypass the system, and a VIDEO LOOP-THROUGH connection is also provided for loop-through setups. Switches enable AC or DC coupling, and 75 ohm or Hi-Z (high impedance) input, which is useful in loop-through applications or where another 75 ohm device is already terminating the input line.

A video amp boosts the input up to 3

## VIDEO EFFECTS



## GENERATOR

*Color correction, deliberate distortion, artistic picture control.  
Our video palette puts it all at your fingertips.*

**RUDOLF F. GRAF and WILLIAM SHEETS**

for the purpose of creating special effects: such as color and/or luminance reversal (positive-negative); posterization, in which the video signal is altered such that there are only a few discrete values of luminance (usually 2, 3, or 4); or solarization, in which the gray scale (luminance) is "folded" on itself, producing an eerie, surrealistic-looking picture that contains both positive and negative tones. Of course, several effects may be performed simultaneously.

Devices that provide a high degree of color control are used in virtually all major TV production facilities. Regardless what the brand name might be, technicians often refer to such a device as a *video palette*; hence, we will also call our device a video palette.

Our video palette is designed to work on any standard NTSC video signal. It has

- b. Advance predictions of the finished appearance of photographic special effects
- c. Negative inspection and analysis

### 3. **Video Production**

- a. Simulation
- b. Special effects
- c. Artistic effects

Some of the video palette's effects are shown in Figs. 1-a, 1-b, 1-c, and 1-d, and they are just a tiny sampling of what is possible. It will be evident after an hour or so of experimentation, using a video source (VCR, TV tuner, etc.) and a video monitor to observe the results, that a wide range of effects are possible by manipulating the front-panel controls.

### **How it works**

A block diagram of the video palette is shown in Fig. 2. A standard baseband

volts p-p, and at the same time inverts it so that the sync tips are positive. The video signal, which is now still unaltered but greater in amplitude and inverted, is then fed to a sync separator and a SPDT CMOS video switch.

The video switch splits the video signal into two components:

1. Synch, blanking, and burst pulses only;
2. Video and chroma information without sync, burst, or blanking.

The reason for the splitting up of the signal is to allow separate processing and treatment of the four signal components: sync, burst, luminance (black-and-white component), and chroma (color-difference). (Figure 3 shows the four components parts of a standard NTSC color signal.)

There are other reasons why it's necessary to extract the discrete signal compo-



FIG.1—THE VIDEO PALETTE'S EFFECTS CAN BE STACKED. In this black and white series, a is a normal picture, b is posterized, c has solarization added, d has negative video added.

nents. For example, the sync signal is used for timing and cannot be modified unless intentional scrambling of the picture is required. If we want an inverted (negative) picture, we cannot just reverse the phase of the whole signal, because the video monitor needs sync pulses of a given polarity; therefore, a simple inverter will not work. If we want to introduce special effects, we may want, for example, to just operate on the chroma signal and leave everything else the same. Therefore, the splitting up of the signal is obviously necessary; otherwise, improper operation of the sync and color-burst circuitry in the monitor, VCR, or TV receiver will result.

Sync and blanking are separated from the burst pulse by a lowpass filter having a cutoff frequency of 2.5 MHz and a maximum rejection frequency of 3.58 MHz.

Luminance and chrominance are separated the same way. Strictly speaking, a comb filter would be the ideal way to separate luminance and chrominance, but it would complicate construction and increase cost. For that application, simple M-derived filters do the job adequately.

### Synchronization

A switching signal to control the video splitting is derived from the original signal's sync information. A sync separator strips the horizontal and vertical sync information from the original signal. (Note that the original signal must be a legitimate NTSC signal, with the sync tips most negative. Therefore, a scrambled signal will not operate this unit.)

The horizontal sync drives a monostable multivibrator having a nominal 53-microsecond pulse width. That multivibrator drives a second multivibrator that generates a gating pulse having a nominal 10-microsecond pulse width. The 10-microsecond pulse is timed to be coincident with the blanking pulse on the original NTSC signal; it is done by adjusting the 53-microsecond multivibrator's pulse width. The 10-microsecond pulse causes the video switch to route the video signal into the sync and burst side of the switch. When the pulse is not present (during horizontal line scan), the video is routed to the video and chroma side of the switch.

Vertical sync is separated in a similar manner. A monostable multivibrator having a delay of one frame (nominally 16 microseconds) is used to trigger a second monostable multivibrator whose output is a pulse having a width of nominally 600-microseconds. That pulse should be timed to occur during vertical retrace. Therefore, the entire composite vertical blanking pulse will be gated to the sync and burst side of the video switch. (The setup of the switching circuit consists of adjusting the delays and pulse widths of the four multivibrators so as to correctly switch the sync pulses, blanking pulses, and the burst pulses to the sync and burst outputs of the video switch.)

The video switch's sync output is fed to a lowpass filter that removes the burst. It then goes to an amplitude control, and then into a summing amplifier, which reassembles the video signal.

The burst output goes to a highpass filter that eliminates the sync. Then the signal is fed to a phase-correction network and on to the burst amplifier, a differential amplifier having two outputs 180° out of phase. A potentiometer connected across both outputs functions as both a gain and polarity control: At the center position there is zero output (no burst); fully clockwise and counterclockwise, full positive or negative burst is available respectively. In that way, the burst phase and amplitude can be altered or corrected as required, independent of everything else. The burst can be varied from plus three times normal to minus three times normal. By using a negative burst phase, the monitor or TV screen will show reversed (complementary) colors. The burst is then fed to the summing amplifier for reassembly into a complete video signal.

Luminance is treated in a similar manner to that of the sync. It goes through a lowpass filter that is similar to the sync filter and is then fed through a level control to the input of the summing amplifier. There it is summed with the sync and the burst information.

Chrominance, or chroma, is extracted by a highpass filter. It is fed through a differential amplifier having positive and negative outputs. (It is similar to the burst differential amplifier.) A potentiometer allows either positive or negative amplified chroma to be fed to the summing amplifier at any desired level. That feature allows weak chroma to be amplified or inverted. Since some 2.5 MHz (or higher) luminance components will be present along with the chroma signal, the chroma control functions as a sharpness control in black and white applications. The ability of using either positive or negative burst with positive or negative chroma at first will seem redundant because negative chroma with a negative burst will yield a positive picture. However, the phase of the high-frequency luminance components will not be the same, and the total effect can be used as a sharpness control for color video.

The summing amplifier has a nominal gain of unity when the level controls for chroma, burst, sync, and luminance are about halfway open. Since the video signal was amplified by a factor of three by the input video amplifier, allowing for normal circuit losses within the video palette, about 2 volts of composite video component is present at the input of the summing amplifier. Therefore, a 2-volt peak-to-peak reassembled video signal is present at the output of the summing amplifier.

You may be wondering what we have really accomplished so far. What we now have is the ability to disassemble the video signal, control each of its four components on an individual basis, and recombine them into a new video signal.

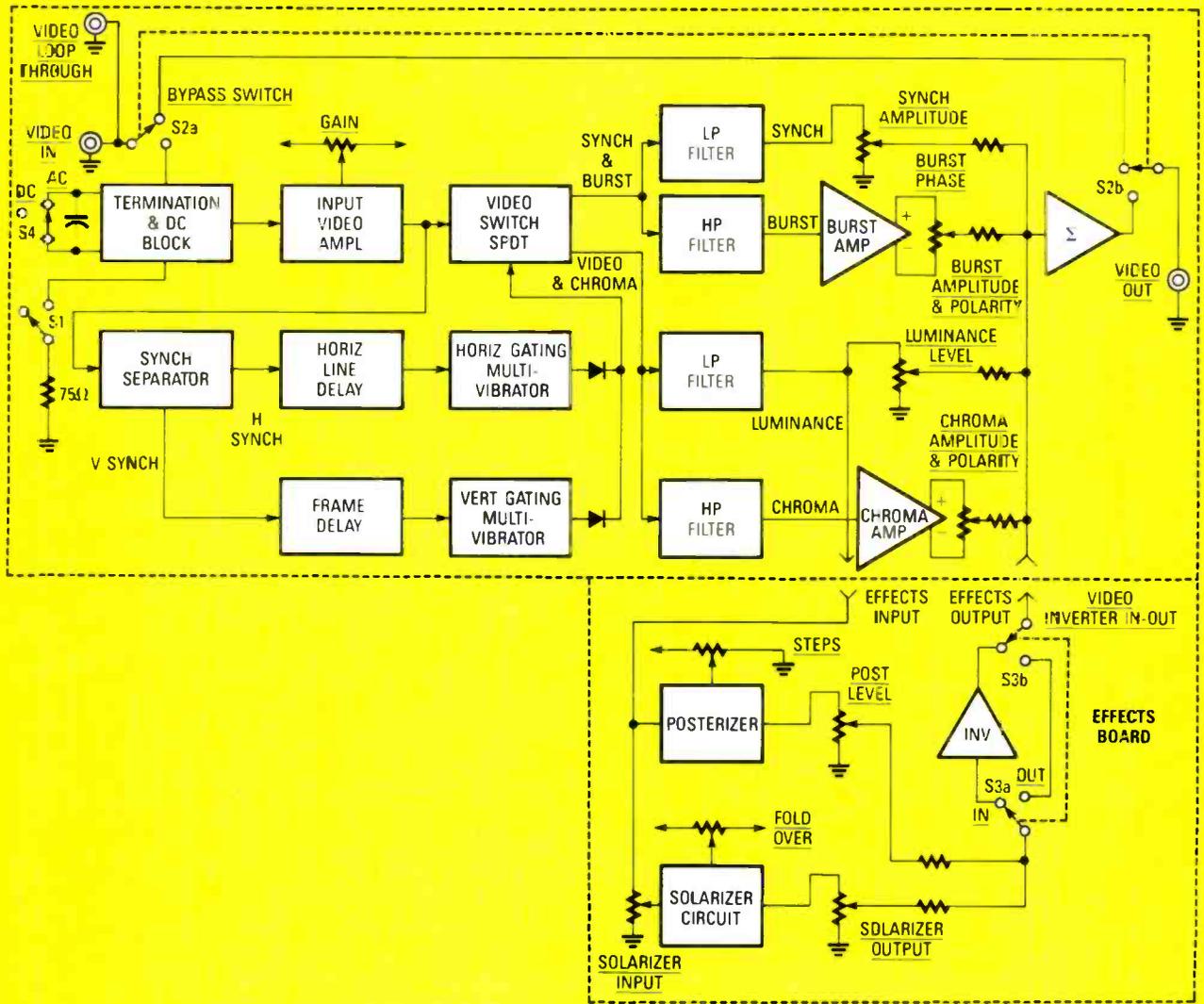


Fig. 2—THE CIRCUITS FOR THE video palette are arranged on two separate circuit boards. A bypass switch allows all functions to be instantly bypassed without having to reset the individual controls.

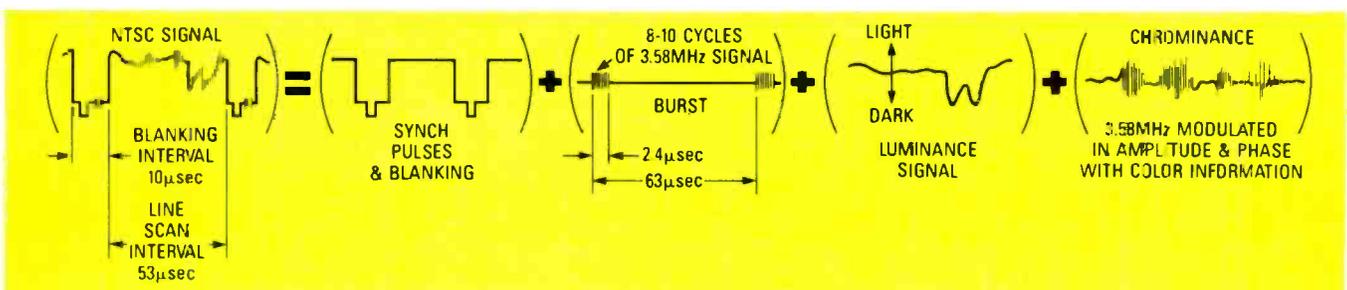


FIG. 3—AN NTSC COLOR SIGNAL has four individual components, all of which can be separately controlled by the video palette.

Depending on the settings of the controls, we might get an improved picture, a degraded picture, or an altered picture. By this method, we can custom-correct individual faults in the video signal. For all practical purposes, we have a graphic equalizer for video.

#### Analog effects

A few analog effects are incorporated in the video palette. Those are inversion, posterization, and solarization.

Inversion, shown in Fig. 4, is simply what it implies: the video signal levels are inverted about a given reference axis. For example, if zero volts represents maximum white and 1 volt represents maximum black (Fig. 4-a), passing the signal through an inverter such that the output is 1 volt when the input is zero volts, and the output is zero volts when the input is 1 volt, will produce an inverted video signal (Fig. 4-b).

Note that a true inverter would just

change the sign. For example, let us take the case of a signal at +0.5 volt, which would represent a middle gray. Ideally, if we invert a gray tone, it is gray. (Gray is its own complementary color.) However, a true inverter would give -0.5 volts output, which would be whiter than white. Therefore, we must add a DC offset of +1 volt to the output so that a zero volt input produces a +1 volt output, thereby restoring the original gray (Fig. 4-c). As shown in Fig. 4-d, that can be done by adding a

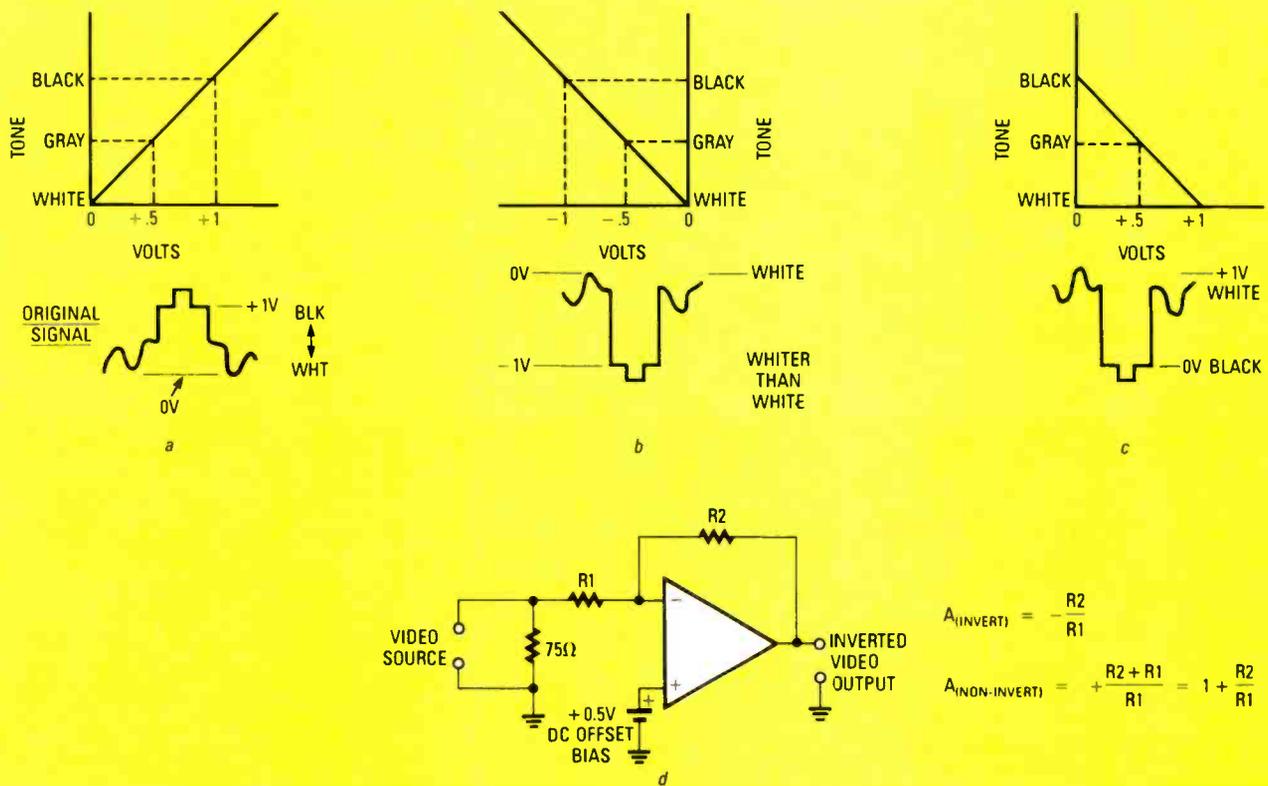


FIG. 4—SIMPLY INVERTING THE VIDEO signal (a) will result in a signal that goes whiter-than-white (b). By using a DC offset bias for the amplifier the signal-level values are restored, but the tones are reversed—white is now black (c). In d we see how the offset is applied through the amplifier's noninverting input.

DC offset level to the amplifier's input. Only +0.5 volt input is needed because the op-amp's configuration has a gain of two at the non-inverting input. ( $A + \text{INPUT} = 1 + R2/R1$ .)

Inverting the luminance signal produces a negative picture. If the original picture is black-and-white it will have the appearance of a black and white photographic negative. If the original is color, the colors will still be correct but the tones will be reversed. (Actually, since the color is really the sum of luminance and chrominance, the hues are unchanged but the saturations may be different, giving the effect described.)

In order to get a negative picture similar to a true color photographic negative (without the masking built into color negative film that is needed to make a color print), you would also invert either the chroma or the burst.

Using the correct light source, if you looked at a photographic color negative with a video camera/monitor set-up, and ran the resulting video through the video palette, you would see a positive color image. In fact, that technique is widely used by the commercial color-photo printing industry to predetermine correct color-printing exposure and filtration (light source color balance) so that the final photographic print is correct the first time. That kind of photo printing technique is known as *video analysis*.

### Posterization

Posterization is the term used to describe the process of converting a photographic or video image of a scene containing a wide range of tones into a scene containing only a few discrete tones, sometimes only two (black and white). No intermediate shading between tones are present. Commonly, four tones are used in practice: white, light gray, dark gray, and black. Colors are sometimes left in their natural state, or they may be saturated (chroma is limited to one value—maximum). In practice, a pleasing visual effect is attained by posterizing only the luminance.

The effect of posterization is shown in Fig. 5-a. Note how the shading from white to black on the ball and cylinder is changed to discrete bands of gray by posterization. Figure 5-b shows how the video ramp waveform is changed to discrete steps by the posterization. A posterized video scene has a distinct computerized or cartoon effect because there are only a few discrete values of luminance. Since a very small difference in luminance at the transition points may produce a large difference in the posterized output, small noise signals, snow, and glitches are enormously magnified, which produces a grainy effect. Although grain is usually considered objectionable, as shown in Fig. 5-c, it can be used to add an artistic effect to the picture.

### Analog to digital

Posterization is done by using an A/D converter to convert the analog video signal to a digital format, and then immediately converting back to analog.


A simplified approach to posterization is shown in Fig. 6. Four comparators are biased with a reference voltage obtained from a resistance voltage divider ( $R_x \times 4$ ). The amplifiers are biased so that amplifier A4 has +1 volt, A3 has + $\frac{3}{4}$  volt, A2 has + $\frac{1}{2}$  volt, and A1 has + $\frac{1}{4}$  volt on their inverting inputs. All four non-inverting inputs are connected to a nominal zero-volts (white) to 1-volt (black) video source.

The outputs of each comparator can be either zero or a positive voltage ( $+V_{out}$ ). Assume  $V_{out} = 5$  volts. Each comparator's output terminates in common load resistor  $R_L$ , which is much smaller than  $R_V$ . Typically,  $R_x = 10$  ohms,  $R_V = 4700$  ohms and  $R_L$  may be about 220 ohms. The comparator amplifiers must be capable of fast response since the video input components are as high as 3 MHz.


Assume the video level is zero. All four amplifiers will have a zero output. As the video level rises to  $\frac{1}{4}$  volt, amplifier A1 will suddenly change state and about  $\frac{1}{4}$  volt will appear across  $R_L$  (5-volt output from A1 attenuated by voltage divider  $R_V$  and  $R_L$ ). As the video level exceeds  $\frac{1}{2}$  volt, A2 will change state and now A2 will contribute a current through its  $R_V$ , so

now there is  $\frac{1}{2}$  volt across  $R_1$ . (With a high-gain comparator, a few millivolts change in the video level produces an abrupt  $\frac{1}{4}$ -volt change in the output across  $R_1$ .) Amplifier A3 conducts at  $\frac{1}{4}$  volt, and A4 conducts at 1 volt. Therefore, a ramp input voltage produces a staircase output with four discrete levels  $+\frac{1}{4}$ ,  $+\frac{1}{2}$ ,  $+\frac{3}{4}$ , and  $+1$  volt (actually five discrete levels because zero volts is a level as well). In that way, we can produce only several discrete levels from a continuously varying level.


By varying the reference voltage we can

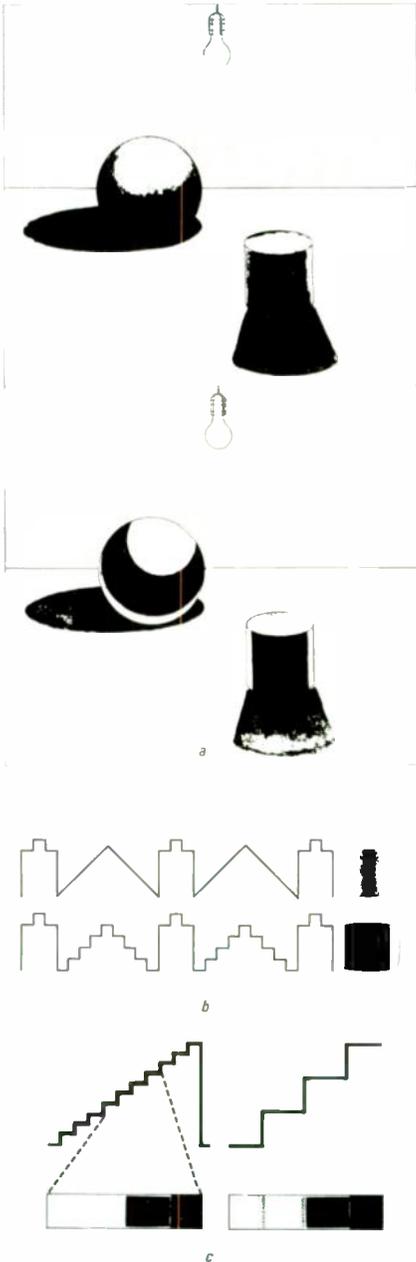

**FIG. 5—POSTERIZATION CHANGES GRADUAL shading to discrete transitions (a). In b we see how the normal video signal, which originally represented increasing and decreasing ramps, is changed to a staircase. In c we see how posterization creates grain at each transition. The grain isn't necessarily a problem because it's often used as a special video effect.**

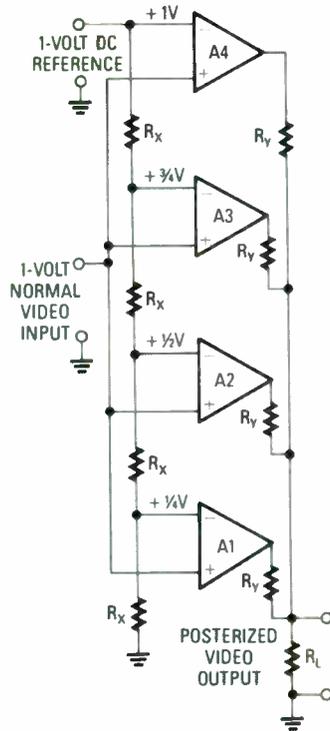

**FIG. 6—AN ELEMENTARY POSTERIZER circuit. The value of the DC reference voltage determines the width of each step.**

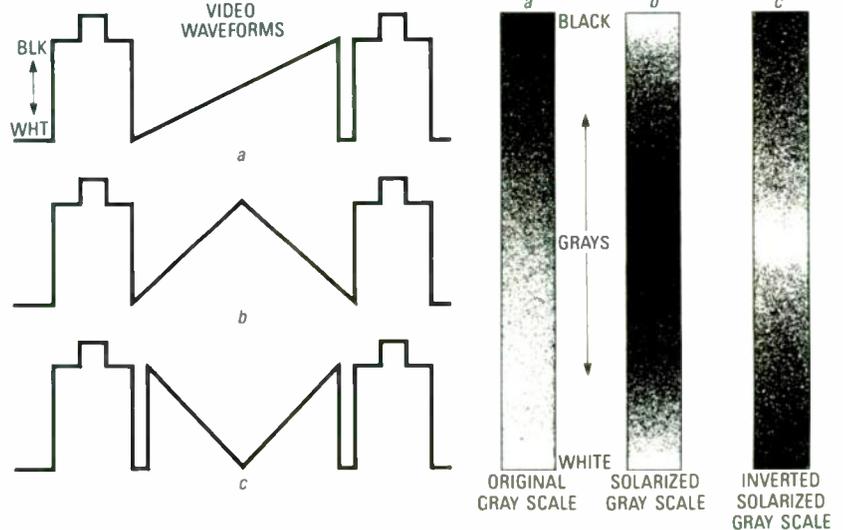

**FIG. 7—SOLARIZATION FOLDS THE SIGNAL back on itself so that white remains white, gray becomes black, and black becomes white, or vice versa. The original signal is shown in a. The solarized signal is shown in b. An inverted solarized signal is shown in c. The original waveform for each condition is shown in d.**

vary the spacing between the steps, and, hence, for a given input video level the number of steps can be varied.

### Solarization

In contrast to posterization, solarization is a linear distortion technique. However, as shown in Figs. 7-a, b, c, and d, what is done is to fold the gray scale back on itself. White becomes white, light gray becomes dark gray, gray becomes black. As the tones tend further toward black, the video output goes back towards white. Therefore, the picture highlights are positive and the shadows turn nega-

the necessary transfer characteristic. Although gains of two and four are shown, we can use any other 2:1 combination, resulting in a different gain figure. In our palette, we used gains of 0.5 and 1, giving an overall loss. That was done so that a larger input signal could be used.

As shown in Fig. 9, the solarization circuit uses a single op-amp. Assume that diode D1 is reverse biased, and that resistor R3 provides unity gain. Since  $R1 = R2$ , only half of the input signal appears at the inverting input.

As the input goes positive, D1 gradu-

*continued on page 86*

### WHERE TO GET PARTS

Next month we will present the schematics and construction detail for the video palette, for which the following items are available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804. The main printed-circuit board, \$12.50; the effects printed-circuit board, \$12.50; the main printed-circuit board and all parts that mount on the board, \$49.95; the effects printed-circuit board and all parts that mount on the board, \$39.95. A kit containing both the main and effects boards and their parts is \$84.95. The effects board, with or without components, is sold only in conjunction with the main board. Include \$2.50 postage and handling per total order. New York State residents must add appropriate sales tax.

tive. Inversion can be used in conjunction with solarization, so that the shadows are positive and the highlights are negative.

Solarization is accomplished by using an amplifier that has the transfer characteristic shown in Fig 8. As shown, two amplifiers, one having a gain of two and one with a delayed gain of minus four—with their outputs combined—result in

**Part 2** LAST TIME, WE looked at the circuit for an FM-stereo/SCA receiver. This month we'll show you how to build that circuit.

## Construction

The parts-placement diagram for the receiver is shown in Fig. 4. The pattern for the single-sided board is shown in PC Service. Upon examination, you may notice that the board uses a rather unusual parts layout. The layout shown was used to solve stability and crosstalk problems that are commonly encountered in high-gain, high-frequency designs of this type. It is based on the authors' experience with similar receivers, and with the particular IC's and transistors used.

The decision to use a single-sided board was made for several reasons. One, it makes it easier for a hobbyist with limited resources to reproduce the PC board at home. It also minimizes stray board capacitances, which can be a real problem at the frequencies involved. However, the use of a single-sided board does present some problems of its own. Such boards are much more difficult to lay out, and present RF grounding and stability problems. Those problems have been solved in the layout shown. Therefore, we *strongly* urge that you use our layout if you are contemplating building the receiver or any portion of it.

When stuffing the board, use a low-wattage iron (25 watts) and keep soldering time to a minimum to avoid overheating the components. All capacitors should be mounted as flush with the board as possible to minimize lead length. Be sure to adhere to the types and values specified in the Parts List. In particular, C16, C19, C37, C43, and C55 should be dipped silver-mica or NPO-ceramic types only.

With the obvious exception of the potentiometers (R71-R75), all resistors are 1/4-watt, 5% types. Again, make sure that all components are mounted flush with the PC board.

Be sure to observe the polarity on all appropriate components, such as the electrolytic capacitors. Varactor diodes D1, D2, and D4, and Zener diode D3 must be oriented correctly or the circuit will not work. Be sure to orient all IC's as shown in Fig. 4; otherwise they will be instantly and permanently damaged when power is applied. Care must be taken with ceramic filters FL1-FL3; they are somewhat delicate and easily broken. When you mount the AFC jumper (between C34 and R17), use a direct run to keep the lead as short as possible.

The tuning potentiometer, R71, should

# SCA/FM-STEREO RECEIVER

## SCA/FM STEREO RECEIVER



*Tune into the "hidden" signals on your FM dial with this SCA receiver.*

RUDOLF GRAF and WILLIAM SHEETS

be mounted off the board, on the front panel. Further, it should be a good-quality multiturn unit for greatest tuning ease. (Note that the R71 included in the kit available from the supplier is a PC-mounted unit; if the supplied R71 is used, it is mounted directly on the board and R18 is deleted. While that configuration is satisfactory for testing and experimentation, we recommend using a good-quality multiturn unit as described for best re-

sults.) If desired, R74 and R75 can also be mounted on the front panel.

Use a cabinet that is ample for the board. In particular, you should be able to mount the board at least 1/2-inch away from the sides, top, or bottom. The unit shown in the photographs has a wood base and a plexiglass front panel. We mounted the board on 1/2-inch metal spacers.

You can arrange the front-panel controls to suit your needs or preferences.

### WARNING!

SCA is not a broadcast service, and SCA transmissions are not intended for reception by the general public. As a result, SCA transmissions may be governed by Section 605 of the FCC Rules, which forbid unauthorized individuals from receiving such communications and using them for their own or other's profit, or divulging their contents, intent, or meaning to any other unauthorized individual.

Many for-profit services make use of SCA, and reception of those in most

cases is permitted by paying subscribers, and under certain circumstances, only. Some not-for-profit services do make use of SCA also, however, such as those providing assistance to the blind. It may be possible to receive those without obtaining prior permission or paying a subscription fee, as long as the terms of Section 605 are observed. We advise you to contact the appropriate programmers in your area for more information and to obtain any necessary authorizations.

Discover—Explore—Experience  
Today's Electronics With ...

# McGraw-Hill's Contemporary Electronics Series

Now you can meet the challenges of today's electronics quickly and easily. This professional level learning series is as innovative as the circuitry it explains and as fascinating as the experiments you build and explore! And it's for anyone who has an interest in electronics... from the hobbyist to the professional.

## Thousands Have Already Experienced the Excitement!

Today's high-tech world demands an entirely new and innovative approach to understanding electronics. That's why McGraw-Hill has developed this unique "hands-on" learning method that brings to life the dynamics of the new electronics. It's a unique combination of interactive materials that gets you involved as you build and experiment with today's latest electronic circuitry.

Just how well this innovative learning approach meets the challenge of the new electronics is confirmed by those who have already completed the Series... "You have put me right into the middle of an extraordinary learning experience. With each lab exercise I have gained a new understanding of the intricacies of today's electronics." Or... "For me, the Series was just the answer. I felt confident within my specialty, but my grasp of other areas of electronics was slipping away. Your Series helped me upgrade my knowledge of the latest electronics concepts." Or this from a company director of training... "We manufacture sophisticated electronic products, with a lot of people in sales, assembly and purchasing. McGraw-Hill has answered a real need in helping our employees see the total picture. They now communicate with customers and each other more effectively."

## Your Involvement in the New Electronics Begins Immediately.

You master one subject at a time with 15 McGraw-Hill *Concept Modules*, sent to you one

every 4 to 6 weeks. You waste no time on extraneous materials or outdated history. It's an entertaining, lively, nontraditional approach to the most modern of subject matter.

Your very first module takes you right to the heart of basic circuit concepts and gets you ready to use integrated circuits to build a digital oscillator. Then, you'll verify the operation of different electronic circuits using a light emitting diode (LED).

And each successive module brings you up to speed quickly, clarifying the latest advances in today's electronics... from digital logic and micro-processors to data communications, robotics, lasers, fiber optics, and more.

## Unique Combination of Interactive Instruction Materials Makes Learning Easy.

Laboratory experiments, vividly illustrated text and interactive cassette tapes all blend together to give you a clear, simplified understanding of contemporary electronics.

With each module, you receive a McGraw-Hill *Action-Audio Cassette* that brings to life the facts and makes you feel as if you're participating in a lively dialogue with experts.

Your ability to quickly make this knowledge your own is further aided by strikingly *illustrated* texts that use diagrams, explanations, illustrations, and schematics to drive home and rein-

force the meaning of each important point. Carefully indexed binders conveniently house all this material, as well as the instructions that will guide you through your "hands-on" lab experiments.

Throughout your Series, *laboratory experiments* reinforce every significant concept. With this essential "hands-on" experience using actual electronic components, you master principles that apply all the way up to tomorrow's VLSI (Very Large Scale Integrated) circuitry.

## Discover, Explore, Experience for Yourself—15-Day Trial.

In all ways, the Contemporary Electronics Series is an exciting learning experience that offers you the quickest and least expensive method available to master today's electronics... and the only one with "hands-on" experience.


To order your first module for a 15-day

trial examination, simply complete the card and send today! If the card is missing, write to us for ordering information.



McGraw-Hill  
Continuing  
Education Center

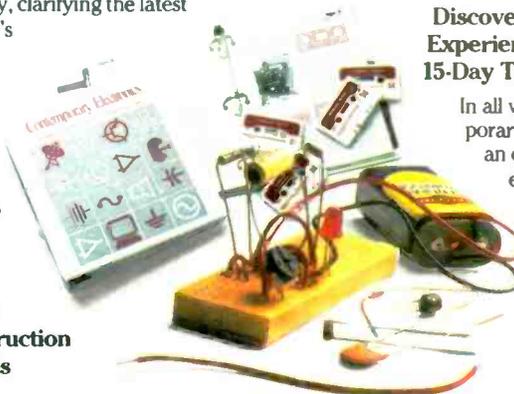3939 Wisconsin Avenue, NW  
Washington, DC 20016



With your first module, you'll build this solderless breadboarding system. As you add additional boards, you create increasingly complex circuits easily and quickly, bringing today's electronics concepts to life.

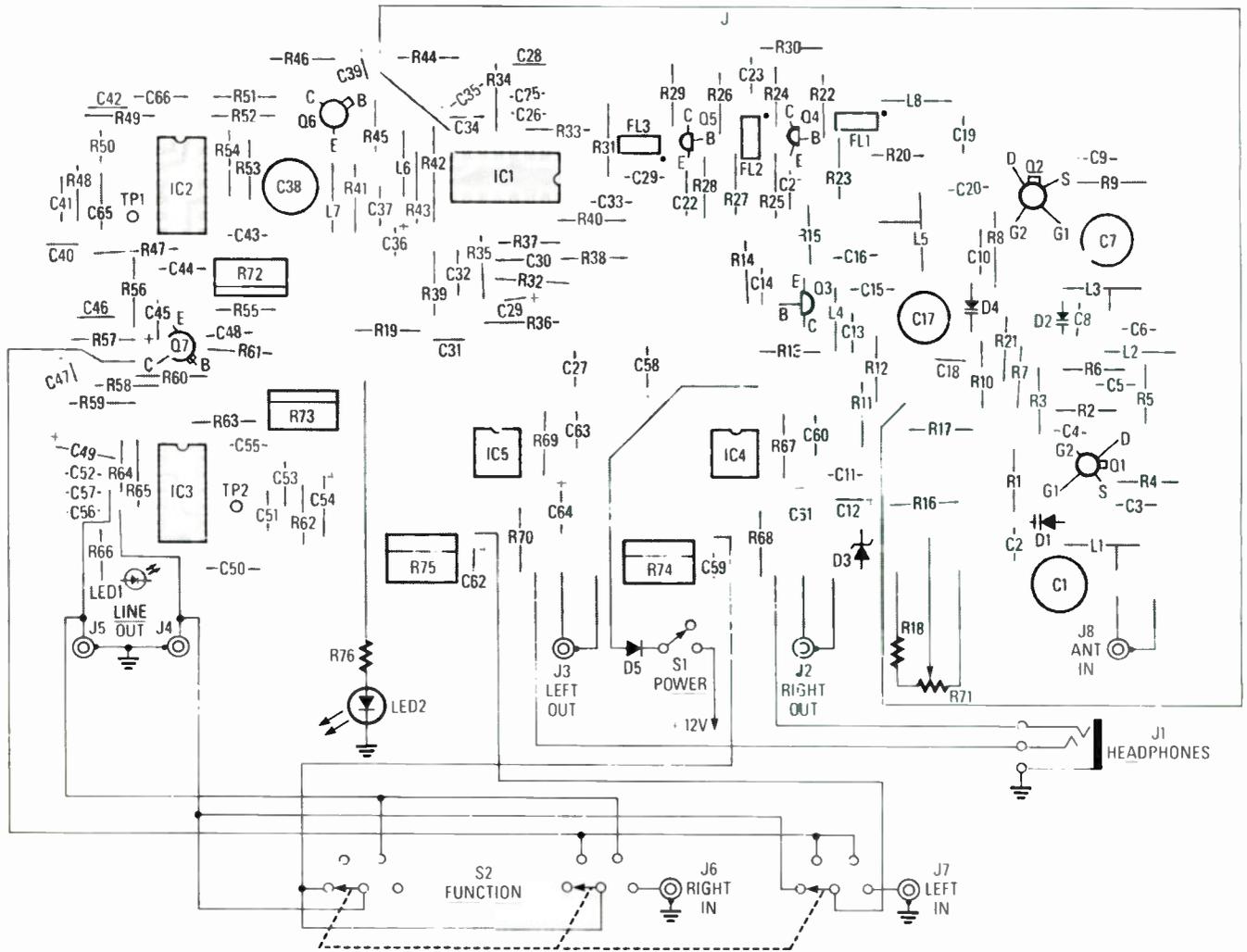


FIG. 4—MOST OF THE COMPONENTS mount on a single-sided PC board. However, for best results, we recommend removing R71, replacing it with a multiturn potentiometer, and mounting that unit on the front panel.

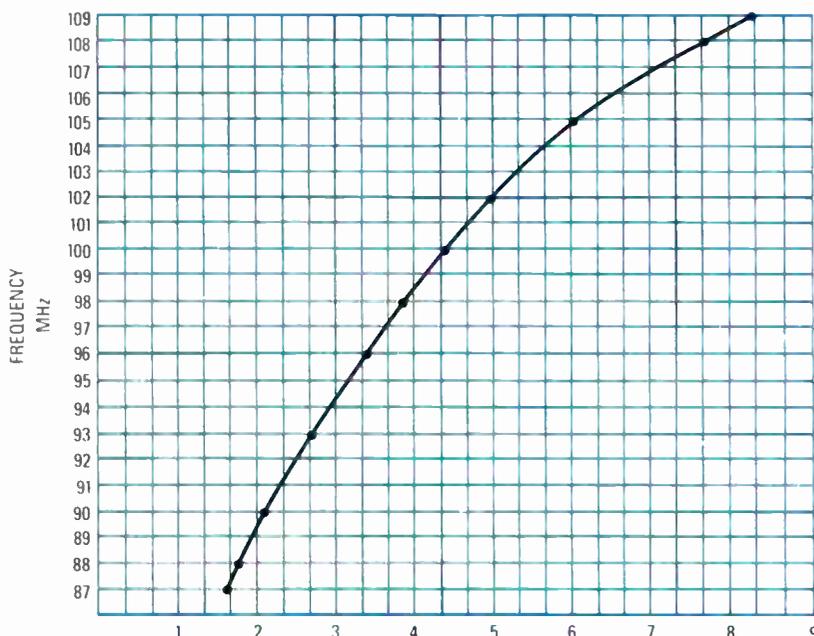


FIG. 5—USE THIS CHART to find the tuning voltage for the frequency of interest. Then adjust the setting of R71 so that voltage appears at the junction of R16 and R17 and tweak C17 until the station is received.

Connect front-panel mounted potentiometers to their appropriate pads using shielded cable for best results, especially if any of the runs are long. If the power supply is located physically close to the receiver, the AC power cord should be routed as far away from the front panel as possible. Otherwise, the leads from the potentiometers (particularly if shielded cable is not used) may be susceptible to AC-hum pickup.

The handwound coils for the front end are made using No. 20 tinned copper wire. They should be wound on a  $\frac{1}{16}$ -inch form: the shank of a  $\frac{1}{16}$ -inch drill bit is ideal for that purpose. Coils L1 and L3 are 5 turns each, and are tapped at 1.5 turns from the grounded end; L5 is four turns, tapped at 1.5 turns from the grounded end. The easiest way to build the coils is to wind each one, install it so that it sits  $\frac{1}{8}$ - to  $\frac{1}{16}$ -inch from the PC board, and then, using a length of No. 22 or 24 wire (a clipped-off lead from a resistor or capacitor is useful for that purpose) install the tap on the coil—simply tack-solder it on. You also can use short lengths of clip-

## PARTS LIST

### Resistors ¼ watt, 10% unless otherwise noted

R1, R3, R7, R8, R10, R46, R60—100,000 ohms  
 R2—47,000 ohms  
 R4, R25, R28, R68, R70—100 ohms  
 R5, R31, R32, R35—470 ohms  
 R6, R21, R39—150 ohms  
 R9, R11—220 ohms  
 R12, R14, R18—2200 ohms  
 R13—3500 ohms  
 R15, R30, R56, R57, R62, R66, R76—1000 ohms  
 R16, R23, R27, R36—R38, R40, R43, R45, R49, R54, R58, R59, R61—10,000 ohms  
 R17—1 megohm  
 R19, R67, R69—10 ohms  
 R20, R24, R29, R33—330 ohms  
 R22, R26—33,000 ohms  
 R34, R42, R44—22,000 ohms  
 R41, R47, R51—R53, R64, R65—4700 ohms  
 R48, R50—18,000 ohms  
 R55, R63—15,000 ohms  
 R71—R75—10,000 ohms, potentiometer

### Capacitors

C1, C7, C17—2–18 pF trimmer  
 C2, C5, C6, C8, C9, C11, C13–C15, C18, C20–C26, C28, C30–C34—0.01 µF, ceramic disc  
 C3, C4, C66—470 pF, ceramic disc  
 C10, C16, C37—100 pF, silver mica  
 C12, C29, C35, C36, C39, C47, C49, C59, C62—10 µF, 16 volts, electrolytic  
 C19—8 pF, silver mica  
 C27—not used  
 C38—3–40 pF, trimmer  
 C40–C43—220 pF, silver mica  
 C44—0.001 µF, Mylar  
 C45, C60, C63—0.1 µF, Mylar  
 C46, C51—0.047 µF, Mylar  
 C48, C52—0.0022 µF, Mylar  
 C50, C53—0.22 µF, Mylar or tantalum  
 C54—0.47 µF, Mylar or tantalum  
 C55, C65—470 pF, silver mica  
 C56, C57—0.022 µF, Mylar  
 C58, C61, C64—470 µF, 16 volts, electrolytic

### Semiconductors

IC1—LM3189N FM receiver IF system (National)

IC2—LM565 phase-locked loop (National)

IC3—LM1310N FM stereo demodulator (National)

IC4, IC5—LM386 audio amplifier (National)

Q1, Q2—40673 dual gate MOSFET transistor

Q3–Q5—2N3563 NPN transistor

Q6, Q7—2N3565 NPN transistor

D1, D2, D4—MV2107 varactor diode

D3—1N757 diode

D5—1N4001 diode

LED1—jumbo red LED

LED2—jumbo green LED

### Other components

L1, L3, L5—see text

L2, L4—1.8 µH

L6, L7—18 µH

CF1–CF3—10.7 MHz ceramic filter

J1—stereo headphone jack

J2–J8—phono jacks, RCA type

S1—SPST toggle switch

S2—3P4T rotary switch

**Miscellaneous**—PC board, No. 20 solid un-insulated wire for winding L1, L3, and L5 (18 inches total required), wire, solder, hardware, knobs, cabinet, etc.

**The following are available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804: Kit consisting of PC board and all PC-board mounted parts (jacks, switches, D5, LED's, power-supply components, etc. not included), \$75.00 plus \$2.50 postage and handling; Etched and drilled PC board, \$12.50 plus \$2.50 postage and handling. NY residents please add appropriate sales tax.**

## PARTS LIST—POWER SUPPLY

C67—2200 µF, 25 volts, electrolytic

C68—0.01 µF, ceramic disc

C69—0.1 µF, ceramic disc

C70—470 µF, 16 volts, electrolytic

T1—117-volt primary, 16–18 volt 500-mA secondary

IC6—LM7812 three-terminal regulator

D6–D9—1N4001 diode

ped resistor or capacitor lead for the pc-board test points.

Once construction is complete, check your work carefully. Make sure that all components are oriented correctly. Examine your work for poor solder joints and for solder bridges. Once you are certain that everything is OK, you can proceed.

### Checkout and alignment.

Begin by setting all potentiometers to the middle of their ranges. Set C38 so it is ½ meshed. Set C1, C7, and C17 so they are about ¼ meshed. Connect two 8-ohm speakers to the audio outputs, or a pair of 32-ohm headphones to the headphone jack. Connect about 6 feet of hookup wire to the antenna input, J8, to serve as a temporary antenna.

Once that is done, measure the DC resistance between the power and ground traces on the board. It should be above 100 ohms. If it is significantly less, you likely have a short somewhere on the board. Find it and fix it before proceeding.

If everything is OK, apply +12-volts DC to the +12-volt input. Check the current drawn from the supply; it should be about 125–150 mA at 12 volts.

When power is applied, you should hear a rushing noise in both speakers (or headphones). If not, find the source of the problem and correct it before going on. If only one channel is dead, the best place to look is around the appropriate audio amp (IC4 or IC5).

Set the FUNCTION switch (S2) for FM-stereo and rotate R71. In most areas of the

U.S. you should hear a few FM signals. Note that at this point the audio may seem distorted. Using a non-conductive tuning tool, adjust C38 for clearest audio (lowest distortion). Adjust R74 and R75 for a comfortable volume level.

Next, we'll calibrate the tuning potentiometer. Locate and identify a weak station at the high end (between 106 and 108 MHz) of the FM broadcast band using a commercial FM receiver. Try to tune that station using our receiver. If your tuning range does not extend high enough, adjust C17 to correct the tuning range. Once the station is tuned in, use Fig. 5 to find its corresponding tuning voltage. Set R71 so that that voltage appears at the junction of R16 and R17. Then tweak the setting of C17 so that the station is tuned at that setting of R71.

To calibrate at the low end of the broadcast band, locate and identify a weak station between 88 and 91 MHz. Adjust R71 to get the appropriate tuning voltage at the junction of R16 and R17 as before. Then, compress or expand the turns of L5 until that station is received at that setting of R71. Double check your calibration to be sure that the entire band is covered.

Once you are satisfied with the band coverage, adjust C1 and C7 for best reception and note their settings. To tweak reception, tune in a weak signal between 88 and 91 MHz. Adjust C1 to see if a different setting will provide better reception. If it does, note whether the adjustment results in increasing (greater meshing) or decreasing (less meshing) the capacitance of C1. Return C1 to its original setting. If increasing the capacitance resulted in better performance, compress L1 for optimum reception; if decreasing capaci-

## SCA RADIO MANUFACTURERS

**Commercial Elects./Multiplex Music**  
 38-40 Washington Avenue, St. Louis, MO 63108

**Dynamic Sound**, PO Box 840, Exeter, NH 03833

**Fox Marketing, Inc.**, 4518 Taylorsville Rd., Dayton, OH 45424

**Johnson Electronics, Inc.**, PO Box 4723, Winter Park, FL 32707.

**McMartin International, Inc.**, 111 Camino Del Rio, Gunnison, CO 81230

**Norver Co., Inc.**, 7300 North Crescent Blvd., Pennsauken, NJ 08110

**Panasonic/Matsushita Technology Center**, 1 Panasonic Way, Secaucus, NJ 07034

**Radio Systems, Inc.**, PO Box 356, Edgemont, PA 19028

**Repro, Inc.**, 1940 Lockwood Way, Orlando, FL 32854

**SCA Data Systems, Inc.**, 3000 Ocean Park Blvd., Suite 1040, Santa Monica, CA 90405

**SMC International**, 14745 Madison Cir., Omaha, NE 68137

**Toa Electronics, Inc.**, 480 Carlton Ct., South San Francisco, CA 94080

## ADDING A FILTER

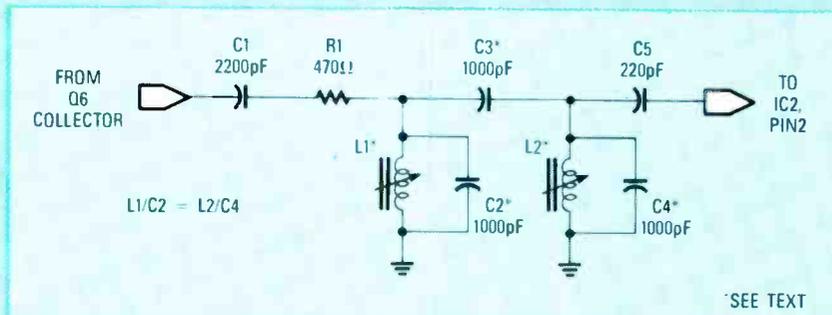



FIG. 1—THIS TUNABLE BANDPASS FILTER effectively suppresses main-channel sputter to provide superior performance for your SCA receiver.

Whether or not the main-channel audio interferes with an SCA signal depends on several factors, both at the receiver and transmitter. In particular, however, the precision of the components used in the Twin-T filter that feeds the SCA demodulator strongly affects how much main-channel sputter and splatter will be heard in the SCA signal's background. If the filter is made from high-tolerance components—1% resistors and capacitors—the main channel suppression will be adequate in most instances.

If you need an SCA signal that is virtually immune to interference by the main channel, then we suggest adding the tunable bandpass filter shown in Fig. 1 to your receiver. The value of L1 and L2 is

found from the formula  $L = (1/6.28 \times f)^2 / C$ , where  $f$  is the SCA subcarrier frequency and  $C$  is the value of the capacitor in the resonant circuit. The values of C2–C4 depend on a number of factors, including the characteristics of the coils used, the impedance at the filter's input and output, etc. Start with a value of 1000 pF for each as shown, but be prepared to experiment with the values of the components marked with an asterisk to obtain optimum performance. Of course, bear in mind that L1/C2 and L2/C4 must be resonant at the subcarrier frequency.

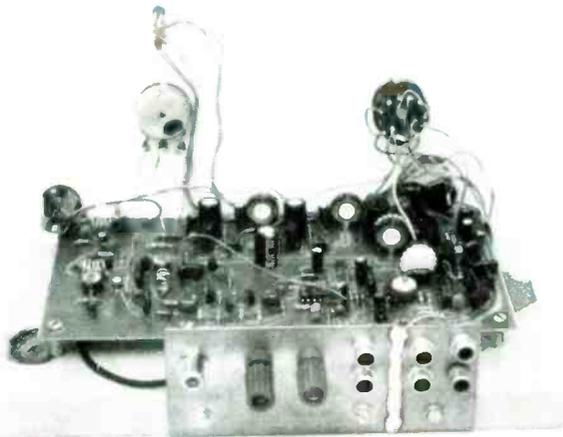The filter can be assembled on a small PC or wire-wrap board and piggy-backed onto the main board with double-sided tape, or small metal brackets. **R-E**



THE AUTHOR'S PROTOTYPE was mounted in a simple homemade cabinet. Whatever cabinet you use, be sure that it is ample to house the board.

tance yielded better reception, expand the coil. Repeat the procedure for C7 and L3. Then tune to a weak station at the high end of the band and repeat. Continue the process until you are satisfied that no further improvement is noted.

Adjust C38 so that the voltage across R43 is zero when a station is tuned in properly. Detuning the station should

cause that voltage to rise or fall slightly ( $\pm 1$  to 2 volts is typical). Adjusting C38 in that manner should produce the clearest audio.

Next, tune in a weak station that you are certain is transmitting its signal in stereo. Adjust R73 for best stereo reception. When R73 is adjusted properly, LED1 should light. For more precise adjust-

ment, connect an oscilloscope or frequency counter to TP1 and adjust R73 to produce a 19-kHz signal.


Now, set S2 for SCA reception and R72 to its midrange position. *Slowly* tune across the FM broadcast band. You may hear several SCA signals. Tune one in and adjust R72 for best reception. If you cannot hear any SCA signals, change the setting of R72 *slightly* and try again. Note that if you do not have good fortune, aligning the receiver in this manner can be tedious and time-consuming, but with patience it can be done. There is, however, a short cut available to you if you have access to a frequency counter or an oscilloscope: Simply connect the instrument to TP2 (pin-6 of IC2) and set R72 to produce a 67-kHz signal there. To tune in other subcarrier frequencies, set potentiometer R72 to produce a pin 6 signal of the appropriate frequency.

If you know that a certain FM station has SCA activity, the receiver's *TUNE* function offers yet another method of alignment. When S2 is set to *TUNE*, the main channel audio is fed to one output, while the SCA audio is fed to the other. That allows you to hear both the main channel and the SCA subcarrier simultaneously. Using a pair of headphones for best results, tune the receiver so that the desired station's main-channel audio can be heard in one ear. Then, adjust R72 until the desired subcarrier can be heard in the other ear.

That completes the alignment procedure. Though there are a lot of steps to follow, most of the adjustments are broad and the radio should work in the FM-stereo position even with just the initial adjustments outlined. An exception to that is the setting of C38, and, to a lesser degree, the setting of C17; correctly adjusting those components requires some precision. Still, if the setting of any component is so critical that even breathing on it causes problems, something is not working properly.
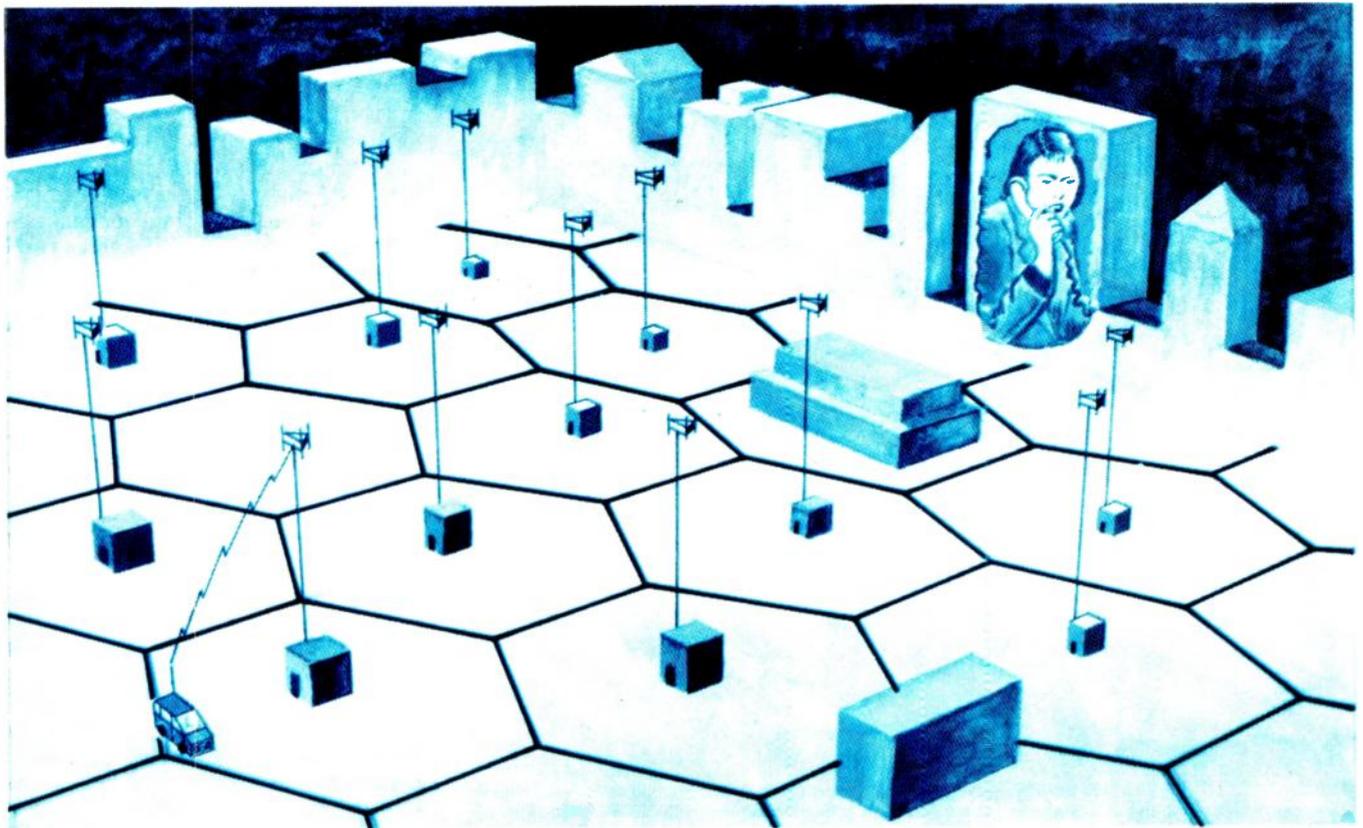
### Searching the bands

One of the authors lives on the New York/Vermont border, about 50 miles north of Albany, NY. From that relatively rural location he has received FM-stereo signals from as far as 170 miles away using only a two-foot clip-lead antenna. In addition, six SCA subcarriers could be received. Obviously, in major metropolitan areas many more SCA signals should be heard. In the New York City area alone, for instance, upwards of 20 FM-radio stations have some type of SCA activity. If you want to find out what stations in your area have SCA activity, and what type of programming is available, an excellent reference is the *FM Atlas and Station Directory*, written by Bruce Elving (FM Atlas Publishing, Adolph, MN 55701-0024). **R-E**



## INSIDE CELLULAR TELEPHONE


*A look inside cellular telephone, and the fascinating technology that has revolutionized mobile communications.*

JOSEF BERNARD

NOT SO LONG AGO, WHEN ONE THOUGHT of a telephone, the image conjured up would be of a jet-black, rotary-dial, electromechanical device. Now, conventional telephones come in a rainbow of colors, sport sleek lines, and feature pushbutton dialing. But even more impressive are the features that are packed inside them. Thanks to microprocessors and memories, phones are capable of storing a telephone-book's worth of most-often-called numbers to be dialed at the push of a button. And that's only the beginning.

But if you think that the phone on your desk or in your kitchen is "smart," then you would have to place cellular mobile phones in the "genius" class. Those phones have to perform a number of sophisticated tasks, including monitoring signal levels and frequency switching, in such a way that the user is not aware of them. Because of that, many people who

use cellular phones daily aren't aware of the high level of technology built into their equipment. That's unfortunate, because

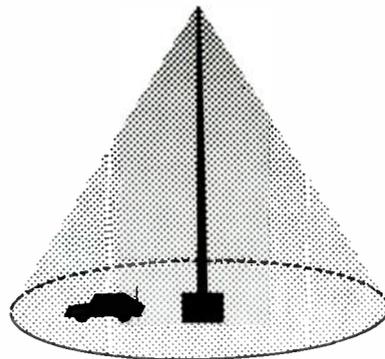

**FIG. 1—EARLY, NON-CELLULAR, MOBILE-phone systems used a centrally located high-power transmitter. Only a few communications channels could be accommodated within a service region.**

the technology inside the phones is, for the most part, much more interesting than the conversations that they transmit.

### Cellular principles

Prior to the development of the cellular system, mobile telephone systems relied on centrally located transmitting and switching equipment to communicate with vehicles subscribing to their services. See Fig. 1. Cellular systems, on the other hand, divide their region of coverage into many small areas, each encompassing only a few square miles. See Fig. 2. It is that territorial subdivision that allows the mobile units to use low-powered transmitters (no more than three watts), and to use and reuse the same frequencies in the same area to increase the number of communications channels available.

There are 999 two-way communica-

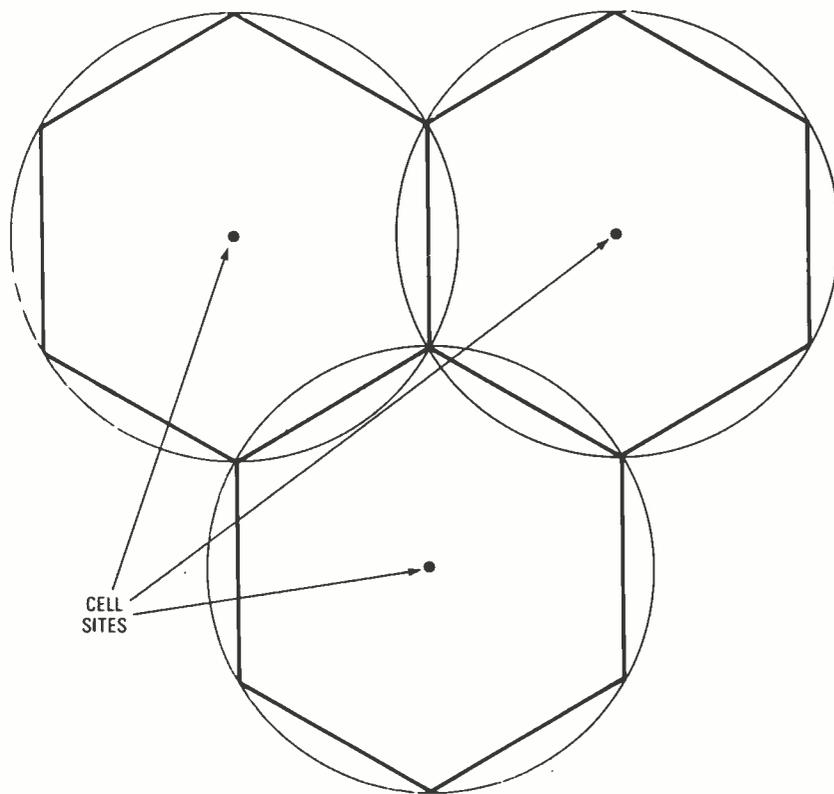


FIG. 2—A CELLULAR SYSTEM DIVIDES its region of service into a number of small cells, each with its own cell site containing a low-power transmitter and receiving equipment. As a vehicle passes between cells, the signal is analyzed and any further communications are handed off to the cell best able to handle them.

tions channels allocated for cellular service, although the phones currently available can use only 666 of them. (The other 333 frequencies were allocated in 1986 and equipment manufacturers, as of this writing, have not yet caught up with the FCC.) Of those channels, 42 are devoted to carrying control signals between cellular phones and the cell sites, where the transmitting and receiving equipment for each cell are located. It is over those channels—which you never hear, and rarely hear about—that a cellular system coordinates its activities.

All kinds of information flows on those channels, including that for coordinating frequency changes, identifying phones, and even adjusting power levels.

### Handing off

When a mobile unit leaves the region of coverage of one cell site and enters that of the adjoining one, it is said to be *handed off* from one cell to the other. There is a lot of behind-the-scenes activity connected with that transfer of responsibility, and the intelligence built into cellular phones handles a lot of it.

As a vehicle equipped with a cellular phone traverses a particular cell, it eventually reaches a point where its signal is no longer strong enough for reliable communications. Fortunately, by the time it

has reached that point, it is well within the region of coverage of an adjacent cell. The handing-off process of transferring the responsibility for a call-in-progress from one cell site to another requires a lot of "intelligence" on the part of both the cell site and the mobile unit.

The first thing that has to be done is to sense when a signal is approaching the point where it is about to become too weak to be usable. That's easy—all you need is what amounts, more or less, to a signal-strength detector. More complicated is the task of determining which new cell site is to receive the hand-off. The cell sites in the system have to "confer" to see which of them is receiving the signal in question the best, and make arrangements for transferring the call without interruption. That's not too difficult, either. The next part of the process, however, is quite complex.

Because adjacent cell sites cannot use the same frequencies, even though others in the same system can, a new set of frequencies must be used after the hand-off. And, since the new cell site will be using different frequencies, so must the mobile phone. That is where the control channels, and the intelligence built into a cellular phone, come into play. The new cell site knows which of its frequencies are in use and which are free, and makes a

decision to allocate one of its frequency pairs (one channel) to the new conversation entering its district. It then transmits, over the control channel, instructions for the cellular phone carrying the conversation to switch to those new frequencies. The phone adjusts the voltages of its frequency synthesizer accordingly, and the conversation continues in the new cell site, on the new frequencies—all of that with only an unnoticeable interruption of a millisecond or two.

### Power levels

A cellular system can use the same frequencies for different conversations at the same time, provided, of course, that the signals of one cell site do not interfere with those of another. That non-interference is accomplished in several ways.

The first is simple coordination of frequencies. While several cells in the same system may use the same frequencies, no two adjacent cells do. That puts cells using the same frequency far enough away from one another that the signal from one to a vehicle in its area, and vice versa, will override another signal from farther away. That is further ensured by the *capture effect*, which is a characteristic of FM, the transmission mode used by cellular phones. If there are two signals on the same frequency, one stronger than the other, the capture effect guarantees that a receiver will lock onto the stronger one, and ignore the weaker. Unless the two signals are nearly identical in strength, the stronger one will completely capture the receiver, and no trace at all of the weaker one will be heard.

All that is the consequence of good planning, and of the nature of FM equipment. Inside a cellular phone is circuitry that adds another level of interference protection. There is a constant dialogue going on between a cellular mobile unit and the cell site it is using. One "topic of conversation" is signal strength. Cellular equipment is low powered. Cell-site transmitters have an output of only 25–35 watts (compared to about 250 watts in older systems using central transmitters), and the mobile equipment a maximum output of three watts—and as low as 600 milliwatts for handie-talkie-size units.

One of the rules of cellular telephony is "use only as much power as you need." Consequently, a cell site monitors the strength of the signal it receives from a mobile unit. If the strength increases to a predetermined level, the cell site sends instructions over the command channel for the low-powered phone to reduce its power to an even lower level. Conversely, if the received signal strength drops, a mobile phone can be instructed to increase its power. Cellular phones are capable of between 3 and 8 discrete output levels. Keeping output power to the minimum required for good communications

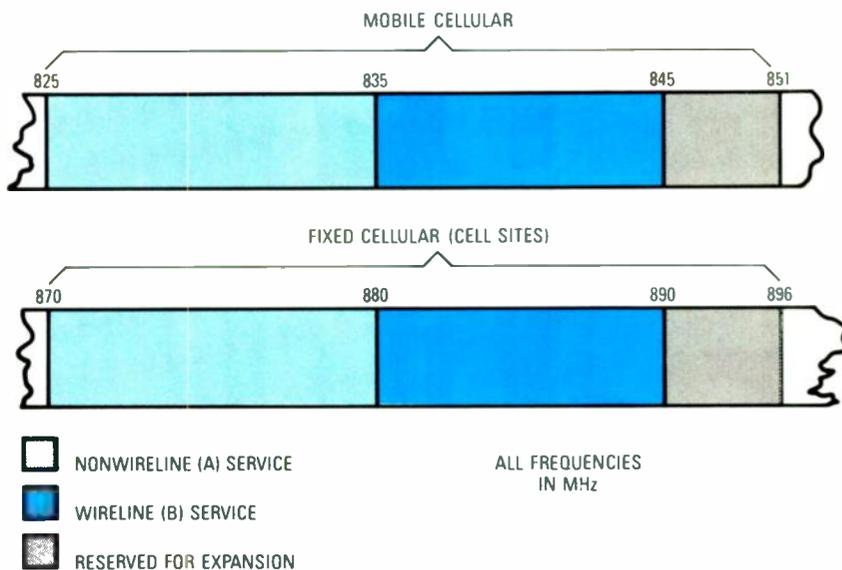


FIG. 3—THE 666-CHANNEL CELLULAR PHONE RF spectrum is divided into bands for fixed and mobile equipment (cell sites and phones), and for non-wireline (A) and wireline (B) service.

also reduces the risk of interfering with communications in a nearby cell.

### NAM's

Every cellular phone contains an "identification" PROM or EPROM. In cellular terminology, this is called a NAM (Numeric Assignment Module). A phone's NAM is programmed at the time the phone is purchased; it contains such information as:

- The telephone number, or ESN (Electronic Service Number), assigned to the phone.
- The serial number given to the phone at the time of its manufacture.
- Personal codes that can be used to lock and unlock the phone electronically, to prevent its unauthorized use.

NAM information is more useful than you might at first imagine. For one thing, it is the job of the NAM to identify the phone containing it to the cellular systems it uses. When a cellular phone is turned on, it makes an announcement over a control channel that says, "Here I am." The cell site responds, "And exactly who are you?" The reply from the phone consists of information contained in its NAM.

That information tells the cellular system several things. First, of course, is that that particular phone is now on the air and is ready to receive calls placed to its number. The cell site is connected to a computer at the MTSO (Mobile Telephone Switching Office), which is the link between the cellular system and the conventional landline phone system, and which recognizes all the cellular phones registered in the calling area it is responsible for. If the phone is a local one, the process is more or less complete at the point of recognition.

Because they are mobile, cellular phones may frequently be used outside of the area in which they are permanently registered. That is called *roaming*, and is one of the outstanding features of cellular telephony. You can take your cellular phone almost anywhere in the country where there is service, turn it on, and use it to call anywhere in the world.

In some areas you can roam and use a foreign system without advance notification. Other cellular systems require that you let them know ahead of time that you are coming. In either case, the NAM information transmitted to the system allows you to log on to it, and tells that system what to do about your billing.



NOT JUST FOR CARS, cellular phones come in portable models, like this one from GE, that keep you constantly in touch.

Cellular phones have a ROAM indicator, which lights when you have left your local area and are in the operating area of another system. (The phone realizes that it has entered a system other than its own, and lets you know that.)

The serial number contained in the NAM, incidentally, can serve a second purpose. Should a phone be stolen and reported so, it is possible for a system to recognize that phone when it is next used. While tracking down the phone would be rather difficult, it is easy to cut off service to that number automatically, avoiding the possibility of your being charged for calls you never made.

### A/B switching

When it established the cellular phone service, the FCC provided for two cellular carriers in each region. One, the *wireline* service, would be operated by a phone company engaged in conventional telephony, frequently the one that already provided landline service to the area. The other, known as the *non-wireline*, service would be operated by a company that was engaged in other forms of mobile communications—perhaps paging, or private two-way radio services. Sometimes a region of cellular service has both types of carriers, and sometimes only one, at least when service is inaugurated. Each service is assigned a separate set of frequencies. See Fig. 3.

Regardless of where in the country you are, the non-wireline service is referred to as the *A service*, and the wireline one as the *B service*. Normally you subscribe to only one service or the other (provided your area offers you a choice), but you may at times have occasion to use the other type—when you are roaming, for example.

To provide for that, cellular phones have A/B switches to allow you to go from one type of service (band of frequencies) to the other. Those switches are generally not mechanical devices, but are programmable from a phone's keypad. Some of the switches are more flexible in their capabilities than are others, and the more sophisticated of them offer at least the following modes of operation:


- A (or B) service only—the other is locked out.
- Give priority to one type of service over the other.
- Automatic selection of the one active service in an area.

Again, it is the intelligence a phone applies to the information coming in over its control channel that makes it possible for it to select the appropriate A or B setting.

When you are roaming, the phone lets you know you are outside of your normal area of use by illuminating its ROAM indicator. Some phones can apply their

*continued on page 93*

# R-E ROBOT

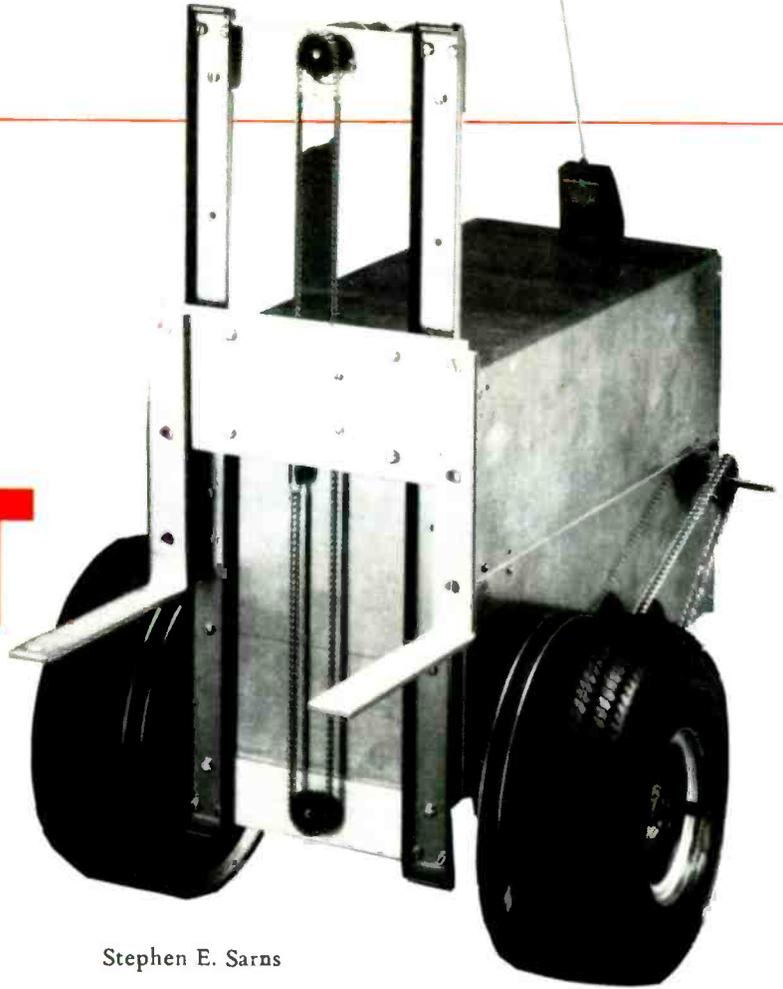

Stephen E. Sarns

Here's an application that can give a robot builder great "joy."

**Part 10** Now that we've finished building the *Robotic Personal Computer (RPC)*, the mechanical drive system, and the interface and controller board, we have a robot that is ready to run. But what are we going to do with it? In this article we are going to show you a simple application program that will demonstrate how to:

- Develop programs on the RPC.
- Read the A/D converter.
- Read the switch status.
- Control motor direction.
- Control motor speed.

In addition, our first application, a joystick controller for the robot, illustrates the use of the underlying Forth-83 language. You will want to become familiar with Forth-83, even though you have the power of the *Robotic Command Language (RCL)* at your disposal, because Forth-83 allows you to extend the RCL to suit your needs. Remember, the RCL is simply an application written in Forth-83. Your application can use the resources of RCL or Forth-83 or both. That is shown graphically in Fig. 1.

### The application

A joystick is attached to the discrete user bus (PL3 on the control board). Analog channel 0 is used to monitor the joystick's forward/backward position. Analog channel 1 monitors its left/right position. For safety, a pushbutton *dead-man* switch is connected to the D7 (data bit 7) input. That switch must be depressed for the robot to operate; if it is released, all power to the motors is cut. The schematic for the joystick hookup is shown in Fig. 2.

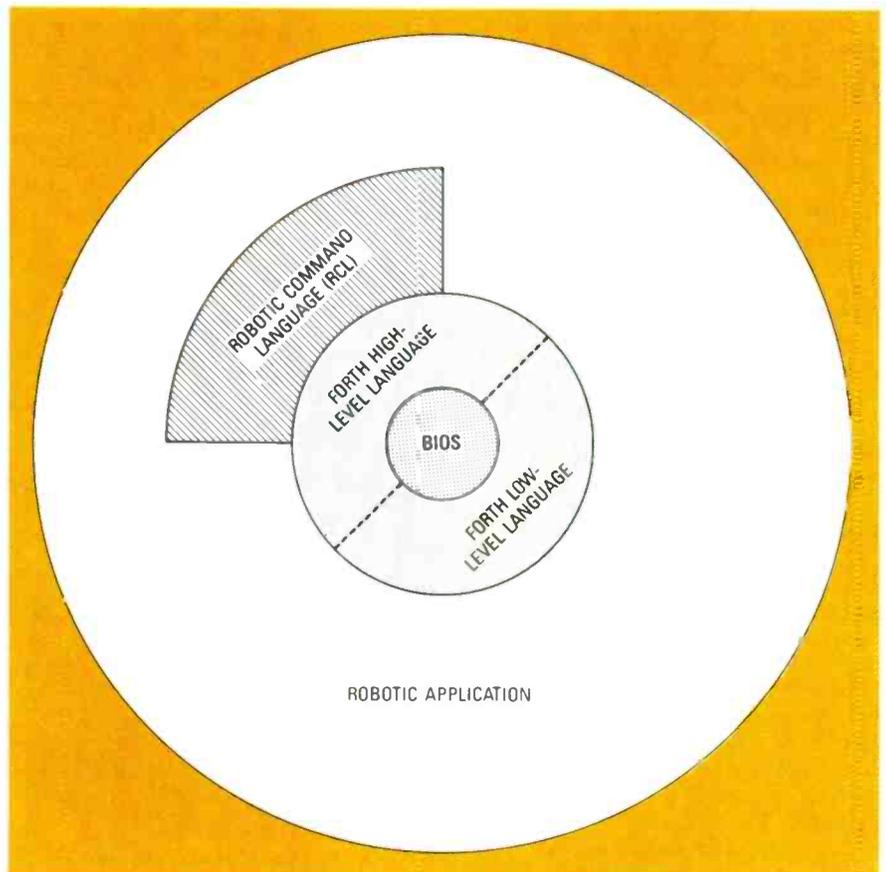


FIG. 1—AN APPLICATION PROGRAM for the robot can be written in RCL, Forth, or both.

All of the code we are going to write will fit into six Forth screens. Therefore, you do not need a disk drive. You can use the RAM word to store all of your source code in virtual memory above 32K. Alternatively, you can attach a disk drive and keep all of your code on disk. Last, you could type in all of the colon definitions from the keyboard, but doing so is handy for testing, not developing an application.

If you are going to use RAM as the development media, power down and install a RAM IC in the IC5 socket on the RPC, execute the RAM word, and remember that you now have virtual memory screens 32 to 39. If you have a disk drive attached, simply insert a disk formatted under MS-DOS version 2.x or the BIOS formatter. Decide where you want to start (never screen 0) among the 360 available screens on the disk. For simplicity and clarity, we'll assume that you'll start your first screen at 32 just like the RAM-based example. Incidentally, the example was developed on a disk, but there is no functional difference after executing the RAM or DISK word.

Install a blank 2764 EPROM at IC31, the EPROM programming socket on the RPC; once again, power should be off when doing that. It's handy to keep an EPROM installed there, especially if you are developing code in RAM and do not want to risk losing it during a power down.

Invoke the editor by typing 32 EDIT. The 32nd screen is read in from disk (or RAM), the terminal's display is cleared, and then the screen of text is listed. Alternatively, you can type EDITOR 32 LIST. Your first command will probably be WIPE; that clears the entire screen. Now begin entering the source code with the editor. When you want to test a word, make sure you FLUSH your changes to disk before you LOAD the screen, otherwise all of your changes will be lost if your system crashes.

### The program

One of the most common criticisms of Forth is that it is unreadable and therefore unmaintainable. We think you will find Forth quite the opposite—if you start at

### LISTING 1

```
Scr # 32
0 / joystick documentation
1
2 / analog channel 0 is used by forward/reverse joystick
3 / analog channel 1 is used by left/right joystick
4 / digital input D7 is a normally open "deadman" switch
5 / variables LSPEED and RSPEED contain the joystick position
6 /   in the range of -127 to +128
7
8
9
10
11
12
13
14
15 -->
Scr #33
0 / joystick - i/o
1 / all low level drivers for reading and controlling here
2
3 hex
4 : atod ( channel number --- byte )
5   dup 150 pc! 150 pc! 100 0 do loop 150 pc@ ;
6 : switch? ( ---f ) 120 pc@ 80 and 0= ;
7 : lmtr-period 36 103 pc! 100 /mod swap 100 pc! 100 pc! ;
8 : rmtr-period 36 113 pc! 100 /mod swap 110 pc! 110 pc! ;
9 : stop-left 0 124 pc! ; ; stop-right 0 125 pc! ;
10 : enable-left 1 124 pc! ; ; enable-right 1 125 pc! ;
11 : l fwd 0 121 pc! 1 120 pc! ; ; r fwd 0 122 pc! 1 123 pc! ;
12 : l rev 0 120 pc! 1 121 pc! ; ; r rev 0 123 pc! 1 122 pc! ;
13
14
15 -->
Scr #34
0 / joystick - joystick interrogation
1 / INTERROGATE reads both channels of a/d. Results of fore/back
2 / are stored in LSPEED and RSPEED. The left/right position is read
3 / and the contents of LSPEED and RSPEED are modified according
4 / to DIFF-CONV
5 hex
6 300 constant maxspeed      variable lspeed      variable rspeed
7
8 : speed-conv ABS 5 * maxspeed swap - ;
9 : diff-conv 5 / ;
10
11 : interrogate
12   0 atod 80 - dup lspeed ! rspeed !
13   1 atod 80 - diff-conv dup negate swap
14   lspeed +! rspeed +! ;
15 -->
```

the end and work backwards. Remember, in Forth, you can design your program

from the top down, meaning that you can figure out how it should work, write that part of the code, and later add the support words to make it work that way. By starting your examination of the application from the end, you will understand how the program works, leaving the details for later.

Therefore, for now we'll ignore the low-level words, which can be rather esoteric, and begin with screen 37, which contains a single word called JOY. That is the joystick program. While it is executing, pushing the stick forward causes the robot to go forward; pulling the stick back causes it to reverse. Turns are made by moving the joystick in the desired direc-

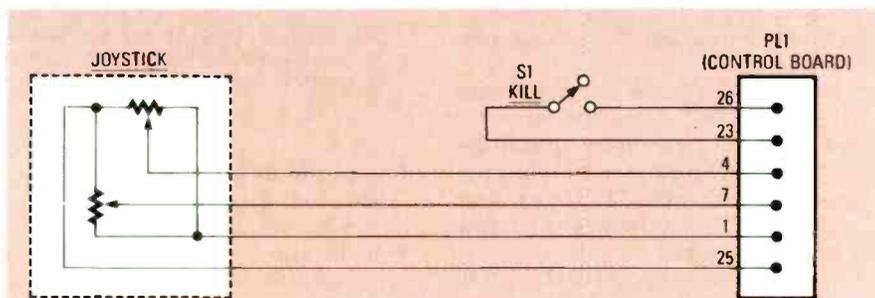


FIG. 2—A SIMPLE JOYSTICK can control the robot. The circuit is wired to the user interface on the control board. For safety, a "deadman" or kill switch must be provided.

## LISTING 1 (continued)

```

Scr #35
0 / joystick - left motor control
1 decimal
2 : leftmotor
3   lspeed @ 10 > switch? and
4   if l fwd lspeed @ speed-conv lmtr-period enable-left then
5   lspeed @ -10 < switch? and
6   if l rev lspeed @ speed-conv lmtr-period enable-left
7   then
8   lspeed @ -10 10 between switch? 0= or
9   if stop-left then ;
10
11 : testleft
12   begin interrogate leftmotor lspeed @ . key ? until ;
13 -->
14
15
Scr #36
0 / joystick - right motor control
1
2 : rightmotor
3   rspeed @ 10 > switch? and
4   if r fwd rspeed @
5   speed-conv rmtr-period enable-right
6   then
7   rspeed @ -10 < switch? and
8   if r rev rspeed @
9   speed-conv rmtr-period enable-right
10  then
11  rspeed @ -10 10 between switch? 0= or
12  if stop-right then ;
13
14
15 -->
Scr #37
0 / joy
1 hex
2
3 : joy
4   begin
5     interrogate rightmotor leftmotor
6     lspeed @ 10 .r rspeed @ 10 .r
7     cr key?
8     if key 0d =
9     else 0
10    then
11    until ;
12
13 decimal
14
15

```

tion. Speed is controlled by the displacement of the joystick.

Note the BEGIN/UNTIL structure on screen 37. The code executed within the loop is indented for easier understanding. The loop repeats or ends depending on the value of an argument left by the IF/ELSE/THEN construct. The loop checks to see if a key has been pressed. If so, the KEY statement retrieves the character and it is compared to a 0DH (carriage return). If the result of the comparison is true, a *true* flag (-1) is left on the stack. If the KEY statement is false, ELSE is executed, which leaves a *false* flag on the stack (0). UNTIL causes the loop to continue until a *true* flag is found on the top of the stack. Thus, JOY will execute until the carriage-return key is pressed.

Why not terminate on any key? Sometimes after you disconnect your terminal, the floating RS-232 input can be subject to noise. Generally, after your code is in ROM and you are running without the terminal, install a shorting bar between RxD and ground on the RS-232 connector.

INTERROGATE (in line 5 of screen 37) is a word that updates the two variables LSPEED (left motor speed) and RSPEED (right motor speed). The numbers in LSPEED and RSPEED range from -128 to +127. Positive means forward, negative means reverse.

The next two words, RIGHTMOTOR and LEFTMOTOR, examine the contents of the words of LSPEED and RSPEED respectively and set the appropriate

motor's speed accordingly.

Finally, the contents of variables LSPEED and RSPEED are fetched and displayed on the screen followed by a carriage return. The .R word is used to right justify the displayed values.

### Testing

Each word should be tested after it is written and compiled into the dictionary (LOADED from disk). A common test/debug method is to load up the stack with a few easily identified values, such as 1, 2, and 3. Then type in each word of the definition being tested (not in a colon definition, but interactively). After each word, execute .S, which prints out the contents of the stack without modifying it. Do so to make sure that nothing has been removed from or left on the stack.

It can be useful to define small test. For example, having defined the word ATOD, which takes a channel number off the stack and returns the value of the corresponding A/D converter, you can make sure that it works with all 8 channels by using the following word:

```

: TEST-ATOD
BEGIN 8 0
DO I ATOD . LOOP CR KEY?
UNTIL ;

```

That word prints out the results of all 8 A/D conversions. Your joystick should show up at the first two positions. Terminate the test by pressing any key.

### SOFTWARE SOURCES


Micro K Systems (15874 East Hamilton Place, Aurora, CO 80013, 303-693-3413) will provide the following: Commented source code in RE-robot disk format, \$2.00. Printed source-code listing, \$15.00. Two 27128 EPROM's with source screens (and without comments) for the R-E Robot, \$39.00. With EPROM's you won't need a disk drive, but you should also obtain the printed listing to read the comments. The Laxen and Perry F83 Model disk with full source code and met-compiler for customizing F83, in MS-DOS 360K format, for a PC compatible computer, \$25.00. (Very useful for learning FORTH if you already have a PC.) All orders must be prepaid. NO COD's. Include \$3.00 for shipping with each order. Additional source code and applications will be available from Micro K Systems. Contact them for more information.

### Speed and direction

The word RIGHTMOTOR, shown in screen 36, examines three possibilities:

- Is the value of RSPEED greater than +10 and is the switch pressed?
- Are the contents of RSPEED less than -10 and is the switch pressed?

*continued on page 63*

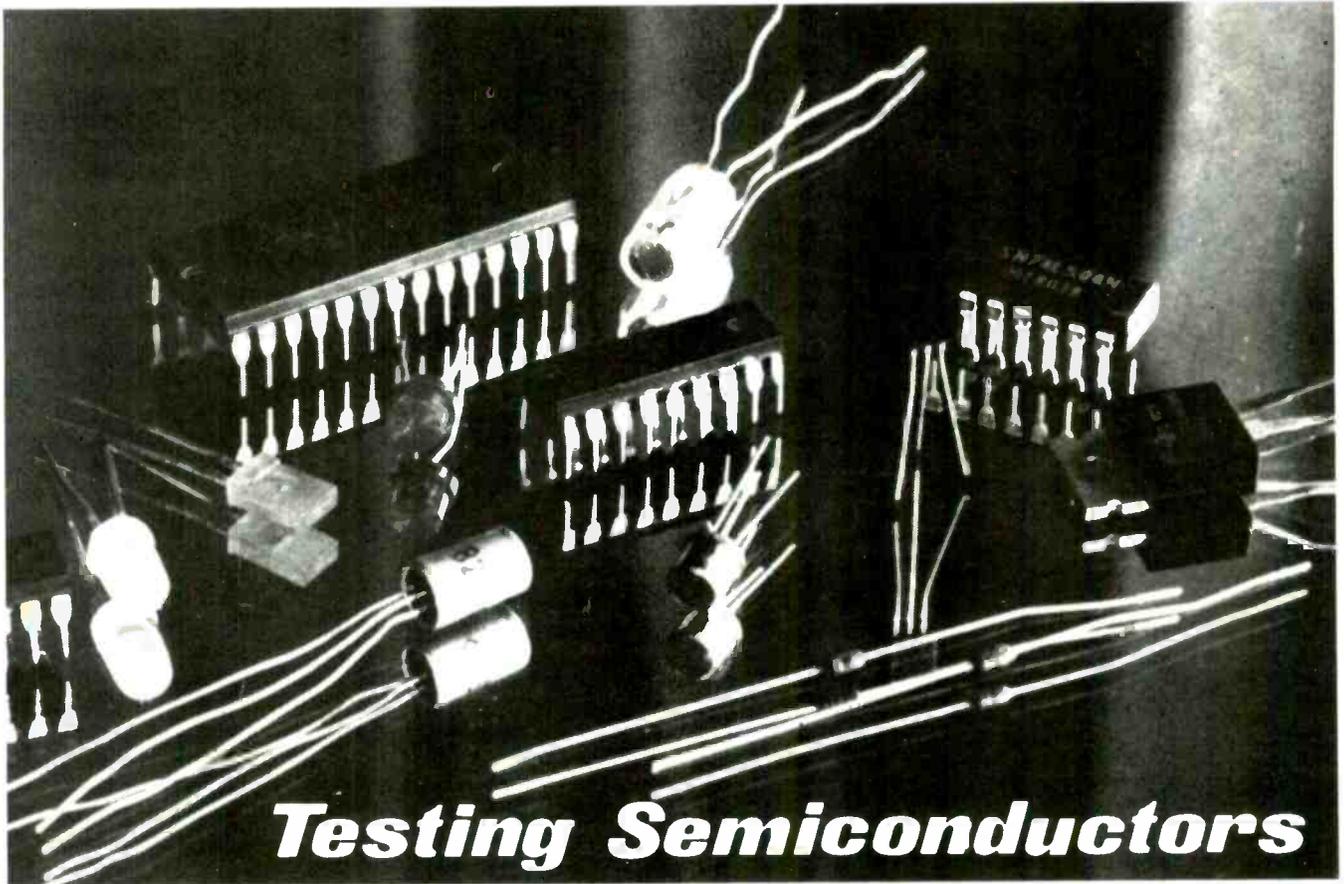

## Testing Semiconductors

Op-amp characteristics and how to measure them

TJ BYERS

**Part 6** THIS MONTH WE'LL turn our attention to a device that is a staple in electronics: the operational amplifier.

The term operational amplifier (op-amp) was coined some years ago to describe the building blocks of analog computers; they performed integration, multiplication, subtraction, and other mathematical operations. Today, mathematical functions are largely performed by digital circuits, and we find that the widest application of the op-amp is in signal conditioning.

### Op-amp basics

There are many different types of op-amps available: they're based on bipolar, JFET, and MOSFET technologies. Regardless of internal makeup, all op-amps function in a similar manner. That is, any voltage difference between the two inputs is reflected in some form at the output. If the input signals are equal, the output voltage will be zero.

In many ways, the op-amp possesses the characteristics of the ideal amplifier: infinite-input impedance, zero-output im-

pedance, infinite bandwidth and gain, and zero noise. In fact, quantifying the ways in which an op-amp differs from the ideal amplifier is the subject of this article.

### Input bias current

Ideally, an operational amplifier has infinite input resistance; realistically, it doesn't. The input transistors must have a finite bias current before they will function properly; and for current to flow there must be a finite impedance.

The value of that impedance varies depending on the type of device. Bipolar-transistor inputs consume quite a bit of current (nanoamps), and have the lowest input impedance. JFET's fare better, and MOSFET's, with their miserly picoampere input requirements, very nearly approach the ideal, with input impedances exceeding 10,000 megohms.

Input bias current is relatively independent of input voltage, and that makes measuring it easy. Input bias can be measured using the circuit shown in Fig. 1. Simply apply a voltage to the input and then read the bias currents directly from the meter.

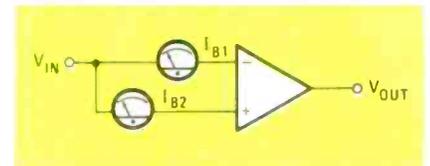


FIG. 1—MEASURE INPUT OFFSET CURRENT of each input separately by applying a common voltage to each.

### Input offset current

In the ideal amplifier, operational characteristics of both inputs would be identical. In real life, though, there is always some difference between the two input transistors.


One difference is called input offset current: it's labeled  $I_{OS}$ , and is calculated as the difference between  $I_{B1}$  and  $I_{B2}$ :

$$I_{OS} = I_{B1} - I_{B2}$$


In that formula,  $I_{B1}$  is the inverting input's bias current and  $I_{B2}$  is the non-inverting input's bias current.

Actually, to obtain the true value of the bias current, the two input currents must be averaged:

$$I_{OS} = (I_{B1} + I_{B2}) / 2$$

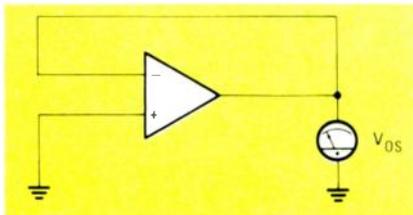

**FIG. 2—MEASURE INPUT OFFSET VOLTAGE** by grounding the non-inverting input. With a bipolar power supply, the inverting input is held at virtual ground by the op-amp's output.

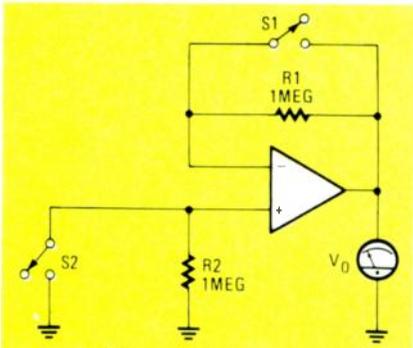

**FIG. 3—OFFSET VOLTAGE AND CURRENTS** may be measured with this circuit, depending on the state of S1 and S2.

As before,  $I_{B1}$  refers to the inverting input and  $I_{B2}$  refers to the non-inverting input.

### Input offset voltage

Another result of mismatched differential-amplifier inputs is offset voltage,  $V_{OS}$ . The error is reflected as a voltage at the output when both of the inputs are grounded.

A test circuit for measuring  $V_{OS}$  is shown in Fig. 2. Looking at the circuit, however, we see that only one input is directly tied to ground; the other is at a *virtual ground*. That concept is important in understanding how op-amps work. One of the basic properties of an ideal op-amp is that its differential input voltage is zero. Hence, when the non-inverting input is tied low, the sum of the voltages at the inverting input must also be zero, or at ground. That sum consists of the input signal and the feedback.

In an ideal device, with no input signal there would be no output. But, in a real device mismatched base-to-emitter (or gate-to-source, as the case may be) voltages between the input transistors will cause a DC offset voltage at the output. Input offset voltage is defined as the voltage necessary at the inputs to bring the output to zero.

Returning to Fig. 2, in that configuration, the op-amp attempts to balance its inputs by forcing the inverting input voltage high or low to compensate for any voltage difference between the two inputs. The result ( $V_{OS}$ ) can be read directly with a voltmeter.

A circuit that allows you to measure all three characteristics (offset voltage and

the input bias currents) is shown in Fig. 3.  $V_{OS}$  is measured by closing both switches S1 and S2. The value is read directly from the meter.

The input bias currents are measured by alternately opening each switch. With S1 open and S2 closed, we read an offset voltage that we'll call V1. Closing S1 and opening S2 gives us V2.  $I_{B1}$  is calculated from this formula:

$$I_{B1} = V1 - V_{OS}$$

$I_{B2}$  is calculated in a similar manner:

$$I_{B2} = V2 - V_{OS}$$

The calculated bias currents are displayed in microamps.  $I_B$  is derived by averaging  $I_{B1}$  and  $I_{B2}$ ;  $I_{OS}$  is the difference between them (in microamps).

### Variations in offset parameters

The values of  $I_{OS}$  and  $V_{OS}$  are dependent on the gains of the input transistors. Generally, the lower the gain of a transistor, the less the offset parameter will be affected. Lower input gains, however, tend to increase input bias currents, and that reduces input impedance. In addition, open-loop gain of an amplifier also has a pronounced effect on the overall influence of the offset parameters.

### Temperature effects

Offset differences can be affected greatly by temperature change. It's not the offset itself that is the culprit. Offset voltage and current can be compensated for in a given circuit simply by using trimmer potentiometers.

The problem is in the tracking of the offset values. Even "perfectly" matched transistors have slightly different temperature curves. The differences arise because of slight temperature gradations within the semiconductor substrate of the device itself, and because of impurities that are introduced during the manufacture of the device.

The result is that one transistor's leakage current or offset voltage can change at a rate that is faster than that of the other transistor, thereby creating mismatched outputs. For example, an offset voltage that is handily compensated for at room temperature may prove too much to han-

dle at 125°F. The overall effect is called temperature drift.

All op-amps are designed to minimize the effects of temperature drift—some just do it better than others. The effects of temperature drift can be measured using the circuit shown in Fig. 3. With both S1 and S2 closed, record the value of  $V_{OS}$  at room temperature. Now raise the temperature and note how  $V_{OS}$  changes. With properly tracking transistors, the change should be slight, if it's noticeable at all. The table in Fig. 4 shows how input bias current of a typical device varies with changes in temperature.

Temperature drift is normally expressed numerically in terms of temperature coefficient. The temperature coefficient of offset voltage is calculated from this formula:

$$\text{TEMPERATURE COEFFICIENT} = \frac{\delta V_{OS}}{\delta T}$$

and the temperature coefficient of offset current is calculated:

$$\text{TEMPERATURE COEFFICIENT} = \frac{\delta I_{OS}}{\delta T}$$

Temperature coefficient usually is specified in units of microvolts per degree Centigrade ( $\mu V/^\circ C$ ) and in units of microamps, nanoamps, or picoamps per degree Centigrade ( $\mu A/^\circ C$ ,  $nA/^\circ C$ , or  $pA/^\circ C$ ), depending on the type of device.

Remember, we're not concerned with the actual change in input bias—it will fluctuate. What concerns us is that the individual input currents change together. The smaller the temperature coefficient, the better the two inputs track.

### Aging


Another factor that influences how an op-amp works is aging. Op-amp characteristics have a tendency to change as operating time increases. Change is especially noticeable in the offset values. Devices that change much can be inconvenient to use, because the equipment in which they're used may have to be calibrated fairly often.

Aging is accelerated with continuous exposure to elevated temperatures—such as that frequently experienced inside an enclosure. Fortunately, aging is not a continuous process. Most changes take place within the first 100 hours of operation. Once stabilized, you can expect an amplifier to perform very reliably over the next 10,000 hours or so.

In fact, forced aging is one way to increase life and enhance the performance of a part, as we shall learn later on in this series.

### Common-mode rejection ratio


Another consequence of imperfect matching is common-mode voltage. Nor-

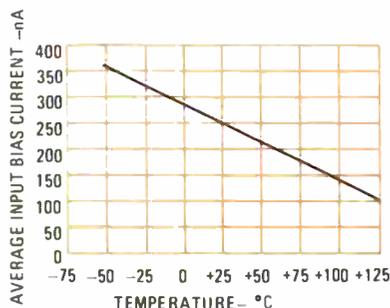


**FIG. 4—INPUT BIAS CURRENT** is a function of temperature.

mally you see it expressed as the common-mode rejection ratio. The common-mode rejection ratio is an important—yet often misunderstood—parameter.

In an ideal amplifier, both inputs—inverting and non-inverting—amplify equally. So, theoretically, identical signals to both inputs should be expected to

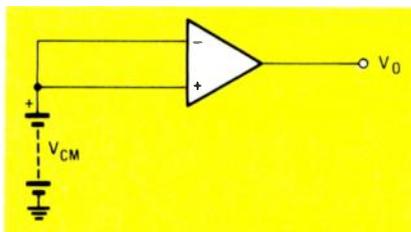

**FIG. 5—SLIGHT GAIN DIFFERENCES** between the inverting and the non-inverting inputs produce an erroneous output voltage. The ratio of the output voltage to the common-mode input voltage is the common-mode rejection ratio.

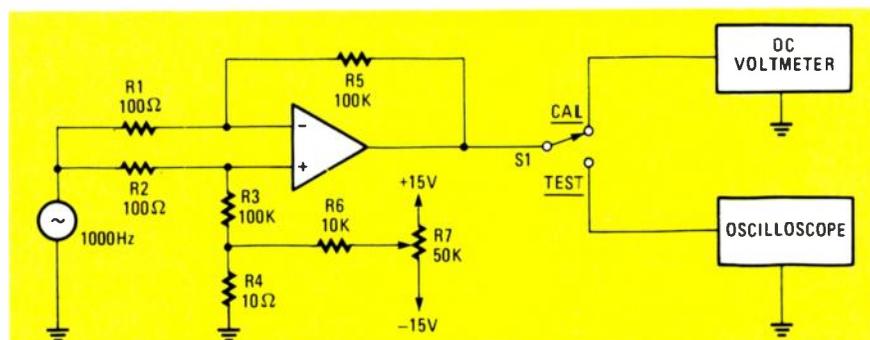

**FIG. 6—TO MEASURE CMRR,** use this test setup. With the 1000-Hz source off, adjust R7 for zero volts DC. Next, apply the test signal and measure the output with the oscilloscope. Last, calculate CMRR as discussed in the text.

result in zero output.

Unfortunately, that's not the case. Due to slight differences in the gain between the two inputs, some output voltage usually is produced for a common-mode input voltage.

Common mode refers to the fact that both inputs are referenced to the same identical source. One way to produce a common-mode condition is to tie the two inputs together and bias them above ground, as illustrated in Fig. 5. The output voltage of that circuit is the common-mode error voltage.

Common-mode error voltage, however, is not a useful parameter. It changes according to the gain of the amplifier and common-mode input voltage. Consequently, it is an ambiguous measurement that is dependent upon circuit conditions and does not relate easily to another amplifier for comparison.

The *ratio* between the common-mode output voltage and the common-mode input voltage, on the other hand, is a constant quantity. It is expressed by the term common-mode rejection ratio—or—more usually—CMRR.

Simply put, CMRR is the amount of resistance the amplifier offers to produc-

ing erroneous common-mode outputs. The higher the value of the CMRR, the smaller the common-mode error.

Although common-mode rejection ratio is a DC quantity, it is more easily measured with an AC source. The circuit shown in Fig. 6 shows one way of determining CMRR.

In that circuit, the common-mode input signal is derived from a 1-kHz signal generator that drives two identical resistors, R1 and R2. The common-mode voltage is developed across the series combination R2 and R3. The 50K potentiometer (R7) compensates for input offset voltage.

To use the test circuit, with no AC input, adjust the 50K potentiometer until the DC voltmeter reads 0 volts. Now set the signal generator to 1 kHz with an amplitude of 1 volt. Measure the AC output voltage, and calculate CMRR as follows:

$$CMRR = 100 / V_O$$

$V_O$  is the AC voltage measured by the scope.

CMRR numbers are rather large, and that makes them difficult to work with. So CMRR is most-often expressed in decibels. The conversion is easily made using this equation:

$$CMRR \text{ dB} = 20 \log (100 / V_O)$$

Monolithic operational amplifiers typically display CMRR values on the order of about 100 dB.

Be aware that the value of CMRR is valid only over a limited common-mode input range. Fortunately, that range is rather large, usually exceeding 90% of the power-supply voltage. Input voltages outside the limit often produce very high common-mode output voltages. However, errors due to CMRR only arise in applications in which the amplifier is used in the non-inverting or the differential configuration. Inverting amplifiers tend to cancel out CMRR error.

Unfortunately, that's all we have room for this time. In the next installment we'll continue our discussion of op-amp test procedures, and we'll show a special circuit for measuring various op-amp characteristics. **R-E**

## R-E ROBOT

*continued from page 60*

- Are the contents of RSPEED between -10 and +10 or is the switch released?

You will see the three IF/THEN statements that test those cases.

Assuming motion is going to take place, RFWD (right-motor forward) or RREV (right-motor reverse) is executed. Those words enable the appropriate relay and disable the other so that motion takes place in the desired direction. It is important to notice that the relays are set before the motor is enabled. That prevents inrush currents from damaging the relay.

Next, the value of RSPEED is fetched and used as an argument to SPEED-CONV. SPEED-CONV takes an argument (from the stack) that is proportional to the speed and returns an argument (on the stack) that is the period of the motor control-frequency generator. Speed may vary from 0 to 128. When reverse motion has been requested, the speed argument is negative. We could NEGATE it before passing it to SPEED-CONV; however, it is more convenient to have SPEED-CONV use the ABS operator to make sure all arguments are positive.

As shown in lines 5 and 9 of screen 36, the output of SPEED-CONV is passed directly to RMTR-PERIOD (right-motor period), which sets the frequency of the 8253 control element in the right motor's phase-locked loop circuit on the control board.

Last, ENABLE-RIGHT (again shown in lines 5 and 9 of screen 36) electronically enables the high-power output stage of the motor-control circuit. If no motion is going to take place, STOP-RIGHT is executed. The code is identical for the left motor; it is shown in screen 35.

Moving on to screen 34, INTERROGATE reads channel 0 of the analog-to-digital converter, converts it to the -128 to +127 range and stores the result in both LSPEED and RSPEED. Next channel 1 (sideways displacement) is read. That result is converted to the  $\pm 128$  range and passed as an argument to DIFF-CONVERT on the stack. The result is duplicated (DUP), one copy negated (NEGATE) and used to alter the contents of LSPEED and RSPEED.

### Low-level control

Now we start getting into the low-level words shown in screen 33. Those words could be rewritten many different ways and the overall program would still function the same, but the response would change. For example, SPEED-CONV could be rewritten to provide a greater range of motion, limit the top speed, or provide a constant speed.

*continued on page 86*

## USING TRIACS AND SCR'S

SCR's and Triacs are high-speed, solid-state switches used in AC- and DC-power control applications. Find out how they work and practical applications for them.

RAY MARSTON

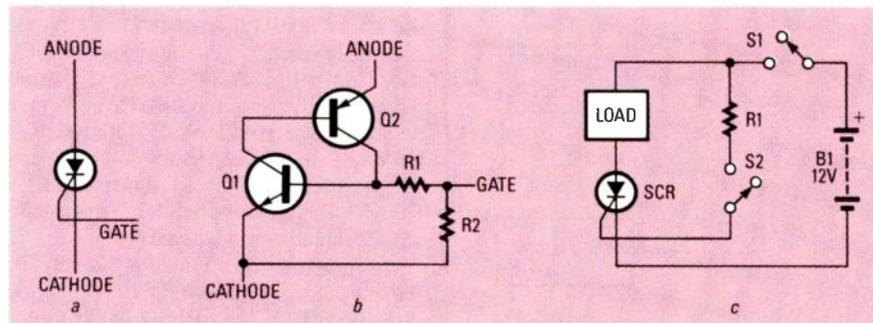


FIG. 1—THE SCR'S SYMBOL (a) and equivalent circuit (b) are shown here. In (c) is shown how the SCR can control a DC-operated load.

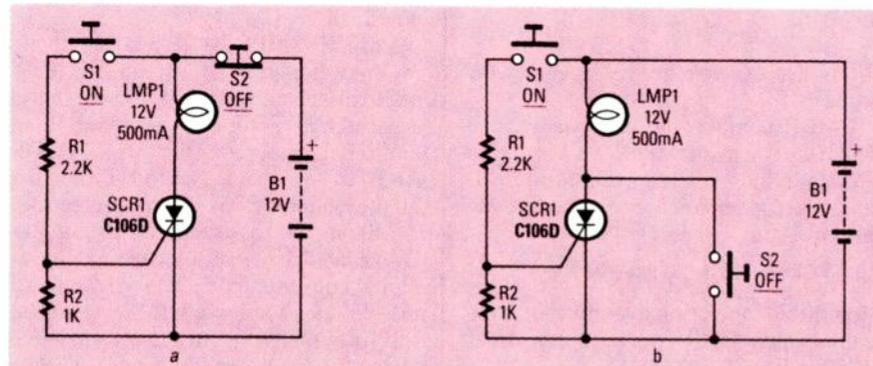


FIG. 2—PRACTICAL SCR CONTROL CIRCUITS are shown in (a) and (b). Both circuits have separate on and off switches.

SCR'S AND TRIACS ARE BOTH MEMBERS OF the thyristor family. The SCR (Silicon Controlled Rectifier), is a four-layer (PNPN) sandwich of semiconductor material. Its symbol is shown in Fig. 1-a, and its equivalent circuit is shown in Fig. 1-b. The circuit is a complementary regenerative switch in which Q1's base current is derived from the collector of Q2, whose base current is in turn derived from the collector of Q1. We'll discuss that regenerative action in much greater detail shortly.

Figure 1-c shows the basic circuit that lets you use the SCR as a switch in a DC

power-control circuit. The circuit works as follows. When power is first applied to the SCR by closing S1, the SCR is "blocked" and appears as an open-circuit switch. That action can be understood by examining Fig. 1-b, where it can be seen that, because Q1's base is shorted to the cathode terminal via R1 and R2, Q1 is cut off through lack of base current. Therefore Q1 feeds no base current to Q2, so it is also cut off. Because both transistors are cut off, only a small amount of leakage current can flow between the anode and cathode terminals.

The SCR can be turned on (made to act

like a closed switch or a forward-biased silicon rectifier) simply by applying a positive gate current. That can be done in the circuit shown in Fig. 1-c simply by closing S2. The gate current thus applied causes the SCR to switch on very quickly.

If the externally applied gate current is sufficiently large, it will cause Q1 to start to turn on. As it does, its collector current feeds Q2's base, thereby causing Q2 to turn on and feed additional base current to Q1, and so on. The way in which the two transistors feed each other is called regenerative switching.

After the SCR turns on and is conducting significant forward current, the SCR stays on even if gate drive is subsequently removed. Therefore, only a brief pulse of gate current will be needed to latch the SCR on. Note in Fig. 1-b that, because of the presence of R1 and R2, the SCR cannot be turned off by shorting or reverse-biasing the gate-cathode terminals of the device.

In fact, the only way of turning the SCR off is by momentarily reducing its anode current below a value known as the *minimum holding current* ( $I_H$ ). So it follows that turn-off occurs automatically in an AC circuit near the zero-crossing point at the end of each half cycle.

A finite amount of internal capacitance exists between anode and gate of an SCR. Consequently, if a sharply rising voltage is applied to the anode, that internal capacitance can cause part of the rising voltage to break through to the gate and thus trigger the SCR on. That "rate effect" turn-on can be caused by supply-line transients, and it sometimes occurs at the moment when power is applied to the SCR's anode. Rate-effect problems can usually be overcome by wiring a simple RC "snubber" network between the anode and the cathode of an SCR; the network limits the rate-of-rise to a safe value.

Those are the basic characteristics of the SCR. As you can see, it's a fairly simple device. When choosing an SCR for a particular application, you'll usually find that the most-significant parameters are the peak voltage and current ratings, the gate sensitivity rating, and (occasionally) the value of the device's minimum holding current. Table 1 lists basic specifications of several popular SCR's.

### Basic DC circuits

SCR's are used in both AC and DC power-control circuits; let's look first at some basic DC circuits. Two ways of using the SCR as a pushbutton-controlled power switch are shown in Fig. 2. In both circuits, the SCR (and thereby the lamp) can be latched on by momentarily closing S1, thereby feeding gate drive to the SCR via R1. In both circuits the gate is tied to

TABLE 1—POPULAR SCR'S

Device	PIV	Current rms average	$V_{GT}$ (max)	$I_{GT}$ (max)	$I_H$ (max)
C106D	400V	4A 2.5A	0.8V	0.2mA	3mA
2N3525	400V	5A 3.2A	2V	15mA	20mA
BT109	500V	6.5A/4A	2V	15mA	3mA
IR122A	100V	8A 5A	1.5V	25mA	30mA
IR122D	400V	8A 5A	1.5V	25mA	30mA
C116D	400V	8A 5A	1.5V	20mA	35mA
C126M	600V	12A 7.5A	1.5V	30mA	35mA

the cathode via R2 to improve stability of the circuit.

Of course, after the SCR turns on, it can be turned off again only by momentarily reducing anode current below the device's  $I_H$  value. In Fig. 2-a the SCR is turned off by momentarily opening S2; in Fig. 2-b that is done by using S2 to short the anode and cathode terminals of the SCR momentarily.

Figure 3 shows another way of turning the SCR off. Here, after the device turns on, C1 charges up to almost the full supply voltage via R3 and the anode of the SCR. When S2 is subsequently closed, it clamps the positive end of C1 to ground, and the charge on C1 forces the anode of the SCR to swing negative momentarily,

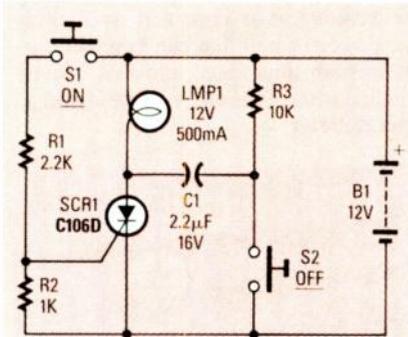


FIG. 3—CAPACITOR TURN-OFF CIRCUIT: C1 charges via R3 so that its right side is positive. When S2 is closed, C1 dumps its charge into the SCR (which is oppositely polarized), thereby turning it off.

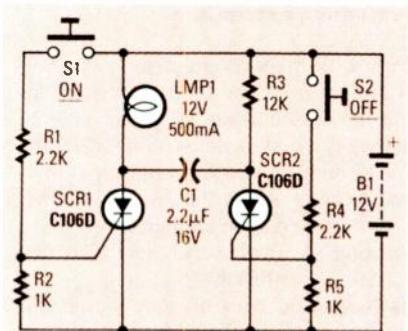


FIG. 4—ANOTHER CAPACITOR TURN-OFF circuit uses a second SCR (SCR2) to control charge dumping by C1.

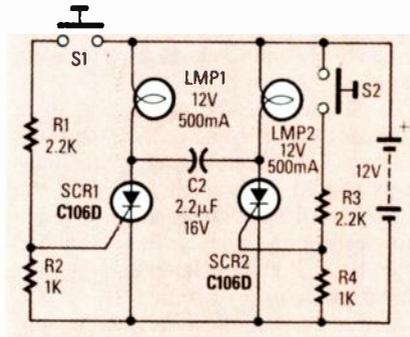


FIG. 5—A BISTABLE LATCH (or flip-flop) can be built from two SCR's.

thereby reverse-biasing the SCR and causing it to turn off. The capacitor's charge bleeds away rapidly, but it has to hold the SCR's anode negative for only a few microseconds to ensure turn-off. Note that C1 must be a non-polarized type.

A variation of the capacitor turn-off circuit is shown in Fig. 4. A slave SCR (SCR2) replaces the turn-off switch (S2) in Fig. 3. The master SCR (SCR1) is turned off by briefly turning on SCR2 via S2. The slave SCR turns off after S2 is released, because the anode current provided by R3 is lower than SCR2's holding current.

Figure 5 shows how the previous circuit can be modified so that it acts as a bistable latch (flip-flop) that drives two independent lamps. To understand how it works, assume first that SCR1 is on and SCR2 is off, so that C1 is fully charged, with its LMP2 end positive. The state of the circuit can be changed by pressing S2. As SCR2 turns on, it turns SCR1 off capacitively via its anode. Capacitor C1 then recharges in the opposite manner (i. e., the left end is now positive). The state of the circuit can be changed again by pressing S1, thus driving SCR1 on by way of its gate, and driving SCR2 off capacitively via its anode.

The DC circuits that we have looked at so far have all used simple resistive loads (lamps), and they have inevitably produced a self-latching action in the SCR's. The circuit shown in Fig. 6, however, shows a simple DC alarm that drives a

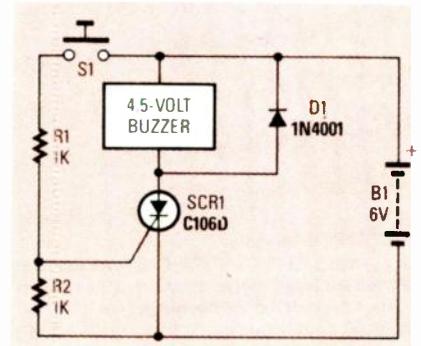


FIG. 6—A BUZZER (or other self-interrupting device) can be used to build an SCR power controller that remains on only so long as S1 is pressed.

"self-interrupting" load, such as a bell or a buzzer. That circuit provides a non-latching action.

When a self-interrupting device is connected to a voltage source, a current flows through a voltage source, a current flows through a built-in solenoid via a pair of contacts. That current induces a magnetic field in the solenoid, and it causes a striker to fly outwards and open the contacts, thereby causing the current to fall to zero and the magnetic field to collapse. After the field collapses, the striker releases and the contacts close again, so current is again applied to the solenoid. That oscillatory action will repeat *ad infinitum*, as long as power is applied to the circuit.

The point is that that type of load functions as a switch that repeatedly opens and closes. When a load of that sort is connected to the Fig. 6 circuit, therefore, the circuit does not latch in the normal way, so the alarm operates only as long as S1 is closed. Because of the inductive nature of that type of load, a damping diode (D1) must be wired across it.

The circuit can be modified to provide a self-latching action simply by wiring a 470Ω resistor in parallel with the alarm, as shown in Fig. 7. The circuit latches because the anode current of the SCR does not fall to zero when the alarm self-interrupts, but to a value that is deter-



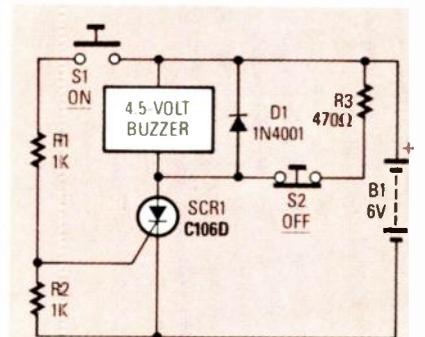



FIG. 7—ADDING A RESISTOR (R3) to the previous circuit allows you it to latch on. Turn it off by pressing S2.

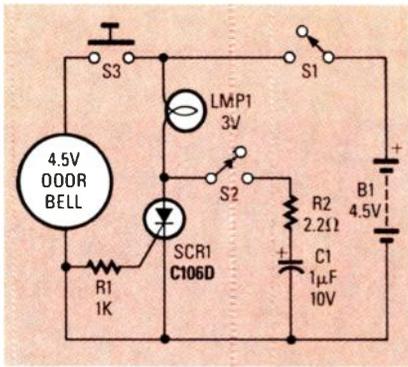


**FIG. 8—RATE-EFFECT TURN-ON:** Note that the SCR has no input signal connected directly to its gate. Closing S1 does not trigger the SCR, but closing S3 does. However, by filtering the spikes generated by the doorbell (by closing S2), the SCR once again will not turn on.

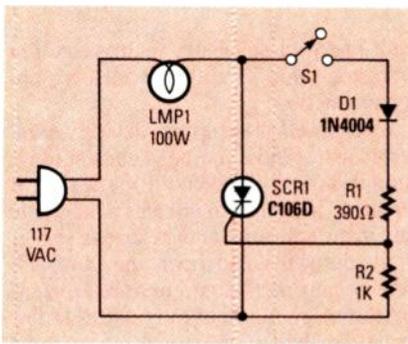

**FIG. 9—AC POWER-CONTROL CIRCUIT:** Close S1 to apply power to the load. After opening S1, the circuit will de-energize at the next zero crossing of the AC signal. Power is only delivered to the load during positive half-cycles.

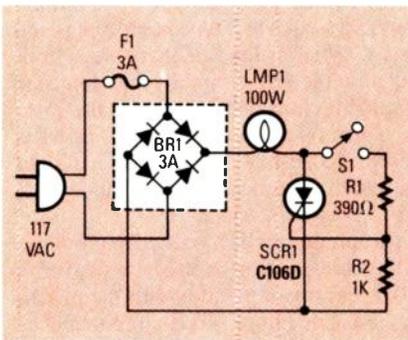

**FIG. 10—FULLWAVE POWER-CONTROL CIRCUIT:** Power will be delivered to the load during each AC half-cycle.

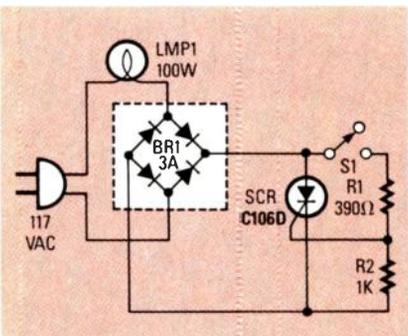

**FIG. 11—ALTERNATE FULLWAVE** power-control circuit places the load in series with the AC side of the bridge, rather than the DC side, as in the previous figure.

mined by the value of R3. The circuit can be unlatched by pressing S2, thereby enabling the anode current to fall to zero when the alarm self-interrupts.

To complete our discussion of DC SCR circuits, Fig. 8 shows a circuit that can be used to demonstrate the rate-effect turn-on of the SCR, and a method of suppressing rate-effect turn-on. In that circuit the SCR uses a 3-volt lamp as its anode load, and it is connected to the 4.5-volt battery supply via S1. In addition, a 4.5-volt doorbell can be connected across the supply via S3; the doorbell allows transient modulation to be applied to the supply line, and thereby to the anode of SCR1. That modulation can cause rate-effect turn-on of the SCR, which has a critical rate-of-rise value of 20 volts/μs. The snubber formed by R2 and C1 can be used to defeat rate-effect turn-on by closing S2.

To demonstrate the rate-effect, open S2, close S1, and then close S3 so that the bell rings. The resulting supply line transients should be enough to trigger the SCR and turn the lamp on; if not, wire a 1-ohm resistor in series with the battery. After the SCR and the lamp turn on, they can be turned off by opening S1.

To demonstrate the effect of the suppresser network, close S2 and S1, and then operate the doorbell via S3. The resistance of the lamp (in combination with R2) acts with C1 as a smoothing network that reduces the rate-of-rise of the anode modulation signal, thereby protecting the SCR against false triggering. The reason that R2 is wired in series with C1 is to limit the capacitor's discharge current to a safe value when the SCR triggers on a legitimate signal.

### Basic AC circuits

Figure 9 shows a basic halfwave on/off circuit driving a 100-watt lamp from the AC power line. With S1 open, no gate drive is applied to the circuit, so the SCR and the lamp are off. When S1 is closed, during a negative half-cycle, the SCR is reverse-biased, and gate signals are inhibited by D1, so the SCR is off. On a positive half-cycle, however, the full available line voltage is applied to the gate via the lamp, D1, and R1.

Shortly after the start of the half-cycle, sufficient voltage is available to trigger the SCR, so it turns on. As it does, its anode voltage falls to near zero, thus removing the gate drive, but the SCR remains self-latched for the duration of the half-cycle. The SCR automatically turns off again when the half-cycle ends and anode current falls to zero.

That circuit provides halfwave operation only. Figures 10 and 11 show two ways of obtaining fullwave operation. In those circuits, the AC is converted to unsmoothed DC via a bridge rectifier, and the rough DC is applied to the SCR. With S1 open the SCR is off, so zero current

flows through the bridge and the load. When S1 is closed, however, the SCR is driven on shortly after the start of each half-cycle of rough DC, so power is applied to the load during both half-cycles.


As the SCR goes on in each half-cycle, gate drive is removed automatically, but the SCR stays latched on for the duration of the half-cycle. The SCR switches off at the end of each half-cycle as its anode current falls to zero, so power is removed from the load when S1 is opened.

In the Fig. 10 circuit the load is connected to the DC side of the bridge. A fuse must be placed on the AC side of the bridge to protect against a possible short in the bridge. However, in the Fig. 11 circuit, the load is placed on the AC side of the bridge. No fuse is needed in that circuit because the load itself will limit currents to a safe value in the event of a bridge failure. You may, however, wish to include a fuse anyway, to protect against a possible load failure.

A pair of SCR's can be wired in inverse parallel (anode to cathode and cathode to anode) to provide fullwave power control without using a bridge rectifier. However, a far more effective way of obtaining fullwave power control is to use a Triac rather than a pair of SCR's.

### Basic Triac theory

You can think of a Triac as two conventional SCR's connected in inverse parallel, arranged so that they share a single gate terminal. The Triac acts as a solid-state power switch that can conduct current in both directions, and that can be switched from off to on by a gate signal of either polarity.

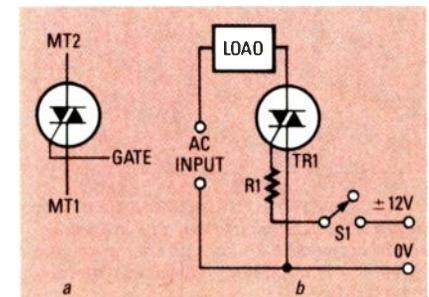

**FIG. 12—THE TRIAC'S** symbol (a) and basic control circuit (b) are shown here.

Figure 12-a shows the Triac's symbol, and Fig. 12-b shows the basic circuit for using the device as an AC power switch. The load is wired in series with the Triac's main terminals, and the combination is wired directly across the AC power line. DC gate drive can be applied to the Triac by closing S1. The basic characteristics of the Triac are as follows.

1. Normally, with no gate signal applied, the Triac is off and functions as an open-circuit switch.

2. If MT2 is appreciably positive or negative with respect to MT1, the Triac

TABLE 2—POPULAR TRIAC'S

Device	PIV	Current rms	V <sub>GT</sub> (max)	I <sub>GT</sub> (max)	I <sub>H</sub> (max)
C206D	400V	3A	2V	5mA	30mA
2N6073	400V	4A	2.5V	30mA	70mA
C226D	400V	8A	2.5V	50mA	60mA
SC146D	400V	10A	2.5V	50mA	75mA
TIC246D	400V	15A	2.5V	50mA	50mA

therefore dangerous. That snag can be overcome in the UJT-triggered isolated-input circuit shown in Fig. 14. In that circuit, as long as S1 is closed, the UJT oscillates at several kHz and thus delivers roughly 50 trigger pulses to the gate of the Triac (via isolation pulse transformer T1) during each half-cycle of the AC power line waveform. Consequently, the Triac is fired by the first trigger pulse occurring in each half-cycle; that pulse occurs within a few degrees of the start of the half-cycle. The point is that the Triac is on almost constantly while S1 is closed, so virtually full power is applied to the load.

Figure 15 shows how the Triac can be used as a simple line switch with line-derived triggering. With S1 open, no gate drive is applied, so the Triac and the lamp are off. Suppose, however, that S1 is closed. At the start of each half-cycle the Triac is off, so voltage is applied to the gate via the lamp and R1. Shortly after the start of the half-cycle, enough drive is available to trigger the Triac, so it and the lamp go on. As the Triac goes on and self-latches, it saturates and thereby removes gate drive until the start of the next half-cycle, thus minimizing R1's dissipation.

The circuit in Fig. 15 can be modified to

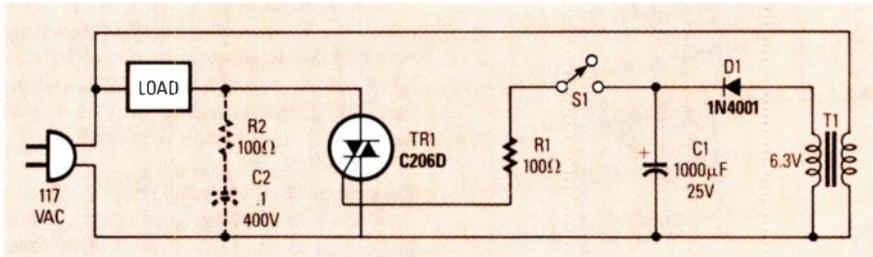


FIG. 13—STEP-DOWN TRANSFORMER T1 provides a low-voltage DC signal for triggering the Triac. The optional R2-C2 network can be used to suppress RFI.

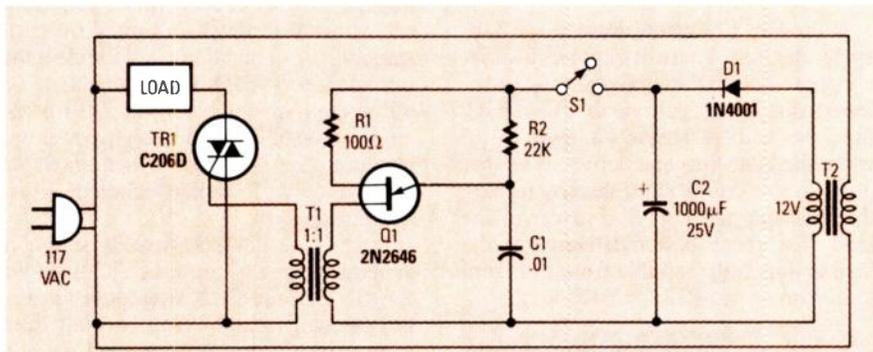


FIG. 14—THE CONTROL CIRCUIT connected to the secondary of T2 causes UJT Q1 to oscillate at about 50 Hz. The secondary circuit is isolated from the primary circuit here, unlike the previous figure.

can be turned on by applying a brief pulse to the gate of the Triac. The device takes only a few microseconds to turn on. A saturation potential of one or two volts is developed across the Triac in the on state. After the Triac turns on, it self-latches and remains on for as long as main-terminal current continues to flow.

3. After the Triac self-latches, it can only be turned off again by reducing its main-terminal current below a minimum holding value. When the Triac is used as an AC power switch therefore, turn-off occurs automatically at the zero-crossing point at the end of each half-cycle, as main-terminal currents fall to zero.

4. The Triac can be turned on by either a positive or a negative gate signal, irrespective of the polarities of the main-terminal voltages. The device thus has four possible triggering modes or "quadrants." With current flowing through MT2 in either the positive or the negative direction, gate current can be either positive or negative. The differences among the four modes are primarily that the device's gate sensitivity is greater when both MT2 current and gate current are the same (positive or negative).

5. Triacs can handle very high surge currents. Typically, a device with a 10-amp (rms) rating may be able to handle a single-cycle non-repetitive 60-Hz surge current of 100 amps.

Table 2 shows basic specifications for several popular Triacs. The information presented there should be sufficient to help you to select a Triac for many applications. With the basics in mind, let's move on and look at practical ways of using the Triac.

### Basic Triac circuits

Figure 13 shows the circuit of a simple DC-triggered Triac power switch, in which the DC supply is derived via step-down transformer T1. When S1 is open, no current flows to the gate of the Triac, so it remains off. When S1 is closed, however, gate drive is applied to the Triac, so it and the load turn on. If an inductive load (a motor, for example) is used in this circuit, the R2-C2 snubber network must be wired in place as indicated to prevent false rate-effect triggering.

In that circuit the negative side of the DC supply is connected directly to one side of the AC power line, so it's live and

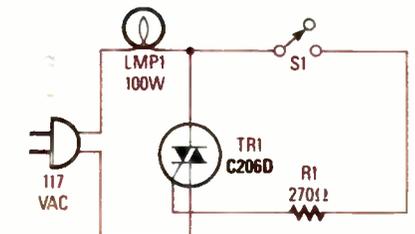


FIG. 15—SIMPLEST TRIAC CIRCUIT is composed of a switch, a resistor, and a Triac.

provide halfwave operation by placing a diode between S1 and R1. The diode's polarity will determine whether the Triac will trigger on positive or negative half cycles.

### Phase-triggered power control

The SCR and Triac circuits that we have looked at so far have all been designed to give a simple on off form of power control. The same devices can, however, easily be used to give fully-variable power control in AC circuits. In fact, they're widely used in lamp dimmers and electric-motor speed controllers, etc. The most widely used system of AC variable-power control is known as the *phase triggering* system.

In a basic phase-triggering circuit that uses a Triac as the power-control element, rather than triggering the Triac directly from the AC power line, it is triggered via a variable phase-delay network that is connected between the power line and the gate of the Triac.

Phase delay works like this. If the Triac

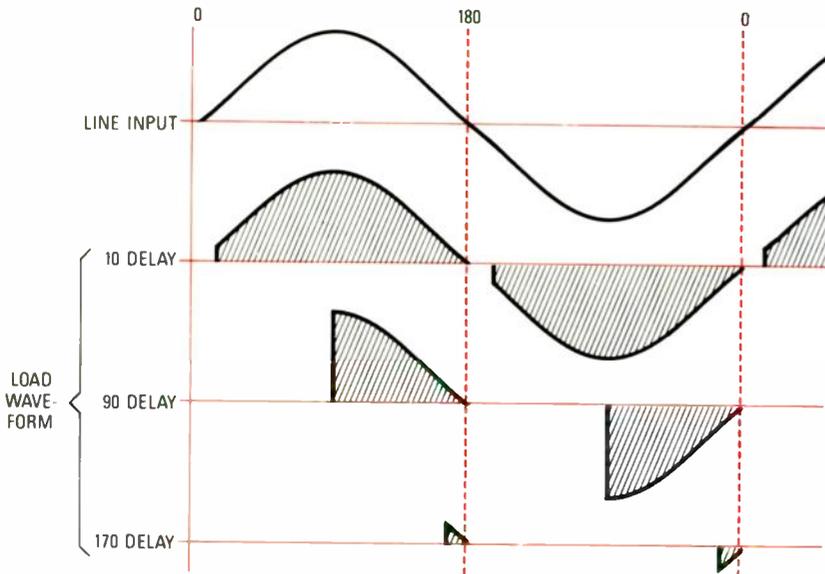


FIG. 16—A VARIABLE AMOUNT OF POWER is delivered to the load depending on when in the AC cycle the device is triggered.

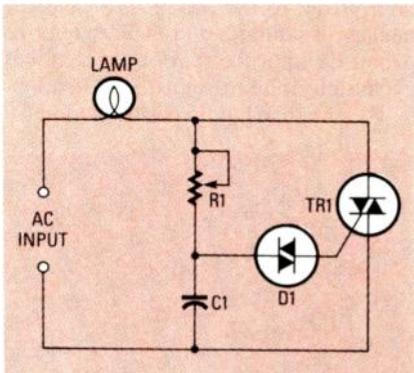


FIG. 17—A DIAC and an RC network provide a simple means of implementing a variable phase-delay network.

is triggered  $10^\circ$  after the start of each half-cycle, most of the power of that half-cycle is fed to the load. On the other hand, if the Triac is triggered  $90^\circ$  after the start of each half-cycle, only half the available power is fed to the load. Finally, if the Triac is triggered  $170^\circ$  after the start of each half-cycle, only a very small part of the available power is fed to the load. Figure 16 illustrates how phase delay works.

There are several methods of obtaining variable phase-delay triggering, but the three most popular ones are to use a line-synchronized UJT, a special-purpose IC, or a Diac/RC network. The latter approach is shown in Fig. 17.

The Diac can be regarded as a bilateral threshold switch. When connected across a voltage source, it functions as a high impedance until the applied voltage rises to about 35 volts, at which point it switches into a low-impedance state and remains there until the applied voltage falls to about 30 volts, at which point it reverts to the high impedance state. It stays in that state until the applied voltage rises to 35 volts, at which point the process repeats.

In the Fig. 17 circuit, during each half-cycle, the R1-C1 network applies a variably phase-delayed version of the AC waveform to the Triac's gate via the Diac. Each time the voltage across C1 rises to 35 volts, the Diac fires and delivers a trigger pulse to the Triac's gate, thereby turning the Triac on and applying power to the load. The mean power delivered to the load is thus fully variable from near-zero to maximum via R1.

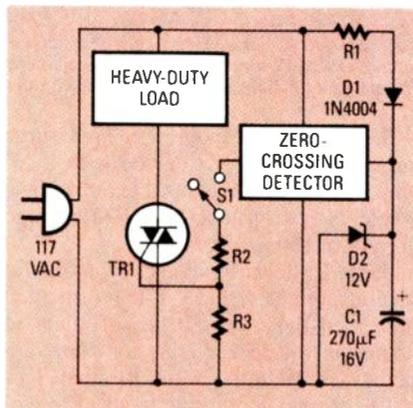


FIG. 18—A ZERO-CROSSING DETECTOR can be used to trigger a triac when power is at a minimum, thereby reducing RFI to a minimum.

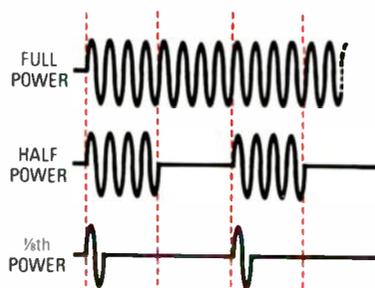


FIG. 19—AN INTEGRAL NUMBER OF CYCLES are passed by the zero-crossing detector to the load.

## Radio-frequency interference

Each time the Triac turns on, load current rises abruptly (in a few microseconds) from zero to a value determined by the load resistance and the instantaneous supply voltage. That transition generates RFI (Radio Frequency Interference). RFI is greatest when the Triac is triggered at  $90^\circ$ , and it is least when the Triac is triggered close to the  $0^\circ$  and  $180^\circ$  zero-crossing points of the waveform.

In a lamp-dimmer circuit where there may be considerable lengths of wiring between the Triac and the load, RFI may be offensive. So, in a practical lamp dimmer, the circuit is usually provided with an LC RFI-suppression network.

## Zero-crossing techniques

When a high-power load (an electrical heater, for example) is driven from Triac circuitry, special techniques must be used to minimize RFI. Even if the Triac is used as a simple on-off switch in such applications, a "spurt" of RFI will be generated each time the switch is turned on; that spurt will be of maximum amplitude if the instantaneous phase delay happens to be  $90^\circ$  at the moment of turn-on. RFI problems can be eliminated in high-power applications by using the synchronous or "zero crossing" gating technique illustrated in Fig. 18.

Here, a low-power 12-volt DC supply is generated directly from the AC lines via R1, D1, D2, and C1. A simple zero-crossing detector (which could be built from several transistors) is connected directly across the power line; it controls the passage of current from C1 to S1 in such a way that the C1 current is made available for only  $5^\circ$  or so on either side of each zero-crossing point of the waveform. So, if S1 is closed, a pulse of gate current is fed to the Triac at the start of each half-cycle at the point at which voltage is closest to zero. Therefore, the Triac always generates minimal RFI as it turns on.

The zero-crossing technique can be used to provide RFI-free variable power to a high-power load by replacing S1 with a variable mark/space-ratio waveform generator, so that a variable and integral number of complete AC cycles are alternately fed (or not fed) to the load.

Figure 19 illustrates the basic principle, in which the total integral period is equal to eight power-line cycles. If power is alternately switched on for four cycles and off for four cycles, the mean load power is equal to half the total available power, and if the power is on for one cycle and off for seven cycles, the mean power is equal to only one eighth of the total available power.

That concludes our discussion of the SCR and the Triac. In this article we've seen many practical example circuits. Now it's up to you to put them to use in your own designs.

R-E

# PC SERVICE

One of the most difficult tasks in building any construction project featured in **Radio-Electronics** is making the PC board using just the foil pattern provided with the article. Well, we're doing something about it.

We've moved all the foil patterns to this new section where they're printed by themselves, full sized, with nothing on the back side of the page. What that means for you is that the printed page can be used directly to produce PC boards!

**Note:** The patterns provided can be used directly only for *direct positive photoresist methods*.


In order to produce a board directly from the magazine page, remove the page and carefully inspect it under a strong light and/or on a light table. Look for breaks in the traces, bridges between traces, and in general, all the kinds of things you look for in the final etched board. You can clean up the published artwork the same way you clean up your own artwork. Drafting tape and graphic aids can fix incomplete traces and doughnuts, and you can use a hobby knife to get rid of bridges and dirt.

An optional step, once you're satisfied that the artwork is clean, is to take a little bit of mineral oil and carefully wipe it across the back of the artwork. That helps make the paper translucent. Don't get any on the front side of the paper (the side with the pattern) because you'll contaminate the sensitized surface of the copper blank. After the oil has "dried" a bit—patting with a paper towel will help speed up the process—place the pattern front side down on the sensitized copper blank, and make the exposure. You'll probably have to use a longer exposure time than you are used to.

We can't tell you exactly how long an exposure time you will need as it depends on many factors but, as a starting point, figure that there's a 50 percent increase in exposure time over lithographic film. But you'll have to experiment to find the best method for you. And once you find it, stick with it.

Finally, we would like to hear how you make out using our method. Write and tell us of your successes, and failures, and what techniques work best for you. Address your letters to:

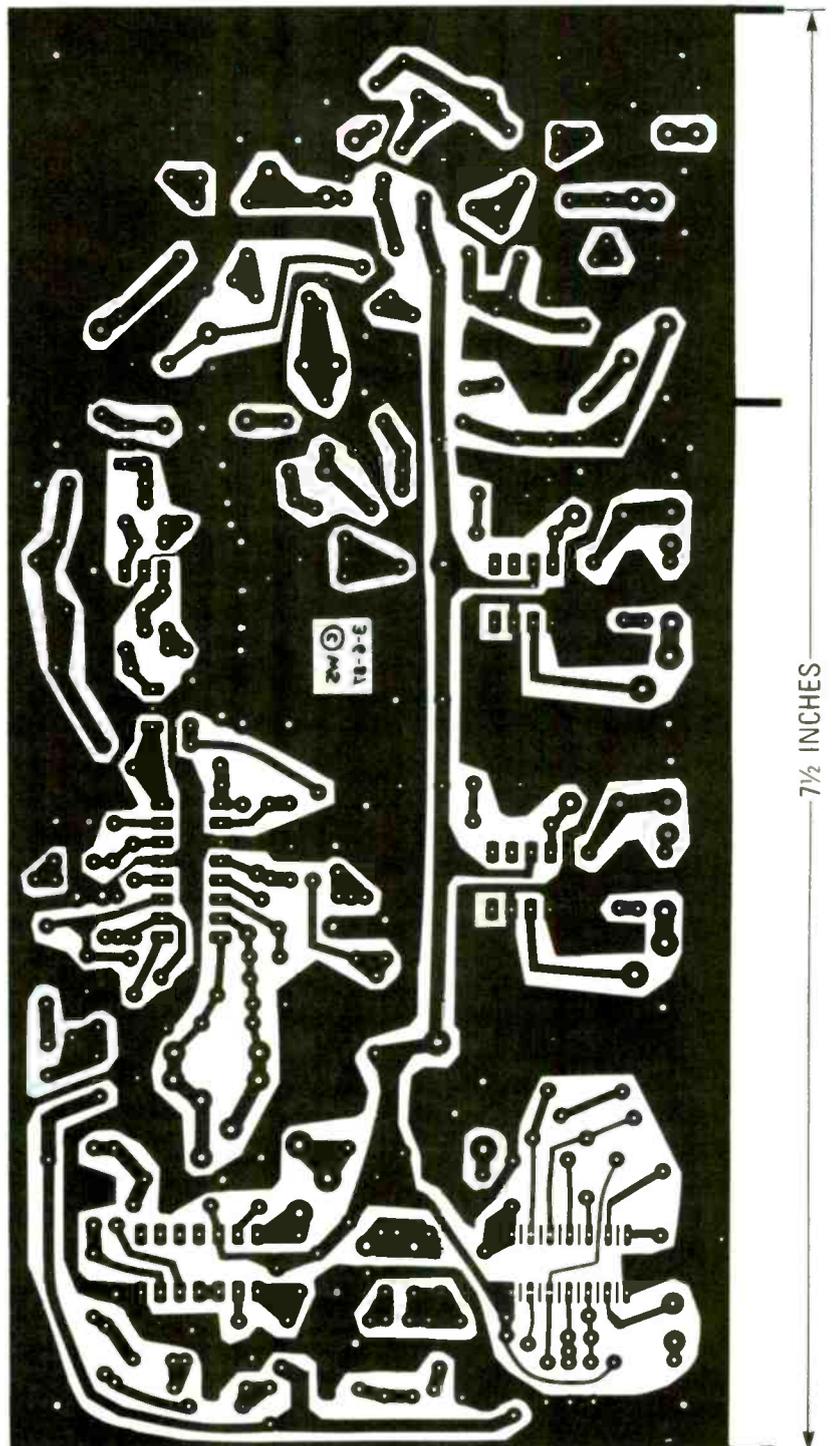**Radio-Electronics**  
Department PCB  
500-B Bi-County Blvd.  
Farmingdale, NY 11735



TUNE IN THE HIDDEN WORLD of FM radio with the SCA receiver. Most of the components mount on this single-sided PC board.

---

---

# PC SERVICE

# COMPUTER DIGEST

VOL. 4 NO. 9 SEPT. 1987

A NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS



BONDWELL 8



DATAVIEW 25



IBM PC CONVERTIBLE

## PORTABLE COMPUTERS

Hands-on tests of 7 hot models



NEC MULTISPEED

## GRAPHICS PROCESSORS

For fast, hi-res images



TOSHIBA T1100 PLUS



TOSHIBA T3100




ZENITH Z183

# CONTENTS


# SEPTEMBER

# 1987


Vol. 4 No. 9

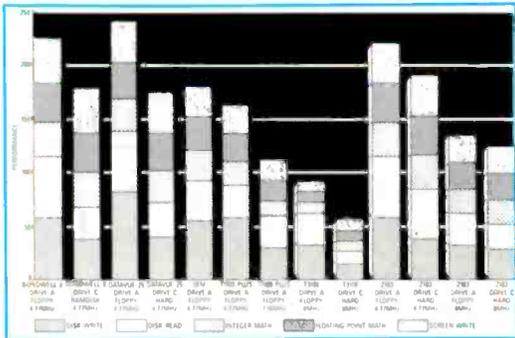

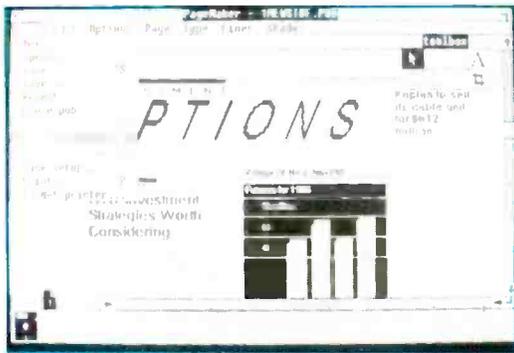**77 PORTABLE COMPUTERS**  
Hands-on reviews of seven hot portables



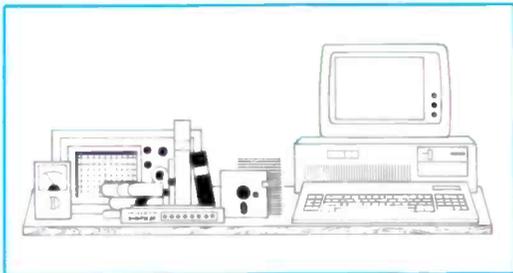**82 GRAPHICS CO-PROCESSORS**  
New chips enhance speed, cut costs



**73 EDITOR'S WORKBENCH**  
HARDWARE: Heathkit printer buffer  
SOFTWARE: Direc-link, The Brooklyn Bridge

# COMPUTER DIGEST

**Larry Steckler,**  
EHF, CET: publisher & editor in chief

**Art Kleiman,**  
editorial director

**Brian C. Fenton,**  
managing editor

**Jeff Holtzman**  
technical editor

**Byron G. Wels,**  
associate editor

**Carl Laron,**  
associate editor

**Robert A. Young,**  
assistant editor

**Teri Scaduto**  
editorial assistant

**Ruby M. Yee,**  
production director

**Karen Tucker,**  
production advertising

**Robert A. W. Lowndes,**  
production associate

**Marcella Amoroso**  
production assistant

**Andrew Duzant,**  
technical illustrator

**Jacqueline P. Cheeseboro**  
circulation director

**Arline R. Fishman,**  
advertising director

ComputerDigest  
Gernsback Publications, Inc.  
500-B Bi-County Blvd.  
Farmingdale, NY 11735

**ADVERTISING SALES 516-293-3000**


Larry Steckler  
Publisher

**NATIONAL SALES**

Joe Shere  
1507 Bonnie Doone Terrace  
Corona Del Mar, CA 92625  
714-760-8967

Cover Photography by Jeff Holtzman  
and André Duzant

# EDITOR'S WORK- BENCH

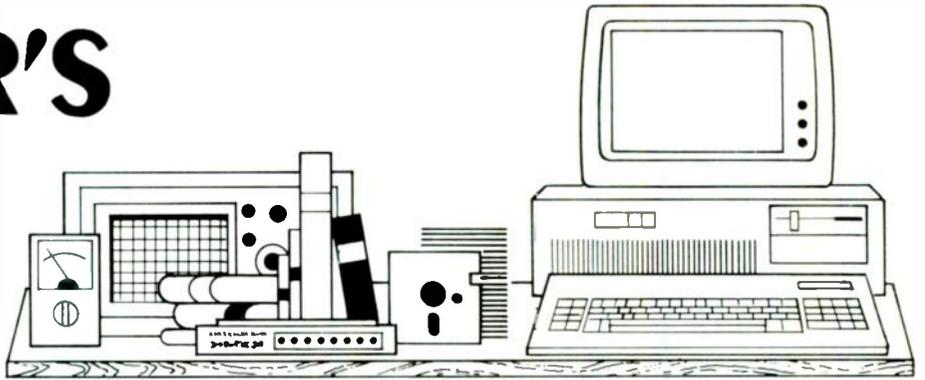

## REPORT FROM ATLANTA

Comdex, held twice a year, is the Computer Dealer's Exposition. As the name suggests, dealers get together with manufacturers, distributors, independent developers, and members of the press to show hardware and software, discuss trends, make deals, eat, drink, and generally be merry. Because of current market conditions (good and getting better), things were merry indeed this year for those involved in the business end of things. For those interested in the technical end of things, there was less cause for celebration.

By number of booths and square feet of floor space, clone manufacturers, distributors, and dealers easily were the most prevalent exhibitors. Most have products that are virtually indistinguishable from one another; very few have products that offer truly advanced features.

### The graphics explosion

There is a great deal of activity in micro-computer graphics these days. There are two reasons for that activity: falling hardware prices (of RAM and custom video chips), and the increasing popularity of graphically oriented software (CAD, drawing and painting programs, and desktop publishing).

Just before Comdex, NEC introduced two new members of the MultiSync line: the MultiSync Plus and the MultiSync XL, with pixel resolutions of 960 x 720 and 1024 x 768, respectively. All MultiSync monitors are compatible with *all* members of the PC family (PC, XT, AT, and PS/2), as well as the Macintosh II. Other monitor manufacturers scrambled to clone the original MultiSync, and will probably do so again with the new models.

Complementing the new high-res monitors, many companies introduced

new high-res adapter cards, most of which provide EGA compatibility, as well as proprietary new modes with resolutions approaching the one-mega-pixel (1024 x 1024) level, often with 16 or more colors. Even though the new boards provide backward compatibility with at least some previous standards (CGA, MDA, Hercules, and EGA), the companies manufacturing those boards must write special drivers for the new non-standard high-resolution modes to be useful, and a special driver must be written for each program that is to use a high-res mode. Inevitably, only the most popular programs (AutoCAD, PageMaker, etc.) will be supported.

The problem is that those video supersets are all incompatible with each other at the software level, even though a multi-scanning monitor can save users from premature hardware obsolescence. Therefore the user may suffer if he buys a video adapter to run a specific application and later on discovers he wants to run other applications that are not supported.

Overall, IBM must take the blame for the situation, because it has been so slow to introduce better adapters, not to mention truly serviceable ones (technical problems prevent an EGA from being used in a multi-tasking environment, for example). In fact, in many ways VGA is really only IBM's attempt to catch up to what other companies have been doing (640 x 480 lines x 16 colors) for some time.

Eventually Microsoft Windows may be what saves PC users from the lack of a true video standard. Programs written to run under Windows are supposed to be ignorant of the underlying hardware, so that, after installation, boards from Tseng Labs, Number Nine Computer, STB, or anyone else will run programs in the best possible resolution, etc. Of course, few programs currently take advantage of the device-independence that Windows can provide. And you need an AT-class machine to run

Windows at an acceptable rate. However, hardware prices are falling, and Windows applications programs are starting to appear, most of which are graphically oriented (drawing and painting programs, desktop publishing, and CAD).

### PS/2

As you might expect, there was much discussion of the impact that the new PS/2 line will have. Right now, it seems that, outside of the corporate market, PS/2 will have little impact. The clone manufacturers clearly aren't worried. In fact, some industry analysts think that IBM may have made a huge marketing blunder, and may even now be offending the corporate market that is its real bread and butter. The reason is that it is currently impossible to buy "classic" machines (XT's and AT's) in quantity. IBM seems to be saying: "Go PS/2 or go elsewhere." It will be interesting to see which way corporate America does go.

We attended a technical seminar on the internal workings of OS/2, and it's clear that the operating system has the kind of facilities that power users have been clamoring for. However, there are two big problems associated with OS/2: it's not available, and it won't let programs written for DOS 2.x and 3.x make use of the new facilities (multi-tasking and megabytes of memory).

Under the 80286 version of OS/2, you'll be able to run only a single DOS application at a time, and it will be a good two years before OS/2-specific programs start to appear. And there's not even a projected release date for a version of OS/2 that takes full advantage of the 80386. However, '386 control programs are available from other vendors (Quarterdeck Systems, The Software Link) right now that will allow you to run multiple DOS sessions. But those control programs are not true operating systems, so you don't get true multi-tasking, wherein several parts of the same program can run simultaneously, pass messages to

each other and to other programs, etc.

It may turn out that OS/2 is the only major program written for the 80286! The editor of a leading computer publication claimed to have seen half a dozen 386-specific applications, and none for the 286. And one analyst stated that anyone writing for the '286 must be as brain-damaged as the chip itself!

Regardless, an intermediate class of programs (called "Family" applications by IBM) will be able to run on both OS/2 and DOS 3.3 (or higher—Microsoft has hinted rather strongly that DOS 3.30 will not be the final release), because the new versions of DOS can provide a pseudo-multi-tasking environment. However, whether any serious software will be written to conform to the "Family" API (Application Program Interface) remains to be seen.

### Optical storage

Several companies (Panasonic and Kodak being among the more prominent) are displaying advanced optical-storage systems. Almost no one was talking about CD-ROM, except one pundit (and president of a company that is a major developer of programming languages) who predicted that CD-ROM will go the route of bubble memory—nowhere. The reason? Actually, there are two: (1) Because read/write optical technology is what's really needed, and (2) the difficulty of mastering (not physically producing) a CD-ROM product

### CASE

You've probably heard of CAE—Computer Aided Engineering. CASE is the corresponding discipline for software types—Computer Aided Software Engineering. It's not a big field yet, but several companies are getting involved in it commercially. The idea behind CASE is to provide an organized way of developing really large software projects that involve many people and an evolving set of design goals. CASE provides a set of graphically-oriented tools for developing design specs, translating them into simulated screens, generating code, obtaining user feedback, incorporating that feedback into the design specs, and so on. By linking all steps by computer, it is hoped that the design cycle can be shortened considerably, thereby allowing evolving user needs to influence design decisions before they are finalized. If you're just starting out and are interested in the design of large systems, check out CASE—it's the wave of the future.

### KEYBOARD DEMO PROGRAM UPDATE

Dave Schubert of The Casino PCBoard BBS (609-652-6030, 300/1200/2400/9600 baud, 8/1/N) was kind enough to send the following corrections and enhan-

cements to the keyboard demo program that appeared in the article "From Keypress to Scan Code" on page 70 of the July issue. Merge the following three lines into the program:

```
235 IF INSTR(NOPRINT$,A$)=0 THEN
    PRINT A$;" "; ELSE PRINT " ";
1210 XBOX = 19:YBOX = 4:XLEN = 7
    :YLEN = 3
3090 DATA F1,F2,F3,F4,F5,F6,F7,F8,F9,
    F10,F11,F12
```

In line 235, note that there is a single space in the quoted string following A\$, and that there are two spaces in the quoted string at the end of the line. The revised line 1210 prevents the right edge of the box from being erased, and the revised line 3090 provides for displaying the F11- and F12-key labels when using an enhanced (101-key) keyboard. Thanks, Dave. ♦♦



### THE BROOKLYN BRIDGE AND DIREC-LINK

Life is simple with one computer. But with two or more, life gets complex, if not chaotic. The problem is this: How do you share files (not to mention printers, disk drives, and other peripherals) among several machines?

More than one fortune has been made in the computer business attempting to answer that question, but, until recently, those answers were too expensive for the hobbyist and small business.

However, things are changing rapidly, especially in the MS DOS world. Now there are many inexpensive ways to connect two (and sometimes more) computers together.

Two solutions to the problem of connectivity (chief buzzword of 1987) are simple hardware/software combinations that allow two PC's (desktop, laptop, or transportable) to communicate via the RS-232 port at speeds about ten times what we normally consider maximum.

There are at least half a dozen "bridge" solutions on the market now; we'll discuss two of the original and more useful of them. One (Direc-Link) emphasizes ease of set up and use; the other (The Brooklyn Bridge) sacrifices easy set-up to provide greater power. We'll examine the latter first.

### The Brooklyn Bridge

White Crane Systems, Inc. (Suite 151, 6889 Peachtree Ind Blvd., Norcross, GA 30092, 404-454-7911) developed and markets The Brooklyn Bridge (\$129.95). You use it by adding a special driver program to the CONFIG.SYS file of the master machine—the one at whose keyboard you'll be typing. For each device (disk drive(s), printer(s), clock, RAM disk, modem—any legitimate DOS device) you wish to access from the remote machine, you add an additional driver (to the master's CONFIG.SYS)

Next you run a program called BRIDGE.COM at the remote machine. Then you reboot the master. At that point you can access the devices for which you have installed drivers. A few examples should make the process clear.

Suppose you want to access the hard disk of a PC from a dual-drive laptop. First add BRIDGE.DEV to the laptop's CONFIG.SYS. BRIDGE.DEV takes care of the first few block (disk) devices—usually two floppies and a hard disk. Then run BRIDGE.COM on the PC. Now you can access the PC's floppy disks and hard disk (as drives C:, D:, and E:) from the laptop with all normal DOS commands (COPY, CD, RD, DEL, etc.).

To access a second hard disk or a RAM disk, you'd add another driver, REMOTE.DEV. To access both the hard disk and the RAM disk, you'd add two REMOTE.DEV files. White Crane also includes a program (DEVICES.COM) that displays the devices installed on your machine and the appropriate line to add to the CONFIG.SYS file.

You can also access serial and parallel ports, and the system clock, by installing a driver for each device. For example, to access the PC's parallel printer from the laptop, you'd add the following line to the laptop's CONFIG.SYS file:

```
device = remote.dev lpt1
```

Depending on your system, the installation procedure can be tricky. For example, at the office I use a single-drive clone with four network drives, a RAM disk, and serial and parallel ports. To access that machine from a laptop, the following lines were added to the laptop's CONFIG.SYS:

```
device = bridge.dev 1
device = remote.dev 2
device = remote.dev 3
device = remote.dev lpt1
```

The first line provides access to the clone's floppy disks; the second, to the network "drives" (C:, D:, E:, F:); the third, to the RAM disk (G:); and the fourth, to the printer attached to the clone. Adding those four drivers consumed only about 3.4K of available memory.

### Direc-Link

Sold by the Micro-Z company (4 Santa Bella Road, Rolling Hills Estates, CA 90274,

# R-E Computer Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775. each. Closing date same as regular rate card. Send order with remittance to Computer Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. Only 100% Computer ads are accepted for this Admart.

**ICs PROMPT DELIVERY!!!**  
 SAME DAY SHIPPING (USUALLY)  
 QUANTITY ONE PRICES SHOWN FOR JUNE 21, 1987

OUTSIDE OKLAHOMA NO SALES TAX

DYNAMIC RAM		
1Mbit	1TC511002P-12	\$27.50
51258	256Kx1 100 ns	6.95
1Mbit	256Kx4 120 ns	32.00
1Mbit	1000Kx1 100 ns	27.50
4464	64Kx4 150 ns	3.50
41256	256Kx1 80 ns	5.35
41256	256Kx1 100 ns	4.40
41256	256Kx1 120 ns	3.45
41256	256Kx1 150 ns	3.20
EPROM		
27512	64Kx8 200 ns	\$9.95
27C256	32Kx8 250 ns	5.40
27256	32Kx8 250 ns	5.50
27128	16Kx8 250 ns	4.65
STATIC RAM		
62256	32Kx8 120 ns	\$12.75
6264LP-15	8Kx8 150 ns	3.25

640K MOTHERBOARD UPGRADE: Zenith 150, IBM PC XT, Compaq Portable & Plus, hp Vectra

OPEN 6 1/2 DAYS, 7:30 AM-10 PM. SHIP VIA FED-EX ON SAT.  
 SUNDAYS & HOLIDAYS. SHIPMENT OR DELIVERY VIA U.S. EXPRESS MAIL.

SAT DELIVERY INCLUDED ON FEDEX ORDERS RECEIVED BY 10:30 AM \$4.10. P. P. \$10.50 2 lbs.

MasterCard, VISA or UPS CASH COD

Factory New, Prime Parts MICROPROCESSORS UNLIMITED, INC.  
 24 000 St. Perinca Ave. (918) 267-4961  
 181 (US) Cir. 74321

No minimum order. Please note that prices are subject to change without notice. Orders received by 9 PM CST can usually be delivered next morning, via Federal Express Standard Air. \$4.00, or guaranteed next day Priority One. \$10.50 (air part, quantity).

CIRCLE 61 ON FREE INFORMATION CARD

**DISK SERVICE MANUAL \$20**  
 Maintain, Repair, Adjust, Align Drives Without Special Equipment or Software. 5.25", 8", Microfloppies. IBM-PC/Compatible, Apple, Commodore, Kaypro, Tandy, Atari, TI, HP, DEC, etc. 12 Chapters, 100+ Photos, Figures. SAVE \$\$\$!

**COMPUTER PHREAKING \$15**  
 Dozens Computer Crime Methods and Countermeasures. How Systems are Penetrated. BIOS Advice; Password Defaults; TEMPEST; Van Eck Methods; Crosstalk Amps. 200 Phreak-Term GLOSSARY.

**CRYPTANALYSIS TECHNIQUES \$15**  
 Five Cryptanalysis Programs (ZDM, BAS, Source Code) for MSDOS Systems. N-Gram, Kasiski, MR, IC Analyses. Disk + Manual. \$25.

**PHONE COLOR BOXES \$15**  
 PHONE RED, BLUE, BLACK, GRAY, SILVER, YELLOW, GREEN, BROWN, PURPLE, WHITE, BEIGE, S&M, CLEAR, CHEESE, and MUTE BOX Plans. Plus CALL-FORWARDING. Much More! Use not recommended.

**HIGH VOLTAGE DEVICES \$15**  
 STRIKER, ZAPPER, BLASTER, JAMMER, FLASHER, STIMULATOR, JACOB'S LADDER, OZONE/PLASMA/VAN DE GRAAFF GENERATORS, GEIGER COUNTER, FENCE CHARGER, etc. Plans, Shocking!

**RADIONICS MANUAL \$20**  
 Comprehensive Manual, Plans on ElectroMagnetic Therapies, Diagnostics, Preventions. 10+ Figures. Includes FDA-approved.

**ELECTROMAGNETIC BRAINBLASTER \$20**  
 Comprehensive Manual and Plans on ElectroMagnetic Weapons and Lab. Devices. Dozens of Figures. Mind Boggling!

**CONSUMERTRONICS**  
 2011 CRESCENT DR. P.O. DRAWER 537  
 ALAMOGORDO, NM 88310

CIRCLE 203 ON FREE INFORMATION CARD

## COMPUTER ASSEMBLY MANUALS



Eliminate Guesswork!  
 Build with Confidence!

**BIG BLUE SEED for IBM™ BUILDERS**  
 Parts list, placement diagrams & instructions for assembling over 75 IBM-compatible bare cards. Latest version includes guides for 640K, Turbo, & AT MthBds. \$17.95

**APPLE SEED II for APPLE™ BUILDERS**  
 Instructions for assembling over 85 Apple-compatible bare cards including II+ & IIe MthBds. For all Apple enthusiasts \$14.95

Both for \$30.00! Also bare cards in stock!  
 Check money-order, VISA MasterCard to

**NuScope Associates\*, Dept RE**  
 P.O. Box 790 • Lewiston, NY • 14092

A Division of Kosmic MicroTech, Inc.

CIRCLE 210 ON FREE INFORMATION CARD

## Heath/Zenith H/Z90 Break the format barrier!

**EMULATE** — Lets your Heath computer read and write these disk formats

Atrix	DEC Rainbow	Magnolia	Royal/Triumph
Altos	Eagle II	Morrow MD	Sanyo 1100
AMPRO	Epson QX-10	NCR DecMate 5	Superbrain
Beehive Trp	Fujitsu CP/M86	NEC PC-8001A	Televideo
CDR Systems	BM CP/M86	Osborne 1	TRS80 CP/M
Cromemco	MS 5000	Olitron	Xerox 820
DEC VT-180	Kaypro II	PMC MicroMate	Zorba

H37 version includes formatting capability

H89 or H8 with H37 ..... \$59  
 For CDR BIOS 2.91 ..... \$49

### CPC CP/M ↔ PCDOS

Transfer files between PCDOS and CP/M disks. Includes access to subdirectories. For H89 or H8 with soft sector controller

CPC — specify controller ..... \$35


Products for Heath/Zenith and other CP/M computers

Call or write for catalog. Add \$4 per order for SH. Terms: Check or Money Order — VISA/MC — COD CA residents add 6% tax

**ANAPRO 805/688-0826**

213 Teri Sue Lane Buellton, CA 93427

CIRCLE 202 ON FREE INFORMATION CARD

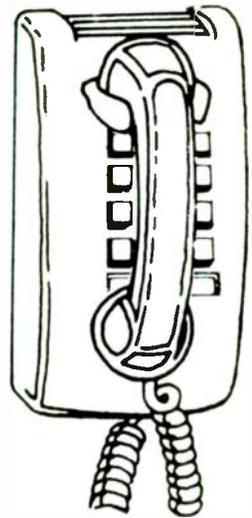

# CALL NOW AND RESERVE YOUR SPACE

- 6 • rate \$800.00 per each insertion.
- Reaches 242,400 readers.
- Fast reader service cycle
- Short lead time for the placement of ads

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Computer Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

213-377-1640) for \$59.50 plus \$5 for shipping. Direc-Link takes the point-and-shoot approach to file transfer. You needn't mess with device drivers, just connect the two machines electrically and run DLINK.COM on both machines. Each machine then displays a diagram of the tree structure of the current disk. You can change disks within the program.

To send a file (or a group of files), use the cursor keys to move the highlight bar to the desired subdirectory. By pressing F9, a list of all files in that subdirectory is displayed. You can mark all files, individual files, or groups of files specified with wildcard characters ( \* and ? ) for transfer. Then press Return to send a file. You have the option of changing the name during transfer. Press

Ctrl-Return to send all marked files with no further intervention.

One nice feature is that you can control both machines from the keyboard of one. Pressing Scri-Lock toggles between local and remote modes. However, in remote mode you must watch the screen of the remote machine; each screen only displays information related to the machine it is connected to.

Another nice feature is that you can set up "script files" to automate transfer of files. You might use a such a file to transfer a salesman's orders on a daily basis.

The first time you run the program, it creates and saves a map of your directory structure. Then, next time you run the program, it loads the map without re-scanning,

which saves time. You can rescan at any time if your directory structure has changed, and the program does remind you to do so each time you start it up.

We had a problem using Direc-Link on our network. It would not display the directory structure of or allow us access to read-only network "drives." However, Micro-Z promptly provided a three-byte patch that allowed us proper access.

### Hands-on

Brooklyn Bridge proved invaluable in setting up our laptop machines for the reviews elsewhere in this issue. Using the XCOPY command of DOS 3.2, we were able to copy entire branch structures (directories with subdirectories) directly to the hard

disks of the Toshiba and Zenith laptops—all with a single command. However, after initial set-up, we found Direc-Link easier to use, especially for transferring just one or two files.

By the way, you can copy an entire sub-directory using Direc-Link, but you must first create it on the target machine. In addition, Direc-Link works only with a single directory at a time—it will not copy branch structures in the point-and-shoot mode, although it can copy multiple directories in script-file mode.

All in all, we'd be hard pressed to say that either program is superior to the other. Brooklyn Bridge allows more flexibility, but it can be difficult to install, and its manual is not well done. Direc-Link is so intuitive that you don't need to read the manual at all. In addition, the cables supplied with Direc-Link had shielded shells and were of better construction than those supplied with The Brooklyn Bridge.

A cable is included with The Brooklyn Bridge for the purchase price; you must buy cables separately to use Direc-Link. Micro-Z sells a set (one with 25-pin females on both ends, and two 9-pin female to 25-pin males) for \$32.50. So even with extra cost, Direc-Link is less expensive than The Brooklyn Bridge. For do-it-yourselfers, the manuals of both products include cable wiring diagrams. Both Micro-Z and White Crane Systems include all software on both 5¼ and 3½ format diskettes. **◆◆**



## HEATHKIT SK-203 PRINTER BUFFER

**S**ome computer accessories are spoilers. After using one, you're spoiled—you can't imagine how you got along without it, and you can't imagine how you'd survive if you had to give it up.

Case in point: the printer buffer. Sure, you can pick up a software spooler from most BBS's, but software spoolers have problems of their own. First, they use up valuable system RAM that might be put to better use loading a spelling checker's dictionary or more data in a CAD or desktop publishing program. Second, an external device can perform tricks that are simply impossible with a software spooler.

The problem with an external buffer—until recently—has only been one of cost.

However, Heathkit's new SK-203 printer buffer (shown in Fig. 1) retails for \$199.95, and, although you can buy a cheaper buffer, you can't buy one with the capabilities of the SK-203 for anything near that price.

### How it works

Like any printer buffer, the SK-203 has a chunk of memory that sits between your computer and your printer. The base model comes with 64K, which can be upgraded to a total of 512K. The remaining features discussed below are included as standard equipment.

The SK-203 has both serial and parallel inputs and outputs, and there are four ways they may be configured: (1) The parallel input can be routed to the parallel output and the serial input can be routed to the serial output; (2) Inputs and output can be

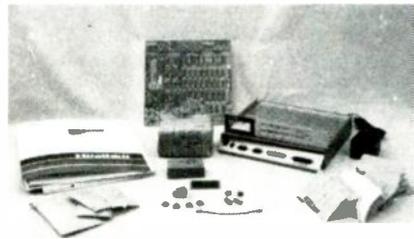


FIG. 1



FIG. 2

crossed—serial-to-parallel and parallel-to-serial; (3) Both inputs can be routed to the parallel output; (4) Both inputs can be routed to the serial output. A front-panel-mounted pushbutton, Swap (shown in Fig. 1), allows limited re-configuration without re-setting DIP switches.

The SK-203 maintains file integrity in all configurations. In other words, when two inputs are fed simultaneously (regardless of output destination), the received files are kept separate. Likewise, when multiple files are received sequentially (regardless of input), they are kept separate.

### Pushbutton control

Front-panel controls include two sets (one each for the serial and parallel inputs) of Clear, Copy, P. Print (see below), Restart, and Offline pushbuttons, and the single Swap pushbutton. (See Fig. 2) Three seven-segment LED's continuously monitor the amount of free memory remaining.

Pressing Clear removes all files (received from the associated input port) from memory. Pressing Copy allows you to increment (to a maximum of 99) and decrement the

number of copies of a file that will be printed. The file that will be copied is the next one received.

The P. Print switch allows you to interrupt a job in progress and send a file to the buffer that will be printed immediately. Restart allows you to begin printing the current file from the beginning, in case of printer malfunction (end of ribbon, out of paper, etc.). Restart also allows you to program the timeout delay that the buffer uses to determine when one file ends and another begins. The default is six seconds. Last, Offline halts output to the associated port. Incoming data continues to be buffered while the buffer is offline.

The rear panel has two 25-pin female sockets for the parallel ports, and two 9-pin (AT-style) male plugs for the serial ports. In addition, the power switch is mounted on the rear panel, and the power jack is also accessible there. A small wall-mounted transformer powers the SK-203.

Inside are three DIP switches and a dozen or so jumper blocks that allow complete control over the serial-communication parameters (150–38,400 baud, word length, stop bits, and parity), data routing, auto form feed, handshake type and polarity, and RAM-IC size (64K or 256K).

### Circuit details

Controlling operation of the buffer is an HD64180 (the Z80 upgrade made by Hitachi) running at 12.288 MHz. It's interesting that the circuit contains no UART—the microprocessor's built-in port handles the serial-to-parallel conversion. All software is contained in an 8K EPROM (2764). There are a total of 34 IC's on the circuit board (if all RAM sockets are filled).

The power cube supplies a nominal nine volts DC; the RS-232 voltages are generated by an Intersil 7662, a CMOS charge pump that uses a couple of 100-µF capacitors to generate the negative RS-232 voltage.

### Building it

The kit went together smoothly. The circuit board is good quality, double sided, and has silk-screened legends marking all component locations. Order of assembly is for the most part logical. Anyone with the slightest experience in electronics assembly would have no trouble building the SK-203; expect to spend eight or ten hours in doing so. Only small hand tools are required; solder is included with the kit.

### The acid test


After tracking down one assembly error (a solder bridge that totally disabled the microprocessor), we put the SK-203 to work, and it has performed flawlessly.

We have two minor complaints with the unit: (1) The lack of detailed troubleshooting information, and (2) The rather disorganized configuration instructions.


In operation, the SK-203 is a fine unit. We recommend it highly. **◆◆**

# PORTABLE COMPUTERS

*We evaluate seven portable PC compatibles.*

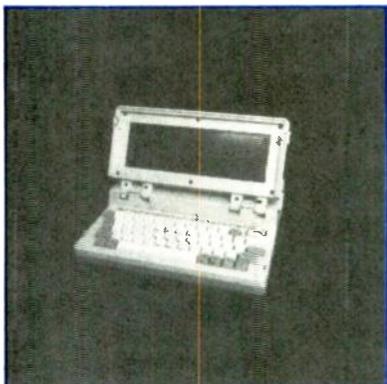

**BONDWELL 8**

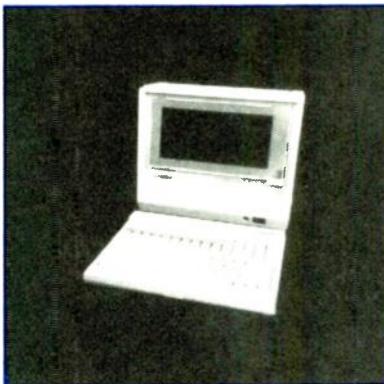


**DATAVIEW 25**



**IBM PC CONVERTIBLE**

**JEFF HOLTZMAN, TECHNICAL EDITOR**

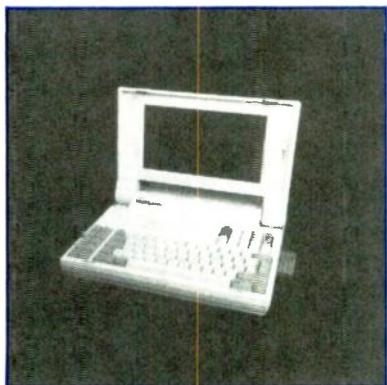

**NEC MULTISPEED**


**F**or several years if you wanted to compute on-the-go, you were limited to using small machines with hard-to-read screens, small amounts of RAM, and software that was (to be charitable) serviceable, but nothing like that obtainable for a desktop machine. However, times have changed. Now you can buy machines from a number of manufacturers that run all standard PC software, in many cases faster than on a standard desktop machine.

For purposes of this review we examined seven machines with list prices ranging from \$1400 to \$4200. (See Table 1.) Screen displays of most battery-powered portables still can't measure up to those of a real CRT, but some (Zenith's and NEC's, for exam-


ple) have improved dramatically. And the screens of several non-battery-powered portables (from Toshiba and Datavue) are every bit as good as a CRT.

To obtain objective measures of performance, we ran special benchmark tests to determine each machine's speed. To obtain some idea of each machine's subjective appeal, we had several persons evaluate each machine. All our findings are presented in tabular form below, along with comments by our reviewers.

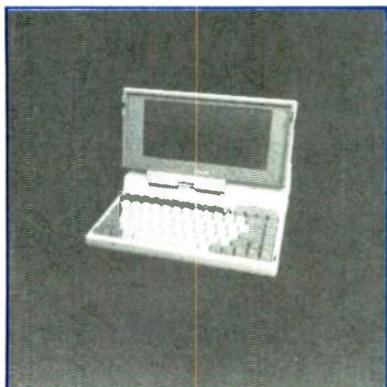Keyboard layouts of all reviewed machines are shown in Figs. 1-7. Of the battery-powered machines, only the NEC has a separate numeric/cursor pad, and only it has full-size function keys arrayed at the left



**TOSHIBA T1100 PLUS**

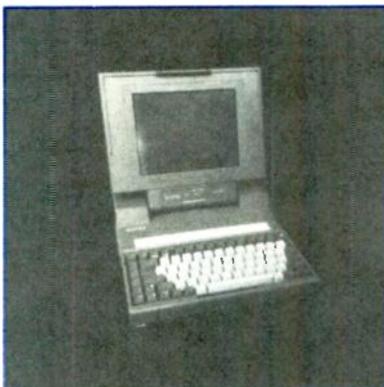

**TOSHIBA T3100**



**ZENITH Z183**



FIG. 1—Bondwell 8



FIG. 2—DatuVue 25



FIG. 3—IBM PC Convertible



FIG. 4—NEC MultiSpeed

side of the machine. (The DataVue's detachable keyboard also has a separate pad containing the numeric/cursor keys.) The other battery-powered machines embed the numeric pad in the main typing area; you must press a special key (usually labeled "FN") simultaneously with the desired key to access the embedded functions. In addition, most of those machines provide a separate cursor-control pad, operation of which will make you appreciate a full-size keyboard.

To get started with our evaluations, first we'll give an overview of each machine's features, and then we'll examine the objective ratings. Next we'll discuss each machine in detail, and wrap up by making recommendations.

### Overview

The Bondwell, DataVue, and IBM machines all use 8088 or 80C88 microprocessors, run at 4.77 MHz, and have no turbo mode. The MultiSpeed and the T1100 Plus use full 16-bit processors and have turbo modes. The Zenith machine uses an 80C88, but provides a turbo mode. Last, the Toshiba T3100 uses an 80286 running at 8 MHz, which gives it the raw processing power of an AT-class machine (and a corresponding price tag).

All reviewed machines except, ironically, IBM's come with a version of DOS; various machines run various versions of DOS, ranging from 2.11 to 3.20. Some machines include software: BASIC, system utilities (SideKick, SuperKey), or applications programs. Table 2 shows the software included with each machine.

Type of screen (and readability) varied tremendously. The T3100 and the DataVue 25 have radiant screens that are visible under just about any lighting condition. However, those machines run only on AC power. The IBM Convertible, the MultiSpeed, and the T1100 Plus have LCD screens without backlighting, which makes them hard to



FIG. 5—Toshiba T1100 Plus

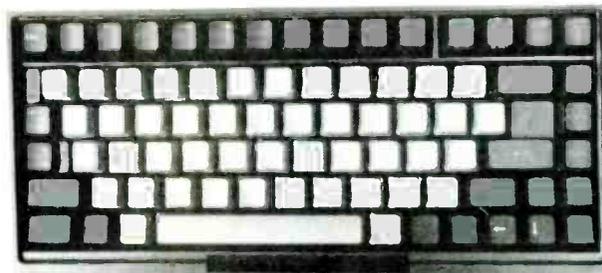


FIG. 6—Toshiba T3100



FIG. 7—Zenith Z183

TABLE 1—BASIC FEATURES

Machine	Price	RAM	Floppy Disk	Hard Disk
Bondwell 8	\$1399	512K	1	---
DatuVue 25	\$3495	768K	1	10 Meg
IBM PC Convertible	\$1695*	640K	2	---
NEC MultiSpeed	\$2195	640K	2	---
Toshiba T1100 Plus	\$2099	640K	2	---
Toshiba T3100	\$4199	640K	1	10 Meg
Zenith Z183	\$3499	640K	1	10 Meg

\* Does not include serial/parallel adapter (\$80)

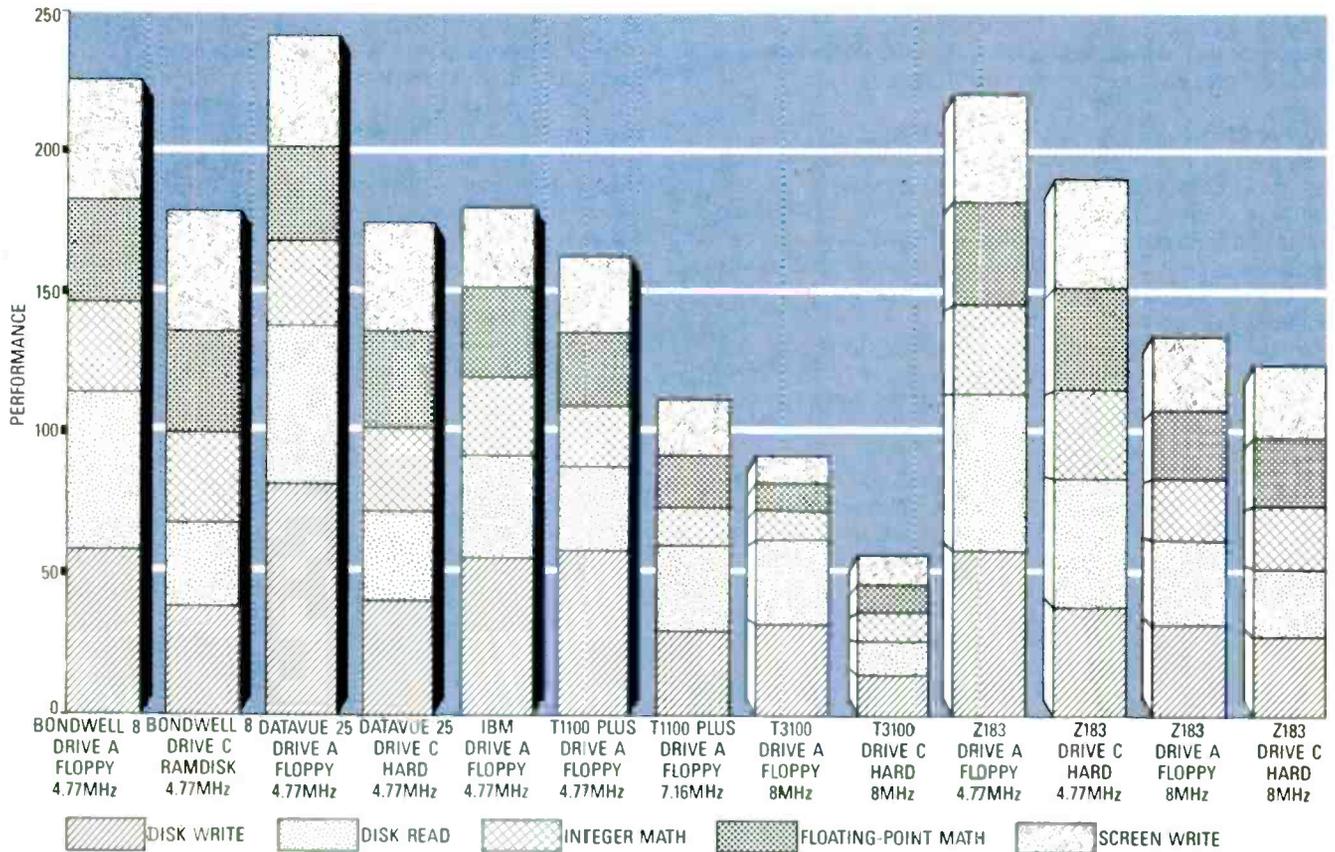


FIG. 8—Benchmark results

read, and makes their cursors hard to locate, under some lighting conditions. Their screens, however, are much more readable than those of a few years ago, so, if you haven't looked at an LCD screen for awhile, you're in for a pleasant surprise. The Bondwell has a backlit LCD screen that is more legible than the non-backlit types, but the best display (of the battery-operated machines) is provided by the Zenith.

#### Portable speed

Shown in Fig. 8 are the results of running five benchmark tests (similar to those used by *Byte* magazine) on each machine. The benchmarks test the speed of reading and writing sequential disk files, processing speed of both integer and floating-point math, and screen-writing speed.

No results are shown for the NEC MultiSpeed because the version of GW-BASIC we had in-house would not run on the MultiSpeed. However, the results of other benchmark programs indicate that the

MultiSpeed is nearly as fast as an AT (and the T3100).

Other than the MultiSpeed, we ran all tests on each machine several times, depending on the number and type of drives, and whether the machine had a turbo mode. In addition, because the Bondwell 8 has only a single floppy-disk drive, we also ran the disk-speed benchmark on a RAM disk. (The RAM-disk program is included with the machine.)

As you can see, the Toshiba T3100 is the fastest machine by far. In fact, it was able to complete *all* tests in approximately the same amount of time it took several other machines to complete just the disk write test. Of course, the T3100 is also the most expensive of the machines we tested.

Now let's discuss each machine. Unless otherwise noted, all machines have as standard features a serial port, a parallel port, and RGB and composite-video outputs, and an external AC adapter.

#### Bondwell 8

At \$1399, the Bondwell is the least expensive of the machines we reviewed. It's also one of the lightest, at 10.5 pounds. It has a single floppy-disk drive, a back-lit LCD screen, and a built-in 300-baud modem. The LCD's backlight can be turned off to conserve power. The machine's serial port is accessed through a non-standard nine-pin female—not male—D connector, so you may need a gender-reverser to access the serial port.

The Bondwell's screen, like that of the Toshiba T1100 Plus, is of the "squashed" variety—it has an aspect ratio of about 3:1, giving graphic images a distorted look. On the plus side, the backlighting provides contrast that is better than the non-backlit models.

Working with one drive can be inconvenient, but inclusion of the RAM-disk program partially offsets that inconvenience. However, any memory used for the RAM disk decreases the size of main memory. But that shouldn't be a problem for intended users—not those running large spreadsheets, databases, etc.

The machine comes with a 300-baud modem as standard equipment, and a special implementation of a public-domain communications program to operate it.

TABLE 2—SOFTWARE

Machine	Dos Version	Software Included
Bondwell 8	2.11	GW-BASIC, FAM-disk, Modem8
Datavue 25	2.11	World Clock, dumb terminal
IBM PC Convertible	3.2*	Application Selector
NEC MultiSpeed	3.2	**
Toshiba T1100 Plus	3.2	Sidekick
Toshiba T3100	3.2	Sidekick, SuperKey
Zenith Z183	3.2	None

\* DOS not included  
 \*\* See text

One quirk is that to format a floppy for 720K capacity, which is standard for 3½ disks, you must add "/3" to the FORMAT command. Otherwise, the disk is formatted for 360K capacity.

### DataVue 25

This machine is one of two AC-only powered models we examined; the Toshiba T3100 is the other. The DataVue is the only machine we tested that comes in the "lunchbox" configuration, wherein the keyboard flips down from a vertically oriented system unit to reveal the screen. The DataVue 25 is available in a wide variety of configurations, some for very good prices, so examine the alternatives carefully.

The DataVue's screen is somewhat squashed, but it uses highly readable electroluminescent backlighting with red letters on an orange background (or vice versa). You can control screen contrast, brightness, and mode directly from the keyboard. The screen tilts through about 45°, latching in six places.

The keyboard is a lightweight battery-operated device (using two AA cells) that communicates with the main unit by infrared light. Our test unit had a maximum range of about 18 inches. To increase range, you can also connect keyboard and system unit with an optional cable.

Although the DataVue comes with a hard disk, you cannot boot from it; you must boot from a floppy and then transfer operations to the hard disk. Because DOS 2.11 is supplied with the machines, files are allocated in 8K chunks, so even a short batch file, for example, is listed in the directory as having a length of 8192 bytes. However, the hard disk has an automatic head-parking mechanism that is activated whenever the machine is turned off.

At 16 pounds, the DataVue 25 is the heaviest of the machines that we reviewed. As one of our reviewers stated, "It's portable—for Mt. T."

The documentation is well-thought-out, well-written, and well-printed. It includes a "Quick-start" section for experienced users, and more-detailed information for those needing instruction in computer and MS-DOS basics.

### IBM PC Convertible

The Convertible is an odd machine that received bad publicity when it was first released. However, IBM dropped the price recently, bringing it more in line with the competition. The machine itself consists only of 640K of RAM and two floppy-disk drives. DOS is not included, nor are serial, parallel, and video ports. However, a program (called The Application Selector) is included; as shown in Fig. 9, the program is a visually oriented shell that allows users to run applications from a graphical interface. In addition, the Application Selector includes several stand-alone programs of its own, including a word processor, a telephone-list manager, a calculator, a scheduler, help screens, and various tools for formatting and copying disks. All those programs run under the Application Selector; you don't need DOS to run them. Further, the user can link his own

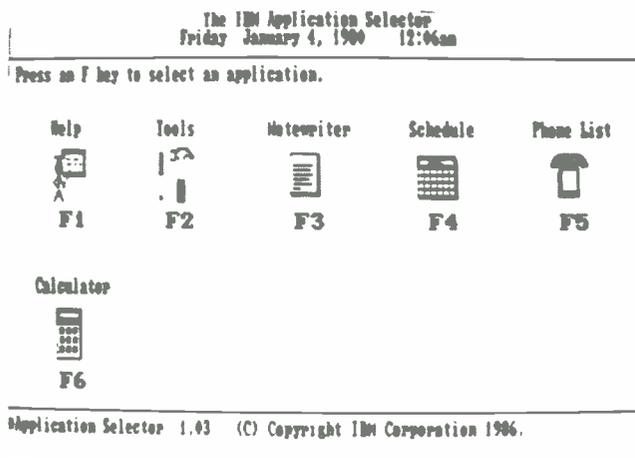


FIG. 9—IBM's application selector

programs to the system and run them from the main menu.

The Convertible's screen is a non-backlit LCD, but it has higher contrast than all other plain LCD's we've seen. The keyboard has the best (stiffest) feel of all the portables we evaluated, but the layout has quirks of its own. (The CapsLock and Control keys are reversed, for example.)

The main unit has no provision for internal add-on hardware, but a number of modules are available that plug into the rear of the unit. (See Fig. 10.) Doing so is simple, but increases size and cost. However, for on-the-road use, the modules can be disconnected easily, thereby increasing portability.

The Convertible has a special "resume" mode that allows you to resume automatically after powering down in the middle of an application program. For example, if you're running a word-pro-



FIG. 10—IBM add-on modules

cessing program and shut the power off, the next time you power up, you'll be at the same place in the same program with all your data intact.

The Convertible's manual is not among the best. It is full of technical jargon ("IPL mode," for example) that tends to negate the ease of use provided by the Application Selector. The applications programs included with the Application Selector are serviceable but limited; they are not acceptable for professional use. However, a beginner can use them for learning purposes, and graduate to more-sophisticated software when ready.

Rumors abound that IBM will introduce a new version of the Convertible with a turbo mode and a backlit screen, but, of course, those are only rumors. If the company does do so (and leaves the price alone), it will have a hot product.

### NEC MultiSpeed

A fast machine with half a megabyte of ROM-based software, the MultiSpeed is highly attractive. It has a supertwist LCD screen that is eminently readable. (Supertwist screens provide higher contrast than regular screens.) Our only complaint is the fact that the friction-locked screen-tilting mechanism is difficult to adjust properly, so we usually propped the screen from the rear to obtain an acceptable reading angle.

The MultiSpeed is very fast, but it wouldn't run our benchmark program, as noted above. We noticed no other incompatibilities. Speed is switchable at the keyboard between 4.77 MHz and 9.54 MHz; the MultiSpeed uses a V30 microprocessor, NEC's version of the 8086. The V30 has a true 16-bit data bus, as opposed to the eight-bit bus of the 8088 microprocessor.

RAM has been implemented in an unusual fashion: 512K of volatile RAM, and 128K of non-volatile (battery-backed) RAM. Part or all of the latter can be configured as a RAM disk whose contents won't go away when power is removed. So, by careful configuration, you could use the MultiSpeed as a "notebook" computer in

the manner of Radio Shack's low-cost non-DOS machines.

The MultiSpeed has 512K of ROM-based software, including a word processor, an outliner, a dialer, a communications program, and a set-up utility. Like that included with the IBM Convertible, the MultiSpeed's software is no match for commercial packages, but it will suffice to get a beginner started. And it can be useful on the road if you want to avoid transporting a number of floppy disks.

### Toshiba T1100 Plus

Another lightweight, compact unit, the T1100 Plus compresses a fast machine in a small package. The supertwist LCD screen is readable under average lighting conditions, but the high aspect ratio (2.2:1) gives graphic images a flattened look. The keyboard's layout (which is identical to the T3100's) is not bad, but we'd prefer a stiffer feel. It's easy to add an internal modem, but the external port connectors are unprotected and are subject to damage in transit. The carrying handle is not centered, so the computer does not hang in a balanced fashion—it bumps into either your leg or external objects. Overall speed (in turbo mode) was the fastest of the machines we tested, except for the T3100 (and the MultiSpeed). Increasing the value of the T1100 Plus is the inclusion of a copy of SideKick. Documentation is excellent, for both beginners and experienced users. A separate MS-DOS manual is included.

### Toshiba T3100

We have no hesitation in stating that the T3100 was our favorite machine (and the most requested by our reviewers). Its gas-plasma display (shown in Fig. 11) is visible under all lighting conditions (even in a totally dark room), but also necessitates AC-only operation. The machine's speed is simply phenomenal, considering its size. The keyboard (which is identical to the T1100's) is adequate, and the hard disk is slow, even compared with the hard disk on a standard XT. But overall, the T3100 provides maximum performance in minimum space. It comes with copies of SideKick and SuperKey, and, as with the T1100 Plus, documentation is excellent.

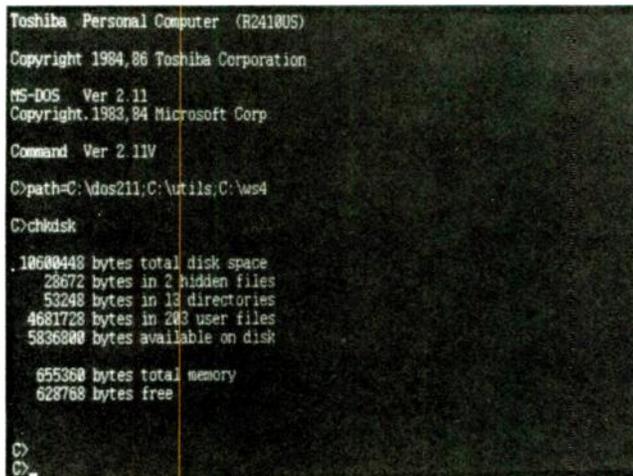


FIG. 11—Toshiba T3100's screen

### Zenith Z183

More reasonably priced than the T3100 is Zenith's machine. It is a battery-powered machine that contains a hard disk, a backlit supertwist LCD screen, and a dual-speed 80C88. The machine is not the heaviest of those we tested, but it will challenge your ability to handle it and carry-on baggage simultaneously. Speed in turbo mode exceeds that of a standard PC, but the Z183 is not as fast as the Toshiba models or the MultiSpeed.

Standard equipment includes a 10-megabyte hard disk, a single 720K floppy disk, and 640K of RAM. In addition, slide controls vary screen brightness and contrast, and LEDs indicate drive activity and low power.

The screen is simply wonderful, for a non-radiant type. It is

legible in just about all lighting conditions, has a true aspect ratio, and is nearly as large as a nine-inch CRT. It is unquestionably the best of the battery-powered machines, and sets a standard that is sure to be emulated. Our only complaint is that at the best contrast/brightness settings for readability, the cursor becomes difficult and sometimes impossible to locate. By reducing contrast, the cursor becomes more visible, but legibility suffers.

The front-mounted carrying handle is properly centered, and a flip-down lid covers the rear-mounted ports. Slots on the left side allow insertion of a modem and a standard keyboard connector. The Z183's keyboard itself has a good feel, and a fairly good layout. The cursor pad is easier to manipulate than that on some portables. A single DIP switch sets the number of drives, turbo or standard speed (8 or 4.77 MHz), etc.

### Upgrades

Since making our evaluations, several manufacturers have introduced new or enhanced models. NEC's MultiSpeed EL is identical to the standard model except for a new backlit screen that provides approximately the same readability as the Z183. The standard model can be upgraded, by the user or by NEC, for about \$500; the upgrade is worthwhile if you use the machine more than occasionally.

Toshiba has introduced several new models, including a six-pound single-drive unit (with DOS 2.11 in ROM, 512K of RAM, and an 80C88), the T1000, that lists for about \$1000. If the street price goes as low as usual, the T1000 will be irresistible. Toshiba also introduced a battery-powered hard-disk model, the T1200.

In early spring, President Reagan imposed trade sanctions on a number of high-tech products from Japan, and portable computers are among the hardest hit. That has led to some price increases, and to forestall further increases, several companies are considering manufacturing their machines in the U.S. NEC, for example, already has several plants employing 6000 workers in this country; gearing up for production of MultiSpeeds should not be difficult.

### Recommendations

There is no single machine that is best for all persons in all circumstances. Depending on your needs and budget, one machine may be more suitable than another. Note that our tables include list prices, which vary from time to time, and which many dealers discount by 30% and even more. Shop around.

For flat-out performance, the T3100 is far and away the best machine. It's also the most expensive, and it requires AC power. If you need a battery-powered portable with a hard disk, then the Z183 is the way to go. Or, if you don't need the hard disk, the Z181 may be suitable; it's a dual-floppy cousin of the Z183.

For the budget shopper, the Bondwell 8 (or possibly the new T1000) is suitable. The IBM Convertible is a solidly built machine, and it includes "starter" software that may suffice students and beginners for some time. It also has a full range of accessories available, and the "resume" mode is a great convenience.


For best overall balance of power and price, you must choose between the T1100 Plus and the MultiSpeed. And due to the MultiSpeed's higher clock speed, the 128K of non-volatile RAM, and the ROM-based software, it represents the best overall value.

### Credits

Our thanks to the manufacturers who generously supplied machines for review: Bondwell (47358 Fremont Blvd., Fremont, CA 94538, 415-490-4300), DataVue (One Meca Way, Norcross, GA 30093-2919, 404-564-5668), IBM (100 Summit Avenue, Montvale, NJ 07645, 800-IBM-2468), NEC Home Electronics (1255 Michael Drive, Wood Dale, IL 60191, 312-860-9500), Toshiba America (Information Systems Division, 9740 Irvine Blvd., Irvine, CA 92718, 714-380-3000), and Zenith Data Systems (1000 Milwaukee Avenue, Glenview, IL 60025).

Further thanks to our reviewers (Julian Martin, Byron Wels, Brian Fenton, Shelli Weinman, Robert Young) for their comments and evaluations. ♦♦♦

# HIGH-RES HIGH-SPEED

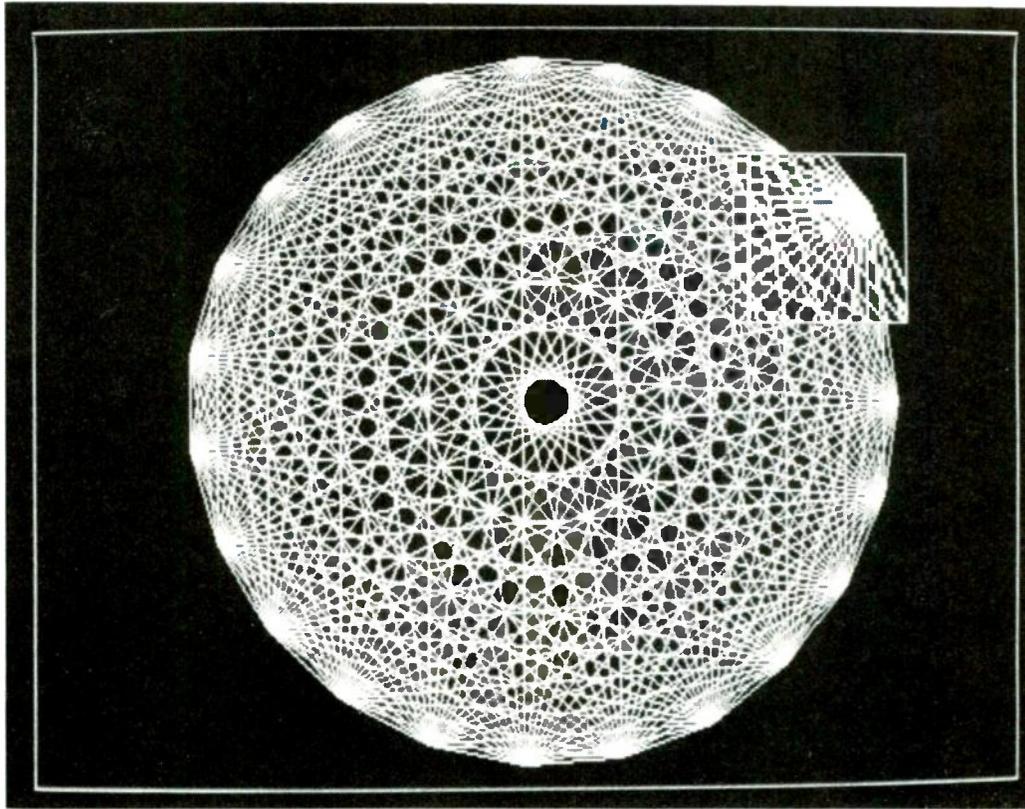

## GRAPHICS CO-PROCESSORS

*Great new graphics processors jazz up computer displays like never before.*

JOSEF BERNARD

Video games used to be the only activities you needed graphics for, but that's no longer the case. Graphics are essential to CAD (Computer Assisted Design) programs, WYSIWYG (What You See Is What You Get) word processors, desktop publishing programs, and even operating-system environments including Microsoft Windows, Digital Research's GEM, and IBM's presentation manager.

The problem is that, on most desktop computers, graphics-dependent programs are slow. And as those programs become more capable and more complex, they extract a greater toll in computational overhead from the computer's microprocessor. Therefore, the microprocessor winds up spending too much time manipulating images and too little time carrying out your commands. That slowdown leads only to frustration.

For example, in high-resolution mode, the output of IBM's relatively crude CGA (Color Graphics Adapter) is composed of an array of  $640 \times 200$  (128,000) pixels, and the position of each must be recalculated every time the display is updated fully. Doing so takes time, and, what is more important from a human-factors point of view, it also frustrates the person using the system, who can do nothing but twiddle his thumbs during the update.

More and more graphics-intensive software is becoming available these days, and, fortunately, special IC's that are specifically designed to increase graphics processing speed are also becoming available. You know that a math co-processor can drastically increase the speed with which the computer does complex math, thereby freeing the microprocessor for other tasks. In a similar

manner, a graphics processor can manipulate graphic images, and doing so has two advantages: the graphics processor can do its work much faster than a general-purpose microprocessor, and it can do it while the microprocessor is working on other things.

### The new generation

Display processors (NEC's 7920, for example) have been around for several years, but the new IC's offer greater capabilities. For example, Intel's 82786 is a true co-processor that, after having been instructed to perform a task, can go off on its own and do it, thereby freeing the microprocessor for other work. And Texas Instruments' TMS34010 is really a complete microprocessor with special graphics-control capabilities.

The Intel device—and most others that have been announced—is a co-processor that works in conjunction with a system's microprocessor. It has a built-in repertory of drawing operations, as shown in Table 1, and it can execute them with little or no attention from the microprocessor after the initial instruction has been given.

The TI device is more than a smart controller. And even though the operations it performs are less sophisticated than those of other graphics IC's, it is much more flexible, so you can accomplish just about anything in software. In fact, TI has developed a library of routines that allow you to program the IC in C. By way of contrast, other graphics controllers are more or less restricted to a fixed set of commands, and in some circumstances much programming may be required to achieve the desired results.

What is it that makes those graphics devices so special? A few quotations from Intel's spec sheet for the 82786 will give you an idea (and keep in mind that the TMS34010 is just as amazing):

- Four megabytes of graphics memory
- 200-MHz CRT's
- 640 × 480 (color) or 1400 × 1400 (monochrome) resolution
- 256 simultaneous colors
- Bit-blitting (block graphics-data transfer).

A block diagram of the TMS34010 is shown in Fig. 1. The IC contains almost all that is required for a complete graphics processing and display system. Note the barrel register, a special type of shift register. In the TMS34010, it can contain a field of 32 bits, and the IC can rotate it completely in a single instruction cycle, which potentially can speed up graphics manipulations enormously. Although the TMS34010 is a 32-bit device, it can be interfaced readily to an eight- or sixteen-bit bus.

### Bit-blitting and hardware windows

The new IC's are intended for use in memory-mapped graphics displays. In that type of display, each pixel on the screen corresponds to a location in the computer's memory. Conversely, the contents of each memory location determines what will appear at a given point on the display.

Several screens of images, libraries of images, of portions of a single image can be stored in RAM simultaneously. By using bit-blitting techniques, those blocks of data can then be moved or operated on as a whole almost instantaneously, making it possible to change or update a display with pre-computed graphics information—there's no need to sit around and wait while the computer recalculates all the lines and shapes that must be redrawn each time the image changes.

TABLE 1—82786 COMMANDS

Command	Opcode
LINK	02
NOP	03
DEF_TEXTURE_OPAQUE	06
DEF_TEXTURE_TRANSPARENT	07
DEF_CHAR_SET_WORD	0A
DEF_CHAR_SET_BYTE	0B
INTR_GEN	0E
ENTER_MACRO	0F
EXIT_MACRO	17
DEF_BIT_MAP	1A
DUMP_REG	29
LOAD_REG	34
DEF_COLOR	3D
DEF_LOGICAL_OP	41
ENTER_PICK	44
EXIT_PICK	45
DEF_CLIP_RECT	46
DEF_CHAR_SPACE	4D
DEF_CHAR_ORIENT	4E
ABS_MOVE	4F
REL_MOVE	52
POINT	53
LINE	54
RECT	58
BIT_BLT	64
ARC_EXCLUSION	68
ARC_INCLUSION	69
POLYGON	73
POLYLINE	74
CIRCLE	8E
CHAR_OPAQUE	A6
CHAR_TRANSPARENT	A7
BIT_BLT_M	AE
INCR_POINT	B4
HORIZ_LINES	BA

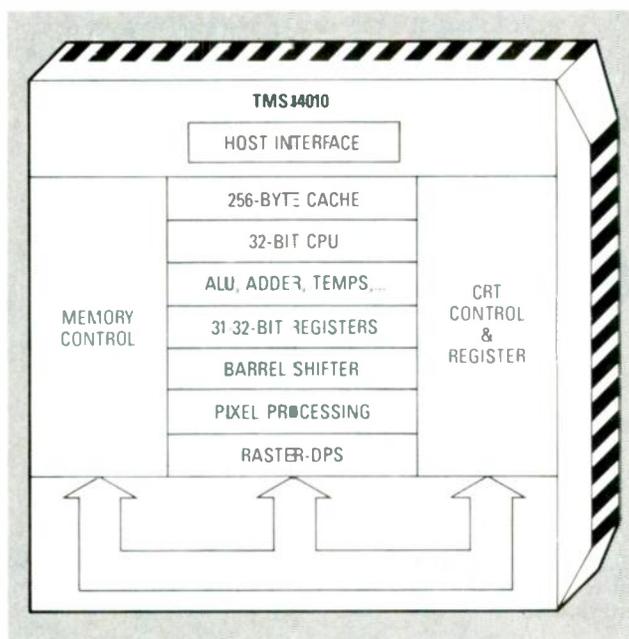


FIG. 1—TEXAS INSTRUMENTS TMS34010 is a 32-bit graphics processor, complete with its own on-board microprocessor.

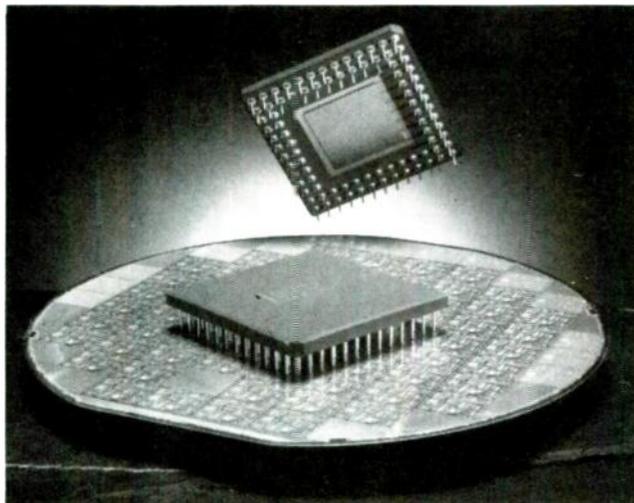


FIG. 2—INTEL'S 82786. The complexity of graphics-processor IC's requires a large number of input and output pins.


Bit-blitting is not a new technique. Commodore and Amiga machines have been using it for some time to achieve high-quality animation and graphics. However, the new graphics controllers will make bit-blitting—and even more advanced techniques—available on MS-DOS systems.

Hardware windowing is one advanced technique that is available on the 82786. Rather than moving big chunks of graphics data around in memory to assemble a complete screen image, hardware windowing allows you to move pointers that tell the 82786 where the data is located. The graphics processor then picks up the data wherever it happens to be located. Speed is thereby increased tremendously.

### Hardware overview

For all that they have to offer, the new graphics controllers are remarkably simple. They require relatively little support from other hardware, because they contain built-in registers for DMA transfers, internal controllers for video DRAM, programmable video timing, and other capabilities.

The T1 processor comes in a 68-pin square PLCC (Plastic Leaded Chip Carrier) package, the Intel device in a slightly larger 88-pin package (See Fig. 2). Both are manufactured using a high-density CMOS process. Power consumption is low; the TMS34010 uses 500 mW and the 82786, 1000 mW.

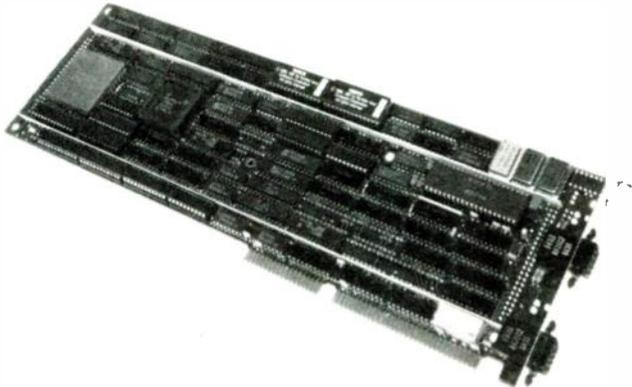

**FIG. 3—NUMBER NINE COMPUTER'S SGT Pepper Graphics System uses both a TMS34010 and an 82786 in order to achieve high performance.**



**FIG. 4—NEW MONITOR TECHNOLOGIES allow you to see an entire page of text at a time, and make working with CAD and desktop-publishing programs easy. Shown here is the Genius, made by Micro Display Systems.**

### Putting them to work

There's more to using the new graphics controllers than just plugging them into a socket and turning on the computer. They require auxiliary hardware to drive a display, and, of course, software, which is usually provided in ROM.

For example, Number Nine Computer (725 Concord Avenue, Cambridge, MA 02138, 617-492-0999) in its SGT Pepper Graphic System, shown in Fig. 3, provides a firmware (software in ROM) interface called NNIOS (Number Nine Intelligent Operating System). The Pepper board actually contains both an 82786 and a TMS34010; NNIOS routes appropriate graphics commands to either, depending on which is more suitable for a given task.

The firmware interface is important because it provides a software standard, of which there are several at the present time. A standard is useful because it gives software developers an easy way to develop applications for various graphics controllers and boards without worrying about the underlying hardware.

The on-board drivers make adapting software to display hardware relatively simple. There is no need for the programmer even to know what kind of board will be used; the firmware will take care of everything else, including determining the resolution at which images will be displayed. Higher-resolution boards will provide more detail than lower-resolution ones automatically.

### Black and white and read all over

It's easy to drive a monochrome display with the new graphics controllers. The primary consideration is bandwidth, and it is not difficult to produce a monochrome display capable of "swallowing" the output of a high-resolution graphics board. Many such monitors exist today; some can even display the contents of an entire page of text (with appropriate software, of course).

For example, the Genius monitor shown in Fig. 4 has a resolution of 736 × 1008, which enables it to show a full 66 lines of 80-column text. It can also do wonders with CAD and desktop publishing programs. The Genius is manufactured by Micro Display Systems, Inc., 1310 Vermillion Street, P.O. Box 455, Hastings, MN 55033, 800-328-9524.

Color displays, particularly the CRT's used, are another story. Ignoring bandwidth issues, the resolution of a color CRT is determined by the number of phosphor dots it contains, and by the size and spacing of those dots. (See Fig. 5). The more dots there are, the more detail will be possible. For example, NEC's MultiSync monitor increased the resolution possible with reasonably priced color monitors to 800 × 560. Previous monitors in the same price range were restricted to a resolution of 640 × 350.

The dot pitch of a CRT, which is usually specified in hundredths of a millimeter, refers to the spacing between phosphor elements. The finer the pitch—the smaller the number—the smaller the dots and the closer together they are. The more dots you can pack together in a given surface area, the greater the resolution you can obtain.

The CRT's used in garden-variety monitors usually have a dot pitch of 0.33 mm, which is adequate for resolving the output of an ordinary CGA card. More expensive monitors have CRT's with a pitch of 0.31 or 0.28 mm. Finer dot pitches are preferred by users of systems containing high-resolution EGA (Enhanced Graphics Adapter) and PGC (Professional Graphics Controller, until recently, IBM's highest-quality PC-based graphics sub-system) cards. But even CRT's with a 0.28-mm pitch may not be capable of doing full justice to the output of the new graphics cards embodying graphics processors.


Monitors that meet the qualifications required for really high-resolution graphics display are not cheap, and probably never will be. However, demand is increasing and manufacturing techniques are improving, so prices should decrease. But, currently, the price of a high-resolution display can easily rival that of the system that drives it.

### Graphics applications

The new graphics controllers offer capabilities that greatly exceed those of the display controllers in common use today. In fact, some people believe that the new IC's do too much, and that their capabilities are unnecessary in the PC marketplace.

However, even though the EGA and the PGC offer much better resolution than the original IBM CGA, there are several reasons why the new graphics controllers are finding a great deal of support now, and why they will continue to do so in the future.

First is speed. If you've ever used a graphics-oriented program environment like Windows on a garden-variety PC (or clone), you know how maddeningly slow the program runs. Windows, in theory, is a terrific idea. The current version does not have the ability to run several programs simultaneously, but it does make it easy to switch among several applications at will. However, each time you switch, Windows has to recompute and redraw the entire screen. Where high-resolution graphics such as CAD images or specialized word-processing fonts—or even the Windows screen itself—are involved, redrawing the screen can take several seconds. The first time you watch it, it's fascinating. But it becomes interminably

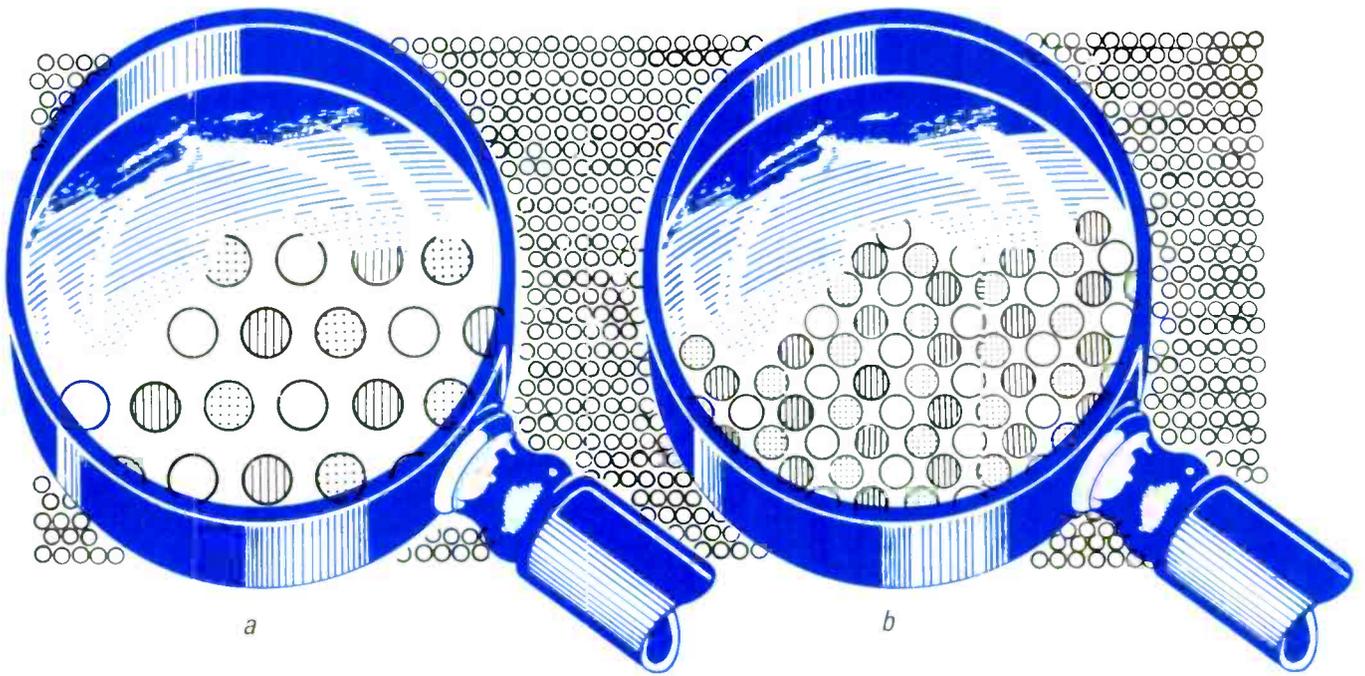


**FIG. 5—RESOLUTION** is determined by the number of dots, their size, and their spacing. Inexpensive monitors have relatively large dots spaced far apart (a). High-res monitors decrease dot size and spacing (b).

boring if you have to sit through it again and again.


With their bit-blitting ability, the new IC's can, depending on the amount of RAM available in a system, store several complete image screens in memory, and recall them as needed in their entirety, without having to recalculate and redraw them each time. That makes switching from one program to another (especially with a fast disk drive or a RAM disk) almost instantaneous, and that in turn makes working in a windowing environment bearable. Animation also becomes practical on a high-resolution scale, providing that the necessary RAM is available.

### Display resolution

The resolution offered by EGA and even PGC boards is inadequate for some applications. Desktop publishing programs, for example, still struggle on most PC systems to show what the finished page will look like. Figures 6 and 7 show how two popular

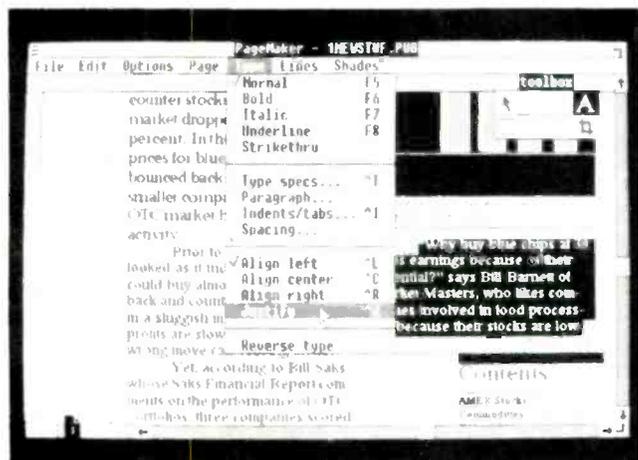

**FIG. 6—ALDUS' PAGEMAKER**, the original desktop-publishing program, was designed first for Apple's Macintosh, and recently has been adapted for the IBM PC family.

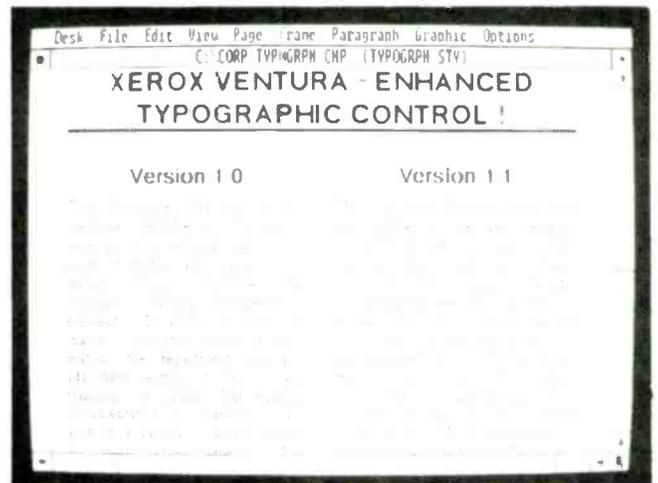

**FIG. 7—XEROX' VENTURA** is another high-stakes player in the desktop-publishing market. The latest version allows you to vary the spacing between letters, thereby improving readability.

programs (Aldus' PageMaker and Xerox's Ventura, respectively) do it. As you can see, those programs try their best to show you how your layout, which may include several typefaces in several sizes, will appear; but what you see on the screen is *not* exactly what you are going to get.

That's a problem because many computer users have no patience with—or understanding of—the limitations imposed by hardware or software. They don't understand why the machine can't show them exactly what they feel they have the right to expect. If what they see isn't close to perfect, then it isn't good enough. For computers to become a more natural and accepted part of the workplace, they will have to come much closer to perfection.

The point is that, due to advances in computer hardware in general, and graphics processing systems in particular, physical page layouts will become as important as—and as easy to manipulate as—the contents of that document. Now that it can easily be previewed and manipulated without a great deal of drudgery, physical appearance will matter as much as correct spelling. ♦♦♦

## R-E ROBOT

continued from page 63

ATOD takes the channel number from the top of the stack, duplicates it, and stores it (using PC!) at I/O port 150H. That sets up the analog input-channel multiplexer. The duplicate copy is used to execute the same sequence of instructions a second time. Although the first port store to 150H started the A/D converter, we

would like to have a few microseconds for the MUX to settle. Starting the converter a second time ensures that the A/D converter has a clean input, one that is not full of switching transients.

SWITCH? fetches the byte of data at port 120H, masks the most significant bit (D7), and tests whether the result is equal to zero. The flag is returned on the stack.

LMTR-PERIOD writes a control byte to the configuration register of the 8253 at 100H. The 8253 is configured for square-wave output and a 16-bit frequency di-

## VIDEO GENERATOR

continued from page 45

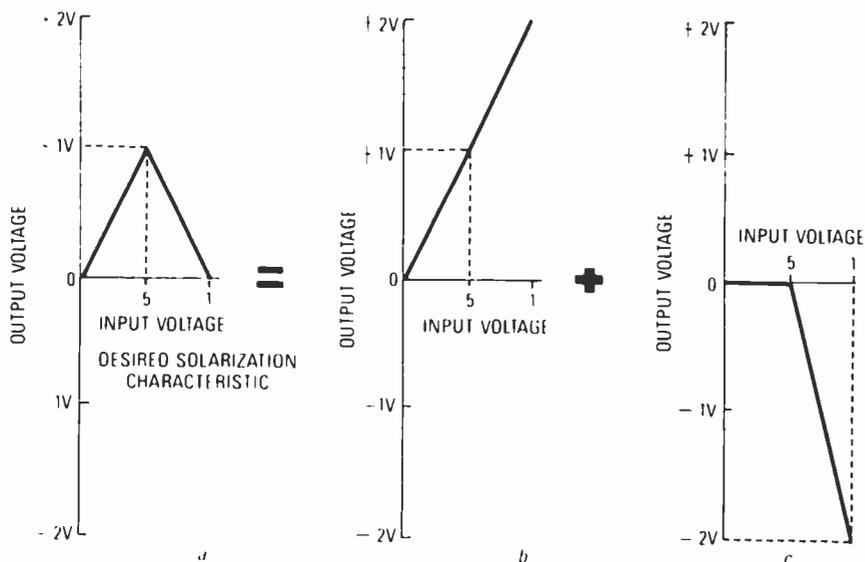


FIG. 8—THE DESIRED AMPLIFIER characteristic needed for solarization, shown in a, can be attained by using two amplifiers having the characteristics shown in b and c. The video palette, however, accomplishes the same task using single controlled-gain amplifier.

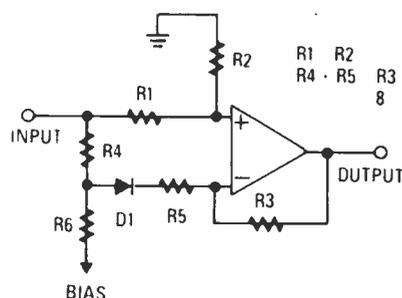


FIG. 9—BY VARYING THE FEEDBACK characteristics of an op-amp, a single stage of amplification can be made to function as a solarizer.

ally becomes forward-biased: The bias from R6 determines the level at which that occurs. When D1 conducts, resistors R3, R5, and R4 form a new feedback network that causes the amplifier gain to increase and also change polarity, which causes the output to reverse direction as the input gets larger.

Strictly speaking, R3 should equal four times R4 and R5. We got visually more

pleasing results when R3 equaled eight times R4 and R5; but that is a matter of personal taste, and is left to the reader's preference. The point at which gain rever-

visor. The next two bytes written to the 8253 will be the 16-bit divisor. LMTR-PERIOD takes an argument from the stack and divides it by 100H, leaving the quotient and remainder (/MOD). That effectively splits the word into the two 8-bit components. Each of these is stored in the 8253 timer 0 at 100H with the two-port store commands (PC!).

STOP-LEFT and STOP-RIGHT disable the motors. ENABLE-LEFT and ENABLE-RIGHT enable the motors. LFWD (left-motor forward), LREV (left-motor reverse), RFWD (right-motor forward), and RREV (right-motor reverse) each set the direction-control relays to the correct state.

That completes the program. Note that screen 32 contains no code at all, simply some explanations and definitions. It can be omitted if desired.

### ROMing your code

After entering, testing, and debugging the source code, it's time to burn an EPROM. The 2764 will hold 8 screens of Forth-83 source code, more than enough. Transfer one screen at a time with the word PROGRAM as follows:

```
32 0 PROGRAM
33 1 PROGRAM
34 3 PROGRAM
35 4 PROGRAM
36 5 PROGRAM
37 6 PROGRAM
```

If you execute ROMed applications, you probably will not have your terminal attached. Until now we have invoked our applications by typing JOY at the terminal. You must include the command JOY as the last word of the last screen. Power down, remove the programmed EPROM, and install it at IC30 on the RPC board, the autostart socket for Forth-83. Press the reset switch and a few seconds later JOY will assume control of the robot.

### Utility of JOY

Actually JOY is quite a bit of fun. You can sit on the robot and drive it anywhere you want to go. The values shown allow about 1 mph forward speed and slow turns. You can rotate the robot with one wheel stopped or each wheel going in opposite directions. The application is a natural for a wheelchair that needs more intelligence than a simple analog joystick could provide.

However, if you ride the robot, be extremely careful! Some values in the routines SPEED-CONV and DIFF-CONV will result in fast acceleration. If you are not careful, it's easy to get pitched off.

After riding, examine your chassis in the vicinity of the motor mounts. If the chassis is becoming bowed out, the torque imposed by the load is too great. Reinforce the rear with a bracket between the two sides before riding again. R-E

# SATELLITE TV



BOB COOPER, JR.,  
SATELLITE-TV EDITOR

## The international connection

THE FAR-REACHING COVERAGE OF GEO-stationary satellites has been well known, significantly documented, and somewhat troublesome to the regulators of the world since the dawn of satellite communications. After more than a decade of active involvement in the business of presenting and delivering programming via satellite, the programming industry worldwide is finally beginning to come to grips with the effects of such wide coverage.

In its most simplistic terms, a satellite transmission has two types of coverage; *intended* recipients and *non-intended* recipients. Under most national (and international) regulations, a satellite signal is considered a national or sub-national service. It is intended to be received by one or more receiving locations, each of which is known to the satellite programmer/operator in advance of the transmission being sent. Those are the intended recipients. Each country in the world has its own laws or rules regulating reception of those transmissions, or there are no laws at all. (We'll get to that situation in a moment.) The content of those laws varies widely and only the United States, Great Britain, and a handful of other countries actually recognize by law that at least some of the transmissions on satellite are open to use by non-intended recipients.

### International law

In cases where laws making it "legal" to intercept transmissions not intended for you do not exist, the attitude of most nations is that it is *not* legal to do so. In other



FIG. 1

words, reception is illegal unless it has been made specifically legal by legislation/law.

However, remember that satellite signals are virtually all national in nature; U.S. satellite signals are intended for U.S. users, Canadian satellites are for Canadian users, Mexican satellites are for Mexican users, and so on. In Europe, only the French presently have a national satellite service and most of the European countries share one or more common satellites (Eutelsat). There, while the satellite may be owned, operated, and shared by multiple countries, the individual channels or transponders are leased by and operated by individual countries. Therefore, under various national laws in Europe, it may be legal to receive and use one channel on Eutelsat (that one that originates in or is intended for use within the recipient's country) but not other channels on the same satellite if those channels carry programming originating in or intended for other countries in Europe.

All of that is very confusing to the layman who buys or builds a satellite-receiving system and discovers not only his own country's signals and programs but those

from neighboring (or not so neighboring) countries. The science of satellite transmissions has not matured yet to the point where it is possible to build a satellite that covers only the United States.

Nor is it possible, or economical, to build a satellite for Europe where one channel covers the UK, another France, a third Denmark and so on. The signals spill outside of the intended coverage area routinely; people with the appropriate equipment can receive those foreign signals, often with great ease. Figure 1 shows the test pattern for a Caribbean superstation that transmits on Westar 5, transponder 23. Though that station's signals are intended for reception in the Caribbean, the photo shown was taken in the U.S.

With rapidly developing domestic markets for their programs, that unintended spillover was largely ignored by programmers for nearly a decade. As an example, if a U.S. satellite programmer purchases rental or "showing rights" for a movie, it pays a negotiated fee based upon the size of its domestic market. No payment is made for viewers located outside of the U.S., and in fact the programmer has no distribution rights outside of the U.S. That means that it can not collect user fees from Bermuda even though there are unintended users there. What's more, legally the programmer must prevent the movie from being seen by those who are located outside the U.S.

### Preventing reception

One method of protecting themselves from unintended

viewing, either inside or outside the region where they have distribution rights, is to encrypt the signal and only accept fees from people residing within the defined viewing area. A British service called The Sky Channel, for example, encrypts their signal and closely controls the distribution of the decoders so that they are available only to viewers located within their domestic market.

Another method of controlling use to within intended regions is

to seek the legal support of the governments outside of the intended viewing areas. For example, through the U.S. State Department, HBO has been successful in getting hotels and other public establishments in Jamaica to cease using HBO's programming in that country. To accomplish that, HBO enlisted the aid of an official agency within the U.S. to intercede with an official agency within the Jamaican government. Encrypting signals is not a

### Caribbean Electronics Magazine

A brand new monthly publication called *Caribbean Electronics Magazine* intended just for people living in and around the Caribbean region is now available from Bob Cooper. If you live in the Caribbean, Florida, or Latin America (only!) and wish to receive a free sample copy, write to CEM, P.O. Box 100858, Ft. Lauderdale, FL 33310, or telephone 305-733-9955. Enclose either business card or amateur/CB QSL card as proof of your residence or business location.



## IF YOU LIVE IN THE CARIBBEAN, CENTRAL AMERICA, NORTHERN S. AMERICA or FLORIDA . . .

### WIN A PARACLIPSE HOME DISH SYSTEM!

Bob Cooper's **CARIBBEAN ELECTRONICS MAGAZINE** is giving away 12 complete Paraclypse 12' home dish systems between September 1, 1987 and August 31, 1988. **FREE.** No obligation of any kind! If you are an amateur radio operator in the 'qualifying area' (see map), simply send us your Ham radio QSL card. If you are in electronics but not a licensed amateur, send your business card. You may enter once per month for each of the 12 months but no more than once per month. The home dish system winners are announced in 'CEM' monthly starting with the November 1987 issue.

**PLUS** - when we receive your QSL card or business card, we will send you a **FREE** sample copy of the most exciting electronics magazine in the Caribbean; Caribbean Electronics. CEM covers every aspect of communications and broadcasting, just for those who live in the Caribbean and countries surrounding the Caribbean. And we do it in English and Spanish with special Spanish summaries for all feature articles.

**OUR** twelve **FREE** home dish systems feature the highly acclaimed Paraclypse 12 foot dish with tuned feed, state-of-the-art solid state actuator/controller, and the top-rated by test AVCOM 2 series receiver system with remote control. This is the best, quality system for home or commercial use in the Caribbean. Find out how our CEM Lab rates everything from power line filters to VCRs, shortwave radios to home computers for Caribbean use in Caribbean Electronics Magazine. Send us your QSL card or business card today!

**CARIBBEAN ELECTRONICS MAGAZINE**  
P.O. Box 100858, Ft. Lauderdale, FL 33310 USA  
Telephone: 305/733-9955; in Florida 800-367-8150

foolproof technique to shut off program use in non-intended areas, of course, since a decoder can be moved from an authorized location to a non-authorized location and still function. And in Europe, where the encryption technology used by satellite programmers is not as secure as it might be, (i.e. bootleg) decoders are freely offered for sale in many countries. A Swiss court recently ruled that within Switzerland it is not illegal to offer for sale or use a decoder that decrypts a French pay-television service.

Similar rulings have come from Canadian courts and they seem to be saying "It is not illegal to offer for sale (non-authorized) decoders within our country if the programming services received with the decoder are not offered in commerce here."

That sort of national attitude bothers programmers who face a form of double jeopardy when their programming is used by non-intended receivers. First, the programmers are under pressures to control the distribution of their services. Should the programmer fail to exercise due diligence (such as by encryption), he is often contractually bound to financial penalties payable to his program sources. But program sources are getting smarter and when they feel that encryption is not adequate due diligence, they are pressuring programmers such as HBO to take things a step further, as was the case in Jamaica.

Not all countries will assist the programmers with their business problems. We'll see why, and then delve deeper into the topic of international satellite reception next time.

R-E

## SERVICE CLINIC

continued from page 30

simplest ways of hunting for an open bypass is to bridge each one with a known-good capacitor and watch the screen to see what effect, if any, the "good" capacitor has on the interference. If the trouble clears up, the bypass you are bridging is open and should be replaced.

If it happens that you can't find a defective bypass by simply bridging it with a known-good capacitor, then it's time to test the suspect capacitor under actual operating conditions. As you would expect, an oscilloscope is a top choice when it comes to making in-circuit tests. (In fact, it's tough to do the job at all without an oscilloscope.)

To use a scope to check a bypass capacitor for proper operation, you set the vertical-input selector to AC and simply touch the test probe to the capacitor's "hot" (non-grounded) terminal. If the bypass capacitor is doing the job it's supposed to be doing you will see no signal on the scope because any AC signal of necessity will have been bypassed to ground. On the other hand, however, if the capacitor is open or leaky, the screen will show some kind of AC signal component because some or all of the signal isn't being bypassed to ground.

One reason the scope's vertical input must be set for AC input rather than for DC is because an open bypass capacitor often has no effect on the B+ value. If you simply measure the B+ voltage it will usually look good because the DC trace displacement can conceal a small AC component. But if the scope cannot display DC at all, unbypassed AC—even a very small amount—will be seen, though it might be necessary to crank up the vertical gain in order to get a readable display.

On the other hand, a leaky bypass capacitor often affects the B+ value, because when a capacitor is "leaky" there is actually a relatively low DC resistance between the positive and negative leads. In a powered (active) circuit, the leak-

age resistance usually becomes part of an unintended voltage divider, thereby reducing the circuit voltage to some degree. Therefore, DC voltage measurements taken on the bypassed circuit will usually point directly at the defective component.

There are even some conditions in which an open bypass capacitor will affect the DC circuit voltage. For example, although an open bypass in a plate or collector decoupling network won't affect the DC circuit values, an open B+ input filter capacitor, such as C2 in Fig. 1, will result in a lower B+. That is because the input filter capacitor charges to, or almost to, the peak value of the rectified AC. If the input filter capacitor is open the rectified AC is processed by the second filter capacitor, which often follows a resistor (for instance, it follows resistor R2 in Fig. 1); hence, under load the voltage across the second capacitor does not reach the peak value, so the overall B+ value is somewhat less than normal.

### Video distortion

Unlike radio oscillation, which usually is heard as squeals and howls, video oscillations caused by defective bypass capacitors often manifest themselves as small distortions in parts of the raster, as traveling wiggles, or as the *Leaning Tower of Pisa* effect, wherein parts of the picture lean to either side. When you see anything in a TV picture that looks odd or out-of-place, start bridging the bypass capacitors while you keep an eye on the picture. You'll know that you've hit the right one because when it is bridged the picture snaps to attention and turns rock-steady.

Often, normal picture detail obscures distortions caused by defective bypass capacitors. You can usually get a better idea of what's going on if you use an oscilloscope to observe a square-wave test signal, because anomalies in the squarewave are immediately apparent—nothing stays concealed when you use your oscilloscope properly. Simply start bridging the bypass capacitors one at a time until the wavetorm snaps to its square shape. R-E

# ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR  
**B.S.E.E.  
DEGREE**



THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

**COOK'S INSTITUTE  
OF ELECTRONICS ENGINEERING**




347 RAYMOND ROAD  
P.O. BOX 20345  
JACKSON, MISSISSIPPI 39209

CIRCLE 209 ON FREE INFORMATION CARD
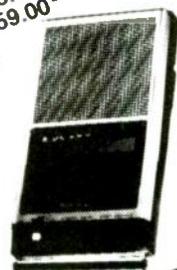
## SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00\*  
14 Hour Model — \$159.00\*

Modified Panasonic Simitone,  
high quality, AC-DC  
Recorders provide 5 or 7  
continuous hours of quality  
recording & playback on  
each side of cassette for a  
total of 10 or 14 hours  
depending on model. Built-in  
features include: • Voice  
level control • Digital  
counter, etc. TDK DC 180  
Cassette Furnished.



### PHONE RECORDING ADAPTER

Records calls automatically. All Solid  
state connects to your telephone  
jack, and tape recorder. Starts  
recording when phone is lifted.  
Stops when you hang up.

\$24.50\*

FCC APPROVED

**VOX VOICE ACTIVATED CONTROL SWITCH**  
Solid state. Self contained. Adjust-  
able sensitivity. Voices or other  
sounds automatically activate and  
control recorder. Uses either re-  
corder or remote mike. \$24.95\*



\*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea.  
Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA,  
MIC, COD's OK. Money Back Guarantee Qty. disc.  
avail. Dealer Inquiries invited. Free data.  
AMC SALES, Dept. A, 9335 Lubec  
St., Box 928, Downey, CA  
(213) 902-4119  
869-8519


CIRCLE 108 ON FREE INFORMATION CARD

# Radio-Electronics mini-ADS



WITH "TV LINE GRABBER" LOOK AT INDIVIDUAL LINES of composite video with your oscilloscope in either Field 1 or 2. Output signals of Line Trigger, Vertical Sync and Field 1 Field 2. Input signal is composite video (RS170 Compatible). Complete unit including wall plug-in power supply. **\$94.95 + \$5.00 S.&H.** C.O.D. orders accepted. **MONITRONICS, INC., 800 W. Rock Creek Rd., Norman OK 73069. (405) 364-0245.**

CIRCLE 214 ON FREE INFORMATION CARD

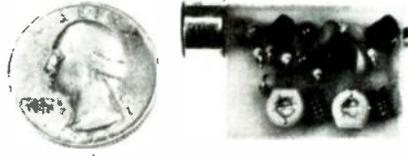

**SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER** on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHZ. Use with any FM radio. Complete kit **\$29.95 + \$1.50 S + H.** Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD



**APPLIANCE REPAIR HANDBOOKS—13** volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. **\$2.65 to \$5.90 each.** Free brochure. **APPLIANCE SERVICE, P.O. Box 789, Lombard, IL 60148. 1-(312) 932-9550.**

CIRCLE 84 ON FREE INFORMATION CARD



**CHAPMAN MFG. CO. KIT #6320** is the most popular tool set in the Chapman line. This kit contains twelve allen hex type adapters, two slotted, two phillips, one 1/4" square drive adapter plus a midjet ratchet, screwdriver handle and extension. Packaged in a pocket sized (4" x 6") vinyl covered steel case. Only **\$22.94 plus \$2.00 for shipping.** Other kits available. Write for free brochures. **THE CHAPMAN MFG. CO., P O Box 250, Dept. RE9, Durham, CT 06422. (203) 349-9228.**

CIRCLE 195 ON FREE INFORMATION CARD



**SYLVANIA 4040 CONVERTER/DECODER \$169.** Gated sync, reconditioned with new wireless remote; 10-day money-back guarantee 30-day warranty. **ZENITH SSAVI \$169, Level II \$199,** reconditioned. SSAVI project handbook **\$6.50** ppd. Surplus N-12s, MLD-1200s: converters, amplifiers, accessories. Radar speed guns for baseball, racing, skiing, etc., from **\$275** used. Catalog **\$1.** Quantity discounts. **AIS SATELLITE, INC., P.O. Box 1226-S, Dublin, PA 18917. 215-249-9411.**

CIRCLE 81 ON FREE INFORMATION CARD

## CALL NOW AND RESERVE YOUR SPACE


- 6 x rate \$745.00 per each insertion.
- Reaches 242,400 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.



**THE LEVITATOR SUSPENDS A METALLIC BALL** in mid-air. The Levitator will amaze everybody as it defies the most basic law of nature. **\$79.95** **NUKE ALERT,** pocket-sized radiation detector monitors Beta, Gamma, and X-ray radiation. Seen on Good Morning America. CES. USA Today. **\$79.95.** All products ready to use Guaranteed. Call or write free catalog (402) 554-0383. Order 1-800-624-1150. **UNITED IMPORTS & MFG., 6846 Pacific St. #2, Omaha, NE 68106.**

CIRCLE 213 ON FREE INFORMATION CARD

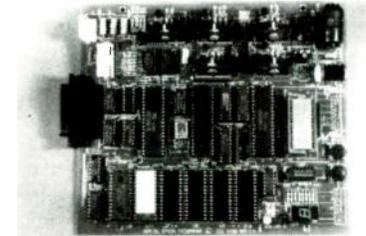

**BUILD STEVE CIARCIA'S INTELLIGENT SERIAL EPROM PROGRAMMER.** • Use Standalone or with Computer/Terminal; • Programs Standard or Fast Algorithm Mode; • Menu Selectable, No Configuration Jumpers; • Programs All 5V 27XXX EPROMs from 2716 to 27512. Includes CMOS and 12.5V Vpp; • Read, Copy, Verify after Write; • Intel Hex File Upload/Download. Full Programmer Kit **\$199.00,** Power Supply add **\$19.00.** S&H **\$5** in USA. CCI, 4 Park St., Suite 12, Vernon, CT 06066. (203) 875-2751.

CIRCLE 200 ON FREE INFORMATION CARD



**PANASONIC CABLE CONVERTERS,** Wholesale and Retail. Scientific Atlanta and Pioneer Cable Converters in stock. Panasonic model 130N 68 channel converter **\$79.95,** Panasonic Amplified Video Control Switch Model VCS-1 **\$59.95.** Scientific Atlanta Brand new Model #8528 550MHZ 80 Channels Converter **\$89.95.** Video Corrector (MACRO, COPYGUARD, DIGITAL) ENHANCER **\$89.95.** Write or call **BLUE STAR IND., 4712 AVE. N, Dept 105, Brooklyn, NY 11234. Phone 1-718-258-9495.**

CIRCLE 85 ON FREE INFORMATION CARD

# Radio-Electronics mini-ADS




**THE ULTIMATE COMPUTER.** IBM-compatible 8 MHz TURBO-XT system. Fully expandable, up to 6 extra cards, 3 extra drives, 6 ROMs and 640K memory. Include monitor, graphics printer display card, 362K floppy drive, game serial ports, 256K 120nS memory, AT-style keyboard, free \$150 program/supply package, including DOS & basic. Monochrome system \$895; color system \$1095. Many options available. **AIS SATELLITE, INC.,** P.O. Box 1226-C, Dublin, PA 18917. 215-249-9411.

CIRCLE 211 ON FREE INFORMATION CARD




**A CAREER START FOR THE 21ST CENTURY.** Since 1905, National Technical Schools has helped people build successful careers. Enter the 21st Century through home study courses in Robotics, Computer Technology and Servicing, Microprocessors, Video Technology, Basic Electronics, Transportation Technology, Climate Control Technology or TV and Radio Servicing. For a FREE catalog, call 1-800-B-BETTER. Or write **NTS/INDEPENDENT TRAINING GROUP,** 456 West M. L. King Jr. Blvd. L.A., CA 90037.

CIRCLE 182 ON FREE INFORMATION CARD

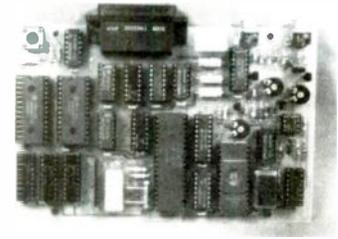

**BUILD STEVE CIARCIA'S NEW VIDEO DIGITIZER.** • True "Frame Grabber", pic takes 1/60th sec • Not bus Dependent - Standalone digitizer • Serial output, transmits 300bps to 57.6Kbps • Resolution: 256 x 244 x 6 w 64 level grayscale • Accepts any NTSC video input. B&W or Color • Optional Rec Display makes Video Telephone • Images can be stored & displayed on IBM PC. Full Digitizer Serial Transmitter Kit - \$249. Call for other options and specs. **CCI,** 4 Park St., Suite 12, Vernon, CT 06066. (203) 875-2751.

CIRCLE 201 ON FREE INFORMATION CARD

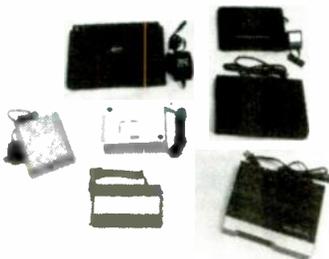


**NEW 442 SYNE WAVE DECODER WITH VARI SYNC**—Replaces the oak N-12 \$80.00, S.B. add on decoder \$99.00, S.B. Tri-Bi decoder \$100.00, Zenith SSAVI \$185.00, S.B.-S.A. decoder \$140.00, Starcom converter \$139.95. Buy a decoder take off \$(10.00). Guaranteed. (402) 331-4957. Call or write for your free catalog. Many other products & quantity pricing. **M.D. ELECTRONICS,** 5078 So. 108th #115A, Omaha, NE 68137.

CIRCLE 212 ON FREE INFORMATION CARD



**LOOKSOUND FM SUNGLASSES.** Super durable sunglasses with that great look. Each one has a state of the art micro FM radio built right in. Great for jogging, bicycling, boating, sports events, etc. \$39.95 plus \$3.00 shipping and handling. Visa, mastercard, and cod. 1-800-522-2636 for orders. (617) 843-1900 for information. **CAMEO ENTERPRISES INC.,** P.O. Box 63 Accord, MA 02018.

CIRCLE 89 ON FREE INFORMATION CARD

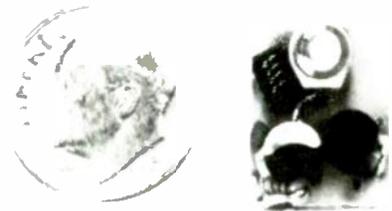

**THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME,** yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to 1/4 mile range. Adjustable from 70-130 MHZ. Complete kit \$29.95 + \$1.50 S + H. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES,** Box 607, Bedford Hills, NY 10507. (914) 232-3878.

CIRCLE 127 ON FREE INFORMATION CARD



**DECODE THE NEW VIDEO TAPE COPY PROTECTION SCHEME.** Bothered by brightness changes, vertical jittering and video noise while watching rented tapes? Stop it with the **LINE ZAPPER.** New kit removes copy protection that often interferes with normal television operation. Complete KIT only \$69.95. Assembled with 1 year warranty \$124.95. Add \$3.00 shipping per unit. Dealer inquiries welcome. **ELEPHANT ELECTRONICS,** Box 41865-L, Phoenix, AZ 85080. (602) 581-1973. Allow 6 weeks for delivery.

CIRCLE 120 ON FREE INFORMATION CARD



**FREE CATALOG OF HARD-TO-FIND TOOLS** is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your free copy today! **JENSEN TOOLS INC.,** 7815 46th St., Phoenix, AZ 85044. (602) 968-6231.

CIRCLE 115 ON FREE INFORMATION CARD




**TRI-MODE DESCRAMBLER PARTS** Original parts as called up in Radio Electronics Feb 1987 article on tri-mode descrambling. Includes pc board, ac adaptor, resistors, capacitors, diodes, pots, transistors, IC's, LED's, toko coil and Plessoy SAW filler. Article included. \$59 plus \$2.50 shipping. **ELECTRONIC PARTS,** Box 276, Alburg, VT 05440 (514) 739-9328.

CIRCLE 194 ON FREE INFORMATION CARD
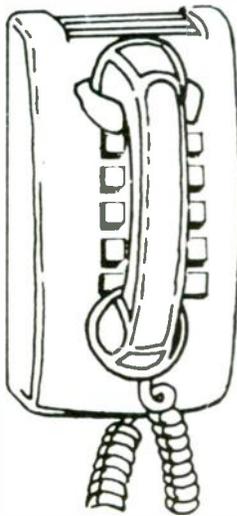
# R-E Engineering Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775 each. Closing date same as regular rate card. Send order with remittance to Engineering Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. Only 100% Engineering ads are accepted for this Admart.



## CALL NOW AND RESERVE YOUR SPACE

- 6 - rate \$800.00 per each insertion.
- Reaches 242,400 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Engineering Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

## Circuit Board Layout Made Easy!

Create and Revise P-C-B Artwork on your IBM or Compatible

- User Friendly
- Supports Microsoft Mouse
- On-line Help Screen
- 2X artwork on printer

Requirements: IBM or compatible PC - 256K memory - CGA card - IBM graphics compatible printer

ONLY \$99.00



2145 Highland Ave. Ste. 201  
Birmingham, Al. 35205  
(205) 933-1122

DEMO DISK \$10.00

CIRCLE 205 ON FREE INFORMATION CARD

## Lil' BITTY TESTER™

LIL' BITTY TESTER - A NEW FAST PORTABLE CONVENIENT AND AFFORDABLE TESTER - A GO NO GO TESTER THAT FITS IN A SHIRT POCKET DESIGNED FOR THE PROFESSIONAL ELECTRONIC TECHNICIAN OR FIELD OF SHOP WORK AND ALSO EASY ENOUGH FOR THE HOBBYIST TO USE

TESTS OUT OF CIRCUIT  
Transistors  
Field Effect Transistors (FET)  
Silicon Controlled Rectifiers (SCR)

Diode  
Light Emitting Diodes (LED)  
Resistor Light Emitting Diodes  
Bridge Rectifiers  
Incandescent Lamps

### TEST CAPABILITIES

Continuity  
Diode Test  
Leakage  
Detect a DC Voltage  
Detect the Polarity of a DC Voltage  
Diode Components  
Diode Test




\$39.95

MAILED AND

FEATURES	SPECIFICATIONS
• 80 - 100% test no adjustment required	• 9V DC transistor battery (not supplied)
• One size fits all 8 pin LED's and diodes	• Test current 100 mA
• 100% test accuracy	• Test current 180 mA
• Tested results with a green or red light depend on test	• 3.3 3.2 L 27.16 W
• No test points are attached to the test leads - terminals are soldered	• 2.8 H
• 90% test accuracy	• 2.8 H in a battery
• DC test current	• 4.0 H in a battery
	• 24 inches long

LIL' BITTY TESTER Inc.  
11 87th Street • Chaska, MN 55011 • 612-425-1422

CIRCLE 185 ON FREE INFORMATION CARD

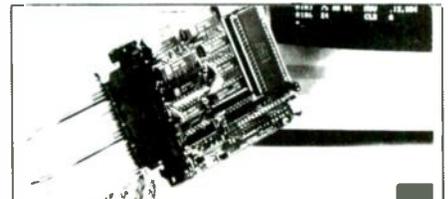

## IBM 8031

IBM® PC based emulators for the 8031 family (8031, 8032, 8344, 80535)

- IBM PC plug-in boards
- Commands like ICE \*S1
- 16 Mhz real time emulation
- 64K emulated memory
- 48 bit wide 16K deep trace buffer with loop counter
- Powerful Macro commands
- Supports PLM 51 and C 51
- In-line assembly "kassambur"
- No external boxes
- Executed time counter
- Trace can be viewed during simulation

PRICE: Emulator \$1795, Trace \$1495

CALL OR WRITE FOR FREE DEMO DISK!


**NOHAU**  
CORPORATION  
11425 E. 11th St.  
Littleton, CO 80130  
(303) 886-1820

EUROPE  
**NOHAU**  
ELEKTRONIK AB  
Lindagatan 5, 713 11 Malmö  
Sweden. NAT. 4609, 425

CIRCLE 183 ON FREE INFORMATION CARD
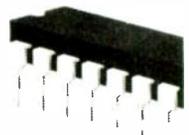
## LINEAR IC EQUIVALENTS & PIN CONNECTIONS

Linear IC Equivalents and Pin Connections



BP141—Shows equivalents & pin connections of a popular user-oriented selection of European, American and Japanese linear IC's 320 pages, 8 x 10 inches. \$12.50 Plus \$2.75 shipping. ELECTRONIC TECHNOLOGY TODAY INC., PO Box 240, Massapequa Park, New York 11762-0240.

## LETTERS

continued from page 16

### SOLDERING TECHNOLOGY

When I received by May 1987 issue of *Radio-Electronics* the other day, I was very pleased to see the article entitled "Soldering: Old Techniques and New Technology." Much to my dismay, however, I found the article to contain errors. The thought behind the article was a good one, but some of the information was very confusing.

The charts shown on pages 47

and 49 can be misleading, which may have lead the author to believe that solder for electrical connections and electronics circuits is composed of 40% tin and 60% lead. A 60/40 tin-lead solder has an alloy designation of Sn60, and, as we learned in high school chemistry, Sn is the chemical symbol for tin. Hence, Sn60 is 60 percent tin.

Also, it should be noted that all good 60/40 solder is cored with rosin flux, and additional flux should not be added to the connection unless you are certain that the added flux is compatible with the flux in the core of the solder.

An exception would be rework of a connection where the original flux has already been "boiled" away.

The author also makes a general statement that no solder can melt at a lower temperature, when, in fact, what he should have said was that no tin/lead solder can melt at a lower temperature.

As always, I am very interested in seeing articles on state-of-the-art technology. Unfortunately, that one left much to be desired.

D.A. HOPKINS  
Senior Instructor, PC-Board Repair Techniques  
Fort Gordon, GA

## CELLULAR TELEPHONE

*continued from page 55*


knowledge of A and B services to that indicator, causing it to flash if the service it encounters is different from the one you have selected. That notifies you that, if you have to switch services manually (perhaps you have locked into one or the other—the recommended method), that is the time to do so.

### What else?

In addition to performing those invisible tasks, the sophistication of cellular phones and phone systems makes using them more convenient.

Of course, they provide such things as auto-redial, muting, and memories that can hold up to 32 phone numbers that can be dialed by just a keypress or two. But just about every phone these days has those features. Cellular phones provide even more!

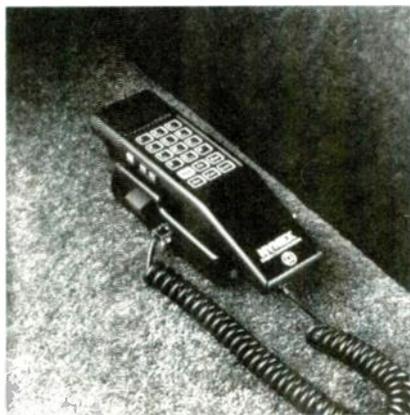A few cellular phones give you the luxury of speech recognition for hands-free dialing. It's really more than a luxury—the less your attention is diverted from your driving, the longer you're likely to be around to make more phone calls. One phone, available from AT&T, not only



THE MODEL CDL205 is from Nynex Mobile Communications.

understands what you say to it but also talks back to you. When you pick up the handset it says, "Name please," and waits for you to tell it whom to call (it can also associate names with phone numbers). If the person you are calling is one of those stored in the phone's memory, the phone will dial the number after you speak the name. If you dial the phone manually, it will announce the digits entered as you punch them in. If the line is busy, you can later tell the phone to redial the number.

Cellular phones also use their intel-

ligence to keep you informed of situations they encounter. We've already seen what the ROSS indicator can tell you. Another indicator, labeled NO SERVICE, lights if the phone encounters no response on its control channels, meaning that there is no cellular service in the area you're in at the moment. That indicator also can be used to let you know when a call is terminated, or when a signal dropout occurs.

Because they already contain a clock circuit for the control of a microprocessor, cellular phones can also provide time-keeping services. The simplest just tell you the length of the last call you made. Others tell you how long you've been engaged in the call you're currently making (that can be quite useful, since cellular phone calls are billed on a per-minute basis). Some phones can tell you how long you've been talking, the total length of time you've used the phone (the timer can be reset to zero whenever you like), and the total number of calls you've made.

Finally, if you leave them on while you're away from them, most cellular phones are able to notify you when you return if you had a call in your absence. They can't tell you who called (although at least one firm has plans to introduce an answering machine for your car), but if you were expecting a call, at least you'll know that it probably came. **R-E**

**You Can Be  
One Of The  
20,000 Technicians  
Certified BY ISCET**




The International Society Of Certified Electronics Technicians offers permanent certification by administering the CET exam with the FCC recognized communications option for \$20. A second exam on FCC regulations for a \$10 fee is required for a Radiotelephone License. Upon passing, technicians receive both a permanent Radiotelephone Operator Certificate and a CET Certificate issued by ISCET.

**ISCET Offers License Renewal**

ISCET has developed a program for registration of those who currently hold a valid Radiotelephone Operator License. By sending a completed application, a photocopy of your FCC License, and \$10 your license will be renewed with the assurance of a recognized national technicians association behind it.

For More Information Contact:  
ISCET 2708 W. Berry, Ft. Worth, TX 76109. (817) 921 - 9101
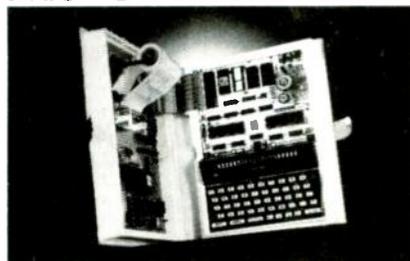
### Learn micro-processing with the new MICRO-PROFESSOR 1P



Students, engineers or technicians—upgrade your micro-processing skills with the new Micro-Professor 1P.

#### The MPF-1P features:

- extensive software support
- more built-in memory
- improved keyboard
- larger display

Three tutorial guides help cover all capabilities. The ideal training tool! MPF-1P will deliver you into the growing world of micro-processing. Invest now!

**Plus—FREE GIFT** Only \$199.95

Check this box for FREE Z-80 Microprocessor Programming and Interfacing textbook when you order within 7 days. \$16.95 value. (Include \$7.50 postage & handling)

**ETRONIX**  
Dept RE0987  
5326 9th Ave. N.E.  
Seattle, WA 98105-3617

For immediate action call TOLL FREE:

**1-800-426-1044**

Full money back guarantee.



CIRCLE 111 ON FREE INFORMATION CARD

## LEARN TV/VCR REPAIR

No Previous Experience Necessary



Now you can train at home in spare time for a money-making career as a TV VCR Repair Specialist. No need to quit your job or school. We show you how to troubleshoot and repair videocassette recorders and TV sets, how to handle house calls and shop repairs for almost any make of television or VCR. You learn about TV receivers, tuners and antennas, x-ray emission, the characteristics of sound, how electrical impulses are converted into a TV picture, and much, much more. Tools are included with your course so you can get "hands-on" practice as you follow the lessons step by step. Send for free facts about opportunities in TV VCR Repair and find out how you can start making money in this great career. Experts show you what to do, how to do it—guide you every step of the way! Everything is explained in easy-to-understand language with plenty of drawings, photos and diagrams.

CALL TOLL-FREE

**1-800-228-5300** Dept. DE087

CALL ANYTIME—Operators to take your call 24 hours a day 7 days a week. No cost. No obligation. No salesman will visit you.

OR MAIL COUPON TODAY

**ICS SCHOOL OF TV VCR REPAIR, Dept. DE087**  
Scranton Pennsylvania 18515

Please send me free facts on how I can learn TV VCR Repair at home in my spare time. No salesman will visit.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. # \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

A Subsidiary of National Education Corporation

CIRCLE 196 ON FREE INFORMATION CARD

# STATE OF SOLID STATE



ROBERT F. SCOTT,  
SEMICONDUCTOR EDITOR

## Micropower op-amp

PRECISION MONOLITHICS, INC. CLAIMS that their new OP-90 micropower op-amp sets new performance standards for similar devices. Although the OP-90's performance is comparable to that of the OP-07, it draws less than 20  $\mu\text{A}$ —which is 1/200,000 the current needed for the OP-07. The OP-90's gain exceeds 700,000 (700V/mV), and common mode rejection is better than 100 dB.

In addition to its unusually low current drain, the op-amp can operate from a single-ended (single) power supply of +1.6 to +36 volts, or from a bipolar (dual) supply of  $\pm 0.8$  to  $\pm 18$  volts. As a single-source device, both input and output are referenced to ground and "zero-in/zero-out" (no static DC output) operation is possible. Input offset is less than 150  $\mu\text{V}$ , so external nulling is not required in most applications.

The OP-90's low offset voltage and high gain enables it to provide precision performance in low-frequency micropower applications. Its exceptionally low voltage and current requirements make the device ideal for battery and solar-power operation in such applications as portable instruments, remote sensors, and satellites.

The OP-90 has the same pinout as the 741, has nulling to  $V^-$ , and can be used to upgrade low-frequency equipment that presently uses the OP-20, ICL8021, HA5141, LF441, or the OPA21. It is available as the OP-90GP in an 8-pin plastic DIP with a commercial temperature range. (At  $T_A = 25^\circ\text{C}$ , maximum offset voltage is 450  $\mu\text{V}$ .) It is also available as the OP-90AZ

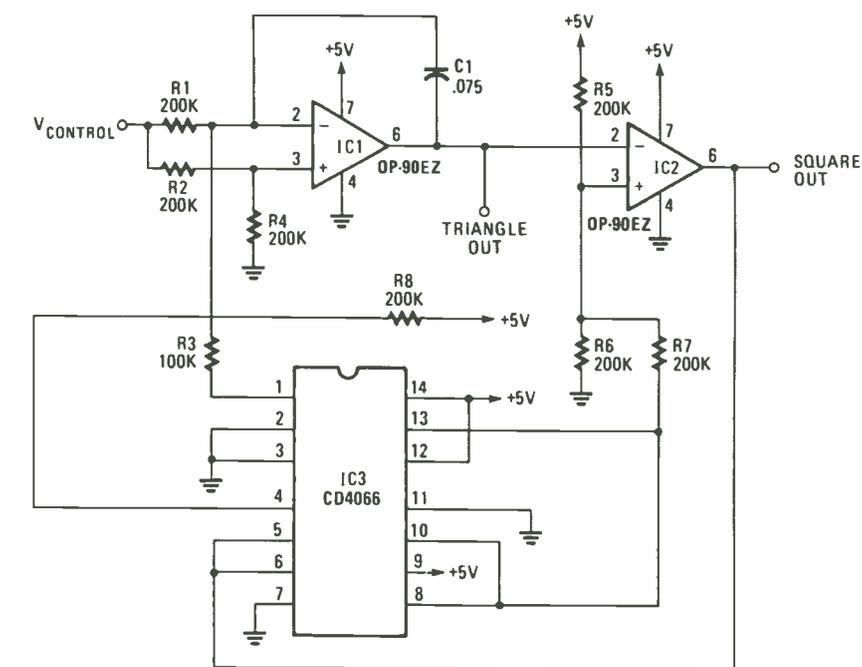


FIG. 1

and OP-90EZ; those are hermetic 8-pin DIP's with the former operating in the military temperature range and the latter in the industrial range. Both have  $V_{OS(max)}$  of 150  $\mu\text{V}$  at  $25^\circ\text{C}$  available. Another version, the OP-90FZ, also in a hermetic DIP; that device operates in the industrial temperature range and has 250- $\mu\text{V}$  maximum voltage offset.

Figure 1 shows how two OP-90's and a CD4066 CMOS quad bilateral switch can be used to make an inexpensive precision voltage-controlled oscillator. The oscillator provides squarewave and triangular-wave outputs up to a few hundred hertz, and draws only 50  $\mu\text{A}$  from a 5-volt power supply.

Op-amp IC1 is connected as an integrator. Op-amp IC2 is used as a Schmitt trigger, with resistors R5, R6, R7 and the associated internal CMOS switches setting the hysteresis to precisely 1.67 volts. The Schmitt-trigger action shapes IC1's output into a triangular waveform of 3.33 volts peak (5.00V - 1.67V). IC2's output is a squarewave whose amplitude swing is essentially zero to +5 volts.

The output frequency for the oscillator shown in Fig. 1 is:

$$f_{out} = V_{in}(\text{volts}) \times 10\text{Hz/V}$$

however, frequency can be varied—within limits—by changing the value of integrating capacitor C1. R-E

# MARKET CENTER

## FOR SALE

TV tunable notch filters, free brochure. **D.K. VIDEO**, Box 63 6025, Margate, FL 33063. (305) 752-9202.

**VIDEO** surveillance system for pvt inv. ins. Adj P.D. radio remote control operates unattended free brochure. **BILL PRICE AND ASSO.**, P.O. Box 568, Niceville, FL 32578.

## CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

**Radio-Electronics Classified Ads**, 500-B Bi-County Boulevard, Farmingdale, NY 11735

**PLEASE INDICATE** in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$23.00.

( ) Plans/Kits ( ) Business Opportunities ( ) For Sale  
( ) Education/Instruction ( ) Wanted ( ) Satellite Television  
( )

Special Category: \$23.00

### PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$42.75)
16 (\$45.60)	17 (\$48.45)	18 (\$51.30)	19 (\$54.15)	20 (\$57.00)
21 (\$59.85)	22 (\$62.70)	23 (\$65.55)	24 (\$68.40)	25 (\$71.25)
26 (\$74.10)	27 (\$76.95)	28 (\$79.80)	29 (\$82.65)	30 (\$85.50)
31 (\$88.35)	32 (\$91.10)	33 (\$94.05)	34 (\$96.90)	35 (\$99.75)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number

Expiration Date

Please Print Name

Signature

**IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**

**CLASSIFIED COMMERCIAL RATE:** (for firms or individuals offering commercial products or services) \$2.85 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS**, 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.30 per word prepaid...no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) 50¢ per word additional (20% premium). Entire ad in boldface, add 20% premium to total price. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **EXPANDED TYPE AD:** \$4.30 per word prepaid. All other items same as for STANDARD COMMERCIAL RATE. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **DISPLAY ADS:** 1" x 2 1/4"—\$320.00; 2" x 2 1/4"—\$640.00; 3" x 2 1/4"—\$960.00. General Information: Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 12th of the third month preceding the date of the issue. (i.e., Sept. issue copy must be received by May 12th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day.

**RESTRICTED technical information:** Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Large selection. Free brochure: MENTOR-Z**, 135-53 No. Blvd., Flushing, NY 1135-

**COMMODORE** chips, distributor factory fresh (e.g. 6526-\$9.95 and many others). C64 power supply—\$27.00. "Commodore Diagnostician", a complete chart for diagnosing faulty IC's \$6.95. Send for complete chips parts catalog. Kasara **MICROSYS, INC.**, 33 Murray Hill Drive, Spring Valley, NY 10977. (800) 642-7634 (outside NY) or (914) 356-3131.



## Quality Microwave TV Antennas

Super High Gain System \$99.95 (+ shipping)  
AMR High Gain System \$79.95 (+ shipping)  
Multi-Channel 1.9 to 2.7 GHz

Dealerships, Qty. Pricing, Replacement Parts

**Philips-Tech Electronics**

P.O. Box 8633 • Scottsdale, AZ 85262

(602) 947-7700 \$3.00 Credit all phone orders!

LIFETIME WARRANTY

MasterCard • Visa • CDS

**TUBES:** "Oldest," "Latest." Parts and schematics. SASE for list. **STEINMETZ**, 7519 Maplewood Ave., RE Hammond, IN 46324.

**TEXT 2 upgrade CD players, other equipment with Audio Amateur, world's only audio construction quarterly. \$18/year; \$30/two. Satisfaction guaranteed MC/VISA (603) 924-9464; checks to Box 576, Dep. E78, Peterborough NH 03458-0576.**

**APEX** screwdriving bits. Any size. Free bargain list. Write: **R. SHOCKEY'S**, 5841 Longford, Dayton, OH 45424.

**WHOLESALE** car stereos, alarms, electronics. Huge selection. Send SASE. **NORMAN ELECTRONICS**, Box 3579A Ridgewood, NY 11386.

**PRINTER** switch w/cables, serial/ parallel \$39.85. Free brochure **HAWK**, 2430 Oarfish Lane, Oxnard, CA 93035.

**PLASMA** sphere, fascinating lightning display. Build yours for \$50, plans \$10, prefilled sphere parts kit \$50, deluxe kit \$75, assembled \$125. exotic catalog \$2. **RIESS**, POB 54625, Dept. E, Phoenix, AZ 85078.

**LASER power supplies** 120V battery operation 1 to 5MW. Adjustable kit \$39.00 1MW kit \$29.00. Send for free data sheet **GENERAL SCIENCE & ENGINEERING ROCH.** N.Y. PO Box 447, 14603.

**MICROWAVE** antennas, multi-channel 1.9-2.7 ghz. dual polarity. Now only \$49.95. Oldest and largest manufacturer. **STAR ELECTRONICS CORP.**, Call 1-800-247-1151 or 1 (602) 939-1151.

**SILVER** solder syringe just add heat \$13.95. **MISCO**, 7619 Detour, Cleveland, OH 44103.

**SIZZLING** deals: Zenith (The Real Thing); Jerold oak scientific Atlanta. No Michigan sales **HOTRONICS** (313) 283-4299.

## CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10M-FM conversions, repairs, books, plans, kits, high-performance accessories. Our 11th year! Catalog \$2.

**CBC INTERNATIONAL, P.O. BOX 31500RE. PHOENIX, AZ 85046**

**FLASHLIGHT** that needs no batteries measures 5' x 3' ideal for every situation money back guarantee \$10 — **SAMUELS ENTERPRISES**, 724 East 231 Street, Bronx, NY 10466.

**FREE** catalog—quality low noise, high gain, VHF UHF pre-amplifiers, VHF to UHF converters, PSUs, power amplifiers 10-1000 MHz, filters, etc. Contact **K.T. ELECTRONICS**, Rathorum, Co. Wicklow, Ireland.

RADIO tubes. Send \$1.00 (refundable) for extensive lists. DIERS, 4276-E North 50th Street, Milwaukee, WI 53216-1313.

TUBES, name brands. New. 80% off list. KIRBY, 298 West Carmel Drive, Carmel, IN 46032.

FREE power supply with Assortment #103 (February '84 article, has printed circuit, TOKO coils(4), 2N3904(2), BQ85, 7812, 74123, MC1330, 1N914, 1N5231B. TELE-ASE-MAST ASSORTMENT #301 (October Article) Printed Circuit with all IC's, transistors, diodes. Only \$25.00/each assortment. Five/\$112.50. Shipping \$3.00. 1 (800) 821-5226 Ext. 426. (orders) or write JIM RHODES INC., P.O. Box 3421, Bristol, TN 37625.

DESCRAMBLER catalog. All brands. Special combo Jerrold 400 and SB3 \$165. Descrambler kit \$39.00 (assembles in half hour). Send \$1.00. MJ INDUSTRY, Box 531, Bronx, NY 10461.

TUBES! 59¢. Year guarantee. Free catalog. Tube tester \$8.95. CORNELL, 4215 University, San Diego, CA 92105.

IS it true...Jeeps for \$44 through the government? Call for facts! 1 (312) 742-1142, ext. 4673.

OLDTIME radio programs on high quality tapes. Comedy! Adventure! Music! Free catalog. CARL F. FROELICH, Heritage Farm, New Freedom, PA 17349.

TEST equipment, reconditioned. For sale. \$1.25 for catalog. WALTER'S, 2697 Nickel, San Pablo, CA 94806. (415) 724-0587.

OLD radio TV schematics. Send \$1.00, make model. RADIO MAPS, P.O. Box 791, Union City, CA 94587.

**A SINGER'S DREAM!**



**REMOVES VOCALS FROM RECORDS!**  
Now You can sing with the world's best bands! The Thompson Vocal Eliminator can remove most or virtually all of a lead vocal from a standard stereo record and leave the background!  
Write or call for a free brochure and demo record.  
LT Sound, Dept. R-1, P.O. Box 338, Stone Mountain, GA 30086 (404) 493-1258

LASERS, components and accessories. Free catalog. M.J. NEAL COMPANY, 6672 Mallard Ct., Orient, OH 43146.

BUILD your own pro monitors 32 pg. 5 part manual discloses design criteria utilized by major manufacturers of pro monitoring systems. Blueprints included! \$25.00 complete to: BRUX ENTERPRISES INC., 2419 Richmond Road, S.I.N.Y 10306.

TUBES, new, unused. Send self-addressed, stamped envelope for list. FALA ELECTRONICS, Box 1376-2, Milwaukee, WI 53201.

ZENITH SSAVI, ready to go \$100.00 plus shipping, order C.O.D. 1 (305) 752-9202.

DECODE nearly any Gated Pulse signal with our new super simple circuit. Works on in-band, AM or FM pilot tone—use with Hamlin, Jerrold, Sylvania. Complete plans and theory only \$13.50 plus \$1.50 P&H. ELEPHANT ELECTRONICS INC., Box 41865-J, Phoenix, AZ 85080. (602) 581-1973.

ROBOT! kits. Books and Plans! Learn to build your own robots. Free catalogs contain hundreds of affordable robot systems. Explore the world of robotics today. Catalog: CEARGS-ROBOTS!, POB 458, Peterborough, NH 03458. (603) 924-3843.

VIDEO scrambling techniques, the original "secret manual" covers Sinewave, Gatedpulse, and SSAVI systems. 56 pages of solid, useful, legible information. only \$14.95 ELEPHANT ELECTRONICS INC., Box 41865-J, Phoenix, AZ 85080. (602) 581-1973.

PHOTOFACT folders, under #1400 \$3.00. Others \$5.00. Postpaid. LOEB, 414 Chestnut Lane, East Meadow, NY 11554.

EQUIPMENT liquidation: Surplus remote-control converters, with touch-type remotes, favorite channel programmable, digital PLL synthesized, automatic fine tuning, switched TV outlet, 30 day warranty, \$35.00. Quantity package 25 + units \$15.00/ea, field run, as is (includes service manual). Oak minicode N12 decoders quantity package 25 + units \$20.00/ea, field run, as is. "Beeping", notch filter CH3 decoders, 30-day warranty, \$15.00/ea, quantity 25 + \$10.00/ea, field run, as is, shipped prepaid. All others add \$3.00 unit shipping. Send money order to ELECTRONICS PRESS, PO Box 10009, Colorado Springs, CO 80932.

TI-99/4A software/hardware bargains. Hard to find items. Huge selection. Fast service. Free catalog. DYNA, Box 690, Hicksville, NY 11801.

FREE IBM clone motherboards bare send \$6.00 P&H. DRUIZ, P.O. Box 26201, Santa Ana, CA 92799-6201.

CABLE TV CONVERTERS. Scientific Atlanta, Jerrold, Oak, Zenith, Hamlin. Many others. "New" VIDEO HOPPER "The Copy Killer". Visa, M/C & Amex Accepted. Toll Free 1-800-826-7623. B&B Inc., 10517 Upton Circle, Bloomington, Mn. 55431.

TOUCH ON LAMP conversion module convert your metallic lamp in minutes to touch on, 3 levels, 200 watts, \$19.95 LSE, Box 424, Sun Prairie, WI 53590

CABLE-TV converters and descramblers. Low prices, quality merchandise, we ship C.O.D. Send \$2.00 for catalog. CABLETRONICS UNLIMITED P.O. Box 266, South Weymouth, MA 02190 (617) 843-5191.

**Parts Express** INTERNATIONAL INC. **HARDWARE AND ELECTRONICS**



**MAGNIFIER LAMP**  
• 4 diopter magnifying lens  
• Uses up to a 60 watt bulb (not included) UL listed 117VAC  
#350-010 **\$2695**



**COPPER CLAD PC BOARD**  
9 x 8 Double Sided #055-300 **\$150**  
18 x 12 Double Sided #055-320 **\$395**



**RS-232 DATA SWITCH**  
• 2 position rotary type • Fully shielded FCC approved  
#130-010 **\$2795**



**PIONEER HORN TWEETER**  
• Frequency response 1800 to 15 000Hz • Power handling capabilities 35W RMS resonant frequency 2 kHz 3" x 3"  
#270-050 **\$650** **\$590** (11.9) (10.9P)



**12" PIONEER WOOFER**  
• Power 65W RMS • 11 oz magnet • 25 to 2500 Hz response • 1 1/2" voice coil  
#280-100 **\$1550** **\$1395** (1.31) (1.10)



**TOROIDAL TRANSFORMER**  
• 120 volt primary 2 - 20V 5A secondaries • 4 1/2" round • 4 lbs  
#120-150 **\$1250** **\$995** (1.31) (1.41P)



**300 PIECE CAPACITOR KIT**  
• A great assortment of different values and working voltages includes electrolytics, ceramics, mylers, and more!  
#020-920 **\$495**

**FREE CATALOG**

Our new 56 page catalog contains thousands of items that you need every day for do-it-yourself projects, product engineering, electronics repair and more. Call us today for your free copy and start saving!



**CALL TOLL FREE**  
**1-800-255-3525**

In Ohio: 1-800-322-3525  
Local: (513) 222-0173

• 15 day money back guarantee. • \$10.00 minimum order. • COD orders accepted • 24 hour shipping • Shipping charge • UPS chart rate (\$2.50 minimum charge). Hours 8:30 a.m. - 6 p.m. EST M-F.

**PARTS EXPRESS INTL INC.**  
340 East First St  
Dayton, Ohio 45402


You can help us raise the colorectal cancer cure rate.

When detected early, the cure rate for colorectal cancer is very high. That's why we urge regular checkups for men and women 50 and over.

Warning signs are a change in bowel habits, blood in the stool.

Your doctor can perform the digital and proct exams, and you take care of the stool blood test at home.

Checkup Guidelines for men and women over 50 without symptoms:  
• digital exam annually  
• stool blood test annually  
• proct exam every 3 to 5 years after 2 negative tests 1 year apart

NO ONE LIVES cancer alone.  
AMERICAN CANCER SOCIETY

## PLANS AND KITS

BUILD this five-digit panel meter and square-wave generator including an ohms, capacitance and frequency meter. Detailed instructions \$2.50. BAGNALL ELECTRONICS, 179 May, Fairfield, CT 06430.

HI-FI speaker systems, kits and speaker components from the world's finest manufacturers. For beginners and audiophiles. Free literature. A&S SPEAKERS, Box 7462, Denver, CO 80207. (303) 399-8609.

VOICE disguisers! FM bugs! Telephone transmitters! Phone snoops! More! Catalog \$1.00 (Refundable): XANDI ELECTRONICS, Box 25647, Dept. 60R, Tempe, AZ 85282.

PROJECTION TV...Convert your TV to project 7 foot picture. Results comparable to \$2,500 projectors...Total cost less than \$30.00 plans and 8" lens \$21.95...Illustrated information FREE...MACROCOMA-GA, Washington Crossing, PA 18977. Creditcard orders 24hrs. (215) 736-3979.

JERROLD gated pulse theory. Twelve information-packed pages covering DI & DIC converter operation. Includes introduction to trimode system. \$6.95 plus \$1.50 postage and handling. ELEPHANT ELECTRONICS INC., Box 41865-J, Phoenix, AZ 85080. (602) 581-1973.

DESCRAMBLE the latest video cassette copy-protection scheme. Our simple line zipper circuit takes the jitter out of your picture. Complete plans and theory only \$13.95 plus \$1.50 postage and handling. PC board and complete kits also available. ELEPHANT ELECTRONICS INC., Box 41865-J, Phoenix, AZ 85080. (602) 581-1973.

MINIATURE electronic devices, like James Bond's. Catalog \$2.00. F&P ENTERPRISES, Box 51272, Palo Alto, CA 94303-L.

CIRCLE 208 ON FREE INFORMATION CARD



**CRYSTAL** radio sets, plans, parts, kits, catalog \$1.00. **MIDCO**, 660 North Dixie Highway, Hollywood, FL 33020.

**CATALOG:** hobby broadcasting/1750 meters/ham/CB: transmitters, antennas, scramblers, bugging devices, more! **PANAXIS**, Box 130-F10, Paradise, CA 95967.

**FREE catalog 99-cent kits**—audio, video, TV, computer parts. **ALLKIT**, 434 W. 4th St., West Islip, NY 11795.

**STRANGE stuff.** Plans, kits, new items. Build satellite dish \$69.00. Descramblers, bugs, adult toys. Informational photo package \$3.00 refundable. **DIRIJO CORPORATION**, Box 212, Lowell, NC 28098.

**PAC-TEC Enclosure** specified in Feb. '87 R-E article on Tri-Mode. Pre-drilled. \$24.95 plus \$2.50 or send to **THE HOBBY HELPER**, P.O. Box 308, Bridgewater, MA 02324.

## WRITE FOR MCGEE'S SPEAKER & ELECTRONICS CATALOG

1001 BARGAINS IN SPEAKERS  
toll free 1-800-346-2433 for ordering only.  
1901 MCGEE STREET KANSAS CITY, MO. 64108

**DETECTIVES**, experimenters. Exciting new plans. Hard to find micro and restricted devices. Large catalog \$5.00 refundable on 1st order. **WILSON**, P.O. Box 5264, Augusta, GA 30906.

**FREE** microprocessors, memory chips, etc. Free electronics magazine subscriptions. Free education in computers. For information write **MICROSAT CORPORATION**, 2401 N.E. Cornell, Bldg. 133, Mail Stop 125, Hillsboro, OR 97124.

**VIDEO TAPE  
COPYGUARD**

**Eliminate the latest copyguard problems  
units from \$59<sup>95</sup> to \$169<sup>95</sup>**

*Deluxe Electronics* ..... (714) 998-6866  
1432 Heim Wy., Orange, Ca. 92665

**DESCRAMBLING**, New secret manual. Build your own descramblers for **Cable and Subscription TV**. Instructions, schematics for SSAVI, gated sync, sinewave. (HBO, Cinemax, Showtime, etc.) \$8.95 + \$1.00 postage. Catalog \$1.00. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

**SATELLITE descrambling manual**, Video Cypher II. Schematics, thorough explanation of digital audio encoding, EPROM code. DES. (HBO, Cinemax, Showtime.) \$10.95 + \$1.00 postage. Catalog \$1.00. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

**WEIRD**, facinating, unusual, fun projects for the electronics gadgeteer. Free information. **TAYLOR ELECTRONICS**, P.O. Box 1612, Destin, FL 32541.

### BUSINESS OPPORTUNITIES

**MECHANICALLY** inclined individuals desiring ownership of small electronics manufacturing business—without investment. Write **BUSINESSES**, 92-R, Brighton 11th, Brooklyn, NY 11235.

**PROJECTION TV**.. Make \$\$\$'s assembling projectors...easy...results comparable to \$2,500 projectors. Total cost less than \$30.00. **PLANS**, 8' **LENS** and dealers information \$20.50. Illustrated information free. **MACROCOMA-GAX**, Washington Crossing, PA 18977. Creditcard orders 24hrs. (215) 736-2880.

**YOUR own radio station!** AM, FM, cable. Licensed or unlicensed. **BROADCASTING**, Box 130-F10, Paradise, CA 95967.

**PERSONAL** computer owners can earn \$1000 to \$5000 monthly offering simple services part time. Free list of 100 services. Write: **C.I.L.G.B.**, P.O. Box 60369, San Diego, CA 92106-8369.

**BIG PROFITS  
ELECTRONIC ASSEMBLY BUSINESS**

Start home spare time investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

**FREE:** Complete illustrated literature  
BARTA, RE-O Box 248  
Walnut Creek Calif 94597

**EARN** thousands with your own electronics business. I do. Free proof, information. **INDUSTRY**, Box 531, Bronx, NY 10461.

**HOME** assembly. Assemble PC boards for video accessories. We supply materials. No experience needed. \$7.50 per hour. Send self-addressed stamped envelope, to: **MICRON-ELECTRONICS**, Box 4716, Akron OH 44310.

### SATELLITE TV

**CABLE TV** Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included \$8.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

**SATELLITE TV** equipment. Buyers guide, discount prices. \$3.00 **N.E.C.S. INC.**, Box 22808-R1, Little Rock, AR 72221.

# GREAT VALUES • FAST SHIPPING • QUANTITY DISCOUNTS

**150MC Digital Frequency Counter**



Frequency Range: 10Hz - 150MHz  
Event Counter: 0 to 99999999 counts (8 Digit)  
Input sensitivity: KHz range 10Hz - 10MHz 50mVrms  
MHz range 1MHz - 150MHz 40mVrms  
Response time: 0.2 second  
Hold Function: Hold the last input signal  
Power Supply: DCGV Battery or DCGV Adaptor  
Dimensions: 9 7/8" x 6 11/16" x 2 3/4"  
Assembled with tested

**FREE AC ADAPTOR AVAILABLE UNTIL STOCKS LAST**

**SM-100**

**ONLY \$99.00**

**HIGH QUALITY PRE-AMPLIFIER WITH 10 BAND EQUALIZER**



**NEW with CD input stage**

Ass. with tested

**\$40.00**

**INFRARED REMOTE CONTROL UNIT**



**FREE DELUXE CONTROL BOX**

**TA-41MKV**

**CAN BE SWITCHED ON TO ANY ELECTRICAL APPLIANCES UP TO 200W!**

**FREE CATALOG**

**2nd. Anniversary**

**FREE \$10 Coupon** with every purchase over \$10

**120W MOSFET POWER AMPLIFIER TA-477**

Kit Metal Cabinet/X-Former (Optional) \$61.28 \$260.00 \$198.88

**PROFESSIONAL COLOR LIGHT CONTROLLER SM-328**

Kit

Ass. with tested

**\$30 \$45**

**STEREO SIMULATOR TA-3000**

UP GRADE YOUR TV & VCR

**NEW FOR 87**

**MARK V PROMISES TO SERVE YOU THE BEST**

Kit only \$25

Ass. with tested

**\$30.00**

**OFFICE HOURS: (PACIFIC TIME)**  
MON.—FRI, 9:30 to 5:00 SAT. 10:00 to 5:00

**INFORMATION: 1-818-282-1196**  
**MAIL ORDER: P.O. BOX 6610 ALHAMBRA, CA 91802**

**100W + 100W NEW CLASS 'A' DC STEREO PRE-MAIN AMPLIFIER**



**TA-1500**

**200W POWERFUL AMP W/MIC MIXER!**

Kit Metal Cabinet/X-Former \$67.00 \$26/\$168.00

**ELECTRONIC ECHO AND REVERBERATION AMPLIFIER**



**TA-2400A**

**REMIK RECORDS W/ECHO EFFECT YOURSELF!**

Ass. with tested

**\$99.85**

**TERMS:** \$10 min order • \$20 min charge card order • Check, money order or phone order accepted • We ship UPS Ground • Add 10% of total order (min \$2.50) for shipping, outside USA add 20% (min \$5.00) • CA residents add sales tax • All merchandise subject to prior sale • Prices are subject to change without notice • Any goods proved to be defective, **MUST BE RETURNED IN ORIGINAL FORM WITH A COPY OF YOUR INVOICE WITHIN 30 DAYS FOR REPLACEMENT**

**MARK V ELECTRONICS INC.,**  
248 EAST MAIN STREET, SUITE 100,  
ALHAMBRA, CA 91801  
TELEX: 3716914 MARK 5

**1-800-423-3483**

**TOLL FREE**

Only for orders paid by Master or Viscard

**IN CAL.: 1-800-521-MARK**

**CIRCLE 93 ON FREE INFORMATION CARD**



# Plug a Friend into Radio-Electronics this Christmas ... and Save \$12!

**This Christmas give an electrifying gift ... plug a friend into Radio-Electronics and brighten his whole new year! Whether electronics is his livelihood or his hobby, your gift will sharpen his focus and illuminate the whole spectrum of electronics throughout the coming year.**

Radio-Electronics will keep him informed and up-to-date with new ideas and innovations in all areas of electronic technology ... computers, video, radio, stereo, solid state technology, satellite TV, industrial and medical electronics, communications, robotics, and much, much more.

He'll get complete plans and printed circuit patterns for building valuable test equipment and electronic devices for home and car — practical money-savers like these ... a TV signal descrambler ... a video test generator ... an auto exhaust analyzer ... a clockboard for his PC ... a radio commercial zapper ... a solid state barometer ... a working robot ... and many others!


**PLUS ... equipment repair and troubleshooting ... circuit design ... new**

product news and buyer's guides ... service clinics ... equipment test reports ... a special "ComputerDigest" section ... regular columns on video, stereo, radio, circuits, solid state, satellite TV and robotics ... and lots more exciting features and articles.

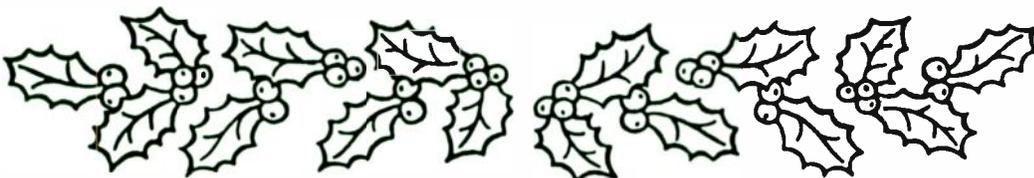**SAVE \$12 ... OR EVEN \$24 ... For each gift of Radio-Electronics you give this Christmas, you save a full \$12.00 off the newsstand price. And as an R-E gift donor, you're entitled to start or extend your own subscription at the same Special Holiday Gift Rate — you save an additional \$12.00!**

No need to send money ... if you prefer, we'll hold the bill till January, 1988. But you must rush the attached Gift Certificate to us to allow time to process your order and send a handsome gift announcement card, signed with your name, in time for Christmas.

So do it now ... take just a moment to fill in the names of a friend or two and mail the Gift Certificate to us in its attached, postage-paid reply envelope. That's all it takes to plug your friends into a whole year of exciting projects and new ideas in Radio-Electronics!



**DESCRAMBLER.** Build our low cost satellite TV video only descrambler for all major movies and sports. Uses all Radio Shack parts. Order P.C. board and instructions by sending cheque, money order, or Visa for \$35.00 U.S. funds to: **VALLEY MICROWAVE ELECTRONICS**, Bear River, Nova Scotia, Canada, BOS-1BO. (902) 467-3577.

**Multi-Channel Microwave T.V. Receivers**



1.9-2.7 GHz Parabolic Dish 40-dB Gain  
**LIFETIME WARRANTY**  
 Complete System \$89.95 (Shipping Incl.)  
 Replacement Components  
 & Expert Repairs Available  
**K & S ELECTRONICS** Call now for same  
 P.O. BOX 34522 day shipping!  
 PHOENIX, AZ 85067 (602) 230-0640  
 VISA/MC/COD For Dealer Rates Call 602-888-4080

**SATELLITE TV** receiver kits! LNAs! Instructions! Schematics! Catalog \$1.00 (refundable): **XANDI ELECTRONICS**, Box 25647, Dept. 21T, Tempe, AZ 85282.

**SCIENTIFIC** Atlanta cable users series 8500 8550 get all channels instructions for simple modification costs under \$10.00 to make. Complete instructions. Send \$10.00 no checks to **K.F. SPECIALTIES**, P.O. Box 443, Forked River, NJ 08731.

**SATELLITE** systems \$295 up. VISA MC available. Catalog \$3. **STARLINK INC.**, 2603-16R Artie, Huntsville, AL 35805.

**10ft Satellite system**, remote controlled, tracker and descrambler with 1 yr free subscription to 20 channels. \$1,495 plus UPS. **VISTA VISION**, 1 (602) 458-5482 after 10 a.m.

**DESCRAMBLERS** for movies, networks. \$149. video only; \$399, complete. Catalog \$4.00. **SKY-WATCH**, 238 Davenport Road, Toronto, Ontario, Canada M5R-1J6.

**LOOK** SPECIAL INTRODUCTORY OFFER  
 Mention This Ad  
 And Take **10% OFF** PRICES LISTED BELOW

**\*5-1/4" FLOPPY DISKS**  
 Software excess, erraced, Guaranteed. DSDD, with New Labels & Sleeves. . . . . \$29.50/100  
**LARGE QTY. PRICES AVAILABLE**

**INFRARED ENERGY DETECTOR KIT**  
 Just \$8.88  
 Allows you to listen to infrared Energy & AC Current.

**COMPLETE 1Mw LASER TUBE & POWER SUPPLY KIT**



\* Assembly Must Conform to Gov't Specs.

- JUST \$129.90**
- \* 2Mw Laser Tube (uncased) . . . \$139.95
  - \* 5Mw Laser Tube (uncased) . . . \$159.95
  - \* 7 to 25 Watt Laser Diode . . . \$14.88
  - \* Infrared Goggles (AN/PAS5) . . . \$399.95
  - \* Jacobs Ladder/Testa Coil Kit . . . \$19.88

**BNF Enterprises**  
 119r FOSTER St.  
 Peabody MA 01960  
 (617) 531-5774  
 Free! 36 Page Catalog

**Customer Pays All Shipping Charges**  
 CIRCLE 206 ON FREE INFORMATION CARD

**Cable TV Converters**

**Why Pay A High Monthly Fee?**

Jerrold Products include "New Jerrold Tri-Mode," SB-3, Hamlin, Oak VN-12, M-35-B, Zenith, Magnavox, Scientific Atlanta, and more. (Quantity discounts) 60 day warranty. For fast service C.O.D. orders accepted. Send SASE (60 cents postage) or call for info (312) 658-5320. **Midwest Electronics, Inc./, HIGGINS ELECTRONICS**, 5143-R W. Diversey, Chicago, IL 60639. MC/Visa orders accepted. No Illinois orders accepted. Mon.-Fri.-9 A.M.-6 P.M. CST

**WANTED**

**INVENTORS!** AIM wants—ideas, inventions, new products, improvements on existing products. We present ideas to manufacturers. Confidentiality guaranteed. Call toll free 1-(800) 225-5800 for information kit.

**INVENTIONS**, ideas, new products wanted! Industry presentation national exposition. Call free 1-(800) 288-IDEA. Canada, 1-(800) 528-6060. X831.

**SURPLUS INVENTORIES** of ICs, transistors, etc., no quantity too small or large. Call **WESTERN TECHNOLOGY**, (303) 444-4403. FAX (303) 444-4473.

**INVENTORS**

**INVENTORS!** Can you patent and profit from your idea? Call **AMERICAN INVENTORS CORPORATION** for free information. Over a decade of service. 1-(800) 338-5656. In Massachusetts or Canada call (413) 568-3753.

**DO IT YOURSELF TV REPAIRS**

**NEW...REPAIR ANY TV...EASY.** Anyone can do it. Write **RESEARCH**, Rt. 3, Box 601R, Colville, WA 99114.

**TUBES - 2000 TYPES DISCOUNT PRICES!**

Early, hard-to-find, and modern tubes. Also transformers, capacitors and parts for tube equipment. Send \$2.00 for 20 page wholesale catalog.

**ANTIQUE ELECTRONIC SUPPLY**  
 688 W. First St. • Tempe, AZ 85281 • 602/894-9503

**EDUCATION & INSTRUCTION**

**F.C.C. Commercial General Radiotelephone license.** Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2223, San Francisco, CA 94126.

**CASSETTE** recorded home study for new General Class FCC license examinations. Seminars in Philadelphia, Detroit, Boston, Washington. **BOB JOHNSON TELECOMMUNICATIONS**, 1201 Ninth, Manhattan Beach, CA 90266. (213) 379-4461.

**HAM licenses supereasy.** Cut exam preps 50%. All classes. Free catalog. **SASE. BAH**, 2549-E4 Temple, Palmbay, FL 32905.

**FCC Commercial General Radiotelephone license** correspondence course. 60 individual lessons for \$89.50. Payment plan. Results guaranteed! Details free. **AMERICAN TECHNICAL INSTITUTE**, Box 201, Cedar Mountain, NC 28718.

**IBM-PC SOFTWARE**

**COMPSS—Computer-Aided circuit design**, selections from basic electricity to circuit designs. Very educational. \$49.95 (614) 491-0832. **ESOF SOFTWARE**, 444 Colton Road, Columbus, OH 43207.

**COMPUTERS**

**TANDY computers!** MSDOS, IBM, compatible. Discount prices! For quote or purchase call 1-800-36-SHACK. **EDGEWOOD COMPUTER CENTER.**

**PAY TV AND SATELLITE DESCRAMBLING NOW 120 PAGES**

Schematics theory bypasses 13 cable 7 satellite systems including After Dark Video \$14.95 & Ed Update Only \$8.95 Exterminator With Vitec Together Latest circuits cloning musketeering data \$12.95 Cable TV Two-way security systems design \$12.95 **MDS MMS Handbooks** For microwave hackers \$9.95 **Build Satellite Systems Under \$600** \$12.95 Any 3 \$26 Summer catalog \$1

**Shojiki Electronics Corp.** 1327A Niagara St., Niagara Falls, NY 14303. COD's 716-284-2163

**DESCRAMBLER MODULE**

**COMPLETE** cable-TV decoder in a mini-module. Latest technology upgrade for Jerrold SB-3 or Radio-Electronics Feb. 1984 project. Available at very-low cost. For literature, **SOUTHTECH DISTRIBUTING**. 1-(800)-821-5226 ext. 130.

**NOTCH FILTERS**

**NOTCH** filters for any channel. Send \$15.00 for sample unit. Specify output channel of converter. Money back guarantee. **DB ELECTRONICS**, P.O. Box 8644, Pembroke Pines, FL 33084.

**THE POSITRAP COOKBOOK:** Build 50-60dB notch filters for pennies. Construction, alignment, fixed, tunable, trimable. Comprehensive **CABLE TV SCRAMBLING AND DESCRAMBLING** theory and practice. Identifying various systems. \$9.95 **CLEARVIEW CABLE COMPANY**, P.O. Box 207, Sterling Heights, MI 48311.

**NUTS & VOLTS MAGAZINE** P.O. Box 1111-E, Pleasanton, CA 94670 714-932-7721

**GIVE YOURSELF A BREAK — A PRICE BREAK!** NUTS & VOLTS WILL **SAVE YOU MONEY** ON ELECTRONIC PARTS & EQUIPMENT. **PLEASE SHOW US WHERE TO FIND UNIQUE, UNUSUAL AND HARD-TO-FIND ITEMS.** **SUBSCRIBE TODAY!**

Subscription Rates:  
 1 Yr. \$10.00  
 2 Yrs. \$18.00  
 3 Yrs. \$28.00  
 1st Class Mail  
 Outside USA \$18.00  
 Canada/Mexico \$20.00  
 Air Mail  
 Foreign \$25.00

*A National Publication For The Buying And Selling Of Electronic Equipment*

**SCIENTIFIC ATLANTA & SB-3**

**SCIENTIFIC ATLANTA** Models 8500 - 8550, remote included...\$240.00 SB-3's...\$74.00 TRI-BI's...\$95.00 SBSA-3's...\$99.00 Zenith (Z-Tac) Descramblers...\$169.00. N-12 (Vari-sync)...\$89.00. M-35B (Vari-sync)...\$99.00. Jerrold-450 and 550-Meg converters...\$95.00. Dealer Discount on (5) units. Brochure available. Call...N.A.S. (213) 631-3552.

**REMOTE CONTROL KEYCHAIN**

Complete w/mini-transceiver and +3-15vdc receiver Fully assembled including plans to build your own auto alarm

**\$14.95** Check, Visa or M/C 30 days return

**VISITECT INC.** (415) 872-0128  
 PO BOX 5442, SO. SAN FRAN., CA 94080

Copies of articles from this publication are now available from the **UMI Article Clearinghouse.**

**UMI Article Clearinghouse**

Mail to: University Microfilms International  
 300 North Zeeb Road, Box 91 Ann Arbor, MI 48106

# Here is just a sample of what you'll find at MCM Electronics

## Tenna 15MHz Dual Trace Portable Oscilloscope

- Dual trace model capable of displaying signals up to 15MHz, for up to two hours on a single charge of its internal battery
- Power can be supplied from either a 12VDC or 120/240V 50/60Hz AC source



## Tenna LCR Meter

- LCR Meter provides a convenient way to accurately measure inductance, capacitance and resistance (.01ohm resolution) on its 3 1/2 digit LCD display



For more specs and Test Equipment see pages 146-154 of Catalog #15

## Anti-Static Work Mat

- A must for the modern service shop
- Use in conjunction with our #21-660 wrist strap to help eliminate static related problems
- 18" x 26"



## Anti-Static Wrist Strap

- This wrist strap when used with our anti-static work mat, will effectively dissipate static charges
- The five foot coiled cord with 1Mohm resistor, snaps to wrist strap to give user added mobility
- Cord is terminated with a banana plug and alligator clip



For complete information see page 136 of Catalog #15



**MCM ELECTRONICS**  
858 E. CONGRESS PARK DR.  
CENTERVILLE, OH 45459  
A PREMIER Company



## Tenna Soldering Station

- Adjustable temperature range of 150°-420° C (300°-790° F)
- Grounded tip for soldering static sensitive devices
- Overheat protection with closed loop temperature control
- Replaceable iron clad tip
- Improved circuit design for greater temperature stability

## Tenna Deluxe Anti-Static Desoldering Tool

- Rugged metal construction
- Anti-static tip
- Nozzle cleaner
- Lightweight and compact
- Disassembles easily for cleaning
- 7 3/4" long x 3/4" diameter

Additional Soldering Equipment can be found on pages 137 and 138 of Catalog #15

## Super Wash

- Powerful spray cleans intricate electronic assembly without harming plastics
- Dries instantly
- Spray literally blasts dirt and grease away
- 24 oz.



## Tuner Cleaner

- Cleans, lubricates, protects
- Cleans and restores dirty and corroded contacts
- Doesn't harm plastics
- 16 oz.



For more Chemicals see pages 128-130 of Catalog #15

## Diskette File Box

- Stores up to 70 — 5 1/4" diskettes
- Case made of anti-static ABS plastic with smoked acrylic cover
- Six adjustable index dividers



## Deluxe Joystick for Atari and Commodore

- For use with Atari, Commodore and other VCS compatible systems
- Two firing buttons
- 5.5' cord with 9 pin plug

Catalog #15 has other Computer Equipment and Accessories on pages 119-127

©1987 MCM Electronics



Be Sure To Call For Your FREE Catalog!  
Over 9,000 Items!  
Call Toll Free 1-800-543-4330

In Ohio 1-800-762-4315 In Alaska and Hawaii 1-800-858-1849

SOURCE CODE: RE-36

CIRCLE 87 ON FREE INFORMATION CARD



# Worldwide • Since 1974

• QUALITY COMPONENTS • COMPETITIVE PRICING  
• PROMPT DELIVERY

Mail Order Electronics - Worldwide  
**Jameco**  
ELECTRONICS

## General Purpose NEW! Prototype PC Boards



JE417 (Pictured)

- Wire Wrap
- Component Testing
- Point-to-Point Wiring
- 31/62 Connection

- JE411 (6 1/2", No Pads, Gen. Purp.) . . . \$12.95  
JE415 (6 1/2", No Pads, PC/XT) . . . \$14.95  
JE417 (6 1/2", Plated w/Pads, PC/XT) . . . \$19.95



**Extender Boards  
Designed for  
Troubleshooting  
and Testing**

JE419 (Pictured)

- JE419 (5 1/4" Extender, 22/44 Connector) . . \$19.95  
JE421 (4 1/4" Extender, 31/62 Connector) . . \$19.95

## Commodore VIC-20 and C-64 Motherboards



May have to troubleshoot or just use for spare parts  
CV20 Includes: (1) 6560, (2) 6522, (1) 6502, (2) 6116P-4, and much more!

CV64 Includes: (1) 6567, (1) 6581, (1) 6510, (1) 82-S100PLA, (1) 901227-03, (2) 6526, and much more!


- CV20 (VIC-20 Motherboard) . . . \$14.95  
08903-3 (SAMS VIC-20 Schematics) . . . \$19.95  
CV64 (C-64 Motherboard) . . . \$49.95  
08906-8 (SAMS C-64 Schematics) . . . \$19.95

### Additional Commodore Accessories

- \*CM-1 (300B Modem VIC-20, C-64) . . \$19.95  
\*JE232CM (RS232 Inter. VIC-20, C-64) . \$39.95  
CPS-10 (C-64 Power Supply) . . . \$39.95  
CPS-128 (C-128 Power Supply) . . . \$59.95

\*Also compatible with C-128 in 64 mode only

## ZUCKERBOARD

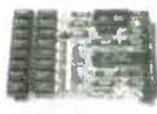

**TANDY 1000  
Expansion Memory  
Half Card**

Expand the memory of your Tandy 1000 (128K Version) to as much as 640K. Also includes DMA controller chip.

- TAN-EM512K Includes 512K RAM . . . \$119.95  
TAN-C Plug-in Clock option chip (only) \$39.95

### SALE! 20Meg Hard Disk SALE!

- T20MB 20MB Hard Disk Drive Board for Tandy 1000 . . \$579.95 \$494.95  
SX20MB 20MB Hard Disk Drive Board for Tandy 1000SX \$589.95 \$499.95



**TANDY 1000  
Multifunction  
Board with  
Clock Calendar**

Expand the memory on your Tandy 1000 (128K Version) to as much as 640K. Complete with an RS232 port, clock/calendar, RAM Disk, Printer Spooler and on-board DMA controller chip.

- MTAN-512K Includes 512K RAM . . \$199.95

## INTRODUCING JAMECO'S NEW COMPUTER KITS!!

Jameco's IBM™ AT Compatible Kit!  
Mini-286 6/8/10/12MHz Kit!



JE1059 \$569.95  
EGA Monitor & Card  
(not included)

Part No.	Description	Price
JE1015	XT/AT Style Keyboard	\$ 59.95
41256-120	512K RAM (18 Chips)	\$ 71.10
JE1012	Baby AT Flip-Top Case	\$ 79.95
JE1032	200W Power Supply	\$ 99.95
JE1022	5 1/4" High Density Disk Drive	\$119.95
JE1045	Hard Disk/Floppy Controller	\$199.95
JE1003	Baby AT Motherboard (Zero-K RAM-incl. Award BIOS ROM)	\$449.95

**NEW! Regular List \$1,080.80  
SAVE \$105.85!**

- JE1008 IBM™ AT Compatible Kit . . . \$974.95  
JE1059 EGA Monitor & Card **SAVE \$30.00** . . \$569.95

### Jameco's IBM PC/XT Compatible Kit

4164-150	128K RAM (18 Chips)	\$20.70
IBM-FCC	Floppy Controller Card	\$34.95
IBM-Case	Flip-Top Case	\$34.95
JE1015	XT/AT Style Keyboard	\$59.95
JE1030	150 Watt Power Supply	\$69.95
JE1050	Mono/Graph. Crd. w/Port	\$69.95
JE1020	5 1/4" DSDD Disk Drive	\$99.95
IBM-MON	12" Mono. Green Monitor	\$99.95
IBM-MB	XT Motherboard (Zero-K RAM-incl. DTK/ERSO BIOS ROM)	\$99.95

**SAVE \$90.35**

**FREE! QUICKSOFT PC  
WRITE WORD PROCESSING  
SOFTWARE INCLUDED!**

Regular List \$590.30

- JE1004 (IBM™ PC/XT Compatible Kit) . . . \$499.95

**Jameco's 4.77/8MHz Turbo IBM Compatible Kit**  
Same as JE1004 except comes with 640K RAM, TURBO 4.77/8MHz motherboard, JE1071 multi I/O with controller and graphics, and AMBER monitor.

**SAVE \$146.50 Regular List \$746.45**

- JE1005 (IBM™ PC/XT Turbo Compatible Kit) . \$599.95

### Additional Add-Ons Available!

RS232HC	RS232 Serial Half Card (PC/XT)	\$ 29.95
EM-100	Expansion Memory Half Card (without RAM) (PC/XT)	\$ 59.95
AMBER	12" Amber Monitor (PC/XT/AT)	\$109.95
PM1200B-2	1200/300Bd Half Card Modem w/out software (PC/XT/AT)	\$119.95
PM1200B-2S	1200/300Bd Half Card Modem w/Mirror Strw (PC/XT/AT)	\$149.95
TTX-1410	14" RGB Color Monitor (PC/XT/AT)	\$289.95

### Color Graphics Card for PC/XT/AT



- Test 40 or 80 x 25 - Graphics 320 or 640 x 200 - Manual included

- JE1052 . . . \$59.95

### EGA Card for PC/XT/AT



- Graphics 720 x 348 - 16 out of 64 colors - Manual included

- JE1055 . . . \$199.95

### I/O Cards for PC/XT/AT



- Printer Port  
- RS232 Port  
- Game Port  
- Manual included

- JE1060 I/O for XT . . . \$69.95  
JE1065 I/O for AT . . . \$69.95

### Multi I/O w/Controller & Graphics for PC/XT



- Printer port - RS232 port - Floppy controller - Graphics - Manual included

- JE1071 . . . \$159.95

## Solderless Breadboard Sockets



JE23



JE27

Part No.	Dim. L x W	Contact Points	Binding Posts	Price
JE20	6 1/2 x 3 1/2	100	0	\$ 2.49
JE21	3 1/4 x 2 1/4	400	0	\$ 4.95
JE22	6 1/2 x 1 1/4	630	0	\$ 6.49
JE23	6 1/2 x 2 1/4	830	0	\$ 7.49
JE24	6 1/2 x 3 1/4	1,360	2	\$13.95
JE25	6 1/2 x 4 1/4	1,660	3	\$24.95
JE26	6 1/2 x 5 3/4	2,390	4	\$29.95
JE27	7 1/4 x 7 1/2	3,220	4	\$39.95

## Jameco ELECTRONICS

### Extended 80-Column Card for Apple IIe



- 80 Col / 64K RAM - Doubles amount of data your Apple IIe can display as well as its memory capacity - Ideal for word processing - Complete with instructions.

- JE864 \$59.95

- ADD-12 (Disk Drive II, II+, IIe) \$99.95

### Additional Apple Compatible Products Available

#### NEW!



**Seagate 20,  
30 & 40MB  
Half Height  
Hard Disk  
Drives**

- ST225 20MB Drive only (PC/XT/AT) \$274.95  
ST225K 20MB w/Controller (PC/XT) \$339.95  
ST238K 30MB w/Cont. (PC/XT/AT) . \$399.95  
ST251XT 40MB w/Cont. Card (PC/XT) . \$599.95  
ST251AT 40MB w/Cont. Card (AT) . . \$659.95



**Jameco PC/XT  
& AT Compatible  
Disk Drives**

- JE1020 (360K Drive, PC/XT/AT) . . \$ 99.95  
JE1022 (1.2MB, AT Compatible) . . \$119.95

### DATA BOOKS

- 30003 National Linear Data Book (82) . . . \$14.95  
30005 Logic Data Book - Vol. II (84) . . . \$14.95  
30009 Intersil Data Book (86) . . . \$ 9.95  
30032 National Linear Supplement (84) . . \$ 6.95  
210830 Intel Memory Handbook (87) . . . \$17.95  
230843 Intel Microsystem Hndbk. Set (87) . . \$24.95

### MUFFIN/SPRITE-STYLE SLOTS



- MUF60 . . . \$9.95  
Torin Industries (4 68" sq., 60 cfm)  
SU2A1 . . . \$8.95  
EG&G Rotron (3 125" square, 20 cfm)

\$20 Minimum Order - U.S. Funds Only  
Shipping: Add 5% plus \$1.50 Insurance

California Residents: Add 6%, 6 1/2% or 7% Sales Tax

Data Sheets - 50¢ each  
Prices Subject to Change

Send \$1.00 Postage for a  
FREE Seasonal Flyer  
FAX 415-592-2503



Send \$1.00 Postage for a  
FREE 1987 CATALOG  
Telex: 176043


©1987 Jameco Electronics

1355 SHOREWAY RD., BELMONT, CA 94002 • FOR ORDERS ONLY 415-592-8097 • ALL OTHER INQUIRIES 415-592-8121

# Radio Shack Parts Place™

## Come in for Your Free '88 Catalog Today!

### Fast "Hotline" Replacement Service

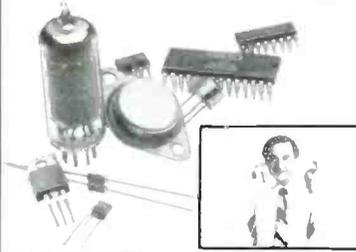

We Can Replace Almost Any IC or Semi—Over 200,000 Substitutions  
No Postage ■ No Minimum

If the part you need is not in our regular stock, we'll check our sub guide and special-order a replacement from the warehouse. Radio Shack also offers this service on selected tubes, crystals and styli.

### Give Your Computer a Voice!



12<sup>95</sup>

Easy to Interface

16<sup>95</sup>

**SPO256-AL2 Speech Synthesizer IC.** This 28-pin device uses a stored program to produce natural-sounding speech. With circuit examples and data. #276-1784 ... 12.95

**CTS256-AL2 Text-to-Speech IC.** Translates ASCII characters into control data for IC at left. Connects to RS-232. With data. 40-pin DIP. #276-1786 ... 16.95

### We're Your Connector Connection


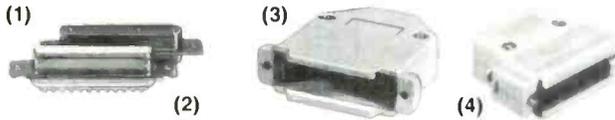


Fig	Type	Pos	Cat No	Only
1	D-Sub Male	25	276-1547	1.99
2	D-Sub Female	25	276-1548	2.99
3	Hood for Above	25	276-1549	1.99

Type	Pos	Cat No	Only
D-Sub Male	9	276-1537	1.49
D-Sub Female	9	276-1538	2.49
Hood for Above	9	276-1539	1.99

(4) **Shielded 25-Position Hood.** Metallized plastic. Preserves EMI/RFI protection when used with shielded cable. #276-1536 ... 1.99

### A Sampling of Solid-State Values

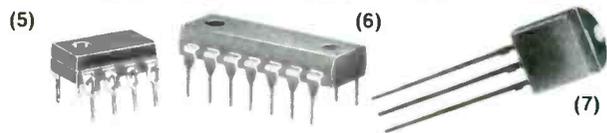

(5) **741 Op-Amp.** #276-007 ... 79c

**1458 Dual Op-Amp.** #276-038 ... 99c

**TLO82 Dual Bifet Op Amp.** #276-1715 ... 1.89

**555 Timer IC.** #276-1723 ... 1.19

(6) **LM324 Quad Op-Amp.** #276-1711 ... 1.29

(7) **2N2222A NPN Transistor.** #276-2009 ... 59c

### Attention-Getters



(8) **Electronic Chime.** Delivers pleasing 80 dB "ding-dong" at 12 VDC. #273-071 ... 7.95

(9) **Blinking Red LED.** Built-in IC driver. #276-036 ... 1.29

**Blinking Green LED.** Use as an alert or in jewelry. #276-030 ... 1.29

### Bargain Bundles



(10) **1/4-Watt Carbon-Film Resistors.** 5% tolerance. Jumbo 500-piece set. #271-312 ... 7.95

**Metal-Film.** 1/4 watt, 1% tolerance. 50 pieces. #271-309 ... 2.79

(11) **Electrolytic Capacitors.** Twenty pieces, assorted values. Up to 50 WVDC. #272-802 ... 1.98

### Low-Cost "Insurance"



(12) **3" Brushless DC Fan.** Lightweight and quiet, yet delivers 27 CFM airflow. Excellent for AC-sensitive circuits. 7 to 13.8 VDC supply. #273-243 ... 14.95

(13) **Heavy-Duty Metal Oxide Varistor.** #276-568 ... 1.99

### Project Finishers




(14) **Project Enclosure.** 1 13/16 x 4 1/8 x 5 1/2". #270-210 ... 3.29

(15) **Instrument Case.** 2 7/8 x 5 5/8 x 5 1/8". #270-250 ... 4.99

(16) **Four-Position Fuse Block.** #270-742 ... 2.19

(17) **Panel-Mount Fuse Holder.** #270-367 ... 1.59

### Switch & Relay Values

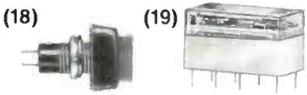

(18) **SPST Push-On/Off.** 3A at 125 VAC. #275-1565 ... 1.59

**Momentary.** #275-1566 ... 1.49

(19) **Submini DPDT Relay.** 12 VDC coil. Contacts rated 1 amp at 125 VAC. #275-213 ... 3.99

**5 VDC-Coil Submini DPDT Relay.** Rated as above. #275-215 ... 3.99

### Capture Solar Energy



**Solar Energy Project Kit.** Complete with solar cell, DC motor, color wheels, propeller and project booklet. #277-1201 ... 9.95

**Silicon Solar Cell.** Manufacturer's prime. 2.5 x 5cm cell. #276-124 ... 3.95

### Audio Amp/Speaker



Terrific as a test-bench or general-purpose amp. Has on/off/volume control, 1/8" phono jacks for input and an external speaker or ear-phone. 200 mW output. Compact—only 3 3/8 x 3 3/16 x 1 3/4". Battery extra. #277-1008


### SW Antenna & Wire



(20) **Complete Shortwave Antenna Kit.** 75 feet of copper antenna wire, 50 feet of lead-in wire, window feedthrough, insulators and instructions. #278-758 ... 8.49

(21) **Heavy-Duty Antenna Wire.** 65 feet. 22-gauge. #278-1329 ... 4.59

### Electronic Tool Kit

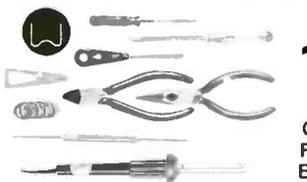

14<sup>95</sup>

Get One For Your Beginner

Ten-piece set has everything necessary to get started—UL listed AC 30-watt soldering iron, stand, solder, soldering aid, needle-nose pliers, diagonal cutter, three screwdrivers and a heat sink. #64-2801

### New! 28-Range FET VOM

49<sup>95</sup>

Works Like A Solid State VTVM

Ten-megohm input sensitivity! Jumbo 5-inch, 3-color scale, beep continuity mode. Measures to 1000 VAC, DC current to 10 amps, resistance to 100 megohms. #22-220



### Dual DC Power Supply

69<sup>95</sup>

Independent Or Slave Operation

Quality and features you wouldn't expect at this low price! Adjustable 0 to 15 volts, up to 30 volts in series mode. Switchable volt/amp meter. Maximum current: 1 amp per channel. Fuse-protected. UL listed AC. #22-121



**Radio Shack®**  
A DIVISION OF TANDY CORPORATION

Prices apply at participating Radio Shack stores and dealers

Over 1000 items in stock: Binding posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multitesters, PC Boards, Plugs, Rectifiers, Relays, Resistors, Switches, Tools, Transformers, Transistors, Wire, Zeners and more!



# 20 MEG HARD DISK DRIVE ON A CARD \$389!

## STATIC RAMS / DYNAMIC RAMS

2101	256x4	(450ns)	1.95
2102L-4	1024x1	(450ns)(LP)	.99
2112	256x4	(450ns)	2.99
2114	1024x4	(450ns)	.99
2114L-4	1024x4	(450ns)(LP)	1.09
2114L-2	1024x4	(200ns)(LP)	1.49
2114L-15	1024x4	(150ns)(LP)	1.95
TMS4044-4	4096x1	(450ns)	1.95
TMM2016-150	2048x8	(150ns)	1.49
TMM2016-100	2048x8	(100ns)	1.95
HM6116-4	2048x8	(200ns)(CMOS)	1.89
HM6116-3	2048x8	(150ns)(CMOS)	1.95
HM6116LP-4	2048x8	(200ns)(CMOS)(LP)	1.95
HM6116LP-3	2048x8	(150ns)(CMOS)(LP)	2.05
HM6116LP-2	2048x8	(120ns)(CMOS)(LP)	2.95
HM6264P-15	8192x8	(150ns)(CMOS)	3.89
HM6264LP-15	8192x8	(150ns)(CMOS)(LP)	3.95
HM6264LP-12	8192x8	(120ns)(CMOS)(LP)	4.49
HM43256LP-15	32768x8	(150ns)(CMOS)(LP)	12.95
HM43256LP-12	32768x8	(120ns)(CMOS)(LP)	14.95
HM43256LP-10	32768x8	(100ns)(CMOS)(LP)	19.95
4116-250	16384x1	(250ns)	.49
4116-200	16384x1	(200ns)	.89
4116-150	16384x1	(150ns)	.99
4116-120	16384x1	(120ns)	1.49
NK4332	32768x1	(200ns)	6.95
4164-150	65536x1	(150ns)(CMOS)(LP)	1.29
4164-120	65536x1	(120ns)	1.95
MCM6665	65536x1	(200ns)	1.95
TMS4164	65536x1	(150ns)	1.95
4164-REFRESH	65536x1	(150ns)(REFRESH)	2.95
TMS4416	16384x4	(150ns)	4.95
41128-150	131072x1	(150ns)	5.95
TMS4464-15	65536x4	(150ns)	6.95
41256-150	262144x1	(150ns)	6.95
41256-100	262144x1	(100ns)	4.95
HM51258-100	262144x1	(100ns)(CMOS)	6.95
1MB-120	1048576x1	(120ns)	19.95
1MB-100	1048576x1	(100ns)	24.95
LP: Low power			
REFRESH: Pin 1 Refresh			

## ★★★★ HIGH-TECH ★★★★★

### NICKEL EXPRESS \$69<sup>95</sup> PC/XT SPEED UP KIT

- INCREASE THE SPEED OF YOUR PC BY 67% OR MORE!
- SIMPLE NO-SLOT INSTALLATION
- SOFTWARE OR HARDWARE SPEED SELECTION
- 8 MHz V20 PROCESSOR & SOFTWARE INCLUDED
- SELECT FOR 3 TURBO FREQUENCIES
- EXTERNAL RESET SWITCH
- OPTIONAL 8088 8 MHz PROCESSOR AVAILABLE

Certain early PCs may not run at 8MHz; these machines may be switched to one of the slower speeds: 6.66 MHz- 40%, 7.37 MHz- 55%, 8.0 MHz- 67%

## ★★★★ SPOTLIGHT ★★★★★

# ORDER TOLL FREE 800-538-5000



## EPROMS

2708	1024x8	(450ns)	4.95
2716	2048x8	(450ns)(5V)	3.49
2716-1	2048x8	(350ns)(5V)	3.95
TMS2532	4096x8	(450ns)(5V)	5.95
2732	4096x8	(450ns)(5V)	3.95
2732A	4096x8	(250ns)(5V)(21V PGM)	3.95
2732A-2	4096x8	(200ns)(5V)(21V PGM)	4.25
27C26A	8192x8	(250ns)(5V)(CMOS)	5.95
2764	8192x8	(450ns)(5V)	3.49
2764-250	8192x8	(250ns)(5V)	3.95
2764-200	8192x8	(200ns)(5V)	4.25
MCM68766	8192x8	(350ns)(5V)(24 PIN)	17.95
27128	16384x8	(250ns)(5V)	4.25
27C256	32768x8	(250ns)(5V)(CMOS)	10.95
27256	32768x8	(250ns)(5V)	7.49
27512	65536x8	(250ns)(5V)	11.95
27C512	65536x8	(250ns)(5V)(CMOS)	12.95
5V: Single 5 Volt Supply			
21V PGM: Program at 21 Volts			

## SPECTRONICS CORPORATION EPROM ERASERS



Model	Timer	Capacity Chip	Intensity (uW/Cm <sup>2</sup> )	Unit Price
PE-14	NO	9	8,000	\$83.00
PE-14T	YES	9	8,000	\$119.00
PE-24T	YES	12	9,600	\$175.00

## 8000

8035	1.49
8039	.95
8052AH BASIC	34.95
8080	2.95
8085	2.49
8087 5 MHz	129.00
8087 2 8 MHz	169.95
8088	6.95
8088-2	9.95
8155	2.49
8748	7.95
8755	14.95
80286	129.95
80287 8 MHz	199.95
80287 8	299.95
80287 10	399.95

## V20 SERIES

V20 5 MHz 8.95  
V20 8 MHz 10.95  
V30 8 MHz 13.95  
\*Replaces 8088 to speed up your PC by 10 to 40%\*

## CRT CONTROLLERS

6845	4.95
68B45	8.95
6847	11.95
HD46505SP	6.95
MC1372	2.95
8275	26.95
7220	19.95
CRT5027	12.95
CRT5037	9.95
TMS9918A	19.95

## 8200

8205	3.29
8212	1.49
8216	1.49
8224	2.25
8237	4.95
8237-5	5.49
8250	6.95
8251	1.69
8251A	1.89
8253	1.89
8253-5	1.95
8255	1.69
8255-5	1.89
8259	1.95
8259-5	2.29
8272	4.95
8279	2.49
8279-5	2.95
8282	3.95
8284	2.95
8286	3.95
8288	3.95

## DISK CONTROLLERS

1771	4.95
1791	9.95
1793	9.95
1795	12.95
1797	12.95
2791	19.95
2793	19.95
2797	29.95
8272	4.95
UPD765	4.95
MB8876	12.95
MB8877	12.95
1691	6.95
2143	6.95
9216	7.95

## Z-80

Z80 CPU	1.69
Z80 CPU	1.79
Z80A CTC	1.89
Z80A DART	5.95
Z80A DMA	5.95
Z80A PIO	1.89
Z80A SIO 0	5.95
Z80A SIO 2	5.95

## BIT RATE GENERATORS

MC14411	9.95
BR1941	4.95
4702	9.95
COM8116	8.95

## 6.0 MHz

Z80B CPU	3.75
Z80B CTC	4.25
Z80B PIO	4.25
Z80B DART	14.95
Z80B SIO 0	12.95
Z80B SIO 2	12.95
Z8671 ZILOG	19.95

## UARTS

AYS-1013	3.95
AY3-1015	4.95
TR1602	3.95
2651	4.95
IM6402	6.95
IM6403	9.95
INS8250	6.95
NS16450	15.95

## 6500

1.0 MHz	
6502	2.69
65C02(CMOS)	12.95
6507	9.95
6520	1.95
6522	4.95
6526	26.95
6532	6.95
6545	6.95
6551	19.95
6561	19.95
6581	34.95

## 2.0 MHz

6502A	2.95
6520A	2.95
6522A	5.95
6532A	11.95
6545A	7.95
6551A	6.95

## 3.0 MHz

6502B	6.95
-------	------

## CRYSTALS

32.768 KHz	95
1.0 MHz	2.95
1.8432	2.95
2.0	1.95
2.097152	1.95
2.4576	1.95
3.2768	1.95
3.579545	1.95
4.0	1.95
4.032	1.95
5.0	1.95
5.0688	1.95
6.0	1.95
6.144	1.95
6.5536	1.95
8.0	1.95
8.0	1.95
10.0	1.95
10.738635	1.95
12.0	1.95
14.31818	1.95
15.0	1.95
15.0	1.95
17.430	1.95
18.0	1.95
18.432	1.95
20.0	1.95
22.1184	1.95
24.0	1.95
32.0	1.95

## CRYSTAL OSCILLATORS

1.0MHz	5.95
1.8432	5.95
2.0	5.95
2.4576	5.95
2.5	4.95
3.2768	4.95
3.5795	4.95
4.0	4.95
4.032	4.95
5.0	4.95
5.0688	4.95
6.0	4.95
6.144	4.95
8.0	4.95
8.0	4.95
10.0	4.95
10.0	4.95
12.0	4.95
12.480	4.95
15.0	4.95
16.0	4.95
18.432	4.95
20.0	4.95
24.0	4.95

## MISC.

MAX232	7.95
TMS99532	19.95
ULN2003	.79
3242	7.95
3341	1.95
MC3470	1.95
MC3480	8.95
MC3487	2.95
11C90	19.95
2513-001	PP 6.95
AYS-2376	11.95
AYS-3600	PP 11.95

## 6800

6800	1.95
6802	4.95
6803	9.95
6809	5.95
6809E	5.95
6810	1.95
6820	2.95
6821	1.95
6840	6.95
6843	19.95
6844	12.95
6845	4.95
6847	11.95
6850	1.95
6883	22.95

## 2.0 MHz

68B00	4.95
68B02	5.95
68B09E	6.95
68B09	6.95
68B21	3.95
68B45	6.95
68B50	2.95
68B54	7.95

## CLOCK CIRCUITS

MM5369	1.95
MM5369-EST	1.95
MM58167	12.95
MM58174	11.95
MSM5832	2.95

## HIGH SPEED CMOS

A new family of high speed CMOS logic featuring the speed of low power Schottky (Bns typical gate propagation delay), combined with the advantages of CMOS: very low power consumption, superior noise immunity, and improved output drive.

74HC00: Operate at CMOS logic levels and are ideal for new, all-CMOS designs.

74HC00	.59	74HC148	1.19
74HC02	.59	74HC151	.89
74HC04	.59	74HC154	2.49
74HC08	.59	74HC157	.89
74HC10	.59	74HC158	.95
74HC14	.79	74HC163	1.15
74HC20	.59	74HC175	.99
74HC27	.59	74HC240	1.89
74HC30	.59	74HC244	1.89
74HC32	.69	74HC245	1.89
74HC51	.59	74HC257	.85
74HC74	.75	74HC259	1.39
74HC85	1.35	74HC273	1.89
74HC86	.69	74HC299	4.99
74HC93	1.19	74HC368	.99
74HC107	.79	74HC373	2.29
74HC109	.79	74HC374	2.29
74HC112	.79	74HC390	1.39
74HC125	1.19	74HC393	1.39
74HC132	1.19	74HC4017	1.99
74HC133	.69	74HC4020	1.39
74HC138	.99	74HC4048	.89
74HC139	.99	74HC4050	.89

74HC700: Direct, drop-in replacements for LS TTL and can be intermixed with 74LS in the same circuit

74HC700	.69	74HC166	3.05
74HC702	.69	74HC174	1.09
74HC704	.69	74HC193	1.39
74HC708	.69	74HC194	1.19
74HC710	.69	74HC240	2.19
74HC711	.69	74HC241	2.19
74HC727	.69	74HC244	2.19
74HC730	.69	74HC245	2.19
74HC732	.79	74HC257	.99
74HC74	.85	74HC259	1.59
74HC775	.95	74HC273	2.09
74HC1138	1.15	74HC367	1.09
74HC1139	1.15	74HC373	2.49
74HC1154	2.99	74HC374	2.49
74HC1157	.99	74HC393	1.59

# EGA CARD AND MONITOR NOW ONLY \$569!

## MONITOR STANDS MODEL MS-100 \$12.95

- TILTS AND SWIVELS
- STURDY ABS PLASTIC CONSTRUCTION

## MODEL MS-200 \$39.95

- TILTS AND SWIVELS
- BUILT-IN POWER STATION
- INDEPENDANTLY CONTROLS UP TO 5 120 VOLT AC OUTLETS
- BUILT-IN SURGE SUPPRESSOR
- UL APPROVED



## CRT MONITORS FOR ALL APPLICATIONS



### CASPER EGA MONITOR

- EGA & CGA COMPATIBLE
- SCANNING FREQUENCIES 15.75 21.85 KHz
- RES 640 x 200 350
- 31mm DOT PITCH 25 MHz
- 16 COLORS OUT OF 64
- 14" BLACK MATRIX SCREEN

**\$399.95**



### CASPER RGB MONITOR

- COLOR GREEN AMBER SWITCH ON REAR
- DIGITAL RGB-IBM COMPATIBLE
- 14" NON-GLARE SCREEN
- RESOLUTION 640x240V
- 39mm DOT PITCH
- CABLE FOR IBM PC INCLUDED

**\$299.95**



### FORTRONICS MONOCHROME

- IBM COMPATIBLE TTL INPUT
- 12" NON-GLARE SCREEN
- VERY HIGH RESOLUTION 1100 LINES (CENTRE)
- 25 MHz BANDWIDTH
- CABLE FOR IBM PC INCLUDED

**\$99.95**

AMBER OR GREEN AVAILABLE

## SOLDER STATION

JDR PART # 168-2C

- FULLY ADJUSTABLE HEAT SETTING WITH TIP TEMPERATURE READOUT
- QUICK HEATING AND RECOVERY
- VARIETY OF REPLACEMENT TIPS ARE AVAILABLE
- RANGE 200°-900°F
- UL APPROVED

**\$4995**



## DISK DRIVES FOR APPLE COMPUTERS

### AP-150

**\$99.95**



- 1/2 HT. DIRECT DRIVE
- 100% APPLE COMPATIBLE
- SIX MONTH WARRANTY

### AP-135

**\$129.95**



- FULL HT SHUGART MECHANISM
- DIRECT REPLACEMENT FOR APPLE DISK II
- SIX MONTH WARRANTY

### AD-3C

**\$139.95**



- 100% APPLE IIc COMPATIBLE, READY TO PLUG IN, W/ SHIELDED CABLE & MOLDED 19 PIN CONNECTOR
- FAST RELIABLE SLIMLINE DIRECT DRIVE
- SIX MONTH WARRANTY

## DISK DRIVE ACCESSORIES

- FDD CONTROLLER CARD \$49.95
  - DISK II ADAPTOR CABLE \$19.95
- ADAPTS STANDARD APPLE DRIVES FOR USE WITH APPLE IIc

## KB-1000

**\$79.95**

CASE WITH KEYBOARD FOR APPLE TYPE MOTHERBOARD

- USER DEFINED FUNCTION KEYS
- NUMERIC KEYPAD W/ CURSOR CONTROL
- CAPS LOCK
- AUTO-REPEAT



## JOYSTICK GC-10

**\$19.95**

- SET X-Y AXIS FOR AUTO CENTER OR FREE MOVEMENT
- FIRE BUTTON FOR USE WITH GAME SOFTWARE
- ATTRACTIVE, SOLID, PLASTIC CASE
- INCLUDES ADAPTOR CABLE FOR IBM, APPLE II, IIc



## APPLE COMPATIBLE INTERFACE CARDS



### EPROM PROGRAMMER

- DUPLICATE OR BURN ANY 27x SERIES EPROM (2716 TO 27128)
- MENU DRIVEN SOFTWARE
- HIGH SPEED WRITE ALGORITHM

RP-525 \$59.95



### 16K RAMCARD

- FULL 2 YEAR WARRANTY
- EXPAND YOUR 48K MACHINE TO A FULL 64K OF MEMORY
- CAN BE USED IN PLACE OF THE APPLE LANGUAGE CARD

RAM-CARD \$39.95



### IC TEST CARD

- QUICKLY TESTS MANY COMMON ICs
- DISPLAYS PASS OR FAIL
- TEST 4000 & 74HC SERIES CMOS, 7400, 74LS, 74L, 74H & 74S

IC-TESTER \$129.95

## MOLDED INTERFACE CABLES

6 FOOT, 100% SHIELDED, MEETS FCC



- IBM PARALLEL PRINTER CABLE 9.95
- CENTRONICS (MALE TO FEMALE) 15.95
- CENTRONICS (MALE TO MALE) 14.95
- MODEM CABLE (FOR IBM) 7.95
- RS232 SERIAL (MALE TO FEMALE) 9.95
- RS232 SERIAL (MALE TO MALE) 9.95
- KEYBOARD EXTENDER (COILED) 7.95
- APPLE II JOYSTICK EXTENDER 4.95

## C. ITOH RITEMAN II PRINTER



- 160 CPS DRAFT, 32 CPS NLO
- 9 x 9 DOT MATRIX
- SUPPORTS EPSON IBM GRAPH CS
- FRICTION AND PIN FEEDS
- VARIABLE LINE SPACING AND PITCH

**\$219.95**

- IBM PRINTER CABLE \$8.95
- REPLACEMENT RIB30M CARTRIDGE \$7.95

## SWITCH BOXES

ALL LINES SWITCHED, GOLD PLATED CONNECTORS, QUALITY SWITCHES

2 WAY \$39.95

- CONNECTS 2 PRINTERS TO COMPUTER OR VICE VERSA

AB-P (CENTRONICS PARALLEL)  
AB-S (RS232 SERIAL)



3 WAY \$99.95

- CONNECTS 3 PRINTERS TO COMPUTER OR VICE VERSA

SWITCH-3P (CENTRONICS PARALLEL)  
SWITCH-3S (RS232 SERIAL)



## POWER STRIP \$9.95

JDR PART # POWER-STRIP

- 15 AMP CIRCUIT BREAKER
- 6 RECEPTACLES
- 6 FOOT POWER CORD
- PILOT SWITCH

## WITH SURGE PROTECTION

JDR PART # MT-660

**\$12.95**

## NASHUA DISKETTES

NASHUA DISKETTES WERE JUDGED TO HAVE THE HIGHEST POLISH AND RECORDED AMPLITUDE OF ANY DISKETTES TESTED (COMPARING FLOPPY DISKS, BYTE 9/84)

- N-MD2D DS DD 5 1/4" SOFT \$9.90
- N-MD2F DS QUAD 5 1/4" SOFT \$19.95
- N-MD2H DS HD 5 1/4" FOR AT \$24.95
- N-FD1 SS DD 8" SOFT \$27.95
- N-FD2D DS DD 8" SOFT \$34.95

## BULK DISKETTE SALE

- 5 1/4" SOFT SECTOR, DS/DD W/TYVEC SLEEVES & HUB RINGS
- \$990** BOX OF 10
- 69c** BULK QTY 50
- 59c** BULK QTY 250

## DISKETTE FILES

- 5 1/4" DISKFILE HOLDS 70 \$8.95
- 3 1/2" DISKFILE HOLDS 40 \$8.95



## 20 MEGABYTE HARD DISK CARD



- SAVES SPACE AND REDUCES POWER CONSUMPTION
- IDEAL FOR PCs WITH FULL HEIGHT FLOPPIES
- LEAVES ROOM FOR A HALF LENGTH CARD IN ADJACENT SLOT

**ONLY \$389**

## Seagate

### 5 1/4" HARD DISK DRIVES

- ST-225 HALF HT 20MB 65ms \$275
- ST-238 HALF HT 30MB 65ms (RL) \$299
- ST-251 HALF HT 40MB 40ms \$599
- ST-277 HALF HT 60MB 40ms (RL) CALL
- ST-4038 FULL HT 30MB 40ms \$559
- ST-4096 FULL HT 80MB 28ms \$1195

### 1/2 HEIGHT FLOPPY DISK DRIVES

- 5 1/4" TEAC FD-55B DS DD \$109.95
- 5 1/4" TEAC FD-55F DS QUAD \$124.95
- 5 1/4" TEAC FD-55GFV DS HD \$154.95
- 5 1/4" MITSUBISHI DS HD \$129.95
- 3 1/2" TOSHIBA KIT DS DD \$149.95

KIT INCLUDES MOUNTING HARDWARE TO FIT 5 1/4" SLOT & FACEPLATES FOR AT & XT

### DISK DRIVE ACCESSORIES

- TEAC SPECIFICATION MANUAL \$5.00
- TEAC MAINTENANCE MANUAL \$25.00
- 1/2 HT MNTG HARDWARE FOR IBM \$2.95
- MOUNTING RAILS FOR IBM AT \$4.95
- 5 1/4" POWER CABLE FOR 5 1/4" FDDs \$2.95
- 5 1/4" FDD POWER CONNECTORS \$1.19

### DISK DRIVE ENCLOSURES WITH POWER SUPPLIES

- CAB-2SV5 DUAL SLIMLINE 5 1/4" \$49.95
- CAB-1FV5 FULL HT 5 1/4" \$69.95
- CAB-2SV8 DUAL SLIMLINE 8" \$209.95
- CAB-2FV8 DUAL FULL HT 8" \$219.95

## BUILD STEVE CIARCIA'S INTELLIGENT EPROM PROGRAMMER

AS SEEN IN BYTE, OCT 86

- STAND ALONE OR RS 232 SERIAL OPERATION
- MENU SELECTABLE EPROM TYPES
- NO CONFIGURATION JUMPERS
- PROGRAMS ALL 5V 27XXX EPROMS FROM 2716 TO 27512
- READ, COPY OR VERIFY EPROM
- UPLOAD/DOWNLOAD INTEL HEX FILES
- PROGRAMMER DRIVER USER MODIFIABLE

Kit includes PCB & all components except case & power supply

**\$199**

CALL FOR VOLUME QUOTES COPYRIGHT 1987 JDR MICRODEVICES

CIRCLE 178 ON FREE INFORMATION CARD

# 20 MEG HARD DISK DRIVE ON A CARD \$389!

## NEW! EVERYTHING-IN-ONE CARD

**MCT-MGMIO \$119.95**

- HERCULES COMPATIBLE MONOCHROME GRAPHICS, 720 x 384 PIXELS
- 1 STANDARD SERIAL PORT INSTALLED, OPTIONAL 2nd PORT AVAILABLE
- 1 PARALLEL PORT AND REAL TIME CLOCK / CALENDAR INCLUDED
- SUPPORTS BOTH DS / DD & DS / DD WHEN USED WITH DOS 3.2 OR JFORMAT



## QUALITY IBM COMPATIBLE MOTHERBOARDS


**TURBO 4.77 / 8 MHz \$129.95**

JDR PART #: MCT-TURBO

- 4.77 OR 8 MHz OPERATION WITH 8088-2 & OPTIONAL 8087-2 CO-PROCESSOR
- DYNAMICALLY ADJUSTS SPEED DURING DISKETTE OPERATION FOR MAXIMUM THROUGHPUT AND RELIABILITY
- CHOICE OF NORMAL / TURBO MODE OR SOFTWARE SELECT PROCESSOR SPEED

**STANDARD MOTHERBOARD \$109.95**

JDR PART #: MCT-XTMB

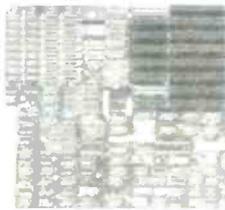

**80286 6 / 8 MHz \$499.00**

JDR PART #: MCT-ATMB

- 8 SLOT (2 EIGHT BIT, 6 SIXTEEN BIT) AT MOTHERBOARD
- HARDWARE SELECTION OF 6 OR 8 MHz
- 1 WAIT STATE
- RESET SWITCH, FRONT PANEL LED INDICATOR AND KEYS LOCK SUPPORTED
- SOCKETS FOR 1 MB OF RAM AND 80287 ON BOARD
- ON BOARD BATTERY BACKED CLOCK OPERATES WITH PC-DOS OR MS-DOS

## 3 1/2" FDD KIT BY TOSHIBA

JDR PART #: FDD-35 KIT

- 720K FORMAT, DOS 3.2 COMPATIBLE
- ALLOWS DATA INTERCHANGE WITH NEW IBM MACHINES
- MOUNTING HARDWARE FOR 5 1/4" SLOT
- FACEPLATES FOR BOTH AT & XT

**\$149.95**

## IBM COMPATIBLE FLOPPY DISK DRIVE

JDR PART #: FDD-360

GOOD QUALITY DRIVES BY MAJOR MANUFACTURERS SUCH AS OUME, TANDON & CDC

- 5 1/4" HALF HEIGHT
- 360K STORAGE CAPACITY
- DS / DD
- 48 TPI

**\$69.95**

## IBM XT STYLE COMPUTER CASE

AN ATTRACTIVE STEEL CASE WITH A HINGED LID. FITS THE POPULAR PC/XT COMPATIBLE MOTHERBOARDS



- SWITCH CUT-OUT ON SIDE FOR PC/XT STYLE POWER SUPPLY
- CUT-OUT FOR 8 EXPANSION SLOTS
- ALL HARDWARE INCLUDED

**\$34.95**

XT STYLE SLIDE TYPE CASE \$39.95

AT STYLE SLIDE TYPE CASE \$89.95

## BUILD YOUR OWN 256K XT COMPATIBLE SYSTEM

- XT MOTHERBOARD \$109.95
- PRO-BIOS (A \$20 VALUE) FREE!
- 256K RAM \$26.95
- 130W POWER SUPPLY \$89.95
- FLIP-TOP CASE \$34.95
- MCT-5150 KEYBOARD \$59.95
- 360K DRIVE \$89.95
- FDD CONTROLLER \$34.95
- MONOGRAPHS CARD \$59.95
- FORTRONICS MONITOR \$99.95

**TOTAL: \$566.15**

## IBM COMPATIBLE KEYBOARDS



**MCT-5060 \$59.95**

- IBM AT STYLE LAYOUT
- SOFTWARE AUTONSENSE FOR XT OR AT COMPATIBLES
- EXTRA LARGE SHIFT & RETURN KEYS
- LED INDICATORS FOR SCROLL, CAPS & NUMBER LOCK
- AUTO REPEAT FEATURE



**MCT-5339 \$89.95**

- IBM ENHANCED STYLE LAYOUT
- SOFTWARE AUTONSENSE FOR XT OR AT COMPATIBLES
- 12 FUNCTION KEYS
- EXTRA LARGE SHIFT & RETURN KEYS
- LED INDICATORS FOR SCROLL, CAPS & NUMBER LOCK
- AUTO REPEAT FEATURE
- SEPARATE CURSOR PAD

**MCT-5150 \$59.95**

XT STYLE LAYOUT

**MCT-5151 \$79.95**

KB5151 - EQUIVALENT

## EASYDATA MODEMS

All models feature auto-dial/answer/redial on busy, Hayes compatible, power up self test, touchtone or pulse dialing, built-in speaker, PC Talk III Communications software, Bell Systems 103 & 212A full or half duplex and more.

### INTERNAL

**EASYDATA-12H \$99.95**

1200 BAUD HALF CARD

**EASYDATA-12B \$119.95**

1200 BAUD 10" CARD

**EASYDATA-24B \$199.95**

2400 BAUD FULL CARD

### EXTERNAL


NO SOFTWARE INCLUDED

**EASYDATA-12D \$119.95**

1200 BAUD

**EASYDATA-24D \$219.95**

2400 BAUD

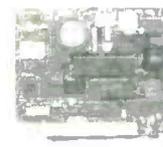

## MCT DISPLAY CARDS

### MCT-EGA

**\$179.95**

100% IBM COMPATIBLE, PASSES IBM EGA DIAGNOSTICS

- COMPATIBLE WITH IBM EGA, COLOR GRAPHICS AND MONOCHROME ADAPTORS
- TRIPLE SCANNING FREQUENCY FOR DISPLAY ON EGA, STANDARD RGB OR HIGH RESOLUTION MONOCHROME MONITOR
- FULL 256K OF VIDEO RAM ALLOWS 640 x 350 PIXELS IN 16 OF 64 COLORS
- LIGHT PEN INTERFACE



### MCT-CG

**\$49.95**

COMPATIBLE WITH IBM COLOR GRAPHICS STANDARD

- SHORT SLOT CARD USES VLSI CHIPS TO INSURE RELIABILITY
- SUPPORTS RGB, COMPOSITE MONOCHROME & COLOR AND AN RF MODULATOR OUTPUT
- 320 x 200 COLOR GRAPHICS MODE
- 640 x 200 MONOCHROME MODE
- LIGHT PEN INTERFACE



### MCT-MGP

**\$59.95**

COMPATIBLE WITH IBM MONOCHROME AND HERCULES GRAPHICS STANDARDS

- SHORT SLOT CARD USES VLSI CHIPS TO INSURE RELIABILITY
- PARALLEL PRINTER PORT, CONFIGURABLE AS LPT1 OR LPT2
- 720 x 348 GRAPHICS MODE
- LOTUS COMPATIBLE
- CAN RUN WITH COLOR GRAPHICS CARD IN THE SAME SYSTEM



## MCT DEVELOPMENT TOOLS


### MCT-PAL

PAL PROGRAMMER

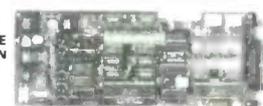**\$269.95**

ONE ARRAY LOGIC CHIP CAN REPLACE 4-5 TTL ICs

- PROGRAMS 20 & 24 PIN PALS FROM TI, NSC & MMI
- EASY TO USE MENU DRIVEN SOFTWARE ALLOWS PROGRAMMING, VERIFICATION, READING, MAP BUILDING & BURNING THE SECURITY FUSE
- READ AND SAVE BURN PROFILES IN JEDEC FORMAT ON YOUR DISK



CUPL STARTER KIT \$49.95

### MCT-MP

MICROPROCESSOR PROGRAMMER

**\$199.95**

PROGRAMS 8741/2/8/9 PROCESSOR CHIPS

- EASY TO USE MENU DRIVEN SOFTWARE SUPPORTS READ, WRITE, BLANK CHECK AND VERIFY OPERATIONS
- PORT ADDRESS SELECTION IS USER CONFIGURABLE
- SAVE AND RESTORE PROGRAM IMAGES ON DISK
- INCLUDES SOFTWARE FOR STANDARD HEX AND INTEL HEX FORMATS




### MCT-EPROM

EPROM PROGRAMMERS

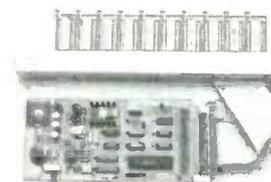**\$129.95**

PROGRAMS 27xx AND 27xxx SERIES EPROMS UP TO 27512

- SUPPORTS VARIOUS MANUFACTURERS FORMATS WITH 12.5, 21 AND 25 VOLT PROGRAMMING
- MENU DRIVEN SOFTWARE ALLOWS EASY MANIPULATION OF DATA FILES
- SPLIT OR COMBINE THE CONTENTS OF SEVERAL EPROMS OF DIFFERENT SIZES
- READ, WRITE, COPY, ERASE CHECK AND VERIFY WITH EASY ONE KEY SELECTION
- INCLUDES SOFTWARE FOR STANDARD HEX AND INTEL HEX FORMATS



4 GANG PROGRAMMER \$189.95

10 GANG PROGRAMMER \$299.95

RADIO-ELECTRONICS

MCT PRODUCTS CARRY A ONE YEAR WARRANTY

COPYRIGHT 1987 JDR MICRODEVICES

**1200B MODEM \$99<sup>95</sup>** FOR IBM W/  
SOFTWARE

**2400B MODEM \$199<sup>95</sup>**

**MULTIFUNCTION CARDS**

FROM MODULAR CIRCUIT TECHNOLOGY

**MCT-MF \$79.95**

ALL THE FEATURES OF AST'S SIX PACK PLUS AT HALF THE PRICE!


- 0 348K DYNAMIC RAM USING 4164s
- INCLUDES SERIAL PORT, PARALLEL PRINTER PORT, GAME CONTROLLER PORT AND CLOCK CALENDAR
- SOFTWARE FOR A RAMDISK, PRINT SPOOLER AND CLOCK CALENDAR



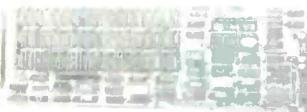**MCT-ATMF \$139.95**

ADDS UP TO 3 MB OF 1 BIT RAM TO THE AT

- USER EXPANDABLE TO 1.5 MB OF ON-BOARD MEMORY (NO MEMORY INSTALLED)
- FLEXIBLE ADDRESS CONFIGURATION
- INCLUDES SERIAL PORT AND PARALLEL PORT
- OPTIONAL PIGGYBACK BOARD PERMITS EXPANSION TO 3 MB



**ATMF-SERIAL 2nd SERIAL PORT \$24<sup>95</sup>**

**MCT-ATMF-MC \$29<sup>95</sup>**

PIGGYBACK BOARD (ZERO K INSTALLED)

**MCT-MIO \$79.95**

A PERFECT COMPANION FOR OUR MOTHERBOARD

- 2 DRIVE FLOPPY DISK CONTROLLER
- INCLUDES SERIAL PORT, PARALLEL PORT, GAME PORT AND CLOCK CALENDAR WITH BATTERY BACK-UP
- SOFTWARE FOR A RAMDISK, PRINT SPOOLER AND CLOCK CALENDAR



**MIO-SERIAL 2nd SERIAL PORT \$15<sup>95</sup>**

**MCT-IO \$59.95**

USE WITH MCT-FH FOR A MINIMUM OF SLOTS USED

- SERIAL PORT ADDRESSABLE AS COM1, COM2, COM3 OR COM4
- PARALLEL PRINTER PORT ADDRESSABLE AS LPT1 OR LPT2 (x378 OR x278)
- CLOCK CALENDAR WITH A BATTERY BACK-UP

**IO-SERIAL 2nd SERIAL PORT \$15<sup>95</sup>**



**MCT-ATIO \$59.95**

USE WITH MCT-ATFH FOR A MINIMUM OF SLOTS USED

- SERIAL PORT ADDRESSABLE AS COM1, COM2, COM3 OR COM4
- PARALLEL PRINTER PORT ADDRESSABLE AS LPTA OR LPTB (x378 OR x278)
- GAME PORT
- USES 16450 SERIAL SUPPORT CHIPS FOR HIGH SPEED OPERATION IN AN AT

**ATIO-SERIAL 2nd SERIAL PORT \$24<sup>95</sup>**



**RAM CARDS**

FROM MODULAR CIRCUIT TECHNOLOGY

**MCT-RAM \$69.95**

A CONTIGUOUS MEMORY SOLUTION FOR YOUR SHORT OR REGULAR SLOT

- SHORT SLOT, LOW POWER PC COMPATIBLE DESIGN
- CAN OFFER UP TO 576K OF ADDITIONAL MEMORY
- USER SELECTABLE CONFIGURATION AMOUNTS OF 192, 384, 512, 256 & 576K, USING COMBINATIONS OF 64 & 256K RAM



**MCT-ATRAM \$149.95**

A POWER USER'S DREAM, 4MB OF MEMORY FOR THE AT

- USER EXPANDABLE TO 2MB OF ON-BOARD MEMORY
- USES FULL 16 BIT PARITY CHECKED MEMORY, 64K OR 256K DYNAMIC RAM
- FLEXIBLE STARTING ADDRESS, ROUND OUT CONVENTIONAL MEMORY TO 640K & ADD EXTENDED MEMORY ABOVE 1MB



**MCT-ATRAM-MC \$39<sup>95</sup>**

2MB PIGGYBACK BOARD (ZERO K INSTALLED)

**MCT-EMS \$129.95**

2MB OF LOTUS/INTEL/MICROSOFT COMPATIBLE MEMORY FOR THE XT

- CONFORMS TO LOTUS/INTEL EMS
- USER EXPANDABLE TO 2 MB
- USES 64K OR 256K DYNAMIC RAM (NO MEMORY INSTALLED)
- USE AS EXPANDED OR CONVENTIONAL MEMORY, RAMDISK OR SPOOLER
- SOFTWARE INCLUDES EMS DEVICE DRIVERS, PRINT SPOOLER AND RAMDISK



**MCT-ATEMS AT VERSION OF THE MCT-EMS \$139<sup>95</sup>**

**Seagate**

**HARD DISK SYSTEMS**  
**20 MB \$339** **30 MB \$399**

Systems include half height hard disk drive, hard disk drive controller, cables and instructions. Drives are pre-tested and warranted for one year.

**Seagate 40 MB AT DRIVE**  
FAST 40ms ACCESS TIME



**\$599**

**DISK CONTROLLER CARDS**

FROM MODULAR CIRCUIT TECHNOLOGY

**MCT-FDC \$34.95**

QUALITY DESIGN OFFERS 4 FLOPPY CONTROL IN A SINGLE SLOT

- INTERFACES UP TO 4 FDSs TO AN IBM PC OR COMPATIBLE
- INCLUDES CABLING FOR 2 INTERNAL DRIVES
- USES STANDARD DB37 CONNECTOR FOR EXTERNAL DRIVES
- SUPPORTS BOTH DS DD AND DS QD WHEN USED W/ DOS 3.2 DR JFORMAT



**MCT-HDC \$89.95**

HARD DISK CONTROL FOR WHAT OTHERS CHARGE FOR FLOPPY CONTROL

- IBM XT COMPATIBLE CONTROLLER SUPPORTS 13 DRIVE SIZES INCLUDING 5, 10, 20, 30 & 40MB
- OPTIONS INCLUDE THE ABILITY TO DIVIDE 1 LARGE DRIVE INTO 2 SMALLER, LOGICAL DRIVES
- INCLUDES CABLING FOR 1 INTERNAL DRIVE



**MCT-RLI \$119.95**

GET UP TO 50% MORE STORAGE SPACE ON YOUR HARD DISK

- INCREASES THE CAPACITY OF PLAYED MEDIA DRIVES BY 50%
- RLL 27 ENCODING FOR MORE RELIABLE STORAGE
- TRANSFER RATE IS ALSO 50% FASTER: 750K sec vs 500K sec
- USE WITH ST-238 DRIVE TO AC-HIEVE 30 MB IN A HALF HEIGHT SLOT



**NEW!**

**MCT-FH \$139.95**

STARVED FOR SLOTS? SATISFY IT WITH THIS TIMELY DESIGN

- INTERFACES UP TO 2 FDSs & 2 HDDs
- CABLING FOR 2 FDSs & 1 HDD
- FLOPPY INTERFACE SUPPORTS BOTH DS DD & DS QD WHEN USED WITH DOS 3.2 OR JFORMAT
- ALL POPULAR HDD SIZES ARE SUPPORTED, INCLUDING 5, 10, 20, 30 & 40MB
- CAN DIVIDE 1 LARGE DRIVE INTO 2 SMALLER, LOGICAL DRIVES



**MCT-ATFH \$169.95**

FLOPPY AND HARD DISK CONTROL IN A TRUE AT DESIGN

- AT COMPATIBLE, CONTROL UP TO 2 360K 720K OR 1.2MB FDSs AS WELL AS 2 HDDs USING THE AT STANDARD CONTROL TABLES
- SUPPORTS AT STYLE FRONT PANEL LED TO INDICATE HD ACTIVITY
- 16 BIT BUSS PROVIDES RAPID DATA TRANSFERS
- FULLY SUPPORTED BY AT BIOS



**JDR Microdevices** 110 Knowles Drive, Los Gatos, CA 95030  
Toll Free 800-538-5000 • (408) 866-6200 • FAX (408) 378-8927 • Telex 171-110

THE JDR MICRODEVICES LOGO IS A REGISTERED TRADEMARK OF JDR MICRODEVICES. JDR INSTRUMENTS AND JDR MICRODEVICES ARE TRADEMARKS OF JDR MICRODEVICES. IBM IS A TRADEMARK OF INTERNATIONAL BUSINESS MACHINES CORPORATION

CIRCLE 180 ON FREE INFORMATION CARD

COPYRIGHT 1987 JDR MICRODEV CES

SEPTEMBER 1987

109

**1200B MODEM \$99.95**

FOR IBM W/  
SOFTWARE

**2400B MODEM \$199.95**

**BARGAIN HUNTERS CORNER**

**300 BAUD MODEM FOR IBM**  
INCLUDES ASCII PRO-EZ SOFTWARE  
**NOW ONLY \$29.95**

**720K FLOPPY DISK DRIVE**

BY MITSUBISHI

- ★ 5 1/4" HALF HEIGHT
- ★ 96 TPI
- ★ 100% IBM COMPATIBLE
- ★ DOUBLE SIDED/QUAD DENSITY

**ONLY \$99.95**

SPECIAL ENDS 8/31/87

**PAGE WIRE WRAP WIRE**  
PRECUT ASSORTMENT  
IN ASSORTED COLORS \$27.50

100ea: 5.5", 6.0", 6.5", 7.0"  
250ea: 2.5", 4.5", 5.0"  
500ea: 3.0", 1.5", 4.0"

**SPOOLS**

100 feet \$4.30 250 feet \$7.25  
500 feet \$13.25 1300 feet \$21.95

Please specify color:  
Blue, Black, Yellow or Red

**WIRE WRAP PROTOTYPE CARDS**  
FR-4 EPOXY GLASS LAMINATE  
WITH GOLD-PLATED EDGE-CARD FINGERS



**XT**

BOTH CARDS HAVE SILK SCREENED LEGENDS  
AND INCLUDES MOUNTING BRACKET

IBM-PR1 WITH .5V AND GROUND PLANE \$27.95  
IBM-PR2 AS ABOVE W/ DECODING LAYOUT \$29.95

**AT**

IBM-PRAT LARGE .5V & GROUND PLANES \$29.95

**S-100**

P100-1 BARE - NO FOIL PADS \$15.15  
P100-2 HORIZONTAL BUS \$21.80  
P100-3 VERTICAL BUS \$21.80  
P100-4 SINGLE FOIL PADS PER HOLE \$22.75

**APPLE**


P500-1 BARE - NO FOIL PADS \$15.15  
P500-3 HORIZONTAL BUS \$22.75  
P500-4 SINGLE FOIL PADS PER HOLE \$21.80  
7060-45 FOR APPLE IIe AUX SLOT \$30.00

**SOCKET-WRAP I.D.™**

- SLIPS OVER WIRE WRAP PINS
- IDENTIFIES PIN NUMBERS ON WRAP SIDE OF BOARD
- CAN WRITE ON PLASTIC, SUCH AS IC #

PINS	PART #	PCK. OF	PRICE
8	IDWRAP 08	10	1.95
14	IDWRAP 14	10	1.95
16	IDWRAP 16	10	1.95
18	IDWRAP 18	5	1.95
20	IDWRAP 20	5	1.95
22	IDWRAP 22	5	1.95
24	IDWRAP 24	5	1.95
28	IDWRAP 28	5	1.95
40	IDWRAP 40	5	1.95

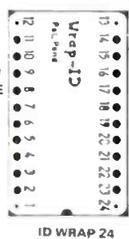PLEASE ORDER BY NUMBER OF PACKAGES (PCK. OF)



**FRAME STYLE TRANSFORMERS**

12.6V AC CT	2 AMP	5.95
12.6V AC CT	4 AMP	7.95
12.6V AC CT	8 AMP	10.95
25.2V AC CT	2 AMP	7.95

**25 PIN D-SUB GENDER CHANGERS**

\$7.95



**SWITCHING POWER SUPPLIES**

**PS-IBM \$69.95**

- FOR IBM PC-XT COMPATIBLE
- 135 WATTS
- -5V @ 15A, -12V @ 4.2A
- -5V @ .5A, -12V @ 5A
- ONE YEAR WARRANTY

PS-IBM 150



**PS-IBM-150 \$79.95**

- FOR IBM PC-XT COMPATIBLE
- 150 WATTS
- -12V @ 5.2A, -5V @ 16A
- -12V @ 5A, -5V @ 5A
- ONE YEAR WARRANTY



**PS-AT \$89.95**

- FOR IBM PC-AT COMPATIBLE
- 220 WATTS
- -5V @ 22A, -12V @ 8A
- -5V @ .5A, -12V @ 5A
- 1 YEAR WARRANTY

PS-AT



**PS-A \$49.95**

- USE TO POWER APPLE TYPE SYSTEMS, 79.5 WATTS
- -5V @ 7A, -12V @ 3A
- -5V @ .5A, -12V @ 5A
- APPLE POWER CONNECTOR

PS-A



**PS-1558 \$34.95**

- 75 WATTS, UL APPROVED
- -5V @ 7A, -12V @ 3A
- -12V @ 250ma, -5V @ 300ma

PS-1558



**CAPACITORS**

**TANTALUM**

1.0µf	15V	.35	47µf	35V	.45
6.8	15V	.70	1.0	35V	.45
10	15V	.80	2.2	35V	.65
22	15V	1.35	4.7	35V	.85
.22	35V	.40	10	35V	1.00

**DISC**

10µf	50V	.05	680	50V	.05
22	50V	.05	001µf	50V	.05
27	50V	.05	0022	50V	.05
33	50V	.05	005	50V	.05
47	50V	.05	01	50V	.07
68	50V	.05	02	50V	.07
100	50V	.05	.05	50V	.07
220	50V	.05	.1	12V	.10
560	50V	.05	.1	50V	.12

**MONOLITHIC**

.01µf	50V	.14	1µf	50V	.18
.047µf	50V	.15	47µf	50V	.25

**ELECTROLYTIC**

RADIAL		AXIAL			
1µf	25V	.14	1µf	50V	.14
2.2	35V	.15	10	50V	.16
4.7	50V	.15	22	16V	.14
10	50V	.15	47	50V	.20
47	35V	.18	100	35V	.25
100	16V	.18	220	25V	.30
220	35V	.20	470	50V	.50
470	25V	.30	1000	16V	.60
2200	16V	.70	2200	16V	.70
4700	25V	1.45	4700	16V	1.25

**DATARASE EPROM ERASER \$34.95**

- ERASES 2 IN 10 MINUTES
- COMPACT-NO DRAWER
- THIN METAL SHUTTER PREVENTS UV LIGHT FROM ESCAPING



**1/4 WATT RESISTORS**

5% CARBON FILM ALL STANDARD VALUES FROM 1 OHM TO 10 MEG. OHM

10 PCS same value .05 100 PCS same value .02  
50 PCS same value .025 1000 PCS same value .015

**RESISTOR NETWORKS**

SIP	10 PIN	9 RESISTOR	.69
SIP	8 PIN	7 RESISTOR	.59
DIP	16 PIN	8 RESISTOR	1.09
DIP	16 PIN	15 RESISTOR	1.09
DIP	14 PIN	7 RESISTOR	.99
DIP	14 PIN	13 RESISTOR	.99

**SPECIALS ON BYPASS CAPACITORS**

.01 µf CERAMIC DISC	100/ \$5.00
.01 µf MONOLITHIC	100/ \$10.00
.1 µf CERAMIC DISC	100/ \$6.50
.1 µf MONOLITHIC	100/ \$12.50

**WISH SOLDERLESS BREADBOARDS**

PART NUMBER	DIMENSIONS	DISTRIBUTION STRIP(S)	TIE POINTS	TERMINAL STRIP(S)	TIE POINTS	BINDING POSTS	PRICE
WBU-D	.38 x 6.50"	1	100				2.95
WBU-T	1.38 x 6.50"			1	630		6.95
WBU-204-3	3.94 x 8.45"	1	100	2	1260	2	17.95
WBU-204	5.13 x 8.45"			4	400	2	24.95
WBU-206	6.88 x 9.06"			5	500	3	29.95
WBU-208	8.25 x 9.45"			7	700	4	39.95



**LITHIUM BATTERY AS USED IN CLOCK CIRCUITS**

3 VOLT BATTERY \$3.95  
BATTERY HOLDER \$1.49



**MUFFIN FANS**

3.15" SQ 14.95 3.63" SQ 14.95  
3.18" SQUARE 16.95

**6' LINE CORDS**


2 conductor .39 3 conductor .99  
3 conductor w/ female socket 1.49

**EMI FILTER \$4.95**

**2 VOLUME SET IC MASTER**  
THE INDUSTRY STANDARD  
**\$129.95**

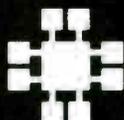**NEW STORE HOURS! M-F: 9-7, SAT: 9-5 & SUN: 12-4**

Visit our retail store located at 1256 S. Bascom Ave. in San Jose, (408) 947-8881



**JDR Microdevices**

110 Knowles Drive, Los Gatos, CA 95030

Toll Free 800-538-5000 • (408) 866-6200

FAX (408) 378-8927 • Telex 171-110

COPYRIGHT 1987 JDR MICRODEVICES

THE JDR MICRODEVICES LOGO IS A REGISTERED TRADEMARK OF JDR MICRODEVICES. JDR INSTRUMENTS AND JDR MICRODEVICES ARE TRADEMARKS OF JDR MICRODEVICES. IBM IS A TRADEMARK OF INTERNATIONAL BUSINESS MACHINES CORPORATION. APPLE IS A TRADEMARK OF APPLE COMPUTER.

TERMS Minimum order \$10.00. For shipping and handling include \$2.50 for UPS Ground and \$3.50 for UPS Air. Orders over 1 lb. and foreign orders may require additional shipping charges—please contact our sales department for the amount. CA residents must include applicable sales tax. All merchandise is warranted for 90 days unless otherwise stated. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sale. A full copy of our terms is available upon request.


# PUT US TO THE TEST!



**AF Signal Generator**  
\$139  
Q-1310

Square/Sine wave output audio signal generator, essential for work on huge range of circuits. With wide 10Hz - 1MHz attun. output and sync.output, it is the perfect partner for the above RF generator.

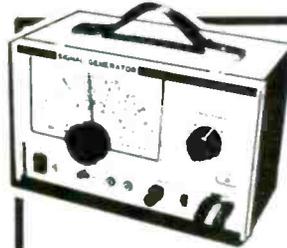**SPECIFICATIONS:**  
Frequency Range: 10Hz - 1MHz  
Accuracy: +/-3 +2Hz  
Output Impedance: 600 ohms unbalanced  
Output Control: 0, -20dB, -40dB and Fine Adjuster  
Sine Wave Output: 10Hz - 1MHz 8V RMS (max)  
Square Wave Output: 10Hz - 10KHz, 10Vp-p (max), 5ma rise time  
Synch: +/-3% of oscillator frequency per V RMS



**Wideband RF Signal Generator**  
\$139  
Q-1312

Now a low cost RF signal generator that's great for checking and aligning IF circuits and tuners in AM, FM, and TV sets plus a huge range of general purpose service, troubleshooting and development work.

**SPECIFICATIONS:**  
Frequency Range: 100kHz to 150MHz in six overlapping ranges.  
Accuracy: +/-3%  
RF Output: 100mV rms approx. (up to 35MHz)  
Modulation: 1kHz internal, 50Hz - 20kHz external  
Audio Output: 1kHz at 1V rms (fixed)  
Crystal Oscillator: 1-15MHz external crystal, HC-6/u holder  
Supply Voltage: 110V

## FET Input Multimeter


This 10MΩ Input impedance FET multimeter is just the tool for quick measurements & reliable service. A high impact shock resistant case, tilt stand, power on LED, and comes with 1 x 9V & 2 x "AA" batteries. The meter scale is mirrored for accuracy and measures 4 1/2".



DC Volts 0-0.3, 1.2, 12, 30, 120, 300, 1200V  
RMS and peak to peak  
AC Volts: 0-0.3, 12, 30, 120, 1200V  
DC Current: 0-0.1uA, 0.3, 3, 30, 300mA, 12A  
AC Current: 0-12A  
Resistance: 0-1000MΩ, 6 ranges

\$79<sup>95</sup>  
Q-1143

## Rack Mount Cabinets

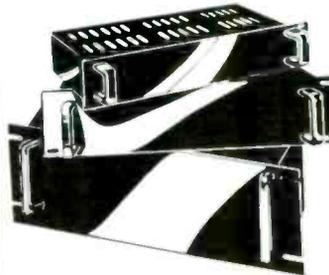

Now in three sizes, these professional quality black instrument cases of aluminum & steel fit standard 19" racks. Heavy gauge (1/8") front panel, ventilated top & bottom panels. Supplied flat, assembles in minutes.

**Slim**  
16 1/2" x 9 1/2" x 1 1/2" 5lbs. 10.5oz. Cat H-2483 \$24<sup>95</sup>  
**Medium**  
16 1/2" x 9 1/2" x 3 1/4" 7lbs. 8oz. Cat H-2482 \$27<sup>50</sup>  
**Large**  
16 1/2" x 9 1/2" x 5 1/2" 9lbs. 5oz. Cat H-2481 \$29<sup>95</sup>



## Zip Rack To Suit 19" Cabinets

The industry standard 19" rack, used by engineers, designers & scientists for years is now available at an affordable price. We carry three sizes of the 19" wide cabinets to fit the 19" rack.

\$49<sup>95</sup>

**Panels To Suit** H-2470  
\$39<sup>95</sup> Custom fit flush mount aluminum top & side panels.  
H-2471

## L Rack To Suit 19" Cabinet

L-shaped 8 section rack constructed of our 3/32 in. angle iron welded at L joint for maximum strength has a rear crossbar for rigidity.

\$17<sup>95</sup>  
H-2468



**Order by Phone**  
**415-368-1066**

Mon - Fri 7a.m. - 6p.m. Pacific Time

**14-Day Satisfaction Guarantee**

**MAIL ORDERS**

DSE, P.O. Box 8021, Redwood City, CA 94063

HEAD OFFICE: 390 Convention Way, Redwood City, CA 94063

We ship UPS Ground unless otherwise requested. Add 5% of order total minimum \$1.50 for shipping. Outside USA add 20% (min \$4). There is an additional \$1.50 handling fee. California residents please add sales tax. VISA and MASTERCARD welcome. Minimum order value \$20.00

**DICK SMITH ELECTRONICS**

To receive your copy of our 148 page catalog circle Reader Service 176

**VLSI**  
**NATIONAL SEMICONDUCTOR • PANASONIC**  
**OR MACHINE • EWC, INC. • INTERSIL**  
**EAC, INC. • J. W. MILLER • AAVD ENGINEER**  
**E. F. JOHNSON • ATLANTIC SEMICONDUCTOR**

**256K (262,144 x 1) DRAM 150NS \$5.70/1; \$39.95/9**  
**Factory Firsts**

**MODES • DIAMOND TOOL • UNGAR •**  
**OR INDUSTRIES • MADE IN U.S.A.**  
**IGAR • YAGED • J. W. MILLER • LUKO**  
**SCHEMICALS • ARIES • PLESSEY**

### INTEGRATED CIRCUITS

#### 7400 TTL

7400	7401	7402	7403	7404	7405	7406	7407	7408	7409
7410	7411	7412	7413	7414	7415	7416	7417	7418	7419
7420	7421	7422	7423	7424	7425	7426	7427	7428	7429
7430	7431	7432	7433	7434	7435	7436	7437	7438	7439
7440	7441	7442	7443	7444	7445	7446	7447	7448	7449
7450	7451	7452	7453	7454	7455	7456	7457	7458	7459
7460	7461	7462	7463	7464	7465	7466	7467	7468	7469
7470	7471	7472	7473	7474	7475	7476	7477	7478	7479
7480	7481	7482	7483	7484	7485	7486	7487	7488	7489
7490	7491	7492	7493	7494	7495	7496	7497	7498	7499

### INTEGRATED CIRCUITS

#### 4000 CMOS

4000	4001	4002	4003	4004	4005	4006	4007	4008	4009
4010	4011	4012	4013	4014	4015	4016	4017	4018	4019
4020	4021	4022	4023	4024	4025	4026	4027	4028	4029
4030	4031	4032	4033	4034	4035	4036	4037	4038	4039
4040	4041	4042	4043	4044	4045	4046	4047	4048	4049
4050	4051	4052	4053	4054	4055	4056	4057	4058	4059
4060	4061	4062	4063	4064	4065	4066	4067	4068	4069
4070	4071	4072	4073	4074	4075	4076	4077	4078	4079
4080	4081	4082	4083	4084	4085	4086	4087	4088	4089
4090	4091	4092	4093	4094	4095	4096	4097	4098	4099

### T1 I.C. SOCKETS

#### SOLDER TAIL DIP SOCKETS

• Single base  
 • Low profile  
 • YOUR CHOICE: TIN OR GOLD\*

\*Minimum 100 units each price per 1000

Part No.	Description	100	1000	10000
TS10	8 pin socket tail	1.15	1.45	1.20
TS11	16 pin socket tail	1.75	1.95	1.35
TS12	24 pin socket tail	2.15	2.25	1.45
TS13	32 pin socket tail	2.55	2.55	1.55
TS14	40 pin socket tail	2.95	2.95	1.65
TS15	48 pin socket tail	3.35	3.35	1.75
TS16	56 pin socket tail	3.75	3.75	1.85
TS17	64 pin socket tail	4.15	4.15	1.95
TS18	72 pin socket tail	4.55	4.55	2.05
TS19	80 pin socket tail	4.95	4.95	2.15
TS20	88 pin socket tail	5.35	5.35	2.25

### 1% Carbon Film Resistors

Available in 1/4 Watt

Part No.	Value	100	1000	10000
R101	100 Ohm	1.15	1.45	1.20
R102	150 Ohm	1.15	1.45	1.20
R103	200 Ohm	1.15	1.45	1.20
R104	300 Ohm	1.15	1.45	1.20
R105	400 Ohm	1.15	1.45	1.20
R106	500 Ohm	1.15	1.45	1.20
R107	600 Ohm	1.15	1.45	1.20
R108	700 Ohm	1.15	1.45	1.20
R109	800 Ohm	1.15	1.45	1.20
R110	900 Ohm	1.15	1.45	1.20

### DISC CAPACITORS

Part No.	Value	100	1000	10000
DC101	100 pF	1.15	1.45	1.20
DC102	150 pF	1.15	1.45	1.20
DC103	200 pF	1.15	1.45	1.20
DC104	300 pF	1.15	1.45	1.20
DC105	400 pF	1.15	1.45	1.20
DC106	500 pF	1.15	1.45	1.20
DC107	600 pF	1.15	1.45	1.20
DC108	700 pF	1.15	1.45	1.20
DC109	800 pF	1.15	1.45	1.20
DC110	900 pF	1.15	1.45	1.20

### TANTALUM CAPACITORS

Part No.	Value	100	1000	10000
TA101	1000 pF	1.15	1.45	1.20
TA102	1500 pF	1.15	1.45	1.20
TA103	2000 pF	1.15	1.45	1.20
TA104	3000 pF	1.15	1.45	1.20
TA105	4000 pF	1.15	1.45	1.20
TA106	5000 pF	1.15	1.45	1.20
TA107	6000 pF	1.15	1.45	1.20
TA108	7000 pF	1.15	1.45	1.20
TA109	8000 pF	1.15	1.45	1.20
TA110	9000 pF	1.15	1.45	1.20

### INTEGRATED CIRCUITS

#### 74500 TTL

74500	74501	74502	74503	74504	74505	74506	74507	74508	74509
74510	74511	74512	74513	74514	74515	74516	74517	74518	74519
74520	74521	74522	74523	74524	74525	74526	74527	74528	74529
74530	74531	74532	74533	74534	74535	74536	74537	74538	74539
74540	74541	74542	74543	74544	74545	74546	74547	74548	74549
74550	74551	74552	74553	74554	74555	74556	74557	74558	74559
74560	74561	74562	74563	74564	74565	74566	74567	74568	74569
74570	74571	74572	74573	74574	74575	74576	74577	74578	74579
74580	74581	74582	74583	74584	74585	74586	74587	74588	74589
74590	74591	74592	74593	74594	74595	74596	74597	74598	74599

### 74HC00 CMOS

74HC00	74HC01	74HC02	74HC03	74HC04	74HC05	74HC06	74HC07	74HC08	74HC09
74HC10	74HC11	74HC12	74HC13	74HC14	74HC15	74HC16	74HC17	74HC18	74HC19
74HC20	74HC21	74HC22	74HC23	74HC24	74HC25	74HC26	74HC27	74HC28	74HC29
74HC30	74HC31	74HC32	74HC33	74HC34	74HC35	74HC36	74HC37	74HC38	74HC39
74HC40	74HC41	74HC42	74HC43	74HC44	74HC45	74HC46	74HC47	74HC48	74HC49
74HC50	74HC51	74HC52	74HC53	74HC54	74HC55	74HC56	74HC57	74HC58	74HC59
74HC60	74HC61	74HC62	74HC63	74HC64	74HC65	74HC66	74HC67	74HC68	74HC69
74HC70	74HC71	74HC72	74HC73	74HC74	74HC75	74HC76	74HC77	74HC78	74HC79
74HC80	74HC81	74HC82	74HC83	74HC84	74HC85	74HC86	74HC87	74HC88	74HC89
74HC90	74HC91	74HC92	74HC93	74HC94	74HC95	74HC96	74HC97	74HC98	74HC99

### WIRE WRAP DIP SOCKETS

• Standard profile  
 • Universal mounting and packaging capabilities  
 • Contact is commutated  
 • 91% through 2.0 mm

Part No.	Description	100	1000	10000
WS10	8 pin wire wrap	1.15	1.45	1.20
WS11	16 pin wire wrap	1.75	1.95	1.35
WS12	24 pin wire wrap	2.15	2.25	1.45
WS13	32 pin wire wrap	2.55	2.55	1.55
WS14	40 pin wire wrap	2.95	2.95	1.65
WS15	48 pin wire wrap	3.35	3.35	1.75
WS16	56 pin wire wrap	3.75	3.75	1.85
WS17	64 pin wire wrap	4.15	4.15	1.95
WS18	72 pin wire wrap	4.55	4.55	2.05
WS19	80 pin wire wrap	4.95	4.95	2.15
WS20	88 pin wire wrap	5.35	5.35	2.25

### 1% Metal Film Resistors

Available in 1/4 Watt

Part No.	Value	100	1000	10000
MF101	100 Ohm	1.15	1.45	1.20
MF102	150 Ohm	1.15	1.45	1.20
MF103	200 Ohm	1.15	1.45	1.20
MF104	300 Ohm	1.15	1.45	1.20
MF105	400 Ohm	1.15	1.45	1.20
MF106	500 Ohm	1.15	1.45	1.20
MF107	600 Ohm	1.15	1.45	1.20
MF108	700 Ohm	1.15	1.45	1.20
MF109	800 Ohm	1.15	1.45	1.20
MF110	900 Ohm	1.15	1.45	1.20

### DISC CAPACITORS

Part No.	Value	100	1000	10000
DC201	100 pF	1.15	1.45	1.20
DC202	150 pF	1.15	1.45	1.20
DC203	200 pF	1.15	1.45	1.20
DC204	300 pF	1.15	1.45	1.20
DC205	400 pF	1.15	1.45	1.20
DC206	500 pF	1.15	1.45	1.20
DC207	600 pF	1.15	1.45	1.20
DC208	700 pF	1.15	1.45	1.20
DC209	800 pF	1.15	1.45	1.20
DC210	900 pF	1.15	1.45	1.20

### TANTALUM CAPACITORS

Part No.	Value	100	1000	10000
TA201	1000 pF	1.15	1.45	1.20
TA202	1500 pF	1.15	1.45	1.20
TA203	2000 pF	1.15	1.45	1.20
TA204	3000 pF	1.15	1.45	1.20
TA205	4000 pF	1.15	1.45	1.20
TA206	5000 pF	1.15	1.45	1.20
TA207	6000 pF	1.15	1.45	1.20
TA208	7000 pF	1.15	1.45	1.20
TA209	8000 pF	1.15	1.45	1.20
TA210	9000 pF	1.15	1.45	1.20

### INTEGRATED CIRCUITS

#### 74LS00 TTL

74LS00	74LS01	74LS02	74LS03	74LS04	74LS05	74LS06	74LS07	74LS08	74LS09
74LS10	74LS11	74LS12	74LS13	74LS14	74LS15	74LS16	74LS17	74LS18	74LS19
74LS20	74LS21	74LS22	74LS23	74LS24	74LS25	74LS26	74LS27	74LS28	74LS29
74LS30	74LS31	74LS32	74LS33	74LS34	74LS35	74LS36	74LS37	74LS38	74LS39
74LS40	74LS41	74LS42	74LS43	74LS44	74LS45	74LS46	74LS47	74LS48	74LS49
74LS50	74LS51	74LS52	74LS53	74LS54	74LS55	74LS56	74LS57	74LS58	74LS59
74LS60	74LS61	74LS62	74LS63	74LS64	74LS65	74LS66	74LS67	74LS68	74LS69
74LS70	74LS71	74LS72	74LS73	74LS74	74LS75	74LS76	74LS77	74LS78	74LS79
74LS80	74LS81	74LS82	74LS83	74LS84	74LS85	74LS86	74LS87	74LS88	74LS89
74LS90	74LS91	74LS92	74LS93	74LS94	74LS95	74LS96	74LS97	74LS98	74LS99

### 4116 200 nec. 14, 3M41 D Ram

Part No.	Description	100	1000	10000
4116	200 nec. 14, 3M41 D Ram	1.15	1.45	1.20

### NEC Memory Chips

Part No.	Description	100	1000	10000
2610	1Kbit SRAM	1.15	1.45	1.20
2611	2Kbit SRAM	1.15	1.45	1.20
2612	4Kbit SRAM	1.15	1.45	1.20
2613	8Kbit SRAM	1.15	1.45	1.20
2614	16Kbit SRAM	1.15	1.45	1.20
2615	32Kbit SRAM	1.15	1.45	1.20
2616	64Kbit SRAM	1.15	1.45	1.20
2617	128Kbit SRAM	1.15	1.45	1.20
2618	256Kbit SRAM	1.15	1.45	1.20
2619	512Kbit SRAM	1.15	1.45	1.20
2620	1Mbit SRAM	1.15	1.45	1.20

### 1% Metal Film Resistors

Available in 1/4 Watt

Part No.	Value	100	1000	10000
MF201	100 Ohm	1.15	1.45	1.20
MF202	150 Ohm	1.15	1.45	1.20
MF203	200 Ohm	1.15	1.45	1.20
MF204	300 Ohm	1.15	1.45	1.20
MF205	400 Ohm	1.15	1.45	1.20
MF206	500 Ohm	1.15	1.45	1.20
MF207	600 Ohm	1.15	1.45	1.20
MF208	700 Ohm	1.15	1.45	1.20
MF209	800 Ohm			

★ QUALITY PARTS ★ DISCOUNT PRICES ★ FAST SHIPPING!

# ALL ELECTRONICS CORP.

## ALL ELECTRONICS CORP.

SEND FOR  
**FREE**  
1987 CATALOG...  
**48 PAGES!**

### SPRING LEVER TERMINALS

Two color coded terminals on a sturdy 2 3/4" x 3 3/4" bakelite plate. Great for speaker enclosures or power supplies.  
**75¢ EACH 10 for \$6.00**



### LIGHT ACTIVATED MOTION SENSOR



This device contains a photo cell which senses sudden changes in ambient light. When an object or person passes within its field of view (about 5') it beeps for several seconds then resets. Could be used as a door annunciator or modified to trigger other devices. 5 1/2" x 4" x 1. Operates on 6 Vdc. Requires 4 AA batteries (not included).  
**CAT# LSMD \$5.75 per unit**

### SOUND EFFECTS BOARD

PC board with 2 1/4" speaker, 2 LEDs, IC, battery snap, other components 2 3/8" x 3". When switch is pushed board beeps and leds light. Operates on 9v battery (not included).  
Experimenter's delight\*  
**CAT# ST-3 \$1.25 ea.**




### MICRO-CASSETTE MECHANISM

Micro-cassette tape transport for standard MC60 or MC45 micro-cassettes 3 Vdc operation. Contains: drive motor, belt, head, capstan, pinch wheel and other components. 3 1/2" X 2 1/4" X 5/8".  
**CAT# MCMC \$3.00 each 10 for \$27.50**


 
### FUSES

**3AG (AGC) SIZE**  
1 1/4 2 2 1/2 3 4 5 6 AMP  
**GMA SIZE**  
1 2 3 4 5 AMP  
5 of any ONE amperage 75¢



### COMMODORE PRINTER PLOTTER

Commodore Model # 1520  
4 inch paper  
Four color X-Y plotter. Standard VIC serial interface allows easy connection to Commodore 64 computers. Up to 80 characters per line.  
**CAT# COM-1520 \$49.95 each**  
**EXTRA pen sets \$1.50 per set.**



### EDGE CONNECTORS

ALL ARE .156" SPACING.

**22 EDGE CONNECTOR \$1.25 ea**  
solder lug style 10 for \$11.00  
**22/44 EDGE CONNECTOR \$2.00 ea**  
PC style 10 for \$18.00  
**22/44 EDGE CONNECTOR \$2.50 each**  
solder lug style  
**28/56 EDGE CONNECTOR \$2.50 ea**  
PC style  
**36/72 EDGE CONNECTOR \$3.00 each**  
PC style  
**43/86 EDGE CONNECTOR \$4.50 each**  
PC style



### 2K 10 TURN

MULTI-TURN POT  
SPECTROL  
#MOD 534-7161  
**\$5.00 EACH**



### RELAYS

**10 AMP SOLID STATE**  
CONTROL 3 32 vdc  
LOAD 140 vac 10 amp  
SIZE 2 1/2" x 1 1/2" x 1/2"  
**\$9.50 EACH 10 FOR \$90.00**



### ULTRA-MINIATURE 5 VDC RELAY

Fujitsu # FBR211NED005M20  
COIL 120 ohms  
CONTACTS 1 amp  
Mounts in 14 pin DIP socket  
**\$1.25 each 10 for \$10.00**



### MINIATURE 6 VDC RELAY

Aromat # RSD-6V  
Super Small S.P.D.T. relay  
Mounts in 14 pin DIP socket  
contacts rated 1 amp @ 30 vdc. Highly sensitive. TTL direct drive possible. 120 ohm coil.  
Operate from 4.3 - 6 vdc.  
COIL 120 ohms **\$1.50 each**  
1 1/4" x 1 1/2" x 7/16" **10 for \$13.50**



### 13 VDC RELAY

CONTACTS - S.P.N.C  
10 amp @ 120 vac  
Energize coil to open contact  
COIL 13 vdc 650 ohms  
**SPECIAL PRICE \$1.00 each**



### 4PDT RELAY

14 pin KH style  
3 amp contacts  
USED but fully tested **\$1.70 each**  
Specify coil voltage desired  
Either 24 vdc or 120 vac  
**LARGE QUANTITIES AVAILABLE**  
**SOCKETS FOR KH RELAY 75¢ each**



### PHOTO-FLASH CAPACITORS

170 MFD 330 Volt  
**CAT# PPC-170 75¢ each**  
400 MFD 330 Volt  
**CAT# PPC-400 \$1.00 ea**



### MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

**S.P.D.T. (on-on)**  
PC style non-threaded bushing  
**75¢ each 10 for \$7.00**



**S.P.D.T. (on-on)**  
Solder lug terminals  
**\$1.00 each 10 for \$9.00 100 for \$80.00**



**S.P.D.T. (on-off-on)**  
Solder lug terminals  
**\$1.00 each 10 for \$9.00 100 for \$80.00**



**S.P.D.T. (on-off-on)**  
PC style non-threaded bushing  
**75¢ each 10 for \$7.00**



**S.P.D.T. (on-on)**  
PC lugs threaded bushing  
**\$1.00 each 10 for \$9.00 100 for \$80.00**



**D.P.D.T. (on-on)**  
Solder lug terminals  
**\$2.00 each 10 for \$19.00 100 for \$180.00**



### COMPUTER GRADE CAPACITORS

**1,400 mfd 200 Vdc**  
3" x 2" dia. **\$2.00**  
**6,400 mfd 60 Vdc**  
4 1/4" x 1 3/8" dia. **\$2.50**  
**7,500 mfd 200 Vdc**  
5 3/4" x 3" dia. **\$4.00**  
**12,000 mfd 40 Vdc**  
4 1/4" x 2" dia. **\$2.50**  
**22,000 mfd 25 Vdc**  
4 3/4" x 2" dia. **\$2.50**  
**48,000 mfd 10 Vdc**  
3" x 2 1/2" dia. **\$2.50**  
**66,000 mfd 15 Vdc**  
3 3/4" x 3" dia. **\$3.50**  
**72,000 mfd 15 Vdc**  
4" x 2" dia. **\$3.50**  
**100,000 mfd 10 Vdc**  
6" x 2 1/2" dia. **\$1.00**

### SP.S.T. TOGGLE SWITCH

CARLING (on-off) RATED: 10 amp @ 125 Vac. All plastic body and toggle.  
**CAT# STS-1 \$1.00 ea.**  
10 for \$8.50  
100 for \$7.50  
**LARGE QUANTITIES**



### LED'S STANDARD JUMBO DIFFUSED T 1-3/4

RED 100 for \$1.50  
10 for \$13.00  
GREEN 100 for \$2.00  
10 for \$17.00  
YELLOW 10 for \$2.00  
100 for \$17.00



### FLASHER LED

5 volt operation red jumbo T 1 1/4 size  
**CAT# LED-4 \$1.00**



### NEW GREEN FLASHER

**CAT# LED-AG \$1.00**  
**BI-POLAR jumbo T 1 1/4 size 2 for \$1.70**



### LED HOLDERS

Two piece holder for jumbo LED  
10 for 85¢ **100 for \$5.00**



### CLEAR CLIPLITE LED HOLDER

Make LED a fancy indicator. Clear  
4 for \$1.00




### D.P.S.T. LIGHTED ROCKER SWITCH

115 vac lighted rocker snap mounts in 1/2" x 1 1/2" hole  
Orange lens 16 amp contact  
**\$1.50**



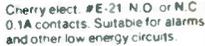
### MINI-PUSH BUTTON

S.P.S.T. momentary normally open 1/4" bushing  
Red button **35¢ each 10 for \$3.00**


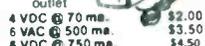
### SNAP ACTION SWITCH

Cherry elect #E-21 N.O. or N.C. 0.1A contacts. Suitable for alarms and other low energy circuits.  
1 1/2" lever.  
**45¢ EACH 10 FOR \$4.20**



### WALL TRANSFORMERS

all plug directly into 120 vac outlet

4 VDC @ 70 ma. **\$2.00**  
6 VDC @ 500 ma. **\$3.50**  
6 VDC @ 750 ma. **\$4.50**  
9 VDC @ 500 ma. **\$5.00**  
12.5 VDC @ 285 ma. **\$3.00**  
18 VDC @ 18 VA and 1.8 VA **\$3.50**  
24 VDC @ 250 ma. **\$3.00**  
MULTI-VOLTAGE @ 500 ma. 3, 4, 5, 6, 7, 8, 9 or 12 VDC **\$7.50**



### TRANSISTORS

2N706 4 for \$1.00  
2N2222A 3 for \$1.00  
PN2222A 4 for \$1.00  
2N2004 3 for \$1.00  
2N2905 3 for \$1.00  
M2955 1 \$1.00  
2N3055 1 \$1.00  
PMO 10K40 1 \$1.00  
TIP 121 75¢  
TIP 125 75¢



## WE'VE MOVED

Our Mail Order Operations to serve U better

**NEW MAILING ADDRESS**  
P.O. BOX 567  
VAN NUYS, CA 91408



### 3rd TAIL LIGHT ?

Sleek high-tech lamp assembly. Could be used as a third auto tail light, emergency warning light, or special-effects lamp. Red reflective lens is 2 3/4" x 5 1/2" is mounted on a 4" high pedestal with up-down swivel adjustment. Includes 12v replaceable bulb.  
**CAT# TLB \$3.95 each.**



### 48 KEY ASSEMBLY FOR COMPUTER OR HOBBYIST

NEW T.I. KEYBOARDS Originally used on computers, these keyboards contain 48 S.P.S.T. mechanical switches. Terminates to 15 pin connector. Frame 4" x 9"  
**CAT# KP-48 \$3.50 each**



NEW T.I. KEYBOARDS Originally used on computers, these keyboards contain 48 S.P.S.T. mechanical switches. Terminates to 15 pin connector. Frame 4" x 9"  
**CAT# KP-48 \$3.50 each**



### SOUND AND VIDEO MODULATOR

T.I.UMI 381-1 Designed for use with T.I. computers. Can be used with video cameras, games or other audio/video sources. Built in A/B switch enables user to switch from T.V. antenna without disconnection. Channel 3 or 4 selection. Operates on 12 Vdc. Hook-up diagram included.  
**CAT# AVMOD \$5.00 each.**



### RECHARGEABLE NI-CAD BATTERIES

AAA SIZE 1.25V **\$1.85**  
AA SIZE 1.25V 500mAh **\$1.85**  
AA with solder tab **\$2.00**  
C SIZE 1.2V 1200mAh **\$3.50**  
SUB-C SIZE solder tab **\$3.50**  
D SIZE 1.2V 1200mAh **\$3.50**



### NI-CAD CHARGER TESTER

Will charge most every size Ni-cad battery available.  
**Cat# UMCC-N \$12.50**




### 8" 15 WATT SPEAKER

C.T.S Model 8B3079 Full range speaker. 100-10,000Hz. Ideal for PA systems. Mounting holes for line-matching transformer.  
**CAT# SK-815 \$3.50 ea.** Case of 8 pcs. **\$25.00 per case**


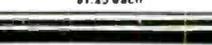
### TELEPHONE COUPLING TRANSFORMER

Slancer # TTPC-8  
600 ohms c.t. to 600 ohms c.t.  
P.C. board mount 3/4" x 5/8" x 3/4"  
**\$1.25 each**



### POLARITY SWITCH

external coaxial relay on a satellite TV system. IDEAL FOR THE EXPERIMENTER AS PARTS Heavy chassis box containing a CA 358 op amp and other parts. Catalog # RDPS  
**\$1.75 each 10 for \$15.00**



### SOLID STATE BUZZER

Star # SMB-06L 6 vdc TTL compatible  
**\$1.00 each 10 for \$9.00**



**STORES**  
LOS ANGELES, CA  
905 S. Vermont Ave.  
213 380-8000  
VAN NUYS, CA  
6228 Sepulveda Blvd.  
818 997-1806



**MAIL ORDERS TO:**  
**ALL ELECTRONICS**  
P.O. BOX 567  
91408  
TWX - 101010163  
**ALL ELECTRONIC**

**QUANTITIES LIMITED**  
MINIMUM ORDERS \$10.00  
CALIF. ADD SALES TAX  
USA: \$3.00 SHIPPING  
NO C.O.D.I.  
FOREIGN ORDERS:  
INCLUDE SUFFICIENT  
SHIPPING

**TOLL FREE ORDERS**  
**800-826-5432**  
INFO • (213) 380-8000  
FAX • (213) 389-7073

# ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page		
		—	McGraw Hill Book Club 36
		—	McGraw Hill Cont. Ed. Series 49
81, 211	A.I.S. Satellite 90	61	Microprocessors Unltd. 75
108	AMC Sales 89	214	Monitronics 90
107	All Electronics 113	117	Mouser 32
103	Allen W.B. 2-	—	NRI 18
—	Amazing Devices 114	182	NTS 91
199	American Design Components 105	71	Mew-Tone Electronics 40
202	Annapro 75	183	Nohau 92
84	Appliance Service 90	210	NuScope Associates 75
206	B N F Enterprises 106	110	Omnitron 35
77	B&K Precision 3	205	PC Boards 92
191	Banner Technical Books 34	—	Pacific Cable 97
98	Beckman Industrial 17	208	Parts Express 96
85	Blue Star Industries 91	204	Pro Corp. 75
109	C & S Sales 23	78	Radio Shack 104
—	C.O.M.B. 26	187, 188	Sencore 27, 29
60	CIE 8	189, 190	Sencore 31, 33
184	Caig Laboratories 22	186	Silicon Valley Surplus 114
89	Cameo Enterprises 91	92, 207	Tektronix CV2, 16
—	Caribbean 88	213	United Imports 90
195	Chapman Tools 90	66	W.S. Jenks 22
200, 201	Circuit Cellar 90, 91	216	Wahl Clipper 28
—	Command Productions 34		
203	Consumertronics 75		
209	Cook's Institute 89		
198	Crystek 30		
127	Deco Industries 90, 91		
176	Dick Smith Electronics 111		
82	Digi-Key 112		
215	E-Z Hook 12		
—	Electronic Technology Today CV3		
194	Electronic Parts 91		
—	Electronics Book Club 57		
120	Elephant Electronics 91		
111	Etronix 93		
100	Firestik II 32		
—	Fordham Radio CV4		
—	Grantham College of Engineering 7		
62	Hameg 13		
193	Heath 14, 15		
196, 197	ICS Computer Training 32, 93		
—	ISCET 93		
65	J & W 25		
59	JDR Instruments 5		
113, 178	JDR Microdevices 106, 107		
179, 180	JDR Microdevices 108, 109		
181	JDR Microdevices 110		
114	Jameco 102, 103		
115	Jensen Tools 91		
185	Lil' Bitty Tester 92		
87	MCM Electronics 101		
212	MID Electronics 91		
93	Mark V. Electronics 98		

**Gernsback Publications, Inc.**  
 500-B Bi-County Blvd.  
 Farmingdale, NY 11735  
 (516) 293-3000  
 President: Larry Steckler  
 Vice President: Cathy Steckler

**For Advertising ONLY**  
 516-293-3000  
**Larry Steckler**  
 publisher  
**Arline Fishman**  
 advertising director  
**Shelli Weinman**  
 advertising associate  
**Lisa Strassman**  
 credit manager  
**Christina Estrada**  
 advertising assistant

**SALES OFFICES**  
**EAST/SOUTHEAST**  
**Stanley Levitan**  
 Eastern Sales Manager  
 Radio-Electronics  
 259-23 57th Avenue  
 Little Neck, NY 11362  
 718-428-6037, 516-293-3000

**MIDWEST/Texas/Arkansas/Okla.**  
**Ralph Bergen**  
 Midwest Sales Manager  
 Radio-Electronics  
 540 Frontage Road—Suite 339  
 Northfield, IL 60093  
 312-446-1444

**PACIFIC COAST/ Mountain States**  
**Marvin Green**  
 Pacific Sales Manager  
 Radio-Electronics  
 15335 Morrison St.—Suite 227  
 Sherman Oaks, CA 91403  
 818-986-2001

## AMAZING SCIENTIFIC & ELECTRONIC PRODUCTS

**PLANS—Build Yourself—All Parts Available In Stock**

- LC7—BURNING CUTTING CO<sub>2</sub> LASER \$ 20.00
- RUBA—PORTABLE LASER RAY PISTOL 20.00
- TCC1—3 SEPARATE TESLA COIL PLANS TO 1.5 MEV 20.00
- ICG1—10M RAY GUN 10.00
- GRA1—GRAVITY GENERATOR 10.00
- EML1—ELECTRO MAGNET COIL GUN/LAUNCHER 6.00

**KITS**

- MFT1K—FM VOICE TRANSMITTER 3 MI RANGE 49.50
- VWPMSK—TELEPHONE TRANSMITTER 3 MI RANGE 39.50
- BTC3K—250.00 VOLT 10-14" SPARK TESLA COIL 199.50
- LHC2K—SIMULATED MULTICOLOR LASER 39.50
- BLS1K—100.000 WATT BLASTER DEFENSE DEVICE 69.50
- ITM1K—100.000 VOLT 20" AFFECTIVE RANGE INTIMIDATOR 69.50
- PSPAK—TIME VARIANT SHOCK WAVE PISTOL 59.50
- PGT1K—SPECTACULAR PLASMA TORNAO GENERATOR 149.50
- MVP1K—SEE IN DARK KIT 169.50

**ASSEMBLED**

- PG70H—MULTICOLORED VARIABLE MODE PLASMA GLOBE "7" 425.00
- BTC10—50,000 VOLT—WORLD'S SMALLEST TESLA COIL 44.50
- LGU40—1MW HeNe VISIBLE RED LASER GUN 299.50
- TAT20 AUTO TELEPHONE RECORDING DEVICE 24.50
- GPV10—SEE IN TOTAL DARKNESS IR VIEWER 299.50
- LIST10—SNOOPER PHONE INFINITY TRANSMITTER 169.50
- IPG70—INVISBLE PAIN FIELD GENERATOR—MULTI MODE 74.50

\* CATALOG CONTAINING DESCRIPTIONS OF ABOVE PLUS HUNDREDS MORE AVAILABLE FOR \$1.00 OR INCLUDED FREE WITH ALL ABOVE ORDERS

PLEASE INCLUDE \$3.00 PH ON ALL KITS AND PRODUCTS PLANS ARE POSTAGE PAID SEND CHECK, MO, VISA, MC IN US FUNDS

**INFORMATION UNLIMITED**  
 P.O. BOX 716 DEPT. RE, AMHERST, NH 03031

## MACINTOSH NOTEBOOKS

PRENTICE HALL BOOKS BY JOHN HEILBORN

### BUY ALL 3 AND GET 1 FREE

8 1/2 BY 11" WELL ILLUSTRATED BOOKS WITH EASY TO READ TYPE EACH IS OVER 200 PAGES AND IS FILLED WITH HINTS, AND SHORTCUTS KNOWN ONLY TO PROGRAM DESIGNERS

**MacPaint** I HAVE USED MacPaint FOR TWO YEARS AND THIS BOOK TAUGHT ME SOME NEW TRICKS

**MacWrite** THIS BOOK CAN CUT YOUR TIME BY 20% WHILE IMPROVING THE APPEARANCE OF YOUR WORK

**MultiPlan** ALL THE HINTS AND SHORTCUTS THE OWNER'S MANUAL LET OUT ARE IN THIS BOOK

**MSDOS 3 BOOK SET 15<sup>99</sup> SET**  
 BY MICRO SOFT

- USERS GUIDE
- DEBUG UTILITY
- PROGRAMMERS REFERENCE

BUY THIS 3 BOOK SET AND LEARN "DOS" AT HOME

**FLOPPY DISK CONTROLLER**  
 IBM COMPATIBLE WITH PRINTER PORT

CONTROLS 2 DRIVES. THE PRINTER PORT IS A DB 25 CENTRONICS AT LPT1 MADE BY TANDON PART NUMBER 188400 **18<sup>99</sup>**

**ROBOTICS PARTS**

**ARM ASSEMBLY \$299<sup>00</sup>**

- ARM MOVES IN 3 DIRECTIONS
- WRIST ROTATES 200 DEGREES
- GRIPS ITEMS UP TO 2 INCHES
- CENTRONICS INTERFACE

**P.W.M. SERVO AMP \$49<sup>00</sup>**

- CONTROLS 6 MOTORS
- CENTRONICS INTERFACE

**MOTORIZED PLATFORM \$99<sup>00</sup>**

- STRONG STEEL CHASSIS
- 2 MOTORS AND WHEELS

Call for a copy of 15 day trial agreement. Tax & freight extra. Send check or add 1.90 for COD. Price may change. Store price may differ. While supplies last. No POs, terms, or credit cards \$5 min postage and handling charge.

**Silicon Valley Surplus** OPEN 10am-6pm  
 415-261-4506 CLOSED SUN & MON  
 4401 OAKPORT OAKLAND CA 94601

**CALL OUR BBS 415-261-4513**

CIRCLE 186 ON FREE INFORMATION CARD

# FOR FREE INFORMATION USE THESE POST-PAID CARDS

- 1 Print your name, address and Zip Code on one of the attached postage-paid cards.
- 2 Circle the number (or numbers) on the card that matches the number at the bottom of each ad or editorial item that you want information on. Advertisers' free information numbers also appear in the ad index on the facing page.
- 3 Mail the card. It's Postage-Paid.

The bottom free-information card is a BUSINESS/PROFESSIONAL CARD. If you use this card you MUST complete the spaces for Company Name, Title, and Phone Number. If these are not filled in, the card will not be processed.

**NOTE:**  
Use the postcard address for Free Product Information only. Address all editorial inquiries to Editor, Radio-Electronics, 500-B Bi-County Blvd., Farmingdale, NY 11735



**Radio Electronics**  
Your favorite electronics magazine and still getting better

## BUSINESS/PROFESSIONAL FREE INFO CARD

Use this card if information requested is for business use. You must fill in company name and phone number.



4-987

Name (please print) \_\_\_\_\_ Title \_\_\_\_\_  
 Company \_\_\_\_\_  
 Dept./MS \_\_\_\_\_  
 Daytime Business Phone \_\_\_\_\_  
 Company Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip+4 \_\_\_\_\_

- Unclear or incomplete mailing info will prevent our processing this request.
- 2  Please send me 12 issues of RADIO-ELECTRONICS for \$16.97 and bill me. (Canada \$22.97 - US Funds only)
- 4  Please send me 12 issues of HANDS-ON ELECTRONICS for \$18.95 and bill me. (Canada \$23.95 - US Funds only)

19 37 55 73 91 109 127 145 163 181 199 217 235 253 271  
 20 38 56 74 92 110 128 146 164 182 200 218 236 254 272  
 21 39 57 75 93 111 129 147 165 183 201 219 237 255 273  
 22 40 58 76 94 112 130 148 166 184 202 220 238 256 274  
 23 41 59 77 95 113 131 149 167 185 203 221 239 257 275  
 24 42 60 78 96 114 132 150 168 186 204 222 240 258 276  
 25 43 61 79 97 115 133 151 169 187 205 223 241 259 277  
 26 44 62 80 98 116 134 152 170 188 206 224 242 260 278  
 9 27 45 63 81 99 117 135 153 171 189 207 225 243 261 279  
 10 28 46 64 82 100 118 136 154 172 190 208 226 244 262 280  
 11 29 47 65 83 101 119 137 155 173 191 209 227 245 263 281  
 12 30 48 66 84 102 120 138 156 174 192 210 228 246 264 282  
 13 31 49 67 85 103 121 139 157 175 193 211 229 247 265 283  
 14 32 50 68 86 104 122 140 158 176 194 212 230 248 266 284  
 15 33 51 69 87 105 123 141 159 177 195 213 231 249 267 285  
 16 34 52 70 88 106 124 142 160 178 196 214 232 250 268 286  
 17 35 53 71 89 107 125 143 161 179 197 215 233 251 269 287  
 18 36 54 72 90 108 126 144 162 180 198 216 234 252 270 288

## FREE INFORMATION CARD

VOID after NOVEMBER 30, 1987  
 Allow 6-8 weeks for delivery of first issue

## POSTAGE-PAID FREE INFORMATION CARD



3-987

Name (please print) \_\_\_\_\_  
 Company Name (if applicable) \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip + 4 \_\_\_\_\_

- Unclear or incomplete mailing info will prevent our processing this request.
- 2  Please send me 12 issues of RADIO-ELECTRONICS for \$16.97 and bill me. (Canada \$22.97 - US Funds only)
- 4  Please send me 12 issues of HANDS-ON ELECTRONICS for \$18.95 and bill me. (Canada \$23.95 - US Funds only)
- Is this your personal copy of RADIO-ELECTRONICS?  
 6  Yes 8  No

19 37 55 73 91 109 127 145 163 181 199 217 235 253 271  
 20 38 56 74 92 110 128 146 164 182 200 218 236 254 272  
 21 39 57 75 93 111 129 147 165 183 201 219 237 255 273  
 22 40 58 76 94 112 130 148 166 184 202 220 238 256 274  
 23 41 59 77 95 113 131 149 167 185 203 221 239 257 275  
 24 42 60 78 96 114 132 150 168 186 204 222 240 258 276  
 25 43 61 79 97 115 133 151 169 187 205 223 241 259 277  
 26 44 62 80 98 116 134 152 170 188 206 224 242 260 278  
 9 27 45 63 81 99 117 135 153 171 189 207 225 243 261 279  
 10 28 46 64 82 100 118 136 154 172 190 208 226 244 262 280  
 11 29 47 65 83 101 119 137 155 173 191 209 227 245 263 281  
 12 30 48 66 84 102 120 138 156 174 192 210 228 246 264 282  
 13 31 49 67 85 103 121 139 157 175 193 211 229 247 265 283  
 14 32 50 68 86 104 122 140 158 176 194 212 230 248 266 284  
 15 33 51 69 87 105 123 141 159 177 195 213 231 249 267 285  
 16 34 52 70 88 106 124 142 160 178 196 214 232 250 268 286  
 17 35 53 71 89 107 125 143 161 179 197 215 233 251 269 287  
 18 36 54 72 90 108 126 144 162 180 198 216 234 252 270 288

## FREE INFORMATION CARD


VOID after NOVEMBER 30, 1987  
 Allow 6-8 weeks for delivery of first issue

## BUSINESS REPLY MAIL

FIRST CLASS PERMIT NC 597 BOULDER, COLORADO

**Radio Electronics**  
 SUBSCRIPTION SERVICE  
 P.O. Box 51866  
 BOULDER, COLORADO 80321-1866

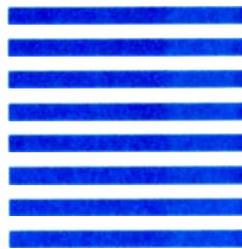NO POSTAGE NECESSARY IF MAILED IN THE UNITED STATES






NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

**BUSINESS REPLY MAIL**  
FIRST CLASS PERMIT NO. 132 DALTON, MA

POSTAGE WILL BE PAID BY ADDRESSEE

**Radio-  
Electronics**

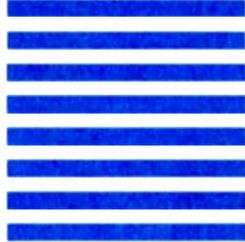FREE PRODUCT INFORMATION  
P.O. Box 388  
DALTON, MA 01226-9990



**For New  
Ideas  
In Electronics  
read Radio-  
Electronics  
every month.**

**During the next  
12 months**

Radio-Electronics will carry up to the minute articles on:

- Computers • Video
- Solid-state technology
- Outstanding construction projects
- Satellite TV • Telephones
- Radio • Stereo • Equipment Reports
- Test equipment • VCR's
- Servicing
- Industrial electronics

**Radio-  
Electronics**

4SJ76

Subscribe today to the magazine that keeps you up-to-date with the newest ideas and innovations in electronics. (If you already are a subscriber, do a friend a favor and pass this subscription card along to him.)

**check offer preferred**

- 1 Year—12 issues **ONLY \$16.97**       2 Years (**SAVE MORE**)—24 issues \$32.97  
 (You save \$10.03 off single copy price)      (You save \$21.03 off single copy price)
- Canada—12 issues \$22.97       Canada—24 issues \$44.97

ALL SUBSCRIPTIONS PAYABLE IN U.S. FUNDS ONLY

- Payment enclosed       Bill Me       Check here if you are extending or renewing your subscription

Name (Please Print) \_\_\_\_\_

Company Name (If applicable) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Allow 6-8 weeks for delivery of first issue



**NEW IDEAS AND INNOVATIONS  
IN ELECTRONICS APPEAR IN EVERY  
ISSUE OF RADIO-ELECTRONICS**

**KEEP UP TO DATE! DON'T MISS  
ANY ISSUES!**

**SUBSCRIBE TODAY!**

**USE THE ORDER CARD ON YOUR  
LEFT!**

**Hands-on  
Electronics**

Formerly Special Projects

Delivers construction article after construction article....Exciting columns including Jensen on DXing, Freidman on computers, Test bench tips, Noll with Calling All Hams, New Products and more.



**SUBSCRIBE TODAY!**

**USE THE REPLY CARDS ON YOUR  
LEFT!**




NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

**BUSINESS REPLY MAIL**  
FIRST CLASS PERMIT NO. 132 DALTON, MA

POSTAGE WILL BE PAID BY ADDRESSEE


**Radio-  
Electronics**

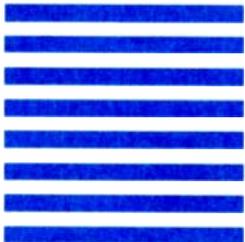FREE PRODUCT INFORMATION  
P.O. Box 388  
DALTON, MA 01226-9990





# Electronics Paperback Books

EVERY BOOK IN THIS AD \$6 OR LESS!

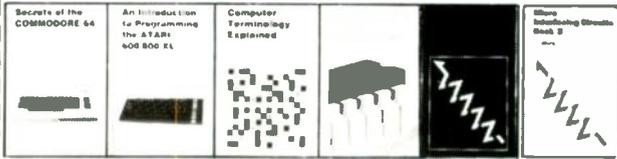

- BP125—25 SIMPLE AMATEUR BAND ANTENNAS.....\$5.00.** All are inexpensive to build, yet perform well. Diodes, beams, triangle and even a mini rhombic
- BP128—20 PROGRAMS FOR THE ZX SPECTRUM AND 16K ZX82.....\$5.75.** Included with each program is a flow chart and a description of what happens. Notes for converting programs for use on other computers are also included
- 160—COIL DESIGN & CONSTRUCTION MANUAL.....\$5.95.** How the hobbyist can build RF, IF, audio and power coils, chokes and transformers. Covers AM, FM and TV applications
- 208—PRACTICAL STEREO & QUADROPHONY HANDBOOK.....\$3.00.** A reference book for all interested in stereo and multichannel sound reproduction
- BP99—MINI-MATRIX BOARD PROJECTS.....\$5.00.** Here are 20 useful circuits that can be built on a mini-matrix board that is just 24 holes by ten copper-foil strips.
- BP157—HOW TO WRITE ZX SPECTRUM AND SPECTRUM+ GAMES PROGRAMS.....\$5.95.** A crystal-clear step-by-step guide to writing your own graphics games programs
- BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 1.....\$5.75.** Oscillators, Timers, Noise Generators, Rectifiers, Comparators, Triggers and more.
- 219—SOLID-STATE NOVELTY PROJECTS.....\$4.95.** Fun projects include the Optomin, a musical instrument that is played by reflecting a light beam with your hand, and many more.
- BP179—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS..... \$5.00.** Data and circuits for interfacing the computer to the robot's motors and sensors.
- BP126—BASIC & PASCAL IN PARALLEL.....\$4.95.** Takes these two programming languages and develops programs in both languages simultaneously.
- 224—50 CMOS IC PROJECTS.....\$5.25.** Includes sections on multivibrators, amplifiers and oscillators, trigger devices, and special devices
- 225—A PRACTICAL INTRODUCTION TO DIGITAL IC'S.....\$4.95.** Mainly concerned with TTL devices. Includes several simple projects plus a logic circuit test set and a digital counter timer
- BP170—INTRODUCTION TO COMPUTER PERIPHERALS.....\$5.95.** Shows how to use a variety of co computer add-ons in as non-technical a way as possible.
- 227—BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS.....\$5.00.** How to tackle the practical side of electronics so you can successfully build electronic projects.
- BP169—HOW TO GET YOUR COMPUTER PROGRAMS RUNNING.....\$5.95.** Shows how to identify error in program and what to do about them.
- 123—FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS.....\$3.75.** Projects include audio distortion meter, super FET receiver, guitar amplifier, metronome and more
- BP24—52 PROJECTS USING IC 741.....\$5.25.** Lots of projects built around this one available IC
- BP110—HOW TO GET YOUR ELECTRONIC PROJECTS WORKING.....\$5.00.** How to find and solve the common problems that can occur when building projects.

- BP33—ELECTRONIC CALCULATOR USERS HANDBOOK.....\$5.75.** Invaluable book for all calculator owners. Tells how to get the most out of your calculator
- BP36—50 CIRCUITS USING GERMANIUM, SILICON & ZENER DIODES.....\$5.00.** A collection of useful circuits you'll want in your library.
- BP37—50 PROJECTS USING RELAYS, SCR'S & TRIACS.....\$5.00.** Build priority indicators, light modulators, warning devices, light dimmers and more
- BP183—AN INTRODUCTION TO CP/M.....\$5.75.** To run and use programs operating under the CP/M operating system you will find this book extremely useful.
- BP42—SIMPLE LED CIRCUITS.....\$5.60.** A large selection of simple applications for this simple electronic component.
- BP127—HOW TO DESIGN ELECTRONIC PROJECTS.....\$5.75.** Helps the reader to put projects together from standard circuit blocks with a minimum of trial and error.
- BP122—AUDIO AMPLIFIER CONSTRUCTION.....\$5.75.** Construction details for preamps and power amplifiers up through a 100-watt DC-coupled FED amplifier.
- BP92—CRYSTAL SET CONSTRUCTION.....\$5.00.** Everything you need to know about building crystal radio receivers
- BP45—PROJECTS IN OPTOELECTRONICS.....\$5.00.** Includes infra-red detectors, transmitters, modulated light transmission and photographic applications
- BP48—ELECTRONIC PROJECTS FOR BEGINNERS.....\$5.00.** A wide range of easily completed projects for the beginner. Includes some no-soldering projects.
- BP49—POPULAR ELECTRONIC PROJECTS.....\$5.50.** Radio, audio, household and test equipment projects are all included
- BP51—ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING.....\$5.50.** Shows how you can make electronic music at home with the simplest and most inexpensive equipment.
- BP56—ELECTRONIC SECURITY DEVICES.....\$5.00.** Includes both simple and more sophisticated burglar alarm circuits using light, infra-red, and ultrasonics
- BP59—SECOND BOOK OF CMOS IC PROJECTS.....\$5.00.** More circuits showing CMOS applications. Most are of a fairly simple design.
- BP72—A MICROPROCESSOR PRIMER.....\$5.00.** We start by designing a small computer and show how we can overcome its shortcomings.
- BP74—ELECTRONIC MUSIC PROJECTS.....\$5.95.** Provides the experimenter with a variety of practical circuits including a Fuzz Box, Sustain Unit, Reverberation Unit, Tremolo Generator and more.
- BP91—AN INTRODUCTION TO RADIO DXING.....\$5.00.** How you can tune in on those amateur and commercial broadcasts from around the world in the comfort of your home
- BP94—ELECTRONIC PROJECTS FOR CARS AND BOATS.....\$5.00.** Fifteen simple projects that you can use with your car or boat. All are designed to operate from 12-volt DC supplies.

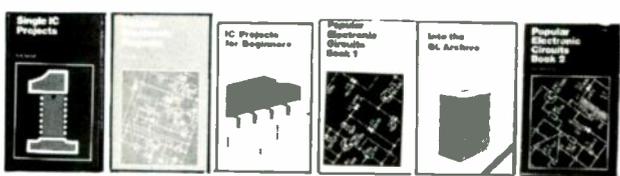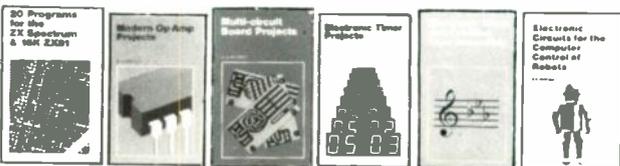

**ELECTRONIC TECHNOLOGY TODAY INC.**  
P.O. Box 240, Massapequa Park, NY 11762-0240

SHIPPING CHARGES IN  
USA & CANADA  
\$0 01 to \$5.00 . . . \$1.00  
\$5 01 to \$10 00 . . . \$1 75  
\$10 01 to 20 00 . . . \$2 75  
\$20 01 to 30 00 . . . \$3 75  
\$30 01 to 40 00 . . . \$4 75  
\$40 01 to 50 00 . . . \$5 75  
\$50.01 and above . \$7.00

**OUTSIDE USA & CANADA**

Multiply Shipping by 2 for sea mail  
Multiply Shipping by 4 for air mail

Number of books ordered

Total price of merchandise . . . \$ \_\_\_\_\_  
Sales Tax (New York State Residents only) . . . \$ \_\_\_\_\_  
Shipping (see chart) . . . \$ \_\_\_\_\_

All payments must  
be in U.S. funds

Total Enclosed \$ \_\_\_\_\_

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

R-9-87

**SCOPE 3½ Digital Multimeters**



**Model DVM-638**  
**\$7995**

- Test leads included
- 11 function, 38 ranges
- Logic level detector
- Audible visual continuity
- Capacitance and conductance measurement


**Model DVM-634**  
**\$5275**

- 7 function, 32 ranges
- Transistor measurement

**Model DVM-636**  
**\$5875**

- 8 function, 37 ranges
- Capacitance measurement

**SCOPE 3½ Digit Capacitance Meter**

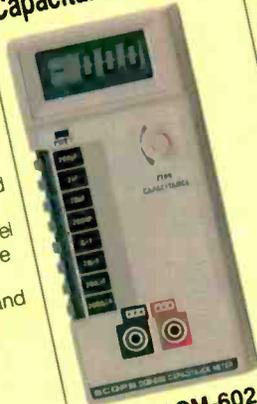

**Model DCM-602**  
**\$5500**

- Test leads included
- 8 ranges with full scale values to 2000 uF
- LSI circuit
- Crystal time base
- Frequency range 80C Hz to 8Hz

**SCOPE Pocket Sized Audio Signal Generator**



**Model RC-555**  
**\$4995**

- Test leads & 9V battery included
- Low distortion sine-wave signal
- 46 step selected frequency
- x1 range 20 Hz to 1.5 KHz/ x10J range 2 KHz to 150 KHz

**SCOPE 4½ Digit LCD Bench Digital Multimeter**



**Model DVM-6005**  
**\$19995**

- Test lead set 6, "D" size batteries included
- 0.4" high characters
- Conversion period: 500 milliseconds
- Automatic, negative polarity

# Mini-Meters with Maxi-Specs

**SCOPE 3½ Digit LCD with 8 Full Functions**

**Model DVM-632**

**\$4495**  
OUR PRICE

Measures only 5 3/8" x 2 13/16" x 1 1/4"

- Deluxe test leads included
- 0.5% accuracy
- Transistor gain test
- Audible continuity checking & diode test
- 10 Amp measurement

Zipped Carrying Case CC-30 **\$450**



**SCOPE 3½ Digit LCD**



Measures only 5" x 2 3/4" x 1 1/4"

**Model DVM-630**  
**\$2995**

- OUR PRICE
- Test leads included
- 0.5% accuracy
- 6 functions, 19 ranges
- Automatic zero adjust
- Low battery indication

Zipped Carrying Case CC-30 **\$450**

ASK FOR FREE CATALOG.

Money orders, checks accepted. C.O.D.'s require 25% deposit.



# Fordham

260 Motor Parkway, Hauppauge, NY 11788

Toll Free **800-645-9518**  
In NY State **800-832-1446**

**Service & Shipping Charge Schedule Continental U.S.A.**

FOR ORDERS	ADD
\$25-\$100	\$4.50
\$101-\$250	\$6.00
\$251-\$500	\$8.00
\$501-\$750	\$10.50
\$751-\$1,000	\$12.50
\$1,001-\$1,500	\$16.50
\$1,501-\$2,000	\$20.00
\$2,001 and up	\$25.00