

JANUARY 1996

Electronics NOW

YOU CAN DESIGN

Printed-Circuit Boards





on your PC with low-cost software

How to use LED Level Indicators in your audio projects

Build the ultimate Telephone Line Simulator for all your testing needs


Understand the jargon Before You Buy your next personal computer

\$3.50 U.S.
\$3.95 CAN.

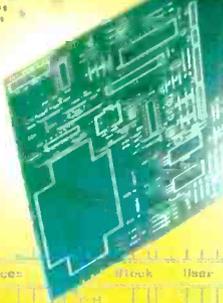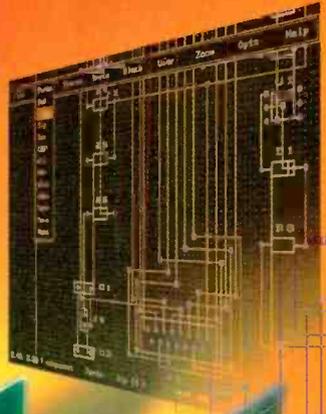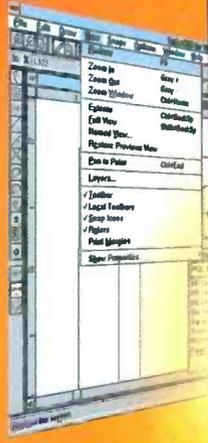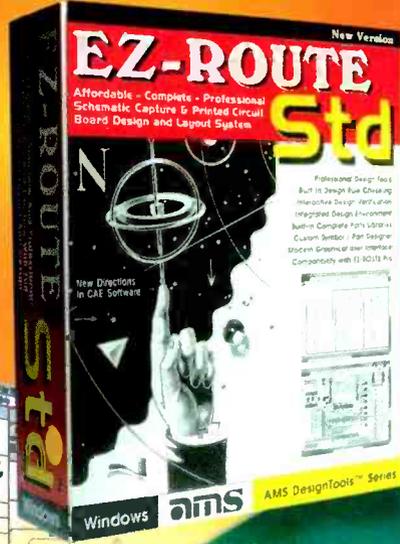

Electronics Workbench


The electronics lab in a computer

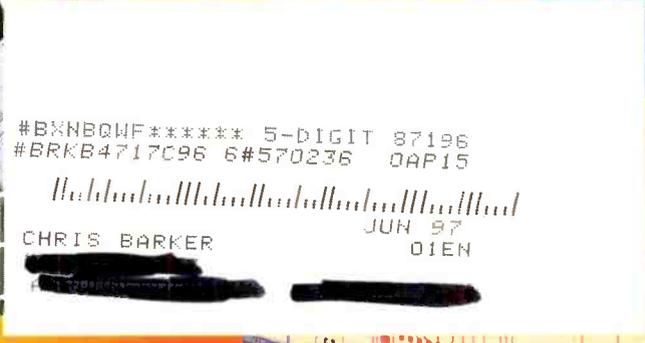

True-rms. True values.

NEW

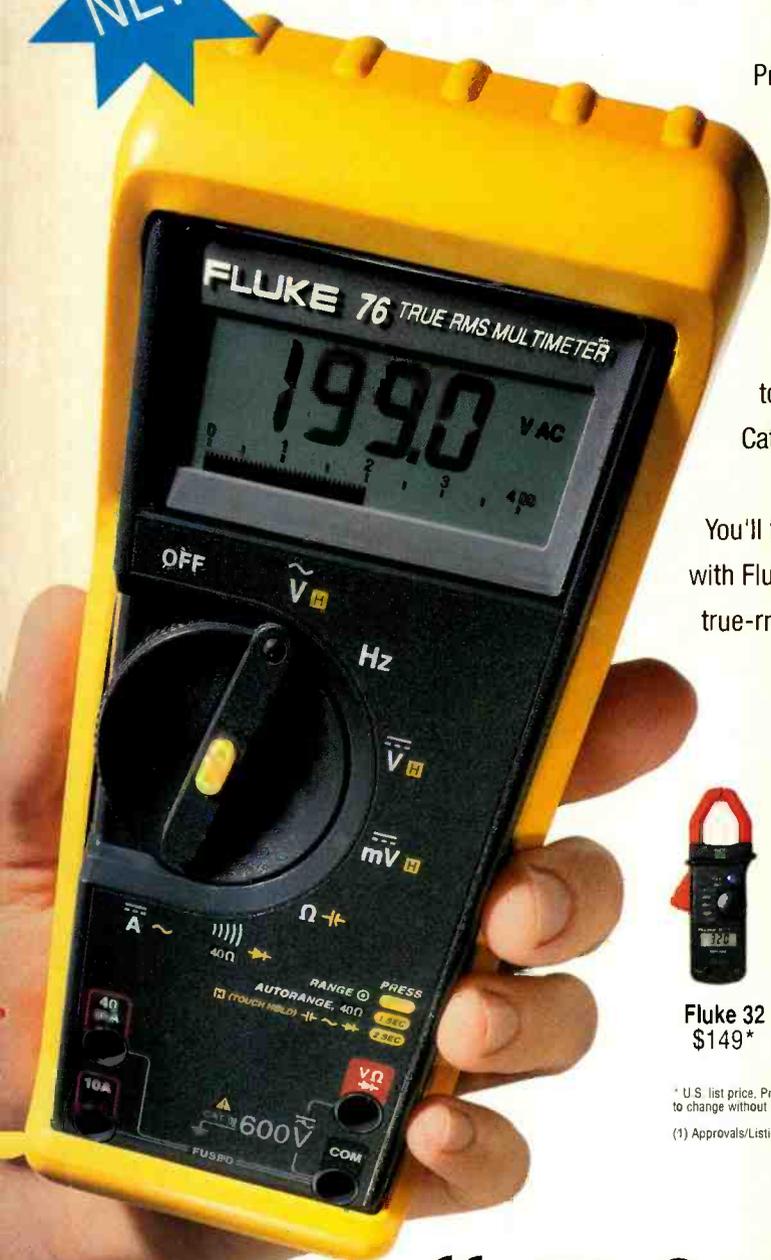Do you troubleshoot non-linear circuits or loads? If so, you need true-rms capability to ensure accurate measurements. Now you can get this capability without having to compromise on quality or safety to stay within your budget.



Priced at just \$199.00*, the new Fluke Model 76 true-rms DMM is the latest in the long line of true-rms values from Fluke. You can use the Model 76 to easily measure true-rms ac current and volts, dc current and volts, ohms, capacitance, continuity, and frequency. And, the Model 76 is the only DMM in its class that meets UL, CE, CSA, and TÜV certification standards and conforms to the IEC 1010-1 product safety standard for Overvoltage Category III.⁽¹⁾

You'll find that kind of true value all the way down the line with Fluke test tools. See your local Fluke distributor to select a true-rms meter that fits whatever your job or budget demands.



Fluke 32
\$149*



Fluke 33
\$269*



Fluke 76
\$199*



Fluke 87
\$335*



Fluke 8060A
\$459*

* U.S. list price. Prices subject to change without notice.

(1) Approvals/Listing pending

© 1995 Fluke Corporation P. O. Box 9090, M/S 250E, Everett, WA USA 98206-9090. U.S. (206) 356-5400. Canada (905) 890-7600. Europe (31 40) 644200. Other countries (206) 356-5500. All rights reserved. Ad no. 00768

CIRCLE 121 ON FREE INFORMATION CARD



FLUKE

Take this GIANT CIRCUIT LIBRARY for only \$14.95

when you join the *Electronics Engineers' Book Club*®


THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS —Vols. 1-4 by Rudolf F. Graf

Hundreds of circuit ideas alphabetically arranged — from Alarm circuits to Zero crossing detector circuits!

"... includes schematics for the latest electronics circuits from industry leaders..."

—Popular Electronics

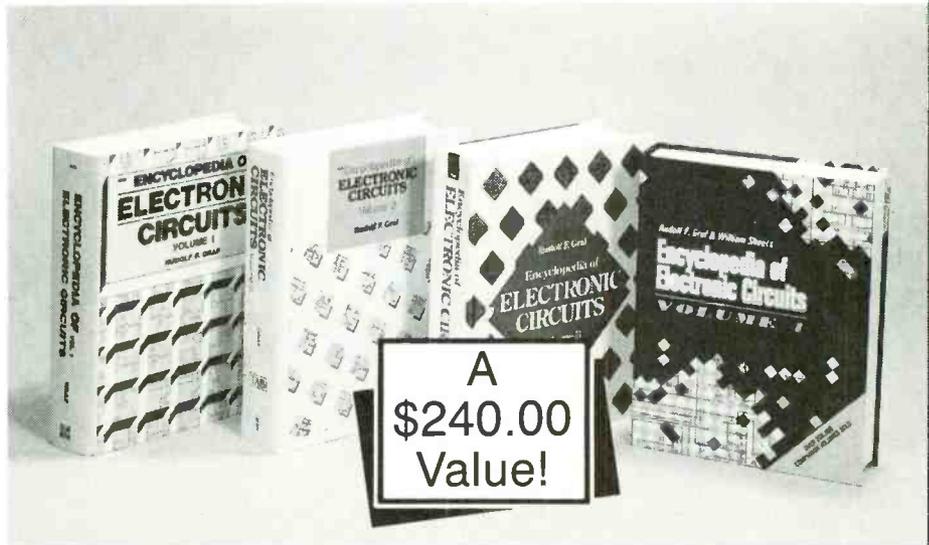Turn to this comprehensive circuit library for hundreds of project ideas . . . valuable troubleshooting and repair tips . . . and concise pinout diagrams and schematics. In each volume you'll find more than 700 electronic and integrated circuits and 100+ circuit categories right at your fingertips to give you ideas you can use on the job or at your workbench.



3,088 total pages 4,490 total illustrations

Book No. 5861488 Hardcover

If coupon is missing, write to: Electronics Engineers' Book Club
A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

As a member of the Electronics Engineers' Book Club . . .

. . . you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. And you'll be eligible for **FREE BOOKS** through the Bonus Book Plan. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time.

Publisher's price shown. ©1995 EIEBC

ELECTRONICS ENGINEERS' BOOK CLUB

A Division of The McGraw-Hill Companies,
P.O. Box 549, Blacklick, OH 43004-9918

YES! Please send me *The Encyclopedia of Electronic Circuits—Vols. 1-4* (5861488), billing me \$14.95 plus shipping/handling & tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days and have my membership cancelled.

Name _____

Address / Apt. # _____

City _____

State _____

Zip _____ Phone _____

Valid for new members only, subject to acceptance by EEBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders.

RP1F196

January 1996, Electronics Now

CONTENTS

JANUARY 1996

ON THE COVER

25 LOW-COST SOFTWARE FOR PC-BOARD DESIGN

The job of designing a printed circuit board continues to grow more demanding as components shrink in size and grow in complexity. Fortunately, personal computers can help make the job easier to bear. In this issue, we look at PC-board layout software packages that are designed to run on your desktop IBM-compatible personal computer. Each package costs less than \$350. Most of the programs are linked in one way or another to the schematic-capture programs that



were reviewed in the September and October 1995 issues of *Electronics Now*. A couple are stand-alone PC-board layout programs, and one, TurboCAD, is a general-purpose CAD program running with a PC-board component library. All of the packages were tested to see how they compare in price, ease of use, and features. — *TJ Byers*


TECHNOLOGY

27 So, You Want To Buy A NEW COMPUTER?



A quick review that explains all of the jargon that you'll hear slung around when you shop for a PC. — *TJ Byers*

37 WAVEFORM GENERATOR CIRCUITS

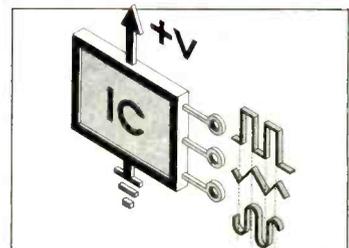

Synthesizers, IC function-generators, and LC-oscillator circuits for generating waveforms. — *Ray M. Marston*

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW. (ISSN 1067-9294) January 1996. Published monthly by Gernsback Publications, Inc., 500 Bi-County Boulevard, Farmingdale, NY 11735-3931. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Canada Post IPM Agreement No. 334103, authorized at Mississauga, Canada. One-year subscription rate U.S.A. and possessions \$19.97, Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax, Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$3.50. © 1995 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.


A stamped self-address envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

BUILD THIS

29 DRESS UP AUDIO PROJECTS WITH SOLID-STATE LEVEL INDICATORS

Light-emitting diodes can be a useful addition to virtually any audio project.

— *Robert C. Richards*

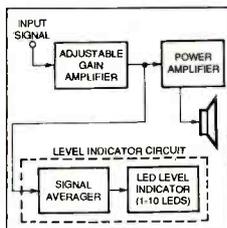

31 PARTY LINE

The ultimate telephone-line simulator offers six different phone extensions, and can even be used as the heart of an intercom system! — *Thomas E. Black*

DEPARTMENTS

6 VIDEO NEWS

What's new in this fast-changing field. — *David Lachenbruch*

14 EQUIPMENT REPORT

Protec 506 digital multimeter.

39 HARDWARE HACKER

Lamps and lighting efficiency. — *Don Lancaster*

45 COMPUTER CONNECTIONS

Wasting disk space. — *Jeff Holtzman*

48 AUDIO UPDATE

Cables and interconnects revisited. — *Larry Klein*



AND MORE

4 WHAT'S NEWS

8 Q&A

12 LETTERS

16 NEW PRODUCTS

20 NEW LITERATURE

150 ADVERTISING SALES OFFICES

150 ADVERTISING INDEX

Electronics NOW

Hugo Gernsback (1884-1967) founder

LARRY STECKLER, EHF, CET,
Editor-in-chief and publisher

EDITORIAL DEPARTMENT

- BRIAN C. FENTON**, editor
- NEIL SCLATER**, associate editor
- JULIAN S. MARTIN**, associate editor
- TERI SCADUTO**, assistant editor
- JEFFREY K. HOLTZMAN**, computer editor
- LARRY KLEIN**, audio editor
- DAVID LACHENBRUCH**, contributing editor
- DON LANCASTER**, contributing editor
- MICHAEL A. COVINGTON, N4TMI**, contributing editor
- EVELYN ROSE**, editorial assistant

ART DEPARTMENT

- ANDRE DUZANT**, art director
- RUSSELL C. TRUELSON**, illustrator

PRODUCTION DEPARTMENT

- RUBY M. YEE**, production director
- KATHRYN R. CAMPBELL**, production assistant
- KEN COREN**, desktop production

CIRCULATION DEPARTMENT

- JACQUELINE P. CHEESEBORO**, circulation director
- THERESA LOMBARDO**, circulation assistant

REPRINT DEPARTMENT

- MICHELE TORRILLO**, reprint bookstore

Typography by Mates Graphics
Cover design by David Loewy

Electronics Now is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*.

Microfilm & Microfiche editions are available. Contact reprint bookstore for details.

Advertising Sales Offices listed on page 150.

Electronics Now Executive and Administrative Offices

1-516-293-3000.

Subscriber Customer Service:

1-800-288-0652.

Order Entry for New Subscribers:

1-800-999-7139.



Audit Bureau of Circulations
Member



WHAT'S NEWS

A REVIEW OF THE LATEST HAPPENINGS IN ELECTRONICS

Pentiums for supercomputers

The Intel Corporation's Beaverton, Ore. operation recently won a contract from the Department of Energy (DOE) to develop what it calls the world's fastest supercomputer. It will include 9000 of Intel's P6 microprocessors, advanced versions of its Pentium processors, yet to be introduced. The processors will be linked in a massively parallel configuration. The cost for the supercomputer has been estimated at \$45 million.

The machine, when built, will be located at Sandia National Laboratories in Albuquerque, N.M. It will be used by DOE scientists to study challenging, data-intensive problems. Included among them will be simulations, the principal means for ensuring the safety, reliability, and effectiveness of U.S.

nuclear weapons without actually testing them.

Intel said its supercomputer would be the first to reach the goal of calculating more than a trillion floating-point operations per second, known as a teraflop. The company sees the supercomputer as a way to enhance its reputation by demonstrating that its production microprocessors can compute in all kinds of machines from laptops to supercomputers. The Beaverton operation used custom-made microprocessors in its previous supercomputers.

Non-levitating magnetic trains


The introduction of high-speed magnetically-levitated trains (called mag-lev) has been delayed by two major stumbling blocks: the high cost of laying suitable tracks and

difficulties in obtaining the rights of way for those tracks. A new concept developed at Sandia National Laboratories, Albuquerque, N. M., has been advanced to get around those problems—a magnetically powered, high-speed train that does not levitate.

The train is called "Seraphim" (for SEgmented RAil PHased Induction Motor). Unlike mag-lev trains, which run with no engine aboard, the Seraphim would carry its own drive mechanism—a gas turbine that powers on-board electromagnets. The pulsed magnets will induce reversed electric currents in a series of aluminum plates bolted to or near the track. The induced currents will create their own magnetic fields, which oppose those of the train. By contrast, mag-lev trains are propelled by magnetic attraction from a series of stationary electromagnetic coils that must be powered along the length of the track

According to the Sandia scientists, the train would be relatively inexpensive to build, and it could run on existing track at speeds of up to 200 miles per hour. Right now, the maximum speed for passenger trains traveling between Boston, New York, and Washington, D.C. is limited to 100 miles per hour, largely by the condition of the tracks. By contrast, demonstration mag-lev trains in Germany and Japan are expected to reach speeds of 300 mph, but they require specially-designed and built track.

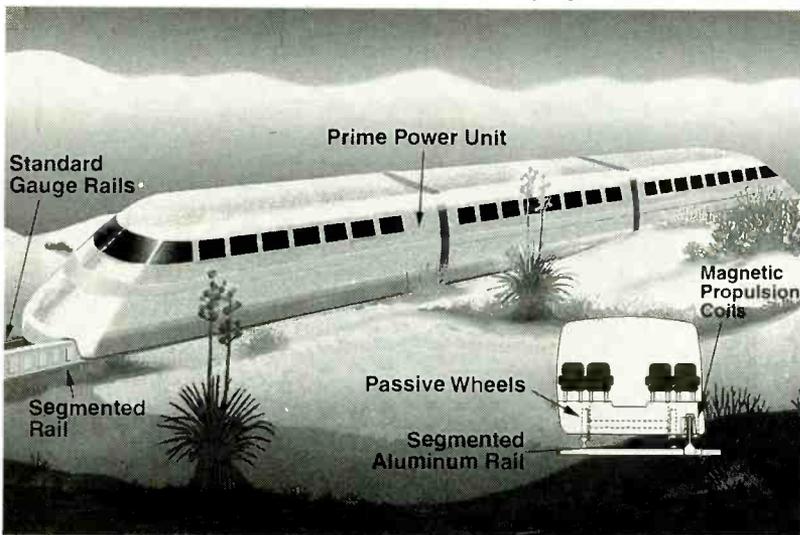Nevertheless, the Sandia scientists say that Seraphim will also be able to go 300 mph on specially laid tracks. A working model, powered by magnetic coils, has reached a speed of 34 miles per hour in a dis-



ARTIST'S CONCEPT OF THE SERAPHIM HIGH-SPEED, MAGNETICALLY POWERED TRAIN shows the ladder-like reaction plates mounted vertically at the sides of the existing railroad track. The inset shows a cross section of one possible train configuration.

tance 12 feet from a standing start. This, they say has demonstrated the validity of the concept.

To facilitate its timely introduction, the Sandia-designed train would travel at speeds limited by the imperfections in existing track. "This is an incremental approach to entry into the world of high-speed, magnetically powered trains," said Robert Turman, manager of Sandia's Magnetic Propulsion Department. "We can speed up the train if the public wants it, at a later time, but more work might be required." He explained that the curves of some sections of existing track are too sharp for high-speed trains. "At that later time, in those locations, we'd either buy new rights-of-way or elevate the track, he added.

In the Seraphim train, the fields pulse on just as the magnets pass the midpoint of the aluminum plates, triggered by optical sensors, to propel the train forward by repulsion. The aluminum plates would be pre-assembled in ladder-like sections (the plates serving as rungs) so that they could be bolted to the track rapidly and inexpensively.

The train would ride on unpowered wheels made of steel or composite materials instead of being levitated by magnetic fields. In this way, the cost and complexity of the system could be further reduced. With this approach, both conventional diesel or electric powered trains could travel on the same track as the new trains. According to Sandia laboratory estimates, the construction costs of their system would be about one-quarter of those for a mag-lev system.

Fuel cells for cars

The fuel cell has long been considered as an alternative power source for private automobiles, but many problems have kept them at arm's length. They include the handling of hydrogen required for their operation and the availability of a suitable low-emission hydrocarbon fuel. Fuel cells have been aboard space shuttles and other spacecraft, but they are costly and are designed to be self sustaining.

continued on page 50



Raise your standard to Wavetek.

Why choose between paying more for a brand name or getting more functions for your money? Get the best of both worlds with **Wavetek**.

Worldwide Service.

Support whenever and wherever you need it.

Tech-preferred Features.

The XL meters have the largest displays, auto-off, data hold, manual and autoranging models in pocket-size convenience.

Quality. Less than 0.5% warranty returns assures continuous reliability.

Selection. Over 35 different **Wavetek** DMMs to meet any measurement need.

User Safety. Conservative voltage ratings, fused inputs, warning beepers, shrouded test leads, and designs that meet worldwide agency approvals.

Total Value. Eight XL Series meters from \$29.95 to \$99.95 to meet any requirement.

You don't need to pay more.
You can't afford to settle for less...

**For the name and location of the
Wavetek dealer near you, call**

1-800-854-2708

(outside the U.S., call 619-279-2200)

Wavetek Corporation

9045 Balboa Avenue,
San Diego, CA 92123

©Wavetek Corp., 1995. Wavetek and the
Wavetek logo are registered trademarks
of the Wavetek Corporation

WAVETEK

CIRCLE 98 ON FREE INFORMATION CARD



VIDEO NEWS

WHAT'S NEW IN THE FAST-CHANGING VIDEO INDUSTRY

BY DAVID LACHENBRUCH

Camcorder standardization

A standard for measuring the light sensitivity of camcorders has been developed by an Electronic Industries Association (EIA) engineering committee and submitted to the American National Standards Institute (ANSI). The new standard will give meaning to low-light claims and make it possible for shoppers to make direct comparisons from make to make and model to model. Until now, there has been no standard and the same camcorder advertised as having sensitivity of one lux in the U.S. may have been rated 8 lux Japan.

The new standard recognizes that low-light sensitivity represents more than luminance alone—the recorded picture must be viewable. Therefore, five different parameters are involved, with minimum standards established for each: luminance level, black level, luminance signal-to-noise ratio, chroma level, and resolution. Measurements can be made using standard test equipment and four easily available charts: standard gray scale chart, 18% gray card, resolution chart, and color chart. Therefore, any well-equipped service shop can check manufacturers' claims.

The standard is entirely voluntary, but it is already being adopted by manufacturers for products to be released this year in the United States. All camcorders and video cameras using the new standard will be identified in ads and instruction manuals as in terms of brightness in lux "measured by the EIA method." It's expected that many camcorders which previously would have been

advertised as having sensitivity of one or two lux will now have to be rated at five, six, or seven lux.

Flash video player


The first practical video player with no moving parts has been announced by NEC in Japan, but production still appears to be about five years in the future. The tiny "Silicon View" player is self-contained with its own 2.5-inch color LCD and battery and fits in a pocket. It uses a solid-state credit-card-size flash-memory card as a storage device instead of tape or disc for the MPEG-1 quality video picture, thereby eliminating all mechanical components. The video player is a companion to a flash memory audio recorder previously developed by NEC. Silicon View's big drawback is playing time. Its 40-megabyte memory card will store only four minutes of video compressed 23-fold. However, NEC says that in

five years it expects 1-gigabit DRAMs to be available in quantities. Using four of these would provide one hour of planning time.

Flash memories, meanwhile, are being developed for a variety of purposes, and the first practical use is expected to be as electronic "film" for consumer-priced digital still cameras. Twelve companies have formed the Compact Flash Association to promote wider use of flash memories and to standardize their use and parameters. Flash cards can hold millions of characters of information and plug into a wide variety of devices, retaining the information when power is turned off or they are removed from a device. They're expected to be used wherever large memory is required in small size.

Flash cartridges are about the size of a pocket matchbox measuring 1.4 by 1.7 inches and 0.13 -inch thick. They are currently available

continued on page 50

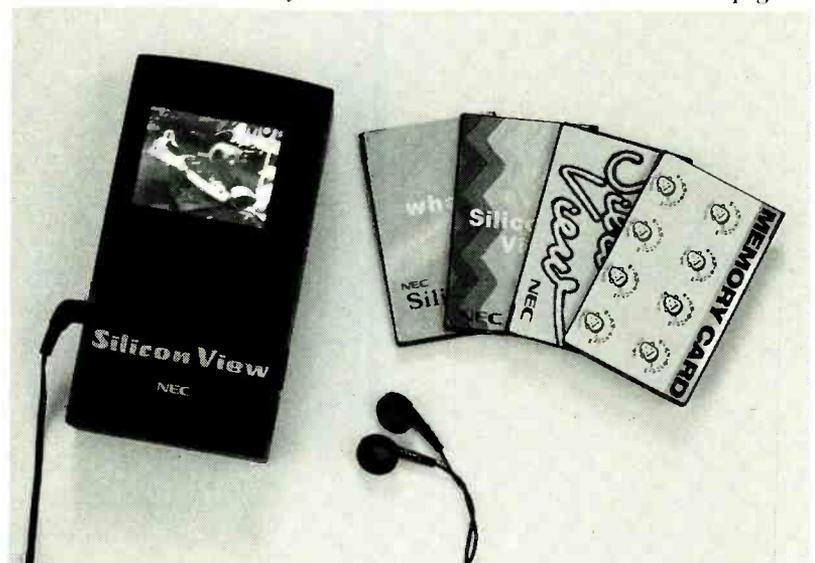

NEC'S SILICON VIEW player has a 2.5-inch color LCD screen. A solid-state flash-memory card, shown to the right, contains the digitally compressed video information.

The Four-Year Electronics Degree Program That Really Hits Home!

Bring The Technology Home With A Bachelor Of Electronics Engineering Degree. No Hassles. No High Cost!



Now's the time to prepare for a profitable career.

We've lowered the cost of higher education.

It's true! You can earn a four-year Bachelor of Electronics Engineering Technology degree today ... and prepare yourself for a high-paying electronics career ... without quitting your job or ever leaving your home. Because World College, an affiliate of the Cleveland Institute of Electronics, offers you the total flexibility of independent study programs proven effective for people like you who truly want to succeed! World College independent study lessons help you build valuable skills

**Mail/Fax Today
or Call
1-800-696-7532**

step-by-step, and expert instructors are personally available to you with a toll-free call. What a way to earn an education!

A world of opportunity.

Where is your career headed? With a four-year bachelor's degree from World College, you call the shots, choosing from incredible, high-paying opportunities in electronics, tele communications, computer, electrical power, and many other growing fields.

World College gives you the skills, the knowledge, the power to take advantage of your best opportunity in electronics. And you can do it all at your own pace!

Without leaving home.

World College continually works to provide its students with the most advanced education tools. From the latest equipment and reference books to breakthrough computer-simulated experiments, students are exposed to the latest technological advancements.

All the equipment, parts, and software you need are included in your affordable tuition, including more than 300 hands-on lab experiments you can complete in your home.

Choose your own pace.

Earn your bachelor's degree on your time — and at your pace — because you pay tuition to World College only as you complete the upper-level semesters close to graduation. The faster you make it through, the less you pay. So you have an incentive to make your future happen quickly — yet the freedom to choose your own pace!

Send today for your FREE course catalog — and give yourself that future you've always wanted — with an electronics degree education from World College.




Take charge of your future in electronics.

Four Powerful Reasons To Connect With World College Today:

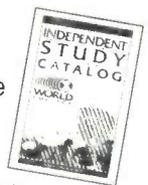1. Earn your four-year degree!
2. Self-paced training!
3. Independent study in your home!
4. Expert instruction!

Give Me The Power!

Send me a FREE World College course catalog today!



(Please Print Neatly)

Name _____

Address _____

City _____

State, Zip _____

Phone () _____

Age _____

**For faster service, call
1-800-696-7532,
or call
1-804-464-4600.**

**Or fax this coupon to
1-804-464-3687.**



Lake Shores Plaza
5193 Drive, Suite 113
Virginia Beach, VA 23455-2500



Affiliated with
Cleveland Institute of Electronics

WAE28



Q & A

READERS QUESTIONS, EDITORS ANSWERS

12-Volt Blinker

Q I would like to connect a 7805 voltage regulator that is fed from a 12-volt battery to a blinking red LED. Do I need capacitors on the regulator and a limiting resistor on the output side to the blinking red LED? I prefer not to use the LM3909 for lack of space.—G. Ross, Vancouver, B.C., Canada

A A blinking red LED, such as Radio Shack's 276-036, contains its own current limiter along with the blinking circuit; you can connect it to the output of a 7805 directly. No capacitor is needed at the output because the 7805 is quite stable without one, and you don't need the slight improvement in regulation that the capacitor would provide. A 0.33- μ F or larger capacitor at the input is recommended to ensure stability, but it might not be necessary (see Fig. 3). To save even more space, you could use a 78L05, which is the low-power version of the 7805, but with a 100 milliamperere maximum output current. Refer back to Fig. 2 for the pinouts.

You're quite right not to use the LM3909 in this application—it would require a rather bulky capacitor (about 300 μ F). The main purpose of the LM3909 is to flash an LED from a 1.5-volt battery, even

though the LED requires 1.8 volts or more. It does this trick by charging the capacitor and then momentarily putting it in series with the battery so that the voltages add.

Power Supply Problems

Q I am having problems with a positive/negative 12 volt regulated power supply (see Fig. 1). Whenever power is applied to the circuit, the 7812 regulator overheats and the 7912 provides a voltage that is less than -12 volts. Can you tell me what's wrong?—M. Schoppert, Orlando, FL

A Taking your first question first, one "gotcha" of negative power supply design is that the pinout of a 7912 isn't the same as a 7812 (see Fig. 2). (Due to a drafting error, some of the pin numbers in our April column were incorrect.)

If mixed-up pins aren't the problem, try removing both of the voltage regulators and see what happens. If the voltages are normal (about 15 to 20 volts, unregulated, on each side), reinstall the regulators one at a time to identify the defective one. If you don't get normal voltages even with the voltage regulators removed, check the capacitors, diodes, and transformer.

The 0.1 μ F capacitors at the outputs improve the regulation and help to ensure stability; the capacitor is optional with the 7812 but required with the 7912.

Cable Shielding

Q I've made a power supply for an audio amplifier. The amplifier has a humming noise when it's run on AC but is fine when run on DC. Does the transformer need more shielding?—M. Schoppert, Orlando, FL

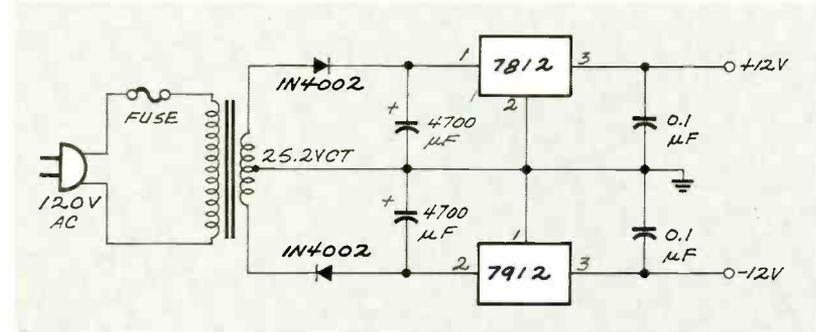


FIG. 1—SPLIT POWER SUPPLY DESIGN.

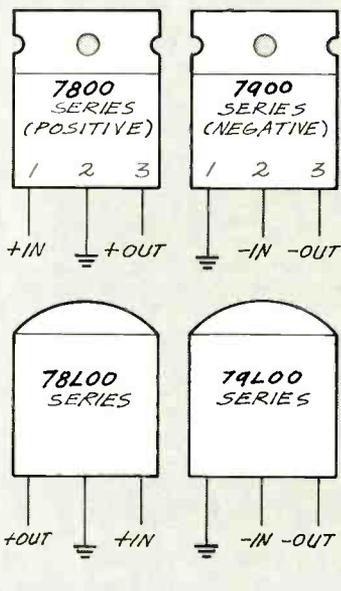


FIG. 2—VOLTAGE REGULATOR PINOUTS aren't all the same. Note differences between positive and negative, and between full-size and low-power versions.

Q I attempted to hook the stereo output of my VCR to the high-level input on my stereo through an audio switch box. I used regular unshielded audio cable and the length was about 50 feet. There was an enormous amount of hum. The layout of the room is such

that it is impractical to move the stereo and VCR closer to each other. I would appreciate any help offered.—C. Pritchard, Brownsburg, IN

A Now both of you know why they make shielded cable. We live in a sea of 60-Hz electromagnetic fields which come from house wiring and are easily picked up by sensitive audio amplifiers, resulting in hum. Near a TV set, there are also strong 60-Hz and 16-kHz fields from the deflection yoke. Shielded cables keep this hum out of the audio. They also keep the amplifier from picking up its own output, which would cause oscillation.

For long cable runs, you might want to use microphone cable or RF cable (RG-8, RG-58, or the like), which has better shielding than ordinary audio patch cords. Make sure that all of the equipment is grounded as specified in its instructions. If any of the items has an unpolarized AC power line plug, try reversing the plug to see if the hum decreases.

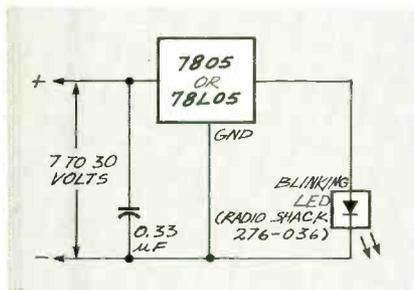


FIG. 3—12-VOLT LED FLASHER CONFIGURATION.

In homebuilt equipment, it's important to build sensitive amplifiers compactly, keeping inputs away from wires that carry AC power. Metal enclosures improve shielding. Two other sources of hum are power supply ripple (unlikely if you're using a regulator IC) and coupling from the transformer. Ripple will diminish if you use a larger filter capacitor; transformer coupling will diminish if you put the transformer just a few inches farther from the circuit.

Speaker cables don't have to be shielded because the speaker impedance is so low (8 ohms) that it would take a gigantic amount of 60-Hz energy to have any audible effect. Telephone wires are unshielded because telephones don't pick up sig-

We Can Think Of 9 Good Reasons To Immunize On Time.

Measles
Mumps
Diphtheria
Tetanus
Hepatitis B
Rubella
Spinal Meningitis
Pertussis
Polio

But You Only Need One.



Immunize On Time.
Your Baby's
Counting On You.
Call 1-800-232-2522



One tree can make
3,000,000 matches.



One match can burn
3,000,000 trees.



A Public Service of The Magazine
© The Advertising Council

HAMEG
Instruments


NEW!

HM304 (35MHz)

HM604-3 (60MHz)

**Unmatched Price
Performance Ratio**

Made in Germany

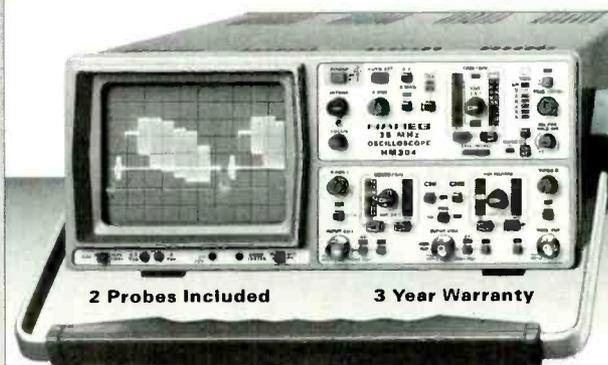

HAMEG gives you a better choice in analog oscilloscopes

- **AUTOSET**
- **SAVE / RECALL Function**
- **Remote Control via RS-232 Interface**
- **Automatic Peak to Peak Triggering**
- **After-Delay-Trigger**
- **Built-in Component Tester**

HM304: 2 x DC-35MHz, 1mV-20V/cm,
Timebase: 0.5s-10ns/cm, Delay with 2nd. Trigger,
Triggerbandwidth: DC-100MHz, ≤ (0.5div.)

HM604-3: 2 x DC-60MHz, 1mV-20V/cm, Delay-Line,
Timebase: 0.5s-5ns/cm, Delay with 2nd. Trigger,
Triggerbandwidth: DC-100MHz, ≤ (0.5div.), 14kV-CRT

The HM304 and HM604-3 are the ideal scopes for your applications and your budget. AutoSet allows you to concentrate on your work without worrying about adjusting the scope. With the **built-in RS-232 interface** its easy to control these analog scopes via your PC.

Call now: Toll-free (800) 247-1241

HAMEG Inc. 266 East Meadow Ave. 1939 Plaza Real
East Meadow, NY 11554 Oceanside, CA 92056
VISA (516) 794-4080 (619) 630-4080
MasterCard (516) 794-1855 (619) 630-6507

CIRCLE 124 ON FREE INFORMATION CARD

nals below 300 Hz or above a few thousand hertz.

Automotive and Kit Questions

Q *Do you have plans on how to convert my 40-amp alternator into a high-amp alternator? Also, are there any kit companies left anywhere? I am interested in building a PC and a TV.—R. Christman, Friendship, WI*

A The alternator question is easy: just take out the old alternator and put in a higher-amperage one, together with the appropriate voltage regulator. Converting an existing alternator isn't practical because you'd have to completely rewind it with heavier wire, which wouldn't fit in the space available.

Kits disappeared because electronic equipment no longer must be wired by hand. It's cheaper to assemble a printed circuit board with automatic machinery than to pack the parts in a box and ship them to the customer for assembly. However, a color TV kit is still available: The Graymark 544 is available from Quantum Electronics, 4 Brisbane Way, Irvine, CA 92715; Tel. 800-858-WATT

For a PC, you don't really need a kit; just order a suitable case, power supply, motherboard, disk drives, and other components from whoever gives the best deal, and put them together. Every town has several people in it who make their living doing just this.

The kits that remain available are generally small items with hobbyist appeal. The biggest kit company is Ramsey Electronics, 793 Canning Parkway, Victor, NY 14564 (1-716-924-4560); they specialize in unusual radio receivers, transmitters, and test equipment.

Old Oscilloscope Manual

Q *Where can I get a manual for an Eico model 460 oscilloscope?—J. T. Haynes, Newark, NJ*

A Eico can still be reached at 363 Merrick Road, Lynbrook, NY

HOW TO GET INFORMATION ABOUT ELECTRONICS

Books: Several good introductory electronics books, including *Building Power Supplies*, are available at Radio Shack.

Our favorite general electronics textbook is *The Art of Electronics*, by Paul Horowitz and Winfield Hill, available from the publisher (Cambridge University Press, 1-800-872-7423) or on special order through any bookstore. Its 1125 pages are full of information on how to build working circuits, with a minimum of mathematics.

Also indispensable is *The ARRL Handbook for Radio Amateurs*, comprising 1000 pages of theory, radio circuits, and ready-to-build projects, available from the American Radio Relay League, Newington, CT 06111, and from ham radio equipment dealers.

Copies of past articles in *Electronics Now*, *Radio-Electronics*, *Popular Electronics*, and *Hands-On Electronics* are available from our Reprint Bookstore, PO Box 4099, Farmingdale, NY 11735 (516-293-3751).

Electronics Now and many other magazines are indexed in the *Readers' Guide to Periodical Literature*, available at your public library. Copies of articles in other magazines can be obtained through your public library's interlibrary loan service; expect to pay about 30 cents a page.

The full text of *Electronics Now* is available in the electronic versions of the *Readers' Guide to Periodical Literature*. *Electronics Now* is also abstracted and indexed in *Academic Abstracts and Magazine Article Summeries* (83 Pine Street, Peabody, MA 01960; Tel: 800-653-2726).

Service manuals for radios, TVs, VCRs, audio equipment, and some computers are available from

11563. Also try Hi Manuals, PO Box 802, Council Bluffs, IA 51502. For general information see "New Life for Old Oscilloscopes," *Electronics Now*, September 1994, pp. 57-64.

Catch the Wind?

Q *I'm trying to measure and record wind speeds in isolated areas. I've looked for a portable, self-powered tachometer, but*

Howard W. Sams & Co., Indianapolis, IN 46214 (1-800-428-7267). The free Sams catalog also lists addresses of manufacturers and parts dealers. Even if an item isn't listed in the catalog, Sams may have a schematic on file that can be copied for you.

Manuals for older test equipment and ham radio gear are available from Hi Manuals, PO Box 802, Council Bluffs, IA 51502.

Replacement transistors, ICs, and other semiconductors, marketed by Philips ECG, NTE, and Thomson (SK), are available through most parts dealers (including Radio Shack on special order). The ECG, NTE, and SK lines contain just a few hundred parts that substitute for many thousands of others; a directory (supplied as a large book and on diskette) tells you which one to use. NTE numbers usually match ECG; SK numbers are different.

Remember that the "2S" in a Japanese type number is usually omitted; a transistor marked D945 is actually a 2SD945.

Hamfests (swap meets) and local organizations can be located by writing to the American Radio Relay League (Newington, CT 06111). A hamfest is an excellent place to pick up used test equipment, older parts, and other items at bargain prices, as well as to meet your fellow electronics enthusiasts both amateur and professional.


Writing to Q&A: We welcome your questions. The most interesting ones are answered in print, usually within 6 to 9 months. Please be sure to include plenty of background information (we'll shorten your letter for publication). We regret that we cannot give personal replies.

all I've found are systems that need an outside power supply.—K. W. Symons, Provo, UT

A You might try using a small hobby-type DC motor as a generator, connected to a voltmeter (analog, not digital, in order to absorb fluctuations). The voltage should be roughly proportional to the speed of rotation, which in turn will indicate wind speed.

Electronics Workbench^{Version 4.1}

**NEW
WINDOWS 95/NT
32 BIT VERSION**

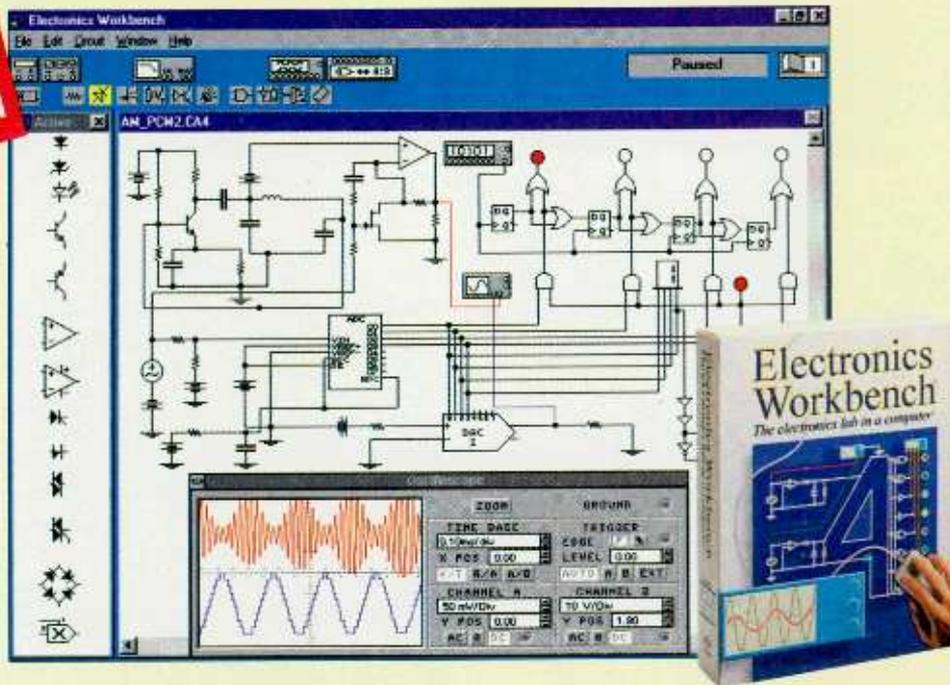

Design and Verify Circuits Faster

Join over 20,000 customers using *the* affordable mixed-signal simulator

Design faster with Electronics Workbench. Mix the analog and digital components and ICs in any combination. And with a click of the mouse, try 'what if' scenarios and fine tune your designs. The built-in SPICE simulator gives you real-world waveforms.

All without programming or netlist syntax errors.

And in minutes. Not hours or days.

You'll be up and running sooner. And create better designs faster with Electronics Workbench. We guarantee it!

Electronics Workbench: \$299

- Click & drag schematic capture
- Mixed analog/digital SPICE simulator
- Instant Bode plots and scrollable waveforms
- 50 analog components with 350 models
- 140 digital components and ICs in TTL and CMOS
- Windows 95/NT/3.1, DOS and Macintosh versions
- Free unlimited technical support
- 30-day money-back guarantee

Engineer's Pack: \$599

- Electronics Workbench
- 2,450 models
- Import/Export SPICE netlists
- Export to PCB packages

To discover more about *the* affordable mixed-signal simulator, call us today at:

800-263-5552

Fax: 416-977-1818

Internet: <http://www.interactiv.com>

INTERACTIVE IMAGE TECHNOLOGIES LTD.

908 Niagara Falls Blvd. #068, North Tonawanda, NY 14120-2060

Telephone: 416-977-5550

BBS: 416-977-3540

CompuServe: 71333,3435

E-mail: ewb@interactiv.com

Australia: 2519-3933 • Brazil: 11-453-5588 • Cyprus: 2621068 • Czech Republic: 19-224908 • Denmark: 33-2540109 • Finland: 0-287-5033 • France: 14-908-9000 • Germany: 711-62-7740 • Greece: 1-524-9981 • Hungary: 1-215-0082 • India: 11-544-1343
Indonesia: 21-470-0815 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-3382-3136 • Malaysia: 3-774-2189 • Mexico: 5-593-5260 • Netherlands: 18-031-7666 • New Zealand: 9-267-1756 • Norway: 22-16-7045 • Philippines: 973-27-0118 • Portugal: 1-81-46609
Singapore: 777-2303 • Slovenia: 61-317-830 • South Africa: 331-6-8309 • South Korea: 22-222-3431 • Spain: 1-383-8335 • Sri Lanka: 1-86-5970 • Sweden: 87-40-5500 • Taiwan: 886-2-366-0080 • Thailand: 662-398-6952 • UAE: 4453505 • UK: 203-23-3216

Trademarks are property of their respective holders. Offer is in U.S. dollars and valid only in the United States and Canada. All orders subject to \$15 shipping and handling charge.

CIRCLE 126 ON FREE INFORMATION CARD



9EA3FP95



LETTERS

SEND YOUR COMMENTS TO THE EDITORS OF ELECTRONICS NOW MAGAZINE

MUSIC VISION CORRECTIONS

An error appeared in the parts placement diagram (Fig. 10) of the article, "Music Vision" (Electronics Now, November 1995). The label for resistor R59 was incorrectly placed; It appeared as an unlabeled jumper located below R60. In addition, the solder-side of the PC board was reversed in the X-ray view, Fig. 10. The corrected version is shown below.—Editor

TELCO IN A BOX CORRECTIONS

I spotted an error in the article, "Telco in a Box" (Electronics Now, September 1995), and a corrected schematic was published. Since then, I have found two other errors. First, resistors R1 and R2 should be at least one-watt resistors but two watts would be better if you want to make allowance for a telephone with an internal short circuit.

Second, the author stated that the telephone company's ring signal pulses "the 50-volt DC line voltage on and off at about 20 Hz." I have found that the ring voltage is much higher than that, and available ring generators provide a much higher voltage. For example, the JEC TECH RG-1 ("Phone Line Simulator," Electronics Now, August 1993) has an output of about 85 volts at 20 Hz. The output of the telephone ringing generator module, No. 56-374, from Hosfelt Electronics is 180 volts peak-to-peak at 20 Hz.

Most telephone equipment will respond to a 60-Hz ring signal. I plan to use a second power transformer, rated for either 24 or 36 volts, with the secondary turns in

series with T1, to give a ring voltage of 50 or 60 volts. I still like the "Telco in a Box" because it is a simple, useful circuit. I have already located defects in several telephones with the breadboarded test circuits I have built.


BILL STILES, CET
Hillsboro, MO

When the November "Letters" column mentioned that several eagle-eyed readers had found an error in the "Telco in a Box" schematic, I assumed someone else would have caught another error in

the circuit.

The standard for telephone connections states that the red ("ring") lead is to have negative polarity with respect to the green ("tip") lead. The design shown does not follow this standard. Most recent RJ-11-based devices are designed so they are polarity insensitive. I assume that was done because, as simple as it might be, keeping the polarity correct is not always done. The article clearly illustrates that specific point.

continued on page 23

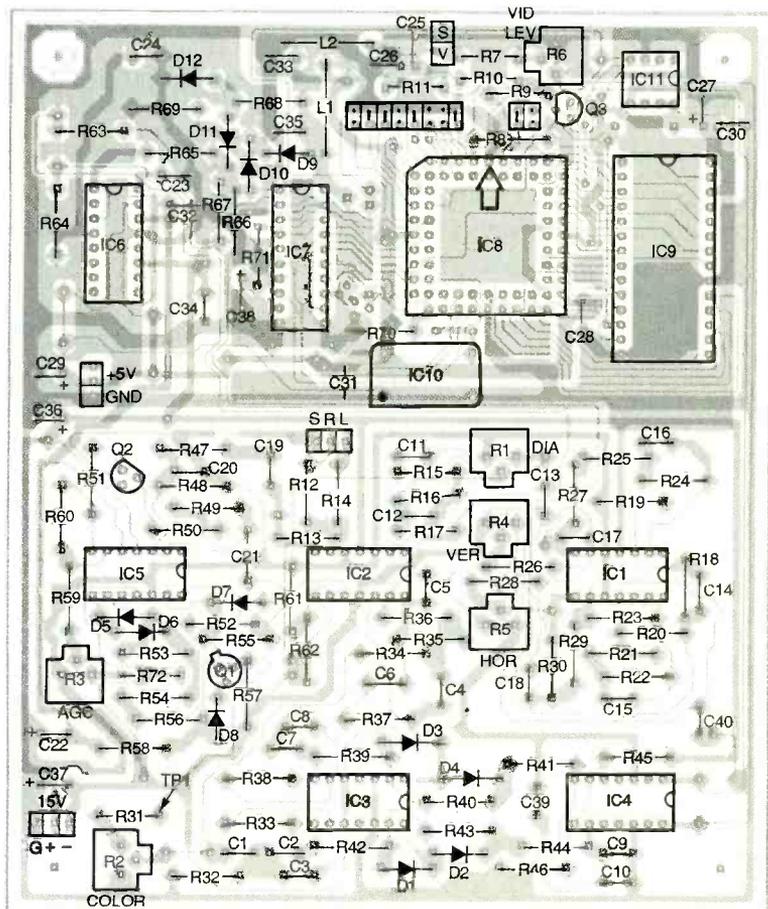

CORRECTED DIAGRAM for Music Vision article.

DECEMBER 1995

NEW SENSOR CORPORATION

20 COOPER SQUARE • NEW YORK, NY 10003
 (212) 529-0466 • (800) 633-5477 • FAX (212) 529-0486

USA MILITARY JAN TUBES *NEW, ORIGINALLY BOXED, AVAILABLE IMMEDIATELY*

TUBE NUMBER	1 PC.	10 PCS.	25 PCS.	50 PCS.	100 PCS.	500 PCS.	1000 PCS.
0A3 JAN	1.15	.90	.75	.65	.55	.45	.40
0C3W JAN RAYTHEON	3.65	2.90	2.30	1.90	1.60	1.30	1.20
5Y3WGTA JAN PHILIPS	4.90	3.90	3.40	2.90	2.60		
6AN8a JAN PHILIPS	5.90	4.70	4.20	3.80	3.15	2.60	2.30
6AS7GA JAN GE	6.15	4.90	3.50	2.90	2.55	2.20	1.90
6BJ7 JAN GE	2.00	1.60	1.40	1.20	1.00	.90	.80
6BL8 JAN SYLVANIA	1.65	1.30	1.10	.80	.65	.50	.45
6BQ7a JAN GE	2.00	1.60	1.35	1.15	.95	.80	.70
6C4WA JAN PHILIPS	4.70	3.75	2.90	2.30	1.80	1.65	1.55
6DJ8 JAN PHILIPS	3.65	2.90	2.30	1.60	1.40	1.15	.95
6EA8 JAN PHILIPS	2.00	1.60	1.35	1.15	.95	.80	.70
6H6 JAN GE	.65	.50	.40	.30	.25	.20	.15
6J5WGT JAN PHILIPS	4.40	3.50	2.60	2.10	1.80	1.65	1.55
6L6GC JAN PHILIPS	21.50	16.90	16.20	15.40	14.90	14.40	13.90
6L6WGB JAN PHILIPS	19.90	15.90	14.90	13.90	12.90	12.20	11.80
6SJ7 JAN GE METAL	1.15	.90	.80	.70	.60	.55	.50
6SL7WGT JAN PHILIPS	7.40	5.90	4.90	4.40	3.90	3.60	3.30
6SN7WGTA JAN PHILIPS	7.40	5.90	4.90	4.40	3.90	3.60	3.30
6SQ7 JAN GE	3.15	2.50	2.00	1.50	1.20	1.15	1.10
6U8a JAN PHILIPS	2.00	1.60	1.35	1.15	.95	.80	.70
6V6GT JAN GE (GLASS)	12.40	9.90	9.50	8.80	8.40	7.60	6.90
6X5WGT JAN PHILIPS	1.90	1.50	1.35	1.20	1.05	1.00	.95
12AT7WC JAN GE	6.15	4.90	4.40	3.90	3.25	2.90	2.70
12AU6 JAN PHILIPS	1.90	1.50	1.25	1.00	.90	.80	.70
12AX7WA JAN GE	9.65	7.70	6.50	5.90	5.40	4.90	4.50
12AX7WA JAN PHILIPS	9.65	7.70	6.50	5.90	5.40	4.90	4.50
12SG7 JAN RCA	1.00	.80	.70	.60	.50	.40	.35
12SH7 JAN GE	1.00	.80	.70	.60	.50	.40	.35
12SL7JAN GE	1.25	1.00	.90	.80	.70	.60	.55
83 JAN GTE	8.75	7.00	6.40	5.80	5.50	4.90	4.65
829B JAN CETRON	8.55	6.85	6.25	5.65	5.35	4.75	4.50
5656 JAN RAYTHEON	7.50	6.00	5.00	4.20	3.30	2.50	2.20
5750 JAN GE	1.00	.80	.70	.60	.50	.40	.35
5751 JAN GE	6.15	4.90	4.30	3.90	3.20	2.70	2.30
5814a JAN PHILIPS	3.75	3.00	2.75	2.50	2.20	2.00	1.90
6080WC JAN GE	6.15	4.90	4.40	3.90	3.40	2.90	2.60
6188 JAN PHIL -MIL 6SL7	11.15	8.90	7.90	6.40	5.90	5.60	5.30
6189W JAN PHILIPS	3.75	3.00	2.75	2.50	2.20	2.00	1.90
6922 JAN PHILIPS	4.25	3.40	2.80	2.10	1.90	1.65	1.45
7581a JAN PHILIPS	19.50	18.00	17.25	16.50	15.75		

January 1996, Electronics Now

MASTER CARD/ VISA ACCEPTED • MIN. ORDER \$100.00 • ALL ORDERS SHIPPED F.O.B. N.Y.C.

CIRCLE 258 ON FREE INFORMATION CARD



EQUIPMENT REPORTS

PROTEK'S DIGITAL MULTIMETER HAS AN RS-232C INTERFACE

Store, process, and print out measurements on your PC with the handheld Protek 506 DMM.

CIRCLE 15 ON FREE INFORMATION CARD



We routinely evaluate new electronic test instruments that have been submitted to us by their manufacturers for review. We then write up our findings in these equipment reports. Needless to say, handheld digital multimeters (DMM) are prominent among the equipment we have reviewed, so when we were offered a new DMM to test, our response was generally ho-hum. However, it turns out that the Protek did come up with an unusual feature to its new 506—an interface for connecting the DMM to a personal computer so you can store, process, and print out measurement data.

Protek's 506 is at the top of its new DMM family that also includes the 504, and 505. The 506 will do everything that the other models will do but it is the only one to offer the RS-232C serial interface that permits the instrument to transfer data to a personal computer. Protek recognized that the PC can supplement the features of its DMM by permitting measurements to be

stored, printed out as a data log, or introduced into spread sheets, reports or graphics.

Basic specifications

The Protek 506 is a $3\frac{3}{4}$ -digit, 4000-count, autoranging DMM with a dual-function liquid-crystal display containing an analog bargraph. It includes a 9,999 (10 MHz)-count frequency counter and annunciators. In addition to its ability to measure all of the basic electrical variables—AC and DC voltage and current (to 20 amperes), and function as an ohmmeter, it provides true RMS readings. Other outstanding features include a ten-location data memory, the ability to measure inductance and capacitance, and a provision to read decibels.

The DMM is packaged a now conventional-appearing, flat, rectangular case with a panel-mounted, 12-position rotary multifunction switch. Eight front panel pushbuttons are assigned to special functions and four panel-mounted jacks accept probes for different mea-

surement scales. The included RS-232C cable plugs into the top of the case. This instrument has a time mode with alarm, clock, and stopwatch, and it can perform min., max., and averaging. In addition, it can do continuity and diode testing.

The evolving DMM market


The Protek 506 is an excellent example of evolutionary progress in handheld DMMs. In the global electronics market, all DMMs have profited from the decreasing price of components due to increasing demand and production volume, particularly for the crucial integrated circuits that handle the conversion of analog measurements to digital values and the display of that data. The ready availability of the DMM conversion chips and display drivers has turned the DMM into a commodity instrument, if not exactly a consumer electronics product.

To set itself apart from other manufacturers, the DMM maker today must include some unusual feature or features to distinguish his products from the hundreds of look-alikes in all price ranges. This raises two questions: do buyers really want those features, and how much are they willing to pay for them? The marketplace inevitably provides the answers.


From the customer's point of view, the DMM, regardless of its country of origin, offers exceptional value in all price ranges. The DMM is arguably the most popular, versatile, and cost-effective instrument available today for the maintenance and repair of electronics. As is true of many other electronics products, the latest DMMs offer more in

continued on page 22

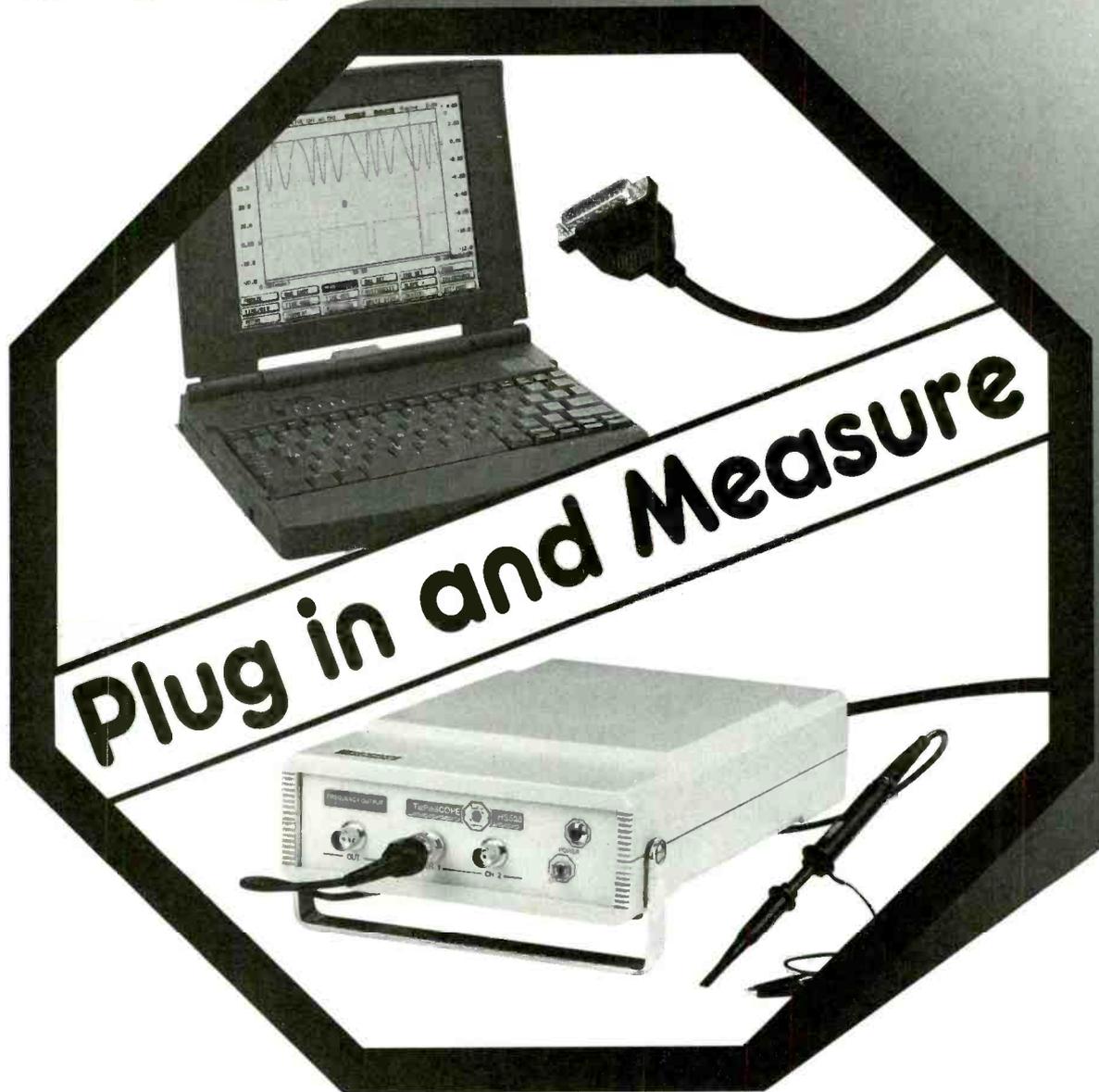STOP! Just Take Two Steps to do Your Measurement



TiePieSCOPE

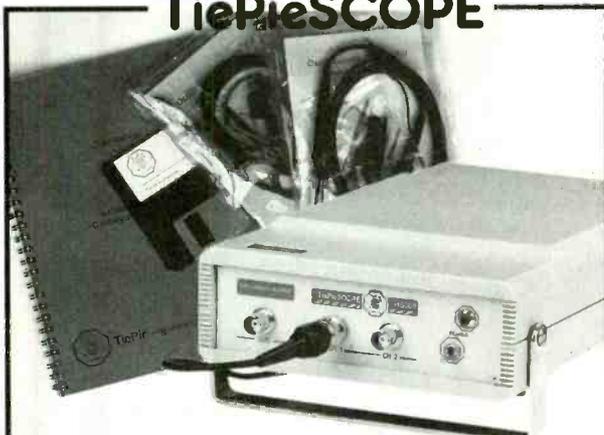

**HS508 Complete set
for US \$1054**

You can simply plug the new TiePieSCOPE - HS508 into the parallel port of your portable or desktop PC. With the advanced software, you can use this two channel, 8 bits, 50 MHz measuring instrument as a fast digital storage oscilloscope, including a lot more features than a single oscilloscope! Moreover, the TiePieSCOPE - HS508 contains a multiple display voltmeter (up to 5 MHz true RMS), a spectrum analyzer with an harmonic distortion meter and a transient recorder for recording a variety of signals.

The TiePieSCOPE - HS508 is supplied complete with user manual, software, and two probes.

Call now for a free demo diskette and our catalog!
Toll-free: 1-800-626-6929

CONWAY Engineering, Inc.

8393 Capwell Drive, Oakland, California USA 94621-2113
Tel.: (510) 568-4028 - Fax: (510) 568-1397

CIRCLE 310 ON FREE INFORMATION CARD

www.americanradiohistory.com



NEW PRODUCTS

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

OSCILLOSCOPE TRIGGER DEVICES

THE SUPERPROBE OSCILLOSCOPE triggering devices from Programmable Designs are instruments that can trigger complex events in digital circuitry and simplify circuit debugging and testing.

Status LEDs permit the monitoring of power, input signals, triggering activity, and clock activity. This instrument includes an interface cable assembly with removable grabbers and gold-plated machined

eight signal inputs. It includes a cable with permanently attached through-hole component grabbers.

SuperProbe pricing ranges from \$99.00 to \$549.00, depending on the model.

PROGRAMMABLE DESIGNS INC.

41 Enterprise Drive
Ann Arbor, MI 48103-9503
Phone: 313-769-7540
Fax: 313-769-7242
E-mail: design@prog-designs.com



CIRCLE 20 ON FREE INFORMATION CARD

They will work with any oscilloscope to provide a wide range of event-triggering options. Four different models are available.

The SuperProbe II has 18 digital logic inputs and a clock input. It supports three clocked triggering modes and one combinatorial (pattern-match) triggering mode. The device works with flexible logic combinations for specifying triggering events. These include no-match triggering for triggering when certain unexpected events occur. This model has separate "pattern select" and "don't care" configuration DIP switches.

contacts that work with IC clips and 0.025-inch posts.

SuperProbe I is a pattern-match or word-recognition version with 17 digital inputs. It allows any logical combination with up to 17 signals to be specified for the trigger event. This model is offered in two versions. The standard version includes an interface cable with permanently attached grabbers for through-hole component leads. The deluxe version has a cable identical to the one included with the SuperProbe II.

The SuperProbe Basic-8 permits pattern-match triggering with up to

INDUSTRIAL CONTROL SYSTEM

THE QED INDUSTRIAL Control System (ICS) from Mosaic Industries is a single-board computer with either a character or graphics LCD display, and a keypad or touchscreen. It has a battery-backed memory, real time clock, analog and digital I/O, board area for prototyping, and provision for serial communications. The system is packaged in an industrial-style enclosure with screw-terminal connections.

This packaged system is intended for many different applications including machine automation, data acquisition, and robotics. The ICS can interpret data from temperature, pressure, and optical sensors; process the input data; and control stepper motors, valves, relays, and other actuators.



CIRCLE 21 ON FREE INFORMATION CARD

Palm-sized plug-in cards introduce isolated high-current outputs and high-voltage inputs, 4 to 20-milliampere signalling, and analog-to-digital or digital-to-analog conversions. The system modules can be programmed in C or Forth from a personal computer with on-board multitasking software.

The QED Industrial Control System with character display and keypad (ICS-AK) is priced at \$995.00. With a graphics display and keypad (ICS-GK), it is priced at \$1190.00.

MOSAIC INDUSTRIES, INC.

5437 Central Avenue, Suite 1
Newark, CA 94560
Phone: 510-790-1255
Fax: 510-790-0925

MONOLITHIC CRT DRIVER

THE LM2406T FROM National Semiconductor is advertised as the industry's first monolithic IC cathode-ray tube driver. This triple-channel, 40-MHz CRT driver, designed for SVGA and XGA monitors. The bipolar device is capable of supporting scan frequencies up to 58 kHz/72 Hz.

The LM2406T can drive a cathode capacitance of 8 pF with a voltage swing of 40 volts peak-to-peak, and it has a rise and fall time of 9 nanoseconds. When paired with National Semiconductor's LM1203N or LM1207N video amplifiers, the combination forms a complete video channel for SVGA and XGA computer monitors.

The monolithic IC includes inter-



CIRCLE 22 ON FREE INFORMATION CARD

nal protection to prevent momentary short circuiting. It reduces monitor component count, simplifies system design and manufacture, and increases

system reliability. It is offered in a reduced-size TO-220 package.

The LM2406T monolithic CRT driver is priced at \$2.50 in quantities of 1000.

NATIONAL SEMICONDUCTOR CORPORATION

2900 Semiconductor Drive
Santa Clara, CA 95052-8090
Phone: 1-800-272-9959

MULTIMETER WITH CLAMP-ON ADAPTER

THE AMPROBE MODEL PMM-1 is designed so that a clamp-on adapter can be connected, allowing it to measure up to 300 amperes. The basic DMM is a 3200-count instrument that measures AC and DC volt-



CIRCLE 23 ON FREE INFORMATION CARD

age to 600 volts and ohms to 30 megohms. It has an annunciated LCD readout and a 65-segment analog bargraph. The DMM offers auto and manual ranging, audible continuity testing and data hold. It also performs diode checks. The PMM-1 has 600-volt AC and DC protection on all ranges.

With the addition of the PMM-C clamp-on adapter, the PMM-1 can

measure up to 300 amperes AC. The adapter jaws will close over conductors up to 1.14-inch in diameter. The combination has an output of 1 millivolt AC per 0.1-ampere AC. With additional optional accessories, the PMM can do infrared scanning and measure up to 1000 amperes AC, 600 amperes DC, temperature, and up to 400 kilowatts.

The PMM-1 digital multimeter with carrying case, test leads, batteries, and a user's manual is priced at \$69.85. The PMM-C clamp-on accessory is priced at \$49.85.

AMPROBE INSTRUMENT


630 Merrick Road
Lynbrook, NY 11563
Phone: 1-800-477-VOLT
or 516-593-5600
Fax: 516-593-5682

COMPUTER CARD FOR MULTIMEDIA PRESENTATIONS.

THE MODEL ME1000 (VGA2-NTSC) plug-in computer card from Methode Electronics allows multimedia presentations to be displayed on a standard television receiver or recorded on a VCR. The card converts VGA computer graphics, computer-aided designs, and multimedia presentations to standard NTSC video output.

The card automatically detects and switches between 640x480 pixel, 320x200 pixel, and 80-column text modes. The plug-in card works with any IBM or compatible personal computer that has an Intel 386, 486, or Pentium processor, an ISA bus, and a graphics card with the appropriate connector.

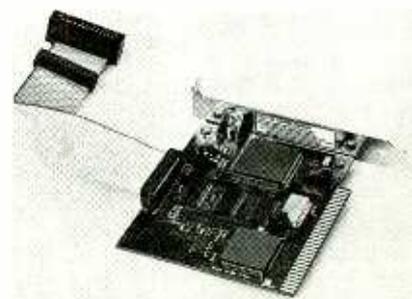The ME1000 also provides flicker-free images, CAD-drawing output with no missing lines, and sharp 80-



CIRCLE 24 ON FREE INFORMATION CARD

CABLE TV CONVERTERS/ DESCRAMBLERS!

- **Novavision 5600, 5700, 5800**
5-lot @ \$195.00 ea.
- **M-80**
10-lot @ \$49.00 ea.
- **TNT Original Digital Dynamite**
10-lot @ \$45.00 ea.
- **PIO TRIPLE-MODE Add On**
10-lot @ \$55.00 ea.

**CALL FOR MANY OTHER
POPULAR MODELS!!**

ALL EQUIPMENT AVAILABLE IN STOCK!
FAST DELIVERIES! WE SHIP WITHIN 24 HOURS!
30 DAY GUARANTEE / 1 YEAR WARRANTY



1-800-818-2282

8 a.m. to 5 p.m. CST, Monday - Friday

PROtech
DISTRIBUTORS, INC.

13 S. Randall Road #507, Algonquin, IL 60102

NOTE: Converters and Descramblers must be used according to The Federal
Cable Television Consumer Protection and Competition Act of 1992
NO ILLINOIS ORDERS ACCEPTED

column text mode. The card conforms to multimedia standards, and it is compatible with AutoCAD and 3D Studio CAD software. It is also compatible with DOS and Windows operating systems. The cards can display 256 colors and are easily installed with the included internal cable.

The ME1000 (VGA2NTSC) plug-in card is priced at \$525.00
METHODE ELECTRONICS, INC.
dataMate Division
7444 West Wilson Avenue
Chicago, IL 60656
Phone: 708-867-9600
or 1-800-323-6858
Fax: 708-867-3149

The AccuMILL software package is compatible with AutoCAD, AutoSKETCH, and CorelDRAW. It can interpret ASCII and HPLG plotter-files running under MS-Windows. The AccuSTEPPER controller is an automated computer interface that controls all three axes.

The AccuMILL/Plus desktop machining center is priced at costs xx.
KEPRO CIRCUIT SYSTEMS, INC.
630 Axminister Drive
Fenton, MO 63026-2992
Phone: 1-800-325-3878
Fax: 314-343-0668

MEMORY TEST PACKAGE

THE SIMCHECK PLUS MEMORY tester from Aristo Computers combines the SIMCHECK memory module tester with a 40-bit port adapter in a single package. Together, they can do complete testing of both




CIRCLE 26 ON FREE INFORMATION CARD

DESKTOP MACHINING CENTER

KEPRO CIRCUIT SYSTEMS has introduced the AccuMILL/Plus, a miniature automated X-Y-Z desktop machining center. It can drill, mill, route, and engraves circuit boards. The machine can be fitted with eight different tools. It can drill through both single- and double-sided circuit boards to 0.00025-inch resolution for short-production runs or prototyping. It can also mill circuit patterns and machine complex three-dimensional objects from plastic, aluminum, brass, wood, or modeling wax.

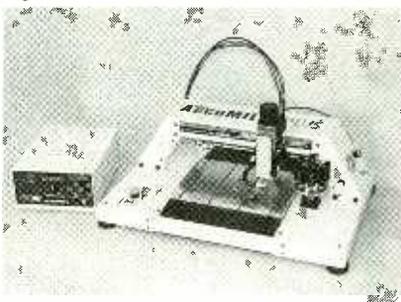The worktable for the AccuMILL/Plus measures 10x14-inches. Its automated tool carousel has eight tool motors. These include one



CIRCLE 25 ON FREE INFORMATION CARD

30-pin and 72-pin single-in-line memory modules (SIMM). The enhanced memory tester includes a universal power supply that can be plugged directly into the tester or into the 40-bit port.

The basic SIMCHECK memory tester tests all standard SIMM and single-in-line (SIP) memory modules with eight or nine bits of 64- and 256-kilobit and 1-, 4-, and 16-megabit memory. The 40-bit port enhances the tester's ability to test 72-pin SIMM modules that have a data bus with up to 40 bits and a maximum memory capacity of 128 megabytes.

SIMCHECK Plus is priced at \$1490.00

ARISTO COMPUTERS INC.
6700 SW 105th Avenue, Suite 300
Beaverton, OR 97008
Phone: 1-800-3-ARISTO
or 503-626-6333
Fax: 503-626-6492

fully automatic, fixed/floating position for accurate milling of irregular surfaces. Adjustments can be made to 0.001 inch. The machine has three different motor speeds: 7000, 28,000, or 50,000 rpm. Three-axis mounting of the tools permits the fabrication of three-dimensional parts.

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS**-You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**
Or, Call 1-800-932-4268 Ext. 90


COMMAND PRODUCTIONS
FCC LICENSE TRAINING, Dept. 90
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

STEREO AUDIO DIGITAL-TO-ANALOG CONVERTER

The PCM1712 stereo audio monolithic IC digital-to-analog converter (DAC) from Burr-Brown includes an 8× oversampling digital filter, a third-order multilevel delta-sigma modulator, a low-pass filter, and an analog output amplifier. It is intended for automotive and consumer electronics products such as CD players, tuners, keyboards, CD-ROM drives, and CD-karaoke systems.

Key specifications for the device include i87-dB THD+N (full scale), 94-dB dynamic range, and 98-dB signal-to-noise ratio. The on-board digital filter has i35-dB stopband attenuation and ±0.17-dB passband ripple. Several special functions are available, including digital attenuation, de-emphasis, soft mute, and double-speed dubbing. The PCM1712 supports both 16-bit normal input data and 16-bit IIS data (32-bits per

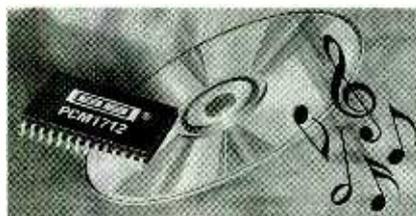

CIRCLE 27 ON FREE INFORMATION CARD

word, continuous clock).

The PCM1712 stereo audio DAC is available in a 28-lead SOIC package, priced from \$2.70 each in quantities of 1000.

BURR-BROWN CORPORATION


P. O. Box 11400
Tucson, AZ 85734
Phone: 1-800-548-6132

HIGH-DENSITY PCB LEDs

LUMEX OPTO/COMPONENTS is offering a new series of high-density LEDs that occupy only half the footprint of standard T-5 LED packages. Consequently, more LEDs can be positioned in limited circuit board space. The new devices feature fool-proof polarity orientation. They are intended for such applications as func-

tion indicators, circuit board fault indicators, and front-panel display backlights.

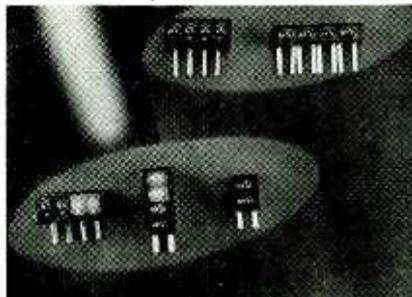The LEDs are available in four configurations: two-vertical (dual-tower), four vertical (quad-tower), and four horizontal (quad-ranch) with either side-by-side or front-to-back



CIRCLE 28 ON FREE INFORMATION CARD

leads for PC-board connection.

The shape of the lenses assures proper polarity orientation. Round and a square flanges around the leads assure proper placement of the LEDs in their compact holders during assembly. The LEDs' 2-mm size and a space-saving holder eliminates spacing between LEDs for high-density installations. Variations in the doping of the LED dies provides high-intensity red, red, yellow, amber, green and even blue. The configurations are available in any color combination, in either standard or low-current models. The LEDs draw from 2 to 20 milliamperes

The Lumex LEDs are priced from \$.50 to \$4.00 per configuration, depending on the number of LEDs, colors, and quantities ordered.

LUMEX OPTO/COMPONENTS INC.

292 East Hellen Road
Palatine, IL 60067
Phone: 708-359-2790

EARN YOUR B.S. DEGREE IN COMPUTERS OR ELECTRONICS



By Studying at Home

Grantham College of Engineering, now in our 45th year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, modem, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Grantham offers three separate distance-education programs, leading to the following accredited degrees:

- (1) The B.S.E.T. with Major Emphasis in Electronics.
- (2) The B.S.E.T. with Major Emphasis in Computers.
- (3) The B.S.C.S. — the Bachelor of Science in Computer Science.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by
the Accrediting Commission of the
Distance Education and
Training Council

GRANTHAM
College of Engineering
Grantham College Road
Slidell, LA 70460



EN




NEW LITERATURE

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

Prototype to Production Catalog No. 955

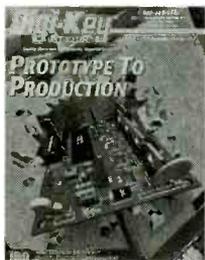Digi-Key Corporation
701 Brooks Avenue South
P. O. Box 677
Thief River Falls, MN 56701-0677
Phone: 1-800-344-4539
free



CIRCLE 337 ON FREE
INFORMATION CARD

Mail-order distributor Digi-Key offers more than 1400 new products from 15 different manufacturers in its latest catalog. Newly introduced

products include ribbon-cable and D-type subminiature connectors from AMP, Inc., power supplies from Power-One, microcontrollers from Microchip, and development systems from Picmaster.

A Quick Index on the first page will speed up finding references to the products being offered. This is supplemented by detailed manufacturer and product indexes. Digi-Key sells just about everything a manufacturer or serious electronic hobbyist needs and its catalog is a valuable reference for the professional designer as well as all advanced hobbyists.

The catalog is arranged alphabetically by manufacturer with alphabetical tabs on the outside edges of the pages for quick reference. A comprehensive index both by product and by manufacturer makes it easy to find what you are looking for in this huge 368-page compendium of electronic parts.

Digi-Key's product line card

includes all the basic passive electronic components, discrete and integrated semiconductor devices, and connectors and cable assemblies and much more. The company offers hand tools, soldering materials, power supplies, and a wide variety of test equipment in addition to all the active and passive component lines that it lists.

Sendmail: Theory and Practice

by Frederick M. Avolio and Paul A. Vixie.
Digital Press
313 Washington Street
Newton, MA 02158-1626
Phone: 617-928-2500
Fax: 617-928-2620
\$29.95



CIRCLE 338 ON FREE
INFORMATION CARD


This book explains the history, architecture, configuration, and maintenance of Sendmail, a standard mail deliverer on Berkeley-Unix systems. Widely used on the Internet, many consider Sendmail impossible to understand. The authors have tried to correct that.

Avolio and Vixie explain how and why Sendmail works and offer practical advice on designing and maintaining an electronic mail system. There are "cookbook recipes" and simplified explanations of how to manage a mail system. It compares E-mail and Sendmail and defines key terms. This book is

great for computer system managers and readers who want to set up and maintain a mail system for computers.

Hipercomm Databook (BR1334/D)

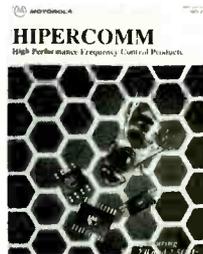Motorola Inc.
Literature Distribution Center
P. O. Box 20924
Phoenix, AZ 85063
Phone: 1-800-441-2447
Fax: 602-994-6430
free



CIRCLE 339 ON FREE
INFORMATION CARD

This is a revised edition of Motorola's Hipercomm Databook. It contains device specifications in the form of data sheets and applications

information for Motorola's frequency-control products. It contains technical data on a broad line of integrated circuits for phase-locked loop circuits. An introductory section simplifies the selection of the right components for a given set of applications requirements.

Motorola's line of low-power prescalers includes products with more than 40 different combinations of frequency, divide ratio, and power to meet the needs of most designs. Information is also included on Motorola's integrated, single-chip synthesizers that conserve power, making them suitable for handheld, battery-operated communications products.

Low Power Communications

Volume 3: QRP Hardware
by Richard Arland, K7YHA.
Tiare Publications
P. O. Box 493
Lake Geneva, WI 53147
Phone: 1-800-420-0579
\$14.95



CIRCLE 340 ON FREE INFORMATION CARD

This is the third volume of three in a series on QRP, an international radio Q signal that means "reduce your power". Previous titles were "QRP Basics" and "Advanced

QRP Operating." This book on low-power communications examines the new and used equipment available for the radio amateur who is planning to upgrade a QRP station that might be communicating with microwatts of power. It includes tips on buying and trading used equipment, and discusses operating accessories of value to the QRP operator.

Arland's book includes a chapter on the planning and erection of antenna towers and another on how to start and run a QRP club. The addresses of QRP clubs and suppliers and manufacturers of QRP equipment are listed in the appendix.

ESD Control Products.

Charleswater
90 Hudson Road
Canton, MA 02021-1407
Phone: 617-821-8370
Fax: 617-575-0172
free



CIRCLE 341 ON FREE INFORMATION CARD

This is the latest catalog from Charleswater on its products for the control of electrostatic discharge (ESD). Many new ESD control products and training aids are included. It also provides up-to-date information


on existing product categories.

Charleswater's product line does include all of the standard accessories necessary to ESD-proof a designated ESD-protected workstation: conductive workplace mats, grounded wrist straps, conductive floor mats, and instruments for testing the integrity of the ground. Also included are conductive tote boxes, protective bags and packaging for vulnerable components and circuits, air ionizers, and conductive sprays.

This catalog also includes a basic tutorial on electrostatic discharge, explaining what it is and how it is controlled by grounding, shielding, and moving-air neutralization.

HF Filter Design and Computer Simulation

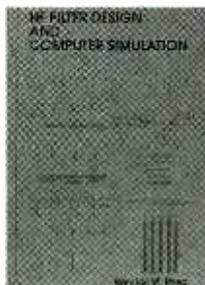by Randall W. Rhea.
McGraw-Hill Book Company
11 West 19th Street
New York, NY 10011
Phone: 1-800-2-MCGRAW.



CIRCLE 342 ON FREE INFORMATION CARD

This book is a complete design guide for printed and LC filters for RF and microwave applications. It includes easy to understand discussions of high-frequency filter theory and accurate

computer simulation models for many different filters. Rhea's book includes a review of the classic design formulas as well as the more recent filter design concepts developments.

The first chapters are devoted to fundamental concepts, with greater emphasis given to lumped-elements than distributed elements. Those chapters are followed by a review of available computer-aided filter-design techniques, including both simulation and synthesis.

The author goes on to discuss distributed low-pass, bandpass, high-pass, and bandstop filters, and he explains how to select the appropriate design for specific applications. **EN**

Where Can You Turn To Learn Good Troubleshooting Skills?

Tech Training
by SENCORE

Sencore introduces training by technicians - for technicians...

Computer Monitor Servicing Course - TC100
(Approved for CEU credit)

You'll learn:

- How to quickly determine monitor types
- How to make all monitors look alike
- How to accurately identify failures

Computer Monitor Servicing Class - TC100T
(Approved for CEU credit)

You'll learn how monitors work, circuit operation, how to make adjustments, and practical troubleshooting.

Call for locations and dates.

Understanding TV Horizontal Stages - TV300

This training package includes a self-study workbook and a 45 minute video.

Tech Choice Troubleshooting Demonstrations

You'll take home valuable tips that you'll put into practice immediately.

- Computer Monitor Troubleshooting
- Profitable TV Troubleshooting
- Simplified VCR Servicing
- Camera/Camcorder Testing & Troubleshooting

Check the city listing below for upcoming Tech Training locations:

Albuquerque • Atlanta • Baltimore • Birmingham (AL)
Boston • Buffalo • Calgary • Chicago • Cincinnati
Cleveland • Dallas • Detroit • Edmonton • El Paso
Houston • Indianapolis • Kansas City • Knoxville (TN)
Los Angeles • Miami • New York City • Oklahoma City
Philadelphia • Phoenix • Pittsburgh • Raleigh (NC)
Reno • San Diego • Seattle • Sioux Falls • Tampa
Toronto • Vancouver •

(Tentative list. Not all Tech Training classes will be held in all locations. Call for details.)

Call 1-800-SENCORE
(736-2673)


SENCORE

3200 Sencore Drive, Sioux Falls, SD 57107
Direct: (605) 339-0100 FAX (605) 339-0317

CIRCLE 128 ON FREE INFORMATION CARD

6207

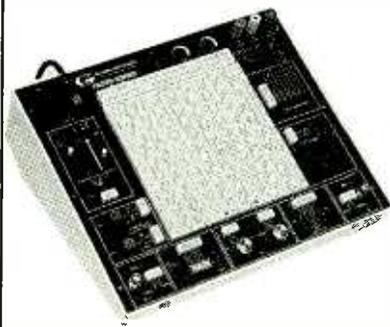AT
\$299.95,
 NO OTHER DESIGN
 WORKSTATION
 GIVES YOU
 SO MUCH
 FOR SO LITTLE.



**PB-503 PROTOBOARD®
 DESIGN STATION**

**OVER \$600 WORTH
 OF WORLD CLASS
 TEST EQUIPMENT
 FOR UNDER \$300!**

(800) 572-1028



**GLOBAL®
 SPECIALTIES**

70 Fulton Terrace
 New Haven, CT 06512

(203) 466-6103
 FAX: (203) 468-0060

an
 Interplex
 Industries
 company

CIRCLE 122 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 14

terms of accuracy, reliability, power conservation, and performance features than did the earlier generations of those products.

The hard fact is that the reliability of the manufacturer or supplier is more important than the county of origin in any purchase decision for a DMM. If the product fails for some reason, can it be repaired economically? Will the vendor stand behind product warranties, or must you throw away the instrument and buy a new one if it conks out?

The DMM market today is stratified, and regardless of where it is made, you get pretty much what you pay for. As in the past, DC accuracy and resolution are all important considerations, despite such attractive features as larger displays or more rugged packaging. Handheld DMMs, like personal computers and other consumer electronics products, have been stuffed with more features with little or no price change.

Open any electronic equipment catalog, visit your local electronics store, or look at the ads in *Electronics Now*, and you'll see 3-digit handheld DMMs priced as low as \$20 and those with 3¹/₄-digit readouts and 0.1% DC accuracy priced at \$200 or higher, with a slew of options in between. Thus, prudent buyers will examine and compare features, check out the reputation of the supplier, and make their decision based on their actual needs today and consider their future measurement requirements.

More on the Protek 506

The Protek 506 DMM is top of the line in a family of three new multimeters that also includes the 504 and 505. It offers 0.3% DC voltage accuracy. The software included with the 506 to support its RS-232C serial interface allows all functions and measurements to be viewed both on the meter and the computer screen simultaneously. The 3¹/₂-inch diskette included with the meter contains the software for Windows and MS-DOS.

In addition to its 20-ampere measurement capability, the Protek 506 can measure current values to 400 microamperes with 0.1-microampere resolution. The autoranging feature can also be turned off, and each range can be set manually. The DMA's light-emitting diode backlight can be turned on and off with a panel push-button to conserve the 9-volt battery. Backlighting is especially useful at night or in locations where normal room lighting is inadequate.

The Protek 506 includes a built-in timer with an alarm that is displayed on the secondary display. The timer can count up to or down from periods up to 10 hours. This feature allows you to make periodic measurements without constantly referring to a clock or watch.

Temperature from -20°C to +1200°C, with 1-degree resolution, can be measured with an optional K-type thermocouple. The thermocouple can be connected with an adapter to the meter's test lead jacks. Temperature in degrees Celsius is shown on the main display and temperature in degrees Fahrenheit is shown in the secondary display.

The 506 can be set to produce a 5-volt peak-to-peak squarewave at three different frequencies: 2048, 4096, and 8192 Hz. Thus, squarewaves at different frequencies can be introduced into circuits under test or for the testing of audio devices such as buzzers, speakers, and transducers. The meter will automatically turn off its power after it has been idle for 30 minutes if you forget to turn it off. However, this feature can be disabled if you must have the power on for more than 30 minutes. The instrument includes overload protection and safety design in compliance with UL 1244 and VDE-0411.

The Protek 506 is definitely in the professional instrument category. However, although it was designed for the professional, its price is low enough to attract the serious hobbyist. The model 506 including carrying case, manual, test lead, 9-volt battery, RS-232C cable, and diskette is priced at \$189.95. (Protek, 154 Veterans Drive, Northvale, NJ 07647, 201-767-7242.)

EN

LETTERS

continued from page 12

However, there is still a lot of older serviceable telephone equipment around that can be tested with the "Telco in a Box." As shown, the circuit will indicate polarity sensitivity (primarily DTMF, or AT&T's TouchTone) to be defective; they will work but will not produce any DTMF. There are DC-operated circuits that depend on the loop current for power. Thus, reversing the polarity is like putting batteries in a radio with their positive and negative terminals reversed.

All that is required to make a telephone polarity insensitive is to design a diode-bridge circuit within the telephone in the tip and ring so that the positive and negative polarities will be correctly delivered to the circuitry, regardless of what the loop polarity is.

JIM DOPSON

Lilburn, GA

DEFENDING THE AMIGA

I am responding to the appalling opening paragraph in Don Lancaster's description of the New Tek toaster ("Hardware Hacker," *Electronics Now*, August 1995). He stated that Amiga was "left in a less-than-stellar position after the sale of Commodore." He also said that an internationally known company in bankruptcy court sold its assets at a "yard sale." But to say that the company threw out the baby and drank the wash water was reprehensible. However, it is true that the transaction was bizarre.

The facts are that New Tek wanted to enter the personal computer market, so it made a PC version. Why did Lancaster have to trash the name Amiga along the way? Commodore was purchased by EsCom, a large company with extensive financial resources and a large distributor base in place. The company intends to continue producing and selling the Amiga. It also has plans to sell rights to the Amiga so it can be cloned. Amiga's future is brighter now than it has been in years.

continued on page 47

Superior 100 MHz Probe

TPI's Most Popular Probe

- 1x - 10x switchable
- Fits all scopes
- Fast risetime - equal to a 200 MHz probe
- Sharp pulse response - clean leading edge
- Replaceable head, cable, ground lead and probe tip
- Slim design for easier handling
- Satisfaction guaranteed - 10 day return privilege

Model SP100B

\$45




Call for free catalog of probes to 300 MHz - Active Probes - Differential Probes - Test Leads and Measurement Accessories

TEST PROBES, INC. **TPI**

9178 Brown Deer Road • San Diego, CA 92121
TEL: 619-552-2090 • FAX: 619-535-1260

Toll Free: 1-800-368-5719

CIRCLE 123 ON FREE INFORMATION CARD

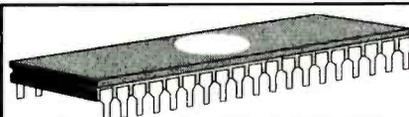

CABLE CONVERTER DIAGNOSTIC TEST CHIP

LOAD FULL ACTIVATION OF CABLE CONVERTER

WE STOCK A COMPLETE LINE OF CHIPS, TOOLS, WIRELESS QUICK INSTALL TEST BOARDS AND DIAGNOSTIC CUBES FOR ALL CONVERTERS!

NEW EXCLUSIVE PIONEER CUBES & BOARD

RESETS E-1 THRU E-8 INSTANTLY, ALL MODELS!!

WHOLESALE PRICING-DEALERS WANTED, CALL

#1 IN CUSTOMER SERVICE & TECH. SUPPORT!

*ALL ORDERS SHIP WITHIN 24HRS, UPS/ FED-X.

*PRIORITY NEXT DAY SHIPPING AVAILABLE!

*SALE- BUY 3 BOARDS GET 1 FREE TILL JAN 96.

*LOWEST PRICE & SUPERIOR PRODUCT GUAR!!

*FRIENDLY COURTEOUS SERVICE. WE'RE PRO'S

VISA **VISUAL**

COMMUNICATIONS INC.

FOR ORDERS 1-800-GO-CABLE

CATALOG & TECH. SUPPORT 717-620-4363 EST. 1977

CABLE TV CHANNELS

EQUIPMENT Direct!

GUARANTEED

FREE 30 DAY TRIAL

SAVE \$1000's

The Nationwide source for cable TV equipment.

"BUY WHERE THE DEALERS BUY"

FREE

TV Cable Descramblers, Converters and Magic Box Catalog. Open Every Day!

Your VCR TAPES CAN PLAY AS CLEAR AS DAY!

Eliminates copy protection on any tape

UNJAM NOW WITH Video Decoder

*Copy any rental/bought tape
*Power Cord and RC Plugs included

CALL NOW!

2 Year Warranty
Member Better Business Bureau

FREE 30 Day Trial!

MEGA ELECTRONICS

1-800-676-6342

VISA • MC • COD

ANTIQUE RADIO CLASSIFIED

Free Sample!

Antique Radio's Largest Circulation Monthly. Articles, Ads & Classifieds.

6-Month Trial: \$17.95. 1-Yr: \$34.95 (\$51.95-1st Class).
A.R.C., P.O. Box 802-L15, Carlisle, MA 01741
Phone: (508) 371-0512 VISA/MC Fax: (508) 371-7129

Be a PC repair expert!

Approved home study. Learn to troubleshoot, repair, install, upgrade, and service computers.

Free literature: 800-223-4542

Name _____ Age _____

Address _____ Phone (____) _____

City/State _____ Zip _____

School of PC Repair, Dept. JJA342, PCDI
6005 Roswell Road, Atlanta, Georgia 30328

January 1996, Electronics Now

RETAILERS THAT SELL OUR MAGAZINE MONTHLY

Alaska

Frigid North Co.
1207 W. 36th Avenue
Anchorage, AK 99503

Alabama

Radio Distributing Supply
121 East Broad Street
Gadsden, AL 35903

Arizona

Dalis Electronics
2829 E. McDowell Road
Phoenix, AZ 85008

California

California Electronics
221 N. Johnson Ave.
El Cajon, CA 90202

Signal Electronics
22307 Ocean Avenue
Torrance, CA 90505

Ford Electronics
8431 Commonwealth Avenue
Buena Park, CA 90621

All Electronics
14928 Oxnard Street
Van Nuys, CA 91411

Gateway Electronics of CA
9222 Chesapeake Drive
San Diego, CA 92123

Mac's Electronics
191 South "E" Street
San Bernardino, CA 92401

Electronics Warehouse
2691 Main Street
Riverside, CA 92501

Orvac Electronics
1645 E. Orangethorpe Ave.
Fullerton, CA 92631

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove, CA 92643

Marvac Dow Electronics
980 S. A Street
Oxnard, CA 93030

Kandarian Electronics
1101 19th Street
Bakersfield, CA 93301

Whitcomm Electronics
105 W. Dakota #106
Clovia, CA 93612

Marvac Dow Electronics
265-B Reservation Road
Marina, CA 93933

Minuteman Electronics
37111 Post St., Suite 1
Fremont, CA 94536

HCS Electronics
6819 S. Redwood Drive
Cotati, CA 94931

Halted Specialties Co.
3500 Ryder Street
Santa Clara, CA 95051

JDR Micro Devices
2233 Branham Lane
San Jose, CA 95124

Metro Electronics
1831 J Street
Sacramento, CA 95814

The Radio Place, Inc.
5675-A Power Inn Road
Sacramento, CA 95824

HSC Electronics
4837 Amber Lane
Sacramento, CA 95841

Colorado

Gateway Electronics of CO
2525 Federal Blvd.
Denver, CO 80211

Centennial Electronics
2324 E. Bijou
Colorado Sps., CO 80909

Connecticut

Signal Electronics Supply
589 New Park Avenue
W. Hartford, CT 06110

Cables & Connectors
2198 Berlin Turnpike
Newington, CT 06111

Electronic Service Prod.
437 Washington Avenue
North Haven, CT 06473

Georgia

Norman's Electronics, Inc.
3653 Clairmont Road
Chamblee, GA 30341

Idaho

The Current Source
5159 Glenwood
Boise, ID 83714

Illinois

Tri State Elex
200 W. Northwest Hwy.
Mt. Prospect, IL 60056

Maryland

Mark Elec. Supply Inc.
5015 Herzel Place
Beltsville, MD 20705

Massachusetts

U-Do-It Electronics
40 Franklin Street
Needham, MA 02194

Michigan

Purchase Radio Supply
327 East Hoover Avenue
Ann Arbor, MI 48104

Norwest Electronics
33760 Plymouth Road
Livonia, MI 48150

The Elec. Connection
37387 Ford Road
Westland, MI 48185

Elec. Parts Specialists
711 Kelso Street
Flint, MI 48506

Professional Data Corp.
1332 US Highway 41 West
Ishpeming, MI 49849

Minnesota

Acme Electronics
224 Washington Avenue N.
Minneapolis, MN 55401

Missouri

Gateway Electronics Of MO
8123-25 Page Blvd.
St. Louis, MO 63130

New Jersey

Lashen Electronics Inc.
21 Broadway
Denville, NJ 07834

New York

Sylvan Wellington Co.
269 Canal Street
New York, NY 10013

R&E Electronics
4991 Rt. 209
Accord, NY 12404

Unicorn Electronics
Valley Plaza
Johnson City, NY 13790

Ohio

Philcap Electronic Suppliers
275 E. Market Street
Akron, OH 44308

Oregon

Norvac Electronics
7940 SW Nimbus Avenue
Beaverton, OR 97005

Portland Radio Supply
234 S.E. Grand Avenue
Portland, OR 97214

Texas

Tanner Electronics
1301 W. Beltline
Carrollton, TX 75006

Mouser Electronics
2401 Hwy. 287 N
Mansfield, TX 76063

Electronic Parts Outlet
17318 Highway 3
Webster, TX 77598

Washington

Amateur Radio Supply Co.
5963 Corson Ave., Ste 140
Seattle, WA 98108

Wyoming

Chris Supply
2007 S. Douglas Hwy., Ste. C
Gillette, WY 82716

**If you'd like to sell our magazine in your store,
please circle 210 on Free Information Card.**

LOW-COST SOFTWARE for PC-BOARD DESIGN

THE JOB OF DESIGNING A PRINTED circuit board continues to grow more demanding. In the past, just about anyone could lay out a PC board by simply reading a schematic and translating the lines into traces on a piece of metal-clad circuit board with a resist-ink pen or dry-transfer decals and tape. Those days are all but gone. Today's circuit boards are made by powerful CAD systems that include many built-in features for design optimization and design-rule checking. Until recently, though, capable circuit design packages were priced out of the range of most hobbyists and many small businesses. Fortunately, that situation has changed, too.

This article looks at twelve PC-board layout software packages that are designed to run on your desktop IBM-compatible personal computer. Each package costs less than \$350. Most of the programs are linked in one way or another to the schematic-capture programs reviewed in the September and October 1995 issues of *Electronics Now*. A couple are stand-alone PC-board layout programs, and one, TurboCAD, is a general-purpose CAD program running with a PC-board component library.

As before, we tested the programs to see how they compare in price, ease of use, and features by producing a board based on a benchmark circuit. Fig. 1 is the schematic drawing of that circuit, which is a functional MIDI interface box for a Sound Blaster (and compatible) sound board. This design was selected because it provides a good mixture of analog and digital ICs, plus an assortment of connectors—the latter of which

You can design professional-quality printed-circuit boards on your desktop PC.

TJ BYERS

is extremely difficult for the software to deal with in terms of library support and layout flexibility. In fact, the connector had to be created or modified in nearly half the programs, which gave us an opportunity to examine the library editor or netlist editor. Finally, each program was printed out and the hard-copy or data file was examined for accuracy and production quality.

PC-board Layout Software

As with schematic capture software, the "devices" needed to build a printed-circuit board are contained in a component library. Basically, a PC-board device is a collection of circles and ovals, called pads, that have the same pattern as the part that will be soldered to them. These patterns are often called footprints because they can be used for many devices with the same pattern—a 14-pin DIP, for example—regardless of their electrical properties.

Most circuit designs are too complex to be constructed using a single layer of copper. Most hobby projects require two layers (top and bottom); many commercial designs need four layers or more. Very often these layers have to be wired together to maintain electrical continuity. This is done using vias (see Fig. 2). When the via goes all the way through the board from the top to bottom, it's called a

through-hole via. As a rule, through-hole vias are used as solder points for resistor, capacitor, and IC leads. Vias that connect one layer of a multi-layer design to the layer just below it is called a blind via. Blind vias that occur within the bowels of a multi-layer PC board are called buried vias. The size and shape of the via is critical to the success of a layout. Generally, the more via options, the better.

Tracks come in many different shapes and sizes, too. Unlike vias, tracks aren't a part of the component library (note the TurboCAD exception). Instead, they are placed on the board using pens with differently "shaped" tips. Different track widths can usually be mixed on the board—at least up to a point. For production reasons, it's desirable for tracks to have rounded or chamfered corners instead of right-angle turns. Most PC-board layout software lets you change copper layers while routing to avoid roadblocks caused by tracks that are already in place; each uses a different mechanism, as detailed below. Ideally, a via should be automatically placed when changing layers. The term "neck down" refers to the ability to change the width of the track as you draw it. However, in programs costing this little, necking down, when available, is usually done afterwards using the track editor. The ultimate in

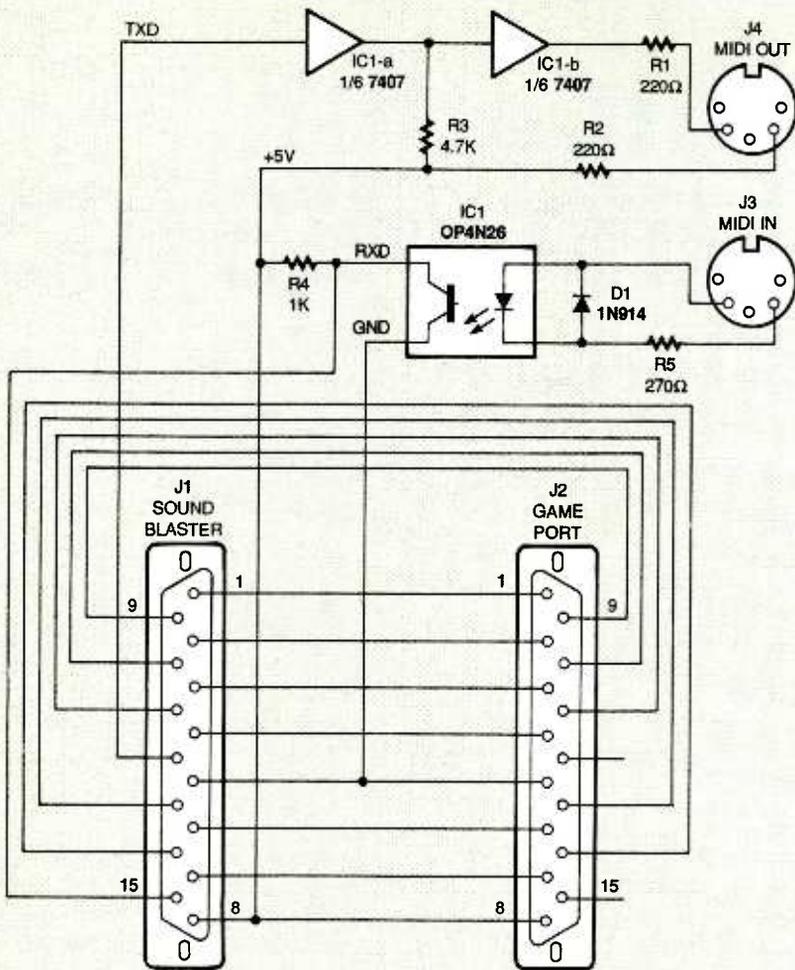


FIG. 1— THIS IS THE ELECTRONICS NOW BENCHMARK circuit used for testing the PC-board layout programs in this review. It is a functional MIDI interface box (J3 and J4) with support for a game port.

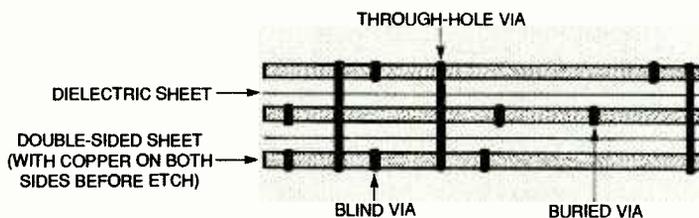


FIG. 2 — MULTI-LAYER BOARDS are typically manufactured as stacks of two-layer boards. For example, a six layer board is made up of three two-layer boards, which are etched first and then bonded together. Vias make connections between the layers.

where the component count is low, to reduce wiring errors, or where there's a repetition of a pattern, such as in a memory module with many identical ICs.

Product:	Easytrax
Version:	2.06
Price:	Free
Platform:	DOS
Publisher:	Protel Technology

Although there might not be any such thing as a free lunch, Easytrax from Protel Technology is as close as you'll ever come to it. Easytrax is a fully-featured, DOS-based PC-board layout program from Protel Technology which originally sold for \$450 and is now available absolutely free. Yep, you heard right. It's freeware! And we're not talking about an obsolete, second-rate program here. Easytrax, the introductory-level member of the Protel family of Electronics Design Automation (EDA) packages, puts professional-quality PC-board layout tools in the hands of students, hobbyists and part-time designers for the cost of a phone call. (See Fig. 3.)

Easy to learn and easy to use, Easytrax can construct PC Boards up to 32-inches square with up to eight layers of copper. Easytrax works on the complete range of IBM PC/XT/AT, PS/2, and compatible computers—plus it can run from floppies as well as a hard disk. The program is supplied with graphics drivers that support video resolutions of up to 1024x768 and 16 colors, though most of the video boards supported are long obsolete. Fortunately, you can download the graphics driver source code from the Protel bulletin board (408-243-0125), which tells you how to write your own graphics driver.

Like many PC-board layout programs, everything on the board is put there by hand, one part or one track at a time. The software doesn't interface with any schematic capture program or any type of netlist.

The Easytrax component li-
continued from page 121

routing, of course, is an autorouter. Two of the programs here have an autorouter—one a full autorouter and the other a pad-to-pad autorouter—and two more have an autorouter option at extra cost.

There are two types of PC-board layout programs, those that stand alone, and those that are linked to a schematic capture program via a netlist. Of

the programs discussed here, only four have a netlist connection, although eight of the programs are associated with a schematic capture package.


PC-board Layout

The following four PC-board layout programs are stand-alone software packages. They range in cost from free to \$129, and are best used for projects

So, You Want to Buy a New Computer?

To be a smart computer shopper, you have to speak the language!

TJ BYERS AND NAOMI WISE

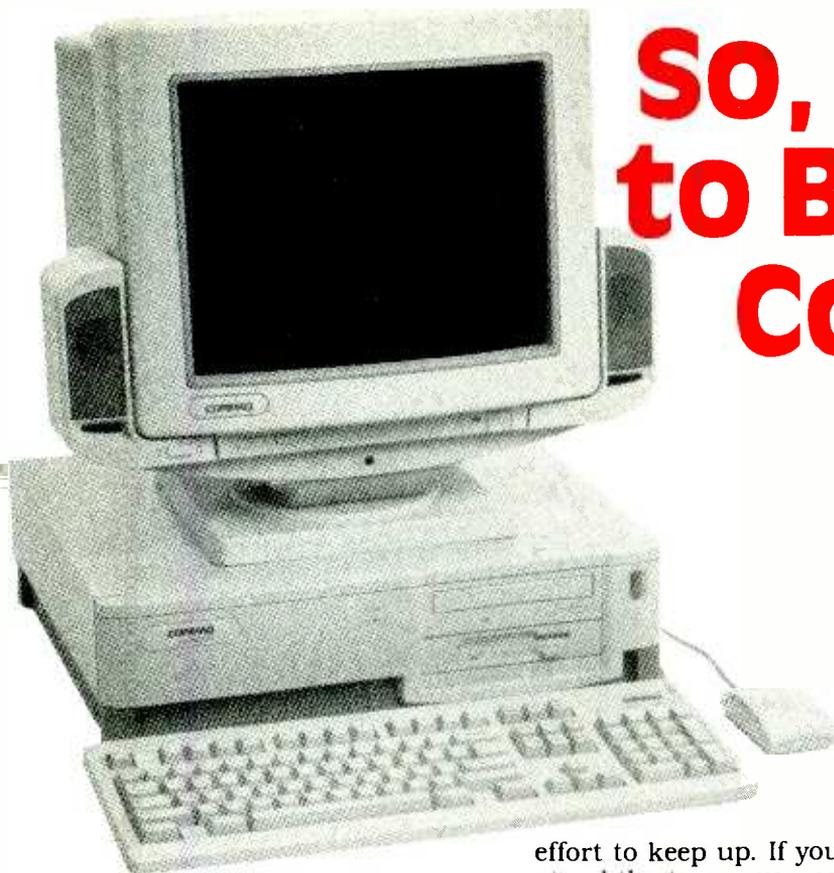

EVEN IF YOU RARELY WATCH TV, you've probably seen the commercial in which a pair of elderly Frenchmen stroll on the banks of the Seine chatting—not about their health, but about their computers' storage capacities. They conclude that only lasers can fulfill their deepest desires. This IBM advertisement has English subtitles. But even the subtitles can seem to be in a foreign language unless you're computer-savvy enough to know that they're talking about CD-ROMs.

If TV advertisements such as those in IBM's "Solutions for a Small Planet" campaign are mildly baffling, print advertisements and live computer salespeople often speak an even more arcane dialect, slinging around jargon like "ASPI" and "RISC" until even veteran nerds can feel bewildered. Unless you understand the language like a native, you're at the mercy of salespeople to translate the computerese for you. Unfortunately, even technically knowledgeable people can find themselves out of touch with new computer terms unless they make a conscious

effort to keep up. If you understand the terms, you can make up your own mind as to what you really need when you buy a new computer—and what fancy features you can easily forego.

The CPU

The most important consideration in choosing a computer is what type of central processing unit (CPU, processor, or microprocessor) it should have. The CPU determines how much your system will cost and how fast your applications will run. CPUs are usually referred to not by names, but by numbers that are a sort of shorthand indication of their speed, power, and capabilities. The CPU's speed isn't the same as its power, however. For example, a 100-MHz 486DX4 can't perform as fast as a 60-MHz Pentium. Today, most PCs run Intel's Pentium or i486 CPUs, or clones of those devices.

The i486 processor. The i486 family of processors, invented by Intel and now cloned by AMD and Cyrix, is the workhorse of the industry. The group includes the 486SX, 486DX, 486DX2, and 486DX4. The SX and DX chips are identical in

every way, except that the DX processors have a built-in floating-point unit (FPU) math coprocessor, and the SX chips don't.

All 486 processors have an external bus width of 32 bits. (A bus is multiple parallel conductors that transfer data between components of a computer system so that they can work together.) The speed of a 486 processor is the rate at which the chip's internal electronics run, which is not necessarily the same as the speed of the motherboard. Older processors, such as the 486SX and 486DX, run at the same speed as the motherboard. The newer processors have clock-doubler (DX2) or -tripler (DX4) circuitry to synchronize the CPU's internal clock with the motherboard's clock, so they can run at twice or three times the speed of the motherboard. (Note that despite its moniker, the 486DX4 doesn't run at four times the motherboard's clock, but three times instead.) The chips' designations (for instance, 486DX2-66, 486SX2-66) reflect the presence of the clock-multiplier.

The members of the 486 family have a 64-bit internal architecture, so they can process instructions and data 64 bits at a time. However, they have only

a 32-bit interface. This is why these CPUs are not always as fast as their names make them sound.

Pentium power. The next step up in power is Intel's Pentium series. Unlike the i486 processors, Pentium chips support an external 64-bit interface, lending a noticeable gain in speed and power. The new architecture also makes full use of *superscalar* programming code that executes two or more instructions per clock cycle as opposed to one instruction per cycle for the i486 series.

Pentiums have six family members divided into two groups: the first consists of the 60-, 66-, and 75-MHz processors. The second group consists of the 90-, 100-, and 133-MHz processors. The 90-, 100- and 133-MHz Pentium processors are not only faster, but they include special features to manage power for "green" operation and to speed up communications between components. Intel has solved the Pentium's little math problem that you might have heard about, so it's unlikely you'll need to worry about chip-based arithmetic errors.

Intel alternatives. NexGen's Nx586 CPU is a low-cost Pentium alternative that's making waves in the mainstream PC market because its 32-kilobyte cache is twice that of the Pentium and four times that of the 486. The bigger a CPU's built-in cache, the faster many applications run (see Table 1). NexGen's RISC processor is 100 percent compatible with all Intel-based processors from the 8088 through the Pentium, and it runs a tad faster than a Pentium processor of equal speed. Unfortunately, it doesn't have a built-in math coprocessor, though it does support an external one.

Popping up frequently in computer ads is the PowerPC, a CPU that was developed jointly by Apple, IBM, and Motorola. PowerPC models (which range from energy-conserving units suitable for laptops, through those for desktops and on up to

TABLE 1—CPU COMPARISONS

CPU	Data Bits	Top Clock Speed	Cache Size	Math Coprocessor
DEC Alpha R4000/R4400	64	275 MHz	—	yes
Pentium	64	150 MHz	—	yes
NextGen Nx586	64	100 MHz	16K	yes
PowerPC 486DX4	64	90 MHz	32K	external
486DX2	64	110 MHz	32K	yes
486SX2	32	100 MHz	8K	yes
486DX	32	66 MHz (1)	8K	yes
486SX	32	66 MHz (1)	8K	no
	32	50 MHz	8K	yes
	32	33 MHz (2)	8K	no

1) AMD 486DX2 and 486SX2 chips run at 80 MHz.

2) AMD 486SX chips run at 40 MHz.

TABLE 2—OPERATING SYSTEM COMPARISONS

Operating System	Windows 95	Windows NT	O/S2 Warp	Windows 3.1	DOS 6.22
Minimum Ram Required	8 MB	8 MB	4 MB	640 K	90K
Disk Space Used	60 MB	66 MB	40 MB	6 MB	5 MB
Password Security	Y	Y	Y	N	N
Runs DOS Applications	Y	Y	Y	Y	Y
Runs Windows Applications in Real Mode	Y	N	Y	Y	N
Runs Windows Applications in Standard Mode	Y	Y	Y	Y	N
Runs Windows Applications in Enhanced Mode	Y	Y	Y	Y	N
Runs 32-bit Applications	Y	Y	Y	N	N

high end workstations) include superscalar microprocessor design that can perform three to four instructions per clock cycle.

Power-PC based systems are also DOS-, Windows-, and Macintosh-software compatible, so if you've got a Mac in the office and a PC at home (or vice versa), you can take your work home and slave around the clock without incompatibility hassles. The manufacturers claim that the PowerPC is faster than a Pentium. However, only the very few applications written specifically for the Power PC run rapidly. Other programs shuffle along in an emulation mode, at about the same poky pace as they'd run on an old 386.

Far faster and more powerful (and costly) are the Alpha and





R4000/R4400 processors. Touted as the fastest desktop processor on earth, the Alpha chip from DEC (Digital Equipment Corp.) blasts off at a sizzling 275 MHz. The more conservative R4000/R4400 CPUs from MIPS run at a tamer 150 MHz.

All three of these devices are RISC processors. However, like the PowerPC, these rockets reach escape velocity only with the few programs that, as yet, have been designed especially for them. However, a special version of Windows NT, called Windows NT 3.5 Workstation, lets you run your present library of DOS and Windows software on computers based on these RISC microprocessors at about twice the speed of a 60-MHz Pentium.

Continued on page 139

Dress Up Audio Projects With Solid-State Level Indicators

ROBERT C. RICHARDS

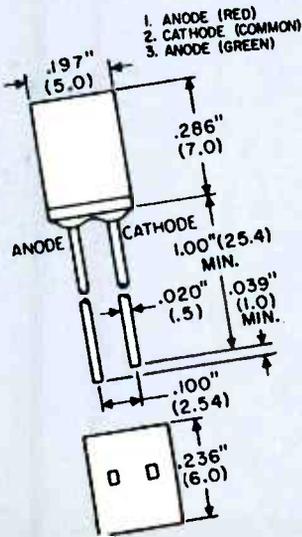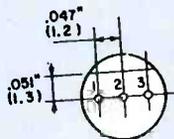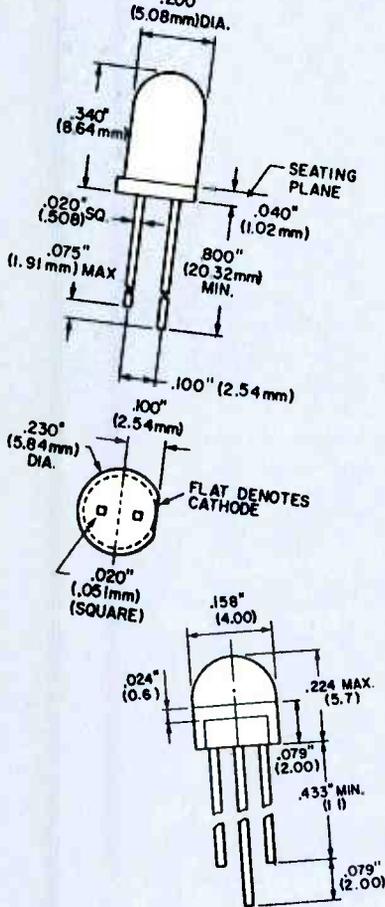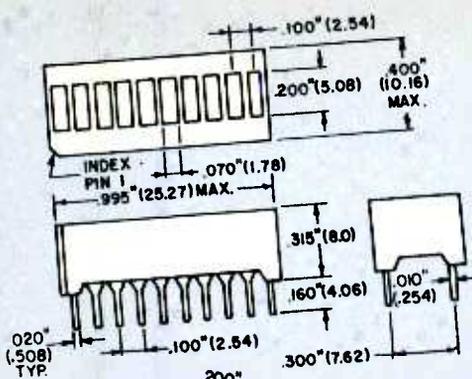

THE D'ARSONVAL (MOVING NEEDLE) analog meter has been the instrument of choice for setting input levels in audio systems for years. Now that most audio equipment has been miniaturized an analog meter will no longer fit on the front panel of the equipment.

This role has been filled by light-emitting diode circuitry. Solid-state level indicators based on a string of LEDs instead of a moving-coil meter are now included in most consumer audio products: from tape decks to baby monitors. They are small, lightweight, inexpensive, and immune to shock damage that could damage an analog meter's delicate meter movement.

This article describes three different methods for adding solid-state LED level indicators to your audio projects. In each, the level indicator selected gives the equipment a more professional appearance than in the original project while providing a useful function.

Typical amplifier

Figure 1 is a block diagram of a typical audio amplifier. The input signal is applied to an adjustable-gain amplifier stage. This first stage raises the voltage of the input signal to a higher audio level for the power amplifier stage, and the amplifier's gain is controlled by the operator with a front-panel knob. The output of this first stage is fed to a power amplifier that drives a loudspeaker. The gain in the adjustable amplifier stage must be high enough to allow the signal from the loudspeaker to be heard after the power amplifier has been amplified. However, this gain must not be so high that the signal becomes clipped and distorted. There is also the possibility that the

loudspeaker could be damaged if it is overdriven.

The level indicator circuit shown in the dashed box (Fig. 1) is useful in alerting the user that the gain of the adjustable amplifier is set improperly. This circuit consists of a signal-averager stage that clips audio signal peaks for a smooth display and an LED level indicator display consisting of from one to ten LEDs. By observing this LED display, the operator can adjust the amplifier for minimum distortion and proper operation.

Signal averager

The signal averager circuit in Fig. 2 will be shared by all of the LED level indicators described in this article. The operational amplifiers are general purpose types. The TL072 dual operational amplifier will save PC board space, and it is a reliable, inexpensive, medium-quality device. The first operational amplifier, IC1-a, is an inverting amplifier whose gain can be adjusted up to 5. Adjustable feedback resistor, R2, sets the circuit gain. It is a PC-board-mounted trimmer that is set once and never adjusted again.

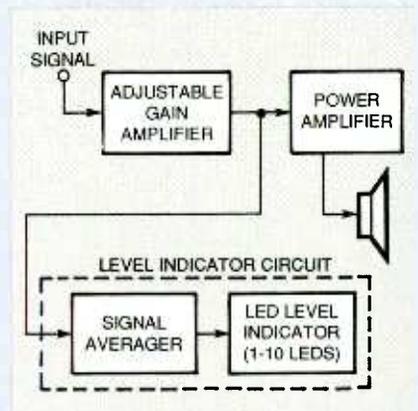


FIG. 1—A TYPICAL AUDIO AMPLIFIER block diagram with a LED level indicator circuit added.

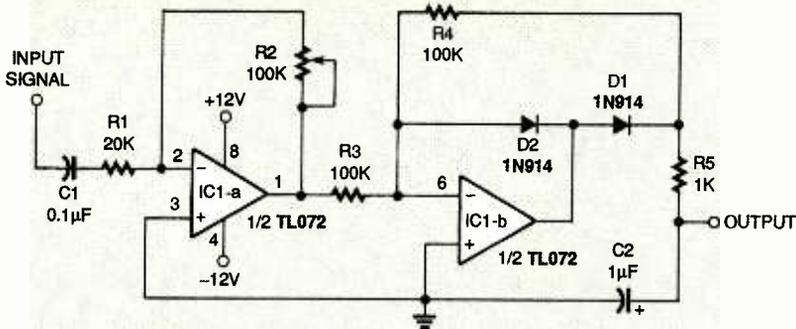


FIG. 2—A SIGNAL-AVERAGER circuit for use with the LED level indicator circuits discussed in the text.

This gain stage links a specific input voltage level to a specific LED indicator.

The second operational amplifier, IC1-b, forms a half-wave rectifier and signal averager that clips the brief peaks and displays them over a longer period of time. By stretching out and smoothing those peaks, as seen on the LED-level display, it will be easier to set the input adjustable-gain amplifier, IC1-a.

One-color LED peak indicator

The simplest solid-state level indicator is a single LED that flashes ON when the input level is high enough to drive the remaining audio stages. However, if you install only one LED, it is more important that it be used to alert the operator to an overload condition. The input level can then be reduced to avoid signal clipping and distortion. It can also reduce the possibility of damage due to excessive heat in the power amplifier and speaker. Most commercial amplifiers have indicators that will signal an overload before the level is high enough to cause an overload. This margin of safety is called *headroom* and it protects the equipment from the consumer who isn't satisfied unless the peak LED flashes occasionally.

The single-color, peak LED circuit is shown in Fig. 3. Unlike the TL072 operational amplifier discussed previously, the LM339 is a comparator. As shown in Table 1, whenever the voltage at the inverting input (labeled “-”) of the LM339 is higher than the voltage at the

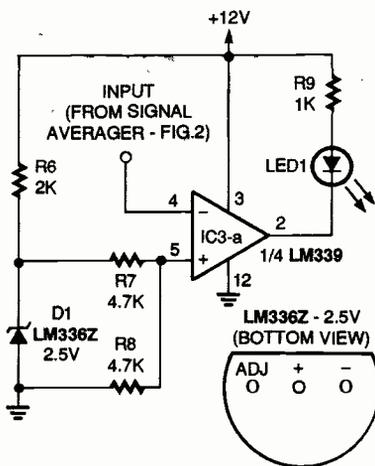


FIG. 3—A SINGLE-COLOR LED peak indicator circuit.

TABLE 1—COMPARATOR OUTPUT STATES

Inverting Input (-)	Noninverting Input (+)	Output
3 Volts	1 Volt	Ground
1	3	Float

noninverting input (labeled “+”), the output of the comparator is internally grounded. However, whenever the voltage at the inverting input is lower than the voltage at the noninverting input, the output of the comparator floats (effectively an open circuit) and no current flows.

The voltage divider consisting of resistor R6 and 2.5-volt precision voltage reference IC2 form a precision voltage reference whose voltage is divided in half at the junction of resistors R7 and R8. This places a reference voltage of 1.25 volts at the comparator noninverting input. Whenever the inverting input

put voltage exceeds the reference voltage, the output will be connected to ground internally and LED1 will light. By connecting the input of this circuit to the output of the averager circuit, the LED will flash on whenever the audio input exceeds the level set with gain potentiometer R2 in Fig. 2. Adjust R2 by applying a maximum level signal to the input of the averager, and then reduce the level slightly to allow for headroom. With the input level now set, adjust R2 until the peak LED just turns on.

Usually the maximum audio level can be determined by listening carefully to the loudspeaker's output. If this method is not sensitive enough for proper calibration, connect an audio signal generator to the input and an oscilloscope across the loudspeaker's terminals. Examine the overload effects on sine-wave, squarewave and sawtooth-waveforms as you adjust the setting of R2.


Tri-color LED level indicator

Some LEDs will light in three colors. Tri-color LEDs have two LED dies in one package (generally one red and one green) which are controlled indepen-

dently. By applying a voltage greater than about 2 volts to the separate pins, the LED can glow red, green, or yellow (when both dies are on). Figure 4 is a tri-color LED circuit. With a low input level, LED2 is off. As the input voltage increases, LED2 turns on and first glows green, then yellow, and finally red.

Resistor R10 and 2.5-volt precision voltage reference IC4 provide a precision voltage reference that is further subdivided by resistors R11, R12, R13, and R14. This chain of resistors creates three different reference voltages that set the voltage thresholds for the three LED

continued on page 148

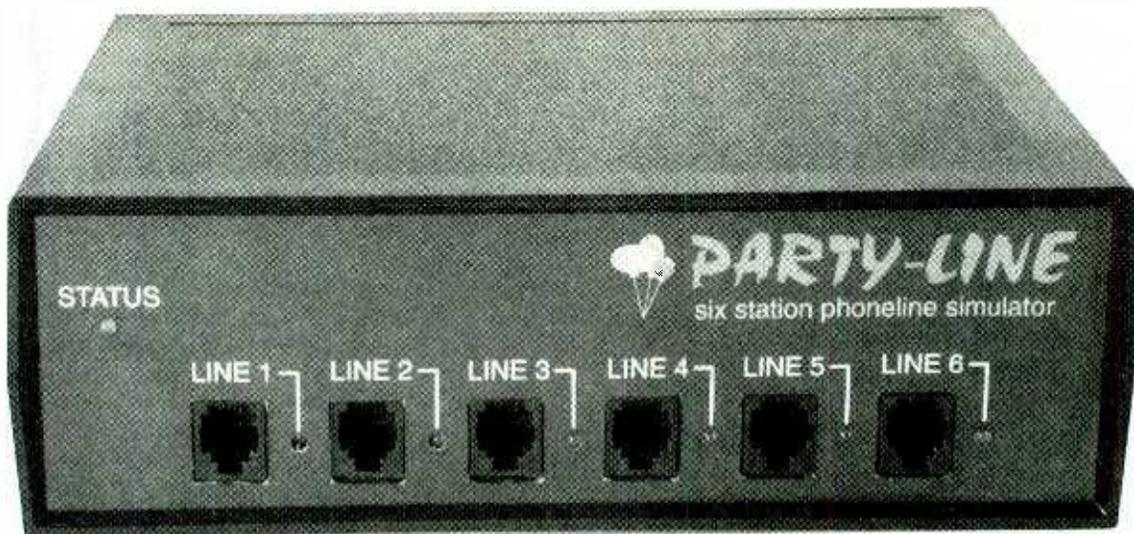

BUILD THE PARTY LINE

Build the ultimate telephone-line simulator

"HEY FRED. CALL ME RIGHT BACK. I'm having trouble with my new telephone gizmo, and I need some test calls." Have you ever found yourself begging friends to call so you could test a new piece of phone gear? Given the number of telephone gadgets we all use these days, it would be great if there was a phone-line simulator that could provide authentic dial tone, ring, and busy signals. Even better would be support for features like Caller ID and Distinctive Ringing. Maybe it could be used as the hub of an in-house intercom as well. Oh yeah—it has to be inexpensive too; who wants to spend \$500–800 for a commercial line simulator?

Party Line is the answer. It's probably the most sophisticated line simulator in its class, and it can be built for less than half the cost of typical low-end commercial units. Of course, some of the savings are due to a little sweat equity, so get your soldering iron ready!

Party Line supports all standard telephone-system features. You can ring up telephones, fax machines, modems, and answering machines.

THOMAS E. BLACK

Just about anything that you can connect to a standard phone-line can be used with this handy device.

Party Line has a feature list as long as your arm; just describing all of its capabilities will take most of our space this month. Next time we'll continue with theory of operation and construction details. But if you're impatient to get started, we are printing the Parts List and Ordering Information this month. Complete and partial parts kits are available; we'll also publish patterns for the dual-sided PC board.

The heart of Party Line is a single-chip microcontroller. Object code for the microcontroller unit (MCU) is available from both the Gernsback BBS (516-293-2283) as file pl6.zip and the author.

Overview

Party Line offers six different telephone extensions (stations); you can freely call from one to another using several dialing methods. Only one call can be

active at a time, but any number of stations can participate (hence the name Party Line). Party Line does not support rotary dialing; all calls must be made using DTMF (dual-tone-multifrequency) tones. Party Line offers life-like dial, busy, and reorder tones. Also, the microcontroller generates an accurate 20-Hz ring tone to ensure reliable device activation.

Party Line also provides four different ring patterns, which provide compatibility with the Distinctive Ringing service now offered by some phone companies. In addition, Party Line can send Caller-ID signals, a feature normally offered only by expensive line simulators. The Caller-ID information may optionally include the latest delivery format, which transmits, along with the standard date, time, and number, the caller's name! Furthermore, Party Line generates standard call-progress tones (dial tone, busy signal, ringing, etc.), so you can use the device to demonstrate and test telephone equipment. In fact, with Party Line, it's almost impossible to tell that you aren't using a real phone system.

PARTS LIST

All resistors are 1/4-watt, 5%, unless otherwise noted.

R1, R39, R40, R43, R46—1000 ohms
 R2, R4, R6, R8, R10, R16—220 ohms
 R3, R5, R7, R9, R17, R21, R48—330 ohms
 R11, R12—220 ohms, 2W, 5%, metal oxide
 R13—R15, R18—R20—220 ohms, 1/2W
 R22, R35, R37, R50—R52—10,000 ohms
 R23, R24, R41—47,000 ohms
 R25—R34, R36, R47, R54, R55—100,000 ohms
 R38—22,000 ohms
 R42, R44—100 ohms
 R45—2.2 ohms
 R49—470 ohms
 R53—300,000 ohms

Capacitors

C1—0.47uF, 200V, metallized polyester
 C2—C4, C6, C8, C15—C17, C25—C27—0.1uF, 50V, monolithic, radial
 C5, C19, C20—0.47uF, 50V, electrolytic, radial
 C7—0.001uF, 50V, polyester, radial
 C9, C24—470uF, 50V, electrolytic, radial
 C10—2200uF, 16V, electrolytic, radial
 C11, C18, C22, C23—10uF, 16V, electrolytic, radial
 C12—C14, C28—27pF, 100V, COG ceramic
 C21—1000uF, 25V, electrolytic, radial

Semiconductors

D1—D7—1N914 signal diode
 D8—D13—1N4002 rectifier, 1A, 100V
 BR1—50V, 1A, W005 or equiv.
 LED1—LED7—Green LED, 3mm
 Q1—TIP110 NPN Darlington transistor
 Q2—TIP115 PNP Darlington transistor
 Q3—PN2222A NPN transistor
 IC1—IC6, IC13—Optoisolator, NEC PS2501-1 or equiv.
 IC7—74HC259 or 74HCT259 addressable latch
 IC8—ULN2003 Darlington array
 IC9, IC11—74HC14 or 74HCT14 hex inverter
 IC10—PIC16C57-XT/P 8-bit Microcontroller, Microchip Tech.
 IC12—LM358N dual low-power op-amp
 IC14—M-991 Call progress tone generator, Teltone Corp.
 IC15—M-8870 DTMF decoder, Teltone Corp.
 IC16—LM317T adjustable regulator
 IC17—LM7812 or LM78M12, 12V regulator
 IC18—LM7805 or LM78M05, 5V regulator

Other components

F1—0.5A, 5 x 20mm fuse
 J1—J6—Modular RJ11, 6/2 or 6/4 receptacle, PCB Mount
 J7—1 x 3, 0.1-inch female header
 JU1—JU4—4 x 2, 0.1-inch pin header

with shorting blocks

P1—1 x 3 0.1-inch pin header
 XTAL1—3.5795 MHz, HC18
 RY1—RY6—DPDT, 12V, DC, 16—20mA coil, DIP package (OMRON G6A-234P-ST15-US-DC12 or equiv.)
 T1—Transformer, split bobbin, dual 115-VAC to dual 6.3-VAC, 2.5VA (Prem SPW401D, Magnetek/Triad FS12-200, or equiv.)
 T2—Telephone coupling transformer, 600:600 (PREM SPT130, Mouser TL016, or equiv.)
 T3—Power transformer, 28VAC center tapped, 300mA

Miscellaneous

IC sockets, 4/40 hardware, TO-220 heatsinks (2 each for IC17 & IC18), AC power cord, 2.5-inch H x 8-inch W x 6-inch L plastic enclosure, PC board, IC sockets, solder, wire, etc.

ORDERING INFORMATION

The following items are available from Digital Products Company, 134 Windstar Circle, Folsom, CA 95630, Voice: (916) 985-7219 Fax: (916) 985-8460. E-mail: DigProd@aol.com
KITS: Parts kit including printed-circuit board, programmed microcontroller, relays, transformers, IC's, resistors, capacitors, documentation, etc., less enclosure: (\$199.95). Enclosure kit includes plastic case, drilled front panel, mounting screws, etc. (\$32.95). Hard-to-obtain IC's, including M-8870, M-991, ULN2003, 74HC14 (2), 74HC259, PS2501-1 (7): (\$31.25). Line transformers (T1, T2) and relays (RY1—RY6): (\$48.50), power transformer kit with T3 (120VAC only), fuse, AC cord: (\$14.75).

PARTS: Printed Circuit Board #PL6-001: (\$34.95). Programmed PIC16C57 (\$22.00). Complete documentation with schematic: (\$7.25). U.S. orders add \$8 S/H for Kits, or \$5 for Parts. Canadian orders add \$14 for Kits, \$9.50 for Parts. Write or fax for shipping information to other countries.

Prices shown in USA dollars. Remit U.S. funds only. CA residents add local sales tax. Money orders, checks, MasterCard, Visa, American Express, and Discover Card accepted. Personal and company checks require bank clearance before shipment and may delay orders 2-3 weeks. Prices and terms subject to change without notice.

mally, if a device works on a POTS (plain old telephone service) line, then it should work with Party Line too. However, some telephone equipment is very particular to telephone-line characteristics, and hence may not work reliably with Party Line. For example, some devices require high talk-path voltages (>28 Volts DC), high line current (>25 mA), or true sinusoidal ring waveforms. Incompatibilities are rare because most vendors use intelligent designs that tolerate varying line signals. If a problem does occur, we suggest trying a different brand of equipment.

One unique Party Line application is as a personal intercom system. Just plug in some inexpensive telephones (or use the second line on some two-line phones), and outfit every room in your home or small office with a direct-dial intercom. You could even add a Caller-ID display to see which extension is calling!

Now let's detail Party Line features: station-to-station and quick dialing; calling all stations; dial-tone silence and recall; Caller-ID identification, blocking, out-of-area, and corrupt checksum; and distinctive ringing.

Station to station dialing

Any station can call any other. If you dial an idle station, it will ring. However, if it is in use, you will hear an authentic busy signal. If you fail to finish dialing the full station number, then a reorder tone (fast busy) will be heard about twenty seconds after entering the last digit.

To maintain realism, both local (seven-digit) and long-distance (eleven-digit) formats may be used. The long-distance number must be preceded by a 0 or a 1.

The six stations are numbered 1-6, but each responds to ten different extensions. For example, Station 1 responds to extensions 10-19. Extension numbers are always two digits long, and must be positioned as the last two digits of the phone number. The extension num-

continued on page 128

Party Line is compatible with most standard telephone devices, including answering ma-

chines, voice mail systems, fax machines, modems, dialers, Caller-ID displays, etc. Nor-

Just like these Fully Trained Electronics Professionals



"Thanks to CIE I have tripled my previous salary, and I am now in a challenging and rewarding new field where only the sky is the limit."

Daniel Wade Reynolds
Industrial Electrician
Ore-Ida Foods



"CIE was recommended to me by my boss. It was appealing since I could study at my own pace at home and during business travel."

Dan Parks
Marketing Manager/Consumer Products
Analog Devices, Inc.



"I loved the flexibility CIE offered. It was the only way I could continue both school and my demanding job."

Britt A. Hanks
Director of Engineering
Petroleum Helicopters, Inc.



"I liked the way the school was set up with laboratory assignments to enforce conceptual learning. The thing which impressed me the most about CIE's curriculum is the way they show application for all the theory that is presented."


Daniel N. Parkman
Missile Electro-Mechanical Technician
U.S. Air Force



"Completing the course gave me the ability to efficiently troubleshoot modern microprocessor based audio and video systems and enjoy a sense of job security."

Tony Reynolds
Service Manager/Technician
Threshold Audio & Video

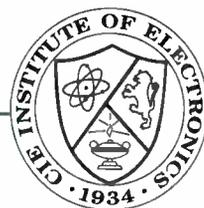Graduate with an Associate Degree from CIE!



CIE is the best educational value you can receive if you want to learn about electronics, and earn a good income with that knowledge. CIE's reputation as the world leader in home study electronics is based solely on the success of our graduates. And we've earned our reputation with an unconditional commitment to provide our students with the very best electronics training.

Just ask any of the 150,000-plus graduates of the Cleveland Institute of Electronics who are working in high-paying positions with aerospace, computer, medical, automotive and communications firms throughout the world. They'll tell you success didn't come easy...but it did come...thanks to their CIE training. And today, a career in electronics offers more rewards than ever before.

CIE'S COMMITTED TO BEING THE BEST...IN ONE AREA...ELECTRONICS.

CIE isn't another be-everything-to-everyone school. CIE teaches only one subject and we believe we're the best at what we do. Also, CIE is accredited by the National Home Study Council. And with more than 1,000 graduates each year, we're the largest home study school specializing exclusively in electronics. CIE has been training career-minded students for nearly sixty years and we're the best at our subject...
ELECTRONICS... IT'S THE ONLY SUBJECT WE TEACH!


CIE PROVIDES A LEARNING METHOD SO GOOD IT'S PATENTED.

CIE's AUTO-PRO-GRAMMED® lessons are a proven learning method for building valuable electronics

career skills. Each lesson is designed to take you step-by-step and principle-by-principle. And while all of CIE's lessons are designed for independent study, CIE's instructors are personally available to assist you with just a toll free call. The result is practical training... the kind of experience you can put to work in today's marketplace.

LEARN BY DOING...WITH STATE-OF-THE-ART EQUIPMENT AND TRAINING.

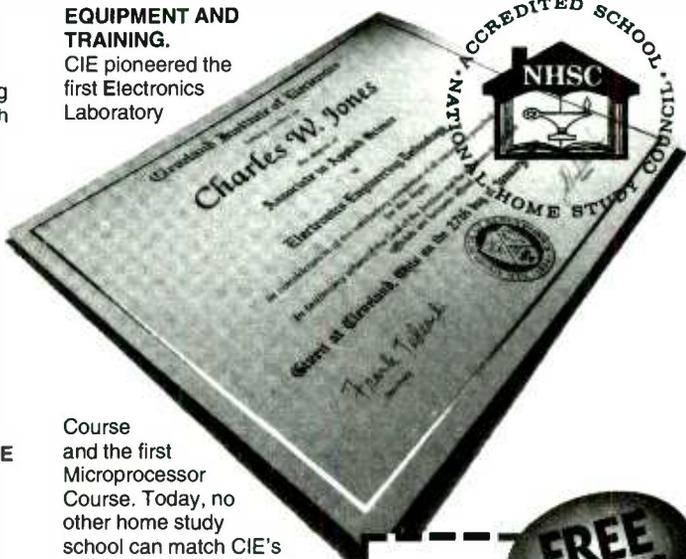CIE pioneered the first Electronics Laboratory



Course and the first Microprocessor Course. Today, no other home study school can match CIE's state-of-the-art equipment and training. And all your laboratory equipment, books and lessons are included in your tuition. It's all yours to use while you study and for on-the-job after you graduate.

PERSONALIZED TRAINING...TO MATCH YOUR BACKGROUND.

While some of our students have a working knowledge of electronics others are just starting out. That's why CIE has developed twelve career courses and an A.A.S. Degree program to choose from. So, even if you're not sure which electronics career is best for you, CIE can get you started with core lessons applicable to all areas in

electronics. And every CIE Course earns credit towards the completion of your Associate in Applied Science Degree. So you can work toward your degree in stages or as fast as you wish. In fact, CIE is the only school that actually rewards you for fast study, which can save you money.



YES! I want to get started. Send me my CIE course catalog including details about the Associate Degree Program. (For your convenience, CIE will have a representative contact you - there is no obligation.)

Please Print Clearly

Name _____

Address _____

City _____

State _____ Zip _____ Age _____

Phone No. _____

Check box for G.I. Bill Benefits.

Veteran
 Active Duty

AE82

Cleveland Institute of Electronics, Inc.
1776 East 17th Street
Cleveland, OH 44114

A School of Thousands.
A Class of One. Since 1934.

Send for CIE's FREE Course Catalog and See How We Can Help Your Career Too!

Aerovox®

DC Film and RFI Suppression Capacitors, Aluminum Electrolytic and AC Oil Capacitors, EMI Filters

AMP

Electrical/Electronic Connectors, IC Sockets, PCB Switches



Time Delayed Relays, Flashers, Timing Controls



Miniature and Subminiature Coaxial Connectors and Cable Assemblies.

AVX CORPORATION

A KYOCERA GROUP COMPANY

MLC, Tantalum and Thin Film Capacitors, Resistors, Networks, Integrated Passive Components, Trimmers, Oscillators, Resonators, Filters, Piezo Devices, and Connectors

CAROL

CAROL CABLE COMPANY INC.

Electronic and Electrical Wire and Cable and Power Supply Cords



Tubing, Conduits, Hose, Sleeveings, Splices, Insulation and Cable Harness Products, Power Cords and Cordsets

Communications Instruments, Inc.

CI Midtex

Relays and Solenoids

COOPER Bussmann

Fuses, Fuseholders, Fuse Blocks, and Fuse Accessories

CORNELL DUBILIER

Capacitors-Aluminum Electrolytics, Mica, AC Oil, Film, MICA Paper and Relays



Dale Electronics, Inc.

Resistors, Networks, Oscillators, Displays, Inductors, Thermistors, Connectors, & Transformers



FOX ELECTRONICS
Quartz Crystals • Clock Oscillators
Surface Mount • Programmable Devices

A
GERNSBACK
PUBLICATION

Electronics Now Magazine



GENERAL DEVICES
Electronic Hardware Manufacturers

MALLORY

North American Capacitor Company
Tantalums, Aluminums, Sonalcers® Ceramics, Films and AC's

M-tron

Quartz Crystals, Clock Oscillators, Hybrid Circuits



Fixed Ceramic Capacitors, Variable Capacitors and Resistors, Crystal Oscillators, Ceramic Filters, Resonators, EMI Filters, Hybrid Circuits and more.

Panasonic Industrial Company

Resistors, Resistor Networks, Ceramic, Film, Electrolytic, Double Layer Capacitors, Potentiometers, Switches, Inductors, Filters, Resonators, Varistors, Thermistors

Philips Components

Philips Electronics North America Corporation

Resistors, Ferrite Components
Aluminum Electrolytic, Film & Ceramic Capacitors



DC Film Capacitors, AC Suppression Capacitors

ROHM

Rohm Electronics Division
Monolithic ICs, Hybrid ICs, Transistors, Diodes, LED, Sensors, Laser Diodes, LCD, Printheads, Resistors, Capacitors



Tantalum Capacitors, Wet & Foil Capacitors, Resistor Networks, Resistor Capacitor Networks, Filters



Monolithic Ceramic, Chip Capacitors

How to keep Production happy, Marketing bullish, and Management ecstatic

DI DANTONA INDUSTRIES, INC.

Batteries: Computer, Cordless Phone, Laptop, Scanner, Alarm and Medical
Antennas: Cordless Phone and Scanner



DEARBORN WIRE AND CABLE L.P.
Wire • Cable • Insulation
Tubing • Cord Sets

EATON

Eaton Corporation, Commercial & Military Controls Operation
Switches, Relays, Displays and Keyboards

KEMET

Electronics Corporation

Multilayer Ceramic and Solid Tantalum Capacitors

KOA SPEER

Resistors, SMT Tantalum Capacitors, Inductors, Resistor Networks, SMT Thermistors

Littelfuse®

CIRCUIT PROTECTION DEVICES

Buy—and sell—electronic components through distribution

The sponsors of this message, proud members of the EIA Components Group, understand that top service to customers requires effectively involving distributors as part of their marketing teams.

Distributor involvement produces lower prices, quicker deliveries, better service overall. The buyer wins...the seller wins.

Leadership stems from not only designing products better and manufacturing them better, but also from marketing them better. And that means selling through distributors.

Leadership is also fostered through the manufacturer's involvement in the Components Group of the Electronic Industries Association. EIA fosters better industry relations, coherent industry standards, and the sharing of ideas. This not only helps us; it also helps you, the customer.

Do it right. Buy through distribution. Sell through distribution. And belong to EIA!



Electronic Industries Association
Components Group
2500 Wilson Blvd.
Arlington, VA 22201
Phone: (703) 907-7536
Fax: (703) 907-7501

Committed to the competitiveness of the American electronics producer.

RAY MARSTON

SINEWAVES CAN BE PRODUCED BY synthesizing them from either digital or analog waveforms. This second article on sinewave generation is about sinewave synthesizers, function generators, and inductance capacitance (LC) oscillator circuits. It picks up from last month's article about resistance-capacitance (RC) sinewave generators that focused on Wien-bridge and twin-T oscillators.


Sinewave synthesizers

Figure 1 is a block diagram of a 1-kHz digital sinewave synthesizer comprised of five D-type flip-flop circuits in a Johnson counter. It is accompanied by the waveforms that would be obtained at four different locations, A, B, C, and D. The figure illustrates how a sinewave can be generated digitally by refining a coarse sinewave in a series of digital steps and then filtering out all of the digital signal's high-frequency components.

In this example, a clock signal is fed to the input of a five-stage Johnson counter. Four of the counter outputs are added together with a resistor network to produce a coarse sinewave which is then converted into a reasonably pure waveform by low-pass filter capacitor C1.

The sinewave output frequency of this circuit is one-tenth of its input clock frequency. To understand this circuit, recall that digital signals generate only odd harmonics. Thus, the harmonics that must be eliminated to obtain a reasonable sinewave are the ninth, eleventh, nineteenth, twenty-first and higher. These are easily filtered out by capacitor C1.

Figure 2 is a simple, low-cost, 1-kHz digital sinewave synthesizer based on a CD4018B CMOS presetable divide-by-N counter. This CMOS monolithic integrated circuit, designated IC1, was developed by RCA but is now produced by Harris Semiconductor and other alternate sources. The sinewave synthesizer also contains Q1, a 2N3904 NPN transistor, that

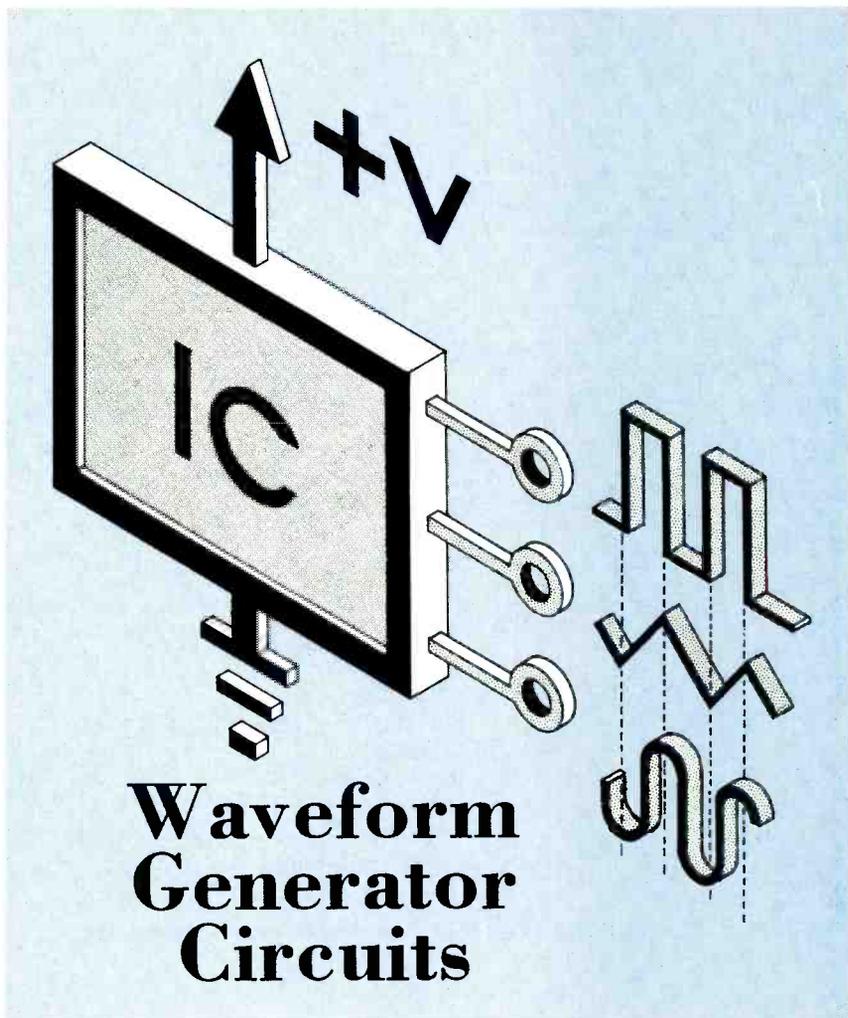

Learn about waveform generation with synthesizers, integrated-circuit function generators, and LC oscillators, and apply that knowledge to your projects.

converts an external 10-kHz input signal which is compatible with the signal on clock pin 14.

The lowest significant harmonic of this circuit's 1-kHz output is the ninth harmonic, at -36 dB relative to the fundamental frequency. (This sinewave has about 2% distortion.) If capacitor C1 is replaced by a second-order low-pass filter, all harmonics are attenuated 65 dB with respect to the fundamental, resulting in high-quality sinewaves with about 0.1% distortion.

Sinewaves can also be synthesized from linear triangular waveforms. Integrated circuits,

available from many sources, will perform this function. One example is the ICL8038, a precision waveform generator made by Harris Semiconductor and alternate-sourced by four other manufacturers. Another example is the XR-2206, made by Exar Corporation and alternate-sourced by at least three other manufacturers.

The Harris ICL8038

The ICL8038 waveform generator can produce accurate sine, square, triangular, sawtooth, and pulse waveforms with a minimum of external components. The frequency or repeti-

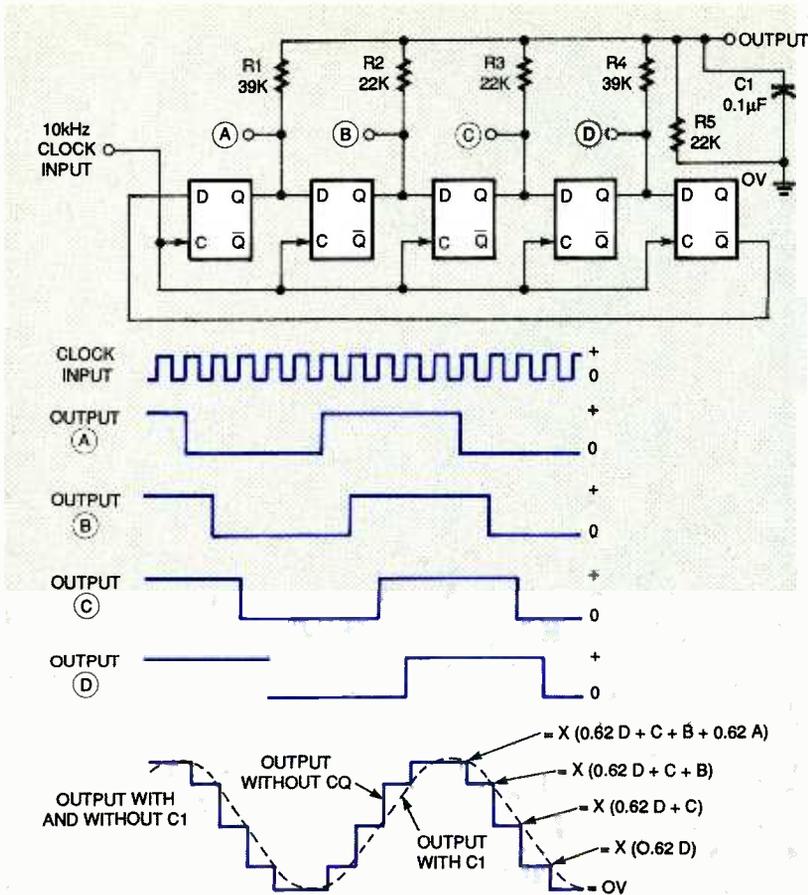


FIG. 1—CIRCUIT AND WAVEFORMS for a 1-kHz digital sinewave synthesizer.

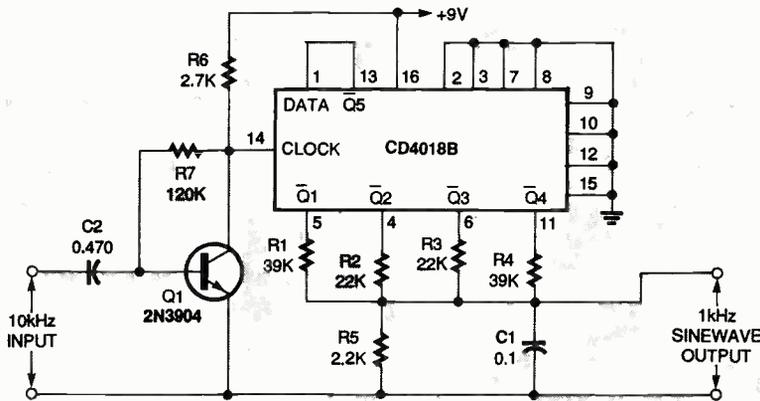


FIG. 2—A 1-kHz DIGITAL SINEWAVE synthesizer circuit.

tion rate can be selected externally from 0.001 Hz to more than 300 kHz with either resistors or capacitors. An external voltage will permit frequency modulation and circuit sweeping.

Figure 3 is the functional block diagram for the ICL8038. It contains two current sources (No. 1 and No. 2), two comparator circuits (No. 1 and No.

2), and a flip-flop. Square waves are obtained from a buffer fed by the flip-flop, and a second buffer is connected on the input sides of the parallel comparators to provide triangle waves. Sinewaves are obtained by passing the triangular waves through a sine converter.

Figure 4 is the pin configuration diagram for the ICL8038. It can be powered either from a

single power supply (10 to 30 volts) or a dual power supply (± 5 to ± 15 volts). The device provides sinewaves with only 1 % distortion and triangular waves with 0.1 % linearity.

Figure 5 is a schematic showing the ICL8038 configured as a sine/square/rectangle-wave generator powered from a single supply. Notice that in this diagram, the FM BIAS pin 7 is short-circuited directly to the FM SWEEP INPUT pin 8. With this configuration, the values of capacitor C1 and resistors R_A and R_B determine operating frequency. The resistors set the operating values of the two internal current sources that alternately charge and discharge external capacitor C1.

Refer again to the functional diagram Fig. 3. Current source No. 2 is switched on and off by a flip-flop, while current source No. 1 remains on continuously. Without going into detail on circuit function, the important point here is that external capacitor C1 charges at a rate set by R_A until its voltage reaches two-thirds of the supply voltage. At that time, the flip-flop is triggered and changes state. External capacitor C1 is discharged linearly at a rate set by R_B until its voltage falls to one-third of the supply voltage. The flip flop is then triggered to change state again and the whole process repeats again.

Resistors R_A and R_B can have values between 1 kilohm and 1 megohm. If these values are equal, the generator circuit runs at a frequency of $0.3/RC$. It generates a symmetrical linear triangular waveform with a peak-to-peak amplitude of 0.33 times the supply voltage on TRIANGLE OUTPUT output pin 3, and a squarewave with a peak-to-peak value of the supply voltage on SQUAREWAVE OUTPUT pin 9, which is loaded by load resistor R_L .

The triangle wave is fed to the IC's internal sine converter which produces a good sine-wave output. Those sinewaves will have a peak amplitude of $0.22 \times$ supply voltage at SINEWAVE OUTPUT pin 2 in Fig. 5

continued from page 130

Lamps and lighting efficiency

Plus a new RGB-to-NTSC converter, ultrafast computers, and product development concepts.

JUST GOT A HELPLINE CALL FROM AN "INVENTOR" TRYING TO "PROTECT" A "NEW" AUTO HEADLIGHT IDEA. TO STOP "DETROIT" FROM STEALING IT. I'VE NEVER HEARD OF "DETROIT" PAYING ANY OUTSIDER FOR AN

untested, undeveloped, or unproved idea. Instead, "Detroit" buys parts from suppliers, and bolts them together to make cars. Automobile manufacturers are in the process of outsourcing much of their product engineering. They are significantly *reducing* their number of suppliers, and holding them to the tightest of razor thin margins.

That's strike one.

Illumination engineering is one of the few things that Fortune 500 companies happen to do very well because it requires a multi-skill project team, combined with ray tracing computers, arcane production engineering, and outstanding access to the world's research base. So, those big boys clearly have an unbeatable home-turf advantage here.

That's strike two.

The most important requirement for any headlight advance is *efficiency*. It is becoming more important because of downsizing in general and electric or hybrid cars in particular. Anything less than 100 lumens per watt won't hack it. You can bet that tomorrow's headlights will *not* be based on a heated filament.

I got the impression the caller

was not a member of the SAE or the IESNA. Nor did he seem to be familiar with the relevant trade journals or to use online sources for research. He seemed to feel that car headlamp efficiency was "not important," and he apparently didn't have the slightest idea about

how woefully inefficient his new design was.

That's a swing and a miss for strike three.

A realistic alternative

Let's assume that you feel that you do have a great "new" headlamp design. What can you do that works out in the real world? Step one is to immerse yourself in relevant trade publications, industry associations, and online information sources so you can make sure that you weren't talking about a product that's been sold for

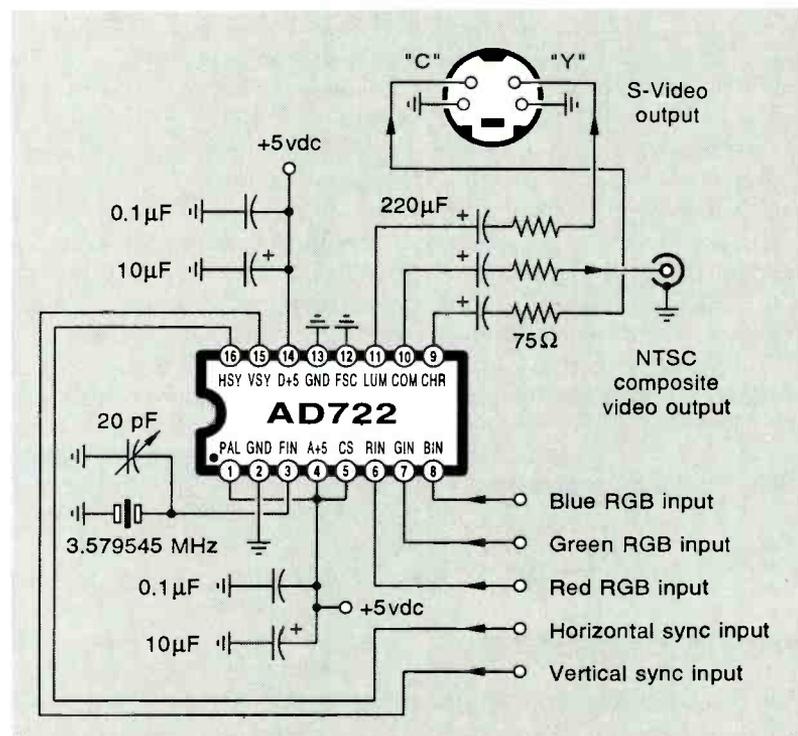


FIG 1—A NEW \$8 RGB-TO-NTSC CONVERTER CIRCUIT. Note that the input sweep rates, interlace, overscan, and program content must be TV-compatible if you want useful results.

decades—or one that long ago fell off the shelf because of inherent problems.

Step two is to ask yourself, “Who likes bright headlights, and have their own wallets in their own back pockets?”

Well, out here on my sand dune, the answer is glaringly obvious: four-wheel-drive desert off-roaders. To these folks, a map light is 50,000 candlepower, and a “running” light can vaporize troublesome boulders at 75 paces—on low beam.

So, first, you would have a few four-wheelers critique your design. If it is any good, you then let the local 4WD club beta test it. Once you have your tested and proven product well received, you sell a few at regional meets. Then you promote it in all the offroad magazines.

Next you seek out one or more of those off road lighting outfits. *K.C. Manufacturing* is but one of the name brand biggies out there. Competitors include *Dick Cepek*, *Hella*, *Explorer*, and *Piaa* corp. But be sure to remember the key insider secret rule for all successful new product development: *They must come to you*. And never vice versa.

Do note that you are *not* selling an idea. Ideas are worth ten cents a bale in ten-bale lots. Instead, you are offering a proven, in-demand, and a ready-to-manufacture product. You have already completed most of the high risk steps.

There is more of my thoughts on becoming a purveyor of risk reduction in RISKDOWN.PDF on my *Genie* PSRT. More thoughts on idea development in general are in my *Blatant Opportunist* and my *Case Against Patents* packages.

An RGB to NTSC converter

I get all sorts of helpline calls from folks who want to use an ordinary color TV set for their computer—instead of buying a pricey high resolution RGB monitor—preferably via the antenna input.

Well, these days, you just can't get there from here. The TV's resolution is too low and the computer screen information content is way too high. Why do you suppose computers are

equipped with all of those fancy high-resolution monitors in the first place?

No matter what you do, there is *no way* you that can display “ordinary” modern computer color spreadsheet or word processor output by RF entry on an unmodified television! All you will get is a hopelessly smeared and violently flickering illegible mess.

On the other hand, if you design your computer screen *content* to be consistent with what your TV set can reasonably and intelligently handle, then you certainly can display it. At least after format conversion. Thus, computers can be used for video titling, for *large* screen data or text, for video editing, for “slide show” presentations, or for abstract art effects.

Analog Devices has developed a greatly improved and easy to use AD722 single-chip RGB-to-NTSC encoder. I've shown a typical circuit in Fig. 1. You can use this IC to convert *already TV viewable* RGB computer output into signals a TV set can understand. But you *can not* use this (or any other scheme I know of) to let a TV replace a high-resolution monitor.

The NTSC TV broadcasting standard was conjured up decades ago to cram color information in to the same RF bandwidth as the monochrome signal and still be compatible with existing sets. This was done by creating a new color *subcarrier* frequency of 3.579545 MHz.

Because of the technology limits at the time, and the need to be backward compatible with existing TVs, the NTSC system required many compromises.

A color TV cannot display com-

HELP LINE

Phone or write all your Hardware Hacker questions to:

Don Lancaster
Synergetics
Box 809-EN
Thatcher, AZ 85552
(520) 428-4073

For fast PSRT access, Modem
(800) 638-8369. On prompt, Type
JOINGENIE. When asked for the
offer code, enter DMD524.

US Internet email access link:
SYNERGETICS@GENIE.GEIS.COM.

new from DON LANCASTER

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. \$28.50

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. THE two books for digital integrated circuit fundamentals. About as hands-on as you can get. \$24.50 each.

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. \$18.50

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. \$119.50

LOTS OF OTHER GOODIES

Ask the Guru I or II or III	\$24.50
Hardware Hacker II or III	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell	\$29.50
Intro to PostScript Video	\$29.50
PostScript Reference II	\$31.50
PostScript Tutorial/Cookbook	\$19.50
PostScript by Example	\$31.50
Understanding PS Programming	\$29.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking in PostScript	\$22.50
LaserWriter Reference	\$19.50
Type 1 Font Format	\$15.50
Acrobat Reference	\$24.50
Whole works (all PostScript)	\$380.00
PostScript Insider Secrets	FREE
Hacking Insider Secrets	FREE

POSTSCRIPT SECRETS

A Book/Disk combination crammed full of free fonts, insider resources, utilities, publications, workarounds, fontgrabbing, more. For most any PostScript printer. Mac or PC format. \$29.50

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. \$39.50

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This two volume set shows you tested and proven real-world alternatives. \$28.50

BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. \$24.50

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. \$24.50

FREE SAMPLES

Well, nearly free anyway. Almost. Do join us on *Genie* PSRT to sample all of the Guru's goodies. The downloading cost on a typical Guru file is 21 cents. Modem access: (800) 638-8369, then a JOINGENIE. Use DMD524 for your keycode.

FREE VOICE HELPLINE VISA/MC

SYNERGETICS
Box 809-EN
Thatcher, AZ 85552
(520) 428-4073

CIRCLE 205 ON FREE INFORMATION CARD

puter data because (A) its horizontal and vertical sync rates, are far too low, (B) it has a severely limited resolution that prevents more than a few dozen color changes on any screen line, (C) its interlaced display causes flicker that makes small characters unreadable, and (D) its overscan hides some of the display.

If you are able to resolve *all* of the problems mentioned, then building an RGB to NTSC converter makes sense. Otherwise, it does not.

Briefly reviewing, video on an RGB system is on separate red, blue and green lines. An extra line or two

when adjacent lines are fairly similar. Since this is *never* the case with small dot matrix characters, small text will flicker badly.

The NTSC signal is purposely overscanned, gruesomely so on older sets. The reason is that if the picture is wrapped around the side of the tube, there will be no possibility of seeing black stripes on the side. Thus *all* NTSC programming *must* guarantee that the useful stuff always ends up *only* in the *center*.

The chip is easy to use. You first apply the usual +5 volts at 30 milliamperes. Also connect pin one to

else put composite sync into pin 16 while making pin 15 positive.

If you have a 4× color subcarrier clock available, input it to pin 3. If not, you can hang a stock *parallel resonant* color burst crystal from pin 3 to ground. Note that resynchronizing to a local crystal may degrade your results.

A logic high on pin 12 selects the 43 subcarrier mode, a low picks the 13 mode.

Be sure to read the data sheet carefully. There are several nasty “gotchas” to getting this chip to interact with VGA and other standards.

Conventional TV receivers require a chroma *delay line* to compensate for color shifts; a circuit equivalent to a delay line is *included* on chip so the results end up nearly identical to a broadcast signal.

The outputs are all at *twice* normal amplitude, letting you directly drive a 75-ohm reverse-terminated load.

Most VGA sources have provision for control by software. Once again, your sync rates and picture content *must* be NTSC-compatible ahead of time, or you’ll get useless results.

Lighting Fundamentals

If you pick up any plain old 60 watt light bulb, it is likely to be rated around 850 *lumens*. That sounds like a bunch, until you find out what a lumen *really* is. Then you discover how badly you’ve been ripped off.

Well, a *lumen* is a measure of the *total output light power*. How many watts of light you will get back after gathering together all the output from all directions. (Well, usually, anyway. Some narrow-beam spotlights cheat and are rated in “effective lumens” instead.)

Being a unit of power, there is a relationship between the output light *lumens* and input electrical *watts*. This relationship also depends on the eye’s sensitivity to colors. The eye responds with the *luminosity curve* shown in figure two. Eye sensitivity is highest in the yellow-green range.

A lumen is defined as 0.001496 watts of yellow-green light. Or 668.5 lumens per watt. A 100% efficient 60 watt yellow-green light bulb can thus produce 40,110 lumens.

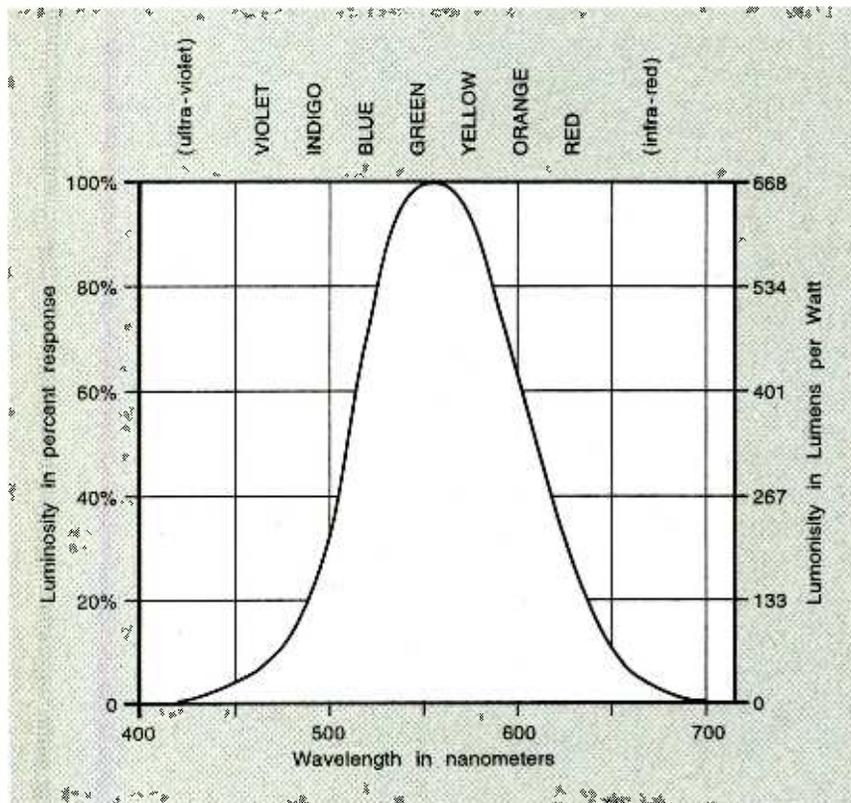


FIG 2—THE LUMINOSITY RESPONSE of the human eye varies with color. It is highest for yellow-green light, and lower for red and blue. White light sources are inherently less efficient than lime green ones.

is output for sync. Or else the sync gets combined onto your green channel. RGB scan rates are typically far higher than any TV can accept.

NTSC instead combines all of the picture information into a baseband black and white *luminance* signal and a color *chrominance* subcarrier.

The NTSC specification requires a pair of interlaced 262-1/2 line *fields* at a vertical sync rate of 59.96 Hertz. The horizontal scan rate is 15,735 Hertz. Interlace reduces flicker *only*

+5 to select NTSC instead of the PAL operation. The RGB outputs of your computer can be fed directly to the red, green, and blue inputs. Three outputs are provided: the composite video, a Y luminance output, and a C chrominance output. These latter two outputs can optionally get routed to an S-video connector.

In addition, you have to get sync and the stable color subcarrier from somewhere. You can input horizontal and vertical sync on separate pins. Or

Which means your plain old light bulb has a yellow-green efficiency of a mere 2.1%! When the other colors are considered, the total barely gets up to seven percent or so. A rating of *fourteen* lumens per watt, which is a result of nearly all the input energy being converted into useless heat.

One solution to efficiency improvement is to operate the lamp hotter. That works, but it also dramatically reduces lamp life. One workaround is the *halogen cycle*, once known as the “quartz-iodine” approach.

The result is still an incandescent lamp, but the “quartz” part means that the bulb temperature can be higher, and the “iodine” vapor part sets up a magic cycle that combines with any tungsten that is boiled off of the filament during hot times, forming a tungsten-iodide gas that is stable only when hot. The gas redeposits the tungsten right back onto the filament when it cools.

The result is a modest improvement in efficiency—Around 15% better for a 52-watt Halogen replacement lamp. The higher initial costs will eat into your energy savings, but the bulbs do last twice as long.

The larger Halogen lamps can produce up to 22 lumens per watt. Two big “gotchas” here: You must *never* touch a halogen bulb with your fingers. The oil from your skin causes a cold spot which can shatter the glass. And the lamps must *not* be continuously turned on and off. The halogen cycle only operates properly when the lamp remains on for hours at a time, with lots of cooling time between uses.

Improving efficiency

Actually, the correct term here is *efficacy*, since the output energy is in a different form from the input. There are many lamp technologies far more efficient than any incandescent. Figure three shows how all these alternates compare.

Light emitting diodes— Many new LEDs are actually *more* efficient than incandescent bulbs, and they last a lot longer, too. Cavers have long ago picked up on all of those orange superbright *Hewlett-Packard* diodes as

backup light sources. The automotive industry is very excited about LED tail lights, both because of their longer life and their “instant on” feature. The latter translates to some *twenty feet* of extra safety margin at thruway speeds.

There is no fundamental physical limit restricting LED efficiency. It is more economics, material science, visual coupling, total output, and a poor performance in the blue region of the spectrum that is holding things up.

Neon lamps— These are just a pair of electrodes in a glass enclosure that is filled with some inert gas such as neon (orange), xenon (blue), carbon dioxide (white), helium (purple), or mercury (green). A current causes a glow discharge and output light.

Neon lamps are potentially very efficient “cold light” sources. The lumens per watt depends on the color. Output power is normally low. High voltages are always required. More information on these is available in *Neon News*, *POP Design*, *Sign Craft* or *Sign Business* trade magazines.

Electroluminescent panels— These are another “cold light” source. Basically, an electroluminescent panel is a capacitor with a phosphor on one electrode. A high AC voltage (100-400 volts) is applied, and its field strength excites the phosphor. The panels can produce many colors, including white. A medium green is usually the brightest.

Best results are obtained at mid audio frequencies. Total light output

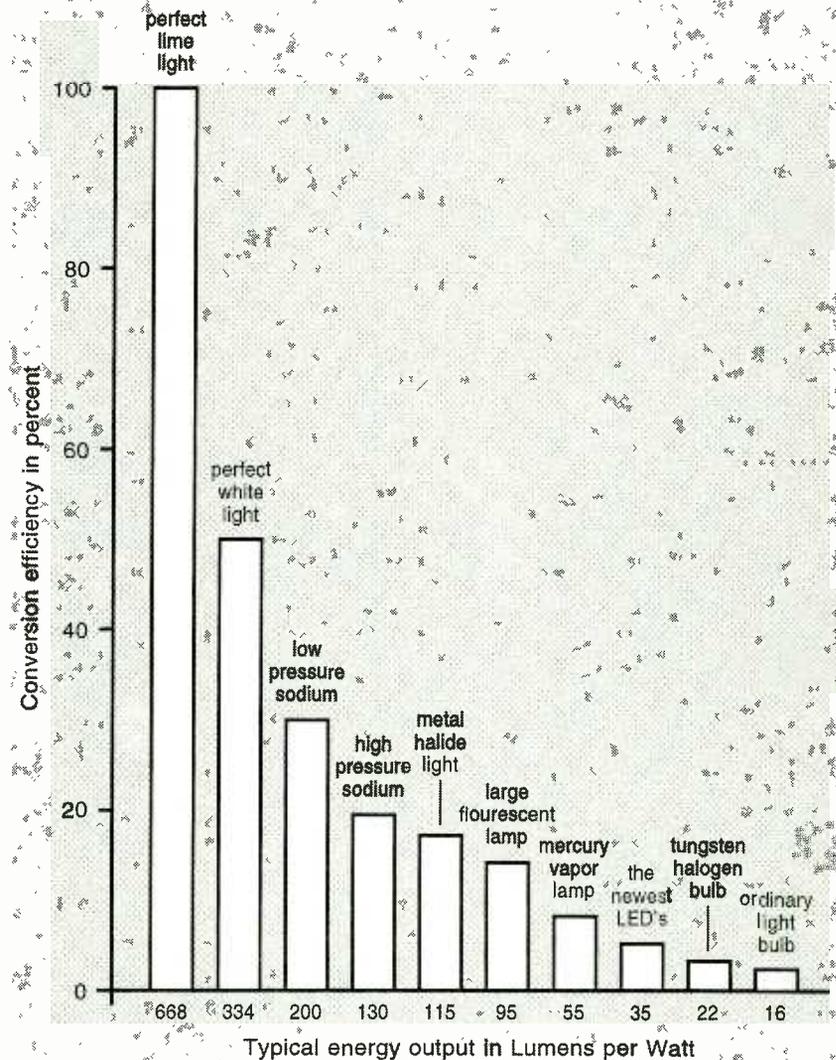


FIG 3—EFFICIENCY RATINGS for several emerging lamp technologies. Note that ordinary incandescent light bulbs are utterly awful.

LAMP AND LIGHTING RESOURCES

is low, and the power factor makes for big time drive problems. The panel brightness drops significantly with time and contamination. Not much seems to be happening lately in new developments here. *Loctite Luminescent* is one source of information and parts.

Fluorescents— A fluorescent lamp has a much better efficiency than any incandescent, up to 100 lumens per watt. A fluorescent lamp works in two stages. First an ionized plasma discharge generates strong and narrow band ultraviolet light. That invisible ultraviolet light then impinges on a phosphor which downconverts most energy radiation into the visible range.

Because fluorescent lamps are current operated, a regulator in the form of a magnetic or electronic ballast is required. Electronic ballasts do offer electrical efficiencies of 85 percent and higher. They also can excite the phosphor at higher frequencies, which can help the bulb to produce more light and less flicker. Dimming is a brand new electronic option.

RF fluorescents— The phosphor of these new bulbs is excited directly by a radio-frequency source. While it is too early to tell, the efficiency of RF fluorescent bulbs should be high, but the costs, circuit complexity, and RF-interface problems must be overcome. Watch for overblown hype and investment scams on these.

Mercury-vapor lamps— These lamps are just a tiny blob of mercury and two electrodes. The mercury is heated somehow, either by direct arcing, or by a gas discharge. The vapor supports a current-limited arc discharge. The bulbs produce a bluish white light. The efficiency is 50 lumens per watt.

Because all these lamps produce a dangerous amount of short wave ultraviolet light, safety filters are a must. The life of mercury-vapor lamps is extremely long at 24,000 hours. Color rendition is only poor to fair. I get the impression their popularity has clearly peaked.

Arc lamps— Those old carbon arc lamps offered very high brightness. Their efficiency is not half bad at 120 lumens per watt, but the traditional

Advance Transformer
10275 W Higgins Road
Rosemont IL 60018
708-390-5000

BHK
1000 S Magnolia Avenue
Monrovia CA 91016
818-357-9667

Bulbman
PO Box 2918
Reno NV 89505
800-648-1163

Bulbtronics
45 Banfi Place
Farmingdale NY
516-249-2272

Carley
1502 W 228th Street
Torrance CA 90501
213-325-8474

Dick Cepek
17000 Kingsview Avenue
Carson CA 90746
800-992-3735

EPRI Journal
PO Box 10412
Palo Alto CA 94303
415-855-2000

Explorer
14100 Kingsley Drive
Gardena CA 90249
310-719-7285

Gilway Technical Lamp
800 W Cummings Park
Woburn MA 01801
617-935-4442

Grainger
2738 Fulton St
Chicago IL 60612
312-638-0536

Gray
4415 Indianapolis Blvd
E Chicago IL 46312
800-238-2244

Hella
201 Kelly Drive
Peachtree City GA 30269
800-247-5924

Hewlett-Packard
PO Box 10301
Palo Alto CA 94303
415-857-1501

Home Power
PO Box 520
Ashland OR 97520
916-475-3179

IESNA
120 Wall Street 17th Fl
New York NY 10005
212-248-5000

JKL Components
13343 Paxton St
Pacomia CA 91331
800-421-7244

KC Lites
PO Box 155
Williams AZ 86046
800-528-0950

Lighting Design & Apps
120 Wall Street 17th Fl
New York NY 10005
212-248-5000

Lighting Research Institute
120 Wall Street 19th Floor
New York NY 10005
212-248-5014

Loctite Luminescent
Etna Road
Lebanon NH
603-448-3444

Neon News
PO Box 668
Volcano HI 96785
808-967-7648

PIAA Corp
15370 SW Millikin Way
Beaverton OR 97006
800-525-7422

Real Goods
966 Mazzoni St
Ukiah CA 95482
800-762-7325

Welch Allyn
4619 Jordan Road
Skaneateles Falls NY 13153

designs consumed carbon rods and needed continuous adjustment. And they did not scale down well.

The *Welch-Allyn* folks have come up with a newer sealed variant called a *short-arc* lamp. This 21-watt point source device offers 75 lumens per watt and is intended for scientific and fiber optic applications. A special ballast is needed. Because it is as much as

43 more efficient than halogens, this sealed lamp seems ideal for battery powered apps, but it's pretty expensive.

Metal halide lamps— By far your most popular bulb for commercial and industrial lighting, metal halide lamps offer efficiencies as high as 125 lumens per watt and good color rendition. Bulb life can approach 20,000

hours. Typical sizes vary from 25 on up to 2000 watts. Special ballasts are required, as is an ultra violet safety filter. The filter is often built into the glass itself. Expect to see these move into home and vehicular lighting.

I'd guess that these would be the obvious choice for most future auto headlights—until something better comes along.

Low-pressure sodium— A clear cut efficiency winner at 200 lumens per watt, these "street lamps" offer extremely long life, low running costs, and outstanding nighttime visual acuity. Astronomers love them because they can dramatically minimize visual pollution. Sadly, their distinctive orange color gives a mesmerizingly awful color rendition. Sizes as small as 18 watts are offered.

High Pressure Sodium— Another sodium lamp variant, this one trades off extreme efficiency for a greatly improved color rendition. At low gas pressures, the emission takes place in distinct spectral lines. As pressure increases, the lines first broaden, and then become more continuous. These can offer 120 lumens per watt with no ultraviolet filter hassles.

A 10,000 hour life is common. The sizes range from 35 up to 1000 watts. The cost is around \$90 in single quantities. Mercury-vapor ballasts can be used. Most operate in any position.

Lighting resources

I have gathered up a few lighting resources for you as this month's sidebar. Besides those I have already mentioned, a few deserve comment.

IESNA, which publishes *Lighting Design and Application* magazine plus a technical research journal, seems to be the main trade association. There is also a *Lighting Research Institute* in the same building.

The EPRI journal is by the *Electric Power Research Institute*, which offers fine reference materials.

The leading industrial source for lamps is *Grainger*. Graphics arts lamps are usually sold by *Bulbman*, *Bulbtronix*, *Gray*, and *HID Systems*, among many others.

Two manufacturers of the smaller lamps are *Gilway* and *Carley*. JKL is a

NAMES AND NUMBERS	
<p>Analog Devices PO Box 9106 Norwood MA 02062 617-329-4700</p> <p>Atmel 2125 O'Nel Drive San Jose CA 95131 408-441-0311</p> <p>Flexible Circuits 6195 Corte del Cedro #110 Carlsbad CA 92009 619-431-2869</p> <p>Focal Press 313 Washington Street Newton MA 02158 617-928-2500</p> <p>GENie 401 N Washington St Rockville MD 20850 800-638-9636</p> <p>Helix Books Addison-Wesley Reading MA 01867 617-944-3700</p> <p>Image Processing Resources PO Box 207 T or C NM 87901 800-735-3596</p> <p>Intel Corporation 2200 Mission College Blvd Santa Clara CA 95052 800-548-4725</p> <p>The Mart 899 Presidential #110 Richardson TX 75081 800-864-1155</p> <p>P-O-P & Sign Design 7400 Skokie Blvd Skokie IL 60077 708-675-7400</p>	<p>Power Transmission Design 1100 Superior Avenue Cleveland OH 44114 216-696-7648</p> <p>Riteco Supply 12999 FM 529 Houston TX 77041 713-896-6200</p> <p>Roland Users Group 7200 Dominion Circle Los Angeles CA 90040 213-685-5141</p> <p>SAE 400 Commonwealth Drive Warrendale PA 15096 412-776-4841</p> <p>Science/AAAS 1333 H St NW Washington DC 20005 202-326-6400</p> <p>Sign Business 1008 Depot Hill Office Pk Broomfield CO 80020 303-469-0424</p> <p>SignCraft PO Box 06031 Fort Myers FL 33906 813-939-4644</p> <p>Siliconix/Temic 2201 Laurelwood Road Santa Clara CA 95054 800-554-5565</p> <p>Synergetics Box 809 Thatcher AZ 85552 520-428-4073</p> <p>Tiare Publications PO Box 493 Lake Geneva WI 53147 800-420-0579</p>

good source for low cost miniature fluorescent lamps, while BHK offers specialized ultraviolet lamps. *Advance* is the leading ballast supplier.

Home Power is a fine magazine for off-grid lighting applications. A high-profile lamp and alternate-energy supplier is *Real Goods Trading*.

Please let me know if I missed any of your favorite sources here. A free *Incredible Secret Money Machine II* for your trouble.

A great read

I was impressed by *The Shoulders of Giants*, a history of early aviation. Written by Phil Scott and published by *Helix Books*.

There was a government aviation fiasco at the time of Kitty Hawk that cost hundreds of times more than the Wright Brothers' success. This program only succeeded in filling the Potomac River with broken bits and pieces of planes and pilots.

The Wright Brother's patent fights clearly set US aviation back far more than their early flights ever advanced it. For decades, even.

The initial transcontinental flight crashed so many times that only an original wing spar and most of the pilot actually ended up on the west coast. And, of course, the Red Baron failed his flight test three times.

continued on page 50

Return to reality

THE EDITORS HAVE GOTTEN ON MY CASE ABOUT THE ESOTERIC NATURE OF SOME RECENT COLUMNS. FINE: BACK TO THE WORLD OF BITS AND BYTES AND SOLDERING IRONS. TOPICS THIS MONTH

include Pentium updates and hard-disk utilization.

Pentium updates

Today's CPU of choice is the Pentium. It is currently available in speeds ranging from 75 to 133 MHz, with faster units (150- and 180-MHz) on the way. If you have an old 486-based computer that you aren't quite ready to part with, Intel sells various OverDrive CPU's, as either 486 upgrades or Pentium upgrades.

At the other end of the spectrum, Intel has announced the successor to the Pentium. If you were hoping for the next logical step (Sexium), you'll be disappointed. Depending on whether you run "true" 32-bit software, you may also be disappointed with performance.

For the 486 upgrade crowd, Intel appears to have done everything possible to confuse the issue. You can follow one of several upgrade paths: a clock-multiplied 486 or a Pentium OverDrive. The clock-multiplied 486 route provides a faster CPU, and in some cases a larger cache than the original CPU (16 kilobytes vs. 8 kilobytes). The Pentium OverDrive

route stuffs a ten-pound Pentium into a five-pound 486 socket.

In general, although an upgrade CPU can improve performance, in no case can it provide system-wide performance equal to that of a

comparable Pentium system. Both the CPU's efficiency at transferring data and internal software optimization of the CPU guarantee that a true Pentium will run faster at a given clock rate than any of the upgrades under discussion.

Nonetheless, recently published data suggests that CPU upgrades, particularly for lower-end 486 systems, can significantly improve performance. Figure 1 summarizes data recently published by the trade weekly *PC Week*. The diamonds represent the cost of each

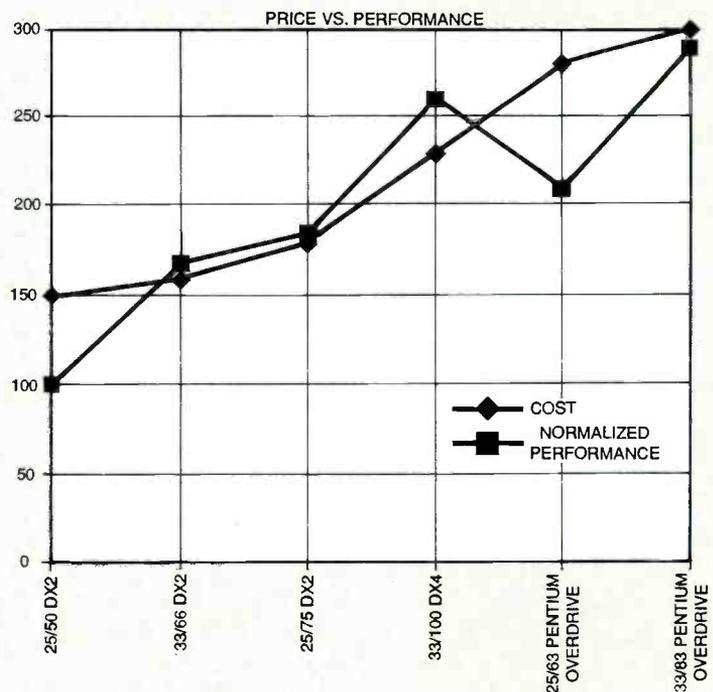


FIG. 1—THIS CHART SHOWS PERFORMANCE IMPROVEMENT percent over a base 486/25 system running application-level benchmarks. Source: *PC Week*, 9/18/95, p. 133.

upgrade level; the squares represent relative performance figures normalized to fit the vertical scale. Performance data is relative to a 25-MHz 486 system.

Several facts are clear. First is that the 25/63-MHz Pentium OverDrive provides poor value. Although its price is higher than its predecessor, it will actually degrade system performance.

Second, although the Pentium OverDrives generally provide better performance than DX2 and DX4 devices, the cost differential is out of line with the performance increase. For example, going from the 33/100 DX4 to the 33/83 Pentium increases cost by 23%, but increases performance only 12%.

The data presented in Fig. 1 is representative only; the original study cross-tabulated the results of upgrading from several CPU's to several others, and results are not consistent across all upgrade paths. In addition, the study unfortunately neglected to include processor upgrades from other manufacturers, including AMD, NexGen, Cyrix, Evergreen Technologies, and Kingston Technologies.

Nonetheless, several conclusions can be drawn. If you've got an old 25- or 33-MHz 486 system, you can obtain fairly good performance improvement by upgrading to a 100-MHz DX4 or 33/83-MHz Pentium OverDrive. The Pentium will provide the best overall performance, but the DX4 provides the best value. Also, if you already have a 25/50- or 33/66-MHz DX2 486, you'll see much more modest improvements. And going from a 100-MHz DX4 to any Pentium OverDrive is a waste of money.

At the high end

Until recently, the successor to the Pentium has gone by the name of P6 (the Pentium was the P5; those are Intel internal code names). It's now official: the new (I almost said next-generation, but that's not quite true) CPU is called the Pentium Pro.

In midsummer, chips and systems went out to vendors and trade publi-

cations, and in recent weeks preliminary benchmark and compatibility tests have come in. The upshot is that if you're running pure 32-bit code (Windows NT, OS/2, or some form of UNIX), the P6 will look like a true next-generation CPU. But if you're running impure 32-bit code (Windows 95 or Windows 3.1), the P6 will look more like a Pentium upgrade, and maybe not even that. In fact, after news of the P6's laggard performance hit the streets, Intel promptly gave it the new name.

According to the company, the name is intended to capitalize on the millions of dollars poured into name-brand recognition advertising. On the other hand, a cynic (I mean a realist) might suggest that it's to lower expectations concerning the P6. Is it a next-generation CPU or an enhanced Pentium? Only Intel's marketing department knows for sure.

Another point is that the current 150-MHz P6 does Windows no better than a 100-MHz Pentium. But

Disk Size (megabytes)	Cluster Size (kilobytes)
128	2
256	4
512	8
1024	16
2048	32
4096	64

Intel plans an aggressive push to faster clock rates; initial estimates are that a planned 200-MHz P6 will surpass any existing Pentium. In short, the P6 does not provide the same relative jump in performance over the Pentium as the Pentium did over the 486. The "586" clone vendors (particularly AMD and Cyrix) are hoping that Intel's stumble with the P6 will provide an opening for their wares—if they can ever get them to market.

In terms of the overall systems market, it seems likely that Pentium systems will remain the mainstay for several years. The P6 may eventually overtake the Pentium, but it may not. If the vast majority of users are going to be using mixed 16/32-bit environments for the next few years, there

seems little incentive to move to the P6. If Windows 95 were to fall flat, and Windows NT were to take over, the P6 would probably move into prominence sooner. But despite its faults, Windows 95 seems to be catching on about as well as Microsoft could have hoped.

Wasting space

This has bothered me for years; as we move to 1-gigabyte and larger hard disks, the problem is only getting worse. The problem is clustering. A hard disk drive consists of one or more platters, each of which contains a set of concentric circles called tracks, each of which is divided into a set of segments called sectors. On a floppy disk, every sector contains 512 bytes of data. On a hard disk formatted for DOS or Windows or OS/2, a sector also contains 512 bytes.

However, because DOS has only 16 bits to keep track of which sectors are used and unused, files are not allocated in units of sectors, but in groups of sectors called clusters. A cluster contains $2K * n$ bytes, where n is a number from 1 to 32. Hard disks smaller than 128 megabytes have 2-kilobyte clusters; today's common 1-gigabyte drives have 16-kilobyte clusters. Table 1 correlates drive and cluster size.

What difference does it make what the cluster size is? If you have lots of large files, it won't make much difference. But if you have lots of small files, DOS will waste a lot of space. For example, assume you have ten 200-byte batch files. The space required to store them is simply $10 \times 200 = 2,000$ bytes. But because each file must be stored starting in a new cluster, some space must be wasted. On a small hard disk (less than 128 MB), those batch files would require $10 \times 2048 = 20,480$ bytes. A 1-gigabyte hard disk, would require $10 \times 16,384 = 163,840$ bytes. For this example, the efficiency of the small disk is $100 \times 2000 \div 2048 = 9.77\%$; for the large disk, it is $100 \times 2000 \div 163,840 = 1.22\%$. Ten percent is bad, but one percent is ridiculous!

Don't get the wrong idea; the fact that a few small files waste a fair amount of space does not mean that

overall disk utilization is that low. Most systems have a mix of large and small files; efficiency typically varies 70–90%.

How do you know what your disk's space efficiency is? You can get a rough estimate using DOS's DIR and CHKDSK commands. By running CHKDSK you can learn your disk's total size, cluster size (CHKDSK reports clusters size as "allocation unit"), and space allocated for files. By typing "DIR /S" from your root directory (and waiting patiently), you'll eventually end up with a display listing total bytes used by the files on your disk. You can then calculate your waste factor as $(1 - (\text{bytes used} \div \text{bytes allocated})) \times 100\%$.

For example, one system on my network has a 1-gigabyte SCSI drive. CHKDSK told me that 784,515,072 bytes were allocated to files, and DIR told me that 627,110,564 bytes were actually stored in those files. Applying the formula, I come up with a waste factor of 20.1%. Twenty percent of 784.5 megabytes is 156.9 megabytes. Wasting 150 megabytes of disk space does not make me happy!

You can get a somewhat more accurate display of disk utilization, along with some other interesting statistics, from a utility, CHKDRIVE, written by *PC Magazine* columnist Jeff Prosis. Jeff's program scans your entire hard disk counting space allocated and used by the files. I'll post a copy of CHKDRIVE.ZIP on the Gernsback BBS (516-293-2283). The file includes both the executable and the C source.

References:

- PC Week, 9/18/95, p. 133.
- Byte, 10/95, p. 26
- PC Magazine, 6/27/95, p. 249
- PC Magazine, 10/10/95, p. 345

DIR /s output

```
Total files listed:
    17,579 file(s)      627,110,564 bytes
                        224,493,568 bytes free
```

Chkdsk output

```
1,050,411,008 bytes total disk space
  21,364,736 bytes in 20 hidden files
  19,382,272 bytes in 1,182 directories
  784,515,072 bytes in 14,047 user files
  224,526,336 bytes available on disk

    16,384 bytes in each allocation unit
    64,110 total allocation units on disk
    13,702 available allocation units on disk
```

Chkdrive output

```
Scanned 14,070 files in 1,183 directories on drive C:
Cumulative length of all files is 648,207,406 bytes
Cluster size is 16,384 bytes (16K)
```

Cluster Size	Overhang (Bytes)	Efficiency
2K	15,336,402	97.7%
4K	33,211,346	95.1%
8K	72,549,330	89.9%
16K	157,623,250	80.4% <--
32K	341,156,818	65.5%
64K	739,124,178	46.7%

HOW MUCH SPACE ARE YOU WASTING? calculate you drive's efficiency and find out.

What's the solution? You can partition large drives into several smaller ones. By keeping the logical drives less than 128 megabytes, you can ensure minimum waste factor. But managing eight or ten drives can be a pain in the rear. And adding another large drive could easily exhaust available drive letters.

Another possibility is to use disk compression—either Microsoft's or a third party's—to decrease the waste factor. The reason is that disk compression programs typically pack files in byte rather than cluster boundaries.

The problem is that disk compression exacts a toll in terms of performance and robustness. In addition, the MS-supplied DOS 6.x compression programs have a maximum compressed volume size of 512 megabytes, which means that you'd have to partition a 1-gigabyte drive into four chunks. The disk compression available in Windows 95 allows volume sizes up to 2 gigabytes, but even that can be a limitation.

The real solution is a better built-in file system. What about it, Microsoft? EN

LETTERS

continued from page 23

When New Tek built the toaster for the Amiga, it was a plug-in card. When it decided to build one for the PC, it had to be a stand-alone unit that could only be interfaced with the PC. The PC does not have the video capabilities or operating system to support a plug-in card. New Tek had to make a stand-alone processor and write an operating system that could handle the taxing video demands. That says volumes about the Amiga

and its "stellar position."

KURT D. SWAIM

Fort Wayne, IN

AN INNOVATIVE HEAT GUN

I recently discovered an inexpensive but useful electronics-related tool. I was loodng into the bore of my Presto Poplite hot-air popcorn popper, and I noticed that it had no moving parts and was able to produce a very hot stream of air from its mesh-covered bore. I realized that this appliance might make a good

heat gun for heat-shrinkable tubing.

I found the same model for sale in a thrift store for \$2. I found I had an excellent benchtop heatgun after I removed the outer housing. The short assembly stands on three legs. I secured its wires with some wire ties and a cable clamp, making use of an existing screw. Also, the unit had some exposed terminals that I covered for safety reasons. I found that the heat comes up so fast that it will shrink the tubing as soon as it's plugged in.

PETER PINETTE

Cape Coral, FL

Cables (and interconnects) revisited

TOM NOUSAIN IS ONE OF THOSE DEDICATED AUDIOPHILES WHO HAVE THE TIME, INTEREST, AND KNOW-HOW TO SCIENTIFICALLY INVESTIGATE POTENTIAL IMPROVEMENTS IN HI-FI PERFORMANCE.

He didn't set out to be a "debunker," but his rigorous test procedures have often made hash of the mystical beliefs propagated by the high-end audio aficionados. In an article in the September issue of the excellent Canadian publication *Sound & Vision* (99 Atlantic Avenue, Suite 302, Toronto, Ontario MK6 3J8, Canada), Tom notes that nothing new has been published on controlled cable-listening tests in about 10 years. In the meantime, audiophile speaker cables have proliferated wildly, all accompanied by preposterous performance claims and outrageous prices.

Tom, who lives in an area well populated by audiophile cable aficionados, asked the members of his audio club to participate in double-blind speaker-cable listening evaluations. The test was to determine whether they could differentiate by ear the performance of their own audiophile cables against ordinary 16-gauge electrical zip-cord. In Tom's words, "The challenge had the majority of potential listeners diving for their shoelaces," but two courageous—or overconfident—listeners accepted the dare. Each audiophile's own system, listening room, and music

served as his test base.

In the series of double-blind listening tests, the participants were asked to distinguish between setups incorporating such cost-wise opposites as a \$900 set of cables and \$15 worth of zip-cord. After a discussion of the test procedures and results, the remainder of Tom's article is an excellent tutorial on the statistical analysis and philosophy of double-blind testing.

Were the two audiophiles able to hear the difference between their own costly and highly touted esoteric cables and the ordinary zip-cord? Much to their shocked surprise they could not. To my surprise, neither one copped out by claiming that the test techniques were somehow flawed and therefore obscured the differences they heard normally under non-test conditions. I guess for some brave souls, at least, the truth will make them free—of excessively expensive cables, that is.

Tom recently conducted a new round of tests with his audio club members, this time comparing high-end "interconnects" to ordinary phono cables. The results were the same: audiophile efforts to pick out their own expensive



SALES OF MINIDISC PRODUCTS have been below expectations so far.

interconnects by ear averaged out to no better than guesswork.

DCC and MD

Have you been as puzzled as everybody else by the increasing proliferation of competing and non-compatible new audio/video products? We have barely bought into one new format before other non-compatible competing formats are introduced. A brief historical review of the hi-fi industry will help explain what I think is going on.

When I first become involved, in the 1950s, each round of audio new-product introductions seemed to embody real advances. Perhaps some of the audible improvements I heard were illusory, but in any case, I found myself compulsively upgrading with, say, a new tuner

that pulled in more stations with less noise, a turntable with lower rumble, a tape recorder with a wider frequency range and lower hiss and flutter, an amplifier with more power and lower distortion, and speakers with higher highs and lower lows. Over the years, the stuff just kept getting better, we audiophiles kept upgrading, our numbers kept increasing—and the hi-fi manufacturers prospered.

Then stereo FM and records appeared. There was the expected grouching and muttering about planned obsolescence and having to buy two of everything, but after a shaky start stereo sold, mono equipment was replaced, the market continued to expand, and the manufacturers smiled all the way to the bank. Stereo equipment, like the mono components it replaced, continued to slowly improve, and consumers upgraded as they found themselves in the mood and with the cash.

Then came “space-age technology” in the form of the transistor. Manufacturers saw a wonderful opportunity to sell new electronic everything to everybody. Unfortunately, it didn’t work out that way. Impatient audiophiles unwary enough to be suckered in by the hyperbolic ads of the day found themselves with tuners that overloaded on strong stations and amplifiers that distorted badly, or blew up, blew out, or quietly died.

It took several years for the transistor manufacturers and component designers to get their acts together, but today’s solid-state equipment is vastly superior to the best of the old tube equipment in reliability and longevity, and at least their equal in sound quality—despite the contrary opinions of a smallish group of die-hard tube fundamentalists.

You couldn’t tell it from the new-equipment ads, but, in general, progress in standard hi-fi components came to a halt about 10 to 15 years ago. Each year’s new models have come with a full complement of bells and whistles and have sounded fine, but most have performed no better than the 5- to 10-year-old units sitting on consumers’ shelves.

The longevity of the equipment

and its fine performance meant that the average music listener was no longer motivated to engage in regular replacement or upgrading. And besides, computers and various video goodies were competing for his discretionary dollars. True, newcomers still entered the audio marketplace, but their numbers were not sufficient to satisfy the expanded capabilities of the mass-market Japanese manufacturers. Their solution? Stop trying to kick start a dormant or too slowly expanding marketplace with new models of old products, but instead develop new product categories to tempt the customer.

Such thinking can indeed pay off, as was demonstrated by car audio equipment, the VCR, the Walkman, CD, and recently, multi-channel home-theater equipment. However, the last decade or so has seen several instances of new formats that haven’t made it. Philips’ digital compact disc (DCC) and Sony’s MiniDisc (MD) are the two latest examples.

The trade publication *Billboard* reports that the DCC is moribund with only 8,000 units sold. And Minidisk sales are also far below expectations.

There’s nothing wrong technically with either product; in fact the MD is a technological *tour de force*. The problem is that both units are designed to meet a consumer demand that never existed, except perhaps in the wish-fulfillment fantasy of some marketing maven. How much marketing research was done to gauge potential consumer interest in the MiniDisc and DCC? Perhaps Philips and Sony—and other manufacturers—would do well to put more effort into market research before committing themselves to costly product-development programs.

Getting OSHA out of our ears


Most of us know the Occupational Safety and Health Administration (OSHA) as the government agency that monitors workplace hazards—including potentially ear-damaging industrial noise levels. In my June 1995 column, I criticized OSHA for not being stringent enough in its noise standard, noting that other reg-

ulating bodies here and overseas have advocated levels significantly lower than OSHA’s legal maximum limit of 90 dB for 8 hours.

Incidentally, OSHA does not do its own research; another related agency, the National Institute for Occupational Safety and Health (NIOSH), establishes the standards that OSHA enforces. Or at least, that’s the way it used to be.

As you may have noticed, there’s a new Republican majority in Congress dedicated to the proposition that government has far too much control over our lives. In their view, we are being oppressed by the agencies that set minimum standards for food contamination, drug effectiveness and safety, product safety, water, air, and land pollution, industrial safety and noise, and so forth. To alleviate this intrusion into private-enterprise competitiveness, the House of Representatives slashed the funding for NIOSH by 25 percent as down payment on the House Budget Committee’s promise to phase out the agency in four years.

Because OSHA and NIOSH, along with the FDA and the EPA, are all on the Republican hit list, I may in the near future no longer have cause to complain about the inadequacy of industrial noise-protection standards and/or their lax enforcement simply because there won’t be any standards to complain about! It isn’t clear to me how U.S. industries will be more competitive worldwide when the U.S. workforce is sick or deaf, but that is just one more thing that I don’t understand about politics in 1995. **EN**

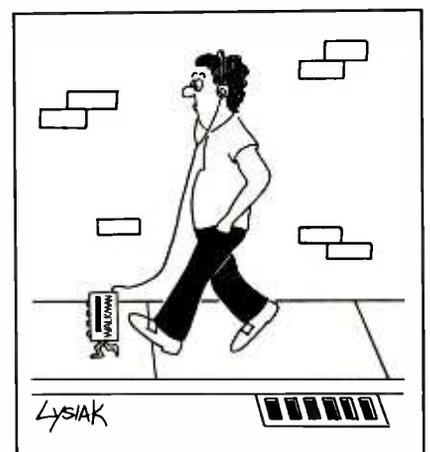

WHAT'S NEWS

continued from page 4

Nevertheless, scientists at Los Alamos National Laboratory in New Mexico are testing a prototype fuel that they believe can overcome these problems and eventually power cars.

Fuel cells convert chemical energy to electrical energy without combustion. Unlike the battery in an electric car, which requires long recharging stops and has a limited driving range, a fuel cell powered vehicle could be refueled quickly. Moreover, it would have nearly the same driving range and performance as a conventional four cylinder car.

The Los Alamos team designed an

power system that runs on multiple proton-exchange membrane fuel cells and is fueled by liquid methanol or wood alcohol. An on-board fuel processor converts the methanol into hydrogen and carbon dioxide. The fuel cell electrochemically combines the hydrogen with atmospheric oxygen to produce DC for powering the car's traction motors.

A 30-kilowatt fuel-cell stack is expected to have a volume of about a cubic foot. After testing it to determine its voltage output as the electrical load and fuel are varied, the fuel-cell stack will be built into a complete methanol-to-electric power system. The propulsion system will be tested over simulated driving conditions.

The overall goal of the Los Alamos, General Motors, and Department of Energy project is to develop an automotive-scale fuel cell that will more than double a car's fuel economy and reduce emissions by as much as 90%. A 10-kilowatt fuel cell was developed in the first phase of the project. The goal of the project's second phase, is the 30 to 50-kilowatts required to match the performance of gasoline-powered cars.

Methanol can be obtained from agricultural waste or from natural gas. It would have to be available at thousands of filling stations, but this is seen as less expensive than installing battery-recharging stations and power plants for battery-powered electric cars. **EN**

VIDEO NEWS

continued from page 6

in 2, 4, 10 and 15 megabyte capacities. A 2-megabyte card could hold 20 to 24 digital snapshots or 30 to 60 minutes of audio or 1,200 pages of double-spaced text and will be available late this year, at something under \$100 to start. An idea of who is interested in flash memory is revealed by membership in the Compact Flash Association: Apple, Canon, Eastman Kodak, Hewlett-Packard, LG Semiconductor (Goldstar), Matsushita (Panasonic), Motorola, NEC, Polaroid, SanDisc (formerly

SunDisc), Seagate, and Seiko Epson. The association plans to make technical specifications and the Compact Flash trademark available under royalty-free licenses to promote the standard.

More digital camcorders

Japanese camcorder manufacturers continue to introduce digital camcorders using the standard "DV" (for digital video) format. JVC's version, described as "the world's smallest camcorder" isn't much bigger than a VHS cassette box. It has a single-CCD pickup and weighs 1.1 pound loaded with battery and mini-cassette.

Panasonic has added a second model to its line, this one with single CCD (the first had three) and a four-inch LCD color monitor. Sharp introduced its first "Digital ViewCam" featuring a five-inch LCD monitor, three CCDs and an interface for connection to a personal computer. The two Sony models introduced previously and Panasonic's three-CCD model (*Electronics Now*, December 1995) are currently available in the U.S., and the new versions are expected here this year as well. None of them will come cheap, with prices starting above \$2,000. But we're talking electronics—so if the price is too steep now, just wait. **EN**

HARDWARE HACKER

continued from page 44

New tech lit

From *Atmel* a new *Flash Memory Application Book*. From *Siliconix*, a data book on the *Little Foot* and *Lite Foot* mini power MOSFETs. These require surprisingly little in the way of heatsinking. From *Intel* a new free CD on their full i960 *Microprocessor Electronic Library*.

Computers that can be billions of times faster than a Pentium (and far cheaper) are described in *Science* for September 8, 1995 on page 1363-64. One of the many options is *quantum computing*, which is expanded upon on

pages 140-145 of *Scientific American* for October of 1995.

Roland magazine is a free publication that covers synthesizers and related electronic music topics. *Roland* has also come up with a new *Sound Canvas*. An entire synthesizer in a single PCMCIA card.

Power Transmission Design is a new trade journal on motion systems. *The Mart* is a big-time major shopper on phone parts and systems.

Flexible Circuits Engineering is a brand new trade journal on bendable printed circuit materials.

Hoop Pine Plywood is a flexible wood suitable for model making and prototypes. Free samples are offered by *Riteco Supply*.

The free *Media Arts Catalog* from *Focal Press* stocks hundreds of titles on everything from nonlinear editing to time codes to script writing.

For high end hardware, try *Image Processing Resources*, which supplies lighting, lenses, cameras, frame grabbers, and more. Lots of great cartoons in the company's free catalog.

A *BBS Radio* directory is available from *Tiare Publications*. But do note that it lists only hobby BBSs. The outstanding Radio board up on *GENie* is not mentioned. Nor is any other major commercial resource. Or anything on the Internet.

Reprints and preprints of most of my stories are available on my *GENie* PSRT RoundTable. **EN**

Electronic SHOPPER



- PRODUCT ENGINEERING
- FIRMWARE DEVELOPMENT

• MICRO CONTROLLER & EPROM HARDWARE & SOFTWARE DEVELOPMENT

"QUALITY IS OUR CAPITAL CONCERN."

Complete On Site Electrical Engineering Lab

- REVERSE ENGINEERING
- RF CIRCUIT DESIGN & MANUFACTURING

From Auto-Routing to CNC Routing to Electronic Assemblies. . .
Capital Electronics is Your Best Route For Printed Circuit Boards.

DESIGN/LAYOUT

- CAD LAYOUT SERVICES
- COMPATIBLE WITH ALMOST ALL CAD SYSTEMS
- FROM SCHEMATICS OR SAMPLE PCB'S
- PHOTOPLOTTING SERVICES
- 28,800 BAUDE MODEM

PRINTED CIRCUIT BOARDS

- SINGLE & DOUBLE SIDED
- MULTI-LAYER & FLEXIBLE PCB'S
- FROM QUICK TURN PROTOTYPES TO SCHEDULED PRODUCTION RUNS
- FINE LINES, SMT
- ELECTRICAL TESTING
- PRECIOUS METAL PLATING

ASSEMBLY SERVICES

- FAST TURN BOARD STUFFING
- WIRE HARNESSSES
- WAVE SOLDERING
- ACQUISITION OF PARTS
- FINAL TESTING
- TURNKEY SERVICES
- CUSTOM ENCLOSURES

For Quick & Competitive Pricing or More Information, Please Call Us Today!

852 Foster Avenue • Bensenville, IL 60106

(708) 350-9510

Fax (708) 350-9760 • Modem (708) 350-9761

Internet Access:

For Automated Info Response:
 INFO@capital-elec.com

E-Mail: Quote@capital-elec.com

Web Access: <http://www.capital-elec.com>

CIRCLE 315 ON FREE INFORMATION CARD

Weeder Technologies

FREE

catalog and construction plans for any of these kits (limit two)
 Call 513-752-0279

Pro-Kit™

P.O. Box 421, Batavia, OH 45103

Educational Kits for the Serious Hobbyist

Caller Block

Connects between your telephone and its wall jack, and prevents the phone from ringing unless the calling party is one which you've entered into memory using your touch-tone phone. Your answering machine can handle all other calls. Change between two separate directories of callers with a simple flip of a switch. \$48.00

Telephone Caller ID

Connects to telephone wall jack. Shows the telephone number of the calling party along with the time of day the call was received, on a 16x1 character LCD display. Stores the info from the last five calls in memory. Complete stand alone, no computer interface needed. \$52.50

Telephone Call Restrictor

Connects to telephone wall jack. Disables all phones on the line if attempting to either: dial a number that has been stored in memory 'Block Mode' or, dial a number that has not been stored in memory 'Allow Mode'. Use touch-tone phone to enter telephone numbers into memory, and choose mode. Program from any phone on the line using your password. \$35.00

50 MHz Frequency Counter

Reads frequency from 1Hz to 50MHz and displays it on a 16x1 character LCD display. Auto-range feature provides floating decimal point and automatically affixes the correct suffix (Hz, KHz, or MHz). Microcontroller based, very few additional components. \$48.50

Telephone Scrambler

Scrambles your voice before sending it over the telephone line, and descrambles it on the other end. Connects between your telephone and wall jack. No modifications are required to your telephone. Full duplex operation. \$43.00

IR Remote Control Receiver

Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. Seven individual I/O pins can be assigned to any button on your remote, and can be configured for either 'toggle' or 'momentary' action. \$32.00

Vocal Filter

An audio device which can be used with a home component stereo system, to filter out the main vocal sound track from standard stereo recordings (CD, tape, record or FM), leaving the background music to sing along with. Produce your own karaoke tapes. \$40.00


DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Connects to your telephone wall jack. Decodes all 16 touch-tones and displays them on an LCD display. Holds the last 240 digits in a nonvolatile memory. Scroll through and view all telephone numbers dialed, credit card numbers entered, etc. \$54.50

In recent independent tests Cool-Amp is proven better than electroplating.

(For 50 years we've said Cool-Amp is "equal to" electroplating in performance. It is better.)

Cool-Amp

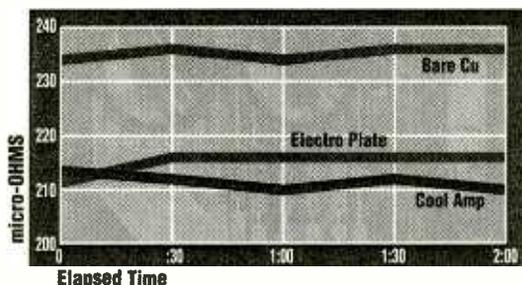


From the report:

"...compare the conducting properties of Cool-Amp silver plating compound with factory silver electro-plated bus and bare copper bus.

"The test results indicated that the contact resistance of the Cool-Amp plated bus connection was slightly lower than that of the electro-plated bus connection and much lower than that of the bare copper bus connection. The final temperature at temperature equilibrium of the bus connection employing Cool-Amp was slightly lower than that of the electro-plated bus connection and the bare copper bus connection..."

Conducto-Lube

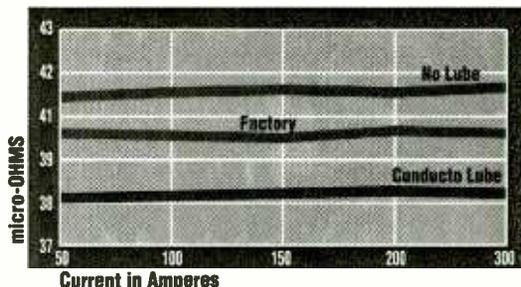


From the report:

"...compare the conducting properties of Conducto-Lube lubricant with factory lubrication and non-lubricated connections on an air switch. Identical test setups and procedures were used for each test so that comparative data could be collected and the relative performance of each type of connection could be quantified.

"The test results indicated that the contact resistance of the switch employing Conducto-Lube was generally lower than that of the factory lubricated switch and the switch that used no lubricant."

Cool-Amp How it works:

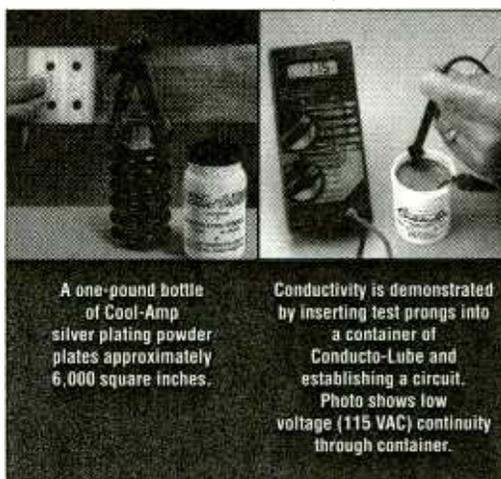- Applies *on the job*. Application is simple. Yet Cool-Amp adheres permanently. As tests show, it is better than electroplating.
- Minimizes overheating and power loss by silver plating high amperage connections.
- Saves time, reduces maintenance. Cool-Amp is so simple to apply on the job. It assures maximum conductivity for copper, brass, or bronze contacts and prevents losses due to oxidation.



A one-pound bottle of Cool-Amp silver plating powder plates approximately 6,000 square inches.

Conductivity is demonstrated by inserting test prongs into a container of Conducto-Lube and establishing a circuit. Photo shows low voltage (115 VAC) continuity through container.

Conducto-Lube How it works:

- This is *the* conductive lubricant; highly conductive because it contains pure silver.
- Originally developed to lubricate switches, to the point tension can be adjusted to factory specs allowing full rated capacity of the switch to be maintained at all times.
- Uses have continued to expand—from switches and breakers—to any application where a conductive lubricant is needed.

*Various tests were performed on both products in the Electro-Test, Inc. facilities in Portland, Oregon during January-March, 1994. Evaluation of plating thickness of Cool-Amp was performed by Surface Science Laboratories of Mountain View, California.

COOL-AMP

Cool-Amp Conducto-Lube Company

15834 Upper Boones Ferry Road
Lake Oswego, Oregon 97035

Order factory direct:
503/624-6426, Fax 503/624-6436

S
K
Y
V
I
S
I
O
N[®]

Skyvision[®] . . .

Wants you to have

The World's Premier Satellite TV Buyer's Guide!




18" - 36" DBS systems, parts,
accessories & programming

Complete product line-up for:

- DBS
- C-band
- Ku-band

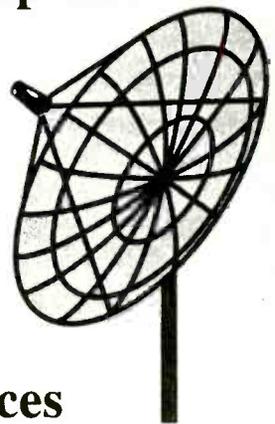Actuators, LNBs, Receivers,
Tools, Accessories, and more!



4' - 24' C/Ku systems, parts,
accessories & programming

Satellite TV products at discount prices



Call Now for Your:

- FREE, Full-Line Catalog and Buyer's Guide
- Discount Flyer. Loaded with discontinued and return items, antiques, plus widgets and gadgets galore!

800-543-3025

☐ Skyvision[®] • 1046 Frontier Dr. • Fergus Falls, MN

• International: 218-739-5231 • Fax: 218-739-4879

Quality Reconditioned Test Equipment



Hewlett-Packard 3311A

Function Generator, 0.1 Hz to 1 MHz, sine, square, triangle and + pulse waveforms.

\$300.00

Fluke 1911A

Frequency Counter, 5 Hz to 250 MHz, measures frequency, period, period average, and totalize. 15 mV sensitivity, 7 digit display.

\$199.00

Hewlett-Packard 332A

Distortion Analyzer measures total distortion down to 0.1% full scale between 5 Hz to 600 kHz,

\$249.00

Fluke 8520A

Digital Multimeter, 5.5 digit, ac/dc volts, 2 and 4 wire ohms, conductance, 20 ppm basic dc accuracy, burst memory and math capabilities.



\$369.00 Special

Hewlett-Packard 8558B

Spectrum Analyzer Plug-In, 0.1 to 1500 MHz, resolution bw from 1 kHz to 3 MHz, amplitude range is -117 to +30 dBm. Automatic and manual sweep.

\$2000.00

Hewlett-Packard 3586B Selective Level Meter

Makes carrier measurements to 32.5 MHz, voice channel measurements from 50 Hz to 100 kHz, can use the 3336B Level Generator as an automatic tracking generator. Opt 004. Like new condition.

\$850.00

Hewlett-Packard 3336B Synthesizer/ Level Generator

Frequency coverage is from 10 Hz to 21 MHz, making the 3336B useful for telephone circuit loop testing on most FDM systems. Includes opt 005. Like new.

\$850.00

Hewlett-Packard 1740A Oscilloscope

100 MHz portable Oscilloscope, 5 mV/div deflection, 50 nS/div max sweep rate expandable to 5 nS/div. Includes 2 probes.

\$500.00

Hewlett-Packard 1725A

275 MHz portable Oscilloscope, 10 mV/div to 5V/div vertical deflection factor, 10 nS max sweep rate, expandable to 1 nS/div. Includes 2 probes.

\$625.00

Hewlett-Packard 1725A/034

As above, opt 034 adds DMM which measures voltage, current and resistance. Includes 2 probes.

\$675.00

Tektronix 475A DM44 Oscilloscope

250 MHz bw, dual channel, 5 mV/div sensitivity, 1nS/div sweep rate. With differential-time/ DMM option. Includes 2 probes.

\$975.00


Hewlett-Packard 239A

Oscillator provides a low distortion sine-wave output with >3 Vrms amplitude from 10 Hz to 110 kHz and less than -95 dB THD to 20 kHz.

\$399.99

Tektronix 492 Spectrum Analyzer

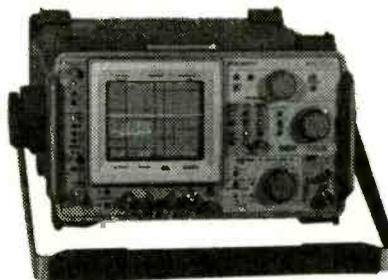50 kHz to 21 GHz, 80 dB dynamic range, amplitude comparison in 0.25 dB steps. Options 01, 02.



\$7500.00

EIP 548A Microwave Frequency Counter

Frequency range 10 Hz to 26.5 GHz in 3 bands, max input for accurate readings is +7 dBm. Opt W36.

\$4000.00

Tektronix 7904 Oscilloscope


Dc to 500 MHz mainframe, .8 ns risetime, 500 ps max sweep rate, CRT readout, accepts up to (4) plug-ins.

\$500.00

Tektronix 7633 Oscilloscope

100 MHz multimode storage scope with the following plug-ins: (2) 7A26 dual trace amplifier, & (1) 7B53A dual time base.

\$850.00 Special

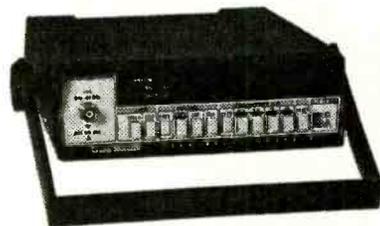

Fluke 1900A

Multifunction Counter, 5 Hz to 80 MHz, provides frequency, period, period averaging and totalize measurements, 6 digit display, 1 MHz low-pass filter.

\$189.00 Special

Phillips PM5712

Pulse Generator, 1 Hz to 50 MHz, amplitude range 0.2V to 10V, DC offset: +2.5V, offers a fixed rise and fall time of 4 ns.

\$550.00

Anritsu ML422B

Selective Level Meter, 50 Hz to 30 MHz, providing highly accurate measurements of signal levels, with the stability of frequency needed to manufacture, install and maintain FDM systems.. Functions as a wideband level meter, psophometer or voice band analyzer.

\$1250.00 New

Wanted Test Equipment call or fax us your list!

Please call for our Free 1995 Catalog

**14455 NORTH 79TH STREET, UNIT #C • SCOTTSDALE, ARIZONA 85260
(602) 483-6202 • Fax (602) 483-6403**

CIRCLE 235 ON FREE INFORMATION CARD



I DOUBLED MY INCOME...


WORK ONLY HALF THE HOURS!

I covered a lot of miles driving a cab for 13 years... but I sure didn't get anywhere! I mean the hours were long. The pay was short. My boss pushed, pushed, pushed all the time. In the meantime bills were piling up. Medical bills. House repairs. Charge cards. Just the everyday things. I was not just behind the wheel. I was behind the eight ball.

That's when I saw a magazine article that talked about the hottest big money-making career opportunities of the 90's. The one that interested me the most pertained to the *NEW explosive SATELLITE DISH/TV/ELECTRONICS field.*

I mailed the coupon for the FREE information kit they offered. I liked what I saw when the information packet came in the mail. What really caught my eye, however, was the idea I could gain all the knowledge I needed to make a success of this business studying in my spare time at home. *Foley-Belsaw's modern, practical hands on course combines simple step-by-step lessons with easy-to-follow video cassette guidance.* No special experience, education or electronics background is necessary. Just average mechanical aptitude to follow simple A-B-C repair procedures that are clearly outlined for you.

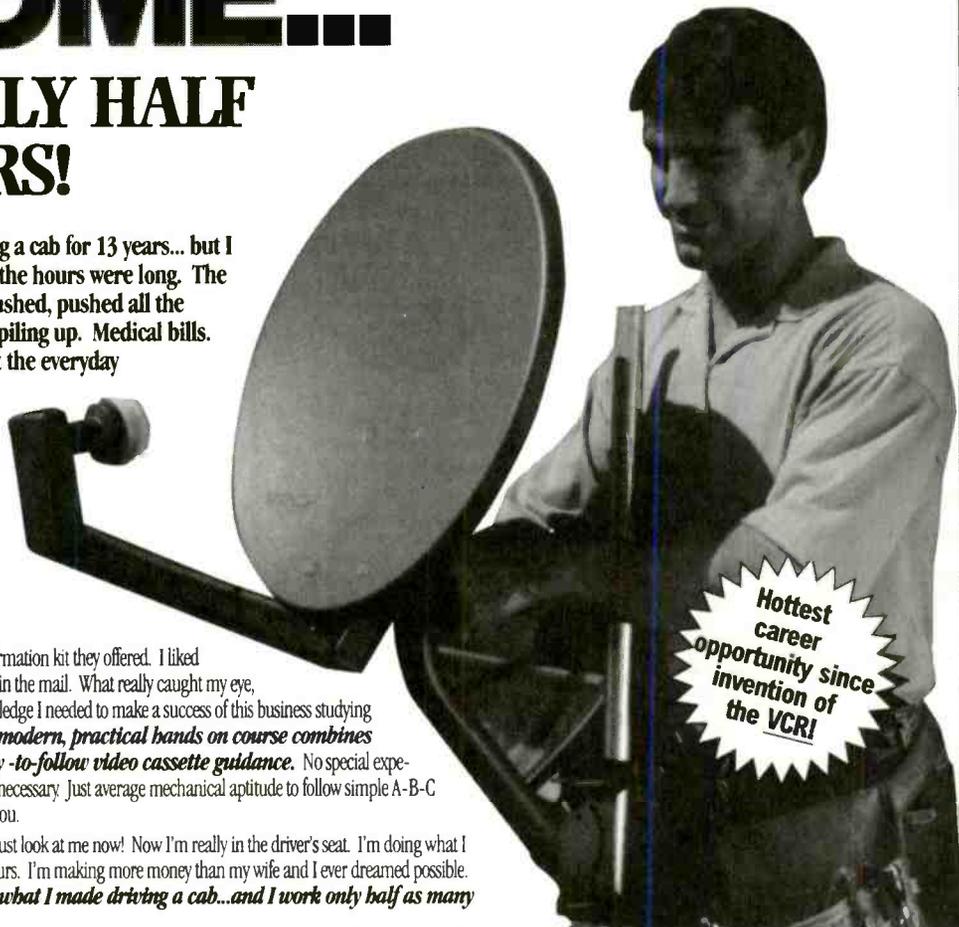I decided to get in on the action... and just look at me now! Now I'm really in the driver's seat. I'm doing what I want to do. I'm my own boss. I set my own hours. I'm making more money than my wife and I ever dreamed possible. *Would you believe I'm making twice what I made driving a cab...and I work only half as many hours.*



Hottest career opportunity since invention of the VCR!

Get in the FAST LANE on the New "INFORMATION SUPERHIGHWAY" Everyone's Talking About!

It's exciting! It's gigantic! The technology of tomorrow is here today! You've been reading and hearing about the amazing INFORMATION SUPERHIGHWAY. *It's so NEW that few technicians are equipped to service this fast emerging field!* *Foley-Belsaw gives you SATELLITE DISH technology (including New MINI-DISH)...* along with the electronics expertise you need to make BIG MONEY servicing TVs and other electronics equipment.

Be Your Own Boss!

It's quick and easy to become an expert at home in your spare time. Earn really BIG money adjusting, installing and repairing *Satellite Dish Systems, TVs, Amplifiers, CD Players, AM/FM Tuners, Home Entertainment Centers.* Every home, every business, every office in your area desperately needs your expertise!

Your Timing Couldn't Be Better!

Never before and probably never again will you have a ground-floor opportunity like this to get into a

booming business of your own, make really big money, be your own boss and enjoy financial freedom and security. The fact you're reading this message shows you're smart enough to realize this!

Learn In Spare Time At Home!

It's easy to learn in your spare time at home. And when you complete the course you will receive Foley-Belsaw's official diploma acknowledging your accomplishment

Send Coupon Today for FREE Kit. No Obligation.

Don't miss out on this once-in-a-lifetime opportunity. Send in the coupon NOW. Get all the facts and study them in the privacy of your own home. There's absolutely no obligation and no salesman will call on you. So don't delay. Mail the coupon today.

"Took in over \$3,200 in the past 10 days!"
H.H., Denver, CO

"Doubled my income within 6 weeks."
R.B., Bakersfield, CA

Mail for FREE Information Package

Foley-Belsaw Institute
6301 Equitable Road
Kansas City, MO 64120-1395



Please Check Only ONE of the Following:

- | | |
|-------------------------------------------------------|-------------------------------------------------------------|
| <input type="checkbox"/> Satellite Dish, Dept. 31197 | <input type="checkbox"/> Locksmithing, Dept. 12736 |
| <input type="checkbox"/> Computer Repair, Dept. 64320 | <input type="checkbox"/> Small Engine Repair, Dept. 52619 |
| <input type="checkbox"/> Gunsmithing, Dept. 92220 | <input type="checkbox"/> Woodworking, Dept. 43499 |
| <input type="checkbox"/> PC Programming, Dept. 35145 | <input type="checkbox"/> Upholstery, Dept. 81168 |
| <input type="checkbox"/> VCR Repair, Dept. 62423 | <input type="checkbox"/> Saw & Tool Sharpening, Dept. 21564 |
| <input type="checkbox"/> Vinyl Repair, Dept. 71103 | |

Name _____

Address _____

City _____


State _____ Zip _____

Call Toll-FREE 1-800-487-2100

New and Pre-Owned Test Equipment

Substantial **SAVINGS** on New & Pre-Owned B+K Precision, Fluke, Hewlett-Packard, Goldstar, Leader, Tektronix, and more ...

LG Precision New Oscilloscope Specials

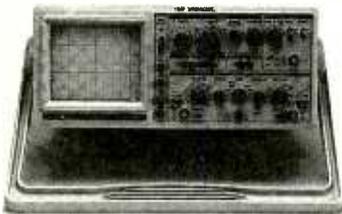

FREE SHIPPING!
ON ALL LG PRECISION EQUIPMENT
ANYWHERE IN THE U.S.
Excluding AK & HI

Model OS-9100P → **\$999.00**
Full 100 MHz Bandwidth! **SUPER SALE!**

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

Professional Quality Digital Storage Oscilloscopes at Affordable Prices!

- Transmit and Receive Data with Standard RS-232C Interface
- Includes FREE Comprehensive Communication Software
- Waveform Save, Calculation, and Print
- Dual Channel, Delayed Sweep, TV Synchronization Trigger
- 20 MS/s Sampling Rate, Two Save Memories
- Switch Between Analog and Digital Modes
- CRT Readout Including Measurement Cursors

Bandwidth	20 MHz	40 MHz	60 MHz
Model	OS-3020	OS-3040	OS-3060
SALE Price	\$1,199.00	\$1,599.00	\$1,899.00

Pre-Owned Oscilloscope Specials

Tektronix 465	100 MHz	\$589.00
Tektronix 465B	100 MHz	\$689.00
Tektronix 475	200 MHz	\$749.00
Tektronix 475A	250 MHz	\$849.00

- Professionally Refurbished
- Calibrated to Original Specifications
- Dual Channel, Calibrated Delayed Sweep
- 90 Day Warranty



Professional Computer Monitor Pattern Generator

Model 1280 \$429.00 **NEW!**

- Tests CGA, EGA, VGA, SVGA, and MAC II Monitors
- Outputs Interface to DB 9, HD 15, DB 15 and BNC
- Interlaced or Non-Interlaced
- Color Bars, Raster, and Crosshatch Patterns

20 MHz Sweep/Function Generator

Model 4040 \$499.00 **NEW!**

- 0.2 Hz to 20 MHz, 5 digit LED Display
- AM & FM Internal or External Modulation
- Sine, Square, Triangle, TTL, CMOS Outputs
- Burst Operation
- External 30 MHz Frequency Counter

Don't Leave Your Computer Unprotected!

Fairstone Uninterruptible Power System..... Reliable Blackout, Brownout, Spike and Surge Protection.

VA Rating	500	600	750
Model	P500	P600	P750
SALE Price	\$239.00	\$269.00	\$329.00

- Sleek Good Looks and Small Footprint Design
- Cold Start Function, LCD Status Display

Automatic Monitoring and Shutdown Software for Windows with cable Only \$79.00

Full line of Oscilloscopes, RF, Video & Audio Test Equipment,
Power Supplies, Meters, Probes and Accessories.



TOLL FREE 1-800-99-METER

Availability of Equipment Subject to Prior Sale
Prices Subject to Change Without Notice

1-800-996-3837

CIRCLE 309 ON FREE INFORMATION CARD

FOTRONIC CORPORATION
P.O. BOX 708
Medford, MA 02155
(617) 665-1400
FAX (617) 665-0780


SECRET ALERT ALARM



Hide this attractive small size alarm in briefcases, medicine chests, drawers, cabinets, etc. and it will silently "stand guard". As soon as someone opens the briefcase drawer, cabinet, etc. it will start sounding a loud beeping sound. Operates on one 9V battery (not included) and uses a light sensitive IC circuit with built-in arming delay. The arming delay allows you 5 seconds to put the unit in a dark place after you arm it. Then, as soon as light strikes it (from someone opening the cabinet door etc.) the alarm sounds until it's once again in the dark. Great for warning you of intrusions into areas that children and intruders should stay out of. These have a Velcro® peel and stick piece on the back of each unit, that allows you to securely hold the unit to the back of a cabinet. Although these alarms are new, they were manufactured several years ago and the adhesive on the double stick velcro surface has dried out on the G6948 units which means on those units you'll have to use glue on the adhesive sides of the velcro if you wish to mount them (mounting is totally optional). The G6949 do not have this problem. Both types are electrically perfect it's only the velcro adhesive problem. Red plastic case is approximately 3" x 2 1/2" x 7/8".

G6948 (Bad Adhesive) \$2.00
G6949 (Good Adhesive) \$2.49

AIRBAG BRAINS

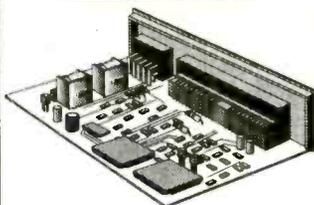

These are sophisticated airbag computer boards for automotive air bags. These have an incredible amount of SMD parts, microprocessor IC, various other ICs, SMD capacitors, diodes, SMD transistors, SMD resistors, relay, regular resistors and capacitors. These are missing the airbag sensors (available below) and they, of course, are sold "as is" only. A few parts will be missing or damaged on each board. Great for study or for a source of parts for projects. Size: 5 1/4" x 4 1/4".

G6978 \$1.00

AIRBAG SENSOR (MECHANICAL TYPE)



Mechanical type precision sensor made for automotive airbag use. They contain a small metal ball which, upon the required amount of "G" force impact, causes a momentary short between two contacts. You can observe the process by connecting a simple circuit consisting of a battery and buzzer or LED to the contacts. If you "jar" the sensor sharply it will light the LED or cause the buzzer to sound momentarily. It seems like this sensor could be used in various unique circuits. Size: 1/2" square x 3/8" thick. Brand new but we have no info or data on it.

G6976 \$1.00

DIGITAL CLOCK MODULE



Displays day of week, date & time. Brand new but battery is dead from storage.

G5911 79¢

GIANT SMD ASSORTMENT



OVER 1,000 PIECES!!

Our largest assortment of tiny SMD parts. You'll find prime LEDs, ceramic capacitors, resistors, transistors, diodes, tantalum capacitors, inductors, etc. in every package. Great way to stock up your parts bins at less than 1 1/2¢ a part! Over 1,000 pieces in a 2" x 3" zip close bag! **NOTE: Many SMD parts are so tiny that the manufacturer does not mark them, however, every part in this assortment is 100% prime and perfect.** Do a little detective work and save over a hundred dollars!

G7128 \$15.00

PHONE ORDERS (602) 451-7454

IF YOU CAN'T FIND WHAT YOU ARE LOOKING FOR, CALL FOR A FREE COPY OF OUR LATEST CATALOG. THIS CATALOG CONTAINS OUR ENTIRE PRODUCT LINE OF ALMOST 4,000 ITEMS AND IT IS STILL GROWING!

100 WATT AUDIO POWER AMPLIFIER IC LM3875



High performance audio power amplifier IC capable of delivering 100 watts instantaneous peak output power or 40 watts continuously into an 8Ω speaker 20Hz-20KHz. Specs: signal-to-noise ratio - 95db(min), output short to ground protection, supply voltage min. - 20VDC, max. - 34VDC, thermal protection, spike protection. Great for stereo power amplifiers (requires 2 units), self-powered speakers, surround sound amplifiers, etc. TRA118, 11 pin power package. Prime with specs and simple application circuit diagram.

G6943 \$4.50


LM78L12 VOLTAGE REGULATOR



Prime T092 case 78L12ACZ 12VDC IC. These are brand new but they have had their leads cut and formed for PC board use. Input voltage up to 35V. Maximum output current: 100mA.

G6996 10/\$1.00
100/\$9.00 • 1,000/\$75.00

SUPER COPPER CLAD ASSORTMENT

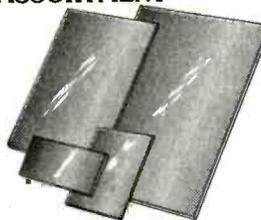

Our best assortment ever. Contains 25 pieces of various size copper clad circuit board blanks. Each is double sided and you will receive thickness types from ultra thin to standard thickness. Minimum size 2" square to a maximum of 6" square. A PC board makers delight.

G2679 \$5.00

20 STRAND FIBER OPTIC CABLE



Flat fiber optic cable consists of 20 individual small diameter fiber optic strands covered by anything that can be cut away and removed. Width of the flat cable is about 1/4". Brand new, sold in minimum 1 foot long lengths. Make beautiful fiber optic displays with the 20 strands!

G7016 \$3.00 Per Foot

BR2325 LITHIUM COIN BATTERIES



Lithium coin battery rated 3V. These are retail blister carded in a set of 3. We are selling the set of 3 cheaper than the price for one

G7022 \$2.00 (PER 3 PACK)

MAGIC LIGHT HIGH TECH MICRO BLACKLIGHT



This precision made UV blacklight is about the size of a beeper but puts out an ultraviolet purple glow that can be used to detect counterfeit currencies, many fluorescent minerals, UV invisible inks, etc. Brand new, uses 2 AA batteries (not included). Attractive black case is only 3" x 1 3/4" x 13/16". With removable belt clip.

G6967 \$6.95

PIR (PASSIVE INFRARED) PEOPLE DETECTING ALARM



Brand new pocket-sized PIR alarm is perfect to take with you on vacations. Protect your hotel room, car, campsite, vacation home, etc. The unit is called the Travel Alert by SnapIt®. It detects people using a sensitive PIR detector, and sounds a loud electronic alarm when they intrude into its field of view. Compact unit is only 4" x 3" x 1 1/4". Operates on one 9V battery (not included).

G6954 \$9.95

9V Alkaline Battery (Stock# G6955): \$1.79

SUPER LED ASSORTMENT




YOU GET LEDs IN THESE COLORS:
• RED
• ORANGE
• YELLOW
• GREEN
YOU EVEN GET A RARE
• BLUE!

Assortment of all types, colors, sizes and shapes of prime quality LEDs. This large assortment even contains a clear LED that lights up blue! Our largest and most spectacular assortment contains 250 pieces.

G6554 \$10.00

FOLDING STEREO HEADPHONES

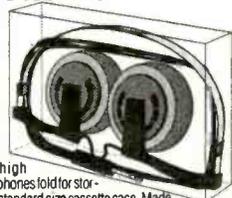

Compact high quality headphones fold for storage inside a standard size cassette case. Made by Gemini, these are not only comfortable but also have an excellent response: 20-20,000Hz, 9dB @ 1KHz. Weight of headphones only 1.5oz. Brand new in retail blister card.


G7018 \$3.95

LASER LIKE LEDs

One of our brightest clear case jumbo T1 3/4 red LEDs produces a brilliant red output.

G6167 4/\$1.00

DELUXE SMD LEARN TO SOLDER KIT

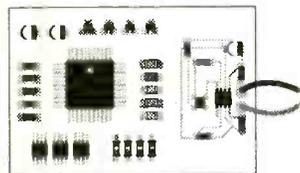

A great way to gain experience in soldering, identification and use of Surface Mount Device (SMD) Technology. Includes a practice section and a working LED flasher. Uses 9V battery (not included). Size of PC board: 2" x 3"

C6719 \$8.69

TINY TRACKBALL



FINAL CLEARANCE!

This is probably the tiniest trackball ever made! It measures only 1 1/16" L x 13/16" W x 3/8" H. Made by Alps for a major laptop computer maker that went out of business. They are very precision made and highest quality. The components are all SMD with an IC marked 3JA101002/TB6012CF and a tiny 8 position connector. They appear to be complete, new and very recent in manufacture. We have no hookup info or schematic, but at this price we know that you'll be impressed and want to experiment with them, use them for replacement or figure out the hookup! Hurry, these may not last long!

G5514 \$1.50 ea.
10/\$10.00

NOTE: All sale prices advertised are valid only through the month of the cover date.

For Phone Orders Call (602) 451-7454
or Fax Your Orders to (602) 451-9495

Minimum Order: \$10.00 (plus \$4.00 Shipping and Handling). We accept MasterCard, Visa and personal checks, however, we cannot accept personal checks on orders outside the United States. Canadians and orders that need US MAIL send minimum \$5.00 S&H. Minimum Foreign Order Amount: \$50.00 (plus shipping and handling).

ELECTRONIC GOLDMINE
PO Box 5408
Scottsdale, AZ 85261

ULTIMATE CABLE

King of Combos Panasonic TCPC175DG2

-  Volume Control
-  Sleep Timer
-  Last Channel Recall
-  Favorite Channel Memory
-  Parental Lockout
-  STD/HRC/IRC Switchable
-  Channel 2/3 Switchable
-  Infrared Remote Control



Model SP+ **\$239**
 A 100% replacement for all Pioneer, all Scientific Atlanta (except baseband), Oak, Hamlin, and Eagle Systems

Model T **\$239**
 Perfect for all TOC xx03/07/08 systems including wireless

Model Z **\$239**
 The one for all Zenith and Zenith/Oak systems.

G7 Combo

-  Last Channel Recall
-  Favorite Channel Memory
-  STD/HRC/IRC Switchable
-  Infrared Remote Control



Timeless Products TPI550PC w/G7 **\$139**
 Timeless Products TPI550PC with all new G7 Tri-Mode decoder installed. This brand new one piece system is a real crowd pleaser. Easy to install and operate.

SSA-TV86

-  Last Channel Recall
-  Parental Lockout
-  STD/HRC Switchable
-  Infrared Remote Control
- Manual Fine Tuning**



SSA-TV86 **\$149**
 This updated SSA-TV86 replaces all SA8500-8580 and PIO 5xxx-61xx.



1-800-338-0400

6325-9 FALLS OF THE NEUSE ROAD, RALEIGH, NC 27615
 CIRCLE 307 ON FREE INFORMATION CARD

Descramblers

	QTY 10	QTY 20
STEALTH 1000-P 5 x 4 Plastic Case w/Toggle	\$49	\$45
TNT 6 x 9 Metal Case w/Toggle	\$45	\$42
TVT-3G 6 x 9 Metal Case	\$42	\$39
MINI-TVT 3 x 6 Metal Case	\$42	\$39
GOLD 3 x 6 Plastic Case	\$42	\$39
APOLLO-J 3 x 6 Metal Case Replaces Purple & SIP	\$49	\$45
FTB-3 6 x 9 Metal Case	\$43	\$39
G7 4 x 4 Board Only	\$39	\$35



	QTY 10	QTY 20
PI0-6300 6 x 9 Metal Case w/Toggle	\$69	\$59
PI0+/TNT 6 x 9 Metal Case w/Toggle	\$69	\$59
PI0 RED 3 x 6 Metal Case Replaces Green & Apollo-P	\$69	\$59
STEALTH 80-P 5 x 4 Plastic Case w/Toggle	\$55	\$49
M-80 6 x 9 Metal Case w/Toggle	\$65	\$59
S-BLUE	\$65	\$59

Converters

	QTY 10	QTY 20
Stargate Elite	\$59	\$55

-  Last Channel Recall
-  Favorite Channel Memory
-  Parental Lockout
-  STD/HRC Switchable
-  Infrared Remote



	QTY 10	QTY 20
TPI 550	\$60	\$57

-  Last Channel Recall
-  Favorite Channel Memory
-  Parental Lockout
-  Infrared Remote Control



	QTY 10	QTY 20
Stargate 550XL	\$99	\$89

-  Volume Control
-  Sleep Timer
-  Last Channel Recall
-  Favorite Channel Memory
-  STD/HRC Switchable
-  Channel 2/3 Switchable
-  Infrared Remote Control



	QTY 10	QTY 20
Centurion	\$65	\$61

-  Sleep Timer
-  Last Channel Recall
-  Favorite Channel Memory
-  STD/HRC Switchable
-  Infrared Remote Control
- 100 Channel Capability
- Fine Tuning



	QTY 10	QTY 20
Panasonic TZPC1453G2	\$79	\$69

-  Sleep Timer
-  Last Channel Recall
-  Favorite Channel Memory
-  Parental Lockout
-  STD/HRC Switchable
-  Infrared Remote Control



	QTY 10	QTY 20
Millennium³	\$69	\$59

-  Sleep Timer
-  Last Channel Recall
-  Favorite Channel Memory
-  Parental Lockout
-  STD/HRC Switchable
-  Infrared Remote Control
- 100 Channel Capability



Build your own one piece combo unit. This converter is perfect for installing a descrambler into. No soldering required, all cable included.

THE ULTIMATE PROMISE

1. COURTEOUS AND PROFESSIONAL SERVICE
2. QUALITY PRODUCTS
3. LOW PRICES
4. PROMPT DELIVERY.
5. SATISFACTION GUARANTEED OR YOUR MONEY BACK!



All prices are for 10 pieces, subject to change without notice. Some quantities may be limited. 30-Day Money Back Guarantee. One year parts and labor warranty.


MON-FRI 10-7 EST
SAT 10-3 EST
FAX 1-800-854-7118

CIRCLE 307 ON FREE INFORMATION CARD

ULTIMATE CABLE

Motron 310 Garfield St Suite 4 *New Low Price!*
 PO Box 2748
ELECTRONICS Eugene, Oregon 97402 **\$59.00**

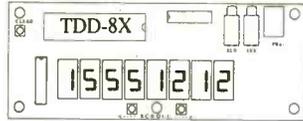The **TDD-8X** features a large 8-digit LED display and decodes all 16 DTMF digits. The 104 character memory is viewed, without loss of data, by scrolling either left or right.



Although a computer is not required, the serial ASCII output allows automatic logging of decoded number groups. ToneLog™, our IBM/Compatible logging software is included. Available accessories include a Plastic Mounting Kit (\$15), Audio/Computer Cables (\$20) and a 12VDC AC Power Adapter (\$10).

Visa, MasterCard, American Express, Discover and Government Purchase Orders accepted. Minimum Government Purchase Order: \$99. COD Cash or Money Order only. S/H: \$6 USA/Canada; \$15 Foreign. COD: \$5.

Info: (503) 687-2118 **Orders: (800) 338-9058** Fax: (503) 687-2492
 Or contact motron.info@emerald.com for a catalog via the Internet

HACKING SATELLITE TV

ALL the FACTS!

The acclaimed hacker's "bible" with all the nitty-gritty technical details

- Analog and digital systems
- Videocrypt and parallels with DirecTV

1-800-483-2423

TO ORDER **560 pages, 6" x 8.5"**
 or for a **FREE** books/software/video CATALOG **\$55 plus \$4 s/h**

BAYLUN publications

1905 Mariposa, Boulder, Colorado 80302, USA
 Telephone: 303-449-4551 FAX: 303-939-8720



Data Acquisition and Electronic Chart Recording

5½ digit (18 bits + sign) resolution, ±200V to ± 0.1µV, .006% accuracy, 15 or 55 conversions/sec. Eight differential input multiplexer. Thermocouple compensation. Digital I/O for control of the measurement process. Powerful Microsoft Windows based software includes programs required for measurements to be rescaled, recorded and graphed with a wide range of selections. Control by programs you write in EXCEL, Visual Basic, Word 6.0 or C++ (Very Easy - Demo Available).



DeltaQuest
 Phone: (408) 997-8644, FAX: (408) 997-6730 From \$239.95
 4960 Almaden Expwy, Suite 238, San Jose, CA 95118

CABLE TV DESCRAMBLERS NOBODY BEATS OUR PRICE!

SAVE MONEY-DON'T RENT

TOCOM **SCIENTIFIC ATLANTA** **ZENITH**
QUANTITY DISCOUNTS! 24 HOUR SHIPPING
MASTER CARD • AMEX • VISA • C.O.D.
CALL VIDEO CONNECTIONS, INC.
JERROLD **1-800-677-0321** **PIONEER**

Anyone implying theft of service will be denied assistance.

All shipping and handling at customer's expense

NO FLORIDA SALES

CW-2D

THE GIANT BLACK BOOK OF COMPUTER VIRUSES is an amazing technical introduction to computer viruses! Over 670 pages long, it covers *everything*, from the simplest 44-byte virus to advanced Darwinian evolving viruses, and viruses for advanced operating systems like OS/2 and Unix. It contains full source for your own anti-virus programs, and for 37 different viruses, as well as detailed explanations which will lead you to mastery of this mysterious and complex subject! **\$39.95+3.00 shipping**

THE COLLECTION CD-ROM is the perfect companion to *The Giant Black Book!* It contains nearly 5000 live computer viruses, 12 megabytes of source code for viruses, virus creation tools and mutation engines, Trojan Horse programs and source for them, not to mention tons of journals and text files (both above ground and underground) about viruses! Also includes the latest anti-virus software. **\$99.95+7.00 shipping.**

Call (800)719-4957 or send your order to:

American Eagle Publications Inc.

P.O. Box 1507, Show Low, AZ 85901

or circle rdr svc # for **FREE** catalog and **FREE** specail report!

DANGER LASERS DANGER

2-3 mW Helium-Neon Laser

Includes 115VAC power supply manufactured by Laser Drive. These are pulls from equipment. Six month warranty. FREE "101 Uses for a He-Ne Laser." pamphlet. Cat. #: HE2
 \$69.00 each!



New Brighter Laser Pointer

You will be amazed at the difference in the brightness of this laser pointer compared to any of the common laser pointers on the market. The lower wavelength (650nm) of this pointer makes it appear 3 times as bright as standard 670nm laser pointers. Features: 5mW laser, velvet "snappy" case, and batteries. One year warranty. Cat. #: LP50 \$65.00



Midwest Laser Products **FREE CATALOG**
 P.O. Box 2187 Bridgeview, IL 60455 Call, write, or poll fax.
 Phone: (708) 460-9595 FAX: (708) 430-9280
 Please include \$7 S&H within US. IL res. add 7.75% sales tax. 30 day satisfaction guarantee.



818-913-6735

ORDER TOLL FREE
1-800-669-4406

24 hr. Fax: 818-912-9598

ERPOM UV ERASER


The ERA-08 EPROM Eraser can hold up to eight devices on its anti-static, conductive foam lined tray. A built-in timer (1-60 min.) provides proper exposure and correct intensity levels, assuring a long life for EPROM's and other erasable devices. A 9V AC adapter is included with the unit.


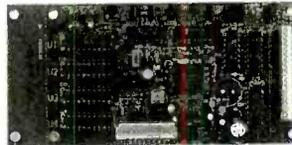
#M12ERA-08 \$98.95

DIGITAL VOICE MODULE

The DVM-58D has variable length message capabilities and can store up to 16 individual messages for immediate playback. Use it to add real voice prompting or instruction to any project, via the mic. input. Standard 1Mb DRAM on-board (32 sec. @ 32K bps) with options to expand up to 16Mb (8 min. @ 32K bps). ADM recording with selectable 16/32/44K bps sampling rates and very low power consumption.



#M105858 \$89.95
1Mb DRAM \$5.15
4Mb DRAM \$21.95

RF TRANSMITTER + ENCODER MODULES

The TX-99 interfaces with the TX-01 as the RF carrier module. 300 MHz AM with a typical range of 50' - 100' line-of-sight. (Key-chain transmitter is also available, model TX-99K \$15.95)

#M109903 \$5.95

The TX-01 Motherboard can encode a 12-bit address code with 4096 possible code combinations or can be used to encode an 8-bit address code with a 4-bit data code.

#M10001 \$9.95



RF RECEIVER + DECODER MODULES

The RE-99 interfaces with the RE-01 as the RF carrier's receiver module and requires only a few solder connections to mate the two. 300 MHz AM.

#M109904 \$6.95


The RE-01 Motherboard will decode a 12-bit address or 8-bit address with 4-bits of data, depending on which of the two included IC's is installed into the board.
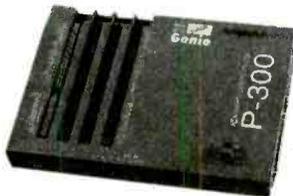
#M10001D \$14.95



PC INTERFACE CARD PROTECTOR

The Data Genie P-300 is a device that allows quick and easy installation of add-on cards or prototype circuits for testing externally on your PC without having to turn off the computer. Maintains complete protection for your motherboard via the built-in protection circuitry & current limit fuses. Adds 3 expansion slots.



#M12P300 \$349.95

PIR DETECTOR

The Medusa Passive Infrared Detector has been tested at 20V/m over the frequency range 20 to 1000 MHz, proving that the unit has ultra-high RFI protection and reliability. With N.C contacts including tamper, plus selectable pulse counts of 1, 3 or 5, Medusa makes for confident installations.

Detects ambient body heat and movement to trigger your connected security system, announcement buzzer, or warning device.



#M113300 \$24.95
3+ at \$19.95 each.

LASER POINTER

The Infillter Laser Pointer is lightweight, durable and can project a beam over 150' to enhance any demonstration or presentation. It even works well on overhead projection screens and can be used in conference rooms, exhibition hall, construction sites, museums, etc.



(2-"AAA" Batteries not included)


#M160012 \$49.95

MELODY DEMO KIT

The HT-38DPB Demo Board comes complete with a preassembled playback board, battery holder and ten Hittek melody IC's. Great for experimenting or adding a musical melody to a project.

Included melodies:

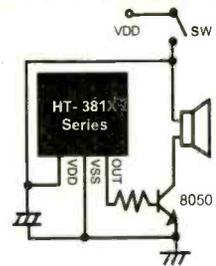Karinka • Happy Birthday • It's A Small World • Home Sweet Home • Yankee Doodle • Rock-A-Bye Baby • Are You Sleeping? • Song Of Joy • My Little Tricycle • When The Saints Go Marching In



#M14HT38DPB \$16.95

\$25 min. order or \$5 process fee.

ORDER BY MAIL:

ELECTRONICS 123
17921 ROWLAND ST.
INDUSTRY, CA 91748

24hr. Product Information

Fax-On-Demand

818-964-8490
Call from your fax machine.

S&H Charges Continental US, up to 3 lbs:

UPS Ground	\$7.00
UPS 3-Day	\$8.00
UPS Blue	\$10.00
UPS Red (Next Day)	\$20.00
COD's Add:	\$4.75
Calif. Orders Add:	8.25% Sales Tax

CANADA S&H Charges, up to 3 lbs:

US Postal, First Class \$10.00
Prepayment by credit card required.
Sorry No COD orders to Canada
(INTERNATIONAL S&H rates: Call/Fax for quote.)

All specifications and pricing are subject to change without notice.

AMAZING Electronic and Scientific Products

Mystery Levitating Device!

Remember War of the World? Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or great science project.

ANT1K Easy to Assemble Kit / Plans \$19.50



Laser Ray Gun



DANGER
VISIBLE LASER RADIATION
AVOID EYE OR SKIN EXPOSURE
TO DIRECT OR SCATTER RADIATION
CLASS II LASER PRODUCT

Advanced project produces a burst of light energy capable of burning holes in most materials. Hand-held device uses rechargeable batteries. 500 joules of flash energy excite either a neodymium glass, yag or other suitable 3" laser rod. This is a dangerous CLASS IV project (individual parts/assemblies available). LAGUN1 Plans \$20.00
LAGUN1K Kit / Plans Price on Request

Extended Play Telephone Recording System

READY TO USE! Automatically controls and records on our X-4 extended play recorder, taping both sides of a telephone conversation. Intended for order entry verification. Check your local laws as some states may require an alerting beeper. TAP20X Ready to Use System \$129.50



Shocker Force Field/Vehcle Electrifier

Neat little device allows you to make hand and shock balls, shock wands and electrify objects, charge capacitors. Great payback for those wise guys who have wronged you!
SHK1KM Easy to Assemble Electronic Kit \$24.50



Electric Charge Gun

All New Technology!



Stuns/immobilizes attackers up to 15 feet away!
*Legal in most state (not in NY, NJ, MA, WI) • More knock-down power than most handguns • No permanent injury • ID coded • Free 80KV stun gun with every purchase.
ECG1 Data Packet, Creditable toward purchase \$10.00
ECG10 Charge Gun, Ready to Use, w/Free 80KV Gun \$249.50


Homing / Tracking Transmitter

Beeper device, 3 mile range.
HOD1 Plans \$10.00 HOD1K Kit / Plans \$49.50

Listen Through Walls, Floors

Highly sensitive stethoscope mike.
STETH1 Plans \$8.00 STETH1K Kit/Plans \$44.50

Infinty Transmitter ++

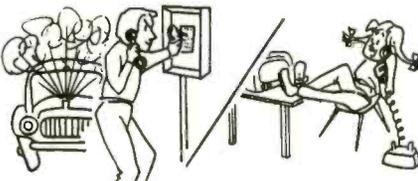

Telephone Line Grabber/ Room Monitor / Controller

All New - The Ultimate in Home/Office Security & Safety! Simple to use! Call your home or office, push a secret tone on your telephone keypad to access: • On premises sounds and voices • Ongoing phone conversation w/break-in capability • Up to 10 external electrical functions, lights, TV, alarms, coffee pots, heater, etc. CAUTION! Check legality with your state's attorney general's office before use for monitoring of voices.
TELECOM2 Kit, includes PC Board \$149.50
TELECOM2 Ready to Use \$199.50

Visible Beam Laser

Easy to build, RED Beam, visible for miles. Use for light shows, window bounce holography, cloud illumination and much more! LAS1KM Kit w/1mw Laser Tube, Class II \$69.50
LAS3KM Kit w/2.5mw Laser Tube, Class IIIA \$99.50

Life is Precious - Protect It!

Hard hitting 200,000 volts of cracking, sizzling plasma. Stuns and immobilizes most attackers
STUN40 Ready to Use \$69.50
STUN10 Smaller Unit \$39.50



Ion Ray Gun

Projects charged ions that induce shocks in people and objects without any connection! Great science project as well as a high tech party prank. IOG3 Plans \$8.00
IOG3K Kit/Plans \$69.50

Invisible Pain Field Generator

Shirt pocket size electronic device produces time variant complex shock waves of intense directional acoustic energy, capable of warding off aggressive animals, etc.
IPG7 Plans \$8.00 IPG7K Kit/Plans \$49.50
IPG70 Assembled \$74.50



1000 Ft++

Potato Cannon

NOT A TOY. Uses electronic or piezo ignition. CAUTION REQUIRED!
POT1 Plans (Dangerous Product) \$10.00

FireBall Gun

Shoots flaming ball - two shot capacity
Great for special effects and remote fire starting. CAUTION REQUIRED!
FIREBALL Plans (Dangerous Product) \$10.00



TV & FM Joker / Jammer

Shirt pocket device allows you to totally control and remotely disrupt TV or radio reception. Great gag to play on family or friends. Discretion required.

EJK1KM Easy to Assemble Electronic Kit \$24.50



ATTENTION: High Voltage Fans!

4,000 volts in the palm of your hand! Experiment with anti-gravity, hovercraft, ion guns, force fields, plasma guns, shock devices, wireless energy and electrical pyrotechnics. Input: 9-14VDC.

MINIMAX4 Ready to Use \$ 19.50



"Laser Bounce" Listener System

NEW - Latest Technology! Allows you to hear sounds from a premises without gaining access. Aim at room window and listen to sounds from within via reflected laser light. Not for illegal use. Requires video tripods.

LWB3K 5mw Laser and Receiver Kit \$149.50
LWB30 Ready to Use, includes Laser Gun Sight \$199.50



5mw Visible Red Pocket Laser

Utilizes our touch power control!
VRL5KM Kit / Plans \$ 74.50



Electronic Hypnotism

Puts subjects under control using highly effective electronic stimuli. Intended for parties and entertainment but must be used with caution. Includes valuable text book reference and plans.
EH2 Plans and Text Book \$19.50

Automotive NEON!



Easy-to-Install 4-Tube Kit for Cars, Trucks, Vans! Available in Pink, Purple, Blue or Green - please specify color when ordering.
RG4K (Specify Color) \$ 129.50

Flash-To-Music Option for above kit FMU1 \$ 29.50



License Frame Kit (Specify Color) LIC1K \$24.50

3 MI FM Wireless Microphone

Subminiature! Crystal clear, ultra sensitive pickup transmits voices and sounds to FM radio. Excellent for security, monitoring of children or invalids. Become the neighborhood disk jockey!
FMV1 Plans \$7.00 FMV1K Kit and Plans \$39.50

Telephone Transmitter - 3 Mi

Automatically transmits both sides of a telephone conversation to an FM radio. • Tunable Frequency • Undetectable on Phone • Easy to Build and Use • Up to 3 Mile Range • Only transmits during phone use. VWPM7 Plans \$7.00
VWPM7K Kit/Plans \$39.50

INFORMATION UNLIMITED

Dept ENS18, Box 716, Amherst, NH 03031
Phone: 603-673-4730 FAX 603-672-5406


MC, VISA, COD, Checks accepted Please add \$5.00 Shipping & Handling

CATALOG
With many more items!
Free with Order or send \$1 P&H

Order by Mail or by 24 Hour Orders-Only Phone
800-221-1705

PALMSCOPE™ 320

ALL IN ONE DSO+DMM+LOGIC+COUNTER

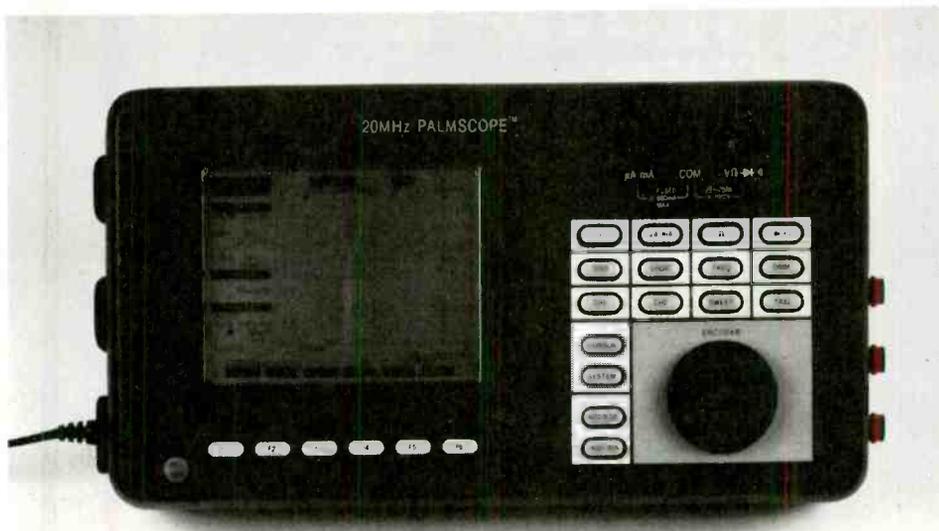

PalmScope-320 features a 20Mhz DSO, 7 digit frequency counter, multimeter and logic scope. It can be operated with built-in battery for 3-4 hours typically. Built in RS-232 port and printer port extend your application. Optional software package is available.

PalmScope 320
\$1695

DSO • Dual channel digital storage oscilloscope (20 MS/sec) • Sensitivity range: 5mV / DIV - 20V / DIV
• Sweep time: 50ns / DIV - 20s / DIV

DMM • Auto-range digital multimeter (4000 counts) • True RMS • DCV, ACV, DCA, ACA, Ohm Diode & continuity measurements

LOGIC • Logic Scope (8 channels, 50ns sample clock) • Selectable level: TTL/CMOS • Timing/State observation of logic signals

COUNTER • 7 digit frequency counter (1 Hz to 20 MHz) • Selectable trigger level and FREQ/PER mode • Basic Accuracy $\pm 10ppm$

General:

- Dual Channel Digital Storage Oscilloscope (20MS/s)
- Auto Range Digital Multimeter (3 3/4 digits, 4000 count)
- Frequency Counter (7 digits, 20 MHz)
- Logic Scope (8 channels, 50ns sample clock)

Display

- Number of Dots: 320(W)x240(H)
- Dot Pitch: 0.30 x 0.30 mm
- Backlight: LED
- Data Out (RS-232C)
- Print Out: Portable Centronix and Epson Printer
- DC jack for AC adapter input
- LOW BATT Indicator

- Operating Temperature: 0°C to 40°C
- Operating Humidity: 0% to 70% R.H.
- Storage Temperature: -20°C to 70°C (0% to 80% R.H.)
- Dimension (LxWxH): 287x152x82 mm
- Weight: 2.0Kg
- Safety Compliance: it is designed to meet Class II per UL-1244, IEC 348 and VDE-0411

Introducing the Model #EDM-89S

5000 Count AUTO Range Digital Multimeter

Twelve Good Reasons To Buy The EDM-89S:

- 3-3/4 Digit, 5000 Count Digital Readout 50 Segment Analog Bargraph
- Auto/Manual, Dynamic Recording
- 0.1% DCV Accuracy, 20 kHz ACV Bandwidth, True-RMS AC Coupled
- 9999 Counts, 10 MHz Frequency Counter, Turbo Speed, and 50mF Capacitance Measurement
- dBm with Selectable Reference Impedance
- Dual Tone/Dual Display Logic Detection
- Relative Mode or Deviation Measurements
- Input Warning, Audible and Visible
- @ OFF Auto Power Off, Sleep Mode
- Overload Protection
- Audible Continuity/Diode Test
- Rugged Fire Retardant Case, Multipurpose Holster



MODEL #EDM-89S
\$179.00



8931 Brookville Road * Silver Spring, Maryland 20910 * 800-638-2020 * Fax 800-545-0058

CIRCLE 264 ON FREE INFORMATION CARD

Robot Kits!

Sonic Rover Robot #3-174 \$27.95

A great, low-priced kit. Runs forward until it bumps object or hears loud noise, reverses turns 90° & resumes. Molded body, red/green LED, great 48 page manual. Requires soldering. *An excellent first robot!* Two AA NiCads INCLUDED!



IR Light Sensing Robot #3-216 \$68.95

Clever infrared sensors system lets this robot wander around & avoids objects - even solve mazes! Dual motors, rubber tires, preassembled gears & circuit board. *No Soldering Required!* Three AA NiCads INCLUDED!



Wall Hugging Mouse Robot #3-215 \$29.95

Classic robot design escapes mazes using the "Left Hand Rule". Two motors & sensing switch guide it along walls and around corners. Preassembled gear box, plastic base & body. *No Soldering Required!* One C NiCad INCLUDED!



Cats watch out!

Mobile Robots Brains & Brawn Kit #3-148 \$489.00

Serious research robot platform from MIT. Develop programs in C or assembly. Includes 68HC11 CPU, memory, sensors, wheels, motors, chassis, software. Companion to Mobile Robots book (3-098). *NOTE: Indicate PC or Mac interface.*



Adaptable Kits!

Power Shovel/Dozer #3-211 \$39.95

An excellent full function robot base! Wire controlled left, right, forward, reverse, plus scoop up & down. Kit has extra track & other useful parts. Two D size NiCads INCLUDED!



Electric Piston Deluxe 5-Pack #3-137 \$39.95

Incredible mini cylinders lift 1 pound! Just 10 cm long, shorten 23 mm with 1V, 5A. Cycles up to 6 times/min. Has five pistons, high current battery & full plans for 4 unique projects.



Solar Car Kit #3-217 \$59.95

Run in the sun! High efficiency solar panel (0.5V, 1200 mAh), special high torque motor & adjustable gearing. Clean design!



Batteries & Chargers



Earth Friendly - Wallet Friendly
High quality nickel-cadmium cells replace hundreds of disposables! Save money! reduce waste! Keep your robots rolling!

AA, 1.25V, 650 mAh	#3-269	\$2.95
C, 1.25V, 1400 mAh	#3-270	\$3.95
D, 1.25V, 1400 mAh	#3-271	\$3.95
9V, 7.2V, 100 mAh	#3-272	\$7.95

Special Charger, Quad AA #3-277 \$14.95!

Charge 1 or 2 pair of AA or one 9V cell. Ideal for all kits above. **BONUS - Includes 4 AA NiCads!**



Charger, 8 Position #3-276 \$29.95

Fully charge up to 4 pairs of AAA, AA, C, D or up to four 9Vs - in just 4 hours!



MONDO • TRONICS Robot Store

Robot Builder's Bonanza #3-114 \$17.95

Practical, ready-to-use circuits, devices, mechanisms, sources, tools, vision, grippers, navigation & more! 336 pgs.



Gadeteer's Goldmine #3-129 \$21.95

Unique high-tech projects & hard-to-find info. Robots, high voltage Tesla & Van de Graaff generators, Kirlian photos, lasers & much more! 400+ pgs.



Mobile Robots #3-098 \$39.95

From MIT, a complete guide to designing & building robots: hardware, software, sensors, motors, "subsumption" software. 300+ pgs. A must for all robotists.



Sensors for Mobile Robots #3-145 \$59.95

Whoa! Everything about sensors: tactile, proximity, range, acoustic, laser, radar, microwave, path following, dead reckoning, compasses, gyros. Fun & Intelligent!



507 Mechanical Movements #3-173 \$9.95

Reprinted from 1893 - when steam was king! Here are 100's of cams, clutches, linkages, latches, ratchets & more! *Don't reinvent the past - use it!* 120 pg. High powered!



The Robot Zoo #3-149 \$19.95

A big, imaginative & fun book about animals that work like robots, or maybe they're robots that work like animals? 50 pages. *For kids of all ages.*



Isaac Asimov's Ultimate Robot CD-ROM \$39.95

Mac #3-135 or Windows #3-138
An incredible interactive collection of robot info, movie clips, demos & more. 100's of pictures, 50+ Asimov stories, animate on-screen robots. "Must have" resource all robot makers. **BONUS 12 pg "Explorer's Guide" FREE!**



Controlling the World With Your PC #3-165 \$35.00

Convert ordinary serial & parallel ports into object-detecting, motor-spinning monsters! 42 circuits AND software in BASIC, C and Pascal! 256 pages, with PC disk.



PIC Source Book #3-202 \$39.95

Program PIC processors the easy way! Proven code to duplicate 30 BASIC functions - serial I/O, analog input, sound, 16-bit math, more. Adaptable to other processors! 104 pgs. w/PC disk.



Order Toll Free!

24-hour Voice Order Line - VISA MasterCard

800-374-5764

Request our FREE Robot Store Catalog!

Mondo-tronics

524 San Anselmo Ave. #107-100
San Anselmo, CA 94960
Questions: 415-455-9330
Fax: 415-455-9333
Email: info@mondo.com
Web: www.RobotStore.com

To Order:
Send check, MO or credit card info.
All orders add \$5.00 P & H.
Calif. orders also add sales tax.

International Orders Welcome! First Class P&H: \$12.00

Robotic Lawn Mower



WeedEater® VIP

Robotic Solar Mower

#3-224 \$1,999.00

An astounding advance in robots & lawn maintenance. Sun powered, whisper quiet, safe, emission free! Range limited by buried wire boundary. Handles 1,450 m² (13,000 ft.) up to 20° slope. Frees you for other work (*or to build robots!*)

Video, Robotic Solar Mower #3-223 \$4.95

See the Robotic Solar Mower in action! Shows robot in operation, blades, setup, even a time lapse sequence of the mower in action. 5 minutes, color, VHS NTSC only.



Robot Movies

We found all our favorites & more! VHS-NTSC format (all U.S. systems.) Ratings in parenthesis.

Video Special Offers!

Buy any 5, take \$10 off your total.
Buy any 10, take \$25 off your total.

• Classic Robot Films		
Metropolis - 1926 (nr)	#3-235	\$29.95
Frankenstein - Restored (nr)	#3-250	\$19.95
Forbidden Planet - 1956 (G)	#3-233	\$19.95
Day the Earth Stood Still (nr)	#3-251	\$19.95
2001: A Space Odyssey (G)	#3-144	\$19.95
Silent Running (PG)	#3-243	\$19.95
• Comedy Robot Films		
Dark Star (G)	#3-231	\$19.95
Sleeper (PG)	#3-244	\$19.95
Young Frankenstein (PG)	#3-252	\$19.95
• Adventure Robot Films		
Batteries Not Included (PG)	#3-255	\$19.95
D.A.R.Y.L. (PG)	#3-258	\$19.95
Short Circuit (PG)	#3-241	\$19.95
Short Circuit II (PG)	#3-242	\$19.95
Runaway (PG-13)	#3-240	\$19.95
• Action Robot Films		
Alien (R)	#3-226	\$19.95
Aliens (R)	#3-227	\$19.95
Alien III (R)	#3-228	\$19.95
Blade Runner - Director's Cut (R)	#3-256	\$19.95
Battlestar Galactica (PG)	#3-229	\$19.95
Logan's Run (PG)	#3-234	\$19.95
RoboCop (R)	#3-237	\$19.95
RoboCop II (PG)	#3-238	\$19.95
RoboCop III (PG-13)	#3-239	\$19.95
Terminator (R)	#3-246	\$19.95
Terminator II (R)	#3-247	\$19.95
THX-1138 (PG)	#3-268	\$19.95
Westworld (PG)	#3-248	\$19.95
• The Star Wars Trilogy		
Star Wars (A New Hope) (PG)	#3-245	\$19.95
Empire Strikes Back (PG)	#3-232	\$19.95
Return of the Jedi (PG)	#3-236	\$19.95
Mondo Robot Video Library	#3-267	\$499.00
Get all 30 films & Save 18% - Over 50 hours of movies!!!		



PICProto Demo Kit #3-180 \$34.95

Discover PIC computer power. Quick & easy kit makes a variable speed metronome. PC board, speaker, parts & programmed PIC 16C54!

Muscle Wires Project Book & Deluxe Kit #3-168 \$59.95

Create direct linear action with Muscle Wires. They contract up to 5% when powered! For robots, models & anything needing strong all-electric motion. 128 page book, full plans for BORIS, a motorless walking robot & 14 others. One meter each 50, 100 & 150 μm dia Muscle Wires. Gol



CircuitMaker[®]

The Complete, Low Cost, Circuit Design System

Professional Schematic Layout

CircuitMaker's schematic capabilities are unmatched and include many advanced editing features not found in similar programs. These powerful features minimize the time and task associated with drawing a schematic and insure a professional looking final product. Printout and export options are numerous and results are of the highest quality. But that's what people have come to expect from CircuitMaker.

More Power
NEW VERSION
S/W Only \$299

Analog, Digital and Mixed-Mode Simulation

CircuitMaker's SPICE3 based analog simulation is fast and accurate. SPICE sub circuits for all base level digital devices provides advanced mixed-mode simulation capability. Digital simulation is live and highly interactive. This powerful simulation trio is tightly integrated into one package and will confirm your circuit designs with accuracy and ease.

Comprehensive Device Library

Version 3 features a state-of-the-art device browser which greatly simplifies the task of organizing and selecting devices. With its newly expanded device library, CircuitMaker now ships with more devices (at no additional cost) than any competing product. If you need a device that isn't provided, CircuitMaker provides industry standard SPICE import and a powerful Macro capability to enable you to create new devices. CircuitMaker provides you with the tools to get the job done right.

Professional Schematic Features
Digital, Analog, and Mixed-Mode Simulation
1000+ Devices/Models
SPICE Export/Import
PCB Export
Retail Price

CircuitMaker	YES	YES	YES	YES	YES	YES	\$299
Electronics Workbench version 4	YES	NO	YES	NO	NO	NO	\$299
Electronics Workbench Engineer's Pack	YES	NO	YES	YES	YES	YES	\$599

Total Customer Satisfaction

At MicroCode Engineering we are committed to total customer satisfaction. When you purchase CircuitMaker you have the confidence of knowing that a trained staff of professionals is available to serve you after the sale. Our free unlimited customer service is second to none! Whether you have general or technical questions they will be answered promptly by a knowledgeable representative.

FREE Functional Demo

A free functional demo is available on the Internet (<http://www.microcode.com>), on CompuServe (GO MICROCODE) and on America Online (keyword search; CircuitMaker). A demo can be purchased directly from MicroCode Eng. for \$10.


Printed Circuit Board Netlist Output

The PCB output capability helps you complete the design cycle, by generating a netlist that can be imported into any compatible PCB program. This is not a costly "add-on" product. It comes standard with every copy of CircuitMaker.

PCB Program

MicroCode Engineering also offers a CircuitMaker compatible, professional level, PCB layout and autorouting program for just \$299. Used in conjunction with CircuitMaker, Autotrax completes a powerful end-to-end circuit design system. Call for details.

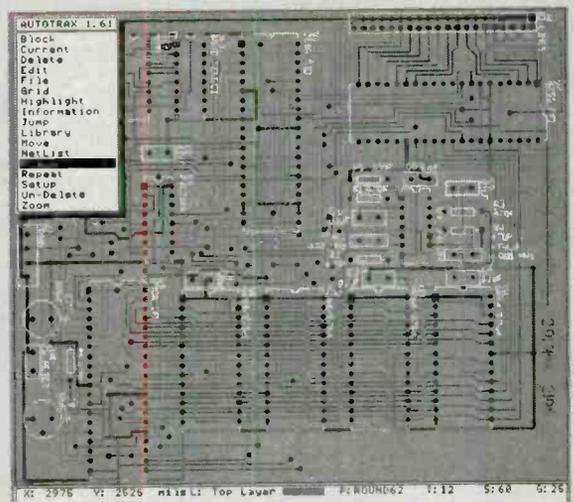"CircuitMaker Shorts The Competition Out, With An Unbeatable Bottom-line"



MicroCode Engineering
573 W. 1830 N., Suite 4
Orem, UT 84057 USA
Phone (801) 226-4470
FAX (801) 226-6532

To order or request additional information call 800-419-4242

Competitive upgrades are available for \$149. Call for details. CircuitMaker is a registered trademark of MicroCode Engineering. All other trademarks are the property of their owners.



BLOWOUT! TIMELINE INC. BLOWOUT!

Over 9 years and 24,000 customers and still growing

LIQUID CRYSTAL DISPLAYS

160 x 128 dot LCD
with built-in controller (T6963C)
20 character x 16 line **\$79.00** or 2 for **\$149.00**

Mfr.: Toshiba TLX-1013-EO.

Unit is EL back-lit. Dim: 5 1/8" L x 4 1/16" H.
The built-in controller allows you to do text and graphics.

240x64 dot LCD with built-in controller. **\$79.00**
Mfr.: AND 4021ST-EO. Unit is EL back-lit. or 2 for **\$149.00**

Alphanumeric—parallel interface

16x1.....3 for \$25.00	20x2.....\$12.00	40x1.....\$10.00
16x1 (ig. char.)...\$12.00	20x4.....\$25.00	40x2.....2 for \$25.00
16x2.....\$8.00	24x2.....\$12.00	40x4.....\$25.00
16x2 (ig. char.)...\$12.00	32x4.....\$15.00	4x2.....\$5.00
16x4.....\$15.00		

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain modules are backlit, call for more info.

Graphics and alphanumeric—serial interface

size	Mfr.	price	size	Mfr.	price
640x480 (backlit)	Epson	\$50.00	480x128	Hitachi	\$15.00
640x400 (backlit)	Panasonic	\$35.00	256x128	Epson	\$20.00
640x200	Toshiba	\$19.00	240x128 (backlit)	Optrax	\$20.00
480x128 (backlit)	ALPS	\$15.00	160x128	Optrax	\$15.00

LASER PRODUCTS

HeNe Laser Head (10Mw max. output) TEM00, 15.5" long MFG: NEC **\$99.00**

Laser Power Supply (for HeNe tube) **\$89.00**

LASER SCANNER ASSEMBLY \$29.00

Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

LASER DIODE (5mW) with collimator \$20.00

VISIBLE LASER DIODE: 5mw at 670nm \$15.00
index guided. Threshold current 40 ma typical.

NETWORK

IRMA BOARD 8 bit \$99.00

Links 3270 mainframe systems to IBM PC

Proteon ProNet-4 Model p1347 Token Ring Board \$79.00

16 bit • 4 Mbps • IEEE 802.2 and 802.5 compatible • twisted pair • interoperable with IBM Token Ring network

POS & BAR CODE

MAGNETIC CARD READER \$25.00

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypad with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

HP bar code wand (HBCS 2300).....\$35.00

POWER SUPPLIES

73 WATT SWITCHING \$15.00 or 2 @ \$25.00. (2) 4 pin power connectors attached

• 115/230 Volt, Dim: 8.5" L x 4.5" W x 2" H • Output: +5V @ 2-9.75 A, +12V @ 0-1.5 A, -5V @ 0-0.4 A, -12V @ 0-0.5 A

68 WATT SWITCHING \$12.00 or 2 for \$20.00. 115/230 Volt, Dim: 5.5" L x 3.2" W x 1.7" H • Output: 5V @ 4 A, 12V @ 4 A

MISCELLANEOUS

ADAPTEC 4070A (RLI) OR 4000A (MFM) SCSI Controller, your choice \$25.00

IBM 370 option XT and AT emulation boards \$50.00

23605 Telo Ave., Torrance, CA 90505

Order desk only: **USA: (800) 872-8878 CA: (800) 223-9977**
L.A. & Technical Info: **(310) 784-5488 Fax: (310) 784-7590**

OEM INQUIRIES WELCOME

MONITORS

Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15Khz. • Ability to do 40 and 80 column.

5 inch Amber	\$35.00
7 inch Amber	\$39.00
9 inch Amber or Green	\$29.95

5" COLOR MONITOR \$49.00

- Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible
- 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.
- Open Frame Construction • Standard Interface Connector
- Degaussing Coil included • Mfr. Samtron



CHARGE COUPLED DEVICES



"The Spy In The Sky" \$29.00 **MATRIX TYPE**

Sony CCD Imager - designed for black and white composite video cameras. Picture elements: 384 (H) x 491 (V)
Chip size 10.7 (H) x 9.3 (V) mm² • Unit cell size 23.0 (H) x 13.4 (V) um².
Ceramic 24 pin DIP package • Mfr: Sony, Part# 016AL

4096 element CCD \$29.00

LINEAR TYPE

1024 element CCD \$15.00

2048 element CCD \$15.00 • 1728 element CCD \$15.00

HACKER CORNER

CELL SITE TRANSCIVER \$99.00

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 Hz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

Encased Black & White Composite CCD Camera with Adapter

IR viewing to 1000 nm 7 1/2 L x 2 3/4 W x 1 1/2 H

Comes complete with CCD camera, mounting nut on bottom of casing.

12VDC power supply. Excellent low light capability, standard RCA NTSC video out.

Great for: entryway security/remote monitoring,

video conferencing/desktop video conferencing

This miniature camera is perfect for multimedia computer applications as well as security and surveillance. NTSC output allows use with all popular video digitizing boards for Apple Macintosh and Microsoft video for Windows. Connects directly to any composite monitor or VCR with "video" input. Its razor-sharp wide-angle lens focuses from two inches to infinity and its state-of-the-art CCD technology accurately captures 16 level grayscale images for Quick Time movies and still pictures. Records at 30 frames per second and 260 lines resolution with excellent low light capability. Uses 12VDC (adapter supplied) and standard RCA cable.

\$89.00

2 for \$159.00

Portable Micro Terminal

Flip up LCD display (9-16 VDC) • Can communicate with any computer having RS 232 port • Can communicate with another Microterminal • Use by itself as electronic notebook •

Onboard microprocessor, data RAM (32K) and Video RAM (64K) • Complex built in diagnostics and set up capabilities. • Original intention for POS applications. •

display size 40x16 (256 x 128 pixels.) Dimensions: 6.3" W,

11"L, 2"H. (With LCD up height is 7.1")

\$99.00

or 2 for **\$149.00**



BAREBONES 286-12 COMPUTER \$49.00 (2 FOR \$79.00)

Slimline desktop case, 100 watt supply, math co-processor support. On board IDE, & Floppy controllers. 2 COM ports and 1 parallel port with software setup. Supports up to 8 Megs using standard 30 PIN SIMMs. Internal room for (1) 3 1/2 inch IDE hard drive and (2) 3 1/2 inch floppies. Four 16 BIT ISA slots, accepts full length AT size cards. Keyboard can be set to no test at boot. Case size is 15.5"W x 16"D x 4"H.

(Motherboard can be purchased separately: **\$29.00 or 2 for \$49.00**)

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.


CHASE SCIENTIFIC COMPANY




INNOVATORS IN VIRTUAL INSTRUMENTS

WINTER 1995-96, CATALOG NO. 3

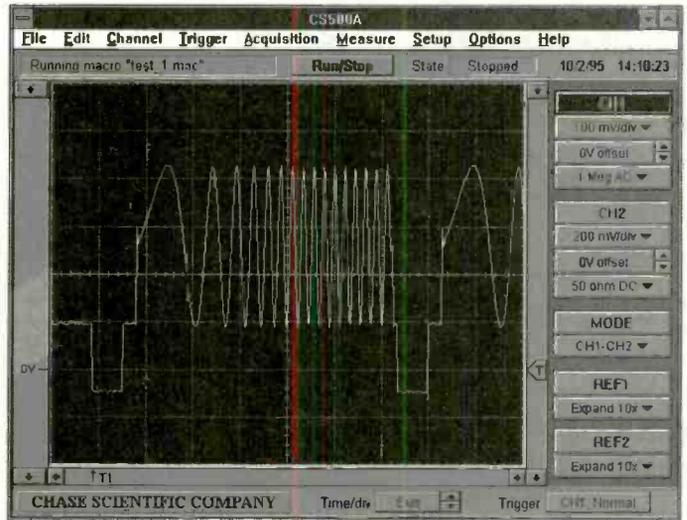Our NEW 500 Megasample/sec PC-Based Digital Storage Oscilloscope offers wider bandwidths (>200 MHz), better triggering (10 levels of intelligent programmability), and MORE MEMORY than any other scope board (up to 8 MEG/ch). - See pg. 3.



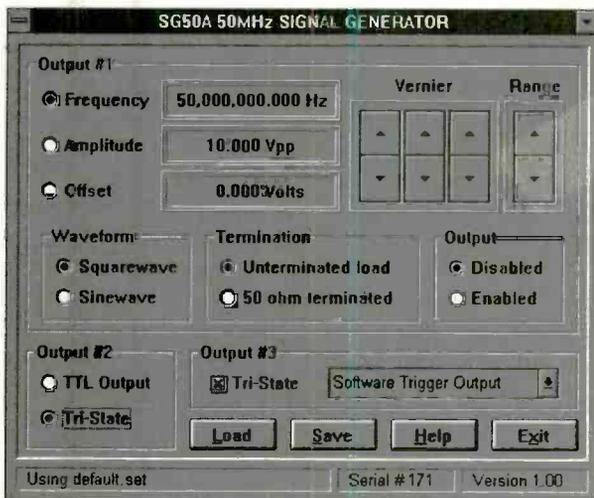This low cost synthesized Sine and Square wave generator produces signals from 0V to 10Vpp over a frequency range of 0.01 Hz to 50 MHz. Be sure to use our fax-on-demand for specifications that are not in this catalog. - See page 7.



Starting at \$239, this 5.5 digit Parallel Port Voltmeter is more powerful than others costing 10x. For slightly more you get 48 input channels, perfect for those thermocouple projects. - See page 2

Call 1-800-866-7899 for the rest of this catalog.

NEW 400 Ms/s PC-BASED Arbitrary Waveform Generator Targeted for 2nd Qtr. 1996

With a 100MHz bandwidth, this is one of the fastest and finest Arbitrary Waveform Generators around. If you

can't simulate your waveforms with this product, it probably can't be done.

Of course at \$995, there isn't much competition. Why is it so cheap you ask? The answer isn't hard to figure out. We're not charging you for power supplies, cases, knobs, microprocessors, monitors, and Fortune 500 overhead.

FOR PHONE IN ORDERS ONLY CALL 1-800-866-7899

We Honor Mastercard, VISA, Money Orders, Personal/Company Checks, and COD.

FOR COMPLETE SPECS Call our Fax-Back Service at 408-464-2584.

TO DOWNLOAD DEMO Software call our BBS at 408-475-6654.

FOR Technical Questions call 408-464-2584, fax 408-479-8572, or send Email to ChaseSci@aol.com, or 74634.1211@compuserve.com, or Write to Chase Scientific, 7960-B Soquel Drive, Suite 191, Aptos, CA 95003

CONTENTS

- 48 Input 5.5 Digit Voltmeter Works Via Parallel Port
- 3 High Performance 500 Ms/s, 200MHz PC Oscilloscope
- 4 Low Cost 20 - 60 MHz PC-Based Oscilloscopes
- 5 PC-based 400 MHz Arbitrary Waveform Generator
- 6 PC-Based Logic Analyzer
- 7 Low Cost 50 MHz PC-Based Signal Generator
- 8 Desktop Temperature Chamber works via Serial Port
- 9 PC-Based Power Supplies
- 10 SuperProbes™ (8-18 input word/pattern recognizers)
- 11 Complete Fax-on-Demand System for PC (we use it !)
- 12 The ULTIMATE Windows™ Calculator (57+ different calculators in one)


Tube & General Purpose Projects

NEW

HIGH QUALITY CHASSIS FOR NEW TUBE PROJECTS!



NEW LARGER SIZES

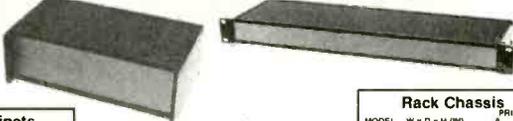


Audio Transformers for Tube Construction

Inputs - Line/Mic			
MODEL	PRI	SEC	PRICE \$
AT-1	150	60k	A MIC INPUT 40.50 42.50
AT-2	15k	15k	B LINE INPUT 40.50 42.50
AT-3	15k	60k	B LINE OUTPUT 46.75 48.50

Tube Outputs			
MODEL	5K	8	1100
OT-1	5K	8	B EL84 3 WATT 9.00 11.00
OT-2	5K	8	B EL84 10 WATT 12.00 16.00
OT-3	7k	4.5-1.8	B EL34 20 WATT 18.00 24.00

Power Supply			
MODEL	#1	SECONDARY	PRICE \$
PT-1	125V	6V3	A PRE 9.00 11.00
PT-2	250-0-250	5V 6V3	B SW 18.00 24.00
PT-3	300-0-300	5V 6V3	A AMP 10W 20.00 26.00
PT-4	400-0-400	5V 6V3	B 20W 24.00 30.00

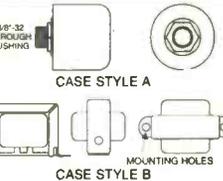

MENTION AD AND TAKE 5% OFF YOUR FIRST ORDER!

FOR MORE INFO REQUEST CATALOG TB-1

Rack Chassis

MODEL	W x D x H (IN)	PRICE \$
1RU5	19 x 5 x 1.75	34.00 44.00
1RU7	19 x 7 x 1.75	36.50 48.50
1RU10	19 x 10 x 1.75	40.75 50.00
1RU12	19 x 12 x 1.75	42.75 56.00
1RU15	19 x 15 x 1.75	45.75 58.00
1RU17	19 x 17 x 1.75	48.75 60.00
2RU5	19 x 5 x 3.5	36.50 48.50
2RU7	19 x 7 x 3.5	38.75 50.75
2RU10	19 x 10 x 3.5	41.25 53.00
2RU12	19 x 12 x 3.5	45.25 58.25
2RU15	19 x 15 x 3.5	48.25 60.50
2RU17	19 x 17 x 3.5	51.25 62.50
3RU5	19 x 5 x 5.25	48.00 58.50
3RU7	19 x 7 x 5.25	48.50 60.75
3RU10	19 x 10 x 5.25	51.00 63.00
3RU12	19 x 12 x 5.25	54.00 68.25
3RU15	19 x 15 x 5.25	57.00 70.50
3RU17	19 x 17 x 5.25	60.00 72.50



SESCOM ALSO STOCKS ALL KINDS OF USEFUL PARTS INCLUDING CONNECTORS, SCREWS, METERS, TOOLS, ETC.

Metal Cabinets

MODEL	W x D x H (IN)	PRICE \$
MC-1A	4 x 3 x 2	12.00 14.00
MC-2A	6 x 3 x 2	14.00 16.00
MC-3A	8 x 3 x 2	16.00 18.00
MC-4A	8 x 5 x 3	14.00 16.00
MC-5A	8 x 5 x 3	18.00 18.00
MC-6A	8 x 5 x 3	18.00 20.00
MC-7A	4 x 7 x 4	16.00 18.00
MC-8A	6 x 7 x 4	18.00 20.00
MC-9A	8 x 7 x 4	20.00 22.00
MC-10A	8.5 x 7 x 1.75	22.00 34.00
MC-11A	6.5 x 10 x 1.75	34.00 36.50
MC-12A	8.5 x 14 x 1.75	36.00 38.50
MC-13A	8.5 x 7 x 3.5	33.50 36.00
MC-14A	8.5 x 10 x 3.5	35.50 38.00
MC-15A	8.5 x 14 x 3.5	37.50 40.00
MC-16A	8.5 x 7 x 1.75	34.50 36.00
MC-17A	17 x 10 x 1.75	36.75 40.25
MC-18A	17 x 14 x 1.75	42.75 46.25
MC-19A	17 x 7 x 3.5	36.75 40.25
MC-20A	17 x 10 x 3.5	42.75 46.25
MC-21A	17 x 14 x 3.5	48.25 46.75

RACKEM 'N' STACKEM Table Top Racks

MODEL	HEIGHT (IN)	RACK UNITS	PRICE \$
RSR-8-19	8	A B	70.00 80.00
RSR-8-18	8	A B	75.00 87.50
RSR-18-19	18	A B	70.00 80.00
RSR-12-19	12	A B	70.00 80.00



PICTURED WITH OPTIONAL RE-1 RACK EARS

RACKEM 'N' STACKEM BOXES

MODEL	W x D x H (IN)	PRICE \$
RSB-3	7.5 x 3 x 1.5	25.00 30.00
RSB-4	7.5 x 3 x 1.5	25.00 30.00
RSB-7	7.5 x 3 x 1.5	38.00 43.00
RSB-9	7.5 x 3 x 1.5	45.00 50.00
RSB-11	7.5 x 3 x 1.5	51.50 56.50
RSB-13	7.5 x 3 x 1.5	58.25 63.25

ASSORTED MOUNTING ACCESSORIES ALSO AVAILABLE

ALL BOXES ARE SHIPPED FLAT FOR EASY FABRICATION
UNLESS OTHERWISE NOTED, BOXES HAVE FLAT PANELS CONSTRUCTED OF .0063" ANODIZED ALUMINUM (SIDES ARE 0.125"). FRONT AND REAR PANELS ARE CLEAR BALANCE OF BOX IS BLACK. BLACK OR GOLD FRONT & REAR AVAILABLE FOR AN ADDITIONAL \$5.00.

LC SERIES

FIELD REMOVABLE TOP AND BOTTOM 0.063" ANODIZED ALUMINUM PANELS. FRONT & REAR PANELS 0.063" GOLD ANODIZED ALUMINUM; OTHER PARTS BLACK ANODIZED. VENTED CAGES & OAK ENDS AVAILABLE.

MODEL	W x D x H (IN)	PRICE \$
LC-1	100 x 100 x 50	45.00 47.50
LC-2	150 x 100 x 50	50.00 52.50
LC-3	200 x 100 x 50	55.00 57.50
LC-4	300 x 100 x 50	60.00 62.50
LC-5	150 x 150 x 75	50.00 54.00
LC-6	200 x 150 x 75	55.00 59.00
LC-7	300 x 150 x 75	60.00 64.00
LC-8	400 x 150 x 75	65.00 69.00
LC-9	200 x 200 x 75	60.00 64.00
LC-10	250 x 200 x 75	65.00 69.00
LC-11	300 x 200 x 75	70.00 74.00
LC-12	425 x 200 x 75	75.00 79.00
LC-13	250 x 250 x 100	70.00 76.00
LC-14	300 x 250 x 100	75.00 81.00
LC-15	350 x 200 x 100	80.00 86.00
LC-16	425 x 250 x 100	85.00 91.00

SESCOM BOXES ARE USED BY HUNDREDS OF CONTRACTORS! USE IS LIMITED ONLY BY YOUR IMAGINATION!

Mini Project Boxes

GREAT LITTLE BOXES FOR LOW COST CONSTRUCTION DESIGNED TO GET THE JOB DONE WITHOUT THE FRILLS!

MODEL	SIZE (IN)	PRICE \$
MPB-1	1.5 x 2 x 1	1.95 2.25
MPB-2	1.5 x 4 x 1	2.40 2.75
MPB-3	1.5 x 6 x 1	2.85 3.25
MPB-4	1.5 x 2 x 1.5	2.05 2.25
MPB-5	1.5 x 4 x 1.5	2.55 2.85
MPB-6	1.5 x 6 x 1.5	3.00 3.60
MPB-7	1.5 x 6 x 3	3.25 3.55
MPB-8	1.5 x 4 x 3	2.75 3.15
MPB-9	1.5 x 6 x 3	4.00 4.50
MPB-10	1.5 x 2 x 5	2.50 3.00
MPB-11	1.5 x 4 x 5	3.00 3.50
MPB-12	1.5 x 6 x 5	4.25 5.05
MPB-13	2 x 2 x 2	2.20 2.60
MPB-14	2 x 4 x 2	2.65 3.15
MPB-15	2 x 6 x 2	4.00 5.00
MPB-16	2 x 8 x 2	6.85 7.35
MPB-17	2 x 2 x 3	2.45 2.95
MPB-18	2 x 4 x 3	2.90 3.50
MPB-19	2 x 6 x 3	4.30 5.30
MPB-20	2 x 8 x 3	4.85 5.45
MPB-21	4 x 8 x 3	4.55 5.15
MPB-22	4 x 10 x 3	4.75 5.45
MPB-23	4 x 12 x 3	5.70 6.50
MPB-24	4 x 14 x 3	6.10 6.80

PERFORATED OR PLENUM ALSO AVAILABLE



1" SQUARE ALUMINUM TUBING



SESCOM, INC.
2100 WARD DRIVE
HENDERSON, NV
89015 U.S.A.

ORDER TODAY
ALL PRICES INCLUDE WORLDWIDE SHIPPING!
A IS USA, CANADA & MEXICO, B IS REST OF WORLD

HOURS
Monday thru Friday
8 am 'til 4 pm (PST)

ORDERS (800) 634-3457 ■ FAX (800) 551-2749
OFFICE (702) 565-3400 ■ FAX (702) 565-4828
TECH LINE (702) 565-3993 M-Th 8 am to 4 pm (PST)
SESCOM, INC. is not responsible for inadvertent typographical errors.
Prices and specifications are subject to change without notice.

CIRCLE 269 ON FREE INFORMATION CARD

CABLE TV DESCRAMBLER KITS

Universal-New Product

This Product includes all the Parts, PC Board, Complete Schematic with Functional Guide. Generates Sync for most Video Applications.

\$79.95

Tri-Mode Descrambler

This product includes all the parts PC Board and AC Adaptor.
NO Enclosure included.

\$59.95

SB-3 Descrambler

This Product includes all the Parts, PC Board and AC Adaptor. Enclosure is not included.

\$44.95

Call Toll Free 1-800-886-8699

M & G Electronics, P.O. Box 3310, No. Attleboro Mass. 02761



Anyone implying theft of Cable service will be denied assistance. NO MASSACHUSETTS SALES!

Robot Explorer Newsletter

Nano-ants, flying robots, Martian explorers. Explore an entire universe of exciting robots. 8 information-packed issues for only \$14.95. Call now! MasterCard/Visa Accepted.


1-(800) GO-ROBOT or 1-(800)467-6268

INTERFACE TO YOUR PC KEYBOARD INPUT!

Our KE-18 Keyboard Encoder converts contact closures into PC compatible keyboard signals.

- Replaces your PC's keyboard or works in addition to it.
- Scan 9x9 matrix or 18 inputs
- PCT, AT, PS2 & Compatibles
- Compact 2.5" x 3.8" Size

Only \$59.95 & \$4 S&H

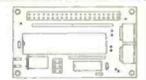

Hogstrom Electronics
2 Green Lantern Blvd.
Endicott, NY 13760
(607) 786-7523

CRYSTAL CONTROLLED SURVEILLANCE

VHF & UHF PROFESSIONAL ENCASED PARTIALLY ASSEMBLED TRANSMITTER KITS
Countersurveillance. Also Tunable 70 to 305 MHz Kits. We Design & Manufacture Our Equipment. Custom Design.

FOR CATALOG SEND \$2.00 TO:
SHEFFIELD ELECTRONICS CO., P.O. Box 377940-C
Chicago, IL 60637-7940. Tel. (312) 324-2196

RAINBOW

KITS

FM STEREO TRANSMITTER

Own your own FM radio station. Any stereo signal you plug into the FMST-100 will be transmitted to any FM radio tuneable from 76 to 108MHz FM. Transmit a wireless link through an auditorium, from your car to your camper, listen to your CD's while mowing the lawn, Play music on one channel sing on the other. Clarity is excellent, aprox. 40dB stereo separation. Length of antenna determines the distance of transmission. Complete with stereo input level controls & crystal for stereo separation. 9v battery operation. SIZE: 1.5" x 2.5" x 3"

FMST-100 KIT \$29.95 / Cabinet \$8.95

PHONE TRANSMITTER

Small but mighty, it fits anywhere. Phone line powered, never needs batteries. Transmits both sides of a phone conversation loud and clear, wireless, to any FM radio at great distances. Variable tunes from 70MHz to 130MHz FM. You can also use it as a speaker phone. SIZE: 1.25" x 6".

TEL-B1 KIT \$12.95 BUILT \$29.95

SUPER SNOOPER BIG EAR

Listen through walls, hear conversations across the room. Add a parabolic reflector and hear blocks away. The BIG EAR can be hidden about anywhere. Makes an ultra sensitive intercom. Can be used as a 1.5W AMP. We supply a mini-electret mike in the kit. Power requirement 6 to 12v DC. SIZE: 1.75" x 1"

AA-1 KIT \$10.95 BUILT \$29.95

WIRELESS FM MICROPHONE

Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal.

The WM-1 kit is a buffered wireless mike that operates from 80MHz to 120MHz FM, the frequency of any broadcast FM radio. Includes a mini-electret mike. 6 to 12v DC. SIZE: 1.25" x 1"

WM-1 KIT \$14.95

DC VOLTAGE MONITOR

If battery status is important, you need this kit. This kit uses 7 LEDs to monitor 12v DC in 1v, 1/2v, or 1/4v steps. Monitor 8v or 5v in 1/4v steps. Great for boats, motor homes, model planes or race car ni-cads. All parts and instructions are included. SIZE: 1.3" x 2.7".

VM-1 KIT \$7.95

The 10GHz Transmitter is back...

The "ZAPPER II"

With it's new and improved design it will not only test your radar detector ... BUT it's tuned to the amateur radio band .


- While your out on American highways personally test yours and your fellow travelers radar detectors.

The "ZAPPER II" is a 10.450 GHz to 10.550 CW oscillator. It has a code key jack installed for those who want to send Morse code.

BUILT \$49⁹⁵ KIT \$39⁹⁵

TV NOTCH

FOR CHANNELS 2 thru 22 ONLY

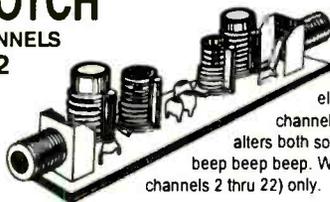

FILTERS

Our TV filters eliminate unwanted TV channels or interference that alters both sound and video with a beep beep beep. Works on cable channels 2 thru 22) only.

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

DF-222 KIT \$14.95

This Manual contains schematics, parts lists & P.C. board layouts for many of the Rainbow Kits. Use your own parts to construct our kits.

KIT BOOK

\$14.95 \$9.95 with the purchase of any kit.

Please add sufficient postage First lb \$5.00 Canada \$7.00 Additional LB. Add \$1.00 US FUNDS ONLY We will accept telephone orders for Visa or Mastercard



To Order Call 317-291-7262



ELECTRONIC RAINBOW INC

6254 LaPas Trail • Indianapolis, IN 46268
FAX 317-291-7269



STROBE LIGHT

Do you need an attention getter, warning light, or flashing light for model airplanes?


Then this kit is for you. Use it as an emergency light for your auto, radio tower, even use it on your bicycle. Has a variable flash rate. Power requirement 6 or 12v DC. Size 3.5"x1.9"

ST-1 KIT \$9.95

MICRO-LIGHT

Visible Over 1 Mile. This is truly an indestructible flash light.

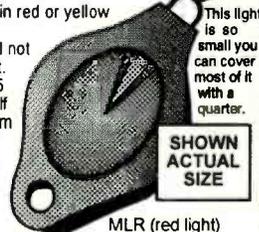- Comes in red or yellow light.
- Bulb will not burn out.
- Uses a 5 year shelf life lithium battery.
- Case made of tough ABS.



This light is so small you can cover most of it with a quarter.

SHOWN ACTUAL SIZE

MLR (red light)
MLY (yellow light) CHOICE \$9.95

4.0mW Laser Diode

Great for making a gun sight, use as a transit, makes a super experimenters project.

The beam is visible with a wavelength of 670 nm. Size of beam is 6mm at 5 meters. Power requirement 3 volts DC at 85mA. Size: 10.5mm x 18.5mm
LDM-5 New Low Price \$59.95

VOICE ACTIVATED SWITCH

This VOX circuit can be used to operate a tape recorder, ham radio, CB radio, or turn on an alarm. The VOX-1 kit has 100MA of output that operates a relay, light, motor, ? What could you do with a sound activated switch? Power requirement 7.5 TO 18vDC. SIZE: 1.5" x 1.3"

VOX-1 KIT \$6.95

WIDE BAND PREAMP

The ideal preamp for scanners, hand held radios, frequency counters. Amplifies low level

(weak) signals. If the signal is extremely low 2 amps can be used in series. 1MHz to 2.5GHz @ 2.8dB NF. 1dB compression = +0 dBm. Gain: 1MHz=20dB to 2.5GHz=6dB. Power requirement 12v DC @ 6Ma. SIZE: 1.2" x .8"

WBA-6 KIT \$19.95



Cellular Phone Battery For Motorola

6V, 700 mA replacement battery for Motorola flip phones. Dark grey color.



Flip Phone Saver/Charger

Plug-in saver/charger for Motorola flip phones. Lifetime manufacturer warranty.



201 PanaVise Jr.

This mini vise is an invaluable bench top companion for the home hobbyist. PV Jr. uses the famous PanaVise design that turns, tilts, and rotates for a full range of movement. Ideal for soldering, gluing, and general work. Features jaws that open to 2-7/8", both vertical and horizontal grooves to hold work, and a fine adjustment knob. Net weight: 1 lb. 4 ozs.



#EN-365-300 \$19.95 EACH

Drive Belt Kit

We've selected 18 of our most popular VCR, cassette and turntable belts to include in this kit. 87 belts total, five each of 17 square belts from 2.3" to 13.2" for VCRs and cassettes, and 2 each of the 23.6" turntable belt. Have the belt you need in stock when you need it. A \$50.00 value. Net weight: 1/4 lb.



#EN-400-910 \$29.95 KIT

Pioneer 8" Woofer with Butyl Surround



8" paper cone woofer with a butyl rubber surround. Butyl rubber is extremely flexible and resists moisture better than foam. Half roll suspends the outside edge of the cone to allow distortion free sound.
 ♦Power handling: 80 watts RMS/150 watts max. ♦Voice coil diameter: 2 inches ♦Impedance: 8 ohms ♦Frequency response: 31-7000 Hz ♦Magnet weight: 30 ozs. ♦SPL: 91 dB 1W/1m ♦Vas: 2.44 ♦Qts: .26 ♦Xmax: .110 ♦Qes: .27 ♦Qms: 6.51 ♦Fs: 31 Hz ♦Net weight: 7 lbs. ♦Manufacturer model number: B20GR30-51F-Q. ♦Hole to hole: 7-3/4".



#EN-290-042 \$34.50 (1-3) \$29.95 (4-11) \$28.45 (12-UP)

Goldstar 20MHz Oscilloscope

The OS9020A combines both high quality and low cost, making it ideal for educational, industrial, and hobbyist applications. Features include: DC-20MHz analog bandwidth ♦6" high luminance CRT ♦Dual channel, dual trace ♦Max sweep time of 20ns/div ♦Trigger level control ♦Separate circuit for TV sync ♦Variable hold-off function.
SPECIFICATIONS: Vertical: Deflection factor: 5mV/div to 5V/div in 10 calibrated steps. Rise time: 17.5ns or less. Max input voltage: 250V (DC/peak AC). Modes: CH1, CH2, ADD, DUAL
 Horizontal: Sweep time: 0.2us/div to 0.2S/div in 19 calibrated steps. Modes: X1, X10, X-Y
 Trigger: Modes: Auto, Norm, TV-V, TV-H. Source: CH1, CH2, LINE, EXT.
GENERAL: Dimensions: 12-1/2"W x 5-1/2"H x 16-3/4"D. Net weight: 16-1/2 lbs. Acceleration potential: 2KV. Power requirements: 100V/120V/220V/240V, 50/60 Hz. Comes complete with power cord, (2) 10:1 probes, and manual.



GoldStar

#EN-394-100 \$385.00 EACH

Computer Monitor Testers




These compact devices can quickly and easily troubleshoot, test, and align computer monitors, without the need for a separate computer. The #390-705 is used to test EGA, VGA, SVGA, VGA-8514A and VESA monitors. The #390-700 is used to test MDA, CGA, EGA, VGA, SVGA, and VGA-8514A monitors. Generates the following video test patterns: color bars, cross hatch, dots, color raster (white, red, green, blue), and windows. Two video connectors are provided: a digital/TTL 9 pin and an analog 15 pin. The testers may be powered by either a 9V battery or an external AC adaptor (not included). Dimensions: 1-1/2" x 3-5/16" x 5-5/8". Net weight: 3/4 lb.


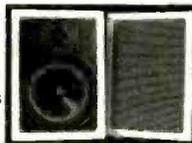
#EN-390-700 (Standard Monitor Tester) \$149.00 EACH
 #EN-390-705 (Monitor Tester w/High Res. VESA) \$149.00 EACH

6-1/2" Two Way System

This is our most popular in-wall. The 6-1/2" polypropylene woofer and 1" textile dome tweeter were specially designed with home theater in mind. 3 piece design make installation in new or existing walls a snap. Textured ABS frame and steel mesh grill are spray paintable to match (or blend into) any decor. System comes with speaker assembly, removable metal grill, heavy steel backer plates, screws and hardware, hole cut-out template, paint mask, and detailed installation instructions.
Specifications: ♦6-1/2" polypropylene cone woofer with poly foam surround. ♦1" textile dome tweeter/midrange. ♦8 ohm impedance. ♦3 component LC crossover network. ♦Frequency response: 50-20,000 Hz. ♦Power handling capability: 60 watts RMS/100 watts max. ♦Sensitivity: 89 dB 1W/1M. ♦Overall dimensions: 8-1/2" W x 12" L x 3-1/2" D. ♦Hole size: 7-1/4" x 10-3/4". ♦Fits into standard 2" x 4" wall. ♦Net weight: 12 lbs. per pair.



#EN-300-036 .. \$104.95 (1-3 PRS) \$96.50 (4-11 PRS) \$85.50 (12 PRS-UP)

12 Ga. Sound King Speaker Wire

Super flex, extra soft 60°C clear PVC insulation. Transfers music signals from the source to the speakers with high definition and clarity. Oxygen free, bare copper rope lay construction. Made in the U.S.A. ♦AWG: 12 ♦Construction: 259 x 36 Ga.



#EN-100-155 (100 ft. spool) \$39.90 (1-3) \$34.90 (4-UP)

♦30 day money back guarantee ♦\$20.00 minimum order ♦We accept Mastercard, Visa, Discover, and company C.O.D. orders ♦24 hour shipping ♦Shipping charge = UPS chart rate + \$1.90 (\$5.00 minimum charge) ♦Hours 8:00 am - 8:00 pm ET, Monday - Friday ♦9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ♦Foreign destination customers, please send \$5.00 U.S. funds for catalog.

Audax 1" Titanium Composite Dome Tweeter



Composed of pure titanium deposited on a polymer diaphragm, this composite offers the exceptional detail of metal domes while retaining the smoothness of soft domes. The result is outstanding clarity, low distortion and very high efficiency.
 ♦Power handling: 70 watts RMS/100 watts max. ♦Voice coil diameter: 1 inch ♦Impedance: 8 ohms ♦Frequency response: 2500-20,000 Hz ♦Magnet weight: 8-1/2 ozs. ♦Fs: 1500 Hz ♦SPL: 93 dB 1W/1m ♦Net weight: 1 lb. ♦Manufacturer model number: TW025M3 ♦Hole to hole: 3-3/8".



#EN-276-070 \$37.90 (1-3) \$34.75 (4-11) \$31.80 (12-UP)

The Wet Look™

The Wet Look™ is a new generation of high gloss polymers formulated especially for the speaker industry. This superior coating provides a protective "coat of armor" for your paper cone speakers. A special UV inhibitor has been added to reduce the decaying effects of the sun's ultraviolet rays. The Wet Look™ makes paper cones resistant to water, humidity, sun, and salt. Best of all, it's easy to apply and cleans up with soap and water. 1 pint can.



#EN-340-510 (Clear) \$8.95 EACH
 #EN-340-512 (Black) \$8.95 EACH

Profile A400 XL 2 Channel, 100 Watt Amplifier

This nice sounding MOSFET stereo amplifier gives you plenty of output power for the money. Includes built-in subwoofer boost, class AB operation, power light strip, bridgeable to 200W mono, thermal protection, variable input sensitivity, gold plated RCA and speaker level inputs. Dimensions: 8-1/4"(W) x 2-1/4"(H) x 8-1/2"(D). Net weight: 6-1/2 lbs.
Specifications: ♦2 Channel: 100W x 100W RMS (4 ohm load, .05% THD) ♦Mono: 200W (4 ohm load, .05% THD) ♦Subwoofer boost frequency: 80 Hz ♦Signal to noise: 100 dB ♦Channel separation: 60 dB ♦Damping factor: 200 ♦Output current: 10 amps per channel max.



#EN-265-136 \$143.50 EACH \$132.80 (2-UP)

Bulldog Model 7002PRO Alarm

The 7002 Pro utilizes a sophisticated microprocessor to offer these technologically advanced features: (2) two remote controls, 6 tone 127 dB siren, keyless entry, active arming, programmable passive arming with doors locking, programmable 30 second chirp, anti-car jacking feature, valet mode, dual stage shock sensor, instant panic, negative and positive door pin trigger inputs, automatic 35 second alarm reset, starter kill relay and socket, 6 function LED status, remote car finder, 2 negative outputs, 30 second last door arming, silent arming/disarming, and arm/disarm confirmation chirp. Lifetime limited factory warranty. Made in the U.S.A. Net weight: 2 lbs.



BULLDOG
CAR & PERSONAL SECURITY SYSTEM

#EN-330-312 \$99.95 EACH

FREE CATALOG



CALL TOLL FREE
1-800-338-0531

Parts Express™
340 E. First St., Dayton, OH 45402-1257
Phone: 513-222-0173 Fax: 513-222-4644

CIRCLE 262 ON FREE INFORMATION CARD



3-In-1 Universal Remote

This remote will operate any remote controlled cable box, TV or VCR at just a fraction of the cost of a factory replacement! This unit is already preprogrammed to include the most common codes. It is attractively styled, durable, and easy to set up and operate. The manufacturer even offers a toll free consumer help line to answer questions and provide customer assistance. Requires 2 AAA batteries (not included).



#EN-180-565 \$11.95 (1-9) **\$9.95** (10-UP)

The Wet Look™

The Wet Look™ is a new generation of high gloss polymers formulated especially for the speaker industry. This superior coating provides a protective "coat of armor" for your paper cone speakers. A special U/V inhibitor has been added to reduce the decaying effects of the sun's ultraviolet rays. The Wet Look™ makes paper cones resistant to water, humidity, sun, and salt. Best of all, it's easy to apply and cleans up with soap and water. 1 pint can.



#EN-340-510 (Clear) **\$8.95** EACH
 #EN-340-512 (Black) **\$8.95** EACH

72 Pin Game Cartridge Connector

Quality replacement for the game cartridge connector used in Nintendo Entertainment Systems (NES). Repeated loading and removal of game cartridges damages the connector contacts and produces symptoms such as a flashing blank screen or distorted picture. Revitalize your unit by replacing the game connector. It's simple; there is no soldering required and only a phillips head screwdriver is needed to complete installation in minutes! Our replacement connector has gold plated game contacts for long life, superior conductivity, and resistance to oxidation. One year warranty.



#EN-091-900 **\$8.95** (1-9) **\$7.95** (10-UP)

BigFoot™


"Copper tip" design standard 1/4" phone plug. Unsurpassed quality ensures low noise and high conductivity connection. All metal/nylon construction with external solder connections. Insulator sleeve included. 5/16" ID barrel. Made in the U.S.A.


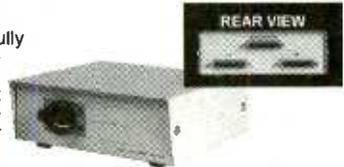
#EN-092-200 (Mono) **\$2.25** (1-9) **\$1.95** (10-49) **\$1.75** (50-UP)
 #EN-092-206 (Stereo) **\$3.25** (1-8) **\$2.90** (10-49) **\$2.65** (50-UP)

RS-232 A-B Switch


High reliability rotary type switch. Fully shielded, heavy gauge steel construction with gold plated connectors. All pins switched through (except ground). Used to switch multiple printers or computers. Full one year warranty. Net weight: 1-3/4 lbs.


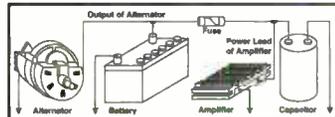
#EN-130-010 **\$9.95** (1-2) **\$8.95** (3-9) **\$7.95** (10-UP)

Car Stereo Power Supply Capacitors

Most car amplifiers' power supplies simply lack the capability to produce large amounts of instantaneous power. These computer grade, car stereo capacitors work by storing energy and supplying, on demand, a quick burst of energy to the power amplifier. The result is tremendous bass punch and dramatically improved transient response. Feature gold plated terminals.



Part #	Value	Voltage	Dimensions	Weight	Price (1-15)	Price (16-UP)
EN-029-1000	1,000,000 uf	16 VDC	3"(dia.) x 8-1/2"	3 lbs.	\$59.80	\$52.80
EN-029-1005	1,000,000 uf	20 VDC	3"(dia.) x 8-1/2"	3 lbs.	79.80	73.50

Printer Cables

25 pin male RS-232 to 36 pin male Centronics connector. Fully shielded and molded cable with all 25 conductors connected. Convenient thumbscrew hardware on the RS-232 connector.



Part #	Length	Price (1-9)	Price (10-49)	Price (50-UP)
EN-130-220	6 ft.	\$4.50	\$3.90	\$2.90
EN-130-225	10 ft.	5.50	4.95	3.75
EN-130-227	15 ft.	8.50	7.90	5.90
EN-130-228	25 ft.	10.90	9.50	7.90
EN-130-229	50 ft.	19.80	17.50	14.90



Video School videos make it easy for anyone to comprehend the complex operations of VCRs, camcorders, and more. From *How to Clean VCRs for the video rental store*, to *Minor Camcorder Repair for the advanced service shop*. There is something for everyone! These tapes also make great new employee orientation videos.

Electronic Video Library


Save over \$25.00 by purchasing this complete library of six Video School instructional videos. You'll receive VCR 1-How To Clean VCRs, VCR 2-Minor VCR Repair I, VCR 3-Minor VCR Repair II, VCR 4-Common VCR Malfunctions, VCR 5-Diagnosing Video Heads, and Cam 1-Minor Camcorder Repair. Net weight: 5 lbs.



BUY THE SET AND SAVE!

#EN-505-550 **\$195.00** EACH

Part #	Description	Price
EN-505-010	VCR 1, How To Clean VCRs	\$28.95
EN-505-020	VCR 2, Minor VCR Repair I	38.95
EN-505-025	VCR 3, Minor VCR Repair II	38.95
EN-505-050	VCR 4, Common VCR Malfunctions	38.95
EN-505-035	VCR 5, Diagnosing Video Heads	38.95
EN-505-030	VCR Test Patterns Alignment Tape	23.95
EN-505-040	Cam 1, Minor Camcorder Repair	38.95
EN-505-085	Microwave Oven Repair	39.95
EN-505-080	Nintendo Repair and Maintenance	33.95
EN-505-090	IBM Compatible Computer Assembly	28.95
EN-505-095	Hi-Fi Alignment Test Tape	29.95

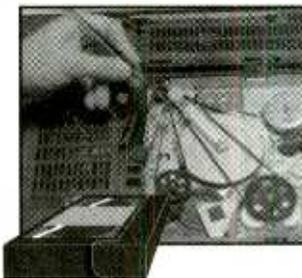

Skew Driver Pro



This unique tool features a gear driven offset bit driver to be used in tight spots or where conventional screwdrivers just won't fit. Includes 1/4" and 3/16" slotted bits, T15 Torx® bit, and 2 phillips bits that are contained in the handle compartment. Can also be used with a 1/4" electric drill. Made in the U.S.A. Net weight: 1/2 lb.

#EN-360-178 **\$39.90** (1-5) **\$34.50** (6-UP)

FREE



CATALOG

Parts Express™
 340 East First St.
 Dayton, Ohio 45402-1257
 Local: 513-222-0173
 FAX: 513-222-4644

CALL TOLL FREE
1-800-338-0531

CIRCLE 262 ON FREE INFORMATION CARD

**8-COLOR LED
A RAINBOW OF LIGHT!
4 for \$11.00**

Imagine an LED capable of producing eight different colors, including near-white! Imagination becomes reality with this T-1-3/4 multi-color LED. Here's the technology: a red chip, a green chip, and two blue chips encased in a diffused T1-3/4 package. Using various current combinations, you can produce red, orange, yellow, green, aqua, blue, violet or white light! Detailed spec sheet included. What can you do with these (beyond the obvious amaze your friends!)? Create a single indicator system, designate various controls by color, make your project something out of the ordinary with multicolor LEDs!

gateway
ELECTRONICS, INC
8123 PAGE BLVD • ST. LOUIS, MO 63130
(314)427-6116
9222 CHESAPEAKE DR. • SAN DIEGO, CA 92123
(619)279-8802
2525 FEDERAL BLVD. • DENVER, CO 80211
(303)458-6444
MAIL ORDERS CALL TOLL-FREE
1-800-669-5810
FAX ORDERS (314)427-3147
**ELECTRONICALLY SPEAKING,
GATEWAY'S GOT IT!**

5 mW LASER
5 MW LASER MODULE \$55.00
Mini 5 mW visible laser module
Wavelength: 630 - 680 nm.
3/4" x 1/2"
COMPLETE UNIT HAS A BUILT-IN POWER SUPPLY AND AN ADJUSTABLE CUMULATING LENS.
OPERATES ON 3 VOLTS DC
(A PAIR OF AA OR AAA BATTERIES WORK GREAT)
WARNING: AVOID DIRECT EYE CONTACT!

PHOTON MICROLIGHT \$10.00
8 Candellas of bright red or yellow light, visible over a mile away! This super-bright LED is secured in a tough ABS case and runs on a 3V lithium battery (included)! It won't burn out because it is an LED! Specify red or yellow when ordering. Battery has a 5 year shelf life and lasts up to 11 hours. (replacement battery \$0.98). Great for home or office use, popular with fire and rescue professionals, pyrotechnicians, stage performers, and more.

**NEW Compaq Laptop Computer
Nicad Rechargeable Battery Pack**
7.2 volts @ 120 mA. Many uses - power your projects for pennies!!!
\$4.95
approx. 3-1/2" x 1" x 3/8"

VIDEO MONITOR
with built-in 2-way switcher \$75.00
9" solid-state Black and White monitor has RCA connector for easy hook-up to your video camera. Built-in 2-way switcher enables you to use two cameras. These refurb units are great for security applications! Approximately 8-1/2" x 8-1/2" x 9-3/8"
(*mail order customers please include \$15.00 for shipping & handling)

LIGHTED HEADSET MAGNIFIER \$27.50
A great new item, this is a hands-free way to see little tiny parts as you work on them without having to be a contortion artist with a soldering iron! The headband style magnifier features bright side lights (4 AAA batteries not included) so you can add a little light to the area without clutching a flashlight under your chin! The velcro adjustable headband fits comfortably around your head, and the "goggles" pull down over your eyes for easy visibility. The visor has a built-in 1.8X lens plus a flip-down magnifier lens and a pull-down loupe for extra magnification power up to 4.8 times!

Passive Infra-red Talking Motion Detector III! \$27.50
"Stay out of that refrigerator!", "Watch your step!" ... The possibilities are mind-boggling with this talking motion detector. You speak into it to record your message (up to 12 seconds long), turn the unit on, and instantly your voice (or your mother-in-law's) reminds anyone in the vicinity that you were expecting them. Message can be changed with the flip of a switch. Uses 4 AA batteries (not included), or an external power source (built-in jack). May be used independently (80 db output) or with an amplified speaker to blast your message throughout the house. Approx 4" x 3-1/2" x 1-1/2".

127 THERMOCOUPLES Peltier Junctions
The peltier junction is a solid-state thermoelectric device. Current applied to the device will produce heat on one side of the device and a cold surface on the other side. Water placed on the surface will freeze or boil depending on polarity of applied voltage. Ideal for applications from 3-12 VDC -- grab a battery and let your imagination run wild!
DOCUMENTATION INCLUDED!!!
Small \$20.00 (approx. 1.17" x 1.17" sq. 12")
Large \$29.50 (approx. 1.56" x 1.56" x .15")

THE FINE PRINT: PRICES SUBJECT TO CHANGE WITHOUT NOTICE * GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS * MASTERCARD, VISA AND DISCOVER ACCEPTED * \$10 MERCHANDISE MINIMUM ON MAIL ORDERS * SUPPLY OF SOME ITEMS IS LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED). \$4.25 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. WHO IS GENERAL FAILURE AND WHY IS HE READING MY DISK!

CIRCLE 243 ON FREE INFORMATION CARD

**Tired of Paying Rent
To Your Cable Company?**

**WHY RENT WHEN
YOU CAN OWN?
TAKE
CONTROL
OF YOUR
TV!!!**



- Over 5 Yrs. Experience
- Excellent Customer Service
- Prompt Delivery Anywhere
- Tell Your Friends About Us
- Call Today For Our LATEST SPECIALS!

**IT'S LEGAL!
Cable TV Converters
& Remotes**

**CALL TODAY!!!
1-800-228-2677**


Mon. thru Fri. / 8 am - 8 pm
Saturday / 9 am - 2 pm



P.O. Box 1282 • Beloit, WI 53511




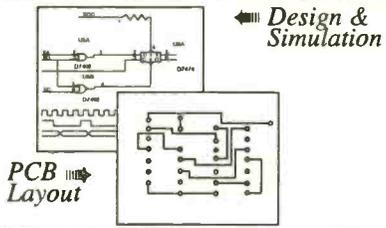**Low Cost CAD Software
for the IBM PC and Compatibles
Now In Windows™ 95**



- Easy to use schematic entry program (SuperCAD) for circuit diagrams, only \$149. Includes netlisting, bill of materials, extensive parts libraries.
- Powerful, event-driven digital simulator (SuperSIM) allows you to check logic circuitry quickly before actually wiring it up. Works directly within the SuperCAD editor from a pull-down menu and displays results in "logic analyzer" display window. Starting at \$149 this is the lowest cost simulator on the market. Library parts include TTL, and CMOS devices.
- Analog simulator (SuperSPICE) for \$149. Allows AC, DC and transient circuit analysis. Includes models of transistors, discretes, and op amps.
- Circuit board artwork editor and autorouter programs (SuperPCB), starting at \$149. Produce high quality artwork directly on dot matrix or laser printers. You can do boards up to 16 layers including surface mount. Includes Gerber and Excellon file output. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- Low cost combination packages with schematics and PCB design: 2-layer for \$399, 16-layer for \$649.

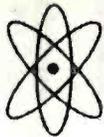Write or call for free demo disks:
MENTAL AUTOMATION, INC.
5415 - 136th Place S.E.
Bellevue, WA 98006
(206) 641-2141
BBS (206) 641-2846



TECH-SYSTEMS

1309 Hwy. 71 Belmar, NJ 07719
908-280-0007 FAX: 908-280-0111

800-435-1516

BUY - SELL - TRADE
VISA & MasterCard Accepted

90 Day Warranty / 10 Day Right of Return

N.I.S.T. Traceable Calibration Available on Most Items

SPECTRUM ANALYZERS

TEK 492/01/02 Spectrum Analyzer 50KHz to 21GHz	\$6,995
Option D1 Adds Internal Preselection and D2 Adds Digital Storage	
TEK 492/02 Spectrum Analyzer 50KHz to 21GHz	6,650
Option 21 18GHz to 40GHz Waveguide Mixer Set	1,775
TEK 496 1kHz - 1800 MHz Spectrum Analyzer	4,750
TEK 7L12 100KHz to 1800MHz Spectrum Analyzer Plug-In	1,850
TEK 7L13 1KHz to 1800 MHz Spectrum Analyzer Plug-In	2,495
TEK TR503 Tracking Generator w/TM503 Power Supply	1,450
HP 141T/B552B/B555A 10 MHz to 18GHz Spectrum Analyzer	2,195
HP 141T Variable Persistence/Storage Display	595
HP 140T Non-Storage Display	425
HP 8553B 1KHz to 110MHz RF Section	450
HP 8554L 100KHz to 1250MHz RF Section	550
HP 8554B 100KHz to 1250MHz RF Section	795
HP 8555A 10MHz to 18GHz RF Section	995
HP 8556A 20Hz to 300 KHz LF Section	450
HP 8552B IF Section	650
HP 8552A Economy IF Section	295
HP 8443A 0.1 to 110MHz Tracking Generator	550
HP 8444A 0.1 to 1300MHz Tracking Generator	795
HP 8444A/059 0.5 to 1500MHz Tracking Generator	1,350
HP 8445B 1.8 to 18GHz Preselector	650
HP 182T Mainframe	495
HP 182T/8557A 10KHz to 350MHz Spectrum Analyzer	1,495
HP 182T/8558B 100KHz to 1500MHz Spectrum Analyzer	3,350
HP 8557A 10KHz to 350MHz Spectrum Analyzer Plug-In	1,250
HP 8558B 100KHz to 1500MHz Spectrum Analyzer Plug-In	2,395
HP 8559A 0.01 to 21GHz Spectrum Analyzer Plug-In	4,450

OSCILLOSCOPES

TEK 465 100MHz Portable Scope	\$595
TEK 475 200MHz Portable Scope	795
TEK 485 300MHz Portable Scope	995
TEK 2465 300MHz Portable Scope	2,595
HP 1741A 100MHz Portable Scope	495
HP 1725A 275Hz Portable Scope	695
HP 54200A 50MHz/200Msa/s Digitizing Scope	2,250
HP 542000 50MHz/200Msa/s Digitizing Scope	2,650
HP 54201D 300MHz/200Msa/s Digitizing Scope	2,995
HP 541100 1GHz/40Msa/s Digitizing Scope	5,995
HP 54111D 500MHz/1Gsa/s Digitizing Scope	6,995
TEK 7603 w/7A18 (X2) & 7B53A Scope	695
TEK 7104 w/7A29 (X2), 7B10 & 7B15 Scope	5,995

Over 600 TEK 7000, 5000 & TM Series Mainframes and Plug-Ins

Call for pricing information

WAVE - DISTORTION - MODULATION

HP 331A Distortion Analyzer 5Hz - 600 kHz	\$195
HP 332A Distortion Analyzer with AM Detector	295
HP 333A Distortion Analyzer with Auto Nulling & High Pass Filter	395
HP 334A Distortion Analyzer with Auto Nulling/High Pass Filter/ AM Detector	495
HP 35B1C Selective Level Meter	995
TEK AA501 Distortion Analyzer	1,295
BOONTON 82AD/01/03/04 Modulation Meter	995
Marconi 2305 2.32GHz Modulation Meter w/IEEE	4,995

STANDARDS & CALIBRATORS

FLUKE 5100B/03/05 Multifunction Calibrator	\$5,750
FLUKE 3330B DC Calibrator	1,995
FLUKE 515A Portable Calibrator AC/DC/RES	1,695
FLUKE 332B DC Calibrator	595
FLUKE 5205A AC Amplifier	2,650
FLUKE 5450A Resistance Calibrator 1 Ohm to 100 megohms/Bppm	1,995
FLUKE 730A DC Transfer Standard	450
FLUKE 750A Reference Divider	450
FLUKE 720A Kelvin Varley Divider	1,895
ESI RV722 DC Voltage 1ppm Accuracy	1,295
DATRON 4200/30/80 Autocal AC Standard	2,495
BOONTON 25A Power Meter Calibrator	450
BOONTON 2500A Power Meter Calibrator	450
HP 8477A Power Meter Calibrator	495
HP 116B3A Range Calibrator	775
TEK PG508 Calibration Generator	1,350
TEK TG501 Time Mark Generator	1,350
TEK SG503 Leveled Sine Wave Generator 250KHz to 250MHz	1,350
TEK SG504 Leveled Sine Wave Generator 245MHz to 1050MHz	2,650
RFL B29G Multi-Function Calibrator	1,495

FREQUENCY COUNTERS

HP 5314A 100MHz Universal Counter	\$225
HP 5315B 100MHz Universal Counter	495
HP 5316A 100MHz Universal Counter	695
HP 5328A/011/030 512MHz/IEEE Universal Counter	695
HP 5328A/011/031 1.3GHz/IEEE Universal Counter	895
HP 5340A/011 18GHz/IEEE Microwave Counter	1,950
HP 5342A/011 18GHz/IEEE Microwave Counter	2,750
HP 5300B/5303B 525MHz Counter	450
HP 5257A Transfer Oscillator for HP 5245 Counters	175
HP 5255A 3 to 12.4GHz Frequency Converter	175
HP 5359A Time Synthesizer	1,895
SYSTRON DONNER 6054B 20Hz to 28.5GHz IEEE Microwave Counter	2,295
TEK DC5009 Programmable 135MHz Universal Counter	695
TEK DC505A 225MHz Universal Counter Plug-In	295
TEK DC508 1.3GHz Universal Counter Plug-In	450

SIGNAL SOURCES

HP 8640B/003 512MHz Signal Generator w/Reverse Power	\$1,895
HP 8640B/001/002 1024MHz Signal Generator w/Audio Oscillator	2,795
HP 8656A 100KHz to 990MHz Synthesized Signal Generator	2,995
HP 8660C/86603A/86632B 2600MHz Synthesized Signal Generator	3,995
HP 8660A/86602A/86632B 1300MHz Synthesized Signal Generator	2,350
HP 8620C Sweeper Mainframe	395
HP 86222A D.01 to 2.4GHz RF Plug-In	1,495
HP 86222B/001 0.01 to 2.4GHz RF Plug-In w/Crystal Markers & 70dB ATTN	1,795
HP 86290C 2 to 18.6GHz RF Plug-In	2,395
HP 86260A 12.4 to 18GHz RF Plug-In	995
HP 8697A 26.5 to 40GHz RF Plug-In	1,450
HP 214B Pulse Generator	1,995
HP 8005B 20MHz Dual Pulse Generator	450
HP 8007B 100MHz Pulse Generator	695
HP 8013B 50MHz Dual Pulse Generator	895
HP 3312A 13MHz Function Generator	895
BOONTON 2000 20GHz Sweep Generator	2,450
TEK FG501 2Hz to 2MHz Function Generator	195
TEK FG502 1KHz to 11MHz Function Generator	295
TEK FG503 1 to 3MHz Function Generator	195
TEK PG501 50MHz Pulse Generator	250
TEK PG502 250MHz Pulse Generator	495
TEK PG508 50MHz Pulse Generator	795
APPLIED MICROWAVE/EPSCO PG5KB 5kW/575 to 925MHz RF Pulser	2,995
VELONEX 380 5kW High Power Pulser	2,995
COBER 605/P27 2kW/10Hz to 1MHz High Power Pulser	1,350

OVER 3000 ITEMS IN STOCK !

Inventory Changes Daily!

OVER 500 DC & AC POWER SUPPLIES !

Any Voltage - Any Current ! CALL

CALL FOR FREE 40 PAGE CATALOG

COMPONENT TEST

HP 4342A Q Meter (22KHz to 70MHz)	\$2,495
HP 4342A/001 Q Meter (10KHz to 32MHz)	1,650
BOONTON 5110 LCR Meter 100Hz, 120Hz & 1 KHz Test Frequency	1,450
includes 5110-1 Test Adapter & 5110-4 Kelvin Clip Adapter	
BOONTON 72BD Digital Capacitance Meter 1MHz Test Freq. 2pF to 2000pF	750
TEK 576 Curve Tracer	2,995
TEK 577/D2 Curve Tracer	1,695
HUNTRON TRACKER 5000 Computer Controlled Troubleshooting System	1,350
SAUNDERS 150C/09 Crystal Test Oscillator Microprocessor Controlled/IEEE/1 to 60MHz	1,695
GENRAD 1630AV Inductance Measuring System	2,995

**We Buy & Sell Service Manuals
Coax/Waveguide Components**


WANTED !

**Surplus Electronic Test Equipment
FAX US YOUR LIST**

FAX: 908-280-0111

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING with the New AES-10

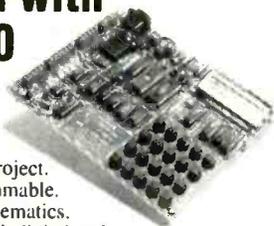The AES-10... a complete learning system, a complete embedded control system. Extensive manuals guide you through your 8051 development project. Assembly, BASIC, and C programmable. All hardware details, complete schematics. Learn to program the LCD, keypad, digital and analog I/Os. The entire board is software reconfigurable for your applications. Everything you need, nothing extra required.



80C32 Computer/Microcontroller board with:

- 32K Byte ROM , 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Two serial ports • 5 interrupt sources • 3 timers • A/D , D/A, PWM and digital I/O • Built in Logic Probe • Power supply (can also be battery operated) • Extended Intel BASIC and AES Monitor in ROM • RS-232 cable to connect to PC for programming • 8051/52 DOS Cross Assembler • Program disks with well documented examples • User's Manual, Language Manual, and Text (over 400 pages).

AES-10 \$285 Complete
Money Back Guarantee

Free Info Pack, M/C Visa
714 - 550-8094
Fax 714 - 550-9941


AES
Advanced Educational Systems

970 W. 17th St., Santa Ana, California, 92706 USA

CALL 1 - 800 - 730-3232

8085 MICROPROCESSOR TRAINING & CONTROL SYSTEM

Are you interested in Single Board Computers and Microprocessor-based control systems? If the answer is yes and you want to know more about these fascinating subjects the PRIMER Trainer is the place to start. The PRIMER teaches more and is easier to use than other comparably priced trainers. Enter a program into RAM, run it, and then burn it into EPROM with the optional EPROM Programmer. The over 100 page Self Instruction manual takes you from binary number systems to processing interrupts. At the end of the manual are working examples of using a photocell, a temperature sensor, making a waveform generator, a programmable timer with alarm, writing to LCDs, scanning keypads, and controlling the speed of a motor. The PRIMER comes with everything you need to start programming in machine language. Continue on to program in Assembler, Forth or BASIC with optional upgrade and software. Upgrade includes: RS232 serial port, a serial cable, 32K of battery backed RAM and Assembler/Terminal software. Picture shown with upgrade option (\$49.95) and optional heavy-duty keypad (\$29.95) installed.

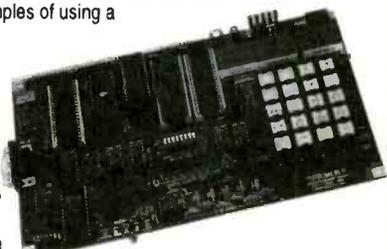

THE PRIMER IS ONLY \$119.95 IN KIT FORM. THE PRIMER ASSEMBLED & TESTED IS \$169.95. RECEIVE ONE FREE POWER SUPPLY WHEN YOU MENTION THIS AD. PLEASE ADD \$5.00 FOR SHIPPING WITHIN THE U.S.

1985 - 1995
10
YEAR
ANNIVERSARY

ENAC, inc.

618-529-4525 Fax 457-0110 BBS 529-5708
P.O. BOX 2042, CARBONDALE, IL 62902


\$449⁹⁵

Device Programmers

\$139⁹⁵

48 PIN
ZIF

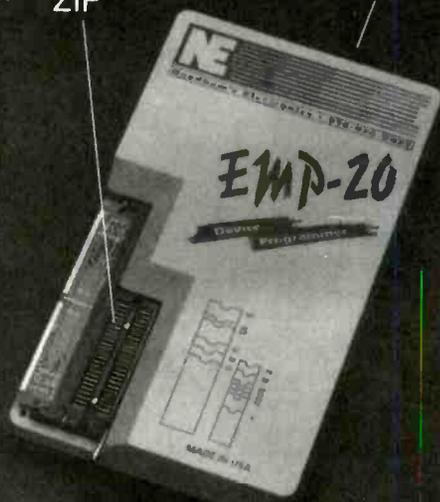Connects to standard
PC parallel printer port



9¹/₂ x 5³/₄ x 1¹/₄

EMP-20

- Easy to use software, on-line help, full screen editor

- **Fast Programming (EMP-20)**

27C010A, 23 seconds
28C020, 34 seconds
27C040, 95 seconds

- **Made in USA**

- 1 Year Warranty

- Technical Support by phone

- 30 day Money Back Guarantee

- FREE software upgrades available via BBS

- Demo SW via BBS (EM20DEMO.EXE) (PB10DEMO.EXE)


- **E(ə)proms** 2716 - 8 megabit, 16 bit 27210-27240, 27C400 & 27C800,

- **Flash** 28F256-28F020, (29C256-29C010 (EMP-20 only))

- **Micros** 8741A, 42A, 42AH, 48, 49, 48H, 49H, 55, 87C51, 87C51FX, 87C751,752

- **GAL, PLD** from NS, Lattice, AMD-16V8, 20V8, 22V10 (EMP-20 only)

PB-10 Internal Card for PC

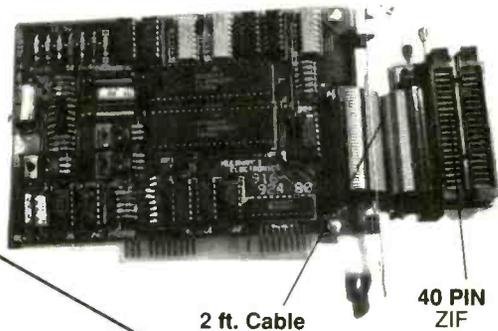

2 ft. Cable

40 PIN
ZIF

FOR MORE INFORMATION CALL

4630 Beloit Drive, Suite 20
Sacramento, CA 95838
(Monday-Friday, 8 am-5 pm PST)

NEEDHAM'S ELECTRONICS, INC.



C.O.D.



(916) 924-8037

BBS 916-924-8094

FAX 916-924-8065

CIRCLE 257 ON FREE INFORMATION CARD

If You DON'T Believe these Professionals

Lane Norman - Normans Electronics Inc. Atlanta GA
A cost effective solution to desoldering equipment at less than half the price of most equipment. It's performance is ASTOUNDING.

Mike Murphy - Service Center Co-Van Nuys CA
The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

Bob Monroe - M.A.R.C. Electronics - Virginia Beach VA
Best investment we've made. Saves time, especially with multi-sided PCB's. Extremely pleased with warranty. Failed within 6 months and replaced by DEN-ON overnight.

Dick Manning - Dicks Electronics - Hartland WI
The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

Dave Hayes - E-H Engineering Ltd - Lincoln NE
Has been a durable & reliable desoldering unit. Our use has been both lab & field application over the last 2 yrs. with positive results.

Bob Sorrels CET/CSM Polytronics Microcomputer - Shreveport LA
We've used our SC7000 almost every day for about three years with virtually no problems. Just clean it before you turn it off for the day.

George Hefner - Hefner Electronics - Coleridge NE
Being a one-men service center, I hesitated to spend the money on a desoldering tool, however all that changed when I nearly ruined a \$400 computer logic board. I use the SC7000 daily. It has cut my desoldering time by 50 to 75%.

Steven Gray - Electronic Wizards - Wichita KS
By far the best desoldering tool we've ever used. Much more suction than other similar types we've tried. No trouble with postage stamp IC's or anything else.


Dennis McMannis - Thorn Services International - Mabelton GA
The SC7000 has decreased my use of wick by 75% and at \$25 a roll, it pays for itself within months. My total bench time is reduced by approx. 20%.

Don Cressin - Certified Electronics Service - Ellicott City MD
We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

Doug Pettit - LuRay Electronics - LuRay VA
We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

Paul Horvat - Service Excellence Inc. - Dumont NJ
It has made a almost impossible job (desoldering a 64 pin CPU) a piece of cake. Glad I found you.

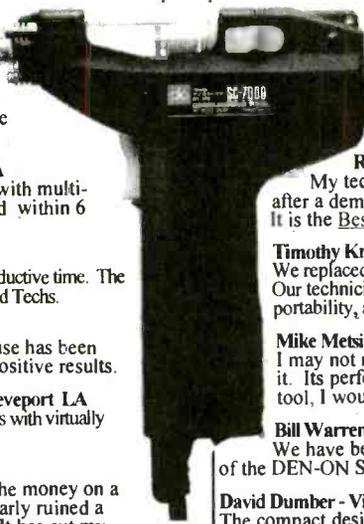Harold Smedberg - Smedberg Electronics - Custer MI
The SC7000 has reduced my damage to PC boards by 90%. It has also decreased my desoldering time by 50%. The best priced tool on the market.



Tom Mullett - JC Penny TD&S - Wausatose WI
The SC7000 is a very easy to use, self-contained desoldering tool. We had a 70% increase in production after the purchase of the SC7000. I highly recommend it.

Paul Reindorf CET - Osage Comm. - Santa Fe NM
This tool has paid for itself over & over again. I don't know how we ever did without it.

Randy Whitehead - Service West - Salt Lake City UT
My techs thought it would be a waste. I bought one anyway after a demo. My techs then fought over it. Now we have three. It is the Best desoldering tool we have ever used.

Timothy Kraft - Monikraft, Inc. - Cherry Hill NJ
We replaced all our existing desoldering stations with the SC7000. Our technicians are very pleased with the improved performance, portability, and reliability over our previous higher priced equipment.

Mike Metsikas - RGB Services - Philadelphia PA
I may not need this tool for every job, but when I do, I swear by it. Its perfect for field service because of it's size. An incredible tool, I wouldn't do another house call without it.

Bill Warren CET/CSM - Warrens Audio & Video - Knoxville TN
We have been extremely satisfied with the quality and durability of the DEN-ON SC7000 as well as with after the sale support.

David Dumber - Video Tech Center, Inc. - Belair MD
The compact design of the SC7000 boast optimum efficiency. I wouldn't trade it's performance for any system at even twice the price.

Keith Sabs - J & M Electronics - Omaha NE It's a must tool for my bench. I can desolder multiple pin IC's quickly and clean. It will even take up large solder amounts on tuner and case grounds.

Ray Wurmnest - Ray's Electronics, Inc. - Bloomington IL
The SC7000 saves time when changing out parts in the home or in the Service Center — Worth every penny we spent.

Don Multerer CET - Sencore - Sioux Falls SD
Good Techs love good tools - light weight, fast, easy to use. I use it to build electronic trainers where parts are removed and circuits modified.

Gale Holloway - Gale T.V., Inc. - Virginia Beach VA
Desoldering has never been easier. We use the SC7000 Desoldering Tool daily. We are fully satisfied with this product.

A.L. Hurdle CET - Corapeake NC The first time I used the SC7000 was on a 64 pin DIP. After removing the solder from the last pin of the IC, it just fell off the board. Highly recommended.

James Dietrich - Dietrich Electronics - Monroe NY Look mom, one hand, & I can go three times faster without breaking a sweat. I'll recommend anyone to DEN-ON Tools.

call FOR Your 15 DAY **FREE TRIAL**

on our

DEN-ON SC7000 Desoldering Tool

Free Trial Offer only valid within the Continental U.S.
30 Day Money Back Guarantee when paid for in advance

HOWARD HEINSTRUMENTS INC 1-800-394-1984 (316) 744-1984
6222 N. Oliver Wichita, KS 67220 **INC** or Fax (316) 744-1994
Jerry Howard CET, President We accept Visa, M/C, Discover, A/E, COD Company Check, and PO's from qualifying Co.'s

CIRCLE 216 ON FREE INFORMATION CARD

www.americanradiohistory.com

ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT
BEST PRICE



DMM 89 \$199.95
Most Advanced DMM
All Purpose & Communication
-80.7 to 81.4 dBm with 4Ω-1200Ω
20 reference impedances
True RMS
Frequency counter: 0.01Hz-10MHz
Capacitance: 1pF-50,000μF
Measure AC volt to 20kHz
5000 counts, 0.1% accuracy
Auto/manual range, fast bar graph
Min/Max/Ave/DH/Relative/Zoom
Auto power off
Input warning
Splash proof
Volt, amp, ohm, logic, diode, continuity
Ruggedized case
Rubber holster included



DMM 2360 \$119.95
DMM+LCR Meter
Very Versatile DMM
Inductance: 1μH-40H
Capacitance: 1pF-40μF
Frequency: 1Hz - 4MHz
Temperature: -40-302 °F
TTL Logic Test: 20MHz
Diode, Continuity
Volt, Amp, Ohm
3999 count display
Peak Hold
Auto power off
Ruggedized case
Temperature probe included
Rubber Holster \$8.00



DMM 20 \$74.95
Inductance: 1μH-40H
Capacitance: 1pF-200μF
Frequency: 1Hz-20MHz
Volt, amp, ohm, diode,
20 Amp AC/DC current
Transistor HFE
Continuity, duty %
Peak hold/Max
Ruggedized case
Rubber holster \$8.00

Full line of DMMs,
economy, compact,
ruggedized, solar cell,
automotive, heavy
duty, industrial,
starts from \$15.95


Fluke Multimeter
Fluke 12 \$84.95
Holster C-10 \$10
Fluke 70 II \$75.95
Fluke 73 II \$97.50
Fluke 75 II \$129
Holster C-70 \$16
Fluke 77 II \$155
Fluke 79 II \$175
Fluke 29 II \$175
Fluke 76 \$175
Fluke 87 \$287
Fluke 867 \$1199
Fluke 97
Scope Meter \$1785




LCR Meter 131D \$229.95
Most Advanced LCR
Dual display: L/Q or C/D
Inductance: 0.1μH-1000H
Capacitance: 0.1pF-10,000μF
Impedance: 1mΩ-10MΩ
0.7% basic accuracy
Auto/manual range
Dissipation factor & Q factor
Serial & parallel mode
Relative mode for comparison
and to remove parasitics
Statistics, tolerance,
Best for design, incoming
testing & production
SMD and chip component
test probe \$25.00



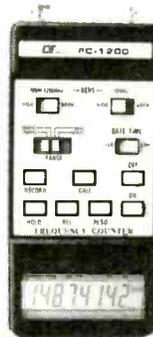LCR Meter 814 \$189.95
Best Resolution LCR
Inductance: 0.1μH-200H
Capacitance: 0.1pF-20,000μF
Resistance: 1mΩ-20MΩ
1% basic accuracy
Dissipation factor indicates leakage
in capacitor and Q factor in inductor
Zero adjustment to reduce parasitics
Best for high frequency RF
SMD and chip component test probe
\$25.00
LIMITED QUANTITY SPECIAL
DIGITAL LCR 680 \$74.95
0.1pF, 1μH, 10mΩ resolution




Frequency Counter FC-1200 \$129.95
Frequency: 0.1Hz-1.25GHz
Display: 8 digit LCD
Period: 0.1μs-0.1s
Records Max/Min/Average
Data hold, relative mode
Telescoping antenna \$8.00
Deluxe case \$5.00
Also Available:
AC/DC clamp meter, Light meter,
Thermometer, pH meter, High
voltage probe, Digital caliper,
Anemometer, Electronic scale,
Force gauge, Tachometer,
Stroboscope, Humidity & EMF
adapter, Sound level meter,
Frequency counter, SWR/field
strength/power meter, Dip meter

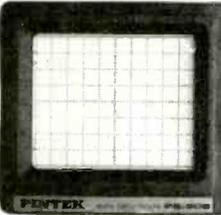


20 MHz Oscilloscope with Delay Sweep PS-205 \$429.95
Dual Trace, Component test, 6" CRT, X-Y Operation, TV Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes each has x1, x10 switch. Best price with delay sweep.
PS-200 20 MHz DUAL TRACE \$339.95
PS-400 40 MHz DUAL TRACE \$494.95
PS-405 40 MHz DELAY SWEEP \$569.95
PS-805 80 MHz DELAY SWEEP \$769.95
Scope Probe: 60MHz x1, x10 \$15, 100MHz x1, x10 \$22
250MHz x1, x10 \$29, 250MHz x100 \$39

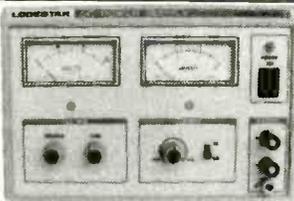
Digital Storage Scope DS-303 30MHz, 20M Sample/sec \$849.95
DS-303P with RS-232 Interface \$1,049.95
Switchable between digital and analog modes
2 K word per channel storage
8 bit vertical resolution (25 Level/div)
Expanded Timebase 10ms/div - 0.5 s/div
Refresh, Roll, Save all, Save CH2, Pre-Trig
Plotter control



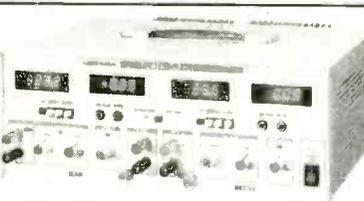DC Power Supply PS-303 \$159.00
0-30 VDC, 0-3A output
Constant voltage & constant current mode
0.02% + 2mV line regulation
0.02% + 3mV load regulation
1 mVrms noise and ripple
Short circuit and overload protected
PS-8200 with digital voltmeter \$179.00
Also available: 30V/5A, 60V/3A, 80V/5A
16V/10A, 30V/10A



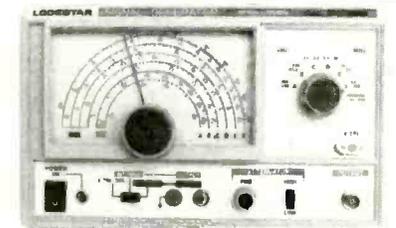DC Power Supply Triple Output PS-8202 \$499.95
Two 0-30 VDC, 0-3A outputs
One fixed 5VDC, 3A output
Capable of independent or tracking operation
Constant voltage and constant current mode
Four digital meters for volt and current display
Excellent regulation and low ripple
Short circuit and overload protected
Also available: 30V/5A triple output \$549.95
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A



RF SIGNAL GENERATOR SG-4160B \$124.95
100 kHz-150MHz sinewave in 6 ranges
RF Output 100mVrms to 35 MHz
Internal 1kHz, External 50Hz-20kHz
AM modulation
Audio output 1 kHz, 1 Vrms

AUDIO GENERATOR AG-2601A \$124.95
10Hz - 1MHz in 5 ranges
Output 0-8Vrms sinewave
0-10Vp-p squarewave
Synchronization: ±3% of oscillation frequency per Vrms
Output distortion:
0.05% 500Hz - 50kHz
0.5% 50Hz - 500kHz
Output impedance: 600 ohm

FUNCTION GENERATOR FG-2100A \$169.95
0.2 Hz - 2 MHz in 7 ranges
Sine, square, triangle, pulse and ramp
Output: 5mV-20Vp-p
1% distortion, DC offset ± 10V
VCF: 0-10V control frequency to 1000:1



RF SIGNAL GEN./COUNTER SG-4162 AD \$229.95
Generates RF signal same as SG-4160B
8 digit frequency counter 1Hz - 150 MHz for internal and external source Sensitivity <50mV

AUDIO GEN./COUNTER AG-2603AD \$229.95
Generates audio signal same as AG-2601A
8 digit frequency counter 1Hz-150MHz for internal and external sources Sensitivity <50mV

FUNCTION GEN/COUNTER FG-2102AD \$229.95
Generates signal same as FG-2100A
Frequency counter 4 digits
Feature TTL and CMOS output
SWEEP FUNCTION GEN./COUNTER \$329.95
0.5Hz to 5 MHz in 7 ranges
Sweep: Linear 10:1/Log 10:1 20ms to 2s
AM Modulation
Gated Burst, Voltage Control Generator
Generator Control Voltage & 8 digit counter
1Hz-10MHz for internal & external sources

ALFA ELECTRONICS
741 Alexander Rd., Princeton, NJ 08540

(800) 526-2532/(609) 520-2002 15 DAY MONEY BACK GUARANTEE. 1 YEAR WARRANTY
FAX:(609) 520-2007 CALL OR WRITE FOR FREE CATALOG AND BEST OFFER.
Visa, Master Card, American Express, COD, Purchase Order Welcome

CIRCLE 213 ON FREE INFORMATION CARD

www.americanradiohistory.com

100 MHz Cursor Readout Scope
4 ch, 8 traces OS-6101 **\$1,499.95**



- * 4 independent channels, 8 traces
- * Time/Voltage cursor measurement
- * ALT triggering function for 4 ch.
- * Sweeps to 2ns/div, Delayed Sweep
- * TV Sync., Ch. 1 output, Z-axis input
- * 2 probes(x1, x10)

100 MHz Scope, 4ch. 8 traces
Best value all purpose scope
OS-6100B **\$1,329.95**



- * 4 channels, 8 traces
- * High sensitivity 500µV/div
- * Sweeps to 2ns/div, Delayed sweep
- * 20 kV accelerating voltage
- * TV sync., Z-axis input
- * A and B gate output
- * Best price 100 MHz scope
- * 2 probes(x1, x10)

50 MHz Triggering Oscilloscope
OS-653 **\$699.95**



- * Dual Channel
- * Hold Off Function
- * Delayed Sweep
- * Built-in Delay Line
- * TV Sync
- * ALT Triggering
- * High sensitivity 1 mV/div
- * Trigger level lock function
- * Z-axis input, CH1 output
- * 2 probes(x1, x10)

20 MHz Oscilloscope
OS-622B **\$344.95**



- * Dual trace, X-Y operation
 - * TV Sync., Z-axis input, CH1 output
 - * High sensitivity 1 mV/div
 - * Trigger level lock
 - * 2 probes (x1, x10)
- OS-623B - 20 MHz w/Delayed Sweep..... \$ 449.95
OS-935 - 5 MHz One channel..... \$ 209.95

DC Linear Power Supplies
Single Output



- * Constant voltage and constant current mode
 - * Voltage regulation ≤0.01%
 - * Current regulation ≤0.2%
 - * Low ripple and noise
 - * Overload and reverse polarity protection
 - * Features 2 analog or 1 digital meter(PS series)
2 analog or 2 digital meters(PR series)
- | | |
|---------------------------------|----------|
| PS-1830 : (0-18V, 0-3A)..... | \$209.95 |
| PS-1830D : Digital Display..... | \$219.95 |
| PS-1850 : (0-18V, 0-5A)..... | \$219.95 |
| PS-1850D : Digital Display..... | \$244.95 |
| PS-3030 : (0-30V, 0-3A)..... | \$224.95 |
| PS-3030D : Digital display..... | \$254.95 |
| PS-6010 : (0-60V, 0-1A)..... | \$209.95 |
| PR-1810H : (0-18V, 0-10A)..... | \$349.95 |
| PR-3060 : (0-30V, 0-6A)..... | \$314.95 |
| PR-6030 : (0-60V, 0-3A)..... | \$314.95 |
| PR-6030D : Digital Display..... | \$399.95 |

Triple Output DC Power Supplies



- * Two variable 0-30VDC, 0-3A outputs
 - * One fixed 5VDC, 3A output
 - * Auto tracking
 - * Auto serial and parallel operation
 - * Constant voltage and constant current mode
 - * Continuous/dynamic load can be selected
 - * Features 4 analog or 2 digital displays
- | | |
|---------------------------------|----------|
| PC-3030 : (0-30V, 0-3Ax2)..... | \$499.95 |
| PC-3030D : Digital display..... | \$549.95 |

Programmable DC Power Supplies




- * High stability, low drift, 4 digit display
 - * Front/rear output-sense switch selectable
 - * Auto step running w/timer settings
 - * 100 point programmability (PPS series)
 - * 50 point programmability (PPT series)
 - * Auto serial and parallel operation (PPT series)
 - * Auto tracking (PPT series), IEEE-488.2 and SCPI compatible command set (optional)
- | | |
|------------------------------------------------|-----------|
| PPS-1860G : (0-18V, 0-6A)..... | \$1099.95 |
| PPS-3635G : (0-36V, 0-3.5A)..... | \$1099.95 |
| PPS-6020G : (0-60V, 0-2A)..... | \$1099.95 |
| PPT-1830G : (0-18V, 0-3Ax2, 0-6V, 0-5A)..... | \$1399.95 |
| PPT-3615G : (0-36V, 0-1.5Ax2, 0-6V, 0-3A)..... | \$1399.95 |

Digital Display Function Generator
FG-8016G **\$239.95**



- * Frequency Range: 0.02Hz to 2MHz
 - * Three Instruments in one: Function generator, Pulse generator & Frequency counter.
 - * Sine, Triangle, Square, TTL Pulse and CMOS output
 - * Built-in 6 digit counter with INT/EXT function
 - * 1000:1 tuning range
 - * Variable DC offset control
- FG-8015 Function Generator
- * 0.02Hz-2MHz (No Counter)..... \$189.95
 - FC-8131 Intelligent Counter 1.3GHz..... \$469.95
 - FC-8270 Intelligent Counter 2.7GHz..... \$629.95
 - UC-2010G Universal Counter..... \$294.95

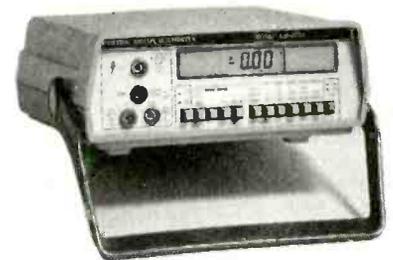Digital Multimeter & C Meter
DM-8034(3½ digits) **\$179.95**



- * 8 Function, AC/DC voltage, AC/DC current, resistance
 - * Built-in C meter, diode test and audible continuity check
 - * High voltage 1000V and 20A range
 - * 0.5% basic accuracy
- DM-8040 (3½ Digits, True RMS)
- * Measures ACV to 50 kHz..... \$339.95
- DM-8055 (5½ Digits)
- * 0.006% basic accuracy
 - * 1µV, 1mΩ, 1nA resolution
 - * dBm measurement
 - * Auto range, relative mode, Max/Min
- DM-8055G(5½ Digits, GPIB)..... \$889.95

Model DM-392
(3½ digits) **\$109.95**



- * Auto/Manual ranging(38 ranges)
- * 42 Segment analog bar graph
- * Data Hold/Min-Max memory /Relative mode
- * Auto power off
- * Overload protection
- * Audible continuity check /diode test
- * Capacitance: 1pF-40µF
- * Frequency: 0.1Hz-1MHz
- * 20 Amp range
- * Double high energy fused (1A, 20A)
- * 0.3% DCV accuracy

- | | |
|-------------------------------------------------|----------|
| DM-351 3½ Digits w/Continuity, Auto Off..... | \$54.95 |
| DM-352 3½ Digits, Cap. Freq. hFE, 20 Amp..... | \$79.95 |
| DM-353 3½ Digits, Cap. Freq. Temp. hFE..... | \$84.95 |
| DM-391 3½ Digits, Auto, Cap. Freq. Min/Max..... | \$99.95 |
| DM-392 3½ Digits, Hold, Min/Max 20Amp..... | \$109.95 |
| DM-393 3½ Digits, Peak, Logic, hFE, Freq..... | \$119.95 |

Roger's Systems Specialist

21021-504 Soledad Canyon Road
Santa Clarita, California 91351

"We Have Great Connections"

Computer • Communications
Network • Audio • Video



Call to Order
800-366-0579

Fax to Order
805-288-2293

Free Catalog with order
Most orders shipped same day

Cables

SCSI \$4/up
SCSI I & III \$14/up
MIDI/Sound Blaster \$15

Accessories

SimmVerters \$22
Sound Card Microphone \$3
Dual RJ11 Wall Plate \$5.50
12vdc Power Fans \$5
Auto Fax/Modem Switch..... \$89
EtherNet Card \$46
Monitor Arms \$39
Keyboard Drawers \$14/up


Cables ★ Connectors ★ Accessories

SCSI II Cable

2' SCSI II HD50 male to SCSI I male

#CC-679-2

\$12⁰⁰

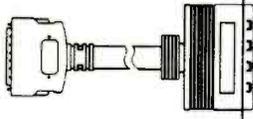

Stereo Headphones

- Exceptional Sound
- 1/4" Stereo Adapter
- 3.5mm Stereo Plug
- Major Brand Name
- Blister Pack

#TM-170-SP **\$7⁰⁰**



Mini D-SUB Gender Changers


All D-Subminiature
genders available

Only 1/2" deep


Just ask for size and gender

most are

\$2⁰⁰ each or less !

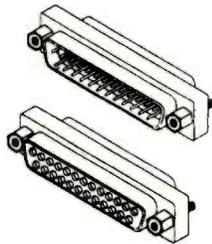

Printer Sharing Device

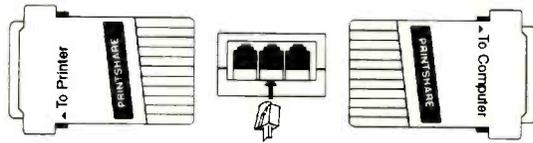

\$34⁹⁵
each


Up to 40 computers to one printer • up to 1500'
Uses 4 conductor phone cable

#CC-222-P for printer #CC-222-C for computer

\$10.00 minimum order • \$4.50 for shipping for pre-paid orders • California add 8.25% tax • No out of state checks

CIRCLE 302 ON FREE INFORMATION CARD

Flat Panels Served Here

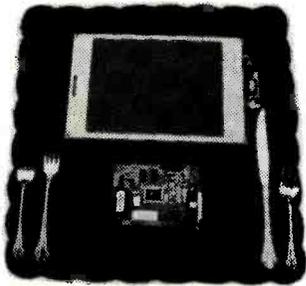

House Specialty - Monochrome LCD Kit \$249

Lo Earth LCD Restaurants Menu

Appetizers (Controllers for PC ISA Bus)

Earth LCD/M Monochrome LCD Controller \$149

EarthVision/ISA Color LCD Controller \$299

Entrées (Include LCD, ISA Controller,
Cable & Backlight Inverter)

Monochrome 9.4" \$249

Color Single Scan 8.2" \$450

Color Dual Scan 9.4" \$749

Color 9.4 TFT \$995

À la Carte (LCD Only)

Mono 9.4" LCD \$95

Color 8.2" Single Scan \$125

Color 9.4 Dual Scan \$399



"The Flat Panel Solutions Company"

P.O. Box 7089 - Laguna Niguel - California - 92607

Ph: (714) 448-9368 - Fax: (714) 448-9316

Email: lcd_king@ix.netcom.com

EPROM+ PROGRAMMING SYSTEM USES PARALLEL PORT

SUPPORTS OVER
600 CHIPS

EPROMS (24, 28, 32 & 40* PIN PLUS 27CXXX)
1702, 2708, 16, 32, 32A, 64, 64A, 128, 128A, 256, 512
513, 011, 010, 101, 301, 1000, 1001, 1024, 210, 020
2000, 2001, 220, 240, 2048, 4001, 4002, 040, 080, 8001
2516, 32, 64, 68764, TMS2716

FLASH EPROMS
28F256, 512, 010, 020 PLUS 29CXXX, 29FXXX

EPROMS & NVRAMS (P1 US CXXX)
2804, 16, 16A, 17, 2864, 64A, 65, 28256, 28C010
X2210, X2212, DS1220, 1225, 1230

SERIAL EPROMS* (8 PIN PLUS CXX)
2401, 02, 04, 08, 16, 32, 65, 2444, 59C11, 8572, 82, 92
9306, 46, 56, 66, 16811, 911, 80011A, ER1400/58657

BIPOLAR PROMS* (16 THROUGH 24 PIN)
74SXXX AND 82SXXX FAMILY

MICROCONTROLLERS* (UV, EE AND FLASH)
8741, 42, 48, 49, 8751, 87C51, 8752, C52, 87C5XXX
87C75X, 89C51, 52, 68705, 68HC705, 68HC711E9
PIC16C5X, PIC16C6X, PIC16C7X, PIC16C8X

*ADAPTER REQUIRED - ASSEMBLED ADAPTERS AVAILABLE / DETAILED DIAGRAMS INCLUDED

- SOFTWARE - READ, VERIFY, PROGRAM, COPY, DISK FILE LOAD & SAVE, CHECKSUM, PLUS A FULL SCREEN BUFFER EDITOR WITH 20 COMMANDS
- READS INTEL HEX, MOTOROLA S-RECORD AND BINARY FILES
- FAST! - MANY DEVICES PROGRAM IN UNDER 10 SECONDS
- RUGGED (9" X 6" X 3"), PORTABLE ENCLOSURE WITH CARRY HANDLE DESIGNED FOR BENCH AND FIELD SERVICE.
- ACCESSORY CONNECTOR FOR FUTURE EXPANSION
- LED INDICATORS SHOW POWER, PROGRAMMING & SYSTEM STATUS
- MADE IN THE USA - 30 DAY MONEY BACK GUARANTEE - 1 YR WARRANTY
- SYSTEM INCLUDES: PROGRAMMING UNIT, POWER PACK, CABLE PRINTED MANUAL AND SOFTWARE

ANDROMEDA RESEARCH
P.O. BOX 222
MILFORD, OHIO 45150
(513) 831-9708
FAX (513) 831-7562

\$289



ADD \$5.00 SHIPPING - \$5.00 C.O.D.


ALL ELECTRONICS CORP.

QUALITY PARTS • DISCOUNT PRICES • FAST SERVICE

EXPERIMENTERS DELIGHT 20 MB TAPE BACK-UP SYSTEM

Interdyne Model # 6025
Designed to back-up an
IBM PC/XT/AT, DOS
2.0 or later.
These units

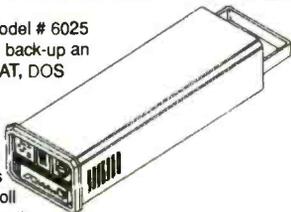were designed to do back-ups on a small roll of 1/4" magnetic tape. The units are 14.6" x 4.75" x 2.9" and weigh 10 lbs. The heavy-gauge metal chassis box contains a tape drive, power supply with fan and other components. Also includes IEC power cord, data cable and 2 rolls of back-up tape. Although these are new units, we do not wish to represent these as useable units.




CAT# TBS-2
\$12.00 each

We are selling them "AS-IS" for parts and experimentation.

PORTABLE SCSI CASE

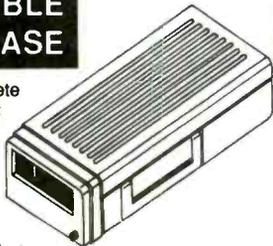Nearly complete case for SCSI device. Includes 40 watt power supply (5 Vdc @ 3 amps, 12 Vdc



@ 2 amps) with cooling fan, power switch, fuse holder, LED socket, power input receptacle, two standard 50 pin SCSI interface jacks, molex-type power connectors, interior cable with 50 pin socket connector and interior mounting rails. Front face plate is an aftermarket piece that doesn't quite go with the box but serves the purpose pretty well. Absent from the case is the switch in back which specifies the device's position in the chain. This can be easily bypassed with a few 0.1" shorting jumpers (our CAT# SJ-1). Also not included is a standard IEC power cord (our CAT# LCAC-60). Off-white case is 14.25" X 7.38" X 3.26" and has a folding handle for easy carrying.

\$19.95 each

CAT# SCSI-1

2 for \$36.00

FORCE SENSING RESISTANCE PAD



Interlink 7.5" x 11.5" x 0.03" thick plastic pad with two separate force sensing resistor circuits embedded in the pad. We have no factory

specs or information on the intended application for the product. It was probably designed for some sort of touch sensitive apparatus. The resistance circuits read between 1.5 Meg and 0.5 Meg when nothing is touching the pad. The resistance decreases to as low as 1.5K ohms when pressure is applied to the pad and appears to be dependent upon force and the amount of surface area acted upon. An interesting device for experimentation.

\$4.50 each

CAT# FSR-1

MERCURY TILT SWITCH



SPST mercury tilt switch. Glass bulb is 0.25" dia. X 0.67" long.


Circuit is closed in vertical position. Rated 750 ma. **\$1.00** each

CAT# MS-15

720K 3.5" INTERNAL FLOPPY DRIVE

Sony # MP-F11W-2Z

Brand new 720 KB floppy drives. Built for an OEM product, these are, in every way, compatible with PC/XT/AT computers except that the faceplate is slightly larger than those on exact replacements. The faceplate size on these is 4.04" X 1.23". (Normal size is 4" X 1"). The faceplate is removable and can be trimmed if desired. In some cases it may work without trimming. Also, we have found that, when used in 5.25" bays with the adapter kit below, the adapter can easily be modified to accommodate the unit. Because of this slight inconvenience, we are selling these drives at an incredibly low price.

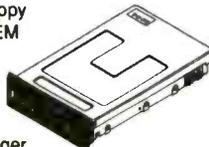

\$14.00 each

CAT# MPF-11SF

10 for \$120.00

INSTALLATION KIT for MPF-11SF

allows for installation into 5.25" drive bays. Simply cut and remove three plastic gussets to install. CAT# FDD-3.5 \$3.50 each


INTERNET USERS!

Visit Our Web Site..

<http://www.allcorp.com/allcorp/>

12 Vdc GEAR MOTOR

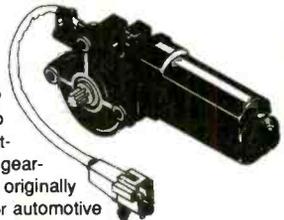Denso Brand 40 RPM @ 12.6 Vdc @ 600 ma. (no load). Right-angle drive gear-head motor originally designed for automotive applications where lots of torque is required. 6.68" long X 3.5" X 1.62" thick. Three mounting holes on 1.9" and 2.6" centers.



\$17.50 each
CAT# DCM-64

LARGE QUANTITY AVAILABLE!

9 FOOT DUAL AUDIO CABLE



9' shielded dual audio cable with color coded (red and yellow) RCA style pin plugs either end. Black cable. **\$1.00** each


CAT# DCB-108

10 for \$8.50 • 100 for \$75.00
1000 for \$500.00

NOTEBOOK COMPUTER CARRYING CASE

Padded carrying case, suitable for most notebook computers or other similar equipment.

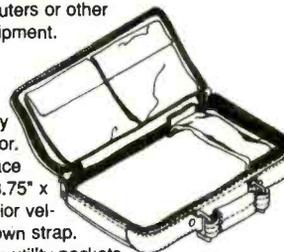Black leatherette exterior. Black heavy nylon interior. Interior space is 14.5" x 8.75" x 2.75". Interior velcro hold-down strap. Two interior utility pockets with velcro flaps. A fraction of the price of most similar cases. **\$9.75** each
CAT # CSE-4



MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write or Fax YOUR LIST.


CALL, WRITE
or FAX For A
Free 64 Page
CATALOG.

Outside the U.S.A.
send \$2.00 postage.

ORDER TOLL FREE **1-800-826-5432**

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

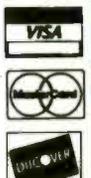E-MAIL allcorp@allcorp.com
FAX (818) 781-2653
INFO (818) 904-0524



NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.


CIRCLE 214 ON FREE INFORMATION CARD

www.americanradiohistory.com

57,953 ELECTRONIC COMPONENTS

Whether you order 1 part or
all 57,953...MOUSER stocks
and...ships same day!!

CALL...(800) 992-9943

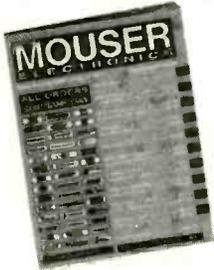

for your
FREE
CATALOG

958 North Main St.
Mansfield, TX 76063


MOUSER
ELECTRONICS
Sales & Stocking Locations Nationwide

VIDEO-AUDIO Modulator

switchable FM/AM Audio

Application for: all TV-STANDARDS (NTSC-SECAM-PAL)

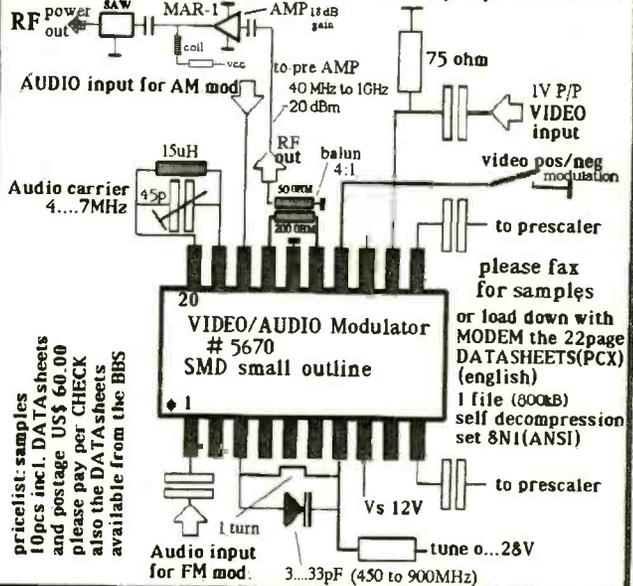CATV-Modulator, Computer, TV-Transmitter &
Video-Generator, Video security systems etc.



pricelist: samples
10pcs incl. DATASheets
and postage US\$ 60.00
please pay per CHECK
also the DATASheets
available from the BBS

please fax
for samples
or load down with
MODEM the 22page
DATASHEETS(PCX)
(english)
1 file (800KB)
self decompression
set 8N1(ANSI)

PICOTRONIC communication
Zollamtstr.48
67663 Kaiserslautern
GERMANY

FAX ++ 49 631 29579
BBS ++ 49 631 21048
Tel ++ 49 631 29187

VOICE CHANGERS! ELECTRONIC KITS AND MORE!

ELECTRONIC KITS!

WE ACCEPT VISA, MC, MO, COD
SHIPPING & HANDLING EXTRA



BUY WITH CONFIDENCE FROM XANDI

- 30-DAY REFUND POLICY
- TECH SUPPORT NUMBER (602-894-0992)


- Powerful 2 stage audio amplifier.
- Tunes 88-108 MHz.
- Up to 1 mile range.
- Requires 9V battery. (Not Incl.)
- Sensitive, picks up sounds at the level of a whisper.



SUPER-MINIATURE FM TRANSMITTER
Super small FM transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip (SMT) parts are pre-assembled to the circuit board.

XST500 E-Z Kit \$44.95

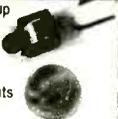- Sensitive audio amplifier, picks up sounds at the level of a whisper.
- Tunes 88-108 MHz.
- Up to 1/2 mile range.
- Miniature photo battery mounts right on circuit board. (Included)



MICRO-MINIATURE FM TRANSMITTER
Including the battery, this is the Worlds smallest FM transmitter. Use with any FM broadcast receiver. Easy to assemble, uses pre-assembled circuit board.

XWB1000 E-Z KIT \$46.95

- Up to 1/2 mile range.
- Miniature photo battery mounts right on circuit board.
- Transmits at 143 MHz.
- Amazing audio sensitivity, picks up sounds at the level of a whisper.



CRYSTAL CONTROLLED FM TRANSMITTER
Including the battery, this is the Worlds smallest crystal controlled FM transmitter. Transmits to any scanner type receiver. Easy to assemble, uses pre-assembled circuit board.

XTL1000 E-Z KIT \$69.95

- Smallest Phone transmitter anywhere!
- Tunes 88-108 MHz.
- Up to 1/4 mile range.
- Attach to phone line anywhere in house.
- No batterie required, powered by phone line.



SUPER-MINIATURE PHONE TRANSMITTER
Worlds smallest FM phone transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip components are pre-assembled to the circuit board.

XSP250 E-Z Kit \$28.95

- Dial your phone from anywhere and listen to the sounds inside your home.
- Two digit Touch Tone code for secure operation.



TELEPHONE SNOOP
The latest in home or office security. Call home from anywhere, enter a two digit security code, and hear the sounds in your home. Automatically turns on without ringing the phone, verifies code, then activates for one and a half minutes.

XPS-CASE KIT \$13.95

XPS1000 C KIT \$55.95

- Transmits a continuous beeping tone.
- Adjustable from 88 to 108 MHz.
- Up to 1 mile range.
- Works with any FM broadcast receiver.



TRACKING TRANSMITTER
Only 0.7 by 2.4 inches, the XTR100 operates at voltages of 3 to 18 Volts and is ideal for use in locating lost model rockets, bicycles, automobiles, games of hide and seek, and contests.

XTR100 C Kit \$29.95

- Covers 1 to 2,000 MHz.
- Compact hand held unit.
- Uses sensitive microwave transistor amplifier.
- Includes miniature loud speaker for audio indication of detected signals.



SUPER SENSITIVE BUG DETECTOR
When the XBD200 intercepts a signal in the 1 to 2,000 MHz range, it emits a growl that increases to a high pitched squeal as the signal strength increases.

XBD200 C Kit \$39.95

- Use with any FM broadcast receiver.
- Hear every sound in an entire house!
- Up to 1 mile range.
- Powerful 2 stage audio amplifier.



MINIATURE FM TRANSMITTER
The XFM100 has a super sensitive microphone and is capable of picking up sounds at the level of a whisper and transmitting them to any FM broadcast receiver.

XFM100 C Kit \$21.95

- Digital voice changing: male to female, female to male, adult to child, child to adult.
- Anonymity on any call.
- Button for normal operation.
- 16 levels of voice masking.



VOICE CHANGING TELEPHONE
STOP THOSE ANNOYING TELEPHONE CALLS! Sound older and tougher when you want to. Not a kit. Fully assembled. Single phone operation only.

TRANSITION 2000 \$89.95

- Digital voice changing: male to female, female to male, adult to child, child to adult.
- Use with any modular phone.
- 16 levels of voice masking.
- Connects between handset and phone.



VOICE CHANGING ACCESSORY
STOP THOSE ANNOYING TELEPHONE CALLS! Sound older and tougher when you want to. Not a kit. Fully assembled. Use with single or multi-line phones.

TRANSITION 2001 \$59.95

- Uninterrupted coverage of 800 to 950 MHz.
- Works with any scanner that can receive 400 to 550 MHz.




800-950 MHz SCANNER CONVERTER KIT
If your scanner can receive 400-550 MHz, just add the XLC900 for uninterrupted 800-950 MHz coverage. It converts all 800-950 MHz signals down to 400-550 MHz so your scanner can receive them! Add our custom case kit for that "Professional" look.

XLC-CASE KIT \$13.95

XLC900 C KIT \$49.95

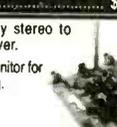- Transmit high quality stereo to any FM stereo receiver.
- Built-in output level monitor for quick and easy tuning.
- Ideal for use with personal CD player.



FM STEREO TRANSMITTER
Transmit full-bodied Hi Fi stereo to any FM stereo receiver. Separate left and right inputs and gain controls. Includes an output booster stage for greater range.

XFS-CASE KIT \$13.95

XFS108 C KIT \$39.95

XANDI Serving the public since 1981
ELECTRONICS, INC.
1270 E Broadway Rd. # 113, Tempe AZ 85282

TOLL FREE ORDER LINE: 1-800-336-7389
FAX LINE: 1-602-731-4748
ASK FOR FREE CATAG OF OUR PRODUCTS

SEND MAIL: XANDI ELECTRONICS
ORDERS TO: BOX 25647
TEMPE, AZ 85285-5647

CIRCLE 281 ON FREE INFORMATION CARD

www.americanradiohistory.com

Quality you can Afford



\$31⁹⁵

#72-2055 Manual Ranging DMM



\$999⁰⁰

#72-6025 100MHz Oscilloscope

TENMA™ TEST EQUIPMENT

Tenma, is rapidly emerging as the top choice of test equipment among today's service professionals. Regardless of your test and measurement needs, Tenma can meet your demands. TENMA's complete line of DMMs, oscilloscopes, frequency counters, power supplies, pattern generators and more, can be found at MCM Electronics. Call today for your free MCM catalog filled with over 21,000 items including service parts, tools, semiconductors and... TENMA test equipment.



**FREE
Catalog**

FREE CATALOG

1-800-543-4330

Hours: M-F 7 a.m.-9 p.m., Sat. 9 a.m.-6 p.m., EST.



MCM ELECTRONICS®
650 CONGRESS PARK DR.
CENTERVILLE, OH 45459-4072
A PREMIER Company

RCA/GE Premier Distributor

Authorized
Panasonic
Quasar/Technics
Original Parts
Distributor

Prices effective until February 29, 1996

CODE: ENS22

Get fast delivery from our distribution facilities near Dayton, OH and Reno, NV!

CIRCLE 197 ON FREE INFORMATION CARD

www.americanradiohistory.com

TECHMART

TEST EQUIPMENT SPECIALISTS

HAMEG Spectrum Analyzers



Model HM5006

0.1-500MHz, -100 to +13dBm. Scanwidth from 50kHz to 50MHz per division. Digital display of center and marker frequencies. Tracking generator from -50 to +1dBm. **\$1,495**

Model HM5005 identical to HM5006 except no tracking generator. **\$1,095**

Model HM5011, 0.15-1050MHz, -100 to +13 dBm. scanwidths from 100kHz to 100MHz / div. Digital display of center & marker frequencies. Tracking generator from -50 to +1dBm **\$2,265**

Model HM5010 identical to HM5011 except no tracking generator. **\$1,885**

Oscilloscopes

Model HM303-4 30 Mhz dual chan., 1mV/div., sync sep., calibrator, component tester. **\$568**

Model HM1004 100 MHz dual chan., 1mV/div., trig., after delay, auto-set, 0.5s to 5ns/div., comp. tester, Opt. RS232 & screen R/O avail. **\$1,215**

Model HM1007 Analog / digital, 100MHz analog, 40Ms/s digital, dual chan., 4x2048x8 trace mem, Opt. PC & printer interfaces avail. **\$1,885**

GOLDSTAR Oscilloscopes



Model 9020G

20MHz, dual trace, sync. split, 1mV/div., with built in 1MHz function generator. **\$485**

Model 9020A, dual trace, sync. split, 1mV/div., Like 9020G but no function generator. **\$379**

FLUKE Multimeters



Model 10	\$63	Model 73	98
Model 12	85	Model 77	159
Model 23	159	Model 79	176
Model 29	175	Model 83	239
Model 70	79	Model 87	299

Other FLUKE Test Instruments

Model 30 Clamp-on ACV, A, ohms	998
Model 33 Clamp-on true RMS A pk., freq.	242
Model 40 AC power, harmonic analyzer	1,080
Model 61 Dig. thermocouple thermometer	134
Model 610 LAN CableMapper	356

Call for pricing on other models and accessories

TEKTRONIX Oscilloscopes



Model THS720 Model TDS320

Model THS720 100MHz, 500 MS/s, 2ch, \$CALL
Model THS710 60MHz, 250 MS/s, 2 ch. CALL
Model TDS320 100MHz, 500 MS/s, 2 ch. CALL

SPECIALS SPECIALS! SPECIALS!

Super discounts on overstocks, slow movers and a couple of discontinued items. ALL NEW!


Mfr./Model	Description	List Sale
Fluke 11	Digital Multimeter	\$79.95 \$62
Fluke 25	Digital Multimeter	235.00 161
Fluke 51	Dig. Thermometer	149.00 111
Fluke 8010A	Digital Multimeter	399.00 263
Fluke 8062A	Digital Multimeter	389.00 289
Fluke 93	Scopemeter	1,395.00 995
Fluke 95	Scopemeter	1,895.00 1,249

TECHMART

800-554-8305

Technical 770-772-9811 Fax 770-772-9780
Shipping 4%, VISA/Mastercard

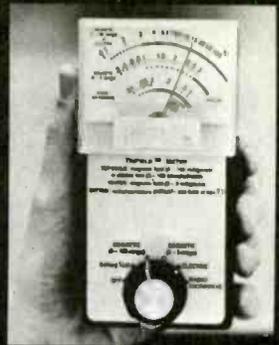NOW YOU CAN "SEE" INVISIBLE FIELDS AND AVOID THEM



Most homes and offices have hot spots with strong artificial electro-magnetic fields, where chronic exposure may cause mental or physical problems. Even the EPA names these fields as suspected carcinogens. You can reduce your risk by avoiding these high-field areas.

The **TriField™** meter detects *far more* of these fields than any other electromagnetic pollution meter. It's the only one that independently reads AC electric fields, AC magnetic fields, *and* radio/microwaves. It also reads field strengths in *all directions simultaneously*. Every other meter that sells for under \$500 reads only magnetic and only in one direction — they can entirely miss a magnetic field unless pointed correctly and are blind to radio/microwaves and electric fields, both of which cause biological effects.

The **TriField™** meter reads all three types of fields numerically and with a **SAFE/BORDERLINE/HIGH SCALE**, weighted proportional to effect on the body. Thresholds are based on epidemiological and laboratory studies. (While no *absolute* hazard thresholds have been established, reduction of *relative* exposure is prudent.)

The **TriField™** meter comes ready-to-use with battery, instructions, and one-year limited warranty. The cost is \$144.50 postpaid.

AlphaLab, Inc. / 1280 South Third West / Salt Lake City, UT 84101-3049
For literature and information, call (503) 543-6545

Tel: (954) 974-6864
Fax: (954) 974-6818

Gateway Products Corp.

Please mail orders to:
P. O. Box: 93-6397
Margate, FL 33093

Popular I.C.s

LM324	45¢
LM339	45¢
LM358	45¢
NE555	40¢
LM556	50¢
LM741	40¢

Deal U3: 12 pcs total, (2pcs of each)...**\$5.00**

Transistors

PN2222A	7¢
PN2907A	7¢
2N3904	7¢
2N3908	7¢
2N4401	7¢
2N4403	7¢

Deal N8: 60 pcs total, (10pcs of ea.)...**\$3.50**

Semiconductors

74LS174	40¢
74LS244	45¢
74LS245	45¢
74LS374	45¢
LM388N	45¢
MC1488	45¢
MC1489	45¢

V. Regulators

LM317T	70¢
7805	50¢
7808	50¢
7812	50¢
7815	50¢
7818	50¢
7824	50¢
7905	50¢
7908	50¢
7912	50¢
7915	50¢
78L05	40¢
78L05	40¢
78L12	40¢

DIODES

1N914	3¢
1N4148	3¢
1N4001 1A/50V	3¢
1N4004 1A/400V	4¢
1N4007 1A/1kV	5¢

Deal P7: 50 pcs total, (10pcs of ea.)...**\$2.00**

Power Diodes

1N5401 3A/100V	8¢
1N5404 3A/400V	9¢
1N5408 3A/1kV	10¢
6A10 6A/100V	24¢
6A100 6A/1kV	32¢

Deal H8: 25 pcs total, (5pcs of ea.)...**\$3.00**

1W Zener Diodes

1N4728A 3.3V	10¢
1N4733A 5.1V	10¢
1N4738A 9.1V	10¢
1N4742A 12V	10¢
1N4744A 15V	10¢
1N4748A 18V	10¢

Deal Z5: 30 pcs total, (5pcs of ea.)...**\$2.00**

Germanium Diodes

1N34A	14¢
1N60	14¢
1N270	28¢

Deal G5: 18 pcs total, (6pcs of ea.)...**\$2.50**

RADIAL LYTICS

1uF/50V	6¢
2.2uF/50V	6¢
3.3uF/50V	6¢
4.7uF/50V	6¢
10uF/50V	7¢
22uF/50V	8¢
33uF/50V	9¢
47uF/50V	10¢

Deal A2: 40 pcs total, (5pcs of each)...**\$3.00**

RADIAL LYTICS

10uF/25V	6¢
22uF/25V	6¢
33uF/25V	6¢
47uF/25V	7¢
100uF/25V	8¢
220uF/25V	14¢
330uF/25V	17¢

Deal A7: 40 pcs total, (5pcs of each)...**\$4.00**

1A SCHOTTKY

1N5817 1A/20V	20¢
1N5818 1A/30V	23¢
1N5819 1A/40V	24¢

Deal Y8: 9 pcs total, (3pcs of each)...**\$2.00**

3A SCHOTTKY

1N5820 3A/20V	32¢
1N5821 3A/30V	36¢
1N5822 3A/40V	40¢

Deal Y9: 9 pcs total, (3pcs of each)...**\$3.00**

Ceramic Disc (All caps rated 50V)

10pF	6¢
22pF	6¢
27pF	6¢
33pF	6¢
47pF	6¢
100pF	6¢
150pF	6¢
220pF	6¢

Deal R4: 40 pcs total, (5pcs of each)...**\$2.50**

Ceramic Disc (All caps rated 50V)

270pF	6¢
330pF	6¢
470pF	6¢
.001uF	6¢
.01uF	6¢
.022uF	6¢
.047uF	6¢
.1uF	6¢

Deal R7: 40 pcs total, (5pcs of each)...**\$2.50**

Mono Caps...8¢ea

.01uF/50V	.047uF/50V
.022uF/50V	.1uF/50V

Deal B5: 40 pcs total, (10pcs of ea.)...**\$2.50**

Tantalum Caps

1uF/35V	18¢
2.2uF/35V	22¢
10uF/35V	50¢

Deal T8: 15 pcs total, (5pcs of each)...**\$3.50**

Toggle Switches

Miniature size 1/4" Panel hole	
on-on	SPDT ... 55¢
on-off-on	SPDT ... 65¢
on-on	DPDT ... 75¢
on-off-on	DPDT ... 85¢

Deal S3: 8 pcs total, (2pcs of each)...**\$5.00**

DEAL W2...\$2.50

120 pcs total (20 pcs of each: 10K, 47K, 100K, 470K, 1M. All 1/4W 5%.

DEAL W5...\$2.50

100 pcs total (20 pcs of each: 10K, 47K, 100K, 470K, 1M. All 1/4W 5%.

400V BRIDGES

1Amp	4Amp
1.5Amp	
DF04M DIP	40¢
W04M Round	35¢
KBL04 In-line	90¢

Deal X8: 6pcs total, (2pcs of each)...**\$3.00**

SOLDER ROLL

SN63/37	
.031" dia	
1 Lb Roll	\$7.80

10.00 minimum order. We accept VISA, MC, MO, Check, No-CODS. Please add \$5.00 for shipping & handling (foreign addresses: \$8.50). Florida addresses add 6% sales tax. Hours: Mon-Fri: 9AM to 5PM, Sat: 9AM to 12PM (EST). All new premium parts. Send for free Catalog.

Who says we have the two best PC diagnostic tools on the market? Just about everyone...

fast & accurate diagnostics from



THE UNIVERSAL DIAGNOSTICS TOOLKIT

Featuring these 2 award-winning diagnostic tools:

Micro-Scope 6.0 & **Post-Probe**
UNIVERSAL DIAGNOSTIC SOFTWARE First Ever Universal P.O.S.T. Card for All PCs



gets a telephone walkthrough during which an experienced technician shows you the features of the product. My technician was quite knowledgeable and helpful."

—Drew Heywood/Inside NetWare 3.12, 4th Edition

"MICRO-SCOPE has helped me and my company save over 20 hard drives through its low level format procedures. I am very happy and impressed with this software. I think MICRO-SCOPE is worth it, no matter the cost."

—Andy Tran, Technician

"Not only did MICRO-SCOPE successfully low-level format an IDE drive that was purposely damaged, but of four drives reporting 'controller error' and thought to be defective, MICRO-SCOPE managed to reformat three of them and restore them to full capacity. The only reason it failed on the fourth is because the drive will not spin up at all. If you ever have trouble convincing anyone of what MICRO-SCOPE will do, y'all just have them give us a call." —Russell Holliman/Software City

Don't take our word for it—read what users and reviewers have to say about the two best PC diagnostic tools on the market:

"Micro 2000's MICRO-SCOPE and POST-PROBE are available separately and in a small kit (the Toolkit) containing diagnostic software and a diagnostic board. If your system fails to boot, this will tell you why, if anything will. If it boots but behaves oddly, this gives you a fighting chance of finding out if it's a hardware error. You name it, this tests it. If you maintain PCs, you'll love it. It gets a User's Choice Award.

—Jerry Pournelle/BYTE Magazine User's Choice Award/May 1994

"[POST-PROBE] is the only card that will function in every system on the market. The documentation is extensive, and not only covers the expected POST Codes for different BIOS versions, but also includes a detailed reference to the bus signals monitored by the card."

—Scott Mueller, from "Upgrading & Repairing PCs," Second Edition

"[The Universal Diagnostics Toolkit] provides the most sophisticated diagnosis and repair of any PC. Ideal for technicians and support staff—in fact anyone who maintains or repairs PCs must have it. This product is a technician's (or serious enthusiast's) dream tool kit."

—SA Computer Buyer/March 1995

"...If you're responsible for technical support of hardware, there's no other tool I'd recommend sooner than MICRO-SCOPE. The product's power, coupled with excellent, prompt and knowledgeable technical support, makes it a sure winner."

—David Welcher/Data Based Advisor Magazine/January 1994

"All in all, we found this hardware/software combination in Micro 2000's UNIVERSAL DIAGNOSTICS system to be superb. It is extremely useful and a definite *must have* for anyone responsible for maintaining computers." —PC Upgrade Magazine/Volume 3, No. 3

"My favorite diagnostic program is MICRO-SCOPE from Micro 2000, Inc. It will test everything you can think of, and a few things that would never occur to you. The list of features is quite long. Every purchaser

- ♦ **Low-Level Formats all PC Drives, even IDEs!**
- ♦ **Works with Windows, Windows NT and Windows '95, OS2, Unix, Xenix and Novell**
- ♦ **Fast & Accurate Diagnostics—Professional Level**
- ♦ **Great Tech Support**

Call Now for Special Pricing:
1-800-864-8008



1100 East Broadway, Suite 301, Glendale, California
 Phone 818/547-0125 • Fax 818/547-0397 • Web Page: <http://www.micro2000.com>
 International orders call: Micro 2000 Australia: 61-42-574144
 or Micro 2000 Europe (UK): +44-462-483-483




Govt. Serv. #: GS-00K-94AGS-5396

DATA ACQUISITION

and Control Hardware for PC's

ANA100 Analog I/O \$ 99

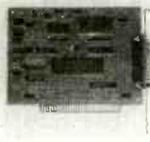


- * 8 Channel 8-Bit
- * 0 to 5 Volt Input
- * 14 TTL I/O lines
- * Analog Output
- * 400KHz Sampling

DIG100 Digital I/O \$ 39



- * 8255 PPI
- * 24 or 48 TTL I/O Lines option
- * Selectable Base Address

ANA150 Analog/Counter... \$ 89

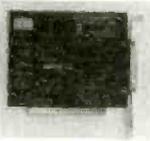

- * 8 Channel 8-Bit
- * 0 to 5 Volt Input
- * 3 16-Bit Counters
- * 400KHz Sampling

DIG200 Counter I/O \$ 79



- * 3 16-Bit Counters
- * 8 TTL Input lines
- * 8 TTL Output lines
- * Selectable Clock Frequency Input

ANA200 Analog I/O \$ 79



- * 1 Channel 12-Bit
- * 0 to 5 Volt Input optional bi-polar
- * 100KHz / 300KHz Sampling rate
- * 24 TTL I/O lines

ANA201 Analog \$ 129



- * 8 Channel 12-Bit
- * x1, x5, x10, x50 Programmable Channel gain
- * 100KHz/300KHz Sampling rate

Engineering Software - PC/MSDOS

Easy-PC Professional XM - Integrated Electronics CAE System, Combines Schematic Capture, Simulation, and PCB Design in one package.... \$ 349

PC-SCOPE - Digital Storage Oscilloscope, 1, 2, 4, or 8 Channel Capture and Display of Data. Works with ANA100, ANA150, and ANA201 Boards..... \$ 39

More Hardware and Software items Ask for our current catalog

We accept MasterCard/Visa Orders

BSOFT Software, Inc.

PHONE 614-491-0832 * FAX 614-497-9971
444 COLTON ROAD * COLUMBUS, OHIO * 43207

D.P & SONS

1-800-403-3741


UNIQUE ITEMS AT A VALUE BUY

SONICEL ULTRA SONIC CLEANER COMPACT UNIT FOR USE ON SM. PARTS - NICAD RECHARGEABLE	\$19.95
24 HOUR LCD 4 EVENT TIMER KIT MICRO-POWERED BY BATTERY-TIMES 4 DIFFERENT FUNCTIONS	\$44.95
AUDIO AMPLIFIER KIT 100W-INCLUDES POWER SUPPLY	\$29.95
MALIBU SINGLE EVENT 24 HR. TIMER 12V 25W WEATHER RESISTANT OUTDOOR TRANSFORMER	\$8.95
GEL CELL..... RECHARGEABLE 6V 4.5-7.5 AH RECONDITIONED WITH GUARANTEE	\$6.95
IDEAL FOR STORAGE GLASS LAB BOTTLES FROM 1000ML@\$2.95, 100ML@\$1.95, 50ML@\$0.95	\$.95
COMPUTER POWER CORDS STANDARD CORD - MINIMUM PURCHASE 10 CORDS	\$.99
6 OUTLET SURGE PROTECTOR HEAVY DUTY CIRCUIT BREAKER	\$4.45
2" SPEAKERS 8 OHM	10 FOR \$1.00
PRINTER CABLE MINIMUM PURCHASE 4 CABLES	\$.75
RIBBON CABLE FROM MUST BUY 10'+ 40 CONDUCTOR \$.13', 34 CONDUCTOR \$.10', 16 CONDUCTOR \$.05'	\$.05'
PLASTIC LENSES FOR PROJECTION TELEVISION 1 LENS=4"MAX., 1 LENS=6"MAX.	\$5.95

* Plus shipping and handling. We accept V, MC, DISC, MO and COD. Call the toll free number above or fax us at 713-789-9740. If you would like more information from us on our large variety of unique products at truly great prices please call or fax us for a free catalog.

You can Build Gadgets! Here are 3 reasons why!

Getting Started In Practical Electronics

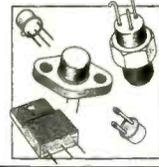

BP345—GETTING STARTED IN PRACTICAL ELECTRONICS \$5.95


If you are looking into launching an exciting hobby activity, this text provides minimum essentials for the builder and 30 easy-to-build fun projects every experimenter should toy with. Printed-circuit designs are included to give your project the professional touch.

BP349—PRACTICAL OPTO-ELECTRONIC PROJECTS...\$5.95

If you shun opto-electronic projects for lack of knowledge, this is the book for you. A bit of introductory theory comes first and then a number of practical projects which utilize a range of opto devices, from a filament bulb to modern infrared sensors and emitters.

Practical Opto-Electronic Projects

R.A. PENFOLD

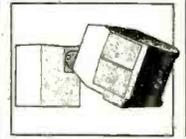

Practical Electronic Music Projects

R.A. PENFOLD



BP363—PRACTICAL ELECTRONIC MUSIC PROJECTS\$5.95

The text contains a goodly number of practical music projects most often requested by musicians. All the projects are relatively low-in-cost to build and all use standard, readily-available components. The project categories are guitar, general music and MIDI.

Mail to: **Electronic Technology Today, Inc.**
P.O. Box 240 • Massapequa Park, NY 11762-0240

Shipping Charges in USA & Canada

\$0.01 to \$5.00.....	\$2.00	\$30.01 to \$40.00.....	\$6.00
\$5.01 to \$10.00.....	\$3.00	\$40.01 to \$50.00.....	\$7.00
\$10.01 to \$20.00.....	\$4.00	\$50.01 and above.....	\$8.50
\$20.01 to \$30.00.....	\$5.00		

Sorry, no orders accepted outside of USA and Canada. All payments must be in U.S. funds only.

Number of books ordered.

Total price of books.....	\$
Shipping (see chart).....	\$
Subtotal.....	\$
Sales Tax (NYS only).....	\$
Total enclosed.....	\$

Name _____
Address _____
City _____ State _____ ZIP _____

Please allow 6-8 weeks for delivery.

ET02



INSTEK


ISO 9002 CERTIFIED MANUFACTURER
Test & Measuring Instruments

SINCE 1975



GFG-8020G

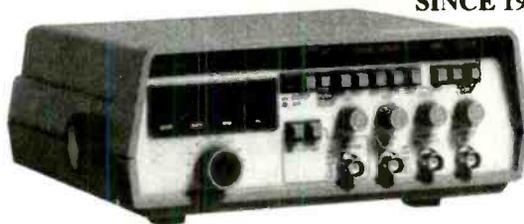- ★ Frequency Range: 0.02Hz to 2MHz
- ★ Sine, Triangle, Square, TTL pulse and CMOS output
- ★ Built-in 4 Digit Counter (INT only)
- ★ Large 0.5" LED DISPLAY
- ★ Variable offset control
- ★ Output Overload Protection



GFG-8016G

- ★ Frequency Range: 0.02Hz to 2MHz
- ★ Three Instruments in one, Function Generator, Pulse Generator & Frequency Counter
- ★ Sine, Triangle, Square, TTL pulse and CMOS output
- ★ Built-in 6 Digit Counter with INT/EXT Function
- ★ 10000:1 tuning range
- ★ Variable DC offset control

GW/INSTEK CELEBRATES ITS 20TH ANNIVERSARY WITH A
COMMEMORATIVE ISSUE OF THE BEST SELLING FUNCTION GENERATORS
IN THE WORLD (IN THE U.S. - TOTAL SALES EXCEEDS 20,000 UNITS):

GFG-8020G & GFG-8016G

FOR THIS SPECIAL OCCASION THE PRICE HAS BEEN REDUCED TO:

GFG-8020G : \$ 219.00

GFG-8016G : \$ 239.00


For a complete catalog of Instek equipment and the Distributor nearest you, please contact: **Instek Corporation**

1205 John Reed Court ■ City of Industry, CA 91745 ■ 818-336-6537 ■ FAX 818-369-1748

CIRCLE 199 ON FREE INFORMATION CARD

MC68HC705PJ1A MICROCONTROLLER PROGRAMMER - \$179.00 EDUCATIONAL STARTER KIT - \$335.00

MODEL PJ1A PROGRAMMER

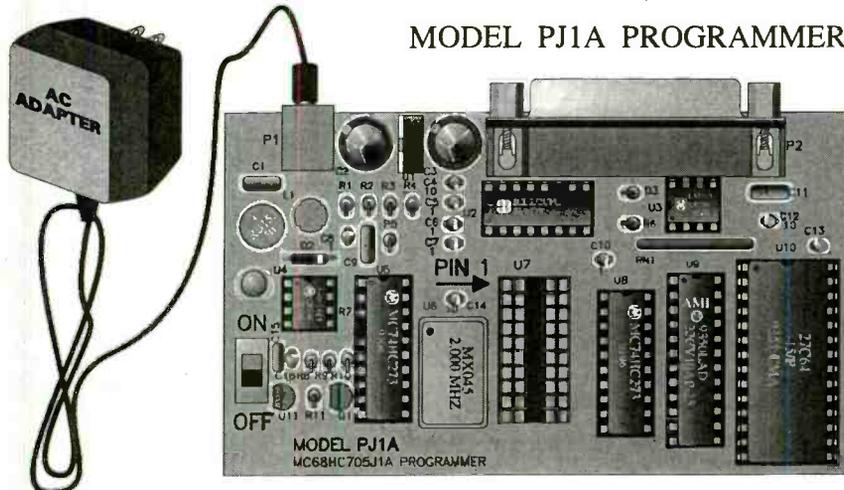

MODEL PJ1A PROGRAMMER
USER'S MANUAL AND
DISTRIBUTION DISKETTE

Motorola's MC68HC705J1A is a marvelously flexible and inexpensive 20 pin microcontroller. The PJ1A connects to a PC serial port and provides the fastest, easiest way to program these devices. The PJ1A programmer, power supply, host PC control software and manual is \$179.00. Learn how to use microcontrollers in embedded systems with the educational starter kit which includes the above plus a PC based cross assembler, Motorola technical specs and applications guide, sample programs with schematic diagrams and an erasable J1A chip for \$335.00.

TECI The Engineers Collaborative, Inc. TEL: (802) 525-3458 FAX: (802) 525-3451
Route 3, Box 8C, Barton, VT 05822

CIRCLE 274 ON FREE INFORMATION CARD

Robot Kits

✓ *Academic-Level Books*
 ✓ *Build it Yourself*
 ✓ *Action Packed*

EASY TO BUILD You do ALL electronic & mechanical assembly using 2-color Instruction Books with step-by-step, well-illustrated directions for assembly, experiments and testing. Each Robot Kit applies different electronic & robotic principles. Learn how Robots work and have fun at the same time!

606A "Scrambler" All Terrain Robot This 6-legged Robot walks over rough terrain. Uses high-tech infrared beam to sense and avoid avoid objects in its path. 32 page Book. **\$37.95**



603A "Copycat" Programmable Robot Program direction, light and sound using detachable keypad (included) or optional PC. Learn digital logic basics. 44 page Book. **\$57.35**

602A "Blinky" Pathfinder Robot Follows path made with a marker pen or tape. Red/green LEDs react to steering changes, adding fun and interest. 28 page Book. Infrared emitter/detectors. **\$36.95**



601A "Scooter" Sound Controlled Robot Backs up, changes direction, goes forward when it hears loud noise or hits an object. Florescent red. 24 page Book. Fast-paced excitement! **\$18.95**

DEPENDABLE PRODUCTS Since 1963, Graymark's ONLY business has been producing educational electronic kits. We do one thing and we do it right. That's why Graymark has the largest selection of electronic kits. And, our *"It works or we fix it"* policy guarantees success for YOU!

ORDER TODAY! Phone: VISA/MasterCard
 Mail: Check/Money Order, VISA/MasterCard
 Add: \$4.00 Shipping

**CALL FOR FREE
 40 PAGE CATALOG**


Graymark

P.O. Box 2015, Tustin, CA 92681

800-854-7393

CIRCLE 200 ON FREE INFORMATION CARD

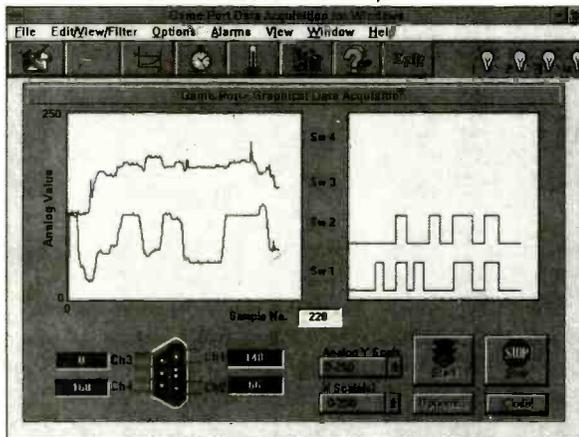Complete Low Cost Data Acquisition System for Windows - \$67



- 8 channel recording (4 analog & 4 switch monitoring channels).
- Record up to 5000 data points per channel per recording.
- Real-time graphical displays of data acquisition e.g. analog & temperature.
- No analog to digital hardware required, uses the PC game (joystick) port.
- Better than 8-bit resolution, selectable sample rates (from minute range to 20 hertz), option for user defined hi- and low- alarms.
- Software calibration features allow calibration of sensors and joystick port.
- Save data in ASCII & BMP formats, supports OLE with EXCEL.
- Built in spreadsheet, ASCII data editor & graph plotting windows.
- Includes extensive documentation, plus examples of PC data acquisition projects (circuits & component suppliers) e.g. temperature, light, voltage, position sensing & switch sensing. For most hardware interfaces little more is required than a resistor to link a voltage or sensor to the joystick port.

Purchase Price \$67 + Shipping and Handling \$5 (USA) or \$7.50 (Canada)
 Phone for further information. Ph. (805) 499 7990


Electronics Now, January 1996

88 Measurement Software, 2238 Adrian St., Newbury Park, CA 91320, USA

**Make your projects speak for themselves...
 Ours do!**

DIGITAL VOICE RECORDERS

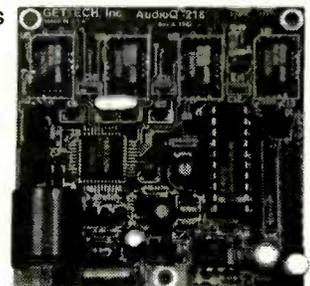- Record up to 218 seconds
- 1 to 8 messages
- High quality speech 12 bit
- Switch-closure actuation
- Sample rates up to 20Khz
- On-board backup
- Direct speaker output
- Wide operating range
- Small size 2.6" X 2.6"
- Made in U.S.A.



MODEL AudioQ[™]218

Call or write for more information
 OEM price and delivery available
 Custom designs and enclosures
 Single unit price \$149.00 plus s+h
 Quantity pricing as low as \$99.00

GETTECH, Inc.

402 Riley Road, New Windsor, NY 12553
 (914) 564-5347

Specifications and price subject to change.

SEC Sun Equipment Corporation **LODESTAR** Lodestar Electronics Corp. Since 1979
 One Year Warranty. 15 Day Money Back Guarantee. OEM welcome.
 School purchase order accepted. Bids accepted. VISA, DISCOVER
 SALES REP./DISTRIBUTORS/OEM WANTED. MASTER, & AMER.
 3121-A Glen Royal Rd., Raleigh, NC 27612
Test Equipment for Cost-Minded People 1-800-870-1955/(919)870-1955 24-hr Fax:(919)870-5720

DC POWER SUPPLY

PS-303 \$159.00
 0-30VDC, 0-3A; 0.02%+2mV line regulation; 0.02%+3mV load regulation; 1mVrms noise & ripple; Short circuit/overload protection; constant current/voltage(CC/CV)
PS-303D \$314.95 dual output, tracking
PS-305 \$219.95, 0-30VDC, 0-5A
PS-305I \$399.95, dual, tracking.
#110 \$289.95 0-60VDC, 0-3A
#112 \$399.95 0-60VDC, 0-5A
#108(#109) \$549.95(\$699.95)
 0-60VDC, 0-3A(5A), dual, independent tracking. Low ripple.
#102(#103) \$399.95(\$489.95) dual 0-30VDC/0-3A(5A), fixed 5VDC/3A, independent tracking operation, constant voltage and current. Slave/Master, Serial/Parallel connection.
PS-1610S(#107) \$289.00(\$399.95) 0-16VDC(0-30VDC), 0-10A.
PS-2243(2245) \$139.00(\$159.00) 0-12/0-24VDC, 3A(5A).
#200(#201) \$179.95(\$239.95) 0-30VDC(digital meter), 0-3A(5A).
#210(#211) \$199.95(\$259.95) two digital meters.
#202(#203) \$499.95(\$549.95) 3 outputs, digital display, dual 0-30VDC/0-3A(5A), a fixed 5VDC/3A, independent tracking operation, constant voltage and current.

AM/FM SWEEMAR SCOPE

SM-6225B/C \$1999.95
 Freq Range: (AM)490KHz, (FM) 10-11.4MHz. Accuracy: ± 0.1%
 Marker: (AM)45KHz, ±5KHz, ±10KHz; (FM)10.7MHz, ±7.5KHz, ±150KHz

STEREO SCOPE OS-7505B \$369.00 trigger, 0-10MHz

ALIGNMENT SCOPE OS-7001A \$369.00 0-200KHz

AM/FM STD SIGNAL GEN.

SG-4110A \$1799.00
 Freq: 100KHz-110MHz
 Display: 6-digit LED
 Accuracy:
 ±(5x10⁻⁵ ± 1 count)
 Resolution: 100Hz (100-34.99MHz), 1KHz (35MHz-110MHz).
 Output: -19dBu, -99dBu, 1dB steps Impedance: 50Ω VSWR 1.2

NTSC TV COLOR BAR PAT. GEN.

CPG-1366A \$199.95
 VHF NTSC,
 Freq.: 45.75, 175.25, 187.25 MHz.
 RF Output: 10mV
 Impedance: 75 Ohm;
 Video Output: BNC, 1Vp-p

SWR/RF POWER METER

J10 \$89.95
 Freq Range: 1R-150MHz.
 RF Power: 0-4W/20W/200W
 SWR Measure: 1.0 - ∞, 4W min.
 Accuracy: 5%-10%; SO-239 plugs.
 Insertion Loss: 0.3dB.
 Input/Output Imp.: 50Ω.
J20 \$89.95, 130-520MHz.
J30 \$119.95, 1.8-520MHz.
SWR-3P \$26.95 1.7-150MHz.
 RF Power: 0.5-10W, 0.5W-100W.
SWK-2P \$22.95, 1.7-30MHz, RF Power: 0.5-10W.
mW RF Power Meter J40 \$219.00, 1R-500MHz; 20mW ~ 2W.

RF SIGNAL GENERATOR

SG-4160B \$124.95
 100KHz-150MHz up to 450MHz on 3rd harmonics; 6 ranges; AM modulation. RF Output: 100mVrms to 3-5MHz. Modulation: Int. 1KHz AM, Ext. 50Hz-20KHz AM.
 Audio Output: 1KHz, 1Vrms.
SG-4162AD \$229.95, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see SG-4160B above.

AUDIO GENERATOR

AG-2601A \$124.95
 10Hz-1MHz, 5 ranges;
 Output Level: sine wave 0-8Vrms, square 10Vp-p
 Output Impedance: 600 Ohm.
 Distortion: <0.05% 500Hz-50KHz, <0.5% 50KHz-500KHz.
AG-2603AD \$229.95, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see AG-2601A above.

FUNCTION GENERATOR

FG-2100A \$169.95
 0.2Hz-2MHz in 7 ranges, Sine, Square, Triangle, Pulse & Ramp
 Output: 5mVp-p-20Vp-p, 1% distortion.
 PCF: 0-10V control freq. to 1000:1.
FG-2102AD \$229.95 generates signals same as FG-2100, 4-digit counter display, TTL & CMOS outputs, 30ppm ± 1 count accuracy
FG-2020B \$159.00 0.5Hz-500KHz; Sine, Square, Triangle.
(FG)2103 \$329.95, Digital sweep generator, 0.5Hz-5MHz in 7 ranges. Operating Mode: sweep, AM, gated burst, VCG.
 Freq. Counter: Int. 0.5Hz-5MHz; Ext. 5Hz-10MHz

FM STEREO MODULATOR

AG-2011A \$549.00
 RF SECTION:
 Carrier: 98MHz ± 2MHz;
 Output: 10mV, 1mV & 0.1mV
 COMPOSITE SIGNALS:
 Pilot: 19KHz ± 2Hz, 0.8Vrms
 INT. MODULATION: 400KHz, 1KHz ± 1%, 1Vrms, distortion < 5% L-R Separation: >50dB.
 EXT. MODULATION: Freq.: 50Hz-15KHz, L-R Separation: >45dB 100Hz-3KHz; >35dB 50Hz-15KHz.

AC MILLIVOLT METER

MV-3100A \$159.95 wide band 5Hz-1MHz, 3 scales, mV, dB & dBm; 300μV-100V in 12 ranges, 10μV resolution; -70-40dB in 12 ranges, 0dB=1Vrms, 0dBm=0.755V; ±3% accuracy; input impedance 10MΩ; Noise <2%.
MV-3201B \$309.95 dual channels, simultaneous measurement.

OSCILLOSCOPE OS-7305B \$249.00 DC-7MHz.

Vertical: 10mV/Div; Horizontal: 250mV/Div, 10Hz-100KHz in 4 ranges; 3" CRT; Internal and External Sync.; Input 1MΩ/35pF.
OS-7010A \$369.00 DC-10MHz, 5" CRT, 10mV/Cm-10V/Cm, 1MΩ.
OS-622B \$344.95 20MHz/dual trace
OS-65J \$699.95 50MHz, dual, delay sweep, ALT trigger, TV syn.
OS-6100B \$1329.95 100MHz, 4ch, 8 traces, delay sweep, best buy

GRID DIP METER

DM-4061 \$89.95 1.5-250MHz, 6 bands, 6 plug-in coils, 2 transistor, and 1 diode.
 Modulation: = 2KHz Sinewave. Crystal Oscillator: 1-15MHz. Wave absorption meter. Using 9VDC power supply.

AUTO DISTORTION METER

DM-3104A \$799.95
MEASUREMENT:
 Range: 0.01%-30%, 0.1/0.3/1/3/10/30% full scale.
 Freq.: 400Hz±10%, 1000Hz±10%(HPF).
 Input: 3mV-100V, ratio measuring 20dB.
 Auto. Switching Ranges: Fundamental Freq. = (fo)±10%.
 Fund. Rejection: >-80dB at (fo)±5%, >-70dB at (fo)±10%.
 Harmonic Accuracy: ±0.5dB, 1R(f)-20KHz.
DM-3204A \$1,599.00 dual channels

FREQUENCY COUNTER

FC-5250C \$119.95
 Freq. Range: 10Hz-220MHz (HF)10Hz-200MHz, (VHF)10MHz-200MHz
 Gate Time: 0.1 & 1sec.
 Max. Input: 10Vp-p
 Input Sensitivity: 35mV 10Hz-200MHz; Display: 7-digit LEDs
 Input Imped.: (HF) 1MΩlin, (VHF) 50Ωohm.
FC-5260A \$146.00
 10Hz-600MHz, 7-digit LEDs.
FC-5270 \$149.95
 10Hz-1.2GHz, 8-digit LEDs.
FC-5600B \$321.00
 10Hz-600MHz, 10-digit LEDs.
(FC)5700 \$329.95 10Hz-1.3GHz, 10-digit LEDs.

SIGNAL TRACER/INJECTOR

SE-6100 \$134.95
 TRACER: Gain Max. 60dB
 Attenuation: 0/20/40/60dB
 Input Imped.: 100KΩohm
 Output Imped.: 600Ωohm, Speaker: 8 Ohm.
 INJECTOR: Freq.: 1KHz
 Squarewavc. Output Level: Continuously variable 0 - 4.5Vp-p.

AUTO. CAPACITANCE METER

CM3300A \$139.00 10 ranges, 99.9pF - 99.9mF, fully automatic.
 Resolution: 0.1pF lowest, 0.1% full scale.
 Accuracy:
 0.5% of full scale ± 1 digit to 99.9μF,
 1% of full scale ± 1 digit to 99.9μF.
 Display: 3 digit LED.
 Unit indicator: pF, nF, μF, mF. Overrange indicator.

WOW-FLUTTER METER

WF-3103A \$699.95
 Freq. Range: 3KHz±10%
 JIS/CCIR, 3.15KHz±10% DIN.
 Range: 0.03, 1/1.3/3% full scale.
 Accuracy: ±5%.
WF-3105A \$799.95, digital;
 Function: LIN/WOW/Flutter/WT.D.
 Freq. Cntr: 10Hz-9.99MHz.
 Indication: CCIR/DIN/JIS.

MICROPROCESSOR/CONTROLLER TRAINING

Now, you can learn and apply Computer control on your PC with our low-cost trainers and lead yourself to the advanced 80386, 80486, etc. Learn ASSEMBLY, C, and BASIC languages programming and debugging, and Microprocessor based system hardware design and troubleshooting. Experiment guide and example programs are included in each trainer. Our trainers are widely adopted by technical colleges.
#088 Trainer \$699.00 8088-8088, teach yourself 8088 assembly language programming.
Features: Assembly language coding, assembler, disassembler, single step and multi-breakpoint program debugger, display and rewrite registers, download/upload programs from/to external systems, I/O drivers, 56-key large size keyboard, LCD display, RS-232, UART, printer interface, two expansion slots, ±5V, ±12V switching power supply, 20 I/O controls available, e.g. servo and stepping motor, dot matrix display, D/A, A/D, sensors.
EDS-8811 \$289.00 EPROM programmer. Burn your own EPROM in just a minute.
8085 \$979.00 learn yourself Intel 8051/8052 Embedded Microcontroller controls.
U-D8CR \$1599.00 Debugger/In-circuit Emulator for Microprocessors and programme.
8051/52 In-Circuit Emulator, APEX-1E assembly language programming and debugging.
CIC-100 \$549.00 I/O control applications, learn ASSEMBLY, C, and BASIC programming languages, 800-pin solderless breadboard for circuit design and test, I/O drivers for controlling relay, step motor, LED, speaker, sensor, etc. Application control modules available.

EDS-8802 \$109.00 Dynamic scanning control
EDS-8803 \$159.00 A/D, thermal sensor controls
EDS-8804 \$89.00 A/D and D/A converters.
EDS-8805 \$239.00 Servo and stepper motors
EDS-8806 \$159.00 Basic I/O experiments
EDS-8807N-16 \$619.00 16 Dot matrix LEDs
EDS-8807N-8 \$419.00 8 Dot matrix LEDs.
EDS-8808 \$269.00 Opto-couple controls.
EDS-8809-1 \$589.00 stepper motor control, digital clock, speaker control, dot matrix LED, matrix keyboard, sign lights, electric piano, stop watch, etc. 24 experiments.
 example programs included.
EDS-8811-DRAM \$589.00 Disk drive control.
EDS-8811-SRAM \$589.00 Disk drive control.

FREE AC/DC adapter with FC-5250C, FC-5260/5270, CPG-1366A, or SE-6100A purchase before 1/31/96, limited quantity.

NEW PRODUCTS

mW RF Power Meter J40 \$219.00
 1.8-500MHz; RF Power: 20mW/200mW/2W; Imp. 50Ω;
 Accuracy: ±10% full scale; N-type connector; SWR <1.15
Computer Monitor Tester MT801
\$175.00 Test MDA, CGA, EGA, VGA, SVGA, 8514A monitors; Video Patterns: color bars, cross hatch, dots, color raster and windows; Two video connectors: digital TTL 9-1) & analog 15-HD; Power: 120VAC.
MT810 \$149; Same as MT801, except Power: 9VDC.

Laser Video Player ONLY \$ 99.00!

BRAND NEW, still packed in original factory boxes with all cables, IR remote control, documentation and instructions! They were originally purchased by McDonnell Douglas corp. Unfortunately they will NOT play current laser disks of any type. We suspect that either this was an early format of laser video disk or they were custom designed for McDonnell Douglas Corp. However, they are an experimenter's goldmine of exotic and hard to find components such as X-Y scanners, Laser diode, beamsplitter, etc.



Laser Bar-Code Scanner Only \$ 55.00!



"Pulls" from Lucky's supermarket stores. Used, but in working condition. Each has a 1-2mW HeNe laser & PSU and many other electronic & optical components.

**CALL FOR OUR
FREE LASER
CATALOG TODAY.**

MWK INDUSTRIES
1269 W. Pomona, Corona, California 91720
(909) 278-0563 FAX (909) 278-4887

CONTROL RELAYS • LIGHTS • MOTORS MEASURE TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY INPUT SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

MODEL 30 \$79



- PLUGS INTO PC BUS
- 24 LINES DIGITAL I/O
- 3 CHANNEL-
- 8 BIT A/D/ IN
- 12 BIT COUNTER
- UP TO 14K SMP/SEC

MODEL 45 \$189



- RS-232 INTERFACE
- 8 DIGITAL I/O
- 8 ANALOG INPUTS
- 2 ANALOG OUTPUTS
- 2 COUNTERS-24 BIT

MODEL 100 \$279



- 12 BIT 100 KHZ A/D
- 4 ANALOG OUTPUTS
- 3 TIMER COUNTERS
- 24 DIGITAL I/O

MODEL 150-02 \$179



- RS-232 INTERFACE
- TRMS, 20 AMPS
- 12 BIT A/D
- OPTO-ISOLATED
- COMPLETE DMM

MODEL 40 \$99



- RS-232 INTERFACE
- 28 LINES DIGITAL I/O
- 8 ANALOG INPUTS
- PWM OUTPUT

MODEL 70 \$239



- RS-232 INTERFACE
- 16 BIT A/D
- 5.5 DIGIT
- UP TO 60 SMP/SEC

Prairie Digital, Inc.

PHONE 608-643-8599 • FAX 608-643-6754
846 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53578

CIRCLE 325 ON FREE INFORMATION CARD

What's the easiest way to get Radio Active?
Dial 1 800 445 7717

TRIDENT

Bearcat

TR2400 \$499
100KHz to 2.06 GHz



TR980 \$299
5MHz to 1GHz



BC220 \$229
Turbo Scan
with 800MHz



BC3000 \$369
25MHz to 1.3GHz



These are a few of our products and price values. For more information dial toll free or use our BBS, or get instant specs & info. from our fax back service.

Toll Free, 24 Hours! For orders or for tech support, dial our 800 number. For Fax Facts Instant catalog sheet service, dial 317 849 8683. Computer BBS

ACE
COMMUNICATIONS
10707 E. 106th St. Fishers, IN 46038

& Fax/Modem, 317-579-2045. Mastercard, Visa, Checks, Approved P.O.'s & COD (add \$5.50) & AMEX, Discover. Prices, specs and availability subject to change. Ground shipping and handling charge \$6.95

CIRCLE 212 ON FREE INFORMATION CARD

www.americanradiohistory.com

DALBANI

the ultimate saving source

For over then ten years, **DALBANI CORP.** was, and still the ultimate saving source . **DALBANI CORP.** is a national and International distributor of quality electronic parts and components servicing the wholesale, retail and manufacturing industry.

Since finding the parts you need should not be a major task, **DALBANI CORP.** maintains a huge stock of the most popular parts that are hard to find. Our service, low prices and quality reflects our commitments to our customers.

DALBANI CORP. keeps customers informed of the latest new items, that gets to our warehouse, thru publications. The multilingual sales dept. coupled with the state of the art computerized order processing, enable us to offer prompt and efficient service to benefit the customer.

We, offer many shipping options. Company checks, COD's, Cash and major credit cards are accepted. There is a \$20.00 minimum order.

We meet our customer needs



For a free 192 catalog please call
TOLL FREE 1-800-DALBANI



**Digital
Multimeter**



**Large Line Of
Semiconductors**



Oscilloscopes



VCR Heads Replacements



**Soldering
Equipments and Tools**



4225 NW 72nd. Miami, Florida 33166

Telephone : (305) 716-1016 or Fax : (305) 594-6588

Business Hours : monday thru Friday 9:00 am to 7:00 pm eastern time

CIRCLE 234 ON FREE INFORMATION CARD

www.americanradiohistory.com

Radiotelephone - Radiotelegraph

FCC Commercial License

Why Take Chances?

Discover how easy it is to pass the exams. Study with the most current materials available. Our Homestudy Guides, Audio, Video or PC "Q&A" disks make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine, Radar, Microwave, New Rules & Regs, Digital Circuitry & more. We feature the Popular "Complete Electronic Career Guide". 1000's of satisfied customers **Guarantee** to pass or money back. Newest Q&A pools.

Send for **FREE DETAILS** or call

1-800-800-7588


WPT Publications
4701 N.E. 47th St.
Vancouver, WA 98661

Name _____

Address _____

City _____ St. _____ Zip _____

1-800-800-7588

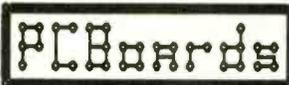

PCB Artwork Made Easy!

PRINTED CIRCUIT DESIGN SOFTWARE
for

Layout-Autorouting-Schematic

- Supports all Video Modes including Super VGA
- Copper Flooding for Building Ground Areas
- Gerber and Excellon Output
- Create Negative & Positive Printouts
- Autoroute Single & Double Sided Boards
- Mirror Image Output for Laser & DeskJet tm
- **NEW DOS Pricing (Ask for New Price List)**
- **NEW! - DOS Ver. - PCBoards 2.0/ PCRoute 5.1**
- **Parts Library-Silk Layer-Includes All Ouput Drivers**
- Great for All Circuit Design Projects!

Download Demos from BBS (205)933-2954

PCBoards Layout Only \$99

Windows tm Layout starts at \$149

Call or Write for Full Product Line, Prices & Demo Packages:

PCBoards
2110 14th Ave. South
Birmingham, AL 35205

(800)473-7227
Fax (205)933-2954
Phone (205)933-1122

❖ ATTENTION CABLE VIEWERS ❖

CABLE VIEWERS...get back to your BASIC Cable Needs

Call 800-577-8775

For information regarding all of your BASIC cable needs.



- 5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT**
- ❖ PRICE
 - ❖ EFFICIENT SALES AND SERVICE
 - ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
 - ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
 - ❖ **ANY SIZE ORDER FILLED WITH SAME DAY SHIPPING**

We handle **NEW** equipment **ONLY** - Don't trust last year's **OBSOLETE** and **UNSOLD** stock!
COMPETITIVE PRICING—DEALERS WELCOME

HOURS: Monday-Saturday 9-5 C.S.T.

It is not the intent of B.E.S.W. to defraud any pay television operator and we will not assist any company or individual in doing the same.
*Refer to sales personnel for specifications.

BASIC ELECTRICAL SUPPLY & WAREHOUSING CORPORATION

P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775

VISA

CABLE TV Universal Descrambler



NEW PRODUCT

MODEL 5000 Fully Assembled \$199.95

Our fully assembled product is tested and *Guaranteed* to work on your system. We will also include an AC adaptor and complete hookup instructions. This unique product will be available for a limited time only!

4000 And 5000 Features

- The latest in Video Amplification Technology.
- New clocking circuits to stabilize color and picture performance.
- The most advanced picture locking circuitry. *The Halcyon Group*
- Inverted Video Option is available. **1-800-664-6999**
- Connects easily to your VCR.
- NO converter box is necessary.

MODEL 4000 KIT \$79.95

The 4000 KIT comes with electronic components and Cad designed PC board. We provide schematic, parts list, wiring diagram, tutorial guide, and FREE in-house support.

Model 4000A Enc Pak \$44.95


The 4000A Enclosure Pak provides the hobbyist, a custom enclosure, AC adaptor and finish accessories to give your kit the professional look.

Anyone implying theft of cable service will be denied assistance.

PUT YOUR PC TO WORK!

THIS IS THE MACHINE YOU'VE BEEN WAITING FOR!

Imagine using your computer to turn 3D CAD drawings into actual working parts! Machine and drill printed circuits directly from blank material. Fabricate intricate mechanical components from raw plastic or aluminum. Route wood to make signs or "digitally" carve three dimensional art objects AND MORE! Sound interesting? You bet it is and with your creativity the sky's the limit! The NEURACTOR CNC-4+, 5, 6, & 7 Desktop Manufacturing Systems may be just the edge you need! Utilizing patent pending technology the NEURACTOR CNC kits provide you with machining resolution of .001". All mechanical components are pre-fabricated, pre-machined, plated and painted. The CNC-4+ machines an area approximately 18"x18"x4.6" and includes four 83 oz/in CY-MOTORS. The CNC-5, 6, & 7 (appx. 42"x42"x4.6", 66"x42"x4.6" and 66"x66"x4.6" respectively) include four 125 oz/in CY-MOTORS. Interface card, 5 amp power supply, 10 pitch steel lead screws, 4 proprietary Slide Block actuator mechanisms, 4 aluminum linear actuator channels, polished steel guide-rods, toolholder bracket, hardware, etc., are included with each unit. (You provide Dremel(tm) Tool or flex-shaft router and work surface.) It's a complete kit! All you do is put it together, calibrate A FREE, FULL-FEATURED 3D CAD/CAM SOFTWARE PACKAGE WITH EACH UNIT! CNC-4+ is \$695 + 29.95 S/H, CNC-5 is \$895 + 69.95 S/H, CNC-6 is \$995 + 79.95 S/H, CNC-7 is \$1195 + \$89.95 S/H. We also have MICRO-DRILLS, FLEX-SHAFTS, MILLS, ETCHERS, CHEMICALS, BLANK BOARDS, ETC. CNC units sold in USA and Canada only, no exports! At these prices, demand is high so please allow 4 weeks minimum for delivery. CALL NOW!

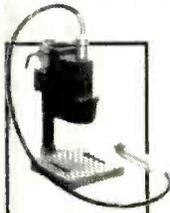


MICRO MACHINING

U.S. CYBERLAB, 14786 Slate Gap Rd., West Fork, AR 72774 (501) 839-8293

IMAGINE THE POWER!


WITH FREE 3D CAD SOFTWARE!

starting at \$695!

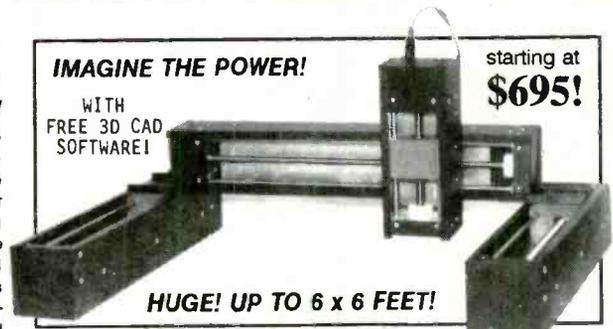

HUGE! UP TO 6 x 6 FEET!

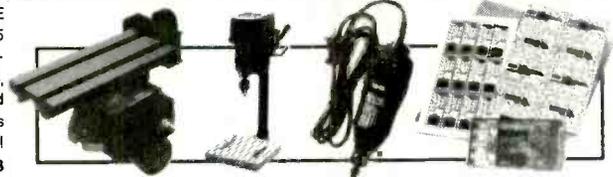It includes 4 proprietary Slide Block actuator mechanisms, 4 aluminum linear actuator channels, polished steel guide-rods, toolholder bracket, hardware, etc., are included with each unit. (You provide Dremel(tm) Tool or flex-shaft router and work surface.)



PHONE (603)434-2544
FAX (603)425-2945

TEST EQUIPMENT SALES

P.O. BOX 986
LONDONDERRY, NH 03053

HEWLETT PACKARD

HP 1630G LOGIC ANALYZER.....	\$1095
HP 1850A LOGIC ANALYZER.....	\$2250
HP 3330B SYNTH/SIG.GENERATOR.	\$650
HP 3336B SYNTH./LEVEL GEN.....	\$565
HP 3488A SWITCH CONTROL UNIT..	\$975
HP 44470A 10 CH. MULTIPLEXER...	\$350
HP 44472A VHF SWITCH.....	\$350
HP 44473A MATRIX SWITCH.....	\$350
HP 415E-001(new) SWR METER.....	\$275
HP 4954A PROTOCOL ANALYZER.....	\$2795
HP 5008A SIGNATURE ANALYZER.....	\$395
HP 5345A 500 MHz COUNTER.....	\$485
HP 5423A STRUCTURAL ANALYZER..	\$895
HP 8012B PULSE GENERATOR.....	\$695
HP 8180A DATA GENERATOR.....	\$2795
HP 8444A-059 TRACKING GEN.....	\$1295
HP 8553B 110 MHz SPEC A P/I.....	\$375
HP 8556A 300 KHz SPEC A P/I.....	\$295
HP 8620D SWEEPER MAINFRAME.....	\$375
HP 86242D 5.9-9 GHz RF PLUG-IN..	\$695
HP 86280A001 18 GHz PLUG-IN.....	\$895
HP 8754A NETWORK ANALYZER.....	\$2995

TEKTRONIX

TEK 2215 80 MHz SCOPE.....	\$499
TEK 2230 DIG. STORAGE SCOPE...	\$2495
TEK 2235 100 MHz SCOPE.....	\$1095
TEK 2445 150 MHz SCOPE.....	\$1795
TEK 2465 300 MHz SCOPE.....	\$2695
TEK 484/DM44 STORAGE SCOPE...	\$595
TEK 465 100 MHz SCOPE.....	\$449
TEK 465B 100 MHz SCOPE.....	\$525
TEK 475 200 MHz SCOPE.....	\$625
TEK 475A 250 MHz SCOPE.....	\$750
TEK 485 350 MHz SCOPE.....	\$825
TEK 7104 1 GHz MAINFRAME.....	\$3695
TEK 7903 100 MHz MAINFRAME....	\$350
TEK 7834 400 MHz STORAGE M.F..	\$495
TEK 7844 DUAL BEAM MF.....	\$495
TEK 7904 500 MHz MAINFRAME....	\$450
TEK 7A13 DIFF. COMPARATOR.....	\$325
TEK 7A18N DUAL TRACE AMP.....	\$79
TEK 7A22 DIFF. AMPLIFIER.....	\$325
TEK 7A24 400 MHz DUAL TRACE...	\$295
TEK 7A26 200 MHz DUAL TRACE...	\$150
TEK 7A29 1 GHz AMPLIFIER.....	\$600

TEKTRONIX

TEK 7A42 LOGIC TRIG. AMP.....	\$995
TEK 7B10 1 GHz TIMEBASE.....	\$395
TEK 7B15 1 GHz DELAYING T/B....	\$395
TEK 7B85 400 MHz DELTA T/B.....	\$195
TEK 7B92A 400 MHz DUAL T/B....	\$350
TEK 7CT1N CURVE TRACER P/I.....	\$395
TEK 7L5 SPECTRUM ANALYZER.....	\$1495
TEK 7L12 1.8 GHz SPEC. A P/I...	\$1795
TEK 7S12 TOR/SAMPLER.....	\$495
TEK 7S14 1 GHz SAMPLER.....	\$695
TEK FG502 11 MHz FUNC. GEN.....	\$275
TEK FG504 40 MHz FUNC. GEN.....	\$695
TEK P6048 DIFF. FET PROBE.....	\$500
TEK P6201 900 MHz FET PROBE...	\$375
TEK P6202A 500 MHz FET PROBE..	\$250
TEK P6452 DATA ACQ. PROBE....	\$50
TEK S6 SAMPLING HEAD.....	\$495
TEK S52 PULSE GEN. HEAD.....	\$495
TEK TG501 TIME MARK GEN.....	\$525
TEK TM503 3 SLOT MF.....	\$150
TEK TM504 4 SLOT MF.....	\$175
TEK TR503 TRACKING GEN.....	\$1250

MISCELLANEOUS

ANALOGIC DP100 MULTIMETER.....	\$295
BECKMAN L-10A MEGOHMMETER....	\$475
BMI 2400 POWER MONITOR.....	\$1795
DATA PREC. 5801 COUNTER.....	\$295
DATRON 1065 5.5 DIGIT DMM.....	\$695
ENI 325LA RF POWER AMP.....	\$1095
KEI 224 CURRENT SOURCE.....	\$1095
KH 6880 DISTORTION ANALYZER...	\$650
ROD-L M100AVS4 HIPOT TESTER...	\$795
WAV 178 PROG. SYNTHESIZER.....	\$1495

NEW EQUIPMENT

TEK TDS320 100 MHz DSO.....	\$3049
TEK TDS420A 200 MHz DSO.....	\$6295
TEK TDS460A 400 MHz DSO.....	\$7685
TEK TAS475 100 MHz SCOPE.....	\$2549
TEK TAS485 200 MHz SCOPE.....	\$3850
TEK THS720 HANDHELD DSO.....	\$2195
FLUKE 99 HANDHELD DSO.....	\$2195
FLUKE 8840A 5.5 DIGIT DMM.....	\$920
FLUKE 79 HANDHELD DMM.....	\$199
FLUKE 87 HANDHELD DMM.....	\$335

CALL FOR LATEST
PRICE LIST!

CUSTOMER SATISFACTION OUR #1 PRIORITY

WE BUY SURPLUS
EQUIPMENT!

EARN MORE MONEY!

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

Or, Call 1-800-932-4268 Ext. 210

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 210
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

MICRO TV CAMERA WITH TRANSMITTER

As small as a package of cigarettes! Complete TV camera with transmitter. Available on VHF channels 7-13. Operates on 9V battery or may be used with a wall adapter for permanent installation. Range up to 300 yards. Perfect for any surveillance application!

CAMERA WITH TRANSMITTER SEMI-KIT UP402 \$399.00

PLUS S&H

Please call for custom configurations.



VIDEO TRANSMITTER KITS

HIGHER POWER VARIABLE FREQUENCY MICRO TV TRANSMITTER

As used in our UP402. Available on VHF channels 7 to 13. Operates from a 9 Volt battery or may be used with an optional wall adapter. May be used with any composite video source. Range up to 300 yards.

PLUS S&H SEMI-KIT UP301 \$139.95

VARIABLE FREQUENCY MICRO TV TRANSMITTER KITS

Seen in the DEC-93 issue of ELECTRONICS NOW. Variable frequency oscillator transmits on either VHF channels 7-13 or UHF channels 14-29. Range up to 100 yards. May be used with any composite video source such as a camcorder. M200 PCBOARD \$14.95

PLUS S&H

M300 KIT \$49.95



XTAL CONTROLLED MICRO VIDEO TRANSMITTER

Circuit board area smaller than a credit card! A perfect companion to your Camcorder, but will also work with any video source. Xtal controlled. Available on UHF channels 14, 24 or Amateur TV frequency 439.25 MHZ. Audio and other frequencies available as a custom option. Uses 9 volt battery or wall adapter. Range up to 1 mile with suitable antenna.

SEMI-KIT UPX51 \$199.95

PLUS S&H with audio \$249.95

5% DISCOUNT FOR MONEY ORDERS

VISA

B.H.S. ELECTRONICS
ELECTRONIC KITS



41 EAGLERIDGE DR. TEL: 1-800-771-8656
BRAMPTON, ONT. CANADA
L6R 1G1 FAX: (705) 466-3268

CIRCLE 201 ON FREE INFORMATION CARD

WESTERN TEST SYSTEMS

Quality • Service • Selection

Phone: 1-303-438-9662

Fax : 1-303-438-9685

530 Compton St., Unit #C

Broomfield, CO 80020

OSCILLOSCOPES & ACCESSORIES

TEK 5B10N 2 MHz Time Base, for 5100 series	\$100.00
TEK 7603 100 MHz 3-slot frame	\$250.00
TEK 7A13 100 MHz Differential Comparator	\$450.00
TEK 7B53A 100 MHz Dual Time Base	\$200.00
TEK R7603 Rackmount 100 MHz Oscscope frame	\$200.00
TEK SC502 15 MHz Dual Trace Oscscope, TM500	\$375.00
TEK 7904 500 MHz 4-slot frame	\$500.00
TEK 7904 System w/7A24,7A26,7B80,7B85	\$1,200.00
TEK 7A24 400 MHz Dual Trace Amplifier	\$450.00
TEK 7A26 200 MHz Dual Trace Amplifier	\$250.00
TEK 7A29 1 GHz Single Channel Amplifier	\$850.00
TEK 7B10 1 GHz Time Base	\$500.00
TEK 7B15 1 GHz Delaying Time Base	\$600.00
TEK 7B80 400 MHz Delayed Time Base	\$200.00
TEK 7B85 400 MHz Delta Delaying Time Base	\$250.00
TEK 7B87 400 MHz Time Base, pretigger clk	\$250.00
TEK R7704 Rackmount 175 MHz Oscscope frame	\$250.00
TEK 7S14 1 GHz Dual Channel Sampling Unit	\$700.00
TEK P6046 100 MHz 1X/10X Div. Probe	\$750.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$400.00

WAVEFORM & GENERATORS

HP 3310A 5 MHz Function Generator	\$325.00
TEK DD501 Digital Delay Generator	\$375.00
TEK FG502 11 MHz Function Generator	\$325.00
WAVETEK 135 2 MHz Lin/Log Sweep/Function Gen	\$275.00
HP 214B 10 MHz Pulse Gen., 50V / 50 ohms	\$2,250.00
HP 8080A 1 GHz Dual Channel Pulse Gen.	\$1,400.00
HP 8082A 250 MHz Pulse Generator	\$1,400.00
TEK PG502 250 MHz Pulse Generator, Tr<1ns	\$700.00
HP 8165A Prog. Signal Source, 1 mHz-50 MHz	\$2,600.00
TEK AVG5105 Arbitrary Waveform Generator	\$3,000.00
TEK PFG5505 Prog. 12 MHz Pulse Function Gen.	\$1,275.00

VOLTAGE & CURRENT

HOLT 11 AC Thermal Converter Set	\$4,500.00
SOLARTRON 7150 5-1/2 / 6-1/2 digit DMM, GPIB	\$550.00
HP 6177C DC Current Source, to 50V,500mA	\$600.00
HP 6181C DC Current Source, 100 V, 250 mA	\$675.00
HP 6186C DC Current Source, to 300V,100mA	\$750.00
KEITHLEY 225 Current Source, 1 nA-99.9 mA	\$450.00

IMPEDANCE & COMPONENT TEST

HP 4800A Vector Impedance Meter	\$550.00
BOONTON 62AD 1 MHz Ind. Meter, 2-2000 uH	\$700.00
BOONTON 72BD 1 MHz Cap. Meter, 2-2000 pF	\$700.00
HP 4342A Q-Meter, 70 kHz-22 MHz, Q=5-1000	\$2,250.00
MEGURO MQ-171 VHF Q Meter, 20-230 MHz	\$1,100.00
E.S.I. RS925 9-Decade Resistance Standard	\$2,000.00
E.S.I. SR1010 Resistance Transfer Standards	\$800.00
FLUKE 5450A Programmable Resistance Standard	\$2,750.00
GR 1409 Standard Mica Capacitors, 0.05%	\$150.00
GR 1432-N 5-Decade Resistor, 0.1 OHM-11K	\$275.00
GR 1432-U 4-Decade Resistor, 0.01-111.1 ohm	\$175.00
GR 1433-X 6-Decade Resistor, 0.1 OHM-111K	\$550.00
HP 4329A High Resistance Meter	\$1,350.00
TEK 576 Curve Tracer, to 220W	\$2,250.00
TEK 577D1/177 Storage Curve Tracer	\$2,250.00
TEK 7CT1N Curve Tracer, to 0.5W	\$500.00

POWER & SUPPLIES

GLASSMAN PS/EG-05R-06 5 kV Power Supply, to 6mA	\$500.00
HP 6002A-opt.01 50V/10A Power Supply, to 200 W	\$875.00
HP 6023A Autoranging Supply, 20V/30A/240W	\$1,150.00
HP 6114A Precision Power Supply, 40V 1A	\$875.00
HP 6261B-027 20V at 50A CV/CC Power Supply	\$675.00
HP 6264B 20V at 20A CV/CC Power Supply	\$500.00
HP 6266B 40V at 15A CV/CC Power Supply	\$400.00
HP 6267B 0V at 10A CV/CC Power Supply	\$550.00
HP 6296A 60V at 3A CV/CC Power Supply	\$400.00
HP 6299A 100V at 750mA CV/CC Power Supply	\$250.00
HP 6438B 60V at 5A CV/CC Power Supply	\$375.00
HP 6255A 40V 1.5A Dual Output Supply	\$500.00
TEK PS503A Dual Power Supply	\$250.00

ACME PS2L-1000 0-75 V/ 0-150 A/ 1000 Watt Load	\$450.00
HP 59501A HPIB Power Supply Programmer	\$175.00
HP 6827A Bipolar Supply/Amp, 100 V 500 mA	\$800.00
KIKUSUI PLZ-72W Prog. Load, 4-110V/0-12A/70W	\$200.00

TIME & FREQUENCY

HP 5315A 100 MHz/100 nS Universal Counter	\$550.00
HP 5316A 100 MHz/100 nS Univ. Count, HPIB	\$750.00
HP 5316A-003 100 MHz/100 nS Univ. 1.3 GHz ch	\$950.00
HP 5370B-001 Time Interval Counter, to 20 pS	\$2,250.00
HP E1420A-10,30 VXI Counter, 200 MHz & 2.5 GHz	\$1,500.00
TEK 7D15 225 MHz Universal Counter/Timer	\$275.00
TEK DC5009 Programmable 135 MHz Count/Timer	\$750.00
TEK DC503A 125 MHz Universal Counter/Timer	\$500.00
TEK DC509 135 MHz High Resolution Counter	\$700.00
FLUKE 7220A-111 1.3 GHz Communications Counter	\$650.00
HP 5340A 18 GHz Frequency Counter	\$1,400.00
HP 5340A-01, 11 18 GHz Counter, OXCO, HPIB	\$1,900.00
HP 5342A-1,4,5 24 GHz Counter, OXCO, DAC, HPIB	\$3,900.00
SYSTRON 6054B-05, 26.26 5 GHz Freq. Counter, GPIB	\$2,400.00
GR 1115C Crystal Frequency Standard	\$1,600.00

AUDIO & BASEBAND

HP 3580A-002 Spectrum Analyzer, 5 Hz-50 kHz	\$1,850.00
HP 3586C Selective Level Meter	\$1,750.00
TEK 7L5-025/7603 20 Hz-5 MHz Spectrum An. w/fft	\$2,250.00
HP 334A Distortion Analyzer, -60 dB THD	\$550.00
HP 339A Distortion Analyzer, -95 dB THD	\$2,400.00
TEK DA408A Distortion Analyzer, 0.0025% THD	\$1,500.00
FLUKE 8920A TRMS Voltmeter, 10 Hz-20 MHz	\$700.00
HP 3400A RMS Voltmeter, 10 Hz-10 MHz	\$250.00
HP 4204A Synthesizer, 10 Hz-1 MHz	\$350.00
ROCKLAND 5100 Synth., 1 mHz-1.999999999 MHz	\$400.00
KROHN-HITE 3202 Dual HP/PL Filter, 20 Hz-2 MHz	\$600.00
KROHN-HITE 3342 Dual Filter, 0.001 Hz-99.9 kHz	\$1,100.00
P.A.R. 189 Filter/Amplifier, 0.1 Hz-110 kHz	\$400.00
ROCKLAND 752A-opt.02 Dual Low Pass Filter, 115 dB/oct	\$1,100.00
TEK AM502 Differential Amplifier	\$575.00

RF & MICROWAVE

HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 5371A Modulation Domain Analyzer	\$5,900.00
HP 8406A Comb Gen., 1/10/100 MHz increment	\$450.00
HP 8443A Tracking Generator, 0.1-110 MHz	\$700.00
HP 8444A-opt.059 Tracking Generator, 0.5-1500 MHz	\$1,500.00
HP 8552B IF Section	\$750.00
HP 8553B RF Section, 1 kHz-110 MHz	\$500.00
HP 8554B RF Section, 0.1-1250 MHz	\$800.00
HP 8555A RF Section, 0.01-18 GHz	\$950.00
HP 8555A System, with 8552B & 141T	\$2,375.00
TEK TR503 Tracking Generator, 0.1-1800 MHz	\$1,750.00
HP 11665B Modulator, 0.15-18.0 GHz	\$375.00
HP 8405A Vector Voltmeter, 1-1000 MHz	\$700.00
HP 85020A Directional Bridge, 0.01-4.3 GHz	\$750.00
HP 85021A Directional Bridge, 0.01-18 GHz	\$1,200.00
NARDA 7000A Microwave Multimeter, 0.1-18 GHz	\$1,950.00
BOONTON 1020 Synth. Sig. Gen., 0.15-540 MHz	\$1,850.00
BOONTON 102C Signal Generator, 0.45-520 MHz	\$850.00
FLUKE 6060A/AN Synthesizer, 10 kHz-520 MHz	\$2,000.00
GIGATRONICS 875/86 Levelled Multiplier, Ka & V band	\$8,000.00
HP 85100V Freq. Multiplier, 50-75 GHz out	\$4,250.00
HP 8660C Synthesizer, with 86603A & 86633B	\$4,250.00
WILTRON 7642A-opt.01 Synth. Sig./Swp Gen., 18-40 GHz	\$9,000.00

EIP 928-opt.9201 Programmable Sweep Gen., 1-18 GHz	\$4,000.00
HP 8620C Sweep Oscillator Frame	\$550.00
HP 8620C-opt.011 Sweep Oscillator Frame, HPIB	\$675.00
HP 86222A RF Plug-in, 10-2400 MHz	\$1,400.00
HP 86222B-opt.2 RF Plug-in, 10-2400 MHz, atten.	\$1,950.00
HP 86290B RF Plug-in, 2.0-18.6 GHz, +10dBm	\$2,000.00
WAVETEK 1067 Sweep Gen., 10-2400 MHz, atten.	\$500.00
BOONTON 42B/41-4B Power Meter, 1 MHz-12.4 GHz	\$475.00
BOONTON 42B/41-4E Power Meter, 1 MHz-18 GHz	\$650.00
BOONTON 42B/42-S/3 Power Meter, 1 MHz-8 GHz	\$375.00
HP 432A/478A Power Meter, 0.01-10 GHz	\$375.00
HP 435A/B481A Power Meter, 10 MHz-18 GHz, 100mW	\$1,000.00
HP 435A/B482A Power Meter, 0.1-4200 MHz, 100mW	\$1,000.00
HP 435A/B482H Power Meter, 0.1-4200 MHz, 3 W	\$1,150.00
HP 435A/B484A Power Meter, 10 MHz-18 GHz, 100W	\$1,000.00
HP K486A WR42 Thermistor Mount, 18-26.5 G	\$400.00
HP Q8486A WR22 Power Sensor, 30.0-50.0 GHz	\$1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40 G	\$400.00
WAVETEK 1034A Portable Power Meter, 0.001-18GHz	\$375.00
AILTECH 7618E Noise Source, 15 dB, 0.01-18 GHz	\$675.00
BOONTON 82AD Modulation Meter, 10-1300 MHz	\$1,000.00
M.S.C. MC5112 Noise Source, 25.5 dB, 1-12 GHz	\$325.00

COAXIAL & WAVEGUIDE

HP 11691D Dir. Coupler, 22 dB, 2-18 GHz	\$500.00
HP 11692D Dual Dir. Coupler, 22 dB, 2-18 GHz	\$900.00
HP 33330D Detector, 10 MHz-33 GHz, APC3.5	\$275.00
HP 764D Dual Dir. Coupler, 215-450 MHz	\$150.00
HP 778D-opt.011 Dual Dir. Coupler, 20 dB, 0.1-2GHz	\$400.00
HP 779D Dir. Coupler, 20 dB, 1.7-12.4 GHz	\$375.00
HP 8472A Crystal Detector, 10 MHz-18 GHz	\$150.00
HP R532A Frequency Meter, 26.5-40.0 GHz	\$500.00
KRYTAR 20202016 Directional Detector, 2-20 GHz	\$200.00
MILITARY AS-1346B Double Ridge Horn, 3-8 GHz, N/FI	\$75.00
NARDA 26298 20 dB Atten., 150 W, DC-1 GHz	\$175.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3090-SERIES Precision Hi Directivity Coupler	\$225.00
NARDA 4000-SERIES SMA Mini Directional Couplers	\$75.00
NARDA 4203-6 Dir. Coupler, 6 dB, 2-18 GHz, SMA	\$225.00
NARDA 5070-SERIES Precision Reflectometer Couplers	\$300.00
NARDA 768-30 30 dB Atten., 20W, DC-11 GHz	\$125.00
TRGAS10WR28 Precision Atten., 0-50 dB	\$1,000.00
WEINSCHEL 1515 Power Divider, DC-18 GHz, SMA	\$125.00
WEINSCHEL 1579 Power Divider, DC-26.5 GHz, 3mm	\$275.00
WEINSCHEL 3200-1 Prog. Atten., 0-127 dB, DC-2 GHz	\$200.00
WILTRON 97SF50-1 Directional Bridge, 0.01-18 GHz	\$1,500.00

MISCELLANEOUS

HP 28687A LAN Wire Test Instrument	\$750.00
HP 4935A Transmission Test Set	\$1,650.00
HP 59401A HPIB Bus Analyzer	\$700.00
TEK 1411R-opt.04 PAL Test Signal Generator	\$2,750.00
TEK 144 NTSC Test Signal Generator	\$700.00
TEK 147A NTSC Test Signal Generator	\$950.00
TEK 1485R Waveform Monitor, NTSC & PAL	\$1,850.00
TEK 521A PAL Vectorscope	\$1,500.00
TEK J16/J6523 Spot Luminance Photometer	\$900.00
HP 59307A HPIB VHF Switch	\$200.00
P.A.R. 5206 Lock-In Amplifier, 2 Hz-200 kHz	\$3,000.00

• VISA • MASTERCARD • OPEN ACCOUNT • 90 DAY WARRANTY • 10 DAY INSPECTION •

CIRCLE 319 ON FREE INFORMATION CARD

www.americanradiohistory.com

CALL TOLL FREE
 1-800-292-7711
 1-800-445-3201 (Can)

C&S SALES

EXCELLENCE IN SERVICE

**WRITE FOR
 FREE CATALOG**



Line Tracker
 MV-963
\$52.95
 (Infra-red Sensor)
 The robot follows
 a black line
 on white paper
 Preassembled PCB



**Dual-Display
 LCR Meter**
 w/ Stat Functions
 B+K Model 878
\$239.95
 Auto/manual range
 Many features
 with Q factor
 High Accuracy

Electronic Tool Kit Model TK-1000
 A professional organizer tool-kit at affordable prices. No student should be without this unique tool kit that holds all the tools you need.

Including:
 Diagonal Cutter
 Long Nose Pliers
 6" Wire Stripper
 Solder 60/40
 6" Screwdriver
 6" Phillips Driver
 Safety Goggles
 IC Puller
 3pc Nut Drivers
 Iron 25W
 Iron Stand
 Solder Wick
 Desoldering Pump
 5 pc Solder Ease Kit
 6pc Precision Screwdrivers

\$39.95



Robotic Arm
 Y-01
\$49.95
 (Wired Control)
 Movement grabs
 & releases,
 lifts & lowers,
 pivots from side to side



**Stereo Cassette Player
 Kit**
 Model
 TR-18K
\$16.95
 Headphones
 Included



**Digital
 Multimeter**
 EDM-83B
\$175.00
 Almost every
 feature available
 Bargain of
 the decade



**Elenco
 LCR + DMM**
 LCM-1950
\$79
 12 Functions
 Freq to 4MHz
 Inductance
 Capacitance



**Digital
 Capacitance
 Meter**
 CM-1555
\$49.95
 Measures capacitors
 from .1pf to 20,000µf



**Digital
 LCR Meter**
 LCR-680
\$79.95
 3-1/2 Digit
 LCD Display
 Inductance
 1uH to 20MΩ



Function Generator
 GF-8026
\$239
 Int/Ext
 Operation
 Sine, Square, Triangle, Pulse
 Ramp, .2 to 2MHz, Freq Ctr




3-3/4 Digit Multimeter
 BK-390
\$139.00
 0.1% DCV accy
 Analog bar graph
 Auto/manual ranging
 Capacitance meas
 Temperature probe



**Digital
 Multimeter Kit**
 w/ Training Course
 M-2665K
\$49.95
 Full function 34 ranges
 Ideal school project
 M-2661 (Assembled) **\$55.00**



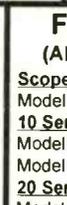Frequency Counter
 F-1225
\$225.00
 8 Digit LED display
 Wide meas range
 High sensitivity
 Data hold function
 Input impedance 1MΩ or 50Ω
 10:1 input attenuation function



Fluke Multimeters
 (All Models Available Call)
Scopemeters
 Model 97 \$1,795
 Model 10 Series \$62.95
 Model 10 \$62.95
 Model 12 \$84.95
 Model 20 Series \$175
 Model 2911 \$175
70 Series
 Model 7011 \$69.95
 Model 7311 \$97.50
 Model 7711 \$149
 Model 7911 \$175
80 Series
 Model 87 \$289



**Triple Power
 Supply**
 XP-620
 By Elenco
\$75.00
 3 fully regulated supplies; 1.5-15V @ 1A, -1.5 to -15V @ 1A or 3-30V @ 1A & 5V @ 3A Kit XP-620K **\$49.95**



**Quad Power
 Supply**
 XP-581
 By Elenco
\$79.95
 Four supplies in one unit; 2-20V @ 2.5A, 5V @ 3A, -5V @ .5A and 12V @ 1A. All regulated and short protected



**High Current DC
 Power Supply**
 BK-1686 **\$169.95**
 3 to 14 VDC Output
 12A @ 13.8V
 For servicing high
 power car stereos,
 camcorders, ham radios, etc.
 Connect 2 or more in parallel



**Wide Band
 Signal
 Generators**
 SG-9000
\$124.95
 RF Frequency 100K-450MHz
 AM modulation of 1KHz Variable
 SG-9500 150MHz **\$239.00**

Telephone Kit
 PT-223K
\$14.95
 Available
 Assembled
 PT-223
\$15.95



**Function Generator
 Blox**
 #9600
 By
 Elenco
\$29.95
 Kit **\$28.95**
 Sine, Triangle, Square Wave



**Learn to Build & Program
 Computers with this Kit**



MM-8000
 By Elenco
\$129.00

From scratch you build a complete system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor, which uses similar machine language as IBM PC.

Digital/Analog Trainer
 Complete Mini-Lab For Building,
 Testing, Prototyping Analog and Digital



By Elenco
 in U.S.A.

XK-525
\$159.95
 Kit
XK-525K
\$129.95

Designed for school projects, with 5 built-in power supplies. Includes a function generator with continuously variable, sine, triangular, square wave forms. All power supplies are regulated and protected against shorts.

**AM/FM Transistor
 Radio Kit**
 with Training Course
 Model AM/FM 108
\$29.95

14 Transistor, 5 Diodes
 Easy to build because
 schematic is printed on the PCB
 Makes a great school project
 Model AM-550 AM Only **\$17.95**

**Telephone Line
 Analyzer**



Kit TT-400K **\$19.95**
 Assembled TT-400 **\$26.95**

WE WILL NOT BE UNDERSOLD
 UPS SHIPPING: 48 STATES 5%
 IL RES 7.5% TAX (\$3 min \$10 max)
 OTHERS CALL

C&S SALES INC.

150 WEST CARPENTER AVENUE, WHEELING, IL 60090
 FAX: 708-520-0085 (708) 541-0710



**15 DAY MONEY BACK
 GUARANTEE**
FULL FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 335 ON FREE INFORMATION CARD




www.americanradiohistory.com

**FREE PROBES
WITH ALL
SCOPES**

**ELENCO ♦ HITACHI ♦ B+K
SCOPES
AT GUARANTEED LOWEST PRICES**

**WRITE FOR
FREE
CATALOG**

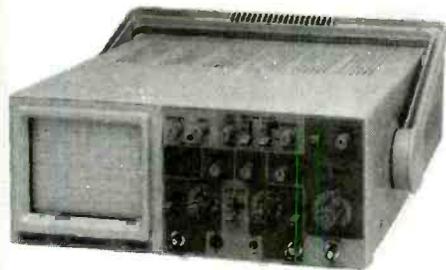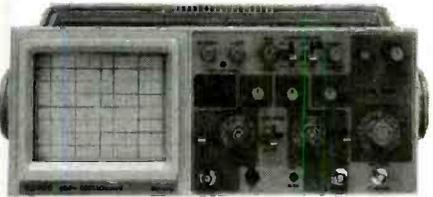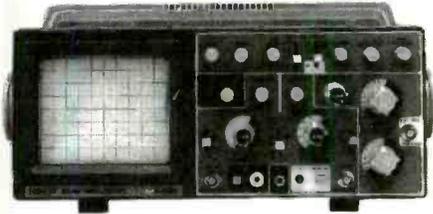**QUALITY - ELENCO OSCILLOSCOPES
2-YEAR WARRANTY**



Dependable Equipment at Affordable Prices

60MHz

S-1360 \$775

Delayed Sweep

S-1365 \$849

Cursor Readout

- ♦ Voltage, Time
- ♦ Frequency differences displayed on CRT

40MHz

S-1340 \$495

2- Channel

S-1345 \$575

Delayed Sweep

- ♦ Beam Find
- ♦ Component Tester

25MHz

S-1325 \$325

2- Channel

S-1330 \$449


Delayed Sweep

- ♦ Beam Find
- ♦ Component Tester

B+K 20MHz

2 Channel

Model 2120 \$389.00

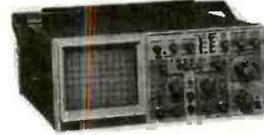

Delayed Sweep

Model 2125 \$539.95

40MHz DUAL -TRACE

Model 1541B

\$749.95

- 1mV/div sensitivity
- Video sync separators
- 2 axis input
- Single sweep
- V mode-displays 2 signals unrelated in frequency

60MHz DUAL-TRACE

Model 2160

\$949.95

- 1mV/div sensitivity
- Sweep to 5ns/div
- Dual time base
- Signal delay line
- Component tester
- V mode-displays 2 signals unrelated in frequency

100MHz THREE-TRACE

Model 2190

\$1,379.95

- 1mV/div sensitivity
- Sweeps to 2ns/div
- Dual time base
- Signal delay line
- 19kV accelerating voltage
- Calibrated delay time multiplier

**20MHz ANALOG with
DIGITAL STORAGE**

Model 2522A

\$869.95

- 20MHz analog bandwidth
- 20MS/s sampling rate
- 2k memory per channel
- 20MHz equivalent time sampling

HITACHI POPULAR SERIES

V-212 - 20MHz, 2 Channel	\$449.00
V-222 - 20MHz, DC Offset	\$695.00
V-422 - 40MHz, Dual Trace	\$849.00
V-522 - 50MHz, Dual Trace	\$975.00
V-523 - 50MHz, Delayed Sweep	\$995.00
V-525 - 50MHz, w/ Cursor	\$1,069.00

HITACHI COMPACT SERIES SCOPES

V-660 - 60MHz, Dual Trace	\$1,375.00
V-665A - 60MHz, DT, w/cursor	\$1,449.00
V-1060 - 100MHz, Dual Trace	\$1,549.00
V-1065A - 100MHz, DT, w/cursor	\$1,695.00
V-1085 - 100MHz, QT, w/cursor	\$2,125.00
VC-6045A - 100MHz, Digital Stor	CALL
VC-6025A - 50MHz, Digital Stor	CALL

**Elenco DS-203 20MHz, 10MS/s
Digital Storage Oscilloscope**



\$749

2K Word Per Channel • Plotter Output
8 Bit Vert. Resolution • 2048 Pts Hor.
Resolution • Much More.....

FLUKE SCOPEMETERS

A handheld instrument that combines a 50MHz, 25MS/s dual channel digital storage oscilloscope with feature-packed 3000 count digital multimeter.



Model 93 - \$1,225
Model 95 - \$1,549
Model 97 - \$1,795

- Autoset, automatically sets voltage, time & trigger
- Multimeter display; 3-2/3 digits (>3000 counts)
- True RMS volts; AC or AC+DC up to 600V

C&S SALES INC.

150 WEST CARPENTER AVENUE, WHEELING IL 60090
FAX 708-520-0085 (708) 541-0710

CALL TOLL FREE

1-800-292-7711

1-800-445-3201 (Can)



15 DAY MONEY BACK GUARANTEE
FULL FACTORY WARRANTY

ALL PRODUCTS ARE FACTORY NEW

PRICE SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 335 ON FREE INFORMATION CARD

www.americanradiohistory.com

NIGHT VIEWERS

FIBER OPTIC TUBES Used 1st gen. 25 or 40mm (input/output window dia). With a suitable 'fast' lens give a good image in half moon light. Can be IR assisted to see in total darkness. Each tube is supplied with an 9V - EHT power supply kit: 25mm tube \$90, 40mm tube \$120

We also have blemished versions of these tubes (not in central viewing area). Satisfaction guaranteed! Both sizes (please specify) & EHT kit \$35

INTENSIFIED NIGHT VIEWER KIT See in the dark! Make your own night scope that will produce good vision in sub-starglight illumination! We supply a three stage fiber optically coupled image intensifier tube and an EHT power supply kit, lens and eyepiece. 25mm \$270, 40mm \$360

SMALL PASSIVE NIGHT VIEWER KIT



Supplied with new and completely assembled USSR made scope. The EHT power supply is supplied in kit form. Will work in extremely low light levels! Best value small night vision scope available: \$220

Tube only from the above and an EHT power supply kit: \$90

IR TUBE AND SUPPLY A tube and supply combination that can be used as the basis of making a very sensitive IR responsive viewer. Typical sensitivity 0.01 lux. Tube and supply kit \$80

CCD CAMERA-VCR SECURITY SYSTEM

Ready made PIR detector module and learning remote control combination can trigger any domestic IR remote controlled VCR to RECORD human activity within a 6m range with an 180° view. Starts VCR recording at first movement and ceases recording a few minutes after the last movement has stopped. Just like commercial CCD-video recording systems costing \$1000's!! No connection needed to your existing VCR. IR detector module, control kit, IR learning remote control and instructions \$70

TINY PCB CCD CAMERA Mono, with auto iris lens, 0.1 lux, IR responsive, can be used in total darkness. 1.8 x 3.75 x 1 inch, weight 1.4 oz. Can be connected to video-in of a standard monitor or VCR. \$99

LOW COST IR ILLUMINATOR KIT Use with CCD camera. Has 42 880nm/30mW LEDs. Variable power output, 10-15V DC operation. \$30

LASERS

HELIUM-NEON 633nm red laser tubes from new and near new equipment. Output power in the range of 2.5 to 7.5mW. Includes our 12V Universal Laser power supply. Warning: High voltage at dangerous energy level 2.5-4mW tube & supply \$50 4-7.5mW tube & supply \$80

VISIBLE LASER DIODE KIT 5mW 670nm visible laser diode and collimating lens, housing and driver kit. Easy to build, very small \$26

GEIGER COUNTER

Ready made Geiger counter detects dangerous Beta and Gamma rays. Two-modes: accumulates counts or terminates count after 1 minute. Alarm sounds if radiation exceeds a safe level. LCD display, 9V battery operation (15mW). \$74

KITS AND BITS

2-CHANNEL UHF REMOTE CONTROL KIT 1 Tx and 1 Rx \$31, extra Tx: \$12

4-CHANNEL UHF REMOTE CONTROL KIT 2 Tx and one Rx: \$68

LASER BEAM COMMUNICATOR KIT: Tx, Rx, plus IR laser: \$39

PLASMA BALL KIT: PCB and components, needs a light bulb: \$18

SLAVE FLASH TRIGGER: Triggers a second flash unit by picking up light from camera mounted flash: \$5.50

SOUND TRIGGERED FLASH: Triggers flash from sound picked up by a microphone, adjustable: \$10

PC DRIVEN ELECTROCARDIOGRAM: Silk screened/solder masked PCB only and 3.5" disk with instructions. Uses common components: \$8

FM TRANSMITTER KIT-MKII: \$8

HIGH POWER IR LEDs 880nm 12° 30mW @ 100mA 10 for \$6

INFRARED FILTER Very high quality IR filter and plastic lens cover. Fits over most torches incl MAGLITES, for a good source of IR. Use with passive and active viewers. \$11

VEHICLE COMPUTER

Solar/battery powered bicycle-vehicle computer. Programmable wheel dia, so can be used on any wheel! Weather and shock resistant, speedometer, average & maximum speed, tripmeter, odometer, auto trip timer, scan, freeze frame memory, clock, pick-up sensor/magnet and mounting hardware supplied. \$25

TINY FM TRANSMITTER

Tiny ready-made self-contained FM transmitter in a small black metal case. Powered by single 1.5V silver oxide LR44/G13 battery with inbuilt mic. Tuning range 88-108MHz, battery life 60 hours, weight 15g. Dimensions: 1.3" x 0.9" x 0.4". \$27

OATLEY ELECTRONICS (AUSTRALIA)

Phone 011 61 2 579 4985

Phone orders Sunday to Thursday

East Coast from 7pm to 2am West Coast 4pm to 11pm

Fax 011 61 2 570 7910

orders and text catalog by email: oatley@world.net

Mastercard, Visacard, American Express cards with phone, fax and email orders

P&P for most orders by Federal Express \$15 - \$25

All prices are in US dollars

TOP SECRET

CONSUMERTRONICS
2011 Crescent Dr., P.O. Drawer 537
Alamogordo, NM 88310

Voice: (505) 439-1776, 439-8551
8AM - 7PM MST, Mon - Sat

Fax: (505) 434-0234, 434-1778 (orders only)

If you get voice, enter #11 #11 any time, 24-hr

Free Tech Support (relates directly to your order or prospective order): Tues. & Thurs. only.

10% Off on orders \$100+ - 15% Off over \$200+

Add \$5 total SH (US, Canada). All items in stock.

VISA, MCARD OK. No CODs or 'bill me's'. New Catalog (200+ offers) \$2 w/order, \$5 w/b (check or MO).

NO dealers. Since 1971. As seen on CBS '60 Minutes', 'Forbes', etc. By John Williams - former Lockheed Senior Engineer, NMSU CS Professor, DOD Electronic Weapons Engineer, NIH Health Physicist.

Wanted: 5 MAC III, PC486 (or better), peripherals, new surplus electronic parts, test equipment - buy, trade.

All software supports all IBM-PC compatible x86 systems (8088 - Pentium)

Off-The-Shelf HARDWARE

Van Eck Systems • Data Card Reader/Writers

• ATM3 • RF/EM/UV/Radar/Ultrasonic/IR/Light/Sound Detectors/Receivers/Xmitters/Jammers/Blasters • Security/Surveillance

• EM Lab/Weaponry/Countermeasures • Neuro-Phone/Alte/Homonymus/Resonant Crystal Radicals

• Voice Disguisers • ESS Infinity Devices • Phone Color Boxes • DTMF Decoders

• Lineman's Handsets • Bug/Tap Detector/Blaster • Bumper Beeper/Child Finder • Panic Button • Carjack/Kidnap Foller • Hidden Presence Detectors • Hearing Assistor • Shriek Module • TENS • Subliminal Mixer/Amp • Vortex Generator • 6th Sense Communicator • Noise Cancel. System • Electronic Downer • Laser • Levitator - more! See our New Catalog!

SPECIAL PROJECTS

We design/build/obtain/repair/modify/maintain/consult on any device/system/process/project - electronic/computer/mechanical/optical (ex: phone/auto/security/radionic/lab/energy/HV/EM/RF/Radar/ultrasonic/IR/UV/commo/consumer) for business/personal/invention needs. Describe & include \$30 pre-engineering fee (no obligation). Time & cost estimates 7-10 days. Confidentiality guaranteed.

CELLPHONE MODS

See our Catalog for our infamous cellphone modification guide (\$89) - detailed, comprehensive, covers all makes - 10 times more info than competitor's 'guide'. (Do Special Projects (above) to get up-to-date hardware/software).

VOICE MAIL HACKING

How Voice Mail Box (VMB) systems are used and the specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BIX, GENESIS, EZ, SYDNEY, PHONE MAIL, AUDIX, CINDY, CENTAGRAM, SPERRY LINK, RSVP, etc. Absolutely required for all users, sysops and security personnel \$29.

PBX HACKING

1,000s of PBXs are hacked to the tune of \$ Billions/yr! While 'VOICE MAIL HACKING' details how VMSs are hacked for 'phun' and profit - including VMS methods for hacking PBXs themselves - 'PBX HACKING' addresses ALL issues relating to PBX hacking, including countermeasures! Can your business or agency afford a \$90,000 phone fraud loss (the average loss due to hacked PBXs)? As described in Forbes Magazine. \$29

PHREAKING CALLER ID & ANI

Details on how they work and dozens of effective ways of defeating Caller ID, ANI, *69, *57, and Call Blocking and *67. Also describes Caller ID, Orange, Beige, Cheese and CF Boxes, ESS, SS7, E-911, various CLASS services, CWA, NON PUB DA, CAMA, DNR, 800-ECR, Diverters, Extenders, Centrax - more. \$29.

Beyond PHONE COLOR BOXES

Dozens phone color boxes described - many circuits. Plus Call Forwarding, Conferencing, Phreak History, Glossary, Diverters, Extenders, Loops, REMOBS, Bridging Heads & Cans, Optocom, 3rd Party and many other non-box methods - more. \$39

ROBOFONE AUTODIALER

Powerful, versatile, menu-driven 'Wargames' autodialer lets you dial any quantity (up to 10K) or mix of local/long distance numbers in any order, over any length of time, whether busy or answered (your choice) and log the times, commands and results to monitor, printer and/or disk. Quick-dial directory of up to 600 numbers. BUSY redial options. Direct modem command and control. All Result Codes, including VOICE and RINGING. Optional shell to terminal program upon CONNECT. Exit to menu or DOS (for batching). Manual + Disk! \$29.

By an ORDER of the MAGNITUDE

The most comprehensive, hard-hitting, hi-tech survival book ever written! Topics include electronics, computers, energy, weapons, concealment, revenge, alarms, etc to survive today's dangerous world. We all face increasingly financially and physically brutal times! Field-expedient use of technology in various threat and conflict environments and scenarios. \$49

COMPUTER PHREAKING

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS, etc are implemented. Dozens of computer crime, abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system (Ed. Glossy, PC Magazine). BBS advice, password defeats, choice - much more! Manual + Disk! \$39.

THE HACKER FILES

Compilation of 100s of the best articles written (in ASCII) by top hackers & phreakers. Covers every major topic in hackerdom! 3 HD Disks! \$59.

Beyond VAN ECK PHREAKING

Caves/dropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the Consumertronics and the original Top Secret Van Eck designs! \$29.

STOPPING POWER METERS

As reported on CBS '60 Minutes': How certain devices can slow down - even stop - without meters - while loads draw full power! Device simply plugs into one outlet and normal loads into other outlets. Also describes meter creep, overload droop, etc. Plans \$29.

I.G. MANUAL: External magnetic ways (applied to the meter itself) to slow down and stop watt-hour meters while drawing full loads. Plans \$19

KW-HB METERS: How watt-hour meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$19. Any 2, \$38. All 3, \$59.

AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and details exposed! 100+ methods detailed, including: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, super-cool, vibration, pulse, high voltage - others. Case histories, law, countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to \$250,000 in cash. Recent \$350,000 ATM crime spree still unsolved! \$39

CREDIT CARD SCAMS

Cardholders, merchants, banks suffer \$ Billions in losses annually because of credit card fraud. Describes every known means of credit card fraud and scams. Protect yourself! \$29.

CONS SCAMS & SWINDLES

Cons & scams and related swindles fleece Americans of \$100+ Billion per year! The most comprehensive survival manual on cons & scams of all kinds - from the classic to hi-tech. Details on 100s and many variations. And countermeasures. Protect yourself! \$39.

STEALTH TECHNOLOGY

Police radar is fascinating! It also has error rates of 10-20%! Every known error mode - stealth method and material used to minimize radar reflections - tactic and strategy to fight unjust radar tickets (that cost you \$100s in insurance and legal cancellation) - methods to detect and jam signals - fully described! \$29.

SECRET & SURVIVAL RADIO

Optimum survival and security radio equipment, methods, freq allocations and voice/data scrambling/encoding. Includes small receivers/transmitters, telemetry, antenna optimizations, remote monitoring and control, security, surveillance, and ultrasonic, fiber-optic and infrared commo. 70+ circuit plans, tables. \$29.

HIGH VOLTAGE DEVICES

High voltage plans: Stun gun, laser, prod, Van, Blaster, Fishar, Zapper, Audio/RF/Radar/Jammer, Fence Charger, Plasma & Van de Graeff Generator, Jacobi's Ladder, Geiger Counter, Ozon Gun, Fish Stunner, Plant Stim., Killray, more! All plans for only \$29.

UNDER ATTACK!

Electromagnetic interference and Electronic Weapon Attacks cause: Cancer, birth defects, and profound psychological, neurological, and cardiovascular ailments. System disorders! Destructive to people, animals, plants, equipment! Includes ACTUAL CASES OF EM ATTACKS (we investigated!) Includes how to verify and pinpoint EM and electronic attack sources, and effective countermeasures. \$29. **EM BRAINBLASTER:** Tutorial and plans for powerful ELECTROMAGNETIC WEAPONS and LAB DEVICES. Optimum circuits, freqs, waveforms, duty cycles, intensities. Thorough. \$29. Both \$49.

RADIONICS MANUAL

Exciting electronic, electronic, electromagnetic therapeutic, diagnostic & preventive devices (mostly experimental). History, descriptions, plans (dozens), availabilitys of Radionics Devices from early to modern. While drugs cost \$100s, electricity costs pennies! \$29. **HEAL YOURSELF:** Plans for 3 major electronic therapeutic devices of types approved by FDA. \$19. Both \$39.

CRYPTANALYTICAL TECHNIQUES

Five powerful menu-driven crypto programs (in COM and BAS source code) to analyze, decrypt 'secure' ciphertexts. Worked-out examples. Recommended by prestigious 'Computers & Security' Manual + Disk! \$29.

ROCKET'S RED GLARE

How to design and build solid-propellant amateur and survival rockets. Emphasis on formulation, manufacture, installation of propellants, motors, igniters, etc. Includes list of commonly available materials, and the design of launch pads and test beds and their electronics. \$29.



FIREWORKS: How firecrackers (M-80s, blockbusters, cherry bombs), small rockets, volcanos, fountains, sparklers and safety fuses are made and colored. Simple, cheap, common ingredients. \$9. Both \$36.

ULTIMATE SUCCESS MANUAL

Underpaid, overworked, harassed or abused? Victim of office politics? Stuck in dead-end job? Can't find a good job? Expect to be laid off, fired, or transferred soon? The ultimate no-holds-barred, looking-after-#1 Machiavellian techniques to find, obtain, optimize and keep top jobs, pay and benefits. The Rules of the Game for a Game without Rules! From resume to CEO. \$29.

Check Out These Deals From CIRCUIT SPECIALISTS!

Ball Bearing 12V DC Fans

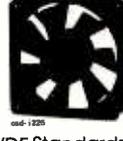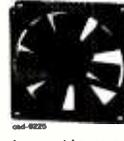

These High Quality Fans feature Ball Bearings and Brushless DC Motors. All of them are designed to meet UL, CSA & VDE Standards. Design these fans into power supplies, computers or other equipment requiring additional air flows for heat removal. These fans are regular Circuit Specialists stock items — they are not surplus.

**INDUSTRY
BEST
PRICING!**

CAT NO	1	10	25	100
CSD 4010-12	\$ 9.88	\$ 6.38	\$5.48	\$4.87
CSD 6025-12	9.38	5.91	5.41	4.71
CSD 8025-12	8.88	5.85	5.19	4.49
CSD 9225-12	8.95	6.14	5.29	4.59
CSD 1225-12	11.45	8.96	7.82	6.85

**O.E.M.
PRICING!**


Specifications

CAT NO	DIMENSIONS (MM)	RATED VOLTAGE (V)	START VOLTAGE (V)	INPUT CURRENT (A)	AIR FLOW (CFM)	STATIC PRESSURE (INCH-H ₂ O)	SPEED (RPM)	NOISE LEVEL (dB)	WEIGHT (g)
CSD 4010-12	40x40x10mm	12	7	0.06	5.1	0.19	5,500	26	20
CSD 6025-12	60x60x25mm	12	5	0.13	13.7	0.165	4,500	28	65
CSD 8025-12	80x80x25mm	12	5	0.16	37.8	0.177	3,000	31	80
CSD 9225-12	92x92x25mm	12	5	0.32	42	0.18	2,800	37	95
CSD 1225-12	120x120x25mm	12	5	0.35	62	0.180	2,500	42	135

Ball Bearing AC Fans



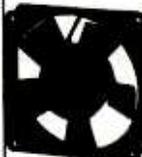Size: 80 x 80 x 38.5mm (3.15 x 3.15 x 1.5")
Weight: 370±10gm (0.82lb.)
Frame/Housing: Aluminum
Impeller: Glass reinforced thermoplastic UL94V-0
Bearing Type: Ball Bearing
Dielectric Strength: 1 minute at 1,500VAC/50-60Hz
Operating Temp: -20°~+85°C
Life Expectancy: 50,000 Hrs (at 25°C, 65%RH)
Motor Protection: Impedance Protected
Safety Approvals: Meets UL, CSA, VDE Standards



Size: 120 x 120 x 25.5mm (4.71 x 4.71 x 1.00")
Weight: 390±10gm (0.86lb.)
Frame/Housing: Aluminum
Impeller: Glass reinforced thermoplastic UL94V-0
Bearing Type: Ball Bearing
Dielectric Strength: 1 minute at 1,500VAC/50-60Hz
Operating Temp: -20°~+85°C
Life Expectancy: 50,000 Hrs (at 25°C, 65%RH)
Motor Protection: Impedance protected
Safety Approvals: Meets UL, CSA, VDE Standards

CAT NO	1	10	25	100
CSA8038AC	\$15.26	\$12.92	\$10.98	\$9.73

CAT NO	1	10	25	100
CSA1225AC	\$15.28	\$12.94	\$11.01	\$9.88

Specifications

CAT NO	DIMENSIONS (MM)	NOMINAL VOLTAGE (V)	FREQUENCY (HZ)	SPEED (RPM)	INPUT POWER (W)	AIR FLOW (M3/MIN)	STATIC PRESSURE (MM)	NOISE LEVEL (dB)
CSA8038AC	80x80x38.5	110/120	50/60	2300/2600	9/7	0.63/0.72	3.5/4.5	31/34
CSA1225AC	120x120x25.5	110/120	50/60	2000/2300	12/10	1.56/1.70	4.6/4.8	23/36

Cool your 486 or Pentium CPU's with one of these CPU Cooling Fans.



**NEW
LOWER
PRICES!!**

CAT NO	DESCRIPTION	1	5	10
CC-M3	Cooling Fan for 486 CPU's	\$7.50	\$6.00	\$5.00
PENTUM FAN	Cooling Fan for Pentium CPU's (Will not fit Pentium 60 or 66MHz)	9.50	8.00	7.00

Plastic Fan Filter Assemblies

These fan filter packages consist of a guard, foam filter media and media retainer for tubeaxial fans. The retainer is easy to install without removing the fan or guard while the foam filter is also simple to clean and change. Use these kits to protect your equipment from airborne contamination and reduce external fan noise.

CAT NO	DESCRIPTION	1	10	25	50
GRM 60	Plastic Fan Filter Kit for 60mm Fans	\$1.76	\$1.42	\$1.20	\$.98
GRM 80	Plastic Fan Filter Kit for 80mm Fans	2.20	1.75	1.48	1.28
GRM 92	Plastic Fan Filter Kit for 92mm Fans	2.60	2.05	1.74	1.40
GRM 120	Plastic Fan Filter Kit for 120mm Fans	2.92	2.19	1.84	1.56

Fan Power Cord 2' Length, SPT-1, AWG18 x 2C, UL/CSA

CAT NO	DESCRIPTION	1	10	25	50
C180	Fan Power Cord	\$1.28	\$1.14	\$.94	\$.78

Metal Fan Filter Assemblies

For use with tubeaxial fans. These wire formed fan guards provide extra safety.

CAT NO	DESCRIPTION	1	10	25	50
FG40-2	Wire Formed Fan Guard for 40mm Fans	\$1.72	\$1.29	\$1.09	\$.86
FG60-4	Wire Formed Fan Guard for 60mm Fans	1.92	1.44	1.19	.96
FG80-5	Wire Formed Fan Guard for 80mm Fans	2.00	1.50	1.24	.99
FG92-5	Wire Formed Fan Guard for 92mm Fans	2.28	1.71	1.39	1.14
FG120-15A	Wire Formed Fan Guard for 120mm Fans	2.52	1.89	1.57	1.26

RECEIVE YOUR FREE COPY OF OUR LATEST 100+ PAGE CATALOG!

It's chock full of all types of electronic equipment and supplies. We've got I.C.'s, capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call 800-528-1417, ext. 5, to leave a message on our catalog request line.

CIRCUIT SPECIALISTS, SINCE 1971

**800-528-1417
602-464-2485
602-464-5824(FAX)**

WE ACCEPT:

VISA, Mastercard, Discover Card & American Express

Fix It Yourself!



- Hands-on, detailed, troubleshooting instructions
- "How to" primer for test equipment: oscilloscopes, frequency counters, video analyzers, etc.
- Schematic diagrams
- Trouble analysis flowcharts
- Preventive maintenance techniques
- Safety precaution checklists
- Comprehensive replacement parts list
- Directory of manufacturers

It's easy, fast, and rewarding to repair it yourself with the Electronics Repair Manual!

Leading Manufacturers Represented...

- Emerson • Nintendo • RCA • Technics
- Hitachi • Panasonic • Sanyo • Toshiba
- IBM • Pioneer • Sharp • Zenith
- NEC • Quasar • Sony and others!

✓ Dozens of Fix-It-Yourself Projects for...

- | | |
|---------------------------------------------|-------------------------------------------|
| <input type="checkbox"/> CD Players | <input type="checkbox"/> Amplifiers |
| <input type="checkbox"/> VCRs | <input type="checkbox"/> Car Radios |
| <input type="checkbox"/> Televisions | <input type="checkbox"/> Air Conditioners |
| <input type="checkbox"/> Camcorders | <input type="checkbox"/> AM/FM Tuners |
| <input type="checkbox"/> Computer Equipment | <input type="checkbox"/> Thermostats |
| <input type="checkbox"/> Fax Machines | ...and more! |
| <input type="checkbox"/> Telephones | |

30-Day Free Trial!




Keep Your Skills Up-to-Date!

The Electronics Repair Manual and the Modern Electronics Manual will be a valuable reference for years to come. Supplements, each containing over 125 pages, add new repair projects, valuable insights into new technologies, diagnostic and repair techniques, electronics projects, and more schematic diagrams into your manual. Just \$35 each plus shipping and handling. Supplements are sent 4-5 times a year and are fully guaranteed. Return any supplements you don't want within 30-days and owe nothing. Cancel anytime.

CIRCLE 300 ON FREE INFORMATION CARD

CME-200CP PINHOLE COLOR CAMERA

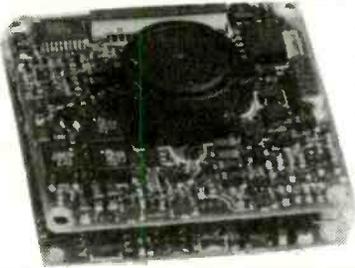

- 1/3" CCD PICKUP DEVICE
- 2.5 LUX SENSITIVITY
- 492 LINES RESOLUTION
- 12 VDC OPERATION
- 1-5/8" x 1-5/8" x 5/8"
- STANDARD VIDEO OUT

\$ 495.00

CAMERA BOARD MODULES

CME-100S	STANDARD LENS CAMERA	\$ 125
CME-100P	PINHOLE LENS CAMERA	\$ 135
CME-100P(M)	PINHOLE LENS CAMERA with BUILT IN MICROPHONE	\$ 145
CME-100C	"C" MOUNT CAMERA	\$ 145
CME-200SCP	1/3" COLOR CAMERA BOARD	\$ 245

CREATIVE MICRO ELECTRONICS, Inc.

P.O. BOX 4477 ENGLEWOOD, CO 80155-4477
PHONE: (800) 771-1295 (Out of Colorado Only)

**CME-2.4T/R 2.4 Ghz 5 CHANNEL -
VIDEO/AUDIO - TRANSMITTER/RECEIVER
SYSTEM - UP TO 500' RANGE -
3,000' WITH DISH ANTENNA
\$ 1,295.00**



CALL OR WRITE FOR FREE CATALOG
PHONE: (303) 771-1288 FAX: (303) 771-1136

Move Up to the Ultimate in Robotic Kits.

OWIKIT™



OWI's "Next Generation" of affordable, rugged Robot Kits challenge the enthusiast to solder circuit boards and mechanically assemble.

Each OWIKIT also incorporates the basic principles of robotic experiments, sensing and locomotion, guaranteeing an exciting, hands-on adventure of knowledge and fun!

But remember! OWI is the recognized founder and leader in Educational Robot Kits. ACCEPT NO IMITATIONS.



GRAND PIANO	BT-802	47 Note Memory	8 Pg. Book	\$ 31.95
ROULETTE	BT-805	Regulation - 38 Numbers	8 Pg. Book	19.95
S-CARGO	OWI-936K	Sound Sensor	47 Pg. Book	29.95
WAO II	OWI-961K	Programmable - Graphic	59 Pg. Book	79.95
SPIDER	OWI-962K	Infrared Sensor	49 Pg. Book	39.95
LINE TRACKER	OWI-963K	Infrared Sensor	48 Pg. Book	39.95
MANTA	OWI-966K	Sound / Touch Sensor	44 Pg. Book	29.95
MOON WALKER	OWI-989K	Solar Sensor	10 Pg. Book	39.95

1160 Mahalo Place
Rancho Dominguez, CA
90220-5443
(310) 638-7970
Fax: (310) 638-8347
WWW: Homepage coming soon.
Look for us under robotic kits.



Order M - F: 8a.m. - 4p.m. PST

BREAST CANCER BEGINS EVEN SMALLER THAN THIS. THAT'S WHY YOU NEED A YEARLY MAMMOGRAM, ESPECIALLY AS YOU GET OLDER. MAMMOGRAMS CAN DETECT LUMPS TOO SMALL FOR YOU TO FEEL AND EARLY DETECTION MAY SAVE YOUR LIFE, SO CALL 1-800-ACS 2345.

GET A MAMMOGRAM. EARLY DETECTION IS THE BEST PROTECTION.

AMERICAN HEART ASSOCIATION MEMORIALS & TRIBUTES




1-800-AHA-USA1

American Heart Association


386 SBC \$83

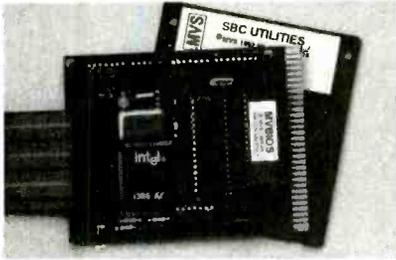OEM (1K) PRICE INCLUDES:
 - 5 SER (8250 USART)
 - 3 PAR (32 BITS MAX)
 - 32K RAM, EXP 64M
 - STANDARD PC BUS
 - LCD, KBD PORT
 - BATT. BACK. RTC
 - IRQ0-15 (8259 X2)
 - 8237 DMA 8253 TMR
 - BUILT-IN LED DISP.
 - UP TO 8 MEG ROM
 - CMOS NVRAM
 USE TURBO C, BASIC, MASM RUNS DOS AND WINDOWS EVAL KIT \$295



\$95 SINGLE PIECE PRICE UNIVERSAL PROGRAMMER

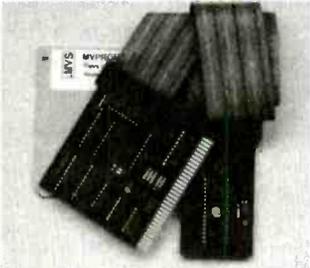- DOES 8 MEG EPROMS
- CMOS, EE, FLASH, NVRAM
- EASIER TO USE THAN MOST
- POWERFUL SCRIPT ABILITY
- MICROCONT. ADAPTERS
- PLCC, MINI-DIP ADAPTERS
- SUPER FAST ALGORITHMS



OTHER PRODUCTS:

8088 SINGLE BOARD COMPUTER OEM \$27 ... *95
 PC FLASH/ROM DISKS (128K-16M) 21 75
 16 BIT 16 CHAN ADC-DAC CARD 55 195
 WATCHDOG (REBOOTS PC ON HANGUP) 27 95


*EVAL KITS INCLUDE MANUAL BRACKET AND SOFTWARE.
 5 YR LIMITED WARRANTY
 FREE SHIPPING
 HRS: MON-FRI 10AM-6PM EST

MVS MVS BOX 850
 MERRIMACK, NH
 (508) 792 9507

Motion Control System

\$249.95

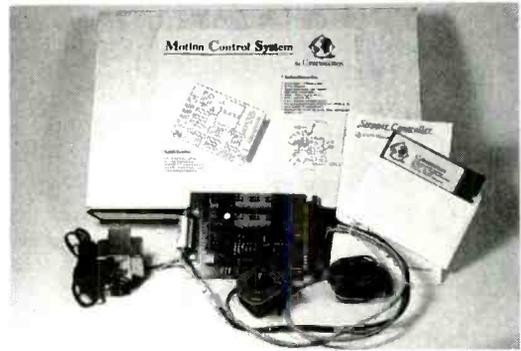Includes Stepper Controller Card, 12VCT Transformer, (2) 4 Phase Stepper Motors. Easy to use I.B.M Software! Connects to any I.B.M. Compatible LPT Port (1,2,3)...



* Nothing more to Buy!

- * Easy Installation 15 minutes or Less!
- * No Tools Required!
- * Design Robots, Plotters, Laser Systems!
- * Drives (2), 4 Phase Stepping Motors!
- * Bi-Directional 8 Bit Read and Write Port!
- * Board Addressable, 16 Possible Choices!
- * Fits in Standard 19" inch Card Rack!
- * With Additional Cards Control 32 Motors on 1 LPT Printer Port!
- * Features Include: Variable Speed, Step, Range, Direction, and On/Off Control!
- * Free QBasic & Gwbasic Source Code \$ 59.95 value! *

Send Check or M.O. to:

CYBERMATION

"Intelligent Controllers"

1943 Sunny Crest Dr., Suite 288,
 Fullerton, CA 92635

Call Us Today!
 Tel (714) 879-2000
 Visa/Master Charge Accepted

* Add \$12.00 S&H; CA residents please add sales tax *

CIRCLE 298 ON FREE INFORMATION CARD

Debco is a Kit Builders Paradise

Electronic Kits - Plans - Parts - Computers - Amateur Radio

Call Debco today for your FREE copy of The Electronic Experimenter's Journal

1 800 423 - 4499

Debco Electronics 4025 Edwards Rd. Cincinnati, OH 45209

CABLE TV EQUIPMENT

We carry a complete line of all major brands including test chips and all accessories

BELOW WHOLESALE PRICES • QUANTITY DISCOUNTS
 30 DAY MONEYBACK GUAR. • 1 YR. WARRANTY

YEARS OF CUSTOMER SATISFACTION
C & C ELECTRONICS

CALL NOW 1-800-995-1749

Immed. Delivery from Giant Stock! Sorry no Florida Sales

CAPACITOR CLOSE-OUT

SAVE 50% to 75% OFF RETAIL

TOP QUALITY PARTS! WHILE SUPPLIES LAST!
 CERAMIC DISC! ELECTROLYTIC! TANTALUM!
 AXIAL / RADIAL! PREFORMED / LONG LEAD!

0.01uF / 50Vdc Disc @ 7¢ each (That's 50% cheaper than most)
 2.2uF / 50Vdc Elec. Radial @ 8¢ each (That's 55% cheaper than most)
 Also, TO-220 Clip-on Heat Sinks @ 15¢ each (That's 60% cheaper than most)

Send SASA for Free catalog to:

JDG, Dept. E11, P.O. Box 20908, Raleigh, NC, 27619

!!! BROADCAST FARTHER !!!

The model 1525 is a 75-110MHz RF amplifier that connects to mono or stereo FM transmitters and produces a powerful 15-20 watt signal which could broadcast up to 5 miles or more! Requires 75-250 mW drive.

Step by step plans complete with part source information and antenna designs... ONLY \$14 PLUS \$2 S&H CATALOG INCLUDED

R Progressive Concepts
 1454 N. MILLS AVE., SUITE A
 CLAREMONT, CA 91711 (909) 626-4969

VISA

(909) 626-4FAX



EVERY LITTLE
 BIT
 HELPS
THE SALVATION ARMY

CABLE CONVERTERS/DESCRAMBLERS

★ ★ ★ ★ SUPER BUYS ★ ★ ★ ★
 ★ FULLY REFURBISHED UNITS ★

TOCOM — JERROLD — SCIENTIFIC ATLANTA — ZENITH — PIONEER

"WE SERVICE MOST CABLE CONVERTERS"

Phone (219) 935-4128



SORRY, NO INDIANA SALES

NATIONAL CABLE BROKERS

1801 W. JEFFERSON ST., PLYMOUTH, IN 46563

OUR POLICY: All products carry a two year warranty. Warranty covers parts and labor and return shipping.
 WARNING: Theft of cable services is a crime. National Cable will not knowingly defraud any pay TV operator and we will not assist any individual or company in doing the same.

Metric

Equipment Sales, Inc.

800-432-3424

Fax: 415-341-8874

E-mail: metricsale@aol.com




Refurbished Scopes, Analyzers, Generators, Counters
 from HP, Tektronix, Fluke, Anritsu and more.

Test & Measurement Instruments


Over 7000 Models • 6-Month Warranty • Save 30-90% • 5-Day Free Trial

Miniature Transmitters and Receivers

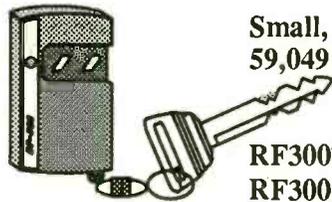


Small, Attractive, High End Quality, 2 Channel 318 MHz Transmitter
59,049 Settable Codes, 120'-300' Range, 1-1/4" x 2" x 9/16", Assembled

		Qty	1	5	10
RF300T	150' Range Transmitter		24.95	19.95	15.95
RF300XT	300' Range Transmitter		29.95	24.95	19.95

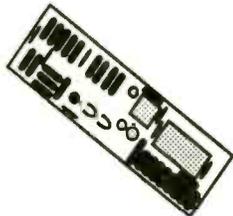

Small, High End Quality, 2 Channel Receiver for the RF300 Transmitters
1-1/4" x 3-3/4" x 9/16" PCB w/ .1" spaced pads for standard connectors
Input: 8-24 vdc Output: Gated CMOS Momentary and Latching Lines

		Qty	1	5	10
RF300R	Receiver, Fully Assembled		24.95	20.95	16.95
RF300RK	Receiver, Complete Parts Kit		19.95	15.95	12.95
RF300PA	Pre-Amplifier. Doubles Range		14.95	11.95	9.95

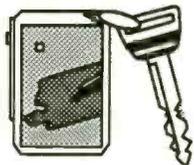

Small, Economical, Single Channel Transmitter and Receiver Set
Set Code, 60' Range, 1-7/8"x2-3/8"x7/16" (T), 2"x2-3/4"x9/16" (R)
Receiver Input: 5 vdc Output: Gated TTL Momentary Line


		Qty	1	5	10
RF60	Transmitter and Receiver Set		24.95	19.95	14.95

Add \$ 4 shipping for first item + \$ 1 for each additional item. Ca. residents add 8.25% tax
Visa, Mastercard, Money Orders Personal Checks and Cash C.O.D.s


Visitect Inc. P.O. Box 14156 Fremont, CA. 94539 (510) 651-1425 Fax (510) 651-8454

CIRCLE 321 ON FREE INFORMATION CARD

MEREDITH INSTRUMENTS

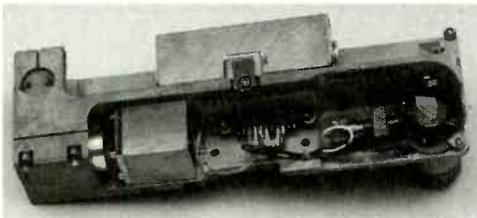


RUBY LASER ASSEMBLIES \$295.00

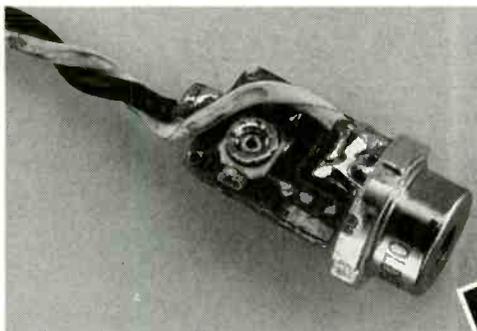


LASER DIODES

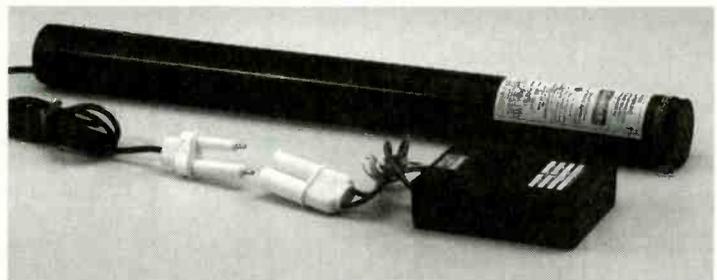New 670 nm 5 mW laser diodes **\$20.00**
New 635 nm 5 mW laser diodes **\$75.00**



GREEN-YELLOW OR ORANGE HE-NE LASER KIT

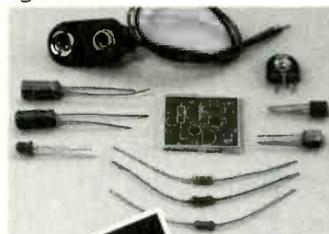We now offer alternative wavelength helium neon lab lasers from **\$195.00**. Add or mix these brilliant colors to your red light show!



LASER DIODE DRIVE CIRCUIT KIT

Its compact size, 19 x 25 mm, is about the smallest that can be made without the use of ICs or surface mount components.

\$15.00



FREE SHIPPING ON ORDERS OVER \$100.00

Call Or Write For A **FREE CATALOG** On LASERS & OPTICS

PHONE: (602) 934-9387
FAX: (602) 934-9482

5035 N. 55TH AVE., #5, P.O. BOX 1724,
GLENDALE, AZ 85301

CIRCLE 252 ON FREE INFORMATION CARD



New Jensen Catalog

- Hard-to-Find Tools, Tool Kits
- Scopes, Meters, Function Generators
- Computer Diagnostics
- Telcom/LAN Testers
- Workbench Accessories

Call for Free Copy



800-426-1194
JENSEN TOOLS INC.
 7815 S. 46th St., Phoenix, AZ 85044

CIRCLE 305 ON FREE INFORMATION CARD

MORE for LESS... Always!

Best Values for Performance, Features and Dependability

DM5050C, 42 Range DMM + CAPACITANCE METER

- Digital Multimeter
 - Resistance - Up to 2,000 MΩ
- Capacitance Meter, Extended Range
 - Up to 20,000μF (9 Range)
 - Zero Adjust Knob
 - Test Leads and Built-in Socket
 - Check Motor Starting & Running Capacitance
- Triggering Lamp

DM5100, 45 Range WIDE RANGE, ELEVEN FUNCTION

- Auto Power Off, Data & Peak Hold
- Measures Wider Range
 - Frequency - Up to 20 MHz
 - Capacitance - Up to 200 μF
 - Resistance - Up to 200 MΩ
 - Current - Up to 20 A AC/DC
- Logic - TTL
- TRhFE

- ± 0.25% Basic DCV Accuracy
- 1.5" Big LCD Display
- 3 1/2 Digit Manual AC/DC Volt & Amp Resistance, Diode Continuity Beeper
- Alligator Clip Test Leads
- Double Insulated Jack
- Deluxe Holster
 - Lead Holders
 - Velcro Hanger
 - Tilt Stand



\$89

- Prices start at \$44.95, measuring AC/DC 10 Amp. & Volt, Resistance, more and including protective Holster
- Lots more High Standard Test Instruments available
 All in One Instrument, Oscilloscope, Power Supply, Function Generator, Freq. Counter, Multimeter, Capacitance, Engine Analyzer, Clamp-On, Electrical Tester and More.
- See your local distributors or Call for Catalog

Bel MERIT
 SOLUTIONS FOR THE TEST INSTRUMENT

26242 Dimension Dr., Suite 110
 Lake Forest, CA 92630
 (714) 586-3700 • FAX: (714) 586-3399

CIRCLE 297 ON FREE INFORMATION CARD

Great books on
SCANNING and
MORE!!

CHEEK

The
Ultimate Scanner!

The King of Scanners takes this step-by-step, richly illustrated, bench manual beyond everything ever published on scanner mods. Bill is a perfectionist who will help you convert your scanner into precisely what you've always wanted! Finally available!!

new!

May 1995,
 244 pages, large format,
 \$29.95.

EMERGENCY RADIO!

Scanning News As It Happens
 Norm Schrein (*Mr. Scanner*)
 214 pages, \$14.95

"Excellent..." *Barry Goldwater*
 "Irresistible" *Bill Cheek*
 "A winner..." *911 Magazine*

SCANNERS & Secret Frequencies

Henry Eisenson
 320 pages, \$19.95

"Must reading."
Electronics Now
 "A giant undertaking"
Monitoring Times
 "You can't miss!" *ASG*
 "The best" *Norm Schrein*

Underground Database

More than 400 listings, 100 pages, large format, \$23.75
SCARY!

Everything that's sort of legal, unless you actually USE it.

1st book \$4 s/h, then \$2 ea.
 CA add 7.75% tax
 Order line 800-546-6707
 All credit cards

INDEX Publishing Group, Inc.
 3368 Governor Dr., Suite 273E
 San Diego, CA 92122

Earn \$4,000 Per Month From Your Home With A Computer!



CBSI 486 Computer Included
Begin part-time and still retain the security of your present position. This is a proven business an individual or couple can run. If you purchase our software and business program, you will receive the computer and printer at no extra cost. If you already own a computer, you may receive a discount. You do not need to own, or know how to run, a computer—we will provide free, home office training. Financing available. We accept AMEX, MC, Visa and Discover.


To receive free explanation cassettes and color literature, call:

1-800-343-8014, ext. 2271

Or Write:

Computer Business Services, Inc.
CBSI Plaza, Ste. 2271, Sheridan, IN 46069

The Pocket Programmer Only \$129.95

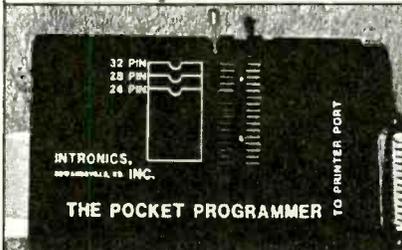

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs Eprom, EEprom, Flash & Dallas Ram. 27(C) / 28(C) / 28F / 29F / 29C & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, PLCC, 5-Gang, 874X, 875X MCU's, 40-Pin X 16 & Serial Eprom's, and Eprom Emulator to 32K X 8.

**Same Name, Address & Phone #
for 13 Years... Isn't it Amazing ?**

Intronics, Inc.


Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add \$4.75 COD
Tel. (913) 422-2094 Add \$4.00 Shipping

Fax (913) 441-1623 Visa / Master Charge

NEW TOOL

Hot-Aero
Miniature Heatgun
For Heat-Shrink Tubing

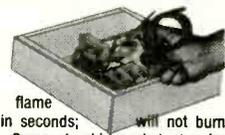For
Equipment Repairmen
Electronics Technicians
Hobbyists & Modelers



Uses most adjustable flame lighters • Shrinks tubing in seconds; will not burn tubing nor components • Compact, shirt-pocket size for toolboxes • Safety-valve mouthpiece • Simple & easy to use • Completely portable • No moving parts • Patented air-injector turbocharges the flame, producing a precise 1/2 inch diameter, super-hot air-stream and no carbon soot mess • Unbreakable & built to last a lifetime • Heats-up instantly & cools-down in seconds • Made with precision & top-quality materials; Hardened stainless steel, Heat-resistant nylon, Polyurethane recoil tubing • Professional • Rugged • Limited lifetime warranty • Satisfaction guaranteed

Limited Time, introductory Price \$14.95

If you solder wire connections together, you will love this tool! Now using heat-shrink tubing with the Hot-Aero is faster, easier and more convenient than tape or big, loud electric heatguns.

Send check/money-order (\$3.00 S/H) to: 

Rose Research & Development

P.O. Box 12212

Santa Rosa, CA 95406

1-800-606-9044

Free Color Brochure

SURVEILLANCE

The Latest High Tech Professional Electronic Devices

Our latest catalog offers a **HUGE** selection of surveillance, privacy devices including: hidden video equipment, electronic kits, telephone recording systems, touch tone decoders, scanners, telephone tap detectors, bug detectors, voice disguisers, telephone scramblers, locksmithing tools, and more. **Catalog \$5.00.**

SPY OUTLET

P.O. Box 337, Buffalo, NY 14226
(716) 691-3476 / (716) 695-8660

BEST DEALER PRICING!

CABLE DIRECT

CONVERTERS • FILTERS
DESCRAMBLERS

IMPROVE YOUR IMAGE WITH
VIDEO STABILIZERS



**100%
MONEY BACK
GUARANTEE!**

**30 DAY
FREE
TRIAL!**

FREE Cable TV Catalog.



Now you can tune-in your favorite cable TV programming and **SAVE \$100'S - EVEN \$1000'S** on premium **CABLE TV EQUIPMENT.**

MODERN ELECTRONICS

1-800-906-6664

2125 S. 156TH CIRCLE • OMAHA, NE 68130

BEST BY MAIL

Rates: Write National, Box 5, Sarasota, FL 34230

OF INTEREST TO ALL

EARN \$10,000.00 MONTHLY with your very own 900#. No investment. FREE details. Telcraf, P.O. Box 410-(ELE), Sugar Valley, GA 30746-0410.

HIGH SCHOOL DIPLOMA At Home, Accredited, Fast, "Failure-Proof" 1-800-470-4723, American Academy, 12651 S. Dixie Highway, Miami, FL 33156.

101 QUESTIONS AND Shocking Answers About AIDS. Only \$5.00. MINORITIES ARE PEOPLE, INC., PO Box 1333-(ELE), New York, NY 10116.

EARN EXTRA INCOME or Financial Security in just an Hour a Day! \$7.00: B&B Innovations, Box 2897-(ELE), Lake Placid, FL 33862.

PROGRAMMERS

1349 DATA I/O CHIPLABS 4800

799 DATA I/O CHIPLABS 3200

579 EETOOLS ALLMAX

249 XELTEK SUPERPRO (R)

599 LOGICAL DEVICES 3000

599 ADVANTECH PC-UPROG

269 SUNSHINE UNIVERSAL

449 TUP-300 HILO SYSTEMS

449 JDR MCT-EMUP

539 TUP-400 HILO

429 NEEDHAMS EMP-20

679 NEEDHAMS SA-20

139 EETOOLS 1 GANG

199 EETOOLS 4 GANG

49 SUNSHINE 1 GANG


99 SUNSHINE 4 GANG

169 SUNSHINE 8 GANG

349 SUNSHINE 16 GANG

GENERAL DEVICE INSTRUMENTS

(408) 241-7376 Fax 241-6375 BBS 983-1234

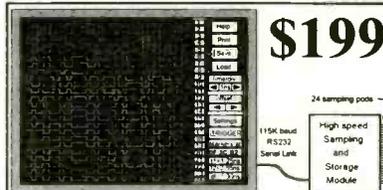

\$199

24 CHANNEL LOGIC ANALYZER

50 MHz sampling speed
Expandable to 192 channels
VGA graphics PC based interface
115K baud RS232 link to host
External clock feature
Programmable trigger
Up to 32K samples per channel
Fully assembled and tested
ONE YEAR WARRANTY

Get this powerful new tool at this incredibly low price!
We accept Visa, MasterCard and COD orders.

ProBoard Circuits

Phone: (409)762-5436 Fax (409)762-4167
100 Market street, Suite 16 Galveston, Texas 77550

CABLE TV

ALL NAME BRANDS
DESCRAMBLERS, CONVERTERS
COMBOS. CALL NOW

WE'LL BEAT THE COMPETITION.

UNIVERSAL SALES 800-647-2371

NEW EASY PC

BRITISH
DESIGN
AWARD

SCHEMATIC and PCB C.A.D

ONLY **\$195**

Includes


• MGA, CGA, EGA & VGA compatible.

• Design large multi layer boards.

• One level pull down menu and quick keys for fast layout.

• Dot matrix, laser, plotter, Gerber & N.C. drill output.

• 6 Month Free update
Free Demo

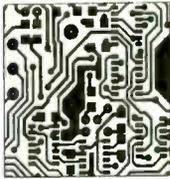


7840 ANGEL RIDGE ROAD
ATHENS, OHIO 45701
(614) 592-1810

Visa & MasterCard Accepted


BLACK FEATHER ELECTRONICS

3 1/2 Digit LCD Panel Meter

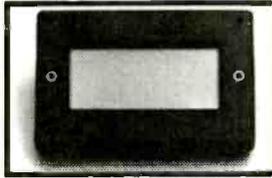

Features: 200mV full scale input 9VDC operation. Decimal point selectable. 13mm digit height, auto polarity indication, zero reading for 0 volt input. Measures 2.67" x 1.73" x 0.28" above panel thickness, 0.57" overall thickness. LCD size: 1.83" x 0.8". Has many useful applications and is easy to install.
CAT# PM-1 **\$17.00 each**

Stepper Motor Controller Kit

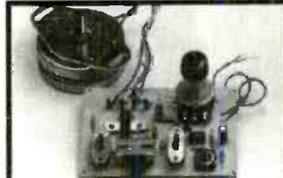

This kit allows you to adjust the speed and direction of a stepper motor. You can move the motor in one step increments or rotate it at a constant speed. Visual indicators show the sequence of motion. Includes stepper motor, pc board, parts and instructions. (12vdc power source not included.)
CAT# SMK-1 **\$25.00 each**

Camcorder Video Tape



HI-8 120 MINUTE TAPE (used)

They were recorded on once and played only a few times. Made by a major brand name manufacturer. Professional series metal topes. Includes plastic jewel box.

CAT# CCT-1

\$3.00 each

10 or more - 2.80 each

1-800-526-3717

645 Temple 7B ▲ Long Beach ▲ California 90814
(310) 434-5641 ▲ FAX (310) 434-9142 ▲

1. California residents must include sales tax.
2. Checks and money order accepted.
3. Quantities limited - prices subject to change.



Invest a stamp



Save a bundle

For the price of a stamp, you can get the latest edition of the federal government's free Consumer Information Catalog listing more than 200 free or low-cost government publications on topics such as federal benefits, jobs, health, housing, education, cars, and much more. Our booklets will help you save money, make money, and spend it a little more wisely.

So stamp out ignorance, and write today for the latest free Catalog. Send your name and address to:

Consumer Information Center
Department SB
Pueblo, Colorado 81009

Is your Cable Company Alienating You?



Say **NO** to unearthly rental fees!

Owning your cable equipment saves you the high cost of monthly equipment rental charges, and gives you control of your TV.


We have the *Best* in

CONVERTERS and DESCRAMBLERS!

Everquest • Panasonic • Jerrold • Zenith • Pioneer
Scientific Atlanta • Oak • Eagle • Hamlin • Tocom

1 800 624-1150

FREE Catalog!

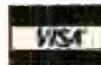

MD Electronics

P.O. Box 241296 • Omaha, NE 68124

© JERROLD, STARCOM, PANASONIC, ZENITH, PIONEER, OAK, SCIENTIFIC ATLANTA, EAGLE, HAMLIN, and TOCOM are all registered trademarks. All references to the above mentioned equipment is for identification purposes only. We are in no way implying that any of the products in this advertisement are original equipment. M.D. Electronics is in no way affiliated with the above mentioned companies or corporations.

SHOW TIME CABLE

Your Cable Connection To The Stars!

Order your **FREE**
catalog today!
1-800-643-4258



STARGATE SST

- Converters & Descramblers
- All Makes & Models
- Quantity Discounts
- 30-day Money Back Guarantee
- Best Warranties

Show Time Cable
643 N 98th St STE 260
Omaha, NE 68114

COD • MasterCard • Visa
Amex • Discover

BOOM MIKE

Electret condenser type. This versatile microphone may be wired for handy-talkie, sound card, telephone, base station, aircraft radio, CB radio, motorcycle intercom, etc. An earphone or miniature speaker may be installed in either or both muffs. The microphone unit can be easily removed and installed on another headset or helmet.

92A001 **\$4.95 each**

MINIATURE SPEAKER



Great for use in Boom Mike (92A001). Only 0.9" dia. by 0.2" thick. 40 Ohm coil, rated at 20 mW has 6" wire leads.

92A007 **\$1.49 each**


Send **\$2.00** for Our Latest Catalog!
\$4.00 Foreign. Refundable on First Order.

ALLTRONICS

2300-D Zanker Road • San Jose, CA 95131
Voice (408) 943-9773 • Fax (408) 943-9776
Catalog by E-Mail: info@alltronics.com
On-Line Ordering: (408) 943-0622

030196

14400-N-8-1-24 Hrs.

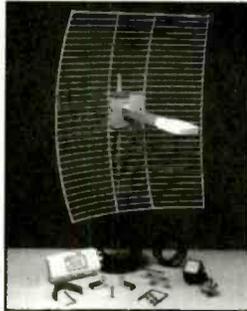

CHALLENGER SYSTEM
33-Channel 52dB+ Gain
Complete Grid \$265
Five Year Warranty
FREE SHIPPING

Quality Microwave TV Systems

**WIRELESS CABLE • ITFS • MMDS
ATV • INTERNATIONAL • S-BAND**
Amplifiers • Antennas • Books • Components
Filters • Systems • Video Products

- RF Frequency 1990 - 2700 MHz
- Cable Ready - VHF - UHF Outputs
- SASE For "FREE" Catalog or Send \$1

PHILLIPS-TECH ELECTRONICS

PO Box 8533 • Scottsdale, AZ 85252

ORDER LINE 800-880-MMDS

CATALOG / INFO 602-947-7700

FAX LINE 602-947-7799

Visa • M/C • Amx • Disc • COD's • Qty Pricing

CIRCLE 327 ON FREE INFORMATION CARD



Finally, a low cost way of getting into the monitor repair business. With the Checker 12 you can test and repair computer monitors with speed and accuracy. The "Checker 12" is an **easy to operate**, hand held, battery, or AC operated computer color monitor pattern generator. With its support of CGA(15.75khz), EGA(22khz), MACII(35khz), and VGA modes 1,2,3 (31.5khz), 800X600(35khz), **1024X768 interlaced** (35khz), **1024X768 non-interlaced**, & **1024X768NI with sync on Green** (48khz), you can easily checkout a monitor in all of its' modes. With its' single mode switch, you know exactly what type of monitor you are testing. You don't have to be a monitor expert to use the Checker 12. Its' front panel color pictures, show just what you should be seeing on the monitor under test. You can quickly tell if the monitor is a VGA, SVGA, or a SVGA/NI. No more guessing. The "Checker 12" provides various test patterns for VGA monitors. X-hatch, for size and linearity and convergence set-up. White screen, for purity and CRT burn evaluation. Color bars and **8 step gray scale** for color tracking and balance. There is also a single color mode that allows for single color channel operation. There is no easier way to test and evaluate monitors than with the Checker 12.

Price: \$295.00 + \$5.00 S&H.

Includes battery, AC adapter, Mac adapter and 120 day warranty

We also have the Checker VI, a six port *stand-alone* VGA (640x480) test pattern generator, **NO computer required**. Just \$249.95.



CMIMI



Computer & Monitor Maintenance

6649 Peachtree Ind., Blvd., Suite N-1 • Norcross GA 30092
1-800-466-4411, 770-662-5633 (Voice), 770-840-8814 (Fax)

CIRCLE 331 ON FREE INFORMATION CARD

"NOW BUYING"
\$\$ BEST PRICES \$\$
AVAILABLE

SCIENTIFIC
ATLANTA
 8536 THRU 8600

PIONEER
 5135 THRU 6300

ZENITH
 1086THRU 1612

JERROLD
 DPV5
 DPBB212
 THRU
 DPV7
 DPBB7

TOCOM
 5503A
 VIP THRU 5507

Midwest's Largest Brokers
(We buy quantities of one to one thousand units)

NATIONAL CABLE BROKERS
(219) 935-4128

16 Bit Control

& Data Acquisition System



from
\$299

DSP

Powerful,
 Easy to use,

Tons of Memory,
 I/O & features:

16.8MHz 68HC16
 RS-232 & RS-485
 RT clock option

34 digital I/Os (7 IRQ)
 + LCD/Keypad port
 + 8 ch 10b fast A/D

Affordable "C" compiler/library
 Multi-tasking kernel
 Up to 256K ea. SRAM, FLASH memory

INTEC INOVENTURES INC.

Ph: (604) 721-5150 FAX: 721-4191

BCD
 electro

**We'll Buy your
 excess inventory**

IC's, Transistors, Diodes,
 capacitors, trimpots, etc. etc.

•Purchase outright

•Consignment

•Partnering agreements

Send your excess list

for a quick offer!

Contact Bob Harris

Phone (214) 343-2170, FAX 1854

email - bcdelect@onramp.net

web - <http://www.bcdelectro.com/bcd>

PRINTED CIRCUIT BOARDS

**LEAD TIME PROBLEMS?
 CALL THE PROFESSIONALS**

- Single Sided
- Double Sided PTH
- Solder Mask
- Component Screen
- Prototyping
- High Production

★ **AMERICAN OWNED
 AND OPERATED** ★

Making PC Boards Since 1966

CALL OR FAX FOR PRICING

K & K ELECTRONICS

170 E. Market St.

Alliance, Ohio 44601

216-821-6478 FAX 216-821-6380

**PEOPLE WHO NEED PEEPHOLES :
 A BIGGER AND BETTER PICTURE**



Surveillance security scope
 2 in. TV screen view
 specify black or white



\$39.95, \$2.00 shipping
 please allow 2 weeks for delivery
 checks payable to: MJD
 PO Box 3260 Idyllwild, CA 92549
 (213) 656-7209

DISTRIBUTORS AND WHOLESALEERS WELCOME!

SAT COM TEST BRDS

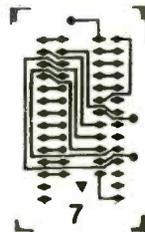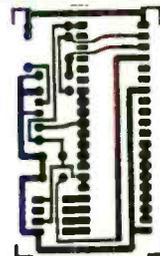

PIO TEST

SC-7

50 - \$2.35 Ea. 50 - \$2.00 Ea.
 100 - \$2.00 Ea. 100 - \$1.50 Ea.
 500 - \$1.18 Ea. 500 - \$.95 Ea.

Send Cert. Check or Money Order to:

K&K Electronics

P.O. Box 2597, Alliance, Ohio 44601

Or Call: **216-821-6478**

Many happy returns.



Give the gift that gives back more than you've given. For as little as \$25, you can give a piece of America to someone you care about. Ask your banker for a gift certificate upon purchase.

Take Stock in America **U.S. SAVINGS BONDS**

A public service of this magazine

Where would Hansel
 and Gretel be without
 a forest?

Only You Can Prevent Forest Fires.



USDA Forest Service and your State Forester.

Free Best Seller! Write:
 Consumer Information Catalog
 Dept. BEST, Pueblo, CO 81009

HOME AUTOMATION

Largest Selection of HOME AUTOMATION products in the World!

Browse us on the WEB!

<http://www.techmall.com/smarthome>

Hundreds of hard-to-find automation, X10, and wireless control products. Computer control of your home, security systems, surveillance cameras, infra red audio/video control, HVAC, pet care automation, wiring supplies, and much more!

HOME AUTOMATION SYSTEMS, INC.

151 Kalmus Drive, Ste L4, Costa Mesa, CA 92626
Questions 714-708-0610 FAX 714-708-0614

800-SMART-HOME

800-762-7846


HOME AUTOMATION SYSTEMS, INC.



FREE

Call 24hrs for FREE
64 page Color Catalog **Over 500**
unique products!

FM STEREO ANTENNA

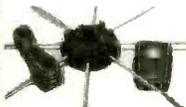

Rembrandt Model 5000, omni-directional 8-element antenna is electronically rotated with remote control unit. 20"L elements; 47" dia assembled. Fits 1.25" dia mast. Includes 50 ft. 4-cond wire & control; 7 lbs. sh.

NEW \$25.00

SOUND-POWERED FIELD PHONE

TA-1 TELEPHONE requires 2-conductor wire connected to another TA-1 for voice communications without batteries. Palm-operated generator "buzz" signals other phone; with plastic case. Useful where radio communications is not practical. 8.5x3.5x3.5, 4 lbs.

USED-CHECKED \$35.00 each; 2 for \$60.00

TA-312 FIELD PHONE, requires two D-batteries (not sound-powered); replaces old EE-8 phones. With canvas case; 12x7x4, 12 lbs. sh.

USED-CHECKED \$65.00



COLLINS S-LINE RADIO



Military-surplus "winged" emblem HF Ham-band equipment; 45 lbs. each. **USED-REPARABLE** (not "mint" condition): **KWM-2A TRANSCEIVER** \$425

With PM-2 supply \$495

30L1 POWER AMPLIFIER with 811A's \$550

516F2 AC SUPPLY for KWM-2A/30L1 \$135

312B4 CONTROL-SPEAKER w/directional coupler \$150

28 VDC 50 AMP SUPPLY

PP-4763A/GRC power supply produces 28 VDC 50 amps from 115/230 VAC 22/11 amp 47-63 Hz input; +/-0.5% regulation. Has meters 0-50 VDC and 0-80 amps DC; 13.5x19.5x15, 145 lbs. (Shipped UPS) **USED** ...\$195.00



JAN-BOXED ELECTRON TUBES

6B4G TRIODE, Sylvania; GA-glass + cathode version of old 6B4G. Does not test like 6B4G in tube checker but performance comparable in most circuits \$17.50

2A3 Penta-USA (but looks Chinese-made) \$14.00

2K25 X-band Klystron, Raytheon blue \$40.00

3BP1 CRT \$15.00, 2/\$25.00 **4D32 Raytheon** \$35.00

4CX300A Eimac \$85.00 **5R4WGB Cetron** \$3.50

1625 NU \$4.50 **5751 ECG-Phil** \$4.00

5998A GE \$9.95 **6146W GE** \$19.95 ea; 10/\$175

Prices F.O.B. Lima, O. • **VISA, MASTERCARD, DISCOVER**

Allow for Shipping • Write for latest Catalog

Address Dept. ES • Phone 419/227-6573 • Fax 419/227-1313

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802




DIGITAL STORAGE

OSCILLOSCOPE

WITH SPECTRUM ANALYZER, DVM, FREQ. COUNTER, AND DATA LOGGER.

\$189.

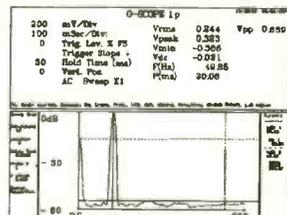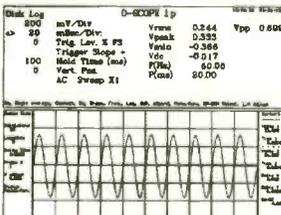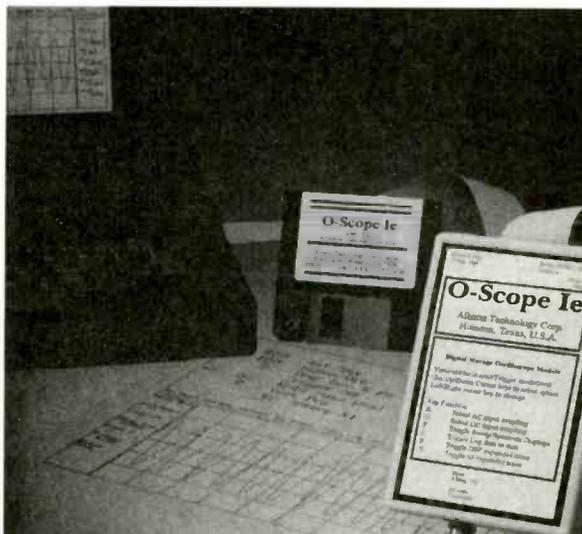O-SCOPE MODULES CONVERT PC'S INTO MULTIPURPOSE TEST AND MEASURING INSTRUMENTS.



FEATURES:

- SMALL & PORTABLE
- USES PRINTER PORT
- USES STD. PROBES
- DC TO 50 KHz
- 10v/div. TO 50 mv/div.
- MADE IN U.S.A.
- SAME DAY SHIPPING

OPTIONS:

- PROBE SETS
- EXTERNAL TRIGGER
- DUAL TRACE
- X-Y PHASE DISPLAY
- EXTENDED BANDWIDTH
- EXTENDED INPUT RANGE
- BATTERY PACK

INCLUDES SOFTWARE & INSTRUCTIONS.

ASSEMBLED AND TESTED..... \$169.

ENHANCED SOFTWARE..... \$ 20.

KIT (WITHOUT CASE)..... \$129.

SHIPPING: \$7.50 (2ND DAY \$11.50)

TO ORDER: SEND CREDIT CARD INFO., M.O., or CHECK, OR YOU MAY CALL 1-800-980-9806

ALLISON TECHNOLOGY CORPORATION

8343 CARVEL, HOUSTON, TX. 77036 U.S.A.
PHONE: 1-713-777-0401 FAX: 1-713-777-4746
BBS: 1-713-777-4753

CIRCLE 283 ON FREE INFORMATION CARD

ATTENTION DEALERS

BUY DIRECT FROM
THE WHOLESALER

GET THE BEST PRICES AND SERVICE

ALL UNITS ARE IN STOCK FOR IMMEDIATE SHIPMENT

DECODERS

	QTY 10	QTY 20	QTY 50+
STEALTH-1000-P.....	\$48	\$45	CALL
TVT-3 GOLD.....	\$41	\$38	CALL
TNT-3.....	\$45	\$42	CALL
STEALTH 80-P.....	\$54	\$49	CALL
M-80.....	\$64	\$58	CALL
PIO+.....	\$68	\$58	CALL

NOVAVISIONS

	QTY 10	QTY 20	QTY 50+
NV-5600.....	\$249	\$239	CALL
NV-5700.....	\$229	\$219	CALL
NV-5800.....	\$229	\$219	CALL
NV-5750.....	\$319	\$299	CALL

NEW CONVERTERS

	QTY 10	QTY 20	QTY 50+
CENTURY CT-3000.....	\$64	\$60	CALL
SA-8511.....	\$75	\$65	CALL

BOSS COMBOS

	QTY 10	QTY 20	QTY 50+
BOSS 1.....	\$225	\$205	CALL
BOSS 2.....	\$235	\$215	CALL
BOSS 3.....	\$245	\$225	CALL

REFURBISHED CONVERTERS

REGAL • SA • PANASONIC

CALL FOR THIS MONTH'S SPECIALS

1-800-808-3356

DIRECT CABLE SUPPLY

Rt. 6 Plaza Mall #290, Honesdale, PA 18341. 30 day money back guarantee. All shipping and handling at customers expense. Anyone implying theft of cable service will be denied sale. NO PA SALES.

DCS-1

New!

Pocket Cube™ with Filter

Wireless cable box tester for authorized cable technicians.

Smallest cube on the market just under 1" x 2"!

Simply clip it onto a 9V battery for 10sec!

Works on J***** models D*5,D*V5,D*7,D*V7,D*BB,C*T.

Only \$69.⁹⁵!

(plus \$8 S&H)

30 Day Warranty!

Quantity discounts available.

Dealers Welcome!

Test chips available for J***** and SA8600.

Order Toll Free

1-800-417-6689

Mon-Fri, 9AM-10PM EST.

If busy please keep trying.

VISA, MC, MO & COD

IEC, P O Box 52347, Knoxville, TN 37950-2347

Pocket Cube is a test generator ONLY.

Do not use these devices without authorization from your local cable company.

No TN sales.

Pocket PIC Programmer \$34.95

Bare board w/ disk



\$59.95

Assembled and tested

- ❖ For PIC16C61, 62x, 71, and 84
- ❖ 40/28 Pin ZIF Adapter for PIC 16C64, 65, 73, and 74 - \$29.95
- ❖ In-Circuit Adapter - \$49.95
- ❖ Runs off 2 - 9 volt batteries or optional AC adapter - \$9.95
- ❖ Includes Assembler
- ❖ PICProto boards - \$9.95-\$17.95

microEngineering Labs

Box 7532 Colorado Springs CO 80933

(719) 520-5323 FAX 520-1867



Surface Mount Chip Component Prototyping Kits—

Only

\$49.95



CC-1 Capacitor Kit contains 365 pieces, 5 ea. of every 10% value from 1p1 to .33µf. CR-1 Resistor Kit contains 1540 pieces; 10 ea. of every 5% value from 10Ω to 10 megΩ. Sizes are 0805 and 1206. Each kit is ONLY \$49.95 and available for Immediate One Day Delivery!

Order by toll-free phone, FAX, or mail. We accept VISA, MC, COD, or Pre-paid orders. Company PO's accepted with approved credit. Call for free detailed brochure.

COMMUNICATIONS SPECIALISTS, INC.
426 West Taft Ave. • Orange, CA 92665-4296
Local (714) 998-3021 • FAX (714) 974-3420

Entire USA 1-800-854-0547

BUGGED??

EAVESDROPPING is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations RIGHT NOW! Are you sure you're safe? **FREE CATALOG** tells you fast! Includes Free Bonus details on far. Exciting, immensely interesting and EXTREMELY profitable (up to \$250/hr) full/part-time income. Call Now! **1-800-732-5000**

SURVEILLANCE

FM TRANSMITTERS MINI (KITS)

- 3-VOLT FM XMTR, up to 300 ft. indoors, 1500 ft. outdoors
- PHONE XMTR, range to 500 ft., uses phone-line power
- Sound-Activated XMTR, range to 500 ft.
- 2-STAGE XMTR, 9-Volt, very powerful

All above require simple soldering at 2 to 4 places. **\$29.95** ea.**

TELE FM WIRELESS MONITORING SYSTEM. (Kit) **\$99.00***

TELE CALL FORWARDER. Transfers incoming calls. **\$99.00***

CALLER ID. Registers incoming number. **\$99.00***

TEL REGISTER WITH PRINTER. Records dialed number, duration, and prints record. **\$139.00***

12-HOUR LONG-PLAY RECORDER. Modified Panasonic. Records 6 hrs. on each side of 120 tape (supplied). Compatible with VOX and Tel Rec Adapter. **\$119.00***

VOX VOICE-ACTIVATED SWITCH. Makes recorder self-activating with voices or other sounds. **\$28.50****

TELE RECORDING ADAPTER. Records incoming and outgoing calls. **\$28.50****

TELEPHONE SCRAMBLERS. Over 4,000 separate codes. **\$199.00***

VOICE CHANGER. Changes man's voice to lady's and vice versa. **\$49.00***

For Shipping & Handling add \$*5.00 and **\$2.00 per item. Colo. residents add sales tax. Mail Order, VISA, M/C, COD's o.k. Inquire for dealer prices. Free catalog.

MUCH, MUCH MORE — OUR 25TH YEAR!
TOLL FREE 1-800-926-2488

A.M.C. SALES, INC.

193 Vaquero Dr., Boulder, CO 80303

Tel: (303) 499-5405, Fax: (303) 494-4924

Mon.-Fri. 8 a.m.-5 p.m. Mtn. Time

CIRCLE 284 ON FREE INFORMATION CARD

Cable Aids Test

Orders Only 1-800-615-9221 Aids Information 407-998-7883

Test Chips that fully activate Jerrold, Tocom, Zenith, SA, Pioneer and more. Quick-Board installation! Prices from \$5 to \$49.95 ea. MC SPECIALTIES 1 Year Warranty! No FL Sales. Not for use in cable co. owned equip. For test or repair only.

VIDEO SYNC GENERATOR



Restores Horizontal and Vertical Sync Lines from Distorted Analogue Video Formats

For Free Information Package on Completed Units and Pricing

• Call Toll Free •
1-800-236-5778

R.C. Distributing • PO Box 552 • South Bend, IN 46624

SPECTRUM PROBE®

This low circuit loading scope probe produces a 60 dB spectrum analyzer display on your inexpensive scope

EMC RFI
Ask for application notes, specifications, sales & warranty info.
255 Spectrum Probe 30 KHz to 2.5 MHz \$279
107 Probe 1 - 100 MHz \$249 (\$279 extra shielding)
Accessory Current Adapters: IAS \$19 IAT \$29

SMITH DESIGN (215) 661-9107
207 E. Prospect Ave., N. Wales, PA 19454

Prototype it..... FAST!

Run ProtoQuick 8051 or 28

- Complete single board computers
- Up to 328 EPROMs and 8K RAM
- 12 sq. in. drilled through proto area
- RS232C serial port w/ 0025 connector
- Dip. sys. in EPROM w/ source code
- Assembled, ready to run - 5¢ only
- IAS-3025 serial assembler included

ProtoQuick 28 and 8051

\$99.00 each

Run prototype applications or experimental hardware from the serial port - WITHOUT PROGRAMMING!

Software Science 3798 Roundabout Road Cincinnati, OH 45244 (513) 561-2060

Communications Systems Laboratories 1-800-529-9483

Hobbyists: Embedded Control Systems for home Automation. **MMCS-10** Cross Point 8x8 Video/Stereo-Audio electronic patch panel \$695.00. **TL-100** Color Organ Kit \$195.00. **T-10** DTMF Gen/Detector \$225.00.

Cable TV: Use our product line to automate your operations on a modest Budget. **VCS-26** Commercial inserter/billing logger - \$1595.00. **VCS-76** Channel Controller-4VCRs, 2 Laser Discs, 2 external sources, Two independent outputs \$2995.00. **MMCS-11** Wide-band Video/Stereo Audio 8x8 CrossPoint Switch, Computer Controllable \$895.00.

Call Toll Free for Info/Catalog or to Order. MasterCard VISA. Fax 1-808-625-7035. 1yr warranty on all products.

Cable TV Descramblers Converters * Filters * Accessories

30 day Free Trial - NO RISK!
Unbeatable wholesale prices!
Affordable extended warranty
1 Year Warranty on all products
Call the cable professionals!



Credit Cards Welcome!
1-800-379-3976

Prices starting as low as \$99!
Orion Electronics

SHOPPER CLASSIFIED

CABLE TV

CABLE-Safe Guarantee cable privacy. The one-way valve for your cable TV signal. Cable signals come in, but they don't go out! \$29.95 + \$3 S&H. VISA/MC. **ELECTROMAN**, Box 24474, New Orleans, LA 70184.

ATTN, cable box owners. Order your ID signal and bullet stopper before it's too late. Send \$20.50 to **R.R. ENTERPRISE**, Box 3532, Easton, PA 18043.

"DESCRAMBLER Schematics Revealed" A powerful guide to descrambling schemes. \$10. VISA/MC. **ELECTROMAN**, Box 24474, New Orleans, LA 71084. (504) 482-3017.

SECRET Cable Descramblers Build your own descrambler for **Less than \$12.00 in seven easy steps!** Radio Shack parts list and **Free** descrambling methods that **cost nothing to try, included.** Send \$10.00 to: **INFORMATION FACTORY**, PO Box 669, Seabrook, TX 77586. For VISA/MC, COD's, (713) 922-3512 Anytime!

UNIVERSAL Descrambler Unscramble signals using your VCR as the tuner. Works with virtually any system, this is the only one you need. Declare cable box independence! \$129.95 + S&H. VISA/MC. **ELECTROMAN**, Box 24474, New Orleans, LA 70184.

DESCRAMBLE Cable with simple circuit added to Radio Shack RF modulator and using VCR as tuner. Instructions \$10.00. **TELECOM**, Box 832 E1, Brusly, LA 70719.

"BULLET Buster" Protect your cable box against the infamous cable "bullet." The "Bullet" Buster acts as an electronic shield. Installs in-line in seconds. Don't wait until it's too late! \$19.95 + \$3 S&H. VISA/MC. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

CABLE Descrambling New secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics for SSAVI, Gated Sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95 + \$2 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

CABLE TV descrambler! Anybody can build with seven parts from Radio Shack. Plans \$8.00. **1 (800) 818-9103.**

DESCRAMBLE All channels by "tricking" your cable box! Complete, easy to follow instructions! Send \$9.95. **INTERPOL**, PO Box 433, Valrico, FL 33594.

CABLE TV Equipment & Accessories Wholesalers welcome! 30 day moneyback guarantee! **Free catalog!** **PERFORMANCE ELECTRONICS INC.**, 1 (800) 800-815-1512.

CABLE Unscrambled Everything you want to know about cable, but are afraid to ask. \$10. VISA/MC. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

TOP Secret. Never released before. Cable companies, cellular phone companies, want to get you now! Learn how they do that! Protect yourself. Privacy, the laws. Better safe than sorry. \$53.95. **RANDALL**, Box 2168 R, Van Nuys, CA 91404.

CABLE descrambler! Build with 7 Radio Shack parts costing \$12. Instructions. \$8. **F.A.S.T.**, Box 369-E1, Pt. Salerno, FL 34992-0369.

CABLE TV TURN-ON CHIPS

SUPER Cable TV "Test Chips". Provides full service activation. Excellent; instructions & illustrations. **Jerrold Starcom**: DP(V)5, DP(V)7, DPBB7, CFT-2000 series. **Pioneer**: BA-5000 thru BA-6700. **Scientific Atlanta**: 8500 thru 8600. **Tocom**: 5503-VIP, 5507. **Zenith**: ST-1000 thru ST-5000. **Call now!! MASTER COMPONENTS**. **1 (800) 233-0570.**

PLANS-KITS-SCHEMATICS

CRYSTAL set Handbook — Visit antiquity by building the radios your grandfather built. Assemble a "Quaker Oats" rig, wind coils that work and make it look like the 1920s! Only \$10.95 plus \$4.00 for shipping and handling. **CLAGGK INC.**, PO Box 4099, Farmingdale, NY 11735. US funds only! USA and Canada — no foreign orders.

ALL-in-one catalog. AM/FM/ham/spy, transmitters, amplifiers, receivers. Voice scramblers/disguisers, audio, TV, Tesla coils, plans, "secret" books, kits, imports, exports and more. Start your own licensed or unlicensed radio station, 60 full pages for \$1.00. **PAN-COM INTERNATIONAL**, PO Box 130-F01, Paradise, CA 95967.

FIBER Optic educational experiments kit includes: tutorial, w/experiments, 40ft. fiber assortment. Cutting tool. \$19.95 + S/H (609) 468-1660.

FREE catalog. Nearly 100 leading-edge kits. KI, PIC. Full instructions, source code SASE. **SCIENCE FIRST**, 95 Botsford Place, Buffalo, NY 14216.

RESTRICTED Top secret hacker information. Cellular/cable surveillance/satellite/software. Make \$100/hour. Catalog — \$3.00. **TELECODE**, PO Box 6426-EN, Yuma, AZ 85366-6426.

UNIVERSAL remote control systems Infrared, RF, miniature transmitters, receivers. Items for novice, technician or educator. Combine your home and vehicle control. Automate anything. **FREE catalog.** **INVENTIVE SOLUTIONS**, PO Box 8, Stratford, NY 13470.

CREDIT Card Secrets Backup your credit cards in PC using system that works. Info \$5 or get a copy of "Theory of Encoding/Decoding in credit cards" for \$29. This document contains everything one may want to know. **CPU ADVANCE**, Box 2434, Harwood Station, Littleton, MA 01460.

ALL schematics, TV's, VCR's, camcorders, audio, fax, monitors, computers, printers, originals, up to date, hard to find from Aiwa to Zenit. \$5.00 and up. **(305) 434-9780.**

FASCINATING electronic devices! Tazer! Dazer! Super Spy microphone! Vocal truth detector! Universal IC tester! Radar and laser jammers! Surveillance! Countermeasures! Ultrasonic! Tesla! High voltage! More! Plans and kits catalog \$2.00. **QUANTUM RESEARCH**, 17919-77th Avenue, Edmonton, Alberta, T5T 2S1.

CIRCUITS! CIRCUITS! The very best in plans, kits, schematics, and books. Too many to list. Satisfaction guaranteed! Send for free listing. **HOBBYTECH**, Dept. EN1, 1748 SE Alder, Hillsboro, OR 97123.

ELECTRO RHEOLOGY Experiment with fluids that harden with applied voltage. Complete plans \$5.00. **WILLIAM ROSS**, Box 26021, Windsor, ON, Canada N9A-7E9.

RADAR JAMMER Complete with schematics, parts list, board layout with artwork, instructions. \$12.95 + \$3.00 S&H. **ARISTOCRAT ENTERPRISE**, 6709 West 119th Street, Suite 503, Overland Park, Kansas 66209. Money back guarantee.

COMPUTER SOFTWARE

HUBBLE Telescope photographs (GIFS)—galaxies in the young universe series, \$9.99 + \$2 shipping. Entire public Hubble Series available. **SPACEPICS**, POB 75711, Oklahoma City, OK 73147.

SECURITY

SECURITY alarm equipment. Do it yourself and save. Cameras, controls, motions, sirens, batteries, switches more. **1 (800) 335-2296** Fax (519) 541-1277.

CABLE TV DESCRAMBLERS



We Carry A Full Line Of Premium Converters And Descramblers Compatible With:

- Scientific Atlanta™ Systems
- Jerrold™ Systems
- Tocom™ Systems
- Zenith™ Systems
- Pioneer™ Systems

SATISFACTION GUARANTEED OR YOUR MONEY BACK!

BEST PRICES FREE CATALOG


Please have the MAKE & MODEL # of your full premium service cable box ready when you call!

ALLSTAR ELECTRONICS

800-782-7214

HOURS: 9-6 M-F 10-3 Sat EST

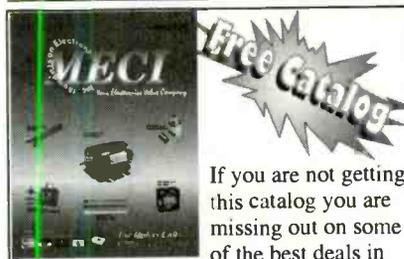It is not the intent of Allstar Electronics to defraud any pay TV operator. Anyone implying theft of service will be denied assistance. All brand names are registered trademarks of their respective owners & are used for reference only. 110-64 Quisena Blvd., 6445, Forest Hills, NY 11375. NO NYS SALES!



If you are not getting this catalog you are missing out on some of the best deals in

electronics today! We have thousands of items ranging from unique, hard-to-find parts to standard production components. Call, write, or fax today to start your free subscription to the most unique catalog in the industry, filled with super values on surplus electronic and hobbyist type items. If you have a friend who would like to receive our catalog, send us their name and address and we will gladly forward them a complementary 100 page catalog.

Why pay more? Call today.



340 East First Street Fax Order Line
Dayton, Ohio 45404 1-800-344-6324

Order Toll-Free
1-800-344-4465

CIRCLE 251 ON FREE INFORMATION CARD

PIC Programmer Development Tools

JM-PICE \$245

- Programmer for PIC 16C5X, 16C6X, 16C7X, 16C84, and 17C4X in DIP packages.
- Assembler and Simulator.
- Emulates program memory, registers, and I/O for the PIC 16C5X.
- Instruction-level emulation for the PIC 16C71 and 16C84.
- Programmer only \$155, Complete package \$245. 15 day money-back guarantee.
- Adapters for emulating 16C6X and 16C7X will be available soon.

80C552

Development System

- 8051 core processor with 8 channel 10-bit A/D and PWM.
- 24 more I/O and RS-232 port.
- 32K ROM and 64K RAM.
- \$120 each SBC. High performance development system includes assembler, disassembler, real-time execution and debugging, monitor program, and examples (\$70 more).
- 80C31 Development System is also available.

ROMY-16 EPROM EMULATOR

Emulates ROM or RAM in 8- and 16-bit systems. \$195 (2716-27256) or \$245 (2716-27010). Window/menu driven interface. 15 day money-back guarantee. Optional assembler, disassembler, and ROM debugger \$100 each CPU.

68HC11 Development System

- Eight channel 8-bit A/D converter.
- 32K ROM and 32K RAM.
- \$120 each SBC. 40x2 LCD \$20.
- Add \$70 for the real-time integrated development system.
- Microprocessor Simulator/Debugger and Custom design are available.

J&M Microtek, Inc.
83 Seaman Road, W Orange, NJ 07052
Tel: (201)325-1892 Fax: (201)736-4567

SHOPPER CLASSIFIED

MISCELLANEOUS ELECTRONICS FOR SALE

TUBES: "oldest", "latest". Parts and schematics. SASE for lists. **STEINMETZ**, 7519 Maplewood Ave., EN 46324, Hammond, IN 46324.

FIBER-Optic Projects — Swing into the new technology by assembling tried and true projects recently published. "Practical Fiber-Optic Projects" - BP374 is only \$9.95. (price includes shipping) **ELECTRONICS TECHNOLOGY TODAY INC.**, PO Box 240, Massapequa Park, NY 11762-0240.

CABLE TV Test Chips for Jerrold, Tocom, Pioneer, Scientific Atlanta, etc...**Quick Installation** New Multi-Mode modules available. Prices from \$5.00 each. 1 (800) 786-9025.

RESTRICTED Information: Surveillance, Locksmithing, Cable, Hacking, investigation, Transmitter kit, Etc. **MENTOR**, Box 1549-Z, Asbury, NJ 07712.

TV Notch filters, free brochure, **MICRO THINC.**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

GREEN Thumb Alert— Electronics enters the Garden! New exciting book points out how gardeners can build simple gadgets to promote success where the elements work against you. Some of the projects are: over/under temperature monitoring, dusk/dawn switching, automatic plant watering, warming cables, etc. "Electronic Projects for the Garden" only \$9.95 (price includes shipping) **ELECTRONICS TECHNOLOGY TODAY INC.**, PO Box 240 Massapequa Park, NY 11762-0240.

WHITE Noise generator, complete with case and power supply. Perfect for getting to sleep and lab projects. Only \$29.95 (plus \$3.50 S&H) Visa/MC call 1 (800) 357-2199, or send check/MO to **COASTAL WINKS**, 6755 Mira Mesa Blvd., #123-282B, San Diego, CA 92121.

A.E. Company Personal security products and basic cable converters. Call for free brochure. Call 1 (800) 234-0726.

PRINTED circuit boards — etched, drilled, tin plated. Single sided \$1.25/sq. inch. **CHELCO ELECTRONICS**, 61 Water Street, Mayville, NY 14757. 1-800-388-8521. Fax (716) 753-3220.

RESISTORS, \$1 a dozen. Catalog \$1, Foreign add \$1. **ZIPFAST**, Box 12238, Lexington, KY 40581-2238.

MICRO Miniature TV Cameras. Color or B/W mounted in clocks, smoke detectors or speakers or unmounted with lens starting at \$300 for B/W. Visa/MC/AMEX. **ESM**, 1-800-658-5849.

PCB design. Why let good designs die because of poor layout? 20 yrs. experience. Professional software. Digital, analog DC-20GHz. Film, gerber, fabrication, assembly, parts list, schematic ready for production. Call/fax **GraphFx**, (818) 882-5661, Box 3007, Chatsworth, CA 91313.

TUBES, new, up to 90% off, **SASE, KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

TEST EQUIPMENT

HP 8640B signal generator \$1700; **HP 8614A** signal generator \$450; **HP 59401A** IEEE-488 bus analyzer \$450; **Tektronix 7834** oscilloscope mainframe \$350; **Sony/Tektronix 308** data analyzer \$500; **Fluke 335A** DC voltage standard \$750; **Fluke 7260A** counter/timer \$350. List available. Phone: (908) 722-6157 Fax: (908) 722-6391.

TEST Equipment pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 US for catalog. Refunded on first order. **J.B. Electronics**, 3446 Dempster, Skokie, IL 60076. (708) 982-1973.

BUSINESS OPPORTUNITIES

MAKE \$75,000 to \$250,000 yearly repairing all kinds IBM monitors. Successful home based business, anywhere. Telephone required. Details: USA \$3.00 cash (no checks) Dealerships: Canada - all foreign countries: \$85.00 for application brochure. **RANDALL DISPLAY**, Box 2168 R, Van Nuys, CA 91404.

600 How-to-books, reports & guides you can reprint & sell. Complete test of all 600 on Windows CD Rom. Just \$99. 1 (800) 457-5477. VISA/MC/AE.

BECOME A millionaire in security industry. High demand. Complete business and operations package. Free details. **LSASE: SECURITY**, Box 1056K, Jeffersonville, IN 47131.

EARN Amazing Profits on the information super-highway! Send **Now** for **Free** report! **PARKSIDE PRESS**, 7527 Berwick Drive, Westland, MI 48185-1414.

\$75 or more per hour with your computer. Several easy and simple ways. Complete details. **LSASE. COMPUTER**, Box 1314M, Jeffersonville, IN 47131.

VIDEO/Audio/Computers repair service for sale. Several locations in Florida. Principals only. Inquiry send to: **T.J.**, PO Box 841324, Pembroke Pines, FL 33024.

200+ per hour as countermeasures expert. Huge untapped market. Easy work. Complete training and business package. Free details. **LSASE. SURVEILLANCE**, Box 1056N, Jeffersonville, IN 47131.

EASY Work! Excellent pay! Assemble products at home. Call toll free 1 (800) 467-5566 Ext. 11068.

EXCELLENT Extra income! Assemble easy products at home. Program guaranteed! 1 (800)-377-6000 Ext. 6870. Open Sunday.

SIGN of the times. Start your own profitable alarm company with monthly recurring revenues. Further details from **A-1**, 940 Murphy Rd. #3, Sarnia, Ontario, N7S-5C4, Canada.

600 How-To-Books, Reports, Guides you can reprint & sell. Complete text of all 600 on Windows CD Rom. Just \$99. **VISA/MC/COD** order by phone 1 (800) 762-9950. 24 hours!

EDUCATION & INSTRUCTION

ELECTRONIC engineering. 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS**, 1203 Grant Avenue, Rockford, IL 61103.

LEARN VCR repair. Great profits. Home study. **P.C.D.I.**, Atlanta, GA. Free literature. 1 (800) 362-7070 Dept. VRA342.

MICROWAVE oven manual, to become a technician. Award winner edition. USA \$42.95, all foreign countries \$69.00. **RANDALL**, Box 2168 R, Van Nuys, CA 91404.

KNOWLEDGE CARDS. Tables. Formulas. Fun and educational. Package \$2.00. Box 12238, Lexington, KY 40581-2238.

ESP Bioelectricity, microwave hearing, comprehensive booklet ... \$1.00; \$2.00 foreign. **RESEARCH ASSOCIATES**, PO Box 3583, Boynton Beach, FL 33424-3583.

LEARN PC assembly language. Disk \$5. Book \$18. **ZIPFAST**, Box 12238, Lexington, KY 40581-2238.

HUBBLE Telescope photographs (GIFs) — Entire public Hubble Series available. **SPACEPICS**, POB 75711, Oklahoma City, OK 73147.

BECOME a professional locksmith. Home study. Free career literature. **P.C.D.I.**, Atlanta, Georgia. 1 (800) 362-7070 Dept. LKA342.

CHRISTMAS SALE!

Save on cable rental fees!

CABLE TV DESCRAMBLERS

WE'LL BEAT ANY PRICE

COMPATABLE REPLACEMENTS
FOR MOST MAJOR SYSTEMS

• 24 HOUR SHIPMENTS!

• 30 DAY MONEY BACK GUARANTEE! • QUANTITY DISCOUNTS!

MASTER CARD / AMEX / VISA / C.O.D

Have make and model number of equipment used in your area ready.
All Shipping & Handling Fees at Customer's Expense.

CALL TOLL-FREE **1-800-284-8432**
CABLE WAREHOUSE


10117 West Oakland Park Blvd., Suite 315, Sunrise, FL 33351

NO FLORIDA SALES

Anyone implying theft of service will be denied assistance.

ACTIVE MICRO We Want Your Excess Inventory

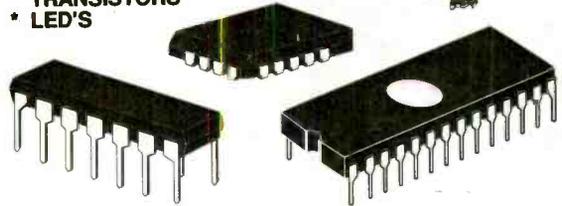- * INTEGRATED CIRCUITS
- * MEMORY (NEW OR USED)
- * EPROMS (NEW OR USED)
- * CIRCUIT BOARDS
- * DIODES
- * TRANSISTORS
- * LED'S



Tel **310-494-4851** Fax **310-494-4913**
1891 Oblispo Ave Signal Hill, CA 90804

SHOPPER CLASSIFIED

HAVE Fun and learn about electronic circuits! Simulate and test circuits on your PC. Get a library of 50 classic circuits and a free SPICE simulator! Apply powerful analysis and design techniques. Plot voltages at any node. Broaden your skills with this ready reference: Opamps, Active/LC filters, Instrumentation, Transistors, RF, Oscillators, and more! Easy to use. HD disks (specify size) and manual \$24. **INSIGHT SOFTWARE**, PO Box 48451, Niles, IL 60714.

It could be a best seller. But it's free.

To get your free catalog, write:
Consumer Information Center
Dept. BEST, Pueblo, CO 81009

SATELLITE EQUIPMENT

FREE catalog — Lowest prices worldwide. Satisfaction guarantee on everything sold - Systems, upgrades, parts, all major brands factory fresh and warrantied. **SKYVISION**, 1012 Frontier, Fergus Falls, MN 56537. 1 (800) 334-6455. Outside US (218) 739-5231.

VIDEOCYEPHER II descrambling manual. Schematics, video and audio. Explains DES, EPROM, CloneMaster, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95, \$2.00 postage. Schematics for Videocypher II Plus, \$20.00. Schematics for Videocypher II 032, \$15.00. Software to copy and alter EPROM codes, \$25.00. VCI Plus EPROM, binary and source code, \$30.00. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

SATELLITE TV organizer for DOS. Two diskettes & instructions. Database software for quick changing transponders. \$19.95 plus \$3.00 S&H. **HUMANFORM ROBOTICS**, PO Box 158486, Nashville, TN 37215.

DSS How it's done. 150 channels received direct with small dish system. Send \$14.95 + \$2.00 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20817.

PATENT SERVICES

PATENT protection can be crucial to capitalizing on your invention. If you are interested in patenting your invention please call **JON M. JURGOVAN**, (registered patent attorney) for free initial consultation. (404) 951-0931 D (404) 240-0979 E.

WANTED

MEDICAL Instrumentation company in northern New Jersey has full-time opening for engineer or highly motivated technician with demonstrated troubleshooting abilities on analog, digital and uP circuits as well as good organizational skills. Call **RHEA**, at (201) 313-7075, 10-5 weekdays.

American Heart AssociationSM
Fighting Heart Disease and Stroke

Would you give your right arm to avoid high blood pressure?

©1995 American Heart Association

DO-IT-YOURSELF AUDIO AMPLIFIER KITS

Mark V Electronics, Inc.
8019 E. Slauson Ave.,
Montebello, CA 90640

Enclosures at Unbeatable prices !

Free Catalog 213/888-8988 Fax 213/888-6868

Order 1-800-521-MARK / 1-800-423-FIVE

In business since 1985

Kit skill levels are specified as ▲ beginner ▲▲ intermediate or ▲▲▲ advanced!

Best Buy

Metal Cabinets with Aluminum Front Panel

LG-1273 3x12x7" \$ 26.50
LG-1684 4x16x8" 32.50
LG-1924 4x19x11 1/2" 38.25
LG-1925 5x19x11 1/2" 42.00
LG-1983 2 1/2 x 19x8" 35.25
LG-1923 3x19x11 1/2" 36.50
LG-1927 7x19x11 1/2" 50.50

LG- Black anodized rack cabinet

Modular Desktop Consoles

L x W x H
LE-453 4x4 3/4 x 3" \$ 7.50
LE-653 6x4 3/4 x 3" 9.75
LE-853 8x4 3/4 x 3" 11.75
LE- Black finished aluminum panel 1mm thick.

Alarm Box with Lock

LB-1085 8 1/4 x 10 1/4 x 5" \$ 18.75
LB-1395 9 1/4 x 13 1/4 x 5" 25.50
LB-1525 12 1/4 x 15 1/4 x 5" 35.25
*LB-1494 9 1/4 x 14 1/4 x 4" 21.50
LB-1383A 8 1/2 x 13 1/4 x 4" 23.25
*No lock & LB- Sheet Metal 0.8mm

Mejor Compra !

New

*LL-1923B 2 1/2 x 19x12" 69.50
*LL-1925A 5x19x12" 79.50

*LL- High quality full Aluminum Cabinet
*LL- Front panel .157" & other panels .078"

- Dimensions in inches ± .05
- Custom-made for other dimensions if over 100 pcs for single model !

Camera Housing

*LD-1244 2 1/2 x 10 1/4 x 4" \$55.00
*LD-1516 3 3/4 x 13 3/4 x 4" 29.50
*LD-1565 4x13 3/4 x 5 1/4" 31.75
*LD- Stainless Steel 0.7mm
*LD- Sheet Metal 1mm

Power Transformers & **Toroidal Transformer

001	28/30V x 2	6A	\$ 30.00
002	36V x 2	3A	25.00
003	40V x 2	6A	32.00
**008	28/30V x 2	6A	40.00
**009	48/53V x 2	8A	66.00
**012	33/40/42Vx2	6A	48.00

TA-800MK2 ▲▲ 120+120W Pre & Main Stereo Amp. (4 lbs.)



Kit: \$ 67.92
Aemb. \$ 88.95

Power Output: 120W into 4 ohms RMS, 72W into 8 ohms RMS. Frequency Response: 10-20KHZ. THD: <0.01%. Tone Control: Bass ±12dB, Mid & Treble ±8dB. Sensitivity: Phono Input, 3mV into 47K. Line, 0.3V into 47K. Signal to Noise Ratio: 86dB. Power Requirement: 40VDC @ 6A. Suggested Mark V model 001 or 008 transformer. Recommended Metal Cabinet LG-1924.

TA-50A/B ▲ Melody Generator

Clearance Sale

Kit: \$ 13.85 \$ 8.80

It uses the latest CMOS ROM technology and plays 8 different tunes. It operates on 2 AA size batteries due to its small current demand. You can adapt the generators to door bells, musical boxes, electronic clock alarms, etc. TA-50A: Jingle Bells... TA-50B: Happy Birthday...

TA-1000A ▲▲ 100W Dynamic Class A Mono Amp (4 lbs.)



Kit: \$ 54.00 Aemb. \$ 74.00

Power Output: 100W into 8 ohms RMS, 125W into 4 ohms RMS. Frequency Response: 10HZ-100KHZ THD: <0.008%. Signal to Noise Ratio: 80dB. Sensitivity: 1V. Power Requirements: 35 to 45VDC @ 3A. Suggested Mark V model 001 or 008 transformer. Capacitor 10,000uf 80V model 016. Recommended Metal Cabinet LG-1924.

TR-503 ▲ Regulated DC Power Supply



Kit: \$ 18.75 Aemb. \$ 27.85

It is short circuit proof and has overload protection. Output voltage is variable over a range of 0-50V. Current limit trip is adjustable up to max of 3A. Suggested Mark V 002 transformer. (1 lb.)

TA-388 ▲▲▲ Class A FET Dynamic Buffer Stereo Pre-Amp (1 lb.)

New



Kit: \$ 64.00 Aemb. \$ 80.00

Frequency Response (at rated output): Overall 10HZ-100KHZ +0.5dB-1dB. THD: Overall <0.007% at or below rated output level. Channel Separation (at rated output 1KHZ): Overall better than 70dB. Hum & Noise: Overall better than 90dB. Input Sensitivity (1KHZ for rated output): 300-600mV. Maximum Output Level: Pre-Amp output 1.8V (0.1% THD). Power Requirement: 30V X 2 AC 500mA.

SM-302 ▲▲ 60+60W Stereo Power Amp



Kit: \$ 75.00
Aemb. \$ 94.00

It provides 3 input jack pairs. One pair accept a high impedance microphone. The two remaining pairs are for high & low level input sources. Power Output: 60W per channel into 4 ohms RMS. 20HZ-20KHZ. THD: <0.1%. Input Sensitivity: Mic/Guitar 10mV, Hi 380mV, Lo 640mV. Ready to plug in when assembled. (11 lbs.)

SM-100 ▲▲▲ 150 MHZ 8 Digit Frequency Counter (2 lbs.)

New Release



Kit: \$ 79.00
Aemb. \$ 99.00

Frequency Range: 10HZ-150MHZ. Gate Time: 0.01s, 0.1s, 1s, 10s. Input Sensitivity: KHZ range 10HZ-10MHZ 20mV(min.). MHZ range 1MHZ-120MHZ 20mV(min.), 120MHZ-150MHZ 35mV (min.), 150MHZ-200MHZ 40mV(typical). Time Base: 10MHZ crystal, ±10 ppm. Input Impedance: 1M ohm. Response Time: 0.2s. Resolution: 0.1 HZ: 10s gate time, 1HZ: 1s gate time, 10HZ: 0.1s gate time, 100 HZ: 0.01s gate time. Hold the last input signal. Reset counter to 0. DC 9V power adapter or 1.5VX4"D" size batteries. (Adapter not included)

School Project Kits Source ...

SM-36	Dynamic Noise Reduction	▲	\$ 26.00
TA-006	6W Mini-Amplifier	▲	9.50
TA-28	Digital Voice Memo	▲▲	25.00
TA-120	36W Class A Power Amp.	▲▲	32.50
TA-201	Microphone Mixer Mono Amp.	▲	20.79
TY-45	20 Bar/Dot Level Display	▲▲	41.45
TY-2	Flourescent Light Driver	▲	14.75

See our catalog for more kits!

Minimum order \$ 20. We accept Visa, MasterCard & Money Orders. Checks allow 2 weeks for clearance. We ship by UPS ground inside US (min \$ 4.00) and ship by US mail outside US. Please call for orders shipping & handling or fax foreign orders. PO Orders are welcome from schools. We are not responsible for typographical errors.

CIRCLE 303 ON FREE INFORMATION CARD

www.americanradiohistory.com



Plug a Friend into
Electronics
NOW[®]
and Save \$26.03*

This Christmas give an electrifying gift ... plug a friend into Electronics Now and brighten the whole new year! Whether electronics is your friend's livelihood or hobby, your gift will illuminate the whole spectrum of electronics throughout the coming year and provide a monthly reminder of your friendship.

Electronics Now will keep your friend informed and up-to-date with new ideas and innovations in all areas of electronics technology ... computers, video, radio, stereo, solid state devices, satellite TV, industrial and medical electronics, communications, robotics, and much, much more.

We'll provide great plans and printed circuit patterns for great electronic projects. In just the last year, Electronics Now has presented amateur TV equipment, computer peripherals, microcontroller programmers, test equipment, audio amplifiers, telephone projects, relay circuits and much more.

PLUS ... equipment troubleshooting techniques ... circuit design ... reports on new technology and products ... equipment test reports ... in-depth coverage on computers, video, audio, vintage radio ... and lots more exciting features and articles.

SAVE \$26.03* ... OR EVEN \$52.06* ... For each gift of Electronics Now you give this Christmas, you save a full \$26.03* off the newsstand price. And as a gift donor, you're entitled to start or extend your own subscription at the same Special Holiday Gift Rate—you save an additional \$26.03*!

No need to send money ... if you prefer, we'll hold the bill till January, 1996. But you must rush the attached Gift Certificate to us to allow time to process your order and send a handsome gift announcement card, signed with your name, in time for Christmas.

So do it now ... take just a moment to fill in the names of a friend or two and mail the Gift Certificate to us in its attached, postage-paid reply envelope. That's all it takes to plug your friends into a whole year of exciting projects and new ideas in Electronics Now!

*Basic sub rate — 1 yr/\$19.97 2 yrs/\$38.97

1995 ANNUAL INDEX

Electronics NOW

Volume 66

Abbreviations: (AUD) Audio Update; (C) Construction; (CC) Computer Connections; (D) Department; (DB) Drawing Board; (ED) Editorial; (ER) Equipment Reports; (HH) Hardware Hacker; (LET) Letters; (QA) Q & A; (WN) What's News

A

Abandon All Hope (Holtzman)(CC)	Nov 130
AC	
and DC Control Circuits (Marston)(C)	Aug 69
Power Drives (Lancaster)(HH)	May 81
Wattmeter (QA)	Nov 8
Acoustic Cancellations (Lancaster)(HH)	Jun 73
Active Audio Filters, High- and Low-Pass (Marston)	Feb 61,(LET)Jun 12
Active Noise Cancellation (Lancaster)(HH)	Sep 46
Add a 3-Digit Display to the Tachometer Circuit (Grossblatt)(DB)	Feb 87
Adobe's Acrobat (Lancaster)(HH)	Jul 75
"All-Channels" FM Transmitter (Lancaster)(HH)	Sep 46
Analyzing Remote Control Output (Hamilton)(C)	Aug 50
Another Patent Horror Story (Lancaster)(HH)	Nov 114
A.P.E. SMD-250 Solder Desolder Station (ER)	May 14
AUDIO (See also AUDIO UPDATE, RADIO)	
Audio	
Amplifier, High-Power Hi-Fi (Metz and Boyce)(C)	Oct 33,Nov 31
Chip (QA)	Jun 8
Connector Overview (Miller)(AUD)	Sep 134
Generator, Computer-Controlled (Covington)(C)	Feb 44
Router Switch Selector Circuit (Grossblatt)(DB)	Jul 83
A PC Board for the (Grossblatt)(DB)	Aug 86
General-Purpose Controller for (Grossblatt)(DB)	Oct 55
Keyboard Section of (Grossblatt)(DB)	Jun 82
Signals from your PC, Precision (Covington)(C)	Feb 44
Build This Subwoofer for Your Car (Rumreich)(C)	Oct 41
Music Vision (Kraft)(C)	Nov 23
"Old" Circuits and a Brand New Topic (Grossblatt)(DB)	Mar 86
AUDIO UPDATE (D)(Klein)	Jan 85, Feb 84, Apr 83 May 89, Jun 81, Jul 81, Aug 84 Sep 134, Oct 53, Nov 120, Dec 50
Audio Connector Overview (Miller)(AUD)	Sep 134
Audio Instructions	Feb 84
Build a Super-Simple Audio/Video Cable Tester for Under \$10	Apr 83
Dance SPL and Medical Music Getting a Quick Fix, Or Service with a Smile	Dec 50
High-Definition Compatible Digital Processing	Oct 53
Letters: Bouquets and Brickbats	May 89
Listening Tests: Sex and the Experienced Listener	Aug 84
More Miscellaneous Matters	Nov 120
Taming the Deafening Decibels Part I	Jun 81
Practicing "Safe Sound"	Jul 81

AUTOMOTIVE

Add a 3-Digit Display to the Tachometer Circuit (Grossblatt)(DB)	Feb 87
Automotive Computer Basics (Lancaster)(HH)	Feb 75
Build This Subwoofer for Your Car (Rumreich)(C)	Oct 41
Converting Spark Count to Engine RPM (Grossblatt)(DB)	Jan 87
ProCar Security System, The (Miga)(C)	Feb 35, Mar 65, May 71, Jun 67

B

BASIC

Stamp Manuals (Lancaster)(HH)	Jul 75
Stamp II Microcomputer (Lancaster)(HH)	Dec 41
Battery Isolator (QA)	Apr 8
Benchtop Function Generator (Bergquist)(C)	Nov 33
Bezier Spline Book (Lancaster)(HH)	Jul 75
Blood Oxygen Measurement (QA)	Nov 8
Brain Implants (Lancaster)(HH)	Mar 79
Bridge Circuits (Marston)	Sep 41
Bridges: Matching Resistors and Capacitors (Marston)	Nov 41
Budget Capacitance Meter (Babcock)(C)	Jun 55
BUILD A/AN THE THIS (See CONSTRUCTION)	

C

Cable Tester (Barbarello)(C)	Jul 69
Cable Tester Kit, Sescom CT-6 (ER)	Sep 15
Cache Mystery (QA)	Sep 7
Call Counter, The (Stern)(C)	Jun 48
Capacitance Meter, Budget (Babcock)(C)	Jun 55
Capacitor Dot Code (QA)	Oct 8
Carbon Monoxide Detector (Gaffigan)(C)	Sep 37
Card Reader for Your PC (Barbarello)(C)	Aug 63
Career, High-Tech, for the '90s (Reis)	Apr 63
Carrier-Current Remote Control (Caristi)(C)	Jun 49
Chip	
Adapter Resources (Lancaster)(HH)	Jun 73
Quik SMD Removal Kit (ER)	Aug 16
Tester, Build a (Hanslip)(C)	Jan 41
Classic Computer Resources (Lancaster)(HH)	Aug 77
Clock, Universal (Tarchinski)(C)	Jun 37
Closed-Loop Control Systems (Eichenberg)	Feb 69
COMPUTER (See also COMPUTER CONNECTIONS)	
Cable Tester (Barbarello)(C)	Jul 69
Card Reader for Your PC (Barbarello)(C)	Aug 63
Computer-Controlled Audio Generator (Covington)(C)	Feb 44
Data Depot's PC Clinic SB (ER)	Dec 13
Five Easy EEPROM Projects (Xu)	Nov 39
Green PCs (Byers)	May 31
Low-Cost Software	

for Electronics (Byers)	Sep 33, Oct 35
Magnetic Storage Tips (Rabin)	May 68
Microprocessors (Bigelow)	Mar 35
PC Cards (Bigelow)	Jun 31
PocketPOST Diagnostic Card (ER)	Nov 13
Power Pincher, The (Lashansky)(C)	May 43
Recycling Memory for Your PC (Schmidt)(C)	Sep 35
COMPUTER CONNECTIONS (D)(Holtzman)	
Jan 27, Feb 89, Mar 92	
Apr 90, May 27, Jun 84	
Jul 85, Aug 26, Sep 124	
Oct 61, Nov 130, Dec 52	
Nov 130	
Don't Interface—Interact	Jan 27
Engineering and Compromise	Aug 26
How to Solve All Your PC Problems	Sep 124
Random Thoughts on Miscellaneous Matters	Dec 52
Retreat of the Barbarians	May 27
Ten Years of Progress— For Better or Worse	Feb 89
UberSoft Uber Alles	Mar 92
Unauthorized Windows	Apr 90
Windows 95 Update	Oct 61
Windows and Warp, Delphi, and the P6	Jun 84
WinHEC '95	Jul 85
Computer Monitor Signal Generator, Sencore CM125 (ER)	Mar 16
Concrete Drain (QA)	Apr 8,(LET)Jun 12, Jul 12 (LET)Aug 12, Oct 14

CONSTRUCTION

AC & DC Control Circuits (Marston)	Aug 69
Analyzing Remote Control Output (Hamilton)	Aug 50
Benchtop Function Generator (Bergquist)	Nov 33
Budget Capacitance Meter (Babcock)	Jun 55
Build A/An	
Chip Tester (Hanslip)	Jan 41
Isolation Transformer (Whisenant)	Jan 63
Build This	
Milliohm Tester (Heil)	Feb 59,(LET)May 10
Power Controller (Roane)	Jan 68,(LET)Mar 14,(LET)May 10
Programmable Sinewave Generator (Portugal)	Jan 43,(LET)Mar 14
Subwoofer for Your Car (Rumreich)	Oct 41
Video Titrer (Michelson)	May 49
Cable Tester (Barbarello)	Jul 69
Call Counter, The (Stern)	Jun 48
Carbon Monoxide Detector (Gaffigan)	Sep 37
Card Reader for Your PC (Barbarello)	Aug 63
Carrier-Current Remote Control (Caristi)	Jun 49
Custom Meter Faces (Withrow)	Apr 51
dB Meter (Pivnichny)	Nov 112
Dual-Trace Converter (McIntire)	Jun 46
Experimenters' Video Receiver (Botts)	Dec 33
Handy Hobby Power Supply (Spiwak)	Jun 43
High-Power Hi-Fi Audio Amplifier (Metz & Boyce)	Oct 33, Nov 31
Infrared Logic Probe (Firman)	Dec 69
Jacob's Ladder (Iannini)	Dec 27
Laser Light Show (Williams)	Apr 33,(LET)Oct 14
Mini Logic	Nov 23
Analyzer (Barbarello)	Feb 47,(LET)Jul 12
Music Vision (Kraft)	Nov 23
Off-Line Regulators (Connell)	Apr 71,(LET)Aug 12

Over/Under-Voltage Protector (Tipton)	Sep 39
Power Control Circuits (Marston)	Jan 59,(LET)Oct 14
Power Pincher, The (Lashansky)	May 43
Precision Audio Signals from your PC (Covington)	Feb 44
ProCar Security System, The (Miga)	Feb 35,Mar 65,May 71,Jun 67
Prototyping Station (Bergquist)	Mar 54
Put That Phone on Hold! (Montegari)	Apr 39
Recycling Memory for Your PC (Schmidt)	Sep 35
Regulated Power Supply for Electrochemistry (Barrow)	Dec 29
Remote Control Adapter (Weeder)	Aug 41
Sinewave Doubler (Swift)	Feb 55
Slide Stepper, The (Swancara)	May 91
Solid-State Thermometer (Spiwak)	Mar 45
Telco in a Box (Cicon)	Sep 43,(LET)Nov 10
Telephone Cost Meter (Rahhal)	Apr 55
Universal Clock (Tarchinski)	Jun 37
Versatile Power Supply (Bergquist)	Dec 31
Video Inverter (Souza)	Jul 41
Voltage Converters (Marston)	Apr 42,(LET)Jul 12
Voltage Cursor Adapter (Campisi)	May 65
Wind Monitor (Leonik)	Aug 57
Working with Smart Displays (Lettow)	Jul 51
WWV Receiver (Heckt)	Mar 49,(LET)Jun 12
Control Circuits, AC & DC (Marston)(C)	Aug 69
Control Systems, Closed-Loop (Eichenberg)	Feb 69
Converting Spark Count to Engine RPM (Grossblatt)(DB)	Jan 87
Custom Meter Faces (Withrow)(C)	Apr 51
Customized Remote Control (QA)	Sep 7

D

Dance SPL and Medical Music (Klein)(AUD)	Dec 50
Data Depot's PC Clinic SB (ER)	Dec 13
dB Meter (Pivnichny)(C)	Nov 112
DC-to-DC Converters, Modular (Eichenberg)	Dec 37
Deafening Decibels, Taming the (Klein)(AUD)	Jun 81,Jul 81
Deceleration Detector (QA)	Mar 8
Degaussing Coil (QA)	Oct 8
Digital Sinewave Generators (Lancaster)(HH)	Mar 79
Disk Errors (QA)	Feb 10
Displays, Smart, Working with (Lettow)(C)	Jul 51
Distortion Reduction Schemes (Lancaster)(HH)	Mar 79
DNA Computer Language, The (Lancaster)(HH)	Apr 75
Don't Interface—Interact (Holtzman)(CC)	Jan 27
DRAWING BOARD (D)(Grossblatt)	Jan 87,Feb 87,Mar 86,Jun 82,Jul 83,Aug 86,Oct 55
Add a 3-Digit Display to the Tachometer Circuit	Feb 87
Audio Router Switch Selector Circuit	Jul 83
Converting Spark Count to Engine RPM	Jan 87
General-Purpose Controller Circuit for Audio Router	Oct 55
Keyboard Section of the All-Electronic Audio Router	Jun 82
"Old" Circuits and a Brand New Topic	Mar 86
PC Board for the Audio Router, The	Aug 86
DSS, Has it been Hacked? (McCormac)	Aug 33
Dual-Trace Converter (McIntire)(C)	Jun 46

E

EE Internet Sites (Lancaster)(HH)	Dec 41
EEPROM Projects, Five Easy (Xu)	Nov 39
E-Field AC Voltage Sensing (Lancaster)(HH)	Jul 75
Electronic Clockwork (QA)	May 8
Electronic Filter Fundamentals (Lancaster)(HH)	Sep 46
Elenco Electronics FO-30 Fiber Optics Kit (ER)	Apr 14
Engineering and Compromise (Holtzman)(CC)	Aug 26
Engineering Economics Review (Lancaster)(HH)	Apr 75
EQUIPMENT REPORTS (D)	Feb 16,Mar 16,Apr 14,May 14,Jul 16,Aug 16,Sep 15,Oct 16,Nov 13,Dec 13
A.P.E. SMD-250 Solder/Desolder Station	May 14
Chip Quik SMD Removal Kit	Aug 16
Data Depot's PC Clinic SB	Dec 13
Elenco Electronics FO-30 Fiber Optics Kit	Apr 14
Fieldpiece HS24K15 Stick Meter Fieldpack	Oct 16
Fluke GMM Graphical Multimeter	Jul 16
PocketPOST Diagnostic Card	Nov 13
Protek P-3502C Oscilloscope	Feb 16
Sencore CM125 Computer Monitor	Mar 16
Signal Generator	Sep 15
Sescom CT-6 Cable Tester Kit	Dec 33
Experimenter's Video Receiver (Botts)(C)	Dec 33

F

Fiber Optics Kit, Elenco FO-30 (ER)	Apr 14
Fibonacci's Sunflowers (Lancaster)(HH)	Jul 75
Fieldpiece HS24K15 Stick Meter Fieldpack (ER)	Oct 16
Five Easy EEPROM Projects (Xu)	Nov 39
Floating a Battery (QA)	Sep 7
Fluke GMM Graphical Multimeter (ER)	Jul 16
FM RBDS Tuner (Lancaster)(HH)	Apr 75
Fourier Series Analysis (Lancaster)(HH)	Aug 77
Function Generator, Benchtop (Bergquist)(C)	Nov 33

G

General-Purpose Controller Circuit for Audio Router (Grossblatt)(DB)	Oct 55
Getting a Quick Fix, Or Service with a Smile (Klein)(AUD)	Jan 85
Getting Connected to the Internet (Bigelow)	Jul 31
GPS Navigation Update (Lancaster)(HH)	Oct 47
Green PCs (Byers)	May 31

H

Hacker PostScript Interface (Lancaster)(HH)	Jan 77
Halogen Cycle Mysteries (Lancaster)(HH)	Jan 77
Handy Hobby Power Supply (Spiwak)(C)	Jun 43
HARDWARE HACKER (D)(Lancaster)	Jan 77,Feb 75,Mar 79,Apr 75,May 81,Jun 73,Jul 75,Aug 77,Sep 46,Oct 47,Nov 114,Dec 41,May 81
AC Power Drives	Jun 73,(LET)Nov 10
Acoustic Cancellations	Sep 46
"All-Channels" FM Transmitter	Nov 114
Another Patent Horror Story	Jul 75
Basic Stamp Manuals	Apr 75
DNA Computer Language, The	Aug 77
Fourier Series Analysis	Jan 77
Halogen Cycle Mysteries	Mar 79
Low-Cost TV Data Displays	Dec 41
Pseudoscience Strikes Again	Feb 75
Scientific Resource	Oct 47
Understanding Pilot Tubes	Aug 33
Has DSS Been Hacked? (McCormac)	Jun 8,(LET)Sep 12
Headphone Amplifier (QA)	Jun 8,(LET)Sep 12
High and Low-Pass Active Audio Filters (Marston)	Feb 61,(LET)Jun 12
-Definition Compatible	Oct 53
Digital Processing (Klein)(AUD)	Oct 33,Nov 31
-Power Hi-Fi Audio Amplifier (Metz & Boyce)(C)	Apr 63,(LET)Aug 12
-Tech Career for the '90s, A (Reis)	Mar 35
HISTORY	Jul 46
Microprocessors (Bigelow)	Nov 29
Scanning Early TV (Clifford)	Jan 8
X-Rays and Their Discoverer (Stroud and Slater)	Jan 8
Howler Substitute (QA)	Jan 8
How to Solve All Your PC Problems (Holtzman)(CC)	Sep 124

I

Incubator for Birds' Eggs (QA)	May 8
Infrared Logic Probe (Firmani)(C)	Dec 69
Intermittent Record Player (QA)	May 8
INTERNET	Oct 47
Directories (Lancaster)(HH)	Jul 31
Getting Connected to the (Bigelow)	Jan 63
Isolation Transformer, Build an (Whisenant)(C)	Jan 63

J

Jacob's Ladder (Iannini)(C)	Dec 27
-----------------------------	--------

K

Keyboard Section of the All-Electronic Audio Router (Grossblatt)(DB)	Jun 82
----------------------------------------------------------------------	--------

KIT BUILDING	Apr 14
Elenco Electronics FO-30 Fiber Optics Kit (ER)	Sep 15
Sescom CT-6 Cable Tester Kit (ER)	Sep 15

L

Laser	Apr 33,(LET)Oct 14
Light Show (Williams)(C)	Jul 8,(LET)Oct 14
Phonograph (QA)	Oct 43
L-C Bridges (Marston)	Oct 43

LETTERS (D)

Letters Bouquets and Brickbats (Klein)(AUD)	Jan 10,Feb 12,Mar 14,Apr 12,May 10,Jun 12,Jul 12,Aug 12,Sep 12,Oct 14,Nov 10,Dec 10
Light Controller Interference (QA)	May 89
Light Turn-on Circuit (QA)	Feb 10
Light Turn-on Circuit (QA)	Jul 8
Listening Tests: Sex and the Experienced Listener (Klein)(AUD)	Aug 84
Logic Analyzer, Mini (Barbarello)(C)	Feb 47,(LET)Jul 12
Logic Probe, Infrared (Firmani)(C)	Dec 69
Long Cable Runs (QA)	Jan 8
Low-Cost	Sep 33,Oct 35
Software for Electronics (Byers)	Mar 79
TV Data Displays (Lancaster)(HH)	Mar 79
Low-Power Clock (QA)	Mar 8

M

Magir:	Apr 75
Digital Sinewave Codes (Lancaster)(HH)	Nov 114
Sinewaves (Lancaster)(HH)	May 68
Magnetic Storage Tips (Rabin)	Nov 41
Matching Resistors and Capacitors, Bridges (Marston)	Nov 41
Memory, Recycling, for Your PC (Schmidt)(C)	Sep 35
Meter Faces, Custom (Withrow)(C)	Apr 51
Meter Shunts (QA)	May 8,(LET)Sep 12
Microcontroller Help (QA)	Jun 8
Microprocessors (Bigelow)	Mar 35
Mid-Flange Mensch Converter (Lancaster)(HH)	Nov 114
MIDI Music Book (Lancaster)(HH)	Dec 41
Millionm Tester, Build This (Heil)(C)	Feb 59,(LET)May 10
Mini	Feb 47,(LET)Jul 12
Logic Analyzer (Barbarello)(C)	Apr 8
Radio Station (QA)	Dec 37
Modular DC-to-DC Converters (Eichenberg)	Apr 8,(LET)Jun 1
Monitor Switcher (QA)	May 81
More Magic Sinewaves (Lancaster)(HH)	Nov 120
More Miscellaneous Matters (Klein)(AUD)	Mar 8
Motherboard Misery (QA)	Jul 16
Multimeter, Graphical, Fluke GMM (ER)	Nov 23
Music: Vision (Kraft)(C)	Oct 47
Mystery Band (Lancaster)(HH)	Feb 75
"Mystery Band" Opportunities (Lancaster)(HH)	Feb 75

N

Narrow Tunable Bandpass Filter (Lancaster)(HH)	Sep 46
Negative Regulator (QA)	Apr 8
Neon Power (QA)	Feb 10
Network Card Settings (QA)	Jul 8
New BASIC Stamps (Lancaster)(HH)	May 81
NEW LITERATURE (D)	Jan 25,Feb 26,Mar 28,Apr 26,May 24,Jun 24,Jul 26,Aug 22,Sep 127,Oct 26,Nov 20,Dec 24
NEW PRODUCTS (D)	Jan 29,Feb 22,Mar 18,Apr 22,May 15,Jun 20,Jul 22,Aug 18,Sep 20,Oct 18,Nov 16,Dec 19
New Tek's Video Toaster (Lancaster)(HH)	Aug 77
Nine-Channel Remote Control (Caristi)(C)	Jun 49
No Hot Boot (QA)	Apr 8
NPN Transistor Dilemma (QA)	Oct 8

O

Off-Line Regulators (Connell)(C)	Apr 71,(LET)Aug 12
"Old" Circuits and a Brand New Topic (Grossblatt)(DB)	Mar 86
Online Services (Lancaster)(HH)	Feb 75
Op-Amp Antenna Amplifier (QA)	Sep 7
Operational Amplifiers (Marston)	Jan 58
Oscilloscope, Protek P-3502C (ER)	Feb 16
Over/Under-Voltage Protector (Tipton)(C)	Sep 39

P

Password Swap (QA)	Oct 8
PC	Aug 86
Board for the Audio Router (Grossblatt)(DB)	Jun 31
Cards (Bigelow)	Dec 13
Clinic SB, Data Depot's (ER)	Oct 8
Thermometer (QA)	May 31
PCs, Green (Byers)	May 31

PC-BOARD DESIGN

continued from page 26

library comes with over 200 components, including a good assortment of connectors and SMD (surface mounted device) footprints. New parts can be added to the library using a library editor. Parts can be selected from the library by name or by highlighting them from a library menu. A browse menu lets you see the components before you lay them down, which eliminates a lot of guess work. Once a device is selected, it may be repeated as many times as you wish.

Tracks may be placed manually or by using the pad-to-pad autorouter. Unlike a conventional autorouter, this single-minded heuristic router uses a very clever algorithm to find an unimpeded path between two specified pads—unless, of course, you've somehow managed to paint yourself into a corner. Getting blocked is hard to do because the router will use all available layers when plotting a path. The router supports six copper layers and two ground planes, and does its own via placement. Unfortunately, the router investigates orthogonal

paths only, which may result in a number of vias that aren't really needed—vias that you will have to optimize on your own. When routing manually, the tracks may be orthogonal, free style, or curved. Track width is selectable in seven increments from 10 to 100 mils for both manual and autorouting, but you cannot change the width on the fly.

All commands can be accessed either through pull down menus or by using keyboard shortcuts. Screen panning is automatic anytime you hit against the edge of the screen, and the zoom function is available during placement and routing. Block functions include move, rotate, copy, delete, hide, and save. Objects may be rotated and flipped (except SMD devices) before and after placement.

Final artwork may be produced on either a dot-matrix or laser printer. Several plotters are supported, too. In addition to layer hardcopy, Easytrax generates artwork for silk-screen, solder, and SMD-paste masks. Easytrax also generates Gerber and Excellon N/C Drill files.

So if you think it's time to reward yourself with that free lunch you've been dreaming of,

help yourself by downloading Easytrax from the Internet, Protel's bulletin board, or the Electronics Now BBS (516-293-2283) under the filename EASYTRAX.ZIP.

Product:	PCAD
Version:	2.2
Price:	\$65
Platform:	DOS
Distributor:	Micronics Technology

Priced at just \$65, PCAD from Micronics Technology is a low-cost PC-board layout program targeted for the casual project maker and hobbyist. The DOS-based program lets you build PC boards up to 20 by 9.8 inches in size on two layers of copper—quite adequate for most of the projects found in the pages of *Electronics Now*. The simplicity of its operation and the no-frills approach make PCAD ideal for users who have little or no experience with making printed circuit boards.

PCAD's library has no devices, *per se*. Instead, component footprints are made using pads, lines, and accompanying nomenclature, which are saved as a block. In fact, this is the method we used to construct the connectors J1 through J4, as well as resistors R1 through R6. After the footprint is defined, it is saved to a file in a "library" directory, where it can be retrieved and used again. However, blocks cannot be rotated, which means you'll have to define a separate block for each different orientation. For example, the vertically-oriented chip IC2 (U2) used in the benchmark layout is saved as DIP14V, while its horizontal counterpart is called DIP14H.

PCAD comes with a large assortment of schematic symbols that can be used to identify parts in the silk-screen layer. Resistors R1 through R6 are a single block made up of two pads and a horizontal resistor symbol. If you wish, a part value, like 2.2K, can be added to the block. The component's annotation is added later by hand; auto annotation is not pro-

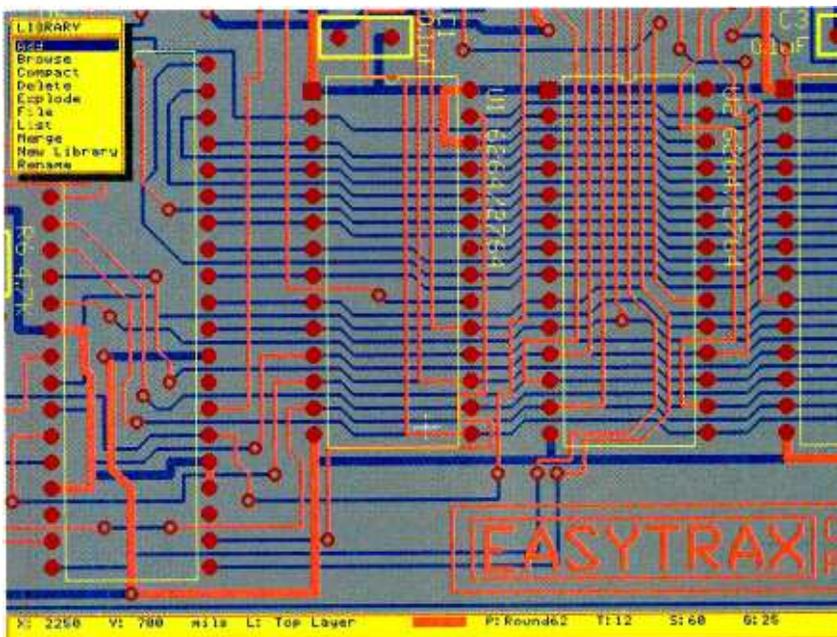


FIG. 3—NO FREE LUNCH? HARDLY. EASYTRAX is an example of what you can get for free. It comes with over 200 library components, which are connected by a pad-to-pad autorouter that uses a clever algorithm to find an unimpeded path between pads.

TABLE 1

	BoardMaker I	CADPAK II PCB II	Circuit Layout	DC/CAD	Easy-PC	Easy-PC Pro	Easytrax	EZ-Route Sid EZ-Logic	PCAD	PCBoards	SuperPCB for Windows	TurboCAD
Price	\$95	\$159	\$80	\$295	\$145	\$349	Free	\$249	\$65	\$99	\$299	\$129
Format	DOS	DOS	DOS	DOS	DOS	DOS	DOS	Windows	DOS	DOS	Windows	Windows
RAM required	512K	640K	512K	640K	512K	640K	512K	512K	640K	512K	4MB	2MB
Hard disk required	N	2MB	5MB	5MB	N	5MB	N	3MB	N	N	2MB	4MB
Maximum board size (inches)	17 x 17	30 x 30	16 x 10	32 x 32	17 x 17	32 x 32	32 x 32	8 x 10	20 x 9.8	6 x 13	16 x 8	
BBS file		ISISDEMO.EXE				EASY-PC.ZIP	EASYTRAX.ZIP				SUPERCAD.ZIP	
Schematic capture												
Included	Y	Y	N	Y	Y	Y	N	Y	N	N	Y(4)	Y(4)
Linked	N	N	N	Y	N	Y	N	Y	N	Y(3)	Y	N
Design rule check	Y	N	N	Y	N	Y	N	Y	N	N	Y	N
PCB Layout												
Automatic part placement	N	N	N	Y	N	Y	N	Y	N	N	Y	N
Repeat part placement	Y	Y	Y	Y	N	Y	Y	Y	Y(1)	N	N	Y
Rotate part prior to place	N	N	Y	Y	N	Y	Y	Y	Y(1)	N	N	Y
Zoom on-the-fly	Y	Y	Y	Y	Y	Y	Y	Y	N	N	N	Y
Auto pan	Y	Y	Y	Y	Y	Y	Y	Y	N	Y	N	Y
Routing Features												
Autorouter available	N	N	N	Y	N	Y	N	Y	N	Y	Y(5)	N
Ratsnest	N	N	N	Y	N	Y	N	Y	N	N	N	N
Pad-to-pad router	N	N	Y	N	N	N	Y	N	N	N	Y	N
Mixed track widths	Y	Y	Y	Y	Y	Y	Y	Y	Y	N	Y	Y
Freehand tracks	N	N	N	N	N	Y	Y	Y	N	N	N	N
Camttered corners	Y	Y	N	Y	Y	Y	N	Y	Y	N	Y	Y
Curved tracks	Y	N	N	Y	Y	Y	Y	Y	N	N	Y	Y
Neck down	Y	Y	Y	N	N	Y	N	N	N	N	Y	Y
Number of copper layers	8	2	2	64	8	14	8	6	2	2	2	16
Auto vias	Y	Y	N	Y	Y	Y	Y	Y	Y	N	Y	N
Blind vias	Y	n/a	n/a	Y	Y	Y	Y	Y	n/a	n/a	n/a	N
Buried vias	Y	n/a	n/a	Y	Y	Y	Y	Y	n/a	n/a	n/a	N
Ground/power planes	N	n/a	n/a	Y	N	N	Y	Y	n/a	n/a	n/a	Y
Library												
Screen directory	Y	Y	Y	Y	N	Y	Y	Y	Y	Y	Y	Y
Part preview	Y	N	N	N	N	N	Y	Y	N	N	Y	Y
Editing Features												
Modify track width	Y	Y	Y	Y	N	Y	Y	Y	N	Y	Y	Y
Change pad size/style	Y	Y	N	Y	N	Y	Y	Y	N	Y	Y	Y
Block												
Copy	Y	Y	N	Y	Y	Y	Y	Y	Y	Y	Y	Y
Move	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y
Rotate	Y	Y	N	Y	Y	Y	Y	Y	N	Y	Y	Y
Save	N	Y(2)	N	Y	N	N	Y	Y	Y	Y	N	Y
Output formats												
Dot-matrix printer	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y
Laser printer	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y
HPGL plotter	Y	Y	N	Y	Y	Y	Y	Y	N	Y	Y	Y
Gerber	Y	Y	Y	Y	Y	Y	Y	Y	N	Y	Y	N
N/C Drill	Y	Y	Y	Y	Y	Y	Y	Y	N	Y	Y	N
1) DIP ICs only												
2) Route tracks only												
3) Has netlist conversion utility												
4) Extra cost												
5) Included												

vided. Blocks are easily modified by simply editing the footprint after it's placed on the circuit board. The block doesn't have to be exploded or unlocked for editing; edited blocks can be saved as the original or to a new block name.

While you can use library blocks to hold IC footprints, it's just as easy to create them using the DIPs editor. The process is as easy as calling up the menu, entering the number of pads, and their spacing. The pads come in 11 different sizes and shapes, including surface-mount pads, which are selected via the TYPE button. The chip can be rotated in 90-degree increments prior to placement. (See Fig. 4.) Once a pattern is defined, it may be placed as many times as you wish with a single mouse click.

Tracks come in four widths only, and are drawn by holding down the left mouse button and scooting the mouse. The track is visible during the drawing process, and it can be generated with 45-degree corners for easier fabrication and reduced RFI radiation. Deleting tracks is a simple matter of clicking on the right mouse button. There are no menus to load or navigate.

In fact, PCAD has very few menus. With a couple of exceptions, everything is done using the keyboard. For example, pads are placed on the board using the F5 through F12 keys, track width is changed using <Ctrl><S>, and <Alt><R> redraws the screen. The silk-screen symbols are also placed via the keyboard. Unfortunately, the number of keyboard functions are far too numerous to commit to memory—especially if you don't use the program regularly. You'll want to keep the manual handy, or, better yet, have a chart of the key functions tacked on a nearby wall.

A real annoyance with PCAD is the lack of a zoom function, which prevents a full view of the board. Fortunately, there are two features that make it less bothersome: auto pan which shifts the board up, down or sideways when the cursor bumps against the screen's

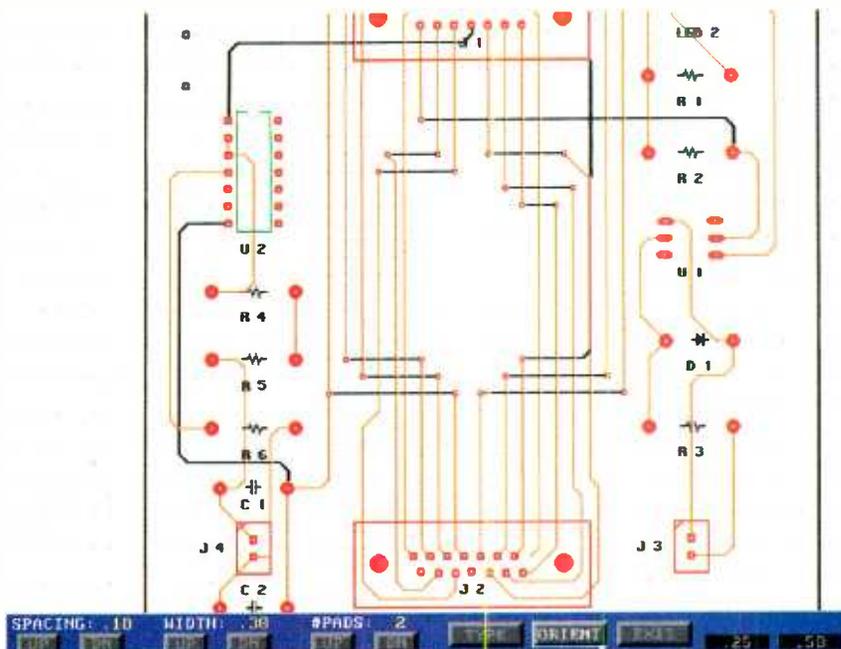


FIG. 4—PCAD'S COMPONENTS ARE MADE using pads, lines, and accompanying nomenclature, which are saved as a block. This is the method we used to construct connectors J1 through J4.

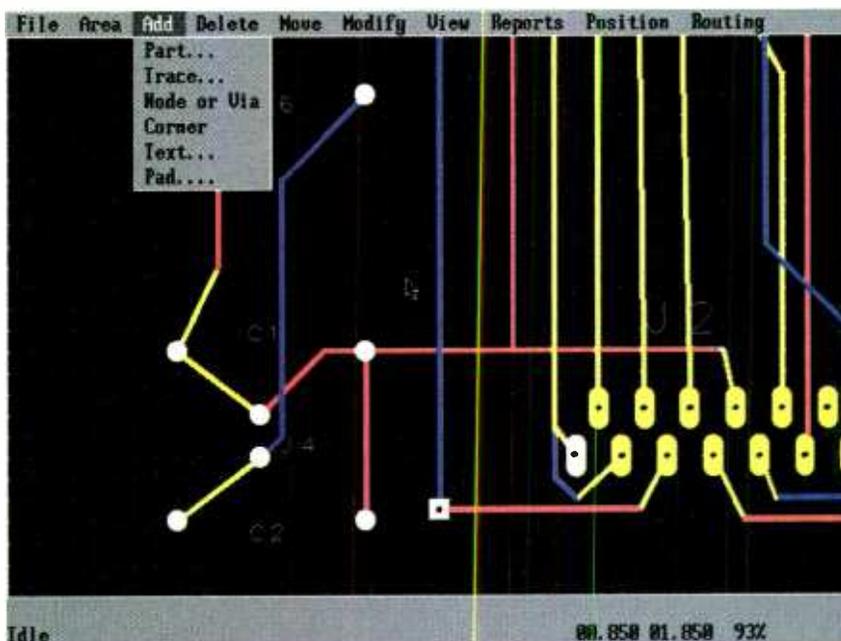


FIG. 5—PC LOGIC IS A STAND-ALONE PC-BOARD LAYOUT program with a pad-to-pad autorouter. Future editions will include a schematic capture companion.

edge, and the ability to display the board at resolutions of 1024 by 768. At 1024 by 768, the visible board area is about 4 by 6 inches, or about one-ninth the total working space. This compares to a viewing area of 3 by 4 inches for standard VGA resolution (640 by 480), which is about one-eighteenth the total working space.

PCAD supports only two out-

put devices: HP LaserJet printers and 24-pin, Epson dot-matrix printers, or their equivalent. Each foil pattern is printed separately, and the images can be rotated and mirrored. Dot-matrix printouts are two times the actual size, and laser prints are actual size. While PCAD has no dedicated options silk-screen or solder-mask printing option, they can

be created by turning the tracks, pads, and characters on and off during printing. For large, complex designs, PCAD can generate Gerber, N/C Drill, and photoplotter files.

Product:	Circuit Layout
Version:	1.1
Price:	\$79.95
Platform:	DOS
Publisher:	PC Logic

Circuit Layout software is a stand-alone PC-board layout program with no companion schematic capture program, although one is reportedly in the works. This \$79.95 program can fabricate two-sided circuit boards up to 10 by 16 inches in size. The program is easy to learn and fairly easy to use, which is good because the 30-page manual is sketchy and way too succinct. Although DOS-

based, Circuit Logic has the look and feel of a Windows program. All operations are accomplished with pull-down menus. Clicking on a menu heading opens up a list of options; to select an option you need to hold down the mouse button and drag the highlight to the desired function. Releasing the button activates the command.

Parts are placed on the circuit board using the Add option (Fig. 5). The Circuit Layout library contains about 50 devices. Despite the low part count, the variety of devices is quite diverse, and includes surface mount devices as well as a hearty helping of DIPs and DB-shell connectors. Unfortunately, the library doesn't have footprints for capacitors or resistors; they are made using pads, which are available from the same menu. Fortunately, it's easy enough to create or modify existing parts using the Parts Editor. For example, the library lacks a 6-pin DIP. No problem. The part was quickly made by deleting two pads from the 8-pin DIP footprint. Once an item is selected from the library, it can be placed repeatedly.

Tracks can be placed manually or by using the pad-to-pad autorouter. Like the Easytrax pad router, the Circuit Layout router can normally find an unimpeded path between two specified pads. Unlike Easytrax, though, it doesn't have automatic via placement. All routing is done on one side of the board. In fact, there is no automatic via support. If you want to change sides, you have to manually add the via, then modify the track using the Modify command. When laying down tracks manually, the track is drawn as a straight line between the two pads, cutting across devices and other tracks. It's up to you to use the Corner and Move commands to route the track or use the expertise of the autorouter to do it for you. A nice feature is the ability to change track width between vias—a feature that mimics necking down for scooting traces between adjacent pads.

Circuit Layout supports only

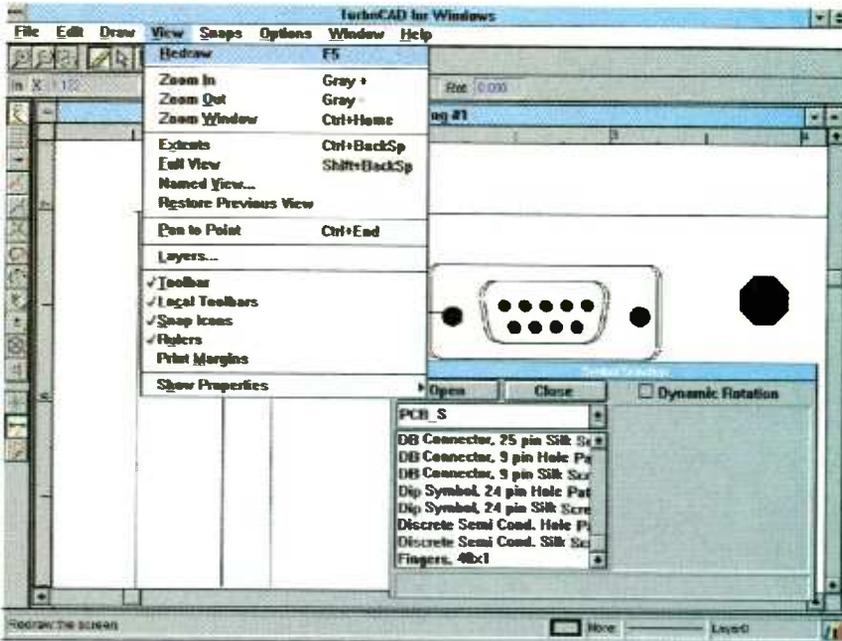


FIG. 6—TURBOCAD'S PRINTED CIRCUIT COMPONENTS are contained in an optional \$29.95 symbol library

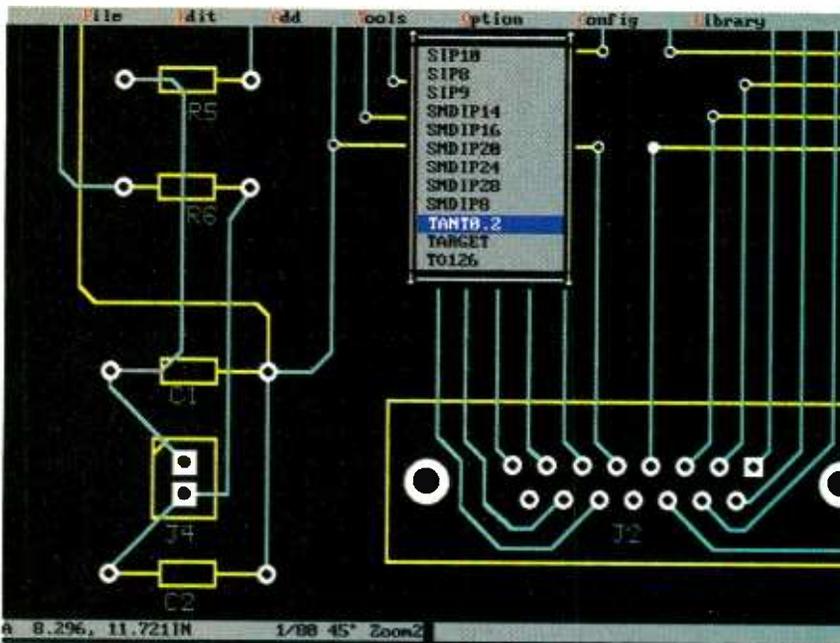


FIG. 7—BOARDMAKER I COMPONENTS are easily accessed from a robust library menu. This is one dynamite program, if you don't mind the working without a net(list).

Epson and LaserJet II compatible printers. In the works, though, is a Gerber and Excellon N/C filer generator.

Circuit Layout is a newcomer to the circuit design arena. The program has been around for only a year, and it has more than a few growing pains. However, the vendor is committed to improving the program and adding companion schematic software to the list of features. This is a serious product that should improve with age.

Product:	TurboCAD for Windows
Version:	2.0
Price:	\$129
Platform:	Windows
Publisher:	IMSI

Unlike schematic-capture programs, which require vast libraries of symbols, most drawing programs are easily adapted for use in printed circuit layout. That's because most component outlines and footprints can be constructed using polylines and a handful of circles, squares, and ovals. In fact, several drawing programs, like TurboCAD, come with a library of PC-board footprints. Priced at a low \$99 (base price), TurboCAD can be used for a wide variety of drawing projects, like business flowcharting and landscaping, as well as designing boards.

The nice thing about generic drawing programs is that they're more flexible than dedicated circuit design packages. For example, TurboCAD supports 16 drawing layers, which can translate into 16 layers of copper, or a dozen layers of copper and four layers dedicated to silk screen, top and bottom solder masks, and drill layout—or any other combination that suits your needs. Drawing programs are also more likely to have a wider zoom range, more primitives (drawing attributes, like polygons and ellipsis), and greater printer/plotter control. Don't expect support for Gerber or Excellon N/C Drill files, though.

TurboCAD's printed circuit components are contained in an optional \$29.95 symbol li-

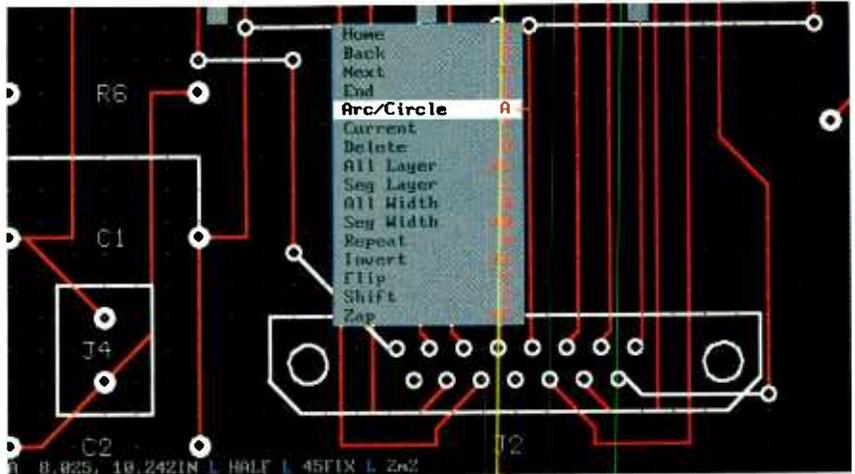


FIG. 8—DESPITE ITS KEYBOARD SHORTCUTS, EASY-PC is comparatively crude, clumsy, and hard to use.

brary (Fig. 6). This library has 11 files, each of which holds a collection of related footprints or pads. For example, TurboCAD's PCB_8 library has 20 resistor footprints, including potentiometers and trimmer potentiometers, and their silk-screen outlines; surface mount pads are found in the PCB_6 library. New symbols are created by binding drawing elements into groups, which are saved as separate files for later import into a new drawing.

Oddly enough, TurboCAD doesn't have a method for scaling line width to a drawing, which means you can't lay down tracks using the line draw function. As the scale of the drawing changes, so does the line, so that it appears the same width no matter what the magnification factor. Instead, tracks are stored in a library as one-tenth-inch-long segments of assorted widths. A track is formed by placing these segments end to end; 45-degree segments are included to create chamfered corners. Fortunately, the process isn't as tedious as it sounds because once a symbol is selected from a library file, it can be placed repeatedly with a single mouse click. It takes but a few seconds to lay down several inches of track. And changing from one layer to another is just a mouse click away. Unfortunately, TurboCAD doesn't support automatic via placement when changing layers, nor does it support blind vias.

Although a larger assortment

of components would be nice (switch and LED footprints are sorely lacking), TurboCAD is extremely easy to use, and well-suited for the task of PC-board layout. However, because it lacks the advanced features you find in most dedicated PC-board layout programs we would recommend it only if you intend to use TurboCAD for other drawing chores when it's not engaged as a PC-board designer.

PC-board Layout with Schematic Draw

These next PC-board layout programs are associated with a schematic capture program reviewed in the September and October 1995 issues of *Electronics Now*. Take note, however, that these programs aren't linked to the schematic capture packages. Instead, they are similar in interface or operation, and are simply bundled together as a convenience and cost saving to the user.

Product:	BoardMaker I
Version:	1.5
Price:	\$95
Platform:	DOS
Distributor:	Ohio Automation

BoardMaker I from Tsien (UK) Limited (Ohio Automation is the U.S. distributor) is a DOS-based package that sells for a low \$95—schematic draw included. Although the schematic draw and PC-board layout programs aren't linked, as they are in schematic capture/PC-board

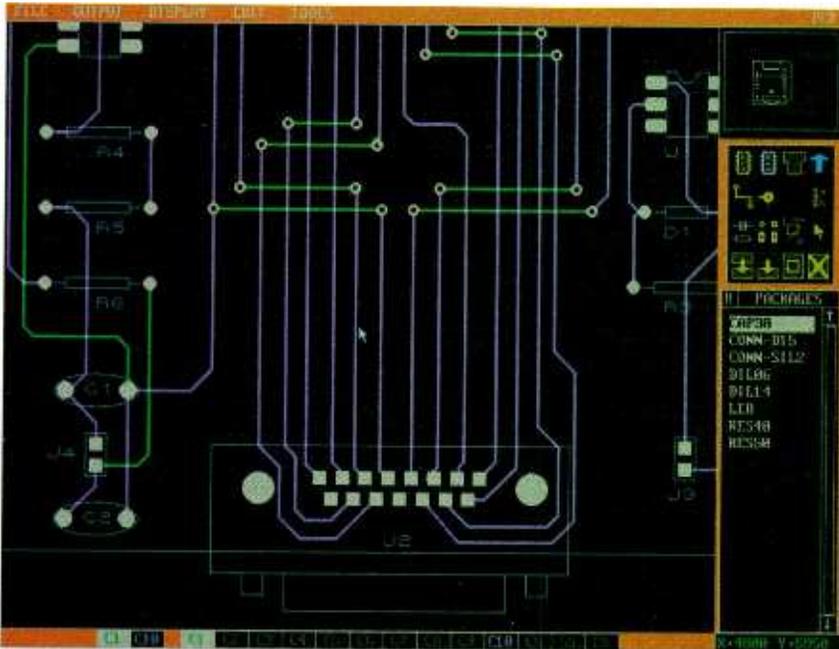


FIG. 9—ONCE YOU GET PAST THE EUROPEAN ICONS, CADPAC II is a very friendly and easy-to-use program. Moreover, the program supports 800-by-600 screens, like the one above, running under DOS, not Windows.

wouldn't expect in a program costing so little—make working with this software a real pleasure. BoardMaker I definitely rates two-thumbs-up.

Product:	Easy-PC
Version:	I0142
Price:	\$145
Platform:	DOS
Distributor:	BSOFT Software, Ohio Automation

Before there was BoardMaker I, the low-cost leader was Easy-PC—the precursor to BoardMaker I. These programs were written by the same person, and in many respects the two are alike. For example, Easy-PC is a DOS-based PC-board layout program with two separate symbol libraries, one for schematic symbols and another for PC-board component footprints and pads. Easy-PC supports up to eight copper layers on boards as large as 17-inches square, there are 128 track widths and pad sizes to choose from, different track widths and pad sizes can be mixed in a design, and the program supports blind vias. The nearly-dual identity is reinforced by the interface, which has the same basic look and feel of BoardMaker I. Yet despite the overwhelming similarities, the two are far from being twins. The first clue is the price: BoardMaker I costs \$95, while Easy-PC costs \$145—\$50 more than BoardMaker I, the up-grade version.

A bigger difference, though, is in the way you perform operations. Compared to most layout programs, Easy-PC's command structure is crude, clumsy, and hard to use (Fig. 8). For example, to place or edit a part, you need to click on a button in the upper left corner. That would be simple enough—if the button were labeled. It isn't, and there are no menu illustrations or tables in the manual that shows what the button does.

Once the menu is open, you are presented with a list of options that lets you place and edit tracks, pads, parts, and text. To place a part, though, you need

layout software, they are built around the same graphics interface and essentially use the same command structure, which makes the package easy to learn. BoardMaker I is easy to use, too, and can fabricate circuit boards up to 17 by 17 inches, complete with up to eight layers of copper plus two silk screen layers.

Basically, BoardMaker I is a PC-board layout program that supports a library of circuit symbols for schematic draw. However, the schematic draw and PC-board layout programs are independent of each other, and you can run only one at a time. An opening menu lets you choose between schematic draw and PC-board layout. The BoardMaker I PC-board symbol library comes with a total of 99 parts that include a good assortment of through-hole devices, plus a handful of SMD footprints. Despite the seemingly small library part count, it contains everything needed to lay out the benchmark board.

New symbols are created with the Library editor, a stand-alone program that's listed as one of the opening menu choices. Like all BoardMaker I programs, the library editor has the same screen setup and command menus.

The components are easily accessed from a pull-down menu (Fig. 7). PC-board components can be rotated and mirrored after placement. Thankfully, the editing commands are easily accessed from seven pull-down menus, and there's a keyboard shortcut for every command or string. Repeat placement is provided.

Because BoardMaker I doesn't support netlist input, all traces have to be routed by hand. However, BoardMaker I supports layer switching, automatic via placement, and blind vias. You can have eight different track widths per layout, ranging in size from 0.002 inch to 0.531 inch, with 128 widths to choose from. Each design can also have 16 different pad sizes. BoardMaker I comes programmed with 15 popular pad sizes, ranging in diameter from 0.010 inch to 0.302 inch, and the ability to choose from 128 pad sizes and styles.

Output can be sent to dot-matrix, LaserJet, and PostScript printers, plus HPGL and DMPL penplotters. Gerber and N/C Drill files are also supported.

This program is extremely easy to learn and use. The ability to zoom and pan during placement and editing—two very powerful features you

to know its exact name as listed in the Appendix of the User's manual. Unlike BoardMaker I, there is no library menu—an oversight that eventually forced us to post the symbol reference chart on a nearby wall. Easy-PC's PC-board layout library comes with 52 symbols (BoardMaker I has 99), which includes a good assortment of connectors, DIPs, SMD, and transistor footprints. New symbols can be created from scratch or by editing existing symbols using a separate library editor program. But you have to quit what you're doing, because only one Easy-PC program can run at a time. Thankfully, the library editor is easier to use than the program itself, because we had to create two devices to build the *Electronics Now* benchmark, and there are no resistor or capacitor footprints. While the library can hold only 100 patterns, there is no limit to the number of libraries you can have. There is a catch: All the symbols for a layout must come from the same library.

Laying down tracks is fairly straightforward, but the fact that you can't see the trace until you click on the endpoints is a real hindrance. Automatic vias are supported, and you can change layers on the fly. All of the menu commands have a keyboard equivalent, which speeds up the drawing process.

Printer and file output is good, with support for dot-matrix, LaserJet, and HPGL printers and plotters. Besides printing individual copper layers, Easy-PC prints top and bottom silk screens, drilling pattern, and solder masks. Also included are utilities that generate Gerber files, N/C Drill, and Photoplotter files, which are used by service bureaus to produce finished PC boards.

When choosing between Easy-PC and BoardMaker I, you have to consider the entire package—both schematic draw and PC-board layout. For schematic draw, Easy-PC wins with a larger component library and the ability to upgrade to Easy-PC Pro, a fully-featured schematic capture and PC-board

layout program. If PC-board layout is a high priority, BoardMaker I wins because it has a larger symbol library and is easier to use.

Product:	CADPAC II PCB II
Version:	2.54
Price:	\$159
Platform:	DOS
Publisher:	R4 Systems Inc.

CADPAC II's PC-board layout program is PCB II, made by Lab-center Electronics and distributed by R4 Systems Inc., of Canada. Its companion schematic draw program is ISIS Supersketch, which was reviewed in the September 1995 issue of *Electronics Now*. When sold together, this dynamic duo costs \$159—only \$10 more than the base version of PC-board II.

PCB II is a DOS-based, entry-level program that can be used to design double-sided boards up to 30-inches square. Once learned, the program is very easy to use, but the learning curve is steeper than most. It's not any worse than a high-end program like Tango, but its European icons and British terminology take a bit of getting used to (Fig. 9). Fortunately, both the schematic draw and PC-board layout programs have the same graphical interface, so you only have to learn it once.

PCB II has almost 300 outlines and footprints stored in three library modules. Over 100 patterns are for general purpose use and the remaining 160 or so are dedicated for surface mounted devices. These two libraries are more or less divided in half, with one containing SMT foot prints for SMD chips, and the other with two-terminal components. There's also an empty module that can be used as a staging area for the assembly of new libraries.

The fastest way to lay out a printed-circuit board using PCB II is to make a list of the components needed, then select them from the appropriate library module, which transfers them in a "shopping" list located on the right side of the screen. Parts are placed on the

WHERE TO BUY

BoardMaker I

Ohio Automation
7840 Angel Ridge Rd.
Athens, OH 45701
(614) 592-1810

CADPAC II

R4 Systems Inc.
1100 Gorman St.
Suite 11B-332
Newmarket, Ontario, Canada L3Y 7V1
(905) 898-0665

Circuit Layout

PC Logic
11 Brook Hollow
Pittsford, NY 14534
(716) 248-9800

DC/CAD

Design Computation
1771 State Highway 34
Farmingdale, NJ 07727
(908) 681-7700

Easy-PC

Easy-PC Pro
BSoft Software, Inc.
444 Colton Rd.
Columbus, OH 43207
(614) 491-0832

Easytrax

Protel Technology, Inc.
2675 Stevens Creek Blvd.
Santa Clara, CA 95051
(408) 243-8143
[ftp://protel.com/http/protel/dostools/easytrax.zip](http://protel.com/http/protel/dostools/easytrax.zip)

EZ-Route Std

Acvanced Microcomputer Systems, Inc.
1460 SW 3rd St.
Pompano Beach, FL 33069
(800) 972-3733

PCAD

Micronics Technology
7709 Skylake Dr.
Fort Worth, TX 76179
(817) 236-5049

PCBoards

PCBoards
2110 14th Ave. South
Birmingham, AL 35205
(800) 473-7227

SuperPC-board for Windows

Mental Automation Inc.
5415 136th Place S.E.
Bellevue, WA 98006
(206) 641-2141

TurboCAD

IMSI
1938 Fourth St.
San Rafael, CA 94901
(415) 454-7101

screen by highlighting a symbol name from the shopping list and clicking on its desired loca-

continued from page 149

PARTY LINE

continued from page 32

bers specify both the desired extension and the ring pattern to use. So to call Station 1, dial any local or long distance number, but substitute for the last two digits the desired extension code (10–19). Refer to Table 1 for the extension number assignments and Table 2 for the ring patterns.

Note that Extensions 00 and 70–99 do not exist, and will always result in a busy signal. Those values can be used to test devices, such as fax machines and modems, that detect busy conditions.

You can also dial a station using just the two-digit extension. Just press the “#” key followed by the two digit extension number. For example, “#50” will ring Station 5 with Type 1 ring pattern. The quick-dial method is perfect for the intercom application, because fewer digits must be dialed.

Calling all stations

You can ring all stations simultaneously by dialing “#0” from any station. To prevent excessive ring current, Stations 1–3 and 4–6 ring in an alternating pattern. The ring pattern follows the industry-standard pattern of a two second ring followed by a four-second silence.

Dial tone silence and recall

Whenever you take a phone off-hook, you immediately receive a dial tone. You can temporarily disable the dial tone by dialing “##”. Hanging up restores normal dial-tone operation.

Whenever you begin a new dial sequence with “*” followed

Extension	Ring Pattern	Remarks
10, 14-19	Normal	Station 1, Normal Ring
11	Long-Long	Station 1, Type 1 Ring
12	Short-Short-Long	Station 1, Type 2 Ring
13	Short-Long-Short	Station 1, Type 3 Ring
...
60, 64-69	Normal	Station 6, Normal Ring
61	Long-Long	Station 6, Type 1 Ring
62	Short-Short-Long	Station 6, Type 2 Ring
63	Short-Long-Short	Station 6, Type 3 Ring

by two digits (00–99), you will hear three short beeps followed by the dial tone. That tone pattern is known as Recall Dial Tone, and is used by the phone company, as well as other phone systems, to indicate that special features are in effect. Party Line uses three recall dial patterns (*67, *61, and *60) for Caller-ID related features. The remaining recall dial patterns are unused. Before we discuss the actual Caller-ID features, we'll provide some background on what Caller-ID is and how it works.

Caller-ID

In case you're not familiar with Caller-ID (CID), it is a popular service provided by the phone company that allows you—before answering your phone—to see the telephone number of the person who is calling you. CID relies on a special 1200-Baud FSK (frequency-shift keying) audio broadcast that occurs between the first and second rings on your phone line. It is a one-way transmission and is sent as a Bell 202 type signal. (If you're interested in the technical details, technical specification number TANNWT-000030 can be obtained through BELLCORE Customer Services, 60 New England Ave., Piscataway, NJ 08854-4196. (908) 699-5800.)

Until recently, many areas offered only the single-message format, which provides the caller's directory number, the time, and the date. A more advanced version uses a multiple message scheme that also includes the name of the caller. Because your phone company provides CID as a custom service, you must pay a small monthly fee to be able to receive it. A special box, which plugs directly into the telephone line, receives and displays the transmission.

CID is widely available in the U.S. and some other countries, including Canada, Australia, and Israel. Unfortunately, not all areas in the U.S. support CID, and several states have prohibited it because they view it as an invasion of privacy. In addition, some foreign countries have adopted incompatible formats. None of those issues affect Party Line operation, because it does not connect to the public switched network. In other words, you can freely use Party Line's CID features, even if CID is not available in your area. Party Line should function with any off-the-shelf CID display, some of which are available for as little as \$25. If you want to use the name-delivery mode, be sure to obtain a compatible unit. (A jumper on the Party Line's PC board enables and disables name-delivery mode.)

The phone number that Party Line transmits in CID format is the same as the phone number used to make the call. For example, if you dial 1-916-985-7219, Station 1 will ring, and the attached Caller-ID box will show that number, along with the date and time and a calling-party name.

TABLE 1—EXTENSION NUMBER ASSIGNMENTS

Station	Extension Range	Remarks
1	10–19	
2	20–29	
3	30–39	
4	40–49	
5	50–59	
6	60–69	
None	09–01,70–99	Not used, always busy

As for the time and date information, Party Line includes a software-based clock. We included the time function so that you can experiment with your Caller-ID products. However, the clock is not designed as a precision timepiece. It may gain or lose a few seconds each day, and the date function must be manually updated every day. (You can set the time and date from the keypad of any attached phone.)

Obviously, the Party Line cannot display real calling-party names. Instead, if your CID display functions in the name and number delivery mode, you'll see one of six stored names, as shown in Table 3, depending on which station made the call. If you dialed using Quick Dial mode, the names shown in Table 3 are not used. Instead, Party Line transmits a message of the form, "STATION X", where X is a number from 1-6 that represents the calling station. That format is perfect for use in the personal-intercom application.

CID Features

Party Line supports three CID-related features: number block, out-of-area, and corrupt checksum. Number block allows the calling party to prevent transmission of his or her name and number information to the receiving station. Activate number block by dialing "*67" before the local or long-distance number. Your CID display will then show a message such as "Number Blocked" or "Private." As with all recall-dial features, the *67 code must be repeated for each call, and may be canceled by hanging up.

The second feature simulates calling from outside your local calling area. When you receive

TABLE 3—CALLER-ID NAMES

Station	Name
1	YOUR NAME HERE
2	MOTHER IN LAW
3	JOHN SMITH JR.
4	ROSIE PORTER
5	ACME COMPUTERS
6	ABBY THOMPSON

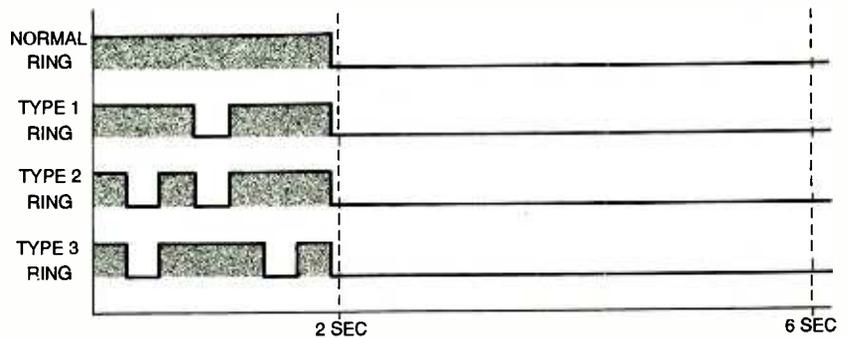


FIG. 1—DISTINCTIVE RING TIMING: Regardless of the ring type, the period of the cycle is six seconds, the last four of which are quiet. Only the ring formats during the first two seconds vary.

such a call via the public switched network, your CID display will show "Out-of-Area," "Number Unknown," or something similar. Activate the out-of-area feature by dialing "*61" before the target number.

Party Line's third CID-related feature allows you to simulate Caller-ID broadcast errors. This feature allows hardware and software developers to test Caller-ID products under simulated noisy line conditions.

The way it works is that a special checksum value is sent with each CID message to help check for errors. Since an incorrect checksum indicates that the delivered message is defective, we can simulate transmission errors simply by deliberately altering the checksum value. To use the corrupt checksum feature, dial "*60" before your local or long distance number. Your CID display box will show an error message or remain blank.

Distinctive ringing

North American readers are familiar with the standard two-on four-off ring pattern. (Other countries use other patterns for their standard ring.) In the past few years, phone companies have started offering new services that depend on different ring patterns. With Party Line you can use and test equipment that responds to distinctive ring patterns.

Not all phone companies call it distinctive ringing. We've seen terms such as Custom Ringing, Ident-a-Ring, Ring-Master, Multi-Ring, RingMate,

SmartRing, Ident-a-Call, Personalized Ring, and others.

Whatever you call it, Distinctive Ringing (DR) allows one physical phone line to respond to two or more different telephone numbers. The catch is that only one number can be active at a time. Nonetheless, DR can be useful for small businesses that want to publish different numbers for voice, fax, and modem, or for households in which teenagers or other family members want separate numbers. The cost of adding DR should be less than adding additional physical lines. With DR active on a line, each dialed number produces a different ringing pattern.

The full ring cycle length is still six seconds, and the four-second silence remains the same. Only what happens during the two-second ring time varies. As shown in Fig. 1, there are three distinctive ring patterns:

- Type 1: Long-Long
- Type 2: Short-Short-Long
- Type 3: Short-Long-Short

Some recent telephone products perform different actions depending on the ring type received. For example, some fax machines automatically use the feature to switch between voice and fax modes. As described earlier, Party Line's DR feature is controlled by the second digit of the two-digit extension number. See Table 2.

How it works

Figure 2 shows a block diagram *continued from page 147*

WAVEFORM GENERATORS

continued from page 38

when R_T has a value of 82 kilohms, as shown.

Sinewave distortion

The circuit in Fig. 5 will generate nonsymmetrical waveforms if the values of R_A and R_B differ. To obtain the purest sine-waves, the circuit must be set to provide waveform symmetry. Figure 6 is a modification of Fig. 5 showing how fixed trimming resistor R_T is replaced by a trimmer potentiometer so that the sinewaves can be adjusted for minimum distortion.

This distortion of this circuit can be as low as 0.8% when it is set to produce fixed frequencies less than 10 kHz. Distortion can be further reduced by modifying the Fig. 6 circuit as shown in Fig. 7. In this circuit, all three trimmer potentiometers, R_3 , R_4 , and R_8 , can be trimmed to obtain optimum performance.

The ICL8038 rarely produces perfectly symmetrical waveforms if organized for variable frequency output applications. Distortion can be 2% or more. It should also be pointed out that the IC tends to run warm. It draws a quiescent current of about 12 milliamperes at 20 volts.

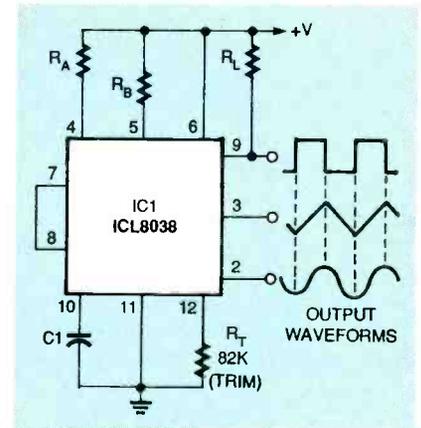


FIG. 5—FIXED-FREQUENCY triangle/sine/squarewave generator.

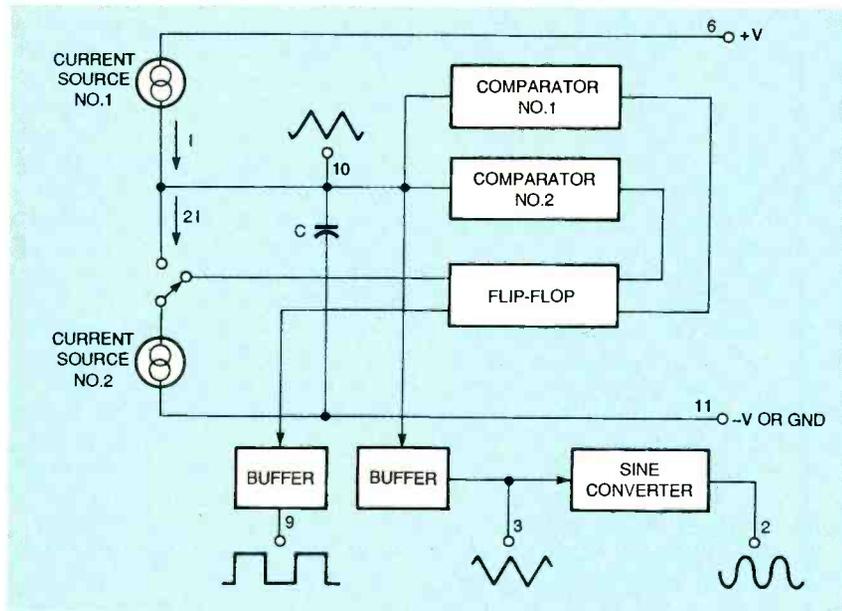


FIG. 3—A FUNCTIONAL DIAGRAM for the Harris ICL8038 waveform generator.

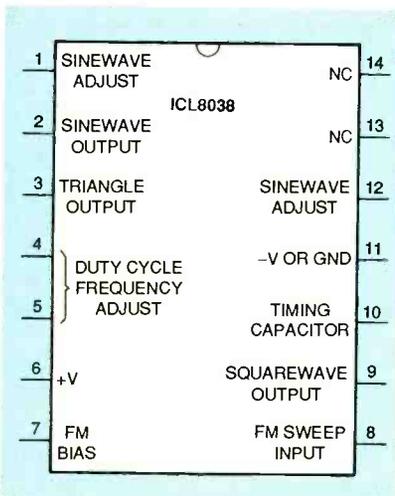


FIG. 4—PIN CONFIGURATION for the Harris ICL8038 waveform generator.

Dual power supplies

The circuits shown in Figs. 5, 6, and 7 are all powered by positive or single-ended power supplies. The three output waveforms all swing about (or are centered on) the value equal to half the supply voltage. However, the circuits can all be powered by dual (positive and negative) power supplies. In those cases, the output waveforms will be centered on the ground bus of the dual supply.

Remember that regardless of the form of the power supply, FM SWEEP INPUT pin 8 is susceptible to unwanted signal noise and hum. The pin should be decoupled with a 0.1 μ F capacitor

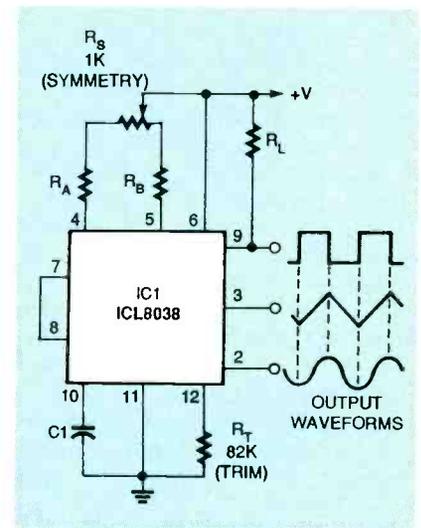


FIG. 6—MODIFIED FIXED-FREQUENCY triangle/sine/squarewave generator.

between pin 8 and the +v pin 6.

The operating frequency of the ICL8038 is directly related to the DC voltage applied between pins 6 and 8. As a result, frequency can be varied or swept by changing this voltage. The frequency can also be modulated by feeding a signal to pin 8. The circuit in Fig. 8, which includes an ICL8083, will function as a manually-controlled, variable-frequency waveform generator. Pin 8 is connected to the wiper of potentiometer R_1 so that the voltage can be varied from two-thirds of the supply voltage to its maximum value.

The lowest frequency is obtained when the voltage at pin 8 equals the supply voltage, and the highest frequency is obtained when the potentiometer wiper is set at two-thirds of the

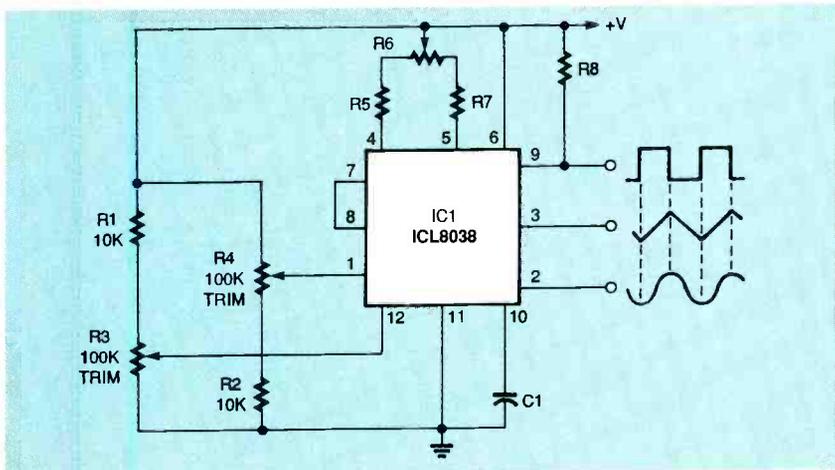


FIG. 7—SQUAREWAVE GENERATOR modified to minimize sine wave distortion.

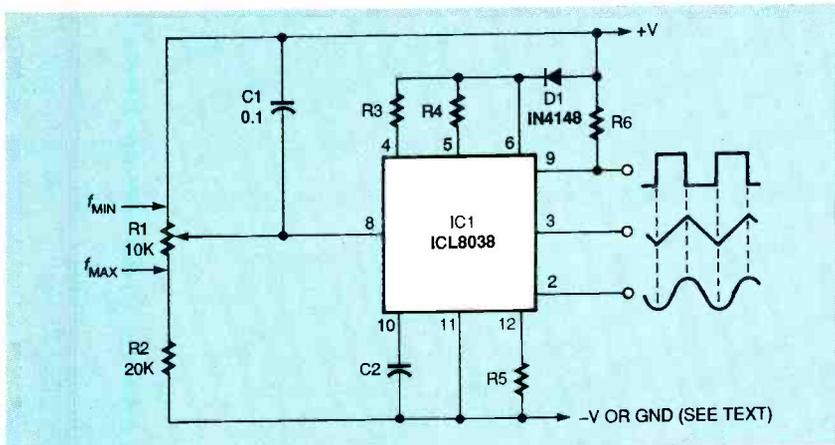


FIG. 8—WIDE-RANGE, VARIABLE-FREQUENCY waveform generator.

to 100 kHz) sine/triangle/squarewave generator formed by combining the circuits in Figs. 7 and 8 and adding an operational-amplifier buffer. To set up this circuit, set potentiometer R4 to its midrange and switch S1 to range 2. Then trim potentiometers R1 and R3 so that the generator can cover the 100-Hz to 10-kHz frequency range by adjusting potentiometer R2.

Next, set potentiometer R2 to give a 1-kHz output, and trim R4 to give a symmetrical squarewave output. Measure the frequency range, and then reset 1 kHz and trim potentiometers R9 and R12 for minimum sine wave distortion. Table 1 gives the frequency ranges that can be obtained from each of the four channel positions of switch S1.

Exar XR-2206

The XR-2206 is an integrated circuit function generator capable of producing stable and accurate sine, square, ramp and pulse waveforms. The output waveforms can be both amplitude and frequency modulated by an external voltage. They can also be frequency-shift


Table 1—Switch Position vs. Frequency

Switch 1 Channel	Frequency range (Nominal)
1	10 Hz to 100 Hz
2	100 Hz to 1 kHz
3	1 kHz to 10 kHz
4	10 kHz to 100 kHz

supply voltage plus 2 volts. This circuit can be varied in frequency over a range of about one thousand to one.


To obtain this range, the highest control voltage on pin 8 must exceed that on pin 6 by a few hundred millivolts. This is achieved by reducing the voltage on pin 6 to about 600 millivolts below the supply voltage with the forward drop of diode D1. However, for optimum frequency stability, both of the circuit's supply voltages must be regulated.

Figure 9 is a wideband (10 Hz

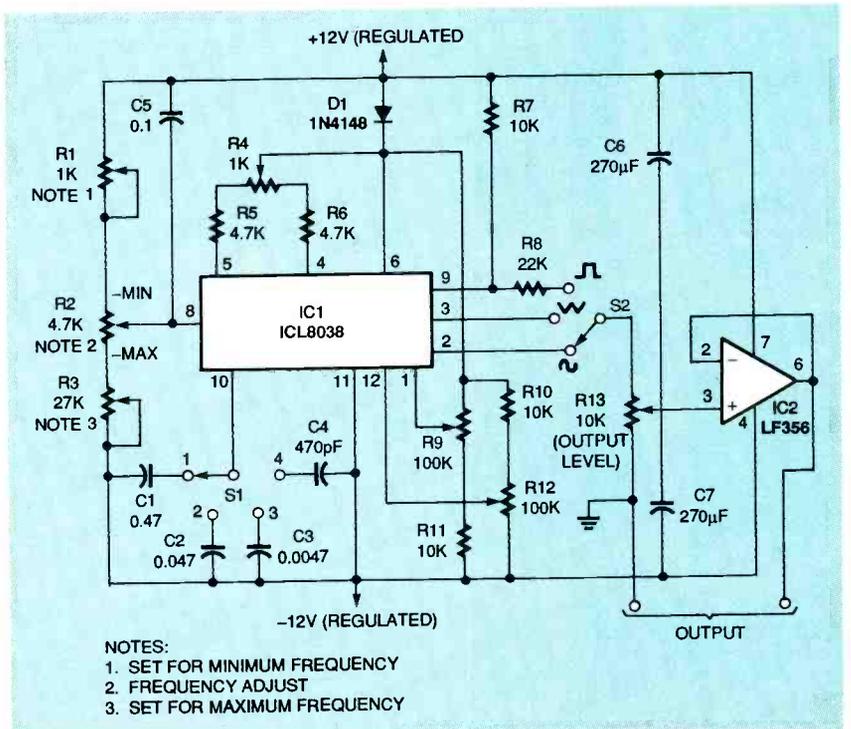

- NOTES:
 1. SET FOR MINIMUM FREQUENCY
 2. FREQUENCY ADJUST
 3. SET FOR MAXIMUM FREQUENCY

FIG. 9—WIDE-RANGE, VARIABLE-FREQUENCY waveform generator with a dual power supply.

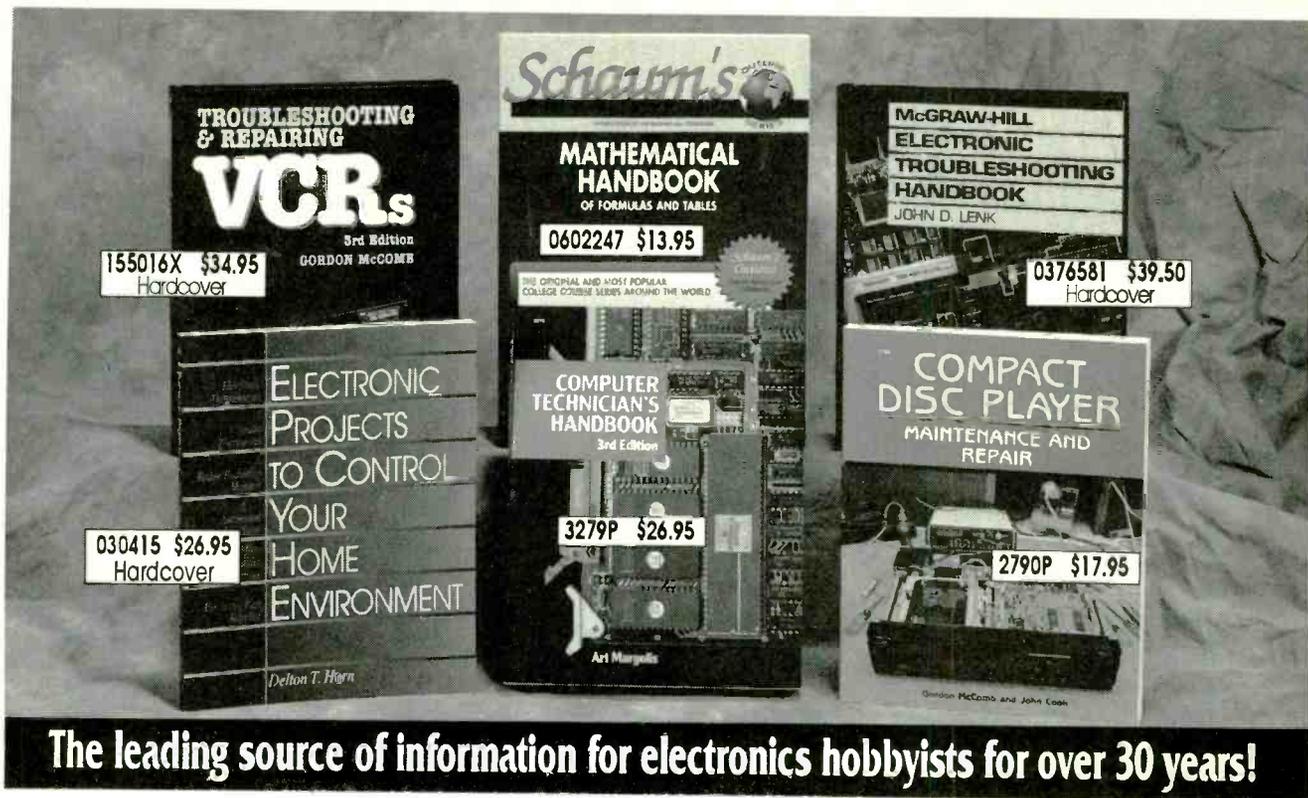

155016X \$34.95
Hardcover

0602247 \$13.95


0376581 \$39.50
Hardcover

030415 \$26.95
Hardcover


3279P \$26.95

2790P \$17.95

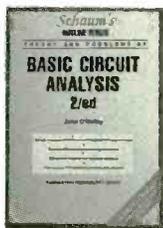The leading source of information for electronics hobbyists for over 30 years!




0478244 \$13.95

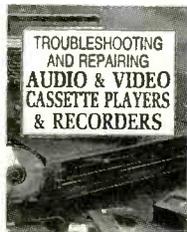


3795P \$19.95




0054088 \$42.95
Hardcover

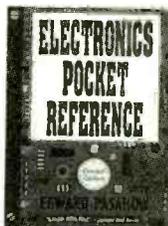


0487375 \$24.95

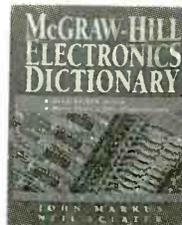

0404348-XX \$49.50
Counts as 2/Hardcover

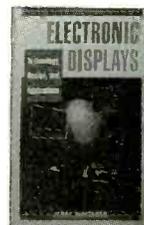


0696217-XX \$55.00
Counts as 2/Hardcover

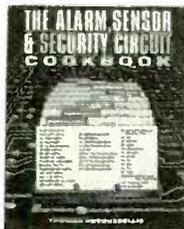


4334H \$29.95
Hardcover



0443017-XX \$50.00
Counts as 2/Hardcover

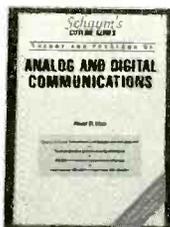


0306362 \$13.95

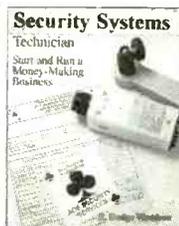


071753 \$19.95




3627P \$19.95

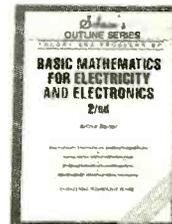

0044392 \$12.95

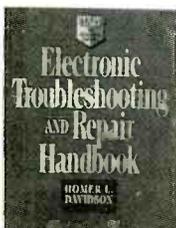


015676X-XX \$69.00
Counts as 2/Hardcover

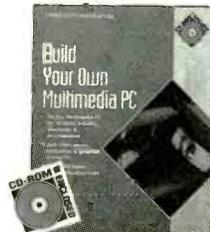

4503P-XX \$36.95
Counts as 2




3475P \$21.95

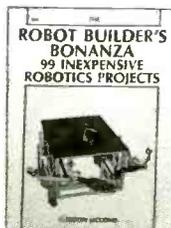

2800P \$17.95



0112738-XX \$45.00
Counts as 2/Hardcover

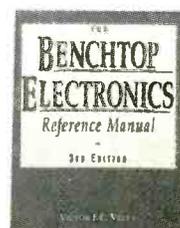


0673764-XX \$54.95
Counts as 2/Hardcover

As a member of the ELECTRONICS BOOK CLUB®... you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.

A shipping/handling charge and sales tax will be added to all orders. All books are softcover unless otherwise noted. If you select a book that counts as 2 choices, write the book number in one box as XX in the next. (Publishers' Prices Shown) ©1996 EBC

5 BOOKS FOR ONLY \$4.95


VALUES TO \$201.90

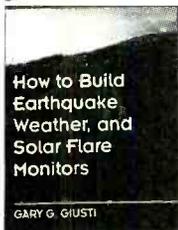


0252092 \$19.95




0410836-XX \$59.50
Counts as 2/Hardcover

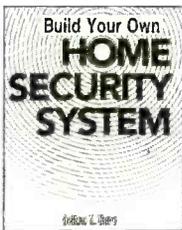

4139P \$16.95

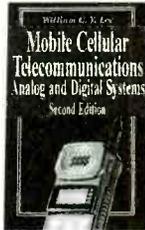


0380899-XX \$60.00
Counts as 2/Hardcover

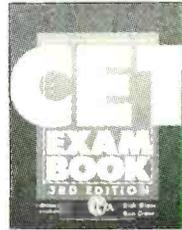


4199P \$17.95



4256P \$18.95

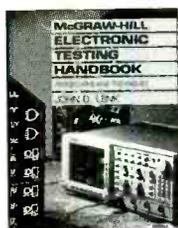


0376026-XX \$45.00
Counts as 2/Hardcover

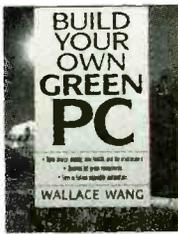


0681562 \$19.95




4360H \$34.95
Hardcover

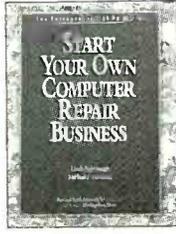


9119018-XX \$32.95
Counts as 2

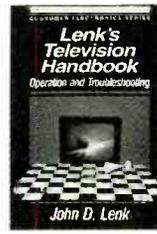

0375178 \$39.50
Hardcover

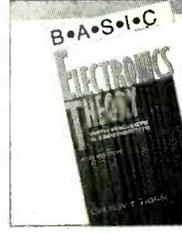


4261P \$24.95

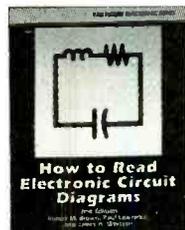

2880P \$15.95




5869284-XX \$46.00
Counts as 2/Hardcover

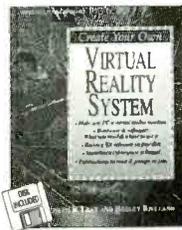


0376514-XX \$44.95
Counts as 2/Hardcover




3669P \$21.95

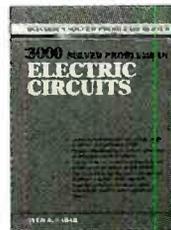

0459363-XX \$21.95
Counts as 2

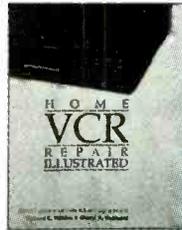


3711P \$19.95

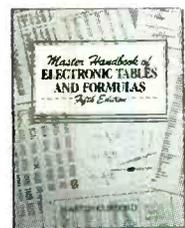

3739P-XX \$24.95
Counts as 2



0240620 \$45.00
Hardcover

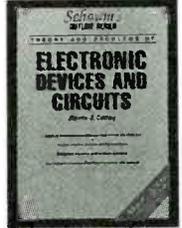


0102740 \$12.95



5869349-XX \$44.00
Counts as 2/Hardcover



4179H \$28.95
Hardcover

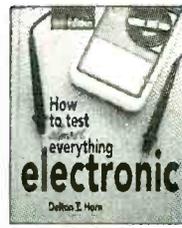

4227P \$15.95

If coupon is missing, write to: Electronics Book Club, A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

Electronics Book Club®

A Division of The McGraw-Hill Companies
P.O. Box 549, Blacklick, OH 43004-9918

YES! Send the 5 books listed below, billing me just \$4.95 plus shipping/handling & tax. Enroll me as a member of the Electronics Book Club according to the terms outlined in this ad. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. A shipping/handling charge and sales tax will be added to all orders.

--	--	--	--

If you select a book that counts as 2 choices, write the book number in one box and XX in the next box.

CHARGE MY: VISA MasterCard AMERICAN EXPRESS DISCOVER ACCT # _____ EXP. DATE _____

BILL ME CHECK OR MONEY ORDER ENCLOSED PAYABLE TO: THE MCGRAW-HILL COMPANIES

NAME _____ SIGNATURE _____ (required on all credit card orders)

ADDRESS/APT. # _____

CITY _____ STATE _____ ZIP _____ PHONE _____

Valid for new members only, subject to acceptance by EBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge and sales tax will be added to all orders. RE196C

PHONE 1(614)759-3666 • FAX 1(614)759-3749
(8:30 a.m. - 5:00 p.m. EST Monday-Friday) (24 hours a day, 7 days a week)

January 1996, Electronics Now

key (FSK) modulated. The IC's operating frequency can be selected externally over a range of 0.01 Hz to more than 1 MHz.

Figure 10 is a functional diagram of the XR-2206 combined with its pinout arrangement diagram. The device includes four functional blocks: a voltage-controlled oscillator (VCO), an analog multiplier and sine shaper, and a set of current switches. It can be powered by either a single or dual power supply.

The VCO produces an output frequency that is proportional to an input current. That current flows in a resistor from the timing terminal to ground. The current switches route current from one of the timing pins to the VCO controlled by a frequency-shift keying (FSK) input pin to produce an output frequency. With two timing pins, two discrete output frequencies can be independently produced for FSK generation applications.

Figure 11 is a function generator circuit that includes an XR-2206 powered by a single power supply. Its operating frequency is inversely proportional to the values of C1 and the combined resistance of resistor R1 and potentiometer R7 in series. Frequency can be varied from 10 Hz to 100 kHz in four decade ranges with the capacitor values given in Table 2. The amplitude of the sine/triangle output can be varied with output-level potentiometer R8, but it can have its maximum value preset by level-control potentiometer R6. The sinewave distortion of this circuit is typically less than 2.5%.

Figure 12 is a modified version of the Fig. 11 circuit that operates from a dual power supply. It is designed to reduce sine-wave distortion to about 0.5% by the adjustment of symmetry potentiometer R3 and distortion-control potentiometer R5. These two controls must be adjusted in unison after the circuit is built, but they need not be adjusted again. The maximum output level of these circuits can be preset by potentiometer R1. It should be set to

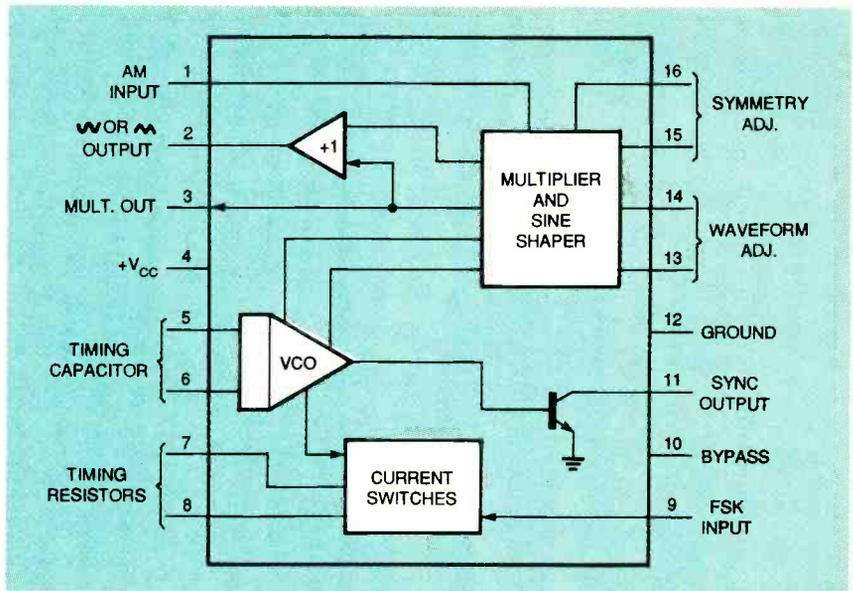


FIG. 10—FUNCTIONAL BLOCK DIAGRAM for the Exar XR-2206 sine/triangle/square-wave generator.

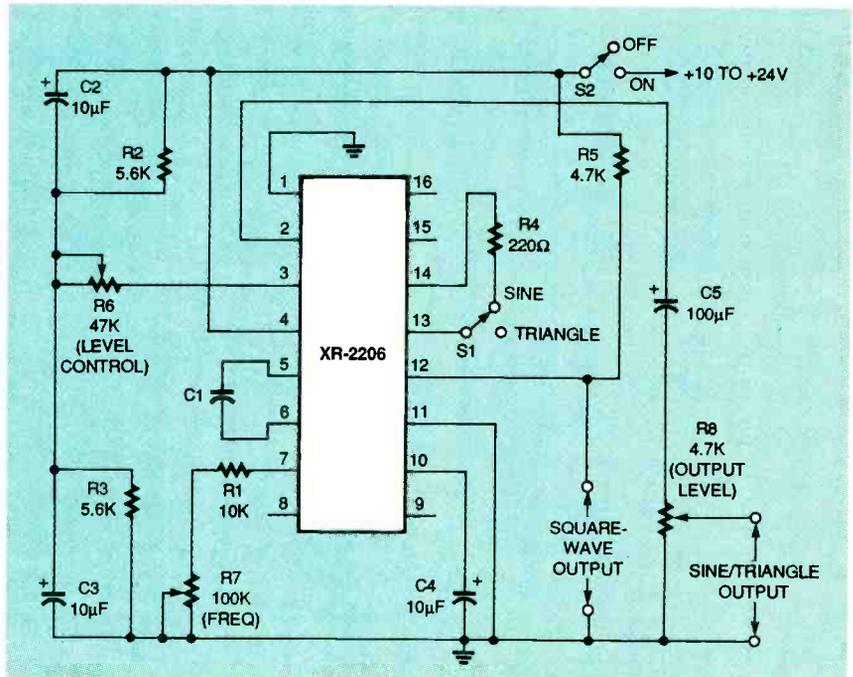


FIG. 11—SINE/TRIANGLE/SQUAREWAVE generator based on the XR-2206.

Table 2—Capacitor Values vs. Frequency

Capacitor C1	Frequency range (Nominal)
1 μ F	10 Hz to 100 Hz
0.1 μ F	100 Hz to 1 kHz
0.01 μ F	1 kHz to 10 kHz
0.001 μ F	10 kHz to 100 kHz

give a maximum output of less than 2 volts RMS to prevent excessive distortion. Table 2 lists

the frequency range of this circuit for each value of capacitor C1, as in Fig. 11.

LC oscillators

The last article in this series discussed the Wien-bridge and twin-T oscillators. Both included resistive-capacitive (RC) tuning networks whose output was limited to several hundred kHz. By contrast, oscillators that include inductive-capacitive (LC) tuning circuits can generate signals from tens of

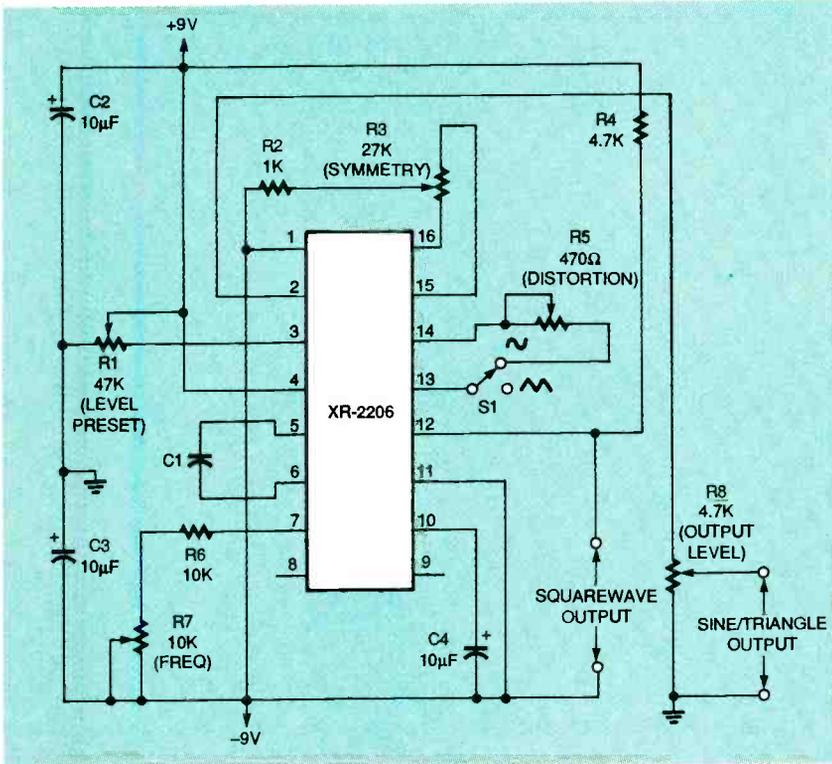


FIG. 12—SINE/TRIANGLE/SQUAREWAVE generator based on the XR-2206 with a dual power supply.

kHz to hundreds of MHz.

A transistorized LC oscillator includes a transistor amplifier and a frequency-selective LC network that provides feedback in accordance with the Barkhausen criteria. Inductive-capacitive networks have inherently high Q or frequency selectivity. Oscillators in this class produce reasonably pure sinewaves, even if the oscillator's loop gain is far greater than unity.

Among the many LC transistor oscillators are the tuned-collector, Hartley, Colpitts, Clapp, and Reinartz oscillators. Figure 13 is a schematic for a tuned-collector oscillator. In this schematic, the base bias for transistor amplifier Q1 is provided by resistors R1 and R2, and resistor R3 that is decoupled by capacitor C2.

The tuned-collector circuit is formed by L1-C1, and the collector-to-base feedback is provided by coil L2 of transformer T1, which is inductively coupled to coil L1. By selecting the phase of this feedback signal, the circuit can give zero-loop phase shift at the tuned frequency. Con-

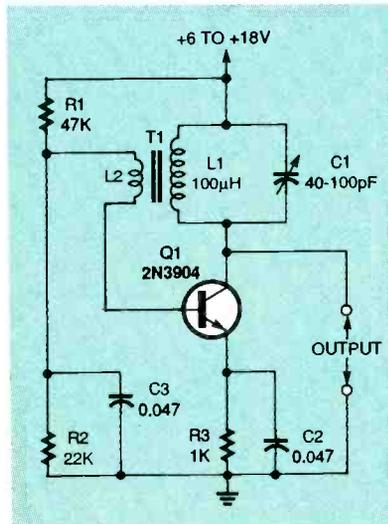


FIG. 13—TUNED-COLLECTOR inductive-capacitive oscillator.

sequently, if loop gain (determined by the turns ratio of T1) is greater than unity, the circuit will oscillate.

The phase relationship between the energizing current and induced voltage of all LC oscillators varies between -90° and $+90^\circ$. It is zero at the center frequency (f) determined by $f = 1/2\pi\sqrt{LC}$. The overall phase shift of the circuit in Fig. 13 is zero.

and the circuit oscillates at this center frequency.

If a tuned-collector oscillator has the component values given in Fig. 13, its center frequency can be varied from 1 MHz to 2 MHz by variable capacitor C1. However, the circuit can easily be modified to operate at frequencies ranging from tens of Hz (with a laminated-iron-core transformer) up to hundreds of MHz.

Hartley, Colpitts, and Clapp

The best-known LC oscillators are the Hartley and Colpitts oscillators, widely used in radio-frequency applications. The Hartley oscillator, as shown in Fig. 14, is a variation of the tuned-collector oscillator shown in Fig. 13. Its frequency-determining resonant tank contains a tapped coil. The collector and base are at the opposite ends of the tuned circuit to provide a 180° phase shift. Feedback occurs through mutual inductance between the two parts of the coil.

In Fig. 14, the collector load coil L1 is tapped at a point 20% along its overall length, and that tap is connected to the oscillator's positive power supply. Inductor L1 acts as an autotransformer, so the signal voltage that appears at the top of L1 is 180° out-of-phase with the signal voltage at its lower (collector Q1) end. The phase of the

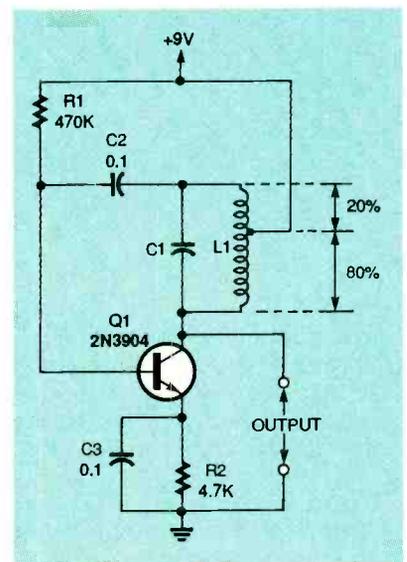


FIG. 14—HARTLEY TUNED-COIL inductive-capacitive oscillator.

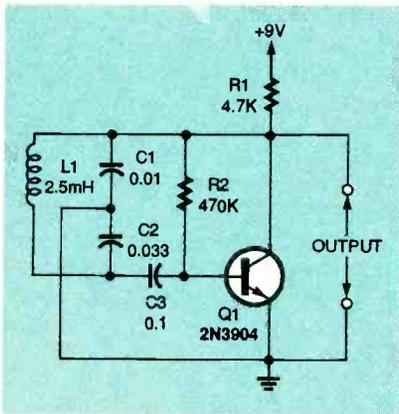


FIG. 15—COLPITTS TUNED-CAPACITOR oscillator.

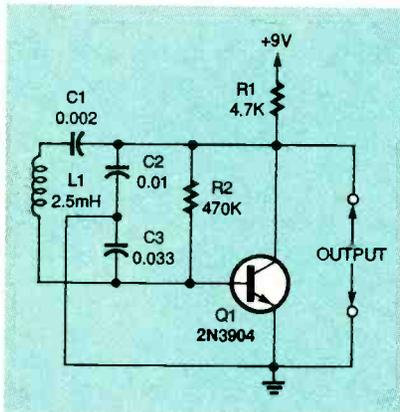


FIG. 16—CLAPP (MODIFIED COLPITTS) LC oscillator.

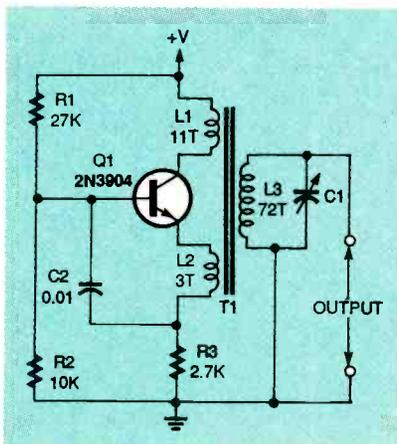


FIG. 17—REINARTZ LC oscillator.

signal voltage at the top of the coil is coupled to the base of Q1 through capacitor C2. The oscillator oscillates at a center frequency set by the values of L and C.

Figure 15 is a schematic for a Colpitts oscillator. It has a frequency-determining resonant tank circuit that includes a capacitive voltage divider. A frac-

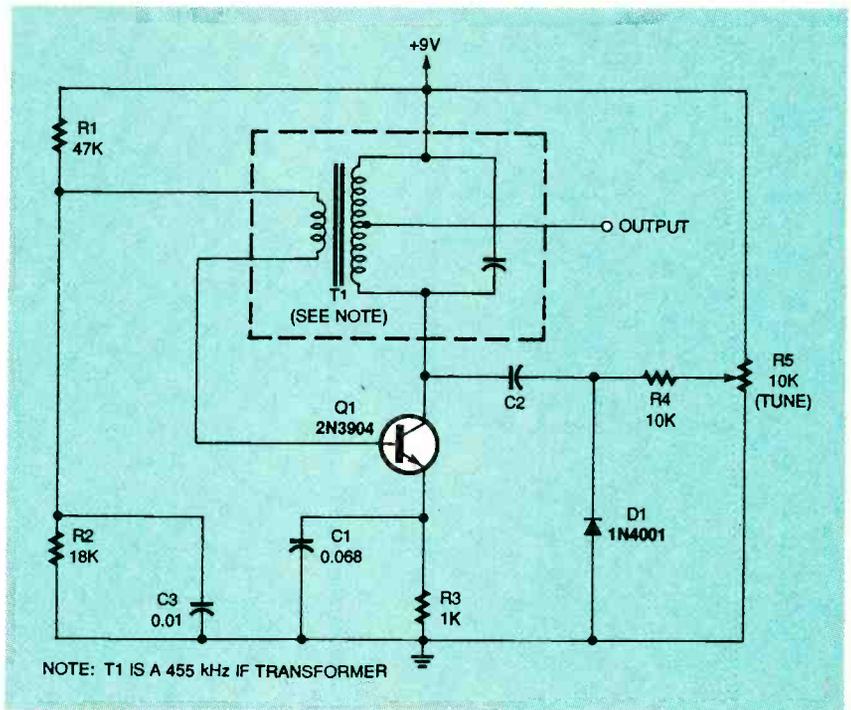


FIG. 18—BEAT-FREQUENCY OSCILLATOR with a silicon diode as the voltage-variable tuning capacitor.

tion of the current flowing in the tank circuit is regeneratively fed back to Q1's base through a coupling capacitor. With the component values shown in Fig. 15, the Colpitts oscillator will oscillate at about 37 kHz.

In Fig. 15, capacitor C1 is in parallel with transistor Q1's input capacitance. As a result, changes in Q1's capacitance due to ambient temperature changes or power supply fluctuations can cause a shift in the oscillator's frequency. This undesirable effect can be minimized and the oscillator's frequency can be stabilized by selecting capacitors C1 and C2 with values that are large with respect to transistor Q1's internal capacitance.

Figure 16 is a schematic for a Clapp oscillator, a modification of the Colpitts oscillator. Its resonant circuit contains a small-value capacitor added in series with the resonant tank coil. The values of that capacitor and the tank coil determine the oscillator's frequency. This modification minimizes the effects of amplifier capacitance on the output frequency.

In this circuit, capacitor C3 is

in series with L1, and its value is small with respect to the values of capacitors C1 and C2. Consequently, the circuit's resonant frequency is determined principally by the L1 and C3 values, and it is not disturbed by variations in the capacitance of transistor Q1. A Clapp oscillator circuit with the component values shown in Fig. 16 will oscillate at about 80 kHz.

Reinartz and cap tuning

Figure 17 is the schematic for a Reinartz oscillator. Regenerative feedback occurs between the collector and emitter of a common-base amplifier transistor Q1. Its frequency is determined by the values of the LC resonant tank circuit, which is inductively coupled to the collector and emitter coils.

The Reinartz oscillator oscillates at a frequency set by the turns ratio of the primary and secondary coils of transformer T1. Figure 17 shows typical transformer turns ratios for oscillation at several hundred kHz. Reinartz oscillators can generate sinewave frequencies up to the UHF region.

Figure 18 is a schematic *continued from page 149*

BUY A NEW COMPUTER

continued from page 28

Operating systems

It's been said that hardware is the computer's brain, while the operating system is the mind—that is, this complex program gives a computer its basic capacity to accept commands and to "learn." (See Table 2.)

The basic operating system of PCs is MS-DOS: a 16-bit operating system developed by Bill Gates, founder of Microsoft, under contract to IBM. To make the computer do what you want under DOS, you have to type in arcane commands in a precise format (neatness counts!). Mistype one character in a long command line, and at best you'll have to retype the whole command—assuming that your DOS typo hasn't flung you somewhere you don't want to be.

Many users struggling with DOS have wondered whether Bill Gates deliberately created such an "unfriendly" system so that he could turn around and sell the world his more friendly overlay, Microsoft Windows. Requiring mouse clicks on graphic icons or word-fields instead of immaculate magic incantations, its operations resemble those of the Macintosh. Windows also gives PCs the capacity to run several applications or work on several files simultaneously (multitasking) by segmenting the screen area. Windows also includes numerous utilities and even some full applications. However, Windows requires a fast processor and considerable RAM (preferably a 486 on up, with at least 8 megabytes of RAM) to juggle these bells and whistles. Nonetheless, Windows has more new and updated applications written for it than any other operating system, making it the vehicle of choice.

About two years ago, Microsoft released Windows NT, a 32-bit stand-alone operating system that dispenses with DOS but in most other respects looks and behaves like regular Windows. The long-delayed Win-

GLOSSARY OF SELECTED COMPUTER TERMS

10Base2—Ethernet local area network using thin coaxial cable wiring. Also called cheapernet and thinnet.

10BaseT—Ethernet local area network using twisted-pair wiring.

Adapter card—A peripheral, such as a modem, built on a printed circuit board that plugs into an empty expansion slot on the motherboard.

AGRAS—An antiglare, antireflection, antistatic screen treatment that reduces glare and reflections from ambient and overhead lighting.

Alpha—A processor from DEC with clock speeds up to 275 MHz.

ANSI—American National Standards Institute. A committee that has developed standards in many fields, including ASCII, terminal emulation, and SQL format.

ARAG—An antireflection, antiglare screen treatment that reduces glare and reflections from ambient and overhead lighting.

ARAS—An antireflection, antistatic screen treatment that reduces glare and reflections from ambient and overhead lighting.

ASCII—American Standard Code for Information Interchange. The interna-

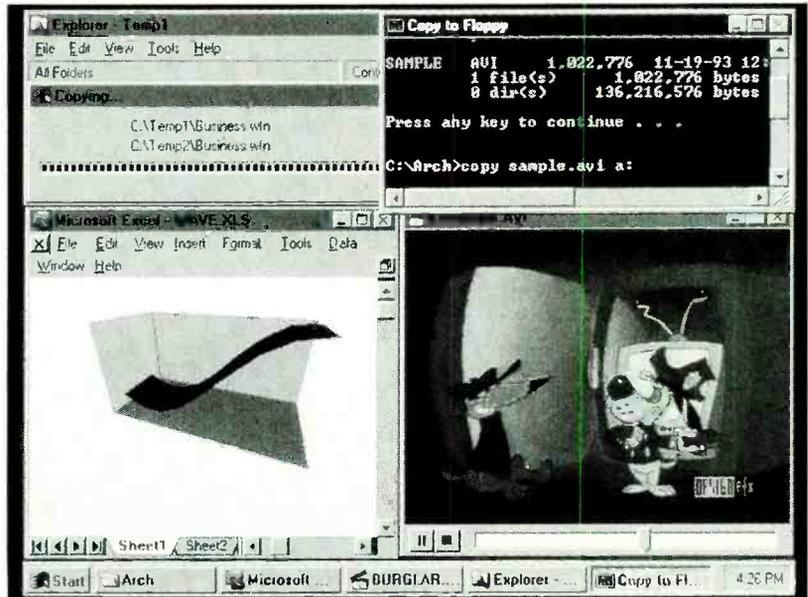


FIG 1— Microsoft's long-awaited Windows 95 was released in late 1995. It includes a redesign of Windows' graphics, and has true "Plug and Play" (called PnP) capabilities.

dows 95, released in August, is a full-bore, 32-bit DOS-free operating system that is replacing Windows in many new off-the-shelf computers. It includes a redesign of Windows' graphics, and has a host of built-in major applications and utilities (see Fig. 1). Applications written specifically for the 32-bit Windows NT and Windows 95 operating systems are plentiful, unlike the long-awaited applications promised for OS/2 WARP.

OS/2 WARP (or simply Warp), much advertised of late, isn't an interstellar drive, but merely IBM's latest foray into the 32-bit operating systems race. It's an update of OS/2, IBM's previous Windows' rival. Whatever its name, it's an umbrella package

that subsumes three operating systems (DOS, Windows and OS/2), but in looks and functioning resembles both Windows and Windows 95. Unfortunately, it only operates at "warp speed" with programs designed specifically for it, which remain few and far between. However, it's expected that Apple may finally waft into Warp, facilitating software sharing between Macs and "warped" PCs.

Parallel processing

Making their desktop PC debut, after serving for many years in the mainframe world, are symmetrical multiprocessor (SMP) systems, which sport dual processors—two CPUs in parallel. In an SMP system run-

tional standard for turning alphanumeric characters and symbols into binary code.

ASP—Advanced Sound Processor. A sound technology introduced by Creative Labs (makers of Sound Blaster) which produces audio quality between that of synthesized voices and wavetables.

ASPI—Advanced SCSI Programming Interface. Developed by Adaptec to improve compatibility among SCSI devices.

associative cache— A cache scheme that saves data to relative memory addresses, as opposed to absolute ad-

ressing. Generally faster than direct-mapped cache.

AUI—Ethernet local area network using 15-pin D-shell connectors. Also called Thick Ethernet.

AVI—Audio video interleaved. Microsoft's standard file format for mixed digital video and audio.

BIOS—Basic input/output system. A small quantity of code used for controlling fundamental computer operations.

bps—Bits per second.

bus—A collection of multiple conductors that act as data paths in a computer along which information is transferred.

bus mastering—A method by which an

expansion card transfers data to another expansion card or other peripheral via the expansion bus without involving the CPU.

cache—Any device, usually RAM, used to temporarily store data for immediate use, to provide faster access.

CAD—Computer-aided design.

CD-ROM—Compact disc, read-only memory. An optical disc that can store up to 680MB of data.

CD-Writer—A drive that lets you create your own CD-ROM discs.

Cheapernet—Ethernet local area network using coax cable wiring. Also called 10Base2 and thinnet.

ning a 32-bit operating system like Windows NT or OS/2, multiple operations can run virtually simultaneously—like the big boys, such as Cray supercomputers. Basically, the two processors divide the work load between them and actually process different parts of the code simultaneously.

Like all faster-than-light setups, it takes special SMP software that knows exactly when and where to split the instructions. In other words, don't expect Excel to run any faster with two CPUs than it does on one. And while most of the ads are for dual Pentium processors, SMP isn't limited to Pentium combinations. (See Fig 2.) For example, a Pentium can be paired with a 486 processor, given the right software.

Memory and performance

While the CPU's speed and type generally establishes the PC's power, other factors such as memory type and size influence how effectively that power is used. There are two kinds of memory: cache memory and main memory.

Cache memory. Cache memory is a small, speedy chunk of RAM that holds the latest data the CPU has used (e.g., the work you're currently doing with an application), allowing immediate access to the data. Without cache, your system would have to consult the slowpoke disk drive constantly. There are two types of cache memory: primary cache and secondary cache. The primary cache is located inside

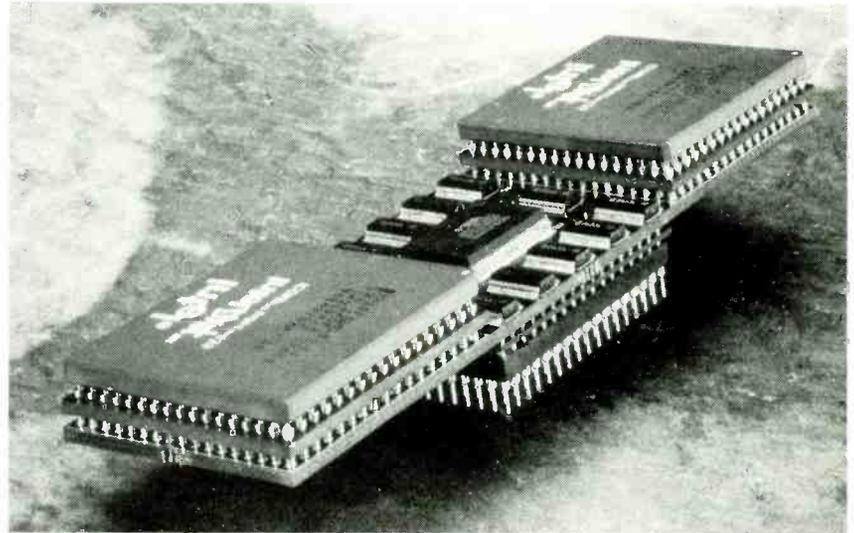


FIG. 2—Symmetric MicroProcessors (SMP) allows two processors to run separate codes at the same time, in parallel. Parallel processing is available as an option in select 486 and Pentium systems. If you wish to upgrade your present 486 system to SMP, Evergreen offers an eloquent solution called the Rev To SMP. It lets you mix and match any combination of 486 processors and/or Pentiums, and has provisions for 256K of secondary cache.

the CPU itself. As pointed out earlier (see Table 1), all CPUs of 486 power and better have a built-in cache of 8K to 32K, depending on the processor. Still, this isn't enough cache for some large applications, so the processors have provisions for what's called secondary cache. The secondary cache is located on the motherboard, and ranges in size from 64K to 1 megabyte. As a rule, the larger the secondary cache, the faster the PC—but not always. It depends on the applications that it is running, so cache size *per se* isn't a good yardstick. Some secondary caches can be expanded, some can't. It's wise to ask about cache upgradability

before you buy in case, next year, you discover that expanding your 128K secondary cache to 512K would greatly improve the performance of your spiffy new CAD program.

You might see an advertisement that says the secondary cache is write-back or associative. Write-back cache holds off writing to the hard disk until there's a lull in CPU activity. Write-through cache, on the other hand, interrupts the CPU to update the hard disk. While write-back is faster than write-through, it's not as safe—data can disappear if the power fails or your romping Rottweiler knocks the power cord out of the wall. Associative cache de-

direct-mapped cache—A cache scheme that saves data to absolute memory addresses for later use.

DMA—Direct memory access. A method where a peripheral or other devices access system memory directly without involving the CPU.

docking station—A desktop platform which has connectors and a power supply for a portable computer so that the portable can connect with a CRT monitor, printer, and other peripherals. Essentially, it turns a portable computer into a desktop computer.

double speed—Denotes a CD-ROM drive that has a data transfer speed of

about 300 kilobytes per second. Triple-speed CD-ROMs run at 450 kilobytes per second, and quad-speed drives run at 600 kilobytes per second.

DTR—Data-transfer rate. A measurement of data throughput. Can be measured in MHz or bits per second (bps).

DTV—Desktop video. Any form of multimedia video that runs on a desktop computer.

DVI—Digital Video Interactive. Intel's standard file format for digital video; requires special hardware.

DX2—Any Intel CPU that runs internally at twice the speed of the motherboard and local bus slot.

eliminates the need for a motherboard cache. Yes, it's a lot faster than motherboard cache memory, but fixed in size. Bottom line: Before you buy, find out what the cache type is and where it's located.

Main memory. Main memory is usually composed of single inline memory modules or SIMMs plugged into the motherboard.

As time passes, and new applications or multimedia packages demand more and more RAM, you'll probably want to expand the size of your main memory. Fortunately, except for the price, that's no big deal—most systems have plenty of room for more SIMMs.

The upgrade price varies. SIMMs come in two versions: 30-pin and 72-pin. The 72-pin variety is more expensive, but is often easier on the wallet because most motherboards that use them allow you to keep using your old SIMMs alongside the new ones, instead of having to replace them all as you generally have to do with the 30-pin variety.

The 72-pin SIMMs are available in two flavors: parity and non-parity. Although parity SIMMs are slightly more expensive, they are recommended because they provide some assurance on the integrity of your data. It is also important to remember that not all motherboards can support the use of non-parity SIMMs.

Expansion slots

Expansion slots are used to plug peripherals into the motherboard (see Fig. 3). Confusion can begin with the phrase *local bus*. In fact, local bus is a bit of a misnomer: local buses are more like expresses, because they run at the same speed as the motherboard when they move data between the CPU and a peripheral (e.g., a video controller). For example, the local bus of a 486SX-25 runs at 25 MHz

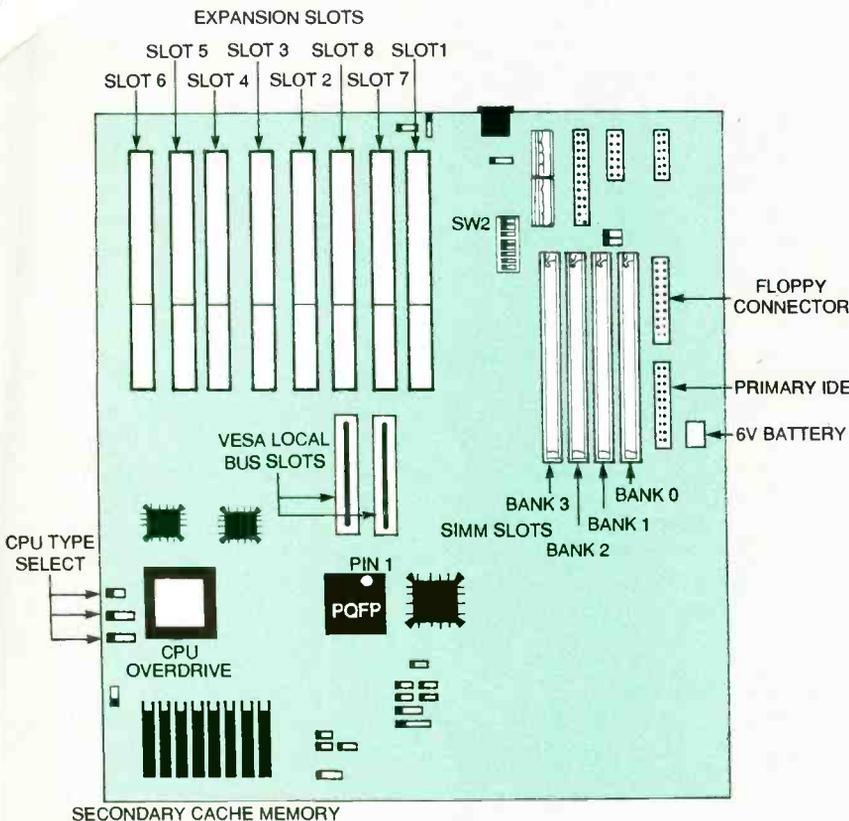


FIG. 3—The typical motherboard has many slots and sockets, starting with ISA/EISA and local bus expansion slots. The slots to the right are for SIMMs RAM, and there are sockets (lower left) for optional secondary cache memory. Many motherboards have a CPU OverDrive socket for upgrading the system.

chip doubler—Any of the 486P
P24 OverDrive family of proc-
CISC—Complex instruction
puting (i486) use instr-
RISC processor
RISC CPU
DOS and
CRT

...ically designed
... math
... Transfer
... ate
...ory,
... low Pen-
... This new
... sor has 256K
... ache built right
... ip, which all but

DX4—Any Intel CPU that runs internally at three times the speed of the motherboard and local bus slot.

EISA—Extended industry-standard architecture. An aging 32-bit motherboard slot that's backward compatible with ISA (see ISA).

emulation mode—A software interface used by Alpha and other CPUs that interprets Windows and DOS instructions and converts them into the processor's native language.

Energy Star—A set of guidelines developed by the Environmental Protection Agency (EPA) to reduce power consumption in computer devices.

enhanced IDE—A recent upgrade of the popular IDE standard that runs at 16.7 MB per second and supports drives as large as 8.2GB.

enhanced parallel port—A parallel port capable of sending and receiving data at speeds approaching 1MB per second (compared to 80KB per second for a standard parallel port).

Ethernet—The most popular local area network (LAN) data transfer protocol. The most common versions are thinnet (10Base2), which uses coaxial cable, and 10BaseT, which uses twisted-pair telephone wire.

expansion slot—Any slot on the moth-

erboard
slot
inst
grade
flat sc
that has
distortion
ically fou
monitors.
fps—Frames
speed at which
are displayed.
FPU—Floating
coprocessor that's

and the local bus of a 486DX2-66 runs at 33 MHz. In contrast, most standard buses (ISA or EISA) run at a leisurely 8 MHz (see Table 3). Obviously, faster is better—but only if you really need the speed. For example, you gain nothing by plugging a 9600-bps modem card into a local bus slot, but if you plug a Windows accelerator video card into the same slot your graphics will gallop.

EISA/ISA. The original PC slot was an 8-bit ISA connector designed for the 8088-based IBM PC. In 1984, the ISA slot was upgraded to 16 bits for use in the IBM PC AT. Today's ISA slot is both 8- and 16-bit compatible, and is supported by the majority of board peripherals on the market.

The higher-priced EISA slot is an enhanced version of ISA that's mainly used in network servers. The best version has a 32-bit interface, and does *bus mastering* (a technique that lets two peripherals talk to each other without involving the CPU). Unfortunately, EISA has never received much support. Although ISA cards will run in EISA slots, they don't get any faster—so to increase your speed, you have to spend the cash to replace your current ISA peripherals with EISA equivalents. This isn't smart even if you can afford it: Even when you use EISA peripherals, the speed increase is noticeable only with a system that does a lot of I/O (input/output), such as a network file server.

VL-Bus and PCI. Both the

TABLE 3—BUS COMPARISONS

Expansion Slot	Data Bits	Typical Bus Speed	Data Transfer Rate
ISA	8/16	8 MHz	20 Mbytes/sec
EISA	32	8 MHz	33 Mbytes/sec
VL-Bus	32	33 MHz	120 Mbytes/sec
PCI Local Bus	32/64	66 MHz	150 Mbytes/sec

VL-Bus (sometimes called VLB or VESA Local Bus) and PCI are local bus slots. Of the two, the newer PCI bus has become much more popular. A few systems claim to support both VL-Bus and PCI but there are apparently problems when the two technologies are mixed. The combination should be avoided unless you're deeply attached to your obsolescing VL-Bus expansion cards.

Although some advertisements make it sound as if these are 64-bit buses, both VL and PCI are still just 32-bit slots. Some Pentium machines do include 64-bit slots, but many vendors still plug the older and cheaper 32-bit cards into them unless the buyer insists on 64-bit models (usually a video board). With 32-bit cards, you get 32-bit performance despite the 64-bit architecture.

Device interfaces

Instead of connecting to the system via a motherboard slot, such important devices as your hard disk and CD-ROM interface through an IDE or SCSI bus.

SCSI. Installing a SCSI interface is no treat, but the end result (when you finally get it

working) can be worth the investment. SCSI offers the advantage of handling up to seven devices—hard disks, CD ROMs, tape backups, and more—although it's not necessarily easy to make all these devices work harmoniously together. Controllers can be cascaded for a total of 28 devices (see RAID). SCSI interfaces come in three different versions, SCSI-1, SCSI-2, and SCSI-3.

SCSI-1 has an 8-bit bus running none-too-fast at 5 MHz, providing a top *data transfer rate* (DTR) of 5 megabytes per second. The popular SCSI-2 is similar to SCSI-1 except for a faster clock rate and/or wider bus. Adding to the confusion, it's divided into fast SCSI-2 and fast/wide SCSI-2. Fast SCSI-2 has a 10-MHz clock running on an 8-bit bus for a DTR of 10 megabytes per second. With fast/wide SCSI-2, the clock is still 10 MHz, but the bus is 16 bits wide which provides 20 megabytes per second DTR. Especially if you're heading for multimedia, the 16-bit SCSI card and SCSI-2 drives are generally considered to be worth the extra cost and hassle because they give faster performance and better compatibility.

to accelerate certain mathematical operations—generally those associated with spreadsheet and CAD applications.

IDE—Integrated drive electronics. The most popular type of hard-disk drive (see text for enhanced IDE).

Internet—A worldwide network of computer networks.

ISA—Industry-standard architecture. The most popular motherboard expansion slot. It typically runs at 8 MHz, which is a lot slower than a local bus slot.

KB/s—Kilobytes per second.

LAN—Local area network. Any inter-office, computer-to-computer connection that lets users share files and data.

LCD—Liquid-crystal display. The display media used for portable computers. It comes in three versions: passive, active, and dual-scan. (See text for details.)

LIS—Lithium-ion storage. The newest technology of batteries used in portable computers. Has a longer life and higher power-to-weight ratio than Ni-Cd or NiMH batteries.

local bus—Any motherboard slot that runs at the interface speed of the CPU. For a 486DX2-66 system, the local bus speed is 33 MHz.

memory cache—Fast RAM used to store frequently-used instructions or

data. There are two types: primary cache, which is built into the CPU, and secondary cache installed on the motherboard.

MIDI—musical-instrument digital interface. A standard created by musical instrument manufacturers for the digitizing of music.

MO—magneto-optical. Any disk drive, including floptical, that uses a laser to write and to read a magnetic disk. Popular sizes are 3½ and 5¼ inches.

MPC—Multimedia PC. A specification that suggests the minimum hardware requirements for multimedia. (See Table 6.)

However, a special 68-pin cable is required for fast/wide. And while SCSI-2 is backward compatible with SCSI-1, you must have a fast/wide hard disk to run at top speed. A third version of SCSI is SCSI-3, which is not the same as fast/wide SCSI-2, and not popularly supported. The confusion here is that Quantum makes a SCSI-3 hard disk that some salespersons assume is SCSI-2 compatible—but it isn't.

IDE. Most new PCs come with an IDE interface built right into the motherboard. IDE devices remain more popular than SCSI devices because they're cheaper and easier to install.

Alas, IDE is a lackluster performer: It's basically meant to drive just a hard disk (not such additional peripherals as CD-ROM) and can only handle drives up to 528MB. Many PC users prefer the more expensive SCSI interface because of the latter's higher throughput, higher drive capacity, and the ability to daisy chain peripherals—not to mention its capacity to run multimedia applications at bearable speed.

However, the newly-developed *enhanced IDE* is poised to give SCSI a good run for its money,

with its easy, affordable "plug and play" operation (see Table 4). This interface goes by several names: it's also called Fast ATA and High Performance ATA (depending on the manufacturer), but its most common name is EIDE. It has a data throughput of 16.7 megabytes per second, nearly that of fast/wide SCSI-2, it can support hard disks as big as 8.2 gigabytes, and one controller can handle four devices (instead of just two). For optimal performance, EIDE must be built into both the system and the drive, so keep this in mind when buying a system. You can't mix EIDE with IDE without losing your performance advantage: Plug a standard IDE hard disk into an enhanced system and it'll slow down the system to its own sluggish pace.

Monitors

The display (monitor) is your window on your PC's activities. You can use an old 14-inch VGA screen, but a superVGA color monitor is what it takes to enjoy a high-powered new computer—especially if you're buying into multimedia. Display terminology is especially bewildering; the most common terms you'll encounter follow. (Those not

discussed can be found in the glossary).

The most popular term is "flat square," which describes the shape of the screen—although not very accurately. Generally found in monitors of 15 inches and larger, a flat-square CRT is neither flat nor square, but it's flatter and squarer than the spherical screen of a typical 14-inch monitor.

Most monitors have some kind of antireflective screen treatment to increase clarity by reducing glare and reflections from overhead lighting. The most common treatment is silica, followed by antireflection, antiglare (ARAG); antireflection, antistatic (ARAS); and antiglare, antireflective, antistatic (AGRAS). While it hasn't been proven that monitor emissions constitute a health risk, most new monitors comply with the Swedish Government's Department of Labor (SWEDAC) MPR II safety specifications for emissions.

Some monitors offer interlaced video mode, which draws the even lines on the screen in one pass and the odd lines on the next. Others monitors are non-interlaced, which means that all the lines are drawn sequentially from top to bottom. The potential downside is a constant headache-making flicker that is created because the top of the picture starts to fade by the time the bottom of the picture is being drawn. Flicker in noninterlaced monitors can be reduced by increasing the refresh rate (see Table 5).

TABLE 4—DRIVE INTERFACE COMPARISON

	Enhanced IDE	SCSI-1	SCSI-2 Fast	SCSI-2 Fast/Wide
Bus Width	8/16 bits	16 bits	8 bits	16 bits
Data Transfer Rate	8 MB/s	16.7 MB/s	5 MB/s	10 MB/s
Largest Hard Disk	528MB	8.2GB	10GB	10GB
Number of Drives	2	4	7	7

MPEG—Moving Picture Experts Group. Video compression schemes (MPEG 1, MPEG 2) used to reduce the size of animated video files.

MPR II—A rating established by Swedish government (SWEDAC) that limits potentially harmful monitor emissions to a safe level.

multimedia—A term used to describe any application that involves CD-ROM, sound, or motion video.

NI—Noninterlace scanning. A video mode that draws images on the screen one line after the other, as opposed to interlaced, which draws the even lines in one pass and the odd lines on the next

pass. Has less flicker than interlaced scanning.

NIMH—Nickel-metal-hydride. The most popular rechargeable battery used in portable computers. It has a longer life than a nickel-cadmium battery and a faster recharge time (about 1 hour compared to 3 hours and more).

Nx586—A low-cost Pentium alternative from NexGen.

OverDrive—Any CPU upgrade chip that boosts the speed or power of 486, DX2, or Pentium system. While OverDrive is a trademark of Intel, other vendors make comparable upgrades that salespersons often mistakenly call

OverDrives.

PCI—The most popular local bus standard.

PCMCIA—Personal Computer Memory Card International Association. The portable computer's equivalent of an expansion slot; uses peripherals the size of a credit card.

Pentium—Intel's high-speed successor to the i486.

Photo CD—A technique developed by Kodak that digitizes photographs and stores the files on a CD.

PowerPC—A processor developed by the collective minds of Apple, IBM, and Motorola that is compatible with both PC

The video display adapter is essentially an adapter card that plugs into a motherboard expansion slot. Most video cards sold today contain a Windows accelerator—a video controller chip that speeds up Windows-based applications. Some of these cards use VRAM for even faster response time, and all use a RAMDAC (sometimes called video DAC) to convert the digital signals into screen colors. The number of bits supported by the RAMDAC determines the number of screen colors. An 8-bit RAMDAC can do 256 simultaneous colors, while a 24-bit RAMDAC does 16.7 million colors. Many highly-pictorial CD-ROM programs recommend using the higher RAMDAC; in addition, this option allows users to decorate their on-screen "desktops" in subtle customized colors.

Upgrading

Many systems are advertised as upgradable—which is mainly true. Virtually all 486SX sys-

tems can be upgraded to 486DX2 status, and many 486DX2 systems can be converted into low-end Pentium compatibles.

CPU Upgrades. Virtually any 486-based PC can be upgraded from a lower to a higher CPU using an OverDrive chip. For example, it's easy enough to turn a 486SX-25 into a 486DX2-50 speedster or a 466DX2 into a 486DX4 with a simple brain (CPU) transplant. New on the scene are Pentium OverDrive chips that claim to turn 486DX2 systems into Pentium-compatibles. Does this mean that one day you could pop a new Pentium chip into your old 486 and give it a new lease on life? Well, not exactly. A 486 motherboard is just a 32-bit springboard, and the Pentium is a 64-bit processor. According to benchmark tests, Intel's Pentium OverDrive upgrade rarely delivers Pentium performance. Instead, you're far more likely to experience 486DX4-75 performance.

In some systems, you have to remove the old CPU from the motherboard to replace it with a faster one. Other machines include an empty socket just waiting for a new CPU. Removing a CPU from a standard socket on the motherboard requires a special tool that looks and works a lot like a small pry bar—and the process also requires great care to avoid damaging the motherboard. Be prepared to set some jumpers, too. Even when there's an empty motherboard socket for the new CPU, substantial force may be needed to insert the new chip, but if you apply too much pressure you can damage the motherboard or the OverDrive's pins.

ZIF Socket. A better solution is the ZIF or zero-insertion-force socket. (See Fig. 5.) ZIFs are two-layer sockets that start with a row of loose-fitting metal connectors mounted in a base plate. Just below the socket's base plate, surrounding these connectors, is a sliding plate drilled with holes that match

TABLE 5—VIDEO CONSIDERATIONS

Monitor Requirements			Video RAM Size vs. Screen Colors			
Resolution	Refresh Rate	Horizontal Scan	512 K	1 MB	2 MB	4 MB
		Frequency				
640 by 480	60 Hz	31.5 kHz	65,536	16.8 million	16.8 million	16.8 million
	72 Hz	39.4 kHz	65,536	16.8 million	16.8 million	16.8 million
800 by 600	60 Hz	38 kHz	256	65,536	16.8 million	16.8 million
	72 Hz	48 kHz	256	65,536	16.8 million	16.8 million
1024 by 768	60 Hz	48 kHz	16	256	65,536	16.8 million
	72 Hz	60 kHz	16	256	65,536	16.8 million
1280 by 1024	60 Hz	64 kHz	4	16	256	65,536
	72 Hz	76 kHz	4	16	256	65,536

and Mac software.

R4000/R4400—Two different processors, the R4000 and R4400, from MIPS that run at speeds up to 150 MHz.

RAID—Redundant array of inexpensive drives. RAID refers to any of several methods where two or more disk drives are used to improve speed and/or reliability of a system. Generally used for networks.

RAMDAC—Random access memory, digital-to-analog converter. The chip that converts digital signals into screen colors. An 8-bit RAMDAC generates 256 simultaneous screen colors, and a 24-bit RAMDAC can do 16.8 million col-

ors.

RISC—Reduced instruction set computing. RISC instructions are very simple and short, which allows the processor to run faster than CISC processors (see CISC).

SB compatible—Sound Blaster compatible. A de facto standard for interfacing the sound card with a CD-ROM drive.

SCSI—Small computer systems interface. Pronounced "scuzzy," SCSI is the fastest interface for hard disks. It's also the most expensive.

SIMM—Single in-line memory module. The staple of main memory, the SIMM

comes in two versions, 30 pin and 72 pin.

SMP—Symmetrical multiprocessor. A technology that uses more than one processor in a single system.

superscalar—An architecture that lets the CPU execute two or more instructions per cycle as opposed to one instruction per cycle.

SX, SX2—An Intel CPU that's identical in every way to its DX and DX2 counterpart, except that it doesn't have a built-in math coprocessor.

TFT—Thin-film transistor. An active semiconductor device built into the screen of an LCD panel to improve



FIG. 4—Enhanced IDE can be added to existing systems by plugging in an EIDE controller card, like the Future Domain card above. These controllers support 16-bit multimedia devices, like IDE CD-ROM drives and IDE tape drives.

those of the socket. When the bottom plate is moved sideways using a lever, the connector holes reduce in size and clamp around the chips pins, making electrical contact and firmly holding the chip in place. Throwing the lever in the opposite direction releases the pressure for effortless chip removal.

Flash BIOS. An annoying thing about buying a state-of-the-art PC is that today's hot product is next month's (or even next week's) antique. The computer you bought at retail two days ago could actually be two versions behind what the company is shipping to vendors today.

To alleviate the problem, several vendors are equipping their systems with flash BIOS. In a nutshell, flash BIOS is a reprogrammable EEPROM device that lets you load the latest BIOS instructions into your PC via a simple program. These programs can be obtained directly from the vendor, or are oftentimes found on popular online services such as CompuServe and America Online.

Multimedia

The fastest growing sector of the PC market is multimedia—a term that generally refers to applications that make special use of audio and video. Popular multimedia applications in-

clude games, computer music, animation video, and reference and educational materials. The latter applications make optimal use of the "laser technology" information storage mentioned in IBM's ad: Instead of cluttering your house with multi-volume, weighty reference tomes, you get a 10-volume reference set stored on one or two tiny discs—with full-color, animated illustrations and sound effects, too.

At the heart of any good multimedia system is a CD-ROM. However, CD-ROM drives vary considerably in performance. For one thing, they come in different speeds. Single-speed CD-ROMs are so slow that their cost savings aren't worth the perpetual aggravation. Double-speed drives, which have a data-transfer rate of 300 kilobytes per second (kB/s). The more expensive drives run at triple speed (450 kB/s) and quadruple speed (600 kB/s). Sextuple-

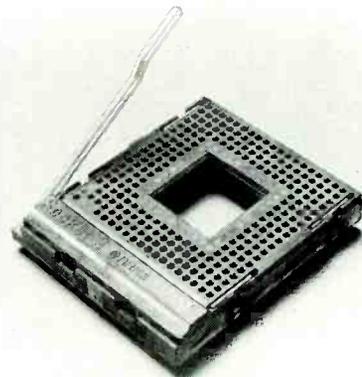


FIG. 5—ZIF sockets permit the easy insertion and removal of CPU chips, preventing damage to the chip and motherboard.

brightness and contrast.

V.32—The communications standard for 9600 bps modems.

V.32bis—The communications standard for 14.4 kbps modems.

V.34—The communications standard for 28.8 kbps modems.

VESA—Video Electronics Standards Association. A trade organization of graphics hardware manufacturers that develop guidelines for video products and expansion slots.

VL-Bus—The VESA local bus. An aging local bus that runs at speeds up to 66 MHz. Also advertised as VLB and VESA LB.

VRAM—Video random access memory. A dual-ported memory that speeds video displays, particularly Windows.

WAV—Microsoft's standard file format for audio sound.

wavetable—A method used by some sound boards to store the actual digital sounds of real instruments, resulting in more realistic sounds than those created by the synthesized voice method.

Windows accelerator—Any video board that uses a video chip with built-in instructions that increase the speed of Windows applications. Very few video boards sold today don't have a Windows accelerator.

speed drives might never see the light of day before new high-density CDs are introduced. Since CD-ROM technology is still fairly primitive, what you can expect from a double-speed installation is snail-speed navigation as you move through many CD-ROM applications (especially those making heavy use of video clips), herky-jerky video visuals, and ill-synchronized sound.

If you haven't bought a CD-ROM yet but you already own (or have your eye on) a bunch of multimedia software, you'll need to choose a system that supports the particular software you want to run. MPC and MPC2 define the minimum system requirements for CD-ROM multimedia applications (see Table 6). CD software packages usually tell you (right on their covers) which of these standards will be required for running the program. Virtually all

new computers sold today exceed the MPC2 specifications.

While you can get sound from your PC's built-in speaker, you won't want to listen to it for long. A better bet would be to buy a sound board. Many sound boards claim to be compatible with the Sound Blaster, which is the *de facto* standard for interfacing the sound card with a CD-ROM. Sound cards commonly have a MIDI port for playing and composing music via an external keyboard or other MIDI device. The number of synthesized voices a sound board has, the better. The typical sound board has 20, more than enough for games, but not enough for serious MIDI work. Wavetables are actual digital recording samples of real instruments, and have a quality that synthesized voices can't match.

Portables

Since its introduction some

ten years ago, the PC-compatible portable computer has undergone an incredible weight loss, from the 18-pound laptop luggage of 1986 down to today's six-pound notebooks and four-pound subnotebooks.

Unlike desktop computers, portables have an LCD screen instead of a CRT. Basically, there are three types of LCDs: passive, dual-scan, and active. Passive LCD displays are the dimmest. They consist of a liquid-crystal panel with a grid of wires on each side of the display forming a matrix. When voltage is applied to the matrix it polarizes the liquid crystal and lets light pass through. However, at VGA scanning rates, the voltage isn't applied long enough for the liquid crystal to completely untwist, which results in low contrast. Dual-scan LCDs improve the contrast by dividing the screen in half, and simultaneously scanning the top and bottom halves. Better yet are active-matrix screens with thin-film transistors (TFTs) on the inside surface that amplifies the current to make the liquid crystal open faster and more fully.

Most notebooks and subnotebooks come with at least one PCMCIA slot. This is the portable's equivalent of the desktop's ISA or local-bus slot: It's used for such plug-in devices as modems, network adapters, hard disks, and memory. PCMCIA cards come in three standard thicknesses (Types I, II, and III), and their slots can be stacked to allow a thicker Type II card to plug into two thinner Type I slots.

Because space inside the portable is so limited, such peripherals as large disk drives and CD-ROMs are often connected externally via the parallel port. A recent advance is the enhanced parallel port, which moves data to and from the computer and external peripherals at a much faster rate than a conventional parallel port. A docking station converts a laptop into a desktop by providing connections for a monitor along with multiple serial and parallel ports.

Until recently, portables were

TABLE 6—MULTIMEDIA REQUIREMENTS

	MPC	MPC2
CPU	386 SX-20	486SX-25
Memory	2 MB	4MB
Hard Drive	30 MB	160 MB
CD-ROM Sustained DTR	150 kbps	300 kbps
Sound		
Sample Playback Rate	22 kHz, 8-bit	44 kHz, 16-bit
Sample Recording Rate	11 kHz, 8-bit	44 kHz, 16-bit
Synthesizer	8-voice, MIDI	8-voice, MIDI
MIDI in/out	Yes	Yes
Video		
Resolution and Colors	640 x 480, 256 colors	640 x 480, 65K colors
Kodak Multi-Session	No	Yes
Digital Video Playback	n/a	320 x 240, 15 fps

powered by Nickel-Cadmium (Ni-Cd) batteries. Today most notebooks and subnotebooks are powered by Nickel Metal Hydride (NiMH) batteries, which are less toxic and store more energy in a smaller space. Lithium storage batteries (LIS), the most efficient and least toxic choice, are just coming into use: They last longer and store more energy per pound than either Ni-Cd or NiMH.

Communications

PC communications tech-

nology has advanced far beyond the lethargic modems of yesterday. Modem speed is measured in bits per second (bps).

Today's lowest-end modems run at 2400 bps (twice as fast as the old 1200 bps models, but still far from rapid—avoid them if you can.) The better ones run at rates of 14.4 kilobits per second (kpbs), and many run at the new standard speed of 28.8 kbps. Modem speed adjusts downward automatically as needed: Two modems of widely different speed (say, 1200 and

14.4K) can still communicate—at the slower modem's rate.

Buying smart

No article about computers can hope to be comprehensive—especially with the speed that the computer industry changes and that computer technology advances. The first rule before you buy is to ask questions; if you don't know what something means, ask. If the vendor won't give you a clear answer, find another one who will. Ω

PARTY LINE

continued from page 129

agram of the circuit. It consists of five major sections: Input, step-up, microcontroller, DTMF decoder and call-progress generator, and power. Note in the figure that there are three separate grounds, one each for the analog circuitry, the digital circuitry, and the high-current devices. The three grounds unite at the power supply.

The input section consists of six identical phone-line interfaces. Each includes an LED status indicator, an opto-coupler that after buffering informs the MCU that a line has gone off-hook, and a DPDT relay that switches the tip and ring connections of a line between the talk and ring circuits.

The step-up circuit buffers the 20-Hz ring signal from the MCU and then uses a push-pull amplifier arrangement to drive a reverse-coupled transformer. The transformer steps the circuit-level ring-voltage up to about 90 volts.

The microcontroller section is the brains of the Party Line. The MCU uses task-based scheduling software to ensure that all activities are tended to in a timely fashion. The MCU reads configuration information, maintains the real-time clock, monitors and controls line status of all six stations, drives the status LED, generates the 20-Hz ring signal, generates the CID tones, and performs general housekeeping.

The DTMF decoder and call-progress generator are built from a couple of special-purpose IC's. One performs DTMF tone decoding, transferring its information to the MCU via the attached bus. The other generates several call-progress tones depending on the binary codes at its inputs. The bus also delivers that binary code, as well as control signals for latching information out of the DTMF decoder and into the call-progress generator.

This section also contains a two-stage op-amp buffer for coupling the MCU-generated CID tones into the audio

portion of the circuit.

Last, the power supply delivers regulated sources of +5-volts DC and +12-volts DC, as well as a regulated +28-volt talk voltage. The only unusual thing about the power supply is that the talk-voltage regulator can be disabled under software control. The purpose of that is to support a seldom-used telephone feature called Calling Party Control (CPC).

When we pick up next time, we'll provide a more detailed description of the circuit, including complete schematics. Then we'll discuss construction, configuration, and use. Ω

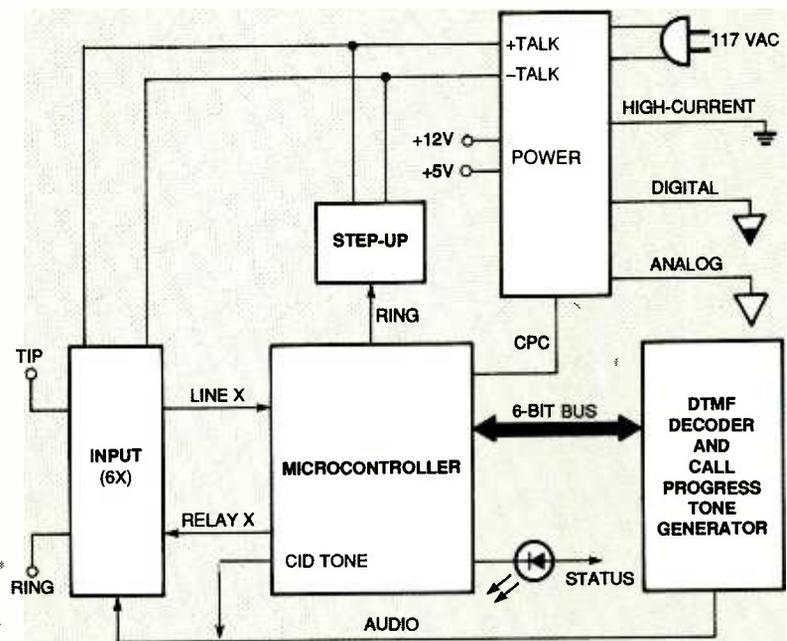


FIG. 2—PARTY LINE BLOCK DIAGRAM: There are separate ground lines for the analog circuitry, the digital circuitry, and the high-current devices.

LEDS FOR AUDIO

continued from page 30

colors. These reference voltages are fed to the three comparators along with the input signal. Notice that the input signal is connected to the inverting (-) input of one comparator (IC3-b) and to the noninverting (+) input of the other two comparators (IC3-c, IC3-d).

The output of these comparators is then connected to LED2. If the output of all of the comparators is floating, the red and green dies in the tri-color LED are biased on by R15 and R16, causing LED2 to glow yellow. However, if the output of a comparator is internally grounded, the connected color element will be pulled below 2 volts, and the element will turn off. Table 2 lists how the various comparators turn on and off to control the separate color dies in LED2 as the input voltage increases.

The comparator reference voltages are set so that reference V_Y is twice as large as V_G and reference V_R is twice as large as V_Y . This power-of-two relationship is commonly found in audio electronics. The reference voltages are: $V_R = 1.26$, $V_Y = 0.63$ and $V_G = 0.32$.

To set the gain level of the amplifier, connect the input of Fig. 4 to the output of the averager circuit in Fig. 2. As with the previous level indicator, apply a maximum-level signal to the input of the averager, and reduce the level to allow for headroom. Then, adjust R2 in Fig. 2 until LED2 just turns red. Now slowly reduce the audio input-signal level at the input to the ampli-

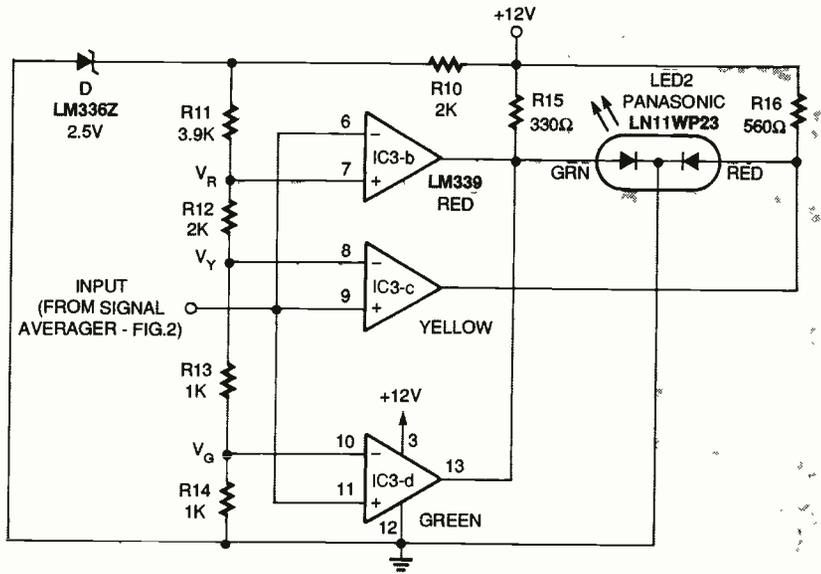


FIG. 4—A TRI-COLOR LED level indicator circuit.

fier. LED2 should change in sequence from red to yellow, then to green, and finally to off.

10-LED bargraph

The third solid-state level indicator consists of a string of ten LEDs in one package. With a low-level signal input, all LEDs are off. As the signal level increases, more LEDs light up until finally all ten are turned on to indicate the maximum level.

The heart of the circuit shown in Fig. 5 is the National Semiconductor LM3915. Internally, this IC is similar to the tri-color LED circuit *in toto*. The LM3915 contains a precision voltage reference, resistor divider chain, and ten comparators to drive the LEDs. This IC also contains current-limiting circuitry that limits the brightness of the LEDs without the need for separate resistors, and logic to select either a bargraph or a moving-dot display. In Fig. 5,

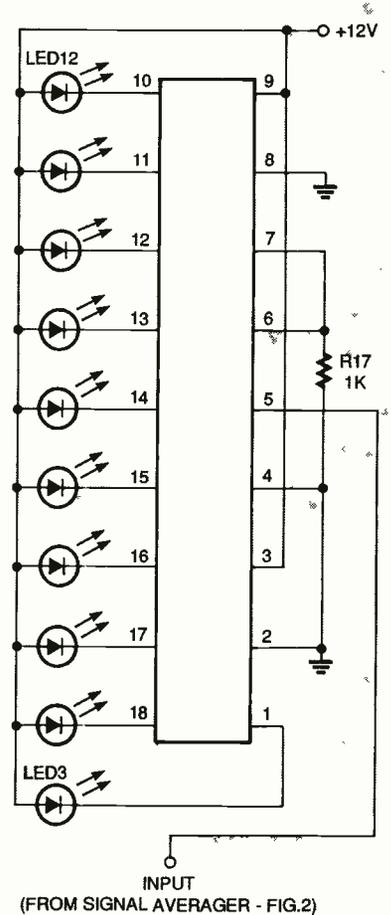


FIG. 5—A TEN-LED BARGRAPH level indicator.

the bargraph display is selected because pin 9 of IC5 is tied to the same voltage point as pin 3 of IC5. If pin 9 is allowed to float,

TABLE 2—TRICOLOR LED COMPARATOR OUTPUT

Input Level	IC3-b Output	IC3-d Output	Green Element	IC3-c Output	Red Element	LED2 Color
Less Than V_C	Float	Ground	Off	Ground	Off	Off
V_G to V_R	Float	Float	On	Ground	Off	Green
V_Y to V_R	Float	Float	On	Float	On	Yellow
More Than V_R	Ground	Float	Off	Float	On	Red

the IC would program one LED to turn on at a time to provide a moving-dot display. The voltage references are set to the standard step increments used in audio electronics equipment to match the response to the volume heard by the human ear.

Set the illuminating response level of the bargraph LED indicator following the same procedure as previously described for the other LED circuits. Connect the output of Fig. 2 of the averager circuit to the input of the bargraph level indicator in Fig. 5. Apply a maximum level signal to the input shown in the averager circuit of Fig. 5, and reduce the input level to allow for headroom. Then adjust R2 in Fig. 2 until the most significant LED (LED12 in Fig. 5) just turns on.

Picking the LED level indicator

The selection of the most appropriate LED level indicator depends on the existing arrangement of controls. If the front panel is already cluttered with knobs and switches, there might only be room for a single LED. However, if the front panel has room to spare, a ten LED bargraph might fit on it. Its installation could give the audio equipment a professional appearance. (Remember, you need two bargraphs for a stereo system.) The LEDs that make up the bargraph can be positioned vertically, horizontally, or even in an arc to convey the impression of a moving needle of a meter. Also, the LEDs can have different colors. Use red for the high levels, green for the low, and yellow for those in-between.

If only one LED will fit on the crowded panel, chose between a single-color LED or a tri-color LED. The tri-color LED has more resolution because it has four color states. However, if all you need is an overload detector, the single-color LED is a better choice because it clearly conveys a message of *too high*.

Finally, keep in mind that the addition of a solid-state level indicator might excite audiophiles who will admire and want to try out your project. Ω

WAVEFORM GENERATORS

continued from page 138

showing how the tuned-collector oscillator in Fig. 13 can be modified to act as a 455-kHz, beat-frequency oscillator (BFO). It is tuned by adjusting a voltage-variable capacitor with potentiometer R5. Transformer T1 is a standard 455-kHz transformer for transistorized circuits, and silicon diode D1 functions as an inexpensive voltage-variable capacitor.

When a small-signal silicon diode is reverse biased, its effective capacitance varies with the applied voltage. Its capacitance value is inversely related to the applied voltage. Some silicon diodes are optimized to function as dedicated voltage-variable capacitors, but the industry standard 1N4001 diode will demonstrate this function satisfactorily for any experimental purposes.

In Fig. 18, capacitor C2 and the effective capacitance of D1 are in series, and the combination is connected across the tuned circuit of transformer T1. (Capacitor C2 blocks DC between transistor Q1 and diode D1.) This configuration permits the Reinartz oscillator's center frequency to be changed by altering the capacitance of D1 with potentiometer R5. Ω



Statement of Ownership, Management and Circulation

(Required by 39 U.S.C. 3685)

14. Publication Title		15. Issue Frequency		16. Number of Issues Published Annually		17. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
18. Complete Mailing Address of Known Office of Publication (Street, City, County, State, and ZIP+4) (Do not leave blank)		19. Complete Mailing Address of Headquarters or General Business Office of Publisher (Do not leave blank)		20. Complete Mailing Address of Principal Office or Place of Publication (Do not leave blank)		21. Complete Mailing Address of the Publisher (Do not leave blank)	
500 BI-COUNTY BLVD., FARMINGDALE, NY 11735		500 BI-COUNTY BLVD., FARMINGDALE, NY 11735		500 BI-COUNTY BLVD., FARMINGDALE, NY 11735		500 BI-COUNTY BLVD., FARMINGDALE, NY 11735	
22. Full Names and Complete Mailing Addresses of Publisher, Editor, and Managing Editor (Do not leave blank)		23. Full Names and Complete Mailing Addresses of Owner (Do not leave blank)		24. Full Names and Complete Mailing Addresses of Known Bondholders, Mortgagees, and Other Security Holders Owning or Holding 1 Percent or More of Total Amount of Bonds, Mortgages, or Other Securities (Do not leave blank)		25. Full Names and Complete Mailing Addresses of Known Contributors (Do not leave blank)	
LARRY STEINER 500 BI-COUNTY BLVD., FARMINGDALE, NY 11735		LARRY STEINER 500 BI-COUNTY BLVD., FARMINGDALE, NY 11735		LARRY STEINER 500 BI-COUNTY BLVD., FARMINGDALE, NY 11735		LARRY STEINER 500 BI-COUNTY BLVD., FARMINGDALE, NY 11735	
26. Publication Title		27. Issue Frequency		28. Number of Issues Published Annually		29. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
30. Publication Title		31. Issue Frequency		32. Number of Issues Published Annually		33. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
34. Publication Title		35. Issue Frequency		36. Number of Issues Published Annually		37. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
38. Publication Title		39. Issue Frequency		40. Number of Issues Published Annually		41. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
42. Publication Title		43. Issue Frequency		44. Number of Issues Published Annually		45. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
46. Publication Title		47. Issue Frequency		48. Number of Issues Published Annually		49. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
50. Publication Title		51. Issue Frequency		52. Number of Issues Published Annually		53. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
54. Publication Title		55. Issue Frequency		56. Number of Issues Published Annually		57. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
58. Publication Title		59. Issue Frequency		60. Number of Issues Published Annually		61. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
62. Publication Title		63. Issue Frequency		64. Number of Issues Published Annually		65. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
66. Publication Title		67. Issue Frequency		68. Number of Issues Published Annually		69. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
70. Publication Title		71. Issue Frequency		72. Number of Issues Published Annually		73. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
74. Publication Title		75. Issue Frequency		76. Number of Issues Published Annually		77. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
78. Publication Title		79. Issue Frequency		80. Number of Issues Published Annually		81. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
82. Publication Title		83. Issue Frequency		84. Number of Issues Published Annually		85. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
86. Publication Title		87. Issue Frequency		88. Number of Issues Published Annually		89. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
90. Publication Title		91. Issue Frequency		92. Number of Issues Published Annually		93. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
94. Publication Title		95. Issue Frequency		96. Number of Issues Published Annually		97. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
98. Publication Title		99. Issue Frequency		100. Number of Issues Published Annually		101. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
102. Publication Title		103. Issue Frequency		104. Number of Issues Published Annually		105. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
106. Publication Title		107. Issue Frequency		108. Number of Issues Published Annually		109. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
110. Publication Title		111. Issue Frequency		112. Number of Issues Published Annually		113. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
114. Publication Title		115. Issue Frequency		116. Number of Issues Published Annually		117. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
118. Publication Title		119. Issue Frequency		120. Number of Issues Published Annually		121. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
122. Publication Title		123. Issue Frequency		124. Number of Issues Published Annually		125. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
126. Publication Title		127. Issue Frequency		128. Number of Issues Published Annually		129. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
130. Publication Title		131. Issue Frequency		132. Number of Issues Published Annually		133. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
134. Publication Title		135. Issue Frequency		136. Number of Issues Published Annually		137. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
138. Publication Title		139. Issue Frequency		140. Number of Issues Published Annually		139. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
142. Publication Title		143. Issue Frequency		144. Number of Issues Published Annually		143. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
146. Publication Title		147. Issue Frequency		148. Number of Issues Published Annually		145. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
150. Publication Title		151. Issue Frequency		152. Number of Issues Published Annually		147. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
154. Publication Title		155. Issue Frequency		156. Number of Issues Published Annually		149. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
158. Publication Title		159. Issue Frequency		160. Number of Issues Published Annually		151. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
162. Publication Title		163. Issue Frequency		164. Number of Issues Published Annually		153. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
166. Publication Title		167. Issue Frequency		168. Number of Issues Published Annually		155. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
170. Publication Title		171. Issue Frequency		172. Number of Issues Published Annually		157. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
174. Publication Title		175. Issue Frequency		176. Number of Issues Published Annually		159. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
178. Publication Title		179. Issue Frequency		180. Number of Issues Published Annually		161. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
182. Publication Title		183. Issue Frequency		184. Number of Issues Published Annually		163. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
186. Publication Title		187. Issue Frequency		188. Number of Issues Published Annually		165. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
190. Publication Title		191. Issue Frequency		192. Number of Issues Published Annually		167. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
194. Publication Title		195. Issue Frequency		196. Number of Issues Published Annually		169. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
198. Publication Title		199. Issue Frequency		200. Number of Issues Published Annually		171. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
202. Publication Title		203. Issue Frequency		204. Number of Issues Published Annually		173. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
206. Publication Title		207. Issue Frequency		208. Number of Issues Published Annually		175. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
210. Publication Title		211. Issue Frequency		212. Number of Issues Published Annually		177. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
214. Publication Title		215. Issue Frequency		216. Number of Issues Published Annually		179. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
218. Publication Title		219. Issue Frequency		220. Number of Issues Published Annually		181. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
222. Publication Title		223. Issue Frequency		224. Number of Issues Published Annually		183. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
226. Publication Title		227. Issue Frequency		228. Number of Issues Published Annually		185. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
230. Publication Title		231. Issue Frequency		232. Number of Issues Published Annually		187. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
234. Publication Title		235. Issue Frequency		236. Number of Issues Published Annually		189. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
238. Publication Title		239. Issue Frequency		240. Number of Issues Published Annually		191. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
242. Publication Title		243. Issue Frequency		244. Number of Issues Published Annually		193. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
246. Publication Title		247. Issue Frequency		248. Number of Issues Published Annually		195. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
250. Publication Title		251. Issue Frequency		252. Number of Issues Published Annually		197. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
254. Publication Title		255. Issue Frequency		256. Number of Issues Published Annually		199. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
258. Publication Title		259. Issue Frequency		260. Number of Issues Published Annually		201. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
262. Publication Title		263. Issue Frequency		264. Number of Issues Published Annually		203. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
266. Publication Title		267. Issue Frequency		268. Number of Issues Published Annually		205. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
270. Publication Title		271. Issue Frequency		272. Number of Issues Published Annually		207. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
274. Publication Title		275. Issue Frequency		276. Number of Issues Published Annually		209. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
278. Publication Title		279. Issue Frequency		280. Number of Issues Published Annually		211. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
282. Publication Title		283. Issue Frequency		284. Number of Issues Published Annually		213. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
286. Publication Title		287. Issue Frequency		288. Number of Issues Published Annually		215. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
290. Publication Title		291. Issue Frequency		292. Number of Issues Published Annually		217. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
294. Publication Title		295. Issue Frequency		296. Number of Issues Published Annually		219. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
298. Publication Title		299. Issue Frequency		300. Number of Issues Published Annually		221. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
302. Publication Title		303. Issue Frequency		304. Number of Issues Published Annually		223. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
306. Publication Title		307. Issue Frequency		308. Number of Issues Published Annually		225. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
310. Publication Title		311. Issue Frequency		312. Number of Issues Published Annually		227. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
314. Publication Title		315. Issue Frequency		316. Number of Issues Published Annually		229. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
318. Publication Title		319. Issue Frequency		320. Number of Issues Published Annually		231. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
322. Publication Title		323. Issue Frequency		324. Number of Issues Published Annually		233. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
326. Publication Title		327. Issue Frequency		328. Number of Issues Published Annually		235. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
330. Publication Title		331. Issue Frequency		332. Number of Issues Published Annually		237. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
334. Publication Title		335. Issue Frequency		336. Number of Issues Published Annually		239. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
338. Publication Title		339. Issue Frequency		340. Number of Issues Published Annually		241. Date of First Issue	
ELECTRONICS NEWS		MONTHLY		12		1/28/95	
342. Publication Title		343. Issue Frequency		344. Number of Issues Published Annually		243. Date of First Issue	

ADVERTISING INDEX

Electronics Now does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page		
212	Ace Communications	90	—
—	Active Micro	115	305
213	Alfa Electronics	78	—
214	All Electronics	81	—
—	Allen Engineering	76	304
283	Allstar Technology	110	303
—	Allstar Electronics	113	197
—	Alltronics	108	—
—	AlphaLab	84	—
284	AMC Sales	112	251
—	American Eagle Publications	62	—
—	Andromeda	80	252
334	Basic Electrical Supply	92	—
—	Baylin Publications	62	—
297	Bel-Merit	105	217
201	BHS Electronics	94	198
—	Black Feather	107	—
—	Boss Distributors	74	—
—	Bsoft Software, Inc.	86	254
335	C&S Sales, Inc.	96	—
315	Capital Electronics	53	255
314	Chase Scientific Co.	69	—
313	Circuit Specialists	99	—
—	Cleveland Inst. of Electronics	35	—
—	Command Productions	18, 94	—
—	Communication Specialists	112	257
—	Computer Business Services	106	258
331	Computer Monitor Maint.	108	—
226	Consumertronics	98	—
310	Conway Engineering Inc.	15	—
228	Cool Amp Conducto Lube	54	202
—	Creative Micro Electronics	102	262
298	Cybermation	103	—
234	Dalbani Electronics	91	327
235	Danbar Sales	56	—
129	Dataman Programmers	CV4	325
—	Delta Quest	62	264
336	Direct Cable Supply	62, 111, 115	—
—	DP Electronics & Sons	86	—
—	Earth Computer Technologies	80	302
241	Electronic Goldmine	59	—
242	Electronic Rainbow	71	130
—	Electronics Tech. Today	86	269
—	Emac Inc.	76	—
—	Fair Radio	110	270
121	Fluke Corporation	CV2	301
299	Foley-Belsaw Company	57	—
309	Fotronic	58	196
243	Gateway Electronics	74	—
308	Gateway Products	84	274
—	General Device Instruments	106	—
—	Get-Tech	88	—
122	Global Specialties	22	275
—	Grantham College	19	—
200	Graymark International	88	307
—	Halcyon Group	93	321
124	Hameg Instruments	9	—
—	Home Automation	110	98
216	Howard Electronics	77	—
—	IEC	112	300
—	Index Publishing Group	105	319
—	Information Unlimited	64	—
199	Instek Corp.	87	—
150	Interactive Image Technologies	11	281
—	Intronics, Inc.	106	—
—	J&M Microtek, Inc.	114	—
—	Jensen Tools	105	—
—	Learn, Inc.	CV3	—
—	M&G Electronics	70	—
—	M.D. Electronics (Everquest)	107	—
—	Mark V Electronics	116	—
—	MCM Electronics	83	—
—	Measurement Software	88	—
—	Mega Electronics	23	—
—	Mendelson Electronics Surplus	113	—
—	Mental Automation	74	—
—	Meredith Instruments	104	—
—	Merrimack Valley Systems	103	—
—	Metric Equipment Sales	103	—
—	Micro 2000	85	—
—	Micro Code Eng.	67	—
—	Micro Engineering Labs	112	—
—	Midwest Laser Products	62	—
—	Ming Engineering	63	—
—	Modern Electronics	106	—
—	Mondo-tronics Inc.	66	—
—	Motron Electronics	62	—
—	Mouser Electronics	82	—
—	MWK Industries	90	—
—	National Cable Brokers	103	—
—	Needham Electronics	76	—
—	New Sensor Corp.	13	—
—	NRI Schools	51	—
—	Oatley Electronics	98	—
—	Ohio Automation	107	—
—	OWI	102	—
—	Parts Express Inc.	72	—
—	PC Boards	92	—
—	Phillips Tech Electronics	108	—
—	Picotronic	82	—
—	Prairie Digital	90	—
—	Print (Pace)	65	—
—	ProBoard Circuits	106	—
—	Protech Dist.	18	—
—	Roger's Systems Specialist	80	—
—	Rose Research & Development	106	—
—	Sencore, Inc.	21	—
—	Sescom Inc.	70	—
—	Show-Time	108	—
—	Skyvision Inc.	55	—
—	Sun Equipment	89	—
—	Tab Books	1, 132	—
—	Tech Systems	75	—
—	TECHMART	84	—
—	TECI	87	—
—	Tektronix, Inc.	16A & B	—
—	Test Equipment Sales	93	—
—	Timeline	68	—
—	U.S. Cyberlab	93	—
—	Ultimate Cable	60	—
—	Visitect Inc.	104	—
—	Visual Communications	23	—
—	Wavetek Corp.	5	—
—	Weeder Technologies	53	—
—	Weka Publishing	100	—
—	Western Test Systems	95	—
—	World College	7	—
—	WPT Publications	92	—
—	Xandi Electronics	82	—

ADVERTISING SALES OFFICES

Gernsback Publications, Inc.
500 Bi-County Blvd.
Farmingdale, NY 11735-3931
1-(516) 293-3000

Larry Steckler
publisher (ext. 201)

Christina Estrada
assistant to the publisher (ext. 209)

Arline Fishman
advertising director (ext. 206)

Adria Coren
credit manager (ext. 208)

For Advertising ONLY

EAST/SOUTHEAST

Stanley Levitan
Eastern Advertising
1 Overlook Ave.
Great Neck, NY 11021-3750
1-516-487-9357
Fax 1-516-487-8402

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Midwest Advertising
One Northfield Plaza, Suite 300
Northfield, IL 60093-1214
1-708-446-1444
Fax 1-708-559-0562

PACIFIC COAST

Blake Murphy
Pacific Advertising
Hutch Looney & Associates, Inc.
6310 San Vicente Blvd.
Suite 360
Los Angeles, CA 90048-5426
1-213-931-3444
Fax 1-213-931-7309

Electronic Shopper

Joe Shere
National Representative
P.O. Box 169
Idyllwild, CA 92549-0169
1-909-659-9743
Fax 1-909-659-2469

Megan Mitchell
National Representative
1201 N. Rainbow Blvd., #50
Las Vegas, NV 89128
1-702-259-7043
Fax 1-702-259-7043

Subscriber Customer Service

1-800-288-0652
7:00 AM - 6:00 PM M-F MST

What's better than speed reading? *Speed Learning.*

Speed Learning has replaced speed reading. It's a whole new way to read and learn. It's easy to learn...lasts a lifetime... applies to everything you read. It may be the most productive course you've ever taken.

Do you have too much to read and too little time to read it? Do you mentally pronounce each word as you read? Do you frequently have to go back and reread words, or whole paragraphs, you just finished reading? Do you have trouble concentrating? Do you quickly forget most of what you read?

If you answer "Yes" to any of these questions — then here at last is the practical help you've been waiting for. Whether you read for business or pleasure, school or college, you will build exceptional skills from this major breakthrough in effective reading, created by Dr. Russell Stauffer at the University of Delaware.

Not just "speed reading" — but speed reading — thinking — understanding — remembering — and — learning

The new *Speed Learning Program* shows you, step-by-proven step, how to increase your reading skill and speed, so you understand more, remember more and use more of everything you read. The typical remark from over one million people taking the Speed Learning program is, "Why didn't someone teach me this a long time ago." They were no longer held back by their lack of skills and poor reading habits. They could read almost as fast as they could think.

What makes Speed Learning so successful?

The new *Speed Learning Program* does not offer you a rehash of the usual eye-exercises, timing devices, and costly gadgets you've probably heard about in connection with speed reading courses, or even tried and found ineffective.

In just a few spare minutes a day of easy reading and exciting listening, you discover an entirely new way to read and think — a radical departure from anything you have ever seen or heard about. Speed Learning is the largest selling self-study reading program in the world. Successful with Fortune 500 corporations, colleges, government agencies and accredited by 18 professional societies. Research shows that reading is 95% *thinking* and only 5% eye movement. Yet most of today's speed reading programs spend their time teaching you rapid eye movement (5% of the problem), and ignore the most important part, (95%) *thinking*. In brief, *Speed Learning gives you what speed reading can't*.

Imagine the new freedom you'll have when you learn how to dash through all types of reading material at least twice as fast as you do now, and with greater comprehension. Think of being able to get on top of the avalanche of newspapers, magazines and correspondence you have to read...finishing a stimulating book and retaining facts and details



FOR FASTER SHIPMENT CALL 1-800-729-7323 OR FAX 1-609-273-7766

more clearly, and with greater accuracy, than ever before.

Listen — and learn — at your own pace

This is a practical, easy-to-learn program that will work for you — no matter how slow a reader you think you are now. The *Speed Learning Program* is scientifically planned to get you started quickly...to help you in spare minutes a day. It brings you a "teacher-on-cassettes" who guides you, instructs, and encourages, explaining material as you read. Interesting items taken from *Time Magazine*, *Business Week*, *Wall Street Journal*, *Money*, *Reader's Digest*, *N.Y. Times* and many others, make the program stimulating, easy and fun...and so much more effective.

Executives, students, professional people, men and women in all walks of life from 15 to 70 have benefitted from this program. Speed Learning is a fully accredited course...costing only 1/4 the price of less effective speed reading classroom courses. Now you can examine the same easy, practical and proven methods at home...in your spare time...without risking a penny.

Examine Speed Learning RISK FREE for 15 days

You will be thrilled at how quickly this program will begin to develop new thinking and reading skills. After listening to just one cassette and reading the preface, you will quickly see how you can achieve increases in both the speed at which you read, and in the amount you understand and remember.

You must be delighted with what you see, or you pay nothing. Examine this remark-

able program for 15 days. If, at the end of that time you are not convinced that you would like to master Speed Learning, simply return the program for a prompt refund. (See the coupon for low price and convenient credit terms.)

RISK-FREE ORDER FORM

YES! I want to try Speed Learning for 15 days without risk. Enclosed is the first of 4 monthly payments of \$32.25*. If I'm not completely satisfied, I may return it for a prompt refund.

SAVE 8.00! I prefer to pay the \$129.00 now, and save the \$8.00 shipping & handling charge. I may still return the program for a full refund.

Method of payment: (Federal Tax Deductible)

Check or money order payable to Learn Incorporated

Charge to: Visa MC Am Ex Discover

Card # _____ Exp. _____

Signature _____

Phone (_____) _____

Name _____

Address _____


City _____ State _____ Zip _____

*Plus \$8.00 shipping and handling. U.S. funds only. For New Jersey residents, sales tax will be added.

learn INCORPORATED Dept. LEC-01, 113 Gaither Drive, Mt. Laurel, NJ 08054-9987

The handiest programmer on earth

DATA MAN PROGRAMMERS

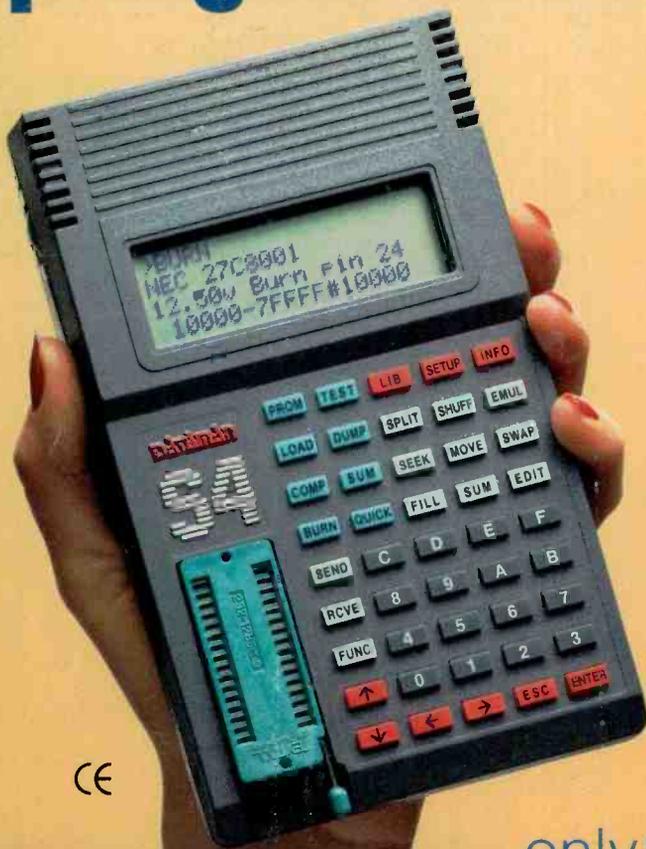

Here's why:

- Totally handheld programmer/emulator
- Fast approved programming algorithms; eg program and verify: National 27C512 in 16 seconds, AMD 29F010 in only 90 seconds
- EPROMs to 16Mbit, 5v, 12v and BOOT-BLOCK FLASH, EEPROMS and PEROMS
- Three year parts and labor warranty
- Full 24 byte on-screen editor
- Continuous programming whilst charging (nonstop operation)
- Designer case - feels as good as it looks
- Big, easy-view 80 character supertwist LCD
- Optional modules available to program PIC (all 16/17 series), 8751, 16-bit EPROMs, MROM-EPROM, 16-bit FLASH, Toshiba 4-bit, Hitachi H8, SERIAL EEPROMS
- Optional sockets for programming and emulating PLCC devices

CE

FREE software upgrades for life
FREE emulation leads
FREE Windows and DOS software

only **\$795** including 4Mbit RAM
 3 year warranty
 30 day free trial

S4's 32 pin ZIF socket programs a huge library of 8 and 16-bit EPROMs, EEPROMS, FLASH, PICs and other popular microcontrollers using manufacturers approved algorithms.

Dataman *never* charge for updates or technical support, a vital factor in determining a cost-effective programming solution for the years ahead. Upgrading your S4's device library couldn't be simpler. As well as our high speed bulletin boards, we also offer full Internet access to our Home Page which contains all the latest software as well as hints and tips. **Built-in emulation** enables you to see your code *before* committing yourself to an EPROM.

Load your program from an EPROM or download code from your PC into S4's memory. Plug S4's emulation lead into the target system, press the emulation key and run the system. Changes can be made using S4's powerful editor, and you can re-run the code to test and confirm changes. When the code is proved to be working, it can then be programmed to a fresh ROM.

The S4 Package comes complete with charger, emulation leads, organiser-style instruction manual, Windows and DOS terminal software *and* a three year warranty.

S4 is always available off the shelf and we ship worldwide on a daily basis. Call now for delivery tomorrow.

Bona-fide US and Canadian customers can try S4 for thirty days without risk. 24,000 engineers worldwide can't be wrong!

Dataman

Dataman Programmers, Inc

22 Lake Beauty Drive, Suite 101
 Orlando, FL 32806, USA
 Tel: (407) 649-3335 Fax: (407) 649-3310
 BBS: (407) 649-3159 24hr
 Modem: V.34/V.FC/V.32bis

Station Road, Maiden Newton,
 Dorset DT2 0AE, UK
 Tel: 01300 320719 Fax: 01300 321012
 Telex: 418442 BBS: 01300 321095
 Modem: V.34/V.FC/V.32bis

Via the Internet:
 Home Page: <http://www.dataman.com>
 FTP access: <ftp://ftp.dataman.com>
 Email: sales@dataman.com

CREDIT CARD
 HOTLINE

800 328-2336

for
 same-day
 dispatch



CIRCLE 129 ON FREE INFORMATION CARD

www.americanradiohistory.com