

MAY 1996

Electronics NOW[®]

FUZZY LOGIC

Understanding this new challenge to traditional control techniques

BUILD A TV TRANSMITTER

Put it to work at 900 MHz

MAKING MEASUREMENTS ACCURATELY


A Kelvin-Varley divider completes our mini metrology lab

KEEP IT COOL!

How to choose the right heatsink for your designs



\$3.50 U.S.
\$3.95 CAN.

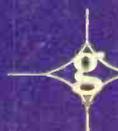

A GERNSBACK PUBLICATION

#BXNBQWF***** 3-DIGIT 871
#BRKB4717C96 6#570236 OAP91



CHRIS BARKER

JUN 97
05EN

87196-4717

True-rms. True values.



Do you troubleshoot non-linear circuits or loads? If so, you need true-rms capability to ensure accurate measurements. Now you can get this capability without having to compromise on quality or safety to stay within your budget.



Priced at just \$199.00*, the new Fluke Model 76 true-rms DMM is the latest in the long line of true-rms values from Fluke. You can use the Model 76 to easily measure true-rms ac current and volts, dc current and volts, ohms, capacitance, continuity, and frequency. And, the Model 76 is the only DMM in its class that meets UL, CE, CSA, and TÜV certification standards and conforms to the IEC 1010-1 product safety standard for Overvoltage Category III.⁽¹⁾

You'll find that kind of true value all the way down the line with Fluke test tools. See your local Fluke distributor to select a true-rms meter that fits whatever your job or budget demands.



Fluke 32
\$149*



Fluke 33
\$269*



Fluke 76
\$199*



Fluke 87
\$335*



Fluke 8060A
\$459*

* U.S. list price. Prices subject to change without notice.

(1) Approvals/Listing pending


© 1995 Fluke Corporation P. O. Box 9090, M/S 250E, Everett, WA USA 98206-9090. U.S. (206) 356-5400. Canada (905) 890-7600. Europe (31 40) 644200. Other countries (206) 356-5500. All rights reserved. Ad no. 00768

CIRCLE 121 ON FREE INFORMATION CARD



FLUKE

Just a reminder.

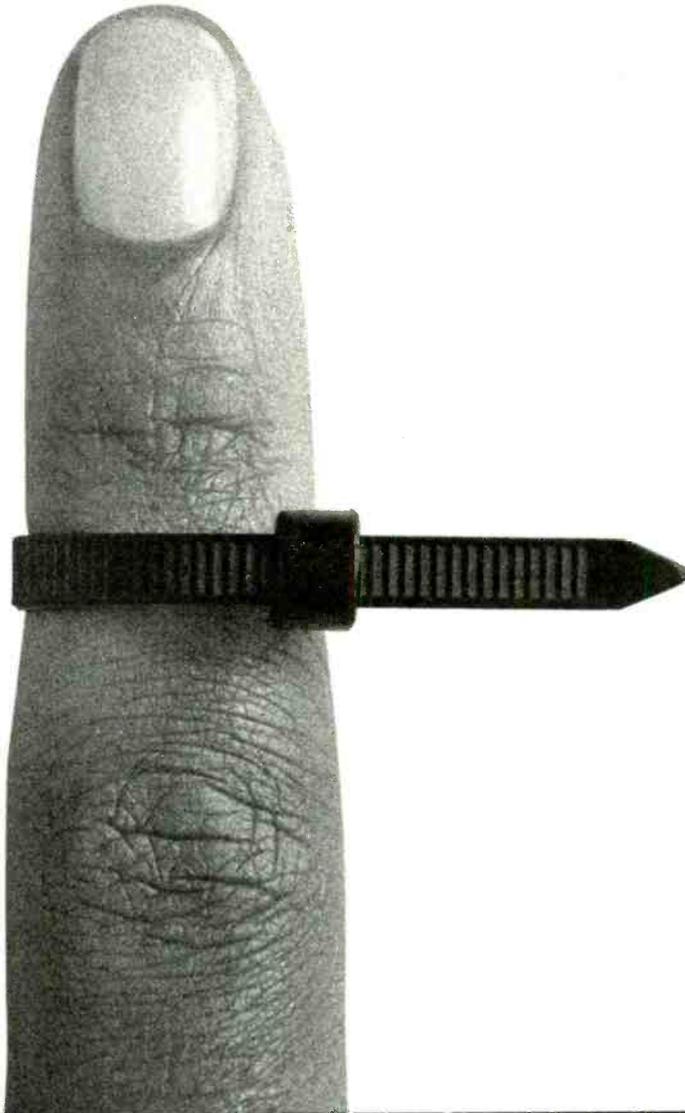

We even have the bits and pieces to organize your bits and pieces.

Adding a phone? Hooking up a home theater system? Putting up an antenna or satellite dish? You don't need the mess of twisting, trailing wires and cables. When neatness counts, you need flexible split tubing to bundle wires, nylon cord ties, beaded wire ties, wall-feedthrough bushings, adhesive clips or wire staples. And you'll find it all at your nearby RadioShack. We've got the products, the parts and the people to help you put it all together. For a store near you, call 1-800-THE-SHACK.



RadioShackSM
You've got questions.
We've got answers.[®]

CIRCLE 78 ON FREE INFORMATION CARD


www.americanradiohistory.com

CONTENTS



MAY 1996

ON THE COVER**29 FUZZY LOGIC**

Just as probability theory is not random, fuzzy logic is not fuzzy or indistinct as its name might imply. Instead, fuzzy logic is based on rigorous mathematical discipline that is a cross between Boolean logic and multivalued set theory. It is a relatively new discipline, with its creation generally credited to Lotfi Zadeh in the mid 1960s. Fuzzy logic has gained credibility throughout the world, where it is found in products ranging from camcorders and washing machines to automobiles and factory-control systems. At long last, it is beginning to catch on in the U.S. as well. — *Byron Miller*

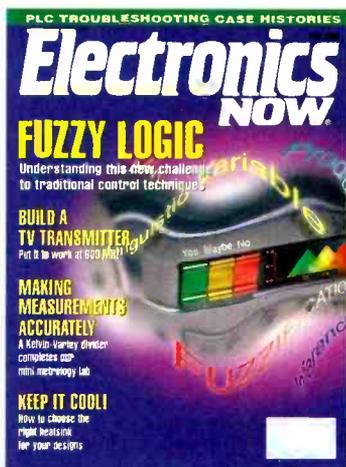**BUILD THIS****31 AMATEUR TV TRANSMITTER**


You can build your own amateur TV station with this sophisticated audio/video transmitter for the 900-MHz code-free amateur band.
— *William Sheets and Rudolf F. Graf*

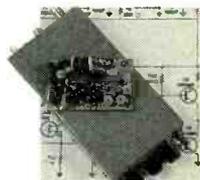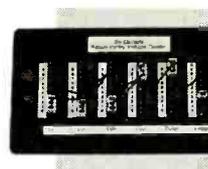**39 MINI METROLOGY LAB**

The final installment of a three-part series on the science of making accurate measurements shows you how to build a Kelvin-Varley divider.
— *Conrad R. Hoffman*

69 PHONE-LINE PRIVACY MODULE

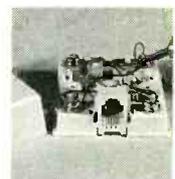This easy-to-build module helps to keep your modem and fax communications from being interrupted if another phone on the line goes off-hook.
— *James Melton*



As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 1067-9294) May 1996. Published monthly by Gernsback Publications, Inc., 500 Bi-County Boulevard, Farmingdale, NY 11735-3931. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Canada Post IPM Agreement No. 334103, authorized at Mississauga, Canada. One-year subscription rate U.S.A. and possessions \$19.97, Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax, Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$3.50. © 1996 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-address envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

TECHNOLOGY


37 TROUBLESHOOTING PLC PROBLEMS

A look at how some interesting troubleshooting problems on the factory floor were solved with the aid of a portable oscilloscope.
— Vaughn D. Martin



41 HOW TO SELECT THE RIGHT HEATSINK

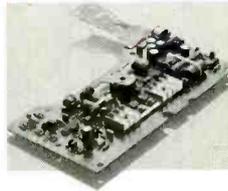Two simple formulas can help to prevent you from making a frustrating and costly error in your electronic designs.
— Mark A. McGuire



DEPARTMENTS

6 VIDEO NEWS

What's new in this fast-changing industry. — Dave Lachenbruch


14 EQUIPMENT REPORTS

Mission Technology's Multiscope Virtual Oscilloscope



43 HARDWARE HACKER

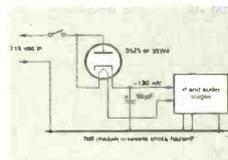Switching power supplies, the hot chassis, and more tricks for the PIC microcontroller.
— Don Lancaster



50 COMPUTER CONNECTIONS

Backing up is hard to do.
— Jeff Holtzman

— AND MORE —

4 WHAT'S NEWS	25 NEW LITERATURE
8 Q&A	138 ADVERTISING SALES OFFICES
12 LETTERS	138 ADVERTISING INDEX
21 NEW PRODUCTS	

Electronics NOW®

Hugo Gernsback (1884-1967) founder

LARRY STECKLER, EHF, CET,
Editor-in-chief and publisher

EDITORIAL DEPARTMENT

- BRIAN C. FENTON**, editor
- JULIAN S. MARTIN**, associate editor
- TERI SCADUTO**, assistant editor
- JEFFREY K. HOLTZMAN**, computer editor
- LARRY KLEIN**, audio editor
- DAVID LACHENBRUCH**, contributing editor
- DON LANCASTER**, contributing editor
- MICHAEL A. COVINGTON, N4TMI**, contributing editor
- EVELYN ROSE**, editorial assistant

ART DEPARTMENT

- ANDRE DUZANT**, art director
- RUSSELL C. TRUELSON**, illustrator

PRODUCTION DEPARTMENT

- RUBY M. YEE**, production director
- KATHRYN R. CAMPBELL**, production assistant
- KEN COREN**, desktop production

CIRCULATION DEPARTMENT

- JACQUELINE P. CHEESEBORO**, circulation director
- THERESA LOMBARDO**, circulation assistant

REPRINT DEPARTMENT

- MICHELE TORRILLO**, reprint bookstore

Typography by Mates Graphics
Cover design by David Loewy

Electronics Now is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*.

Microfilm & Microfiche editions are available. Contact reprint bookstore for details.

Advertising Sales Offices listed on page 136.

Electronics Now Executive and Administrative Offices
1-516-293-3000.

Subscriber Customer Service:
1-800-288-0652.

Order Entry for New Subscribers:
1-800-999-7139.



Audit Bureau
of Circulations
Member




WHAT'S NEWS

A REVIEW OF THE LATEST HAPPENINGS IN ELECTRONICS

Self-pulsating laser for DVD

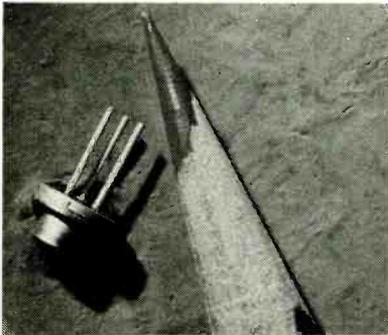Toshiba Corporation of Japan has introduced a visible laser diode designed specifically for use with the DVD (digital video disk technology) format. The TOLD9450-MC is the first commercialized self-pulsating laser diode to operate at a wavelength of 650 nanometers. Its short wavelength makes the device well-suited to meet the high recording density needs of DVD applications.



TOSHIBA'S SELF-PULSATING LASER DIODE operates at a wavelength of 650nm, meeting the high recording density needs of DVD applications.

Using Toshiba's Multi Quantum Well (MQW) structure and a saturable absorber layer, the TOLD9450MC provides effective, stable self-pulsation and reduced operating current. The design allows for noise suppression, achieving a relative intensity noise (RIN) of less than -130 dB/Hz at room temperature. Through optimization of the layer structure, stable laser operation is delivered over a wide temperature range.

The small package size (5.6-mm diameter) allows system designers to reduce the size of the optical

pickup head. The cathode-case type pin configuration allows a positive power supply to be used.

New superconductor under development

Scientists at the Westinghouse Electric Corporation's Science & Technology Center in Pittsburgh have been studying a more rugged and versatile electronic material for use in semiconductors. The material, silicon carbide (SiC), promises electronic devices that operate reliably at much higher temperatures and power levels than devices made from the materials used today, such as silicon or gallium arsenide.

Although the potential advantages of silicon-carbide devices has been known for more than 25 years, early interest waned because it was difficult to make crystals of the needed purity and uniformity in useful sizes. The Westinghouse program, which recently received a \$4.5-million government contract, is devoted to overcoming that problem. The study, funded by the U.S. Advanced Research Projects Agency through Wright-Patterson Air Force Base in Ohio, is a three-year effort to develop low-defect, three-inch diameter crystals and large-area epitaxial layers of semiconductor quality.

SiC-based devices would perform better, be more efficient, and cost less in a variety of uses. For instance, they could serve as sensors in hot environments such as car and aircraft engines and be used in lightweight, high-power electronic systems for applications like electronic vehicles. The devices also

have potential applications in radar, computer memories, and broadcasting. In power-plant control systems, SiC devices promise increased reliability thanks to another key advantage (significantly higher resistance to damage from ionizing radiation that devices made with materials now in common use.

300-mm wafer implanted

A newly developed serial process, known as high current ion implanter, has successfully been used to implant 300-mm wafers. The serial implanter was developed by Varian Ion Implant Systems and Diamond Semiconductor Group (DSG), both of Gloucester, MA. Concept and feasibility funding was provided by the Advanced Technology Program of the National Institute of Standards and Technology (NIST).

"As the industry advances to 300-mm, its goals are to increase productivity, reduce costs, and reduce risks," said Bruce Thayer, Varian's marketing manager. "A 300-mm wafer offers 2.5 times the yield of a 200-mm substrate."

"By processing wafers serially, the overall complexity of the system is decreased dramatically, and the reliability can be greatly enhanced," added DSG president Manny Sieradzki. "Serial processing offers major improvements in process flexibility and 'wafer inventory' or 'device factory' management over present high-current ion implanters, which implant wafers in batches of 13 or more."

continued on page 49

Overpowered.


UP TO 2 GS/s SAMPLE RATE
The highest sample rates you can find in this class.

THE TEKTRONIX NAMEPLATE
From the world leader in oscilloscope technology, all the service and support you'd expect.

FAST FOURIER TRANSFORM (FFT)
Analyze waveforms faster. What others charge \$500 or more for is built right in.

DIGITAL REAL TIME
Single-shot capture up to 400 MHz on each channel. The power to see reality, not some approximation of it.

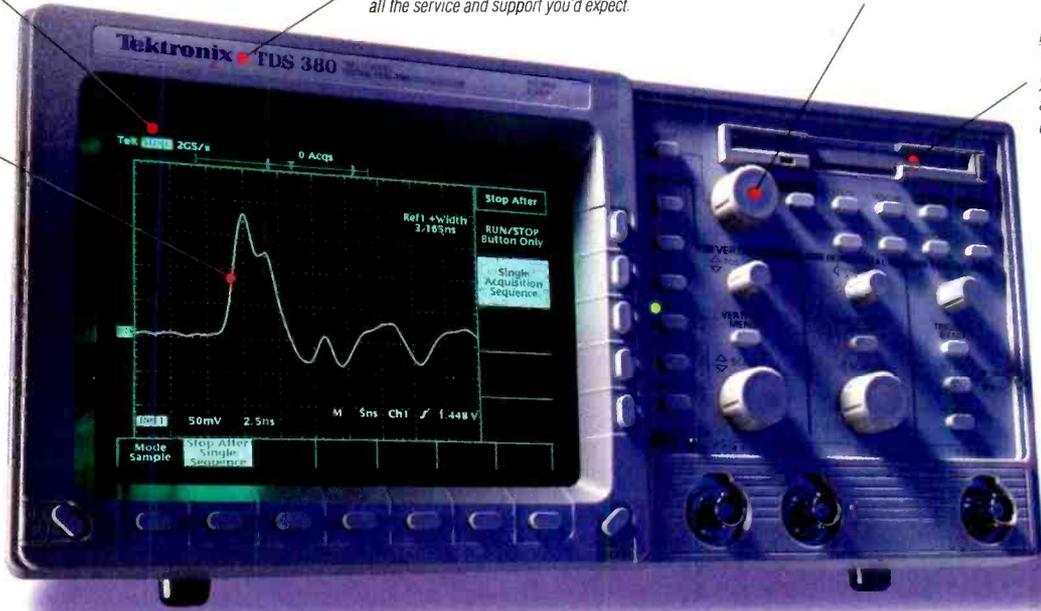FLOPPY DISK DRIVE
Transfer data directly to your PC for documentation and analysis. A Tektronix exclusive at this price.



Underpriced.

With the breakthrough new TDS 300 Series, Tektronix redefines the price-performance benchmark in oscilloscopes. Numbers tell the story: A sample rate of up to 2 GS/s and a bandwidth of up to 400 MHz take you to the highest level of performance, Digital Real Time (DRT).

DRT is an exclusive oversampling technology that lets these scopes beat the real-world challenge of displaying infrequent, single-shot events.

You'll see things the other scopes can't even capture. The new TDS 300 Series also offers

Starting at \$2,495

FFT and Disk Drives – features others charge hundreds of dollars more for, or don't even have. The biggest breakthrough, though, is in the number on the price tag. The TDS 300 Series starts at \$2,495. For this price, you get a level of performance you'd expect only in scopes twice as expensive. Contact your Tektronix Authorized Distributor for details, or call 1-800-479-4490, Action Code 311. And prepare to be overwhelmed.



TDS 340, \$2,495
100 MHz, 500 MS/s, DRT, FFT




TDS 360, \$3,495
200 MHz, 1 GS/s, DRT, FFT, Disk Drive



TDS 380, \$4,595
400 MHz, 2 GS/s, DRT, FFT, Disk Drive

Tektronix

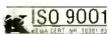

*Manufacturers suggested retail prices shown. ©1995 Tektronix, Inc. All rights reserved. Tektronix is a registered trademark of Tektronix, Inc. <http://www.tek.com> 40A-MU6220

CIRCLE 92 ON FREE INFORMATION CARD

www.americanradiohistory.com



VIDEO NEWS

WHAT'S NEW IN THE FAST-CHANGING VIDEO INDUSTRY

BY DAVID LACHENBRUCH

Making DVD incompatible

One of the advantages of digital video recording is that it finally exorcises an old bugaboo—incompatibility among the world's television systems. Thus any video-recorded DVD disc can be playable on any TV set anywhere in the world, given the proper player (which converts the digital video to analog of the proper national standard). That might be the conventional wisdom—but to the movie industry, that's a major disadvantage. So Hollywood and the electronics-manufacturing fraternity have agreed on a scheme to wipe out that problem and, in fact, make interchangeability more restrictive than ever.

With videocassettes, the movie industry relies on incompatibility to orchestrate release dates, particularly between the United States and Europe. Because an NTSC videocassette is unplayable on a conventional PAL VCR, that results in a national barrier preventing premature release of movies in certain countries.

Most U.S.-made movies are released in this country before their European release. Release on videocassette follows theatrical release by varying periods, depending on the success of the movie in the theater. Thus a videocassette recorded in NTSC could be released here while the same movie is still playing in theaters in England, for example. In the eyes of the movie industry, that's an advantage. Even if a European were to bring a videocassette home from

the U.S., he or she couldn't play it on a standard British VCR, which will only play videocassettes in the PAL format.

Such artificial roadblocks don't exist with the digital DVD system. The same disc could be used anywhere in the world (and is made even more universal by being able to accommodate multiple soundtracks for various languages. But that very desirable feature would wipe out the movie producers' ability to control release of their films on home discs. The issue was brought to light by Louis Feola, president of MCA Home Video, who said that his company wouldn't release any of its films to DVD unless the situation were corrected. He was backed privately by several other movie companies.

After some hurried conferences, the DVD Forum, which developed standards for the system in the first place, agreed to consider a proposal which would go far beyond the use of national TV standards to block "interplayability" of discs. The proposal likely to be adopted would divide the world into five to seven different regions, based largely on the normal sequence of theatrical movie releases. Each region would be assigned a code to be installed as a digital flag on DVD discs. All players programmed for sale in each particular region would reject any disc designed to be sold in a different region.

Thus, for example a movie disc designed for sale in the U.S. would be unplayable on players in use in, say, South America or China. That flagging process reportedly is quite simple and wouldn't necessarily hold up the expected September

release date for DVD players and discs.

Copyright problems remain

A more serious barrier to the release of DVD movies is the copying problem. Because perfect digital-to-digital copies and near-perfect digital-to-analog copies could be made from DVDs, movie companies are balking about releasing their films on DVD before a law is in place to bar copying of digital discs. Although there is agreement between manufacturers and producers about the contents of such a law, the technical details must still be spelled out, and its passage is far from certain.

While the contents of the agreement had not been released by our press time, it's understood that it involves a technology called Copy Generation Management System (CGMS), which would make it impossible to make a digital copy of a digital disc. To block copying of DVDs onto analog media, such as videocassettes, the legislation is expected to specify "Colorstripe" technology developed by Macrovision. Colorstripe would make bootleg analog copies of digital discs virtually unwatchable because of the presence of disturbing stripes of color.

Although the precedent for digital video anti-copy legislation is the Audio Home Recording Act (AHRA), there are major differences. The AHRA permits one direct digital copy to be made from a digital audio recording (CD or DAT), but prevents that copy from

continued on page 49

Take this GIANT CIRCUIT LIBRARY FOR ONLY \$14⁹⁵

when you join the *Electronics Engineers' Book Club*[®]


Hundreds of circuit ideas alphabetically arranged—from Alarm circuits to Zero crossing detector circuits!

"...includes schematics for the latest electronics circuits from industry leaders..." —Popular Electronics

Turn to this comprehensive circuit library for hundreds of project ideas...and concise pinout diagrams and schematics. In each volume you'll find more than 700 electronic and integrated circuits and 100+ circuit categories right at your fingertips to give you ideas you can use on the job or at your workbench.

THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS

Volumes 1-4
by Rudolf F. Graf

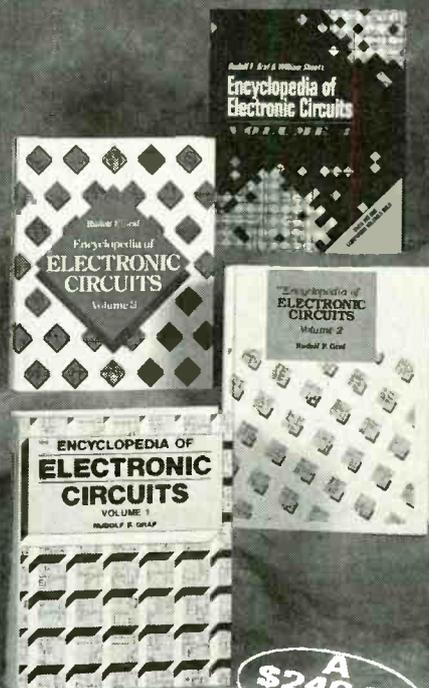

A \$240.00 Value

3,088 total pages
4,490 total illustrations

If coupon is missing, write to: Electronics Engineers' Book Club,
A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

As a member of the Electronics Engineers' Book Club...

...you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. And you'll be eligible for FREE BOOKS through the Bonus Book Plan. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time. Publishers' price shown. ©1996 EEBC

ELECTRONICS ENGINEERS' BOOK CLUB[®]

A Division of The McGraw-Hill Companies,
P.O. Box 549, Blacklick, OH 43004-9918

YES! Please send me *The Encyclopedia of Electronic Circuits—Vols. 1-4* (5861488), billing me just \$14.95 plus shipping/handling & sales tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days for a full refund and have my membership cancelled.

Name _____

Address/Apt. # _____

City _____

State _____

Zip _____ Phone _____

Valid for new members only, subject to acceptance by EEBC. Canada *must* remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders. RPIF596



Q & A

READERS QUESTIONS, EDITORS ANSWERS

Timing Light As Stroboscope

Q I have a timing light which operates off a car battery and a connection to a spark plug wire. Is there some way to modify the light for use as a stroboscope? — M. M., Elko, Nev.

A A timing light is a special kind of stroboscope that flashes whenever a particular spark plug fires, enabling you to see what position the engine is in at that moment. What you need is a way to trigger it

through a spark plug wire.

Timing lights that connect directly to a spark plug aren't so easy to fool; they are triggered by the high voltage from the ignition coil, which isn't easy to simulate safely.

Bear in mind that the maximum frequency of a timing light is about 20 Hz. Above that frequency, timing lights tend to skip pulses. You might be able to speed up a timing light by reducing the value of the high-voltage capacitor across the flashtube; the light will then be dimmer, but the capacitor will

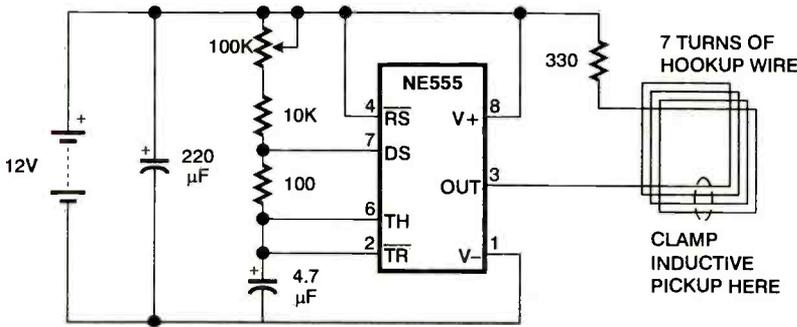


FIG. 1—THIS OSCILLATOR will trigger a timing light for non-automotive use as a stroboscope.

without using an automobile engine.

There are two ways a timing light might attach to the wiring of the engine: by direct connection or through an inductive pickup. If your timing light has an inductive pickup, you're in luck — you can use the circuit in Figure 1 to trigger it. The NE555 produces brief pulses of current in the wire, which is wound into a loop to increase the amount of induction; we used seven turns, but one or two turns may suffice. To the timing light, these pulses look like the pulses that flow

charge up more quickly for the next flash.

Xenon Flashtube Theory

Q I'm interested in building a battery-operated flasher circuit using a xenon strobe tube. I understand that the xenon tube operates in the kilovolt range. Any ideas? — D. B. S., Saylorsburg, Pa.

A The actual operating voltage across a xenon flashtube is about 300 volts, stored in a capacitor as shown in Fig. 2. To make the tube

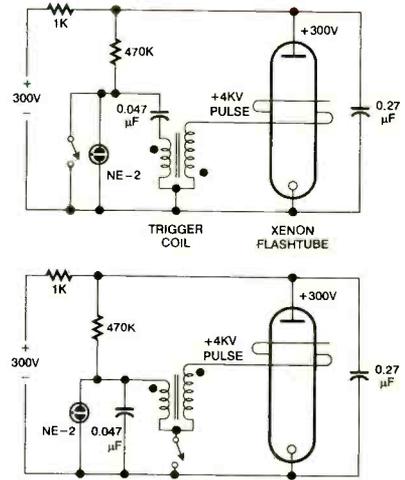


FIG. 2—BASIC CIRCUITS FOR FLASHING a xenon tube. Choose the circuits that fits the polarity of the trigger coil.

flash, a step-up transformer called a *trigger coil* provides a momentary pulse of several kilovolts to a wire wrapped around the middle of the tube. This is coupled capacitively to the gas inside the tube and makes it start to ionize. As soon as the gas becomes conductive, the capacitor discharges through the flashtube and there is a bright flash of light; then the capacitor has to charge up again for the next flash.

The trigger pulse, in turn, comes from a smaller capacitor which is charged up to about 70 volts and then suddenly discharged through the primary of the trigger coil. As Figure 2 shows, the exact circuit depends on the polarity of the trigger coil, indicated by dots in the diagram; if in doubt, simply try it both ways.

The NE-2 lamp serves as a voltage regulator and "ready" light. The switch can be replaced by an SCR.

Now all you need is a battery-operated 300-volt power supply. The easiest way to get one is to use

What's better than speed reading? *Speed Learning.*

Speed Learning has replaced speed reading. It's a whole new way to read and learn. It's easy to learn...lasts a lifetime... applies to everything you read. It may be the most productive course you've ever taken.

Do you have too much to read and too little time to read it? Do you mentally pronounce each word as you read? Do you frequently have to go back and reread words, or whole paragraphs, you just finished reading? Do you have trouble concentrating? Do you quickly forget most of what you read?

If you answer "Yes" to any of these questions — then here at last is the practical help you've been waiting for. Whether you read for business or pleasure, school or college, you will build exceptional skills from this major breakthrough in effective reading, created by Dr. Russell Stauffer at the University of Delaware.

**Not just "speed reading" — but
speed reading — thinking —
understanding — remembering —
and — learning**

The new *Speed Learning Program* shows you, step-by-proven step, how to increase your reading skill and speed, so you understand more, remember more and use more of everything you read. The typical remark from over one million people taking the *Speed Learning* program is, "Why didn't someone teach me this a long time ago." They were no longer held back by their lack of skills and poor reading habits. They could read almost as fast as they could think.

What makes Speed Learning so successful?

The new *Speed Learning Program* does not offer you a rehash of the usual eye-exercises, timing devices, and costly gadgets you've probably heard about in connection with speed reading courses, or even tried and found ineffective.

In just a few spare minutes a day of easy reading and exciting listening, you discover an entirely new way to read and think — a radical departure from anything you have ever seen or heard about. *Speed Learning* is the largest selling self-study reading program in the world. Successful with Fortune 500 corporations, colleges, government agencies and accredited by 18 professional societies. Research shows that reading is 95% *thinking* and only 5% eye movement. Yet most of today's speed reading programs spend their time teaching you rapid eye movement (5% of the problem), and ignore the most important part, (95%) *thinking*. In brief, *Speed Learning gives you what speed reading can't.*

Imagine the new freedom you'll have when you learn how to dash through all types of reading material at least twice as fast as you do now, and with greater comprehension. Think of being able to get on top of the avalanche of newspapers, magazines and correspondence you have to read...finishing a stimulating book and retaining facts and details



FOR FASTER SHIPMENT CALL 1-800-729-7323 OR FAX 1-609-273-7766

more clearly, and with greater accuracy, than ever before.

Listen — and learn — at your own pace

This is a practical, easy-to-learn program that will work for you — no matter how slow a reader you think you are now. The *Speed Learning Program* is scientifically planned to get you started quickly...to help you in spare minutes a day. It brings you a "teacher-on-cassettes" who guides you, instructs, and encourages, explaining material as you read. Interesting items taken from *Time Magazine*, *Business Week*, *Wall Street Journal*, *Money*, *Reader's Digest*, *N.Y. Times* and many others, make the program stimulating, easy and fun...and so much more effective.

Executives, students, professional people, men and women in all walks of life from 15 to 70 have benefited from this program. *Speed Learning* is a fully accredited course...costing only 1/4 the price of less effective speed reading classroom courses. Now you can examine the same easy, practical and proven methods at home...in your spare time...without risking a penny.

Examine Speed Learning RISK FREE for 15 days

You will be thrilled at how quickly this program will begin to develop new thinking and reading skills. After listening to just one cassette and reading the preface, you will quickly see how you can achieve increases in both the speed at which you read, and in the amount you understand and remember.

You must be delighted with what you see, or you pay nothing. Examine this remark-

able program for 15 days. If, at the end of that time you are not convinced that you would like to master *Speed Learning*, simply return the program for a prompt refund. (See the coupon for low price and convenient credit terms.)

RISK-FREE ORDER FORM

YES! I want to try *Speed Learning* for 15 days without risk. Enclosed is the first of 4 monthly payments of \$32.25*. If I'm not completely satisfied, I may return it for a prompt refund.

SAVE 8.00! I prefer to pay the \$129.00 now, and save the \$8.00 shipping & handling charge. I may still return the program for a full refund.

Method of payment: (Federal Tax Deductible)

Check or money order payable to Learn Incorporated

Charge to: Visa MC Am Ex Discover

Card # _____ Exp. _____

Signature _____

Phone (_____) _____

Name _____

Address _____

City _____ State _____ Zip _____

*Plus \$8.00 shipping and handling. U.S. funds only. For New Jersey residents, sales tax will be added.

Learn Dept. LEC-01, 113 Gaither Drive,
INCORPORATED Mt. Laurel, NJ 08054-9987

EARN YOUR B.S. DEGREE IN COMPUTERS OR ELECTRONICS



By Studying at Home

Grantham College of Engineering, now in our 45th year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, modem, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Grantham offers three separate distance-education programs, leading to the following accredited degrees;

(1) The B.S.E.T. with Major Emphasis in Electronics.

(2) The B.S.E.T. with Major Emphasis in Computers.

(3) The B.S.C.S. — the Bachelor of Science in Computer Science.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by
the Accrediting Commission of the
Distance Education and
Training Council

GRANTHAM
College of Engineering
Grantham College Road
Slidell, LA 70460

a junked photographic flash unit, which will also contain the xenon tube and trigger coil. For complete instructions on converting a camera flash into a stroboscope, see our sister publication, *Popular Electronics*, November 1995, pp. 77-78 (available from our reprint bookstore). And remember, *strobe circuits are dangerous*; the capacitor in a camera flash can deliver a painful or even lethal shock. Always be sure to discharge every high-voltage capacitor through a 1-kilohm resistor before touching any of the components.

Rain Alarm

Q I need a circuit that will operate a relay or solid state switch when a sensor detects water or rain. — D. B., Aggasiz, B.C., Canada.

A Fig. 3 shows a circuit that will do the job. It relies on the ability of water to conduct electricity. The sensor consists of two pieces of metal just close enough together that a drop of water will bridge them. An especially good sensor can be made out of two pieces of a metal comb, arranged as shown in the diagram, but much simpler sensors will often do the job. To be sure of catching the first drop of rain, you might feed the sensor through a funnel; make sure it's open to the air so that the water will dry up

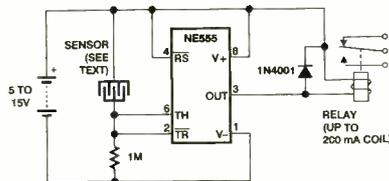


FIG. 3—THIS RAIN DETECTOR circuit closes the relay when water bridges the gap between the metal electrodes.

when the rain ends.

Electrically, the circuit uses a 555 timer IC as a level detector. The 555 supplies *hysteresis*—that is, its turn-on voltage is higher than its turn-off voltage—and this keeps the relay from "chattering" when a barely-detectable amount of water is present. You can use any low-voltage relay whose coil draws no more than 200 mA; solid-

state relays will also work fine.

If the water you want to detect is very pure (such as distilled water leaking from a tank), it may not conduct electricity; in that case, increase the 1-megohm resistor to 2.2 megohms. On the other hand, if the circuit trips too easily and gives false alarms, decrease the resistor to 220k.

Tubes For FETs

Q I have several pieces of useful tube-type RF and audio equipment that I would like to convert to use FETs in place of the tubes. I could start from scratch, but would feel better if I could benefit from others' experience. Do you know of any publications on tube-to-FET conversions, or could you give me some basic guidelines? Thanks. — B. G., Bellefontaine, Ohio.

A There is enough electrical similarity between vacuum tubes and N-channel junction field-effect transistors (JFETs) that you can sometimes substitute one for the other. The catch is that most FETs can't handle the high voltages; there is tremendous unit-to-unit variation among FETs of the same type, so you may have to select particular units; and the overall conductance of an FET is higher, so you'll have to add some resistance in series with the FET.

The classic article on tube-to-FET conversion, by Howard Sartori, appeared in *QST*, April 1977, pp. 45-50, with follow-ups in September 1977, pp. 38-39, and December 1978, p. 39. (We can't supply copies of this, but your public library can probably obtain them.) Sartori used a special 300-volt JFET, the 2N6449, which is, unfortunately, apparently no longer available.


The best way to convert tube equipment to use FETs nowadays is to reduce the supply voltage to about 20 volts, then put an FET in place of the tube and adjust the values of other components as required. You can use Sartori's circuits as a starting point, but considerable experimentation will be necessary. Fortunately, when the conversion is done, the circuits will be more stable and will consume less power.

EN

Two ways to fit a 100 MHz benchtop scope in your hand.



Bigger hands.

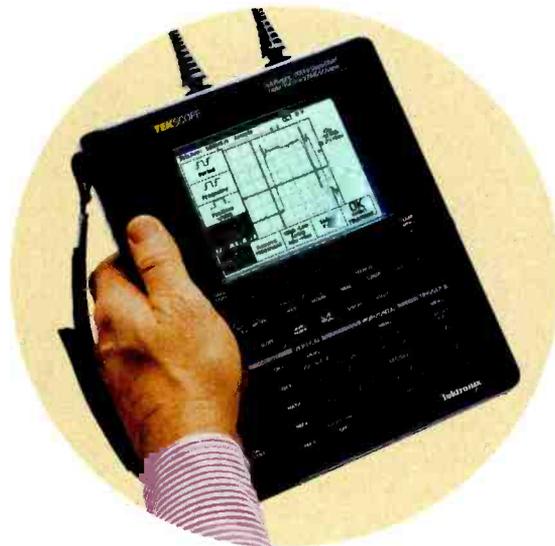

TekScope™



Got huge hands? Then you can probably lug a benchtop scope around the field. For the rest of us, there's TekScope™, the first hand-held with true 100 MHz bandwidth and 500MS/s sample rate on both channels. It's got the familiar Tek interface, a bright, backlit display and is priced at just \$2195 MSRP. Call 1-800-479-4490, action code 709, or visit our Web site at <http://www.tek.com>.

Tektronix



LETTERS

SEND YOUR COMMENTS TO THE EDITORS OF ELECTRONICS NOW MAGAZINE

SOUPED-UP ALTERNATOR

R. Christman, whose letter appeared in "Q&A" in the January issue of *Electronics Now*, might be interested to know that the ampacity of at least some automotive alternators can be increased.

I use a full-size Ford to tow a travel trailer. When I bought the car a number of years ago, I soon discovered that the alternator was not up to the task. I obtained an exchange stator for the alternator from a friend in the automotive electric business. That stator had been rewound by a remanufacturer to allow the alternator to put out 100 amps. I'm not sure what the stock alternator was, although it was probably rated at 60 amps. The original rectifier/regulator assembly was reused. After I rebuilt the alternator (using new bearings and brushes as well as the beefed-up stator), I had it tested and found that it could actually put out up to 120 amps. That alternator has been going for many years now, and the diodes and regulator have survived.

The edited note from R. Christman did not indicate what type of car he is dealing with, but it might be worth his while to check with a local automotive electric business.

PETER KNIP

Gilliam, Manitoba, Canada

ELUSIVE HUM

Larry Klein's "Audio Update" column discussing the "elusive hum" in Taos, New Mexico (*Electronics Now*, December 1995) reminded me of a letter published in *Electronics World* (*Wireless World*)

in their October, 1995 issue. After making references to a similar mysterious noise, the writer stated, "I found the cause of the sound by accident when I was holidaying in France. A sewerage pump went out of order for a few days, and the low-frequency tone disappeared (there was no other pump for several miles around.) It sounds to me as if that very perceptive person has precisely identified the source, and it certainly "is real and entirely natural."

By the way, thanks for all the material on noisy school dances. I would like to suggest another sonic problem area in schools: their band programs. My daughter has been participating in the marching band program, both as a musician and as a color guard performer. She has reported ringing in her ears for a time after several performances. That problem is potentially more severe than noisy dances, because the events (and practice sessions) are a great deal more frequent.

MIKE HARDWICK

Salem, OR

I am sure that machinery of one kind or another is responsible for many mysterious noises all over the world, but it seem illogical to me to generalize from a French sewerage pump to a phenomenon in the Southwestern United

States. It's a safe bet that if a noisy U.S. pump were the culprit, the investigators in the area would have found it.

Thanks for alerting me to the various school band programs as a potential source of ear damage. Regular participants in such events would be well advised to invest in ear protectors such as the EPA-rated E-A-R Hi-Fi Earplugs. They are designed not for maximum attenuation, but rather for an approximately 12-dB reduction across the audio band while preserving a natural sound quality. Write to Cabot Safety Corporation, 5407 West 79th Street, P. O. Box 78130, Indianapolis, IN 46268-8130; phone 317-872-0330; or fax 317-872-5993.—Larry Klein

SORRY, MAC

"Buy a Macintosh!" was the title of a letter that appeared in the March 1996 issue of *Electronics Now*. Well, all I have to say is, "Sorry, Mac."

From what I've observed over the last several years, the Macintosh computer is going the way of the Sony Betamax recorder. Regardless of how many users attempt to protect the machine, no matter how much better its processor than the competition's, people are going to go for the system with the best software and hardware support (IBM and its clones).

My information has been gleaned from break rooms and retail stores. From the common folk, people who want to buy a computer and not have to scour the stores for hardware or software compatible with their "type" of machine. Just ask any Tandy 1000 owner and you'll see what I mean.

Write To:
Letters,
Electronics Now Magazine,
500 Bi-County Blvd.,
Farmingdale, NY 11735

Due to the volume of mail we receive, not all letters can be answered personally. All letters are subject to editing for clarity and length.

I'm not going to defend one architecture against another (I've never owned a Mac (although I have owned a TI-99 and a Color Computer II. I've decided that it's much better to buy a Ford Model T than a Daimler Benz automobile when you live in the United States. One might be better than the other, but try buying accessories (or service) for one or the other and you'd see what I mean.

The word from the break rooms is that Apple is looking for a buyer for the company. Apparently, the school systems in America (major financial backers for Apple) are switching to IBM computers. It seems that they are waking up to the fact that training kids on Macs and sending them into an IBM world is a losing proposition. Also, parents are getting tired of having to buy both types of computer, one for them and one for the kids. And the kids are losing.

If you are a Mac supporter, good for you. I stand behind your decision and wish you luck in your endeavors. If you are undecided about what to purchase for your initial system and are computer illiterate (as we all were, at one time), look around your town. Ask your friends what they use. And, in the end, remember that the final decision is yours and that you will have to live with that decision for a while.

RANDY JONES
Colville, WA

LOW-COST PCB-SOFTWARE ADDITION

I enjoyed the recent reviews of low-cost schematic capture/simulation and PCB software packages (*Electronics Now*, February 1996). However, since the reviewer covered each area separately, he overlooked a great package offered at a super price. Protel Technology bundled their DOS-based schematic-capture and PCB programs in a packaged called DOS Pack Design System, which sells for \$395.

It features Autotrax, an enhanced version of Easytrax (reviewed in the January issue of *Electronics Now*). The DOS Pack schematic/PCB system includes 3000 components, a PCB footprint library, a component editor, full auto placement, an auto router,

design verification and rule checking, SMD support, linking to 99 sheets, and much more.

In addition, the Autotrax netlist function is compatible with many popular formats. Although Autotrax is a DOS-based program, it is very stable running under Windows. I was able to switch between it and my electronic-simulation software without any problems. In fact, Autotrax quickly (and easily) converted my designs to a prototype-ready layout in just a few minutes. When compared to other programs on the review chart, I found Autotrax ranked first. It received a "Yes" in every category except the ability to neck down between pads.

Protel previously offered the system for as much as \$1590. At \$395, it is a lot of power for a little price. If offered separately, the schematic-capture and PCB programs would cost less than \$200 each, putting them in the range of your reviews. After trying the demo and comparing the competition, I've decided to order DOS Pack. The demo can be found on the Protel BBS at 408-243-0125 or on the Internet at <http://www.protel.com>.

GEORGE JULIAN
Boise, ID

BAN THE 741 IC!

I am a long-time subscriber to *Electronics Now* and rely on it for the latest electronics news and techniques. I have seen several articles using the 741 op-amp. That chip is an embarrassment to the audio world and should be replaced. It has a low slew rate and a high noise figure. Its only redeeming features are its price and availability.

Younger readers and others new to audio electronics need to be informed of other ICs that can be used to provide superior performance, such as the AD744 and 5543. Those chips are among the best performing audio ICs when combined with high-grade capacitors, low-noise resistors, and regulated power supplies.

In the future, please instruct your authors not to use a sub-standard chip like the awful 741.

WARREN BAIN
Bristow, VA

Find the Right Electronic Component Fast



D.A.T.A./P/A/L™ D.A.T.A. Parametric Access Library

This PC-based CD-ROM reference offers fast, easy access to over 1.6 million current and discontinued ICs and discrete semiconductors. Custom configured to your specifications, D.A.T.A./P/A/L provides up to 25 parametric values and references over 1,100 component manufacturers. (Prices start at \$360/Category)

D.A.T.A.

A Division of Information Handling Services Inc.

D.A.T.A. Business Publishing
tel: 800-447-4666 Ext. EPG-B
303-799-0381 Ext. EPG-B
fax: 303-799-4082
data.product.management@ihs.com

ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR
**B.S.E.E.
DEGREE**

THROUGH HOME STUDY

Our Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete the program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through our Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the engineering level. Advance rapidly! Many finish in 12 months or less! Students and graduates in all 50 states and throughout the world! Established Over 50 Years! Write or call for free Descriptive Literature. (601) 371-1351

COOK'S INSTITUTE
OF ELECTRONICS ENGINEERING



4251 CYPRESS DRIVE
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD



EQUIPMENT REPORTS

A VIRTUAL OSCILLOSCOPE AND RECORDER FROM MISSION TECHNOLOGY.

Turn your personal computer into a multipurpose laboratory test instrument with Multiscope.

CIRCLE 15 ON FREE INFORMATION CARD



Every electronic hobbyist dreams of owning a complete set of laboratory-grade electronic test instruments to speed up circuit test procedures and analyze faults quickly and accurately. The principal obstacle, of course, has been the expense. A complete set of dedicated instruments could cost thousands of dollars, a drain on the hobbyist's budget, particularly if he or she has a family, rent to pay, and food to put on the table. This is where computer based virtual instruments enter the picture.

Thanks to the availability of fast, powerful, personal computers at low prices and inexpensive virtual instrument hardware and software, the goal of obtaining many of those instruments can be achieved for less than \$400—assuming you own a late model IBM or compatible computer. It is true, however, that some compromises must be made because virtual instruments do not quite match the performance of their stand-alone, dedicated counterparts.

A new virtual instrument from Mission Technology, Inc. (PO Box 3016, Teaneck, NJ 07666, 1-800-880-7688) turns a personal computer into a digital storage oscilloscope, a real-time strip-chart recorder, a dual digital voltmeter, a digital frequency counter, a waveform analyzer and a spectrum ana-

lyzer for only \$399.

The Multiscope Responsive Oscilloscope (see Fig. 1) connects to a parallel port on an IBM-compatible computer. The software included with the virtual instrument module runs under the Microsoft Windows operating system, and the computer provides both the control and display functions.

The responsive oscilloscope case has two BNC jacks, one for channel A and the other for channel B, and a D-type output connector on its front panel. The virtual oscillo-

scope has 16 frequency ranges and the recorder has a user-definable sampling interval from 0.055 second to eight hours and a buffer for up to 16,000 samples per channel.

The Multiscope has a digital bandwidth of 20 MHz and an analog bandwidth of 1 MHz. Input impedance is 1-megohm, and it has an eight-bit multiplexed input connector and AC or DC coupled triggering. Accuracy is specified as within 5% for signals of 200 kHz or less. Display update speed is directly linked to the speed of the computer's microprocessor. For example, a personal computer with an Intel i486 DX2 50 MHz processor can update the screen about once every half second on most time-base ranges.

The oscilloscope display has a built-in digital presentation of DC, RMS, and peak-to-peak AC volts and frequency. Oscilloscope settings can be made automatically or

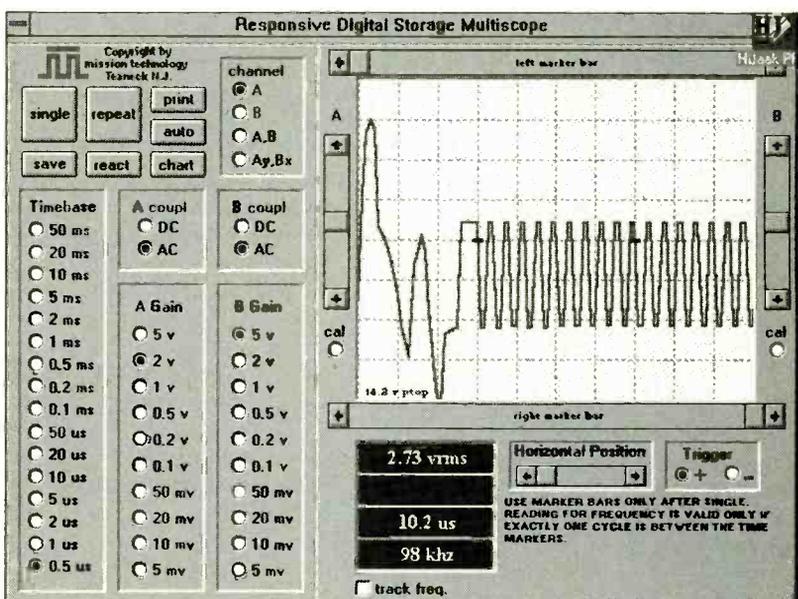


FIG. 1—THE VIRTUAL STORAGE OSCILLOSCOPE display as it will appear on your computer's monitor.


Better Designs —Faster

Guaranteed with Electronics Workbench!

Just click and drag to create and edit schematics. Mix analog and digital devices in any combination with full control over values, models and behavior. Try 'what if' scenarios and fine tune effortlessly. And on-screen waveforms always match actual circuit response. You'll create better designs faster—*Guaranteed!*

Guaranteed Satisfaction

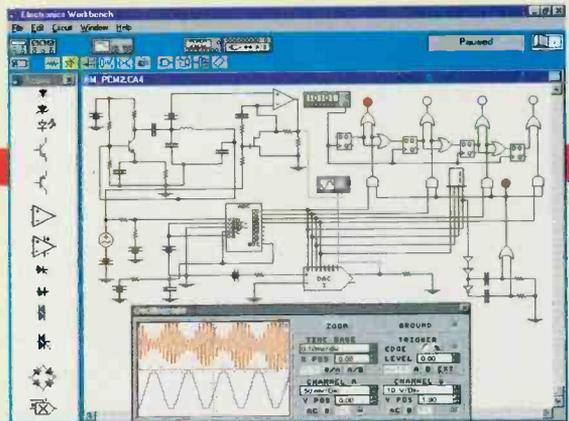Join over 40,000 customers and experience the power, flexibility and value that only Electronics Workbench offers. Receive unequalled service and free, unlimited technical support by phone, fax, e-mail, WWW, CompuServe and BBS. You'll be delighted. *We guarantee it.**



True Mixed-Mode Power

Connect any analog or digital device to any other device without limit. Only Electronics Workbench offers this professional power for under \$2,000.

Real-World Digital


Real-world TTL and CMOS, complete with propagation delays and fanout. Unique at this price.

32-Bit Speed

Integrated SPICE analog and native-mode digital simulation in full 32-bit. Unique at this price.

Real-World Results

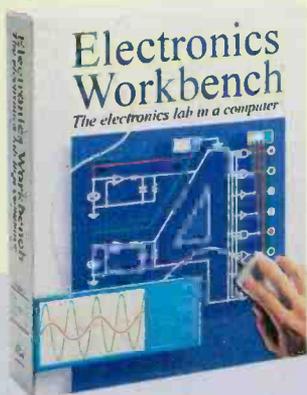Unlimited supply of over 200 components and ICs and 350 real-world models—all perform as real devices.



Electronics Workbench®

\$299

*30-DAY MONEY-BACK GUARANTEE

VERSION 4.1 FOR WINDOWS 95/NT/3.1, DOS AND MACINTOSH.

Ask about our Engineer's Pack with thousands of additional models and more. Version 4.0 users call for your free upgrade.

800-263-5552



Fax: 416-977-1818 Internet: <http://www.interactiv.com>
CompuServe: 71 333,3435/BBS: 416-977-3540/E-mail: ewb@interactiv.com

INTERACTIVE IMAGE TECHNOLOGIES LTD., 908 Niagara Falls Boulevard, #068, North Tonawanda, New York 14120-2060/Telephone 416-977-5550
TRADEMARKS ARE PROPERTY OF THEIR RESPECTIVE HOLDERS. OFFER IS IN U.S. DOLLARS AND VALID ONLY IN THE UNITED STATES AND CANADA. ALL ORDERS SUBJECT TO \$15 SHIPPING AND HANDLING CHARGE

Australia: 2-519-3933 • Belgium: 2-384-73-09 • Brazil: 11-453-5588 • Chile: 2-236-0300 • Cyprus: 2-62-1068 • Czech Republic: 42-48-23454 • Denmark: 33-25-0109 • Finland: 0-297-5033 • France: 14-908-9000 • Germany: 711-62-9740 • Greece: 1-524-9981 • Hungary: 1-215-0082
India: 11-578-7055 • Indonesia: 21-470-0815 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-3382-3136 • Malaysia: 3-774-2189 • Mexico: 5-593-5260 • Netherlands: 18031-7666 • New Zealand: 9-267-1756 • Norway: 22-16-7045 • Philippines: 973-27-0118
Portugal: 1-81-46609 • Singapore: 777-2303 • Slovenia: 61-317-830 • South Africa: 331-6-8309 • South Korea: 2-2-222-3431 • Spain: 1-383-8335 • Sweden: 8-740-5500 • Taiwan: 886-2-366-0080 • Thailand: 66-2-398-6952 • UAE: 4-453505 • UK: 203-23-3216


CIRCLE 126 ON FREE INFORMATION CARD




155016X \$34.95
Hardcover




0404348-XX \$49.50
Counts as 2/Hardcover

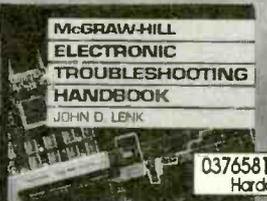

0376581 \$39.50
Hardcover

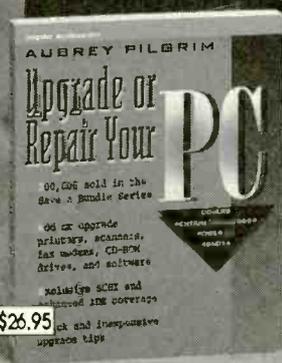

0501149 \$26.95

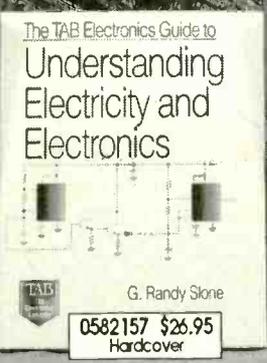


0582157 \$26.95
Hardcover




9119018-XX \$32.95
Counts as 2

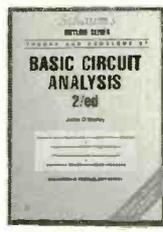The leading source of information for electronics hobbyists for over 30 years!




0478244 \$13.95

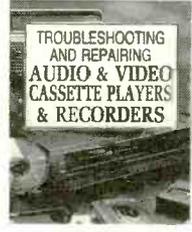

1577564 \$22.95



0156786 \$24.95

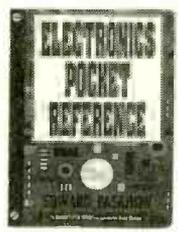

0487375 \$24.95




0717753 \$19.95




076509X \$17.95




0497060 \$29.95
Hardcover

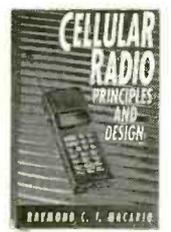


0443017 \$50.00
Hardcover

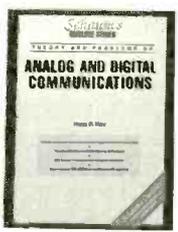


0306362 \$13.95

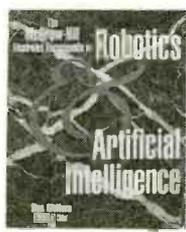

0236135-XX \$40.00
Counts as 2/Hardcover

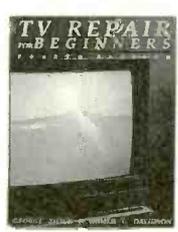


073092X \$19.95

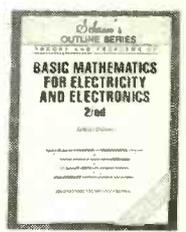

0044392 \$12.95




0380899-XX \$60.00
Counts as 2/Hardcover

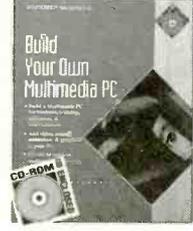


9122264-XX \$39.95
Counts as 2




0155593 \$22.95

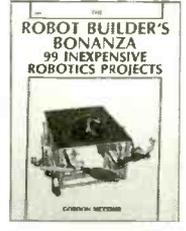

1571469 \$18.95

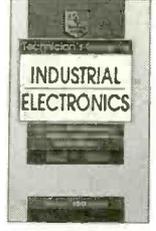

0112738 \$45.00
Hardcover

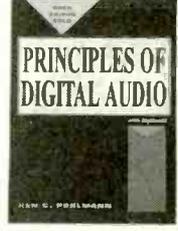

0504687-XX \$59.00
Counts as 2/Hardcover


As a member of the ELECTRONICS BOOK CLUB®... you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.
A shipping/handling charge and sales tax will be added to all orders. All books are softcover unless otherwise noted. If you select a book that counts as 2 choices, write the book number in one box and XX in the next. (Publishers' Prices Shown) ©1996 EBC

PHONE 1(614)759-3666 • FAX 1(614)759-3749
(8:30 a.m. - 5:00 p.m. EST Monday-Friday) (24 hours a day, 7 days a week)


5 BOOKS FOR ONLY \$4.95

Plus 1 book FREE upon prepayment


VALUES TO \$243.90

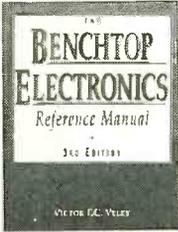

0673764-XX \$54.95
Counts as 2/Hardcover

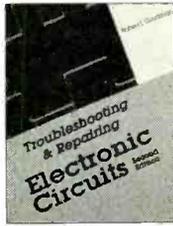


1573119 \$19.95

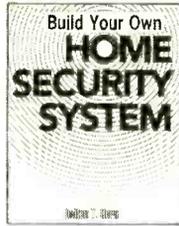

0303932 \$17.95




1561579 \$17.95

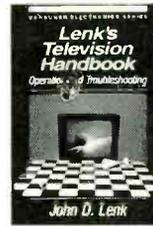


0375178 \$39.50
Hardcover



0304165 \$26.95
Hardcover

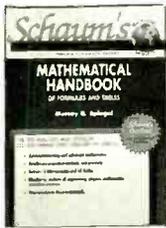

0602247 \$13.95

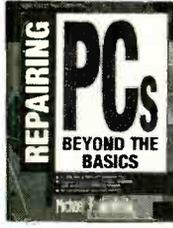

0305226 \$34.95
Hardcover




Q650772 \$34.95
Hardcover




0304122 \$17.95




0376026-XX \$45.00
Counts as 2/Hardcover

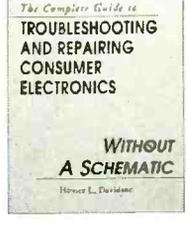


0156492 \$34.95
Hardcover

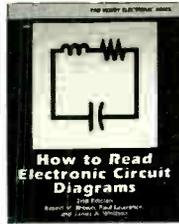

1554637 \$16.95

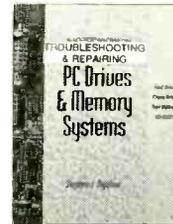


0053146 \$24.95

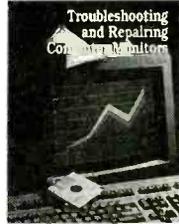

0054088-XX \$42.95
Counts as 2/Hardcover




1575472 \$27.95

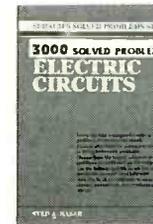


0459363-XX \$22.95
Counts as 2




0707618 \$19.95

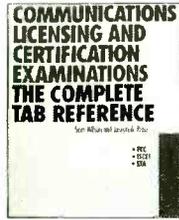


0708223-XX \$44.95
Counts as 2/Hardcover

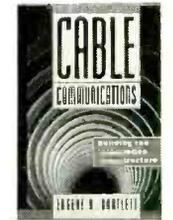

0053553-XX \$50.00
Counts as 2/Hardcover

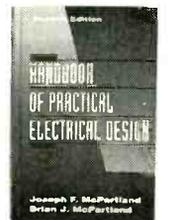


0458200-XX \$62.50
Counts as 2/Hardcover

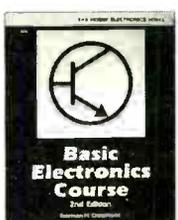

1574875 \$19.95



0052387 \$28.95
Hardcover

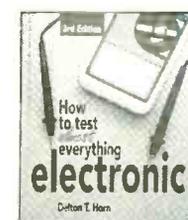

0304068 \$15.95



If coupon is missing, write to: Electronics Book Club®, A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918



Electronics Book Club

A Division of The McGraw-Hill Companies
P.O. Box 549, Blacklick, OH 43004-9918

YES! Send me the 5 books listed below, for \$4.95 plus shipping/handling & tax, and enroll me as a member of the **Electronics Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled.

--	--	--	--

If you select a book that counts as 2 choices, write the book number in one box and XX in the next box.

- Bill me** (FREE book not available with this payment option.)
 - Yes!** I want the FREE BOOK indicated at right. My introductory payment of \$4.95 plus \$4.95 shipping/handling and applicable sales tax is enclosed.
 - CHECK OR MONEY ORDER ENCLOSED PAYABLE TO:** The McGraw-Hill Companies
- Please charge my:** VISA Master Card American Express Discover

Code # of my
FREE BOOK:

SINGLE
SELECTION ONLY

ACCT# _____ Exp. Date _____

NAME _____ SIGNATURE _____ (required on all orders)

ADDRESS/APT. # _____

CITY _____ STATE _____ ZIP _____ PHONE _____

Valid for new members only, subject to acceptance by EBC. U.S. orders are shipped 4th class Book Post. Applicants outside the U.S. and Canada will receive special ordering instructions. Canada must remit in U.S. funds drawn on U.S. banks. Canadian orders are shipped International Book Post - add \$9.25 shipping/handling. A shipping/handling charge and sales tax will be added to all orders.

RE596C

May 1996, Electronics Now

Raise your standard to Wavetek.

Why choose between paying more for a brand name or getting more functions for your money? Get the best of both worlds with Wavetek.

Worldwide Service.

Support whenever and wherever you need it.

Tech-preferred Features.

The XL meters have the largest displays, auto-off, data hold, manual and autoranging models in pocket-size convenience.

Quality. Less than 0.5% warranty returns assures continuous reliability.

Selection. Over 35 different Wavetek DMMs to meet any measurement need.

User Safety. Conservative voltage ratings, fused inputs, warning beepers, shrouded test leads, and designs that meet worldwide agency approvals.

Total Value. Eight XL Series meters from \$29.95 to \$99.95 to meet any requirement.

You don't need to pay more.
You can't afford to settle for less...

For the name and location of the Wavetek dealer near you, call

1-800-854-2708

(outside the U.S., call 619-279-2200)

WAVETEK



Wavetek Corporation
9045 Balboa Avenue,
San Diego, CA 92123

©Wavetek Corp., 1995. Wavetek and the Wavetek logo are registered trademarks of the Wavetek Corporation.

manually. There are ten gain ranges from 5 volts per division to 5 millivolts per division. The test results can simply be viewed, or they can be saved to disk, or printed out.

The system provides protection against overvoltages up to 200 volts, transmitted electromagnetic interference from the computer is eliminated because the Multiscope circuitry is housed in a separate enclosure that acts as a shield. Moreover, the case can be located away from the computer. Input impedance is 1megohm. Multiscope has an eight-bit multiplexed input connector and it can be AC or DC triggering. An AC to DC adapter, two BNC 1 to 1 probes with alligator clip leads, and a parallel printer cable are included in the purchase price.

Multiscope in action

The Multiscope is plugged into the personal computer's parallel port with the data cable provided, and it obtains its power from the AC to DC adapter supplied. An on/off switch is the only control on the unit, and an illuminated LED indicates when power is on.

The operating software is on one 3.5-inch floppy disk. An oscilloscope icon appears on the screen when the software has been successfully installed. Double-clicking on the icon will run the software only if the unit is turned on and connected to the computer's parallel port.

The software will automatically locate the parallel port to which the unit is connected. On our first attempt to run the software all we got was a message box saying that either our port was non-standard or that power was not on. Fortunately, this glitch was solved when we found that we forgot to connect the power cord to the Multiscope. Once power was applied, we were in business.

The first display that appears is the digital storage oscilloscope. Menus pop up when the controls are clicked. The display (see Fig. 1) shows the controls on the left side and the instrument display on the right. An oscilloscope-type display appears above a digital voltage (DC, RMS, and peak-to-peak) and frequency

continued on page 27



NEW PRODUCTS

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

Flash Multimode OTDR

DESIGNED FOR USE IN LAN fiber-optic cable installation and maintenance service, Wavetek's Flash Multimode Mini-OTDR (Optical Time Domain Reflectometer) offers simple four-button operation, allowing any technician to become proficient with its use with little training and in minimal time. At 3-1/2 pounds, the Flash Multimode is the smallest and lightest instrument of its type today.

It is available in 850-nm, 1300-nm, and dual-wavelength models.

The Flash Multimode can be used to test all physical media used in today's complex LAN applications, including copper cable and fiber optics. It provides all the features and functions needed for complete fiber-optic cable installation and maintenance testing, including a unique macro capability for recalling sequences of operations with the

push of a single button, ghost detection and elimination, and a small (5 nanosecond) pulse width.

Each standard model includes two rechargeable NiCd batteries with charger, Flash ROM-based Validation software, internal memory for storing 32 trace results, an operating manual, and a carrying case. The Pro models also include an AC adapter, an extended carrying case, Wintrace software for storing and viewing test results on a PC, and 512K extended memory for storing 50 additional traces.

Prices for the Flash Multimode OTDR start at \$9300 for the 850-nm Standard model.

WAVETEK CORPORATION

*Instruments Division
9045 Balboa Avenue
San Diego, CA 92123
Phone: 619-279-2200
Fax: 619-565-9558*




CIRCLE 20 ON FREE INFORMATION CARD

Instavu Oscilloscopes

SEVERAL NEW MODELS have been added to Tektronix' TDS700A series of InstaVu acquisition oscilloscopes and TDS 500B series of digital storage oscilloscopes. Both lines offer users the confidence of an analog scope and the power of a digital scope. Proprietary InstaVu signal-acquisition technology lets users capture up to 400,000 waveforms per second, making the new scopes as fast as the world's fastest analog scopes.

InstaVu is designed to quickly pinpoint and capture unpredictable, rapidly changing signals—infrequent glitches, metastable behavior, and time jitter—that might never be detected by conventional analog or digital scopes or specialized triggering. The technology combines

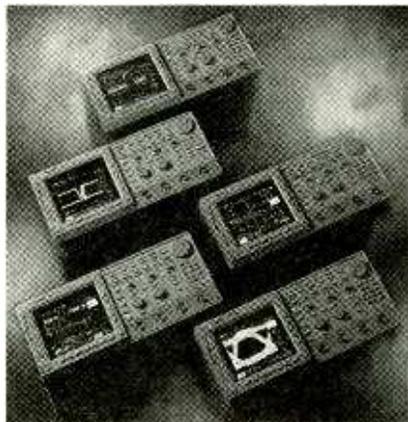high-speed acquisition memory with high-speed display rasterization to increase acquisition performance and ensure instantaneous live display of all signal changes. In design and debug applications, debug time is reduced from hours to seconds.



CIRCLE 21 ON FREE INFORMATION CARD

The TDS 784A, TDS 744A, and TDS 742A each feature color displays, bandwidths up to 1 GHz, sample rates up to 4 GS/s, and acquisition rates up to 400,000 Wfm/sec. The four-channel TDS 540B and the two-channel TDS 520B each feature 500-MHz bandwidth, up to 2 GS/s sample rate, monochrome displays, and up to 100,000 Wfm/sec acquisition rate. All models also offer extendible record length to capture and store complex, long-duration waveforms; sophisticated triggering capabilities, including setup/hold, slew rate, and time-out; and Channel Deskew, which increases time-measurement accuracy by compensating for external timing errors. A simple graphical user interface with more than 200 intuitive icons and on-line help makes the instruments easy to use.

The TDS 540B and TDS 520B cost \$14,950 and \$9500, respectively. The TDS 784A costs \$34,495. The TDS 744A and the TDS 724A cost \$17,950 and \$12,200, respectively.

TEKTRONIX MEASUREMENT BUSINESS DIVISION
*P. O. Box 1530
 Pittsfield, MA 01202
 Phone: 1-800-426-2200
 (when prompted, press 3 and ask for program 493)
 E-mail:*

22 <http://www.tek.com/Measurement>

Needle-Tip Pen Oiler

SYCON CORPORATION'S Lubit-8 Pen Oiler is filled with a lubricant containing Teflon[®] that is ideal for maintaining a wide variety of products, ranging from scientific instruments to cameras, guns, and fishing tackle. The lubricant is a blend of natural and synthetic oils with microminiature particles of Teflon and Fluon[®] held in permanent suspension. It is unaffected by -60°F to $+500^{\circ}\text{F}$ temperatures, is very slippery, resists dust, does not coagulate, and leaves no oily residue.

The Pen Oiler features a needle tip that precisely dispenses the lubricant, one drop at a time, making it well suited for use where sprays and oil cans are impractical. About the size of a fountain pen, the Lubit-8 can be clipped to a shirt pocket or carried in a field service kit.




CIRCLE 22 ON FREE INFORMATION CARD

The Lubit-8 Pen oiler is available in cartons of 36 units for a list price of \$93.24.

SYCON CORPORATION
*280 Eliot Street
 Ashland, MA 01721
 Phone: 508-881-8852
 Fax: 508-881-4703*

RF Power Transistors

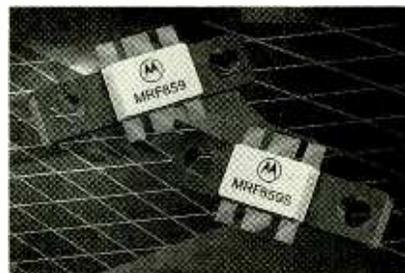MOTOROLA'S MRF859 AND MRF859S RF power resistors operate in the 800-960-MHz range with an output power of 6.5 watts. The rugged devices can be used in large-signal,



CIRCLE 23 ON FREE INFORMATION CARD


common emitter, class A linear amplifier applications in industrial and commercial equipment. Other features include a 11.5-dB minimum power gain, 3rd order intercept of $+47\text{-dBm}$ minimum, and a noise figure of 6-dB typical. The MRF859 power transistor is packaged in a flange case, and the MRF859S is in a flangeless package.

Pricing for the MRF859 and the MRF859S RF power transistors is \$48.62 in low volumes.

MOTOROLA, INC.—E 114
*5005 East McDowell Road
 Phoenix, AZ 85008
 Phone: 602-244-6108
 Fax: 602-244-4597*

Solder-on Adapters

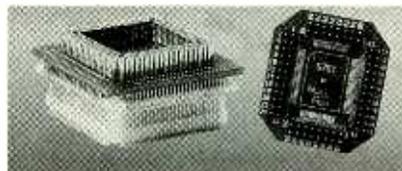DESIGNED FOR USE IN THE design and testing of new circuitry, where target ICs are sometimes unavailable, ITT Pomona's solder-on adapters offer an economical, risk-free, reliable test interface. As generic interfaces, the solder-on adapters work on standard EIAJ (metric) and JEDEC surface-mount technology layouts for any chips with the same lead pattern.



CIRCLE 24 ON FREE INFORMATION CARD

The adapters provide the crucial interface between circuit boards and test instruments so that engineers can design and test circuitry. Each base comes with a breakout board for connection to logic analyzers and other test instruments, with access via 0.025-inch square pins. Providing

secure connections, the solder-on adapters are an alternative to "reusable" adapters.

The solder-on adapters range in lead count from 80 to 240 pins, and are priced from \$260 to \$1190.


ITT POMONA ELECTRONICS

1500 East Ninth Street
Pomona, CA 91766-3835
Phone: 1-800-241-2060
Fax: 909-629-3317

Environmentally Safe Component Cooler

THE FEDERAL CLEAN AIR Act, which bans the intentional and non-essential release of CFCs, makes the old method of cooling components with canned CFC refrigerants obsolete. Containing no CFCs or HCFCs, Va-Tran Systems' COMP-CO²LD component cooler provides a convenient, safe, environmentally sound, and cost-effective way to perform localized component and circuit testing. It is intended for locating thermal inter-

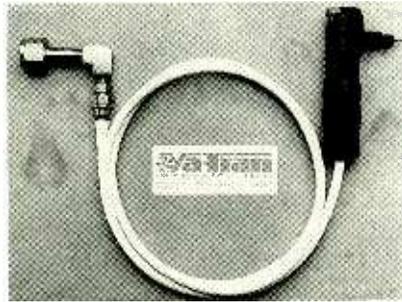mittent electrical components, cooling and testing boards for continuity or stress fractures, disassembling or mating tight-fitting metal parts, or for freezing adhesives for easy removal.



CIRCLE 25 ON FREE INFORMATION CARD

The COMP-CO²LD system, which uses common, recycled carbon dioxide, allows components to reach temperatures as low as -109°F. The spray pattern is easily adjustable, allowing the right amount of CO² to reach the test area. One small cylinder of CO² lasts for hours.

The COMP-CO²LD with a six-foot hose terminating in a standard CO² cylinder adapter costs \$350. A

complete system including a CO² cylinder and cart is available for \$650.

VA-TRAN SYSTEMS

677 Anita Street
Chula Vista, CA 91911
Phone: 1-800-379-4231
Fax: 619-423-4604

Subminiature Relays For Telecommunications

THE R70 SERIES OF SUB-miniature relays from NTE Electronics are specially designed for use in telecommunications, computer/peripheral equipment, and interface applications. The high-performance, 1-amp relays feature high sensitivity, compact design, fully sealed construction, and low power consumption. They are intended for use in OEM design and as replacement parts in telecommunications and computer equipment.

The R70 series is available in coil voltages of 3, 5, 6, 12, and 24 volts DC, and come standard with SPDT contacts. The relays weigh only 0.08

CABLE CONVERTER DIAGNOSTIC TEST CHIP

LOAD FULL ACTIVATION OF CABLE CONVERTER

WE STOCK A COMPLETE LINE OF CHIPS, TOOLS, WIRELESS QUICK INSTALL TEST BOARDS AND DIAGNOSTIC CUBES FOR ALL CONVERTERS!

*****ANYONE IMPLYING ILLEGAL USE WILL BE DENIED SALE. WE SELL PRODUCTS ONLY!! TO TECHNICIANS OR CABLE REPAIR FACILITIES!!**

#1 IN CUSTOMER SERVICE & TECH. SUPPORT!
*ALL ORDERS SHIP WITHIN 24HRS, UPS/ FED-X.
*PRIORITY NEXT DAY SHIPPING AVAILABLE!
*SALE= BUY 5 BOARDS GET 1 FREE TILL MAY96.
*LOWEST PRICE & SUPERIOR PRODUCT GUAR!!
*FRIENDLY COURTEOUS SERVICE. WE'RE PRO'S

VISA **VISUAL**

COMMUNICATIONS INC.
FOR ORDERS 1-800-GO-CABLE
CATALOG & TECH. SUPPORT 717-620-4363 EST. 1977

ANTIQUE RADIO CLASSIFIED
Free Sample!

Antique Radio's
Largest Circulation Monthly.
Articles, Ads & Classifieds.

6-Month Trial: \$17.95. 1-Yr: \$34.95 (\$51.95-1st Class).
A.R.C., P.O. Box 802-L15, Carlisle, MA 01741
Phone: (508) 371-0512 VISA/MC Fax: (508) 371-7129



PC Compatible

- Model 506 with built-in RS-232C optically isolated interface.
- Windows and DOS software allows data to be displayed analyzed and stored.



DMM

- True RMS AC Voltage and Current measurements.
- Dual backlit display for AC Voltage, Frequency and Temperature; and Relative Mode.
- Inductance, Capacitance and Decibel measurements.
- 10 memory locations, Min/Max/Avg mode for storing highest, lowest and average measurement value.

That has

- Temperature (°C and °F), Diode test and Continuity
- Buzzer plus Time and Stop Watch.
- Data hold, Auto power off, Logic probe and Signal output.
- Handheld, 20A input with warning beeper, overload protection on all ranges, test probes and RS-232 cable.


it All.
\$209⁹⁵



Free MS-DOS & Windows Systems



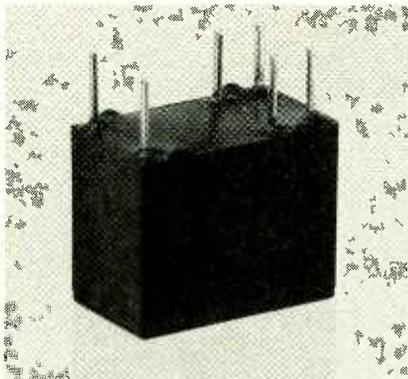154 Veterans Drive, Northvale, NJ 07647
Tel: (201)767-7242 Fax: (201) 784-0611



CIRCLE 26 ON FREE INFORMATION CARD

ounces and operate at temperatures ranging from -30°C to $+70^{\circ}\text{C}$. They feature dielectric strength of 1000 VAC between coil and contacts and 400 VAC between contacts of the same polarity. Resistance is 100 megohms maximum.

The R70 series, in 1000-piece quantities, costs less than \$2 each.

NTE ELECTRONICS, INC.


44 Farrand Street
Bloomfield, NJ 07003
Phone: 1-800-683-6837
(including Canada)
Fax: 1-800-683-3338

Robotics Project Board

THE HANDY BOARD, FROM the Media Laboratory at the Massachusetts Institute of Technology, is a microcontroller board intended for experimental and educational robotics projects. It is the latest in a series of boards released under MIT's free licensing policy, in which the PC board artwork, schematics, and even the driver software may be freely licensed for personal, educational, and commercial applications.

The compact, handheld board features the Motorola 68HC11 CPU with 32K of battery-backed RAM, a 16'2-character LCD screen, four DC motor outputs, 16 powered sensor inputs, infrared I/O, and a built-in nickel-cadmium rechargeable battery. The Handy Board runs Interactive C, a multitasking cross-platform development system for computers running the MS-DOS, Macintosh, and Unix operating systems.

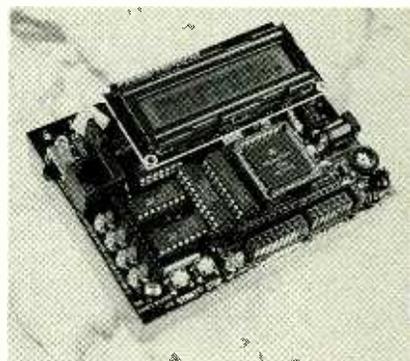Assembled, complete Handy Board systems cost less than \$250; kits cost less than \$200. Kits and assembled



CIRCLE 27 ON FREE INFORMATION CARD

systems are distributed by Gleason Research (gleason@tiac.net; 617-641-2551); CW Technology (cwtech@infinet.com; 800-547-7479); and Digital Micro Systems (dutta.4@osu.edu; 614-299-2566). Blank printed circuit boards are sold by Douglas Electronics (info@douglas.com; 510-483-8770).

THE MEDIA LABORATORY

Massachusetts Institute of Technology
Room E15-320
20 Ames Street
Cambridge, MA 02139-4307
<http://el.www.media.mit.edu/groups/el/projects/handy-board>



EN



NEW! turboSIM NEW!



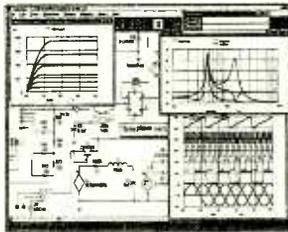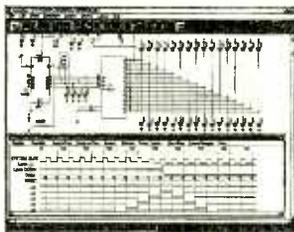32-bit native mixed Analog/Digital circuit simulation



- * Powerful 16 and 32-bit versions for Windows 3.1, Win32, Windows 95, Windows NT
- * Includes TurboSIM, TurboSPICE, TurboSCOPE, TurboLOGIC, all in ONE easy program.
- * 10 libraries with hundreds of analog and digital devices 74XX, CMOS, LED's, 555-timer, Test Instruments, Transistors, OP AMPS, Transmission lines, Signal Generators more.
- * Includes TurboLIB Symbol Editor to design your own additional devices and sub-circuits.
- * Supports hierarchical designs and generates TangoPRO compatible PCB Layout netlist.
- * Import/Export Spice netlist. Accepts models/macro models from other manufacturers.
- * Advanced real-time simulator displays analog and digital waveforms during simulation.
- * Powerful circuit debug functions, Triggered, Sequential, and Combinational break points, Trap timing violations, and Digital-glitch detection.
- * Powerful TurboSCOPE plots math expressions including sin, cos, tan, real part, imaginary part, bode plots, magnitude, phase, decibels, derivatives and more even during simulation.
- * Available analysis include AC, DC, Transient, Pole-Zero, Noise, Transfer-Function more.
- * Free demo at <http://www.islandlogix.com> or <http://pages.prodigy.com/L/JIA/LJSN87A>

Regularly \$299
Limited time offer \$149
plus shipping.

- * Student Price \$79
- * Teachers eligible for free copy
- * Site Licenses Avail
- * Dealer Discount Avail.
- * Visa/Master Card/Money Order.

Island Logix Inc.
P.O. Box 157
Waukegan IL 60079 USA
PH: 708-360-0458
FAX: 708-360-0468

CIRCLE 130 ON FREE INFORMATION CARD

Invest a stamp...Save a bundle

For the price of a stamp, you can get the latest edition of the federal government's free Consumer Information Catalog. It lists more than 200 free or low-cost publications on federal benefits, jobs, health, housing, education, cars, and more.

So stamp out ignorance with our free Catalog. Send your name and address to:
Consumer Information Center, Department SB, Pueblo, Colorado 81009



One tree can make
3,000,000 matches.



One match can burn
3,000,000 trees.



A Public Service of The Magazine
by The Advertising Council




NEW LITERATURE

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

The Road Ahead

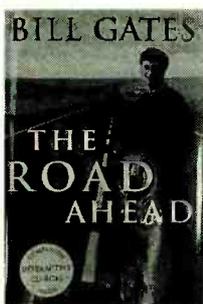by Bill Gates with Nathan Myhrvold
Viking
375 Hudson Street
New York, NY 10014
Phone: 212-366-2000
\$29.95



CIRCLE 40 ON FREE INFORMATION CARD

Where the budding "information superhighway" will eventually lead us is anybody's guess—but if anyone is qualified to do such guessing, it is Microsoft

co-founder, chairman, and CEO, Bill Gates. This book presents Gates' optimistic vision of how today's emerging technologies will change the way we work, play, and live in the future.

"We are all beginning another great journey," Gates writes. "We are watching something historic happen, and it will affect the world seismically, rocking us the same way as the discovery of the scientific method, the invention of printing, and the arrival of the Industrial Age did."

Gates presents a brief overview of the development of the Information Age before turning his attention to the Information Highway—the global network of personal computers and other information appliances that he believes will be available in homes and businesses within the next ten years. He foresees that the worldwide "information market" or "exchange" will provide unprecedented access to information, services, and products, empowering


more people to participate in everything ranging from their children's education to the political process.

Gates describes some of the products that he expects will soon become available and that promise to change the way we learn, work, shop, and socialize. He then covers specific areas in which he believes the implications of the Information Highway will be most strongly felt. In education, Gates predicts, on-line textbooks, multimedia documents, and easy authoring tools will allow teachers to customize a curriculum for students who learn at different speeds and allow students to explore information interactively. In politics, on-line forums could be used to mobilize people into a coherent political movement, and e-mail could provide voters with more direct access to elected officials. Gates envisions a business world filled with smaller, more efficient companies, and an electronic global marketplace in which the middlemen are cut out of most transactions. Telecommuting will ease the stress on urban infrastructures and could even cause socioeconomic transformations as workers are no longer physically tied to the workplace. Using his own under-construction home as a prototype, Gates describes the house of the future as one that can anticipate and meet its occupants' needs automatically.

The book includes an interactive, multimedia CD-ROM that contains the complete text, hundreds of multimedia hyperlinks, a special video interview with Gates (which can also be played on an audio CD player), video simulations of future technology, and a World Wide Web browser.

The Internet Yellow Pages Third Edition

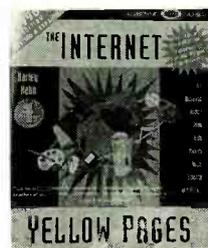by Harley Hahn
Osborne McGraw-Hill
2600 Tenth Street
Berkeley, CA 94710
Phone: 1-800-227-0900
\$29.95



CIRCLE 39 ON FREE INFORMATION CARD

Now you can let your fingers do the walking down the information highway, thanks to this comprehensive directory.

Arranged in the familiar style of a phone book, its listings are grouped in alphabetical order by category. Each listing contains a brief description, written in a witty, engaging style.

The book has been updated to cover the best and most popular sites on the Internet. The vast array of Internet sites has been pared down to include only those that are useful and fun, and that guide users to other related information. The new edition includes art, games, jobs, humor, movies, pets, religion, sexuality, and more. Those who need a little nudge toward rebellion can check out "Harley Hahn's List of 25 Things to Do When You Should Be Working." And off-beat souls should enjoy the listings found under the heading "Bizarre": Contortionism, Gross and Disgusting, Ouija, Psychic CB, and Roommates from Hell, and several dealing with vampires are just a sampling.

The guide provides more than mere listings of categories and Internet addresses. It offers infor-

mation about each topic listed, hints about what to expect when accessing sites, and humorous "advertisements" highlighting interesting resources that might otherwise be overlooked.

1996 Electronics Parts & Accessories Catalog

Parts Express

340 East First Street

Dayton, OH 45402-1257

Phone: 1-800-338-0531

free



CIRCLE 38 ON FREE INFORMATION CARD

This 228-page catalog is filled with electronic parts and accessories geared toward the consumer-electronics industry and the technical hobbyist. It includes a broad

array of CATV and VCR repair parts, semiconductors, tools and technician aids, test equipment, computer accessories, chemicals, adhesives, telephone products, specialized connectors, and instructional books and videotapes. Its full line of professional sound equipment includes wire and audio accessories such as raw loudspeaker drivers for home, car, and home-theater applications.

1996 Master Catalog

Jensen Tools, Inc.

7815 South 46th Street

Phoenix, AZ 85044

Phone: 1-800-426-1194

Fax: 602-438-1690

free



CIRCLE 37 ON FREE INFORMATION CARD

Offering a combination of test and diagnostic instruments with quality tools and accessories, this catalog represents a comprehensive, one-stop source of hard-to-find tools and

specialty tool kits for radio amateurs and electronics hobbyists. The color-

ful, 240-page book presents the latest additions to the Jensen Tool Kit (JTK) line and introduces seven models of the economical new Vantage line.

The catalog also features products from many leading tool and test-equipment manufacturers, including state-of-the-art items from Fluke, B+K Precision, Extech, Biddle, Wavetek, Tektronix, Navtel, Datatran, and others. Also included are wire, cable and connectors, inch/metric tools, PC diagnostics, fiber-optic products, power monitors and meters, soldering and SMT rework stations, cases, and shipping containers.

The Downloader's Companion for Windows 95

by Scott Meyers, Catherine Pinch & Chris Sells

Prentice Hall

1 Lake Street

Upper Saddle River, NJ 07458

Phone: 1-800-383-2419

Fax: 201-236-7141

E-mail: corpsales@prenhall.com.

\$21.95



CIRCLE 36 ON FREE INFORMATION CARD

Thousands of games, programs, sounds, pictures, and even multimedia movies are yours for the taking from computer networks such as the Internet, CompuServe, and America Online—if you know how to

download them. Downloading is the art of moving files from other computers to yours and translating those files into a usable format. Downloadable files are usually in a form that your computer cannot immediately understand. The files are compressed, archived, encoded, or perhaps even all three. Pictures might be in GIF, JPEG, or some other format.

This book-and-disk package explains all of those terms and formats, and provides all the software you need to effortlessly download programs to your PC. It offers insider's

tips that allow you to learn without spending time and money on online trial and error. The book not only tells you how to download files, but also how to determine what's in the file, what it's good for, and how you can use it.

The disk includes WinZip, a Windows 95 compression/uncompression interface that can work with all the most common archive formats. It also provides quick file viewers and instructions for accessing files in a variety of formats, including pictures and graphics in GIF, JPEG, BMP, and TGA; MPEG movies; and sounds and music in WAV, VOC, AU, and others.

Your Mobile Companion

by Roger Burch, WF4N

The American Radio Relay League

225 Main Street


Newington, CT 06111

Phone: 203-666-1541

Fax: 203-665-7531

\$12

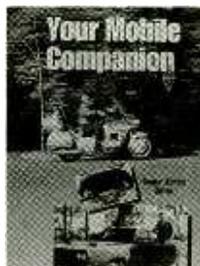Whether you're just getting into mobile operating or are looking for new ways to enjoy mobile hamming, this book is for you. The book provides practical, hands-on advice on setting up and mobile station and getting it on



CIRCLE 35 ON FREE INFORMATION CARD

the air. It shows what to do and what not to do, and is full of tips and ideas to optimize mobile operating.

The book contains all the information you need to make informed decisions. It helps you pick the best of the bands; sort through all the different models of equipment available to choose the right gear for your needs; successfully complete even the trickiest installations; and choose the best antenna and decide between top, rear, and on-the-glass mounting. Once you're up and running, the book explains where and how to operate to get the most out of your mobile station, and provides proven solutions to automotive interference problems. **EN**

EQUIPMENT REPORTS

continued from page 20

readout. Slide controls for positioning the A- and B-channel waveforms are located around the periphery of the display.

The autoranging feature works only when periodic signals with constant amplitude are being measured. In all other measurements the time base and gain ranges must be set manually. The autoranging mode takes a few seconds to find the correct settings and display the waveform. A sample of the waveform can be obtained in a single or repeat mode, and then the gain and time base settings should be adjusted to set the instrument on the proper range.

The time base can be adjusted from 0.5 microseconds per division to 50 milliseconds per division in 16 ranges, and gain can be adjusted from 5 volts per division to 5 millivolts per division in 10 ranges. A secondary menu makes it possible for Multiscope to react to a range of different input conditions.

A chart button on the oscilloscope display sets Multiscope in its recorder mode. Start and stop buttons turn the recorder on and off. Pressing a pair of up/down buttons adjusts chart recorder gain, and the sample interval

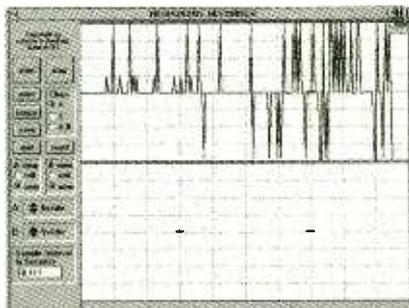


FIG. 2—THE VIRTUAL RECORDER display as it will appear on your computer's monitor.

can be keyed in by the user.

The DB-25 connector on the front panel provides different signals for use with other equipment. Output channels C and D are provided on the connector. Pin 25 goes to an inactive external trigger option. An option that calls for additional software and hardware permits Sample data set on chan-

nels A or B to be externally initiated or controlled.

Various accessories are also available from Mission Technologies. A software package that contains the source code (fully commented to explain its operation) is available for an additional \$100, bringing the total cost to \$499. An external triggering software package and relay (to be installed by the user or at the factory) is an additional \$38. An eight-bit ISA parallel port card for computers whose ports are not compatible with the Multiscope is available for \$12.

Multiscope is not a true substitute for the stand-alone instruments it emulates, but then it costs a lot less. Rather than buy a bench full of dedicated instruments, Multiscope offers measurement capability that is more than adequate for most hobbyist and experimenter applications. It fills that gap between a multimeter and a bench full of dedicated test instruments. If you want to see how your personal computer can double as a collection of quality test instruments, buy the Multiscope. **EN**

PROTO-BOARD®

The breadboard you only buy once.



At Global Specialties® we make one kind of breadboard, the very best, PROTO-BOARD®. **American made and Guaranteed for life.**

PROTO-BOARD® brand breadboards and the complete Global line of test instruments are in stock at fine electronic distributors everywhere.



GLOBAL SPECIALTIES




Can't Wait! Call Toll-Free
1-800-572-1028

70 Fulton Terrace, New Haven, CT 06512
(203) 466-6103 • Fax: (203) 468-0060

an
Interplex Industries company

CIRCLE 122 ON FREE INFORMATION CARD

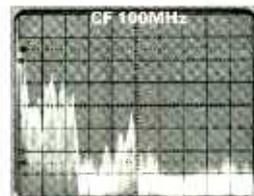Check your design's EMI performance with a Spectrum Analyzer and HZ530 before third party compliance testing.



Switch mode power supply radiation measured with HM5010 and E-Field probe
HZ530: E-Field, H-Field and High-Impedance Probe set

Price \$ 680.00

HZ530 Near Field Sniffer Probe Set

- EMI Diagnostics at the prototype level
- Refining circuit and screening design
- Location of hot spots and leaks
- Monitoring production performance
- Compatible with any Spectrum Analyzer

Don't let EMC become your Problem!

HAMEG Inc.

call toll-free at:
(800) 247-1241

1939 Plaza Real
Oceanside, CA 92056

(619) 630-4080
(619) 630-6507

266 East Meadow Ave.
East Meadow, NY11554

(516) 794-4080
(516) 794-1855

CIRCLE 131 ON FREE INFORMATION CARD

RETAILERS THAT SELL OUR MAGAZINE MONTHLY

Alaska

Frigid North Co.
1207 W. 36th Avenue
Anchorage, AK 99503

Alabama

Radio Distributing Supply
121 East Broad Street
Gadsden, AL 35903

Arizona

Dalis Electronics
2829 E. McDowell Road
Phoenix, AZ 85008

California

California Electronics
221 N. Johnson Ave.
El Cajon, CA 90202

Signal Electronics
22307 Ocean Avenue
Torrance, CA 90505

Ford Electronics
8431 Commonwealth Avenue
Buena Park, CA 90621

All Electronics
14928 Oxnard Street
Van Nuys, CA 91411

Gateway Electronics of CA
9222 Chesapeake Drive
San Diego, CA 92123

Mac's Electronics
191 South "E" Street
San Bernardino, CA 92401

Electronics Warehouse
2691 Main Street
Riverside, CA 92501

Orvac Electronics
1645 E Orangethorpe Ave.
Fullerton, CA 92631

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove, CA 92643

Marvac Dow Electronics
980 S. A Street
Oxnard, CA 93030

Kandarian Electronics
1101 19th Street
Bakersfield, CA 93301

Whitcomm Electronics
105 W. Dakota #106
Clovis, CA 93612

Marvac Dow Electronics
265-B Reservation Road
Marina, CA 93933

Minuteman Electronics
37111 Post St., Suite 1
Fremont, CA 94536

HCS Electronics
6819 S. Redwood Drive
Cotati, CA 94931

Halted Specialties Co.
3500 Ryder Street
Santa Clara, CA 95051

JDR Micro Devices
2233 Branham Lane
San Jose, CA 95124

Metro Electronics
1831 J Street
Sacramento, CA 95814

The Radio Place, Inc.
5675-A Power Inn Road
Sacramento, CA 95824

HSC Electronics
4837 Amber Lane
Sacramento, CA 95841

Colorado

Gateway Electronics of CO
2525 Federal Blvd.
Denver, CO 80211

Centennial Electronics
2324 E. Bijou
Colorado Sps., CO 80909

Connecticut

Signal Electronics Supply
589 New Park Avenue
W. Hartford, CT 06110

Cables & Connectors
2198 Berlin Turnpike
Newington, CT 06111

Electronic Service Prod.
437 Washington Avenue
North Haven, CT 06473

Georgia

Norman's Electronics, Inc.
3653 Clairmont Road
Chamblee, GA 30341

Idaho

The Current Source
5159 Glenwood
Boise, ID 83714

Illinois

Tri State Elex
200 W. Northwest Hwy.
Mt. Prospect, IL 60056

Maryland

Mark Elec. Supply Inc.
5015 Herzel Place
Beltsville, MD 20705

Massachusetts

U-Do-It Electronics
40 Franklin Street
Needham, MA 02194

Michigan

Purchase Radio Supply
327 East Hoover Avenue
Ann Arbor, MI 48104

Norwest Electronics
33760 Plymouth Road
Livonia, MI 48150

The Elec. Connection
37387 Ford Road
Westland, MI 48185

Elec. Parts Specialists
711 Kelso Street
Flint, MI 48506

Professional Data Corp.
1332 US Highway 41 West
Ishpeming, MI 49849

Minnesota

Acme Electronics
224 Washington Avenue N.
Minneapolis, MN 55401

Missouri

Gateway Electronics Of MO
8123-25 Page Blvd.
St. Louis, MO 63130

New Jersey

Lashen Electronics Inc.
21 Broadway
Denville, NJ 07834

New York

Sylvan Wellington Co.
269 Canal Street
New York, NY 10013

R&E Electronics
4991 Rt. 209
Accord, NY 12404

Unicorn Electronics
Valley Plaza
Johnson City, NY 13790

Ohio

Philcap Electronic Suppliers
275 E. Market Street
Akron, OH 44308

Oregon

Norvac Electronics
7940 SW Nimbus Avenue
Beaverton, OR 97005

Pennsylvania

Business & Computer Bookstore
213 N. Easton Road
Willow Grove, PA 19090

Texas

Mouser Electronics
2401 Hwy. 287 N
Mansfield, TX 76063

Electronic Parts Outlet
17318 Highway 3
Webster, TX 77598

Washington

Amateur Radio Supply Co.
5963 Corson Ave., Ste 140
Seattle, WA 98108

Wyoming

Chris Supply
2007 S. Douglas Hwy., Ste. C
Gillette, WY 82716

**If you'd like to sell our magazine in your store,
please circle 210 on Free Information Card.**

FUZZY LOGIC IS NOT AT ALL AS ITS name might imply. Rather than being indistinct, it is a rigorous mathematical discipline that is based on fuzzy-set theory, which is a cross between multi-valued set theory and Boolean logic. Lotfi Zadeh of the University of California, Berkeley, is credited with its creation in 1965. However, portions of his theory trace their origins to multi-valued set theory of the 1920's.

Zadeh observed that as a system become more complex, the need to describe it with precision becomes less important. He also observed that precision in complex systems is often unnecessary. Zadeh's premise is that it is possible to describe a system's behavior and control laws linguistically.

Precision is expensive, especially when used for solving problems. Getting close is often good enough. Fuzzy logic exploits this "good-enough" mentality through imprecision. It uses imprecision the same way that humans do to solve problems. For example it is certainly possible to heat a room to within a hundredth of a degree. Alternatively, a fuzzy logic controller might heat the same room to within one degree. This is a situation where the extra precision is exorbitant.

Fuzzy logic enables designers to simulate human thinking by quantifying concepts such as hot, cold, far, near, soon, and long. Fuzzy logic relies on the notion that measurements are more useful when they are expressed in linguistic terms, rather than described to the sixth decimal point. In other words, fuzzy logic reduces complex problems into manageable sets called *fuzzy sets*.

Consider, for example, describing a person's height in fuzzy sets. Few would argue that a person who is seven feet tall is "tall," and a person who is three feet tall is "short." But what about someone who is five foot five? Fuzzy logic would give that person some degree of membership in the tall set, and a somewhat higher degree of membership in the short set.

FUZZY LOGIC

A new challenger is threatening to dethrone traditional control techniques as the method of choice. This article describes the challenging techniques of fuzzy logic.

BYRON MILLER


Traditional control theory

Fuzzy set theory has applications in many different disciplines. One, in particular, is fuzzy-logic control theory. Fuzzy-logic control theory is an alternative to traditional control theory.

In traditional control theory, a controller controls a system. A system is a collection of things that are connected in some way. This collection of connected elements performs a single function. Consider a heating system, for example. The heating

system is composed of a thermostat, sensors, and a heating unit. All of the individual elements are connected together to perform one function.

A control system is a physical system that either commands or regulates itself or another system. There are many examples of control systems. For instance, an electric switch controls the flow of electricity. A person driving a car controls the speed and direction of that car. A heating system makes use of the thermostat to regulate a

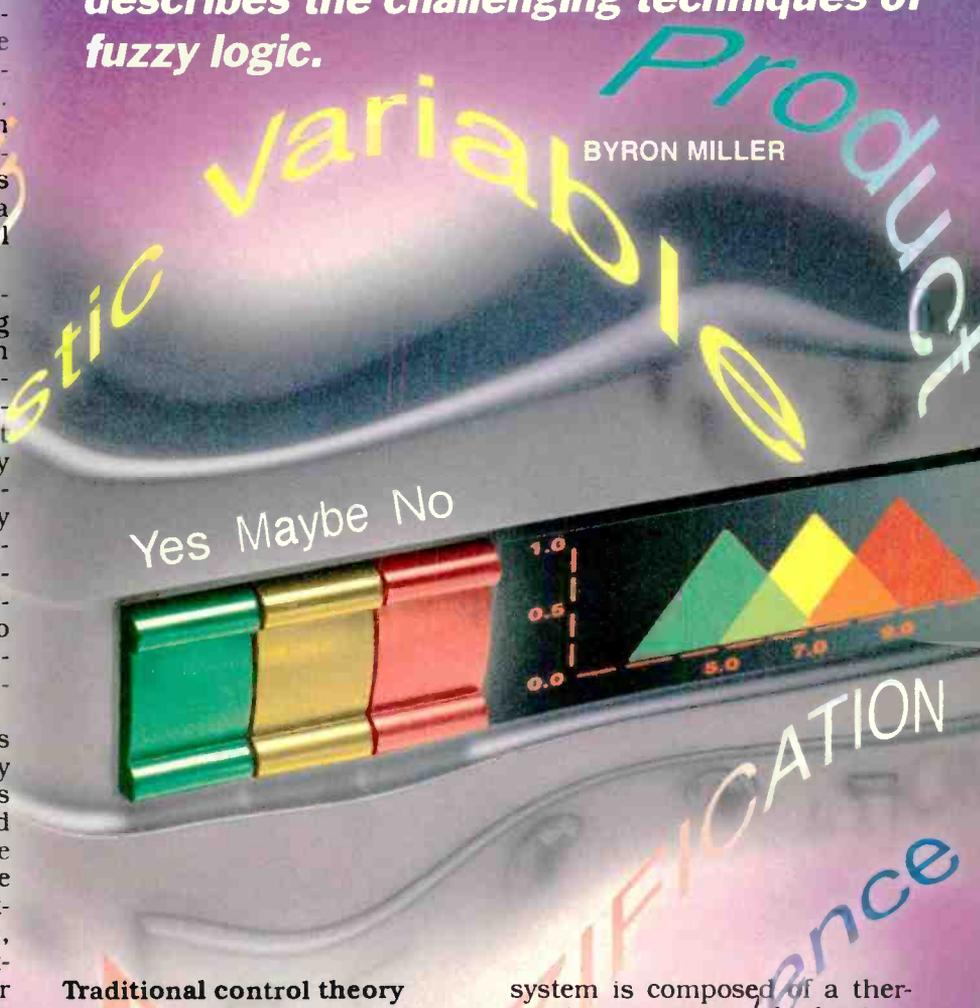

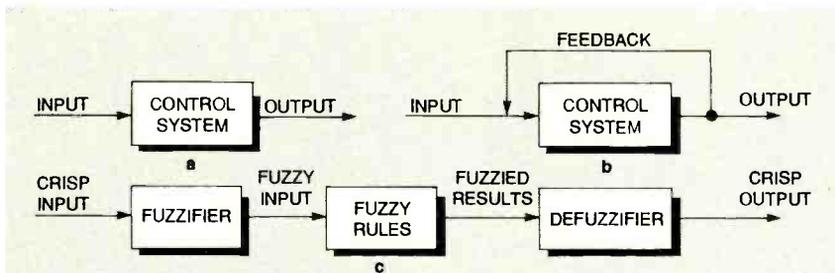


FIG. 1—CONTROL SYSTEM BLOCK DIAGRAMS. A general control system (a), closed-loop system (b), and a typical rule-based fuzzy-logic controller (c).

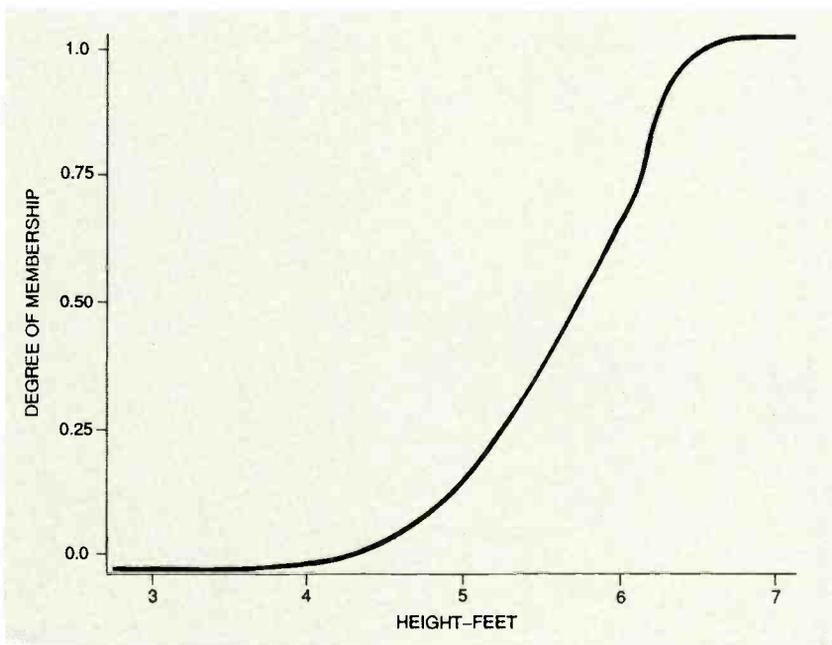


FIG. 2—THE SET "TALL" represented graphically.

room's temperature.

Figure 1-a shows a typical control system. It has one or more inputs and one or more outputs. The box marked "control system" is where the processing occurs. The type of processing that occurs within the control system is classified as either *open-loop* or *closed loop*.

An open-loop control system is one in which the control action is independent of the output. In other words, the control system's output is directly related to its input. For example, an open-loop control system takes its inputs, does some computation on those inputs, and produces an output.

A closed-loop system differs from the open-loop system in that its output is dependent on both the input and the output. Figure 1-b shows a closed-loop

system. The output is made a function of both the input and the output by *feedback*. In most systems, the feedback component forms an extra input to the system.

A calculator is an example of an open-loop system. Input is in the form of number and operation-code (opcode) keypresses. The calculator takes the input, operates on the input based on the opcode, and produces an output based on the result of the operation.

A car being driven is an example of a closed loop system. The person adjusts the speed of the car by pressing the gas pedal. The feedback in this system is the person, who regulates the flow of gas to the engine based on the speedometer. Thus if the person wants to increase speed to 55 miles per hour (MPH) he presses the gas pedal, and the

car accelerates. The car continues its acceleration until the person sees that the speedometer reads 55 MPH, and he eases off the gas pedal.

The most commonly used control systems today are based on the proportional-integral-derivative (PID) method. James Watt is often credited for the creation of classical control theory on which the PID method is based. The PID method controls a system by reading the input sensors and applying a mathematical equation to the inputs to produce the output. Typically the output from this type of system is used to control some kind of actuators to regulate the flow of something. One example is an actuator which is used to control the flow of steam from a turbine. The mathematical equations that the PID is based on are usually complex, and are time consuming to define, build, and test.


Fuzzy-logic control theory

In general, a fuzzy-logic control system has three components. The first is the *fuzzification* section. This section is responsible for taking real input data (also referred to as crisp data), and converting it to data that has meaning to the fuzzy system. Next, the fuzzified data is applied to the *fuzzy-rule base* section. Fuzzy control systems are typically the feedback type. Consequently, the feedback in a fuzzy control system occurs within the rule-base section. The result of the rule-base section is fuzzified output data. This fuzzified output data is converted back to real or crisp data through the *defuzzification* section. A typical fuzzy control system is shown in Figure 1-c. When a control system is implemented it is often referred to as a controller.

A fuzzy controller is made up of fuzzy variables, rules, sets, and translation mechanisms that transform input data into fuzzy data, and vice versa. Fuzzy variables are similar to regular variables, except that they are used to describe things that are multi-valued. For instance the

Continued on page 56

AMATEUR TV TRANSMITTER

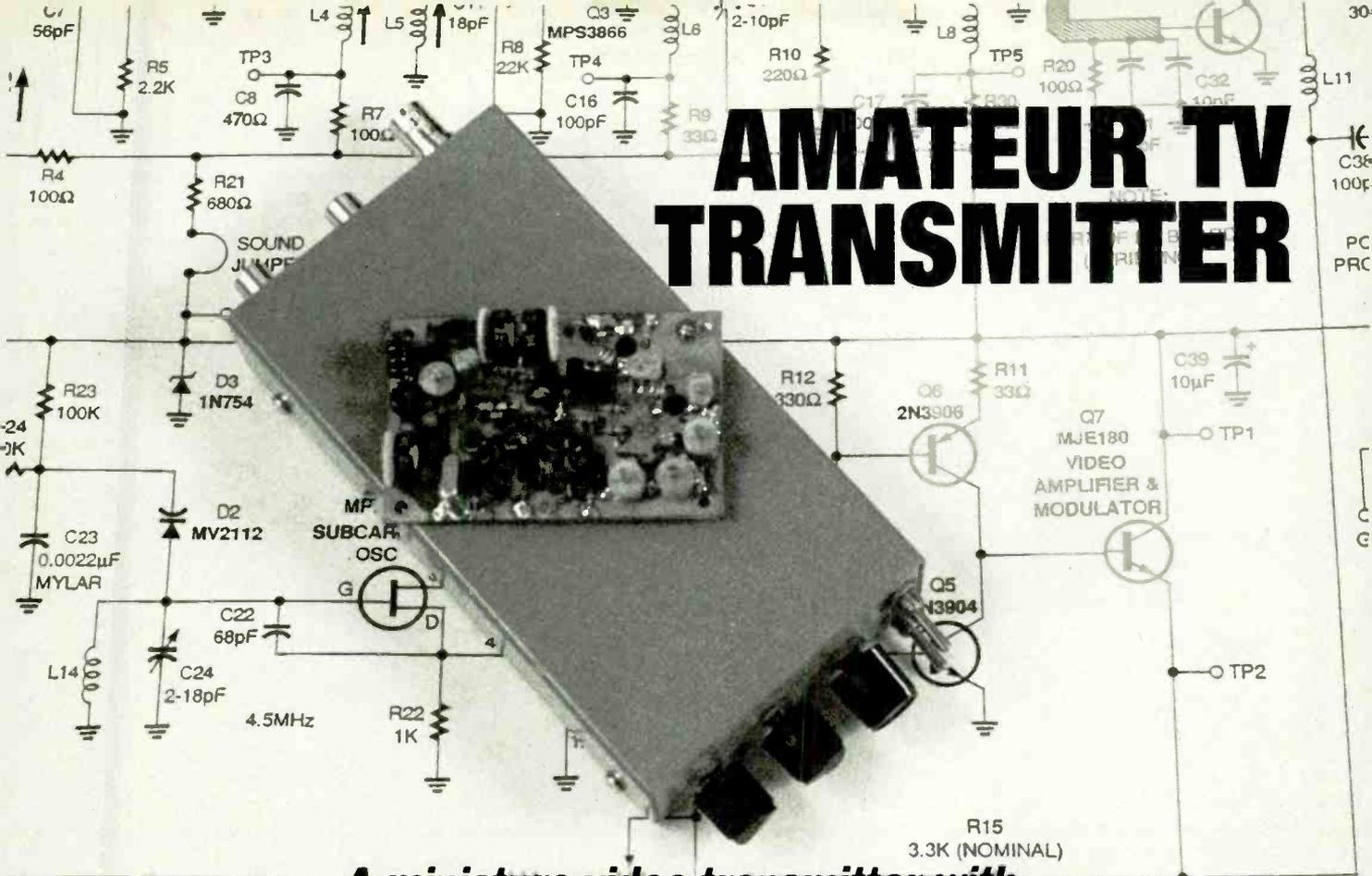

A miniature video transmitter with sound carrier for the 900-MHz amateur radio band

William Sheets, K2MQJ & Rudolf F. Graf, KA2CWL

YOU CAN BUILD A MINIATURE AMATEUR radio TV transmitter and put it to work in a variety of applications from radio-controlled videography to two-way communications—and just about any other video application that might strike the fancy of experimenters and amateur radio operators. Now, small CCD cameras help to keep the cost low.

Don't confuse the Mini 900 ATV transmitter with video-link devices operating in the 900-MHz band. The Mini 900 is very small (1.75 × 2.75 × 0.75 inch), develops 500 milliwatts of RF output, is crystal controlled, and has produced clean pictures at distances over 5 miles, using simple antennas at both ends of the transmission path. Note that the 902-928 MHz band is available to ham radio operators holding a valid Technician Class license or higher. A license is required to operate this project in the U.S. (No Morse code test is required

for the Technician license.) The transmitter is for experimental non-commercial use only and its application is subject to radio amateur rules and regulations in the U.S. and other countries.

Operation of the Mini 900 ATV transmitter on commercial TV frequencies is illegal in the U.S. and for other nations. The device has *not* been submitted for FCC type acceptance and is *not* legal for commercial use.

The Mini 900 must be operated so that the entire RF signal lies within the 902-928-MHz band when operated in the U.S. This means picture carrier frequencies of 906.5 and 923.5 MHz inclusive. A good choice for most radio amateurs is 910.25 MHz. U.S. operators should check their local areas first. Other common carrier frequency alternates are 922.25 and 923.25 MHz.

The Mini 900 accepts an NTSC video signal and gener-

ates a video-modulated RF signal including a standard 4.5-MHz sound subcarrier in the 902 to 928-MHz band. The signal from the Mini 900 can be received on any standard TV receiver fitted with a suitable RF downconverter capable of tuning the 902-928 MHz Amateur band. The transmitter's small size (1.75 × 2.75 inches) is comparable to many small PC board cameras and is small enough for radio-controlled applications in which a video link is needed.

The Mini 900 can operate from a 10 to 14-volt DC power supply, with minor adjustments in the transmitter's video drive. Lead acid, NiCd, or alkaline power packs may be used. RF power output will be 0.2 to 0.7 watts over the power-supply voltage range. Nevertheless, the author used a 13.2-volt DC power supply and it is referenced throughout this article.

Operation over 900-940 MHz

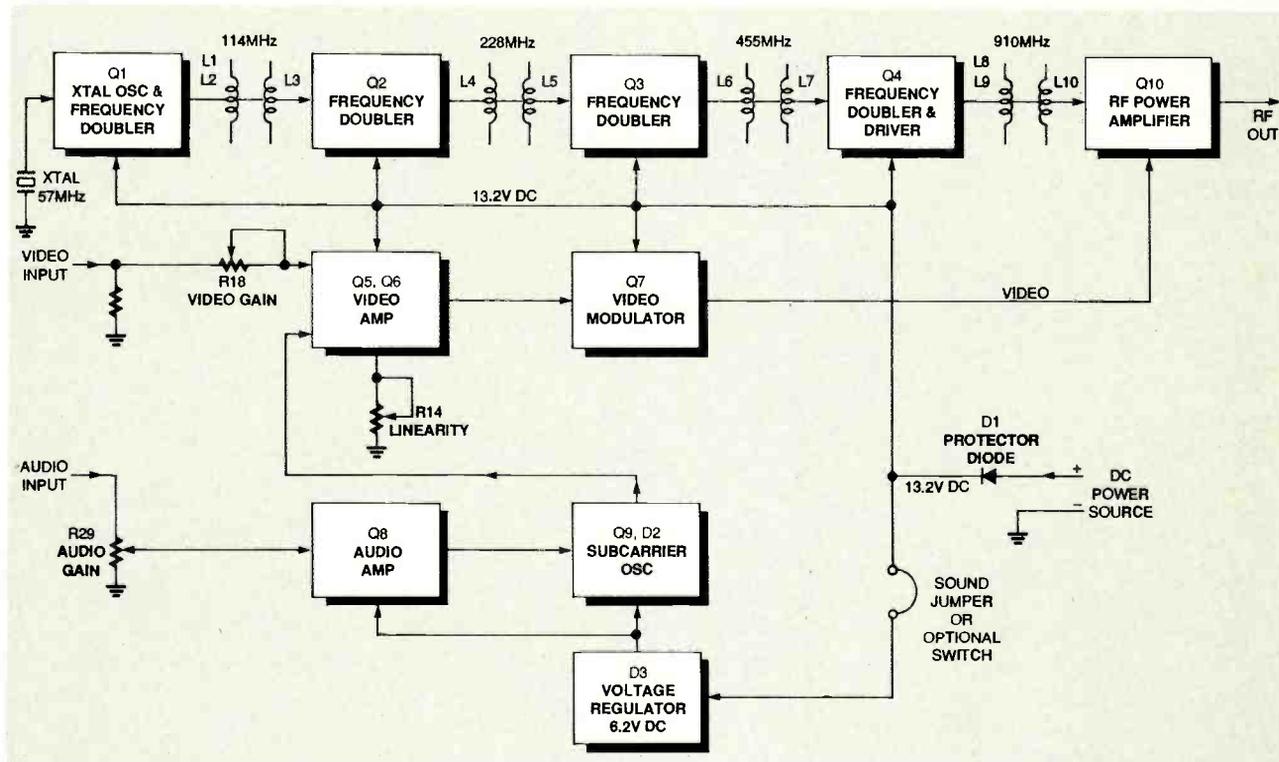


FIG. 1—BLOCK DIAGRAM for the Mini 900 ATV transmitter illustrating signal generation and flow. It is a good idea to refer to this diagram while following the details in the schematic diagram in Fig. 2.

is possible with the Mini 900 for export (non-US) use. The Mini 900 can easily be retuned for a 5.5 MHz sound subcarrier used by the PAL system. The video input requirement is standard 1-volt peak-to-peak, negative sync signal. The video amplifier and modulator are DC coupled, but a capacitor can be installed in series with the input if AC coupling is desired. Audio inputs from 5 millivolts to 1 volt can be accommodated.

This project can be built from scratch, in two to four evenings, depending on the builder's experience. Due to the unit's small size and many small parts, and the high frequencies present, this project is not recommended for beginners.

How it works

The Mini 900 consists of a crystal oscillator operating around 57.5 MHz, a series of frequency multiplier stages to multiply the crystal oscillator frequency by a factor of sixteen, and an RF power amplifier. Refer to Fig. 1 for the functional block diagram of the Mini 900 circuit and Fig. 2 for a detailed schematic diagram. The RF-

power amplifier is amplitude-modulated by a video amplifier that boosts the video input signal to a required level. An audio amplifier stage boosts the audio input which in turn frequency modulates a 4.5 MHz VCO (voltage-controlled oscillator) to generate a sound subcarrier. The FM subcarrier is combined with the video in the modulator. If no audio is needed this feature can be disabled by disconnecting a jumper.

Transistor Q1 is a crystal-controlled oscillator using a 56–59 MHz crystal, XTAL1, in a common-base transistor circuit (see Fig. 2). At the series-resonant frequency of the crystal, the base of Q1 is nearly grounded. Coils L1 and C2 are tuned slightly above resonance, causing oscillation at the crystal frequency. The signal generated is rich in harmonic frequencies.

A filter, consisting of L2, C3, C4, L3, C6 and C7, couples the second harmonic of the crystal's 112-118 MHz signal to frequency-doubler stage Q2. This stage further doubles the signal frequency to 225-240 MHz. A filter, consisting of C9, L4, C10, L5, C11, and C37, suppresses all

frequencies other than those in the 225-240 MHz range. Also, the filter matches the input of the next stage, frequency doubler Q3. Transistor Q3 doubles this signal to half the final output frequency, 450 to 470 MHz. At this point, about 30 milliwatts of RF power is present.

A filter, consisting of C12, L6, C15, C13, C14, and L7, forms a matching network to couple the RF energy from Q3 to Q4, and also filters out unwanted signals. Transistor Q4 doubles this signal to the final output frequency, 900-940 MHz, supplying about 50 to 80 milliwatts of RF driving power. A double-tuned coupling network, consisting of C18, C19, L9, L10, C20, C31, and C32, matches the output of Q4 to the base of Q10. This network has tuned stripline coupled inductors (see Fig. 2) that are actually copper strips etched on the PC board.

RF power amplifier Q10 supplies an RF output of between 0.2 and 0.7 watt depending on supply voltage. A coupling network, consisting of L11, C33, L12, C34, C35, L13, and C36, matches a 50-ohm antenna load

Continued on page 61



ALL KINDS OF INDUSTRIAL PROCESSES are controlled electronically these days. The most common control device that an industrial technician is likely to encounter is the programmable logic controller (PLC). Troubleshooting PLC's can be tricky. However, when part of a manufacturing operation is shut down, the technician is under tremendous pressure to isolate the problem, fix it, and get the system up and running again. Last month's article, "All About PLC's", explained how PLCs work and how they are used. This article examines some real-world examples of PLC problems and how they are solved.

A portable oscilloscope is the most important instrument to have when troubleshooting industrial systems on the factory floor. New technology has reduced both the size and weight of the required test gear. For example, the Tektronix TekMeter is a dual-channel, auto-ranging portable scope plus a true rms multimeter in a compact lightweight package with an LCD screen. Although this article

references the TekMeter exclusively, it is only one of a growing number of portable instruments in a competitive market. Fluke, for example, offers similar instruments that also target industrial technicians and engineers.

Most PLCs in industrial applications incorporate a variety of self-test features that verify correct sensor operation. However, they are not foolproof. Many electrical malfunctions can be solved only by using an oscilloscope together with your eyes. Take, for example, this case history where an optical sensor was used to count items passing over a conveyor belt.

Too many counts

Figure 1 is a diagram of the packaging operation in which cans were counted as they travelled along a conveyer belt. As each can passed through the optical detector, it produced a pulse that was fed into a PLC's digital input port. The sensor output delivered one pulse for each can that passed by, providing an accurate cumulative

When industrial control systems go wrong, grab a portable scope, and start troubleshooting!


VAUGHN D. MARTIN

Troubleshooting PLC Problems

total of the number of items.

When the new line was set into operation, it was expected to process 100 cans per minute, or 48,000 cans per eight-hour shift (100 cans per minute times 60 minutes per hour times 8 hours per shift = 48,000 cans.) However, at the end of the shift, the system had counted 50,000 cans, according to the PLC logging function. Nevertheless, there were exactly 2000, 24-can cases, verifying the original 48,000-can computation. Obviously, either the PLC counting program had been incorrectly programmed or the sensor input was receiving pulses for cans that weren't there.

The first step in troubleshooting was to check the counting program by connecting a pulse generator to the PLC input as in Fig. 2, and setting it to generate exactly 10 pulses. An oscilloscope was then connected across the pulse generator to verify proper operation. It showed 10 pulses, and the PLC logging program showed 10 counts. That indicated that the PLC program was probably not at fault, and pointed instead to the sensor or its cabling.

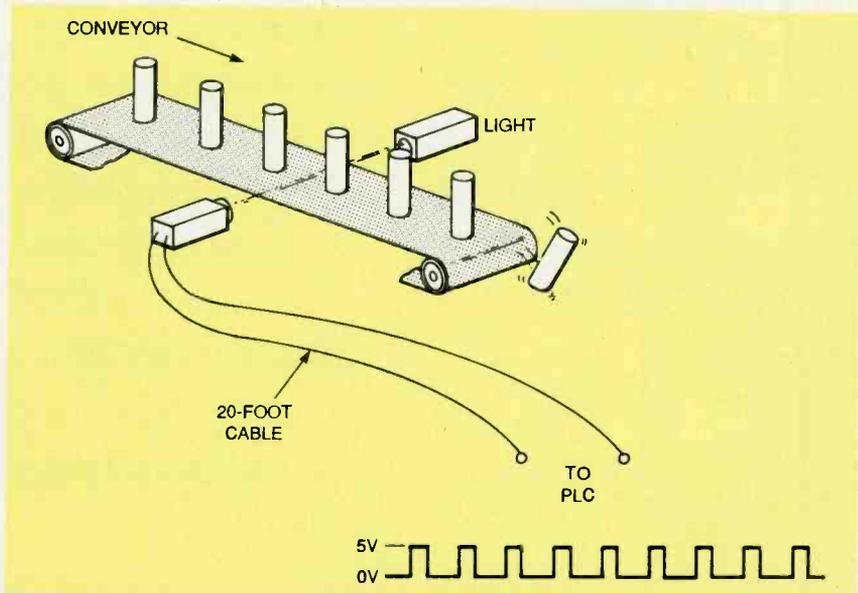

examine if anything happened in the process only once each carton-filling cycle. We noticed that a small linear motor was energized after each carton was filled to push the carton off the conveyor belt and onto a sealing roller line. Naturally, our investigation then turned to this new suspect.

We reconnected the PLC to the process line and the optical sensor, and connected our scope's channel 1 (CH1) input to the optical sensor output. Then we connected the scope's channel 2 (CH2) input to the linear push motor's control line (ahead of the AC relay or triac controller) as shown in Fig. 3. Then we started the line and set the scope's trigger for the positive edge on CH2; the resulting

FIG. 1—TYPICAL OPTICAL SENSOR SET UP TO COUNT items as they travel along a production line.

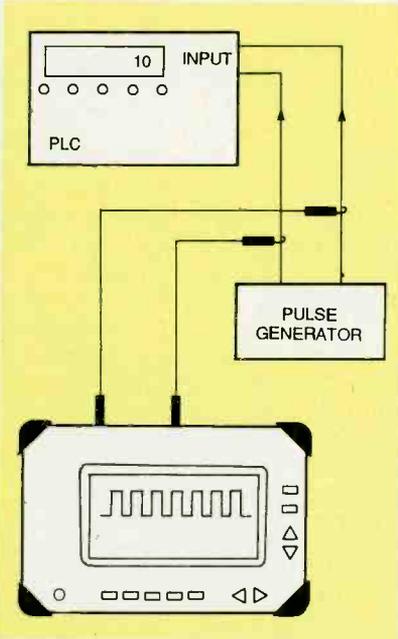


FIG. 2—THIS INSTRUMENT HOOKUP is used to detect the extra, erroneous counts.

Examining the evidence

Since more cans were counted than were packed, it seemed that some stray pulses had slipped into the optical sensor cable that fed the PLC input. Some 2000 stray pulses, to be exact (50,000 - 48,000). That number proved to be a clue in itself because a little deduction showed that it wasn't a random number. Divide the number of expected cans by the excess pulse error count (48,000 ÷

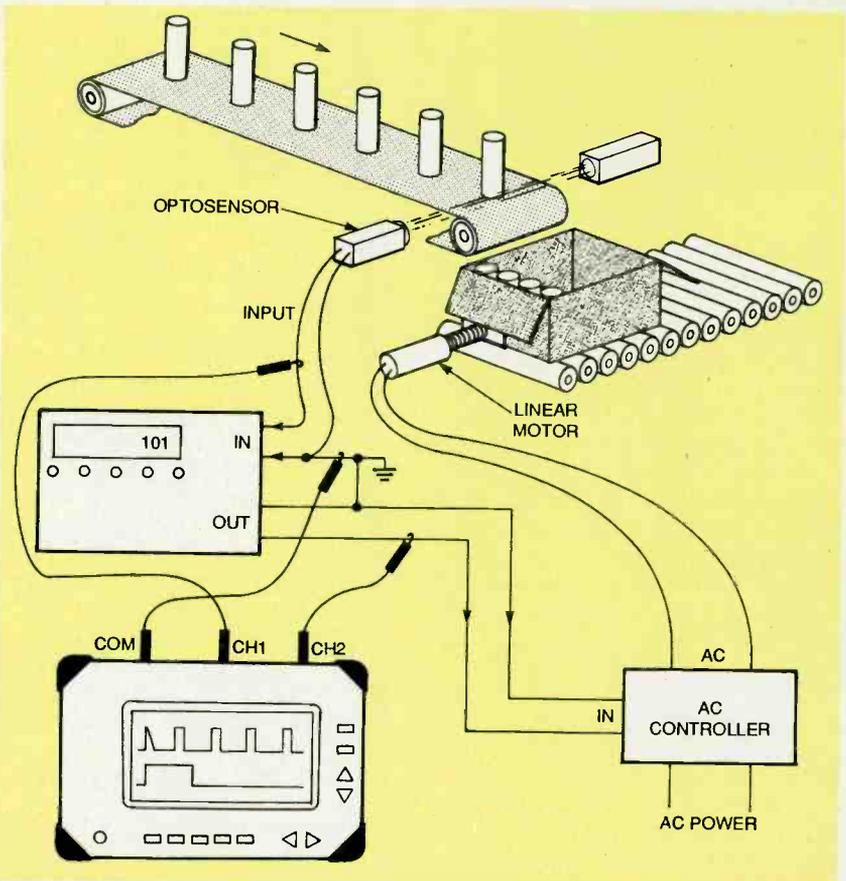


FIG. 3—TROUBLESHOOTING THE PLC CONTROLLER. Connections between the PLC and the process are shown. We can also see how the scope was used to monitor the system.

2000) and the result is 24. That didn't seem to mean anything at first, but it was the exact number of cans that are in each carton. So now we decided to

examine if anything happened in the process only once each carton-filling cycle. We noticed that a small linear motor was energized after each carton was filled to push the carton off the conveyor belt and onto a sealing roller line. Naturally, our investigation then turned to this new suspect.

Just like these Fully Trained Electronics Professionals



"Thanks to CIE I have tripled my previous salary, and I am now in a challenging and rewarding new field where only the sky is the limit."
Daniel Wade Reynolds
Industrial Electrician
Ore-Ida Foods



"CIE was recommended to me by my boss. It was appealing since I could study at my own pace at home and during business travel."
Dan Parks
Marketing Manager/Consumer Products
Analog Devices, Inc.



"I loved the flexibility CIE offered. It was the only way I could continue both school and my demanding job."
Britt A. Hanks
Director of Engineering
Petroleum Helicopters, Inc.




"I liked the way the school was set up with laboratory assignments to enforce conceptual learning. The thing which impressed me the most about CIE's curriculum is the way they show application for all the theory that is presented."
Daniel N. Parkman
Missile Electro-Mechanical Technician
U.S. Air Force



"Completing the course gave me the ability to efficiently troubleshoot modern microprocessor based audio and video systems and enjoy a sense of job security."
Tony Reynolds
Service Manager/Technician
Threshold Audio & Video

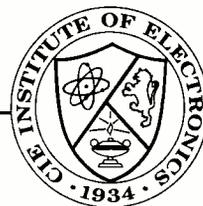Graduate with an Associate Degree from CIE!



CIE is the best educational value you can receive if you want to learn about electronics, and earn a good income with that knowledge. CIE's reputation as the world leader in home study electronics is based solely on the success of our graduates. And we've earned our reputation with an unconditional commitment to provide our students with the very best electronics training.

Just ask any of the 150,000-plus graduates of the Cleveland Institute of Electronics who are working in high-paying positions with aerospace, computer, medical, automotive and communications firms throughout the world. They'll tell you success didn't come easy...but it did come...thanks to their CIE training. And today, a career in electronics offers more rewards than ever before.

CIE'S COMMITTED TO BEING THE BEST...IN ONE AREA...ELECTRONICS. CIE isn't another be-everything-to-everyone school. CIE teaches only one subject and we believe we're the best at what we do. Also, CIE is accredited by the National Home Study Council. And with more than 1,000 graduates each year, we're the largest home study school specializing exclusively in electronics. CIE has been training career-minded students for nearly sixty years and we're the best at our subject...
ELECTRONICS... IT'S THE ONLY SUBJECT WE TEACH!

CIE PROVIDES A LEARNING METHOD SO GOOD IT'S PATENTED. CIE's AUTO-PRO-GRAMMED® lessons are a proven learning method for building valuable electronics

career skills. Each lesson is designed to take you step-by-step and principle-by-principle. And while all of CIE's lessons are designed for independent study, CIE's instructors are personally available to assist you with just a toll free call. The result is practical training... the kind of experience you can put to work in today's marketplace.

LEARN BY DOING...WITH STATE-OF-THE-ART EQUIPMENT AND TRAINING. CIE pioneered the first Electronics Laboratory



Course and the first Microprocessor Course. Today, no other home study school can match CIE's state-of-the-art equipment and training. And all your laboratory equipment, books and lessons are included in your tuition. It's all yours to use while you study and for on-the-job after you graduate.

PERSONALIZED TRAINING....TO MATCH YOUR BACKGROUND. While some of our students have a working knowledge of electronics others are just starting out. That's why CIE has developed twelve career courses and an A.A.S. Degree program to choose from. So, even if you're not sure which electronics career is best for you, CIE can get you started with core lessons applicable to all areas in

electronics. And every CIE Course earns credit towards the completion of your Associate in Applied Science Degree. So you can work toward your degree in stages or as fast as you wish. In fact, CIE is the only school that actually rewards you for fast study, which can save you money.



YES! I want to get started. Send me my CIE course catalog including details about the Associate Degree Program. (For your convenience, CIE will have a representative contact you - there is no obligation.)

Please Print Clearly

Name _____

Address _____

City _____

State _____ Zip _____ Age _____

Phone No. _____

Check box for G.I. Bill Benefits.

Veteran

Active Duty

AE86

Cleveland Institute of Electronics, Inc.
1776 East 17th Street
Cleveland, OH 44114

A School of Thousands.
A Class of One. Since 1934.

Send for CIE's FREE Course Catalog and See How We Can Help Your Career Too!

activated. Not only did the heightened pulse look different from the can-count pulses, it had a different timing delay than that of the 100 can-per-second pulses. But the PLC logged the pulse just as though there were a 25th can in each box.

Diagnose the problem

Using the same scope connections, with the line still run-

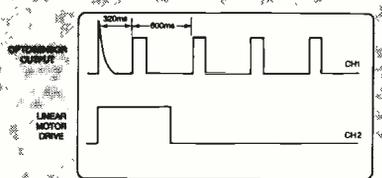


FIG. 4—WAVEFORMS ON THE SCOPE SCREEN quickly identified the problem as an extra spurious pulse.

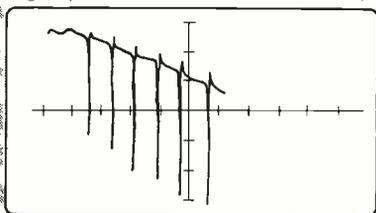


FIG. 5—WAVEFORM OF THE COOL-DOWN thermal output as it appeared on the scope display.

ning, we attempted to eliminate the extraneous pulse. As we examined the physical layout of the plant floor, we found that the optical sensor cable passed by and directly over the housing of the linear motor. Immediately we suspected that magnetic coupling between the motor and the sensor output line leading to the PLC was causing the extra pulse. As we watched the scope display we tried rerouting the sensor cable. As we did so we noted that the decaying pulse on the sensor line disappeared, eliminating the problem. Then we had a fully operational—and correctly functioning—packing line.

Taking the heat off

Another case history where an oscilloscope saved the day was in solving a problem in an annealing furnace. It had been producing perfect coil springs for two months, but it suddenly began producing weak springs that failed and were being returned by customers as defective. Quality control verified the problem, and they agreed: The springs were weak and lacking proper tensile strength. We im-

mediately suspected some change in the cycle of the annealing furnace. We looked back at the annealing logs for the past few weeks and found that the annealing cycle had been shortened from the original 18 hours to 16 hours. The log revealed that the two-hour change took place during the night when no workers were in the plant, and no one noticed the change. When the crew arrived the next morning they incorrectly assumed that the coils had been properly tempered overnight.

Checking out timers

This time there were two puzzles to solve. First we had to find out why the process failed. Then we had to reset the PLC to provide the correct timing cycle. Most of the cycle was controlled by timers. The only exception was the cooling phase, in which the coils remained in the oven until they cooled to less than 400 degrees Fahrenheit.

Obviously, we checked the timers first, and found that they were all operating correctly. That pointed to a possible cool-down cycle problem. As we examined the PLC operating logs from the past two-week's cool-down cycles, we found that cool-downs were running only about one to two hours, or two hours shorter than what would be normal. Aha! That is where the problem was hiding!

Since we knew that the cool-down time was controlled by the thermocouple reading, we connected a portable scope to the PLC thermocouple input and watched as the furnace switched from its soak to its cool-down phase.

We connected the scope's CH1 to the thermocouple output, selected the autorange mode, and set the sweep to its slowest speed—1 minute per division on the TekMeter. This made ten minutes of cool-down visible at any time. After about six minutes of cool-down we saw the scope trace in Fig. 5. The spikes on the line were abnormal, so we watched closely and noticed that they occurred about once

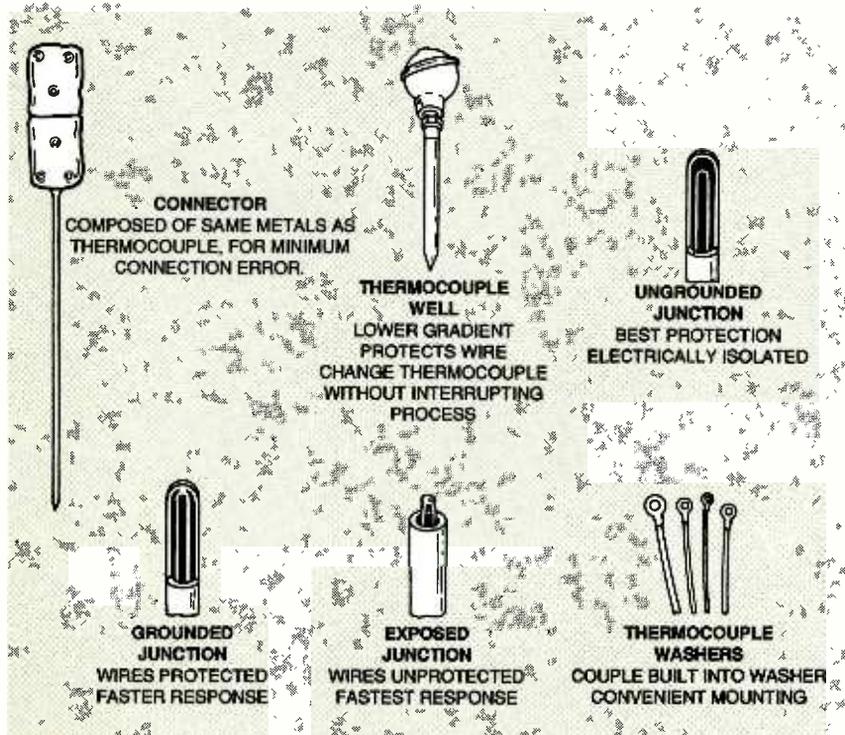


FIG. 6—TYPICAL THERMOCOUPLE CONFIGURATIONS that we will encounter in industrial applications.

Continued on page 73



Build a Kelvin-Varley voltage divider to complete the mini metrology lab.

MINI METROLOGY LAB

CONRAD R. HOFFMAN

THE FIRST TWO PARTS OF THIS SERIES showed how to build a voltage standard and a null detector. This final article shows how to build a precision voltage divider to complete the mini metrology lab. The voltage divider is a key component of the measurement lab because it allows both larger and smaller voltages to be compared to the voltage standard. It can also act as one side of an ultra-precise resistance bridge, allowing many different values of resistance to be compared to a single known resistance standard.

Of the many types of divider schemes, the Kelvin-Varley divider (KVD) is one of the most useful and desirable because it combines both superb ratio accuracy and high resolution. Found almost exclusively in calibration labs, the KVD is used for the most critical calibrations and measurements.

Commercial KVDs are often

accurate to 1 part per million (PPM) or even 0.1 PPM. Unfortunately prices for commercial units start at about \$4000, and can easily exceed \$10,000. The cost of precision wirewound or bulk metal-foil resistors, multi-deck switches, and substantial hand labor, conspire to keep commercial KVDs beyond the reach of experimenters.

So can you build a decent KVD without breaking the bank? Absolutely! We'll get into the details shortly, but here are a few specifications to whet your appetite. Our KVD is a full six-decade device, just like the commercial ones. It will resolve 1 PPM. Though the design goal was an absolute accuracy of 20 PPM or .002%, the prototype was twice as good—it was better than 10 PPM at all settings! The total cost of the project is under \$75, but a well-stocked junk box can reduce that substantially.

How does it work?

The best way to understand how a Kelvin-Varley divider works is to look at just one decade, shown in Fig 1. There are 11 resistors in the main divider string, but two of them are in parallel with the output divider, in this case, a potentiometer. The value of the output divider is chosen so that the parallel combination of it and the other two resistors is equal to one step of the main divider. Thus, the circuit is the equivalent of a simple ten-resistor divider.

No matter where on the main divider the output divider is placed, the circuit that results is always a ten-resistor divider. Since the output divider is a potentiometer, any voltage between the two tap voltages can be selected.

The simple output divider (potentiometer) can be replaced by another decade constructed in the same manner as the first.

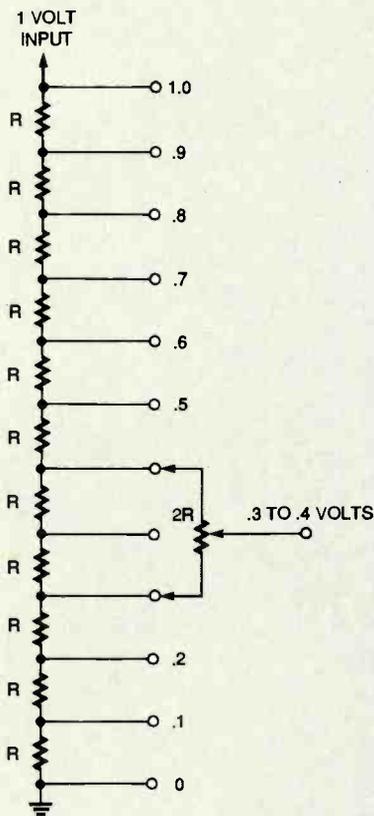


FIG. 1—A SINGLE KVD DECADE. Note that the circuit is equivalent to a 10-resistor divider.

The decade must, of course, have a total resistance equal to twice the resistor value used to construct the first decade. Each additional decade increases the resolution by a factor of ten. In theory you can add as many decades as you want, but the divider accuracy is always limited by the first decade.

The last decade is a simple ten-resistor divider, since there is no divider in parallel with any of its elements. The top position is the "carry" position, so full output from the KVD will be 9-9-9-9-9-10. Sometimes, a potentiometer is used for the last decade, giving continuous resolution over the full range of the divider.

Figure 2 shows the full KVD configuration. Trimmer networks have been added so that any decade can be shunted to the correct total value. That way you have to be concerned only with resistor matching, not exact resistor values.

You might notice that the re-

sistor values used in each decade set an absolute minimum value for the following decade. The traditional series is 10K, 2K, 400, 80, 16, and 3.2 ohms, with no shunts. This KVD is designed to use standard value resistors, and to have reasonable

value shunts. Thus, the values are somewhat different. Remember, you can only shunt a decade one way—down!

Design issues

One of the biggest problems in designing this project was finding an affordable way to do the switching. Older KVDs used unique rotary switches which had dual multiple leaf wipers and large brass lugs for contacts. The high contact pressure resulted in very low resistance. Most modern KVDs use high quality two deck wafer switches. Unfortunately, the old switches are no longer available, and the modern replacements are quite expensive. However, the switch design presented here will fit anyone's budget—the "switches" cost just over a dollar each!

The decade resistors are mounted on six twelve-pin headers. Switching is done by moving a plug up and down the header. A three-hole plug is used, with only the end holes connected to the next decade. The physical layout very much resembles the schematic, helping to reinforce the principles of KVD operation. It is also reminiscent of early dividers and bridges that used brass plugs to make connections between adjacent resistors.

The other design issue is the type of resistors to use. Wire-wound or bulk metal-foil resistors would be ideal, but they would cost several dollars each, pushing the cost of the KVD out of many people's reach because of the tolerances and quantities required.

The best easily obtainable resistor is the 1% metal-film type. Its temperature coefficient or tempco is not the best, and its stability isn't well characterized, but those factors can be worked around. If the resistors are selected carefully, and they are put to work over a reasonable temperature range, they can provide quite acceptable performance. However, it is important to check the ratio accuracy occasionally. Although I had some doubts about at-

Continued on page 74

PARTS LIST

All fixed resistors are metal film, RN55D, 1%, or better. See text for selection process.

- R1–R11—10,000 ohms, selected
- R12–R22—2050 ohms, selected
- R23–R33—412 ohms, selected
- R34–R44—100 ohms
- R45–R65—24.9 ohms
- R66—806,000 ohms
- R67—825,000 ohms
- R68—4220 ohms
- R69—499 ohms
- R70—100 ohm multitrurn trimmer
- R71, R72—50,000 ohm multitrurn trimmer
- R73, R74—1000 ohm multitrurn trimmer

Connectors

- J1–J6—12 Pin Header, Molex 26-48-1121
- P1–P6—3-Position Connector, Molex 09-50-8031
- J7, J8—5-way Binding Posts, Red
- J9, J10—5-way Binding Posts, Black

Miscellaneous

- Terminals, Molex 08-52-0072, (Digikey WM2302-ND), case, small rubber grommets, epoxy, hot glue or cyanoacrylate, hookup wire, 22 AWG, insulated, multistrand (two colors required) 9V batteries (3), resistors for comparison bridge (2K, 49.9K), trimmer potentiometer for comparison bridge (1K, multitrurn), brass strip (.015" thick, or similar)

Note: For those needing lower temperature coefficient and greater stability, precision bulk metal foil resistors can be ordered in small quantities from: Vishay East, #1 Precision Place, Hagerstown, MD 21742; (301) 739-8722 or Vishay West, 3431 - I Pomona Blvd., Pomona, CA 91768; (909) 594-6737. High quality ceramic rotary switches are available for this project from the author. Please inquire as to price and availability: Conrad Hoffman, 4391 County Road #1, Canandaigua, NY 14424-9611; E-mail 73260.2255 @compuserve.com

MARK A. McGUIRE

HEATSINKING IS USUALLY OF LITTLE concern in low-power circuits. Most of the time you can bolt the component's metallic tab to a scrap of metal, or maybe to the chassis, without further concern as to how hot it might get. Low-power applications require minimal thermal mass—a few square centimeters of sheet metal—to transfer the small amount of heat generated by a low-power semiconductor to the air.

Nevertheless, heatsinking is of crucial concern for power components in circuits designed to take full advantage of their capabilities. The power component and its driving components can be destroyed when heat cannot be drawn away fast enough.

Two simple formulae will tell you how hot your semiconductors will get in operation. Using them eliminates guesswork and the accompanying apprehension about guessing wrong and making a mistake.


Convection

The design objective for cooling semiconductors is to take advantage of natural convection, which is the transfer of heat by a circulating gas or fluid, in this instance, by ambient air at room temperature. The amount of heat that can be transferred by convection is proportional to the surface area of metal exposed, the velocity of the air passing over the surface, and the temperature difference between the two. This article is limited to the discussion of convective heat transfer to vertical surfaces and natural (as opposed to fan-driven) convective air flow. Nevertheless, even with this limitation, it covers most cooling problems posed by the project designs undertaken by most experimenters.

The power semiconductor is considered a resistive element, as far as the heatsink is concerned. Thus the voltage drop across the device multiplied by the current through it (or I^2R in the case of a power MOSFET)

HOW TO SELECT THE RIGHT HEATSINK

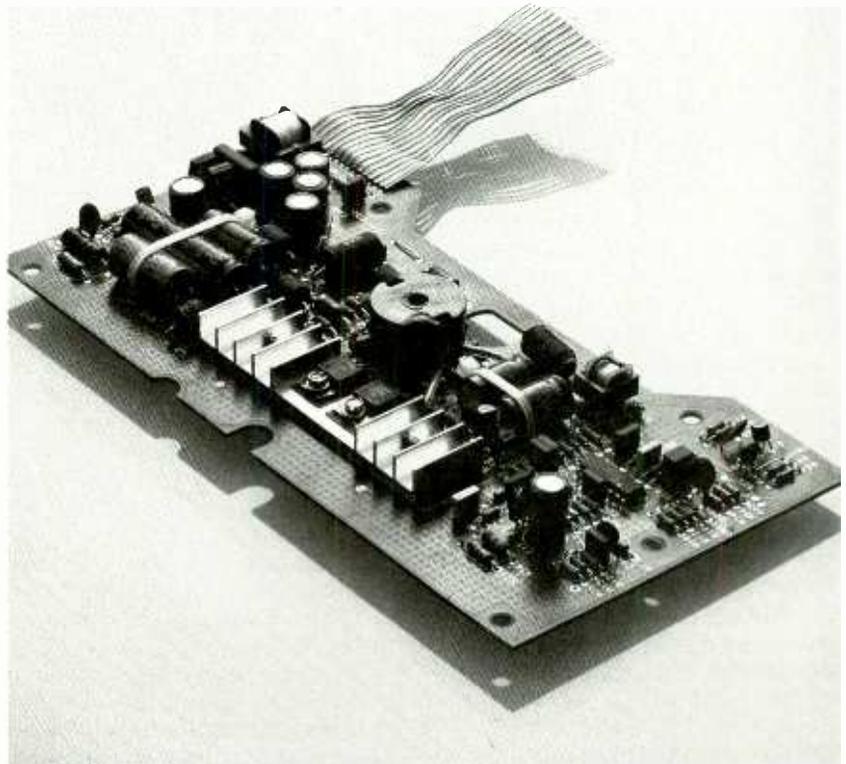*From project design to assembly,
two easy equations assure
sure-fire cooling!*




multiplied by the time factor (percent of time it is conducting divided by 100), equals the heat equivalent in watts that the device generates and that must be dissipated into the air by the heatsink. For a simple linear power-supply semiconductor, this is a straightforward calculation. For a semiconductor power switching transistor, the calculation is more involved. For an audio amplifier you might have to estimate dissipation. In any case, make the calculation of the heat to be dissipated equal to the heat in watts as accurate and conservative (on the high side) as you can.

If you have the data sheet for the semiconductor device you

will mount on a heatsink, look up its junction-to-case thermal impedance, and case-to-sink thermal impedance. These impedance values are expressed in degrees C per watt, and mean that for every watt of heat power the junction dissipates, it will be a specific number of degrees C hotter than the case—the same applies from the case to the heatsink. If you intend to keep the junction at or below 100° C, and the junction-to-case thermal impedance is 10° C/watt, then 7.5 watts will raise the junction temperature to 100° C, even if the case is kept at a constant 25° C—which might be possible if it were immersed in running water.

Typical junction-to-case ther-

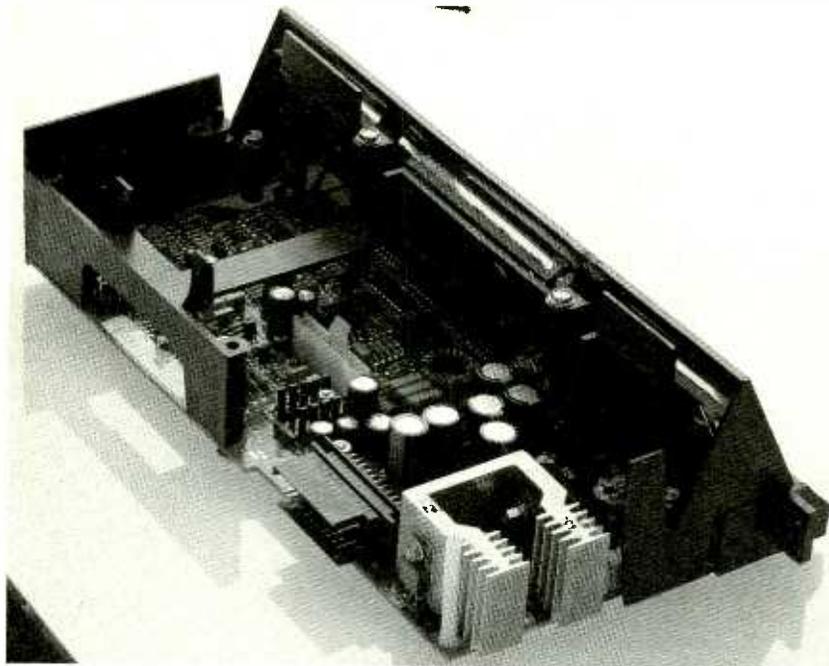

HEATSINKS come in many various sizes and shapes, but the physics of selection is unique and covered in text. Compare this heatsink with the one on the first page of this story.

mal impedances (Z_{JC}) are 1°C/W for an International Rectifier IRFZ40 MOSFET, and 1.52°C/W for 2N3055. A typical TO-220 case-to-sink thermal impedance (Z_{CS}) is 1°C/W , and for a TO-3 case, 0.12°C/W . Estimate the junction-to-case thermal impedance for your specific semiconductor device using these values for guidance if you do not have the device's data sheet.

Design considerations

What is the maximum temperature the semiconductor's junction should reach? Many circuit designers usually peg the maximum junction temperature at 80°C , because the semiconductor's characteristics will be seriously degraded at higher temperatures, and thermal runaway is a danger for bipolar transistors. Do not take the manufacturer's data sheet claims of maximum watt values and junction temperature seriously. These values are valid only when the device is continuously cooled so that the case is held to a constant 25°C .

Air cooling

What is the ambient air temperature? Remember, the semi-

conductor device might be inside an enclosure where other heat-producing devices are contributing to the temperature of the ambient air. If you are sure that normal room air can gain free access to the device, you can assume 25°C , but be careful. Recall that the ambient temperature rises in the summer, and 100°F equals 38°C .

Knowing these facts, you can determine ΔT , or the expected temperature difference between the as-yet-unknown heatsink size and the air that will provide the cooling.

$$\Delta T = T_{\text{MaxJ}} - [W_J \times (Z_{JC} + Z_{CS})] - T_{\text{AA}}$$

where Z_{JC} is the junction-to-case thermal impedance, Z_{CS} is the case-to-sink thermal impedance, T_{AA} is the ambient air temperature, T_{MaxJ} is the maximum junction temperature, and W_J is the junction wattage.

Example: You want to operate a 2N3055 transistor as a motor control, drawing 3 amperes. You will find that the transistor drops 1.2 volts at this current value, and know the maximum duty cycle will be 50%, or 0.5. So, $3 \times 1.2 \times 0.5 = 1.8$ watts. If you decide on a 80°C maximum junction temperature, and 25°C

ambient air so that

$$\Delta T = 80 - [1.8 \times (1.52 + 0.12)] - 25$$

$$\Delta T = 52^\circ\text{C}$$

The ΔT computation reveals that the estimated heatsink might be 52°C hotter than the air under these conditions. How big, then, must this heatsink be? The answer is calculated as follows:

$$A = W_J \times 5630 \div \Delta T^{5/4}$$

where A = area of the heatsink vertical surface in square centimeters. If you prefer to work with square inches:

$$A = W_J \times 872.6 \div \Delta T^{5/4}$$

In the case of the 2N3055 transistor and using the previous equation for heatsink surface area in square inches, this is

$$A = 1.8 \times 872.6 \div 52^{5/4}$$

$$A = 11.2 \text{ square inches}$$

Thus a heatsink of at least 11.2 square inches of vertical surface area located in free air will do the required cooling job for the transistor.

If you intend to use two or more identical semiconductor devices on the same heatsink, and they are drawing similar currents (e.g. parallel devices), you can do the calculation as if it is for a single device if you calculate the heat power of the combination, and divide the thermal impedances by the number of devices. Dissimilar semiconductor devices should be mounted on different heatsinks.

Example: Two IRFRZ40 power MOSFETs are connected in parallel in a low-voltage switching power supply. The currents are likely to surge to 40 amperes through both devices, and their duty cycles might approach 80%. The on-resistance of the IRFZ40 (the device is conducting) at 80°C is about 0.036 ohm, so the parallel pair will exhibit a resistance of 0.018 ohm to the 40 amperes, giving $0.018 \times 40 \times 0.8 = 23$ watts. Assume a worst case at 38°C as if you were in an Arizona desert during the summer.

Continued on page 48

Switching power supplies, the hot chassis, and more PIC tricks

SWITCHING-MODE POWER SUPPLIES ARE NOW USED PRETTY NEAR EVERYWHERE, ESPECIALLY IN PERSONAL COMPUTERS AND PERIPHERALS. INSTEAD OF DOING A DIRECTLY CONVERTING POWER AT 60 HERTZ, raw DC is first created.

The DC, in turn, powers a high-frequency oscillator of some sort. Isolation, power conversion and regulation are typically done at a 20 kilohertz or higher frequency.

Switchmode advantages include high efficiency, light weight, low heat, small size, tight regulation, reduced heatsinking, and low costs. Transformers in particular are much smaller and lighter than their counterparts in linear power supplies. So are most filter capacitors.

Even though severe safety hazards and oddball circuits may be involved, these supplies can end up fairly easy to understand and service.

Let's take a closer look at some of the fundamentals.

The hot chassis then and now

Your power utility provides you with a 220 volt center-tapped home service. The center tap is grounded. Two individual 110 volt arms are split out to supply various circuits in your home. Thus, one end of each 110 volt line is "hot" and one is "grounded". Should you get between hot and ground, you can receive a fatal shock.

Anything that plugs into the power line needs some way of deal-

ing with possible shock hazards—both to the end user and to anyone doing service. A power transformer is one costly yet effective solution.

At one time, low cost AM radios avoided the use of a transformer by going to the hot chassis system of Fig. 1. One side of the AC power line was physically connected to the chassis of the radio. Plugs in those days were not polarized, so you had a 50-50 chance that the chassis would be hot. Touch the chassis and you are toast!

The reasoning was that the brittle plastic case and easily broken knobs would sort of protect an average user. Well, so long as no one put their fingers in the back. And service techs were supposed to know better. Besides, none of the fatalities ever complained.

I am utterly amazed that scads of people weren't electrocuted by these obvious hazards. Service people (at least the ones that survived) quickly learned to respect a hot chassis.

If you were brave, you touched the chassis through a neon test light. If the lamp dimly lit, you then reversed the plug. If you were smart, you used an isolation transformer instead.

Premium hi-fi's and television sets made use of weighty and expen-

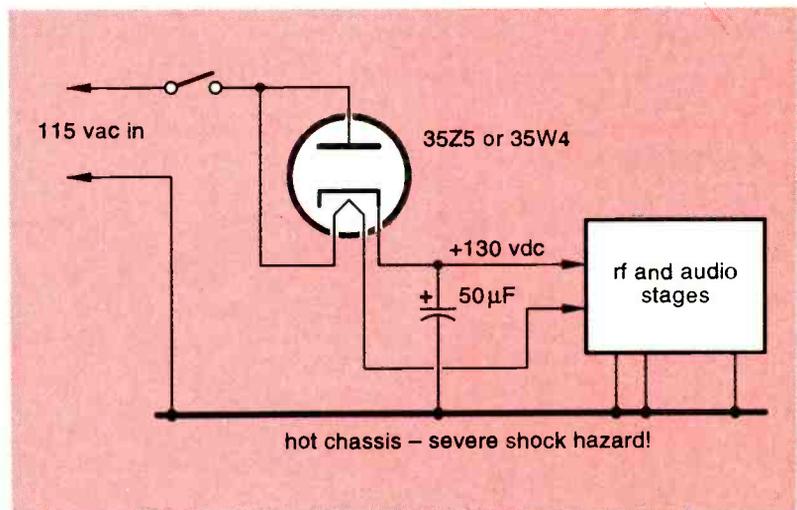


Fig. 1—THE HISTORIC "HOT CHASSIS" PROBLEM. Tube type "AC-DC" am radios had one side of the ac power line connected directly to their metal chassis. Depending on how the line cord was plugged in, you had a 50-50 chance of receiving a bad shock when you touched the chassis.)

new from
DON LANCASTER

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. \$28.50

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. THE two books for digital integrated circuit fundamentals. About as hands-on as you can get. \$24.50 each.

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. \$18.50

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. \$119.50

LOTS OF OTHER GOODIES

Ask the Guru I or II or III	\$24.50
Hardware Hacker II or III	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell	\$29.50
Intro to PostScript Video	\$29.50
PostScript Reference II	\$31.50
PostScript Tutorial/Cookbook	\$19.50
PostScript by Example	\$31.50
Understanding PS Programming	\$29.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking In PostScript	\$22.50
LaserWriter Reference	\$19.50
Type 1 Font Format	\$15.50
Acrobat Reference	\$24.50
Whole works (all PostScript)	\$380.00
Synergetics Surplus Catalog	FREE
Technical Insider Secrets	FREE

POSTSCRIPT SECRETS

A Book/Disk combination crammed full of free fonts, insider resources, utilities, publications, workarounds, fontgrabbing, more. For most any PostScript printer. Mac or PC format. \$29.50

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. \$39.50

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set reveals to you tested and proven real-world alternatives. \$28.50

BLATANT OPPORTUNIST I

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. \$24.50

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. \$24.50

FREE SAMPLES

Well, nearly free anyway. Almost. Do join us on GENIE PSRT to sample all of the Guru's goodies. The downloading cost on a typical Guru file is 21 cents. Modem access: (800) 638-8369, then a JOINGENIE. Use DMD524 for your keycode.

FREE VOICE HELPLINE VISA/MC

SYNERGETICS
Box 809-EN
Thatcher, AZ 85552
(520) 428-4073

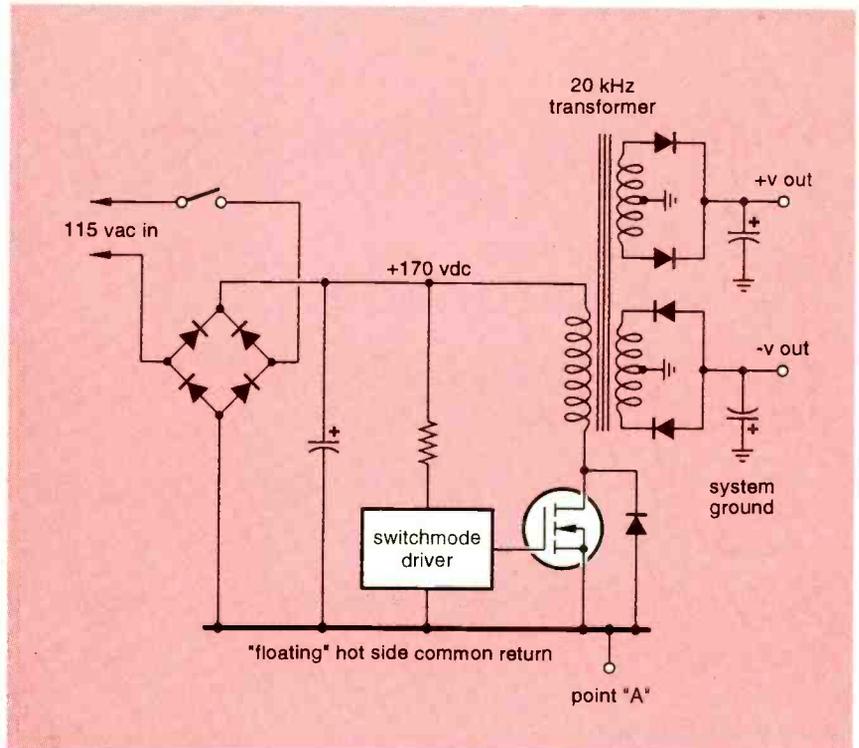


Fig. 2—A TYPICAL SWITCHING POWER SUPPLY. Note that there is an EXTREME shock hazard to the left of the transformer. Be sure to note that connecting a scope ground lead to point "A" will instantly blow one or more power diodes! An isolation transformer MUST get used for ALL service.

sive power transformers. As circuits went solid state and the total power needs dropped, at least some of these went to today's lower power wall-mount transformers. The only hazard here is inside your small throwaway unit.

But transformers were still needed if higher powers or lots of different supply voltages were required. These remained big and expensive. Until someone got the brilliant idea to use high frequency transformers instead of 60-Hz ones.

All other things being equal, a 20 kHz transformer only needs 1/33rd the weight and volume of a 60-Hz one. Even better yet, you saved two ways on filter capacitors. First because of the increase in frequency. And even more so since you were now dealing with easily-filtered square waves.

These new high frequency circuits are known as switching mode power supplies. As Fig. 2 shows us, the end user is fully safety isolated and has nothing to worry about.

Not so the service person.

For there is now a hot side and a

cold side to any switch mode supply. There are high to very high voltages on the hot side. A person servicing tube radios gets a shock every now and then as a painful reminder. It was not nearly as unheard of as in most modern repairs.

There is an extreme shock danger on the hot side of any switching mode power supply!

Moreover, there is usually a diode bridge on the input. So, the negative side of the filter capacitor is always one diode drop removed from the hot side of the AC power line!

If you connect a scope ground to the "ground" side (point "A") of your filter capacitor, you will immediately blow out at least one of the diodes in the bridge regardless of whether any fuse is present. The diode will usually blow first because you just put the full line voltage directly across it. Also, in the process, you are likely to vaporize your scope probe lead, burn yourself, and receive a severe shock.

So, the old "hot chassis" problem is now back in spades. And it's much worse than before. Because reversing your line cord (A) is not possible and

POWER SUPPLY RESOURCES

Analog Devices

PO Box 9106
Norwood MA 02062
(617) 329-4700

Coilcraft

1102 Silver Lake Rd
Cary IL 60013
(800) 322-COIL

Electronic Component News

1 Chilton Way
Radnor PA 19089
(215) 964-4345

Electronic Products

645 Stewart Ave
Garden City NY 11530
(516) 227-1300

Ferroxcube

2001 W Blue Heron Blvd
Riviera Beach FL 33404
(407) 881-3200

Galco

26010 Pinehurst Dr
Madison Heights MI 48071
(800) 521-1615

International Rectifier

233 Kansas St
El Segundo CA 90245
(310) 322-3331

Linear Technology

1630 McCarthy Blvd
Milpitas CA 95035
(408) 432-1900

Magnetics Inc

Box 391
Butler PA 16003
(412) 282-8282

Maxim

120 San Gabriel Dr
Sunnyvale CA 94086
(800) 998-8800

Motion Magazine

Box 6430
Orange CA 92613
(714) 974-0200

Motorola

5005 E McDowell Rd
Phoenix AZ 85008
(800) 521-6274

National Semiconductor

2900 Semiconductor Rd
Santa Clara CA 95052
(800) 272-9959

PCIM

2472 Eastman Ave #33-34
Ventura CA 93003
(805) 658-0933

Phillips Magnetics

1033 Kings Highway
Saugerties NY 12477
(914) 246-2811

Power Transmission Design

1100 Superior Ave
Cleveland OH 44114
(216) 696-7648

Sensors

174 Concord St
Peterborough NH 03458
(603) 924-9631

SGS

1000 East Bell Road
Phoenix, AZ, 85022
(602) 867-6100

Supertex Inc

1350 Bordeaux Drive
Sunnyvale CA 94089
(408) 744-0100

Surplus Traders

PO Box 276
Alburt VT 05440
(514) 739-9328

Tecor Electronics

1801 Hurd Drive
Irving, TX 75038
(214) 580-1515

Texas Instruments

PO Box 809066
Dallas TX 75380
(800) 336-5236

Toko

1250 Feehanville Drive
Mt Prospect IL 60056
(708) 297-0070

Unitrode

580 Pleasant St
Watertown MA 02172
(617) 926-0404

isolate the real culprit: Very few integrated circuits or diodes do much of anything below 0.3 to 0.6 volts. I next injected an 0.4 volt peak-to-peak triangle wave to points C and D, with the power cord disconnected and all grounds removed.

With any 42-volt, one-amp supply, you'd expect that the 20 kHz no-load input impedance at this point to be well above 42 ohms. Instead, it was way down in the milliohms. Telling us that the short was real. Gotcha!

But a check on the high voltage output winding did reveal a smallish triangle wave. And, on switching to a square wave, transformer-type droop and ringing appeared. So there was at least some hope.

Tektronix does provide some jumpers to simplify servicing. Cutting these did not help at all.

But we already knew that from the previous resistance tests! Duh.

The next logical step would have been to remove the transformer from the circuit board and thoroughly test it. That, however, is a slow and painful process. So, just for luck, I first ran an ohmmeter around the diodes. Sure enough, there was a dead short across the diodes on the 30 volt supply.

The usual candidate for a shorted part is the filter capacitor. A shorted diode in any properly designed and inherently current limited supply is extremely unlikely.

But a good diode would never let this weak test signal even reach the capacitor! If the capacitor were bad, a larger input signal (above 0.6 peak volts) would clip, not reveal a total short, which was my reason for using a triangle wave in the first place.

I ignored this obvious fact, and removed the filter capacitor anyway. Sure enough, as you might expect it tested just fine out of the circuit. At least as a quick and dirty "watch it kick" ohms test.

Lifting one end of each diode did in fact reveal one of them to be a dead short. In my experience, that's very rare indeed.

Note that these are higher speed power diodes that have special short recovery times. But even direct from Tektronix, their exact part cost only fifty-five cents.

SomeTips

Once again, please remember that any misplaced scope ground lead can instantly ruin a line-operated switch mode supply! Always use an isolation transformer, and think before you connect or measure!

Getting information and parts from Tektronix can sometimes be tricky. Older parts and manuals are no

longer available, and certain key newer items seem to be outrageously overpriced.

An outstanding alternate Tektronix resource is Stan Griffiths and his fine *Oscilloscopes* —Restoring a Classic book. Stan also knows of several low cost sources for long-gone to modern Tektronix parts. These private sources did not wish to be listed in any nation-

al magazine, but they sometimes can be made available to you when you call or write Stan.

I've also got a major collection of genuine Tek manuals available at reasonable prices. Write or call for info. Or grab the listing off GENie PSRT as file SURPCAT1.PDF.

Power supply resources

For this month's resource sidebar, I thought we'd review a few places to go for power supply information.

Your finest supplier is probably Maxim, who provide lots of application notes and free samples. Other chip sources include National, Motorola, Analog Devices, Unitrode Inc, International Rectifier, Texas Instruments, and Linear Technology.

One useful trade journal is PCIM. A good power supply web site can be found at <http://motioncontrol.com>

A complete review for all power electronics appears as NUTS46.PDF in my GENie PSRT library. I've also got a large pile of aerospace quality lab power supplies at very low prices in our freebie surplus flyer. Printed copies are available with a phone request or can be obtained online interactive as SURPCAT1.PDF.

Another PIC trick

I've been doing a lot more with the PIC microprocessor, especially for new magic sinewave development. Uh, it seems that plain old shift-right and shift-left commands are missing from the PIC instruction set. Among many other uses, these are real handy for dividing or multiplying by two.

Several helpline callers have also requested these commands. Fig. 4 shows some easy workarounds. Just use a rotate right or left through the carry, and then repair the possible damage with a second zero-forcing code byte. Even with two clocks and two cycles, this patch still blows the competition away.

Let me know if there's any other PIC programming tricks you want to see. A free Incredible Secret Money Machine II book will go to a dozen of the best requests. A magic sinewave tutorial appears as MAGSINT.PDF on GENie PSRT. I'll also be happy to mail you a free copy on request.

```
REGISTER SHIFT RIGHT-
This method first clears the carry...
BRIGHT1 BCF S,C ;clear the carry flag
        RRF F,1 ;rotate all bits right

This method repairs possible damage instead...
BRIGHT2 RRF F,1 ;rotate all bits right
        BCF F,7 ;force bit 7 to zero

REGISTER SHIFT LEFT-
This method first clears the carry...
SLEFT1 BCF S,C ;clear the carry flag
        RLF F,1 ;rotate all bits left

This method repairs possible damage instead...
SLEFT2 RLF F,1 ;rotate all bits left
        BCF F,0 ;force bit 0 to zero

OPTIONS-
Use of RLF F,0 or a RRF F,0 puts shifted result into the accumulator instead.
To shift a value already in the accumulator on low end PIC devices, MOVWF to
temporary register storage, then use above methods. Note the accumulator is
already register mapped on 17CXX PIC chips.
Note also that the carry flag exits in an unknown state.
```

Fig. 4—THE PIC MICROCOMPUTER lacks simple "shift right" and "shift left" instructions. Here is how to provide them in two or three code bytes.

Cheap low current fuses

As we've seen a time or two in the past, Recharger magazine is the best source for all laser printer cartridge reloading info. It appears that some epsilon minuses at Xerox have recently been including sequentially blowable fuses in their laser printer cartridges. Their intent is to make recharging a tad more challenging.

The fuses are apparently rated at 20 milliamperes and 200 volts. The host blows the first fuse after a few hundred copies, the second when it thinks toner is low, and third when it decides your toner is out.

Several Recharger authors are now looking for a low cost source for low-current fuses. A fast check into any distributor's catalog reveals that low-current fuses are insanely expensive and ridiculously hard to find.

Well, in nearly all lower current protection schemes these days, you substitute a cheap and automatically resetting posistor instead. Such as those made by Raychem. A posistor's resistance sharply increases with the heating caused by an increasing load

current. This resistance change will in turn greatly reduce the available power delivered to the rest of your circuit. Reset is automatic, happening shortly after the overload goes away. But a posistor clearly will not work where any fuse is to be intentionally and permanently blown.

Instead, try using a single strand of #000 steel wool! These have a near zero cost and typically will open in the tens of milliamperes. The strands are usually solderable if you do not touch them. And if you use a better grade of liquid solder flux.

This same trick works just fine in a student lab to protect milliameters and microammeters. Hang a pair of reverse-parallel silicon diodes across the meter terminals, and put a single strand of steel wool in series.

New tech lit

From Mitsubishi, a superb *ASSP Availability Guide*. Covering all sorts of interesting chips. Including the M65830 digital echo, M50194 digital reverb, 66330 fax codec, the 67405 surround sound processor, and 66512

HEATSINKING

continued from page 46

$$\Delta T = 80 - [23 \times (0.5 + 0.5)] - 38$$
$$\Delta T = 19^\circ \text{C}$$

The size of the heatsink is then:

$$A = 23 \times 872.6 \div 19^{5/4}$$

$$A = 506 \text{ square inches}$$

The required 506 square inches might seem excessive, but a typical large heatsink that measures $5 \times 4 \times 2\frac{5}{8}$ inches which has 250 square inches of surface area would require another one to adequately dissipate the heat. Of course, those big heatsinks can be expensive, and if they cost more than the device itself, you might want to redesign the circuit with more semiconductor devices in parallel. This will lower the resistance and the heat that must be dissipated.

Experimenter's notes

Your finger is a rather unreliable temperature measuring device. A small thermistor, calibrated on the kitchen stove in a pot of distilled water with a confectioner's thermometer, is a much better approach if you must know how hot things will be for your project's semiconductors.

Be sure to coat the contacting surfaces of the semiconductor and heatsink with thermally-conductive grease before mounting the device on the heatsink. Without adequate heat transfer through the contacting surfaces, the semiconductor will be destroyed regardless of the size of the heatsink. The thermally-conductive grease might be supplied with the semiconductor or the mounting hardware kit or it can be obtained separately.

If you have trouble with the $\frac{5}{4}$ exponent of ΔT equation, find the logarithm of this number in a logarithmic table, multiply it by 1.25, and find the antilog of the result. If this doesn't help, a scientific or engineering calculator can provide the numbers. Ω

NAMES AND NUMBERS

Comlinear
4800 Wheaton Drive
Fort Collins CO 80525
(970) 226-0500

Stan Griffiths
18955 SW Blanton
Aloha OR 97007
(503) 649-0837

ITS World
859 Willamett Street
Eugene OR 97401
(541)343-1200

Eastman Kodak
343 State
Rochester NY 14650
(716) 724-4385

LZR Electronics
8051 Cessna Avenue
Gaithersburg MD 20879
(301) 921-4600

The Mart
899 Presidential Ste 110
Richardson TX 75081
(800) 864-1155

Mitsubishi
1050 E Arques Ave
Sunnyvale CA 94086
(408) 730-5900

Parallax
3805 Atherton Rd #102
Rocklin CA 95765
(916) 624-8333

Raychem
300 Constitution Drive
Menlo Park CA 94025
(800) 227-7040

Recharger
4218 W Charleston Blvd
Las Vegas NV 89102
(702) 438-5557

Synergetics
Box 809
Thatcher AZ 85552
(520) 428-4073

Tektronix
PO Box 500
Beaverton OR 97077
(800) 835-9433

Telecom Gear
15400 Knoll Trail Ste 500
Dallas TX 75248
(800) 866-3241

Temic
2201 Laurelwood Road
Santa Clara CA 95056
(408) 970-5700

Tessco
34 Loveton Circle
Sparks MD 21152
(800) 472-7373

Vetra Systems
275J Marcus Blvd
Happauge NY 11787
(516) 434-3185

laser beam controller.

From Comlinear, a data book on high performance analog amplifier chips. From Tessco, a new full line catalog of wireless communications equipment and supplies.

A very useful *IRDA Compatible Data Transmission Design Guide* is now offered by Temic. Included are the IRDA infrared communications specifications.

Ricoh has application notes and data sheets available on the new 5A128 low-cost speech-recognition circuits. A free new *Glossary of Image Sensor Terms* tutorial is offered by Kodak.

There's a brand new trade journal on intelligent transportation systems called, of all things, *ITS World*. This one features everything you might ask about from smart highways to GPS to CD ROM maps.

The best two telecommunication shoppers are Telecom Gear and The

Mart. One source for phone premise wiring and parts that I've found is LZR Electronics.

I do get a lot of calls from readers wanting remote PC keyboards, RS232 adaptors and extenders. Dozens of products to handle these tasks are offered by Vetra Systems. A PIC is the obvious choice to build your own instead. Start with the *Basic Stamp* from Parallax.

A reminder that I've just reprinted my *Active Filter Cookbook* for the seventeenth time. Refer to my nearby Synergetics ad in this issue for full purchasing details.

I've also acquired quite a unique collection of classic microprocessor trainers. Everything from genuine KIM-1's to gold plated HP 5036A's to superb little book-shaped Z80 Micro Professors. The latter with printers, no less. They all are both usable and highly collectible. You can write or call for bargain pricing. **EN**

WHAT'S NEWS

continued from page 4

Source of high-temperature superconductivity found?

IBM scientists have found evidence suggesting that a fundamentally new type of electron behavior is responsible for the so-called "high-temperature" superconductivity first discovered a decade ago in a certain class of ceramic materials. The finding is considered an important step toward understanding the details of why superconductivity (the flow of electricity without energy-robbing resistance) requires much less cooling in some materials than in others.

It is hoped that understanding the mechanism that creates high-temperature superconductivity will eventually lead to the creation of new materials with predictable superconducting properties. The ultimate (though perhaps impossible) goal, is to find superconductors that don't require any cooling. Such materials would revolutionize the distribution and use of electricity by eliminating the substantial heat and energy loss caused by electrical resistance.

It is believed that all superconductivity results from the ability of electrons to overcome their mutual repulsion and pair up in ways that allow them to pass unimpeded through the host material. Conventional "low-temperature" superconductivity is caused by a form of "s-wave pairing," in which charge-induced vibrations in the material hold the pairs together.

However, not all physicists believe that s-wave pairing should be the starting point for explanations of high-temperature superconductivity. Some postulate that "d-wave" electron pairing, in which the electrons' magnetic spins are critical, might be the basis for the phenomena.

Scientists at IBM's T.J. Watson Research Center in Yorktown Heights, New York, and their collaborators at State University of New York campuses in Buffalo and Stony Brook

present the most convincing evidence yet for d-wave electron pairing. While the IBM research does not pinpoint a particular mechanism as creating high-temperature superconductivity, it does limit the choices significantly.

At the heart of the experiments are four tiny rings (0.002 inches, about the diameter of a fine human hair) of a high-temperature superconducting material in which the elements thallium and barium are interspersed between sheets of copper oxide ($Tl_2Ba_2CuO_{6+\delta}$, or Tl2201). The scientists created the rings atop a substrate material made of three wedges, each with a different crystalline orientation. The rings were placed so that two of them spanned two crystalline orientations, one touched none, and only one crossed all three crystal boundaries. Because the atomic spacings of Tl2201 are nearly equal to those of the substrate, the crystalline orientation of any part of the superconducting ring exactly matches that of the wedge beneath it, and a transition region was forced above each wedge boundary.

When a scanning SQUID microscope was passed over the rings and recorded the observed magnetic fields, the scientists detected a spontaneous magnetic field emanating only from the ring that crossed all three crystal boundaries. That ring had a total magnetic field (or flux) exactly half the fundamental unit that occurs in rings of conventional superconductors.

The presence of that "half-flux quantum effect" was a sure indication of unusual (most likely d-wave) pairing. That is because d-wave superconductors with the specific crystalline orientations chosen in the experiment exhibit a "phase inversion" in the superconducting current that runs around the ring covering three orientation changes. Theory predicts that to compensate, such a phase inversion produces an extra current and an associated magnetic field equivalent to a half-flux quantum. The rings with no change of orientation, or with two changes, have no such inversion, and therefore show no spontaneous magnetization. Such phase inversions are now impossible in superconductors having standard s-wave pairing. **EN**

VIDEO NEWS

continued from page 6

software to be placed in a special fund to reimburse copyright owners. Neither the one-copy nor the royalty provision is expected to be incorporated in the DVD legislation. Whether the slow progress of anti-copy legislation will hold up the release of movies on DVD still remains to be seen.

"Living-room" PC/TV

Gateway 2000, the direct-sale personal-computer manufacturer, thinks that it's time for the family computer to come out of the den and into the living room, swallowing up the family TV and stereo as it moves. Gateway has developed the "Destination" system to let the entire family gather around the computer in the living room for a game of Mortal Kombat, a CD-ROM visit to a museum, a trip on the Internet—or, perhaps, just "Sesame Street" on PBS.

The Destination system has a 31-inch Mitsubishi data-grade monitor, a computer with a 120-MHz Pentium processor, and other goodies including 6×CD-ROM, a fax modem, and the works. In addition, it has a TV card and circuits to double the apparent resolution of TV programs by non-interlaced line interpolation. It can be purchased with or without its own stereo sound system, including speakers. Finally, it features a wireless keyboard, an RF wireless remote control, and a wireless "FieldMouse," along with an on-screen program-guide grid system. All that for "under \$4000." In the future, Gateway plans to integrate the system with a Digital Satellite System (DSS) receiver and DVD player.

The use of PCs is "becoming more and more group-oriented," according to Gateway's research. "We found that PCs are inherently flawed from a usability standpoint when more than one person tries to use it. The screens are too small, the cables on the inputs are difficult to pass between users, and the furniture that generally surrounds a desk in a den doesn't lend itself to hours of comfort while in use. **EN**

Backing up is hard to do

SOME COMPANIES ARE TAKING THE WINDOWS 95 PHILOSOPHY TOO FAR. THERE SEEMS TO BE A MOVEMENT AFOOT TO "DUMB DOWN" THE CAPABILITIES OF SOFTWARE PACKAGES SPECIFICALLY BUILT FOR WINDOWS 95.

I've seen several examples of this recently, but the most troublesome is a tape backup program I bought to run another recent purchase, a SCSI-based Digital Audio Tape (DAT) unit (model C1533A) made by HP.

I'm very happy with the hardware. It is unbelievably fast compared with the Colorado QIC-80 system I'd been using for several years. The HP can store up to 8 GB of data, has built-in hardware compression, and from the SCSI point of view, was completely plug and play.

DAT drives are more expensive than QIC drives, but they're about ten times faster, and the media cost is much lower. For example, in single-unit quantities, a name-brand 90-meter DAT tape costs about \$10 and stores about 2GB. A name-brand 120-meter tape costs about \$20 and stores about 8 GB. (The 120M tapes use a higher recording density, if the DAT drive supports it.)

By contrast, a 250-MB DC-2120 (QIC) tape costs about \$12. Enough tapes to hold 2 GB cost nearly \$100; 8 GB would cost about \$400. And swapping out all those tapes would not be fun. In fact, tape swapping to accomplish a single backup was what drove me to a

higher performance system in the first place.

On the other hand, \$200 buys enough DAT tapes to implement a decent tape-rotation scheme, so that you can keep off-site archival copies in case of catastrophe. The tellers at my local bank all know me now because they see me so often as I drop off the latest backup in my safe-deposit box.

In addition, the DAT drive is so much faster, and the capacity so much higher, that I can perform

redundant backups and still have plenty of room for occasional system snapshots as the need arises. The bottom line is that for the first time in years, I've got a backup system that really makes me feel secure.

HW+, SW-

As much as I like the hardware, however, the software leaves something to be desired. Actually, the drive itself came with no software. When I managed the network at a former employer, I used a DOS-based version of a program called NovaBack. I never had any trouble with it, and at about \$100, the cost was right. So I ordered a copy of NovaBack to accompany the drive. (The backup program that comes with Windows 95 supports QIC but

LISTING 1—DAILY.BAT

```
@echo off
rem backup all local drives, no logging
rem 4dos required

rem Append to tape
rem Modified files only
rem Subdir logging
rem Don't update archive bit

set xxDate=%_dow, %_date
set xxStartTime=%_time
set xxLog=C:\nb95\BACKUP.LOG
set xxTargets=C: D: E: F:

cdd C:\nb95
start /w bkp )%xxLog {VDHY-*SMG1EI=("HP
[4])T"%xxDate}%xxTargets ("EXCLUDES.BUP")
echo Daily Backup %xxDate: Start=%xxStartTime,
Done=%_Time, Result=%? >>%xxLog
exit
```

not SCSI tape drives.)

NovaBack came with a diskette and a little card with four screen shots that documented portions of the user interface and provided no useful information. My prior experience with NovaBack led me to believe that there was a richness not covered by the card, so I ordered a manual for an additional \$20. The order card described the manual as "the Ultimate Backup & Restore Operators Manual," but it didn't quite live up to that description. Rather, it arrived with a more-detailed explanation of obvious features of the user interface.

I called the company and a very grumpy tech-support guy promised to fax me what I needed. Two days later, no fax. By now I was starting to get angry. Called again. Another promise made, another promise broken. Called again, finally reached someone who seemed both pleasant and competent, and within an hour the fax arrived.

Now there was an example of clear, expository technical writing! Actually, it was a warmed-over version of the "technical" documentation for a ver-

sion of the program that ran on a different platform. Nonetheless, it had enough detail that I was able to accomplish my goal.

All I wanted to do was automatically perform different types of backups with different sets of parameters (daily, weekly, monthly, ...). I knew the DOS version supported an extensive set of command-line parameters for specifying what to back up, what to skip, how to perform logging, and so on. I assumed that the Windows 95 version would support at least a similar set of parameters. And I didn't want to use the Windows 95 user interface to the backup program. The graphical front-end to NovaBack is not what I would call a study in usability or convenience.

Also, NovaBack comes with a scheduler, but it's weak compared to the one that comes with Microsoft's Plus pack for Windows 95, which I was already using for other purposes. Configuring an automatic backup under NovaBack thus entailed modifying parameters in two separate applications. I wanted a more uniform

approach, one that would allow me to tweak settings as various needs arose.

I ran a few tests and pretty much got things working the way I wanted using the Microsoft scheduler and the OS/2 version of the NovaBack command-line parameters, with a couple of exceptions. The backup program is supposed to return a DOS ERRORLEVEL code to specify the result of a backup, but the routine always returns a zero. And the logging function doesn't exactly work as advertised.

4DOS and logging

Part of what I wanted this new backup system to do was provide a quick go/no-go indication so that I could check the status of last night's backup each morning on arriving at the office. To accomplish that, I built a 4DOS batch file. In case you're not familiar with 4DOS, it is a COMMAND.COM replacement that allows you to run programs and batch files, and to perform general system maintenance chores.

4DOS has a much richer command language, both at the command line

NOW Find the Right Part for Your VCR!



with
the

ISCET VCR CROSS REFERENCE

NEW! The Fifth Edition is contained on a diskette for IBM PC AT/XT compatibles, DOS 2.1 or higher. The disk software allows technicians to search by manufacturer for model numbers and description of part numbers. A parts editing sequence gives an on-screen view of all substitutes for parts entered. With the diskette, the technician can update files by adding model and parts

The 119-page Fifth Edition of the VCR Cross Reference contains both model and part number cross references. Over 1300 new parts and 360 new models have been added.

VCR's are made in a few factories from which hundreds of different brand names and model numbers identify cosmetically-changed identical and near-identical manufactured units. Interchangeable parts are very common. An exact replacement part may be available only a few minutes away from you even though the original brand-name supplier is out of stock. Also, you may be able to cannibalize scrap units at no cost.

crosses of future models. The Fifth Edition can be printed on pages completely from the diskette.

The ISCET VCR Cross Reference, Fifth Edition, is on 8 1/2 x 11-in., pre-punched pages and sell for **\$38.00**. The 3 1/2 inch diskette sells for **\$69.95** and you can view listings from a monitor or printed page.

**Only \$38.00 for pages
\$69.95 diskette**

**Clagg Inc.
VCR CROSS REFERENCE OFFER
P.O. Box 4099
Farmingdale, New York 11735**

Name _____
Business _____
Address _____
City _____
State _____ Zip _____
Phone _____

Enclosed **\$38.00** for the ISCET VCR Cross Reference, Fifth Edition.

Enclosed **\$69.95** for the diskette containing the ISCET VCR Cross Reference, Ver. 6.0. Please specify:

5 1/4 Diskettes (2) 3 1/2 Diskette (1)

Include \$3.00 for shipping each Cross Reference (Pages or Diskette)

The total amount of my order is \$ _____

Check enclosed—do not send cash.

Visa MasterCard Exp. Date ___/___/___

Signature _____

New York State residents must add applicable local sales tax to total.

CB03

RESOURCES

4DOS

JP Software
P.O. Box 1470
East Arlington, MA 02174
(617) 646-3975.

*Microsoft Windows 95
Resource Kit (\$49.95) Microsoft Press*
Redmond, WA
ISBN: 1-55615-678-2

Windows 95 Secrets
Brian Livingston and Davis Straub
IDG Books
Foster City, CA
ISBN: 1-56884-453-0

NovaBack,
Novastor Corp.
80-B West Cochran Street
Simi Valley, CA 93065
(805) 579-6700

and in batch files, than plain old DOS. 4DOS has been around for years; in all the time I've been using it, I've run across only one program it was incompatible with, and that was a very specialized industrial-monitoring system. Versions 5.51 and later of 4DOS support long file names.

Microsoft's System Agent (the scheduler) launches a 4DOS shell at 1:30 am six days a week. The command line for the 4DOS shell includes a call to DAILY.BAT, shown in Listing 1.

DAILY uses several neat 4DOS features to provide my snapshot log. First it sets up local environment variables to store copies of the current day of the week (Mon, Tue, ...), date, time, log file, and backup targets.

DAILY then uses 4DOS's CDD command to change both drive and directory at once.

It then uses the Start command (available in both 4DOS and from the Windows 95 command line) to launch the backup program with the parameters specified by the environment variables.

The "/w" following Start means that the batch file must wait for the specified program to complete before going on to the next line. Without the "/w," the batch file would start the backup program and immediately perform the next line. In this case the start and end times are equal.

The next line simply appends a status line to the specified log file. The status line shows the date, start time,

stop time, and the ERRORLEVEL. Right now the latter is always zero, but maybe NovaStor will get its act together one of these days. I can still get a good indication of health by observing start and stop times. Any large divergence from one day to the next warrants further investigation.

Last, the Exit command terminates the 4DOS instance after DAILY completes.

Dumb and dumber

In sum, I'm very happy with the hardware, but less than impressed with the software. What really concerns me is what appears to be a growing tendency to provide dumber-down versions of software for the Windows 95 environment. Some vendors appear to be operating under the assumption that Windows 95 users have no use for command-line driven utilities, and so don't document advanced features, and perhaps even disable some capabilities. In the case discussed here, it's particularly ironic, since the graphical user interface provided to insulate us poor users from the command line is itself so poor.

Bookshelf

If you do want to dig beneath the surface of Windows 95, two indispensable resources are Microsoft's own *Windows 95 Resource Kit*, and *Windows 95 Secrets*, by Brian Livingston.

The resource kit contains more than 1300 pages of information on Windows 95 setup, customization, and configuration. If you're interested in Windows 95 networking, user and system configuration, user and system policies, file sharing, or custom installations, the Windows Resource Kit is must-have documentation.

If the Windows Resource Kit is oriented toward system administrators, Livingston's 900-page book is geared toward end users. Fortunately, the author realizes that few will have the patience to read every word, so he thankfully highlights many of the real nuggets with marginal icons.

Both books come with disks containing various documentation files and utility programs. The Windows Resource Kit comes with a hypertext

version of the book, a utility for changing screen resolution without rebooting, sample installation scripts, a registry backup tool, a command-line based shortcut maintenance utility, and more. *Secrets* comes with a CD full of shareware programs, of which a few seemed useful.

E-mail

Concerning Microsoft's dominance of desktop computing, Lauren Colby writes, "I run a law office. Law offices account for 90% of the market for word processing software. In a law office, the secretaries need two things: SPEED and RELIABILITY. We can't possibly use Windows in our office. Even though we're running 90 MHz Pentiums with 16 MB memory, Windows is just too slow and too unreliable."

Owen Rubin and I exchanged some heated email. Owen upbraided me for my attitude about Apple: "It is obvious you have a PC and hate the Mac so you proclaim the death of something you do not have. Perhaps you bought PC before Macs were affordable and are now stuck? Exactly like the Ford driver who trashes a BMW driver really because they don't own such a car. It's called envy, and it is showing badly." As I told Owen, I own both PC's and Macs. For me it's not a question of religion, but of business, and I support clients on both platforms. By the way, Owen and I did end up friends. I still think Windows 95 is a better Mac than Mac, and I'm sure he still thinks the opposite.

Concerning my February column, Ed Glembotski writes, "Again your column hit it right on the head. I am 75-year-old has-been, Ham (K6SAR), and retired electro-mechanical engineer who feels like I am left holding the bag every once in awhile. I enjoyed the Commodore 64 trip with a full bag of programs (including Geos), and when Jack T. dropped us midstream, I finally gave away that boat anchor. The same with the great Atari 1040st. Now I'm running Windows 95 with a home-assembled 486DX2-66, with 20 MB of RAM and a 1 GB hard disk. I do hope to hang in there for a while."

Let me know what you think: jkth@acm.org.

EN

The Four-Year Electronics Degree Program That Really Hits Home!

Bring The Technology Home With A Bachelor Of Electronics Engineering Degree. No Hassles. No High Cost!



Now's the time to prepare for a profitable career.

We've lowered the cost of higher education.

It's true! You can earn a four-year Bachelor of Electronics Engineering Technology degree today ... and prepare yourself for a high-paying electronics career ... without quitting your job or ever leaving your home. Because World College, an affiliate of the Cleveland Institute of Electronics, offers you the total flexibility of independent study programs proven effective for people like you who truly want to succeed! World College independent study lessons help you build valuable skills

**Mail/Fax Today
or Call
1-800-696-7532**

step-by-step, and expert instructors are personally available to you with a toll-free call. What a way to earn an education!

A world of opportunity.

Where is your career headed? With a four-year bachelor's degree from World College, you call the shots, choosing from incredible, high-paying opportunities in electronics, telecommunications, computer, electrical power, and many other growing fields.

World College gives you the skills, the knowledge, the power to take advantage of your best opportunity in electronics. And you can do it all at your own pace!

Without leaving home.


World College continually works to provide its students with the most advanced education tools. From the latest equipment and reference books to breakthrough computer-simulated experiments, students are exposed to the latest technological advancements.

All the equipment, parts, and software you need are included in your affordable tuition, including more than 300 hands-on lab experiments you can complete in your home.

Choose your own pace.

Earn your bachelor's degree on your time — and at your pace — because you pay tuition to World College only as you complete the upper-level semesters close to graduation. The faster you make it through, the less you pay. So you have an incentive to make your future happen quickly — yet the freedom to choose your own pace!

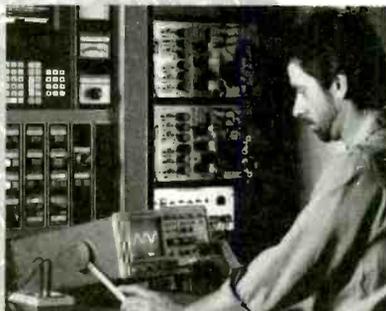Send today for your FREE course catalog — and give yourself that future you've always wanted — with an electronics degree education from World College.



Take charge of your future in electronics.

Four Powerful Reasons To Connect With World College Today:

1. Earn your four-year degree!
2. Self-paced training!
3. Independent study in your home!
4. Expert instruction!

Give Me The Power!

Send me a FREE World College course catalog today!



(Please Print Neatly)

Name _____

Address _____

City _____

State, Zip _____

Phone () _____

Age _____

**For faster service, call
1-800-696-7532,
or call
1-804-464-4600.**

**Or fax this coupon to
1-804-464-3687.**



Lake Shores Plaza
5193 Drive, Suite 113
Virginia Beach, VA 23455-2500



Affiliated with
Cleveland Institute of Electronics

WAE32

FUZZY LOGIC

continued from page 30

fuzzy variable "tall" can be defined for a range of values. Traditional Boolean variables assume only true or false values, so a person can be either tall, or not tall, depending on how you define what tall is.

In fuzzy logic, the person can be a "somewhat tall", or some percentage of what you define as tall. This percentage of tall is often referred to as the *fuzzy membership set*. Unlike Boolean logic, fuzzy logic provides a way to describe partial membership. Figure 2 shows how the degree of membership in the fuzzy set "tall" might be defined as a function of height. A person who is three feet tall has zero membership in the set. Conversely, someone who is seven feet tall has a membership of one. Well, the difference between Boolean set theory comes in when a person is five feet, three inches—then they are described as being a 0.25 percent member of the set tall

Groups of sets are defined in fuzzy controllers. Usually they overlap, and are odd in value. This is because better performance can be achieved when doing so. When grouped together, these sets form what is

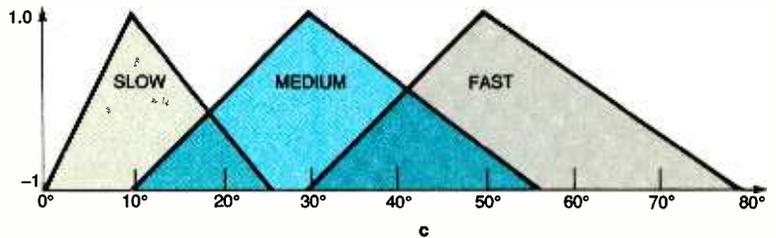
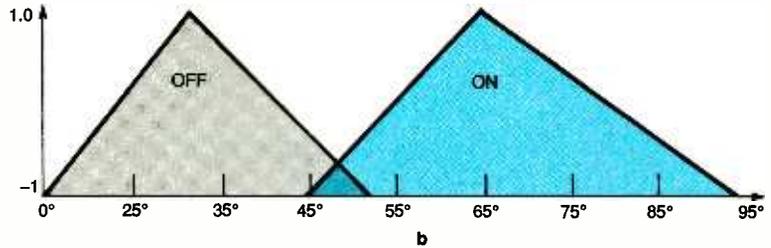
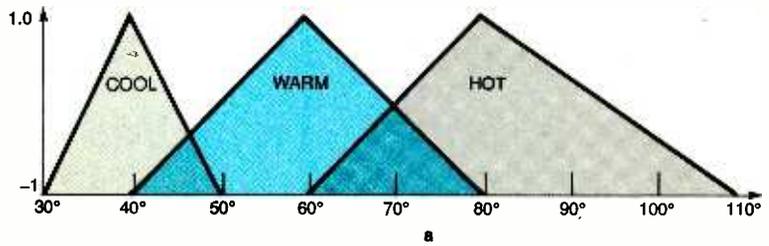


FIG. 5—INPUT AND OUTPUT MEMBERSHIP SETS for room temperature (a), thermostat state (b), and fan speed (c).

referred to as the *total membership set*, or just the membership set. The controller has one or more variables which are applied to the membership set, and an output is chosen based on the rules. Fuzzy rules are a

series of "if-then" rules that are used to produce an output. Figure 3 shows what a typical membership set of a fuzzy controller might look like.

As previously mentioned, a fuzzy variable represents a relationship to a given set. For instance, a variable "height" might take on several values relating to the height set. Potential values are *short*, *medium*, and *tall*. If-then rules perform the processing of the variables and their associated sets. Now assume that some action is taken based on the value of the variable "height." For example, consider another variable, "amount-of-fabric." A hypothetical rule might be: If "height" is *tall* then "amount of fabric" is *large*. As you can see, the new variable "amount of fabric" has a set of values associated with it.

In summary, a rule performs some action based on the value of some other variables. The terminology usually used to describe components of the if-

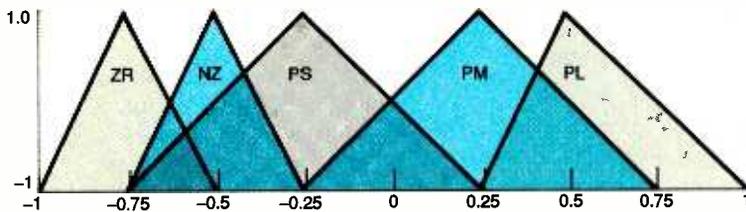


FIG. 3—A TYPICAL MEMBERSHIP SET might be represented as shown here.

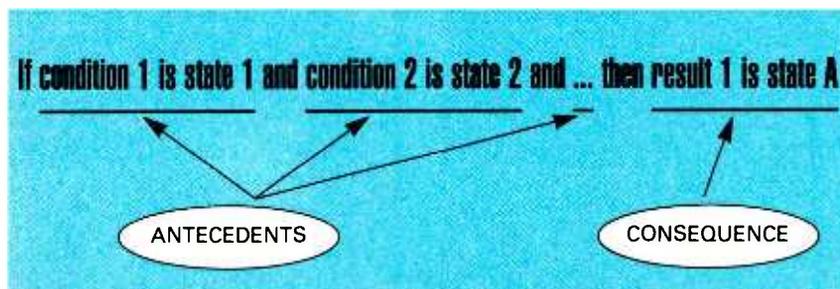


FIG. 4—THE ANTECEDENT AND CONSEQUENCE portions of a rule.

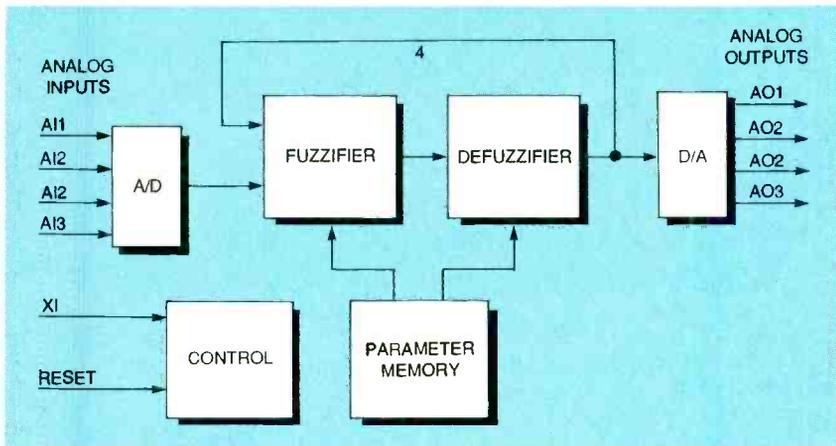


FIG. 6—BLOCK DIAGRAM OF ADAPTIVE LOGIC'S NLX220 fuzzy-logic controller.

then statement is *antecedent* and *consequence*. The antecedent is the portion of the statement that precedes the "then," and the consequence is the portion that follows. Thus, "height is tall" is the antecedent portion of the statement, and "then amount-of-fabric is large" is consequence. Figure 4 shows the antecedent and consequence portions of a typical if-then statement.

Assume that you want to implement a fuzzy-logic controller to regulate a room's temperature. You would begin by defining the variables. The thermostat controller has two inputs and a single output. The first input is called "room-

temp." and it represents the room's temperature. The second input variable is called "fan-speed," and it controls the fan motor that blows air over the heating element. There is a single output variable for this example called "thermostat," which controls the fan.

Your next step would be to define the fuzzy values for each of the input and output variables. "Room-temp" might have several value options, such as *cool*, *warm*, and *hot*. Fan-speed is either *slow*, *medium*, or *fast*. And finally, "thermostat" is either *on* or *off*. Figure 5 shows the ranges for the input and output variables. Once the variables, and their values are defined,

you are ready to describe the rules that process the input.

As previously mentioned, rules are a series of "if-then" statements. It is important to define enough rules to adequately define the behavior of the system over its operating region or *control surface*. In our example, our rules may look something like:

- *if room-temp cool and thermostat on, then fan-speed slow*
- *if room-temp cool and thermostat on, then fan-speed medium*
- *if room-temp warm and thermostat off, then fan-speed slow*
- *if room-temp warm and thermostat on, then fan-speed medium*
- *if room-temp hot and thermostat off, then fan-speed slow*

By examining the rules, you can determine exactly how the system will behave for a particular input. The specific ranges of the values are up to the user to define. Thus, *cool* might be defined as a number between 40 and 75 degrees, *warm* between 60 and 95, and *hot* between 90 and 110. It is up to the user to define the range for the fuzzy set, and make sure the rules describe all values within this range.

Based on our model, if the room temperature is 70 degrees and the thermostat is on, then conditions are set for the second-to-last rule, and the fan speed will be set to medium. But what if conditions are met for more than one rule? Then all the rules that have their conditions met are summed together to produce a weighted average for the fan-speed output variable. Remember that on and off for the variable thermostat consists of a range that is defined, say between zero and one. The summation process ensures that result is in the ball park that is needed. After the result is computed, it is then run through the defuzzifier to produce a usable output.

Hardware solutions

Hardware and software solutions are available to help developers quickly create new products based on fuzzy logic.



FIG. 7—THE DEVELOPMENT SYSTEM for the NLX220

Fuzzy logic controllers can be implemented with general-purpose microprocessors. This hardware approach is very popular among developers because fuzzy logic is not memory- or computation- demanding. Typical code for these controllers requires less than 1,000 bytes of memory storage. Also for the majority of applications, an eight-bit microprocessor can handle the necessary computations. The microprocessor approach is used after a model is verified by software simulation. The resulting code composing the fuzzy controller is burned into read-only memory (ROM). Microprocessor-based fuzzy-logic controllers work for a wide range of systems. However, there are situations when another hardware solution is required.

Dedicated fuzzy integrated circuits are used in situations where either speed or a large rule set is required. Fuzzy chips are 10 to 100 times faster than general-purpose microprocessors that run fuzzy-logic code in software. Several manufacturers make hardware to handle these demands.

Togai Infraclogic, Inc. for example, makes a line of dedicated fuzzy controllers that the company claims are 10 times faster than an Intel 486 configured as a fuzzy controller. Its RISC (reduced instruction-set computer) FC110 IC handles up to 800 rules. Similarly, it processes these rules at a rate in excess of over 200,000 rules per second.

Siemens dedicated fuzzy controller is the 81C99, which is a coprocessor that interfaces to most microprocessors. The 81C99 acts as an accelerator for a general purpose microprocessor by off-loading resource-intensive calculations of complex fuzzy-logic systems from the microprocessor. This device is also RISC-based. Additionally, it can support as many rules as external memory allows, and it can process these rules at a rate of 7.9 million rules per second!

Adaptive Logic (formerly American Nerualogix, Inc.) also makes a dedicated fuzzy logic



FIG. 8—SATURN'S FUZZY-LOGIC transmission controller is based on the 68HC11 microcontroller.

controller, the inexpensive, high-performance NLX220. A block diagram of the controller is shown in Fig. 6. It handles up to four analog inputs and outputs. It accomplishes real-time I/O through on-chip analog-to-digital (A/D) and digital-to-analog (D/A) converters. Furthermore it supports 111 rules, and can process them at a speed in excess of 800,000 rules per second. The NLX220 also has software development support through the NeuralLogic Insight development system (Fig. 7), which enables users to simulate and configure the NLX220 quickly to produce products. Applications for this device include temperature, motion, power, and pressure control.

Software-development tools for fuzzy logic are not essential, but they are extremely helpful for two reasons: First, the simulations offer immediate feedback on whether or not the model is valid. Second, the resulting output can be used to feed hardware implementation models.

Several software packages exist which aid in the development of fuzzy systems. These packages have a wide range of functionality. All of the packages allow models to be simulated. Some restrict the number of inputs and outputs available, while others provide users with added functionality such as graphical user interfaces, plotting ability, and even code generation for hardware. Some are packages for development, and others are for educational purposes. Most of the full-blown development tools are available at

prices ranging from several hundred to several thousands of dollars. FIDE, Cubicalc, and TeachFuzz are representative of packages that are in the high, medium, and low price range.

FIDE stands for Fuzzy Inference Development Environment. It is a tool developed by Apronix, and also sold through Motorola. It is at the high range of the price spectrum costing between \$1995 and \$3495, depending on the configuration. FIDE is a graphical development tool for Motorola's microcontroller line. It features a graphical input via matrix rule grid (similar to a spreadsheet). It simulates fuzzy systems as well as producing assembly output for the 6805, 6811, 6816, and 68000 microprocessors. It also generates C code which allows the implementation of portable embedded controllers.

CubicCalc is a development tool by HyperLogic. This tool is typical of the medium priced development systems. It costs in the range of \$495 to \$795, depending on the options. It has a graphical front-end for simulating and plotting fuzzy systems. It also supports tracing for debugging. CubicCalc also produces C code output like the high-end solution. Similarly HyperLogic also produces a low-end version (\$175) called CubiQuick. It is meant as an educational tool, and is a limited version of CubicCalc.

TeachFuzz is an educational tool for exploring fuzzy-logic concepts. This product is at the low-end of the fuzzy logic product spectrum. Priced at \$24.95, TeachFuzz is an application

that allows users to simulate a two-input, one-output fuzzy logic controller to teach how a fuzzy controller is built. This product runs as a shell, and requires text files as its inputs and outputs. This product runs both on the Macintosh and the PC. This is a good tool for those interested in experimenting with fuzzy-logic fundamentals.

Fuzzy-logic design methodology

Designing a fuzzy-logic controller is a four-step process. It consists of knowledge extraction, model construction, model testing and model tweaking. Moreover, the successful implementation of a fuzzy controller depends on common sense and intuition.

Knowledge extraction is the process of learning how a system works or how it should work. This is usually accomplished in one of two ways. The first is to analyze or observe a system in operation. And the second is to interrogate an expert.

The observation/analyzing process consists of watching the system in operation, looking for relationships between components of the model. For instance, referring back to the heating system, notice that a relationship exists between the setting of the thermostat, the blower motor, and the room temperature. System relationships are isolated, and defined as variables. Thus the relationship between the thermostat, the motor's speed and the room temperature is described by making each a variable. Once the variables are defined, the exact nature of their relationship must be determined. This is done by looking for cause and effect relationships between the variables. For instance, is the motor's speed affected by the thermostat, or vice versa?

An expert is someone who knows the system very well. He might not know the system variables, or their direct relationships, but what he does know is how the system behaves overall. When dealing with a

system expert, it is up to the designers to quantify the expert's knowledge of variables and relationships. This process begins by interviewing the expert, starting with the general and moving to the specific. A log of questions should be asked. The goal is to quantify the expert's knowledge about the system into input and output variables, and how they relate to each other. First extract the variables, and then zero in on how they relate. This process is time-consuming, and there is no cookbook method for gathering this information.

Once the system behavior is understood, the system must be

be:

If temperature is hot and pressure is high, then valve is open.

This example has two antecedents and one consequence. However, a rule's antecedents and consequences are not limited. Any rule may have one or more antecedents and consequences. Moreover, the behavior of a particular system is made up of a series of rule statements. The number of total rules is dependent on the complexity of the system. If the system is simple, it may be defined by only a few rules. On the other hand, if the system is complex, it may take several hundred rules to describe.

After the model is documented it is ready to be built. Building the model consists of translating the variables, rules, and their corresponding sets to an implementation tool. This tool can be one of the hardware or software development tools previously mentioned.

Assume that the implementation tool is software. Then the variables, sets, and rules must be put into a format that the tool understands. Input for the tool occurs through files, or through a user interface. For instance the TeachFuzz application gets its input from files. The files are made up of definitions of sets, rules, input/output variables, and input data. Once the files are formatted for the tool, the model is ready for testing through simulation.

The software tool tests the model through simulation. During the test, all types of inputs are run through the model to see if it behaves as expected. If it does, the model is considered good, or valid. Otherwise, the model needs tweaking.

Tweaking consists of iterating the previous steps until the model tests out as valid. Invalid models occur for several reasons. The most common is the set of rules for the system are incomplete. Typically, this problem occurs as a result of insufficient rules to handle all input data for a specific region.

The next cause of invalid models is undefined sets, which

FUZZY RESOURCES

Adaptive Logic
800 Charcot Ave., Suite 112
San Jose, CA 95135

Apronix
2150 North First Street, Suite 300
San Jose, CA 95131

HyperLogic Corp.
1855 East Valley Parkway, Suite 210
Escondido, CA 92027

Siemens
10950 N. Tantau Ave.
Cupertino, CA 95014

Togai Infraclogic, Inc.
5 Vanderbilt
Irvine, CA 92718

documented. The documentation's notation can be as formal as mathematical formulas, or as informal as English. Since fuzzy logic is linguistically rich, it makes sense to use English to describe a system's behavior. The input and output variables are words that accurately describe the set they represent such as tall, distance, and temperature. Additionally, succinct words are used to describe the multiple values that a variable has. For instance variable distance may be close, intermediate, and far. The next step in documenting is recording its behavior.

The behavior of the system is described in a fuzzy-logic control system in terms of its set of rules. Rules are a set of "if-then" statements. A typical rule might

occurs when a set for an input or output variable is missing altogether. Correcting this problem when the set is completely missing is straightforward. This is accomplished by figuring out the domain for a given variable, formatting it in terms of the tool notation, and including its definition so that the tool can find it.

The third reason for an invalid model is incompletely defined sets. This is a variation of the previous problem, except in this case the set is defined, but it is not adequately defined for the region.

Usually this problem occurs when there are not enough partitions of a variable's set. In the thermostat model the variable thermostat is has possible values of either on or off. What if the thermostat variable requires more states? Then additional subsets must be defined to accommodate this situation. For example, extra states like "nearly on" and "almost off" or "just turned off" may be added to fix this problem.

An extra word is in order concerning building the model. Before going through the effort of converting the model to the implementation tool's format, make sure the model makes sense. Walk through the model with test data on paper. Give it some random values and compute the output. Then check it to see if it falls within the defined region. For fuzzy logic this is easy, because of its linguistic nature.

Applications

Fuzzy-logic applications are sweeping the globe. Japan presently is producing more products than all other countries combined. However, this situation is changing rapidly as Asia, Europe, and even the U.S. discover that fuzzy-logic methods can reduce the time required to produce a product.

In Asia, fuzzy logic provides additional features for appliances while improving efficiency and simplifying the user interface. Matsushita produces a washing machine that effectively has 600 settings! The ma-

chine uses sensors as feedback elements to gauge the washer system. One set of sensors measures how well the soap dissolves in the water. Another set of sensors captures the amount of dirt in the water. A third set of sensors keeps track of the load of the washer. Thus if the water is fairly clean, the fuzzy logic controller specifies a short wash cycle. On the other hand, if the water is dirty a fairly long wash cycle is set. Similarly, if a few clothes are in the machine, the washer uses less water. Conversely a full load of clothes causes the washer to use the most water. Efficiency is always maximized.

European countries are also embracing fuzzy logic controllers in their products. Klockener-Moeller GmbH in Germany is using fuzzy logic in its industrial programmable logic controllers (PLC). One application of its fuzzy PLC is wind power. The PLC controls the pitch in wind generators. The fuzzy PLC improves system efficiency under complex control situations. For example, when a rotor blade passes the tower, it crosses the wind shade created by the tower itself. The wind shade causes a dip in the energy output, and the PLC compensates for this dip.

Japan claims that most products it produces are fuzzy-based. For instance, several manufacturers make smart vacuum cleaners that operate by detecting differences in floor conditions, and adjust the brush height accordingly. Panasonic uses fuzzy logic technology to produce jitter-free pictures in its line of video camcorders.

Cannon makes use of fuzzy logic to create an auto-focus feature for its cameras. One of Japan's most impressive achievements is the fuzzy-logic controlled transit system. All facets of the journey are controlled via this system. The ride is so smooth that many officials boast that this system provides a smoother ride and more accurate stops than human operators could hope to.

In the U.S., fuzzy logic prod-

ucts are beginning to emerge. Allen-Bradley produces a line of fuzzy PLCs. Eaton is using the technology to inspect soda cans for printing defects. Whirlpool is making use of fuzzy controllers in some of its refrigerator models.

Cars are a natural application of fuzzy logic. Saturn is an advocate of fuzzy-logic technology, using it in anti-lock brake systems and for transmission control. (See Fig 8.) For instance, Saturn's transmission controller is based on Motorola's 68HC11, and takes up only 500 bytes of code! Saturn's transmission controller works by using fuzzy logic to assist in braking on downhill grades. The controller accepts information about speed, throttle, position, brake-application intensity, and the amount of braking time. With this information, the controller determines the appropriate gear for downshifting as a car accelerates downhill. The resulting operation is smooth, and the average driver never notices the downshifting. However, as a result of the controller's action, less braking is required, resulting in longer brake life.

Fuzzy logic allows you to become a controller designer without the overhead of traditional techniques. You do not have to learn calculus to use fuzzy logic. This results in a faster learning curve than traditional techniques. It is a natural choice for designers due to its linguistic nature, as well as its ability to speed up the product development cycle.

Augmenting the development cycle decreases the time to market for a product. That is, the time it takes to put a product on the market is compressed. Furthermore, this compression is due to several factors. The first is a shorter learning curve. Secondly, designs are implemented quickly using superior tools. Thirdly, once implemented the design is quickly verified and modified if necessary. All of these factors translate to a robust technique which is hard to beat in the controller design arena. Ω

ATV TRANSMITTER

continued from page 32

connected to the collector of Q10 and suppresses harmonic frequencies. The RF output is a relatively pure signal between 900-940 MHz.

Video and audio modulation

To apply video modulation to this RF carrier, the supply voltage for Q10 is taken from the emitter of video modulator Q7. Transistors Q5, Q6, and Q7 are connected as a feedback amplifier with a gain of about 5 to 10. Video input to the transmitter is amplified in this circuit and also inverted in polarity so that sync and black levels are positive going. The video signal at the emitter of Q7 is superimposed on the supply voltage to Q10. In turn, Q10 amplitude modulates the RF output from Q4. Potentiometer R14 sets the carrier level of the RF output for symmetrical modulation and

potentiometer R18 sets the modulation level for maximum without distortion or clipping.

The Mini 900 also provides a 4.5-MHz audio subcarrier. Incoming audio is fed to gain control R29. Audio from R29 then is fed through C27 to the base of Q8. Audio from Q8 is fed to varactor diode D2 via C25 and R24. Diode D2 is part of the frequency-determining network of 4.5-MHz subcarrier oscillator Q9. Circuit elements D2, C24, C21, C22, and L14 make up the 4.5-MHz tuned circuit. Audio voltage on D2 changes its capacitance, causing frequency modulation to occur. Trimmer capacitor C24 sets the 4.5 MHz sound subcarrier frequency.

The subcarrier output from Q9 is fed into the video modulator via C30, where it is mixed with the video. A jumper in series with the supply to 6.2-volt Zener diode D3 and R21 permits disabling Q8 and Q9 if no sound is necessary. An optional external switch or removed

jumper will power down the sound circuit for longer battery life. Diode D3 and C29 supply a clean, regulated 6.2 volts bias to Q8 and Q9. Resistor R21 and C28 decouple the sound circuit from the DC supply. For PAL systems the number of turns on L14 is reduced to allow 5.5-MHz operation.

Diode D1 protects the Mini 900 circuitry against accidental reverse polarity from the external power supply and C39 provides supply line bypassing.

The DC voltage supply to the transmitter should be very clean and stable. Any noise or ripple in the supply voltage can modulate the RF carrier and cause severe distortion in the received video. Less than 50 millivolts of ripple and noise is permissible, less being more desirable. Dedicated battery packs offer the best option for a noise-free voltage source, otherwise voltage regulation and additional filtering should be considered.

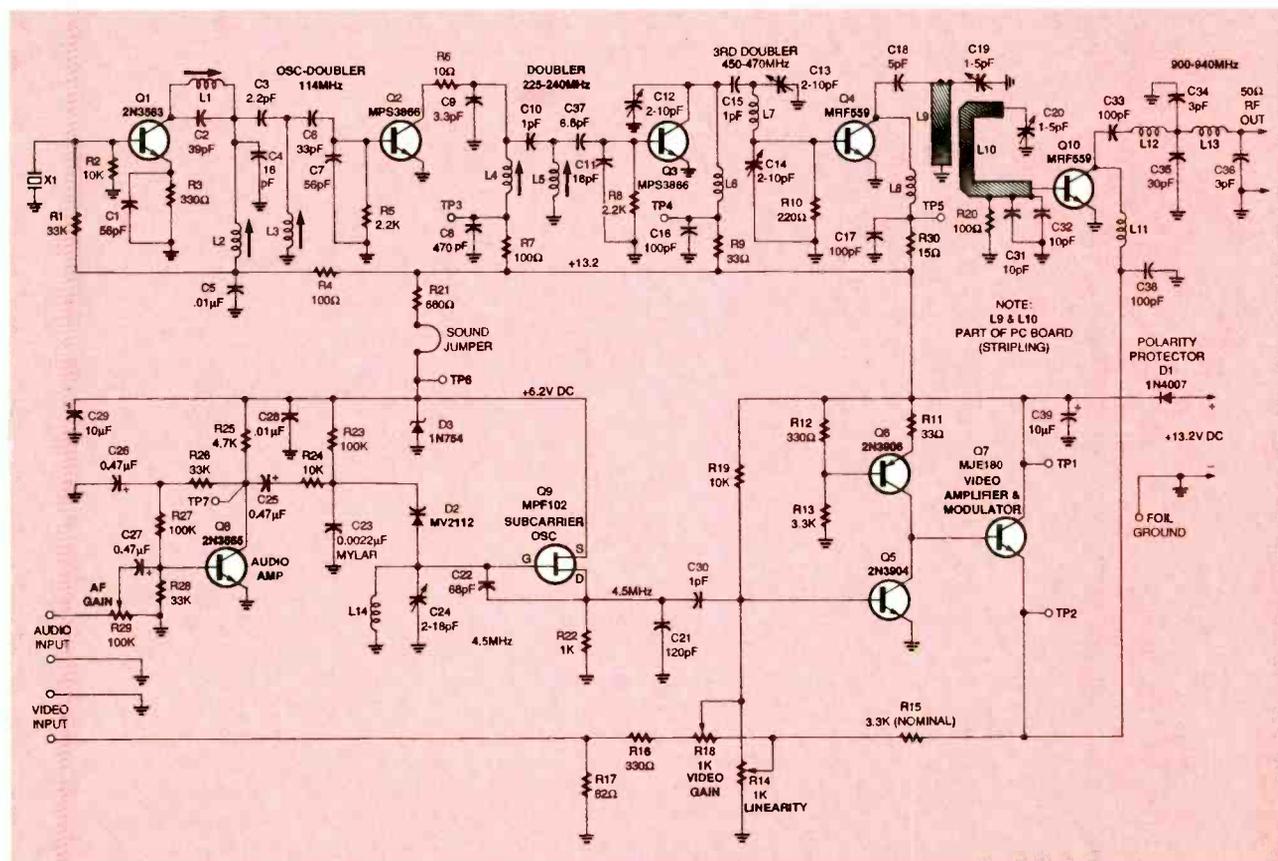


FIG. 2—SCHEMATIC DIAGRAM for the Mini 900 ATV transmitter. All the parts in the diagram fit on a 2¼ × 1¼-inch two-sided foil printed circuit board. An understanding of the circuit diagram will enable builders to easily perform alignment and troubleshooting procedures.



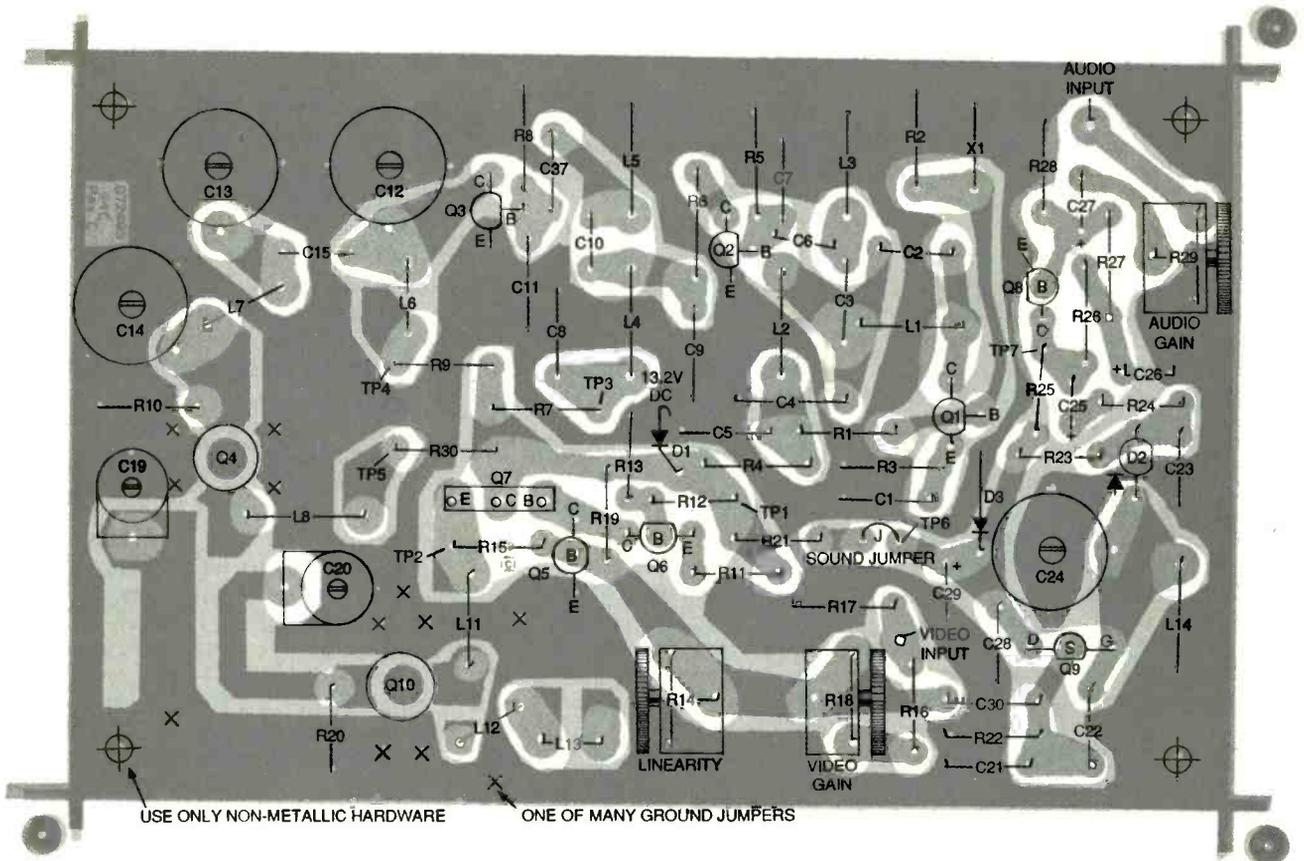


FIG. 3—COMPONENT SIDE PARTS PLACEMENT diagram for the Mini 900 ATV transmitter PC board. Solder all component ground leads to the top and bottom foil surfaces. Use #22 bare and tinned wire to jumper together the ground planes of the top and bottom foils.

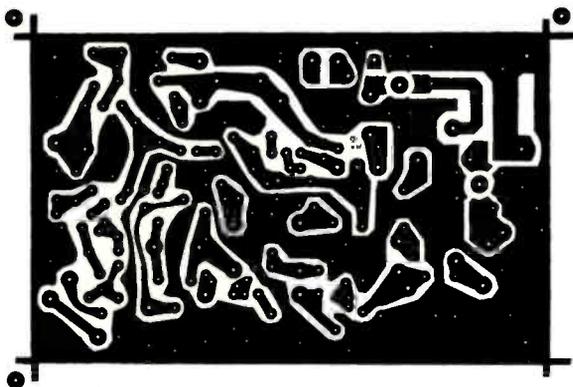

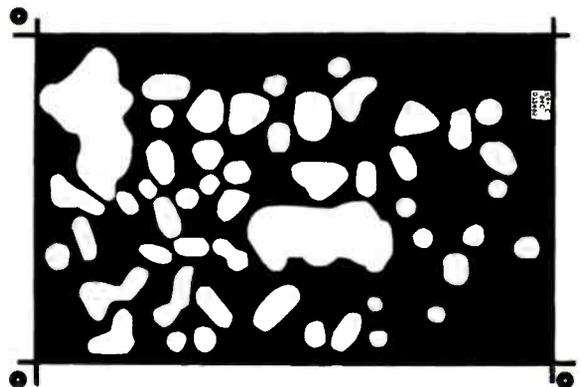TOP VIEW (component side) of PC board shown same size.



BOTTOM VIEW (solder side) of PC board shown same size.

Putting it together

Before beginning construction, familiarize yourself with the circuit diagram in Fig. 2 and the PC board layout. Refer to Figs. 3 and 4. To get an idea of the compactness of the printed-circuit board, glance at the same-size foil diagrams in this article. Use good lighting.

It is helpful to insert first a few large parts such as trimmer capacitors and potentiometers to

serve as landmarks. Constantly refer to the parts placement diagrams in Fig. 3 and 4 to avoid mistakes. The grounded leads of all trimmer capacitors and grounded leads of all resistors must be soldered on both sides of PC board because the board holes are not plated through. This is essential for good RF grounding. Except where access may be difficult later in construction, *do not* solder any

connections until as many components as possible are inserted. All coils are installed after the other components are inserted and soldered.

All parts are mounted tight and close to board—there can be no exceptions. Zero lead length is essential in high-frequency RF circuits. Remember that the Mini 900 operates at UHF frequencies and lead lengths are critical—they intro-

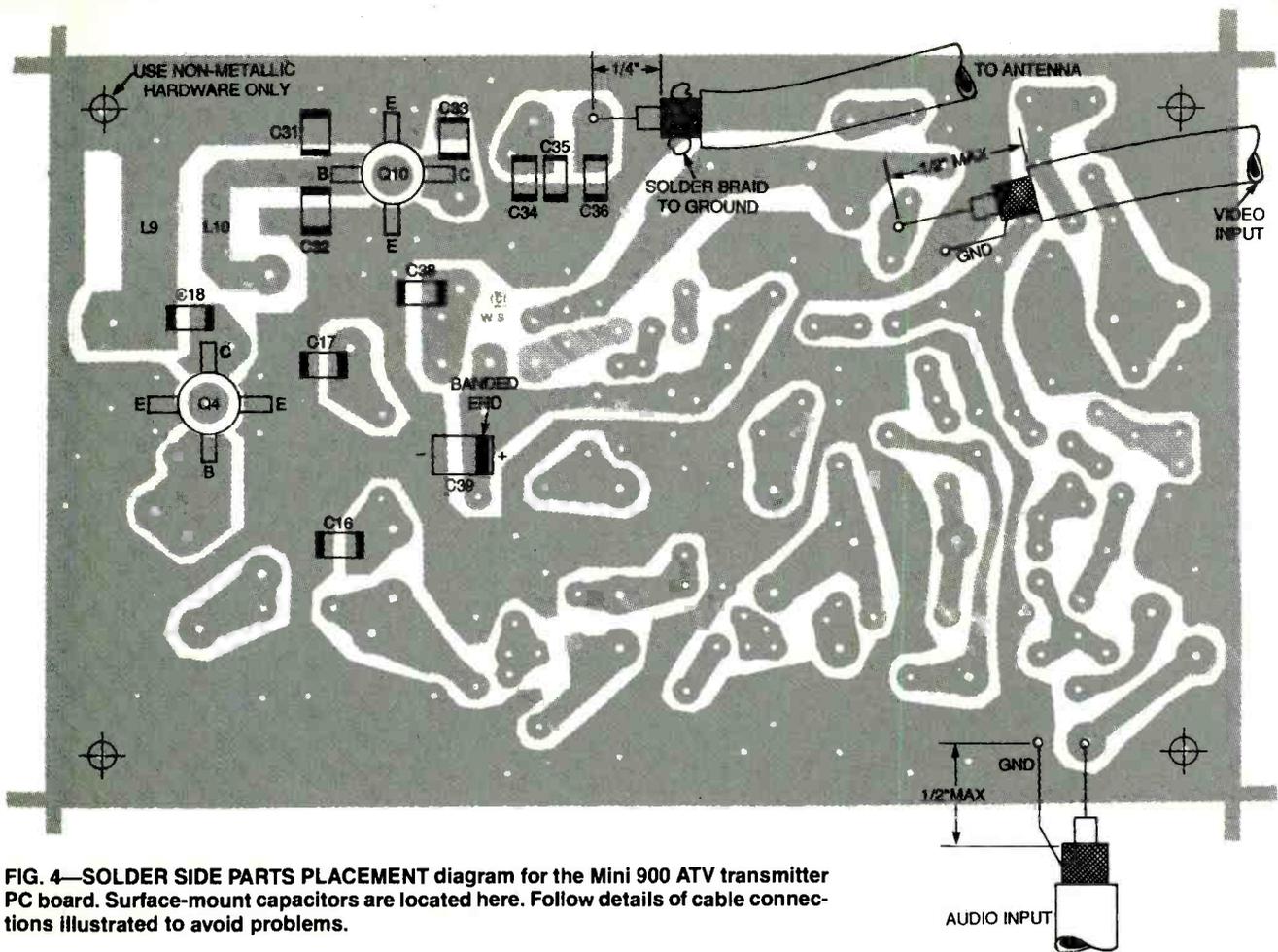


FIG. 4—SOLDER SIDE PARTS PLACEMENT diagram for the Mini 900 ATV transmitter PC board. Surface-mount capacitors are located here. Follow details of cable connections illustrated to avoid problems.

duce unwanted inductance and stray capacitance.

Install all fixed resistors and solder in place (see Fig. 3). The next step is to install and solder trimmer side terminals to top side of the PC board. Be careful not to melt the plastic. Do not solder the bottom at this time. Install all ground-plane jumpers that connect top and bottom ground planes (See Fig. 3).

Install capacitors with wire leads. Pre-formed leads should be straightened with pliers so as to fit as close to board as possible. Watch polarity of all electrolytic capacitors so as not to accidentally reverse polarity. Do not install surface-mount capacitors until a later step. Install all transistors, except Q4 and Q10. Check for correct orientation of transistor leads. All transistors should be 1/8 inch from surface of board. Solder the emitter leads of Q2 and Q3 to the top of the PC board where they pass through the ground foil.

Install D1, D2 and D3, checking the polarity (marking band) before and after soldering. Solder the ground lead of D3 to the top side of the PC board where it contacts it. Note that D1 (1N4007) has only one lead inserted in board (banded end). The other end is formed into a hook and is used as a terminal for attaching the DC supply positive lead wire. Diode D2 looks like a transistor with only two leads. Refer to Fig. 3 before installing D3.

Using scissors, trim the crystal leads to $\frac{3}{16}$ inch and install. Do not use diagonal cutters as the mechanical shock produced during cutting can damage the crystal. Solder a short wire to the top of the crystal and run this lead to ground.

Carefully fabricate all coils and install them in the PC board. The winding of the coils are detailed in a sidebar entitled "Coil Winding Data." Be sure that no turns short together on L6, L7, L8, L11. The bottom

turn of L1 connects to the collector of Q1: L2 bottom turn, to the junction of C3 and C4; and L3 bottom turn, to the junction of C3 and C6. Use an 8-32 screw to hold L1, L2, L3, L4 and L5 during installation. After installing coils, remove screw and insert tuning slugs fully into coils. Note that coils L11, L12, L13 are fabricated on a 6-32 screw while all others except toroid L14 use an 8-32 screw as a winding form. Use a small drop of paraffin wax or candle wax to retain tuning slugs in coils.

Install C16, C17, C33, C38 (100-pF surface-mount capacitors); C18 (5-pF surface-mount capacitor); then C31 and C32 (10-pF surface-mount capacitors); C34, C35 and C36 (3-pF surface-mount capacitors) and C39 on the underside of the PC board. Refer to Fig. 4 for capacitor location and sidebar entitled "How to Install Surface-mount Capacitors" for soldering details. Caution: Check the polarity on C39 as it is soldered in

PARTS LIST

All fixed resistors are 1/8-watt, 5%, unless otherwise specified.

R1, R26, R28—33,000 ohms
R2, R19, R24—10,000 ohms
R3, R12, R16—330 ohms
R4, R7, R20—100 ohms
R5, R8—2,200 ohms
R6—10 ohms
R9, R11—33 ohms
R10—220 ohms
R13—3,300 ohms
R14, R18—1,000 ohms potentiometer, thumbwheel type, PC mount
R15—3,300 ohms (see Note 1)
R17—82 ohms
R21—680 ohms
R22—1000 ohms
R23, R27—100,000 ohms
R25—4,700 ohms
R29—100,000 ohms potentiometer, thumbwheel type, PC mount
R30—15 ohms

Capacitors (See Note 3)

C1, C7—56 pF, NPO
C2—39 pF, NPO
C3—2.2 pF, NPO
C4, C11—18 pF, NPO
C5, C28—0.01 μ F disk, GMV
C6—33 pF, NPO
C8—470 pF, GMV
C9—3.3 pF, NPO
C12, C13, C14—2-10 pF trimmer
C10, C15—1 pF, NPO
C16, C17, C33, C38—100 pF, surface-mount type
C18—4.7 or 5.0 pF, NPO, surface-mount (use either value)
C19, C20—1.5-5 pF trimmer
C21—120 pF, NPO or SM
C22—68 pF, NPO
C23—0.0022 μ F, 50-volt, Mylar
C24—2-18 pF trimmer
C25, C26, C27—0.47 or 1.0- μ F, 35-volt tantalum electrolytic (use either value)
C29—10 μ F, 16-volt electrolytic
C30—1 pF or 2.2 pF, NPO (see Note 2)
C31, C32—10 pF, NPO surface-mount
C34, C35—3 pF, NPO
C36—30 pF, NPO
C37—6.8 pF, NPO
C39—10 μ F, 16-volt, surface-mount

Inductors

See Coil Wind Chart for details of coil construction.

L1, L2, L3, L4, L5, L14—No. 22 enameled solid-copper wire
L6, L7, L8, L11, L12, L13—No. 22 bare tinned solid-copper wire

5—Ferrite slugs, blue, 8-32

1—Toroid core for L14

Semiconductors

D1—1N4007 rectifier
D2—MV2112 varactor
D3—1N754 Zener diode, 6.2-volts
Q1—2N3563 transistor
Q2, Q3—MPS3866 transistor
Q4, Q10—MRF559 transistor
Q5—2N3904 transistor
Q6—2N3906 transistor
Q7—MJE180 video amplifier modulator
Q8—2N3565 transistor
Q9—MPF102 JFET

Miscellaneous

X1—56.890625-MHz crystal (910.25 MHz). Note: Alternate crystal frequencies are 57.640625 MHz (922.25 MHz) and 57.703125 MHz (923.25 MHz).

1—printed-circuit, 2-sided board, etched and drilled.

1—8-32 screw for coil winding

1—6-32 brass screw for coil winding and tuning aid

Note 1: R15 resistance range is 2,200 to 4,700 ohms depending on the video gain desired. Default value is 3,300 ohms. Estimated video gain vs. R15 resistance values are: $5 \times = 2,200$ ohms, $7 \times = 3,300$ ohms, and $10 \times = 4,700$ ohms.

Note 2: Use either 1 pF or 2.2 pF for C30. Value selected determines sound subcarrier level.

Note 3: All capacitors less than 120 pF are NPO types with ceramic bodies. All capacitors with a specified working voltage are electrolytic types. All 0.01 μ F and 470 pF capacitors are GMV ceramic disk types.

A complete parts kit for the Mini 900 ATV transmitter, consisting of the PC board and all parts that mount on it, is available from: North Country Radio, PO Box 53, Wykagyl Station, New Rochelle, NY 10804. Kit is furnished with crystal for 910.25 MHz as standard, or alternately 922.25 or 923.25 MHz if specified with order. Kit price: \$81.50 plus \$4.50 for postage and handling. New York residents must add 8.25% sales tax. A catalog packed with cameras and other amateur TV kits and electronic projects is available. Please send SASE (75 cents) plus \$1.00 to cover handling (refundable with order).

ponent leads that pass through top ground and bottom ground planes as possible. Disc capacitors may be somewhat difficult, but solder as many as possible. This very important step provides good RF grounding. Be careful not to melt plastic trimmer capacitors and potentiometers.

Now install the MRF559 transistors, Q4 and Q10 (see Fig. 4). The long lead of the MRF559 is the collector. Trim leads to length and install Q4 and Q10 with thicker side in holes provided in the PC board. The manufacturer's logo on the transistors will be visible from the bottom of PC board. The plane of leads should be flush with bottom of PC board.

Carefully inspect all work completed thus far. Look for solder bridges, poor or cold solder joints, missing parts, incorrect parts placement, etc. You are ready to electrically check out the board once the assembly is satisfactorily done and you check the accuracy of the placement of each part and solder joint.

Checkout and tune-up

Do not proceed with this section until you have thoroughly checked out the construction as described in the last step of the instructions. You should have access to the suggested basic test equipment if you are to obtain optimum performance. It is futile to try to tune for best picture. It is, for example, possible to get a good picture and have only ten foot range of transmission. It is also possible to inadvertently overload the video monitor and get a lousy picture on it from a perfectly operating circuit board, and spend hours tracing nonexistent problems. Therefore use our procedure and experiment later when you are sure everything works properly.

The use of a metal standoff or other metallic material in the vicinity of L9 near the corner mounting hole in the PC board (See Figs. 3 and 4) can upset the stripline coupling network L9-L10. This will affect the setting of C19 and also may reduce the

place and afterwards: the banded side is positive (+).

Install sound jumper (J) near

D3 (see Fig. 3). Install all ground jumpers in the holes indicated in layout. Solder as many com-

attainable RF power output from the transmitter. For this reason, note the following precautions:

- Only use nylon or other non-metallic hardware in the corner hole next to coil L9.
- Keep the PC board at least ¼ inch from metallic or RF lossy materials.
- Keep any external wiring away from PC board especially near L9 and L10.


First verify that the DC voltages are correct and that the video modulator is working. Set the power supply to zero volts. Connect the negative lead of your power supply to the ground foil on the board. Next connect a lead from the positive terminal of the power supply through an ammeter (0-500 mA range) to the power input terminal which is the hooked end of diode D1. If the power supply has an ammeter, you can use it instead of an external ammeter. Now slowly raise the voltage to 10 volts. If more than about 100 mA is drawn, turn off the power supply and check your board for wiring errors, short circuits, solder bridges, etc. Power up again and if more than 100 mA is drawn, check to see if any part gets hot or smokes. If so, find the cause and repair assembly errors and/or damaged parts before proceeding.

Test points

Seven test points are shown on the schematic diagram in Fig. 2. These are intended for tune-up and diagnostic use on a finished, operating transmitter. Not all of the test points (listed below) are used in the tuneup procedure.

Test Point	Location	Volts DC
TP1	Collector, Q7	+13.2
-	Collector, Q1	+12.6
-	Collector, Q2	+13.2
TP6	Drain, Q9	+6.8
TP7	Collector, Q8	+3.5
-	Collector, Q4	>+2.0 to <+11.5*
TP2	Emitter, Q7	>+2.0 to <+11.5*

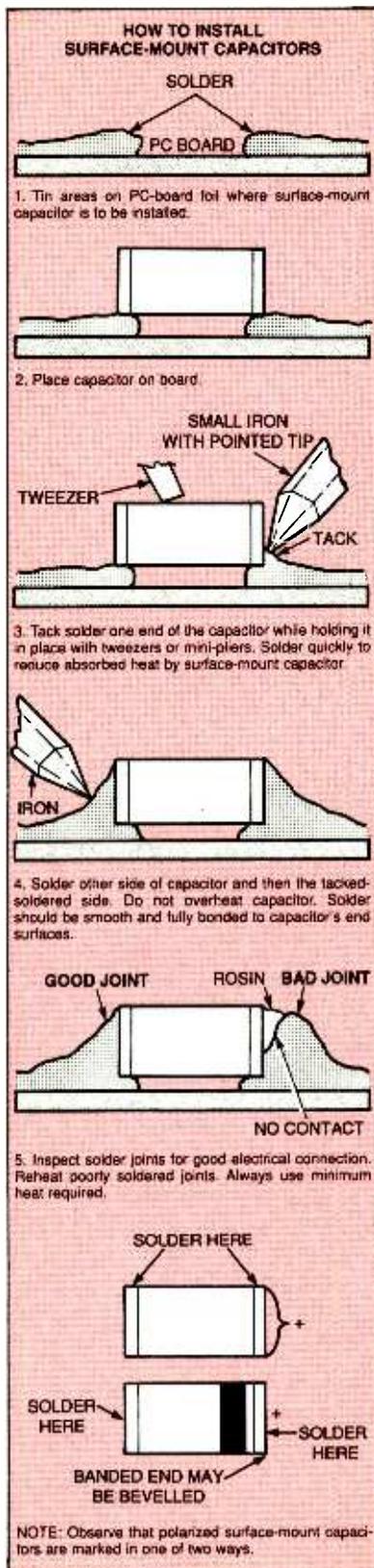*These voltages depend on the setting of R14 and R18. Verify this before proceeding further.



If everything is satisfactory at 10 volts, set the power supply voltage to 13.2 volts. Connect a voltmeter negative lead to the power supply negative terminal

and check for following voltages using the positive lead of the voltmeter:

Set potentiometer R14 so that voltage at emitter of Q7 (TP1) is 6.0-volt DC. Connect a frequency counter between TP2 and ground. You should see a stable reading between 4 to 5 MHz. Set C24 for a counter reading of 4.495 to 4.505 MHz. This sets the sound subcarrier frequency. If you cannot obtain this frequency, but obtain a stable reading that is either too low or too high, remove or add a turn, respectively, to toroidal coil L14. You must have a stable reading. Ignore anything else. Use an oscilloscope to verify high-frequency oscillation at the source terminal of Q9. (For PAL applications this frequency will be 5.5 MHz and not 4.5 MHz.)

If all voltage tests are satisfactory, set potentiometer R18 at mid-range and set potentiometer R14 for maximum voltage reading on the emitter of Q7 (TP2). There should be at least 11.0-volts DC at TP2. If necessary, reset R18 so you get the 11 volts or more.


Tuning the RF circuits

RF stages Q2, Q3, and Q4 and video amplifier Q5 are operated in class C mode. In the absence of an input signal, they are "off" and draw no current. An input signal causes the stages to turn on and draw a current that is somewhat proportional to the input signal. Therefore, by monitoring the collector current of a stage, the drive signal supplied to that stage can be monitored. Test points are used to monitor stage currents by reading the DC voltage drop across resistors in the collector circuits. Typical collector current of stage Q2 is 25-40 mA; Q3 and Q4, 30-60 mA. Transistor Q5 is tuned for maximum RF output into a 50-ohm dummy load.

Connect the negative (-) lead of your VOM or DVM TP3 and the positive (+) lead to test point TP1. Make sure the supply voltage is set to 13.2-volts DC. Set the slug in oscillator coil L1 all the way inside. Now back out the slug with a plastic align-


**COIL WINDING DATA
FOR THE MINI 900 TRANSMITTER**

Coil	No. of Turns
L1	7.5
L2, L3, L5	3.5
L4	2.5

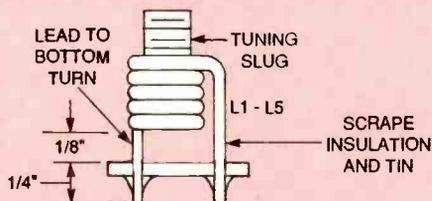


Wind coils L1-L5 using #22 enameled wire on an 8-32 screw. Form leads as shown in diagram. Scrape off enamel and tin wire ends as shown. Bottom of last winding is mounted 1/8-inch above PC board. Install coils on PC board using 8-32 screw as holder. Once soldered in place, remove screw and thread in 8-32 Cambion blue tuning slug.

Coil	No. of Turns
L6	0.5
L7	1.5
L8	4.0

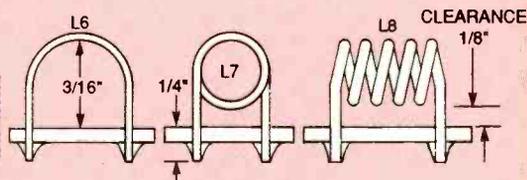


Wind coils L6-L8 using #22 bare, tinned wire on an 8-32 screw. Form leads as shown in diagrams to allow 1/8-inch clearance for L7 and L8. Remove screw. Spread turns evenly to fit on PC board mounting holes and solder in place.

Coil	No. of Turns
L11	2.5
L12	0.5
L13	0.5

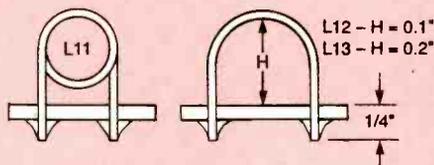

Wind coils L11-L13 using #22 bare, tinned wire on a 6-32 screw. Form leads as shown in diagrams. Remove screw. Spread turns of L11 evenly to fit on PC board mounting holes and solder in place. Solder coils L12 and L13 in place carefully observing height dimensions.

Coil	No. of Turns
L14	13

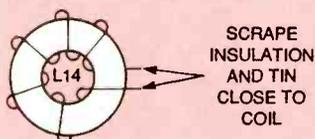

Toroidal coil L14 is wound on a 0.375-inch diameter ferrite core. Use fine sandpaper to remove sharp edges from the toroid-hole ends to avoid scraping of wire insulation when winding coil. Use #22 enameled wire (about 10-inches long). Pass the wire through the hole 13 times—each pass is a turn. Space turns evenly on toroidal form. Scrape off enamel and tin wire ends as shown. Install on PC board tight to surface.

ment tool, while watching the meter. At some point the voltage reading on the meter should sharply jump up to a higher reading, then tune for a peak reading. Then back the slug of L1 out of the coil so the reading decreases about 5-10%. Next adjust the slugs of L2 and L3 for a maximum reading. Repeat adjustments of L2 and L3 until no further voltage increase is obtained on the meter. Next remove the power and set trimmer capacitors as follows:

- C12 35% mesh
- C13 20% mesh
- C14 20% mesh

- C19 35% mesh
- C20 50% mesh

See Fig. 3 for locations of the above trimmer capacitors.

Connect a 50-ohm dummy load suitable for 900 MHz across the output of the RF power amplifier (junction C36 and L13, and foil ground.). Use 50-ohm coaxial cable and make the connection short. See Fig. 4 for proper cable-connection method. Connect the cable to the 50-ohm dummy load using a suitable connector to match your load (BNC or N-types, usually). Use proper adapters as required. Type RG188 or RG316


coaxial cable is preferred. Cable type RG174 is also satisfactory, but tends to melt rather easily when soldered. Some sort of indicator on the load is necessary to see the RF output, but it does not need to be calibrated—a relative reading is satisfactory.

Restore power to the PC board. Readjust L2 and L3 as before. Now remove the negative meter probe from TP3 and connect it to TP5. The meter's positive probe is still connected to TP1 (13.2- volts DC).

Start with a range setting on the multimeter that will adequately show readings in the 1-volt DC range. Verify that the trimmers are preset. Adjust L4, L5, C12, and C13 for maximum meter reading. Then, readjust L2 and L3 to further increase this reading as much as possible. Repeat this procedure until no further improvement is noted. Capacitor C14 is not touched and is left as preset during this step. The reading obtained in this step may be typically 1 to 1.5 volts.

Repeat L4, L5, C12 and C13. Continue this process until no further increase in the meter reading can be obtained. The settings for the trimmer capacitors should not be too far from the original preset positions. If they are radically different, check to see if L4, L5, L6, and L7 are properly wound and that the correct parts are installed in the circuit board positions. Coil L4 has only 2.5 turns and may not securely hold the slug in position. Use a small drop of paraffin wax as a temporary cement to prevent the coil's slugs from falling out or shifting during handling and tune-up.

Adjust C14 for a dip (minimum reading at TP5) from the reading in the previous step. This dip in the reading may be around 30-50%. Do not worry about the exact amount as long as a significant dip is obtained. It should be fairly near the preset mesh, 10 to 30% or thereabouts. If the dip occurs at over 35% mesh, this indicates something has been improperly tuned or there is an error in assembly. Capacitor C14 should not be meshed more than 35%

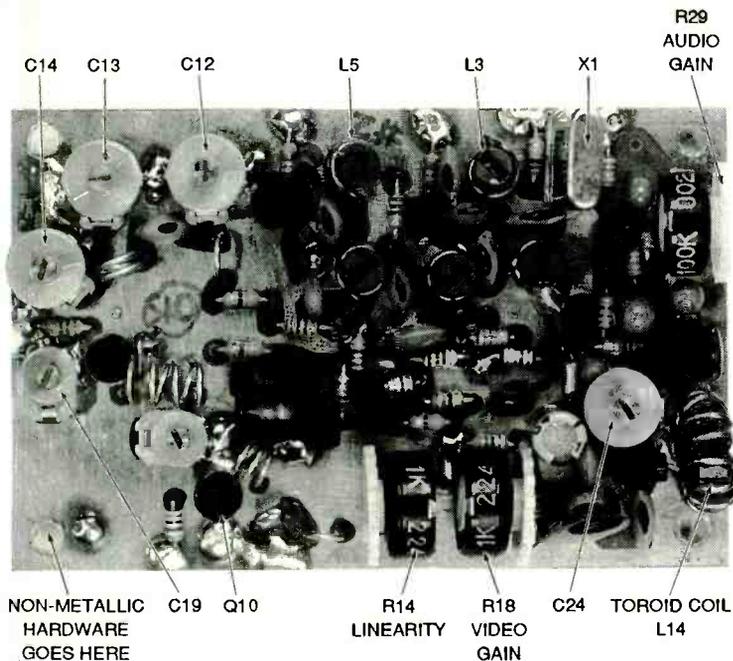


Component side of the PC board shown with all the parts installed and ready for cable connection to video and audio inputs and antenna. A few of the components are identified to facilitate compatible recognition with Fig. 3.

as this indicates incorrect tuning.


Carefully and slowly adjust C19, while watching the RF output power meter and the power-supply current. A sharp rise in power-supply current and an indication on the RF power meter will be noted at some point around the preset position of C19, typically 30 to 40% meshed. No other setting is acceptable. The tuning elements are fixed in the PC board and therefore have close tolerances. Next, adjust C20 for maximum RF output. Then, go back to L4 and L5, and readjust them for maximum RF output, followed by re-peaking C12, C13, and C14 to further improve output. Reduce the supply voltage to 10-volts DC and verify there is still RF power output as seen at the indicator on the dummy load. About 20% or more of the previous output should still be obtained. If not, repeat previous steps starting with L2 until you achieve this.

You should be able to obtain RF output below 8.5 volts from the power supply before the RF power drops out completely and the RF power should vary smoothly with supply voltage, no sudden jumps or reversals at higher voltages, if the tune-up procedure was done correctly. There is some interaction between tuning adjustments. Also, the power-supply voltage can affect the value of transistor internal capacitances, resulting in some slight variation of optimum tuning settings over a voltage range. It is strongly recommended to perform initial tune-up at 13.2-volts DC, and make sure that all is functioning properly. If other supply voltages are to be used (9 to 15-volts DC) you should then re-tune the Mini 900 at the alternate supply voltage.

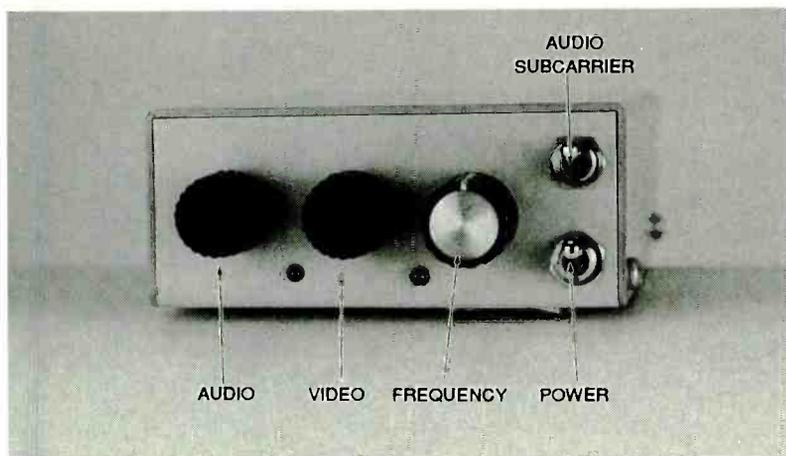At 15 volts (maximum) power-supply voltage, the Mini 900 will have less tolerance to fault conditions such as over-voltage and high antenna VSWR (greater than 2:1). Conversely, at 9-volts DC (minimum) power-supply voltage, there is no room left to allow for lowered supply voltage (weak or exhausted batteries,



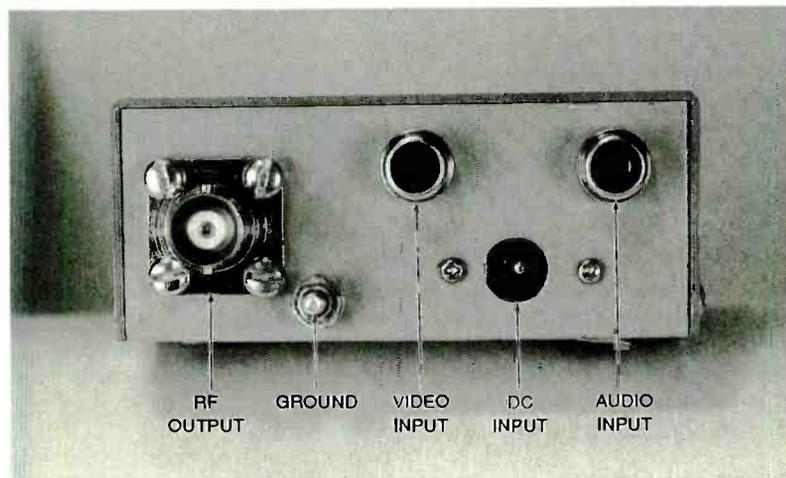FRONT PANEL for the Mini 900 shows the operator's controls. The FREQUENCY control is a modification that was eliminated in the final prototype.



THE REAR PANEL is where all input and output connectors are located. A screw-terminal grounding post should not be ignored when setting up the transmitter.

etc.). For this reason, 11 to 14-volts DC is suggested as an operating supply voltage.

About 0.5-watts RF output or more should be obtained with a 13.2-volts DC supply. At 10-volts DC, typically 0.2 watt; at 15-volts DC, typically 0.7-watt will be obtained. This is *peak envelope power* (PEP) and occurs on video signal's sync tips. Average power varies with video modulation and will be 20 to 60% of this figure, depending on the modulating signal. If, after all tuning adjustments are optimized, power output seems a little low, it is possible that the inductances of L12 and/or L13 are too high.

Check L12 and L13 by bringing a brass or copper screw near the coils, first L12 and then L13. The presence of the brass screw reduces the coils inductance. If the power output increases slightly, reduce the size of the corresponding inductor until this test fails to produce an increase. These inductors are electrically and physically small and there is a tendency for most builders to make them too large. Conversely, if no improvement is detected, leave them alone, and check C33, C34, C35, and C36 to see if they are correctly mounted and are not cracked or broken. Make sure that R14 and R18 are set for maximum voltage (at least 11.5 volts) at TP2.

The final adjustments

The last step is the checkout of the video modulator. You will need a suitable receiver or monitor capable of tuning to 902-928 MHz or to whatever crystal you have installed. Connect the transmitter to an antenna such that its radiating element is at least 5 feet from the PC board and at least 10 feet from the receiver. No antenna should be needed on the receiver. Connect a source of video (1-volt, peak-to-peak, 75-ohm, negative sync) to the video input of the transmitter (across the junction of R16- R17 and ground). Connect audio signal to audio input point (across R29). A VCR with a tape playing is an excellent video/audio

source.

Set R18 and R29 to mid-range settings. Apply power to the Mini 900 and adjust R14 so the RF power output drops to half its original level. Turn on the receiver and activate the VCR or other source of video and audio. Watching the picture, adjust R14 and R18 for a good stable picture, without rolling, or white or black level clipping. Adjust R29 for best sound. Set the receiver's volume at normal level during this adjustment. Readjust R14, R18 and R29 as needed.

Do not attempt any RF adjustments using the received picture. If a satisfactory picture cannot be obtained, make sure you are not overloading your receiver with excess RF signal or that you are not causing the RF signal to interfere with your source of video. Some video equipment may not work properly in strong RF fields so do not immediately assume the transmitter is to blame.

The video modulator in the Mini 900 is DC coupled. A drop in supply voltage due to battery depletion may cause sync clipping to occur. If this operating condition is expected, set the alignment adjustments at lowest expected supply voltage. An increase in supply voltage usually has no effect in this regard. The circuit design assumes a reasonably constant supply voltage, -1 to +2 volt variation at 12 to 14-volt levels. At 10 volts, no more than 0.75 volt drop would be advisable without readjustment of R14 and R18.

After alignment procedure is completed, it is a good idea to glue the tuning slugs in L1 through L5 in place, and to coat the toroidal coil L14. Use Duco cement or any clear lacquer for this purpose. Avoid pigmented paints as certain pigments can introduce losses into the coils. After the cement dries, a slight readjustment of the 4.5 MHz subcarrier frequency (C24) might be required.

Using the Mini 900

The Mini 900 ATV transmitter can be used in a variety of


applications for video transmission and should be suitably mounted. Current amateur band plans for 902-928 MHz suggest the use of two channels (picture carrier frequencies) for ATV use at 910.25 and at 922.25 MHz. This is not a legal requirement but a recommendation to follow that avoids possible interference with other amateur stations. Check the ARRL repeater directory or with local amateurs active in ATV to determine what picture carrier frequencies to use.

Also remember to maintain good RF practice and to shield all cables (video, audio and DC) to the board. Shielded audio cable can be used for short runs for video and audio, but for the antenna lead use a short length of RG188, RG316 or RG174 cable. These cables are very lossy so do not be surprised to experience a 20% power loss in a 2 or 3-foot cable.

Make sure to mount the transmitter in a shielded enclosure. If the overall weight is a consideration, a thin plastic enclosure wrapped with sheet copper foil might be used. Copper foil with a thickness of 0.001 or 0.0015-inch is usually available at hobby and craft stores. Solder all seams in the copper where possible. Keep the radiating antenna as far as you can from other devices that may be RF sensitive. This can be a challenge in R/C models. Use the best antennas possible. The Mini 900 may be limited to a low-gain antenna such as a simple quarter-wave whip. The 900-MHz receiver might require a higher gain antenna. Resist the temptation to use those cute little stub and rubber duckies when significant range is required. The larger types of antennas perform better, all things being equal.

The authors used a pair of corner reflectors for the range test and obtained a clean picture at over 5 miles, and a fair picture 12 miles away at favorable locations. Range is more a function of terrain than anything else. A corner reflector antenna consists of a half-wave

Continued on page 73

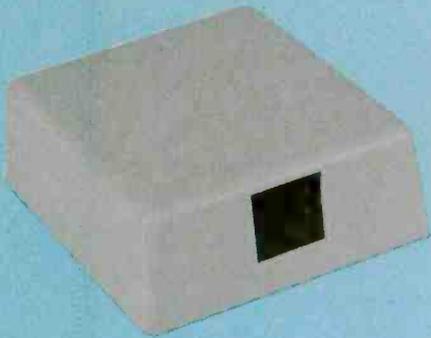

A specialized two-lead semiconductor is a complete project that will protect your modem communications from interruptions.

PHONE-LINE PRIVACY MODULE

MODEMS ENABLE COMPUTER owners to communicate with other computer owners, and access fax machines and network services all over the world. You can download more information about almost any subject than is found in your local library in less time than it takes to get there! You can send orders for merchandise, requests for information, or send your opinion to a radio station right from your keyboard.

With all this convenience comes a problem: You can be interrupted during the middle of all this high-speed, compressed-data, multiple handshake communications by the simple act of your two-year-old child picking up a phone in another part of the house and saying "Hi Granny" into the mouthpiece! Even five minutes lost can be aggravating.

One obvious solution is to have two phone lines—and the accompanying two bills from the phone company. A better solution would be an automatic way to ensure that the person, modem, or machine using the phone line has exclusive use of the line. Such an arrangement is possible without the resources of NASA and the national budget. In fact, the exclusive use of the phone line can be arranged at your house or business just by adding a single semiconductor in series with each phone that might interfere with modem operation.

Phone basics first

Although the "how" of operating a phone across the phone network is so simple as to be second nature to everyone (re-

member that two-year-old child), the behind-the-scenes operation is more complicated. Consider the operation of a phone line that runs from the telephone company's CO (central office) to your home.

Start with the phone on-hook (hung-up is the common expression) waiting for a call to be made. When all the phones on the same line are on hook, the phone line from the CO is an open loop. There will be a voltage of between 30 and 50 volts DC standing on the line, and no current will be flowing.

When a phone goes off-hook, a switch inside the telephone connects the phone instrument to the phone line, and presents a terminating load of approximately 600 ohms. This 600-ohm load causes a DC current to flow in the loop between your home and the CO. This DC current signals the CO that you wish to make a call. The amount of current flowing depends on the distance the phone is from the CO, since the current has to travel many miles through the phone lines to your house. The farther away your home is from the CO, the lower the loop current, and consequently, the lower the voltage seen at your home telephone. Typically, the off-hook voltage might vary between 12 and 18 volts.

Equipment at the CO places an audio dial tone signal on the line going to your house to let you know that connection to the CO has been made and you can now proceed with dialing. The CO listens for the DTMF (digital-tone, multiple-frequency) signals from the phone's keypad, and the call is routed at the CO to a destination. The equipment at the CO then waits for you to break the connection by hanging up, which it determines when the loop current no longer exists.

For incoming calls, the CO places an AC ringing voltage from 90 to 130 volts AC onto the DC voltage standing on your open-loop line. A capacitor in the telephone provides a closed loop for the ring signal when the phone is on hook. The capacitor passes the AC through to the ringing circuitry, and your phone rings. When you pick up the phone, you complete the DC loop as mentioned previously, and the CO knows you have picked up the phone. The CO discontinues the ringing signal, interconnects the originator's phone to yours, then monitors the loop current, waiting for you to hang up.

One-component project

To isolate the modem from the phones and achieve uninter-

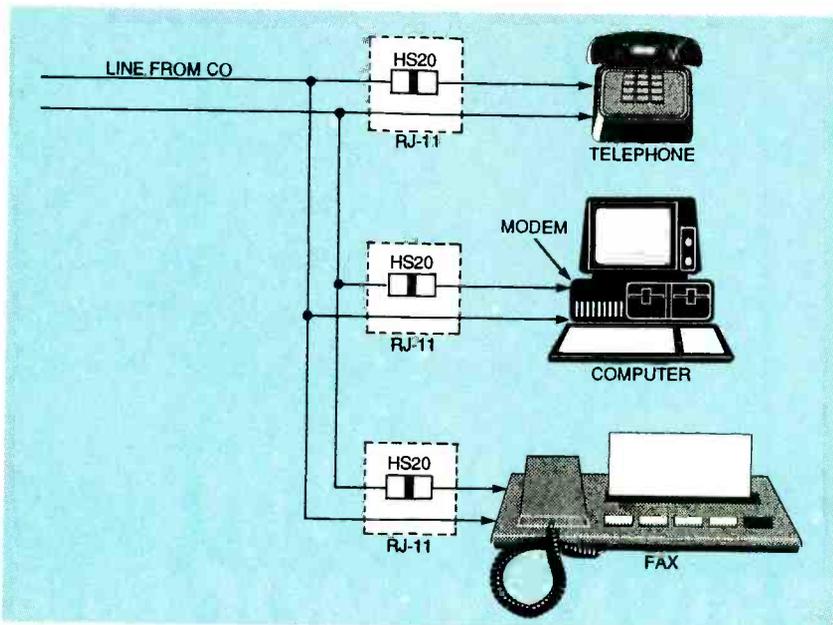


FIG. 1—INSTALLATION SCHEMATIC DIAGRAM for installing the HS20 bilateral silicon trigger switches in your home-phone network. The HS20's can be installed within the communicating device or inside a RJ-11-type terminal block.

Basic plus one part

Here is how your home phones will operate after the installation of the HS20 bilateral silicon trigger switches: With the modem and the phone line on-hook, 30 to 50-volts DC is standing on the line, and is present at the modular plug for each phone. If your modem goes off-hook, it closes the loop, and the HS20 sees the 30 to 50 volts across it.

Because the HS 20 is manufactured to trigger at 20 volts, it triggers, and becomes a very low resistance (about a 2-volt drop) part of the loop circuit. Should the other phone(s) in the circuit now try to access the line, nothing will happen. The voltage on the circuit, with the modem accessing the line, has dropped to somewhere between 6 and 18 volts. This voltage is not enough to fire the trigger switch at the phone's site, and the HS20 remains in a high-impedance (resistance) state. You do not have loop current flowing in the line to your voice phone, and you have not interrupted the modem's reception or transmission.

The HS20 works equally well the other way: If you are on the voice phone first, no other phone equipped with a trigger in the loop can interfere. The other phone will be silent, and cannot hear your phone conversation. Also, you cannot use your modem.

Installation

You can determine from the schematic drawing in Fig. 1 that the HS20 can be placed anywhere in each telephone's line so as to effect only that device. The RJ-11 block (Fig. 2) is the best place to install the HS20 in series with one wire of the inner pair of the modular jack. Unless you have more than one phone line, the inner pair of the modular cord will always be the pair from the CO. In some cases, it might be easier to open the phone's plastic case and locate the inner pair of wires, and solder the HS20 into one of the lines.

It does not make any difference which of the two wires of

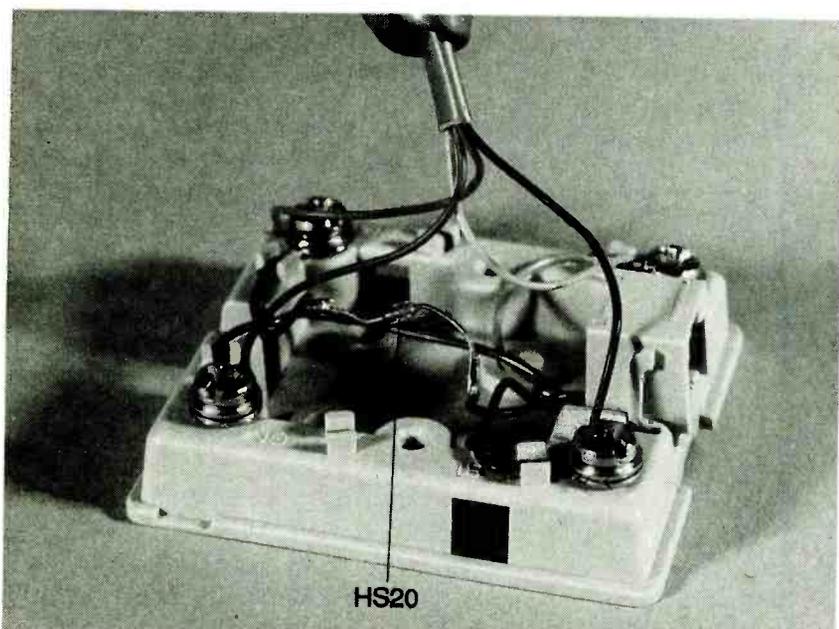


FIG. 2—INSIDE VIEW of a RJ-11 type terminal with the HS20 bilateral silicon trigger switch installed. Communications emanating from a phone or modem plugged into this block will not interfere with other similarly connected devices.

rupted communications requires the installation of HS20 bilateral silicon trigger switches manufactured by Teccor Electronics. Normally, the HS20 is used in commercial light dimmers as part of the triggering circuit for a triac. It prevents current from flowing until the voltage has built up to a definite, repeatable value, then fires

(or begins conducting) at a point in the AC waveform that allows for positive triggering of the triac. However, those performance characteristics are ideal for this application. All you have to do is install one semiconductor in each of the phones that you want to safeguard from jamming your modem's communications.

the line is used, and you do not have to stay on the same wire from one device to the next. The HS20 is also not polarity sensitive, so either lead of the semiconductor can be connected to either line in the loop. Again, you need to put one HS20 in the line for each device you want to protect including the modem. Any phone connected to the line without the HS20 in its line will be able to butt-in on your conversation, or on your data or fax transfer.

One HS20 bilateral silicon trigger switch is required for each phone and modem you intend to protect; the minimum quantity is two semiconductors for a home with one modem and one phone. If you are having trouble obtaining the HS20 bilateral silicon trigger switches from electronic parts suppliers, you can purchase them from SolarWorks, 2747 Wentworth Drive, Grand Prairie, TX 75052 for \$4 each, plus \$0.50 postage and handling per order. Ω

TROUBLESHOOTING

continued from page 38

each minute. As we listened to the machinery and watched the pulses, we heard a cooling fan switching just as each new spike occurred. Then we realized that the problem was the spike. It was fooling the PLC, and making it think that the temperature had dropped below threshold during one of the spikes, when the temperature dropped near 400 degrees.



THE TEK METER saved the day!

Now it's so obvious

A visual inspection of the thermocouple cables revealed that a portion of its shield had been worn away because of the vibration of a nearby cooling fan. Figure 6 shows some typical thermocouple hardware for those who are not already familiar with them. Replacing the cable got the annealing cycle back to normal, and the springs were springy again! We and our portable scope found and eliminated a costly factory problem.

The preceding examples illustrate just a few of the ways that a portable scope can be used to find and cure factory process problems. In addition to these simple cases, we can use the DVM and oscilloscope functions to find power-quality problems caused by dirty AC, bad power factors, and unbalanced phase power. We can also evaluate SCR- and triac-based motor controls for voltage, phase, and frequency conditions, factors governing efficiency. Finally, we can detect and cure sensor signal degradation with the simplicity of using a pocket DMM. Ω

ATV TRANSMITTER


continued from page 68

dipole mounted near a reflecting surface consisting of two plane conducting surfaces at an angle, usually 60 to 90 degrees. The dipole is parallel to the line of intersection of these surfaces and 0.25 to 0.4 wavelengths away from the intersection. Typical gain of these antennas is 8 to 12 dB over a dipole.

A fair quality picture with minor snow requires better than 20 dB signal-to-noise ratio of the received signal. A 20 dB signal-to-noise ratio voice signal means very comfortable copy (assuming AM modulation). A fair picture means it has some snow, certainly useful for facial identification.

In the author's tests, the Mini 900 was mounted on the back of a corner reflector with 11-inch square sides at a 90-degree angle. The antenna was 30 feet above ground on a hilltop at the author's home, 12 air miles east of Glens Falls, NY. The receiver setup used a similar but slightly smaller antenna with a low-noise downconverter mounted on the back of the antenna. The matching downconverter for the Mini 900 ATV transmitter project and corner reflector antenna construction will be covered in future issues.

The downconverter was feeding a 12-volt DC TV receiver, the receiving setup located on the front seat of the author's vehicle. At best sites, the transmitter location was visible with high-power binoculars, so line-of-sight conditions were had, but a good picture was still obtained with some obstructions. However, in hilly terrain with heavy foliage, range was as short as half a mile when hills blocked the signal. R/C airplanes typically have line-of-sight conditions in most cases. Typical range with 3-inch whip antennas at the transmitter and receiver would be about one mile or so line-of-sight, less for obstructed paths. Use the best antennas possible for the situation you face. Ω

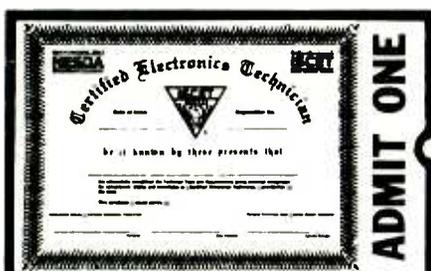

Your Ticket To SUCCESS

Over 28,000 technicians have gained admittance worldwide as certified professionals. Let your ticket start opening doors for you.

ISCET offers Journeyman certification in Consumer Electronics, Industrial, Medical, Communications, Radar, Computer and Video. For more information, contact the International Society of Certified Electronics Technicians, 2708 West Berry Street, Fort Worth, TX 76109; (817) 921-9101.

Name _____
Address _____
City _____
State _____ Zip _____

Send material about ISCET and becoming certified.

Send one "Study Guide for the Associate Level CET Test." Enclosed is \$10 (inc. postage).

METROLOGY LAB

continued from page 40

tempting this project with commonly available resistors, the results have been excellent.

Selecting resistors

You must select resistors for the divider out of a batch of ordinary 1% metal-film devices. Even though 1% is more than two orders of magnitude worse than what we need, any given bag of 200 resistors is almost certain to contain at least one suitable set, and usually more than one.

The process of selecting eleven resistors that are matched to better than 40 PPM is not difficult, merely tedious. To make the job as easy as possible, you

can build a comparison bridge with "quick insertion" clips, just like commercial bridges use.

A simple comparison bridge circuit is shown in Fig. 3. Build it on some scrap perforated construction board, and be sure to use a multi-turn trimmer potentiometer, or the bridge will be impossible to zero. The resistor clips are made from .015-inch brass, cut with scissors and bent with needle nosed pliers. Drill the brass strips, deburr them, then clean them with steel wool before bending.

Bridge power is supplied from three 9-volt batteries in series. The best detector is the null detector described last month. However a DVM that can resolve 0.1 millivolt is also acceptable. With a resistor installed on the

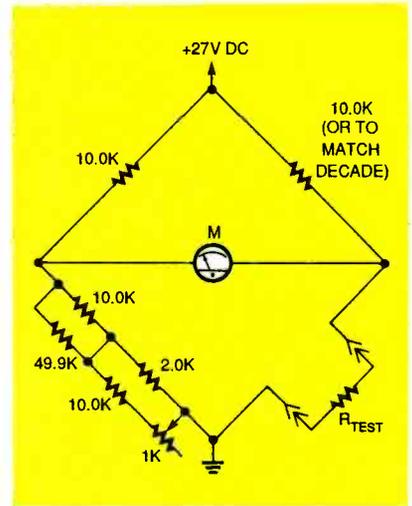


FIG. 3—BUILD THIS COMPARISON BRIDGE to match resistors for the KVD.

clips, you should be able to zero the bridge by adjusting the trimmer potentiometer. Note

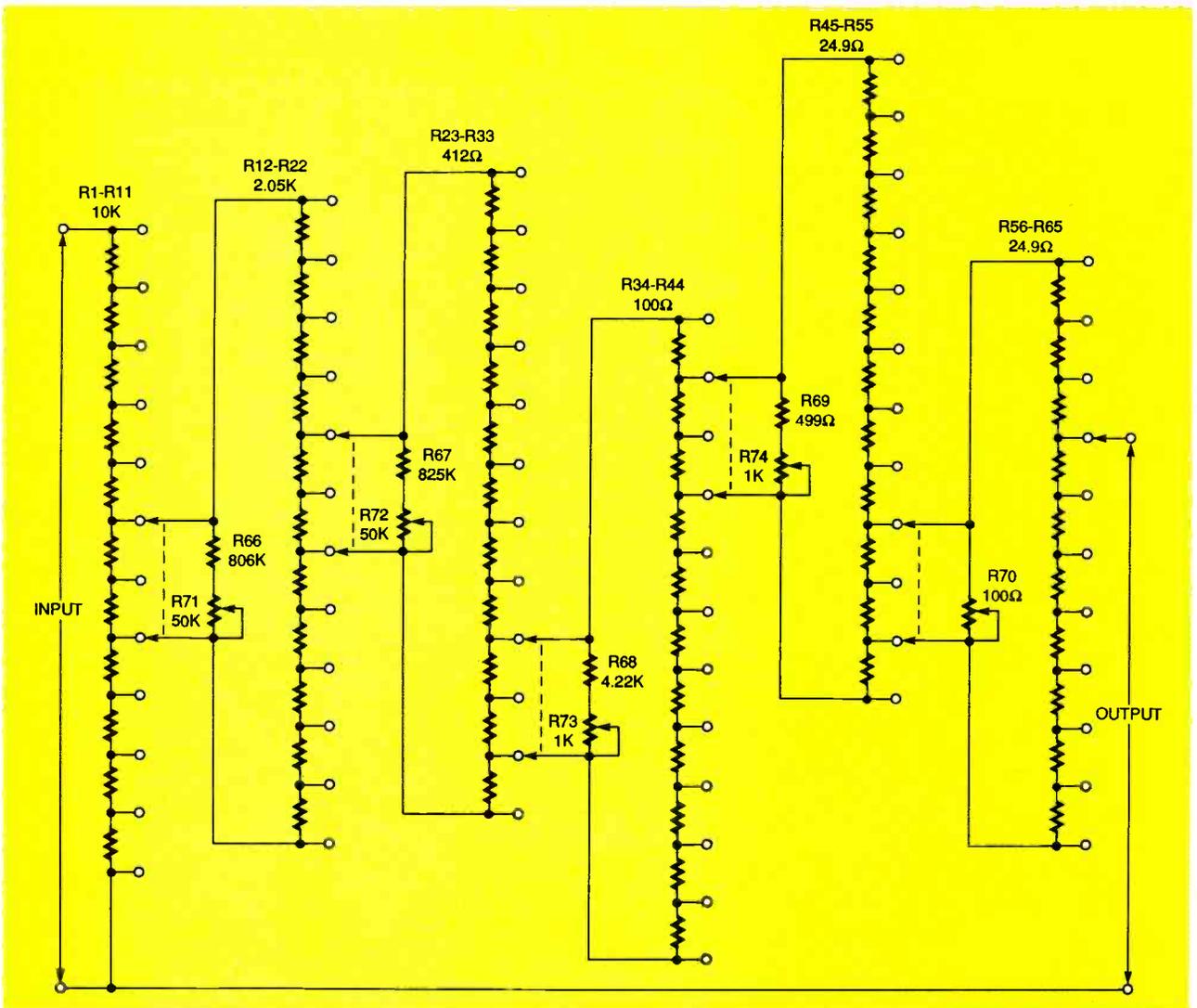


FIG. 2—THE COMPLETE KELVIN-VARLEY DIVIDER. The setting shown equals 0.45187.

that it takes 10–20 seconds to get a stable reading to the precision you need.

The first order of business is to get an idea of the average value of your resistors, and sort them into roughly matched groups. Since all of the resistors have values within 1%, the bridge will be nearly balanced at all times. You will not have to re-zero it; instead, just read the deviation on the null detector (or DVM). The bridge has a very narrow range of adjustment. You might have to pad one of the upper legs slightly if it won't zero.

An excellent way to keep track of the resistors is to use a piece of perforated construction board as a sorting board. Put a piece of masking tape on the long edge and label the holes. Start with zero in the center, then 10 millivolts per hole, going outwards from zero each way. Minus should be on the left. You will soon see where most of the resistors fall, and can re-zero the bridge to put this value in the center. I find that a four by six inch board is enough. If the average value is near the center, resistors off the edge are unlikely to match, and can be put aside.

Measure each resistor, put it into the appropriate hole in the sorting board. As you test more and more resistors, the sorting board becomes a visual histogram of the resistor values!

With luck, there should be several columns with high numbers of resistors. Separate these columns, combining them with the columns on either side. Measure these resistors again, increasing the sensitivity of the detector, and sorting them every 1/2 millivolt.

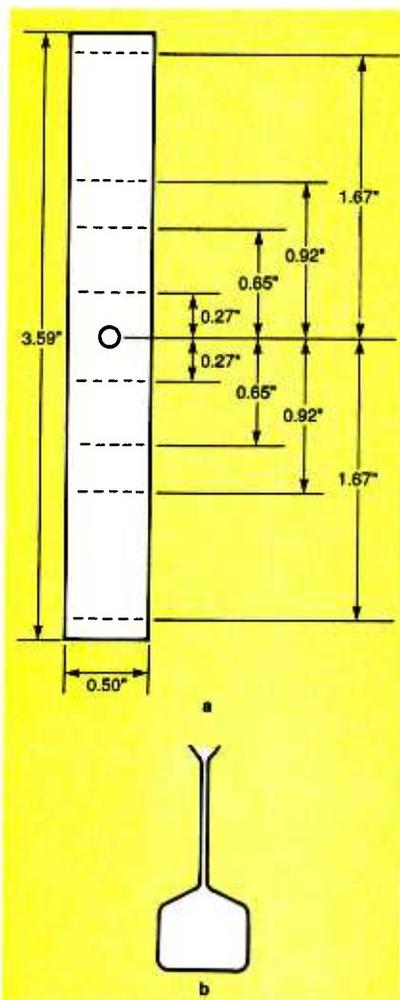


FIG. 4—BEND A 0.015-inch BRASS STRIP as show to form a clip for inserting resistors into the comparison bridge.

From adjacent columns, it should be possible to find 11 resistors that are all within 1/2 millivolt of each other, and hopefully, a few spares. No doubt there will be a few people who don't "win" on the first bag of resistors. If this is your fate, either order another bag, or live with a bit lower accuracy.

Once you have resistors for the first decade selected, re-

measure them a few times until you have confidence that all the parts are within a 1/2 -millivolt window. Congratulations, the hardest part is over!

Select the resistor sets for each subsequent decade in the same manner. You will have to change the reference resistor in the bridge for each value. The required match for each succeeding decade becomes less critical. The last three decades don't require matching, but I like to check them on a DVM just to be sure they are close. See Table 1 for values and matching requirements.

Assembly

The connector headers are epoxied to the top panel of the enclosure. I used a piece of phenolic sheet, but a piece of circuit board material would work equally as well. Remove the copper by etching or peeling it off.

Figure 5, a 1:1 copy of the panel layout, makes a handy drill template. Just tape a copy of it in position on the panel, then use a center punch to mark the holes. Drill on the punch marks. Clean everything carefully, then epoxy the connector headers in place. Try to keep the epoxy off the pins. Small rubber grommets in the wire exit holes will protect the wires and give the unit a more finished appearance.

Solder the decade resistors to the underside of each header as shown in the photo. Since excessive heat can change the resistor values, be sure to leave the leads long and heat-sink each lead while soldering. A pair of long nose pliers can be used as a heat sink.

The padding networks are at-

TABLE 1—MATCHING REQUIREMENTS

KVD Decade	Resistor Value	Resistor Match	Bridge Offset with 27V Applied	Padding Network (Typical)	Padded Value
1	10KΩ	±0.0037%	±0.25 mV	-	-
2	2.05KΩ	±0.037%	±2.5 mV	820K (806K+50K pot)	20K
3	412Ω	±0.37%	±25 mV	844.6K (825K+50K pot)	4.1K
4	100Ω	±1%	-	4.68K (4.22K+1K pot)	824Ω
5	24.9Ω	±1%	-	1.01K (499Ω+1K pot)	200Ω
6	24.9Ω	±1%	-	62.25Ω (100Ω pot)	49.8Ω

Six Decade Kelvin-Varley Voltage Divider

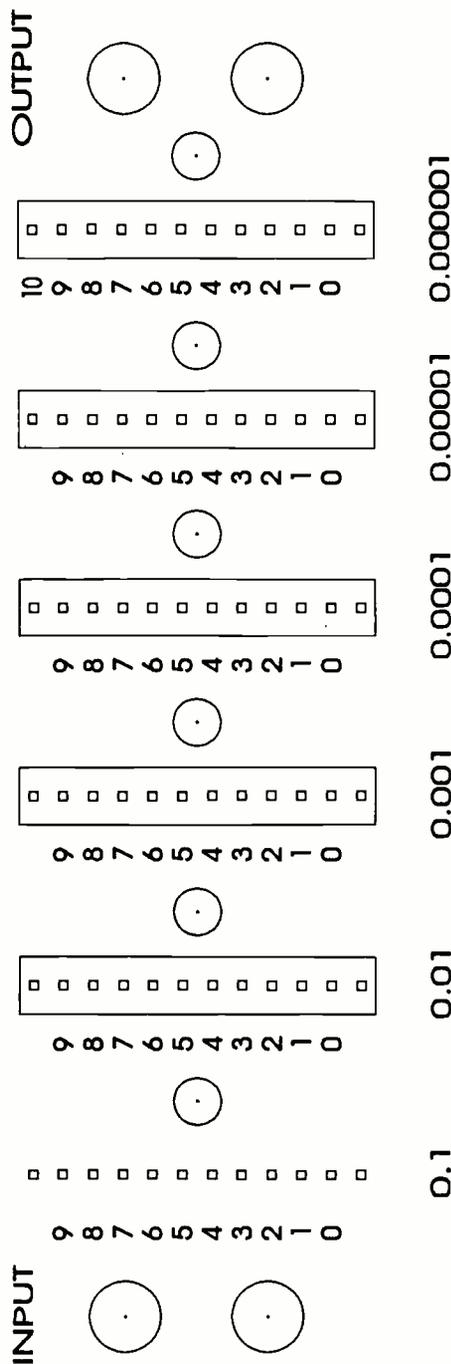


FIG. 5—THE KVD FRONT PANEL makes a handy drilling guide. It is shown full-size here.

tached across the full decades, and can be held in place with a drop of hot glue or epoxy. Each decade connects to its plug via a 6" twisted wire pair. Since the plugs are reversible, use two different colors of wire to avoid confusion. The plug for the last decade uses only one wire, so you may want to saw off the un-

needed portion. Also, cut off the unused header pin from the same decade.

If you build a KVD using rotary switches, you will have to work out the connections for the particular switches you use. Generally, the resistors will be mounted in series around one of the decks, and the other deck

will be wired in parallel, but offset by two positions.

Adjustment

The final step is to adjust the padding networks. This step has the potential to be confusing, so study the figures and instructions carefully. What you will do is attach clip-leads to turn each decade into a Wheatstone bridge, with the previous decade included as one of the bridge's arms. It is then a simple matter to adjust the previous decade and null the bridge.

This technique isolates each decade, and is the only way to accurately adjust the KVD. Do not attempt to adjust the decades with an ohmmeter, because it is not accurate enough, and the multiple current paths will give incorrect readings. Note that the voltages used are common battery voltages, if you don't have a suitable power supply handy.

1. Start with the output decade (No. 6). Attach power supply, the null detector, and a shorting lead to decade No. 5, as shown in Fig. 6. Because the resistances are low, do not apply more than 3 volts DC. Adjust the trimmer network on decade No. 6 for null.

2. Shut off the power and carefully move all of the clip-leads to the next decade (No. 4). Apply 3 volts DC and adjust the trimmer network on decade No. 5 for a null reading.

3. Move to decade No. 3 and adjust the trimmer network on decade No. 4, using about 9 volts DC.

4. Move to decade No. 2 and adjust decade No. 3, using about 18 volts DC.

5. Finally, move to decade No. 1 and adjust decade No. 2. Use 27 volts DC and make this adjustment as carefully as possible.

6. Recheck all the decades until you are confident that they are stable and correctly adjusted.

7. Finish up by installing the KVD in its enclosure

Making precision measurements

The simplest application of the KVD is to measure voltages


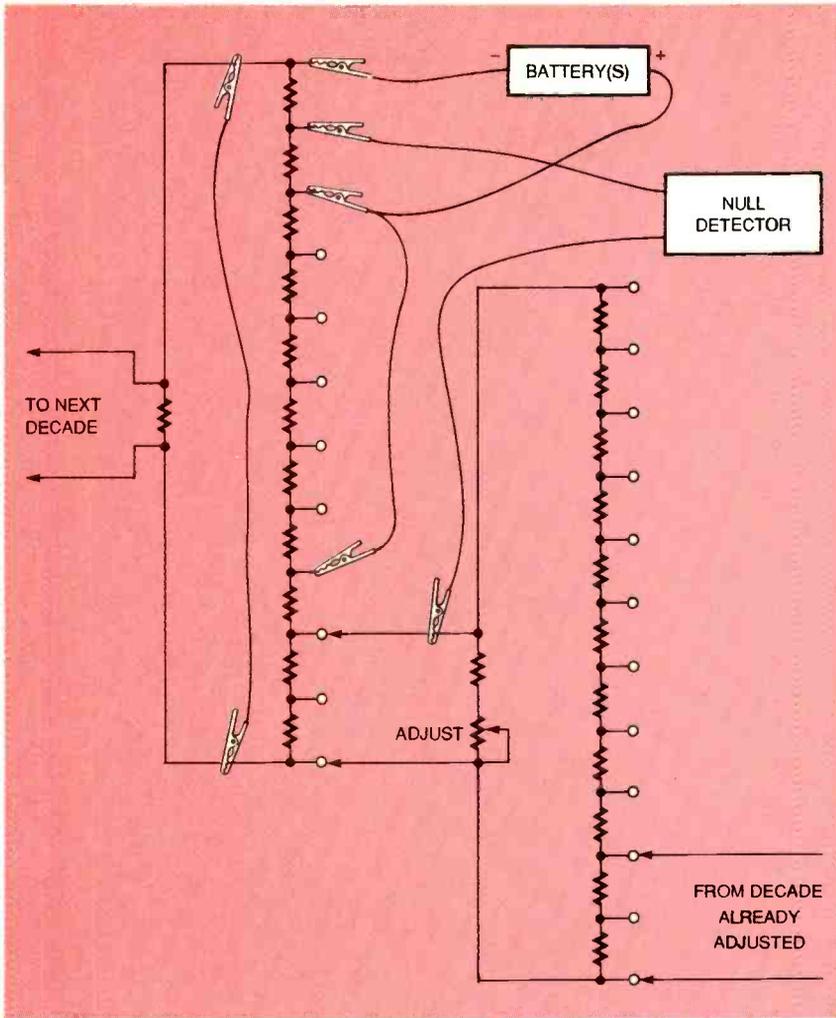


FIG. 6—HOOK UP CLIP LEADS AS SHOWN to adjust the padding networks.

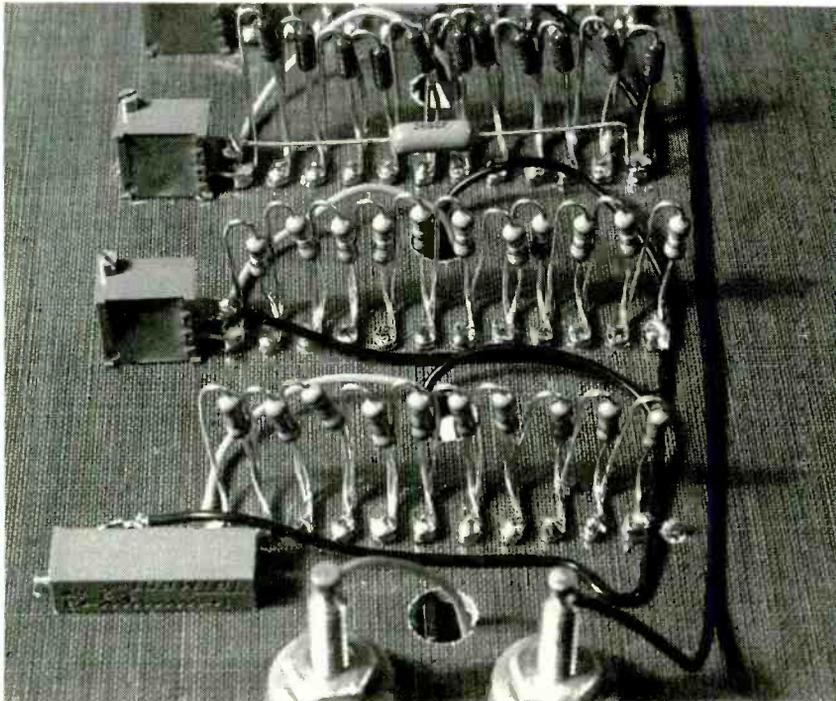

A CLOSE-UP view of the KVD wiring.


from zero up to the value of your voltage standard. The setup is shown in Fig. 7. Adjust the KVD settings until the null meter reads zero, then multiply the KVD reading times the exact value of the voltage standard.

Warning: Because the divider connections are exposed, do not use this divider with high voltages (above 40 volts), as there would be a risk of shock.

Using the voltage standard from the first installment of the series, this setup will easily check or calibrate the references used in 14-bit digital systems.

Remember: *The KVD is only accurate if no current is flowing in the output leg.* Thus, it is always used for null measurements, never as a source of current. For example, you cannot accurately measure the output of the KVD with a voltmeter, because the resistance of the meter would form a divider with the KVD, lowering the voltage slightly.

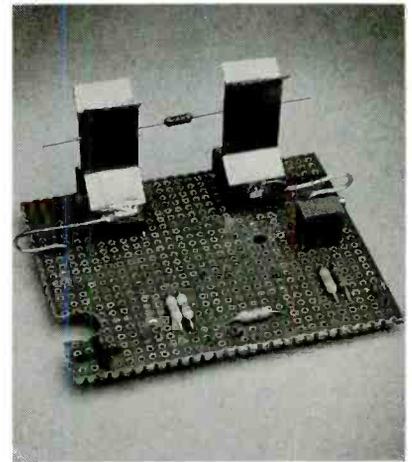To measure voltages higher than the voltage standard, you can divide them down with the KVD, then null to the voltage standard. See Fig. 8.



THE COMPARISON BRIDGE can be built on perforated construction board.

This method does load the source. To avoid that, another stable voltage source can be used. The source drives the KVD, and is adjusted to null with the voltage standard. The unknown voltage is then measured as in Fig. 7, but with the higher temporary standard.

The KVD can also be used as

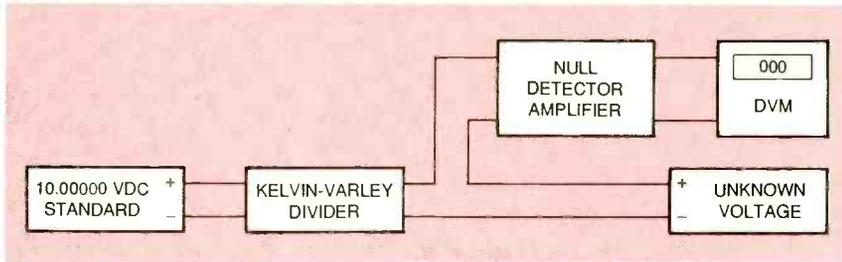


FIG. 7—THE SIMPLEST KVD MEASUREMENT SETUP.


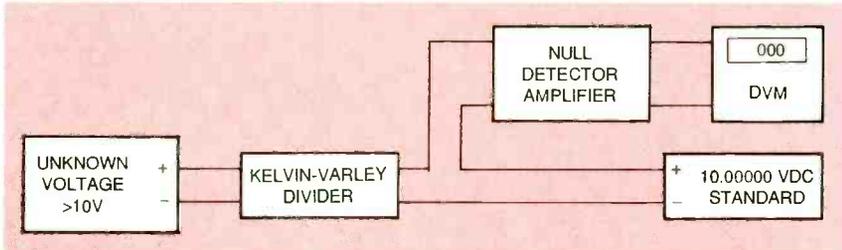


FIG. 8—THE KVD CAN BE USED TO MEASURE VOLTAGES above 10 volts with this setup.

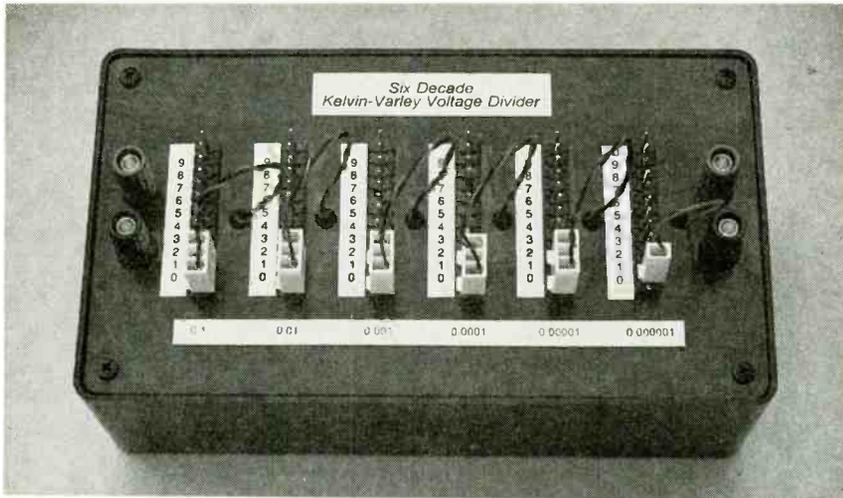

THE COMPLETE SIX-DECADE KVD installed in its case.

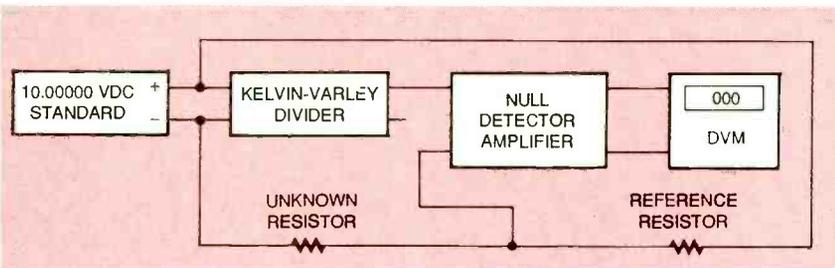


FIG. 9—USING THE KVD AS A BRIDGE.

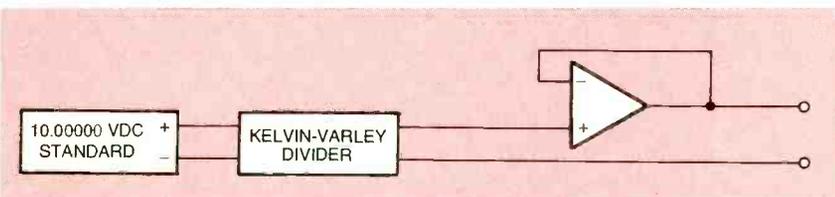


FIG. 10—THE KVD CAN BE USED AS A VOLTAGE SOURCE with this setup.

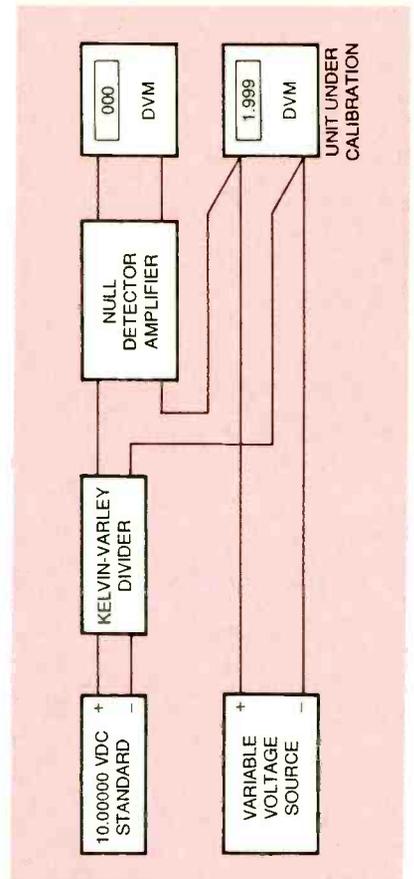


FIG. 11—TYPICAL CALIBRATION SETUP for the KVD.

one half of a Wheatstone bridge. If you have one or more precisely known resistors, you can accurately compare many different values to them. See Fig. 9.

Finally, the voltage standard and KVD can make a superb low current voltage source. The KVD is accurate only if no current is flowing in the output tap, so it must be buffered. See Fig. 10. This is a particularly useful arrangement for checking analog-to-digital converters.

We hope you enjoy building the equipment presented, and increasing your knowledge of traditional metrology techniques and making measurements that are accurate! Ω

REFERENCES

- Basic Electrical Measurements, Melville B. Stout, Prentice-Hall, 1950
- Calibration: Philosophy in Practice, Fluke Corp., 1994
- JRL Precision, Vol. 1 No. 2, Julie Research Laboratories Inc., 1958
- JRL Precision, Vol. 3 No. 5, Julie Research Laboratories Inc., 1960

Electronic SHOPPER[®]

CABLE TV DESCRAMBLER KITS

Universal-New Product

This Product includes all the Parts, PC Board, Complete Schematic with Functional Guide. Generates Sync for most Video Applications.

\$79.95

Tri-Mode Descrambler

This product includes all the parts PC Board and AC Adaptor. NO Enclosure included.

\$59.95

SB-3 Descrambler

This Product includes all the Parts, PC Board and AC Adaptor. Enclosure is not included.

\$44.95



Call Toll Free 1-800-886-8699

M & G Electronics, P.O. Box 3310, No. Attleboro Mass. 02761



Anyone implying theft of Cable service will be denied assistance.

NO MASSACHUSETTS SALES!

Weeder Technologies

Ask for our
FREE
catalog of other exciting kits.
Call 513-752-0279

Pro-Kit[™]

P.O. Box 421, Batavia, OH 45103

Educational Kits for the Serious Hobbyist

Home Automation

Connects between a TW523 and an RS-232 serial port. Use your computer to receive and transmit all X-10 commands. Create your own program to control your home automation system, turning on/off any device plugged into an electrical outlet with response to time/date, or another X-10 transmission. \$38.50

Caller ID / RS-232

Connects between a telephone wall jack and an RS-232 serial port. Decodes the caller ID data sent over the phone line and sends it to your computer in a pre-formatted ASCII character string. Create your own program to log the name, number, date, time of all incoming calls. \$34.50

Telephone Call Restrictor

Connects to telephone wall jack. Disables all phones on the line if attempting to either: dial a number that has been stored in memory "Block Mode" or, dial a number that has not been stored in memory "Allow Mode". Use touch-tone phone to enter telephone numbers into memory, and choose mode. Program from any phone on the line using your password. \$35.00

50 MHz Frequency Counter

Reads frequency from 1Hz to 50MHz and displays it on a 16x1 character LCD display. Auto-range feature provides floating decimal point and automatically affixes the correct suffix (Hz, KHz, or MHz). Microcontroller based, very few additional components. \$46.50

Telephone Scrambler

Scrambles your voice before sending it over the telephone line, and descrambles it on the other end. Connects between your telephone and wall jack. No modifications are required to your telephone. Full duplex operation. \$43.00

IR Remote Control Receiver

Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. Seven individual I/O pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. \$32.00

Vocal Filter

An audio device which can be used with a home component stereo system, to filter out the main vocal sound track from standard stereo recordings (CD, tape, record or FM), leaving the background music to sing along with. Produce your own karaoke tapes. \$39.00


DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Connects to your telephone wall jack. Decodes all 16 touch-tones and displays them on an LCD display. Holds the last 240 digits in a nonvolatile memory. Scroll through and view all telephone numbers dialed, credit card numbers entered, etc. \$54.50

In recent independent tests Cool-Amp is proven better than electroplating.

(For 50 years we've said Cool-Amp is "equal to" electroplating in performance. It is better.)

Cool-Amp

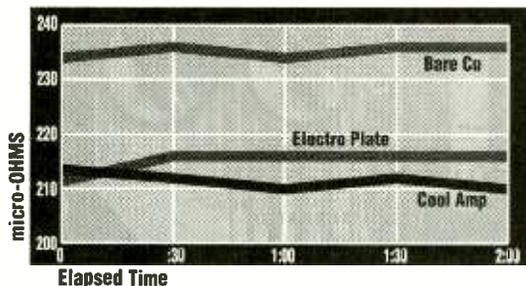


From the report:

"...compare the conducting properties of Cool-Amp silver plating compound with factory silver electro-plated bus and bare copper bus.

"The test results indicated that the contact resistance of the Cool-Amp plated bus connection was slightly lower than that of the electro-plated bus connection and much lower than that of the bare copper bus connection. The final temperature at temperature equilibrium of the bus connection employing Cool-Amp was slightly lower than that of the electro-plated bus connection and the bare copper bus connection..."

Conducto-Lube

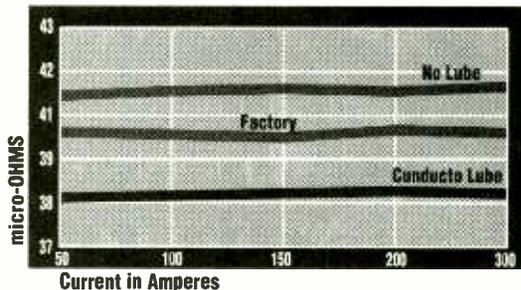

From the report:


"...compare the conducting properties of Conducto-Lube lubricant with factory lubrication and non-lubricated connections on an air switch. Identical test setups and procedures were used for each test so that comparative data could be collected and the relative performance of each type of connection could be quantified.

"The test results indicated that the contact resistance of the switch employing Conducto-Lube was generally lower than that of the factory lubricated switch and the switch that used no lubricant."

Cool-Amp

How it works:

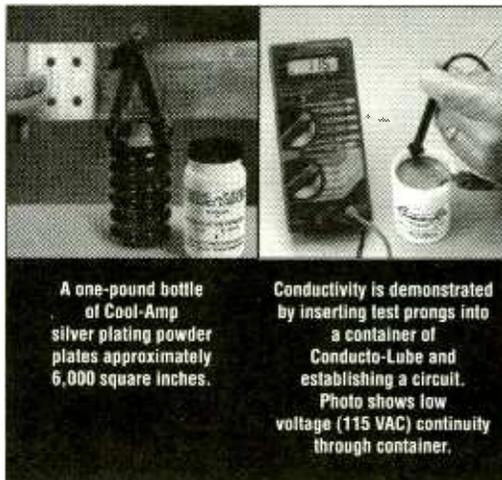- Applies *on the job*. Application is simple. Yet Cool-Amp adheres permanently. As tests show, it is better than electroplating.
- Minimizes overheating and power loss by silver plating high amperage connections.
- Saves time, reduces maintenance. Cool-Amp is so simple to apply on the job. It assures maximum conductivity for copper, brass, or bronze contacts and prevents losses due to oxidation.



A one-pound bottle of Cool-Amp silver plating powder plates approximately 6,000 square inches.

Conductivity is demonstrated by inserting test prongs into a container of Conducto-Lube and establishing a circuit. Photo shows low voltage (115 VAC) continuity through container.

Conducto-Lube

How it works:

- This is *the* conductive lubricant; highly conductive because it contains pure silver.
- Originally developed to lubricate switches, to the point tension can be adjusted to factory specs allowing full rated capacity of the switch to be maintained at all times.
- Uses have continued to expand—from switches and breakers—to any application where a conductive lubricant is needed.

*Various tests were performed on both products in the Electro-Test, Inc. facilities in Portland, Oregon during January-March, 1994. Evaluation of plating thickness of Cool-Amp was performed by Surface Science Laboratories of Mountain View, California.

COOL-AMP

Conducto-Lube

Cool-Amp Conducto-Lube Company

15834 Upper Boones Ferry Road
Lake Oswego, Oregon 97035
Order factory direct:
503/624-6426, Fax 503/624-6436

Get the best, most accurate diagnostics for problem PCs...

Low-Level Formats IDE Drives!

the UNIVERSAL DIAGNOSTICS TOOLKIT



Compatible with any PC & Operating System!



Call Now for Information on Special Pricing:

1-800-864-8008

OR Fax (818) 547-0397



1100 East Broadway, Suite 301, Glendale, California
Phone 818/547-0125 • Fax 818/547-0397

Web Page: <http://www.micro2000.com>

International Orders please call:

Micro 2000 Australia.....61-42-574-144


Micro 2000 UK.....44-462-483-483

Micro 2000 Amsterdam.....31-206-384-433

CIRCLE 224 ON FREE INFORMATION CARD

New Releases:

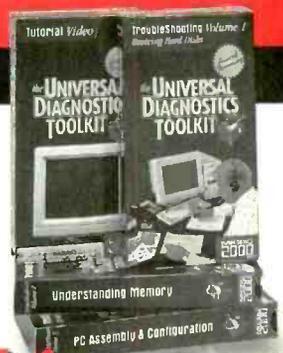Call about our Tutorial and TroubleShooting Series on video cassettes! A wealth of technical help at your fingertips.



Micro-Scope 6.1

UNIVERSAL DIAGNOSTIC SOFTWARE



Fully O/S independent diagnostic software...

Call for upgrade pricing & complete new features list!

MICRO-SCOPE Universal Computer Diagnostics was developed to satisfy the expanding need for accurate system diagnosis in the rapidly growing desktop computer market. Patterned after super-mini and mainframe diagnostic routines, MICRO-SCOPE runs independently of any standard operating system, and is therefore at home on any machine in the Intel world. Speed, ease-of-use, and razor sharp ACCURACY are a few of the advantages that arise from this system independence. **Jerry Pournelle** awarded MICRO-SCOPE & POST-PROBE the User's Choice Award in the May 1994 issue of Byte Magazine, saying: "You name it, this tests it. If you maintain PCs you'll love it."

- ◆ **LOW-LEVEL FORMAT**—Performs Low-level format on all drive types including IDE drives. This function cannot hurt IDE drives.
- ◆ **TRUE HARDWARE DIAGNOSTICS**—Accurate testing of CPU, IRQ's, DMA's, memory, hard drives, floppy drives, video cards, etc.
- ◆ **IRQ CHECK**—Talks directly to hardware and shows I/O address and IRQ of devices that respond.
- ◆ **O/S INDEPENDENT**—Does not rely on O/S for diagnostics. Talks to PC on hardware level. All tests are full function regardless of O/S (i.e. Windows, Novell, UNIX, OS/2).
- ◆ **IRQ DISPLAY**—Show bits enabled in IRQ chip for finding cards that are software driven (Network, Tape Backup, etc.).
- ◆ **MEMORY EXAMINE**—Displays any physical bit of memory under 1 Meg. Very useful for determining memory conflicts and available memory space.
- ◆ **AND MUCH MORE...** We don't have enough space here for everything this software can do!

Post-Probe

First Ever Universal P.O.S.T. Card for All PCs!


Use this Power-On Self-Test card to debug any "dead" PC that won't boot...

"This is the only card that will function in every system on the market. The documentation is extensive, and not only covers the expected POST Codes for different BIOS versions, but also includes a detailed reference to the bus signals monitored by the card." —**Scott Mueller** from his globally recognized book, *Upgrading & Repairing PCs, Second Edition*

- ◆ Includes pads for voltmeter to attach for actual voltage testing under load.
- ◆ 4 LEDs monitor +5vdc -5vdc +12vdc -12vdc.
- ◆ Monitors Hi & Lo clock and OSC cycles to distinguish between clock chip or crystal failure.
- ◆ Monitors I/O Write and I/O Read to distinguish between write and read errors.
- ◆ Accurately monitors progress of POST for computers *without* POST codes.
- ◆ Reads POST codes from any IBM or compatible that emits POST codes. ISA/EISA/MCA.
- ◆ Compatible with Micro Channel computers.
- ◆ Dip switch allows easy selection of I/O ports to read.
- ◆ Includes tri-state **LOGIC PROBE** to determine actual chip failures.
- ◆ Manual includes chip layouts and detailed POST procedures for all major BIOS's.
- ◆ **AND MUCH MORE...** call for more details.



Govt. Serv. #: GS-00K-94AGS-5396

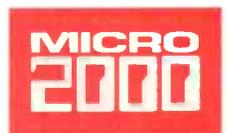

BRIGAR ELECTRONICS

7-9 ALICE ST.

BINGHAMTON, NY 13904



PHONE (607) 723-3111
 FAX (607) 723-5202
 E-MAIL BRIGAR2@aol.com

\$30.00 MIN ORDER

SEND FOR FREE CATALOGUE

SERVING: *INDUSTRY *SCHOOLS *HOBBYISTS *EXPERIMENTERS *CONSUMERS

OPEN: MONDAY THRU FRIDAY 7:30 AM TO 4:30 PM, SATURDAY 7:30 AM TO NOON



CREDIT CARD DISCOUNT

\$ 0.00 - \$99.99 NET
 \$100.00 - 249.99 Less 10%
 \$250.00 - 499.99 Less 15%
 \$500.00 - 999.99 Less 20%

Answering Machine Code-a-phone #1750
 FEATURES: *One touch play back *Ring delay(1,2,3,4) *Auto out going message check *Variable out going message *Built in cassette *No call disconnect *Voice-activated recording *Led message display *Fast forward,rewind,pause & rr (Removed from service good cond.)
 Original COST \$179.00
 COMMERCIAL Quality

SALE PRICE \$7.95



ULTRASONIC LIGHT SWITCH
 Motion Sensing Automatic SWITCH
 Replaces existing wall switch - operates from 120vac power. 750W max. load. Great for home alarm systems or controlling lights & small appliances. Adjustable time & sensitivity, on-off switch - led trip indicator - Color: White -
 Size: 5"w x 5"h x 1-3/8"d -
 Energy Savings 30 to 60%

**PRICE \$12.95 EA.
 5 FOR \$60.00**



**HI VOLUME FAN - 115 VAC
 NIDEC-TORIN TA600S**

.250/.20 AMP 3200 RPM
 IMPEDANCE PROTECTED.
 50/60 HZ - MODEL # A32060-10
 SIZE: 6.25"DIA. X 1 1/2"THICK
 BRAND NEW FACTORY BOXED.

**PRICE... \$14.95 EA.
 5 for \$60.00**



**3M STATIC CONTROL
 FLOOR & TABLE MATS**
 8200 series - 2 ft. X 5 ft mat
 3 LAYER CONSTRUCTION
 COLOR BROWN
 SPECIAL ... \$25.00



ROHM # SLR47VR3F
 RED LED T 1-3/4
 5MM DIFFUSED LED
 100 PCS. @ 10¢ EA.
 500 PCS. @ 7¢ EA.
 1000 PCS.@ 5¢ EA.



STEPPING MOTOR - AIRPAX
 100 STEPS/REV. = 3.6 Step angle
 *bi polar wound-
 bi-directional *2 PH
 *Torque 75 oz/in
 *SIZE: 1.5"SQ X 1 3/8"
 *3.2VDC *6.8AMP \$2.25



HE381

Power Products
 Linear power supply module
 Input: 115VAC 50/60 271 ma
 OUTPUT: 5VDC 5000 ma
PRICE .. \$20.00




CMOS EPROM #NMC27C256Q-200
 28 PIN DIP 256K (32 X 8)
 SPEED 200 NS
 LIST PRICE \$5.00

**BRIGAR
 PRICE.. \$1.75**



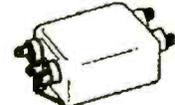CURTIS INDUSTRIES #F1200AA20
 10 AMP 250VAC - 20AMP 115VAC
 50/60HZ-size: 2"w x 2 1/2"l x 1 1/2"h
 .250" QUICK Connect terminals D.
 Brand new
 factory Boxed
**BRIGAR SALE
 PRICE \$3.50**



**TELEDYNE SOLID STATE RELAY
 PART # 615-8500**
 CONTROL VOLTS: 3-32VDC **TELEDYNE**
 RATED: 10AMP @ 250VAC
 50/60HZ -
 OPTO ISOLATED - SPST
 Connection: screw or
 quick Connects
PRICE... 1 - 99 PCS. 100 PCS - UP
 \$ 10.95 \$ 9.95



MEMOREX AUDIO PATCH CABLE
 6 FT. RCA MALE TO RCA MALE
 BLACK CABLE MOLDED ENDS.-
 MONO CABLE - BLISTER PACKED
 FOR DISPLAY. SALE PRICE.. \$1.00



3 COND 14 AWG
 * LENGTH: 4 FEET * O.D. .375"
 * COLOR: GREY * TYPE: SJT
 * CSA APPROVED
 * strip and untinned ends.
 Standard 3 prong molded plug.
PRICE \$1.25 EA.



**ASTROSYN MINIANGLE Stepper Motor
 #23LQ-C202-01H**
 *144 STEPS *30 oz in. Hold torque
 *BI POLAR - 2 PHASE
 *4 WIRE *1.9 Vdc/PHASE
 * 0.75 AMP/PHASE
 *WEIGHT 3/4 LB
 * SIZE: 1-1/2"H X 2-1/4"DIA
 *Mounting plate: 2-1/4"sq.
SPECIAL SALE.. \$12.95



CONTROL TRANSFORMER #522013
 * PRIMARY: 120VAC
 * Secondary 12V C.T. @ 4 AMP
 SIZE: 3 3/4"W X 3 1/2"H X
 3 3/4"DEEP
 BASE MOUNT
 WEIGHT: 7 1/4 LBS

PRICE. \$7.95




GRAY FLAT RIBBON CABLE
 #YP3301 50 COND. 28 AWG (7/36)
 .010" Thick pvc insul. 300V - 105 °c
 awm style 2651 mil-c-49055/1-13a
 ul approved .050 Cond. Spacing
 black polarity stripe. Will terminate to
 any standard idc connector -2.5"Wide
 Brand New Factory Boxed.
 ORIGINAL PRICE \$360.00
 300 FT. REEL ... \$69.00



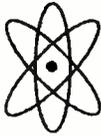LOOK FOR US SOON
 ON THE WEB AT
<http://www.binghamton.com/brigar/>





TECH-SYSTEMS

1309 Hwy. 71 Belmar, NJ 07719
908-280-0007 FAX: 908-280-0111

800-435-1516

BUY - SELL - TRADE
VISA & MasterCard Accepted

90 Day Warranty / 10 Day Right of Return

N.I.S.T. Traceable Calibration Available on Most Items

SPECTRUM ANALYZERS

TEK 492/D1/D2 Spectrum Analyzer 50KHz to 21GHz	\$6,995
Option D1 Adds Internal Preselection and D2 Adds Digital Storage	
TEK 492/D2 Spectrum Analyzer 50KHz to 21GHz	6,650
Option 21 18GHz to 40GHz Waveguide Mixer Set	1,775
TEK 496 1KHz - 1800 MHz. Spectrum Analyzer	4,750.
TEK 7L12 100KHz to 1800MHz Spectrum Analyzer Plug-In	1,850
TEK 7L13 1KHz to 1800 MHz Spectrum Analyzer Plug-In	2,495
TEK TR503 Tracking Generator w/TM503 Power Supply	1,450
HP 1411/B552B/B555A 10 MHz to 18GHz Spectrum Analyzer	2,195
HP 141T Variable Persistence/Storage Display	595
HP 140T Non-Storage Display	425
HP B553B 1KHz to 110MHz RF Section	450
HP B554L 100KHz to 1250MHz RF Section	550
HP B554B 100KHz to 1250MHz RF Section	795
HP B555A 10MHz to 18GHz RF Section	995
HP B556A 20Hz to 300 KHz LF Section	450
HP B552B IF Section	650
HP B552A Economy IF Section	295
HP B443A 0.1 to 110MHz Tracking Generator	550
HP B444A 0.1 to 1300MHz Tracking Generator	795
HP B444A/O59 0.5 to 1500MHz Tracking Generator	1,350
HP B445B 1.8 to 18GHz Preselector	650
HP 182T Mainframe	495
HP 182T/B557A 10KHz to 350MHz Spectrum Analyzer	1,495
HP 182T/B558B 100KHz to 1500MHz Spectrum Analyzer	3,350
HP B557A 10KHz to 350MHz Spectrum Analyzer Plug-In	1,250
HP B558B 100KHz to 1500MHz Spectrum Analyzer Plug-In	2,395
HP B559A 0.01 to 21GHz Spectrum Analyzer Plug-In	4,450

OSCILLOSCOPES

TEK 465 100MHz Portable Scope	\$595
TEK 475 200MHz Portable Scope	795
TEK 485 300MHz Portable Scope	995
TEK 2465 300MHz Portable Scope	2,595
HP 1741A 100MHz Portable Scope	495
HP 1725A 275Hz Portable Scope	695
HP 54200A 50MHz/200Msa/s Digitizing Scope	2,250
HP 54200D 50MHz/200Msa/s Digitizing Scope	2,650
HP 54201D 300MHz/200Msa/s Digitizing Scope	2,995
HP 54110D 1GHz/40Msa/s Digitizing Scope	5,995
HP 54111D 500MHz/1Gsa/s Digitizing Scope	6,995
TEK 7603 w/7A1B (X2) & 7B53A Scope	695
TEK 7104 w/7A29 (X2), 7B10 & 7B15 Scope	5,995

Over 600 TEK 7000, 5000 & TM Series Mainframes and Plug-Ins

Call for pricing information

WAVE - DISTORTION - MODULATION

HP 331A Distortion Analyzer 5Hz - 600 KHz	\$195
HP 332A Distortion Analyzer with AM Detector	295
HP 333A Distortion Analyzer with Auto Nulling & High Pass Filter	395
HP 334A Distortion Analyzer with Auto Nulling/High Pass Filter/ AM Detector	495
HP 35B1C Selective Level Meter	995
TEK AA501 Distortion Analyzer	1,295
BOONTON B2AD/D1/O3/O4 Modulation Meter	995
Marcconi 2305 2.32GHz Modulation Meter w/IEEE	4,995

STANDARDS & CALIBRATORS

FLUKE 5100B/O3/O5 Multifunction Calibrator	\$5,750
FLUKE 3330B DC Calibrator	1,995
FLUKE 515A Portable Calibrator AC/DC/RES	1,695
FLUKE 332B DC Calibrator	595
FLUKE 5205A AC Amplifier	2,650
FLUKE 5450A Resistance Calibrator 1 OHM to 100 megohms/Bppm	1,995
FLUKE 730A DC Transfer Standard	450
FLUKE 750A Reference Divider	450
FLUKE 720A Kelvin Varley Divider	1,895
ESI RV22 DC Divider 1ppm Accuracy	1,295
BOONTON 4200/30/BD Autocal AC Standard	2,495
BOONTON 25A Power Meter Calibrator	450
BOONTON 2500A Power Meter Calibrator	450
HP B477A Power Meter Calibrator	495
HP 11683A Range Calibrator	775
TEK PG506 Calibration Generator	1,350
TEK TG501 Time Mark Generator	1,350
TEK SG503 Leveled Sine Wave Generator 250KHz to 250MHz	1,350
TEK SG504 Leveled Sine Wave Generator 245MHz to 1050MHz	2,650
RFL B29G Multi-Function Calibrator	1,495

FREQUENCY COUNTERS

HP 5314A 100MHz Universal Counter	\$225
HP 5315B 100MHz Universal Counter	495
HP 5316A 100MHz Universal Counter	695
HP 5328A/D11/D30 512MHz/IEEE Universal Counter	695
HP 5328A/D11/D31 1.3GHz/IEEE Universal Counter	895
HP 5340A/D11 18GHz/IEEE Microwave Counter	1,950
HP 5342A/D11 18GHz/IEEE Microwave Counter	2,750
HP 5300B/5303B 525MHz Counter	450
HP 5257A Transfer Oscillator for HP 5245 Counters	175
HP 5255A 3 to 12.4GHz Frequency Converter	175
HP 5359A Time Synthesizer	1,895
SYSTRON DONNER 6054B 20Hz to 26.5GHz IEEE Microwave Counter	2,295
TEK DC5009 Programmable 135MHz Universal Counter	695
TEK DC505A 225MHz Universal Counter Plug-In	295
TEK DC508 1.3GHz Universal Counter Plug-In	450

SIGNAL SOURCES

HP 8640B/O03 512MHz Signal Generator w/Reverse Power	\$1,895
HP 8640B/O01/O02 1024MHz Signal Generator w/Audio Oscillator	2,795
HP 8656A 100KHz to 990MHz Synthesized Signal Generator	2,995
HP 8660C/86603A/86632B 2600MHz Synthesized Signal Generator	3,995
HP 8660A/86602A/86632B 1300MHz Synthesized Signal Generator	2,350
HP 8620C Sweeper Mainframe	395
HP 8622A 0.01 to 2.4GHz RF Plug-In	1,495
HP 8622B/O01 0.01 to 2.4GHz RF Plug-In w/Crystal Markers & 70dB ATTN	1,795
HP 86290C 2 to 18.6GHz RF Plug-In	2,395
HP 86260A 12.4 to 18GHz RF Plug-In	995
HP 8697A 26.5 to 40GHz RF Plug-In	1,450
HP 214B Pulse Generator	1,995
HP 8005B 20MHz Dual Pulse Generator	450
HP 8007B 100MHz Pulse Generator	695
HP 8013B 50MHz Dual Pulse Generator	695
HP 3312A 13MHz Function Generator	895
BOONTON 2000 20GHz Sweep Generator	2,450
TEK FG501 2Hz to 2MHz Function Generator	195
TEK FG502 1KHz to 11MHz Function Generator	295
TEK FG503 1 to 3MHz Function Generator	195
TEK PG501 50MHz Pulse Generator	250
TEK PG502 250MHz Pulse Generator	495
TEK PG508 50MHz Pulse Generator	795
APPLIED MICROWAVE/EPSCD PG5KB 5kW/575 to 925MHz RF Pulser	2,995
VELONEX 3B0 5kW High Power Pulser	2,995
COBER 605/P27 2kW/10Hz to 1MHz High Power Pulser	1,350

OVER 3000 ITEMS IN STOCK !

Inventory Changes Daily!

OVER 500 DC & AC POWER SUPPLIES !

Any Voltage - Any Current ! CALL

CALL FOR FREE 40 PAGE CATALOG

COMPONENT TEST

HP 4342A Q Meter (22KHz to 70MHz)	\$2,495
HP 4342A/O01 Q Meter (10KHz to 32MHz)	1,650
BOONTON 5110 LCR Meter 100Hz, 120Hz & 1 KHz Test Frequency	1,450
includes 5110-1 Test Adapter & 5110-4 Kelvin Clip Adapter	
BOONTON 72BD Digital Capacitance Meter 1MHz Test Freq. 2pF to 2000pF	750
TEK 57B Curve Tracer	2,995
TEK 577/D2 Curve Tracer	1,695
HUNTRON TRACKER 5000 Computer Controlled Troubleshooting System	1,350
SAUNDERS 150C/O9 Crystal Test Oscillator Microprocessor Controlled/IEEE/1 to 60MHz	1,695
GENRAD 1630AV Inductance Measuring System	2,995

**We Buy & Sell Service Manuals
Coax/Waveguide Components**

WANTED !

**Surplus Electronic Test Equipment
FAX US YOUR LIST**

FAX: 908-280-0111

Unbeatable Discount Prices

1 YEAR WARRANTY
15 DAY MONEY BACK GUARANTEE



MT-100
Reg. \$599.
\$419.00

Four Instruments in One Instrument

- Function Generator**
 - Sine, Square, Triangle, Pulse, Skewed Sine, Ramp, TTL
 - 0.2 Hz ~ 2MHz
- Frequency Counter**
 - 8 Digit LED
 - 1 Hz ~ 100MHz
 - ± (1 Hz + 1 dgt. + Time Base Error)
- Power Supply**
 - 3-1/2 Digit LCD
 - Triple output: #1. 0-50V, 0.5A MAX
 - #2, 15V, 1A #3. 5V, 2A
- Digital Multimeter**
 - 3-1/2 Digit LCD
 - DCV, ACV, Ω, DCA, ACA
 - ± (0.5% + 2 dgts)

FG-140 2MHz Function Generator
Reg. \$249. **\$149.00**



- 0.2 Hz ~ 2.0 MHz, 7 Decades
- Sine, Square, Triangle, Pulse, Ramp, Skewed Sine
- VCF, Symmetry
- Variable DC Offset Control

2MHz Sweep Function Gen. w/Freq. Counter

FG-150
Reg. \$399. **\$229.00**



- 4 Digit LED Display
- Sine, Square, Triangle, TTL, Pulse, Ramp, Skewed Sine
- Linear/Logarithmic Sweep
- 10 MHz Freq. Counter

1.0GHz Frequency Counter, High Resolution

FC-200
Reg. \$399. **\$219.00**



- 1.0 Hz ~ 1.0 GHz
- 8 Digit LED Display
- Auto & Manual Range
- 4 Selectable Gate Times
- 1MΩ & 50Ω Input Impedance

Oscilloscope Probe Set
Switch Selectable X1/X10



- HP-9060, 60MHz Reg. \$29. **\$17.00**
HP-9150, 150MHz Reg. \$49. **\$27.00**
HP-9250, 250MHz Reg. \$59. **\$37.00**



PS-500 DC Power Supply
Reg. \$249. **\$159.00**

- 0-30VDC
- 0.1-3A
- Short & Overload Protection




PS-540 DC Power Supply
Reg. \$399. **\$249.00**

- 0-16VDC
- 0.1-10A
- Short & Overload Protection

Deluxe O'scopes w/Phillips CRT.

"BEST BUY!"

OS-3304
Reg. \$499. **\$349.00**

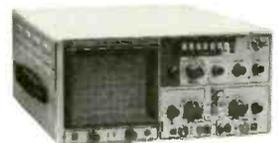

OS-3304 25MHz, Dual Trace

- DC to 25 MHz. Dual Channel
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
- Rise time 14n Sec. or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 2kV
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

OS-3324
Reg. \$599. **\$429.00**



OS-3324, 3 Function

- OS-3304
- Dual Component Tester/Comparator

OS-3344
Reg. \$899. **\$649.00**



OS-3344, 5 Function

- + 2 + 3 • OS-3324
- Frequency Counter 100MHz, 7 Digit LED Display
- Function Generator 0.02 Hz to 2.0 MHz

OS-3315 40MHz, Dual Trace Sweep Delayed
Reg. \$799. **\$549.00**



- DC to 40 MHz. Dual Channel
- Delayed Sweep 100nS to 1.0S 7 decade
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
- Rise time 8.5nS or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 12kV
- Variable Hold Off
- 16ns ~ 1.0s Time Base
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC



Bel MERIT
DM5050C
DM5100

Reg. \$149.
\$89.00

Including
Deluxe
Holster

Features (DM5050C/DM5100)

- Basic DCV Accuracy: ± 0.25%
- AC/DC Volt & Amp, Ohm
- Diode, Continuity Beeper
- Alligator Clip Test-Leads
- Lead Holders/Velcro Strap Holster

DM5050C, DMM + Capacitance

- 9 Function / 42 Range
- Multimeter
 - Ohm: Up to 2000MΩ
 - Amp: AC/DC 2 Amp
- Extended Capacitance Meter (9 Range)
 - 0.1pF - 20,000μF
 - Zero Adjust Knob
- Trig Lamp

DM5100, Wide Range w/Logic

- 11 Function / 45 Range
- Auto Power Off
- Data Hold & Peak Hold
- Freq: Up to 20MHz
- Amp: Up to 20A AC/DC
- Ohm: Up to 200MΩ
- Capacitance: 1p - 200μF
- Logic: TTL, TR hFE

Digital Engine Analyzer
Reg. \$119. **\$69.00**



- DM230**
- 3 1/2 Digit LCD
 - Engine Analyzer Taco, Dwell, Duty Cycle
 - DMM DCV, DCA, Ω
 - Temperature 0 ~ 1.999°F
 - Diode
 - Continuity
 - Holster, Temp. Probe, Clip Leads

Capacitance Meter
Reg. \$79. **\$49.00**



- CM210**
- 3 1/2 Digit LCD
 - 0.1p-20,000μF 9 Ranges
 - 0.5% basic Accu.
 - Zero Adjust Knob
 - Test Leads & Built in Socket

Pen-Type DMM w/Logic
Reg. \$79. **\$59.00**



- DM150**
- 3 1/2 Digit
 - Dual Display
 - Auto & Manual
 - DCV, ACV, ACA, DCA, Ω
 - Logic CMOS/TTL
 - Data Hold
 - Diode
 - Continuity

Multifunction DMM
Reg. \$99. **\$64.00**



- DM4050**
- 3 1/2 Digit
 - Basic Accuracy: 0.25%
 - Heavy Duty, 20A AC/DC Resistance 20MΩ
 - Capacitance
 - Freq. up to 20MHz
 - TR-hFE
 - Diode
 - Continuity
 - Deluxe Holster


BMC Your Best Source for
High Standard Electronics
P.O. Box 744, Lake Forest, CA 92630-0744

Order & Free Catalog
800-532-3221
(714) 586-2310 Fax (714) 586-3399



DELUXE TIMEBASE KIT


SALE

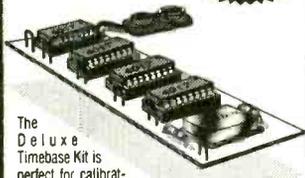

The Deluxe Timebase Kit is perfect for calibrating instruments, studying various instruments, viewing waveforms on an oscilloscope, etc. Features 5 separate outputs: 1MHz, 100KHz, 10KHz, 1KHz, and 100Hz. Uses a precision 1MHz crystal controlled oscillator and 4 CMOS ICs to divide the frequencies down to the lower frequencies. Very stable and precise. Operates from a 9V battery (not included). Size of PC board: 1 5/8" x 3 5/8". Complete with all parts, PC board and instructions. Skill level 2.

C6717 \$6.95

SUPER FAX "EYES & BRAINS"

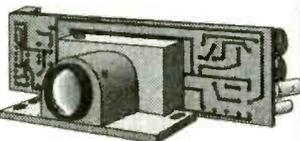

These are the "eyes and brains" of a fax machine. Consists of a small lens coupled to a circuit board containing the popular NEC UPD 794D or NEC 7990 charge couple optical scanning IC, resistors, capacitors, etc. We don't have the specs or schematics but for anyone building, repairing or experimenting with fax or optical scanning these are a must. Size about 1 5/8" W x 5 1/2" L x 2 3/4" thick. Sold as is only because these may have a damaged part or two.

G7317 \$6.95

100 WATT AUDIO POWER AMPLIFIER IC LM3875



High performance audio power amplifier IC capable of delivering 100 watts instantaneous peak output power or 40 watts continuously into an 8Ω speaker 20Hz-20KHz. Specs: signal-to-noise ratio - 95db(min), output short to ground protection, supply voltage min. - 20VDC, max. - 84VDC, thermal protection, spike protection. Great for stereo power amplifiers (requires 2 units), self-powered speakers, surround sound amplifiers, etc. TRA11B, 11 pin power package. Prime with specs and simple application circuit diagram.

G6943 \$4.50

CABLE READY PLUS™

NEW ITEM!



Back panel

These were made to restore the VCR features you like to use that your cable box takes away. Allows you to record a selected station tuned in on the cable box while watching a completely different one from your VCR tuner. Also restores PIP on TVs that have this feature!

We made a special closeout purchase of these units from the manufacturer as they will no longer offer this item (due to the fact that a few cable companies are scrambling the channels which prevents this device from working in some areas of the country). Because of this fact some of these may have been customer returns, however, they are like new and come with all accessories, and instruction manual in an attractive retail package!


Even if your cable company is scrambling the signal you'll want to own one of these as they have a very sleek black (6 5/8" x 5 1/8" x 1 3/8") metal and plastic case which can be used in making your own professional looking projects and has a built-in video amp with various electronic parts. Features a power on/off switch with red LED power on indicator, two 3' F to F cables, two 6' RCA to RCA cables, and an AC adapter.

Original Value \$129.95

Our Price Only \$14.95!

G7370

FOLDING STEREO HEADPHONES

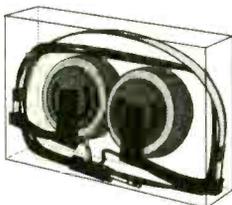

Compact high quality headphones fold for storage inside a standard size cassette case. Made by Gemini, these are not only comfortable but also have an excellent response. 20-20,000Hz, 90dB @ 1KHz. Weight of headphones only 1.5oz. Brand new in retail blister card.

G7018 \$3.95

PHONE ORDERS (602) 451-7454

IF YOU CAN'T FIND WHAT YOU ARE LOOKING FOR, CALL FOR A FREE COPY OF OUR LATEST CATALOG. THIS CATALOG CONTAINS OUR ENTIRE PRODUCT LINE OF ALMOST 4,000 ITEMS AND IT IS STILL GROWING!

AMPLIFIED FM ANTENNA

NEW ITEM!



Bring in those hard to receive FM stations with this attractive sleek design amplified FM antenna. Type FM600 by Gemini. High quality, brand new unit in manufacturer's box features gain control and AC adaptor with instructions. Blowout Price!

G7170 \$16.95

SUPER LED ASSORTMENT



YOU GET LEDs IN THESE COLORS:

- RED
- ORANGE
- YELLOW
- GREEN
- BLUE!

YOU EVEN GET A RARE BLUE!

Assortment of all types, colors, sizes and shapes of prime quality LEDs. This large assortment even contains a clear LED that lights up blue! Our largest and most spectacular assortment contains 250 pieces.

G6554 \$10.00

ANTISTATIC MAT




NEW ITEM!

Brand new beige colored antistatic mat. Has convenient snap attachment on left or right side of mat plus flexible coiled cord with clip to attach to your wrist strap. Great for use when changing out hard drives, working with computers, static sensitive ICs, etc. You get a 11 5/8" x 22" mat with 2 built-in snaps and a snap-on coiled cord with clip.

G7171 \$8.95

DELUXE SMD LEARN TO SOLDER KIT

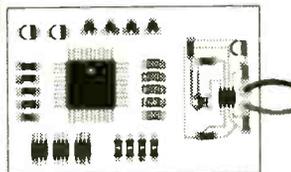

A great way to gain experience in soldering. Identification and use of Surface Mount Device (SMD) Technology. Includes a practice section and a working LED flasher. Uses 9V battery (not included). Size of PCB board: 2" x 3".

C6719 \$8.69

SECRET ALERT ALARM



Hide this attractive small size alarm in briefcases, medicine chests, drawers, cabinets, etc. and it will silently "stand guard". As soon as someone opens the briefcase drawer, cabinet, etc. it will start sounding a loud beeping sound. Operates on one 9V battery (not included) and uses a light sensitive IC circuit with built-in arming delay. The arming delay allows you 5 seconds to put the unit in a dark place after you arm it. Then, as soon as light strikes it (from someone opening the cabinet door etc.) the alarm sounds until it's once again in the dark. Great for warning you of intrusions into areas that children and intruders should stay out of. These have a Velcro® peel and stick piece on the back of each unit, that allows you to securely hold the unit to the back of a cabinet. Although these alarms are new, they were manufactured several years ago and the adhesive on the double stick velcro surface has dried out on the G6948 units which means on those units you'll have to use glue on the adhesive sides of the velcro if you wish to mount them (mounting is totally optional). The G6949 do not have this problem. Both types are electrically perfect it's only the velcro adhesive problem. Red plastic case is approximately 3" x 2 1/2" x 7/8".

G6948 (Bad Adhesive) \$2.00
G6949 (Good Adhesive) \$2.49

LASER LIKE LEDS

One of our brightest clear case jumbo T1 3/4 red LED produces a brilliant red output.

G6167 4/\$1.00

MISSILE/ARTILLERY NOSE CONE



UNIQUE ITEM!

We are not sure what these are from, perhaps a Howitzer shell or some military missile. What we do know is that they are brand new, hollow and made out of what we believe is spun aluminum that has been polished. They are precision made and have an inner threaded base with 4 small gripper points on the outside of the nose cone to tighten it onto the body of the missile. The overall size of nose cone is about 6 1/4" tall x 3 1/4" dia. at base. Brand new but may have some tarnish from being stored (just polish them up). Great conversation piece.

G7172 \$8.00 ea. 4/\$30.00

GIANT SMD ASSORTMENT



OVER 1,000 PIECES!

Our largest assortment of tiny SMD parts. You'll find prime LEDs, ceramic capacitors, resistors, transistors, diodes, tantalum capacitors, inductors, etc. in every package. Great way to stock up your parts bins at less than 1 1/2¢ a part! Over 1,000 pieces in a 2" x 3" zip close bag! **NOTE: Many SMD parts are so tiny that the manufacturer does not mark them, however, every part in this assortment is 100% prime and perfect.** Do a little detective work and save over a hundred dollars!

G7128 \$15.00

NOTE: All sale prices advertised are valid only through the month of the cover date.

For Phone Orders Call (602) 451-7454 or Fax Your Orders to (602) 451-9495




Minimum Order: \$10.00 (plus \$5.00 Shipping and Handling). We accept MasterCard, Visa and personal checks, however, we cannot accept personal checks on orders outside the United States. Canadians and orders that need US MAIL send minimum \$5.00 S&H. Minimum Foreign Order Amount: \$50.00 (plus shipping and handling).

ELECTRONIC GOLDMINE
PO Box 5408
Scottsdale, AZ 85261


AMAZING Electronic and Scientific Products

Mystery Levitating Device!

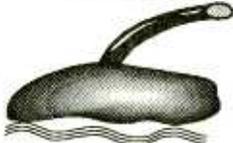

Remember War of the Worlds? Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or great science project.

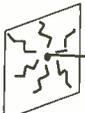ANT1K Easy to Assemble Kit / Plans \$19.50



Laser Ray Gun


DANGER
 DANGEROUS LASER RADIATION
 AVOID EYE OR SKIN EXPOSURE
 TO DIRECT OR BOUNDED RADIATION
 CLASS IV LASER PRODUCT



Advanced project produces a burst of light energy capable of burning holes in most materials. Hand-held device uses rechargeable batteries. 500 joules of flash energy excite either a neodymium glass, yag or other suitable 3" laser rod. This is a dangerous CLASS IV project (individual parts/assemblies available). LAGUN1K Plans \$20.00

LAGUN1K Kit / Plans Price on Request

Extended Play

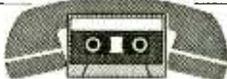

Telephone Recording System

READY TO USE! Automatically controls and records on our X-4 extended play recorder, taping both sides of a telephone conversation. Intended for order entry verification. Check your local laws as some states may require an alerting beeper.

TAP20X Ready to Use System \$129.50



Shocker Force Field/ Vehicle Electrifier

Neat little device allows you to make hand and shock balls, shock wands and electrify objects, charge capacitors. Great payback for those wise guys who have wronged you!

SHK1K Easy to Assemble Electronic Kit \$29.50



Electric Charge Gun

All New Technology!



Stuns/immobilizes attackers up to 15 feet away!

*Legal in most state (not in NY, NJ, MA, WI) • More knock-down power than most handguns • No permanent injury • ID coded • Free 80KV stun gun with every purchase.

ECG1 Data Packet, Creditable toward purchase \$10.00

ECG10 Charge Gun, Ready to Use, w/Free 80KV Gun \$249.50

Homing / Tracking Transmitter

Beeper device, 3 mile range.

HOD1 Plans \$10.00 HOD1K Kit / Plans \$49.50

Listen Through Walls, Floors

Highly sensitive stethoscope mike.

STETH1 Plans \$8.00 STETH1K Kit/Plans \$44.50

Infinity Transmitter ++



Telephone Line Grabber/ Room Monitor / Controller

All New - The Ultimate in Home/Office Security & Safety!

Simple to use! Call your home or office, push a secret tone on your telephone keypad to access: • On premises sounds and voices • Ongoing phone conversation w/break-in capability • Up to 10 external electrical functions, lights, TV, alarms, coffee pots, heater, etc. CAUTION! Check legality with your state's attorney general's office before use for monitoring of voices.

TELECON1K Kit, includes PC board \$149.50

TELECON10 Ready to Use \$199.50

Visible Beam Laser

Easy to build, RED Beam, visible for miles. Use for light shows, window bounce holography, cloud illumination and much more! LAS1KMC Kit w/1mw Laser Tube, Class II \$69.50

LAS3KMC Kit w/2.5mw Laser Tube, Class IIIA \$99.50

Life is Precious - PROTECT IT!

Hard hitting, crackling, sizzling HIGH VOLTAGE plasma! Stuns and immobilizes most attackers

STUN200 Ready to Use, 200,000V \$69.50

STUN120 Smaller Unit, 120,000V \$39.50

NEW High Power Ion Ray Gun

Projects charged ions that induce shocks in people and objects without any connection! Great science project as well as a high tech party prank. IOG7 Plans \$15.00

IOG7K Kit/Plans \$99.50

Invisible Pain Field Generator

Shirt pocket size electronic device produces time variant complex shock waves of intense directional acoustic energy, capable of warding off aggressive animals, etc.

IPG7 Plans \$8.00 IPG7K Kit/Plans \$49.50

IPG70 Assembled \$74.50

1000 Ft++ Potato Cannon

NOT A TOY. Uses electronic or piezo ignition. CAUTION REQUIRED!


POT1 Plans (Dangerous Product) \$10.00

FireBall Gun

Shoots flaming ball - two shot capacity Great for special effects and remote fire starting. CAUTION REQUIRED!

FIREBALL Plans (Dangerous Product) \$10.00

TV & FM Joker / Jammer

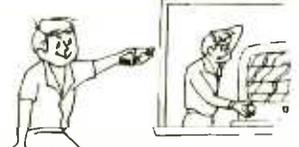

Shirt pocket device allows you to totally control and remotely disrupt TV or radio reception. Great gag to play on family or friends. Discretion required.

EJK1KM Easy to Assemble Electronic Kit \$24.50

ATTENTION: High Voltage Fans!

4,000 volts in the palm of your hand! Experiment with anti-gravity, hovercraft, ion guns, force fields, plasma guns, shock devices, wireless energy and electrical pyrotechnics. Input: 9-14VDC.

MINIMAX4 Ready to Use \$19.50



"Laser Bounce" Listener System

NEW - Latest Technology! Allows you to hear sounds from a premises without gaining access. Aim at room window and listen to sounds from within via reflected laser light. Not for illegal use. Requires video tripods.

LWB3K 5mw Laser and Receiver Kit \$149.50

LWB30 Ready to Use \$199.50

5mw Visible Red Pocket Laser

Utilizes our touch power control!

VRL5KM Kit / Plans \$74.50

Electronic Hypnotism

Puts subjects under control using highly effective electronic stimuli. Intended for parties and entertainment but must be used with caution. Includes valuable text book reference and plans.

EH2 Plans and Text Book \$19.50

Automotive



NEON

Easy-to-Install 4-Tube Kit for Cars, Trucks, Vans! Available in Pink, Purple, Blue or Green - please specify color when ordering.

RG4K (Specify Color) \$129.50

Flash-To-Music Option for above kit FMU1 \$29.50



License Frame Kit (Specify Color) LIC1K \$24.50

3 Mi FM Wireless Microphone



Subminiature! Crystal clear, ultra sensitive pickup transmits voices and sounds to FM radio. Excellent for security, monitoring of children or invalids. Become the neighborhood disk jockey!

FMV1 Plans \$7.00 FMV1K Kit and Plans \$39.50

Telephone Transmitter - 3 Mi

Automatically transmits both sides of a telephone conversation to an FM radio. • Tunable Frequency • Undetectable on Phone • Easy to Build and Use • Up to 3 Mile Range • Only transmits during phone use. VWPM7 Plans \$7.00

VWPM7K Kit/Plans \$39.50

Dept ENS-19, Box 716, Amherst, NH 03031

Phone: 603-673-4730 FAX: 603-672-5406

MC, VISA, CDD, Checks accepted Please add \$5.00 Shipping & Handling

CATALOG

With many more items! Free with Order or send \$1 P&H

Order by Mail or by 24 Hour Orders-Only Phone 800-221-1705

INFORMATION UNLIMITED

DIGITAL is the FUTURE
Introducing...

“The New Kid on The Block”



18" Digital Dish

The
Dish is Small
The
Programming
is BIG

We've been hearing a lot lately about the new little dishes. The DISHSM Network System is the latest, and he arrived as a shining star. He is small, attractive and the latest in technology, but what really sets him apart is the programming he delivers to your Television screen.

The DISHSM Network is chock full of the most popular programming at prices much lower than the competition. Call us now for more information. Digital just may be in your future.



Beat The Rush Call Now
800-500-9264
Special Digital Hotline

30%-60%
Savings
Compared to
Other Digital
Programming

If you have one of these. . .
“Keep it Running Strong”
With a Discount Buyers Guide


If you are the owner of a C/Ku-band Full View Satellite System we know you'll want to keep it up and running strong. The Skyvision Discount Buyers Guide will give you advice and products to get job done right.

You Will Find a Wide Selection of:

- Complete Systems
- Advanced Upgrades
- Parts & Accessories
- Tune Up Tools & Advice
- Technical Tips Galore
- Discount SkyPac Programming

For Your Free Issue Call Now
800-543-3025

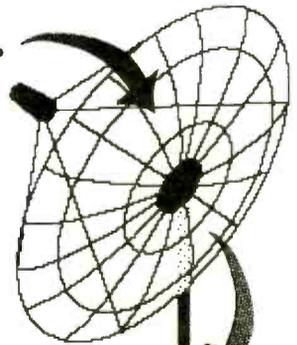Need a repair item Fast??
“We'll Get It Out Today”



The most complete
Big Dish Satellite
Discount Buyer's Guide!
Get your FREE copy now

DO-IT-YOURSELF AUDIO AMPLIFIER KITS

Mark V Electronics, Inc.
8019 E. Slauson Ave.,
Montebello, CA 90640

In business since 1985

Mention AD and
take 10% off your
1st order!

Enclosures at Unbeatable prices !

Free Catalog 213/888-8988 Fax 213/888-6868

Order 1-800-521-MARK / 1-800-423-FIVE

Kit skill levels are specified as ▲ beginner ▲▲ intermediate or ▲▲▲ advanced!

Best Buy

Metal Cabinets with Aluminum Front Panel

LG-1273 3x12x7" \$ 26.50
LG-1684 4x16x8" 32.50
LG-1924 4x19x11 1/2" 38.25
LG-1925 5x19x11 1/2" 42.00
LG-1983 2 1/4x19x8" 35.25
LG-1923 3x19x11 1/2" 36.50
LG-1927 7x19x11 1/2" 50.50

LG- Black anodized rack cabinet

Modular Desktop Consoles

L x W x H
LE-453 4x4 3/4x3" \$ 7.50
LE-653 6x4 3/4x3" 9.75
LE-853 8x4 3/4x3" 11.75
LE- Black finished aluminum panel 1mm thick.

Alarm Box with Lock

LB-1085 8 1/2x10 1/4x5" \$ 18.75
LB-1395 9 1/4x13 1/4x5" 25.50
LB-1525 12 1/2x15 1/4x5" 35.25
*LB-1494 9 1/4x14 1/4x4 1/4" 21.50
LB-1383A 8 1/2x13 1/4x4" 23.25

*No lock & LB- Sheet Metal 0.8mm

Mejor Compra !

New

*LL-1923B 2 1/4x19x12" 69.50
*LL-1925A 5x19x12" 79.50

*LL- High quality full Aluminum Cabinet
*LL- Front panel .157" & other panels .078"
*LL- Gold plated cap screw for front panel

- Dimensions in inches ± .05
- Custom-made for other dimensions if over 100 pcs for single model !

Camera Housing

*LD-1244 2 1/4x10 1/4x4" \$55.00
*LD-1516 3 3/4x13 3/4x4" 29.50
*LD-1565 4x13 3/4x5 1/4" 31.75
*LD- Stainless Steel 0.7mm
*LD- Sheet Metal 1mm

Power Transformers & **Toroidal Transformer

001 28/30V x 2 6A \$ 30.00
002 36V x 2 3A 25.00
003 40V x 2 6A 32.00
**008 28/30V x 2 6A 40.00
**009 48/53V x 2 8A 66.00
**012 33/40/42Vx2 6A 48.00

TA-800MK2 ▲▲ 120+120W Pre & Main Stereo Amp. (4 lbs.)



Kit: \$ 67.92
Asmb. \$ 86.95

Power Output: 120W into 4 ohms RMS. 72W into 8 ohms RMS. Frequency Response: 10-20KHZ. THD: <0.01%. Tone Control: Bass ±12dB, Mid & Treble ±8dB. Sensitivity: Phono Input, 3mV into 47K. Line, 0.3V into 47K. Signal to Noise Ratio: 86dB. Power Requirement: 40VDC @ 6A. Suggested Mark V model 001 or 008 transformer. Recommended Metal Cabinet LG-1924.

TA-28MK2 ▲ Digital Voice Memo



Kit: \$ 25.00

Asmb. \$ 9.90
Internal 8-bit AD/DA converter with alias filter. Sensitive electret microphone. Offers choice of 8 or 16 seconds recording time by changing the sampling frequency. Has internal 256k memory. Simple operation - LED shows operation mode. Operates on 5 to 6 volt battery or AC adaptor.

AF-3 ▲▲▲ 300W MOSFET High Power Mono Amp. (7 lbs.)



Kit: \$ 165.00 Asmb. \$ 195.00

Power Output: 300W into 4 ohms RMS. 200W into 8 ohms RMS. Frequency Response: 10HZ-20KHZ. THD: <0.03%. Signal to noise ratio: 91dB. Input Sensitivity & Impedance at 1KHZ, 1V 47K. Load Impedance 4-16 ohms. Power Requirement: ±55 to ±65VDC 8A. Suggested Mark V model 009 Transformer. Capacitor 10,000uf 80-100V model 016 or 019. Recommended Metal Cabinet LG-1925 for each channel.

TR-503 ▲ Regulated DC Power Supply



Kit: \$ 18.75 Asmb. \$ 27.65

It is short circuit proof and has overload protection. Output voltage is variable over a range of 0-50V. Current limit trip is adjustable up to max of 3A. Suggested Mark V 002 transformer. (1 lb.)

TA-388 ▲▲▲ Class A FET Dynamic Buffer Stereo Pre-Amp (1 lb.)



Kit: \$ 64.00 Asmb. \$ 80.00

Frequency Response (at rated output): Overall 10HZ-100KHZ +0.5dB-1dB. THD: Overall <0.007% at or below rated output level. Channel Separation (at rated output 1KHZ): Overall better than 70dB. Hum & Noise: Overall better than 90dB. Input Sensitivity (1KHZ for rated output): 300-600mV. Maximum Output Level: Pre-Amp output 1.8V (0.1% THD). Power Requirement: 30V X 2 AC 500mA.

SM-302 ▲ 60+60W Stereo Power Amp



Kit: \$ 75.00
Asmb. \$ 94.00

It provides 3 input jack pairs. One pair accept a high impedance microphone. The two remaining pairs are for high & low level input sources. Power Output: 60W per channel into 4 ohms RMS. 20HZ-20KHZ. THD: <0.1%. Input Sensitivity: Mic/Guitar 10mV, Hi 380mV, Lo 640mV. Ready to plug in when assembled. (11 lbs.)

SM-100 ▲▲ 150 MHZ 8 Digit Frequency Counter (2 lbs.)



Kit: \$ 79.00 \$ 65.00
Asmb. \$ 99.00

Sale

Frequency Range: 10HZ-150MHZ. Gate Time: 0.01s, 0.1s, 1s, 10s. Input Sensitivity: KHZ range 10HZ-10MHZ 20mV(min.). MHZ range 1MHZ-120MHZ 20mV(min.), 120MHZ-150MHZ 35mV (min.), 150MHZ-200MHZ 40mV(typical). Time Base: 10MHZ crystal, ±10 ppm. Input Impedance: 1M ohm. Response Time: 0.2s. Resolution: 0.1 HZ: 10s gate time, 1HZ: 1s gate time, 10HZ: 0.1s gate time, 100 HZ: 0.01s gate time. Hold the last input signal. Reset counter to 0. DC 9V power adapter not included.

School Project Kits Source

SM-36 Dynamic Noise Reduction ▲ \$ 26.00
TA-006 6W Mini-Amplifier ▲ 9.50
TY-13 20 Color LED Level Meter ▲ 9.90
TA-120 36W Class A Power Amp. ▲▲ 32.50
TA-201 Microphone Mixer Mono Amp. ▲ 20.79
TY-45 20 Bar/Dot Level Display ▲▲ 38.25
TY-2 Fluorescent Light Driver ▲ 14.75

See our catalog for more kits!

Minimum order \$ 20. We accept Visa, MasterCard & Money Orders. Checks allow 2 weeks for clearance. We ship by UPS ground inside US (min \$ 4.00) and ship by US mail outside US. Please call for orders shipping & handling or fax foreign orders. PO Orders are welcome from schools. We are not responsible for typographical errors.

CIRCLE 223 ON FREE INFORMATION CARD

DALBANI

the ultimate saving source

For over then ten years, **DALBANI CORP.** was, and still the ultimate saving source . **DALBANI CORP.** is a national and International distributor of quality electronic parts and components servicing the wholesale, retail and manufacturing industry.

Since finding the parts you need should not be a major task, **DALBANI CORP.** maintains a huge stock of the most popular parts that are hard to find. Our service, low prices and quality reflects our commitments to our customers.

DALBANI CORP. keeps customers informed of the latest new items, that gets to our warehouse, thru publications. The multilingual sales dept. coupled with the state of the art computerized order processing, enable us to offer prompt and efficient service to benefit the customer.

We, offer many shipping options. Company checks, COD's, Cash and major credit cards are accepted. There is a \$20.00 minimum order.

We meet our customer needs



For a free 192 catalog please call

Toll Free 1-800-325-2264



**Digital
Multimeter**



**Large Line Of
Semiconductors**



Oscilloscopes



VCR Heads Replacements



**Soldering
Equipments and Tools**



4225 NW 72nd. Miami, Florida 33166

Telephone : (305) 716-1016 or Fax : (305) 594-6588

Business Hours : monday thru Friday 9:00 am to 7:00 pm eastern time

CIRCLE 234 ON FREE INFORMATION CARD

Toronto

Surplus

& Scientific Inc

608 Gordon Baker Rd. Willowdale,
Ontario Canada zip: M2H-3B4

TEL: (416) 490-8865



OFFICE: (905) 887-0007 FAX: (905) 887-0006

SORRY, WE DON'T HAVE A CATALOG YET. CALL OR FAX US FOR SPECIFIC ITEMS. WE'RE ALWAYS GETTING 'NEW' STUFF!

**WALLACE & TIERNAN
PRECISION PRESSURE
GAUGE**



0-10 inches of WATER (new)
Super nice, finest made. \$85.00ea

**PRC-66
BATTERIES**



Contains 80 Energizer
"AA" Alkaline cells
\$10.00ea

**MINIATURE
TAUGHT-BAND RATE
GYRO (NEW) \$20.00**



**ARC 116 UHF
POWER**



**AMPLIFIER (NEW)
\$75.00**

**SCOTCH-LITE
REFLECTIVE TAPE**
3.5in wide



(HIGH INTENSITY)
\$1.00/ft or
\$100.00/150ft roll.

**RF COAXIAL SWITCH
TNC Connectors (NEW)
\$24.00**



**HIGH VOLTAGE
VACUUM CAPACITORS
\$20.00ea**



**GIBSON GIRL emergency
transmitting set AN/CRT-3
COMPLETE UNIT \$275.00**

**5 Mw LASER TUBE
IN MOUNT \$65.00**



SIMPSON 635 VOM



Used
but
good
condition, not tested
with case: \$35.00

100pf
@ 20kV or 250pf @ 5Kv

**MINIATURE DC HOUR
METER \$27.50ea**



**RECTIFIER/RELAY
KIT: Motorola rectifier
MR1265FL300V @700
AMP (new).
\$22.00**



**CHATILLON
FISH SCALE**


0-30lbs or 0-15kga
\$35.00

**24VDC FAN 5" x 5"
\$10.00**




**HEWLETT PACKARD
8640B SIGNAL GENERATOR**

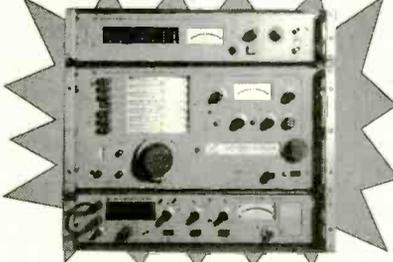Industry Standard sig-gen 500Khz-512Mhz fea-
tures internal phase lock/synchronizer and digi-
tal freq readout. +19to -145 dBm output.
AM,FM,Ext and Pulse modulation.
Price: \$1695.00 OPT 001 add \$100.00
OPT 003 add \$150.00



**ROHDE & SCHWARZ
SMDA 41314
AM/FM SIG GENERATOR**

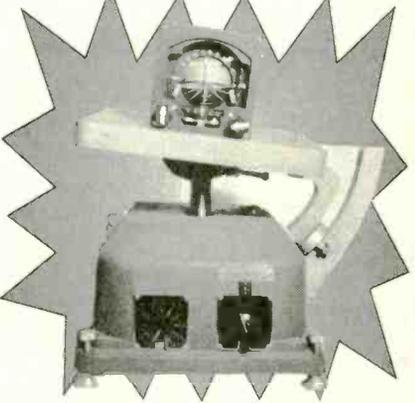This high performance generator operates from
0.4Mhz-484Mhz. Modes of operation are AM,
FM with 12 standard mod freq's of 3-6KHz.
S/N ratio typ 130 dB at 20 KHz from carrier.
This unit is supplied with the BN413115 Freq-
control unit (phase lock) and VOR/ILS test
generator. Very nice stuff for connoisseurs of
fine German made test equipment.
Price: \$995.00



**IDEAL AEROSMITH INC.
GYRO SCORSBY TABLE**

Model 1411BVS-30 scorsby table with digital
speed and direction control. Features include auto
reverse in the oscillate mode and nice quiet opera-
tion. The flight director (sitting on the table) is
mfg'd by Litton Systems or Astronautics. These
are great for simulators or just foolin' around.
What's so great is that both axis are driven by D.C.
servo motors that allows operation from a com-
puter with slight modification for feedback. They're
certainly the neatest precision instrument.
Scorsby Table Price: \$1595.00
Flight Director Price: \$ 195.00




**HEWLETT PACKARD HP3312
SWEEP/FUNCTION GENERATOR**

Well designed and easy to use, this function
generator combines economy and quality into
one compact unit. Freq range is 0.1Hz-13MHz,
output into 50 ohms is 10.0VP-P. Sweep-
AM,FM, or tone burst. This unit features-sync.
out, trig. phase, symmetry, offset and more.
Price: \$935.00 ea. Fully checked.


**All Prices in U.S. Dollars
Please include telephone/fax
number with mail-in orders.
Orders must be prepaid by
guaranteed instrument.**

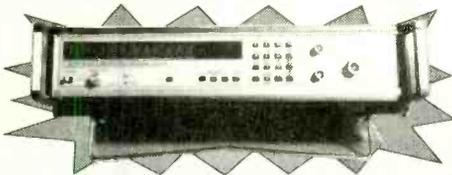Manuals available at extra cost
CIRCLE 229 ON FREE INFORMATION CARD



**MICROWAVE FREQUENCY COUNTER
EIP MODEL 545A**

The 545A easily covers 10Hz-18GHz frequency range with -30dbm relative sensitivity and 10 watt (+40dB) input damage protection. In addition, the 545A also measures RF power to 0.1 dB with an overall accuracy of 0.5dB. The unit comes with internal ovenized oscillator. Like-new condition. Price: \$2295.00

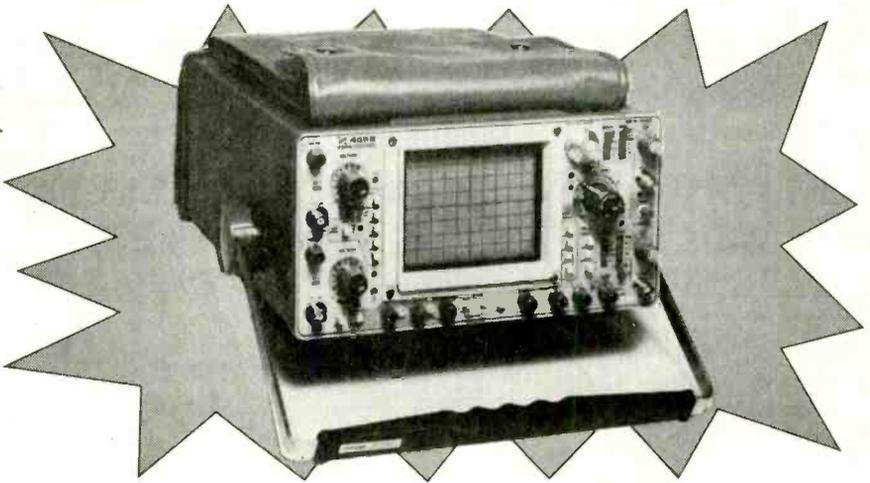

TEKTRONIX 465B

Proof is in the pudding when it comes to this instrument's track record. There's no doubt, that popularity speaks many languages when speaking of the "465B" or 465M. This excellent instrument continues the tradition of the standard 465 oscilloscope by adding useful features such as CH-1, CH-2 sum or difference, trigger view in any combination, alternate sweep and trace selection versatility. Many technicians dream of owning a quality 100-MHz oscilloscope, but funding rarely permits. Fortunately, we were recently able to acquire a limited supply of 465B-s in nearly new condition. Our *LOW PRICES* will likely permit "you" to own one of the best scopes anywhere in the country. If your need is current and action *swift* you too will be a member of a growing club!!!

**SELECTED EXCELLENT COND.....\$849.00
TEKTRONIX 465-M. 100MHz.....\$695.00**

These instruments are fully checked out. They are supplied with an original front panel cover and complete service manual. Original TEK Probes are \$75.00 each with each purchase.



MILITARY STANDARD D.C. GENERATOR


Superior QUALITY plus rugged design are features of this deluxe 2 cylinder 4 stroke gasoline generator. The control panel contains meters for voltage & current indication, main circuit breaker and voltage adjustment. Shielded wires and plugs comprise the RFI suppression ignition system eliminating most radio noise. These units are "new" in the original carton complete with operators manual and only require fuel and oil for operation; output voltage is adjustable approx. 10-32v (28v nom) @ 53.3A (1.5Kw) continuous duty load.

Price: \$379.00 New in Orig. Carton.
You will be impressed!!!!

**COLLECTOR ALERT - \$39.00
8-DAY AIRCRAFT
CLOCK
1-7/8" dial**



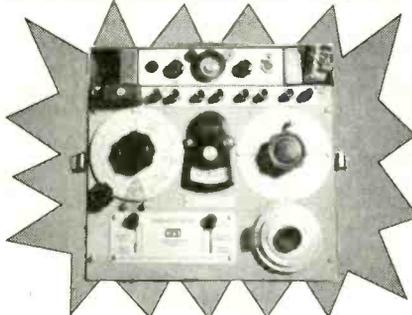Great collectors item for the ham shack, fifties vintage funct/chkd.



**ESI MODEL 250 DA
IMPEDANCE BRIDGE**

Resistance range- 0.1 milliohms - 11 megohms, capacitance 0.1pf-1100mf, inductance 0.1 μH to 1100 Hy. Dissipation factor (R/X or D) 0.001 to 1000. Internal oscillator 1 KHz.

Used, not functionally checked.....\$95.00
Functionally checked.....\$165.00



**"SERIOUS" POWER SUPPLY
TCR 20S135**

Output voltage is adjustable from 0-20V With a current limited maximum output of 135 clean DC amps. Digital LCD meters present both voltage and current along with LEDs for CC or CV operation. These units are currently wired for 220v operation but can be reconfigured for 110v operation. They're good & heavy but lightly priced at: \$895.00 Good condition.

-HP 351A TRANSMISSION TEST SET	\$ 950.00	-CROWN MODEL 7560 1KW PWR AMP. DC - 40KHz	\$1,800.00	-EATON NM-17/27A EMI FIELD INT. METER	\$1,500.00
-HP 3581A WAVE ANALYZER	\$1,295.00	-DATRON 4000A DC & OHMS CALIBRATOR	\$4,500.00	-FLUKE 5100A CALIBRATOR	\$3,800.00
-HP 4260A LCR BRIDGE	\$ 385.00	-WILD RC-8 AERIAL PHOTOGRAPHY CAMERA	\$ 950.00	-KIKISUI POWER SUPPLY 0-110Voutput @ 60ADC	\$2,500.00
-HP 4948A IN-SERVICE TIMS (brand new)	\$3,995.00	-ENI MOD 310L 250KHz-110MHz @ 50db GAIN	\$ 565.00	-AN12060 AMPLIFIER FOR PRC 25	\$ 175.00
-HP 5006A SIGNATURE ANALYZER	\$ 450.00	-ENI MOD 406L 150 KHz-250MHz @ 40db GAIN	\$ 650.00	-BOONTON 824D AM/FM MOD-METER	\$1,275.00
-HP 5315A UNIVERSAL COUNTER (1 GHz)	\$ 675.00	-GOULD 220 CHART RECORDER	\$ 750.00	-BOONTON 102F SIG. GEN. 1040MHz	\$1,295.00
-HP 54111D COLOR DIGITAL STORAGE SCOPE	\$5,500.00	-GOULD RS 3800 PROGRAMABLE CHART RECORDER/w MOD 5900 SIG CONDITONER & DC AMPS (NEW)	\$6,500.00	-COLLINS 651S-1 RECEIVER	\$1,250.00
-HP 6472C POWER SUPPLY 0-64V @ 0-150A	\$1,800.00	-III- ENERGY CORP. DISCHARGE CAP. 1μF @ 20KV \$ 300.00 140μF @ 6KV	\$1,000.00	-GRT-22 UHF POWER AMPLIFIER	\$ 200.00
-HP 8160A OPT-20 PROG PULSE GEN	\$2,995.00	-MARCONI 2018 SYNTHESIZED SIGNAL GENERATOR 80KHz - 520MHz	\$1,750.00	-HARRIS RF280 HF/TACTICAL TRANSCEIVER	\$1,500.00
-HP 8505 NETWORK ANALYZER SYSTEM	\$6,000.00	-ROHDE & SCHWARZ SIG GENERATOR. 4-484MHz \$ 750.00		-R392 RECEIVER -5.30MHz	\$ 165.00
-HP 8558B SPECTRUM ANALYZER .01-1.5GHz	\$2,350.00	-SCHENCK DYNAMIC BALANCING MACHINE MOD CAB570 WITH- BED . SENSORS & MANUAL	\$4,500.00	-T195 100w COMPANION XMTR TO 392	\$ 85.00
-HP 8559A SPEC-ANALYZER .01-22GHz	\$4,995.00			-WAVETEK 3002 RF SIG. GENERATOR	\$ 795.00
-TEK FG-504 FUNCTION GENERATOR (40MHz)	\$ 875.00			*****ATTENTION DIVERS-GAS DRIVEN COMPRESSORS*****	
-TEK 1502 TDR w/CHART REC	\$2,200.00			-BAUER 11CFM 3500 PSI COMPRESSOR SYSTEM	\$3,500.00
-TEK 2465 300 MHz OSCILLOSCOPE	\$2,750.00			-BAUER K14 3500 PSI COMPRESSOR SYSTEM	\$2,750.00

Books that work the way you work... SPECIAL OFFER

No obligation



NEW FROM JOHN LENK



1996, paperback
~~\$29.95~~ \$26.95
0-7506-9821-7



1996, paperback
~~\$29.95~~ \$26.95
0-7506-9510-2



1996, paperback
~~\$29.95~~ \$26.95
0-7506-9820-9




June 1996, paperback
~~\$29.95~~ \$26.95
0-7506-9508-0

Butterworth-Heinemann brings you something for everyone from John Lenk's Simplified Design Series. These books are all-inclusive, one-stop guides. Each has step-by-step instructions and diagrams that make it easy-to-use for the student, experimenter, and professional. All are available in paperback.



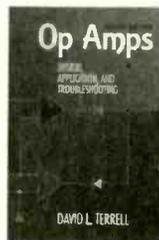
1995, hardcover
~~\$49.95~~ \$44.95
0-7506-9505-6



1996, hardcover
~~\$49.95~~ \$44.95
0-7506-9702-4



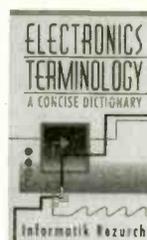1995, paperback
~~\$29.95~~ \$26.95
0-7506-9694-X



1996, paperback
~~\$12.95~~ \$10.95
0-7506-9751-2




1996, paperback includes disk
~~\$39.95~~ \$35.95
0-7506-9700-8



July 1996, hardcover
~~\$49.95~~ \$44.95
0-7506-9747-4



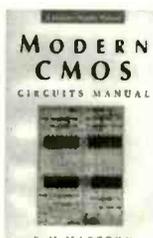
1995, paperback
~~\$47.95~~ \$42.95
0-7506-2489-2



1996, paperback
~~\$28.95~~ \$25.95
0-7506-2565-1



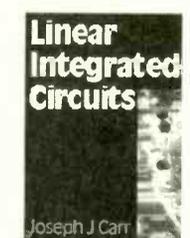1995, paperback
~~\$47.95~~ \$42.95
0-7506-2281-4



1996, paperback
~~\$37.95~~ \$33.95
0-7506-2591-0

Please send me the book(s) listed below at 10% off! Phone: 1-800-366-BOOK FAX: 1-800-446-6520

Please add \$4.00 for handling for the first item ordered and \$1.50 for each additional item ordered to all check and credit card orders. Billed orders will be charged additional shipping based on weight and destination. All US orders must include your state sales tax. Prepayment or company purchase order is required for all orders. Canadian customers please pay by credit card or in US funds and include 7% GST on books and handling. Prices subject to change without notice.

Write book number(s) here

--	--	--	--

Charge my: VISA AMEX MC Card # _____ EXP Date _____

Name _____ Signature _____

Address _____ City/ State/ ZIP _____

Tel _____ E-mail _____

Visit us on the Internet @ <http://www.bh.com/bh/el>

Send me a FREE catalog (item 642)



313 Washington Street, Newton, MA 02158
from outside US and Canada, call 617-928-2500


TS123

CIRCLE 215 ON FREE INFORMATION CARD

BLACK FEATHER ELECTRONICS

VIDEO CLARIFIER

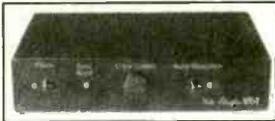ELIMINATES ADVERSE EFFECTS OF VIDEO COPY-GUARDS!




State-of-the-art circuitry restores original (master) quality to all video tapes. Allows for flawless viewing of all prerecorded video's whether rented, purchased or produced at home (even copy-protected tapes), for your personal home use. Unique auto Sync Boost feature eliminates horizontal instability and restores tapes to broadcast quality. Noise Reduction Circuit filters out the "snow" and other annoying interference. Compatible with all VCRs and T.V.s. includes AC adapter.

CAT #VC-1 **\$59.95 each**

ULTRA-MINI FM RADIO

WOW! SOUNDS GREAT!

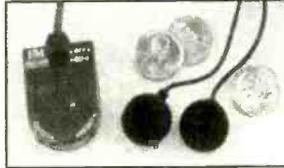


Fit an entire orchestra in the palm of your hand and still have room for the concert tickets with this Mini FM Radio that has an incredible sound. Features on/off button, seek button and reset button. Includes battery. If this isn't the world's smallest, it's close to it. But the sharp, clear sound that comes out will make you think you have a jam box. Black.

CAT #FM-1 **\$19.95 each**

3 1/2 DIGIT PANEL METER


This meter has many useful applications such as Voltmeter, Thermometer, Db Meter, Watt Meter, Current Meter, Capacitance Meter, Lux Meter and LCR Meter. Features include: 200mV full scale input sensitivity, single 9VDC operation and decimal point selectable. In addition, it has 13mm figure height, automatic polarity indication, guaranteed zero reading for 0 volt input and high input impedance (>100M ohms). Specifications: Max input 199.9mV DC-Max. Display: 1999 counts (3-1/2 digits). Measuring method: Dual slope integration A-D converter system, plus many other features.

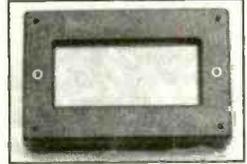

CAT #PM-1 **\$9.95 each**

STEPPER MOTOR CONTROLLER KIT

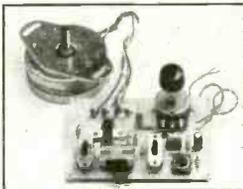This kit allows you to adjust the speed and direction of a stepper motor. You can move the motor in one step increments or rotate it at a constant speed. There are a set of visual indicators that show the sequence of motor. Includes stepper motor, pc board, parts and instructions.



(12Vdc power source not included)

CAT #SMK-1 **\$25.00 each**

LASER POINTER

5mW LASER POINTER!

Make a point with your laser pointer. Pointers are the most effective way to demonstrate your drawings, schematics, presentation, and charts. Just press and point! The beam shoots out across the room and puts a red dot on the wall up to 350 feet away. Operates on 2AAA batteries (included). wt. 2.3oz., wavelength 670nm/5mW output. Measures: .5" diameter x 5.75" L



CAT #LP-1 **\$39.99 each**

TALKING MEMO RECORDER

TALKING MEMO RECORDER / KEY CHAIN

Records and plays messages up to 16 seconds (i.e. parking spaces, things to do, etc.) 16 seconds is a long time to dictate! Measures 3" x 1.95". Battery operated (included).



CAT #TM-1 **\$19.95 each**

FM WIRELESS MIKE KIT

POWERFUL

2 stage, wireless mike kit transmits over .5 mile (up to 1 Km in the open) Tunable to the upper part of FM broadcast band. Circuit does require the ability to "tweak" RF circuits by stretching or compressing coils. With mike and 9V battery clip. Operates from 6-12V DC. 2.75" x .625" x .5" WT .06



CAT #FM-32 **\$10.95 each**

9V DC FM TRANSMITTER KIT

POWERFUL

FM transmitter. Transmits over 100 meters in building and over 500 meters outside using .95 or .5 wavelength of wire. Transmits to the upper part of FM broadcast band (100-108MHz). Circuit requires the ability to "tweak" RF circuits. Operates on 9V DC. 1.75" x .75" x .375" WT .05



CAT #FM-18 **\$9.95 each**

CAMCORDER VIDEO TAPES

HI-8 120 MINUTE VIDEO CASSETTE TAPES (used)

They were recorded on once and played only a few times. Made by a major brand name manufacturer. Professional series metal tapes. Includes plastic jewel box.




NOTE: Other tapes available.
CAT #CCT-1 **\$3.00 each**
10 or more • **2.80 each**

EMERGENCY LIGHT

THE AMAZING EMERGENCY LIGHT!

Never ever needs batteries! This waterproof unit is powered by pumping the handle--this action moves a flywheel which activates a dynamo. The dynamo produces a DC voltage and current that powers the light. Great for the car, home and boat. Never be without a light when the power goes out due to earthquakes, floods or other disasters. Operates when completely submerged in water. The dynamo can be stripped out for experimentation.

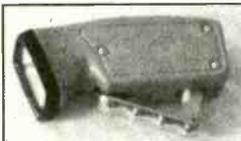


CAT # EL-1 **\$9.95 each**

TELEPHONE TRANSMITTER KIT

JUST LIFT THE HANDSET!

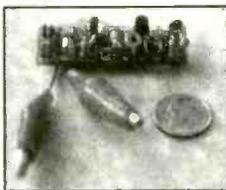
Phone line powered and activated when handset is lifted. Uses phone wires for antenna. Transmits over short distance (100ft) to the lower part of FM broadcast band (90-95MHz). Circuit does not require the ability to "tweak" RF circuits. WT .06



CAT #FM-16 **\$9.95 each**

STROBE KIT

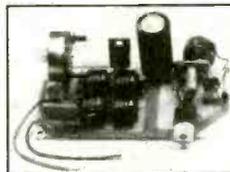This kit allows you to vary the rate of strobe flashes 60 to 120 flashes per minute. Operating voltage is adjustable depending on how you wire the kit. It will work on 4.5, 6 and 12 VDC. Includes pc board, parts and instructions.



CAT #SLK-1 **\$7.50 each**



Black Feather ELECTRONICS
Electronic Components, Supplies, Parts & Kits

645 Temple Avenue #7 ▲ Long Beach ▲ CA 90814
Local Phone Number (310) 434-5641
Hours: Monday - Friday 9 a.m. to 5 p.m. (Pacific Time)

California residence must include sales tax by county: 7.25 or 7.5 or 7.75 or 8.25 or 8.5
Check, Money Order, VISA or MasterCard.
Shipping in USA > \$4.00
NO C.O.D.S. - Do not send cash.

PLEASE NOTE...We Are Not Responsible For Printing Errors, Quantities Are Limited, Prices Are Subject to Change Without Notice, Some Pictures May Vary From the Actual Item, Store Prices May Vary from Catalog Prices, Quantity Pricing is Subject to Freight Considerations

CALL TOLL FREE! 1-800-526-3717

CIRCLE 280 ON FREE INFORMATION CARD

BLOWOUT! **TIMELINE INC.** BLOWOUT!

Over 9 years and 24,000 customers and still growing

LIQUID CRYSTAL DISPLAYS

160 x 128 dot LCD with built-in controller (T6963C)
 20 character x 16 line **\$79.00** or 2 for **\$149.00**

Mfr.: Toshiba TLX-1013-EO.
 Unit is EL back-lit. Dim: 5 1/8" L x 4 1/16" H.
 The built-in controller allows you to do text and graphics.

240x64 dot LCD with built-in controller. **\$79.00**
 Mfr: AND 4021ST-EO. Unit is EL back-lit. or 2 for **\$149.00**

Alphanumeric—parallel interface

16x1.....3 for \$25.00	20x2.....\$12.00	40x1.....\$8.00
16x1 (lg. char.)...\$12.00	20x4.....\$25.00	40x2.....2 for \$25.00
16x2.....\$8.00	20x4 (lg. char.)...\$25.00	40x4.....\$25.00
16x2 (lg. char.)...\$12.00	24x2.....\$12.00	4x2.....\$5.00
16x4.....\$15.00	32x4.....\$10.00	

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain modules are backlit, call for more info.

Graphics and alphanumeric—serial interface

size	Mfr.	price	size	Mfr.	price
640x480 (backlit)	Epson	\$35.00	480x128	Hitachi	\$15.00
640x400 (backlit)	Panasonic	\$25.00	256x128	Epson	\$20.00
640x200	Toshiba	\$15.00	240x128 (backlit)	Optrex	\$20.00
480x128 (backlit)	ALPS	\$15.00	160x128	Optrex	\$15.00

LASER PRODUCTS

HeNe Laser Head (10mW max. output) TEMOO, 15.5" long MFG: NEC **\$99.00**
Laser Power Supply (for HeNe tube) **\$89.00**

LASER SCANNER ASSEMBLY \$29.00
 Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

LASER DIODE (5mW) with collimator \$20.00

VISIBLE LASER DIODE: 5mw at 670nm \$15.00
 index guided. Threshold current 40 ma typical.

POLYGON MOTOR UNIT & DRIVER

Ten-sided first surface mirror mounted on an armature that spins at 125 revolutions per second yielding a beam sweep rate of 1250 sweeps per second. The driver for the polygon unit requires 24 volts and plus and minus 12 volts to operate. There is also an f-theta lens in front of the polygon scanning mechanism with a three inch diameter. Great for optical experiments, etc. Very high quality units. (MFR: JAPAN ELECTRONICS)

\$79.00

NETWORK

Proteon ProNet-4 Model p1347 Token Ring Board \$79.00
 16 bit • 4 Mbps • IEEE 802.2 and 802.5 compatible • twisted pair • interoperable with IBM Token Ring network

POS & BAR CODE

MAGNETIC CARD READER \$25.00

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypad with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

HP bar code wand (HBCS 2300).....\$35.00

POWER SUPPLIES

73 WATT SWITCHING \$15.00 or 2 @ \$25.00, (2) 4 pin power connectors attached
 • 115/230 Volt, Dim: 8.5" L x 4.5" W x 2" H • Output: +5V @ 2-9.75 A, +12V @ 0-1.5 A, -5V @ 0-0.4 A, -12V @ 0-0.5 A

68 WATT SWITCHING \$12.00 or 2 for \$20.00, 115/230 Volt,
 Dim: 5.5" L x 3.2" W x 1.7" H • Output: 5V @ 4 A, 12V @ 4 A

MISCELLANEOUS

ADAPTEC 4070A (RL) OR 4000A (MFM) SCSI Controller, your choice \$25.00

IBM 370 option XT and AT emulation boards \$35.00

23605 Telo Ave., Torrance, CA 90505

Order desk only: **USA: (800) 872-8878 CA: (800) 223-9977**
 L.A. & Technical Info: **(310) 784-5488 Fax: (310) 784-7590**

OEM INQUIRIES WELCOME

MONITORS

Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15KHz. • Ability to do 40 and 80 column.

5 inch Amber	\$35.00
7 inch Amber	\$39.00
9 inch Amber or Green	\$29.95

5" COLOR MONITOR \$49.00

- Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible
- 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.
- Open Frame Construction • Standard Interface Connector
- Degaussing Coil included • Mfr. Samtron



CHARGE COUPLED DEVICES



"The Spy In The Sky" \$29.00

MATRIX TYPE

Sony CCD Imager - designed for black and white composite video cameras. Picture elements: 384 (H) x 491 (V)
 Chip size 10.7 (H) x 9.3 (V) mm² • Unit cell size 23.0 (H) x 13.4 (V) um².
 Ceramic 24 pin DIP package • Mfr: Sony, Part# 016AL

4096 element CCD \$29.00

1024 element CCD \$15.00

2048 element CCD \$15.00

LINEAR TYPE

1728 element CCD \$15.00

HACKER CORNER

CELL SITE TRANSCIVER \$99.00

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 MHz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier; channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

Encased Black & White Composite CCD Camera with Adapter

IR viewing to 1000 nm 7 1/4 L x 2 1/4 W x 1 1/4 H
 Comes complete with CCD camera, mounting nut on bottom of casing, 12VDC power supply. Excellent low light capability, standard RCA NTSC video out. **\$89.00**

Great for: entryway security/remote monitoring, video conferencing/desktop video conferencing **2 for \$159.00**

This miniature camera is perfect for multimedia computer applications as well as security and surveillance. NTSC output allows use with all popular video digitizing boards for Apple Macintosh and Microsoft video for Windows. Connects directly to any composite monitor or VCR with "video" input. Its razor-sharp wide-angle lens focuses from two inches to infinity and its state-of-the-art CCD technology accurately captures 16 level grayscale images for Quick Time movies and still pictures. Records at 30 frames per second and 260 lines resolution with excellent low light capability. Uses 12VDC (adapter supplied) and standard RCA cable.

Portable Micro Terminal \$99.00 or 2 for \$149.00

Flip up LCD display (9-16 VDC) • Can communicate with any computer having RS 232 port • Can communicate with another Microterminal • Use by itself as electronic notebook • Onboard microprocessor, data RAM (32K) and Video RAM (64K) • Complex built in diagnostics and set up capabilities. • Original intention for POS applications. • display size 40x16 (256 x 128 pixels.) Dimensions: 6.3" W, 11" L, 2" H. (With LCD up height is 7.1")



BAREBONES 286-12 COMPUTER \$49.00 (2 FOR \$79.00)

Slimline desktop case, 100 watt supply, math co-processor support. On board IDE, & Floppy controllers. 2 COM ports and 1 parallel port with software setup. Supports up to 8 Megs using standard 30 PIN SIMMS. Internal room for (1) 3 1/2 inch IDE hard drive and (2) 3 1/2 inch floppies. Four 16 BIT ISA slots, accepts full length AT size cards. Keyboard can be set to no test at boot. Case size is 15.5"W x 16"D x 4"H.

(Motherboard can be purchased separately: \$29.00 or 2 for \$49.00)

CORNER CUBE \$29.00

Solid Glass Retro-Reflector
 Unit is a trihedral prism with three mutually perpendicular faces. It reflects incoming light rays precisely back in the direction they came from, regardless of the angle of the corner cube itself. It is thus self aligning. Made for a military weapons program. Can be used for laser based ranging (distance measuring), seismology, multipass interferometry, and many other optical experiments. Diameter: 66.5 mm Height: (face to point) 40.2 mm Flatness: 1/8 wave @ 632.8 nm

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

SEE US
NOW AT
<http://www.cit.com/>

**CIRCUIT
SPECIALISTS
INC.**

**Check Out
What
We
Have
To Offer:**

**680MB
TAPE
BACKUP**

INCLUDES

- Internal Tape 700 Drive
- Complete Documentation
- Cables and Mounting Hardware
- Easy-to-Use DOS & Windows Software
- Uses QIC-3010 (3M3000XL \$34.90)

Only \$119



Teac Tape 700 **\$119**

MULTI-FUNCTION DIGITAL & ANALOG I/O MULTI-LAB PACKAGE

The ACL-711S is a low cost, but fully integrated package designed for applications of general lab and industrial automation. It contains:

- **8 Single-Ended A/D Inputs**
 - Resolution: 12 bits
 - Input Range: -5V to +5V
 - Trigger Mode: Software trigger only
- **One Analog Output (D/A)**
 - Resolution: 12 bits
 - Output Range: 0 to +5V or 0 to +10V
- **16 Digital Inputs**



- **16 Digital Outputs**
- **ACLD-7115** Wiring terminal board (furnished with ACL-711S)
- **Utility Software Disk** Driver routines for BASIC and Quick-BASIC, demo and example programs

ACL-711S **\$199**

24-BIT COLOR FLATBED SCANNER

- High-Speed 3-Pass Scanner
- Long Lasting Cold Cathode Technology (10,000Hrs)
- Up to 2400x2400dpi (300x600 hardware)
- Intelligent LCD Panel
- TWAIN Compliant
- Includes: PhotoStacker, WordLinx OCR & Media-House Multimedia Document Manager Software
- Includes SCSI Interface Card



**A6000C
\$329**

A6ADF Optional 50pg Doc Feeder

\$359

A6TK Optional Transparency Kit

\$259

DIGITAL PANEL METERS

- 200mV Full Scale Input Sensitivity
- Single 9 Volt DC Operation
- Decimal Point Selectable
- Auto Polarity Indication
- High Input Impedence (>100M ohm)



AS LOW AS \$5.25 EACH

CAT NO	DESCRIPTION	1	10	25	100	250
PM-128	3-1/2 Digit LCD Panel Meter	\$ 9.90	\$ 7.09	\$ 6.40	\$ 5.86	\$ 5.25
PM-129	3-1/2 Digit LED Panel Meter	11.49	9.54	8.67	7.95	6.95
PM-328	4-1/2 Digit LCD Panel Meter	19.88	16.40	14.90	13.66	11.93

This very easy to use tool is a "must have" if you need to straighten the pins on your IC's. Made from anti-static material, this tool is suitable for IC's from 8 to 20 pins (narrow side) and 24-48 pins (wide side). A grounding terminal is also built-in to the tool allowing for easy grounding when using this tool at a fixed location.



CAT NO	1	10	100
ICS-01	\$7.18	\$6.44	\$4.89


PC218902 (AT-BUS)



- Board Length: 13-1/8" (333mm)
- Board Width: 4-5/16" (110mm)
- Double Sided, 3-Hole Solder Pads and Power Buses
- Space Reserved for: Header, 32x2, 0.1" Spacing and Pin Grid Array

CAT NO	1	5
PC218902	\$25.66	\$20.25

PC218904 (AT-BUS)

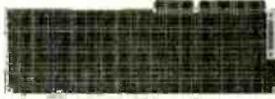

- Board Length: 13-1/8" (333mm)
- Board Width: 4-5/16" (110mm)
- Double Sided, Pad-Per-Hole and Power Buses
- Space Reserved for: 1 D-Type Connector, 25-pin

CAT NO	1	5
PC218904	\$25.42	\$20.06

PC218903 (XT-BUS)



- Board Length: 13-1/8" (333mm)
- Board Width: 4-5/16" (110mm)
- Double Sided, Pad-Per-Hole and Power Buses
- Space Reserved for 1 D-Type Connector, 25-Pin

CAT NO	1	5
PC218903	\$23.51	\$18.63

PC232904 (Multi-BUS)



- Board Length: 12" (305mm)
- Board Width: 6-3/4" (171mm)
- Double Sided, Pad-Per-Hole and Power Buses
- Space Reserved for 1 Header, 100x2, 0.1" Spacing

CAT NO	1	5
PC232904	\$38.40	\$29.80

PC207905 (STD-BUS)



- Board Length: 6-1/2" (165mm)
- Board Width: 4-7/16" (113mm)
- Double Sided, 3-hole Solder Pads, Ground Plane and Power Bus
- Space Reserved for 1 Header, 34x3, 0.1" Spacing

CAT NO	1	5
PC207905	\$13.66	\$11.25

PC412902 (VME-BUS)



- Board Length: 6-5/16" (160mm)
- Board Width: 3-15/16" (100mm)
- Single Sided, Pad-Per-Hole and Power Buses
- Space Reserved for 1 D-Type Connector, 25-Pin

CAT NO	1	5
PC412902	\$7.06	\$6.00

RECEIVE OUR LATEST 132 PAGE CATALOG!

It's chock full of all types of electronic equipment and supplies. We've got IC's, capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call 800-811-5203, ext. 5, to leave a message on our catalog request line.



CIRCUIT SPECIALISTS, SINCE 1971

**800-811-5203
602-464-2485
602-464-5824(FAX)**

WE ACCEPT:





DIGITAL STORAGE OSCILLOSCOPE

WITH
SPECTRUM
ANALYZER,
DVM, FREQ.
COUNTER,
AND DATA
LOGGER.

\$189.

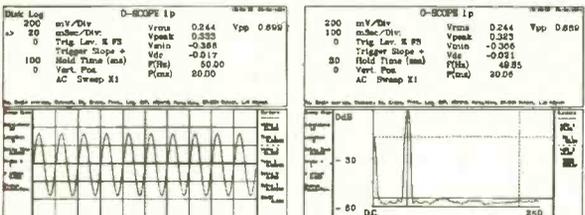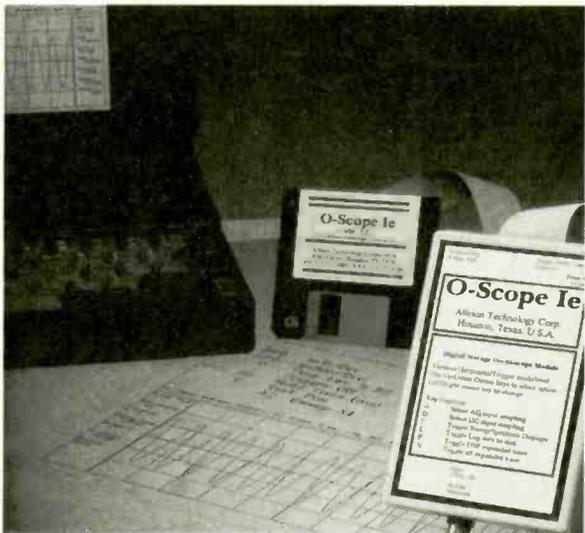**O-SCOPE
MODULES
CONVERT PC'S
INTO
MULTIPURPOSE
TEST AND
MEASURING
INSTRUMENTS.**



FEATURES:

- SMALL & PORTABLE
- USES PRINTER PORT
- USES STD. PROBES
- DC TO 50 KHz
- 10v/div. TO 50 mv/div.
- MADE IN U.S.A.
- SAME DAY SHIPPING

OPTIONS:

- PROBE SETS
- EXTERNAL TRIGGER
- DUAL TRACE
- X-Y PHASE DISPLAY
- EXTENDED BANDWIDTH
- EXTENDED INPUT RANGE
- BATTERY PACK

INCLUDES SOFTWARE & INSTRUCTIONS.

ASSEMBLED AND TESTED..... \$169.
ENHANCED SOFTWARE..... \$ 20.
KIT (WITHOUT CASE)..... \$129.
SHIPPING: \$7.50 (2ND DAY \$11.50)

TO ORDER: SEND CREDIT CARD INFO., M.O., or CHECK, OR
YOU MAY CALL **1-800-980-9806**

ALLISON TECHNOLOGY CORPORATION

8343 CARVEL, HOUSTON, TX. 77036 U.S.A.
PHONE: 1-713-777-0401 FAX: 1-713-777-4746
BBS: 1-713-777-4753

TOP SECRET

CONSUMERTRONICS
2011 Crescent Dr., P.O. Drawer 537
Alamogordo, NM 88310

Voice: (505) 439-1778, 439-8551
8AM - 7PM MST, Mon - Sat

Fax: (505) 434-0234, 434-1778 (orders only; if you get voice, enter #11 any time), 24-hr Home Page: visit our popular home page and let your friends: <http://users.aol.com/wlzguru/hit-tech.html>

Free Tech Support (relates directly to your order or prospective order): Tues. & Thurs. only 10% Off on orders \$100+ - 15% Off over \$200+ Add \$5 total SH (US, Canada). All items in stock. VISA, MCard OK. No CODs or 'bill me's'. New Catalog (200+ offers) \$2 w/order, \$5 w/b (check or MO). NO dealers. Since 1971. As seen on CBS '60 Minutes', Forbes, etc. By John Williams - former Lockheed Senior Engineer, NMSU CS Professor, DOD Electronic Weapons Engineer, NIH Health Physicist.

Wanted: 5 MAC IIx, PC486 (or better), peripherals, new surplus electronic parts, test equipment - buy, trade. *All software supports all IBM-PC compatible x86 systems (8088 - Pentium)

Off-The-Shelf HARDWARE

Van Eck Systems • Data Card Reader/Writers • ATM3 • RF/EM/Wave/Radar/Ultrasonic/IR/Light/Sound Detectors/Receivers/Xmitters/Jammers/Blasters • Security Surveillance • Neurophone/RF/Hieronymus/Resonant Crystal Radionics • EM Lab/Weaponry/Countermeasures • Voice Disguisers • ESS Infinity Devices • Phone Color Boxes • DTMF Decoders • Lineman's Handsets • Bug/Tap Detector/Blaster • Bumper Beeper/Child Finder • Panic Button • Carjack/Kidnap Follower • Hidden Presence Detectors • Hearing Assistor • Shrlck Module • TENS • Subliminal Mixer/Amp • Vortex Generator • 6th Sense Communicator • Noise Cancel. System • Electronic Dowsler • Levitator - more! See New Catalog!

SPECIAL PROJECTS

We design/build/obtain/repair/modify/maintain/consult on any device/system/process/project - electronic/computer/mechanical/optical (ex: phone/auto/security/radionic/lab/energy/HV/EM/RF/radar/ultrasonic/IR/UV/commo/consumer) for business/personal/invention needs. Describe & include \$30 pre-engineering fee (no obligation). Time & cost estimates 7-10 days. Confidentiality guaranteed.

1-GBYTE DATABASE

Let us search our massive 1.0 Giga-byte Hi-Tech Survival Database for you. Virtually every major Hi-Tech Survival topic covered in depth. Some private files. See New Catalog.

CELLPHONE MODS

See our Catalog for our infamous cellphone modification guide (\$69) - detailed, comprehensive, covers all makes - 10 times more info than competitor's 'guide'. (Do Special Projects above to get up-to-date hardware/software). **FREE DATA SEARCH!** As a special FREE service to our C&CP customers, we will perform one FREE search of our massive cellphone database if requested within 30 days of your purchase of C&CP. Data now on cellphones is so great, we can fit in C&CP only that to greatest demand. Search results not guaranteed. Request by mail (don't fax); include a #10 SASE.

VOICE MAIL HACKING

How Voice Mail Box (VMB) systems are used and the specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BIX, GENESIS, EZ, SYDNEY, PHONE MAIL, AUDIX, GINDY, CENTAGRAM, SPERRY LINK, RSPV, etc. Absolutely required for all users, sysops and security personnel! \$29.

PBX HACKING

1,000s of PBXs are hacked to the tune of \$ Billions/yr! While 'VOICE MAIL HACKING' details how VMSs are hacked for 'phunt' and proflit - including VMS methods for hacking PBXs themselves - 'PBX HACKING' addresses ALL issues relating to PBX hacking, including countermeasures! Can your business or agency afford a \$90,000 phone fraud loss (the average loss due to hacked PBXs)? As described in Forbes Magazine. \$29

PHREAKING CALLER ID & ANI

Details on how they work and dozens of effective ways of defeating Caller ID, ANI, *59, *57, and Call Blocking and *67. Also describes Caller ID, Orange, Beige, Cheese and CF Boxes, ESS, S57, E-911, various CLASS services, CNA, NON PUB DA, CANA, DNR, 800-ECR, Diverters, Extenders, Centrex - more. \$29.

Beyond PHONE COLOR BOXES

Dozens phone color boxes described - many circuits: Plus Call Forwarding, Conferencing, Phreak History, Glossary, Diverters, Extenders, Loops, REMDBS, Bridging Heads & Cans, Oplocm, 3rd Party and many other non-box methods - more. \$39.

HACKING ANSWERING MACHINES

How answering machines are hacked to listen to - even erase - messages, and to convert them into mini-VMSs. And countermeasures - protect yourself from snoops, stalkers, burglars and pranksters! \$29.

CREDIT CARD SCAMS

Cardholders, merchants, banks suffer \$ Billions in losses annually because of credit card fraud. Describes every known means of credit card fraud and scams. Protect yourself! \$29.

AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed. Include: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic strips, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, suscept., laser, vibration, pulse, high voltage - others. Case histories, law, countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to \$250,000 in cash! Recent \$350,000 ATM crime spree still unsolved! \$39.

CONS. SCAMS & SWINDLES

Cons & scams and related swindles (lieccs) Americans of \$100+ Billion per year! The most comprehensive survival manual on cons & scams of all kinds - from the classic to hi-tech. Details on 100s and many variations. And countermeasures. Protect yourself! \$39.

COMPUTER PHREAKING

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS, etc. are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system (Ed. Chloca, PC Magazine). BBS advice, password defeats, glossary - much more! Manual + Disk! \$39.

Beyond VAN ECK PHREAKING

Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the Consumertronics and the original Top Secret Van Eck design! \$29.

The HACKER FILES

Compilation of 100s of the best articles written (in ASCII) by top hackers & phreakers. Covers every major topic in hackerdom! 3 HD Disks! \$59.

STOPPING POWER METERS

As reported on CBS '60 Minutes': How certain devices can slow down - even stop - wallout meters - while loads draw full power! Device simply plugs into one outlet and normal loads into other outlets. Also describes meter creep, overload drop, etc. Plans \$29. **I.G. MANUAL:** External magnetic wyes (applied to the meter itself) to slow down and stop wallout meters while drawing full loads. Plans \$19. **KW-HR METERS:** How wallout meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$19. Amp 2, \$38. All 3, \$59.

UNDER ATTACK!

Electromagnetic Interference and Electronic Weapon Attacks cause: Cancer, birth defects, and profound psychological, neurological, cardiovascular and immune system disorders! Destructive to people, animals, plants, equipment! Includes ACTUAL CASES OF EM ATTACKS (we investigated) including how to verify and pinpoint EMI and electronic attack sources, and effective countermeasures. \$29. **EM BRAINBLASTER:** Tutorial and plans for powerful ELECTROMAGNETIC WEAPONS and LAB DEVICES. Optimum circuits, freqs, waveforms, duty cycles, Intensities. Thorough. \$29. Both \$49.

RADIONICS MANUAL

Excellent electrical, electronic, electromagnetic therapeutic, diagnostic & preventive devices (mostly experimental). History, descriptions, plans (dozens), availabilities of Radionics Devices from early to modern. While drugs cost \$100s, electricity costs pennies! \$29. **HEAL THYSELF!** Plans for 3 major electronic therapeutic devices of types approved by FDA. \$19. Both \$38.

HIGH VOLTAGE DEVICES

HV devices plans: Stun Gun, Taser, Prod, Cane, Blaster, Flasher, Zapper, Audio/RF/Radar Jammer, Fence Charger, Plasma & Van de Graaff Guns, Jacob's Ladder, Geiger Counter, Ozone Gun, Fish Stunner, Plant Stim., Kirlian, more! All plans for only \$29.

STEALTH TECHNOLOGY

Police radar is fascinating! It also has error rates of 10-20%! Every known error mode - stealth method and material used to minimize radar reflections - tactic and strategy to fight unjust radar tickets (that cost you \$100s in insurance and risk cancellation) - methods to detect and jam signals - fully described! \$29.

SECRET & SURVIVAL RADIO

Optimum survival and security radio equipment, methods, freq allocations and voice/data scrambling/encoding. Includes Small receivers/transmitters, telemetry, antenna optimizations, remote monitoring and control, security, surveillance, and ultrasonic, fiber-optic and infrared commo. 70+ circuit plans, tables. \$29.

By an ORDER of the MAGNITUDE

The most comprehensive, hard-hitting, hi-tech survival book ever written! Topics include electronics, computers, energy, weapons, concealment, revenge, alarms, etc. to survive today's dangerous world. We all face increasingly financially and physically brutal times! Field-expedient use of technology in various threat and conflict environments and scenarios. \$49.

ROCKET'S RED GLARE

How to design and build solid-propellant amateur and survival rockets. Emphasis on formulation, manufacture, installation of propellants, motors, igniters, etc. Includes list of commonly available materials, and the design of launch pads and test beds and their electronics. \$29. **FIREWORKS:** How firecrackers (M-80s, bookbusters, cherry bombs), small rockets, volcanos, fountains, sparklers and safety fuses are made and colored. Simple, cheap, common ingredients. \$9. Both \$36.



How to get an AOL Web Page

Web pages are powerful forums for presenting views and offers, exchanging data, organizing around common interests, hyperlinking to other sites, etc. - YOUR world-wide magazine! Available info on how to create and upload web pages to AOL is often erroneous, misleading and incomplete. Step-by-step details on how to create and upload your AOL web page. And how more than one can be posted from the same screenname. Plus lots of info. \$19 (not an HTML language web or AOL page) - also for educational purposes only.

B² SPICE v 2.0

B² LOGIC v 3.0

for windows™ and macintosh™

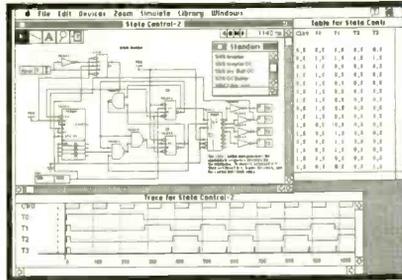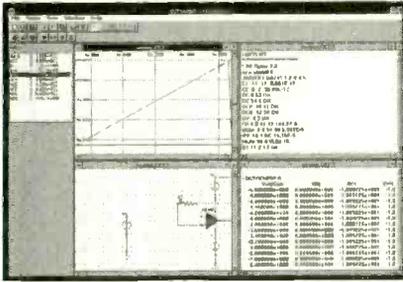

B² SPICE v 2.0 \$199

- Simulations: Transient, DC, AC, Noise, Distortion, & More
- Build your own symbols & parts
- Full SPICE 3f5 implementation
- Hundreds of devices
- Device & Model Property Editing
- Flexible Visualization of Results: customized graphs and tables
- Version 2.0 for Windows
- Version 1.1 for Mac & Power Mac

Why Design Circuits the Hard Way?

B² SPICE and **B² LOGIC** are the most powerful and affordable integrated analog and digital circuit design, simulation, and analysis packages available. **B² SPICE** and **B² LOGIC** neatly integrate the schematic editor, simulator, and graphics post processor. They are fully integrated and interactive and are extremely easy to use for **Windows™**, **Macintosh™**, and **Power Mac™**. Both **B² SPICE** and **B² LOGIC** are currently in use at over 100 major universities and many leading Fortune 500 companies such as The University of Michigan, Stanford, AT&T, General Electric, and Hewlett Packard, to mention a few!

B² Logic v 3.0 \$199

- EDIF File Format Output
- Enhanced PLD Simulation Capture
- Subcircuit Probing
- Over 100 components available

ELECTRONIC DESIGN PACKAGE \$299

- Includes **B² SPICE** & **B² LOGIC**



Beige Bag Software

1756 Plymouth Road • Suite 370
Ann Arbor • Michigan • 48105

Phone 313. 332. 0487

Fax 313. 332. 0392

E-Mail info@beigebag.com

Url http://www.beigebag.com

CIRCLE 335 ON FREE INFORMATION CARD

- Demo Disks Available
- University & Student Prices Available
- Site Licenses Available
- Dealer Inquiries Welcome

WE SELL RED, BLUE-GREEN & IR

LASERS

HUNDREDS OF UNITS TO CHOOSE FROM!
PRICES AS LOW AS \$40.00!

- Experiments
- Laser Light Shows
- Cutting & Burning
- Communications

We also carry
books and plans
about LASERS.

CALL FOR FREE CATALOG!

TEL (909) 278-0563

FAX (909) 278-4887

MWK INDUSTRIES

1269 W. Pomona, Corona, California 91720


See our catalog on the internet.

HTTP://WWW.PWEB.COM/MWK/MAIN.HTM

EMAIL: MKENNY1989@AOL.COM

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING with the New AES-10

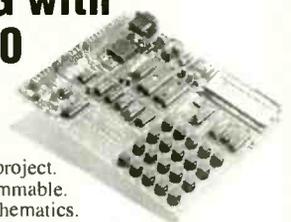The AES-10... a complete learning system, a complete embedded control system. Extensive manuals guide you through your 8051 development project. Assembly, BASIC, and C programmable. All hardware details, complete schematics. Learn to program the LCD, keypad, digital and analog I/Os. The entire board is software reconfigurable for your applications. Everything you need, nothing extra required.



80C32 Computer/Microcontroller board with:

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Two serial ports • 5 interrupt sources • 3 timers • A/D, D/A, PWM and digital I/O • Built in Logic Probe • Power supply (can also be battery operated) • Extended Intel BASIC and AES Monitor in ROM • RS-232 cable to connect to PC for programming • 8051/52 DOS Cross Assembler • Program disks with well documented examples • User's Manual, Language Manual, and Text (over 400 pages).

AES-10 \$285 Complete
Money Back Guarantee

Free Info Pack, M/C Visa
714 - 550-8094
Fax 714 - 550-9941

AES


Advanced Educational Systems

970 W. 17th St., Santa Ana, California, 92706 USA

CALL 1 - 800 - 730-3232

8085 MICROPROCESSOR TRAINING & CONTROL SYSTEM

Are you interested in Single Board Computers and Microprocessor-based control systems? If the answer is yes and you want to know more about these fascinating subjects the PRIMER Trainer is the place to start. The PRIMER teaches more and is easier to use than other comparably priced trainers. Enter a program into RAM, run it, and then burn it into EPROM with the optional EPROM Programmer. The over 100 page Self Instruction manual takes you from binary number systems to processing interrupts. At the end of the manual are working examples of using a photocell, a temperature sensor, making a waveform generator, a programmable timer with alarm, writing to LCDs, scanning keypads, and controlling the speed of a motor. The PRIMER comes with everything you need to start programming in machine language. Continue on to program in Assembler, Forth or BASIC with optional upgrade and software. Upgrade includes: RS232 serial port, a serial cable, 32K of battery backed RAM and Assembler/Terminal software. Picture shown with upgrade option (\$49.95) and optional heavy-duty keypad (\$29.95) installed.

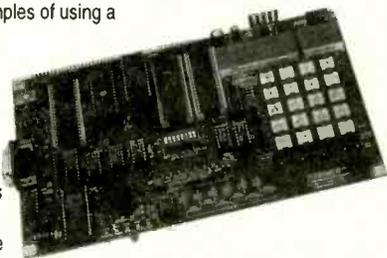

THE PRIMER IS ONLY \$119.95 IN KIT FORM. THE PRIMER ASSEMBLED & TESTED IS \$169.95. RECEIVE ONE FREE POWER SUPPLY WHEN YOU MENTION THIS AD. PLEASE ADD \$5.00 FOR SHIPPING WITHIN THE U.S.

1985-1995
10
YEAR
ANNIVERSARY

ENAC, inc.

618-529-4525 Fax 457-0110 BBS 529-5708
P.O. BOX 2042, CARBONDALE, IL 62902

NEW LOW COST COMPACT LASER

650 nm laser pointer

• **5 TIMES BRIGHTER**
actual size

- only 2.3" Length
- Solid aircraft aluminum housing
- 3-4mW output
- Includes 3 silver oxide watch batteries
- Battery life 2-3 hours
- Warranty 1 year

PRICE: \$59.00

This laser blazes like a torch.

TO ORDER CALL

1 (800) 996-6873



HI-Q PRODUCTS, INC.

506 N. Garfield Ave., Suite 200, Alhambra, CA 91801

TEL: (818) 308-4400 FAX: (818) 308-4406

Say you saw it in *ELECTRONICS NOW* and 1st 200 customers will receive a free transmission hologram.

What's the easiest way to get Radio Active?

Dial 1 800 445 7717

TRIDENT | Bearcat

TR2400 \$499
100KHz to 206 GHz



BC230 \$229
Turbo Scan
with 800MHz



BC3000 \$369
25MHz to 1.3 GHz



Trident Spectrum Analyzer

1-1300MHz in two bands with a Span that's variable from 500 MHz to 10 MHz. 80db on Screen Range, marker generator, 200K/10K selectable bandwidth, -117dBm Sensitivity, outputs to any x/y o'scope.
\$699.00

These are a few of our products and price values. For more information dial toll free or use our BBS, or get instant specs & info. from our fax back service.

Toll Free, 24 Hours! For orders or for tech support, dial our 800 number. For Fax Facts Instant catalog sheet service, dial 317 849 8683. Computer BBS


ACE
COMMUNICATIONS
10707 E. 106th St. Fishers, IN 46038

& Fax/Modem, 317-579-2045. Mastercard, Visa, Checks, Approved P.O.'s & COD (add \$5.50) & AMEX, Discover. Prices, specs and availability subject to change. Ground shipping and handling charge \$6.95

CIRCLE 212 ON FREE INFORMATION CARD

PALMSCOPE™ 320

ALL IN ONE DSO+DMM+LOGIC+COUNTER

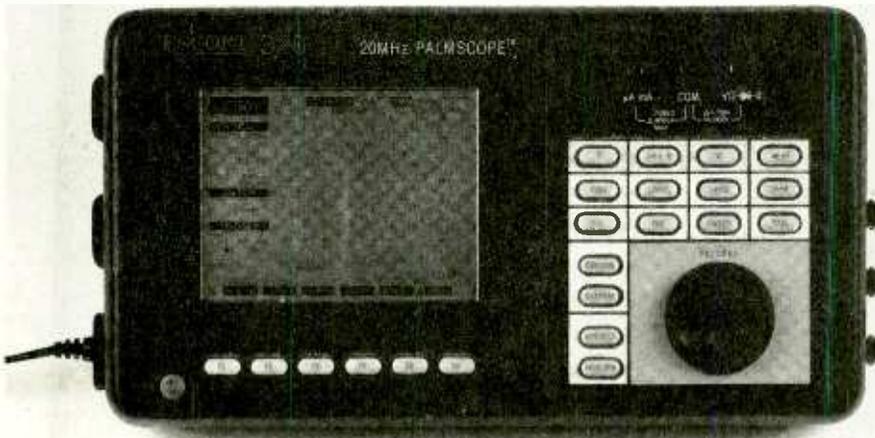

PalmScope-320 features a 20Mhz DSO, 7 digit frequency counter, multimeter and logic scope. It can be operated with built-in battery for 3-4 hours typically. Built in RS-232 port and printer port extend your application. Optional software package is available.

PalmScope 320
\$1695

DSO • Dual channel digital storage oscilloscope (20 MS/sec) • Sensitivity range: 5mV / DIV - 20V / DIV
• Sweep time: 50ns / DIV - 20s / DIV.

DMM • Auto-range digital multimeter (4000 counts) • True RMS • DCV, ACV, DCA, ACA, Ohm Diode & continuity measurements

LOGIC • Logic Scope (8 channels, 50ns sample clock) • Selectable level: TTL/CMOS • Timing/State observation of logic signals

COUNTER • 7 digit frequency counter (1 Hz to 20 MHz) • Selectable trigger level and FREQ/PER mode • Basic Accuracy $\pm 10\text{ppm}$

General:	Display	
• Dual Channel Digital Storage Oscilloscope (20MS/s)	• Number of Dots: 320(W)x240(H)	• Operating Temperature: 0°C to 40°C
• Auto Range Digital Multimeter (3 3/4 digits, 4000 count)	• Dot Pitch: 0.30 x 0.30 mm	• Operating Humidity: 0% to 70% R.H.
• Frequency Counter (7 digits, 20 MHz)	• Backlight: LED	• Storage Temperature: -20°C to 70°C (0% to 80% R.H.)
• Logic Scope (8 channels, 50ns sample clock)	• Data Out (RS-232C)	• Dimension (LxWxD): 287x152x82 mm
	• Print Out: Portable Centronix and Epson Printer	• Weight: 2.0Kg
	• DC jack for AC adapter input	• Safety Compliance: it is designed to meet Class II per UL-1244, IEC 348 and VDE-0411
	• LOW BATT Indicator	

Introducing the Model #EDM-89S

5000 Count AUTO Range Digital Multimeter

Twelve Good Reasons To Buy The EDM-89S:

- 3-3/4 Digit, 5000 Count Digital Readout 50 Segment Analog Bargraph
- Auto/Manual, Dynamic Recording
- 0.1% DCV Accuracy, 20 kHz ACV Bandwidth, True-RMS AC Coupled
- 9999 Counts, 10 MHz Frequency Counter, Turbo Speed, and 50mF Capacitance Measurement
- dBm with Selectable Reference Impedance
- Dual Tone/Dual Display Logic Detection
- Relative Mode or Deviation Measurements
- Input Warning, Audible and Visible
- @ OFF Auto Power Off, Sleep Mode
- Overload Protection
- Audible Continuity/Diode Test
- Rugged Fire Retardant Case, Multipurpose Holster



MODEL #EDM-89S
\$179.00



8931 Brookville Road * Silver Spring, Maryland 20910 * 800-638-2020 * Fax 800-545-0058

CIRCLE 264 ON FREE INFORMATION CARD

EPROM+ PROGRAMMING SYSTEM USES PARALLEL PORT

EPROMS (24, 28, 32 & 40* PIN PLUS 27CXXX)
1702, 2708, 16, 32, 32A, 64, 64A, 128, 128A, 256, 512
513, 011, 010, 101, 301, 1000, 1001, 1024, 210, 020
2000, 2001, 220, 240, 2048, 4001, 4002, 040, 080, 8001
2516, 32, 64, 68764, TMS2716

FLASH EPROMS
28F256, 512, 010, 020 PLUS 29CXXX, 29FXXX

EEPROMS & NVRAMS (PLUS CXXX)
2804, 16, 16A, 17, 2864, 64A, 65, 28256, 28C010
X2210, X2212, DS1220, 1225, 1230

SERIAL EEPROMS* (8 PIN PLUS CXX)
2401, 02, 04, 08, 16, 32, 65, 2444, 59C11, 8572, 82, 92
9306, 46, 56, 66, 16811, 911, 80011A, ER1400/58657

BIPOLAR PROMS* (16 THROUGH 24 PIN)
74SXXX AND 82SXXX FAMILY

MICROCONTROLLERS* (UV, EE AND FLASH)
8741, 42, 48, 49, 8751, 87C51, 8752, C52, 87C5XXX
87C75X, 89C51, 52, 68705, 68HC705, 68HC711E9
PIC16C5X, PIC16C6X, PIC16C7X, PIC16C8X

* ADAPTER REQUIRED - ASSEMBLED ADAPTERS AVAILABLE / DETAILED DIAGRAMS INCLUDED

- SOFTWARE - READ, VERIFY, PROGRAM, COPY, DISK FILE LOAD & SAVE, CHECKSUM, PLUS A FULL SCREEN BUFFER EDITOR WITH 20 COMMANDS
- READS INTEL HEX, MOTOROLA S-RECORD AND BINARY FILES
- FAST! - MANY DEVICES PROGRAM IN UNDER 10 SECONDS
- RUGGED (9" X 6" X 3"), PORTABLE ENCLOSURE WITH CARRY HANDLE DESIGNED FOR BENCH AND FIELD SERVICE.
- ACCESSORY CONNECTOR FOR FUTURE EXPANSION
- LED INDICATORS SHOW POWER, PROGRAMMING & SYSTEM STATUS
- MADE IN THE USA - 30 DAY MONEY BACK GUARANTEE - 1 YR WARRANTY
- SYSTEM INCLUDES: PROGRAMMING UNIT, POWER PACK, CABLE PRINTED MANUAL AND SOFTWARE

ANDROMEDA RESEARCH
P.O. BOX 222
MILFORD, OHIO 45150
(513) 831-9708
FAX (513) 831-7562

SUPPORTS OVER
600 CHIPS



\$289




ADD \$5.00 SHIPPING - \$5.00 C.O.D.

DATA ACQUISITION

and Control Hardware for PC's

ANA100 Analog I/O \$ 99

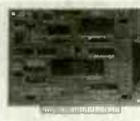

- * 8 Channel 8-Bit
- * 0 to 5 Volt Input
- * 14 TTL I/O lines
- * Analog Output
- * 400KHz Sampling

DIG100 Digital I/O \$ 39




- * 8255 PPI
- * 24 or 48 TTL I/O Lines option
- * Selectable Base Address

ANA150 Analog/Counter... \$ 89



- * 8 Channel 8-Bit
- * 0 to 5 Volt input
- * 3 16-Bit Counters
- * 400KHz Sampling

DIG200 Counter I/O \$ 79

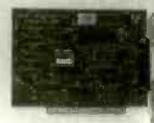

- * 3 16-Bit Counters
- * 8 TTL Input lines
- * 8 TTL Output lines
- * Selectable Clock Frequency Input

ANA200 Analog I/O \$ 79



- * 1 Channel 12-Bit
- * 0 to 5 Volt input optional bi-polar
- * 100KHz / 300KHz Sampling rate
- * 24 TTL I/O lines

ANA201 Analog \$ 129



- * 8 Channel 12-Bit
- * x1, x5, x10, x50 Programmable Channel gain
- * 100KHz/300KHz Sampling rate

Engineering Software - PC/MSDOS

Easy-PC Professional XM - Integrated Electronics
CAE System, Combines Schematic Capture,
Simulation, and PCB Design in one package.... \$ 349

More Hardware and
Software Items
Ask for our current catalog

PC-SCOPE - Digital Storage Oscilloscope, 1, 2, 4, or
8 Channel Capture and Display of Data. Works with
ANA100, ANA150, and ANA201 Boards..... \$ 39


We accept
MasterCard/Visa Orders

BSOFT Software, Inc.

PHONE 614-491-0832 * FAX 614-497-9971
444 COLTON ROAD * COLUMBUS, OHIO * 43207

CELLULAR PROGRAMMING KITS!

**LIMITED
FIRST
TIME
OFFER!!**

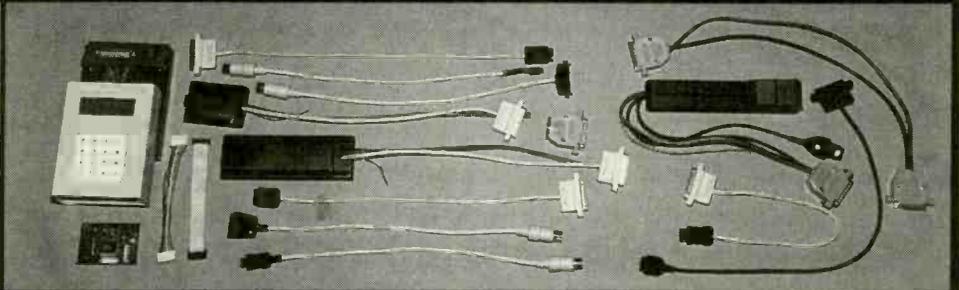

KIT #	PROGRAMS THE FOLLOWING PHONES	PRICE
1	MOTOROLA ONLY w/elite & 951C !!!	\$1995
2	Above PLUS NEC P100-200-300-400-600-700	\$2195
3	All of above PLUS SONY	\$2395
4	All of above PLUS GE (old & new mode)	\$2595
5	All of above PLUS AUDIOVOX (does new 800!)	\$2795
6	All of above PLUS MITSUBISHI/DiamondTel	\$2995

All Kits come
COMPLETE with
cables.... **SIMPLE**
detailed assembly
instructions....
plus **EASY** to
understand
instructions on
how to operate.

All kits are sold for **EDUCATIONAL PURPOSES ONLY!**

CALL US TODAY AT 770.973.8474 or e-mail ctg@mindspring.com

CIRCLE 319 ON FREE INFORMATION CARD

www.americanradiohistory.com

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 64 Page CATALOG.
Outside the U.S.A. send \$2.00 postage.

PHOTOVOLTAIC DETECTOR



Miniature silicon solar cell converts light impulses directly into electrical charges. Unlike a conventional photo diode or transistor, it generates its own power and does not require any external bias. Generates 0.4 vdc in moderate light. Silicon cell is mounted on a 0.31" x 0.23" x 0.07" thick plastic carrier and has pc leads on 0.2" centers. Large quantity available.

CAT # PVD-2

75¢ 10 for \$6.50 • 100 for \$50.00

Great Price! 800 MA UNIVERSAL WALL ADAPTOR

Multi-voltage power source eliminates the use of batteries in many electronic products. This handy device has 6 voltage settings between 3 and 12 Vdc. Universal power plugs fit almost every product. Polarity switch. UL and CSA listed.



\$9.50 each

CAT # MOA-800

"CLAM SHELL" CELLULAR CONTROL HEAD MOUNTING KIT

The "Clam Shell" kit is designed for mounting a cellular phone control head in a vehicle. It will work well for mounting many kinds of communications or audio equipment in cars or elsewhere. Made of heavy-gauge steel, featuring a full 180 degree tilt, a pre-drilled top plate with threaded holes that fit a majority of cellular control heads, it includes complete mounting hardware.



\$2.50 each

CAT # CMT-2

RECHARGEABLE BATTERY 12 VOLTS 9 A/H

Rechargeable lead acid battery. Prepped for use in a product which hasn't yet come to market. They are 5.9" x 2.55" x 4.42" high and have a strip of foam padding stuck to one side. They have standard 1/4" quick-connect/ solder terminals. Weight: 8 lbs.




CAT # GC-129

\$28.50 each

8 for \$208.00

7 RELAYS, 4 VOLTAGE REGULATORS (and lots of other good stuff)

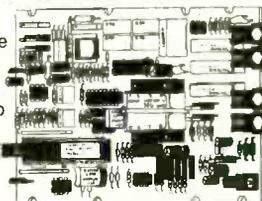This pc board was a telephone line-sharing switch. A great source of cheap parts. On it you will find 3 LM317T voltage regulators, 1 LM340T-5 regulator with heatsink, 2 crystals, seven relays, a power transformer, a 600 ohm coupling transformer and at least 50 other parts. The voltage regulators alone are worth \$5.00. Check it out!



CAT # EX-1218

\$3.50 each

SUB-MINIATURE SNAP ACTION SWITCH

CHERRY DG1C-BJ07 S.P.D.T. Body size: 0.51" long X 0.255" high X 0.255" wide. Lever with ridged end simulates roller action. Rated 3 amps @ 125 Vac, 2 amps @ 30 Vdc. PC pins on 0.2" centers. Large quantity available.




CAT# SMS-133

2 for \$1.00

100 for \$45.00
1000 for \$350.00

"HI-8" VIDEO CASSETTE (USED)

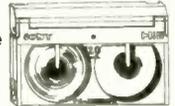SONY Hi-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box. Satisfaction Guaranteed.



\$3.00 each

CAT # VCU-8

10 for \$28.00 • 100 for \$250.00

PHOTO RESISTOR

Silonex # NSL 4582 Cadmium Sulfide photoconductive cell. 22 ohms in bright light. 2 meg ohms dark. Plastic encapsulated. 0.29" x 0.26" x 0.07". 1.5" long wire leads.




CAT # PRE-12 **75¢**

10 fc. \$6.00 • 100 for \$50.00

RANGE 20 METERS (65.6 FEET) INDOOR/OUTDOOR PHOTOELECTRIC SWITCH

SICK Optex # WS/WE260-M230 Invisible infrared beam and switch is useful for a variety of security, safety and sensing applications such as perimeter alarms, electric gate or garage door controls or conveyor line sensing. Modulated beam covers a 20 meter distance even with poor visibility. IP-66 enclosure rating makes it dust proof and splash resistant, suitable for most outdoor conditions. Light/dark switching selector. Sensitivity adjustment control. LED power and sense indicators. Two position cable entry gland (90 deg. apart) accepts 1/2" threaded conduit and a variety of wire sizes. Glass fiber-reinforced plastic housings are 3.05" x 2.5" x 1". Supply voltage: 22-240 Vac. Solid State Output: 0.5 amp (must have load to operate). Includes mounting brackets and hardware. UL and CSA listed.

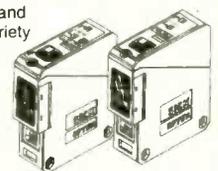

CAT # PES-4

\$40.00 each

ORDER TOLL FREE

1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524

<http://www.allcorp.com/>

E-MAIL allcorp@allcorp.com



NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D • Shipping and Handling \$5.00 for the 48 Continental United States - ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

CIRCLE 214 ON FREE INFORMATION CARD

www.americanradiohistory.com

May 1996, Electronics Now

EARN MORE MONEY!

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

Or, Call 1-800-932-4268 Ext. 210

COMMAND PRODUCTIONS


FCC LICENSE TRAINING, Dept. 210
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

NIGHT VIEWERS

SMALL PASSIVE NIGHT VIEWER KIT

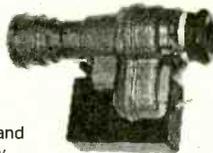Supplied with new and completely assembled USSR made scope. The EHT power supply is supplied in kit form. Will work in extremely low light levels! Best value small night vision scope available: \$220
Tube only from the above and EHT supply kit: \$90



FIBER OPTIC TUBES Used 1st gen. 25 or 40mm (input/output window dia). With a suitable 'fast' lens give a good image in half moon light. Can be IR assisted to see in total darkness. Each tube is supplied with an 9V - EHT power supply kit: 25mm tube \$90, 40mm tube \$120
We also have blemished versions of these tubes (not in central viewing area). Satisfaction guaranteed! Both sizes (please specify) & EHT kit \$35

INTENSIFIED NIGHT VIEWER KIT

See in the dark! Make your own night scope with good vision in sub-starlight illumination! We supply a 3-stage fiber optically coupled image intensifier tube and an EHT power supply kit, lens and eyepiece. 25mm \$270, 40mm \$360

IR TUBE AND SUPPLY A tube and supply combination that can be used as the basis of making a very sensitive IR responsive viewer. Typical sensitivity 0.01 lux. Tube and supply kit \$80

GEIGER COUNTER

Ready made Geiger counter detects dangerous Beta and Gamma rays. Plug-in probe, can be extended with cable, computer Interface (serial), visual and audible indication of detected particles. \$52

KITS and BITS

2-CHANNEL UHF REMOTE CONTROL KIT 1 Tx and 1 Rx \$31, extra Tx: \$12

4-CHANNEL UHF REMOTE CONTROL KIT Two Tx and one Rx: \$68

LASER BEAM COMMUNICATOR KIT: Tx, Rx, plus IR laser: \$39

PLASMA BALL KIT: PCB and components, needs a light bulb: \$18

SLAVE FLASH TRIGGER: Triggers a second flash unit by picking up light from camera mounted flash: \$5.50

SOUND TRIGGERED FLASH: Triggers flash from sound picked up by a microphone, adjustable: \$10

PC DRIVEN ELECTROCARDIOGRAM: Silk screened/solder masked PCB only and 3.5" disk with instructions. Uses common components: \$8

HIGH POWER IR LEDs 880nm 12² 30mW @ 100mA 10 for \$6

INFRARED FILTER Very high quality IR filter and plastic lens cover. Fits over most torches incl MAGLITES, for a good source of IR. Use with passive and active viewers. \$11

CCD CAMERA-VCR SECURITY SYSTEM

Ready made PIR detector module and learning IR remote control combination sets any IR remote controlled VCR to *RECORD* activity within a 6m range and 180° view. Starts recording at first movement and stops a few minutes after the last movement. Just like commercial systems costing \$1000's!! No connection needed to your VCR. PIR detector, control kit, IR learning remote control and instructions \$70

TINY PCB CCD CAMERA Mono, with auto iris lens, 0.1 lux, IR responsive, can be used in total darkness. 1.8 x 3.75 x 1 inch, weight 1.4 oz. Can be connected to video-in of a standard monitor or VCR. \$99

Email and the WWW

See and download our latest catalog and other info. Over 300 kits. Explore! <http://www.hk.super.net/~diykit>
email orders: oatley@world.net
(From Feb 96: oatley@ozemail.com.au)

LOW COST IR ILLUMINATOR KIT Use with CCD camera. Has 42 880nm/30mW LEDs. Variable power output, 10-15V DC operation. \$30

LASERS

HELIUM-NEON 633nm red laser tubes from new and near new equipment. Output power in the range of 2.5 to 7.5mW. Includes our 12V Universal Laser power supply. *Warning: High voltage at dangerous energy level!* 2.5-4mW tube & supply \$50 4-7.5mW tube & supply \$80

VISIBLE LASER

DIODE KIT 5mW 660nm visible laser diode and collimating lens, housing and driver kit. Easy to build, very small \$30



VEHICLE COMPUTER

Bicycle-vehicle computer, can be used on any size wheel! Speedometer, average & maximum speed, tripmeter, odometer, auto trip timer, clock, pick-up sensor/magnet and mounts supplied. \$25

TINY FM TRANSMITTER

Tiny ready-made self-contained FM transmitter in a small black metal case. Powered by single 1.5V silver oxide LR44/G13 battery with inbuilt mic. Tuning range 88-108MHz, battery life 60 hours, weight 15g, Dimensions: 1.3" x 0.9" x 0.4". \$27

OATLEY ELECTRONICS (AUSTRALIA)

Phone 011 61 2 579 4985

Phone orders Sunday to Thursday

East Coast from 7pm to 2am West Coast 4pm to 11pm

Fax 011 61 2 570 7910

Mastercard, Visacard, American Express cards with phone, fax and email orders

P&P for most orders by Federal Express \$15 - \$25

All prices are in US dollars

Electronic CAD for Windows


Professional Windows tools at an affordable price with powerful features to make designing faster. WinBoard PCB layout delivers sophisticated interactive routing for complex designs, plus it has the tools needed for high-speed circuits, analog, RF and SMT designs.

WinDraft® Schematics

- ◆ 32 bit Windows application with multiple document interface and floating toolbar.
- ◆ Supports hierarchical designs and electrical rules checking.
- ◆ Over 11,000 unique library parts and symbol editor included.

WinBoard™ PCB layout

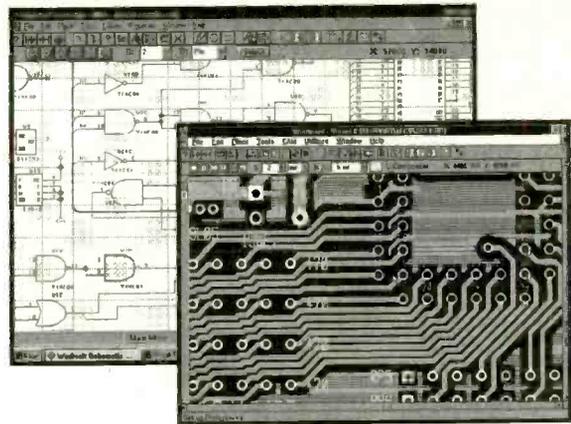- ◆ Supports 16 layers, multiple copper pours, and advanced features for RF designs.
- ◆ Complete through hole and SMD library.
- ◆ CAM Support includes BOM, in-circuit test, NC Drill, Gerber, Pick & Place, DRC.



Prices start at only ... \$250

Information is available on the Ivex World Wide Web. An evaluation copy with a complete 80 page Getting Started Guide is only \$20.

World Wide Web: <http://www.ivex.com>

Tel: (503) 531-3555
 Fax: (503) 629-4907
 BBS: (503) 645-0576



CIRCLE 318 ON FREE INFORMATION CARD

CONTROL

RELAYS • LIGHTS • MOTORS

MEASURE

TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY

INPUT

SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

MODEL 30 \$79  <ul style="list-style-type: none"> • PLUGS INTO PC BUS • 24 LINES DIGITAL I/O • 8 CHANNEL- • 8 BIT A/D IN • 12 BIT COUNTER • UP TO 14K BMP/SEC 	MODEL 45 \$189  <ul style="list-style-type: none"> • RS-232 INTERFACE • 8 DIGITAL I/O • 8 ANALOG INPUTS • 2 ANALOG OUTPUTS • 2 COUNTERS-24 BIT
MODEL 100 \$279  <ul style="list-style-type: none"> • 12 BIT 100 KHZ A/D • 4 ANALOG OUTPUTS • 3 TIMER COUNTERS • 24 DIGITAL I/O 	MODEL 60 \$179  <ul style="list-style-type: none"> • 8 2-AMP RELAYS • 16 DIGITAL I/O • 1 6-BIT ANALOG INPUT
MODEL 40 \$99  <ul style="list-style-type: none"> • RS-232 INTERFACE • 28 LINES DIGITAL I/O • 8 ANALOG INPUTS • PWM OUTPUT • OPTIONAL 12 BIT A/D 	MODEL 70 \$239  <ul style="list-style-type: none"> • RS-232 INTERFACE • 18 BIT A/D • 5.5 DIGIT • UP TO 60 BMP/SEC

NEED A CUSTOM PCB? TRY US.

PRAIRIE DIGITAL, INC.


PHONE 608-643-8599 • FAX 608-643-6754
 846 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53578

CIRCLE 225 ON FREE INFORMATION CARD

Make your projects speak for themselves... Ours do!

DIGITAL VOICE RECORDERS

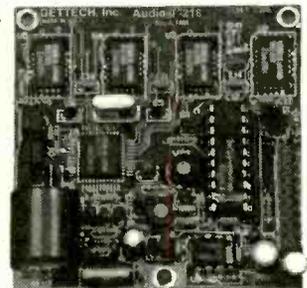- Record up to 218 seconds
- 1 to 8 messages
- High quality speech 12 bit
- Switch-closure actuation
- Sample rates up to 20Khz
- On-board backup
- Direct speaker output
- Wide operating range
- Small size 2.6" X 2.6"
- Made in U.S.A.



MODEL AudioQ™-218

Call or write for more information
 OEM price and delivery available
 Custom designs and enclosures
 Single unit price \$149.00 plus s+h
 Quantity pricing as low as \$99.00

GETTECH Inc.

402 Riley Road, New Windsor, NY 12553
 (914) 564-5347

Specifications and price subject to change.

RF POWER TRANSISTORS AND TUBES


In depth stocking of popular and hard-to-find Electronics Parts.

Transistors

2SC1969
2SC2290 • 2SC2879
2SC2312
2SC2879
MRF454 • MRF455

Tubes

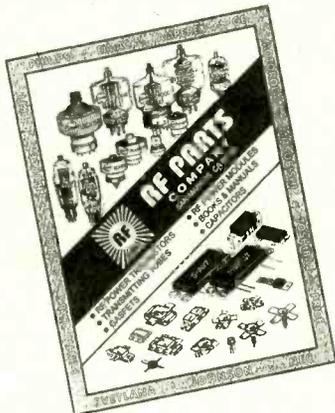6KD6 • 6LF6
6LQ6 • M2057
8950 • 6146B
811A • 572B
3-500Z • 3-500ZG



Order your **FREE** copy of our new Catalog by writing or calling us now.

Tel: (619) 744-0700 • Fax: (619) 744-1943



RF PARTS

435 SOUTH PACIFIC STREET
SAN MARCOS, CA 92069

DIRECT FREQUENCY READOUT SCPC AUDIO RECEIVER

FULL COMMERCIAL FEATURES



UNIVERSAL SCPC-200 AUDIO RECEIVER

SERVICES ON SCPC RADIO

All Sports • News Networks • AP - UPI • Radio Nets • Talk Shows • Hometown Sports • Music - Classical, Jazz, Rock • Major Radio Stations • Financial News • Over 430 Channels and Growing.

FEATURES OF THE SCPC-200

Easy Direct Frequency and Transponder Tuning - 50 TO 90 MHz (LCD) • 50 Channel Memory Bank • C and Ku Band Agile - 950 - 1450 MHz • Automatic LNB Drift Compensation (ADC) • Automatic Companding • Digital Frequency Lock-On (DFL) • High Quality Audio • Commercial Digital Synthesizer • Full LCD Display • Built in U.S.A. by the Leading SCPC Receiver Manufacturer

INTRODUCTORY PRICE \$399 plus S & H - CALL: 1-614-866-4605

UNIVERSAL ELECTRONICS, INC.

Communications Specialists
4555 GROVES RD., SUITE 12, COLUMBUS, OH 43232
(614) 866-4605 FAX (614) 866-1201


\$449⁹⁵

Device Programmers

\$139⁹⁵

48 PIN ZIF

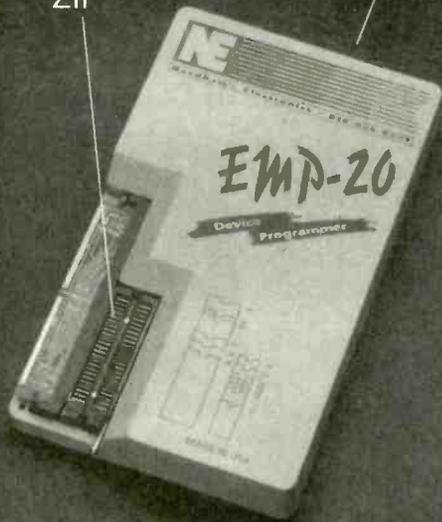Connects to standard PC parallel printer port



9^{1/2} x 5^{3/4} x 1^{1/4}


EMP-20

- Easy to use software, on-line help, full screen editor
- **Fast Programming** (EMP-20)
27C010A, 23 seconds
28C020, 34 seconds
27C040, 95 seconds

Made in USA

- 1 Year Warranty
- Technical Support by phone
- 30 day Money Back Guarantee
- FREE software upgrades available via BBS
- Demo SW via **BBS (EM20DEMO.EXE) (PB10DEMO.EXE)**
- **E(e)proms** 2716 - 8 megabit, 16 bit 27210-27240, 27C400 & 27C800,
- **Flash** 28F256-28F020, (29C256-29C010 (EMP-20 only))
- **Micros** 8741A, 42A, 42AH, 48, 49, 48H, 49H, 55, 87C51, 87C51FX, 87C751,752
- **GAL, PLD** from NS, Lattice, AMD-16V8, 20V8, 22V10 (EMP-20 only)

PB-10 Internal Card for PC

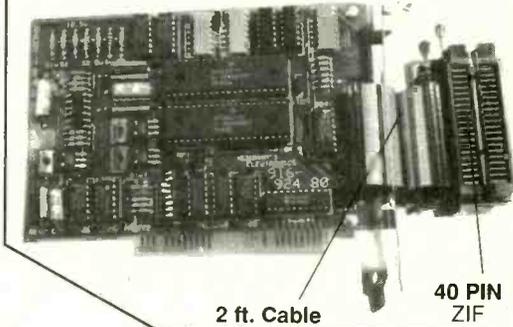

2 ft. Cable

40 PIN ZIF

FOR MORE INFORMATION CALL

4630 Beloit Drive, Suite 20
Sacramento, CA 95838
(Monday-Friday, 8 am-5 pm PST)

NEEDHAM'S ELECTRONICS, INC.



C.O.D.



(916) 924-8037
BBS 916-924-8094
FAX 916-924-8065

Parts Express™

301 Standard PanaVise

Designed for the professional and hobbyist, the model 301 turns, tilts and rotates to achieve the desired position. Durable nylon jaws open 2-1/4". Net weight: 3 lbs.

PANA VISE



#EN-365-305 \$39⁹⁵ EACH

Headband Magnifier


Features double lens for choice of 2.2x or 3.3x magnification and Velcro type headband. Net weight: 1/2 lb.



#EN-360-672 \$19⁹⁵ EACH

GoldStar Oscilloscopes

GoldStar

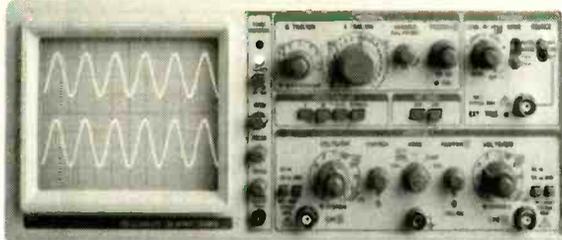

Part #	GoldStar #	Description	Price
EN-394-116	OS9100P	100MHz	\$899.95
EN-394-115	OS9060D	60MHz	699.95
EN-394-110	OS9040D	40MHz	599.95
EN-394-105	OS9020G	20MHz w/generator	449.95
EN-394-100	OS9020A	20MHz	349.95

Weller WLC100 Soldering Station

The Weller WLC100 solder station is adjustable from 5 to 40 watts. Includes 40 watt pencil iron. UL approved. Net weight: 1-3/4 lbs. One year manufacturer warranty.



Weller

\$39⁹⁵ EACH

#EN-372-120

CAIG DeoxIT Deoxidizer

DeoxIT is a fast-acting deoxidizing solution that cleans, lubricates, and improves conductivity on all metal connectors and contacts. Seals and protects all electrical connections. Reduces intermittent failures, arcing, wear, and abrasion. Temperature range: -34 degrees C to 200 degrees C. Use as a general treatment for connectors, contacts, and other metal surfaces.

NEW!
MINI
SPRAY


CAIG
LABORATORIES, INC.



Part #	CAIG #/Description	Solution	Price (1-11)	Price (12-23)	Price (24-UP)
EN-341-200	DeoxIT D5, 5 oz. Spray	5%	\$7.95	\$7.15	\$6.45
EN-341-202	DeoxIT Mini Spray, 15 g.	5%	4.95	4.50	3.95
EN-341-205	DeoxIT D100, 2 oz. Spray	100%	10.95	9.85	8.85
EN-341-210	DeoxIT Pen Applicator	100%	9.95	8.95	8.05
EN-341-215	DeoxIT Vial w/brush, 7.4 ml.	100%	6.95	6.25	5.65
EN-341-220	DeoxIT Precision Dispenser	100%	14.95	13.45	12.10

B & W CCD Board Cameras

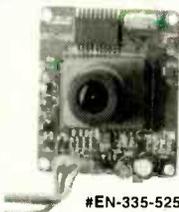Ultra miniature, high performance 1/3" CCD single board cameras feature a built-in 3.6mm wide angle lens and 400 lines of resolution. Requires a 12 VDC power supply (our #120-1100). Dimensions: 1-1/2" W x 1-3/4" H x 1" D.



#EN-335-525



#EN-335-530

#EN-335-525 (Standard lens) \$149⁹⁵ EACH

#EN-335-530 (Pin hole lens) \$169⁹⁵ EACH

#EN-120-1100 (12VDC power supply) \$7¹⁵ EACH

150 MHz Oscilloscope Probe Kit


Deluxe probe kit features a modular design for longer life, switchable 10:1 probe with 150 MHz bandwidth, 2.8 ns rise time, and adjustable capacitance from 10-35 pF. 60" in length. Kit includes 6" detachable ground lead, sprung hook, trimming tool, 2 channel identifier clips, and replacement tip. Includes plastic case.


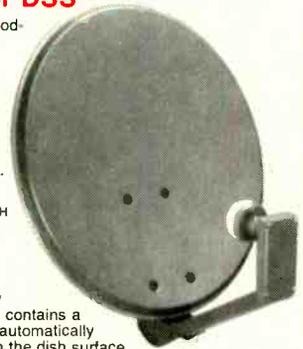
#EN-390-100 \$29⁹⁵ EACH

Sure Shot 18" Dish for DSS®

Built heavier and stronger than OEM models, able to withstand 120 MPH wind gusts! "Perfect Curve" manufacturing process allows for maximum signal reflectivity. Ideal for replacement of damaged OEM dishes or for additional viewing locations. Sure Shot comes complete with mounting hardware and instructions. Limited lifetime warranty. LNBF not included. Net weight: 13 lbs.



#EN-210-405 \$49⁹⁵ EACH

Hot Shot 18" Dish for DSS®

The Hot Shot features the same quality construction as the Sure Shot, but also contains a safe low voltage, heating element that automatically eliminates ice, snow, and moisture from the dish surface. Hot Shot comes complete with mounting hardware, heater power supply and instructions. Note: 2 conductor, 18 gauge heater wire not included. Limited lifetime warranty. LNBF not included. Net weight: 27 lbs.

#EN-210-400 \$139⁹⁵ EACH

Grundig LNBFs

Made in England quality! Designed to work in extreme real world conditions. Features "true circular polarization". For use with the Sure Shot and Hot Shot dishes or as a replacement for lightning damaged RCA DSS LNBFs. Available in single or dual feed. 18 month warranty. Net weight: 1 lb.

#EN-210-420 (Single feed) \$79⁹⁵ EACH

#EN-210-425 (Dual feed) \$99⁹⁵ EACH

Phone FM Transmitter Kit



This small circuit, when connected to a phone line, transmits both sides of a telephone conversation into the FM radio band in the 90-95MHz area. The phone line itself is used as an antenna. Includes all components and instructions.

#EN-320-067 \$9⁹⁵ EACH

2 Stage FM Transmitter Kit



Easy to build and tune in the upper part of the FM band. Reaches over 1/2 mile (depending on conditions). Uses RF transistor for its final stage. Requires a 9V battery (not included). High quality PCB and components. Circuit schematic provided.

#EN-320-066 \$10⁹⁵ EACH

**FREE CATALOG
CALL TOLL FREE
1-800-338-0531**



340 E. First St., Dayton, OH 45402-1257 ♦ Phone: 513-222-0173 ♦ Fax: 513-222-4644

♦30 day money back guarantee ♦\$20.00 minimum order ♦We accept Mastercard, Visa, Discover, and company C.O.D. orders ♦24 hour shipping ♦Shipping charge - UPS chart rate + \$1.90 (\$5.00 minimum charge) ♦Hours 8:00 am - 8:00 pm ET, Monday - Friday ♦9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ♦Foreign destination customers please send \$5.00 U.S. funds for catalog. ♦Quantity pricing available.

CIRCLE 262 ON FREE INFORMATION CARD

Tel: (954) 974-6864
 Fax: (954) 974-6818

Gateway Products Corp.

Please mail orders to:
 P. O. Box: 93-6397
 Margate, FL 33093

Popular I.C.s

LM324...45¢
 LM339...45¢
 LM358...45¢
 NE555...40¢
 LM556...50¢
 LM741...40¢

Deal U3: 12 pcs total,
 (2pcs of each)...\$5.00

Transistors

PN2222A...7¢
 PN2907A...7¢
 2N3904...7¢
 2N3906...7¢
 2N4401...7¢
 2N4403...7¢

Deal N8: 80 pcs total,
 (10pcs of ea.)...\$4.00

Semiconductors

74LS174...40¢
 74LS244...45¢
 74LS245...45¢
 74LS374...45¢
 LM386N...45¢
 MC1488...45¢
 MC1489...45¢

DIODES

1N914...3¢
 1N4148...3¢
 1N4001...1A/50V...3¢
 1N4004...1A/400V...4¢
 1N4007...1A/1KV...5¢

Deal P7: 50 pcs total,
 (10pcs of ea.)...\$2.00

RADIAL LYTICS

1uF/50V...6¢
 2.2uF/50V...6¢
 3.3uF/50V...6¢
 4.7uF/50V...6¢
 10uF/50V...7¢
 22uF/50V...8¢
 33uF/50V...8¢
 47uF/50V...10¢

Deal A2: 40 pcs total,
 (5pcs of each)...\$3.00

Ceramic Disc
 (All caps rated 50V)

10pF...6¢
 22pF...6¢
 27pF...6¢
 33pF...6¢
 47pF...6¢
 100pF...6¢
 150pF...6¢
 220pF...6¢

Deal R4: 40 pcs total,
 (5pcs of each)...\$2.50

Toggle Switches

Miniature size
 1/4" Panel hole

on-on...SPDT...50¢
 on-off-on...SPDT...80¢
 on-on...DPDT...70¢
 on-off-on...DPDT...80¢

Deal S3: 8 pcs total,
 (2pcs of each)...\$5.00

Popular CMOS

CD4001B...30¢
 CD4011B...30¢
 CD4013B...40¢
 CD4017B...50¢
 CD4028B...40¢
 CD4050B...40¢
 CD4068B...40¢
 CD4069B...40¢

Deal V8: 16 pcs total,
 (2pcs of each)...\$5.00

More Transistors

MPSA05...15¢
 MPSA13...15¢
 MPSA27...15¢
 MPSA42...15¢
 MPSA06...15¢
 MPSA92...15¢

Deal Q2: 30 pcs total,
 (5 pcs of ea.)...\$4.00

V. Regulators

LM317T...70¢
 7805...50¢
 7808...50¢
 7812...50¢
 7815...50¢
 7818...50¢
 7824...50¢
 7905...50¢
 7908...50¢
 7912...50¢
 7915...50¢
 78L05...40¢
 79L05...40¢
 78L12...40¢

Power Diodes

1N5401...3A/100V...8¢
 1N5404...3A/400V...9¢
 1N5408...3A/1KV...10¢
 6A10...6A/100V...24¢
 6A100...6A/1KV...32¢

Deal H8: 25 pcs total,
 (5pcs of ea.)...\$3.00

RADIAL LYTICS

10uF/25V...6¢
 22uF/25V...6¢
 33uF/25V...6¢
 47uF/25V...7¢
 100uF/25V...8¢
 220uF/25V...9¢
 330uF/25V...14¢
 470uF/25V...17¢

Deal A7: 40 pcs total,
 (5pcs of each)...\$4.00

Ceramic Disc
 (All caps rated 50V)

270pF...8¢
 330pF...8¢
 470pF...8¢
 .001uF...8¢
 .01uF...8¢
 .022uF...8¢
 .047uF...8¢
 1uF...8¢

Deal R7: 40 pcs total,
 (5pcs of each)...\$2.50

DEAL W2...\$2.50

120 pcs total (20 pcs of
 each: 10K, 47K, 100K,
 1k, 4.7k. All 1/4W 5%.

DEAL W5...\$2.50

100 pcs total (20 pcs of
 each: 10K, 47K, 100K,
 470K, 1M. All 1/4W 5%.

DEAL M3...\$5.00

7805 7812
 7905 7912
 12 pcs total
 (3pcs of each)

More Transistors

2N2222A...30¢
 2N4124...13¢
 2N4128...13¢
 2N5401...16¢
 MPSH10...15¢
 2N3055...65¢
 TIP31C...55¢
 TIP32C...55¢
 TIP117...55¢
 TIP120...60¢
 TIP125...65¢

CRYSTALS

3.5795MHz...65¢
 4.0000MHz...95¢
 11.0000MHz...95¢
 11.0592MHz...95¢

1W Zener Diodes

1N4728A...3.3V...10¢
 1N4733A...5.1V...10¢
 1N4739A...9.1V...10¢
 1N4742A...12V...10¢
 1N4744A...15V...10¢
 1N4748A...18V...10¢

Deal Z5: 30 pcs total,
 (5pcs of ea.)...\$2.50

1A SCHOTTKY

1N5817...1A/20V...20¢
 1N5818...1A/30V...23¢
 1N5819...1A/40V...24¢

Deal Y8: 9 pcs total,
 (3pcs of each)...\$2.00

Mono Caps...8¢ea

.01uF/50V .047uF/50V
 .022uF/50V .1uF/50V

Deal B5: 40 pcs total,
 (10pcs of ea.)...\$2.50

400V BRIDGES

1Amp 1.5Amp
 4Amp

DF04M...DIP...40¢
 W04M...Round...35¢
 KBL04...In-line...90¢

Deal X8: 6pcs total,
 (2pcs of each)...\$3.00

DEAL J1...\$3.50

78L05
 78L12
 10 pcs total
 (5pcs of each)

5mm (T1 3/4) Diffused LEDs

Red...8¢
 Green...10¢
 Yellow...12¢

Deal L3: 30 pcs total,
 (10pcs of ea.)...\$2.50

Computer Stuff

6ft printer cable...\$4
 8ft VGA extension...\$4
 3-b serial mouse...\$9
 101 key keyboard...\$19
 1.44Mb 3.5" drive...\$29
 1Gb hard drive...\$230

Germanium Diodes

1N34A...14¢
 1N60...14¢
 1N270...28¢

Deal G5: 18 pcs total,
 (6pcs of ea.)...\$2.50

3A SCHOTTKY

1N5820...3A/20V...32¢
 1N5821...3A/30V...36¢
 1N5822...3A/40V...40¢

Deal Y9: 9 pcs total,
 (3pcs of each)...\$3.00

Tantalum Caps

1uF/35V...18¢
 2.2uF/35V...22¢
 10uF/35V...50¢

Deal T6: 15 pcs total,
 (5pcs of each)...\$3.50


SOLDER ROLL

SN63/37
 .031" dia
 1 Lb Roll
\$7.80

 \$10.00 minimum order. We accept VISA, MC, MO, Check, No-CODs. Please add \$5.00 for shipping & handling (foreign addresses: \$8.50). Florida addresses add 6% sales tax. Hours: Mon-Fri: 9AM to 5PM, Sat: 9AM to 12PM (EST). All new premium parts. Send for free Catalog.

CIRCLE 220 ON FREE INFORMATION CARD

Video Camera Blowout Sale!

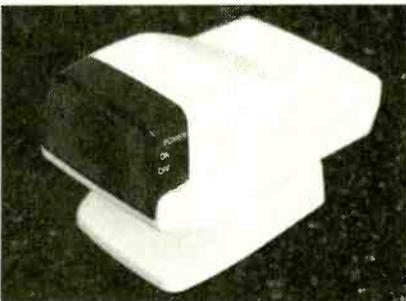

When a major multimedia company closed a division, they surplused a limited quantity of quality **COLOR CCD** video cameras. These cameras were part of a high end video conferencing system.

Manufactured by a division of Panasonic, these units are designed to sit on top of a computer monitor and can be used for video conferencing, security, ATV, or multimedia purposes.


- 330 line **COLOR CCD** imager
- 3 lux sensitivity for low light applications
- Standard IV p-p NTSC output
- Built-in microphone with preamp
- Standard RCA video and audio jacks
- Includes 12v wall mount transformer
- Auto iris with sensitivity adjust
- 5mm fixed focus lens from 10" to infinity
- 5" long x 3" wide x 3" high - 7.5oz.

**Call Today!
 Limited Quantity!**

This OEM paid over \$400.00 each. **Your price is only \$179.00 plus \$5.00 shipping/handling** (continental US only).

Sycard Technology MasterCard and Visa accepted
 1180-F Miraloma Way CA orders add Sales Tax
 Sunnyvale, CA 94086 Sorry, No CODs
 (408) 749-0130 or (408) 749-1323 Fax

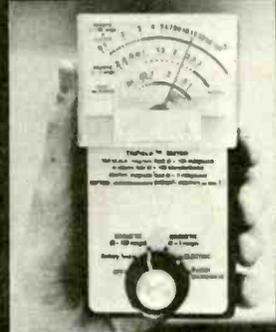NOW YOU CAN "SEE" INVISIBLE FIELDS AND AVOID THEM



Most homes and offices have hot spots with strong artificial electro-magnetic fields, where chronic exposure may cause mental or physical problems. Even the EPA names these fields as suspected carcinogens. You can reduce your risk by avoiding these high-field areas.


The **TriField™** meter detects far more of these fields than any other electromagnetic pollution meter. It's the only one that independently reads AC electric fields, AC magnetic fields, and radio/microwaves. It also reads field strengths in all directions simultaneously. Every other meter that sells for under \$500 reads only magnetic and only in one direction — they can entirely miss a magnetic field unless pointed correctly and are blind to radio/microwaves and electric fields, both of which cause biological effects.

The **TriField™** meter reads all three types of fields numerically and with a SAFE/BORDERLINE/HIGH SCALE, weighted proportional to effect on the body. Thresholds are based on epidemiological and laboratory studies. (While no absolute hazard thresholds have been established, reduction of relative exposure is prudent.)


The **TriField™** meter comes ready-to-use with battery, instructions, and one-year limited warranty. The cost is \$144.50 postpaid.

AlphaLab, Inc. / 1280 South Third West / Salt Lake City, UT 84101-3049
 For literature and information, call (503) 543-6545

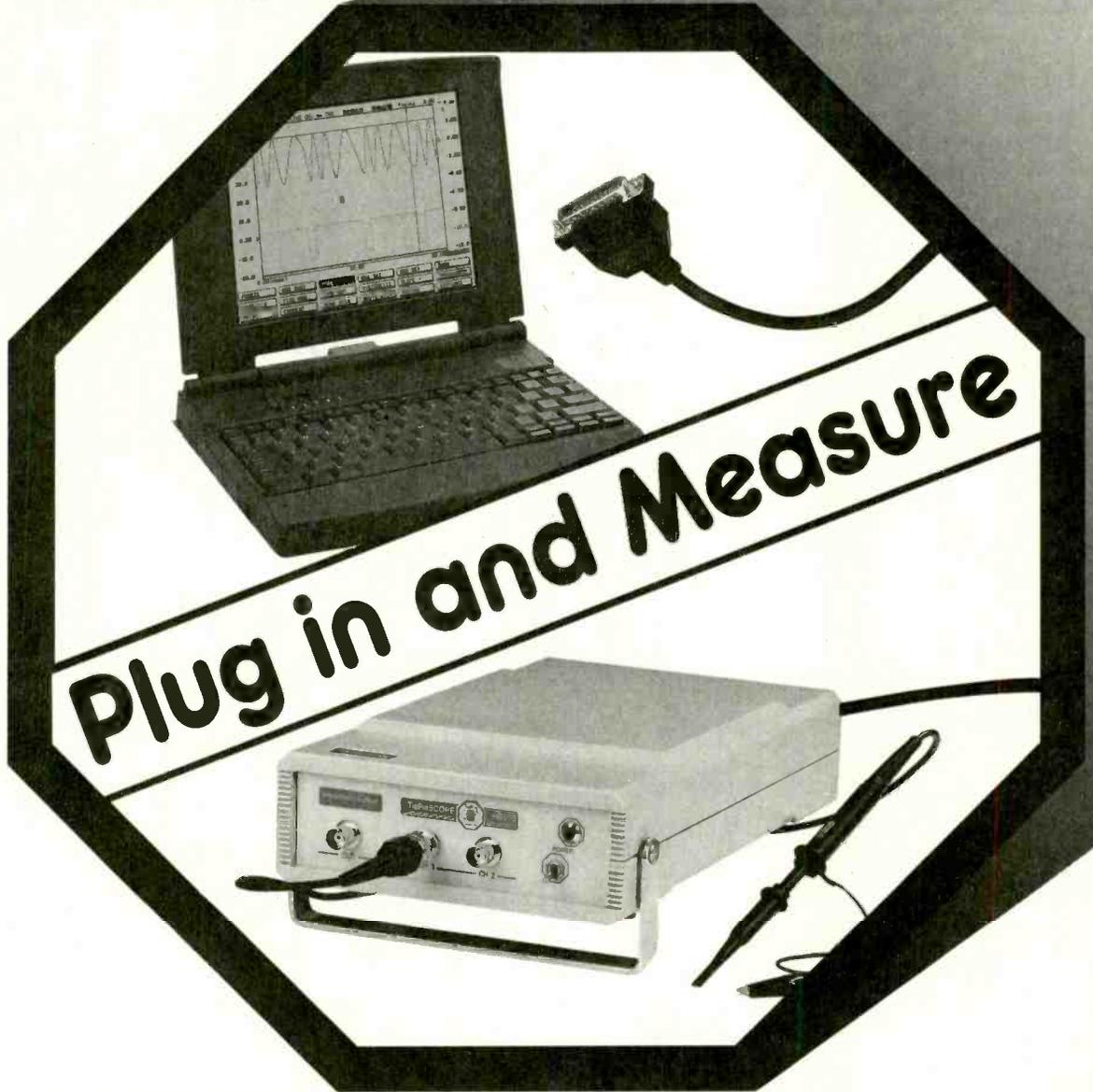STOP! Just Take Two Steps to do Your Measurement



TiePieSCOPE

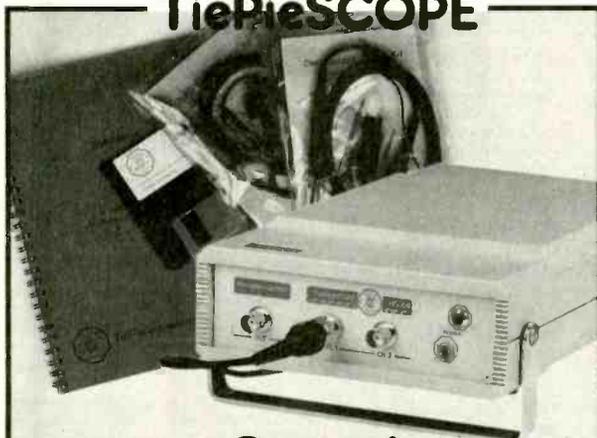

HS508 Complete set for US \$1054

You can simply plug the new TiePieSCOPE - HS508 into the parallel port of your portable or desktop PC. With the advanced software, you can use this two channel, 8 bits, 50 MHz measuring instrument as a fast digital storage oscilloscope, including a lot more features than a single oscilloscope! Moreover, the TiePieSCOPE - HS508 contains a multiple display voltmeter (up to 5 MHz true RMS), a spectrum analyzer with an harmonic distortion meter and a transient recorder for recording a variety of signals.

The TiePieSCOPE - HS508 is supplied complete with user manual, software, and two probes.

Call now for a free demo diskette and our catalog!!
Toll-free: 1-800-626-6929

CONWAY Engineering, Inc.

8393 Capwell Drive, Oakland, California USA 94621-2113
Tel.: 510 568-4028 - Fax: 510 568-1397 BBS Tel.: 510 568-6533

Internet Address: <http://www.crl/~conway/>

CIRCLE 310 ON FREE INFORMATION CARD

ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT
BEST PRICE




DMM 89 \$179.00

Most Advanced DMM
All Purpose & Communication
-80.7 to 81.4 dBm with 4Ω-1200Ω
20 reference impedances
True RMS
Frequency counter: 0.01Hz-10MHz
Capacitance: 1pF-50,000μF
Measure AC volt to 20kHz
5000 counts, 0.1% accuracy
Auto/manual range, fast bar graph
Min/Max/Ave/DH/Relative/Zoom
Auto power off
Input warning
Splash proof
Volt, amp, ohm, logic, diode, continuity
Ruggedized case
Rubber holster included



DMM 2360 \$449.95 NOW \$109.95

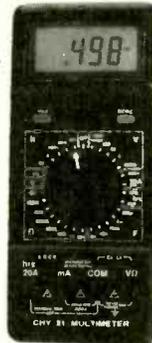DMM+LCR Meter
Inductance: 1μH-40H
Capacitance: 1pF-40μF
Frequency: 1Hz - 4MHz
Temperature: -40-302°F
TTL Logic Test: 20MHz
Diode, Continuity
Volt, Amp, Ohm
3999 count display
Peak Hold
Auto power off
Ruggedized case
Temperature probe included



DMM 20 \$74.95

Inductance: 1μH-40H
Capacitance: 1pF-200μF
Frequency: 1Hz-20MHz
Volt, amp, ohm, diode,
20 Amp AC/DC current
Transistor HFE
Continuity, duty %
Peak hold/Max
Ruggedized case
Rubber holster \$8.00

Full line of DMMs,
economy, compact,
ruggedized, solar cell,
automotive, heavy
duty, industrial,
starts from \$19.95

Fluke Multimeter
Fluke 12 \$84.95
Holster C-10 \$10
Fluke 70 II \$75.95
Fluke 73 II \$97.50
Fluke 75 II \$129
Holster C-70 \$16
Fluke 77 II \$155
Fluke 79 II \$175
Fluke 29 II \$175
Fluke 76 \$175
Fluke 87 \$287
Fluke 867 \$1199
Fluke 97
Scope Meter \$1785
Fluke 105
Scope Meter \$2799



LCR Meter 131D \$229.95


Most Advanced LCR
Dual display: L/Q or C/D
Inductance: 0.1μH-1000H
Capacitance: 0.1pF-10,000μF
Impedance: 1mΩ-10MΩ
0.7% basic accuracy
Auto/manual range
Dissipation factor & Q factor
Serial & parallel mode
Relative mode for comparison
and to remove parasitics
Statistics, tolerance,
Best for design, incoming
testing & production
SMD and chip component
test probe \$25.00



LCR Meter 814 \$189.95

Best Resolution LCR
Inductance: 0.1μH-200H
Capacitance: 0.1pF-20,000μF
Resistance: 1mΩ-20MΩ
1% basic accuracy
Dissipation factor indicates leakage
in capacitor and Q factor in inductor
Zero adjustment to reduce parasitics
Best for high frequency RF
SMD and chip component test probe
\$25.00

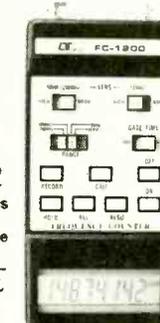
LIMITED QUANTITY SPECIAL
DIGITAL LCR 680 \$74.95
0.1pF, 1μH, 10mΩ resolution



Frequency Counter FC-1200 \$129.95

Frequency: 0.1Hz-1.25GHz
Display: 8 digit LCD
Period: 0.1μs-0.1s
Records Max/Min/Average
Data hold, relative mode
Telescoping antenna \$8.00
Deluxe case \$5.00

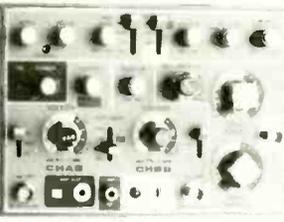Also Available:
AC/DC clamp meter, Light meter,
Thermometer, pH meter, High
voltage probe, Digital caliper,
Anemometer, Electronic scale,
Force gauge, Tachometer,
Stroboscope, Humidity & EMF
adapter, Sound level meter,
Frequency counter, SWR/field
strength/power meter, Dip meter




20 MHz Oscilloscope with Delay Sweep PS-205 \$429.95

Dual Trace, Component test, 8" CRT, X-Y Operation, TV
Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes
each has x1, x10 switch. Best price with delay sweep.
PS-200 20 MHz DUAL TRACE \$339.95
PS-400 40 MHz DUAL TRACE \$484.95
PS-405 40 MHz DELAY SWEEP \$569.95
PS-605 80 MHz DELAY SWEEP \$789.95
PS-1000 100 MHz DUAL TRACE \$989.95
Scope Probe: 60MHz x1, x10 \$15, 100MHz x1, x10 \$22
250MHz x1, x10 \$28, 250MHz x100 \$39


Digital Storage Scope DS-303 30MHz, 20M Sample/sec \$849.95

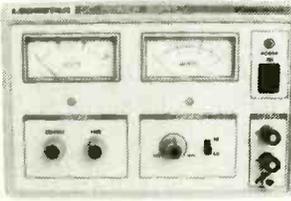DS-303P with RS-232 interface \$1,049.95
Switchable between digital and analog modes
2 K word per channel storage
8 bit vertical resolution (25 Level/div)
Expanded Timebase 10ms/div - 0.5 s/div
Refresh, Roll, Save all, Save CH2, Pre-Trig
Plotter control



DC Power Supply PS-303 \$159.00

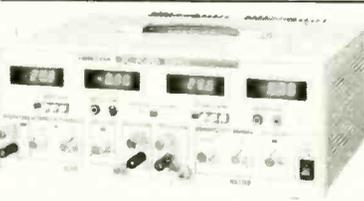0-30 VDC, 0-3A output
Constant voltage & constant current mode
0.02% + 2mV line regulation
0.02% + 3mV load regulation
1 mVrms noise and ripple
Short circuit and overload protected
PS-8200 with digital voltmeter \$179.00
Also available: 30V/5A, 60V/3A, 60V/5A
16V/10A, 30V/10A



DC Power Supply Triple Output PS-8202 \$499.95

Two 0-30 VDC, 0-3A outputs
One fixed 5VDC, 3A output
Capable of independent or tracking operation
Constant voltage and constant current mode
Four digital meters for volt and current display
Excellent regulation and low ripple
Short circuit and overload protected
Also available: 30V/5A, triple output \$549.95
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A



RF SIGNAL GENERATOR SG-4160B \$124.95

100 kHz-150MHz Sinewave in 6
ranges
RF Output 100mVrms to 35 MHz
Internal 1kHz, External 50Hz-20kHz
AM modulation
Audio output 1 kHz, 1 Vrms

AUDIO GENERATOR AG-2601A \$124.95

10Hz - 1MHz In 5 ranges
Output: 0-8Vrms sinewave
0-10Vp-p squarewave
Synchronization: ±3% of oscillation
frequency per Vrms
Output distortion:
0.05% 500Hz - 50kHz
0.5% 50Hz - 500kHz
Output impedance: 600 ohm

FUNCTION GENERATOR FG-2100A \$169.95

0.2 Hz - 2 MHz in 7 ranges
Sine, square, triangle, pulse and ramp
Output: 5mV-20Vp-p
1% distortion, DC offset ± 10V
VCF: 0-10V control frequency to 1000:1



RF SIGNAL GEN./COUNTER SG-4162 AD \$229.95

Generates RF signal same as
SG-4160B
8 digit frequency counter 1Hz - 150
MHz for internal and external
source Sensitivity <50mV

AUDIO GEN./COUNTER AG-2603AD \$229.95

Generates audio signal same as
AG-2601A
8 digit frequency counter 1Hz-
150MHz for internal and external
sources Sensitivity <50mV

FUNCTION GEN./COUNTER FG-2102AD \$229.95

Generates signal same as FG-2100A
Frequency counter 4 digits
Feature TTL and CMOS output

SWEEP FUNCTION GEN./COUNTER \$329.95

0.5Hz to 5 MHz in 7 ranges
Sweep: Linear 10:1/Log 10:1 20ms to 2s
AM Modulation
Gated Burst, Voltage Control Generator
Generator Control Voltage & 8 digit counter
1Hz-10MHz for internal & external sources

ALFA ELECTRONICS
741 Alexander Rd., Princeton, NJ 08540

(800) 526-2532/(609) 520-2002 15 DAY MONEY BACK GUARANTEE. 1 YEAR WARRANTY
FAX:(609) 520-2007 CALL OR WRITE FOR FREE CATALOG AND BEST OFFER.
Visa, Master Card, American Express, COD, Purchase Order Welcome
CIRCLE 213 ON FREE INFORMATION CARD

Electronics Now, May 1996

100 MHz Cursor Readout Scope 4 ch, 8 traces OS-6101 \$1,499.95



- * 4 independent channels, 8 traces
- * Time/Voltage cursor measurement
- * ALT triggering function for 4 ch.
- * Sweeps to 2ns/div, Delayed Sweep
- * TV Sync., Ch. 1 output, Z-axis input
- * 2 probes(x1, x10)

100 MHz Scope, 4ch. 8 traces Best value all purpose scope OS-6100B \$1,329.95




- * 4 channels, 8 traces
- * High sensitivity 500µV/div
- * Sweeps to 2ns/div, Delayed sweep
- * 20 kV accelerating voltage
- * TV sync., Z-axis input
- * A and B gate output
- * Best price 100 MHz scope
- * 2 probes(x1, x10)

50 MHz Triggering Oscilloscope OS-653 \$699.95



- * Dual Channel
- * Hold Off Function
- * Delayed Sweep
- * Built-in Delay Line
- * TV Sync
- * ALT Triggering
- * High sensitivity 1 mV/div
- * Trigger level lock function
- * Z-axis input, CH1 output
- * 2 probes(x1, x10)

20 MHz Oscilloscope OS-622B \$344.95

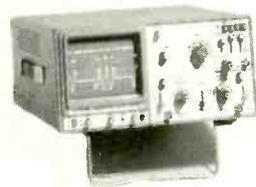

- * Dual trace, X-Y operation
 - * TV Sync., Z-axis input, CH1 output
 - * High sensitivity 1 mV/div
 - * Trigger level lock
 - * 2 probes (x1, x10)
- OS-623B - 20 MHz w/Delayed Sweep..... \$ 449.95
OS-935 - 5 MHz One channel..... \$ 209.95

DC Linear Power Supplies Single Output



- * Constant voltage and constant current mode
 - * Voltage regulation ≤0.01%
 - * Current regulation ≤0.2%
 - * Low ripple and noise
 - * Overload and reverse polarity protection
 - * Features 2 analog or 1 digital meter(PS series)
2 analog or 2 digital meters(PR series)
- | | |
|---------------------------------|----------|
| PS-1830 : (0-18V, 0-3A)..... | \$209.95 |
| PS-1830D : Digital Display..... | \$219.95 |
| PS-1850 : (0-18V, 0-5A)..... | \$219.95 |
| PS-1850D : Digital Display..... | \$244.95 |
| PS-3030 : (0-30V, 0-3A)..... | \$224.95 |
| PS-3030D : Digital display..... | \$254.95 |
| PS-6010 : (0-60V, 0-1A)..... | \$209.95 |
| PR-1810H : (0-18V, 0-10A)..... | \$349.95 |
| PR-3060 : (0-30V, 0-6A)..... | \$314.95 |
| PR-6030 : (0-60V, 0-3A)..... | \$314.95 |
| PR-6030D : Digital Display..... | \$399.95 |

Triple Output DC Power Supplies



- * Two variable 0-30VDC, 0-3A outputs
 - * One fixed 5VDC, 3A output
 - * Auto tracking
 - * Auto serial and parallel operation
 - * Constant voltage and constant current mode
 - * Continuous/dynamic load can be selected
 - * Features 4 analog or 2 digital displays
- | | |
|---------------------------------|----------|
| PC-3030 : (0-30V, 0-3Ax2)..... | \$499.95 |
| PC-3030D : Digital display..... | \$549.95 |

Programmable DC Power Supplies



- * High stability, low drift, 4 digit display
 - * Front/rear output-sense switch selectable
 - * Auto step running w/timer settings
 - * 100 point programmability (PPS series)
 - * 50 point programmability (PPT series)
 - * Auto serial and parallel operation (PPT series)
 - * Auto tracking (PPT series), IEEE-488.2 and SCPI compatible command set (optional)
- | | |
|--|-----------|
| PPS-1860G : (0-18V, 0-6A)..... | \$1099.95 |
| PPS-3635G : (0-36V, 0-3.5A)..... | \$1099.95 |
| PPS-6020G : (0-60V, 0-2A)..... | \$1099.95 |
| PPT-1830G : (0-18V, 0-3Ax2, 0-6V, 0-5A)..... | \$1399.95 |
| PPT-3615G : (0-36V, 0-1.5Ax2, 0-6V, 0-3A)..... | \$1399.95 |

Digital Display Function Generator FG-8016G \$239.95



- * Frequency Range: 0.02Hz to 2MHz
 - * Three Instruments in one: Function generator, Pulse generator & Frequency counter
 - * Sine, Triangle, Square, TTL Pulse and CMOS output
 - * Built-in 6 digit counter with INT/EXT function
 - * 1000:1 tuning range
 - * Variable DC offset control
- | | |
|---|----------|
| FG-8015 Function Generator..... | \$189.95 |
| * 0.02Hz-2MHz (No Counter)..... | \$189.95 |
| FC-8131 Intelligent Counter 1.3GHz..... | \$469.95 |
| FC-8270 Intelligent Counter 2.7GHz..... | \$629.95 |
| UC-2010G Universal Counter..... | \$294.95 |

Digital Multimeter & C Meter DM-8034(3½ digits) \$179.95



- * 8 Function, AC/DC voltage, AC/DC current, resistance
 - * Built-in C meter, diode test and audible continuity check
 - * High voltage 1000V and 20A range
 - * 0.5% basic accuracy
- | | |
|---|----------|
| DM-8040 (3½ Digits, True RMS)..... | \$339.95 |
| * Measures ACV to 50 kHz..... | \$339.95 |
| DM-8055 (5½ Digits)..... | \$649.95 |
| * 0.006% basic accuracy..... | \$649.95 |
| * 1µV, 1mΩ, 1nA resolution..... | \$649.95 |
| * dBm measurement..... | \$649.95 |
| * Auto range, relative mode, Max/Min..... | \$649.95 |
| DM-8055G(5½ Digits, GPIB)..... | \$889.95 |


Model DM-392 (3½ digits) \$109.95



- * Auto/Manual ranging(38 ranges)
- * 42 Segment analog bar graph
- * Data Hold/Min-Max memory
- * /Relative mode
- * Auto power off
- * Overload protection
- * Audible continuity check /diode test
- * Capacitance: 1pF-40µF
- * Frequency: 0.1Hz-1MHz
- * 20 Amp range
- * Double high energy fused (1A, 20A)
- * 0.3% DCV accuracy

- | | |
|---|----------|
| DM-351 3½ Digits w/Continuity, Auto Off..... | \$54.95 |
| DM-352 3½ Digits, Cap. Freq. hFE, 20 Amp..... | \$79.95 |
| DM-353 3½ Digits, Cap. Freq. Temp. hFE..... | \$84.95 |
| DM-391 3½ Digits, Auto, Cap. Freq. Min/Max..... | \$99.95 |
| DM-392 3½ Digits, Hold, Min/Max 20Amp..... | \$109.95 |
| DM-393 3½ Digits, Peak, Logic, hFE, Freq..... | \$119.95 |

Construction Tools for Audio & More!

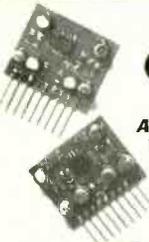

MENTION AD AND TAKE 5% OFF YOUR FIRST ORDER!

BUILD THAT AUDIO PROJECT WITH SESCOM AUDIO SIPS

Hasse-free SIP circuits have 9 pins on 0.1" centers. Approx. 1.1" W x 1.0" H x 0.5" D

Audio SIPs

DESCRIPTION	MODEL	A*	B**
DUAL GEN PURPOSE GAIN AMPS	SIP-1	20.00	20.50
DUAL ELECTRONIC MIC INPUT AMPS	SIP-2	25.00	25.50
DUAL ELECTRONIC LINE INPUT AMPS	SIP-3	25.00	25.50
DUAL ELECTRONIC LINE OUTPUT AMPS	SIP-4	25.00	25.50
LINE AMP WITH BUFFER STAGE	SIP-5	15.00	15.00
DUAL SUMMING AMPS	SIP-6	21.00	21.50
DUAL HEADPHONE AMPS	SIP-7	20.00	20.50
ALC - LINE LEVEL	SIP-8	25.00	25.50
DUAL VCA	SIP-9	20.00	20.50
FOUR COMMON BUFFER AMPS	SIP-10	19.00	19.50
DUAL ELECTRONIC SWITCH	SIP-11	21.00	21.50
VIDEO DA - 3 OUTPUTS	SIP-12	35.00	35.50
DUCKER	SIP-13	20.00	20.50
ELECTRONIC MIC-LINE PAD	SIP-14	22.00	22.50
AUTO FEEDBACK CONTROLLER	SIP-15	30.00	30.50
FUNCTION GENERATOR - SINE-SQUARE WAVE	SIP-16	30.00	30.50
AUDIO OSC / METER DRIVER	SIP-17	22.00	22.50
RUMBLE SCRATCH FILTER	SIP-18	20.00	20.50
MIC PRE-AMP / WATT AMP	SIP-19	18.00	18.50
OC/DC CONVERTER	SIP-20	18.00	18.50
DUAL GAIN AMPS - SINGLE SUPPLY	SIP-21	20.00	20.50
DUAL SUMMING AMPS - SINGLE SUPPLY	SIP-22	20.00	20.50
LIMITER - FAST ATTACK / SLOW RELEASE	SIP-23	20.00	20.50
DUAL UNITY GAIN BUFFERS	SIP-24	20.00	20.50
AC POWER SUPPLY ±18V OUT	SIP-PS	30.00	31.00
AC TO 8VDC REGULATED CIRCUIT	SIP-18V	20.00	20.50

WE ALSO HAVE PC BOARDS TO MAKE CONSTRUCTION WITH SIPS EVEN EASIER!

Audio Transformers


PRIMARY WINDING	USE SECONDARY	POWER RATING	MAGNETIC CORE	CASE STYLE	MODEL	PRICE
150/150 150/150	LO	1	-18	-30	DB	M-75 37.25
18.75/75 150/150	LO	1	+30	-30	DB	M-45 76.50
18.75/75 150/150	LO	1	+30	-30	DB	M-45 76.50
18.75/75 150/150	LO	1	+30	-30	DB	M-45 76.50
150 800	O	1	-24	NONE	S	M-119 23.90
150 800	O	1	-24	NONE	S	M-119 23.90
150/800 150/800	O	1	-18	-10	DB	M-72 57.25
150/800 150/800	O	2	-18	-10	DB	M-73 37.25
150/800 150/800	O	1	+18	-30	DB	M-80 48.75
150/800 150/800	O	2	+18	-30	DB	M-81 78.50
150/800 150/800	O	1	+30	-30	DB	M-80 48.75
150/800 150/800	O	2	+30	-30	DB	M-81 78.50
150/800 150/800	O	2	+30	-30	DB	M-82 134.90
150/800 800	LL	1	-10	NONE	L	M-67 21.40
150/800 800	LL	1	-10	-30	DB	M-65 29.60
150/800 800	LL	1	-10	-30	DB	M-9 39.40
150/800 800	LL	1	-10	-30	DB	M-31 40.50
150/800 900	LL	1	+4	-30	DB	M-88 54.90
150/800 900	LL	1	+4	-30	DB	M-89 37.25
150/800 900	LL	1	+18	-10	DB	M-97 56.50
150/800 900	LO	4	+18	-10	DB	M-74 37.25
150/800 900	LO	4	+18	-10	DB	M-83 78.50
150/800 900	LO	1	+30	-10	DB	M-100 66.75
150/800 900	LO	4	+30	-10	DB	M-82 46.75
150/800 900	LO	4	+30	-10	DB	M-84 134.90
150/800 5k	MI	1	-10	NONE	L	M-111 21.40
150/800 5k	MI	1	-10	-30	DB	M-109 26.90
150/800 5k	MI	1	-10	-30	DB	M-102 39.40
150/800 5k	MI	1	-10	-30	DB	M-108 40.50
150/800 5k	MI	1	+18	-10	DB	M-112 37.25
150/800 5k	MI	1	+18	-10	DB	M-103 78.50
150/800 5k	MI	1	+30	-10	DB	M-113 42.90
150/800 5k	MI	1	+30	-30	DB	M-104 134.90
150/800 15k	LL	1	-10	NONE	L	M-68 21.40
150/800 15k	LL	1	-10	-30	DB	M-5 29.60
150/800 15k	LL	1	-10	-30	DB	M-9 39.40
150/800 15k	LL	1	-10	-30	DB	M-31 40.50
150/800 15k	LL	1	+4	-30	DB	M-89 37.25
150/800 15k	LL	1	+4	-30	DB	M-85 54.90
150/800 15k	LL	1	+18	-10	DB	M-97 56.50
150/800 15k	LL	1	+18	-10	DB	M-99 78.50
150/800 15k	LL	1	+30	-10	DB	M-100 66.75
150/800 15k	LL	1	+30	-10	DB	M-77 48.75
150/800 15k	LL	1	+30	-30	DB	M-115 134.90
800 800	LL	1	+18	-30	DB	M-117 37.70
3.75/15k 15k/15k	LL	1	+18	-10	DB	M-76 57.25
3.75/15k 15k/15k	LL	1	+18	-30	DB	M-23 78.50
3.75/15k 15k/15k	LL	1	+30	-10	DB	M-94 48.75
3.75/15k 15k/15k	LL	1	+30	-30	DB	M-19 134.90
15k 15k	LL	1	+18	-10	DB	M-115 27.70
15k 15k	LL	1	-10	-30	DB	M-58 21.40
15k 15k	LL	1	-10	-30	DB	M-54 29.60
15k 15k	LL	1	-10	-30	DB	M-32 39.40
15k 15k	LL	1	-10	-30	DB	M-33 49.50
15k 15k	LL	1	+30	-10	DB	M-94 37.25
15k 15k	LL	1	+4	-30	DB	M-89 37.25
15k 15k	LL	1	+4	-30	DB	M-85 54.90
15k 15k	LL	1	+18	-10	DB	M-99 56.50
15k 15k	LL	1	+18	-10	DB	M-97 56.50
15k 15k	LL	1	+30	-10	DB	M-100 66.75

MI = MIC INPUT, LL = LINE INPUT, LO = LINE OUTPUT, O = OUTPUT

We also stock over 75 small parts for audio construction! SESCOM has it all; with just one call!

GREAT LITTLE BOXES

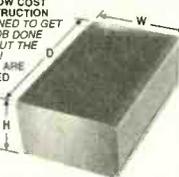FOR LOW COST CONSTRUCTION DESIGNED TO GET THE JOB DONE WITHOUT THE FRILLS! BOXES ARE SHIPPED FLAT



Mini Project Boxes

MODEL	W x D x H in.	A*	B**	OPT**
MPB-1	1 x 2 x 1	2.05	2.35	1.35
MPB-2	1 x 4 x 1	2.55	2.65	1.90
MPB-3	1 x 6 x 1	3.00	3.35	2.45
MPB-4	1.5 x 2 x 1.5	2.15	2.35	1.60
MPB-5	1.5 x 4 x 1.5	2.65	2.95	2.45
MPB-6	1.5 x 6 x 1.5	3.10	3.80	3.30
MPB-7	1.5 x 2 x 3	2.35	2.65	2.05
MPB-8	1.5 x 4 x 3	2.85	3.25	3.30
MPB-9	1.5 x 6 x 3	4.15	4.65	4.55
MPB-10	1.5 x 2 x 5	2.60	3.60	3.30
MPB-11	1.5 x 4 x 5	3.00	3.70	4.40
MPB-12	1.5 x 6 x 5	4.40	5.20	6.25
MPB-13	2 x 2 x 2	2.30	2.70	1.90
MPB-14	2 x 4 x 2	2.75	3.25	3.00
MPB-15	2 x 6 x 2	4.55	5.15	4.15
MPB-16	2 x 8 x 2	6.85	7.60	5.25
MPB-17	3 x 2 x 3	2.55	3.05	2.45
MPB-18	3 x 4 x 3	3.00	3.65	4.15
MPB-19	3 x 6 x 3	4.35	5.05	5.80
MPB-20	3 x 8 x 3	4.80	5.65	7.50
MPB-21	4 x 6 x 3	4.70	5.30	4.45
MPB-22	4 x 10 x 3	5.65	6.10	10.55
MPB-23	4 x 12 x 3	5.90	6.50	12.55
MPB-24	4 x 14 x 3	6.30	7.00	14.50

New Boxes for '96 BOX-IT™ ENCLOSURES

Large Project Boxes

MODEL	W x D x H in.	A*	B**
LPB-1	4 x 6 x 2	10.50	12.50
LPB-2	5 x 7 x 2	11.00	13.00
LPB-3	5 x 9.5 x 2	12.75	15.25
LPB-4	6 x 8 x 2	13.75	16.25
LPB-5	7 x 7 x 2	11.50	13.75
LPB-6	7 x 9 x 2	13.75	16.25
LPB-7	7 x 11 x 2	15.50	18.50
LPB-8	7 x 13 x 2	17.75	21.00
LPB-9	7 x 15 x 2	25.25	30.00
LPB-10	10 x 17 x 2	30.75	36.50
LPB-11	13 x 17 x 2	36.50	43.25
LPB-12	4 x 6 x 3	12.25	14.50
LPB-13	5 x 7 x 3	13.25	15.75
LPB-14	5 x 9.5 x 3	15.25	18.00
LPB-15	7 x 12 x 3	19.50	23.25
LPB-16	7 x 15 x 3	25.50	30.25
LPB-17	8 x 12 x 3	25.00	29.50
LPB-18	8 x 17 x 3	27.50	32.50
LPB-19	10 x 12 x 3	29.75	35.25
LPB-20	10 x 14 x 3	30.00	35.50
LPB-21	10 x 17 x 3	31.50	37.50
LPB-22	12 x 17 x 3	35.75	42.25
LPB-23	14 x 17 x 3	44.00	52.00
LPB-24	17 x 17 x 3	45.00	53.25

WRITE OR FAX FOR CATALOGS

CONSTRUCTOR'S HARDWARE, AUDIO SIPS & AUDIO TRANSFORMERS

Fax Orders Toll Free 800-551-2749 U.S. & Canada (Mexico dial 95 first) 800-551-2749 Australia 1800-12-8491



SES, INC. 2100 WARD DRIVE HENDERSON, NV

ORDER TODAY ALL PRICES INCLUDE WORLDWIDE SHIPPING *A IS USA, CANADA & MEXICO; *B IS REST OF WORLD \$30.00 MINIMUM ORDER



HOURS Monday thru Friday 8 am 'til 4 pm (PST)

ORDERS (800) 634-3457 FAX (800) 551-2749 OFFICE (702) 565-3400 FAX (702) 565-4828 TECH LINE (702) 565-3993 M-Th 8 am to 4 pm (PST) SESCOM, INC. is not responsible for inadvertent typographical errors. Prices and specifications are subject to change without notice.

CIRCLE 269 ON FREE INFORMATION CARD

ARC SALES LTD.

262 OLD NEW BRUNSWICK RD. PISCATAWAY, NJ 08854




We offer an extensive inventory of PREOWNED ELECTRONIC TEST EQUIPMENT

- LIQUIDATION PRICES
- TESTED AND GUARANTEED
- FAX OR CALL FOR LIST

FAX 908-981-1244 PH 908-981-9600 -- 800-220-0044 EXT 154 OR 120 VISA/MC/AMEX

386 SBC \$83

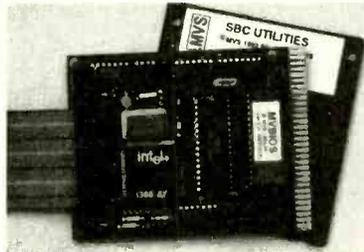

- OEM (1K) PRICE INCLUDES:
- 5 SER (8250 UART)
 - 3 PAR (32 BITS MAX)
 - 32K RAM, EXP 64M
 - STANDARD PC BUS
 - LCD, KBD PORT
 - BATT. BACK RTC
 - IRQ0-15 (8259 X2)
 - 8237 DMA 8253 TMR
 - BUILT-IN LED DISP.
 - UP TO 8 MEG ROM
 - CMOS NVRAM


USE TURBO C, BASIC, MASM RUNS DOS AND WINDOWS EVAL KIT \$295

\$95 SINGLE PIECE PRICE UNIVERSAL PROGRAMMER

- DOES 8 MEG EPROMS
- CMOS, EE, FLASH, NVRAM
- EASIER TO USE THAN MOST
- POWERFUL SCRIPT ABILITY
- MICROCONT. ADAPTERS
- PLCC, MINI-DIP ADAPTERS
- SUPER FAST ALGORITHMS

OTHER PRODUCTS: 8088 SINGLE BOARD COMPUTER OEM \$27 ... *95 PC FLASH/ROM DISKS (128K-16M) 21 75 16 BIT 16 CHAN ADC-DAC CARD 55 195 WATCHDOG (REBOOTS PC ON HANGUP) 27 95

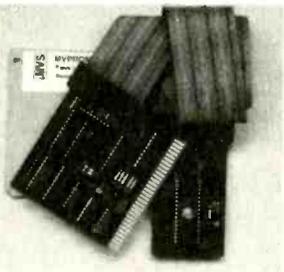*EVAL KITS INCLUDE MANUAL BRACKET AND SOFTWARE. 5 YR LIMITED WARRANTY FREE SHIPPING HRS: MON-FRI 10AM-6PM EST



MVS BOX 850 MERRIMACK, NH (508) 792 9507

Quality Reconditioned Test Equipment



Hewlett-Packard 3325A

Synthesizer/ Function Generator, 1 μ z to 21 MHz, wideband sweeper, programmable, 11 digit resolution.

\$2000.00

Hewlett-Packard 3586B Selective Level Meter

Makes carrier measurements to 32.5 MHz, voice channel measurements from 50 Hz to 100 kHz, can use the 3336B Level Generator as an automatic tracking generator. Opt 004. Like new condition.

\$850.00

Hewlett-Packard 3336B Synthesizer/ Level Generator

Frequency coverage is from 10 Hz to 21 MHz, making the 3336B useful for telephone circuit loop testing on most FDM systems. Includes opt 005. Like new.

\$850.00

Hewlett-Packard 334A

Distortion Analyzer, 5 Hz to 600 kHz range, measures total harmonic distortion down to 0.1 % full-scale. Residual noise below 25 μ V. Voltage measurement over a range 300 μ V to 300 V rms full scale.

\$369.00

Hewlett-Packard 3456A

Digital Voltmeter, 6.5 digit system, measures dc, true RMS ac voltage and resistance. Five full scale dc ranges from 0.1 V to 1000 Ω to 1 G Ω resistance in 8 ranges.

\$800.00

Hewlett-Packard 5334A

Universal Counter, 200 Mhz, built in automatic rise time, duty cycle, pulse width, slew rate and phase measurements. Automatic triggering.

\$1650.00

Hewlett-Packard 8901A

Modulation Analyzer, 150 kHz to 1300 MHz, measures AM and FM to 1% accuracy, measures RF frequency and power, completely automatic, options available.

\$5500.00

Hewlett-Packard 8903A

Audio Analyzer, measures distortion, SINAD, signal-noise, frequency (20 Hz to 150 kHz), ac and dc level, options available.

\$2750.00

Tektronix 475A DM44 Oscilloscope

250 MHz bw, dual channel, 5 mV/ div sensitivity, 1ns/ div sweep rate. With differential-time/ DMM option. Includes 2 probes.

\$975.00

Tektronix 465 Oscilloscope

100 MHz bw, dual trace, 5 mV/div sensitivity, 5 ns/ div sweep rate, 8 x 10 cm CRT, includes 2 probes.

\$590.00

Tektronix 485 Oscilloscope

350 MHz bw, dual trace, 5 mV/ div sensitivity, 1 ns/ div sweep rate, 3.0 div/ ns writing speed, selectable input impedance.

\$1000.00

Hewlett-Packard 8012B

Pulse Generator, 50 MHz, variable transition times down to 5 ns, \pm 10V amplitude; selectable source impedance, ideal for testing TTL.

\$675.00

Tektronix 454 Oscilloscope


DC to 150 MHz, 5 mV/ div sensitivity, dual trace, .05 μ s to 5s/ div timebase plus sweep delay circuit.

Special \$450.00

Tektronix 492 Spectrum Analyzer

50 kHz to 21 GHz, 80 dB dynamic range, amplitude comparison in 0.25 dB steps. Options 01, 02.

\$7500.00

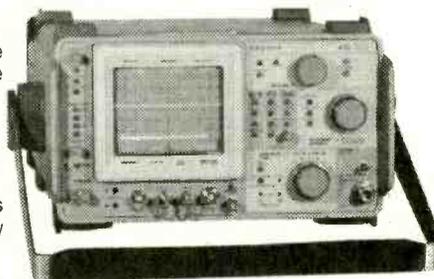

Tektronix 492 Opt 01, 02, 03

\$8250.00

**Wanted Test Equipment
call or fax us your list!**


Fluke 8600

Digital Multimeter, 4.5 digit led, .02% accuracy, 5 functions.

\$159.00

Fluke 1900A

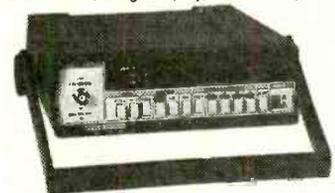Multifunction Counter, 5 Hz to 80 MHz, provides frequency, period, period averaging and totalize measurements, 6 digit display, 1 MHz low-pass filter.



\$189.00 Special

Fluke 720

Kelvin-Varley Voltage Divider, 0.1 ppm resolution, 0.1 ppm of input absolute linearity.

\$2050.00

Fluke 5200A

Programmable ac calibrator, outputs from 100 μ V rms to 120 V rms at 50 mA. Frequency range 10 Hz to 1 MHz, amplitude range is 1 mV to 1000 V.

\$2350.00

Fluke 5215A

Power Amplifier, output voltages to 1100 Vrms, max output of 200 W, frequency from 10 Hz to 100 kHz.

\$2350.00

Hewlett-Packard 8656B

Synthesized Signal Generator, 100 kHz to 990 MHz, 10 Hz resolution, \pm 1.0 dB absolute level accuracy, 150 ms frequency switching speed, HP-IB.

\$5000.00

Hewlett-Packard 8568A

Spectrum Analyzer, 100 Hz to 1.5 GHz, 10 Hz resolution, trace markers w/ amplitude/frequency readout.

\$13900.00

Hewlett-Packard 8569B

10 MHz to 22 GHz, input preselection, 1.7 to 22 GHz, resolution 100 Hz to 3 MHz.

\$9200.00

Please call for our Free 1995 Catalog

14455 NORTH 79TH STREET, UNIT #C • SCOTTSDALE, ARIZONA 85260
(602) 483-6202 • Fax (602) 483-6403

CIRCLE 235 ON FREE INFORMATION CARD

**DANBAR
SALES COMPANY**

VOICE CHANGERS! ELECTRONIC KITS AND MORE!

ELECTRONIC KITS!

WE ACCEPT VISA, MC, MO, COD
SHIPPING & HANDLING EXTRA



BUY WITH CONFIDENCE FROM XANDI

• 30-DAY REFUND POLICY
• TECH SUPPORT NUMBER (602-894-0992)

- Powerful 2 stage audio amplifier.
- Tunes 88-108 MHz.
- Up to 1 mile range.
- Requires 9V battery. (Not incl.)
- Sensitive, picks up sounds at the level of a whisper.



SUPER-MINIATURE FM TRANSMITTER
Super small FM transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip (SMT) parts are pre-assembled to the circuit board.

XST500 E-Z Kit \$44.95

- Sensitive audio amplifier, picks up sounds at the level of a whisper.
- Tunes 88-108 MHz.
- Up to 1/2 mile range.
- Miniature photo battery mounts right on circuit board. (Included)



MICRO-MINIATURE FM TRANSMITTER
Including the battery, this is the Worlds smallest FM transmitter. Use with any FM broadcast receiver. Easy to assemble, uses pre-assembled circuit board.

XWB1000 E-Z KIT \$46.95

- Up to 1/2 mile range.
- Miniature photo battery mounts right on circuit board.
- Transmits at 143 MHz.
- Amazing audio sensitivity, picks up sounds at the level of a whisper.



CRYSTAL CONTROLLED FM TRANSMITTER
Including the battery, this is the Worlds smallest crystal controlled FM transmitter. Transmits to any scanner type receiver. Easy to assemble, uses pre-assembled circuit board.

XTL1000 E-Z KIT \$69.95

- Smallest Phone transmitter anywhere!
- Tunes 88-108 MHz.
- Up to 1/4 mile range.
- Attach to phone line anywhere in house.
- No batterie required, powered by phone line.



SUPER-MINIATURE PHONE TRANSMITTER
Worlds smallest FM phone transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip components are pre-assembled to the circuit board.

XSP250 E-Z Kit \$28.95

- Dial your phone from anywhere and listen to the sounds inside your home.
- Two digit Touch Tone code for secure operation.



TELEPHONE SNOOP
The latest in home or office security. Call home from anywhere, enter a two digit security code, and hear the sounds in your home. Automatically turns on without ringing the phone, vents code, then activates for one and a half minutes.

XPS-CASE KIT \$13.95

XPS1000 C KIT \$55.95

- Transmits a continuous beeping tone.
- Adjustable from 88 to 108 MHz.
- Up to 1 mile range.
- Works with any FM broadcast receiver.



TRACKING TRANSMITTER

Only 0.7 by 2.4 inches, the XTR100 operates at voltages of 3 to 18 Volts and is ideal for use in locating lost model rockets, bicycles, automobiles, games of hide and seek, and contests.

XTR100 C Kit \$29.95

- Covers 1 to 2,000 MHz.
- Compact hand held unit.
- Uses sensitive microwave transistor amplifier.
- Includes miniature loud speaker for audio indication of detected signals.



SUPER SENSITIVE BUG DETECTOR
When the XBD200 intercepts a signal in the 1 to 2,000 MHz range, it emits a growl that increases to a high pitched squeal as the signal strength increases.

XBD200 C Kit \$39.95

- Use with any FM broadcast receiver.
- Hear every sound in an entire house!
- Up to 1 mile range.
- Powerful 2 stage audio amplifier.



MINIATURE FM TRANSMITTER

The XFM100 has a super sensitive microphone and is capable of picking up sounds at the level of a whisper and transmitting them to any FM broadcast receiver.

XFM100 C Kit \$21.95

- Digital voice changing: male to female, female to male, adult to child, child to adult.
- Anonymity on any call.
- Button for normal operation.
- 16 levels of voice masking.



VOICE CHANGING TELEPHONE
STOP THOSE ANNOYING TELEPHONE CALLS!
Sound older and tougher when you want to. Not a kit. Fully assembled. Single phone operation only.

TRANSITION 2000 \$89.95

- Digital voice changing: male to female, female to male, adult to child, child to adult.
- Use with any modular phone.
- 16 levels of voice masking.
- Connects between handset and phone.



VOICE CHANGING ACCESSORY
STOP THOSE ANNOYING TELEPHONE CALLS!
Sound older and tougher when you want to. Not a kit. Fully assembled. Use with single or multi-line phones.

TRANSITION 2001 \$59.95

- Uninterrupted coverage of 800 to 950 MHz.
- Works with any scanner that can receive 400 to 550 MHz.



800-950 MHz SCANNER CONVERTER KIT
If your scanner can receive 400-550 MHz, just add the XLC900 for *uninterrupted* 800-950 MHz coverage. It converts all 800-950 MHz signals down to 400-550 MHz so your scanner can receive them! Add our custom case kit for that "Professional" look.

XLC-CASE KIT \$13.95

XLC900 C KIT \$49.95

- Transmit high quality stereo to any FM stereo receiver.
- Built-in output level monitor for quick and easy tuning.
- Ideal for use with personal CD player.



FM STEREO TRANSMITTER
Transmit full-bodied Hi Fi stereo to any FM stereo receiver. Separate left and right inputs and gain controls. Includes an output booster stage for greater range.

XFS-CASE KIT \$13.95

XFS108 C KIT \$39.95

XANDI Serving the public since 1981
ELECTRONICS, INC.
1270 E Broadway Rd. # 113, Tempe AZ 85282

TOLL FREE ORDER LINE: 1-800-336-7389
FAX LINE: 1-602-731-4748
ASK FOR FREE CATAG OF OUR PRODUCTS

SEND MAIL XANDI ELECTRONICS
ORDERS TO: BOX 25647
TEMPE, AZ 85285-5647

CIRCLE 281 ON FREE INFORMATION CARD

CELLULAR EQUIPMENT

ESN RECC DECODER kit

An affordable alternative. Decodes audio level signal, must be used in conjunction with a scanner. Call or fax for specifications.

.....\$445

TEST MODE Software

Works with a wide variety of phones. Repairs phones, activates certain features, etc.

.....Call

Cellular Masters, Corp.

805-652-0654

567 W. Channel Islands Blvd. #188, Port Hueneme, CA 93041

The GIANT Black Book of Computer Viruses



Enter the secret world of computer viruses with this incredible book! Find out how viruses work, while learning *coding secrets that make your computer software capable of amazing feats*. Explore the PC as well as Windows and OS/2 internals. Learn how to get a super user account on a UNIX system with

a virus. Get the inside scoop on the incredible KOH virus - a beneficial virus that will keep your data encrypted for you. More than just a dry textbook, this book is an *excellent tutorial in assembler* that will hold your interest with a fascinating subject! It includes **full source** and explanations of 37 different viruses and four different anti-virus programs!

ALL NEW
FOR 1996!

672 page Book \$39.95
Program Disk \$15.00

Shipping \$3

Call (800)719-4957 now!

to order (Visa/MC/COD) or call or write for free catalog!
American Eagle Publications, Inc.
P. O. Box 1507
Show Low, AZ 85901

CIRCLE 317 ON FREE INFORMATION CARD

PROFESSIONAL DESOLDERING with the

Lane Norman - Normans Electronics Inc.
Atlanta GA 404-451-5057

A cost effective solution to desoldering equipment at less than half the price of most equipment. Its performance is ASTOUNDING.

Mike Murphy - Service Center - Van Nuys CA 818-785-7805
The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

Bob Monroe - M.A.R.C. Electronics - Virginia Beach VA 804-468-3932
Best investment we've made. Saves time, especially with multi-sided PCB's. Extremely pleased with warranty. Failed within 6 months and replaced by DEN-ON overnight.

Dick Manning - Dicks Electronics - Hartland WI 414-367-8339
The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

Dave Hayes - E-H Engineering Ltd - Lincoln NE 402-466-6720
Has been a durable & reliable desoldering unit. Our use has been both lab & field application over the last 2 yrs. with positive results.

Bob Sorrels CET/CSM Polytronics Microcomputer - Shreveport LA
We've used our SC7000 almost every day for about three years with virtually no problems. Just clean it before you turn it off for the day.

George Hefner - Hefner Electronics - Coleridge NE 402-283-4333
Being a one-man service center, I hesitated to spend the money on a desoldering tool, however all that changed when I nearly ruined a \$400 computer logic board. I use the SC7000 daily. It has cut my desoldering time by 50 to 75%.

Steven Gray - Electronic Wizards - Wichita KS 316-686-8324
By far the best desoldering tool we've ever used. Much more suction than other similar types we've tried. No trouble with postage stamp IC's or anything else.

Dennis McMannis - Thorn Services International - Mabelton GA
The SC7000 has decreased my use of wick by 75% and at \$25 a roll, it pays for itself within months. My total bench time is reduced by approx. 20%.

Don Cressin - Certified Electronics Service - Ellicott City MD 301-461-8008
We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

Doug Pettit - LuRay Electronics - LuRay VA 703-743-5400
We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

Paul Horvat - Service Excellence Inc. - Bergenfield NJ 201-387-7776
It has made a almost impossible job (desoldering a 64 pin CPU) a piece of cake. Glad I found you.



Harold Smedberg - Smedberg Electronics - Custer MI
The SC7000 has reduced my damage to PC boards by 90%. It has also decreased my desoldering time by 50%. The best priced tool on the market.

Tom Mullett - JC Penny TD&S - Wausatose WI 414-259-2486
The SC7000 is a very easy to use, self-contained desoldering tool. We had a 70% increase in production after the purchase of the SC7000. I highly recommend it.

Paul Reindorf CET - Osage TV & Comm. - Santa Fe NM 505-471-8930
This tool has paid for itself over & over again. I don't know how we ever did without it.

Randy Whitehead - Service West - Salt Lake City UT 801-262-4069
My techs thought it would be a waste. I bought one anyway after a demo. My techs then fought over it. Now we have three. It is the Best desoldering tool we have ever used.

Timothy Kraft - Monikraft, Inc. - Cherry Hill NJ 609-751-3252
We replaced all our existing desoldering stations with the SC7000. Our technicians are very pleased with the improved performance, portability, and reliability over our previous higher priced equipment.

Mike Metsikas - RGB Services - Philadelphia PA
I may not need this tool for every job, but when I do, I swear by it. Its perfect for field service because of it's size. An incredible tool, I wouldn't do another house call without it.

Bill Warren CET/CSM - Warrens Audio & Video - Knoxville TN
We have been extremely satisfied with the quality and durability of the DEN-ON SC7000 as well as with after the sale support.

David Dumber - Video Tech Center, Inc. - Belair MD 410-893-8448
The compact design of the SC7000 boast optimum efficiency. I wouldn't trade it's performance for any system at even twice the price.

Keith Sals - J & M Electronics - Omaha NE 402-291-7100 It's a must tool for my bench. I can desolder multiple pin IC's quickly and clean. It will even take up large solder amounts on tuner and case grounds.

Ray Wurmnest - Ray's Electronics, Inc. - Bloomington IL
The SC7000 saves time when changing out parts in the home or in the Service Center — Worth every penny we spent.

DEN-ON SC7000

- ◆ Totally Self Contained diaphragm vacuum pump and AC motor for high vacuum suction or reversible hot air blow for SMD removal.
- ◆ 100Watt Ceramic heater with zero-crossover switching heater control circuit which prevents spikes and leakage currents.
- ◆ Unique patented long lasting filter cartridge design. Solder builds up on easily cleaned baffle, while air flows around the outside of baffle.
- ◆ Totally ESD Safe. The housing contains carbon and the tip is at ground potential for complete ESD Protection.
- ◆ Maximum vacuum of 600mmHg is attained in 0.2 seconds.
- ◆ Temperature adjustable from 300°C - 450°C or 572°F - 842°F

Call Now for SPECIAL PRICING to readers of ELECTRONICS NOW



Visa - M/C - Discover - American Express - Terms to Qualifying Companies
30 Day Money Back Total Satisfaction Guarantee - One Year Parts and Labor Warranty

HOWARD ELECTRONIC INSTRUMENTS INC
6222 N. Oliver Wichita, KS 67220

Toll Free U.S. and Canada

1-800-394-1984

International

(316) 744-1984

or Fax **(316) 744-1994**

CIRCLE 222 ON FREE INFORMATION CARD

CUSTOMER
SATISFACTION
#1 PRIORITY

TEST EQUIPMENT SALES

WE BUY
SURPLUS
EQUIPMENT

TEK 465.....100 MHz 2 CH. SCOPE.....\$475

HP 1650B....80 CH. LOGIC ANALYZER.....\$3495

(W/ BRAND NEW CRT)

DATA I/O 1020L...GANG PROGRAMMER...\$950

HP 1980B.....DIGITIZING OSCOPE.....\$1095

(W/ 4 CH. & DIGITAL STORAGE)

ENI 325LA.....POWER AMPLIFIER.....\$1195

FLUKE 6039A...FREQ. SYNTHESIZER.....\$895

FLUKE 343A.....DC CALIBRATOR.....\$950

GUILDLINE 9577.....7.5 DIGIT DMM.....\$995

HP 16515A.....1 GHz TIMING MODULE.....\$1495

WAVETEK SPG2000..PULSE GENERATOR.....\$1995

(INCLUDES 2 CHANNELS)

VALHALLA 2500..CURRENT CALIBRATOR...\$595

TAS 112...PHONE NETWORK SIMULATOR...\$3495

KEYTEK M801-5.....SURGE NETWORK P/I.....\$3495

NEW TEKTRONIX SCOPES W/ 3 YEAR
MFG. WARRANTY !!

TEK TDS 340.....100 MHz 500MS/s SCOPE
W/ DRT & FFT.....\$2495

TEK TDS 360.....200 MHz 1 GS/s SCOPE
W/ DRT, FFT & DISK DRIVE.....\$3495

TEK TDS 380.....400 MHz 2 GS/s SCOPE
W/ DRT, FFT & DISK DRIVE.....\$4595

TEK TDS 640A.....500 MHz 2 GS/S SCOPE
W/ DRT & 4 CHANNELS.....\$9425



P.O. BOX 986
LONDONDERRY, NH 03053

PHONE (800) 684-4651
FAX (603) 425-2945

ASK ABOUT OUR NEW
TEKTRONIX & FLUKE
PRODUCTS



CABLE TV Universal Descrambler



NEW PRODUCT

MODEL 5000 Fully Assembled \$199.95

Our fully assembled product is tested and *Guaranteed* to work on your system. We will also include an AC adaptor and complete hookup instructions. This unique product will be available for a limited time only!

4000 And 5000 Features

- The latest in Video Amplification Technology.
- New clocking circuits to stabilize color and picture performance.
- The most advanced picture locking circuitry.
- Inverted Video Option is available.
- Connects easily to your VCR.
- NO converter box is necessary.

The Halcyon Group
1-800-664-6999

Anyone implying theft of cable service will be denied assistance.

Model 4000 Kit \$79.95

The 4000 KIT comes with electronic components and Cad designed PC board. We provide schematic, parts list, wiring diagram, tutorial guide, and **FREE** in-house support.

Model 4000A Enc. Pack \$44.95

The 4000A Enclosure Pack provides the hobbyist, a custom enclosure, AC adaptor and finish accessories to give your kit the professional look.



PUT YOUR PC TO WORK

THIS IS THE DREAM MACHINE YOU'VE BEEN WAITING FOR

2.5, 3, & 4 AXIS CNC/DNC DESKTOP MANUFACTURING UNITS

STARTING AT
\$495.00

FREE
CAD/CAM
SOFTWARE

- AUTOMATICALLY PROTOTYPE PC BOARDS & MACHINE 3D PARTS FROM CAD
- CARVE, ROUTE, MILL, & DRILL WOOD, PLASTICS, & LIGHT METALS
- FREE POWERFUL 3D CAD/CAM SOFTWARE WITH EACH UNIT
- INEXPENSIVE CNC KITS AND ASSEMBLED CNC UNITS
- NOW OVER 20 DIFFERENT MODEL-OPTIONS
- EXPEDITE & SUPER-EXPEDITE AVAILABLE



SIZES FROM 12"x 12"
TO HUGE 6'x 6' UNITS


ORDER NOW! 501-839-8293 U.S. CYBERLAB, INC., 14786 SLATE GAP ROAD, WEST FORK, AR 72774

CALL NOW FOR INSTANT SPECS 501-839-8293 24 HR. FAX-BACK SERVICE

New and Pre-Owned Test Equipment

Substantial **SAVINGS** on New & Pre-Owned B+K Precision, Fluke, Hewlett-Packard, Goldstar, Leader, Tektronix, and more ...

Goldstar New Oscilloscope Specials

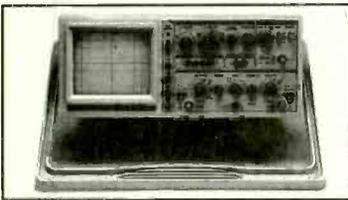

FREE SHIPPING!
ON ALL GOLDSTAR EQUIPMENT
ANYWHERE IN THE U.S.
Excluding AK & HI

Model OS-9100P → **\$999.00**
Full 100 MHz Bandwidth! **SUPER SALE!**

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

Professional Quality Digital Storage Oscilloscopes at Affordable Prices!

Bandwidth	20 MHz	40 MHz	60 MHz
Model	OS-3020	OS-3040	OS-3060
SALE Price	\$1,199.00	\$1,599.00	\$1,899.00

- Transmit and Receive Data with Standard RS-232C Interface
- Includes FREE Comprehensive Communication Software
- Waveform Save, Calculation, and Print
- Dual Channel, Delayed Sweep, TV Synchronization Trigger
- 20 MS/s Sampling Rate, Two Save Memories
- Switch Between Analog and Digital Modes
- CRT Readout Including Measurement Cursors
- Includes Two Probes, 2 Year Warranty

20 MHz Sweep/Function Generator Model 4040 \$499.00 **NEW!**

- 0.2 Hz to 20 MHz, 5 digit LED Display
- AM & FM Internal or External Modulation
- Sine, Square, Triangle, TTL, CMOS Outputs
- Burst Operation

Pre-Owned Oscilloscope Specials

Tektronix 465	100 MHz	\$589.00
Tektronix 465B	100 MHz	\$689.00
Tektronix 475	200 MHz	\$749.00
Tektronix 475A	250 MHz	\$849.00

- Professionally Refurbished
- Calibrated to Original Specifications
- Dual Channel, Calibrated Delayed Sweep
- 90 Day Warranty

LOWEST PRICES EVER!

New Fluke Multimeters

The Industry Standard in Multimeters:

Model 75 Series II ...\$128.00	Model 83 ...\$232.00
Model 77 Series II ...\$153.00	Model 85 ...\$265.00
Model 79 Series II ...\$172.00	Model 87 ...\$285.00



Power Supplies

Model 1680 Fixed 13.8V, 6A	\$50.00
Model 1682 Fixed 13.8V, 15A	\$99.00
Model 1740 0-40V, 6A Dual LED Meters	\$499.00
Model 1760 Tri-Output (2)0-30V, 2A (1)4-5.6V, 5A .	\$649.00

Counters, Generators, Video Test, & More....

Model 1856A 2.4 GHz Multi-Function Counter	\$499.00
Model 1823 175 MHz Universal Counter	\$399.00
Model 1806 100 MHz Multi-Function Counter	\$249.00
Model 1211D Color TV Pattern Generator	\$235.00
Model 1249A NTSC Generator w/RGB	\$569.00
Model 4017 10 MHz Sweep/Function Generator	\$369.00
Model 1653 Isolated AC 1-150V, 2A Supply	\$319.00

Full line of Oscilloscopes, RF, Video & Audio Test Equipment,
Power Supplies, Meters, Probes and Accessories.



TOLL FREE 1-800-99-METER

1-800-996-3837

Availability of Equipment Subject to Prior Sale
Prices Subject to Change Without Notice

FOTRONIC
CORPORATION
P.O. BOX 708
Medford, MA 02155
(617) 665-1400
FAX (617) 665-0780

CIRCLE 219 ON FREE INFORMATION CARD



- PRODUCT ENGINEERING
- FIRMWARE DEVELOPMENT

"QUALITY IS OUR CAPITAL CONCERN."

*Complete On Site
Electrical Engineering Lab*

- REVERSE ENGINEERING
- RF CIRCUIT DESIGN & MANUFACTURING

- MICRO CONTROLLER & EPROM HARDWARE & SOFTWARE DEVELOPMENT

From Auto-Routing to CNC Routing to Electronic Assemblies...
Capital Electronics is Your Best Route For Printed Circuit Boards.

DESIGN/LAYOUT

- CAD LAYOUT SERVICES
- COMPATIBLE WITH ALMOST ALL CAD SYSTEMS
- FROM SCHEMATICS OR SAMPLE PCB'S
- PHOTOPLOTTING SERVICES
- 28,800 BAUDE MODEM

PRINTED CIRCUIT BOARDS

- SINGLE & DOUBLE SIDED
- MULTI-LAYER & FLEXIBLE PCB'S
- FROM QUICK TURN PROTOYPES TO SCHEDULED PRODUCTION RUNS
- FINE LINES, SMT
- ELECTRICAL TESTING
- PRECIOUS METAL PLATING

ASSEMBLY SERVICES

- FAST TURN BOARD STUFFING
- WIRE HARNESSSES
- WAVE SOLDERING
- ACQUISITION OF PARTS
- FINAL TESTING
- TURNKEY SERVICES
- CUSTOM ENCLOSURES

*For Quick & Competitive Pricing or More Information,
Please Call Us Today!*

852 Foster Avenue • Bensenville, IL 60106

(708) 350-9510

Fax (708) 350-9760 • Modem (708) 350-9761

Internet Access:

For Automated Info Response:
INFO@capital-elec.com

E-Mail: Quote@capital-elec.com

Web Access: <http://www.capital-elec.com>

CIRCLE 332 ON FREE INFORMATION CARD

❖ ATTENTION CABLE VIEWERS ❖

CABLE VIEWERS...get back to your BASIC Cable Needs

Call 800-577-8775

For information regarding all of your BASIC cable needs.

5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
- ❖ **ANY SIZE** ORDER FILLED WITH SAME DAY SHIPPING

We handle NEW equipment ONLY - Don't trust last year's OBSOLETE and UNSOLD stock!
COMPETITIVE PRICING—DEALERS WELCOME

HOURS: Monday-Saturday 9-5 C.S.T.

It is not the intent of B.E.S.W. to defraud any pay television operator as we will not assist any company or individual in doing the same.
*Refer to sales personnel for specifications.

**BASIC
ELECTRICAL
SUPPLY &
WAREHOUSING
CORPORATION**

P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775

CIRCLE 334 ON FREE INFORMATION CARD

SEC Sun Equipment Corporation

3121-A Glen Royal Rd., Raleigh, NC 27612

Test Equipment for Cost-Minded People

LODESTAR LodeStar Electronics Corp. Since 1979
 One Year Warranty. 15 Day Money Back Guarantee. OEM welcome.
 School purchase order accepted. Bids accepted. VISA, DISCOVER
 SALES REP./DISTRIBUTORS/OEM WANTED. MASTER, & AMER.
 1-800-870-1955/(919)870-1955 24-hr Fax:(919)870-5720

DC POWER SUPPLY

PS-30J \$159.00
 0-30VDC, 0-3A, 0.02%+2mV line regulation; 0.02%+3mV load regulation; 1mVrms noise & ripple, Short circuit/overload protection; constant current/voltage(CC/CV)
PS-30JD \$314.95 dual output, tracking
PS-30S \$219.95, 0-30VDC, 0-5A

PS-30SD \$399.95, dual, tracking.
8110 \$289.95 0-60VDC, 0-3A
8112 \$399.95 0-60VDC, 0-5A
8108(8109) \$549.95(\$699.95) 0-60VDC, 0-3A(5A), dual, independent tracking. Low ripple.
8102(8103) \$399.95(\$489.95) dual 0-30VDC/0-3A(5A), fixed 5VDC/3A, independent tracking operation, constant voltage and current. Slave/Master, Serial/Parallel connection
PS-1610S(8107) \$289.00(\$399.95) 0-16VDC(0-30VDC), 0-10A
PS-224J(224S) \$139.00(\$159.00) 0-12/0-24VDC, 3A(5A)
8200(8201) \$179.95(\$239.95) 0-30VDC(digital meter), 0-3A(5A) **8210(8211) \$199.95(\$259.95)** two digital meters.
8202(8203) \$499.95(\$549.95) 3 outputs, digital display, dual 0-30VDC/0-3A(5A), a fixed 5VDC/3A, independent tracking operation, constant voltage and current.

AM/FM SWEEMAR SCOPE

SM-6225B/C \$1999.95
 Freq Range: (AM)490KHz, (FM) 10-11.4MHz, Accuracy: ± 0.1%
 Marker: (AM)455KHz, ±5KHz, ±10KHz; (FM)10.7MHz, ±7.5KHz, ±150KHz

STEREO SCOPE OS-7505B \$369.00 trigger, 0-10MHz.

ALIGNMENT SCOPE OS-7001A \$369.00 0-200KHz.

AM/FM STD SIGNAL GEN.

SG-4110A \$1799.00
 Freq: 100KHz-110MHz
 Display: 6-digit LED
 Accuracy: <±(5x10⁻⁵ ± 1 count)
 Resolution: 100Hz (100-34.99MHz), 1KHz (35MHz-110MHz).
 Output: -19dBu, -99dBu, 1dB steps. Impedance: 50Ω VSWR 1.2.

NTSC TV COLOR BAR PAT. GEN.

CPG-1366A \$159.95
 VHF NTSC,
 Freq: 45.75, 175.25, 187.25 MHz.
 RF Output: 10mV
 Impedance: 75 Ohm,
 Video Output: BNC, 1Vp-p

SWR/RF POWER METER

J10 \$89.95
 Freq Range: 1.8-150MHz.
 RF Power: 0-4W/20W/200W
 SWR Measure: 1.0 - ∞, 4W min.
 Accuracy: 5%-10%; SO-239 plugs.
 Insertion Loss: 0.3dB

J20 \$89.95, 130-520MHz
J30 \$119.95, 1.8-520MHz
SWR-3P \$26.95 1.7-150MHz
 RF Power: 0.5-10W, 0.5W-100W
SWR-2P \$22.95, 1.7-30MHz, RF Power: 0.5-10W
mW RF Power Meter J40 \$219.00, 1.8-500MHz, 20mW - 2W.

RF SIGNAL GENERATOR

SG-4160B \$124.95
 100KHz-150MHz up to 450MHz on 3rd harmonics, 6 ranges; AM modulation. RF Output: 100mVrms to 3-5MHz. Modulation: Int 1KHz AM, Ext. 50Hz-20KHz AM.
 Audio Output: 1KHz, 1Vrms.
SG-4162AD \$229.95, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see SG-4160B above.

AUDIO GENERATOR

AG-2601A \$124.95
 10Hz-1MHz, 5 ranges;
 Output Level: sinewave 0-8Vrms, square 10Vp-p
 Output Impedance: 600 Ohm.
 Distortion: <0.05% 500Hz-50KHz, <0.5% 50KHz-500KHz.
AG-2603AD \$229.95, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see AG-2601A above.

FUNCTION GENERATOR

FG-2100A \$169.95
 0.2Hz-2MHz in 7 ranges; Sine, Square, Triangle, Pulse & Ramp
 Output: 5mVp-p-20Vp-p, 1% distortion.
 VCF: 0-10V control freq. to 1000:1

FG-2102AD \$229.95 generates signals same as FG-2100, 4-digit counter display, TTL & CMOS outputs, 30ppm ± 1 count accuracy
FG-2020B \$159.00 0.5Hz-500KHz, Sine, Square, Triangle
(FG)2103 \$329.95, Digital sweep generator, 0.5Hz-5MHz in 7 ranges. Operating Mode: sweep, AM, gated burst, VCG.
 Freq. Counter: Int. 0.5Hz-5MHz; Ext. 5Hz-10MHz

FM STEREO MODULATOR

AG-2011A \$549.00
 RF SECTION:
 Carrier: 98MHz ± 2MHz,
 Output: 10mV, 1mV & 0.1mV
 COMPOSITE SIGNALS:
 Pilot: 19KHz ± 2Hz, 0.8Vrms
 INT. MODULATION: 400KHz,
 1KHz ± 1%, 1Vrms, distortion < 5%; L-R Separation: >50dB.
 EXT. MODULATION; Freq: 50Hz-15KHz
 L-R Separation: >45dB 100Hz-3KHz, >35dB 50Hz-15KHz.

AC MILLIVOLT METER

MV-3100A \$159.95 wide band 5Hz-1MHz, 3 scales, mV, dB & dBm: 300μV-100V in 12 ranges, 10μV resolution, -70-40dB in 12 ranges, 0dB=1Vrms, 0dBm=0.775V; ±3% accuracy; Input impedance 10MΩ; Noise <2%.
MV-3201B \$309.95 dual channels, simultaneous measurement.

OSCILLOSCOPE

OS-7305B \$249.00 DC-7MHz.
 Vertical: 10mV/Div, Horizontal: 250mV/Div, 10Hz-100KHz in 4 ranges; 3" CRT, internal and External Sync; Input 1MΩ/35pF.
OS-7010A \$369.00 DC-10MHz 5" CRT, 10mV/Cm-10V/Cm, 1MΩ
OS-622B \$344.95 20MHz/dual trace
OS-653 \$699.95 50MHz, dual, delay sweep, ALT trigger, TV syn
OS-6100B \$1329.95 100MHz, 4ch, 8 traces, delay sweep, best busy

GRID DIP METER

DM-4061 \$89.95 1.5-250MHz, 6 bands, 6 plug-in coils. Modulation = 2KHz Sinewave. Crystal Oscillator: 1-15MHz. Wave absorption meter. Using 9VDC power supply.

AUTO DISTORTION METER

DM-J104A \$799.95
 MEASUREMENT:
 Range: 0.01%-30%, 0.1/0.3/1/3/10/30% full scale.
 Freq: 400Hz±10%, 1000Hz±10%(HPF).
 Input: 3mV-100V, ratio measuring 20dB.
 Auto. Switching Ranges: Fundamental Freq. = (fo)±10%, Fund. Rejection: >80dB at (fo)±5%; >70dB at (fo)±10%.
 Harmonic Accuracy: ±0.5dB, 1.8(fo)-20KHz.
DM-J204 \$1,599.00 dual channels.

FREQUENCY COUNTER

FC-5250C \$119.95
 Freq Range: 10Hz-220MHz (MHF) 10Hz-20MHz (VHF) 10MHz-200MHz (Gate Time: 0.1 & 1 sec. Max. Input: 10Vp-p).
 Input Sensitivity: 35mV 10Hz-200MHz. Display: 7-digit LEDs.
 Input Imped. (HF) 1MΩ, (VHF) 50Ω.

FC-5260A \$146.00 10Hz-600MHz, 7-digit LEDs.

FC-5270 \$149.95 10Hz-1.2GHz, 8-digit LEDs.

FC-5600B \$321.00 10Hz-600MHz, 10-digit LEDs.

(FC)5700 \$329.95 10Hz - 1.3GHz, 10-digit LEDs.

SIGNAL TRACER/INJECTOR

SE-6100 \$134.95
 TRACER: Gain Max 60dB
 Attenuation: 0/20/40/60dB
 Input Imped.: 100KΩ
 Output Imped.: 600Ω
 Speaker: 8 Ohm.
 INJECTOR: Freq: 1KHz
 >50dB
 Squarewave; Output Level: Continuously variable 0 - 4.5Vp-p.

AUTO. CAPACITANCE METER

CMJ300A \$139.00 10 ranges, 99.9pF - 99.9mF, fully automatic.
 Resolution: 0.1pF lowest, 0.1% full scale.
 Accuracy: 0.5% of full scale; 1 digit to 99.9μF, 1% of full scale; 1 digit to 99.9μF.
 Display: 3 digit LED.
 Unit indicator: pF, nF, μF, mF. Overrange indicator.

WOW-FLUTTER METER

WF-3103A \$699.95
 Freq Range: 3KHz±10%
 JIS/CCIR, 3.15KHz±10% DIN.
 Range: 0.03/1/3/3% full scale.
 Accuracy ±5%.
WF-3105A \$799.95, digital.
 Function: LIN/WOW/Flutter/WT.D.
 Freq Cntr: 10Hz-9.99MHz.
 Indication: CCIR/DIN/JIS.

MICROPROCESSOR/CONTROLLER TRAINING

Now, you can learn and apply Computer control on your PC with our low-cost trainers and lead yourself to the advanced 80386, 80486, etc. Learn ASSEMBLY, C, and BASIC languages programming and debugging, and Microprocessor based system hardware design and troubleshooting. Experiment guide and example programs are included in each trainer. Our trainers are widely adopted by technical colleges.

8088 Trainer \$699.00 80C-8088, teach yourself 8088 assembly language programming.
Features: Assembly language coding, assembler, disassembler, single step and multi-breakpoint program debugger, display and rewrite registers, download/upload programs from/to external systems, I/O drivers, 56-key large size keyboard, LCD display, RS-232, UART, printer interface, two expansion slots, ±5V, ±12V switching power supply, 20 I/O controls available, e.g. servo and stepping motor, dot matrix display, D/A, A/D, sensors, ...
EDS-8811 \$289.00 E(P)ROM programmer. Burn your own EPROM in just a minute.
80C-8052 \$979.00 learn yourself Intel 8051/8052 Embedded Microcontroller controls.
U-D80C \$1599.00 Debugger/In-circuit Emulator for Microprocessors and programme.
8051/52 In-Circuit Emulator, APEX-IE assembly language programming and debugging.
CIC-100 \$549.00 I/O control applications, learn Assembly, C, and BASIC programming languages, 800-pin solderless breadboard for circuit design and test, I/O drivers for controlling relay, step motor, LED, speaker, sensor, etc. Application control modules available.

EDS-8802 \$109.00 Dynamic scanning controls
EDS-8803 \$159.00 A/D, thermal sensor controls
EDS-8804 \$89.00 A/D and D/A converters.
EDS-8805 \$239.00 Servo and stepper motors
EDS-8806 \$159.00 Basic I/O experiments.
EDS-8807N-16 \$619.00 16 Dot matrix LEDs.
EDS-8807N-8 \$419.00 8 Dot matrix LEDs.
EDS-8808 \$269.00 Opto-couple controls.
EDS-8809-1 \$589.00 stepper motor control, digital clock, speaker ctrl, dot matrix LED, matrix keyboard, sign lights, electric piano, stop watch, etc. 24 experiments.


example programs included
EDS-8811-DRAM \$589.00 Disk drive control.
EDS-8811-SRAM \$589.00 Disk drive control.

FREE AC/DC adapter with FC-5250C, FC-5260/5270, CPG-1366A, or SE-6100A purchase before 1/31/96, limited quantity.

NEW PRODUCTS

mW RF Power Meter J40 \$219.00
 1.8-500MHz, RF power: 20mW/200mW/2W; Imp: 50Ω; Accuracy ±10% full scale; N-type connector; SWR <1.15

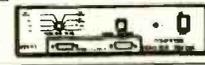
Computer Monitor Tester MT801
 \$175.00 Test MDA, CGA, EGA, VGA, SVGA, 8514A monitors; Video Patterns: color bars, cross hatch, dots, color raster and windows; Two video connectors: digital TTL 9-D & analog 15-HD; Power: 120VAC.
MT810 \$149. Same as MT801, except Power: 9VDC.



CALL TOLL FREE
(800) 292-7711
Se Habla Español

C&S SALES
EXCELLENCE IN SERVICE

WRITE FOR A
FREE 60 PAGE
CATALOG!

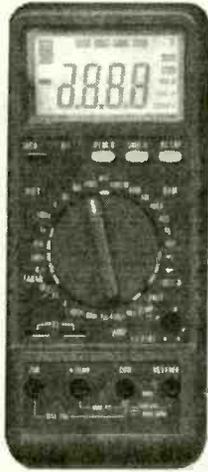

M-6000

Features:

- Computer Interface and Software with RS-232 Output
- Frequency to 4MHz
- Capacitance to 40nF
- Large 3 3/4 LCD display
- Temperature to 1999°F
- TTL logic
- Data/Peak hold
- Audible continuity
- Auto power off
- Unit indicator
- Diode Test

\$99.95

NEW!

TK-3000

\$89.95

Tools Included:

- SR-2 - Deluxe Soldering Iron
- SH-1 - Soldering Iron Stand
- ST-1 - Diagonal Pliers
- ST-2 - Long Nose Pliers
- ST-30 - Deluxe Wire Stripper
- SE-1 - Solder Ease Kit
- ND-3 - 3 pc. Nut Driver Set
- TL-8 - Precision Screw Drivers
- ST-5 - Screw Driver Slotted 3/16"
- ST-8 - Screw Driver #1 Phillips
- ET-10 - IC Puller
- SP-2 - Solder Pump
- ST-20 - Safety Goggles
- ST-9 - Pocket Screw Driver
- ST-4 - Solder Tube
- SW-3 - Solder Wick




NEW!

A professional technician service tool kit in a metal reinforced tool case with heavy-duty handle and locks. A removable pallet handles most of the tools listed with more room for tools and parts in the lower half.

2MHz Function Generator
Model 4010

- Sine, Square, Triangle, Pulse and Ramp output
- Variable duty cycle

\$195.95

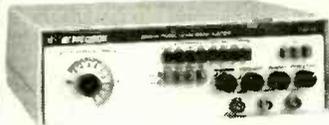

MX-9300 Four Functions in One

- One instrument with four test and measuring systems:
 1.3GHz Frequency Counter • 2MHz Sweep Function Generator
 Digital Multimeter • Digital Triple Power Supply
 (0-30V @ 3A, 15V @ 1A, 5V @ 2A)

\$479.95



NEW

Model XP-581

4 Fully Regulated DC Power Supplies in One Unit
 4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A
 1 Variable - 2.5 - 20V @ 2A

\$85



Digital Multimeter
Model EDM-83B

\$169

18 Functions including freq to 20MHz, cap to 40µF, inductance to 40H, True RMS, Data Hold/min./max./avg., TTL logic.

Digital Multimeter
Model M-1700

\$42.95

11 functions including freq to 20MHz, cap to 20µF. Meets UL-1244 safety specs.



Fluke Multimeters

70 Series

- Model 7011 ... \$69.95
- Model 7311 ... \$97.50
- Model 7511 ... \$135.00
- Model 7711 ... \$154.95
- Model 7911 ... \$175.00

80 Series

- Model 83 ... \$235
- Model 85 ... \$269
- Model 87 ... \$289

B&K Precision Multimeters

- Model 391 ... \$149
- Model 390 ... \$139
- Model 389 ... \$109
- Model 388A ... \$99
- Model 2707 ... \$79
- Model 2860A ... \$85


Kit Corner

over 100 kits available

PT-223K

\$15.95

Phone kit with training course.

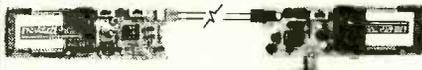

Fiber Optics Technology
with training course

Model FO-30K
\$19.95

Model AM/FM-108K
Transistor Radio Kit

\$29.95



M-1005K
Compact Multimeter Kit

\$19.95

6 Functions & Transistor Test



XK-550 Digital / Analog Trainer


Elenco's advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square wave forms. 1560 tie point breadboard area.

XK-550
Assembled and Tested

\$169.95

XK-550K - Kit
\$139.95

Tools and meter shown optional

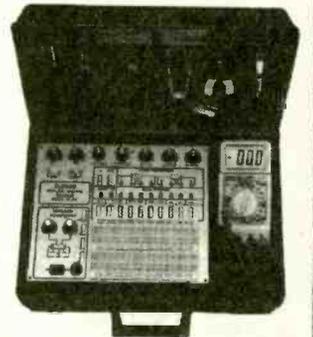

WE WILL NOT BE UNDERSOLD

C&S SALES, INC.

UPS SHIPPING: 48 STATES 5%
 OTHERS CALL (\$5 min. / \$15 max.)
 IL RES. 8% TAX

150 W. CARPENTER AVENUE
 WHEELING, IL 60090
 FAX: (847) 520-9904 (847) 541-0710

15 DAY MONEY BACK
GUARANTEE
FULL FACTORY WARRANTY
 PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 218 ON FREE INFORMATION CARD

**FREE PROBES
WITH ALL
SCOPES**

OSCILLOSCOPES

Lowest Prices of the Year!

**WRITE FOR A
FREE 60 PAGE
CATALOG!**

**Japan Quality
But not Japan Prices!
Hitachi
Laptop Color
Digital Scopes**

NEW! **NEW!**



150MHz 60MS/s VC-5460 \$3695
50MHz 30MS/s VC-5430 \$2695
20MHz 15MS/s VC-5410 \$1795

100MHz
VC-6145 - Storage
4 Channel 100MS/s ... **\$4795**
VC-6155 - Storage 100MS/s \$3995
VC-6545 - Storage 40MS/s \$2995
V-1585 - 4 Channel \$2095
V-1565 w/ Cursors \$1795
V-1560 \$1595

50/60MHz
VC-6525 - Storage 20MS/s \$2795
VC-6524 - Storage 20MS/s \$2295
V-695 - 60MHz w/ Cursors \$1549
V-555 - w/ Cursors \$1095
V-552 \$949
V-509 - Battery Operated . \$1795

20MHz
VC-5025A - 20MS/s
DSO w/ DMM **\$1160**
VC-5025 - 20MS/s
DSO w/ DMM **\$935**
VC-6523 - Storage 20MS/s \$1995
V-252 \$449
V-209 - Battery Operated . \$1425

Quality Scopes by Elenco



60MHz
DS-603 **\$1350**

- Analog / Digital Storage
- 20MS/s Sampling Rate

S-1365 \$795

- Analog w/ Cursors

S-1360 \$759

- Analog with Delayed Sweep

40MHz
S-1345 **\$569**

- Analog with Delayed Sweep

S-1340 \$489

- Analog

25/30MHz
DS-303 **\$1095**

- Analog / Digital Storage

S-1330 \$439

- 25MHz Analog
- Delayed Sweep

S-1325 \$335

- 25MHz Analog


**2 Year
Warranty**

OSCILLOSCOPE SELECTION CHART

ANALOG		Sensitivity (max)	No. of Channels	Sweep Rate Max ns/div	Delayed Sweep	Video Sync	Component Tester	Beam Find	Time Base	
Model	Bandwidth MHz									
S-1365	60	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2	
S-1360	60	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2	
S-1345	40	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2	
S-1340	40	1mV/div	2	10ns/div	No	Yes	No	No	1	
S-1330	25	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2	
S-1325	25	1mV/div	2	10ns/div	No	Yes	No	No	1	
DIGITAL STORAGE		Analog Sen (max)	No. of Channels	Sampling Rate	Memory Channel	Internally Backed Up	Pretrigger %	Output		
Model	Bandwidth MHz								2K	2K
DS-303	30	1mV/div	2	20MS/S	2K	Yes	0, 25, 50, 75	RS232		
DS-603	60	1mV/div	2	20MS/S	2K	Yes	0, 25, 50, 75	RS232		

B&K Precision at Discount Prices

20MHz Analog
2120 - **\$389.95**
2125 - **\$539.95**
Delayed Sweep

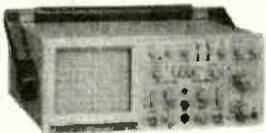

Model 1541C
40MHz
\$695
Dual Trace

Model 2160
60MHz Dual Trace
\$949
Dual Time Base • Delayed Sweep

**60MHz with
Cursors readouts
and Dual Time Base**
Model 2260
\$1225

Model 2190A
100MHz 3 Channel
\$1379
Dual Time Base • Delayed Sweep

Fluke Scopemeters



91 \$1225
92 \$1525
96 \$1795
97 \$1795
97A \$2945
99 \$2095
Call or write for
complete specs.

WE WILL NOT BE UNDERSOLD

C&S SALES, INC.

UPS SHIPPING: 48 STATES 5%
OTHERS CALL (\$5 min. / \$15 max.)
IL RES. 8% TAX

150 W. CARPENTER AVENUE
WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

CIRCLE 218 ON FREE INFORMATION CARD

**15 DAY MONEY BACK
GUARANTEE**

FULL FACTORY WARRANTY
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

USE ELECTRONICS NOW CLASSIFIEDS

READ BY ELECTRONIC BUYERS AND SELLERS AND TRADERS

INSTRUCTIONS FOR PLACING YOUR AD!

HOW TO WRITE YOUR AD

TYPE or PRINT your classified ad copy **CLEARLY** (not in all capitals) using the form below. If you wish to place more than one ad, use a separate sheet for each additional one (a photo copy of this form will work as well). Place a category number in the space at the top of the order form (special categories are available). If you do not specify a category, we will place your ad under miscellaneous or whatever section we deem most appropriate.

We cannot bill for classified ads. **PAYMENT IN FULL MUST ACCOMPANY YOUR ORDER.** We do permit repeat ads or multiple ads in the same issue, but in all cases, full payment must accompany your order.

WHAT WE DO

The first word and company name of each ad are set in bold caps at no extra charge. No special positioning, centering, dots, extra space, etc. can be accommodated.

RATES

Our classified ad rate is \$2.50 per word. Minimum charge is \$37.50 per ad per insertion (15 words). Any words that you want set in bold are each .40 extra. Indicate bold words by underlining. Words normally written in all caps and accepted abbreviations are not charged anything additional. State abbreviations must be post office 2-letter abbreviations. A phone number is one word.

If you use a **Box number** you must include your permanent address and phone number for our files. **ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**

For firms or individuals offering Commercial products or Services. **Minimum 15 Words.** 5% discount for same ad in 6 issues within one year; 10% discount for same ad in 12 issues. **Boldface (not available as all caps),** add .40 per word additional. **Entire ad in boldface,** add 20%. **Tint screen behind entire ad,** add 25%. **Tint screen plus all boldface ad,** add 45%. **Expanded type ad,** add \$4.00 per word.

General Information: A copy of your ad must be in our hands by the 13th of the fourth month preceding the date of issue (i.e. Sept issue copy must be received by May 13th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding work day. Send for the classified brochure.

DEADLINES

Ads not received by our closing date will run in the next issue. For example, ads received by November 13 will appear in the March issue that is on sale January 17. **ELECTRONICS NOW** is published monthly. No cancellations permitted after the closing date. No copy changes can be made after we have typeset your ad. **NO REFUNDS,** advertising credit only. No phone orders.

CONTENT

All classified advertising in **ELECTRONICS NOW** is limited to electronics items only. All ads are subject to the publishers' approval. **WE RESERVE THE RIGHT TO REJECT OR EDIT ALL ADS.**

AD RATES: \$2.50 per word. Minimum \$37.50

Send you ad payments to:

ELECTRONICS NOW 500 Bi-County Blvd, Farmingdale, NY 11735-3931

CATEGORIES

100 -- Antique Electronics	270 -- Computer Equipment Wanted	450 -- Ham Gear Wanted	630 -- Repairs-Services
130 -- Audio-Video Lasers	300 -- Computer Hardware	480 -- Miscellaneous Electronics For Sale	660 -- Satellite Equipment
160 -- Business Opportunities	330 -- Computer Software	510 -- Miscellaneous Electronics Wanted	690 -- Security
190 -- Cable TV	360 -- Education	540 -- Music & Accessories	710 -- Telephone
210 -- CB-Scanners	390 -- FAX	570 -- Plans-Kits-Schematics	720 -- Test Equipment
240 -- Components	420 -- Ham Gear For Sale	600 -- Publications	730 -- Wanted

CLASSIFIED AD COPY ORDER FORM

Place this ad in Category # _____

Special Category \$30.00 Additional _____

1 - \$37.50 2 - \$37.50 3 - \$37.50 4 - \$37.50

29 - \$72.50 30 - \$75.00 31 - \$77.50 32 - \$80.00

5 - \$37.50 6 - \$37.50 7 - \$37.50 8 - \$37.50

33 - \$82.50 34 - \$85.00 35 - \$87.50 36 - \$90.00

9 - \$37.50 10 - \$37.50 11 - \$37.50 12 - \$37.50

37 - \$92.50 38 - \$95.00 39 - \$97.50 40 - \$100.00

13 - \$37.50 14 - \$37.50 15 - \$37.50 16 - \$40.00

Total words _____ \$2.50 per word = \$ _____

17 - \$42.50 18 - \$45.00 19 - \$47.50 20 - \$50.00

Bold Face _____ \$0.40 per word = \$ _____

21 - \$52.50 22 - \$55.00 23 - \$57.50 24 - \$60.00

Special Heading _____ \$30.00 = \$ _____

25 - \$62.50 26 - \$65.00 27 - \$67.50 28 - \$70.00

Other _____ = \$ _____

Total classified ad payment \$ _____ enclosed

TOTAL COST OF AD \$ _____

Check Mastercard Visa

Card # _____ Expiration Date ____/____


Signature _____

Name _____ Phone _____

Address _____ City State Zip _____

RAINBOW KITS

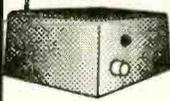Many of our kits are available completely built



FM STEREO TRANSMITTER

Own your own FM radio station. Any stereo signal you plug into the FMST-100 will be transmitted to any FM radio tuneable from 76 to 108MHz FM. Transmit a wireless link through an auditorium, from your car to your camper, listen to your CD's while mowing the lawn, Play music on one channel sing on the other. Clarity is excellent, approx. 40dB stereo separation. Length of antenna determines the distance of transmission. Complete with stereo input level controls & crystal for stereo separation. 9v battery operation. SIZE: 1.5" x 2.5" x 3"

FMST-100 Cabinet \$8.95 KIT \$29.95



PHONE TRANSMITTER

Small but mighty, it fits anywhere. Phone line powered, never needs batteries. Transmits both sides of a phone conversation loud and clear, wireless, to any FM radio at great distances. Variable tunes from 70MHz to 130MHz FM. You can also use it as a speaker phone. SIZE: 1.25" x .6"


TEL-B1 BUILT \$29.95 KIT \$12.95



SUPER SNOOPER BIG EAR

Listen through walls, hear conversations across the room. Add a parabolic reflector and hear blocks away. The BIG EAR can be hidden about anywhere. Makes an ultra sensitive intercom. Can be used as a 1.5W AMP. We supply a mini-electret mike in the kit. Power requirement 6 to 12v DC. SIZE: 1.75" x 1"

AA-1 BUILT \$29.95 KIT \$10.95

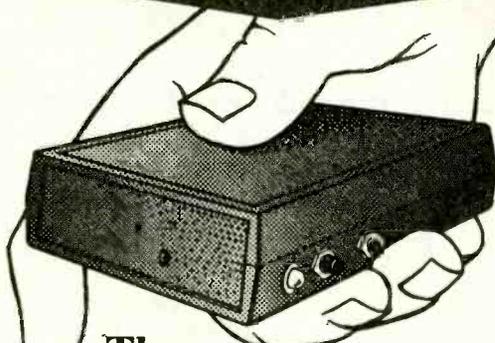


The "ZAPPER II"

With it's new and improved design it will not only test your radar detector...BUT it's tuned to the amateur radio band.

- While your out on American highways personally test yours and your fellow travelers radar detectors.

The "ZAPPER II" is a 10.450 GHz to 10.550 Transmitter

KIT \$39⁹⁵ BUILT \$49⁹⁵

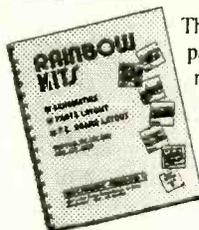

This Manual contains schematics, parts lists & P.C. board layouts for many of the Rainbow Kits. Use your own parts to construct our kits.


KIT BOOK \$14.95
\$9.95 with the purchase of any kit.



WIRELESS FM MICROPHONE

Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal. The WM-2 kit is a buffered wireless mike that operates from 80MHz to 120MHz

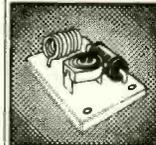
FM, the frequency of any broadcast FM radio. Includes a mini-electret mike. 6 to 12v DC. SIZE: 1.25" x 1"
WM-2 KIT \$14.95



MICRO-MINIATURE PHONE TRANSMITTER

We haven't seen a smaller phone transmitter than the MMPT2 kit. Powered by the phone, it requires no battery. Transmits both sides of a phone conversation to an FM radio up to a 1/4 mile away. Tunable from 88 to 108MHz FM. Attach it to one phone or add it to the line to pick up all incoming calls. The MMPT2 is undetectable if properly installed. Unit has surface mounted parts, you install the leaded parts. Size .45" x .6"

MMPT2 KIT \$29.95

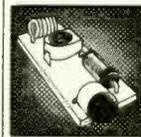

MICRO-MINIATURE WIRELESS MIKE

So small you could hide this one on some real bugs! It's the smallest we've ever seen. With it's super sensitive mike it transmits a whisper or a room of conversation to an FM radio, tunable from 88 to 108MHz FM. With a proper antenna it transmits about 1/2 mile. The kit is made with surface mounted parts, we have already mounted these parts. You install the leaded parts. Power requirement 6 to 12v DC. Size .35" x .9"


MMWMS KIT \$34.95



STROBE LIGHT

Do you need an attention getter, warning light, or flashing light for model airplanes? Then this kit is for you. Use it as an emergency light for your auto, radio tower, even use it on your bicycle. Has a variable flash rate.

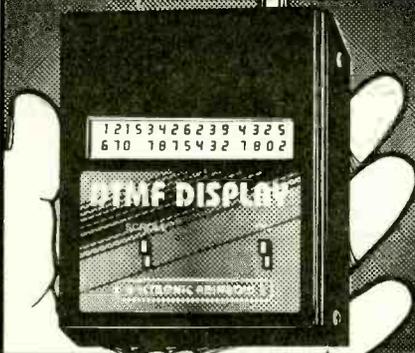Power requirement 6 or 12v DC. Size 3.5"x1.9"
ST-1 KIT \$11.95




Press a button and learn every number dialed on your phone

Okay. Caller ID's tell you what number is calling you. But what about the calls made from your phone? Now, return from work or vacation and know the answer. The new DTMF Recorder electronically logs and saves every number dialed. This is the same high-tech magic used by detectives and government spies. Now yours. Does your wife or husband make expensive long distance calls and then deny it? Does your son or daughter call that low-life you forbade them to talk to? Now know.

- Decodes digits 0 thru 9, #, *, A, B, C, on a 2 line 16 character LCD display.
- Clicks into your phone or extension in seconds, with no special wiring or hassles, or jack it to the incoming service panel in your garage.
- Records all numbers dialed, including local numbers that don't appear on your bill.
- Records credit card numbers entered through your phone key-pad.
- Records Voice mailbox, answering machines, and modem access numbers.
- Records Cellular or repeater phone numbers heard over your phone. Even hook to a scanner, and learn scores of emergency phone numbers. Also decodes tones stored on a tape recorder. Never before has such sophisticated gear been available to the public. And not at this price.

Power requirement 9v DC. SIZE: 3.5" x 4" x 1" BLACK ANODIZED ALUMINUM CABINET
DIS-1 KIT \$119⁹⁵ BUILT \$159⁹⁵

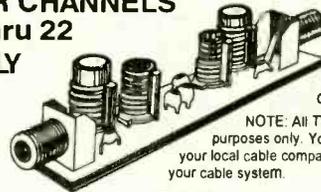TV NOTCH FILTERS FOR CHANNELS 2 thru 22 ONLY



DF-222

Our TV filters eliminate unwanted TV channels or interference that alters both sound and video with a beep beep. Works on cable channels 2 thru 22) only.

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

KIT \$14.95

Please add sufficient postage First lb \$5.00 Canada \$7.00
Additional LB. Add \$1.00 US FUNDS ONLY
We will accept telephone orders for Visa or Mastercard



To Order Call
317-291-7262



ELECTRONIC RAINBOW INC

6227 Coffman Rd. • Indianapolis, IN 46268
FAX 317-291-7269

DANGER LASERS DANGER

LASERS

2-3 mW Helium-Neon Laser
Includes 115VAC power supply manufactured by Laser Drive. These are pulls from equipment. Six month warranty. FREE "101 Uses for a He-Ne Laser." pamphlet. Cat. #: HE2 \$69.00 each!



New Brighter Laser Pointer
You will be amazed at the difference in the brightness of this laser pointer compared to any of the common laser pointers on the market. The lower wavelength (650nm) of this pointer makes it appear 3 times as bright as standard 670nm laser pointers. Features: 5mW laser, velvet "snappy" case, and batteries. One year warranty. Cat. #: LP50 \$65.00



Midwest Laser Products **FREE CATALOG**
P.O. Box 2187 Bridgeview, IL 60455
Phone: (708) 460-9595 FAX: (708) 430-9280
Call, write, or poll fax.
Please include \$7 S&H within US. IL res. add 7.75% sales tax. 30 day satisfaction guarantee.

HOME AUTOMATION

Largest Selection of HOME AUTOMATION products in the World!

Browse us on the WEB!
<http://www.techmall.com/smarthome>

Hundreds of hard-to-find automation, X10, and wireless control products. Computer control of your home, security systems, surveillance cameras, infra red audio/video control, HVAC, pet care automation, wiring supplies, and much more!

HOME AUTOMATION SYSTEMS, INC.
151 Kalmus Drive, Ste L4, Costa Mesa, CA 92626
Questions 714-708-0610 FAX 714-708-0614

800-SMART-HOME Call 24hrs for FREE 64 page Color Catalog **Over 500 unique products!**

800-762-7846



CABLE TV

ALL NAME BRANDS
DESCRAMBLERS, CONVERTERS
COMBOS. CALL NOW
WE'LL BEAT THE COMPETITION.
UNIVERSAL SALES 800-647-2371

The Electronic Experimenter's Journal

It's part catalog, part magazine and part data book with kits, parts, plans, articles, and application notes.
Call for your **FREE** copy today



Debco Electronics
4025 Edwards Rd.
Cincinnati, OH 45209 **1 800 423-4499**

Prototype it..... FAST!

with ProtoQuick 8051 or 28

- Converts single board computers
- Up to 32K EPROM and 8K RAM
- 12 so on (shared through probe area)
- RS232 C serial port w/ 0025 cable
- Chip sys. in EPROM w/ source code
- Assembled, ready to run - 5v only
- AIS 2005 cross assembler included!


\$99.00 each

Run prototype applications of experimental hardware from the serial port - WITHOUT PROGRAMMING!

Software Science
Schwartz Science
3750 Roubidoux Road
Channahon, OH 43134 USA
(513) 561-2060

Motron 310 Garfield St Suite 4 *New Low Price!*
PO Box 2748 **\$59.00**
Eugene, Oregon 97402

The TDD-8X features a large 8-digit LED display and decodes all 16 DTMF digits. The 104 character memory is viewed, without loss of data, by scrolling either left or right. Although a computer is not required, the serial ASCII output allows automatic logging of decoded number groups. ToneLog™, our IBM/Compatible logging software is included. Available accessories include a Plastic Mounting Kit (\$15), Audio/Computer Cables (\$20) and a 12VDC AC Power Adapter (\$10). Visa, MasterCard, American Express, Discover and Government Purchase Orders accepted. Minimum Government Purchase Order: \$99. COD \$5. (Cash or Money Order only); S/H: \$6 USA; \$10 Canada; \$15 Foreign
Info: (541) 687-2118 **Orders: (800) 338-9058** Fax: (541) 687-2492
Or contact motron.info@emerald.com for a catalog via the Internet

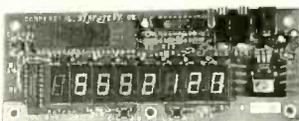

Satellite TV 'BIBLE'

4th 'DIGITAL' edition

The acclaimed 'bible' of satellite TV
- ALL the TECHNICAL DETAILS -

- Operation, installation & troubleshooting of analog and digital satellite systems
- The transition from analog to digital TVRO

1-800-483-2423
TO ORDER
or for a FREE books/software/video CATALOG



HOME SATELLITE TV
INSTALLATION
AND TROUBLESHOOTING
MANUAL
4th Edition

324 pages
8-1/2" x 11"
\$30 plus \$4 s/h

Baylan Publications
1905 Mariposa, Boulder, Colorado 80302, USA
Telephone: 303-449-4551 FAX: 303-939-8720

Radiotelephone - Radiotelegraph

FCC Commercial License

Why Take Chances?

Discover how easy it is to pass the exams. Study with the most current materials available. Our **Homestudy Guides, Audio, Video or PC "Q&A" disks** make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine, Radar, Microwave, New Rules & Regs, Digital Circuitry & more. We feature the Popular "Complete Electronic Career Guide". 1000's of satisfied customers **Guarantee** to pass or money back. Newest Q&A pools.

Send for **FREE DETAILS** or call
1-800-800-7588

WPT Publications
4701 N.E. 47th St.
Vancouver, WA 98661

Name _____
Address _____
City _____ St. _____ Zip _____

1-800-800-7588

May 1996, Electronics Now

FACTCARDS



Jampacked with information at your fingertips

■ ALL YOU NEED to know about electronics from transistor packaging to substitution and replacement guides. FACTCARDS numbers 34 through 66 are now available. These beautifully-printed cards measure a full three-by-five inches and are printed in two colors. They cover a wide range of subjects from Triac circuit/replacement guides to flip-flops, Schmitt triggers, Thyristor circuits, Opto-Isolator/Coupler selection and replacement. All are clearly explained with typical circuit applications.

■ WANT TO EXPAND your knowledge of electronics? Do it the easy way

by studying the Electronics Fact Cards. Do you travel to and from your job each day? Drop a handful of cards in your pocket before you leave, and the bus becomes a schoolroom! At home, you can build some of the projects and not only have fun building and using them, but learn how they work at the same time.

■ YOU'LL BE AMAZED both at how rapidly you learn with these cards, and how easy it is to understand. These new cards are available right now. Don't miss out. Send your check or money order today.

FACTCARDS—Facts at your fingertips for Experimenters and Project Builders!

Please send one copy of FACTCARDS at \$3.50. Shipping \$1.00 (U.S. and Canada only).

Please send _____ copies of FACTCARDS. Total cost is sum of copy price and First Class postage and handling cost multiplied by number of card sets ordered.

New York residents add sales tax to total cost of each order.

Please print

Allow 6-8 weeks for the material to arrive.

(Name) _____

(Street Address) _____

(City) _____

(State) _____

(Zip) _____

Detach and mail today:
CLAGGK Inc.
P.O. Box 4099
Farmingdale, NY 11735

All Payment must be in U.S. Funds!

BS168

PCBoards

PCB Artwork Made Easy!

PRINTED CIRCUIT DESIGN SOFTWARE

for

Layout-Autorouting-Schematic

- Supports all Video Modes including Super VGA
- Copper Flooding for Building Ground Areas
- Gerber and Excellon Output
- Create Negative & Positive Printouts
- Autoroute Single & Double Sided Boards
- Mirror Image Output for Laser & DeskJet tm
- NEW DOS Pricing (Ask for New Price List)
- AutoCADtm - DXF output
- Parts Library-Silk Layer-Includes All Output Drivers
- Great for All Circuit Design Projects!

Download Demos from BBS (205)933-2954

PCBoards Layout Only \$99

Windowstm Layout starts at \$149

Call or Write for Full Product Line, Prices & Demo Packages


PCBoards

2110 14th Ave. South
Birmingham, AL 35205

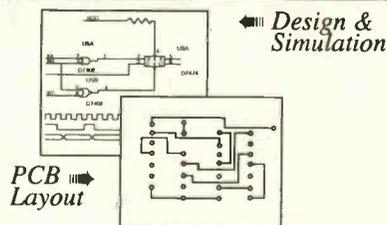(800)473-7227

Fax (205)933-2954
Phone (205)933-1122

Low Cost CAD Software for the IBM PC and Compatibles Now In WindowsTM 95



- Easy to use schematic entry program (SuperCAD) for circuit diagrams, only \$149. Includes netlisting, bill of materials, extensive parts libraries.
- Powerful, event-driven digital simulator (SuperSIM) allows you to check logic circuitry quickly before actually wiring it up. Works directly within the SuperCAD editor from a pull-down menu and displays results in "logic analyzer" display window. Starting at \$149 this is the lowest cost simulator on the market. Library parts include TTL, and CMOS devices.
- Analog simulator (SuperSPICE) for \$149. Allows AC, DC and transient circuit analysis. Includes models of transistors, discretes, and op amps.
- Circuit board artwork editor and autorouter programs (SuperPCB), starting at \$149. Produce high quality artwork directly on dot matrix or laser printers. You can do boards up to 16 layers including surface mount. Includes Gerber and Excellon file output. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- Low cost combination packages with schematics and PCB design: 2-layer for \$399, 16-layer for \$649.

Write or call for free demo disks:

MENTAL AUTOMATION, INC.
5415 - 136th Place S.E.
Bellevue, WA 98006
(206) 641-2141
BBS (206) 641-2846



VIDEO CAMERA TRIPOD

SOLIOEX VT-84HQ TRIPOD designed for video or photo cameras. 3-section metal legs with center brace have quick-release tabs. Extends from 24" to 58" height. Has tilt-head with swivel plus bubble level and "quick-release" platform for easy camera mount-dismount. 5 lbs sh. **NEW** \$29.95


LOG-PERIODIC ARRAY

DORNE & MARGOLIN ARRAY for 30-76 MHz with 3:1 VSWR; rated 65 watts CW. 50 ohm input; BNC connections. Mounts to 2.5" dia pipe. P/o AS-2236/ GRC. Packed size: 10"x42"x10"; unfolds to 10 foot square. 20 lbs sh.



#DM-199-38-7634, **NEW** \$59.50

FM STEREO ANTENNA

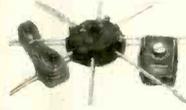

Rembrandt Model 5000, omni-directional 8-element antenna is electronically rotated with remote control unit. 20"L elements; 47" dia assembled. Fits 1.25" dia mast. Includes 50 ft. 4-cond wire & control; 7 lbs. sh.

NEW \$25.00

SOUND-POWERED FIELD PHONE

TA-1 TELEPHONE requires 2-conductor wire connected to another TA-1 for voice communications without batteries. Palm-operated generator "buzz" signals other phone; with plastic case. Useful where radio communications is not practical. 8.5x3.5x3.5, 4 lbs.

USED-CHECKED \$35.00 each; 2 for \$60.00

TA-312 FIELD PHONE, requires two D-batteries (not sound-powered); replaces old EE-8 phones. With canvas case; 12x7x4, 12 lbs. sh.

USED-CHECKED \$65.00



JAN-BOXED ELECTRON TUBES

6B4GA TRIODE , Sylvania; GA-glass + cathode version of old 6B4G. Does not test like 6B4G in tube checker but performance comparable in most circuits	\$17.50
2A3 Penta-USA (but looks Chinese-made)	\$14.00
2K25 Raytheon blue	\$40.00
3BP1 CRT	\$15.00, 2/\$25.00
4CX300A/8167 Eimac	\$85.00
4D32 Raytheon	\$35.00
5R4WGB Cetron	\$3.50
1625 NU	\$4.50
5691 Richardson	\$8.00
5751 GE	\$3.50
5998A GE	\$9.95
6146W GE	\$19.95 ea.; 10/\$175
6922 Phillips-ECG, industrial 6DJ8	\$3.00 ea.; 10/\$24.00; 100/\$185.00


Prices F.O.B. Lima, O. • VISA, MASTERCARD, DISCOVER
Allow for Shipping • Write for latest Catalog
Address Dept. ES • Phone 419/227-6573 • Fax 419/227-1313

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

ACTIVE MICRO We Want Your Excess Inventory

- INTEGRATED CIRCUITS
- MEMORY (NEW OR USED)
- EPROMS (NEW OR USED)
- CIRCUIT BOARDS
- DIODES
- TRANSISTORS
- LED'S

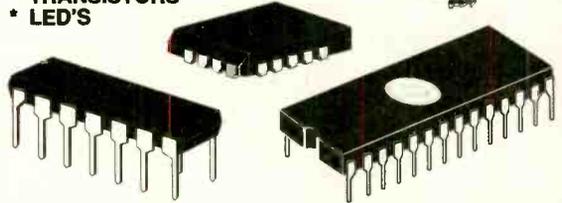

Tel 310-494-4851 Fax 310-494-4913
1891 Obispo Ave Signal Hill, CA 90804

The Greatest Thing Since Sliced Bread

Our free Consumer Information Catalog lists more than 200 free and low-cost government booklets that are helpful and practical. To get your free copy, send your name and address to:

Consumer Information Center
Department GT
Pueblo, Colorado 81009

BREAST CANCER BEGINS
EVEN SMALLER THAN THIS.
THAT'S WHY YOU
NEED A YEARLY
MAMMOGRAM.
ESPECIALLY AS
YOU GET OLDER.
MAMMOGRAMS
CAN DETECT
LUMPS TOO
SMALL FOR
YOU TO FEEL
AND EARLY
DETECTION
MAY SAVE
YOUR LIFE,
SO CALL
1-800-
ACS
2345.

GET A MAMMOGRAM.
EARLY DETECTION IS THE BEST PROTECTION.
A Division of
AMERICAN
SCANS
CORPORATION


FREE HOME AUTOMATION CATALOG!



Home Controls' color catalog features truly affordable X-10 powerline controls, IR products, CCD cameras, wireless home control devices, security products, drapery controls, audio systems, and everything you can imagine for the remote and automated control of your home!

Call Toll Free
1-800-CONTROL

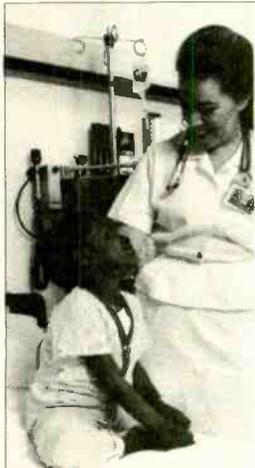Contact us by E-Mail: homectrl@electriciti.com
Lowest Prices Guaranteed • Same Day Shipping • Superior Technical Support
No Minimum Order • Fabulous Freebies • Great Selection!



Precious Life

Not too many years ago, this nurse was a patient at St. Jude Children's Research Hospital. She fought a tough battle with childhood cancer. And won.


Until every child can be saved, our scientists and doctors must continue their research.

To find out how you can help, call 1-800-877-5833.




ST. JUDE CHILDREN'S
RESEARCH HOSPITAL
Danny Thomas, Founder

Miniature Transmitters and Receivers

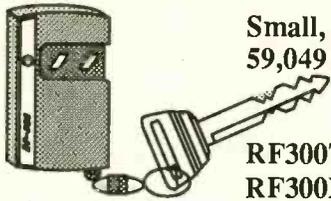


Small, Attractive, High End Quality, 2 Channel 318 MHz Transmitter
59,049 Settable Codes, 120'-300' Range, 1-1/4" x 2" x 9/16", Assembled

		Qty	1	5	10
RF300T	150' Range Transmitter		24.95	19.95	15.95
RF300XT	300' Range Transmitter		29.95	24.95	19.95

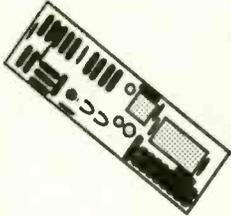

Small, High End Quality, 2 Channel Receiver for the RF300 Transmitters
1-1/4" x 3-3/4" x 9/16" PCB w/ .1" spaced pads for standard connectors
Input: 8-24 vdc Output: Gated CMOS Momentary and Latching Lines

		Qty	1	5	10
RF300R	Receiver, Fully Assembled		24.95	20.95	16.95
RF300RK	Receiver, Complete Parts Kit		19.95	15.95	12.95
RF300PA	Pre-Amplifier. Doubles Range		14.95	11.95	9.95

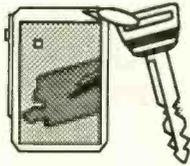

Small, Economical, Single Channel Transmitter and Receiver Set
Set Code, 60' Range, 1-7/8"x2-3/8"x7/16" (T), 2"x2-3/4"x9/16" (R)
Receiver Input: 5 vdc Output: Gated TTL Momentary Line

		Qty	1	5	10
RF60	Transmitter and Receiver Set		24.95	19.95	14.95

Add \$ 4 shipping for first item + \$ 1 for each additional item. Ca. residents add 8.25% tax
Visa, Mastercard, Money Orders Personal Checks and Cash C.O.D.s

Visitect Inc.

P.O. Box 14156 Fremont, CA. 94539 (510) 651-1425 Fax (510) 651-8454

CIRCLE 321 ON FREE INFORMATION CARD

Earn \$1000

A Week While You Learn High Paying VCR Repair.

Earn While You Learn . . .
Secrets Revealed . . .



Train at Home

If you are able to work with small hand tools and possess average mechanical ability, you could earn top dollar part time or full

time. Our learn by doing method teaches you how to work on VCR's without boring unnecessary electronic basics.

For Free Information Package Send Coupon to:
Foley-Belsaw Institute, 6301 Equitable Road,
Kansas City, MO 64120

Check VCR or another High Paying Career Field

(Check One Box Only)


- VCR Repair, Dept. 62496
- Computer Repair, Dept. 64393
- TV/Satellite Dish, Dept. 31268
- Computer Programming, Dept. 35216
- Computer Specialist, Dept. 38068
- Networking Specialist, Dept. 39055
- Electrician, Dept. 95075



Since 1926

Name _____
Address _____
City _____
State _____ Zip _____


CIRCLE 331 ON FREE INFORMATION CARD

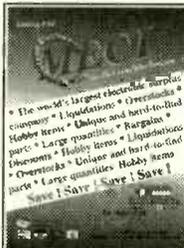

Free Catalog

If you are not getting this catalog you are missing out on some of the best deals in electronics today! We have thousands of items ranging from unique, hard-to-find parts to standard production components. Call, write, or fax today to start your free subscription to the most unique catalog in the industry, filled with super values on surplus electronic and hobbyist type items. If you have a friend who would like to receive our catalog, send us their name and address and we will gladly forward them a complementary 100 page catalog.

Why pay more? Call today.

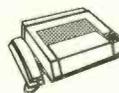

340 East First Street Fax Order Line
Dayton, Ohio 45402 1-800-344-6324

Order Toll-Free
1-800-344-4465

CIRCLE 251 ON FREE INFORMATION CARD

BEST DEALER PRICING!

CABLE DIRECT

CONVERTERS • FILTERS
DESCRAMBLERS

IMPROVE YOUR IMAGE WITH
VIDEO STABILIZERS



100%
MONEY BACK
GUARANTEE!

30 DAY
FREE
TRIAL!

FREE Cable TV Catalog.



Now you can tune-in your favorite cable TV programming and **SAVE \$100'S - EVEN \$1000'S** on premium CABLE TV EQUIPMENT.

MODERN ELECTRONICS

1-800-906-6664

2125 S. 156TH CIRCLE • OMAHA, NE 68130

1 - CHIP MICROCONTROLLER TRAINER



PARTS KIT INCLUDING:

- Programmed Motorola 68705P3 (only 1 IC required)
- Display 1 X 16 Alphanumeric LCD
- Keypad 5 X 4
- 4 MHz clock oscillator, reset switch, R, C

MANUALS - experiments & programming - 200+ pgs

\$89 plus shipping and handling

VISA, MC, COD CA residents add CA sales tax

Just Add Wire And +5VDC To Get Started

SQUARE 1

ELECTRONICS

P.O. Box 501, Keiseyville, CA 95451
 Order (800) 220-3916
 Support (707) 279-8881
 FAX (707) 279-8883
 Hours 7AM - 4PM Pacific M - F

CIRCLE 232 ON FREE INFORMATION CARD

SURVEILLANCE

FM TRANSMITTERS MINI (KITS)

- 3-VOLT FM XMTR, up to 300 ft. indoors, 1500 ft. outdoors
- PHONE XMTR, range to 500 ft., uses phone-line power
- Sound-Activated XMTR, range to 500 ft.
- 2-STAGE XMTR, 9-Volt, very powerful

All above require simple soldering at 2 to 4 places.
\$29.95 ea.**

TELE FM WIRELESS MONITORING SYSTEM.
 (Kit) **\$99.00***

TELE CALL FORWARDER. Transfers incoming calls **\$99.00***

CALLER ID. Registers incoming number. **\$99.00***

TEL REGISTER WITH PRINTER. Records dialed number, duration, and prints record. **\$139.00***

12-HOUR LONG-PLAY RECORDER. Modified Panasonic. Records 6 hrs. on each side of 120 tape (supplied). Compatible with VOX and Tel Rec Adapter. **\$119.00***

VOX VOICE-ACTIVATED SWITCH. Makes recorder self-activating with voices or other sounds. **\$28.50****

TELE RECORDING ADAPTER. Records incoming and outgoing calls. **\$28.50****

TELEPHONE SCRAMBLERS. Over 4,000 separate codes. **\$199.00***

VOICE CHANGER. Changes man's voice to lady's and vice versa. **\$49.00***

For Shipping & Handling add *\$5.00 and **\$2.00 per item. Colo. residents add sales tax. Mail Order, VISA, M/C, COD's o.k. Inquire for dealer prices. Free catalog.

MUCH, MUCH MORE — OUR 25TH YEAR!

TOLL FREE 1-800-926-2488

A.M.C. SALES, INC.

193 Vaquero Dr., Boulder, CO 80303
 Tel: (303) 499-5405, Fax: (303) 494-4924
 Mon.-Fri. 8 a.m.-5 p.m. Mtn. Time

CIRCLE 231 ON FREE INFORMATION CARD

CABLE TV DESCRAMBLERS



We Carry A Full Line Of Premium Converters And Descramblers Compatible With:

- Scientific Atlanta™ Systems
- Jerrold™ Systems
- Tocom™ Systems
- Zenith™ Systems
- Pioneer™ Systems

SATISFACTION GUARANTEED OR YOUR MONEY BACK!

BEST PRICES FREE CATALOG

Please have the MAKE & MODEL # of your full premium service cable box ready when you call

ALLSTAR ELECTRONICS

800-782-7214

HOURS: 9-6 M-F 10-3 Sat EST

It is not the intent of Allstar Electronics to defraud any pay TV operator. Anyone implying theft of service will be denied assistance. All brand names are registered trademarks of their respective owners & are used for reference only. 110-64 Queens Blvd., 4465, Forest Hills, NY 11375. NO NYS SALES!

Robot Kits


- ✓ *Academic-Level Books*
- ✓ *Build it Yourself*
- ✓ *Action Packed*

EASY TO BUILD You do ALL electronic & mechanical assembly using 2-color Instruction Books with step-by-step, well-illustrated directions for assembly, experiments and testing. Each Robot Kit applies different electronic & robotic principles. Learn how Robots work and have fun at the same time!

606A "Scrambler" All Terrain Robot This 6-legged Robot walks over rough terrain. Uses high-tech infrared beam to sense and avoid avoid objects in its path. 32 page Book. **\$37.95**



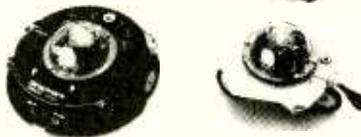602A "Blinky" Pathfinder Robot Follows path made with a marker pen or tape. Red/green LEDs react to steering changes, adding fun and interest. 28 page Book. Infrared emitter/detectors. **\$36.95**



603A "Copycat" Programmable Robot Program direction, light and sound using detachable keypad (included) or optional PC. Learn digital logic basics. 44 page Book. **\$57.35**

601A "Scooter" Sound Controlled Robot Backs up, changes direction, goes forward when it hears loud noise or hits an object. Florescent red. 24 page Book. Fast-paced excitement! **\$18.95**

DEPENDABLE PRODUCTS Since 1963, Graymark's ONLY business has been producing educational electronic kits. We do one thing and we do it right. That's why Graymark has the largest selection of electronic kits. And, our **"It works or we fix it"** policy guarantees success for YOU!

ORDER TODAY! Phone: VISA/MasterCard
 Mail: Check/Money Order, VISA/MasterCard
 Add: \$4.00 Shipping

CALL FOR FREE 40 PAGE CATALOG

Graymark

P.O. Box 2015, Tustin, CA 92681

CIRCLE 221 ON FREE INFORMATION CARD

800-854-7393

PIC Programmer Development Tools

JM-PICE \$245

- Programmer for PIC 16C5X, 16C6X, 16C7X, 16C84, and 17C4X in DIP packages.
- Assembler and Simulator.
- Emulates program memory, registers, and I/O for the PIC 16C5X.
- Instruction-level emulation for the PIC 16C71 and 16C84.
- Programmer only \$155, Complete package \$245. 15 day money-back guarantee.
- Adapters for emulating 16C6X and 16C7X will be available soon.

80C552 Development System

- 8051 core processor with 8 channel 10-bit A/D and PWM.
- 24 more I/O and RS-232 port.
- 32K ROM and 64K RAM.
- \$130 each SBC. High performance development system includes assembler, disassembler, real-time execution and debugging, monitor program, and examples (\$70 more).
- 80C31 Development System is also available.

ROMY-16 EPROM EMULATOR

Emulates ROM or RAM in 8- and 16-bit systems. \$195 (2716-27256) or \$245 (2716-27010). Window/menu driven interface. 15 day money-back guarantee. Optional assembler, disassembler, and ROM debugger \$100 each CPU.

68HC11 Development System

- Eight channel 8-bit A/D converter.
- 32K ROM and 32K RAM.
- \$120 each SBC. 40x2 LCD \$20.
- Add \$70 for the real-time integrated development system.
- Microprocessor Simulator/Debugger and Custom design are available.

J&M Microtek, Inc.
83 Seaman Road, W Orange, NJ 07052
Tel: (201)325-1892 Fax: (201)736-4567

Pocket Cube™

Wireless cable box tester for authorized technicians. Surface Mount Technology. Works on J***** models D*5, D*V5, D*7, D*V7, D*BB, C*T, W*R.

Only \$59.⁹⁵!

(plus \$8 S&H)

30 Day Warranty

Pocket Cube with filter \$69.95+S&H
Quantity discounts available.
Dealers Welcome.

NEW!

Pocket Cube Plus™

For testing of raw boxes.

CALL!

Test chips available for J***** and SA8600.

Order Toll Free


1-800-417-6689

Mon-Fri. 9AM-5PM EST

If busy please keep trying.

VISA, MC, MO or CASHIERS CHECK
IEC, P O Box 52347, Knoxville, TN 37950-2347
Pocket Cube is a test generator ONLY.
Do not use these devices without authorization from your local cable company and local officials
No TN sales.

The Pocket Programmer Only \$129.95

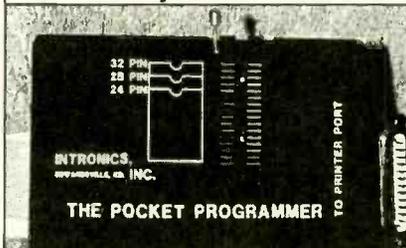

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs Eprom, EEprom, Flash & Dallas Ram. 27(C) / 28(C) / 28F / 29F / 29C & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, PLCC, 5-Gang, 874X, 875X MCU's, 40-Pin X 16 & Serial Eprom's, and Eprom Emulator to 32K X 8.


Same Name, Address & Phone # for 13 Years... Isn't it Amazing?

Intronics, Inc.
Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add \$4.75 COD
Tel. (913) 422-2094 Add \$4.00 Shipping
Fax (913) 441-1623 Visa / Master Charge

OUR LOWEST PRICES!

B&K 20MHz Dual Trace Oscilloscope Probes Included

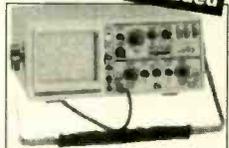- 1 mV/div sensitivity
- AUTO/NORM triggered sweep operation
- AC, TVH, TVV and line coupling
- Calibrated 19 step time base with x-10 magnifier




model #2120 2 Year Warranty **385.00**
model #2125 w/delayed sweep **529.95**
model #2190A 100MHz 3 Ch **1339.95**

Call For Free! 40 Page Catalog

Pinhole Camera

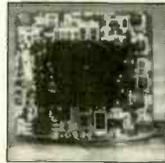
- Requires 1/16" opening size
- 1-1/2" x 1-1/2" x 7/8"
- Power 7.5-12VDC n
- 8 lux
- 3.8mm lens included
- 380 lines resolution
- 12V DC Power Supply 9.95



model #CVC50PH **139.95**

Protek Test Equipment

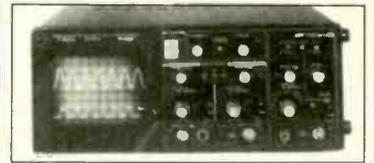20 MHz Oscilloscope Dual Trace w/ Component Checker



#P3502C Dual Trace **375.95**
#P2510 100 MHz 3 Ch. 8 Trace **1195.00**

Cutting Edge The model 506 meter has a RS-232C serial interface. Measured values are transmitted to the computer via an interface cable and supplied software WINDOWS and MS-DOS.
DCV 1000V ACV 1000V AC/DC Current 20A
Res. 40 meg Ω freq. 10MHz
REG. -189.95
model #506 **169.95**

Metal Detector Wand by Garrett Special

model #MD1 **145.95**
Sale!

Elenco Digital Capacitance Meter

- 1 UF to 20,000 UF
- Banana jack and special insertion jack included

model #CM-1555
49.95

Call For FREE Catalog & Technical Assistance

Add \$8.95 Shipping/Handling
NYS Add Tax
Visa/MC/Discover/Amex

ALL PHASE
VIDEO-SECURITY INC.
WHOLESALE VIDEO WAREHOUSE

MAIL ORDERS TO:
70 CAIN DR.
BRENTWOOD, NY 11717

1-800-945-0909

FAX: 516-435-7494

American Heart Association

EXERCISE.



TRAVEL LIGHT.

Is your Cable Company Alienating You?



Say **NO** to unearthly rental fees!

Owning your cable equipment saves you the high cost of monthly equipment rental charges, and gives you control of your TV.


We have the *Best* in

CONVERTERS and DESCRAMBLERS!

Everquest • Panasonic • Jerrold • Zenith • Pioneer
Scientific Atlanta • Oak • Eagle • Hamlin • Tocom

1 800 624-1150

FREE Catalog!

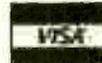


Member of
National Consumer
Cable Association

MD Electronics

P.O. Box 241296 • Omaha, NE 68124

© JERROLD, STARCOM, PANASONIC, ZENITH, PIONEER, OAK, SCIENTIFIC ATLANTA, EAGLE, HAMLIN, and TOCOM are all registered trademarks. All references to the above mentioned equipment is for identification purposes only. We are in no way implying that any of the products in this advertisement are original equipment. M.D. Electronics is in no way affiliated with the above mentioned companies or corporations.

CIRCLE 304 ON FREE INFORMATION CARD

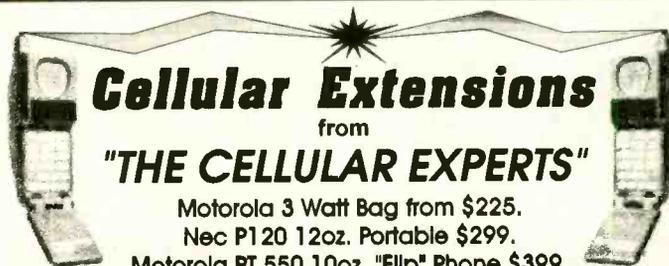

Cellular Extensions

from

"THE CELLULAR EXPERTS"

Motorola 3 Watt Bag from \$225.

Nec P120 12oz. Portable \$299.

Motorola PT 550 10oz. "Flip" Phone \$399.



Others available, buy new from us, or send us your phone.
Get a second or third phone with no additional monthly charges!
Motorola, NEC, Panasonic, Audiovox and many others!


Fax Back Hotline, For 24hr. info. call from your FAX (714) 581-7460 or call

(8 0 0) 4 5 7 - 4 5 5 6

Nationwide paging available. C.G.C. Dealer inquires welcome.

May 1996, Electronics Now

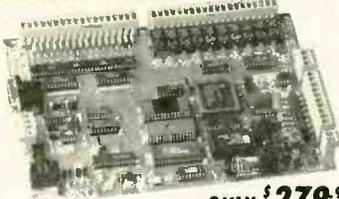BASIC PROGRAMMABLE CONTROLLER APPLICATION READY!



ONLY \$279⁹⁵

FEATURES: complete real world interface • plug on I/O connectors • 10 power relay outputs • 16 isolated inputs • 3 LED outputs • 8 ch 10 bit A/D • 2 ch 8 bit D/A • 80C552 micro • 14.7 Mhz clock speed • 32 K battery SRAM • 32 K ROM • RTC • I2C expansion bus • RS232/485 serial port • full two-way X10 communication with optional controller • single 12 Vdc operation • complete line of I/O expansion boards

APPLICATIONS: Industrial control • HVAC systems • home automation X10 controller • security • data logging • remote control & monitoring

SYLVA Control Systems a division of Sylva Energy Systems Inc.
519 Richard Street, Thunder Bay, Ontario, Canada P7A 1R2
Ph. 807-683-6795 Fax 807-683-6485 BBS 807-767-0587

WEB PAGE: <http://www.sylvacontrol.baynet.net>
Email: sylva@mail.baynet.net

Printed Circuits in Minutes Direct From LaserPrint!

8 1/2" x 11"
* Or Photocopy
**Use standard household iron or P-n-P Press.

1. LaserPrint*
2. Press On**
3. Peel Off
4. Etch



Use Standard Copper Clad Board
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100
Visa/MC/PO/Ck/MO \$4 S&H

Techniks Inc.
P.O. Box 463
Ringoes NJ 08551
ph. 908.788.8249 fax 908.788.8837
<http://chelsea.ios.com/~techniks>
Retail Dealer Inquires Invited

"NOW BUYING" \$\$\$ BEST PRICES \$\$\$ AVAILABLE

SCIENTIFIC ATLANTA™ 8536 THRU 8600	PIONEER™ 5135 THRU 6300
ZENITH™ 1086 THRU 1612	JERROLD™ DPV7 DPBB7
TOCOM™ 5503A VIP THRU 5507	DPV70 DPBB70 CFT

Midwest's Largest Brokers
(We buy quantities of one to one thousand units)

NATIONAL CABLE BROKERS
(219) 935-4128

NEW EASY PC


BRITISH DESIGN AWARD

SCHEMATIC and PCB C.A.D

ONLY **\$145**

Includes

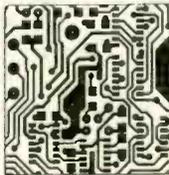- MGA, CGA, EGA & VGA compatible.
- Design large multi layer boards.
- One level pull down menu and quick keys for fast layout.
- Dot matrix, laser, plotter, Gerber & N.C. drill output.
- 6 Month Free update
Free Demo



7840 ANGEL RIDGE ROAD
ATHENS, OHIO 45701
(614) 592-1810
Visa & MasterCard Accepted

New ELECTRONIC GUN ! Add FIREPOWER to almost anything!

web: <http://www.hoopsware.com>
email: sales@hoopsware.com

Amazing new Electronic Gun has only one moving part - the projectile! Imagine the possibilities!! This simple, silent, and inexpensive project uses parts mostly available from Radio Shack and can be built in as little as 30 minutes. The same principles can be used to build a silent weapon with devastating force! You must be over 18 years of age to order. Complete plans only \$15.00 (\$20.00 Canada and Mexico). Order #GGUN.




VISA/MC ORDERS (702) 322-8875
or send check or M.O. to:

Hoopsware
P.O. Box 3079, Dept. EN
Sparks, NV 89432-3079

16 Bit Control

& Data Acquisition System

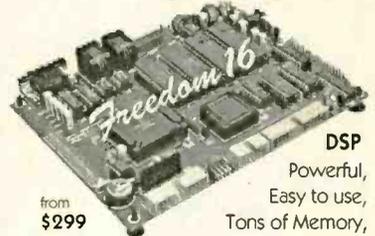

DSP
Powerful,
Easy to use,
Tons of Memory,
I/O. & features:

16.8MHz 68HC16
RS-232 & RS-485
RT clock option

34 digital I/Os (7 IRQ)
+ LCD/Keypad port
+ 8 ch 10b fast A/D

Affordable "C" compiler/library
Multi-tasking kernel
Up to 256K ea. SRAM, FLASH memory

INTEC INOVENTURES INC.

Ph: (604) 721-5150 FAX: 721-4191

CABLE CONVERTERS/DESCRAMBLERS

★ ★ ★ ★ **SUPER BUYS** ★ ★ ★ ★
★ **FULLY REFURBISHED UNITS** ★

TOCOM™ ★ JERROLD™ ★ SCIENTIFIC ATLANTA™ ★ ZENITH™ ★ PIONEER™
"WE SERVICE MOST PRIVATELY OWNED CABLE CONVERTERS"

Phone **(219) 935-4128**



SORRY, NO INDIANA SALES

NATIONAL CABLE BROKERS

1801 W. JEFFERSON ST., PLYMOUTH, IN 46563

OUR POLICY: All products carry a two year warranty. Warranty covers parts and labor and return shipping.
WARNING: Theft of cable services is a crime. National Cable will not knowingly defraud any pay TV operator and we will not assist any individual or company in doing the same.

INTERFACE TO YOUR PC KEYBOARD INPUT !

Our KE-18 Keyboard Encoder converts input from switches and keypads into PC compatible keyboard signals.


- Use with or without your own PC's keyboard
- Scans 9 x 9 matrix or 18 individual inputs
- PCXT, AT, PS/2 and Compatibles
- Looks like a Keyboard to your Computer



Hagstrom Electronics
2 Green Lantern Boulevard
Endicott, NY 13760 (607) 786-7523

BUGGED??

EAVESDROPPING is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations **RIGHT NOW!** Are you sure you're safe? **FREE CATALOG** tells you fast! Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and **EXTREMELY** profitable (up to \$250 hr) full/part-time income. Call Now! **1-800-732-5000**

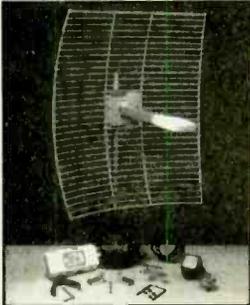

Quality Microwave TV Systems

**WIRELESS CABLE - ITFS - MMDS
ATV - INTERNATIONAL - S-BAND**
Amplifiers • Antennas • Books • Components
Filters • Systems • Video Products

- RF Frequency 1990 - 2700 MHz
- Cable Ready - VHF - UHF Outputs
- SASE For "FREE" Catalog or Send \$1

PHILLIPS-TECH ELECTRONICS

PO Box 8533 • Scottsdale, AZ 85252

CHALLENGER SYSTEM
33-Channel 52dB+ Gain
Complete Grid \$265
Five Year Warranty
FREE SHIPPING

ORDER LINE 800-880-MMDS
CATALOG / INFO 602-947-7700
FAX LINE 602-947-7799

Visa • M/C • Amx • Disc • COD's • Qty Pricing

CIRCLE 325 ON FREE INFORMATION CARD



Finally, a low cost way of getting into the monitor repair business. With the Checker 12 you can test and repair computer monitors with speed and accuracy. The "Checker 12" is an **easy to operate**, hand held, battery, or AC operated computer color monitor pattern generator. With its support of CGA(15.75khz), EGA(22khz), MACII(35khz), and VGA modes 1,2,3 (31.5khz), 800X600(35khz), **1024X768 interlaced(35khz)**, **1024X768 non-interlaced**, & **1024X768NI with sync on Green** (48khz), you can easily check out a monitor in all of its' modes. With its' single mode switch, you know exactly what type of monitor you are testing. You don't have to be a monitor expert to use the Checker 12. Its' front panel color pictures, show just what you should be seeing on the monitor under test. You can quickly tell if the monitor is a VGA, SVGA, or a SVGA/NI. No more guessing. The "Checker 12" provides various test patterns for VGA monitors. X-hatch, for size and linearity and convergence set-up. White screen, for purity and CRT burn evaluation. Color bars and **8 step gray scale** for color tracking and balance. There is also a single color mode that allows for single color channel operation. There is no easier way to test and evaluate monitors than with the Checker 12.

Price: \$295.00 + \$5.00 S&H.

Includes battery, AC adapter, Mac adapter and 120 day warranty

We also have the Checker VI, a six port *stand-alone* VGA (640x480) test pattern generator, **NO computer required**. Just \$249.95.



CMIMI



Computer & Monitor Maintenance

6649 Peachtree Ind., Blvd., Suite N-1 • Norcross GA 30092
1-800-466-4411, 770-662-5633 (Voice), 770-840-8814 (Fax)
We're on the WEBB at <http://www.computermonitor.com>

CIRCLE 217 ON FREE INFORMATION CARD

Throbbing Modems

by Joshua Bagby,
of Penthouse fame!

The reviews tell it all:
this is the #1 book on
cyber-intimacy! 290
pages, November 1995,
\$17.95 **NEW!**

ULTIMATE Scanner

Bill Cheek's 3rd book
on scanner mods is just
terrific! Enter the 21st
century with the mad
modmaster. 242 pages,
highly illustrated, large
format, 1995, \$29.95

EMERGENCY RADIO!

Scanning the news
as it happens

by Norm Schrein, "Mr.
Scanner," President of
the Bearcat Radio Club
214 pages, \$14.95

TravelScan

*Good Frequencies
Across America*
Henry Eisenson (FINALLY!)
150 pages, 1/96, \$9.95

NEW (1/96)
Great reviews!

Smart Casino Gambling
Olaf Vancura, PhD
364 pages, \$24.95

**Cheating at Blackjack,
SQUARED**
Dustin D. Marks
208 pages, \$24.95

S/h \$4 1st book, then \$2 ea.
CA add tax.

✓ our WWW site!

INDEX Publishing Group, Inc.
3368 Governor Dr., Suite 273S
San Diego, CA 92122
Fax orders: (619) 281-0547
Toll free orders: 800-546-6707
www.electrictiti.com/~ipgbooks
e-mail: ipgbooks@indexbooks.com

MONDO • TRONICS • Robot Store

Your source for:

Miniature Robot Kits

Robot Books

Robot Electronic Kits

Muscle Wires®

Robot Videos

& more!



Controlling the World
With Your PC #3-165 \$35.00
Book, 256 pages w/PC disk.



Sonic Rover Robot Kit
#3-174 \$27.95

Visit our electronic store
on the World Wide Web:

www.robotstore.com
or email us to receive our email catalog.

Mondo-tronics Inc
524 San Anselmo Ave. #107-103
San Anselmo, CA 94960
email: info@mondo.com

SURVEILLANCE

The Latest High Tech
Professional Electronic Devices
Our latest catalog offers a HUGE selection
of surveillance, privacy devices including:
hidden video equipment, electronic kits,
telephone recording systems, touch tone
decoders, scanners, telephone tap
detectors, bug detectors, voice disguisers,
telephone scramblers, locksmithing tools,
and more. Catalog \$5.00.

SPY OUTLET

P.O. Box 337, Buffalo, NY 14226
(716) 691-3476/(716) 695-8660



**Communications
Systems
Laboratories**
1-800-629-9483

Hobbyists- Embedded Control Systems for home
Automation. **MMCS-10** Cross Point 8x8 Video/Stereo-
Audio electronic patch panel \$695.00. **TL-100** Color
Organ Kit \$195.00. **T-10** DTMF Gen/Detector \$225.00.
Cable TV- Use our product line to automate your
operations on a modest Budget. **VCS-26** Commercial
Insert/billing logger. \$1595.00. **VCS-76** Channel
Controller-4VCRs, 2 Laser Discs, 2 external sources,
Two independent outputs \$2995.00. **MMCS-11** Wide-
band Video/Stereo Audio 8x8 CrossPoint Switch,
Computer Controllable \$895.00.
Call Toll Free for Info/Catalog or to Order. **MasterCard**
VISA. Fax 1-808-625-7035. 1yr warranty on all products.

VIDEO SYNC GENERATOR



Restores Horizontal and Vertical
Sync Lines from Distorted
Analogue Video Formats

For Free Information Package on Completed Units and Pricing

• Call Toll Free •
1-800-236-5778

R.C. Distributing • PO Box 552 • South Bend, IN 46624

CRYSTAL CONTROLLED SURVEILLANCE

VHF & UHF PROFESSIONAL ENCASED PARTIALLY
ASSEMBLED TRANSMITTER KITS
Countersurveillance. Also Tunable 70 to 305 MHz Kits. We
Design & Manufacture Our Equipment. Custom Design.

FOR CATALOG SEND \$2.00 TO:

SHEFFIELD ELECTRONICS CO., P.O. Box 377940-C
Chicago, IL 60637-7940, Tel. (312) 324-2196

BUY BONDS

Cable TV Descramblers

Converters * Filters * Accessories

30 day Free Trial - NO RISK!
Unbeatable wholesale prices!
Affordable extended warranty
1 Year Warranty on all products

Free
Catalog



Call the cable professionals!

Credit Cards Welcome!

1-800-379-3976

Prices starting
as low as \$99!

New Surveillance Devices!

Smoke Alarm and Table Clock Video Cameras

Ultra miniature video cameras hidden in smoke
alarm or alarm clock - your choice. Wide field of view
and super .1 lux low light sensitivity! Undetectable!

Best price on surveillance cameras anywhere!

Telephone Transmitter Kit hidden in dual modular adaptor.
Transmits both sides of conversation to any FM radio up to 1/4
mile. "SnapKit" technology. Uses phone line for power and
antenna! Goes completely unnoticed. **MA-100** \$25.95

High quality cassette deck plugs
directly into telephone jack! Records up to
12 hours of conversations on a single cassette.
Recording starts and stops automatically when
phone is used! **Vis a/MC (214)255-7490**

THR-12
12 Hour
Telephone Recorder
\$99.95 Free shipping! Check/Money orders also accepted

Seymour-Radix Inc. Box 166055-N Irving, TX 75016
Now you can visit us on the internet at <http://www.why.net/home/sr/>

CABLE TV CONVERTERS

Equipment & Accessories
Wholesalers Welcome

Call **VISION TIME PRODUCTS**
1-800-310-1153 M-F 8a-8p
NO TENN SALES

ELECTRONIC SHOPPER

PROGRAMMERS

Advantech LabTool 48
1295. ADVANTECH LABTOOL48
669. EETOOLS ALLMAX PLUS
596. ADVANTECH PC-UPROG
569. MOD-MCT-EMUPA
429. XELTEK SUPERPROII
329. XELTEK SUPERPROIIR
424. NEEDHAMS EMP-20
189. XELTEK ROM MASTER II
149. XELTEK ROM MASTER I
135. EETOOLS ROM MAX I
189. EETOOLS ROM MAX 4
419. EETOOLS PROMAX
49. SUNSHINE I GANG
125. SUNSHINE 8 GANG

Needham
EE Tools
Needham
Xeltek

General Device Instruments
Sales 408-241-7376
Fax 241-6375 BBS 983-1234

It's Here!!!

PBASIC* Compiler

Put BASIC Stamp I programs
directly into your PIC -
no BASIC Stamp necessary!

Creates editable assembler source and
hex files for use with any PIC programmer.

Introductory price \$99.95

❖ Pocket PIC Programmers from \$34.95

❖ PICProto prototyping boards \$9.95-\$19.95

*BASIC Stamp and PBASIC are trademarks of Parallax, Inc.


microEngineering Labs

Box 7532 Colorado Springs CO 80933
(719) 520-5323 FAX 520-1867

Smart Battery Charger

JUN 87 QST

BY WARREN DION N18BH

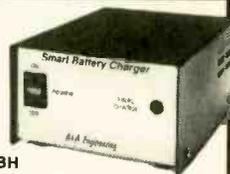

FOR GEL-CELLS or LEAD ACID BATTERIES.
Features: Precision temperature tracking voltage
reference & three mode charging sequence.
Standard kit is for 12V @ 1/2 or 1 Amp, user
selectable. Can be connected to the battery
indefinitely, will not overcharge. Weighs 2 pounds
and measures 4"W x 5 1/2"D x 2 1/2"H. Finished
enclosure included in kit.

Complete Kit Only \$59.95
Assembled & Tested \$79.95

CA Residents add 7.75% sales tax. S&H: \$5.00
(insured). Foreign orders add 20%. For more info
or price list; send legal size SASE (52c) to:

A&A Engineering
2521 W. La Palma #K • Anaheim, CA 92801
(714) 952-2114 • FAX: (714) 952-3280



EZ-EP DEVICE PROGRAMMER - \$169.95

- Fast** - Programs 27C010 in 23 seconds.
- Portable** - Connects to PC Parallel Port.
- Versatile** - Programs 2716-080 plus EE and Flash (28F,29C) to 32 pins.
- Inexpensive** - Best for less than \$200


- Correct implementation of manufacturer algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web page.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters.

Adapters Available	
EP-51 (8751,C51)	\$39.95
EP-11 (68HC11 E/A)	\$59.95
EP-PIC (16C5x,61,62x,71,84)	\$49.95
EP-PIC64 (16C62,83,64,65,73,74)	\$39.95
EP-PEEL (ICT 22V10, 20G10, 18V8)	\$59.95
EP-SEE (93x,24x,85x)	\$34.95
EP-16 (16bit 40 Pin EPROMs)	\$49.95
EP-49 (8742,48,49)	\$49.95
EP-750 (87C750,751,752)	\$59.95
EP-Z8 (Z86E03,04,05,06,07)	\$39.95
EP-55 (8755)	\$39.95
EP-51-PLCC (8751, C51)	\$59.95
EP-PIC-SOIC (16C5x,61,62x,71,84)	\$59.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-LCC (LCC EPROMs)	\$49.95

M'L Electronics
 3526 Jasmine #4; Los Angeles, CA 90034
 310/837-7818 Fax/BBS: 310/841-6050
<http://www.cs.ucla.edu/cs/grade-gs3/loving/www/m2l.html>
 CA orders add 8.25% sales tax. Ground shipping: \$5. 3 Day - \$7. 2 Day \$10. Overnight \$17. COD \$4.75.

ACTUAL SIZE B&W CCD BOARD CAMERA

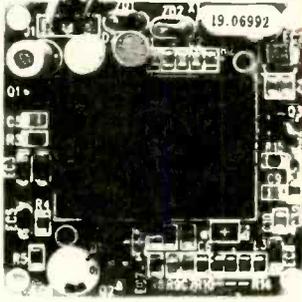3.6mm Adjustable manual focus or 5.5mm pin hole lens
LATEST SONY HYPERHAD IMAGE SENSOR
 PIN HOLE LENS ONLY NEEDS 1/16" HOLE TO SEE THROUGH
 RESOLUTION: MORE THAN 380 LINES
 MIN. ILLUMINATION: 0.4 LUX
 SENSITIVE TO IR LIGHT
 S/N RATIO: BETTER THAN 50DB (AGC OFF)
 POWER: 9 - 13 VDC LESS THAN 150 MA
 WILL RUN ON 9 VOLT BATTERY
 BUILT-IN ELECTRONIC AUTO IRIS
 SHUTTER SPEED: 1/60 - 1/50,000 SEC
 VIDEO OUTPUT: 75 OHM, 2/1 INTERLACE
 1.0 VOLT P/P COMPOSITE
 CONNECTS TO ANY MONITOR OR VCR



- 1.5" SQ. HIDE THIS CAMERA IN PICTURES
- SMOKE DETECTORS
- THERMOSTATS
- LAMPS
- CLOCKS
- RADIOS



Plug in power supply \$ 6.95
 QTY 3.6mm PIN HOLE
 1-3 \$ 115.00 \$ 130.00
 4-9 \$ 110.00 \$ 125.00

BC ELECTRONICS
 1508 LEXINGTON - BEDFORD, TEXAS 76022
PHONE (817) 267-7792 FAX (817) 283-7797

SHOW TIME CABLE

Your Cable Connection To The Stars!

Order your **FREE** catalog today!
1-800-643-4258



STARGATE SST

- Converters & Descramblers
- All Makes & Models
- Quantity Discounts
- 30-day Money Back Guarantee
- Best Warranties


Show Time Cable
 643 N 98th St STE 260
 Omaha, NE 68114

COD • MasterCard • Visa
 Amex • Discover

Motion Control System

\$249.95

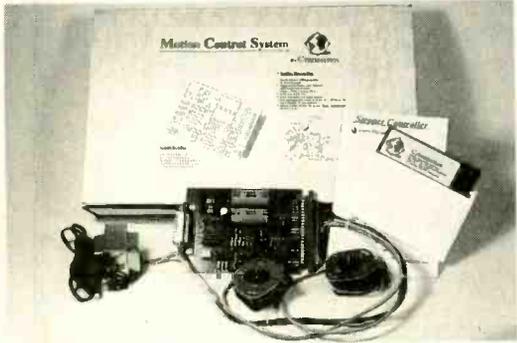Includes Stepper Controller Card, 12VCT Transformer, (2) 4 Phase Stepper Motors, Easy to use I.B.M Software! Connects to any I.B.M. Compatible LPT Port (1,2,3)....



- * **Nothing more to Buy!**
- Easy Installation 15 minutes or Less!
- No Tools Required!
- Design Robots, Plotters, Laser Systems!
- Drives (2), 4 Phase Stepping Motors!
- Bi-Directional 8 Bit Read and Write Port!
- Board Addressable, 16 Possible Choices!
- Fits in Standard 19" inch Card Rack!
- With Additional Cards Control 32 Motors on 1 LPT Printer Port!
- Features Include: Variable Speed, Step, Range, Direction, and On/Off Control!
- Free QBasic & Gwbasic Source Code \$ 59.95 value! *

Send Check or M.O. to:

CYBERMATION
 "Intelligent Controllers"

Call Us Today!
 Tel (714) 879-2000
 Visa/Master Charge Accepted

1943 Sunny Crest Dr., Suite 288,
 Fullerton, CA 92635

* Add \$12.00 S&H; CA residents please add sales tax *

Advanced Circuit Designs will...

PALS
 Test all functions and write code to perform the same task.

GALS
 Extract out the exact same fuse map, depending on the manufacturer and type.

Microprocessors
 Extract out the exact same code for PIC, 16C54, 16C55, 16C56, 16C57, and 16C84.
 Extract out the exact same code for Motorola 68705 series
 (U3, U5, R3, R5, P3, P5), 80993, and 68HC705C8.
 ACD also works with Intel, AMD, and other microcontrollers not listed.

Schematics
 Design/layout schematics, and generate printed circuit board gerber files for projects.

Call about our secure integrated circuit readers!
 ACD can also provide additional resources for populating your circuit boards.
 ACD works with copywritten secured devices only when the copyright holder is the customer.
 Disclaimer: ACD also works with secured devices that have not been copywritten.

Call TODAY for a price quote!
(703) 764-5361
 please leave a message

ACD
 Advanced Circuit Designs, Inc

1765-F Burke Centre Parkway, Suite 317, Burke, Virginia 22015 (703) 764-5361

CLASSIFIED

CABLE TV

ATTN. cable box owners. Order your ID signal and bullet stopper before it's too late. Send \$23.00 to R.R. ENTERPRISE, Box 3532, Easton, PA 18043.

SECRET Cable Descramblers Build your own descrambler for **Less than \$12.00 in seven easy steps!** Radio Shack parts list and Free descrambling methods that **cost nothing** to try, included. Send \$10.00 to: **INFORMATION FACTORY, PO Box 669, Seabrook, TX 77586.** For VISA/MC, CODs, (713) 922-3512 Anytime!

DESCRAMBLE Cable with simple circuit added to Radio Shack RF modulator and using VCR as tuner. Instructions \$10.00. **TELECOM, Box 832 E5, Brusly, LA 70719.**

CABLE Descrambling New secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics for SSAVI, Gated Sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2 postage. **CABLETRONICS, Box 30502R, Bethesda, MD 20824.**

CABLE TV Equipment & Accessories Wholesalers welcome! 30 day moneyback guarantee! Free catalog! **PERFORMANCE ELECTRONICS INC., 1 (800) 815-1512.**

CABLE descrambler! Build with 7 Radio Shack parts costing \$12. Instructions \$8. F.A.S.T., Box 369-E5, Ft. Salerno, FL 34992-0369.

CABLE TV Test Chips for Jerrold, Tocom, Pioneer, Scientific Atlanta, etc... **Quick Installation!** New Multi-Mode modules available. Prices from \$5.00 each. **1 (800) 786-9025.**

CABLE-safe. Guarantee cable privacy. The one-way valve for your cable TV signal. Cable signals come in, but they don't go out! \$29.95 + \$3.00 S&H. VISA MC AMEX. **ELECTROMAN, Box 24474, New Orleans, LA 70184. (504) 482-3017.**

"DESCRAMBLER Schematics Revealed" A powerful guide to descrambling schemes. \$10.00. VISA MC AMEX. **ELECTROMAN, Box 24474, New Orleans, LA 70184. (504) 482-3017.**

REVOLUTIONARY New Technology. Does all cable boxes. For free catalog call **MEGA 1 (800) 676-6342.**

UNIVERSAL Descrambler. Unscramble signals using your VCR as the tuner. Works with virtually any system, this is the only one you need. Declare cable box independence! Fully assembled. \$129.95 + \$5.00 S&H. VISA MC AMEX. **ELECTROMAN, Box 24474, New Orleans, LA 70184. (504) 482-3017.**

"BULLET Buster". Protect your cable box against the infamous cable "bullet". The "Bullet" Buster acts as an electronic shield. Installs in-line in seconds. Don't wait until it's too late! \$19.95 + \$3.00 S&H. VISA MC AMEX. **ELECTROMAN, Box 24474, New Orleans, LA 70184. (504) 482-3017.**

CABLE Unscrambled. Everything you want to know about cable, but are afraid to ask. \$10.00. VISA MC AMEX. **ELECTROMAN, Box 24474, New Orleans, LA 70184. (504) 482-3017.**

TOP Secret! Never released before. Cable companies, cellular phone companies, want to get you now! Learn how they do that! Protect yourself. Piracy, the laws. Better safe than sorry. \$53.95. **RANDALL, Box 2168 R, Van Nuys, CA 91404.**

CABLE Descrambler! Anyone can build in **seven steps** with **Radio Shack** parts. Plans \$5.00. **1 (800) 818-9103.**

TEST aids. Jerrold, Pioneer & S.A. quick boards \$15.00. S.A. micros \$20.00. E2 clearer test aid (6300-6750) \$15.00. Zenith & Tocom \$12.00. **External activators** Jerrold \$85.00. PIO & S.A. \$110.00. **Filters** \$20.00. **Audio boards** \$20.00. **Remotes** \$10.00. **Security bits** \$10.00. (718) 241-2560. 8AM-1PM EST. No N.Y. sales!

ZENITH test chips — activates full test mode. \$24.95. Technical support with order. **SUN-COAST MARKETING, 1 (800) 850-6566.**

CABLE filter, build your own— plans, parts, PC board, case. \$11.00. **VIDEO MEDIA, Box 97-0408, Coconut Creek, FL 33097. 1 (954) 752-9202.**

CABLE TV notch filters. Tunable from 50 to 300 Mhz (channels 0 thru 36). Eight different models available so specify frequency or channel number when ordering. \$30.00 each. Large quantity discounts. Call 1 (800) 433-6319 to receive our brochure or place an order. **STAR CIRCUITS, PO Box 94917, Las Vegas, NV 89193.**

SATELLITE EQUIPMENT

FREE catalog — Lowest prices worldwide. **SKY-VISION, 1012 Frontier, Fergus Falls, MN 56537. 1 (800) 334-6455.** See full page ad The Shopper Section.

VIDEOCYpher II descrambling manual. Schematics, video and audio. Explains DES, EPROM, CloneMaster, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95. \$2.00 postage. Schematics for Videocypher II Plus, \$20.00. Schematics for Videocypher II 032, \$15.00. Software to copy and alter EPROM codes, \$25.00. VCII Plus EPROM, binary and source code, \$30.00. **CABLETRONICS, Box 30502R, Bethesda, MD 20824.**

DSS card fix only \$249.00. Works with all makes and models. Turns on all channels including PPV. Send \$249.00 to **REQUEST, 5201 Kingston Pike, Suite 6-106, Knoxville, TN 37919.** Limited quantities available.

EDUCATION & INSTRUCTION

ELECTRONIC engineering. 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS, 1203 Grant Avenue, Rockford, IL 61103.**

LEARN VCR repair. Great profits. Home study. P.C.D.I., Atlanta, GA. Free literature. **1 (800) 362-7070 Dept. VRF342.**

LEARN PC repair-troubleshooting, servicing. Home study. Free literature. P.C.D.I., Atlanta, GA. **1 (800) 362-7070. Dept. JJF342.**

BECOME a professional locksmith. Home study. Free career literature. P.C.D.I., Atlanta, GA. **1 (800) 362-7070. Dept. LKF342.**

ESP, Bioelectricity, microwave hearing, comprehensive booklist... \$1.00; \$2.00 foreign. **RESEARCH ASSOCIATES, PO Box 3583, Boynton Beach, FL 33424-3583.**

LEARN PC assembly language. Disk \$5.00. Book \$18.00. **ZIPFAST, Box 12238, Lexington, KY 40581-2238.**

HUBBLE Telescope Photographs (GIFS)— Entire public Hubble Series available. **SPACEPICS, PO Box 75711, Oklahoma City, OK 73147.**

COMPUTER SOFTWARE

HUBBLE Telescope photographs (GIFS)— **Galaxies in the Young Universe** Series, \$9.99 + \$2.00 shipping. Entire public Hubble Series available. **SPACEPICS, PO Box 75711, Oklahoma City, OK 73147.**

WANTED

INVENTIONS, ideas, new products! Presentation to industry/exhibition at national innovation exposition. Patent services. **1 (800) 288-IDEA.**

MISCELLANEOUS ELECTRONICS FOR SALE

TUBES: "oldest", "latest". Parts and schematics. SASE for lists. **STEINMETZ, 7519 Maplewood Ave., EN 46324, Hammond, IN 46324.**

FIBER-Optic Projects — Swing into the new technology by assembling tried and true projects recently published. "Practical Fiber-Optic Projects" - BP374 is only \$9.95. (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC., PO Box 240, Massapequa Park, NY 11762-0240.**

GREEN Thumb Alert— Electronics enters the Garden! New exciting book points out how gardeners can build simple gadgets to promote success where the elements work against you. Some of the projects are: over/under temperature monitoring, dusk/dawn switching, automatic plant watering, warming cables, etc. "Electronic Projects for the Garden" only \$9.95 (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC., PO Box 240 Massapequa Park, NY 11762-0240.**

CB Radio modifications! Frequencies, 10M, sliders, FM, amplifiers, books, kits, repairs, high-performance accessories. The best since 1976! Catalog \$3.00. **CBCI, Box 31500EN, Phoenix, AZ 85046.**

CBers Order new CB Trick III CB book. Shows CB tune ups, amplifiers, and expert CB info! Send \$19.95 to **MEDICINE MAN CB, PO Box 37, Clarksville, AR 72830.**

BUILD Electronic surveillance devices! Secrets revealed! Download Phone Bug Plan from BBS! Free information! **TECHNOTES, Box 388-EN, Tehachapi, CA 93581-0388. BBS/Fax (805) 823-1549.**

RESISTORS 20 for \$1.00. LEDs 4 for \$1.00. Catalog \$1.00. **ZIPFAST, Box 12238, Lexington, KY 40581-2238.**

STEPPER Drives. Original cost \$600.00 now \$29.95. New in box. **TRC IND., Nevada, MO. (417) 667-4477.**

POOR reception on your A.M. radio? Our Signal Booster will help. Guaranteed! Send \$2.00 for details (refundable with order). **FALA ELECTRONICS, PO Box 1376, Dept. 4, Milwaukee, WI 53201.**

SEAGATE. 540 MB SCSI hard drive. Model # ST5660N with built in remote start sensor. \$200.00. Chicago, IL (312) 585-3726. Ask for John.

BUSINESS OPPORTUNITIES

EASY work! Excellent pay! Assemble products at home. Call toll free **1 (800) 467-5566** Ext. 5192.

FREE Invention Package: DAVISON & ASSOCIATES offers customized development, patenting, and licensing of new products and ideas. Proven results: **1 (800) 677-6382.**

MAKE \$75,000.00 to \$250,000.00 yearly repairing all kinds of IBM monitors. Successful home based business, anywhere. Telephone required. Details: USA \$3.00 cash (no checks). Dealerships: Canada-all foreign countries: \$85.00 for application brochure. **RANDALL DISPLAY, Box 2168 R, Van Nuys, CA 91404.**

Plant Trees for America™
To receive 10 free Colorado blue spruces, send a \$10 membership contribution to:

 **The National Arbor Day Foundation**
100 Arbor Avenue, Nebraska City, NE 68410

SECURITY

SURVEILLANCE Privacy security protection. Catalog \$5.00. **SPY EMPORIUM**, 6065 Hillcroft, Suite 413, Houston, TX 77081. (713) 774-1000.

PERSONAL protection products, investigator kits, telephone security, debugging equipment, listening devices, covert cameras, manufactured in Canada. Catalog \$5.00. **PERSONAL PROTECTION PLUS**, 237 Dagenais Boul. E., Vimont, PQ H7M 5V9, Canada.

TEST EQUIPMENT

TEST Equipment pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 US for catalog. Refunded on first order. **J.B. Electronics**, 3446 Dempster, Skokie, IL 60076. (847) 982-1973.

TECHNICIANS: Electronic component tester for use with oscilloscope. Satisfaction guaranteed. \$29.95 plus S&H. Info: **ELECTROHM**, 529 Brentwood, Lawrence, KS 66049.

QUALITY used test equipment for sale. Call, fax or write for list. **RIDGE EQUIPMENT**, PO Box 84, Mt. Airy, MD 21771. (301) 831-7671.

PLANS-KITS-SCHEMATICS

CRYSTAL set Handbook — Visit antiquity by building the radios your grandfather built. Assemble a "Quaker Oats" rig, wind coils that work and make it look like the 1920s! Only \$10.95 plus \$4.00 for shipping and handling. **CLAGGK INC.**, PO Box 4099, Farmingdale, NY 11735. US funds only! USA and Canada — no foreign orders.

ALL-in-one catalog. **AM/FM/ham/spy**, transmitters, amplifiers, receivers. Voice scramblers/disguisers, audio, TV, Tesla coils, plans, "secret" books, kits, imports, exports and more. Start your own licensed or unlicensed radio station, 60 full pages for \$1.00. **PAN-COM INTERNATIONAL**, PO Box 130-F05 Paradise, CA 95967.

UNIVERSAL remote control systems infrared, RF, miniature transmitters, receivers. Items for novice, technician or educator. Combine your home and vehicle control. Automate anything. **FREE** catalog. **INVENTIVE SOLUTIONS**, PO Box 8, Stratford, NY 13470.

FASCINATING electronic devices! Tazer! Dazer! Super Spy Microphone! Vocal truth detector! Universal IC tester! Radar and laser jammers! Surveillance! Countermeasures! Ultrasonic! Tesla! High voltage! More! Plans and kits catalog \$2.00. **QUANTUM RESEARCH**, 17919-77th Avenue, Edmonton, Alberta, T5T 2S1.

FREE Catalog. 100 Leading-Edge kits. K1, PIC. Full instructions, source code. 1 (800) 875-3214. **SCIENCE FIRST**, 95 Botsford Place, Buffalo, NY 14216.

CABLE TV TURN-ON CHIPS

SUPER Cable TV "Test Chips". Provides full service activation. Excellent! Instructions & illustrations. **Jerrold Starcom**: DP(V)5, DP(V)7, DPBB7, CFT-2000 Series. **Pioneer**: BA-5000 thru BA-6700 **Scientific Atlanta**: 8500 thru 8600. **Tocom**: 5503-VIP, 5507. **Zenith**: ST-1000 thru ST-5000. Call Now!! **MASTER COMPONENTS**. 1 (800) 233-0570.

Trees Make a World of Difference™

Find out how trees can make a world of difference for you, and your neighborhood. For your free brochure write: Trees For America, The National Arbor Day Foundation, Nebraska City, NE 68410.

 **The National Arbor Day Foundation**

There's a life
to be saved right now.

Please give blood.

Call 1-800 GIVE LIFE



American Red Cross

Cable Aids Test


Orders Only 1-800-615-9221 Information 407-998-7883

Test Chips that fully activate Jerrold, Tocom, Zenith, SA, Pioneer and more. Quick-Board installation! Prices from \$5 to \$49.95 ea. **MC SPECIALTIES** 1 Year Warranty! No FL Sales. Not for use in cable co. owned equip. For test or repair only.

CABLE TV CONVERTERS

Equipment & Accessories
Wholesalers Welcome

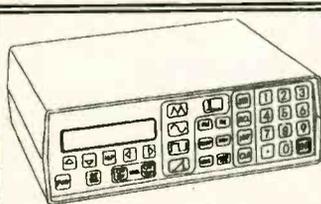Call VISION TIME PRODUCTS
1-800-310-1153 M-F 8a-8p
NO TENN SALES



Model 1010 Synthesized
Sweep/Function Generator \$395

- DC to 12 MHz** (opt. 2) - .005 Hz min. step size
- AM and FM modulation** using internal synthesized modulation source
- Log or linear frequency sweeping** with calibrated markers
- CW Pulses** from 25 ns to 100 sec. User can specify independent repetition frequency
- Sine or square Burst** mode (1 to 65535 pulses per burst) - Internal synthesized burst rate generator
- Triangle & Sawtooth CW** or triggered
- Options available:** ±2 ppm accuracy, RS-232 interface with Windows/DOS software, Labview VI coming soon, OEM boards available
- Applications:** Hobbyist, Technician, Engineer, Education, Circuit design lab, Electronics or Biomedical research

PWI/MobileFax

2533 North Carson St. Suite 1956
Carson City, NV 89706

(800) 910-4099 FAX (805) 379-9447



CABLE T.V.

DESCRAMBLERS


Lowest prices, guaranteed!

CFS Electronics

(formerly C & C Electronics)

(800) 995-1749

VISA, MC, AMEX, C.O.D.

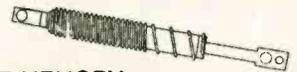

SHAPE-MEMORY LINEAR ACTUATOR

This one inch-pound actuator is made of brass and plastic, and incorporates a helical spring made of the nickel-titanium alloy called Tinel®. This metal enables the actuator to perform a unique set of electromechanical functions. The device provides linear actuation in minimal space, without gears or converters, with nominal one-pound force continuously throughout its stroke. Applications include robotics, doors, valves, toys, shutters, security devices, manipulators and many others. The unit may be operated by temperature or electricity. Spec sheets included.

Nominal Specifications: Operating voltage: 1V, 5A. Electrical resistance: 0.2 Ohms. Pull in cycle: 2 sec. Relax cycle: 8 sec. De-energized length: 100mm. Energized length: 75mm. Diameter: 9mm. Stroke: 20mm. Self-activating temperature: 165°F.

95T001 \$7.95 each

Send \$2.00 for our Latest Catalog!
\$4.00 Foreign. Refundable on First Order.

ALLTRONICS

2300-D Zanker Road • San Jose, CA 95131
Voice (408) 943-9773 • Fax (408) 943-9776

World Wide Web: <http://www.alltronics.com>
On-Line Ordering: (408) 943-0622

14400-N-8-1-24 Hrs.

030596

Robot Explorer Newsletter

Nano-ants, flying robots, Martian explorers. Explore an entire universe of exciting robots. 8 information-packed issues for only \$14.95. Call now! MasterCard/Visa Accepted.

1-(800) GO-ROBOT or 1-(800)467-6268

!!! BROADCAST FARTHER !!!

The model 1525 is a 75-110MHz RF amplifier that connects to mono or stereo FM transmitters and produces a powerful 15-20 watt signal which could broadcast up to 5 miles or more! Requires 75-250 mW drive. Step by step plans complete with part source information and antenna designs... **ONLY \$14 PLUS \$2 S&H** NO C.O.D.'S

Progressive Concepts
BOX 588 STREAMWOOD, IL 60107
(708)736-9822 FAX: (708)736-0353



ADVERTISING INDEX

Electronics Now does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page		
—	A&A Engineering	132	—	IEC	128
212	Ace Communications	98	—	Index Publishing Group	131
—	Active Micro	125	—	Information Unlimited	86
—	Advance Circuit Design	133	126	Interactive Image Tech.	15
213	Alfa Electronics	108	—	Intronics, Inc.	128
214	All Electronics	101	130	Island Logix	24
—	All Phase Video Security	128	318	IVEX Design International	103
—	Allen Engineering	97	—	J&M Microtek, Inc.	128
—	Allison Technology	96	—	Learn Inc.	9
—	Allstar Electronics	127	—	M ² L	133
—	Alltronics	135	304	M.D. EElectronics (Everquest)	129
—	AlphaLab	106	—	M&G Electronics	79
231	AMC Sales	127	223	Mark V Electronics	88
317	American Eagle Publications	112	—	Merrimack Valley	110
—	Andromeda	100	251	Mendelson Electronics Surplus	126
—	ARC Sales	110	—	Mental Automation	124
334	Basic Electrical Supply	116	224	Micro 2000	81
—	Baylin Publications	123	230	Micro Code Eng.	CV4
—	BC Electronics	133	—	Micro Engineering Labs	132
335	Beige Bag	97	—	Midwest Laser Products	123
297	Bel-Merit	84	—	Modern Electronics	126
—	Black Feather	93	—	Mondo-tronics Inc.	132
336	Brigar Electronics	82	—	Motron Electronics	123
—	Bsoft Software, Inc.	100	—	MWK Industries	97
215	Butterworth Heinemann	102	—	National Cable Brokers	130
218	C&S Sales	118	257	Needham Electronics	104
—	Capital Electronics	116	—	NRI Schools	71
—	Cellular Masters	112	—	Oatley Electronics	102
—	CGC	129	262	Parts Express Inc.	105
216	Circuit Specialists	95	—	PC Boards	124
—	Cleveland Inst. of Electronics	37	325	Phillips Tech Electronics	131
—	Command Productions	102	225	Prairie Digital	103
217	Computer Monitor Maint.	131	264	Print (Pace)	99
226	Consumertronics	96	129	Protek	23
310	Conway Engineering Inc.	107	—	PWI/Mobile Fax	135
58	Cook's Institute	13	78	Radio Shack	1
228	Cool Amp Conducto Lube	80	—	RC Distributing Co.	132
319	CTG	100	—	RF Parts	104
—	Cybermation	133	269	Sescom Inc.	110
—	D.A.T.A. Business Publishing	13	—	Show-Time	133
234	Dalbani	89	270	Skyvision Inc.	87
235	Danbar	111	232	Square I Electronics	127
241	Electronic Goldmine	85	227	Sun Equipment	117
—	Electronic Rainbow	122	—	Sycard Technology	106
—	Electronics Tech Today	CV3	—	Tab Books	7, 16
—	Emac Inc.	98	197	Tech Systems	83
—	Fair Radio	125	92	Tektronix, Inc.	5
121	Fluke Corporation	CV2	—	Tektronix, Inc.	11
331	Foley-Belsaw Co.	126	—	Test Equipment Sales	114
219	Fotronic	115	275	Timeline	94
220	Gateway Products	106	229	Toronto Surplus & Scientific	90
—	General Device Instruments	132	—	U.S. Cyberlab	114
—	Get-Tech	103	—	Universal Electronics, Inc.	104
122	Global Specialties	27	321	Visitect Inc.	126
—	Grantham College	10	—	Visual Communications	23
221	Graymark International	127	98	Wavetek Corp.	20
—	H-Q Products	98	—	Weeder Technologies	79
—	Halcyon Group	114	211	Weka Publishing	121
—	Hameg	27	—	World College	55
—	Home Automation	123	—	WPT Publications	123
—	Home Controls	125	281	Xandi Electronics	112
222	Howard Electronics	113			

ADVERTISING SALES OFFICES

Gernsback Publications, Inc.
500 Bi-County Blvd.
Farmingdale, NY 11735-3931
1-(516) 293-3000
Fax 1-(516) 293-3115

Larry Steckler
publisher (ext. 201)

Christina Estrada
assistant to the publisher (ext. 209)

Arline Fishman
advertising director (ext. 206)

Adria Coren
credit manager (ext. 208)

For Advertising ONLY

EAST/SOUTHEAST

Stanley Levitan
Eastern Advertising
1 Overlook Ave.
Great Neck, NY 11021-3750
1-516-487-9357
Fax 1-516-487-8402

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Midwest Advertising
One Northfield Plaza, Suite 300
Northfield, IL 60093-1214
1-847-559-0555
Fax 1-847-559-0562

PACIFIC COAST

Blake Murphy
Pacific Advertising
Hutch Looney & Associates, Inc.
6310 San Vicente Blvd.
Suite 360
Los Angeles, CA 90048-5426
1-213-931-3444 (ext. 224)
Fax 1-213-931-7309

Electronic Shopper

Joe Shere
National Representative
P.O. Box 169
Idyllwild, CA 92549-0169
1-909-659-9743
Fax 1-909-659-2469

Megan Mitchell
National Representative
1201 N. Rainbow Blvd., #50
Las Vegas, NV 89128
1-702-259-7043
Fax 1-702-259-7043

Subscriber Customer Service

1-800-288-0652
7:00 AM - 6:00 PM M-F MST

Electronics Paperback Books


How to Use Op Amps



□ **BP88—How to Use Op Amps...\$5.95.** A designer's guide that covers operational amplifiers. Serving as both a source book of circuits and a reference book for design calculations. The text is non-mathematical and easy to understand by most readers.



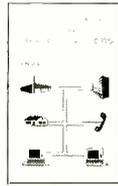□ **BP113—30 Solderless Breadboard Projects-Book 2...\$5.95.** Companion to BP107. Presented in exactly the same style using "Verbloc" breadboards. All the breadboard projects in this book are based on CMOS logic integrated circuits.



□ **BP177—Introduction to Computer Communications...\$5.95.** Details on types of modems and their suitability for specific application, plus details of connecting various computers to modems, and modems to the telephone system.



□ **BP350—Electronic Board Games...\$6.00.** Twenty novel electronic board games that you can build from the plans in this book. Some games are motor racing, searching for buried treasure or for gold in Fort Knox. — there is something for you to build and enjoy!



□ **BP61—Beginners Guide to Digital Techniques...\$5.00.** Covers the basics of digital techniques—decimal, binary, octal and hexadecimal numbering systems are covered plus insights on weighted and non-weighted binary-coded-decimal codes and alphanumeric codes. The basic building blocks of circuit logic, the common AND, OR, NAND, NOR and EXCLUSIVE-OR gates and bi-stables are thoroughly covered.



□ **BP285—A Beginners Guide to Modern Electronic Components...\$6.50.** It is easy for newcomers to electronics to become confused. There are a great many different types of components available often with numerous variations of each type. This book presents the reader with a vast amount of invaluable parts information to enable the right component to be selected every time for repairs and projects.



□ **PCP103—Practical MIDI Handbook...\$9.95.** The Musical Instrument Digital Interface (MIDI) is surrounded by a great deal of misunderstanding. This book is aimed at musicians and technicians who want to explore the vast capabilities of MIDI. It covers MIDI-based equipment you can use: keyboards, drum machines, sequencers, effects units, mixers, drum pads guitars. There's also a section on computer music.




□ **PCP119—Electronic Music and MIDI Projects...\$14.95.** Save cash by building the MIDI gadgets you need. Want a MIDI Thru box, program change pedal, Metronome, analog echo unit? Over 16 practical and very useful music and MIDI projects.



□ **BP121—How to Design and Make Your Own PCBs...\$5.75.** Simple methods for copying printed-circuit board designs from magazines and books on to copper. Covers all aspects of simple PCB construction as comprehensively as possible.



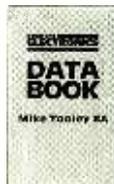□ **BP44—IC 555 Projects...\$5.95.** Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer integrated-circuit chip is one such device. Included are basic and general circuits used by most hobbyists.



□ **PCP109—Everyday Electronics Data Book...\$10.00.** An invaluable source of electronics information—the text contains sections that deal with the underlying theory of electronic circuits and a wide range of practical electronic uses for everyone.




□ **BP301—Antennas for VHF and UHF...\$6.00.** From installing a TV or FM antenna to setting up a multi-antenna array for shortwave listening or amateur radio, this book explains the basics of VHF and UHF antenna operation and installation. The text describes in easy-to-understand terms the essential information about how antennas work, the advantages of different antenna types, and how to get the best performance.



□ **BP297—Loudspeakers for Musicians...\$6.25.** Contains all the information that a working musician needs to know about loudspeakers: the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, available fittings, finishing and how to connect multi-speaker arrays, etc. Includes ten enclosure designs with plans.



□ **PCP110—Electronic Power Supply Handbook...\$10.95.** All types of power supplies used for electronics purposes are covered in detail, starting with cells and batteries and extending by way of rectified supplies and linear stabilizers to modern switch-mode systems, IC switch-mode regulators, DC-converters and inverters. The devices, their operating principles and typical circuits, are dealt with in detail.

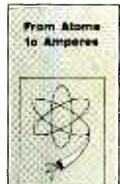

□ **BP254—From Atoms to Amperes...\$6.50.** Explains in crystal-clear terms the fundamentals behind the whole of electricity and electronics. Really helps you to understand the basis of the complex subject perhaps for the first time ever.



□ **PCP101—Practical Digital Electronics Handbook...\$9.95.** An introduction to digital circuits, logic gates, bi-stables, timers, micro-processors, memory and I/O devices. A special feature of the book is the section on digital test gear projects.



□ **BP315—Introduction to the Electromagnetic Wave...\$5.95.** A fundamental and easy-to-understand approach to a complicated theory topic. The beginner requires no more than elementary mathematics and basic knowledge of electronics.



□ **#228—Essential Theory for the Hobbyist...\$5.25.** Supplies to the hobbyist background knowledge tailored to the specific requirements of the hobbyist. Relevant material is presented in a readable manner with minimum mathematics.

TEST EQUIPMENT SPECIALS

- **BP239—Getting the Most from Your Multimeter...\$5.95**
Covers analog and digital gear, component and gear testing.
- **BP267—How to Use Oscilloscopes & Other Testing Equipment...\$6.95**
Get with the next step to proficient troubleshooting.
- **PCP111—Electronic Test Equipment Handbook...\$13.95**
The all-purpose, all-pro handbook that covers basics to in-circuit testing.

SUBSTITUTION GUIDES FOR HOBBYISTS

- **BP85—International Transistor Equivalents Guide...\$7.50**
The ultimate guide to replacing foreign and domestic transistors.
- **BP108—International Diode Equivalents Guide...\$5.95**
Rectifiers, Zeners, LEDs, OCIs, diacs, triacs...all hobby types.
- **BP140—Digital Equivalents and Pin Connectors...\$12.50**
A master reference for builders who design projects.

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. BOX 240, Massapequa, NY 11762-0240

Name _____
Address _____
City _____ State _____ Zip _____
PE6

SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00\$2.00
\$5.01 to \$10.00\$3.00
\$10.01 to 20.00\$4.00
\$20.01 to 30.00\$5.00
\$30.01 to 40.00\$6.00
\$40.01 to 50.00\$7.00
\$50.01 and above\$8.50

SORRY No orders accepted outside of USA & Canada

Total price of merchandise \$ _____
Shipping (see chart) \$ _____
Subtotal \$ _____
Sales Tax (NYS only) \$ _____
Total Enclosed \$ _____

Number of books ordered

All payments must be in U.S. funds!

CircuitMaker[®]

The Virtual Electronics Lab[™]

where you can launch today's electronics project
into tomorrow and beyond...

The screenshot displays the CircuitMaker 3.5 interface with a menu bar (File, Edit, Macros, Options, View, L1, L2) and a toolbar. The main workspace shows a schematic for a rocket launch system. Key components include a 74LS168 counter, a 74LS47 decoder, a 74LS74 flip-flop, a 74LS85 comparator, and a 4321 counter. The circuit is divided into functional blocks: 'Launch' (input buttons), 'Warning Count' (74LS74 and 4321), 'Count down to launch' (74LS168 and 74LS47), and 'Alarm' (74LS85 and a speaker). A TraxMaker menu is open on the left, listing various editing and simulation functions. The status bar at the bottom shows coordinates and layer information.

TraxMaker[™]

- DOS version only \$299
- 30 day satisfaction guarantee
- user definable "Design Rules"
- imports CircuitMaker PCB netlist
- automatic or manual routing of tracks
- 8 layer, 32" x 32" maximum board size
- automatic or manual component placement

New Product

CircuitMaker[®]

- still only \$299
- PCB netlist export
- includes 1500+ devices
- SPICE netlist import/export
- 30 day satisfaction guarantee
- professional schematic features
- digital, analog and mixed-mode simulation

New Window 95/NT/3.1x Versions

Call now to order your complete circuit design system
or request additional information:

800-419-4242

MicroCode Engineering
573 W. 1830 N. Suite 4
Orem, UT 84057 USA
Phone (801) 226-4470
FAX (801) 226-6532



CIRCLE 128 ON FREE INFORMATION CARD

FREE ON-LINE DEMO
AOL: file search, CircuitMaker
CompuServe: GO MICROCODE
Internet: <http://www.microcode.com>
All trademarks are the property of their owners