

NOVEMBER 1996

Electronics NOW

Build a PC Board Assembly System

Our semi-automated system makes project building easier than ever


Keep your telephone conversations interruption-free with the **Phone Line Sentinel**

Build a **Milliohm Adapter**

Measure even the tiniest resistances accurately

**Get picture-perfect
results with the**

Zonal Enlarging Meter

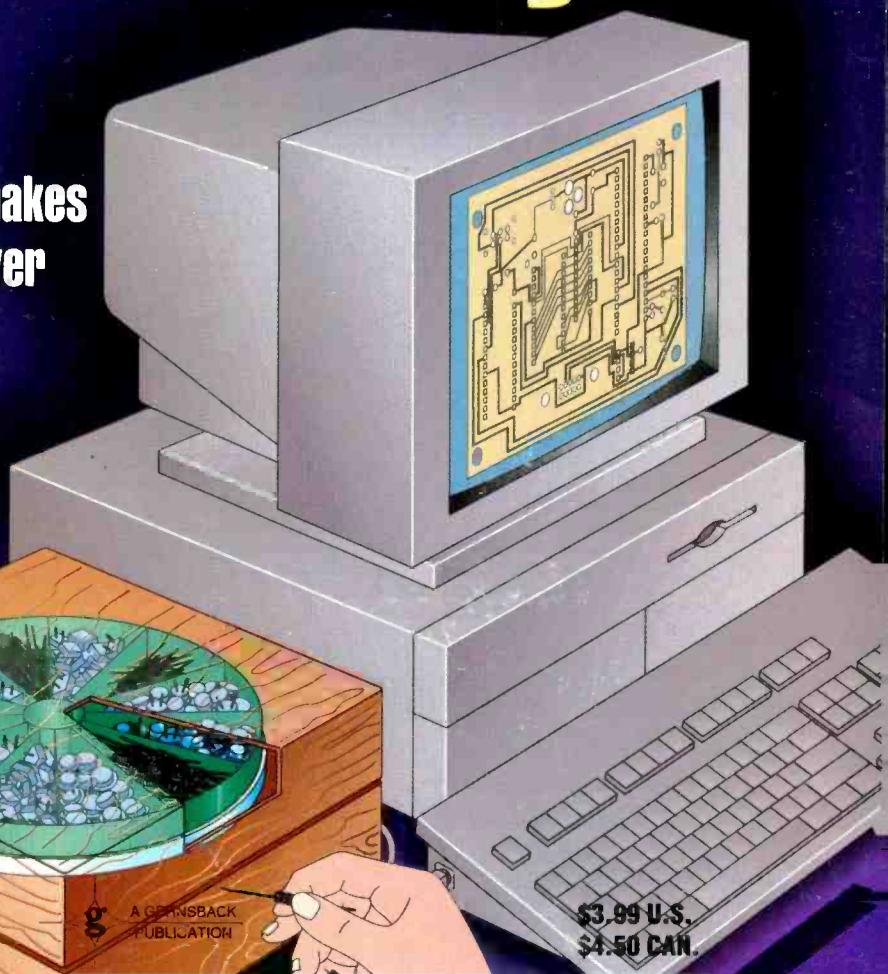

**\$3.99 U.S.
\$4.50 CAN.**

#BXNBQWF***** 5-DIGIT 95066
#BRK6041S090 6#303178 OAP39

1000 1000 1000 1000 1000 1000 1000 1000 1000 1000

11/16/2023

CHRIS BURKE

1 1 ∈ ℙ

Rugged.

Reliable.

100 MHz scope.

But one new


feature really

stands out.



(Here's a hint.)

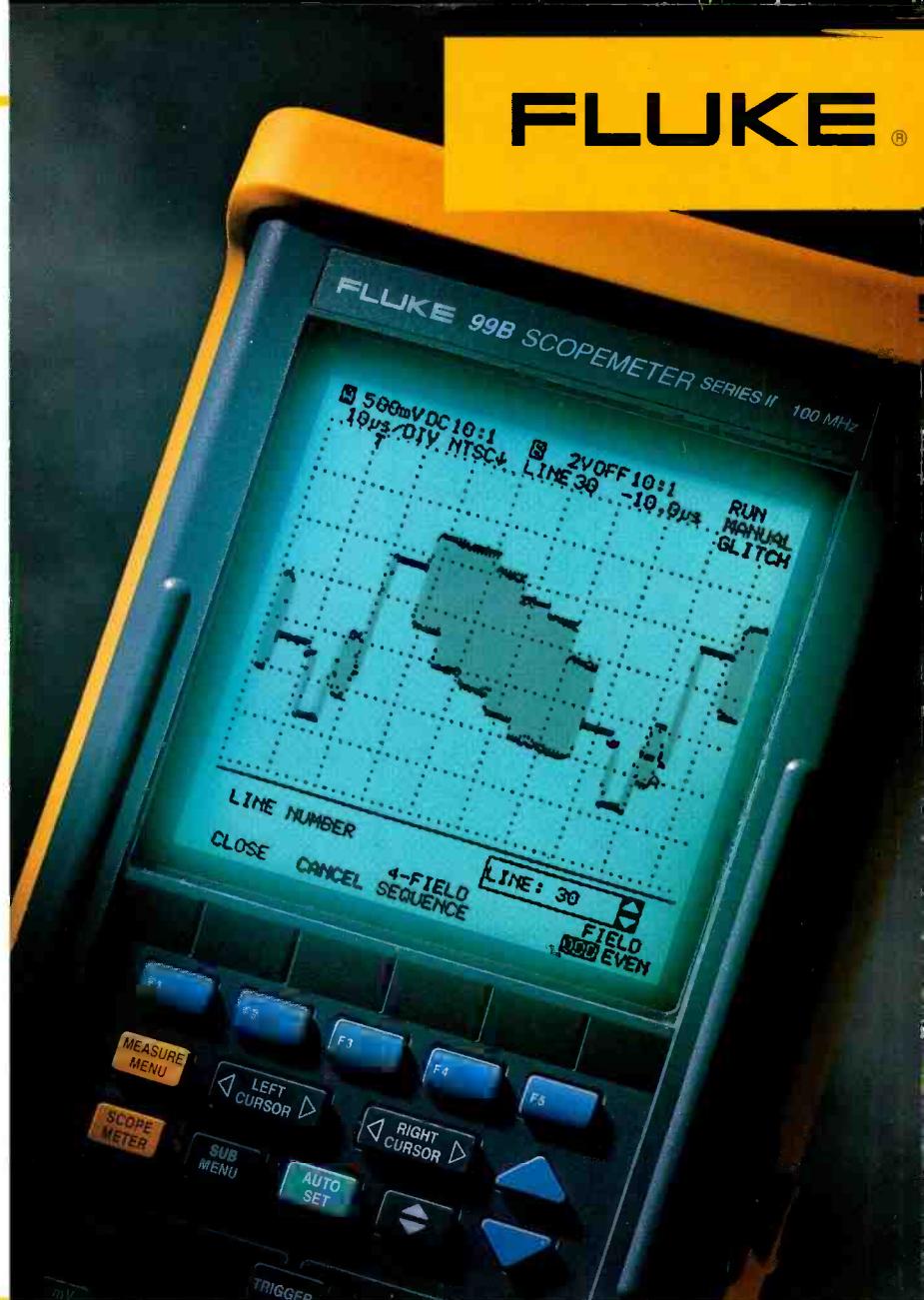**The new ScopeMeter® 99B
test tool, now with a
10X brighter screen.**



Daylight or darkness. Indoors or out. No matter where you're troubleshooting, it's easier with our new ScopeMeter 99B. It's the same rugged, dependable, hand-held scope you know, only it's much easier to read — thanks to a new cold cathode fluorescent screen that's literally 10 times brighter.

It's also much more accurate, with its 100 MHz bandwidth and

5 Gigasamples/second repetitive sampling rate. There's even 30k of deep memory, a new time and date clock feature, plus longer lasting performance with up to 4 hours of battery life.

It's time you saw the light yourself. To get your hands on the powerful new ScopeMeter 99B, call Fluke today at **1-800-44-FLUKE**. Or visit our web site at www.fluke.com.



©1996 Fluke Corporation, P.O. Box 9090, M/S 250E, Everett, WA, USA 98206-9090, U.S. (800) 44-FLUKE or (206) 356-5400. Canada (905) 890-7600. Europe (31) 40 2 678 200. Other Countries (206) 356-5500. All rights reserved. FLU-116-100

CIRCLE 121 ON FREE INFORMATION CARD

www.americanradiohistory.com

Take this GIANT CIRCUIT LIBRARY FOR ONLY \$14⁹⁵

when you join the
Electronics Engineers' Book Club[®]

Hundreds of circuit ideas
alphabetically arranged—from
Alarm circuits to Zero
crossing detector circuits!


"...includes schematics for the latest electronics circuits from industry leaders..."

—Popular Electronics

Turn to this comprehensive circuit library for hundreds of project ideas...and concise pinout diagrams and schematics. In each volume you'll find more than 700 electronic and integrated circuits and 100+ circuit categories right at your fingertips to give you ideas you can use on the job or at your workbench.

THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS

Volumes 1-4
by Rudolf F. Graf

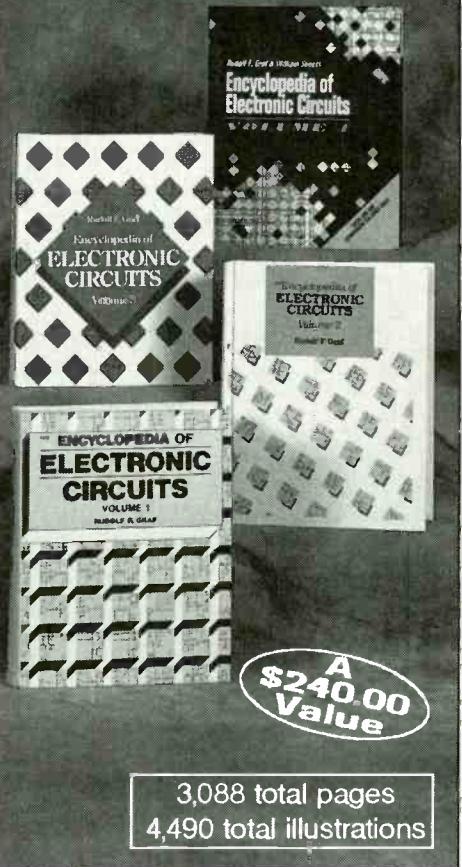

A
**\$240.00
Value**

3,088 total pages
4,490 total illustrations

If coupon is missing, write to: Electronics Engineers' Book Club,
A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

As a member of the Electronics Engineers' Book Club...you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. And you'll be eligible for FREE BOOKS through the Bonus Book Plan. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time. Publishers' price shown. ©1996 EEBC

ELECTRONICS ENGINEERS' BOOK CLUB[®]

A Division of The McGraw-Hill Companies,
P.O. Box 549, Blacklick, OH 43004-9918

YES! Please send me *The Encyclopedia of Electronic Circuits—Vols. 1-4* (5861488), billing me just \$14.95 plus shipping/handling & sales tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days for a full refund and have my membership cancelled.

Name _____

Address/Apt. # _____

City _____

State _____

Zip _____ Phone _____

Valid for new members only, subject to acceptance by EEBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders.
RPIF1196

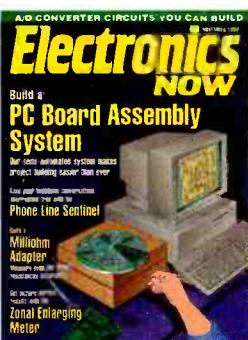
CONTENTS

NOVEMBER 1996

ON THE COVER**33 BUILD THIS AUTOMATIC PARTS TRAY**

The trend these days in industry is toward more and more automation. For example, in electronics, robotics is used to pick and place surface-mount components on printed-circuit boards with unerring accuracy. While such a level of automation is beyond the reach of almost any hobbyist, it is possible to bring some of its benefits to nearly any workbench. This month, we present the first part of a system that will, under computer control, greatly simplify the task of assembling PC boards. It is an automatic parts tray that brings to hand the next part to be mounted on the board. Coupled with a computer display that shows the location of that part on the board, project building may never be easier. Best of all, it is inexpensive to build and use.

— James J. Barbarello

**BUILD THIS****40 MILLIOHM ADAPTER**

Use it to accurately measure even the smallest resistance.
— Skip Campisi

43 ZONAL ENLARGING METER

It is easier to use and gives better results than standard darkroom equipment.

— Michael A. Covington

50 HOBBY SPECTRUM ANALYZER

We put the finishing touches on this under-\$100 unit.

— Bob Kopski

53 PHONE LINE SENTINEL

Put an end to phone-call interruptions.

— Mordechai Saad

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 1067-9294) November 1996. Published monthly by Gernsback Publications, Inc., 500 Bi-County Boulevard, Farmingdale, NY 11735-3931. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Canada Post IPM Agreement No. 334103, authorized at Mississauga, Canada. One-year subscription rate U.S.A. and possessions \$19.97, Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax, Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$3.50. © 1996 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.


A stamped self-address envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

TECHNOLOGY

55 USING THE 7107

The versatile 7107 A/D converter and display driver is a virtual voltmeter on a chip, but it can be used to do much more than just measure voltage, as you will see in this compendium of circuits that you can build and use.

— Carl J. Bergquist

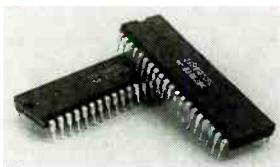


DEPARTMENTS

8 VIDEO NEWS

What's new in this fast-changing industry. — David Lachenbruch

**18 EQUIPMENT REPORTS**

DynaPulse PC-based blood-pressure monitor.

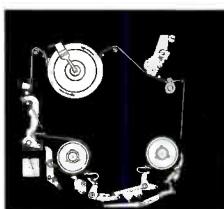
**61 TECH MUSINGS**

Understanding digital filters, using your time profitably, and more

— Don Lancaster

68 SERVICING

Troubleshooting VCR tape-path alignment. — Robert Epperson

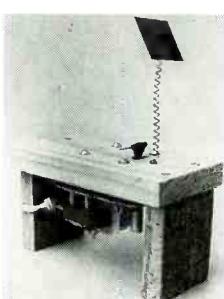**70 LASER EXPERIMENTS**

Generating laser-light patterns. — Carl J. Bergquist

74 AUDIO UPDATE

Microphone basics. — Larry Klein

77 COMPUTER CONNECTIONS

IP addressing and HTML coding. — Jeff Holtzman

AND MORE

4 EDITORIAL**22 NEW PRODUCTS****8 WHAT'S NEWS****25 NEW LITERATURE****11 LETTERS****136 ADVERTISING INDEX****14 Q&A****136 ADVERTISING SALES OFFICE**

Electronics NOW®

Hugo Gernsback (1884-1967) founder

LARRY STECKLER, EHF, CET,
Editor-in-chief and publisher

EDITORIAL DEPARTMENT

CARL LARON, editor
JOSEPH J. SUDA, associate technical editor

JULIAN S. MARTIN, associate editor
TERI SCADUTO, assistant editor

MICHAEL A. COVINGTON, N4TMI
contributing editor

JEFFREY K. HOLTZMAN,
computer editor

LARRY KLEIN, audio editor

DAVID LACHENBRUCH,
contributing editor

DON LANCASTER,
contributing editor

EVELYN ROSE, editorial assistant

ART DEPARTMENT

ANDRE DUZANT, art director
RUSSELL C. TRUELSON, illustrator

PRODUCTION DEPARTMENT

RUBY M. YEE, production director
KATHRYN R. CAMPBELL,
production assistant

KEN COREN,
desktop production director
LISA BAYNON, desktop production

CIRCULATION DEPARTMENT

JACQUELINE P. CHEESEBORO,
circulation director
TERESA LOMBARDO,
circulation assistant

REPRINT DEPARTMENT

MICHELE TORRILLO,
reprint bookstore

Typography by Mates Graphics
Cover design by David Loewy

Electronics Now is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*.

Microfilm & Microfiche editions are available. Contact reprint bookstore for details.

Advertising Sales Offices listed on page 136.

Electronics Now Executive and Administrative Offices
1-516-293-3000.

Customer Service:
1-800-999-7139.
7:00 AM - 6:00 PM M-F MST



Audit Bureau
of Circulations
Member

Buy One Get One

50%
off!

Explore the Caribbean
on a 6 or 13 day
sailing adventure.

Call your travel agent or
1-800-327-2601
<http://www.windjammer.com>



P.O. Box 190120, Dept. 5569
Miami Beach, FL 33139-0120

June - mid Dec. sailings only. Restrictions apply.

**ATTENTION!
ELECTRONICS
TECHNICIANS**
EARN YOUR
**B.S.E.E.
DEGREE**
THROUGH HOME STUDY

Our Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete the program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through our Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the engineering level. Advance rapidly! Many finish in 12 months or less! Students and graduates in all 50 states and throughout the world! Established Over 50 Years! Write or call for free Descriptive Literature. (601) 371-1351

COOK'S INSTITUTE
OF ELECTRONICS ENGINEERING

CIE 4251 CYPRESS DRIVE
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD

EDITORIAL

Introducing www.gernsback.com

In my first editorial (September 1996), I mentioned that we were making our long awaited move onto the Internet. Well, that move is now largely complete and everyone here is extremely excited about it.

Our Web site, www.gernsback.com, hosts the home pages of both **Electronics Now** and our sister magazine, **Popular Electronics**. But there is also much more. By the time you read this, our FTP site will be up and running. There you will find all of the current and past story-related files for both titles.

Also in the works is a searchable article index. Need to find out if or when we covered a specific topic? Just go to our site and you'll have your answer with just a few keystrokes. The system is undergoing testing now, and we hope to have it operational by early next year.

Also on the way are discussion forums. If you are looking for somewhere to discuss the pros and cons of a particular project, article, or issue, it's the place to go. You'll also be able to interact with other readers on just about any electronics-related topic.

Our Web site is also where you'll find late-breaking updates for our stories and projects. We, of course, publish significant corrections and updates as soon as we become aware of them. However, due to publishing schedules, it can sometimes take months for them to appear in print. Now, that information will be available to you almost as soon as we have it.

There's also information on our two most current issues, subscription information with online ordering, back-issue ordering, links to our editorial and other staff members, links to our advertisers, and much more. Check it out and let us know what you think. You can contact me at claron@gernsback.com.

Carl Laron
Editor



=



A DAY

If this satellite deal won't get you off the couch, check your pulse.

Been thinking about satellite TV? Come to RadioShack. Now for as little as a dollar a day, you can own an RCA®-brand DSS system with programming. Up to 200 channels on USSB® and DIRECTV®. Or subscribe to PRIMESTAR®, with equipment and programming, also for as little as a buck a day. You can have up to 95 channels with no equipment to buy. If access to tons of movies, pay-per-view, music and sports with digital picture and sound gets your heart racing, come on in. For a store near you, call **1-800-THE SHACK™**.

RCA-brand system and programming sold separately. PRIMESTAR system and programming included in monthly payments. Price and equipment may vary. Installation cost not included. Some restrictions apply. Broadcast networks are only available to customers in those limited areas not served by local affiliates. Blackout and other restrictions may apply.



RadioShack
You've got questions.
We've got answers.®

CIRCLE 78 ON FREE INFORMATION CARD

www.americanradiohistory.com



VIDEO NEWS

WHAT'S NEW IN THE FAST-CHANGING VIDEO INDUSTRY

BY DAVID LACHENBRUCH

HDTV is on the Air

The first station to transmit digital high-definition TV is WRAL-HD, now broadcasting from Raleigh, North Carolina, on UHF Channel 23 under an experimental license from the FCC. That sister station of WRAL-TV mainly has been transmitting numbers for field measurements, but is sending full-bandwidth HDTV at its full authorized power of 100 kHz. The station plans to start transmitting actual video programs in the near future, using tapes provided by PBS and CBS. The station's executives have been talking with receiver manufacturers and are confident that HDTV sets will be in area stores by next spring.

Two more HDTV stations were due shortly at our deadline. The industry's model high-definition station, being financed by the Electronic Industries Association (EIA) and the Maximum Service Television trade association, was scheduled to take to the air soon at NBC's WRC-TV in Washington, D.C. Washington-based WETA, a PBS affiliate, is also building an HDTV counterpart, due on the air this year. The first HDTV receivers are expected to sell for more than \$2000.

Olympics in HDTV

At one time, the U.S. electronics and broadcasting community had planned to use the 1996 Summer Olympics in Atlanta as a showcase for American technology by broadcasting the games in HDTV. American HDTV slipped a cog as it wasn't quite ready. But the Olympics—390 hours of it—went on the air in HDTV anyway. It just wasn't American HDTV.

The Europeans and the Japanese collaborated to record 24 hours of Olympic competition daily in high definition.

Backed by a grant from the European Union, Germany's ZDF network covered the games in 1250-line high definition, while Japan's NHK used its 1125-line equipment.

ZDF's coverage was converted to 1125 lines and sent, along with NHK's coverage, by satellite to Japan, where it was broadcast using Japan's analog Hi-Vision system from satellite to homes. ZDF's coverage, along with the NHK signal, was also converted to a PALplus signal for transmission to Europe, where it was broadcast to virtually all European countries. PALplus is an improved-definition system that permits specially equipped widescreen TVs to show widescreen pictures with full definition, while other sets display the same widescreen image as a letterbox picture. The additional information required to bring the letterbox picture to 625-line quality is encoded digitally in the black area above and below the widescreen picture.

DBS Prices Falling

Prices of direct-to-home satellite equipment are falling rapidly, thanks to competition and subsidies by programmers. While the first digital satellite receivers for the DSS system—introduced under the RCA brand, using an 18-inch antenna—sold for \$600 and up, some prices are now as low as \$199. But there's a catch. The programming for these systems is available by subscription only. Obviously, those who install the equipment have to have programs. So the program providers increasingly are helping to subsidize equipment prices.

The first major move in that direction came from EchoStar, which was in a good position to undertake such a project because it sells both the programming and the hardware. It stunned its

competitors by offering a receiver and antenna for \$199 with the purchase of a year's programming at \$300. The promotion was so effective in test areas that it was offered nationwide last summer.

Not to be outdone, DSS, the biggest selling system, was planning a similar promotion. In it, DirecTV and U.S. Satellite Broadcasting, which supply programming for the DSS system, would give the equipment suppliers—including RCA, Sony, and Panasonic—a subsidy to bring the price down to \$399, and then send buyers a \$200 rebate in addition, effectively reducing the hardware price to \$199. While details have not been finalized at press time, the program should be in effect now, or starting soon, though perhaps in a somewhat different form.

The situation is reminiscent of what happened in the cellular-phone industry, where service providers are subsidizing phone instrument prices. The DBS competition hasn't yet gotten to the point where the receiver is free—but stay tuned.

WebTV Becomes Contagious

There is absolutely no evidence that combining the 1990's fad of Web browsing with the television fad begun in the 1950's is a workable idea, but profit-starved TV manufacturers and Silicon Valley entrepreneurs are joining forces to test the idea in a large-scale way.

Probably the most persuasive force in that direction is WebTV Network, which has signed Sony and Philips (Magnavox) to supply set-top boxes to let consumers surf the Internet on their large-screen TVs from their easy chairs. The box provides on-line access and e-mail service to TV users, and has a slot for smart-card financial transactions.

The box will cost somewhere between \$200 and \$400.

The box is connected to a phone jack and the TV's audio and video terminals. It contains a 33.6-kilobyte-per-second modem and a 64-bit Orion MIPS RISC microprocessor. WebTV features its own Internet guide and simple menus for navigation, along with parental-control software. Wireless and wired keyboards will be available as e-mail accessories, although mail can be authored using an on-screen depiction of a keyboard as well. Sony and Magnavox are expected to have the boxes in stores before year-end.

Other TV manufacturers are using different approaches. As reported here, Zenith is fielding a Net-browsing TV, but prefers the built-in approach to the separate set-top box. RCA's parent, Thomson Consumer Electronics, has been demonstrating prototypes of its "Genius Home Theater," which combines Internet access, e-mail, CD-ROM changer, and other computer features with a high-end 35-inch TV set. Thomson says that it might offer a simplified Web-browsing TV or attachment as well.



RCA'S "GENIUS THEATER" PROTOTYPE is one of a host of new PC/TVs.

Another TV manufacturer, Curtis Mathes, plans to introduce a combination computer and TV set. Computer manufacturer Gateway 2000 is already selling such a combination. Dubbed Destination, it includes a 31-inch TV set and an electronic program guide.

Actually, Toshiba probably foreshadowed the so-called "marriage" of PC and TV in 1994 with its "TIMM" (for Toshiba Integrated Multimedia Monitor), a 20-inch monitor and TV set designed for use both as a TV and a high-quality audio and video monitor for PCs. Unfortunately, it didn't sell particularly well.

Wavetek. The Way Value IS Measured.

leads and are approved to IEC1010-1 safety standards.

Our commitment to reliability and high-quality is backed by the industry's only "No Hassle" warranty program. If your XT Series meter requires warranty service, your local dealer replaces it immediately. Call today for full details and the names of your local Wavetek distributors. You'll find that when it comes to Wavetek performance and price, nothing else measures up.

Wavetek Corporation
9145 Balboa Avenue, San Diego, CA 92123
(800) 854 2708

WAVETEK

Temperature. There is an XT Series DMM right for you. With oversized character displays, these DMMs are as easy to read as they are to use. All have fully-fused current inputs and input warning beepers to protect you and the meter. Each comes with safety test

LCR55

Full-function LCR, extra test features for "best-buy" in a component checker.

- Inductance
- Capacitance
- Resistance
- Transistor
- Dual Diode



85XT

A precision True-RMS reading DMM, ideal for equipment like


- 4 1/2 digit
- 0.05%
- Accuracy
- True-RMS
- Frequency
- Duty Cycle



25XT

A full-C-meter in a DMM, and more! Ideal for HVACR, building or plant maintenance.

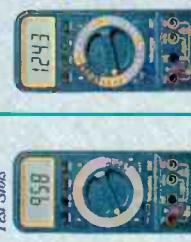- Temperature
- Capacitance
- Frequency
- Max-Hold
- Full Capacitance
- 0.1pf to 20mF
- Capacitance Zerling & Test Slope



23XT

Electronic and electrical test functions for general duty and HVACR.

- VAC Safety Tester™
- Temperature
- Capacitance
- Logic
- Frequency
- Capacitance
- Logic



27XT

A unique combination of DMM and component checking in a single meter.

- Inductance
- Capacitance
- Logic
- Frequency
- Capacitance
- Logic

Accessories include current clamps, RF & HV probes, temperature converters, hoisters, boots and carrying cases.

For the best values in digital multimeters everyone is turning to the Wavetek XT Series. Each of these full-function DMMs measures voltage, current, resistance, and also a set of additional electrical or electronic properties you work with every day. Inductance, Capacitance, Frequency,





WHAT'S NEWS

A REVIEW OF THE LATEST HAPPENINGS IN ELECTRONICS


Measuring Individual Carbon Nanotubes

Researchers at NEC Corporation (Japan) and NEC Research Institute (Princeton, NJ) have succeeded in measuring electrical conductivity in individual carbon nanotubes. Using an evaluation method developed by scientists at NEC and Micron Europe, they discovered that each nanotube has unique electronic properties, including both metallic and non-metallic behavior, and that the differences between nanotubes are far greater than expected. The results confirm that, at this scale, geometry and electronic properties are closely linked.

By attaching four 80-nanometer tungsten leads directly to individual nanotubes, and using a focused ion beam (FIB) system, the NEC scientists were able to achieve a more accurate and informative evaluation of the nanotubes' properties. It was learned that the current carrying capacity of nanotubes is extremely high, the temperature dependence of the conductivity greatly differs between nanotubes, different segments of a single nanotube do not always have the same temperature profile, and nanotubes have significant variation in resistivities.

The interest in carbon nanotubes has been stimulated by theoretical predictions that their electronic properties would be strongly modulated by small structural variations. In particular, the diameter and helicity of carbon atoms in the nanotube shell are believed to determine whether the nanotube is metallic or a semiconductor. Prior to the NEC method of measuring individual nanotubes, however, experimental evidence had been mainly linked to bulk measurements.

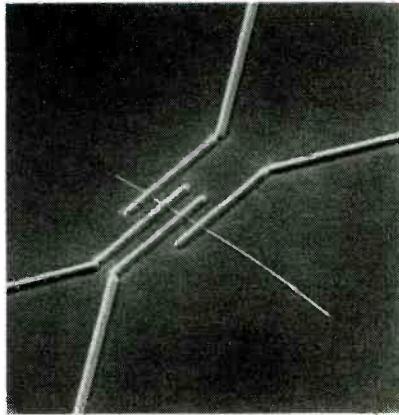"This work opens up for the first time full electrical measurements on carbon nanotubes," said Dr. William Gear, president of NEC Research Institute. "These tubes may be able to function as



NEC RESEARCHERS MEASURE the electrical conductivity of individual carbon nanotubes by attaching four 80-nanometer-wide tungsten leads to each nanotube.

wires with a diameter about one hundredth the line-width used in current 16-megabit memory chips. Early results suggest that nanotubes can be fabricated with a very wide range of electrical properties.

Solar Success Story

Engineers from Sandia National Laboratories (Albuquerque, NM) played a key role in the development of Solar Two, a large pilot solar power plant that is capable of producing 10 megawatts of electricity—enough to supply power to 10,000 homes. The project was sponsored by the Solar Two Consortium, a group of ten organizations led by Southern California Edison Company, and the Department of Energy (DOE). At a June 5 dedication ceremony, presided over by DOE Secretary Hazel O'Leary, Solar Two was officially connected to the utility grid in Southern California.

Solar Two is unique in its use of molten salt to capture and store the sun's heat. The solar plant uses large, sun-tracking mirrors to concentrate sunlight on a receiver that sits atop a tower. The concentrated sunlight heats the molten

salt as it flows through the receiver. The hot liquefied salt is then piped away, stored, and used when needed to produce steam to drive a turbine/generator that produces electricity.

Solar Two's predecessor, Solar One, was a direct-steam solar generator that operated from 1982 to 1986. Solar One generated steam directly from water in its receiver, and was plagued by low energy-storage efficiency and interrupted operation from passing clouds. Solar Two, in contrast, can operate smoothly through intermittent clouds and continue generating electricity long into the night.

Sandia conducted large-scale experiments on the components needed in a molten-salt system at its Central Receiver Test Facility in Albuquerque. "Sandia played a key role in providing assistance by transferring molten-salt technology to the project, by leading the Technical Advisory Committee which oversaw all technical aspects of the project, and by supporting the design, construction, and startup of the plant through the outstanding efforts of its staff," said Gary Burch, director of the DOE's Thermal and Biomass Power Division.

IC Expo/96

Co-sponsored by Wescon, EE Times, Electronic Buyer's News, and OEM Magazine, IC Expo/96 is scheduled to take place as part of Wescon/96 on October 22–26, 1996, at the Anaheim Convention Center in Anaheim, California. The Wescon International Electronics Conference and Exhibition is a major OEM event for electronics, computer, and communications professionals.

The IC Expo/96 show-within-a-show, an extensive semiconductor trade exhibition, will celebrate the 25th anniversary of the microprocessor—and the 45th anniversary of Wescon—with a series of

continued on page 12



LETTERS

SEND YOUR COMMENTS TO THE EDITORS OF ELECTRONICS NOW MAGAZINE

L/C Meter Correction

In my article, "Build This Self-Calibrating L/C Meter" (*Electronics Now*, June 1996), I inadvertently submitted the incorrect schematic diagram. The schematic published was for an experimental unit that used a different display module and thus had different pinouts on the CPU-to-display interface. The PCB layout is correct, so any units built using a printed circuit board should be okay. This proves the saying, "To err is human, to really foul things up use a computer."

A copy of the correct schematic can be obtained by requesting it and sending a self-addressed, stamped envelope to the address below. The correct schematic is also available as lcmsch.gif on the Electronics Now BBS (516-293-2283).

NEIL HECKT

Almost All Digital Electronics
1412 Elm Street SE
Auburn, WA 98092

New Product Correction

Thank you for mentioning HC Protek's D-980 digital Multimeter in the July "New Products" column. Unfortunately, two errors appeared. First, the DC accuracy specification was cited as 5%. The actual specification is 0.5%.

Our Web site URL was also incorrect. The correct URL is <http://www.techexpo.com/WWW/hcprotek>.

ROY TAFFARO

HC Protek Applications Engineer
Northvale, NJ

Non-Stereo Compressor

I would like to share my thoughts about the article, "Build a Stereo Compressor" (*Electronics Now*, August 1996). Although the two-channel compressor project will prove to be a fine addition to someone's audio-processing needs (Analog Devices makes great, innovative ICs), it is not a stereo compressor.

For the unit to operate in the stereo mode, both rectifier log converters from channels one and two would need to be summed into a single control voltage that would then feed directly to the VCAs of both channels in a strapped configuration, thereby preserving correct stereo imaging. By that I mean that any high-level peak appearing in only one channel will cause an equal amount of gain reduction in both channels, keeping the left/right balance correct.

Any two-channel processor, when connected to a stereo signal (*i.e.*, complete mix), would process the left and right channels independently. If a sudden loud signal appeared in only one channel, such as a lead instrument that was panned hard left or right within a total stereo mix, only that channel's VCA would respond, causing the overall level in that channel to decrease. That decrease in level to only one channel will cause image shifting. All mono information (bass drum, bass guitar, etc.) would sound off-center from the original mix.

As a two-channel compressor, I'm sure the unit will be a wonderful addition to an effects rack. As for stereo compressing a final mix, say from CD or DAT to a cassette format—no way!

RON TOZIER

Newton, KS

Laser Article Brought Into Focus

In reading the August installment of "Laser Experiments," I found what I

Write To:
Letters,
Electronics Now Magazine,
500 Bi-County Blvd.,
Farmingdale, NY 11735

Due to the volume of mail we receive, not all letters can be answered personally. All letters are subject to editing for clarity and length.

believe to be several serious errors. First of all, a diffraction grating does not consist of thousands of very small parallel prisms per millimeter, as suggested. In actuality, a diffraction grating consists of many closely spaced parallel lines scored onto an aluminized plastic or polished glass surface. Those lines break up light into its component frequencies by the physical process of diffraction (the interference produced when light encounters an obstacle), as their name implies. Each scratch serves as a source of scattered light. Prisms operate through the entirely different process of refraction—the selective bending of different light wavelengths as they pass from one media (such as air) to another (such as glass). If gratings really operated as microscopic prisms as suggested, then they would have to be called refraction gratings!

Another type of grating consists of many parallel apertures or obstacles that ideally present a pass-block squarewave type pattern to the incident wave front. Yet another type (there are many), called a "blazed" grating, consists of grooves cut onto a glass surface whose serrated edges do resemble an array of prisms but which still operates by diffraction. Consult any standard physics or optics text for more details.

Another statement in the article suggested that the focusing of "light" is somehow more crisp and pronounced than that obtainable by other forms of electromagnetic energy such as "radio or sound." The big error here is that sound is *not* a form of electromagnetic energy. In addition, there is no fundamental difference between radio waves and visible light. They are both EM waves that differ only in their frequency. Radio waves are routinely focused by parabolic antennas and the like.

A further misconception was that placing black tapes around a bent glass rod would act as a shield to keep light from escaping out the sides. In reality,

the process called "Total Internal Reflection" is what keeps light trapped within the rod or optical fiber. To operate, the incident light rays must enter the rod at an angle less than some critical angle determined by the material of the rod or fiber and the surrounding medium. If the incident angle exceeds that value, or if the rod/fiber is bent too sharply, then light can indeed leave through the sides. However, black tape will not redirect the light back into the pipe or cause Total Internal Reflection to occur, as implied.

Several times in the article, the author mentioned that lasers are coherent and monochromatic, but still contain all the other colors in the visible spectrum (albeit in small quantities). Thus, the article continued, colored light can be produced by passing laser light through a prism or a frosted plastic sheet. While it is true that no laser is perfectly monochromatic (the frequency spectrum is predominantly distributed over a band known as the line width), its bandwidth is extraordinarily narrow. For a common He-Ne laser, the line width is roughly 1500 MHz, which might seem large compared to radio frequencies but is less than 1/1000 of

one percent of the visible light spectrum. Technically, all frequencies in that narrow band are of different "colors." But to suggest that a full-color spectrum can be obtained through refraction of laser light is nonsense. Lasers are called monochromatic or quasi-monochromatic for good reason. Any colors thus perceived are due to interactions with ambient sunlight or non-monochromatic room illumination.

The use of the word "sub-reflection" to describe the speckling effect produced by shining laser light off a diffuse surface is non-informative. The speckles are caused by a stationary interference pattern set up in the space in front of the surface. Due to the long coherence length of the laser light, individual reflections from the rough surface combine together coherently at each point in space with a random but stationary (non-changing) phase to create the speckles. When viewed in sunlight, the speckles might take on various colors.

While lenses are extremely important in optical science, the rules that govern the focusing of laser light (Gaussian beams) are not quite the same as those for non-coherent light. This

difference had disastrous consequences for some early designers of optical systems using lasers, who used the standard rules of geometrical optics and couldn't figure out why their systems failed to work! The interested reader can find a wealth of information on these topics in the many available books on lasers, optics, laser electronics, holography, and other related fields.

JAY RABKIN
Pasadena, CA

Audio System Integration Update

In "Audio Update" (*Electronics Now*, August 1996), Franklin Miller stated that it is optimum to match microphone impedance to the input impedance of the mixer. That is wrong. If the impedances are matched, the level will drop 6 dB and the signal-to-noise ratio will drop 3 dB. For condenser microphones with a built-in amplifier, there will be a bass roll-off and added distortion.

Instead, the input impedance should be at least ten times the source impedance. That mismatch is called a "bridging load."

DAVID HADAWAY
Ridge, NH

EN

WHAT'S NEWS

continued from page 8

industry events. Hundreds of exhibits will display many of today's most advanced microelectronics products and technologies by leading semiconductor manufacturers. Industry and editorial advisers have structured the event to meet the needs of technology professionals from the communications, computer, and high-end VLSI components industries, who need to know the latest in microprocessors, microcontrollers, memories, ASICs, and communications ICs.

The Applications Conference on Communications and Computer Technologies will provide extensive solutions-oriented presentations in a series of several one- and two-hour sessions. New and emerging technologies will be featured in multiple sessions throughout the conference.

Information about Wescon/96 and IC Expo/96 is available by phone (800-877-2668), fax (310-641-5117), e-mail (m.potthoff@ieee.org), and Web site 12 (<http://www.wescon.com>).

Scholarship Donation

The Consumer Electronics Manufacturers Association (CEMA) announced that DeVry Institute has contributed \$60,000 in scholarships to the winners of the Electronics Products Servicing Competition, held June 27 at the 1996 Skills Championships in Kansas City, Missouri.

Throughout the year, students compete in local, regional, and state competitions sponsored by the Vocational Industrial Clubs of America (VICA). The competitions culminate in VICA's annual Skills USA Championships, which pit state title winners against each other. CEMA sponsors the electronic skills portion of the championships.

DeVry awarded scholarships to both the secondary and post-secondary winners of the electronics competition. Both scholarships, valued up to \$30,000, will cover full tuition to any of the DeVry Institutes in the United States. As a private, degree-granting higher-education system, DeVry, with 13 campuses throughout the United States and Canada, offers

bachelor's degree programs in electronics-engineering technology, computer-information systems, business operations, accounting, and telecommunications management, as well as an associate's degree program for electronics technicians.

"Consumer electronics manufacturers rely heavily on qualified technologists and technicians for the installation, servicing, and maintenance of their products," said Don Hatten, vice president, CEMA Product Services. "The generous DeVry scholarships will provide our two winners with a valuable education and an opportunity for promising careers once they graduate."

CEMA, through its Product Services Department, supports vocational education programs that offer training for those entering the servicing profession. CEMA also provides in-depth preparatory training for students seeking engineering degrees.

Information on CEMA is available via EIA/CEMA's World Wide Web Site at <http://www.eia.org/cema>. Information on DeVry programs can be accessed at <http://www.devry.com>.

EN

SEC Sun Equipment Corporation **LODESTAR Lodesstar Electronics Corp. Since 1979**
 One Year Warranty. 15 Day Money Back Guarantee. OEM welcome.
 School purchase order accepted. Bids accepted. VISA, DISCOVER
SALES REP/DISTRIBUTORS/OEM WANTED. MASTER, & AMER.
1-800-870-1955/(919)870-1955 24-hr Fax:(919)870-5720

DC POWER SUPPLY

PS-303 \$159.00
 0-30VDC, 0-3A, 0.02%+2mV line regulation, 0.02%+3mV load regulation, 1mVrms noise & ripple, Short circuit/overload protection, constant current/voltage(CCV/CV)
PS-303D \$314.95 dual output, tracking
PS-305 \$219.95, 0-30VDC, 0-5A

PS-305D \$399.95, dual, tracking.

8110 \$289.95 0-60VDC, 0-3A.

8112 \$399.95 0-60VDC, 0-5A.

H108(8109) \$549.95 (\$699.95)

0-60VDC, 0-3A(5A), dual.

independent tracking. Low ripple.

8102(8103) \$399.95 (\$489.95) dual 0-30VDC/0-3A(5A), fixed 5VDC/3A, independent tracking operation, constant voltage and current Slave/Master, Serial/Parallel connection.

PS-1610S(8107) \$289.00 (\$399.95) 0-16VDC(0-30VDC), 0-10A.

PS-2243(245) \$139.00 (\$159.00) 0-12/0-24VDC, 3A(5A).

8200(8201) \$179.95 (\$239.95) 0-30VDC(digital meter), 0-3A(5A). **8210(8211) \$199.95 (\$259.95)** two digital meters.

8202(8203) \$499.95 (\$549.95) 3 outputs, digital display, dual 0-30VDC/0-3A(5A), fixed 5VDC/3A, independent tracking operation, constant voltage and current.

AM/FM SWEEMAR SCOPE

SM-6225B/C \$1999.95
 Freq Range: (AM)490KHz, (FM) 10-11.4MHz, Accuracy ± 0.1%
 Marker: (AM)455KHz, ±5KHz, ±10KHz, (FM)10.7MHz, ±7.5KHz, ±150KHz.

STEREO SCOPE OS-7505B \$369.00 trigger, 0-10MHz

ALIGNMENT SCOPE OS-7001A \$369.00 0-200kHz

AM/FM STD SIGNAL GEN.

SG-4110A \$1799.00
 Freq: 100KHz-110MHz
 Display: 6-digit LED
 Accuracy:
 ±(5x10-5 ± 1 count)
 Resolution: 100Hz (100-34.99MHz), 1KHz (35MHz-110MHz).
 Output: -19dBu, -99dBu, 1dB steps. Impedance: 50Ω VSWR 1.2.

NTSC TV COLOR BAR PAT. GEN.

CG-1366A \$159.95
 VHF NTSC;
 Freq.: 45.75, 175.25, 187.25 MHz;
 RF Output: 10mV.
 Impedance: 75 Ohm.
 Video Output: BNC, 1Vpp

SWR/RF POWER METER

310 \$89.95
 Freq. Range: 1.8-150MHz
 RF Power: 0.4W/20W/200W
 SWR Measure: 1.0 ~ 4W min.
 Accuracy: 5%-10%, SO-239 plugs
 Insertion Loss: 0.3dB.
 Input/Output Imp.: 50Ω.
320 \$89.95, 130-520MHz
330 \$119.95, 1.8-520MHz
SWR-JP \$26.95 1.7-150MHz,
 RF Power: 0.5-10W, 0.5W-100W.
SWR-2P \$22.95, 1.7-30MHz, RF Power: 0.5-10W
 MW RF Power Meter 340 \$219.00, 1.8-500MHz, 20mW ~ 2W.

MICROPROCESSOR/CONTROLLER TRAINER

Now, you can learn and apply Computer control on your PC with our low-cost trainers and lead yourself to the advanced 80386, 80486, etc. Learn ASSEMBLY, C, and BASIC languages programming and debugging, and Microprocessor based system hardware design and troubleshooting. Experiment guide and example programs are included in each trainer. These trainers are widely adopted by technical colleges.

8088 Trainer \$699.00 BGC-8088, teach yourself 8088 assembly language programming. Features: Assembly language coding, assembler, disassembler, single step and multi-breakpoint program debugger, display and rewrite registers, download/upload programs from/to external systems, I/O drivers, 56-key large size keyboard, LCD display, RS-232, UART, printer interface, two expansion slots, ±5V, ±12V switching power supply, 20 I/O applications available, e.g. servo/stepping motors, dot matrix display, D/A, A/D, sensors, ...

8051/8052 Embedded Microcontroller \$979.00 BGC-8052, teach yourself Intel 8051/8052 Microcontroller controls. 8051/8052 is one of the most popular Microcontroller used in today's appliance controls and is compatible with the new powerful MCS 251.

8051/52 In-Circuit Emulator, APEX-IE assembly language programming and debugging

CIC-100 \$549.00 I/O control applications, learn Assembly, C, and BASIC programming languages, 800-pin solderless breadboard for circuit design and test, I/O drivers for controlling relay, step motor, LED, speaker, sensor, etc. Application control modules available.

RF SIGNAL GENERATOR

SG-4160B \$124.95
 100KHz-1MHz up to 450MHz on 6 bands, 6 plug-in coils.
 3rd harmonics, 6 ranges, AM modulation, RF Output: 100mVrms to 3-5MHz. Modulation Int: 1KHz AM, Ext: 50Hz-20KHz AM.
 Audio Output: 1KHz, 1Vrms.

SG-4162AD \$229.95, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see SG-4160B above.

AUDIO GENERATOR

AG-2601A \$124.95
 10Hz-1MHz, 5 ranges;
 Output Level: sinewave 0-8Vrms, square 10Vp-p.
 Output Impedance: 600 Ohm.
 Distortion: <0.5% 500Hz-50KHz, <0.5% 50KHz-500KHz.

AG-2603AD \$229.95, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see AG-2601A above.

FUNCTION GENERATOR

FG-2100A \$169.95
 0.2Hz-2MHz in 7 ranges, Sine, Square, Triangle, Pulse & Ramp
 Output: 5mVp-p-20Vp-p, 1% distortion.

FG-2100C 0-10V control freq. to 1000:1.

FG-2102AD \$229.95 generates signals same as FG-2100, 4-digit counter display, TTL & CMOS outputs, 30ppm ± 1 count accuracy

FG-2020B \$159.00 0.5Hz-500KHz, Sine, Square, Triangle (FG)2103 \$329.95, Digital sweep generator, 0.5Hz-5MHz in 7 ranges. Operating Mode: sweep, AM, gated burst, VCG.

Freq. Counter Int. 0.5Hz-5MHz, Ext. 5Hz-10MHz.

FM STEREO MODULATOR

AG-2011A \$549.00
RF SECTION:
 Carrier: 98MHz ±2MHz;
 Output: 10mV, 1mV & 0.1mV

COMPOSITE SIGNALS:
 Pilot: 19KHz ±2Hz, 0.8Vrms

INT. MODULATION: 400KHz, 1KHz ±1%, 1Vrms, distortion < 5% L-R Separation, >50dB.
EXT. MODULATION: Freq: 50Hz-15KHz
 L-R Separation: >45dB 100Hz-3KHz, >35dB 50Hz-15KHz.

AC MILLIVOLT METER

MV-3100A \$159.95 wide band 5Hz-1MHz, 3 scales, mV, dB & dBm, 300μV-100V in 12 ranges, 10V/20V resolution, -70-40dB in 12 ranges, 0dB=1Vrms, 0dBm=0.755V, ±3% accuracy, Input impedance 10MQ, Noise <2%. **MV-3201B \$309.95** dual 0.1% full scale, channels, simultaneous measurement, 0-4.5Vp-p.

OSCILLOSCOPE

OS-7305B \$249.00 DC-~7MHz
 Vertical: 10mV/Div, Horizontal: 250mV/Div, 10Hz-100KHz in 4 ranges, 3° CRT, internal and External Sync: Input: 1MQ/35pF.
OS-7010A \$369.00 DC-~10MHz 5° CRT, 10mV/Cm-10V/Cm, 1MQ
OS-622B \$344.95 20MHz/dual trace channels, simultaneous measurement, 0.1% full scale, 0-4.5Vp-p.

OS-653 \$699.95 50MHz, dual, delay sweep, ALT trigger, TV sync.

OS-6100B \$1329.95 100MHz, 4ch, 8 traces, delay sweep, best buy

EDS-8804 \$89.00

A/D and D/A converters.

EDS-8805 \$229.00 Servo and stepper motors.

EDS-8806 \$159.00 Basic I/O experiments.

EDS-8807N-16 \$169.16 16 Dot matrix LEDs.

EDS-8807N-8 \$419.08 8 Dot matrix LEDs.

EDS-8808 \$269.00 Opto-couple controls.

EDS-8809-1 \$589.00 Stepper motor control.

Digital clock, speaker ctrl, dot-matrix LED, mat-

rix keyboard, sign

lights, electric piano, stop watch,

24 experiments, example programs included.

20% Off, DC POWER SUPPLIES

DEMO UNITS: **8102** triple outputs, 0-30V-0-

3A, 5V/3A serial/parallel \$399.95 \$319.95

PS-303D dual outputs, \$344.95 \$252.95.

GRID DIP METER

DM-4061 \$58.95 1.5-250MHz,

6 bands, 6 plug-in coils.

2 transistor, 1 diode

Modulation: 2KHz Sinewave. Crystal Oscillator: 1-15MHz.

Wave absorption meter. Using 9VDC power supply.

AUTO DISTORTION METER

DM-3104A \$799.95

MEASUREMENT:

Range: 0.01%~30%.

0.1/0.3/1/3/10/30% full scale.

Freq.: 400Hz ±10%, 1000Hz ±10% (HPF).

Input: 3mV-100V.

Ratio measuring 20dB.

Auto. Switching Ranges: Fundamental Freq. = (fo)±10%.

Function Rejection: >80dB at (fo)±5%; >70dB at (fo)±10%.

Harmonic Accuracy: ±0.5dB, 1.8(fo)-20KHz.

DM-3204 \$1,599.00 dual channels.

FREQUENCY COUNTER

FC-5250C \$119.95

Freq. Range: 10Hz-220MHz, (HF)10Hz-20MHz,

(VHF)10MHz-200MHz, Gate Time: 0.1 & 1sec.

Max. Input: 10Vp-p.

FC-5260A \$146.00

10Hz-600MHz, 7-digit LEDs.

FC-5270 \$149.95

10Hz-1.2GHz, 8-digit LEDs.

FC-5600B \$321.00

10Hz-600MHz, 10-digit LEDs.

(FC)5700 \$329.95 10Hz ~ 1.3GHz, 10-digit LEDs.

SIGNAL TRACER/INJECTOR

SE-6100 \$134.95

TRACER: Gain Max. 60dB

Attenuation: 0/20/40/60dB

Input Imped.: 100KΩ

Output Imped.: 600Ω

Speaker: 8 Ohm.

INJECTOR: Freq. 1KHz

Squarewave, Output Level: Continuously variable 0 - 4.5Vp-p.

AUTO. CAPACITANCE METER

CM300A \$139.00 10 ranges, 99.9pF ~ 99.9mF, fully automatic

Resolution: 0.1pF lowest,

0.1% full scale.

Accuracy:

0.5% of full scale ±1 digit to 99.9μF,

1% of full scale ±1 digit to 99.9μF.

Display: 3 digit LED.

Unit Indicator: pF, nF, μF, mF. Overrange indicator.

WOW-FLUTTER METER

WF-3103A \$699.95

Freq. Range: 3KHz-10% JIS/CCIR, 3.15KHz-10% DIN.

Range: 0.03/1/3/3% full scale.

Accuracy: ±5%.

WF-3105A \$799.95, digital;

Function: LIN/WOW/Flutter/WTD.

Freq. Critr: 10Hz-9.99MHz.

Indication: CCIR/DIN/JIS.

NEW PRODUCTS

mW RF Power Meter 340 \$219.00

1.8-500MHz. RF power 20mW/200mW/2W; Imp.: 50Ω.

Accuracy: ±10% full scale; N-type connector, SWR <1.15

Digital DC Power Supply 8300 (8301)

\$199.95 (259.95), 0-30V/3A(5A), CC/CV.

Electronic UHF Attenuator 085E

(087E) \$399.00, DC-950MHz, Imp. 50/75Ω, 1 dB step.

Computer Monitor Tester MT810

\$175.00 Test MDA, CGA, EGA, VGA, SVGA, 8514A

monitors. Video Patterns: color bars, cross hatch, dots, color raster and windows. Two video connectors: digital

TTL 9-D & analog 15-HD, Power: 120VAC.

MT810 \$129. Hand held model. Power: 9VDC.

PS-303D dual output, \$344.95 \$252.95.

www.americanradiohistory.com

CIRCLE 319 ON FREE INFORMATION CARD

Q & A

READERS QUESTIONS, EDITORS ANSWERS

Electronic Dog Whistle

Q I would like to build a transmitter that emits a sound that only dogs can hear. It needs to be able to transmit approximately 100 to 150 yards. — J.S., Duluth, GA.

A Try the circuit in Fig. 1; it's an audio oscillator that adjusts from about 6 kHz to 25 kHz. The speaker is a piezo-electric tweeter; ordinary speakers aren't very efficient at those frequencies.

To check the oscillator, set R2 to its maximum resistance; you'll hear a loud squeal. Then adjust R2 to put the frequency above the range of human hearing. Use a pushbutton switch and train the dog to recognize a distinctive series of ultrasonic beeps.

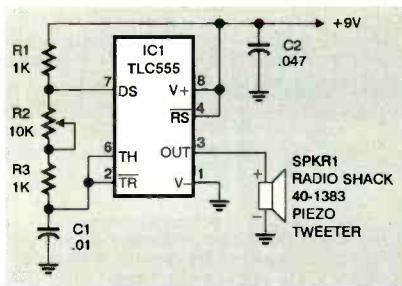


FIG. 1—THIS OSCILLATOR emits a tone that can be varied between 6 and 25 kHz. The higher frequencies can not be heard by most humans, although dogs can hear it just fine.

comparable to its weight in pounds.

Car batteries aren't rated in amp-hours because their total capacity isn't especially important; in fact they're designed never to be deeply discharged. What matters in a car battery is the total number of amps that it can deliver in cold weather ("cold cranking amps"), even though if you kept drawing current at that rate, the battery would go dead in just a couple of minutes.

What's an Amp-Hour?

Q Can you please explain to me the meaning of amp-hours, and how they are figured in reference to a car battery? — B. M., Huntsville, TX.

A Certainly. The amount of energy you can get out of a battery depends on its voltage (which is fixed), the number of amps that the load draws, and the number of hours before the battery runs down. Multiply the amps by the hours and you get amp-hours.

For example, a battery that can supply 3 amps for 4 hours has a capacity of 12 amp-hours ($3 \times 4 = 12$). The same battery could supply 1 amp for 12 hours, or 12 amps for 1 hour, or 2 amps for 6 hours, and so on.

To give you some realistic numbers, an alkaline D cell is good for about 10 amp-hours (which is actually quite impressive considering its small size). An alkaline 9-volt battery is only good for 0.4 amp-hour, but that's enough to power a 50-mA (0.05-amp) transistor radio for 8 hours. And here's a handy rule of thumb: The amp-hour capacity of a 12-volt lead-acid battery is roughly

Since you asked for a rule of thumb, we'll do an approximate calculation; greater precision would gain us nothing because there is so much variation between NiCd batteries.

For good current regulation, the AC voltage should be at least twice that of the battery. The resistance depends on the voltage drop, but since the current is only flowing half the time, the resistance should be only half the value given by Ohm's Law.

Here's a concrete example. Suppose you're charging a 7.2-volt, 1200-mAH (1.2-AH) battery pack from a source of 18 volts AC, and you want to charge in 6 to 7 hours at C/5. First, find the average charging current:

$$I = C/5 = 1.2/5 = 0.24 \text{ ampere}$$

Next, the resistance, using $R = E/I$ and then halving it:

$$R = 0.5 \times E/I = \\ 0.5 \times (18 - 7.2)/0.24 = 22.5 \text{ ohms}$$

Finally, the resistor dissipation is found using $P=I^2R$ with the average charging current:

$$P = I^2R = (0.24)^2 \times 22.5 = 1.3 \text{ watts}$$

So a 22-ohm, 2-watt resistor will do the job just fine. You'll find that batteries of different voltages (such as 7.2 and 9.6 V) can often be charged in the same charger as long as their amp-hour ratings are similar. Also, you can charge a higher-

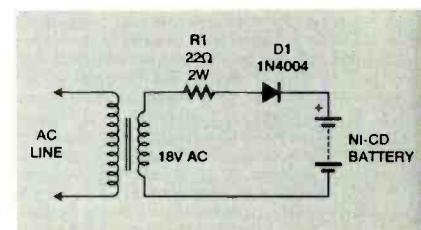


FIG. 2—WHILE THERE ARE many different NiCd-battery charger circuits, a simple resistor/diode combination like this one will do the job.

S
K
Y
V
I
S
I
O
N

1046 Frontier Drive Fergus Falls, MN 56537 Fax: 218-739-4879



*"The
DISH™ is Small,
The
Programming
BIG"*

Call now for your FREE
Skyvision 2000 Catalog of
Home Entertainment Systems

Compare to Cable and Other 18" dishes

Curious about those little dishes? Meet the newest arrival, the DISH™ Network System. This shining star, is small, attractive and the latest in technology, but what really sets it apart is the programming it delivers to your television screen. The DISH™ Network is full of the most popular programming at prices much lower than the competition. Call Skyvision now for more information.

Make digital your future...Today.

Beat The Rush!
Call the Digital Hotline Now!
800-500-9264



The Best Television Comes on a DISH™

DISH Network is a service mark of EchoStar Comm. Corp.

If you have one of these... . .

**"Keep it Running Strong"
With a Discount Buyer's Guide**

If you are the owner of a C/Ku-band Full View Satellite System, we know you'll want to keep it up and running strong. The Skyvision Discount Buyer's Guide will give you advice and products to get the job done right.

You Will Find a Wide Selection of:

- Complete Systems
- Advanced Upgrades
- Parts & Accessories
- Tune-Up Tools & Advice
- Technical Tips Galore
- Discount Skypac™ Programming

For Your Free Issue Call Now

800-334-6455

Need a repair item Fast??

"We'll Get It Out Today"



The most complete
Big Dish Satellite
Discount Buyer's Guide!
Get your FREE copy now

CIRCLE 270 ON FREE INFORMATION CARD

amp-hour battery in a charger designed for batteries of lower capacity by prolonging the charging time.

Purists will no doubt note that we've ignored the diode voltage drop and the difference between RMS and average current. For all practical intents and purposes, they have no effect in this application.

NiCd Zapping

Q I have several non-functioning NiCd battery packs. I've found several battery zappers in Rudolf Graf's Encyclopedia of Electronic Circuits, but the circuits show widely varying zapping voltages and currents. How do I determine what voltage and current I need to use for this? — G. A. H., Santa Fe, NM.

A Unfortunately, NiCd zapping is not an exact science. In fact, manufacturers don't recommend it at all, because it never leaves a battery as good as new. But we all know that it works and can often enable you to get several more weeks' or months' use out of an otherwise defunct battery.

The purpose of zapping is to clear an internal short circuit by burning away small crystalline structures that have formed inside a cell. There are many different techniques. One method is to charge a 1000- μ F capacitor to about 12 volts, then apply it briefly to the battery terminals. Another is to charge the battery briefly with heavy current (2 or 3 amps) while watching the terminal voltage; chances are it will come up to normal after half a minute or so. Make sure the current is indeed limited to 3 amps, since higher currents can make the battery explode.

All of those techniques are hit-or-miss, and the battery usually develops the same problem again in a short time. But there's no harm in trying. If possible, you should open up the battery pack to test and "zap" the individual cells. Be aware that some battery packs contain fuses that can be blown by the zapping process.

Video In Dim Light

Q I have a Sony 8mm camcorder and would like to be able to shoot video in low-light and extremely-low-light situations. Of course a video light will work up

HOW TO GET INFORMATION ABOUT ELECTRONICS

Books: Several good introductory electronics books are available at RadioShack, including one on building power supplies.

An excellent general electronics textbook is *The Art of Electronics*, by Paul Horowitz and Winfield Hill, available from the publisher (Cambridge University Press, Tel: 800-872-7423) or on special order through any bookstore. Its 1125 pages are full of information on how to build working circuits, with a minimum of mathematics.

Also indispensable is *The ARRL Handbook for Radio Amateurs*, comprising 1000 pages of theory, radio circuits, and ready-to-build projects, available from the American Radio Relay League, Newington, CT 06111, and from ham radio equipment dealers.

Copies of past articles: Copies of past articles in *Electronics Now* and *Popular Electronics* (post 1991 only) are available from Claggk, Inc., Reprint Department, P.O. Box 4099, Farmingdale, NY 11735 (Tel. 516-293-3751).

Electronics Now and many other magazines are indexed in the *Reader's Guide to Periodical Literature*, available at your public library. Copies of articles in other magazines can be obtained through your public library's interlibrary loan service; expect to pay about 30 cents a page.

Service manuals: Manuals for radios, TVs, VCRs, audio equipment, and some computers are available from Howard W. Sams & Co., Indianapolis, IN 46214 (Tel: 800-428-7267). The free Sams catalog also lists addresses of manufacturers and parts dealers. Even if an item isn't listed in the catalog, it pays to call Sams; they may have a schematic on file which they can copy for you.

Manuals for older test equipment and ham radio gear are available from Hi Manuals, PO Box 802, Council Bluffs, IA

to a certain distance, but what about objects farther away? Is there some kind of adapter that can be mounted on the camcorder to provide daytime range at night? — M. M., Denver, CO.

A You're probably thinking about image-intensifier tubes, which are photoelectric devices that amplify a faint image. These are used in military night-vision binoculars and other instruments.

51502, and Manuals Plus, Box 637, Spanaway, WA 98387.

Replacement transistors, ICs, and other semiconductors: Replacement components for a wide variety of popular devices is marketed by Philips ECG, NTE, and Thomson (SK) and are available through most parts dealers (including RadioShack on special order). The ECG, NTE, and SK lines contain a few hundred parts that substitute for many thousands of others; a directory (supplied as a large book and on diskette) tells you which one to use. NTE numbers usually match ECG; SK numbers are different.

Remember that the "2S" in a Japanese type number is usually omitted; therefore, a transistor marked D945 is actually a 2SD945.

Hamfests (swap meets) and local organizations: These can be located by writing to the American Radio Relay League (Newington, CT 06111; <http://www.arrl.org>). A hamfest is an excellent place to pick up used test equipment, older parts, and other items at bargain prices, as well as to meet your fellow electronics enthusiasts both amateur and professional.

Internet: On the Internet, electronics is discussed in Usenet newsgroups such as *sci.electronics.repair*, *sci.electronics.components*, *sci.electronics.design*, and *rec.radio.amateur.homebrew*. "For sale" messages are permitted only in *rec.radio.swap* and *misc.industry.electronics.marketplace*.


Many electronic-component manufacturers now have web pages; see the directory at <http://www.hitex.com/chipdir/>, or try addresses such as <http://www.ti.com> and <http://www.motorola.com> (substituting any company's name or abbreviation as appropriate). Many IC data sheets can be viewed online.

Image tubes and instruments that use them are available from STANO Components, Inc., PO Box 2048, Carson City, NV 89702 (Tel: 702-246-5281, Internet: <http://www.stano.night-vision.com>). You'll need a complete night vision scope with optics to form a viewable image, not just the tube alone; then you can aim the camcorder into the instrument instead of your eye.

continued on page 28

CircuitMaker®

The Virtual Electronics Lab™

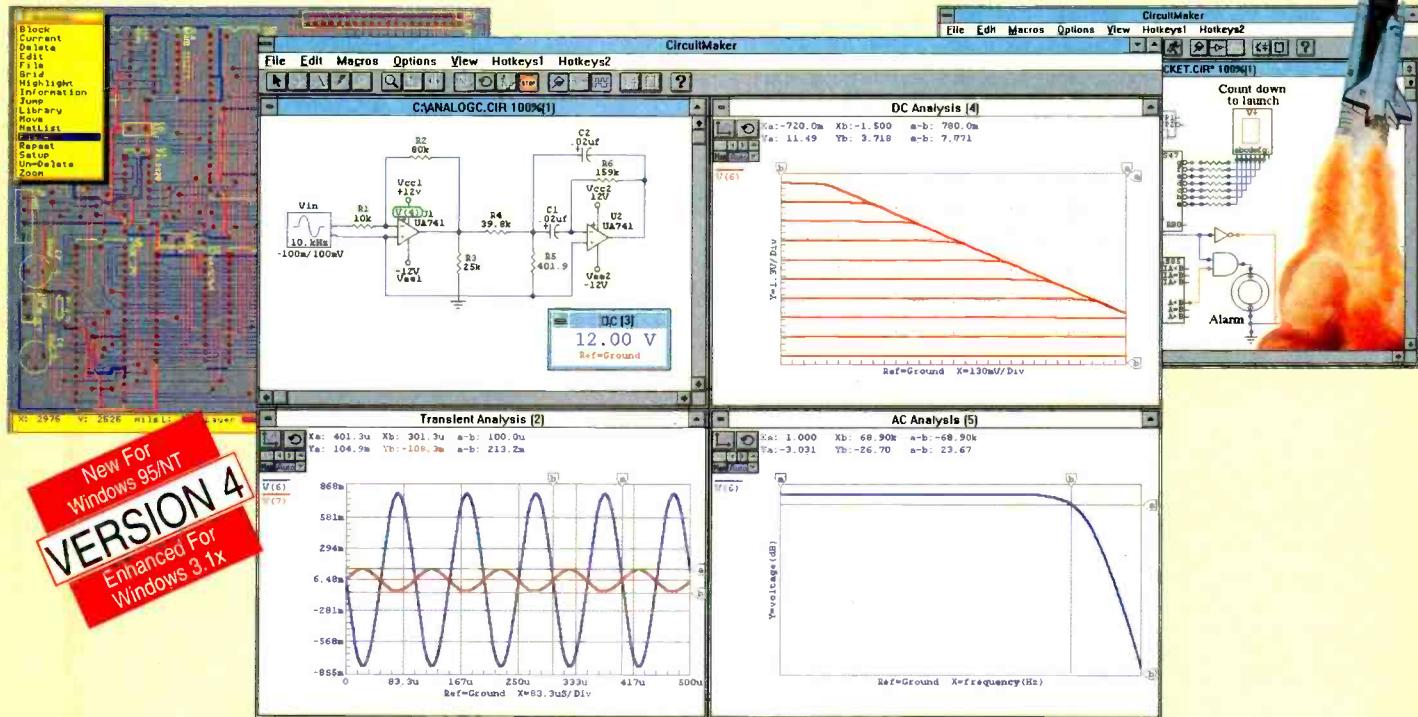

Professional Schematic Layout

CircuitMaker's schematic capabilities are unmatched and include many advanced editing features not found in similar programs. These powerful features minimize the time and task associated with drawing a schematic and insure a professional looking final product. Printout and export options are numerous and results are of the highest quality. But that's what people have come to expect from CircuitMaker.

Unlimited, Indestructible Devices

CircuitMaker ships with over 1500 devices. That's more (at no additional cost) than any competing product. If you need a device that is not included, CircuitMaker provides industry standard SPICE import and a powerful macro capability. These indestructible devices accurately emulate actual devices and enable the user to try all those "what if" scenarios with no risk and at no additional cost.

Accurate Simulation & Advanced Analysis

CircuitMaker features analog, digital and mixed-mode simulation. Obviously, simulation is of no value if the results are not accurate. CircuitMaker's simulation engine is based on Berkeley SPICE3, which is renowned for it's accuracy. That's why we can factually state that CircuitMaker provides it's user with the most accurate simulation available. Furthermore, CircuitMaker provides a wealth of analysis capabilities not found in other products in it's class. No other product offers this much simulation muscle at such a reasonable price.

Printed Circuit Board Output

CircuitMaker's PCB output capability helps you complete your design cycle, by generating a netlist that can be imported into any compatible PCB program. This is not a costly "add-on module", it comes standard with every copy of CircuitMaker. MicroCode Engineering also offers TraxMaker, a professional level, PCB layout and autorouting program for just \$299. Used in conjunction with CircuitMaker, TraxMaker completes a powerful end-to-end circuit design system.

	Full SPICE Compatibility	SPICE Export/Import	PCB Export	Retail Price
CircuitMaker	YES	YES	YES	\$299
Electronics Workbench version 4	YES	NO	NO	\$299
Electronics Workbench Engineer's Pack	YES	NO	YES	\$599

"CircuitMaker Shocks The Competition, With An Unbeatable Bottom-line"

Total Customer Satisfaction

At MicroCode Engineering we are committed to total customer satisfaction. When you purchase CircuitMaker you have the confidence of knowing that a trained staff of professionals is available to serve you after the sale. Our free unlimited customer service is second to none! Whether you have general or technical questions they will be answered promptly by a knowledgeable representative.

FREE Functional Demo

A free functional demo is available on the Internet at <http://www.microcode.com>, on CompuServe (GO MICROCODE) and on America Online by doing a file search for CircuitMaker.

Call now to order or
request additional information

800-419-4242



EQUIPMENT REPORTS

A PC-BASED BLOOD-PRESSURE MONITOR FROM PULSE METRIC.

Monitoring and recording blood pressure is easy with the DynaPulse.

CIRCLE 15 ON FREE INFORMATION CARD



It seems that people are becoming more and more aware of their own personal health. We're all more concerned today about what we eat, what we're exposed to, and so on. One aspect of that is an increased awareness of our cardiovascular health.

While the best way to monitor that is to make sure you visit your doctor regularly, in our hectic schedules, sometimes that gets put off longer than it should. To keep an eye on such things as pulse and blood pressure, some people have their own equipment. But even so, you have to be careful in taking measurements and then have to record the statistics.

The newest, easiest way to take and keep track of those measurements is to use Pulse Metric, Inc.'s (6190 Cornerstone Court East, Suite 103, San Diego, CA 92121; Tel: 619-546-9461, 800-927-8573) DynaPulse 200M, which is computer-controlled and keeps track of the records for you. The 200M monitor unit is housed in an attractive plastic enclosure that connects to a PC or Mac computer. You need DOS 3.3 or higher, Windows 3.0 or higher, or Macintosh System 6.0.7 or higher.

The kit comes with an inflatable, adult-sized cuff and inflation bulb that plugs into the side of the monitor. Different-sized arm cuffs—child-size and oversize—are optionally available. The monitor connects to the computer via a serial cable. Software then converts your computer screen into a cardiovascular laboratory. We tested DynaPulse on a

PC running Windows 95 and it couldn't have been easier to use. We were busy taking readings, printing charts, and storing records within minutes of installing the software.

About Blood Pressure

The pressure of the blood flowing through the arteries is known, obviously enough, as blood pressure, which varies as the heart beats. When the heart pushes blood out from the heart, the pressure increases, and the *systolic* or maximum blood pressure is achieved. When the heart relaxes, the pressure in the artery decreases, and the *diastolic* or minimum pressure is reached. The average pressure throughout the pulse cycle is called the Mean Arterial Pressure (MAP). The units of measurement for blood pressure are millimeters (mm) of mercury, or Hg. Systolic blood pressure is given first followed by the diastolic blood pressure, or systolic/diastolic in mmHg. Normal blood pressure typically has a high from about 130 to 139 and a low from 85 to 89.

In healthy human beings, blood pressure can increase temporarily during stressful activities, including drinking coffee and smoking, but will return to normal when the activity ceases. However, when it stays high over a long period of time, a person is said to have high blood pressure, or *hypertension*.

Unfortunately, you have to actually measure your blood pressure to know if it's normal or high. There's no other way to know if a problem exists—until it is too late.

Using the DynaPulse

The DynaPulse 200M is the perfect way to keep track of your blood pressure, your whole family's blood pressure, or even all of your customers' blood pressures if you happen to be a pharmacist or something similar. Note however, that we're only saying "keep track of" blood pressure, and nothing about interpreting it. Unless you are a doctor, you always have to consult one. A doctor is the only person qualified enough to interpret blood pressure and pulse-rate readings.

You can buy the DynaPulse 200M in one of three versions. The clinical version, \$499, is designed for hypertension screening in clinical environments with the ability to store a virtually unlimited patient database, trend and statistical analysis, histogram display, pulse-waveform analysis, and a physician's reference. The educational version, priced at \$295, is designed for teaching and comes complete with curriculum and lab material. A home version, which costs \$179, is simpler and can keep track of up to six people.

We found DynaPulse very easy to use. The software installed without a hitch, and we connected it to the COM1 port on a PC (software settings allow for operation on any available com port). There isn't even an on/off switch on the 200M, as software activates the unit when necessary. An inflatable cuff—just like your doctor's—wraps around your arm and secures with Velcro. A squeeze bulb with a relief valve inflates the cuff. But instead of having the output pressure tube connected to a mercury-filled instrument, it plugs into the DynaPulse monitor, which contains a semiconductor pressure sensor. The monitor, which is powered by four AAA batteries, converts the input pressure readings from the arm cuff into an RS-232 signal that your PC can understand.

When you use the DynaPulse, you can immediately begin measuring blood

continued on page 73

GET HERE.

LEARN A SKILL YOU ENJOY...
...THEN FIND A JOB THAT HAS A FUTURE.

Everyone has to start somewhere.

As 150,000 CIE graduates have discovered, independent study from The Cleveland Institute of Electronics can get you where you want to be. In a secure, financially rewarding, exciting career field of your choice.



Industrial Robotics


Since 1934, CIE has been on the forefront of an ever expanding technological revolution.

ment. CIE's curriculum is unique from other independent-study schools in the respect that we not only provide hands-on training utilizing today's technology we also instill the knowledge and understanding of why technology works the way it does. This is the foundation upon which every CIE graduate can trace their success back to and in which CIE's reputation as a quality learning facility is based on.



Project Engineer

Independent study is not for everyone. But, if you have the desire, the basic intellect and the motivation to succeed, CIE can make it happen. Our learning program is patented and each lesson is designed for independent study while our instructors are available to assist you whenever you feel you need help. In fact, CIE's curriculum is so well respected many Fortune 1000 companies utilize it for their own employees.

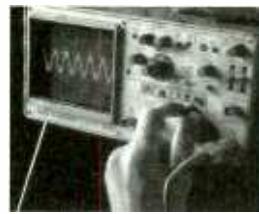

Telecommunications

CIE offers personalized training to match your background with over ten career courses, an Associate Degree Program and a Bachelor Degree Program through our affiliation with World College. And every CIE graduate got started

in a successful career the same way you can...by sending for your free CIE course catalog and judging for yourself if CIE's for you.



Electronics

Back then it was radio and TV, today it's computer technology, programming and the electronics that make it all possible. Today and yesterday's similarities are

uncanny... Employers are looking for qualified applicants to hire and having a hard time finding them.

Students at CIE receive the training and the education needed to get hired and to succeed in challenging fields such as computer programming, robotics, broadcast engineering, and information systems management.

START HERE...

YES! Please send me more information on:

- CIE's Associate Degree Program
- CIE's Computer Programming Course
- CIE's 12 Career Courses
- World College's Bachelor Degree Program

AE92

Name _____

Address _____

City _____

State _____ Zip _____

Phone: _____

Check for G.I. Bill Details

Active Duty Veteran



Computer Programming

CIE

*It's More Than Just Training...
...It's an Education.*

1776 East 17th Street
Cleveland, OH 44114
(216) 781-9400 • 1-800-243-6446



NEW PRODUCTS


USE THE FREE INFORMATION CARD FOR FAST RESPONSE

Digital Real-Time Oscilloscopes

THE TDS 200 SERIES OF DIGITAL real-time (DRT) oscilloscopes from Tektronix cost about half the price of existing entry-level digital scopes and offer a combination of features that will

contain full contrast at all sweep speeds and gain settings. Any signal that triggers the scope will be clearly visible on screen.

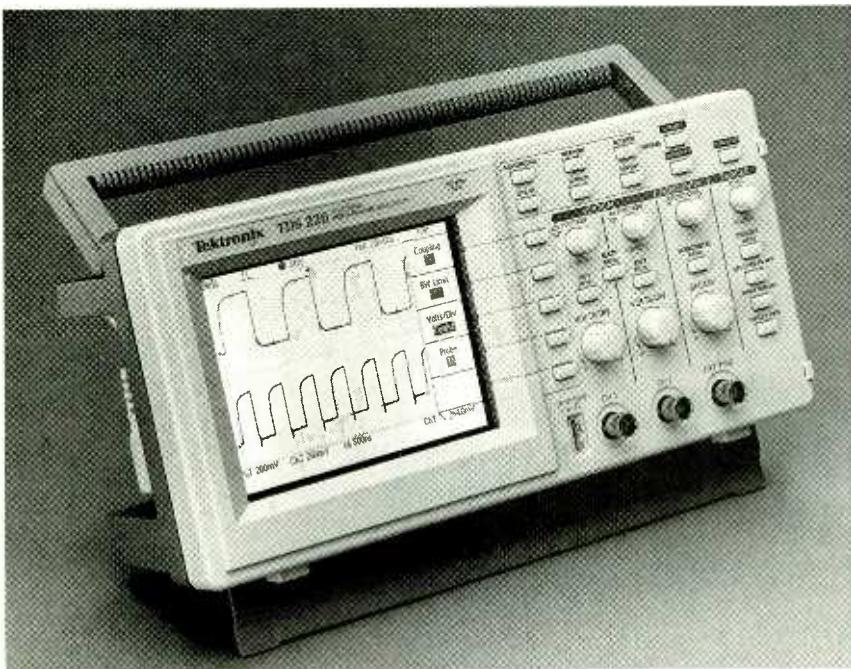The TDS 200 series relies on Tektronix DRT oversampling technology to



CIRCLE 20 ON FREE INFORMATION CARD

overcome customers' objections to making the switch from analog to digital scopes. Designed for manufacturing, education, and service applications, the 60-MHz TDS 210 and the 100-MHz TDS 220 are priced competitively with similarly equipped analog scopes. They also offer superior measurement capability, analog-like controls and operating modes, and compact size—about one-fourth the size of other benchtop oscilloscopes.

One reason for that compact size is that both units in the TDS 200 series feature a bright, high-contrast, liquid-crystal display with a wide viewing angle. Unlike analog scope displays, the LCD main-

provide excellent waveform quality, update rate, and stability. Both models sample at 1 GS/s—at least ten times their bandwidth—which allows users to capture signal details invisible on analog scopes. Pre-programmed automatic measurements enable users to quickly quantify waveforms: period, frequency, cycle RMS, mean, and peak-to-peak. Other productivity features include automatic setups (similar to autoranging in a digital multimeter), stored reference waveforms, and stored front-panel setups that are not lost when the power is turned off.

The user interface looks and feels "analog," bringing back many of the

front-panel knobs that are familiar to analog-scope users. Routine functions such as gain, sweep speed, and vertical/horizontal positioning, are immediately accessible and respond like analog-scope controls. Automated digital functions are controlled by a simplified on-screen menu system, available in ten user-selectable languages.

The TDS 210 and TDS 220 carry suggested U.S. list prices of \$995 and \$1695, respectively.

TEKTRONIX, INC.

P.O. Box 500

Beaverton, OR 97077-0001

Tel: 1-800-479-4490, action code 317

DSP Filter

MFJ Enterprises' MFJ-781 DSP filter will add "brick wall" DSP filtering to any TNC or multimode data controller, allowing you to copy signals buried in noise and QRM—signals you can't even hear. The device will improve all modes on any model TNC, and it will give you an array of 100 sharp *No*Ring* linear-phase FIR filters. You can choose 20 filters to include on the front-panel switch for easy, one-knob selection.

The MFJ-781 plugs between your transceiver and multimode. It features input and output level controls and an accurate, easy-to-use input level indicator. Automatic gain control helps keep your audio level constant during signal fade. The on/off/bypass switch provides a true bypass.



CIRCLE 21 ON FREE INFORMATION CARD

Under severe QRM, the filter will greatly improve copy of packet, AMTOR, PACTOR, GTOR, Clover, RTTY, SSTV, WeFAX, Fax, CW, and just about any other digital mode. You can choose from 64 data filters with 16 mark/space pairs, four shifts, and four baud rates. Interference is 40-dB down, 60-Hz outsize passband. You also get 32 CW filters with eight CW tones (300-1000 Hz) and four bandwidths (50-500 Hz). Four customized filters are optimized for VHF packet, Clover, WeFAX, and SSTV.

The MFJ-781 DSP filter has a suggested retail price of \$129.95. For MFJ-1278B's, order the MFJ-780 plug-in DSP filter, priced at \$99.95.

MFJ ENTERPRISES, INC.

P. O. Box 494

Mississippi State, MS 39762

Tel: 601-323-5869 or 1-800-6477-TECH

Fax: 601-323-6551 or 1-800-647-1800

True-RMS Clamp Meter

Electrical contractors, plant-maintenance engineers, electricians, and utility technicians will find B+K Precision's Model 369 multifunction clamp meter to be convenient and useful for measuring high electrical currents without direct electrical contact. The handheld instrument measures true-RMS AC current to 700 amps from 45 Hz to 1 kHz, and DC current to 700 amps with 2% accuracy. AC and

DC voltage can be measured to 750 volts with 1% accuracy, using test leads. The clamp can be used to measure resistance from 0.1 to 4000 ohms and frequency from 0.1 Hz to 10,000 Hz with 0.2% accuracy.

The Model 369 can also measure instantaneous AC amperes using its crest mode, which can log peak currents as high as 1000 amps. Data hold instantly freezes the displayed reading. Continuity check sounds a tone to verify an unbroken electrical path. Min-Max mode logs a running record of minimum, maximum, and average values.

The meter accepts conductors up to two inches in diameter. Its large, 4000-count LCD readout includes a 41-segment bar graph for peaking, nulling, and easy identification of varying signals.

The Model 369 clamp-on meter, complete with battery, clip-on carrying case, test leads, and manual, costs \$199.

B+K PRECISION

6470 West Cortland Street

Chicago, IL 60635

Tel: 1-800-462-9832

Fax: 312-794-9740

Four-Piece Inspection Light

Specifically designed for the field technician, Moody's Acu-Min Inspection Light allows light to shine on hard-to-

ducting rod, and a mirror. The straight rod conducts the battery-powered xenon light down straight passages. The curved rod conducts light around corners to reach areas not normally visible. The small mirror fits snugly on both conducting rods to expand the user's field of view. The set comes packaged in a vinyl pouch.

The Acu-Min Inspection Light (stock #58-0235) costs \$42.95.

MOODY TOOLS, INC.

42-60 Crompton Avenue

East Greenwich, RI 02818-0230

Tel: 1-800-TOOL-INC

Fax: 401-885-4565

Memory Tester

Aristo Computers' SIMCHECK II is a third-generation, state-of-the-art memory tester. With a fast 486 processor and sophisticated time-delay circuitry, the tester allows users to accurately test today's—and tomorrow's—large memory devices. The stand-alone, portable unit tests both 72-pin and 30-pin SIMM modules in sizes up to 4Gx40 with a 96-pin expansion slot for future add-on companion testers. The SIMCHECK II measures RAS and CAS access time at 1-ns resolution. It includes a generic interface for the Automatic Handler, parallel printer, and other devices. The fully automatic test program allows non-technical personnel to operate the tester with the push of a single button, yet



CIRCLE 24 ON FREE INFORMATION CARD

still allows engineers to set up complex custom tests.

The SIMCHECK II has a retail price of \$2495.

ARISTO COMPUTERS INC.

6700 SW 105th Avenue, Suite 300

Beaverton, WA 97008

Tel: 1-800-3ARISTO or 503-626-6333

Fax: 503-626-6492




CIRCLE 22 ON FREE INFORMATION CARD

reach areas. The set contains a flashlight, a straight conducting rod, a curved con-

Workstation Surge Protection

The Back-UPS Office from American Power Conversion is a multipath power device intended to combat hardware damage caused by surges and prevent data loss from brownouts and blackouts. The device offers multi-outlet surge protection, phone line protection for on-line users, network data-line protection for corporate workstations, and battery backup for CPUs. Aimed at the small-office/home-office (SOHO) market, and backed by a \$25,000 equipment-protection guarantee, the device protects against all power problems on all power paths to a computer and peripherals including printers, scanners, external tape drives, and fax machines.

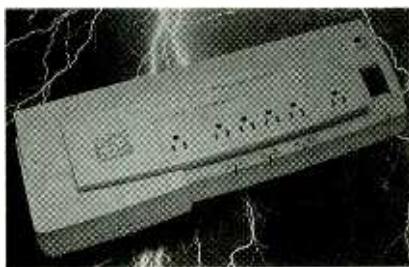

CIRCLE 25 ON FREE INFORMATION CARD

The Back-UPS Office offers six outlets, all with surge-suppression and EMI/RFI filtering, and three of them also provide battery power for data protection. The device provides 7 to 13 minutes of battery backup during a power disruption, allowing the user plenty of time to shut down the system in an orderly manner. Modem protection safeguards users' Internet access and prevents PC damage from surges and spikes entering through the "back door." An indicator lets the user know when a new battery is needed. A site-wiring fault indicator detects wiring problems in the building that could cause potential fire hazards. Unique "BlockSafe" outlet spacing allows transformer blocks to be used without sacrificing other outlets.

The Back-UPS Office surge protector costs \$179.

AMERICAN POWER CONVERSION

P. O. Box 278

132 Fairgrounds Road
West Kingston, RI 02892

Tel: 1-800-877-4080
Fax: 401-789-3710

Web site: <http://www.apcc.com>

900-MHz Cordless Phone

Sanyo's Model CLT-986 900-MHz, digital spread-spectrum cordless telephone features a call-management caller-ID system, AC power-failure protection, and—for those who need still more freedom than that afforded by mere cordless phones—a "Speak Station" handset speakerphone for hands-free communication. The 900-MHz direct-sequence, spread-spectrum technology extends the transmission range and virtually eliminates interference. The digital technology also makes it difficult for eavesdroppers to tap into the signal.



CIRCLE 26 ON FREE INFORMATION CARD

AC power-failure protection allows the CLT-986 to be used even during interruptions in the supplied line power. The back-up battery pack, built into the base of the unit, uses four "AA" alkaline batteries. The speakerphone handset also provides two-way paging. Sanyo's call management system is intended for use with the Caller ID service provided by local phone companies. With a recorded log of up to 20 calls, the system maintains a list of caller names with bi-lingual prompts, call times, dates, and last call received, with area-code editing capability. A 16-digit, two-line LCD readout on the handset allows the user to scroll through recorded data. Other features include one-hour quick charge, dual keypad operation, and 20-number memory.

The CLT-986 cordless telephone has a suggested retail price of \$349.99.

SANYO

21350 Lassen Street
Chatsworth, CA 91311-2329

Tel: 818-998-7322

Fax: 818-701-4149

Interface Converter

New safety standards such as IEC 8081-2 place limits on the shock hazards to which people are subjected when using electronic devices in a medical environment. Telebyte's Model 287 RS-232 to RS-422 opto-isolated interface converter satisfies those stringent requirements for computer systems.

The Model 287 does not require a separate AC or DC input because the power required is extracted from the PC's RS-232 interface. That power is further conditioned to develop an isolated power supply to operate the link side of the interface converter.



CIRCLE 27 ON FREE INFORMATION CARD

A DB9 female connector allows the converter to be directly attached to any PC communications port, and an RJ-12 modular connector creates the link interface. A DTE/DCE switch allows the user to reverse the transmit data and receive data signals to interface to a different type of port. Data is accommodated at rates up to 19.2 kilobytes per second. The transmit- and receive-data signals use the four inner pins of the RJ-12 connector, and the two outside pins are reserved for grounding a shield on the link cable, if one is used. The ground path includes a ground stud to which a 12-inch ground connection is attached. The Model 287 will withstand a 4-kilovolt discharge with the ground connection.

The Model 287 RS-232 to RS-422 converter costs \$155.

TELEBYTE TECHNOLOGY, INC.

270 Pulaski Road

Greenlawn, NY 11740

Tel: 516-423-3232 or 1-800-TELEBYT

Fax: 516-385-8184

E-mail: sales@telebyteusa.com

Web site: <http://telebyteusa.com>



NEW LITERATURE

USE THE FREE INFORMATION CARD FOR FAST RESPONSE


Practical Electronics Handbook Fourth Edition

by Ian Sinclair

Butterworth-Heinemann

225 Wildwood Avenue, Unit B
P.O. Box 4500
Woburn, MA 01801
Tel: 617-928-2500

\$32.95

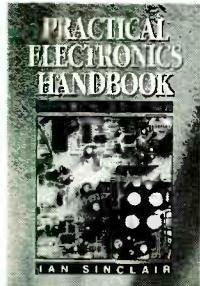

CIRCLE 337 ON FREE INFORMATION CARD

This comprehensive book provides a practical collection of circuits, rules of thumb, and design data for professional engineers, students, and electronics hobbyists. Enough background is included to make the book accessible to beginners and to facilitate the understanding and development of a range of basic circuits. For those with more electronics experience, the book can serve as a compact compendium of everyday information and a convenient reminder of electronic principles and circuits.

Topics covered include passive components, active discrete components, discrete-component circuits, linear ICs, digital ICs, microprocessors and microprocessor systems, transferring digital data, digital-to-analog conversions, computer aids in electronics, and hardware components. The fourth edition has been updated with new chapters and sections covering topics such as sensing components, connectors, and soldering.

Switch Catalog #103

Switches Plus

192 Pepe's Farm Road
Milford, CT 06460
Tel: 1-800-792-4757

Fax: 1-800-792-5877

Web site: <http://www.switchesplus.com/>
Free



CIRCLE 338 ON FREE INFORMATION CARD

An all-metal, sealed, vandal-proof keypad leads off the new line of keypad devices included in this catalog. The brochure also features a wide variety of heavy-duty and signal-level pushbuttons, pilots, and selectors; emergency stop switches; snap-acting switches; joystick controls; pulse counters; and power supplies. All products feature UL and international approvals as well as ISO 9001 certification. The 56-page catalog contains ordering information, descriptions, illustrations, technical specifications, and prices.

Fuzzy Logic for Real World Design

by Ted Heske and Jill Neporent Heske

Annabooks

11838 Bernardo Plaza Court
Suite 102A

San Diego, CA 92128

Tel: 619-673-0870 or 1-800-462-1042

Fax: 619-673-1432

\$49.95, including disk



CIRCLE 339 ON FREE INFORMATION CARD

language fuzzy kernel, complete with

directions for cross-compiling it for a variety of Motorola and Intel microcontrollers. The diskette also contains all of the source code that is presented in the book.

The first three chapters present an overview of fuzzy-logic history, terminology, and theory of operation. Subsequent chapters discuss engineering fundamentals, embedded-systems considerations, and hardware/software partitioning. The book also discusses object-oriented fuzzy-logic design and C++ implementation. A fuzzy-logic primer ties it all together. Appendices include a list of fuzzy-logic development tools and suppliers, and instructions for cross-compiling the fuzzy kernel for a variety of Motorola microcontrollers.

Multimedia DSO Teaching Aid

Metrix

P.O. Box 332

Brea, CA 92622-0332

Tel: 714-992-1239

\$10



CIRCLE 340 ON FREE INFORMATION CARD


The Metrix OX-8020 CD-ROM is an interactive, multimedia demonstration of how to use a digital storage oscilloscope (DSO). Instruction is presented in French, English, German, and Spanish. Aimed at both teachers and students, the CD-ROM can be used for on-the-job or classroom instruction. Besides an introduction to the use of oscilloscopes to capture and store waveforms, the CD-ROM demonstrates how, after acquisition, data can be manipulated and displayed different ways, and how measurements can be output to plotters, computer files, and monitors.

Although it uses the Metrix OX8020

digital storage scope as a model, the disk can be used with a PC alone. Minimum system requirements are a 486 multimedia PC (with audio board), 8 megabytes of RAM, a video card, a CD-ROM drive, Windows 3.1, and at least 10 megabytes of free hard-drive space.

The Corporate Intranet: Create and Manage an Internal Web for Your Organization

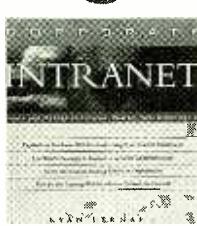by Ryan Bernard
John Wiley & Sons, Inc.
605 Third Avenue
New York, NY 10158-0012
Tel: 1-800-225-5945
Web site: <http://www.wiley.com/compbooks/>
\$29.95



CIRCLE 341 ON FREE INFORMATION CARD

While many companies use the Internet to provide their outside customers with in-depth on-line information, relatively few take advantage of internal, or Intranet, Web sites. A corporate Intranet site is an inexpensive yet powerful alternative to other forms of internal communications. It is a secure, interactive network that allows employees to instantly access, view, and contribute to live product-management documents, regardless of what kind of computer is being used.


This book shows Internet-savvy managers, marketers, and other communications specialists how they can dynamically distribute and share vital information across their organizations—even reaching foreign subsidiaries and home-offices. It presents a practical overview of everything needed to allow a computer network to support an Intranet system. After introducing basic Web tools and technology, the book helps various departments within a corporation budget to plan and promote the Intranet. It explains how to provide outside employees with secure access, and how to create “public” and “private” channels to interface the Intranet with the Internet. Case studies from Sun Microsystems, Chevron Petroleum,

Digital Equipment, and Nortel enhance the text.

Easy Calculator Math for Electronics

by Larry R. Luchi
Limelight Books
Division of Tiare Publications
P. O. Box 493
Lake Geneva, WI 53147
Tel: 414-248-4845

\$17.95 plus \$3 shipping and handling

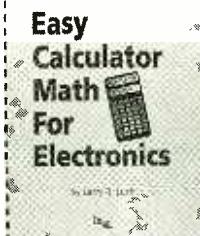

CIRCLE 342 ON FREE INFORMATION CARD

This study guide helps readers make quick work of math problems involving electronics. It takes the reader through each required step in more than 30 formulas used in electronics; topics include Ohm's Law, phase angles, component values for resonance, transistor characteristics, and much more.

Each formula is carefully explained, with one or more step-by-step examples presented in an easy-view, easy-to-follow format. Explanations of terminology and theory are also included, along with diagrams to help readers understand the material.

Coaxial Products Catalog #1995

Pasternack Electronics
P. O. Box 16759
Irvine, CA 92713
Tel: 714-261-1920
Fax: 714-261-7451

Free



CIRCLE 343 ON FREE INFORMATION CARD


This compact catalog squeezes a wealth of information into its 81 pages of small-print text. Featured product lines include more than 20 different types of coaxial connectors, coax cable, adapters, cable-cutting and crimping tools, four types of attenuators, adapters, breakouts, coaxial switches,

patch cords, terminations, shorts, cable assemblies, directional couplers, power dividers, and twinax cables and connectors. The catalog includes photographs and pricing for single units as well as quantity discounts.

Modern CMOS Circuits Manual

by R. M. Marston
Newnes
an imprint of Butterworth-Heinemann
225 Wildwood Avenue, Unit B
P. O. Box 4500
Woburn, MA 01801
Tel: 617-928-2500

\$28.95

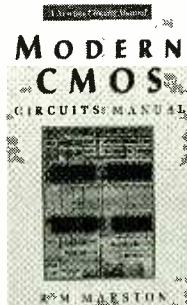

CIRCLE 344 ON FREE INFORMATION CARD

The first in a new series of circuit manuals from frequent *Electronics Now* contributor Ray Marston, this book examines operating principles and practical applications of modern medium-speed and fast CMOS digital ICs. The informative, “how-to” text is accompanied by 470 carefully selected circuits, diagrams, graphs, and tables. Detailed descriptions of more than 120 modern CMOS ICs and their practical applications are included. Aimed at design engineers and technicians, the book’s clear layout and easy-to-understand explanations also make it a good starting point for students and hobbyists.

Each chapter opens with an examination of the basic principles of the subject, followed by the presentation of circuits and useful data. The first chapter describes and explains digital-IC basics, CMOS and TTL principles, the various CMOS sub-families, and the basic rules of CMOS usage. Chapter 2 gives a practical introduction to CMOS fundamentals via the 4007UB IC, which can be used in both digital and linear applications. Subsequent chapters deal with modern logic circuitry, CMOS bilateral switches and data selectors, waveform-generator circuitry, clocked flip-flop and counter circuits, ICs, special counter/dividers, data latches, registers, comparators, code converters, and specialized ICs

Catch Our New Waves



Function Generator Breakthrough!

Introducing all new B+K Function Generators offering wider frequency bandwidths at new value pricing.
Beats the competition big time!



Product Features . .

- Proprietary integrated circuit doubles bandwidth for best performance and reliability.
- All the basic functions plus
 - Sine, Square and Triangle waves
 - TTL and CMOS outputs
 - Variable waveform symmetry
 - Variable DC offset.
- Made in the USA



* Manufactured in USA from domestic and imported parts.

For the name of your nearest B+K distributor
Call 1-800-462-9832

8am-5pm, CST, weekdays

Bandwidth Counter	TTL	CMOS	SWP.	AM/FM	Price	Model
2MHz	•	•			\$229	4010
5MHz	•	•			\$284	4011
10MHz	•	•	•	•	\$369	4017
20MHz	•	•	•	•	\$499	4040

Compare this price with
those \$1,200 units!



BK PRECISION®
MAXTEC INTERNATIONAL CORP.

Domestic and International Sales
6470 W. Cortland St., Chicago, IL 60635
Tel: 312-889-1448 • Fax: 312-794-9740
Canadian Sales: DCS Electronics, Ltd.
Tel: 905-683-4500 • Fax: 905-683-8074

such as multiplexers and decoders. The final chapter presents a miscellaneous collection of CMOS circuits.

Master Source-Book 1996 Edition 2

Industrial Computer Source

P. O. Box 910557

San Diego, CA 92191-0557

Tel: 1-800-523-2320

Fax: 619-677-0898

E-mail: industrial.computer@industry.net

Web site: <http://www.industry.net/ind-compsrc>


Free



CIRCLE 345 ON FREE INFORMATION CARD

This 192-page catalog is filled with computer and network solutions, including software and complete integrated systems. Product categories include CPUs, chassis, rack enclosures, systems servers, embedded

controllers, drive controllers, multimedia cards, monitors, CD and tape backup systems, diagnostics and development boards and software, analog and digital I/O products, PC instrumentation, communications devices, software tools, and applications software. New product highlights include 166-MHz Pentium CPUs and the GIRSystem chassis for EMI containment. Photographs, descriptions, and prices are offered for each product, as well as dimensional outlines where applicable. The catalog also provides reference sections and product comparison charts.

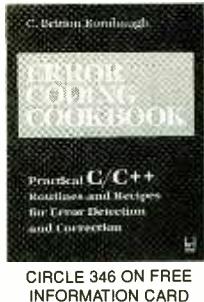

CIRCLE 346 ON FREE INFORMATION CARD

Unless you happen to be an abstract mathematician, you're likely to get lost in the maze of error-correction coding that is a crucial element of any signal-processing or communications system. This book strives to simplify the complexities of error coding.

This non-theoretical guide clearly explains the error-coding process. It offers complete, step-by-step instructions on how to select the most appropriate code for your particular application, design the corresponding coders and decoders, and implement many of the most well-known and frequently used codes for error correction. The book's clear descriptions of each code are reinforced by worked-out examples and a brief review of only the necessary math. The accompanying disk provides access to ready-to-use C and C++ programs for generating hundreds of codes for error detection and correction. **EN**

Error Coding Cookbook: Practical C/C++ Routines and Recipes for Error Detection and Correction

by C. Britton Rorabaugh

McGraw-Hill, Inc.

11 West 19th Street

New York, NY 10011

Tel: 1-800-2-MCGRAW

\$50, including disk

Q & A

continued from page 16

PIC Information

Q I've designed an electronic product that I think could be greatly improved by using PIC microcontrollers. To redesign, I need information about microcontrollers. If you have any information that you can share with me, I would greatly appreciate it. — T. Z., Easton, PA.

A Go straight to the horse's mouth and get a set of PIC manuals (including the *Embedded Control Handbook*) from Microchip, Inc., 2355 West Chandler Boulevard, Chandler, AZ 85224 (Tel: 602-786-7200). Also take a look at their Web page, <http://www.microchip.com>, and Don Lancaster's web page, <http://www.tinaja.com>. Don Lancaster is our "Tech Musings" columnist, and he has written a lot about PICs.

Other than the manuals, there's no general book about PICs as far as we know. If you're entirely new to microcontrollers, you may want to start with the 8051 family simply because good textbooks are available. One of the best

is *The 8051 Microcontroller*, by Kenneth J. Ayala, published by West; any bookstore should be able to order that for you. If you go with an 8051-family controller, consider the Philips 87C750; it's cheap (under \$5) and a development kit that attaches to your PC is available from Philips for less than \$100.

We've Been Surpassed

In the July installment of "Q&A" (see page 14), a reader asked how to light either a red or a green LED at the flip of a single SPST switch. We published a circuit with 3 resistors and a transistor. Several readers wrote in with simpler

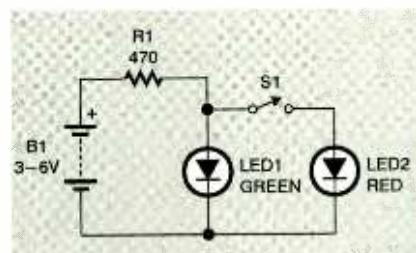


FIG. 3—THIS SIMPLER SOLUTION to the switch-operated LED problem takes advantage of the fact that red LEDs have a lower voltage drop than green ones.

solutions. Figure 3 shows the simplest, submitted by D. L. Bare of Kirby, Wyoming. Red LEDs have a lower voltage drop than green ones, so if you connect red and green LEDs in parallel, only the red one lights.

Mr. Bare points out that the voltage of an LED is directly related to the amount of energy in each photon—higher at shorter wavelengths of light. Thus infrared LEDs take the lowest voltage, and blue LEDs, the highest. The moral? Never connect LEDs in parallel—if there's even a slight difference in wavelength, the lower-wavelength LED will take all the current.

Thanks to everyone who wrote in!

Writing to Q&A

As always, we welcome your questions. The most interesting ones are answered in print, usually within 9 months. Please be sure to include plenty of background information (we'll shorten your letter for publication). *If you are asking about a circuit, please include a complete diagram.* We regret that due to the volume of mail, we cannot give personal replies. **EN**

The Four-Year Electronics Degree Program That Really Hits Home!

Bring The Technology Home With A Bachelor Of Electronics Engineering Degree. No Hassles. No High Cost!



Now's the time to prepare for a profitable career.

We've lowered the cost of higher education.

It's true! You can earn a four-year Bachelor of Electronics Engineering Technology degree today ... and prepare yourself for a high-paying electronics career ... without quitting your job or ever leaving your home. Because World College, an affiliate of the Cleveland Institute of Electronics, offers you the total flexibility of independent study programs proven effective for people like you who truly want to succeed! World College independent study lessons help you build valuable skills

**Mail/Fax Today
or Call
1-800-696-7532**

step-by-step, and expert instructors are personally available to you with a toll-free call. What a way to earn an education!

A world of opportunity.

Where is your career headed? With a four-year bachelor's degree from World College, you call the shots, choosing from incredible, high-paying opportunities in electronics, telecommunications, computer, electrical power, and many other growing fields.

World College gives you the skills, the knowledge, the power to take advantage of your best opportunity in electronics. And you can do it all at your own pace!

Without leaving home.

World College continually works to provide its students with the most advanced education tools. From the latest equipment and reference books to breakthrough computer-simulated experiments, students are exposed to the latest technological advancements.

All the equipment, parts, and software you need are included in your affordable tuition, including more than 300 hands-on lab experiments you can complete in your home.

Choose your own pace.

Earn your bachelor's degree on your time — and at your pace — because you pay tuition to World College only as you complete the upper-level semesters close to graduation. The faster you make it through, the less you pay. So you have an incentive to make your future happen quickly — yet the freedom to choose your own pace!

Send today for your FREE course catalog — and give yourself that future you've always wanted — with an electronics degree education from World College.




Take charge of your future in electronics.

Four Powerful Reasons To Connect With World College Today:

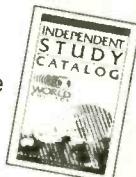- 1. Earn your four-year degree!**
- 2. Self-paced training!**
- 3. Independent study in your home!**
- 4. Expert instruction!**

Give Me The Power!

Send me a FREE World College course catalog today!



(Please Print Neatly)

Name _____

Address _____

City _____

State, Zip _____

Phone () _____

Age _____

**For faster service, call
1-800-696-7532,
or call
1-804-464-4600.**

**Or fax this coupon to
1-804-464-3687.**



Lake Shores Plaza
5193 Drive, Suite 113
Virginia Beach, VA 23455-2500



Affiliated with
Cleveland Institute of Electronics

WAE38

RETAILERS THAT SELL OUR MAGAZINE MONTHLY

Alaska

Frigid North Co.
1207 W. 36th Avenue
Anchorage, AK 99503

Arizona

Dalis Electronics
2829 E. McDowell Road
Phoenix, AZ 85008

California

California Electronics
221 N. Johnson Ave.
El Cajon, CA 90202

Signal Electronics
22307 Ocean Avenue
Torrance, CA 90505

Ford Electronics
8431 Commonwealth Avenue
Buena Park, CA 90621

All Electronics
14928 Oxnard Street
Van Nuys, CA 91411

Gateway Electronics of CA
9222 Chesapeake Drive
San Diego, CA 92123

Mac's Electronics
191 South "E" Street
San Bernardino, CA 92401

Electronics Warehouse
2691 Main Street
Riverside, CA 92501

Orvac Electronics
1645 E Orangethorpe Ave.
Fullerton, CA 92631

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove, CA 92643

Marvac Dow Electronics
980 S. A Street
Oxnard, CA 93030

Kandarian Electronics
1101 19th Street
Bakersfield, CA 93301

Whitcomm Electronics
105 W. Dakota #106
Clovia, CA 93612

Marvac Dow Electronics
265-B Reservation Road
Marina, CA 93933

Minuteman Electronics
37111 Post St., Suite 1
Fremont, CA 94536

HCS Electronics
6819 S. Redwood Drive
Cotati, CA 94931

Halted Specialties Co.
3500 Ryder Street
Santa Clara, CA 95051

Metro Electronics
1831 J Street
Sacramento, CA 95814

The Radio Place, Inc.
5675-A Power Inn Road
Sacramento, CA 95824

HSC Electronics
4837 Amber Lane
Sacramento, CA 95841

Colorado

Gateway Electronics of CO
2525 Federal Blvd.
Denver, CO 80211

Centennial Electronics
2324 E. Bijou
Colorado Spgs., CO 80909

Connecticut

Signal Electronics Supply
589 New Park Avenue
W. Hartford, CT 06110

Cables & Connectors
2198 Berlin Turnpike
Newington, CT 06111

Electronic Service Prod.
437 Washington Avenue
North Haven, CT 06473

Florida

Sanya Electronics
596 NW 99th Ct.
Miami, FL 33172

Georgia

Norman's Electronics, Inc.
3653 Clairmont Road
Chamblee, GA 30341

Illinois

Tri State Elex
200 W. Northwest Hwy.
Mt. Prospect, IL 60056

Maryland

Mark Elec. Supply Inc.
5015 Herzl Place
Beltsville, MD 20705

Amateur Radio Center
1117 West 36th Street
Baltimore, MD 21211

Massachusetts

U-Do-It Electronics
40 Franklin Street
Needham, MA 02194

Michigan

Purchase Radio Supply
327 East Hoover Avenue
Ann Arbor, MI 48104

Norwest Electronics
33760 Plymouth Road
Livonia, MI 48150

The Elec. Connection
37387 Ford Road
Westland, MI 48185

Elec. Parts Specialists
711 Kelso Street
Flint, MI 48506

Minnesota

Acme Electronics
224 Washington Avenue N.
Minneapolis, MN 55401

Missouri

Gateway Electronics Of MO
8123-25 Page Blvd.
St. Louis, MO 63130

William Elec & Ind Supply
803 Davis Blvd.
Sikeston, MO 63801

New Jersey

Lashen Electronics Inc.
21 Broadway
Denville, NJ 07834

New York

Sylvan Wellington Co.
269 Canal Street
New York, NY 10013

R&E Electronics
4991 Rt. 209
Accord, NY 12404

Unicorn Electronics
Valley Plaza
Johnson City, NY 13790

Ohio

Philcap Electronic Suppliers
275 E. Market Street
Akron, OH 44308

Oregon

Norvac Electronics
7940 SW Nimbus Avenue
Beaverton, OR 97005

Pennsylvania

Business & Computer Bookstore
213 N. Easton Road
Willow Grove, PA 19090

Texas

Mouser Electronics
2401 Hwy. 287 N
Mansfield, TX 76063

Electronic Parts Outlet
17318 Highway 3
Webster, TX 77598

Washington

Amateur Radio Supply Co.
5963 Corson Ave., Ste 140
Seattle, WA 98108

Wyoming

Chris Supply
2007 S. Douglas Hwy., Ste. C
Gillette, WY 82716

If you'd like to sell our magazine in your store,
please circle 210 on Free Information Card.



BUILD THIS AUTOMATIC PARTS TRAY

Learn how to use stepper motors, and build a great system that simplifies PC-board assembly in the process.

JAMES J. BARBARELLO

Stepper motors are simultaneously exciting and intimidating for the hobbyist. There's something fascinating about a precision device with so many uses. That fascination dampens, however, when you consider the logistics of obtaining steppers, not to mention the hardware and software required to drive them. Wouldn't it be nice to see a complete project using parts obtainable in small quantities at low cost?

Well, this project does just that. Using a readily available 5-volt stepper motor and a handful of common parts, we'll create a computer-controlled device called the Automated Parts Tray (APT). Using a short and simple QBasic program, APT demonstrates the principles of optimizing PC-board assembly. APT uses a stepper-controlled rotating parts bin along with a graphical display of PC-board component locations to help ensure that the right parts are inserted in the right spots on the board in optimal order of assembly.

APT can handle boards up to 6 x 8 inches. In addition, the project can be expanded easily to include closed-loop control. Further, it can even be used as the basis for a mini PC-board drilling system. (Those enhancements will be presented in future articles.) Best of all, you don't need a lot of money or special mechanical skills. All key parts are readily available from a single, well-established mail-order source, and parts cost about \$30.

All about APT. APT is a simplified adaptation of a semi-automatic electronics manufacturing system that has been in commercial use for years. The system is semi-automatic in that an operator must manually pick up and insert each part, but the actual part and its location are automatically determined and displayed.

In the commercial version, a series of trays are stacked vertically, like pies in a dessert display in a diner. Each tray contains several bins. The mechanism is such that all bins but one are covered. The cover can be visualized as a pie from which one slice has been removed. The area of the removed slice corresponds to the exposed bin. Each bin contains a specific part (a 10K resistor, a 2N2222 transistor, and so on).

The PC board being assembled mounts in a holder in front of the operator. To prepare for a part to be inserted, an X-Y table under the PC board moves a solid-state light source (a high-intensity LED or low-intensity laser) directly under a hole in the PC board, where one lead of the part to be inserted will go. Then a parts tray rotates so the bin containing the correct part is exposed. The operator takes a part from the tray and inserts it into the position indicated by the lighted holes.

Our version contains one tray with twelve bins. However, the software can accommodate tray changes during parts insertion, thereby affording an unlimited number of bins. And instead of using a mechanically complicated X-Y table and solid-state light

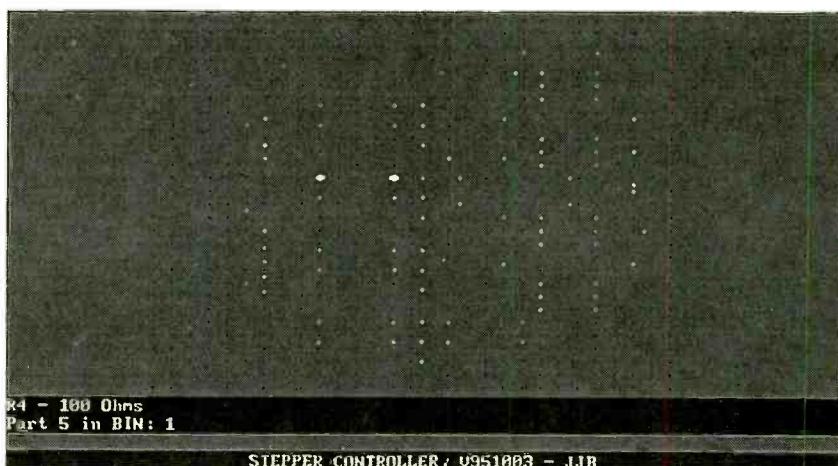


Fig. 1. The automated-parts-tray screen displays a grid overlaid with mounting holes for each component. The current component is highlighted.

source, our version displays a graphical replica of the PC board, all component holes, and a special representation of where the current part should be inserted. Figure 1 shows an example.

The mechanics of this project are quite simple, for two reasons. One is our use of an easily obtainable rotating "Lazy Susan" tray available anywhere kitchen products are sold. (We had good luck with a *Rubbermaid* brand tray.) Second is that we control tray movement using a direct-drive system, thereby eliminating the need for lead screws or gears. So let's get started.

The Stepper and Drive Circuit. The stepper motor is a two-phase, four-wire type. It consists of a permanent-magnet rotor and two field coils, as shown in Fig. 2. Table 1 lists the specifications for the selected motor. When the field coils are switched in the proper sequence, they attract the rotor, pull it to a precise position, and hold it there. By energizing coils A and B in the sequence shown in Table 2, the rotor will move precisely 7.5°, which amounts to 48 discrete steps through its rotation.

In Table 2, note that the four inner columns represent two things: The motor winding leads (A, A*, B, B*), and the PC parallel-port pin numbers that control those leads. Those numbers correspond to the pin numbers shown in the schematic (Fig. 3). Pin 2 represents the least-significant bit, and Pin 5 represents the most-significant bit. Column six of Table 2 shows the decimal value that should be written to the port to achieve the desired bit pattern for each step in the sequence.

As shown in Fig. 3, it doesn't take much in the way of electronics to drive a stepper. The circuit contains four identical functional blocks. The

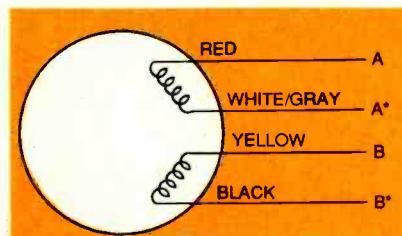


Fig. 2. A two-phase, four-wire stepper motor consists of a permanent-magnet rotor and two field coils.

TABLE 1—STEPPER MOTOR SPECIFICATIONS

Item	Description
Motor	Bipolar (2 phase) AIRPAX stepper motor (LB2773-M1)
Size	2.25 (D) × 0.99 (H) inches
Weight	0.61 lb
Electrical	5-volts DC, 800 mA, 6.25 ohms
Resolution	7.5 degrees/step
Shaft	0.25 (D) × 0.75 (L) inches
Mounting Holes	Two 0.2-inch mounting holes, spaced 2.6-inches apart
Torque	100 g-cm (detent), 1080 g-cm (holding)

TABLE 2—MOTION CONTROL SEQUENCE

STEP	A(5)	B*(4)	B(3)	A*(2)	Decimal
1	1	0	1	0	10
2	0	0	1	1	3
3	0	1	0	1	5
4	1	1	0	0	12

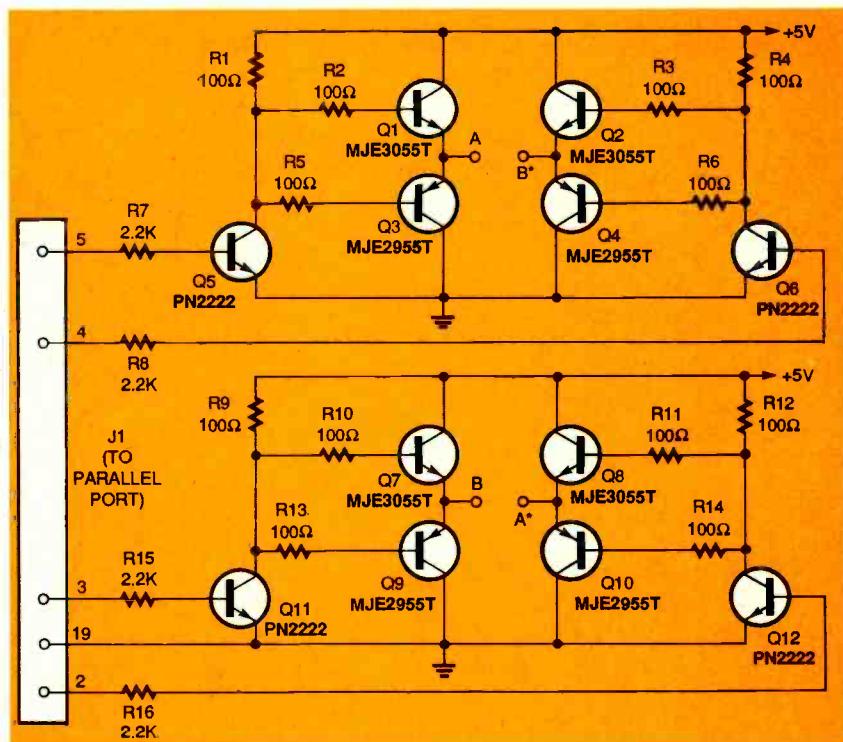


Fig. 3. The driver circuit allows a standard PC parallel port to alter the direction of current flow in both windings of the stepper motor according to the states of the four inputs.

purpose of each block is simply to provide a path from one end of a motor winding to either +5 volts or ground. By alternately switching the polarity of the voltage applied across the windings, we can cause motion to occur.

To see how that works, let's concentrate first on the block that controls the A lead. That block contains Q1, Q3, and Q5, along with the associated resistors. If pin 5 of J1 goes high, Q5 conducts, bringing its collector near ground. That in turn forward-biases

Q3, which brings its emitter near ground. Of course, V_{CE} of both Q5 and Q3 depends on the current being drawn by the load.

Now let's examine the block that controls the A* lead, including Q8, Q10, and Q12, and the associated resistors. If pin 2 of J1 goes low, the collector of Q12 goes high. That in turn causes Q8 to conduct, and Q10 to remain off. So, with A low and A* high, a current path has been established through Q8, coil A of the stepper motor, and Q3.


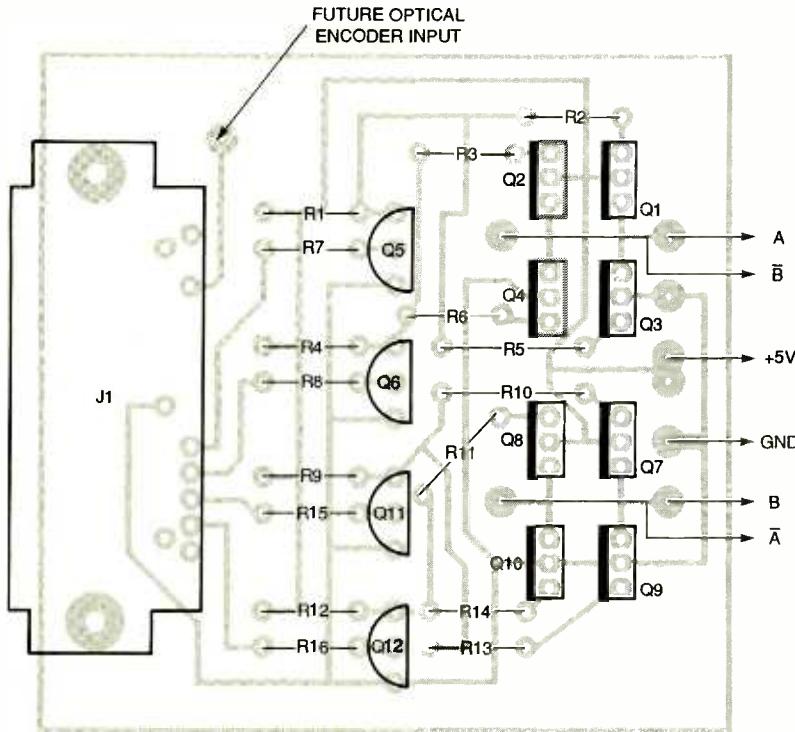


Fig. 4. Mount all components as shown here. A future installment will show how to use the optical encoder inputs.

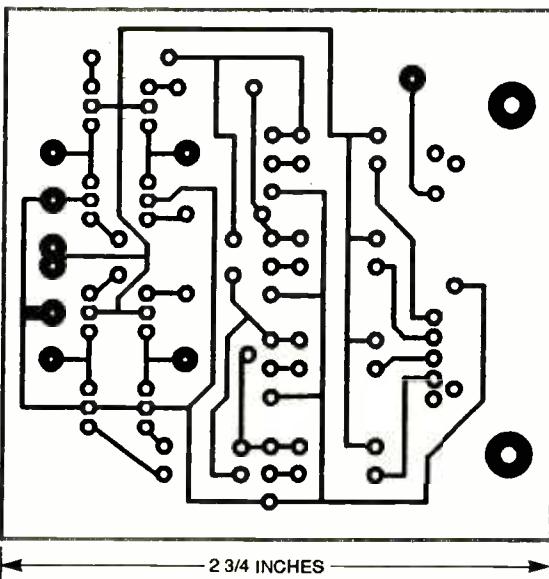

Use this foil-pattern when etching the PC board.

Moving the Stepper. By driving input pins 2–5 in the proper sequence, we can cause motion to occur. We've already seen the motion-control sequence in Table 2. The question now is how to deliver that sequence in a format acceptable to the motor. The code fragment in Listing 1 shows how. Note that we sequentially output the decimal values from column six of Table 2, with a delay of about 150 ms

after each. The delay is required to accommodate the mechanical inertia of the stepper motor. Without the delay, the control sequences would arrive from the PC so fast that the motor would simply sit there and chatter!

Power Considerations. Many stepper-motor control circuits use a current-limiting resistor to prevent excess-

LISTING 1— MOVING THE STEPPER

```

OUT 888, 10 : GOSUB DELAY
OUT 888, 3 : GOSUB DELAY
OUT 888, 5 : GOSUB DELAY
OUT 888, 12 : GOSUB DELAY
...
END

DELAY:
START1 = TIMER
WHILE (TIMER-START1) < 0.15 : WEND
RETURN

```

sive current from causing the motor to overheat. In our circuit, the relatively large current demand of the motor causes a measurable voltage drop across the power-providing transistors (in the preceding example, Q3 and Q8). Each will have a V_{BE} drop approaching 1 volt. Therefore, the stepper motor coil sees a net of only about 3 volts. With a coil resistance of 6.25 ohms, the current provided is then 3/6.25, or about 480 mA. That is well within the motor's dissipation capability, so no current-limiting resistor is required.

The tradeoff, of course, is that the motor provides less than maximum torque. That's acceptable in our application, but it might not be in others. You could increase torque by increasing the supply to six volts without modifying the circuit. You might be tempted to increase the supply to seven volts to offset the V_{BE} drops in the transistors and provide full power to the coils. That increase is not recommended, however, as you will exceed the motor's ability to dissipate heat, leading, naturally enough, to overheating.

We calculated current demand of each coil in this circuit configuration as about 400 mA. That implies that a 1-amp power supply should be sufficient. However, depending on the actual V_{BE} drops across the transistors, as well as variations in the motor coils, that value could increase to 1 amp or even more. To provide a margin of safety, we recommend use of a 1.5- or 2-amp power source.

There are many sources for new 5-volt, 1.5–2 amp power supplies. However, you can save a bundle by buying surplus. For example, some suppliers sell suitable power supplies for less than \$10. A potential draw-

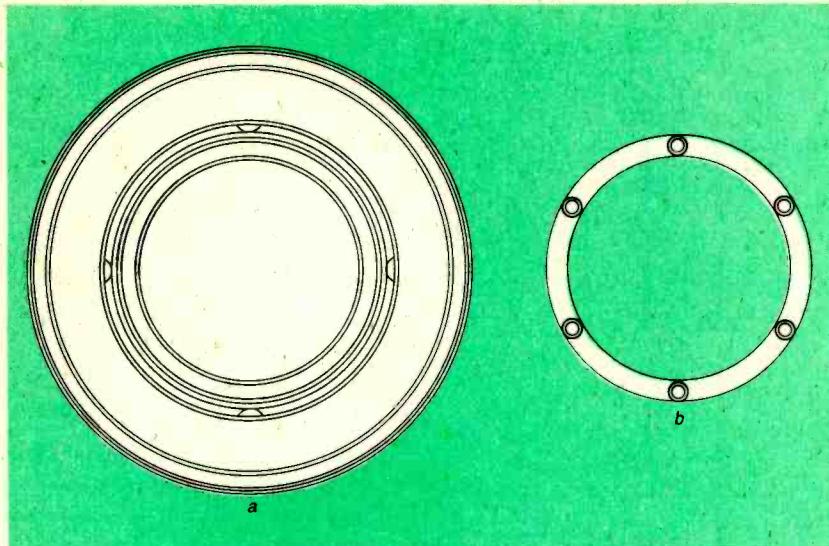


Fig. 5. The rotating tray—the complete assembly is shown in a, and the ball-bearing ring in b.

various diameters; to be consistent with our prototype, try to obtain one that has about a 10-inch diameter. Figure 5-a shows a bottom view of a typical tray. It has a concentric ring that is press-fit under four equally spaced tabs. Under the ring is a ball-bearing assembly, as shown in Fig. 5-b. Holding the tray firmly, distort the concentric ring so it can slip past one of the tabs. Then slide the ring free of the tray and discard the ring. Remove the ball-bearing assembly and save it.

Now we have to find the exact center of the tray. That is most easily accomplished with a center finder. If you don't have one, you can use a clear plastic protractor and a straight edge. As shown in Fig. 6, place the two corners of the protractor against the inside lip of the tray and draw a line

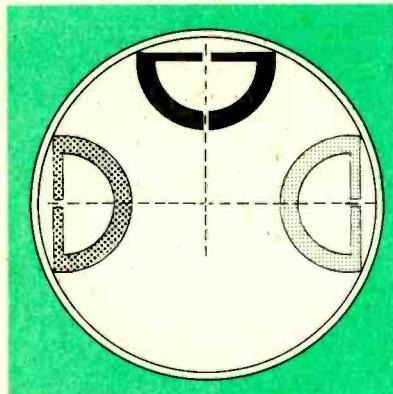


Fig. 6. Finding the center of the tray using a protractor and a straight edge; the point where the lines cross is the center of the circle.

back of that type of supply is that it may require a minimum load at all times. If that minimum isn't met, voltage may rise, for example, to about 5.3 volts. That presents no problem in our application.

Construction. Begin construction with the motor-control circuitry. A PC board layout accompanies this article; the parts-placement diagram appears in Fig. 4. Install the sixteen resistors first. Then install the eight TO-220 package transistors, ensuring both that you install the MJE3055s and MJE2955s in the right positions, and that they have the correct orientation. Next install the four TO-92 transistors (Q5, Q6, Q11, and Q12), again with the proper orientation. Now remove the connectors (if any) on the ends of the

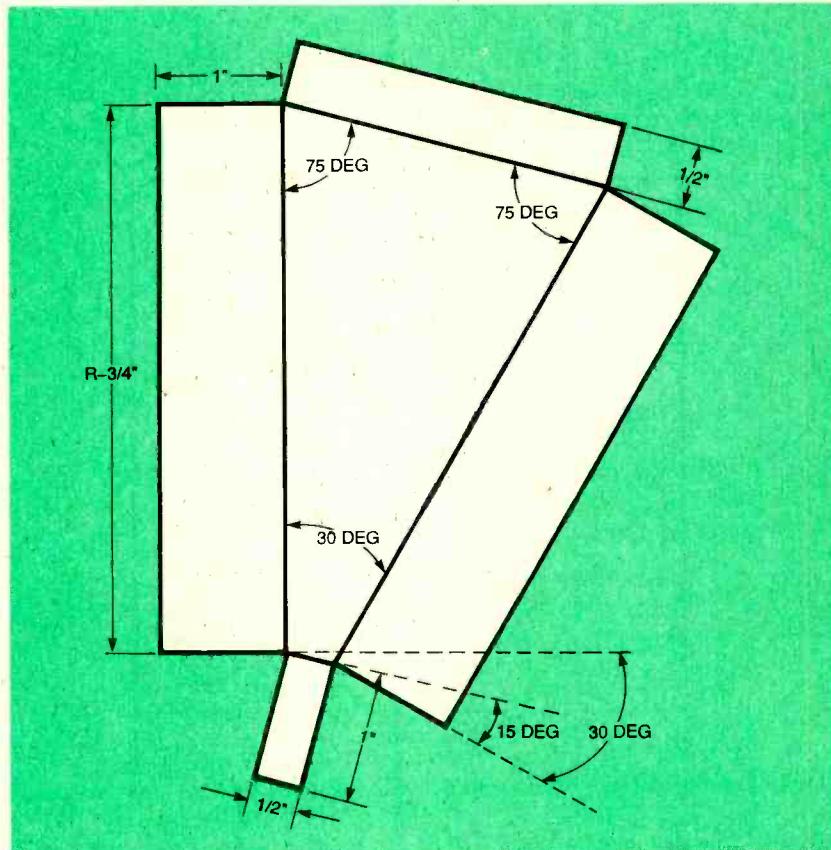


Fig. 7. Use this pattern to create the bins. The length of a side is given by the radius of the tray minus three-quarters of an inch. You'll need twelve of these.

stepper motor leads, and connect them to the appropriate points on the PC board. Attach the positive and negative power supply leads to the PC board.

Now let's look at the mechanics, starting with the tray. Trays come in

from the center marker on the straight portion of the protractor through the 90° indicator on the protractor's arc. Do the same thing at three or more locations on the tray. Where the lines cross is the exact center of the tray. (In geometric terms, each protractor

PARTS LIST FOR THE AUTOMATIC PARTS TRAY

R1-R6, R9-R14—100-ohm, $\frac{1}{4}$ -watt resistor
 R7, R8, R15, R16—220-ohm, $\frac{1}{4}$ -watt resistor
 Q1, Q2, Q7, Q8—MJE3055T NPN transistor, TO-220 case
 Q3, Q4, Q9, Q10—MJE2955T PNP transistor, TO-220 case
 Q5, Q6, Q11, Q12—PN2222 NPN transistor, TO-92 case
 J1—DB-25 connector, female, PC-mount
 5-volt DC, 6.25-ohm coil, bipolar stepper motor (Airpax LB82773-M1; JAMECO 117954 or equivalent); PC board; 5-volt/2-amp power supply (JAMECO 107326, 109276, or equivalent); 2.5-mm female power jack; 2.5-mm male power plug; Universal shaft coupler (JAMECO 106606 or equivalent) (2); Rubber coupler (JAMECO 106622 or equivalent); "Lazy Susan" tray (Rubbermaid or equivalent, 10-inch diameter); $\frac{1}{4}$ -20 \times 1 $\frac{1}{2}$ -inch machine bolt; $\frac{1}{4}$ -20 nut (2); 1 $\frac{1}{4}$ \times 4-inch aluminum or plastic panel; #4 sheet metal screws (4); #6 or #8 sheet-metal screws (2); 24 \times 36-inch piece of "Oaktag" or poster paper; $\frac{1}{2}$ -inch plywood; $\frac{1}{4}$ -inch Luan mahogany plywood; glue, nails, DB-25 extension cable, solder, wire, etc.

Note: The following are available from James J. Barbarello, 817 Tennent Road, Manalapan, NJ 07726: PC Board; APT-PC (\$12.00). Software including source and executable code for all software in the series, sample data files, and an enhanced version of the APT software (including the optical encoder application); APT-S (\$12.00). All prices include shipping. International orders add \$5.00 (U.S. funds only). NJ residents must add appropriate sales tax. The author will accept phone calls 6-8:00 PM EST., Monday through Friday **ONLY** (908-536-5499). The author will gladly answer written questions if accompanied by a self-addressed stamped envelope.

edge is a chord, and the line you draw is a perpendicular bisector of that chord. Perpendicular chord bisectors are, by definition, along a radius, and therefore cross the circle's center).

Drill a $\frac{1}{4}$ -inch diameter hole in the

LISTING 2—STEPPER CONTROL PROGRAM

```

REM** STEPPERS.BAS (c) 1995, JJ Barbarello
REM** V951007
CLS : DEF SEG = 64: DEFINT A: add = 888
DIM a(4): a(1) = 5: a(2) = 3: a(3) = 10: a(4) = 12
abinold = 1: ainit = 12: OUT add, ainit
COLOR 15, 1: LOCATE 2, 1: PRINT SPACE$(79)
LOCATE 2, 26: PRINT "APT STEPPER CONTROLLER TESTER"
COLOR 7, 0: LOCATE 10, 20: PRINT "Position Tray At Bin 1, then press Enter"
waitforenter:
a$ = INPUT$(1)
IF a$ <> CHR$(13) THEN SOUND 800, 1: SOUND 500, 1: GOTO waitforenter
LOCATE 10, 20: PRINT SPACE$(40)
loop01:
LOCATE 10, 27: PRINT "TRAY CURRENTLY AT BIN: "; abinold
LOCATE 20, 10: PRINT SPACE$(60)
LOCATE 20, 23: LINE INPUT "Which Bin (1-12, Enter to end)... "; abin$
IF LEN(abin$) = 0 THEN END
abin = VAL(abin$): IF abin < 1 OR abin > 12 THEN BEEP: GOTO loop01
abin2 = abin: IF abin2 < abinold THEN abin2 = abin2 + 12
asteps = abin2 - abinold
SELECT CASE asteps
    CASE 1 TO 6
        lo = 1: hi = 4: steps = 1
    CASE IS > 6
        lo = 4: hi = 1: steps = -1: asteps = 12 - asteps
    CASE IS < 0
        lo = 4: hi = 1: steps = -1: asteps = -asteps
END SELECT
OUT add, ainit
bin = abinold
FOR i = 1 TO asteps
    FOR j = lo TO hi STEP steps
        OUT add, a(j)
        IF i > 1 AND i < asteps THEN delay = .075 ELSE delay = .125
        start! = TIMER
        WHILE (TIMER - start!) < delay: WEND
    NEXT j
    bin = bin + steps
SELECT CASE bin
    CASE IS = 0
        bin = 12
    CASE IS = 13
        bin = 1
    CASE ELSE
END SELECT
LOCATE 10, 27: PRINT "TRAY CURRENTLY AT BIN: "; bin; SPACE$(2)
SOUND 625, 1
NEXT i
IF steps = -1 THEN
    OUT add, a(lo)
    ainit = a(lo)
ELSE
    ainit = a(hi)
END IF
start! = TIMER
WHILE (TIMER - start!) < 1: WEND
OUT add, 0
abinold = abin
GOTO loop01
END

```

center of the tray. Obtain a $\frac{1}{4}$ -20 machine screw at least 1 $\frac{1}{2}$ -inch long, and two $\frac{1}{4}$ -20 machine nuts. Thread

one nut on the screw and insert the screw into the drilled hole from the top of the tray. Now thread the other

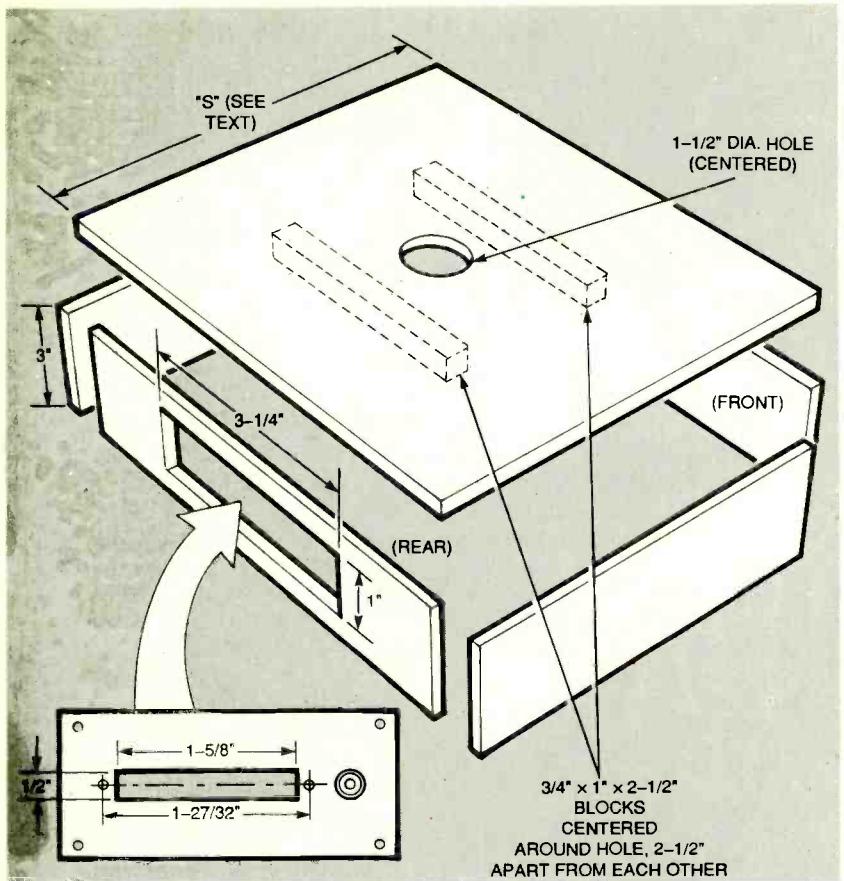


Fig. 8. One-half inch plywood serves well in building the case. The blocks on the underside hold the stepper motor, and the slot in the rear panel is for a mounting plate that connects power and the parallel port.

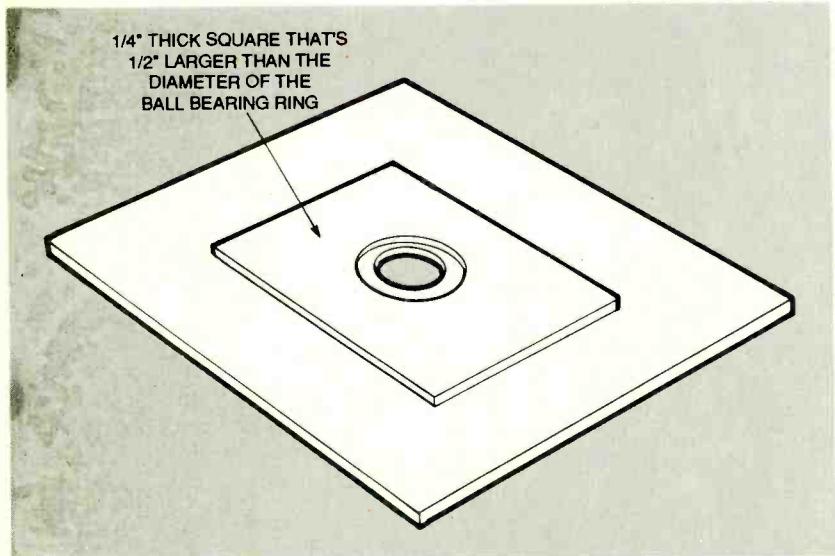


Fig. 9. The spacer provides clearance for the shaft-coupling mechanism.

nut onto the screw, locking it in place. Do not tighten the nuts at this point, as the protruding length of the screw will be adjusted later.

The next task is to make the twelve bins. Figure 7 shows a pattern for one

bin. Note that all dimensions are constants, except the length, which is defined as $R - \frac{3}{4}$ -inch. Measure the inside diameter of the tray and divide by two to obtain the radius. For example, the author's prototype used a

10½-inch diameter tray, and $10\frac{1}{2}/2 - \frac{3}{4} = 4.5$ -inches. You can make the bins from thin aluminum, wood, plastic, or other materials. An effective alternative is poster paper (commonly called "Oaktag" paper). It's easy to work with, has the thickness of about five normal sheets of paper, and is stiff enough to hold the required bends.

Using the length calculated for your tray, cut twelve blanks. Fold the four flaps upward, being careful to fold them straight and along the lines indicated on the pattern. Secure the tabs with transparent tape. When all twelve bins are complete, arrange them in a circle and secure them to one another where they meet with additional transparent tape. With careful assembly, the bins should fit snugly into the tray. However, an exact fit isn't necessary. The requirement is for twelve approximately equal bins in an assembly that won't rotate inside the inner lip of the tray.

Building the Case. Now we're ready to build the case. We used ½-inch plywood for our prototype. Form a square box with a closed top and an open bottom, as shown in Fig. 8. Side dimension S should be ½-inch larger than the outside diameter of the tray, plus twice the thickness of the material you're using for the case top cover. For example, with our 10½-inch tray and ½-inch plywood for the cover, $S = 10.5 + 0.5 + 2 \times 0.5 = 12$ inches.

A good material for the box top is ¼-inch luan mahogany plywood. Draw a line through diagonal corners and mark the point where the lines cross. Draw a line through the center perpendicular to the sides. Draw two parallel lines on either side of that one, each 1¼-inch from the first line. You should end up with two lines straddling the centerline of the top, and 2½-inches from each other.

Drill or otherwise form a 1½-inch hole at the center of the top. The actual diameter or shape is not critical, as long as the opening is at least 1 inch in diameter. Now prepare two ¾ × 1 × 2½-inch blocks. Attach the two blocks to the underside of the top and along the two parallel lines drawn previously. Screw or glue the blocks in place.

Measure the diameter of the ball-bearing assembly (BBA) shown in Fig. 5-b. Add ½-inch to that amount, and

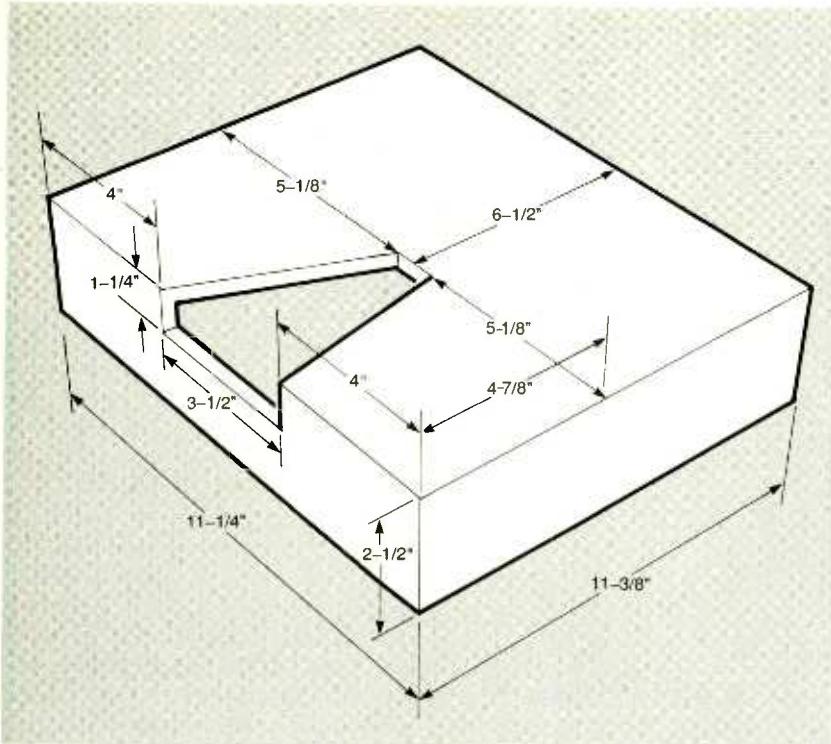


Fig. 10. The top cover is the same size as the base, and has a wedge-shaped cutout to allow access to the current bin.

call it L. Cut a piece of $\frac{1}{4}$ -inch material into a square, with sides of length L, to form a spacer. Form a $1\frac{1}{2}$ -inch opening similar to that formed in the top and secure the spacer to the top of the case. Align the BBA to the spacer so it is concentric with the center hole, as shown in Fig. 9. After that's done, staple or otherwise attach the BBA to the spacer.

Create a centered rectangular opening $1 \times 3\frac{1}{2}$ inches in the rear side as shown. Then make a cover of plastic or metal and mount J1 to the cover. Also mount a power connector, and attach the cover to the rear panel with #4 sheet metal screws.

Using the value of S calculated earlier, build a cover, as shown in Fig. 10. The height should be $2\frac{1}{2}$ inches. Do not drill a center hole; instead, form a wedge-shaped cutout as shown in Fig. 10. Using a 30-60 triangle, draw two lines from the center to one end, forming a pie shaped wedge. Fatten the wedge by drawing lines parallel to the first two lines, but $\frac{1}{4}$ -inch farther out. Extend the two lines down the front side and then connect them, forming a rectangle. Then, to trim the sharp edge of the wedge, draw a line $\frac{3}{4}$ -inch from the center. Cut out the wedge.

Final Assembly and Checkout. To finish up we need to mount the stepper motor and connect its shaft to the $\frac{1}{4}$ -20 bolt with a flexible coupling. Start by centering the tray on the case bottom. Hold it in place temporarily with masking tape. Position the motor against the blocks with the shaft of the motor facing the bolt. If the motor has a gear attached, remove and discard it. Adjust the bolt's depth as necessary so it and the shaft almost touch. Position the motor so the bolt and shaft are concentric, and mark the position of the two mounting holes. Attach the motor to the blocks with #6 or larger sheet-metal screws. Remove the masking tape.

Attach one shaft coupler to the motor shaft, and another to the bolt. Place a rubber coupler in one of the shaft couplers, and loosen the nuts holding the bolt. Mate the two couplers. Adjust the bolt depth so the tray floats $\frac{1}{16}$ to $\frac{1}{8}$ -inch above the BBA. The object is to minimize drag, but allow the bearings to come into use if the tray tips slightly from uneven weight distribution. Tighten the nuts to secure the bolt.

Attach the power connector and the DB-25 connector to the parallel port of your PC using an appropriate

cable. Mark the front flap of one of the bins as "1," and place numbered slips of paper in each bin, beginning with bin 1 and going counter-clockwise. Place the bin assembly in the tray so bin 1 is accessible through the wedge cutout in the top.

Type the test program shown in Listing 2 into QBasic. Center bin 1 in the opening and run the program. As you select different bins, the tray should rotate to show the appropriate bin through the opening.

That's it for this installment. Next time, we'll present the general-purpose APT program, show how to create the AS-CLI data file for a PC board, and use the program to populate the stepper controller's own PC board. We'll also show how to add an optical encoder that can provide position feedback for the stepper motor.


Ω

ANTIQUE RADIO CLASSIFIED Free Sample!



Antique Radio's
Largest Circulation Monthly
Articles, Ads & Classifieds.
6-Month Trial: \$18.95. 1-Yr: \$36.95 (\$53.95 1st Class).
A.R.C., P.O. Box 802-L17, Carlisle, MA 01741
Phone:(508) 371-0512 VISA/MC Fax:(508) 371-7129

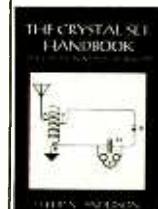Get your copy of the CRYSTAL SET HANDBOOK




Go back to antiquity and build the radios that your grandfather built. Build the "Quaker Oats" type rig, wind coils that work and make it look like the 1920's! Only **\$10.95** plus **\$4.00** for shipping and handling. CLAGK Inc., P.O. Box 4099, Farmingdale, NY 11735. USA Funds ONLY! USA and Canada—no foreign orders. Allow 6-8 weeks for delivery. MA01

THE COLLECTED WORKS OF MOHAMMED ULLYES FIPS

#166—By Hugo Gernsback. Here is a collection of 21 April Fools Articles, reprinted from the pages of the magazines they appeared in, as a 74-page, $8\frac{1}{2} \times 11$ -inch book. The stories were written between 1933 and 1964. Some of the devices actually exist today. Others are just around the corner. All are fun and almost possible. Stories include the Cordless Radio Iron, The Visi-Talkie, Electronic Razor, 30-Day LP Record, Teleyglasses and even Electronic Brain Servicing. Get your copy today. Ask for book #166 and include **\$16.00 (includes shipping and handling)** in the US and Canada, and order from CLAGK Inc., P.O. Box 4099, Farmingdale, NY 11735-0793. Payment in US funds by US bank check or International Money Order. Allow 6-8 weeks for delivery.

MA05

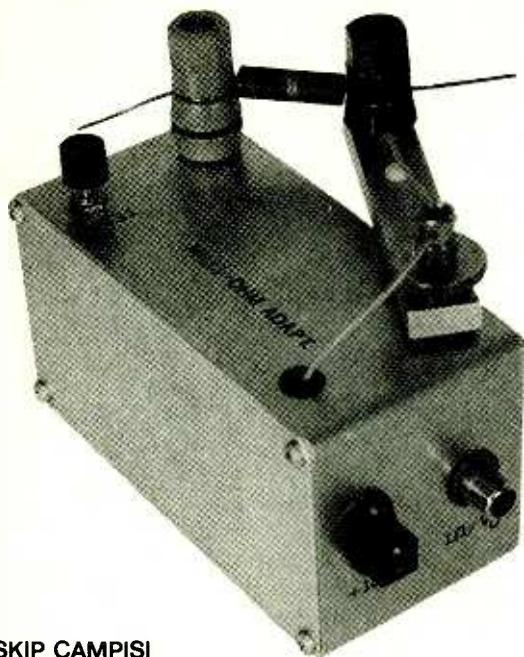

SKIP CAMPISI

Have you ever tried to measure accurately a low-value resistance, only to find that your test leads had a higher resistance than the device you were measuring? Even with a meter capable of *nulling* out the lead resistance, the null is never stable due to the hooks or clips used for the connections.

The Milliohm Adapter was specially designed to get around that problem and to do it with an accuracy of $\pm 1\%$ for readings over a range of 10 milliohms (0.01 ohms) to 5.0 ohms. Used with a 4½-digit DVM, the adapter can resolve resistances as low as 10 microohms, and be able to measure the resistance of a short length of hookup wire! Checking switch-contact resistance is a breeze with the adapter plugged into your DVM.

When measuring a resistance below 1.0 ohm, the leads of a resistor contribute significant error to the reading. Thus, a novel circuit approach was taken in designing the adapter. To generate an output-signal voltage high enough to be measured easily, a current of about 1.0 ampere is desirable. That current could easily fry some circuit components and damage the unit under test. However, by applying a low duty-cycle, 1.0-ampere pulse, no damage will occur. By using Kelvin voltage sensing probes right at the connections to the resistance, all of the other voltage

drops due to the 1.0-ampere pulsed current in the other leads are essentially eliminated.

About the Circuit. The schematic diagram (Fig. 1) for the adapter can be partitioned into four sections: power supply, oscillator, current source, and peak detector. The R_x (resistance to be measured) is connected between BP1 and BP2, and with the 1.0-ampere pulse applied to R_x , the resulting output transfer function appearing at J1 is 1.0 ohms-per-volt output to the DVM.

The power supply consists of IC2, a 78L12 voltage-regulator chip that provides regulated +12 volts to the circuit, and a 2N2222 transistor, Q2, which provides -0.7 volts to IC3 and a virtual power ground to the rest of the circuit. Transistor Q2 is used as a diode-connected transistor; that type produces only half of the ripple voltage that would appear if a standard rectifier were used. Battery B1 is user selectable and, although 18 volts is specified in the schematic diagram, it also can be any voltage source from 15-volts DC to 25-volts DC. For example, two series-connected 9-volt batteries will power the adapter quite nicely. Further, note that the prototype shown in the photos does away with B1 entirely; it uses a 117-volt AC power-pack adapter rated at 17.4-volts DC at 50 mA plugged into a jack on the instrument. Power switch S2 was not used on the prototype.

Build This MILLI-**OHM** ADAPTER

Extend the range of your DMM down to the milliohm level with this inexpensive, easy-to-build adapter.

A TLC555 CMOS timer, IC1, is configured as an astable multivibrator operating at a frequency of about 100 Hz. The components used provide a duty-cycle of 99%; thus, a negative-going pulse of about 100 μ s results at the output, which in turn gates (switches) the current source on for 100 μ s at a duty-cycle of 1%. The resulting average current is 10 mA—safe for almost all circuits and circuit elements.

Light-emitting diodes LED1 and LED2 are standard red LEDs that have a forward voltage of about 1.75 volts each, and they are used as the voltage-reference diodes. As Q1 (a TIP125) has a forward voltage of about 1.5 volts, about 2.0 volts appears across R2 and R3, whose net resistance is 2.0 ohms; thus, a current pulse of 1.0 ampere is generated at Q1's collector. The current pulse is supplied via a capacitive-discharge type set-up, from C1 (100 μ F), which is recharged via R1 (33 ohms) during the 99% off state.

Adequate compensation for any temperature drift by Q1's two base-emitter junctions are provided by LED1 and LED2, and calibration is provided via CAL potentiometer R4, which adjusts the LEDs' forward voltage by varying the bias current. The prototype adapter uses a one-turn potentiometer for R4; you might wish to use a multi-turn trimmer instead. Also, you can trim fixed resistors R2 and R3 to adjust into R4's calibration range.

The TLC272 CMOS dual op-amp, IC3, is configured as a positive voltage-peak detector, which converts



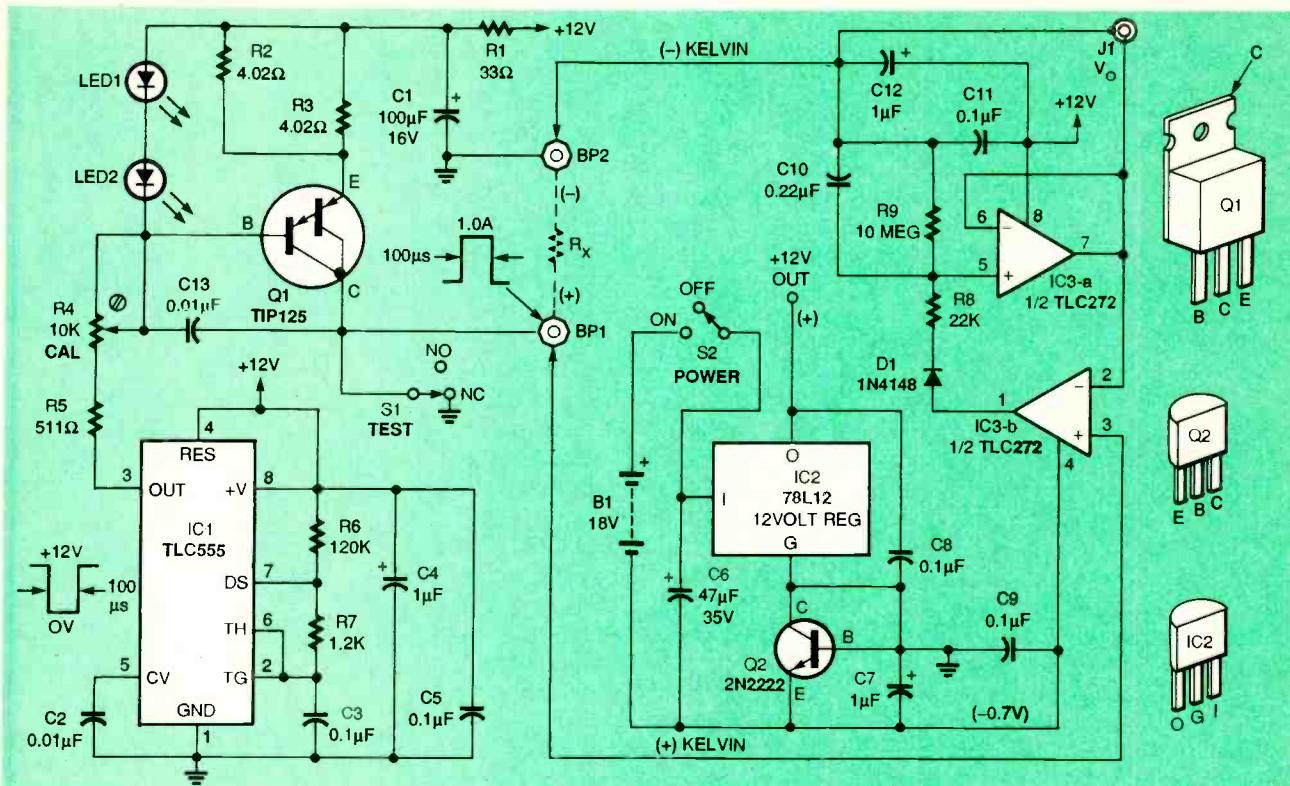


Fig. 1. Here's the schematic diagram for the Milliohm Adapter. The circuit can be separated into four sections: power supply, oscillator, current source, and peak detector.

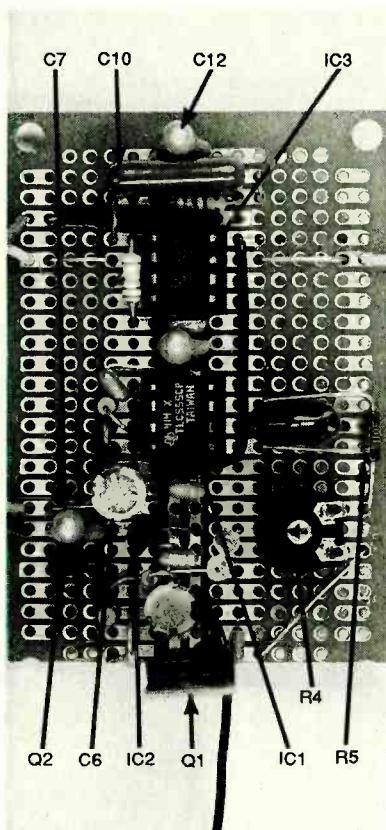

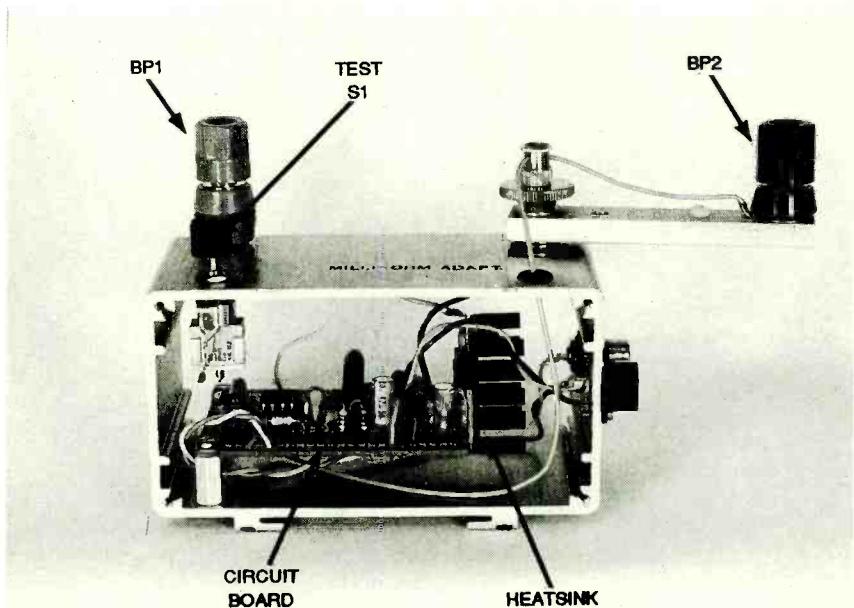A piece of a PC board that matches a solderless board supports most of the circuit's parts. Layout is not critical; however neatness is important.



A view of the Milliohm Adapter before the side covers are installed. Note that the heat sink has been attached to the Darlington transistor Q1 and stands free of any metallic contact.

the 1% duty-cycle voltage pulse generated across "R_x" to a steady DC voltage having the exact magnitude of the pulse's peak voltage value. Thus, the output at J1 is a DC voltage with the transfer function of 1.0-ohm-per-volt across R_x.

Construction. The only critical sections of the adapter are the binding-post connections to the resistance to be measured. Use a pair of jumbo (5-way) binding posts rated for 15 amps or more; the posts specified in the Parts List have large-area gold-plated

contacts that make the physical and electrical securing of "R_X" very good. Once you have selected the binding posts, the next thing you must decide is how to mount them. The spacing between BP1 and BP2 must be mechanically variable to allow easy adjustment for various resistor sizes, wire lengths, etc.

The best method for mounting the binding posts is to leave the positive terminal (BP1) fixed, and have the negative ground terminal (BP2) movable. There are three different options to accomplish this: leave BP2 dangling from its leads without any mechanical mount; cut a slot in your cabinet so that BP2 can slide back and forth in the slot; or mount BP2 on an arm that pivots on a stud, thus rotating away from BP1 for adjustment. The last method was used for the prototype. Pick any of the methods and mount the binding posts so that they are level with each other, using shims or washers where needed. Be sure to insulate BP1 from the cabinet (which has to be aluminum), while BP2 should

be electrically connected to the cabinet.

The prototype uses a cabinet made from extruded aluminum having a $\frac{3}{32}$ -inch thick wall for drilling and tapping for machine-screw attachments. For chassis boxes made from aluminum sheet metal, you can use ordinary machine screws, lock washers, and nuts.

The prototype cabinet measures 2-inches wide by $4\frac{1}{8}$ -inches long by $2\frac{1}{8}$ -inches high. Binding post BP1 is mounted at one end of the cabinet top, with a 10-32 \times 1-inch screw protruding out of the other end. On this stud rides the swing arm, which is made from a piece of $\frac{1}{4}$ -inch thick by $\frac{5}{8}$ -inch wide by 3-inch long aluminum bar. One end of the arm has a clearance hole for the 10-32 stud, and BP2 is mounted at the other end, along with a lug for the Kelvin connection. The arm rides on washers and is locked in place with a $\frac{3}{4}$ -inch diameter, 10-32-thread knurled nut (a wing nut works fine, also). At its closest position, the binding post terminal spacing is

PARTS LIST FOR THE MILLIOHM ADAPTER

SEMICONDUCTORS


- IC1—TLC555 or TLC555CN CMOS timer integrated circuit.
- IC2—78L12 12-volt, 100-mA, positive-regulator integrated circuit
- IC3—TLC272/TS272CN CMOS dual op-amp, integrated circuit
- Q1—TIP125 PNP Darlington transistor
- Q2—2N2222 PNP general-purpose transistor
- D1—1N4148 switching diode
- LED1, LED2—Light-emitting diode, red, T1 case

RESISTORS

- (All fixed resistors are $\frac{1}{4}$ -watt, 5% units, unless otherwise noted.)
- R1—33-ohm
- R2, R3, R_C—4.02-ohm, 1%, metal film
- R4—10,000-ohm, one-turn potentiometer, PC mount, cermet (see text)
- R5—511-ohm, $\frac{1}{4}$ -watt, 1%, metal-film
- R6—120,000-ohm
- R7—1200-ohm
- R8—22,000-ohm
- R9—10,000,000-ohm

CAPACITORS

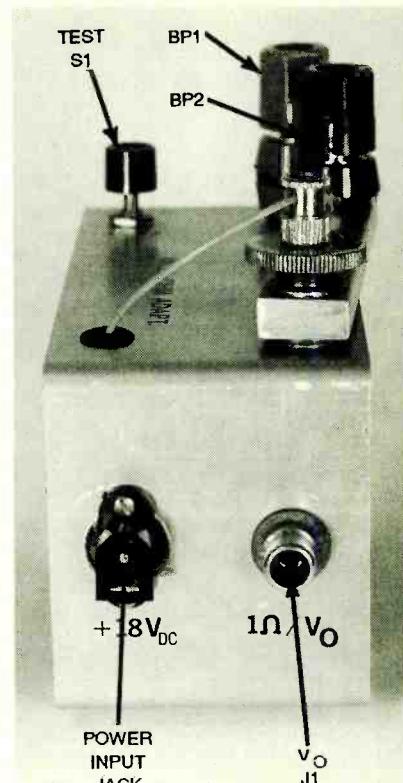- C1—100- μ F, 16-WVDC, electrolytic
- C2, C13—0.01- μ F, monolithic ceramic



The power input jack (optional, see text) and insulated RCA phono jack (J1) that supplies the output signal to the DVM mounts on one side of the case

about $\frac{3}{4}$ inch apart, which can be opened to a maximum of about $5\frac{1}{2}$ inches. Output jack J1 and an optional power-input jack are mounted on one end of the cabinet with normally-closed push-button switch S1 (test) mounted on the top, near BP1. Jack J1 has to be isolated from ground. Use fiber shoulder washers or an insulated phono jack made for the purpose. If you use POWER switch S2, mount it near S1 for the most convenience.

Assemble the circuit board, following the parts location shown in the photos, on a $1\frac{1}{8}$ -inch by $2\frac{1}{8}$ -inch circuit board (see Parts List) starting with Q1 on one end of the board. Attach a small heat sink to Q1. Install two 8-pin DIP sockets and potentiometer R4 as shown; then add the rest of the components and interconnects leaving long leads for connecting the jacks and switches. The positive Kelvin lead is a separate wire connected directly from pin 3 of IC3 to binding-post BP1, and the collector tab of Q1 is also connected directly to BP1 via a separate wire.

(Continued on page 79)

*Get picture-perfect results
every time with this easy-to-build,
easy-to-use darkroom aid.*

MICHAEL A. COVINGTON

BUILD A ZONAL ENLARGING METER

Most enlarging exposure meters tell you how many seconds to expose print paper. The Zonal Enlarging Meter described here does not! Instead, it tells you how light or dark each area of the picture will turn out, based on a selected standard exposure time for your enlarger.

When in the photo darkroom, you position the Zonal Enlarging Meter with one hand and adjust the lens

opening of the enlarger with the other hand. The exposure setting technique using the Zonal Enlarging Meter is much faster than twisting the dials on a conventional enlarging meter and it assists in obtaining a correctly exposed enlargement that fits all the brightness zones of the negative into the response range of print paper, from stark white to jet black. Ordinary enlarging meters measure only one zone which is usually a high-

light or skin tone, and just guess where the other zones will fall. The Zonal Enlarging Meter lets you measure any area of the enlarger's project image on the paper surface and adjust the lens opening until that area is as light or as dark as you want it to be.

How it Works. The heart of the Zonal Enlarging Meter circuit (Fig. 1) is a National Semiconductor LM3915 LED bargraph driver IC, which lights any-

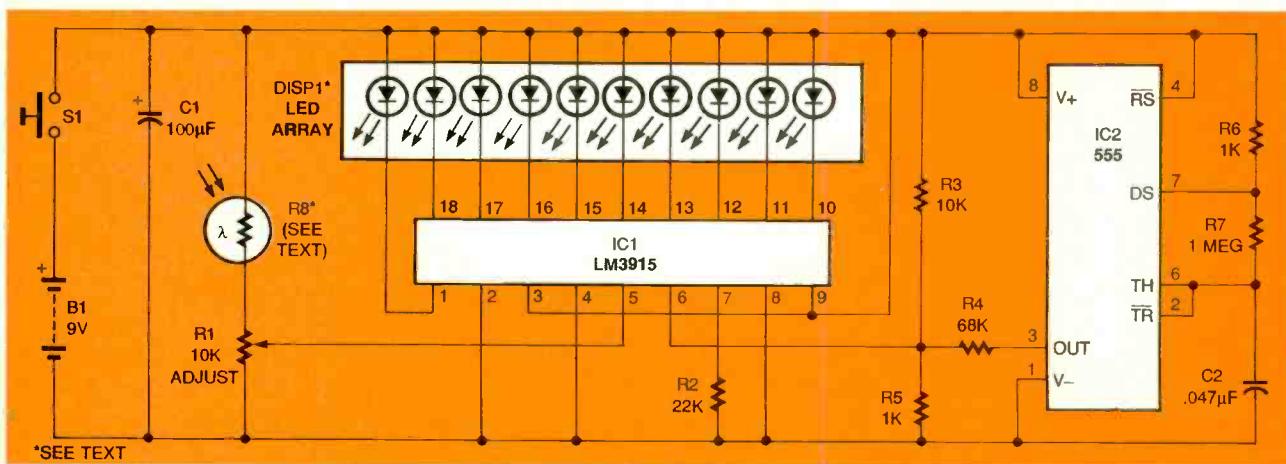


Fig. 1. Here's the schematic diagram for the Zonal Enlarging Meter. Light falling on photoresistor R8 causes LEDs in the bar-graph display DISP1 to illuminate. The number of LEDs that come on is logarithmically proportional to the light intensity.

where from 0 to 10 LEDs depending on the ratio of the input voltage on pin 5 to the reference voltage on pin 6.

The trigger voltages for the LEDs in bar-graph display (DISP1) are arranged along a logarithmic scale, just like photographic exposures, and the total voltage range is 10 to 1. Because of some nonlinearity in the photoresistor's response to light-intensity change, the range of light levels that the meter actually covers is more like 30 to 1, which is ideal because it slightly exceeds the density range of a properly exposed negative.

Each LED in DISP1's bargraph display has three states, off, flashing, and fully on; that feature lets you read a total of 20 steps rather than just 10. The flashing effect is produced by the 555 oscillator (IC2), which makes the reference voltage at pin 6 of IC1 fluctuate

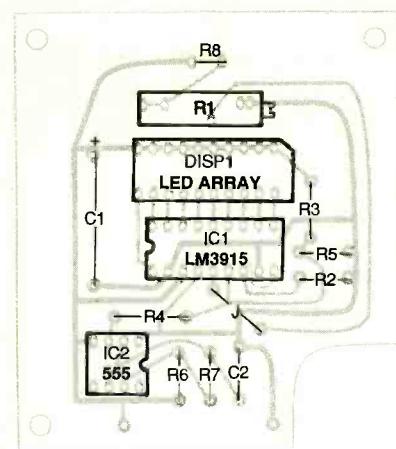


Fig. 2. Parts location diagram shows that the PC board is uncluttered and easy to assemble. Mounting holes align with the screws used to close the plastic case.


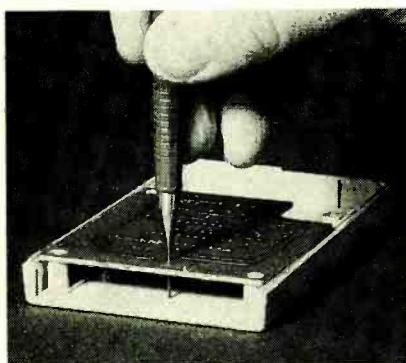


Fig. 3. Prior to inserting parts onto the PC board, extend the lead of an automatic pencil through the holes in the board to locate openings in the case cover for the LED bar-graph display DISP1 and photoresistor R8.

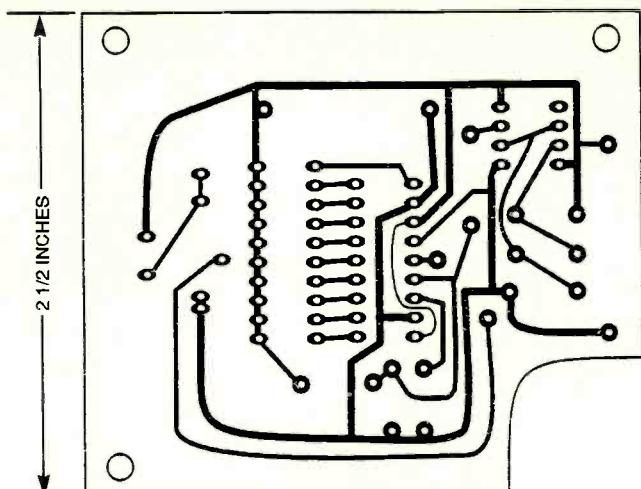

Same-size foil-pattern diagram for the meter's PC board. Carefully drill holes so that integrated-circuit chips and display chip mount quickly.

PARTS LIST FOR THE ZONAL ENLARGING METER

SEMICONDUCTORS

DISP1—10-LED bar-graph display, red (Mouser 351-2402 or equiv.)
IC1—LM3915 LED logarithmic-bargraph driver integrated circuit (National Semiconductor)
IC2—555 timer-oscillator integrated circuit

RESISTORS

(All fixed resistors are $\frac{1}{8}$ -watt, 5% units.)

R1—10,000-ohm, 10-turn, $\frac{3}{4}$ -to 1-inch long, trimmer potentiometer
R2—22,000-ohm
R3—10,000-ohm
R4—68,000-ohm
R5, R6—1,000-ohm
R7—1-megohm
R8—Cadmium sulfide photoresistor (see text and note below).

ADDITIONAL PARTS AND MATERIALS

B1—9-volt transistor-radio battery
C1—100- μ F, 16-WVDC, electrolytic capacitor
C2—0.047- μ F, ceramic capacitor
S1—Normally-open, momentary-contact, push-button switch
Plastic-case enclosure (includes battery connector; Pac-Tec HML-9VB. RadioShack 270-211, or equiv.), PC circuit-board material as needed (see text), wire, solder, etc.

NOTE: A suitable photoresistor, type 76C59, is available from Mouser Electronics, 2401 Highway 287 North, Mansfield, TX 76063, phone 800-346-6873.


so that an LED that is just on the verge of turning on will flash. To simplify the circuit, you can leave out this flashing

feature by omitting IC2, R4, R6, R7, and C2.

Choosing a Photoresistor. The choice of cadmium sulfide photoresistor (R8) used in the meter depends on what is available and what kind of paper and exposure time you like to use. You'll need one whose resistance is somewhere between 50K and 500K at the light level corresponding to a mid-gray tone in a picture printed on your paper with your exposure time.

One commercially available photoresistor that works well is the type 76C59 available from Mouser Electronics (see the Parts List). It's rated for a resistance of 20K to 50K ohms at a light intensity of 10 lux (1 foot-candle), and 20 megohms in total darkness. The light level for a mid-gray tone in a 5-second exposure on most fast enlarging papers is about 1 lux; at that light level, this photoresistor has a resistance of about 300K.

Another way to get a suitable photoresistor is to buy a surplus assortment and test the photoresistors until you find a suitable one. The testing procedure is simple. First, reject any photoresistors whose resistance in total darkness is less than 2 megohms, or which take more than a few seconds to stabilize when placed in darkness after exposure to room light. One way to put a photoresistor into total darkness is to wrap it in several layers of black cloth, plastic, or electrical tape. Avoid aluminum foil; it reflects light and tends to develop cracks that will throw your readings awry.

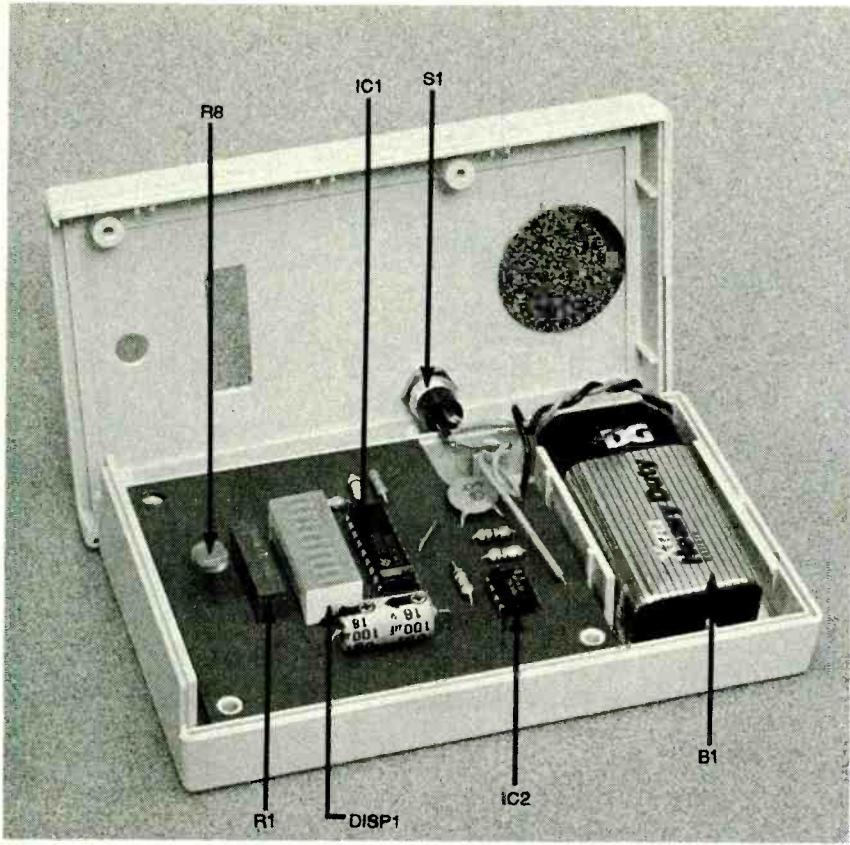

The Zonal Enlarging Meter with PC circuit board and battery B1 in position just prior to closing the plastic case. Note the holes cut for the photoresistor R8 and LED bar-graph display DISP1. The photoresistor is mounted above the PC board to be flush with the inside surface of the case's cover.

Next, set up your enlarger to make a properly exposed print on your usual paper with your usual exposure time. Then put the photoresistor on a mid-gray area of the projected image, turn off the safelight, and measure the resistance. If it's between 50K and 500K, and the resistance in total darkness is at least 10 times higher, you have a workable photoresistor. If the photoresistor's test measurements are outside that range specified above, you can still use the photoresistor by substituting a different value for R1. The resistance of R1 should be about 1/50 to 1/2 that of the photoresistor.

Putting it Together. The Zonal Enlarging Meter is housed in a Pac-Tec HML-9VB plastic enclosure (see Parts List). The illustration of the foil-side pattern of the printed-circuit board provided is same-size and can be used to produce a PC board using any of the photographic techniques available. You can assemble the project equally well on perfboard or a universal, pre-drilled circuit board. The parts loca-



Here's the Zonal Enlarging Meter all closed up and ready for use.

tion diagram in Fig. 2 should be followed closely no matter what circuit board you use.

The photograph in Fig. 3 shows how to locate the holes for the photoresistor and the LED display in the plastic case cover once you've made the circuit board. To cut the rectangular opening for the LED bar-graph display (DISP1) in the case, drill

holes in the corners directly over the display, then join them with a jeweler's saw if you have one. If you don't have a jeweler's saw, simply drill more holes until you have an approximately rectangular opening. Either way, finish the hole carefully with a file. Even though it is not attached to the hole in the cover, the photoresistor should stand up high enough on its leads so that it doesn't pick up stray light from the LEDs.

Calibration. Set up your enlarger to make a properly exposed print with your usual paper and exposure time. Place the meter on a mid-gray area of the image, turn off the safelight, and press S1. Adjust R1 so that five of the ten LEDs are on.

Now explore the rest of the picture. You will probably find that two or three LEDs come on in the densest areas of the negative that will show detail on the print, and eight LEDs are illuminated in the thinnest areas that will show detail. You may find it useful to make a set of strips of paper exposed at the light level of one LED, two LEDs, up to ten, so that you can see the exact shade of gray that corresponds to each meter reading. Once you have the desired adjustment for your darkroom operation, close up the meter's case. You are now ready to produce quality, full-tonality photographs at a rapid pace on the first try with each negative. Ω


CABLE CONVERTER DIAGNOSTIC TEST CHIP

LOAD FULL ACTIVATION OF CABLE CONVERTER
WE STOCK A COMPLETE LINE OF CHIPS, TOOLS,
WIRELESS QUICK INSTALL TEST BOARDS AND
DIAGNOSTIC CUBES FOR ALL CONVERTERS!
***ANYONE IMPLYING ILLEGAL USE WILL BE ***
DENIED SALE. WE SELL PRODUCTS ONLY!! TO
TECHNICIANS OR CABLE REPAIR FACILITIES!!
#1 IN CUSTOMER SERVICE & TECH. SUPPORT!
*ALL ORDERS SHIP WITHIN 24HRS, UPS / FED-X.
*PRIORITY NEXT DAY SHIPPING AVAILABLE!
*SALE= BUY 5 TEST BOARDS AND GET 1 FREE.
MONDAY THRU FRIDAY - 8AM-7PM EST.
[HTTP://WWW.AMERICANINTERNET.COM/GOCABLE](http://WWW.AMERICANINTERNET.COM/GOCABLE)

VISUAL COMMUNICATIONS INC.
FOR ORDERS 1-800-GO-CABLE
CATALOG & TECH. SUPPORT 717-620-4363 EST. 1976



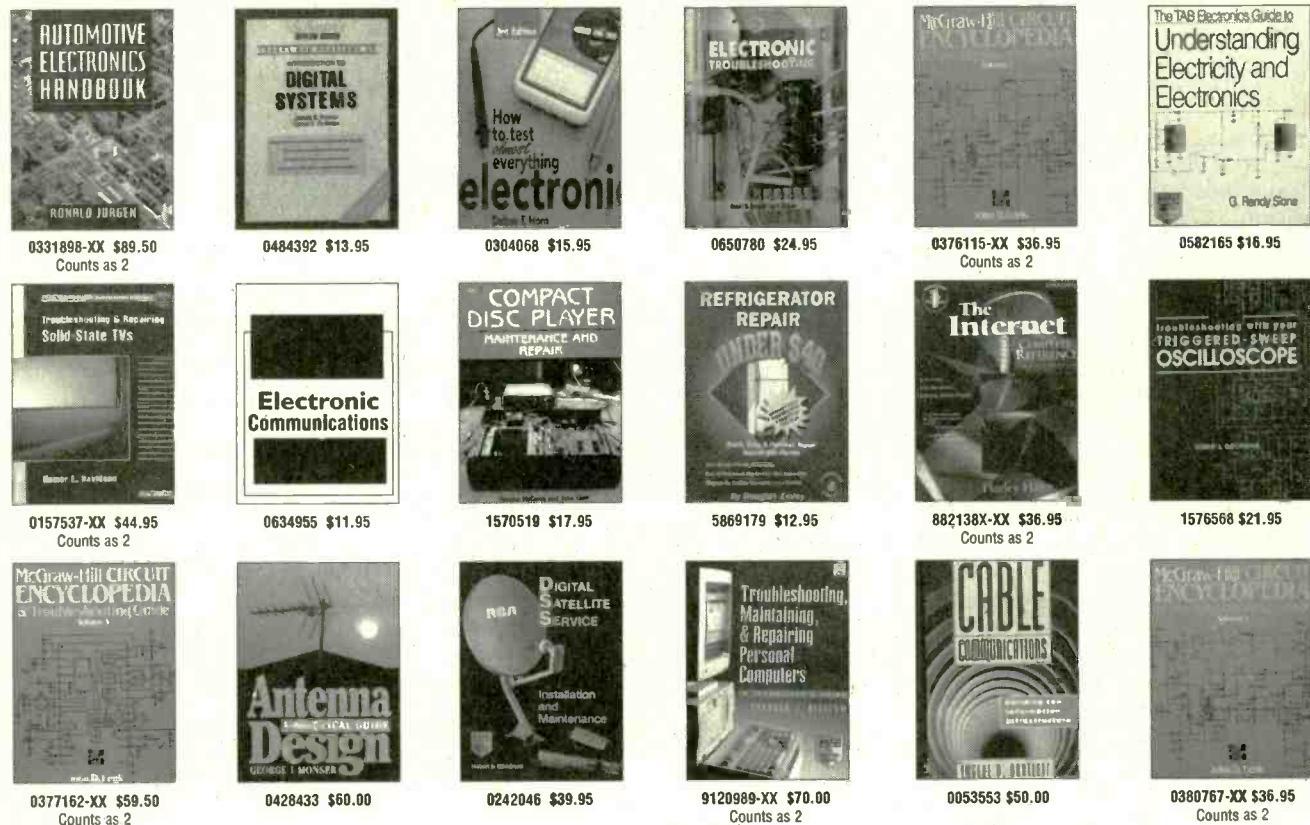The leading source of information for electronics hobbyists for over 30 years!




As a member of the ELECTRONICS BOOK CLUB®

You'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.

A shipping/handling charge and sales tax will be added to all orders. All books are softcover unless otherwise noted. If you select a book that counts as 2 choices, write the book number in one box and XX in the next. (Publishers' Prices Shown) ©1996 EBC

5 BOOKS FOR ONLY \$4.95

VALUES TO \$243.90

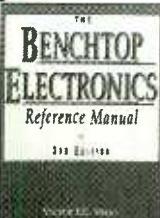

0673764-XX \$54.95
Counts as 2/Hardcover




1573119 \$19.95



1561579 \$17.95



0156492 \$34.95

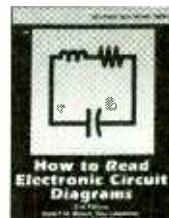

1554637 \$16.95



0376581XX \$39.50
Counts as 2/Hardcover



1575472 \$27.95



0707618 \$19.95



0380899-XX \$60.00
Counts as 2/Hardcover




1574875 \$19.95



0304084-XX \$24.95
Counts as 2




1577564 \$22.95

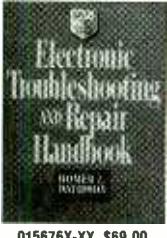


015676X-XX \$69.00
Counts as 2



0717753 \$19.95

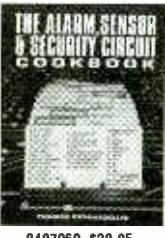


0497060 \$29.95

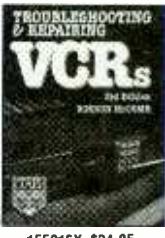


155016X \$34.95
Hardcover




9122264-XX \$39.95
Counts as 2

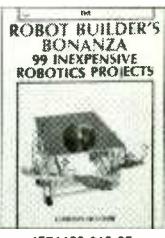


1571469 \$18.95

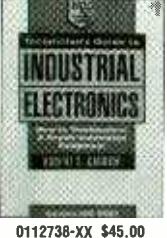

0112738-XX \$45.00
Counts as 2/Hardcover

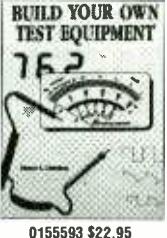


0155593 \$22.95

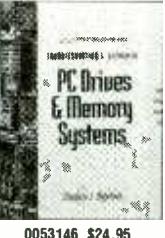

0053146 \$24.95



9119018-XX \$32.95
Counts as 2

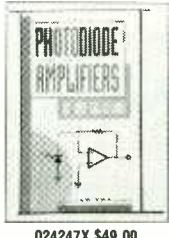

024247X \$49.00



0487375 \$24.95

If coupon is missing, write to: Electronic Book Club, A Division of The McGraw-Hill Companies, PO Box 549, Blacklick, OH 43004-9918



A Division of The McGraw-Hill Companies,
P.O. Box 549, Blacklick, OH 43004-9918

YES! Please send me the books listed below, billing me just \$4.95 plus shipping/handling & tax. Enroll me as a member of the **Electronics Book Club®** according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days without obligation and have my membership cancelled.

--	--	--	--	--

If you select a book that counts as 2 choices, write the book number in one box and XX in the next.

Signature _____
(required on all orders)

Address/Apt. # _____

City/State _____

Zip _____ Phone _____

Valid for new members only, subject to acceptance by EBC. U.S. orders are shipped 4th Class Book Post. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. Publishers' prices shown. A shipping/handling charge & sales tax will be added to all orders. RE1196C

BUILD THIS Hobby Spectrum Analyzer



BOB KOPSKI

At less than \$100 to build, this spectrum analyzer is a must for every hobbyist!

Over the last two months we have discussed the theory behind the \$100 Hobby Spectrum Analyzer and built and tested its various boards and subassemblies. Now it's time to put everything together and finish up the project.

Functional Interconnection and Test.

Connect all four functional modules together on the bench top for a final check. This is not the cleanest RF arrangement, but it is workable for initial inter-module checkout.

Hook up the bench supply and current meter to the DC/DC converter and regulators battery lead. Turn on the HSA power switch but not the comb generator switch, and slowly run up the variable supply from zero, watching the current drain behavior as you advance to 12-volts DC. Look for a current draw of 26-31 mA. Turn on the comb generator; the current draw should increase 5-8 mA. Turn the comb generator off.

Connect the log amplifier output temporarily to the oscilloscope input, and the trigger output to the oscilloscope's trigger input. Set the vertical coupling to AC, and the range to 0.1 volts/division. Set the sweep to 1-mS per division. Set the IF ATTEN to normal, and the INPUT SWITCH to mid-position (50

ohms). You should see a noisy baseline trace having about 0.1 volt peak-to-peak of noise. Be sure the oscilloscope is triggered for a stable display. Turn on the comb generator. You can expect a mess of vertical lines to appear on the oscilloscope. If so, you're now ready to do final assembly and alignment.

Cabinet Assembly. All modules and related parts easily fit in the specified cabinet; nevertheless, care is required in marking, drilling, and installing everything.

Start by flattening the dimples in the cabinet bottom where the feet screws were intended to go. The rubber feet can be glued on later. Hold a Universal prototyping board on the cabinet floor and mark four hole locations for the stack bolts. The rear board edge should be located 0.5-inch inside the rear panel, and as far to the right side of the cabinet as possible. Drill the holes. The stack screws are #6 machine screws. It is easier to slip the Universal prototyping boards over the #6 screws if the holes in the boards are drilled out to $\frac{5}{32}$ -inch diameter.

Next, drill the holes for the four phono jacks on the rear panel located on a line 1 $\frac{1}{8}$ -inch up from the cabinet floor to clear the stacked boards inside. Jack-to-jack spacing and elec-

trical assignment are not critical. Glue or double stick tape a $\frac{1}{4}$ -inch thick, $\frac{3}{4}$ -inch wide, 2 $\frac{1}{2}$ -inch wood or foam spacer block on the rear cabinet wall right behind the battery box location. Attach a strip of self-adhesive-backed Velcro tape to the battery box bottom and the cabinet inside floor, and trial mount the battery box.

The front panel is the most difficult mechanical task. With the RF circuit

PARTS SUPPLIERS

DC Electronics

P.O. Box 3203
Scottsdale, AZ 85257-3203
Tel: 800-467-7736

Digi-Key Corp.

701 Brooks Ave So
 Thief River Falls, MN 56701-0677
Tel: 800-344-4539

Electronix Express

365 Blair Road
Avenel, NJ 07001
Tel: 800-972-2225

Hosfelt Electronics Inc.

2700 Sunset Blvd.
Steubenville, OH 43952-1158
Tel: 800-524-6464

Ocean State Electronics

P.O. Box 1458
6 Industrial Drive
Westerly, RI 02891
Tel: 401-596-3080


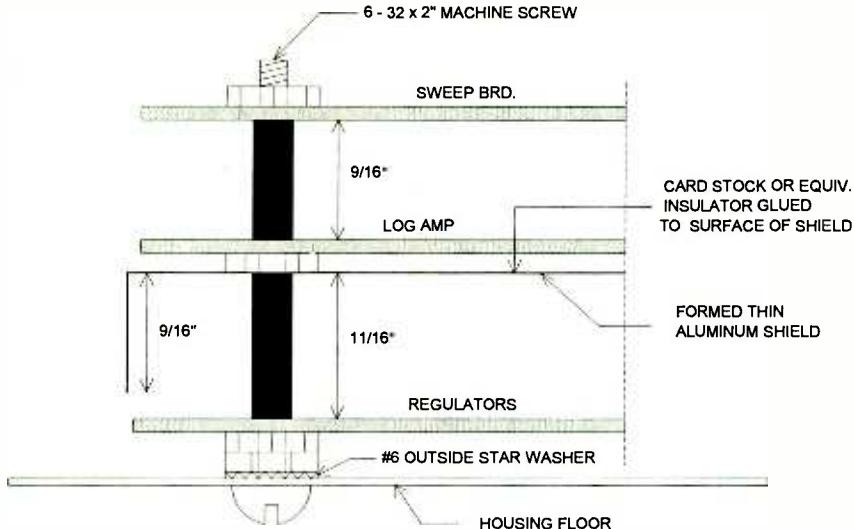


FIG. 12—MODULE STACK ASSEMBLY details are illustrated here (not to scale). Aluminum shields between the log amplifier module and DC/DC converter and regulators module provides RF shielding from stray radiation generated in the DC/DC converter circuitry.

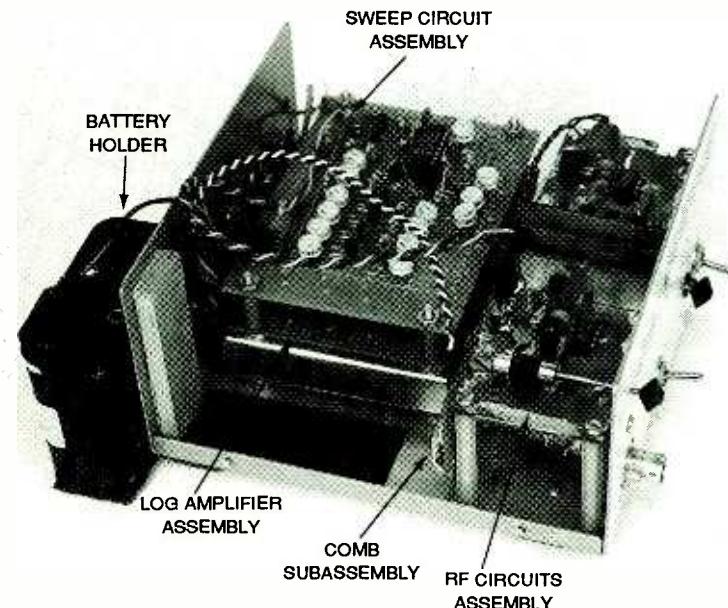

FRONT PANEL OF THE HSA mounts four switches and a BNC connector for the input signal. The rear panel (not shown) has four RCA phono jacks that provide three output signals and a battery test point.

module in hand, mark off the various hole centers in the front panel. There are two critical hole locations: the $\frac{5}{64}$ -inch holes for the switch push rods (discussed in a moment). Make sure the alignment is correct before you drill. Use a $\frac{5}{8}$ -inch chassis punch to make the clearance opening for the BNC connector. Finally, the panel screw just above the BNC connector is a 4-40- $\frac{1}{4}$ -inch screw. It screws into a tapped hole in the BNC mounting plate to draw the latter snug against

the rear surface of the cabinet front panel.

Locate and drill the four mounting holes in the cabinet floor for the RF circuit module spacers ("legs"). The mounting holes for the toggle switches and POWER LED2 are not critical. Make push rods for the switches using $\frac{1}{16}$ -inch brass rod, a decorative bead glued on for a knob, and model-plane wheel collars to capture the sliding switch knobs themselves. Install all the electronics/interconnections in


the cabinet as in the drawings and photos. Temporarily omit the topmost stack nuts (Fig. 12), so that the sweep board can be lifted to access the log amplifier.

Final Alignment. Temporarily connect the unused preamplifier output test point to the oscilloscope vertical, and connect the trigger output to the oscilloscope trigger input. Power up. Connect a lead to a source of 145-MHz signal and allow the lead to radiate near the double-tuned 145-MHz filter. Tune the second local oscillator trimmer capacitor C27 and the filter capacitor trimmers C13 and C17 iteratively (again and again) for both a visible audio frequency heterodyne and maximum signal as well. Remove the 145-MHz signal.

Position the start of the baseline sweep precisely at the left most graticule line on the oscilloscope. Turn on the comb generator. Readjust the sweep circuit board adjustments (in the same sequence as before) to progressively locate the spectral lines on subsequent graticule divisions. The sweep offset (R7) and sweep gain (R10) board-mounted controls are used to set the lines from zero to mid-screen (50-MHz) beginning with the 10-MHz component on the first graticule line. The remaining adjustments cover the last 50 MHz. Unlike the earlier rough tuneup, you can now use the segment gain adjustments (R17, R19, R21, and R23) for fine-fitting the entire sweep shape. Work with all the screw adjustments; you can't hurt anything, and you'll observe that sweep alignment goes easily.

If you find that you can't quite hit the highest and/or one or two of the lowest frequencies, note that the HSA will likely not tune below 1-2 MHz. As for the high-end difficulties, try adjusting RF circuit module capacitor C6 in conjunction with re-spacing the loops in inductor L2. The trick is to have a suitable ratio of L and C and enough motion in C (via varactor D1) to cover the band.

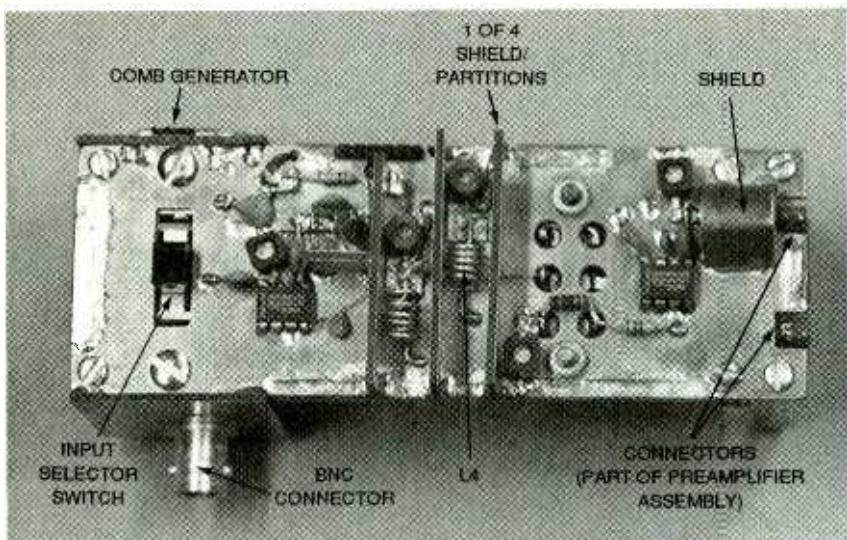Fine tune the HSA using one of the comb generator's spectral lines. The 30-MHz line is good, or an external source can be used. Connect the unused preamplifier output to the oscilloscope vertical input and the trigger output to the oscilloscope trigger input. Power up. Center up the




THE RF CIRCUITS MODULE has two subassemblies—preamplifier and comb generator. Note the partition/shield area in the center that isolates the two sections of 145-MHz bandpass filter. Inductor L4 has a tap on the first turn (bottom in photo) that is difficult to see in this view.

desired spectral line on the oscilloscope display, and then use the scope magnifier if it has one. You should see a symmetrical heterodyne bubble including a "suck out" at zero beat. Fine tune the IF trimmer capacitors C13 and C17 iteratively for a smooth sharp passband peak with the heterodyne dead center.


Switch in the IF attenuator and increase signal or oscilloscope gain as necessary to re-display the bubble. It will likely be detuned. Adjust attenuator-compensation capacitor C18 to reshape the display. Note that the bubble should have $\frac{1}{10}$ the amplitude of the original signal (it is 20 dB down).

The adjustment of the V+ level is somewhat subjective and somewhat quantitative. Lower voltages reduce the overall HSA gain; the highest values increase it significantly. However, along with higher gains comes more noise, jitter and trash near the baseline. The baseline may also take on an undulating or curvy appearance. Another indication is an unaccounted baseline spike located at about 72 MHz. Setting V+ to a compromise level eliminates all the above unpleasantness and provides for very good operation as well. The prototype's V+ setting is about 5.7 volts.

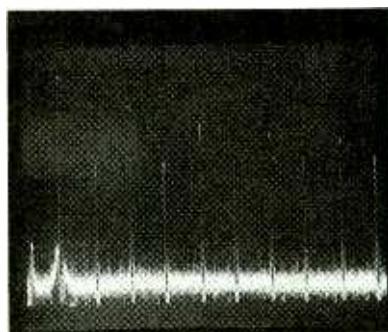The spectral line at the 10-MHz position can be used to help adjust HSA amplitude performance. Locate the top of that line on an upper oscilloscope's graticule line at three



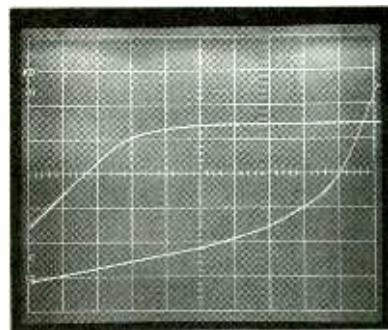A VIEW OF THE HSA comb generator oscilloscope display after the alignment procedure is completed.



THE SWEEP-CIRCUIT OUTPUTS as viewed on an oscilloscope. The lowermost curve is the varactor (sweep) drive waveform—the bottom grid line is 0.0 volts, 5-volts per division. The uppermost waveform is the local-oscillator boost waveform—1-volt/division, top of trace is 4.5 volts. Both curves are displayed on a 1-ms/division time base.

main graticule divisions up from center face. This is the -30-dBm level. The

base-line noise should be down around the third main division below center line (almost six divisions below the signal). Set the IF attenuator to -20 dB. The signal should fall two vertical divisions. If it travels less, increase log amplifier output gain (R28); if it travels more, decrease the gain. Continue the adjustment until the attenuator change and the change in display agree. This calibrates the 10-mV/dB log constant.

Adjust log amplifier input gain (R2) so that logging begins above the base-line noise (positive noise peaks should not appear compressed). In all the steps above, be sure the base-line clipper trimmer (R26) is set to just trim off negative going spectral lines and not infringe on the magnitude of the base-line noise. Trimmer R26 will require resetting during the above procedures.

With that done, the 30-MHz line should be 10 dB lower than the 10 MHz line. The 50-MHz line should be down 5 more dB. The 70-MHz line should be about 3 dB down from that. Finally, the 90-MHz line should be 21 dB below the 10-MHz line. The latter is the line most likely to be off due to the comb-generator-waveform quality limitations. Finally, pay no attention to the even-order spectral lines; if the comb generator waveform were ideal they would not be present at all.

Frequency flatness is best confirmed with a quality signal source/power meter combination. The rough tuneup of the local oscillator boost given earlier should be fairly good, but if you have access to a flat source you can fine tune the boost function. The adjustments R33 and R30 control boost waveform "zero" and ramp rate respectively. The setting of R35 controls the waveform effect on local oscillator power.

Hints. The Hobby Spectrum Analyzer just begins to overload for signals exceeding -30 dBm. This is about 20 mV peak-to-peak on 50-ohm lines. Distortion manifests itself in several ways including baseline "buckling" at the base of such a spectral line, and "splatter" across the display. This situation can often be controlled with the input and/or IF attenuators.

It is sometimes convenient to transformer couple RF energy into the HSA.

(Continued on page 118)



PHONE LINE SENTINEL

Put an end to phone-call interruptions with the Phone-Line Sentinel—it will let others know when you're on the line.

MORDECHAI SAAD

WE ALL KNOW HOW ANNOYING IT CAN be when you're in the middle of an important phone call and somebody else picks up the line and says "Oh, I didn't know you were on the phone." And it's all the more annoying when they start dialing without first checking for a dial tone. Of course, such an interruption can be devastating to a fax or modem transmission. If you are regularly plagued with such interruptions, then you need one of our Phone-Line Sentinels placed next to every phone in your house. The PC board measures only 1 × 1.8 inches.

How it works

The nominal voltage of a telephone line, when not in use, is about 50 volts DC. As soon as the line is in use, meaning that a telephone on the line has been picked up, the line drops to about 5 volts DC. Therefore, all we need is a voltage-level sensor to detect whether or not the line is in use. The Phone-Line Sentinel is just that; it monitors the phone-line voltage and lights an LED to let you know when the telephone line is in use.

At the heart of the circuit, shown in Fig. 1, is IC1, an ultra-low-current voltage-level sensor.

Using that IC, the circuit draws "no" current (about 5 µA) when the phone line is not in use, and negligible current (about 3 mA) when the line is in use. Power for IC1 is supplied from the phone line via R2, D1, and C1. Transistor Q1, which powers LED1, is driven directly from IC1 whenever the proper voltage level has been detected. Resistor R1 limits the current flow through LED1, and R3, R4, and D2 divide the phone-line voltage down to a proper level for IC1. Protection from phone-line transients is provided by resistor R5 and varistor R6.

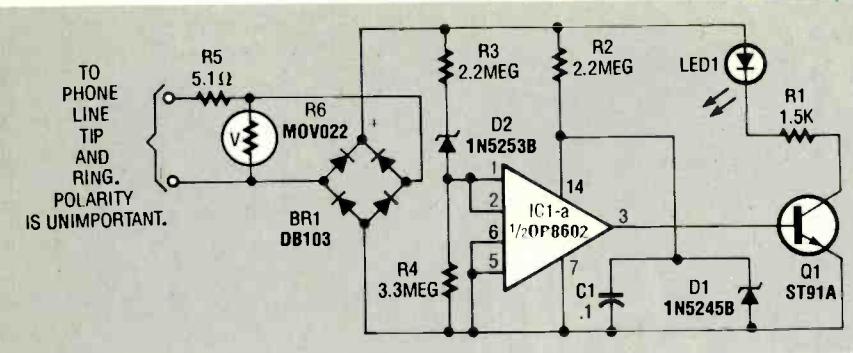


FIG. 1—AT THE HEART of the circuit is an ultra-low-current voltage-level sensor that draws only about 5 μ A when the phone line is not in use.

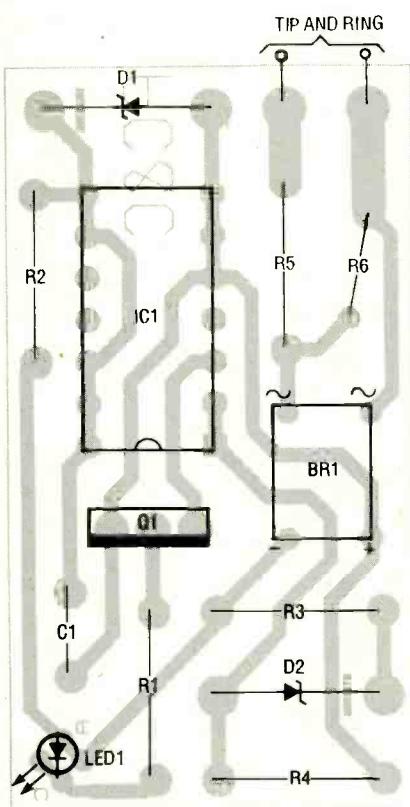


FIG. 2—IF YOU'RE USING A PC board, follow this parts-placement diagram. The LED can be mounted so that it can be bent in any direction, or remain straight up.

Construction

The Phone-Line Sentinel is available as a kit (or completed unit) from the source mentioned in the parts list. However, if you can dig up all of the parts on your own, you can point-to-point wire the circuit, or make your own board from the foil pattern we've provided.

If you're building the circuit using a PC board, simply follow the parts-placement diagram in Fig. 2. If you'll notice, the LED can be mounted on the board in


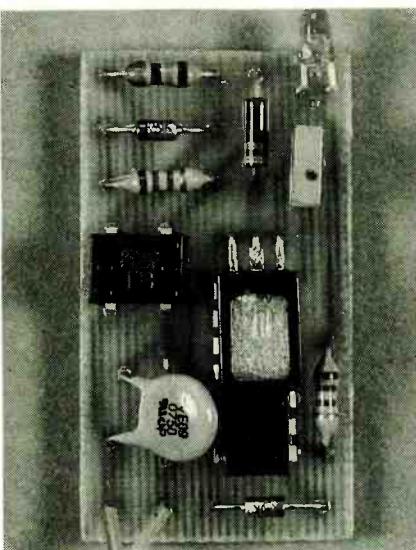


FIG. 3—THE COMPLETED BOARD should look something like this.

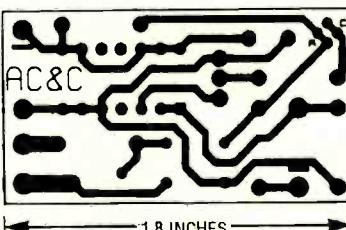

USE THIS FOIL PATTERN to make your own PC board.

two positions, so that it can be bent in any direction, or remain straight up. You can also mount the LED on leads as long as you like, allowing the board to be hidden from view, or perhaps inside a telephone if there's enough room, leaving only the LED indicator in view. We'll leave the details up to you. Just be sure to observe the LED's polarity on the board regardless of how you install it.

Connecting the unit to a phone line is easy. If you have a spare

PARTS LIST

All resistors are 1/4-watt, 5%.

R1—1500 ohms
R2, R3—2.2 megohms
R4—3.3 megohms
R5—5.1 ohms
R6—MOV022 varistor

Capacitors

C1—0.1 μ F, 50 volts, ceramic

Semiconductors

IC1—OP8602 ultra-low-current voltage-level sensor

D1—1N5245B 15-volt Zener diode

D2—1N5253B 25-volt Zener diode

BR1—DB103 bridge rectifier

LED1—light-emitting diode

Q1—ST91A NPN transistor

Miscellaneous: PC board, modular phone cord or hookup wire, solder, etc.


Note: The following items are available from TelMore, 11 Market Dr., Syosset, NY 11791: A complete kit, including PC board and all parts in Parts List (above), \$14.99. An assembled and tested unit, \$19.99. With the assembled units, you must specify which way you want the LED positioned. With the LED pointing straight up, order LIUD-UP; with it pointing to the long side of the board, order LIUD-LS; with it pointing to the short side, order LIUD-SS; and with it mounted off the board on wire leads, order LIUD-W. Add \$1.75 for the -W model. Please add \$7.50 for shipping and handling to all orders. NY State residents must add appropriate sales tax.

jack in a desirable location, all you have to do is solder the tip and ring (green and red) wires of a modular phone cord to the board as shown in Fig. 2. Otherwise you can use whatever wire you like and connect it to the line however you see fit. Figure 3 shows the completed board.

Testing the circuit is as simple as using it. Just connect it to the phone line; the LED should be off if the line is on-hook. Then, if you pick up any phone on the line, the LED should light. After the operation of the circuit checks out, it's time to decide what you're going to do with it. Because of the extremely compact size of the board, the neatest thing you can do is mount one inside every phone you own, with only the LED left exposed. If you do a neat job, it will look like it was factory installed.

The 7107 A/D converter/display driver has been on the market for so long, its versatility tends to be overlooked. Get re-acquainted with this amazing voltmeter-on-a-chip: the device with a thousand-and-one uses.

CARL J. BERGQUIST

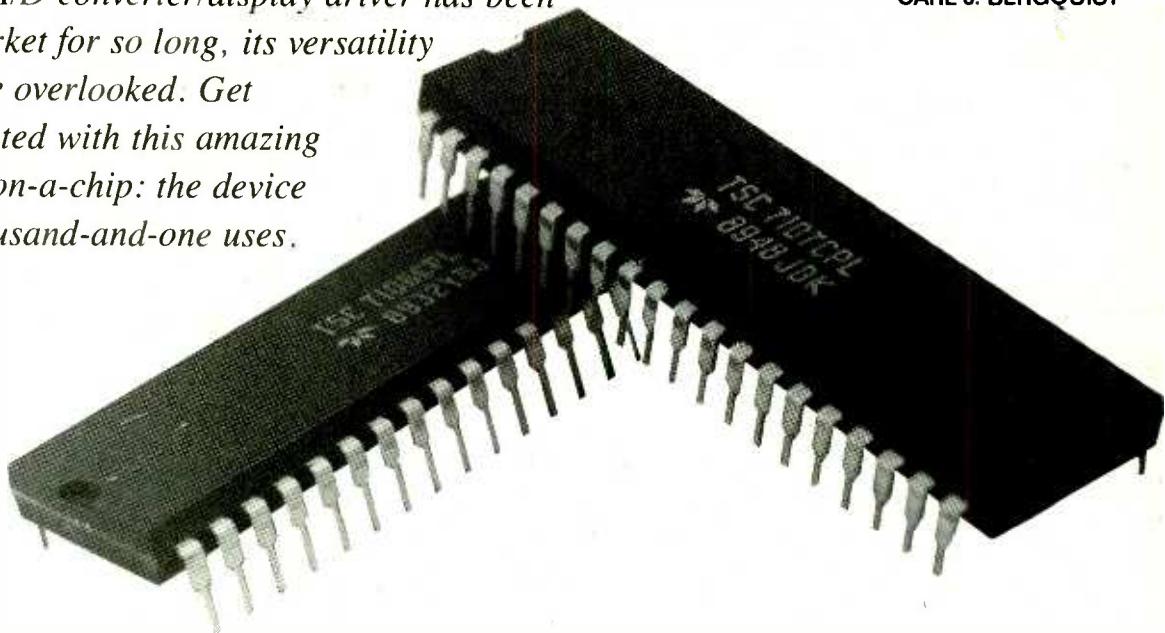

With the invention and introduction of the seven-segment light-emitting diode (LED) display, adding an information display to the front panel of almost any project has become commonplace. Digits are easier to read than analog meters, and tend to "dress up" the appearance of the completed unit.

Those displays, of course, do not light themselves, but rely on logic and driver circuitry to display the desired information. The combination of a binary or decade counter with a decoder/driver is one way to display information on the LEDs, especially in clock applications, but a more versatile method is an analog-to-digital converter.

A number of options are available along that line. Combining a Motorola 14433 3½-digit A/D converter or an RCA CA3162 A/D converter with an RCA CA3161 BCD-to-7-segment decoder/driver chip is one way to go, but for ease of use, low cost, and low component count, it's hard to beat the Intersil/Harris ICL7107/7106 3½-digit A/D converter/display driver.

Originally designed primarily as a voltmeter, the 7107 is a combination analog-to-digital converter, reference voltage, timing clock, and decoder/driver circuit all on a single CMOS IC. It features high accuracy, low power consumption, and directly

USING THE 7107

drives instrument-sized, common-anode, 7-segment LED displays. The 7106 is the liquid-crystal display (LCD) version of that device and incorporates a backplane driver.

The number of support components needed for operation of the 7107 are minimal: five capacitors, four resistors, a potentiometer, and the display. Add a split five-volt power supply, and the 7107 becomes a complete 3½-digit voltmeter with a full-scale reading of either 200 mV (199.9) or 2 volts (1.999), depending on the values selected for the support components. Another attractive feature is that since both chips have been on the market for several years, their price through catalog distributors has dropped to below four dollars each.

With the basic voltmeter circuit, any measurement, value, or quantity that either exists as a voltage or can be converted to a voltage will provide the input. The 7107 is then easily calibrated to display that measurement or value digitally.

So, the possibilities are limitless. Volt-

age, current, resistance, inductance, light, temperature, speed, capacitance, frequency, etc., can all be directly displayed through simple transducer circuits. We'll show you how to do that, and armed with that knowledge, it is very convenient to either equip projects and new designs with digital displays, or modernize older gear.

7107 Circuit Operation. Figure 1 is the schematic for a basic 2-volt configuration. Power for the chip is applied to pin 21 for ground, pin 26 for -5 volts, and pin 1 for +5 volts. Pins 2–20, and 22–25 connect the device to the LED display, with pin 19 driving the ½ digit, or the leading "1", on the display. Pin 20 indicates when the input voltage drops below 0 volts, so it can be used to drive a minus sign on the display.

Pins 30 and 31 accept the negative and positive inputs, respectively, while pins 35 and 36 handle the reference voltage generated by a resistor-potentiometer divider network. The lo

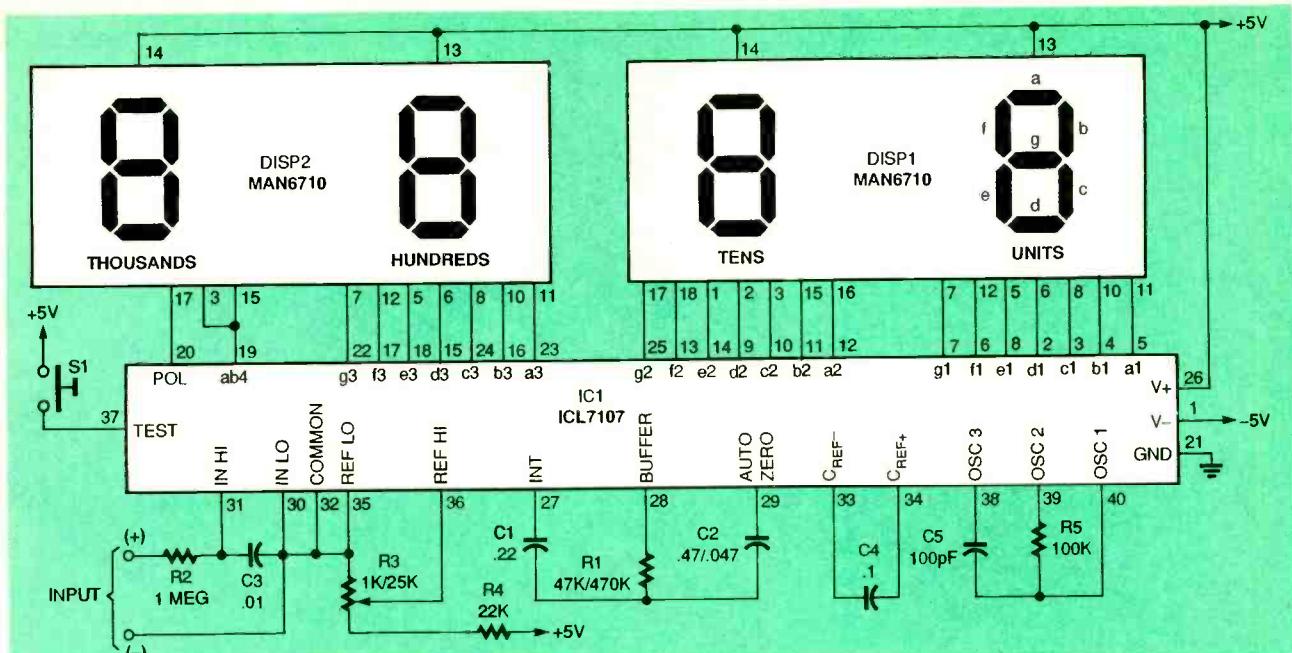


Fig. 1 The 7107 was originally designed to be a self-contained, highly accurate voltmeter. By changing the values of C_2 , R_1 , and R_3 , the 7107 can have a range of 200-mV or 2 volts.

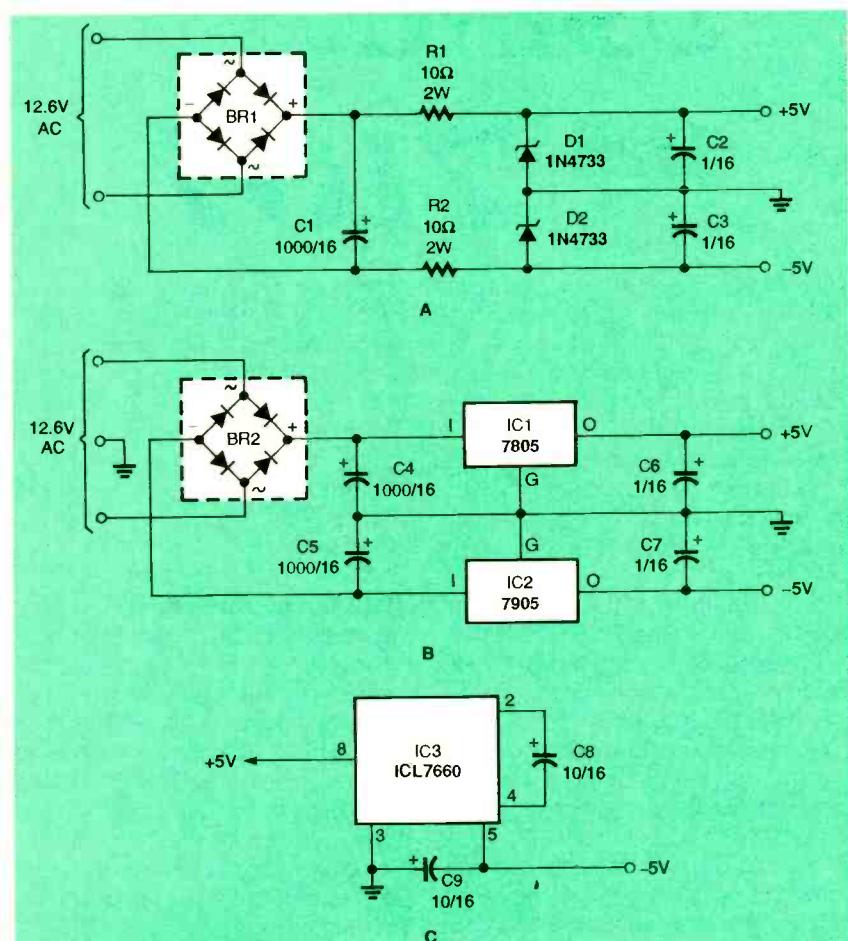


Fig. 2. Here are a few different methods of generating the + and -5-volt power required by the 7107. A pair of Zener diodes (A) are handy if the transformer you want to use does not have a center tap. A pair of three-terminal regulators (B) and a center-tapped transformer also work well. An interesting alternative is the ICL7660 chip (C), which generates a negative-voltage output from a positive-voltage input.

reference (pin 35), analog common (pin 32), and negative input (pin 30) are tied together in any application where the input signal is "floating" with respect to the power supply. The analog common also provides the reference voltage for the auto zero feature, which maintains a zero reading for a 0-volt input.

Pins 38, 39, and 40 provide access for the clocking circuit. The recommended values result in a frequency of 48-kHz (3 readings per second), which generally gives excellent performance. If a different frequency is desired, the equation $f = 45/RC$ can be used to find the component values needed. If you keep R at 100,000 ohms, the formula will select the correct value for C . In addition to the RC arrangement, a crystal can be connected between pins 39 and 40, or an external oscillator signal can be fed into pin 40.

With the exception of R_1 , C_2 , and R_3 , component values are common to both the 200-mV and 2-volt configurations. Resistor R_1 provides linearity over the input range. Recommended values are 47,000 ohms for a 200-mV range, and 470,000 ohms for the 2-volt range.

Auto-zeroing capacitor C_2 has an effect on noise in the circuit. For the 200-mV scale, a value of 0.47- μ F improves noise immunity, while 0.047- μ F is adequate for the 2-volt version. That

smaller value also improves recovery speed of the circuit. A value of 1,000 ohms for potentiometer R3 in the lower-voltage meter is increased to 25,000 ohms to provide a wider reference range for the higher-voltage meter.

For maximum accuracy and stability, it is best that all capacitors, with the exception of C5, be of the Mylar variety. With its lower dielectric absorption, that type of capacitor will provide superior performance. Capacitor C5 can be a standard ceramic disc or silver-mica type, and all resistors are 5% carbon film.

One disadvantage of the 7107 is the need for a split 5-volt power supply, but there are several simple ways to meet that requirement. If a bench supply is at hand, it usually has ± 5 volts available, either as a separate output or through the use of the adjustable supplies. If that source is not convenient, or a separate self-contained supply is preferred, Fig. 2 shows three different approaches.

In Fig. 2-a, input power from a small step-down transformer is first rectified by bridge rectifier BR1 and smoothed by capacitor C1. A pair of 1N4733 Zener diodes (D1 and D2) regulate the input power to the needed 5 volts.

PARTS LIST FOR THE 7107 VOLTMETER

SEMICONDUCTORS

IC1—ICL7107CPL, A/D converter/
LED display driver, integrated
circuit
DISP1, DISP2—dual 7-segment
common-anode LED display
(MAN6710 or similar)

RESISTORS

(All fixed resistors are $\frac{1}{4}$ -watt, 5%
units.)

R1—47,000-ohm/470,000-ohm

R2—1-megohm

R3—1000-ohm/25,000-ohm,
potentiometer, (see text)

R4—22,000-ohm

R5—100,000-ohm

CAPACITORS

C1—0.22- μ F, Mylar
C2—0.47- μ F/0.047- μ F, Mylar (see
text)


C3—0.01- μ F, Mylar

C4—0.1- μ F, Mylar

C5—100-pF, ceramic-disk

ADDITIONAL PARTS AND MATERIALS

IC sockets, hookup wire, etc.

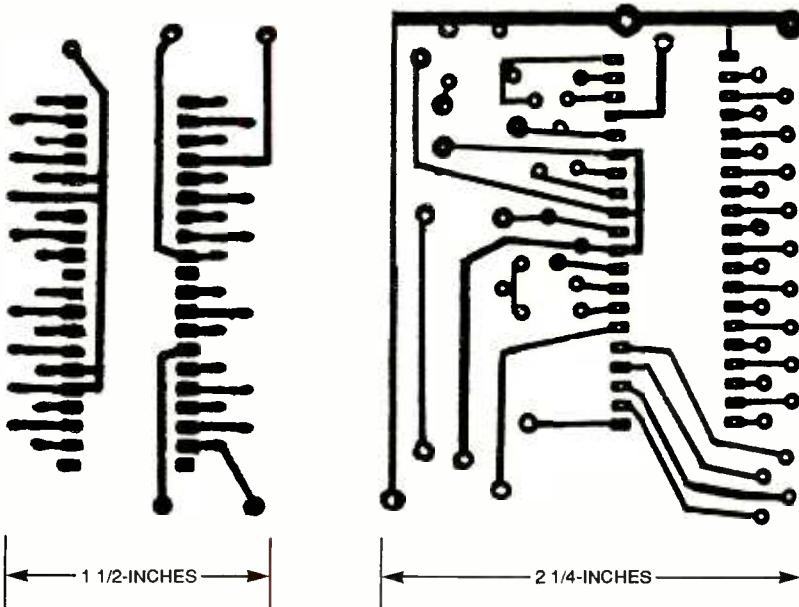

Here are the foil patterns for the basic 7107 voltmeter and the LED display. A split power supply and a handful of passive components turn the 7107 into an accurate, easy-to-use instrument. Putting the display on a separate board makes the project more versatile in terms of mounting arrangements. You can also combine both boards into one if you need to.

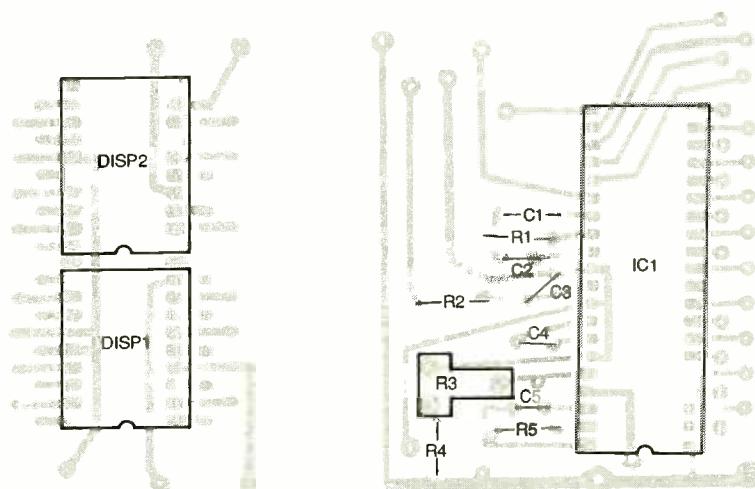


Fig. 3. If you want to build your own 7107 voltmeter, you can follow the parts placement diagrams here. Using sockets for the 7107 and the displays make troubleshooting easy.

Actually, the diodes are rated at 5.1 volts, which is well within the 7107's tolerance. Resistors R1 and R2 limit the current that flows through the Zener diodes themselves. The remaining circuitry is a standard "rail" power supply.

Figure 2-b illustrates a similar configuration utilizing positive- and negative-output linear voltage regulator ICs. However, we are using a center-tapped transformer to form a true split power supply. A disadvantage of a center-tapped transformer is the added expense. However, never try to

get around that by using a non-center-tapped transformer and connecting one side of the AC input to ground. Although that would work, it would create a "hot" ground: a potentially dangerous situation. Any extra money spent on the proper transformer will be far cheaper than spending several days in a hospital should some component in the circuit fail. Be sure both the 7805 and 7905 voltage regulators have adequate heat sinks.

Figure 2-c uses a voltage-con-

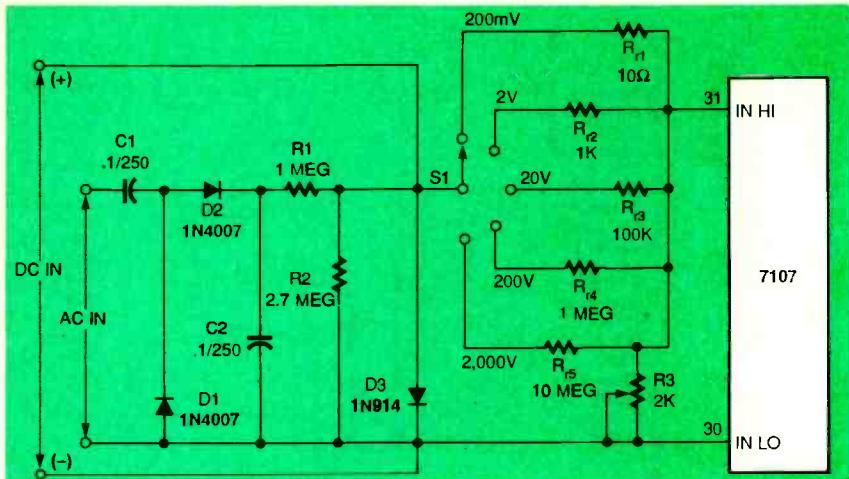


Fig. 4. Adding this circuit to the 7107 produces a versatile digital voltmeter (DVM). Both AC and DC voltages in five ranges up to 2,000 volts are accurately measured.

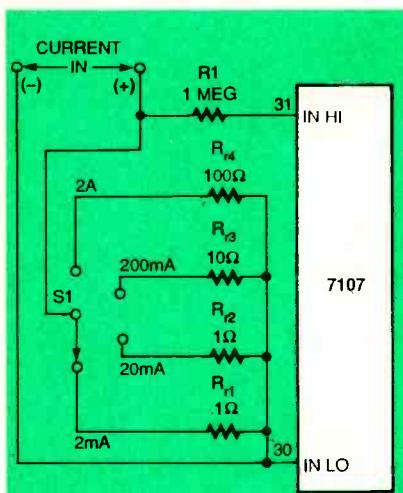


Fig. 5. With this circuit, the 7107 can measure DC current. The rotary switch lets you select from four ranges, with a capacity up to 2 amps.

version technique. In that circuit, either the Teledyne TSC7660 or the Intersil/Harris ICL7660 will work. Both are 8-pin DIP packages with identical pinouts. If a 7660 is used, the power supply need only deliver +5 volts. The 7660 converts that input voltage to -5 volts, giving us a split supply.

Construction of the Basic 7107 Meter.

Meter. While breadboard or point-to-point wiring can be used, printed-circuit techniques work best. Foil patterns are included for a printed-circuit board based on the sample circuit in Fig. 1. Separate boards are used for the main circuit and the display. Multi-color ribbon cable works well as hook-up wire between the two boards. Keeping the sections separate affords a little more versatility. If you wish, the

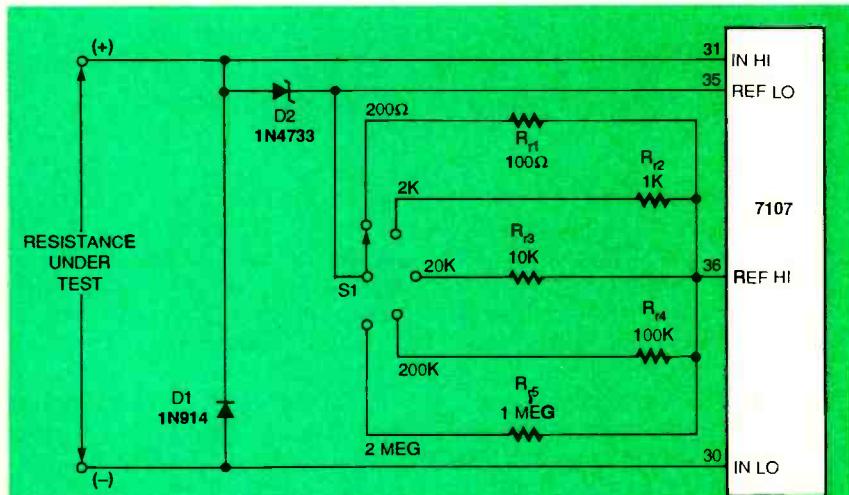


Fig. 6. Although you could measure resistance with a simple voltage-divider circuit, the use of a Zener diode and a switch-selectable resistor to change the 7107's reference voltage makes it easier to measure resistances up to 2 megohms.

LED readouts and main circuit can be combined onto one board. It's a simple matter to merge the two patterns together.

Regardless of how you handle your PC boards, use a 40 pin IC sockets for both the 7107 and the LED displays. That makes changing the 7107 or the displays easy if you need to. The parts-placement diagram in Fig. 3 will aid in component insertion at the proper locations. When installing the discrete components, the only orientation to observe is the IC itself, as the capacitors are non-polarized.

Like the display circuit, the power-supply circuit can either be put on the main PC board or kept separate. Convenience or personal preference will, of course, influence which way you decide to go. With all three sections completed and connected together, we can move on to the next step.

Testing and Operation of the 7107

Meter. Before installing the 7107 chip itself, confirm that the correct voltages are present at the power supply, and at pins 1, 21, and 26 of the 7107 socket. If a problem is encountered, double-check the wiring and component placement for errors. Once the proper voltages are verified, disconnect the power and plug the 7107 into its socket. Turn the power back on, and the display should read "000".

Apply +5-volts to pin 37, and "-1888" should be displayed. Pin 37 is the test input and activates all segments. A permanent switch can be added if the test function is to be used often. However, do not leave the test on for more than a few minutes if you're using the 7106. The test function on that chip applies straight DC instead of squarewaves to the LCD segments. That might cause the image to "burn" into the LCD.

Apply a known, stable voltage to the + and - inputs. Adjust potentiometer R3 until the display reads that voltage. The meter is now calibrated and ready to go.

Another method of calibration is to read the actual reference voltage at pins 35 (REF LO) and 36 (REF HI). For the 200-mV meter, that reading should be as close to 100 mV as possible. For the 2-volt meter, 1 volt is the needed measurement.

That procedure will also be useful if

ormal voltage reference is needed. In some applications where the transducer output is above or below the standard meter parameters, it is easier to adjust the reference voltage to accommodate the transducer, rather than attempt to correct the transducer's output voltage. In any event, always adjust the reference to one half the input voltage.

Additionally, a decimal point can be displayed by hard wiring a 470-ohm resistor from ground to the pole of a four-position rotary switch. With the four contacts connected to the four decimal points on the display, the decimal point can easily be placed wherever it is needed.

Applications and Input Transducers.

With the basic digital meter built and tested, it's time to put the unit to work. As we mentioned earlier, any value or measurement that is a voltage or can be converted to a voltage can be displayed, but only if we connect what we need to measure to the meter properly. That is where the input circuits and transducers come into play.

Voltage Measurements. Since the 7107 is a voltage-measuring device, let's look at that application first. Figure 4 is a circuit for a digital voltmeter (DVM) that will measure voltages from 0 to 2,000 volts in five ranges. The circuit can measure both alternating and direct current, with C1, C2, D1, D2, R1, and R2 acting as a rectifier/filter for AC measurement. Resistors R_{rx} and R3 form a selectable input-voltage divider. Rotary switch S1 connects any one of the five resistors, R_{r1}-R_{r5}, for the selected voltage range.

Once that input circuit has been connected to the 7107, choose a known voltage source, either AC or DC. Select the appropriate range with S1, and adjust R3 to obtain a display that matches the known source. That will fine-tune the circuit for future voltage measurements.

Current Measurements. The next basic measurement to consider is current. We do that by passing the current through a shunt resistor. The shunt develops a voltage across itself in proportion to the amount of current flowing through it. That voltage can be measured by the 7107 meter.

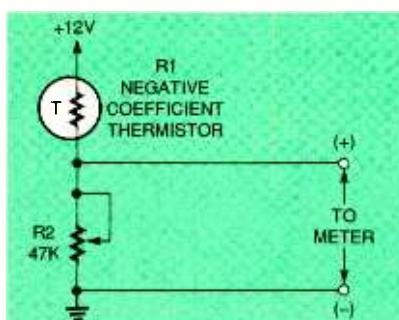


Fig. 7 A simple voltage-divider circuit using a negative-temperature-coefficient (NTC) thermistor as a low-cost and accurate method of measuring temperature with the 7107. An NTC thermistor's resistance drops as its temperature rises. If you switch the locations of R1 and R2, the reading on the 7107 will drop with rising temperature.

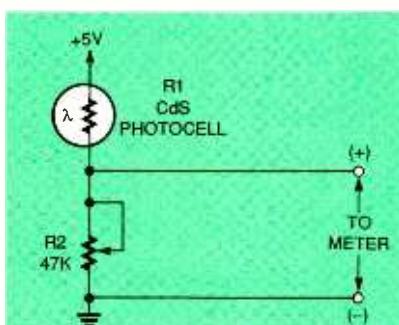


Fig. 8. We can measure light intensity the same way we measure temperature by substituting a cadmium-sulfide (CdS) photocell for the thermistor in Fig. 7. In most CdS photocells, resistance will drop with an increase in brightness. Should you need to have the 7107's display reading drop as the photocell gets brighter, or if you have a photocell that increases in resistance with exposure to light, simply switch the positions of R1 and R2.

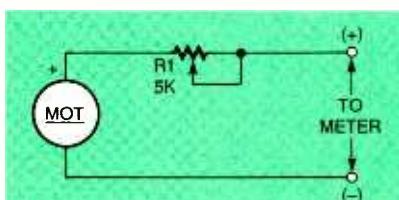


Fig. 9. You can use a small permanent-magnet motor as a tachometer. Attach the motor's armature to whatever spinning shaft you want to measure, and the voltage generated by the motor can be read directly by the 7107.

Figure 5 is the schematic of a four-range system, where R_{r1}-R_{r4} controls the range and acts as the shunt. Resistors R1 and R_{r1}-R_{r4} form a voltage divider that provides the input for the

meter. A rotary switch arrangement similar to the range selector in Fig. 4 works nicely for the ammeter as well. The values for the shunt resistor are selected by S1. Using 1% precision metal-film resistors gives the greatest accuracy.

Resistance Measurements. The last type of value commonly measured by most digital multimeters (DMMs) is resistance, and Fig. 6 illustrates a method for that. Zener diode D2 develops an external reference voltage, allowing S1 to select one of R_{r1}-R_{r5} to control the on-chip reference voltage. A DC voltage is generated across the unknown resistance, and that value is then processed by the 7107 and displayed.

That measurement could also be done with a standard voltage-divider circuit, but the problem with that method is that R_{r5} would have to be in the 500-megohm range for the 200,000- to 2-megohm setting. That is a difficult value to obtain, especially at precision levels. Adjusting the reference voltage results in a workable value for R_{r1}-R_{r5}.

Temperature Transducer. There are a number of ways to measure temperature. Figure 7 is a simple and surprisingly accurate method. In that configuration, a 47,000-ohm potentiometer provides as calibration, and a negative-temperature-coefficient (NTC) thermistor acts as the temperature probe. By applying 12 volts and setting the decimal point on the display between the units and tens digit, readings to an accuracy of $\frac{1}{10}^{\circ}$ can be achieved. Again, the circuit is a voltage divider.

Light Measurement Transducer.

The light transducer in Fig. 8 is almost identical to the temperature sensor. The only differences are a 5-volt supply voltage and the use of a cadmium-sulfide (CdS) photocell in place of the thermistor. Changes in ambient light shining on the photocell changes the resistance of the cell. That in turn changes the voltage produced by the divider. Any change in light intensity will be shown in the display. The display can be calibrated to indicate "f-stops" for photography work, or can be an arbitrary numerical value for which a chart or graph

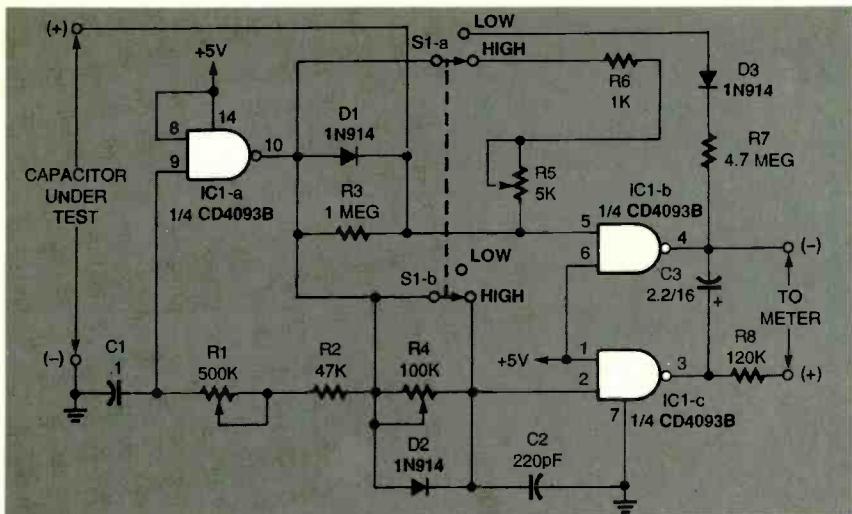


Fig. 10. With this circuit, the 7107 gains the ability to measure the value of capacitors from 2 pF to 2 μF. Potentiometer R4 adjusts the circuit for a zero reading, while R1 and R5 calibrate the low and high ranges.

can be developed as appropriate. By using a photocell with a range of 500-ohms illuminated to 2- to 3-megohms dark, very sensitive results can be achieved with the circuit.

Those two circuits illustrate how any device that changes resistance due to any circumstance can be plugged into the divider network. You can try replacing the CdS photocell with a 1,000-ohm potentiometer. After calibrating with the 47,000-ohm variable resistor, the exact value of the potentiometer between 0 and 1,000 ohms will be displayed.

Speed Measurements. Figure 9 shows a method of measuring rotary speed. Since the 7107 is a voltmeter, and electromagnetic motors produce a voltage when their armatures are rotated, the measurement circuit is extremely simple. A 5,000-ohm potentiometer is used for calibration, with one end connected to the positive motor pole, and the other tied to the HI input (pin 31). The negative side of the motor goes to the LO input (pin 30). When the motor shaft is coupled to a rotating object, the voltage developed is proportional to the speed of rotation. That system can be used for tachometers, wind-speed indicators, generator-voltage monitors, and the like.

Capacitance Meter. One of the most useful bench tools around is the digital capacitance meter. Those meters will save not only time, but money as well. Surplus capacitors are

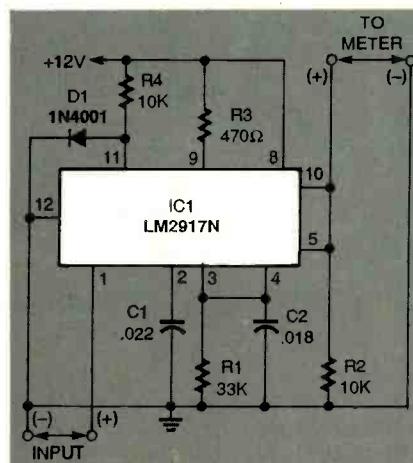


Fig. 11 Adding an LM2917 to the 7107's inputs lets you measure lower frequencies up to about 10 kHz.

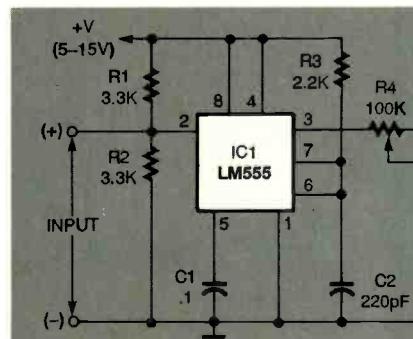


Fig. 12 To measure higher frequencies than the LM2917 can handle, this circuit does the job quite well. Frequencies in 3 ranges up to 2 MHz (1.999 x 1000) can be measured.

often sold by the pound at a greatly reduced price, but due to factory marking, or no marking at all, it can be hard to determine the values of those. A capacitance meter solves the problem, but most commercial meters are


relatively expensive.

Figure 10 is the schematic for a unit that makes use of a 4093 quad 2-input NAND Schmitt trigger, and will measure capacitors from 2 pF to 2 μF in two ranges. The low setting handles 2 to 1,000 pF while the high setting is for capacitor values from 0.001 to 2 μF. The circuit hooks up directly to the 7107.

Once connected to the 7107, calibration is simple. Turn the unit on and adjust R4 for a zero reading. With S1 in the low setting, connect a 100-pF capacitor to the test leads, and adjust R1 for a reading of "0100". Then switch S1 to the high setting, and with a 1-μF capacitor connected to the test leads, adjust R5 for a "1000" display. With that done, the meter is now ready to test and measure capacitors within the meter's range.

It is a good idea to conduct those last two steps with several known capacitors to fine-tune the calibration. While not shown in the schematic, it is common practice when using CMOS-technology ICs to connect the inputs of any unused logic gates (e.g., pins 11 and 12 of IC1) to either ground or the positive voltage. That will reduce power consumption and interference. On a final note, be sure the + 5-volt supply is well regulated to maintain accuracy.

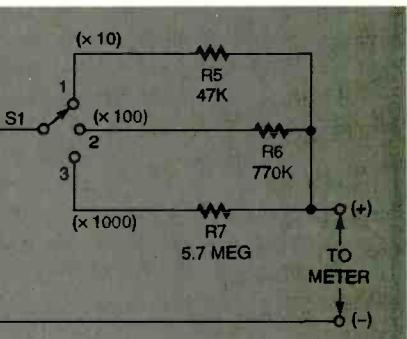Frequency Measurements. Figure 11 uses the LM2917N frequency-to-voltage converter in a standard configuration. That device is a simple and



inexpensive way of displaying frequency with the 7107. The 2907/2917 series was originally designed for tachometer systems, and is limited to frequencies from DC to about 10,000 Hz. (Continued on page 79)

Understanding Digital Filters, Using Your Time Profitably, and More

I RECENTLY GOT A HELPLINE CALL FROM SOMEONE WHO STRONGLY FEELS THAT THEY HAVE ONCE AND FOR ALL SOLVED THE CELLULAR-PHONE FRAUD PROBLEM. THAT SOLUTION WAS BASED ON THE USE OF HIS ELEGANT SYSTEM-

software modification. The question was how to profitably market the concept. Well, maybe, or maybe not.

Without a closer look, and even if it did not have any obvious or hidden flaws, the chances are that this caller's simple solution would only further escalate the cell wars a notch. But that's not the problem.

The problem is that certain things can be sold by small-scale start-ups or independent individuals, while some can not. Whenever you come up with what you think is a solution to an industry problem, it seems to me that there are

three key questions you should ask:

- **Are you an industry insider?** Do you aggressively subscribe to all the field's trade journals, read its books, attend its shows, and network with its experts? Do you thoroughly *grok* the fundamental technical and marketing principles of the industry?

If not, the odds are overwhelming that you're developing a non-solution to a non-problem. You probably do not possess the skills or the tools to even understand the real problem, let alone correct it. And that the "gotchas" here are certain to "git ya."

- **Does the field welcome innovation?** If the industry 1) has areas that are highly regulated; 2) has a complex infrastructure; 3) is controlled from a solidly entrenched oligopoly; or 4) requires major changes for your concept to fly, it is not a reasonable place for you to be spending your time and effort. Also, avoid investing time in fields populated by lawyers eager to eat innovators for lunch, or one that is subject to lawsuits, etc.

- **Can you sell six of them?** Your best concepts are those you can sell to real people who have real wallets in their back pockets, with real credit cards in them. If you cannot sell a few of your designs to your friends, there is no way you will ever sell lots of them to your enemies.

Let's look at some "for instances." If reasonably priced, your improved laptop battery would be instantly gobbled up as a sure-fire winner. But that very same battery technology for an electric car is pretty near certain to get ruthlessly stomped upon.

A new personal-airplane design is guaranteed to bankrupt you—every time. But a variant sold as a quarter-sized R/C model kit could be a very popular product, especially when it doubles as a video platform.

More to the point: A snap-on accessory that an end-user can attach to a phone to eliminate cellular fraud is workable. But fundamental changes in the cellular standards and distribution are not. At least not for most small scale startups or outside individuals.

Sure, it's real difficult not to get excited about a new concept. Long ago, I allowed low-pressure pneumatic

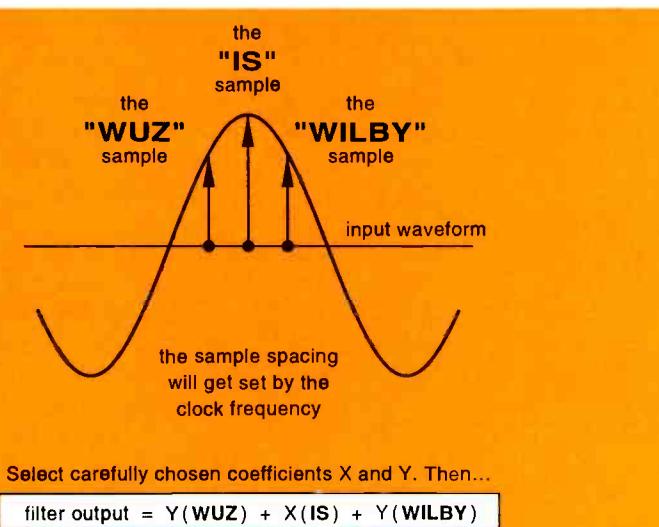


FIG. 1—THE "TRISAMP" is a useful building block that can let you understand, design, test, debug, and apply digital filters.

new from **DON LANCASTER**

ACTIVE FILTER COOKBOOK

The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. \$28.50

CMOS AND TTL COOKBOOKS

Millions of copies in print worldwide. THE two books for digital integrated circuit fundamentals. About as hands-on as you can get. \$28.50 each.

INCREDIBLE SECRET MONEY MACHINE II

Updated 2nd edition of Don's classic on setting up your own technical or craft venture. \$18.50

LANCASTER CLASSICS LIBRARY

Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. \$119.50

LOTS OF OTHER GOODIES

Ask the Guru I or II or III	\$24.50
Hardware Hacker II, III or IV	\$24.50
Micro Cookbook I	\$19.50
PostScript Beginner Stuff	\$29.50
PostScript Show and Tell	\$29.50
Intro to PostScript Video	\$29.50
PostScript Reference II	\$34.50
PostScript Tutorial/Cookbook	\$22.50
PostScript by Example	\$32.50
Understanding PS Programming	\$29.50
PostScript: A Visual Approach	\$22.50
PostScript Program Design	\$24.50
Thinking in PostScript	\$22.50
LaserWriter Reference	\$19.50
Type 1 Font Format	\$16.50
Acrobat Reference	\$24.50
Whole works (all PostScript)	\$380.00
Synergetics Surplus Catalog	FREE
Technical Insider Secrets	FREE

POSTSCRIPT SECRETS

A Book/Disk combination crammed full of free fonts, insider resources, utilities, publications, workarounds, fontgrabbing, more. For most any PostScript printer. Mac or PC format. \$29.50

BOOK-ON-DEMAND PUB KIT

Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. \$39.50

THE CASE AGAINST PATENTS

For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set shows you Don's tested and proven real-world alternatives. 28.50

BLATANT OPPORTUNIST !

The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. \$24.50

RESOURCE BIN I

A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. \$24.50

FREE SAMPLES

Check Don's Guru's Lair at <http://www.tinaja.com> for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resources, too. Tech help, hot links to cool sites, consultants. email: don@tinaja.com

FREE US VOICE HELPLINE

VISA / MC

SYNERGETICS
BOX 809-NV
Thatcher, AZ 85552
(520) 428-4073

CIRCLE 205 ON FREE INFORMATION CARD

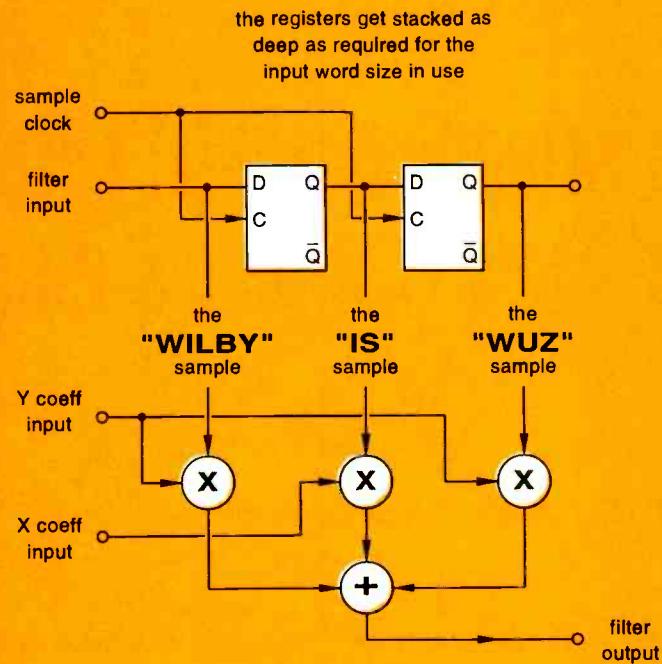


FIG. 2—DIGITAL FILTERS can be much more powerful than analog ones because they can look both forward and backward in time. The need for a "time machine" is avoided by using the shift-register scheme shown here.

robotics to gobble up all sorts of time and resources. And my magic sinewave development is currently using as much as twenty hours a day of my time. But, as hard as it is to do, you must focus on stuff that is technically challenging and still marketable by a small scale start-up if you are to be successful. Asking the fundamental questions outlined above ahead of time can save you lots of hours and grief and lets you focus your time and energy in better directions.

For much more on all this, see my *Case Against Patents* package, WHEN2PAT.PDF on www.tinaja.com, and, of course, my *Incredible Secret Money Machine*.

Digital Filters

Most books on digital filters seem excessively and unnecessarily arcane to me. This month, let's instead try a totally different and off-the-wall approach.

A filter is just some frequency-selective network that is designed to favor certain frequencies over others. It is usually used to isolate a desired signal or to improve the signal-to-noise ratio of a system. For example, the treble control on your hi-fi is a low-pass filter, the bass control is a high-pass filter, and AM radio tuning uses a bandpass filter.

Traditional filters were originally built with capacitors and inductors. Many of those were replaced long ago by active filters—combinations of resistors, capacitors, and op-amps that exactly fake inductors. You can find more details on that in my *Active Filter Cookbook*.

In contrast, a digital filter takes an existing pile of numbers and runs multiply-and-add calculations upon them to create a new pile of numbers whose behavior will, we hope, be "better" in some way or another than the original. For instance, a stream of digital video can become digitally high-pass filtered to improve its sharpness, or low-pass filtered for softening or to eliminate slanted "jaggies".

Plus and Minus

There are bunches of advantages to digital filters. First and foremost, a well designed digital filter is always "correct" and never needs "tuning". A digital filter could easily be adjusted over an incredibly wide range using software. Digital filters can often be swept without any nasty transients.

Special circuitry could be totally eliminated if the digital filtering gets done inside a stock microprocessor or a DSP digital signal processor.

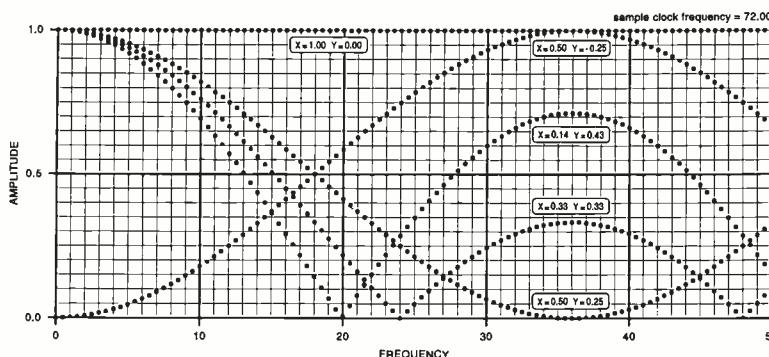


FIG. 3—HOW A TRISAMP'S FREQUENCY RESPONSE varies when its X and Y coefficients are changed.

Best of all, a digital filter can do certain tasks that end up being difficult or impossible when using classic analog designs. For one thing, in a sense, they can look forward and backward in time. That is, unlike capacitors and inductors, they can react to currents and voltages that are yet to happen; classic analog components can only react to things that have already occurred.

Examples here include "brick-wall" filters with extremely sharp cutoffs and linear-phase filters that attenuate a waveform's harmonics without any time-shifting distortion.

There are also disadvantages and limitations to digital filters. While they are a lot simpler than some may have you believe, they still are rather hard to understand.

You do already have to have your pile of numbers before you can filter them. Thus, A/D and D/A conversion might be needed in your system.

There is a really ugly property of digital filters called aliasing. If you sample any waveform less than twice per cycle, you might "fold over" and generate lower-frequency noise and artifacts. Very rarely, aliasing can be a valuable tool, one that lets you do digital mixing, downsampling, or a downconversion. But far more often, aliasing is a major nuisance that must be dealt with by pre-filtering.

Here's a rule to follow when working with digital filters: Input signals to a digital filter must get prefiltered so that zero energy exists above one-half of your sample frequency. That is, unless you have some really good reason to be doing otherwise!

The dynamic range of any digital filter is limited by several factors. Those

include your input and output word sizes, truncation errors, and any round-off errors.

Because you are often adding up very small differences between large values, the internal word size usually has to be much larger than that of the input or output. Thus, digital filters are much more suited to larger input signals than to very small ones.

Simpler digital filters apply integer math or fixed-point arithmetic. Such filters are faster and easier to implement, but have reduced dynamic range.

Exotic digital filters can use a full floating-point processing for all their math. While more accurate, floating-point filters often run much slower, either restricting the maximum input frequency or forcing you to move to non-real-time applications.

Finally, if your filter only works with a small number of samples, you might get into some ugly windowing problems. Softening the edges of a window or making sure that the edges happen where they don't cause problems are two

possible cures. Watch out for that windowing detail, or it will nail you every time.

Trisamp Building Blocks

My approach in the *Active Filter Cookbook* was to use a basic analog building block called a second-order section. No matter how exotic your filter response, all you really ended up with was a pile of those cascaded sections. And each section only had two possible adjustments—the cutoff frequency and its damping.

Let's try something similar here. I'll call our basic building block a "trisamp," and it is shown in Fig. 1. Just as you can use and cascade second order analog sections, you can use and cascade trisamps.

A trisamp gathers in three samples of a waveform. Which I will call "wuz," "is," and "wilby." It then scales them and adds them all together by using this fairly simple rule:

$$\text{output} = Y(\text{was}) + X(\text{is}) + Y(\text{wilby})$$

Since a digital filter is a linear type of "thingy," it should not matter what frequency or what phase we use for our analysis. Thus, we can apply just one frequency at a time to determine our overall response and arbitrarily pick an "is" phase of 90 degrees.

For a single-frequency sinewave input, your output should be a scaled amplitude clone of your input. The output will be larger or smaller than the input, depending on the values and signs of X and Y, and upon the ratio of your input frequency to the sample-rate clock.

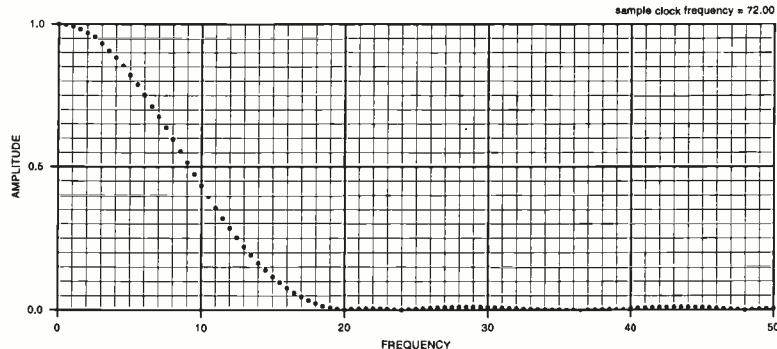


FIG. 4—A LOW-PASS FILTER built by cascading three trisamps. This is a "distortionless" or linear-phase filter that is extremely difficult to build using older analog techniques. To simplify your final design, using ordinary algebra easily reduces three cascaded trisamps into a single, seven-sample "septisamp." Additional samples improve response shape.

```
% PostScript triple cascaded trisamp digital filter designer v 2.04
%
% Copyright c 1996 by Don Lancaster and Synergetics, Box 809, Thatcher, AZ
% 85552 (520) 428-4073 http://www.tinaja.com All commercial rights and all
% electronic media rights are fully reserved. Reposting is expressly forbidden.
%
% For best results, improve with Guru Gonzo PostScript utilities. Enhanced and
% fully annotated version available as TRISAMP.PS on www.tinaja.com

% draw a graph:
110 350 translate 8 dup scale 0.03 setlinewidth 1 setlinecap gsave 0 0 moveto 51
{0 0 moveto 0 20 rlineto 1 0 translate} repeat stroke grestore gsave 0 0 moveto 21
{0 0 moveto 50 0 rlineto 0 1 translate} repeat stroke grestore 0.12 setlinewidth
gsave 3 { -0.5 0 moveto 50.5 0 rlineto 0 10 translate} repeat stroke grestore gsave
6 { 0 -0.5 moveto 0 20.5 rlineto 10 0 translate} repeat stroke grestore

/dot { newpath 0.150 0 360 arc fill } def % dot utility

/tripletrisamp {0 0.5 50{/freq exch store 180 freq mul sampfreq 2 div div cos
coeffB mul 2 mul coeffA add /firstholt exch store firstholt abs 20 mul freq exch
dot 180 freq mul sampfreq 2 div div cos coeffD mul 2 mul coeffC add /secondhold
exch store secondhold abs 20 mul freq exch dot 180 freq mul sampfreq 2 div div
cos coeffF mul 2 mul coeffE add coeffC coeffD 2 mul add div /thirdhold exch store
thirdhold abs 20 mul freq exch dot firstholt secondhold mul thirdhold mul abs 20
mul freq exch dot} for} def

% ///// demo - remove or alter before reuse. /////

/sampfreq 72 def % set sample clock frequency
/coeffA 2.0 4 div def % center of first trisamp
/coeffB 1.0 4 div def % pair
/coeffC 1.0 3 div def % center of second trisamp
/coeffD 1.0 3 div def % pair
/coeffE 1.0 7 div def % center of third trisamp
/coeffF 3.0 7 div def % pair

tripletrisamp showpage quit % do it and flaunt it
```

FIG. 5—THIS POSTSCRIPT TRIPLE TRISAMP exploration utility could make you an instant digital-filter-design expert. The code shown here can be easily expanded.

The X and Y values are known as coefficients. And while you could select different coefficients for "was" and "wilby," that change would add or remove time delay to your response.

Forcing the coefficients for "was" and "wilby" to always be identical can give you the class of "distortionless" filters known as linear-phase filters. Those are especially significant for data communications applications, and can be extremely difficult to do when using the older and more traditional analog design methods.

Which leaves dealing with

Negative Time?

So how do you find out who "wilby" is without a time-travel machine?

Simply look one stage previous in the shift register scheme of Fig. 2, or access one sample address earlier in a memory data bank. This is sort of the same way

any vertically delayed scope lets you look at the waveform edge you have just triggered on.

Let's look at the responses we can expect from a trisamp as we vary its coefficients and the input frequency. Naturally, I prefer to use the superb PostScript general purpose computer language for this. I will use 72 clock samples per fundamental cycle.

Figure 3 shows you several trisamp responses. Positive Y values result in low-pass shapes and negative Y values result in band-pass shapes. Also, in general, the overall peak gain is set by the absolute value of the sum of X and Y. Gains near unity are often used to keep the results from getting too large or disappearing entirely.

For instance, a Y value of zero and an X value of one simply copies the peak value to the output for a flat or an all pass response. Next, consider Y = 0.25

and X = 0.50. At low frequencies, "wuz," "is," and "wilby" are nearly on top of each other, so they pretty much sum to 1.0 and give us nearly unity gain.

But at the frequency whose time period equals exactly 36 clock cycles, an interesting result happens. "Wuz" and "wilby" end up on negative cycle peaks, and "is" sits on a positive cycle peak. In other words, they sum to zero!

Other X and Y coefficients create the shapes shown. By themselves, those shapes may be interesting. But they aren't all that useful. So, to get useful response shapes, you must cascade your trisamps.

Figure 4 shows a highly desirable linear-phase, low-pass filter made by cascading the three trisamps shown. Note the excellent stopband response. And the modest droop in the passband is fairly typical of linear-phase filters. Most important, there is zero excess phase shift to higher frequency harmonics. That property is very important in telecomm filters and for wave analysis.

Yes, you can easily re-graph this result in semi-log frequency-vs.-decibels for a more traditional-appearing, classic response plot. Among other features, that re-plot would make the stopband zeros more obvious.

Actually, nobody really cascades trisamps. Go through some simple algebra and you can quickly prove that any two cascaded trisamps are the same as a five-coefficient filter. And three cascaded trisamps are the same as a seven-coefficient filter. So you apply a pentasamp or a septsamp instead. All digital filtering amounts to is finding the right coefficients to use for the result you are after.

PostScript code to do a seven-coefficient filter made from three cascaded trisamps is shown in Fig. 5. You could easily use that routine to explore fancier digital-filter response shapes on your own. Just modify the coefficients with your favorite word processor or editor. Then send it to GhostScript or route it to almost any PostScript printer.

Lots more PostScript-as-language details are found on www.tinaja.com For an amazing range of applications, PostScript can completely blow away the more traditional general purpose computer languages.

Incidentally, more coefficients are normally chosen for fancier shapes.

Plug a Friend into

Electronics

NOW®

*and Save \$26.03**

This Christmas give an electrifying gift ... plug a friend into Electronics Now and brighten the whole new year! Whether electronics is your friend's livelihood or hobby, your gift will illuminate the whole spectrum of electronics throughout the coming year and provide a monthly reminder of your friendship.

Electronics Now will keep your friend informed and up-to-date with new ideas and innovations in all areas of electronics technology ... computers, video, radio, stereo, solid-state devices, satellite TV, medical electronics, communications, robotics, and much, much more.

We'll provide great plans and printed circuit patterns for great electronic projects. In just the last few years, Electronics Now has presented amateur TV equipment, robots, computer peripherals, microcontroller programmers, test equipment, audio amplifiers, telephone projects, relay circuits, and much more.

PLUS ... equipment troubleshooting techniques ... circuit design ... reports on new technology and products ... equipment test reports ... in-depth coverage on computers, video, audio, vintage radio ... and lots more exciting features and articles.

SAVE \$26.03* ... OR EVEN \$52.06* ... For each gift of Electronics Now you give this Christmas, you save a full \$26.03* off the newsstand price. And as a gift donor, you're entitled to start or extend your own subscription at the same Special Holiday Gift Rate—you save an additional \$26.03*!

No need to send money ... if you prefer we'll hold the bill till January, 1997. But you must rush the attached Gift Certificate to us to allow time to process your order and send a handsome gift announcement card, signed with your name, in time for Christmas.

So do it now ... take just a moment to fill in the names of a friend or two and mail the Gift Certificate to us in its attached, postage-paid reply envelope. That's all it takes to plug your friends into a whole year of exciting projects and new ideas in Electronics Now!

*Basic sub rate — 1 yr/\$19.97 2 yrs/\$38.97

Names and Numbers

**American Institute
of Organbuilders**
PO Box 130982
Houston, TX 77219
(713) 529-2212

Clement Engineering
PO Box 1086
Severna Park, MD 21146
(410) 268-6736

Compu-Mart
899 Presidential, Ste. 110
Richardson, TX 75081
(800) 864-1155

Dukane Ultrasonics
2900 Dukane Drive
St Charles, IL 60174
(708) 584-2300

Genesis Microchip
2111 Landings Drive
Mountain View, CA 94043
(415) 428-4277

Harris Semiconductor
Box 883
Melbourne, FL 32902
(407) 724-7000

ICT
2123 Ringwood Avenue
San Jose, CA 95131
(408) 434-0678

Mitel
2321 Morena Blvd., #M
San Diego, CA 92110
(619) 276-3421

Qualcomm Inc
6455 Lusk Blvd.
San Diego, CA 92121
(619) 587-1121

Redmond Cable
15331 NE 90th Street
Redmond, WA 98052
(206) 882-2009

Schott
3 Odell Plaza
Yonkers, NY 10701
(914) 968-8900

Seagate
920 Disc Drive
Scotts Valley, CA 95066
(408) 438-6550

Synergetics
Box 809
Thatcher, AZ 85552
(520) 428-4073

Thomson CFS
40G Commerce Way
Totowa, NJ 07511
(201) 812-9000

Wale Apparatus
400 Front Street
Hellertown, PA 18055
(800) 334-WALE

Western Reserve Games
21651 Tungsten Road
Euclid, OH 44117
(800) 531-1230

Your first few printouts (and anything "new" after that) will always be very slow.

A local hard disk instead saves a font cache for you. There is normally not any speed-difference slowdown on your first few files.

Hard disks are also real useful for PostScript-as-language apps where they can serve as your primary I/O. They are also quite handy to log what is coming into your printer, to solve interface hassles, to convert formats, or to grab otherwise inaccessible data or commands. Once you have used a PostScript printer that offers a hard disk, it is unthinkable to ever again so much as walk through a room housing a printer that lacks one.

The only tiny 5SiMX problem is that the HP disk drive has been undeliverable—and it appears permanently so now as HP has gone completely out of the hard-drive business. Well, it turns out you can easily substitute your own hard drive—for as little as \$35—after you know and understand a few simple things.

Let's excerpt some key info from the HPs *LaserJet 5SiMX Developer's Quick Reference Guide*:

"The standard 2½-inch ATA IDE disk drive interface is supported. (ATA stands for 'AT Attachment, as in the IBM PC-AT bus. And IDE stands for Intelligent Drive Electronics.) This printer is designed to allow these drives to be mounted directly to the formatter board.

"The disk drive attaches to four standoffs. It is electrically connected via a ribbon cable.

"The Seagate ST9420AG is the disk that has been qualified to work in the LaserJet 5SiMX printer."

The developer's guide is available through HP Developers. My favorite source for custom cables is Redmond Cable. The oddball 2-millimeter bulk ribbon cable and connectors are sold by Digi-Key or Mouser (this is sometimes called a mini-IDE or "European" cable).

Bargain drives often show up in *Compu-Mart*, *Computer Hot Line*, and similar publications. Note that non-Seagate drives may be larger and have different mounting holes. Older and larger 3½-inch drives are most likely not worth the hassle. Besides needing excess supply current, their larger pinouts take a special adaptor.

Typical hardware building-block chips offer four coefficients each. Those can get cascaded "wide" to handle twelve to sixteen or more coefficients. Or, they can be cascaded "deep" to handle the number of bits in a fixed-point word. Harris and Qualcomm are two big sources for these dedicated chips, but you can easily do the same thing with a PIC microprocessor.

I've been using digital filters as an important part of my magic-sinewave research. Magic sinewaves are my brand new way for simplifying and dramatically improving the efficiency of such products as variable-speed induction-motor drives, solar panels, and electric cars. You can find a lot more about them and all the new research opportunities they present on my Magic Sinewave shelf, which is in the www.tinaja.com reference library.

5SiMX Hard Drives

As we saw a couple of months or so ago, the Hewlett-Packard 5SiMX is an ideal mid-range PostScript laser printer,

one well suited to book-on-demand publishing. Its many features include genuine Adobe PostScript Level II, 24 pages-per-minute print speed, a page-flipping duplex, 11 × 17 capability, refillable toner cartridges (offering excellent economics), 600 DPI resolution, and photo halftone enhancements; and all the service manuals and parts are readily available.

It also has, at least in theory, a hard disk.

Scant few printer users appreciate how absolutely crucial a local hard disk is for a PostScript printer (though Apple and QMS have had them for years). First, your hard disk lets you store lots of fonts. Second, it lets you stash all of your book-on-demand files so you'll never have to tie up a network resending them. That same storage lets you do a run unattended for overnight BOD publishing.

The same goes in spades for often-used forms or patterns. When a diskless PostScript printer is first turned on, all of those needed font bitmaps have to be laboriously built up into a font cache.

Navigation Resources

Advanstar Communications

7500 Old Oak Blvd.
Cleveland, OH 44130
(800) 598-6008

GPS World

859 Willamette St.
Eugene, OR 97401
(503) 343-1200

Institute of Navigation

1800 Diagonal Rd., #480
Alexandria, VA 22314
(703) 683-7101

ITS World

859 Willamette Street
Eugene, OR 97401
(503) 343-1200

NASA Tech Briefs

41 E 42nd St., #921
New York, NY 10017
(212) 490-3999

NavTech Books & Software

2775 S Quincy St., #610
Arlington, VA 22206
(800) NAV-0885

SAE

400 Commonwealth Drive
Warrendale, PA 15096
(412) 776-4841

Trimble

585 N Mary Avenue
Sunnyvale, CA 94086
(408) 481-8000

Dukane. Bunches of traditional pipe-organ building info gets sold by the American Institute of Organbuilders, who offer various newsletters and conferences.

Two unusual glass topics: Glass paints are newly available through Wale Apparatus, while Foturan is a new photo-etchable glass product line from the Schott folks.

That long unclaimed \$10,000 prize for anybody able to convincingly demonstrate dowsing techniques to locate a buried water pipe has just been upsized to \$640,000. Contact www.randi.com for details. There's more on pseudoscience bashing in general on www.tinaja.com

For more on the fundamentals of digital integrated circuits, read my *CMOS Cookbook* and *TTL Cookbook*, either by themselves or as part of my bargain *Lancaster Classics Library*, per my nearby Synergetics ad.

As usual, many of the mentioned resources appear in our Names & Numbers and Navigation-Resources sidebars. A reminder that a no charge technical helpline is available per the Need Help box. Funding and time constraints strictly limit that service to U.S. callers only. Let's hear from you! EN

The last three digits of the Seagate part number are apparently its size. In the case of the unit referenced above, it is 420 megabytes.

Be extremely careful when you experiment here on your own! Any crossed cable can destroy both your drive and the printer electronics. Do not attempt to interface a SCSI drive. Unless you know all about fancy and expensive IDE to SCSI conversions. And, of course, never hot swap an IDE drive! Always turn power off.

On your PostScript software side, the drive is called "%disk0%." Fonts usually go in a fonts subdirectory. Although half a gig is vastly more storage than you are likely to need for this, there's one curious limitation: You are only allowed 1000 different files on your drive. Filenames can be one to 100-characters long. Nulls, backslashes, percents, end-of-file, and spaces are disallowed characters.

Again, much more on BOD in general can be found in my *Book-on-Demand Publishing Kit*.

Navigation Resources

I just got a flyer from Advanstar Communications on their brand new bookstore. This one focuses on GPS Global Positioning System and GIS Geographical Info System texts.

Because of that flyer, and since it's been a while, I thought we might summarize several of the better navigation info sources as this month's resource sidebar.

A good place to start is with the Navtech Bookstore. Then go on to those shows and publications from the

Institute of Navigation. Two important trade journals in this area are *GPS World* and *ITS World*; the latter focuses on "Intelligent Transportation Systems."

Finally, here's a reminder that Trimble has a great nav tutorial it calls *GPS—A Guide to the Next Utility*. Hot links to several useful GPS and nav sources are also found on www.tinaja.com.

New Tech Lit

New from Thomson-CSF, a new data book on their CCD Image Sensing Products. From Mitel comes an analog and digital Telecomm data book.

The PC1802 Stereo Enhancement Processor chip from ICT uses 3-D psychoacoustics to "spread out" the apparent source of stereo sounds. The new GMVLD10, from Genesis Microchip, is a real-time video-line doubler integrated circuit that is useful for de-interlacing. Uses for it include TV-to-monitor conversions and video walls.

The MIM Module from Clement Engineering can be useful for balloon telemetry and other remote sensing apps. Original jukebox manuals are sold by Western Reserve Games.


Some info on power ultrasonics appears in the *Waves* newsletter from

NEED HELP?
Phone or write all your US Tech Musings questions to:

Don Lancaster
Synergetics
Box 809-EN
Thatcher AZ, 85552
Tel: 520-428-4073

US email: don@tinaja.com
Web page: <http://www.tinaja.com>

MULTIMEDIA on the PC!

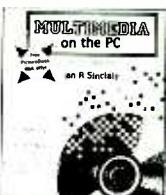
What is Multimedia? What can it do for you? It can do lots of nice things! This 184-page book helps you create your own multimedia presentation. Multimedia applications by people like you can revolutionize educational and business applications as well as bring more FUN, FUN, FUN into your leisure computer activities.

Mail coupon to:

Electronics Technology Today, Inc.
P.O. Box 240
Massapequa Park, NY 11762-0240

Please send me my copy of *Multimedia on the PC* (PCP120). I enclose a check or money order for \$18.95 to cover the book's cost and shipping-and-handling expenses. NY state resident must add local sales tax.

Name _____

Address _____

City _____ State _____ Zip _____

All orders must be paid in U.S. funds only. Sorry, no orders accepted outside of USA and Canada. Please allow 6-8 weeks for delivery.

MA02

Troubleshooting VCR Tape Path Alignment

WHEN EVERYTHING IS SET UP RIGHT IN A WELL-DESIGNED VCR, IT WILL RECORD AND PLAYBACK CLEAR, SHARP PICTURES. BUT EVEN MINOR MISADJUSTMENTS IN THE TAPE PATH COULD SEVERELY IMPACT THE QUALITY OF THE

video or the audio, or both. If there are severe misadjustments in the tape path, the tape itself can be damaged.

Figure 1 diagrams the tape path in a Hitachi VHS VCR. It is typical of, though not identical to, the path that VHS recording tape follows in many modern VCRs. The five key areas in the tape path that require adjustment to ensure that the tape travels in the proper vertical plane are shown in the diagram. As we go on we will describe each adjustment point and its importance in a properly aligned tape path.

Reel Table Height

The first tape-path point in Fig. 1 is where the reel-table height is set. That setting determines the height of the tape as it is taken up or supplied from either the supply or take-up reel tables. If either table height is misadjusted, making the tape lower or higher than normal, the edge of the tape can be damaged. Figure 2 shows how a misadjustment there can cause tape curling. In that example the reel table is too high, affecting the height of the tape at the entry point to the guide. The result is tape curling at the top edge of the tape, which can permanently destroy or distort the audio or control tracks on the tape. As shown in Fig. 3, those tracks are at the top and bottom edges of the tape. That kind of problem shows up as dis-

torted audio, with level changes; intermittent speed changes; or tracking problems.

Another problem caused by improper reel-table height is that it could cause the tape to be rewound into its VHS cassette improperly. That rewinding can

cause the tape to bind, and in some instances stretch, causing symptoms similar to those of tape-edge damage.

Tape Tension

Tape tension is the applied force of the tape at some particular point along the tape path of the VCR. In VHS VCRs, tape tension is regulated to insure video signal interchangeability between VCRs. Incorrect tape tension produces a number of different playback problems. Those problems show up as:

- **Tape Skew**—flagging or bending of the picture at the top of the viewing

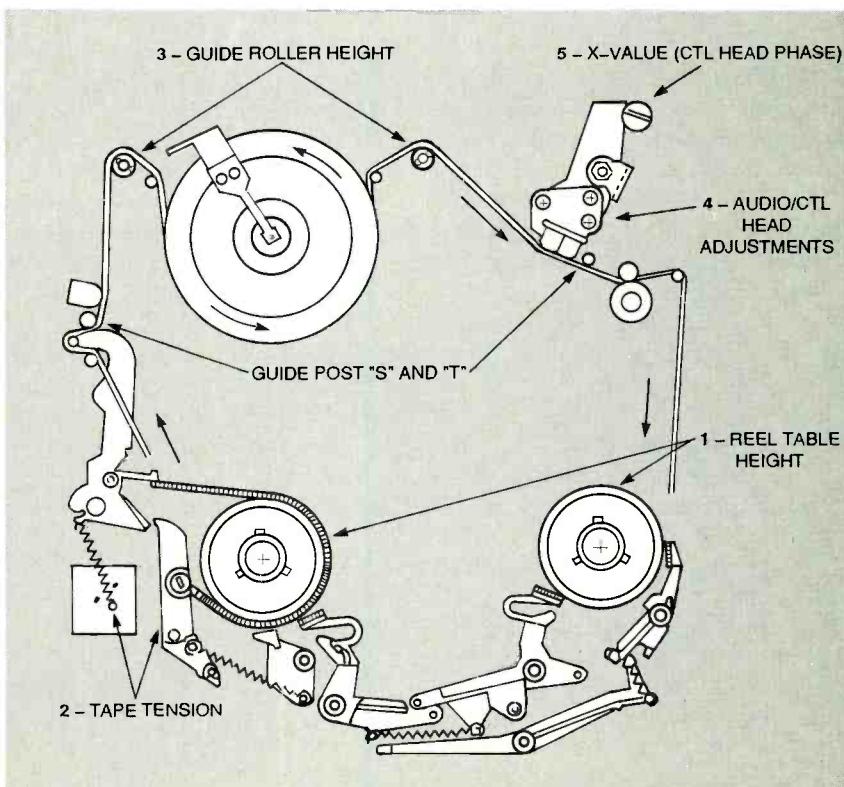


FIG. 1—THE VHS TAPE PATH shown here is from a Hitachi unit, but it is common to many VHS VCR's. Note the five major adjustment points.

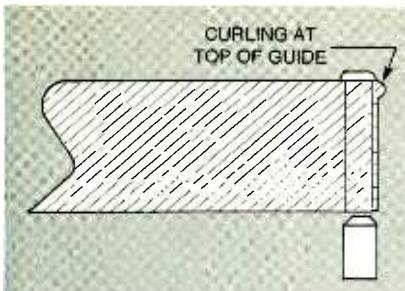


FIG. 2—TAPE CURLING AT THE TOP of the tape guide can be caused by a misadjusted reel-table height. If severe, it can physically damage the tape.

screen. That vertical bending is caused by horizontal time-base errors in the horizontal-sync pulses on the tape. Correct tape tension reduces horizontal time-base errors.

- **Intermittent Blue Screen**—triggered by the loss or excessive distortion of the playback video-sync signals. System-control microprocessors often monitor the sync signal, sending control codes to the character generator, which activates the blue screen whenever abnormalities are detected.

- **Upper Cylinder, Tape-Guide Damage**—severe, excessive tape tension can actually damage the upper cylinder and tape guides, causing surface scarring or excessive head wear.

Proper tape tension is clearly one adjustment that must not be overlooked. It is maintained throughout the tape path by a tension band, which is wound around the supply-reel table that continuously controls the braking force applied to the table. That braking force provides a variable resistance to the rotation of the supply reel when the tape is being withdrawn from the cassette-supply hub. To change the braking

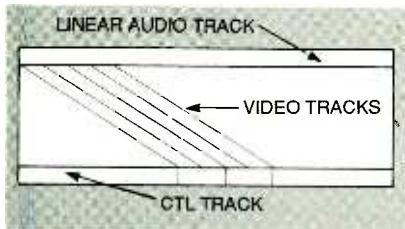


FIG. 3—THE AUDIO SIGNAL SITS ALONG the top edge of the VHS tape. Control signals are placed along the bottom edge.

force, a tension band is connected to a tension-arm assembly using a pole that is in continuous contact with the tape as shown in Fig. 4. The tape itself determines the pole position relative to the tape tension at any given point in time. As the tape is pulled from the supply-

reel table with more (or less) force, the pole position changes in proportion to the force, and the band around the supply-reel table alternately loosens (with increased tape-pull force) or tightens (with decreased tape-pull force) to maintain a constant back tension (resistance) against the tape.

Guide Rollers

Figure 5 shows two additional components that play an important part in determining the position of the tape as it travels though the tape path. Since no two VCRs have precisely the same mechanical path for tape travel, the supply and take-up guide-roller heights are adjustable to maintain interchangeability when playing back prerecorded video-cassettes. The guide rollers determine the height of the tape at the entrance and exit of the video-drum assembly, and control the tape travel across its surface. That ensures the correct positioning of the video head with respect to the video signals recorded on the tape (particularly the proper placement of the video-sync signals), and the point at which the video heads were switched from CH1 to CH2 during the initial recording.

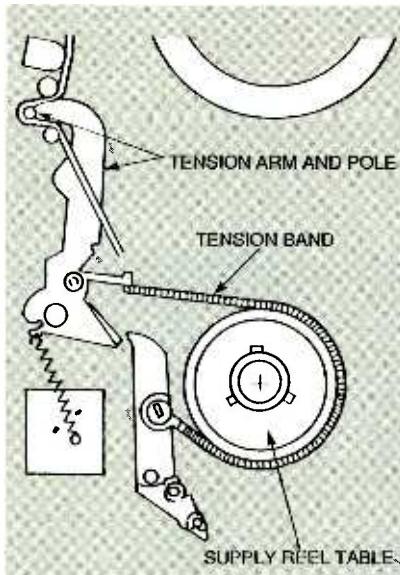


FIG. 4—TAPE TENSION MECHANICS are illustrated here. The tension band does most of the work.

Figure 6 shows what happens if a supply-guide roller is misadjusted. Note the noise bar that appears at the top of the screen. The particular guide roller that is misadjusted, and the degree of misadjustment, determines the number of noise bars and where they appear on

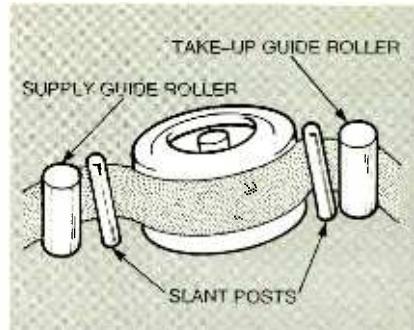


FIG. 5—TWO GUIDE ROLLERS—one before the video-drum assembly, one after—determine the tape position as it travels across the video heads.

the screen. A misadjusted guide roller can also cause tape curling, which results in distorted audio and distorted picture (noise bars, vertical jitter, and intermittent blue screen).

ACE Head

The ACE-head assembly is shown in Fig. 7. It is comprised of three heads that together support the audio and servo functions of the VCR. Those are:

- **Audio Erase Head**—a high-frequency AC bias current flows through the erase head to remove any previously recorded audio signal.

- **Linear Audio Head**—records and plays back the linear audio signal.

- **Control Track Head**—records a 30-kHz signal onto the tape to form a video-head reference. When a tape is played back, the video-head phase is aligned with respect to that recorded control signal.

The ACE head is adjusted to assure proper playback of the linear audio signal and to insure proper tracking when playing back prerecorded tapes. When adjusting the ACE head assembly, two of

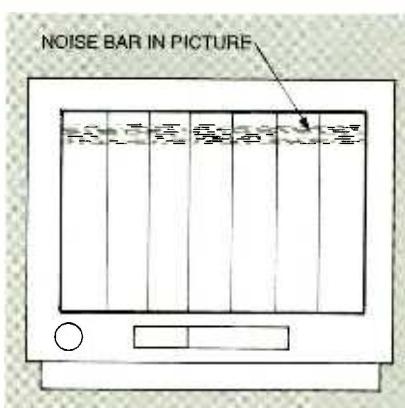


FIG. 6—THE NOISE BAR THAT APPEARS in the picture can be caused by a misadjusted guide roller.

Generating Laser-Light Patterns

THIS MONTH, WE ARE GOING TO TURN OUR ATTENTION TO THE WORLD OF GEOMETRIC PATTERNS AND SIGNS. THE LASER MARKET IS TEEMING WITH EQUIPMENT, RANGING FROM SIMPLE X-Y AXIS UNITS AND SCANNERS TO

elaborate, computerized professional controllers. All are designed to manipulate one or more laser beams into designs, patterns, moving artwork, lettering, or even sheets of light.

Such equipment is remarkable in terms of what it does, but costs start in the \$100 range for the most basic set-up and go up to \$15,000 and more for highly sophisticated machines.

While such specialized professional equipment is wonderful to work with, it is overkill for our experimentation purposes, and its cost puts it out of reach for many. But that doesn't mean that we can't experiment with laser special effects. Let's take a look at some of the simple and inexpensive equipment that can be built and methods that can be used to produce many of the same effects as the commercial units.

Simple Pattern Generators

To start, let's re-visit a set-up first discussed in the July 1996 installment of this column, and shown in Fig. 1. Mount a spring to a stand, as illustrated there, and attach a 1-inch-square piece of Mylar or top-surface mirror to the spring's free end. That set-up is the basis for several different simple pattern generators.

One tip when working with springs is that the action can be adjusted by expanding or contracting the coil. As a

general rule, a spring becomes springier when stretched. Use that principle to control the amount of reaction to touch or vibration.

Once the set-up is assembled, aim your laser so the beam reflects off the Mylar or mirror onto a flat, light-colored surface, and then give the spring a tap. That tap will make the spring oscillate, and the beam will follow suit. Thanks to the persistence-of-vision characteristics of the human eye, the

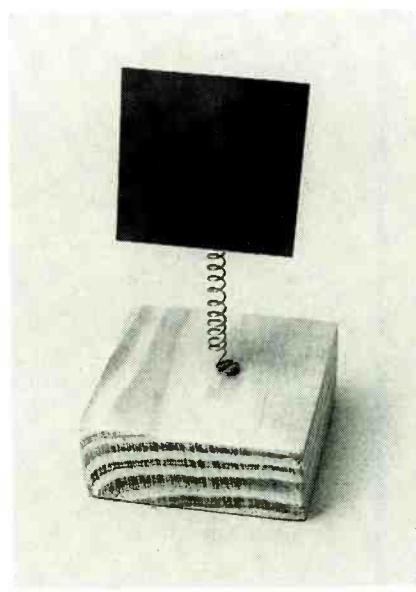


FIG. 1—A SQUARE MYLAR REFLECTOR attached to a spring that is anchored to a block of wood is one of the most basic laser-light reflectors.

WARNING!!!

This article deals with and involves subject matter and the use of materials and substances that may be hazardous to health and life. Do not attempt to implement or use the information contained herein unless you are experienced and skilled with respect to such subject matter, materials and substances. Neither the publisher nor the author make any representations as for the completeness or the accuracy of the information contained herein and disclaim any liability for damages or injuries, whether caused by or arising from the lack of completeness, inaccuracies of the information, misinterpretations of the directions, misapplication of the information or otherwise.

rapid movement of the spot generates random patterns and designs on the surface.

Repeat that step several times. Note that the patterns are never exactly the same twice. A blast of air or strong vibration can also vibrate the spring and create new light effects. Experiment with different forces and make note of what happens.

Electronic Pattern Generator

If you set up a small gear-reduction motor, rigged with an arm (say, a nail, for example) that will gently nudge the spring on each revolution, you'll have a way to produce more repeatable patterns for longer periods of time. The photo in Fig. 2 shows one way that can be done.

An electromagnet or solenoid can also be used to pulse the spring and move the reflector. Those devices can be driven from the output of an electronic timer that is also used to control the frequency of the pulse. Figure 3 shows a suitable circuit for a simple timer.

For more dramatic effects, use a dual timer, like the one shown in Fig. 4. In that circuit, first one electromagnet, then the other, is activated, and the sequence repeats. If the two electromagnets are placed at right angles to each other, a north-south, east-west movement can be established. That movement can produce some very interesting designs, especially if you vary the oscillation rate by changing the capacitance and resistance values.

Motorized Pattern Generators

Motors and mirrors make an excellent combination for generating graphics.

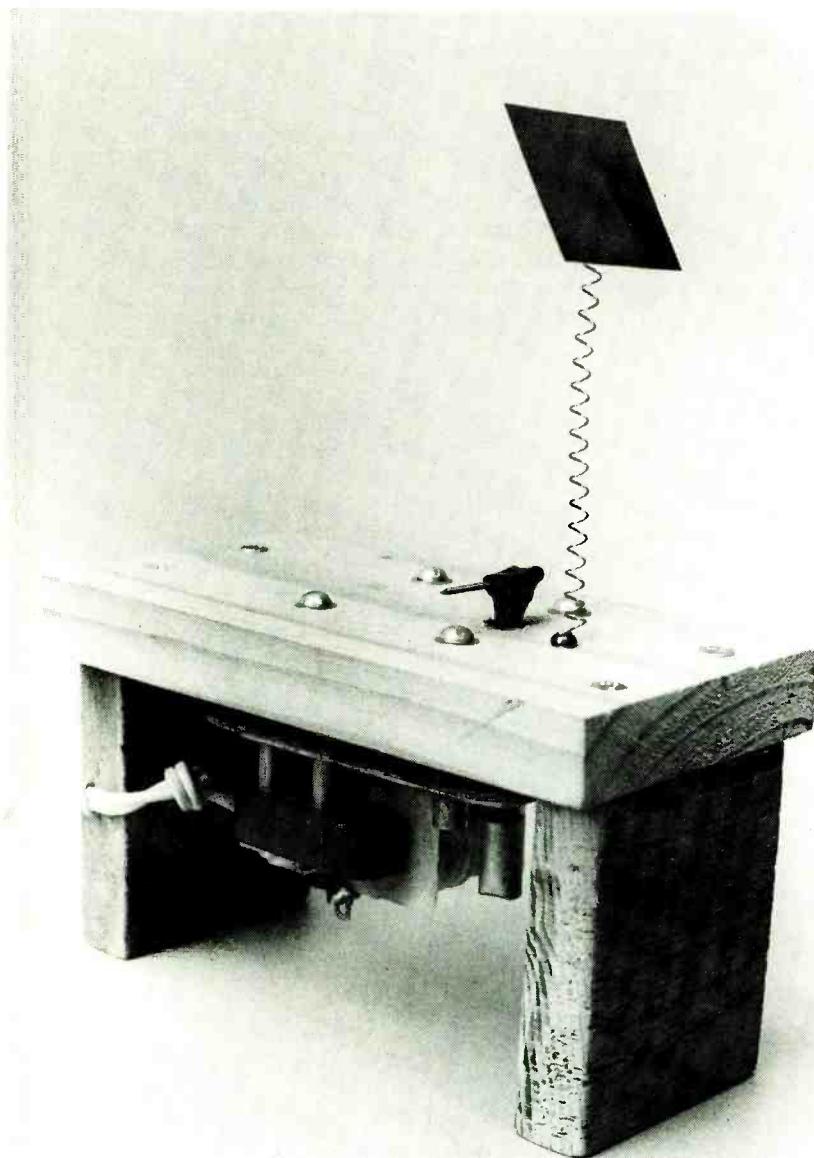


FIG. 2—FOR REPETITIVE VIBRATIONS, this simple set-up works well. A small gear-reduction motor rotates a nail, which strikes the spring one time each revolution. That rotation creates a repetitive movement in the reflector.

Attach reflective surfaces to the shafts of the motors. Then arrange the assemblies at various angles to each other. Now direct the laser beam between the mirrors and onto a screen. As the motors turn the mirrors, additional angle changes occur that vary the pattern.

Figure 5a shows a variation of the circuit in Fig. 4 that can be used to control a pair of motors. When the motors are connected to the circuit as shown in Fig. 5b, it will turn the individual motors on and off. If, on the other hand, you use the arrangement shown in Fig. 5c to control a single motor, it will make that motor first rotate in one direction and

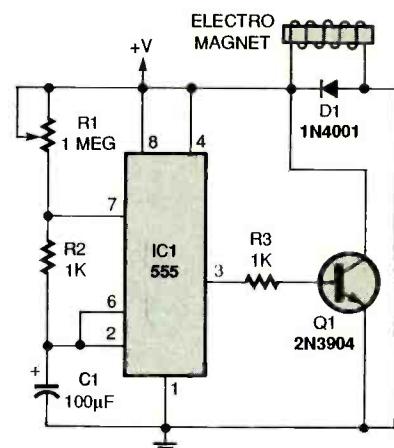


FIG. 3—A SIMPLE TIMER built around a 555 gives you a switching electromagnet to use to create laser-light patterns.

then the other. That set-up has all kinds of useful applications.

If you want to add yet another variable, you can provide a speed control by connecting a 5000-ohm potentiometer in series with the motor and power supply. Another variation would be to replace the flat mirrors with either convex or concave surfaces. One last area to consider is reflecting the laser beam off liquid surfaces such as water, oil, paint, etc. Different beam angles and vibrations of the substance being used as the

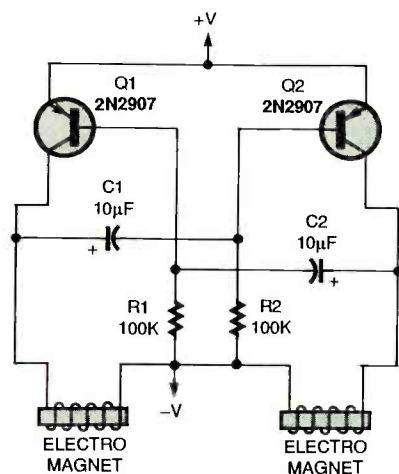


FIG. 4—IF THE ELECTROMAGNETS in this dual-timer circuit are arranged perpendicular to each other, a north-south, east-west motion can be established.

reflector can produce some delightful and interesting results.

It is obvious that a nearly endless variety of effects could be produced by making minor or more extensive

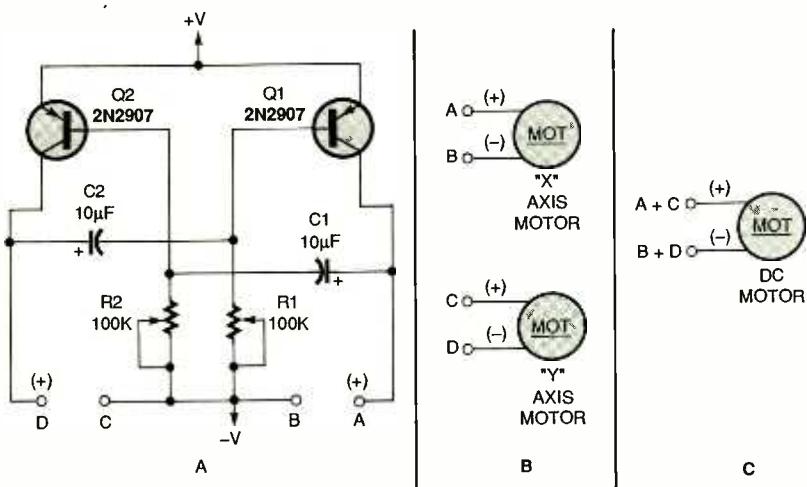


FIG. 5—THE MOTOR-CONTROL CIRCUIT (A) can be used to alternately turn two motors on or off (B). It can also be used to make one motor turn first in one direction and then the other (C).

changes to the basic set-up. Spend some time experimenting with the ideas presented, as doing so is a valuable source of knowledge.

Holiday and Other Displays

So, aside from special effects at rock concerts, what practical applications are there for what we have learned? Well, how about using lasers to create holiday displays that would be the talk of the neighborhood. Holidays, such as Christmas, Halloween, and Independence Day all lend themselves to the special effects lasers could produce. For

example, use mirrors, lenses, fiber optics, and such to uniquely personalize Christmas trees and other decorations with stunning light shows. The displays can be stationary or moving. They could spell out a holiday message. You are only limited by your imagination and the complexity of your design. If a PC is available, try setting up a program to control both the optics and mechanics for a variety of unusual results.

Halloween offers an endless opportunity for creativity. Just imagine the selection of spooky displays you could build around your laser. A spectacular demon-

stration for the Fourth of July could be assembled with the help of mirrors and motors to simulate fireworks. Let your imagination loose and when you do come up with a great idea, put it down on paper and send it to **Electronics Now**, Laser-Experiments Editor, 500 Bi-County Blvd., Farmingdale, NY 11735, or simply e-mail to lartronics@aol.com.

While on the subject of gaining attention, why not take a look at the possibilities for advertising. A swirling, pulsating light show projected on a billboard or a showroom ceiling or wall will immediately attract people passing by. In addition to the movement, there is something about the color and quality of the red light from a helium-neon laser that is difficult to ignore. The collimation not only makes the light bright, but also gives the beam and the surfaces it comes in contact with a shimmering effect that is hard to describe. For whatever reason, the experience is visually pleasant for most people.

EN

SERVICING

continued from page 69

the adjustments affect the way the tape travels across the tape path. These are the tilt and height adjustments.


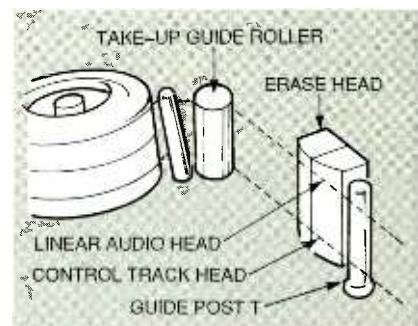


FIG. 7—ACE-HEAD ASSEMBLY is composed of three separate heads—audio erase, linear audio, and control track.

X-Value

The X-value adjustment, also known as the CTL head phase, or tape-interchangeability adjustment, is used to set the position (horizontally) of the ACE head. It insures that the recorded video signal and control-signal phase relationship is maintained when playing back tapes from different VCRs. You can be sure that tracking linearity is correct when the X-value is properly set.

EN

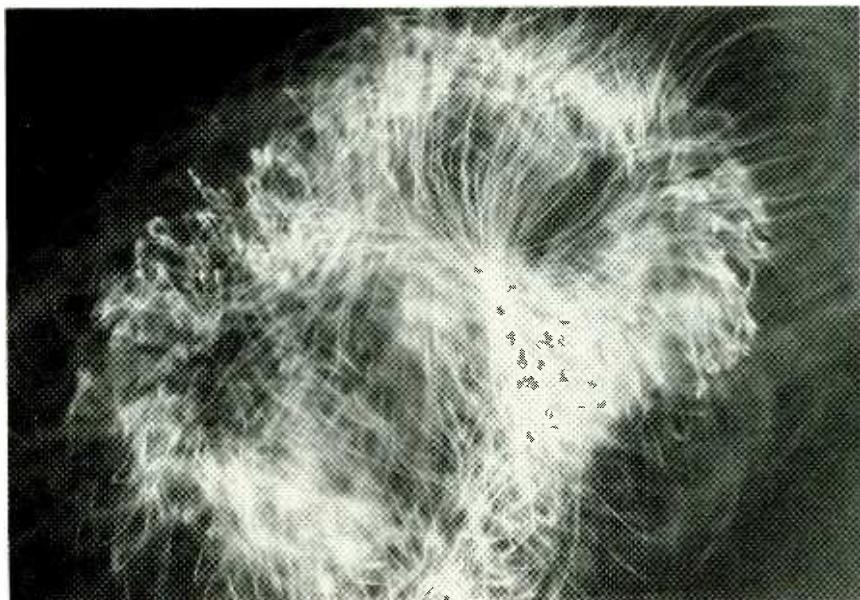

THIS IS ONE EXAMPLE of the kinds of light patterns that you can create using the information in this article.

EQUIPMENT REPORTS

continued from page 18

pressure or you can enter a new user. Each new user gets their own password and set of records. If you want, you can set the upper and lower pressure limits for each measurement—the smaller the range, the quicker each measurement can be made.

With everything connected and the software running, you simply follow software prompts to wrap the cuff around your arm, tighten the air valve on the bulb, start pumping, stop pumping and wait, and then to loosen the valve and release the air. The process takes about 30 seconds. All results appear on-screen and can be saved or printed.

The DynaPulse measures blood pressure in much the same way as a physician does. The inflatable cuff presses on the artery in your arm to the point where blood stops flowing. Then, as pressure is released, blood starts flowing at some point. At that point, the blood swirls in a turbulent flow causing a sound a doctor can hear with a stethoscope, and variations in pressure that DynaPulse can detect. The point where blood starts to flow is measured as the higher pressure point (systolic). At some point as pressure is released, the turbulence ceases; that's the lower pressure point (diastolic).

While it will not (and should not) replace a physician, DynaPulse is excellent for medical screenings by qualified personnel, or for home use to keep track of your blood pressure between doctor's visits. It also makes it very easy to store your results where they will never get lost. You can display long-term trends to monitor the effects of diet, exercise, medication, and so on (again, any diet or exercise regimen should first be discussed with and approved by your physician). Whether you're keeping track of just yourself, your whole family, or an entire organization, the DynaPulse 200M simplifies the task of taking and storing blood-pressure readings. **EN**

EARN YOUR B.S. DEGREE IN COMPUTERS OR ELECTRONICS



By Studying at Home

Grantham College of Engineering, now in our 46th year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, modem, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Grantham offers three separate distance-education programs, leading to the following accredited degrees:

(1) The B.S.E.T. with Major Emphasis in Electronics.

(2) The B.S.E.T. with Major Emphasis in Computers.

(3) The B.S.C.S.—the Bachelor of Science in Computer Science.


An important part of being prepared to move up is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by
the Accrediting Commission of the
Distance Education and
Training Council

GRANTHAM
College of Engineering
Grantham College Road
Slidell, LA 70460

You can Build Gadgets! Here are 3 reasons why!

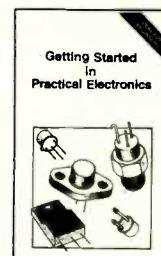


BP345—GETTING STARTED IN PRACTICAL ELECTRONICS \$5.95


If you are looking into launching an exciting hobby activity, this text provides minimum essentials for the builder and 30 easy-to-build fun projects every experimenter should toy with. Printed-circuit board designs are included to give your project a professional appearance.

BP349—PRACTICAL OPTO-ELECTRONIC PROJECTS \$5.95

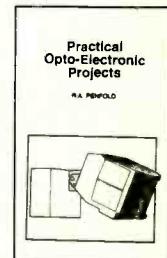If you shun opto-electronic projects for lack of knowledge, this is the book for you. A bit of introductory theory comes first and then a number of practical projects which utilize a range of opto devices, from a filament bulb to modern infrared sensors and emitters—all are easy to build.



Practical Electronic Music Projects

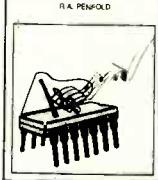

BP363—PRACTICAL ELECTRONIC MUSIC PROJECTS \$5.95

The text contains a goodly number of practical music projects most often requested by musicians. All the projects are relatively low-in-cost to build and all use standard, readily-available components that you can buy. The project categories are guitar, general music and MIDI.

Mail to:

**Electronic Technology Today, Inc.
P.O. Box 240
Massapequa Park, NY 11762-0240**

Shipping Charges in USA & Canada

\$0.01 to \$5.00	\$2.00	\$30.01 to \$40.00	\$6.00
\$5.01 to \$10.00	\$3.00	\$40.01 to \$50.00	\$7.00
\$10.01 to \$20.00	\$4.00	\$50.01 and above	\$8.50
\$20.01 to \$30.00	\$5.00		

Sorry, no orders accepted outside of USA and Canada. All payments must be in U.S. funds only.

Number of books ordered.

Total price of books..... \$ _____

Shipping (see chart) \$ _____

Subtotal \$ _____

Sales Tax (NYS only) \$ _____

Total enclosed \$ _____

Name _____

Address _____

City _____ State _____ ZIP _____

Please allow 6-8 weeks for delivery.

Only You Can Prevent Forest Fires.



Ad Council

Microphone Basics

SOUND IS GENERATED THROUGH A SPECIFIC MECHANICAL PROCESS. THAT IS, SOME PHYSICAL DEVICE MOVES OR VIBRATES, IN TURN MOVING THE AIR AROUND IT. ONE SIMPLE EXAMPLE IS A TUNING FORK. IF YOU HIT THE TUNING FORK

with a hammer (see Fig. 1), the fork vibrates at one specific frequency determined by its size and shape. The vibrations of the fork move the air around it. When those movements reach your ear, they are converted into electrical energy and sent to your brain to be processed and interpreted. (Of course, there is a lot more going on here than what we've just outlined; but, for our purposes, this simplified explanation will suffice).

Well, that process could also be used to describe how a microphone works. Like the ear, all microphones are sound conversion devices—they take sound and change it into electrical energy. There are three basic steps in this process:

1. Sound waves move the diaphragm inside the microphone.
2. The voice coil also moves, since it is attached to the diaphragm.
3. When the voice-coil moves, electrical energy is generated in the coil since it is located inside the microphone's magnet structure (magnet and magnetic housing).

The kind of microphone just described, shown in Fig. 2, is a dynamic or moving-coil type. The sound wave that reaches the microphone must be strong enough (or, rather, loud enough) to move the mass of the diaphragm and the coil assembly. That type of microphone works well, but does have some limita-

tions. It usually generates a small peak, sometimes called presence, somewhere between 2 and 5 kHz. Extremely-low and extremely-high frequencies can also give dynamic microphones some trouble. However, dynamic microphones are very durable and do not require any special handling. That's why they are so commonly used.

The amount of electrical energy that a microphone can put out partly depends on the amount of acoustical energy that reaches its transducer. In general, the louder the sound, the greater the electrical energy the microphone will produce, but there are limiting factors—the maximum possible movement of the voice coil for one.

Sound that we hear is usually measured in dB SPL (sound pressure level). That measurement ranges from 25-dB SPL (the level in a quiet broadcasting studio for recording music) to 140-dB SPL (a 50-HP siren). An average full symphony or orchestra has a dynamic

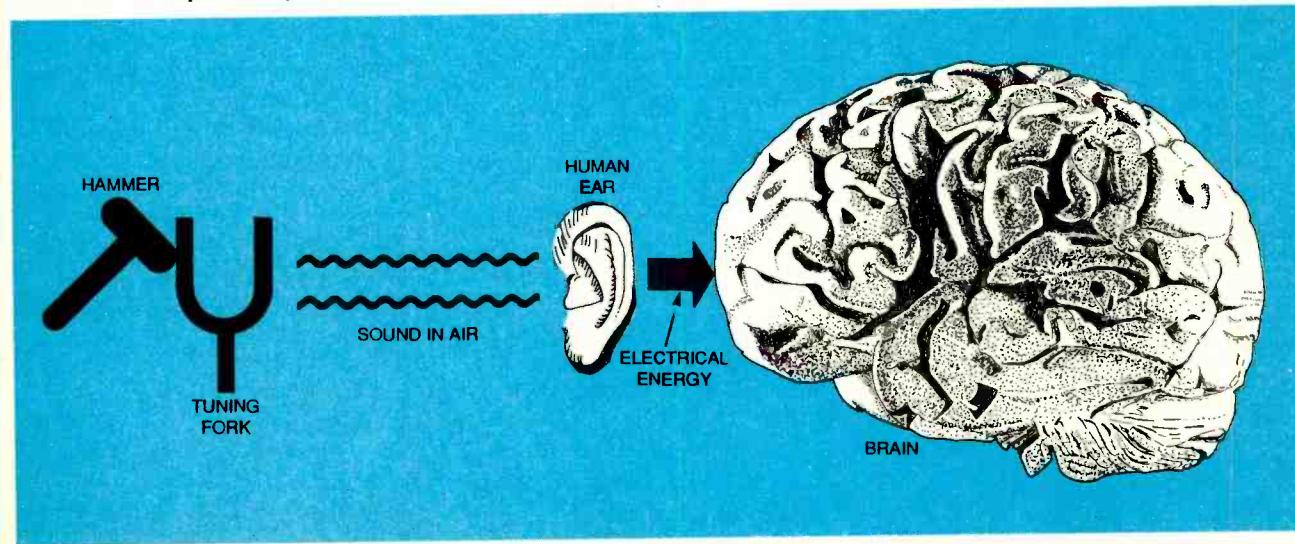


FIG. 1—HOW SOUND IS GENERATED. Striking a tuning fork is the method illustrated here.

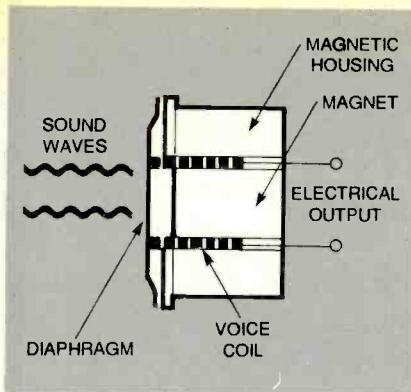


FIG. 2—MICROPHONES CONVERT sound waves into electrical signals.

range of 20 to 100 dB. The human ear has a dynamic range of about 120 dB, which is a ratio of a trillion to one. Analog recording has a 60-dB range (a million to one). Digital recording has a range of 90 dB (a billion to one).

As you can see from the above, the human ear is a very fine instrument indeed and should be treated with respect. Therefore, a microphone that can convert the air movement into an electrical signal within the very large dynamic range of the ear has a difficult job, at best.

Micophone Efficiency

Microphones work best when they are positioned as close as possible to the sound-generating source. As shown in Fig. 3, the voltage produced by a microphone falls off with the inverse square of the distance. Put another way, the voltage the microphone produces increases geometrically as the distance from the sound source decreases. However, there is a limit. If the microphone is too close to the sound source, there is a proximity effect that causes the low frequencies to

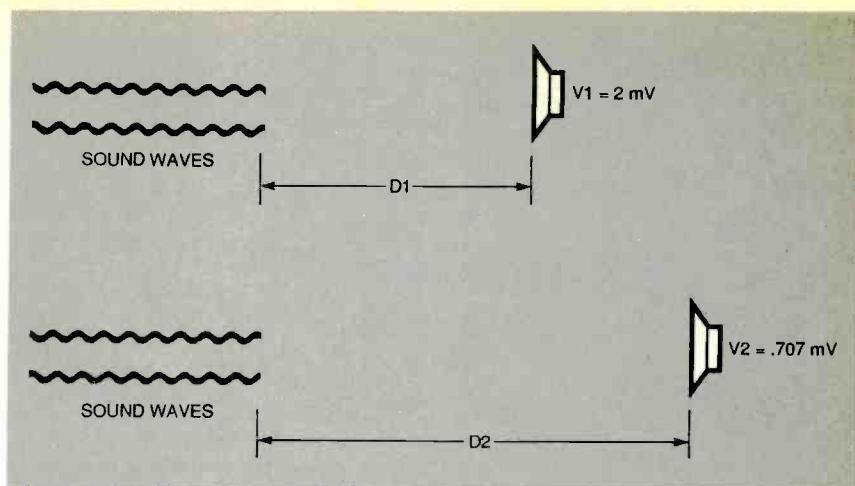


FIG. 3—A MICROPHONE'S OUTPUT FALLS OFF as it gets farther away from the source of the sound.

have a greater build-up than the high frequencies.

It is important to realize that microphones are never 100% efficient (their precise efficiency is not important to this discussion), and many factors come into play to reduce efficiency still further. For example, even temperature and humidity are important factors in the sound-reproduction process. That is one reason why studio recording is ordinarily very uniform, while remote recording can be quite variable. It is also why something that worked once might not seem right at another time. Most of those problems can be solved, but microphone users need to be aware that they can and do occur.

Types of Microphones

There are several different types of microphones. The first and most common is the dynamic microphone that we have been talking about. It has a small diaphragm with a coil of magnet wire

attached to it (see Fig. 4) that sits in the field of a permanent magnet.

The electret condenser type is the next most popular in today's marketplace. It is a permanently charged capacitor type with an FET amplifier built in. It is shown in Fig. 5.

Another type of microphones is the capacitor type; it is the forerunner of the electret type. Its major drawback is that it needs a power supply to charge its plates. An RF capacitor microphone is another quality way to convert sound waves into an electrical signal.

Acoustical Characteristics

Next, let's look at the acoustical characteristics of microphones, in order of their popularity. Figures 6, 7, and 8 are polar diagrams that show the pickup patterns of various microphone varieties. All three have some common elements and all are for a 1-kHz signal. At other frequencies the patterns might be different.

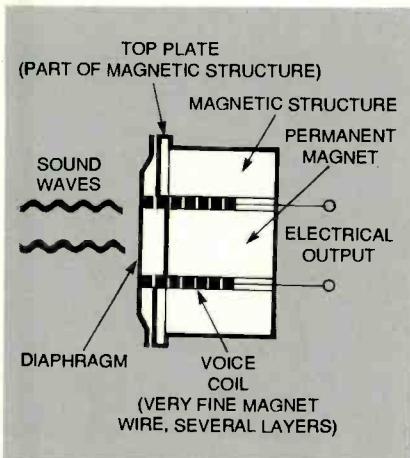


FIG. 4—THE BASIC DYNAMIC MICROPHONE. It is probably the most commonly used variety.


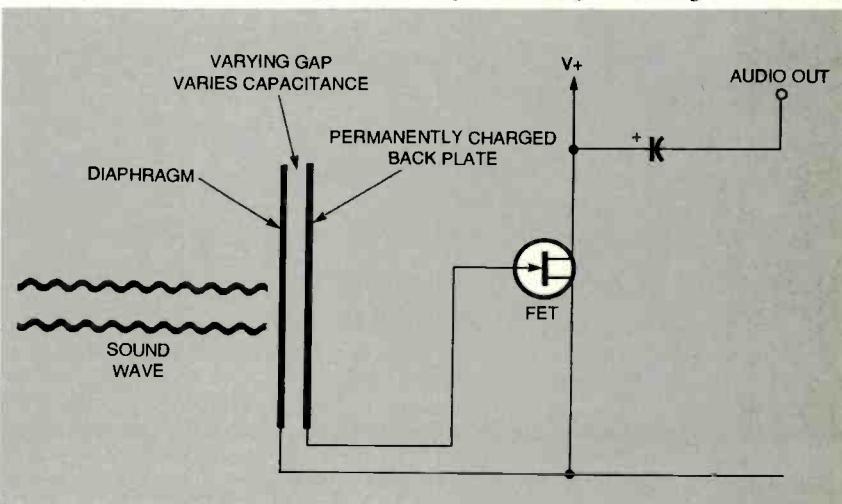


FIG. 5—AN ELECTRET CONDENSER MICROPHONE features a built-in FET amplifier.

VCR

Cross Reference

**NOW Find the right Part
for your VCR**

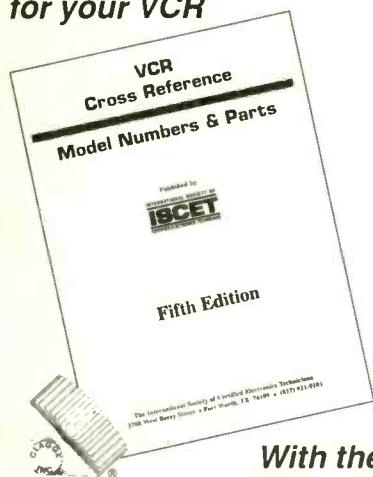

With the

IS CET VCR CROSS REFERENCE

This 119-page reference contains both model and part-number cross-references updated to include 1994 units.

VCR's are made in a few factories from which hundreds of different brand names and model numbers identify cosmetically-changed identical and near-identical manufactured units. Interchangeable parts are very common. An exact replacement part may be available only a few minutes away from you even though the manufacturer supplier is out-of-stock. You may be able to cannibalize scrap units at no cost!

The IS CET VCR Cross Reference is pre-punched for standard loose-leaf binding... \$38.00 plus \$3.00 for shipping for each Reference.

**Claggk Inc.
VCR CROSS REFERENCE OFFER
P.O. Box 4099
Farmingdale, New York 11735-0793**

Name _____

Business _____

Address _____

City _____

State _____ Zip _____

Phone _____

Enclose \$38.00 for the Fifth Edition of the IS CET VCR Cross Reference and \$3.00 for shipping for each Reference.

The total amount of my order is \$ _____

Check enclosed—do not send cash.

or please charge my credit card.

Visa MasterCard Exp. Date _____ / _____

Card No. _____

Signature _____

New York State residents must add applicable local sales tax to total. US funds only. Use US bank check or International Money Order.

CB02

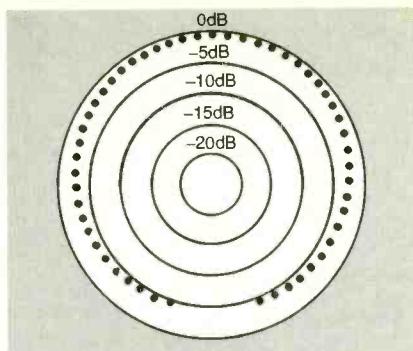


FIG. 6—A MICROPHONE WITH AN OMNI-DIRECTIONAL pattern like this one picks up sounds from all directions.

Every microphone has its own polar pattern. The manufacturer will generally supply it with the microphone, or the information might be in the catalog or other literature. The key to selecting the right microphone is to know which pattern is the correct one to use for a particular application.

The most common type is the omnidirectional. As its name implies, an omnidirectional microphone receives the acoustical waves in a pattern that is equal all around in a circular fashion. Note that the plot in Fig. 6 shows that the pickup in the rear does have some loss, but that loss is small enough to ignore.

The next type of pickup pattern is the cardioid. It has better pick-up from the front of the microphone than from the rear, as shown in Fig. 7. That type of pickup is very popular for live performances. That's because it greatly reduces the chance of acoustical feedback (although it is far from the total answer to that common problem).

The hyper-cardioid/super-cardioid microphone has some features of the cardioid microphone, but the pickup pattern is even more pronounced (see

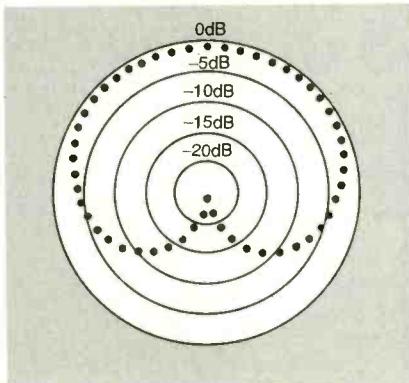


FIG. 7—A CARDIOID PICKUP PATTERN reduces the likelihood of acoustic feedback.

Fig. 8). Though that microphone is useful where feedback is likely to be a real problem, one drawback is that it might have too narrow a pickup pattern for some applications.

The last type of microphone we will discuss is the gun/interference tube. It is used to pick up sounds at a distance. That microphone has some special uses, especially in electronic newsgathering and in film and TV production, to pick up dialogue where a wireless microphone is impossible to use for some technical reason. While we have not shown a polar plot for that type, obviously, they are highly directional.

It is important to remember that

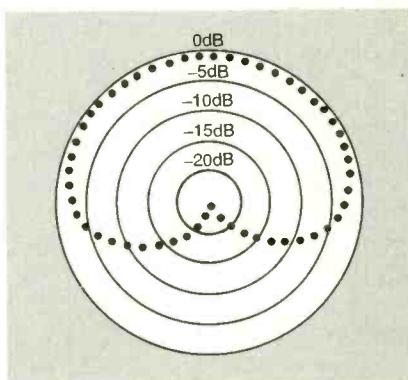


FIG. 8—WHEN FEEDBACK PROBLEMS are severe, try a hyper-cardioid type that delivers the polar pattern shown here.

there is no one microphone that can solve all acoustic problems. You must try different ones in different situations. After some practice, you will have a good understanding of what works for what situation.

EN



IP Addressing and HTML Coding

THREE WERE SEVERAL MISLEADING AND INCORRECT STATEMENTS IN MY COLUMN ON INTERNET RESOURCES (AUGUST 1996). I THINK THAT THE TOPICS ARE IMPORTANT AND INTERESTING ENOUGH THAT WE'LL REVISIT THEM IN

somewhat greater depth for our discussion this month.

The first problem was my statement, "Thus, a textual address like jkh@acm.org eventually gets resolved to a numeric address like 127.0.0.1." Actually, the numeric address is a machine address, not some sort of user alias. As Lou Sortman pointed out, "There is a mapping between IP addresses and domain (host) names, but the user part of an e-mail address is resolved by the Mail Transfer Agent on the referenced host (or Mail eXchanger) and has nothing at all to do with any part of the IP address." Thanks also to Ron Dozier for information in this area.

Lou also clarified some details of where HTTP ends and TCP begins: "In the HTTP protocol, the client issues a request to the server and the server responds with the status, a header (which you described with the HEAD command), and any requested data (if applicable). Your description added two extra parts (client initiates "transfer" and server acknowledges the connection). Those are not part of HTTP. They are part of the transport protocol (TCP on the Internet)."


Regarding CGI (Common Gateway Interface), Lou stated, "CGI programs can be accessed with the GET method as well as the POST method. You specified that only the POST method can be

used. Later, you say that mostly what is transferred with the GET method is simple HTML files. Statistically, that is probably true, but it is also used quite a lot for other file types (sound files, images, etc.) and even CGI programs."

Lou also disagreed with my assessment of CGI: "CGI is not an awkward

hack. It is the most portable way of handling CGI programs on differing operating systems and written in differing languages, including interpreted ones such as Perl and the Bourne shell. There is a place for more efficient schemes for executing code on the server, but there are portability and resource consumption issues that would make CGI a better solution in many cases."

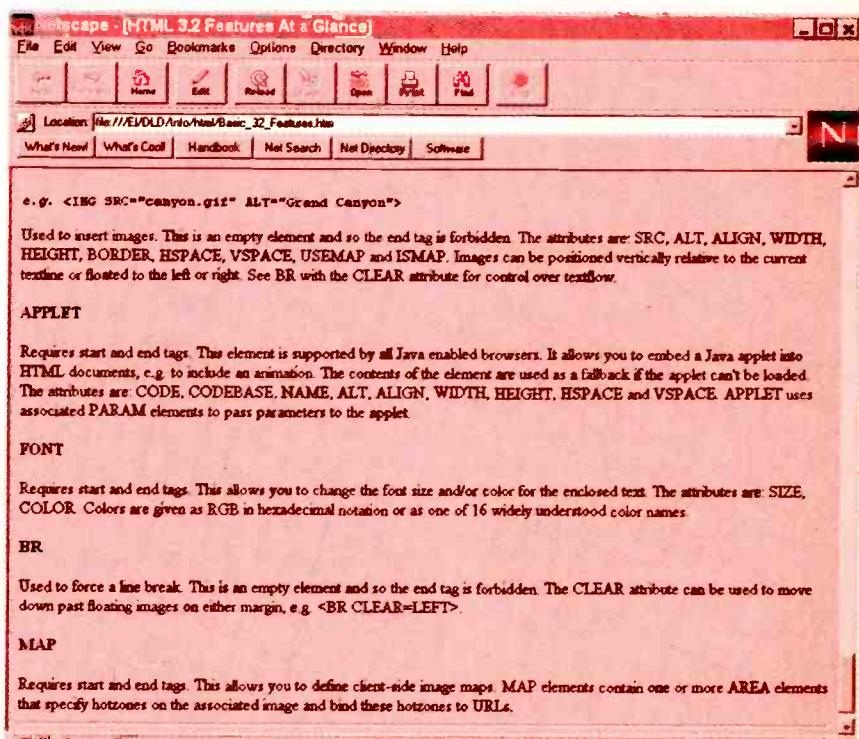I agree that CGI has the virtue of portability. However, it lacks elegance and performance. As the Microsoft steamroller overtakes Internet technology, I think we'll see the company's direct-access Internet Server Application Pro-



THE HTML 3.2 SPECIFICATION adds support for Java Applets, and several new tags for specifying text formatting. HTML 4.0 should be out by the end of the year.

gramming Interface (ISAPI) become much more widely used than CGI. And even if MS were to drop dead tomorrow, other vendors (*e.g.*, Netscape) have comparable solutions.

Lou also disagreed with my assessment of HTML. "HTML was intended to be platform independent. It was quite intentional that there were no font or color tags in the original spec. Leaving the precise manner of interpreting the document content and markup up to the browser was a good thing. The reason that people have problems with documents looking different on different browsers is that they decided that they wanted to do things that HTML was never intended for. HTML is a markup language. It is not a page description language. Ask Don Lancaster (the world's biggest PostScript proponent) about the difference. There may be a need for an open page-description language with hypertext capabilities on the WWW, but the problems that you cite are not shortcomings of HTML."

Here Lou and I have a major disagreement. I'm certainly aware of the distinction between a markup language and a page-description language. The problem is that HTML is rapidly becoming a page-description language.

HTML and SGML

HTML is an application of SGML (Standard Generalized Markup Language, defined by ISO Standard 8879:1986). SGML purposely separates document content from document structure and document formatting. An SGML "document" actually has two components: the document itself, and a Document Type Definition (DTD). The DTD is like a style sheet (in the MS Word sense). In a pure SGML document, the document has no direct formatting. Nothing is ever marked bold or italic; fonts are not specified by name, nor are colors; nor is any type of layout information (*e.g.*, tab stops and line spacing) embedded in the document. The document never has anything but content and tags specifying format and structure. The tags are interpreted according to the DTD associated with the document.

In that way, the DTD can change without changing the underlying document. Thus, the same document can be presented in several different ways sim-

ply by associating the document with different DTDs.

That may seem like an esoteric feature, but it's not. For example, a big problem in creating software documentation is reuse of material. There are printed manuals and on-line, hypertext documents. Often, they share much of the basic content. But it is extremely rare for them to have a strict, two-way, one-for-one correspondence. The on-line stuff invariably needs something that the manual does not, and *vice versa*. Conversely, the manual invariably has stuff that you don't want in the online version, and *vice versa*. Similar types of problems are pervasive throughout every aspect of electronic publishing

LISTING 1—TEMPLATE FOR DELPHI COMMAND-LINE UTILITY

```
program Test;
{$APPTYPE CONSOLE}
begin
  writeln('Howdy, world...')
end.
```

The problem with Web pages that look different on different browsers is that the details of the HTML DTD are interpreted differently by different browsers. Netscape interprets the DTD one way, Microsoft another, and so on. If it were just a question of fonts and colors, the graphics designers might be unhappy, but things would still work. It's when Microsoft and Netscape each goes off and defines new tags to accomplish special feats (*e.g.*, frames, tables, embedded applications, and so on) that both page designers and end users end up suffering.

Some of the latest format-related HTML features (*e.g.*, font tags, color tags, and cascading style sheets) in effect embed the DTD directly within the document, and that is directly contrary to both the letter and the spirit of SGML.

It's also true that some of the very oldest HTML tags do the same things. For example, HTML has tags for directly marking text as boldface, ****, and italic, *<I>*. However, directly marking text in any fashion is counter to the SGML model. There are more general tags that are usually, but not necessarily, rendered as bold and italic: **** and **, respectively. Those are the correct tags to use.

Theory and Practice

Is this a theoretical discussion with no practical application? No. Many Internet citizens still browse with text-only browsers. And as the technology continues to infiltrate other areas (*e.g.*, pagers, cell phones, PDAs), consistent understanding and interpretation of tagging conventions is important. By thinking at a more abstract, general level (*e.g.*, emphasized rather than italic), page designers will better be able to serve a wider audience.

At the bottom of what I dislike about HTML is that it was not designed with a broad set of capabilities and long-term interests in mind. Rather it was a hack thrown together to prove a concept. The creators then lost control, and market evolution took over. Long term, that's probably best. But short term, it makes life difficult for end users, page developers, browser vendors, and new technologies, such as alphanumeric pagers. PostScript, though proprietary, was designed with a full set of capabilities. It has not shown the need to evolve every few months. But that's moot, because HTML is the standard for the Internet. How long will it be before we see HTML-based laser printers?

Delphi Tip

Delphi is a Pascal-based visual development environment for Windows 32 (Win95 and NT). I compared it in some depth with MS Visual Basic in last month's column. Delphi can also be used to create traditional command-line utilities, although Borland has certainly deemphasized that capability, and has hardly documented how to do it.

Listing 1 shows a shell for such an application. The key is line 2, which tells the compiler that this is to be a console app, not a GUI app. To compile the program, use DCC32.EXE, which is located in Delphi's ..\BIN directory. Also, the compiler must be able to find SYSTEM.DCU, which is located in the ..\LIB directory. To do some really retro non-GUI command-line based development, all you need is the compiler, the system unit, and your favorite text editor. It'll all actually fit on a floppy disk with plenty of room to spare!

That's all for now. Until we meet again next time, you can stay in touch via jkh@acm.org.

USING THE 7107

(Continued from page 60)

Hz. While it is not well-suited for frequency counters, it is an excellent choice for automobile tachometers, audio-frequency meters, pulse- and function-generator displays, and other such applications. The 2917 interfaces directly with the 7107, but might require a simple op-amp buffer at the input. If the output is erratic, a 0.1- μ F Mylar capacitor connected in series with the positive input will usually correct the problem.

For frequency counting, the LM555 timer is a better choice, as that chip will handle higher frequencies. Figure 12 is the schematic for a 555 frequency-to-voltage converter that can display up to a maximum of 1.999 MHz. The 100,000-ohm potentiometer (R4) functions as calibration, and S1 selects one of three resistors that determines range.

The display reading is multiplied by 10 for range 1, 100 for range 2, and 1,000 for range 3. A 1999 reading in range 2 would be equivalent to an input frequency of 199,900 Hz. A display of 0865 in range 3 would represent 865,000 Hz.

The range of the counter can be further expanded through the use of input pre-scalers. Those ICs will divide an input frequency, usually by 10, before applying it to the counter. A single pre-scaler would increase the input capability to 19,990,000 Hz, while cascading two pre-scalers would take it up to 199,900,000 Hz. Again, there is the multiplication factor to consider. When using pre-scalers, the displayed value is multiplied first by the range factor, then by the pre-scale factor to get the actual measurements.

The 11C90 and 95H90 ICs are two common pre-scalers, but the drawback with them is their expense. Those chips are not exactly economical, although the 95H90 can sometimes be found on the surplus market for as little as \$6 to \$10.

Other applications. Now that you're an expert on the 7107, the knowledge gained will perhaps prompt you to expand projects, designs, or equipment, and possibly inspire ideas for future projects. LED and LCD displays are highly informative, and can add

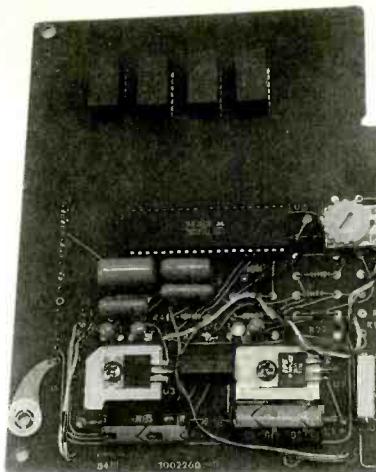


Fig. 13. A section of an alarm board, bought through surplus, that contains a 7107. This particular board also contains the \pm 5-volt power supply.

to the functionality of many types of electronic equipment. A project that takes advantage of the 7107's voltage-measuring capabilities is the author's "Versatile Power Supply" article in the December, 1995 issue of **Electronics Now**. That project is a bench-type power supply with a 7107-driven LED readout that displays the level of the output voltage.

Only a few applications were covered in this article. With a little thought or as practical needs arise, many other ideas will present themselves. For example, the Intersil data book illustrates a circuit for a digital torque meter, using a resistance-dependent strain gauge.

One area to watch for an economical source of devices is the surplus market, as the 7107 and 7106 can be found on many circuit boards. The surplus circuit board in Fig. 13 is an example of that type of source. The chip is usually mounted in a socket, and can be removed for use in one of your own projects. Frequently, the basic meter circuit is intact, and can be used as is with minor modifications. The 7107 can be found in some alarms, satellite receivers, antenna-positioning units, salvaged digital panel meters, counters, controllers, and a variety of other equipment. Be sure and keep an eye out for them when surplus "bargains" are advertised.

So, pick up a couple of 7107s and try adding one to your next project. The chip is quite easy to work with, and the results you could achieve can be very gratifying.

MILLI-OHM ADAPTER


(Continued from page 42)

Run a wire directly from the ground connection of C1 on the board to a lug on the 10-32 stud supporting the swing arm. The common connection including C10, C11, C12, R9, and J1 is the negative Kelvin lead, which is *not* to be connected to ground on the board. Connect the Kelvin lead in this fashion: Run an insulated lead from the common connection of C10, C11, and C12 through a grommet located in the top of the cabinet near the stud, then through an "eyelet" located on the stud itself, and finally make the connection to the lug on BP2.

Mount the completed board on a pair of 1/2-inch spacers in the bottom of the cabinet and connect the remainder of the panel components to the board. Install the ICs in their sockets and close the cabinet. Prepare an output cable using a twisted pair of wires (do not use coaxial cable) with an RCA phono plug on one end, and a suitable plug for your DVM on the other end. A 12-inch length is sufficient.

Calibration. Power up the adapter and allow it to warm up for about five minutes, allowing the temperature to stabilize in the cabinet. Connect the adapter to your DVM, open the cabinet, and connect a clip-lead jumper from the base lead of Q1 to its emitter lead. The resulting voltage, which can now be read on your DVM, is the offset voltage of IC3; make a note of that voltage, which can be anywhere from 0 volt to \pm 10 millivolts. Remove the clip lead. Using your DMM, measure the exact value of R_C (4.02 ohm, 1%), minus your test lead resistance. Connect R_C to BP1 and BP2, push the TEST switch, S1, and adjust CAL potentiometer R4 so that the output from J1 (about 4.02 volts) indicates the exact value of R_C added to IC3's offset voltage. Re-assemble the cabinet and the milli-ohm adapter is complete and ready for use.

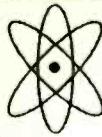In actual use, connect the unknown resistance (R_x) at the exact points on its leads from which you want to measure, take the reading, and subtract IC3's offset voltage for the proper value at 1 ohm/volt. That procedure will ensure the best possible accuracy. Ω



TECH-SYSTEMS

1309 Hwy. 71 Belmar, NJ 07719

908-280-0007 FAX: 908-280-0111

90 Day Warranty / 10 Day Right of Return

N.I.S.T. Traceable Calibration Available on Most Items

SPECTRUM ANALYZERS

TEK 492/01/02 Spectrum Analyzer 50KHz to 21GHz	\$6,995
Option 01 Adds Internal Preselection and 02 Adds Digital Storage	
TEK 492/02 Spectrum Analyzer 50KHz to 21GHz	6,650
Option 21 18GHz to 40GHz Waveguide Mixer Set	1,775
TEK 496 1KHz - 1800 MHz Spectrum Analyzer	4,750
TEK 7L12 100KHz to 1800MHz Spectrum Analyzer Plug-In	1,850
TEK 7L13 1KHz to 1800 MHz Spectrum Analyzer Plug In	2,495
TEK TR503 Tracking Generator w/TM503 Power Supply	1,450
HP 141T/8552B/8555A 10 MHz to 18GHz Spectrum Analyzer	2,195
HP 141T Variable Persistence/Storage Display	595
HP 140T Non-Storage Display	425
HP 8553B 1KHz to 110MHz RF Section	450
HP 8554L 100KHz to 1250MHz RF Section	550
HP 8554B 100KHz to 1250MHz RF Section	795
HP 8555A 10MHz to 18GHz RF Section	995
HP 8556A 20Hz to 300 KHz LF Section	450
HP 8552B IF Section	650
HP 8552A Economy IF Section	295
HP 8443A 0.1 to 110MHz Tracking Generator	550
HP 8444A 0.1 to 1300MHz Tracking Generator	795
HP 8444A/059 0.5 to 1500MHz Tracking Generator	1,350
HP 8445B 1.8 to 18GHz Preselector	650
HP 182T Mainframe	495
HP 182T/8557A 10KHz to 350MHz Spectrum Analyzer	1,495
HP 182T/8558B 100KHz to 1500MHz Spectrum Analyzer	3,350
HP 8557A 10KHz to 350MHz Spectrum Analyzer Plug-In	1,250
HP 8558B 100KHz to 1500MHz Spectrum Analyzer Plug In	2,395
HP 8559A D.01 to 21GHz Spectrum Analyzer Plug In	4,450

OSCILLOSCOPES

TEK 465 100MHz Portable Scope	\$595
TEK 475 200MHz Portable Scope	795
TEK 485 300MHz Portable Scope	995
TEK 2465 300MHz Portable Scope	2,595
HP 1741A 100MHz Portable Scope	495
HP 1725A 275Hz Portable Scope	695
HP 54200A 50MHz/200Ms/s Digitizing Scope	2,250
HP 54200B 50MHz/200Ms/s Digitizing Scope	2,650
HP 542010 300MHz/200Ms/s Digitizing Scope	2,995
HP 541100 1GHz/40Ms/s Digitizing Scope	5,995
HP 541110 500MHz/1Gsa/s Digitizing Scope	6,995
TEK 7603 w/7A1B (X2) & 7B53A Scope	695
TEK 7104 w/7A29 (X2), 7B10 & 7B15 Scope	5,995

Over 600 TEK 7000, 5000 & TM Series Mainframes and Plug-Ins

Call for pricing information

WAVE - DISTORTION - MODULATION

HP 331A Distortion Analyzer 5Hz - 600 kHz	\$195
HP 332A Distortion Analyzer with AM Detector	295
HP 333A Distortion Analyzer with Auto Nulling & High Pass Filter	395
HP 334A Distortion Analyzer with Auto Nulling/High Pass Filter/ AM Detector	495
HP 3581C Selective Level Meter	995
TEK AA501 Distortion Analyzer	1,295
BOONTON B2AD/01/03/04 Modulation Meter	995
Marconi 2305 2.32GHz Modulation Meter w/IEEE	4,995

OVER 3000 ITEMS IN STOCK !

Inventory Changes Daily!

OVER 500 DC & AC POWER SUPPLIES !

Any Voltage - Any Current ! CALL

CALL FOR FREE 40 PAGE CATALOG

COMPONENT TEST

HP 4342A Q Meter [22KHz to 70MHz]	\$2,495
HP 4342A/001 Q Meter [10KHz to 32MHz]	1,650
BOONTON 5110 LCR Meter 100Hz, 120Hz & 1 KHz Test Frequency includes 5110.1 Test Adapter & 5110.4 Kelvin Clip Adapter	1,450
BOONTON 728D Digital Capacitance Meter 1MHz Test Freq, 2pF to 2000pF	750
TEK 576 Curve Tracer	2,995
TEK 577/02 Curve Tracer	1,695
HUNTRON TRACKER 5000 Computer Controlled Troubleshooting System	1,350
SAUNDERS 150C/09 Crystal Test Oscillator Microprocessor Controlled/IEEE / 1 to 60MHz	1,695
GENRAO 163DAV Inductance Measuring System	2,995

800-435-1516

BUY - SELL - TRADE

VISA & MasterCard Accepted

STANDARDS & CALIBRATORS

FLUKE 5100B/03/05 Multifunction Calibrator	\$5,750
FLUKE 3330B DC Calibrator	1,995
FLUKE 515A Portable Calibrator AC/DC/RES	1,695
FLUKE 332B DC Calibrator	595
FLUKE 5205A AC Amplifier	2,650
FLUKE 5450A Resistance Calibrator 1 OHM to 100 megohms/Bppm	1,995
FLUKE 730A DC Transfer Standard	450
FLUKE 750A Reference Divider	450
FLUKE 720A Kelvin Varley Divider	1,895
ESI RV722 DC Divider 1ppm Accuracy	1,295
DATRON 4200/30/80 Autocal AC Standard	2,495
BOONTON 25A Power Meter Calibrator	450
BOONTON 2500A Power Meter Calibrator	450
HP 8477A Power Meter Calibrator	495
HP 116B3A Range Calibrator	775
TEK PG506 Calibration Generator	1,350
TEK TG501 Time Mark Generator	1,350
TEK SG503 Leveled Sine Wave Generator 250KHz to 250MHz	1,350
TEK SG504 Leveled Sine Wave Generator 245MHz to 1050MHz	2,650
RFL 829G Multi-Function Calibrator	1,495

FREQUENCY COUNTERS

HP 5314A 100MHz Universal Counter	\$225
HP 5315B 100MHz Universal Counter	495
HP 5316A 100MHz Universal Counter	695
HP 5328A/011/030 512MHz/IEEE Universal Counter	695
HP 5328A/011/031 1.3GHz/IEEE Universal Counter	895
HP 5340A/011 18GHz/IEEE Microwave Counter	1,950
HP 5342A/011 18GHz/IEEE Microwave Counter	2,750
HP 5300B/5303B 525MHz Counter	450
HP 5257A Transfer Oscillator for HP 5245 Counters	175
HP 5255A 3 to 12.4GHz Frequency Convertor	175
HP 5359A Time Synthesizer	1,895
SYSTRON DONNER 6054B 20Hz to 26.5GHz IEEE Microwave Counter	2,295
TEK DC5009 Programmable 135MHz Universal Counter	695
TEK DC505A 225MHz Universal Counter Plug In	295
TEK DC508 1.3GHz Universal Counter Plug In	450

SIGNAL SOURCES

HP 8640B/003 512MHz Signal Generator w/Reverse Power	\$1,895
HP 8640B/001/002 1024MHz Signal Generator w/ Audio Oscillator	2,795
HP 8656A 100KHz to 990MHz Synthesized Signal Generator	2,995
HP 8660C/86603A/86632B 2600MHz Synthesized Signal Generator	3,995
HP 8660A/86602A/86632B 1300MHz Synthesized Signal Generator	2,350
HP 8620C Sweeper Mainframe	395
HP 86222A D01 to 2.4GHz RF Plug In	1,495
HP 86222B/001 D01 to 2.4GHz RF Plug-In w/Crystal Markers & 70dB ATTN	1,795
HP 86290C 2 to 18.6GHz RF Plug In	2,395
HP 86260A 12.4 to 18GHz RF Plug In	995
HP 8697A 26.5 to 40GHz RF Plug In	1,450
HP 214B Pulse Generator	1,995
HP 8005B 20MHz Dual Pulse Generator	450
HP 8007B 100MHz Pulse Generator	695
HP 8013B 50MHz Dual Pulse Generator	695
HP 3312A 13MHz Function Generator	895
BOONTON 2000 20GHz Sweep Generator	2,450
TEK FG501 2Hz to 2MHz Function Generator	195
TEK FG502 1KHz to 11MHz Function Generator	295
TEK FG503 1 to 3MHz Function Generator	195
TEK PG501 50MHz Pulse Generator	250
TEK PG502 250MHz Pulse Generator	495
TEK PG508 50MHz Pulse Generator	795
APPLIED MICROWAVE/EPSCO PG5KB 5kHz/575 to 925MHz RF Pulser	2,995
VELDONEX 380 5kW High Power Pulser	2,995
COBER 605/P27 2kW/10Hz to 1MHz High Power Pulser	1,350

**We Buy & Sell Service Manuals
Coax/Waveguide Components**

WANTED !

Surplus Electronic Test Equipment

FAX US YOUR LIST

FAX: 908-280-0111

Electronic SHOPPER[®]



TEST EQUIPMENT SALES



MC & VISA
ACCEPTED

P.O. BOX 986
LONDONDERRY, NH 03053

PHONE (800) 684-4651
FAX (603) 425-2945

ASK ABOUT OUR NEW
TEKTRONIX & FLUKE
PRODUCTS

TEK SG504.....1 GHZ SINE WAVE GENERATOR.....\$2795
HP 8111A.....PULSE/FUNCTION GENERATOR.....\$1995
TEK 2465.....300 MHz 4 CH. SCOPE.....\$2850
TEK 2445.....150 MHz 4CH. SCOPE.....\$1850
TEK 2465BDM..400 MHz 4 CH. SCOPE w/DMM.....\$6695
TEK 465.....100 MHz 2 CH. SCOPE.....\$475
HP 1650B.....80 CH. LOGIC ANALYZER.....\$3595
HP 3325A.....SYNTH./FUNC. GENERATOR.....\$1995
TEK 7L5.....SPECTRUM ANALYZER P/I.....\$1495
(INCLUDES L3 MODULE)

DIO 2900.....PROGRAMMING SYSTEM.....\$2195
BMI 2400.....POWER LINE MONITOR.....\$1295
ELGAR 251.....AC POWER SOURCE.....\$750
TEK 2235.....100 MHz 2 CH. SCOPE.....\$995
**NEW TEKTRONIX SCOPES W/ 3 YEAR
MFG. WARRANTY !!**
TEK THS 720...100 MHz 500MS/s HANDHELD
SCOPE & DMM.....\$2195
TEK TDS 340.....100 MHz 500 MS/s SCOPE
W/DIGITAL REAL TIME & FFT\$2695
TEK TDS 420A....200 MHz 4 CH. SCOPE
W/ DRT, FFT & DISK DRIVE.....\$6295
FLUKE 45.....DUAL DISPLAY BENCHTOP
DIGITAL MULTIMETER.....\$679

NEW SCOPES
IN STOCK

Weeder
Technologies

PO Box 421, Batavia, OH 45103

Electronic KITS!
from
\$29 to \$55

FREE
CATALOG!



Pro-KitTM

513-752-0279

weedtech@igloo.com

Home Automation

Connects between a TW523 and an RS-232 serial port. Use your PC or Mac to receive and transmit all X-10 commands. Create your own program to control your home automation system, turning on/off any device plugged into an electrical outlet with response to time/date, other X-10 transmissions or any other computer input stimuli.

Caller ID / RS-232

Connects between a telephone wall jack and an RS-232 serial port. Decodes the caller ID data sent over the phone line and sends it to your PC or Mac, in a pre-formatted ASCII character string. Create your own program to log the name, number, date, and time of all incoming calls.

Telephone Call Restrictor

Connects to telephone wall jack. Disables all phones on the line if attempting to either: dial a number that has been stored in memory 'Block' mode or, dial a number that has not been stored in memory 'Allow' mode. Use touch-tone phone to enter telephone numbers into memory, and choose mode. Program from any phone on the line using your password.

50 MHz Frequency Counter

Reads frequency from 1Hz to 50MHz and displays up to 7 digits on a 1x16 character LCD display. Auto-range feature provides floating decimal point and automatically affixes the correct suffix (Hz, kHz, or MHz). Microcontroller based provides for very small parts count, only 2" x 3" big.

Telephone Scrambler

Scrambles your voice before sending it over the telephone line. Prevent eavesdropping from an extension or tap. Connects between your telephone and wall jack. No modifications are required to your telephone. Full duplex operation.

IR Remote Control Receiver

Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. Seven individual I/O pins can be assigned to any button on your remote, and can be configured for either 'toggle' or 'momentary' action.

Caller Block

Connects between your telephone and its wall jack. Prevents your telephone from ringing unless the calling party is one which you've entered into memory using your touch-tone phone. Can also be set to allow all callers 'except' those which you've entered into memory.

DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Connects to your telephone wall jack. Decodes all 16 touch-tones and displays them on an LCD display. Holds the last 240 digits in a non-volatile memory. Scroll through and view all telephone numbers dialed, credit card numbers entered, etc.

BLOWOUT! TIMELINE INC. BLOWOUT!

Over 10 years and 27,000 customers and still growing

LIQUID CRYSTAL DISPLAYS

240x64 dot LCDs with built-in controller.
AND 4021ST-EO. Unit is EL back-lit. \$79.00 or 2 for \$149.00
OPTREX. DMF5005 \$69.00 or 2 for \$129.00

160 x 128 dot LCD with built-in controller (T6963C)

20 character x 16 line \$79.00 or 2 for \$149.00

Mfr.: Toshiba TLX-1013-EO. Unit is EL back-lit. Dim: 5/8" L x 4 1/8" H.
The built-in controller allows you to do text and graphics.

Alphanumeric—parallel interface

16x1	3 for \$25.00	20x2	\$12.00	40x1	\$8.00
16x1 (ig. char)....	\$12.00	20x4	\$25.00	40x2	2 for \$25.00
16x2	\$8.00	20x4 (ig. char)....	\$25.00	40x4	\$25.00
16x2 (ig. char)....	\$12.00	24x2	\$12.00	4x2	\$5.00
16x4	\$15.00	32x4	\$10.00		

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" Interface • 98 ASCII character generator • Certain models are backlit, call for more info.

Graphics and alphanumeric—serial interface

size	Mfr.	price	size	Mfr.	price
640x480 (backlit)	Epson	\$35.00	480x128	Hitachi	\$15.00
640x400 (backlit)	Panasonic	\$25.00	256x128	Epson	\$20.00
640x200	Toshiba	\$15.00	240x128 (backlit)	Optrex	\$20.00
480x128 (backlit)	ALPS	\$15.00	240x64	Epson	\$20.00
			160x128	Optrex	\$15.00

LASER PRODUCTS

HeNe Laser Head (10mW max. output) TEMOO. 15.5" long MFG: NEC \$99.00
Laser Power Supply (for HeNe tube) \$89.00

LASER SCANNER ASSEMBLY \$29.00

Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

LASER DIODE (5mW) with collimator \$20.00

VISIBLE LASER DIODE: 5mw at 670nm \$15.00

Index guided. Threshold current 40 ma typical.

POLYGON MOTOR UNIT & DRIVER \$79.00

Ten-sided first surface mirror mounted on an armature that spins at 125 revolutions per second yielding a beam sweep rate of 1250 sweeps per second. The driver for the polygon unit requires 24 volts and plus minus 12 volts to operate. There is also an f-theta lens in front of the polygon scanning mechanism with a three inch diameter. Great for optical experiments, etc. Very high quality units. (MFR: JAPAN ELECTRONICS)

NETWORK

Proteon ProNet-4 Model p1347 Token Ring Board \$49.00

16 bit • 4 Mbps • IEEE 802.2 and 802.5 compatible • twisted pair • interoperable with IBM Token Ring network

POS & BAR CODE

MAGNETIC CARD READER \$25.00

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypad with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

HP bar code wand (HBCS 2300).....\$25.00

POWER SUPPLIES

SWITCHING POWER SUPPLY \$12.00 or 2 for \$20.00 115/230 Volts

73 WATT (2) 4 pin power connectors attached • Dim: 8.5" L x 4.5" W x 2" H

Output +5V @ 2-9.75A, A+12V @ 0.1-5A, -5V @ 0.4-0.6A, -12V @ 0-0.5A

68 WATT Dim: 5.5" L x 3.2" W x 1.7" H • Output: 5V @ 4 A, 12V @ 4A

60 WATT Dim: 8 1/4" x 4 1/4" x 3" • Output: 5V @ 6A + 12V @ 1A - 5V @ 1A - 12V @ 1A

CHARGE COUPLED DEVICES

"The Spy In The Sky" \$29.00

Sony CCD Imager - designed for black and white composite video cameras. Picture elements: 384 (H) x 491 (V)
Chip size 10.7 (H) x 9.3 (V) mm² • Unit cell size 23.0 (H) x 13.4 (V) µm². Ceramic 24 pin DIP package • Mfr: Sony, Part# 016AL

4096 element CCD \$19.00

1024 element CCD \$15.00

2048 element CCD \$15.00 • 1728 element CCD \$15.00

LINEAR TYPE

23605 Telo Ave., Torrance, CA 90505

Order desk only: USA: (800) 872-8878 CA: (800) 223-9977
L.A. & Technical Info: (310) 784-5488 Fax: (310) 784-7590

OEM INQUIRIES WELCOME

MONITORS

Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15Khz • Ability to do 40 and 80 column.

5 inch Amber \$29.00 • 7 inch Amber \$39.00

9 inch Amber or Green \$29.95

5" COLOR MONITOR \$49.00

• Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible

• 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.

• Open Frame Construction • Standard Interface Connector • Degassing Coil included • Mfr: Samtron

2 for \$89.00

MISCELLANEOUS

ADAPTEC 4070A (RLL) OR 4000A (MFM), SCSI Controller, your choice \$25.00

IBM 370 option XT and AT emulation boards \$35.00

HACKER CORNER

POINT OF SALE BANK TERMINAL \$49.00 or 2 for \$89.00

• LCD Display 20 Char. x 4 Line • Printer 16 Column Dot Matrix • Epson • 24 Key Domed Membrane Keypad • Intel 80C32 Processor • 2 PCMCIA Sockets (ICC Slots) • Dallas DS1287 Realtime Clock • 2 Solid State Buzzers (Piezo Electric) • 4 Crystals • Rockwell Modem Chip • Telephone Line Interface (4 Pin "RJ" Connector) • RS-232 Interface (8 Pin "RJ" Connector) • NI-CAD Battery Pack Inside Note: We have not been able to bypass an access code in the software. Thus while time of day and other introductory things are displayed on LCD, the full original capabilities of this unit cannot be guaranteed. Also, we do not have a source for the smart cards that were to go in the PCM CIA sockets. Requires 12 volt adapter for power. (Not included) Dimensions: 9-1/2" L x 6-1/4" W x 2-1/2" D • Original cost over \$450.00

CAMERA BLOCK \$149.00

FOR ROBOTICS AND EVERYTHING ELSE

Unit is for Hi Band 8mm CamCorders, includes 8x zoom lenses, D/D converters, built-in CCD 2/3 in, 420 thousand picture elements, complementary mosaic filters. Excellent performance. High resolution, high sensitivity, low lag, low smear, good color reproduction, no distortion, 1/60-1/1000sec variable speed digital shutters, TTL auto focus, auto white balance, one-push auto white balance, auto/manual iris and gain up switch. Can be controlled by a 4bit micro computer. Remote controlling is possible for zoom and focusing. NOTE: These are PAL (European Standard) Units. SONY PART #EVI-101 (PAL)

CELL SITE TRANSCEIVER \$79.00 2 for \$149.00

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 HMZ below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

Encased Black & White Composite CCD Camera with Adapter

IR viewing to 1000 nm 7 1/2 L x 2 1/2 W x 1 1/2 H

\$89.00

Comes complete with CCD camera, mounting nut on bottom of casing,

12VDC power supply. Excellent low light capability, standard RCA NTSC video out.

2 for \$159.00

Great for: entryway security/remote monitoring, video conferencing/desktop video conferencing

This miniature camera is perfect for multimedia computer applications as well as security and surveillance. NTSC output allows us with all popular video digitizing boards for Apple Macintosh and Microsoft video for Windows. Connects directly to any composite monitor or VCR with "video" input. Its razor-sharp wide-angle lens focuses from two inches to infinity and its state-of-the-art CCD technology accurately captures 16 level grayscale images for QuickTime movies and still pictures. Records at 30 frames per second and 260 lines resolution with excellent low light capability. Uses 12VDC (adapter supplied) and standard RCA cable. Service manual, schematics and circuit descriptions included.

Portable Micro Terminal \$99.00 2 for \$149.00

Flip up LCD display (9-16 VDC) • Can communicate with a computer having RS 232 port • Can communicate with another Microterm • Has a built-in floppy disk drive • Has a built-in microphone, data RAM (32K) and Video RAM (64K) • Has a built-in keyboard and set up capabilities • Original intention for POS applications • display size 40x16 (256 x 128 pixels) • Dimensions: 6.3" W, 11" L, 2" H. (With LCD up height is 7.1")



BAREBONES 286-12 COMPUTER \$49.00 (2 FOR \$79.00)

Slimline desktop case, 100 watt supply, math co-processor support. On board IDE, & Floppy controllers. 2 COM ports and 1 parallel port with software setup. Supports up to 8 Megs using standard 30 PIN SIMMs. Internal room for (1) 3 1/2" 1.2" inch IDE hard drive and (2) 3 1/2" 1/2" inch floppies. Four 16 BIT ISA slots, accepts full length AT size cards. Keyboard can be set to no test at boot. Case size is 15.5" W x 16" D x 4" H. (Motherboard can be purchased separately: \$29.00 or 2 for \$49.00)

.6" COMPOSITE MINIATURE COLOR DISPLAY \$149.00

Fully encased. Dim: 1.3" x 1.3" x 4". 12 Volts DC power, NTSC signal. 250 H x 300 V resolution. Focus adjustable eyepiece. Applications include camcorder viewfinder, helmet mounted display, etc. Original cost over \$600.00

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

**FREE CATALOG
CALL TOLL FREE
1-800-338-0531**

E-Mail: xpress@parts-express.com



Parts Express™

**30 DAY MONEY
BACK GUARANTEE!**

340 E. First St., Dayton, OH 45402-1257
Phone: 513-222-0173 • Fax: 513-222-4644

Amplified Indoor FM Antenna

17" tall, amplified FM antenna. Improves reception with weak FM signals. 18 dB of gain. Includes AC adaptor, gain control, and 75 ohm coaxial cable terminated with an "F" connector.



**HOT
NEW
ITEM!**

#EN-219-055 \$12⁹⁰

Cable TV Stereo Decoder


When used in conjunction with a cable TV converter or cable ready VCR, this handy device allows you to feed the cable TV stereo signal into your home sound system for superb audio reproduction of your favorite shows, movies, and sporting events.


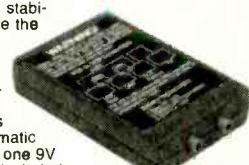
#EN-189-110 \$19⁹⁰

Digital Video Stabilizer


The digital video stabilizer will eliminate the constant picture distortion caused by the copyright protection on movie videotapes. This unit is fully automatic and operates on one 9V battery which is included.



\$17⁹⁵

Decoy Cameras

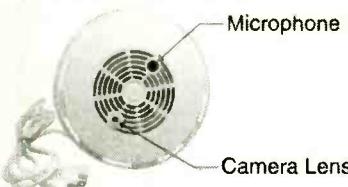These 1/3" CCD cameras offer a clever means of disguise. Both feature a 3.6mm wide angle lens, built-in electronic shutter, and a 12 VDC power supply. Minimum illumination: 0.3 lux. 400 line resolution. Smoke detector decoy camera includes an audio output.



Part #	Description	Price
EN-335-535	Smoke detector decoy	\$249.50
EN-335-540	Decoy clock camera	299.95

**AFFORDABLE
HIGH TECH
SURVEILLANCE!**



Portasol/Weller Butane Soldering Tool

**NO CORDS,
NO BATTERIES!**



This cordless, refillable, butane powered soldering tool is ideal for any on-site soldering job. Provides up to 35 watts with a temperature range up to 700 degrees F. Includes flint ignitor in plastic case, safety cut off switch, and C-2 chisel tip.

#EN-372-150 \$25⁹⁵

5" Sealed Back Midrange

5" heavy duty sealed back midrange with deluxe mesh grill. 1" aluminum voice coil. Popular midrange for auto sound installations. ♦Power handling: 35 watts RMS/50 watts max ♦Voice coil diameter: 1 inch ♦Impedance: 8 ohms ♦Frequency response: 800-10,000 Hz.

#EN-280-030 \$7⁵⁰



150 MHz Oscilloscope Probe Kit

Deluxe probe kit features a modular design for longer life, switchable 10:1 probe with 150 MHz bandwidth, 2.8 ns rise time, and adjustable capacitance from 10-35 pF. 60" in length.

#EN-390-100 \$29⁹⁵



**GREAT
VALUE!** \$29⁹⁵

1" Titanium Dome Tweeter

Features a ferro fluid cooled Kapton voice coil and a rubber surround. Very natural sounding high frequency reproduction with extended response to 30KHz.

♦Power handling: 50 watts RMS/75 watts max ♦Voice coil diameter: 1" ♦Impedance: 8 ohms ♦Frequency response: 2500-30,000 Hz.

#EN-275-050 \$16⁵⁰

**RESPONSE
TO 30KHz!**




\$16⁵⁰

3 Channel Color Organ Kit

This sound to light unit features three separate outputs, which can be controlled independently. Each output reacts to three different bands of the musical spectrum: bass, midrange, and treble. Has built-in microphone, so no connection is required to music source, but a line input is provided.

#EN-320-210

velleman-kit HIGH-Q

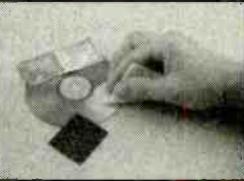

\$1⁹⁵

**SUPER
QUALITY
KIT!**



\$59⁹⁵

6-1/2" Woofer

Polymer resin treated paper cone with poly foam surround. Long throw voice coil design helps to deliver powerful bass output. Perfect for bookshelf type speakers. Mtg. #C16L020-51F. ♦Power handling: 60 watts RMS/120 watts max. ♦Voice coil diameter: 1-1/4 inches ♦Impedance: 8 ohms ♦Frequency response: 57-7000 Hz.

#EN-290-023

PIONEER



\$19⁹⁵



♦30 day money back guarantee ♦\$20.00 minimum order ♦We accept Mastercard, Visa, Discover, and company C.O.D. orders ♦24 hour shipping ♦Shipping charge = UPS chart rate + \$1.90 (\$5.00 minimum charge) ♦Hours 8:00 am - 8:00 pm ET, Monday - Friday ♦9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ♦Foreign destination customers please send \$5.00 U.S. funds for catalog. ♦Quantity pricing available.

CIRCLE 262 ON FREE INFORMATION CARD

1-800-338-0531


DIGITAL STORAGE OSCILLOSCOPE

WITH

SPECTRUM
ANALYZER,
DVM, FREQ.
COUNTER,
AND DATA
LOGGER.

from
\$189.

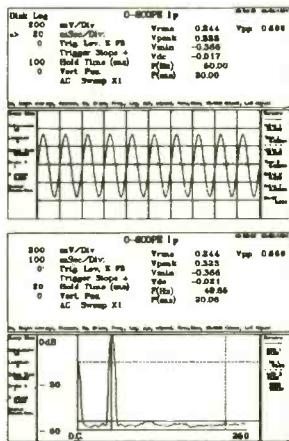O-SCOPE
MODULES
CONVERT PC'S
INTO
MULTIPURPOSE
TEST AND
MEASURING
INSTRUMENTS.



No room on the bench? Too much to carry? Why lug a scope around? Just toss an O-SCOPE into laptop case or tool kit. When you need a Digital Storage Scope, Spectrum Analyzer, Data Logger, or DVM, plug the O-SCOPE into a PC printer port and see it all on the monitor. Continuous, delayed, or triggered sweeps can be frozen on the screen, printed out, or saved to disk. Frequency spectrums DC to 500KHz.

Both single and dual channel models accept standard scope probes and works on 286 or faster desktop and laptops.

FEATURES:

- SMALL & PORTABLE
- USES PRINTER PORT
- USES STD. PROBES
- DC TO 500 KHz (Oscope II)
- 10v/div. TO 50 mv/div.
- X-Y DISPLAY (Oscope II)

MADE IN U.S.A.

INCLUDES CABLE, SOFTWARE & MANUALS

O-SCOPE I (DC-50KHz, single trace) \$189.
O-SCOPE II (DC-500KHz, dual trace) \$349.
SHIPPING: \$7.50 (2ND DAY \$11.50)

SAME DAY SHIPPING

O-SCOPE I (DC-50KHz, single trace) \$189.
O-SCOPE II (DC-500KHz, dual trace) \$349.
SHIPPING: \$7.50 (2ND DAY \$11.50)

SEND CREDIT CARD INFO., M.O., or CHECK, OR CALL

1-800-980-9806

Allison Technology Corporation

8343 CARVEL, HOUSTON, TX. 77036 U.S.A.

PHONE: 713-777-0401 FAX: 713-777-4746 BBS: 713-777-4753

<http://www.atcweb.com>

TOP SECRET

CONSUMERTRONICS
2011 Crescent Dr., P.O. Drawer 837
Alamogordo, NM 88310

Please order by Mail or Fax only ---
Fax: (505)434-0234, 439-1776 (orders only; if you get voice, enter #11#11 any time), 24-hr
Customer Service & Tech Support: (505)439-8551 (8AM-6PM MST, Mon-Sat)

Relates directly to your order or prospective order.

Web Site: Visit our popular site (tell your friends) at <http://users.aol.com/wlzguru/hl-tech.html>

10% Off on orders \$100+ 15% Off over \$200+

Add \$5 total SH (U.S. Canada). All items in stock. Postal M.O. is fastest. VISA, MC OK. COD (\$49-\$99), add \$8. New Catalog (200+ offers) \$2 w/ order, \$5 w/o (no CC), \$24 foreign.

Since 1971. As seen on CBS "60 Minutes," Forbes, etc. By John Williams - former Lockheed Senior Engineer, NMSU CS Professor, DOD Electronic Weapons Engineer, NIH Health Physicist. Sold for educational purposes only.

Wanted: 5 MAC IIs, PC486 (or better), peripherals, new surplus electronic parts, test equipment - buy, trade,

*All software supports all IBM-PC systems

Off-the-Shelf HARDWARE

Van Eck Systems ★ Data Card Reader/Writers ★ ATM3 ★ Security Surveillance ★ RFEM ★ Wave Radar ★ Ultrasonic/Light Sound Detectors/Receivers ★ Xmitters/Jammers/Blasters ★ Neuronics/RIF/E-Hieronymus/Resonant Crystal Radionics ★ EM Lab Weaponry/Countermeasures ★ ESS Infinity Devices ★ Voice Disguisers/Lineman's Hand-Sets ★ Buy Tap Detector/Blaster ★ Phone Color Boxes ★ DTMF Decoders ★ CarJack/Kidnap Blaster ★ Bumper Beeper Child Finder ★ Panic Button ★ Shrike Module ★ TENS ★ Subliminal Mixer/Amp (Ultrasound & Infrasound) ★ Electronic Dowsers ★ Hidden Presence Detectors ★ Hearing Assistor ★ Vortex Generator ★ 5th Sense Communicator ★ Noise Cancel System ★ Levitator - many more! See our New Catalog!

SPECIAL PROJECTS

We design/build/obtain/repair/modify/mainain/consult on any device/system/process/project - electronic/computer/mechanical/optical (ex: phone/auto/security/radio/cable/baby/energy/HV/FM/IR/ultrasonic/UV/commo/consumer) for business/personal/invention needs. Describe & include \$30 pre-engineering fee (no obligation). Time & cost estimates 7-10 days. Confidentiality guaranteed.

CELLPHONE MODS

See our Catalog for our infamous cellphone modification guide (\$69) - detailed, comprehensive, covers all makes - 10 times more info than competitor's "guide". (Do Special Projects above to get up-to-date hardware/software). **Free Data Search:** As a special FREE service to our C&P customers, we will perform one FREE search of our massive cellphone database! If requested within 30 days of your purchase of C&P Data now on cellphones is so great, we can fit in C&P only that in greatest demand. Search result not guaranteed. Request by mail (don't fax), include a #10 SASE.

PAGER (Beeper) MANUAL

Describes in detail how Pagers work, different types and uses, frequencies, advantages over and uses with cellphones, and tips and tricks. And how Pagers are hacked and countermeasures. Includes the plans for your own **Personal Pocket Paging System** (transmitter and receiver). \$49.

HACKING FAX MACHINES

Describes in detail how Fax machines are hacked and countermeasures (hacking Faxes is much more complex than just connecting a third Fax to the phone line). Includes Fax protocols, commo parameters, and 2:1 and 4:1 compression. And insights into designing Fax Interception devices and modifying existing Faxes into Stealth Faxes on the job. \$49.

VOICE MAIL HACKING

How Voice Mail Box (VMB) systems are used and the specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BIX, GENESIS, EZ, SYDNEY, PHONE MAIL, AUDIX, CINDY, CENTAGRAM, SPERRY LINK, RSVP, etc. Absolutely required for all users, sysops and security personnel! \$29.

PBX HACKING

1,000s of PBXs are hacked to the tune of a Billions/Yr. While "VOICE MAIL HACKING" details how VMSS are hacked for "phun" and profit - Including VMSS methods for hacking PBXs themselves - "PBX HACKING" addresses ALL issues relating to PBX hacking, including countermeasures! Can your business or agency afford a \$90,000 phone fraud loss (the average loss due to hacked PBXs)? As described in Farber Magazine, \$29.

PHREAKING CALLER ID & ANI

Details on how they work and dozens of effective ways of defeating Caller ID, ANI, #89, #57, and Call Blocking and #67. Also describes Caller ID, Orange, Beige, Cheese and CF Boxes, ESS, SS7, E-911, various CLASS services, CNA, NDN PUB DA, CAMA, DNR, 800-ECR, Divert, Extenders, Centrafix - more. \$29.

COMPUTER PHREAKING

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS, etc are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system (Ed, Cholice, PC Magazine), BBS advice, password defeats, glossary - much more! Manual + Disk! \$29.

Beyond PHONE COLOR BOXES

Dozens phone color boxes described - many circuits, Plus Call Forwarding, Conferencing, Phreak History, Glossary, Dialers, Extenders, Loops, REMOTS, Bridging Heads & Cans, Optocom, 3rd Party and many other non-box methods - more! \$39.

HACKING ANSWERING MACHINES

How answering machines are hacked - listen to - even erase - messages, and to convert them into mini-VMBs. And countermeasures - protect yourself from snoops, stalkers, burglars and pranksters! \$29.

CREDIT CARD SCAMS

Cardholders, merchants, banks suffer \$ Billions in losses annually because of credit card fraud. Describes every known means of credit card fraud and scams. Protect yourself! \$29.

AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed. Include: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping/splicing, Inside Job, super-cool, vibration, pulse, high voltage - others. Case histories, law, countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to \$250,000 in cash! Rec. \$350,000 ATM crime spree still unsolved! \$39.

CONS., SCAMS & SWINDLES

Cons & scams and related swindles fleece Americans of \$100+ Billion per year! The most comprehensive survival manual on cons & scams of all kinds - from the classic to hi-tech. Details 100s and many variations. And countermeasures. Protect yourself! \$39.

INTERNET CONS & SCAMS

Internet cons, scams and related frauds now rake in \$2+ Billion annually! Most are done anonymously and with little fear of prosecution (difficult to prove and to find the perpetrators). Described in detail, includes countermeasures. \$29.

Beyond VAN ECK PHREAKING

Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the Consumertronics and the original Top Secret Van Eck designs! \$29.

The HACKER FILES

Compilation of 100s of the best articles written (in ASCII) by top hackers & phreakers. Covers every major topic in hackerdom! 3 HD Disks! \$59.

STOPPING POWER METERS

As reported on CBS "60 Minutes": How certain devices can slow down - even stop - wattmeters - while loads draw full power! Device simply plugs into one outlet and normal loads into other outlets. Also describes meter creep, overload drop, etc. Plans \$29.

L.O. MANUAL

External magnetic ways (applied to the meter itself) to slow down and stop wattmeters while drawing full loads. Plans. \$25. **KW-HR METERS:** How wattmeters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polypath Meters. Experimental results to slow and stop meters by others! \$25. Any 2, \$47. All 3, \$89.

UNDER ATTACK!

Electromagnetic Interference and Electronic Weapon Attacks cause: Cancer, birth defects, and profound psychological, neurological, cardiovascular and immune system disorders. Destructive to people, animals, plants, equipment! Includes **ACTUAL CASES OF EM ATTACKS** (we investigated!) Includes how to verify and pinpoint EMI and electronic attack sources, and effective countermeasures. \$29. **EM BRAINBLASTER:** Tutorial and plans for powerful ELECTROMAGNETIC WEAPONS and LAB DEVICES. Optimum circuits, freqs, waveforms, duty cycles, intensities. Thorough. \$29. Both \$49.

MIND CONTROL

Concern and fear increases over EM and ultrasonic mind (body) control technologies - especially implants! Unfortunately, there is much more misinformation and disinformation published than facts. Some victims are controlled and exploited by arm-chair "experts" and so-called victims' assistance groups - one even demands the **policing** of the Internet to prevent and remove postings! It doesn't approve of \$39. Visit our site at: <http://users.aol.com/wlzguru/mindcontrol.html>

RADIONICS MANUAL

Exciting electrical, electronic, electromagnetic therapeutic, diagnostic & preventive devices (mostly experimental). History, descriptions, plans (dozens), availability of RADIONICS Devices from early to modern. While drugs cost \$100s, electricity costs pennies! \$29. **HEALTHYSELFS:** Plans for 3 major electronic therapeutic devices of types approved by FDA. \$19. Both \$39.

HIGH VOLTAGE DEVICES

44 devices plans: Stun Gun, Laser, Prod, Cane, Blaster, Flasher, Zapper, Audio-RF-Radar Jammer, Fence Charger, Plasma & Van de Graaff Gens., Jacob's Ladder, Geiger Counter, Ozone Gen., Fish Stunner, Plant Stim., Kirlian, more! All plans for only \$29.

STEALTH TECHNOLOGY

Police radar is fascinating! It also has error rates of 10-20%. Every known error mode - stealth method and material used to minimize radar reflections - tactic and strategy to fight unjust radar tickets (that cost you \$100s in insurance and risk cancellation) - methods to detect and jam signals - fully described! \$29.

SECRET & SURVIVAL RADIO

Optimum survival and security radio equipment, methods, freq allocations and voice/data scrambling/encoding. Includes small receivers/transmitters, telemetry, antenna optimizations, remote monitoring and control, security, surveillance, and ultrasonic, fiber-optic and infrared commo. 70+ circuit plans, tables, \$29.

CRYPTANALYSIS TECHNIQUES

Five powerful menu-driven crypto programs (in COM and BAS source code) to analyze, decrypt "secure" ciphertexts. Worked-out examples. Recommended by prestigious "Computers & Security" Manual + Disk! \$29.

WHITE-STAR ELECTRONICS

TEL: 405-631-5153 FAX: 405-631-4788

CONVERTERS:	20	50	100+
Regal CR-83	45	39	35
* New, Panasonic TZPC 145	75	69	65
DQN-5 (2 or 3) (unmodified)	45	39	35
DRZ-3 PJ (unmodified) 70 Channel Plain	35	32	29
DRX-3 PJ (unmodified) 60 Channel Plain	32	30	27

Call for FREE catalog.

405-631-5153




REMOTE CONTROL

HAND UNITS:	20	50	100+
Jerrold Replaces: 400/450/550	4.95	4.50	4.25
Scientific Atlanta: 075/175/475	4.95	4.50	4.25
8600: On screen display	7.50	7.00	6.50
Pioneer: BR 81, 82	4.95	4.50	4.25
Panasonic: Call for model #	7.50	7.00	6.50
Zenith: All	4.95	4.50	4.25
Tocom: 5503-VIP, 5503-A	7.00	6.50	6.25
Universal: 4 in 1 R/M	7.50	7.00	6.50

Call for Oak, Hamlin, Regal-83, Regency, Texscan, and all others.

Tamper-Bit tools: (10-lot)

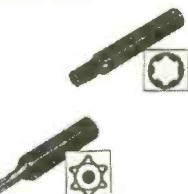Jerrold compatible bits:
1/4" Stacom Bit
\$8.00
Oval Round D
\$20.00
Torx Bit:
Tocom T-8
\$8.00
Zenith T-10,T-15
\$8.00
Pioneer T-20
\$8.00
Scientific Atlanta T-20
\$8.00
Pio 63XX Oval
\$20.00
Bit Driver Handle
\$4.00



We carry most remote hand units. If you don't find the one you're looking for, we can locate for you.

Specializing in large quantities.

HOURS: Monday thru Friday 9 am to 5 pm Central Time.

Call for FREE catalog.

CIRCLE 314 ON FREE INFORMATION CARD

RF POWER TRANSISTORS AND TUBES


In depth stocking of popular and hard-to-find Electronics Parts for Transmitters & Linear Amplifiers

Popular Transistors

2SC1969
2SC2166 • 2SC2290
2SC2312C • 2SC2879
MRF454 • MRF455
MRF455A • MRF477
MRF492 • MRF497
SRF3749 • SRF7000-90

Popular Tubes

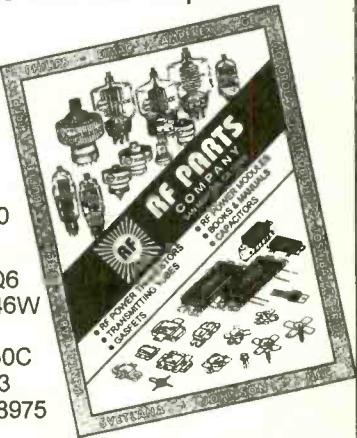6KD6 • 6JS6C • 6LQ6
M2057 • 6146B • 6146W
3-500Z • 3-500ZG
811A • 572B • SV6550C
7558 • 8417 • 8873
8874 • 8875 • 8877 • 8975



Order your FREE copy of our new Catalog by writing or calling us now.

(619) 744-0700 • (800) 737-2787

Fax: (619) 744-1943



RF PARTS

435 SOUTH PACIFIC STREET
SAN MARCOS, CA 92069

REMOTE CONTROL A/B SWITCH



\$ 29⁹⁵

A/B/C SWITCH **\$39⁹⁵**

Plus Shipping - Money Back Guarantee
DEALER PRICING ON REQUEST

CONTROLLED BY ANY REMOTE!

Now you can switch between two TV signal sources without getting up or even reaching for a different remote control! Simply press any button on any remote control and hold it down for two seconds. QuikSwitch contains a patented sensor that causes it to switch sources each time it receives an uninterrupted infrared signal for two seconds. And you won't need a spare AC outlet, because QuikSwitch operates a full year on 2 "AA" alkalines, 3 years on lithiums!

HIGH ISOLATION

100% SOLID STATE

MADE IN U.S.A.



MILESTONE PRODUCTS


5698 WESTBOURNE AVE - COLUMBUS, OH 43213

I-800-535-7827

Licensed Under U.S. Patents 4,935,733 and 5,047,765 Other Patents Pending



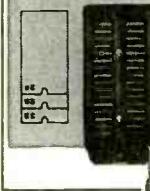EZ-EP
M'L ELECTRONICS
Los Angeles, California (310) 637-7618



EZ-EP DEVICE PROGRAMMER - \$169.95

- Fast** - Programs 27C010 in 23 seconds.
- Portable** - Connects to PC Parallel Port.
- Versatile** - Programs 2716-080 plus EE and Flash (28F,29C) to 32 pins.
- Inexpensive** - Best for less than \$200
- Correct implementation of manufacturer algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web page.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters.

Adapters Available

EP-51 (8751,C51)	\$39.95
EP-11 (68HC11 E/A)	\$59.95
EP-PIC (16C5x,61,62x,71,84)	\$49.95
EP-PIC64 (16C62,63,64,65,73,74)	\$39.95
EP-P-EEL (I2T 22V10, 20G10, 18V8)	\$59.95
EP-SEE (93x,24x,85)	\$34.95
EP-16 (16bit 40 Pin EPROMs)	\$49.95
EP-49 (8742,48,49)	\$49.95
EP-750 (87C750,751,752)	\$59.95
EP-ZB (Z86E03,04,05,06,07)	\$39.95
EP-55 (8755)	\$39.95
EP-PLCC (8751,C51)	\$59.95
EP-PIC-SOIC(16C5x,61,62x,71,84)	\$59.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-LCC (LCC EPROMs)	\$49.95

M'L Electronics
3526 Jasmine #4, Los Angeles, CA 90034
310/637-7818 Fax/BBS: 310/841-6050
<http://www.cs.ucla.edu/csd-grads/gs3/loving/www/m2l.html>
CA orders add 8.25% sales tax. Ground shipping - \$5. 3 Day - \$7.
2 Day \$10. Overnight \$17. COD \$4.75.

BEST DEALER PRICING!

CABLE DIRECT
CONVERTERS • FILTERS
DESCRAMBLERS

IMPROVE YOUR IMAGE WITH
VIDEO STABILIZERS

100%
GUARANTEE!



30 DAY
FREE
TRIAL!

FREE Cable TV Catalog.



Now you can tune-in your favorite
cable TV programming and
SAVE \$100'S - EVEN \$1000'S
on premium CABLE TV EQUIPMENT.

**MODERN
ELECTRONICS**

1-800-906-6664

2125 S. 156TH CIRCLE • OMAHA, NE 68130




Unusual,
detailed how-to books, manuals, references,
old & new, for experimenters, builders, and
mad scientists on high voltage, Tesla, crystal
sets, very early radio and television, vacuum
tube gear, plastics, chemistry, lasers, more!
Repair cameras! Make neon signs! Make
whiskey! Hydrogen fuel! A solar cell! A wind-
mill! Electric bicycle! More! Highest quality!
Guaranteed! Big illustrated catalog! Write!

Lindsay's Technical Books

PO Box 538-EBA, Bradley IL 60915
fax: 815/935-5477 • lindsay@keynet.net

Prototype it..... FAST!

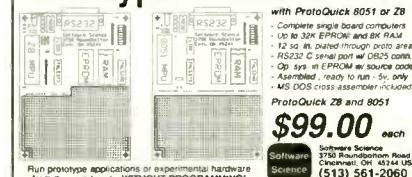

NEW!! Checker 12 E Monitor tester



COLOR BARS, GRAY SCALE & SWEEPS TO 64 K Hz!!!!!!

The "Checker 12" is an easy to operate, hand held, battery, or AC operated computer color monitor pattern generator. With its support of CGA(15.75khz), EGA(22khz), MACH(35khz), and VGA modes 1,2,3 (31.5khz), 800X600(35khz), **1024X768** interlaced (35khz), **1024X768 non-interlaced**, & **1024X768NI with sync on Green** (48khz), **++ 2 NEW VGA MODES>>> 56 kHz x 70 Hz & 64 kHz x 70 Hz**. With its single mode switch, you know exactly what type of monitor you are testing. Its front panel color pictures, show just what you should be seeing on the monitor under test. You can quickly tell if the monitor is a VGA, SVGA, or a SVGA/NI, guessing. The "Checker 12" provides various test patterns for VGA monitors. X-hatch, for size and linearity and convergence set-up. White screen, for purity and CRT burn evaluation. Color bars and 8 step gray scale for color tracking and balance. There is also a single color mode that allows for single color channel operation.

Price: \$339.00 + \$5.00 S&H.

Includes battery, AC adapter, Mac adapter and 1 year warranty
(upgrade your Checker 12 to a 12 E for \$49, call for details)

Please call about our other monitor test products, and offers, or visit our Webb site.



CMM

Computer & Monitor Maintenance

6649 Peachtree Ind., Blvd., Suite N-1 • Norcross GA 30092
1-800-466-4411, 770-662-5633 (Voice), 770-840-8814 (Fax)
We're on the WEBB at <http://www.computermonitor.com>

CIRCLE 331 ON FREE INFORMATION CARD

MCM ELECTRONICS®

**Value And Selection
From One Source...**

- Test Equipment from Tenma, Fluke, Hitachi, Leader, B+K
- Name Brand and Low Cost Generic Technician's Tools
- OEM and Generic TV/VCR repair parts
- Over 10,000 American and Original Japanese Semiconductors

MCM offers a comprehensive line of tools and test equipment engineered for the repair of computers, TVs, VCRs and more. In addition, you will find a wide variety of OEM and low cost generic TV/VCR parts, passive components and semiconductors, over 25,000 items in all, stocked and ready to ship.



**SAVE
23%**

IR Remote Control A/B Switch

Allows wireless switching between two 75ohm inputs. Ideal for cable, antenna, dish or dual cable systems. Requires 12VDC, 100mA, AC adaptor included. Remote requires two "AA" batteries, not included. UL listed.

#32-4425 Reg. \$25.75 Sale \$19.75

Prices effective
October 3 through November 16, 1996

Hours: M-F 7 a.m.-9 p.m., Sat. 9 a.m.-6 p.m., EST.

For Complete Information On the items
listed, or a FREE catalog, Call...

1-800-543-4330



MCM ELECTRONICS®
650 CONGRESS PARK DR.
CENTERVILLE, OH 45459-4072
A PREMIER Company

Fast Delivery From Distribution Centers Near Reno, NV and Dayton, OH.

**20th Anniversary
1996**

CODE: ENS28

ELECTRONICS NOW READERS ONLY!

Save up to 50% on select items!

Take advantage of

this tremendous offer.

Call today, time is limited!

To take advantage of this offer,

you must supply this special price code:

CODE: ENS28

**RITE
OFF**

**Projection Television
(PTV) Coolant**

Popular fluid is used by many large screen TV manufacturers and is a must when replacing CRTs in projection televisions. Direct replacement for Magnavox #4835-310-57233 and RCA 212072. 7.5 oz. can, 24 cans per case.

#20-2040 Reg. \$4.99

**SAVE
20%**



Sale \$3.99

#22-1145



#22-1150

**SAVE
50%**

Security Bit Drivers

For Nintendo and Sega

Driver bits allow easy removal of security screws found on many home video games, cartridges and accessories. $\frac{1}{4}$ " hex size fits standard $\frac{1}{4}$ " nut driver (MCM #22-1620) and most rechargeable screwdrivers. Available in two sizes.

#22-1145 3.8mm Reg. \$2.99 Sale \$3.99

#22-1150 4.5mm Reg. \$2.99 Sale \$3.99



**FREE
Catalog**

Authorized
Panasonic
Quasar/Technics
Original Parts
Distributor

RCA / GE
Premier
Distributor

CODE: ENS28

CIRCLE 327 ON FREE INFORMATION CARD

ALFA ELECTRONICS



DMM 89 \$179.00

Most Advanced DMM

All Purpose & Communication
-80.7 to 81.4 dBm with 4Ω-1200Ω
20 reference impedances
True RMS
Frequency counter: 0.01Hz-10MHz
Capacitance: 1pF-50,000μF
Measure AC volt to 20kHz
5000 counts, 0.1% accuracy
Auto/manual range, fast bar graph
Min/Max/Ave/DH/Relative/Zoom
Auto power off
Input warning
Splash proof
Volt, amp, ohm, logic, diode, continuity
Ruggedized case
Rubber holster included



**DMM A91
\$49.95**

NOW \$45.00

**Plus Free Case
Solar Cell Powered
Large Display**

Diode, Continuity
Volt, Amp, Ohm
Data Hold
Auto power off
7 functions, 19 ranges
3.5 Digit, 0.6% accuracy
Auto/Manual ranging
Energy saver
Student & hobbyist's favor



**DMM 20
\$74.95**

Inductance: 1μH-40H
Capacitance: 1pF-200μF
Frequency: 1Hz-20MHz
Volt, amp, ohm, diode,
20 Amp AC/DC current
Transistor HFE
Continuity, duty %
Peak hold/Max
Ruggedized case
Rubber holster \$8.00

Fluke Multimeter
Fluke 12 \$84.95
Holster C-10 \$10
Fluke 70 II \$75.95
Fluke 73 II \$97.50
Fluke 75 II \$129
Holster C-70 \$16
Fluke 77 II \$155
Fluke 79 II \$175
Fluke 29 II \$175
Fluke 76 \$175
Fluke 87 \$287
Fluke 867 \$1199
Fluke 97
Scope Meter \$1785
Fluke 105
Scope Meter \$2799



**LCR Meter 131D
\$229.95**

Most Advanced LCR

Dual display LQ or C/D
Inductance: 0.1μH-1000H
Capacitance: 0.1pF-20,000μF
Impedance: 1mΩ-10MΩ
0.7% basic accuracy
Auto/manual range
Dissipation factor & Q factor
Serial & parallel mode
Relative mode for comparison
and to remove parasitics
Statistics, tolerance,
Best for design, incoming
testing & production
SMD and chip component
test probe \$25.00



**LCR Meter 814
\$189.95**

Best Resolution LCR


Inductance: 0.1μH-200H
Capacitance: 0.1pF-20,000μF
Resistance: 1mΩ-20MΩ
1% basic accuracy
Dissipation factor indicates leakage
in capacitor and Q factor in inductor
Zero adjustment to reduce parasitics
Best for high frequency RF
SMD and chip component test probe
\$25.00

**LIMITED QUANTITY SPECIAL
DIGITAL LCR 680 \$74.95
0.1pF, 1μH, 10mΩ resolution**

**Frequency Counter
FC-1200 \$129.95**


Frequency 0.1Hz-1.25GHz
Display: 8 digit LCD
Period: 0.1μs-0.1s
Records: Max/Min/Average
Data hold, relative mode
Telescoping antenna \$8.00
Deluxe case \$5.00

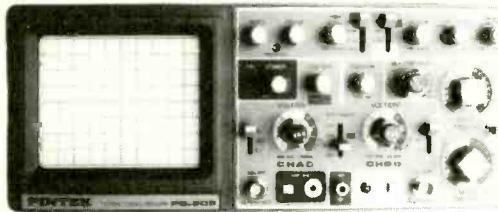Also Available:
AC/DC clamp meter, Light meter,
Thermometer, pH meter, High
voltage probe, Digital caliper,
Anemometer, Electronic scale,
Force gauge, Tachometer,
Stroboscope, Humidity & E&M
adapter, Sound level meter,
Frequency counter, SWR/field
strength/power meter, Dip meter




**20 MHz Oscilloscope with Delay
Sweep PS-205 \$429.95**

Dual Trace, Component test, 6" CRT, X-Y Operation, TV
Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes
each has x1,x10 switch. Best price with delay sweep.
PS-200 20 MHz DUAL TRACE \$339.95
PS-400 40 MHz DUAL TRACE \$494.95
PS-405 40 MHz DELAY SWEEP \$569.95
PS-605 80 MHz DELAY SWEEP \$769.95
PS-1000 100 MHz DUAL TRACE \$999.95
Scope Probe: 60MHz x1, x10 \$15, 100MHz x1, x10 \$22
250MHz x1, x10 \$29, 250MHz x100 \$39

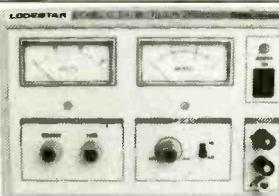

**DC Power Supply
PS-303 \$159.00**

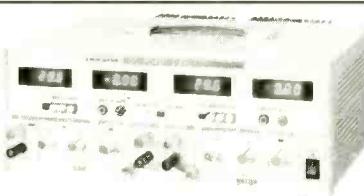0-30 VDC, 0-3A output
Constant voltage & constant current mode
0.02% +2mV line regulation
0.02% +3mV load regulation
1 mVrms noise and ripple
Short circuit and overload protected
PS-8200 with digital voltmeter \$179.00
Also available: 30V/5A, 60V/3A, 60V/5A
16V/10A, 30V/10A




Digital Storage Scope

DS-303 30MHz, 20M Sample/sec \$849.95

DS-303P with RS-232 Interface \$1,049.95
Switchable between digital and analog modes
2 K word per channel storage
8 bit vertical resolution (25 Level/div)
Expanded Timebase 10ms/div - 0.5 s/div
Refresh, Roll, Save all, Save CH2, Pre-Trig
Plotter control


**DC Power Supply Triple Output
PS-8202 \$499.95**

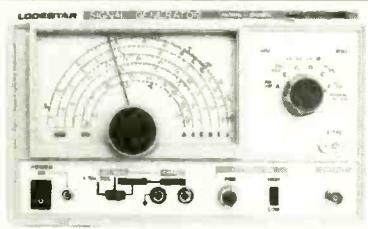Two 0-30 VDC, 0.3A outputs
One fixed 5VDC, 3A output
Capable of independent or tracking operation
Constant voltage and constant current mode
Four digital meters for volt and current display
Excellent regulation and low ripple
Short circuit and overload protected
Also available: 30V/5A, triple output \$549.95
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A



**RF SIGNAL
GENERATOR
SG-4160B \$124.95**

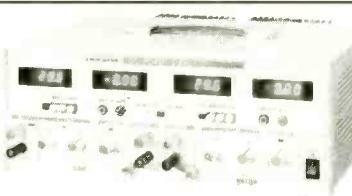100 kHz-150MHz sinewave in 6
ranges
RF Output 100mVrms to 35 MHz
Internal 1kHz, External 50Hz-20kHz
AM modulation
Audio output 1 kHz, 1 Vrms



**AUDIO GENERATOR
AG-2601A \$124.95**

10Hz - 1MHz in 5 ranges
Output: 0.8Vrms sinewave
0-10Vp-p squarewave
Synchronization: ±3% of oscillation
frequency per Vrms
Output distortion:
0.05% 500Hz - 50kHz
0.5% 50Hz - 500kHz
Output impedance: 600 ohm

**FUNCTION GENERATOR
FG-2100A \$169.95**

0.2 Hz - 2 MHz in 7 ranges
Sine, square, triangle, pulse and ramp
Output: 5mV-20Vp-p
1% distortion, DC offset ± 10V
VCf: 0-10V control frequency to 1000:1

**FUNCTION GEN/COUNTER
FG-2102AD \$229.95**
Generates signal same as FG-2100A
Frequency counter 4 digits
Features TTL and CMOS output

**SWEEP FUNCTION
GEN./COUNTER \$329.95**

0.5Hz to 5 MHz in 7 ranges
Sweep: Linear 10:1/Log 10:1 20ms to 2s
AM Modulation
Gated Burst, Voltage Control Generator
Generator Control Voltage & 6 digit counter
1Hz-10MHz for internal & external sources



**RF SIGNAL
GEN./COUNTER
SG-4162 AD \$229.95**

Generates RF signal same as
SG-4160B
6 digit frequency counter 1Hz - 150
MHz for internal and external
sources Sensitivity <50mV

**AUDIO
GEN./COUNTER
AG-2603AD \$229.95**

Generates audio signal same as
AG-2601A
6 digit frequency counter 1Hz-
150MHz for internal and external
sources Sensitivity <50mV

15 DAY MONEY BACK GUARANTEE, 1 YEAR WARRANTY

(800) 526-2532/(609) 520-2002
FAX:(609) 520-2007
Visa, Master Card, American Express, COD, Purchase Order Welcome


CIRCLE 213 ON FREE INFORMATION CARD

100 MHz Cursor Readout Scope
4 ch., 8 traces OS-6101 \$1,499.95




- * 4 independent channels, 8 traces
- * Time/Voltage cursor measurement
- * ALT triggering function for 4 ch.
- * Sweeps to 2ns/div, Delayed Sweep
- * TV Sync, Ch. 1 output, Z-axis input
- * 2 probes(x1, x10)

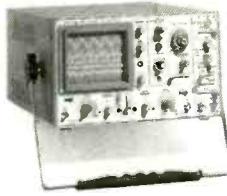100 MHz Scope, 4ch. 8 traces
Best value all purpose scope
OS-6100B \$1,329.95




- * 4 channels, 8 traces
- * High sensitivity 500 μ V/div
- * Sweeps to 2ns/div, Delayed sweep
- * 20 kV accelerating voltage
- * TV sync, Z-axis input
- * A and B gate output
- * Best price 100 MHz scope
- * 2 probes(x1, x10)

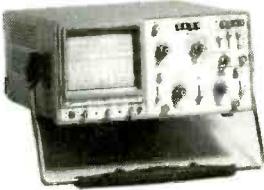50 MHz Triggering Oscilloscope
OS-653 \$699.95



- * Dual Channel
- * Hold Off Function
- * Delayed Sweep
- * Built-in Delay Line
- * TV Sync
- * ALT Triggering
- * High sensitivity 1 mV/div
- * Trigger level lock
- * Z-axis input, CH1 output
- * 2 probes(x1, x10)

20 MHz Oscilloscope
OS-622B \$344.95

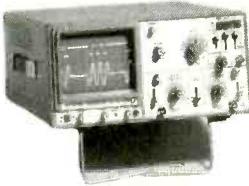

- * Dual trace, X-Y operation
- * TV Sync, Z-axis input, CH1 output
- * High sensitivity 1 mV/div
- * Trigger level lock
- * 2 probes (x1, x10)

OS-623B - 20 MHz w/Delayed Sweep \$449.95

OS-935 - 5 MHz One channel \$209.95

DC Linear Power Supplies Single Output



- * Constant voltage and constant current mode
- * Voltage regulation $\leq 0.01\%$
- * Current regulation $\leq 0.2\%$
- * Low ripple and noise
- * Overload and reverse polarity protection
- * Features 2 analog or 1 digital meter(PS series)
2 analog or 2 digital meters(PR series)

PS-1830 : (0-18V, 0-3A)	\$209.95
PS-1830D : Digital Display	\$219.95
PS-1850 : (0-18V, 0-5A)	\$219.95
PS-1850D : Digital Display	\$244.95
PS-3030 : (0-30V, 0-3A)	\$224.95
PS-3030D : Digital display	\$254.95
PS-6010 : (0-60V, 0-1A)	\$209.95
PR-1810H : (0-18V, 0-10A)	\$349.95
PR-3060 : (0-30V, 0-6A)	\$314.95
PR-6030 : (0-60V, 0-3A)	\$314.95
PR-6030D : Digital Display	\$399.95

PR-1810H : (0-18V, 0-10A) \$349.95

PR-3060 : (0-30V, 0-6A) \$314.95

PR-6030 : (0-60V, 0-3A) \$314.95

PR-6030D : Digital Display \$399.95

PR-1810H : (0-18V, 0-10A) \$349.95

PR-3060 : (0-30V, 0-6A) \$314.95

PR-6030 : (0-60V, 0-3A) \$314.95

PR-6030D : Digital Display \$399.95

PR-1810H : (0-18V, 0-10A) \$349.95

PR-3060 : (0-30V, 0-6A) \$314.95

PR-6030 : (0-60V, 0-3A) \$314.95

PR-6030D : Digital Display \$399.95

PR-1810H : (0-18V, 0-10A) \$349.95

PR-3060 : (0-30V, 0-6A) \$314.95

PR-6030 : (0-60V, 0-3A) \$314.95

PR-6030D : Digital Display \$399.95

PR-1810H : (0-18V, 0-10A) \$349.95

PR-3060 : (0-30V, 0-6A) \$314.95

PR-6030 : (0-60V, 0

Learn By Example!

The PRIMER 8085 Based Microprocessor Training and Control System shows you how to program by example. Program examples take you from writing simple programs to controlling motors. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port, a serial cable, 32K of battery backed RAM and Assembler/Terminal software.

EXPERIMENTS USING THE PRIMER INCLUDE:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Using the Primer as an EPROM Programmer

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed.

ENAC, inc.
P.O. BOX 2042, CARBONDALE, IL 62902
618-529-4525 Fax 457-0110 BBS 529-5708

1985 - 1996
OVER
10
YEARS
OF SERVICE

VOICE CHANGERS! ELECTRONIC KITS AND MORE!

PUT 15 YEARS OF EXPERIENCE TO WORK FOR YOU

Ever since we started in 1981, people have been telling us what they want, and we've delivered. We are pleased to offer a line of quality engineered kits, an iron clad guarantee, fast delivery, great prices, and a highly competent technical support staff that's just a phone call away if you need help. Prices subject to change without notice. Shipping and handling extra. In general our products are available in one or more of the following forms:

COMBO-KIT
Indicated by a **C** in the part number. These are complete kits with all parts, a printed wiring board, and assembly instructions.

E-Z KIT

Indicated by an **E-Z** in the part number. These are partially assembled and require some simple assembly before they can be used.

ASSEMBLED

These products are assembled, tested and ready to use.

143.79 MHz CRYSTAL CONTROLLED TRANSMITTER KITS



XTR300 E-Z
TRACKING TRANSMITTER KIT
Transmits continuous beep-beep tone. Ideal for locating lost or stolen items. Range up to 1/2 mile. Simply install the battery holder and the antenna wire and the unit is ready to use. Custom frequencies available. 3 Volt photo battery included.

88-108 MHz FM RECEIVER

XMR2000
Assembled \$29.95

- Worlds smallest FM radio
- As small as a hearing aid
- Weighs less than 1/4 oz.
- Digital touch tuning
- Ideal for use with our 88-108MHz FM transmitters

CRYSTAL TRANSMITTER KITS

- Ultra-miniature surface mount construction.
- E-Z kit approach makes assembly a snap.
- Miniature battery and holder mounted directly to the circuit board.
- Transmit to any scanner type receiver

XTL3000 E-Z
LONG RANGE TRANSMITTER KIT
Sensitive built in microphone with amazing audio sensitivity. Picks up sounds at the level of a whisper. With a range of up to 1 mile, this is our longest range transmitter. Custom frequencies available. 3 Volt photo battery included.

XTL1000 E-Z
TRANSMITTER KIT
Sensitive built in microphone with amazing audio sensitivity. Picks up sounds at the level of a whisper. Up to 1/2 mile range. Custom frequencies available. 3 Volt photo battery included.

88-108 MHz FM STEREO TRANSMITTER KIT

- Separate level control for both left and right channels.
- Output level circuit with test points for quick and easy tuning.
- Transmits from any stereo audio source to most any FM stereo receiver.

XANDI ADVANCED HOBBY KITS

XFS 108
Combo \$39.95
E-Z \$64.95

XLC 900
Combo \$49.95
E-Z \$76.95

800-950MHz SCANNER CONVERTER KIT

- Uninterrupted coverage of the 800 to 950 MHz band!
- Works with any 400-550MHz scanner.
- Gain: 8 dB typical.
- Noise figure: 3 dB typical.

ORDER BY PHONE:

ORDER LINE: 1-800-336-7389
FAX: 1-602-731-4748

TECH SUPPORT BY MAIL:

XANDI
ELECTRONICS, INC.
1270 E. Broadway Rd. #113
Tempe, AZ 85282

88-108 MHz FM TRANSMITTER KITS



XST 500 Voice transmitter. Range up to 1 mile. Supersensitive mic. Uses 9 volt battery. Uses surface mount components.

XWB 1000 Voice transmitter. Range up to 1/2 mile. Includes mic and battery on circuit board. Uses surface mount components.

XFM 100 Voice transmitter. Range up to 1 mile. 9 v battery and leadless components.

XSP 250 Super-miniature telephone transmitter. Range 1/4 mile. Powered by phone line. Uses surface mount components.

XTR 100 Tracking transmitter. Range up to 1 mile. Uses 9 volt battery. Transmits a BEEP - BEEP tone.

XTT 100 Telephone transmitter. Range up to 1 mile. Uses 9 volt battery.

**BUY WITH CONFIDENCE
FROM XANDI ELECTRONICS, INC.
ASK ABOUT OUR COMPLETE CATALOG**

PHONE VOICE CHANGER

16 levels of digital voice changing. Sound tougher, older or younger, female or male. Powered by 4 AA batteries. (Batteries not included).

Works with regular or multi-line phones. Connects between handset and phone. Note: will not work with cordless or handset type telephones.

T-2001
Assembled \$69.95

BUG DETECTOR

XBD500
Assembled \$149.95

- Professional quality.
- Not a kit, ready to use.
- Covers 1 to 2,000MHz.
- Uses a unique innovative integrated circuit amplifier.
- Adjustable sensitivity.
- Audio jack for privacy ear phone. Any interrupted signal causes an audio tone that increases from a low pitched growl to a high pitched squeal as the signal strength increases.

CIRCLE 281 ON FREE INFORMATION CARD



NOW YOU CAN "SEE" INVISIBLE FIELDS AND AVOID THEM

Most homes and offices have hot spots with strong artificial electro-magnetic fields, where chronic exposure may cause mental or physical problems. Even the EPA names these fields as suspected carcinogens. You can reduce your risk by avoiding these high-field areas.

The **TriField™** meter detects far more of these fields than any other electromagnetic pollution meter. It's the only one that independently reads AC electric fields, AC magnetic fields, and radio/microwaves. It also reads field strengths in all directions simultaneously. Every other meter that sells for under \$500 reads only magnetic and only in one direction — they can entirely miss a magnetic field unless pointed correctly and are blind to radio/microwaves and electric fields, both of which cause biological effects.

The **TriField™** meter reads all three types of fields numerically and with a SAFE/BORDERLINE/HIGH SCALE, weighted proportional to effect on the body. Thresholds are based on epidemiological and laboratory studies. (While no absolute hazard thresholds have been established, reduction of relative exposure is prudent.)

The **TriField™** meter comes ready-to-use with battery, instructions, and one-year limited warranty. The cost is \$144.50 postpaid.

AlphaLab, Inc. / 1280 South Third West / Salt Lake City, UT 84101-3049
For literature and information, call (503) 543-6545

Electronic CAD for Windows

Professional Windows EDA tools at an affordable price with powerful features to make designing faster. WinBoard PCB layout delivers sophisticated interactive routing for complex designs, plus it has the tools needed for high-speed circuits, analog, RF and SMT designs.

WinDraft® Schematics


- ◆ Use True-Type fonts. Quickly copy and paste into other applications.
- ◆ Supports hierarchical designs, electrical rules checking, Annotation & Bill of Materials.
- ◆ Thousands of library parts and symbol editor included.

WinBoard™ PCB layout

- ◆ Supports 16 layers, multiple copper pours, and advanced features for RF designs.
- ◆ SMD & through hole library with on-line graphical editor.
- ◆ CAM outputs include BOM, in-circuit test, NC Drill, Gerber, Pick & Place, & Advanced Design Rule Checking (DRC).

With our unique **pin capacity** versions you only pay for what you need. You choose the base configuration to suit your needs today, and expand that configuration to handle increased pin capacity as your design requirements change.

New Versions Available Now

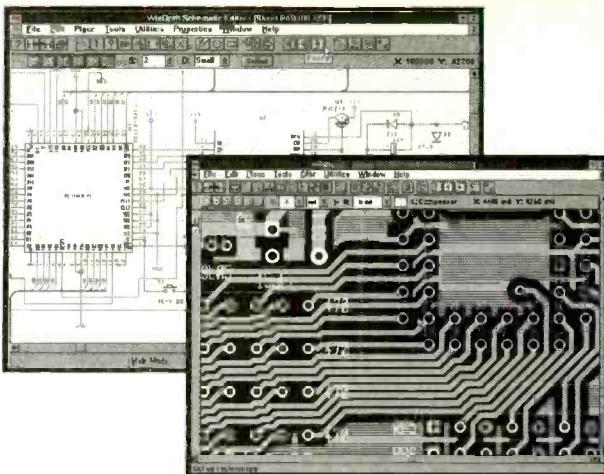

\$ 250 WinDraft or WinBoard - P650
\$ 495 WinDraft or WinBoard - unlimited

\$ 895 WinBoard P650 with CCT Specctras® autorouter.

Thousands of satisfied customers are using this new generation of powerful and affordable Windows EDA tools from Ivex. Your satisfaction is guaranteed!

World Wide Web: <http://www.ivex.com>

Information and free evaluation version is available on the Ivex WW Web, FTP and BBS.

Tel: (503) 531-3555
Fax: (503) 629-4907
BBS: (503) 645-0576



Ivex Design International. 15232 NW Greenbrier Parkway. Beaverton, Oregon 97006. USA.

ADV2_1

CIRCLE 329 ON FREE INFORMATION CARD

ROBOTIC MACHINING

ROUTE, MILL, DRILL, CARVE, ENGRAVE, PAINT . . .
IN WOOD, PLASTIC, VINYL, PC BOARD, & LIGHT METALS!

- 4 & 5 MOTOR GANTRY MILL CONFIGURATIONS
- PC COMPUTER CONTROLLED CNC/DNC
- IMPORT/EXPORT FILES TO OTHER CADS
- AUTO-BACKLASH COMPENSATION
- PRE-MACHINED HEAVY CASTINGS
- SIMULTANEOUS 4 AXIS MOTION
- FREE 3D CAD/CAM SOFTWARE
- AVAILABLE IN KITS OR ASSEMBLED
- EXPEDITE SERVICE ALSO AVAILABLE
- OPTIONAL ALUMINUM WAY COVERS
- .0005" RESOLUTION / AMERICAN MADE

STARTING AT
\$695.00



U.S. CYBERLAB, INC. 14786 SLATE GAP RD., WEST FORK, AR 72774

CALL NOW FOR INSTANT SPECS 501-839-8293 24 HR. FAX-BACK

PIC Programmer

Development Tools

JM-PICE

\$245

- Programmer for PIC 16C5X, 16C6X, 16C7X, 16C84, and 17C4X in DIP packages.
- Assembler and Simulator.
- Emulates program memory, registers, and I/O for the PIC 16C5X.
- Instruction-level emulation for the PIC 16C71 and 16C84.
- Programmer only **\$155**, Complete package **\$245**. 15 day money-back guarantee.
- Adapters for emulating 16C6X and 16C7X will be available soon.

80C552

Development System

- 8051 core processor with 8 channel 10-bit A/D and PWM.
- 24 more I/O and RS-232 port.
- 32K ROM and 64K RAM.
- \$130 each SBC. High performance development system includes assembler, disassembler, real-time execution and debugging, monitor program, and examples (\$70 more).
- 80C31 Development System is also available.

ROMY-16

EPROM EMULATOR

Emulates ROM or RAM in 8- and 16-bit systems. **\$195** (2716-27256) or **\$245** (2716-27010). Window/menu driven interface. 15 day money-back guarantee. Optional assembler, disassembler, and ROM debugger \$100 each CPU.

68HC11

Development System

- Eight channel 8-bit A/D converter.
- 32K ROM and 32K RAM.
- \$120 each SBC. 40x2 LCD \$20.
- Add \$70 for the real-time integrated development system.
- Microprocessor Simulator/Debugger and Custom design are available.


J&M

Microtek, Inc.

83 Seaman Road, W Orange, NJ 07052
Tel: (201)325-1892 Fax: (201)736-4567

The Pocket Programmer

Only \$129.95

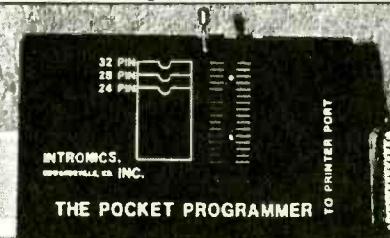

The portable programmer that uses the printer port of your PC instead of a internal card. Easy to use software that programs Eprom, EEPROM, Flash & Dallas Ram. 27(C) / 28(C) / 28F / 29F / 29C & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, PLCC, 5-Gang, 874X, 875X MCU's, 40-Pin X 16 & Serial Eprom's, and Eprom Emulator to 32K X 8.

Same Name, Address & Phone # for 13 Years... Isn't it Amazing ?

Intronics, Inc.


Box 13723 / 612 Newton St.

Edwardsville, KS 66113 Add \$4.75 COD

Tel. (913) 422-2094 Add \$4.00 Shipping

Fax (913) 441-1623 Visa / Master Charge

BAC552ES CONTROLLER

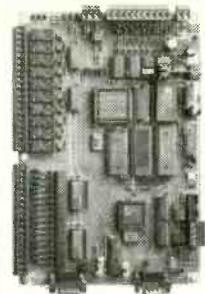

- Enhanced BASIC Language
- Philips 80C552 MCU
- 6" x 9" circuit board
- 10 SA relay outputs
- 3 LED or logic outputs
- 16 opto-isolated inputs
- 8 ch. 10 bit analog inputs
- 2 ch. 8 bit analog outputs
- Real Time clock/calendar
- 128K Static RAM
- 128K FLASH memory
- 256 byte serial EEPROM
- 3 serial ports (RS232/485)
- IIC bus expansion
- Plug-on I/O terminal blocks
- Single 12Vdc operation

APPLICATION READY ONLY

Includes \$14.95 Connector Package!

\$34.95

APPLICATIONS: Industrial control • HVAC systems • security • home automation • data logging • remote control & monitoring

SYLVA Control Systems a division of Sylva Energy Systems Inc.

519 Richard Street, Thunder Bay, Ontario, Canada P7A 1R2

Ph. 807-768-2487 Fax 807-683-4585 888 807-767-0587

WEB PAGE: <http://www.sylvacontrol.baynet.net>

Email: sylva@mail.baynet.net

16 Bit Control

& Data Acquisition System



from **\$299**

DSP
Powerful,
Easy to use,

Tons of Memory,

I/O & features:

16.8MHz 68HC16 34 digital I/Os (7 IRQ)
RS-232 & RS-485 + LCD/Keypad port
RT clock option + 8 ch 10 bit fast A/D

Affordable "C" compiler/library
Multi-tasking kernel
Up to 256K ea. SRAM, FLASH memory

INTEC INOVENTURES INC.

Ph: (604) 721-5150 FAX: 721-4191
<http://www.islandnet.com/~iii>

WINDOWS 95

—One Step at a Time

Don't know what to do when confronted with Microsoft's Windows 95 screen? Then you need a copy of **Windows 95—One Step at a Time**. Develop your expertise with the straight-forward presentation of the frequently-used features that make Windows 95 so valuable to the PC user.



To order Book BP399 send \$6.95 plus \$3.00 for shipping in the U.S. and Canada only to **Electronics Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.

INTERFACE TO YOUR PC KEYBOARD INPUT !

Our KE-18 Keyboard Encoder converts input from switches and keypads into PC compatible keyboard signals.

- Use with or without your own PC's keyboard
- Scans 9 x 9 matrix or 18 individual inputs
- PCXT, AT, PS2 and Compatibles
- Looks like a Keyboard to your Computer

Hagstrom Electronics

2 Green Lantern Boulevard

Endicott, NY 13760 (607) 786-7523



ONLY \$44.95

Keep your PCs up & running with the 100% accurate fix...

Loop-back Plugs—9-pin serial, 25-pin serial and 25-pin parallel plugs, used for external I/O port testing.

Universally Compatible

Works with any IBM or compatible computer and any operating system (DOS, Windows 95 & NT, OS/2, Unix, Novell, etc.)

Micro-Scope™ diagnostic diskettes—containing the best PC diagnostic tools on the market. Comes with both 3.5" and 5.25" disks to work with any PC.

Durable Zip-up Leatherette Carrying Case—all your tools in one organized, easy to carry toolkit.

Complete Micro-Scope Manual—easy to follow testing procedures and detailed error code descriptions. See the features list at left to view some of the incredible wealth of testing capabilities this program contains.



Tri-State Logic Probe—works with Post-Probe to enable testing down to individual chip level.

Post-Probe™ Diagnostic Card—when Post-Probe detects an error, a 2-digit BIOS code will display on the card telling you exactly what's wrong with your PC. 100% compatible with all ISA, EISA, Compaq and Micro-Channel PCs.

Micro-Channel Adapter Card—(behind Post-Probe card) allows Post-Probe to be used with Micro-Channel equipped computers.

Extensive Post-Probe Manual—exhaustively complete, containing BIOS error codes for most PCs on the market. Look up the 2-digit error code in this manual and instantly diagnose your PC's problems. Also contains common chip diagrams, descriptions and complete troubleshooting tips.

Micro-Scope™

UNIVERSAL DIAGNOSTIC SOFTWARE
Fully O/S Independent diagnostic software...



Call for upgrade pricing & complete new features list!

Jerry Pournelle awarded MICRO-SCOPE & POST-PROBE the User's Choice Award in the May 1994 issue of Byte Magazine, stating: "You name it, this tests it. If you maintain PCs you'll love it."

♦ **LOW-LEVEL FORMAT**—Performs low-level format on all hard drives including IDE drives. ♦ **TRUE HARDWARE DIAGNOSTICS**—Accurate testing of CPU, IRQ's, DMA's, memory, hard drives, floppy drives, video cards, etc. ♦ **RELOCATES TRACK 0** on hard drives that support relocation. ♦ **IRQ CHECK**—Talks directly to hardware and shows I/O address and IRQ of devices that respond. ♦ **O/S INDEPENDENT**—Does not rely on O/S for diagnostics. Talks to PC at hardware level. All tests are full function regardless of O/S (i.e. Windows, Novell, UNIX, OS/2). ♦ **IRQ DISPLAY**—Shows bits enabled in IRQ chip for finding cards that are software driven (Network, Sound Card, etc.). ♦ **MEMORY DISPLAY**—Displays any physical bit of memory under 1 MB. Very useful for determining memory conflicts and available memory space. ♦ **AND MUCH MORE...**—We don't have enough space here for everything this software can do!

Govt. Orders: NSN-7030-01-421-6459

Professional Diagnostics from

MICRO 2000™

Call Now for Latest Pricing
1-800-864-8008

© 1996 Micro 2000, Inc. All Rights Reserved.
CIRCLE 325 ON FREE INFORMATION CARD



Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

...with the AES learning system/embedded control system.

Extensive manuals guide you through your development project. All programming and hardware details explained. Complete schematics. Learn to program the LCD, keypad digital, analog, and serial I/O. for your applications.



THREE MODELS AVAILABLE. Choose from an Intel 8051, Intel 8088, or Motorola 68HC11 based system. All models come with:

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details (over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279.
Money Back Guarantee


Call for Free Info Pack, or see
WEB at <http://www.aesmicro.com>
714-550-8094, FAX 714-550-9941



Call 1-800 -730-3232

AES 970 W. 17TH STREET. SANTA ANA. CA 92706. USA

386 SBC \$83

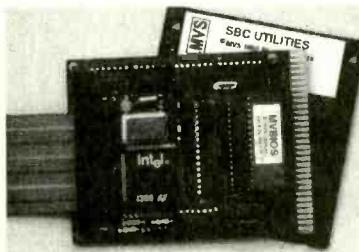


OEM (1K) PRICE
INCLUDES:
-5 SER (8250 USART)
-3 PAR (32 BITS MAX)
-32K RAM, EXP 64M
-STANDARD PC BUS
-LCD, KBD PORT
-BATT. BACK RTC
-IRQ0-15 (8259 X2)
-8237 DMA 8253 TMR
-BUILT-IN LED DISP
-UP TO 8 MEG ROM
-CMOS NVRAM

USE TURBO C,
BASIC, MASM,
RUNS DOS AND
WINDOWS
EVAL KIT \$295

\$95 SINGLE
PIECE
PRICE
**UNIVERSAL
PROGRAMMER**

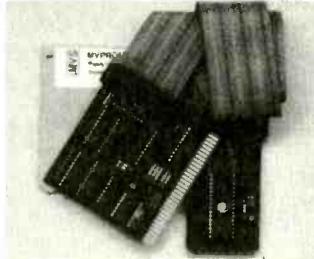- DOES 8 MEG EPROMS
- CMOS, EE, FLASH, NVRAM
- EASIER TO USE THAN MOST
- POWERFUL SCRIPT ABILITY
- MICROCONT. ADAPTERS
- PLCC, MINI-DIP ADAPTERS
- SUPER FAST ALGORITHMS



OTHER PRODUCTS:
8088 SINGLE BOARD COMPUTER OEM \$27 ... *95
PC FLASH/ROM DISKS (128K-16M) 21 75
16 BIT 16 CHAN ADC-DAC CARD 55 195
WATCHDOG (REBOOTS PC ON HANGUP) 27 95

*EVAL KITS INCLUDE MANUAL
BRACKET AND SOFTWARE.
5 YR LIMITED WARRANTY
FREE SHIPPING
HRS: MON-FRI 10AM-6PM EST



MVS BOX 850
MERRIMACK, NH
(508) 792 9507

DATA ACQUISITION

and Control Hardware for PC's

ANA100 Analog I/O \$ 99



- * 8 Channel 8-Bit
- * 0 to 5 Volt Input
- * 14 TTL I/O lines
- * Analog Output
- * 400KHz Sampling

DIG100 Digital I/O \$ 39



- * 8255 PPI
- * 24 or 48 TTL I/O Lines option
- * Selectable Base Address

ANA150 Analog/Counter... \$ 89



- * 8 Channel 8-Bit
- * 0 to 5 Volt input
- * 3 16-Bit Counters
- * 400KHz Sampling

DIG200 Counter I/O \$ 79



- * 3 16-Bit Counters
- * 8 TTL Input lines
- * 8 TTL Output lines
- * Selectable Clock Frequency input

ANA200 Analog I/O \$ 79



- * 1 Channel 12-Bit
- * 0 to 5 Volt input optional bi-polar
- * 100KHz / 300KHz Sampling rate
- * 24 TTL I/O lines

ANA201 Analog \$ 129



- * 8 Channel 12-Bit
- * x1, x5, x10, x50 Programmable Channel gain
- * 100KHz/300KHz Sampling rate

Engineering Software - PC/MSDOS


Easy-PC Professional XM - Integrated Electronics cad system, Schematic Capture, Circuit Analysis, and PCB Design in one software package \$ 399.00

PC-SCOPE - Digital Storage Oscilloscope, 1, 2, 4, or 8 Channel Capture and Data Display. Works with ANA100, ANA150, and ANA201 Boards \$ 39.00

MasterCard/Visa orders accepted
More hardware and software items available, Call for information or
See our catalog on the internet: <http://www.bssoft.com>
E-mail: sales@bssoft.com

BSOFT Software, Inc.

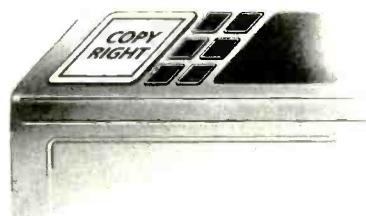Phone 614-491-0832 * Fax 614-497-9971
444 Colton Road * Columbus, OH * 43207



THE MOST
**AN IMPORTANT PART
OF YOUR PHOTOCOPIER
ISN'T PART OF
YOUR PHOTOCOPIER**

Having a machine may not permit you to photocopy books, journals, newsletters and magazines.

The Copyright Clearance Center CAN.

Contact us to find out

how you too can COPY RIGHT!™

COPYRIGHT CLEARANCE CENTER

222 Rosewood Drive, Danvers, MA 01923 □ Tel. (508) 744-3350 □ Fax (508) 741-2318

©1993 Copyright Clearance Center

"Get the skills you need at a price you can afford!"

Earn up to \$45 an hour or more as a skilled Computer Programmer.

Cash in on the explosion of opportunities. Start your new career or even open a business of your own as a highly-paid computer programmer.

Computer programmers today can almost write their own ticket to financial well-being and job satisfaction. Only Foley-Belsaw's unique in-home training programs can give you the skills you need at a price you can afford.

You'll learn the three hot computer languages — QBasic, C and Visual Basic. You'll even work with the hot new C++. With this easy-to-learn knowledge, you'll write your first QBasic program by the end of the first SkillPak of lessons. Soon you'll be programming sound and graphics, and even learning how to program for the Windows environment — the most popular application program today.

It's easy to cash in!


Look at some of the things professional computer programmers do. "Wrote a C program to clean up a WordPerfect file; edited the resulting file as data errors were found." This work would take a trained programmer less than five hours to complete, and they could make over \$200 for the work. That's money you could be making — and soon — with training from the Foley-Belsaw Institute of Computer Programming.

Everything is included!

We provide you with all the materials you'll need to become a professional computer programmer. You'll receive 37 lessons, designed for you by the Foley-Belsaw Professional Programmer Staff. Other valuable materials include a *Programmer's Handbook*, *Programmer's Examples* on two 3.5 inch disks, *Programmer's Flowchart Template*, and a booklet, *Selecting the Right Computer*.

Other schools force you to buy a complete computer package as part of their training program. At Foley-Belsaw we understand that your needs as a programmer may not fit into a "one size fits all" approach. Why should you pay hundreds of dollars for a computer system that you may not need?

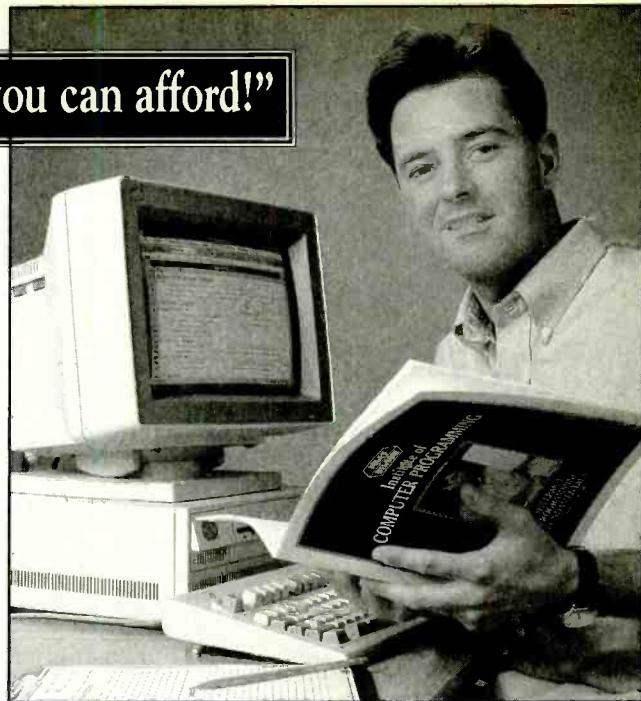We'll tell you what you need to know so that when you're ready to buy your own computer, you can get the machine that fits your needs at the lowest possible price. That's the Foley-Belsaw way.



Get the free facts today.

Whether you want to change careers, have a profitable part-time job or start your own business, Foley-Belsaw Institute's new computer programming course is the first step. A profitable future in computer programming can be yours. Call or write today for a fact-filled information kit including a free copy of *Computer Programming — A Profitable Career In Your Spare Time*. See how easy it is to begin a money-making career as a sought-after computer programmer. Our free full-color information kit outlines the steps of the computer programming course and shows you everything you will receive as part of your training.

Mail this coupon or call today
Toll Free 1-800-487-2100!

Your free opportunity kit will be rushed to you!

If coupon is missing, write to: Foley-Belsaw Company, 6301 Equitable Road, Kansas City, MO 64120

Call or complete & return this coupon to: Foley-Belsaw Institute, 6301 Equitable Road, Kansas City, MO 64120

YES! Rush me a free information kit on Computer Programming right away. Dept. 35281

Other career courses:

- Locksmithing, Dept. 12871
- Small Engine Repair, Dept. 52747
- Saw & Tool Sharpening, Dept. 21687
- VCR Repair, Dept. 62561
- Computer Repair, Dept. 64458
- TV/Satellite Dish Repair, Dept. 31333
- Gunsmithing, Dept. 92361
- Woodworking, Dept. 43619
- Upholstery, Dept. 81288
- Vinyl Repair, Dept. 71221
- Electrician, 95136
- Computer Specialist, 38129
- Networking Specialist, 39116

I understand that there is ABSOLUTELY NO OBLIGATION and NO SALESMAN WILL CALL.

Name _____

Address _____


City _____ State _____ Zip _____



**FOLEY
BELSAW**
Since 1926

CIRCLE 307 ON FREE INFORMATION CARD


Low Cost CAD Software Now In Windows™ 95

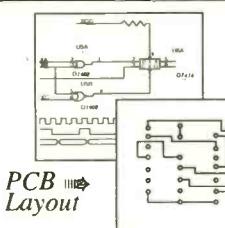

- Easy to use schematic entry program (**SuperCAD**) for circuit diagrams, only \$149. Includes netlisting, bill of materials, extensive parts libraries.
- Digital simulator (**SuperSIM**) allows you to check logic circuitry quickly before actually wiring it up. Works directly within SuperCAD and displays results in "logic analyzer" display window. Starting at \$149 this is the lowest cost simulator on the market. Library parts include TTL, and CMOS devices.
- Analog simulator (**mentalSPICE**) for \$149. Allows AC, DC and transient circuit analysis. Includes models of transistors, discrete, and op amps.
- Circuit board artwork editor and autorouter program (**SuperPCB**), starting at \$149. Produce high quality artwork directly on dot matrix or laser printers. You can do boards up to 16 layers including surface mount. Includes Gerber and Excellon file output. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- New! Complete electronic design package (**SuperMAX**) including schematic editor, analog and digital circuit simulation, and printed circuit board layout with autorouter for only \$549!

Write or call for free demo disks:
MENTAL AUTOMATION INC.
5415 - 136th Place S.E.
Bellevue, WA 98006
(206) 641-2141
Internet: <http://www.mentala.com>

PIC it µP!

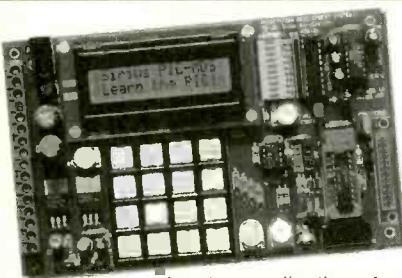

The PIC-MDS is a complete training and development environment for the mid-range PIC™ microcontrollers. Proven in classrooms, the PIC-MDS lets **you** learn to use and

develop applications for PIC microcontrollers quickly and easily. Our step-by-step examples guide you from simple programs through to keypad scanning, serial I/O, LCD display, A/D conversion, data logging, and interrupt routines.

The PIC-MDS Professional Pack includes:

- PIC16C71 & PIC16C84 microcontrollers
- EPIC Programmer & PM assembler
- detailed training manual with disk
- in-circuit programming cable & socket
- ZIF socket • buffered LED port indicators
- 2 X 16 LCD display • 2 analog pots • RS-232 port
- 256 byte serial EEPROM • crystal/resonator socket
- 5V & variable DC power supply • AC voltage adapter
- all I/O pins on screw terminals & PICBUS connector
- all code examples in Microchip and Parallax™ syntax

only
\$299!

Also Available:

- | | |
|---|--------------|
| Professional Board
(no programmer) | \$259 |
| Hobbyist Pack | \$199 |
| (kit, no ZIF, '84 only) | |
| Hobbyist Board | \$139 |
| (kit, no ZIF, '84 only,
no programmer) | |
| Teachers manual | Call |
- Prices exclude shipping. Parallax is a registered trademark of Parallax, Inc. PIC & Microchip are trademarks of Microchip Technology Inc.

Sirius
microSystems

Visit our Web page: <http://www.siriusmicro.com>

172 Harvard Road
Waterloo, ON N2J 3V3
CANADA
+1-519-886-4462 (ph.)
+1-519-886-4253 (fax)
support@siriusmicro.com

EPROM+ PROGRAMMING SYSTEM USES PARALLEL PORT

**SUPPORTS OVER
600 CHIPS**

EPROMS (24, 28, 32 & 40* PIN PLUS 27CXXX)
1702, 2708, 16, 32, 32A, 64, 64A, 128, 128A, 256, 512
513, 01, 010, 101, 301, 1000, 1001, 1024, 210, 020
2000, 2001, 220, 240, 2048, 4001, 4002, 040, 080, 8001
2516, 32, 64, 68, 764, TMS2716

FLASH EPROMS
28F256, 512, 010, 020 PLUS 29CXXX, 29FXXX

EPROMS & NVRAMs (PLUS CXXX)
2804, 16, 16A, 17, 2864, 64A, 65, 28256, 28C010
X2210, X2212, DS1220, 1225, 1230

SERIAL EPROMS* (8 PIN PLUS CXX)
2401, 02, 04, 08, 16, 32, 65, 2444, 59C11, 8572, 82, 92
9306, 46, 56, 66, 16811, 911, 80011A, ER1400/58657

BIPOLAR PROMS* (16 THROUGH 24 PIN)
74XXX AND 82XXX FAMILY

MICROCONTROLLERS* (UV, EE AND FLASH)
8741, 42, 48, 49, 8751, 8752, C52, 87C5XXX
87C75X, 89C51, 52, 68705, 68HC705, 68HC711E9
PIC16C5X, PIC16C6X, PIC16C7X, PIC16C8X

*ADAPTER REQUIRED ASSEMBLED ADAPTERS AVAILABLE / DETAILED DIAGRAMS INCLUDED

SOFTWARE - READ, VERIFY, PROGRAM, COPY, DISK FILE LOAD & SAVE, CHECKSUM, PLUS A FULL SCREEN BUFFER EDITOR WITH 20 COMMANDS
•READS INTEL HEX, MOTOROLA S-RECORD AND BINARY FILES
•FAST! MANY DEVICES PROGRAM IN UNDER 10 SECONDS
•RUGGED (9" X 6" X 3"), PORTABLE ENCLOSURE WITH CARRY HANDLE DESIGNED FOR BENCH AND FIELD SERVICE.
•ACCESSORY CONNECTOR FOR FUTURE EXPANSION
•LED INDICATORS SHOW POWER, PROGRAMMING & SYSTEM STATUS
•MADE IN THE USA - 30 DAY MONEY BACK GUARANTEE - 1 YR WARRANTY
•SYSTEM INCLUDES: PROGRAMMING UNIT, POWER PACK, CABLE PRINTED MANUAL AND SOFTWARE

ANDROMEDA RESEARCH
P.O. BOX 222
MILFORD, OHIO 45150
(513) 831-9708
FAX (513) 831-7562

\$289



ADD \$5.00 SHIPPING - \$5.00 C.O.D.

PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAMS DATA I/O ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



PROMAX	ADVANTECH LABTOOL	629 EETOOLS SIMMAX
EMP-20	689 ICE TECH MICROLY	795 CHROMA SIMM/SIP
MEGAMAX	669 EETOOLS ALLMAX +	350 MOD-MCT-EMUPA/R
MEGAMAX4	429 EETOOLS PROMAX	279 MOD-MCT-EMUP/R
SIMM/SIP TESTER	439 EETOOLS MEGAMAX	49 EPROM 1G TO 512K
EMUPA	539 EETOOLS MEGAMAX4	79 EPROM 1G TO 1MEG
	529 XELTEK SUPERPRO II P	429 XELTEK SUPERPRO II
	269 XELTEK SUPERPRO L	199 EPROM 1G TO 1MEG
	179 XELTEK ROMMASTER II	199 EPROM 1G TO 8MEG
	479 MOD-MCT-EMUPA	129 EPROM 4G TO 8MEG
		250 EPROM 8G TO 8MEG




General Device Instruments

Sales 408-241-7376 Fax 241-6375 BBS 983-1234

Web www.generaldevice.com E-Mail icdevice@best.com



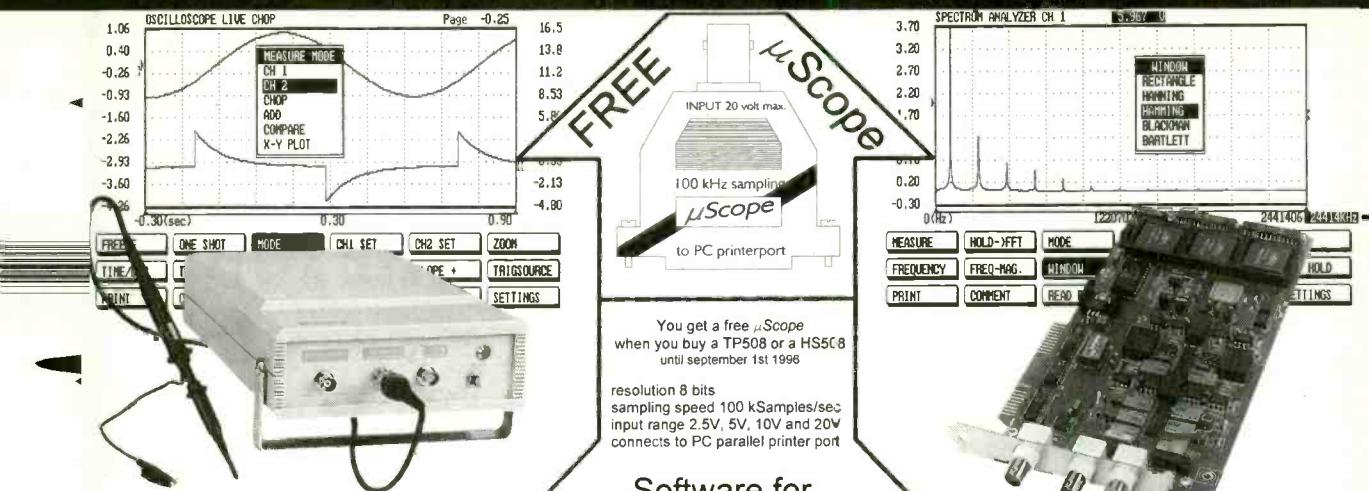-SPY, INC.
ELECTRONIC SURVEILLANCE &
PRIVACY ASSURANCE DEVICES
Cell & Home Phone Scamblers, Covert
Video Cameras, State of the Art Electronic Devices
"YOU NEVER KNOW WHO'S WATCHING OR LISTENING"
For a Full Catalog Send \$5 Check or M.O. to
I-SPY, Inc., PO Box 1707EN Amherst, NY 14226
or call (716) 874-1707



TiePieSCOPE HS508

- interface PC parallel printer port
- sampling speed 50 Msamples/sec
- resolution 8 bits
- input range 50 mV/div - 20V/div
- record length 32KByte/channel
- price US\$1054 incl. software, user manual and 2 probes (1:1/1:10 switchable)

Software for the PC-based instruments


contains an Oscilloscope, a Spectrum analyzer, a Voltmeter, and a Transient recorder. All instruments are controlled in the same intuitive way and provide for saving and recalling waveforms and settings, cursor measurements, hard-copy on matrix / laser printer and online help. Minimum requirements: a 80286-based PC with 2MByte and running MSDOS 3.3 or higher.

Call toll-free 1-800-626-6929 for a free demo disk and our catalog

Easy installation: just plug in and measure

TP508

- interface PC-XT/AT ISA slot
- sampling speed 50 Msamples/sec
- resolution 8 bits
- input range 5 mV/div - 20 V/div
- record length 32 KByte/channel
- price US\$1098 incl. software, user manual and 2 probes (1:1/1:10 switchable)

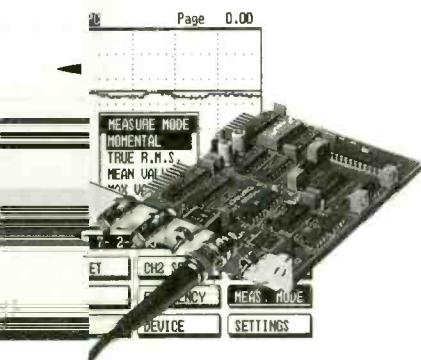


TP5008

- interface PC-XT-AT ISA slot
- sampling speed 200ksamples/sec
- resolution 8 bits
- input range 125 mV/div - 5 V/div
- programmable analog output channel
- price US\$307 incl. software, user manual and 2 probes (1:1/1:10 switchable)



HANDYSCOPE

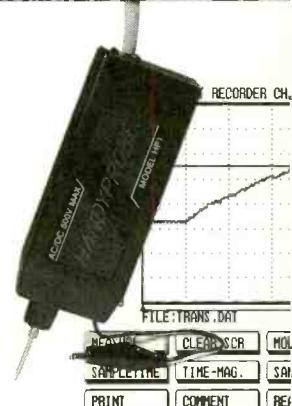- interface PC parallel printer port
- sampling speed 100ksamples/sec
- resolution 12 bits
- input range 125 mV/div - 5 V/div
- no external power required
- price US\$499 incl. software, user manual and 2 probes (1:1/1:10 switchable)



HANDYPROBE

- interface PC parallel printer port
- sampling speed 100ksamples/sec
- resolution 8 bits
- input range 125 mV/div - 100 V/div
- no external power required
- price US\$169 incl. software, user manual

CONWAY Engineering, Inc.

8393 Capwell Drive, Oakland, California USA 94621-2113

Tel: (510) 568-4028 Fax: (510) 568-1397

BBS: (510) 568-6533 Internet: <http://www.crl.com/~conway/>

Call toll-free 1-800-626-6929 for a FREE demo disk and a catalog of all our instruments!

CIRCLE 320 ON FREE INFORMATION CARD



EARN MORE MONEY!

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to
\$60 an hour
and more!

Learn at home in spare time.
No previous experience needed!

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! GUARANTEED PASS—You get your FCC License or money refunded. Send for FREE facts now. MAIL COUPON TODAY!

Or, Call 1-800-932-4268 Ext. 210

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 210
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

ONLY COOL-AMP SILVERPLATES ON THE JOB.

From a customer testimonial:

"Ok, your edge connectors don't connect. Or you want to plate your own PC creations, but you don't want to bother with electro-plate solutions. The plating on the socket...has worn off and no longer makes reliable contact...what are you going to do now?"

"Give the people at Cool-Amp a call. They have a silver plating compound I have used for the past couple of years that solves all of the above problems and more. This white powder has an infinite shelf life...and is easy to use.

"It will actually put a permanent silver plate on copper, brass or bronze...There are no messy or dangerous chemicals. Application could not be easier. Use a clean rag and a little bit of water and just rub it on a clean surface. In minutes you can permanently silver plate a circuit board or replate a power amp tube or socket.

"It has saved me time, money and my sanity."

Cool amp has even outperformed electroplating in recent tests. It is time-proven since 1944.

COOL-AMP


AND CONDUCTO-LUBE. THE SILVER-BASED CONDUCTIVE LUBRICANT.

The upstart, since 1952. Developed for switches, uses continue to expand to all applications needing a conductive lubricant.

Conducto-Lube

**ORDER FACTORY DIRECT:
503-624-6426 or FAX 503-624-6436**

Quality Reconditioned Test Equipment from Danbar

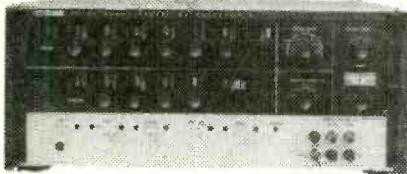

Fluke 5200A

Programmable ac calibrator, outputs from 100 μ V rms to 120 V rms at 50 mA. Frequency range 10 Hz to 1 MHz, amplitude range is 1 mV to 1000 V.

Special \$1500.00

Fluke 5215A

Power Amplifier, output voltages to 1100 Vrms, max output of 200 W, frequency from 10 Hz to 100 kHz.

Special \$1500.00

Fluke 5220A

Transconductance Amplifier, lets you calibrate meters and shunts, 20 amps output dc or rms ac, 0.25% basic dc accuracy.

\$2800.00

Fluke 720A

Kelvin-Varley Voltage Divider, 0.1 ppm resolution, 0.1 ppm of input absolute linearity.

Special \$1000.00

Fluke 5100B Calibrator

Calibrator for analog and digital multimeters up to 4.5 digits, five functions: direct or alternating voltage or current plus resistance. Opt 03, 05.

\$4350.00

Fluke 5101B Calibrator

Similar to 5100B but has procedure storage feature. Opt Y5000 Interface buffer for 5205A, 5215A and 5220A.

\$5000.00

Fluke 335D

Dc Standard Null Detector, 1 μ V to 1000 Vdc with .001% accuracy.

\$750.00

ESI RV622A Dekavider

Decade voltage divider, 6 dial, 10,000 Ω .

\$199.00



Please call for our Free 1996 Catalog



CIRCLE 235 ON FREE INFORMATION CARD

14455 NORTH 79TH STREET • UNIT C • SCOTTSDALE • ARIZONA 85260
(602) 483-6202 • FAX (602) 483-6403

Fluke 5440B

Direct Voltage Calibrator, 0 to 1100V range, completely automatic internal calibration, procedure storage module for single button set-up, completely programmable through the GPIB/ IEEE-488 interface.

\$5600.00

Fluke 931B

True RMS Voltmeter, measures .01 to 1100 V in 5 ranges over 2 Hz to 1 MHz frequency range.

\$450.00

Fluke 5450A

Resistance Calibrator, 17 standard resistors in 1 box, decade values from 1.0 Ω to 100 M Ω , 1.9 multiples from 1.9 Ω to 19 M Ω , GPIB/IEEE-488 programmable.

\$1250.00

Fluke 343A

Dc Voltage Calibrator, 7 decade instrument with a basic accuracy of 20 ppm and a resolution of 1 μ V on the 10 μ V range, 0 to 1100V output, 0 to 25 mA, 0.1 ppm resolution.

\$1000.00

Fluke 752A

Reference Divider, 10:1 and 100:1 division ratios, ratio accuracy of 0.2 ppm on 10:1 ratio, ratio accuracy of 0.5 ppm on 100:1 ratio, built-in calibration bridge.

\$1750.00

Fluke 332D

DC Voltage Calibrator, output voltage ranges from 0 to 1111.1110 Vdc and is set by 7 in-line decade switches.

\$149.00

Fluke 5205A

Precision Power Amplifier, extends the range of 5700A, 5100B series, 5200A or 5400B calibrators, output voltages to 1100V rms, \pm 1500V dc, max output power 220 watts, dc to 100 kHz.

Special \$2000.00

Fluke 540B

Transfer Standard, this is a thermal instrument used for precise measurement and calibration of ac voltage and current, voltage transfers from 0.25 to 1000 Vrms in 14 ranges with a frequency from 5 Hz to 1 MHz.

\$550.00

ESI DB62

Variable Resistor, 6 decades, 11,111,100 Ω , 10 M Ω max in .01 Ω steps.

\$199.00

Fluke 515A

Portable Calibrator provides dc voltage, ac voltage and resistance standards in a compact unit. 0 to 100 Vdc, 2 μ V resolution, 0 to 100 Vac, 0 to 10 mA rms.

\$1500.00

Fluke 845AR


Voltmeter/ Null Detector, high input impedance, 1 μ V to 1000V in 19 ranges, input resistance 100 M Ω on 300 mV and above, 10 M Ω on 100 mV and below.

Special \$300.00

Datron 4000A

Autocal Standard, high-precision calibrator with exceptionally high stability and full system capability. Provides dc voltage calibration facilities in 8 decade ranges from \pm 100 μ V to 1000 V, 7.5 digit, IEEE 488.

\$5000.00

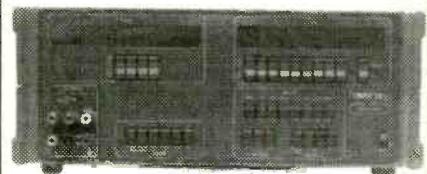

Fluke 8922A

True RMS Voltmeter, 2 mV to 700V ranges, 4 digit display, relative dB, 2 Hz to 11 MHz.

\$700.00

Fluke A55 Set of 9

High Frequency Thermal Converters, set of 9 pieces.

\$1500.00



SEE US
NOW AT

<http://www.cir.com>

CIRCUIT
SPECIALISTS
INC.

Check Out What We Have To Offer:

Fantastic DMM Offer!!!

Don't let the price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch. **Rubber Boot Included**

General

Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity

Overrange Indication: 3 Least Significant Digits Blank

Temperature for Guaranteed Accuracy:

23°C±5°C RH<75%

Temperature Ranges:

Operating: 0°C to 40°C (32°F to 104°F)

Storage: -10°C to 50°C (14°F to 122°F)

Power: 9V Alkaline or Carbon-Zinc Battery(NEDA1604)

Low Battery Indication: BAT on Left of LCD Display

Dimensions: 188mm long x 87mm wide x 33mm thick

Net Weight: 400g

DC Voltage (DCV)

Range: Resolution: Accuracy:

200mV 100µV

2000mV 1mV

20V 10mV

200V 100mV

1000V 1V

Maximum Allowable Input: 1000V DC or Peak AC.

DC Current (DCA)

Range: Resolution: Accuracy:

200µA 100nA

2000µA 1µA

20mA 10µA

200mA 100µA

10A 10mA

Overload Protection: mA Input: 2A/250V fuse.

AC Voltage (ACV)

Range: Resolution: Accuracy:

200V 100mV

750V 1V

Frequency Range: 45Hz-450Hz

Maximum Allowable Input: 750V rms

Response: Average Responding. Calibrated in rms of a Sine Wave.

CAT NO

DESCRIPTION

9300G Rugged High Quality DMM with Rubber Boot \$19.00

Switchable Scope Probe Sets

(Selectable X1/Ref/X10) These high quality scope probe sets are for oscilloscopes up to 60MHz (model HP9060) or 150MHz (model HP9150). Both sets include a handy storage pouch and include an IC test-hook adapter for the probe. The BNC connector rotates to avoid cable tangle or kink. Cable length is 1.4 meters.



CAT NO	DESCRIPTION	PRICE EACH
HP-9060	Scope Probe Set DC~60MHz	\$16.49
HP-9150	Scope Probe Set DC~150MHz	24.95

PRICE EACH

SEE OUR ON-LINE CATALOG AT

<http://www.cir.com>

Positive Photo Resist Pre-Sensitized Printed Circuit Boards



These pre-sensitized printed circuit boards are ideal for small production runs. They provide high resolution and excellent line width control. High sensitive positive resist coated on 1oz. copper foil allows you to go direct from your computer plot or art work layout. No need to reverse art.

Single-Sided, 1oz. Copper Foil on Paper Phenolic Substrate

CAT NO	DESCRIPTION	PRICE EACH
PP101	100mm x 150mm/3.91" x 5.91"	\$2.55
PP114	114mm x 185mm/4.6" x 6.6"	2.98
PP152	150mm x 250mm/5.91" x 9.84"	5.40
PP153	150mm x 300mm/5.91" x 11.81"	6.15

Single-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	PRICE EACH
GS101	100mm x 150mm/3.91" x 5.91"	\$3.90
GS114	114mm x 185mm/4.6" x 6.6"	4.80
GS152	150mm x 250mm/5.91" x 9.84"	8.69
GS153	150mm x 300mm/5.91" x 11.81"	10.20

Double-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	PRICE EACH
GD101	100mm x 150mm/3.91" x 5.91"	\$5.07
GD114	114mm x 185mm/4.6" x 6.6"	5.95
GD152	150mm x 250mm/5.91" x 9.84"	10.47
GD153	150mm x 300mm/5.91" x 11.81"	11.95

Etching Chemicals/Ferric Chloride

A dry concentrate that mixes with water to make 1 pint of etchant, enough to etch 400 sq. inches of 1oz board.

PRICE EACH

CAT NO	DESCRIPTION	PRICE EACH
ER-3	Makes 1 pint	\$3.50



Developer

This product is used as the developer on our positive photo-resist printed circuit boards. Includes instructions. 50 gram package, mixes with water.

PRICE EACH

CAT NO	DESCRIPTION	PRICE EACH
POSDEV	Positive Developer	\$.95



Etching Tank

This handy etching system will handle PC boards up to 8" x 9", two at a time. Ideal for etching your PCBs! System includes an air pump for etchant agitation, a thermostatically controlled heater for keeping etchant at optimum temperature and a tank that holds 1.35 gallons of etchant. A tight fitting lid is also supplied to prevent evaporation when system is not being used. Typical etching time is reduced to 4 minutes on 1oz. copper board!

REDUCES ETCHING TIME!

CAT NO	DESCRIPTION	PRICE EACH
12-700	Etch Tank System	\$37.95

Desoldering Pumps

These powerful plastic body desoldering pumps are designed for easy one hand operation for fast, efficient desoldering. Double O-ring piston seals for maximum suction.



PRICE EACH

CAT NO	DESCRIPTION	PRICE EACH
08-366S	Large Desoldering Pump	\$15.89
08-366E	Regular Desoldering Pump	10.89
08-366TIP	Replacement Tip	1.95

Electronic Soldering System Here's the ideal solution when Temperature Control is required. Easy to use slide control allows user to set system from 300°F to 840°F. Voltage to iron from control unit is 24V Iron heating power is 48W. Replaceable 5.3mm tip is standard. Replacement irons and tips are available.


CAT NO	DESCRIPTION	PRICE EACH
		1 5
SL10	Temp Controlled Soldering Iron	\$56.00 \$50.00
SL24V	Spare 24V Soldering Iron	10.50 7.50



Electronic Soldering System with LED Display

Deluxe temperature controlled system with LED display for maximum accuracy. Temperature is adjustable from 160°-480°C (320°-900°F). Iron heating power is 48 Watts. Runs on 24V from controller unit. Replacement irons and tips are available. Tip size is 5.3mm.


CAT NO	DESCRIPTION	PRICE EACH
		1 5
SL30	Deluxe Soldering System w/LED	\$86.00 \$75.00
SL24V	Spare 24V Soldering Iron for SL10 or SL30	AS LOW AS '75 10.50 7.50

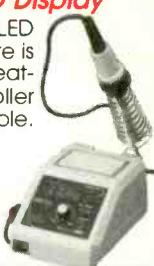

Replacement Tips for SL10/SL30 We now offer a variety of replacement tips for the SL10/SL30 soldering stations.

CAT NO	DESCRIPTION	PRICE EACH	CAT NO	DESCRIPTION	PRICE EACH
		1 5			1 5
821	1/32" Pencil Tip	\$1.39 \$1.19	825	1/8" Chisel Tip	\$1.49 \$1.29
822	1/32" Pencil Tip	1.39 1.19	826	3/64" Chisel Tip	1.49 1.29
823	1/64" Pencil Tip	1.39 1.19	827	3/64" Pencil Tip	1.59 1.39
824	1/16" Chisel Tip	1.49 1.29			

Ball Bearing 12V DC Fans

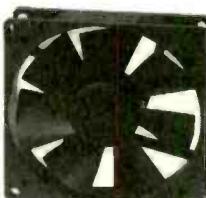

These High Quality Fans feature Ball Bearings and Brushless DC Motors. All of them are designed to meet UL, CSA & VDE Standards. Design these fans into power supplies, computers or other equipment requiring additional air flows for heat removal. These fans are regular Circuit Specialists stock items — they are not surplus.

INDUSTRY BEST PRICING!

Specifications

CAT NO	RATED DIMENSIONS (MM)	VOLTAGE (V)	START VOLTAGE (V)	INPUT CURRENT (A)	AIR FLOW (CFM)	STATIC PRESSURE (INCH-H ₂ O)	SPEED (RPM)	NOISE LEVEL (dB)	PRICE EACH	WEIGHT (g)
CSD 4010-12	40x40x10mm	12	7	0.06	5.1	0.19	5,500	26	\$ 9.88	4.87
CSD 6025-12	60x60x25mm	12	5	0.13	13.7	0.165	4,500	28	9.38	5.41
CSD 8025-12	80x80x25mm	12	5	0.16	37.8	0.177	3,000	31	8.88	5.19
CSD 9225-12	92x92x25mm	12	5	0.32	42	0.18	2,800	37	8.95	5.29
CSD 1225-12	120x120x25mm	12	5	0.35	62	0.180	2,500	42	11.45	7.82

- **SOLDER**
- **SOLDER**
- **SOLDER**
- **SOLDER**
- **SOLDER**
- **SOLDER**



Weststock high quality 60/40(Sn%Pb%), .031" and 63/37, .031" diameter. This is prime JIS certified solder that we maintain as a regular stock item (It is not "Left-overs, Rejects or Surplus") and you can buy it from us at a fraction of the price that you are used to.

Tired of Paying Inflated Prices for Solder?

CAT NO	DESCRIPTION	PRICE EACH
RH60-1	1-lb. Spool, .031", 60/40	\$ 6.90 \$ 5.96 \$ 5.30
RH63-1	1-lb. Spool, .031", 63/37	6.95 6.10 5.41
RH60-4	4.4-lb. Spool, .031", 60/40	24.00 21.90 17.92
RH60-TUBE	6-oz. Tube, .031", 60/40	.99 .89 .79

CCD Camera - IR Responsive

As Low As \$109!!

This black and white monochrome CCD Camera is totally contained on a PCB (70mm x 46mm). The lens is the tallest component on the board (27mm high from the back of the PCB) and it works with light as low as 0.1 lux. It is IR Responsive for use in total darkness. It comes with six IR LED's on board. It connects to any standard monitor, AUX or video input on a VCR or through a video modulator to a TV. Works with a REGULATED 12V power supply (11V-13V). Hooks up by connecting three wires: red to 12V, black to ground (power & video) and brown to video signal output.

CAT NO	DESCRIPTION	PRICE EACH
CA-H34A	PCB Mounted IRCCD Camera	\$125.00 \$109.00



!!!!!! SEE OUR ON-LINE CATALOG AT <http://www.cir.com> !!!!!!!

CIRCUIT SPECIALISTS, INC.
SINCE 1971

**800-811-5203
602-464-2485
602-464-5824(FAX)**

WE ACCEPT:



RECEIVE OUR LATEST 132 PAGE CATALOG!

It's chock full of all types of electronic equipment and supplies. We've got I.C.'s, capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call 800-811-5203, ext. 5, to leave a message on our catalog request line.



BRIGAR ELECTRONICS

7-9 ALICE ST.-BINGHAMTON, NY 13904

PHONE: (607) 723-3111
FAX: (607) 723-5202
E-MAIL: BRIGAR2@aol.com

SEND FOR
FREE
CATALOGUE



CREDIT CARD DISCOUNT
\$ 0.00 - \$ 99.99 NET
\$100.00 - \$249.99 LESS 10%
\$250.00 - \$499.99 LESS 15%
\$500.00 - \$999.99 LESS 20%
\$1000.00 AND UP LESS 25%

WE
PAY
MORE?

SERVING: ■ INDUSTRY ■ SCHOOLS ■ HOBBYISTS ■ EXPERIMENTORS ■ CONSUMERS

OPEN: MONDAY THRU FRIDAY 7:30AM TO 4:30 PM, SATURDAY 7:30AM TO NOON



PORTABLE FLUORESCENT - MINI LIGHT

Plug in anywhere - No Wiring - as bright as a 20-Watt Bulb.
 ■ Energy efficient fluorescent bulb costs only pennies a day.
 ■ Plugs into any standard outlet
 ■ Convenient ON/OFF switch
 ■ Completely portable -plugs into any standard outlet.
 ■ Lasts up to 3 years with normal use.
 ■ UL Listed. - 3.5watt - 120vac
 ■ Size: 5-1/4"Long x 1-1/4"H x 1-3/4"deep
 ■ Color: White
 Use at Home: kitchen, hallway, stairway, bedroom etc.
 Use away: RV, Boat, Motel room, Camp


BRAND NEW - DISPLAY PACKED.



SNAPIT
A LEVITON DIVISION

**SALE....
\$4.95 EA.**

ULTRASONIC LIGHT SWITCH MFG: LITRONIC
 REPLACES EXISTING WALL SWITCH - OPERATES FROM 120VAC POWER. GREAT FOR HOME ALARM SYSTEMS OR CONTROLLING LIGHTS & SMALL APPLIANCES - ADJUSTABLE TIME & SENSITIVITY, ON-OFF SWITCH - LED TRIP INDICATOR - COLOR: WHITE
SIZE: 5" W x 5" H X 1-3/8"D
 CAN BE USED WITH SINGLE OR DOUBLE SWITCHES.
 ON/AUTO SWITCH TURNS LIGHTS OFF MANUALLY WHEN NECESSARY OR LEAVES LIGHTS IN UTOMATIC CONTROL MODE.
 • VOLTAGE 120 OR 277VAC 50/60HZ
 • MIN LOAD 80 WATT 120V
 • MAX LOAD 1000W 120V
 SENSOR LOW POWER ULTRASONIC 25KHZ
 • SENSOR COVERAGE: 250 SQ. FT. WITH 180 DEG. DETECTION FIELD
 • ADJUSTMENT: SENSITIVITY & TIME OUT (10 TO 25 MINUTES)
 • DOCUMENTATION & SCHEMATIC INCLUDED.
 ENERGY SAVINGS 30 TO 60%
 ORIGINAL PRICE \$100.00
SPECIAL SALE PRICE
 \$12.95 EA.
 5 FOR \$60.00

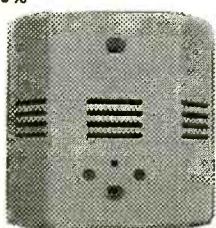

MOTION SENSING AUTOMATIC SWITCH

OPTREX #DMF5014NF-SEW INTELLIGENT GRAPHIC LCD MODULE "SUPERTWIST" Modules utilize surface mount technology. Displays Blue pixels on White background. Modules have E-L Backlighting - Graphic Figure Character Display. Unit comes complete with built in drivers & 8 bit tti interface.


• **CONTROL LSI T6963C TOSHIBA**
 • **VIEW ANGLE: 6.00 • DOT SIZE: .44(W) x .57(H) mm**
 • **DOT PIXELS 143(W) x 153(H) mm • VIEW AREA 74.8(W) x 98.4(H) mm**
 • **DC VOLTAGE: 5VDC • GRAPHIC, FIGURE & CHARACTER DISPLAY**
 • **HIGH CONTRAST & WIDE VIEW ANGLE • FILM TYPE BACKGROUND**

Using this information, one should be able to interface the LCD to any microcontroller or a microprocessor.

PROGRAM DISKETTES contains list of all commands, a file that contains list of initialization steps, and a text file that has the 68hc11 program

LIST PRICE... \$119.95

BRIGAR SPECIAL \$59.95

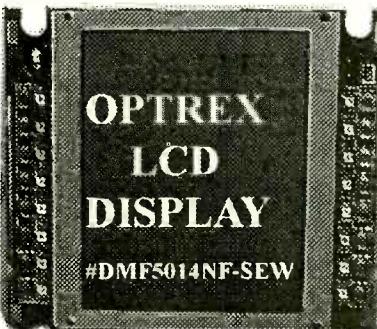

DISPLAYS COMES COMPLETE WITH 3.5"
DISKETTE. FILES CONTAIN 68HC11 PROGRAM, LIST OF COMMANDS AND Initialization steps, Schematic, and pin out



AEROVOX

P2066601YR
 1.9 UF @ 660V 50/60 HZ
 SIZE: 2-1/4" H x 2" W x 1" D
 PRICE..... .90 EA.



AEROVOX # N20R7001YR
 1.6 UF @ 700V 60HZ
 SIZE: 2-1/16" H x 2" W x 1" D
 PRICE.... \$1.00 EA.

COMPUTER PRODUCTS
POWER CONVERSION

5 - 9 WATT DC/DC CONVERTER
 PART # EM951S
 OUTPUT: ± 12 VDC ± 375 MA
 INPUT: 5 VOLT DC
 PC MOUNTABLE
 500V ISOLATION
 REGULATED LINE: 1.2%
 REGULATED LOAD: 8%
 REFLECTED RIPPLE: 75MA P-P
 Size: 2" square x .4" thick
 REGULAR PRICE ... \$20.00
 PRICE SLASHED \$4.95

CHICAGO MINIATURE LAMPS
 # CM385 - Base Style: midget flanged
 Brand New - Packed 100 pcs./card
 28 volts .04 amp - 50,000 life Hours
 Bulb style: T-1 3/4 - Same as 387 Lamps except has twice the life hours.
 Regular Price .. 60¢ ea.
BRIGAR SPECIAL
 SALE 20¢ EA.



AT LAST! DC-20 MHZ SYNTHESIZED PERFORMANCE FOR ONLY \$795!



- DC-20 MHz, .1 Hz resolution, DC offset
- Linear/Log Sweep
- Dualtone Generation
- Internal/External FSK
- Internal/External AM
- Burst
- Internal/External FM
- DTMF Generation
- Internal/External PM
- DTMF Detection
- Internal/External SSB
- Power Level Measmt
- Internal/External BPSK
- Power Level Measmt

Quantity 1
Made in U.S.A.
\$795

The SG-100 gives you .1 Hz synthesized precision and a wide diversity of modulation functions all of which can be performed using an internally generated or externally applied signal. You also get signal analysis functions that are just not offered on any other signal source such as DTMF Detection and Power Level Measurement. And because you can download new instrument functions to Flash memory, you can ensure that your SG-100 will never become obsolete.

The SG-100 is available NOW and is ready to turn your engineering bench into a real powerhouse!



C.O.D. P.O.
Telulex Inc.
2455 Old Middlefield Way S, Mountain View, Ca. 94043 (415) 938-0240
Fax: (415) 938-0241 http://www.telulex.com email:sales@telulex.com

The **Smallest, Most Secure, Best Range, 3 Channel**
Remote Receiver.



Security Receiver for... Home Automation, Garage Doors, Home Security Add On, Auto Convenience Package (Door Locks, Trunk Pop, Windows-Up/Down, Car Start), N/O or N/C Contacts.

Security - 70 billion hopping codes with anti-scan processing. Unbreachable security; never repeats the same code twice. Double EEPROM memory.

Incredible Range - No cross talk or blockage. Range up to 1000 feet.

3 Channel - Our universal receiver controls up to 3 items with only one receiver (optional relay needed). Push both buttons together for third channel output.

Interfaces with most home and auto security systems for easy remote integration. Comes with (1) three channel receiver, (1) long range three channel remote, (1) universal 120 VAC transformer.

ALL FOR ONLY \$99.95 + shipping & sales tax.

Street Smart Security
619) 462-1167

7147 University Avenue • La Mesa, CA 91941
Send, Fax or Call Order In - Use Credit Card or Check. Fax (619) 462-0652

❖ ATTENTION CABLE VIEWERS ❖ CABLE VIEWERS... get back to your **BASIC** Cable Needs



Call 800-577-8775

For information regarding all of your **BASIC** cable needs.

5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ **PRICE**
- ❖ **EFFICIENT SALES AND SERVICE**
- ❖ **WE SPECIALIZE IN 5, 10 LOT PRICING**
- ❖ **ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)**
- ❖ **ANY SIZE ORDER FILLED WITH SAME DAY SHIPPING**

We handle **NEW** equipment **ONLY** - Don't trust last year's **OBsolete** and **UNsold** stock!
COMPETITIVE PRICING—DEALERS WELCOME

HOURS: Monday-Saturday 9-5 C.S.T.


It is not the intent of B.E.S.W. to defraud any pay television operator and we will not assist any company or individual in doing the same.
Refer to sales personnel for specifications.

BASIC
ELECTRICAL
SUPPLY &
WAREHOUSING
CORPORATION

P.O. Box 8180 • Bartlett, IL 60103 • 800-577-8775


CIRCLE 334 ON FREE INFORMATION CARD

Miniature Transmitters and Receivers

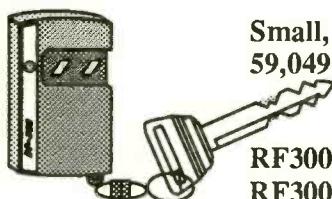


Small, Attractive, High End Quality, 2 Channel 318 MHz Transmitter
59,049 Settable Codes, 120'-300' Range, 1-1/4" x 2" x 9/16", Assembled

	Qty	1	5	10
RF300T 150' Range Transmitter		24.95	19.95	15.95
RF300XT 300' Range Transmitter		29.95	24.95	19.95

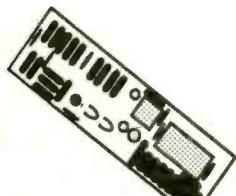

Small, High End Quality, 2 Channel Receiver for the RF300 Transmitters
1-1/4" x 3-3/4" x 9/16" PCB w/ .1" spaced pads for standard connectors
Input: 8-24 vdc Output: Gated CMOS Momentary and Latching Lines

	Qty	1	5	10
RF300R Receiver, Fully Assembled		24.95	20.95	16.95
RF300RK Receiver, Complete Parts Kit		19.95	15.95	12.95
RF300PA Pre-Amplifier. Doubles Range		14.95	11.95	9.95

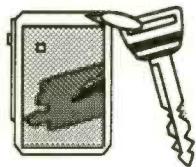

Small, Economical, Single Channel Transmitter and Receiver Set
Set Code, 60' Range, 1-7/8"x2-3/8"x7/16" (T), 2"x2-3/4"x9/16" (R)
Receiver Input: 5 vdc Output: Gated TTL Momentary Line

	Qty	1	5	10
RF60 Transmitter and Receiver Set		24.95	19.95	14.95

Add \$ 4 shipping for first item + \$ 1 for each additional item. Ca. residents add 8.25% tax
Visa, Mastercard, Money Orders Personal Checks and Cash C.O.D.s

Visitect Inc.

P.O. Box 14156 Fremont, CA. 94539 (510) 651-1425 Fax (510) 651-8454

CIRCLE 316 ON FREE INFORMATION CARD

WORLD'S SMALLEST UHF X-tal Locked Video Transmitters \$99.00

So small the transmitter, camera and battery will fit into a cigarette pack!!!

Used by hundreds in covert CCTV, R/C models, movie Special Effects, and Law Enforcement. "I've utilized your transmitters in covert video installations for about one year... previously, I used costly wireless units from Pelco, MVP, and Supercircuits. Nothing approaches the VidLinks in terms of power, picture quality, size, and value. Thank you."

R. Leslie, CCTV Installer, NY.

"Incredible color, resolution... easy to use, convenient. Very cool." P. Davis, Props, CA.
"... like having a TV station in your pocket."

J. Ramsay, Electronic Hobbyist, FL.

LIVE REMOTE VIDEO FROM: \$99.00

ACTUAL SIZE !!!

VidLink 100: 100mW Power- upto 1/4 Mile
\$199.00 New! High-Powered

VidLink 15: 15mW Power- upto 150 Feet
\$99.00 New! Low Price- Same Size!

Covert Camera: 1 1/4" sq. Pinhole Lens
\$169.00 Pro Grade Japanese Quality!

*** Audio Module Now Available. Call. ***

Check/MO, COD +\$5.00, S&H \$5.50



AEGIS
RESEARCH

#671-1225 E. Sunset Dr.
Bellingham, WA
98226-3529 USA

1-604-224-0416

Visit our virtual catalog on the INTERNET at:

<http://www.lynx.bc.ca/virtualspy>

WE SELL RED, BLUE-GREEN & IR

LASERS

HUNDREDS OF UNITS TO CHOOSE FROM!
PRICES AS LOW AS \$40.00!

- ★ Experiments
- ★ Laser Light Shows
- ★ Cutting & Burning
- ★ Communications

We also carry
books and plans
about LASERS.

CALL FOR FREE CATALOG!
TEL (909) 278-0563
FAX (909) 278-4887

MWK INDUSTRIES

1269 W. Pomona, Corona, California 91720

See our catalog on the internet.

<HTTP://WWW.PWEB.COM/MWK/MAIN.HTM>

EMAIL: MKENNY1989@AOL.COM

DALBANI




CALL TOLL FREE
1-800-325-2264

\$20 MINIMUM ORDER
CALL NOW FOR YOUR
232 PAGE FREE CATALOG
1-800-325-2264

HOT PRICES ON POPULAR SEMI'S

Order No.	Brand	Min.	Price
BU-208	TESLA	10	\$1.49
BU-208/O	TOSHIBA	1	4.50
2N-3055	TESLA	10	0.60
2N-3773	TESLA	5	1.20
2SD-1398	SANYO	10	1.49
2SD-1650	SANYO	5	1.69
STRD-1005	SANKEN	1	4.15
STR-30130	SANKEN	1	2.66
STRS-6301	SANKEN	1	8.50
TA-7777N	TOSHIBA	1	6.96
TTA-2005	SGS	5	1.49

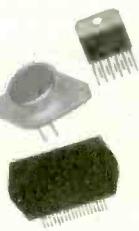

COLOR CODED LEADS HEAVY DUTY

ORDER NO 56-500

- 11" Long Wire Lead
- Insulated 1 1/2" Alligator Clips
- 20 Gauge Wire Size • 10 Leads
- BLACK, GREEN, RED, YELLOW, WHITE

SOLDER WICK

- Solder Remover
- Length 5 Feet

ORDER NO 51-1050



TEMPERATURE CONTROLLED SOLDERING STATION

- Adjustable Temp.: 300°F - 790°F - 150°C - 480°C
- Grounded Tip for Soldering :
- Static Sensitive Devices, Heater Aid.
- Led Power Temperature Indicator
- Overheat Protection W/ Temperature Control
- Auxiliary Grounded Terminal
- Comes in digital LED display
- 48 Watts soldering iron

ORDER NO 51-1035



CODE EN96

PLEASE MENTION WHEN ORDERING

Items are subject to availability.
Prices are subject to change without any prior notice.

FLYBACK TRANSFORMERS



\$12.50
Replaces
GOLDSTAR 154-074R
ORDER NO 63-0189

TUN-O-WASH®
ORDER NO 30-0100

\$7.50
(CFC Free)

Fast drying electronics grade cleaner for tuners, controls and PC boards.

TUN-O-WASH is excellent cleaner and degreaser for tuners, controllers and PC boards.
• Designed for cleaning and degreasing consumer electronics • Cleans in one step, no rinsing required • Contains no ozone depleting compounds • CFC and HCFC free
• Not for use on energized equipment
• 12.5 Oz aerosol (12 cans per case)



VCR ALIGNMENT TOOL KIT

ORDER # 50-888

The most popular

- VCR Head puller
- Retaining ring remover
- Spring hook
- Micro screwdriver
- Hex key set • Fitted vinyl • Soft zippered case
- Dimensions: 9 1/2"(W) X 12 1/4"(L)
- 7 Assorted head & guide aligners
- 3 Reversible screwdrivers (Small-Flat-Philips)



UNIQUE REALTIME OSCILLOSCOPE BUILT-IN FUNCTION GENERATOR

Order N° 50-820



1 MHZ FUNCTION GENERATOR

Features

- Wider than specified frequency response • High deflection factor of 1mV/div. • Wide dynamic range up to 30MHz without waveform distortion • Algebraic sum of CH1 and CH2 • Low drift with compensation circuit • Superb trigger sensitivity • Maximum sweep rate of video signals with internal TV sync. separator • Jitterless trigger circuitry • CH1 signal output terminal available • Variable trigger hold-off • High precision X-Y phase difference measurement up to 50kHz • Built-in function generator with BNC output of 50Ω and TTL • Three kinds of waveform are available with 50Ω output • Flat output waveform frequency up to 1MHz

Specifications:

Vertical deflection: • Bandwidth :DC coupled (DC to 20MHz normal), AC coupled :(10Hz to 20MHz normal) • Deflection factor: 5mV/div to 5V/div in 10 calibrated steps of 1-2-5 sequence • Rise time: 17.5nS or less

Horizontal deflection: • Time Base A: 0.2μs to 0.2S/div in 19 calibrated steps.1-2-5 sequence • Uncalibrated continuous control between steps of at least 1: 2.5.



Manuf # OS-9020G

20MHz 2-CH DUAL TRACE

DIGITAL MULTIMETERS NEW! Digital

DALCO

- Overload protect 1000VDC or peak AC on all other ranges
- Input impedance 10M Ohm on all ranges • Base accuracy range ± 0.5 % to ± 1.0 % • Resistance 200Ω, 2K, 20K, 200K, 2M, 20M
- Audible continuity response lower than 50Ω • DC Voltage 200mV, 2V, 20V, 200V, 1000V AC Voltage 200mV, 2V, 20V, 200V, 700V

ORDER NO 50-815



LOGIC Probe

ORDER NO 51-1015

- Length: 8 inches
- Range: 4.5 To 15 VDC
- Includes Test Leads • Compatible With TTL,DTL,RTL,HTL,CMOS, NMOS Logic



SOLDER ROLL

- 1 LB Spool
- 370 deg F melting point
- Fastest solder
- Alloy 60/40, tin lead, non corrosive flux, Diam. 1.2mm

ORDER NO 51-1005

Universal Audio/video Remote

ORDER NO 82-1055

- Controls basic functions of TV, VCR, cable box, and CD or laser player • Ergonomic design! Main buttons are in line with natural thumb motion • Two-minute memory allows time to replace batteries without reprogramming • Programming reminder sticker inside battery compartment • Sleep time for 60, 30, or 15 minutes(according to your TV) • Set key recessed to prevent accidental deprogramming • Spanish instruction included • Requires four AAA Batteries (not included)

MAGNAVOX

Smart. Very smart

\$9.95

- Cable (11 brands)
- VCR (68 brands)
- TV (77 brands)
- Compact disc and Laser Disc (94 brands)





4225 N.W. 72nd AVE MIAMI, FLORIDA 33166 TEL : (305) 716-1016 FAX : (305) 594-6588

CIRCLE 234 ON FREE INFORMATION CARD

Tel: (954) 974-6864
Fax: (954) 974-6818

Gateway Products Corp.

Please mail orders to:
P. O. Box: 93-6397
Margate, FL 33093

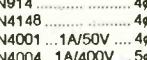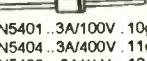Popular I.C.s  LM324 ... 45¢ LM338 ... 45¢ LM358 ... 45¢ NE555 ... 40¢ LM556 ... 50¢ LM741 ... 40¢ Deal U3: 12 pcs total, (2pcs of each)... \$5.00	Transistors  PN2222A ... 8¢ PN2907A ... 8¢ 2N3904 ... 8¢ 2N3906 ... 8¢ 2N4001 ... 8¢ 2N4003 ... 8¢ Deal N8: 60 pcs total, (10pcs of ea)... \$4.50	Semiconductors  74LS174 ... 40¢ 74LS244 ... 45¢ 74LS245 ... 45¢ 74LS374 ... 45¢ LM386N ... 45¢ LM393N ... 40¢ MC1488 ... 45¢ MC1489 ... 45¢ Deal P7: 50 pcs total, (10pcs of ea)... \$2.00	DIODES  1N914 ... 4¢ 1N4148 ... 4¢ 1N4001 ... 1A/50V ... 4¢ 1N4004 ... 1A/400V ... 5¢ 1N4007 ... 1A/1KV ... 6¢ Deal A2: 40 pcs total, (5pcs of each)... \$3.00	RADIAL LYTICS  1UF/50V ... 8¢ 2.2uF/50V ... 8¢ 4.7uF/50V ... 8¢ 10uF/50V ... 9¢ 22uF/50V ... 10¢ 33uF/50V ... 11¢ 100pF ... 7¢ 150pF ... 7¢ 220pF ... 7¢ Deal R4: 40 pcs total, (5pcs of each)... \$2.50	Ceramic Disc  (All caps rated 50V) 10pF ... 7¢ 22pF ... 7¢ 27pF ... 7¢ 33pF ... 7¢ 47pF ... 7¢ 100pF ... 7¢ 150pF ... 7¢ 220pF ... 7¢ Deal S3: 8 pcs total, (2pcs of each)... \$5.00	Toggle Switches  Miniature size 1/4" Panel hole
Popular CMOS  CD4001B ... 30¢ CD4011B ... 30¢ CD4013B ... 40¢ CD4017B ... 50¢ CD4028B ... 40¢ CD4050B ... 40¢ CD4066B ... 40¢ CD4069B ... 40¢ Deal V8: 16 pcs total, (2pcs of each)... \$5.00	More Transistors  MPSA05 ... 49¢ MPSA13 ... 15¢ MPSA27 ... 15¢ MPSA42 ... 15¢ MPSA56 ... 15¢ MPSA92 ... 15¢ Deal Q2: 30 pcs total, (5pcs of ea)... \$4.00	V. Regulators  LM317T ... 69¢ 7805 ... 49¢ 7808 ... 49¢ 7812 ... 49¢ 7815 ... 49¢ 7818 ... 49¢ 7824 ... 49¢ 7905 ... 49¢ 7908 ... 49¢ 7912 ... 49¢ 7915 ... 49¢ 7805 ... 39¢ 7805 ... 39¢ 7812 ... 39¢ Deal H8: 25 pcs total, (5pcs of ea)... \$4.00	Power Diodes  1N5401 ... 3A/100V ... 10¢ 1N5404 ... 3A/400V ... 11¢ 1N5408 ... 3A/1KV ... 12¢ 6A10 ... 6A/100V ... 32¢ 6A100 ... 6A/1KV ... 42¢ Deal A7: 40 pcs total, (5pcs of each)... \$4.00	RADIAL LYTICS  10uF/25V ... 8¢ 22uF/25V ... 8¢ 33uF/25V ... 8¢ 47uF/25V ... 9¢ 100uF/25V ... 10¢ 220uF/25V ... 12¢ 330uF/25V ... 19¢ 470uF/25V ... 23¢ Deal R7: 40 pcs total, (5pcs of each)... \$2.50	Ceramic Disc  (All caps rated 50V) 270pF ... 7¢ 330pF ... 7¢ 470pF ... 7¢ 001uF ... 7¢ 01uF ... 7¢ 022uF ... 7¢ 047uF ... 9¢ 1uF ... 10¢ Deal X8: 6 pcs total, (2pcs of each)... \$3.00	DEAL W2 ... \$2.50
DEAL M3 ... \$5.00 7805 7812 7905 7912 12 pcs total (3pcs of each)	More Transistors  2N2222A ... 30¢ 2N4124 ... 11¢ 2N4126 ... 11¢ 2N5401 ... 14¢ MPSH10 ... 13¢ 2N3055 ... 69¢ TIP31C ... 55¢ TIP32C ... 55¢ TIP117 ... 55¢ TIP120 ... 60¢ TIP125 ... 65¢ Deal L8: 30 pcs total, (10pcs of ea)... \$2.50	Crystals ... 99¢ ea  3.5795MHz, 4.000MHz 11.0MHz, 11.0592MHz	1W Zener Diodes  1N4728A ... 3.3V ... 10¢ 1N4733A ... 5.1V ... 10¢ 1N4739A ... 9.1V ... 10¢ 1N4742A ... 12V ... 10¢ 1N4744A ... 15V ... 10¢ 1N4746A ... 18V ... 10¢ Deal Z5: 30 pcs total, (5pcs of ea)... \$2.50	1A SCHOTTKY  1N5817 ... 1A/20V ... 22¢ 1N5818 ... 1A/30V ... 23¢ 1N5819 ... 1A/40V ... 24¢ Deal Y6: 9 pcs total, (3pcs of each)... \$2.00	Mono Caps ... 9¢ ea  .01uF/50V ... 47uF/50V 022uF/50V ... 1uF/50V Deal B5: 40 pcs total, (10pcs of ea)... \$2.50	DEAL W5 ... \$2.50
DEAL J1 ... \$3.50 78L05 78L12 10 pcs total (5pcs of each)	CHEAP STUFF  TO-220 heat sink ... 29¢ Mini push-button ... 29¢ 30W solder iron ... \$3.95 6ft printer cable ... 3.95¢ 6ft VGA cable ... 3.95¢ 3-b serial mouse ... 8.95¢ Deal G5: 18 pcs total, (6pcs of ea)... \$2.50	Germanium Diodes  1N34A ... 15¢ 1N60 ... 15¢ 1N270 ... 30¢ Deal Y8: 9 pcs total, (3pcs of each)... \$3.00	3A SCHOTTKY  1N5820 ... 3A/20V ... 32¢ 1N5821 ... 3A/30V ... 36¢ 1N5822 ... 3A/40V ... 39¢ Deal T6: 15 pcs total, (5pcs of each)... \$3.50	Tantalum Caps  1uF/35V ... 18¢ 2.2uF/35V ... 22¢ 10uF/35V ... 49¢ Deal R1: 15 pcs total, (5pcs of each)... \$3.50	SOLDER ROLL  SN63/37 .031" dia 1 Lb Roll \$7.80	

\$10.00 minimum order. We accept VISA, MC, MO, Check, No-CODs. Please add \$5.00 for shipping & handling (foreign addresses: \$8.50). Florida addresses add your applicable county sales tax. Hours: Mon-Fri: 9AM to 5PM (EST). All new premium parts. Send for free Catalog.

CIRCLE 330 ON FREE INFORMATION CARD

The Hacker's Companion CD-ROM

Want a war-dialer program or something to crack a password? Do you want to learn how the phone company gets ripped off, or learn how to build a red box, or modify a cellular phone? Want to see what the security holes in a VAX are? Or how to compromise a Unix machine or a BBS? Want to learn how to use the system in ways you never imagined possible? This CD is the place to look! It contains all kinds of computer, telephone and general hacking information. Even a video of dutch hackers breaking into a classified US military computer! In all, 552 megabytes of fascinating information that's hard to get anywhere else!

PC-Compatible CD-ROM \$49.95

Shipping \$3

Call (800)719-4957 now!

to order (Visa/MC/COD) or call or write for **FREE CATALOG** of hard-to-get information about computer viruses, computer hacking, security and cryptography!!

American Eagle Publications, Inc.
P. O Box 1507
Show Low, AZ 85901

CIRCLE 315 ON FREE INFORMATION CARD

Electronic Engineering Works 5.1



1 ANALOG CIRCUIT SIMULATOR

Fastest Simulator on the market. Active & Passive circuits. Up to 70 nodes, 225 elements. Programmable Models for active devices. 10 Programmable Input Transients. Edit circuits. Calc, Plot and Print AC voltages, AC currents, DC current, DC voltage, DC Sweep, Input and Output transients, power Plots: Lin, Log, Semi, Polar, etc.

2 ANALOG SIMULATOR W/DRAW

3 ACTIVE FILTERS DESIGN

Design/Analyze active LPF, BPF, HPF, Butterworth, Chebyshev, Bessel & All pass filters. Plot response.

4 TRANSIENT SYSTEM ANALYSIS

Calc, plot transient response of system H(s). 14 Input Transients, Inverse Laplace. Edit H(s). More

5 POLYNOMIAL OPERATIONS

Calc polynomials Roots, Product & Coefficients.

11 POWER SUPPLY DESIGN AND ANALYSIS

Design and analyze switching and linear supplies. Design AC/DC and DC/DC Converters. Design Power Transformers, with up to 50 windings. Design Power Inductors and Current Transformers. Switchers include Buck, Boost, Buck-Boost, Flyback. Perform Stability Analysis of Switchers. Design LC Filters. Includes Mag Core Tables, Gain/Phase Plots & Data. VGA req.

12 DIGITAL LOGIC SIMULATOR WITH DRAW

★ ANALOG CIRCUIT SIMULATOR (module 1) ... \$ 69 **Performance Guarantee**

★ ANALOG SIMULATOR W/ DRAW (modules 1,2) ... \$ 89 **PC AT 340K BASE**

★ EE WORKS 5.1 STD (modules 1,2,3,10,12) ... \$129 **MEM 64M VGA COLOR**

DISP WITH 260K VIDEO **DISP WITH 260K VIDEO**

★ EE WORKS 5.1 PRO (all 12 modules) ... \$295 **HIGHER MS MOUSE**

DRIVE, LASER OR DOT MATRIX PRINTER **DRIVE, LASER OR DOT MATRIX PRINTER**

FAST, ACCURATE & THOROUGH

GEOBAN ENGINEERING, PO BOX 658, RIDGECREST CA 93556

PROFESSIONAL DESOLDERING with the

Lane Norman - Normans Electronics Inc. Atlanta GA 404-451-5057
A cost effective solution to desoldering equipment at less than half the price of most equipment. It's performance is ASTOUNDING.

Harold Smedberg - Smedberg Electronics - Custer MI
The SC7000 has reduced my damage to PC boards by 90%. It has also decreased my desoldering time by 50%. The best priced tool on the market.

Mike Murphy - Service Center - Van Nuys CA 818-785-7805
The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

DEN-ON SC7000

Bob Monroe - M.A.R.C. Electronics - Virginia Beach VA 804-468-3932
Best investment we've made. Saves time, especially with multi-sided PCB's. Extremely pleased with warranty. Failed within 6 months and replaced by DEN-ON overnight.

Dick Manning - Dicks Electronics - Hartland WI 414-367-8339
The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

Dave Hayes - E-H Engineering Ltd - Lincoln NE 402-466-6720
Has been a durable & reliable desoldering unit. Our use has been both lab & field application over the last 2 yrs. with positive results.

Bob Sorrels CET/CSM Polytronics Microcomputer - Shreveport LA
We've used our SC7000 almost every day for about three years with virtually no problems. Just clean it before you turn it off for the day.

George Hefner - Hefner Electronics - Coleridge NE 402-283-4333
Being a one-men service center, I hesitated to spend the money on a desoldering tool, however all that changed when I nearly ruined a \$400 computer logic board. It has cut my desoldering time by 50 to 75%.

Steven Gray - Electronic Wizards - Wichita KS 316-686-8324
By far the best desoldering tool we've ever used. Much more suction than other similar types we've tried. No trouble with postage stamp IC's or anything else.

Dennis McMannis - Thorn Services International - Mabelton GA
The SC7000 has decreased my use of wick by 75% and at \$25 a roll, it pays for itself within months. My total bench time is reduced by approx. 20%.

Don Cressin - Certified Electronics Service - Ellicott City MD 301-461-8008
We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

Doug Pettit - LuRay Electronics - LuRay VA 703-743-5400
We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

Paul Horvat - Service Excellence Inc. - Bergenfield NJ 201-387-7776
It has made a almost impossible job (desoldering a 64 pin CPU) a piece of cake.

Specifications

- Totally Self Contained diaphragm vacuum pump and AC motor for high vacuum suction or reversible hot air blow for SMD removal.
- 100Watt Ceramic heater with zero-crossover switching heater control circuit which prevents spikes and leakage currents.
- Unique patented long lasting filter cartridge design. Solder builds up on easily cleaned baffle, while air flows around the outside of baffle.
- Totally ESD Safe. The housing contains carbon and the tip is at ground potential for complete ESD Protection.
- Maximum vacuum of 600mmHg is attained in 0.2 seconds.
- Temperature adjustable from 300°C - 450°C or 572°F - 842°F

Visa - M/C - Discover - American Express - Terms to Qualifying Companies
30 Day Money Back Total Satisfaction Guarantee - One Year Parts and Labor Warranty

HOWARD
HEI
LECTRONIC
INSTRUMENTS
6222 N. Oliver Wichita, KS 67220 INC

Toll Free U.S. and Canada

1-800-394-1984

E-Mail sales@heinc.com


Web Site www.heinc.com

International (316) 744-1993
or Fax (316) 744-1994


CIRCLE 323 ON FREE INFORMATION CARD

\$449⁹⁵

Device Programmers

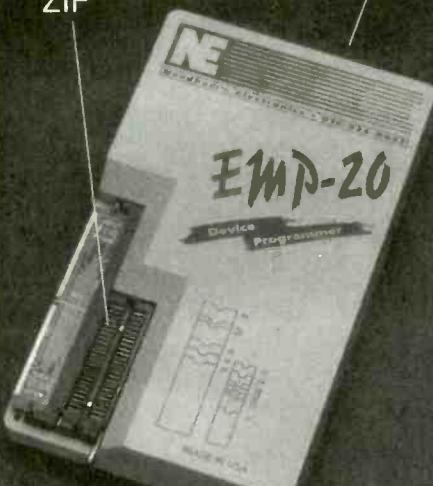\$139⁹⁵**48 PIN
ZIF**Connects to standard
PC parallel printer port9^{1/2} x 5^{3/4} x 1^{1/4}**EMP-20**

- Easy to use software, on-line help, full screen editor
- **Fast Programming** (EMP-20)
27C010A, 23 seconds
28C020, 34 seconds
27C040, 95 seconds
- **Made in USA**
- 1 Year Warranty
- Technical Support by phone
- 30 day Money Back Guarantee
- FREE software upgrades available via BBS
- Demo SW via BBS (EM20DEMO.EXE) (PB10DEMO.EXE)
- E(e)proms 2716 - 8 megabit, 16 bit 27210-27240, 27C400 & 27C800,
- Flash 28F256-28F020, (29C256-29C010 (EMP-20 only))
- Micros 8741A, 42A, 42AH, 48, 49, 48H, 49H, 55, 87C51, 87C51FX, 87C751, 752
- GAL, PLD from NS, Lattice, AMD-16V8, 20V8, 22V10 (EMP-20 only)

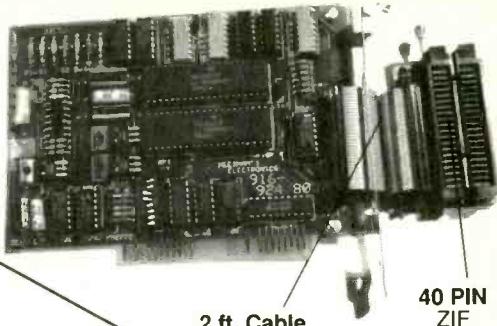PB-10 Internal Card for PC

4630 Beloit Drive, Suite 20
Sacramento, CA 95838
(Monday-Friday, 8 am-5 pm PST)

NEEDHAM'S ELECTRONICS, INC.

C.O.D.

**(916) 924-8037****BBS 916-924-8094****FAX 916-924-8065**

CIRCLE 257 ON FREE INFORMATION CARD

Mark V Electronics, Inc.
8019 E Slauson Ave
Montebello CA 90640
Free Catalog 213/ 888-8988
Fax 213/ 888-6868

Kit: \$ 89.80
Asmb.: \$ 114.80

- Low distortion, stability & superb transient response.
- 2 pairs MOSFET transistors.
- Highly sensitive & fool-proof.
- Loudspeaker protection circuit.

120-250W MOSFET Power Mono Amp. # AF-2

Kit: \$ 64.00
Asmb.: \$ 80.00

- Field effect transistors.
- Symmetry circuit.
- Wide frequency response & low distortion.
- Power supply regulation.
- Time delay relay. # TA-388

Class A FET Dynamic Buffer Stereo Pre-Amp

It is short circuit proof & has overload protection. Output voltage is variable over a range of 0-50V. Current limit trip is adjustable up to max of 3A.

Regulated DC Power Supply # TR-503

School Project Kits Source...

SM-36	Dynamic Noise Reduction	\$ 26.00
SM-720	AC/DC Stereo Pre & Main Amp	77.00
TA-006	6W Mini-Amplifier	9.50
TA-120	36W Class A Power Amp	32.50
TA-201	Microphone Mixer Mono Amp	20.79
TY-45	20 Bar/Dot Level Display	38.25
TA-28	Digital Voice Memo kit	\$ 9.90
TY-35	FM Wireless Microphone kit	6.99

Clearance Sale...

TA-28 Digital Voice Memo kit

TY-35 FM Wireless Microphone kit

Do-It-Yourself Audio Amplifier & Electronic Kits more than 60 items available!

ORDER 1-800-521-MARK / 1-800-423-FIVE

- Input program source switching.
- Phono pre-amp stage with RIAA equalization. Kit: \$ 64.00 Asmb.: \$ 80.00
- 3 tone controls. Asmb.: \$ 80.00
- Built-in speaker protection circuit & power supply rectifier.

120Wx2 Pre & Main Stereo Amp. # TA-800MK2

- Accurate & easy to operate. Kit: \$ 79.00 Asmb.: \$ 99.00
- Frequency 10Hz-150MHz.
- Hold function available.
- AD/LSI circuitry.
- Input impedance 1M ohm.
- For adjustment, test & repair...

150MHz 8 Digit Frequency Counter # SM-100

- Super fast acting relay protects speaker against destructive DC voltage. Can connect directly to a power amp. or can use a separate power supply. Has a 3 sec turn-on delay to avoid turn-on thumps.

Stereo Loudspeaker Protector # TY-25

- This unit provides 3 input jacks pairs. One pair accept a high impedance microphone. The two remaining pairs are for high & low level input sources.

The unit is ready to plug into the AC power when assembled. Case & transformer are included.

60W+60W Stereo Power Amp # SM-302**METAL CABINETS**

Aluminium Front Panel

LG-1273	3x12x6 ^{1/4} "	\$ 26.50
LG-1684	4x16x8"	32.50
LG-1924	4x19x11 ^{1/2} "	38.25
LG-1925	5x19x11 ^{1/2} "	42.00
LG-1983	2 ^{1/2} x19x8"	35.25
LG-1923	3x19x11 ^{1/2} "	36.50
LG-1927	7x19x11 ^{1/2} "	50.50
LG-	Black anodized rack cabinet	

Best Buy

New

New

LL-1923B 2^{1/2}x19x12" \$ 69.50

LL-1925A 5x19x12" 79.50

*LL-Full Aluminum, Front .157" & other .078"

**LL-Gold plated cap screw for front panel

LB-1085 8^{1/4}x10^{1/4}x5" \$ 18.75LB-1395 9^{1/4}x13^{1/4}x5" 25.50LB-1525 12^{1/4}x15^{1/4}x5" 35.25*LB-1494 9^{1/4}x14^{1/4}x4^{1/4}" 21.50LB-1383A 8^{1/4}x13^{1/4}x4" 23.25

*No lock & LB-Sheet Metal 0.8mm

Alarm Box with LockLB-1085 8^{1/4}x10^{1/4}x5" \$ 18.75LB-1395 9^{1/4}x13^{1/4}x5" 25.50LB-1525 12^{1/4}x15^{1/4}x5" 35.25*LB-1494 9^{1/4}x14^{1/4}x4^{1/4}" 21.50LB-1383A 8^{1/4}x13^{1/4}x4" 23.25

*No lock & LB-Sheet Metal 0.8mm

Camera Housing*LD-1244 2^{1/2}x10^{1/4}x4" \$ 55.00**LD-1516 3^{1/2}x13^{1/4}x4" 29.50***LD-1565 4x13x5^{1/4}" 31.75

*LD-Stainless Steel 0.7mm

**LD-Sheet Metal 1mm

#001 28/30Vx2 6A \$ 30.00

#002 36Vx2 3A 25.00

#003 40Vx2 6A 32.00

#004 24Vx2 6A 25.00

#005 26Vx2 3A 19.00

#006 18Vx2 5A 19.00

#007 53Vx2 8A 47.00

#008*28/30Vx2 6A 40.00

#009*48/53Vx2 8A 66.00

#012*33/42Vx2 6A 48.00

#013*33/42Vx2 6A 48.00

#014*33/42Vx2 6A 48.00

#099*33/42Vx2 6A 48.00

#100*33/42Vx2 6A 48.00

#101*33/42Vx2 6A 48.00

#102*33/42Vx2 6A 48.00

#103*33/42Vx2 6A 48.00

#104*33/42Vx2 6A 48.00

#105*33/42Vx2 6A 48.00

#106*33/42Vx2 6A 48.00

#107*33/42Vx2 6A 48.00

#108*33/42Vx2 6A 48.00

#109*33/42Vx2 6A 48.00

#110*33/42Vx2 6A 48.00

#111*33/42Vx2 6A 48.00

#112*33/42Vx2 6A 48.00

#113*33/42Vx2 6A 48.00

#114*33/42Vx2 6A 48.00

#115*33/42Vx2 6A 48.00

#116*33/42Vx2 6A 48.00

#117*33/42Vx2 6A 48.00

#118*33/42Vx2 6A 48.00

#119*33/42Vx2 6A 48.00

#120*33/42Vx2 6A 48.00

#121*33/42Vx2 6A 48.00

#122*33/42Vx2 6A 48.00

#123*33/42Vx2 6A 48.00

#124*33/42Vx2 6A 48.00

#125*33/42Vx2 6A 48.00

#126*33/42Vx2 6A 48.00

#127*33/42Vx2 6A 48.00

#128*33/42Vx2 6A 48.00

#129*33/42Vx2 6A 48.00

#130*33/42Vx2 6A 48.00

#131*33/42Vx2 6A 48.00


#132*33/42Vx2 6A 48.00

#133*33/42Vx2 6A 48.00
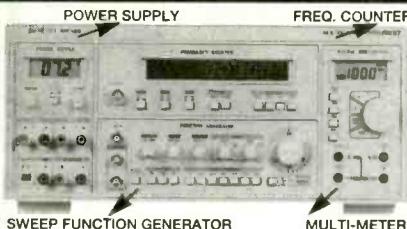
#134*33/42Vx2 6A 48.

Unbeatable Discount Prices

1 YEAR WARRANTY
15 DAY MONEY BACK GUARANTEE



SWEEP FUNCTION GENERATOR

MULTI-METER


MT-100

Reg. \$599.

\$419.00

FG-140 2MHz Function Generator

Reg. \$249. **\$149.00**

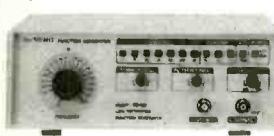

- 0.2 Hz ~ 2.0 MHz, 7 Decades
- Sine, Square, Triangle, Pulse, Ramp, Skewed Sine
- VCF, Symmetry
- Variable DC Offset Control

Oscilloscope Probe Set

Switch Selectable X1/X10



- HP-9060, 60MHz Reg. \$29. **\$17.00**
HP-9150, 150MHz Reg. \$49. **\$27.00**
HP-9250, 250MHz Reg. \$59. **\$37.00**

2MHz Sweep Function Gen. w/Freq. Counter

Reg. \$399. **\$229.00**



Four Instruments in One Instrument

1 Function Generator

- Sine, Square, Triangle, Pulse, Skewed Sine, Ramp, TTL
- 0.2 Hz ~ 2MHz

2 Frequency Counter

- 8 Digit LED
- 1 Hz ~ 100MHz
- ± (1 Hz + 1 digit. + Time Base Error)

3 Power Supply

- 3-1/2 Digit LCD
- Triple output: #1. 0-50V, 0.5A MAX
- #2, 15V, 1A #3. 5V, 2A

4 Digital Multimeter

- 3-1/2 Digit LCD
- DCV, ACV, Ω, DCA, ACA
- ± (0.5% + 2 digits)

1.0GHz Frequency Counter, High Resolution

Reg. \$399. **\$219.00**



FC-200

Reg. \$399. **\$219.00**

- 1.0 Hz ~ 1.0 GHz
- 8 Digit LED Display
- Auto & Manual Range
- 4 Selectable Gate Times
- 1MΩ & 50Ω Input Impedance

PS-540 DC Power Supply


Reg. \$399. **\$249.00**



- 0-16 VDC
- 0.1 ~ 10A
- Short & Overload Protection

Deluxe O'scopes w/Phillips CRT.

OS-3304 Reg. \$499. **\$349.00**

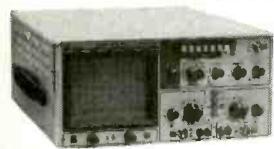

OS-3324 Reg. \$599. **\$429.00**



OS-3344 Reg. \$899. **\$649.00**



OS-3304 25MHz, Dual Trace

- 1 • DC to 25 MHz. Dual Channel
• 6" Rectangular CRT with Internal Graticule 10x8cm (Philips P31)
• Uncalibration LED.
• High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
• Rise time 14n Sec. or less.
• Full TV Trigger for TV-V & TV-H
• Acceleration Potential 2kV
• 60MHz (X1.X10) Probe Kit: 2 sets
• Power: 115/230V AC

OS-3324, 3 Function

- 1 • OS-3304
2 • Dual Component Tester/Comparator

- 3 • Triple DC Power Supply 5VDC, +12 VDC, -12VDC

OS-3344, 5 Function

- 1 + 2 + 3 • OS-3324
4 • Frequency Counter 100MHz, 7 Digit LED Display
5 • Function Generator 0.02 Hz to 2.0 MHz

"BEST BUY!"

OS-3315

40MHz, Dual Trace Sweep Delayed

Reg. \$799. **\$549.00**



- DC to 40 MHz. Dual Channel
- Delayed Sweep 100nS to 1.0S 7 decade
- 6" Rectangular CRT with Internal Graticule 10x8cm (Philips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
- Rise time 8.5nS or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 12kV
- Variable Hold Off
- 16ns ~ 1.0s Time Base
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

Bel MERIT

DM5050C DM5100

Reg. \$149. **\$89.00**

Including
Deluxe
Holster



Digital Engine Analyzer

Reg. \$119. **\$69.00**



DM230

- 3 1/2 Digit LCD
- Engine Analyzer
- Taco, Dwell, Duty Cycle
- DMM
- DCV, DCA, Ω
- Temperature 0 ~ 1.999°F
- Diode
- Continuity
- Holster, Temp. Probe, Clip Leads

Capacitance Meter

Reg. \$79. **\$49.00**



CM210

- 3 1/2 Digit LCD
- 0.1p-20,000μF 9 Ranges
- 0.5% basic Accu.
- Zero Adjust Knob
- Test Leads & Built in Socket

Pen-Type DMM w/Logic

Reg. \$79. **\$59.00**



DM150

- 3 1/2 Digit
- Dual Display
- Auto & Manual
- DCV, ACV, ACA, DCA, Ω
- Logic CMOS/TTL
- Data Hold
- Diode
- Continuity
- Deluxe Holster

Multifunction DMM

Reg. \$99. **\$64.00**



DM4050

- 3 1/2 Digit
- Basic Accuracy: 0.25%
- Heavy Duty, 20A AC/DC Resistance 20MΩ
- Capacitance
- Freq. up to 20MHz
- TR-hFE
- Data Hold
- Diode
- Continuity
- Deluxe Holster

Features (DM5050C/DM5100)

- Basic DCV Accuracy: ± 0.25%
- AC/DC Volt & Amp, Ohm
- Diode, Continuity Beeper
- Alligator Clip Test-Leads
- Lead Holders/Velcro Strap Holster

DM5050C, DMM + Capacitance

- 9 Function / 42 Range
- Multimeter

Ohm: Up to 2000MΩ

Amp: AC/DC 2 Amp

- Extended Capacitance Meter (9 Range)
- 0.1pF - 20,000pF
- Zero Adjust Knob

• Trig Lamp

DM5100, Wide Range w/Logic

- 11 Function / 45 Range

• Auto Power Off

• Data Hold & Peak Hold

• Freq: Up to 20MHz

• Amp: Up to 20A AC/DC

• Ohm: Up to 200MΩ

• Capacitance: 1p - 200pF

• Logic: TTL, TR hFE

BMC Your Best Source for
High Standard Electronics

P.O. Box 744, Lake Forest, CA 92630-0744

Order & Free Catalog
800-532-3221

(714) 586-2310 Fax (714) 586-3399


CIRCLE 335 ON FREE INFORMATION CARD



Motion Control System

\$299.95

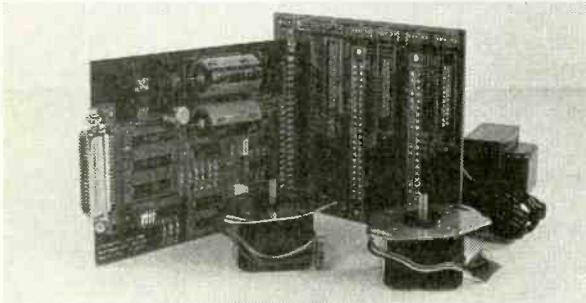INCLUDES NEW! (3) Slot Motherboard, Dual Stepper Controller Card, 12VCT 3 Amp Transformer, (2) Stepper Motors, Easy to use I.B.M Software!



Complete System "Nothing more to Buy!"

Unit# SCK-2000

- Design Robots, Plotters, Laser Systems, CNC Machines!
- Drives (2), 100 step, 3.6 degree, 4 Phase Stepping Motors!
- Unipolar 12v motors full step control. Torque is 8oz inches!
- Bi-Directional 8 Bit Read and Write Port!
- Board Addressable, 16 Possible Choices!
- Fits in Standard 19" inch Card Rack!
- Connects to any compatible I.B.M. LPT Port (1,2,3).
- With Additional Cards Control 32 Motors on 1 LPT Printer Port!
- Features Include: Variable Speed, Step, Range, Direction, and On/Off Control!
- System is expandable, Add I/O cards, Slave cards, and Amplifier cards.
- Free QBasic & Gwbasic Source Code \$ 59.95 value! *

Send Check or M.O. to:

CYBERMATION

"Intelligent Controllers"

Call Us Today!

Tel (714) 879-2000

Fax (714) 992-2082

Visa/Master/Amex Charge Accepted

1943 Sunny Crest Dr., Suite 288,
Fullerton, CA 92635

Units are in stock and ready to be shipped!
Add \$12.00 S&H: CA residents please add sales tax.

Satellite TV 'BIBLE'

4th 'DIGITAL' edition

The acclaimed "bible" of satellite TV
— ALL the TECHNICAL DETAILS —

- Operation, installation & troubleshooting of analog and digital satellite systems
- The transition from analog to digital TVRO

1-800-483-2423

TO ORDER

or for a FREE books/software/video CATALOG

HOME SATELLITE TV
INSTALLATION
AND TROUBLESHOOTING
MANUAL



324 pages
8-1/2" x 11"
\$30 plus \$4 s/h

BAYLIN publications

1905 Mariposa, Boulder, Colorado 80302, USA
Telephone: 303-449-4551 FAX: 303-939-8720

Robotic Arm Kit \$180.00

lynxmotion



Build your own Robotic Arm.
The kit comes complete with all hardware, base enclosure, structural components, servos, servo controller kit, software and an illustrated assembly manual. Makes an excellent addition to a small mobile robot base. Great for teaching motion control.

S&H charges: USA \$7.50, international \$15.00 (surface) or \$25.00 (air mail). 10% off for 10 or more. IL residents add 6.25% to total.


Send check or money order to:
Technical Service & Solutions
104 Partridge Road
Pekin, IL 61554-1403 USA

We accept
Mastercard
and Visa

Tel: 309-382-1816
Fax: 309-382-1254
www.lynxmotion.com
jfrye@mtco.com

"6-WAY COPY CAT \$1495.00*

**ASK
ABOUT
EE3!**

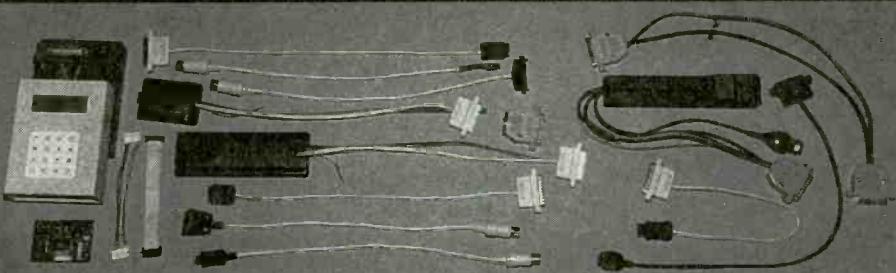

MENU# PROGRAMS THE FOLLOWING PHONES

PRICE

1	MOTOROLA ONLY w/elite & 951C !!!	\$1495
2	Above PLUS NEC P100-200-300-400-600-700	FREE
3	All of above PLUS SONY	FREE
4	All of above PLUS GE /Ericsson (newest mode)	FREE
5	All of above PLUS AUDIOVOX (does new 800!)	FREE
6	All of above PLUS MITSUBISHI/DiamondTel	FREE

Not a
Kit!

Full 5 year
warranty!

*Cables optional

All units are sold for EXPERIMENTAL AND EDUCATIONAL PURPOSES ONLY!

CALL US TODAY AT 770.973.8474 ..web page @ www.celltec.com

CIRCLE 305 ON FREE INFORMATION CARD

www.americanradiohistory.com

ATTENTION DEALERS

BUY DIRECT FROM THE WHOLESALER

GET THE BEST PRICES AND SERVICE

ALL UNITS ARE IN STOCK FOR IMMEDIATE SHIPMENT

ADD-ONS

	QTY 5	QTY 10	QTY 20	QTY 50+
STEALTH-1000-P	\$55	\$48	\$45	CALL
TVT-3 GOLD	\$48	\$41	\$38	CALL
TNT-3	\$52	\$45	\$42	CALL
STEALTH 80 - P	\$61	\$54	\$49	CALL
M-80	\$70	\$64	\$58	CALL
PIO+	\$75	\$68	\$58	CALL

NEW CONVERTERS

CENTURY CT-3000	\$68	\$64	\$60	CALL
SA - 8511	\$75	\$70	\$65	CALL

NOVAVISIONS

NV-5600	\$205	\$195	\$185	CALL
NV-5700	\$195	\$185	\$175	CALL
NV-5800	\$195	\$185	\$175	CALL
NV-5750	\$305	\$295	\$285	CALL

BOSS COMBOS

BOSS 1	\$210	\$195	\$185	CALL
BOSS 2	\$210	\$195	\$185	CALL
BOSS 3	\$210	\$195	\$185	CALL

ZENITHS

ST-1600	\$210	\$195	\$185	CALL
---------	-------	-------	-------	------

REFURBISHED CONVERTERS

REGAL • SA • PANASONIC CALL FOR THIS MONTH'S SPECIALS

1-800-800-0766

KIMTRONICS INC

30 day money back guarantee. All shipping and handling at customers expense.
Anyone implying theft of cable service will be denied sale. NO FLORIDA SALES.

WE WILL MEET OR BEAT ALL COMPETITOR'S PRICES IN THIS MAGAZINE

KIM-3

CIRCLE 328 ON FREE INFORMATION CARD


MEMBRANE SWITCH KITS!

FLAT PANEL KEYPADS
ASSEMBLE IN
MINUTES WITH YOUR
LEGEND

AVAILABLE IN 4, 12,
16, 24 & 40 KEY TYPES

CONNECTOR
AND BEZEL
INCLUDED!

OPTIONAL
"CLICKDOMES"
AVAILABLE

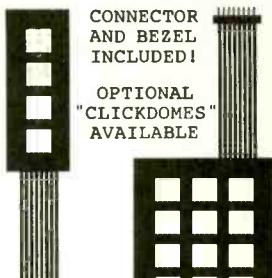

INDUSTRIAL TYPES AVAILABLE

MORE THAN 30 LAYOUTS
TO FIT MOST
APPLICATIONS

CALL FOR FREE
BROCHURE


SIL-WALKER

880 CALLE PLANO,
UNIT N
CAMARILLO, CA
93012


PHONE: (805) 389-8100

FAX: (805) 484-3311

VISA / MASTERCARD

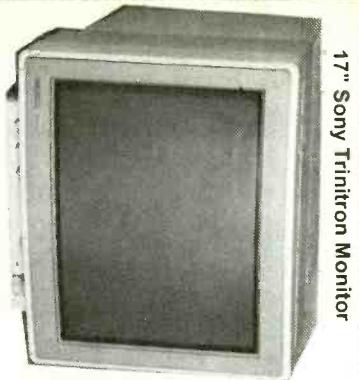


17" Sony Trinitron Monitor

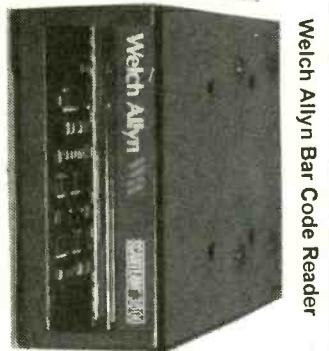

Welch Allyn Bar Code Reader

Fascinating
Corner
Prism
Cube

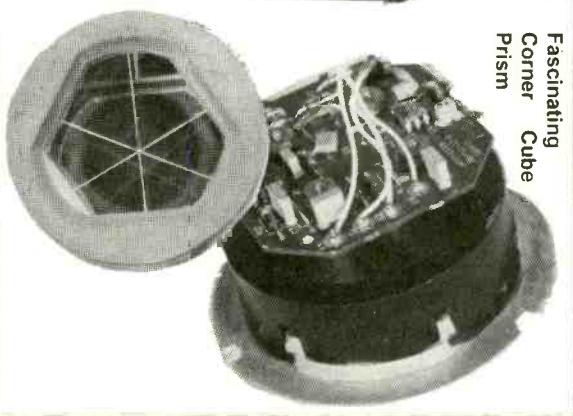

One of the most
fascinating optical
components, the corner cube directs
light back to its source. Used by
surveyors, planted on the moon by
Apollo astronauts, these beautiful gem-
like prisms are usually quite expensive.

This is our most popular item. In good condition, they meet new unit specs. Not a multisync, works fine with Macintosh, or on IBM with Photon video card. Tuned, with cables for Mac \$225.00. With Photon video \$375.00. Basic monitor \$175.00 52 Lbs Shipping. \$49.00 Postpaid. Unused.

Dear Readers,

Ordering from V&M Surplus is easy. No minimum order, no hidden charges, most items postpaid. Your satisfaction guaranteed or your money back. I am an avid collector, and right now I am looking for the following items: Norden Bombsight, M209 Converter (crypto-machine), K9 Ball Turret Sight. Cash or trade. *Jackson B. Tandy CPO, CCRW*

Vision and Motion Surplus

50 Main Street (Rear)
Ashland MA 01721


1-800-471-0747, 1-508-881-4900

BROADCAST TRANSMITTER

The FMS2 studio quality transmitter is FULLY crystal controlled and programmable to any FM broadcast frequency.

Unit features: ALC, 2:1 compressor, audio buffer / amplifier, pre-emphasis, roll off filter, stereo generator, digital PLL tuning, 75 MHz-125MHz bandwidth, 500mW power output and a special introductory price of only \$295.00 US

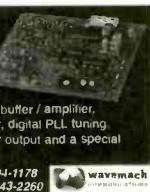SCHEMATICS FOR UNIT \$27 CATALOG 800-504-1178
FAX POLL INFO 416-243-1067 TEK LINE 416-243-2260



Robot Explorer Newsletter

Nano-ants, flying robots, Martian explorers. Explore an entire universe of exciting robots. 8 information-packed issues for only \$14.95. Call now! MasterCard/Visa Accepted.

1-(800) GO-ROBOT or 1-(800)467-6268

!!! BROADCAST FARTHER !!!


The model 1525 is a 75-110MHz RF amplifier that connects to mono or stereo FM transmitters and produces a powerful 15-20 watt signal which could broadcast up to 5 miles or more! Requires 75-250 mW drive.

Step by step plans complete with part source information and antenna designs . . . ONLY \$14 PLUS \$2 S&H NO C.O.D.'S

P Progressive Concepts
BOX 586 STREAMWOOD, IL 60107
(708)736-9822 FAX: (708)736-0353



TRAVEL LIGHT.

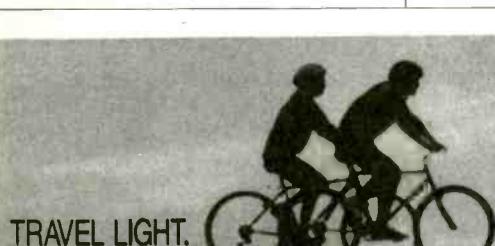

American Heart Association

EXERCISE.

AMAZING ELECTRONIC & SCIENTIFIC DEVICES

Lasers, Tesla, Ions, Anti-Gravity, Magnetics & More!

Plans • Ready-to-Use • Easy-to-Build Kits



Laser Ray Gun

Handheld,


battery operated.
Produces an intense

burst of light capable of burning holes.

LAGUN2 Plans \$20.00
LAGUN2K Kit / Plans Price on Req

250KV Tesla Coil

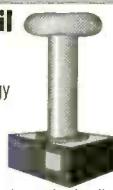10-14" of Explosive
Bolts of Lightning!
• Transmit Wireless Energy
• Ion Motors
• Anti-Gravity
• Strange and bizarre
pyrotechnical effects
• Many other experiments shown in detail
• Award winning science project!



BTG3 Plans \$15.00
BTG3K Kit/Plans with coil \$299.50
BTG30 Assbld Ready to Use \$399.50
BTG4 Plans, 500KV unit \$20.00

Visible Beam Gas Lasers

Millions degree temp equiv. Illuminates low
level clouds

- Light Shows
- Window Listener
- Optical Projects
- 12/115V
- Science Project

LAS1KM 1 mw, low cost Kit \$69.50
LGG6K 2-3mw Kit \$119.50
HNE70 5-7mw, ready to use \$299.50

Ion Ray Gun


Project Energy!
Star Wars technology demonstrates
weapons potential. IOG7K Kit/Plans \$99.50

4000 Volts 10ma High Voltage

Module - Ready to use - for many projects
from hoverboards to pyrotechnics.
MINMAX4 While they last! \$19.50

Gravity Generator

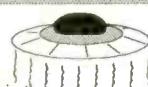Levitate an object!
Great science fair project!
GRA1 Plans \$15.00
GRA1K Power Supply Kit/Plans \$99.50
GRA10 Assbld Kit/Plans \$149.50



Includes text book on Anti-Gravity theory!

"Talking"

Plasma Globe

Spectacular color. Pulsates to music,
sounds! 8-9", with intensity and sound
controls. PLASMA1 Ready to Use \$79.50



ATTENTION: Experimenters & Researchers!

Anti-Gravity, Rail & Coil Guns, Mass Warping,
Levitation Research, Exploding Water, Propulsion Drivers,

Lattice Snapping, EMP etc. Loss-less Energy Charger
with triggered spark switch. • Adjustable 500 to 3KV out

• Charges up to 25KJ • Programmable Output

HEP1 Plans \$15.00

HEP1K Kit/Plans with 500J \$399.50

HEP10 Lab Assembled - to your spec's.



Write, call or fax for price & delivery

...shown connected to potential rail gun system

Solid State Tesla Coil



• Generate fiery electrical
plasma discharge
• Powers light and
objects without contact
• Experiment with electrical and mechanical
fields. TCS3 Plans \$8.00
TCS5K Kit/Plans 12VDC \$49.50

Pioneer a Futuristic Weapon!




Electric Gun -
prototype designed
in our lab - Join the research!
• Ballistic Velocities
• Handheld • Battery Operated
• Labelled as DANGEROUS Product
Experiment now before it is classified as a
firearm! EGUN1 Plans \$20.00
(Must be 21 for purchase of hardware)

We can design and build high voltage systems

- to your spec's!

Call or fax us with your requirements!

TACTICAL ELECTRONICS

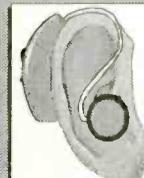

Cybernetic Ear!

Enhances normal
hearing 3-4 times!

Adjustable volume control,
fits easily into either
ear. Many, many uses.

Ready to Use!
CYBEREAR \$19.95

Telephone Line Grabber

Infinity Transmitter

Use any Tone phone to monitor
a premises, access other calls or control up
to 8 devices! TELCON3K PlansKit \$99.50
TELCON30 Ready to Use \$149.50



ALL NEW

3 Mi Voice Transmitter

• Ultra-Sensitive Mike
• Crystal Clear
• Tunes 80-130 MHz.
FMV1 Kit/Plans \$39.50



Long Range Microphone

24" dish focuses
signals to an ultra-
high gain amplifier.
PM5K Kit/Plans \$149.50



• Optional wireless module transmits
captured sounds to an FM radio.
WM5K Kit for Wireless Option \$29.50

FireBall Gun

Shoots flaming ball - two shot
capacity. Great for special effects and
remote fire starting. CAUTION REQUIRED!
FIREBALL Plans (dangerous product) \$10.00



Phasor Sonic Blast Pistol

Rids areas of unwanted pests.
Trains and conditions wild and
domestic animals. Great for
barns, attics, cellars, gardens.
PPP1K Kit/Plans \$39.50

Shocker

Force Field/ Vehicle

Electrifier

Make hand and shock balls, shock wands
and electrify objects. Great payback for
those wiseguys!
SHK1K Easy to Assemble Kit \$19.50



3 Mi Telephone Xmitter

• Tune-able 80-130 Mhz • Undetectable
• Only transmits when phone is used
VWPM7K Kit/Plans \$39.50



Extended Play Telephone Taping System

• Tapes Phone Conversation • Extends
Tape X4 • Check Local Laws before using!
TAP30X Ready to Use \$84.50

Invisible Pain Field

Intruder Deterrent

System detects intrusions and turns on a
sonic field of pain, causing disorientation,
acute paranoia, nausea and more. The
perpetrator - man or animal - soon vacates!
Protects 4 individual areas up to 5000 sq ft.
Non hazardous when used as instructed.
PPG4K Kit/Plans \$129.50
PPG40 Ready to Use \$199.50



See In Total

DARKNESS!

• High Quality IR Night Vision
Scope with IR illuminator.
SD10 Ready to Use \$199.50



Electric Charge Gun

Life is Precious -
PROTECT IT!
Stuns & immobilizes attackers
15 feet away! Check your state
laws for legality. More knockdown
power than most handguns. No
permanent injury. ID coded.
ECG1 Data
(Creditable to purch) \$10.00



ECG10 Charge Gun, Ready to Use,
includes FREE Stun Gun! \$249.50

STUN GUNS - sold separately:

STUN100 100,000 Volts \$34.50
STUN200 200,000 Volts \$49.50

VISIT US ON THE WEB!

<http://www.amazing1.com>

3 Mi Tracker Transmitter

• Tunable Output
• Uses FM Radio
• Excellent Signal Beacon
HOD1K Kit/Plans \$39.50




MIND CONTROL!

Places subjects under your
control. Programmable audible
& visual stimuli with biofeedback. Induces
strange & bizarre hallucinations without
drugs. Caution - not FDA approved.
MIND2 Plans \$15.00
MIND2K Kit and Plans \$49.50
MIND20 Assembled Unit \$69.50



FANTASTIC BRIGHTNESS!

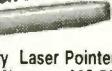High Quality Laser Pointer
LAPN64 15mw equiv, 2000' \$39.50
LAPN61 50mw equiv, 4000' \$84.50



100' Potato Cannon

Not a Toy! Uses electronic or piezo
ignition. CAUTION REQUIRED!
POT1 Plans (dangerous product) \$10.00



CATALOG!

FREE with Order or
send \$1 P&H

24 Hour Phone

800-221-1705

Orders Only Please!

INFORMATION UNLIMITED


Dept ENS-6, Box 716, Amherst, NH 03031

Phone: 603-673-4730 FAX: 603-672-5406

MC, VISA, COD, Checks accepted Please add \$5.00 S & H

New and Pre-Owned Test Equipment

 **Goldstar**

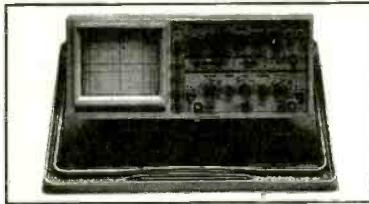

Model OS-9100P → **\$899.00**

Full 100 MHz Bandwidth!

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

FREE SHIPPING!
ON GOLDSTAR EQUIPMENT
ANYWHERE IN THE U.S.
Excluding AK & HI

 **BK PRECISION**
MAXTEC INTERNATIONAL CORP. Model 4040 \$499.00

20 MHz Sweep/Function Generator

- 0.2 Hz to 20 MHz, 5 digit LED Display
- AM & FM Internal or External Modulation
- Sine, Square, Triangle, TTL, CMOS Outputs
- Burst Operation
- External 30 MHz Frequency Counter

NEW!

 C.O.D. **TOLL FREE 1-800-99-METER**

CIRCLE 318 ON FREE INFORMATION CARD

Pre-Owned Oscilloscope Specials

B + K Precision 1476 10 MHz \$229.00
Great Starter Scope!

Tektronix 465	100 MHz	\$599.00
Tektronix 465B	100 MHz	\$699.00
Tektronix 475	200 MHz	\$799.00
Tektronix 475A	250 MHz	\$899.00

- The Industry Standard of Oscilloscopes
- Dual Channel, Calibrated Delayed Sweep
- Professionally Refurbished
- Aligned & Calibrated to Original Specifications
- 6 Month Warranty - The Longest Available!

LOWEST PRICES EVER!

NEW FLUKE MULTIMETERS & TEKTRONIX OSCILLOSCOPES

The Industry Standard in Multimeters

Model 79 II ..\$172.00 Model 87 ..\$285.00

NEW!

TEKTRONIX TDS SERIES
ON SALE!

Test Equipment Depot

A FOTRONIC CORPORATION COMPANY

P.O. BOX 708 Medford, MA 02155


1-800-996-3837

(617) 665-1400 • FAX (617) 665-0780

CADPAK for Windows

PROFESSIONAL SCHEMATIC CAPTURE AND PCB SOFTWARE

NEW PRICE FOR WINDOWS!! \$199

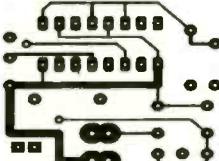

ISIS is an Easy To Use Schematic Drawing Tool.

- Automatic wire routing & dot placement.
- Exports diagrams to other applications.
- Full control of drawing appearance.
- Libraries with thousands of components.

- ARIES for Windows**
- Powerfull CAD Software for PCB Generation
- Advanced routing
 - Libraries, including SMT
 - Includes Gerber Viewing
 - Fast & Easy to use.
 - Exports diagrams to DTP.
 - 30" x 30" board

LOW PRICES!

STARTS AS LOW AS \$199 FOR WINDOWS, \$159 FOR DOS

PRICES IS IN US FUNDS - PLEASE INCLUDE \$15 S/H

R4 SYSTEMS INC.

1100 GORHAM ST. SUITE 11B-332
NEWMARKET ONTARIO
CANADA L3Y 7V1

905 898-0665 FAX 905 898-0683 BBS 905 898-0508

Internet r4system@astral.magic.ca

FREE DEMO
WRITE OR CALL
TODAY

MICRO TV CAMERA WITH TRANSMITTER

As small as a package of cigarettes! Complete TV camera with transmitter. Available on UHF channels 14 or 24. Operates on 9V battery or may be used with a wall adapter for permanent installation. Range up to 1 mile. Perfect for any surveillance application!

CAMERA WITH TRANSMITTER
UPX402.....\$459.00

PLUS S&H

Please call for custom configurations.

NEW!

XTAL CONTROLLED MICRO VIDEO TRANSMITTER

Circuit board area smaller than a credit card! A perfect companion to your Camcorder, but will also work with any video source. Xtal controlled. Available on UHF channel 14 or 24. Audio and other frequencies available as a custom option. Uses 9V battery or wall adapter. Range up to 1 mile with suitable antenna.

SEMI-KIT UPX51.....\$199.00

PLUS S&H with audio.....\$249.00

5% DISCOUNT FOR MONEY ORDERS



B.H.S. ELECTRONICS
ELECTRONIC KITS

41 EAGLERIDGE DR.
BRAMPTON, ONT
CANADA
L6R 1G1

TEL: 1-800-771-8656
FAX: (705) 466-3268

ALL ELECTRONICS


C O R P O R A T I O N

SET OF 12, SPDT NUMBERED LIGHTED SWITCHES

Twelve push-on/push-off switches (only 6 pictured). Each switch has a 0.6" square yellow lens with a 0.25" high black numeral 1 through 12. They are lighted by a 28 volt, #85 wedge base incandescent lamp which can be easily replaced if a different voltage is desired.

CAT #PBL-12

\$15.00
per set of 12

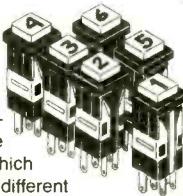

SPECIAL! REDUCED PRICE 12 POSITION BARRIER STRIP



20 amp, single row, pc mount barrier strip with screw-clamp terminals. Just slip wire under clamp and tighten it down. 12 terminals on 0.375" centers. Black thermoplastic strip is 4.56" X 0.61". Barriers between screws are 0.63" high. Large quantities available.


CAT #TER-124

65¢ each

100 for \$50.00
1000 for \$300.00

"HI-8" VIDEO CASSETTE (USED)

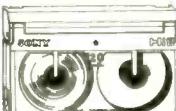SONY Hi-8
Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box. Satisfaction Guaranteed.



\$3.00
each

CAT # VCU-8

10 for \$28.00 • 100 for \$250.00

ORDER TOLL FREE

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D • Shipping and Handling \$5.00 for the 48 Continental United States - ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX
or E-MAIL For A
**Free 64 Page
CATALOG.**

Outside the U.S.A.
send \$2.00 postage.

THERMOELECTRIC COOLER PELTIER JUNCTIONS




These incredible miniature solid state heat pumps raise or lower temperature in a small area almost instantly. Utilizing the Peltier effect these modules perform the same cooling or heating functions as freon based refrigerators but they do it with no moving parts, and are very reliable. Current applied to the device will produce heat on one side and cold on the other side, up to 68° C difference between the two sides. Modules can be mounted in parallel to increase the heat transfer effect or can be stacked to achieve high differential temperatures. 127 thermocouples per device. Operates on 3-12 Vdc. Requires a heatsink to prevent overheating.

2 WAY CROSSOVER

JBL # 70561

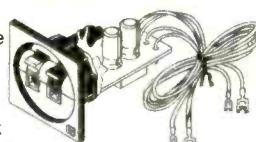No specs available on this two way crossover made for JBL speakers. 2.38" square black plastic backplate has color-coded spring lever terminals and fits a 1.95" diameter hole. Crossover is attached to backplate and extends 3.17" behind mounting plate. Color coded wire leads.




CAT # LX-70561

\$3.50
each

LARGE HEATSINK

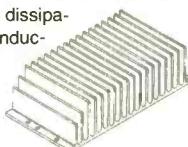Extruded aluminum heatsink for high heat dissipation. Ideal for semiconductors or thermoelectric coolers. 6.75" X 5" X 2.27" high. Flat on one side with some small predrilled holes. 18 cooling fins.



CAT # HS-19

\$10.00
each

ULTRA-BRIGHT LED

Rohm # SLA-580MT-E49 T-1 3/4 GREEN, water clear in off state. 500+ mcd @ 2.1 v, 16ma.


CAT# LED-33

2 for \$1.00

100 for \$40.00 • 1000 for \$300.00

SPECIAL PRICING! 12 VDC MINI-FAN

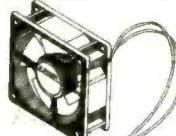Sunon # KD1206PTS1
12Vdc, 2.2 W fan. 60mm X 60mm X 25mm. Black plastic housing. Five blade impeller. 18" pigtail leads. While Supply Lasts!



CAT# CF-35

\$4.00
each

10 for \$35.00

1.18" (30 mm) square
X 0.15" (3.8 mm) thick.

\$17.00
each

CAT# PJT-1
5 for \$75.00

1.57" (40 mm) square
X 0.15" (3.8 mm) thick.

\$26.00
each

CAT# PJT-2
5 for \$110.00

Quantity Pricing Available!

12 Vdc 1 AMP WALL TRANSFORMER

2.1 mm co-ax plug center positive.

CAT# DCTX-1212

\$6.00
each

1-800-826-5432

FAX (818) 781-2653 • INFO (818) 904-0524

INTERNET <http://www.allcorp.com/>

E-MAIL allcorp@allcorp.com




Toronto Surplus & Scientific

608 Gordon Baker Rd. Willowdale,
Ontario Canada zip: M2H-3B4
TEL: (416) 490-8865
Inc.



OFFICE: (905) 887-0007 FAX: (905) 887-0006

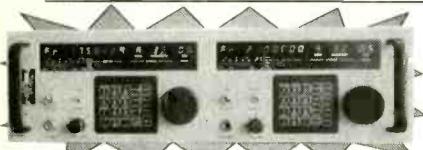
*****SHIPPING IS NOT INCLUDED IN THESE PRICES, PLEASE CALL FOR RATES*****



CUBIC COMMUNICATIONS DUAL VLF/HF RECEIVER

This High-Tech surveillance receiver features two fully independent high performance radios in one rack cabinet. Covers 5kHz-30MHz with a full compliment of filters incl. USB/LSB plus RS-232 remote control. The units we have in stock are in very nice condition.

Price: \$2395.00 ea.

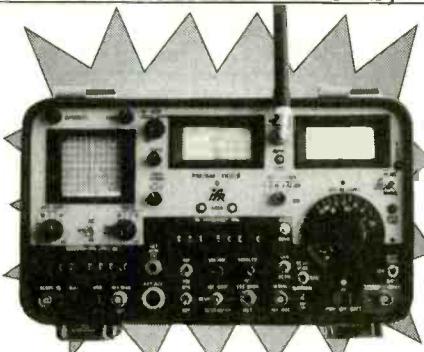

IFR 1100S

COMMUNICATIONS MONITOR

FM/AM-1100S is a synthesized AM/FM/SSB receiver/signal generator. Frequency range is 300Khz-1Ghz, it contains a 60 watt RF power meter, deviation/modulation meter, oscilloscope, spectrum analyzer, tone generator and internal high stability freq.-standard. It's a radio repair shop in one cabinet.

Price: \$4250.00 Fully Checked.

IFR 1000SA as above except without spectrum analyzer. Price: \$2750.00 Fully Checked.


-NEW IFR 1000 Instrument covers with sinad meter and scope probe (new unused). \$275.00



HEWLETT PACKARD


HP 331A DISTORTION ANALYZER

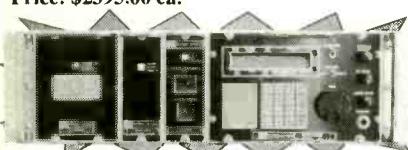Industry Standard unit covers 5Hz-600kHz & measures total harmonic distortion down to .1% full scale. We are blowing these out as-is, untested but, most we've shipped in the past have worked. Price: \$99.00 (units are scratched).



WATKINS JOHNSON WJ-9040 SERIES RECEIVER

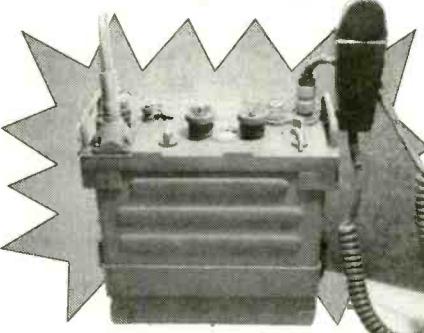This awesome radio covers 200Hz-1400MHz in 13 bandwidths of AM, AM Slideback, FM, CW and SSB demodulation modes. Contains lots of features and you can bet this is a super-rare find in the used market. Price: \$5450.00
CALL for DETAILS!!!



HEWLETT PACKARD 8640B SPECTRUM ANALYZER OPT-E96

This High Performance instrument features 3 Hz video bandwidth over the 1kHz - 1.5Ghz frequency range. Automatic zoom, signal track, multiple store/recall are only a few of the very powerful functions you will find coupled with a high performance synthesized LO and built in freq counter.


Price: \$16995.00 Fully Checked



HEWLETT PACKARD 8640B SIGNAL GENERATOR

Industry Standard sig-gen 500Khz-512Mhz features internal phase lock/synchronizer and digital freq. readout. +19 to -145 dBm output. AM, FM, Ext and Pulse modulation.


Price: \$1695.00 OPT 001 add \$100.00
OPT 003 add \$150.00

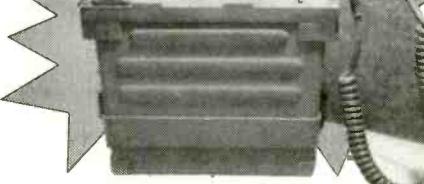

PRC 25 - MILITARY TACTICAL TRANSCEIVER

Fabulous quality and design are standard in this 30Mhz-75.95 Mhz tactical transceiver.

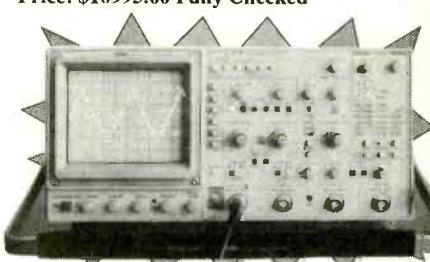Output power level from 1.1-2 watts 150Hz squelch. The units we just received are reconditioned (newly painted) ready for issue and include the battery box. Price: \$245.00



TEK 2246 OSCILLOSCOPE

This user friendly oscilloscope features, 100MHz bandwidth on four channels, onscreen scale factors, versatile triggering, 2mV/Div vert sensitivity, delayed sweep, hands-off voltmeter and smart cursors.

Looks very clean. Price: \$1950.00



HEWLETT PACKARD HP3312 SWEEP/FUNCTION GENERATOR

Well designed and easy to use, this function generator combines economy and quality in one compact unit. Freq range is 0.1Hz-13MHz output is 10.0VPP into 50 ohms. Sweep, CW, AM, FM, or tone burst. This unit features-sync. out, trig. phase, symmetry, offset and more. Price: \$935.00 ea. Fully checked.


All Prices in U.S.
Please include telephone/fax # with
mail-in orders. Orders must be prepaid
by guaranteed instrument.
Prices do not include shipping.
Please call us if you have any questions

Manuals available at extra cost

CIRCLE 317 ON FREE INFORMATION CARD

(No catalog available yet!)

Nov. 96

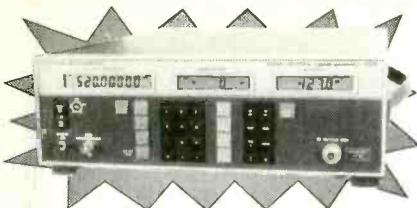

MARCONI SYNTHESIZED

SIGNAL GENERATOR Model 2018

Freq range 80Khz-520Mhz with calibrated output levels from -127 dBm to +13dBm. Resolution 10Hz. It can be freq, phase or amplitude modulated from ext or int modulation sources. RF output resolution is 0.1dB. reverse power protection of up to 50W is possible without damage to the instrument. This instrument is microprocessor controlled and very easy to use, a must for any serious repair or development lab. Price : \$1750.00 Checked



"CAL" ASTRONAUTICS

MOBILE SATELITE COMMUNICATIONS STATION



MILITARY STANDARD D.C. GENERATOR

Superior QUALITY plus rugged design are features of this deluxe 2 cylinder 4 stroke gasoline generator. The control panel contains meters for voltage & current indication, main circuit breaker and voltage adjustment. Shielded wires and plugs comprise the RFI suppression ignition system eliminating most radio noise. These units are "new" in the original carton complete with operators manual and only require fuel and oil for operation; output voltage is adjustable approx. 10-32v (28v nom) @ 53.3A (1.5Kw) continuous duty load.

Price: \$379.00 New in Orig. Carton.

You will be impressed!!!

COLLECTOR ALERT - \$39.00
8-DAY AIRCRAFT


CLOCK 1-7/8" dial

Great collectors item for the ham shack, fifties vintage funct/chkd.



This is a box chock full of "current" high-end communications technology. These units were designed so that mobile land based vehicles could keep in touch (via Geostationary Inmarsat satellite network) with home base using an intelligent data terminal. The terminal features a back-lit 4 line LCD display and illuminated keys; one of the transceiver's most impressive features is an "L" Band 1.2-1.55GHz 60 watt amplifier. The fabulous helix antenna (with LNA built-in) is an amazing design with all kinds of active and passive devices surface-mounted on to the antenna reflector. We consider this the "ultimate" gadgeteer's goodie pack" with all kinds of up-to-date RF satellite ground technology. These systems come complete in their original shipping container with all cables and mounting bracket. Best of all they operate on 12 VDC. Operators manual supplied (but, there isn't any subscriber data).

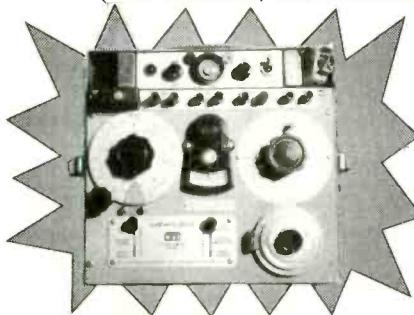(NOT TESTED) IN GOOD CONDITION.....\$345.00




ESI MODEL 250 DA IMPEDANCE BRIDGE

Resistance range- 0.1 milliohms - 11 megohms, capacitance 0.1pf-1100mf, inductance 0.1 μH to 1100 Hz. Dissipation factor (R/X or D) 0.001 to 1000. Internal oscillator 1 KHz.

Used, not functionally checked.....\$95.00

Functionally checked.....\$165.00

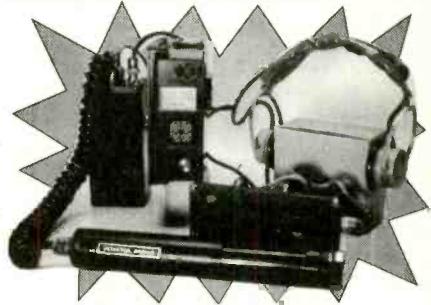

PDR-63 PORTABLE RADIACTIVE METER

This portable radia set is loaded with all kinds of extras featuring six ranges of sensitivity for both Gamma or Beta radiation measurements.

The 1st scale 0-1 rad/hr up to 0-5000 rad/hr. The unit comes supplied with headset & bat/charger.

Req's only 4 AA Batteries. Price: \$149.95


- CROWN MODEL 7560 1KW PWR AMP. DC - 40KHz	\$1,800.00
- DATRON 4000A DC & OHMS CALIBRATOR	\$4,500.00
- EATON NM-17/27A EMI FIELD INT. METER	\$1,500.00
- ENI MOD 310L 250KHz-110MHz @ 50db GAIN	\$ 365.00
- ENI MOD 406L 150 KHz-250MHz @ 40db GAIN	\$ 350.00
- FLUKE 5100A CALIBRATOR	\$3,800.00
- FLUKE 7261A FREQ. COUNTER 520mHz	\$ 475.00
- GOULD 221 CHART RECORDER	\$ 450.00
- GOULD RS 3800 PROGRAMABLE CHART RECORDER/w MOD 5900 SIG CONDITIONER & D/C AMPS (NEW)	\$3,500.00
- HII ENERGY CORP. DISCHARGE CAP. 1μF @ 20KV	\$ 300.00
- ROHDE & SCHWARZ SIG GENERATOR 4-584MHz	\$ 750.00
- TEK FG504 FUNCTION GENERATOR (40MHz)	\$ 875.00
- TEK 1502 TDR w/CHART REC	\$2,200.00
- TEK 465 OPT 5 TV-TRIG	\$ 849.00
- TEK 465B 100MHz OSCILLOSCOPE	\$ 895.00
- TEK 465M 100MHz OSCILLOSCOPE	\$ 695.00
- TEK 485 350 MHz OSCILLOSCOPE	\$ 1195.00
- TEK 4260A LCR BRIDGE	\$ 385.00

- HP 4984A IN-SERVICE TIMS (brand new)	\$2,995.00
- HP 5006A SIGNATURE ANALYZER	\$ 650.00
- HP 5315A UNIVERSAL COUNTER (1 GHz)	\$ 875.00
- HP 6472C POWER SUPPLY 0-64V @ 0-150A	\$1,800.00
- HP 8505 NETWORK ANALYZER SYSTEM	\$4,980.00
- HP 8588I SPECTRUM ANALYZER 0.1-1.5GHz	\$2,350.00
- HP 859A SPEC-ANALYZER 0.1-22GHz	\$3,995.00
- MARCONI 2018 SYNTHESIZED SIGNAL GENERATOR 80KHz - 520MHz	\$1,750.00
- ROHDE & SCHWARZ SIG GENERATOR 4-584MHz	\$ 750.00
- TEK FG504 FUNCTION GENERATOR (40MHz)	\$ 875.00
- TEK 1502 TDR w/CHART REC	\$2,200.00
- TEK 465 OPT 5 TV-TRIG	\$ 849.00
- TEK 465B 100MHz OSCILLOSCOPE	\$ 895.00
- TEK 465M 100MHz OSCILLOSCOPE	\$ 695.00
- TEK 485 350 MHz OSCILLOSCOPE	\$ 1195.00
- TEK 1750 WAVEFORM/VECTOR MONITOR	\$1,850.00
- SENCORE VA62 VIDEO TEST SYSTEM	\$1,995.00
- BOONTON 82AD AM/FM MOD-METER	\$1,275.00
- COLLINS 6515-1 RECEIVER	\$1,250.00
- GRT-22 UHF POWER AMPLIFIER	\$ 200.00
- R392 RECEIVER 5-30MHz	\$ 165.00
- T195 100+ COMPANION XMTR TO 392	\$ 85.00
- WATKINS JOHNSON 8626A-4 with WJ8626-1 & SPN 108 5KHz-30 MHz MIL-SPEC communications receiver	\$3,950.00
- WAVETEK 3002 RF SIG. GENERATOR	\$ 795.00
*****ATTENTION DIVERS-GAS DRIVEN COMPRESSORS*****	
- BAUER 11CFM 3500 PSI COMPRESSOR SYSTEM	
combines a four stage compressor and 4 cyl wisconsin engine on a cart with storage tanks and controls or electric version available	\$3,500.00
- BAUER K14 3500 PSI COMPRESSOR SYSTEM same as above except uses briggs & stratton 8hp motor	\$2,750.00

CIRCLE 317 ON FREE INFORMATION CARD


SPECTRUM ANALYZER

(Continued from page 52)

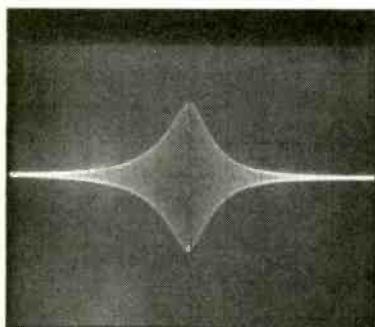

THE OSCILLOSCOPE'S VIEW of the bubble sampled from the preamplifier assembly's test point after the 145-MHz IF filter alignment. The oscilloscope's 10× time-base magnifier is switched on. You should be able to see the zero beat at the center of the bubble.

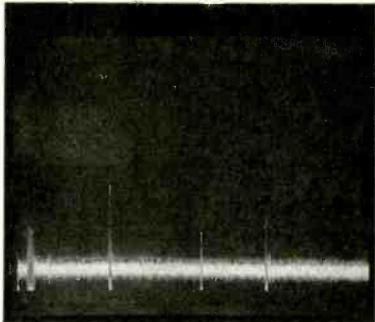For example, EMI on cables might be best observed by passing the cable through a toroid ferrite. Wrap a few turns of finer wire as a secondary and



THE OSCILLOSCOPE'S DISPLAY of the HSA output when a short-wire antenna is connected to the BNC connector. The extreme left burst is an unknown signal. Local radio-control signals from left to right are at 27.995 MHz, 53.4 MHz, and 72.280 MHz.

connect to the HSA. This allows examination of what is on a suspect cable but avoids electrostatic pickup.

It is also possible to extend the reach of the HSA with a length of coax cable with a one or two turn sniffer loop on the pickup end. In all cases, be careful when working around

power lines or line-powered equipment.

Parts and Supplies Hints. All parts and supplies for the Hobby Spectrum Analyzer came from electronics parts mail-order suppliers listed in the sidebar and from local hardware, model hobby, craft, and RadioShack stores. No single parts source can supply everything needed. A very few parts such as slide switches and beads came only from Digi-Key. The NE602IC came from Ocean State Electronics and DC Electronics. The MV209 varactor comes from DC Electronics or Hosfelt. Many catalogs list ceramic disc capacitors; however, the RadioShack capacitor assortment #272-806 has all the smaller picofarad values on the RF circuit module. Consider using cut-to-length plastic ball pen handles for spacers. Metal and plastic tubing of many sizes as well as brass, aluminum, tin plate, and copper sheet is available at model hobby shops.

Ω

Robot Kits

You do ALL electronic & mechanical assembly using well-illustrated Instruction Books with assembly, experiments and testing. Each model applies different electronic & robotic principles.

606A "Scrambler" All Terrain Robot This 6-legged Robot walks over rough terrain. High-tech infrared beam senses and avoids objects in its path. 32 page Book.

\$35.95



602A "Blinky" Pathfinder Robot Follows path made with a marker pen or tape. Red/green LEDs react to steering changes, adding fun and interest. 28 page Book. Infrared emitter/detectors.

\$36.95

- ✓ Academic-Level Books
- ✓ Build it Yourself
- ✓ Action Packed

603A "Copycat" Programmable Robot Program direction, light and sound using detachable keypad (included) or optional PC. Learn digital logic basics. 44 page Book. \$57.35

601A "Scooter" Sound Controlled Robot Backs up, changes direction, goes forward when it hears loud noise or hits an object. Fluorescent red. 24 page Book. Fast-paced excitement!

\$16.95

Technical Books - Graymark carries a selection of technical books, including Robot Books. Dependable Products - Since 1963, Graymark's ONLY business has been educational electronic kits. We do one thing and we do it right.

ORDER TODAY! Phone: VISA/MasterCard/Discover/AMEX
Mail: Check/Money Order, Credit Cards
Add: \$4.00 Shipping

**CALL FOR FREE
44 PAGE CATALOG**


800-854-7393

BREAST CANCER BEGINS EVEN SMALLER THAN THIS. THAT'S WHY YOU NEED A YEARLY MAMMOGRAM, ESPECIALLY AS YOU GET OLDER. MAMMOGRAMS CAN DETECT LUMPS TOO SMALL FOR YOU TO FEEL AND EARLY DETECTION MAY SAVE YOUR LIFE, SO CALL

**1-800-
ACS
2345.**

GET A MAMMOGRAM.
EARLY DETECTION IS THE BEST PROTECTION.

A Safety Service of
Mammogram
Production

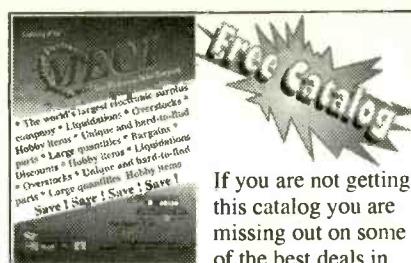

If you are not getting this catalog you are missing out on some of the best deals in electronics today! We have thousands of items ranging from unique, hard-to-find parts to standard production components. Call, write, or fax today to start your free subscription to the most unique catalog in the industry, filled with super values on surplus electronic and hobbyist type items. If you have a friend who would like to receive our catalog, send us their name and address and we will gladly forward them a complementary 100 page catalog.

Why pay more? Call today.



340 East First Street Fax Order Line
Dayton, Ohio 45402 1-800-344-6324

**Order Toll-Free
1-800-344-4465**


CIRCLE 251 ON FREE INFORMATION CARD

Don't waste another minute, send today for the latest free Catalog and a free sample booklet. Send your name and address to:

**Consumer Information Center
Department TH
Pueblo, Colorado 81009**

ACTIVE MICRO We Want Your Excess Inventory

- * INTEGRATED CIRCUITS
- * MEMORY (NEW OR USED)
- * EPROMS (NEW OR USED)
- * CIRCUIT BOARDS
- * DIODES
- * TRANSISTORS
- * LED'S

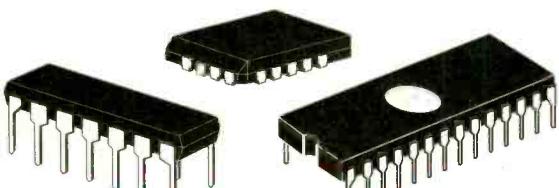

**Tel 310-494-4851 Fax 310-494-4913
1891 Obispo Ave Signal Hill, CA 90804**

HOME AUTOMATION

World's Largest Selection!

Widest Selection of X-10 Devices Available

Hundreds of hard-to-find automation, X-10 and wireless control products. Computer interfaces, software, development tools, lighting control, telephone systems, security systems, surveillance cameras, infra-red audio/video control, HVAC, pet care automation, wiring supplies, books and videos and much more!



Packed with Pictures
& Diagrams


HOME AUTOMATION SYSTEMS, INC.

Questions: 714-708-0610 Fax: 714-708-0614
e-mail: catalog@smarthome.com
<http://www.smarthome.com/smarthome>

24 Hours **Call 800-SMART-HOME 800-762-7846**

**Lowest Prices
Guaranteed!**

AUDIO DISTORTION ANALYZER

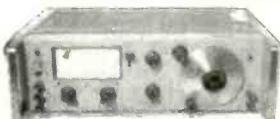

HEWLETT-PACKARD 331A ANALYZER measures total distortion 0.1% to 100% of full scale in 7 ranges over 5 Hz to 600 KHz. Fundamental rejection >80 DB. Voltmeter indicates 300 uv to 300 V rms in 13 ranges, 10 DB per range. Requires 115/230 VAC; 16.8x5x15.3, 24 lbs sh.

USED-CHECKED with manual \$360 \$215

H-P AUDIO OSCILLATOR

HEWLETT-PACKARD 200CD OSCILLATOR, popular tube-type audio generator covers 5 Hz to 600 KHz in five bands; output 10 volts into 600 ohms or 20 V open circuit. Requires 115/230 VAC 50-400 Hz. 7" Wx10.8" Hx12.5" D, 20 lbs sh.

USED-CHECKED w/book \$125.00



TA-838/PT FIELD PHONE

MILITARY TELEPHONE has push-button numeric tone pad and is designed for 2- or 4-wire communications; replaces old EE-8 and TA-43/312 field phones. Ringing signal possible only in 4-wire hook-up. TA-838 can also be operated over standard telephone lines. Rugged thermoplastic construction; requires four C-cell batteries. 6.9x8x5, 8 lbs. sh

USED-CHECKED \$85.00
Operators Manual \$10.00



JAN-BOXED ELECTRON TUBES

2A3 Penta-USA (but looks Chinese-made)	\$14.00
2K25 Raytheon blue ...	\$40.00
4CX300A/8167 Eimac	\$65.00
4D32 Raytheon	\$35.00
6B4GA Sylvania	\$17.50
1625 National-Union	\$4.50
5691 Richardson	\$6.50
5751 ECG	\$3.50
5814A ECG = 12AU7	\$3.25
5998A Sylvania	\$9.95
7025 GE = 12AX7A	\$7.50
6146W GE	\$19.95 ea; 10 for \$175.00
6922 ECG = 6DJ8	\$3.50 ea; 10 for \$28.00; 100 / \$200.00
7360 ECG	\$15.00
8552 ECG, 12V Version 6146	\$12.00
7581A ECG, 35 W version of 6L6GC	\$17.50 ea; 10 / \$150.00

Prices F.O.B. Lima, O. • VISA, MASTERCARD Accepted.

Allow for Shipping • Write for latest Catalog

Address Dept. ES • Phone 419/227-6573 • Fax 419/227-1313

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

Printed Circuits in Minutes Direct From LaserPrint!

8 1/2" x 11"
* Or Photocopy
** Use standard
household iron
or P-n-P Press.



Use Standard Copper Clad Board
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100
Visa/MC/PO/Ck/MO \$4 S&H
Techniks Inc.
P.O. Box 463
Ringo NJ 07551
ph. 908.788.8249 fax 908.788.8837
<http://chelsea.ios.com/~techniks>
Retail Dealer Inquiries Invited

Smart Battery Charger

JUN 87 QST


BY WARREN DION N1BBH

FOR GEL-CELLS or LEAD ACID BATTERIES. Features: Precision temperature tracking voltage reference & three mode charging sequence. Standard kit is for 12V @ 1/2 or 1 Amp, user selectable. Can be connected to the battery indefinitely, will not overcharge. Weighs 2 pounds and measures 4" W x 5 1/2" D x 2 1/2" H. Finished enclosure included in kit.

Complete Kit Only \$59.95
Assembled & Tested \$79.95

CA Residents add 7.75% sales tax. S&H: \$5.00 (Insured). Foreign orders add 20%. For more info or price list; send legal size SASE (52c) to:

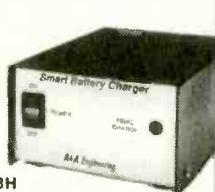A&A Engineering
2521 W. La Palma #K • Anaheim, CA 92801
(714) 952-2114 • FAX: (714) 952-3280



"WE PURCHASE" \$\$ TOP PRICES \$\$ PAID

JERROLD™
DPV7
FPBB7
CFT

PIONEER™
5135
6110
6300

TOCOM™
5503 VIP
5507

**ATLANTIC
SCIENTIFIC™**
8570
8580
8590
8600

Midwest's Largest Brokers
We Buy Quantities of Ten To A Thousand Units
NATIONAL CABLE BROKERS
(219) 935-4128

UPGRADE YOUR COMPUTER!

VISAMC
Welcome!
959 W. 5th St. • Reno, NV 89503
(702) 322-8875 • Fax (702) 324-9900
www.techass.com • sales@hoopsware.com

Memory

1Mb (1x6-70 ns)	\$9
4Mb (4x6-70 ns)	\$42
4Mb (1x32-80 ns)	\$25
8Mb (2x32-60 ns)	\$52
16Mb (4x32-60 ns)	\$98
32Mb (8x32-60ns)	\$188

CPU's

256K ISA VGA	\$23
Trident 8900 1Mb	\$38
ISA SVGA	\$38
Trident 9440 1Mb	\$38
VLB SVGA	\$38
SIS 1MB ISA SVGA	\$38
Trident 9860 1Mb PC	\$45
SVGA nMPEG	\$45

Sound Cards

16-bit Sound Blaster Pro compatible	\$40
16-bit SB Pro/PNP	\$40
Sound Blaster 32 PnP	\$41

Modems

14.4 Int/Fax/Modem	\$38
28.8 Int/Fax/Modem	\$38
mVoice	\$67
28.8 Super/Fax/Modem	\$102
28.8 Int/Fax/Modem for Windows	\$115
33.6 Int/Fax/Modem	\$115

Hard Drives

WD 540 Mb IDE	\$160
WD 850Mb IDE	\$175
WD 1.2Gb IDE	\$230
WD 1.8Gb IDE	\$250
WD 2.1Gb IDE	\$340

Video Cards

256K ISA VGA	\$23
Trident 8900 1Mb	\$38
ISA SVGA	\$38
Trident 9440 1Mb	\$38
VLB SVGA	\$38
SIS 1MB ISA SVGA	\$38
Trident 9860 1Mb PC	\$45
SVGA nMPEG	\$45

Sound Cards

16-bit Sound Blaster Pro compatible	\$40
16-bit SB Pro/PNP	\$40
Sound Blaster 32 PnP	\$41
16-bit SB Pro/PNP	\$41
Sound Blaster 32 PnP	\$41

Modem

14.4 Int/Fax/Modem	\$38
28.8 Int/Fax/Modem	\$38
mVoice	\$67
28.8 Super/Fax/Modem	\$102
28.8 Int/Fax/Modem for Windows	\$115
33.6 Int/Fax/Modem	\$115

Hard Drives

WD 540 Mb IDE	\$160
WD 850Mb IDE	\$175
WD 1.2Gb IDE	\$230
WD 1.8Gb IDE	\$250
WD 2.1Gb IDE	\$340

Video Cards

256K ISA VGA	\$23
Trident 8900 1Mb	\$38
ISA SVGA	\$38
Trident 9440 1Mb	\$38
VLB SVGA	\$38
SIS 1MB ISA SVGA	\$38
Trident 9860 1Mb PC	\$45
SVGA nMPEG	\$45

Sound Cards

16-bit Sound Blaster Pro compatible	\$40
16-bit SB Pro/PNP	\$40
Sound Blaster 32 PnP	\$41
16-bit SB Pro/PNP	\$41
Sound Blaster 32 PnP	\$41

Modem

14.4 Int/Fax/Modem	\$38
28.8 Int/Fax/Modem	\$38
mVoice	\$67
28.8 Super/Fax/Modem	\$102
28.8 Int/Fax/Modem for Windows	\$115
33.6 Int/Fax/Modem	\$115

Hard Drives

WD 540 Mb IDE	\$160
WD 850Mb IDE	\$175
WD 1.2Gb IDE	\$230
WD 1.8Gb IDE	\$250
WD 2.1Gb IDE	\$340

Video Cards

256K ISA VGA	\$23
Trident 8900 1Mb	\$38
ISA SVGA	\$38
Trident 9440 1Mb	\$38
VLB SVGA	\$38
SIS 1MB ISA SVGA	\$38
Trident 9860 1Mb PC	\$45
SVGA nMPEG	\$45

Sound Cards

16-bit Sound Blaster Pro compatible	\$40
16-bit SB Pro/PNP	\$40
Sound Blaster 32 PnP	\$41
16-bit SB Pro/PNP	\$41
Sound Blaster 32 PnP	\$41

Modem

14.4 Int/Fax/Modem	\$38
28.8 Int/Fax/Modem	\$38
mVoice	\$67
28.8 Super/Fax/Modem	\$102
28.8 Int/Fax/Modem for Windows	\$115
33.6 Int/Fax/Modem	\$115

Hard Drives

WD 540 Mb IDE	\$160
WD 850Mb IDE	\$175
WD 1.2Gb IDE	\$230
WD 1.8Gb IDE	\$250
WD 2.1Gb IDE	\$340

Video Cards

256K ISA VGA	\$23
Trident 8900 1Mb	\$38
ISA SVGA	\$38
Trident 9440 1Mb	\$38
VLB SVGA	\$38
SIS 1MB ISA SVGA	\$38
Trident 9860 1Mb PC	\$45
SVGA nMPEG	\$45

Sound Cards

16-bit Sound Blaster Pro compatible	\$40
16-bit SB Pro/PNP	\$40
Sound Blaster 32 PnP	\$41
16-bit SB Pro/PNP	\$41
Sound Blaster 32 PnP	\$41

Modem

14.4 Int/Fax/Modem	\$38
28.8 Int/Fax/Modem	\$38
mVoice	\$67
28.8 Super/Fax/Modem	\$102
28.8 Int/Fax/Modem for Windows	\$115
33.6 Int/Fax/Modem	\$115

Hard Drives

WD 540 Mb IDE	\$160
WD 850Mb IDE	\$175
WD 1.2Gb IDE	\$230
WD 1.8Gb IDE	\$250
WD 2.1Gb IDE	\$340

Video Cards

256K ISA VGA	\$23
Trident 8900 1Mb	\$38
ISA SVGA	\$38
Trident 9440 1Mb	\$38
VLB SVGA	\$38
SIS 1MB ISA SVGA	\$38
Trident 9860 1Mb PC	\$45
SVGA nMPEG	\$45

Sound Cards

16-bit Sound Blaster Pro compatible	\$40
16-bit SB Pro/PNP	\$40
Sound Blaster 32 PnP	\$41
16-bit SB Pro/PNP	\$41
Sound Blaster 32 PnP	\$41

Modem

14.4 Int/Fax/Modem	\$38
28.8 Int/Fax/Modem	\$38
mVoice	\$67
28.8 Super/Fax/Modem	\$102
28.8 Int/Fax/Modem for Windows	\$115
33.6 Int/Fax/Modem	\$115

Hard Drives

WD 540 Mb IDE	\$160

<tbl_r cells="2" ix="5" maxcspan="1" maxrspan="1

Books that work the way you work... SPECIAL OFFER

No obligation

**SAVE
OVER 10%**

**NEW
FROM
JOHN LENK**

JOHN D. LENK

**SIMPLIFIED
DESIGN
OF SWITCHING
POWER
SUPPLIES**



1996, paperback
\$29.95 \$26.95
0-7506-9821-7

JOHN D. LENK


**SIMPLIFIED
DESIGN OF
MICROPOWER
AND BATTERY
CIRCUITS**



1996, paperback
\$29.95 \$26.95
0-7506-9510-2

JOHN D. LENK

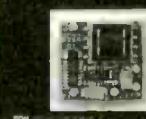**SIMPLIFIED
DESIGN
OF LINEAR
POWER
SUPPLIES**



1996, paperback
\$29.95 \$26.95
0-7506-9820-9


JOHN D.

**SIMPLIFIED
DESIGN
OF
IC
AMPLIFIERS**




June 1996, paperback
\$29.95 \$26.95
0-7506-9508-0

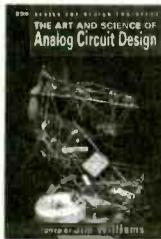Butterworth-Heinemann brings you something for everyone from John Lenk's Simplified Design Series. These books are all-inclusive, one-stop guides. Each has step-by-step instructions and diagrams that make it easy-to-use for the student, experimenter, and professional. All are available in paperback.



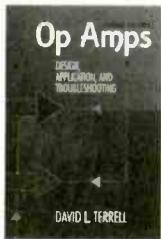
1995, hardcover
\$49.95 \$44.95
0-7506-9505-6



1996, hardcover
\$49.95 \$44.95
0-7506-9702-4



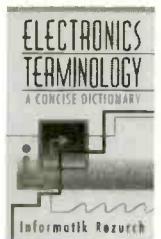
1995, paperback
\$29.95 \$26.95
0-7506-9694-X




1996, paperback
\$29.95 \$10.95
0-7506-9751-2



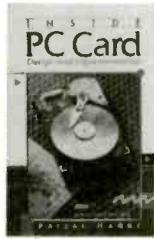
1996, paperback
includes disk
\$39.95 \$35.95
0-7506-9700-8



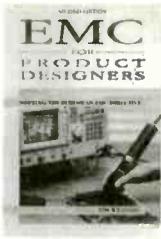July 1996, hardcover
\$49.95 \$44.95
0-7506-9747-4



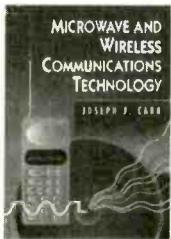
1996, paperback
\$49.95 \$42.95
0-7506-2466-3



1996, paperback
\$49.95 \$39.95
0-7506-9707-5



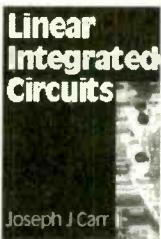1995, paperback
\$49.95 \$42.95
0-7506-2281-4



1996, paperback
\$39.95 \$33.95
0-7506-2591-0

Please send me the book(s) listed below at 10% off! Phone: 1-800-366-BOOK FAX: 1-800-446-6520

Please add \$4.00 for handling for the first item ordered and \$1.50 for each additional item ordered to all check and credit card orders. Billed orders will be charged additional shipping based on weight and destination. All US orders must include your state sales tax. Prepayment or company purchase order is required for all orders. Canadian customers please pay by credit card or in US funds and include 7% GST on books and handling. Prices subject to change without notice.

Write book number(s) here

--	--	--	--	--

Charge my: VISA AMEX MC Card # _____ EXP Date _____

Name _____ Signature _____

Address _____ City/ State/ ZIP _____

Tel _____ E-mail _____

Visit us on the Internet @ <http://www.bh.com/bh/el> Send me a FREE catalog (item 642)

**BUTTERWORTH
HEINEMANN** 313 Washington Street, Newton, MA 02158
from outside US and Canada, call 617-928-2500

CIRCLE 333 ON FREE INFORMATION CARD

TS123

CALL TOLL FREE
(800) 292-7711 orders only
Se Habla Español

C&S SALES

EXCELLENCE IN SERVICE

**CALL OR WRITE FOR
A FREE 60 PAGE
CATALOG!**
(800) 445-3201

XK-550 Digital / Analog Trainer

Elenco's advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square wave forms. 1560 tie point breadboard area.

**XK-550
Assembled and Tested**

\$169.95

XK-550K - Kit
\$139.95

Tools and meter shown optional



GF-8026 w/ Frequency

- Linear and Log Sweep
- .02Hz to 2MHz
- Counter Range 1Hz to 10MHz
- 4 Digit Display

\$225

Auto Ranging Hand-Held DMM w/ Bar Graph Model EDM-163

\$99.95



7 Functions with data hold
Compares to Fluke Model 77II

MX-9300 Four Functions In One

- One instrument with four test and measuring systems:
1.3GHz Frequency Counter • 2MHz Sweep Function Generator
Digital Multimeter • Digital Triple Power Supply
(0-30V @ 3A, 15V @ 1A, 5V @ 2A)



\$479.95

Digital Multimeter Model M-1700

\$39.95

11 functions including freq to 20MHz,
cap to 20μF. Meets UL-1244 safety
specs.



Model XP-581

- 4 Fully Regulated DC Power Supplies in One Unit**
4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A
1 Variable - 2.5 - 20V @ 2A



Fluke Multimeters

70 Series	80 Series
Model 70II \$69.95	Model 83 \$235.00
Model 73II \$97.50	Model 85 \$269.00
Model 75II \$135.00	Model 87 \$289.00
Model 77II \$154.95	
Model 79II \$175.00	

B&K Precision Multimeters

Model 391 \$159.00	Model 388A \$99.00
Model 390 \$139.00	Model 2707 \$79.00
Model 389 \$109.00	Model 2860A \$85.00

Kit Corner

over 100 kits available

PT-223K

\$15.95

Phone kit
with
train-
ing
course.



**Fiber Optics
Technology
with training course**

Model FO-30K


\$19.95



Model AM/FM-108K Transistor Radio Kit

with training course

\$29.95

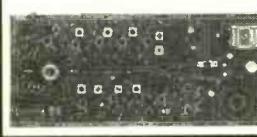

M-1005K Compact Multimeter Kit

\$19.95

6 Functions
& Transistor
Test



WE WILL NOT BE UNDERSOLD

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8% Sales Tax

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 520-9904 (847) 541-0710
http://www.elenco.com/cs_sales/



**15 DAY MONEY BACK
GUARANTEE**
FULL FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 308 ON FREE INFORMATION CARD



TK-3000

\$89.95

Tools Included:

- SR-2 - Deluxe Soldering Iron
- SH-1 - Soldering Iron Stand
- ST-1 - Diagonal Pliers
- ST-2 - Long Nose Pliers
- ST-30 - Deluxe Wire Stripper
- SE-1 - Solder Ease Kit
- ND-3 - 3 pc. Nut Driver Set
- TL-8 - Precision Screw Drivers
- ST-5 - Screw Driver Slotted 3/16"
- ST-6 - Screw Driver #1 Phillips
- ET-10 - IC Puller
- SP-2 - Solder Pump
- ST-20 - Safety Goggles
- ST-3 - Pocket Screw Driver
- ST-4 - Solder Tube
- SW-3 - Solder Wick

A professional technician service tool kit in a metal reinforced tool case with heavy-duty handle and locks. A removable pallet handles most of the tools listed with more room for tools and parts in the lower half.

**FREE PROBES
WITH ALL
SCOPES**

OSCILLOSCOPES

Lowest Prices of the Year!

CALL OR WRITE FOR
A FREE 60 PAGE
CATALOG!
(800) 445-3201

B&K Precision Scopes

60MHz ANALOG WITH DIGITAL STORAGE

Model 2560



\$1995

20MHz ANALOG WITH DIGITAL STORAGE

Model 2522A



\$869.95

100MHz THREE-TRACE

Model 2190A



\$1379.95

60MHz DUAL-TRACE

Model 2160A



\$949.95

40MHz DUAL-TRACE

Model 1541C



\$695

60MHz, CURSORS & READOUTS, DUAL TIME BASE

Model 2260



\$1225

20MHz DUAL-TRACE

Model 2120 - 2 Year Warranty

Special \$389.95

Model 2125 with delayed sweep

\$539.95

- 1mV/division sensitivity
- AUTO/NORM trigger sweep operation
- AC, TVH, TVV and line coupling
- Calibrated 19 step time-base with x10 magnifier
- Compact low-profile design

Affordable Spectrum Analyzers by B&K

500MHz Series


Model 2615 - \$1595

Model 2620 w/ tracking generator - \$1895

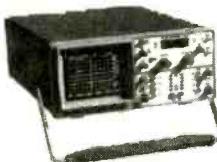1.05GHz Series

Model 2625 - \$2395

Model 2630 w/ tracking generator - \$2995



HURRY... AT PRICES THIS LOW THEY'LL BE GONE FAST! HITACHI SCOPES Inventory Reduction Sale Lowest Prices of the Decade!

V-209 - 20MHz Battery Operated Was \$1505, NOW \$1095 Save \$410	V-695 - 60MHz w/ Cursors Was \$1815, NOW \$1395 Save \$420
V-422 - 40MHz Was \$965, NOW \$765 Save \$200	V-1065A - 100MHz w/ Cursors Was \$2139, NOW \$1565 Save \$574
V-525 - 10MHz w/ Cursors Was \$1355, NOW \$955 Save \$400	V-1560 - 100MHz Was \$1790, NOW \$1490 Save \$300
V-552 - 50MHz Was \$1195, NOW \$850 Save \$345	V-1565 - 100MHz w/ Cursors Was \$1960, NOW \$1595 Save \$365
V-555 - 50MHz w/ Cursors Was \$1375, NOW \$975 Save \$400	V-252 - 20MHz \$419

WE WILL NOT BE UNDERSOLD

C&S SALES, INC.

150 W. CARPENTER AVENUE

WHEELING, IL 60090

FAX: (847) 520-9904 (847) 541-0710

http://www.elenco.com/cs_sales/

CIRCLE 308 ON FREE INFORMATION CARD

Fluke Scopemeters



91	\$1225
92B	\$1445
96B	\$1695
97	\$1795
97A	\$2945
99B	\$2095

Call or write for
complete specs.

15 DAY MONEY BACK GUARANTEE

FULL FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents Add 8% Tax



- PRODUCT ENGINEERING
- FIRMWARE DEVELOPMENT

- MICRO CONTROLLER & EPROM HARDWARE & SOFTWARE DEVELOPMENT

**"QUALITY
IS OUR
CAPITAL
CONCERN."**

Complete On Site Electrical Engineering Lab

- REVERSE ENGINEERING
- RF CIRCUIT DESIGN & MANUFACTURING

From Auto-Routing to CNC Routing to Electronic Assemblies...
Capital Electronics is Your Best Route For Printed Circuit Boards.

DESIGN/LAYOUT

- CAD LAYOUT SERVICES
- COMPATIBLE WITH ALMOST ALL CAD SYSTEMS
- FROM SCHEMATICS OR SAMPLE PCB'S
- PHOTOPLOTTING SERVICES
- 28,800 BAUDE MODEM

PRINTED CIRCUIT BOARDS

- SINGLE & DOUBLE SIDED
- MULTI-LAYER & FLEXIBLE PCB'S
- FROM QUICK TURN PROTOTYPES TO SCHEDULED PRODUCTION RUNS
- FINE LINES, SMT
- ELECTRICAL TESTING
- PRECIOUS METAL PLATING

ASSEMBLY SERVICES

- FAST TURN BOARD STUFFING
- WIRE HARNESSES
- WAVE SOLDERING
- ACQUISITION OF PARTS
- FINAL TESTING
- TURNKEY SERVICES
- CUSTOM ENCLOSURES

*For Quick & Competitive Pricing or More Information,
Please Call Us Today!*

852 Foster Avenue • Bensenville, IL 60106

(708) 350-9510

Fax (708) 350-9760 • Modem (708) 350-9761

Internet Access:

For Automated Info Response:
INFO@capital-elec.com

E-Mail: Quote@capital-elec.com

Web Access: http://www.capital-elec.com

CIRCLE 332 ON FREE INFORMATION CARD

Radiotelephone - Radiotelegraph **FCC** Commercial License

Why Take Chances?

Discover how easy it is to pass the exams.

Study with the most current materials available. Our Homestudy Guides, Audio, Video or PC "Q&A" disks make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine,

Radar, Microwave, New Rules & Regs, Digital Circuitry & more. We feature the Popular "Complete Electronic Career Guide". 1000's of satisfied customers Guarantee to pass or money back. Newest Q&A pools.

Send for FREE DETAILS or call

1-800-800-7588

WPT Publications
4701 N.E. 47th St.
Vancouver, WA 98661

Name _____

Address _____

City _____ St. _____ Zip _____

1-800-800-7588

CONTROL RELAYS • LIGHTS • MOTORS MEASURE TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY INPUT SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

MODEL 30 \$79



- PLUGS INTO PC BUS
- 24 LINES DIGITAL I/O
- 8 CHANNEL-8 BIT A/D IN
- 12 BIT COUNTER
- UP TO 14K BMP/SEC

MODEL 45 \$189




- RS-232 INTERFACE
- 8 DIGITAL I/O
- 2 ANALOG INPUTS
- 2 ANALOG OUTPUTS
- 2 COUNTERS-24 BIT

MODEL 100 \$279



- 12 BIT 100 KHZ A/D
- 4 ANALOG OUTPUTS
- 3 TIMER COUNTERS
- 24 DIGITAL I/O

MODEL 60 \$179

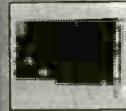

- 8 AMP RELAY
- 16 DIGITAL I/O
- 1 8-BIT ANALOG INPUT

MODEL 40 \$99



- RS-232 INTERFACE
- 28 LINES DIGITAL I/O
- 8 ANALOG INPUTS
- PWM OUTPUT
- OPTIONAL 12 BIT A/D

MODEL 70 \$239



- RS-232 INTERFACE
- 16 BIT A/D
- 8.5 DIGIT
- UP TO 60 BMP/SEC

NEED A CUSTOM PCB? TRY US.

PRAIRIE DIGITAL, INC.

PHONE 608-643-8599 • FAX 608-643-6754

846 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53573


CIRCLE 321 ON FREE INFORMATION CARD

Synthesized FM Stereo Transmitter



Microprocessor controlled for easy freq programming using DIP switches, no drift, your signal is rock solid all the time - just like the commercial stations. Audio quality is excellent, connect to the line output of any CD player, tape deck or mike mixer and you're on-the-air. Foreign buyers will appreciate the high power output capability of the FM-25; many Caribbean folks use a single FM-25 to cover the whole island! New, improved, clean and hum-free runs on either 12 VDC or 120 VAC. Kit comes complete with case set, whip antenna, 120 VAC power adapter - easy one evening assembly.

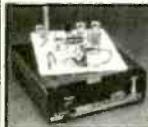FM-25, Synthesized FM Stereo Transmitter Kit \$129.95



Tunable FM Stereo Transmitter

A lower cost alternative to our high performance transmitters. Offers great value, tunable over the 88-108 MHz FM broadcast band, plenty of power and our manual goes into great detail outlining aspects of antennas, transmitting range and the FCC rules and regulations. Connects to any cassette deck, CD player or mixer and you're on-the-air, you'll be amazed at the exceptional audio quality! Runs on internal 9V battery or external power from 5 to 15 VDC, or optional 120 VAC adapter. Add our matching case and whip antenna set for a nice finished look.

FM-10A, Tunable FM Stereo Transmitter Kit \$34.95

CFM, Matching Case and Antenna Set \$14.95

RF Power Booster Amplifier



Add some serious muscle to your signal, boost power up to 1 watt over a frequency range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM Stereo transmitters, providing radio service through an entire town. Power required: 12 to 15 volts DC at 250mA, gain of 3dB at 10 MHz, 10 dB at 1000 MHz. For a neat, professionally finished look, add the optional matching case set!

LPA-1, Power Booster Amplifier Kit \$39.95

CLPA, Matching Case Set for LPA-1 Kit \$14.95

LPA-1WT, Fully Wired LPA-1 with Case \$99.95



Micro FM Wireless Mike

World's smallest FM transmitter. Size of a sugar cube! Uses SMT (Surface Mount Technology) devices and mini electret condenser microphone, even the battery is included. We give you two complete sets of SMT parts allowing for any errors or mishaps built it carefully and you've got extra SMT parts to build another! Audio quality and pick-up is unbelievable, transmission range up to 300 feet, tunable to anywhere in standard FM band 88 to 108 MHz. 7/8" w x 3/8" h x 3/4" h.

FM-5 Micro FM Wireless Mike Kit \$19.95

Crystal Controlled Wireless Mike



Super stable, drift free, not affected by temperature, metal or your body! Frequency is set by a crystal in the 2 meter Ham band of 146.535 MHz, easily picked up on any scanner radio or 2 meter rig. Changing the crystal to put frequency anywhere in the 140 to 160 MHz range crystals cost only five or six dollars. Sensitive electret condenser mike picks up whispers anywhere in a room and transmit up to 1/4 mile. Powered by 3 volt Lithium or pair of watch batteries which are included. Uses the latest in SMT surface mount parts and we even include a few extras in case you sneeze and loose a part!

FM-6, Crystal Controlled FM Wireless Mike Kit \$39.95

FM-6WT Fully Wired FM-6 \$69.95

Call for our Free Catalog !

RAMSEY

Super Pro FM Stereo Radio Transmitter



A truly professional frequency synthesized FM Stereo transmitter station in one easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features

we've packed into the FM-100. Set frequency easily with the Up/Down freq buttons and the big LED digital display. Plus there's input low pass filtering that gives great sound no matter what the source (no more squeals or swishing sounds from cheap CD player inputs!) Peak limiters for maximum 'punch' in your audio - without over modulation, LED bargraph meters for easy setting of audio levels and a built-in mixer with mike and line level inputs. Churches, drive-ins, schools and colleges find the FM-100 to be the answer to their transmitting needs, you will too. No one offers all these features at this price! Kit includes sharp looking metal cabinet, whip antenna and 120 volt AC adapter. Also runs on 12 volts DC.

We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

FM-100, Professional FM Stereo Transmitter Kit \$299.95

FM-100WT, Fully Wired High Power FM-100 \$429.95

Speech Descrambler Scrambler

Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. The technology used is known as speech inversion which is compatible with most cordless phones and many police department systems, hook it up to scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC, RCA phone type jacks. Our matching case set adds a super nice professional look to your kit.

SS-70A, Speech Descrambler/Scrambler Kit \$39.95

CSS, Custom Matching Case and Knob Set \$14.95

SS-70AWT, Fully Wired SS-70A with Case \$79.95

AC12-5, 12 Volt DC Wall Plug Adapter \$9.95

Tone-Grabber Touch Tone Decoder / Reader



Dialed phone numbers, repeater codes, control codes, anywhere touch

tones are used, your TG-1 will decode and store any number it hears. A simple hook-up to any radio speaker or phone line is all that is required, and since the TG-1 uses a central office quality decoder and microprocessor, it will decode digits at virtually any speed! A 256 digit non-volatile memory stores numbers for 100 years - even with the power turned off, and an 8 digit LED display allows you to scroll through anywhere in memory. To make it easy to pick out numbers and codes, a dash is inserted between any group or set of numbers that were decoded more than 2 seconds apart. The TG-1 runs from any 7 to 15 volt DC power source and is both voltage regulated and crystal controlled for the ultimate in stability. For stand-alone use add our matching case set for a clean, professionally finished project. We have a TG-1 connected up here at the Ramsey factory on the FM radio. It's fun to see the phone numbers that are dialed on the morning radio show!

Although the TG-1 requires less than an evening to assemble (and is fun to build, too!), we offer the TG-1 fully wired and tested in matching case for a special price.

TG-1, Tone Grabber Kit \$99.95

CTG, Matching Case Set for TG-1 Kit \$14.95

TG-1WT, Fully Wired Tone Grabber with Case \$149.95

AC12-5, 12 Volt DC Wall Plug Adapter \$9.95



Mini-Peeper Micro Video Camera

Super small, high quality fully assembled B & W CCD TV camera the size of an ice cube! Provides excellent pictures in low light (2 lux), or use our IR-1 Infra-Red light source to invisibly illuminate an entire room on a pitch black night! Imagine the possibilities... build it into a smoke detector, wall clock, lamp, book, radio. Exact same camera that's in big buck detective catalogues and stores. Kit includes: fully assembled CCD camera module, connectors, interface PC board kit with proper voltage regulation and filtering, hook-up details, even a mini microphone for sensitive sound! Two models available: Wide Angle Lens 3.6mm/4.5, adjustable focus lens, 92 degree view; Pinhole Lens 5.5mm/4.5, 60 degree view. The Pinhole Lens is physically much flatter and provides even greater depth of focus. The camera itself is 1.2" square. The Wide Angle Lens is about 1" long, Pinhole Lens about 1/2", interface PC board is 1" x 2" and uses RCA jacks for easy hook-up to VCRs, TVs or cable runs. Power required is 9 to 14 VDC @ 150 mA. Resolution: 380 x 350 lines. Instruction manual contains ideas on mounting and disguising the Mini-Peeper along with info on adding one of our TV Transmitter kits (such as the MTV-7 unit below) for wireless transmission!

MP-1, Wide Angle Lens CCD TV Camera Outfit \$169.95

MP-1PH, Pin-Hole Lens CCD TV Camera Outfit \$189.95

MicroStation Synthesized UHF TV Transmitter



You now can be in the same league as James Bond. This transmitter is so small that it can fit into a pack of cigarettes - even including a CCD TV camera and battery! Model airplane enthusiasts put the MTV-7A into airplanes for a dynamic view from the cockpit, and the MTV-7A is the transmitter of choice for balloon launches. Transmitter features synthesized, crystal controlled operation for drift-free transmission of both audio and video on your choice of frequencies: Standard UHF TV Channel 52 (which should only be used outside of the USA to avoid violating FCC rules), and 439.25 MHz or 911.25 MHz which are in the amateur ham bands. The 439.25 MHz unit has the nifty advantage of being able to be received on a regular 'cable-ready' TV set tuned to Cable channel 68, or use our ATV-74 converter and receive it on regular TV channel 3. The 911.25 MHz unit is suited for applications where reception on a regular TV is not desired, an ATV-79 must be used for operation. The MTV-7A's output power is almost 100 mW, so transmitting range is pretty much 'line-of-sight' which can mean many miles! The MTV-7A accepts standard black and white or color video and has its own, on-board, sensitive electret microphone. The MTV-7A is available in kit form or fully wired and tested. Since the latest in SMT (Surface Mount Technology) is used to provide for the smallest possible size, the kit version is recommended for experienced builders only. Runs on 12 VDC @ 150 mA and includes a regulated power source for a CCD camera.

MTV-7A, UHF TV Channel 52 Transmitter Kit \$159.95

MTV-7AWT, Fully Wired Channel 52 Transmitter \$249.95

MTV-7A4, 439.25 MHz TV Transmitter Kit \$159.95

MTV-7A4WT, Fully Wired 439.25 MHz Transmitter \$249.95

MTV-7A9, 911.25 MHz TV Transmitter Kit \$179.95

MTV-7A9WT, Fully Wired 911.25 MHz Transmitter \$269.95

ATV-74, 439.25 MHz Converter Kit \$159.95

ATV-74WT, Fully Wired 439.25 MHz Converter \$249.95

ATV-79, 911.25 MHz Converter Kit \$179.95

ATV-79WT, Fully Wired 911.25 MHz Converter \$269.95

RAMSEY ELECTRONICS, INC.

793 Canning Parkway

Victor, NY 14564

Order Toll-free: 1-800-446-2295

Sorry, no tech info or order status at this number

Technical Info, Order Status

Call Factory direct: (716) 924-4560



ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$4.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.



Cellular Extensions

from
"THE CELLULAR EXPERTS"

Motorola 3 Watt Bag from \$225.

Nec P120 12oz. Portable \$299.

Motorola PT 550 10oz. "Flip" Phone \$399.

Nation
WIDE
Paging

Others available, buy new from us, or send us your phone.
Get a second or third phone with no additional monthly charges!
Motorola, NEC, Panasonic, Audiovox and many others!

Fax Back Hotline, For 24hr. info. call from your FAX (714) 581-7460 or call


(800) 457 - 4556

Nationwide paging available. C.G.C. Dealer Inquiries welcome.

LASERS & ACCESSORIES


WE SPECIALIZE IN
*Laser and Laser
Related Surplus
Inventory*

HENE LASERS

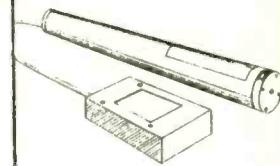


- Complete Systems
- Plasma Tubes
- Power Supplies

DIODE LASERS

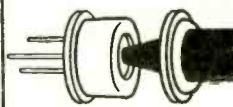

- Visible I/R
- Complete Modules
- Collimating Optics
- Drive Circuits

ACCESSORIES

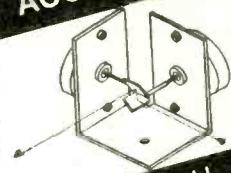

- Books
- Optics
- Electro-Optics

CALL FOR A FREE CATALOG!

We want your Laser related surplus items. Call or Fax us today for a quote!

MEREDITH INSTRUMENTS

P O Box 1724
5035 N. 55th Ave. #5
Glendale, AZ 85301

Phone: 602-934-9387
Fax: 602-934-9482

[HTTP://WWW.MI-LASERS.COM](http://WWW.MI-LASERS.COM)

Move Up to the Ultimate in Robotic Kits.

OWIKIT™



OWI's "Next Generation" of affordable, rugged Robot Kits challenge the enthusiast to solder circuit boards and mechanically assemble.

Visit our homepage @
<http://www.owirobot.com>

Each OWIKIT also incorporates the basic principles of robotic experiments, sensing and locomotion, guaranteeing an exciting, hands-on adventure of knowledge and fun!

But remember! OWI is the recognized founder and leader in Educational Robot Kits. ACCEPT NO IMITATIONS.

EDUCATORS • HOBBISTS • ENGINEERS

EK
ELEKIT

1160 Mahalo Place, Suite B
Rancho Dominguez, CA
90220-5443

(310) 638-7970

Fax: (310) 638-8347



Order M-F: 8am - 4pm PST

NEW


ROBOT.TECH.CURR.	MV-RTC	Teacher's Manual	158 Pg. Book	74.95
ELECTRO-MAGNETIC TRAIN				14.95
S-CARGO	OWI-936K	Sound Sensor	47 Pg. Book	29.95
WAO II	OWI-961K	Programmable - Graphic	59 Pg. Book	69.95
SPIDER	OWI-962K	Infrared Sensor	49 Pg. Book	49.95
LINE TRACKER	OWI-963K	Infrared Sensor	48 Pg. Book	49.95
MANTA	OWI-966K	Sound / Touch Sensor	44 Pg. Book	29.95
MOON WALKER	OWI-989K	Solar Sensor	10 Pg. Book	34.95

CIRCLE 322 ON FREE INFORMATION CARD

**TURN YOUR PC INTO A
DIGITAL STORAGE
OSCILLOSCOPE!**

The PC-MultiScope by mission technology

Featured in May '96 Electronics Now!

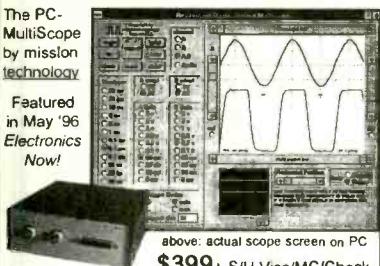

above: actual scope screen on PC
\$399+ S/H/Visa/MC/Check

Dual channel; up to 20Ms/sec sampling; 2Mhz analog bandwidth; install thru PC parallel port; easy Windows interface; strip chart recorder/spectrum analyzer modes; ext. trig. +\$40; VB source code +\$99

AMAZE ELECTRONICS CO.

Tel: 800-996-2008 Fax: 408-996-0366

<http://www.hooked.net/users/amaze>
or email: amaze@hooked.net



Restores Horizontal and Vertical Sync Lines from Distorted Analogue Video Formats

For Free Information Package on Completed Units and Pricing

- Call Toll Free •
1-800-236-5778

R.C. Distributing • PO Box 552 • South Bend, IN 46624

CELLULAR PROGRAMMERS!

COPYCAT MOTOROLA CELLULAR PROGRAMMER: program any Motorola Phone up to 95IC. Complete Assembly: \$999

COPYCAT KIT ONLY (unassembled complete with instructions): \$750

ERICSON CLIP (program through the keypad): \$350

OKI 900 modified (up to 5 numbers programmed in): \$400

OKI CHIP only: \$75

Also different programs available for all brands!
FOR DEALERS ONLY MASTER FILES AVAILABLE

DISCOUNT FOR QUANTITIES.

PH: 718-575-1474 718-768-4963

Fax: 718-369-3989

E MAIL: 104170.3043@COMPUSERVE.COM

CABLE TV CONVERTERS

Equipment & Accessories
Wholesalers Welcome

Call C&D ELECTRONICS

1-800-310-1153 M-F 10a-8p



Quality Microwave TV Systems

**WIRELESS CABLE - ITFS - MMDS
ATV - INTERNATIONAL - S-BAND**
Amplifiers • Antennas • Books • Components
Filters • Systems • Video Products

- RF Frequency 1990 - 2700 MHz
- Cable Ready - VHF - UHF Outputs
- SASE For "FREE" Catalog or Send \$1

PHILLIPS-TECH ELECTRONICS

PO Box 8533 • Scottsdale, AZ 85252

ORDER LINE 800-880-MMDS

CATALOG / INFO 602-947-7700

FAX LINE 602-947-7799

Visa • M/C • Amx • Disc • COD's • Qty Pricing


CIRCLE 310 ON FREE INFORMATION CARD

INSTOCK

quality \kwl - st - \ noun

- An inherent and essential feature or element: exhibiting a degree of excellence and superiority.
syn. see Mouser Electronics

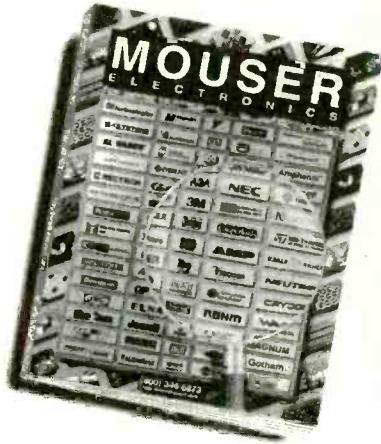Call for your
FREE 332
page catalog
TODAY!



67,092 Products

126 Manufacturers

All Orders Ship Same Day

- Passive Components ■ Semiconductors
- Electromechanical ■ Connectors/Cable
- Surface Mount and Through Hole

**MOUSER®
ELECTRONICS**

958 North Main St., Mansfield, TX 76063

800-346-6873

FAX: 817-483-0931

<http://www.mouser.com>
sales@mouser.com

PC-Based 6MHz Sweep/Function Generator

\$549

- Wide frequency range from 0.2Hz to 6 MHz
- Sine, square, triangular output waveforms plus sweep function
- 3 operating modes: sweep, gated burst and voltage control frequency
- Designed and made in USA

Turn your PC into a test station with :

Dual 100 MHz Universal Counter	\$399
60 MHz Digital Storage Scope	\$749
100 MHz Digital Storage Scope	\$999

TC INSTRUMENTS INC.®

Tel: (909) 622-2006
Fax: (909) 622-7778
<http://www.tcinst.com>



**ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 30 DAY WARRANTY**

WE BUY TEST EQUIPMENT AND COMPONENTS.

TEK 7A13 DIFFERENTIAL COMPARATOR	\$150.00	TEK 7B15 1 GHZ DELAYING TIME BASE	\$250.00
TEK 7A16 PROG.200MHZ VERT.AMPLIFIER	\$75.00	TEK 7B50A 150 MHZ TIME BASE	\$75.00
TEK 7A17 150 MHZ SINGLE TRACE AMPLIFIER	\$50.00	TEK 7B52 DUAL TIME BASE	\$75.00
TEK 7A18 75 MHZ DUAL TRACE AMPLIFIER	\$50.00	TEK 7B53 100 MHZ DUAL TIME BASE	\$75.00
TEK 7A19 600 MHZ SINGLE TRACE AMPLIFIER	\$150.00	TEK 7B70 200 MHZ TIME BASE	\$75.00
TEK 7A22 DIFFERENTIAL AMPLIFIER	\$200.00	TEK 7B71 DELAYING TIME BASE	\$75.00
TEK 7A24 400 MHZ DUAL TRACE AMPLIFIER	\$200.00	TEK 7B80 400 MHZ DELAYED TIME BASE	\$100.00
TEK 7A26 200 MHZ DUAL TRACE AMPLIFIER	\$75.00	TEK 7B85 400 MHZ DELAYING TIME BASE	\$125.00
TEK 7D11 DIGITAL DELAY UNIT	\$50.00	TEK 7B90P PROGRAMABLE TIME BASE	\$200.00
TEK 7D12 A/D CONVERTER MAINFRAME	\$50.00	TEK 7B92A 500 MHZ DELAYING TIME BASE	\$125.00
TEK 7D13 DIGITAL MULTIMETER	\$50.00	TEK AM302 DIFFERENTIAL AMPLIFIER	\$75.00
TEK 7M11 DUAL 50 OHM DELAY LINE	\$100.00	TEK MX5010 MULTIFUNC.INTERFACE EXTN.	\$200.00
TEK 7M13	\$50.00	TEK 7834 400 MHZ STORAGE MAIN FRAME	\$400.00
TEK 7S11 SAMPLING PLUG IN	\$200.00	TEK 7844 400 MHZ MAIN FRAME	\$400.00
TEK 7S12 GENERAL PURPOSE SAMPLER	\$350.00	TEK 7854 400 MHZ DIGITAL STORAGE FRAME	\$500.00
TEK 7S14 1 GHZ SAMPLING PLUG IN	\$350.00	TEK 7904 500 MHZ MAIN FRAME	\$250.00
TEK PS5010 PROG.TRIPLE POWER SUPPLY	\$250.00	TEK 7104 1GHZ FRAME WITH-	\$2750.00
TEK 485 350 MHZ PORTABLE SCOPE	\$600.00	(TA29,TA29,7B10,7B15)	
KEITHLEY 480 PICOAMMETER	\$300.00	TEK 2235 100MHZ OSCILLOSCOPE	\$650.00
LEADER LBO516 100MHZ OSCILLOSCOPE	\$300.00	TEK 2246 100MHZ OSCILLOSCOPE	\$1200.00
GENRAD 1657 RLC BRIDGE	\$750.00	GENRAD 1658 RLC BRIDGE	\$900.00
SENCOR LCS3 CAP-IND. METER	\$400.00	TEK 608 MONITOR	\$650.00
FLUKE 8505A 6.5 DIGIT DMM	\$250.00	TEK 577 DI/177 CURVE TRACER	\$1500.00
TEK DA8910 WITH PROBES	\$750.00	HP 1651 LOGIC ANALYZER	\$1200.00
TEK 7D20 PROGRAMABLE DIGITIZER	\$500.00	HP 8012A PULSE GENERATOR	\$400.00
FLUKE 343A DC VOLTAGE CALIBRATOR	\$750.00	BRADLEY 192 O-SCOPE CALIBRATOR	\$750.00
TEK 453 50 MHZ OSCILLOSCOPE	\$200.00	TEK 475 200 MHZ OSCILLOSCOPE	\$500.00
AVCOM PSA-35A SPECTRUM ANALYZER	\$1000.00	LEADER LBO516 100 MHZ OSCILLOSCOPE	\$300.00
SENCORE LCS3 CAP-IND. METER	\$400.00	RACAL-DANA 1991 160 MHZ COUNTER	\$300.00
EMI SCR300-3 POWER SUPPLY	\$300.00	TEK 608 MONITOR	\$650.00
HP 141T/8553B/8552B SPECTRUM ANALYZER	\$1500.00	HP 8601 110 MHZ SWEEP/SIGNAL GEN.	\$350.00

Invest a stamp...Save a bundle

For the price of a stamp, you can get the latest edition of the federal government's free Consumer Information Catalog. It lists more than 200 free or low-cost publications on federal benefits, jobs, health, housing, education, cars, and more.

So stamp out ignorance with our free Catalog. Send your name and address to:
Consumer Information Center, Department SB, Pueblo, Colorado 81009

Cable TV Descramblers

Converters * Filters * Accessories

Free Catalog

30 day Free Trial! NO RISK!

Unbeatable wholesale prices!

Affordable extended warranty

1 Year Warranty on all products

Call the cable professionals!

Credit Cards Welcome!

1-800-379-3976

Ori
on Electronics

Prices starting
as low as **\$99!**

New Surveillance Devices !

SMOKE ALARM Ultra miniature video cameras hidden in smoke and Table Clock alarm clock - your choice. Wide field of view Video Cameras and super .1 lux low light sensitivity! Undetectable!

SC-600

TC-70 High quality B/W with 420 lines of resolution for ultra sharp images.

\$219.95 ea.

THR-12

High quality cassette deck plugs directly into telephone jack!

12 Hour

Records up to 12 hours of conversations on a single cassette.

Telephone

Recorder \$99.95 Free shipping! Check/Money orders also accepted

Seymor-Radix Inc.

Box 166055-N Irving,TX 75016

Now you can visit us on the Internet at: <http://www.wny.net/home/sr>

MULTI FREQUENCY CUBES!

WIRELESS CABLE BOX TESTER

EXTERNAL AND INTERNAL MULTI-FREQUENCY WORKS ON ALL MODELS: J****, SA, PIONEER, ALSO FOR CFT 2200!

WORKS EVERYWHERE.

AUTOMATIC FREQUENCY FINDER!

60 DAYS WARRANTY

QUANTITY DISCOUNT AVAILABLE

DEALERS WELCOME!

PH: 718-575-1474 718-768-4963

Fax: 718-369-3989

E MAIL: 10417.3043@COMPUSERVE.COM

AMEX, MO & COD

Pocket cube is a test generator only

CABLE TV CONVERTERS

Equipment & Accessories
Wholesalers Welcome

Call C&D ELECTRONICS

1-800-310-1153 M-F 10a-8p

SURVEILLANCE

The Latest High Tech Professional Electronic Devices

Our latest catalog offers a **HUGE** selection of surveillance, privacy devices including: hidden video equipment, electronic kits, telephone recording systems, touch tone decoders, scanners, telephone tap detectors, bug detectors, voice disguisers, telephone scramblers, locksmithing tools, and more. Catalog \$5.00.

SPY OUTLET

P.O. Box 337, Buffalo, NY 14226
(716) 691-3476/(716) 695-8660

WE HAVE IT ALL!

Surveillance

Infinity Transmitters
FM Wireless Transmitter Kits
Vehicle Tracking Systems
Bug Detectors
Caller I.D.
Wired Mikes
Telephone Register with Printer
Long-play Recorders
Shotgun Mikes
Telephone Recording Adapters
Alcohol Testers
Telephone Scramblers
Hidden Video Cameras
Telephone Tap Detectors
Drug Testers
MUCH, MUCH, MUCH MORE.

Our 27th Year!

Small catalog FREE.

Larger catalog send \$5.

Mail Order only.

Visa, MasterCard and C.O.D. accepted.

Inquire for dealers' prices.

A.M.C. SALES, INC.193 Vaquero Dr. • Boulder, CO 80303
Mon.-Fri. 8 a.m.-5 p.m. Mtn. Time**800-926-2488**

(303) 499-5405 • Fax (303) 494-4924

**PHONE LINE
MANAGER****Better than Caller ID!**

This device detects an incoming call. If you subscribe to caller ID, the unit will automatically receive and display the caller's telephone number. If not, the unit will ask the caller to enter their telephone or personal ID number. The device will then display and compare this telephone or personal ID number to a memory bank of numbers that you've installed. If the system finds a match your phone will ring. If the system does NOT find a match, the caller will be directed to leave a message. All messages are digitally recorded. No tape or answering machine necessary. New, in factory cartons, with documentation.

96U001

\$59.95 each

UHF LINEAR AMPLIFIER

890 to 940 MHz. Gain: 17dB. Bias: 18V @ 100mA. Used in cellular communications equipment.

96V001

\$14.95 each

Send \$2.00 for our Latest Catalog!

\$4.00 Foreign. Refundable on First Order.

ALLTRONICS

2300-D Zanker Road • San Jose, CA 95131
Voice (408) 943-9773 • Fax (408) 943-9776
World Wide Web: <http://www.alltronics.com>
On-Line Ordering: (408) 943-0622
14400-N-8-1-24 Hrs

Shipping Additional on All Orders..

CABLE TV DESCRAMBLERS



We Carry A Full Line Of Premium Converters And Descramblers Compatible With:

- **Scientific Atlanta™ Systems**
- **Jerrold™ Systems**
- **Tocom™ Systems**
- **Zenith™ Systems**
- **Pioneer™ Systems**

**SATISFACTION GUARANTEED
OR YOUR MONEY BACK!****BEST PRICES FREE CATALOG**
Please have the MAKE & MODEL # of your full premium service cable box ready when you call**ALLSTAR ELECTRONICS****800-782-7214****HOURS: 9-6 M-F 10-3 Sat EST**

It is not the intent of Allstar Electronics to defraud any pay TV operator. Anyone implying theft of service will be denied assistance. All brand names are registered trademarks of their respective owners & are used for reference only. 110-64 Queens Blvd., #465, Forest Hills, NY 11375. NO NYS SALES!

Many Electronics inc
RFT, FTG, PIO-Supers,
Filters, FTG KIT's
800-716-3561 9-7est

BUGGED??



EAVESDROPPING is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations RIGHT NOW! Are you sure you're safe? **FREE CATALOG** tells you fast! Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and EXTREMELY profitable (up to \$250 hr) full/part-time income. Call Now! **1-800-732-5000**

Cable **Test**
Orders Only
1-800-615-9221 **407-998-7883**

Information
Test Chips that fully activate Jerrold, Tocom, Zenith, SA, Pioneer and more. Quick-Board installation!
Prices from \$5 to \$49.95 ea. MC SPECIALTIES
1 Year Warranty!
No FL Sales. Not for use in cable co. owned equip. For test or repair only.

MICRO SIZE CCD VIDEO CAMERAS

- Wireless Models Available.
- Color Board Cameras
- "Y" / "C" SVHS signal.
- Models to 600 Line Res.
- 9V Battery Operation.
- Monitor in Darkness with IR Option.
- Can be plugged into any VCR or Monitor.
- Stealth/Covert Cameras.
- Low Lux/Low Noise.
- Low Power Consumption.
- Standard NTSC Output.
- Options: Lenses/Wireless/Fiber Optics & More.

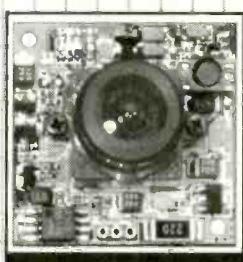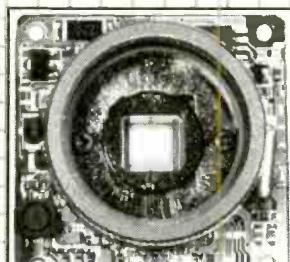**MB-750U (1.25" sq.)****MB-750UX (1.5" sq.)**

Visit Polaris Ind. Web Site at:
<http://www.polarisusa.com>

**MB-750P (1.25" sq.)**

Polaris Industries
1-800-752-3571

141 West Wieuca Road • Suite 300 • Atlanta GA • 30342-3251 • Tech Info: 404-252-3340 • FAX 404-252-8929

New Literature
Available for
All Models

Same Day
Shipping
from Stock!



New! Surveillance, & PIC microcontroller, project kits.

Most kits use surface mount technology. Among the kits are an ultra small wireless FM mic. and our new phone transmitter SLeach™. All kits include our exclusive surface mount soldering guide. Many kits under \$20, call!

Pager Decoder Interface for your PC, Only \$19.95 + S&H

Includes shareware software.

We carry the TDA2005 20W Power Amplifier IC. Great for auto alarm projects!

Order 1-800-417-6689

Mon. - Fri. 9AM-5PM ET.

Visa, MC, Money Orders
IEC, P O Box 52347, Knoxville, TN
37950-2347

Sorry, no refund for used kits.

Do not use these devices without authorization from your local officials.

Prices subject to change. No TN sales.

This ad quotes cash discount pricing.

Returns are subject to a restocking fee.

©1996 IEC

TRIDENT



\$699⁰⁰

SV150

**1000KHz to 1.00GHz
Spectrum Analyzer System
Up to 500MHz Span. Two bands.**

All the advantages of a Spectrum Analyzer at a very affordable price. Great for interference and signal hunting. RS232 connect for logging signals to disk. Real time display sweep outputs on any X,Y scope. Variable span and sweep rate. Marker function and selectable bandwidth. Demods in AM/NFM/WFM plus BFO for CW/SSB modes. For instant information use our fax back service at 317 849 8683, #405. Or, email Scanns@www.acecomms.com . http://www.acecomms.com/Scanns.



Order Line: 1 888 445 7717

10707 E. 106th, Fishers, IN 46038 International: 317 842 7115
Fax 317 849 8794 Email: Scanns@www.acecomms.com

CIRCLE 289 ON FREE INFORMATION CARD

CABLE CONVERTERS/DESCRAMBLERS

★ ★ ★ ★ SUPER BUYS ★ ★ ★ ★ ★ FULLY REFURBISHED UNITS ★

TOCOM™ ★ JERROL'D™ ★ SCIENTIFIC ATLANTA™ ★ PIONEER™
"WE SERVICE MOST PRIVATELY OWNED CABLE CONVERTERS"

Phone (219) 935-4128



SORRY, NO INDIANA SALES

NATIONAL CABLE BROKERS

1801 W. JEFFERSON ST., PLYMOUTH, IN 46563

OUR POLICY: All products carry a two year warranty. Warranty covers parts and labor and return shipping.

WARNING: Theft of cable services is a crime. National Cable will not knowingly defraud any pay TV operator and we will not assist any individual or company in doing the same.



LASERS

Pen & Pointer in One

- Four Times Brighter
- Mont Blanc™ Style Pen



This laser pointer functions as a fine writing instrument and laser pointer all in one. The 650nm laser appears four times brighter than standard laser pointers. Output power: 3.5 to 4.5 milliwatts. Includes batteries and gift box. One year warranty.

Cat. #: LPPEN

\$57.00

FREE CATALOG

30 Day Satisfaction Guarantee.

- | | |
|-----------------|-----------------------|
| • Helium-Neon | • Ruby |
| • Argon | • Scanners |
| • Semiconductor | • Lightshow Equipment |



Midwest Laser Products


Email: mlp@nlenx.com
VISA / MC Accepted

P.O. Box 262, Frankfort, IL 60423

Phone: (815) 464-0085 FAX: (815) 464-0767

Please include \$7.50 S&H within US. IL res. add 7.75% sales tax.

CONVERTERS & DESCRAMBLERS

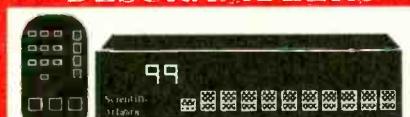

TARGET ELECTRONICS

(800) 995-1749

We sell Test Chips!
MC, VISA, AE, C.O.D

DEALERS
WELCOME!



One tree can make 3,000,000 matches.



One match can burn 3,000,000 trees.

The Electronic Experimenter's Journal

It's part catalog, part magazine and part data book with kits, parts, plans, articles, and application notes.

Call for your FREE copy today

Debco Electronics
4025 Edwards Rd.
Cincinnati, OH 45209



1 800 423-4499



A Public Service of This Magazine
& The Advertising Council





Electronic Training Videos From UCANDO

Now you can learn from the same training videos that are being used by technical schools, the Army, Navy, Air Force, Coast Guard, CET's and industries all across the United States and around the world. Advancing your troubleshooting skills has never been easier, thanks to UCANDO's extraordinary video training library. These unique training videos will teach you more in less time as you watch theory come to life. Each video is approximately one hour long and comes complete with a student workbook.



Basic Series

MODEL	DESCRIPTION	REGULAR	SALE
VT201	Direct Current: Series circuits, Parallel Circuits, Ohm's law, how to use the DMM. 55 Minutes	44.95	39.95
VT202	Alternating Current: The sine wave, coils, capacitors, transformers. 62 minutes	44.95	39.95
VT203	Semiconductors: Semiconductor theory, common diodes, transistors, switching devices. 57 Minutes	44.95	39.95
VT204	Power Supplies: Rectifier circuits, filter circuits, regular circuits, troubleshooting. 56 Minutes.	44.95	39.95
VT205	Amplifier: Amplifier basics, class A, class B, class C, operational amplifiers. 57 Minutes	44.95	39.95
VT206	Oscillators: LC and RC oscillators, crystal oscillators, crystal ovens. 56 Minutes	44.95	39.95

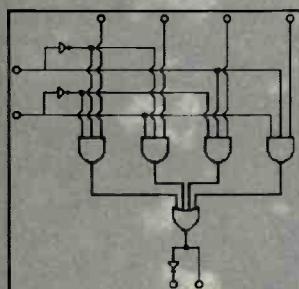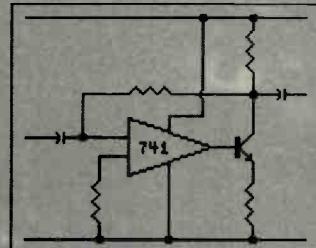


Digital Series

MODEL	DESCRIPTION	REGULAR	SALE
VT301	Digital 1: Digital basics, basic gates, binary notation, binary math, decimal notation. 54 Minutes	44.95	39.95
VT302	Digital 2: Octal notation, hexadecimal notation, flip-flops, counter circuits. 55 Minutes	44.95	39.95
VT303	Digital 3: Complement numbers, multiplexers, registers, decoder drivers, displays. 56 Minutes	44.95	39.95
VT304	Digital 4: R-2R DAC circuits, binary weighted no.s, slope circuits, S/A & flash circuits. 57 Minutes.	44.95	39.95
VT305	Digital 5: Memory devices, ROM, PROM, EPROM, EEPROM, SRAM, DRAM, MBM. 56 Minutes	44.95	39.95
VT306	Digital 6: The central processing unit, input devices, output devices. 56 Minutes	44.95	39.95

Other Popular Videos

MODEL	DESCRIPTION	REGULAR	SALE
VT401	AM Radio: Major stages of AM, signal conversion, signal detection, audio reproduction, AM stereo. 61 Minutes	44.95	39.95
VT402	FM Radio Part 1: Bandwidths, RF amplifier, mixer-oscillator, IF amplifier, limiter FM detector. 58 Minutes	44.95	39.95
VT403	FM Radio Part 2: Frequency doubler, stereo demultiplexer, audio amp stages, digital data encoding/decoding. 58 Minutes	44.95	39.95
VT404	TV Part 1, Intro to TV: Gain an overview of the television system and how the stages work together. 56 Minutes	44.95	39.95
VT405	TV Part 2, The Front End: UHF-VHF tuning stages, automatic fine tuning, remote control. 58 Minutes	44.95	39.95
VT406	TV Part 3, Audio: The sound strip, stereo TV, secondary audio programming, professional channels. 57 Minutes	44.95	39.95
VT501	Understanding Fiber Optics: Basic fundamentals, cable design, connectors, couplers, splicing. 58 Minutes	44.95	39.95
VT502	Laser Technology: Laser theory, types of lasers, applications, safety precautions. 57 Minutes	44.95	39.95
VT102	Intro to VCR Repair: This video is designed for the serious technician. (workbook not available). 84 Minutes	44.95	39.95
VT103	Learn How To Clean Your Own VCR: This video is not technical, but will save you money. (workbook not available). 32 Minutes	29.95	25.95

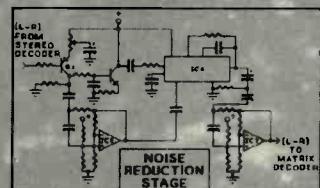

SAVE EVEN MORE!
Buy any six videos for only \$216.00. Order your UCANDO videos today!




PRINT™
Products International

Call for your free 84 page test instrument catalog today!!!
8931 Brookville Road * Silver Spring, Maryland * 20910

* Phone 800-638-2020 * Fax 800-545-0058 * email SMPRODINTL@AOL.com

CIRCLE 264 ON FREE INFORMATION CARD

Fix It Yourself!

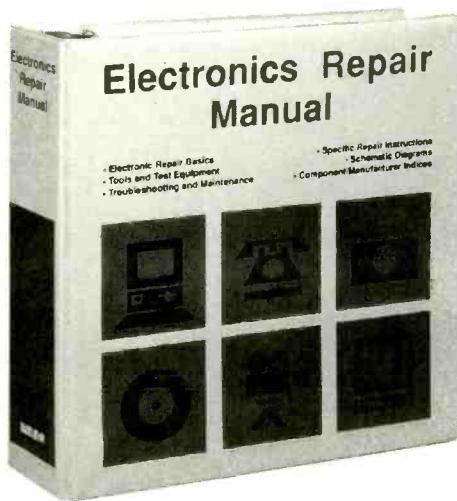

It's easy, fast, and rewarding to repair it yourself with the Electronics Repair Manual!

✓ Dozens of Fix-It-Yourself Projects for...

- CD Players
- VCRs
- Televisions
- Camcorders
- Computer Equipment
- Fax Machines
- Telephones

- Amplifiers
 - Car Radios
 - Home Appliances
 - AM/FM Tuners
 - Thermostats
- ...and more!**

Keep Your Skills Up-to-Date!

The Electronics Repair Manual and the Modern Manual Electronics Manual will be a valuable reference for years to come. Supplements, each containing over 125 pages, add new repair projects, valuable insights into new technologies, diagnostic and repair techniques, electronics projects, and more schematic diagrams into your manual. Just \$35 each for Electronics Repair and \$49.50 each for Modern Electronics plus shipping and handling. Supplements are sent 4-5 times a year and are fully guaranteed. Return any supplements you don't want within 30-days and owe nothing. Cancel anytime.

3

CIRCLE 311 ON FREE INFORMATION CARD


Leading Manufacturers Represented...

- Emerson • Nintendo • RCA • Technics
- Hitachi • Panasonic • Sanyo • Toshiba
- IBM • Pioneer • Sharp • Zenith
- NEC • Quasar • Sony and others!


**30-Day
Free
Trial!**



Build It Yourself!

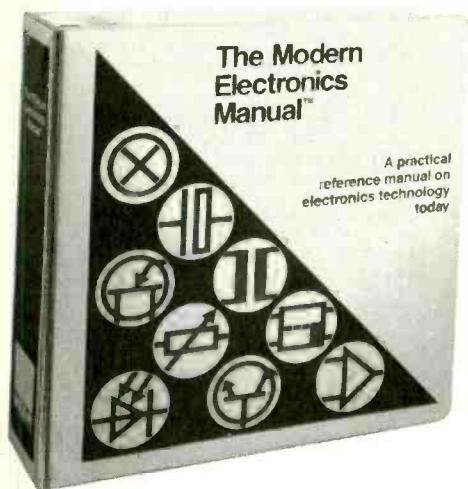

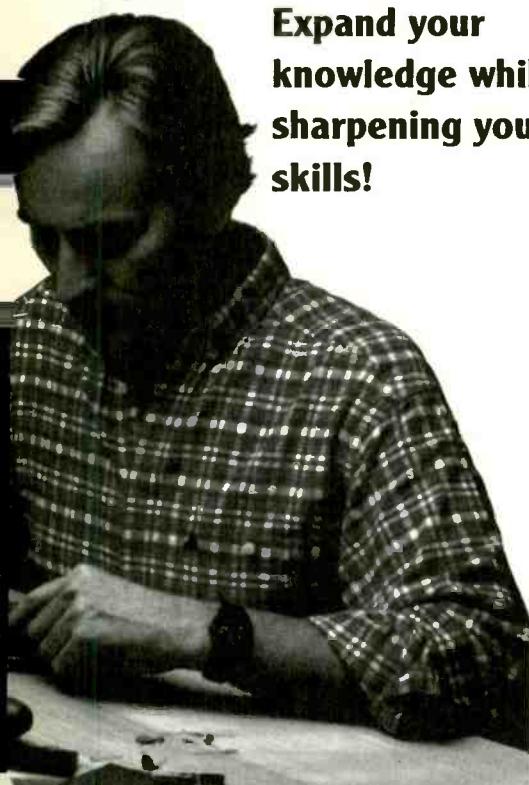Expand your knowledge while sharpening your skills!



✓ Dozens of Exciting Projects such as...

- Simple Logic Probe
 - Multi-Purpose Gas Detector
 - Digital Combination Lock
 - Radiation Detector
 - Portable Frequency Counter
- ...and many other projects!

- A lifetime of exciting electronics projects
- Complete project plans
- Step-by-step instructions, flow charts, schematics, and photos
- Troubleshoot and repair
- Make your own printed circuit board (acetate board layouts provided)
- Component suppliers' addresses
- Handy 3-ring workbench binder

Electronics Fundamentals...

- Electronic Components and their Characteristics
 - The Op-Amp Explained
 - General Diagnostic Techniques
- ...plus much more!

30 Day Free Trial Order Form

- Yes! Please rush me my copy of:
- Electronics Repair Manual for only \$59.95 32856
- Modern Electronics Manual for only \$59.95 32857
- Both Manuals for just \$99.95. 32858

I may take \$10 off the total price when I enclose my check or credit card authorization by 12/31/96. Plus, I get free shipping and handling! I understand that if I am not satisfied, I may return the book(s) within 30 days for a full 100% refund of the purchase price.

My payment is enclosed. I've deducted \$10 if I am ordering by 12/31/96.

No. Exp.

Check Enclosed.

Optional express delivery (available in U.S. only).

Enclose an additional \$10 and we'll guarantee delivery within 5 business days from receipt of your order (prepaid orders only; no P.O. Boxes).

Bill me later including \$6.50 shipping and handling per book, subject to credit approval. *Signature and phone number required to process your order. P.O. Box addresses must be prepaid.*

Signature (required) _____

Daytime phone () _____

Mr./Mrs./Ms. _____

Company _____

Street Address _____

City _____ State _____ Zip _____

Shipping and handling to Canada, \$10 (U.S. Currency); Overseas, \$15 (foreign orders must be prepaid); CT residents add 6% sales tax. Supplements will be sent 4-5 times a year on a fully guaranteed, 30-day trial basis. They may be cancelled at any time.

MAIL TO: WEKA Publishing, Inc.

1077 Bridgeport Avenue, P.O. Box 886, Shelton, CT 06484

Call 1-800-222-WEKA or fax to 1-800-256-5915 for fast service!

CIRCLE 311 ON FREE INFORMATION CARD

MONDO • TRONICS

ROBOT STORE

* KITS *

Your

* BOOKS *

Mailorder

* PARTS *

Source

* VIDEOS *

For

* MODELS *

Robots!

* MORE! *

(REQUEST OUR FREE CATALOG)

WWW.ROBOTSTORE.COM

800-374-5764

Or write to us:

524 San Anselmo Ave #107-120
San Anselmo CA 94960

Phone 415-455-9330

Fax 415-455-9333

Email info@mando.com

CLASSIFIED

SATELLITE EQUIPMENT

FREE catalog of big dish systems, upgrades, and accessories. Warranties, satisfaction guaranteed. **SKYVISION**, 800-334-6455, 1012 Frontier Drive, Fergus Falls, MN 56537. www.skyvision.com. See our full page ad in the Shopper Section.

THE best television comes on a **DISH™**. Digital 18" satellite systems, mobile satellite systems, home entertainment accessories, and more. **SKYVISION** 800-500-9264; 1018 Frontier Drive, Fergus Falls, MN 56537. www.skyvision.com. See our full page ad in the Shopper Section.

VIDEOCYPHER II descrambling manual. Schematics, video and audio. Explains DES, EPROM, CloneMaster, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95, \$2.00 postage. Schematics for Videocypher II Plus, \$20.00. Schematics for Videocypher II 032, \$15.00. Software to copy and alter EPROM codes, \$25.00. VCII Plus EPROM, binary and source code, \$30.00. **CABLETELEVISIONS**, Box 30502R, Bethesda, MD 20824.

OBTAINING sound for your VCII and VCII Plus is easy. No codes needed. Details 1(800) 211-5635.

DSS reverse engineering package. Software, schematics, chip programmer plans, reviews & more! \$49.95. VISA/MC. **TELECODE**, 1-(520) 726-2833.

SOUND for Videocypher-11 and plus without codes. Free details. SASE. **NASSIRIAN**, Box 382-E, Rio Linda, CA 95673.

PLANS-KITS-SCHEMATICS

CRYSTAL set Handbook — Visit antiquity by building the radios your grandfather built. Assemble a "Quaker Oats" rig, wind coils that work and make it look like the 1920's! Only \$10.95 plus \$4.00 for shipping and handling. **CLAGGK INC.**, PO Box 4099, Farmingdale, NY 11735. US funds only! USA and Canada — no foreign orders.

FREE Catalog. 100 Leading-Edge kits. K1, PIC. Full instructions, source code. 1 (800) 875-3214. **SCIENCE FIRST**, 95 Botsford Place, Buffalo, NY 14216.

BUILD your own DC motor control. 1 to 480 amps w/surplus parts. **BEYOND ELECTRONICS**, 1 (800) 747-2861. Free catalog.

AWESOME kits: Voice changer, levitator, laser, gas sensor and more! Catalog \$1.00. **LNS TECHNOLOGIES**, 20993 Foothill Blvd., Suite 307R, Hayward, CA 94541.

ELECTRONIC Project Kits. www.qkits.com 1-888-GO-4-KITS. 292 Queen St., Kingston, ON, K7K 1B8. **QUALITY KITS**.

HACKERS Catalog. Hard-to-find kits and assembled equipment (Red box, spy, cable, etc.) Low prices. \$1.00. **SMITH-04**, Box 371, Cedar Grove, NJ 07009.

EDUCATION & INSTRUCTION

ELECTRONIC engineering. 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS**, 1203 Grant Avenue, Rockford, IL 61103.

LEARN VCR repair. Great profits. Home study. **P.C.D.I.**, Atlanta, Georgia. Free literature. (800) 362-7070 Dept. VRM342.

LEARN PC repair-troubleshooting, servicing. Home study. Free literature. **P.C.D.I.**, Atlanta, Georgia. (800) 362-7070 Dept. JJM342.

BASIC mechanics for electronic technicians. Send S.A.S.E. to **RM COMPANY**, PO Box 2124, Pomona, CA 91768.

SECURITY

SURVEILLANCE Privacy security protection. Catalog \$5.00. **SPY EMPORIUM**, 6065 Hillcroft, Suite 413, Houston, TX 77081. (713) 774-1000.

TEST EQUIPMENT

TEST Equipment pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 US for catalog. Refunded on first order. **J.B. ELECTRONICS**, 3446 Dempster, Skokie, IL 60076. (847) 982-1973.

TECHNICIANS: Electronic component tester for use with oscilloscope. Satisfaction guaranteed. \$29.95 plus S&H. Info: **ELECTROHM**, 529 Brentwood, Lawrence, KS, 66049. Fax: (913) 832-2481.

MISCELLANEOUS ELECTRONICS FOR SALE

TUBES: "oldest", "latest". Parts and schematics. SASE for lists. **STEINMETZ**, 7519 Maplewood Ave., EN, Hammond, IN 46324.

FIBER-Optic Projects — Swing into the new technology by assembling tried and true projects recently published. "Practical Fiber-Optic Projects" - BP374 is only \$9.95. (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC.**, PO Box 240, Massapequa Park, NY 11762-0240.

GREEN Thumb Alert — Electronics enters the Garden! New exciting book points out how gardeners can build simple gadgets to promote success where the elements work against you. Some of the projects are: over/under temperature monitoring, dusk/dawn switching, automatic plant watering, warming cables, etc. "Electronic Projects for the Garden" only \$9.95 (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC.**, PO Box 240 Massapequa Park, NY 11762-0240.

CBers Order new CB Trick III CB book. Shows CB tune ups, amplifiers, and expert CB info! Send \$19.95 to **MEDICINE MAN CB**, PO Box 37, Clarksville, AR 72830.

RESISTORS 20 for \$1.00. LEDs 4 for \$1.00. Catalog \$1.00. **ZIPFAST**, Box 12238, Lexington, KY 40581-2238.

POOR reception on your A.M. radio? Our Signal Booster will help. Guaranteed! Send \$2.00 for details (refundable with order). **FALA ELECTRONICS**, PO Box 1376, Dept. 4, Milwaukee, WI 53201.

POWERIZE yourself! New "easy use", low cost, personal computer peripheral for non-computer experts. Connects serial port. **Measure/Log** physical conditions. **Control** machines, mechanical-electrical devices, processes. Can send data/control/alarms via modem. Time interval controller, too. **Convenience, productivity, profit!** Includes detailed training manual; tells how! lots of free software! Information: **CYBER BOX**, Box 53743, Lubbock, TX 79453, 1 (800) 299-6971.

CONVERTER- descramblers: Examples, Zenith Ztac \$225.00, Scientific Atlanta 85XX \$185.00, 8580 compatible \$215.00, 8600 \$335.00, DPV-7212 compatible \$215.00, Jerrold 400 \$115.00. All Pioneer test generator \$150.00. Most makes in stock, COD ok. **OUNT HOOD ELECTRONICS**, (503) 543-7239.

BUY BONDS

CLASSIFIED

INVENTORS

REGISTERED Patent Attorney. Free handbook/ advice. Patent/trademark protection for your ideas. 1 (800) 876-6670. J.P. HALVONIK.

CABLE TV TURN-ON CHIPS

SUPER Cable TV "Test Chips". Provides full service activation. Excellent; Instructions & illustrations. **Jerrold Starcom:** DP(V)5..DP(V)7..DPBB7..CFT-2000..CFT-2200 Series. **Pioneer:** BA-5000 thru BA-6700. **Pioneer: Custom Programmer** (Clears E2 & rewrites new I.D. codes). **Scientific Atlanta:** 8500 thru 8600. **Tocom:** 5503-VIP..5507. **Zenith:** ST-1000 thru ST-5612. Call Now!! **MASTER COMPONENTS.** 1 (800) 233-0570.

THE CABLE TV SUPER CUBE

THE Mobilizer!! External "Test Cube" activator. Easy plug-n-play operation. Excellent instructions & illustrations. Supports all DP(V)7..DPBB7..CFT-2000..CFT-2200 series converters. **New enhanced performance features:** Locked box revitalizer! Restore command! Plus much more! **Dealers wanted!** Call Now!! **MASTER COMPONENTS** 1 (800) 233-0570.

CABLE TV

ATTN, cable box owners. Order your ID signal and bullet stopper before it's too late. Send \$23.00 to **R.R. ENTERPRISE**, Box 3532, Easton, PA 18043.

CABLE Descrambling New secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics for **SSAVI**, Gated Sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

CABLE TV Equipment & Accessories Wholesalers welcome! 30 day moneyback guarantee! Free catalog! **PROFORMANCE ELECTRONICS INC.**, 1 (800) 815-1512.

CABLE TV Test Chips for Jerrold, Tocom, Pioneer, Scientific Atlanta, etc... Quick Installation! New Multi-Mode modules available. Prices from \$5.00 each. 1 (800) 786-9025.

CABLE-safe. Guarantee cable privacy. The one-way valve for your cable TV signal. Cable signals come in, but they don't go out! \$29.95 + \$3.00 S&H. VISA/MC/AMEX. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

"CABLE Unscrambled. Everything you want to know about cable, but are afraid to ask. \$10.00.

"Descrambler Schematics Revealed" A powerful guide to descrambling schemes. \$10.00.

"Baseband Video Explained." Discover what a Baseband Signal is and how it's constructed. \$10.00. Special offer. Get all three for only \$25.00! VISA/MC/AMEX. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

UNIVERSAL Descrambler. Unscramble signals using your VCR as the tuner. Works with virtually any system, this is the only one you need. Declare cable box independence! Fully assembled. \$129.95 + \$5.00 S&H. VISA/MC/AMEX. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

"BULLET Buster". Protect your cable box against the infamous cable "bullet". The "Bullet" Buster acts as an electronic shield. Installs in-line in seconds. Don't wait until it's too late! \$19.95 + \$3.00 S&H. VISA/MC/AMEX. **ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

CABLE Descrambler! Anyone can build in seven steps with Radio Shack parts. Plans/Kit from \$5.00 plus free bonus!! 1 (800) 818-9103.

DESCRAMBLER Cable using simple circuit. E-Z to follow instructions \$10.00. Complete kit with free "Bullet Stopper". \$20.00. 1 (800) 522-8053.

CABLE Bullet "Terminator/I.D. Blocker." Electronically shields yourself and your box. Factory direct. Lifetime Guarantee \$14.95. 1 (800) 820-9024.

CABLE TV notch filters. Request our free brochure by calling our voicemail at 1 (800) 433-6319 or write to **STAR CIRCUITS** PO Box 94917, Las Vegas, NV 89193. Visit our web site at <http://our-world.compuserve.com/homepages/starcircuits>

CABLE test modules/cubes. Pioneers, S/A, Tocoms, Jerrolds. Latest technology. Quantity discounts. Voice/Fax (718) 426-8515.

CABLE TV testers/descramblers. All makes/models. Best prices guaranteed! 1 Yr. warr. <http://www.concentric.net/rmvideo1> or call (602) 581-1496.

CABLE TV, descramblers, converters. Quantity discounts. 30 day free trial. Competitive prices. Call now! 1 (800) 322-0921 **REGAL SALES, INC.**

DESCRAMBLE cable with simple circuit added to Radio Shack RF modulator and using VCR as tuner. Instructions \$10.00. **TELCOM**, Box 832 E11, Brusly, LA 70719.

25 + Master test chip files. Jerrold, Scientific-Atlanta, Tocom, Pioneer, Zenith. Software & book. \$79.95. **TELECODE** 1 (520) 726-2833.

CARL'S Electronics- The Cable Hacker's Guide, stopping power meters, and electronic plans now available on-line. <http://www.ultranet.com/~carlton>. Call for a free catalog (508) 534-3228.

WIRELESS cubes for any box \$150.00. Instruction, plans, parts list - \$7.00. Call (718) 545-5146. 1 Year warranty.

JERROLD - RFT's, FTG's. Lowest prices. Minimum order 5. 4pm to 8pm Eastern 1 (607) 734-2262.

R.F.T.'s \$58.00!, Diagnostic cubes, F.T.G.'s with filter \$58.00! (JER..PIO..S.A.) 1 (800) 688-0097. Testers for educational only.

COMPUTER SOFTWARE

JOYSTICK-To-Mouse. Now run Windows with any joystick! "Fly" the internet! 3.x/95 compatible. Only \$29.95! www.IMGPresents.com 1 (818) 346-3581, 1 (800) 889-0987.

COMPONENTS

RARE blue LEDs 12 for \$18.00, includes \$4.00 S&H. CA residents add \$1.44 tax. Hurry, quantities limited. **DIGITON**, 18620 Hatteras Street, #254, Tarzana, CA 91356-1827.

TRANSFORMERS - TOROIDAL: 37&52VA, 120V-30VCT & 7.5V RMS. Simple, compact and cost effective solution to supplying +5V and ±15V for digital/analog projects. Dealers welcome. **OMEGATRON**, (418) 831-1749.

EXERCISE.

American Heart Association





InfoSource

"Incredible Value!"
-Pam Eifert

"Bursting with info!"
-Pat Holt

"A VR smorgasborg!"
-Sid Mirza

FIVE GREAT PUBLICATIONS! ONE LOW PRICE!

Virtual Reality an Exploding Technology is an exclusive report on the explosion of VR in medical, amusement, consumer and other arenas. Plus news blurbs on market entry by heavyweights & Fortune 500's.

VR Resource Directory is your guide to hundreds of companies involved in VR products, books, software, professional trade organizations, clubs, more!

VRML Primer explains VRML, building virtual worlds on the Internet, great VR worlds to visit on the Internet, ABCs of setting up your own Internet home page, more!

Desktop VR contains a complete primer on using VR on your PC, plus, where to get low cost HMDs (head mounted displays) & other equipment, the famous Mattel Powerglove hack (converting a \$69 Powerglove for use with VR), Powerglove sources, listing of virtual world building software, comprehensive listing of HMD compatibility with popular games & software, more!

VR InfoMania contains great listings of Internet websites devoted to VR, VR books, VR magazine articles & research papers, Internet FTP download sites & VR-related newsgroups, article listings from back issues of VR magazines, where to go to experience real VR, reviews of popular VR books, glossary of VR terms, great VR applications, the future of virtual sex, more!

FREE BONUS!

The first 1,000 orders will receive the publication **VR Cartoons** featuring dozens of funny cartoons about VR! Yours absolutely FREE! Limited printing, don't miss out! Order today!



Five Publication Set!
Plus FREE BONUS "VR Cartoons"

99 Value! **ONLY \$49.95***
Special Price
Introductory Price!
Only \$39!
Limited Time!

Plus \$3.00 S&H
Calif. residents
add sales tax

2-3 Day Delivery \$7.50
FedEx Overnight Air \$14.95

30-Day 100% Satisfaction
Money-Back Guarantee!

24 HOUR
TOLL FREE
ORDER LINE
FAX ORDERS 619-485-8968

Send Check or Money Order to: Virtual Reality Publishing
1648 Bernardo Center Drive, Suite 378, San Diego CA 92128

*Same day shipping on orders received before 4 pm EST. Personal check orders held 2 weeks for check to clear. No COD orders. All orders must be paid in US funds. Call for int'l S&H charges. We participate in the BBB Care Program through the Better Business Bureau of San Diego.

ORDER TODAY... HAVE IT TOMORROW!!

ADVERTISING INDEX

Electronics Now does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page
— ABC Electronics	130	— Lindsay Publications	86
— AES	94	— M ² L Electronics	86
289 Ace Communications	130	326 Mark V Electronics	108
— Active Micro	119	327 MCM Electronics	87
— Aegis Research, Canada	104	251 Mendelson Electronics Surplus	119
213 Alfa Electronics	88	— Mental Automation	96
214 All Electronics	115	— Meredith Instruments	126
— Allison Technology	84	— Merrimack Valley Systems	94
— Allstar Electronics	129	325 Micro 2000	93
— Alltronics	129	128 MicroCode Engineering	17
— AlphaLab	90	— Micro Engineering Labs	92
— Amaze Electronics	127	— Midwest Laser Products	130
— AMC Sales	129	— Milestone Products	85
315 American Eagle Publications	106	— Modern Electronics	86
— Andromeda	96	— Mondo-tronics Inc.	134
77 B&K Precision	27	324 Mouser Electronics	127
334 Basic Electrical Supply	103	— MWK Industries	104
— Baylin Publications	110	— National Cable Brokers	130
335 Bel-Merit	109	257 Needham Electronics	108
— BHS Electronics	114	— NRI Schools	9
336 Brigar Electronics	102	322 OWI	126
— Bsoft Software, Inc.	94	262 Parts Express Inc.	83
333 Butterworth Heinemann	121	310 Phillips Tech Electronics	127
337 C&S Sales, Inc.	122	— Polaris Industries	129
— CGC	126	321 Prairie Digital	124
332 Capital Electronics	124	264 Print (Pace)	131
312 Circuit Specialists	100	— R-4 Systems Inc.	114
— Cleveland Institute of Electronics	21	78 Radio Shack	5
— Command Productions	98	266 Ramsey Electronics	125
331 Computer Monitor Maintenance	86	— RC Distributing Co.	127
226 Consumertronics	84	— RF Parts	85
320 Conway Engineering Inc.	97	— Sil Walker	112
58 Cook's Institute of Elec. Eng.	4	— Sirius Micro Systems	96
228 Cool Amp Conducto Lube	98	270 Skyvision Inc.	15
305 CTG	110	— Street Smart Security	103
— Cybermation	110	319 Sun Equipment	13
234 Dalbani Electronics	105	— Tab Books	1, 46
235 Danbar Sales	99	— TC Instruments	130
— Emac Inc.	90	273 Tech Systems	80
— Electronic Technology Today	73	— Technical Serv. & Solutions	110
— Fair Radio	119	92 Tektronix, Inc.	CV3
121 Fluke Corp.	CV2	290 Telulex	103
307 Foley-Belsaw Co.	95	— Test Equipment Sales	81
318 Fotronic	114	275 Timeline	82
330 Gateway Products	106	317 Toronto Surplus & Scientific	116
— General Device Instruments	96	— U.S. Cyberlab	91
— Geo-Ban Engineering	106	— Virtual Reality Publishing	135
— Grantham Col. of Engineering	73	— Vision & Motion Surplus	112
309 Graymark International	118	316 Visitec Inc.	104
— Home Automation	119	— Visual Communications	45
323 Howard Electronics	107	98 Wavetek Corp.	7
— IEC	130	— Weeder Technologies	81
— Information Unlimited	113	311 Weka Publishing	132
126 Interactive Image Technologies	CV4	314 White Star Electronics	85
— Intronic, Inc.	92	— Windjammer Barefoot Cruises	4
329 IVEX Design International	91	— World College (Div. of C.I.E.)	31
— J&M Microtek, Inc.	92	— WPT Publications	124
328 Kimtronics	111	281 Xandi Electronics	90

ADVERTISING SALES OFFICES

Gernsback Publications, Inc.

500 Bi-County Blvd.
Farmingdale, NY 11735-3931
1-(516) 293-3000
Fax 1-(516) 293-3115

Larry Steckler
publisher (ext. 201)

Christina Estrada
assistant to the publisher (ext. 209)

Arline Fishman
advertising director (ext. 206)

Michele Torrillo
advertising assistant (ext. 211)

Adria Coren
credit manager (ext. 208)

For Advertising ONLY

EAST/SOUTHEAST

Stanley Levitan
Eastern Advertising
1 Overlook Ave.
Great Neck, NY 11021-3750
1-516-487-9357
Fax 1-516-487-8402

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Midwest Advertising
One Northfield Plaza, Suite 300
Northfield, IL 60093-1214
1-847-559-0555
Fax 1-847-559-0562
bergenjr@aol.com

PACIFIC COAST

Janice Woods
Pacific Advertising
Hutch Looney & Associates, Inc.
6310 San Vicente Blvd.
Suite 360
Los Angeles, CA 90048-5426
1-213-931-3444 (ext. 228)
Fax 1-213-931-7309

Electronic Shopper

Joe Shere
National Representative
P.O. Box 169
Idyllwild, CA 92549-0169
1-909-659-9743
Fax 1-909-659-2469

Megan Mitchell

National Representative
1201 N. Rainbow Blvd., #50
Las Vegas, NV 89108-6819
1-702-259-7043
Fax 1-702-259-7043

Customer Service

1-800-999-7139
7:00 AM - 6:00 PM M-F MST

The scope can be held with one hand. The awards can't.



The TekScope® Handheld Digital Oscilloscope has won virtually every major award a handheld scope or DMM can. Because it allows you to sample at 500 MS/s on both of its channels simultaneously. Because it comes with Isolated Channel™ Architecture. Because it has a True RMS DMM. All surrounded by an intuitive, rugged package that will rest comfortably in the palm of your hand. For these reasons and more, TekScope has repeatedly been voted number one by customers like yourself.

Awards can be a handful, sure. But we're not complaining. For more information, call 1-800-479-4490, Action Code 722, or visit us at www.tek.com.

Tektronix


Better Designs - Faster

*Guaranteed with
Electronics Workbench!*

Just click and drag to create and edit schematics. Mix analog and digital devices in any combination with full control over values, models and behavior. Try 'what if' scenarios and fine tune effortlessly. And on-screen waveforms always match actual circuit response. You'll create better designs faster—Guaranteed!

Guaranteed Satisfaction

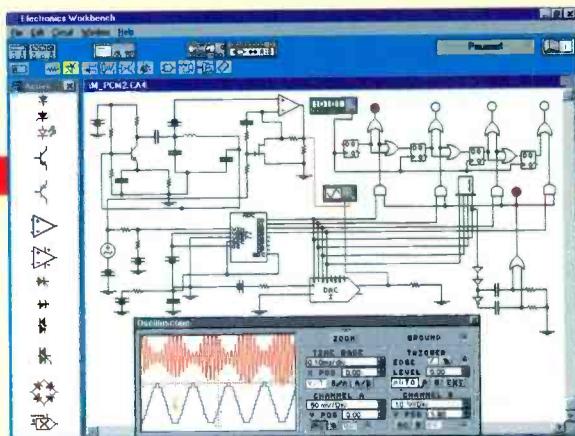Join over 70,000 customers and experience the power, flexibility and value that only Electronics Workbench offers. Receive unequalled service and free, unlimited technical support by phone, fax, e-mail, WWW, CompuServe and BBS. You'll be delighted. We guarantee it.*



True Mixed-Mode Power

Connect any analog or digital device to any other device without limit. Only Electronics Workbench offers this professional power for under \$2,000.

Real-World Digital


Real-world TTL and CMOS, complete with propagation delays and fanout. Unique at this price.

32-Bit Speed

Integrated SPICE analog and native-mode digital simulation in full 32-bit. Unique at this price.

Real-World Results

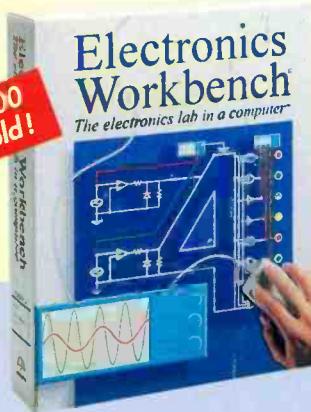Unlimited supply of over 200 components and ICs and 350 real-world models—all perform as real devices.



Electronics Workbench®

\$299

***30-DAY MONEY-BACK GUARANTEE**

VERSION 4.1 FOR WINDOWS 95/NT/3.1, DOS AND MACINTOSH.

Ask about our Engineer's Pack with thousands of additional models and more.
Version 4.0 users call for your free upgrade.

800-263-5552



Fax: 416-977-1818 Internet: <http://www.interactiv.com>
CompuServe: 71333,3435/BBS: 416-977-3540/E-mail:ewb@interactiv.com

INTERACTIVE IMAGE TECHNOLOGIES LTD., 908 Niagara Falls Boulevard, #068, North Tonawanda, New York 1420-2060/Telephone 416-977-5550
TRADEMARKS ARE PROPERTY OF THEIR RESPECTIVE HOLDERS. OFFER IS IN U.S. DOLLARS AND VALID ONLY IN THE UNITED STATES AND CANADA. ALL ORDERS SUBJECT TO \$15 SHIPPING AND HANDLING CHARGE

Australia: 2-519-3933 • Belgium: 2-384-73-09 • Brazil: 11-453-5588 • Canada: 416-977-5550 • Chile: 2-236-0300 • Cyprus: 9-641-801 • Czech Republic: 4-823-454 • Denmark: 33-25-0109 • Finland: 0-297-5033
France: 1-49-08-90-00 • Germany: 711-62-7740 • Greece: 1-524-9981 • Hungary: 1-215-0082 • India: 11-578-7055 • Indonesia: 21-470-0815 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-5395-2126
Malaysia: 3-774-2189 • Mexico: 5-593-5260 • Netherlands: 10-450-4949 • New Zealand: 9-267-1756 • Norway: 22-1670-45 • Philippines: 973-27-0118 • Portugal: 1-814-6609 • Singapore: 777-2303 • Slovenia: 61-317-830
South Africa: 331-6-8309 • South Korea: 2-3452-9757 • Spain: 1-383-8335 • Sweden: 8-740-5500 • Taiwan: 2-366-0080 • Thailand: 2-398-6952 • UAE: 4-453505 • UK: 203-23-3216 • USA: 416-977-5550

CIRCLE 126 ON FREE INFORMATION CARD