

DECEMBER, 1953

DEC 21 1953

Radio-Television SERVICE DEALER

TV - AM - FM - SOUND

Includes: **"VIDEO SPEED SERVICING"**
"TV FIELD SERVICE" Data Sheet Sections




The Professional Radio-TVman's Magazine
Reaching Every Radio TV Service Firm Owner in the U.S.A.



ALEXANDER FLAKADIS
ALEX RADIO LAB
1701 W 25TH ST
CLEVELAND OHIO
2A -MAY 56 30-560

TRIO

proudly announces

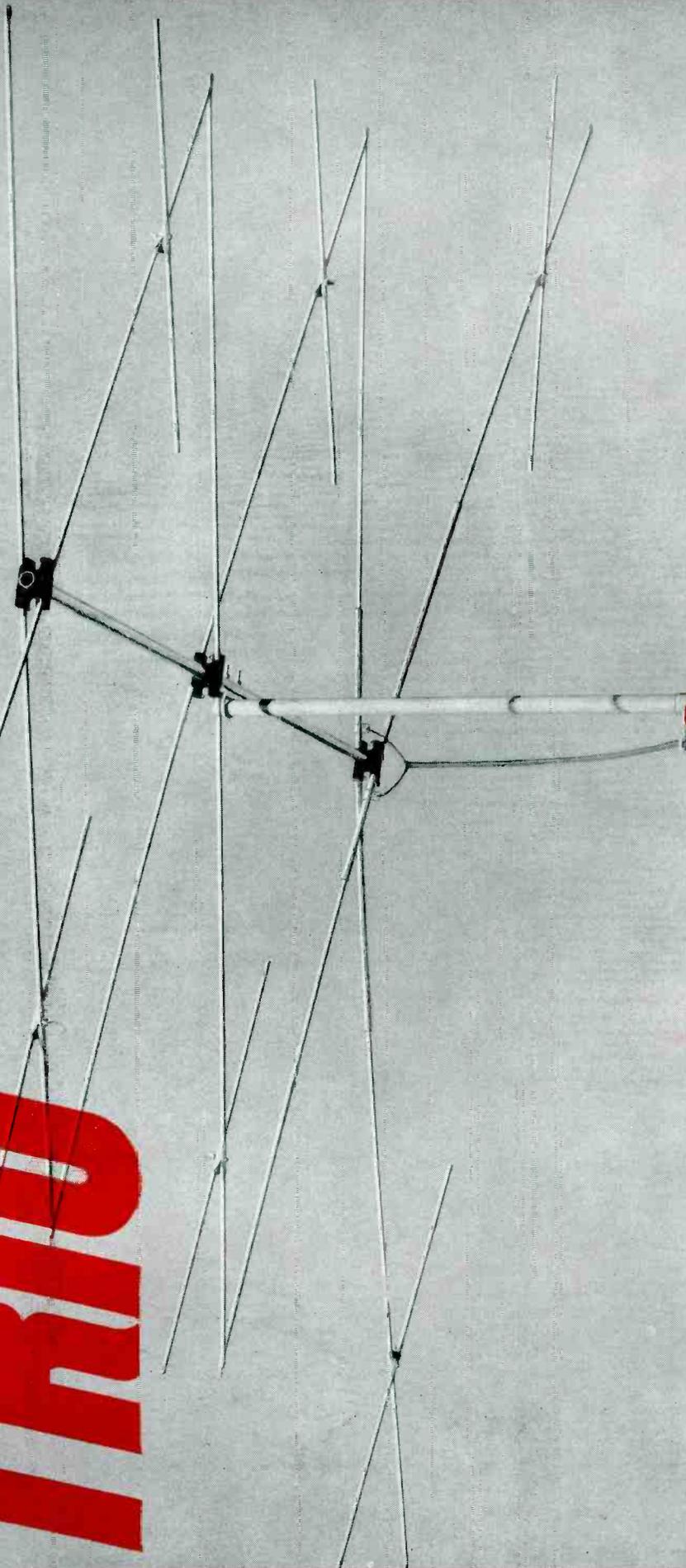

The New ZIG-ZAG

"TWIN-SIX"

(A significant addition to the Zig-Zag line)

... the greatest advance ever made in ALL-CHANNEL antenna design!


Not content to bring out just another all-channel antenna, TRIO studied and tested every other model available. Months of research produced the "Twin-Six", a Zig-Zag that provides all of the desirable features indicated above. Quantitative ratings for antennas are practically meaningless because of some exaggerated claims. For this reason, the "Twin-Six" is announced without the usual gain charts. The new "Twin-Six", however, equals and, in most cases, greatly exceeds the gains of these antennas on every channel. For instance, the "Twin-Six" showed a 2 to 6 db higher gain than a competitive antenna which is advertised as having a 12 db gain.

MINUTE-UP ASSEMBLY

There's no antenna easier to assemble. Shipped with all hardware mounted on the boom. Complete assembly consists of matching elements to color coded insulators and snapping on spring clips. Improper assembly impossible.



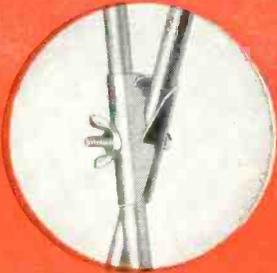Insulators come mounted on boom and are so designed that "shorting-out" is impossible. Antenna elements mounted merely by snapping on the spring clips.



Pre-assembled high channel elements are swung into position and quickly locked by mating brackets.

NEW ZIG-ZAG "TWIN-SIX" OFFERS:

Measurable Higher Gain On All VHF Channels Than Any Other Single Bay All-Channel Antenna

PLUS

1. One Horizontal Bay Does It All!
2. Single Lead-In Operation!
3. Easy-Up, One Minute Assembly!
4. Rugged Construction Throughout — No Droop, No Sag! Light Weight — Attractive Appearance!
5. UHF Reception For All Primary Areas!
6. Low Standing Wave Ratio!
7. Built and Backed by TRIO — A Name You Can Trust!
8. Competitively Priced!






TRIO

MANUFACTURING CO. GRIGGSVILLE, ILL.



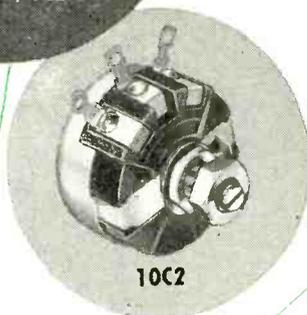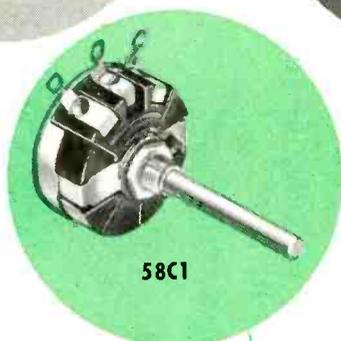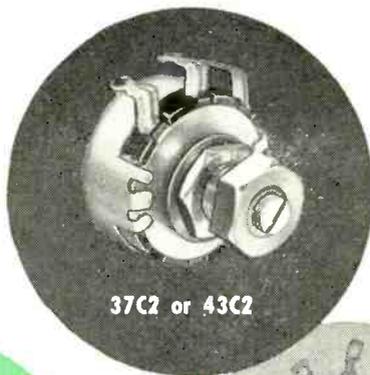Team the new Zig-Zag "Twin-Six" with the dependable TRIO rotator for the maximum in TV enjoyment!



Where better-than-standard
components are desirable...



CLAROSTAT

C-Line Controls

A new line of composition-element and wire-wound controls designed specifically for custom-built, industrial, laboratory or other semi-critical applications. These controls are *de luxe versions* — mechanically and electrically — of the popular Clarostat standard types widely used in radio-TV sets and for the servicing thereof.

With factory-assembled fixed $1\frac{1}{8}$ " round shaft (C1) or $\frac{1}{8}$ " screwdriver-slot shaft (C2) with split locking bushing.

All exposed metal parts have corrosion-resistant finish. Terminals have suitable finish for ease of soldering.

Close-fitting covers — no holes or cut-outs. Maximum protection against dust and dirt.

Ratings: 37C1 and 37C2 composition-element, 1 watt; 43C1 and 43C2 wire-wound, 2 watts; 58C1 and 58C2, 3 watts; 10C1 and 10C2, 4 watts.

Electrical tolerances plus/minus 10% for composition-element controls up to 100,000 ohms; plus/minus 20% from 100,000 ohms to 10 megohms.

Wire-wound controls within plus/minus 5% in all ohm-ages. Independent linearity to plus/minus 1% for 58C1 and 58C2, and 10C1 and 10C2 controls; for 43C1 and 43C2, plus/minus 2%.

Available with switches on special order.


Units sealed in dustproof plastic bags within standard Clarostat cartons. Factory-fresh appearance and condition, regardless of shelf life.

If you want still better-than-standard quality, performance and life, insist on Clarostat C-LINE controls.

STAND PAT WITH
C

CLAROSTAT Controls & Resistors

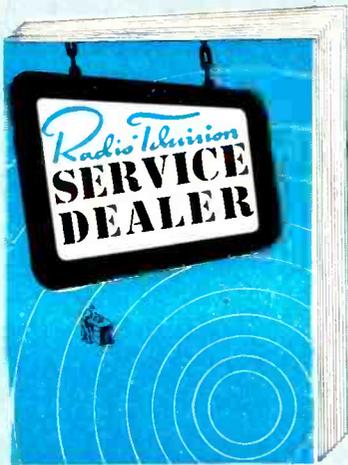CLAROSTAT MFG. CO., INC., DOVER, NEW HAMPSHIRE
In Canada: Canadian Marconi Co., Ltd., Toronto, Ontario



Every Service Firm Owner in the U. S. A.
Receives SERVICE DEALER Monthly
DISTRIBUTION THIS ISSUE OVER 63,000

COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.
 VOL. 14, NO. 12 DECEMBER, 1953

EDITORIAL STAFF

Publisher
SANFORD R. COWAN

Editor
SAMUEL L. MARSHALL

Assistant Editor
NORMAN EISENBERG

Contributing Editors
LEONARD LIEBERMAN
ROBERT T. DARGAN
RUDOLF F. GRAF
MARVIN KLEIN
SAN D'ARCY

BUSINESS STAFF

Advertising Director
SANFORD L. CAHN

Advertising Manager
HARRY N. REIZES

Eastern Adv. Sales
JACK N. SCHNEIDER

Production Manager
DAVID SALTMAN

Circulation Manager
HAROLD WEISNER

Assistant Circulation Manager
EDWARD J. HARMAN

BRANCH OFFICES

CHICAGO

HAROLD F. MANN
 333 No. Michigan Ave.
 Franklin 2-7100

LOS ANGELES

TED E. SCHELL
 2700 West Third Street
 Dunkirk 2-4889

CLEVELAND

RICHARD E. CLEARY
 Commercial Bank Bldg.
 Berea, Ohio
 BErea 4-7719

FEATURE ARTICLES

TV Troubleshooting Using Key Test Points, Part 1, <i>by Bob Dargan</i>	14
New method makes servicing quicker, more profitable.	
CBS Colortron, Part 2.....	22
Application, installation, and adjustment procedures.	
TV Sound Circuits, Part 3, <i>by Rudolf F. Graf</i>	26
Aligning the Foster-Seeley discriminator.	
Color TV, Part 2, <i>by Leonard Lieberman</i>	33
Serviceman's approach to newest thing in TV.	
R.C. Circuits, Part 2, <i>by Cyrus Glickstein</i>	35
More information for the technician on these important networks.	

CIRCUIT AND SERVICE DATA

Video Speed Servicing Systems Data Sheets (VSSS)	
Du Mont Chassis No. RA 164.....	43
G.E. Model No. 17C 103.....	45
Philco Chassis No. Deflection D1, etc.....	47
Sylvania Chassis No. 437.....	49
Rider TV Field Service Manual Data Sheets	
Bendix Chassis No. T17-7; 717.....	51
G.E. Model No. 17T10, 11, 12, 21.....	55
Raytheon Chassis No. 24T2.....	59

DEPARTMENTS

Editorial.....	4	New Products.....	38
Guest Editorial.....	10	Trade Literature.....	39
Trade Flashes.....	12	Circuit Court.....	40
The Answer Man.....	30	Association News.....	67
Advertising Index.....	80		

Note: Our annual index, listing all items that have appeared in RTSD during the year of 1953, will be printed in our next issue, January 1954.

RADIO-TELEVISION SERVICE DEALER is published monthly by Cowan Pub. Corp., 67 West 44th St., New York 36, N. Y. Subscription price: \$1 for 2 years in the United States, & U.S. Poss. Elsewhere \$1 per year additional. Single Copies 25c. Reentered as second class matter Sept. 25, 1950 at the Post Office at New York, N. Y. under the Act of Mar. 3, 1879. Copyright 1953. Cowan Pub. Corp.

POSTMASTER: SEND FORM 3579 TO RADIO-TELEVISION SERVICE DEALER, 67 WEST 44th ST., NEW YORK 36, N. Y.



EDITORIAL...

by S. R. COWAN
PUBLISHER

TELECAST OF COLOR

WITHOUT advance publicity, on October 31st WNBC-TV, (Chan. 4, N.Y.C.), presented Bizet's "Carmen" in full color, using the newly approved technical specifications of the National Television System Committee, and with permission of FCC.

Those people who had color TV sets in several sections in and near New York City, for test purposes, reported without exception that the telecast came in superbly. Many also opined that in comparison to monochrome (black & white) reception the color TV program was so far superior and so much more enjoyable that it would merely be a question of time before monochrome would be obsolete. That's logical, for if one had the choice of viewing the same motion picture in either monochrome or color, naturally the color version would get preference, all other factors being equal.

But the more important aspect of the unpublished color telecast experiment was the fact that the general public who viewed the opera at home on their monochrome receivers, (not knowing it was being telecast in color), did not get inferior reception. In other words, the compatible system devised by NTSC works beautifully. Now it is believed that FCC approval will be granted before long.

However, as we have stated frequently, should FCC give color its okay, the fact remains unchanged, color TV sets will not reach the public in any appreciable quantity for many months. In the interim, services would be wise to assimilate all the information of *reliable nature* that they can obtain regarding color TV. To date practically nothing of importance or value to servicemen has been published on the subject, and when the material is available this journal will be the first to release it.

COLOR TV'S PROBLEMS

As yet television manufacturers themselves frankly admit that they still have much to learn about the phenomena and idiosyncrasies associated with color TV reception. Thus fortified they also admit that color TV may give the servicing profession many heartaches too, though they hope to circumvent that as much as possible by passing on to us in the service field pertinent information as and when they get it.


One "expert" whose opinion we highly regard tells us that he believes the very success of color

TV public acceptance may rest in the hands of the Service Profession. For example, according to this well-informed friend, color set antenna installations cannot be handled in the same manner as monochrome installations. (They're as unlike each other as UHF and VHF). We'll amplify this: We all know that at present most home TV sets pick up 2 or 3 stations beautifully and at the same time fall off a bit on the other receivable signals. For sake of clarification let's say that the other 2 or 3 stations come in with a bit of a "ghost". Yet the "ghosts" in most cases are so minor as to be acceptable, or as our expert informant put it: "they are tolerated by the eyes without excessive offense." However, in regard to color TV—*absolutely no ghost effect whatever can be tolerated* on any station, in our friend's opinion. He maintains that "ghosts" in a color receiver have a tendency toward spoiling the picture to the extent that it would not be *tolerable* to the normal viewer.

The solution to this problem is not yet at hand. Possibly new antennas, or new circuitry design might help. But from a practical viewpoint it would seem to us that much of the solution lies in being able to orient properly the receiving antenna. Yes, we believe that *every* new home TV antenna installation (regardless of where it is, city or fringe, near or far from transmitter), made from this point on should include an antenna rotating device. Ultimately in signal areas of 4 or more stations it might be necessary to have two antenna installations, *each with its own rotator*.

THE CUSTOMERS WRITE

ONLY a few days ago our November issue reached a small part of its total of 64,000 distribution. But already our desk is loaded with hundreds of complimentary letters. Most praise the over-all fine text content and of course many allude to the new section "TV Field Service" by John F. Rider. Some hailed it and the "Question & Answer" department as being "the greatest contributions to servicing by any magazine in years." With humble pride we acknowledge with thanks, by means of this editorial, all of you correspondents who were so cordial and nice in writing us. At the same time we promise that even better helps to the Service Profession are in preparation for immediate release in future issues of "*Service Dealer*."

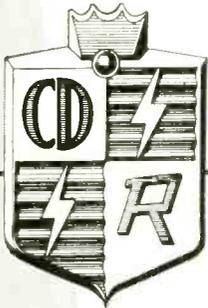

the CDR Rotor

sells faster...sells easier

because.....

The best line of TV Rotors money can buy

It is the complete line of quality rotors, with a model and type to best serve 'most every type application.

TV Spot Campaign

To reach the buying public, an intensive campaign on Television in key markets pre-selling CDR ROTORS for you.

Newspaper Advertisements

Also directed at the consumer, a supporting campaign in key city newspapers exploiting the advantages of the CDR ROTOR.

Moving Displays

It's causing excitement everywhere, this display that is an eye and traffic stopper, a silent salesman for the CDR ROTOR.

Envelope Stuffers

Here's another selling tool that may be mailed directly to your customers, selling them the CDR ROTOR in their home.

Newspaper Mats


A full set of completely prepared advertisements for dealers and distributors to capture extra CDR ROTOR business.

Window Streamers


They let everybody going into and by your store know that you have the CDR ROTORS, a colorful and eye-catching streamer.



TR-12

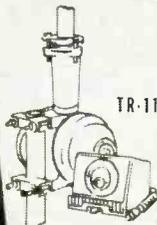

TR-11

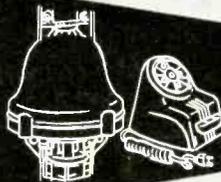

TR-2



THE RADIART CORPORATION
CLEVELAND 13, OHIO



CORNELL-DUBILIER ELEC. CORP.
SOUTH PLAINFIELD, NEW JERSEY

Mister Service Organization Owner

A suggestion by:



**Here's a sure way to speed up your shops!
service volume and increase your profits!**

We do *not* want you to buy a subscription to "Service Dealer." We won't accept such an order if you send it in because under our new controlled circulation policy we send a copy of "Service Dealer" every month to every established radio-TV service firm owner in the USA without cost or obligation.

However—much of the nation's actual radio and TV service work is done by employed technicians—the installers, the field servicemen, and the bench men who work for you—and for service shops like yours.

Your field and bench technicians must be kept abreast of the latest servicing techniques—they must have at hand *for their own reference and use* speed-ups to servicing such as "VSSS" data sheets and Rider's "TV Field Service Manual" data sheets. Every issue of "Service Dealer" is chock-full of exclusive technical data that is invaluable to all servicemen—shop owners and employed technicians alike.

All the material published in "Service Dealer" enables servicemen to do their work more efficiently, in less time, and by simpler means. The more speed and productivity a technician has—the more jobs he can do in a working day—with the end result that employed technicians will earn more for their employers, and employers in turn will be able to pay their technicians better wages out of increased profits.

Now "Service Dealer" welcomes and accepts 2-year paid subscriptions from all employed radio-TV technicians for only \$1.00. (2-year subscription is 24 issues.)

You shop owners should tell your employed technicians about our new policy. Show your employees the copy of "Service Dealer" we're sending to you. They'll see at a glance how fine our text material is. They'll want to receive *their own* copy of "Service Dealer" every month. Perhaps you might want to buy subscriptions for your technicians as it's a tax deduction expense. Or, you might want to split the cost of the subscription with them. The important point is this:—it will pay you, and it will pay your technicians, to get "Service Dealer" every month!

EMPLOYED TECHNICIANS—TEAR OUT—USE THIS COUPON

EMPLOYED TECHNICIANS — 24 ISSUES for \$1.00

RADIO-TV SERVICE DEALER NEW
67 W. 44 St., New York 36, N. Y. RENEWAL

Gentlemen:

Here is \$1.00 for which enter my 2-year subscription.

Name

Address

City Zone State

Employed by (Name of firm)

Firm's business address

City Zone State

Your Position or Title

Check whether firm is:

Service Organization or Dealer having Service Dept.

If some other type of company describe:

(If a group of sub. orders are being sent, simply type the list—give each man's title)

The Quality of Your Service
can be no better than the
Quality of the Parts You Handle



WHEN POOR QUALITY OR FAULTY
DESIGN OF A COMPONENT PART
CAUSES TROUBLE—YOU ARE MORE
LIKELY TO GET THE BLAME THAN
THE MAKER OF THE PART.




In Fuses the **BUSS** Trademark represents unquestioned High Quality!

Why take a chance with your goodwill, reputation and profits when BUSS and FUSETRON Fuses are available?

To maintain highest quality *every BUSS and FUSETRON fuse used by the electronic industries is electronically tested.* A sensitive testing device rejects any fuse that is not correctly calibrated, properly constructed and right in all physical dimensions.

BUSS quality means dependable electrical protection under all service conditions and — BUSS quality means fuses that blow to protect — never needlessly.

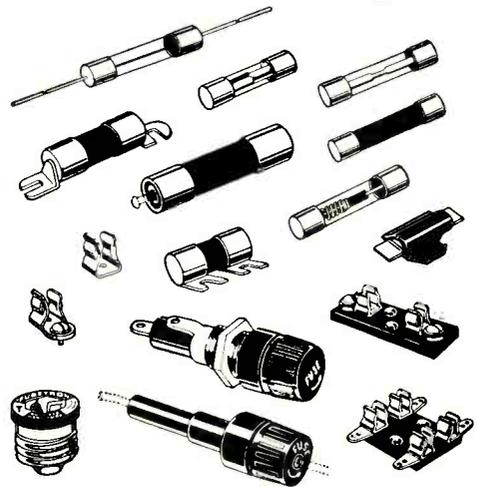That's why for over 38 years it has just been good business for distributors and service organizations to handle only BUSS Fuses — the KNOWN brand.



FOR MORE INFORMATION Mail this coupon

BUSSMANN Mfg. Co. (Division of McGraw Electric Co.)
University at Jefferson, St. Louis 7, Mo. SD-1253

Please send me bulletin SFB containing facts on
BUSS small dimension fuses and fuse holders.

Name _____

Title _____

Company _____

Address _____

City & Zone _____ State _____ 1253

famous

Telrex 4-BAY "CONICAL-V-BEAMS"®


**-the acknowledged
champion in 1948 and
STILL CHAMPION!**

Install genuine Telrex "Conical-V-Beams," the Patented uni-directional, one transmission line array. Models for Ch. 2 to 13 or Ch. 2 to 83. See and hear the difference!

If UHF is available or expected, install Telrex "Duo-Band Conical-V-Beam" series. The perfect for rotation hi-gain... hi-F-to-B all-band one transmission line array with automatic transition from low to hi band with no lossy "distribution" pads.


"Conical-V-Beams" are designed for easy stacking as required for your particular reception area. 1 bay "C-V-B" for pri-area, 2 bay "C-V-B" for sec-area, 4 bay "C-V-B" for fringe areas... If a 4 bay "C-V-B" does not provide a usable TV picture, TV reception is either impossible or impractical!

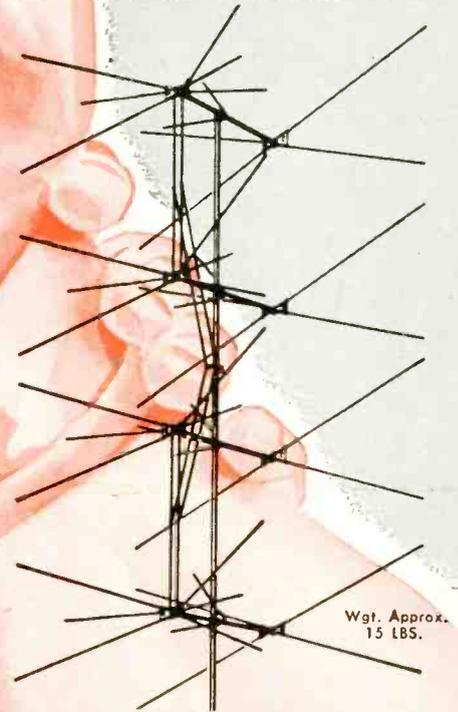Broadbanded single channel highest gain hi-F-to-B yagis also available from Telrex Antenna Headquarters, builders of world renowned communication yagis for amateur or commercial use.



**CHAMPION-FOR-DISTANCE
MODEL 8X-TV***

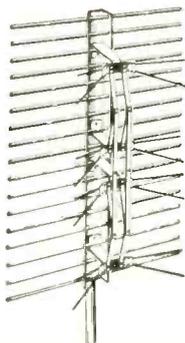The Ultimate in long distance arrays. Guaranteed to out-perform any antenna or combination of cut-to-frequency antennas. When used with Duo-Band splines it comprises the ultimate from Ch. 2 to 83. Unequaled for reception up to 200 miles.




ULTRA-HI GAIN UHF "CONICAL-V-BEAM" MODEL 84

- Four bay uni-directional array
- All in-phase signal addition at all frequencies with no lobe splitting
- All-aluminum light weight and rugged

PRE-ASSEMBLED, PRECISION TUNED 5-ELEMENT YAGI

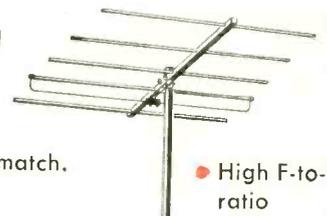- High gain, broad-band response
- Excellent 300 ohm impedance match.



- High F-to-B ratio

WRITE FOR
COMPLETE TELREX
BULLETINS, TODAY!

Telrex INC.
"CONICAL-V-BEAMS"
BETTER BY DESIGN

*PATENTED
ASBURY PARK 5,
NEW JERSEY

Insist on a genuine "Conical-V-Beam." Look for the Telrex Trade-Mark!

Depend on Mallory
for
Approved Precision Quality

The sales leader—
proved in every UHF area



Now...

The MALLORY CONVERTER Packs *ALL* Features in Half the Size!

*The new Model 88 has these important Sales Advantages
originated by Mallory:*

Less than half as large . . . measuring only $7\frac{5}{8}$ " wide x $5\frac{9}{16}$ " high x $4\frac{5}{8}$ " deep . . . yet full Mallory quality.

It has linear tracking. Tuning is easier, more exact than ever. No bunching of channels.

The Preselector in the new 88 protects against image interference, oscillator radiation and interference at the IF frequency. It insures better selectivity.

The Mallory 88 Converter adds *all* UHF channels to *any* TV set without sacrificing a single VHF channel.

Design refinements and precision quality of the 88 assure high quality picture definition and easy tuning.

The customer has nothing more to buy, no adjustments to make for additional new channels . . . even if he moves to another area.

Installation is easy. It only takes a few minutes to connect the antenna and power leads from the Converter to the set. It can be done right in the customer's home.

ASK YOUR MALLORY DISTRIBUTOR for complete details of the new, handsome, compact Model 88 Converter. It can be your answer to bigger profits . . . just as all Mallory Converters have been for dealers in areas where UHF is already on the air.

P. R. MALLORY & CO., Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



W. L. PARKINSON, Manager
Product Service, General Electric Co.

In this second in a series of guest editorials, we learn what a factory service manager does and how his department ties in with the work of the service man.

RETAIL dealers and servicemen often ask me: "What are the responsibilities of a factory service manager?; What are the functions of a factory service department?" The factory service manager provides a definite service in helping to produce satisfied customers. I believe the situation at General Electric is typical of this important job in any radio-television manufacturing organization.

The factory service manager's broad responsibilities are as follows:

1. Formulation and enforcement of service policy.
2. Preparation and publication of technical information.
3. Field engineering.
4. Operation of factory service shop.
5. Quality control.
6. Consumer relations.

The service manager operates at staff level and is responsible for formulating recommended policies to be adopted by management with respect to service responsibilities. Upon approval and adoption of such policies it is the service manager's duty to enforce the policy.

The timely preparation and publication of service notes, service bulletins, customer operating instructions and pertinent technical information is a most important function of the service department. This group keeps the field advised on technical problems; supplies information on replacement parts, production changes and field modifications. Close coordination between this group, engineering, field engineering, quality control, and the parts department, is necessary for efficient operation of each of these sections.

The field engineering group is responsible for training of distributor and dealer technical personnel and provides assistance to distributors in establishing and maintaining adequate service in the field. This group advises the wholesale distributor on replacement parts stock, processes claims for defective parts returned and keeps the factory advised on all technical problems encountered in the field. This group is also responsible for field testing new products before production. The factory engineering and manufacturing sections lean heavily on the advice and council of these men in the field. Close coordination between field engineering, technical publications, quality control and the parts department is required for maximum efficiency of the service department.

A small service department is maintained at the factory to handle problems reported from the field.


Close coordination between this group, factory engineering and manufacturing, and other sections of the service department, is required for an overall efficient service operation.

The quality control section sample-checks each day's production to make sure that the product meets consumer acceptance standards. This group has the authority to release for shipment first production of new models or to withhold shipments on current production if quality does not meet acceptance standards. Close cooperation is required between this group, factory production and engineering sections, and other sections of the service department, to insure shipment of a satisfactory product to the field.

The consumer relations group handles distribution of service and technical information and all correspondence with consumers, dealers, servicemen and distributors. This group works closely with field engineering, technical publications, quality control, sales, and the service shop to insure satisfactory relations with wholesale distributors, dealers and servicemen, and to provide prompt assistance on consumer complaints received at headquarters.

In addition to these broad responsibilities, the factory service manager acts as a technical consultant to managers of sales, advertising, engineering, manufacturing and production. The factory service manager should be a diplomat, a salesman, and an engineer. He needs an active mind, a strong constitution, cast iron stomach and lungs, a sympathetic heart, and the hide of an elephant.

WE are occasionally disturbed by letters from servicemen and dealers indicating that they lack sufficient service data. We are all the more chagrined at this because we are bending every effort to provide the detailed and comprehensive service bulletins designed to make the servicing of our receivers simple and speedy. Since our literature is written by former servicemen, it is a labor of love. This technical data is available to *anyone* servicing our receivers; he need only contact his General Electric distributor. I believe this technical data can be effectively used as are other trouble shooting tools—to save time, and thus make money for servicemen.

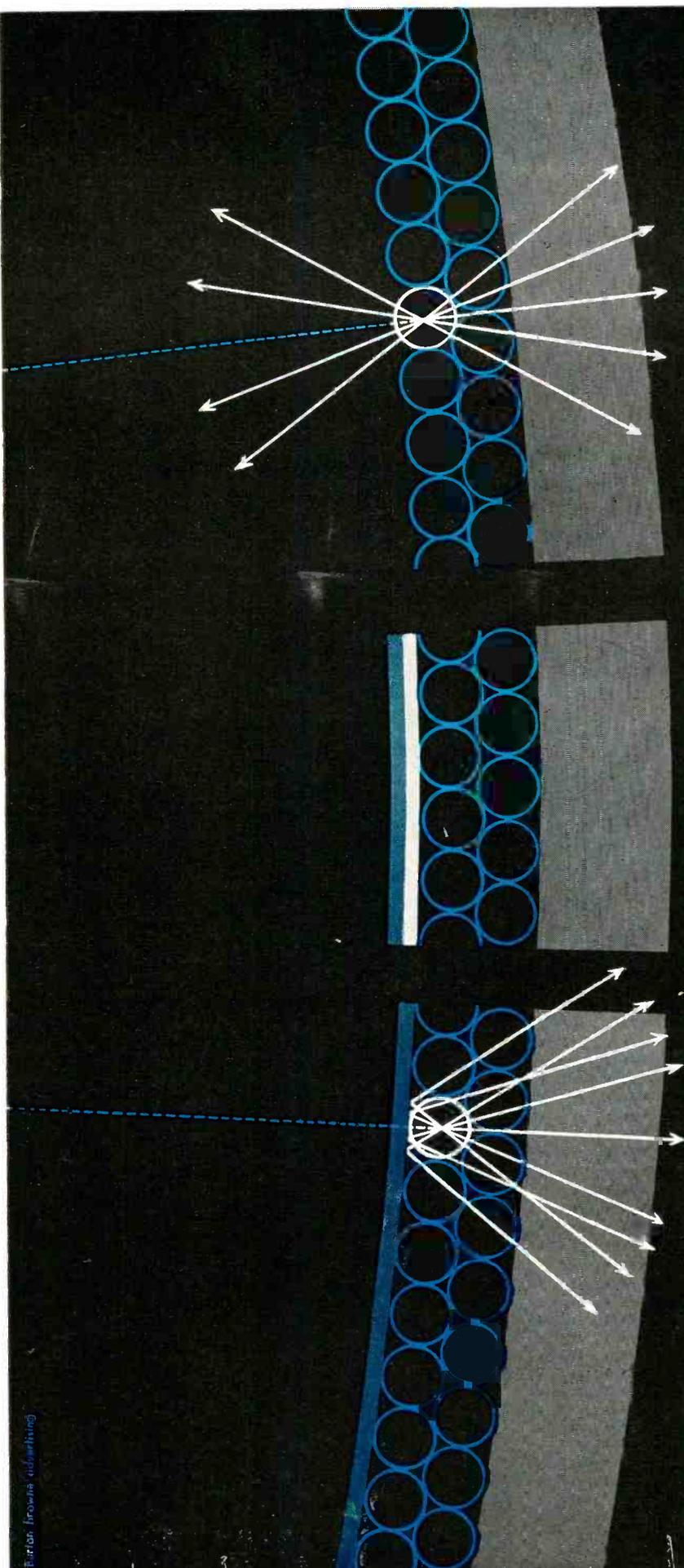

what
Aluminizing
means

Aluminizing means the efficient use of light—light is energy—energy is the pay-off.

Aluminizing means a brighter TV picture, greater contrast, lower beam current, smaller spot size, sharper focus, reduced screen scorch—all from the efficient use of light.

On the inside of any TV tube face is a coating of phosphor crystals—the picture screen. As the electron beam—tracing the picture—strikes these crystals, they glow, giving off light in all directions. And there's the problem! Half the light thus generated is *inside* the tube, either lost to usefulness or lighting areas that should be dark. Both brightness and contrast suffer.

But—put a mirror behind the phosphor and “wandering” light is reflected back through the tube face. *Aluminizing creates this desired mirror!*

To aluminize a picture tube, deposit a nitrocellulose film evenly over the phosphor. Over that, deposit a film of aluminum only millionths of an inch thick—*just thick enough to reflect the light and just thin enough to let the electrons pass through*. Under heat, evaporate the nitrocellulose film to leave a thin smooth coating of aluminum. Result—an efficient light reflecting mirror to specifications.

Simple as it sounds, Rauland research engineers worked for three years to solve the problem and were among the first to do so.

Rauland

Perfection through Research

ZENITH Subsidiary

SAVE ON INSTRUMENTS!

- do better testing with fewer instruments
- avoid buying costly equipment you don't really need
- discover new uses for old instruments
- learn all about ALL instrument types; how to use them more efficiently; how to interpret their readings



BASIC ELECTRONIC TEST INSTRUMENTS
by Rufus P. Turner
254 pages, 171 illus.
Price only \$4

Get the real "low-down" on

- Current and voltage meters
 - TV pattern generators
 - Grid-dip oscillators
 - Oscilloscopes
 - Ohmmeters
 - Volt—Ohm—Milliammeters
 - V-T voltmeters
 - Power meters
 - Capacitor checkers
 - Impedance meters
 - Special-purpose bridges
 - Tube testers
 - TV sweep and marker generators
 - Distortion meters
 - TV linearity pattern generators
 - Square-wave generators
 - R-F signal tracers
 - Signal generators
 - R-F test oscillators
 - Inductance checkers
 - R-F and A-F measuring devices
- ... and over 30 other standard instrument types!

This book can save you hundreds of dollars by avoiding unnecessary instrument purchases. And it can help you handle all kinds of testing faster and more accurately in the bargain by putting old instruments to better use!

Actually, **BASIC ELECTRONIC TEST INSTRUMENTS** is a complete training course covering over 60 instrument types for TV and radio service, ham and experimental use.

Included are complete details on simple meters for current and voltage; ohmmeters and V-O-M's; V-T voltmeters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes (this material alone is worth the entire price of the book to busy servicemen!); r-f test oscillators and signal generators; audio test oscillators; radio frequency and audio frequency measuring devices; audio-amplifier testing devices; r-f signal tracers and tube testers.

Among other things, it is a complete training course in the latest instruments including grid-dip oscillators, TV sweep and marker generators, TV linearity pattern generator, square-wave generators, distortion meters and others.

LEARN THESE MONEY-SAVING TRICKS!

You discover new uses for VOM's, oscilloscopes, signal generators, etc. You see how to extend the range of many old instruments; how to use power drain measurements for fast TV trouble-shooting; how a bridge can be built from old instruments; how to measure r-f impedance the easy way; how to measure inductance and capacitance with a grid-dip oscillator and dozens of other money-saving "tricks."

Use coupon now for 10-day FREE trial

10-DAY FREE TRIAL

Dept. RSD-123, Rinehart Books, Inc., Technica Div., 232 Madison Ave., New York 16, N. Y.

Send Turner's **BASIC ELECTRONIC TEST INSTRUMENTS** for 10-day FREE examination. If I decide to keep book, I will then remit \$4.00 plus postage. Otherwise I will return book postpaid promptly and owe you nothing.

Name.....
Address.....
City, Zone, State.....

OUTSIDE U. S. A.—Price \$4.50 cash only.
Money back if book is returned in 10 days.

TRADE FLASHES

• • •

750 TV Station Approvals Seen

750 television stations will have been authorized by the Federal Communications Commission, "and perhaps another 100 by the end of next year," Rosel H. Hyde, FCC chairman disclosed at the Association of National Advertisers annual meeting. Of 525 authorized stations, 250 are now in actual operation in 166 markets. About 112 of those markets are one-station markets. In 48 of the one-station markets, additional stations have been authorized, and for 24 of the markets, there are contending applications. The 525 authorized stations, plus the 200 stations applied for, would cover 80 per cent of the United States population. It is not expected that the present high rate of station construction to continue indefinitely. The growth of television in small communities will depend on the extent that industry finds such operations profitable.


New CBS-Hytron Service Plan

The CBS-Hytron Certified Quality Service Plan hinges around a service tag that is attached to each set serviced by the service-dealer. On the back of the tag is space to list all parts used in servicing the set, as well as the individual charges made for them. On the face of the tag, there is space allowed for entering total charges for parts and labor . . . sales tax . . . and the grand total charge. The key to this tag's value rests in a statement that appears at the top of the tag which reads: "This certifies that parts used in servicing this set are new and of standard make and quality. All charges are made in accordance with industry standards." Since the tag itself carries an imprint of the service-dealer's name and address, it is the service-dealer himself who is certifying the work, parts, and charges.

This Certified Quality Service tag serves an additional purpose, because part of it functions as a claim check. On the perforated bottom section of the tag, the claim check, appears the statement of the certifying dealer: "Your set is being serviced by technically trained men using the latest equipment so necessary for Quality radio and TV service."

(Continued on page 64)

by every test

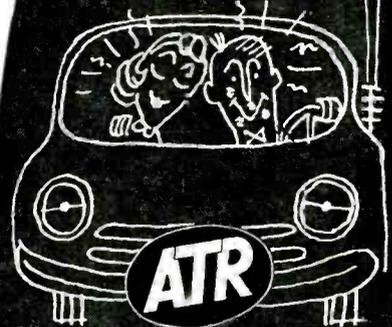

is BEST!



ATR AUTO RADIO VIBRATORS

Have Ceramic Stack Spacers
A COMPLETE LINE OF VIBRATORS

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life. Backed by more than 22 years of experience in Vibrator Design, Development, and Manufacturing.

Free



"A" Battery Eliminators, DC-AC Inverters, Auto Radio Vibrators



NEW MODELS NEW DESIGNS NEW LITERATURE

See your jobber or write factory

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA—U. S. A.

CUSTOMERS EVERYWHERE KNOW
 SYLVANIA TUBES JUST
 CAN'T BE BEAT FOR QUALITY!



WHY SYLVANIA PRODUCTS MEAN BETTER BUSINESS!

YOU'RE really on board the *better-profit* special when you feature Sylvania Picture Tubes and Receiving Tubes.

Your customers know Sylvania as a pioneer in the development of fine radio and television products. From the very beginning, the name Sylvania has stood for the highest possible quality. And, as the industry has progressed and expanded, Sylvania has taken great care to maintain its recognized leadership.

Now, due to advanced manufacturing techniques and precision testing methods, Sylvania tubes can point to outstanding records, both in long life and fine performance. Today 7 of the 10 leading set manufacturers use Sylvania Picture Tubes and Receiving Tubes.

So, if you want *recognized quality* working on your side . . . *sell Sylvania!* Call your local Sylvania Distributor for the latest fall prices and money-making promotion offers, or write to: Sylvania Electric Products Inc., Dept. 3R-2212, 1740 Broadway, New York 19, N. Y.

SYLVANIA

 LIGHTING • RADIO • ELECTRONICS • TELEVISION

RADIO-TELEVISION SERVICE DEALER • DECEMBER, 1953

**Television keeps telling
 about Sylvania quality**




Sylvania's popular nation-wide television show "Beat the Clock" continues to tell millions of your customers week after week, all through the year, about the unbeatable quality of Sylvania products.

In Canada: Sylvania Electric (Canada) Ltd.
 University Tower Bldg., St. Catherine Street, Montreal, P. Q.

TV TROUBLE SHOOTING

USING Key Test Points

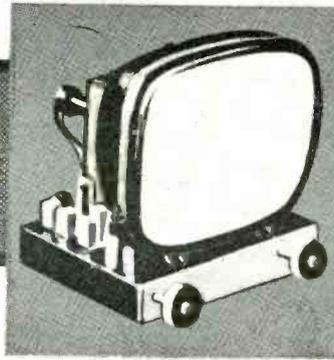

by **BOB DARGAN**

THE TV receiver performs the job of intercepting an incoming channel signal which contains a number of different types of signals. These signals are amplified, rectified and otherwise acted upon by different sections of the receiver through which they are routed, and the end result is picture and sound.

The entire operation could be a complicated one from a service point of view. However, if we confine ourselves to the channels in the receiver through which certain signals pass, we can simplify the servicing problems considerably.

At specific points in any receiver certain signals and waveforms must be present for proper operation. The quickest and most efficient method of servicing is to utilize these so-called check points as the means of ascertaining whether or not the desired signals are present and then to proceed to where they are missing. This technique isolates the stage or stages which are not functioning and points to the location of the defective component.

It is the purpose of this series to acquaint the technician with common key test points and to apprise him of the techniques that should be used

in following through on the servicing of the receiver.

Television key test points are circuit locations. The voltages at these key points reveal to the technician quickly and easily the condition of the stage and section of the receiver, that is whether it is working or not. Key test points are the working tools of the technician and as much a part of his equipment as his voltmeter or 1/4 inch socket wrench.

The technician is wealthy or poor in key test points dependent upon his ability to understand electronic fundamentals and to apply them practically


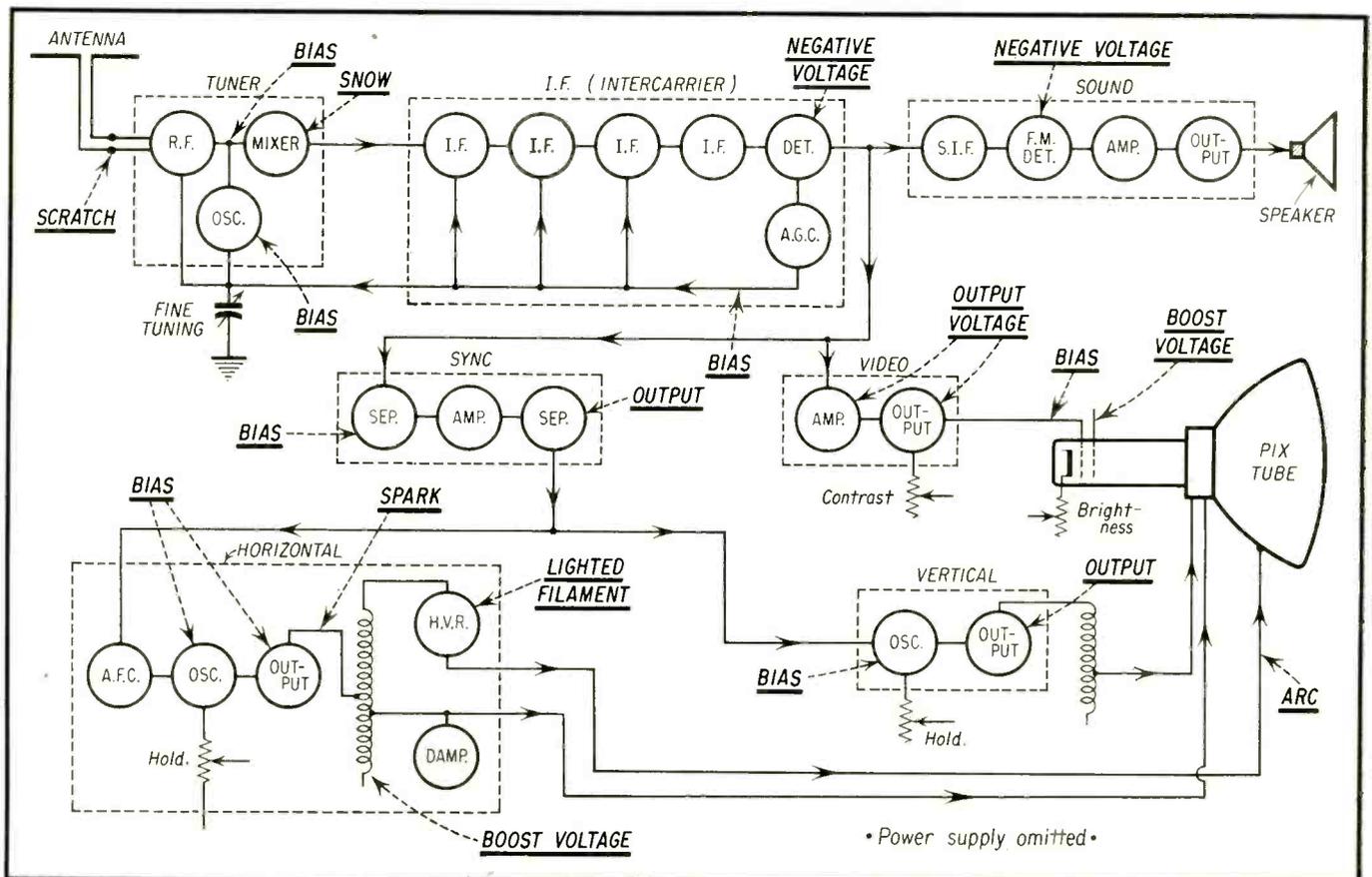


Fig. 1—Major test points common in most TV receivers.

MERIT

HOLLYWOOD, HOLLYWOOD and CHICAGO!

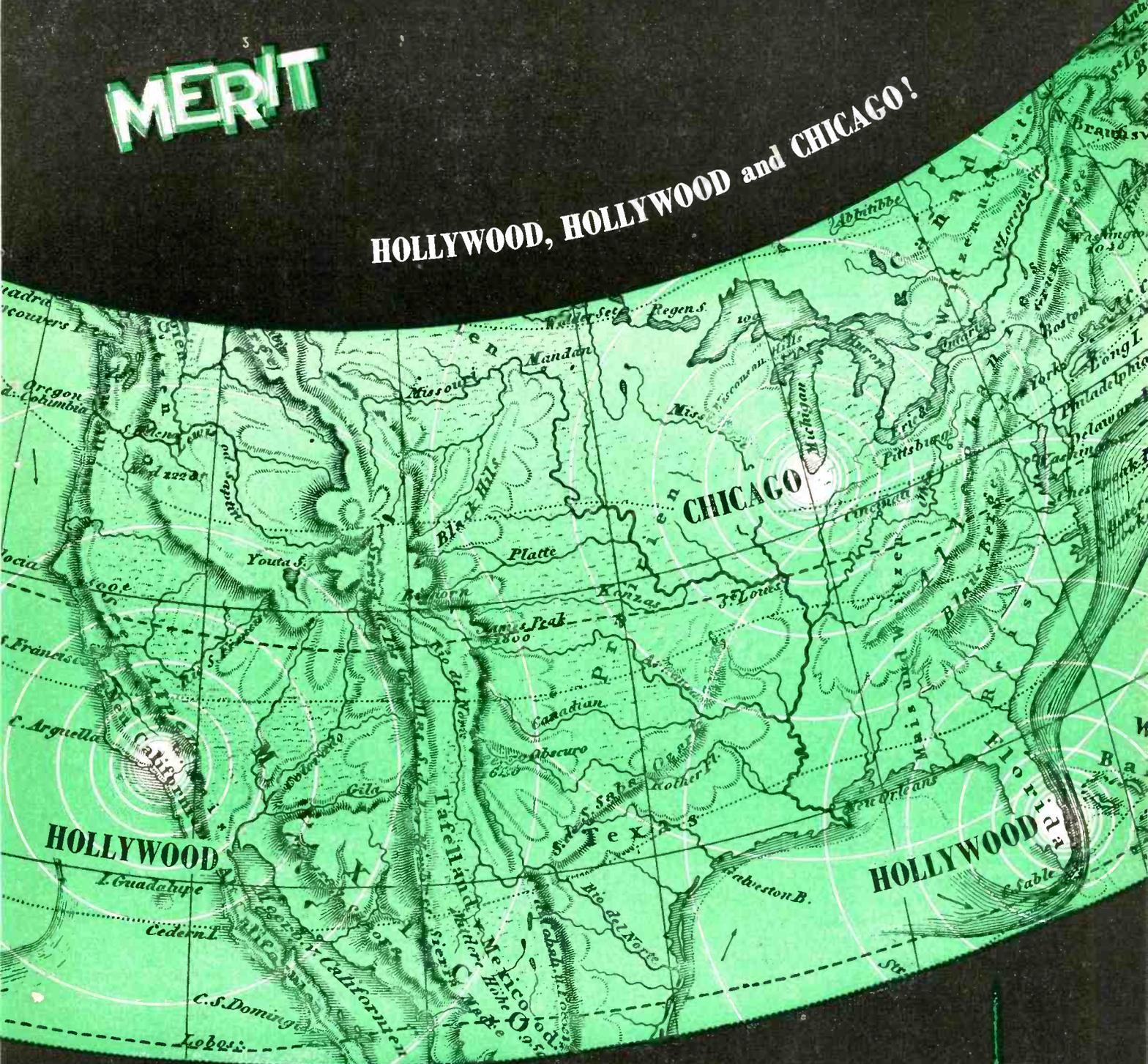

East coast, West coast or the middle of the country, Merit's plants are where you need them . . . for, Merit is the only independent coil and transformer manufacturer devoted exclusively to the serviceman's TV problems.

Take advantage of MERIT'S faster service.

Find Merit's complete line, Tape Marked,* listed in John Rider's Tek-File and Howard Sam's Photofacts and Counter Facts to help you.


And! Be sure to get Merit's latest complete Replacement Guide.

Forty pages of replacement data and schematics, including IF-RF coils, an exclusive Merit feature.

*originated by Merit

MERIT COIL AND TRANSFORMER CORPORATION

4425 North Clark Street
Chicago 40, Illinois • LO. 1-6311

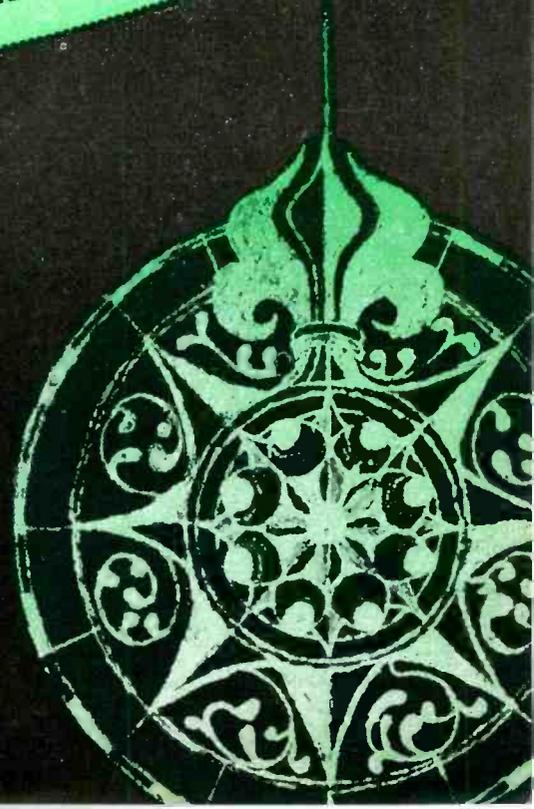

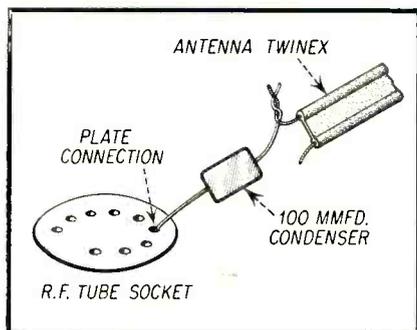


Fig. 2—Condenser used in testing *rf* stage. Note RF tube is removed.

to his service work. There are many of these quick, simple test checks which competent technicians make use of and have accumulated. It is through the use of this type of checking that speed in servicing can be accomplished. The technician should be able to go to any stage and know whether the stage is doing the job it is supposed to or not. It is the knowledge and application of good electronic theory that enables him to be outstanding and accomplish more jobs than the average serviceman. The good technician is continually building his knowledge of key test points as he comes upon them because they are the "skills of the trade."

The drawing, Fig. 1, indicates some of the test points common in most television receivers. These are only a few of the major ones. Many more will be delved into as the different TV sections are covered.

The value of these test points lies in the fact that they can be used with a VTVM on a 20,000 ohm-per-volt meter and therefore will prove equally useful in the customer's home where elaborate test equipment is not available. These test points will not eliminate the need and use of more elaborate test equipment but should enable the technician to do more "wood-chopping" before the equipment is required.

In the following paragraphs we will endeavor to indicate how these test points are made use of. The procedure will follow the general signal as it progresses from stage to stage.

The Tuner Section

The first section of the receiver to be considered is the tuner or front end. Many possible checks will be provided and it is up to the technician to adopt the procedures that most suit him. Naturally, he will be able to supplement these checks with some of his own.

A "V" type antenna should be

part of a serviceman's working equipment. The "V" antenna can be used to determine the amount of signal strength present and a comparison can be made with the amount received from the roof antenna, if one is used.

In most customers' homes, a "V" type antenna will pick up at least enough signal to provide audio and picture when the antenna on the roof is in question or when there is no picture or sound.

Also, the "V" type antenna can be used to ascertain whether TVI flashes or other noise and outside troubles are actually being received in the antenna on the roof. After a television antenna has been up for three or four years overhauling is usually in order. The "V" type antenna can therefore aid in quickly determining whether the trouble is in the TV chassis or comes from the outside antenna.

Testing The RF Amplifier Stage

The major purpose of the *rf* stage in the tuner is to provide amplification and selectivity for the incoming channel signals. Tuned circuits are usually switched into the grid and plate circuits of the tube to select the desired channel.

In testing these stages in the tuner, the tests would be of no value if the *if* strip were inoperative because the signal would not be able to pass through the *if* strip to the sound section and picture tube. Therefore, in this discussion on tuners it is assumed that the trouble has been isolated to the tuner and the balance of the receiver is trouble free.

There are many ways of testing the *rf* stage. Some entail the use of signal generators and other equipment which will not be discussed in this article. One method is to shock-excite the circuit. This can be done with the ordinary voltmeter used for checking voltages. The shock to the tuned circuits caused by connecting the meter and disconnecting it at the plate and grid circuits should cause flashes in the picture and static noise from the speaker, indicating that signals are passing through the various circuits. Even moving the *rf* amplifier tube in and out of the socket should produce noticeable clicks in the speaker accompanied by flashes in the raster as the tube connections are made and opened. A similar check can be made by scratching the antenna leads to the connecting screws where the leads are normally fastened. This should produce the same effect. When switching the tuner from one channel to the next, making and breaking the con-

tacts should produce the same effect, that is, enough of a shock to the tuned circuits should result so that the signal is produced which makes its way through the *if* strip, sound system (even with FM detector circuits), and video amplifier. Evidence of this disturbance will be present at the CRT and speaker.

An effective test of the *rf* amplifier stage may be made by removing the *rf* tube and connecting a small condenser (100 to 500 μ f for *dc* blocking purposes), in series with one leg of the antenna as shown in Fig 2. The pig-tail of the condenser is used as a probe and inserted into the plate connection on the socket. If a better signal is received than with the antenna at the normal connection it indicates trouble in the *rf* stage.

The Mixer Stage

In many receivers a test terminal is provided on top of the tuner for test purposes and alignment. This test terminal usually connects into the mixer grid. There should be as good a picture with the antenna connected to the mixer grid or test point as when it is connected into the plate circuit of the *rf* amplifier tube.

The mixer grid or test point can be grounded intermittently. This should produce flashes and static which demonstrates that signals can pass through the entire video and sound system. Here again, the tube in the mixer circuit can be moved in and out of the socket and clicks and flashes produced.

As in the *rf* tube a small loop of wire may be connected around the grid pin of the mixer tube as in Fig. 3 and the antenna lead-in connected to the wire. Test adaptors are available commercially for this purpose. The adaptor is made so that the tube plugs into it, and the adaptor plugs into the



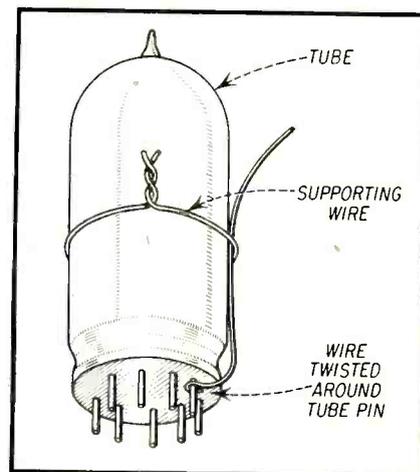


Fig. 3—Test loop for *rf* tube.

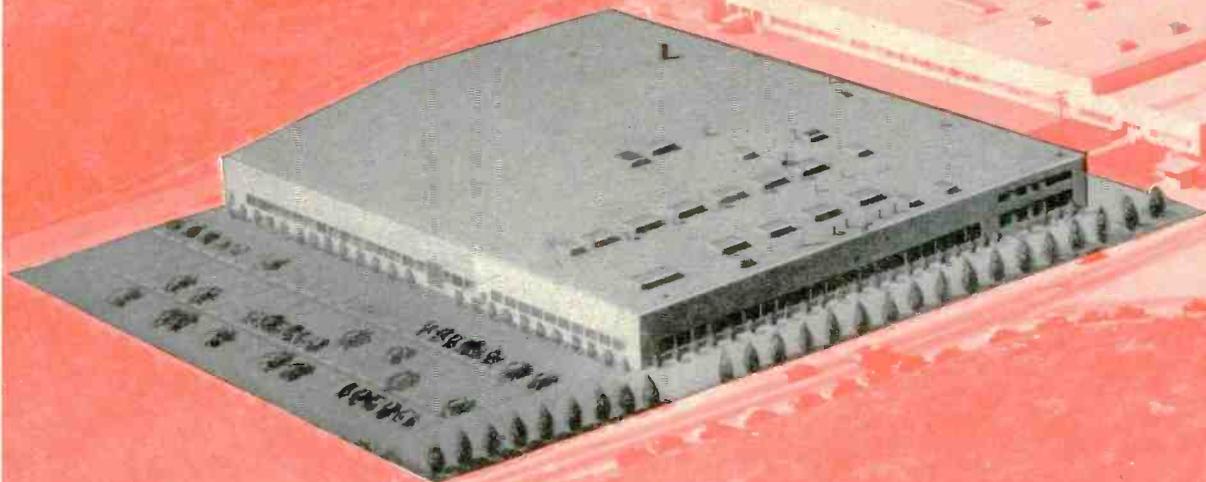It takes the **WORLD'S** Newest **PICTURE TUBE PLANT**...



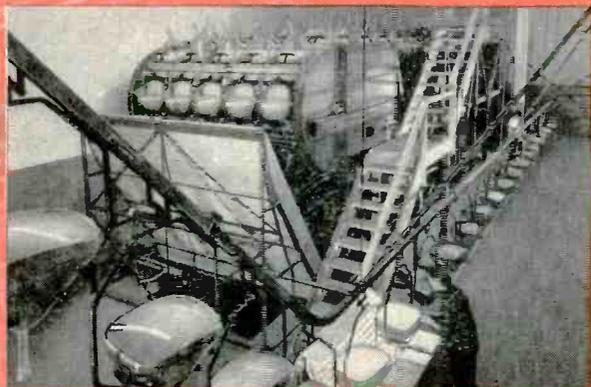
Equipped with the **WORLD'S** Largest **SETTLING MACHINE**...



A BAKE OVEN as Big as They Come ...



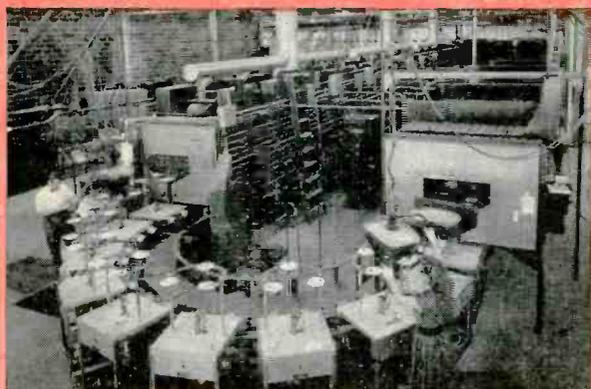And the **WORLD'S** Largest **EXHAUST MACHINE**...



to make the **WORLD'S** Finest **TELEVISION PICTURE TUBES**...

RAYTHEON  **PICTURE TUBES**

The only way to make large screen (21", 24" and 27") TV Picture Tubes of unsurpassed quality is to make them with equipment especially designed to handle and produce them. That's why Raytheon built and has in operation this miracle of a picture tube plant, which houses the world's finest, largest and most advanced equipment and methods for making large size Picture Tubes. This magnificent new plant is one more indication of Raytheon's dedication to a single ideal — to continue to supply you with the finest quality Television and Radio Tubes the world has ever known.



RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division

Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Cal.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • NUCLEPIC TUBES • MICROWAVE TUBES

tube socket. Around the circumference of the adaptor are lugs which permit connection to the tube elements. In the arrangement of Fig. 3 the same thing can be accomplished. The connection of the antenna to the wire will demonstrate whether the mixer and oscillator stages are working by providing picture and sound if they are normal. A "V" type antenna can therefore be connected into the individual circuits as shown in Fig. 4 to make certain that these stages are operating. This will permit quick, easy location of an open circuit in the signal path because the signal will not be passed at the connection where the circuit is open.

Usually the quickest check of whether or not the mixer tube is working is to examine the raster for snow or noise. If there are noise pulses present in the picture tube the mixer circuit is operating. The amount of noise generated in the mixer circuit is usually not sufficient to be heard from the speaker even with the volume control advanced to the maximum position. If a large amount of noise is present in the speaker it is being passed by the *rf* stage, indicating that it is operating. This does not, however, mean that the local oscillator is operating. The oscillator circuit will now have to be checked if the receiver is not producing picture and sound.

Note: Before continuing we might point out that one of the common troubles in tuners, whether wafer switch type or turret, is dirt and grease that form on the contact surfaces. Wiping the contacts with a good contact cleaner fluid is most always the cure for weak pictures and noisy tuners that exhibit flashes on the pix tube. A smart technician makes this one of his first operations when servicing tuners.

The Local Oscillator

The local oscillator generates a different frequency signal for each channel, this frequency being adjustable over a small range with the fine tuning control. The signal from the local oscillator is fed to a mixer tube where it mixes with the signal provided by the *rf* amplifier, (Fig. 5). The mixing cycle which is the numerical difference of the two signal frequencies, the *rf* carrier and the local oscillator. The *if* stages amplify the signal to a suitable level for detection.

To determine if the local oscillator is working use a 20,000 ohm-per-volt meter (or a vacuum tube voltmeter). Connect a 50,000 ohm or larger resistor in series with the meter lead only when using the 20,000 ohm-per-volt

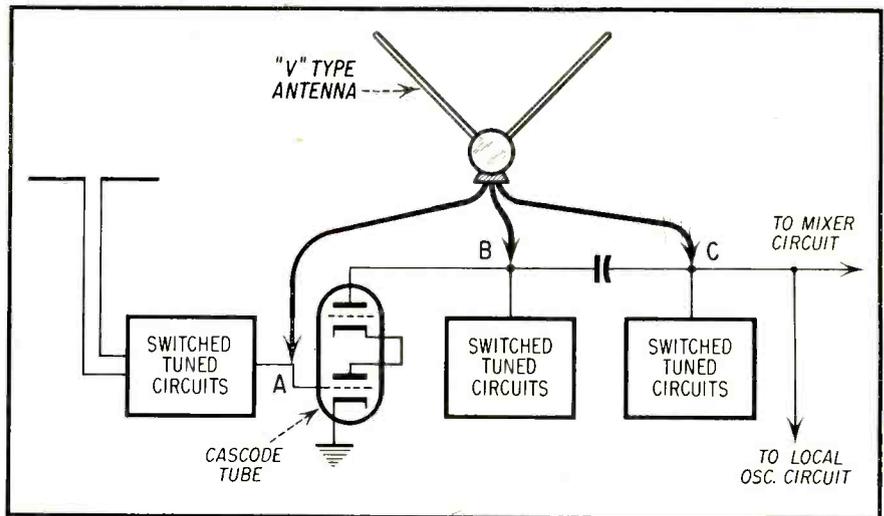


Fig. 4—"V" Type Antenna for testing individual stages.

meter to prevent loading the circuit. The vacuum tube voltmeter has a very high input impedance and will not cause loading so that this resistor is not needed in series with the VTVM lead. Connect the *dc* negative lead of the meter to either the grid of the mixer or the grid of the oscillator tube. At the mixer grid the voltage should be at least 2 volts minus if the local oscillator is feeding the mixer through the coupling condenser. At the oscillator grid the voltage will be higher, around 6 volts minus or more with respect to B minus or chassis whichever connection is called for. If the negative voltages are present at these points the local oscillator is operating.

The negative voltages are developed as the circuit oscillates. They are present only if the circuit is functioning properly. The actual numerical value depends on the strength of these

oscillations. When checking the oscillator the presence of these negative voltages reveals immediately the condition of this circuit.

Another method of determining if an oscillator is functioning is to measure the plate voltage under three conditions. These are as follows:

- A. With the tube out of the socket, the open circuit voltage will be the highest of the three voltages.
- B. With the tube in the socket and the channel selector on channel and everything operating as it should be, the plate voltage should be lower than open circuit voltage but not as low as the voltage reading described below. This last reading first requires a small piece of wire wrapped around the pin as in Fig. 3. Then proceed as follows:
- C. Position the channel selector in

[Continued on page 72]


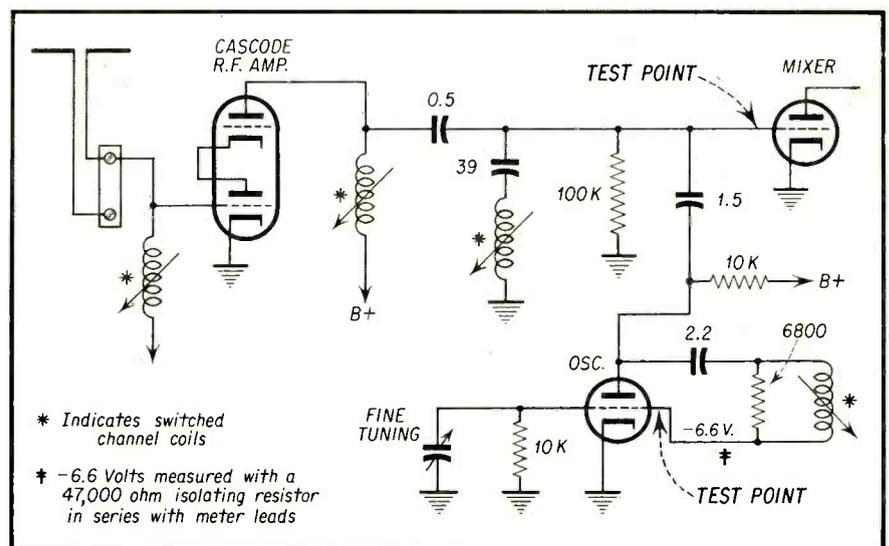
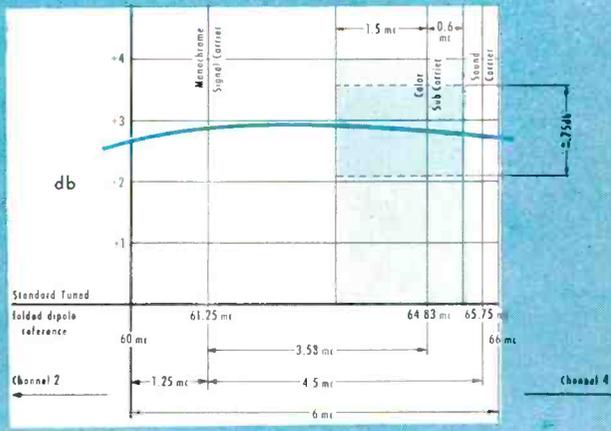


Fig. 5—Testing local oscillator and mixer stages.

you're ready for

COLOR TELEVISION

with an AMPHENOL **INLINE***

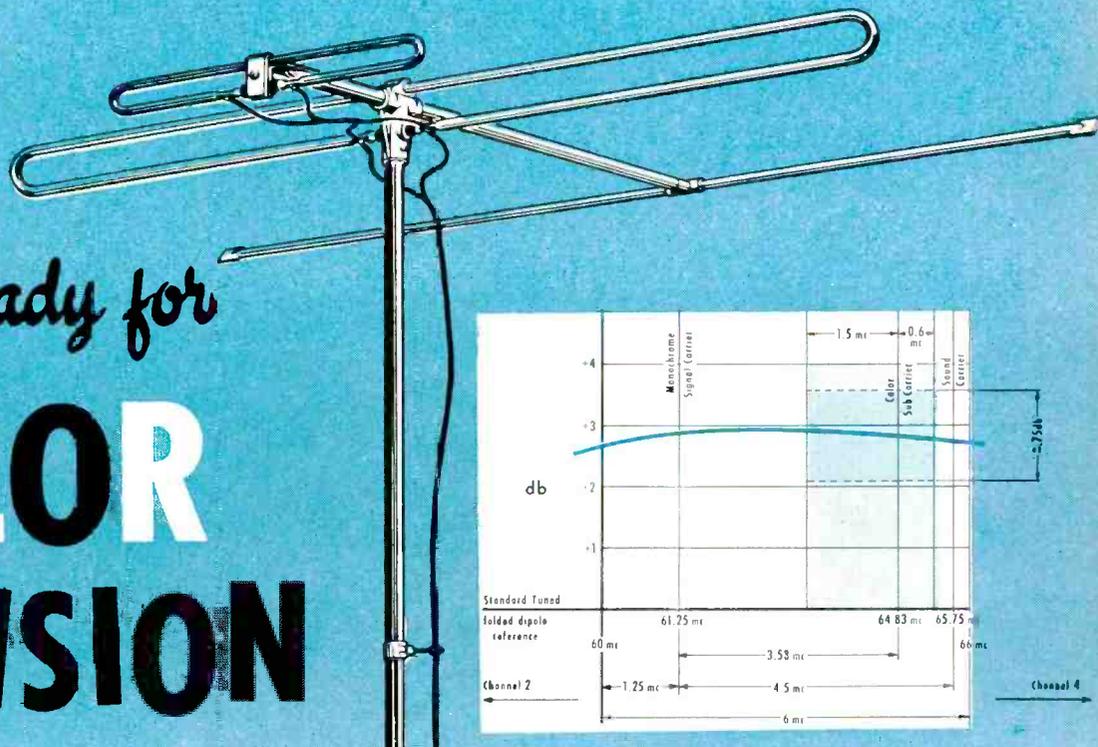

CHANNEL 3

Color television is fast becoming a reality! Sets are expected to be available the first part of next year and stations are purchasing the necessary transmitting equipment. Initial costs, unfortunately, will be high but as improvements in design and production are achieved the price of color television will become within everyone's reach.

The consumer is concerned with the problems presented by television in color. He has read reports on prices and availability; all have been conflicting. He knows, however, that his set will have to be replaced or converted. What he does not know is that if he has an AMPHENOL INLINE*, there will be no extra expense in antenna or installation! AMPHENOL engineers provided for color in the original design of the INLINE*.

Every dealer, distributor and installer will want to acquaint their customers with this reassuring information. The color television market is potentially tremendous. It certainly will prove of benefit if the consumer can be reassured on one part of the cost of conversion to color.

The fact that AMPHENOL INLINES are able to receive color television so well reflects favorably upon the engineering ability of AMPHENOL. For in ordinary black and white television the same level-gain design has proved valuable. Set owners know, now, that their AMPHENOL INLINE* is providing them with the best black and white picture their sets can deliver.

*Reissue U.S. Pat. No. 23,273

Antenna Electrical Requirements for COLOR TELEVISION

Information now available on color television has made it clear that the receiving antenna must have these characteristics:

- 1 Antenna gain must be flat, no gain or loss greater than one db, within 1.5 mc below and 0.6 mc above the color sub-carrier* (a width of 2.1 mc).
- 2 Antenna gain must be held down across the FM frequencies. Rejection of FM signals is much more important in color than in black and white television.

*Channel frequency widths are at present divided between the monochrome amplitude modulation picture carrier and the frequency modulation sound carrier. The addition of the color sub-carrier is made at 3.58 mc above the monochrome carrier.

The AMPHENOL INLINE* fully meets the two conditions listed above. Besides being engineered to reject FM signals, from 88 mc to 108 mc, the INLINE provides very level gain across all channels, particularly over the color sub-carrier. Typical of the INLINE's performance on all channels is the gain chart† illustrated above for channel 3.



†Measured in accordance with proposed RETMA standards.

AMERICAN PHENOLIC CORPORATION
chicago 50, illinois



THIS ANTENNA OUT-PERFORMS:

this ... this ... this ... or this

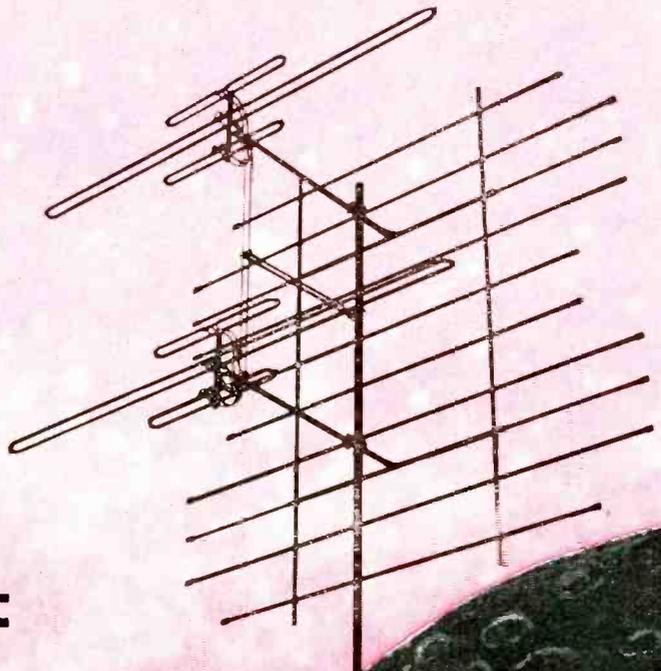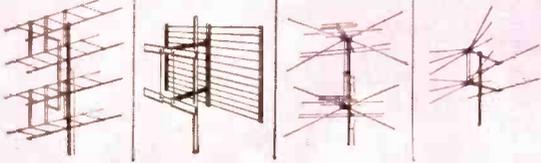

the AMAZING VHF CHAMPION*


a NEW KIND of Antenna
that out-performs every all-channel
VHF antenna ever made — —
and many Yagis, too!

America's servicemen have spoken! In only 2 months, they've made the CHAMPION the nation's top-selling VHF antenna! It's the highest gain all-channel VHF antenna ever developed, and its performance has now been proven by over 30,000 outstanding installations.

Only the CHAMPION has the unique new "Tri-Pole", a triple-powered dipole system in which the Low Band dipole also functions as three dipoles tied together, in phase, on the High Band.

Folded dipoles throughout give close to 300 ohms impedance across entire band. Lightweight, all-aluminum construction. Available in one, two, or four-bays.


CHANNEL MASTER CONQUERS SPACE!

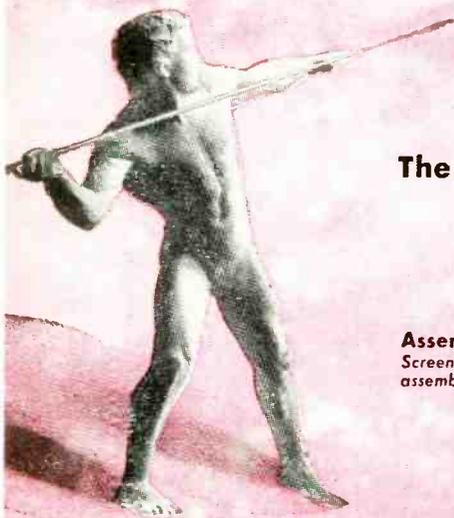

The stacked CHAMPION provides:

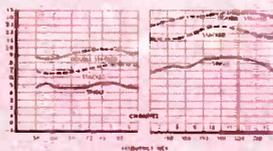- 11-13 DB High Band gain
- 6½-7½ DB Low Band gain

Assembles faster than a five-element Yagi.
Screen "Pops-Up" instantly. "Tri-Pole"
assembly just snaps into place.



horizontal
polar pattern
(relative
voltage)



CHANNEL MASTER CORP.
ELLENVILLE, N. Y.



model no.		list price
325	single bay	\$20.83
325-2	two bay	42.36
325-4	four bay	88.89
Separate Stacking Harnesses		
325-3	2 bay harnesses	\$2.00
325-5	4 bay harnesses	4.15

*Pat. Pend.

3 great, new **UHF** antennas

by **CHANNEL MASTER**

STACKED TWIN CORNER REFLECTOR model no. 406-2



The most powerful UHF fringe area installation you can make today!

- Broad Band coverage — yet out-performs most stacked Yagis.
- Covers every UHF channel, not just segments of the band.
- New impedance-matching, two-stage stacking system.

Another original Channel Master development!

Model No.	Description	List Price
406	Twin Corner Reflector	\$18.06
406-2	2-Bay Twin Corner Reflector. Stacking harness furnished free.	36.10
405-3	Stacking harness only, furnished separately.	2.08

up to
17½ DB

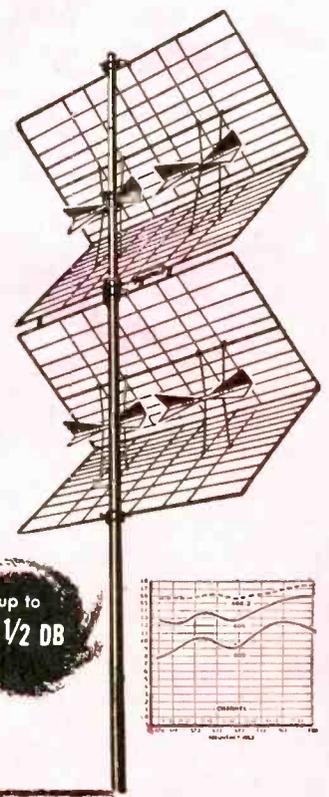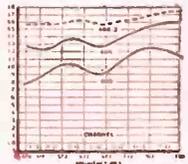


*powerful
new
antennas
span
vast
distances*

the first UHF CORNER REFLECTOR with optional "2-way" mounting!

model no. 409

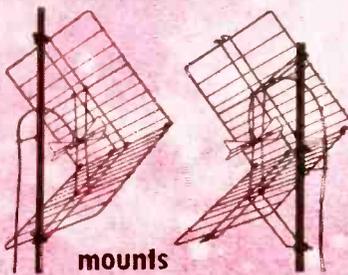Only CHANNEL MASTER'S CORNER REFLECTOR can be adapted to any kind of UHF installation — with or without VHF — at no extra cost. Every antenna contains all necessary hardware and braces for BOTH popular types of mounting. Sharp directivity and unusually high gain across entire UHF band.



mounts

this way . . . or this way

only
\$903
list

Installs instantly! Original Channel Master assembly feature: Screen swings open like a book — dipole assembly snaps into place.

"SWEET 16" The World's First 16-Element UHF Yagi!

- Custom-designed for your particular area.
- Super-power! Sensational fringe area reception.
- Delt-Weld design. Elements WELDED to crossarm. Delta-matched dipole gives uniform impedance.
- Wide band coverage, up to 21 channels.
- Average gain: 13 DB single
16 DB stacked

model no. 420



Send for complete technical literature.

CHANNEL MASTER CORP.
ELLENVILLE, N. Y.




CBS COLORTRON



Application considerations, installation and adjustment procedures are dealt with in this final installment.

(PART 2)

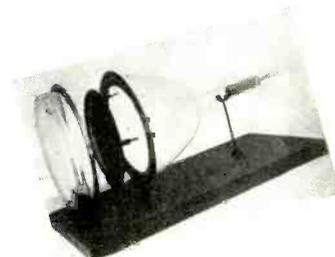

Tube Handling

THE CBS-Colortron should never be lifted by its neck alone. It is recommended that the tube be lifted by the glass bulb and neck, or by the bulb alone. Occasionally, during transportation of the tube, small particles may become lodged between the tube elements. When voltages are applied, momentary sparking may be observed. This sparking is merely an indication of particles being dislodged. It may be necessary, however, to remove some particles by slight tapping. In this case, the tube should be placed on a padded surface with its axis parallel to the surface. Slight tapping with the fingers will, in most cases, dislodge the particles. Special care should be taken to avoid striking or otherwise damaging the metal flange near the face plate of the tube.

In general, the conventional precautions exercised in the handling of black and white tubes apply as well in the handling of the CBS Colortron.

Cover For Face Plate

A safety glass should be mounted in front of the tube when installed in a television cabinet to provide protection against accidental striking of

the face plate and possible tube implosion. This precaution is similar to conventional black-and-white tube requirements.

Supports

Supports for the CBS-Colortron, which weighs approximately 18½ pounds, should be in the form of an insulated support at the large end of the tube and another near the small end of the bulb. Support for this tube should never be provided at the neck of the tube. Since the deflection yoke must be free to move in an axial and traverse direction, tube supports in this area are also not advisable.

High-Voltage Requirements

Briefly stated, the high-voltage requirements of the CBS-Colortron are: anode, 20,000 volts with a maximum current drain of 600 microamperes; convergence electrode, 9,300 volts with a maximum drain of 5 microamperes; and focus electrode, 3,100 volts with a maximum current drain of 400 microamperes. In addition, the regulation of the anode and convergence voltages must be maintained within two per cent to prevent misregistration.

The regulated voltages for the convergence electrode and anode may be derived from a flyback-type deflection system that employs a tapped autotransformer. These voltages are obtained from the full winding of the autotransformer. The focus voltage is obtained from a separate tap of the same autotransformer that supplies the rectifier used for the focus voltage.

Since two-per cent regulation is required for the anode and convergence voltage supply, a shunt regulator or corona discharge tube should be employed.

Adjustment of the focus and convergence potentials can be achieved by

TYPICAL RATINGS - Design-Center Values	
Anode voltage	20,000 volts d-c
Grid-No. 4 (convergence) voltage	11,000 volts
Grid-No. 3 (focus) voltage	3,100 volts
Grid-No. 2 (deflecting) voltage, each gun	500 volts d-c
Grid-No. 1 (control) voltage, each gun	200 volts d-c
Heater-cathode voltage	3 volts d-c
Positive-beam voltage	3 volts d-c
Positive-cathode voltage	4 volts
Peak interpenetration voltage, each gun	110 volts
Heater resistance w/o. respect to cathode	180 volts
During warm-up period: not to exceed 15 seconds	150 volts
After warm-up	140 volts
Heater positive w/o. respect to cathode	15 volts
GENERAL CHARACTERISTICS	
Electrical Data	
Heater for unipotential cathode, each gun	0.3 volts
Voltage	1.8 amperes
Current	1.8 amperes
Focusing method	Electrostatic
Convergence method	Electrostatic
Deflection method	Magnetic
Deflection angle (approximate)	45 Degrees
Electron gun, three	Red, Blue, Green
Phosphor	Development No. R-11 Development No. R-12 Development No. G-11
Fluorescence	Red Blue Green
Phosphorescence	Red Blue Green
Persistence	Red Blue Green
Direct tripartite electron capacitance (approximate)	
Grid No. 1 of any gun to all other electrodes except No. 1 grid of other two guns	7.5 uuf
Three cathodes externally tied together to all other electrodes	17.5 uuf
Grid No. 3 (all three No. 3 grids tied together internally) to all other electrodes	12.0 uuf
Grid No. 4 (common to all three guns) to all other electrodes	7.0 uuf
Screen	Metall-beaded, tripartite, phosphor-dot type
Phosphor-dot arrangement	Approximately 250,000 triangular green, each containing a blue, red, and green dot (a total of 750,000 dots)
Mechanical Data	
Approximate weight	18 1/2 pounds
Face-plate overall length	26 1/8 inches
Maximum diameter	15 3/8 inches
Screen diameter	15 1/2 inches
Sub contact	Metall-flange seal
Base	Small-shall flange design
Mounting position	Any
Socket	Pinch STC1502 or equivalent
TYPICAL OPERATING CONDITIONS	
Anode voltage	20,000 volts
Grid-No. 4 (convergence) voltage	9,300 volts
Grid-No. 3 (focus) voltage	3,100 volts
Grid-No. 2 voltage of 200 volts, each gun	+15 to -100 volts
Grid-No. 1 voltage of -75 volts, each gun	
Grid-No. 2 voltage, each gun	110 volts
Maximum grid-No. 4 current	5 microamperes
Maximum peak grid-No. 1 current	100 microamperes
CRITICAL VALUES	
Maximum grid-No. 1 circuit resistance, each gun	1.5 megohms
Dynamic-convergence voltage, approximate	500 volts
Dynamic-focus voltage, approximate	100 volts
* Heaters electrically paralleled within the tube.	
** Does not include the a-c component of the convergence voltage.	
# For visual estimation of the undeflected, focused spot.	
#† Peak-to-peak value. This a-c voltage is synchronized with the scanning and does not include any voltage developed during the blanking time.	
To reduce the effects of stray magnetic fields on color purity, a magnetic shield is recommended. This shield should fit snugly around the lower portion of the glass bulb. Outline drawing of a recommended shield is shown on page 17.	
CAUTION	
Because the rating of this tube permits operation at voltages as high as 20,000 volts, shielding of the tube for X-ray radiation may be necessary whenever operating conditions involve voltages in excess of 10,000 volts. Sufficient shielding is usually provided by the safety glass in front of the tube.	


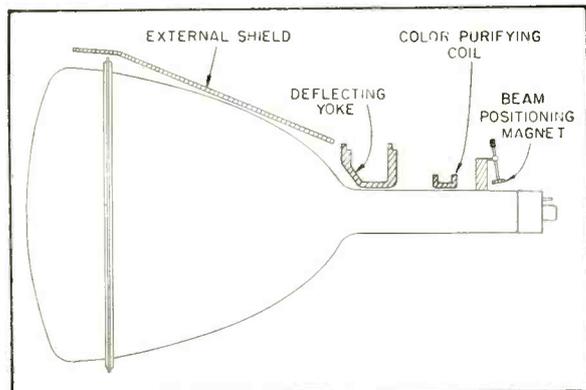



Fig. 4—Cross-sectional view of external components used with tri-color tube. Note the arrangement of these important components.

THE *American* IDEA

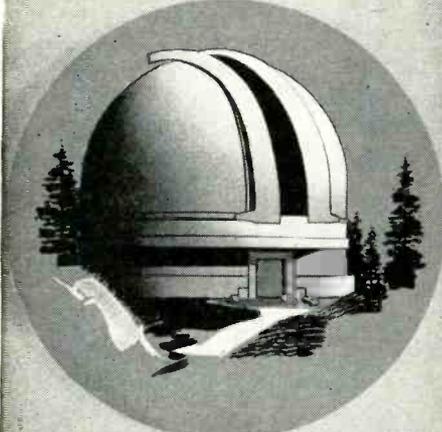

"To find and follow the better way"... Out of the vision of Dr. George Ellery Hale came the great "American Idea" that resulted in the creation of the "Glass Giant of Palomar"—world's largest telescope—to gather new light from the farthest stars for the searching eye of science.

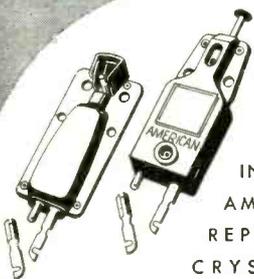With us, the "American Idea" is, by directed effort and applied know-how, to continue to lead in bringing you electronic products of the highest quality.



INSIST ON
AMERICAN
REPLACEMENT
CRYSTAL
CARTRIDGES

Send for FREE catalog 46



American microphone co.

370 South Fair Oaks Ave. • Pasadena, 1, Calif.

2. Energize the color-purity coil.
3. Move the purity coil along the neck of the tube, while simultaneously rotating it, until the purest red field is obtained in the center of the screen. It will be noted that the pattern on the screen also contains alternate blue and green fields extending radially out from this red center.
4. Slide the deflection yoke in the direction of the face plate until the most uniform red field is obtained over the entire screen.

Once the most uniform red field is obtained, slight readjustment of the color purity coil may be required to achieve optimum color purity. The adjustment may be made by varying the current through the purity coil or by additional movement of the coil.

After obtaining optimum purity of the red field, the blue and green fields should be separately checked. No further adjustment of the color-purity coil should be necessary.

Convergence is the next characteristic to be adjusted. This adjustment procedure must be made in two separate parts. Convergence adjustment is facilitated by use of a spot generator. This spot generator should be capable of producing equally spaced horizontal and vertical rows of spots on the phosphor screen. Each of these spots contains individual red, blue, and green components. Proper convergence is attained when the three color components are superimposed.

Initially, the static convergence voltage is adjusted so that spots near the center portion of the screen are converged. If this condition is not obtained, the beam-positioning magnets should be adjusted until the spots within a small central area of the screen are converged.

Dynamic convergence can be optimized after the static convergence is attained. Horizontal dynamic convergence is obtained by adjustment of the waveform and amplitude of the horizontal-dynamic-convergence voltage. This voltage should be varied until each spot of a horizontal row near the center of the screen is converged. Vertical convergence is attained by varying the vertical-dynamic-convergence voltage until each spot of a vertical row near the center of the screen is converged. Because of the interaction between the horizontal-and-vertical-convergence adjustments, it is recommended that these adjustments be performed alternately until optimum convergence is obtained.

The final adjustment of the CBS-Colortron is the setting of the color

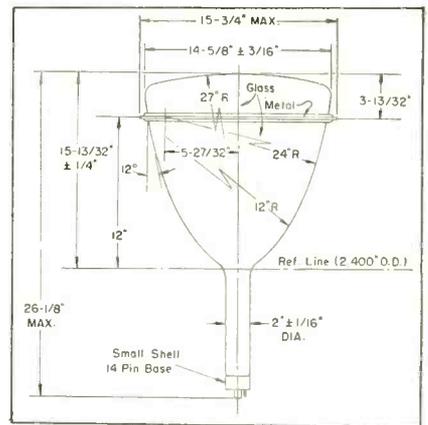


Fig. 6—Outline and mounting dimensions of the new CBS colortron.

balance. As was previously stated, the transfer characteristics and bias voltages of the three gun must be adjusted to produce a grey scale with no color tinting.

The following steps should be taken to achieve color balance.

1. Set each grid-No. 2 voltage at the same value.
2. Set each grid-No. 1 voltage so that a low-level grey field is obtained on the screen.
3. Increase the brightness level of the composite field on the screen. This may be done by varying a master brightness control, or by varying a signal voltage simultaneously applied to all No. 1 grids.
4. As the brightness is increased during Step 3, observe which color becomes dominant.
5. Reduce the brightness of the field to the level in Step 2.
6. Reduce the Grid-No. 2 voltage of the gun controlling the dominant color.
7. Repeat steps 3 through 6 until no color tinting is observed over the required brightness level.

This color-balancing procedure can be simplified by the use of a combination of a density wedge and flying-spot scanner.

The foregoing adjustment procedure represents the method that achieves the fastest alignment consistent with optimum operational quality. After these steps have been completed, further adjustment should not be required. But further adjustment of the various components can be made to overcome any undesirable characteristics that may result from improper initial adjustment.

For typical operational potentials and currents refer to the tentative data chart on page 22.

S.P.A. *

30

MODEL

9.95

LIST

Snyder

PHILADELPHIA

UHF/VHF

Directronic[®]

PORTABLE TV ANTENNA

SENSATIONAL CRISS-CROSS PHASING ELEMENT

- All Channels 2-83
- Maximum Adjustments
- Two 3-Section Staffs
- Gold Tone Brass Staffs
- Brass Plated Phasing Bar

*** SALES PROMOTION APPEAL**

Directronic 6-POSITION BEAM SELECTOR

GIVES clearest picture ON EVERY CHANNEL *INSTANTLY NO WAITING*

- Aids in impedance matching, ghost elimination, orientation.

RETAILED WITH A 5-DAY MONEY BACK GUARANTEE

SNYDER MFG. CO. ANTENN-GINEERS[®] PHILADELPHIA, U.S.A.


BELLEVUE TUBE MILL, INC., PHILADELPHIA, A Snyder AFFILIATE

SNYDER ANTENN-GINEERS LTD., TORONTO, CANADA, A Snyder AFFILIATE

WORLD EXPORT: ROBURN AGENCIES, INC., NEW YORK 7, N. Y.



Symposium Series No. 8

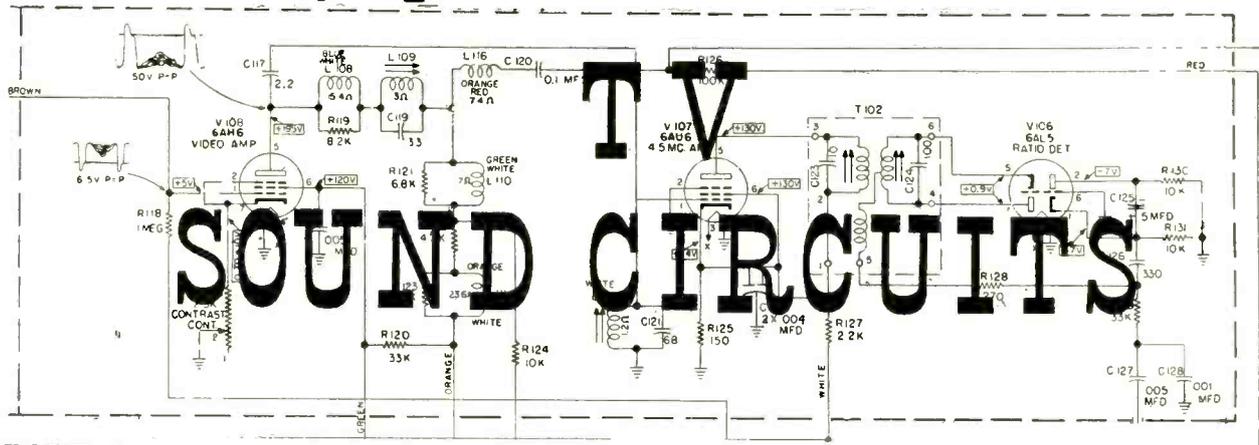

PART 3

by RUDOLF F. GRAF

Aligning Foster Seeley Discriminator

We have a choice of two separate and distinct methods we may use to align this circuit. The first method requires only two pieces of test equipment available in even the smallest shop, namely a *vtvm* and an AM signal generator with a range high enough to cover the sound *if* of the receiver. If a *vtvm* is not available, a multimeter with a sensitivity of 20,000 ohms per volt or better will also serve very nicely.

The alternate method requires an oscilloscope and a sweep generator. This sweep generator should have a built-in marker generator and if not, a separate marker generator is required. Of course both generators must cover the *if* range of the receiver under test. A crystal oscillator makes a good and accurate marker for this purpose. For intercarrier sets which are now more and more becoming the standard of the industry, the *if* is 4.5 *mc*. Now let us see, step by step, how the alignment of the Foster Seeley Discriminator is accomplished. The circuit is shown in Fig. 6.

AM Generator—VTVM Method

1. Set the generator to the audio *if* of the receiver and turn modulation OFF.

2. Connect the probe of the *vtvm* to point (G) at the limiter grid and set the meter to 10-DCV, and to its lowest range. If a connection at this point is inconvenient, the meter may be connected between point (A) and ground. The results will be the same but in this case the lowest +DCV range must be used.

3. Connect the generator output to the antenna terminals or the mixer grid if a conventional TV receiver is used, or to the grid of the video amplifier if the set has intercarrier sound. (In a conventional TV it would be advisable to disable the local oscillator when aligning the sound circuit. This may be done by removing the oscillator tube.)

4. Peak all of the *if* stages for maximum meter reading. If the meter goes off scale, do not increase the range, but decrease generator output.

5. Connect generator to point (G) and meter (still on lowest range) to (A).

6. Adjust primary of discriminator transformer for maximum meter reading.

7. Move meter to (B) and adjust secondary of discriminator transformer for zero reading. This zero must occur between a plus and a minus peak.

8. In order to check linearity of alignment, set meter to midscale with Zero Adjustor, and connect it to point (B) and ground. Move the generator frequency several kilocycles above and below the *if*. For equal deviation from the center frequency, the meter should give equal deflections in a positive and negative direction. If this does not occur repeat the alignment from the beginning.

Sweep Generator-Scope Method

1. Connect vertical input lead from scope to point (B) and connect a good ground between the scope and the chassis.

2. Set sweep generator to the audio *if* of the receiver under test and adjust for a sweep width of approximately 300 *kc*. Connect generator output to point (G). Set marker generator to the sound *if*. If an external marker is used turn the modulation OFF.

3. Connect the horizontal deflection voltage from the FM generator to the horizontal input of the scope to obtain the "S" curve shown in Fig. 10.

4. Adjust the primary of the discriminator transformer for proper linearity. (See Fig. 10)

5. Adjust the secondary of the discriminator transformer for proper center frequency as indicated by the marker pip. (See Fig. 10)

6. Vary the marker frequency above and below the *if* to check the width of the linear portion of the S curve. The frequency covered by the marker generator in going from the top to the bottom of the linear portion indicates the bandwidth of the circuit.



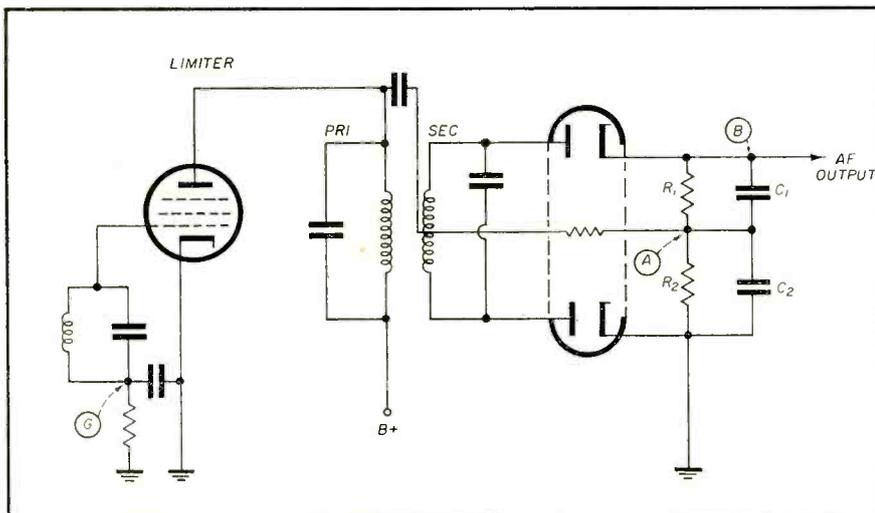



Fig. 6—Foster-Seeley discriminator with all test points indicated in the diagram.

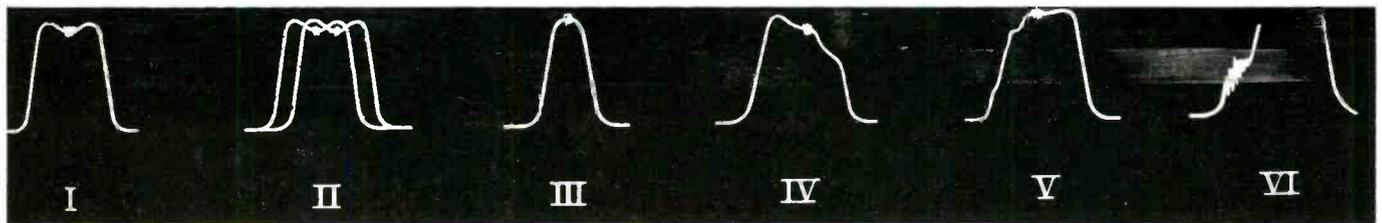


<p>I Proper response curve at points G or A, marker pip in center. Pattern's top should be as flat as possible; yet have required bandwidth.</p>	<p>II Same as I, only pattern of return trace not in phase with pattern of forward trace. Adjust PHASE CONTROL on the sweep generator.</p>	<p>III Response curve too narrow to accept full signal. Realign in order to increase the bandwidth.</p>	<p>IV Asymmetrical response curve will cause distortion in sound. Realign for better response curve.</p>	<p>V Another asymmetrical response curve; this time the non-symmetry is on the other side. Realign.</p>	<p>VI Curve indicates undesirable oscillations. May be due to poor grounds, open bypass condensers, poor shielding or bad tube.</p>
--	--	---	--	---	---

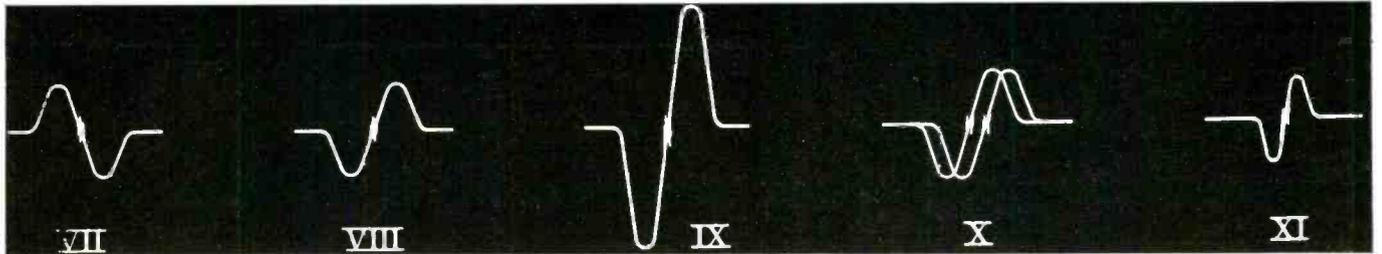

<p>VII Proper response curve at point (B) of ratio detector or Foster-Seeley discriminator. Curve is symmetrical and smooth.</p>	<p>VIII Same pattern as in (7), except horizontal deflection voltages are 180° out of phase with respect to each other.</p>	<p>IX Vertical gain control of 'scope is set too high. Pattern looks out of proportion; is difficult to analyze.</p>	<p>X Same as (8), except that return trace pattern is not in phase with forward trace pattern. Some people prefer this dual pattern to the superimposed single pattern.</p>	<p>XI Curve indicates insufficient band-width; will distort the signal. Realignment is definitely indicated.</p>
--	---	--	---	--

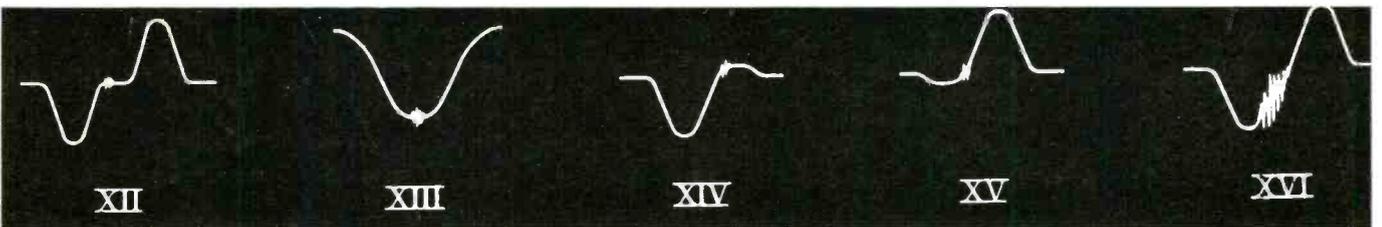

<p>XII Distorted "S" type curve. Secondary of discriminator transformer must be adjusted to obtain curve shown in (8).</p>	<p>XIII Another form of distortion in the "S" curve. In this case the primary of the discriminator transformer must be adjusted.</p>	<p>XIV Pattern produced if one of the diodes has a lower emission than the other. Tube must be replaced.</p>	<p>XV Another pattern produced by poor emission of one of the diodes, this time the other diode. As in (14), the tube must be replaced.</p>	<p>XVI "S" curve indicating undesirable oscillation. May be due to same trouble indicated in (6).</p>
--	--	--	---	---

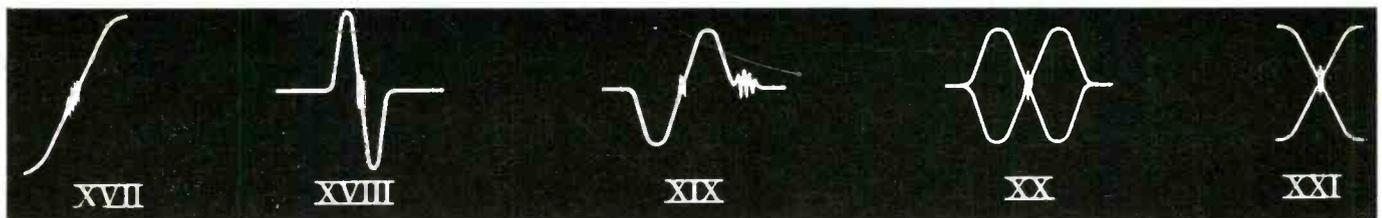

<p>XVII Pattern produced if FM generator has insufficient sweep, or if sweep width is insufficiently advanced. This pattern does not give enough data.</p>	<p>XVIII Sweep width of FM generator set too far. Pattern too narrow to indicate bandwidth and linearity properly. Reduce sweep width of generator signal.</p>	<p>XIX Detector response curve okay, but some oscillation present at a frequency outside the band used. Will not affect sound but should be checked.</p>	<p>XX Butterfly or double "S" curve produced by using internal sweep of the 'scope set at 120 cps. Cross-over point should occur at IF of the set.</p>	<p>XXI Same curve as in (20), except that sweep width of the FM generator has been reduced.</p>
--	--	--	--	---

Fig. 10—Response curves obtained on CRT 'scope showing proper patterns and those indicating trouble in set.

7. Connect the FM generator output with the marker signal to the antenna terminals or the mixer grid in a conventional receiver, or to the grid of the video amplifier if the set has intercarrier sound. (As before, it is advisable to disable the local oscillator if you are dealing with a conventional TV receiver.)

8. Connect the lead from the vertical input of the scope to point (A).

9. Adjust all of the *if* stages for proper response. (See Fig. 10) Do not attempt to realign the discriminator transformer at this time.

10. Always keep the gain control on the scope as high as possible and the output from the generator very low. This must be done so as to avoid any possibility of saturating the limiter and getting a faulty alignment.

11. To check the overall alignment leave the generator where it is and reconnect the scope at point (B). The straight "S" curve should appear again. If any slight touch-ups are required they may be done now.

Aligning Ratio Detector

As with the Foster Seeley discriminator, we again have a choice of two methods of alignment. As before, one of the methods requires the use of an AM generator and a meter. The other employs an FM generator with a suitable marker and an oscilloscope. When we use the former of the two methods, there is a little alignment aid that is necessary when we deal with the Unbalanced Ratio detector. This little "gimmick" is shown in Fig. 8 in the form of two dotted resistors R_1 and R_2 . The actual value of these resistors is not critical, but they should be some-

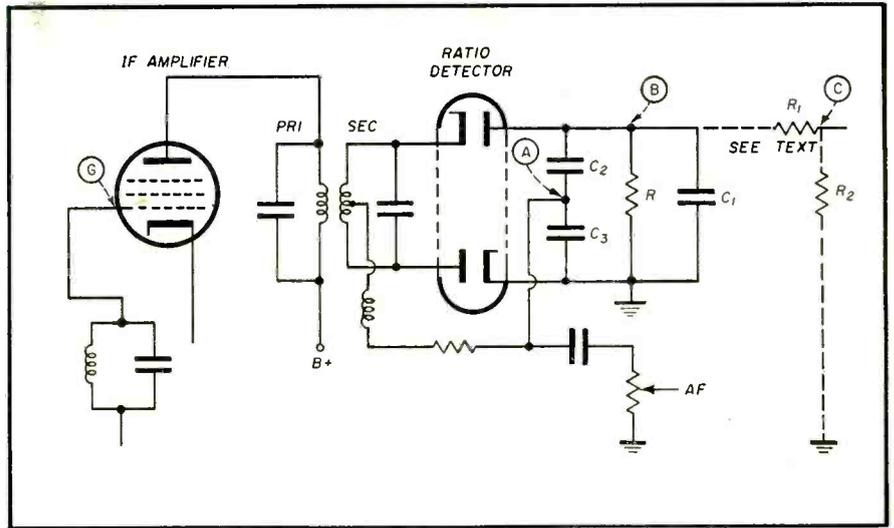


Fig. 8—Schematic diagram of an unbalanced ratio detector with test points indicated.

where between 100,000 and 200,000 ohms each. The thing that is important however, is that the two resistors are accurately matched. That is, their actual measured values should be as close to each other as possible. They should not differ from each other by any more than at the most 1%. Once you have selected such a pair of resistors, put them aside, and save them for use anytime you have to align an unbalanced Ratio detector. The alignment instruction that follow apply to the balanced and the unbalanced Ratio detector.

AM Generator-VTVM Method—Unbalanced Ratio Detector. (Fig. 8)

1. The two matched resistors described above are required for this alignment. Connect them between point (B) and ground in such a manner, that

their junction point (C) is readily accessible.

2. Set the generator to the audio *if* of the receiver and turn modulation OFF.

3. Set the meter to -DCV on its lowest range and connect to point (B).

4. Connect the generator output to the grid of the *if* amplifier. (Point (G)).

5. Adjust the primary for maximum meter reading.

6. Connect the Common lead of the meter to point (C) (the junction of the temporarily added resistors) and the other meter lead to point (A). Now align the secondary for true zero reading.

7. In order to check the linearity of alignment leave all connections as in 6 above. Set the meter to mid-scale or any other reference point with the ZERO ADJUST. Move the generator frequency several kilocycles above and several kilocycles below the sound *if*. For equal deviations from the center frequency, there should be equal deflections in a positive and negative direction. If this does not happen, repeat the alignment process from the beginning.

8. Remove resistors R_1 and R_2 and save for future use. Detector alignment is now complete.

9. In order to align the *if* stages, reconnect the meter between (B) and ground, and adjust all *if* circuits and sound traps for peak reading.

AM Generator-VTVM Method Balanced Ratio Detector. (Fig. 7)

1. Set the generator to the audio *if* of the receiver and turn modulation OFF.

2. Set the meter to -DCV on its lowest range and connect to point (B).

3. Connect the generator output to point (G) on the grid of the *if* amplifier.


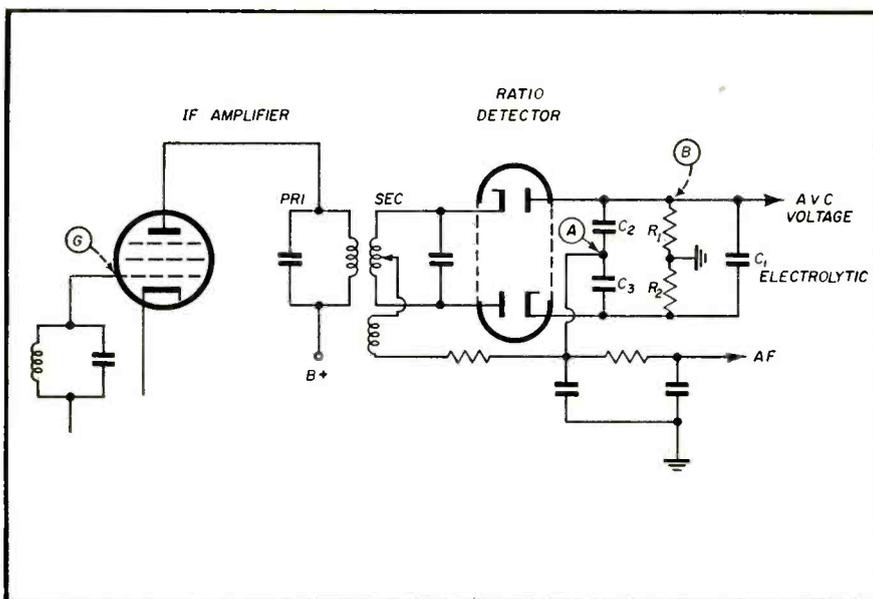


Fig. 7—Schematic diagram of balanced ratio detector with test points indicated. The audio signal is taken from point A.

NEW JFD "3-in-one" LIGHTNING ARRESTER

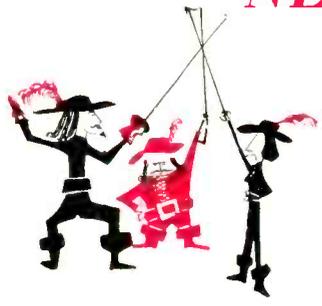

No. AT110 with hardware for wall or window sill mounting, \$1.50, list.

No. AT110S with stainless steel strap for pipe mounting, \$1.75 list.

Both feature the patented JFD strain-relief lips which prevent contact washers from ripping the lead-in wires apart!



JFD MANUFACTURING COMPANY, INC

World's largest manufacturer of tv antennas and accessories; Brooklyn 4, New York

one for all... all for one

1. for UHF or VHF tubular twin lead
2. for VHF flat twin lead
3. for VHF or UHF open wire

4. Adjust the primary for maximum meter reading. If the needle goes off scale, reduce the generator output rather than increase the meter range.

5. Move the meter to point (A), and align the secondary for true zero reading. This zero must occur between a positive and negative peak.

6. The linearity of alignment should now be checked as outlined in step 7 above.

7. Detector alignment is now complete. In order to align the *if* stages, reconnect the meter to point (B), and peak all *if* stages and sound traps.

Sweep Generator-Scope Method For Balanced Or Unbalanced Detector

1. Connect the vertical input lead from the scope to point (B), and properly interconnect the grounds of the scope, the chassis under test and the signal generator (S).

2. Set the sweep generator to the audio *if* of the receiver, and adjust the sweep width to approximately 300 kc. Also set the marker generator to the *if* of the receiver. Connect signal at *if* grid (G).

3. Temporarily disconnect one side of the electrolytic condenser *CI*.

4. Connect the horizontal deflection voltage from the sweep generator to the horizontal input terminals of the oscilloscope to obtain an "S" curve. (See Fig 10)

5. Adjust the primary and secondary to obtain a linear "S" curve with the correct center frequency. It may be required to alternate adjustments between the primary and the secondary before a final setting is obtained.

6. Reconnect *CI*.

Trouble Shooting

Trouble in the FM detector stage can


show up as poor sensitivity, noise, distorted output, high frequency hiss, or any combination of the above. Troubles of this type do not originate at the detector every time they occur, so it is important that we eliminate all other stages before we "dig" into the detector. We should look for trouble before, as well as after the detector. The audio stage can be quickly checked with a phono-pickup and the stages before the detector should be subjected to the usual procedures for troubleshooting, such as tube checking and voltage and resistance analysis as well as signal tracing. The detector circuit is, of course, subject to the usual troubles such as open resistors and coils, and shorted, leaky or open condensers.

A simple method of determining whether the trouble is before or after the discriminator involves the voltage across the grid resistor in the limiter shown in Fig. 6. If a negative voltage is developed across this resistor (point (G) to ground) when an *if* signal is applied to the preceding stages, then the trouble is after this point. Now, if the audio stages have also been found to be OK, the trouble has been localized to the stage between the limiter and the audio amplifier—the detector. If the noise level of the audio signal becomes abnormally high, the trouble probably lies in the limiter. You will recall from the beginning of this article that the limiter clips off all noise pulse since the discriminator is not able to eliminate them. Hence if there is noise, the limiter is not doing its job. The limiter is operated with *unusually low* plate and screen voltages. Check them to see if they are as low

as they should be. If they are higher than the manufacturer's service notes specify, that stage works simply like another *if* amplifier and does not clip off the noise pulses. If you can not get a true zero at point (B), this may be due to the fact that the two diodes have widely different characteristics, or that the two resistors *R1* and *R2* are not sufficiently close in value, or simply that the set is not aligned properly. Various conditions of alignment are shown in Fig. 10, and this chart should be kept handy when aligning FM detector stages.

Now the ratio detectors in Figs. 7 and 8 do not require a limiter because the electrolytic condenser *CI* together with whatever resistance is in parallel with it absorb and suppress noise pulses. Hence, if the set becomes noisy, the condenser and the resistor (or resistors if the detector is of the balanced type) should be checked. This condenser is a high capacitance-low voltage type which usually does not short, but like all electrolytics it may lose capacitance after a while, particularly if the set has been idle.

If the higher audio frequencies are unusually strong and if there is a strong hiss, we should suspect the condenser used in the de-emphasis network. Due to heat this condenser may open. This trouble may occur in any FM receiver regardless of the type of detector used. This trouble is not always noted since it may generally be almost completely compensated for by an adjustment in the setting of the tone control. Low output is generally caused by bad tubes, misalignment or leaky coupling condensers in the first *af* amplifier.

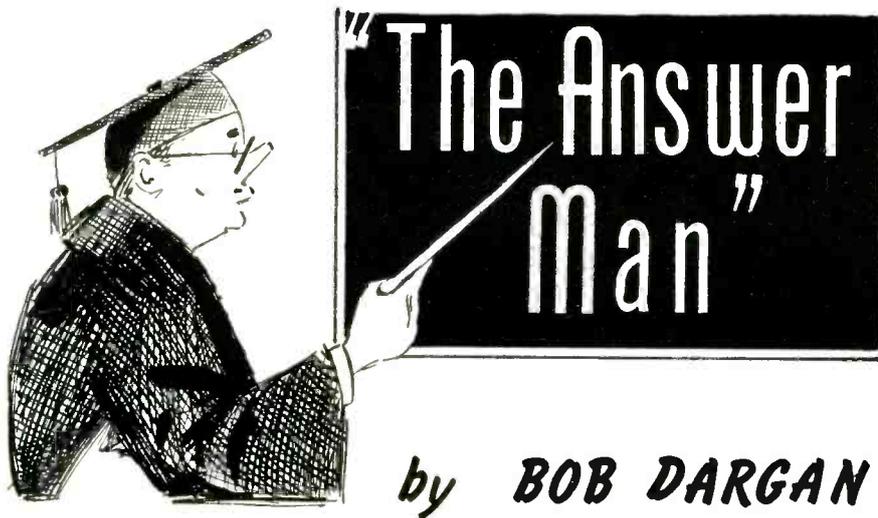

Do you have a vexing problem pertaining to the repair of some TV set? If so, send it in to the Answer Man, care of this magazine. All inquiries acknowledged and answered.

Dear Answer Man:

I have a model RCA 7T104 which goes out of sync after an operation of from an hour on. Before going out of sync there is a noticeable pull on the right side of the picture tube as when the horizontal oscillator transformer is out of adjustment. Adjusting the horizontal drive and lock-in range has no effect once it drops out of sync, but when the width control is turned full counter-clockwise it will drop into sync but this narrows the picture. I have changed the resistors in the hold control, etc., with no effect.

C. A. S.
Bronx, N.Y.

Dear C. A. S.:

One of the most common failings of Television servicemen is their negligence in replacing all tubes by substitution in the circuits where the

trouble can possibly exist. It always goes without saying that the tubes should have been substituted. In this case the 6SN7 and 6BG6 tubes are assumed to be good tubes.

The most probable cause of drifting of the horizontal frequency is the blocking oscillator condenser, 180 μf at the grid, pin #4, of the 6SN7 horizontal blocking oscillator. The condenser is changing capacitance during the first hour period until the phase comparer can no longer take care of the correction of the frequency, with the result that the horizontal oscillator goes out of sync. See Fig. 1.

The horizontal oscillator is corrected in frequency when the width control is rotated counter-clockwise because in this circuit the B plus voltage is fed to the width control through the variable arm. When the width con-

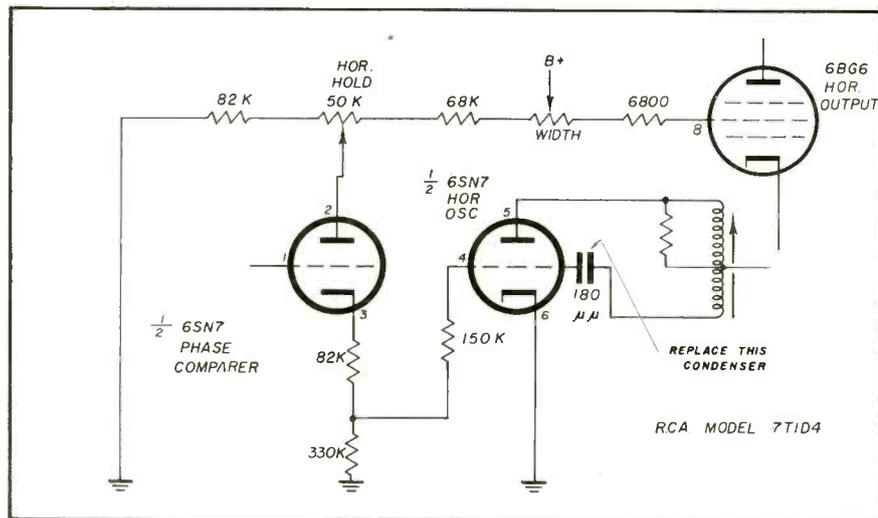


Fig. 1—Changing blocking oscillator condenser in RCA Model 7T104.

trol is adjusted in the minimum width position that same position permits maximum voltage to be supplied to voltage divider resistors of the horizontal hold control. The increase in positive voltage supplied to the hold control causes heavier conduction in the phase comparer tube with a resultant larger voltage supplied from the cathode circuit of the phase comparer to the grid, pin #4, of the horizontal blocking oscillator. The increase in grid voltage supplied to the horizontal blocking oscillator brings it back into frequency correcting for the change in capacity of the condenser.

• • •

Dear Answer Man:

I have several customers who have complained to me about a ghost on Channel 2. I have tried a number of things to correct this trouble and they have not worked out. The problem is rather common, I understand, and therefore I have not done much about it. What do you suggest?

L. M.
Chicago, Ill.

Dear L. M.:

There are a number of things that can cause this type of trouble. Ghosts on Channel 2 are often caused by the antenna. Changing the type in many

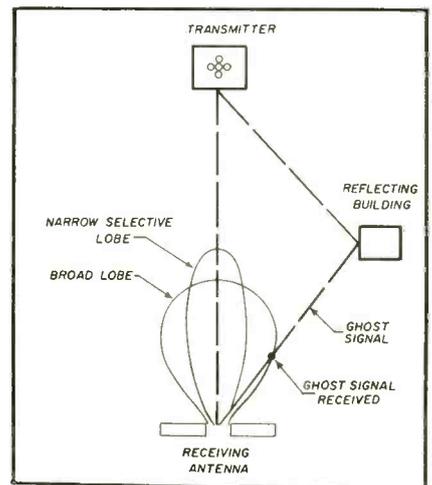


Fig. 2—Broad lobe antenna brings in ghosts with greater amplitude.

cases will correct the ghost. Most TV antennas are not cut to favor Channel 2 with the result that ghosts can originate because of the mismatch at the antenna and in the transmission line. Also, a very broad receiving lobe can cause this trouble if the ghost is due to reflections and therefore caused by a delayed second signal. See Fig. 2.

Mismatch resulting in standing waves and reflections on the transmission line can also cause ghosts on a particular channel. One type of stubbing has been found to be very

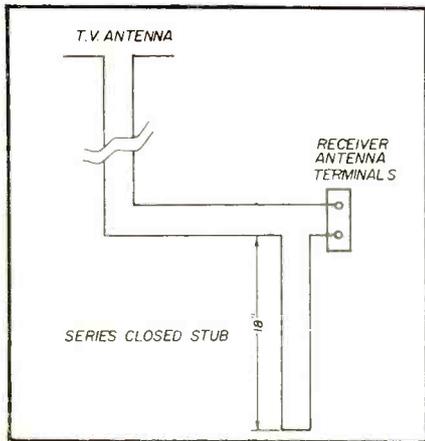


Fig. 3—Use of series closed stub to eliminate ghosts on channel 2.

effective. It is the closed stub in series with one side of the transmission line. This stub will cancel the reactive component at the receiver and the termination will be mostly resistive. In most cases the stub should be of the closed type. The technician starts with a piece of twinlead of about 24 inches and reduces the length to about 18 inches which is the optimum in many instances. However, there are other cases where an open stub is more effective in balancing out the reactive component.

Stubbing of the antenna to give better reception is not something new, but most technicians think only in terms of parallel stubs and never consider the series type as illustrated in Fig. 3. Stubbing is experimental and usually involves a *cut-and-try* procedure. In general the series closed stub about 18 inches long has proven successful in eliminating many ghost problems on Channel 2.

One other point concerning this is the mixer plate coil. The mixer plate

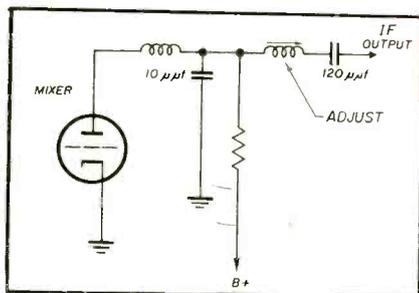


Fig. 4—Adjusting mixer plate coil can eliminate ghosts on channel 2.

circuit can in some cases cause this difficulty also. The staggered tuned coil in the mixer plate circuit can be adjusted one turn in either direction to help overcome the apparent ghost if the technician is careful (Fig. 4). He should be able to return to the original setting if no improvement is experienced.

LAST CHANCE!

Time is running out on this very special introductory offer. After January 1, 1954, Sangamo will accept no more orders from jobbers for these kits. Be sure to get yours while they are still available.



this
Sangamo
Telechief
SPECIAL
INTRODUCTORY
OFFER

will soon
be withdrawn.
See your jobber today!

Only
\$24.00

Slightly higher in Canada

Here's a deal you can't afford to miss. You get a basic balanced inventory of fast-moving "Telechiefs"—assortment based on national popularity—PLUS a heavy gauge steel chest with two extra drawers for small parts—PLUS your choice of 100 attractive folders to promote your business. You get all this for only \$24.00—the dealer net price of the capacitors alone. (They list at \$40.00.)

Get acquainted with the Telechief today—join the thousands of alert servicemen who have already taken advantage of this big bargain in premium molded paper tubular capacitors.



You can have 100 of any of these business-building folders without extra cost—a sample of each is enclosed in the kit.



Those who know... choose Sangamo

BC48-17A

SANGAMO ELECTRIC CO. MARION ILLINOIS

Dear Answer Man:

I am a TV serviceman and have converted a smaller TV receiver for use with a 21 inch size picture tube. The conversion worked out very nicely except for one difficulty. After a few hours of operation the high voltage system develops a blooming condition as the brightness control is advanced.

I have replaced the 1B3 high voltage rectifier tube four times and after each replacement the set works fine for a period of hours and then the same condition develops. What do you think is the cause of this condition?

T. T.

New Hyde Park, Long Island


Dear T. T.:

A condition of repeated blooming often occurs in receivers due to insufficient filament voltage being applied to the high voltage rectifier tubes. In series with one side of the filament lead to the high voltage rectifier tube is a resistor and the purpose of this resistor is to reduce the voltage available from the transformer to a proper value for the operation of the H.V. rectifier tube.

If the voltage applied to the tube is larger or smaller than required, difficulties will develop. If the voltage is insufficient to heat the emitting ma-

[Continued on page 66]

THE "TELCO TEN"

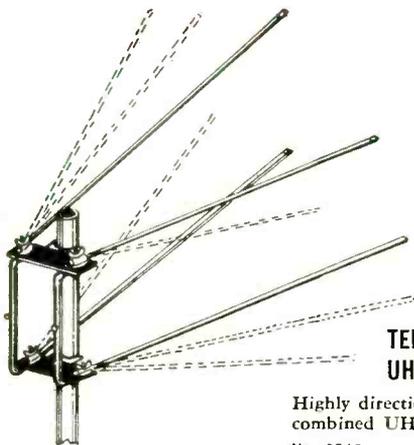


NEW!

TELCO "DOUBLE V" UHF-VHF ANTENNA

Highly directional...adjustable for combined UHF-VHF 50°-70°-90°.
No. 9010 List \$6.95

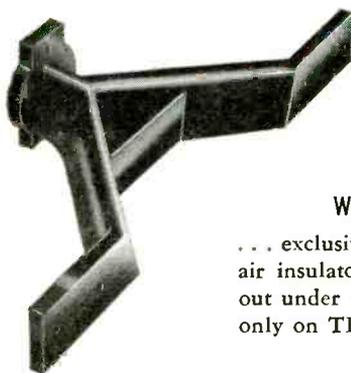... the "T" formation line—T for Top Quality and T for Ten Antenna Styles. Insist on TELCO ... the best TV antennas for the greatest "show" on earth.




WISHBONE

... exclusive with TELCO, is a free air insulator that prevents shorting out under any condition ... found only on TELCO UHF Antennas.

FREE CATALOG—illustrates all TELCO products. Available at your jobber or write direct today!



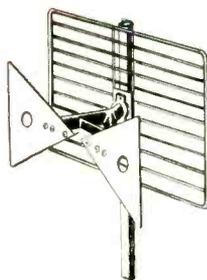
TELEVISION HARDWARE MFG. CO.
DIVISION OF GENERAL CEMENT MFG. CO.
914 Taylor Street Rockford, Illinois




TELCO UHF "GOLDEN GRID" SUPER DELUXE BUTTERFLY ANTENNA
No. 8965 List \$5.95



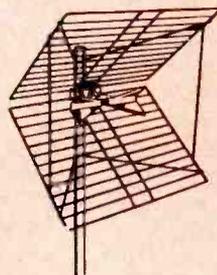
TELCO UHF "GOLDEN GRID" STANDARD BUTTERFLY ANTENNA
No. 9001 List \$3.95



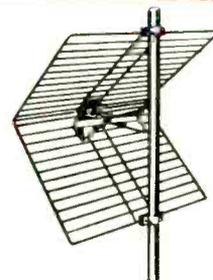
TELCO UHF "GOLDEN GRID" DELUXE CORNER REFLECTOR ANTENNA
No. 8984 List \$11.25



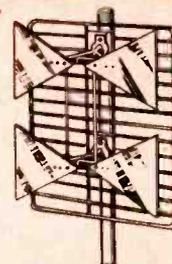TELCO UHF "GOLDEN GRID" STANDARD CORNER REFLECTOR ANTENNA
No. 9002 List \$11.25



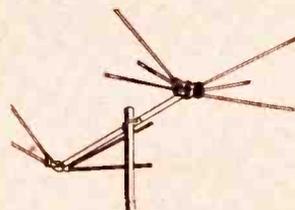
TELCO UHF "GOLDEN GRID" 2-STACK DOUBLE TIE ANTENNA
No. 9004 List \$7.50 less mast




TELCO VHF CONICAL ANTENNA
No. 8700 List \$9.25



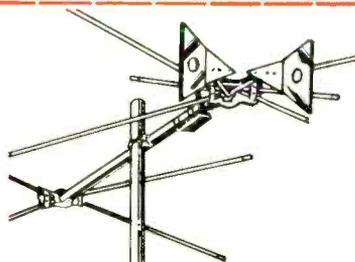TELCO VHF SUPER CONICAL ANTENNA
No. 8902 List \$19.85



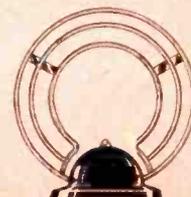TELCO UHF-VHF UNIVERSAL CONICAL ANTENNA
No. 8981 List \$16.25



TELCO UHF-VHF "GOLDEN HALO" INDOOR ANTENNA
No. 9000 List \$4.95

COLOR TV

by **LEONARD LIEBERMAN**

Basic principles of color TV transmission and reception explained for the serviceman

THE NTSC color system (Fig. 1) consists of a transmitting section in which a scene is scanned by a three color camera. The camera output is then mixed with other necessary signals so that the transmitted signal is composed of the following elements:

1. An amplitude modulated video r-f carrier signal corresponding to the present monochrome signal.
2. An amplitude and phase modulated color sub-carrier.
3. The same horizontal and vertical sync signals as transmitted at present plus an additional color sub-carrier reference signal (color burst).
4. The sound system remains the same as at present.

At the receiver, the signal is treated as at present up to the video detector. The sound and sync sweep systems remain the same with some slight modifications. The brightness or luminance portion of the video signal is handled through video amplifiers, essentially the same as at present. The color or chrominance signal is processed in the color decoder so that at its output we have the original three color signals. These signals, when added to the lumi-

nance signal at the input of the color CRT, result in a reproduction of the scene at the camera.

Picture Channel Consideration

Before going into the details of the blocks in Fig. 1, let us first examine the basic principles of the color system. In the monochrome signal, the picture details are determined by:

1. The degree of whiteness of the scanned element (white and different shades of grey and black).

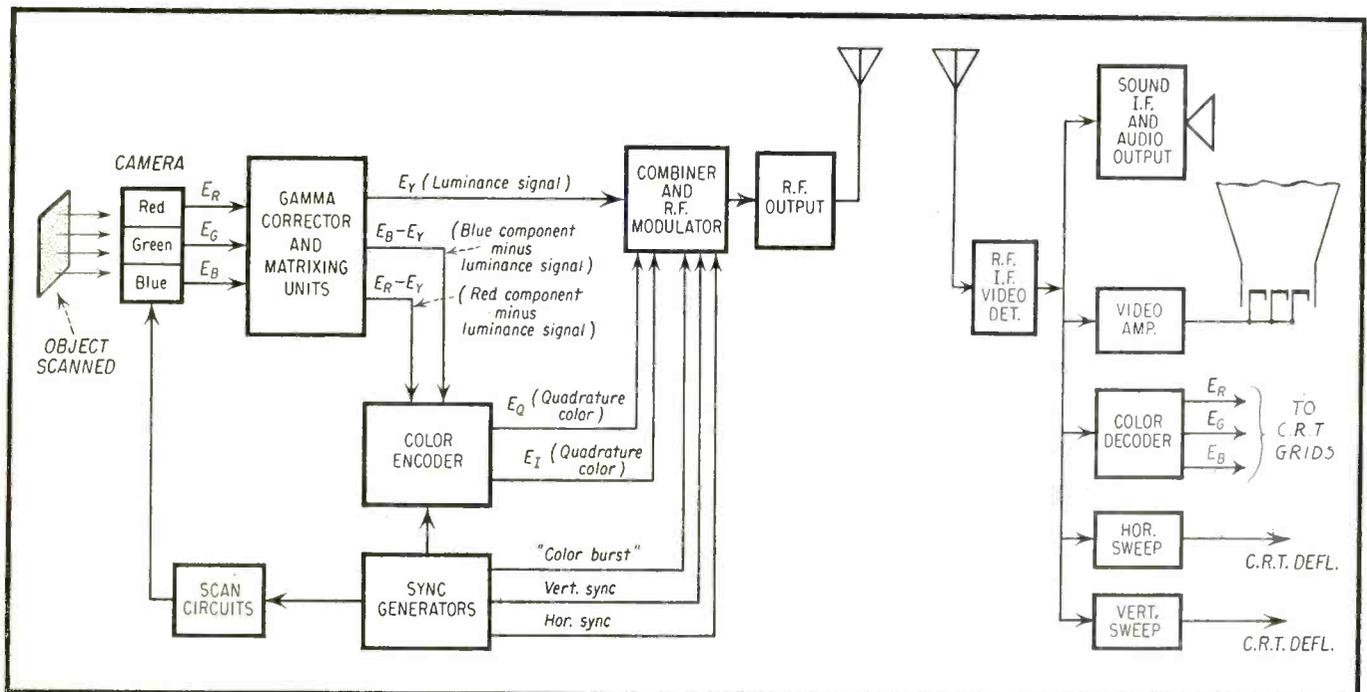


Fig. 1—Block diagram of NTSC System showing transmitter and receiver.

2. The degree of brightness of the over-all scene.

In the color picture, as stated previously (*Nov. RTSD*), the picture detail is determined by:

1. Hue (color).
2. Saturation (shade of color).
3. Over-all scene brightness.

In the NTSC compatible color system, the equivalent of the monochrome video information is carried in what is known as the *luminance* channel. This channel is an amplitude modulated signal at the video carrier frequency. It is a vestigial side-band modulated signal, as at present.

The color information is carried on an additional frequency which is both phase and amplitude modulated. This is called the chrominance or chroma channel.

Where no provision is made in the receiver to demodulate the chrominance sub-carrier, as in present monochrome sets, only the luminance channel appears at the CRT. In this way, a color picture can be received in black and white on a monochrome receiver. In the color TV receiver, however, the demodulated chrominance channel is added to the luminance channel at the CRT and the result is a color picture.

Chrominance Channel Considerations

Let us look a little closer into some of the relationships of the luminance and chrominance channels. It has been proven that the eye, at normal viewing distance, is insensitive to fine detail in color. That is, the eye tends to integrate the fine color details, at a distance, into a single color. The result is that the chroma channel does not need as wide a frequency response as the luminance channel.

The chroma channel itself, consists of two sub-channels. These sub-channels operate at the same frequency, but in a certain fixed phase relationship to each other (90°). The purpose of this phase difference will be discussed in detail further on in this article.

Fig. 2 shows the demodulated luminance and chrominance channels in their relation to each other. A quick glance would seem to indicate that there is a contradiction between what was said previously about the low-frequency requirements of the chroma channel and its position on the video curve. Further examination, however, will reveal that although the *color sub-carrier* is at 3.58 mc, the actual frequencies modulating this carrier extend 1.3 mc below the sub-carrier and

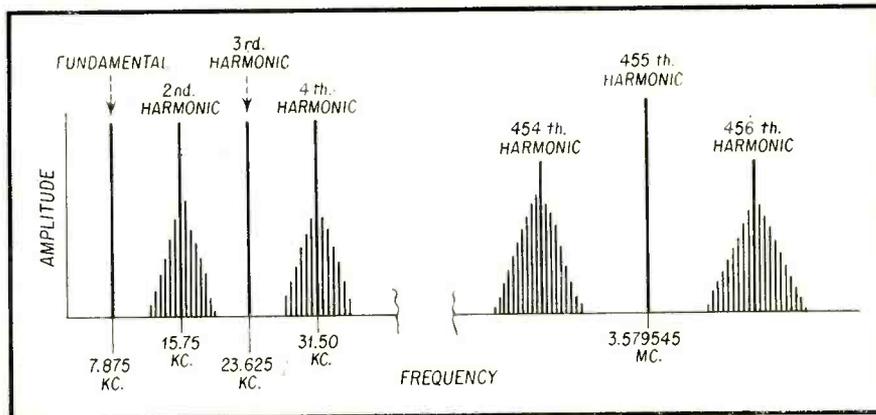


Fig. 3—"Interleaving" showing video clusters of energy.

about 300 *kcs* above the sub-carrier. Looking at this response curve by itself, we observe that it is comparatively narrow with respect to the *video* response curve.

The chroma channel consists of two sub-channels for the following reason:

Refer to Fig. 1. Observe that three individual color signals are extracted from the color camera. These signals are then mixed in a suitable network and we have, as a result, three new signals. These are:

2. E_Q and E_I can be considered as a separate signal transmitted in such a way that they do not interfere with each other or with the luminance signal.

In summation, we might qualitatively point out that the E_Q and the E_I signals contain elements of all three original colors and by proper electronic mixing of these two signals we can reproduce the three original colors in the receiver. The additions and selection of the proper proportions of the several signals is known as *matrixing*.

Sub-Carrier

The origin and composition of the color sub-carrier is the heart of the NTSC system. A detailed examination of this signal is, therefore, in order. The first thing to note before discussing the component of this signal, is that we will encounter a number of ideas, which, while used in other branches of communication, will be completely new concepts to the busy practicing serviceman. We will try to explain them as simply as possible without extensive mathematics. So for the sake of simplicity, a number of statements will be made and left to the enterprising serviceman for the mathematics involved.

The first principle under this heading is the fact that in the video signal, the energy present is not in a continuous band of power, but is so bunched that there exists, at the odd harmonics of half the line frequency, *no energy*. Fig. 3 shows how the even harmonics of half line frequency contain the video information in clusters of energy around the even harmonic positions on the graph. Note that in between (odd harmonic positions) no energy is present. It is possible, at this point, to insert another signal the basic frequency of which is an odd harmonic of half the line frequency without disturbing the original signal. This process is

[Continued on page 78]

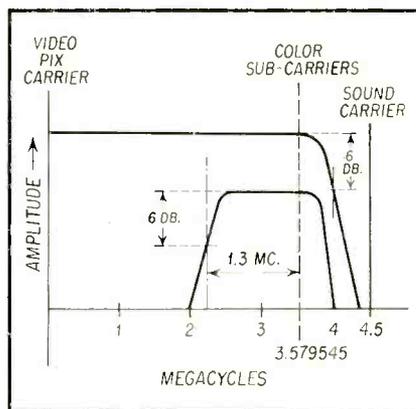


Fig. 2—Relationship of video carrier and color sub-carrier in NTSC system.

1. E_Y , which is a combination of certain proportions of all three original colors added together.
2. $E_R - E_Y$, which is the result of the subtraction of E_Y from the original full red signal.
3. $E_B - E_Y$, which is the result of the subtraction of E_Y from the original full blue signal.

The complete transmitted video channel contains E_Y as the black and white signal and E_Q and E_I which are derived through an additional network (color encoder) from $E_R - E_Y$ and $E_B - E_Y$.

Now here is where the crux of the whole system of color transmission is made possible:

1. E_Y is transmitted as a separate black and white signal on the original pix carrier.

RC CIRCUITS

by Cyrus Glickstein

A GOOD point to remember is that in the blocking oscillator type of sawtooth generator the trapezoidal waveform is not quite the same at the output of the oscillator. This is because the primary of the blocking oscillator transformer is in the discharge path, and has an inductive effect, Fig. 8a. The typical trapezoidal waveform for such a circuit is shown in Fig. 8b. The output waveform may also be modified somewhat in sawtooth generator circuits which use feedback from the output stage to the oscillator stage.

A clear understanding of series RC circuits helps the technician analyze how voltage is distributed around a circuit. A good example to test your ability in this direction is a multivibrator type of circuit used in many different types of electronic equipment, as shown in Fig. 9. There is $-85V$ bias on V1, because of the voltage divider arrangement in the cathode. This is sufficient to cut off V1. V2 is conducting. From the information given on the diagram, a) what voltage is C1 charged up to? b) When a large negative square wave is applied to the grid of V2 and cuts the tube off, what is the voltage across R1 at the instant V2 is cut off?

The answer to a) is 30V. A coupling condenser (in the usual type of circuit connection) charges up to the value of dc voltage on the plate of the tube to which it is connected. The condenser therefore charges up to the value of plate voltage on V2. The answer to b) requires a more detailed explanation. When V2 is cut off by a large negative square wave, the plate voltage of V2 starts to rise to the B+ value (+150V) and C1 starts to charge to this new value. The equivalent circuit at this instant can be represented by Fig. 10a or even more simply by Fig. 10b.

Theory of series R-C circuits, covered in first installment, is now applied as a means of understanding four basic and important circuit types.

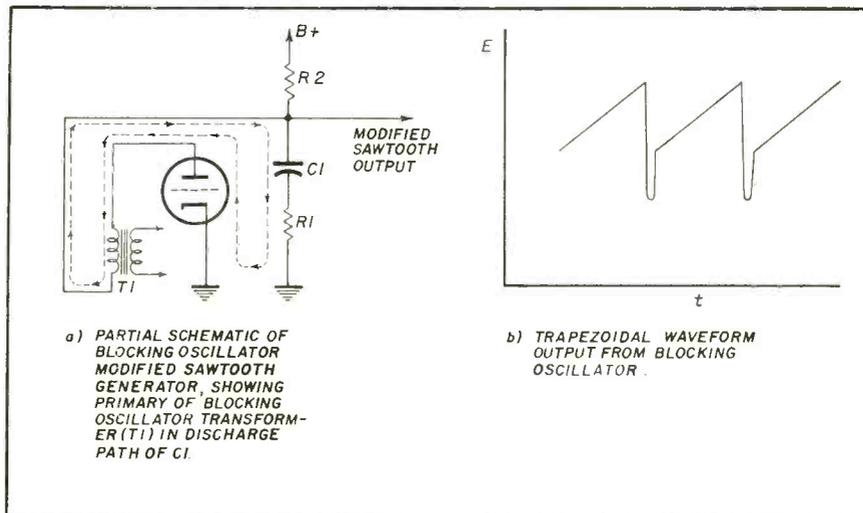


Fig. 8—Condenser discharge in blocking oscillator.

Since V2 is cut off, the condenser starts to charge through the charge path of R1 and R2. The voltage already across the condenser (30V) can be considered to buck the source voltage of the battery (B+). The difference in voltage can be considered to divide across the resistors in the circuit at the instant the condenser starts to charge. Since there is 150V in the battery and 30V across the condenser, the difference of 120V divides proportionally across the two resistors. There is 80V across R1 (100K) and 40V across R2 (50K). Incidentally, plate voltage of V2 at this instant rises from +30V to +110V, which is 40V (the drop across R2) less

than B+. Then as the condenser charges, the voltage across both resistors drops accordingly.

We now come to a very important group of series RC circuits for the electronics technician—differentiating and integrating circuits. A brief review of this action in series circuits will be made at this point, so it can be compared to similar action in more complex circuits, where definite differences will be found in the results.

Differentiating and integrating circuits have the property of changing the shapes of complex waveforms, such as square waves, sawtooth waves, etc.

The shape of a sine wave is not changed in going through these circuits, although the phase is shifted.

A differentiating circuit, Fig. 11, has a short time constant, and the output is taken off the resistor. By a short time constant is meant an RC or time constant ($T = R \times C$) value that is short compared to the time of an incoming signal. For example, assume a square wave has a frequency of 10,000 cycles per second. One cycle is equal to 100 microseconds. Each half of the square wave is applied to make the condenser charge up first in one direction then in the other. The duration of each half of the cycle is 50 microseconds, Fig. 11. This square wave is applied across a circuit with a time constant of 5 microseconds (R is 5K, C is .001 μ f, $RC = 5,000 \times .001 \times 10^{-6}$ or 5 microseconds). This means the condenser will charge to 63% of the source voltage (peak voltage of the square wave) in 5 microseconds, and to the full (100%) source voltage in 5 RC or 25 microseconds. In other words, the condenser becomes completely charged

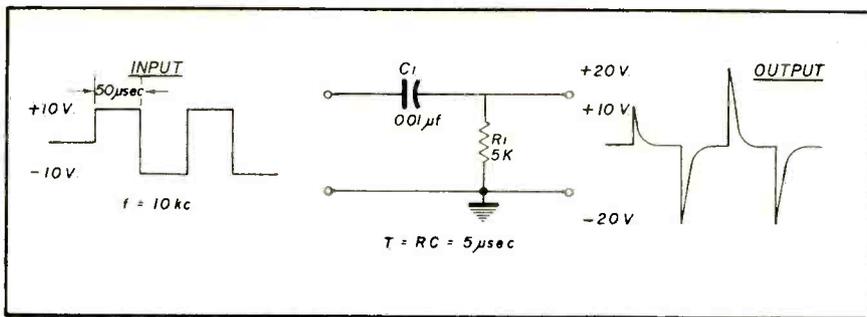


Fig. 11—Differentiating circuit showing input and output waveforms.

before the polarity of the square wave reverses. The input square wave is changed to the output differentiated wave or pips as shown in Fig. 11. Note that after the first half-cycle, the output waveform has double the peak-to-peak voltage as compared to the input waveform. This is typical of differentiated circuits, since the condenser acts very much like a condenser in a voltage-doubling circuit in a power supply. The charged condenser acts in series with the source voltage and the combined voltage is applied across the resistor at the first instant the polarity changes in every half-cycle.

An integrating circuit does the opposite. A large time constant is used and the output is taken off the condenser (Fig. 12a). A familiar example of such a circuit is the integrating circuit in TV which is used to distinguish between vertical and horizontal pulses, Fig. 12b. Narrow horizontal pulses do not occur for long enough time to charge up the condensers in the integrating circuit to any substantial

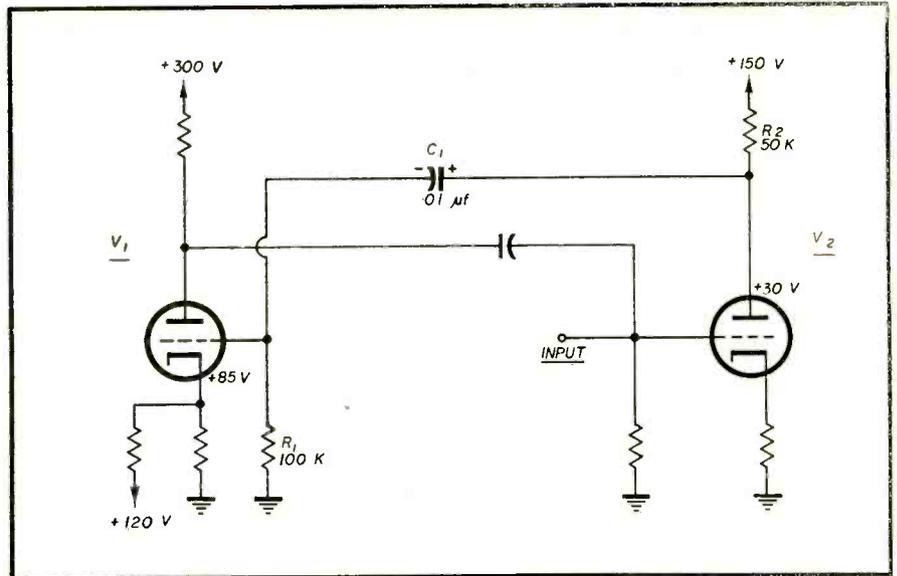


Fig. 9—Multivibrator circuit—V1 cut off, V2 conducting.

value. This is true because the condensers have a large time constant (take a comparatively long time to charge as compared to the input fre-

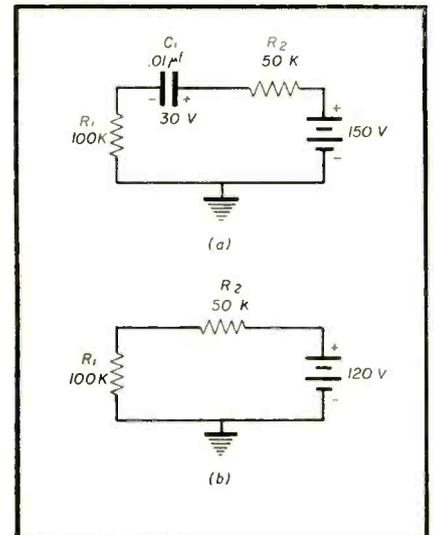


Fig. 10—Equivalent circuits of multivibrator (Fig. 9) at instant V2 is cut off. C1 discharges across R1.

how differently they behave as compared to series circuits.

[To Be Continued]

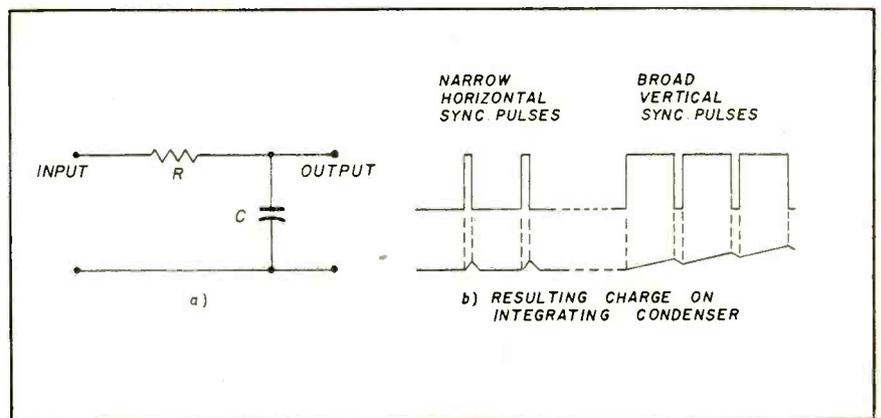


Fig. 12—Basic integrating circuit. Large RC time constant causes sync pulse inputs to result in integrated output across C .

AN ALL-CHANNEL UHF

CONVERTER



MODEL NO. RC-53
Patent Pending

only

\$

19.95

Regency


Div. I. D. E. A., Inc.
7900 Pendelton Pike
Indianapolis 26, Indiana
Telephone: Cherry 2466

Burton Browne

New




Products

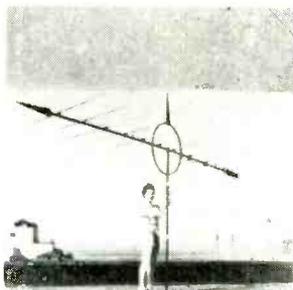


New Ward Antennas

Two new TV antennas have been introduced by Ward Products Corporation, Division of the Gabriel Co., Cleveland, Ohio. The Circle-vane and the Dymon-vane, designed by Dave Chapman, industrial designer, are made of strong aluminum elements with cross-arms of Jones and Laughlin Perma-Tube. This electric weld steel tubing is coated inside and out with Vinsynite, an exclusive pastic-type corrosion-resistant finish. The Circle-vane is for use in rural or suburban fringe areas where high sensitivity is required. It consists of 10 horizontal aluminum elements fastened to the Perma-tube cross-arm. The Dymon-vane conical type antenna is for use in metropolitan areas where both low and high band TV stations transmit in the same general direction. Design of the Circle-vane is based on the original concept of Dr. Yagi who patented the first directional radio antenna about 1919.

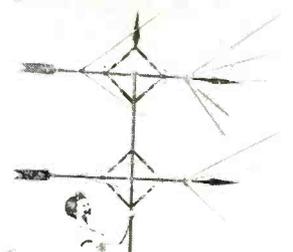

VTVM Training Aid

EICO has produced a new aid for teaching the use of the vacuum tube voltmeter. This demonstrator is a giant replica of EICO's Model 221. Actual size is 14 $\frac{3}{4}$ " x 3 $\frac{3}{8}$ ". It features movable function and range switches and a settable dial pointer. Available to schools and instructors, the teaching aid has an oversize dial face and authentic markings. For further details write to Electronic Instrument Co., Inc., 84 Withers St., Brooklyn 11, N.Y.

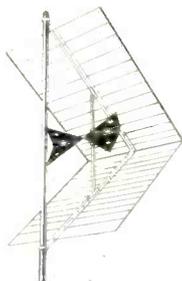

New Tesco Antenna

A single bay corner UHF antenna, Model 706, has been introduced by TV Products Co. ("TESCO"), Springfield Gardens, N.Y. Model 706 is an all channel UHF antenna designed for fringe areas. It is factory pre-assembled for quick installation. Also known as the "Cor-Tenna," the Model 706 is reported to make possible a gain of 14.8 db.


Kirby Xfmr Tester

The Model 98 Flyback Transformer Tester indicates shorted turns in the flyback transformer by the power absorption method and will indicate as low as one shorted turn. In addition, it will test for continuity on yokes, transformers, switches, etc. Further information on this portable, compact, and time-saving device is available from Kirby Products Corp., 175 Fifth Avenue, N.Y. 10, N.Y.



Duotone Hi-Fi Speakers


Duotone of Keyport, N.J. announces a new line of hi-fi speakers designed to replace woofer-tweeters. The new speakers feature "Ticonal," a new magnet steel giving a high flux density that makes possible an air gap of twice the normal depth. The "Master" range includes an 8 $\frac{1}{8}$ ", a 10", and two 12" models. Frequency responses vary from 40 to 13,500 cps in the 8 $\frac{1}{8}$ " to 40 to 20,000 cps in the finest 12".

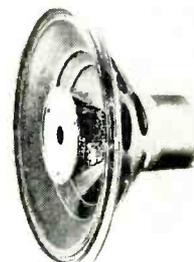

Under-Counter


Cash Drawer

Many stores and shops have experienced a need for an under-counter cash drawer. The lower section of this drawer has 10 currency compartments. A sliding tray—the top section—has 5 coin tills for handling loose coins and 5 coin compartments for handling packaged coins. Size is 21 $\frac{1}{2}$ " long x 20 $\frac{1}{8}$ " wide x 6 $\frac{3}{8}$ " deep. Further details on this Model G-1 may be had by addressing Indiana Cash Drawer Co., Shelbyville, Ind.

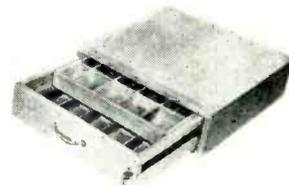

South River Antenna

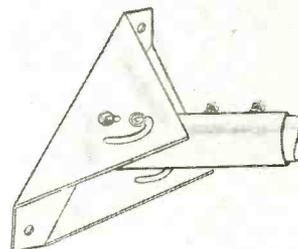South River Metal Products Co., Inc. announces its new type of TV antenna roof mounting. The RM-15 has South River's "walkup-drop lock" feature in which the antenna and mast are inserted into the mast holder from a horizontal position, and then "walked up" to a vertical position where a notch holds the antenna erect. The RM-15 may be mounted on either a flat or pitched roof.



New Masco Booster


Masco's new Tunable VHF-TV Cascadian Booster increases the signal strength at least 56 times (35 db.) average on all channels. Field proven, the Cascadian provides high gain and bandwidths continuously for all channels 2 to 13. Permeability tuning and a single control knob are featured. For further information, write to the Mark Simpson Mfg. Co., Inc., 32-38 49th St., Long Island City 3, N.Y.



UHF-VHF Universal Standoff

A new universal standoff eliminates the metal ring from around the transmission line. It is said to overcome problems of standing waves and voltage losses and to permit the closest approach possible to running a transmission line in free space. It accommodates all types of transmission line without the need to thread. Write to Argyle Electronic Co., 8 West 18th Street, New York 11, N.Y. for further information.



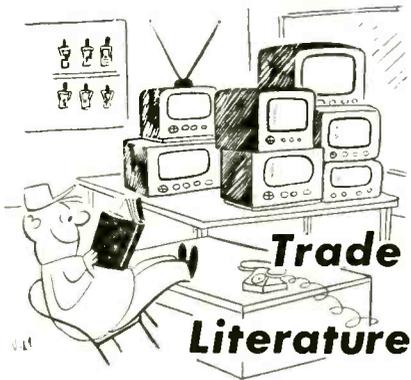

Through the cooperation of Snyder Manufacturing Company, Philadelphia, the new 1954 edition of *TV Tenna Tips* is being made available free to all in the television field. A new feature of the publication this year is the "Antenna Selector," a special section of "Antennas for Areas" recommended by Matt Mandl and Ed Noll. In this feature, the best antennas for each area are noted, with first, second and third choices being listed. Also included in the subject matter are the latest *uhf* and *vhf* data, Directronic antennas, Yagis, Installation Do's and Don'ts, Dimension Guide, Channel Frequencies, Helpful Hints and many other subjects relating to television antennas. The publication is illustrated throughout with diagrams and charts. This pocket size reference manual is being offered free to TV servicemen, service dealers, dealers, distributors, salesmen, manufacturers and "Hams." Free copies may be obtained by writing to Snyder Manufacturing Company, Philadelphia 40, Pa.

John F. Rider, Publisher, Inc., 480 Canal St., New York 13, N. Y., announces a new publication "*How To Troubleshoot A TV Receiver*," by J. Richard Johnson. Written to aid the service technician to systematically troubleshoot all TV receivers, this step-by-step guide tells the reader where to start troubleshooting and how to continue, from the moment he is told or observes what the symptoms are. Complete listings are given of materials, tools, tubes and test equipment required to troubleshoot in a customer's home or the service shop. The primary purpose of the book is to teach the technician how to approach TV troubleshooting systematically, rather than by means of hit or miss time-consuming practices. This latest book in the publisher's "how to" series on TV and radio servicing contains approximately 128 pages in a paper binding.

HERE IT IS...

SOLVES THE MOST DIFFICULT TV TROUBLE-SHOOTING PROBLEM!

- Takes the Guesswork Out of Horizontal Sweep Circuit Servicing
- Saves Time
- Inexpensive
- Easy-to-Operate



The

KIRBY

Model No. 98

FLYBACK TRANSFORMER TESTER

Detects shorted turns in Flyback Transformer and indicates as low as one shorted turn.

Tests transformer while in Television Receiver.

Also tests continuity on yokes, coils, speakers, switches, etc.

Suggested Dealer Net Price **\$39⁹⁵**

See your Local Distributor or write direct.

MANUFACTURED BY

KIRBY PRODUCTS CORPORATION
 20 EAST HERMAN STREET., PHILADELPHIA 44, PA.
 GENERAL SALES OFFICE: 175 5th Ave., New York 10, N. Y.


The new *Stancor Transformer 24-page catalog* carries complete electrical and physical specifications on almost 500 transformers for radio, television, high-fidelity, amateur, military, and other electronic applications. A cross index chart between obsolete power transformers and the current "8400" series power transformers has been included.

This catalog is available, without charge, by writing the Chicago Standard Transformer Corporation, Standard Division, Elston and Addison, Chicago 18, Illinois.

A new condensed price list on all Sprague "bread and butter" service capacitors and resistors has just been announced. Mounted on a wall, or almost any place, the sheet makes an ideal, ready reference of the most widely used Sprague ratings. Dealers will find it a convenient way to determine what the customer should pay, as well as an easy means of checking inventory of "must" components. The new list P-143 may also be obtained by writing Sprague Products Company, 71 Marshall Street, North Adams, Mass.

[Continued on page 76]

CIRCUIT COURT

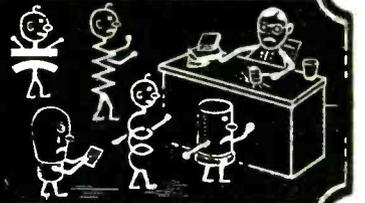

Du Mont RA 164—Sync Separator

The sync separator in the Du Mont RA 164 (Fig. 3) uses a 6BE6 as the separator. As shown in Fig. 1, the first grid is fed a sync-phase negative signal from the video detector. The third grid is coupled to the plate of the video amplifier. The signal from this source is sync-phase positive. The signals fed to the grids are then 180° out of phase. The characteristics of the 6BE6 are such that as long as plate current flows, the third grid acts as the control grid. The first grid, however, can cut the tube off. The third grid can only apply the signal when the first grid is above cut-off.

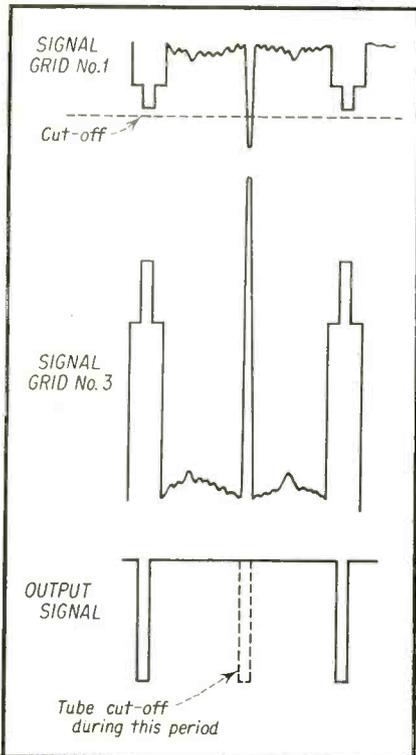


Fig. 2—Signals fed to first and third grids in sync separator using 6BE6.

The bias on grid #1 is set so that the top of the sync pulse is just above the cut-off point. Figure 2 shows what happens when a noise pulse whose amplitude is greater than that of the sync pulse. The noise pulse drives grid #1 beyond cut-off, therefore, during this period what appears on grid #3 does not appear in the output.

Noise pulses on the sync pulse will, of course, cut off the tube and the sync pulse from the output. The os-

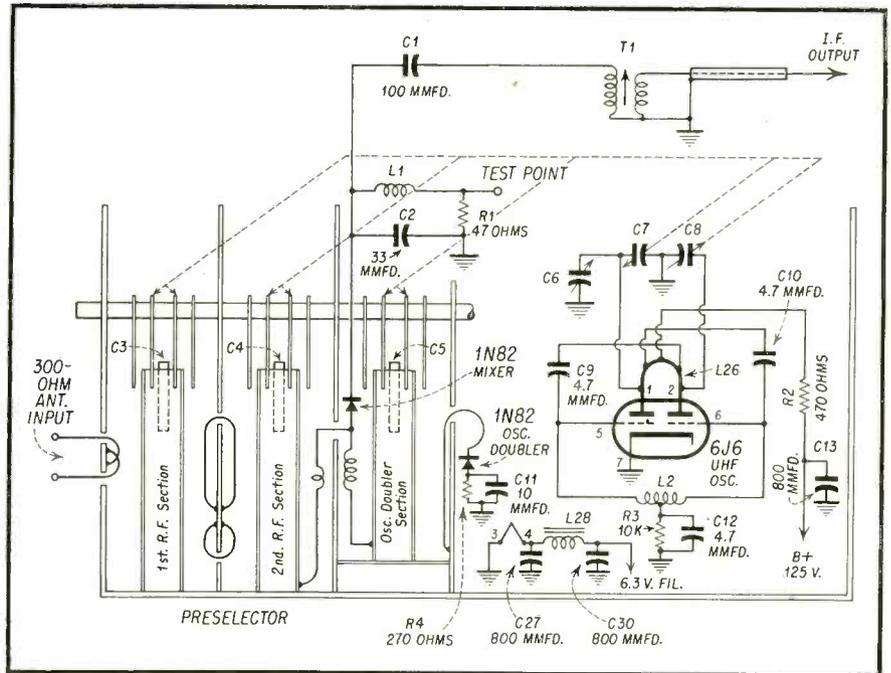


Fig. 3—Schematic of General Industries UHF tuner.

illator circuits, however, are so designed that the flywheel effect of the oscillators will keep them in sync until the reappearance of the sync pulses.

General Industries UHF Tuner

THIS *uhf* tuner, one of the more popular makes used by manufacturers for the *uhf* channels, is shown schematically in Fig. 3. This unit works on the oscillator frequency doubler principle.

The 6J6 tube operates as a balanced push-pull oscillator. The in-phase volt-

age required to keep the unit oscillating is supplied to the opposite grid by each of the plates. This operation is a modification of a Hartley oscillator. The oscillator is tuned to half the frequency needed for the *uhf* channels.

Crystal #1 (1N82) is fed the output of the 6J6. As a non-linear device, the output of this crystal is rich in the harmonics of the oscillator. A circuit tuned to the oscillator's second harmonic couples the crystal #1 output

[Continued on page 76]

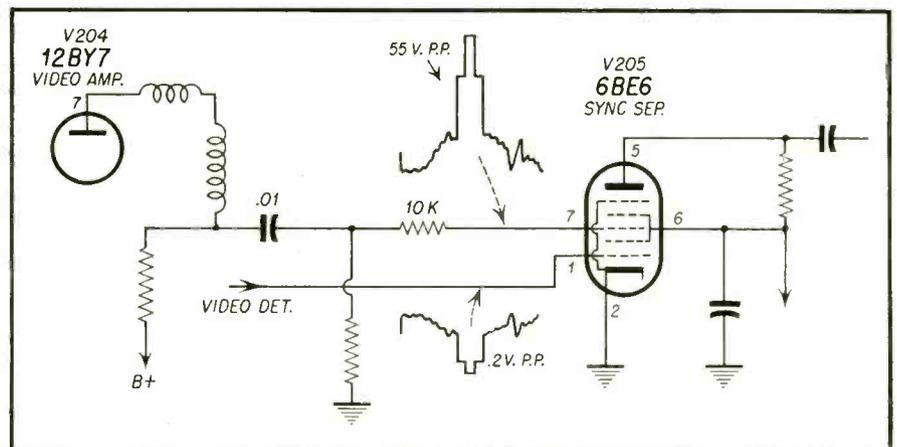


Fig. 1—Simplified schematic, Du Mont RA-164 sync separator.

FREE-your Choice of NEW PHONO-CARTRIDGE CARRY-KIT or DISPLAY-DISPENSER



Handy All-Metal
Carry-Kit Holds
6 E-V Cartridges


Complete E-V
Interchangeability
Chart on both sides
makes servicing
positive and easy



PLUS
WINDOW or
DOOR DECAL



PLUS
REVISED SET-MODEL
REPLACEMENT GUIDE

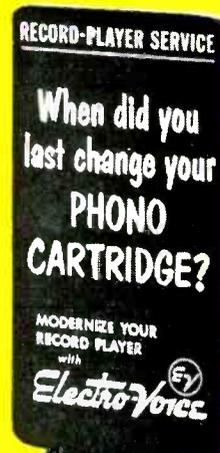

10,000,000 PHONOGRAPHS ARE WAITING TO BE SERVICED

Get your share with these E-V aids to sales!

Again E-V gives you a positive profit-maker—and helps make you the authority on Phono-Service in your community!

Free of extra cost, from your E-V Distributor, you can get your choice of new Cartridge Carry-Kit or Display Dispenser plus professional Decal and up-to-date set-model Replacement Guide, with every purchase of any 6 E-V Phono Cartridges.


Furthermore, the new E-V high output, high compliance, permanent Ceramic Cartridges revolutionize servicing. They are not affected by moisture or heat—can be carried in your service kit or kept on display without fear of deterioration. And they are directly interchangeable with silent-needle type crystal cartridges that do not use a thumb screw—yet cost no more than crystal. They are part of the famous E-V Basic 6 Preferred Types that make over 92% of all cartridge replacements.

Take advantage of this offer now! Make money selling cartridge replacements. Cash in on the \$70,000,000 phono-cartridge modernization replacement market.

For a limited
time only.

SEE YOUR E-V
DISTRIBUTOR TODAY

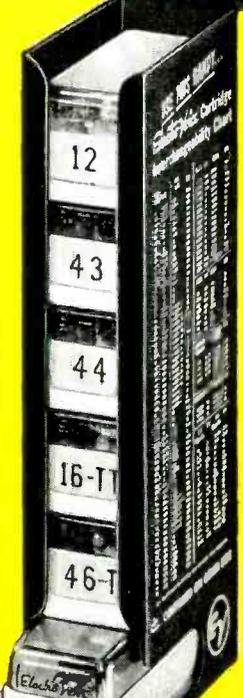6-Cartridge
Metal
Display
Dispenser
for Wall
or Shelf



Each E-V Cartridge In
Two-Tone Jewel-like
Golden Yellow Plastic Box

Electro-Voice

BUCHANAN, MICHIGAN

Export: 13 E. 40th St., New York 16, U.S.A., Cable: Arlab

FOR A LIMITED TIME ONLY

REPAIRMEN SERVICEMEN

TV
RADIO
HOME REPAIRS
APPLIANCES



CRAFTSMAN
QUALITY



"At Last a Case Designed for You"

- PRACTICAL, EASY TO CARRY
- PROFESSIONAL APPEARANCE
- BIG SIZE 21" x 12" x 7 1/2"
- ALL STEEL CONSTRUCTION

Look at these features! Six plastic-clear boxes for small parts . . . A seven partition removable metal tray . . . Four partitioned bins on one side, two extra large on the other. Heavy gauge metal throughout, with full length hinge, cylinder lock with two keys, two heavy suitcase type catches and metal handle.

ALL THIS FOR

\$13.95
PREPAID

No C.O.D. Orders. Send Check or Money Order to:
HARDWARE DEPT. (STOCK NO. S-399)
SEARS, ROEBUCK AND CO.
403 S. STATE STREET • CHICAGO 5, ILLINOIS

Service Men!

THE GUARDIAN SERIES 200 RELAY...



Interchangeable
COIL and CONTACT
SWITCH ASSEMBLIES
Save Time—Cut Costs!

★ Coil assembly includes coil and field piece. Contact assembly consists of switch blades, armature, return spring and mounting bracket. Standard and Midget contact assemblies in either S.P.D.T. or D.P.D.T. are interchangeable and can be used with any of 13 coils described below.

CONTACT SWITCH ASSEMBLIES

CAT. NO.	TYPE	AMPS	COMBINATION
200-1	Standard	8 amps	Single Pole Double Throw
200-2	Standard	8 amps	Double Pole Double Throw
200-3	Standard Contact Switch Parts Kit with complete assembly and wiring details		
200-4	Standard	12.5 amps	Double Pole Double Throw
200-5	Standard	8 amps	Four Pole Double Throw
200-M1	Midget	8 amps	Single Pole Double Throw
200-M2	Midget	8 amps	Double Pole Double Throw
200-M3	Midget Contact Switch Parts Kit with complete assembly and wiring details.		

13 COILS ASSEMBLIES

A.C. COILS*		D.C. COILS	
CAT. NO.	VOLTS	CAT. NO.	VOLTS
200-6A	6 A.C.	200-6D	6 D.C.
200-12A	12 A.C.	200-12D	12 D.C.
200-24A	24 A.C.	200-24D	24 D.C.
200-115A	115 A.C.	200-32D	32 D.C.
		200-110D	110 D.C.
		200-5000D	

*All A. C. coils available in 25 and 60 cycles

GUARDIAN ELECTRIC

1605-P W. WALNUT STREET

CHICAGO 12, ILLINOIS

A COMPLETE LINE OF RELAYS SERVING THE RADIO INDUSTRY

Do You Service Mobile Gear?

If so, you will find the latest publication released by Cowan Publishing Corp. invaluable in providing information on reducing noise interference, setting generator and regulator levels, selecting antennas, setting up test equipment, etc.

It is the **RADIO AMATEURS' MOBILE HANDBOOK**. Available from many distributors and parts jobbers, or send in the coupon below with \$2.00.

SUBSCRIPTION RATES:

1yr. \$3.00, 2yrs. \$5.00, 3yrs. \$7.00

CQ MAGAZINE

SD

67 West 44th St., New York 36, N. Y.

Enclosed find \$_____ to cover this order for the

RADIO AMATEURS' MOBILE HANDBOOK (\$2. each)

HANDBOOK to be sent to:

Name _____

Address _____

City _____ Zone _____ State _____

CQ MAGAZINE

SD

67 West 44th St., New York 36, N. Y.

Enclosed find \$_____ for a _____ year


subscription to be sent to: New Renewal

Name _____

Address _____

City _____ Zone _____ State _____

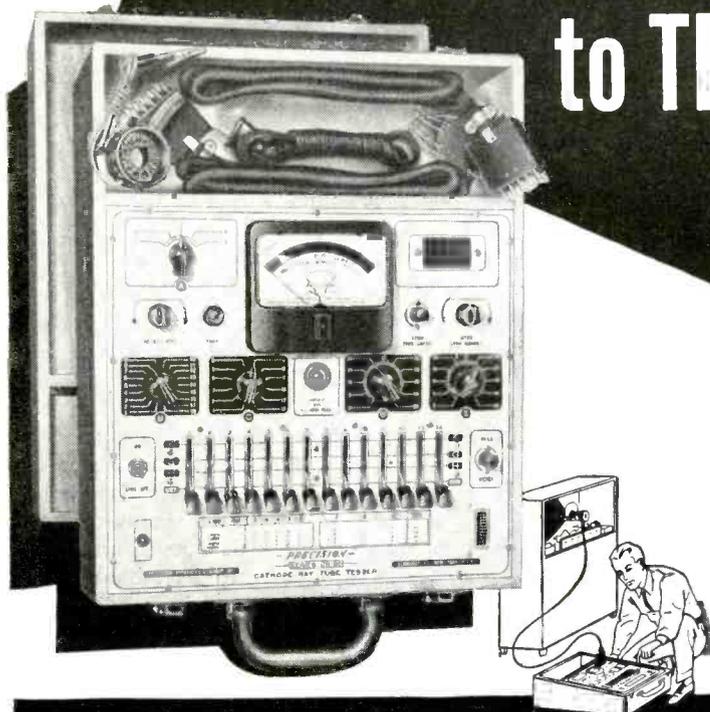It takes a CR TUBE TESTER to TEST a CR TUBE...



...because CR tubes are electrically and physically different from all other types of electron tubes! Some of the more obvious differences include:

- PICTURE PRODUCING BEAM CURRENT
- EXTREMELY LOW ANODE CURRENTS
- DIFFERENT, MULTIPLE OPERATING VOLTAGES
- HIGH LEAKAGE and SHORT CHECK LIMITS
- MORE and DIFFERENT TUBE ELEMENTS
- ELECTROSTATIC FOCUS ELEMENT
- ELECTROSTATIC DEFLECTION PLATES
- ELECTROMAGNETICALLY FOCUSED GUN
- ELECTROMAGNETICALLY DEFLECTED BEAM
- ETC., ETC., ETC.

YES, IT TAKES A CR TUBE TESTER TO TEST A CR TUBE...
AND THE **PRECISION CR-30**
WAS SPECIALLY DEVELOPED FOR THIS VERY IMPORTANT PURPOSE!


TESTS ALL TV PICTURE TUBES Magnetic & Electrostatic
Oscilloscope & Industrial Types
...FOR BEAM CURRENT INTENSITY (Proportionate Picture Brightness)

Stop Guess-Checking with CABLE ADAPTERS!

- Receiving tube checkers were made for testing receiving tubes and NO CABLE ADAPTER can adapt them to do the job of the CR-30.
- CABLE ADAPTERS only check for filament continuity, a degree of inter-element short and a so-called emission test.
- CABLE ADAPTERS do not test for the all-important, picture producing beam current.

You can't afford to guess when you test the most expensive component of a TV set.
Be sure with **PRECISION Model CR-30!**

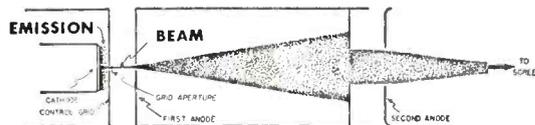IT IS THE ELECTRON BEAM (and NOT total cathode emission) which traces the pictures on the face of the CR tube.



Cathode emission can be high, and yet Beam Current (and picture brightness) unacceptably low. The CR-30 will reject such tubes because it is a Beam Current tester. Conversely, cathode emission can be low and yet Beam Current (and picture brightness) perfectly acceptable. The CR-30 will pass such tubes because it is a Beam Current Tester.

The CR-30 incorporates additional special test facilities necessary for overall performance evaluation of the CR tube as will permit positive answer to the question "Is it the Picture Tube or the TV Set?" And the CR-30 gives the answer in but a fraction of the time required to test the other 2 dozen or so tubes in the set.

SERIES CR-30: In hardwood, tapered, portable case, with hinged, removable cover. 17¼" x 13¾" x 6¾". Complete with standard picture tube cable, universal CR tube test cable and detailed instruction manual. Shipping weight: 22 lbs.
NET PRICE \$104.75



PRECISION APPARATUS COMPANY, INC.

92-27 HORACE HARDING BLVD., ELMHURST 13, N. Y.

Export Division: 458 Broadway, New York 13, U.S.A. • Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., 560 King Street, W., Toronto 2B

TRADE FLASHES

[from page 12]

More TV Sets Than Bathtubs!

The Minneapolis-St. Paul area now has more television receivers in use than home telephones or bathtubs.

According to W. C. Johnson, vice president of Admiral Corporation, there are approximately 405,000 television receivers within the Minneapolis-St. Paul receiving area. That compares with the Northwestern Bell Telephone Company's count of about 370,000 home phones in the 40 mile area around the Twin Cities and the Census Bureau's estimate of 280,000 bathtubs—presumably in use.

The Admiral executive said that the amazing acceptance of television in

the home put over 25,000,000 sets in use throughout the country in the short period of seven years. He said there are 50,000,000 telephones in service throughout the United States, but pointed out that telephones had a substantial head start on TV, since the first instruments were installed in New England over 70 years ago.

JFD Daily Production of 17,000 Antennas Sets Output Record

Mr. Julius Finkel, President of the JFD Manufacturing Company, Inc., of Brooklyn, N.Y., announces an all-time high in TV antenna production. The JFD organization, Mr. Finkel stated, manufactures 10,000 outdoor antennas and 7,000 indoor antennas daily. This substantial increase in production is attributed to the new

4-story factory (140,000 square feet of manufacturing space) on 62nd Street—a plant specifically designed for the manufacture of television antennas.

DuMont Heralds "Telectronic" Age

America is entering a new age—the "Telectronic Age" according to Dr. Allen B. Du Mont, television pioneer and president of Allen B. Du Mont Laboratories, Inc. In a recent address before the Industrial Council at Rensselaer Polytechnic Institute, Dr. Du Mont stated that the new age would "effect tremendous changes in our patterns of thought, morals, actions, commercial operations, and everyday living." In explaining the "Telectronic Age," Dr. Du Mont said: "The Telectronic Age symbolizes to me electronics with visibility. It embraces the idea of a useful television system applied to the facts of everyday living."

Dr. Du Mont cited many examples of the Telectronic Age in action. He called attention to its use as a vital tool in education, in medicine, in factories, in atomic plants, in financial institutions, and in transportation.

The role of Telectronics, according to Dr. Du Mont, has a potential much greater than the commonly accepted factors of television entertainment and culture. Its greatest usefulness, he stated, will be in closed-circuit type of transmissions. He indicated that the innumerable applications of electronics combined with vision over privately connected circuits would make this type of transmission more important than commercial broadcasting.

Leader Electronics, Inc., Moves

Leader Electronics, Inc. announce they have moved to larger quarters "to meet the unprecedented demand for Leader products." New address: 2925 East 55th St., Cleveland 27, Ohio.

RCA Ready To Start Delivery Of Color TV

The Radio Corporation of America has announced that it will soon commence delivery of compatible color television equipment to enable stations across the nation to broadcast color programs in their areas. The announcement indicated an early start for the first color television programs to be broadcast after the Federal Communications Commission approves standards for a compatible color system for television.

"One or more stations in 57 different cities have already placed orders with RCA Victor for color broadcast



You and your customers will be amazed at the speed and simplicity of handling small parts with this ruggedly built, all-steel, 18 drawer Model 11 Equipto Cabinet! It requires little space...measures only 34" x 13 3/4" x 12". May be used individually, in stacks, under counters, or in shelving.

The cabinet has heavy gauge frame welded into solid, one-piece assembly. Sturdy drawers (11" x 5 3/8" x 3 1/8") slide freely without swaying or sticking. Every drawer is separated into 3 compartments by flush-fitting dividers which adjust on 1" centers. This provides 54 compartments per cabinet. Each is fully enclosed on all sides and bottom to prevent protrusion of parts, needless damage, and jamming of drawer.

Dividers are slanted at top to keep label in full view...simplify removal of parts. Extra dividers may be added to increase number of compartments, if desired. Label holders on all drawers and compartments permit quick identification of all parts. Finish is olive green baked enamel.

WRITE TODAY FOR FREE CATALOG OF COMPLETE LINE

Equipto sells only through jobbers — never direct!



Ideal for storage of capacitors, condensers, phonograph needles, chokes, nuts, bolts, screws and lock washers.

Equipto
AURORA, ILLINOIS

Division of Aurora Equipment Company
810 Prairie Avenue, Aurora, Illinois
Manufacturers of steel shelving . . . parts bins . . . drawer units

[Continued on page 74]



MANDL'S TELEVISION SERVICING Means

- Quicker, More Accurate Trouble-Shooting
- Fewer Call-Backs
- More Satisfied Customers

An increasing number of TV servicemen are finding the 'Mandl way' the answer to quicker, more accurate trouble-shooting and greater customer satisfaction.

A complete Master Trouble Index makes it easy for you to locate the exact source of trouble quickly. It's in the form of a handy chart, listing the various hums, sound distortions, streaks, bars, focus defects and 100 other trouble symptoms in sound and picture together with the possible causes of each and the page on which servicing instructions are given.



Written by the nationally known expert

MATTHEW MANDL

Author of the "Television Servicing Clinic" in *Radio Electronics* and of regular articles on the technical and servicing problems of radio and television in other leading trade magazines; Director of Electronics and TV courses at Temple University; former operator of a radio station and owner of his own servicing business.

other practical features

plus new data on transistors cascade tuners automatically focused tubes and other recent developments

- Special servicing instruction for color TV; for VHF and UHF receivers; the latest circuits and innovations.
- Large, clear schematics of commercial circuits for all basic parts of the TV receiver.
- New, original photographs showing trouble symptoms as they appear

on the TV screen for quick identification.

- Handy lists of troubles that may occur in each section of the TV receiver and the exact procedure for correcting each.
- Full explanation of unusual hard-to-find troubles, where they occur, how to overcome them.
- Ways of improving overall performance, improve gain, reduce ghost reception, minimize interference.

You'll Learn Easily From This Book

It is written in the clearest, simplest, most practical terms by a man who is nationally known for his helpful articles on radio and TV servicing. From these step-by-step explanations and illustrations you'll clearly understand just how each unit in the TV receiver functions, how it is set up by the various manufacturers, what flaws may occur in it, what points in the circuitry cause these flaws, how they affect the other components in the unit, and how they show up on the TV screen. All faults likely to occur, including those hard-to-find troubles are fully dealt with. And you won't be confused by unnecessary theory. Only the essentials actually needed for practical servicing are given in clear, easy-to-follow terms.

You'll Find Full Instruction on

Simple signal tracing procedures • How to improve reception in fringe areas • How to use the oscilloscope and other test equipment • How to trouble-shoot keyed A.C.C. and synchroguide circuits; align I.F. stages • Any many trade tricks for diagnosing troubles in minimum time. \$5.50

Coming Soon!

Matthew Mandl's

Television Service Course Laboratory Manual

Learn TV Servicing by Experiment

with this brand new manual. It's a work book of experiments designed to give you practical experience in trouble-shooting and servicing procedures of television receivers.



Do you know enough about hearing aids?

Hearing Aids

by Matthew Mandl

A rapidly increasing number of the 15,000,000 hard-of-hearing people in this country are turning to hearing aids which ALL REQUIRE SERVICING! This book explains the operation of modern hearing aids, the differences between the various types of earpieces, amplifiers, batteries, etc.; what may go wrong with them; how to locate trouble, and how to make adjustments and replacements. \$3.50

Radio and Television Mathematics

by Bernard Fischer

"A book for the place of honor beside its natural partner, the slide-rule," says *Radio Electronics*. Here are step-by-step solutions for hundreds of circuit problems in radio, TV and industrial electronics. Whatever YOUR problem, whether it is how to correct the power factor of a motor, find the impedance and length of a matching stub between a TV antenna and its transmission line, or any of hundreds of other problems you're apt to encounter, here is the clear and exact solution. \$6.75

FREE ON-APPROVAL OFFER!

THE MACMILLAN COMPANY, DEPT. R.S.,
60 FIFTH AVENUE, NEW YORK 11, N. Y.

Please send me the books I have checked below. In 10 days I will either return the book or you may bill me at the prices shown, plus a small delivery charge. (SAVE: send check or money order and we pay postage.)

- TV SERVICING \$5.50 RADIO AND TV MATH \$6.75
 HEARING AIDS \$3.50

Signed

Address

ANSWER MAN

[from page 31]

terial sufficiently, the tube may operate satisfactorily for a few hours but a blooming condition will develop which can be corrected temporarily by the substitution of another tube. However, the proper correction is to reduce the value of the series filament dropping resistor, thereby increasing the filament voltage to the tube (Fig. 5). As an example, if the filament dropping resistor is 4.7 ohms, reduce it to 3.3 ohms.

In this problem as stated in the letter, it is very possible that the wrong

resistor was used or the transformer requires a lower resistor even though service literature indicates the proper resistor is in use.

On the other hand, too much filament voltage can be detrimental to the high voltage rectifier tube. If the filament on the tubes repeatedly opens, it is more than likely due to the voltage being too high. This would require the series filament resistor to be increased in value. If the resistor is 4.7 ohms it can be increased to 6.8 ohms. This type of difficulty could easily occur if the picture tube is over-scanned, thereby causing too much filament voltage to be applied from the transformer.

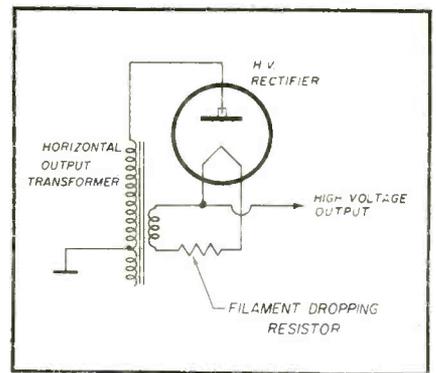


Fig. 5—Reducing value of filament dropping resistor increases voltage.

Dear Answer Man:

I have used several universal replacement yokes in servicing TV receivers and I do not seem to have any luck with them. Most frequently my trouble is a ripple in the left-hand side of the picture and raster, with several vertical bars. It appears to be some kind of damper trouble due to the yoke. Have you any suggestions as to what I can do to overcome this?

A. S. P.

Washington, D. C.

Dear A. S. P.:

It is suspected that the yoke does not have a damping resistor and condenser across the top horizontal deflection coil as illustrated in Fig. 6. Some


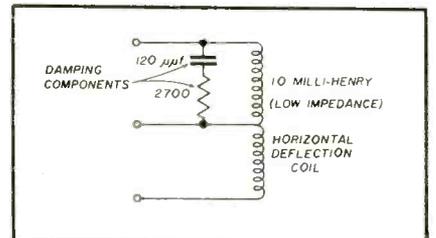


Fig. 6—If 120 μf condenser shorts, it gives the effect of a shorted yoke. yokes have been made available without these components and it is therefore necessary to install them. Suitable values are 2700 ohms for the resistor and 120 μf for the condenser. The series 2700 ohm resistor and 120 μf condenser are connected in parallel with the top horizontal coil and are used for damping purposes. Without them the left side of the picture can contain a ripple. This is most common with the low impedance yokes of 10 millihenry inductance. However, an open condenser across the 30 millihenry high impedance type yoke can also produce the same result.

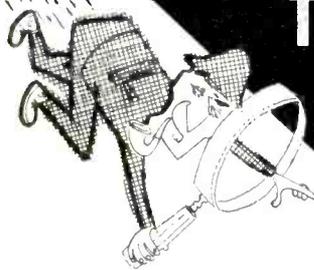These damping condensers should have at least a 2000 volt rating and are usually connected on the yoke itself. On occasion they short across giving the effect of a shorted yoke. Technicians have been known to replace the yoke when the trouble was actually a shorted condenser.




LOOKING for the RIGHT TV REPLACEMENT TRANSFORMER?



you'll find it in

STANCOR'S NEW TV REPLACEMENT GUIDE

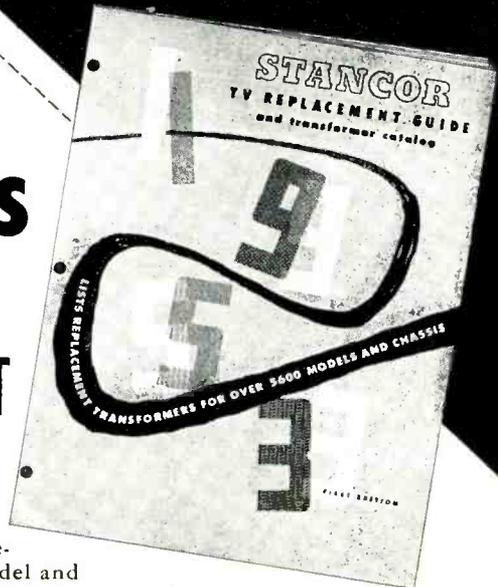

Easier to use . . . lists replacements by manufacturer's model and chassis number and also by original part number.

Up-to-date . . . over 5600 models and chassis are covered, including virtually all sets built prior to 1953 as well as most 1953 models.

You'll save time and trouble when you use this valuable Stancor reference. Get it now from your Stancor distributor, or write us directly for your free copy.

FIVE NEW STANCOR EXACT REPLACEMENT FLYBACKS

Many of these units are the result of recommendations of the Stancor Servicemen Advisory Board, composed of the top TV servicemen throughout the country.

PLUS A-8126, Universal vertical blocking-oscillator transformer for all Philco sets, including 1953 models.

Stancor Part No.	Exact Replacement For	No. of Models Using Flyback
A-8137	Hoffman #5035	29
A-8220	Philco #32-8555	24
A-8221	Philco #32-8565	18
A-8222	Philco #32-8533 & #32-8534	38
A-8223	Philco #32-8572	15



CHICAGO STANDARD TRANSFORMER CORPORATION

3586 ELSTON AVENUE • CHICAGO 18, ILLINOIS

EXPORT SALES—Roburn Agencies, Inc., 39 Warren St., New York 7, N. Y.

ASSOCIATION NEWS

NATESA

Frank J. Moch, president of the National Alliance of Television-Electronics Service Associations, said today that the fifth annual NATESA Convention, to be held in Chicago next Fall will introduce what he termed "a revolutionary new idea in trade association meetings" in which all thirty-nine affiliated associations will participate.

"Planning for the event was started during the recent NATESA convention here," Moch said, "to give us a full year in which to perfect the idea. In my opinion it will prove to be the most valuable and practical idea yet offered the industry, and will be geared to the growing importance of the service industry in relation to manufacturers."

"We have felt for some time that the present concept of trade association conventions and shows needed a drastic rejuvenation to keep pace with this fast-moving industry," Moch said, "and our 1954 NATESA Convention gives us an ideal opportunity to put those theories into practice."

Moch did not elaborate on the plan, except to say that it will be submitted for approval of all affiliated groups in the Alliance soon. Tentative dates selected for the Chicago meeting are mid-September, 1954.

UARTS

The Utah Association of Radio and Television Servicemen, Salt Lake City, has become affiliated with the National Alliance of Television and Electronic Service Association.

ARTSNY

Station WNBC and WNBT have joined forces with Associated Radio-Television Service men of New York, Inc., in a concentrated campaign for better, more fairly-priced radio and television receiver service in the Greater New York area.

Every star seen and heard on the two NBC Flagship Stations in New York will join in this first-of-its-kind public service campaign supporting topflight service by the ARTSNY.

On-the-air spots will outline the objectives and rigid code of ethics of

the organization. Other spots will urge viewers and listeners to put their television and radio receivers in top operating condition "to get the most enjoyment out of WNBC-WNBT's new fall programs."

While urging radio-TV audiences to insist on the best, most reliable service available—the best being provided by ARTSNY—more than \$2,000 a day, seven days a week, will be devoted to the campaign by WNBC-WNBT. Over a month's period, the stations will devote more than \$60,000.00 to the ARTSNY Salute. Many of the TV announcements will display the organization's seal while the station urges


televisioners to watch for this insignia when a repair man calls at their home.

ETA

Electronic Technicians Association recently held the first of a series of 1953 lectures for radio and television servicemen and dealers, co-sponsored by Sylvania Electric Products. The event was held in the Veterans Memorial Building, Highland Park, Michigan, with more than 900 persons attending.

Ralph L. Carew, Chairman of the ETA discussed the progress of the association and the established code of ethics for members. Emery H. Lee, FCC, delivered an interesting talk on

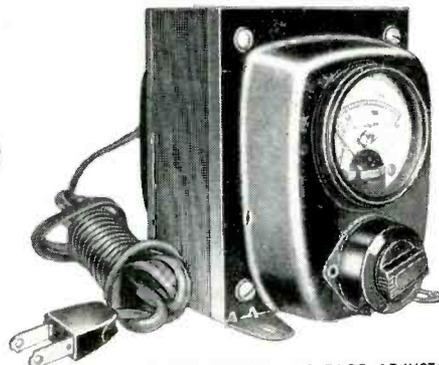**EVERY
SERVICEMAN
NEEDS THIS
VOLTAGE
ADJUSTOR**



T-8394M MANUAL VOLTAGE ADJUSTOR

Where low voltage is affecting TV reception, the service man can detect the condition at once with a T-8394M Acme Electric Voltage Adjustor. And by a simple demonstration he can sell a Voltage Adjustor to the TV set owner. Sales are easy to make because demonstration while servicing a set quickly convinces its owner that the voltage regulation is essential to good TV reception.

How To Use The T-8394M VOLTAGE ADJUSTOR on Service Calls

With the tap switch set at 115 volts, the meter reading will show incoming line voltage. Thus it can be instantly determined if line voltage is lower than normal required for good TV set performance.

The T-8394M Voltage Adjustor can also be used to reproduce the operating condition about which the customer complains by turning tap switch to the voltage which simulates such condition. For example, customer complains that evening program pictures flicker and shrink. When service man calls next day all operation appears normal — voltage tests out properly. But, by adjusting voltage to 97 volts the condition about which the complaint was made is reproduced. This indicates low voltage condition during evening that can be corrected with a T-8394M Voltage Adjustor.

Not A Gadget — A High Quality Unit You'll Be Proud To Use

The T-8394M Voltage Adjustor can be installed instantly, no tools needed. Just plug into most convenient outlet. Then plug television cord into secondary receptacle on Voltage Adjustor.



FOR COMPLETELY AUTOMATIC VOLTAGE CONTROL

Regardless of line voltage supply, the Automatic Voltrol corrects voltage fluctuation over a range from 95 to 130 volts. The voltmeter supplied indicates secondary voltage while unit is in operation. A built-in relay automatically disconnects circuit when set is turned off.

Acme Electric
TRANSFORMERS

ACME ELECTRIC CORPORATION
MAIN PLANT: 4612 WATER STREET • CUBA, N. Y.
West Coast Engineering Laboratories:
1375 West Jefferson Boulevard. • Los Angeles, California
In Canada: Acme Electric Corp. Ltd.
50 North Line Road • Toronto, Ontario

TVI filtering. Andrew Ferguson, Sprague Products, offered many suggestions regarding capacitors. William Anderson, Sylvania's Field Engineer discussed UHF—servicing and test equipment, antennas and reception. He felt confident the average serviceman would be able to work into UHF without much difficulty. He supplemented his remarks by using a projector and slides for a clearer understanding.

NEDA Regional Conferences

National Electronic Distributors Association's program for a series of

regional educational conferences for distributors was given form and substance in a committee meeting held October 30, 31, and November 1, in Pittsburgh at the Greater Pittsburgh Airport Hotel.

The group voted unanimously to hold the first of the conferences in New York City at the Hotel New Yorker. The date was not definitely decided on, but has narrowed down to February 8 or March 1, 1954.

Invitations to attend will be sent to distributors, members and non-members of NEDA, in the area of the Keystone Chapter, New York Metro-

politan Chapter area, upstate New York, Yankee Chapter area, and Southern New England area.

NEDA-Wisconsin

The Wisconsin Chapter of the National Electronic Distributors Association held its annual election of officers on October 19, at the Milwaukee Athletic Club, Milwaukee, Wisconsin.

New President of the group is John A. Swanson, Standard Radio Parts Company, Racine. Other officers elected are Harris E. Sterman, Harris Radio Corporation, Fond du Lac, Vice President; Byron C. Deadman, Northern Radio & Television Co., Green Bay, Secretary; and Charles B. Deadman, Radio Distributors, Madison, Director.

NETSDA

NETSDA has gone on record endorsing a TV Lecture Course for the coming year which is promoted by many leading manufacturers for NETSDA members. It was decided by the delegates that under their Charter, three meetings per year will be held. The first Sunday in February, May and October was selected as regular meeting dates for the organization. The next meeting will be held in Philadelphia, Pa., Sunday, February 7, 1954. Mr. John Wheaton, 464 Sagamore Avenue, East Williston, Long Island, N. Y., is Corresponding Secretary.

TV Group Secures Charter

Television Service Dealers Association of Wyoming Valley, Pa. was recently granted a charter of incorporation by decree of Judge W. A. Valentine. The organization has offices at 336 Wyoming Avenue, Kingston, Pa. An application for a charter was filed August 3 and signed by 10 incorporators. The petition said the association's objective was to foster the interest of television sales and servicing industry in Wyoming Valley. Two of its aims were to create a code of ethics for the servicing industry and a uniform rate schedule.

New Service Group Incorporated At Charlotte, N.C.

Radio and Television Service Association, Inc., has recently been issued a non-stock certificate of incorporation. The corporation has no capital stock and participation is by membership. It is a service organization at the management level, with the object of bringing together owners and managers of radio and television repair

Only ROHN TOWERS
ARE PROVED IN CONSTRUCTION, DESIGN, USE & SALES

3 standard self-supporting ROHN steel towers for your every need!

Famous ROHN FOLD-OVER TOWER (Pat. Pending)

Fold-Over Tower uses standard tower sections plus an inexpensive easy-to-use "fold-over" kit. The perfect answer to this type tower requirement.

NO. 5—A 9-in. triangular designed tower especially designed for TV needs. Can be used up to 40-ft. non-guyed or guyed to 80-ft. An economical, yet sturdy, permanent tower. Can be climbed as can all ROHN Towers.

NO. 10—The standard 12-in. design—heavy duty tubular steel, electric welded and heavily cross-braced through out. Used by thousands coast-to-coast. Up to 50-ft. non-guyed—guyed to 120-ft.

NO. 20—Uses a 14-in. triangular design—the heavy duty tower. Ideal for communications and where greater height is required.

All ROHN towers in 10-ft. sections for easy erection and transportation.

ROHN TELESCOPING MASTS

Come in 20, 30, 40 and 50 ft. sizes. Easily erected, heavy-duty seamless steel tubing throughout.

PLUS A COMPLETE LINE OF ACCESSORIES:

- UHF Antenna Mounts For Towers For Masts
- Wall Mounts


Also House brackets, guy brackets, etc., all ROHN designed!

Contact your ROHN distributor for FREE catalog or write:

ROHN MANUFACTURING COMPANY

DEPT. RTS
 116 LIMESTONE
 BELLEVUE,
 PEORIA,
 ILLINOIS

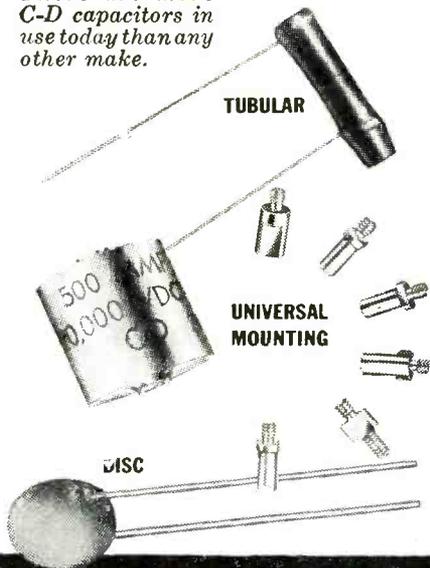There are more C-D capacitors in use today than any other make.



There's a C-D ceramic with the "Million Dollar Body" for every requirement



Every one a winner

A line of the most popular, fast-moving sizes, in both general purposes and temperature compensating types. Ask your C-D jobber about them today! He's listed in your local Classified Telephone Directory. For catalog write to Dept. RS123 Cornell-Dubilier Electric Corp., South Plainfield, New Jersey

CONSISTENTLY DEPENDABLE

CORNELL-DUBILIER
CAPACITORS



PLANTS IN: SO. PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND KOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD AND FOUNTAIN SPRINGS, N. C. SUBSIDIARY: RADIANT CORP., CLEVELAND, OHIO



R. H. SCHNEBERGER

NATIONAL SERVICE MANAGER

OF *Crosley* SAYS...

"... we are glad to see the wide distribution of our information in Rider's Radio-TV-PA Manuals, Tek-Files, TV MANUFACTURERS' RECEIVER TROUBLE CURES Series, UHF PRACTICES AND PRINCIPLES, etc. We keep all of this information in our technical library. When we hold our monthly service classes the distributors, dealers and independent service men who use these manuals and books comment on their accuracy and reliability.

"For the past 20 odd years we

have observed that people in the Radio-TV Servicing Industry have always considered Rider servicing data, both Manuals and Tek-Files, to be an "encyclopedia" of our industry. We are glad to see such technical literature disseminated to the servicing fraternity."

MR. SERVICE SHOP OWNER:

Your integrity, reputation... the "good will" you establish... can only be built or maintained by servicing your customers with the best!

And now TEK-FILE... ONLY \$1.50 per pack

Dependable replacement parts listings beginning with TV 10 and TEK-FILE pack 57

For easier radio servicing... use Rider's 22 AM-FM Radio Manuals

JOHN F. RIDER

PUBLISHER, INC.
480 Canal Street, New York 13, N. Y.

In Canada, Mr. Charles W. Pointon
1926 Gerrard Street, East
Toronto, Ontario

Export Agent:
Roburn Agencies, Inc.
39 Warren Street
New York 7, New York

West Coast Office:
4216-20 W. Jefferson Blvd
Los Angeles, California

Cable Address:
Roburnage N. Y.

Engineered for the Purpose . . .

Copperweld GUY STRAND

TRADE MARK

provides REAL GUYING CONFIDENCE



SOLD BY
RECOGNIZED
PARTS DISTRIBUTORS

Copperweld DOESN'T STRETCH


Soft wire guys frequently stretch badly in service and go slack. This means a wobbly antenna and poor reception. Copperweld Guy Strand is hard drawn—has the strength to stay taut—holds the antenna firmly in place—improves reception.

Copperweld COMBATS RUST

A guy weakened by rust may go unnoticed until a storm brings down the antenna, causing damage many times the cost of the guy. Copperweld Guy Strand is protected against rust by a molten-welded layer of pure copper on each wire. Its strength is lasting.

Copperweld is EASY TO INSTALL

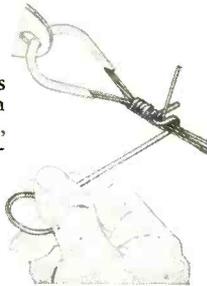No clamps or clips are needed. An ingenious serving tool—one furnished free with each standard length of strand—turns out neat, tightly wrapped dead-ends as strong and permanent as the strand itself.



Write today for further details.

COPPERWELD STEEL COMPANY

Glassport, Pa.

and service businesses for their mutual interest and the betterment of their profession. In addition to promoting cooperation among service dealers, the group attempting to protect customers by adhering to a code of ethics. Meetings are held on the third Tuesday of each month. Group discussions and technical speakers constitute the programs.

The 26 charter members have elected Avery C. Kimbiri, Radio Television and Appliance Co., as President; James Gupton, Foy Electric Co., Inc., Vice-President; Robert Lamb, Lamb Radio and Television Co., Inc., and Harry Murray, Murray's Radio and Television Service, Secretary.

The ultimate aim of our association, Mr. Kimbiri said, "is to build up the prestige of the service dealer to a point where the general public will not be afraid to call on any service shop displaying the organization's emblem."

Color TV Symposium Sponsored By Chicagoland Reps

The Chicagoland Representatives and their guests, including many industry leaders in this area, and numbering 250 in all, were given a frank and honest appraisal on the status of color TV Monday evening, November 2, at Nielson's Restaurant.

The panel, consisting of several industry leaders who spoke "off the record," told the group what, in their opinion, they expected 1954 to bring. They discussed the impact expected on the industry, the problems faced by broadcasters and manufacturers, as well as distributors and service men. A true picture of color TV was presented, starting from the first sets which would be offered to the public with a time table of developments and improvements expected. The limitations and problems were honestly revealed, perhaps for the first time, to as large an industry group. A lively question and answer period followed the speeches.

The panel consisted of Kenneth C. Prince, Executive Secretary of EP & EM and General Manager of the Electronic Parts & Equipment Shows, Inc., acting as moderator; Earl W. Ewald, Director of Tube Engineering, Crosley Corporation, presenting the problems and viewpoint of the color tube manufacturers; Robert W. Galvin, Executive Vice President of Motorola, presenting the manufacturers' point of view; and Harry Alter, President of the set distributor organization bearing his name, covering the distributors' expectations and problems.

Solutions for RADIO-TV Service Business Problems

Now at your Radio-TV Parts Distributor



104 TV SERVICE CALL BOOK

50 Triplicate sets of invoices for use on service calls in sales-book form with space for dealer rubber stamp. Also available with dealer 4-line imprint.

Ask your distributor for details and special imprint order form.

See our complete line of job tickets, service contracts, service systems, service reports, guarantee forms, call routers, collection systems at your Parts Distributor.


Write for Catalog RT

OELRICH PUBLICATIONS

4135 N. Lawler Ave. Chicago 41, Ill.




TV Voltage Trouble?

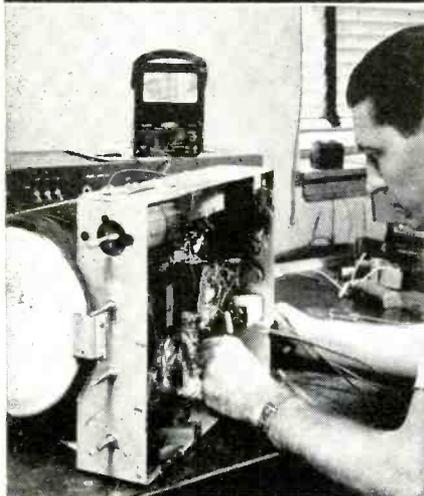

TeleVolt AUTOMATICALLY corrects fluctuating line voltage

Low voltage causes poor television reception. If your customers' line voltage is bad, supply the television manufacturers' specified voltage by plugging in a SOLA TeleVolt Constant Voltage Transformer between the set and wall outlet. It will also protect costly components against damaging high voltage surges. The TeleVolt is a patented voltage regulator that automatically stabilizes voltage within $\pm 3\%$ with line fluctuations as great as $\pm 15\%$; it is not a voltage booster.

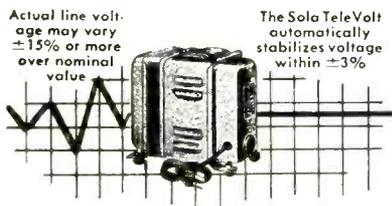

Write today for Bulletin AC-CV-175 or see your electronic distributor

SOLA Tele Volt

Automatic Constant Voltage TRANSFORMERS


SOLA ELECTRIC CO.
4633 W. 16th St. Chicago 50, Ill.

a bear for punishment



C-D does it again with its new Cub

Outperforms any other
molded tubular

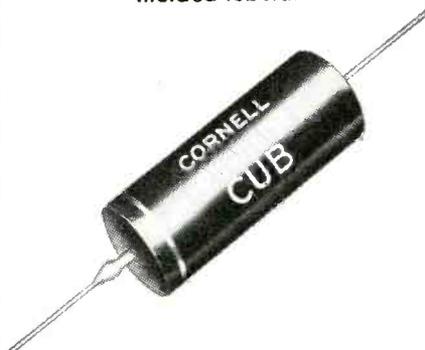

- * A better-looking tubular with
- * A better humidity seal.

Get more for your money by insisting on C-D's new "CUB-KIT".

For your nearest C-D authorized jobber see the Yellow Pages of your Classified Phone Book. Write for Catalog to: Dept. RS3 Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey

CONSISTENTLY DEPENDABLE

CORNELL-DUBILIER CAPACITORS



There are more
C-D capacitors in
use today than any
other make.

PLANTS IN SO. PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, W. I.; INDIANAPOLIS, IND.; SANFORD AND FOGUAT SPRINGS, W. C. SUBSIDIARY: RADIART CORP., CLEVELAND, OHIO

JUST OUT!


the book that teaches
you fast, expert
service techniques

"AM-FM SERVICING SHORT-CUTS"

by Milton S. Kiver

Based on
Actual
Case
Histories

shows you how
to solve
tough jobs
FAST

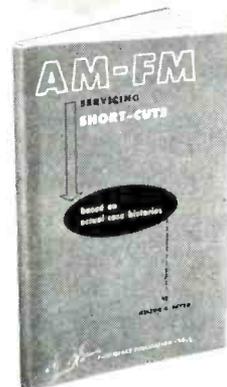

Pays For Itself on Your First Repair

This practical book describes a series of actual AM and FM service case histories, each presenting a specific problem about a specific receiver. The symptoms of the trouble are described and then followed by a step-by-step explanation of how the service technician localized and tracked down the defect. Finally, there is a detailed explanation of how this particular trouble can be tracked down and solved in *any* receiver.

The book is divided into ten sections, each of which deals with specific troubles, such as hum, oscillations, weak sets, etc. The handy index makes it possible to refer instantly to the specific troubles and solutions discussed in the various case histories. The discussions which follow each case history are invaluable—they explain how to apply the proper time-saving techniques to any AM or FM receiver. Here, in one handy volume, is the successful experience of experts—to make your service work easier, quicker, more profitable. 152 pages, 5½ x 8½".

The Book that Pays for Itself
on a Single Service Job

**ORDER
TODAY**

ORDER RK-1
ONLY
\$1.50

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write to Howard W. Sams & Co., Inc., 2209 East 46th St., Indianapolis 5, Ind.

My (check) (money order) for \$..... enclosed. Send..... copy(ies) of "AM-FM Servicing Short-Cuts" (\$1.50 ea.)

Name.....

Address.....


City..... Zone..... State.....

"TIP WRENCH"

GETS NUTS, BOLTS And SCREWS Into "Hard-To-Get-At" Places—HOLDS THEM FIRMLY WHILE TIGHTENING

Or, "TIP WRENCH" goes in and unloosens them and takes them OUT. "TIP WRENCH" is built to work in deep. Holds Nuts, Bolts and Screws where fingers can't hold them. With "TIP WRENCH" you can stop fumbling and save valuable minutes in either REPAIR or LINE PRODUCTION WORK . . . In total, it SPEEDS THE JOB—SAVES THE COST MANY TIMES OVER.

"TIP WRENCH" SOCKET POCKET-WRENCH

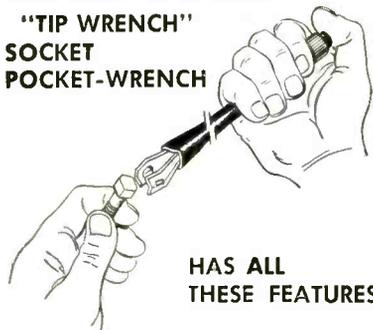

HAS ALL THESE FEATURES:

1. It grips—starts—tightens (or loosens). Just one setting.
2. It GRIPS FIRMLY. A nut or bolt won't slip or turn. For screws, the screw driver blades—one in each jaw—engage the slot in the screw head.
3. By thumb pressure on the plunger head, the Jaws slide out and OPEN, the nut, bolt or screw is inserted, gripped firmly, and the user is ready to go in and complete the job.
4. "TIP WRENCH" is a TOUGH TOOL—for TOUGH JOBS. Built of finest materials and precision manufactured . . . It's RUST PROOF, too.
5. SHOCKPROOF. Has a tough Vinylite insulated shank.
6. Knurled—Hardened Steel Jaws slide in form-fitting barrel which "take the pressure" when tool is in use.
7. Capacity: No. 2 to No. 12 Nut or Screw.

THREE CONVENIENT SIZES:

No. 1. Capacity: No. 2 to No. 8 Nut or Screw 8 1/2"

No. 2. Capacity: No. 6 to No. 12 Nut or Screw 8 3/4"

No. 3. Capacity: No. 6 to No. 12 Nut or Screw 4 1/4"

EACH ORDER A SET **\$1.35**



ORDER THROUGH YOUR JOBBER . . . If he cannot supply immediately, ORDER DIRECT—but GIVE US YOUR JOBBER'S NAME . . . SAVE MONEY & TIME—with "TIP WRENCH"

Sold on A Money-Back Guarantee
Address: "TIP WRENCH" DIVISION
SMITH HEAT TREATING CO.
5865 Wilmington Ave., Los Angeles 1, Cal.

KEY TEST POINTS

[from page 18]

between channels or short the grid to chassis. This makes the oscillator circuit inactive. The grid bias on the tube should no longer be present. Remember that this bias is due to the feedback of the signal voltage from the plate circuit to the grid circuit where it causes the grid to draw current thereby charging up the coupling condenser. Now with no grid bias the tube will conduct heavily and the plate voltage will be lower than either of the two readings in A and B. If the three plate voltages are found to exist in the relative amounts indicated above it is reasonable to assume that the oscillator tube is functioning. This plate voltage information is included only as a supplementary check for cases where there is doubt as to the condition of the oscillator. However, in most cases, checking the grid bias on the oscillator and mixer tubes should be enough to confirm whether or not the oscillator is working properly.

[To Be Continued]

"HOW TO" BOOKS

Simple and Practical



HOW TO TROUBLESHOOT A TV RECEIVER

by J. R. Johnson

A step-by-step guide for newcomers to rapid systematic troubleshooting. Read this book and start out on the right foot!

Over 120 (5 1/4 x 8 1/4") pp. **\$1.80**

HOW TO USE SIGNAL AND SWEEP GENERATORS

by J. R. Johnson

First book on all types of signal and sweep generators. Gives test uses and discusses problems and their solutions in using this equipment. Applications of all signal and sweep generators in AM, FM radio and TV servicing.

Over 140 (5 1/2 x 8 1/2") pages. **\$2.10**

POSITIVE CURES FOR TV TROUBLES

TV MANUFACTURERS' RECEIVER TROUBLE CURES VOL. 1, VOL. 2, VOL. 3 and VOL. 4

Positive cures for TV troubles! Gives you exact directions for correcting TV receiver performance "bugs"! Each cure is official, factory-authorized, direct from the receiver's manufacturer. Listings by manufacturer and model or chassis number. Helps correct the most difficult faults—picture jitter, hum instability, buzz, tearing, etc.

Vol. 1, 115 pages (5 1/4 x 8 1/4") **\$1.80**

Covers 12 brands, Admiral through Dumont

Vol. 2, 117 pages (5 1/4 x 8 1/4") **\$1.80**

Covers 11 brands, Emerson through Jackson

Vol. 3, 119 pages (5 1/4 x 8 1/4") **\$1.80**

Covers 16 brands, Kaye-Halbert through Philco

Vol. 4, Over 115 pages (5 1/4 x 8 1/4") **\$1.80**

Covers 10 brands, Philharmonic through Shaw TV

VOLUME 5 COMING SOON!

Prominent manufacturers not in first 4 volumes

One Service Job Will More Than Pay

The Cost of This Series of Books!

UHF TELEVISION ANTENNAS AND CONVERTERS

by A. Lytel

Latest information on all types of converters, antennas, transmission lines. Valuable for UHF installation techniques.

Over 128 (5 1/4 x 8 1/4") pp. **\$1.80**

GUIDE TO AUDIO REPRODUCTION

by David Fidelman

A to Z explanation of the reproduction of sound, design, construction, assembly and testing of sound systems and their components. Valuable for service technicians, engineers, amateurs.

Over 250 (5 1/2 x 8 1/2") pp., illus. **\$3.50**

OBTAINING AND INTERPRETING TEST SCOPE TRACES

by J. F. Rider

Over 500 actual photographs of test scope traces. Shows how to use scopes and what traces mean. Valuable for servicing TV receivers, FM and AM radio receivers, audio systems and test equipment. Specific test equipment set-ups shown with each application. No other book like it! Over 140 pages. **Only \$2.40**

TV SWEEP ALIGNMENT TECHNIQUES

by Art Liebscher, Test Equipment Specialist

Never before has there been a book such as this on TV sweep alignment! An expert gives you accurate time-saving methods—and tells you how they work. Introduces the new Supermark method. Chock-full of sweep curve pictures. Valuable for servicing in UHF signal areas. 123 (5 1/2 x 8 1/2") pp., illus. **\$2.10**

Write for complete RIDER catalog

Buy these books now from your jobber . . . bookstore . . . if not available from these sources, write to:

HICKOK
Model 670

PROFESSIONAL 5" 'SCOPE with DC Amplifiers

- 15 millivolt sensitivity.
- Stable, clean bright trace, good locking.
- Wide band vertical amplifier, from DC; useable to 5 MC.
- Write for technical details . . .

THE HICKOK ELECTRICAL INSTRUMENT CO.
23 Dupont Ave., Cleveland 8, Ohio

JOHN F. RIDER PUBLISHER, INC.
480 Canal Street, New York 13, N. Y.

New and Popular

Mueller

PRODUCTS



COMPLETELY INSULATED
Alligator Clip
New No. 62 Insulator. Covers Mueller 60 Series Alligator Clips.

NEEDLE CLIP

Pierces insulation—makes quick contact anywhere along insulated wire. No. 50-C.



WEE-PEE-WEE CLIP

A small slim-nosed clip for miniaturized circuits. Phosphor bronze. No. 88.



STAND-OFF INSULATOR

The most versatile! Grips masts, guy wires or gutters. No. 135.



SEND FOR FREE SAMPLES & CATALOG 1905

Mueller Electric Co.
1605 E. 31st St., Cleveland 14, O.



PAMPER

YOUR TV AND

RADIO SETS

WITH DEPENDABLE

OHMITE®


REPLACEMENTS

Little Devil® COMPOSITION RESISTORS




Tiny, yes... but what dependability, ruggedness, and stability! And they provide an extra margin of safety—being rated at 70C rather than 40C. Completely sealed and insulated by molded plastic, they meet all JAN-R-11 requirements... are available in 1/2, 1, and 2-watt sizes in all RTMA values.

TYPE AB NOISE-FREE POTENTIOMETERS

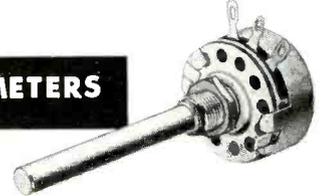

Because the resistance material in these units is solid-molded—not sprayed or painted on—continued use has practically no effect on the resistance. Often, the noise-level decreases with use... and they provide exceptionally long, trouble-free service. Rated at 2 watts, with a good safety factor.

BROWN DEVIL® AND DIVIDOHM® RESISTORS

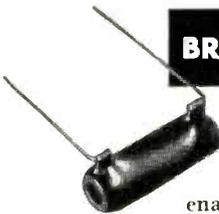

BROWN DEVIL fixed resistors and DIVIDOHM adjustable resistors are favorite vitreous-enameled units! DIVIDOHM resistors are available in 10 to 200-watt sizes; BROWN DEVILS in 5, 10, and 20-watt sizes.



WRITE FOR STOCK CATALOG



Be Right With...

OHMITE

RHEOSTATS • RESISTORS • TAP SWITCHES


OHMITE MFG. CO.
3640 Howard St.
Skokie, Ill.
(Suburb of Chicago)

KENCO KATE SAYS

"NO INSTALLATION PROBLEMS when you use KENCO MOUNTS"



Kenco MINUTE MOUNT ONE PIECE CHIMNEY MOUNT

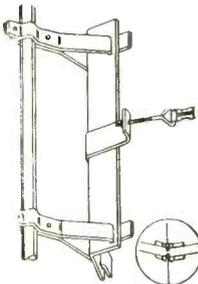

Model 5C-SS

Fastest, easiest chimney mount to install. Bearing feet top and bottom prevent rocking on irregular chimneys. Snap-in feature holds mast while applying hardware. Carriage bolts for easy one hand lockup. One piece welded construction. Heavy gauge steel—hot dipped galvanized. 12 ft. stainless steel band and stainless steel seals. 3 Easy-slide corner guards for uniform tightening and protection of bands.



KENWOOD ENGINEERING CO., INC.
Kenilworth, New Jersey

KESTER

TRADE FLASHES

[from page 64]

FASTER ACTING

EASIER TO USE

LONGER LASTING

THE BEST

Since the most important single step in Radio-Television Servicing is soldering . . . it's just plain good sense to use the best — KESTER SOLDER . . . Key Name in Solder for More Than 50 Years.

KESTER SOLDER COMPANY
4239 Wrightwood Avenue • Chicago 39, Illinois
Newark 5, New Jersey • Brantford, Canada

SOLDER

for **like - new** performance

replace with original **ROGERS** full-focus deflection yokes



Since most of the better TV sets are made with **ROGERS** Deflection Yokes, this same top quality yoke should be used for replacement. With over 25 years of electronic know-how, **ROGERS** Precision Engineered Products make TV sets perform *like new*.

ROGERS Full-Focus Deflection Yoke assures double brilliance with knife-edge sharpness over the entire screen. Each **ROGERS** yoke—precision tested for perfect focus—is designed for peak performance and extra long life.

"the eye tells why"

packaged individually—attractively

ROGERS ELECTRONIC CORP. 43-49 Bleecker St. New York 12, N. Y.

FREE: Send for new catalog "B" listing TV set models and **ROGERS** Yoke and Flyback replacements, or see your jobber.

equipment. This equipment is now in production," T. A. Smith, vice president in charge of the company's Engineering Products Department, disclosed.

Mr. Smith said that deliveries of the first items of color equipment will commence in December. These items, consisting of color monitors and terminal apparatus to be added to existing TV transmission equipment, will enable stations to telecast programs received over telephone circuits.

Ram Educational Forum On TV Sweep Circuits

Ever since 1952, as a service to the television repair industry **RAM** Electronics has had a team of factory engineers touring the important centers of the country to disseminate valuable data and trouble-shooting hints. The latest 5th such forum, held under the joint sponsorship of all **RAM** St. Louis distributors, featured **RAM**'s Al Friedman (National Sales Coordinator) and Victor Markosian (Chief Engineer).

Over 600 servicemen attended the meeting, which covered such topics as: basic functions of each sweep component, considerations in choosing sweep replacements, trouble-shooting sweep circuits, variations in sweep circuits and components, 90-degree deflection circuits and their applications, and current and future developments in sweep components.

To learn when the **RAM** team will forum in your city, write directly to **RAM** Electronics, Irvington-on-Hudson, New York, or inquire at your local distributor.

CBS-Hytron Sets Price For Color TV Picture Tubes

CBS-Hytron, electronic-tube manufacturing division of Columbia Broadcasting System, Inc. recently established a price of \$125 for its new color television picture tube, the **CBS-Colortron**.

John Q. Adams, vice-president in charge of sales, announced that this is the price that will be charged television set manufacturers for sample tubes in the 15-inch size. It compares with a cost of \$200 for the more complicated planar-mask tube.

The **CBS-Colortron** is a revolutionary, low-cost and greatly improved picture tube, simple to mass produce. Developed by a team of **CBS-Hytron** engineers, after two years of research and development, it was first demonstrated here in October.

A Full Size
LIGHTNING ARRESTER
at the Price of a Midget



LIGHTNING ARRESTER

MODEL TA5 Real protection against lightning and static charges — the RADIART Lightning Arrester has all the features! Fits anywhere... inside or out... handles standard or jumbo leads... no wire stripping necessary... does not unbalance the line... low internal capacity... no loss of signal... internal resistance "leaks off" static discharges! UNDERWRITERS LABORATORIES APPROVED.

THE **RADIART** CORPORATION
CLEVELAND 13, OHIO

WIRE WARNING!

WHY

pay more for questionable quality* tubular TV lead-in wire?

*subject to patent infringement.

LOOK



for highest quality license-labeled* Tubular TV Wire...

*JSC Tubular Wire is manufactured under license of Amphenol Pat. 2543696.

DEMAND



the most for your wire dollar... get BOTH Quality**! AND Low Price**!

**JSC—Highest in Quality... Lowest in Price.

JSC NEW Twin Tubular
TV Lead - In Wire...

The best low loss, low cost 300 ohm lead-in for UHF and VHF television.

Rain, snow, dirt or salt deposits do not materially affect impedance and electrical efficiency.



JSC tubular construction contains and protects the concentrated field of energy and reduces to a minimum high ratio signal losses.

Always Look for Orange and Blue Disc of Quality

WEN "Quick-Hot" ELECTRONIC SOLDERING GUN

567 HOURS CONTINUOUS SERVICE

250 WATT
110-120 VOLT AC



and only **\$12⁹⁵**

Which Soldering Gun?

You be the judge! Three competitive soldering guns were to be plugged in each morning... kept-connected, operative, HOT all day. But Soldering Gun "A" lasted only 1/4 hours, burned out its transformer and started smoking! Gun "B" burned out in 21 minutes! The WEN Soldering Gun with Feraloy tip scored 567 HOURS! Or compare this way — the WEN Gun with 50c Feraloy tip averages 25,000 soldering connections. Gun "A" (replacement tip 25c) 800 connections. Gun "B" (new tip \$5.00) 1,627 connections. That means your soldering connections need cost you but 1/500 of 1c — using the WEN Gun. Practically lasts forever under ordinary conditions.

THEN THERE'S THE NEW
Electric
WEN SANDER-POLISHER

Only **\$13⁹⁵**

Ideal for home use and many shop operations. It's light (2 1/2 lbs.) quiet like an electric razor and handy to work with. Operates 240 strokes per second. Sands wood, metal, polishes furniture, your car — anything. Even gives a good massage



RADIO SUPPLY STORES SELLING THOUSANDS

 GUN "A" 1 1/4 HR.	 GUN "B" 21 MIN.	 WEN GUN
--------------------------	------------------------	----------------

Get the Facts! — See Your Jobber or Write —

WEN PRODUCTS, INC., 5808 Northwest Highway, Chicago 31, Ill.

(Export sales — Scheel International, Inc., Chicago)

Announcing
THE NEW
Miller
TV COIL
REPLACEMENT GUIDE

ASK YOUR JOBBER
FOR YOUR COPY TODAY
(Replacement Catalog No. 154)

THE MILLER EMBLEM
- ASSURES THE FINEST IN RADIO AND TV REPLACEMENT COMPONENTS

For a Complete Listing of MILLER PRODUCTS Get Our Latest General Catalog.
J. W. MILLER COMPANY
5917 South Main Street • Los Angeles 3, California

First Aid for "Customer Headaches!"
business display signs for Radio & TV Service

25 SALES SERVICE MESSAGES

designed to promote better customer-dealer relations and to help the dealer:


- Increase Tube Sales
- Make Tube Testing more profitable
- Eliminate "Estimate Disagreements"
- Reduce Tube Refunds
- Sell antennas and accessories
- Sell reconditioned TV sets

And Other Important Sales & Service Messages
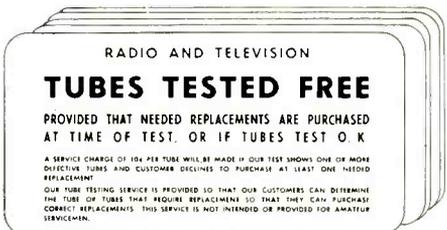
#800 Business Sign Kit..... **\$2.50** Complete Kit

Catalog on Request
See our complete line of Stock Forms at your Distributor Now.

OELRICH PUBLICATIONS 4135 N. LAWLER AVE.
CHICAGO 41, ILL.



The #800 Business Sign Kit contains 25 messages printed on heavy 5" x 10" wood grain finish cards all dealing with specific dealer needs and problems. For easy fastening a sheet of sticky tacks is included in each kit. See it at your Radio-TV parts distributor NOW.

MOVING?

When you change your address please notify our circulation department as soon as possible. This is to your advantage, since it takes approximately 5 weeks to have your stencil changed and duplicate copies cannot be sent. Be sure to give your old as well as your new address.

RADIO-TV SERVICE DEALER

67 West 44th St.
New York 36, N. Y.

TRADE LIT.

[from page 39]

A new catalog, four-page, multi-colored, is now available on the complete line of electronic equipment manufactured by Perma-Power Company, 4727 North Damen Avenue, Chicago 25, Illinois.

A color code calculator covering both capacitors and resistors is being produced by Centralab, 900 East Keefe Avenue, Dept. G-44, Milwaukee, Wis. By setting seven rotating wheels, capacitance or resistance, tolerance, and temperature co-efficient can be read directly. The calculator covers RTMA color code specifications on normal and extended range tubular ceramic capacitors and radial or axial lead resistors.

The 3rd revised and enlarged edition of Milton S. Kiver's well-known book *Television & FM Receiver Servicing*, published recently, has in addition to helpful material on troubleshooting, antennas, installation and servicing covered in previous editions, a whole new chapter on UHF and new material on test instruments, Cascode tuners, keyed sync separators and more. List price is \$4.20. D. Van Nostrand Company, Inc., 250 Fourth Avenue, New York 3, N. Y.

CIRCUIT COURT

[from page 40]

to crystal #2 (1N82) the mixer diode. The antenna is coupled into a pre-selector which is essentially a tuned line with a variable condenser across it to vary the electrical length of the line. This pre-selector is coupled to another tuned pre-selector which operates in the same way as the first one did. The purpose of the second pre-selector is to improve the image-rejection characteristics of the tuner and at the same time make the matching of the antenna and mixer impedances simpler.

The mixer heterodynes the output of this pre-selector and that of the doubler. The output is coupled by means of the detector load into the *if*. This *if* is generally 40 mc, although it can be either 82 mc for feeding the front end of a *vhf* tuner or 21.25 mc for sets that use this as their video *if* frequency.

If You Want SPEAKERS

ORDER OXFORD

World's Largest Producer of Speakers



Used by more manufacturers for original equipment than any other brand

OXFORD


3911 South Michigan Avenue, Chicago 15, Illinois

OXFORD ELECTRIC CORP.

Export: ROBURN AGENCIES, New York City



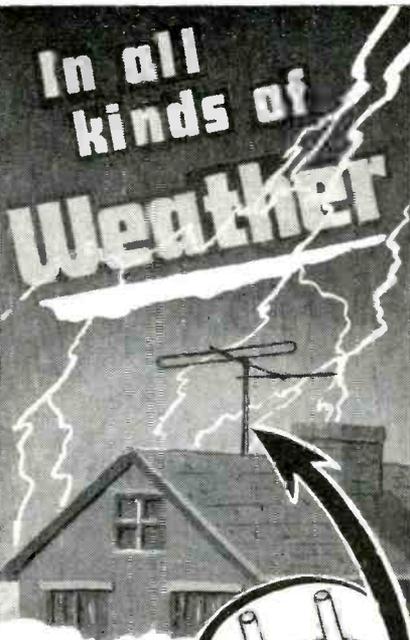In Canada: Atlas Radio Corp., Ltd, Toronto



GIVES BETTER UHF RECEPTION

"ANACONDA" the finest UHF Foam Polyethylene transmission line—

- No Moisture Problems!
- No Termination Problems!
- Extremely Lightweight!
- Low Attenuation!



THIS ↑



← NOT THIS

Has all channel reception for both UHF and VHF

We have UL approved universal type "Lightning Arrestor" for use with all Anaconda UHF lines and other types of flat or round TV wires. A stripper for easy installation is also available.

Write for Samples and New Descriptive Literature

Sold through recognized jobbers only!


"National distributors and warehouse for ANACONDA denseath television and radio wires and cables"

Columbia WIRE & SUPPLY CO.

2850 Irving Park Road • Chicago 18, Ill.

for extreme accuracy and stability...

AEROVOX
Carbofilm
RESISTORS

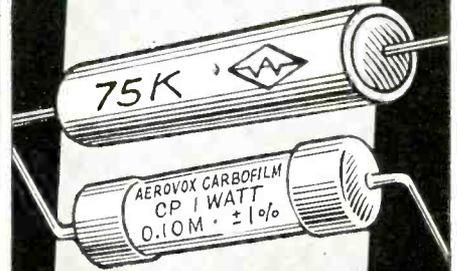

Made under Western Electric license agreement, these carbon-deposit resistors serve a real need in test equipment and laboratory-grade instruments.

Packed and sealed in plastic tubes to insure quality-control accuracy. 1/2, 1 and 2 watts.

Also available in metal-cased hermetically-sealed construction for superlative stability under the most adverse climatic conditions. 1/2, 1 and 2 watts.

Aerovox also offers popular resistor types such as insulated-molded carbons and wire-wounds.

Ask your Aerovox distributor for Carbofilm precision resistors, as well as popular insulated-molded carbons and wire-wounds. Stocked for your convenience!



FOR RADIO-ELECTRONIC & INDUSTRIAL APPLICATIONS

AEROVOX CORPORATION


NEW BEDFORD, MASS., U.S.A.

In Canada: AEROVOX CANADA LTD., Hamilton, Ont.
Export: 41 E. 42nd St., New York 17, N. Y.

ARGYLE

again revolutionizes
TV installation
business... one look
shows you
how

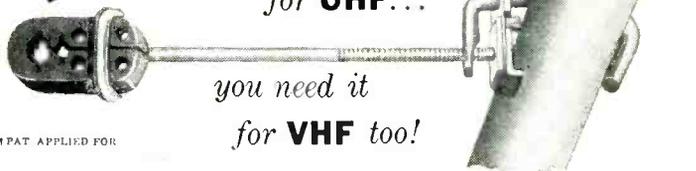The Argyle Mast Type Universal Standoff combined with the new Argyle Mast-Lok clamp permits the best installation possible. Is stronger, more versatile—clamps will not slip or loosen... entire installation is done in a few seconds.



a must
for UHF...

you need it
for VHF too!

PAT. APPLIED FOR

Now—Argyle introduces Mast-Lok... the clamp used in conjunction with the Universal Mast Type Standoff! Available at no difference in price.

The strongest, quickest, and most positive method of securing standoffs to the mast... heavy duty steel with a re-inforced cantilever clamp.

- Improves Reception... rigid engineering and lab tests prove that the New Argyle Universal Standoff tends to substantially reduce coupled-in effects and related evils in the line.
- Big Time Saver... you can actually save 75% of your installation time.
- No Threading—use any type of wire at all... Flat, Tubular, Open, Rotor—When ordering MAST-LOK with Argyle Universal Standoffs*—add letters MC after model number of standoff... Separately model AMC-12.



ARGYLE ELECTRONICS CO.

8 West 18th Street, New York 11, N. Y. • CH 2-2093

COLOR TV

[from page 34]


known as "interleaving." The harmonic which has been chosen for the sub-carrier frequency works out to be the 455th harmonic of $15,750$, which equals 3.579545 mc.

The second principle explains how two signals can be transmitted at the same frequency. It has been found that by displacing two signals 90° with respect to each other, both can modulate a single carrier to produce a phase modulated signal in which the individual signals do not interfere with each other. This is known as *quadrature transmission*.

At the receiver, suitable circuits can extract the original signals. This process takes place in the color decoder and is known as synchronous demodulation.

The third new principle is the fact that an r-f signal can be transmitted containing the sideband resulting from beating a carrier with a modulating signal but omitting the signal carrier frequency itself. This system is known as *suppressed carrier transmission*. Further, in this system, it is not necessary to transmit both sidebands in their entirety. One sideband plus a portion of the other can be sent. This is known as *vestigial sideband-suppressed carrier transmission*. One of the color channels is of this nature. The other channel, due to its low pass-band, is sent double sideband.

South River ★★ NEWS ★★

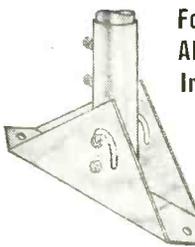

For ONE-MAN
ANTENNA Roof
Installations

ROOF
MOUNT

Model
RM-15

Newly improved model enables installation man to "walk up" antenna and mast from horizontal to vertical position where they then drop and lock securely. Man is then free to guy the mast on any 10 ft. or less installation. (May also be used for higher installations.) Features $5\frac{1}{2}$ " long, heavy gauge steel mast holder to accommodate masts up to $1\frac{1}{2}$ " O.D. Embossed at all critical points for extra strength.

Heavily plated for rust resistance.

Write for new 1953 catalog.

In Canada A. T. R. Armstrong Co., Toronto

SOUTH RIVER METAL
PRODUCTS CO., INC.

SOUTH RIVER, N. J.

PIONEER AND OUTSTANDING PRODUCER
OF FINEST LINE OF ANTENNA MOUNTS

ILLINOIS CAPACITORS HAVE BEEN SERVING SERVICEMEN FOR OVER 19 YEARS



TYPE IHT

The complete dependability of ILLINOIS electrolytic capacitors has made them a favorite with servicemen everywhere!

For over 19 years, ILLINOIS CONDENSER COMPANY has been producing quality capacitors—and during this time has been responsible for many important advancements in electrolytic capacitor construction. Millions of ILLINOIS capacitors, now in service, are proving their absolute dependability.

Used as original equipment by leading TV and radio manufacturers, ILLINOIS electrolytics are "first choice" of servicemen for all replacements!

Write for new Catalog!



ILLINOIS CONDENSER CO.
1616 NORTH THROOP STREET • CHICAGO 22, ILL.

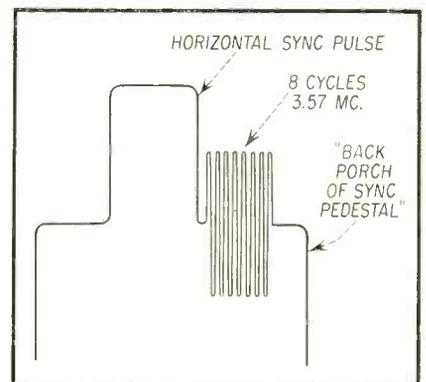


Fig. 4—Color burst; receiver oscillator is put into sync with transmitter.


Suppressed carrier transmission is needed because if we do not suppress the 3.58 mc carrier, interference between this carrier and the luminance signal will take place during the reproduction of the white portions in a scene. This way, when there is no

don't be vague...

insist on
SPRAGUE

TEL-OHMIKE®

CAPACITOR-
RESISTOR
ANALYZER

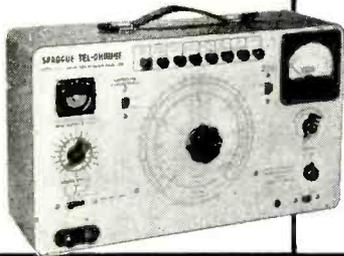

SPRAGUE

NORTH ADAMS, MASS.

don't be vague...

insist on
SPRAGUE

Twist-Lok*
'lytics



*Trademark

SPRAGUE

NORTH ADAMS, MASS.

RADIO-TELEVISION SERVICE DEALER • DECEMBER, 1953

modulation, there is absolutely no output from the color channel.

The last item to note is that the quadrature signals are in fixed reference to the sub-carrier at the transmitter. The receiver, itself, does not have such a reference signal for demodulation purposes. Therefore, a separate 3.579545 mc oscillator is used at the receiver. This oscillator is kept in phase sync with the transmitter sub-carrier by means of a color-burst. This burst consists of from 8-10 cycles of the sub-carrier signal inserted on the back porch of the regular signal sync pedestal (Fig. 4). This color burst brings the receiver oscillator into exact phase sync with the transmitter oscillator resulting in a reference phase for demodulating.

Fig. 5 shows the relationships of the various signals when four bars (saturated red, saturated green, saturated blue and white) are transmitted.

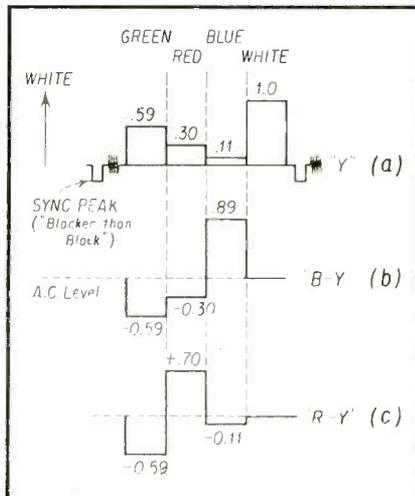


Fig. 5—Relationships of signals when four color bars are transmitted.

Fig. 5a represents the amplitude relationships of the four bars in the luminance channels as they would be at the output of this section. Fig. 5b shows the relative amplitudes in the output of the B-Y channel before modulation in the transmitter, and after demodulation in the receiver. By addition of the B-Y and the luminance signals we come out with the blue signal only, the white signal serving as the light reference. The same analysis can be applied to the R-Y channel (Fig. 5c) to derive the red bar. As for the green bar, there is a slightly more complicated process mixing certain proportions of R-Y and B-Y. This resultant signal is inverted and mixed with the luminance channel to extract the green bar. In this manner the individual colors are made available at the proper terminals of the CRT.

[To Be Continued]

don't
be
vague...

insist on
SPRAGUE
BLACK
BEAUTY®



TELECAP®
tubulars

SPRAGUE

NORTH ADAMS, MASS.

don't

be

vague...

insist

on

SPRAGUE

NORTH ADAMS, MASS.

FREE! NEW '54 EDITION

SIMPLIFIES TV ANTENNA INSTALLATIONS AND SALES




INCLUDES LATEST UHF/VHF DATA & EXCLUSIVE "ANTENNA SELECTOR"

Completely revised by TV authorities Matt Mandl and Ed Noll, this essential pocket size manual includes the exclusive "Antenna Selector", Directronic Antennas, Dimension Guide, Channel Frequencies, Proper Feed Methods, Helpful Hints... everything about every type of TV antenna.

FREE To TV Servicemen, Service Dealers, Dealers, Distributors, Hams, Salesmen, Manufacturers

Publication Price \$1.
Yours free if you write at once.

MAIL THIS COUPON TODAY-

SNYDER MFG. CO., Dept. "B"
22nd & Ontario Sts., Phila. 40, Pa.
Please send free copy of TV 'TENNA TIPS

Name _____
Address _____
City _____ Zone _____ State _____

● **ADVERTISING INDEX** ●

Acme Electric Corp. 67 Agency: Scheel Advtg. Agency, Inc.	Miller, J. W. Company 76 Agency: Industrial Advertising Co.
Aerovox Corporation 77 Agency: Austin C. Lescarboua	Mueller Electric Company 73
American Microphone Co. 24 Agency: Baber, Kraus & Woolsey, Inc.	Oelrich Publications 70, 76 Agency: Sander Rodkin Advtg. Agency
American Phenolic Corp. 19 Agency: Burton Browne Advtg.	Ohmite Manufacturing Co. 73 Agency: The Fensholt Advtg. Agency
American TV & Radio Co. 12 Agency: Firestone-Goodman Advtg.	Oxford Electric Corp. 77 Agency: Sander Rodkin Advtg. Agency
Argyle Electronics 78 Chambre Advtg.	Precision Apparatus Co., Inc. 63 Agency: Shappe-Wilkes, Inc.
Belden Mfg. Co. Cover 3 Agency: The Fensholt Company	Radiart Corporation, The 5, 75 Agency: Stern & Warren
Bussmann Mfg. Co. 7	Rauland Corporation 11 Agency: Burton Browne Advertising
Channel Master Corp. 20, 21 Agency: Duso Advertising, Inc.	Radio Corp. of America Cover 4 Agency: J. Walter Thompson Co.
Chicago Standard Transformer Corp. 66 Agency: Burnet-Kuhn Advtg. Co.	Raytheon Mfg. Co. 17 Agency: Walter B. Snow & Staff, Inc.
Clarostat Mfg. Co., Inc. 2 Agency: Austin C. Lescarboua	Regency 37 Agency: Burton Browne Advtg.
Columbia Wire & Supply Co. 77 Agency: Sander Rodkin Advtg. Agency	Rider, John F. Pub., Inc. 69, 72 Agency: Conti Advtg. Agency, Inc.
Copperweld Steel Company 70 Agency: Marsteller, Gebhardt & Reed, Inc.	Rinehart Books, Inc. 12 Agency: The Harry P. Bridge Co.
Cornell-Dubilier Electric Corp. 69, 71 Agency: Friend, Reiss, McGlone Advtg.	Rogers Electronic Corp. 74 Agency: A. D. Adams Advtg.
Electro-Voice, Inc. 41 Agency: Henry H. Teplitz Advtg.	Rohn Manufacturing Co. 68 Agency: Jackson, Haerr, Peterson & Hall, Inc.
Equipto 64 Agency: Arthur R. Mogge, Inc.	Sears, Roebuck & Co. 42 Agency: The W. E. Long Co.
Guardian Elec. Mfg. Co. 42 Agency: Kennedy & Company	Sams, Howard W. & Co., Inc. 71 Agency: George Brodsky Advtg.
Hickok Electrical Instrument Co. 72 Agency: Ritchie & Sattler, Inc.	Sangamo Electric Company 31 Agency: Arthur R. Mogge, Inc.
Illinois Condenser Co. 78 Agency: Bartz Advtg. Agency	Smith Heat Treating Co. 72 Agency: Clark Collard Advtg. Agency
Jersey Specialty Co. 75 Agency: George Gero Advertising	Snyder Mfg. Co. 25, 80 Agency: Brooks & London
JFD Manufacturing Co., Inc. 29 Agency: Burton Browne Advtg.	Sola Electric Co. 71 Agency: Sidney Clayton & Associates
Kenwood Engineering Co. 73	South River Metal Products Co. 78 Agency: Ari-Copy Advtg. Agency
Kester Solder Company 74 Agency: Paul J. Steffen Co.	Sprague Products Company 79 Agency: The Harry P. Bridge Company
Kirby Products Corp. 39 Agency: Kap Studios	Sylvania Electric Products, Inc. 13 Agency: Cecil & Presbrey, Inc.
MacMillan Co., The 65 Agency: Atherton & Currier, Inc.	Television Hardware Mfg. Co. 32 Agency: Paul J. Steffen Co.
Mallory, P. R. & Co., Inc. 9 Agency: The Aitkin-Kynett Company	Telrex, Inc. 8 Agency: George Homer Martin Advtg.
Merit Transformer Corp. 15 Agency: Burton Browne Advertising	Trio Manufacturing Company 1, Cover 2 Agency: Bartz Advtg. Agency
	Wen Products, Inc. 75 Agency: R. W. Sayre Co.



Belden

Aptitude-Tested

INTERCOMMUNICATIONS CABLES

Aptitude-tested Belden Intercommunications Cables are available for every type of installation and for every type of equipment. The permanence and trouble-free performance of Belden Inter-Com Cables assure you constant quality in your work. For more profitable installations, specify Belden Inter-Com Cable.

Belden Manufacturing Company
 4639 W. Van Buren Street.
 Chicago 44, Ill.

	For Station-to-station and extension Wiring (Unshielded)		For Station-to-terminal Wiring (Unshielded)		For Station-to-station and Extension Wiring (Shielded)	
A.W.G. and No. Condrs.	22-2	22-12	22-12	22-3	22-3	22-3
Stranding	Solid	Solid	7x30	7x30	7x30	7x30
Nom. Diam (inches)	.145	.265	.310	.210	.220	.220
No. Pairs	1	6	6	Not Paired	Not Paired	Not Paired
Insulation Thickness (inches)		.010	.010	.010	.010	.010
Tinned Copper Shielding	None	None	None	Over 1 conductor	Over 1 conductor	Over 3 conductors
						
	8740	8743	8747	8734	8735	8735

GENERAL PURPOSE PLASTIC INSULATED CABLES.

Flexible, lightweight, and small diameter. Applications include control, annunciator, and communication circuits.

A.W.G. and No. Condrs.	22-4	22-3	22-5	22-7 18-2
Stranding	7x30	7x30	7x30	7x30 16x30
Nom. Diam (inches)	.168x.276	.140	.170	.245
No. Pairs	2			
Insulation Thickness (inches)	.015	.010	.010	.010 .018
Tinned Copper Shielding	Over 1 pair			
				
	8732	8443	8445	8449

Belden
Radio WIRE

The
Aptitude-Tested **LINE**

Have you hung up

your shingle?

IT PAYS TO KEEP GOOD COMPANY . . . and it's good business to advertise the good company you keep.


Thousands of dealers and servicemen are using the sales-magic in the RCA name to instill confidence in their customers. Identifying *your* name with RCA pays off in dollars and cents.

And it's so easy to do . . . because RCA's new Dealer Identification Program provides you with a handsome "shingle" with your name on it, that you'll be proud to display in your shop. When a customer sees this Dealer Identification Plaque he *knows* you are using the best tube products available.

So, we ask . . . "Have you hung up *your* shingle yet?" If not, be sure to see your **RCA Tube Distributor** today and learn how *you* can qualify for a Registered Dealer Plaque at no extra cost.

Unlock the door to bigger profits

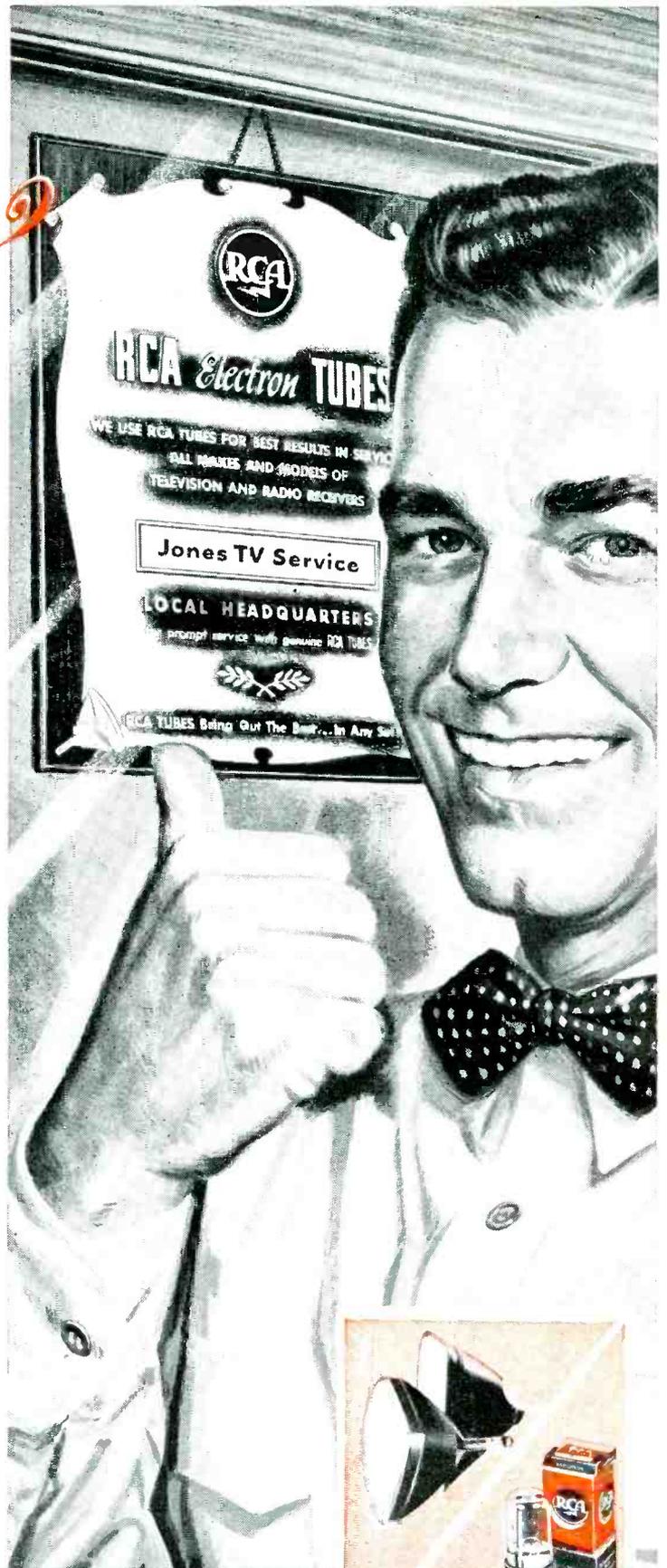Here's *your* key to better business . . . RCA's dynamic Dealer Identification Program. Ask your *RCA Tube Distributor* for your copy of the colorful, 16-page booklet "A Magic Pass-Key to Customer Confidence." It tells you how — for the first time—you can become a Registered Dealer . . . and get *extra* sales benefits.



RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N. J.