

DEC. 21st

1929

RADIO


REG. U.S. PAT. OFF.

WORLD

15
CENTS

404th Consecutive Issue—EIGHTH YEAR

SUPERAUDIBLE SOUND TRANSMISSION

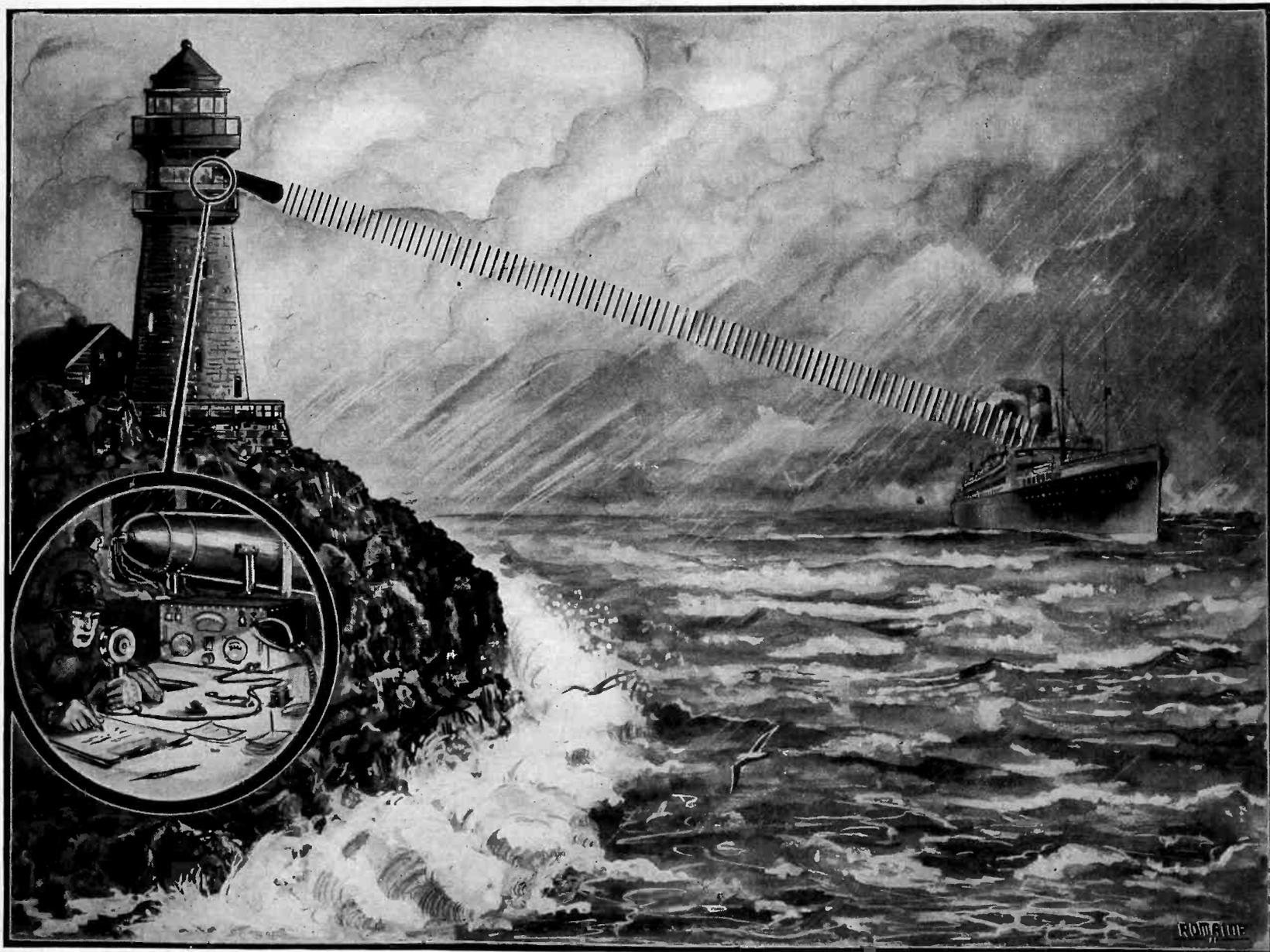


A lighthouse communicating with a ship at sea by means of a beam of modulated superaudible sound waves. Where light cannot penetrate these sound waves go through easily. See pages 5, 6 and 7.

HB 33 and HB 44 Construction

RADIO WORLD, published by Hennessy Radio Publications Corporation. Roland Burke Hennessy, editor; Herman Bernard, managing editor and business manager, all of 145 West 45th Street, New York, N. Y.


The Latest in Tuning Equipment

SHIELDED COIL

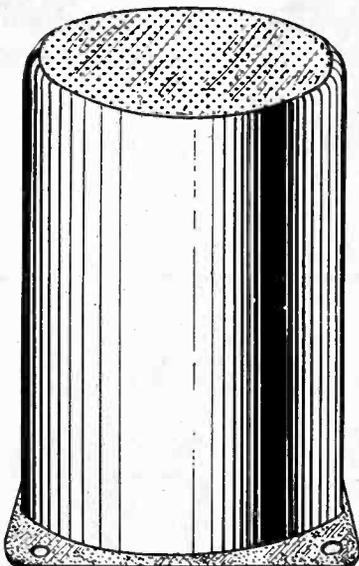


RF transformer in aluminum shield 2 3/4" square at bottom, 3 3/4" high. If metal sub-panel is used no extra base is needed. Coils have brackets on. You must assemble in shield yourself and solder winding terminals to built-in lugs. For all circuits and stages, including screen grid tubes.
 Cat. No. SH3 for .00035 mfd.\$0.95
 Cat. No. SH5 for .0005 mfd.\$1.00
 Cat. S11B (extra base)\$0.10

BERNARD TWO-TUBE TUNER ASSEMBLY

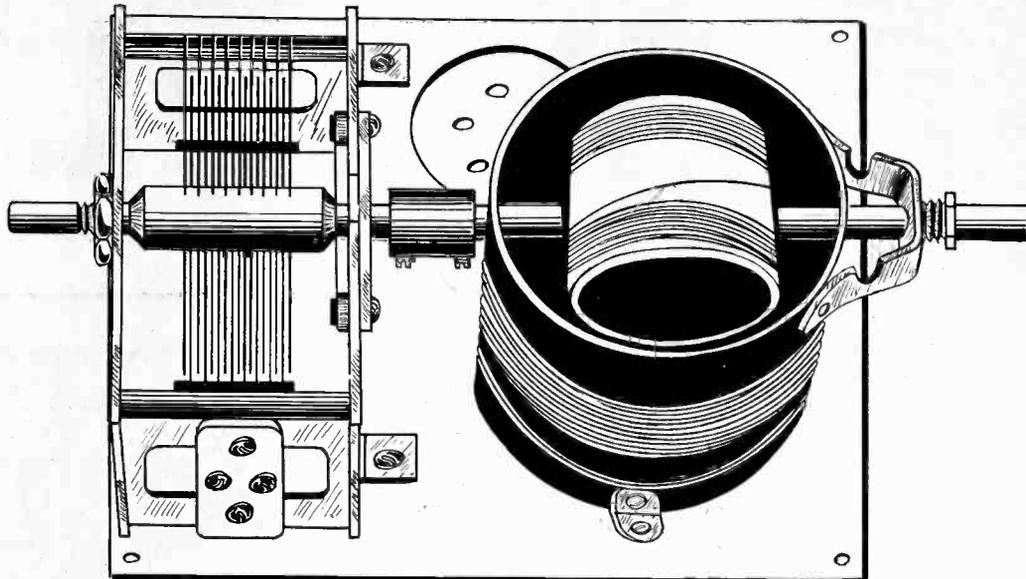


For building a tuner consisting of a stage of screen grid radio frequency amplification and a detector, AC or battery-operated, use the Bernard two-tube tuner assembly. Suitable for single control with one drum dial or separately tuned stages with two flat-type dials. The assembly consists of antenna stage (BTL-AC or BTL-DC), having Bernard Tuner BT3A, a .00035 mfd. condenser, socket, link and aluminum base. The detector input stage (BTR-AC or BTR-DC) consists of the same parts, but the coil has a tuned primary with untuned input to detector. Assemblies are unwired but are erected.
 The condenser has shaft protruding at rear, so if two dials are used coil is put at front panel in either instance and for AC operation, 224 Rf and 224, 227 or 228 detector, order Cat. No. BTL-AC and BTR-AC at \$6.00.
 For battery operation of filaments, 222 Rf and 222, 240, 201A or 112A detector, order Cat. No. BTL-DC and BTR-DC at \$6.00.
 [Note: for drum dial single control an 80 mmfd. equalizing condenser is necessary. This is extra at \$0.35. Order Cat. EQ-80.]

ANTENNA COUPLER

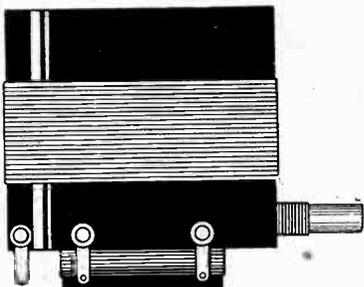


Cat. No. VA5—\$0.85
FOR .0005 MFD. CONDENSER
 Moving primary and fixed secondary, for antenna coupling. Serves as volume control
 Cat. No. VA3 for .00035 mfd.\$0.90

BERNARD TUNERS

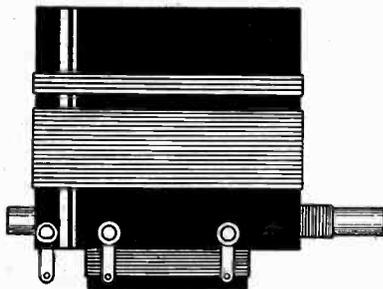


Cat. No. BT5A—\$1.35
FOR .0005 MFD. CONDENSERS

Bernard Tuner BT5A for .0005 mfd. for antenna coupling, the primary being fixed and the secondary tuned. This coil is used as input to the first screen grid radio frequency tube. Secondary has moving coil.
 Cat. No. BT3A for .00035 mfd. ..\$1.35
 Bernard Tuner BT3B for .0005 mfd. for working out of a screen grid tube, tuned primary, untuned secondary. Primary has moving coil.
 Cat. BT3B for .00035 mfd. ..\$1.35

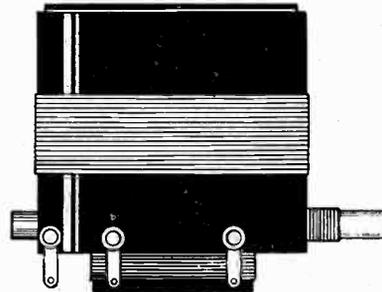


Cat. No. BT5B—\$1.35
FOR .0005 MFD. CONDENSER

SG TRANSFORMER

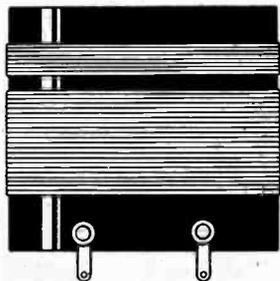

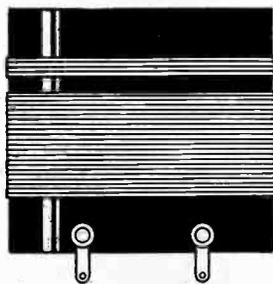Cat. No. SGS5—\$0.60
FOR .0005 MFD. CONDENSER
 Interstage radio frequency transformer, to work out of a screen grid tube, primary untuned.
 Cat. No. SGS3 for .00035 mfd.\$0.65




Cat. No. RF5—\$0.60
FOR .0005 MFD. CONDENSER

DIAMOND PAIR

Cat. No. RF5—\$0.60
FOR .0005 MFD. CONDENSER
 Antenna coil for any standard circuit, and one of the two coils constituting the Diamond Pair.
 Cat. No. RF3 for .00035 mfd. \$0.65
 Cat. No. SGT5—\$0.85
FOR .0005 MFD. CONDENSER
 Interstage 3-circuit coil for any hookup where an untuned primary is in the plate circuit of a screen grid tube.
 SGT3 for .00035 mfd. \$0.90

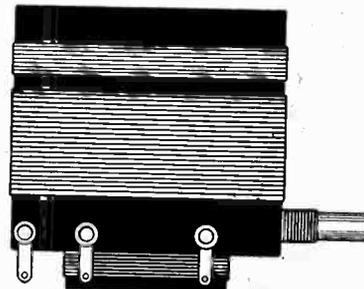Order the Diamond Pair, Cat. DP5 for .0005 mfd. at\$1.45
 Order the Diamond Pair, Cat. DP3 for .00035 mfd. at\$1.55
 [Note: These same coils are for AC or battery circuit.]




Cat. No. SGT5—\$0.85
FOR .0005 MFD. CONDENSER



FL4 \$0.30

Flexible insulated coupler for uniting coil or condenser shafts
 Order Cat. FL4 at\$0.30
 Equalizing condenser, 80 mmfd., for connection across any tuning condenser where ganging is resorted to, or for equalizing independently tuned circuits to make dials track.
 Order Cat. EQ80 at\$0.35

STANDARD TUNER

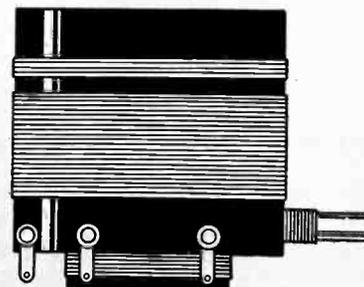

The standard three-circuit tuner is used with primary in the plate circuit of any RF tube, AC or battery type, excepting only screen grid tube. For .0005 mfd. order T5 at\$0.85
 For .00035 order Cat. T3 at\$0.90
 All coils have 2 1/2" diameter, except the shielded coil, which is wound on 1 3/4".
 The coils are wound by machine on a bakelite form, and the tuned windings have identical inductance for a given capacity condenser, i. e. .0005 mfd. or .00035 mfd. Full coverage of the wave band is assured.
 All coils with a moving coil have single hole panel mounting fixture. All others have base mounting provision. The coils should be used with connection lugs at bottom, to shorten leads.
 Only the Bernard Tuners have a shaft extending from rear. This feature is necessary so that physical coupling to tuning condenser shaft may be accomplished by the insulated link.

Screen Grid Coil Company,
 145 West 45th Street,
 New York, N. Y. (Just East of Broadway.)

Enclosed please find \$..... for which please send at once the following parts:

- Cat. No. at \$
- Cat. No. at \$
- Cat. No. at \$
- Please ship C. O. D.

Name

Address

City State

Short Wave Circuit




National Thrill Box, 4-tube short wave circuit, 15 to 535 meters, battery-operation of filaments; B supply, either batteries or eliminator.

Get a real kick out of listening to foreign stations on a real short-wave circuit, the National Thrill Box. Uses one 222 screen grid RF amplifier, one 200A detector, one 240 first audio and one 171A or 112A output. Single control. Buy the parts and build the circuit in two hours. Data sheet shows dial settings where foreign stations come in. Cat. SW4EF, all parts, including decorative brown steel cabinet, all six plug-in coils, list price \$51.90 (less tubes). Your price \$31.00.

Guaranty Radio Goods Co.
143 West 45th Street New York City

Horn Unit \$2.25

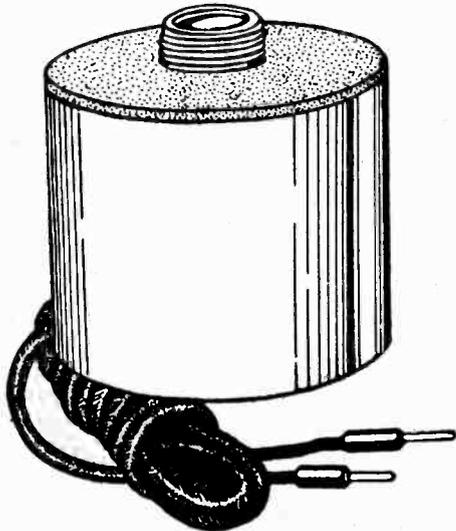

This unit is pre-eminent for horn-type speakers such as the exponential horns or other long tone travel horns. The faintest word from a "whispering tenor" or the tumultuous shout of the crowd or highest crescendo of the band is brought out clearly, distinctly. Stands up to 450 volts without filtering. Works right out of your set's power tube, requiring no extra voltage source. Standard size nozzle and cap are die-cast aluminum, one piece, with milled platinum-like finish. The casing is full nickel, of highest possible polish. Works great from AC set, battery set or any other set, push-pull or otherwise.

For Portable Use

This unit can be used in a portable without any horn attached and will give loud reproduction. Order Cat. 225, with 4 1/2 ft. cord attached. (Shipping weight, 2 lbs.) \$2.25

Air-Column Horn

8-ft. tone travel molded wood horn (less unit No. 225) is obtainable already mounted in a baffle box. Outside overall dimensions of baffle box, 21 1/4" high, 18" wide, 15" front to back. Shipping weight, 27 lbs. Order Cat. 596 @ \$8.00

Acoustical Engineering Associates,
145 W. 45th St., N. Y. City (Just E. of Bway).

Please ship C. O. D.
 Cat. No. 225 @ \$2.25 Cat. No. 596 @ \$8.00

Name


Address

City State

FIVE-DAY MONEY-BACK GUARANTEE

For Christmas EVERY DAY!

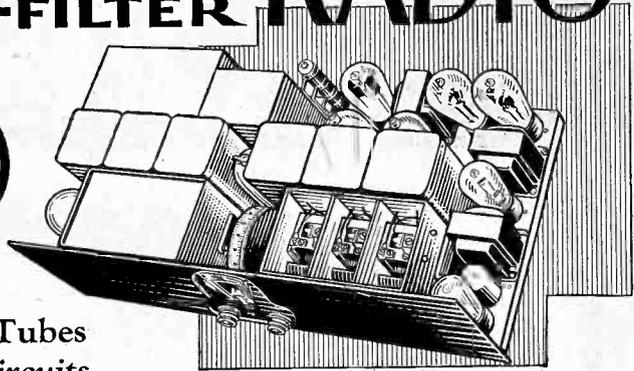OWN the World's Premier Custom-Built RADIO BAND-FILTER



Screen Grid Tubes
Six Tuned Circuits

YOU don't have to be an acoustical expert to recognize superlative tone—nor a radio engineer to know when you're listening to a program from the other side of the world—sweet, clear, free from noise or interference.

But the more you know about the fine points of radio design, the greater your appreciation of what Hammarlund engineers have accomplished in the new Custom-Built "Hi-Q-30" Band-Filter Screen-Grid Radio.

Here's amazing power, sensitivity, selectivity, tone, beauty; with unlimited choice of cabinets and speakers. For the first time a unit-built chassis with the chief units ready-wired and factory-tested. A. C. and battery models, \$139.50 to \$1,175, complete, less tubes.

Ask your local custom-radio builder to demonstrate the "Hi-Q-30" and to build one for you. Or assemble it yourself. It is easy and perfect results are assured.



BLACKSTONE

Choice of
FINEST CABINETS
And Speakers

MAIL COUPON for
the 48 page "Hi-Q-30"
MANUAL.



WINDSOR

The "Hi-Q-30" chassis fits standard stock cabinets. Nine beautiful, specially selected models are supplied by Hammarlund. Fully described in "Hi-Q-30" Manual.

HAMMARLUND-ROBERTS, Inc.
424-438 W. 33rd St., New York, N. Y.

Enclosed 25c (stamps or coin) for 48-page "Hi-Q-30" Manual.

NAME

ADDRESS

(RW-2)

NEW DRAKE'S ENCYCLOPEDIA—1,680. Alphabetical Headings from A-battery to Zero Beat, 1,025 Illustrations, 920 Pages, 240 Combinations for Receiver Layouts. Price, \$6.00. Radio World, 124 W. 45th St., N. Y. C.

ARISTOCRAT FLOOR SPEAKER—With Molded Wood Horn and Horn Motor built in. Great value. \$14.00. Acoustical Engineering Associates, 143 W. 45th St., N. Y. C.

HIGHEST RESISTANCE PHONES, \$1.65—You can't beat them at the price. Send now. Guaranty Radio Goods Co., 143 W. 45th St., N. Y. C.

TRIAL SUBSCRIPTION, 8 WEEKS, \$1.00. Send \$1 and we will send you Radio World for 8 weeks, postpaid. RADIO WORLD, 145 West 45th St., N. Y. City.

READ OUR CLASSIFIED ADS

And use this department if you have anything to sell. 10c a word, \$1 minimum. Radio World, 145 W. 45th St., N. Y. City.


Hi-Q 30 Wholesale Prices!

Write or wire!
Guaranty Radio Goods Co.
143 West 45th St.,
New York City


LOOK AT YOUR WRAPPER

You will see by the date thereon when your subscription for Radio World expires. If the subscription is about to run out, please send us renewal so that you will not miss any copies. Subscription Department, RADIO WORLD, 145 West 45th St., N. Y. City.


Power Amplifier Equipment

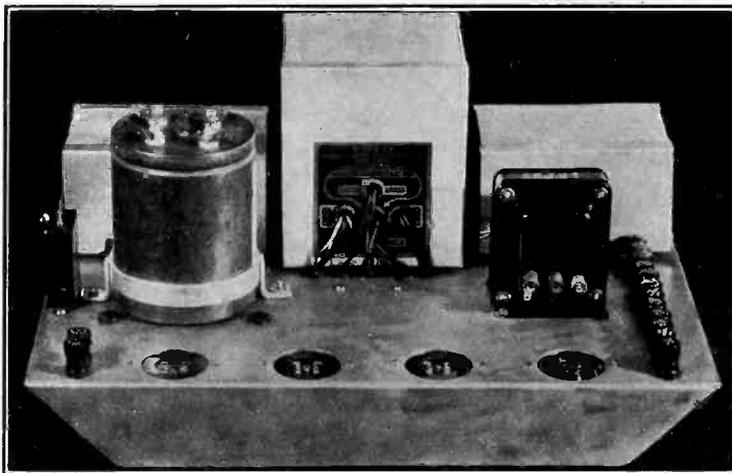

At left is illustrated a push-pull power amplifier, using a first stage of resistance coupled audio, 280 rectifier and two 245s in push-pull, as described in the November 2d issue of Radio World. Abounding volume and faithful tone reproduction are assured. The Polo Filament-Plate Supply, two Polo center-tapped audio chokes and a Multi-Tap Voltage Divider are used, with a Q 2-8, 2-18 Mershon condenser, an input push-pull audio transformer and auxiliary equipment. The total parts, including cadmium-plated steel sub-panel, come to \$43.57 net, the best power amplifier for that modest amount. Provision is made for phonograph pickup plug insertion. Thirteen output voltages are provided, including 300, 180, 75, 50 and an assortment of nine different voltages under 50 available for bias. All A, B and C voltages are provided for the power amplifier and for a tuner to be used with it employing 227, 224 or 228 tubes. Order Cat. PO-245-PA @ \$43.57 net, for 50-60 cycles, 110 volts. [For 25 cycles order PO-245-PA-25 @ \$48.57. For 40 cycles order PO-245-PA-40 @ \$46.07.] Sub panel alone, cat. SPO @ \$3.50

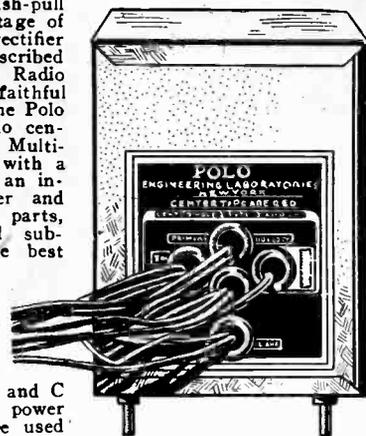

Polo 245 Filament Plate Supply (less chokes) has four windings, all save primary center-tapped (red) is 4 1/4" wide, 5" high, 4" front to back. Weight, 9 lbs. Filament windings, 2.5 v. at 12 amps., 2.5 v. at 3 amps. (for 245 filaments), 5 v. at 2 amps. for 280 rectifier, and 724 v. @ 80 m.a., center-tapped. Order Cat. PFPS @ \$7.50. [For 25 cycles order Cat. PFPS-25 @ \$12.00.] [For 40 cycles order Cat. PFPS-40 @ \$10.00.]

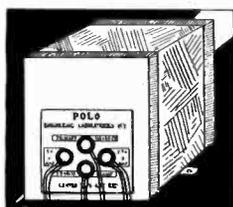


Polo Filament Transformer Only four windings, consists of 50-60 cycles 110 v. winding, 2 1/2 v. at 12 amps., 2 1/2 v. at 3 amps., 5 v. at 2 amps. All windings, save primary, are center-tapped (red). Size, 4 1/4" high x 3 3/4" wide x 3" front to back. Weight, 6 lbs. Order Cat. PFT @ \$4.25. [For 25 cycles order PFT-25 @ \$7.00; for 40 cycles order PFT-40 @ \$6.25.]

By-pass Condensers
For by-passing B+ leads to ground or C minus from 200 v. post or less, where current is less than 10 m.a., 1 mfd. paper dielectric condensers are useful. Order LV-1 @ \$0.50 ea.

Filter Condensers
For high voltage filtration next to the rectifier, use 1 or 2 mfd. The 2 mfd. makes the output voltage a little higher.
Order Cat. HV-1 (1,000 v. DC, 550 v. AC) @ \$1.76
Order Cat. HV-2 (1,000 v. DC, 550 v. AC) @ \$3.52

Filament-Plate-Choke Block
Same as Filament-Plate Supply, except that two 50 henry chokes are built in. Six windings: primary, 110 v., 50-60 cycles; 2.5 v. at 12 amps.; 2.5 v. at 3 amps.; 5 v. at 2 amps.; 724 v. at 80 m.a.; choke All AC windings center-tapped (red), except primary. Connect either end of a choke to one end of other choke for midsection. Order Cat. P-245-FPCH @ \$10.00 [For 40 cycles order P-245-FPCH-40 @ \$13.50.] [For 25 cycles order P-245-FPCH-25 @ \$14.50.]

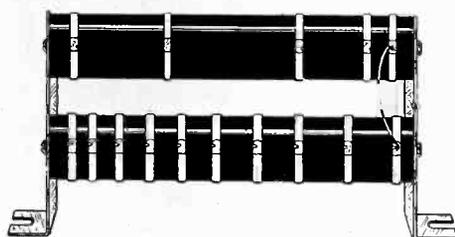

Two rugged, expertly engineered wire-wound, enamelled resistors, mounted in series, one atop the other, with fourteen useful lugs, providing all necessary choice of voltages without the uncertainty of adjustable variable resistance.

The Multi-Tap Voltage Divider has a total resistance value of 13,850 ohms, in the following steps: 3,000, 4,500, 2,000, 800, 700, 600, 550, 500, 450, 400, 200, 100 and 50 ohms. With the zero voltage lug (at lower left) the total number of useful lugs is fourteen. The resistance stated are those between respective lugs and are to be added together to constitute 13,850 ohms total.

A conservative rating of the Multi-Tap Voltage Divider is 50 watts, continuous use. The unit is serviceable in all installations where the total current drain does not exceed 125 milliamperes.

Extreme care has been exercised in the manufacture of the Multi-Tap Voltage Divider. It is mounted on brackets insulated from the resistance wire that afford horizontal mounting of the unit on baseboards and subpanels.


There long has been a need for obtaining any necessary intermediate voltage, including all biasing voltages, from a Multi-Tap Voltage Divider, but each lug has to be put on individually by hand, and soldered, so that manufacturing difficulties have left the market barren of such a device until now.

The Multi-Tap Voltage Divider is useful in all circuits, including push-pull and single-sided ones, where the current rating of 125 milliamperes is not seriously exceeded and the maximum voltage is not more than 400 volts. If good ventilation is provided, this rating may be exceeded 15 per cent.


The expertness of design and construction will be appreciated by those whose knowledge teaches them to appreciate parts finely made.

When the Multi-Tap Voltage Divider is placed across the filtered output of a B supply which serves a receiver, the voltages are in proportion to the current flowing through the various resistances. If a B supply feeds a receiver with two-stage audio amplifier, the last stage a single-sided 245, then the voltages would be 250 maximum for the power tube, 180, 135, 75, 50, 40, 35, 30, 25, 16, 10, 6 and 3. By making suitable connection of grid returns the lower voltages may be used for negative bias or even for positive voltage on the plates.

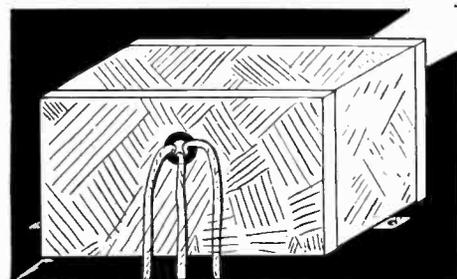If push-pull is used, the current in the biasing section is almost doubled, so the midtap of the power tubes' filament winding would go to a lug about half way down. Order Cat. MTVD at \$3.95.



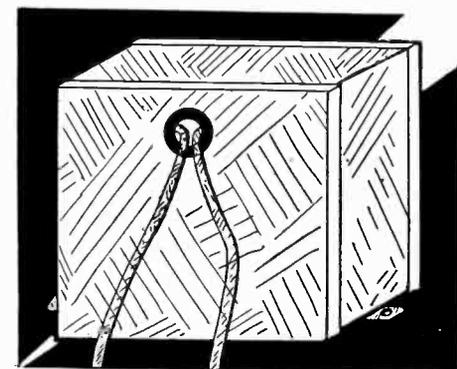Center-tapped double choke, 125 m.a. rating, 30 henrys in each section. Used for filtering B supply or for a push-pull output impedance, where speaker cords go directly to plates of tubes. Center tap is red. Order Cat. PDC @ \$3.71.



Single 30 henry 100 m.a. choke for filtered output (where condenser is used additionally) or for added filtration of a B supply. Order Cat. PSC @ \$2.50.

ACOUSTICAL ENGINEERING ASSOCIATES,
143 West 45th St., N. Y. City.
(Just East of Broadway.)

Please ship at once the following:

Quantity	Cat. No.	Product	Price
<input type="checkbox"/>	PO-245-PA	Power amp. parts, 50-60 c.	\$43.57
<input type="checkbox"/>	PO-245-PA-40	Same, 40 cycles	46.07
<input type="checkbox"/>	PO-245-PA-25	Same, 25 cycles	48.57
<input type="checkbox"/>	PFPS	Fil. plate supply, 50-60 c.	7.50
<input type="checkbox"/>	PFPS-40	Same, 40 cycles	10.00
<input type="checkbox"/>	PFPS-25	Same, 25 cycles	12.00
<input type="checkbox"/>	PFT	Fil. trans., 50-60 c.	4.25
<input type="checkbox"/>	PFT-40	Same, 40 cycles	6.25
<input type="checkbox"/>	PFT-25	Same, 25 cycles	7.00
<input type="checkbox"/>	P-245-FPCH	Power-filter block	10.00
<input type="checkbox"/>	P-245-FPCH-40	Same for 40 cycles	13.50
<input type="checkbox"/>	P-245-FPCH-25	Same for 25 cycles	14.50
<input type="checkbox"/>	PDC	Single choke	2.50
<input type="checkbox"/>	PSC	Multi-tap volt. div.	3.95
<input type="checkbox"/>	MTVD	Double c.-t. choke	3.71
<input type="checkbox"/>	Q2-8, 2-18B	Mershon with bracket	5.15
<input type="checkbox"/>	LV-1	200 v., 1 mfd. by-pass cond.	0.50
<input type="checkbox"/>	HV-1	1,000 v., 1 mfd. filter cond.	1.76
<input type="checkbox"/>	HV-2	1,000 v., 2 mfd. filter cond.	3.52
<input type="checkbox"/>	SPO	Subpanel	3.50

Enclosed please find check—money order—for the above. [Note: Canadian remittance must be by postal or express money order.]


Please ship C.O.D.

NAME.....

ADDRESS.....

CITY..... STATE.....

5-DAY MONEY-BACK GUARANTEE!

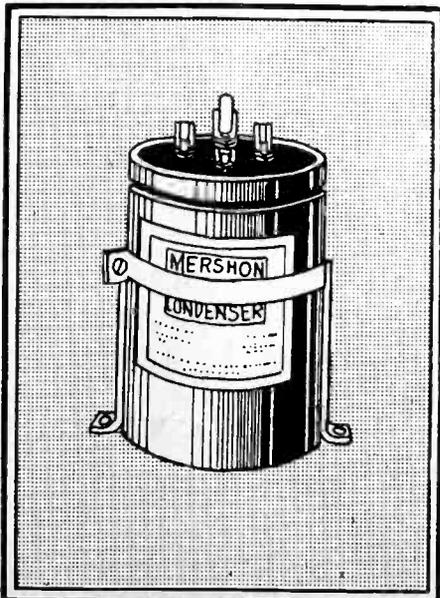

The Mershon electrolytic condenser, 415 volts DC, for filtering circuits of B supplies. Q 2-8, 2-18 has four capacities in one copper casing: two of 8 mfd. and two of 18 mfd. The copper case is negative. The smaller capacities are nearer the edge of the case. The vent cap should not be disturbed, and the electrolyte needs no refilling or replacement.


Mershon electrolytic condensers are instantly self-healing. Momentary voltages as high as 1,000 volts will cause no particular harm to the condenser unless the current is high enough to cause heating, or the high voltage is applied constantly over a long period.

High capacity is valuable especially for the last condenser of a filter section, and in by-passing, from intermediate B+ to ground or C+ to C-, for enabling a good audio amplifier to deliver true reproduction of low notes. Suitably large capacities also stop motor-boating.

Recent improvements in Mershons have reduced the leakage current to only 1.5 to 2 mils total per 10 mfd. at 300 volts, and less at lower voltages. This indicates a life of 20 years or more, barring heavy abuse.

In B supplies Mershons are always used "after" the rectifier tube or tubes, hence where the current is direct. They cannot be used on alternating current.

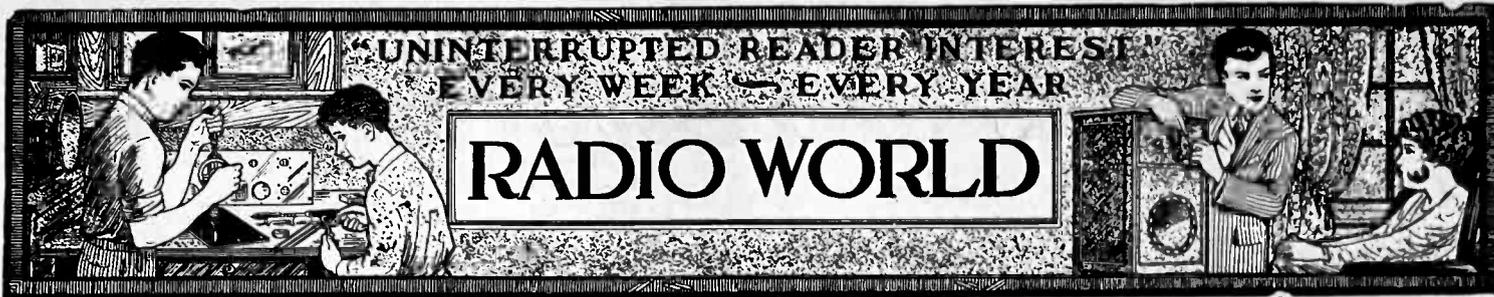The Mershon comes supplied with special mounting bracket. Order **\$5.15** Q 2-8, 2-18 B @



Vol. XVI, No. 14 Whole No. 404
 December 21st, 1929
 15c per Copy, \$6.00 per Year
 [Entered as second-class matter, March, 1922, at the Post Office at New York, N. Y., under act of March, 1879.]

Technical Accuracy Second to None
 Latest Circuits and News
EIGHTH YEAR

A Weekly Paper published by Hennessy Radio Publications Corporation, from Publication Office, 145 West 45th Street, New York, N. Y. (Just East of Broadway) Telephone. BRyant 0538 and 0559

RADIO WORLD, owned and published by Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y. Roland Burke Hennessy, president and treasurer, 145 West 45th Street, New York, N. Y.; M. B. Hennessy, vice-president, 145 West 45th Street, New York, N. Y.; Herman Bernard, secretary, 145 West 45th Street, New York, N. Y. Roland Burke Hennessy, editor; Herman Bernard, business manager and managing editor; J. E. Anderson, technical editor.

Sound You Can't Hear

Transmission of Superaudible Waves for Signalling

By *J. E. Anderson*

Technical Editor

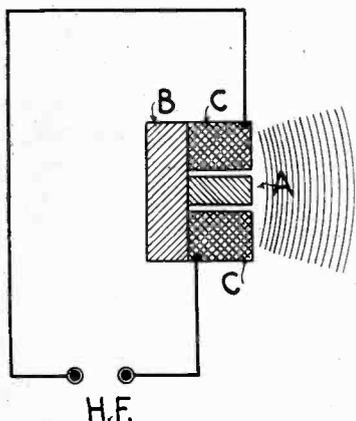


FIG. 1
 CROSS SECTION OF A SUGGESTED MAGNETOSTRICTION GENERATOR OF HIGH FREQUENCY SOUND WAVES.

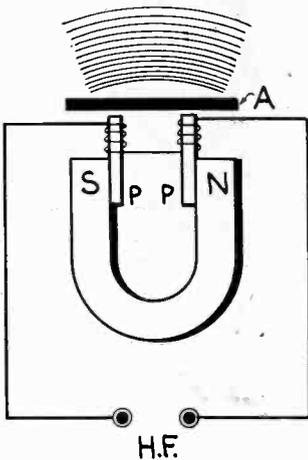


FIG. 2
 HIGH FREQUENCY SOUND WAVES CAN ALSO BE GENERATED BY MEANS OF A DEVICE OPERATING ON THE HEADSET PRINCIPLE.

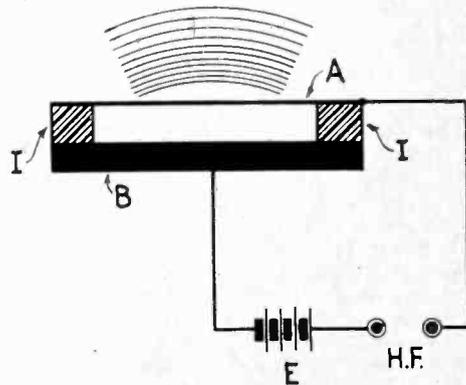


FIG. 3
 A TINY CONDENSER TYPE SPEAKER CAN BE USED FOR GENERATING SUPERAUDIBLE SOUND WAVES.

It is certain that in the future there will be a great deal of interest in supraaudible sound vibrations and that innumerable uses will be found for them in communication. We discussed this subject briefly last week, indicating in what manner they could be made audible after transmission and also suggesting how they might be produced. We shall now give additional suggestions on the subject, particularly with regard to their transmission and generation.

It must be remembered that the art of transmitting intelligence by means of supraaudible sound vibrations is still in the experimental stage and that it is impossible at this time to be as specific as when dealing with a developed art like broadcasting or the transmission and reception of radio waves.

The science of acoustics has lain practically dormant for thirty years. Just a few years ago there was practically no interest in the subject in physical laboratories. Very few scientific papers appeared in the technical journals throughout the world and the subject was treated lightly in the schools. Most attention was given to mechanics, electricity and magnetism.

BROADCASTING REVIVES ACOUSTICS

It was not until broadcasting was established that the subject of acoustics was revived. Talking pictures gave the subject an additional impetus and a tremendous one. At this time there is, perhaps, no other subject in physical science in which there is a greater interest and more rapid development.

At first the interest was mainly in the reproduction of audible sounds with the object of getting tone realism. This led to work on the acoustic properties of rooms and auditoriums to prevent echoes. Improvements have been made in every phase of the subject, but nearly all this work has dealt with sounds of audible frequencies. Very little has been done in the supraaudible region.

During the war sound waves in water were made use of to a considerable extent both for communication and for the detection of the presence of enemy submarines. Superaudible sound waves have also been made use of in sounding the depths of the ocean. Of course, these applications of sound waves in water are not limited to supraaudible frequencies but include audible sounds as well.

Sounding of the ocean is based on the known rate of travel of sound in water. A ship generates a sound of some kind under water. This sound may be a type of explosion or it may be a continuous sound. The sound transmitted from the ship travels down to the bottom of the ocean where it is reflected back to the ship. If the time it takes the sound to make the round trip is measured accurately the depth can be computed from the known velocity of sound in water and the time measured. If the velocity of sound in water is V , the time of a round trip is T , then the depth D is given by the formula $D=TV/2$.

CONTINUOUS WAVE METHOD

This applies to the case when an explosive sound is transmitted. If a continuous sound is transmitted the procedure is different. The transmitted and the reflected sound waves form a standing wave pattern with alternate loops and nodes. The distance between two adjacent nodes is one half wavelength. If the number of these half wavelengths and the length of each one are known the distance to the bottom is known. In order to make the distance an integral multiple of half wavelengths it is necessary to vary the frequency of the sound transmitted until there is a pressure node at the ship or at the transmitter. The bottom is always a pressure node.

The frequency of the sound when this condition is established is readily determined from the calibration of the oscillator. It remains to determine the number of half wavelengths between

Ear as Detector of Modul

Speaking Arc Transmits Signal at

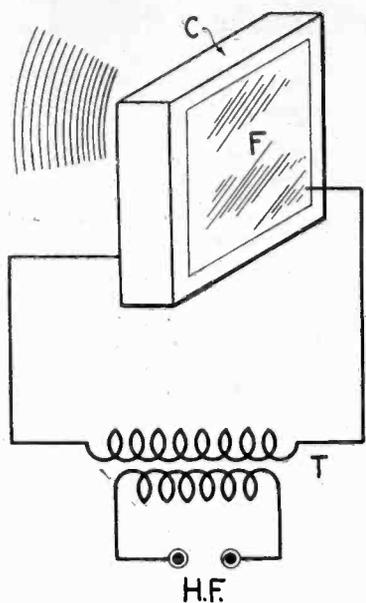


FIG. 4

THE PIEZO OSCILLATOR, OR SPEAKER, IS ONE CONVENIENT DEVICE FOR GENERATING SUPER-AUDIBLE SOUND WAVES.


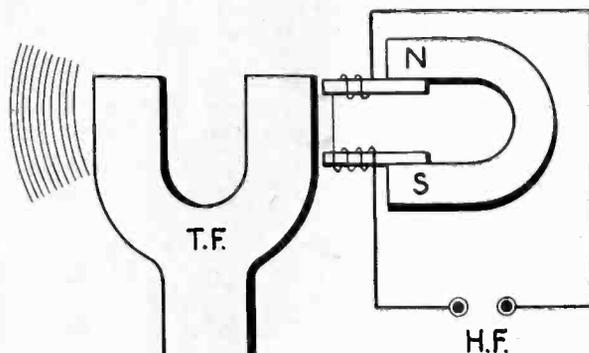


FIG. 5

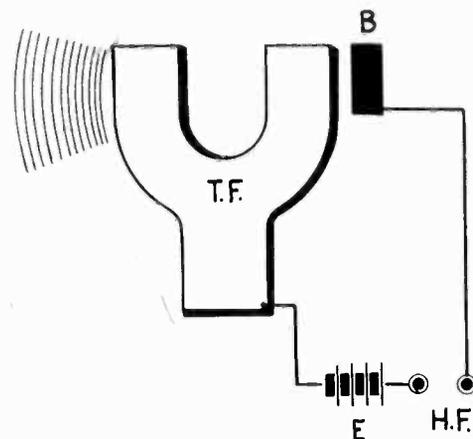A TUNING FORK CAN BE CONSTRUCTED SO THAT ITS NATURAL FREQUENCY FALLS ABOVE THE AUDIBLE LIMIT.



HIGH FREQUENCY TUNING FORK DRIVEN BY ELECTRIC ATTRACTION ON THE PRINCIPLE OF THE CONDENSER SPEAKER.

the bottom and the surface. This can be determined if the approximate depth is known or by means of another measurement. For example, the explosion method might give an approximate value of the depth and the continuous method a more accurate value.

In order to detect the reflected wave as it arrives to the surface it is necessary to have a sensitive sound detector, which may be a specially constructed microphone. If the depth of the water is considerable the reflected wave will be weak and a sensitive detecting device becomes necessary.

The detection of the presence of submarine is based on the fact that the submarine vibrates and sends out sound vibrations in the water. The vibrations may come from the hull or from the propeller. A sensitive water microphone attached to the detecting ship can pick up these vibrations. If there is one of these microphones on each side of the ship the direction of the submarine craft can be determined on the same principle as the direction of a radio station is determined or by the principle on which a human being can determine the source of a sound, that is, the binaural method of hearing.

GENERATORS OF SOUND

There are many different types of high frequency sound generators. Some are suitable for very high frequencies while others are suitable for audio frequencies and those frequencies just above the audible range.

In Fig. 1 is shown a cross section of a possible magnetostriction generator. B is a heavy metal plate very securely lodged in some support. A is a short length of magnetostrictive material such as monel metal, and CC is a coil of wire surrounding this rod, but not touching it. The rod may be attached to the plate B by means of a large machine screw.

The rod A has a certain natural frequency of vibration lengthwise. If an electric current having a frequency equal to this natural frequency of vibration be impressed at the terminals H F and thus sent through the coil CC the rod will be set into vibration at its natural frequency. The more nearly the frequency of the current is equal to the natural frequency of the rod, and the greater the driving current, the more vigorous will be the lengthwise vibration of the rod be.

The frequency of the rod is determined by its mass, by its length, and by the elastic constants of the material. The rod will vibrate in a quarter wavelength because it is free at one end and rigid at the other. There is a motion loop at the free end and a motion node at the fixed end. The necessary constants for determining the frequency are known for all magnetostrictive materials so that a length which will give any desired frequency can be calculated.

The rod will also respond to current having harmonic frequencies of the fundamental natural frequency. The condition is that the frequency is such as to drive the rod in odd multiples of a quarter wavelength. Thus a rod which has a fundamental in the audible length can be driven at superaudible frequencies.

Since the free end of the rod moves to and fro sound waves

will be generated in the air just as if the surface of the end were a diaphragm of a loudspeaker.

HEADSET GENERATOR

An ordinary headset can also be used as high frequency generator. As is well known when a heterodyne frequency is impressed on a headset and the frequency is increased, the sound can be heard up to the limit of audibility, somewhere between 10,000 and 20,000 cycles per second. As the pitch of the sound increases a time will come when nothing is heard because the sound is too feeble. However, if the headset is moved slightly to or from the ear the sound will be heard again. This is due to resonance in the air cavity between the diaphragm and the ear drum, which increases the intensity manifold.

When the sound ceases because its pitch passes beyond audibility it does not cease in the air, although it gets less and less intense due to the fact that the headset diaphragm cannot follow the rapid vibrations. In order to increase the intensity it is necessary to tune the diaphragm to the high frequency. To tune it it is necessary to make the diaphragm stiffer and at the same time, if possible, lighter in weight. The principle of the headset generator is shown in Fig. 2.

This method of generating high frequency sound waves is limited by the fact that the electromagnet ceases to be effective at the higher frequencies and also by the fact that the capacity across the armature winding will by-pass the high frequency driving current. Sometimes it is possible to tune the winding.

VIBRATING PLATE

It is not necessary that A in Fig. 2 be a round diaphragm such as those used in headsets. It may be a steel plate or a steel bar of suitable length and thickness, rigidly mounted in two supports. Or it may be rigidly mounted at one end and free at the other, but in that case the bar must be shorter for a given frequency of vibration.

Another method of generating high frequency sound waves is based on the principle of the condenser speaker. This is illustrated in Fig. 3. A is a light and rigid diaphragm or plate or bar of metal separated from another fixed plate B by insulators II. This condenser is polarized by means of a battery E and driven by a high frequency current impressed at H F. If the frequency of the driving current is equal to the natural frequency of the armature A the armature will vibrate vigorously and send out sound waves.

Instead of using a metal plate for A it may be made of glass or quartz covered with tin foil. The attraction will be between the plate B and the tin foil, but since the tin foil is attached to the non-conducting plate this will vibrate. A higher frequency is possible with the quartz or glass than with a steel plate. This condenser generator is not limited to the extent of the magnetically driven armature in Fig. 2.

A practical suggestion for the construction of this device may not be amiss. Let B be a circular plate ground plane on the side toward the armature plate. In the center of the plate turn

ated Superaudible Waves

Lower Than Radio Frequencies

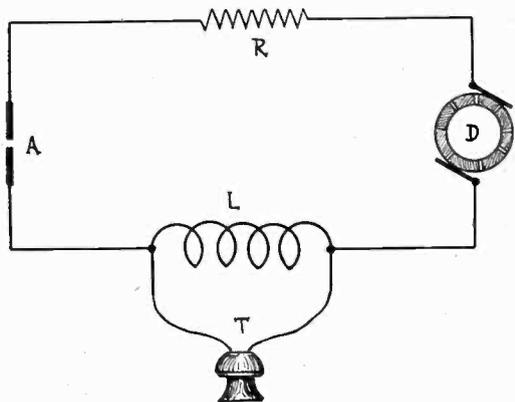


FIG. 7

THE SPEAKING ARC IS ONE OF THE OLDEST AND BEST KNOWN LOUDSPEAKERS. IT WORKS AT HIGH FREQUENCIES AS WELL AS AT LOW.

out a shallow recess a few thousandths inch deep. A flat-ground ring is thus left around the periphery of the plate. On this place a glass disc and clamp it on the metal plate. Cement a circular piece of tin foil in the center of the glass away from the metal plate. The glass, which should be thin, will serve as insulator and the member II becomes a part of the fixed plate.

PIEZO OSCILLATOR

Fig. 4 shows the principle of a piezo oscillator. C is the crystal cut in the form of a parallelepiped and covered on both sides with tin foil. The driving force is impressed across the plate by connecting the secondary of a transformer to the two pieces of tin foil. This plate has many natural periods of vibration as it can vibrate in all three of its dimensions as well as in harmonics of these modes of vibration.

The piezo crystal may be had in both Rochelle salt and in quartz. Rochelle salt is more piezo-active than quartz and can be obtained in larger pieces. Quartz is more readily available because it is used in frequency standards for radio transmitters. Quartz is also more suitable for the higher frequencies.

Several watts of power can be put into a tiny quartz crystal and a large part of this power can be radiated as high frequency sound.

TUNING FORK OSCILLATORS

Some of the oldest tone generators are tuning forks. These come in all frequencies from the lowest audible to the highest. But since they are mostly used for pitch determination in music they are usually in the musical range.

A tuning fork essentially is a bar of steel supported at its center. The fact that a fork is bent into the shape of a U does not materially alter the principle. Each prong is a quarter wavelength since it is free at one end and fixed at the other. Due to the construction it is uncertain just where the effective fixed end is and the effective end of one prong does not coincide with that of the other. When the form vibrates the two free ends always move in opposite directions, either away from or toward each other.

A tuning fork can be maintained in continuous vibration by electrical means and two methods are illustrated in Figs. 5 and 6. In Fig. 5 it is driven by an electromagnet, which may well be a headset unit, and in Fig. 6 it is driven by electric force in the same manner as a condenser speaker.


In either case the fork must be mounted rigidly. So must the driving member whether it be the headset unit or the electrically charged plate B in Fig. 6. As in the case of Fig. 3, the plate B must be insulated from the armature, the fork, and a polarizing voltage E must be impressed between the two.

Fig. 6 is more suitable for high frequency operation since it is not limited by the electromagnet nor by the capacity of the winding.

HARMONICS OF FORKS

Each fork has a given natural frequency of vibration. When the driving current or electric force has exactly this frequency the fork will vibrate with a large amplitude, and relatively little force is needed to maintain the vibration. If the driving frequency differs but slightly from the natural frequency of the fork, the amplitude will be extremely small.

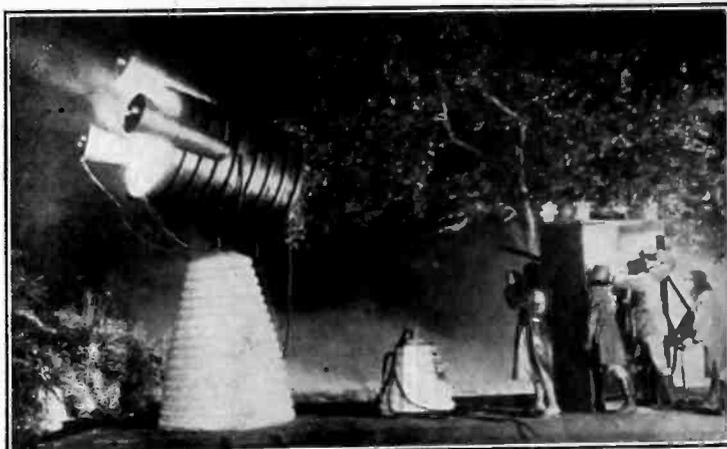A tuning fork has harmonics or higher natural frequencies of vibration, but these frequencies are not simple harmonic. That is, they do not bear an integral relationship with the fundamental frequency. For example, the second natural frequency is about 5.5 times the fundamental frequency instead of twice the fundamental.



(Underwood & Underwood)

SOUND WAVES OF EXTREMELY SHORT WAVES CAN BE TRANSMITTED IN A SHARP BEAM LIKE LIGHT WAVES BY A DEVICE SIMILAR TO THE ONE ILLUSTRATED HERE, WHICH SENT OUT "DEATH RAYS."

If a tuning fork is to vibrate at a very high frequency its prongs must be short and stubby. That is, the weight of the prongs must be concentrated near the base and the fork must be quite rigid.

THE SPEAKING ARC

The speaking arc is another sound generator which is not limited in frequency range. A simple circuit diagram of such an arc is shown in Fig. 7. A is a carbon electrode arc such as is used for illumination. A 200 volt direct current generator D supplies the necessary current to operate the arc and a resistance R is put in the circuit to control the current. A current of about 10 amperes is suitable. The distance between the two carbon electrodes should be several centimeters (1 inch equals 2.54 cm.). A large inductance L of low resistance is put in series with the circuit and across the coil is impressed the signal. T may be an ordinary microphone. If this is spoken into the voice will come out of the arc with remarkable fidelity.

Instead of speaking directly into the transmitter T the output of an audio amplifier may be connected across the coil L, and the signal may originally be derived from a pick-up unit and a phonograph or from a microphone.

If it is desired to transmit superaudible frequency sounds by means of the arc coil L should have a lower inductance, and particularly a lower distributed capacity, and the output of a vacuum tube oscillator operating at a superaudible frequency should be impressed across it. Of course, it is not necessary to use direct coupling between the source of the oscillation and the coil, but L may well be the secondary of a transformer, provided the transformer is such that the heavy current can flow through the secondary without serious complications.

MODULATED HF SOUND

If the high frequency current driving any of the devices in Figs. 1 to 7 is modulated by an audible frequency current the sound emitted by the sound generator will also be modulated. If a suitable detector for this modulated sound can be found it would be possible to transmit intelligence by carrier sound waves just as broadcasting is now conducted by carrier radio waves. As was explained last week, the ear detects modulated superaudible waves, so that the modulated sound waves should be audible without the aid of any mechanical or electrical devices whatsoever.

Condenser Leaks

THE ELECTROLYTIC condenser in my power pack passes a good deal of current, or at least it seems that way to me. I connect a milliammeter between the case of the condenser and the B minus side of the rectifier, and there is a deflection. It is not the same all the time but depends on how many of the sections of the condenser I use. Is this a characteristic of the condenser or is it a defect in mine only?—A. B. S.

If the current is not more than a few milliamperes it is a characteristic of the condenser as some current always flows through it, and of course, the current that does flow depends directly on the capacity you use, or on the number of sections in use. The amount of current that flows depends on the amount of impurities in the active metal electrode. A current of a few milliamperes does no harm for it simply adds a little to the bleeder current in the rectifier.

Constructional Helps to Bu

Separately Shielded Cascade Used in

By Herman

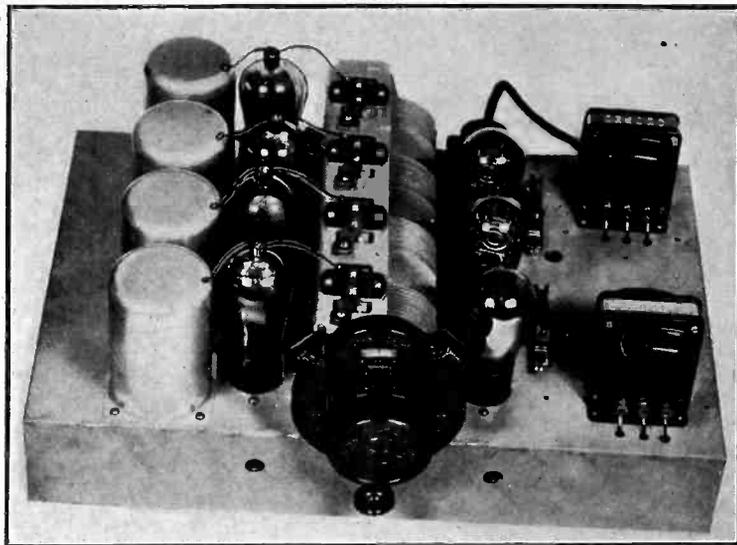


FIG. 1
TOP VIEW OF THE HB33 TAKEN FROM THE FRONT.

[Herewith are published constructional data on the HB33 and HB44. The 33 is for battery operation of filaments. The 44 is for AC. Both use three stages of screen grid tuned RF, individually shielded, and shielded input to the screen grid detector. The first audio stage is resistance coupled. The second is push-pull transformer coupled. In the 33 the output tubes are 112A, in the 44 they are 245s. Next week, it is expected, the picture diagram of the wiring of the 33 will be ready for publication.—Editor]

TWO ultra-sensitive companion circuits, the HB 33 for battery operation of filaments and optional use of B batteries or a B eliminator for plate supply, and the HB44, completely AC operated, use the same subpanel. Viewing the steel subpanel from the front, the shielded coils are at left, the sockets next, and the tuning condenser, a four-gang device, at center. This arrangement prevails also for the AC model.

The only difference is in the type of sockets used, the UX sockets being supplied for battery-operated model, the UY sockets for the other. These are the four sockets representing the three stages of screen grid radio frequency amplification and the screen grid detector. You yourself affix the sockets by means of 6/32 machine screws and nuts.

MOUNT CONDENSER FIRST

The first thing to mount on the subpanel is the four-gang condenser. The subpanel has holes drilled in it for this purpose, so no brackets are necessary. The holes are of two types: small ones and large ones. The small ones are for passing screws that one removes from the rotor or frame connection of the condenser. If the condenser is mounted on one side, the trimming condensers will be on

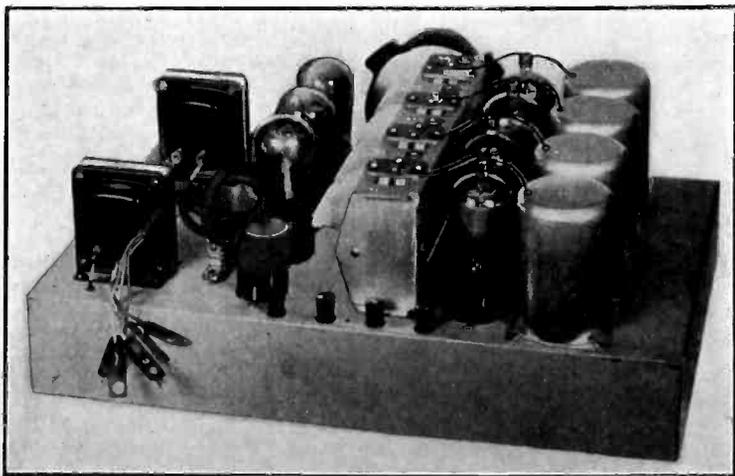


FIG. 2
REAR VIEW OF THE HB33. NOTE THE CABLE PLUG INSERTED IN SOCKET AT LEFT, ALSO THE TAGGED BATTERY ENDS OF THE CABLE.

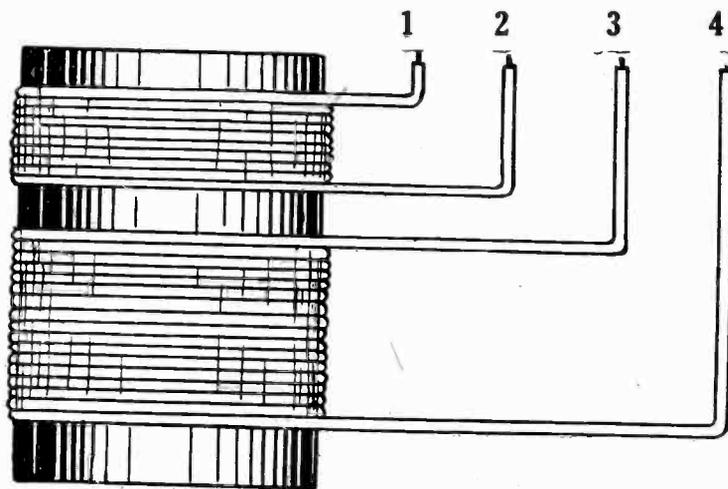


FIG. 3
HOW TO CONNECT THE COILS FOR MAINTAINING CORRECT POLARITY IN THE INTEREST OF STABILITY OF THE TUNER. THIS POLARITY IS TO BE OBSERVED FOR THE HB33 AND THE HB44, WHICH USE THE SAME COILS.

top, easy of access. This is the only way the condenser can be mounted so that proper elevation will be preserved, in connection with the drilling in the cabinet, and proper safeguard made against short-circuiting. Between the condenser and the top of the subpanel at each of the eight points put two extended insulators, not for insulation but for elevation. $\frac{3}{4}$ " No. 6/32 machine screws must replace those removed from the condenser.

The large holes simply pass the heads of screws so that the grid connection to the stators will not be shorted to ground.

To make doubly sure of no continuity from grid to ground, remove the grid screws, also, and the lock washers used on them. Now put a flat insulating washer between the condenser and the lock washer, so that when you tighten down, the washer is in full view. These washers are a part of the condenser assembly.

Having finished this work of mounting, test for short circuits. Connect the pilot lamp furnished with the parts, and which is to be used for dial illumination, across a $1\frac{1}{2}$ volt dry cell, to make sure it lights. Even if a 6 volt lamp is used, $1\frac{1}{2}$ volts will give an indication. Of course higher voltage than $1\frac{1}{2}$ may be used, if desired.

Now attach an insulated wire lead to one side of the pilot lamp bracket, and connect the lead to one side of the test cell, baring free end. Connect a wire lead from the other pole of the cell, with free end bared. Continuity will show up by illumination. If the two leads are connected between stator and rotor of each of the four sections at a time, no light should appear. If there is illumination, trace down and cure the short. When no light appears anywhere in the four places proceed with the rest of the assembly.

SOCKETS GO ON NEXT

Mount the four sockets in place at left. For the HB33 these are four UX or four-spring sockets. Mount with filament holes at rear. For the HB44, the AC model, place sockets with cathodes pointing toward front, all four sockets in the same relative position. This brings the plate at right, nearest in both models to the coil to which it will be connected ultimately.

In the HB33 the filaments of the three other sockets are placed toward the front panel. Notice this differs from the position of the sockets used in the tuner.

In the HB33 the eighth socket hole houses an AC socket of the UY or five-spring type, because a cable is plugged in, for battery connections. There are only five leads to the cable, taking care of (1) common A minus, B minus and C plus; (2), A plus; (3), B plus 22 to 45; (4), C minus $4\frac{1}{2}$ and (5), C minus 9. The other lead, B plus 135 volts, is taken through a separate insulated wire lead from the midtap of the output transformer primary. Tie a knot above the subpanel so that any strain placed on this lead will be taken up by the knot instead of by the connection at the transformer post.

The two audio resistor mountings may be placed between the two audi transformers or in line next to the sockets, as shown in Fig. 1, above. The placement makes no difference. In the HB44 the resistors have to be mounted as shown in the photographs, because the other room is taken up by power apparatus.

The holes are provided for the audio transformers to be mounted on top in the HB33. In the HB44 the center-tapped output im-

Builders of HB 33 and HB 44

Tuner, With High Gain on All Waves

Bernard

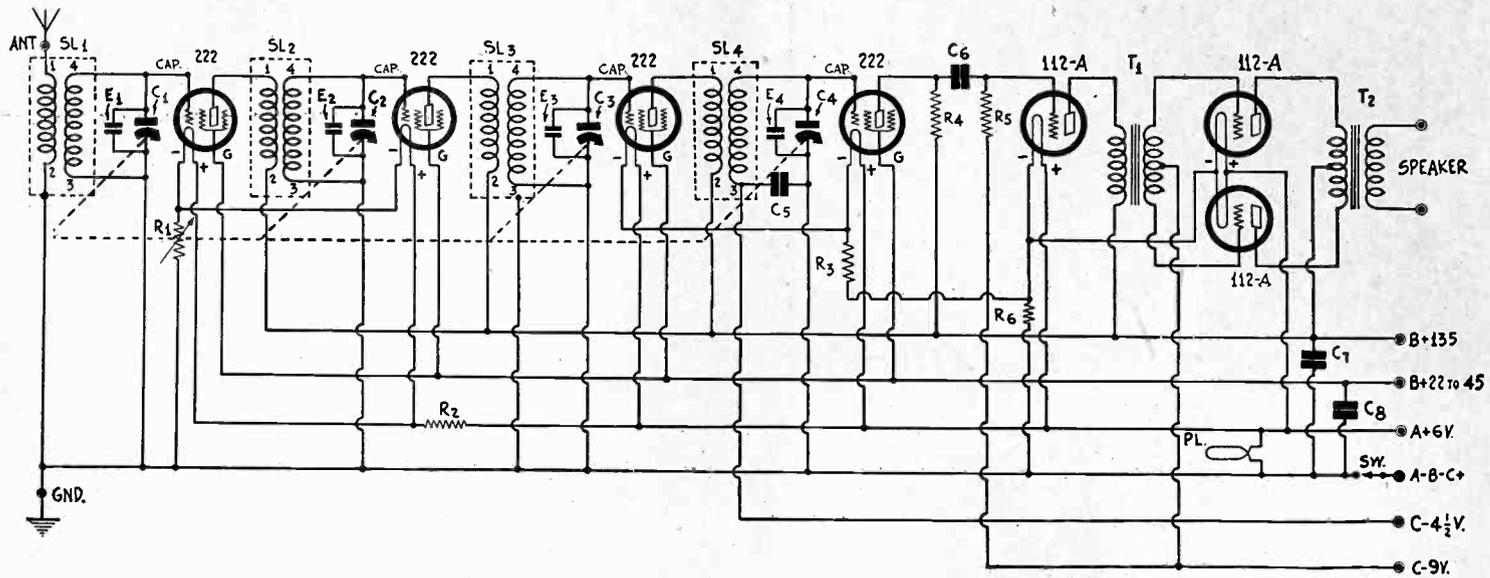


FIG. 4
CIRCUIT DIAGRAM OF THE HB33, A HIGHLY SENSITIVE SCREEN GRID RECEIVER, ECONOMICAL IN A BATTERY POWER CONSUMPTION, AND WORKABLE ON B BATTERIES OR B ELIMINATOR. THE DETECTOR BIAS SHOULD BE SUBJECTED ON EXPERIMENT, AND A SMALL CONDENSER TRIED FROM DETECTOR PLATE TO GROUND, AS EXPLAINED IN THE TEXT.

pedance is mounted on top, but the filter choke is mounted on bottom, as will be related more fully.

Now mount the coils. These have small toed-in brackets, and holes in the subpanel coincide with the holes in the brackets. Use 6/32 machine screws and nuts. In mounting the coils notice that the primary is on top and the secondary on bottom, and that the primary lugs come out on one side and the secondary lugs on the other. The same relative polarities of the connections is preserved as stated in a previous article, but the position of the primary on top may confuse some, so Fig. 3 is printed herewith to clarify this point.

Mount the coils so that the secondary connection lugs are toward the tuning condenser, hence the primary lugs are toward the left. You will find the outer (lower) terminal of the secondary at right, toward the front, the grid return at right toward the rear of the subpanel, the aerial or plate connection of the primary at left front and the ground or B plus connection at left rear. The distinction is made between aerial and plate, ground and B plus because the aerial coil has its primary going to antenna and ground, while the three other coils have primary going to plate and B plus.

The shields should not be put on until all the wiring has been completed. The reason is that you will handle the subpanel assembly considerably, and under certain circumstances may be tempted to use the shields for support. The coils are not high enough to be endangered by this.

Immediately the coils are in place the leads from them to the sockets may be wired. Be sure that the antenna binding post is insulated from the subpanel. A flat type insulator should be placed

between the binding post head and the subpanel, another flat type underneath, and then a collar type insulator underneath, if the type of binding post is used that is intended for mounting on bakelite. The other type, for metal subpanels, needs either a small metal washer or a couple of flat type insulators between the head and the subpanel, to take up a little free room, so that the nut underneath will bite the collar at bottom.

SUBPANEL GROUNDED A MINUS

In wiring from plates of three tubes to coils and plate of the detector tube to the plate resistor, be sure to make the proper connections. The subpanel will be worked from the bottom, and the socket springs are not marked. When you view the socket from top for the battery model, for instance, the filament holes will be at rear in the RF channel, hence the plate will be at left. If you turn the subpanel upside down in such manner as to cause the front to be at the rear, the same right-and-left relationship holds. Otherwise you would reverse the relative positions and might get mixed up. Also remember that the G post goes to the B plus 22 to 45 volts, and is the screen grid, not the familiar control grid as in other tubes. The control grid in this instance is the cap of the tube.

In mounting the ground post, connect it to contact with subpanel without insulation, as the subpanel is then used as grounded A minus and may be picked up at any point for that purpose. Run the A— cable plug lead to ground post for this purpose. Then filament resistors too may go directly to subpanel.

The diagram of the HB33 should be followed as shown with two possible exceptions. One is that a fixed condenser from plate of the detector tube to ground sometimes improves detecting action, which is true if not enough inherent capacity exists from plate to filament in the tube, but if there is enough then the extra condenser is not to be used. In any instance the condenser should not be of more than .001 mfd., and it is preferable to use about .0005 mfd. Any fixed mica condenser from .0001 to .0005 mfd. will serve the purpose.

The second point is that the bias on the detector tube, marked minus 4 1/2 volts, may have to be changed somewhat, particularly in an upward direction. When grid bias detection is used, especially in a battery model receiver, sometimes the constructor wires everything "exactly according to the diagram" and yet receives no signals.

REASON FOR NO SIGNALS

The reason is, most likely, that the proposed detector tube is getting a bias that provides amplification instead of detection. This bias may be critical with some 222 tubes, and if so, put a potentiometer of 25,000 ohms or more resistance across 12 volts of C bias, or across a greater voltage, and connect grid return to the arm. Then move the arm until best detection is produced. Measure the voltage between the arm and negative filament. Then provide the necessary bias as follows: allow 2.7 volts dropped in the filament resistors R6 and R3, subtracting this from the reading obtained, and provide the difference through the external bias battery.

In wiring the cable, regard the five-prong socket with heater (large holes) toward you. This brings the grid at center rear, with cathode at left and plate at right. These words are used merely

LIST OF PARTS

- SL1, SL2, SL3, SL4—Four stage individually shielded coil cascade for .00035 mfd. (Cat. SH-3 of Screen Grid Coil Co.)
- C1, C2, C3, C4—Four gang .00035 mfd. condenser with equalizers E1, E2, E3, E4.
- C5, C6—Two .01 mfd. mica fixed condenser.
- C7, C8—Two 1.0 mfd. bypass condensers 200 volt DC working voltage.
- R1, Sw—30-ohm rheostat with switch, knob, insulators.
- R2, R3—Two 6.5-ohm fixed filament resistors.
- R4—One .05 meg. Lynch metallized resistor.
- R5—One 5.0 meg. Lynch metallized resistor.
- R6—One 1-ohm fixed filament resistor.
- T1—One push-pull input transformer.
- T2—One push-pull output transformer.
- PL—Pilot lamp and bracket.
- Ant., Gnd. Speaker—Four binding posts.
- One drilled steel cabinet, brown crinkle finish.
- One vernier full-vision dial.
- One flanged subpanel with seven UX sockets and one UY socket.
- Four grid clips.
- One 5-lead connector cable.

Sensitivity Increased With H

Independent Bias Resistor Used for

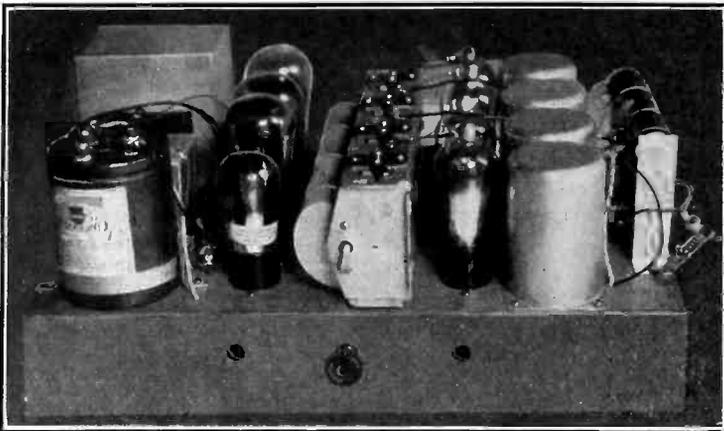


FIG. 5

HERE IS WHAT IS ALMOST AN ACCURATE FRONT VIEW OF THE HB44. SEE IF YOU CAN DISCOVER WHAT'S WRONG. COMPARE WITH ILLUSTRATIONS ON NEXT PAGE.

(Continued from preceding page)

descriptively, as no cathode, grid or plate is concerned. The equivalent leads to the heater springs are A plus and A minus, and so marked, so use the left-hand heater spring as A minus, by connection to ground binding post, the right-hand as A plus. Then your cable is automatically marked correctly as to these. The other marks on the cable, at the battery connection end, are P, C and G. Use P for B plus 22 to 45, C as C minus $4\frac{1}{2}$ volts and G as C minus $9\frac{1}{2}$ volts. You may mark these terminals on the cable accordingly.

PLACEMENT OF SHIELDS

After all wiring, put on the shields. It is necessary to drill a $\frac{6}{32}$ hole on top of the shield to pass a lead to the cap of the tube and the stator connection of the tuning condenser. First solder this lead, which should be 8" long. It goes to the coil lug at right front, when you look at the top of the subpanel with dial toward you. All holes may be in the shields at center at the edge, where the shield curves at top, drilled midway between base dimension, except the shield for the detector, which should have its hole $\frac{1}{2}$ " off center, as it were, in the direction of the rear of the subpanel.

To attach the coils, take each one separately, hold it horizontally, at or near the bottom of the subpanel, and pass through it the lead that is to go to cap. Solder a grid clip where the lead passes the cap of the tube and solder the other end to the stator connection of the nearest section of the tuning condenser. It will be found the 8" lead is a little too long, but snip it down to size. Now mount the rheostat switch, insulating it with special insulators furnished with the parts, although insulation is only to avoid resort to a possibly poor automatic connection to A minus.

The circuit may be worked out of the cabinet for testing. Adjust the trimming condensers carefully, as previously described. (December 14th issue.)

You will find two extra holes on the front flap of the subpanel. These are at left and right. If desired you may put a trimming condenser of the variable type across the first and second tuned circuits and these holes make this possible. A little better sensitivity always results when this is done, although the convenience of strictly single tuning control without manipulated trimmers is preferred by most persons. The front panel trimming condensers need be of only small capacity, anything from 20 to 50 mfd.

RHEOSTAT HOLE

In putting the receiver in the cabinet it is well to provide for mounting brackets. Small brackets should be used, and so placed, two at each side, left and right, that the bracket is flush with the subpanel and cabinet bottom. Then the dial holes in the cabinet will coincide with the position of the parts.

However, it may be found in some instances that the hole for the rheostat does not coincide. Simply put the subpanel assembly in place in the cabinet and drill the subpanel flange through the hole that is in the cabinet. Use a $\frac{1}{4}$ " drill and widen the hole with a taper reamer.

To mount the subpanel inside the cabinet it is necessary to remove the shaft of the four gang condenser. The movable plates of the condenser are thus removed. This is easily done. Simply loosen the eight set-screws on the condenser rotors and pull out the shaft. Then put the assembly in the cabinet, put the washer in place, slide the rod through the cabinet hole, condenser front, and washer. First put the rotor with plates totally unmeshed, in any position, except that the cutout plates are toward the condenser frame, and slide the shaft through this section. Repeat this process, except for washer, in the three other instances, and tighten down. It will be

found that the rotors can be moved freely when the plates are totally out of mesh. Be sure that a rotor plate overlaps toward the front: Tighten down the setscrew at rear of condenser frame and the eight set-screws of the rotors. Then readjust the trimmers.

The pilot light bracket has two insulated wire leads. Knot these at the bracket to fasten to a screw that protrudes from the dial. The light will shine through two holes in the front of the cabinet called for convenience the front panel, although the cabinet front is a part of the cabinet itself.

Some may desire to wind their own coils for this circuit. Therefore they will desire to know the diameters and number of turns. Here are these data:

Diameter, $1\frac{3}{4}$ inches bakelite, outside diameter; height, 3".

Primary, 43 turns.

Secondary, 93 turns.

Size of wire, No. 29 enamelled.

These data do not coincide exactly with those for the commercial coils, the slight difference being accounted for by a difference in wire size, and not by a difference in performance.

These coils are for .00035 mfd. For .0005 mfd. use 80 turn secondaries.

SINCE the publication of the circuit diagram of the HB44, the super-sensitive AC receiver using three stages of tuned screen grid radio frequency amplification, screen grid detector, resistance coupled first audio and transformer coupled audio for push-pull output, reports have been received from builders of the circuit.

One man said that he had tuned in WHN from upper Manhattan, and that he was proud of the feat. It must be admitted that WHN, too, is in New York City, only about eight miles from where he lives. The point is that the immediate locality about his home is regarded as a dead spot so far as WHN is concerned, and that no one ever before had reported the reception of this station in the two square blocks which encompass the builder's home. So he was proud of the performance of the HB44 and immediately started building another as a Christmas present to his sister.

GOT PLENTY OF DISTANCE

He also submitted a list of distant stations so long as to be tiresome even to the designer of the circuit, particularly as these stations had been tuned in by the designer from his home in another part of the city as far back as last September.

Considerable experimental work was done on the HB44, hence it is an outperformer. Even now it is suggested that some slight changes be made from the design originally published, these changes being embodied in the schematic diagram published herewith. They reduce even the small hum originally present and increase the sensitivity, a strange but welcome combination. Usually when sensitivity rises, the hum increases.

The filter has been changed to incorporate the double choke that was originally used as the output device, as this is a husky unit and well suited to the purpose. The output device now becomes a smaller centertapped choke. The detector bias is obtained through an independent resistor, instead of from the voltage divider, as this reduced even the small hum originally present and heightened sensitivity. The grid return of the radio frequency tubes is somewhat critical, and to take care of this a Clarostat Humdinger, of 30 ohms, is used in series with the low end of the voltage divider. Then one end of the Clarostat resistor goes to grounded B minus and the other end to the first lug of the voltage divider. The lugs on the voltage divider may be considered to be in the order of their profusion, so you begin counting from that section where the lugs are numerous, and find that there are fifteen, of which fourteen are useful, two being interconnected, because the voltage divider consists of two series resistors.

BIAS FROM 2.7 VOLTS DOWN

The cathode connection of the radio frequency tubes goes to the midtap of the Humdinger, and this midtap is adjustable by a screwdriver, so adjust it for greatest sensitivity and leave it that way.


As about 90 milliamperes flow through this resistor you may obtain a total drop of 2.7 volts, but will find greatest sensitivity below 2 volts. There is no occasion for determining the bias voltage, as the sensitivity test, determined by listening for loudest response, is entirely sufficient.

When the circuit is built as shown it is truly remarkable. It is good indeed when built either way, as the changes are not revolutionary in any sense. Some may ask if the circuit is in its final form now, and the answer must be, let's hope not. The same layout and parts will be used, but if any improvements ever can be discovered, facts about them certainly will be published. When the day comes to say a circuit is final then the last incentive to improvement has disappeared, or the declarant is a hopeless egotist.

In connection with the change in the filter section, the capacities used necessarily had to be apportioned to other positions. So now we find that simply a 1 mfd. high voltage condenser, 1,000 volts DC continuous duty rating, 550 volts AC rating, is next to the rectifier.

um Reduction in the HB 44

Detector Stage, With Adjustable RF Bias

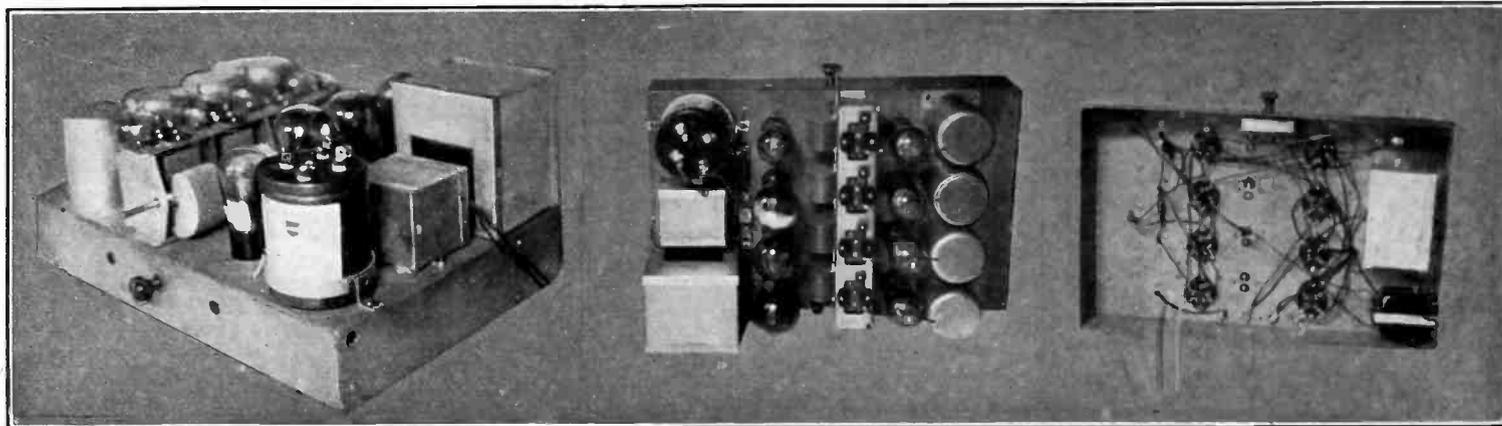

FIGS. 6, 7 AND 8

AN EXPERIMENTAL SET-UP OF THE HB44, AT LEFT, FIG. 6, IS AN ANGULAR VIEW. THE TUNING GANG CONDENSER IS MOUNTED DIRECTLY ON THE SUBPANEL. FIG. 7, CENTER, IS A TOP VIEW, AND FIG. 8 A BOTTOM VIEW. NOTE WHERE THE PUSH-PULL INPUT TRANSFORMER IS MOUNTED.

Then at the midsection of the double choke comes an 18 mfd. section of the Mershon electrolytic condenser, while at the end of the choke chain comes the other 18 mfd. section, leaving two 8 mfd. sections, one to bypass the approximately 180-volt lead, the other to bypass the biasing section for the push-pull 245 power tubes. The other bypass condensers are 1 mfd. each, low voltage rating (200 volts DC continuous duty). The only difference between a filter condenser and a bypass condenser is that the word filter is used generally where the voltage rating is high and by-pass when it is low.

EXTRAORDINARY RESULTS

Fig. 9 shows the circuit of the HB44, while Fig. 10 clarifies the connections to the voltage divider. This is a Multi-Tap Divider, and it will stand the strain without getting more than merely warm. It is a specially designed instrument for high current circuits. The present circuit uses high current, but as AC operation renders that very economical, there is no disadvantage. Even if the operating cost were high, which it is not, any possessor of this circuit would feel he was spending his money in a good cause, as the results are extraordinary.

One thing is absolutely essential if you are to have any success at all with this circuit. You must know how to use the Mershon condenser. It is rated at more than 400 volts DC continuous duty, and will stand it, so there is no danger in this circuit whatsoever. But if you are unaware that the copper can is negative, and make a wrong connection, you will run into trouble. The bracket is connected to the subpanel, and the subpanel itself is used as grounded B negative, and all grid returns made thereto, so the can must be negative. Unless you go to extraordinary pains to insulate the copper case, and perhaps use it as some positive connection, as one man tried to do, you will come out all right. Also note that there are different capacities, two eights and two eighteens. The smaller capacities are nearer the edge of the copper case. There is a difference and you can measure it with a ruler, if your eye deceives you.

The directions for mounting parts for the tuner have been stated in reference to the HB33, which is the battery-operated counterpart of the HB44, and these directions should be followed. At the left-hand side, between the shields and the edge of the subpanel, the voltage divider is to be placed. You will have to drill two holes $7\frac{1}{2}$ " apart to secure the brackets of the voltage divider to the subpanel, and a few more holes to pass leads through. These brackets are insulated from all potentials on the divider, and do not constitute an automatic connection of the end of the voltage divider to negative. Anyway, between the lowest lug of the Multi-Tap and the grounded subpanel the Humdinger is placed, and the connection to negative of the B supply is made in that way.

POWER APPARATUS

As for mounting the power apparatus, the Polo filament-plate supply is placed at right rear, and holes therefor being in the subpanel. It is well to use a couple of insulating washers or other devices, simply to keep the Polo block elevated so that air will circulate underneath, but the case of the block ought to be grounded, and this may be done by soldering to a lug on one of the screws protruding under the subpanel after the block has been mounted, and connecting to ground.

Next to the filament-plate supply comes the output impedance, as you work toward the front of the subpanel. At front is the Mershon. The audio resistor mountings are lined up between this power apparatus and the sockets at right, the space between the mountings

being just enough to enable connection of the specified .01 mfd. condenser. Be very careful to put three flat insulating washers between the mounting's hole and the subpanel, otherwise there might be a short, due to the lug hardware of the mounting being flush with the bottom of the mounting itself. This admonition applies to the HB33 as well as to the HB44.

Underneath, at the "power" end, are placed the audio push-pull input transformer and the double choke used in the filtration. There is a knack to mounting these parts.

ORDER OF MOUNTING

The order of procedure is as follows: First mount the double filter choke, which is the large double choke, underneath. This is oblong. Put it in position so that its length runs in a front-and-back direction. The subpanel holes will guide you. A strip of metal that is spot-welded to the case of this large double choke extends far enough to enable the holes in the strip to be used for mounting purposes, but before tightening down on the screws it is necessary to insert cardboard strips to take up any play. Then tighten as hard as you desire. The strips go on both sides of the mounting flap. Rigidity must be preserved, because otherwise any possibility of vibration might evidence itself in hum.

The head of one of the screws will be under where the Mershon will rest, but the plane is made uniform by putting other screws in similar position, to afford an even resting place for the Mershon, even though these screws will serve no other purpose.

However, it is not the Mershon that is mounted now, but the audio transformer. This goes on the side flange, and holes are provided in the subpanel. Only three of the holes are used, as the fourth is almost inaccessible, except to a very deft person, or one who has a lifetime to devote to such things. There is no need to make the fourth connection. It is advisable to have the secondary toward the flange, therefore connect insulated wire to the secondary so that the connections can be made easily, without resort to establishing contact to the binding posts after the audio transformer is mounted. Now you may put the output choke in place, flap left to right.

In any of the wiring, since the subpanel is grounded B negative, or C minus, depending on the viewpoint, you may want to make connections to screws already driven through subpanel holes. However, do not solder to screws. It is bad practice and a lazy method. Use a lug, tighten it fast, and solder to the lug. Then if ever you desire to remove the mounted part you may do so easily.

There is a large round hole near the power transformer where all necessary leads may be dropped underneath the subpanel, since virtually all the wiring is done underneath. The filament leads and high voltage leads and some others go through this $\frac{1}{2}$ " hole. For some other leads it is necessary to drill a few $\frac{6}{32}$ machine screw holes in the subpanel. Do not tap these holes.

A precaution that every one should take is to use wire that is well insulated. Steel when drilled or punched leaves a hard edge, as do nearly all metals used for subpanels, therefore the edge may cut into the insulation and cause a short. But if the insulation is strong this won't happen. The insulation on the leads coming out of the Polo filament-plate supply and double choke are strong enough for this safeguard, and see that any wire that you provide is at least as well insulated.

Mount the Mershon only after all the rest of the circuit is wired. Make the connections to the lugs on the Mershon.

GETS DX IN DAYTIME

The circuit, built exactly as diagrammed, has been working for several days in the laboratory, and has managed to do exceptional

Gets DX in Daytime

High Sensitivity Established in Stable Circuit

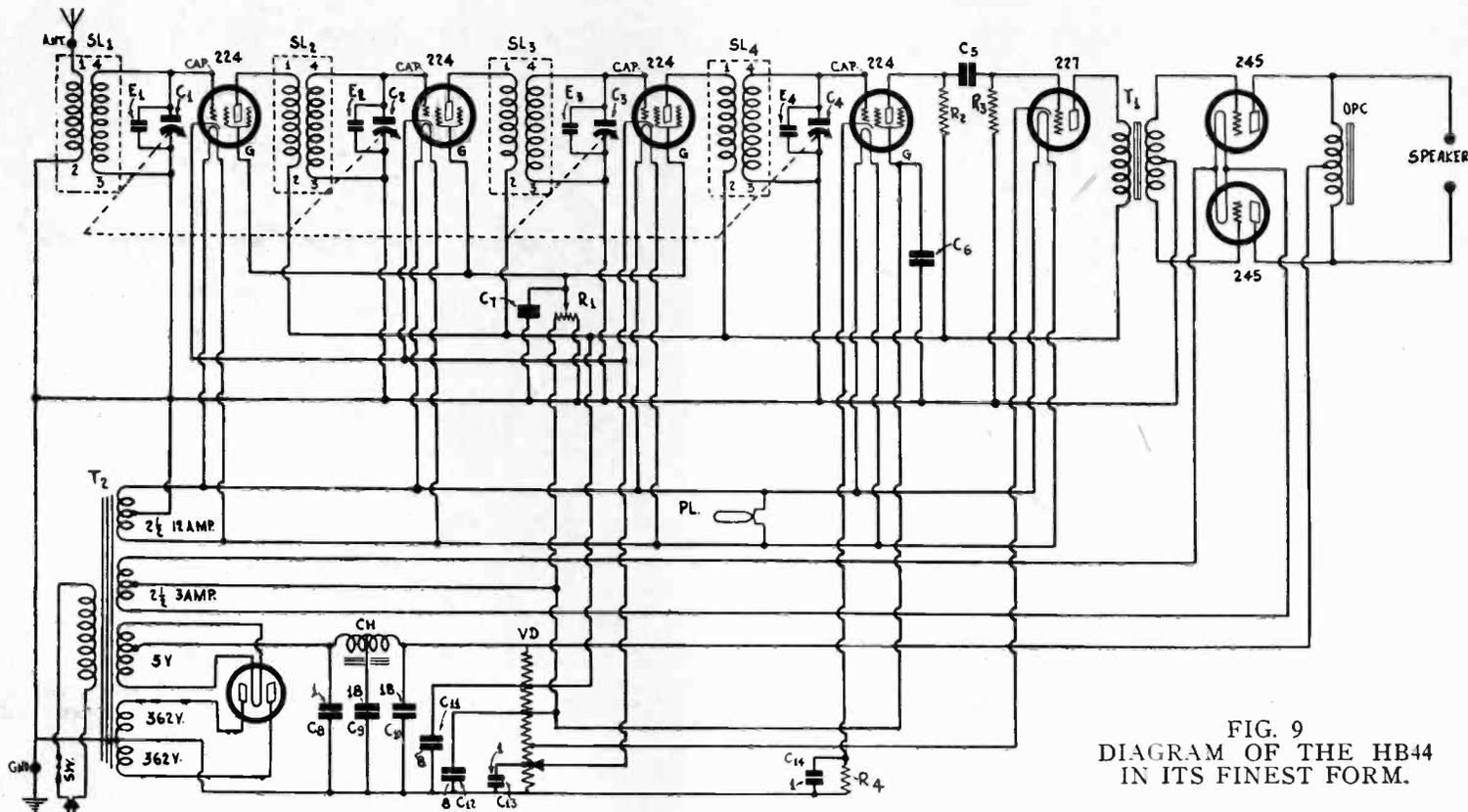


FIG. 9
DIAGRAM OF THE HB44
IN ITS FINEST FORM.

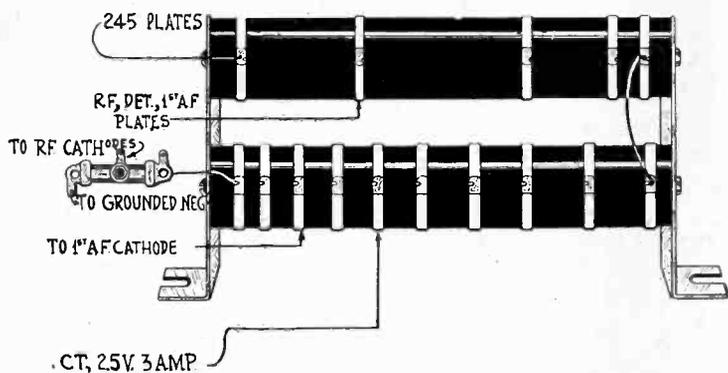


FIG. 10
HOW CONNECTIONS ARE MADE TO THE MULTI-TAP
VOLTAGE DIVIDER.

the same voltage is used for the screen grids, reduced effectively through positioning of the potentiometer knob.

In some instances instead of running the potentiometer to the same lug or lead that carries to the midtap of the power tubes filament winding, the lead for the potentiometer may go to the next highest lug on the voltage divider, with an extra 1 mfd. from this point to ground.

The circuit is sensitive, indeed, as has been stated, and is rated at 9 microvolts per meter, on an actual test, with laboratory instruments. This is not as great a sensitivity as develops in some other special receivers, but that does not deny the fact that 9 microvolts per meter is a greater sensitivity than is possessed by ninety-nine and nine-tenths percent of all the receivers on earth. In fact, not one in 5,000 receivers in use is as sensitive as this.

The circuit takes four and a half hours to build, going at a steady, uninterrupted gait. If you work slowly it will take five to six hours, but, as has been suggested, it is worth every cent and every moment you put into it.

LIST OF PARTS

- SL1, SL2, SL3, SL4—Four stage individually shielded coil cascade for .00035 mfd. (Four Cat. SH-3 of Screen Grid Coil Co.).
- C1, C2, C3, C4—One four gang .00035 mfd. condenser with equalizers E1, E2, E3, E4 built in.
- C5—One .01 mfd. mica condenser.
- C6, C7, C13, C14—Four 1 mfd. 200 volt DC bypass condensers.
- C8—One 1 mfd., 550 v. AC filter condenser.
- C9, C10, C11, C12—One Mershon consisting of four condensers, two of 8 mfd. and two of 18 mfd. with bracket (Cat. Q 2-8, 2-18 B).
- R1—One Electrad 25,000 ohm potentiometer with knob and two insulators.
- R2—One 50,000 ohm Lynch metallized resistor (.05 meg.), with mounting.
- R3—One Lynch 5.0 meg. metallized grid leak, with mounting.
- R4—One 5,000 ohm resistor with mounting.
- VD—One Multi-Tap Voltage Divider, 13,850 ohms, 14 taps.
- T1—One push-pull input transformer.
- OPC—One center-tapped output choke.
- T2—One Polo filament-plate supply, Cat. PFPS (Note: For 40 cycles use PFPS-40, for 25 cycles use PFPS-25).
- Ch—One double filter choke coil, 30 henrys each section, 100 ma.
- SW—One pendant AC switch with 12 ft. cable.
- PL—One 2.5 volt pilot lamp and bracket.
- Speaker (+), (-), Ant., Gnd.—Four binding posts with insulators.
- One Clarostat Humdinger, 30 ohms.
- One subpanel 17½"x11½", with five UY and three UX sockets.
- One vernier dial.
- One brown crinkle finish drilled steel cabinet.
- Four National grid clips.

work. Even in daytime it picks up distance, while at night steady speaker volume is obtained from stations throughout the United States and Canada. The entire wavelength spectrum may be tuned in, besides, but if by any chance the circuit tunes to higher wavelengths than are in the broadcast band, it may not tune low enough, so take off enough turns of wire, the same off of each secondary, to bring in the lowest wavelength. Then the highest will come in. The reason is that the relative position of the condenser in respect to the subpanel affects the actual capacity of the condenser. The subpanel may be regarded as part of the frame of the condenser, and the rotor plates function at this potential. The elevation of the condenser by means of elevating washers, to a height above the subpanel not exceeding ¼", should get rid of any odd tuning characteristics that would be present otherwise. Hence the coil data are given for a little more inductance than would be necessary in most instances, a better plan by far, since if the number of turns were too few it would not be easy to add more, whereas it is always easy to take off some turns, particularly as the wire adheres to the form and does not spring off.

The connection to the primary of the filament-plate supply is made by means of a through pendant switch. The leads from the power transformer primary are brought through to the rear of the cabinet, outside, and the switch is then attached, one lead being continuous, the other interrupted by the switch. Then an AC cable is connected to the equivalent binding posts at the end of the switch, and at the end of the cable a male plug is attached.

All the voltages desired should be obtained if the diagram is followed and the input is something around 110 volts. There will be discrepancies, of course, but nearly all of these are immaterial. If 150 volts show up on the plates, since that voltage is all-sufficient, accept it. The power tube bias voltage will run around 50 volts, and

Intermediate Tuning

Super-Heterodyne Coils Need Trimmers

By Knollys Satterwhite

[Here is another installment of the serial article entitled "The Superheterodyne." Next week, issue of December 28th, additional information will be given on the Superheterodyne.—Editor.]

It is not necessary that the intermediate frequency transformers in the Superheterodyne have the same number of turns and the same size tuning condenser just so the transformers are resonant at the same frequency. This suggests the desirability of having a means of adjusting the transformers to the same frequency before they are put into the receiver. Accurate adjustment is not possible because as soon as the transformers are put into the circuit they will be different because the capacities have changed. But it is possible to adjust them so closely that the differences occurring later can be taken up by means of the trimming condenser which should be across each tuning condenser.

The best way of adjusting the intermediate frequency transformers externally is to compare them against a standard oscillator. For this standard one of the intermediate frequency transformers and a tube can be used. The other transformers, one at a time, are then connected into a similar oscillating circuit and adjusted until the beat between the oscillators is zero, or at least very low.

CONNECTION OF OSCILLATOR

Suppose the intermediate frequency transformers have been wound with the intention of tuning the secondary. Then the tuned circuit is connected in the grid circuit of a tube and the primary is connected to the plate circuit. Only one connection will produce oscillation, that is, only one connection of the primary leads after the secondary terminals have been connected arbitrarily. When oscillation has been produced mark the terminals so that they can be connected in the amplifier in the same manner. That is to say, the lead connected to the grid of the oscillator tube should later be connected to the grid of the tube following the transformer and the lead to the plate of the oscillator should be connected to the plate of the tube preceding the transformer in the amplifier.

When two oscillators, the standard and one other, have been connected up and when they are operated by the same plate battery, a beat note will be heard in a headset connected in series with the battery and the two plate circuits. If the two frequencies happen to be nearly the same at the beginning the beat note may not be heard because the two oscillate at the same frequency. A .5 mfd. condenser connected across the headset will loosen the coupling between the oscillator so that they will operate at different frequencies down to as low as 30 cycles. If the adjustment is within 500 cycles it is good enough.

ADJUST THE TURNS

Suppose a high frequency note is heard indicating that an adjustment of the turns is necessary. Which way should the turns be changed? That is, should they be increased or decreased? It is not convenient to add turns because that would require soldering a wire to one of the leads of the tuned winding and putting more wire on. It is more convenient to remove turns. In order to know what to do it is necessary to determine which transformer has the greater frequency. Suppose the finger is pointed to one of the grids of the oscillators without actually touching it. The beat frequency will change as the finger approaches because the capacity is being increased. Note the direction of the change in the beat frequency whether it is up or down as the finger approaches. Now point the finger to the grid of the other oscillator. The change in the frequency should now be in the opposite direction. By this means it is possible to determine which of the two circuits has the greater frequency of oscillation, remembering that the frequency of the oscillator toward the grid of which the finger is pointed decreases as the finger approaches.

Retain the transformer having the higher frequency. For the other substitute one of the transformers to be tested and repeat the experiment. Again retain the one having the higher frequency. In this manner it is possible to pick out the transformer which oscillates at the highest frequency in the whole set. Use this transformer as the standard.

REMOVING TURNS

When the transformer having the highest frequency is used as the standard, all the other transformers can be adjusted to that frequency by removing turns. In adjusting a given transformer do not remove more than one turn at a time, and do not cut the removed wire immediately but only remove it from the form. It may be necessary at any stage to put it back on again. When the adjustment begins the beat frequency may be above audibility. To test this point the finger toward the grid of the standard oscillator. If

the beat is above audibility the finger should bring the note within the audible range.

This determined, remove a turn from the tuned circuit of the coil not in the standard oscillator. Note the beat note. Remove another turn and again note the change. A time will come when the beat note is low enough to fall within the limit of toleration, 500 cycles say. This may be either above or below the frequency of the standard oscillator.

When one of the transformers has been adjusted in this manner remove it from the circuit, not forgetting to mark the terminals as previously suggested. Put in one of the others. When all have been adjusted and marked all of the transformers, including the one used as standard, are ready to be put into the amplifier. Of course any excess wire may be cut off permanently as soon as a turn has been removed and it has been found that it is not necessary to put it back on again.

RAPID VARIATION OF FREQUENCY

It may be found that single turn will cause a great change in the frequency of oscillation. This will be the case when there is a relatively small number of turns and a relatively large capacity in the tuned circuit. In that event it is necessary to use a larger trimming condenser than when the number of turns on each transformer is large and the capacity in each tuned circuit is small. The trimmer condenser always should bear a certain relationship to the total capacity in the circuit, say 10 per cent.


The adjustment of the intermediate filters after the coils have been put into the amplifier should be done after the shielding has been put in place. In order to reach the trimmer condenser from the outside of the shield the condenser may be mounted on the shielding and the knob made to extend outside. If the trimmer is of the type which is adjusted by means of a screwdriver it should be mounted inside the shield in such manner that it can be reached through a hole in the shielding by means of a wooden or other insulating screwdriver. Certain types of trimmers, notably those used for trimming radio frequency tuners, are so constructed that they could safely be mounted outside the shielding. If the adjusting screw is grounded any screwdriver can then be used for making the adjustment.

ADJUST FOR LOUDEST VOLUME

The simplest way to adjust finally is to tune in the Superheterodyne on a station and adjust for loudest volume, just as is done in radio frequency circuits. If the trimmer used is of the type which is adjusted by means of a knob, the adjustment is very easily done, but it will not necessarily remain in adjustment unless the knob is locked after its proper position has been found. In connecting the trimmer condensers across the tuned circuits, the rotor should be connected to the grounded or low RF potential side of the circuit. This should be observed for the type which adjusts with a screwdriver as well as for the knob type of condenser.

When the intermediate frequency transformer is of the tuned primary type the preliminary adjustment is done in the same way as when the tuned secondary type is used, but the tuned winding should be put in the plate circuit of the oscillator and the untuned winding in the grid circuit of the same tube. In removing wire from the tuned circuit in this case care should be exercised against possible short circuit. The loose wire is at high DC potential and if it touches the ground side where the insulation is weak or removed the battery will be short-circuited.

Simple, Practical Tuner

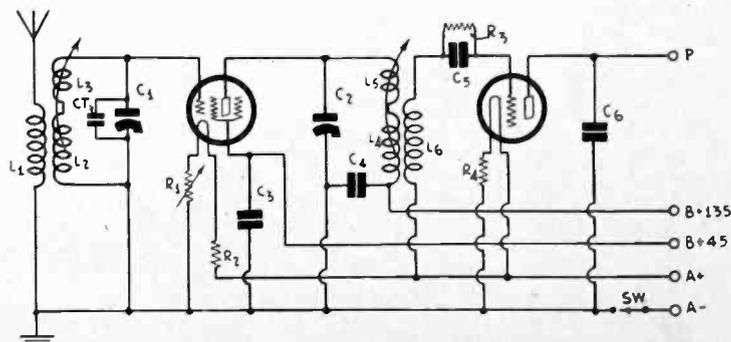

HERE IS A TUNER FOR BATTERY OPERATION, TO FEED A POWER AMPLIFIER. THE BERNARD TUNER ASSEMBLIES ARE USED. SEE ARTICLE IN NEXT WEEK'S ISSUE, DECEMBER 28TH.

Pointers on Wiring th

Compensation Provided for the Antenna Len

THE length of the antenna used with the Hammarlund HiQ-30 receiver affects the tuning characteristics to some extent, as it does in practically all other receivers. For this reason two binding posts are provided at the input, one connecting with a tap on the primary inductance and the other connecting with the end of the coil. When a short antenna is used the entire coil should be employed and when a long outdoor antenna is used it should be connected to that binding post which goes to the tap on the primary. If the entire coil is used when the antenna is long the signals are likely to be too great.

Of course, when the object is to receive stations remote from the receiver, the entire primary winding may be used even when the antenna is long.

There is also a certain dependence between the antenna and the length of the waves being received, no matter what the length of the antenna may be. Stations on the lower half of the broadcast band can be received with greater volume when the entire primary inductance is used, and those on the higher half may be received with greater intensity when only a part of the coil is used.

Because of these inevitable differences the operator of a HiQ-30 should try both binding posts to determine which gives the more satisfactory operation on the antenna at hand for stations of different frequencies and at different distances from the receiver. For routine reception, that is, for the reception of the most popular stations, which are likely to be local stations, it is usually best to connect the antenna to that post which gives the lower signal strength, because this will give volume aplenty under the stated conditions.

GRID BIAS PROVISION

In an AC operated receiver it is important to take every precaution against the entrance of hum into the signal. One of the means for minimizing hum, which is used in the HiQ-30, is the use of individual grid bias resistors for every tube, or stage, not only in the audio amplifier but also in the radio frequency amplifier. While it is not readily apparent by glancing at the circuit diagram that a separate resistor is used for the last stage in the HiQ-30, since the bias resistor appears to be a portion of the voltage divider, a close inspection will show that the plate current of the last stage alone flows through that portion of the voltage divided which is placed below the grounded point, and that is the sole criterion for the individuality of the resistor.

In the 227 tube stage preceding the push-pull there is also an individual resistor to provide the bias, but this is located in the usual position so there can be no confusion.

In the same manner the bias is obtained for the radio frequency tubes, except that in the first two the normal plate current is augmented in the bias resistors by means of resistors from B plus to the cathodes. Thorough by-passing is done on these resistors to minimize feedback both of the positive and negative types. Therefore neither oscillation at radio frequency nor decrease in the sensitivity will result.

GROUNDING THE HEATER

Another feature which reduces the hum is the grounding of the mid-point of the heater near the tubes by means of a center-tapped resistor across the heater winding. This is in addition to the center-tap on the 2.5 volt winding, which is not directly grounded.

The HiQ-30 is, of course, built on a metal subpanel, which is grounded. This permits grounding all components that should be grounded without the necessity of running long leads, and it also simplifies the job of wiring the circuit. This arrangement also helps to prevent hum since the panel is a better conductor than any wire could be.

Hum is also prevented by shielding, and this has been done with particular thoroughness in this receiver. The tuning condensers are individually shielded, as are the tuning coils in the band pass filter and the inter-tube tuners. All transformers, whether they are operating at power or audio frequencies, are shielded both magnetically and electrically. There is no chance for interaction among the parts.

AUDIO QUALITY

The audio frequency amplification is adequate to permit the use of the sensitive grid condenser grid leak method of detection without the slightest overloading in the detector. The constants of the grid leak and grid condenser have been chosen so as to effect the optimum compromise between detection efficiency and fidelity of audio output. The values of the by-pass condenser and the radio frequency choke in the plate circuit of the detector have been selected with the same object in view. Hence the audio output from the detector is undefiled with harmonics and contains all the essential frequencies in true proportion. It remains for the amplifier to increase the signal level to loudspeaker intensity without introducing either frequency or wave form distortion.

The first condition for retention of the good quality is that the applied plate voltages be adequate. The built-in power supply does deliver sufficiently high voltages without fluctuation. The second

condition is that the grid bias values be chosen to meet the requirements of the tubes and the high plate voltages. These are provided for as has been described.

THE AUDIO TRANSFORMERS

It remains for the audio transformers to do their work without introducing any frequency distortion. These transformers have been designed and built especially for the HiQ-30 to the most exacting specifications. That they perform in a satisfactory manner becomes evident the instant one hears the performance of the receiver. There is a certain feeling of fulness and richness to the tone which is satisfying. This effect, of course, is a combination of the contributions of the band pass filter in the tuner, the audio frequency amplifier and the loudspeaker.

And what kind of speaker is recommended by the designers? That depends on the output transformer chosen. There is one for magnetic speakers of relatively high impedance and another for dynamic speakers of relatively low impedance. In this classification the inductor dynamic comes in the magnetic class. Naturally, since the output of the receiver is considerable, a speaker of a large cone should be used in order to radiate as much sound as possible. If an inductor or a dynamic type speaker is used its cone should be at least 10 inches in diameter.

A magnetic speaker, including the inductor type, has the advantage that no external source of direct current is required. The permanent magnet supplies the field, and this field is steady so that there can be no hum introduced into the signal by the speaker. Radio receivers emitting a hum are often wrongfully condemned when it actually is the speaker which is to blame for the trouble.

TUBES USED IN THE RECEIVER

The HiQ-30 requires three tubes of the 224 heater screen grid type. These step up the signal at radio frequency to an enormous

Right or

[The following questions are based on technical articles published in last week's issue. Read this week's issue carefully and know the answers to next week's questions before those questions are put.—Editor.]

(1)—A pretuner of the band pass filter type can be used in front of a radio receiver for increasing the effective selectivity to a high degree without at the same time cutting the side frequencies in the signal.

(2)—Satisfactory tuning characteristics in receivers can be obtained by combining the effects of a band pass filter and an ordinary tuner.

(3)—If a grid resistor, grid leak detector is used and it is desired to connect a phonograph pick-up to the detector grid so as to transform the tube to an amplifier it can be done simply by connecting the unit between the cathode and the grid. It is not necessary to open the radio frequency input circuit.

(4)—Putting a filter circuit in the supply line to an AC set does not take out line noises because most of the noise comes in as a radio frequency signal just as any desired signal.

(5)—Modulated sound waves of superaudible frequency can be heard without any form of detection.

(6)—An electric arc such as is used for arc lighting can be made to speak and act as a loudspeaker.

(7)—If a tuning fork of superaudible frequency were driven by a modulated electric current the modulation frequency would be heard due to the varying amplitude of the fork, but there would be no frequency distortion because the fork would vibrate at only one frequency.

(8)—Sound waves of very short length can be focused and transmitted in a narrow beam just like light.

(9)—The cause of motorboating in a radio receiver is the feedback in the radio frequency tuner.

(10)—The voltage drop in the leads to the heaters of AC tubes is entirely negligible even if fine hook-up wire is used.


ANSWERS

(1)—Right. The characteristics of the band pass filter are such that the transmission between two predetermined frequencies is practically constant and of a high order and the transmission outside those frequencies is practically zero. If the two frequencies are chosen properly when the filter is designed the band will cover just 10 kilocycles. The filter can be used as a pre-selector as well as a tuner between tubes.

(2)—Right. A band pass filter can be made such that the transmission at the carrier frequency is slightly less than that at frequencies close to it. The ordinary tuner can be made such

AC Model Hi-Q 30

Grid Bias Provisions Carefully Selected

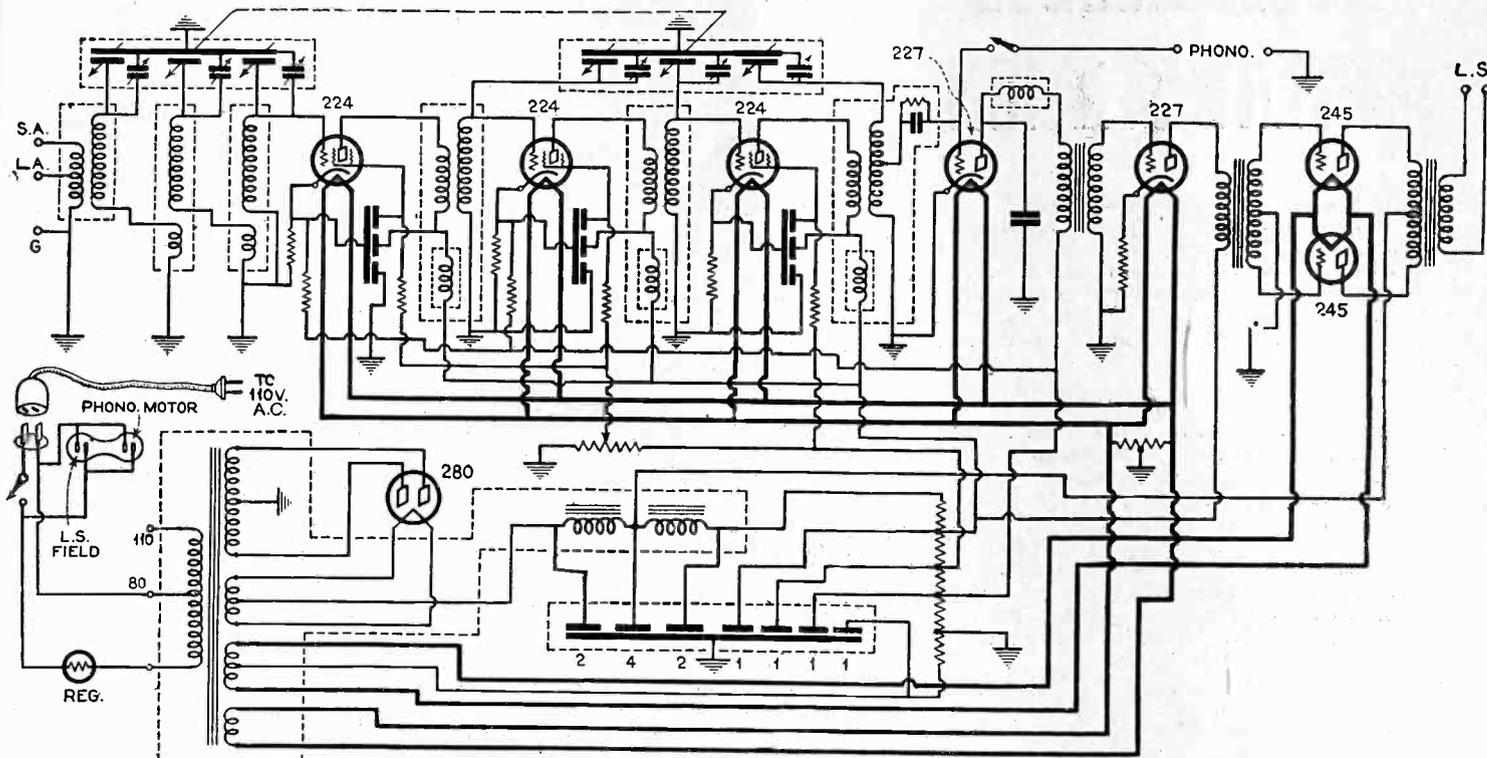

Wrong?

that its peak coincides with the hollow in the band pass filter curve. The combined effect is a band pass curve with a flat top, provided that the constants of the two components are chosen correctly.

(3)—Right. If it were not for the grid condenser this could not be done because the tuning coil would short-circuit the pick-up unit, but the grid condenser has such a high impedance to audio frequencies that practically the full voltage generated in the pick-up unit is impressed on the grid. It will cause a partial short-circuit at the highest audio notes but this is an advantage for it takes out much of the scratch and other high frequency noise.

(4)—Wrong. It takes out much of the noise provided that the elements of the filter be chosen properly, because much of the noise actually does come into the set by way of the power line. If the noise is picked up by the antenna, however, the filter does not do much good, unless it is placed near the source of the noise.

(5)—Wrong. If they are superaudible sounds how can they be heard? They cannot without detection because detection in this case signifies making them audible. However, since the ear has the properties of a rectifier, intense modulated sound waves may be heard without an external rectifier.

(6)—Right. The singing and the speaking arc is a well-known phenomenon in physics. The arc intensity fluctuates at an audible rate and the change in the heat produces corresponding fluctuations in the air. A speaker of this type is capable of exceptional fidelity. The light also varies so that the arc could be used for transmitting sound through the medium of light. A photoelectric cell exposed to the varying light would pick up the light fluctuations and transform them to electrical vibrations. Direct current must be used on the arc.

(7)—Wrong. There would be a good deal of frequency distortion because the fork is a highly resonant system which would cut off the higher side frequencies. It would act the same as a highly resonant electric circuit in this respect.

(8)—Right. They can be focused the same way as light with a concave reflector. If the sounding source were placed in the focus of a long and narrow parabolic reflector the waves would move out in a narrow beam.

(9)—Wrong. The radio frequency tuner has nothing to do with the trouble. It is the impedance in the B supply circuit which is the cause of it.

(10)—Wrong. If the leads are fine there will be a high voltage drop in them because the current is heavy, and it may be that the tubes will not get enough voltage for proper operation. Either very heavy leads should be used or else individual leads should be run from the supply transformer to each tube.

degree, signifying that the receiver is exceptionally sensitive. The detector tube is a 227 type, as is the first audio frequency amplifier. The two final tubes in the push-pull stage are 245 type. These are easily capable of putting out an undistorted power of 3 watts, which is more than sufficient for any home. What is more, the receiver has an amplification so high that this output can be obtained from distant stations even when a small indoor antenna is used.

For rectifier in the power supply one 280 full wave rectifier is used. This can supply a current up to about 110 milliamperes, which is much more than the circuit requires. The power transformer and the chokes have been proportioned so that the full rated voltage is obtained when the normal current for all the tubes and the voltage divider is drawn.

The construction of the HiQ-30 is a simple matter. The various major units are already wired so that the construction is reduced to the assembly of mechanical parts, for each of which there is a definite niche. After the mechanical assembly the wiring is even more simple.

Fine Adjustment of Grid Bias

I HAVE A voltage divider with sliders on it but want to use a portion of the resistor for grid bias. Is it possible to adjust the grid bias for screen grid tubes with sufficient accuracy in this manner?—L. W.

It depends largely on how high the resistance is per turn on the voltage divider. You cannot vary the bias by smaller voltage steps than the drop in each turn. The drop in each turn also depends, of course, on the current flowing in the resistor. If the current is high there will be a considerable drop in each turn. This is likely to be the case when the circuit is arranged so that the resistor is also used for plate voltage purposes for then the entire plate and bleeder current will flow through that portion which is used for grid bias and this is likely to be quite high. A way out of the difficulty is to connect a high resistance with sliders on it across that portion of the main resistor which is used for bias. A very small current will flow through the high resistance and voltages can therefore be adjusted more accurately. For example, suppose that the total current involved is 85 milliamperes and that the highest grid voltage is 85 volts. The total resistance for bias should then be 1,000 ohms. If a 25,000 ohm resistor is connected across this 1,000-ohm section the total effective resistance will be 4 per cent less than 1,000 ohms and the grid bias will be correspondingly lowered. But this drop exists both in the 25,000 ohm and the 1,000-ohm resistors, since they are parallel. The drop in each turn of the 25,000 ohm resistor may be only a small fraction of a volt whereas the drop in each turn of the 1,000 ohm resistor may be several volts.

BOARD ITSELF WOULD ASSESS EVERY STATION

Washington.

Assessment of a graduated scale of fees for all licensed users of the ether, and provision for handling charges for the handling of routine applications of all kinds, is recommended to the Senate by the Federal Radio Commission as a means of defraying the costs of administering radio in the United States.

Senate Asked Advice

In a report submitted in compliance with a Senate resolution for the creation of a license fee system, the Commission recommends three alternate proposals for levying fees upon holders of licenses of every character. The cost of radio regulation for the fiscal year ending June 30th, 1929, was declared to have been \$628,103.29, of which \$265,018.88 was expended by the Commission and the rest by the Department of Commerce.

It is recommended that a flat fee of \$100 be assessed for handling applications for station licenses and a fee of \$25 for construction or licensing applications for new service.

Renewals at \$10

Applications for renewal of outstanding license would be taxable at \$10 and applications for modification of existing licenses would entail a fee of \$15. These fees, the report states, would total about \$840,445 and would just about meet the expense of administering radio regulation, allowing for a natural increase in the expense and a decrease in revenue.

WSAI on Air Again After a Suspension

Washington.

WSAI, of the Crosley Radio Corporation, Cincinnati, which had been ordered off the air on the grounds that it had violated regulations as to frequency deviation, has been reinstated and its license renewed until January 31st.

KYA, of San Francisco, Cal., which also had been ordered off the air for alleged violations, was reinstated and given a 30-day license. It will operate on its former wavelength, pending action by the Commission on formal application for renewal of license.

WORTH THINKING OVER

NOW that radio is away beyond the point where it is regarded by the easy-money boys as a racket for the sale of stock to the shining lights on the sucker lists, there is no reason why Wall Street's up and downs should affect its stability. To be sure, those concerns that have been more interested in selling handsome certificates of doubtful value—and not even so doubtful to the knowing ones—instead of radio goods of value, have felt the effect of the recent deflation. However, radio, like the automobile, goes marching on and during the coming year will probably break all its own records. It's the old story of nothing being able to knock out something that the public insists on having.

New Manual

The Radio Manual, new and completely revised edition, by George E. Sterling and Robert S. Kruse, B.S., has just been published by D. Van Nostrand Company, New York. (\$6.00)

As the name of the book indicates, it is a reference volume on radio theory and practice, which is indispensable to radio operators on sea and land and is useful to all who are interested in radio as a profession or a hobby. It is a store of information from which any one can draw with profit.

Chapter I takes up the elementary principles of electricity and magnetism and is especially recommended to those who wish to become acquainted with the basic principles underlying radio theory and science.

Chapter II deals with motors and generators, which is a subject that should be of interest to commercial radio operators and to operators for talking movies. There are in all nineteen chapters covering the entire field of radio as the art stands today.

Missouri Protests Wave Used in Denver

Jefferson City, Mo.

The Attorney General of Missouri, Stratton Shartel, has sent a protest to the Federal Radio Commission against the assignment of 630 kilocycles to KFEL and KFXF, at Denver, Col., claiming that this assignment will interfere with law enforcement in the State of Missouri.

The Attorney General states that this assignment will interfere materially with the operation of WOS at Jefferson City, Mo.

"We in Missouri are very anxious about this matter," the protest says, "because our radio broadcasts educational matters almost entirely and we are now planning upon using it to assist us in the enforcement of the laws of the State by establishing a hook-up with every sheriff's office and with members of the State police, which we expect to put into effect shortly."

Titles to Be Given After the Rendition

The Sylvania Products Company, tube manufacturers of Emporium, Pa., sponsors of the "Sylvania Foresters" program, has decided that instead of naming a selection prior to its rendition, the announcer will be instructed to declare it upon its conclusion. This is the idea of B. G. Erskine, president of the company. He said:

"I am not much different from any other broadcast listener. I seldom pay any attention to introductory announcements and it makes me mad as the devil when I have enjoyed an orchestral or vocal number to discover that its name is lost forever, after it is over. And I hope this improvement will generally be adopted, for my sake and for the forty million others who listen in."

Set Passes All Tests So Burglars Steal it

Evanston, Ill.

Burglars entered the home of John W. Morehead, at the approved midnight hour while the family was out of the city. The intruders had a grand time, testing Morehead's radio set for volume and clarity. Then the finicky housebreakers tested it thoroughly for DX. The receiver passing all these tests, they stole it.

Wide Inquiry Into Static

A far-reaching inquiry into all phases of regulation, which may widely affect the entire Committee on Interstate Commerce during its resolution passed granting the committee authority subjects to be considered has been prepared by the Committee. The outline as to be applied

Monopoly: Monopoly in manufacturing—If such monopoly, is it legitimate? Are m related?

Monopoly in communications—Does such m ated? If such monopoly exists, is it necessary?

Legislation with reference to foregoing—Should persons be barred from receiving licenses (a) for broadcasting? (b) for broadcasting? Should the persons found guilty of monopoly of radio of radio apparatus be included in bill? Should to persons found guilty of monopoly of radio by other means or by unfair methods provisions of section 12 as to revocation of license section 13, giving court authority to revoke of antitrust laws, be included in legislation? act of 1927) prohibiting operators of radio companies, etc., and vice versa, if purpose or States and foreign countries or create a monopoly

Radio stations as common carriers: Shall riers? (a) shall broadcasting stations be regulated as point-to-point communications system choose own programs but be regulated as to common-carrier obligation? Shall chain broadcast (a) as to furnishing service upon demand? (b) requirement as to furnishing facilities upon demand?

Shall zone system be continued, modified, Shall Congress regulate the matter of clear channel? Shall Congress regulate limits of power of broadcast stations? Shall license fees for radio stations be required for broadcasting stations?

Shall larger powers of censorship be granted? Shall a special radio department be created? Should act provide for supervision of issues of radio? Should provision be made requiring approval of American stations and stations in foreign countries?

Literature

John Machatterre, 248 1/2 W. 5th Ave., Columbus, Ohio.

S. Leibowitz, 89 Pleasant St., Providence, R. I.

C. A. Simon, 1919 Burnet Ave., Syracuse, N. Y.

Fred Rohde, 1962-72nd St., Brooklyn, N. Y.

David Garrick, 2932 Gladstone, Detroit, Mich.

Don D. Miller, 5439 1/2 Ballard Ave., Seattle, Wash.

Harold M. Hall, Box 335, Laguna Beach, Calif.

H. C. Carlson, R. No. 1, Firth, Idaho.

Elmer K. Sterling, 332 S. Patterson Park Ave., Baltimore, Md.

George Giles, 119B S. Missouri, Atlantic City, N. J.

Nat. Seidman, 300 Berriman St., Brooklyn, N. Y.

G. A. Swinford, 256 Herzberg St., Gadsden, Ala.

Josef A. Liccardo, 91 New Jersey Ave., Brooklyn, N. Y.

San Jon Garage, J. B. Gordon, San Jon, New Mex.

J. O. Sneed, Box 305, Copperhill, Tenn.

Sol Alexander, 61 Sterling St., Newark, N. J.

Harley A. Boltz, 1639 E. Walnut, Des Moines, Iowa.

C. Wallen, 80 Berkely St., Boston, Mass.

Walter E. Reitz, Jr., 1213 N. Patterson Park Avenue, Baltimore, Md.

W. W. Dowdle, Steens, Miss.

H. V. Zumwalt, R. 7, Box 269A, Seattle, Wash.

Anton Adasiewics, Central Garage, Stambaugh, Mich.

Arthur B. H. McKenney, 18, North 10th St., East St. Louis, Ill.

Alfred F. Stankus, 9710 Normal Ave., Chicago, Ill.

Anthony Basharkwica, 3878 Third Ave., New York City.

Walter D. Cunningham, 110 Carmathen St., St. John, N. B.

L. L. Savage, Savage Radio Service, Carbondale, Wash.

J. C. L. Crone, 2580-9 West, Seattle, Wash.

Marshall Chipman, R. No. 1, Grand Rapids, Mich.

S. Patrette, 240 N. 15th St., San Jose, Calif.

Arthur Petit, 177-154th St., Harvey, Ill.

Nicholas S. Metro, 147 Thompson St., Buffalo, N. Y.

Under Way Licenses and Fees

Washington.

...involving communication, manufactures and industry, will be conducted by the Senate consideration of the Couzens bill, pursuant to the order to make this investigation. An outline of the bill is being prepared by the Hon. William C. Green, recently appointed counsel for the Senate.

...such monopoly exist? If so, how created? ...solely in manufacturing and in communications

...solely exist? If such monopoly exists, how created? ...best interest of United States?

...manufacturers of apparatus used in radio transmission point-to-point transmission, foreign or domestic provisions of section 11 directing refusal of license to manufacture through control of manufacture or sale of apparatus used in radio transmission through exclusive traffic arrangement-competition, be included in the bill? Should such provisions be included in the bill? Should provisions of section 15 of proposed bill (sec. 17 of radio communications systems owning interest in cable system) be included in legislation?

...broadcasting stations be classed as common carriers to serve the public upon demand in same manner as telephone companies?

...practices, etc., as public utilities without special regulations as to rates, etc., but without special supervision?

...channels? Should such stations be permitted to operate on same frequencies as public utilities without special regulations as to rates, etc., but without special supervision?

...broadcasting stations? Should such stations be permitted to operate on same frequencies as public utilities without special regulations as to rates, etc., but without special supervision?

...Point-to-point communications stations? Should such stations be permitted to operate on same frequencies as public utilities without special regulations as to rates, etc., but without special supervision?

...Commission? Should such stations be permitted to operate on same frequencies as public utilities without special regulations as to rates, etc., but without special supervision?

...Commission to handle administrative matters? Should such stations be permitted to operate on same frequencies as public utilities without special regulations as to rates, etc., but without special supervision?

...Securities by communications companies? Should such stations be permitted to operate on same frequencies as public utilities without special regulations as to rates, etc., but without special supervision?

...by Commission of traffic contracts between stations? Should such stations be permitted to operate on same frequencies as public utilities without special regulations as to rates, etc., but without special supervision?

Forum

I HAVE read RADIO WORLD since it was published, and I enjoy it very much.

I am pleased to see that you publish battery receivers, as there has been too much of electric sets.

I have built radio sets since 1919, so have some experience. I have not yet heard of an electric set sold at radio stores that can come up to battery sets.

I built the first Neutrodyne set that was in this state years ago and still have it as a souvenir. It still does its work. Now my special line is Supers.

I have been a pharmacist for years but go in for radio. As it is I build sets as a side line and repair them.

Gustave Simmons, Bilings, Mont.

THE most amazing thing to me in many a day was to see a letter in your October 12th issue in which complaint is made of a lack of AC circuits for home construction and it was suggested that too much attention was being given to battery circuits.

I have been interested in radio for a number of years and since the AC craze arrived have been lamenting loud and long the neglect of battery sets. I do know that some radio magazines practically quit printing anything whatsoever along the battery set line while the great majority of manufacturers quit making sets for battery operation. Recently there has appeared in some quarters a little recognition of how large a number of people there are who live where there is no power supply. I notice that Atwater Kent, Crosley and Radiola are offering rather up-to-date sets with screen grid tubes for battery operation. However I contend that even now the people who must use battery sets are not receiving half the attention that they should in proportion to their numbers.

It was a pleasure, then, to see in your October 12th number mention of what look like two good battery circuits. I refer to the "Push Pull Battery Model Diamond" and the "Battery Model of HB Compact."

Where I live, we are about 25 miles from the nearest station, WWVA, which has 5,000 watts power, while KDKA, 50,000 watts, is 65 miles away, but we find that many sets are not selective enough.

A sensitive set is particularly desirable here, for operation is quiet and distant signals should be well received where there is sufficient selectivity. Therefore the ideal battery set we are looking for should possess both selectivity and sensitivity. Naturally we want good tone. We are not so much interested in enormous volume. We find that a 112A gives pretty good volume and we feel that two such tubes in push pull would give us plenty of power.

Do you know of anything good in a battery-operated Superheterodyne? Most of them have been so expensive and also used so many tubes that the battery current was almost prohibitive but it seems to me that recent developments ought to overcome this.

J. Mack Gamble, Hannibal, Ohio.

A THOUGHT FOR THE WEEK

WHY not make it a Radio Christmas? Everybody is interested in radio—absolutely everybody from President Hoover, who broadcasts his messages for the information of the whole country, down to the youngster who wants to be thrilled by a bedtime story.

So let's make it a Radio Christmas and the radio dealer will call us blessed.

REVELATION OF RECORDS IS PUT IN EXACT FORM

Washington.

All doubts as to the methods to be used in broadcasting records were settled by the latest general order of the Federal Radio Commission, amending its previous order on this subject.

"The amendments were adopted to clear up clear up misunderstanding among broadcasters as to just what was required of them in the way of announcements of this sort," said Commissioner Lafount. "Under the existing order, broadcasters may coin their own descriptive phrases, and are not certain as to how far they may go."

Where a recording or transcript is made exclusively for broadcasting purposes and is not offered for sale to the public, the broadcasters must announce:

"This program is an electrical transcription made exclusively for broadcast purposes."

Words to Use

As to other mechanical reproductions broadcasting stations must be the exact words: "This is a talking machine record," "This is a phonograph record," or "This is a graphophone record," the amended order specifies. The full text of the amended order (No. 78) follows:

It is ordered that General Order No. 52 be, and the same is hereby amended to read as follows:

I.—Ordinary phonograph records, mechanical piano players, etc. All broadcasting stations shall announce clearly and distinctly the character of all mechanical reproductions broadcast by them, the announcement to immediately precede the broadcasting of each record. In such announcements each talking machine, phonograph or graphophone record used, whatever its character, shall be described by the use of the exact words: "This is a talking machine record," or "This is a phonograph record," or "This is a graphophone record"; each player piano selection used shall be described as played by "mechanical piano player"; every other mechanical reproduction shall be similarly described by the terms generally understood and used by the public and meaning such mechanical reproduction.

Exclusive Records

II.—Exclusive transcriptions for broadcast purposes. Where a recording or transcript is made exclusively for broadcasting purposes and is neither offered or intended to be offered for sale to the public, each such recording shall be immediately preceded and followed by the following statement: "This program is an electrical transcription made exclusively for broadcast purposes."

Broadcasting stations shall not use such records, transcriptions or piano player rolls when the length of the rendition thereof exceeds 15 minutes, unless provision is made for the announcement of the station call letters which must be given together with the statement above set forth at least once every 15 minutes.


Wanted

- F. Rastetter, 240 E. Oxford, Alliance, Ohio.
- Robert P. Murphy, Box 269, Ft. Wayne, Ind.
- A. Schneider, 214 S. 10th St., Reading, Pa.
- Eugene B. Clark, Jr., Sunmount, Santa Fe, N. M.
- J. Thielk, 312 W. Giddens, Tampa, Fla.
- W. Brady, 4212 Agnes Ave., Kansas City, Mo.
- Thos. Wm. Mallow, 4162 Lee Ave., St. Louis, Mo.
- Ernest W. Fair, Box 64, Cap. Hill Sta., Oklahoma City, Okla.
- Ralph L. Arthur, 910 St. Joseph St., So. Haven, Mich.
- Capt. E. S. Coutant, c. o. Print Kraft, Stuart, Fla.
- V. R. L. Dwyer, New Plymouth, Vinton Co., Ohio.
- Fred. J. Merklein, 22 Moffat St., Brooklyn, N. Y.
- Lifton L. Lane, 439 Bringham St., Philadelphia, Pa.
- LeRoy Jordan, 4232 W. Monroe, Chicago, Ill.
- Edenson, 651 Belmont, Chicago, Ill.
- as. K. Barron, 48 Ida St., Troy, N. Y.
- Stanley Levan, 239 Chestnut St., Reading, Pa.
- Stephen L. Holland, 3 Syndicate St., Newport, N. H.
- Toy C. Barrows, 31 Kelton St., Athol, Mass.
- Alvin Miller, 5511 Market St., Philadelphia, Pa.
- R. Yates, 62 Hazelhurst Ave., Richmond, Va.
- Castle Radio Service, Box No. 5, Lafayette Hill, Pa.
- L. C. Hyde, 1010 E. N. 3rd St., Sweetwater, Texas.
- Lewel Adams, c. o. S. R. Putnam, LaJolla, Calif.
- Charles Stevenson, 135 Wash. Pl., Hasbrouck Hgts., N. J.
- A. R. Scarborough, Sebastopol, Miss.
- Wm. F. Sweitzer, 422 No. 11th St., Allentown, Penna.
- Tom Harrington, A-1 Radio & Service, 3601 E. 10th, Long Beach, Calif.
- Shinichi Seki, 1710 Fort Street, Honolulu, Hawaii.
- G. H. Monk, 233 8th Ave., So. Charleston, W. Va.
- Alvin W. Miller, 717 N. Ninth St., Reading, Pa.
- Bernard J. Bruns, 13 S. Pulaski St., Baltimore, Md.
- Guy O. Linderman, 137 Cable St., Bellingham, Wash.

A Question and Answer Department conducted by Radio World's Technical Staff. Only Questions sent in by University Club Members are answered. The reply is mailed to the member. Join now!

RADIO UNIVERSITY

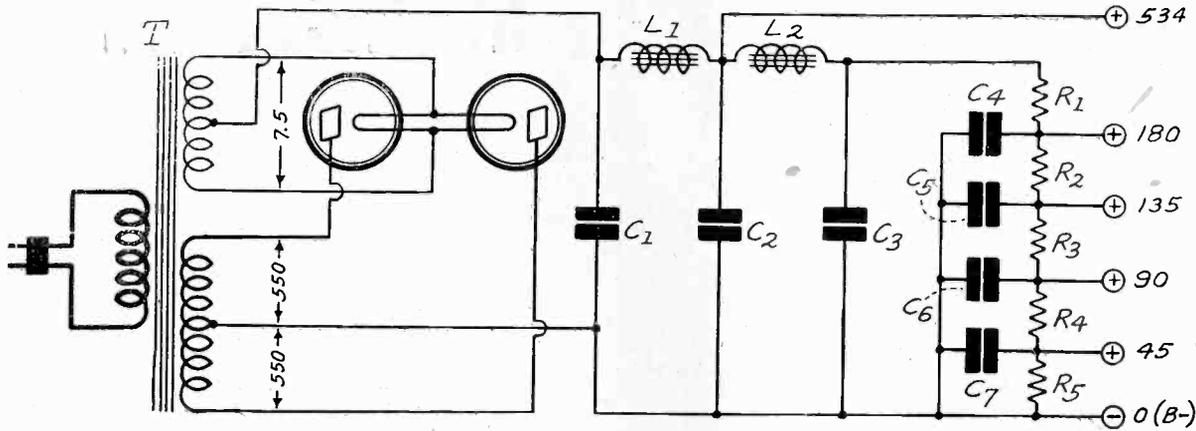Annual subscriptions are accepted at \$6 for 52 numbers, with the privilege of obtaining answers to radio questions for the period of the subscription, but not if any other premium is obtained with the subscription.



HEAVY DUTY B SUPPLY

FIG. 814

THE CIRCUIT OF A HEAVY DUTY POWER SUPPLY USING TWO 281 RECTIFIER TUBES AND SUITABLE FOR USE ON A CIRCUIT IN WHICH THE LAST STAGE CONTAINS TWO 250 TYPE TUBES.

I HAVE transformers and choke coils for a heavy duty B supply which I wish to hook up. Will you kindly publish a suitable diagram. One of the chokes has a rating of 10 henries and the other a rating of 30 henries. Please indicate the order in which these two coils should be connected. The B supply is supposed to operate a push-pull amplifier using two 250 tubes as well as a number of other AC tubes.—T. R. R.

The circuit diagram shown in Fig. 814 should meet your requirements. The 10-henry coils is L1 and the 30-henry coil L2. The plate supply for the two 250 tubes is taken from the junction of these two coils. If you need a voltage between 45 and 90 volts for the screen voltage on 224 tubes it can be obtained by connecting a 5,000 ohm potentiometer across R4 and connecting the screens to the slider.

INDUCED CURRENTS

A FEW YEARS ago we were told that metal bodies in the fields of tuning coils reduced the selectivity and therefore that every bit of metal had to be removed from the coils as far as was practical. But now inductance coils are put inside shields some of which are quite close to the coils and completely surround them. Don't these shields induce losses in the coils thereby decreasing the selectivity? It seems to me that radio engineers have made a complete about-face. Are they right now or were they right before?—W. H. C.

It is true that if pieces of metals are in the fields of coils currents are induced in them and that these currents lower the selectivity of the tuned circuits. But now-a-days when we have tubes which amplify tremendously and several tuners it is not necessary to make each tuner as selective as when only one or two tuners and possibly not more than one radio frequency amplifier were used. It is not necessary to take extreme precautions to get a high order of amplification because the tubes amplify enough and it is not necessary to make each tuned circuit of a selectivity more than average because several such tuners will make the overall selectivity satisfactory.

Moreover, it is necessary to use shielding because with the high amplification afforded by several stages of screen grid tubes the amplification is so high that radio frequency oscillation would be uncontrollable without the shielding. Also, without shielding there would be direct coupling between adjacent coils and this might actually lower the selectivity more than the shielding does.

INDUCTOR DYNAMIC

WHY is an inductor speaker called dynamic? It seems in no way different from a magnetic speaker of the double magnet type. Is as good quality possible from an inductor as from a regular dynamic?—J. J. K.

Every type of speaker must have a name and inductor dynamic is a good name for this speaker. No particular reproducer has a monopolistic right to the name dynamic as the term can be applied to any type that is powerful. The inductor dynamic is a magnetic speaker but so is the electro-dynamic speaker. In one a permanent magnet is used to establish a field, in the other an electromagnet. Even a dynamic could be made with a permanent magnet and many speakers have been made in this way in foreign countries. The main distinction between the inductor and the dynamic is that in the inductor the armature is a piece of iron and the armature coil is fixed and in the dynamic the armature coil is moving.

Sure, the inductor dynamic is capable of as good quality as the

regular dynamic speaker. The quality of which each is capable is largely a matter how each has been constructed.

VOLTAGE ON THE CATHODE

WHAT IS the voltage usually applied to the cathode of a heater type tube? In radio articles I have frequently noted that voltage is measured with respect to a certain point. What does that mean? When the voltage at a certain point is measured what has any other point got to do with it? May be my conception of voltage is all wrong.—A. F. A.

The voltage at any point is meaningless taken by itself. It must be taken with respect to some other point. Mentioning the voltage on the plate we mean the voltage of the plate with respect to the cathode, or electron-emitting electrode. Likewise when we speak of the bias on the grid we mean the voltage on the grid with respect to the cathode or electron-emitting electrode. When we speak of the voltage on the filament, or on the heater, we mean the voltage at one end of it with respect to the other end, or we mean the voltage difference between the two ends.

The voltage on the cathode has no meaning at all unless some other point is specified. For any particular tube the voltage on the cathode is zero because that is the starting point for measuring voltages on the elements of the tube. If ground is taken as the point of zero voltage in the set as a whole, the voltage on the cathode with respect to ground may be different from zero. It may be negative or positive according to connections, but usually it is positive because in most instances the lowest voltage point in the circuit is grounded. Sometimes there is a voltage between the cathode and the heater. This may make the cathode negative or positive with respect to the heater depending on the connections.

Voltage has no more meaning than height or depth without some reference point. When we say that a building is so many feet high we mean that the top of the building is so many feet above the ground, and when we say that a well is so many feet deep we mean that the bottom is so many feet from the surface of the ground. It is the same with voltage.

HEAVY CURRENT DRAIN

WHEN THE plate current through a grid bias resistor is augmented by a resistor connected between B plus and the cathode is not the total current drawn from the B supply considerably increased? If so, what is the advantage of the cathode bleeder, since current drawn from the B supply is used in either instance?—W. H. P.

It is increased by the amount that flows through the resistor from the cathode to the B supply. But the scheme is not used except when the normal plate current in the tube is very small as in detector and resistance coupled circuits. The total current need not be more than the normal current in a transformer coupled circuit. If the scheme were not used with tubes in which the normal plate current is very small the grid bias resistor would have to be excessively large and it would result in high reverse feedback which would render the tube ineffective as detector or amplifier. For example, if the tube is a 240, having a mu of 30, and it is adjusted so that the grid bias is 3 volts, obtained from a resistor drop, the effective amplification is 14. If a grid battery of the same voltage is used the amplification is 21.4. The load

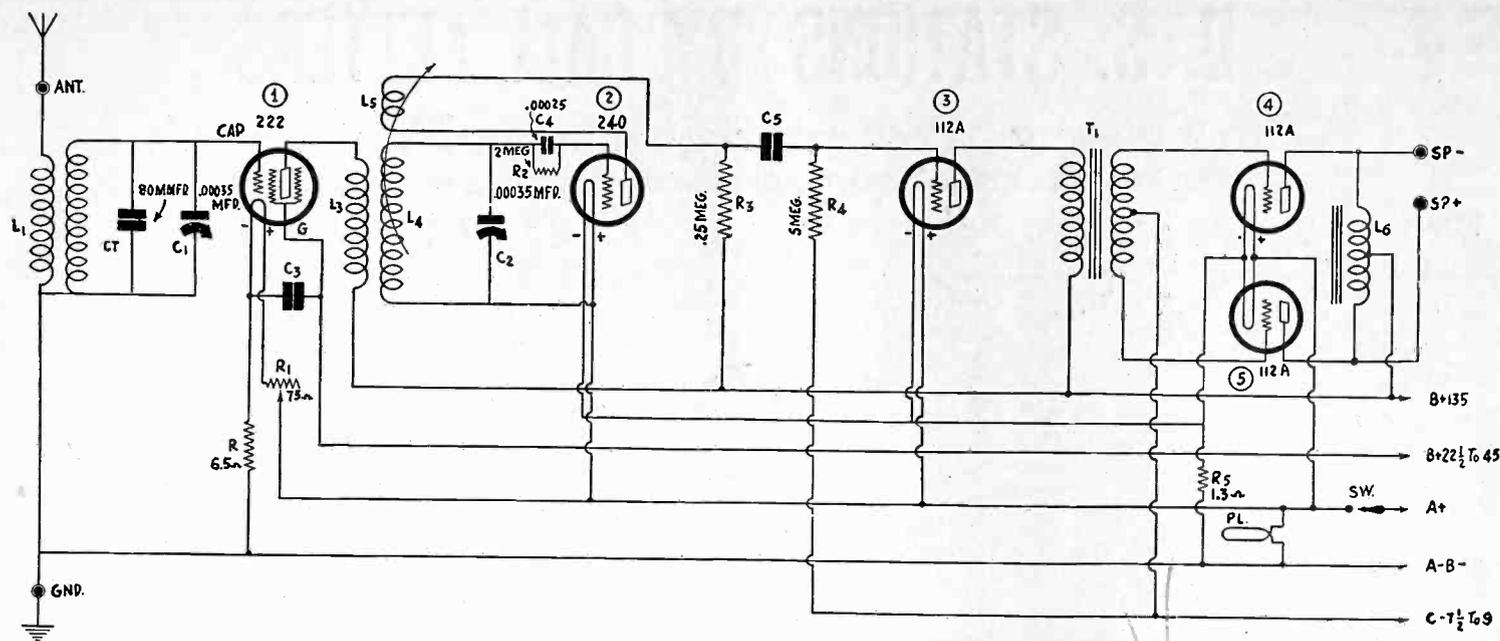


FIG. 815 FOR THE RECEPTION OF LOCAL STATIONS WITH GOOD QUALITY AND PLENTY OF LOUDSPEAKER VOLUME THIS CIRCUIT HAS BEEN FOUND TO GIVE COMPLETE SATISFACTION

resistance in each case is supposed to be 100,000 ohms and the internal resistance of the tube 40,000 ohms. A similar reduction results in the detector, except that it is greater.

MICROPHONIC NOISES

MY RECEIVER is very sensitive to mechanical jars and shocks, and it is very annoying because the set sings out even when the people above me walk around with a heavy step. Can you suggest a remedy for this condition?—H. J. G.

In most instances this trouble can be cured by simply putting in a different detector tube, one which is not so sensitive. The sensitivity is usually due to some structural defect in the tube, or a break in the grid support. In less severe cases it may be the first audio amplifier which is at fault, and the cure is the same. The trouble can often be ameliorated by loading the weak tube with a lead cap so that it will not vibrate so easily. However, there is no better way than to replace the tube. If jars in the building are transmitted to the receiver rubber buffers will help, or the receiver may be placed on a carpet.

CONDENSERS BREAK DOWN

I HAVE tried several electrolytic condensers in my power pack, but all have been defective. I am now wondering whether it is possible to get one that is all right. Surely if so many condensers are defective there is a structural weakness which accounts for the trouble.—P. C. C.

The probability is that all the electrolytic condensers you have tried have been all right. Not many of these condensers are defective. The trouble usually is that the voltage applied across the condensers is higher than the rated voltage. Keep the voltage below this level and there will be no trouble. When the rated voltage is exceeded the condenser acts as if short-circuited, often causing a sputtering sound in the loudspeaker.

FILAMENT CURRENT INTERMITTENT

I HAVE A filament current supply in which a dry type rectifier is used. At first the filament current was steady and the operation of the receiver entirely satisfactory, but lately the filament current has been quite irregular. The volume from the set, of course, has fluctuated sympathetically. What is the matter with the rectifier and how can it be remedied?—P. S. W.

The rectifier wears out in time, often in a short time, and the only remedy is to replace it with a new one. At least that is the simplest way of overcoming the trouble. If a rectifier unit wears out in a very short time you must overload it, that is, draw too much current from it. Perhaps you have to break the circuit up so that you can use two of the rectifier elements in parallel. That would be more economical than to overload a single one and overload it all the time.

TRAVELER WANTS LOUDSPEAKER

I AM TRAVELING from place to place with an amplifier and loudspeaker, setting the equipment up a few days or a week at a time. For traveling I need a light speaker but still I want something capable of good quality. Can you suggest a speaker that is comparatively light and of good quality?—J. J. O'B.

The lightest speaker capable of good quality is an inductor dynamic and it would seem that that would be suitable for the purpose. A further reduction in the weight of the equipment could be effected by using resistance coupling in the audio amplifier in place of the usual transformer coupling. Transformers

capable of good quality are usually very heavy, especially compared with resistance couplers.

RECEIVER FOR LOCAL STATIONS

I AM LOOKING for a simple receiver to be used exclusively for the reception of local station. It should not have more than two tuners but the audio frequency amplifier should be capable of very good quality. I would prefer a push-pull output stage suitable for use with an inductor speaker.—E. D. S.

Fig. 815 seems to fill your requirements. The resistance coupler between the detector and the first audio tube insures good quality up to the first amplifier and the push-pull coupler following carries on to the loudspeaker. Of course, the quality depends largely on how good the push-pull coupling transformer and the center-tapped output choke are.

Join

Radio World's

UNIVERSITY CLUB

And Get Free Question and Answer Service for the Coming 52 Weeks. This Service for University Subscribers Only

Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below. Your name will be entered on our subscription and University Club lists by special number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your queries. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

NO OTHER PREMIUM GIVEN WITH THIS OFFER

[In sending in your queries to the University Department please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City. Enclosed find \$6.00 for RADIO WORLD for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name

Street

City and State.....

U. S. STATIONS BY CALL LETTERS

With Location, Power, Frequency and Wavelength

FROM FEDERAL RADIO COMMISSION, AS CORRECTED TO DECEMBER 12TH

[The transmitter location of each station is given, but where the studio is located in some other city or town, the studio location is given also, designated by the letter "S." Where two different powers are given, the larger is usually for daylight use only. "Kc" stands for frequency in kilocycles, "kw" for power in kilowatts, "M" for wavelength in meters.]

Station	Transmitter	Power	k.	M.	Station	Transmitter	Power	k.	M.
WEHC	Emory, Va.	100	1370	218.8	WJSV	Mt. Vernon Hills, Va.	10kw.	1460	205.4
WEHS	Evanston, Ill.	100	1500	199.9	WJW	Mansfield, Ohio (Formerly WLBV.)	100	1210	247.8
WELK	Phila., Pa.	100	1370	218.8	WJZ	Bound Brook, N. J. S-New York City, N. Y.	30kw.	760	394.5
WEMC	Berrien Springs, Mich.	1kw.	590	508.2	WKAQ	San Juan, P. R.	500	890	336.9
WENR	WBCN-Chicago, Ill.	50kw.	470	344.6	WKAR	San Juan, P. R.	1kw.	1040	288.3
WEVD	Forest Hills, N. Y. S-New York City	500	1300	230.6	WKAV	Laconia, N. H.	100	1310	228.3
WEW	St. Louis, Mo.	1kw.	760	394.5	WKBB	Joliet, Ill.	100	1310	228.3
WFAA	Dallas, Texas	10kw.	800	374.5	WKBC	Birmingham, Ala.	100	1310	228.3
WFAN	Philadelphia, Pa.	500	610	491.5	WKBF	Indianapolis, Ind.	500	1400	214.2
WFBC	Knoxville, Tenn.	50	1200	249.9	WKBH	La Crosse, Wis.	1kw.	1380	217.3
WFBG	Atoona, Pa.	100	1310	228.3	WKBI	Chicago, Ill.	50	1500	199.9
WFBJ	Collegeville, Minn.	100	1370	218.8	WKBN	Youngstown, Ohio	500	570	526
WFBY	Syracuse, N. Y.	750	900	331.1	WKBO	Jersey City, N. J.	250	1450	206.8
WFBM	Indianapolis, Ind.	1kw.	1230	243.8	WKBP	Battle Creek, Mich.	50	1420	211.1
WFBP	Baltimore, Md.	250	1270	236.7	WKBO	New York, N. Y.	250	1350	221.1
WFDF	Flint, Mich.	100	1310	228.3	WKBS	Galesburg, Ill.	100	1310	228.3
WFT	Philadelphia, Pa.	500	560	535.4	WKBP	Amersville, Ind.	100-150	1500	199.9
WFTW	Hopkinsville, Ky.	1kw.	940	319	WKBW	Amherst, N. Y. S-Buffalo, N. Y.	5kw.	1470	204
WFJC	Akron, Ohio	500	1450	206.8	WKBZ	Ludington, Mich.	50	1500	199.9
WFKD	Wissinoming, Pa. S-Philadelphia, Pa.	50	1310	228.3	WKEN	Grand Island, N. Y. S-Buffalo, N. Y.	1kw.	1040	288.3
WFLA	WSUN-Clearwater, Fla.	2 1/2kw.	900	331.1	WKJC	Lancaster, Pa.	100	1200	249.9
WFLA	Lancaster, Pa.	15	1310	228.3	WKRC	Cincinnati, Ohio	500	550	545.1
WGBB	Freeport, N. Y.	100	1210	247.8	WKY	Oklahoma City, Okla.	1kw.	900	331.1
WGBC	Memphis, Tenn.	500	1430	209.7	WLAC	Nashville, Tenn.	5kw.	1490	201.2
WGBF	Evansville, Ind.	500	630	475.9	WLAP	Louisville, Ky.	30	1200	249.9
WGBI	Scranton, Pa.	250	880	340.7	WLB	WGMS-Minneapolis, Minn.	500	1250	239.9
WGBS	Astoria, L. I., N. Y. S-New York City	500	1180	254.1	WLB	Muncie, Ind.	50	1310	228.3
WGCM	Gulfport, Miss.	100	1210	247.8	WLB	Kansas City, Kans.	100	1420	211.1
WGCP	Newark, N. J.	250	1250	239.9	WLBG	Ettrick, Va. S-Petersburg, Va.	250	2kw.	900
WGES	Chicago, Ill.	500	1360	220.4	WLBW	Oil City, Pa.	500	1260	238
WGH	Newport News, Va.	100	1310	228.3	WLBX	L. I. City, N. Y.	100	1500	199.9
WGHP	Fraser, Mich. S-Detroit, Mich.	750	1240	241.8	WLBZ	Bangor, Maine	500	620	483.6
WGL	Fort Wayne, Ind.	100	1370	218.8	WCI	Ithaca, N. Y.	50	1210	247.8
WGMS	WLB-See WLB-WGMS				WLEX	Lexington, Mass.	500	1360	220.4
WGN	WLIB-Elgin, Ill.				WLEY	Lexington, Mass.	100-250	1420	211.1
WGR	Amherst, N. Y. S-Buffalo, N. Y.	1kw.	550	545.1	WLB	WGN-See WGN-WLIB			
WGST	Atlanta, Ga.	250	890	336.9	WLIT	Philadelphia, Pa.	500	560	535.4
WGY	S. Schenectady, N. Y.	50kw.	790	379.5	WLOE	Chelsea, Mass. S-Boston, Mass.	100-250	1500	199.9
WHA	Madison, Wis.	750	940	319	WLS	Crete, Ill. S-Chicago, Ill.	5kw.	870	344.6
WHAD	Milwaukee, Wis.	250	1120	267.7	WLSI	WDFW-See WDFW-WLSI			
WHAM	Victor Twp., N. Y. S-Rochester, N. Y.	5kw.	1150	260.7	WLTH	Brooklyn, N. Y.	500	1400	214.2
WHAP	Carlstadt, N. J. S-New York City	1kw.	1300	230.6	WLW	Mason, Ohio S-Cincinnati	50kw.	700	428.3
WHAS	Jeffersontown, Ky. S-Louisville, Ky.	10kw.	820	365.6	WLWL	Kearny, N. J. S-New York City	5kw.	1100	272.6
WHAZ	Troy, N. Y.	500	1300	230.6	WMAC	Cazenovia, N. Y.	250	570	526
WHB	Kansas City, Mo.	500	950	315.6	WMAK	Martinsville, N. Y. S-Buffalo, N. Y.	750	900	331.1
WHBC	Canton, Ohio	10	1200	249.9	WMAL	Washington, D. C.	250-500	630	475.9
WHBD	Mt. Orab, Ohio	100	1370	218.8	WMAN	Columbus, Ohio	50	1210	247.8
WHBF	Rock Island, Ill.	100	1210	247.8	WMAQ	Addison, Ill. S-Chicago	5kw.	670	447.5
WHBL	Sheboygan, Wis.	500	1410	212.6	WMAY	St. Louis, Mo.	100-250	1200	249.9
WHBQ	Memphis, Tenn.	100	1370	218.8	WMAZ	Macon, Ga.	250-500	890	336.9
WHBU	Anderson, Ind.	100	1210	247.8	WMBA	Newport, R. I.	100	1500	199.9
WHBY	West De Pere, Wis. S-Green Bay Wis.	100	1200	249.9	WMBC	Detroit, Mich.	100	1420	211.1
WHDF	Calumet, Mich.	100	1370	218.8	WMBD	Peoria Hts., Ill.	500w.-1kw.	1440	208.2
WHDH	Gloucester, Mass.	1kw.	830	361.2	WMBF	WIOD-See WIOD-WMBF			
WHDI	Minneapolis, Minn.	500	1180	254.1	WMBG	Richmond, Va.	100	1210	247.8
WHDC	WABO-Rochester, N. Y.	500	1440	208.2	WMBH	Joplin, Mo.	100-200	1420	211.1
WHFC	Cicero, Ill.	100	1500	199.9	WMBI	Addison, Ill. S-Chicago	5kw.	1080	277.6
WHIS	Bluefield, W. Va.	100	1420	211.1	WMBO	Auburn, N. Y.	100	1370	218.8
WHK	Cleveland, Ohio	1kw.	1390	215.7	WMBO	Brooklyn, N. Y.	100	1500	199.9
WHN	New York, N. Y.	250	1010	296.9	WMBR	Tampa, Fla.	100	1210	247.8
WHO	Des Moines, Iowa	5kw.	1000	299.8	WMC	Memphis, Tenn.	500-1kw.	780	384.4
WHP	Lemoyne, Pa. S-Harrisburg, Pa.	500	1430	209.7	WMCA	Hoboken, N. J. S-New York City, N. Y.	500	570	526
WIAS	Ottumwa, Iowa	100	1420	211.1	WMES	Boston, Mass.	50	1500	199.9
WIBA	Madison, Wis.	100	1210	247.8	WMMN	Fairmont, W. Va.	250-500	890	336.9
WIBG	Elkins Park, Pa.	50	930	322.4	WMP	Lapeer, Mich.	100	1500	199.9
WIBM	Jackson, Mich.	100	1370	218.8	WMRJ	Jamaica, N. Y.	10	1420	211.1
WIBO	Desplaines, Ill. S-Chicago, Ill.	1 1/2kw.	560	535.4	WMSG	New York, N. Y.	250	1350	221.1
WIBR	Steubenville, Ohio	50	1420	211.1	WMT	Waterloo, Iowa	250	600	499.7
WIBS	Jersey City, N. J.	250	1450	206.8	WNAC	WBIS-Quincy, Mass. S-Boston, Mass.	1kw.	1230	243.8
WIBU	Poynette, Wis.	100	1310	228.3	WNAD	Norman, Okla.	500	1010	296.9
WIBW	(near) Topeka, Kan.	1kw.-500w.	580	516.9	WNAT	Philadelphia, Pa.	100	1310	228.3
WIBX	Utica, N. Y.	100-300	1200	249.9	WNAX	Yankton, S. Dak.	1kw.	570	526
WICC	Easton, Conn. S-Bridgeport, Conn.	500	1190	252	WNB	Binghamton, N. Y.	50	1500	199.9
WIL	St. Louis, Mo.	100-250	1200	249.9	WNBH	New Bedford, Mass.	100	1310	228.3
WILL	Urbana, Ill.	250-500	890	336.9	WNBK	Knoxville, Tenn.	50	1310	228.3
WILM	Wilmington, Del.	100	1420	211.1	WNBO	Washington, Pa.	100	1200	249.9
WIOD	WMBF-Miami Beach, Fla.	1kw.	560	535.4	WNB	Memphis, Tenn.	500	1430	209.7
WIP	Philadelphia, Pa.	500	610	491.5	WNBW	Carbondale, Pa.	10	1200	249.9
WISN	Milwaukee, Wis.	250	1120	267.7	WNBX	Springfield, Vt.	10	1200	249.9
WJAC	Johnstown, Pa. (Formerly WHBP.)	100	1310	228.3	WNBZ	Saranac Lake, N. Y.	50	1290	232.4
WJAD	Waco, Texas	1kw.	1240	241.8	WNJ	Newark, N. J.	250	1450	206.8
WJAG	Norfolk, Nebr.	1kw.	1060	282.8	WNOX	Knoxville, Tenn.	1kw.	560	535.4
WJAK	Marion, Ind.	50	1310	228.3	WNR	Greensboro, N. C.	250	1440	208.2
WJAR	Providence, R. I.	250-400	890	336.9	WNYC	New York, N. Y.	500	570	526
WJAS	North Fayette Twp. S-Pittsburgh, Pa.	1kw.	1290	232.4	WOAI	San Antonio, Texas	5kw.	1190	252
WJAX	Jacksonville, Fla.	1kw.	1260	238	WOAN	Lawrenceburg, Tenn.	500	600	499.7
WJAY	Cleveland, Ohio	500	620	483.6	WOAX	Trenton, N. J.	500	1280	234.2
WJAZ	Mt. Prospect, Ill. S-Chicago, Ill.	5kw.	1480	202.6	WOBT	Union City, Tenn.	100-250	1310	228.3
WJBC	La Salle, Ill.	100	1200	249.9	WOBU	(near) Charleston	250	580	516.9
WJBI	Red Bank, N. J.	100	1210	247.8	WOC	Davenport, Iowa	5kw.	1000	299.8
WJBK	Ypsilanti, Mich.	50	1370	218.8	WOCL	Jamestown, N. Y.	25	1210	247.8
WJBL	Decatur, Ill.	100	1200	249.9	WODA	Paterson, N. J.	1kw.	1250	239.9
WJBO	New Orleans, La.	100	1370	218.8	WODX	Springhill, Ala. S-Mobile, Ala.	500	1410	212.6
WJBT	WBBM-See WBBM-WJBT				WOI	Ames, Iowa	5kw.	560	535.4
WJBU	Lewisburg, Pa.	100	1210	247.8	WOKO	Mt. Beacon, N. Y. S-Poughkeepsie, N. Y.	500	1440	208.2
WJBW	New Orleans, La.	30	1200	249.9	WOL	Washington, D. C.	100	1310	228.3
WJB	Gadsden, Ala.	50	1210	247.8	WOMT	Manitowoc, Wis.	100	1210	247.8
WJDX	Jackson, Miss.	500-1kw.	1270	236.1	WOOD	Furnwood, Mich. S-Grand Rapids, Mich.	500	1270	236.1
WJJD	Mooschart, Ill.	20kw.	1130	265.3	WOPI	Bristol, Tenn.	100	1500	199.9
WJKS	Gary, Ind.	500-1 1/2kw.	1360	220.4	WOQ	Kansas City, Mo.	1kw.	610	491.5
WJLR	Sylvan Lake Village, Mich. S-Detroit, Mich.	5kw.	750	399.8					

(Continued on next page)

Station	Transmitter	Power	kc.	M.	Station	Transmitter	Power	kc.	M.	Station	Transmitter	Power	kc.	M.
WOR	Kearny, N. J.				KFIF	Portland, Ore.	100	1420	211.1	KNX	Los Angeles, Calif.			
	S-Newark, N. J.	5kw.	710	422.3	KFIO	Spokane, Wash.	100	1230	243.6		S-Hollywood, Calif.	5kw.	1050	285.5
WORC	Auburn, Mass.				KFIZ	Fond du Lac, Wis.	100	1420	211.1	KOA	Denver, Colo.	12½kw.	830	361.2
	S-Worcester, Mass.	100	1200	249.9	KFJB	Marshalltown, Iowa	100	1200	249.9	KOAC	Corvallis, Ore.	1kw.	550	545.1
	(formerly WKBE)				KFJF	Oklahoma City, Okla.	5kw.	1470	204	KOB	State College, New Mexico	10kw.	1180	254.1
WORD	Batavia, Ill.				KFJI	Astoria, Ore.	100	1370	218.8	KOCW	Chickasha, Okla.	250&500	1400	214.2
	S-Chicago, Ill.	5kw.	1480	202.6	KFJM	Grand Forks, N. D.	100	1370	218.8	KOH	Reno, Nev.	100	1370	218.8
WOS	Jefferson City, Mo.	500-1kw.	630	475.9	KFJR	Portland, Ore.	500	1300	230.6	KOIL	Council Bluffs, Iowa	1kw.	1260	238
WOV	Secaucus, N. J.				KFJV	Fort Dodge, Iowa	100	1310	228.3	KOIN	Sylvan, Ore.			
	S-New York City	1kw.	1130	265.3	KFJZ	Fort Worth, Texas	100	1370	218.8		S-Portland, Ore.	1kw.	940	319
WOW	Omaha, Neb.				KFKA	Greeley, Colo.	500&1kw.	880	340.7	KOL	Seattle, Wash.	1kw.	1270	236.1
WOWO	Ft. Wayne, Ind.	10kw.	1160	258.5	KFKB	Millford, Kans.	5kw.	1050	285.5	KOMO	Seattle, Wash.	1kw.	920	325.9
WPAP	WQAO-See WQAO-WPAP				KFKU	Lawrence, Kans.	1kw.	1220	245.8	KOOS	Marshfield, Ore.	50	1370	218.8
WPAW	Pawtucket, R. I.	100	1210	247.8	KFKX	KYW-See KYW-KFKX				KORE	Eugene, Ore.	100	1420	211.1
WPC	Chicago, Ill.	500	535.4		KFLV	Rockford, Ill.	500	1410	212.6	KPCB	Seattle, Wash.	50	1210	247.8
WPCB	Hoboken, N. J.				KFLX	Galveston, Texas	100	1370	218.8	KPJM	Prescott, Ariz.	100	1500	199.9
	S-New York City	500	810	370.2	KFMX	Northfield, Minn.	1kw.	1250	239.9	KPO	San Francisco, Calif.	5kw.	680	440.9
WPEN	Philadelphia, Pa.	100-250	1500	199.9	KFNF	Shenandoah, Iowa	500&1kw.	890	336.9	KPOF	Denver, Colo.	500	880	340.7
	(formerly WPSW)				KFOR	Lincoln, Nebr.	100&250	1210	247.8	KPPC	Pasadena, Calif.	50	1200	249.9
WPG	Atlantic City, N. J.	5kw.	1100	272.6	KFOX	Long Beach, Calif.	1kw.	1250	239.9	KPO	Seattle, Wash.	100	1210	247.8
WPOE	Patchogue, N. Y.	30-100	1420	211.1	KFPL	Dublin, Texas	15	1310	228.3	KPRC	Sugarland, Texas			
WPOR	WTAR-See WTAR-WPOR				KFPM	Greenville, Texas	15	1310	228.3		S-Houston, Texas	1kw&2½kw.	920	325.9
WPS	State College, Pa.	500	1230	243.8	KFPW	Siloam Springs, Ark.	50	1340	223.7	KPSN	Pasadena, Calif.	1kw.	950	315.6
WPTF	Raleigh, N. C.	1kw.	680	440.9	KFPY	Spokane, Wash.	500	1340	223.7	KPWF	Westminster, Calif.	5 to 10 kw.	1490	201.2
WQAM	Miami, Fla.	1kw.	1240	241.8	KFOA	KMOX-See KMOX-KFOA				KQV	Pittsburgh, Pa.	500	1380	217.3
WQAN	Scranton, Pa.	250	880	340.7	KFOE	Anchorage, Alaska	100	1230	243.8	KQW	San Jose, Calif.	500	1010	296.9
WQAO	WPAP-Cliffside, N. J.				KFOU	Holy City, Calif.	100	1420	211.1	KRE	Berkeley, Calif.	100	1370	218.8
	S-New York City, N. Y.	250	1010	296.9	KFQW	Seattle, Wash.	100	1420	211.1	KREP	Phoenix, Ariz.	500	620	483.6
WQBC	Utica, Miss.	300	1360	220.4	KFQZ	Hollywood, Calif.					(formerly KFAD)			
WQBZ	Weirton, W. Va.	60	1420	211.1	KFRC	San Francisco, Calif.	1kw.	610	491.5	KRGV	Harlingen, Texas	500	1260	238
WRAF	LaPorte, Ind.	100	1200	249.9	KFRU	Columbia, Mo.	500	630	475.9	KRLD	Dallas, Texas	10kw.	1040	288.3
WRAK	Erie, Pa.	50	1370	218.8	KFSD	San Diego, Calif.	500&1kw.	600	499.7	KRMD	Shreveport, La.	50	1310	228.3
WRAW	Reading, Pa.	100	1310	228.3	KFSG	Los Angeles, Calif.	500	1120	267.7	KRSC	Seattle, Wash.	50	1120	267.7
WRAX	Philadelphia, Pa.	250	1020	293.9	KFUL	Galveston, Texas	500	1290	232.4	KSAC	Manhattan, Kans.	500&1kw.	580	516.9
WRBI	Tifton, Ga.	20	1310	228.3	KFUM	Colorado Springs, Colo.	1kw.	1270	236.1	KSAT	Birdsville, Texas			
WRBJ	Hattiesburg, Miss.	10	1500	199.9	KFUO	Clayton, Mo.	500&1kw.	550	545.1		S-Fort Worth, Texas	1kw.	1240	241.8
WRBL	Columbus, Ga.	50	1200	249.9	KFUP	Denver, Colo.	100	1310	228.3		(formerly KTAT)			
WRBO	Greenville, Miss.	100	1210	247.8	KFVD	Culver City, Calif.	250	710	422.3	KSCJ	Sioux City, Iowa	1kw.	1330	225.4
WRBT	Wilmington, N. C.	100	1370	218.8	KFVS	Cape Girardeau, Mo.	100	1210	247.8	KSD	St. Louis, Mo.	500	550	545.1
WRBU	Gastonia, N. C.	100	1210	247.8	KFWB	Hollywood, Calif.	1kw.	950	315.6	KSEI	Pocatello, Idaho	250	900	331.1
WRC	Washington, D. C.	500	950	315.6	KFWF	St. Louis, Mo.	100	1200	249.9	KSL	Salt Lake City, Utah	5kw.	1130	265.3
WREC	Whitehaven, Tenn.				KFWI	San Francisco, Calif.	500	930	322.4	KSMR	Santa Maria, Calif.	100	1200	249.9
	S-Memphis, Tenn.	500&1kw.	600	499.7	KFWM	Richmond, Calif.	500&1kw.	930	322.4	KSO	Clarinda, Iowa	500	1380	217.3
WREN	Lawrence, Kans.	1kw.	1220	245.8	KFXD	Jerome, Idaho	50	1420	211.1	KSOO	Sioux Falls, S. D.	2kw.	1110	270.1
WRHM	Fridley, Minn.				KFXX	Denver, Colo.	250	630	475.9	KSTP	Westcott, Minn.			
	S-Minneapolis, Minn.	1kw.	1250	239.9	KFYJ	Edgewater, Colo.	50	1310	228.3		S-St. Paul, Minn.	10kw.	1460	205.4
WRJN	Racine, Wis.	100	1370	218.8	KFXM	San Bernardino, Calif.	100	1200	249.9	KTAB	Oakland, Calif.	1kw.	560	535.4
WRK	Hamilton, Ohio	100	1310	228.3	(formerly KFWC)					KTAP	San Antonio, Texas	100	1420	211.1
WRNY	Coytesville, N. J.				KFXX	Oklahoma City, Okla.	100	1310	228.3	KTBI	Los Angeles, Calif.	750	1320	230.6
	S-New York City, N. Y.	250	1010	296.9	KFFY	Flagstaff, Ariz.	100	1420	211.1	KTBR	Portland, Ore.	500	1300	230.6
WRR	Dallas, Texas	500	1280	234.2	KFYO	Abilene, Texas	100&250	1420	211.1	KTBS	Shreveport, La.	1kw.	1450	206.8
WRUF	Gainesville, Fla.	5kw.	1470	204	KFYR	Bismarck, N. D.	500	550	545.1	KTHS	Hot Springs Nat'l Park, Ark.	10kw.	1040	288.3
WRVA	Mechanicsville, Va.				KGA	Spokane, Wash.	5kw.	1470	204	KTM	Santa Monica, Calif.			
	S-Richmond, Va.	5kw.	1110	270.1	KGAR	Tucson, Ariz.	100	1370	218.8		S-Los Angeles, Calif.	500	780	384.4
WSAI	Mason, Ohio				KGB	San Diego, Calif.	250	1360	220.4	KTNT	Muscataine, Iowa	5kw.	1170	256.3
	S-Cincinnati, Ohio	500	1330	225.4	KGBU	Ketchikan, Alaska	500	900	331.1	KTSA	San Antonio, Texas	1&2kw.	1290	232.4
WSAJ	Grove City, Pa.	100	1310	228.3	KGBX	St. Joseph, Mo.	100	1370	218.8	KTSL	Cedar Grove, La.			
WSAN	Allentown, Pa.	250	1440	208.2	KGBZ	York, Nebr.	500&1kw.	930	322.4		S-Shreveport, La.	100	1310	228.3
WSAR	Fall River, Mass.	250	1450	206.8	KGCA	Decorah, Iowa	50	1270	236.1	KTSM	El Paso, Texas	100	1310	228.3
WSAZ	Huntington, W. Va.	250	580	516.9	KGCI	San Antonio, Texas	50	1370	218.8	KTUE	Houston, Texas	5	1420	211.1
WSB	Atlanta, Ga.	1kw.	740	405.2	KGCR	Watertown, S. D.	100	1210	247.8	KTW	Seattle, Wash.	1kw.	1270	236.1
WSBC	Chicago, Ill.	100	1210	247.8	KGCU	Mandan, N. D.	100	1200	249.9	KUIJ	Longview, Wash.	10	1500	199.9
WSBT	South Bend, Ind.	500	1230	243.8	KGCX	Wolf Point, Mont.	100&250	1310	228.3	KUOA	Fayetteville, Ark.	1kw.	1390	215.7
WSDA	WSGH-See WSGH-WSDA				KGDA	Dell Rapids, S. D.	50	1370	218.8	KUSD	Shreveport, La.	500&750	890	336.9
WSPA	Montgomery, Ala.	500	1410	212.6	KGDE	Fergus Falls, Minn.	50	1200	249.9	KUT	Austin, Texas	500	1120	267.7
WSGH	WSDA-Brooklyn, N. Y.	500	1400	214.2	KGDM	Stockton, Calif.	50	1100	272.6	KVEP	Portland, Ore.	15	1500	199.9
WSIX	Springfield, Tenn.	100	1210	247.8	KGDY	Oldham, S. D.	15	1200	249.9		(formerly KWBS)			
WSJS	Winston-Salem, N. C.	100	1310	228.3	KGEF	Los Angeles, Calif.	1kw.	1300	230.6	KVI	Des Moines, Wash.			
	(formerly WJ2Z)				KGEG	Yuma, Colo.	50	1200	249.9		S-Tacoma, Wash.	1kw.	760	394.5
WSM	Nashville, Tenn.	5kw.	650	461.3	KGER	Long Beach, Calif.	100	1370	218.8	KVL	Seattle, Wash.	100	1370	218.8
WSMB	New Orleans, La.	500	1320	227.1	KGEW	Fort Morgan, Colo.	100	1200	249.9	KVOA	Tucson, Ariz.	500	1260	238
WSMC	Dayton, Ohio	200	1380	217.3	KGEZ	Kalispell, Mont.	100	1310	228.3	KVOO	Tulsa, Okla.	5kw.	1140	263
WSOA	Deerfield, Ill.				KGFF	Alva, Okla.	100	1420	211.1	KVOS	Bellingham, Wash.	100	1200	249.9
	S-Chicago, Ill.	5kw.	1480	202.6	KGFG	Oklahoma City, Okla.	100	1370	218.8	KWCR	Cedar Rapids, Iowa	100	1310	228.3
WSPD	Toledo, Ohio	500&1kw.	1340	223.7	KGFI	Corpus Christi, Texas	100	1500	199.9	KWEA	Shreveport, La.	100	1210	247.8
WSSH	Boston, Mass.	100&250	1420	211.1	KGFL	Los Angeles, Calif.	100	1420	211.1	KWG	Stockton, Calif.	100	1200	249.9
WSUL	Iowa City, Iowa	500	600	499.7	KGFJ	Hallock, Minn.	50	1200	249.9	KWJJ	Portland, Ore.	500	1060	282.8
WSUN	WFLA-See WFLA-WSUN				KGFK	Raton, N. Mex.	50	1370	218.8	KWK	St. Louis, Mo.	1kw.	1350	221.1
WSVS	Buffalo, N. Y.	50	1370	218.8	KGFN	Ravenna, Nebr.	50	1310	228.3	KWKC	Kansas City, Mo.	100	1370	218.8
WSYR	Syracuse, N. Y.	250	570	526	KGFX	Pierre, S. D.	200	580	516.9	KWKH	Kennonwood, La.	10kw.	850	352.7
WTAD	Quincy, Ill.	500	1440	208.2	KGGC	San Francisco, Calif.	50	1420	211.1	KWLC	Decorah, Iowa	100	1270	236.1
WTAG	Worcester, Mass.	250	580	516.9	KGGF	Picher, Okla.	500	1010	296.9	KWSC	Pullman, Wash.	500	1220	245.8
WTAM	Brecksville Village, Ohio				KGGM	Albuquerque, N. Mex.	250&500	1330	245.8	KWWG	Brownsville, Texas	500	1260	238
	S-Cleveland, Ohio	50kw.	1070	280.2	KGGH	Pueblo, Colo.	250	1320	227.1	KXA	Seattle, Wash.	500	570	

Highest Grade Key Tubes at Defiant Prices!

Screen Grid Tubes

224 at \$1.43

222 at 1.18

Power Tubes

245 at 1.28

112A at .78

171A at .78

Other Tubes

227 at .90

226 at .68

280 at 1.13

201A at .53

The above constitute the nine most popular tubes used in radio today. Despite the severely low prices the Key tubes are firsts of the very first quality. Besides, there is a five-day money-back guaranty! The above tubes are manufactured under licenses granted by the RCA and its affiliated companies.

All prices are net and represent extreme discount already deducted.

228 HIGH-GRAIN DETECTOR

Increase the sensitivity of modern AC-operated circuits by substituting the new 228 AC high mu tube (large amplification), for the 227 tube otherwise used as detector in up-to-date circuits. The result is immediately obvious in the greatly increased volume. Otherwise weak, distant stations come in stronger and tone quality is improved. Simply substitute the 228 for the 227 in the detector socket only. No wiring change of any kind is required. Price, \$1.88.

GUARANTY RADIO GOODS CO., 143 West 45th St., N. Y. City. (Just East of Broadway).

Enclosed please find \$..... for which ship at once tubes marked below:

- 228 AC high mu.....\$1.88
- 224 AC screen grid.....\$1.43
- 245 AC power tube.....\$1.28
- 226 AC amplifier......68
- 227 AC det.-amp......90
- 280 AC rectifier.....\$1.13
- 222 battery screen grid.....\$1.18
- 112A power tube......78
- 171A power tube......78
- 201A battery tube......53
- Matched pair of 245s for push-pull (for both).....\$2.56
- Matched pair 171As for AC push-pull (for both).....\$1.80
- Matched pair of 112As for push-pull (for both).....\$1.80

Name

Address

City State

Put cross here if C. O. D. shipment is desired.

Canadian remittance must be by postal or express money order.

5-Day money-back guaranty

No. 9

\$21 NET

to Dealer



Tests Screen-Grid

Readrite

Set and
Tube Tester

The simplest of all testers to use. Not a switch or binding post to manipulate. The meters are all instantly interchangeable. Only one push button for grid condition. The three A.C. voltmeters are repulsion type 0-6, 0-15, 0-150. The three D.C. voltmeters have high resistance, 0-8, 0-50, 0-500. The three D. C. Milliammeters are 0-10, 0-50, 0-300. A.C. Voltmeters may be used as milliammeters for

testing rectifier tubes, thereby obtaining more accurate readings.

Case is light in weight, covered with grained leatherette, size 10 1/2" x 7 1/2" x 3 3/4". A most flexible tester, complete for present day testing and immediately adapting itself to future needs. Every service man should have the READRITE No. 9—A truly remarkable tester.—An investment usually paid for in the first few calls.

LIST PRICE NO. 9 — \$35.00 COMPLETE

Send for catalog of Readrite instruments, resistors, etc.

Readrite Meter Works,

12 College Ave.

Bluffton, Ohio

ESTABLISHED 1904

CLAROSTAT

Not just the name of a product, but the name of a service dedicated to better radio results. CLAROSTAT stands for variable and fixed resistors, volume controls, automatic line voltage ballasts, socket antennas, etc.

CLAROSTAT MFG. CO.,
291 North 6th Street Brooklyn, N. Y.

LYNCH

TUBADAPTA
For Better TONE


List Price..\$2.50

Improves reception and prolongs life of expensive power tubes. Used in last audio stage. Write for descriptive circular and complete catalogue Lynch Guaranteed Radio Products. LYNCH MFG. CO., Inc., 1775 B'way, N. Y.



Aristocrat Floor Speaker

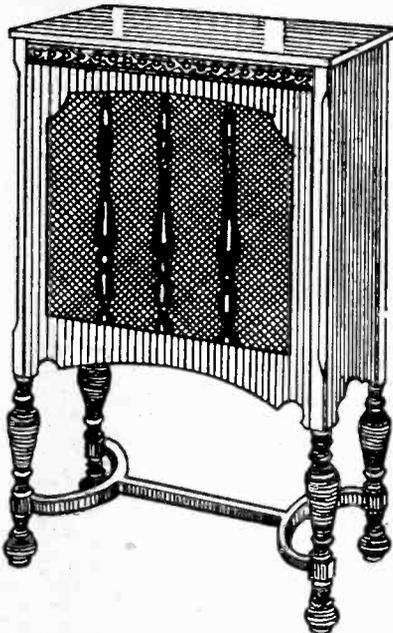With Molded Wood Horn of 6 ft. tone travel (exponential type) with baffle and horn motor built in. Extraordinary bargain. **\$14.00**



The speaker cabinet is walnut finish, 33" high, 24 1/2" wide, 17 1/2" deep, with carved legs. Golden cloth grille covers front opening. Built inside is No. 595 molded wood horn with baffle and No. 203 driving motor unit that stands 250 volts without filtration. Horn and motor removable. Table alone is worth price asked.

Shipped C.O.D. if desired.

Acoustical Engineering Associates
143 WEST 45th STREET NEW YORK CITY

Orders - Inquiries

60 pages
Send for FREE COPY
Can be Secured by MAIL

POLK'S REFERENCE BOOK and Mailing List Catalog

Gives counts and prices on over 8,000 different lines of business. No matter what your business, in this book you will find the number of your prospective customers listed. Valuable information showing how to use the mails to secure orders and inquiries for your products or services is given.

Write for FREE Copy

R. L. POLK & CO., Detroit, Mich.

Largest City Directory Publishers in the World. Branches in Principal Cities. Mailing List Compilers—Business Statisticians. Producers of Direct Mail Advertising.

NEW DRAKE'S ENCYCLOPEDIA

1,680 Alphabetical Headings from A-battery to Zero Beat; 1,025 Illustrations, 920 Pages, 240 Combinations for Receiver Layouts. Price, \$6.00. Radio World, 124 W. 45th St., N. Y. C

MICROPHONE LIGHTERS—For cigars or cigarettes, with button switch at top. Press switch, and lighter acts instantaneously. \$1.00. Model B lighter on tray, \$1.50. Radio World, 145 W. 45th St., N. Y. C.

DOING THE BEST WE CAN

Radio World has been receiving so many subscriptions of late that the Subscription Department is somewhat behind in its work. Please give us time to enter your subscription. We will enter all subscriptions as fast as we possibly can.

PUBLISHERS OF RADIO WORLD.


RADIO WORLD BOOK SERVICE

AS the first and only national radio weekly, now in its eighth year, RADIO WORLD publishes the most timely, up-to-date news of radio circuits and events in the set-building and broadcasting fields. Technical accuracy second to none. Get a copy at your news-stand today, 15c. RADIO WORLD advises impartially on all radio topics, including what text books to buy, and helps you to read the books properly. Every book advertised on this page is essential to your radio library.

Five New Volumes Offer Short-Cut to Knowledge!

MORECROFT

"Elements of Radio Communication"

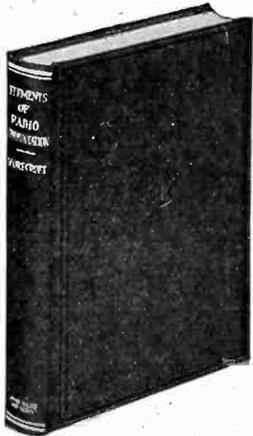

The latest book by Prof. John H. Morecroft, of the Engineering Department of Columbia University, and past president of the Institute of Radio Engineers, is his "Elements of Radio Communication," a book for the novice to enjoy. We regard this as the best elementary book to inform you authoritatively on the technical phases of radio in plain language, without requirement of mathematical knowledge. The book is a complete course on the elements of radio, containing much material never before published. It has 226 pages, 170 illustrations and a complete index. Just out, it is the book of the year in radio. Cloth bound. Order Cat. ME @\$3.00

By the same author: "Principles of Radio Communication," second (new) edition. This book is for advanced students. It is the standard of excellence in its field. It covers much the same ground as the later book, only much more fully and more technically. Contains 1,001 pages, 831 illustrations. Cloth bound. Order Cat. MP @\$7.50

MOYER and WOSTREL

"Radio Receiving Tubes"

The need for an elementary book on radio tubes that answers all the important questions has been filled by James A. Moyer, Director of University Extension, Massachusetts Department of Education, and John F. Wostrel, Instructor in Radio Engineering, Division of University Extension, Massachusetts Department of Education.

This new book is a complete discussion of tube principles, functions and uses, thoroughly up-to-date. In this book the essential principles underlying the operation of vacuum tubes are explained in as non-technical a manner as is consistent with accuracy. The book covers the construction, action, reactivation, testing and use of vacuum tubes as well as specifications for vacuum tubes and applications for distant control of industrial processes and precision measurements. 297 pages, cloth bound. Order Cat. MWT @\$2.50


By the same authors: "Practical Radio," including the testing of radio receiving sets, 378 pages, 223 illustrations. Cloth bound. Order Cat. MWPR @\$2.50
"Practical Radio Construction and Repairing," 319 pages, a companion volume. Order Cat. MWPRC @\$2.00
[NOTE: The standard book on tubes for advanced students is "The Thermionic Vacuum Tube," by Hendrik Van der Bijl. Order Cat. VDB @\$5.00]

ANDERSON and BERNARD

"Power Amplifiers"

Here is the first book to be published on the subject of "Power Amplifiers." Now printing, it is certain to fill a void in radio literature. The whole subject is fully covered in a masterful theoretical discussion of audio amplifiers and power supplies, supplemented by constructional chapters, with complete wiring diagrams and specification of parts. Learn while you build! J. E. Anderson, M. A., technical editor of RADIO WORLD, and Herman Bernard, LL. B., managing editor of RADIO WORLD, both of the Institute of Radio Engineers, have explained fully the phenomena of power amplifiers. Learn all about motorboating and its cures, push-pull theory and practice, grid bias methods and effects, vacuum tubes in audio circuits, AC and battery type AF amplifiers, phase relationships, common impedance, filter systems, by-pass condenser effects, necessities for tone quality, values of coupling constants, and a host of other topics associated with power amplification, including speech amplifiers and "talkie" installations.

More than 200 pages and more than 100 illustrations are devoted to an analysis of this outstanding radio subject. "Power Amplifiers" is authoritative, original and comprehensive. It is free from the traditional errors that have crept into this subject. The theoretical part of the book can be understood by most novices, while the constructional part, that capitalizes the previously imparted knowledge, is thoroughly understandable by anybody. There is virtually no mathematics in the book. Cloth bound. Order Cat. PAM @\$3.50

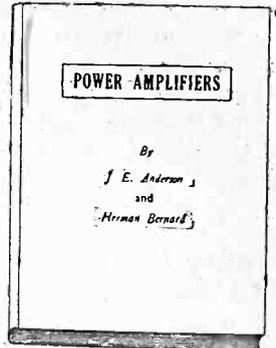

RIDER

"Service Man's Manual"

Two new books by John F. Rider, R. E., Member, Institute of Radio Engineers, constitute the series grouped by him under the heading "Service Man's Manual." Part I is "Mathematics of Radio." Part II is "Trouble Shooter's Manual."

The value of one of these books is more than doubled by the possession of the other.

"The Mathematics of Radio," 128 pages, 8 1/2 x 11", 119 illustrations, bridges the gap between the novice and the college professor. It gives a theoretical background so necessary for a proper understanding of radio and audio circuits and their servicing. Flexible cover. Order Cat. MOR @\$2.00

The first comprehensive volume devoted exclusively to the topic uppermost in every service man's mind is "Trouble Shooter's Manual," just published. It is not only a treatise for service men, telling them how to overcome their most serious problems, and fully diagramming the solutions, but it is a course in how to become a service man. It gives all the details of servicing as they have never been given before. Finding the right mode of attack, applying the remedy promptly and obtaining the actual factory-drawn diagrams of receivers always have been a big load on the service man's chest. But no more. Rider, expert on trouble shooting, has produced the outstanding volume on servicing, and has taken the load off the service man's chest!

This book is worth hundreds of dollars to any one who shoots trouble in receivers—whether they be factory-made, custom-built or home-made receivers. The home experimenter, the radio engineer, the custom set-builder, the teacher, the student—all will find this new book immensely informative and absolutely authoritative.

MORE THAN 100 WIRING DIAGRAMS OF RECEIVERS MADE BY MORE THAN FORTY DIFFERENT SET MANUFACTURERS ARE PUBLISHED IN THIS BOOK, INCLUDING OLD MODELS AND LATEST MODELS! RCA, ATWATER KENT, CROSLLEY, MAJESTIC, ZENITH, STROMBERG CARLSON, KOLSTER, FEDERAL, FADA, Etc. 240 pages, size 8 1/2 x 11"; 200 illustrations. Imitation leather cover. Order Cat. TSM @\$3.50

FREE! Read Radio World Every Week



RADIO WORLD will help you in your radio work, so you will be able to use meters most valuably. Keep abreast of new circuits, intimate details on perfecting existing sets, get inside track on sensitivity, distance reception, tonal quality, and news of radio, technical and non-technical. Enjoy the writings of McMurdo Silver, J. E. Anderson, Herman Bernard, John F. Rider and a host of other radio engineers in RADIO WORLD. You can find no magazine that better caters to your needs than RADIO WORLD. Short waves? RADIO WORLD will tell you all about them. Extremely sensitive broadcast receivers? Their construction and operation are fully discussed with confident regularity. Power supplies—push-pull or otherwise? AC receivers? Screen grid tubes? Large receivers that give a super-abundance of performance—small, economical receivers that give performance out of all comparison to their size? Are you interested in these? Then you're interested in RADIO WORLD.

See the list of nine meters at left. Obtain one or more of these meters free, by sending in \$1 for 8-weeks' subscription, entitling you to one meter; \$2 for 16 weeks, entitling you to two meters; \$3 for 26 weeks, entitling you to three meters; \$4 for 35 weeks, entitling you to four meters; \$5 for 44 weeks, entitling you to 5 meters; \$6 for 52 weeks, entitling you to six meters.

Present RADIO WORLD mail subscribers may renew their subscription under this remarkably generous offer. Put a cross in square.

RADIO WORLD

Gentlemen: Enclosed find \$..... for which please send items checked on coupon. (R -10)

145 W. 45th St., N. Y. City—Published Weekly.
All Newsstands, 15c per copy—\$3, six months—\$6 a year

- 0-6 Voltmeter D.C.....Cat. 326
- 0-50 Voltmeter D.C.....Cat. 337
- 6-Volt Charge Tester D.C.....Cat. 23
- 0-10 Amperes D.C.....Cat. 338
- 0-25 Milliamperes D.C.....Cat. 325
- 0-50 Milliamperes D.C.....Cat. 350
- 0-100 Milliamperes D.C.....Cat. 390
- 0-300 Milliamperes D.C.....Cat. 399
- 0-400 Milliamperes D.C.....Cat. 394

<input type="checkbox"/> CAT. ME @.....\$3.00	<input type="checkbox"/> CAT.....326 Name
<input type="checkbox"/> CAT. MP @.....\$7.50	<input type="checkbox"/> CAT.....337
<input type="checkbox"/> CAT. PAM @.....\$3.50	<input type="checkbox"/> CAT.....23
<input type="checkbox"/> CAT. MWT @.....\$2.50	<input type="checkbox"/> CAT.....338
<input type="checkbox"/> CAT. MWPR @.....\$2.50	<input type="checkbox"/> CAT.....325 Address
<input type="checkbox"/> CAT. MWPRC @.....\$2.00	<input type="checkbox"/> CAT.....350
<input type="checkbox"/> CAT. MOR @.....\$2.00	<input type="checkbox"/> CAT.....390
<input type="checkbox"/> CAT. TSM @.....\$3.50	<input type="checkbox"/> CAT.....399
<input type="checkbox"/> CAT. VDB @.....\$5.00	<input type="checkbox"/> CAT.....394 City..... State.....

RADIO WORLD'S BOOK SERVICE

has been found of great value not only by radio fans, constructors, etc., but also by radio and other technical schools throughout the country. See the radio books advertisements in this issue.


TRIAL SUBSCRIPTION

Send \$1 for trial subscription for 8 weeks, starting with current issue, or of any recent issue. Radio World, 145 W. 45th St., N. Y. City.

A GREAT ADVERTISING MEDIUM!

That describes Radio World. Rates on application. Radio World, 145 W. 45th St., N. Y. C


O-1 MA, \$5.95

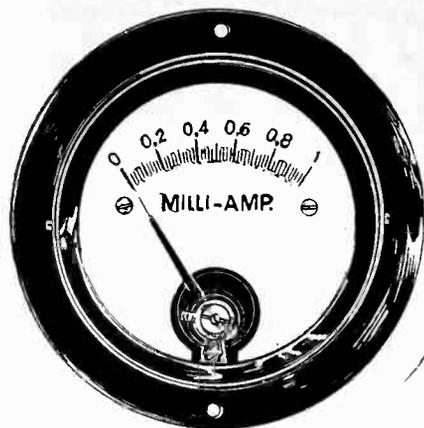

Here is a 0-1 milliammeter, accurate to plus or minus 1% clearly legible to two-one hundredths of a milliampere at any reading (20 microamperes). This expertly made precision instrument is offered at the lowest price so far for a 0-1 ma. Order Cat. FO-1 at \$5.95. C. O. D. orders accepted.

Guaranty Radio Goods Co.
143 West 45th Street,
New York City


AERIAL TUNER Improves Your Reception

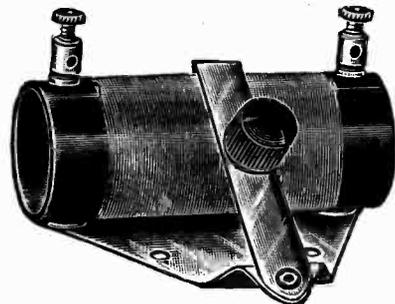

Remove aerial lead from set. Connect aerial instead to one of the binding posts of the Aerial Tuner. Connect the other binding post of the Aerial Tuner to antenna post of your set. Then move the lever of the Aerial Tuner until any weak station comes in loudest. The lever need not be moved for every different frequency tuned in. The Aerial Tuner acts as an antenna loading coil and puts the antenna's frequency at any frequency in the broadcast band that you desire to build up. Price, 85c.

GUARANTY RADIO GOODS CO.
143 West 45th Street
New York City
(Just East of Broadway)

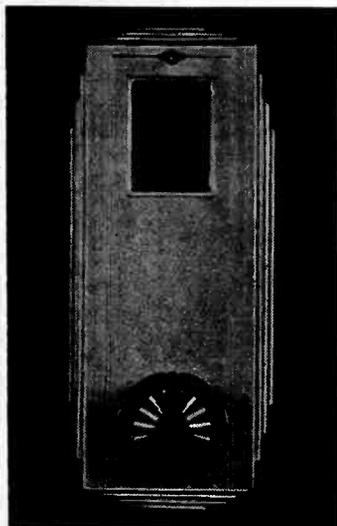BRILLIANT, NEW NATIONAL MODERNISTIC PROJECTION DIAL WITH RAINBOW FEATURE



Modernize the appearance of your receiver by installing the brilliant new National dial, with color wheel built in, so that as you turn the dial knob one color after another floods the screen on which the dial numbers are read. On this screen the numbers are projected, so that you get the same dial reading from any position of the eye. This is just what DX hunters want—laboratory precision of dial reading.

The escutcheon is of modernistic design. The Velvet Vernier mechanism drives the drum superbly. Order today. Remit with order and we pay cartage. Shipments day following receipt of order.

GUARANTY RADIO GOODS CO.
143 W. 45th St., N. Y. City (Just E. of B'way)
Enclosed please find \$3.13 for which please send me dial marked below:
 Cat. HC6, National modernistic drum dial, with color wheel built in, pilot bracket, 6-volt pilot lamp for storage battery or A eliminator sets; hardware; instructions \$3.13
 Cat. HC2½, same as above, but with 2½-volt AC pilot lamp 8.13
 Order C.O.D. and I pay cartage.

NAME
ADDRESS
CITY STATE

RADIO WORLD'S BOOK SERVICE has been found of great value not only by radio fans, constructors, etc., but also by radio and other technical schools throughout the country. See the radio books advertisements in this issue.

LACAULT'S BOOK

"Super-Heterodyne Construction and Operation," giving the master's most masterful exposition of the theory, performance and construction of this fascinating type of circuit, is a necessity to every serious radio experimenter. More than 100 pages and more than 50 illustrations. Buckram cover. This book by B. E. Laeault, FREE if you send \$1.00 for an 8-weeks subscription for Radio World. Present subscribers may accept this offer. Subscription will be extended.

RADIO WORLD 145 W. 45th St., N. Y. City
Just East of B'way

NATIONAL

Velvet B Eliminator \$16.13
180 Volts (220 Tube Free)



Latest Model National Velvet-B, Type 8880, in handsome crackle finish black metal casing, for use with sets up to and including six tubes. Input 105-120 volts AC, 60 to 60 cycles. Output, 180 volts maximum at 35 milliamperes. Three variable output intermediate voltages. (Det., RF, AF). Eliminator has excellent filter system to eliminate hum, including 50 henry choke and 18 mfd Marshon condenser. No motorboating! (Eliminator Licensed under patents of the Radio Corporation of America and associated companies.)

Guaranty Radio Goods Co.
143 W. 45TH STREET
(Just East of Broadway)
NEW YORK CITY

New Junior Model POLO UNIT \$4

The famous twin magnet principle for double sensitivity, large magnets for great flux, permanently adjusted armature, all are in the new junior model Polo Unit. Weight, 2¾ lbs. Stands 150 volts unfiltered. Stands up to 250 push-pull filtered. Works any output tube, power or otherwise. Supplied with 10-ft. cord. Order unit now. Five-day money-back guarantee. Shipped C. O. D. if desired.

Acoustical Engineering Associates
143 West 45th Street
New York City
(Just East of Broadway)

RADIO WORLD and "RADIO NEWS"

BOTH FOR ONE YEAR @ \$7.00

You can obtain the two leading radio technical magazines that cater to experimenters, service men and students, the first and only national radio weekly and the leading monthly, for one year each, at a saving of \$1.50. The regular mail subscription rate for Radio World for one year, a new and fascinating copy each week for 52 weeks is \$6.00. Send in \$1.00 extra, get "Radio News" also for a year—a new issue each month for twelve months. Total, 64 issues for \$7.00.
 If renewing Radio World subscription, put cross square.
RADIO WORLD, 145 West 45th Street, New York, N. Y.

Quick Action Classified Ads

Radio World's Speedy Medium for Enterprise and Sales

10 cents a word — 10 words minimum — Cash with Order

EDISON STORAGE BATTERIES—100 volts \$6.50; ¼ Horsepower Alternating Motors \$7.00. Hoffmann Electrical Shops, 904 North Fifth, Philadelphia, Pa.

"MATHEMATICS OF RADIO"—A great help to everybody interested in radio. \$2 postpaid. Radio World, 145 W. 45th St., N. Y. City.

RECENT NUMBERS OF RADIO WORLD, for 1929, 15c per copy. Any 7 copies for \$1. Radio World, 145 W. 45th St., N. Y. City.

TELEVISION and all about it in "A B C of Television," by Raymond Francis Yates. \$3 postpaid. Radio World, 145 W. 45th St., N. Y. City.

"EVERYBODY'S AVIATION GUIDE." By Maj. Pagé. \$2 postpaid. Also "Modern Aircraft" by same author. \$5. postpaid. Radio World, 145 W. 45th St., N. Y. City.

"A B C OF AVIATION." By Maj. Pagé. \$1.00 postpaid. Radio World, 145 W. 45th St., N. Y. City.

WORLD'S BEST AVIATION BOOKS: "A B C of Aviation," \$1.00; "Modern Aviation Engines," \$9.00 postpaid. Both by Maj. Pagé. "Aerial Navigation and Meteorology," By Capt. Yancey. \$4.00 postpaid. Radio World, 145 W. 45th St., N. Y. City.

"AERIAL NAVIGATION and METEOROLOGY." By Capt. Yancey. \$4.00 postpaid. Radio World, 145 W. 45th St., N. Y. City.

TRIAL SUBSCRIPTION, 8 WEEKS, \$1.00. Send \$1 and we will send you Radio World for 8 weeks, postpaid. **RADIO WORLD**, 145 West 45th St., N. Y. City.

EVERYTHING IN RADIO
At attractive Prices Sets or parts
Orders shipped exactly as ordered. Prompt service. Write for prices. Inquiries invited. Send your address.
ALL RADIO CO., 417 North Clark St., Chicago


BE SURE TO READ the advertisement on another page of this issue about the HB Compact. Guaranty Radio Goods Co., 143 W. 45th St., N. Y. City.

TWO FOR ONE. Radio World for 52 weeks and Radio News twelve months at the combination rate of \$7. Radio World, 145 W. 45th St., N. Y.

"MODERN AIRCRAFT," By Maj. Pagé. \$5. postpaid; and "Everybody's Aviation Guide." By Maj. Pagé, price \$2. postpaid. Latest and best up-to-date aviation books. Radio World, 145 W. 45th St., N. Y. City.

THREE CHRISTMAS GIFT BOOKS FOR SERVICE MEN!

- "Trouble Shooter's Manual"** *The most popular and fastest-selling book in radio today. Wiring diagrams of commercial receivers are contained in this outstanding book.*
 - "Mathematics of Radio"** *A sure route to a good grasp on radio technique. Radio theory outlined so that anybody can understand it.*
 - "Testing Units for Service Men"** *Circuits and Methods of Testing Equipment, particularly use of individual meters and of meters united in combination testers.*
- These Three Books by John F. Rider Constitute an Outstanding Asset to All Possessors!

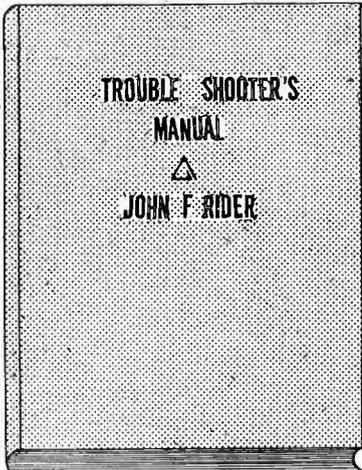

"Trouble Shooter's Manual"


is the first comprehensive volume devoted exclusively to the topic. The 240 pages include 200 illustrations devoted to wiring diagrams of factory-made receivers, besides other illustrations. It is not only a treatise for service men, telling them how to overcome their most serious problems, and fully diagramming the solutions, but is a course in how to become a service man.

This book is worth hundreds of dollars to any one who shoots trouble in receivers—whether they be factory-made, custom-built or home-made receivers.

Besides 22 chapters covering thoroughly the field of trouble shooting, this volume contains the wiring diagrams of models, as obtained direct from the factory, a wealth of hitherto confidential wiring information released for the first time in the interest of producing better results from receivers. You will find these

diagrams alone well worth the price of the book. The wiring diagrams are of new and old models, of receivers and accessories and as to some of the set manufacturers, all the models they ever produced are shown in wiring diagrams! Here is the list of receivers, etc., diagrams of which are published in this important and valuable book:

- Wiring Diagrams of All These Receivers**
- | | | |
|--|---|---|
| R. C. A.
60, 62, 20, 64, 30, 105, 51, 16, 32, 50, 25 A.C., 28 A.C., 41, Receptor S.P.U., 17, 18, 33. | ZENITH
39, 39A, 392, 392A, 40A, 35PX, 35APX, 352X, 352APX, 37A, 35P, 35AP, 352P, 352AP, 34P, 342P, 33, 34, 35, 35A, 342, 352, 352A, 362, 31, 333, 353A, power supply ZE17, power supply ZE12. | FADA
50/80A receivers, 460A, Fada 10, 11, 30, 31, 10Z, 11Z, 30Z, 31Z, 16, 17, 32, 16Z, 32Z, 19, (18, special, 192A-192S and 192BS units, R30A, 430A, and SF 50/80A receivers, 460A receiver and R60 unit, 7 A.C. receiver, 475 UA or CA and SF45-75 UA or CA, 50, 70, 71, 72, C electric unit for special and 7 A.C. receivers, ABC 6 volt tube supply, 86V and 82W, E180Z power plant and E 420 power plant. |
| FEDERAL
Type E series filament, Type E series filament, Type D series filament, Model K, Model H. | MAJESTIC
70, 70B, 180, power pack 7BP3, 7P6, 7P3 (old wiring) 8P3, 8P6, 7BP6. | FRED EISEMANN
NF5, FE18, NR70, 470, NR57, 457, NR11, NR80 D.C. |
| ATWATER-KENT
10B, 12, 20, 30, 35, 48, 32, 38, 40, 38, 36, 37, 40, 42, 52, 50, 44, 43, 41 power units for 37, 38, 44, 43, 41. | FRESHMAN
Masterpiece, equaphase, G, G-60-S power supply, L and LS, Q15, Q, K60-S power supply. | COLONIAL
26, 31 A.C., 31 D.C. |
| CROSLEY
XJ, Trirdyn 3R3, 801, 401, 401A, 608, 704, B and C supply for 704, 704A, 704B, 705, 706. | STROMBERG-CARLSON
1A, 2B, 501, 502, 523, 524, 635, 638, 403AA power plant, 404 RA power plant. | WORKRITE
8 tube chassis, 6 tube chassis. |
| STEWART-WARNER
300, 305, 310, 315, 320, 325, 800, 520, 525, 700, 705, 710, 715, 720, 530, 535, 750, 801, 802, 806. | All-AMERICAN
6 tube electric, 8 tube 80, 83, 84, 85, 86, 88, 6 tube 60, 61, 62, 65, 66, u and 8 tube A.C. power pack. | AMRAD
70, 7100, 7191 power unit. |
| GREBE
MU1, MU2, synchrophase 5, synchrophase AC6, synchrophase AC7, Deluxe 428. | DAY FAN
OEM7, 4 tube, 5-5 tube 1925 model, Day Fan 8 A.C., power supply for 6 tube A.C., B power supply 5524 and 5525, motor generator and filctr, 6 tube motor generator set, 6 tube 110 volt D.C. set, 6 tube 32 volt D.C. set. | SPARTAN
A.C. 59. |
| PHILCO
Philco-electric, 82, 86. | | MISCELLANEOUS
DeForest F5, D10, D17. Super Zenith Magnavox dial, Thermodyne, Grimes 4DL Inverse duplex, Garod neodyne, Garod EA, Ware 7 tube, Ware type T, Federal 102 special, Federal 59, Kennedy 220, Operadio portable, Sleeper RX1, Amrad inductrol. |

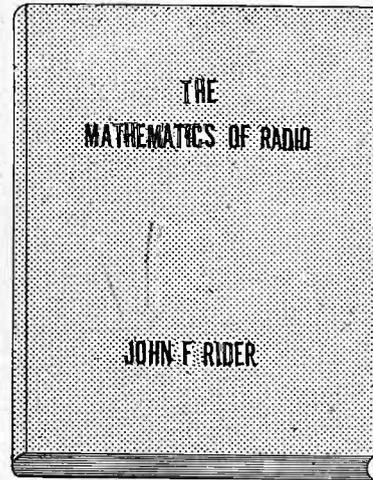

"Mathematics of Radio"

TABLE OF CONTENTS:

- OHM'S LAW.**
- RESISTANCES:** Basis for resistance variation, atomic structure, temperature coefficient, calculation of resistance variation, expression of ampere, volt and Ohm fractions, application of voltage drop, plate circuits, filament circuits, filament resistances, grid bias resistances.
- DC FILAMENT CIRCUITS:** Calculation of resistances.
- AC FILAMENT CIRCUITS:** Transformers, wattage rating, distribution of output voltages, voltage reducing resistances, line voltage reduction.
- CAPACITIES:** Calculation of capacity, dielectric constant condensers in parallel, condensers in series, voltage of condensers in parallel, in series, utility of parallel condensers, series condensers.
- VOLTAGE DIVIDER SYSTEMS FOR B ELIMINATORS:** Calculation of voltage divider resistances, types of voltage dividers, selection of resistances, wattage rating of resistances.
- INDUCTANCES:** Air core and iron core, types of air core inductances, unit of inductances, calculation of inductance.
- INDUCTANCE REQUIRED IN RADIO CIRCUITS:** Relation of wavelength and product of inductance and capacity, short wave coils, coils for broadcast band, coupling and mutual inductance, calculation of mutual inductance and coupling.
- REACTANCE AND IMPEDANCE:** Capacity reactance, inductance reactance, impedance.
- RESONANT CIRCUITS:** Series resonance, parallel resonance, coupled circuits, bandpass filters for radio frequency circuits.
- IRON CORE CHOKERS AND TRANSFORMERS:** Design of chokes, core, airgap, inductance, reactance, impedance, transformers, half wave, full wave windings.
- VACUUM TUBES:** Two element filament type, electron emission, limitations, classifications of filaments, structure, two element rectifying tubes, process of rectification, tungar bulb.
- THREE ELEMENT TUBES:** Structure of tube, detector, grid bias, grid leak and condenser, amplifiers, tube constants, voltage amplification, resistance coupling, reactance coupling, transformer coupling, variation of impedance of load with frequency, tuned plate circuit.
- POWER AMPLIFICATION:** Square law, effect of load, calculation of output power, undistorted output power, parallel tubes, push-pull systems, plate resistance.
- GRAPHS AND RESPONSE CURVES:** Types of paper, utility of curves, types of curves, significance of curves, voltage amplification, power amplification, power output, radio frequency amplification.
- MULTIPLE STAGE AMPLIFIERS:** Resistance coupling, reactance coupling, tuned double impedance amplification, underlying principles, transformer coupling, turns ratio, voltage ratio, types of cores, late current limitation, grid current limitation.
- ALTERNATING CURRENT TUBES:** Temperature variation hum, voltage variation hum, relation between grid and filament, filament circuit center tap, types of AC tubes.
- SCREEN GRID TUBE:** Structural design, application, amplification, associated tuned circuits, radio frequency amplification, audio frequency amplification.

HERE ARE THE 22 CHAPTER HEADINGS


- | | |
|-------------------------------------|---|
| Servive Procedure | Trouble Shooting in "B" Battery Eliminators |
| Practical Application of Analysis | Speakers and Types |
| Vacuum Tubes | Audio Amplifiers |
| Operating Systems | Trouble Shooting in Audio Amplifiers |
| Aerial Systems | Troubles in Detector Systems |
| "A" Battery Eliminators | Radio Frequency Amplifiers |
| Troubles in "A" Eliminators | Trouble Shooting in RF Amplifiers |
| Trouble Shooting in "A" Eliminators | Series Filament Receivers |
| "B" Battery Eliminators | Testing, and Testing Devices |
| Troubles in "B" Battery Eliminators | Troubles in AC Sets |
| | Troubles in DC Sets |

"Testing Units for Service Men."

A 43-page, liberally illustrated book on testing units and circuits. Tells what equipment a service man should have and how to use it most effectively and quickly. Rapidity of operation is one of the points stressed throughout this valuable book, as a service man's time is his chief stock in trade.

CONTENTS

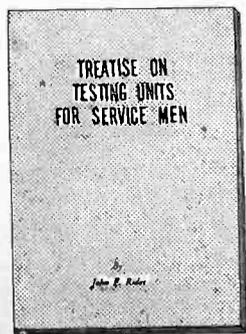- Tube Reactivator and Voltages
- Calibrated Vacuum Tube Bridge
- General Utility Tube Tester
- AC-DC Receiver Tester
- Eliminator Testers
- Signal Generator for Receiver Testing
- Oscillators
- Cathode Ray Oscillograph
- Indicating Systems
- Tube Voltmeters
- Measurement of Inductance, Impedance, Capacity, DC Resistance
- Multi-Range Meters
- Service Station Test Bench



RADIO WORLD, 145 West 45th St., New York, N. Y.
(Just East of Broadway)

Enclosed please find:

- \$3.50 for which please send me postpaid "Trouble Shooter's Manual" (Cat. TSM), by John F. Rider, 240 pages, 8 1/2 x 11", more than 200 illustrations, including wiring diagrams of commercial receivers as advertised; imitation leather cover, gold lettering.
- \$2.00 for which please send me postpaid "Mathematics of Radio" (Cat. MOR), by John F. Rider, 128 pages, 8 1/2 x 11", 119 illustrations, flexible cover.
- \$1.00 for which please send me postpaid "Treatise on Testing Units for Service Men" (Cat. TU), by John F. Rider, 43 pages, 6 1/2 x 9 1/2".
- If ordering C.O.D., put cross in this square.

NAME.....

ADDRESS.....

CITY..... STATE.....

[Canadian remittances must be made by postal or express money order.]

SPECIAL CHRISTMAS SUBSCRIPTION BLANK

Send him Radio World for 52 issues as a Christmas present, a constant reminder throughout the year of your thoughtfulness.

Radio World
145 W. 45th St., N. Y. City

Enclosed find \$....., for which please enter annual subscription for Radio World to the names and addresses at the righthand side:

Subscription Price

\$6.00 a year (52 issues); \$6.50 to Canada and \$7.00 to foreign countries.

Sent By:

Street No.

City and State

Name

Street or R. F. D.

Town State


Name

Street or R. F. D.

Town State

CONE ASSEMBLY WITH DOUBLE MAGNET UNIT

\$4.95

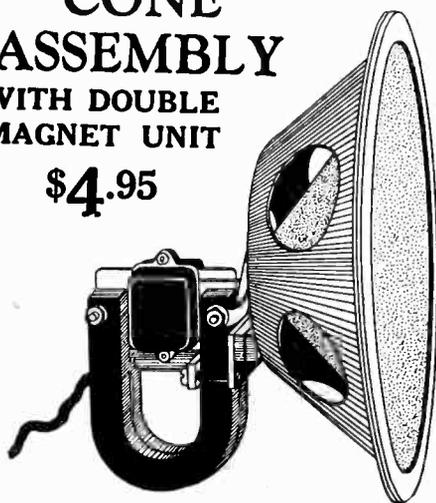


An excellent magnetic type speaker for installation in any cabinet. The unit is a double-magnet Paratone, with two magnet coils, for utmost sensitivity. Each horseshoe magnet is 3/4" thick. The magnet coils are forever protected against dust and other foreign, injurious substances, by special bakelite housings. The pin is reverse drive. The cone frame is metal. The 9" cone is specially treated buckram.

All assembled, with long cord, ready to play. Shipping weight 6 lbs. **\$4.95** (Cat. CAS) Net

The unit alone (cord included). It will operate any type sounding surface, including paper, cloth, wood, etc. Shipping weight 4 lbs. (Cat. UA) **\$2.95** Net

Guaranty Radio Goods Co.
145 West 45th St., New York City

NEWEST BOOK ON VACUUM TUBES

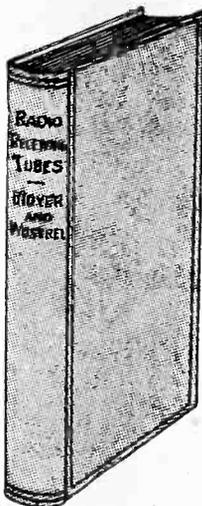

"RADIO RECEIVING TUBES," by James A. Moyer and John F. Wostrel, first edition just off the press. No radio service man, experimenter or student of radio should be without this authoritative book on the principles and applications of vacuum tubes. It answers all your questions relating to receiving, amplifying and rectifying tubes. It is a complete discussion of tube principles, functions and uses, thoroughly up-to-date.

In this book the essential principles underlying the operation of vacuum tubes are explained in as non-technical a manner as is consistent with accuracy. The book covers the construction, action, reactivation, testing and use of vacuum tubes as well as specifications for vacuum tubes and applications for distant control in industrial processes and precision measurements.

Price **\$2.50**

RADIO WORLD


145 West 45th Street, New York City
(Just East of Broadway)

PLEASE GIVE US TWO WEEKS

for changing your address, showing new renewal expiration date, etc. Subscription orders are arriving in such large numbers that it takes two weeks to effectuate the change. **RADIO WORLD**, 145 West 45th St., N. Y. City.

SEPARATE TESTER COMBINATION

Consists of two-meter assembly in neat black metal case, with an external high resistance meter. The two meters in the case read (a) 0-20, 0-100 milliamperes; (b) 0-10 volts, AC or DC, same meter reads both. The external high resistance meter reads 0-600 volts, AC or DC (same meter reads both). Thus you can test any plate current up to 100 ma., any filament voltage, AC or DC, up to 10 V., and any plate voltage, or line voltage or other AC or DC voltage, up to 600 volts. Five-prong plug, screen grid cable, and 4-prong adapter included. Order Cat. ST-COMB @.....\$11.00 2-meter assembly, cable plugs, Cat. 215 @ \$7.00 0-600 AC-DC meter alone, Cat. M600 @ \$4.95

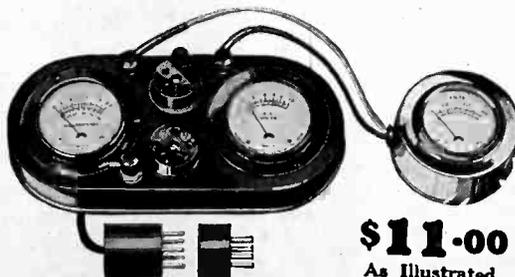

\$11.00
As Illustrated

Guaranty Radio Goods Co., 143 West 45th St., N. Y. City

Multi-Tap Voltage Divider

TWO rugged, expertly engineered wire-wound, enamelled resistors, mounted in series, one atop the other, with fourteen useful lugs, providing all necessary choice of voltages without the uncertainty of adjustable variable resistance.

The Multi-Tap Voltage Divider has a total resistance value of 13,850 ohms, in the following steps: 3,000, 4,500, 2,000, 800, 700, 600, 550, 500, 450, 400, 200, 100 and 50 ohms. With the zero voltage lug the total number of useful lugs is fourteen. The resistances stated are those between respective lugs and are to be added together to constitute 13,850 ohms total.

A conservative rating of the Multi-Tap Voltage Divider is 50 watts, continuous use. The unit is serviceable in all installations where the total current drain does not exceed 125 milliamperes.

Extreme care has been exercised in the manufacture of the Multi-Tap Voltage Divider. It is mounted on brackets insulated from the resistance wire and that afford horizontal mounting of the unit on baseboards and subpanels.

There long has been a need for obtaining any necessary intermediate voltage, including all biasing voltages, from a Multi-Tap Voltage Divider, but each lug has to be put on individually by hand, and soldered, so that manufacturing difficulties have left the market barren of such a device until now.

The Multi-Tap Voltage Divider is useful in all circuits, including push-pull and single-sided ones, where the current rating of 125 milliamperes is not seriously exceeded and the maximum voltage is not more than 400 volts. If good ventilation is provided, this rating may be exceeded 15 per cent.

The expertness of design and construction will be appreciated by those whose knowledge teaches them to appreciate parts finely made.

When the Multi-Tap Voltage Divider is placed across the filtered output of a B supply which serves a receiver, the voltages are in proportion to the current flowing through the various resistances. If a B supply feeds a receiver with two-stage audio amplifier, the last stage a single-sided 245, then the voltages would be 250 maximum for the power tube, 180, 135, 75, 50, 40, 35, 30, 25, 16, 10, 6 and 3. By making suitable connection of grid returns the lower voltages may be used for negative bias or even for positive voltage on the plates.

If push-pull is used, the current in the biasing section is almost doubled, so the midtap of the power tubes' filament winding would go to a lug about half way down.

Order Cat. MTVD at \$3.95.

Polo Engineering Laboratories,
143 W. 45th St., N. Y. City.

Gentlemen: Enclosed please find \$3.95 for which please send at once one Multi-Tap Voltage Divider, 13,850 ohms, 14 taps, mounted on brackets, 50 watt rating; Cat. MTVD.

Name

Address

CityState

Blueprint FREE!

Get a free blueprint of either circuit listed on the coupon below, by sending \$1.00 for eight weeks' subscription for RADIO WORLD, or send \$1.50 for 13 weeks' (quarter of a year) and get both blueprints free!

RADIO WORLD, 145 W. 45th St., N. Y. City
Enclosed please find:

- \$1 for which send RADIO WORLD for 8 weeks and send free blueprint of the battery model 4-tube Screen Grid Diamond of the A1.
- \$1 for which send RADIO WORLD for 8 weeks and send free blueprint of the 4-tube AC Screen Grid Diamond of the A1.
- \$1.50 for which send RADIO WORLD for 13 weeks and send both blueprints free. (If renewing a subscription put cross here.)

NAME

ADDRESS

CITY..... STATE.....

MICROPHONE LIGHTERS

For cigars or cigarettes, with button switch at top. Press switch, and lighter acts instantaneously. \$1.00. Model B lighter on tray, \$1.50. Radio World, 145 W. 45th St., N. Y. C.



Equip Yourself Now With Necessary Meters!

To do your radio work properly you need meters. Here is your opportunity to get them at no extra cost. See the list of nine meters at left. Heretofore we have offered the choice of any one of these meters free with an 8-weeks subscription for RADIO WORLD, at \$1, the regular price for such subscription. Now we extend this offer. For the first time you are permitted to obtain any one or more of all of these meters free, by sending in \$1 for 8-weeks subscription, entitling you to one meter; \$2 for 16 weeks, entitling you to two meters; \$3 for 24 weeks, entitling you to three meters; \$4 for 32 weeks, entitling you to four meters; \$5 for 40 weeks, entitling you to 5 meters; \$6 for 48 weeks, entitling you to six meters. Return this offer with remittance, and check off desired meters in squares at left.

RADIO WORLD will help you in your radio work, so you will be able to use the meters most valuably. Keep abreast of all the new circuits, intimate details on perfecting existing sets, and get inside track on sensitivity, distance reception, tonal quality, and news of radio, technical and non-technical. Enjoy the writings of Dr. Lee De Forest, McMurdo Silver, J. E. Anderson, Herman Bernard and a host of other radio engineers who contribute their knowledge to you through the medium of RADIO WORLD, the first and only illustrated national radio weekly. You can find no magazine that better caters to your needs than RADIO WORLD. Short waves! RADIO WORLD will tell you all about them. Extremely sensitive broadcast receivers! Their construction and operation are fully discussed with confident regularity. Power supplies—push-pull or otherwise! AC receivers! Screen grid tubes! Large receivers that give a super-abundance of performance—small, economical receivers that give performance out of all comparison to their size! Are you interested in these? Then you're interested in RADIO WORLD. Present mail subscribers may renew their subscription under this remarkably generous offer. Put a cross in square.

Your Choice of These Nine Meters FREE!

<input type="checkbox"/> 0-5 Voltmeter D.C.	No. 328
<input type="checkbox"/> 0-50 Voltmeter D.C.	No. 337
<input type="checkbox"/> 0-Volt Charge Tester D.C.	No. 23
<input type="checkbox"/> 0-10 Amperes D.C.	No. 338
<input type="checkbox"/> 0-25 Milliamperes D.C.	No. 325
<input type="checkbox"/> 0-50 Milliamperes D.C.	No. 350
<input type="checkbox"/> 0-100 Milliamperes D.C.	No. 390
<input type="checkbox"/> 0-300 Milliamperes D.C.	No. 399
<input type="checkbox"/> 0-400 Milliamperes D.C.	No. 394

RADIO WORLD
145 W. 45th St., N. Y. City—Published Weekly.
All Newsstands. 15¢ per copy—\$3. six months—\$6 a year



GUARANTY RADIO GOODS CO.
143 West 45th Street, New York, N. Y.

One Tube? Two Tubes? Three Tubes? Four Tubes?

Circuits for Schoolboys—Easy to Build, Very, Very Inexpensive!

- A One Tube Receiver, parts costing \$4.25!
 - A Two Tube Audio Amplifier, parts costing \$5.23!
 - A Three Tube Speaker—Operating Circuit, parts costing \$11.10!
 - A Four Tube Speaker—Operating Circuit, parts costing \$12.72!
- The construction of these circuits, with a pictorial diagram as one of the illustrations, was described by Jack Tully, himself a schoolboy, in RADIO WORLD. See list below.
- Sept. 21st and 28th issues, One-Tube DX Set, by Jack Tully; two-part article.
 - Oct. 5th, Three-Tube Single Dial Speaker Set, by Jack Tully.
 - Oct. 12th, Two Stage Transformer, Coupled Audio Amplifier, by Jack Tully.
 - Oct. 19th, Four-Tube DX Speaker Set, by Jack Tully. 15 cents a copy. Order at once while these copies are available.

RADIO WORLD, 145 W. 45th St., New York

Blueprint of the New One-Dial

Push-Pull Battery Model SG DIAMOND

Full-sized picture diagram of the wiring, with list of parts. This 5-tube receiver is really superlative. It gives you screen grid radio frequency amplification and push-pull output, most economically.

Send \$1.00 today for this blueprint or order it shipped C. O. D.

RADIO WORLD

145 West 45th Street
Just East of Broadway New York City

EVERY WEEK in RADIO WORLD appears a feature article of intense interest to schoolboys. Parents and other relatives will bring great delight to youngsters by sending \$3 for a 6 months' subscription for RADIO WORLD (26 issues) in the youngster's name.—RADIO WORLD, 145 West 45th Street, New York City.

SUBSCRIBE NOW!

RADIO WORLD, 145 West 45th St., New York City. Enclosed please find my remittance for subscription for RADIO WORLD, one copy each week for specified period:

- \$6 for one year, 52 issues.
- \$3 for six months, 26 issues.
- \$1.50 for three months, 13 issues.
- This is a renewal of an existing mail subscription (Check off if true).

Your name

Address

City

LACAULT'S BOOK

GIVES YOU A FINE UNDERSTANDING OF the SUPER-HETERODYNE

R. E. LACAULT, E.E., I.R.E., who died recently, was one of the outstanding authorities on the Super-Heterodyne. He wrote a book, "Super-Heterodyne Construction and Operation," that explains in a non-technical manner the phenomena associated with a Super-Heterodyne. More, it gives a clear outline of the way such a receiver functions, and naturally gives the clues to solving virtually all the troubles that may arise in a Super.

So thoroughly did Lacault do his work that he covered associated topics, thus making his book a delight on radio in general, including advice on trouble-shooting. Therefore the service man, the home experimenter, the custom set builder and the student will welcome this book.

It consists of 103 pages and includes 68 illustrations. It is bound in maroon buckram.

There are three valuable tables in the book, also. One classifies harmonics into groups, e.g., sound, radio, short waves, heat, light, chemical rays, X-rays and "unknown." Another is a trouble-shooting chart, classifying "trouble experienced" and "causes" and referring to the text for specific solutions. The third is a table for converting broadcast frequencies to wavelengths (accurate to .1 of a meter) or for converting the wavelength into frequency.

THE book begins with a comparison of alternating and direct current and proceeds to a discussion of the relation of wavelength to frequency. Then tuning is explained.

Condensers, coils, induction, vacuum tube operation and testing, earphones and speakers, rectification, oscillation, grid condenser action, modulation, grid bias detection, regeneration, beat notes, frequency changing, audio amplification, batteries, aeriads, loops, wiring, sockets, and shielding are only some of the other important topics covered.

Besides, there is an entire chapter on the construction of a Super-Heterodyne receiver, with list of parts, front, top and rear views of set, front panel layout, shield dimensional drawings, schematic diagram of wiring and picture diagrams of the top and bottom views of the subpanel.

You Can Get This Book At Once!

You will want this book not only for present reading but also for future reference. It is authoritative and highly informative. Send for it now! It's free with each order for an eight weeks' subscription for RADIO WORLD. Present subscribers may renew under this offer. Their subscriptions will be extended eight weeks. Please use coupon.

RADIO WORLD, 145 W. 45th St., N. Y. City
(Just East of Broadway)

Gentlemen: Enclosed find \$1.00. Please enter my subscription for RADIO WORLD for eight weeks at \$1.00 and send me at once one copy of R. E. Lacault's "Super-Heterodyne Construction and Operation." FREE!

I am a subscriber at present. (Check off if true.)

Name

Address

City..... State.....

5-DAY MONEY-BACK GUARANTEE

If C. O. D. desired, put cross here.

Component Parts

for
ONE-DIAL

PUSH-PULL BATTERY DIAMOND

[Check off parts you want. Each part is sold separately.]

- L1L2—Antenna coil RF3 @ \$ 0.80
 - L3L4L5—3-circuit SG coil SGT3 @..... 1.30
 - L6—Push-pull output transformer 2.83
 - T1—Push-pull input transformer 3.41
 - CT—80 mfd. equalizer35
 - C1, C2—Two .00035 mfd. ext. shafts @ 90c 1.96
 - C3, C5—Two .01 mfd. mica condensers..... .70
 - R—One 6.5 ohm filament resistor..... .25
 - R1, Sw—One 75 ohm switched rheostat.. .80
 - R2, C4—2 meg. Lynch leak, grid clip condenser51
 - R3—One .25 meg.30
 - R4—One 5.0 meg.30
 - R5—One 1.3 ohm filament resistor..... .20
 - Ant., Gnd., Sp. (+) Sp. (—)—Four posts @ .1040
 - One drilled front panel 7x18" 1.85
 - One socketed, self-bracketing metal sub-panel, all holes drilled..... 3.50
 - One National new modernistic drum dial with color wheel, pilot bracket, 6v. lamp, hardware, knob 3.13
 - Two matched knobs for rheo. and tickler @ .1836
 - Five vari-colored cable leads @ .07..... .35
 - Flexible link and insulated shaft..... .55
 - One screen grid clip..... .06
- All parts\$23.91

GUARANTY RADIO GOODS CO., 143 W. 45th St., N.Y.C.
(Just East of Broadway)

Enclosed please find \$..... for which please mail at once the parts for the Push-Pull Battery Model Diamond of the Air as checked off above.

If ordering C.O.D. put check mark here.

Name

Address


City..... State.....

TRIAL SUBSCRIPTION, 8 WEEKS, \$1.00. Send \$1 and we will send you Radio World for 8 weeks, postpaid. RADIO WORLD, 145 West 45th St., N. Y. City.

"AERIAL NAVIGATION and METEOROLOGY." By Capt. Yancey. \$4.00 postpaid. Radio World, 145 W. 45th St., N. Y. City.

0-60,0-300
HIGH RESISTANCE
DC VOLTMETER

With three 28" tipped leads built in

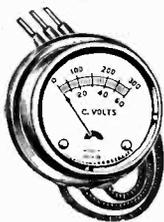

J-246 Voltmeter, for measuring all direct current voltages, including B eliminators. 0-60, 0-300 (double range).

A portable type, high resistance meter, 2 1/4" outside diameter, for close reading of direct current voltages up to 60 volts, and for reading DC voltages up to 300 volts. Three vari-colored 28" insulated leads, with jack tips, are built in. Black is minus, yellow is 60 volts maximum and red is 300 volts maximum. These voltages are marked at the meter outlets. Cat. J-246. Net price, \$2.28.

Multiplier, with jack terminals, to increase range 0-300 range to 0-600. Cat. J-106JT (with jack terminals), net price, \$1.18.

GUARANTY RADIO GOODS CO.
143 West 45th St., N. Y. City

MORECROFT

New second edition of "Principles of Radio Communication," by Prof. John H. Morecroft, of the Electrical Engineering Department of Columbia University and past president of the Institute of Electrical Engineers. This is an outstanding and authoritative book on the subject.

This large book on radio principles and practice is something that you must not be without. Every set builder, every designer, every engineer, every service man, simply must have this book. Ready reference to all intricate problems makes this volume invaluable. Set builders, experimenters, distributors, dealers, salesmen and teachers, students and operators, all find Morecroft their standby, and now the new second edition awaits you. 1,001 pages and 83" illustrations in this cloth-bound volume.

Price \$7.50

RADIO WORLD

145 West 45th Street
New York City

(Just East of Broadway)

RADIO WORLD'S BOOK SERVICE has been found of great value not only by radio fans, constructors, etc., but also by radio and other technical schools throughout the country. See the radio books advertisements in this issue.

All Parts for

HB33-\$28.33

HB44-\$46.44

THE HB33 is a three-stage screen grid radio frequency amplifier, with screen grid power detector, all shielded, 112A first audio and 112A push-pull output. Single dial control, seven-tube circuit. Price includes all parts and crinkle brown finish drilled cabinet. Order Cat. HB33 at \$28.33 (less tubes).

THE HB44 is the same fundamental circuit as the HB33 but is for AC operation. Three stages of screen grid RF, with screen grid power detector, all shielded, 227 first audio and 245 push-pull output. Single dial control 7-tube circuit and 280 rectifier, 8 all told. Price includes all parts, including power equipment, socketed subpanel (8 sockets, including one for 280 rectifier) and crinkle brown finish drilled cabinet. Order Cat. HB44 at \$46.44 (less tubes).

GUARANTY RADIO GOODS CO.

143 West 45th Street
New York, N. Y.

(Just East of Broadway)

- Remittance with order.
- Ship C. O. D.

RADIO WORLD, 145 W. 45th St., N. Y. City.
(Just East of Broadway)

- Enclosed please find \$3.00 for which please send one aluminum subpanel 10x20" for the new battery model 4-tube SG Diamond of the Air, with sockets built in, and with self-bracketing front and side and rear supports; also send hardware and insulating washers.
- Enclosed please find \$2.35 for which please send 7x21" drilled Bakelite front panel for the new battery model Diamond.
- Enclosed please find \$3.25 for the 10x20" aluminum subpanel, etc., for the new AC Screen Grid Diamond.
- Enclosed please find \$2.35 for the 7x21" drilled Bakelite front panel for the new AC Screen Grid Diamond.
- Enclosed please find \$5.00 for both the aluminum subpanel, etc., and the drilled Bakelite front panel of the battery model.
- Enclosed please find \$5.25 for both the aluminum subpanel, etc., and the drilled Bakelite front panel of the AC model.

Name

Address

City..... State.....

For That Boy at Christmas Time

Why not have us send him **RADIO WORLD** for the coming year and keep him abreast of all that is going on in radio? Besides, every week **RADIO WORLD** will carry him a message that suggests your thoughtfulness.

Also, on receipt of your \$6, we shall take pleasure in sending him a special letter to the effect that you have requested us to put his name on our subscription list for 52 issues.

Subscription Dept., **RADIO WORLD**, 145 W. 45th St., N. Y. C.

BROADWAY-HOLLYWOOD

World's most intriguing places. Where famous stage, screen, radio stars live their lives. Intimate stories of their stage and personal doings in

NEW YORK STAR National Illustrated Amusement Weekly

Edited by Roland Burke Hennessy. Clever writers cover comedy, tragedy, fascination of professional life. Portraits and unusual pictures of favorites. 10c copy, \$5 year (52 issues). **SPECIAL: 12 issues \$1 and experts answer your questions. FREE. STAR, 1562 Broadway, New York.**



Fourteen Circuits

Each Shown in Colored Picture Diagram, Colored Schematic Diagram and Front Panel Layout

Get This **FREE** Book!

Complete AC electric receivers, with B eliminators included, also AC receivers without B eliminators, also battery operated models, all easy-to-build circuits, using your own parts.

RADIO WORLD, 145 W. 45th St., N. Y. City.
(Just East of Broadway)

Gentlemen: Enclosed please find \$1.00 for which please send me **Radio World** each week for eight weeks (regular price, \$1.20) and besides send me a **FREE** copy of the 1929 edition of **The Radio Blueprint Library of AC and Battery Hookups**.

Name

Address

City..... State.....

Note: Present mail subscribers may take advantage of this offer by putting a cross in this square. Your subscription will be extended eight weeks.

[Canadian remittance must be by postal or express money order, due to high discount rate on cashing Canadian checks in New York.]

PUBLISHERS CAN SUPPLY ALL 1929 SUMMER COPIES OF RADIO WORLD

If you have missed any copies of **Radio World** for the summer of 1929 and want to complete your file, let us know what issues you are short and we will mail them to you at 15c a copy, or any seven issues for \$1.00, mailed postpaid.

Circulation Dept., **Radio World**, 145 W. 45th St., N. Y. City.

FILL OUT AND MAIL NOW

SUBSCRIPTION BLANK

RADIO WORLD

RADIO WORLD

145 West 45th Street, New York City

Please send me **RADIO WORLD** for months, for which

SUBSCRIPTION RATES:

- Single Copy.....\$.15
- Three Months..... 1.50
- Six Months..... 3.00
- One Year, 52 Issues..... 6.00
- Add \$1.00 a Year for Foreign Postage; 50c for Canadian Postage.

please find enclosed

Surpassing Results from HB Compact!

Screen Grid Circuit for AC or Battery Operation Is a Knockout!

THE screen grid tubes, both AC and battery types, 222 and 224, promised much. They could be used to provide actual amplification of 150 per stage, as compared with 8 per stage for a general purpose tube. If only the screen grid tube could be used at full practical amplification! Then a few tubes would do the work of many! At radio frequencies it was found that tuning the plate circuit put the mule kick into the set.

Sensitivity

But the whole wave band could not be tuned in. So Herman Bernard invented a coil—the Bernard dynamic tuner—that accomplished the trick. Full amplification plus full wave-band coverage! That's why his HB Compacts, only four tubes (plus a 280 in the AC model) perform like eight-tube sets! The sensitivity is incredibly high.

It would be far short of an accomplishment to hook indifferent audio onto a grid leak-condenser detector. So in both models he used a power detector, two resistance audio stages producing undistorted volume exceeding that of any ordinary two-stage audio amplifier, amplification sufficient to load up the power tube in each instance. And in the case of the AC model HB Compact it is a 245, with 1,600 milliwatts maximum undistorted power output, standing enough gaff for a small hall! And what tone realism! Breath-taking! Nothing in radio ever excelled this tone quality! Nothing! Absolutely nothing!

Realism

As the prices quoted in the list of component parts show, these advantages may be obtained economically. The battery model draws only 21 milliamperes of plate current, .664 amperes of filament current. Large B batteries would last a year at that rate, for average use, and a small A battery require recharging only every two months to ten weeks!

And this amazingly sensitive, most thrilling and utterly economical circuit gives you all the selectivity you will require, unless you live close to a powerful broadcasting station. So you get a super-abundance of results, in an unusual but thoroughly tried and tested, positively proven circuit!


HB Compact, battery model, uses a 222 RF amplifier, a 240 (high mu) power detector, a 222 first audio and a 112A or 171A power tube. The RF tube's plate circuit is tuned by a new type coil that has a moving segment as part of the tuned inductance, with step-up ratio to untuned detector grid. The audio is resistance-coupled. A 7x14" front panel may be used, with baseboard, but the HB Compact Steel Cabinet, decorated brown, with satin aluminum subpanel, sockets affixed, is recommended.

Selectivity

HB Compact, AC model, uses a 224 RF amplifier, a 224 space charge power detector, a 224 first audio and a 245 output tube, with 280 rectifier. Except for the space charge feature, not suitable in the battery model, and the larger power tube, not economically powered by batteries, the two models are fundamentally the same. The AC model is still more sensitive, however.

The same steel cabinet is recommended for the AC model, while the aluminum subpanel has the five sockets affixed and the type of each tube (except detector) printed on each socket.

Order what individual parts you want.

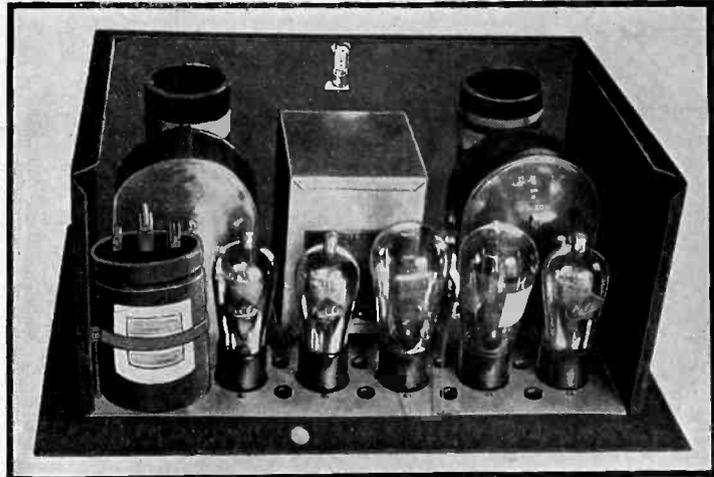

View of the HB Compact AC Model, the tubes being, left to right 224 detector, 224 first AF, 245 power tube, 280 rectifier and 224 BF. The subpanel is only 9 1/2 x 14 1/4", yet everything save the speaker is in this small space!

Component Parts for HB Compacts

AC MODEL

L1L2L3—Bernard Antenna Tuner BT5A.....	\$2.50
L4L5L6—Bernard Interstage Tuner BT5B	2.50
CT—One 80 mmfd. equalizer35
C1, C2—Two .0005 Dustproof @ \$2.50.....	5.00
C3, C4, C5—Four .01 mfd. @ .35.....	1.40
C7—One 1 mfd. 500V AC85
C8, C9, C10, C11—Merphon Q2-8, 2-18B	5.15
C12, C13—Two 1 mfd. 200 V. DC @ .50.....	1.00
R—One 25,000 ohm wire-wound pot.....	1.50
R1, R2, R3, R4—5, 1.0, .05 5.0 meg. @ .35.....	1.40
T1—Polo 245 Power Supply Cat. P245PS.....	10.00
2500, 4400, 774, 50, 8 (20 watt) Voltage Divider.....	1.75
PL—Bracket and 2.5 v. AC lamp.....	.70
OC, C6—Output choke, 2 mfd. 500 v. AC cond.	3.85
SP—, SP+—Two binding posts @ .10.....	.20
Three National grid clips @ .06.....	.18
F—One 1 amp. cart. fuse with base.....	.50
Aluminum socketed subpanel, 9 1/2 x 14 1/4", 8 brackets.....	3.25
Steel cabinet, crackled brown finish, 7 x 15 x 9 1/2.....	4.00
3 Insulating washers @ .0309
Two full-vision dials with pointers @ 75c.....	1.50
One AC pendant switch, double opening.....	.40
One 12 ft. length AC cable72
Two rolls Corwico braidite @ .3570
Two flexible couplers (links) @ .35.....	.70
	\$50.19

Kelly tubes: Three 224 @ \$3, one 245 @ \$2.25, one 280 @ \$1.75.....\$13.00

BATTERY MODEL

L1L2L3—One Bernard Tuner for antenna circuit, for .0005 mfd. tuning (BT5A of Screen Grid Coil Co.)	\$2.50
L4L5L6—One Bernard Tuner for screen grid interstage coupling, for .0005 mfd. tuning (BT5B of Screen Grid Coil Co.).....	2.50
C1, C2—Two .0005 mfd. Dustproof tuning condensers @ \$2.50.....	5.00
CT—One Hammarlund 80 mmfd. equalizing condenser.....	.35
C3, C4, C5—Three .01 mfd. mica fixed condensers @ .35.....	1.05
R1—One .25 meg. metallized resistors.....	.30
R2, R4—Two 5.0 meg. metallized resistors @ .30.....	.60
R3—One .075 meg. metallized resistor40
R5, SW—One 75-ohm rheostat with switch attached.....	.80
R6—Two resistors, one 1.3 ohms, the other 6.5 ohms (both).....	.45
Ant., Gnd., Sp.—, Sp.—. Four binding posts (all).....	.40
One drilled steel cabinet 7" high, 9 1/2" front to back, 15" wide.....	4.00
Two dials with pointers (both).....	1.50
One pilot light bracket with 6-volt DC lamp.....	.70
One 9 1/2 x 14 1/4" satin finish aluminum subpanel with sockets affixed, and supplied with insulated bushings, supporting brackets, and resistor clips	2.00
Two insulated links (flexible couplers) (both).....	.70
One 7-lead battery cable50
	\$23.75

Kelly tubes: Two 222, one 240, one 112A or 171A, total, \$9.20.

[The HB Compacts were designed and built by Herman Bernard. The battery model was described in the August 24th, 31st, September 7th and 14th issues of Radio World.]

Please Use This Coupon


GUARANTY RADIO GOODS CO.
143 West 45th St., N. Y. City, Just E. of B'way.

Enclosed please find \$..... for which please send me component parts for the HB Compact as checked off above.

NAME

ADDRESS


CITY..... STATE.....

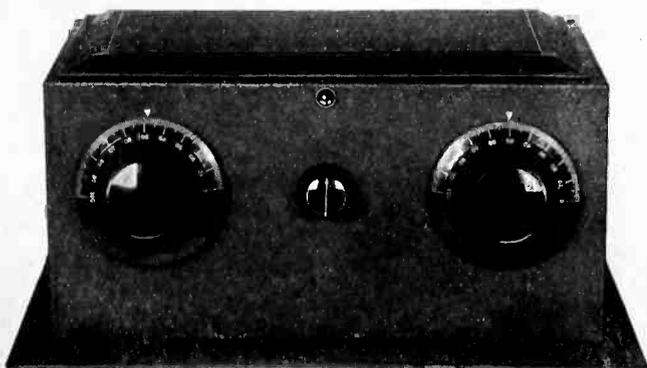

Front view of the HB Compact. The view is the same for AC or battery model. For batteries the switch is built in the rheostat. For AC a pendant switch is used at rear, in the AC cable.



NEW J-245-X TROUBLE-SHOOTING JIFFY TESTER

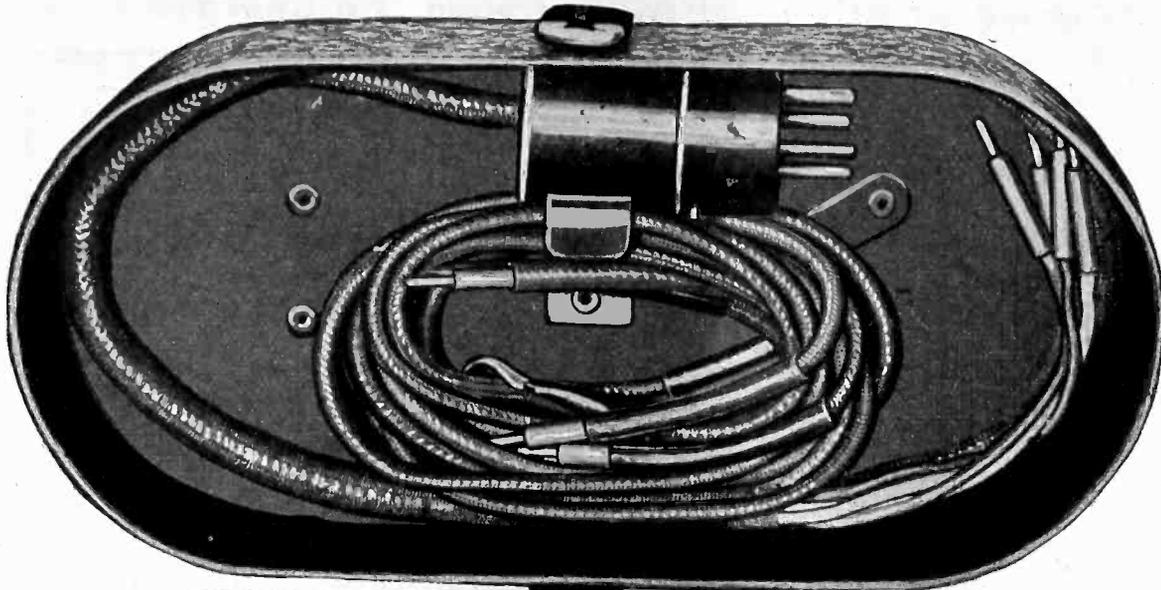Illumination Continuity and Polarity Tester FREE with Each Outfit!



Your Price
\$15.82

Complete

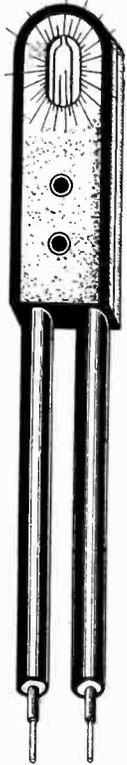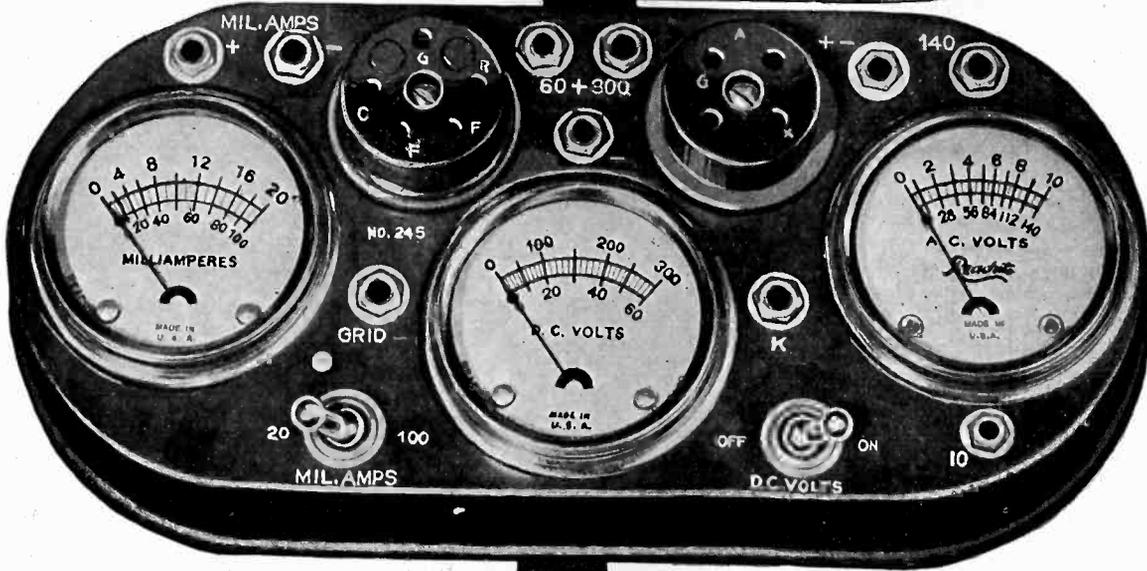


Illumination Tester, Vest Pocket Size, Shows Shorts and Opens Visually, also polarity of DC line. A Neon lamp is built in.



The three-meter assembly, in the crackle-brown finish carrying case, with slip-on cover in place. The handle is genuine leather. The buckled strap holds the cover on.



Illustration above is 2/3 scale.

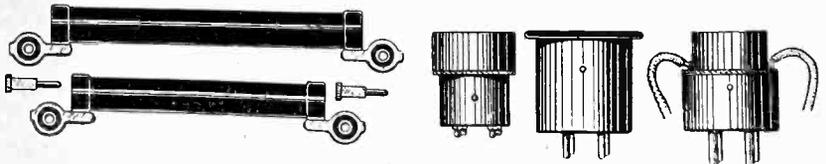

J-111 Multiplier, upper left, with tip; below it, J-106 Multiplier with tip; plugs, left to right, J-19, conforms UV socket to UX plug; J-20, conforms UX tester socket to UV199 tube; J-24, to test Kellogg and old style Arcturus tubes.

Makes All Necessary Tests in a Jiffy and Simplifies Service Work!

THE new Jiffy Tester, J-245-X, is a complete servicing outfit. It consists of a three-meter assembly in a metal case, with slip-on cover and a cable plug. There are ten adapters. It is vital to have the complete outfit so you can meet any emergency.

With this outfit you plug the cable into a vacated socket of a receiver, putting the removed tube in the tester, and using the receiver's power for making these tests: plate current, up to 100 milliamperes; plate voltage up to 300 volts; filament or heater voltage (AC or DC), up to 10 volts.

Each meter may be used independently. One of the adapters—a pair of test leads, one red, the other black, with tip jack terminals—serves this purpose. Multiplier J-106 extends the range of the DC voltmeter to 600 volts, but this reading must be obtained independently, as must readings on the 0-60 scale of the DC voltmeter. Independent reading of the AC voltmeter for line of voltage is necessary; also to use 0-140 scale while Multiplier J-111 extends the AC scale to 560 volts for reading power transformer secondaries.

The other adapters permit the testing of special receiver tubes, so that tests may be made, in all, of 22 different tubes: 201A, 200A, UX199, UV199, 120, 240, 171, 171A, 112, 112A, 245, 224, 222, 228, 280, 281, 227, 226, 210, 250, Kellogg tubes and old style Arcturus tubes.

WHEN servicing a radio set, power amplifier, speech amplifier or sound reproduction or recording equipment, the circuits and voltages are almost inaccessible, unless a plug-in tester is used.

The Jiffy 245-X plugs in and does everything you want done. It consists of:

- (1)—The encased three-meter assembly, with 4-prong (UX) and 5-prong (UY) sockets built in; changeover switch built in, from 0-20 to 0-100 ma.; ten vari-colored jacks, five of them to receive the vari-colored tipped ends of the plug cable; grid push-button, that when pushed in connects grid direct to the cathode for 224 and 227 tubes, to note change in plate current, and thus shorts the signal input.
- (2)—4-prong adapter for 5-prong plug of cable.
- (3)—Screen grid cable for testing screen grid tubes.
- (4)—Pair of Test Leads for individual use of meters.
- (5)—J-106 Multiplier, to make 0-300 DC read 0-600.
- (6)—J-111 Multiplier, to make 0-140 AC read 0-560.
- (7)—Two jack tips to facilitate connection of multipliers to jacks in tester.
- (8), (9), (10)—Three adapters so UV199 and Kellogg tubes may be tested.
- (11)—Illumination Tester.

The illumination tester will disclose continuities and opens and also the polarity of DC house mains. It is as handy as a pencil and fits in your vest pocket. It works on voltages from 100 to 400. There are two electrodes in a Neon lamp in the top of the instrument. On AC both electrodes light. On DC only one lights, and that one is negative of the line, the light being on the same side as the lead. Hence the illuminator shows whether tested source is AC or DC, and if DC, which side is negative.

Even the output of the speaker cord will show a light. Also, the device will test which fuses are blown in fused house lines, AC or DC. Besides it tests ignition of spark plugs of automobiles, boats and airplanes, also faulty or weak spark plugs.

Just flash on the illumination tester momentarily. It will last about 4,000 flashes.

GUARANTY RADIO GOODS CO.
143 West 45th Street, Just East of Broadway,
N. Y. City.

Please send me on 5-day money-back guaranty your J-245-X Jiffy Tester, complete, with all 10 adapters, and with illuminated Tester FREE with each order. Also send instruction sheet, tube data sheet and rectifier tube testing information.

Enclosed please find \$15.82 remittance. Ship at your expense. [Canadian must be P.O. or Express M.O.]

Please ship C. O. D. @ \$15.82 plus cartage and P.O. fee.

NAME

ADDRESS

CITY STATE

5-DAY MONEY-BACK GUARANTY

RADIO AND OTHER TECHNICAL BOOKS

At a Glance

- RADIO**
- "Audio Power Amplifiers," by Anderson and Bernard \$3.50
 - "Elements of Radio Communication," by Morecroft 3.00
 - "Foothold on Radio, A," by Anderson and Bernard 1.00
 - "Mathematics of Radio," by Rider 2.00
 - "Practical Radio," by Moyer & Wostrel 2.50
 - "Practical Radio Construction and Repairing," by Moyer & Wostrel 2.00
 - "Principles of Radio Communication," by Morecroft 7.50
 - "Radio Blueprint Library" - AC Hook-ups35
 - "Radio Cyclopaedia," by Drake 6.00
 - "Radio Receiving Tubes," by Moyer & Wostrel 2.50
 - "Superheterodyne Construction and Operation," by Lacault25
 - "Thermionic Vacuum Tube, The," by Van der Bijl 5.00
 - "Trouble Shooter's Manual," by Rider 3.50

TELEVISION

- "A B C of Television," by Yates 3.00

- AVIATION**
- "A B C of Aviation," by Maj. Page 1.00
 - "Aerial Navigation and Meteorology," by Capt. Yancy 4.00
 - "Everybody's Aviation Guide," by Maj. Page 4.00
 - "Ford Model 'A' Car," Its Construction, Operation and Repair—by Maj. Page 2.00
 - "Modern Aircraft," by Maj. Page 5.00
 - "Modern Aviation Engines," by Maj. Page 9.00

RADIO WORLD
 145 West 45th Street
 New York, N. Y.
 (Just East of Broadway)

NEW Morecroft

"Elements of Radio Communication," by Prof. John H. Morecroft, of the Engineering Department of Columbia University, is the latest book on radio by this outstanding authority.

This book is entirely new and contains matter which never before has been published. It is written in plain language so that every radio novice can understand it, yet it is a complete course in the elements of radio.

It contains 266 pages, 170 illustrations and a complete index. Price \$3.00.

RADIO WORLD


145 West 45th St., New York, N. Y.

RECENT NUMBERS

for the current year are procurable at the rate of 15c a copy, or 8 copies for \$1.00. **RADIO WORLD**, 145 West 45th St., N. Y. City.

4-GANG CONDENSER

With Trimmers
 Built in **\$3.95**

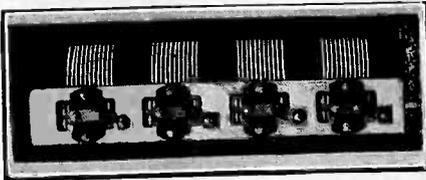


Capacity of each of the four sections is .00035 mfd. Overall length 11". Accurate capacity and precise alignment. Used in HB33 and HB44.

Guaranty Radio Goods Co.
 143 West 45th Street,
 New York City

New DRAKE'S ENCYCLOPEDIA

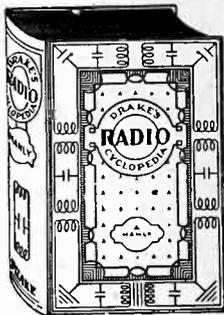A reference work that has subjects classified in alphabetical order.



Each rule, fact, method plan, layout, and diagram is instantly picked out and separated from everything else by placing all subjects in alphabetical order with cross references for every imaginable name under which the information might be classed.

This alphabetical arrangement lets the experienced worker refer directly to the one thing in which he is interested at the moment without hunting through non-essentials. The needs of the beginner are cared for.

The important articles deal primarily with receivers and reception. They do not stop with the electrical end, but go also into the mechanics of construction.

- BOOK IS 2 1/2" THICK.
- WEIGHS 3 1/4 LBS., 1,025 ILLUSTRATIONS.
- 1,680 Alphabetical Headings from A-battery to Zero Beat
- 1,025 Illustrations, Diagrams, Layouts and Graphs
- 920 Pages, Each 6 by 9 inches
- 240 Combinations for Receiver Layouts

OF THE PRINCIPAL ARTICLES

159 Concern service men, 129 help the set builder 162 help the experimenter, 155 interest the student 75 assist in sales work, 73 interest set owners.


PRICE, \$6.00

Reprint with order and we pay cartage. Canadian remittance must be by postal or express money order Order C. O. D. and you pay cartage.


RADIO WORLD, 145 W. 45th St., N. Y. City

MICROPHONE LIGHTERS

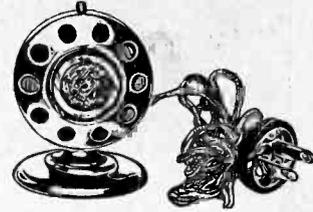for cigars or cigarettes, with button switch at top. Press the switch and light up!



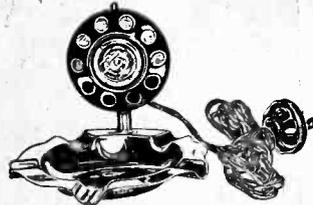Model A lighter, microphone design, with 5-ft. AC cable and plug. Works on 110 volts, AC any frequency and on direct current. Price \$1.00



Model B lighter, microphone design, on tray, with 5-ft AC cable and plug. Works on 110 volt AC, any frequency, and on direct current. Exactly the same lighter as the other, only tray is added. Price.....\$1.50


This lighter is instantaneous. Hold button down only long enough to light a cigar or cigarette. The two models are furnished in attractive sprayed finish. Both are very compact! For instance, the tray is only 4 1/2" in diameter. Use these lighters in your home and for holiday gifts.

The heater element is renewable.

- RADIO WORLD, 145 West 45th St., N. Y. City**
- Please send me Model A Microphone Lighter at \$1.00
 - Please send me Model B at \$1.50.
 - Enclosed is remittance [Canadian must be P.O. or express money order.]
 - Ship C. O. D.

Name:
 Address:
 City: State:

NATIONAL SCREEN GRID TUNER

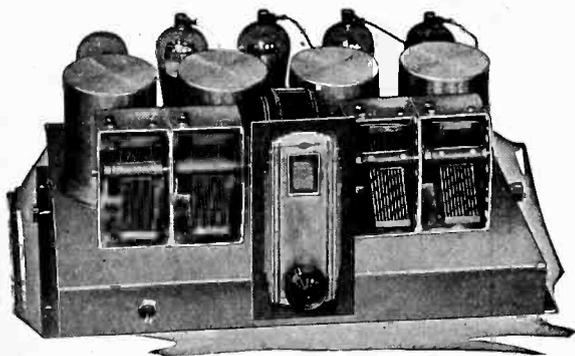


The most sensitive tuned radio frequency tuner so far developed, the MB-29 is long on distant reception, and penetrates seemingly unsurmountable barriers to reception. On the MB-29 the stations come in no matter where you are. The MB-29, designed by James Millen and Prof. Glen H. Browning, is the choice of the most discriminating. It is designed only for AC operation, uses four stages of screen grid EF and a power detector (227). Use 135 to 180 volts on the detector. Testimonials from radio's hardest-boiled experts prove this is the circuit of circuits. Buy the parts and find fullest radio delight. You will be sure nobody else has a tuner as good as yours, unless he too has an MB-29. Complete component parts for National Screen Grid Tuner MB-29, mounted on frosted aluminum chassis, including rainbow modernistic drum dial HC. Order catalog No. MB-29-K, list price, less tubes, \$69.50. Your price **\$40.00**

MB-29

Push-Pull Amplifier

The National Velvetone Push-Pull Power Amplifier (shown at right) consists of an AC-operated filament-plate supply, with two stage transformer audio amplifier and output transformer built in. Made only for 110-V., 50-60 cycles. Sold only in completely wired form, licensed under RCA patents.

The new Power Amplifier has been developed and built to get the very most out of the MB-29. It is a combination power supply and audio amplifier, using a 280 tube for a rectifier, one stage of transformer audio with a 227 tube and a stage of push pull amplification with two 245s. It furnishes all power for itself and for the MB-29, as well as the audio channel. Order catalog PPPA, list price, completely wired and equipped with phonograph jack, (less tubes) \$97.50. Your price, **\$55.00**

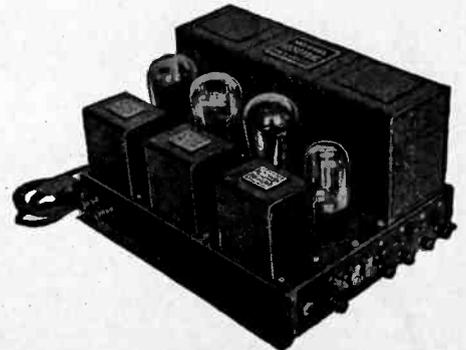

View of National Velvetone Push-Pull Power Amplifier, an expertly made A, B and C supply and audio amplifier, producing marvelous tone quality.

GUARANTY RADIO GOODS CO.

143 WEST 45TH STREET

NEW YORK CITY


Highest Grade Speakers at Lowest Prices!

T - E - M - P - L - E F - A - R - R - A - N - D



Temple AC Dynamic Model 10, in a beautiful cabinet. The speaker chassis is one of the finest made. There are an output transformer and dry rectifier built in. The cabinet has decorated walnut front and back, with carved grille ornament. An AC switch is accessible underneath cabinet. Rear is removable for adjustment of resistor knob to match the impedance of your receiver's output tube. Connect plugged AC cable to 110 volts AC, 50 to 60 cycles, and connect tipped cords to speaker post of receiver. This remarkable speaker Cat. TEM-10 at only.....

\$15.34

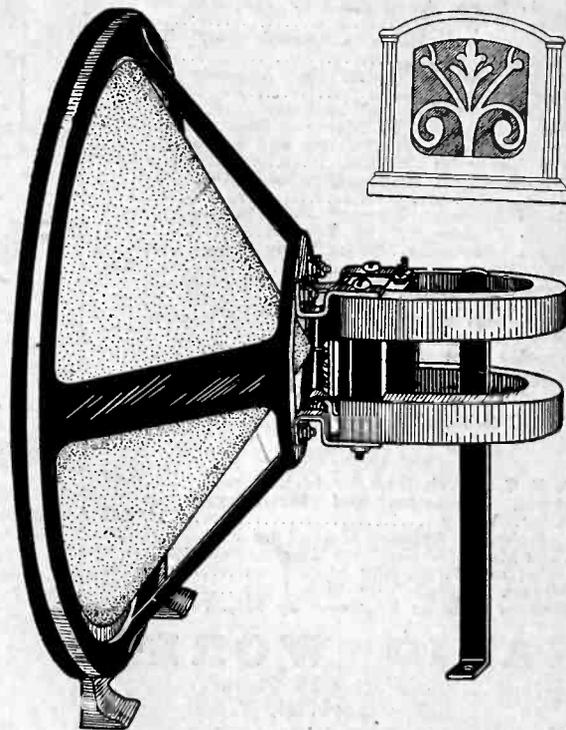

Farrand Inductor Chassis, consisting of the unit, cone, spider, bracket, assembled, but not in a cabinet.

Model 6-G, 10" extreme diameter of cone front rim **\$9.00**

Model 10-G, 12" extreme diameter of cone front rim **\$10.00**

Model 10-G-PP for connection to push-pull, requiring no output device, because unit is constructed as a center tapped output impedance. Center tap is yellow and goes to B+. Tipped cords go direct to plates. Outside diameter 12"..... **\$11.00**

Brookfield cabinet, No. 10 or No. 6 for those speakers, **\$6.50**


R - O - L - A

Rola Model D-10 dynamic chassis, less cabinet, for 110 volts 50-60 cycles AC. Dry rectifier and output transformer built in. The fine workmanship of this chassis is shown in the illustrations of the front and rear views. Extreme diameter of rim 9 inches but baffles with cutouts down to 7 inches may be used.


This is the biggest dynamic chassis bargain we have ever offered and enables you at low price to obtain one of the best chassis made. Tone is most excellent.

Order Cat. No. RO-10 at

\$11.34

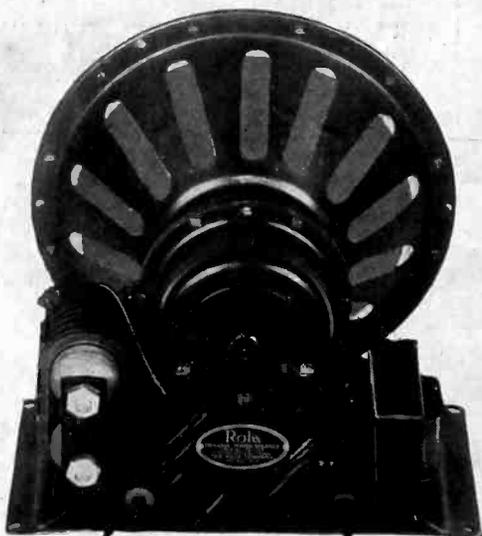

Rear view of the Rola chassis

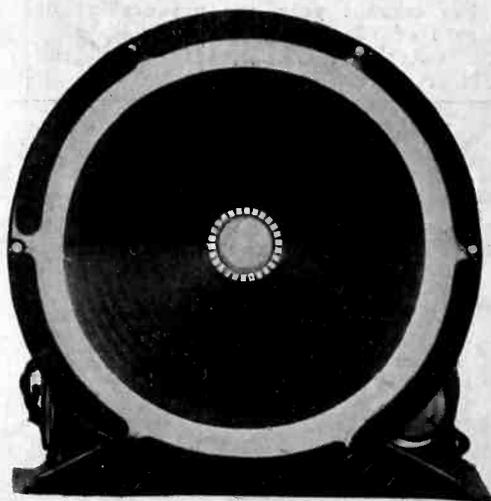

Front view of the Rola chassis. Holes are provided for attachment to your own baffle. The rim is protected by a lining of felt. The voice coil (center) is firmly mounted.

Acoustical Engineering Associates
143 West 45th Street, New York City. (Just East of Broadway)

- Gentlemen: Enclosed please find money order check for \$..... for which please send me at once
- One Model 6-G Farrand Inductor \$9.00
 - One Model 10-G Farrand Inductor 10.00
 - One Model 10-G-PP Farrand Inductor 11.00
 - One Model 10 Brookfield cabinet 6.50
 - One Model 6 Brookfield cabinet 6.50
 - One TEM-10 Temple Dynamic in cabinet 15.34
 - One RO-10 Rola dynamic chassis 11.34
- For C. O. D. shipment put cross here

Name

Address

City State

[Prepaid orders shipped same day as received. Canadian remittance must be by postal or express money order.]

The Temple, Rola and Farrand speakers are highly recommended by us for true tone and high volume. They are extremely sensitive as well. The chassis (Farrand and Rola) will work without a baffle, but it is preferable to provide one. The Temple requires no extra baffle, as the cabinet is itself a baffle box.

All three speakers are sold in factory-sealed cartons. Immediate delivery.

Model 10-G-PP Farrand may be used in push-pull without any output device. Connect yellow lead to B+, tipped leads to power tube plates. May be used on single output by ignoring yellow lead.