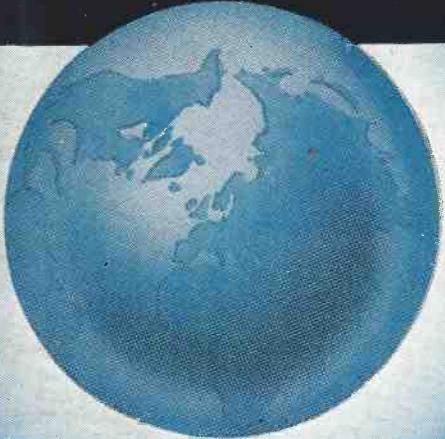


2/-

The

SHORTWAVE

Magazine




Ed. N.

**EXCLUSIVELY FOR THE
RADIO EXPERIMENTER &
TRANSMITTING AMATEUR**

VOL. VI No. 12 FEBRUARY 1949

WEBB'S Radio Map & Globe

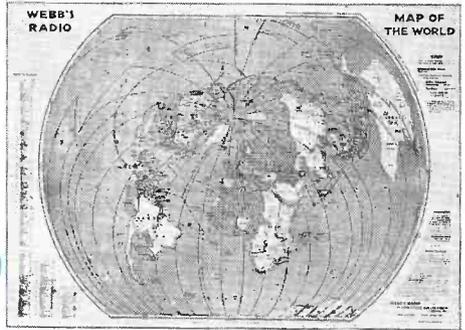

IN NEW EDITIONS

WEBB'S Radio Map OF World

INDISPENSABLE FOR THE
RADIO "SHACK"

Shows the true directivity of any place in the world and gives amateur radio international prefixes, also indicates the time of day for the world.

Originally printed in 1936, many thousands of radio men have proved its use time and time again.

ENTIRELY NEW PRINTING

with revised and up-to-date Call Signs prefixes, coded to country and time-zones, combined with improved printing in multi-colours.

Printed in full colours on heavy white paper, size 40 in. x 30 in., price 4/6, plus 6d. postage.


(Also on heavy linen rollers, price 11/6, plus 9d. postage.)

This Map is drawn on an azimuthal projection and looks strange to those accustomed to Mercator's projection, but, giving directivity and Great Circle distances, it performs many functions for radio men that the original map cannot do. Printed on the margin is an index to Call Signs and full explanation of use of time-zones and "Great Circle" projection.

WEBB'S New Radio Globe

UP TO DATE IN EVERY DETAIL

An improved and enlarged version of our famous pre-war globe brought right up to date with new continental boundaries and Amateur Radio Prefixes. The enlarged diameter (13½") greatly increases map area, and a compass fitted in the base makes correct orientation simple. Invaluable for quick location of unfamiliar calls and a handsome adjunct to receiver or transmitter. Price 47s. 6d. to callers. 50s. by rail.

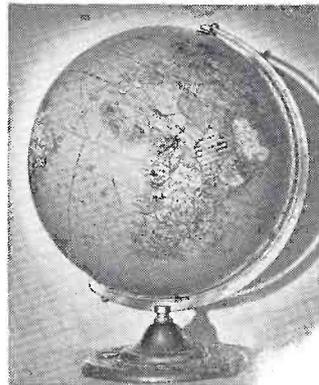

Diam.

13½"

Price

47/6

(Pack-aging and carriage 2/6 extra)

Webb's Radio * 14, SOHO ST., OXFORD ST., LONDON, W.1.


Telephone : GERrard 2089.

Note our Shop Hours : 9 a.m. to 5.30 p.m., Sat : 9 a.m. to 1 p.m.

'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark

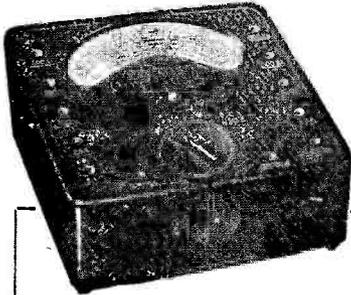A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set. Stocks are now available of these two famous "Avo" Instruments. If you have any difficulty in obtaining one locally, please send us the name and address of your nearest Radio Dealer.



The UNIVERSAL AVOMINOR

A small but highly accurate instrument for measuring A.C. and D.C. voltage, D.C. current, and also resistance. It provides 22 ranges of readings on a 3-inch scale, the required range being selected by plugging the leads supplied into appropriately marked sockets. An accurate moving-coil movement is employed, and the total resistance of the meter is 200,000 ohms.

The instrument is self-contained for resistance measurements up to 20,000 ohms and, by using an external source of voltage, the resistance ranges can be extended up to 10 megohms. The ohms compensator for incorrect voltage works on all ranges. The instrument is suitable for use as an output meter when the A.C. voltage ranges are being used.

D.C. VOLTAGE
 0-75 millivolts
 0-5 volts
 0-25 "
 0-100 "
 0-250 "
 0-500 "

A.C. VOLTAGE
 0-5 volts
 0-25 "
 0-100 "
 0-250 "
 0-500 "

D.C. CURRENT
 0-2.5 milliamps
 0-5 "
 0-25 "
 0-100 "
 0-500 "

RESISTANCE
 0-20,000 ohms
 0-100,000 "
 0-500,000 "
 0-2 megohms
 0-5 "
 0-10 "

*Size: 4½ ins. x 3½ ins. x 1½ ins.
 Net weight: 18 ozs.*

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

Price : £8 : 10 : 0

GUARANTEE

The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new Avominor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

CURRENT
 0-3 milliamps.
 0-6 "
 0-30 "
 0-120 "
VOLTAGE
 0-6 volts.
 0-12 "
 0-60 "
 0-120 "
 0-300 "
 0-600 "
RESISTANCE
 0-10,000 ohms
 0-60,000 "
 0-800,000 "
 0-8 megohms



The D.C. AVOMINOR

A conveniently compact 2½-inch moving coil precision meter for making D.C. measurements of milliamps, volts and ohms. The total resistance of the meter is 100,000 ohms, and full scale deflection of 300 v. or 600 v. is obtained for a current consumption of 3mA. or 6mA. respectively.

*Size: 4½ ins. x 3½ ins. x 1½ ins.
 Net weight: 12 ozs.*

Complete as above.

Price : £4 : 4 : 0

● Complete descriptive Booklet available on application to the Sole Proprietors and Manufacturers:—


THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
 WINDER HOUSE, DOUGLAS STREET, LONDON, S.W.1 TELEPHONE VICTORIA 3404/9

THE "COMMANDER"

Double Superhet COMMUNICATIONS RECEIVER

PRICE £48.10.0, carriage paid in Gt. Britain

★
SUPER
SELECTIVITY

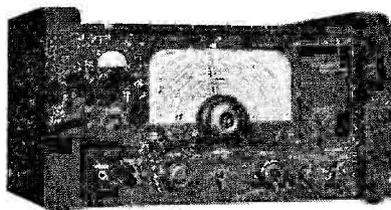

★
SUPER
STABILITY

Built into this beautiful desk console you have the finest Amateur Communications Receiver ever designed and produced in the British Isles.

BRIEF SPECIFICATION:—1.7 TO 31 MCS CONTINUOUS COVERAGE ● SEPARATE ELECTRICAL BANDSPREAD ● 3-POSITION SELECTIVITY ● DIRECT READING DIAL CALIBRATED IN MEGACYCLES ● SUPER NOISE LIMITER ● MICROVOLT SENSITIVITY ● EXCELLENT SIGNAL/NOISE RATIO ● ILLUMINATED S METER ● VOLTAGE STABILISER ● BFO ● 1.6 MC AND 100 KC I.F. STAGES ● 3 WATTS OUTPUT ● TOTAL OF 11 VALVES.

For illustrated literature send 2½d. stamp to:—

RADIOVISION (LEICESTER) LTD., 58/60 RUTLAND ST., LEICESTER
Hire Purchase Facilities Phone: 20167

G6YA

WESTERN GATEWAY HEADQUARTERS
FOR RADIO EQUIPMENT AND STORES

G2BAR

New and unused
1196
Transmitter
Receiver

Complete as shown


Operates 'phone and M.C.W.
from 4-3-6-7 mcs. Easily
modified for other frequencies.

SPECIFICATION

Transmitter: EF50 Pierce Xtal Oscillator; TT11 (VT501), P.A.; EL32 (VT52), Modulator.

Receiver: EF39, R.F. amplifier; EK32, frequency changer; EF39, I.F. amp.; EF36, A.V.C. amp; EF36, A.F. amp. and "mike" amp.; EBC33, 2nd detector and output.

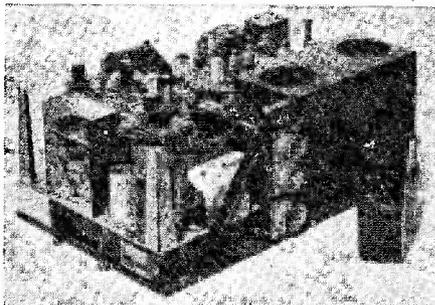Power Unit: Operates from 24v giving an output of 6.3v for heaters, and approx. 250v H.T.



View with
Trans. and Rec.
covers removed.
Circuits supplied
with each

45/-

plus carriage

General: 4-spot frequencies, trans. and receive, selected by auto-selection. Capable 15 watts input 'phone and M.C.W. Ideal for small boats, field day, and mobile use.

Extras: 4-way, type 12, push-button controller with trans./rec. switch, as shown, 5/-. Crystals, 5100, 5980, 6180, 6720 kc, 4/6 each. Transit case, 2/6. Carriage: Add 5/- for goods carriage, 7/6 passenger train in England and Wales.

ARTHUR H. RADFORD

A.M.I.E.E.

G6YA

A.M.BRIT.I.R.E.

23, Bedminster Parade, Bristol, 3

Telephone: 64314.

Open Saturdays: 9-5.30 p.m.

RADIO CLEARANCE LTD.

27 TOTTENHAM COURT ROAD, W.I

MUS 9188

RECEIVERS R.U. 19

6-valve straight receiver with 3 R.F. stages, using plug-in coil packs, H.R.O. type. Valves : 3 78's, 2 77's, 1 1642. Black crackle case, 15" x 8" x 8". Provision for remote or local control. Dial cal. 0-100. Supplied new, complete with valves and 6 coil packs covering : Q, 187-305 ; P, 281-455 ; Q, 524-844 ; E, 1285-2155 ; G, 2960-4620 ; H, 3865-6265 ; M, 5075-7780 ; K, 8750-1395 kc/s. £4/10/-, carriage paid.

PERSONAL RECEIVERS B.C.728C

7-valve receiver with 1.4v valves, R.F. VT173, mixer VT171, osc. VT173, I.F. VT173, det. and audio VT172, output VT174, bias rect. VT174 ; covers 2-6 Mc/s, with 4 push buttons adjustable 2-2.6, 2.6-3.5, 3.5-4.5, 4.5-6.0 Mc/s respectively. Operates from 2v acc by 2v vib., with 12v vib. for charging 2v acc. Carried slung on shoulder. Supplied brand new with valves, telescopic aerial, 2v acc., 2 vib., mounting accessories and instruction book. Built-in loudspeaker. £9/9/-.

MASTER OSCILLATORS

V.F.O. by Wilcox Gay. Type M.I. 19467A. Uses 807 electron-coupled osc., very stable, well screened. Employs 2 circuits : (a) Using cath. grid, screen, tuning 1.5 Mc/s in 6 bands. (b) Plate circuit as multiplier ; tuning 2-10 Mc/s in 3 bands. Incorporates grid choke, grid leak, grid current meter (0-10mA) for intermediate amplifier. Supplied brand new in original cartons, with installation accessories and instruction book. £5/10/-, carriage 5/-.

CRYSTAL MULTIPLIERS

Wilcox Gay, Type M.I. 19468. This is a xtal osc. using 807. Freq. range 2-7 Mc/s. Also incorporates 0-10mA grid current meter, etc. Supplied brand new in original cartons, with accessories, book, etc., 45/-.

MAINS TRANSFORMERS

Primary, 0-11C-200/250v 50 c/s. Secondaries, 230-0-230v, 100mA, 5v 2A, 6.3v 2A, C.T. 15/6.
 Primary 200/250v 50 c/s. Secondaries, 275-0-275v, 120mA, 4v 2A, 4v 3A, 13/6.
 Primary, 200/250v 50 c/s. Secondaries, 460v 200mA, 210v 15mA, 6.3v 5A. 18/-.
 Primary, 200/250v 50 c/s. Secondary, 110v. Rating, 60w. Enclosed. 19/6.
 Primary tapped for use on 80v 2,000 c/s, 115v 50 c/s, 180v 500 c/s, and 230v 50 c/s. Secondaries, 5v 5A, 6.3v 6A, 350-0-350v. Marked as 100mA, but will carry over 200mA, as rating is 133 watts. Weight 12 lb. Size 5" x 4" x 5". A beautiful job. 26/6. All trans. are new and boxed.

SMOOTHING CHOKES

| | | | | | | | |
|--------------------|----------------|-------------------|------|------------------|-----|-----|------|
| 20H, 40mA, 220 Ω | ... | ... | 3/11 | 5H, 200mA, 90 Ω | ... | ... | 7/6 |
| 10H, 80mA, 150 Ω | ... | ... | 5/- | 5H, 120mA, 140 Ω | ... | ... | 5/- |
| 20H, 300mA, 150 Ω, | Weight 13 lb., | size 7" x 5" x 5" | ... | ... | ... | ... | 20/- |

ELECTROLYTICS

8mF 170v, 1/9 ; 8mF 350v, 2/3 ; 8mF 450v, 2/6 ; 16mF 350v, 3/- ; 16mF 450v, 3/6 ; 8+8mF 450v, 4/- ; 8+24 350v, 3/- ; 16+16 350v, 4/- ; 16+24 350v, 4/6 ; 16+16 450v, 4/6 ; 16+8 450v, 4/6 ; 24mF 350v, 2/6 ; 16+24+8mF 450v, 5/9 ; 100mF 3v, 4d. ; 100mF 6v, 6d. ; 25mF 25v, 1/6 ; 25mF 50v, 1/9 ; 50mF 50v, 2/- . Post extra.

LOUDSPEAKERS, P.M.

5", less trans., 13/6 ; 5", with trans., 16/11 ; 6½", less trans., 15/11 ; 10", with trans., 32/6. All brand new, boxed, with all. speech coils.

METERS, MOVING COIL

Metal cased, 2" circular, 0-500 micro/amp., 7/6 ; 0-15/600v (requires ext. res.), 6/6. 0-20 or 0-40 amp. (with shunts), 5/- . Bakelite cased, 2" square, 0-500 micro/amp., 9/6 ; 0-1mA, 7/6 ; 0-5mA, 6/- ; 0-50mA, 7/- ; 0-150mA, 6/- ; 0-300V D.C. (series res. supplied), 7/- . Bakelite cased, 2½" circular, 0-100 micro/amp. F.S.D., scaled megohms 4-2.5m-infl., 18/6 ; 0-500 micro/amp., 16/6 ; 0-30mA, 7/- ; 0-50mA, 8/6 ; 0-100mA, 9/6 ; 0-200mA, 9/6 ; 0-1mA, desk type, 15/- ; 0-15v, 7/- ; 100-0-100v, centre zero, 1mA F.S.D, 7/-.

MODULATORS B.C.456B

3 Valves, 1-1625, 1-1215, 1 VRI50/30. Brand new, 13/6.

R.F. UNITS

| | | | |
|--|-----|-----|--------------------|
| Type 24, with valves, used, good condition | ... | ... | 8/6 plus 1/6 post |
| Type 25, with valves, used, good condition | ... | ... | 10/6 plus 1/6 post |
| Type 26, with valves, brand new, boxed | ... | ... | 28/- plus 1/6 post |

TRANSMITTER TUNING UNITS

Westinghouse Elect. C.A.Y. 47155. Type C. Covers 1.5-3 Mc/s. Variometer tuned, with S.M. dials, etc. in black crackle case. 17/6.
 Westinghouse Elect. C.A.Y. 47154A. Type F. Covers 6-9 Mc/s, with condenser tuning, S.M. dials, black crackle case. A nice job. 22/6.

CONTROL UNITS

With 2 2" square moving coil meters, flush mounting, 0-5mA and 0-40v, toggle SW, 5- and 7-pin sockets. 8/6. Post 1/-.

RECEIVERS, TYPE 78

5 Valves, VR91, ARTH2, 6J5, VR53, VR92. Covers 2.4-13 Mc/s in 2 bands. Xtal calibrator with 100 kc xtal. Heaters wired for 26v. Feeds out on I.F. of 560 kc/s. Brand new in transit case, 37/6.
 Type 76 covers 150-505 kc/s, with 3 valves, VR53, ARTH2, EA50, S.M. dial as 78, but no xtal calibrator. 27/6.

F.M. RECEIVERS, B.C.603

10-valve receivers covering 20-28 Mc/s. Tuneable or 10 channels available by push buttons. I.F. 2.65 Mc/s. Bandwidth 80 kc/s. Power output, 2 watts to built-in 5" speaker. Provision for phones. Line up : R.F. 6AC7, Mod. 6AC7, osc. 6J5, 2 IF's 12SG7, limiter 6AC7, det. 6H6, A.F. and B.F.O. 6SL7, A.V.C. 56L7, output 6V6. Brand new. £6/19/6.

SAMSONS SURPLUS STORES

RADAR RECEIVER TYPE 184. Complete with 14 valves, including: 1 CU6G, 4 VR91, 7 VR65, 1 VU111, 1 VR92. This receiver contains a 45 Mc/s I.F. strip ideal for television construction. Brand new. £2/5/-. Carriage extra.

PARCEL OF VALVES. Brand new ex-Government valves. 1 VR56, 1 VR65, 1 VR54, 3 VR135, 1 6J5G. Price £1.

CATHODE RAY UNIT 162C. Complete with 2 C.R. Tubes VCR517 and VCR139, 3 VR65, 1 V652, 4 diodes, resistors, condensers, etc. Suitable for vision construction. Brand new in maker's packing case, £3/17/6, carriage 3/6.

A.M. RECEIVERS TYPE 1355. Complete with 8 VR65, 1 5U4G, 1 VU120. Ideal for vision construction. 30/-. Post 3/6.

CO-AXIAL CABLE. 30 ft. length of cable, 80 ohm. A Pye male connector each end. Brand new. 8/6 each.

R.F. UNITS, TYPES 25 and 27, for use with the 1355. Complete with valves, 16/6, post 1/6.

MINE DETECTOR UNITS. Wonderful component value, comprising 3 IT4 valves and bases, 9 condensers, volume control, 8 resistors, etc. 19/6, post 6d.

HEAVY-DUTY TRANSFORMERS. 12v 70A. Input 200/250v. £4/10/-, carriage 4/-.

AMERICAN REMOTE CONTROL UNITS. Brand new. Suitable for telephone units. Wonderful component value with hand generator, bell unit, multi-way switch, condensers, etc. 15/-, post 1/6.

MODULATOR TYPE 67. Wonderful component value. Including transformer 345.0-345v 200ma, 6.3v 5A, 6.3v .25A, 5v 2A. Input 230v, 5 VR65, 2 VR54, 1 VR116, 1 5Z4G. H.D. Smoothing choke and hosts of resistors, condensers, etc. 69/6 plus carriage.

169/171 EDGWARE ROAD, LONDON, W.2

Tel: PAD 7851

125 TOTTENHAM CT. RD., LONDON, W.1

Tel: EUS 4982

All orders and correspondence to our Edgware Road branch, please.

LAWRENCE'S RADIO BARGAINS

Special Components for Receivers BC453-4-5. Medium wave coils, Type BC453 and BC455, instructions supplied. Stipulate type required. 10/6 each.

A.C. Power Packs. 230v. Plugs on to rear of RX. Eliminates power modifications. Complete with valve 6X5. 45/-. Genuine dynamotors, plug-on type. 14v or 28v. 12/6.

Brand New Receivers, BC348. In sealed makers' cartons, with Handbook. £19.

Radio Altimeter Test Sets, Type 6 (A.merican). Stabilised Power Unit. Transmitter unit employs acorn triodes. Magnificent instrument case. Complete with cables and circuit. £4/10/-.

New Power Relays. Operate on 230v A.C. Heavy duty contacts for 1 kw. 17/6.

New R.C.A. Quality Amplifiers, Type M1/11220A. 230v A.C. Output 20 watts from 4 6J7, 2 6L6, 1 5U4. Handsome cabinet. £16/5/-.

New U.H.F. Receivers, Type AN/CRW2. 1 6SG7, 1 6J5, 2 6SL7, 2 6SN7. Plug-in coils, 60 mcs. Power unit 28v. 23/-.

New Cathode Ray Scope Units, BC929, Tube 3BP1. Panel controls for shift, focus brilliance, etc. Seven valves, including H.V. rectifier. Instrument case. An ideal unit for conversion to test scope. 70/-.

New Rack Assemblies for Receivers 78 and 76. Contain 3 valuable relays. 8/-.

New 3cm Radar Scanning Antenna Units. Parabolic reflector. 2 Powerful D.C. motors. Precision gearing. With cable. 25/-.

New Valves. At 10/-. 5Z4 metal, 6C4, 6L6, 1622. At 7/6—3Q5, 5U4G, 6AG5, 6AJ5, 6B4, 6B8, 6F6, 6J7, 6SQ7, 7C5, 7F7, 7Y4, 9D6, 12K8, 25L6, VR150, 807, 9001, EF36, KT33C. At 6/6—2X2, 5V4, 1625, EF50. At 5/—6AC7, 6J5, 6K6, 6SA7, 6SG7, 6SL7, 6SN7, 6SR7, 7V7, 1A6, 12SK7, 12SR7, SP61, V960, 956. At 4/6—6SH7, 8D2, 12C8, 12J5, 12SQ7. At 2/9—6H6, 7193, EA50. All guaranteed. Two or more valves post free, otherwise add 6d.

Brand New P.M. Speakers. Plessey 6½" high flux type, with transformer 7,000 ohms, 15/-; Truvox 5", 13/9; 8", 14/-; Rola 3½", 13/3.

New Receivers. Type IFF/BC966 or ABK1. 13 6v valves. Valuable dynamotor with gearbox which converts to A.C. motor. Complete in makers' carton with control panel and maintenance manual. 29/6.

Receivers BC357. 2 Valves. 60-80 mcs. With circuit diagram. 9/6.

New Reflector Klystrons. Western Electric 723A/B. 30/-.

New Receivers. Type 76. 150-505 kcs. 3 6v valves. In fitted case with circuit, 30/-. Receivers BCA0/429-6 6v valves. 201-398 kcs, 2.5-7.7 mcs, plug-in HRO type coils, 4-gang tuning condenser, 37/6. Receivers type 1125-2 valves, freq. 30 mcs, with circuit diagram. 8/-.

New Amplifiers. Type 16129. Midget 9D6 valve. Enamelled case, 10x4x3". Ideal for deaf aid or personal set conversion. 15/-.

Terms C.W.O. Prices include carriage. No lists.

LAWRENCE'S, 61 Byrom Street, Liverpool, 3. CENTRAL 4430

EX-GOVERNMENT STOCK DISPOSAL !



The finest
RADIO VALUES
ever offered!

SATISFACTION GUARANTEED OR MONEY REFUNDED !

RECTIFIER RA77B

Western Electric. Contains 3-5T4, 1-6SQ7, 1-VR150, 2-6Y6, transformers, smoothing chokes, etc. Brand new in original cartons. Size 19" x 5" x 7".

45/-

CATHODE RAY TUBES

VCR97 New, Crated **33/6**
 5NPI New, Cartoned **33/6**
H.V. RECTIFIER 2X2
 New, Boxed.....**6/-**

COAXIAL CABLE

Best quality 52 ohms polyethylene. Fitted standard coaxial end plugs. Length 50'.

6/6 per length

10 Mc/s CRYSTAL

Brand new with ceramic socket. American

25/-

RECEIVER TYPE 1355

Incorporating 7-7 mc/s.I.F.'s. Good condition

33/6

INDICATOR TYPE

ID6/APN4

American. 24 valves plus 5CPI C.R.T. and 100 kc/s crystal. Excellent condition

£4

INDICATOR TYPE BC992B

Contains 7-inch C.R.T. type 1813P7 and 8 valves—6N7, 6AG7, 6H6, 705A and 807. Brand new in cartons. Size 11" x 19" x 15".

£3/10/-

R.F. UNIT TYPE 25

40/50 mc/s to 7.5 mc/s. Brand new in cartons

15/-

NO CARRIAGE OR PACKING CHARGES !

★ TERMS
 Cash with Order.
 Send Money Order or Postal Order to :

R.F. UNIT TYPE 26

65/50 mc/s to 7.5 mc/s. Brand new in cartons

35/-

★ ANY TRANSFORMERS CAN BE WOUND TO CUSTOMERS' OWN SPECIFICATIONS

PRICE UPON REQUEST

SYNCHRONISER TYPE BC993B

Western Electric. Contains 16 valves—6N7, 6SN7, 6AC7, 6SL7, 713A, 2X2, 1S5, 3-inch C.R.T. type 1806P and microammeter. Brand new in cartons. Size 10" x 20" x 8".

£4

MAINS TRANSFORMERS


230 V.A.C. input 50 cycles. 450/0/450/120 m/a. 5v, 3A ; 6.3v, 5A ; 4v, 2A ; 4v, 2A ; 1750v, E.H.T. 10 m/a. **SPECIALLY INSULATED 4v WINDINGS.** Robust construction. Specially manufactured to our specification. NOT Surplus **£4/10/-**

WESTON PRODUCTS (Liverpool) LTD.


71 Great George Street · Liverpool • Telephone ROYAL 5754/5



DE LUXE AND POTTED TYPE TRANSFORMERS

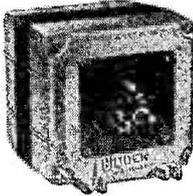

De Luxe Type

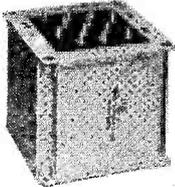

Potted Type

MAINS TRANSFORMERS

- D.T.M.11. 250-0-250 60 m/a
- D.T.M.12. 275-0-275 120 m/a
- D.T.M.13. 350-0-350 120 m/a
- D.T.M.14. 425-0-425 150 m/a
- D.T.M.15. 500-0-500 150 m/a

All above available in 4v or 6v filament windings.

- D.T.M.16. 650-0-650 250 m/a
- D.T.M.17. 750-0-750 250 m/a
- D.T.M.18. 1250-1000-0-1000-1250 300 m/a
- D.T.M.19. 1500-0-1500 350 m/a
- D.T.M.20. 2000-0-2000 350 m/a

- D.T.M.21. 500-450-450-500v 250 m/a. 0-4v.-5v. 6a. 4v or 6-3v. 3a. CT. 4v. or 6-3v. 4a. CT.
- D.T.M.22. 350-0-350v. 180 m/a. 0-4v.-5v. 4a. 0-4v.-6-3v. 3a. CT. 4v. or 6-3v. 4a. CT.

MAINS TRANSFORMERS

- P.T.M.11. 250-0-250 60 m/a
- P.T.M.12. 275-0-275 120 m/a
- P.T.M.13. 350-0-350 120 m/a
- P.T.M.14. 425-0-425 150 m/a
- P.T.M.15. 500-0-500 150 m/a
- P.T.M.16. 650-0-650 250 m/a
- P.T.M.21. Spec. as D.T.M.21
- P.T.M.22. Spec. as D.T.M.22

• All above available in 4v or 6v filament windings.

SPECIAL MAINS AND OUTPUT TRANSFORMERS


Woden Quality Components are available for the 'Electronic Engineering,' Home-built 'Television,' 'Wireless World' Williamson Amplifier and other popular circuits appearing in the leading Journals.

Send for complete catalogue.

WODEN TRANSFORMER CO. LTD.

MOXLEY ROAD BILSTON STAFFORDSHIRE

TELEPHONE: BILSTON 41959/0

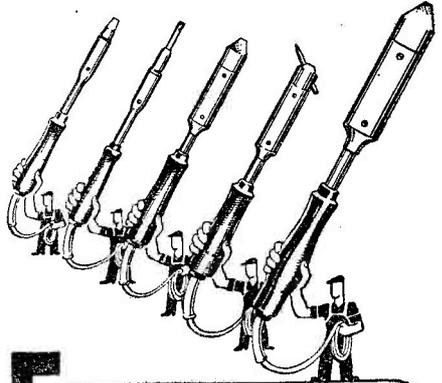

5 SOLON MODELS

SOLON electric soldering irons have proved their capacity for continuous service under the most exacting conditions. 5 models; 240 watt oval tapered bit; 125 watt oval tapered and round pencil bits and 65 watt oval tapered and round pencil bits. Each model complete with 6 feet of Henley 3-core flexible. Now available from stock. Write for folder Y.10.



W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden, London, E.C.1

INSTRUMENT CO.

244 HARROW ROAD, LONDON, W.2.

R1355 RECEIVER complete with RF25. Needs only minor modifications to give the perfect vision receiver. 47/6 plus 5/- carriage.

TYPE 6 INDICATOR containing VCR97, Pot/Meters, and a host of useful components including valves, etc. £3/19/6 Plus 15/- carriage, 7/6 refunded on return of packing case.

EHT TRANSFORMER giving 2,500 volts and 6.3 volts at 3-amps and 4 volts at 3 amps. £2/18/- Post free.

CONDENSERS. 8 Mfds., 450 volt working. Post free 1/9 each
EHT RECTIFIER H.V.U.I. Post free 8/-

"INEXPENSIVE TELEVISION" BOOKLET at 1/6. Shows how to make your Television from Ex-Govt. Units listed above.

ADJUSTABLE THERMO-STATIC SWITCHES. Suitableable for mains voltages. Post free, each 8/6


Ex-R.A.F. AMPLIFIER 1134 Ideal for use with a microphone, or can be used as an amplifier without modification. Complete with wooden transit case. 16/9 Post free

MAINS TRANS. Stand up and Drop-through type. Primary 200-250 volts. Secondary 350-0.350 80mA, 5 volts 2 amps, 4 volts, 3 amps. Post paid £1

SCREENED FLEX. 10/- Suitable for mikes. 100ft.
12 ASSORTED RELAYS for experimental purposes. 12/9 Post free

INFRA-RED TUBE 14/6 Post free

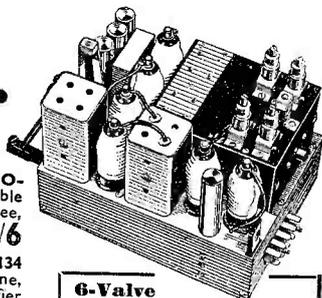2½" FLUSH MOVING IRON AMMETER 0-25 7/6 Post free



6-Valve

SUPERHET


Receiving Unit of the well-known TR1198 which covers 4.3 to 6.7 mc/s. Among the many useful components are:—1 pr. standard IP transformers (460 kc/s), iron dust cores, 2, 1 MF2D, 600v working condensers; 4, 1 metal tubular condensers, 1 MIO transformer; 1 phone output transformer, 2 pot meters, 10 fixed condensers of standard values; more than 2 doz. resistors from 200 ohms to 1 megohm; 6 International octal valve holders; 2 tag boards; 1 Yaxley switch; 4 pre-set .0001 condensers and tuning coil. In fact a 6-valve superhet mounted on steel chassis, size 8½" x 6" x 2½". Less valves, post free, 10/-.

With valves, 29/8, plus 2/6 pkg. and ins.
This Set can be easily modified for Car Radio or 4-Station Push Button Receiver.
Data Book, 1/6 extra.

Write for full list of bargains to Dept. "M"

INSTRUMENT CO., 244 Harrow Road, London, W.2

Telephone: CUN 0508

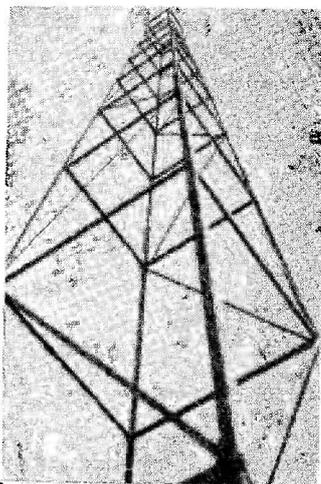

Here it is! Just the job!!

Self-supporting steel tower for that beam

NO GUY WIRES!

- 32' high. Immensely strong
- Engineer designed and built
- Complete and ready to assemble (painted aluminium over red oxide)
- Easy to erect
- Immediate delivery

ONLY **£18.10.0** Carriage paid

GALVANISED £5 EXTRA

EXPORT ENQUIRIES INVITED

EASY PAYMENTS ARRANGED

Sole Agents and Distributors:

G 6 Q A

82 MOLYNEUX STREET,
ROCHDALE, LANC'S

TEL: 3549

VALLANCE'S BARGAINS AND VALUES

THREE ONLY. SIGNAL GENERATORS,

TYPE I-72-J. Made for the Signal Corps of the U.S. Army by the Espey Manufacturing Company of New York. Covers 100kcs. to 32 mcs. in five bands, with 400 cps. modulation. The maximum R.F. output voltage is over 30 millivolts. Band selection is achieved by means of a coil turret. Coarse and fine attenuators are provided for R.F. and A.F. (400 cps) output. An out switch is provided, giving choice of a modulated or unmodulated signal or audio (400 cps) output, and an output jack and screened lead is provided for both R.F. and A.F. outputs. Mains input 100v 50-60 cps. Supplied in dark green crackle cabinet, provided with a removable cover, secured by four snap catches. Size $15\frac{1}{8} \times 6\frac{1}{2} \times 9\frac{7}{8}$ ". Supplied complete with instruction manual. A first-class job. Price £16/17/6. Carriage paid.

AUTO TRANSFORMERS. Radiospares. 200-250v to 110v 100 watts. Suitable for the U.S. Signal Generator. Price 30/- post free.

MOVING COIL HAND MICROPHONES. Moving coil-mike insert fitted-in bakelite case with "press to talk" switch. Price 4/6 post free.

HEADPHONES—TYPE HS38. Similar inserts, cord and plug to type HS33 previously advertised, but fitted with adjustable rubber supports for earpieces and rubber headbands. Impedance 600 ohms. Price 5/6 post free.

BENDIX RADIO COMPASS UNITS. Once again we are able to offer this excellent unit in first-class condition. 15 valves: 4 6K7, 2 6B8, 2 2051, 6N7, 6SC7, 6L7, 6J5, 5Z4, 200-1,750 kc/s. Makes a fine medium wave broadcast receiver. Price £4/17/6. Carriage paid.

BASES FOR VCR97 TUBES. 2/9 post free.

LIONEL AUTOMATIC BUG KEYS. Made for the U.S. Army by the Lionel Corporation of New York. Built on heavy black crackle base with all other parts plated. Complete with switch. Brand new, £2/11/6, post free.

METERS 0-1 ma. DC. FSD. 2" diameter. Sangamo Weston. Complete with mounting clip. Brand new and boxed. Price 10/-, post free.

0-1 amp FSD R.F. THERMO-COUPLE. Resistance 0-3 ohms. $2\frac{1}{2}$ " diameter with $\frac{1}{2}$ " flange. Brand new and boxed. Price 5/-, post free.

0-100 ma. D.C. FSD. Resistance 0-5 ohm $2\frac{1}{4}$ " square face. Hole required, 2" diameter. Actual scale calibrations, 0-300. Brand new and boxed. Price 7/-, post free.

24v DIMMER SWITCH BOX. Comprising one 200 ohm + 200 ohm wire-wound potentiometer, one 400 ohm potentiometer with switch (isolating slider from track), one SPDTM bakelite toggle switch, and two connector sockets. Mounted on bakelite base, size 6" x 4". New, 2/6, post free.

E.M.I. CATHODE RAY TUBES. $3\frac{1}{2}$ " Green screen. 800v H.T. Short persistence. Electrostatic deflection. Complete with base, 19/-, post free.

L.T. RECTIFIERS. 12v. In small bakelite case with 120 ohm resistor. 1/9, post free.

STOCK LINES

DOUGLAS MIDGET COIL PACK. Medium and long waves. Oscillator coil mounted on wavechange switch with separate aerial coil. I.F. 465 kc/s. Complete, with all trimmers, padders and circuit. Boxed 23/6, post free.

RESISTORS. 1 watt. All values. 8d. each. $\frac{1}{2}$ watt. All values, 4r. each.

ELECTROLYTIC CAPACITORS. T.C.C. Micro-pack, 8 mfd 450v.w., 5/3. T.C.C. 8 mfd 350v.w. 2/9. Dubilier 8 mfd 500v.w. Wire ends, 4/9. All tubular. All prices post free.

PAPER CAPACITORS. 4 mfd 500v.w. 4/6, post free.

VALUES! VALUES! VALUES! EF50, 7/6; 5R4GY, 7/6; VR75/30, VR90/0B3, VR105/30, all 12/6; 8B4, 18/9; 205G, 15/-; PT15, 32/6; RK34, 20/-; K78C, 25/-; TT11, 20/-; OP38/600 (equiv. T20), 21/-.

VOLUME CONTROLS. WIRE WOUND. 25 ohm 1 watt, 5/3; 50 ohm 1 watt, 5/3; 100 ohm 1 watt, 5/9; 300 ohm 6 watt, 4/8; 500 ohm 3 watt, 2/8; 1,000 ohm 3 watt, 2/7; 5,000 ohm 1 watt, 1/11; 10,000 ohm 1 watt, 3/6; 20,000 ohm 1 watt Varley, 7/3; 25,000 ohm 3 watt, 2/8; 10,000 ohm 3-watt, with switch, 7/10. Price 1/- extra (minimum), postage and packing.

VALVEHOLDERS—CERAMIC. 4-pin Eng., 5-pin Eng., 1/3; 7-pin Eng., 1/6; Int. octal, 1/6; Loctal (EF50), 6d.; 7-pin UX, 1/6; B7G, 1/6.

Faxolin. 7-pin Eng., 8d.; 9-pin Eng. (AC/PT), 2/6; CRT, 12-pin (with locating key), 2/8; 4-, 5-, 6- and 7-pin UX, all 9d.; Int. octal, 9d.

Amphenol. 4-pin Eng., 11d.; 5-pin Eng., 1/-; 7-pin Eng., 1/4; Mazda octal, 1/-; 4-pin UX, 11d.; 5-pin UX, 1/-; Int. octal, 11d.; American loctal, 6d.; B8A and B8G, 9d.; side contact, 2/3. Plus 9d. (minimum), post and packing.

METERS. Taylor Junior, 120A, £8/8/-; D.C. Avomminor, £4/10/-; Universal Avomminor, £8/10/-; Pifco radiometer, 25/-, Plus 1/6, post and packing.

THE "BRITAN" DIAL & DRIVE ASSEMBLY. An excellent all-wave dial of the airplane type. Covers 16-50 metres, 200-500 metres, 900-2,000 metres. Calibrated in wavelengths and station names. Glass dial with calibrations in green, yellow and white with white pointer. Size $8\frac{1}{2} \times 5\frac{1}{2}$ ". Supported in rubber cushions by black back plate with brackets for mounting on chassis. Complete with $1\frac{1}{2}$ " drive drum to fit $\frac{1}{2}$ " condenser spindle, and cord drive lead with $\frac{3}{8}$ " bush, and $\frac{1}{2}$ " spindle, 1 1/2" long. Price 18/8, post free.

A.M.C. DIAL AND DRIVE ASSEMBLY. A fine three-waveband dial assembly for superhet work. Scale finished in brown and cream and calibrated in frequency wave-lengths and station names. S.W. + 16-50 metres. M.W. 200-550 metres. L.W. 800-2,000 metres. Size of opening required, $10\frac{1}{2} \times 4$ ". Complete assembled ready for use, 22/9, post free.

Speedy Postal Service C.W.O. or C.O.D.

When sending C.W.O. please include sufficient extra for post and packing

Vallance & Davison Ltd

Dept. S.W.M.

144 BRIGGATE, LEEDS 1

Tel: 29428/9

Staff call signs: G2HHV, G3ABD, G3CML.

BUTLER RADIO

FAVERSHAM

Manufacturers of—

- VHF and UHF Components
- Co-axial Antennæ
- Inductances, etc.

Trade enquiries invited

Stockists of—


- G.E.C. and Eddystone Receivers and Components
- Philips Microphones
- E.M.I. Products

**76 PRESTON STREET
FAVERSHAM, KENT**


Telephone : Faversham 2004

(Right) Type 145C
Tuning Unit for
145 m/c band

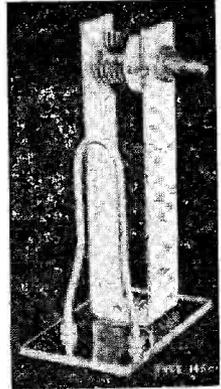(Below) Type 420A
Variable Line Induc-
tance for 420 m/c
band



Price list on applica-
tion

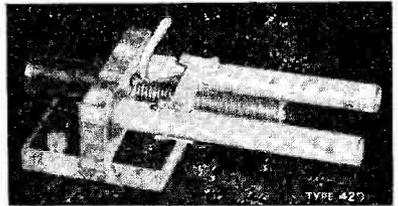

BENSON'S BETTER BARGAINS

R28/ARCS. Brand New. 100-150 mcs. Receiver with circ. diagram, 10 valves, less xtals, 45/-.
Receiver Type 76. 150-505 kcs. ECH35, EA39, EA50, in transit case, unused, 27/6.

RI355—Television Rx Unit. Brand New, 45/-, used 37/6.

R.F. Units. Type 25 17/6, Type 24 (converts to 25) 15/-.

PP-2/APQ-5 Amplifier with 4 6Y6, 2 5U4G, 1 6X5, 1 6SL7, 2 VR150/30, 45/-.

BC453, 454, 455. Spare I.F.S. set 7/6 (3). Spare coils, set of 3, 5/-.

28v Dynamotors 6/-. **Plug-On Mains Units** with 6 X 5 rectifier, 230v input, 250v D.C. and 12v A.C. output. Converts any of these Rx's to immediate mains operation, 47/6.

Metal Rectifiers—your enquiries invited. Many types at rockbottom prices.

Xtals. 7010, 8090 kcs 8/6. Odd frequencies 5'1 to 6'78, 7'3 to 8'9 kcs, 5/6.

Modulator Units BC456B. Boxed. 1 1625, 1 1215, 1 VR150/30, etc., 15/-.

Antenna Relay BC442A, metered, 6/-.

Toroidal Potentiometers. Ceramic, 12 ohms 5 amps $\frac{1}{2}$ amp, each, 8/6; 260 ohms $\frac{1}{2}$ amp, 5/-.

Vitreous Resistors, 35k 35w, 30k 25w, each, 1/-; 25k 15w, 1/3.

Carbon Pots. 5 meg, 3/6.

No. 19 Set Supply Units. 12v D.C. to 275 and 500v, 17/6.

SCR522 Supply Units. P.E.94 28v D.C. to 300, 150, 13v D.C. Dynamotor convertible to A.C. motor (approx. $\frac{1}{4}$ H.P.), 19/6.

Oil Filled Condensers. 4 mfd 1000v. w., 4/-;

Terms C.W.O. No C.O.D.

1 mfd, 1,500v.w., 2/6; .01 mfd, 1,000v.w., 9d.

Electrolytic 30 mfd, 100v.w., 1/-.

Chokes. 300 ohm, 100 mA, 4/6. **Toggles,** 9d.

Epicyclic drives, 1/3.

Bulgin Twin Fuseholders 1/-. **Tele. Jackplugs**

2-way or 3-way, 1/6 pair. **Slidlock Fuses,** 5 amp,

1/3.

Yaxleys 3-pole, 3-way, 3-bank, 3/6, 2-pole,

6-way, 1/6, 2-pole, 11-way, 2/6.

Camera Controls Type 35. Cased, 17/6.

Venier impulse clockwork movements, boxed,

120 p.m. 10 hr. running, 10/6. **American 36 hr.**

$\frac{1}{2}$ min. pulses, luminous, 15/- boxed.

Ferranti Pushpull Driver Transformers.

Double secondary, each 2 $\frac{1}{2}$: 1 boxed, 7/6. **Creed**

Highspeed Relays. 500 micro amps, boxed 15/-.

Convertible Dynamotors. With gearbox,

boxed, 17/6. **Less gears,** 12/6. **Headsets** with

mic. moving coil or carbon (Tannoy), 7/6.

Transceivers No. 38. Complete, boxed, less

connectors, 65/-.

Pulleys Composition, metal bushed, in holder 9d.

Valves. At 4/6—SR4GY, 6SN7, 6SL7, EF50,

6SH7, EF39, EF30, 9D2, VR150/30, 1215, 7C5,

7Y4, 7F7, 28D7, 1625, SP61, SP41, OZ4. At 3/-

6H6, EB34, EA50, 7193. At 7/6—6V6G, 6Y6G,

5U4G, 5Z4G, ECH35.

Callers Only. **Indicators** APN4, Type 62, 929A,

etc. **Bendix Rx's** 4 types. **SCR522's** with A.C.

Power Pack. T9/APQ2, BC348, R1155, 50 cycle

input Oscilloscopes, etc. etc., ad infinitum.

You are respectfully invited to enquire for any gear you may require. Immediate reply given. SAE please, enquirers!

Carriage Paid. Lists shortly.

BENSON'S, 308 RATHBONE RD., LIVERPOOL 13 - STONEYCROFT 1604

CLYDESDALE

For Bargains in Ex-Services Electronic Equipment

BRAND NEW IN MAKER'S
CARTONS

BC-436 SPEECH MODULATOR

A Unit of the SCR-274-N
(Command) Equipment

Employing screen modulation, complete with valves, 1625, 1215, and Stabilizer VR150/30, Transformers, chokes etc. (less Dynamotor) in metal case 10½ x 7½ x 4½ ins.


Clydesdale's price only **19/6** each post paid

Ex-U.S. NAVY. R/28ARC5 VHF Receiver. for 100-150 mc/s.

A 10-valve superhet complete with 4/717A's, 2/12SH7's, 2/12SL7's, 12SK7, 12A6, motor tuning, etc. (less dynamotor and Xtals) in metal case 13¾ x 7 x 4½ ins.

47/6 each

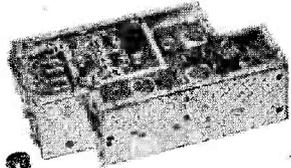Interested in Petrol Electric Generators? Large selection available, ask for special list.



Ex. R.A.F. Vernier Slow Motion Drive.



A Muirhead Unit with an illuminated escurcheon graduated in degrees, 0-180°. Ratio 38:1. Diameter 3". As used in R.F. Units, 26 and 27, fits standard spindle. A removable lamp holder plugs into the


top of the drive unit and provides a marked logging point.

Clydesdale's price only **9/6** each Carriage paid

BRAND NEW EX-TANK CORPS MORSE KEY

Enclosed type with knee straps, dimensions 5¾ x 2 x 2 ins. with lead and jackplug, easily removed from case. Key and Plug Assembly No. 9.

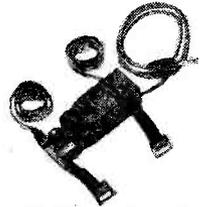Clydesdale's price only **2/11** each Post paid



BRAND NEW 12" RECORDING METAL DISKS

Lacquer coated, single sided
In sealed metal box, containing approximately 16.

priced at **35/-** per box Carriage paid



BRAND NEW, PORTABLE. Volt-ohm-meters with shoulder length carrying sling.

Scale calibrated to: 0-5000 ohms. 0-50 Ma. 0-1.5 Volts. 0-3 Volts. Range of Meter to: 0-500 ohms. 0-50000 ohms. 6 Ma. 60 Ma. 1-5 Volts.

Voltage Range can easily be extended by

adding resistances to suit individual requirements.

Clydesdale's price only **16/6** each Post paid

Meter is contained in black plastic case, size 3¾ x 3¾ x 2½ ins. with unsplinterable glass front and removable back having all the instructions printed on it.

E11. CARBON DESK- STAND MICROPHONE

Double button carbon mic. in moulded P.O. style mouthpiece on desk stand with weighted base, finish gloss black, height 12", base dia. 5¼", wire to 3 p. plug with 2 yds. 3 core flex.

Clydesdale's price only **10/6** each Post paid

New Ex-R.A.F. BATTERY AMPLIFIER A1368.

A 2 stage, 2 valve amplifier, for intercom, and Xmtr mod pre-amp, with valves VR35 (QP22B) VR21 (PM2HL) transformers, etc. Complete (less batteries) in black metal case 7 x 4½ x 4½ ins. Improved version of A1134.

Clydesdale's price only **11/6** each Post paid

Send now for New Illustrated Lists. Please print Name and Address

CLYDESDALE SUPPLY CO LTD • 2 BRIDGE STREET GLASGOW - C.5

'Phone: SOUTH 270619

VISIT OUR BRANCHES IN ENGLAND, SCOTLAND AND NORTHERN IRELAND

H. WHITAKER G3SJ

10 YORKSHIRE STREET, BURNLEY Phone 4924

MICROPHONES. Rothermel Xtal Torpedo, $8\frac{1}{2} \times 3\frac{1}{2}$ ", with chrome grill and chrome swivel arm, complete with plug and socket, and 8 ft. of screened cable. Sensitivity level minus 54db., impedance 80,000 ohm at 1,000 cycles. Flat response from 30 to 6,000 cy. List price £18/18/-. Brand new and boxed, limited quantity at £4/5 each ROTHERMEL D104, at £5. SHAFESBURY RIBBON, £12. STANDARD TEL. M.C. "Ball mike," £5. SHAFESBURY xtal, £3/10/-. U.S. Condenser, with push to talk button, T24., £5. POST OFFICE desk, 7/6. T.17 hand with push to talk switch, 5/-. M.C. hand, 7/-. R.A.F. Throat magnetic, 3/-. U.S. Lip, 2/6. SHURE carbon inserts foundation of a perfect mike by world-famous maker. 1/6.

U.S. POWER SUPPLY UNITS. TYPE 34H. Input 110/250v 50 cy. OUTPUT 1,100v 350 mills. D.C. 12v 14 amp. A.C. 10v 2 amp. D.C. for relays, mike energising, etc. FAN-COOLED THERMOSTATICALLY. PUSH-BUTTON STOP-START. ONE MINUTE THERMAL DELAY SWITCH FOR HIGH VOLTAGE. PROVISION FOR REMOTE CONTROL BY RELAY. THREE AUTOMATIC CIRCUIT BREAKERS, which trip if a short on TX. In welded steel cases with black crackle finish size. Weight 180lb. net. 230lb packed in original transit cases. PRICE COMPLETE WITH TWO 866 RECTIFIERS, £12. Carr. for. A FEW 34G, and 34E, with variable voltage control, and metered both A.C. and D.C., at £18.

CLAPP OSCILLATOR. Constructed from the well-known T.U. units, this Osc. rapidly coming to the fore with a stability equal or better than xtal. Its chief feature is its ability to key with a lag circuit WITHOUT CHIRP. The Clapp overcomes this difficulty with ease. Break in is an easy matter with a real T9 note. The unit has three stages with the 6C5 osc. stage, keyed for break in. This is followed by a 6F6 isolator with a 6V6 output, with a vr150 voltage stabiliser. The units are accurately calibrated with approx. 3 divisions per KC., and provided with CO-AX lead for either coupling to an existing xtal socket, or link coupling to the grid of a buffer, doubler. Three models available, 160/80, 80/40, 40/20, all of which are band-switched, and complete with valves and VR-150, but less power supply; a nominal power pack of 250/300v D.C., and 6-3 A.C. required for immediate operation. A really quality V.F.O. at the competitive price of £7/10/-. (Due to heavy demand delivery is approx. 7 days.)

MULLARD RES. CAP. BRIDGE. GM4140/1 230v A.C. mains, brand new in original cartons, £7. METERS FER. 0/150 mills 2" square. 7/6; WESTON 0/50 0/200, 0/500, 2 $\frac{1}{2}$ " round flush, 10/- each. 0/1 Weston, ditto, 14/-. Electrostatic Voltmeters, 4 $\frac{1}{2}$ " round flush, 0/5000v, 17/6. TAYLOR 0/500 mills, 3" round flush. 17/6.

XTALS. Ex-U.S. SIGNAL CORPS. Over 2,000 amateurs are already using these xtals with complete satisfaction. They are unrepeatable at the prices offered. Have you had yours? To commercial users and others we have good stocks available in most freqs. Your enquiries welcomed. All are by the leading American manufacturers, Biley, R.C.A., Stand, M.P., etc. All are in sealed holders, with raised edge air gap plates, in standard U.S. FT4 type holders, with half-inch pin spacing, except B.C.610 type, which are $\frac{3}{8}$ ". SPECIAL OFFER FOR 28Mc BAND. 7,300/7,500 kc. (X4). LIMITED QUANTITY. OUR CHOICE OF FREQ. 7/6 each, 72/- per doz.

7,000/7,300 kc., any freq., plus-minus 1kc., 12/6. 3,500/3,800 kc., any freq., plus-minus 1kc., 15/-. FOR 144 MC BAND. 6,000/6,083 kc., 8,000/- 8,220 kc., 9,000/9,250 kc., any freq., 15/-. For I.F.'s 290/400 kc., 800/1,040 kc., with the exception of 1,000 kc., 12/6.

R.C.A. 100kc., 30/- (U.S. 3-pin HOLDER). PRACTICALLY ANY FREQ. OUTSIDE THE AMATEUR BANDS. Quotations by return.

RAVON TEST METERS. Brand new and boxed. Size 8" x 6 $\frac{1}{2}$ " x 3" with carrying strap. A.C. volts 0/10, 0/100, 0/500, 0/1,000. D.C. volts, 0/1, 0/10, 0/100, 0/500, 0/1,000. Mills. 0/5, 0/10, 0/50, 0/100, 0/500. Watts 0/4. Resistance point 2 of an ohm to 20 meg, in four ranges. Capacity 100pf to 1 mf, in two ranges. Millivolts 0/100. All ranges by 21-way rotary switch. Complete with fused test prods. The moving coil is pivoted with sapphire jewels. Knife edge pointer with anti-parallel mirror. The meter is housed in high grade black bakelite moulded case, highly polished with all edges rounded. A grand bargain at £10.

ELECTROLYTIC CON. Metal can, 20mf. 50v wkg., one-hole fixing, in sealed cartons and perfect condition. 1/-, 10/- doz.

VALVEST.X. 805, 45/-; 807, 12/6; 808, 37/6; 811, 45/-; 813, 70/-; 814, 40/-; 100th, 60/-; 250th, 100/-; 304th, 100/-; HK257b, 60/-; 1,£25, 6/- (60/- doz.); 2C26, 10/-; 2C22, 4/- (36/- doz.); 832, 17/6.

RECTIFIERS RG240/A, 20/-; 866, 25/-; 836, 20/-; 6XS, 5W4, 5U, 5V4, all 7/6. 5U4, 10/-; 5R4 GY, 7/6.

BUTTON BASE. 1001, 1A3, 1S5, 1T4, 3S4, 3A4, 1R5, all 7/6; 955 acorn, 7/6.

VALVES. RX.6J7, 6SJ7, 6K7, 6SK7, 6G6, 6SH7, 6AC7, 1852, 6SC7, 6J5, 6C5, 6R7, 6SG7, 6H6, 6SL7, 6K6, 6Q7, 6Y6, 1LN5, 1A5, 117Z6, 12SK7, 12A6, 12SR7, 12SG7, 12K8, 12SA7 12S7, 12I5, 12C8, 9004, all at 7/6. 6V6, 6N7, 6SN7, at 8/- 6L7, 1316, at 10/- 6L6, 12/6.

VALVES UNBOXED. A large quantity of 6H6, and 6SH7, taken from IFF units. All are new and guaranteed perfect to clear at 24/- a doz.

TUNING INDICATOR. 6E5 at 8/-. Selenium cell, R.C.A., 923 UX base, 17/6.

VALVE HOLDERS. ALL CERAMIC. OCTAL, 1/-; 4-PIN UX, 1/-; 807, 1/3. R.C.A. 813, 7/6. LOCTAL, 6d. 4-pin Jumbo, 6/-.

SMOOTHING CHOKES. 1,500v, 500 mills 15hy, 25/-; 1,000v, 10hy 150 mills, 10/6; U.S. Potted, 150 mill, 5/9; 250-mill 7/6. SWINGING, 2 $\frac{1}{2}$ to 24 hy, 450 mills, 10,000v insulation, 30/-. COSSAR twin L.F., 4 hy 90 mills + 4 hy 90 mills, 6/-.

VITREOUS RESISTORS. 225 ohm, 20 watt, 5,000 ohm 20 watt, 35,000 ohm 35 watt, all at 1/-; 50,000 50 watt, at 2/-; 20,000 120 watt, at 2/-.

TO AR88 USERS

Are you satisfied with the performance of your AR88, or would you like to improve it? The signal to noise ratio can be improved beyond all recognition, especially on 10 metres, by the simple expedient of replacing your first R.F. amplifier valve 6SG7, by a 717a, and re-trimming the R.F. stage only. It has to be heard to be really believed, especially on 10, and makes a wonderful difference to be able to turn up that R.F. gain, and hear signals O5 that are normally S3 due to noise. We can supply this valve R.F. Pen 717 a mushroom Amp. at 12/6.

CELESTION

The quality of reproduction secured from Celestion Speakers greatly increases the pleasure of radio in the home.

The model illustrated has an attractively designed Cabinet with a special mahogany finish, it employs an 8" speaker of high sensitivity and excellent response. It is fitted with a volume control and is one of the finest 8" extension speakers available.

All interested in other Celestion Cabinet and Chassis models should write for Illustrated Brochure "S.W."


WHERE TO BUY CELESTION SPEAKERS
The Public are requested to order from their local Radio Dealer.

Wholesalers are supplied by the Sole Distributors: CYRIL FRENCH LTD., High St., Hampton Wick, Middx. Phone: KINGston 2240.

Manufacturers should please communicate direct with:

CELESTION LTD., SUMMER ROAD, THAMES DITTON, SURREY

Telephone: **Emberbrook 3402-5**

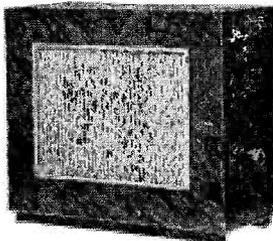

STANDARD 8 CABINET MODEL

Mahogany finish

Size: Height 10" Width 12" Depth 5 1/2" **PRICE £3:18:0**
Price with Universal Transformer **£4:4:0**

Technical Details of CHASSIS Model for use with your own cabinet. Dia. 8". Baffle opening 7 1/2". Voice coil impedance at 400 cps., 2.3 ohms, Pole dia. 1". Flux density gauss, 8,000. Total gap flux, 31,000. Peak power capacity 4 watts.

Price less transformer **£1:17:6**
(Suitable for outputs 1-5 ohms)

Price with Universal transformer **£2:3:6**
(Suitable for all Receivers)

LASKY'S RADIO

★ FEBRUARY SPECIALS

FOR CALLERS ONLY

STANDARD RACKS (Ground station type 3)
Complete with amplifier, type 10A/9589. Power unit, type 6, operating from 230v 50 c.p.s. input. Lower control unit, type 10A/9590. Remote control unit, type A (less valves). There is only a limited quantity of these most excellent bargains. Condition varies from brand new. Dimensions: 20" wide, 64" high.

LASKY'S PRICE, FROM **99/6**

FOR CALLERS ONLY

AERIAL MASTS

32 ft. high in 9 sections. Complete with aerial. The complete kit is supplied in canvas carrying case with handles.

LASKY'S PRICE **69/6**

MODULATOR UNIT, TYPE 64

Containing 7 valves: 2 EF50, 1 807, 2 high voltage rectifiers, type CV54, 1 CV85 (special type), 1 CV73. Also 3 relays, high voltage condensers, resistances, pot/meters and other components. Enclosed in metal case, size 10" x 18" x 6". Weight, 30 lb.

LASKY'S PRICE **22/6** Carriage 5/ extra

BRAND NEW AND UNUSED IN ORIGINAL WATERPROOF WAXED CARTONS

No. 19 SET POWER SUPPLY UNITS

12/24v input. Contains 275v vibrator supply, and 500v motor generator supply, fully smoothed and fused. Unit supplied complete with spare vibrator, and spare 0Z4 rectifier, also all connecting plugs and leads. Operating and instruction booklet supplied with each unit. A BEAUTIFUL PIECE OF WORKMANSHIP.

LASKY'S PRICE **45/-** Carriage 5/- extra

AERIAL RODS

The sectional type as used in the Walkie Talkie Mk. 58. Each rod is steel, heavily copper-plated and sprayed khaki. Length 14". Any number of rods can be fitted together.

LASKY'S PRICE **3/-** per dozen, post free

INDICATOR UNIT, TYPE 62

Containing 20 valves and a 6" cathode ray tube, type VCR97 (short persistence). Valve line-up: 16 SP61, 2 EA50, 2 EB34. Dozens of useful components, resistances, condensers, 117 Mc/s crystal, 16 pot/meters, etc. Totally enclosed in metal case, size 18" x 8 1/2" x 11". Weight, 40 lb. Enamelled grey or black with coloured control knobs.

LASKY'S PRICE **59/6** Carriage 7/6 extra

The cathode ray tube is tested before despatch.

Send a 2½d stamp for our current monthly bulletin of ex-Government bargains.

LASKY'S RADIO, 370 Harrow Road, Paddington, London, W.9
(Opposite Paddington Hospital)

Telephone: CUNningham 1979.

Hours: Mon. to Sat., 9.30 a.m. to 6 p.m. Thursday half-day.

PREMIER RADIO

MORRIS AND CO. (RADIO) LTD.,

All Post Orders To: JUBILEE WORKS, 167 LOWER CLAPTON RD.
LONDON, E.S. (Amherst 4723, 2763, 3111)

NOW OPEN. LARGE NEW PREMISES AT
152 & 153 FLEET STREET (Central 2833)

NOW OPEN. NEW BRANCH AT
207 EDGWARE ROAD, W.2 (Ambassador 4033)

GOVERNMENT SURPLUS MAINS TRANSFORMERS. All are for use on 230v 50 cycle mains.

| | | |
|------|---|------|
| Type | | |
| 33 | 38v 2a. Tapped at 32, 34, 36v | 15/- |
| 42 | 500-0-500v 170mA 4v 4a | 25/- |
| 44 | 10v 5a, 10v 5a, 10v 5a | 35/- |
| 50 | 12v 70a. An ideal Transformer for soft heating or welding.. | 60/- |
| 51 | 350-0-250v 60mA, 6.3v 1a, 6.3v 2.5a | 12/6 |
| 58 | 250-0-250v 60mA, 5v 2a, 6.3v 2.3a | 15/- |
| 54 | 275-0-275v 60mA, 5v 2a, 6.3v 2.3a | 15/- |
| 55 | 250-0-250v 100mA, 5v 2a, 6.3v 3.5a | 17/6 |
| 56 | 330-0-330v 70mA, 5v 2a, 6.3v 2.3a | 17/6 |
| 57 | 300-0-300v 70mA, 4v 2a, 4v 3.5a | 17/6 |

E.T. TRANSFORMERS. For 200-230v 50c input half wave. For use with valve or metal rectifier. Used in a voltage doubling circuit, these will give slightly over double the half-wave output. We can supply suitable rectifiers.

| | | |
|-----------|--------------------------|------|
| E.H.T. 1. | Output 800v | 17/6 |
| E.H.T. 2. | Output 1,000v and 2-0-2v | 25/- |
| E.H.T. 3. | Output 2,000v and 2-0-2v | 35/- |

MINE DETECTOR PANELS. include three IT4 valves, 12-1 Midget Trans., three ceramic valveholders, 15 condensers and resistors, etc. 20/-. Without valves, 9/-.

WIRE WOUND RESISTORS. 50K : 0 watt, 4/-, 20K 200 watt, 4/-, 2K +12K 150 watt, 4/-, 75K 100 watt, 4/-, 350 Ω 75 watt, 2/-, All vitreous enamelled.

TELEVISION MAGNIFYING LENS. Suit any 5", 6", or 7" tube. Increase picture size considerably, 29/6.

P.P. DRIVER TRANS. Split Sec, super quality, 10/-.

METERS

| Deflec- tion | Mark- ing | External Dimen- sions | Movement | Price |
|----------------|-----------|-----------------------|----------|-------|
| 1mA 0-100 | 31" | M/C | 15/11 | |
| 1mA 0-1 | 21" x 21" | M/C | 7/6 | |
| 5mA 0-5 | 21" | M/C | 5/- | |
| 30mA 0-30 | 31" | M/C | 10/6 | |
| 50mA 0-50 | 21" x 21" | M/C | 8/6 | |
| 150mA 0-150 | 21" | M/C | 8/- | |
| 250mA 0-250 | 31" | M/C | 10/6 | |
| 2-5 amp. 0-2.5 | 31" | Thermo. | 5/- | |
| 15v 0-15 | 31" | M/I | 7/6 | |
| 20v 0-20 | 21" x 21" | M/C | 5/9 | |
| 40v 0-40 | 21" x 21" | M/C | 5/9 | |
| 5000v 0-5 | 4 1/2" | Elect. | 50/- | |
| 500mA 0-500 | 21" | M/C | 7/6 | |

ALUMINIUM CHASSIS

Substantially made of bright aluminium with four sides.

| | |
|----------------------|------|
| 7" x 3 1/2" x 2" | 4/6 |
| 9 1/2" x 4 1/2" x 2" | 5/6 |
| 10" x 8" x 2 1/2" | 7/- |
| 12" x 8" x 2 1/2" | 7/9 |
| 14" x 9" x 2 1/2" | 8/3 |
| 16" x 8" x 2 1/2" | 8/6 |
| 20" x 8" x 2 1/2" | 10/6 |
| 23" x 10" x 2 1/2" | 13/6 |

2v BAKELITE CASED ACCUMULATORS by Oldham, Dagenite, Exide, etc. New and unused, unspillable vents. 7" x 4" x 2", each 8/6

BATTERY CHARGER KITS. 6v 1a (tapped at 2v), 22/6, 12v 1a .. 27/6 (These incorporate Metal Rectifiers and Transformers. For 200-250v, A.C. mains.

SECTIONAL WHIP AERIALS. Seven sections which plug into each other making an Aerial 14ft. long .. each 3/6
Insulated Bases .. each 2/6

C.R. TUBES. VCR97, 6" diameter, green screen, 4v 1a. Heater, 2,500v max. H.T. Complete with socket, in maker's original cartons, 35/-.

C.R. TUBES. E.M.14/1 Cathode Ray Tubes 3 1/2" diameter, green screen, short persistence, 4v 1.5a Heater, 800v H.T. Complete with socket, 17/6 each.

NEW TRF RECEIVERS
Complete and ready for use in Bakelite Cabinet, 12" x 6" x 6".
3 Valves plus metal rectifier, medium and low wavebands.
A.C. or A.C./D.C. for 200-250v mains.
Pre-War Price £7/19/6 including P.T.

R.1155 POWER SUPPLY UNIT (incorporating output stage). A robust unit contained in a black enamelled case, 10" x 8" x 6", which makes the receiver. There are two models for 100-250v 50 cycle mains. Each one gives an output of 250v at 80 mA, which is ample for the R.1155 with the output stage. With output stage, 70/- Power pack only, 50/-.

P.M. LOUDSPEAKERS by amous makers. 5" W.B. or Truevox. 2-3 ohms, 10/-; 5" Celestion, 2-3 ohms, 12/6 5" Rola, 2-3 ohms, 16/6; 8" Rola Magnavox, 2-3 ohms, 17/6; 6" Rola 2-3 ohms, 16/6; 8" Rola, 2-3 ohms, 17/-; 10" Rola, 2-3 ohms, 23/6; 12" Rola, G12, 15 ohms, 35/-. Output transformers H.T. required for above 2/11 extra (except G12).

COLLARO ELECTRIC GRAMOPHONE MOTOR with "12" turntable. A.C. 100/250v.

CONRAD ELECTRIC GRAMOPHONE MOTOR. 9" turntable. 200/250v A.C. 57/6
All above motors include purchase tax.

NEW 2-VALVE ALL WAVE KIT. 15 to 2,000 meters. Switched Coil Pack ready wired and tested. 2 Mazda H123 Valves, Phones, H.T. and L.T. Batteries, Condensers, resistors, diagrams and steel case, all ready to assemble, £3/10/-, including P.T.

MIDGET RADIO CIRCUITS in Brown Bakelite. Can be supplied for the above Midget Kit at 25/-, including P.T.

MIDGET SUPERHET RADIO KIT with Illuminated Glass Dial. All parts including Valves, M/O Speaker and Instructions. 4 valves plus Metal Rectifier. 15-30 metres and 200-257 meters. 200 to 250v A.C. or A.C./D.C. mains. Slate which is required. Size, 10" x 6" x 6". £8/5/-, including Purchase Tax.


THE FAMOUS R1155 RECEIVER
Frequency range, 18.5 mcs-75 kcs. in 5 wavebands. 10 Valves including magic eye, completely enclosed in black metal case 18" x 9" x 9", £8/8/-. All tested and in perfect order.

Valves at Low Prices—6SN7, 6/6; 12SR7, 6/6; 6SH7, 6/6; 6F5, 5/-; 12SN7, 6/6; 1T4, 6/-; 12RH7, 7/3; 12BL7, 7/6; 6K7 met, 7/6; 6B7, 5/-; 6B9, 5/-; 6J7G, 7/6; 6K7, 7/6; 7H7, 5/-; 7C7, 7/6; 7Q7, 6/8; VR95-954, 4/-; OV172, 5/-; OV73-1125, 10/-; VU11-V1907, 10/-; V870-745, 7/6; VR57-SK32, 7/6; CV67, 10/-; VR78-D1, 2/6; VU39-MU14, 7/6; OV6-DET20, 5/-; VR65-SP81, 3/6; VU133-VU60, 10/-; 3B24, 10/-; VR503-KT33c, 7/6; VR1-E660, 5/-; VR92-EA50, 5/-; VR13B-EE54, 7/6; VR50A-807, 7/6; VR115-V872, 10/-; VR54-EB34, 3/6; VR56-EP36, 6/-; 9D2, 7/6; 8D2, 7/6; 15D2, 7/6; 4D1, 7/6; 110C, 10/-; 11A5, 8/6; 11D5, 7/6; 3D6, 3/6; 9005, 6/6; 6S67, 6/6; 6X5, 7/6; 5U4, 6/-; 892, 25/-; 832, 25/-; 931A, 23/-; 634, 5/-; 6AC7, 5/-; 5B4, 5/-; 6V6, 5/-; 6SK7, 5/-; 6SL7, 5/-; 6SA7, 5/-.

COLLARO AUTO CHANGERS. Mixer-changer rim-drive. High fidelity, crystal pick-up. Repeat reject mechanism. £14/6/8.

COLLARO AC/DC GRAMOPHONE MOTORS, with turntable, but without pick-up or auto stop, £8/5/6.

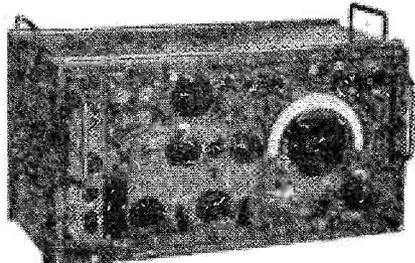UNIT TYPE AS582A. Brand new, contains two ceramic base 807, one 5U4G, one EF50, one EA50. A large quantity of condensers, chokes, resistors, etc. 30/-.



R107. ONE OF THE ARMY'S FINEST COMMUNICATIONS RECEIVERS. (See "N.W.", August, 1945), 9 valves, R.F. amp. acc. Frequency Changer, 2 P.T.'s (435 kh, 2nd Detector), AVC. Af. amp. A.C. mains, 100-250v or 12v acm. Frequency range 17.5 to 7 mc/s, 7.25 mc/s to 2.9 mc/s, 3.0 to 1.2 mc/s. Monitor L.S. built in. Complete. Write for full details. £16/16/-, Carriage Paid.

NEW DECEMBER CATALOGUE NOW READY

INDEX TO
ADVERTISERS

| | |
|-----------------------------------|------------------|
| | <i>Page</i> |
| A.C.S. Radio..... | 916 |
| Amateur Radio Service.... | 912 |
| Automatic Coil Winder.... | 841 |
| Barnes Radio | 914 |
| Belling & Lee | 856 |
| Bensons | 850 |
| Berry's Ltd..... | <i>Cover iv</i> |
| B.I.E.T. | 910 |
| Bird, S. S. | 911 |
| Brighton Trade Services.... | 915 |
| Brookes Crystals Ltd..... | 911 |
| Brown, S. G..... | 843 |
| Bulls, J. | 907 |
| Butler Radio..... | 850 |
| Candler System..... | 917 |
| Carlton Coil Winding..... | 920 |
| Celestion | 853 |
| Clydesdale Supply Co. Ltd.... | 851 |
| Coulphone Radio..... | 919 |
| Dale International | 907 |
| Davis, Alec, Ltd. | 904 |
| Electradix Radios..... | 914 |
| E.M.I. | 905 |
| Fanthorpe | 909 |
| Fields | 905 |
| Fon Radio | 919 |
| Frith Radiocraft | 918 |
| G.L.G. Radio | 920 |
| General Sound & Vision Co. | 904 |
| H.A.C. Short-Wave Products | 920 |
| Haynes, A. G. | 917 |
| Henleys | 847 |
| Hoile, A. C. | 915 |
| H.P. Radio Services Ltd..... | 914 |
| Instrument Co. | 848 |
| Johnsons | 915 |
| Lawrence G. | 845 |
| Laskys | 853 |
| Lyons Radio..... | 912 |
| M.O.S. | <i>Cover iii</i> |
| Multicoore | 856 |
| Odeon Radio..... | 911 |
| P.C.A. Wireless | 914 |
| Pill & Partners..... | 913 |
| Premier Radio | 854 |
| Pullin (M.I.)..... | 905 |
| Radford, Arthur H. | 842 |
| Radio & Elect. Mart | 908 |
| Radio Clearance | 844 |
| Radiocraft | 916 |
| Radiographic | 908 |
| Radio Exchange | 909 |
| Radiovision (Leicester) Ltd. | 842 |
| Samsons Surplus Stores | 845 |
| Short Wave (Hull) Radio..... | 904 |
| Small Advertisements..... | 914-920 |
| Smith, H. L. | 919 |
| Smith, M. F. | 918 |
| Southern Radio Supply Co. | 913 |
| Southex Trading | 920 |
| Tele-Radio (1943) Ltd..... | 843 |
| Torbay Electric..... | 910 |
| U.E.I. Corp. | 910 |
| University Radio | 918 |
| Vallance & Davidson Ltd.... | 849 |
| W.D. Sales | 906 |
| Webb's Radio | <i>Cover ii</i> |
| Weston Products | 846 |
| Whitaker, H. | 852 |
| Whiteley, T. A. | 848 |
| Woden Transformers | 847 |
| Young | 913 |

SHORT WAVE MAGAZINE

FOR THE RADIO AMATEUR & AMATEUR RADIO

Vol. VI FEBRUARY 1949 No. 67

CONTENTS

| | |
|---|-------------|
| | <i>Page</i> |
| Editorial | 857 |
| Broad-Band Exciter by V. J. Copley-May (G3AAG)..... | 858 |
| Backyard Skywire by L. H. Thomas, M.B.E. (G6QB)..... | 862 |
| Full-Power Modulator by F. H. Lane (G3GW) | 865 |
| TUSB on Top Band by A. P. Kerford-Byrnes (G6AB)..... | 866 |
| DX Commentary by L. H. Thomas, M.B.E. (G6QB)..... | 870 |
| Power Pack Design, Part I by P. E. Leventhall, B.Sc. (G3CJJ)..... | 877 |
| Two-metre CC Converter by M. D. Mason (G6VX) | 881 |
| The VHF Bands by E. J. Williams, B.Sc. (G2XC) | 887 |
| Another Modulation Monitor by A. B. Wright (G6FW)..... | 892 |
| Other Man's Station—G8GI | 897 |
| New QTH's | 898 |
| Here and There | 899 |
| “QC MCC”—Results Magazine Club Contest | 900 |

Editor: AUSTIN FORSYTH, O.B.E. (G6FO)

Advertisement Manager: P. H. FALKNER

Assistant Editor: L. H. THOMAS, M.B.E. (G6QB)

Published the first Wednesday each month at 49 Victoria Street, London, S.W.1
Telephone: Abbey 2384. Annual Subscriptions: Inland 20s. Abroad 22s. post paid



Copyright Reserved throughout the World

AUTHORS' MSS.

Articles submitted for editorial consideration must be typed double-spaced with wide margins, on one side only of quarto sheets, with diagrams shown separately. Photographs should be clearly identified on the back. Payment is made for all material used, and a figure quoted in the letter of acceptance. It is a condition of acceptance that copyright of all material used passes to the Short Wave Magazine, Ltd., on publication.

THE SHORT WAVE LISTENER ASSOCIATED WITH THIS
MAGAZINE IS SPECIALLY FOR THE RECEIVING ENTHUSIAST

'BELLING LEE' AERIAL SPARES

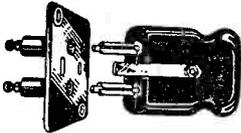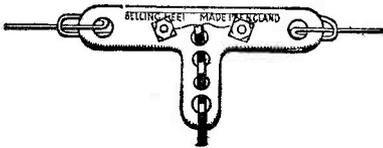

'T' STRAIN INSULATOR

Designed to take the feed from the centre of a half-wave dipole.

L333 in porcelain. Price each 3s. 3d.

Y7713 80 ft. lengths of cadmium copper aerial wire. Price each 9s. 0d.

BALANCED TWIN FEEDER

L336 75-85 ohm. Per yard 7½d.

L334 65 ft. of L336 on reel, each 13s. 6d.

Y772 80 ft. lengths of L336, each 16s. 9d.

TWO-WAY CONNECTORS

L607/PG 2-pin plug, each 2s. 10d.

L607/SI L607/S2 2-way sockets, each 6d.

"Fouling pin" on plug provides non-reversability with socket S.1 and reversability with S.2.


BELLING & LEE LTD

CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDDXX

THE EFFICIENCY OF YOUR APPARATUS MAY DEPEND ON

A ha'porth of solder

It costs only about a ha'penny more to make 500 joints with Ersin Multicore Solder than it does with cheap solder. Ersin Multicore Solder gives you a guaranteed standard of sound precision joints, and high-speed soldering with freedom from 'dry' or H.R. joints. Your transmission and reception depend on this standard of quality, and it costs so little to ensure it. Be sure — use only Ersin Multicore Solder.

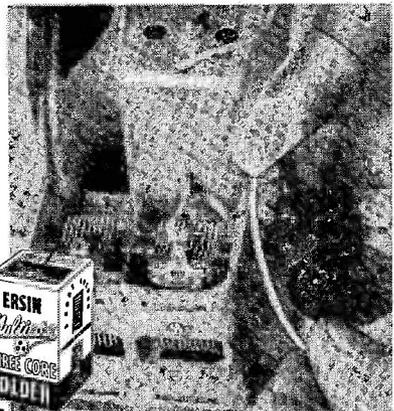

PRICES SIZE 1 CARTONS

| Catalogue Ref. No. | Alloy Tin/Lead | S.W.G. | Approx. length per carton. | List price per carton (subject) |
|--------------------|----------------|--------|----------------------------|---------------------------------|
| C16014 | 60/40 | 14 | 32 feet | s. d. 6 0 |
| C16018 | 60/40 | 18 | 84 feet | 6 9 |
| C14013 | 40/60 | 13 | 20 feet | 4 10 |
| C14016 | 40/60 | 16 | 44 feet | 5 3 |

ERSIN MULTICORE SOLDER

MULTICORE SOLDERS LTD., MELLIER HOUSE, ALSEMARLE STREET, LONDON, W.1.

REGent 1411

EDITORIAL

Facts

The time has now come when we should be expecting the Atlantic City decisions still outstanding to be implemented—in particular, the release of the promised 21 mc band, which has apparently already been made available in some countries.

When 15 metres is opened to us, British amateurs in particular may feel that they are well provided for in the useful part of the spectrum. Broadly, we have coverage from one to ten thousand megacycles. It is true that frequencies above about 500 mc, though of considerable interest to the pure experimenter, are of little present use for amateur *communication*—and it is upon the essential factor of two-way communication that the whole structure of international Amateur Radio rests.

In this matter of frequency allocations, there are a few plain truths which all amateurs should bear in mind. We do not get our bands because the authorities think we deserve them, nor because we are expected to make new discoveries, nor even because the amateur organisations are strong enough or sufficiently influential to compel an allocation. We get our bands because they are reserve frequency areas of vital importance in time of war ; amateur occupancy of these bands ensures that they are kept open for immediate taking over should the need ever arise. And by the same token, amateurs themselves comprise an important, not to say indispensable, reserve of technical man-power for the communications branches of the Services.

So we see that it is a fair assumption that Amateur Radio, to the present general pattern, will always be allowed to continue so long as the frequencies we occupy in peace can be used to advantage in war. This solemn thought may serve to dispel certain widely-held and carefully fostered misconceptions as to how and why Amateur Radio is able to continue to expand and develop in its own way.

Austin Forsyth G6FO.

Broad-Band Exciter

Using Labgear Couplers

By V. J. COPLEY-MAY (G3AAG)

THE appearance of a design for an exciter unit within these pages can by no stretch of the imagination be heralded as a novelty; however, the author hopes that the "broad band" exciter described here brings out a few unusual features that will warrant the attention of readers.

On looking through past *Magazine* articles on exciters one gets the impression that the designs are all very similar and any individuality they possess is achieved mainly in the method of layout and construction.

Having built an exciter of conventional type some two years ago and persevered with its inadequacies, an attempt to design and build a new unit eliminating the snags of the old one looked like being time well spent, even if it only served to discontinue temporarily the author's contribution to the local QRM!

To tabulate the failings of earlier exciters will show the advantages of this BB exciter, as each one of the obstacles has either been overcome or reduced to insignificance in the design now presented.

- (1) The requirement for retuning when changing from one end of a band to the other, or band changing. In some designs a succession of stages has to be retuned and—horror of horrors—*coil changing* is necessary.
- (2) Too high a power consumption considering what the unit is doing. Unnecessarily large valves used for doubling.
- (3) Lack of flexibility.
- (4) Tendency for the generation of undesired harmonics.
- (5) Too many knobs.
- (6) Inaccessibility.

To suggest that earlier designs possess *all* these faults would of course be a gross injustice; many of them are excellent, but as the writer sees it, all have at least one of these snags.

Design

Employment of Labgear Broad-Band Couplers eliminated the first failing and the use of wafer switches in band changing looked after the fifth point.

The examination of the complete circuit in Fig. 1 shows that a single 807 is employed as a straight-through amplifier for

A very desirable feature of any good exciter is that while being one-knob control on the VFO, it should provide full drive over a wide band of frequencies without inter-stage tuning adjustment in the exciter itself. The unit here described meets this requirement by the use of Labgear wide-band couplers, which eliminate tuning operations between stages. This exciter can also be used as it stands as a QRP transmitter.—Ed.

driving the PA and provides adequate drive for almost any PA encountered in normal amateur practice.

The straight-through use of the 807 allows the exciter unit to be operated by itself as reasonably efficient QRP transmitter. The tank circuit of this valve is of turret construction and home manufacture; full details are given herewith. Output is provided on 3.5, 7, 14, 21 or 28 mc with either internal or external VFO.

It must be admitted that the inclusion of the VFO was rather an afterthought, as one VFO is already available at this station; however, space being available and the possibility existing that the unit may some day be required for Field Day or self-contained QRP operation encouraged the incorporation of a good VFO. In addition, it was desired to experiment with the Clapp version of the Colpitts oscillator. Little need be said of the Clapp circuit except that it is a considerable advance on the conventional ECO and even shows a marked improvement on the triode-connected Colpitts from the point of view of stability and keying characteristics. In this last feature, the Clapp scores heavily in that the keying characteristics are almost unaffected by the inclusion of keying lag circuits. BK is thus possible.

V1 and V2 (*see* circuit) are oscillator and isolator respectively. Note that a valve of low *cga* and high effective stage gain characteristics is used in the V2 position. V3, V4, V5 and V6 are cathode-follower, 3.5 to 7, 7 to 14 and 14 to 28 mc doublers; 21 mc output is obtained by tripling in the driver from the 7 mc doubler.

The use of a cathode-follower is one way to present a reasonable match to the co-axial input from the VFO without using an input tuned circuit with the possibility of undesired feedback. The screen and grid are effectively earthed, and oscillation becomes a virtual impossibility.

The Labgear units are really band-pass

couplers with link coupling between tanks; the "pay off" (as the W's might say) being that one has a large number of tuned circuits to get to a desired frequency and the consequent discouragement to the amplification of TV harmonics.

The output tank is neither of high Q nor highly efficient design but is quite adequate for the purpose. Examination of the photograph showing the under-side of the chassis illustrates how all decoupling leads associated with the doublers are taken to one earthing point, made possible by the arrangement of valves and tuned circuits. No leads are more than half-an-inch long and parasitics are thereby considerably discouraged.


The photographs and circuit give the whole story and naturally considerable tolerance is acceptable in the choice of individual components. Components that that should be within + or - 10 per cent. are starred, and some additional information governing the reason for the selection of components is given in the list.

Operation


At G3AAG no unit works the first time it is installed in the rack—there are always initial teething troubles. However, with

this unit the only set-back on switching on was a DC arc from one of the tank circuits to the link, a fault remedied in the design of Fig. 1. Once corrected, the unit performed as anticipated and was entirely free from any parasitics or snags. One of the first contacts with a local confirmed that the signal was clean and free from "whiskers."

Operation and adjustment are fairly obvious, but a few hints may help to get the best out of the unit. Power supplies being connected, and assuming that wiring is correct, connect excitation or key the VFO, setting the frequency to the middle of the band. The trimmers of the band-pass couplers (not the cores) should be adjusted for maximum urge to the driver grid (about 1 mA) on all ranges. Swinging the VFO from one end of the band to the other (PA off, *please!*) should not affect the drive very much. With the unit as used at G3AAG the change is 0.1 mA (0.9 mA at edges, 1 mA in the middle of the band). The appropriate tank coil should be selected and tuned for minimum dip in the plate meter. The plate current dips from about 70 mA to only 20 mA, indicating a pretty poor tank circuit, *but* also indicating that re-

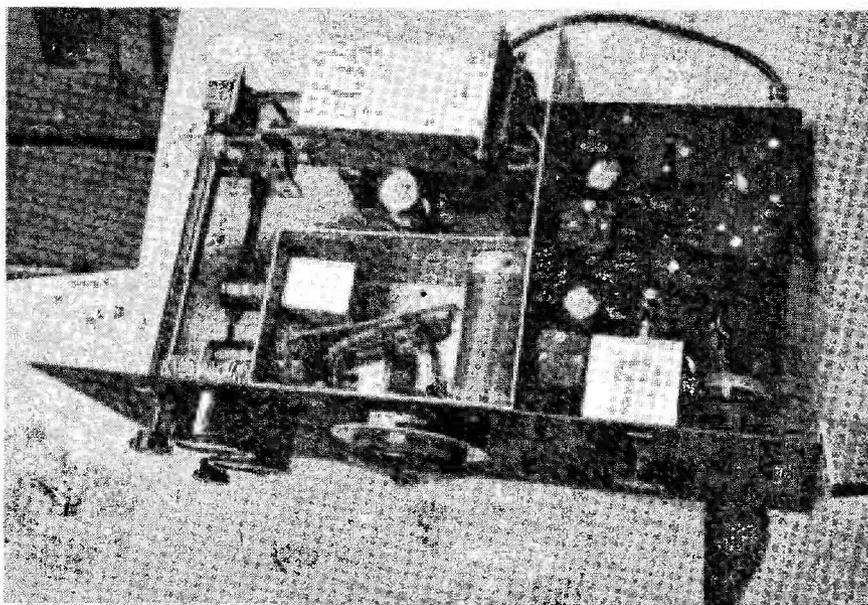

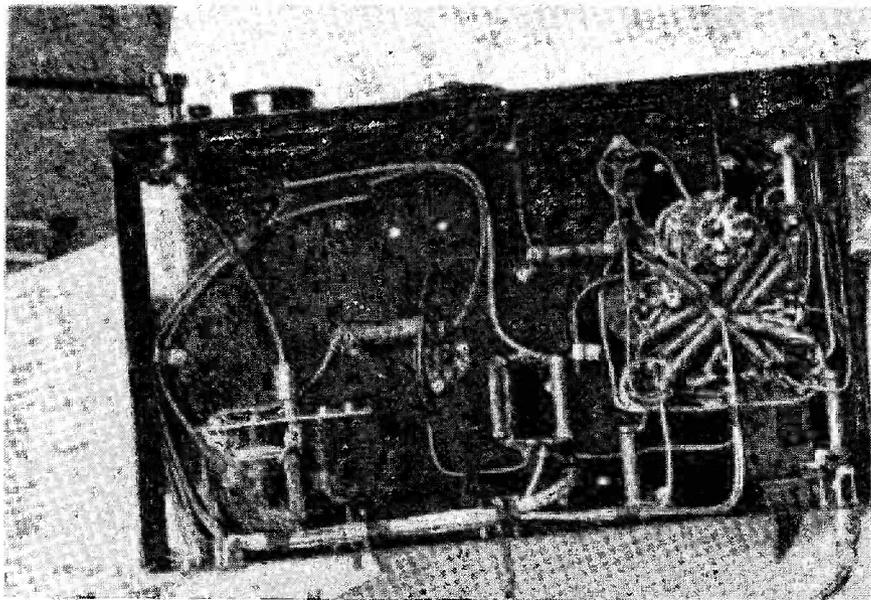Topside view of the Broad-Band Exciter chassis with the lid of the VFO removed; V1, V2, are mounted on the side of the VFO box. The driver is in the horizontal screening can at the back of the chassis.



Underneath the chassis ; the band change switch is operated from the front panel through gearing. The common earth point for the decoupling capacities is clearly visible.

adjustment over a wide frequency change is a waste of time—and not required—which is the essence of the whole unit ; in any case, as stated before, the drive is

sufficient for most needs. R1 is the drive control and permits direct control of the PA grid current without further exciter adjustments.

Table of Values


Broad-Band Exciter Unit

C1, C2, C3, C5, C9, C12, C14, C24, C26, C27,
= .01 μ F mica
C4, C6, C7, C8 = .005 μ F mica
C10, C11, C13, C16 = .001 μ F mica
*C17, C22 = 160 μ F variable. Eddystone (see
circuit caption)
*C18 = 60 μ F mica
C19 = .002 μ F, 1,500 volt DC
C20, C25, C28 = 100 μ F, silver mica
C21 = 830 μ F, silver mica
C23 = 3-30 μ F concentric trimmer. (For
setting edge of band)
R1 = 100,000 ohms, ww, variable
*R2 = 47,000 ohms, 1 watt
R3 = 1,200 ohms, $\frac{1}{2}$ watt
R4 = 6,200 ohms, $\frac{1}{2}$ watt
*R5, R7, R11, R19 = 3,300 ohms, $\frac{1}{2}$ watt
*R6, R8, R10, R12 = 350 ohms, 2 watt
*R13 = 27,000 ohms, 1 watt
*R14 = 100,000 ohms, $\frac{1}{2}$ watt
*R15 = 10,000 ohms, $\frac{1}{2}$ watt
R16 = 47,000 ohms, $\frac{1}{2}$ watt
R17 = 350 ohms, 1 watt
R18 = Meter shunt
L1 = 3.5-3.8 mc Labgear coupler
L2 = 7-7.5 mc Labgear coupler
L3 = 14-14.85 mc Labgear coupler

L4 = 28-29.7 Labgear coupler
L5 = 9T $\frac{3}{8}$ in. O.D. 18 SWG, 1 in. long
L6 = 2.5 mH RFC
L7 = 38T 24 DSC close wound, 3 turn link
L8 = 21T 24 DSC close wound, 3 turn link
L9 = 12T 18 SWG enamel, spaced 1 in. 3
turn link
L10 = 6T 14 SWG enamel, spaced 1 in. 3
turn link

All coils L5, L7, L8, L9, L10, wound on $\frac{3}{8}$ " dia. paxolin formers. Links 24 SWG PVC covered bell wire.

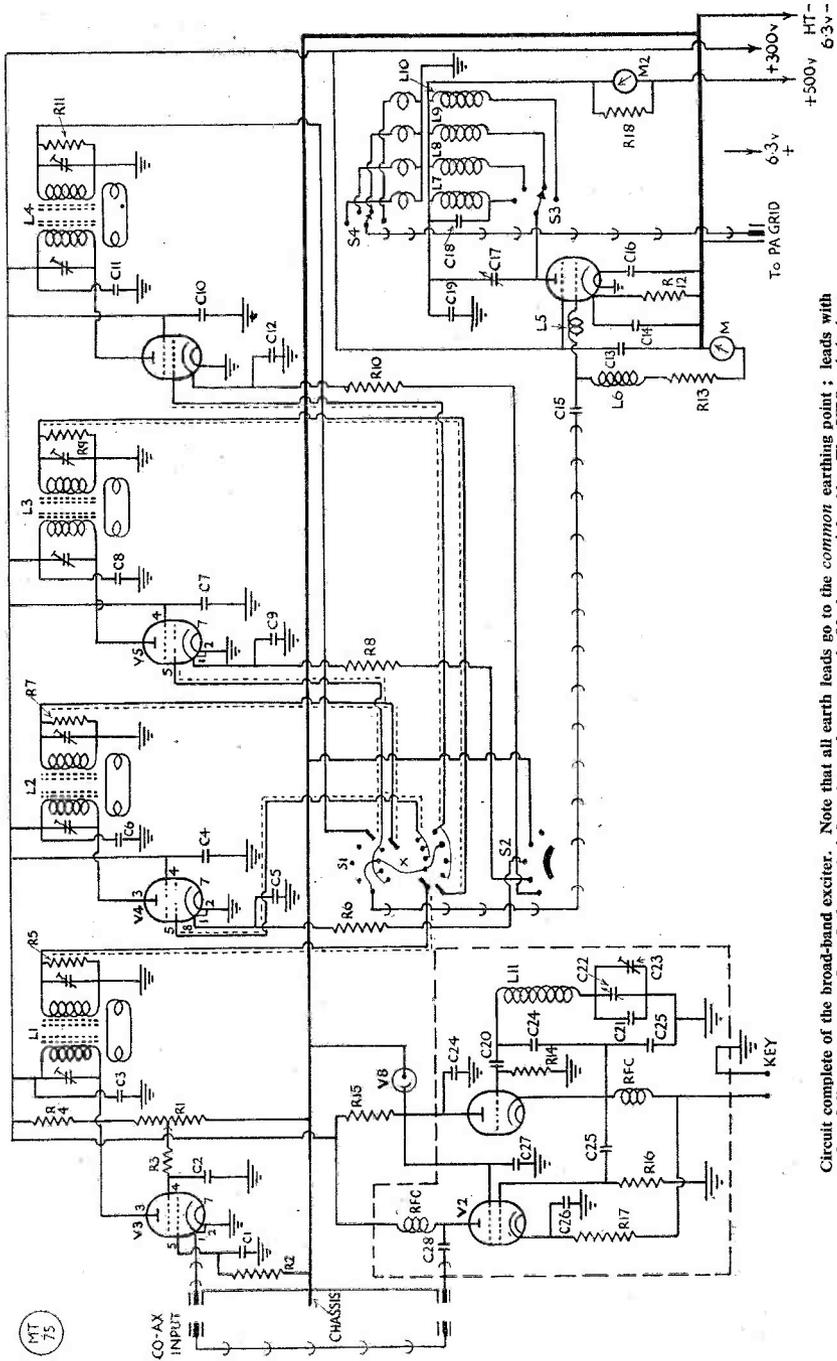L11 = 65 μ H. Tension wound Invar on ceramic form. From oscillator 145.
RFC = 2.5 mH
S1 = 2 wafer, 4 bank, 4-way each bank
S2 = 1 wafer, 1 bank, 4-way with shorting slide
S3 = 1 wafer ceramic, 1 bank 4-way
S4 = 1-wafer, 1-bank, 4-way
S1, S2 = ganged
S3, S4 = ganged
V1 = 6J6
V2, V3 = GSK7
V4, V5, V6 = 6V6
V7 = 807
V8 = VR150/30



Circuit complete of the broad-band exciter. Note that all earth leads go to the common earthing point; leads with a dotted line are screened, and those circled at intervals are run in 80-ohm coaxial cable. The YFO unit is in a separate screening box; values specified for C21 and C22 will give YFO output in the CW areas only of the bands covered, but increasing C22 and a small reduction of C21 will allow full coverage.

MT
75

Backyard Skywire

Some Simple Multi-Band Aerial Systems

By L. H. THOMAS, M.B.E. (G6QB)

DURING the past few months the writer, in his guise of DX Commentator, has received at least a dozen letters suggesting that "anyone can work DX with a spacious garden full of Sterba Curtains, Rhombics or even Vee Beams." The implication, obviously, is that without these little aids to success the working of DX is a difficult matter.

Now it happens to be a fact that many of the outstanding figures in the DX world (at any rate in Great Britain) are not by any means so equipped. Many of them have only the simplest types of aerial, and some of them work under great difficulties in this matter.

It seems, therefore, an opportune moment to come to the defence of the modest aerial, or what one correspondent calls the "Backyard Skywire" and to try to indicate that if your garden is no more than 70-ft. long (including the space taken up by the house) there is still hope. Of course it is realised that there are many to whom even a straight run of 70 ft. would be a great luxury, but we happen to know something about 67-ft. aerials from personal experience, and propose to write of them.

The location is shown roughly in Fig. 1; there are two somewhat wobbly trees, both 35 to 40 ft. high, and about 75 ft. apart. The station window happens to come almost half-way between them, and the whole house is underneath the direct run between the trees. On one chimney-stack is a television aerial some 6 ft. from the transmitting aerial and *above* it. The line between the two trees is almost exactly East-West.

When licences were restored in early 1946, some considerable head-scratching resulted in the erection of a 33-ft. Windom (full-wave for 28 mc), which was thought to be the most convenient and most useful aerial for that time, when we had only the 28 mc band to use for DX purposes. This looked like Fig. 2 and worked beautifully. DX was easy in those days, and a pair of 807's putting about

He has a taste for playing with aeri-als and as he works from a site no larger than the average suburban plot, G6QB's solutions for the aerial problem are essentially practical and will be of great interest to a large number of readers. This article is based upon aerial experiments and results obtained during the last three years.—Ed.

70 watts into that Windom got around the world in fine style on both 'phone and CW. In fact that original pair worked 100 countries on 28 mc! The full-wave aerial, of course, gave the characteristic "four-leaf clover" polar diagram with the lobes roughly NW NE, SE and SW, which is by far the prettiest pattern that can be derived from a stationary East-West run.

Twenty-Metre Operation

When the 14 mc band was about to be released, however, it became obvious that the 33-ft. Windom would not be a very useful two-band aerial, because it was desired to work in directions other than North and South on 14 mc. So, with much trepidation (because the old aerial was so good on 28 mc) it was changed to a 67-ft. Windom—by the simple expedient of adding some 33 ft. 6 in. of wire and leaving the tap where it was! The tap, originally, was about 4 ft. 8 in. off centre, so it now became roughly 12 ft. off centre.

Tests on 28 mc showed that the new length (now looking like Fig. 3) did everything that the old one had done. True, the lobes were theoretically now only 36 deg. off the line of the aerial instead of 54 deg., but this naturally didn't matter very much. And when the 14 mc band came into use the new aerial performed more or less as hoped for and was a very faithful servant for quite a long time. It was also used on Top Band by the simple expedient of series-tuning it against a direct earth, and one of the first contacts was G6ZO/I in Caserta (with 10 watts, naturally), so it appeared to be doing us proud on 1.7 mc, too.

When 7 mc was released it worked as an ordinary Windom, but on 3.5 mc there was always considerable difficulty in loading this particular aerial. Nothing seemed to make it "draw" properly, although it went so unexpectedly well on 1.7 mc. So, after quite a lot of use on all five bands, it was hauled down and another aerial tried.

This one (see Fig. 4) retained the same 67-ft. top, but had another 67 ft. tacked on to the east end. Of this some 45 ft. sloped down at about 60 deg. to the horizontal,

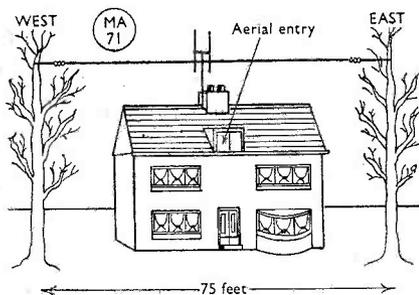


Fig. 1. Location diagram for any aerial system at G6QB.

but at right-angles to the main run, and the remaining 22 ft. or so doubled back to the window. (The little post shown in these drawings is about 20 ft. south of the trees and the main aerial.) We rather hoped that by end-feeding this 134-ft. aerial we should be able to retain the good characteristics of the 67-ft. top on the higher frequency bands, and thought that the radiation from the "feeder," being vertically polarised, would not interfere with the top too much.

Five-Band Solution

This was more or less how it seemed to work out. On 14 mc it appeared to be as good in all parts of the world as the 67-ft. Window; on 28 mc, if anything, it was slightly down, particularly for Africa. On 3.5 mc, being an end-fed half-wave (albeit of curious shape) it went exceedingly well and succeeded in putting signals into VE, VO, W and ZL with no trouble at all. On 1.7 mc it was now a quarter-wave Marconi, tuned against earth; and signals at distances up to 100 miles in daylight were definitely better than before.

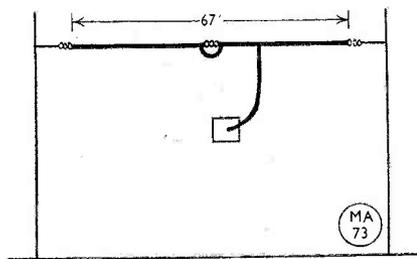


Fig. 3. The 33-ft. Window modified to work full-wave on 14 mc, by the addition of 33 ft. 6 in. of wire—see text.

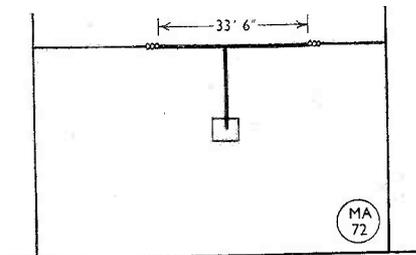


Fig. 2. The 1946 33-ft. Window, for full-wave operation on 28 mc, the only communication band then open.

So here we had a tolerably efficient five-band aerial, although restricted to a 67-ft. top; and it is, even now, the only five-band aerial we can think of for a "plot" of the size at G6QB.

But, of course, no amateur will ever be content to keep what he has—even if it seems to be working well—so something had to be done. In this case it was that radiating vertical portion that caused the worry, and it was therefore replaced by 67-ft. of 600-ohm feeder. It was argued that this should improve matters on 28 and 14 (and probably 7), and that in any case for the two LF bands the "live" feeder could be end-fed and the transmitter would, in fact, think it was still end-feeding the old 134-ft. run.

Zepp Feeding

This is where we were wrong, and we still have not found out why. The "Zepp" (Fig. 5) simply did not pay dividends. True, it seemed to work moderately well on 14 and 28 mc, but it did not take long to find that better reports were received from practically all parts if the two feeders were connected together at the bottom and end-fed, just as the aerial before it was!

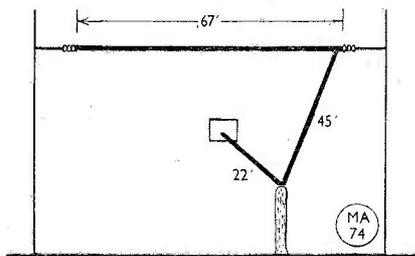


Fig. 4. An end-fed 134-ft. "wavy long-wire" for all-band operation.

There was apparently no catch in this; yet the Zepp tuned perfectly, with nearly equal currents in the feeders, and the transmitter loading was right. Tuning was sharp, and everything worked normally. But that Zepp simply did not do its stuff.

So before scrapping the 600-ohm line for good, we did some thinking and decided to try the so-called "centre-fed Zepp." In other words a 67-ft. top, fed in the middle with 600-ohm line. This would give us two dipoles in phase on 14 mc and two "full-waves in phase" on 28 mc. On 7 mc it would be a normal doublet and on the two top bands it would just have to take its chance. Further, it would be possible to change the characteristics on 14 and 28 mc by connecting the feeders together and running the affair as a "T" aerial. In fact, the behaviour on 14 mc in this condition ought to be that of a 14 mc full-wave aerial with a radiating vertical feeder. It has more or less worked out in that way, and looks like Fig. 6. The only

direction," but the percentage of calls answered went up at once, and even CQ's began to bring in nice pieces of DX, which they had never done with the end-fed Zepp. There was no change in the general level of conditions at the time of making the alteration, and it just seems that this aerial, with 33 ft. 6 in. of vertical (or rather "upwards") and two 33 ft. 6 in. runs at the top, seems to be ideal for all-round 14 mc work.

Throughout all the tests the PA has remained the same (a single-ended 813 running at 1,000 volts and 125 mA), although all sorts of exciter units and VFO's have been injected into it.

Obviously other variants are possible, but it is thought that this proof of the ability to use five different kinds of aerial in a 70-ft. space may possibly put ideas into the heads of those who have been inclined to despair.

It should, in fairness, be admitted that we have now secured the services of

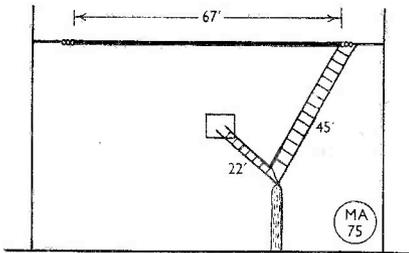


Fig. 5. The Zepp-fed 67-ft. roof, found disappointing at this location.

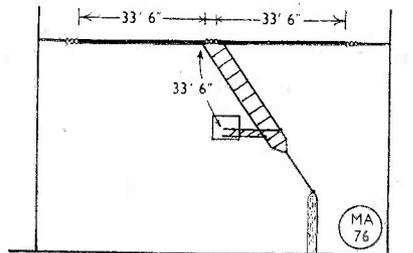


Fig. 6. Another variation on the 600-ohm feeder theme, discussed in the text.

stations on 14 mc that definitely prefer the dipoles to be fed in phase are KL7's, KH6's and ZS's, which seems about right. The rest of the world comes back when the two feeders are connected together and tapped on the *same* end of the coupling coil.

The only puzzling thing is that with this latter condition (which is a complete waste of a 600-ohm line) the aerial is quite the best of the whole series for 14 mc work. We cannot find any sign of a "preferred

another tree in a different direction, but the long wire (167-ft.) which runs to this is used only for the top bands and the faithful 67-ft. run remains the mainstay of the station on the DX bands. Yet another arrangement has been tried on it, in fact, with a 72-ohm line feeding the top at a point a quarter of the way along, but this confines operation to 14 mc. On this band it works excellently, but the arrangement is not flexible enough for continued use in a five-band station.

"COIL INDUCTANCE TABLES"

This is the second edition of an extremely useful and most comprehensive booklet from which can be obtained coil design data for given parallel capacities from 5 to 500 $\mu\mu\text{F}$ over a frequency range of

1.8 to 60 mc, in various wire gauges from 10 to 28 S.W.G. *Coil Inductance Tables*, 5s. 3d. post free (overseas 6s.) of Technical Inspection, 14 Silverston Way, Stanmore, Middlesex.

Full-Power Modulator

Design to Give 80 Watts of Audio

By F. H. LANE (G3GW)

THE modulator described here has been in use at this station for the past two years and has given yeoman service. It successfully modulates a 150-watt transmitter. The writer is averse to "microphone hugging" and likes to work comfortably, leaning back in the operating chair and talking naturally with the

This is a complete speech amplifier-modulator arrangement, with 807's in Class-AB2, to give enough audio output to modulate a 150-watt carrier. It employs a high-gain pentode for the input stage, to work with a crystal microphone.—Ed.

microphone about 2 ft. away. Using a D104 crystal microphone full modulation is easily obtained (at 150 watts) with the instrument 5 ft. away and the gain 50 per cent. advanced. All reports give the speech quality as "excellent."


The high gain is due to the use of an SP61 (VR65), or the equivalent in the 4-volt range SP41 (VR65a), for V1. This stage is stabilised by thorough decoupling in anode and screen circuits. Hum is kept down to negligible proportions by very

Table of Values

Speech Amplifier-Modulator

- C1, C7, C10 = 50 μ F, 12-volt electrolytic
- C2 = 0.25 μ F, 350-volt working
- C3, C8 = 0.1 μ F, 350-volt working
- C4 = 2 μ F, 350-volt working
- C5 = 4 μ F, 350-volt working
- C6, C9, C11 = 8 μ F, 350-volt working
- R1 = 5 megohm, $\frac{1}{2}$ watt
- R2, R11 = 1,000 ohms, $\frac{1}{2}$ watt
- R3, R4 = 100 ohms, 1 watt
- R5 = 500,000 ohms, $\frac{1}{2}$ watt
- R6 = 100,000 ohms, $\frac{1}{2}$ watt
- R7, R8 = 40,000 ohms, $\frac{1}{2}$ watt
- R9 = 1 megohm potentiometer
- R10, R14 = 1,000 ohms, $\frac{1}{2}$ watt

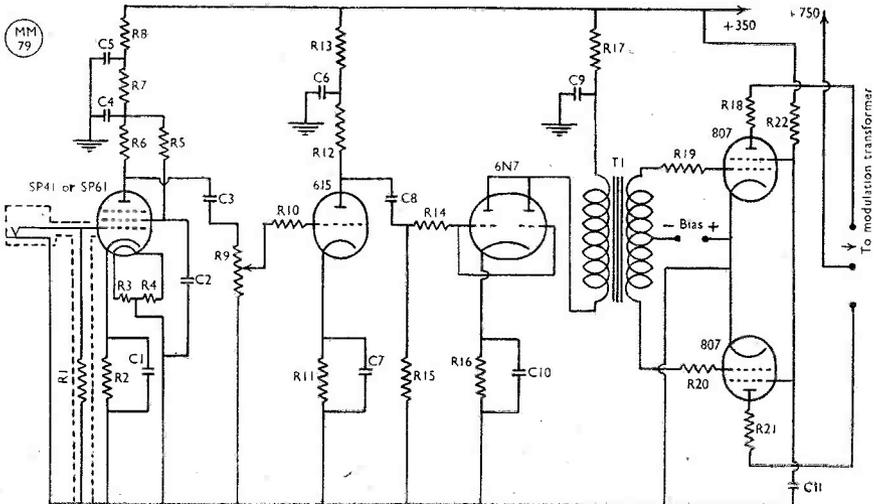- R12 = 250,000 ohms, $\frac{1}{2}$ watt
- R13 = 15,000 ohms, $\frac{1}{2}$ watt
- R15 = 500,000 ohms, $\frac{1}{2}$ watt
- R16 = 500 ohms, $\frac{1}{2}$ watt
- R17 = 5,000 ohms, 1 watt
- R18-R21 = 30 ohms, $\frac{1}{2}$ watt
- R22 = 2,500 ohms, 1 watt
- T1 = Suitable driver transformer
- V1 = SP41 (VR65a-4 volt) or SP61 (VR65-6 volt)
- V2 = 6J5 or 6J5G
- V3 = 6N7
- V4, V5 = 807



Circuit of the speech amplifier-modulator; it will provide full control for a 150-watt carrier.

thorough screening of the input circuit and the use of a "hum-dinger" in the filament supply. It is essential to use screened connections right from the grid cap of the SP61 and also to fit a fully screened input socket.

The following stage, V2, is conventional with a 6J5; if a 6J5G is employed it is desirable to use a screening can. V3 is also quite usual, with a 6N7 having both sections strapped to form a single triode. V2 and V3 employ thorough anode decoupling and grid stoppers. V1, V2 and V3 utilise an HT supply of 350 volts.

Modulator

The 6N7 driver stage is transformer coupled to the modulators—two 807's in Class-AB2. When fully driven, the output is in the region of 80 watts. A bias of 30 volts is applied to the grids, being derived from ordinary 9-volt bias batteries in series. Resistors are included in grid and anode circuits to prevent generation of parasitics. It is very desirable to maintain the screen voltage as stable as possible. As the 807 anode current varies over a wide range, it was considered advisable to obtain the screen voltage

from the 350-volt supply and also to tie the screen to ground with an 8 μ F condenser. It is also desirable to obtain the plate voltage (700 v.) from a power pack incorporating a choke input filter; but at this station, owing to lack of volts, condenser input is employed to good effect. As the current drain from the power supply varies from 50-200 mA with drive, a transformer rated at 250 mA should be fitted.

Construction

A chassis 8 in. \times 12 in. \times 2½ in. is employed. This is ample if, as in the case of the writer, the output modulation transformer is mounted elsewhere, *i.e.* in the PA power pack. Care is needed in wiring the filament side—keep the leads as far as possible from grid connections, and screened wire should be used. Remember the essential point—*screen the SP61 input circuit from and including the top grid cap right down to and including the input socket and grid leak.*

Finally, the writer emphasises that for a circuit of this simple nature, the sensitivity, quality and output combined with stable operation that can be obtained is remarkable.

TU5B on Top Band

Another Conversion Design

By A. P. KERFORD-BYRNES (G6AB)

EXAMINATION of the TU5B showed that it was an extremely well-made piece of apparatus built for rugged service during the war. There are various TU serial numbers, and they formed the tuning unit for the Type BC375 transmitter, into which they were plugged, similar to the manner in which the coils are plugged into an HRO receiver.

Tracing out the circuit of the unit gave the connections as shown in Figs. 1 and 4. As a result it was decided that here was the best part of a transmitter suitable for 160 metres, which only needed the addition of a couple of valves, meter and a few condensers and resistances to complete. Another point which decided the writer to adapt the tuning unit in this manner was the rugged nature of its construction;

The TU5B, still one of the most popular surplus items, is well worth the price as a Top Band foundation unit. This is not the first of such designs to appear in these pages, and it will probably not be the last!—Ed.

it seemed a pity to strip down such a well-made piece of equipment only to build it up again in a different form.

Circuit for 1.7 mc

The circuit adopted is shown above the dotted line in Figs. 2 and 3; this makes clear the relationship of the various components to the socket holes on the insulated strip of the TU5B. The numbers given are those of the sockets reading from right to left when looking at the back of the panel of the tuning unit. The only modification made to the unit itself is the cutting of the two wires leading from the small variable condenser, and one wire from each of the .0004- μ F mica condensers. The variable condenser can be left in place or removed—in the author's case it was left in place, this being the easier of the two alternatives!

Two pieces of angle-iron, ½ in. \times ½ in. \times

$\frac{1}{16}$ in., were found in the junk box and cut to a length of 14 in. The four conical securing studs were removed from the crackle-finished cabinet in which the tuning unit was housed and the angle-irons were drilled to marry up with the four holes on the panel. The securing studs were then bolted through the four holes in the angle-irons and the unit was secured to these by means of the slide fasteners, thus holding the two angle-irons upright.

A piece of paxolin, $16\frac{3}{4}$ in. \times $6\frac{1}{2}$ in., was obtained and four holes were drilled in it, two at each end so that it could be bolted to the two vertical angle-irons above the front panel of the tuning unit. A circular hole was cut in the centre of this with a fretsaw, for fitting a 0/100 mA meter, and two wafer-type octal holders were mounted on the back of the panel in the positions shown, spaced out by means of $\frac{3}{8}$ -in. pillars. A key jack was also fitted.

The angle-irons and top panel can now be removed temporarily from the unit; the next step in construction is the removal of the screws along the top of the tuning unit panel which secure the insulated strip containing ten sockets. When these four screws are taken out, the insulated strip is carefully pushed back-

wards and a $1\frac{1}{2}$ -in. 4 BA cheese-headed bolt is put through each socket with the head towards the panel. A nut is then threaded on each bolt and securely tightened. After all the ten bolts have been fixed in the socket holes the insulated strip is replaced on the back of the panel. Great care will have to be exercised when moving the insulated strip as it is liable to fracture.

The panel is then wired-up with 14-gauge tinned copper wire for rigidity. When all the panel wiring is complete with the exception of the connections to the ten 4 BA bolts, replace the panel on the angle-irons and refix the angle-irons to the

CALIBRATION CHART

| kc | A | B | C | kc | A | B | C |
|------|----|------|-----|------|----|------|-----|
| 1720 | -2 | 877 | -31 | 1870 | -2 | 2005 | -67 |
| 1730 | -2 | 969 | -34 | 1880 | -2 | 2069 | -69 |
| 1740 | -2 | 1041 | -37 | 1890 | -2 | 2137 | -71 |
| 1750 | -2 | 1128 | -40 | 1900 | -2 | 2199 | -72 |
| 1760 | -2 | 1205 | -43 | 1910 | -2 | 2270 | -74 |
| 1770 | -2 | 1287 | -44 | 1920 | -2 | 2337 | -76 |
| 1780 | -2 | 1369 | -46 | 1930 | -2 | 2458 | -78 |
| 1790 | -2 | 1447 | -50 | 1940 | -3 | 357 | -17 |
| 1800 | -2 | 1517 | -51 | 1950 | -3 | 418 | -18 |
| 1810 | -2 | 1593 | -54 | 1960 | -3 | 469 | -20 |
| 1820 | -2 | 1662 | -56 | 1970 | -3 | 535 | -21 |
| 1830 | -2 | 1732 | -58 | 1980 | -3 | 591 | -23 |
| 1840 | -2 | 1798 | -61 | 1990 | -3 | 648 | -24 |
| 1850 | -2 | 1872 | -63 | 2000 | -3 | 702 | -26 |
| 1860 | -2 | 1936 | -65 | | | | |

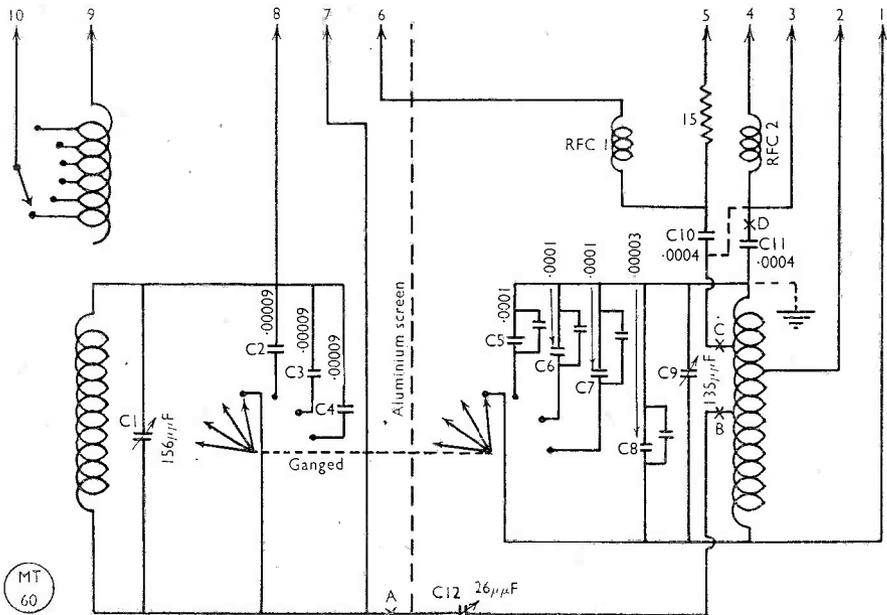


Fig. 1. Cut wires where marked X, at points A, B, C and D. Make two additional connections as shown dotted.

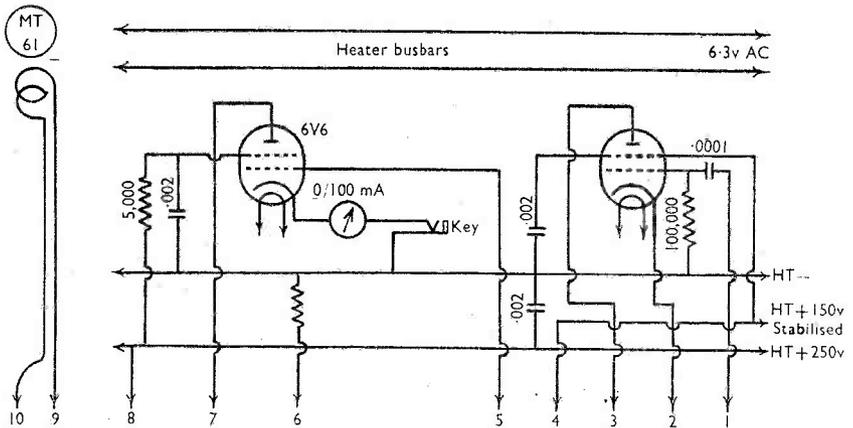


Fig. 2. Circuit of the additional panel for the TUSB to obtain operation on 1.7 mc.

tuning unit. When the panel is eventually in place the final connections can be made to the 4 BA bolts. Constructors will find it much easier when fixing the 6.3-volt and HT busbars to mount them on 4 BA bolts, so that they are at different distances from the back of the panel; this will enable wires to cross them in safety.

Modulator Connection

A separate stabilised 150-volt HT feed

is run to the plate and screen of the first 6V6 and by-passed by a $.002 \mu\text{F}$ condenser, so that the plate and screen of the PA can be modulated by running the 250-volt HT through the secondary of a modulation transformer before it is connected to the HT positive busbar. A four-core cable is used to connect the busbars to the power supply. The PA stage takes 40 mA when off resonance and 13 mA when tuned to maximum dip. Connecting the aerial

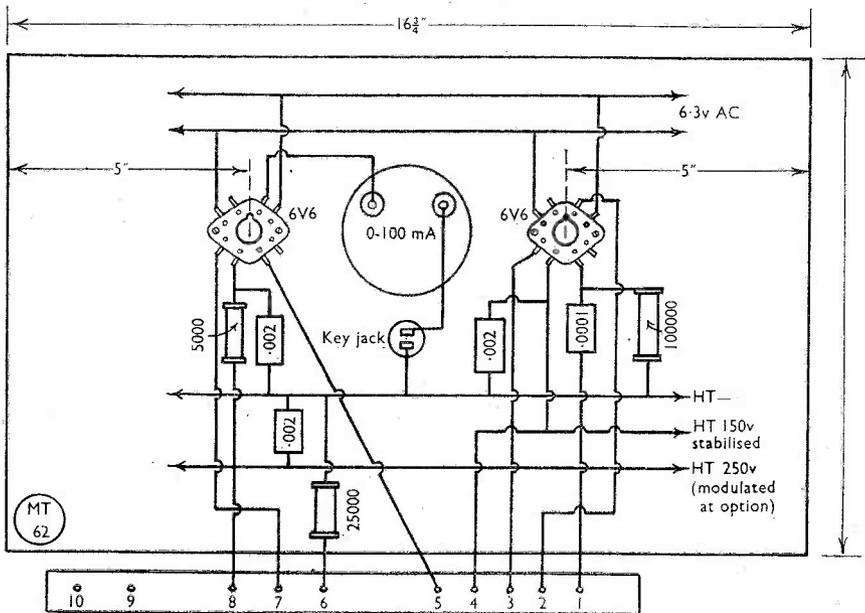


Fig. 3. Showing location of components on additional panel.

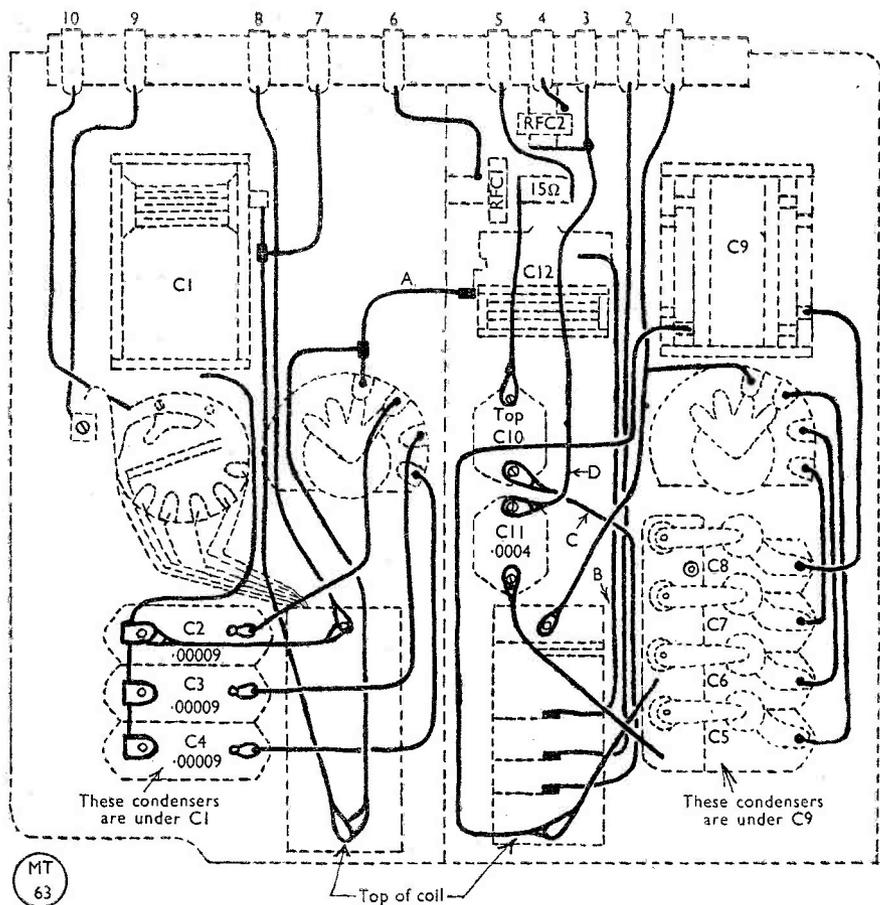


Fig. 4. Mechanical layout of TUSB, with positions A, B, C, D, marked—see Fig. 1.

increases the cathode current to 38 mA. As it was noticed that none of the components in the TUSB was connected to the chassis it was decided to take the chassis to the HT negative busbar by means of a wire placed under one of the self-threading screws and soldering the other end to the busbar. The transmitter has been used here on both 'phone and CW with excellent results.

The aerial coupling switch is used as a link point on the PA tank and a twisted pair is run from sockets 9 and 10 on the panel to the standard aerial tuning unit. At this QTH, the aerial tuner consists of 30 turns of No. 18 gauge enamelled wire

wound on a 2-in. diameter tube. One end of this coil is connected to a 152-ft. aerial and the other end via a .0005 μ F tuning condenser to a 102-ft. counterpoise. A four-turn link is used at the aerial coil end.

Amateurs who possess one of these tuning units but are reluctant to dismantle it on account of the splendid workmanship could do worse than build themselves a Top Band transmitter as outlined here—on which they could QSX to their hearts' content on 160 metres!

A chart showing the calibration of the author's completed transmitter is given in the table, as a guide for other constructors.

DX COMMENTARY

ON CALLS HEARD, WORKED & QSL'd

Well, well ! What a month ! There may still be a few people about who don't realise what has been happening, but let us hasten to put them in the picture. This time, all the excitement has been transferred from our usual DX bands and the really frantic activity has settled down on 3.5 and 7 mc, where most of the active stations have been working all sorts of unexpected DX. What with the breakthrough of VK's on 3.5 mc and the steady accumulation of DX on 7 mc—even at mid-day—the customers have been kept pretty busy changing coils.

But before we go into details band by band, let us deal with the event of 1948—the WAZ Marathon. Results have now been sifted out, checked and counter-checked, and generally pored over, so that we can proclaim the winning stations, as under :

Phone and CW Section

1st : G2EC — 40 Zones, 174 Countries
 2nd : G8KP — 40 Zones, 169 Countries
 3rd : G4CP — 40 Zones, 149 Countries

Phone Only Section

1st : G3DO — 35 Zones, 115 Countries
 2nd : G3DAH — 35 Zones, 97 Countries

Hearty congratulations to these operators on their stout work during 1948. We are not running a Marathon in 1949, but no doubt they will all find something to tax their capabilities during the very exciting year that is ahead. Judging by the "new faces" showing up on 7 and 3.5 mc, we feel that the Four-Band DX Table will shortly grow too big for one column !

Rivalry in Zone 20

It is interesting to note that we have had two stations in Zone 20 reporting their Marathon scores during 1948. SV1RX (now G3FNJ) had a score of 39Z and 129C at the time he left Athens—early in the year. On the other hand ZC1CL started up in Transjordan late in the year and apparently finished up with a score of

By L. H. THOMAS, M.B.E. (G6QB)

37Z and 122C—although he may have improved on those figures by December 31. G3FNJ (now London, N.W.6) says it was nice to know there was *some* competition out there in Zone 20 !


The 80-metre Witch-Hunt

And now for the news that everyone is waiting for. It all seems to have started with G6CJ (Stoke Poges) who, remembering that the first VK contacts on the band were made about 24 years ago and that the DX came through again in 1935-36, persuaded VK5KO to try his luck on 3.5 mc *in the evenings*. The VK did this, and the result was a QSO with G2KO (Driffield) on December 12, 1948. This is believed to be the first of the present series, and certainly was VK5KO's first G QSO on the band.

The second G station to make it was G3ACC (London, S.E.22). She worked VK5KO at 1930 on December 16, and was overjoyed to receive his Air Mail QSL at the end of the year ; this was sent to us for inspection—practically under armed guard ! G5BZ (Croydon) worked VK5KO on December 26, and since then contacts have been too numerous to mention.

G5BJ (Birmingham) persuaded ZC6XY to come up on the band, and made the first 80-metre phone contact between G and ZC6 ; G8VB (London, W.5) made the second, with S8 phone both ways, and is running a schedule ; 'VB also worked KV4AA on CW and three CT1's on phone. Incidentally, G8VB passes on the sad news that Harold Ward (VE1GR) is now a Silent Key. He will be missed on the band.

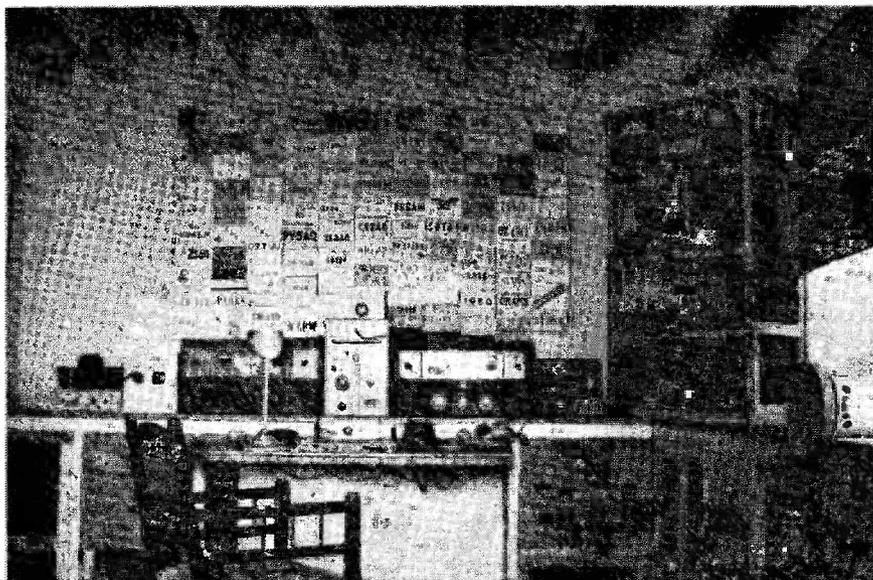Since the blossoming forth of these first DX contacts, new stations have been arriving thick and fast, with an incredible number of "phoneys" among them. With the help of the regular DX operators we have tried to sift them out, with the following results : *Certainties*—VK5KO, VK4EL, VK7YL, VK2RA, ZL4GA (all



VP6CDI, Barbados, B.W.I., is as well known with his new call as he was when G2CDI of Stokenchurch, Bucks. The interesting thing is that he still uses the original 25-watt Tx with the same 807 which collected 132 countries for G2CDI ; it has brought in 117 under the VP call.

1900-2100) ; PY7WS, KH6IJ (2200), CE3BC, KL7GH (2200), VS2BC (2000), ZC8PM, VP2LA, ZL4IE (0815). *Queries* : YJ2FF (evenings), VS6AJ, VS7LA, VP8CH, ZS1M, and ZS1T (0800). *Definite Phoneys* : VK5KO (S8 at 0900 !), VS9AN (station closed), YA3B, AC4YN, G2PL (Wallington) says he is amazed at the number of phoneys and even more at the gullibility of certain G's who are taken in by them. G6HL (Shepperton) says the same and suggests that some of the 7 mc DX is pretty smelly, too.

The QRP fraternity have been doing well with the genuine stuff. G3EIZ (Liverpool), with 25 watts, has worked VK2RA, 5KO, 7YL and OX3MG. He was called by the doubtful YJ2FF—let's hope he proves genuine. G3CRK (Southall), likewise with 25 watts, raised OX3MF and VE1GU. G3BDQ (St. Leonards) worked VE, W and CT3, the interesting thing in his case being the use of a "curly" 66-foot aerial 20 feet high at one end and 4 feet at the other !

Best QRP performance reported to date is by GW8WJ (Prestatyn), who, with 8 watts, has worked VK5, KP4, OX, VO, VE1 and W1, 2, 3 and 4. The PA stage was a 6V6 !

ST2AM (Khartoum) is reported to be "on the way" to the 3.5 mc band. The significance of ZC6XY and ZC8PM is, of course, that they are in Asia and make a 3.5 mc WAC a nice target at which to aim.

Spivvery and Bad Manners

This particular DX-hunt has shown up band operating and bad manners more than ever, for the reason that all the G stations are much stronger than the DX. Thus, a small group of G's calling ill-timed "CQ DX's" can completely ruin the DX for everyone. This has been the chief trouble all along. A VK calls CQ ; all the pack descend on him. So far, so good. But now the "long-caller" shows up as a menace, by blotting out the VK's reply to the fortunate one. Hardly any of the interested parties having heard the VK's come-back at all, some of them sit tight, but some call him again ; the real spoilers of the DX sit *on the same frequency* and proceed to call CQ DX again !

With only two or three DX stations there and a whole flock of G's (all crowded, by the way, between 3500 and 3510—a senseless procedure if ever there was one) what is the use of calling CQ DX ? It's just that some people are too aggressive to

FOUR-BAND DX

| Station | Countries Worked | | | | | Power |
|---------|------------------|-------|------|--------|-------|----------------|
| | 28 mc | 14 mc | 7 mc | 3.5 mc | Total | |
| G6HL | 118 | 118 | 70 | 29 | 159 | 150 |
| G6QB | 105 | 147 | 58 | 30 | 173 | 150 |
| G3DO | 91 | 138 | 30 | 16 | 167 | 150 |
| G2BJY | 81 | 46 | 24 | 4 | 105 | 25 |
| G2WW | 76 | 155 | 31 | 20 | 165 | 60,150 |
| G2VD | 64 | 148 | 39 | 21 | 156 | 150 |
| G8QX | 63 | 95 | 17 | 12 | 120 | 150 |
| GC2CNC | 61 | 134 | 52 | 8 | 162 | Phone 10/50 |
| G8IP | 59 | 110 | 33 | 13 | 127 | 3/150 |
| G6OM | 55 | 28 | 30 | 20 | 87 | ? |
| G3COJ | 50 | 31 | 21 | 1 | 83 | 75 |
| G2VJ | 41 | 59 | 12 | 4 | 84 | 25/150 |
| G3ATU | 40 | 139 | 44 | 24 | 150 | 10/150 |
| G2AO | 32 | 111 | 33 | 29 | 119 | 150 |
| G2HIF | 30 | 42 | 9 | 6 | 64 | 150 |
| G8IH | 27 | 164 | 55 | 14 | 172 | Phone 7/150 |
| G5HH | 27 | 81 | 37 | 22 | 98 | 25/75 |
| G2YS | 25 | 96 | 22 | 21 | 107 | 150 |
| G8VG | 24 | 96 | 48 | 17 | 117 | 60/75 |
| G3AKF | 21 | 64 | 30 | 22 | 83 | 60/150 |
| G2DLJ | 19 | 112 | 36 | 24 | 115 | 120 |
| G8VB | 13 | 88 | 29 | 41 | 110 | 150 |
| G5WC | 12 | 112 | 49 | 1 | 114 | 45 |
| G3AKU | 11 | 123 | 12 | 21 | 130 | 30 |
| G8LO | 10 | 106 | 27 | 10 | 106 | 150 |
| G2AVP | 8 | 144 | 47 | 19 | 153 | 25/120 |
| G5FA | 8 | 114 | 77 | 7 | 124 | 100 |
| G2AVC | 7 | 55 | 22 | 15 | ? | 10/100 |
| GW3ECH | 6 | 32 | 5 | 7 | 36 | 25 |
| G3AGQ | 5 | 22 | 35 | 25 | 50 | 6/150 |
| G5GK | 4 | 92 | 78 | 3 | 174 | 150 |
| ON4JW | 2 | 172 | 65 | 23 | 176 | 35/75 |
| G3ACC | 2 | 102 | 5 | 19 | 102 | 150 |
| G4QK | 2 | 73 | 22 | 19 | 77 | 100 |
| G2DHV | 2 | 58 | 21 | 12 | 61 | 25/60 |
| G3BDQ | 1 | 105 | 26 | 18 | 107 | 25/150 |
| G3EIZ | 1 | 25 | 6 | 31 | 39 | 25 |
| G8PG | 1 | 25 | 28 | 10 | 38 | 14/14 |

sit quiet and listen. They *must* stick out both elbows and yell "Stand back, you scum ; I, the great I, am going to work this one. And if I don't get him I'll see that you all hear what a punch there is behind my signal." Ah, well ; if you are bad-mannered on the air you are probably bad-mannered off the air, too, so there's nothing much we can do about it.

G5WP did have a shot at inducing VK5KO to call QML once. 'KO did so, and everyone shot up to 3600 to call him, but by the time they had finished tuning up and playing around he was calling a plain ordinary CQ again and everyone charged back on to his frequency. So there is VK5KO calling G's, and on his frequency are (a) about ten G's calling him ; (b) about ten more calling CQ DX ; (c) a DA working a PA ; (d) a G6 happily chatting about his Christmas dinner with a G3 ; (e) a G sending strings of ABC's and dots while he tests his new key on the air.

The 7 mc News

Goodness knows the 3.5 mc DX is startling enough, but some of the arisings on 7 mc are even more unusual. Note the times of some of these QSO's : KH6IJ and ZL4FT (0815), CM6AH (0830), YV1AI (0850), W4SLW/KL7 (0915), KL7QK (0950), W6LHN (1000), VE7VC (1015).

Pause for breath. Now note *this* lot : VS2BC (1045), YJ2FF (1050), W7IYA (1100), ZD9AA (1100), KM6AD (1145), VR2FI (1205), VR1CC (1220), KV4AA (1430).

Some of these seem almost incredible, but if you've tried working KM6AD at 1145 through French phone, Swiss gramophone records, twenty-five G's calling him and a local vacuum cleaner, you'll admit that it's real enough !

Other nice ones are YK1AF (1955), VQ4RAW and VQ5JTW (1930), HZ1JE (1930), VP2KS, 4TZ and 6JS (midnight) and XE2CB (0820).

For the stations and times in the previous paragraphs we are indebted mainly to G5FA (London, N.11), G2AVP (Stradishall), G8IH (London, W.5) and G6HL (Shepperton). All of them have had very nice pickings from the bunch.

Other 7 mc news comes from ON4JW (Brussels, who has worked KV4AA, VQ5JTW and HR1AT ; from G8IP (Hampton) who found VQ5JTW "out-standing" ; from G3ATU (Roker) who, still chasing Wycoming on 7 mc, continues to get VE7's instead ; and from G3ESP (Wakefield) who worked W3KNY with 12 watts on the band.

Some New Ones

Now a slight break from DX for some new arrivals in the way of prefixes. YK replaces AR1, for Syria; YK1AF is already on the air. JA is now in use for Japan, and DL2, DL4 and DL5 for Germany (but still *not* German nationals). KC6 is the prefix for the Caroline Islands; KC6EA, 14 mc at mid-day, is old W8WEA/Truk. KR6 is Okinawa instead of J9. KG6IA-6IZ series is allotted to Iwojima.

The 14 mc DX

By comparison with 7 mc, 14 seems quite tame. But some nice steady work goes on. G2AVP (Stradishall) has piled up VP3CW, KX6AF, J2AAO, HZ1AU and PZ1NB. G2EC (London, W.1) and G2PL (Wallington) were both able to work AC2MA in Bhutan, after which 'MA packed up the station, so the rest of us are unlucky. 'PL, by the way, has one target in life now, which is to get his "200 confirmed." ON4JW and G3ATU both managed to raise VQ1CUR in Zanzibar; he, too, has packed up and is now VQ4CUR again. G3ATU worked W7KMV/Iwojima on 14 CW, and he was the first G ever heard there on 14 mc. 'ATU has also received his QSL from W6ODD/FI8, so he is pretty happy man these days.

G3DXC (Roehampton) and G3DER (Compton Bassett) both remark on AG2AG (Trieste), who is, we think, genuine. 'DXC has been pirated by someone whose name is Jack (his own is Doug!), and has heard "ZL1S," the phoniest of phoneys, complete with S9 key-clicks. 'DER, with 50 watts, has raised ZD9AA, PZ1NB, UL7BS, UI8KAA and scads of VK, ZL and ZS stations.

28 mc

Ten-metre news is quite dull, really, for it is obvious that the band is nowhere near as good as last year. But at least two lucky ones, G3ATU (Roker) and G3COJ (Hull) have worked VU7AF at Khatmandu, Nepal. 'COJ has also collected CPIAP (1740), ZS3G (1030), FE8AB (1230), and EP1RY (1025). He also passes on the news that the Philippines are now using the prefix DU. He worked DU1VVS, ex-KA1VVS.

G6HL (Shepperton) says that TA3FAS is not quite the black sheep that he seems; he is only allowed to work for the purposes of handling traffic (but does he *have* to do it on 28000 kc phone?) 'HL heard XI1YI, or XI1NM1. Now who the heck is *he*? He was drifting roughly from 28040 to 28085 kc.

G8KP (Wakefield) turns in a long list of 28 mc DX, mostly on phone, and tells us that his confirmations now number 143.


21 mc News

Yes, that cross-head *does* say 21 mc! G3COJ (Hull) has been listening on the band and has heard SM5KM, UR2KAE and UA9DP; he also tells us that ZE and VU stations are now licensed for the 21 mc band.

From Overseas

D2CH remarks that he likes the Four-Band idea, but why not make it Five Bands? He has 14 countries confirmed on 1.7 mc. ZC1AL writes to say that the following stations are now operating in the Arab area of Palestine: ZC1AB, 1AL/ZC6, 6GC, 6JL and 8PM.

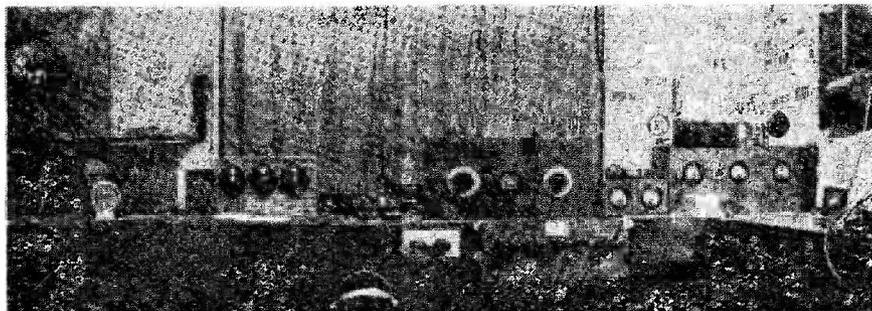VS2CQ (QTH in list) now has a BC348 and hears the DX replying; he has worked ON and PA but no G as yet. He




Another view of G6QB—then located at Thornton Heath, South London—in the pre-1930's. The equipment in view, l. to r., is frequency meter, 1-V-1 Rx, 50-watt PA on 14 mc, the modulator unit, and the exciter stage, CO DESB-LSSB.

says he is the first authentic VS2CQ and will QSL 100 per cent. He was in England until August, 1948, so any VS2CQ QSO's before that were shady. VQ4SS is ex-G3SS but is not yet active in Kenya. He hopes to be on the air in early March, and is already hearing G's. As a matter of fact he sends some Calls Heard, but as they are all on 28 and 14 mc and hardly DX we are not using them this time.

ZD4AM (Tafo) made a complete WAC in new countries as soon as he put up his new aerial. The stations were UC2CB, CT3AA, KZ5IP, OA4AP, VS2CH and W8SIR/KG6. He heard KX6AF but was unlucky. Harold makes a plea for honest reporting, and says he has been reported T9 or T9X when he *knows* that his note was T8 at best, owing to trouble.

ON4JW (Brussels) tells us that ON4QF has now gone to the Congo and has become OQ5QF. He also asks us to make it clear that *all* ON stations with three-letter calls are pirates; to say nothing of a few of the two-letter people as well! The Belgian PO is so worried about piracy that it has eased off on the exam, to make some of them official!! UBA is also co-operating by giving Morse lessons on 3515 kc at 1930 for an hour. (Hope they keep off those VK's).

G5IH (HMS *Duke of York*) spent a lot of time at VP6CDI's station in Barbados and says that the W's aren't content with replying to "CQ G—no W" calls from 'CDI—they wax offensive into the bargain and one of them sat on the frequency calling "CQ, not VP6CDI, Louse!" Apparently 28 mc is not so bad, but attempts to contact Europe on 14 mc meet with every conceivable kind of sharp practice. G5IH says he was given a terrific welcome

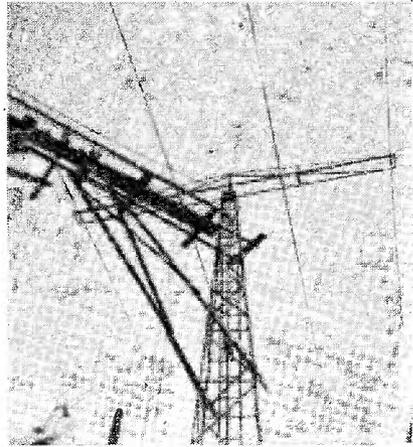

This is the 14 mc beam (and mast) at VE7AFM, who was G3NQ at Whitstable not long ago. The "bridge", connected by speech-line to the Tx position, is used to reach the aerial for tuning purposes. The input runs just the 500 watts to this impressive erection—oh, well, they can do it in Canada!

in Barbados, and was astonished at the succession of S9 QSO's with 'CDI's little 25-watter, which still (as in Stokenchurch days at G2CDI) uses an 807 doubler in the final.

Ex-G3CNM (s.s. *Padana*) is still plugging away at the possibility of obtaining Maritime Mobile licences for our own fellows. He wants all sea-going operators who are in favour of MM's to drop him a card. He will send the lot, with a letter, to the Board of Trade. His full address is F. Armstrong, Radio Officer, s.s. *Padana*, c/o Mackinnon Mackenzie & Co., P.O. Box 122, Bombay. During a recent visit to New Zealand, 'CNM operated a QRP portable with the ZL1 suffix and had lots of fun—particularly when he left the suffix out and called CQ de G3CNM on 3.5 mc! He worked nearly every ZL in Auckland, as well as a snip in the guise of VR5PL. He tried to find ZL1MP (ex-GW6AA) but only succeeded in losing his way and being chased off an estate by a ferocious gentleman with a ditto dog!

General News

G2ZC (Farnham) tells us that VK9NR (QTH in list) is active on 28, 14 and 7 mc from 0700-0800. 'ZC also remarks that ZL4BQ and ZL4GA are father and son, and *both* members of FOC! G2WW (Penzance) has at last finished his rebuild,

1948 MARATHON

TOP SCORERS

| Station | Zones | Countries |
|--------------|-------|-----------|
| Phone and CW | | |
| 1. G2EC | 40 | 174 |
| 2. G8KP | 40 | 169 |
| 3. G4CP | 40 | 149 |
| 4. G3AAE | 40 | 113 |
| 5. G3DO | 39 | 130 |
| 6. G2AVP | 39 | 129 |
| 7. G2VD | 39 | 127 |
| 8. G3ATU | 38 | 137 |
| Phone only | | |
| 1. G3DO | 35 | 116 |
| 2. G3DAH | 35 | 97 |
| 3. G3ZI | 32 | 81 |
| 4. G2VJ | 29 | 72 |

and is now on with 808's in the PA and a TZ40 modulator. All his QSO's since then have been on phone, and he lists so much DX that we can't even quote from it. He wishes there were a 1949 Marathon; by January 10, his score was 11Z and 38C!

G3CRK (Southall) has had a QSL from Bulgaria (which doesn't check) giving an alleged report on signals from his "famous station" and asking for four 32 μ F condensers and British amateur magazines. The old racket again. G6BB (Streatham) has passed on his TRF battery 3-valver, with the aid of which he has worked 102 countries, and awaits the arrival of a super-Rx. Weak DX please note—he will now hear you.

G2NM (Bosham) says that a recent contact with ZD9AA showed him that he could still get thrills out of DX. GC2CNC (Jersey) says that he did not imply disapproval of contests (see last month); merely feels that there are too many of them, especially at week-ends. . . . GC2AWT (Jersey) says he is fed-up with bad criticisms heard on the air. Some of the best phone on the band has been described as terrible—doubtless because of the frequency response of the receiver, selective fading and so on—and he suggests that technical comments and advice should be left to those really

DX QTH's

| | |
|-------|---|
| AR8XA | Francis Semerarò Orsini, Hotel Normandy, Beyrouth |
| EA8CO | Crescencio Olias, Box 346, Las Palmas, Tenerife, Canary Islands. |
| EQ2L | c/o U.S. Embassy, Teheran, Persia. |
| MI3NC | AP0 843, c/o PM, New York. |
| MI3ZZ | Box 379, Asmara, Eritrea. |
| OQ5DE | c/o Symetain Compagnie, Kalima, Nr. Kindu, Belgian Congo. |
| VK9NR | N. Roberts, c/o Dept. of Civil Aviation, Norfolk Island, via Sydney, N.S.W. |
| VS2CQ | G. F. Bloomfield, Box 150, Kuala Lumpur, Malaya. |
| VU7AF | ARC of India, Box 6666, Bombay 20 (Station at Khatmandu, Nepal). |
| YK1AF | QSL via W3KXS (Station in Damascus). |

ZONES WORKED LISTING

POST WAR

| Station | Z. | C. | Station | Z. | C. |
|---------------------|----|-----|---------------------|----|-----|
| Phone and CW | | | Phone and CW | | |
| ON4JW | 40 | 176 | GM3CSM | 36 | 99 |
| G6QB | 40 | 173 | G2YS | 35 | 107 |
| G8IH | 40 | 172 | G5WC | 34 | 114 |
| G4CP | 40 | 168 | G8PL | 34 | 109 |
| G3DO | 40 | 167 | G2BJY | 33 | 105 |
| G2WW | 40 | 165 | G3BNE | 32 | 82 |
| G2AVP | 40 | 153 | G3ACC | 31 | 102 |
| G8IP | 40 | 127 | G3FNJ | 31 | 76 |
| G2FSR | 39 | 162 | Phone only | | |
| G2VD | 39 | 156 | G3DO | 37 | 135 |
| G3BI | 39 | 146 | G8QX | 35 | 120 |
| G4AR | 39 | 131 | G3DAH | 34 | 99 |
| G2AO | 39 | 119 | G6CB | 31 | 87 |
| G5MR | 39 | 110 | G2VJ | 31 | 84 |
| G6PJ | 39 | 85 | | | |
| G3ATU | 38 | 150 | | | |
| G3AKU | 38 | 130 | | | |
| G5FA | 38 | 124 | | | |
| G8KU | 38 | 116 | | | |
| G3DAH | 37 | 113 | | | |
| GC2CNC | 36 | 162 | | | |
| G6BB | 36 | 102 | | | |

qualified to give them. We have certainly heard some terrifying suggestions made from time to time, some of which would certainly blow the gear or the operator sky-high.

GW3ECH (Trecwn) tells us that SU1HF is now back home as W6IAQ/5, and he says that all SU stations now on the air are either very brave or very foolish.

Department of Low Moans

You didn't think you could get away without a few grouses, did you? But we have kept them until the end. G2AO (Malvern) says a character known to him as the Arch-Spiv practically drove him off 14 mc, and now he's cropped up on 3.5. With his T7 note he practically oozes "Get off the air, boys; I'm going to work this one."

G3ESP (Wakefield) suggests that wielders of bug keys shouldn't send fast until they know how to—a recent "569" report, sent twelve times fast, contained 6's with every number of dots from two to seven! Phones which are in the CW bands and modulated 150 per cent also come in for comment.

GW3ZV (Rhigos) says there are too many moans, and "Spiv" is just another name for someone who works the chap you are after. When they pile up, he says, he either joins the pile and takes what's coming or goes off the air.

G4QK (Croydon) remarks that al-

though one of the advantages of a Clapp oscillator is that it will key nicely, even through a lag circuit, some of them dish out wonderful key-clicks. G2HIF (Didcot) pleads for more use of the 28 mc band for local phone, in the evenings after the DX has gone. As he rightly points out, there are lots of kilocycles there and some of the local chatter on 3.5 and 7 mc is now causing more interference with DX than it would on 28 mc. If the lack of activity after 2030 is due to TVI, he suggests that it is a bad thing. There's too much of the attitude that QRT is the only cure for TVI; there *are* answers, and lots of people have found them, but not those who have gone off the air.

1.7 mc Postscript

Last month we mentioned that G3AUR was heard 135 miles South of the Azores on the top band. Now G3AUR (Benson) writes to say that he is very sorry, but he wasn't—he only operates on 7 and 3.5 mc. So it was either a pirate or a misread call. G2YY (Berwick) has, however, received a very nice report, according to G3AFL (Berwick), in the shape of an Air Mail from Habbaniya, Iraq, where his 1.7 mc signals were 459 at 2250 on December 11. A very nice piece of DX, this.

And on the subject of Top Band working, G5AU (Warrington) is running a series of enterprising tests which will be of great interest to many 1.7 mc operators. By holding it up on a number of balloons, he is testing a vertical (or near vertical) aerial 530-ft. long, on 1840 kc from 2300 on Saturday evenings and on 1740 kc from 0600 on Sundays; all transmissions will be on phone, and reports (which should be sent through us) are particularly requested from outside the British Isles.

Competitive Stuff

This month we publish only the top-scorers in the 1948 Marathon, which is now past history. Also, anent the remark last month about regretfully having to place ourselves at the top of the Four-Band Table (28 mc Order of Merit), we are glad to say that G6HL arrived in the nick of time and takes top place with the fine score of 118 countries on 28 mc. Next month the list will be in order of 14 mc scores once more.

Don't forget that if we don't hear from you for three consecutive months your score is automatically removed from the list to make way for others.

For the time being we will continue to publish the list of Post-War Zones and Countries worked, but we regard the



“... A long CQ call ...”

Four-Band List as the main thing and are glad that it has become so popular.

Closing date for next month will be February 9, first post. Please note this, because on account of the short month it is about the earliest deadline we have yet had. All letters, lists and so on to be sent as usual, please, to DX Commentary, *Short Wave Magazine*, 49 Victoria Street, London, S.W.1. What will next month's mail bring? Anything might happen. So 73 and BCNU.

*Read the
Short Wave Magazine Regularly*

Power Pack Design

Condenser and Potential-Divider Values, Voltage Stabilisation and the Bias Supply

By P. E. LEVENTHALL, B.Sc. (G3CJJ)

PART I

(This useful article deals in detail with many obscure points in connection with power supply design. Too often, amateur power packs are thrown together without due regard to the correct choice of values for the service required.—Ed.)

WHILST designing a power supply recently it was borne upon the writer that there is scarcely any information available on the subject in a form suitable for assimilation by the average amateur.

In discussing the matter with several of them, the writer was forced to the conclusion that power supplies have hitherto been built on a system of hit-or-miss guesswork. This is particularly so in the case of the condenser input filter where there seems to be great difficulty in deciding on the correct value of the input or reservoir condenser.

The amateur generally regards the power supply as the least important part of his equipment and simply wires up the standard full-wave circuit using any condensers which may be to hand.

It will be clear that this is an unfortunate state of affairs when one realises that a power pack is required for practically every piece of apparatus in the station and may give rise to many troubles, from intolerable hum in a receiver to frequency creep in a transmitter.

It is with a view to easing this unsatisfactory position that this article has been written and it may not come amiss to give, by way of preamble, a few short notes on the operation of the reservoir condenser.

Basic Theory

The wave-form of the output voltage across the resistance load of the simple half-wave rectifier system Fig. 1a, is shown by the graph Fig. 1b. The resulting wave-form when a condenser is placed across the load is shown by the heavy line in Fig. 1c. The corresponding figures for full-wave rectification are shown at Figs. 2a, 2b and 2c. The dotted line represents the DC output voltage while the thick line is the superimposed ripple voltage.

It can be seen that the ripple voltage, or

hum, has twice the frequency of the supply in the full-wave case and is therefore more easily filtered off.

The rectifier conducts only during a small part of each cycle when the applied voltage is near its peak, and the reservoir condenser charges up to this peak value. The charging ceases when the peak is passed, and the condenser begins to discharge through the load until the voltage across the condenser becomes lower than the rising voltage of the next half-cycle (or full cycle in the case of a half-wave rectifier), when the charging begins again. It is clear then that the condenser acts as a reservoir which is partially emptied and refilled during each half-cycle.

The smaller the charge and discharge with respect to the total charge on the condenser, the less will be the fluctuation or ripple of the voltage, *i.e.* the larger the condenser for a given current drain, the less the ripple or the better the smoothing.


The DC voltage across the condenser equals the peak AC voltage *minus* the average ripple voltage. since the ripple decreases as the capacity of the reservoir condenser increases, it is plain that increasing the size of the condenser increases the effective DC voltage until the limiting case when the ripple is negligible, and the DC voltage across the condenser (or load) equals the peak value of the applied AC voltage.

A simple analysis shows that

$$V = E_{\text{peak}} - \pi IX$$

where V is the DC voltage across the reservoir condenser, E_{peak} is the peak value of the applied AC voltage, I is the load current in amps, and X is the reactance of the condenser (in ohms) at the ripple frequency.

The equation may be used as it stands to give most of the information necessary in the design of a power supply, but the

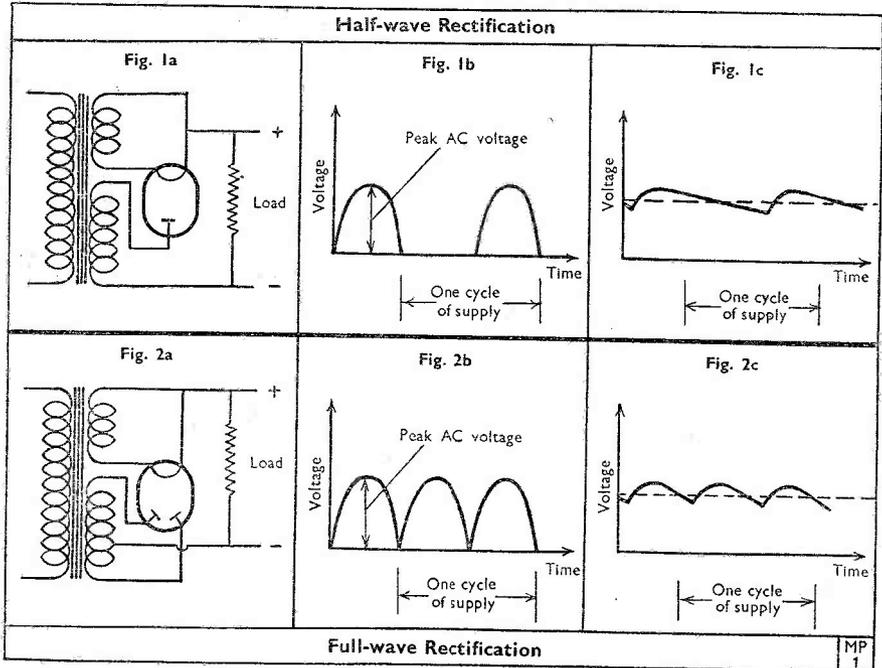MP
1

author has constructed a nomogram which greatly simplifies the task.

Using the Nomogram

The nomogram may be used to find the capacity of reservoir condenser necessary to give a required output from a given transformer, to find what transformer would be necessary to give a stated output using a specified condenser, or to find what output would be obtained using a specified transformer and condenser.

The nomogram has been constructed for full-wave rectification of 50 cycle AC, but may be used for half-wave rectification or for any other frequency by multiplying the values of capacity on the left-hand scale (A) by $(100/f)$, where f is the lowest frequency component of the ripple.

It is necessary to calculate the value of $E_{peak} - V$, where E_{peak} is 1.4 times the rated value of the transformer, and V is the required output voltage. In order to simplify matters to the utmost a "yardstick" has been provided to convert RMS values to peak values. Its range may be increased by multiplying both sides by 10 or 100 as required.

Examples

(1) A receiver requires a power supply

of 300 volts at 120 mA. The rectifier is of the full-wave type connected to a 50-cycle supply. If the input condenser of the filter (*i.e.*, reservoir condenser) is $8\mu F$ what will be the required AC voltage?

Place a straight edge between 120 on the load scale (B) and 8 on the capacity scale (A). The straight edge then intersects scale (C) at 80 volts. Therefore the peak AC input required is $300 + 80 = 380$ volts and converting this to RMS values we have 271 volts.

Hence a 275-0-275 volt transformer capable of supplying 120 mA would be suitable.

(2) Given a transformer with a secondary delivering 350 volts (RMS) each side of centretap, what size input condenser is required to obtain a DC supply of 480 volts at 5 mA?

The peak AC voltage is 350×1.4 (or from the "yardstick") = 490 volts. Therefore, Peak AC - Required DC = $490 - 480 = 10$ volts. Placing a straight edge between 10 on scale (C) and 5 on scale (B) it intersects at $2.5\mu F$ on scale (A) and this is the capacity of input condenser required.

(3) A 500-volt transformer used on 50 cycle AC is to have its output half-wave

rectified. What will be the resulting DC output at 200 mA if an 8 μ F condenser is used?

The peak AC is 700 volts (from "yardstick"). Since the fundamental ripple frequency is now 50 cycles we must multiply all numbers on scale (A) by 100/50, i.e. by 2. The original 4 μ F mark now becomes 8 μ F. Placing a straight edge between 4 on scale (A) and 200 on scale (B) we have intersection at 250 volts on scale (C). Therefore the DC voltage output equals Peak AC - 250 = 450 volts.

If the resistance of the smoothing choke following the reservoir condenser is known, the voltage drop across it may be found by Ohm's Law and added to the required DC voltage. If the rectifier valve is mercury vapour type an extra 15 volts may be added for the drop across the valve.


The nomogram may be employed for

all values of load current from 1 mA to one ampere. It may be used for all voltages since $(E_{peak} - V)$ does not depend on the absolute value of E_{peak} . For instance, if for a given current drain and condenser size, the DC output voltage is 100 volts less than the peak AC input it will be so regardless of whether the peak AC is 150, 729 or 10,000 volts, so long as the current drain and the condenser capacity remain the same.


The Filter Circuit

The smoothing filter is another piece of apparatus which, though very important, is often imperfectly understood. This need not be so as its mode of operation can be quite simply explained.

Fig. 3a represents the ordinary type of filter circuit as used by amateurs, the terminals A and B being connected across the reservoir condenser. The input to


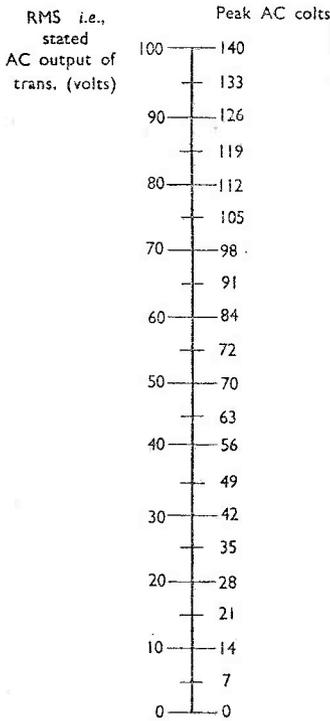


"YARDSTICK"

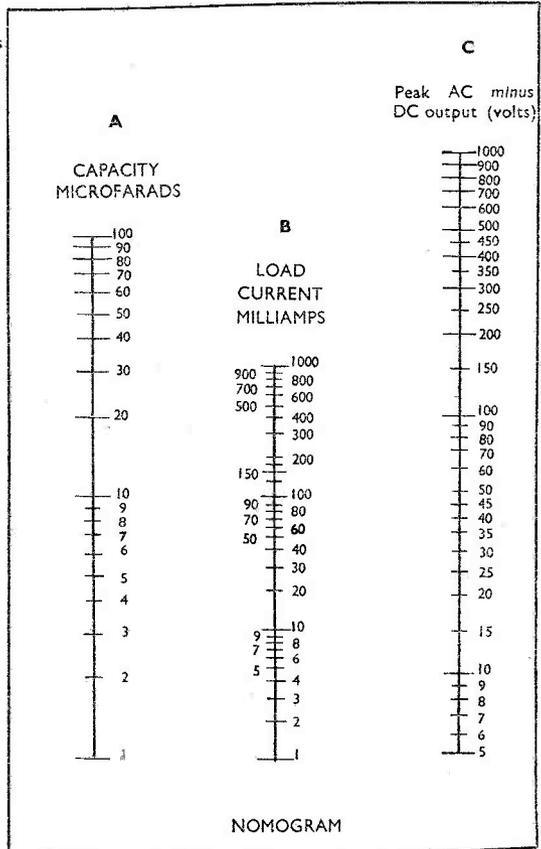

NOMOGRAM



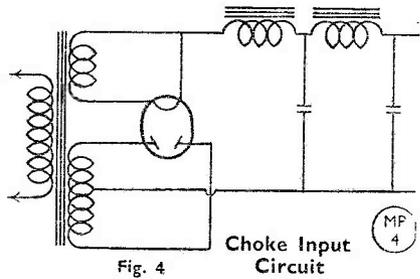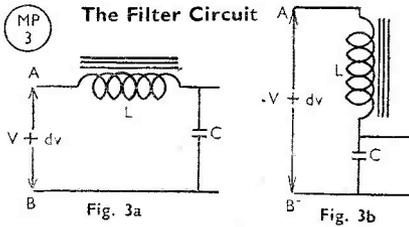

A and B therefore, consists of a steady voltage V , with a superimposed ripple voltage of magnitude dV .

If the filter circuit is redrawn in the form shown in Fig. 3b, its operation at once becomes apparent as it is no more than a voltage divider or potentiometer.

As far as the DC component V is concerned, the condenser presents an infinite impedance to this and the total DC voltage is obtained across the condenser, minus only the ohmic loss due to the resistance of the wire in the choke.

The ripple component (which is AC) fares differently. The choke presents a high impedance to the ripple frequency, while the condenser acts almost as a short circuit.

Thus, the greater part of the ripple voltage appears across the choke and only a very small part across the condenser with the DC component.

It is in this way that the filter performs its operation of smoothing the rectified supply.

This result may be quite easily expressed quantitatively.

The magnitude of the ripple voltage across the condenser is given by

$$dV \times \text{Reactance of } C = \frac{dV \times 1/C\omega}{\text{Reactance of } L \& C = L\omega - 1/C\omega}$$

where L is in henries
 C is in farads
 dV is in volts

and ω is the pulsantance of the ripple frequency and equals $2\pi f$.

This expression reduces to approximately

$$\frac{dV \times 10^6}{4 LC \pi^2 f^2}$$

where C is now in microfarads (μF).

As an example, suppose $L=30$ henries, $C=8 \mu F$, $f=2 \times 50=100$ cycles/sec. Then the magnitude of the ripple across the condenser equals

$$\frac{dV \times 10^6}{4 \times 30 \times 8 \times \pi^2 \times 10^4} = \frac{dV}{96}$$

Thus the ripple voltage has been attenuated to $1/96$ of its previous value or to approximately 1 per cent. Further attenuation of the same order may be

obtained by connecting another such filter after the first one.

It is clear from the expression above that the attenuation of the ripple depends upon the values of L , C and f , the ripple becoming smaller as these are increased.

Therefore, in order to obtain good smoothing the advice is to use full-wave rectification ($f=2 \times$ supply frequency), and to make L and C as large as possible. It is, of course, necessary to see that the working voltage of the condensers is not exceeded and that the chokes can pass the required current. The resistance of the chokes must be such that they do not cause too great a voltage drop at the required current.

Choke Input Filter

Where good regulation of a heavy power supply is required (such as for a large class-B modulator) it is often preferable to use a choke input filter as shown in Fig. 4. Filter stages as described in the previous section may be added to give any required degree of smoothing.

Advantages of the choke input filter as compared with the condenser input filter are,

(a) The regulation is better, *i.e.* the output voltage is more nearly constant when the load is varied.

(b) The condenser charging current is reduced owing to the choke being interposed between the rectifier and the condenser. This restriction of the current prolongs the life of the rectifier and is particularly useful in the case of mercury vapour rectifiers.

The choke is usually of the swinging type, and for design data it is merely necessary to refer to the manufacturer's details for the rectifier being used.

The voltage output for a given transformer and rectifier is less with the choke input filter than with condenser input.

(Part II of this article will follow)

Two-Metre CC Converter

New All-Triode Design for the 144-146 mc band


By M. D. MASON (G6VX)

(It can fairly be said that the design here presented typifies the very latest in VHF receiver techniques. It is a crystal-controlled converter tuned on the IF side and can be operated with any modern communications receiver. Our contributor brings out a number of very interesting design problems in VHF receiver circuitry and shows how they should be met.—Ed.)

THE more simple a converter becomes, the better it seems to perform, a point which is proved by the performance of this all-triode design.

The crystal-controlled converter to be described is probably the simplest and cheapest yet devised. The only requirement for smooth performance is a reasonably good communication receiver, free from unwanted signal pick-up within the IF channel with the converter in operation. The IF channel considered is the range

over which the receiver is tuned to cover the 144-146-mc band—in this case 8-10 mc. When this condition is satisfied, signals on two metres are handled with the same ease as when the set is used direct, working on the 8-10 mc band with its normal aerial. Hard-bitten operators do not really worry about the congestion on the HF bands—they only grumble a little but still work who they want. Well, let the QRM come to 144 mc and with this converter you will be more than half-way equipped to cope with the worst congestion.

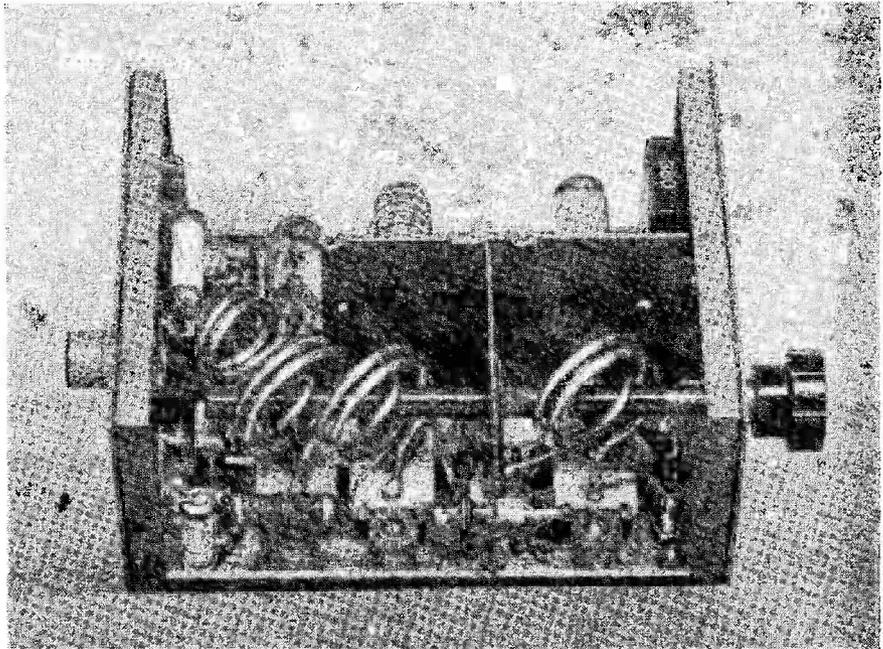

Underside view of the 144 mc converter. The permeability tuner is clearly visible, working in the fields of the RF circuit inductances.

MR
93

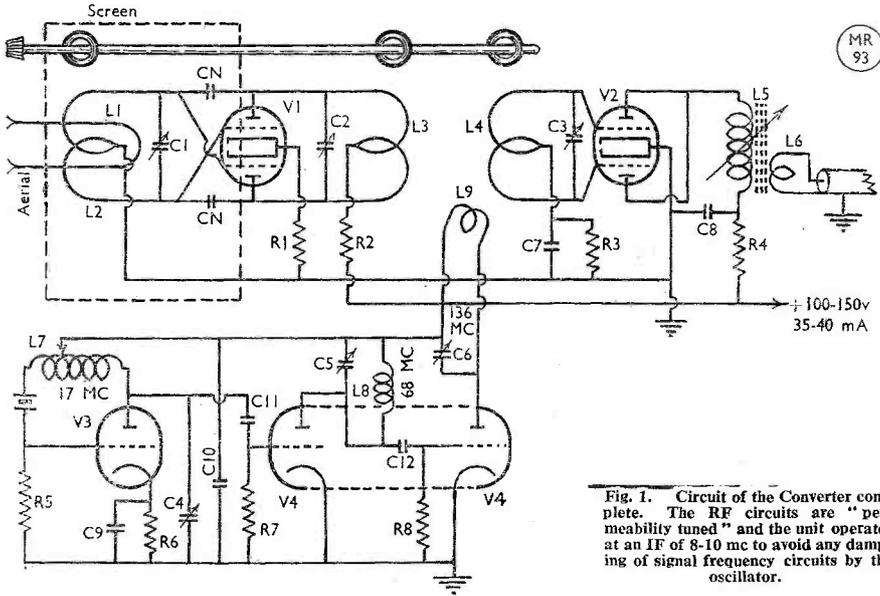


Fig. 1. Circuit of the Converter complete. The RF circuits are "permeability tuned" and the unit operates at an IF of 8-10 mc to avoid any damping of signal frequency circuits by the oscillator.

Circuit

The RF stage was developed after several broad-band amplifiers had been used, all producing very good results. It was felt that a little off-channel discrimination would be worth having if this could be achieved in some simple manner. All the gain required can quite easily be realised from two stages of broad-band RF amplifiers, adjusted for 2 mc bandwidth using, say, 6AK5's. A single 6AK5 with optimum concentric line input and output circuits will out-perform the broad-band amplifiers as far as noise and selectivity are concerned, but this system requires some expert plumbing for a pretty job.

The neutralised push-pull triode RF stage has had some very convincing support from leading VHF workers, and seems fully to justify its consideration when quiet RF amplification is the object.

This RF amplifier is, indeed, well worth a trial on its own, since it can be constructed so easily. It may be tested by link coupling to the regular two-metre receiver. The noise increase is only just noticeable, but when the tuning is peaked on a signal the real benefit is immediately apparent.

The 6J6 mixer was chosen for its clean symmetrical input circuit at signal frequency. Optimum oscillator injection is

Table of Values

Fig. 1. Circuit of the 2-Metre CC Converter


- C1-C6 = 3-30 μ F trimmers
- C7 = 50 μ F
- C8, C9 = .001 μ F
- C10 = .01 μ F
- C11 = 15 μ F
- C12 = 25 μ F
- Cn = $\frac{1}{2}$ -in. dia round discs spaced 1/32-in.
- R1 = 50 ohms, 1 watt
- R2 = 3,000 ohms, 1 watt
- R3 = 1 megohm
- R4 = 50,000 ohms
- R5 = 10,000 ohms
- R6 = 150 ohms
- R7, R8 = 47,000 ohms
- L1 = One turn 20 SWG enamelled
- L2, L3, L4 = Two turns 14 SWG silvered $\frac{3}{8}$ -in. I/D. spaced 1/16-in.
- L5 = 50 turns 40 SWG on $\frac{1}{2}$ -in. dia iron-dust core, adjusted for 9 mc
- L6 = 10 turns 30 SWG wound close to L5
- L7 = 21 turns 30 SWG on $\frac{3}{8}$ -in. former, tapped at 7 turns
- L8 = 5 turns 20 SWG Tinned on $\frac{3}{8}$ -in. rod, turn spacing equal to wire diameter
- L9 = Two turns 14 SWG silvered wire $\frac{3}{8}$ -in. I/D

Note: L1, L3, L4 mounted at 45 deg. to shaft. Spacing L3-L4, $\frac{3}{8}$ -in. Spacing L4-L9 $\frac{3}{8}$ -in.

V1, V2, V4 = 6J6

V3 = 6J6 or 6C4

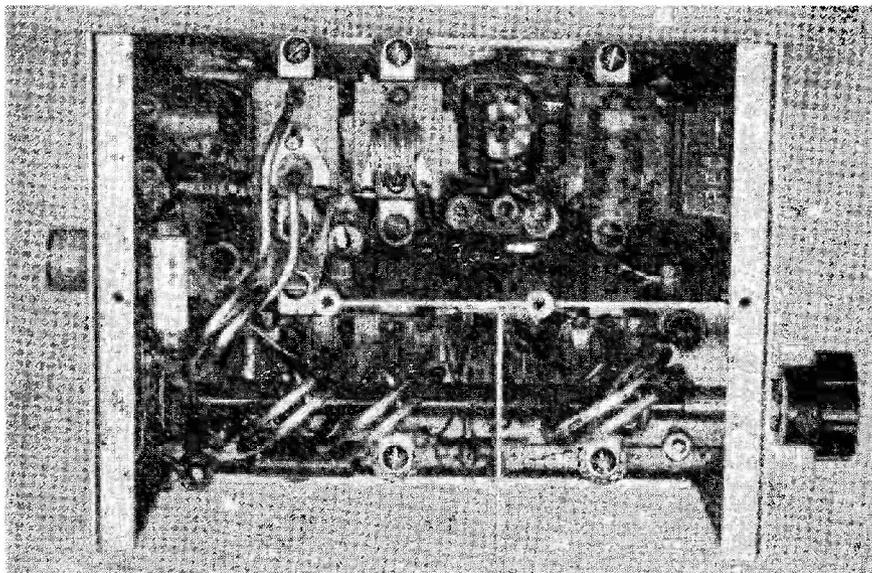One side of heater line earthed. Crystal of 5666-66 kc for 8-10 mc IF. RF tuning by means of $\frac{3}{8}$ -in. I/D completed rings of 14 SWG silvered wire mounted at 45 deg. to paxolin control shaft.



Another view of the underside of the G6VX converter.

not too critical and conversion efficiency is quite good, with the added advantage of low noise. This particular circuit in conjunction with a 6J6 is recommended by RCA for operation up to 600 mc.

The IF Side

A few suggestions are in order for choosing a suitable tunable IF to use with a fixed HF oscillator or crystal-controlled converter. The most important point to check is that the main receiver is free from unwanted pick-up on any of the bands that may be usable for the IF. This check can be quickly performed by connecting the aerial terminal to chassis *via* a very short connection. Then turn up the RF and audio controls, switch on the BFO, and search the desired band for unwanted signals. This test is worth doing both for day and night time conditions, since signal strengths can vary so widely depending on conditions at any time. Supposing a few weak signals are found, do not give up until a check is made to determine whether or not they are coming in through the HT power or heater wiring.

The power input cable is another source of pick-up. When a separate power supply is in use, by-pass the heater leads to chassis with $.01 \mu\text{F}$ condensers just after the heater heads enter the set. Do the

same with the HT leads, but place in series with each a 1 mH choke, and by-pass the set side of the chokes to chassis with $.01 \mu\text{F}$ condensers. If the RF stages of the set are sufficiently screened in the first place, the filters should complete the job.

One other possible source of slight pick-up is the coaxial cable connecting the converter to the set. A useful tip to help eliminate this trouble is to use an *additional screen* over the top of the first coaxial cable. This can be made by pulling the centre core out of a larger size coaxial cable and then threading the small one through. Bond the screens together at each end. Another worth-while precaution for avoiding unwanted pick-up on the tunable IF range is to place a 1 mH HF choke in the HT lead, inside the converter. At the same time by-pass the "hot" heater lead to chassis.

The choice of IF can be governed by several considerations: Available crystals on hand; calibration of the main set; and band-spread and ease of logging. It is convenient to use a spot where the dial reads almost directly, *i.e.* 24-26 mc or 14-16 mc or 34-36 mc or 4-6 mc.

Choice of IF

A design factor comes into the choice of the final IF. If careful shielding of the

144 mc amplifier and aerial input is not possible or convenient, it is a good tip to use a high IF so that the local oscillator frequency is well removed from the signal frequency, otherwise several volts on the grids of the RF amplifier may completely overload this stage and render it worse than useless. It must be remembered that the selectivity of the usual coil-condenser arrangement at 144 mc can be measured in megacycles and not in kilocycles. The exception to this is a properly designed coaxial line tuner. The converter being described has sufficient shielding to allow an IF as low as 6 mc without any trouble. It will be realised from these remarks that a mixer giving the lowest possible injection voltage for optimum conversion will help a great deal in avoiding RF amplifier overloading by the local oscillator. Another important point in selecting the tuning range is to determine the IF of the main receiver, and whether the oscillator tracks on the HF or LF side of signal frequency. These points must be known so that a suitable crystal can be selected to avoid unwanted "birdies" being generated. The crystal frequency for the converter must be on the LF side of 144 mc if the main receiver is to read the same way as the dial calibrations, and not backwards.

Crystal Frequency

Choosing the fundamental crystal frequency: Suppose an IF of 8-10 mc is convenient, the final oscillator frequency must be 136 mc, *i.e.* $136 + 8 = 144$. If the main receiver IF is 455 kc and its own HF oscillator tracks on the high side of the signal, no harmonic of the crystal must fall in the range of 144 to 146.5 mc, or 8 to 10.5 mc. If the image-ratio of the main receiver is not very good, crystal harmonics must not fall in the range of 8 to 11.5 mc. When this point is taken care of, it is still possible to receive strong stations in the 144 to 146 mc band on their correct frequency, and again at 910 kc removed. This only occurs when the image ratio at 8 to 9 mc is very poor. Of course, a possible solution to all these difficulties is to feed the converter directly into a good TRF receiver. It works very well, but the usual advantages of noise limiters and crystal gates are not normally available, and the main idea of using your favourite receiver on VHF is lost.

Working backwards from 136 mc, the next possible harmonics are 68 mc and 44 mc. Warning! Do not touch 44 mc with any kind of tuned circuit; TV smells this one out yards away! But 68 mc can

be generated from 34 or 17 mc; this means that the lowest crystal frequency to be considered is 17 mc. It must be remembered that if the same accuracy of calibration on 144 to 146 mc is desired as when the main receiver is tuned on the 8 to 10 mc range, the converter crystal must be *exact*, so that the 136 mc oscillator frequency is nothing but 136 mc. Whatever errors appear will misplace all signals by that amount.

Fortunately, a crystal oscillator circuit recently described from America is just right for making use of nominal low-frequency crystals on the third harmonic, which in this circuit appears as the fundamental. Therefore, to generate 34 mc a 11.3333 mc crystal could be used. However, it is much cheaper to make it a 5666.6666 mc crystal and let the oscillator frequency be 17 mc.


It is fairly safe to say that practically any of the "surplus" crystals mounted in the small-type holders can be made to go off at their third harmonic without any difficulty. The only points to watch are that the crystal is perfectly clean, that the LC ratio of the oscillator circuit is correct, and that the feedback winding is just sufficient to produce oscillation with the crystal in circuit.

Construction

The converter can be made up in any convenient form as long as certain precautions are taken. It is important that the RF amplifier be built symmetrically and screened as much as possible. The 6J6 RF valve is mounted so that the grids are on one side of the screening partition and the plates on the other. The neutralising condensers are placed so that one connection from each goes directly through the screen partition and connects to the crossed-over grid leads. The coils have been mounted directly on their respective trimming condensers. The trimmers are mounted on half-inch lengths of $\frac{3}{8}$ -in. polystyrene rod. A trimming hole is drilled through the chassis so that the final adjustment can be made with the bottom covers in place. This assembly is common to all trimmers and coils.

The tuning system is straightforward in construction, and very easy to build and adjust. The amount of frequency coverage is determined to some extent by the diameter of the tuning loop. The dimensions given cover about 143 to 147 mc for 180 deg. rotation. Tracking troubles are quite easy to overcome since the coils tune fairly flatly. The aerial coupling is very

MR
94

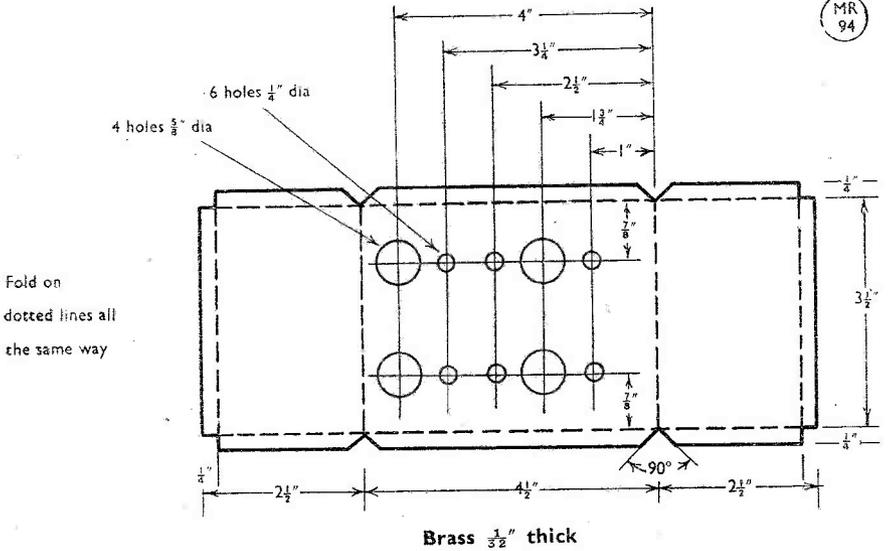

Fold on dotted lines all the same way


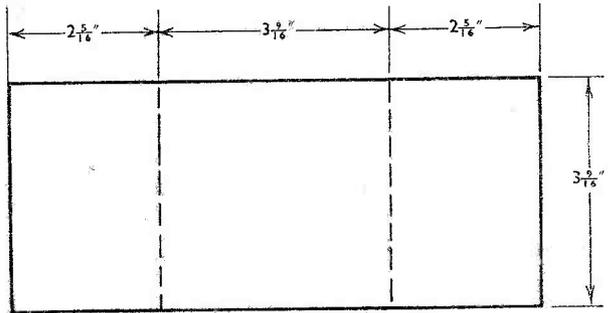
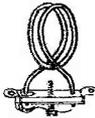


Fig. 2. Detail of the chassis construction.

tight, consisting of one turn almost in line with the two on the input coil. The coupling is adjusted by bending the single turn at right angles to the input coil for minimum coupling. The amplifier plate winding and mixer grid coil are far more critical for tracking. The coupling is fairly loose, and the trimmers are very effective. All trimmers are set for the HF end of the band and the spacing between turns is adjusted to vary the inductance at the LF end. The tuning loops should all be spaced symmetrically in the centres of their respective coils. When the tuning shaft is rotated 180 deg. the loops should have moved together from a position at right

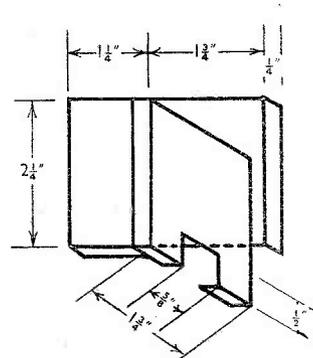

angles, to a position perfectly in line with the coils.

Neutralising of the RF stage may be checked in several ways. One method is to place a 25 mA meter in series with the 3,000-ohm HT feed. When the tuning loops are rotated or when any of the coils are touched there should be *no change* in the plate current once the neutralising condensers have been set correctly. The second way is to put the converter in operation, and when the RF tuning is rotated, oscillations all over the 144 band will appear if the amplifier is not neutralised. Adjust the condenser until the amplifier becomes perfectly stable. A third method suggested is to connect up the converter with no HT on the RF stage. Tune in a strong local signal and then adjust the neutralising condenser until minimum signal gets through the RF stage. When the HT is now applied the amplifier should be working correctly. The use of the 3,000-ohm 1-watt resistor in the plate feed was found to give more stable operation than a more normal RF choke.

From the photograph it can be seen that the coils are mounted by soldering to the eyelets on the trimmers. These eyelets are soldered to the plates on the opposite side, otherwise a very poor contact may develop. The oscillator socket should be connected as follows: Pin 1, anode; 2, blank; 3, earth; 4, heater; 5, blank; 6, grid; 7, cathode. When this sequence is observed, either a 6J6 or a 6C4 may be used with no change in operation.

Mechanical Construction

The chassis size is $4\frac{1}{2}$ in. long by $3\frac{1}{2}$ in. wide by $2\frac{1}{4}$ in. deep. The centre screen is 3 in. long and the dividing screen which mounts through the RF is $1\frac{1}{4}$ in. The outside cover just meets this screen and therefore encloses the input circuit more or less completely. The converter could be built much larger without affecting the performance. In fact, one was built where the crystal control section is completely separate from the signal circuits. The 136 mc signal was link-coupled to the mixer and results were just as good. The neutralising condensers were made by fitting two thin metal discs, $\frac{1}{8}$ in. diameter, on to the small ceramic tube removed from a Philips' 3-30 μF trimmer. The same results could be achieved by twisting two pieces of insulated wire together, long enough to make up a condenser of 2 to 3 μF .

One or two final points when adjusting

aerial coupling: If the aerial coupling is made too loose, the aerial trimmer will appear quite critical, and if the amplifier is only just neutralised a great increase in noise will appear which may give the impression of colossal gain. This condition is unstable, and will be upset by a strong local signal; at the same time the signal-to-noise ratio is nowhere near optimum. When this converter is operated in conjunction with a HQ-120 receiver, the RF gain control on the latter is set so that the background with BFO in operation and the converter HT off is just perceptible. When the converter is switched on there is a slight increase in noise, but when the aerial is connected there is a very definite increase. This condition is very comfortable to operate, and there is not much fear of missing any signals that should be heard. When the receiver is operated in semi-sharp crystal filter position there is practically no noise at all, although the sensitivity is just the same.

CARDS IN THE BOX

If your call is here, it is because there are card(s) being held for you by our QSL Bureau, and we have not got your address. Please send a large stamped self-addressed envelope to BCM/QSL, London, W.C.1, and the cards will be forwarded on the next G clearance. Should you want your callsign and address to appear in our "New QTH's" column, please mention it at the same time; this will also ensure publication of your QTH in the *Radio Amateur Call Book* in due course.

G2AKU, 2ALV, 2BZT, 2HCR, 2HHP, 2KS, 2KZ, 2ND, 2PH, 3AAP, 3AAW, 3AEA, 3ATX, 3AVV, 3BER, 3BIT, 3BMY, 3BOQ, 3BQT, 3BRZ, 3CBQ, 3CFP, 3CLT, 3CXY, 3CZA, 3DAQ, 3DBY, 3DEO, 3DEZ, 3DKJ, 3DNP, 3DOK, 3DPE, 3DPH, 3DQA, 3DQL, 3DRE, 3DRP, 3DRT, 3DSG, 3DUB, 3DUD, 3DUP, 3DWK, 3DXI, 3DYD, 3DYZ, 3DZR, 3DZU, 3EAJ, 3EBG, 3EBR, 3ECP, 3ED, 3EDO, 3EDV, 3EFX, 3EGJ, 3EGK, 3EGV, 3EHA, 3EIP, 3EJH, 3EJP, 3EJV, 3EKG, 3EKW, 3EKY, 3ELI, 3ELL, 3ELQ, 3ENO, 3EOG, 4JZ, 4QA, 6GU, 6IW, 6SP, 8PT, GC2AW, 2FMU, G13AXE, 3ECQ, 3EEP, 4BA, GM2AZN, 2CAP, 3BS, 3EJS, 3EMG, 3ENJ, 5PJ, GW3CYB, 3DPO, 3DXP, 3EOP.

THE VHF BANDS

By E. J. Williams, B.Sc. (G2XC)

Lull in Activity—

Notes on Propagation—

Club Progress—

Individual Reports—

MOST of our experienced VHF enthusiasts have come to recognise the types of weather that produce DX conditions, and as a result many are tending to appear on the bands only when conditions are likely to be favourable. This is regrettable, for not only does it discourage newcomers but occasional good spells pass by without there being sufficient activity on the band to take advantage of them.

There is, however, another aspect of the question and we believe many may share our own view that if only a limited time is available for Amateur Radio, then it is best to do the constructional work during the periods of poor conditions and operate when the bands are open for DX! One therefore hopes that the low level of activity of which everyone is complaining this month may indicate much benchwork in progress preparatory to renewed activity in the coming months!

Conditions generally have been poor compared with November, although there have been indications of occasional good days. To judge by the strength of the TV signals on the South Coast during the Christmas period VHF conditions must have been very good indeed. December 25 and 27 were outstandingly good evenings. Other good evenings are mentioned in the individual reports.

Propagation Notes

No apologies are made for returning to a subject which has been discussed on numerous occasions in the last twelve months. More than once has it been given as your conductor's personal opinion that ducting failed to explain at all adequately the good GDX conditions so frequently encountered on 5 metres during the past few years. We are well aware that the long-distance radar effects experienced during the war were explained by this theory, but in every case the phenomenon occurred *over the sea* and usually in hot climates where temperatures and humidity conditions would almost certainly be very different from those existing *over land* in this country.

By the ducting theory VHF DX is due to super-refraction which is caused by

an abnormal gradient of refractive index with height in the lower atmosphere, or troposphere. The rate at which the refractive index decreases with height is determined by three factors, viz. pressure, temperature and humidity. At the surface of the earth the refractive index of the air is of the order of 1.0003, and decreases in the tropospheric regions by about .000012 per 1,000 feet under "normal" conditions. By "normal" is meant occasions when there are no markedly rapid changes in humidity, and when temperature decreases gradually with height. The bending produced in radio waves by this change in the index is small and far less than the curvature of the earth's surface. It does, however, extend the "radio-horizon" to beyond the geometrical horizon, the extension being about 1/5. To produce a curvature equal to that of the earth the refractive index must decrease by .000048 per 1,000 feet. This figure is the generally accepted one and can easily be obtained by a consideration of the dimensions of the earth. Under such conditions a ray radiated horizontally from a transmitter would just follow the earth's curvature, while all rays leaving the transmitting aerial at angles below horizontal will ultimately reach the earth's surface.

If the gradient of refractive index exceeds the figure given above, then some of

| TWO METRES COUNTIES WORKED LIST | |
|------------------------------------|-------------------|
| Worked | Station |
| 25 | G2AJ, G2AXG |
| 23 | G2IQ |
| 20 | G5NF |
| 19 | G2NM, G4LU |
| 18 | G2CIW, G5BY, G6PG |
| 17 | G2XC |
| 15 | G8KZ, G8QX |
| 14 | G2NH, G5RP, G6LK |
| 13 | G5BM |

the horizontal radiation will be bent sufficiently to come down again. Thus, some of the rays are trapped as if in a duct and travel round the earth's surface, aided sometimes by reflections at the ground. The effectiveness of the trapping is dependent on the height of the duct and the wavelength, long waves requiring larger ducts than short waves. Hence ducting is most noticeable on VHF and UHF.

Analysis of Conditions

An examination of the Air Ministry data for most of the good dates of the post-war years has failed to reveal even one occasion on which a ground-based duct with the necessary gradient of $\cdot 000048$ per 1,000 feet has existed, although figures of up to $\cdot 00004$ have been obtained on rare occasions due to particularly favourable dispositions of temperature and humidity. But such a figure will not do more than extend the VHF horizon somewhat. It will not produce a true duct. Further, GDX has been reported on many days when there has been no indications whatever of even a tendency towards a ground-based duct. On these dates the characteristic tropospheric phenomenon is always the existence of an elevated temperature inversion and/or humidity gradient, frequently at a height of 3,000 to 5,000 feet. If such a layer is to return signals to earth by pure refraction the index gradient will have to be considerably in excess of $\cdot 000048$, as the length of path in the layer where most, if not all, the bending has to be produced is small compared with the total distance from transmitter to receiver. Again, such gradients do not exist over the British Isles, but there is no reasonable doubt that GDX conditions are produced by the elevated humidity contrasts and inversions.

In view of the arguments set out above it appears to us that the actual turning back of the waves must be reflection, aided of course by the condition of grazing incidence produced by refraction.

The reason for dealing with this topic at some length is that we were recently challenged by one reader to prove our grounds for arguing with the "experts"! We are not sure that we are really arguing, as so far we have seen no paper dealing with GDX in the British Isles. Your commentator is still open-minded on the subject and ready to listen to arguments showing that he is wrong—to which end the correspondent mentioned is providing a full article for the *Short Wave Magazine*.

Individual Reports

G2ADZ (Oswestry) enquires what has happened to activity in the South. He found conditions very good on December 17 and 23. On the former date G3DEP (Ryde) was worked, but nought else, and on the latter G2NH and G6YP provided the DX. G2ADZ usually comes on at 1830 and keeps going until 2130, but finds it tiring listening to nothing! A maximum activity period from 1930 to 2300 daily is suggested by him and we strongly commend this to all 144 mc operators. The Cheltenham stations G5BM and G6ZQ provide consistent signals in Oswestry, 83 miles away, under all weather conditions—including six inches of snow on G2ADZ's beam. Signal strength is better than was obtained on 5 m. and never less than S7. But QRK's are not so good at G4LU 250 feet higher up. GW5SA has been heard through (?) the Welsh mountains.

G2AOL (Otford, Kent) still continues active on five, and hopes to do so until the bitter end. He occasionally finds a new station and has reached 97; his target was 100 by the end of 1949. G2AOL is there daily, 1830 to 1915 and 2215 to 2245, and says all callers are welcome. G2BMZ has been endeavouring to receive the TV programmes in Torquay and in spite of some extremely poor conditions has met with a measure of success.

G2CIW (Brentwood) now has a crystal controlled convertor in use on 2 metres and finds it markedly superior to anything he has yet built. The line-up is 6F6 7 mc CO, 6V6 quintupler, 9002 quadrupler into EC52 mixer. RF stage is 6J6 cathode coupled, and IF is 3.4 to 5.4 mc on AR77. G2IQ (Sheffield) reports activity very low in his area, but comments that he frequently hears London stations at S7, working each other, and asks whether they do not want to work DX or have they forgotten there are stations outside London? However, he finds G6VX as consistent as ever he was.

Two-Metre DX Working

| Worked | Station |
|------------------|--|
| Over 350 miles | G2IQ, G5BY |
| 300 to 350 miles | G2BMZ, G2MA, G4LU, G6WT |
| 250 to 300 miles | G2XC, G6OS, G8DM |
| 200 to 250 miles | G2AJ, G2CIW, G2OI, G3DEP, G5MQ, G5RP, G5TZ, G6DH, G6PG |


G3APY (Kirkby, Notts) has been inactive due to illness. In Lancashire G3DA (Speke) has maintained a schedule for six weeks with G5CP (Sale); but they have failed to find any kindred spirits. G2OI and G3BY are heard occasionally. On November 8 G3DMU (Scunthorpe) and G2IQ were worked. Both G3DA and G5CP are on 144.14 mc daily at 1900, and at intervals up to 2230.

G3DCV (March) is yet another to join the ranks of the DX TV enthusiasts and finds he receives AP very well when the barometer is high. G3EHY (Banwell, Somerset) reports increasing activity on two metres in his area, at least three stations putting out good signals. Much time was wasted due to an absorption wavemeter being 6 to 8 mc off calibration. Now that this has been rectified it has been possible to locate the band and signals are coming in. A 3-ele. w.s. beam is up and a number of carriers have been heard from over London way. A little more signing on CW would be appreciated at G3EHY. His converter is CV66-EF54-EC52 into BC-342. An EF54 RF stage was found to be noisy, and a test is to be made with a 6AK5 between the CV66 and the mixer. G3EHY has tried neutralised triodes using 6J6, but in spite of the low noise level and good gain, finds the GGT superior; IF is 18 mc. Active in his area are G3YH and G6JG, both in Bristol, the former VFO on 145 mc, and the latter with MCW and RT on 145.3 mc.

G4LU (Pant, Salop) has worked only six stations in the past month, although they included two new counties. G8DM was a good signal on December 20, G5MA being heard the same evening. G8WV was worked on December 27, the solitary DX occupant of the band at the time. The first 11 days of 1949 produced *nil* results for G4LU. We hope the remaining 354 may be a little better!

G4LX (Newcastle) has now deserted five and is on two metres only. Frequency is 145.116 and he beams on London nightly at 2230. G3CYY is also active and G2BDQ is nearly ready. The last-named is in a poor spot for working South but hopes for some GM's.

G4LX again complains of the poor response to QSL's. Being in a rare county all stations working him make special requests for cards and he has been in the habit of sending these direct whenever possible. In spite of this a large number of stations have failed to reply. He has supplied us with a list of these—so look out, you VHF Century Club claimants!

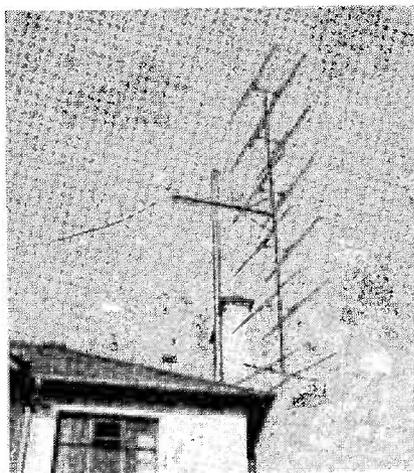

The 24-element two-metre beam at G6WT, Torquay, S. Devon. This is a Chinese copy of the W2NLY version and gives tremendous gain on both transmission and reception.

A ZB2 Unit has been modified as described in the December 1948 *Short Wave Magazine*, but on his model G4LX has had to use 4-turn coils instead of 3 turns, and also found the IF coil tuned to too high a frequency. He wants some information on switching 600-ohm line by means of $\frac{1}{4}$ -wave stubs.

G5BM (Cheltenham), now active on 2 m., has been spending much time on converter design. The final set-up is 6AJ5 RF and 6J6 mixer/osc, with 30 mc IF into HQ120X. A 6J6 cathode-coupled RF amplifier is to be added in front of the present RF stage. He confirms the consistency of the path to G2ADZ and he is usually active 1900 to 2030 and again from 2215 to 2300. A 6-ele. c.s. beam is mounted above his 10 m. beam; frequency is 145.35 mc. On January 9 G5BM worked G2IQ and on January 12, G2OI.

G5MR (Bognor) has doubts about his Rx on 145 mc, although he has heard G6OS at 200 miles. The line-up is EF54-954-955. A crystal job is being designed. G5RP (Abingdon) is still active on five, but has made a new converter for two metres. This is based on the 220 mc converter described in *QST* for October, 1948. On 420 mc G5RP has two receivers in operation—an ASB7 and a P29. The Tx is under way, and a CC converter.

G6DH (Clacton) has been working ON4FG and PAØPN regularly in spite of

the winter season. F8OL, F8NW and F8ZF have also been QSO'd. ON4FG calls G6DH at 1840 daily. G6DH calls "Test 2," beamed ESE, at 1845; and CQ beamed WSW at 2200.

G6HD (Beckenham) is concentrating at 430 mc, and has worked G2FKZ at nearly four miles using 'phone. His Tx is CV82 oscillator and the Rx R.1359. The aerial is a dipole in-a corner reflector, and fires east.

G6WT (Torquay) is active nightly at 1900 and 2200, just to see if the 2 m. band is open. He worked G2NM on January 13. G8PX (Oxford) has a beam 16 feet high for 2 m. and hopes to push it up a bit soon. He has worked G2CIW and describes a CC convertor built by a local listener. It has a pair of "lighthouses" in a cross-neutralised RF stage followed by 6J6's, the designer saying that triodes are the only valves to use on 144 mc. We know others who agree!

In Scotland GM3BBW and GM6SR are there every evening at 2200 and would appreciate reports. From France F8OL comments on the excellent November conditions, when there was a strongly

negative gradient of humidity and rapid increase of temperature in the first 900 feet above ground. He remarks that the horizontal field strength of G6DH, PAØZQ and ON4FG reached 5mV/m, which is stronger than the value for rectilinear propagation in free space with no attenuation. F8OL also worked G6WT, though in that direction the local hills subtend more than 3½ degrees above horizontal.

Fiveband Club

During recent months the Fiveband Club has grown substantially in numbers, and plans for social and technical meetings for the coming year are under discussion. With a little more space available this month we would like to give new readers some details of the Club and its activities.

The prime object of the Fiveband Club is to encourage VHF operation and membership is open to all amateur transmitters working on the VHF bands, irrespective of their affiliations. Applicants should send a signed statement that they are actively engaged in VHF work and give an undertaking to encourage and support all such activity so far as they are able. An attractive membership certificate is issued, and no fees of any sort are levied, as the running expenses of the Club are met by the *Short Wave Magazine*. There are thus no conditions of membership other than activity on VHF, nor do we even restrict membership to direct subscribers to the *Magazine*.

On the other hand, regular reports from members are greatly appreciated and help to provide the news in these columns. Club circulars are issued every few months with news of members, including full QTH's. A committee (consisting of G3APY, G5RP, G5YV and G6VX) advises us on matters of policy and organises area meetings. It is hoped to arrange a meeting in the Midlands in mid-summer, while discussions are in progress regarding a suitable centre for a meeting in the South in the spring. Oxford, Bristol and Portsmouth are among the places suggested. The London area members, under G6VX, have recently started a very useful 145 mc frequency measuring service and the first list of frequencies has been circulated to the Club. It is hoped to issue amendments every few months.

The VHF Century Club

The VHF Century Club is open to all Fiveband Club members who can produce 100 post-war QSL's confirming two-way

VHF CENTURY CLUB

LIST OF CERTIFICATED MEMBERS

| | | |
|------------|------------|-------|
| *G2AJ(200) | G3CWW(150) | *G5PY |
| G2AXG | G3DA | G5RP |
| G2CIW | G3DCV | G5YV |
| G2HDY | G3WW | G6HD |
| G2KI | G4AP | G6KB |
| *G2MR | G4IG | G6MN |
| G2MV | G4RO | G6OS |
| G2NH | *G5BD(170) | *G6VX |
| G2OI | G5BM | G6XM |
| G2RI | *G5BY | G8GX |
| *G2XC(250) | G5GX | G8SM |
| G3ABA | G5JU | G8TS |
| G3APY | G5LQ | G8UZ |
| G3BLP | G5MA | |
| G3CGQ | G5PP | |

Total : 43 Full Members

ASSOCIATE MEMBERS

| | | |
|------|------|------|
| G3IS | G8KL | G8WC |
| G5UM | G8LY | |

*Founder Member

contacts on frequencies above 50 mc. Full rules are as follows :

(1) Cards should be sent by registered post to the address at the end of these notes. They will be returned in a similar way.

(2) The following count as separate QSL's for the purpose of the Club :

- (i) (a) Card from a station at his fixed home QTH.
- (b) Card from his alternative (/A) QTH.
- (c) Card from his portable (/P) QTH.
- (d) Card from his new home QTH if he moves to a new postal area.

- (e) Card from his new /P location if it is in a different county from his original /P site.
- (ii) Stations worked from your portable or /A QTH may be counted provided they have not already been included in the list of those worked from the normal home QTH.

- (iii) A station worked on more than one frequency band may be counted once for each band, provided separate QSL's are obtained. All bands 50 mc and upwards may be included.

(3) All applications for membership must be accompanied by a signed statement that the applicant has replied 100 per cent. to all QSL's received and will continue to do so. A list of the stations to whom the QSL's refer should also be included.

(4) Operators who have worked more than 100 stations (but who have not the QSL's to prove it) may claim *associate membership* by sending a list of the 100 stations. Full membership will be strictly limited to those who can produce the cards.

(5) The VHF Century Club is open only to members of the Fiveband Club.

Special attention is directed to Rule 3, as many applications have been received in the past without this statement.

Quick Ones

G6MN is staying on five till it goes, and though he has found it deserted recently has at last brought in G2XS for Norfolk, making 150 stations in 35 counties ; on 145 mc, G6MN has worked the only station heard so far—G21Q. . . . G5PY has also found 58 mc a bit quiet recently, so has got himself going on 430 mc, with G2FKZ and G3CU as best DX at about four miles ; G3AHB/A has, however, heard G5PY at about 14 miles, at Hayes. The G5PY Tx is a modified 105 Unit, with 6 watts, a "Q" aerial and an R.1359 receiver. . . . G5BY remarks that as he is busy on a complete reorganisation of his station, he has nothing much to report ; he asks us to mention that he is temporarily out of cards, but everyone due a G5BY card will get one in due course. . . . G3CU, one of the 70-cm. kings, reports a fair amount of activity on the 420 mc band in the London area ; calls he lists are G2FKZ, G2RD, G2RF, G2WS, G3AHB/A, G3CU, G5PY and G6HD, which strikes us as being very satisfactory. Not all have yet worked each other, but most have heard two or three stations ; G2FKZ appears to have the best location, as he is able to work all but G2RF and G2WS. Though G3CU himself is on CC for 70 cm., others are mainly self-excited—a condition which will no doubt right itself as time goes on. Any-

way, so much enthusiasm for the 420 mc band is very encouraging. Further to this, G3AHB/A reports that on January 22 he was heard by G2WS/P (Oxtd) at 24 miles, R5, S5 ; G2WS/P also worked G2FKZ. So the coverage increases—well done !

Packing Up Five

As operations on our 58 mc band, both before the war and since the source from which all amateur VHF activity has sprung in this country, are to cease on March 31, it is proposed to wind up Five Metres with a general survey in the April issue of the *Magazine*.

This means that we shall want to get Five-Metre Counties Worked right up-to-date, as that panel has for so long been not only the measure of individual achievement on 58 mc, but also an indication of the steady collective progress made in VHF working. So please let us have your final claims by the due date in March, and provided nobody works another county after that date, the final panel will appear in April.

In Conclusion

May we again draw your attention to the suggested maximum activity period every evening from 1930 to 2030. Although 144 mc gear can be operated without interference to television a large number of the London area VHF operators are keen viewers and consequently activity in the South falls markedly during TV hours. So Northerners should note that 2030 to 2200 is *not* a good time to look for Southern DX.

We have also been asked by more than one reader to urge all G stations to stay in the HF half of the 144-146 mc band and to leave the LF end for the Continentals. So far we have not heard any G's in the LF portion. Reports for next month should reach us by February 11 addressed E. J. Williams, G2XC, *Short Wave Magazine*, 49 Victoria Street, London, S.W.1. CU on March 2.

DIRECT SUBSCRIBERS

Readers who would like to be sure of the *Magazine* every month by having it delivered by post on publication are invited to become direct subscribers. The cost is 20s. (22s. overseas), post free, for a year of twelve issues. Order to the Circulation Manager, Short Wave Magazine, Ltd., 49 Victoria Street, London, S.W.1.

Another Modulation Monitor

And a Discussion on Depth of Control and Power Levels

By A. B. WRIGHT (G6FW)

UNDER the present congested conditions prevailing in the amateur 'phone bands, the importance of making the fullest possible use of one's carrier is well understood by all telephony operators. But there are many, particularly among the beginners, to whom a simple explanation of the methods of obtaining that magical "hundred per cent." figure may be of some value—and there are others of us, who imagine we are fully modulated, to whom a simple form of modulation percentage checker might be useful.

The original purpose of this article was to describe an easily constructed modulation meter-cum-'phone monitor, but it is felt that a few words on the subject of modulation, besides stressing the value of such an instrument, would be of some help in introducing the subject.

Importance of Full Modulation

All methods of modulation aim at producing the maximum of audible output in the receiver, and this is effected entirely by variation of either the amplitude or the frequency of the transmitted carrier. In this article amplitude modulation alone will be considered since this is the system in common use on our communication bands.

Any full treatment of the theory of amplitude modulation would require a much longer and more detailed article than the present one, and as the average 'phone beginner requires practical advice rather than large doses of theory and mathematics, some knowledge of the principles of modulation will be assumed.

Supposing, then, we have our unmodulated 100-watt carrier. To modulate this carrier to the 100 per cent. level requires the addition of 50 watts of audio to be superimposed upon it. This extra 50 watts is expended in the generation of the two sidebands on either side of the carrier.

Under perfect conditions of modulation the positive and negative excursions of the

This article does more than describe a modulation level indicator which is easy to build and adjust—it will be of the greatest assistance to those who have yet to familiarise themselves with some of the practical problems of modulating the carrier.—Ed.

radiated sidebands will be equal and opposite in amplitude, with the result that the S-meter of a receiver tuned to the signal will show no variation due to modulation. If the S-meter moves up or down to any degree it must be because the positive or negative modulation peaks are excessive.

When the carrier is 100 per cent. modulated, using a sine wave input, the average carrier power is increased by 50 per cent. whilst the *peak* power is increased to four times the carrier power. To modulate the carrier 50 per cent. only 12.5 watts of audio are required (again assuming a sine wave input) but in this case the peak power reaches only 2.3 times the carrier power.

As mentioned earlier, the audible output from the other fellow's receiver depends entirely upon the range of variation in the sideband power and from the figures given above it is clear that a 50 per cent. modulated carrier falls far short of the 100 per cent. modulated carrier in producing the maximum possible amount of audio power in the distant receiver. As a matter of interest, the accompanying table (Table 1), gives a few pertinent facts concerning the comparatively steep falling off in peak carrier power and aerial current for four values of modulation percentage.


Table 1

| Percentage Modulation | Ratio Peak Power To Unmodulated Carrier Power | Percentage Current Increase |
|-----------------------|---|-----------------------------|
| 100 | 4.0 | 22.5 |
| 70 | 2.9 | 11.6 |
| 50 | 2.3 | 6.1 |
| 30 | 1.7 | 2.2 |

It must be stressed that the above figures all assume a sine wave input to the modulator, as represented by a pure audio tone or a whistle. With speech input rather different conditions obtain, as speech waveforms are very peaky and when a transmitter is adjusted for 100 per cent. modulation on speech *peaks* the *average* depth of modulation is in the region of 40-50 per cent. only.

Effects of Over-Modulation

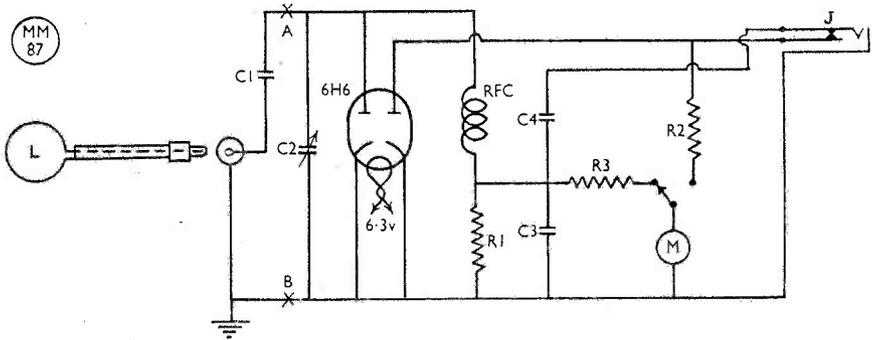The latter statement will make it clear why it becomes so easy to over-modulate on speech inputs, and why some method of



Circuit of G6FW's modulation meter/monitor. It can be calibrated to read modulation depth directly.

modulation monitoring is necessary if such a state of affairs is to be avoided. Much BCI trouble and reports of spurious radiation can be caused by over-modulation, due to high damping of the 'phone signal resulting in induced voltages in nearby aerials, power wiring and so on, an effect which can seldom be cured by the usual wave trap or line filter.

It is a common experience to be given over the air a report of under-modulation when a glance at an oscilloscope shows the signal to be fully modulated or even over-modulated on *speech peaks*. The explanation is, of course, that the station at the receiving end is judging modulation percentage by comparing the *average* speech level with the strength of the carrier. The high speech peaks, which on the oscilloscope are giving evidence of full modulation, contain very little power and simply add nothing to the audible signal—but at the same time they may over-modulate the carrier causing "sideband splash" and even BCI trouble at the transmitter end.

The only remedy for this state of affairs is speech clipping—or cutting-off the high frequency speech peaks—in the speech amplifier or modulator by means of suitable audio filters. It would require more space than is available now to deal fully with this subject, but it would seem to be the only answer to the problem of putting out a carrier which is as fully modulated as possible on speech, while at the same time avoiding over-modulation. Briefly, by cutting off the peaks, the average depth of control can be increased without reaching over-modulation.

Observing Modulation Effects

The whole problem of modulation makes

Table of Values

The Modulation Meter

| | |
|--------|----------------------------------|
| C1, C3 | = 0.001 μ F, mica |
| C2 | = 100 μ F, airspaced trimmer |
| C4 | = 0.1 μ F, paper |
| R1, R2 | = 50,000 ohms |
| R3 | = 150,000 ohms |
| RFC | = 2.5 mH, RF choke |
| J | = Closed circuit jack |
| L | = 1 or 2 turn link |
| M | = 0.1 mA, Milliammeter |

it a virtual necessity to have in the station some means of estimating modulation depth if over-modulation is to be avoided—or conversely, if it is evident from reports that modulation is down.

It will now be clear that one cannot altogether rely on reports received over the air unless the distant station is checking the transmission on an oscilloscope, though the effects of a grossly over-modulated or very under-modulated carrier are evident without actual measurement being necessary.

All the text-books say that when modulating the PA plate meter needle must be stationary, and an upward or downward kick of the needle certainly indicates faulty operation.

A downward kick of the needle can however, indicate poor regulation of the PA plate power supply, especially where the PA and modulator are receiving current from the same power pack. Under these conditions, however, it will usually be found that an RF ammeter in the aerial feeders will kick upwards despite the fact that the PA meter would seem to indicate "downward modulation."

The usual reason for the unsteadiness of the PA plate meter is carrier shift, caused by the carrier power shifting upwards when

the average power in the positive half cycles of the speech wave form exceeds that of the negative half cycles, and *vice versa*. A similar movement can be observed on the receiver S-meter or on the meter of the diode 'phone monitor which it is the main purpose of this article to describe.

Several conditions can cause carrier shift. First, for 100 per cent. modulation the PA must be capable of quadrupling its power output on peaks. Most modern RF valves, if run under the conditions and within the ratings specified by the manufacturers, can be used in a PA with the assurance that a modulation capability of 100 per cent. is possible, provided the following precautions are taken :

The driver valve must be capable of supplying sufficient drive to the PA grid or grids. Lack of drive is perhaps the most common cause of downward carrier shift and should be the first point to be given attention if "downward modulation" becomes evident.

Secondly, the PA must be adequately biased to beyond twice the cut-off value if it is to be run in true Class-C. It is no use decreasing the bias on the PA in an endeavour to increase the grid current, as by doing so the operating conditions are changed and the PA will no longer present a pure resistance to the modulator, as it would do in Class-C—that is, the PA plate current will not vary in direct proportion to the plate voltage when the latter is swung upwards and downwards under modulation. It is also clear that to preserve these conditions the correct load must be applied to the PA by varying the aerial coupling until the PA is drawing the amount of current specified under given values of plate and screen voltages.

Thus, any attempt to increase the PA output by increasing aerial coupling beyond its optimum value will result in improper conditions of modulation, as the downward kick of the PA plate current meter will show.

Visible Indications

Upward carrier shift, as shown by an upward kick of the plate meter or receiver S-meter, can mean over-modulation, but can also be caused by self-oscillation in the PA stage, either parasitic oscillation caused by wrong disposition of the components or wiring, incorrect values of by-pass condensers, or by self-oscillation caused by incomplete neutralisation.

And so, whilst the plate needle will indicate whether or not all is well with our modulation we are still in the dark regarding the actual *depth* of modulation.

In a transmitter described by the writer in the *Short Wave Magazine* (December, 1947, January, 1948) use was made of a lamp link-coupled to the PA tank to indicate modulation, but here again the indication is rough and ready, and the device was incorporated merely to give the operator visible assurance that the PA was being modulated. With practice it does become possible to judge by the relative increase in brilliance of the bulb whether the carrier is being adequately modulated, but that is all.

Then, again, it is possible to estimate modulation depth by noting the increase in aerial current in accordance with the figures given in Table 1. The usual thermocoupled meter is however, heavily damped and sluggish in operation and while a sustained sine wave input (or whistle) to the speech amplifier will produce an increase in the meter reading, it cannot possibly follow the rapid fluctuations produced by speech.

On speech input the increase in aerial current is a measure of modulation percentage only to this extent : No increase indicates very low percentage, a slight increase of from 5 to 10 per cent. indicates a fairly high percentage, while an increase of 15 per cent. is almost certain to mean over-modulation.

The ideal method of checking modulation is by means of a cathode ray oscilloscope, which will give us a picture of the actual carrier under modulation. (See *Short Wave Magazine*, December, 1948). An oscilloscope is the only instrument which will follow faithfully the vagaries of the speech wave form, enabling the operator to see at a glance whether the speech peaks are over-modulating the carrier. The actual modulation percentage can also be estimated with some degree of accuracy by connecting the oscilloscope so as to present the familiar trapezoid pattern when the carrier is being modulated, and then comparing the lengths of the vertical sides of the trapezoid pattern.

But again, unless the source of modulation is a sine wave (which it never is on speech !) the shape of the trapezoid will be constantly changing and it is difficult to measure the actual percentage of modulation when speech input is being used.

Simple Modulation Meter

The writer has for some time employed a very simple form of modulation meter which does not require the use of an oscilloscope, apart from the initial calibration of the instrument, and yet enables the

operator to form a fairly accurate estimation of the depth of modulation.

The circuit of the instrument is given in Fig. 1, being the basis of most modulation monitor circuits and having no claim to originality. It enables the operator to check modulation percentage with a fair degree of accuracy on sine wave input, and whilst it will naturally not follow the peaks of speech, the *average level of speech modulation* can be read off from the meter, due allowance being made for peaks. The instrument also functions as an excellent 'phone monitor and gives a visible indication of the amount of hum and noise on the carrier.

In effect, the modulation meter consists of a linear AC voltmeter, which compares the average RF carrier voltage with its audio frequency component, one diode of the 6H6 serving as a rectifier of the carrier RF voltage, the other diode rectifying the audio voltage.

Construction Points

Construction of the meter can take any convenient form, the model used at the writer's station being mounted on a narrow panel in the transmitter rack, the actual meter components being totally enclosed in a screened aluminium box, with the 6H6 mounted centrally on a vertical metal strip.

The actual disposition of the components is not critical so long as the audio side is kept well clear of the RF components.

Voltage is picked up by a 2-turn insulated link placed a few inches from the PA tank and fed into the modulation indicator *via* a length of 72-ohm coax cable terminating in a coax-plug which engages with a socket in the rear of the box.

With the carrier on and the meter switched in series with R3 the needle will be deflected to an extent dependent upon the proximity of the link to the PA tank coil.

Variable condenser C2 should now be adjusted to balance out the reactance of the transmission line, and should be tuned for maximum deflection of the meter. The coupling of the link to the PA tank coil should now be adjusted so that the meter reads, say, 0.8 mA,

in an 0-1 mA instrument, although the setting is purely arbitrary and may be adjusted to any convenient figure. The meter is now reading the average carrier voltage.

Switching the meter in series with R2 will return the needle to zero unless there is hum or noise on the carrier, when the meter will be deflected accordingly. A sustained whistle into the microphone will send the meter needle upwards to an extent depending upon the depth of modulation and if the carrier is being modulated 100 per cent. the needle will go to the point of the original setting—in the example just given, 0.8 mA. Modulation percentages of less than 100 per cent. will result in correspondingly lower readings, whilst any deflection beyond the carrier level figure indicates over-modulation. The meter reading is linear and modulation percentages may thus be read off directly from the meter.

In this connection it would probably be more convenient to set the carrier level figure at precisely 1 mA when the percentages can be read off with greater ease, although in this case little allowance is made for over-modulation indication. Plugging a pair of headphones into the jack enables the quality of the transmission to be monitored, although under these conditions the meter reading is meaningless.

The meter could, of course, be mounted in a box separate from the transmitter, and a coil and condenser connected between



This happy-looking chap is DU1AI, Pampanga, Philippine Islands, with a fine array of gear.

points A and B, when the instrument could be moved around the operating room and even used as a field-strength meter. The AC-fed 6H6 does not however lend itself to mobile operation and the writer prefers to have the modulation meter fitted permanently to the transmitter.

Whilst crystals of the 1N34 type can be used in an instrument of this description the writer has been unable to obtain them and cannot give any data for their use in the instrument. The plug-in type ex-radar crystals which are fairly plentiful on the surplus market do not seem to be applicable to this circuit owing to their non-linear rectification, and their low current limitation.

XTAL XCHANGE

Below are this month's offerings; negotiations should be conducted direct and it should also be noted that we can now only accept insertions for crystals within the communication bands, or for 100-1000 kc bars of certified accuracy. Notices should be set out in the form shown here, on a separate slip headed "Xtal Xchange—Free Insertion."

GC2CNC, 8 Havre-des-Pas, Jersey, C.I.

Has QCC octal based 100 kc bar and 3163 kc standard two-pin QCC crystal. Wants QCC types in CW area 3-5 mc band.

G2DDM, 34 Birch Avenue, Romiley, Cheshire.

Has new unused 7075 kc QCC Type P crystal mounted. Wants 7005 or 7008 kc US Signals type.

G3ALA, Oakley Training College, Cheltenham, Glos.

Has 7280 kc crystal, Standard Radio. Wants frequency 7000-7150 kc.

G3AUB, 4 Southcliffe Road, Reddish, Stockport, Cheshire.

Has QCC Type P5 7015 kc crystal. Wants similar type for frequency between 3500 and 3515 kc.

G5KC, 123 Kingsway West, Acomb, York.

Has QCC 3510 kc crystal, with certificate. Wants same make 1753 kc, or nearest.

G6FV, 5 Station Road, Teynham, Nr. Sittingbourne, Kent.

Has standard two-pin crystals 1875, 1890, 3500, 7010, 7040, 7050, 7150, 7210, 7270 and 7300 kc. Wants frequencies 7065-7140 kc, or 14 mc crystals.

SWL, 23 Carnarvon Road, Redland, Bristol, 6.

Has QCC Type P5 7037 kc crystal. Wants 100 kc bar.

For a low power transmitter an 0-500 microammeter may be used instead of the meter specified, when a more sensitive instrument will result. In any case great care should be taken in adjusting the link, both from the personal safety standpoint and to avoid damage to the meter movement, and the transmitter should always be switched off when such adjustments are made.

If the specified component values are adhered to, the modulation meter will be reasonably accurate, but it is advisable to check the instrument by comparison with an oscilloscope, using a sine wave input.

Under usual operating conditions, with speech input an average deflection of 60 to 70 per cent indicates that the carrier is being adequately modulated, and whilst the meter will not of course follow the occasional high energy voice peaks, adjustment of the speech amplifier gain so as to restrict the maximum speech percentages to this sort of figure will ensure that no serious over-modulation takes place, and at the same time the operator can be assured at a glance that his modulation is such that the transmitter is being operated with maximum effectiveness.


TRF 1-V-1 AMATEUR RECEIVER

The current (February) issue of our *Short Wave Listener* carries a full-length constructional article, by J. N. Walker (G5JU), on a modern three-stage TRF receiver, using branded parts throughout. This receiver is specially designed for level performance over the whole short-wave range, employs the latest types of miniature plug-in coils, and incorporates bandspread tuning for easy operation on the amateur frequencies. This is it for anyone who wants an easily built receiver of the simpler type, either for general use or as a stand-by.

★

RECORDED THANKS

At a recent meeting of the Bradford Amateur Radio Society, a talk and demonstration on BSR recording gear was given by G2UY. As several B.A.R.S. members have reason to be very grateful to the Queensland Division of the Wireless Institute of Australia, a record was made expressing their thanks; an opening speech by G3UI, the president, and G6KU preceded messages from some 14 individual members, the disc then being despatched to VK with the good wishes of all concerned.

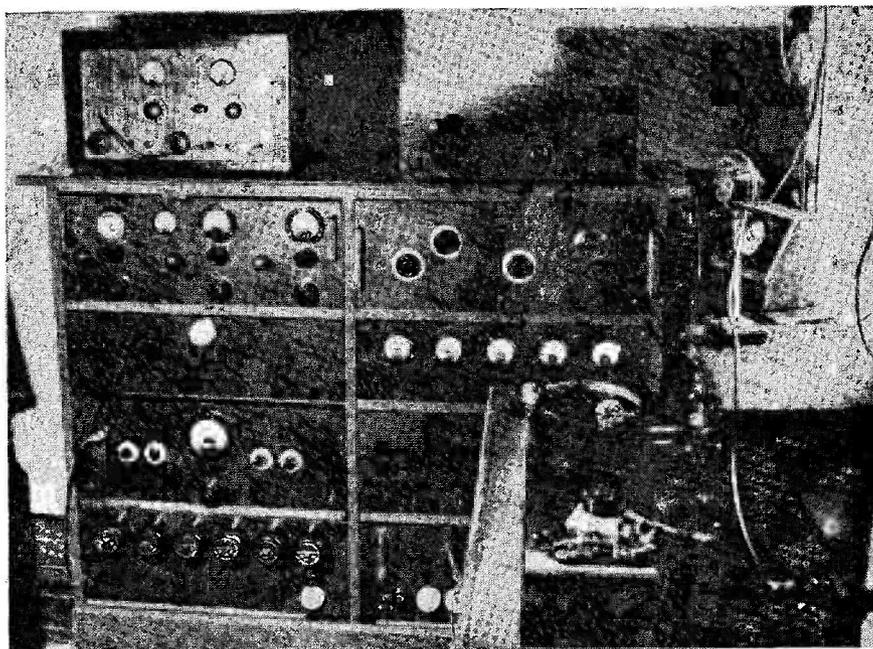

The other man's station G8GI

Here is a view of G8GI, the station owned and operated by C. B. Raithby, School House, Helpringham, Sleaford, Lincs.

The transmitter can be either CC or VFO at will, the general arrangement being Exciter-PA with two RF amplifiers—one on 3.5 mc with an 808, and the other for 7, 14 and 28 mc using a 35T. With crystal control, a separate CO-Buffer unit with its own stabilised power pack is employed; the VFO unit is also separately powered and consists of a 1.7 mc Hartley oscillator, untuned buffer and doubler.

Output from either of these self-contained units is fed to the exciter, arranged to give drive on any band 3.5-28 mc with the PA to be used. Level input of about 100 watts can be obtained to the PA on all bands; for telephony transmission, a speech amplifier-modulator ending in a pair of TZ40's gives full control of the carrier.

For CW operation, keying can be accomplished in several ways, including remote control *via* relays. Station monitoring facilities include an oscilloscope, and frequency checking equipment is also available. To round off the transmitting side, a small "CW-only" Tx is installed for operation on the 1.7 mc band.

Receivers are an S11X for the lower frequency bands, a converter for 14 and 28 mc, and a Type 26 unit for 58 mc reception. The aerial at present in use is a 330-ft. long-wire, about 36-ft. high, Zepp fed on all bands through a 600-ohm line 66-ft. long—though the roof length is incorrect for 3.5 mc working. Bands mainly operated are 1.7, 3.5, 7 and 28 mc, on which G8GI can be heard on both CW and telephony. His layout is neat, and the units shown in this photograph are grouped in such a way that they interconnect conveniently.

NEW QTH's

This space is available for the publication of the addresses of all holders of new call signs, or changes of address of transmitters already licensed. All addresses published here are automatically included in the quarterly issue of the Call Book in preparation. QTH's are inserted as they are received, up to the limit of the space allowance. Please write clearly and address on a separate slip to QTH Section.

- G2AOL W. S. Hall, 49 Sidney Gardens, Otford, Kent.
- G2BAA W. H. Forshaw, 202 Thicknesse Avenue, Beech Hill, Wigan, Lancs.
- G2BAT D. H. Phillips, Falbay Guest House, Clare Terrace, Falmouth, Cornwall.
- G2BND F. L. H. Jones, 16 Gayhurst Road, Dalston, London, E.8.
- G2FIP J. E. Kirk, 24 Marsham Road, Kings Heath, Birmingham, 14.
- G2HLM P. Weaver, 10 Roselyn, Harlescott, Shrewsbury, Shropshire.
- G3AHR A. R. Thomson, 63 Chestnut Avenue, Oswestry, Shropshire.
- GW3BRI S. D. Jones, 75 Manor Road, Abersychan, Pontypool, Mon. (Tel: Talywain 291.)
- G3CBW/A H. Walker, 92 Nelson Street, South Bank, Middlesbrough, Yorks.
- GM3CIG J. E. Priddy, 38 Selvaige Street, Rosyth, Fife, Scotland.
- G3CMB/A A. D. Stears, G.P.O. Hostel, Oswestry, Shropshire.
- G3CZU Dorking & District Radio Society, 5 London Road, Dorking, Surrey.
- G3DBE H. J. Goodyear, 2/35 Grove Lane, Handsworth, Birmingham, 21.
- G3DFV F. N. Fovargue, 30 Hare Street, Grimsby, Lincs.
- G3DGJ W. A. Sparks, 36a Lovely Lane, Warrington, Lancs.
- G3DJC Capt. I. W. Peck, 1 Dean Park Villas, Plymstock, S. Devon. (Tel: 3218).
- G3DJE G. Ehunley, 4 Barnstable Mansions, Rosebery Avenue, London, E.C.1.
- G3DLL A. Eades, 5 Ash Avenue, Runcorn Road, Birmingham, 12.
- G3DMY F. W. Leatt, Haldon, 49 Rivermead Road, Exeter, Devon.
- G3DNO A. E. Machin, 4 Westwick Road, Sheffield, 8.
- G3EBA D. R. Wilde, 21 Great Croft, Cromer Street Estate, Kings Cross, London, W.C.1.
- G3EBF J. C. Perry, 51 Nimrod Road, Streatham, London, S.W.16.
- GM3ECI F/Sgt. D. W. McKay (ex-D3HD), Transmitter Site, R.A.F. Leuchars, Fife, Scotland.
- G3ECP J. & T. Brown, Flat 8, Ambervale, Ashover, Chesterfield.
- G3ECW A. E. Prentice, 14 Queen Mary Avenue, East Tilbury, Essex.
- G3ECY H. T. Hamer, The Orchard, Down Road, Portishead, Somerset.
- GW3EEX D. G. John, 154 Old Road, Neath, Glam.
- G3EFG R. C. Smith (ex-VK3YQ), 55 Kelvin Avenue, Palmers Green, London, N.13.
- G3EHG R. V. Jordan, Ravensdale, 70 Westbourne Road, Wolverhampton.
- G3EHR C. T. Bown, 55 North Street, Atherstone, Warks.
- G3EHV F. R. Tipping, 90 Westenra Avenue, Overpool, Ellesmere Port, Cheshire.
- G3EJR J. B. Armstrong, 1 Hartley Street, Wolverhampton, Staffs.
- G3EKM A. W. Tonkyn, Trewindie, Tregurra Lanc, Truro, Cornwall.
- G3ELU C. R. Robbins, 23 Innis Road, Earlsdon, Coventry, Warks.
- G3EMI M. P. Hopkins, 54 Norman Road, Northfield, Birmingham, 31.
- GC3EML J. Watson, Noirmont, Grouville, Jersey, Channel Islands.
- G3END K. Callow, 40 Elkesley Road, Welbeck Colliery, Mansfield, Notts.
- G3ENR J. F. G. Hucklebridge, 146 Richmond Road, Montpellier, Bristol, 6.
- G3EOS A. H. Greasley, Jennifer Cottage, Herongate, Rickmansworth, Herts.
- G3EPG M. N. Fletcher, Butler's Hill, Cheadle, Stoke-on-Trent, Staffs.
- G3EPI J. K. Bond, 23 Harding Street, Londonderry, Northern Ireland.
- G3EPJ A. S. Bendell, Merry Meadow, Dunster, Somerset.
- G3EPO K. I. Procter, 2 Mill Road, Hertford, Herts.
- G3EPZ R. G. Brown, 61 Debdon Gardens, Heaton, Newcastle-upon-Tyne, 6.
- GM3EQD J. K. Weir, c/o Cunningham, 23 Windsor Terrace, Glasgow, N.W.
- G3EQE J. H. Wess, 47 Barnhey Crescent, Meols, Hoylake, Cheshire.
- G3EQM J. A. Theobald, 66 Nelgarde Road, Catford, London, S.E.6.
- G3EQP A. F. D. Giddy, 99 Greenham Road, Muswell Hill, London, N.10.
- G3EQU J. E. A. Mortimer, 71 The Fairway, N. Wembley, Middlesex.
- G3EQX J. L. Rowe, Farmhill, Southchurch Boulevard, Southend-on-Sea, Essex.
- GM3EQY D. A. E. Samson, 56 Elm Row, Edinburgh 7, Scotland.
- G3ERA J. Wood, 37 Laines Road, Steyning, Sussex.
- G3ERB L. N. Goldsford, Evesleigh, 246 Chester Road, Whitby, Wirral, Cheshire.
- G4HT E. Preston, D.Sc., Ph.D., F.R.I.C., F.Inst.P., 8 Montpellier Court, Montpellier Road, Ealing, London, W.5.
- G4MM J. M. Miller, 81 Tolhill Road, Loughborough, Leics.
- GW5SA D. Price-Jones, Darran Court, Neath, Glamorgan.
- GM6RV/A W. B. Sirling, Rusken, Seamill, West Kilbride, Ayrshire, Scotland.

CHANGE OF ADDRESS

- G2HIF C. Sharpe, 12 Rossett Park Road, Harrogate, Yorks.
- G3AHF W. Howarth, 2 Mervyn Road, Owlley Wood, Weaverham, Cheshire.
- G3BA T. P. Douglas, M.B.E., 18 New Street, Daventry, Northants.
- G3CBW H. Walker, 64 Ayresome Street, Middlesbrough, Yorks.
- G3CZN Maj. A. G. Acland, R.A., Markham House, Badminton, Glos.
- G3CZN/A Maj. A. G. Acland, R.A., Lammacks, Braydon, Swindon, Wilts.
- G3DNT B. N. Gregory (ex-D2AQ), 2 Pinfold Estate, Tideswell, Buxton, Derbyshire.
- G3DRS N. H. Brown, 13 Corporation Road, Audenshaw, Manchester.
- GM3DXJ T. Holbert, 5 Society Street, Maybole, Ayrshire, Scotland.
- GM3PB A. Herring, 81 Arrowsmith Avenue, Glasgow, W.3.
- G4HI W. Smith, 15 Sharpsham Avenue, Skipton-in-Craven, Yorks.
- G5AM C. P. Cowell, 5 Holywell Cottage, Bishops Hill, Ipswich, Suffolk.
- G5GG L. G. Young, 63 Paddington Grove, Bournemouth, Hants.
- G6AD N. Kellett, 91 Kings Road, Melton Mowbray, Leics.

Here and There

Index Vol. VI

The next issue of the *Short Wave Magazine* commences Vol. VII, and will contain as a loose insert a complete Index to Vol. VI, the twelve issues to date.

At about this time, we are frequently asked if we can supply bound volumes of the *Magazine*, or undertake the binding of readers' own sets. Regretfully, the answer is "No"—not at a reasonable price, anyway. Our advice is always to get any such binding done locally, as it is usually both quicker and cheaper!

Callsign Changes

The turn of the year brings into force a certain number of country-prefix changes, some of which will affect amateur operators—see "DX Commentary" in this issue. By the official Allocation List, some of the Russian sequences look as if they might alter; others affected are Hungary, Norway, Lebanon, China, Denmark, Chile, French and Portuguese Colonies, Venezuela and a cluster of British Colonies. In some of these cases, there is no actual need for a change, so that a listing now would only be misleading—but it is quite likely that some unexpected prefixes will be heard from genuine DX locations. As they are unearthed, we shall notify them.

And just as this was being tapped out, a new one came in! Amateurs in the American Zone of Germany are now using a two-letter suffix instead of three, e.g. D4AKW prior to January 15, becomes DL4KW—and, remember, the DL2-DL4-DL5 indicators are Allied Forces and not German national callsigns.

Radiovision's "Hambander"

This has been a popular amateur-band receiver in the lower-priced category for a long time now; as we know, a large number are in use both by transmitters and SWL's. The latest on the "Hambander" is that the price has just been reduced to £17/10s. nett, and at this figure it is indeed very good value for money.

Photographs

We are always glad to see photographs of Amateur Radio interest—either equip-

ment, stations or personalities. Any that are used are paid for, and can be returned if specially required; the block-making process involves no damage to the face of the print.

All photographs should be clearly identified on the back, and though they can be any size, *must* be clear and sharp. It ought also to be mentioned that on occasion we have to hold prints for some time before they actually appear—so if we already have one of yours, don't feel you must write in to know if it has been lost!

Maps and Manuals

We can still supply the *DX Zone Map* (for wall mounting, price 6s. post free) and the *DX Operating Manual*, 2s. 8d. Together, they tell you all you need to know about DX operating in all its aspects, how the Zone areas are arranged, the country prefixes in each Zone, and much else of vital interest and importance to anyone in the slightest degree active in the DX field. Order on the Circulation Manager, Short Wave Magazine, Ltd., 49 Victoria Street, London, S.W.1.

Readers' Half-Guinea Ideas

As mentioned on p.818 of our January issue, we shall be happy to disburse 10s. 6d. a time for short hints, tips, kinks or wheezes with a touch of originality; if a sketch helps the story, which should be short and to the point, include one. Whether we shall be able to run this feature regularly, or even to start it, depends upon the material sent in—we want this to be a readers' feature exclusively.

ZB3 Correction

The article on the ZB3 converter in our December issue contained two minor errors, both of which would be obvious to anyone undertaking the conversion. The left-hand heater pin of V101 must be earthed; and under "Mixer Conversion," R110 is not actually removed, but disconnected from the anode of V103 and taken to the IFT, as directed later in the text. G3BJB also remarks that of course a stabilised power supply should be provided for the unit.

C Q M C C

THE MAGAZINE TOP-BAND CLUB CONTEST

THE 1948 *Magazine*

Club Contest was undoubtedly the most successful of the series; not only from the point of view of the number of entries, although that is a good sign, but also on account of the great keenness and competitive spirit shown.

For the Contest a total of 39 entries was received; and, of these, 28 Clubs sent in their final logs.

Here is the result :

- 1st : Rhigos and District Radio Club, GW3FFE (2275).
 2nd : Coventry Amateur Radio Society, G3FAB (1981).
 3rd : Wirral Amateur Radio Society, G2AMV (1880).

These scores are considerably higher than last year's, chiefly on account of generally increased activity on the band. All credit to the winners, nevertheless, for rounding up so many of the available stations.

Rhigos worked with three operators (GW3ZV, GW2UL and GW3CDP) and they were having trouble with the gear for the first five days, with the result that they did not really get going until the Thursday evening. This did not necessarily reduce their score because of the limitation of operating hours.

Coventry, who were first in 1946 and third in 1947, maintained their fine record by filling the gap and scoring a second this time. They had no fewer than eleven operators: G2FTK, 2LU, 2YS, 3BVJ, 3CZS, 3FAB, 4NB, 5GR, 5SK, 5ZX and 6WH.

Wirral ran a station which was operated by G2AMV, assisted by G3AKC, 3AVI, 3BOC, 3DLF, and 8BM—six operators in all.

The Scoring System

About half the Clubs sending in comments suggested that the scoring system was too favourable to "zones" outside G; the other half considered it to be fair enough. Our own opinion is that

DECEMBER

4-12, 1948

it cannot be too far out, from the mere fact that GW and GM stations have *not* romped away with the

top five places! Admittedly, the fact that non-G stations score two points for every contact with a G is a big help to them, but their geographical position is a hindrance. We shall review the system very carefully before next year.

"Zone" Multipliers


Most of the top scorers worked seven zones—G, GC, GI, GW, GM, D2 and OZ. Only one station—G2AMV (Wirral)—managed to work eight, the extra one being GD. No one can deny that geography helped slightly in this case! OK's, ON's and PA's were heard on the band, but were believed to be "sub-harmonics" from the 3.5 mc band or just plain pirates. Only one station—G3CKR/A (Warrington)—worked OK1EM, but as their report was 599 they thought he was a pirate and did not claim the multiplier. By a fortunate chance it makes no difference to their position in the list whether he was genuine or not.

General Comment

One criticism is universal, and inevitable: That stations who were not entrants but called "CQ MCC" just because they heard everyone else doing it caused a lot of confusion. We know it only too well—we had to check all lists very carefully for claims of 3 points where they were not justified—and some of the scores have unfortunately been pared down by as many as 300 points for this reason. On the other hand many Clubs did manage to sort things out and avoided making a single excess claim. The general suggestion is that on another occasion a "flash" circular be sent to all Clubs at the very last moment, giving the full list of *bona fide* entrants.

Bouquet from the Judges

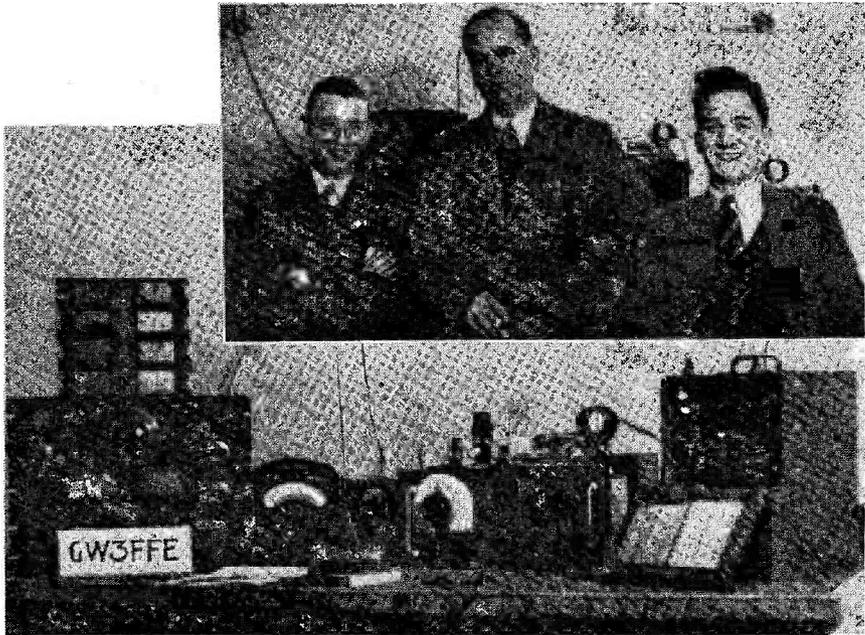A special word of thanks for the neatest logs goes to Coventry, Beaumanor, Edgware and Derby. The latter's log (not



Rhigos were the winners of our Third Annual 1.7 mc Club Transmitting Contest, with the remarkable score of 2,275 points. Several operators helped to man the station, and between them put up a magnificent performance.

typed) was as easy to check as any of those that were, and was quite a beautiful piece of work.

Comments and Criticisms

Again we have to thank most of the entrants for their really helpful and thoughtful criticisms of the event. In spite of minor grumbles in some cases, all Clubs say that they thoroughly enjoyed it and that they are just bursting to get after each other again. Fifteen clubs say that the general standard of operating was "excellent"; two say it was "above average" but one (Rhigos, the winner!) says it was "very low"!

Local phone stations come in for a slating by many Clubs, and one or two such stations, on being asked to be tolerant, merely replied "Here not MCC so nothing to do with us." This, of course, they were fully entitled to say—but fortunately we don't *all* insist on our "rights" all the time. West Somerset says that local phones were heard complaining about the CW QRM—a good sign of the activity on the band. Spen Valley, on the other hand, suspects some of the local phones of not being able to read code.

Ten clubs say that the scoring system kept up the excitement right until the bitter end; in fact Wirral was still "in the queue" for an OZ with only half an hour to go. Eight clubs counter this opinion by saying that it became very tedious towards the end. Rhigos says all credit should be given to the many non-entrants who came on specially for the fun of the contest; Southend says it is a pity that so many stations come on the band *only* for contests.

Coventry suggests, for the future, a closure at 2300 for the benefit of operators who have a strenuous day's work in front of them.

Burton worked with only one operator—G2DAN; Morley was operated only by G3ABG, and not at all on the 8th or 9th. North Angus had only one operator (GM6RI) and no mains, the whole equipment being battery-vibrator supplied.

Garats Hay remark that it was their first contest and that the last day was the most exciting of all. Kirkcaldy was "short of ops"!

Only one topic remains—our old friend "conditions"—but as roughly half

ANALYSIS TABLE

| CLUB | CALL-SIGN | MULTIPLIER | TOTAL |
|------------------------------|-----------|------------|-------|
| 1. Rhigos | GW3FFE | 7 | 2,275 |
| 2. Coventry | G3FAB | 7 | 1,981 |
| 3. Wirral | G2AMV | 8 | 1,880 |
| 4. Neath and Port Talbot .. | GW3EOP | 6 | 1,812 |
| 5. Edgware | G3ASR/A | 7 | 1,771 |
| 6. Derby | G3ERD/P | 7 | 1,596 |
| 7. Garats Hay | G3CHR | 7 | 1,589 |
| 8. North Angus | GM6RI | 6 | 1,554 |
| 9. Grafton | G3AFT | 7 | 1,456 |
| 10. Beaumanor | G3BMR | 7 | 1,449 |
| 11. Warrington | G3CKR/A | 7 | 1,260 |
| 12. Morley | G3ABG/A | 6 | 1,242 |
| 13. Burton on Trent | G2DAN | 7 | 1,218 |
| 14. West Kent | G4IB | 6 | 1,056 |
| 15. { Harrow | G3EFX/P | 6 | } 972 |
| { Baldock | G3EAJ | 6 | |
| 17. Petersfield | G3DDM | 6 | 810 |
| 18. Scarborough | G8KU | 5 | 800 |
| 19. Mansfield | G2DTQ | 6 | 786 |
| 20. Stroud | G2FRG | 5 | 735 |
| 21. Grays | G3DLC | 5 | 730 |
| 22. West Somerset | G3SB | 5 | 665 |
| 23. Southend | G3AXN | 4 | 656 |
| 24. Bovingdon | G3DGS | 4 | 524 |
| 25. Wanstead and Woodford .. | G3BRX | 4 | 436 |
| 26. Nottingham | G3EKW | 3 | 402 |
| 27. Spen Valley | G2CSJ | 3 | 342 |
| 28. Kirkcaldy | GM3CVL | 3 | 261 |

the entrants say that they were exceedingly good and the others say they were very poor we don't propose to comment! Maybe the fact that so many have not had much experience of the band has something to do with it. Judging from the scores we should say that conditions were above average; but even that is difficult to judge because of the greatly increased occupancy of the band.

Apart from giving the entrants a thrill and an enjoyable week, we hope this Contest has served one other purpose—to prove that 1.7 mc is the ideal Club Band. If all Clubs would do something about running top-band schedules with others, some very useful co-operation should result.


Finally, from your Club Secretary, many thanks for the splendid support. And now don't go off the band until next December, but start getting some really red-hot ideas together!

EDITORIAL NOTE :—We must apologise to those Clubs sending in the usual report for this issue for having to drop "Month with the Clubs" this time. No doubt because of their Contest participation, few Clubs have actually reported routine activity, and it was therefore decided to devote the space to a fuller account of the Contest than has been possible in previous years.

Date for next "Month with the Clubs"
Report : February 9.



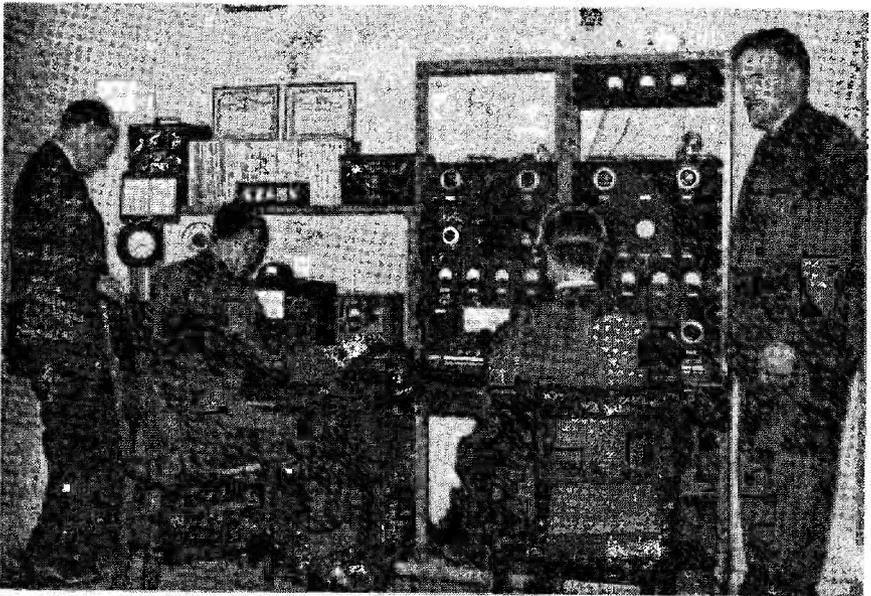Coventry were again placed in the Third MCC, and were close runners-up to Rhigos. The station was operated under call G3FAB.



The Wirral boys did very well to gain third place in MCC, remotely located as they are. Six operators took turns on G2AMV ; in the picture are, l. to r., G8BM, G3DLF, G2AMV and G3BOC. The other two were G3AVI and GK3AC, who unfortunately were unable to be there when this was taken.

MORE S-POINTS PER WATT
with a G.S.V. Beam

Constructed throughout in the new non-corrodible Manganese-Aluminium castings and tubing developed by G.E.C., we can supply any type of beam to your own specification.

STANDARD BEAMS (Approx., 10 days deliver)

- BT328 28 mc. 3-Element T-match £3/15/6
 - BD328 28 mc. 3-Element Delta-match £3/7/6
 - BFD328 28 mc. 3-Element Folded Dipole £3/10/-
 - BD214 14 mc. 2-Element 8JK Delta-match £8/17/6
 - BFD444 145 mc. 4-Element Folded Dipole £2/15/-
 - BFD344 145 mc. 3-Element Folded Dipole £2/5/-
- All above complete with booms and provision for 1" or 2" Drive-rod.

BGP544 145 mc. Ground-plane Vertical £2
TVGB Television Ground-plane Birmingham Area or TVGL Television, Ground-plane, London Area, £1/9/-.

TVRB Television, Folded Dipole and Reflector, Birmingham or TVRL Television, Folded Dipole and Reflector, London, £3/10/-.

Aerial construction for business radio projects, etc., quoted for on special basis.

For Release Soon, 35-ft. sectional triangular pyramid pylons, in manganese aluminium. In kit form, extra 5 ft. sections can be added at any time. Base approx. 1/5 height, top 1 ft. triangle.

BLACK CRACKLE PANELS, 19 x 8 3/4" 5/-; 19 x 10 1/2" 5/3.

CALL-SIGN PLATES, 6 1/2 x 2", die-cast in white bronze; raised polished letters on black ground, 6/6, plus postage.

G.S.V. CO.,

142 Westmount Road, S.E.9
ELT. 6050

SHORT WAVE (HULL) RADIO

G5GX

RECEIVERS

- Eddystone 640 £27/10/-
- R.M.E. 69 £22/10/-
- A.R.77 £25
- B.2 with power pack £9
- H.R.O. Senior. Cabinet Model, 1-7-30 mc/s., with power pack £30

SECTIONAL METAL MASTS

33', in canvas bag, complete with guys, pickets, etc. £2/5/-
(Carriage 5/-)

VARIABLE CONDENSERS — CERAMIC INSULATION

- 250 mmf. 6/6
- 120 mmf. 6/-
- 100 mmf. 4/-
- 60 mmf. 3/9
- 40 mmf. 2/9
- 15 mmf. 2/4

Write for details of our new H.P. Terms

SHORT WAVE (HULL) RADIO

30/32 Prince's Avenue, HULL
Telephone : 7168



18 TOTTENHAM COURT RD., LONDON, W.1. Phone : MUSEum 2453, 4539

SHOP HOURS : MONDAYS—FRIDAYS 9—5.30. SATURDAYS 9—1

The following items are extracted from our complete "TELEVISOR" list, which is now available. Please send stamped addressed envelope for copy. In addition, demonstration models of the completed units are now on display for the guidance of constructors. Come and see it working.

| | |
|---|---------|
| METAL WORK (Please note reduced prices) | £ s. d. |
| Complete chassis work of Vision Receiver in tin plate, drilled, etc., to original specification | 1 9 0 |
| As above for Sound Receiver | 1 5 0 |
| As above Sync. Separator and Time Bases steel chassis, black finish | 13 6 |
| As above Power Pack and Sound Stage, steel chassis, black finish | 17 6 |

| | |
|---|-------|
| TRANSFORMERS AND CHOKES | |
| Mains Transformers—STEWART 350-0-350v 250mA, 6-3v 6A, 4v 8A, 0-2-6-3v 2A, 4v 3A | 5 5 0 |
| EHT Transformer, SCANCO TELEVISION Type ST7, 4,000v 10mA Max., 4v and 3v 2A | 2 8 0 |
| Smoothing Choke, EH 250mA, Stewart type | 1 5 9 |
| Choke 10H 80mA, Stewart type | 13 6 |

| | |
|---|--------|
| SCANNING EQUIPMENT | |
| Set Scanning Coils SCANCO TELEVISION Type ST | 1 5 6 |
| Focus Coil SCANCO TELEVISION Type ST8 | 1 10 0 |
| (Max. D.C. 40mA. Suitable for 9" or 12" CRT) | |
| Line Output Transformer, SCANCO TELEVISION Type ST8 | 1 5 6 |
| (Ratio 4-5:1. Max. D.C. 75mA on primary) | |

| | |
|--|------|
| MISCELLANEOUS | |
| Complete set of Coils and Chokes, wound to specification, for ELECTRONIC ENGINEERING Televisor. All boxed and labelled | 15 0 |
| Aladdin Formers and Cores | 10 |
| Colvour wire-wound Potentiometers, 100K | 6 8 |
| All other values | 5 6 |
| Erie Resistors, as specified, 1 or 2 watt rating | 4 |

In addition, we can offer the full range of TCC Condensers, Belling & Lee components and sundry items to complete the job.

| | |
|---|-------|
| Separate single-winding Televisor Coils | s. d. |
| Separate double-winding Televisor Coils | 1 6 |
| Rubber Masks for CRT's 9" black | 2 0 |
| 9" stone | 9 6 |
| 12" black | 11 3 |
| 12" stone | 13 0 |
| 21" stone | 21 6 |

Special offer of SURPLUS Valves
All tested and fully guaranteed. Postage and special packing, 9d. per valve and 2d. for each additional valve.

| | | | |
|----------|--|-------|------|
| EF50 | R.F. Pentode | s. d. | 6 0 |
| | (Or special offer of 10 for 50/-) | | |
| EA50 | 6-3v Diode | | 4 0 |
| D1 | 4v Diode | | 3 6 |
| 68L7 | Twin Triode | | 9 6 |
| 68N7 | Twin Triode | | 9 6 |
| VR105/30 | Stabiliser | | 7 6 |
| 68K7 | Variable mu | | 6 6 |
| 6HG | Double Diode | | 2 6 |
| 68H7 | R.F. Pentode | | 4 6 |
| KT44 | Tel. Pentode | | 7 6 |
| 6B4 | Output Triode | | 3 8 |
| 6J5 | General-purpose Triode | | 4 6 |
| DET20 | VHF Triode | | 3 6 |
| 1L4 | 1-4 v R.F. Pentode | | 7 6 |
| 6AC7 | Televisor Pentode | | 6 0 |
| 6P61 | R.F. Pentode | | 3 0 |
| 2X2 | H.V. Rectifier 4-5 KV 7-5mA, 2-5v 1-5A heater | | 7 6 |
| 35T | Transmitting Triode 70 watt dissipation 5v 4A Heater | | 35 0 |

FULL MAIL ORDER FACILITIES

Please add postage



CONSISTENTLY
Accurate

PULLIN 'S' METER

The Pullin S Meter has been designed for use on amateur band communication receivers. The meter is mounted in a bench stand with terminals on top. Two scales are printed on the dial, thus serving as a dual purpose meter.

An instructional leaflet is supplied with each meter. This gives the user full instructions for wiring up and explains in detail the value of the resistors and potentiometer to be used in the circuit.

Price, £ 3 . 6 . 0.



Address all Enquiries to

We can give early deliveries — write for full details —

MEASURING INSTRUMENTS (PULLIN) LTD.

Dept. K. Electrin Works, Winchester St., London, W.3. Phone ACOrn 4651/4

Auto Transformers. 3" cube plus terminals 230v A.C. Input, 115v Output. 80 watt Shrouded, 6/- each.

Transformers 200-0-200 80 mA 6·3v 3 amps, 5v 2 amps, Input 230v A.C. 12/6 each.

A.C./D.C. Voltmeters 0-300v 2½" panel mounting. Brand new and boxed 12/6

Chokes. 20 Henries, 100 mills. 4/6.

A real first class inter-valve 6V6 push-pull transformer 7/6.

Variable Condensers. 50 Pfs Ceramic Midget 1/6 each.

Valves VR92 Diode 6·3 EB34, 3/-; EF50, 6J5, P61, 4/6; EBC33, EF36, EF39, 6SN7, 5/6; 6V6G, 6SK7, 6SJ7, 5U4, SP4, EK32, 7/- All brand new. Please include 4d. postage or proportionate amount for larger orders.

GET THIS CLEARANCE LINE WHILE IT LASTS

TR1196 Receiver Unit containing EBC33, EK32, 2 EF36, 2 EF39: 6-valve Superhet covering 4·3 to 6·7 mc/s. Can easily be converted to any frequency. Contains two 460 kcs Ifs. Brand new at the Bargain price of 25/- plus 2/- carriage.

Our Money Back Guarantee is your Safeguard

FIELD'S

435-437 Stratford Road., Sparkhill,
Birmingham 11

Obtain the **P.M.G.** **CERTIFICATE** with the personal assistance of *E.M.I. Scientists*—

A special correspondence course for those wishing to take the P.M.G. certificate has been planned by E.M.I. Institutes. It brings you tuition under the personal supervision of E.M.I. scientists, several of whom hold the transmitting licence. **DAYTIME ATTENDANCE** and other **CORRESPONDENCE** courses, covering radio, basic television, etc. are also available.

A former student writes—“*I passed the examination without any trouble and should like to thank you for a very fine course*”—R. V. (Carshalton).

Write for details to :—The Principal,
E.M.I. INSTITUTES LIMITED
Dept. 14, 43 Grove Park Road, Chiswick, London
E.M.I. Institutes—backed by the Electronic Organization which includes “H.M.V.”, Marconi-Phone, Columbia, etc.

YOU CAN OWN A TELEVISION RECEIVER!

THE extension of television transmissions to the Provinces is fast becoming a reality. The Midlands will soon benefit by this incomparable home entertainment, and closely following the Birmingham transmitter are others to eventually embrace the United Kingdom.

Since the inception of our "W.D. Televisor", the volume of enquiries, orders and repeat orders has steadily increased in number.

Prospective purchasers for miles around have, in many instances, trekked to our premises at Ruislip to view the finished prototype. Saturday afternoon proves the peak period, and even those originally sceptical of our claims concerning the receiver have registered mixed amazement and pleasure at the clarity of reception — an inherent feature of the "W.D. TELEVISOR."

Its conversion from ex-Government equipment is made comparatively simple by our 7/6 explanatory manual, a profusely illustrated and lucidly expounded data. The modifications involved should therefore present no terrors to a person ordinarily conversant with radio fundamentals.

Featured in the booklet is a detailed price list of necessary items. The three basic units are the Vision Receiver IF Strip, the Radar Indicator and the Merribull Transformer type UT7. These are priced respectively at £2/15/-, £3/15/-. and £5/10/-. If the three units are simultaneously purchased a saving of 10s. is effected, as the charge is then progressively reduced to £11/10/-.

Every component thereafter required is specified, and we are in the happy position of being able to supply immediately from stock. At the outset you are advised to acquire the booklet together with the three equipments noted above; the smaller components necessary may already be in your possession.

May we extend to you an invitation to visit us at Ruislip during viewing hours? You will be instantly impressed and convinced.

CONCLUDING

We close with a warning. The demand is going to be exceptionally heavy. Our Despatch staff will be inundated and orders must be treated in strict rotation. We seek your kind co-operation and request that orders be submitted with the minimum of delay.

There is no need to hesitate. Hundreds of satisfied customers will testify to the efficiency of the "W.D. TELEVISOR", probably the finest post-war apparatus marketed.

QUESTIONS and ANSWERS

Q. What, please, is the size of the picture?

A. Approximately 8" x 4" but this can be proportionately enlarged by a magnifying lens which we can supply at £1 19 6, plus 2/6 delivery. (Smaller, cheaper but less powerful lenses available from 29/6.)

Q. What is the colour of the picture?

A. Most people who have seen a demonstration agree that the green and black picture is no real disadvantage, and in any event there is no reason why a black and white picture tube should not be fitted as soon as these are available from the tube manufacturers.

Q. Why isn't a large black and white tube used?

A. Because the only tube really suitable for television extensively used by the Services is the 5" green and black VOR97. Large black and white tubes were utilised in isolated cases, but it would be hardly practical for us to issue data and specify parts that are unobtainable.

Q. Is the set difficult to construct?

A. There is quite an amount of work involved, but it is emphasised that anyone capable of reading a circuit diagram and possessing basic radio knowledge is competent to undertake the task.

Working in the evenings, it will probably take you about a month to construct your first TV Receiver. Subsequent models, however, could be made within a much shorter period. (Constructors can be put in touch with one another with view to mutual help.)

Q. Is the Circuit superhet or straight?

A. Straight receivers are used for both sound and vision reception.

Q. What is the total cost?

A. The total cost is just under £18 but—

SHOULD YOU SO DESIRE. THE GOODS CAN BE SUPPLIED ON FAVOURABLE H.P. TERMS. SEND US 25% OF THE TOTAL PLUS CARRIAGE. THE BALANCE, INCLUDING A NOMINAL INTEREST, CAN BE EXTENDED OVER TWELVE MONTHS!

Q. Is a special aerial necessary?

A. Yes, as with all televisors a specially designed aerial should be used to give best pictures. This need not be expensive, we can supply one at 15/-, plus 1/- postage. This would be suitable for mounting in the loft or the bedroom.

Q. Will the set operate outside the normal T.V. area?

A. Assuredly. Within limits, it has come to our notice that our set functions where commercial models fail. Please bear in mind, however, that perfect results cannot be expected in these weak areas and the addition of a pre-amplifier (we can supply details of a suitable circuit, 2/3) is recommended for areas over 50 miles from Alexandra Palace.

Q. Can all the parts be replaced?

A. Yes, indeed, all parts are standard—even the Cathode Ray Tube. We expect always to be able to provide spare parts at reasonable prices.

Q. Can any other questions be answered?

A. OUR 7/6 INFORMATION CONTAINS 26 FOOLSCAP PAGES OF DATA INCLUDING 26 WIRING DIAGRAMS AND PHOTOGRAPHS. IT CONTAINS ALL THE DATA THE AVERAGE CONSTRUCTOR REQUIRES. If, however, you are beset by difficulties, more information will be dispensed provided your questions are written on our Query Form, Mark 2. Under no circumstances can queries of a technical nature be answered either by telephone or to callers. Our booklet "50 Pitfalls of T.V. Constructors," price 2/3, is also recommended.

Q. What are the service numbers of the equipment used?

A. The Mark 2 Televisor uses Indicator type 62—Receiver type 194—The Mains Transformer, which is not ex-Government, carries full manufacturers' guarantee. This transformer is the Merribull type UT7.

Q. Is data available covering other units?

A. Yes. Mark 1 data shows how Indicator type 6 and Receiver type 3131 or 3132, or 3170 or 3084 and Merribull Transformer type UT6 could be used. The price of this data is 7/6 post free. If required, please ensure that Mark 1 data is in fact ordered.

Q. One final question; can this Televisor be modified for use in the Birmingham area?

A. The only difference will be due to the frequency of the Birmingham transmission. As this frequency is higher than that used in the London area, the coils used in both Vision and Sound Receivers will require less turns of wire than at present.

W. D. SALES

4 Electron House,
Windmill Hill,
Ruislip Manor, Mdx.

BOOKS. You can order from us practically any publication required. Following titles just arrived : Foundation of Wireless, 7/6. Wireless Servicing Manual, 10/6. Television Rec. Equipment, 12/6. Radio Data Charts, 7/6. Short Wave Radio, 10/6. Radio Anti-interference, 2/6. Valve Application Manual, 5/-. Modern Battery Receivers, 2/6. Inductance Manual, 2/6. Frequency Modulation, 2/6. Communication Receivers, 2/6.



★
VALVES from 5/10 up. Please send for List. You can order C.O.D. any Valve Type—we may have it, even if it is a rare and different type.

★
 Equivalents Charts including Quick Reference Index, 1/8.

★
T U 5 B

You can make a Super V.F.O. from the instructions which the A.R.R.L. League has given permission to reprint from Q.S.T. with the U.S. Signal Corps TUSB Tuning Unit. Price complete with instructions, 22/6, and carriage 3/6.

APN4. Amer. Indicator Unit, suitable for television or a super C.R.O. Contains 26 6-3v midjet valves, 5" C.R.T. 5CP1 also .01 100kc/s crystal and 100 other parts. £5/3/4. Carriage 10/-. returnable packing, 7/6.

TRI196. 6 - Valve Superhet Receiver Unit suitable for conversion to Home or Car Radio. Price with valves, 19/-. Carriage 2/6.

POTENTIOMETERS wire wound 5 ohms, 1,000 ohms, 5,000 ohms, 10,000 ohms,, 20,000 ohms, 25,000 ohms, 2/- each.

14ft. fast (seven section) **AERIALS**, very rigid. Ex-Govt. Bargain. Post 7/6 free.

METERS—all models available, AVO, TAYLOR, etc. Easy terms on Taylor Instruments.

Q-MAX Chassis Cutters, all sizes at 12/6, Keys 1/-.

SOLDER Multicore, 13 SWG 4/10, 16 SWG 5/3.

J. BULL (S) 246 HIGH ST., HARLES DEN N.W.10

HAVE YOU ordered your copy of the 1949 A.R.R.L. RADIO AMATEUR HANDBOOK?

●
We can already see that the demand for the New 1949 Twenty-Sixth Edition of the famous American Radio Amateur Handbook published by the American Radio Relay League will be an all-time record.

●
 Once again the handbook will contain the very latest up-to-date technical and constructional articles dealing with all matters on Ham Radio.

The demand for this **New 700-page** Edition throughout the Amateur world will be exceptionally heavy. Don't be disappointed, get your order in at once to secure delivery from the first printing. Your copy will be posted direct to you from the United States immediately it is published.

IMPORTANT

A.R.R.L. execute all orders in strict rotation. The first printing will soon be exhausted, so don't delay—order now!!!

| | | |
|------------------------|-------------------------|--------------------------|
| 1949 EDITION | READY THIS MONTH | 12/6 POST PAID |
|------------------------|-------------------------|--------------------------|

DALE INTERNATIONAL

Publications Limited
 105 BOLSOVER STREET, LONDON, W.1

ORDER FORM

1949 A.R.R.L. RADIO AMATEUR HANDBOOK

Please arrange for the above publication to be posted direct to me from the U.S.A. immediately it is published. I enclose 12/6

NAME.....

ADDRESS.....

If you would rather not deface your Magazine, then just order by letter

THE RADIO & ELECTRICAL MART (G3BSW) of 253-B PORTOBELLO ROAD, LONDON, W.II

Phone : Park 6026

R.A.F. Type 22. Transmitter receivers, 2-8 mcs. Crystal controlled. This superb 13-valve set, complete with 12v power pack, rnkie and head-phone set, comes to you tested and ready for use in green canvas (with leather corners) holdall carrying case, as new, for bargain price of £15 Add 10/- for wood crate (returnable).

U.S. Signal Corps 15-Watt Amplifiers. Complete except for power pack—contains 2 1619 tubes (better than 6L6's). Price 50/-.

R.A.F. 12v Vibrator Pack with P.P. audio amplifier, complete at the low price of 30/-.

Type BC347. U.S. Signals Interphone Amplifier. 6F8 twin triode in P.P. Case measures $5\frac{1}{2}'' \times 2\frac{1}{2}'' \times 4''$. Excellent mike amplifiers. Price 10/-.

Test Set, Type 46. New battery-operated frequency meters, 2 to 23.5 mcs. Made by Marconi instruments. Can be adapted to all-wave by inclusion of LW and MW coils. 40/- each.

Type T.G. 10-F. U.S. Signals Morse Keyer Unit. This beautifully made 25w amplifier in black crackle finished case, $21'' \times 14'' \times 11''$, also contains a variable speed motor, photo-electric cell, and exciter lamp. Ideal for conversion to sound unit of cine projector. New, £15. Add 10/- for crate (returnable).

Write for lists containing hundreds of items in short supply. Send us your requirements. Remember, money-back guarantee.

Type 2. Valve tester. Contains 5" 0-500 micro-ammeter. Price £3/15/-.

Type 3002. R.A.F. UHF Units, containing 10 valves—easily adaptable for 2-metre use. Price £1. **B.C.453 A or B.** If you own one of these excellent receivers, we can offer you a medium band coil pack which has been designed by Meteor Electronics at our request and is easily mounted. Complete circuit diagrams and coil pack, 17/6. You will be delighted with the results.

2-Metre Oscillator or Signal Generator. Using CV1197 Acorn. Requires only LT 6.3v and 120v HT supply to work. Complete with circuit, 16/6.

Khaki Canvas Parachute Cases. New. Ideal for conversion to school satchels, tool holdalls, shopping bags, brief cases, etc. Price 2/- each.

T.R.1196. These 6v Superhets are the best buy of the day. With circuit 29/6.

Mains Power Supply. Complete Unit in black metal case $9'' \times 6'' \times 6''$. Unit consists of heavy duty transformer—rectifier valve—smoothing choke—condensers—panel light—switch—input and output plugs. Input 200/260v A.C. Output 6.3v at 3.5 amps HT. 350v at 80mA—larger supply available by changing rectifier valve. Price £3/5/-.

RADIOGRAPHIC LTD., of Glasgow

RECEIVER, TYPE 1088A. Designed to key a remote transmitter dispensing with land lines, etc. Tunes from 180-280 KCS. Meter 0-10 M/A tuning indicator. Battery operated from 120v H.T. and 2v L.T. $10'' \times 7'' \times 2''$ with metal cover, less valves. Weight 14 lbs. Price 27/6. Carriage paid.

ADMIRALTY OSCILLATOR UNIT, W6283. Oscillator Section for Admiralty Transmitter type 7AD. Silver-plated lecher line with disc type tuning condensers. Trimming tool is provided. Lechers mounted on Polystyrene. Aerial coupling is by twin coaxial line. Complete 150-200 MCS transmitter ready for operation, brand new. Packed makers' cartons, $11'' \times 6'' \times 3\frac{1}{2}''$. Complete with 2 valves. Type CV63. 25/- Carriage paid.

EX-R.A.F. DESK MICROPHONES. Single button carbon desk microphone with P.O. table stand as used by R.A.F. ground stations, complete with 5 ft. heavy screened cable and jack plug. A DEFINITE BARGAIN. 6/8 each.

INDICATOR UNITS, TYPE 198A. Complete with I.C.R.T. Type 138A, $3\frac{1}{2}''$ diam. 4 VR65 (SP61) valves. 1 EA50 valve. 1 VR54 (EB34) valve. $16'' \times 12'' \times 5\frac{1}{2}''$. Can be adapted as a television unit, oscilloscope, etc. Price 37/- Carriage paid.

SLOW MOTION DIAL DRIVE 12913. Slow motion dial and drive with semi-circular scale, 6" at base, 2" broad, with eight scales calibrated from 100 KCS-20-MCS. Dial movement directly driven or through 100 to 1 step down ratio. Precision drive as fitted to various R.A.F. and Navy test equipment. 8/6 each. Carriage paid.

DIPOLE AERIALS, TYPE AN95A. Heavy metal rod, $13\frac{1}{2}''$ long and $\frac{1}{4}''$ dia., screwed at one end, base

of heavy paxolin, 3" dia. and $\frac{1}{4}''$ thick, fitted with coaxial socket and metal plate. Supplied with Polystyrene insulated plug. Aerial rod could be adapted for any frequency, flush fitting, waterproof. Ideal ground plane aerial. Television, V.H.F. or car radio fitting. 4/- each. Carriage paid.

METER INDICATOR UNITS, TYPE I. Two D.C. movements mounted side by side. Windings in series, each have a resistance of 500 ohm. Contained in circular metal case, approx. $3\frac{1}{2}''$ dia. Full scale deflection is 115 microamps. D.F. indicator as fitted to the RI155 receiver. Can be adapted for "S" Meters. Brand new. 7/6 each. Carriage paid.

HAND GENERATORS (Ex-Dinghy transmitters). Complete with handle for manual operation. Output of 6v and 300v D.C. Can be used as mains driven motors on 200-250v A.C. or D.C., wind generators, rotary transformers. 6/10 each. Carriage paid.

TRANSMITTER UNITS. 1-500 K/cps Crystal (accuracy 25%) and a quantity of very useful components, ex-dinghy transmitter units. Wired and mounted on paxolin, base $7\frac{1}{2}'' \times 5\frac{1}{2}''$. 7/6 each. Carriage paid.

OSCILLATOR UNIT, TYPE G44. Lecher line oscillator covering 60 CMS (500 MCS) to 120 CMS (250 MCS). Metal chassis and cabinet, $16\frac{1}{2}'' \times 4'' \times 4\frac{1}{2}''$. Lecher lines calibrated in centimeters. Shorting bar and variable coupling plate. Designed for two RL18's. Could be modified to take acorns, etc. Fitted with modulation transformer. Supplied with each unit is a circuit diagram and graph for converting the lecher reading to wavelength. An ideal UHF transmitter, signal generator, etc. Brand new and unused. Price 15/- each. Carriage paid.

RADIOGRAPHIC LIMITED, 66 OSBORNE STREET, GLASGOW, C.I

Phone: BELL 3776

'Grams : RADGRAPH, GLASGOW

Surplus Bargains

AR88LF—The famous super communications Rx, 30.5 mc/s to 1.485 mc/s; and 550 kc/s to 73 kc/s. 14 Valves, noise limiter, xtal filter, etc. In first-class condition, and completely realigned. A few only at **£30**, plus **£1** carriage.

1147 RECEIVER—Another Super Set. 30 mc/s to 1.5 mc/s, 13 valves (inc. stabiliser), optional amplified A.G.C., 5 tuned RF circuits, built-in speaker, and a performance at least equal to the AR 88. Self-contained for 115v mains, and we supply FREE a 2:1 transformer. Rack mounting. BRAND NEW. Only **£30**, plus **£1** carriage.

TU7, TU10, TU26—The last few of these well-known units, in excellent condition, but without outer cases. 5/-, plus 2/- carriage.

12/24V AC/DC MOTORS—Made by Hoover, as fans, detachable fan and housing. BRAND NEW. 12/6, plus 2/6 carriage.

POWER UNIT, TYPE 4—4 Metal H.T. rectifiers, 38 μ F \times 500 VDC electrolytics, 2 smoothing chokes, 4 \times 1 condensers, vibrator trans-

former, etc. Soiled, but a REAL SNIP at 10/-, plus 3/- carriage.

WAVEMETER G73—A standard signal generator, with its own xtal calibrator. This superb instrument uses a separate unit (fitted inside the case) for crystal calibration purposes. It is complete, with carrier level meter, constant impedance attenuator, 400 cps modulation, and is mains (115/230v) operated, with provision for battery operation for portable work. In grey steel cabinet, with canvas case, calibration book, meter and all valves, but less 1,000 kcs xtal. They are BRAND NEW. Photo on application. **£12/10/-**, plus 10/- carriage.

0/300 VDC Moving Coil meters, brand new, boxed. 5/-.

0/3.5 A—Thermocouple meters—used. 3/6.

0/100 mA (scaled 0/300) m/c meters, used. 3/6. All 9d. carriage.

PHONES—Moving coil, 5/-. Diaphragm, 3/6.

MOVING COIL MIKES, 2/6. Carriage 9d.

RADIO EXCHANGE CO. 9 CAULDWELL ST.,
BEDFORD
Phone : 5568

A. FANTHORPE

6-8 HEPWORTH'S ARCADE, HULL

Tel. : HULL 35694

RECEIVER, TYPE 76. Contains R.F. and F.C. stages covering 150-505 kcs. with EF39, ECH35 and EA50 valves. Tuning by means of a 160 pf 3-gang condenser with 25:1 geared drive, giving 24" of logging scale. Also included are a desynn trimmer with 12v motor, P.O. type relay, 20 resistors, 10 condensers, Yaxley type switch, coils, etc. Ideal for conversion to frequency meter, etc. Complete in metal case, 6 $\frac{1}{2}$ \times 8 $\frac{1}{2}$ \times 10". Brand new, in wooden transit case. 28/6, carriage paid.

MODULATOR, TYPE 76. Contains the I.F. stages, etc., for the receiver type 76, with 3 type EF39, 2 type EF36, 1 type EBC33, 2 type KT33C and one EF50 valves. Motor generator 24v 6 amps input, two outputs of 250v 200 m.a. each. Also 8 fuseholders, 3 P.O. type relays, condensers, resistors, westectors, etc. A Bargain at 47/6. Carriage paid.

TUNING UNIT, TYPE CAY47154A. Covering 6,200-9,050 kcs. V.F.O. section contains variable condenser, air-spaced padder, ceramic switch, and dial 0-800 degrees. P.A. section contains 85 pf condenser with .2" spacing, aerial tuning inductance, 2 ceramic switches, 2 air-spaced padders and 2 ceramic spindle couplers. In metal case 12" \times 9" \times 10". 15/-. Carriage paid.

TUNING UNITS, TYPE T.U.6.B. Covers 3-4.2 mc. Brand New and Boxed. 16/6. Carriage paid T.U.7, 8 and 9, in good condition. 10/-.

TYPE 25 CONVERTERS. Contain 3 SP61, 5-way 3-bank ceramic switch. 15 3-30 pf air-spaced concentric trimmers. 6/6. Post paid.

CONTROL UNITS. For 19 set. Contain three Yaxley type switches. One 3-pole 3-way 2-bank. One 4-pole 2-way 2-bank. One 3-pole 3-way 3-bank. 3 pointer knobs, one red warning light. Brand New and boxed. 5/9. Post paid.

DURAL TUBE. Cut to any length. 1" 20g., 7d. per ft. Max. 10 ft. 2" 20g., 1/- per ft. Max. 11 ft. 2" 17g., 1/3 per ft. Max. 14 ft. All prices carriage paid.

ALUMINIUM SHEET. Cut to your requirements. 22 gauge, 1/4 sq. ft.; 20 gauge, 1/9 sq. ft.; 18 gauge, 2/- sq. ft.; 16 gauge, 3/- sq. ft. All prices carriage paid.

STANDARD RACKS. 6 ft., for 19" panels. Drilled $\frac{1}{2}$ - $\frac{1}{2}$ " I.E.A. Constructed of 3" \times $\frac{1}{2}$ " steel channel, with heavy base plate. 55/-. Carriage paid.

38 A.F.V. XMTR/RCVR. Frequency 7.3-9 mcs. 6 valves. C'omplete with spare valves, 12v vibrator, etc. In two units, power unit and output stage in one, receiver and transmitter in the other. Less junction cable. Brand New and Boxed. 52/6. Carriage paid.

Send 2 $\frac{1}{2}$ d. stamp for list

TELEVISION CONSTRUCTION FROM EX-GOVT. GEAR. We have had a tremendous response for the Constructional Details advertised last month. These show how to modify Radar Units for TV reception, and are supplied gratis with the units, which cost £5/10/-. Alternatively, they will be supplied on receipt of 7/6, which will be allowed against the purchase of the units within 14 days. A combined H.T. and E.H.T. mains transformer is factory built, and costs £5/10/-, but if purchased with the Radar Units the total cost is £11/10/-, showing an additional saving of 10/-. The stocks of units are holding out, but please bear with us if there is few days' delay in delivery. Please add 12/6 carriage, plus 10/- deposit on returnable packing case.

THE A.C. R.1155 RECEIVER. This superb R.A.F. 10-valve superhet communications receiver, covering 75 kcs-18.0 mcs in 5 wavebands, is now available for use on A.C. Mains, and complete with speaker, at ONLY £18/10/-. An illustrated fully descriptive leaflet is available on request.

INDICATOR UNIT 62A. Contains 12 valves, EF50, 2 of EB34, 4 of SP61, 3 of EA50, and 6" tube VCR97, and shoals of condensers, resistors, potentiometers, etc. A marvellous buy for breakdown, or conversion to a super CRO. ONLY 89/6. Carriage 12/6, plus 10/- on case.

INDICATOR UNIT 162B. Contains 6" tube VCR517 and 3" tube VCR139, 3 valves SP61, 4 of EA50, and CV67 Klystron, in addition to the usual mass of small components. ONLY 67/6. Carriage as above.

TEST SET TYPE 74. This is an oscilloscope used by the R.A.F. for VHF work. The time base requires slight alteration for normal use. Has a 3" CRT type VCR139, 3 valves SP61, 1 of 6J5G, 1 of 6Q7, 1 of 5Z4, 1 of SU2150A, 1 of E1148. Has built-in power pack in addition. First come, first served at £5/10/- while they last. A few only available. Carriage and case charge as above.

MAGNIFYING LENS FOR 6" TUBES. Just what is wanted to bring up the size and definition of the TV set using a 6" tube, or of a 'scope. A new manufactured item, not Government surplus. ONLY 29/6, postage 1/6.

C.W.O. Please,

S.A.E. FOR LISTS

U.E.I. CORP,

The Radio Corner, 138 Gray's Inn Road, London, W.C.1

(Phone : TERminus 7937)

Open until 1 p.m. Saturdays, we are 2 mins. from Chancery Lane Station (High Holborn), and 5 mins. from Kings Cross

HAVE YOU

had your **FREE** copy of our 32-page illustrated catalogue? It's about the same size as this magazine, with everything from A to Z, and good illustrations of all the important items.

No surplus gear is listed, all articles mentioned are the current products of the makers concerned, no need to bother what condition they are in, very much different to some of the surplus going about.

We sell a large amount of surplus as well, and issue special lists from time to time, copies of which are sent free to all customers on our regular mailing list. Are **YOU** on it? All orders are **POST FREE**, we're about the only firm that do this, no need to bother with postage, and every order is actually despatched on the same day that we receive it, a real **RETURN OF POST SERVICE**.

Orders large or small are attended to promptly, so if you only want a few resistors, couple of condensers, or a coil, send us your order.

The following are just a few of the things described and illustrated in the catalogue.

Belling-Lee plugs, sockets, fuses, aerial kits, etc.; Danco: the complete range of their well-known products is available; Gardners transformers, chokes, etc., a very wide range stocked; Muirhead National HRO dials; Partridge transformers, chokes and the rest of their range here; Sifam instruments, including full details of their 3½" moving coil, multi-range test set, at a really amazingly low price; All Taylor instruments are here, and we do the H.P. terms for these; Wearite coils, switches, I.F. transformers, etc. Condensers, valves, and hundreds of other things. Send a Post Card now, simply write "Catalogue Please", and your name and address, it's quite easy, and we'll have your copy in the post straight away. If you're wanting anything at the moment, just mention it, and we will send full information.

TORBAY ELECTRIC

43 Colley End Park · Paignton · S. Devon

OPPORTUNITIES IN RADIO



Get this **FREE** Book!

"ENGINEERING OPPORTUNITIES" reveals how *you* can become technically qualified at home for a highly paid key appointment in the vast Radio and Television industry. In 108 pages of intensely interesting matter it includes full details of our up-to-the-minute home study courses in all branches of **RADIO AND TELEVISION**, A.M.Brit.I.R.E., A.M.I.E.E., City and Guilds, Special Television, Servicing, Sound-film Projection, Short Wave, High Frequency and General Wireless Courses.

We definitely guarantee

"NO PASS—NO FEE"

If you're earning less than £10 a week this enlightening book is for *you*. Write for your copy to-day. It will be sent **FREE** and without obligation.

**BRITISH INSTITUTE OF
ENGINEERING TECHNOLOGY**

149 Shakespeare House,
17-19 Stratford Place, London, W.1

"Cyldon"

Type No. 14
1 1/4" long
1 1/8" wide
3/8" high

Type No. 10
1 1/4" long
1 1/8" wide
3/8" high

**MCA-DIELECTRIC
TUNING
CAPACITORS**

SYDNEY S. BIRD & Sons Ltd.
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDLESEX.
Phone: ENfield 2011-2 Telegrams: "Cyldon, ENfield"

FREQUENCY CONTROL

IN ANY OF THESE RANGES

which may be multiplied for VHF
KCS.

- | | | |
|-------------|-------------|--------------|
| 1750-2000 ; | 3500-3800 ; | 6000-6083 ; |
| 6150-6192 ; | 7000-7425 ; | 8000-8111 ; |
| 8207-8526 ; | 9333-9900 ; | 10500-10725, |
- for 32/6 (or 40/- if freq. is specified)

ALSO

14 mcs UNIT

Operating on fundamental mode, to
nearest 10 kcs. From stock at 35/-

direct from

BROOKES CRYSTALS LTD.

10 STOCKWELL STREET,
GREENWICH, LONDON, S.E.10
GRE 1828

ODEON RADIO

STOCKTAKING BARGAINS

We offer below a number of items which have become "shopsoiled" or which have been constructed by us for display purposes or to special order. All are guaranteed in perfect condition electrically, and prices are particularly advantageous, in many cases considerably less than the value of the components.

1,500v 300Ma POWER PACK, rack mounting, using Woden transformers and chokes and 866 rectifiers, complete with valves.

Reduced from £27/10/- to **£15**

750v 250Ma POWER PACK as above.

Reduced from £20 to **£10**

DENCO DR20 Broadcast Receiver, ten wave bands, 550 Kc to 27.2 Mc. Exceptional short-wave performance due to use of special Denco coil turret. Handsome walnut cabinet. Illustrated leaflet sent on request.

Reduced from £37/10/- to **£20**

EDDYSTONE 5 and 10 metre converter as described in Eddystone Short Wave Manual No. 5. Superhet circuit, using EF54's and EC52. Complete with valves and coils for two bands.

Reduced from £12/10/- to **£7/10/-**

MULLARD GM4140 Resistance-Capacity Bridge, measures capacity from 10mmf to 10mf and resistance from 0.1 ohm to 10 meg-ohms. Provision for use as open bridge and for power factor measurement. Reduced from £13/13/- to **£7/10/-**

RADIO-AID Crystal Frequency Sub-standard, provides crystal frequencies of 100 Kc/s and 1,000 Kc/s, with multi-vibrator giving 10 Kc points. Tuned output ensures strong harmonics at high frequencies. Provision for modulation of signal. An invaluable adjunct to any amateur station.

Reduced from £24 to **£10**

40-watt MODULATOR, 6SJ7, 6J5, PP 6J5, PP 807's, Woden transformers used throughout, with multi-ratio output transformer. Built-in 650v power supply, rack mounting, complete with valves.

Reduced from £30 to **£15**

DENCO COIL TURRETS for S.W. Receiver constructors—

Type CT2, Mixer and Oscillator 465 Kc/s, frequency coverage 150 Kc/s to 30 Mc/s in four bands.

Reduced from £3/10/- to **£2**

Type CT3, RF, Mixer and Oscillator, frequency coverage 1.5 Mc/s to 42 Mc/s in three bands. Vernier control for bandspread, I.F. frequency 1.6 Mc/s. Complete with bandset and bandspread dials.

Reduced from £6/10/- to **£4/10/-**

LABGEAR Electronic Fault Tracer—combines the functions of Signal Generator, Audio Oscillator, Resistance and Capacity Bridge, and Neon Insulation Tester. HT and LT voltages available for external use. The signal in a radio receiver can be traced from aerial terminal to loudspeaker, enabling very rapid location of faults. Illustrated leaflet available on request.

Reduced from £34/10/- to **£20**

ODEON RADIO

Everything for the Amateur

56 College Road, Harrow, Middx.

Telephone: HARrow 5778

Lyons Radio

3 GOLDHAWK ROAD,
SHEPHERDS BUSH, LONDON, W.12

Telephone : Shepherds Bush 1729

Morse Oscillator Sets (R.A.F. Valve Buzzer type 2)

An excellent set for morse practise. Incorporates switch to select five different notes with facility for providing interference in order to practise under difficult conditions. In wooden cases, size 9" x 8" x 8". Battery operated. Specification includes valve type VR21, valve type VR22, morse key and pair of phones. Complete outfit (less batteries), 32/6. Oscillator only, 15/-, carriage 2/6.

Heavy Duty L.F. Chokes

Made by Foster Transformer Co.
5 Henries at 650mA. D.C. resistance approx. 25 ohms. Weight 34 lbs. The connecting terminals on these magnificent chokes have been slightly damaged in transit but they are otherwise perfect and are unused. Price only 17/6 each plus 2/6 carriage.

R.F. Units Type 24

This converter unit is designed for 20-30 mcs but is easily modified for frequencies up to 45 mcs. Practically brand new and complete with 3 valves. 12/6 each, postage 1/6.

Motor Blowers

For 12 or 24v A.C./D.C. Perfect order 10/6, postage 1/6.

Wavemeters, Class D Mk. II

These portable heterodyne wavemeters are now almost too well known to require further description but briefly they cover a frequency of 1.9 to 8 mcs and, in 1 mc steps, from 1 to 25 mcs. Accuracy assured by use of twin 100/1,000 kcs crystal. Takes 1 amp at 6v to operate. These we now offer are not quite new but have been fully reconditioned and are in perfect working order. Supplied in teak transit cases and include valve, vibrator, crystal and instructions. £4/15/- carriage paid.

Wheatstone Receivers

Brand new unused weight driven Wheatstone receivers. Standard post office type. £9/15/-, carriage 5/-.

New Radio Publications

"Radio Valve Applications" 5/3 post free.
"Using Ex-Service Radio Apparatus" (includes valve equivalents list) 2/8 post free.

THE MAIN AMATEUR SERVICE OF THE NORTH

G6HP FOR H.P.


H.P. Means :

Houses of Parliament to the uninitiated.

High Power to the QRP wallah

Panama to the DX Hound

and HIRE PURCHASE to You

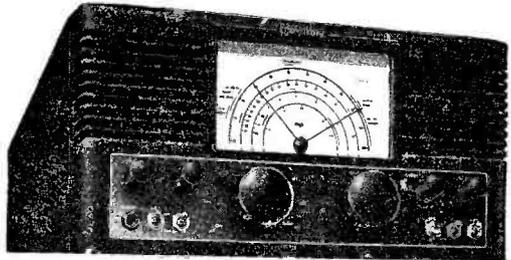

EDDYSTONE 640 AMATEUR COMMUNICATIONS RECEIVER

The finest British-made Amateur Communications Receiver of all time bar none.

Now available on VERY EASY Personal Deferred Payment Account. A much better proposition than any Surplus Receiver.

CONSIDER. For £5/15/- deposit and 78 weekly payments of 6/- into a local Bank YOU TOO can become the proud possessor of a BRAND NEW GUARANTEED EDDYSTONE 640 RECEIVER.

Don't delay—write to-day—big demand expected.

Full details and illustrated brochure gratis.

PRICE **£27.10** CASH
Delivery by return. Carriage paid.
Guaranteed for 12 months.
"Better than my H.R.O. G3SN."
We are busy with Mail Order work, but always welcome callers. If unable to call, may we send you a copy of our latest list SWL ?

AMATEUR RADIO SERVICE, CANNING STREET, BURNLEY

TEL
2999

G2AK

The Month's Bargains

G2AK

Transformers. Input 200/250v in 10v steps. Secondaries, 500/500v 120ma, 4v 3.5A c.t., 4v 4a c.t., 4v 4A c.t. and 10v 1A. 4v can be connected to give 6v if required. Beautiful job, not pitched-in junk. Our price 30/-, packing and carriage 1/6.

Transformers. Input 200/250v in 5v steps. Secondaries, 1,100/1,100v 300ma and 4v 1A for indicator. Worth £4. Our price 30/-, packing and carriage 1/6.

Some of both of the above have broken terminal strips, but are guaranteed perfect otherwise. VERY LIMITED QUANTITY AVAILABLE.

Dummy Aerials. Brand new in metal case, complete with 5, 10, 20 ohm Vacuum type 100-watt Non-Inductive load resistor. A rare bargain at only 7/6 each, postage and packing 1/-. Silver-plated 14-gauge copper wire for V.H.F. coils, 7' lengths, 1/-.

Feed Through Insulators. Ceramic, complete with 5" x 1/2" rod, nuts and washers. Only 1/- each, or 1/9 pair.

Large Stand-offs, Ceramics, 3" high, 1 1/4" diam., 3/8" Fixing Screw in base, 3/8" hole for Elements. Only 1/- each, or 10/- doz.

15 mfd 50v metal-cased Bias Condensers, as used in the Q-Fiver. 9d. each, or 7/6 doz.

3-Gang variables, brand new, 226pf per section. Few only available at 5/6 each.

Collins 7-valve Communications Receivers. Few only left now of this famous Rx. Coverage 1.5 to 12mc in 3 Bands, all ceramic coils and switches. Write for photo and details. Fitted with 12v tubes and priced at only £6/10/-.

Bargains in New Valves. TZ40, 30/-; 250TH, 45/-; 100TH, 35/-; 813, 55/-; 832 and 832A, 25/-; 807, 7/6; 6AG7, 10/-; GU50, 15/-; 5R4GY, 7/6; metal 6N7, 11/-; 6J6, 15/-; 6C4, 11/-; 6AG5, 12/6; 6F6G, 6V6 and 6V6gt, 9/-; U52, 10/-; DH63, 8/6; KTZ63, 8/6; 6S17, metal, 9/-; 6SG7, 9/-; 6SK7, 7/6; 6SQ7, 7/6; 12SK7, 125A7, 125Q7 and 12A6, 5/- each.

Rack Mounting Power Units. Designed for the 1132 Rx Standard, 200/250v input. 230/250v output at 100 mA, also 6.3v at 4/5 amps with m.a. meter, price £3. packing and carriage 7/6.

Ceramic 2 1/2" Coil Forms. Complete with 5-Pin plug base, similar to Eddystone type 1090 and 1091. Our Price only 5/- each, or 4 for 17/6.

Pyrex Glass Insulators. 7" long, 4/6 pair. 8 mc XTALS, 0825, 8050, 8075 and 8100 kc, for 144mc octal pins. Price 12/6 each.

100 kc Oscillator Units. Complete with Xtal and valve. Mounted on sub-chassis, wired ready to drop into your Rx, requires only HT and LT. Price 25/-.

Genuine RCA AR88 Mains Trans. 110/240v 25/110c. Price 55/-, post and packing 2/6.

AR88D and AR88LF Instruction Manuals, available at 16/6 each.

Small Filament Trans. Input 210/250v 50c. Output 12v 2A, 20/-, Ditto, 25v 1A (for Q Fiver), 20/-, post and packing 1/-.

BC221's, as new, with built-in stabilised power supply for standard input. Few only available, £15.

FOR ALL YOUR HAM REQUIREMENTS

CHAS. H. YOUNG, The Red House, Phillips St., Aston, Birmingham, 6 Phone: ASTon Cross 3381

Southern Radio's Wireless Bargains

BENDIX COMMAND RECEIVERS. BC454, 3.6 megs (1/fs 1415 kcs) and BC455, 6.9-11 megs. (1/fs 2,830 kcs). Ideal for conversion to AC/DC receivers and car radios. 6 valves, 12SK7 (3), 12SR7 (1), 12A6 (1), 12KB (1). Brand New and boxed, either set, 35/-, plus 1/6 postage.

CONTROL BOXES FOR BC453, BC454 and BC455 RECEIVERS. Three slow-motion drives and dials, three 50,000-ohm volume controls and six rotary switches. 12/6 each, post 1/-.

DRIVE ADAPTORS AND KNOBS FOR BC453 SERIES. Gives slow-motion drive on any comn and receiver, easily fitted. 2/6 per set, post 3d.

MARCONI 60-OHM HEADSETS. Leather headbands. 5/- each, post 6d.

FRACTIONAL HORSE-POWER MOTORS. Approx. 1/16th, 2,000 r.p.m. 4 1/2" x 2 1/2" dia. Black crackle finish, 15/- each, post 1/6.

TRANSMITTER TUNING UNITS. T.U.9B. (7,700-10,000 kcs), T.U.10B (10,000-25,000 kcs) and T.U. 26 (200-500 kcs). Any unit £1, plus 2/6 carriage.

WESTECTORS W.X.6 and W.112. 6/- per dozen, post 4d.

DRIVE CABLES FOR COMMAND RECEIVERS. 14 ft. long, 8/6, post 6d.

FOURTEEN-FOOT WHIP AERIALS. In 7 interlocking sections. Copper, 4/6 each, post 6d.

THROAT MICROPHONES. Low impedance, with 3-ft. lead and plug. 3/6, post 4d.


CONTACTOR TIME SWITCHES. By Venners or Smiths. Two impulses per second given by 10-hour movement. Ideal for darkroom work. In soundproof boxes with thermostatic control. Brand New, 10/-, post 1/4.

24-Volt MOTORS with slow-motion gearing and smoothing circuit. 10/6, post 1/-.

MERCURY SWITCHES. On/Off, length 1 1/2", 3/8" diameter. 5/- each. Post 6d.


SOUTHERN RADIO SUPPLY LIMITED
46 Lisle Street, London, W.C.2. GERrard 6653

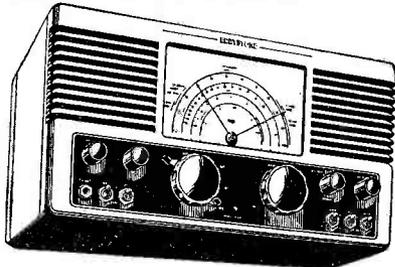RECEIVERS for WEST COUNTRY AMATEURS EDDYSTONE 640



DELIVERY FROM STOCK
CASH £27-10-0 or
£5-15-0 down. 6/- per week.

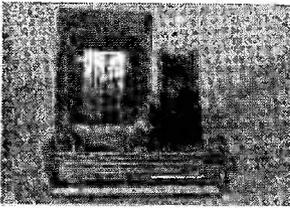G. N. PILL & PARTNERS
49 COBOURG STREET, PLYMOUTH
Telephone: 2239




**COMMAND
POWER
PACK FOR
BC453, BC454
BC455**

45/-
post paid

230v AC. Wired and Tested. Fitted 6 x 5 Rectifier. Just Clip On. No Alterations to Wiring. Mains Cord fitted ready for instant use.

**BC 348
POWER
PACK**

70/-
post paid

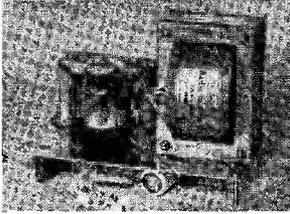

230v AC Power Pack. Fits exactly in place of Dynamotor. Fully smoothed. 5 screw connections only. Fitted 6 x 5 Rectifier. On-Off switch. Ready for instant use. These units are manufactured by us exclusively to highest standard

H. P. Radio Services Ltd.

Britain's Leading Radio Mail Order House
55 County Road, Walton, Liverpool, 4
Est. 1935 Tel: Aintree 1445
Staff Call Signs: G3DGL, G3DLV

ALWAYS AT YOUR SERVICE

Electradix British Bargains

TRANSFORMERS. Auto 230/110v 85 watts, 25/-; 150 watts, 35/-; 1,000 watts, £7/10/-. Double wound 230/12v in 1v steps, 4 amps, 45/- B.T.H. Transformer, 200-230-250v input, 2v 20 amps and 75v 6 amps with 15 taps output, 45/-. Carriage 5/-. Transformers for rewind with lams and wire, 500 watt size, 25/-.

HEADPHONES. Special offer of phones suitable for crystal reception; with headband and cord, lightweight, with bakelite caps and case, 5/6 pr.; two pairs, 10/-, post free. Moving coil headphones, 45 ohms resistance, in bakelite case with cap with moving coil, mike and cords, 10/6.

MAGNETS. New Swift Levick instrument perm. magnets, circular 1 3/8" dia., 1/8" thick, Polar gap 1/2", drilled poles; lift 3 lbs., 4/- each. Alni disc magnets, 3/8" dia., 3/8" thick, with 1/8" hole, 3/6.

ELECTRO MAGNETS. Powerful 1/2 6/25v D.C. with screw-in solenoid core, weight 1 lb., 10 ozs., 2 1/2" x 1 1/2", will lift 7/28 lbs. Type No. 1, 4/- Small 2/6v D.C. electro magnets, weight 10 ozs., lift 1 1/2 to 4 lbs., 7/6.

DIMMERS. Panel dimmers, totally enclosed, for valves, small light control or safety switches on test circuits, 100 ohms 1/2 amp, 2/6; 50 ohms 1/2 amp, 2/6.

Please include postage for mail orders.

ELECTRADIX RADIOS

214 Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

BARNES RAD.-ELEC. CO.

12 Pipers Row, Wolverhampton

Television Sound and Vision Receivers, complete with 10 valves. R1355, 30/-, plus 5/- carriage, etc.; R1116, 8-valve battery all-wave superhets (tested), £11 (send 3d. for special leaflet); 12v D.C. new Canadian amplifiers, with 2 valves, output 6K6, 30/-; Yaxley switches, 2 bank each, 1 pole 6 way, 2/9, bargain; 3-gang (long spindle) midget condensers, 54+54+33pF, 5/3; push-button units, 8-pole change-over on each of 4 buttons, with knobs, 7/6; telephone selectors, 3 bank each, 25 way, with continuous running contacts, 8/6. Huge lists in preparation, send 3d. to mail.

HRO's. 5 coils (4 bandspread), loudspeaker, power pack, excellent condition, 100 per cent efficiency, £31 each; AR-88-D loudspeakers, completely new, £45; NC200 loudspeaker, excellent condition, £30.

HALLICRAFTERS. BC-610 with speech amplifiers and aerial tuning units, new sets of valves, excellent working condition. Offers.

NEW 60W transceivers, 829 output, high-class superheterodyne receiver, 2-8 or 4-16 mc/s, phone/cw, very compact, weight 13 lbs, supply from power pack or converter. Offers.

P.C.A. WIRELESS WORKSHOP
THE ARCHES,
CAMBRIDGE GROVE, LONDON, W.6

SMALL ADVERTISEMENTS

TRADE ADVERTISEMENTS

9d. per word, minimum charge 12/-. No series discount: all charges payable with order. Insertions of radio interest only accepted. Add 25% for Bold Face (Heavy Type). No responsibility accepted for errors.

ELECTRIC Bulbs, any voltage, any amperage, any type, promptly available. Suxip Lamps, Ltd. 239 High Holborn, London, W.C.1. HOLborn 0225, 4343.

WANTED.—WESTERN ELECTRIC VALVES. TYPES 101F, 102F, 272A OR B, 310A OR B, 311A, 313C, 323A, 328A, 329A, 348A, 349A 352A, 373A, 374A, 393A, 394A, 121A BALLAST LAMPS.—BOX NO. 409.

WANTED.—W. E. CARRIER TELEPHONE AND CARRIER TELEGRAPH EQUIPMENT AND COMPONENTS, FILTERS, REPEATING COILS, TRANSFORMERS, EQUALIZERS. TYPE CFI, CF2, H. C. AND OTHER CARRIER EQUIPMENT, TELEPHONE AND TELEGRAPH RECEIVERS. BOX NO. 410.

WANTED.—TELETYPEWRITERS COMPLETE, COMPONENTS OR PARTS, ANY QUANTITY AND CONDITION.—BOX NO. 411.

MASON'S, Wivenhoe, Nr. Colchester. The Denco MDCR19 Communications receiver is now in production. We have full details. We can always supply the latest Denco and Eddystone goods. Send 9d. now for our 54-page illustrated catalogue.

QSL CARDS and LOG BOOKS, APPROVED G.P.O. SAMPLES FREE. ATKINSON BROS., PRINTERS, ELLAND, YORKS

SMALL ADVERTISEMENTS

TRADE—continued.

COPPER Wires; Enamelled, tinned, litz, cotton/silk covered. All gauges. BA screws, nuts, washers, soldering tins, eyelets. Ebonite and laminated bakelite panels, tubes. Paxolin coil formers. Tufinol rod. Permanent detectors, etc. List S.A.E. Trade supplied. —Post Radio Supplies, 33 Bourne Gardens, London, E.4.

AMERICAN Books on Radio wanted; secondhand, clean, also British.—Post to Bulls, 246 High Street, Harlesden, N.W.10.

WEBB'S RADIO REQUIRE A TECHNICAL SALESMAN, PRINCIPAL DUTIES ORGANISATION AND FURTHERANCE OF "HAM" SALES. WE PREFER A LICENSED AMATEUR WITH SOME COMMERCIAL EXPERIENCE, BUT KENNESS AND GENERAL ADAPTABILITY IS MAJOR CONSIDERATION.—WRITE G6VA, WEBBS, 14 SOHO STREET, W.1.

WANTED.—Small quantities in good condition. Monitor Unit Type 28 or 27. Transmitter TR3529A. Power Unit 529. Test Set TS34/AP. Modulator Unit Type 158A. Test Set TS13/AP. Amplifier A.3583 or A.3531. Signal Generator Type 52. Also 3 cm. waveguide components.—Box No. 467.

THERMO Units containing two 7 mc Xtals, 4/- each. 4 mc Units, 1/- each. 7275 and 4 mc Blanks, 1/- each.—Thomas, GW3AX, Roseland, Kettle, Bishopston, Swansea.

WANTED.—Supplies of American Valves, Types ICSGT, ID8GT, 931-A, 3A5, 3E29, 3O4, 6E5, 6J6, VR-75/30, 82, 83, 816, 829-B, 874, TL-450. Send details of quantities and prices of each type to Box No. 468.

QUANTITY DCC Copper Wires and Ex-Government Condensers, moulded, mica, neoprene, silver mica, ceramic, tubular cans, trimmers. Write for list.—G. Barmaper, 1 New Court, Carey Street, London, W.C.2. Holborn 5244.

ALUMINIUM chassis and panels; standard sizes by return, special sizes made promptly. Holes punched for valveholders, etc. Ours or your items finished in black crackle or grey cellulose. Estimates free. Note new address.—E.A.D., 18 Broad Road, Lower Willingdon, Sussex.

Q5R9 Beams, 2½ to 20 metres. Masts, lashings, bearings, rotators, etc. S.A.E. list.—Emdo, Ace Works, Staines.

LONG Range Television with the Q5R9 folded dipole multi-element aerial. S.A.E. for illustrated brochure.—Emdo, Ace Works, Staines.

G200'S VR91 (EF50), VR65, VR65A, 615gt, 6H6, VR137 (RL16), 5/-, 6SH7, 6AC7, 6SQ7, 6L5, 6/6.—A. C. Hoile, 55 Union Street, Maidstone. Loose 83579.

BERRY'S (SHORT WAVE) LTD. have vacancies for Senior and Junior Counter Staff. Applicants must be well versed in HAM gear. Full particulars of age, past experience, salary required, etc., should be sent to 25 High Holborn, W.C.1. All applications will be treated in confidence.

WANTED.—Items of ex-Service airborne equipment, British and American. Offer lists can include all types of unused or good-condition apparatus. Particularly want DM28 (all letter suffixes), Dynamotors from BC348, all types American plugs and sockets, flexible drives (state lengths) used between pilot's panel and BC453 receivers, and similar. Quantities large and small purchased at fair prices.—Box No. 470.

SET superhet coils, long, medium, short, twin gang condenser, four pole switch pair standard 465 kc IF's, with circuit, 13/6. Write for lists.—Cohen, 67 Raleigh Avenue, Hayes, Middlesex.

IFT'S 465 kc, iron-cored, 6/- pair. Electrolytics, new 1 not Govt. surplus, 450v wkg. 8 mF, 2/3 each. 8-8 mF, 3/6 each. 16-8 mF, 4/- each, etc. Send for list.—T. G. Howell & Co., 29 McWilliam Road, Woddingdean, Brighton, 7.



"... going QRT now OM, must get a 2½d. stamp off to Johnsons"—Colin has heard the news!..

JOHNSONS SPECIAL VALVE BARGAIN LIST—IS HERE!

MAGNIFICENT OFFER
15,000 U.S.A. VALVES!

Brand new valves, in makers' packing, at real bargain prices! All the popular types from 2/6 each. Here's the chance to refit your equipment and obtain spares at a fraction of usual cost. Many rare types listed.



DON'T MISS YOUR COPY—

A 2½d. stamp, with your name and address, brings a copy of our latest Bulletin together with the Special Valve Lists—new remarkable offers in receivers, etc. Full details of the new Eddystone "680" are described and other interesting news items. Immediate delivery from stock of the popular Eddystone "640", the Hambander, etc.—real DX at low cost. Terms as usual. Write to Johnsons, today!



JOHNSONS (RADIO SPECIALISTS)
MACCLESFIELD, CHES.
TEL. 4080

EDDYSTONE

'640' £27 10s, 9d.
H.P. Terms available.

Orders now being booked in strict rotation
Full range of components.
All C.O.D. orders promptly executed.
Send for Catalogue, 1/- post free.

SPECIAL OFFER

P.M. Speakers
Goodman's, Truvax, Rola (as available).
5 inch 13/-; 6 inch 14/-; 8 inch 16/-
including packing and postage.

B.T.S.

THE Radio firm of the South.
63 London Road, Brighton, 1, Sussex.
Phone : Brighton 1555

Radio G200 Announces

ALTIMETER Unit ARNI. Tx.Rx. 4 Acorns VR150/30 and 8 Metal Octal valves, tuned resonant lines, relays, motor generator, condensers, etc. etc. This high quality American-built job, new in original packing, G200's price.....Only 70/-.

12-Volt Vibrator Units. Ex-No. 22 set, the very thing for car radio H.T. Only 19/6

GENEMOTORS. 11.5v D.C. in, 250v 125Ma D.C. out. Only 19/6
11.5v D.C. in, 490v 65Ma D.C. out. This gives about 250v D.C. run from a 6v car supply.....Only 19/6

A. C. HOILE, 55 UNION ST., MAIDSTONE, KENT - - - - - LOOSE 83579

RADIATING COSTS !

The simplest way of obtaining reasonable power at the lowest cost, together with reliability and efficiency, is to invest in a RADIOCRAFT Type 44 or 44P Transmitter.

The Type 44 gives four-band coverage from a single crystal and uses an 807 as PA on all bands. With a 350v supply, inputs of 25 watts are easily obtained. For full details write for List M/9.

Type 44 Transmitter, £7.

Type 44P (incorporates power supply), £13/2/6.

A Type 44 can be inspected at any one of the following agents :—

Messrs. Johnsons (Radio), Macclesfield, Cheshire.
Messrs. A.C.S. Radio, of Bromley, Kent,
Messrs. Worboys & Tourtel, Southampton, Hants,
Messrs. Wardhaugh's Radio Service, Hexham,
Northumberland.

EDDYSTONE 640 RECEIVER

This popular receiver can now be obtained on easy payment terms. We are Eddystone agents and will be pleased to let you have all details.

Radiocraft Ltd

11 Church Road, Upper Norwood, S.E.19
LIVINGSTONE 4787

A.C.S. RADIO

Specialists in Short Wave Equipment, offer the following selection from stock :—

VARIABLE CONDENSERS

Raymart : VC40X, 4/- ; VC100X, 5/6 ; VC160X, 6/6 ; MC60X, 5/- ; 500pF variable condensers, single, 3/6 ; twin and three-gang, 7/6.

COIL FORMERS

Raymart : 4-pin plain, 2/- ; 4-pin threaded, 2/3. Eddystone: 6-pin 537, plain, 2/3; 538, threaded, 2/6.

TRANSMITTING KEYS

Enclosed pattern, new and boxed, 2/9.

CHOKES

Lennox : 10H 90m/A, 200 ohms, 10/- ; 10H 150m/A, 200 ohms, 14/-.

Midget Chokes, 10H 40m/A, 300 ohms, 5/3.

R.F. Chokes, 2.5mH, ceramic former, 1/-.

Eddystone 1010, 1.25mH, 1/9.

Eddystone 1066, 13mH, 3/-.

COILS

Wearite "P" coils, all types, 3/-.

Lennox Coil Packs, 3-wave band, 31/-.

Lennox Super-Het Tuning Coils, medium and long wave, 7/6 pair.

Lennox I.F. Transformers, 465 kc/s, iron core tuned, 16/- pair.

I.F. Transformers, 125 kc/s, 21/- pair.

(valek set of 3 short-wave coils, plug-in type, 9/- per set.

(Postage extra on above items, please)

SEND FOR OUR DETAILED CATALOGUE AND DETAILS OF EDDYSTONE RECEIVERS AND RADIOCRAFT TRANSMITTERS, ETC. WRITE TO

A.C.S. RADIO

44 WIDMORE RD BROMLEY, KENT.
Phone RAVENSBOURNE 0156

SMALL ADVERTISEMENTS

TRADE—continued.

BC221 POWER PACKS. 200-250v AC INPUT, £2.—M. A. WESTON, HARMAN'S CROSS, CORFE CASTLE, DORSET.

BARGAIN Sale Lists !—23d. stamp to : Johnsons (Radio), Macclesfield, Cheshire.

VALVES ?—See our advertisement on Page 915 of this issue.—Johnsons (Radio), Macclesfield, Cheshire.

MAKE your own S-Meter. New boxed 2½ in. square M/C meters, flush mounting, F.S.D. 1 mA, right-hand zero, graded temperature, 4/9 each. 2-Bank 6-Pos. ceramic switches, 1/10 each. 465 kc iron-cored IFT's, 7/6 pr. 240/6.3v 2 amp. fl. xfms., 8/9. 6K7GT's, 6X5GT's, 6G6G's, 5/6. All post free. Stamp list.—J. T. Anglin, G4GZ, 233 Welholme Road, Grimsby.

HALLICRAFTER transmitters Type HT4E, complete to makers' latest specification, covering all amateur bands up to 30 mc, with speech amplifier, connecting cables, etc. Immediate deliveries in quantity. **HALLICRAFTER HT14** 50-watt Marine Radio Telephone, complete with all valves, crystals, and covering amateur and marine bands from 1-6.4 mc. Immediately available from Hallicrafter United Kingdom distributors.—McElroy-Adams Manufacturing Group, Ltd., 46 Greyhound Road, W.6.

G6QA PERSONAL SERVICE BY POST. BC-221, ABSOLUTELY BRAND NEW, £12/10/-. CARR. PAID. FEW WITH DIRTY CASES, BUT OTHERWISE AS NEW, £10, CARR. PAID. A FEW MODULATED TYPES AT £2 EXTRA. CRYSTALS 5 TO 7 MC, 3/6. 8 MC FOR 144 MC, 7/6. CURE YOUR TVI. SEE QST DEC. VACUUM CONDENSERS, 50 MMF, 7/6. CRYSTAL MULTIPLIERS, COMPLETE WITH SPARE 807 FOR CONVERSION TO CLAPP VFO, £2/2/6. COMPLETE ANTENNAS, 3/6 and 4/6. MANY OTHER BARGAINS TOO NUMEROUS TO MENTION. WE HAVE LARGE STOCKS OF VALVES, METERS, RESISTANCES LARGE AND SMALL, CONDENSERS ALL VALUES. WRITE FOR LISTS AND YOUR REQUIREMENTS. SEE ALSO DISPLAY ADVERT. ALL ITEMS POST FREE.

Q-WAY High Voltage "Jones" type Plugs and Sockets, with crackle covers, 1/6 Pair complete, 12/- dozen pairs ; £3/10/- per 100 pairs, carriage paid.—Jack Porter, Ltd., Collese Street, Worcester.

VALVES unused. 83, 6/6 ; 803, 43/- ; RCA807, 15/- ; 813, 48/- ; 814, 45/- ; 829, 28/- ; 866/866a, 19/- ; 872a, 36/- ; 956, 10/6 ; OZA, IT4, 6/- ; 2A3, 5Z3, 5Z4, 6L6, 6K8, 7/6 ; 6B7, 6J5, 6CS7, 6/6 and many others. Send P.O. or C.O.D.—P. & B. Supply Centre, Ltd., 56 Draycott Place, S.W.3.

QSL'S and LOGS by MINERVA. The best there are. Samples from Minerva Press, Elm Park, Essex.

QSL CARDS. Distinctive and attractive designs. Samples and prices from—G5KT, 35 Hillside Avenue, Kingswood, Bristol. . .

FOR SALE, 28 only, 3 corrugation metal flange top and bottom "Steatite" porcelain insulators for transmitting aerials ; 30,000v working, 15/- each.—Apply, Box No. 480.

READERS' ADVERTISEMENTS

3d. per word, min. charge 5/-, payable with order. Box numbers 1/6 extra.

AR88D for sale, complete with manual, £40. Sky Buddy, £10. Both carriage forward.—G4JI, 41 Willoughby Road, Boston, Lincs.
FOR SALE.—R1116 Rx, less D.F. in working condition, including case with C. Diagram. Offers over £7.—M. Colgrove, 10 Kingsley Avenue, Rugby.

SMALL ADVERTISEMENTS
READERS'—continued.

TYPE P.C.R. receiver for sale. Internal power pack and speaker, S-meter, RF gain control, £12.—Apply N. Brokensha, 160a Haverstock Hill, Hampstead, N.W.3.

EDDYSTONE 504X, built-in S-meter, speaker unit and Brown's 'phones, instructions manual; as new. Snip! £35.—Box No. 456.

AR88 535 kc to 32 mc. Showroom condition, complete with handbook, £55 or nearest offer.—76 Etherley Road, West Green, London, N.15.

RME69 Xtal filter, noise suppressor—requires re-alignment. Best offer over £25.—G3ZI, Cedar House, Philipot Lane, Chobham, Surrey.

ASB8 420 mc 12-valve double superhet, light-house RF stage, brand new, with details if required, £6.—G3BLB, 38 London Road, Kingston, Surrey.

RCA AR88LF communication receiver; guaranteed as brand new, complete with instruction manual, £35. No offers.—Box No. 458.

FOR Sale: Eddystone S640, one owner, as new. Eddystone 5 and 10 converter, Webbs built. Offers around £26 both, or would sell separately.—Box No. 459.

EDDYSTONE 640 in carton, new. S-meter, Brown's phones; 5-in. speaker, instruction manual, £30 near. Phone: FOR. 6383.

3 HAMMARLUND HV/Conds. Valves: 3, KT8; 2, 807; 1, 1625; 2, PX4; 2, PX25. Xtals: OCC, 71.25, 3500. Absorb W/Meter, 23-36 mc. Meters: RF, 0-5A; 0-5mA, 0-40/120 mA; 4 V/Conds. VFO SM Drive. First £2 10s. secures.—341 O'd London Road, Hastings.

SHORT Wave Magazine, 20 copies 1946-48, £1. Short Wave Listener, 13 copies 1947-48, 5/-. QST, 12 copies 1944-45, 10/-.—Martin, 3 Cliff Avenue, Loughborough, Leics.

IAM emigrating offers AR88, lab. aligned, £40. New items: CV73, CV85, 10/-; 6V6G, 807, VU133, CV54, 6Q7G, KT63, 7/6; EF50, 5/-; 7193, L63, 3/-; 0-5 + 0-5 mF, 2,200v, 8/6; .05 mF, 3,300v, 5/-; 1 and 2 mF, 9d. Pots, relays, pairs steel handles, 1/-. Steel ventilated cabinets with quick release chassis 21 in. x 11 1/2 in. x 8 in., perfect, for power or mod. units, 7/6. 18-480v dynamotor, 3-speed drive, £1. Junk box parcels, 5/- five lbs. Also used serviceable items—6SH7GT, 2/6; 6H16, 0/2A, 7193, 2/-. Nuts, bolts, washers, 2/3 gross. Valve bases, 3/- doz. C.W.O. Please add little postage.—Edwards, 12 Coledale Drive, Stanmore.

SELLING HRO Senior, 6 coils, being aligned commercially; BC221 working; 6v Hallicrafter P/Pack. Two R1147 (one 954 missing). Govt. 12v Tx, 807 x 807, slight damage. Valves 807, RK34, 955, others BII complete. Much mangled, seen solid service, Kent. Offers lot.—Box No. 460.

SALE.—HRO Senior, p/pack, 6 sets coils, first-class condition. First best offer secures.—G3CGE, 42 Norham Avenue, Southampton.

150W Tx, 6L6-807-813, complete with power packs and rack; BC342, and auto transformer. The lot, £25.—Lesley Cottage, Elm Park, Stanmore, Middlesex.

60WATT PP plate mod. Tx, rack, rotary beam Complete £12. BC348, £10. Demonstration, G2XJ, 51 Arcadian Gardens, Wood Green.

WANTED, late Collins model VFO. Also Hallcrafters SX42. Either must be brand new condition. Full details, please. Would exchange latest model Super Pro for SX42.—Box No. 464.

EXCHANGE: Complete Amateur Station for small car, 1939, plus cash adjustment. Transmitter rack built. 250 watts—push-pull triodes in final; Class B modulator; Cabinet Transmitter for 160 metres, with three-stage modulator. Receiver AR88, in first-class order. Three frequency meters and monitors. Cathode Ray Modulation 'scope. Xtal microphone, Morse key with filter unit. Beam elements for 28 mc. Spares and equipment galore.—Box No. 463.

MORSE CODE Training

There are Candler Morse Code Courses for

BEGINNERS AND OPERATORS

Send for this free

"BOOK OF FACTS"

It gives full details concerning all Courses.

JUNIOR Scientific Code Course for beginners. Teaches all the necessary code fundamentals scientifically.

ADVANCED High-speed Telegraphing for operators who want to increase their w.p.m. speed and improve their technique.

TELEGRAPH Touch Typewriting for those who wish to become expert in the use of the typewriter for recording messages and for general commercial uses.

Code Courses on Cash or Monthly Payment Terms

IRREFUTABLE EVIDENCE

of the value of the Candler System of Morse Code Training is given in the "Extracts from students' letters," included with every "Book of Facts." Send for a copy now.

THE CANDLER SYSTEM CO.

(55S.W.) 121 Kingsway, London, W.C.2

Candler System Co., Denver, Colorado, U.S.A.

A. G. HAYNES & SONS

STROBE UNITS. 6xEF50, 5xEA50, 1xVRI16. 7 Pots. Dozens condensers, resistances, relays, etc. In original sealed cases. Price 35/-, carriage 3/-.

RECEIVER, TYPE 78. 5 Valves (6-3v), tuning condensers, 100 Kc/s xtal, 13-2-4 Mc/s. Brand New. In original cases. Only a few at 30/-, plus 3/6 carriage.

R.C.A. 15-Watt amplifiers, 4x6J7, 2x6L6, 1x5V4G. Crackle case. Brand New, in wood transit case, £12/10/-, carriage 10/-. A few, less valves, £9/10/-, carriage 10/-.
8 MFD electrolytics, 500v D.C. working. Tubular, ali. case. 3/- each.

1,000 MFD, 25v D.C., 3/-, 15v D.C., 2/6.

1355 RECEIVER for television. Excellent condition. Complete with 10 valves, 30/-, carriage 5/-.

MOVING COIL Headphones, 5/- pair. M/c Mikes, 2/6, post 9d.

BC347, 1 valve (6F8) amplifier, 5/-, carriage 9d.

SATISFACTION GUARANTEED

14 ST. MARY'S ST., BEDFORD

SMITH for all Radio Components

EDDYSTONE, RAYMART, WEARITE, etc.

Send for Lists ● Quick Service

Eddystone "640" £27/10/-, Cat. 6d. 145 Mc/s Guide, 1/6.

Everything for Rx or Tx supplied. Coils, Transformers, Condensers, Valves, etc.

SMITH

98 West End Road, Morecambe, Lancs.

Telephone : Morecambe 436.

WE OFFER

A large range of used and new Test Equipment, Converters, Recorders, Amplifiers, Motors, Transformers, etc. All guaranteed and at very attractive prices.

We buy good modern used equipment of all types for spot cash.

UNIVERSITY RADIO LTD.

22 LISLE STREET, LONDON, W.C.2.

Tel.: GER 4447 and GER 8582.



BARGAIN★

★ PARCELS

OF BRAND NEW SUNDRIES

TAG STRIPS

40 each of the 3 types illustrated

Total 120 for 5/-, plus 6d post.

Get a stock in NOW !

VALVE HOLDERS


8 each of the 3 types illustrated, UX4, B9G, 4p. ENG.

Total 24 for 5/-, plus 6d post.

SLEEVING

1, 1½ and 2 mm ASSORTED COLOURS 72-yard bundle 5/-, plus 6d post.

Latest Lists Free on Request

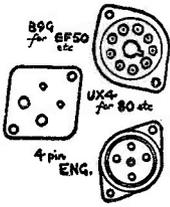

SATISFACTION GUARANTEED OR CASH REFUNDED INSTANTLY!

Frith RADIOCRAFT Ltd.
69-71 CHURCH GATE LEICESTER
G2R1 G3C98 G3BY1

PHONE 58927

SMALL ADVERTISEMENTS

READERS'—continued.

BC610 Transmitter complete, modified up to 30 mc, aerial coupler, auto transformer, speech amplifier, spare valves, first-class condition. Offers?—Addie, G8LT, Heatherland, Old Woking Road, Woking.

AMATEUR, ORT. has for sale—Receivers : 1155A, 125/-; BC455, 17/6; quantity of very cheap transmitter spares. Write for details. *Wireless World* Quality Amplifier with RF tuner, 7 valves, £12.—Box No. 462.

MICROPHONE. S.T.C. Type 4017A moving coil, as used B.B.C. Cost £20. With mounting ring and plug. £7 7s. or offer. *R.S.G.B. Bulletins*, April 1940 to date. Offers?—G2HNO, 45 Parkwood, Bourne-mouth.

R1224 3 band, 1-10 mc, 5v superhet. New; excellent stand-by receiver; complete phones, transit case, carriage paid, £4/15/-—Box No. 461.

HAMBANDER with speaker, £18. Avo Valve Tester, £14. Avo Oscillator, £11. Avo Capacity Bridge, £9. All as new.—Macdonald, 38 Densiloe Avenue, Hillingdon, Middlesex.

WANTED.—Panoramic Adaptor in good condition, with instruction book. Also 3rd IF transformer for AR77E.—Box No. 465.

AR88D, £35; Hallicrafter S22R, 110 kc to 18 mc. £12; both perfect condition. Buyer collects.—Malvern, 12 Rotunda Terrace, Cheltenham.

POWER Pack, voltage stabilised. Brand new, fitted with three 4-in. meters, 9 valves, LT, 6.3 and 12.6v 15 amps., HT 400v 300 mA, 230v 50 c.p.s. Last word in power supply for transmitters. Beautiful looking job, weight approx. 1½ cwt.—For particulars, Max Conu, 5 Orchard Gardens, Putson, Hereford.

640 Receiver, brand new with speaker and S-meter. £27/10/-—Apply Max Conu, 5 Orchard Gardens, Putson, Hereford.

BC348 with 230v AC mains pack, £17. Or will part exchange for Panoramic Adaptor, or an S27 VHF receiver, or similar HF receiver.—J. Torry, 57 Graig Park Avenue, Newport, Mon.

EDDYSTONE 400X (Similar 358X) modified to double superhet, 1.6 mc and 110 kc IF, band-pass crystal filter, noise limiter; 14 mc coil unit and coils, suitable for 28 mc uncalibrated.—£10 or best offer to G3BNE, 116 Haverstock Hill, Hampstead, N.W.3.

NEW.—813's (2), 30/-; 803's (2), 30/-; T240's (6), 20/-; 866's (6), 20/-; 35T's (2), 20/-; 832, 20/-; Xformers (2), 350v, 80 mA, 6.3 and 5v Lts, 15/-; TCS6 Rx, 7-valve superhet. Some mods. 1.5 to 14.5 mc, £5/10/-, plus carriage. Details supplied.—G3CUN, 148 Duncroft Road, Birmingham, 26.

TG-10 Automatic keyer, contains variable speed AC motor and 30-watt amplifier, £10. Super-Pro 18-valve receiver, £25, or exchange BC348Q and cash.—75 Edgehill Road, Winton, Bournemouth.

SALE.—Hammarlund Super-Pro, SP200X, 1.25 mc-42 mc; RCA AR88LF, RME-69. All with speakers and manuals. Best offers over 50, £38 and £22 respectively. (5) RCA boxed, 866/866A's, 16/- each.—G3CXD, 9 Kingsway East, Newcastle, Staffs.

SALE.—RME-69, noise limiter, good condition, £30. Advance sig. gen., Type E, Model 1; 100 kc to 60 mc continuous, new, £17/10/-. New transformers, Woden : JJM2, £3/5/-; DTM16, £3/18/-; DTF14, £1/7/- . Accept £52 for the lot, or offers?—Hazel Drive, Nottingham Drive, Wingerworth, Chesterfield.

HAMBANDER for sale, perfect condition. First £18 secures. Delivered free.—Box No. 469.

R1116A double-superhet battery receiver, in excellent condition, best offer over £7. —Dutton, 111 Ferney Road, E. Barnet, Herts.

R1155 with power pack, 6V6, £7/10/- . Tx; crystal, coils, etc., black crackle Eddy-stone panel, three meters, professional look, £8. Buyer collects. Must clear.—36 Claude Road, Peckham, S.E.15.

SMALL ADVERTISEMENTS READERS'—continued.

CRYSTALS. All tested and guaranteed: 5-7 mc, 5/- each; 144 mc by 27 times, 10/- DC-9 1000 kc, 22/6. Powder for grinding, 2 oz. sample, 1/6. Can supply larger quantities.—Box No. 475.

145 MC—BC-639A 11-valve Bendix, good condition less 1 valve, bargain at £7, plus 10/- if despatched, CR100, with noise-limiter and S-meter socket, excellent condition, £20 to caller only, 829B, genuine 2 hrs. use. Only £2.—G6VD, 9 Cecilia Road, Clarendon Park, Leicester.

RCA AR77E, 54-31 mc, in six bands, band spread, xtal, S-meter, noise-limiter, BFO, etc.; flywheel tuning, cabinet re-sprayed, chrome lifting handles and control guards; completely re-valved. Exceptional condition, complete with spare set valves, speaker, 'phones and manual, £38.—Morton, Dryden Street, Barrow-in-Furness.

EDDYSTONE 2-valve Presselector, absolutely new, all coils for amateur bands, and valves, £6.—10 Moor Park Road, Northwood, Middlesex.

ATP7'S, as used in 21 set, 50/- each. Standard Telephones 5B/502A (RK20, 12v filaments), 30/-. CV1199 (95-v stabilisers), 12/6. All new.—2 Chestnut Close, London, N.14.

SKY CHAMPION S20, perfect, with new valves, £15. Other gear S.A.E. for list, owner emigrating.—Box No. 471.

BC348, New, internal mains power pack, S-meter spare valves, £15. SCR522 with valves, crystal, £8. VRI50's, new, boxed, 6/-.—Box No. 472.

WANTED.—Modified BC221 in exchange for Ever-Ready personal Rx, or sell. Offers?—Cave, 161 Grangehill Road, Eltham, London, S.E.9.

HALLICRAFTER ARR5 28-146 mc, 3 ranges, HAM/FM, noise-limiter, S-meter, 2 RF, acorns, £15. New condition, BC-348, £14. Mk. IV freq. meter, AC 230v, £5. Franklin VFO, 4v, National engraved dial, £3/15/-. W.E.M.C. Studio mike, brand new, £5. Phillips T.C. cold electrodes, £4/10/- (cots £15).—G5CP, 33 Manley Road, Sale, Ches. Sale 3816.

A FINE Busch microscope, full accessories, library, value £45. Violin, N. Audinot, Dodd bow, library, value £40. Both or either exchanged for AR88 Type Rx. Full details to interested enquirers, Box (Kent) 474.

FOR sale.—Rothermel Senior Crystal pick-up, 11 clean issues 1948 QST. £2 the lot.—Grain, 15 Waverley Gardens, Grays, Essex.

WANTED.—Canadian Marconi Sender No. 52, required to operate with matching receiver of same make. State condition.—Box No. 473.

B2 Tx and Rx with P/P, £7/10/- or nearest. T10G Keyer, £10 or nearest. Both excellent condition and working order.—Perkins, G3MA, 40 Calton Road, Gloucester.

G.E.C. M/C microphone, Type BCS2285, 3506 kc, etc., £2 each. Elf circuit breakers, 10/-. Two-way insulated connectors, 1/- doz. Details.—Raitby, G8G1, Helpringham, Sleaford, Lincs.

TU9B; TUB8; TUB6; New, 11/6 each (carriage, 2/6); Three, 40/-. Carriage Paid. TU26B; TU5B, 20/- each.—Knight, 82 Fairfield Road, Widnes.

AMATEUR must sell up: HRO with coils in fitted case, rack model, £35. BC348 adapted for mains, with 6V6 output, £15. MCR1 complete with mains-pack, all coils, £5. Airey, 101 Thornton Road, Morecambe, Lancs.

CR100 Super condition, 60 kc-30 mc, 2RF, 1F, xtal filter, £25. Box No. 476.

B2 Rx, Complete, power pack, phones, mains, batt., leads; Want 1155 complete, good.—209 Countess Road, Walthamstow, London, E.17.

NO. 19 Tx/Rx, complete, £6/10/-. 2 only heavy duty mod. transformers, multi-ratio, 35/- each. 1624 (807), new, 3 for 10/- Carriage extra on all articles. S.A.E.'s answered.—10 Clare Terrace, Falmouth.

WANTED.—BC221 modulated—813 base, pair 809's.—BM/CDN, W.C.1.

NO SHOP KEEPS ALL YOU WANT—WE KEEP MORE THAN MOST. THAT'S WHY PEOPLE SAY—

**“You'll probably get it at
SMITH'S, Edgware Road”**

Pay us a visit and see for yourself.

H. L. SMITH & CO. LTD.
287-9 Edgware Road, London, W.2

Near Edgware Road Met. and Bakerloo

Phone: PAD 5891. Hours: 9-6 (Thurs., 1 o'clock)

SLOUGH, BUCKS

We have an excellent selection of specialised components for short wave and television construction. Eddystone 640, £27/10/- cash. H.P. £5/15/- down, 6/- per week for 78 weeks. Write to-day for full details.

THE FOLLOWING PRICES MUST INTEREST YOU

ALUMINIUM CHASSIS, 18-GAUGE.—
14" x 9" x 2½", 9/-; 12" x 8" x 2", 7/6; 10" x 7" x 2", 6/6; 8" x 6" x 2", 5/3.


BLACK CRACKLE PANELS.—19" x 12", 6/-; 19" x 10½", 5/3; 19" x 3½", 3/1½.

C.W.O. Please add postage

FON RADIO CO. (GXXC)

7 Station Approach, Slough, SLOUGH 22526

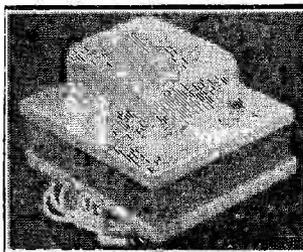COULPHONE RADIO PRODUCTS MAINS TRANSFORMERS



PRICE 15/6 (plus 1/- post and packing)

Why buy surplus transformers when you can have a brand new, fully guaranteed job at the right price. Standard size. Drop through type with top shroud. Interleaved and impregnated windings. Screened primaries, tapped 200, 230, 250v.

| | |
|-------------------------------------|----------|
| (a) 250-0-250v 60mA, 6-3v 3A, 5v 2A | ... 15/6 |
| (b) 250-0-250v 60mA, 4v 4A, 4v 2A | ... 15/6 |

Following types have universal L.T. windings enabling 4, 5 or 6-3v valves to be used:

| | |
|--|----------|
| (c) 250-0-250v 80 mA, 0-4-6-3v 4A, 0-4-5v 2A | 18/- |
| (d) 300-0-300v 80mA, L.T.'s as (c)... | 18/- |
| (e) 350-0-350v 80mA, L.T.'s as (c)... | 18/- |
| (f) 250-0-250v 100 mA, L.T.'s as (c) | ... 21/6 |
| (g) 300-0-300v 100mA, L.T.'s as (c) | ... 21/6 |
| (h) 350-0-350v 100mA, L.T.'s as (c) | ... 21/6 |

Terms: C.W.O. or C.O.D.

COULPHONE RADIO,

“The Return of Post Mail Order Service.”
58 Derby Street, Ormskirk, Lancs. Phone 496

CARLTON COILWINDING CO.

"A NAME TO NOTE AND REMEMBER"
offer a New Price List for 1949

Standard Lines include :—
Shrouded Mains Transformers, tapped primary 250-0-250v 80mA, 0-4-6-3v 4A, 0-4-5v 2A, 30/-;
Drop Through, half shroud, specification as above, 29/6;
Drop Through, half shroud, as above, but 350-0-350v 80mA, 29/6;
Auto 230/115v 50 watt, 18/-; 100 watt 22/6;
L.T. Transformer, open type, tapped primary, 0-4-6-3v 4A; 0-4-5v 3A 22/6;
RF Choke, 8mH 350mA, 5/-;
BC453 medium wave coil units, 10/-;
Multi-Ratio Modulation Transformer, 30-watt audio, maximum D.C. 150mA, shrouded with solder-tag panel, 45/-.
Rewinding service. Wholesale, Retail and Export enquiries invited.

Carco Works, Church Road, Birkenhead. Phone : 3585

DESIGNED FOR MODERN APPLICATION
G.L.G. METAL FABRICATIONS MEET THE DEMAND FOR MECHANICAL STABILITY

Chassis, 16 gauge, four sided, 16 stock sizes include :
2½" deep, 8½" x 5½" 4/9 3" deep, 9" x 6" 5/9
10" x 8" 6/9 12" x 9" 8/6
14" x 9" 8/6 13" x 8" 8/6
16" x 8" 8/9 18" x 10" 12/6

Reinforced, rivetted corners, 2/- per chassis extra.
PANELS. Durable black crackle, 14 gauge, 19" x 10½", 8/9; 19" x 8½", 7/9; 19" x 7", 6/9; 19" x 3½", 4/-. Metalwork to specification. Wooden components from stock.
SPECIAL this month. Brand new 16-gauge al. chassis, 17" x 10" x 2". Only 7/6 each, post 9d. Ex-AM chokes, 20 hen. 200 Ma, 200 ohms. New, 12/6. Post 1/-.

Stamp for Lists

G.L.G. RADIO, 15 Halcyon Rd., Newton Abbot

CALL SIGN PLATES



For Hams, SWL's and Clubs. Bright polished and lacquered letters on black crackle background. Robustly made in zinc alloy. Plate size, 5¼" x 2¼".

Desk type (as shown), 12/6 each. Panel type (plate only, drilled for mounting) 10/3 each. Postage paid, Cash with order.

London stockists : Webb's Radio, Soho St., W.I., or write : SOUTHEX TRADING CO., G3AEN, 66 Victoria Street, London, S.W.1

H.A.C.

Short-Wave Equipment

Noted for over 15 years for Short-Wave Receivers and Kits of quality

One Valve Kit, Model "C" Price 20/-
Two " " " " "E" " 43/-

These kits are complete with all components, accessories, and full instructions. Before ordering send stamped addressed envelope for descriptive catalogue.

Note new sole address:—

"H.A.C." SHORT-WAVE PRODUCTS (Dept. VIC.) 66 New Bond St., London, W.1

SMALL ADVERTISEMENTS

READERS—continued.

S27 v.g. cond., re-valved. Transformer 500-0-500v 425 mA, 3-15-0-3-15v, 4-2 a, 3-15-0-3-15v, 0-3A, 2-5-0-2-5v, 6A. Choke 20H 500 mA. 10 in. P.M. speaker in cabinet; also 40 mostly new valves. £25 lot or offers singly.—A. A. Littlewood, 10 Elms Drive, Kirkella, Hull, Yorks.

AR88d new condition, £40. S27, £20. AR77, £30. 1,200v 200 mA, WH Power Pack, £5.—G2FXR, Darsham, Suffolk.

HRO new, unused, rack mounting. Complete with coils for 50 kc-30 mc, moving coil phones and instruction manual, £40. Type 145 VFO, needs power pack, £8. Class D vavemeter, unused in wooden carrying case, £5. Four BC-603 B aerial tuning units, brand new in cartons, 15/- each. Coils low impedance co-ax, approx. 50 yards, 15/-. Woden UMI modulation transformer, new in packing, £2. HRO rack with 3 steel chassis and black crackle panels, new, undrilled, £5. BRS.17424, 20 Milk Street, Tyldesley, Lancs.

SX24 with matched 10 in. speaker. Unscratched, recently re-aligned. Offers over £25? Eddystone 5-10 complete, by Webb's, cost £13; unused, £7.—Heath, G3ABS, Denbydale, Yorks.

AR77E for sale. This receiver has been in use for just over a year and has been maintained in perfect condition. Re-valved and re-aligned recently. Exceptionally good performance on 28 mc. £35 or best offer.—Apply G6QB, *Short Wave Magazine*.

FOR sale. R116A battery communications superhet. £6 plus carriage. Wanted HRO, AR88 or CR100.—Box No. 477.

FL transformers, 7-5 twice 6-3, 5 and 4v, heavy duty, weight approx. 12 lb., useful Tx or bench, 55/-. Nife cells, 1-3v 10/15 AH, size 6 in. x 1½ in. x 1½ in., unspillable, useful wireless. electric bells, hand lamps, LT, HT, etc., 3/- each. AF3 intervalve transformers, 3/- each. B2 ceramic coil formers, 1/6. Tubular condensers -1 mF, 7d. each; -01, -005, 6d. each. All new, carriage paid.—Thompson, G2FXK, 82 Walsall Road, Aldridge, Staffs.

TELEVISION—1949 Invicta, Brand new with manufacturer's guarantee, bargain 48 guineas.—BM/CDN, W.C.1.

SX28 as new, with Instruction Book. Best offer over £30. CR100, perfect condition. Best offer over £20. Leaving country only reason for sale.—Box No. 478.

R1155 modified, 6V6 output, internal power pack and monitor speaker. 200 kc-18 mc continuous coverage. £12/10/-, or nearest. Frequency Standard for 230v operation, 1000/100/10 kc points, £5 or nearest. Perkins, 40 Calton Road, Gloucester.

BC348: excellent condition, with ten-metre converter, "Q5'er", S-Meter, 10in. speaker and 230v AC supply. Offers near £20.—G4CF, 132 Liverpool Road South, Burscough Town, Ormskirk, Lancs.

SALE or EXCHANGE. BC342 by R.C.A., also SB221 A.H. and EDDYSTONE 358. Wanted: Transmitting gear, AR88, etc. QTH Birmingham. Suggestions appreciated.—Box No. 479.

RCA 200-watt multi-ratio modulation transformer, fully shrouded, soiled but O.K., 15/-. New, unused, 25/-. RCA 30-watt output or push-pull driver transformer, multi-ratio, fully shrouded, new, unused, 10/-. Full details supplied. Carriage extra.—Box No. 457.

FOR Sale.—Complete transmitter, built in two 63-in. racks, relay controlled, fully metered. RME-69 complete with DB20 and DM36. View by appointment only.—Write Stewart, 13 Elm Drive, St. Albans.

OFFER.—150/250-watt CW Tx, rack mounted with set spare valves, 14/28 mc, ECO control; 25-watt 80m. phone/CW Tx, rack mounted; BC348 Rx, less power unit. All first-class condition.—Offers to G5JY, 81 Woodbridge Road, Guildford, Surrey.


AVO 7 Universal meter for cash sale, guaranteed as new, with resistance unit.—Box No. 466.

MINE DETECTORS

A U.S.A. Mine Detector Amplifier complete with 3 IT4 valves. Brand new and unused and consisting of an R.C. Amplifier housed in weatherproof aluminium case with battery compartments.

ONLY 22/6 (post free)

Spare valves 7/6 each
 Amplifier, less valves 7/6 (post.free)

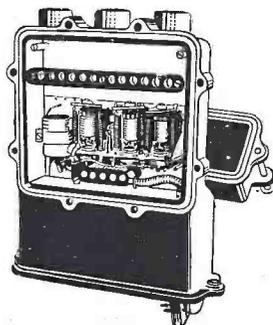

PLESSEY 2-GANG CONDENSERS

A standard '0005 2-gang condenser with fixing feet and long spindle. Brand new stock. Only 7/- (9d. extra for postage).

BALLAST RESISTORS

British-made equivalents to U.S.A. types C9266, K52H, K55B or K55H.

All at 7/6 each, plus 9d. postage.

HEAVY DUTY L.F. CHOKES

These are indeed a super job. 5 Henry 750 m/a or 15 Henry 250 m/a; overall size 7½" x 7½" x 7½". Four fixing feet—7" between centres. Electrostatic screen.

Brand new. Only 50/- (carriage paid).

OUTER CASES

A brand new cover, useful for construction work, storage bins, etc., etc. Overall size 6" x 5" x 14½". Reinforced at ends. Fixing brackets. Steel painted black matt finish. 5/- each (post free).

13- VALVE U.H.F. COMMUNICATIONS RECEIVER, TYPE RI392A

These are of a very recent RAF design and cover the 100-150 Mcs band without adaptation.

There are two RF stages, mixer, three IF stages, BFO, delayed AVC, Xtal oscillator and two multipliers. Fitted with tuning meter. Rack mounting with silver-plated chassis. Supplied complete with valves: 1 6I5G, 4 EF39, 2 6Q7G, 1 6J7, 5 EF54. 6-67 Mcs crystal supplied which can be ground to suit required frequency (operating on 18th harmonic).

In very good condition and supplied at the keen price of

£10.10.0 (carriage paid).

MEASURING INSTRUMENTS

OUR RANGE OF METERS :

| Scale | Type | Shape | Size | Mounting | Price |
|------------|-------------------------------|----------------------------------|----------|-------------|-------|
| M/amps | | | | | |
| 0-5 | Moving Coil D.C. | Square | 2" | Flush | 5/- |
| 0-30 | Moving Coil D.C. | Round | 2½" | Flush | 6/9 |
| 0-40/120 | Moving Coil D.C. Dual Reading | Round | 2" | Proj. | 7/- |
| 0-50 | Moving Coil D.C. | Round | 2-2½" | Proj. | 7/- |
| 0-100 | Moving Coil D.C. | Rectangular with shorting switch | 3" x 2½" | Proj. | 12/6 |
| 10-0-10 | Moving Coil D.C. | Round | 2½" | Proj. | 7/- |
| Ammeters | | | | | |
| 0-5 | R.F. Thermocouple | Square | 2" | Flush | 5/- |
| 0-4 | R.F. Thermocouple | Rectangular with shorting switch | 3" x 2½" | Proj. | 6/6 |
| 20-0-100 | Moving Coil D.C. | Round | 2½" | Flush | 5/6 |
| 0-14 | Moving Iron | Round | 4½" | Switchboard | 15/- |
| 0-20 | Moving Coil D.C. | Round | 2" | Proj. | 5/6 |
| 0-25 | Moving Iron D.C. | Round | 2½" | Flush | 5/6 |
| 0-30 | Moving Coil D.C. | Square | 2" | Flush | 7/- |
| 50-0-50 | Moving Coil D.C. | Square | 2" | Flush | 5/6 |
| Voltmeters | | | | | |
| 0-150 | Moving Coil D.C. | Round | 2½" | Flush | 5/6 |
| 0-300 | Moving Coil D.C. | Square | 2" | Flush | 5/6 |
| 0-2000 | Electrostatic | Round | 2½" | Flush | 22/6 |
| 0-3500 | Moving Coil D.C. | Round | 3½" | Proj. | 15/- |

All in maker's boxes. Postage extra according to quantity. Terms : Cash with Order. Remittances to E. & G. Distributing Corporation Limited.





MAIL ORDER SUPPLY CO.,
 Dept. SWM, 3 ROBERT STREET,
 HAMPSTEAD ROAD, LONDON, N.W.1
 Callers to : 24 NEW RD., LONDON, E.1
 Stepney Green 2760-3906

MODERNISE YOUR GEAR USE T.C.C. PLUG-IN ELECTROLYTICS

All-aluminium construction. Plain foil electrodes.

| | |
|--|------|
| 16mfd. 500v Peak, 600v Surge | 11/- |
| 32mfd. 450v Peak, 550v Surge | 12/- |
| 8-8mfd. 500v Peak, 600v Surge | 12/6 |
| 16-16mfd. 450v Peak, 550v Surge | 13/6 |
| 8-8-4mfd. 500v Peak, 600v Surge | 15/- |
| 16-16-8mfd. 450v Peak, 550v Surge | 15/6 |

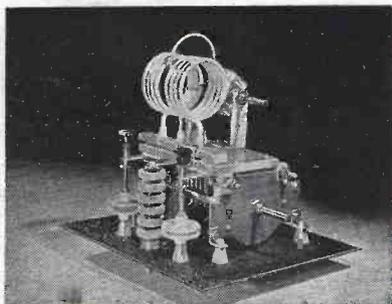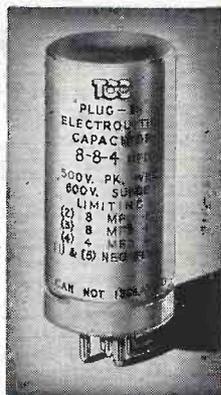PLUGS INTO STANDARD BRITISH 5-PIN VALVE-BASE



A complete P.A. TANK UNIT for maximum power 150 watts and 2,000 volts high tension. Complete as illustrated £6/13/-

BERRY'S FIRST AGAIN with the coloured chart of FREQUENCY ALLOCATIONS

as agreed at the Atlantic Conference

6/6 post free

All types of amateur equipment, including P.A.'s, Modulators, Exciters, Power Packs, etc., built to specification.

★ ILLUSTRATED CATALOGUE 3d. POST FREE ★

"ARNINE" AERIAL KIT

A folded dipole aerial for transmitting and receiving. Aerial span is calibrated for all popular short wave bands. Complete with 300 ohms feeder, polythene moulded connector and strain insulators. FDA20 £3/2/6
FDA40 £3/12/6

SIGNAL GENERATORS

| | |
|-------------------------------------|----------|
| Advance 100Kcs-60Mcs | £23/10/- |
| B. P. L. 100Kcs-30Mcs | £21 |
| Taylor 100Kcs-45Mcs | £15/10/- |
| AVO Test Bridge | £11 |
| AVO Valve Tester | £16/10/- |
| AVO Model 7 | £19/10/- |
| AVO Universal | £8/10/- |
| AVO D.C. Minor | £4/4/- |
| AVO Electronic Test Meter | £35 |
| "S" Meter suitable for AR88's... .. | £3/3/- |

LONDEX AERIAL Change-over Relay, working from 4 or 5v heater supply £3/3/-

MICROPHONES

| | |
|---------------------------|---------|
| MEICO M. Coil | £5/5/- |
| TRIX M. Coil | £6/10/- |
| RESLO M. Coil | £6/3/9 |
| Rothermel Crystal... .. | £5/5/- |
| Philips Sound Cell | £6/16/6 |
| Table Stand... .. | £1/17/6 |
| Ring | 12/6 |

XTAL-OSC PLATE Complete range of engraved nickel nameplates (30 different markings) improves the look of your rack each 6d.

"Q-MAX" Combined Absorption Wavemeter and Phone Monitor for checking harmonics and parasitics; and oscillators, doublers and power amplifiers for correct frequencies. All amateur bands covered by means of plug-in inductances. Price, with any one inductance 35/-
Extra inductances each 3/9

BERRY'S (SHORTWAVE) LTD

25, HIGH HOLBORN * LONDON * W.C.1

(OPPOSITE CHANCERY LANE) TELEPHONE: HOLBORN 6231