

Vol. 1 No. 12 - 1923, 1924


# The Wireless Constructor

6<sup>D</sup>  
MONTHLY

EDITED BY  
PERCY W. HARRIS

“Secret Broadcasting”  
Possibilities

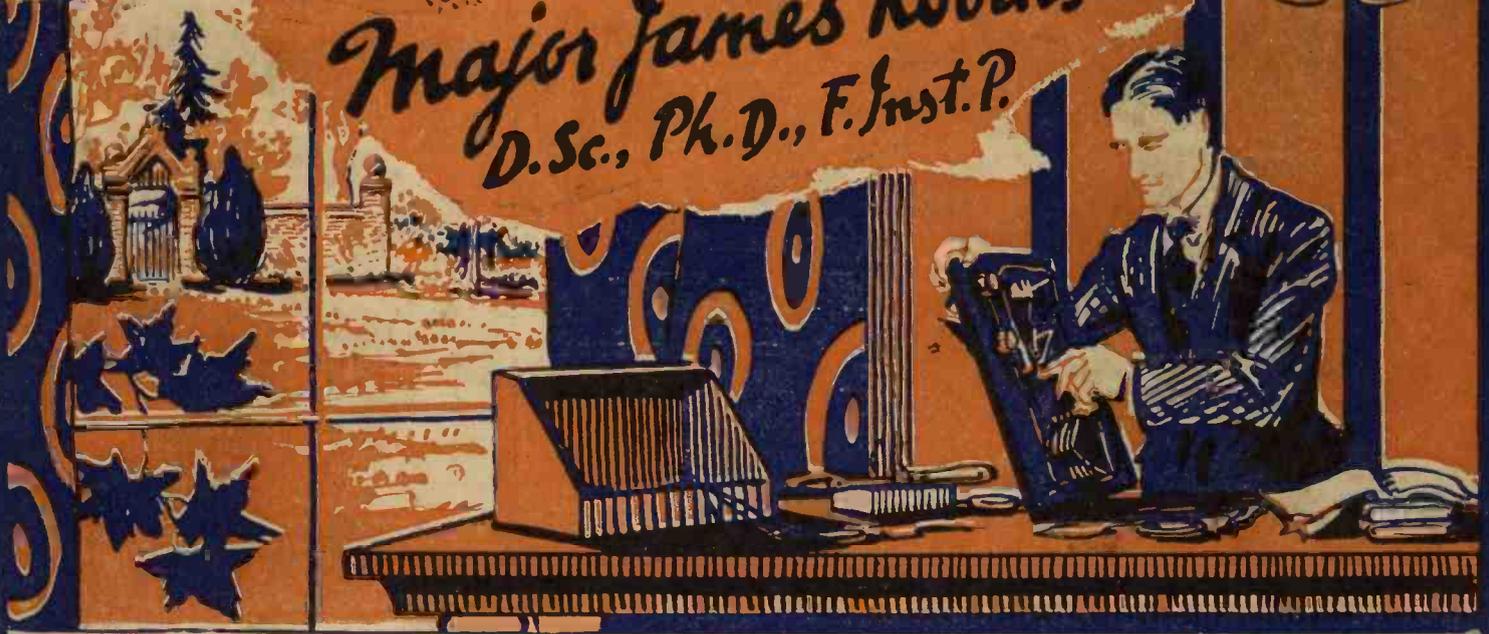by  
Major James Robinson  
D.Sc., Ph.D., F.Inst.P.



“WIRELESS”  
THE ONE-WORD WEEKLY

No. 1

OUT  
TO-DAY

2D.

FREE BLUEPRINT INSIDE

*Now on Sale*

## SPLENDID AUTUMN DOUBLE NUMBER

Contains articles of great interest and value to every radio enthusiast.

Major James Robinson, D.Sc., Ph.D., F.Inst.P., Etc., Director of Research at the Radio Press Elstree Laboratories, and late Technical Wireless Head of the Royal Air Force, writes on "Forthcoming Developments in Radio." Dr. Robinson's article is a brilliant forecast of the immediate developments in radio reception.


"Anode-Input Circuits," by John Scott-Taggart, F.Inst.P., A.M.I.E.E., shows the reader how he can obtain the greatest satisfaction from experiments on this fascinating subject.

Percy W. Harris, M.I.R.E., Editor of "THE WIRELESS CONSTRUCTOR," back from his tour in the U.S.A., describes some of his interesting experiences and investigations in the States. You cannot afford to miss it! 156 profusely illustrated pages.

**BUY YOUR COPY TO-DAY!**

PRICE

**1/6**

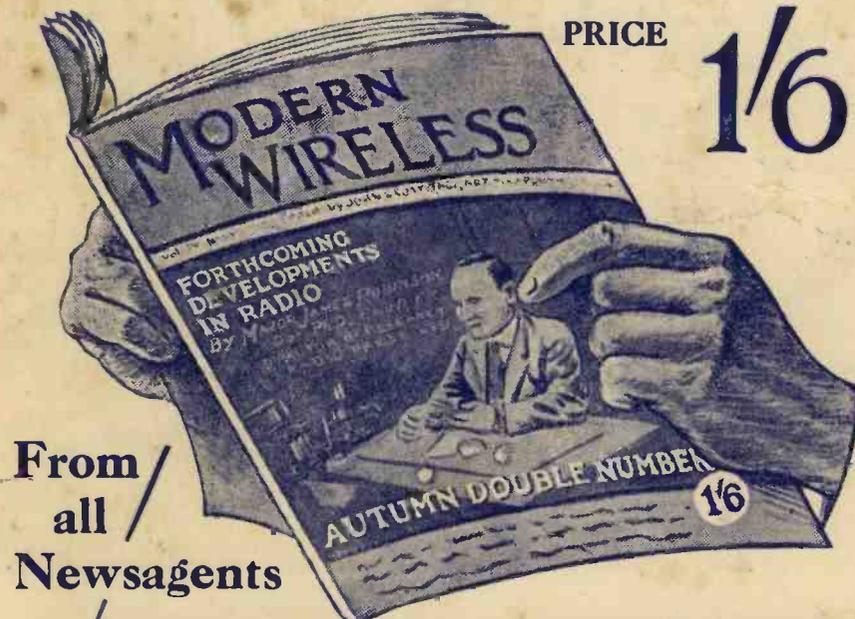

From  
all  
Newsagents



### SELECTION FROM — CONTENTS —

#### HOW TO MAKE:

- " A Simple Eight Valve Super-sonic Receiver. By W. H. Fuller.
- " The "Harmony Four" Receiver. By Percy W. Harris, M.I.R.E.
- " The "America Three" Receiver. By Stanley G. Rattee, M.I.R.E.
- " A Single Valve Reflex Set. By A. Johnson-Randall.
- " A Simple Crystal Receiver. By D. J. S. Hartt, B.Sc.
- Anode-Input Circuits. By John Scott-Taggart, F.Inst.P., A.M.I.E.E.
- Getting the Most from H.F. Valves. By J. H. Reyner, B.Sc., A.C.C.I., D.I.C.
- A Listener in New York. By Percy W. Harris, M.I.R.E.
- Receiving Daventry. By A. D. Cowper, M.Sc.
- Call Signs of Experimental Transmitting Stations.

# Modern Wireless

EDITED BY JOHN SCOTT-TAGGART, F.INST.P., A.M.I.E.E.

Barclays Ad.

# The WIRELESS CONSTRUCTOR

— Edited by Percy W. Harris —

Vol. 1. No. 12. **CONTENTS** OCTOBER

Receiving in "Dead" Spots By PERCY W. HARRIS, M.I.R.E.	1047	Solving an Aerial Difficulty By C. P. ALLINSON.	1072
Deputy-Director of Research Appointment of Capt. H. L. Crowther, M.Sc.	1051	Experimenting with the Low-loss Reinartz Receiver By G. P. KENDALL, B.Sc.	1080
Possibilities of Secret Broadcasting By Major JAMES ROBINSON, D.Sc., Ph.D., F.Inst.P.	1054	Appointment of J. H. REYNER, B.Sc., A.C.G.I., D.I.C., to the Staff of Radio Press, Ltd.	1087
A Simple Home-Constructed Single- Valve Set By A. V. D. HORT, B.A.	1058	A Simple Variometer-Tuned Crystal Set By PERCY W. HARRIS, M.I.R.E.	1088
Why We Built Daventry By Capt. P. P. ECKERSLEY.	1035	Mr. Gumblethorpe Builds His Set What are these Kilocycles? By J. H. REYNER, B.Sc., A.C.G.I., D.I.C.	1091 1097
On the Verge of New Developments By JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.	1070	"Wireless"—A New One-Word Weekly Hints and Tips on Metal Working	1104 1109



## CLARKE'S "ATLAS" FILAMENT CONTROLS

*The Aristocrats of Rheostats*

Patent No. 16,427

No wire to scratch, scrape, or wear out.  
No powder to pack and give flickering control.


Cuts out the guess work. Gives constant control and added life to valves. Saves its cost on current economy alone. Is a deciding factor in bringing in the distant stations.

50 Ohms Resistance      One hole fixing

Price only **6/6** each



External View

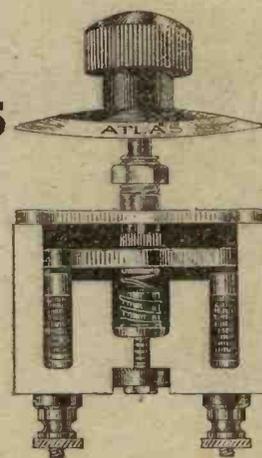

Sectional View

H. CLARKE & CO. (Mcr.) LTD. *Radio Engineers* Atlas Works, Old Trafford, MANCHESTER

Telephones—Trafford Park 683 and 793.

Telephones—"Pirtoid, Manchester."




## Ideals & Realism

The world is in a hurry now-a-days. In no age has man wanted to make realities of ideals so quickly. Radio is one example. Constant improvement, perpetual research—and the result to-day is worthily shown by the perfection of Sterling components.

While there is no such thing as finality in progress, it is nevertheless true that Sterling components built into a set will provide a radio reproduction of a quality that leaves but little room, if any, for improvement.

Sterling components—by test, by comparison, by reputation—are admittedly supreme.

Ask your Dealer for List No. 373D.

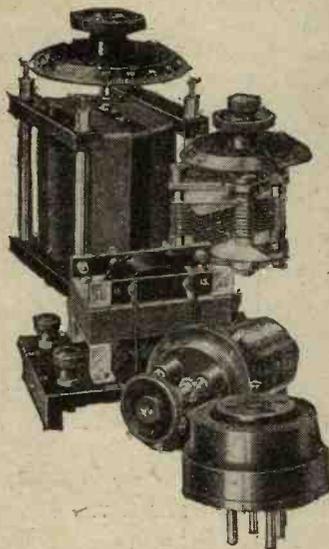

# for realism in radio — STERLING Components

Including:  
High Grade Variometers, Square Law Condensers, Interval Transformers, Reaction Units, Non-Pong Valve Holders, and every other conceivable component for the radio constructor.

## At your Radio Dealers

Sole Agents: THE MARCONIPHONE COMPANY, LIMITED  
210-212, TOTTENHAM COURT ROAD, LONDON, W.1

*Director of Research:*  
Major JAMES ROBINSON,  
D.Sc., Ph.D., F.Inst.P.  
*Scientific Adviser:*  
Prof. G. W. O. HOWE,  
D.Sc., M.I.E.E.  
*Advisory Editors:*  
Professor  
R. WHIDDINGTON,  
M.A., D.Sc., F.R.S.  
Prof. C. L. FORTESCUE,  
M.A., M.I.E.E.

# The : WIRELESS : CONSTRUCTOR

*Staff Editors:*  
E. H. CHAPMAN, M.A.  
D.Sc.  
A. D. COWPER, M.Sc.  
R. W. HALLOWS, M.A.  
G. P. KENDALL, B.Sc.  
A. JOHNSON-RANDALL,  
STANLEY G. RATTEE,  
M.I.R.E.  
J. H. REYNER, B.Sc.,  
A.C.G.I., D.I.C.

Vol. 1. OCTOBER, 1925 No. 12.

## Receiving in "Dead" Spots

A LOW-LOSS TWO-VALVE NEUTRODYNE RECEIVER

By PERCY W. HARRIS, M.I.R.E., Editor


VERY frequently I receive letters from readers who complain that the ordinary single-valve set (with or without a note-magnifying valve attached to it) will not give satisfactory results in their particular districts, which seem, from what they tell me, to be "dead" spots. They do not wish to invest in an elaborate multi-valve set, because of the cost of building, valves and accumulator charging. True, the reduction in price of dull emitter valves has considerably simplified the accumulator problem, but what is often needed is a set which will give them the results they require with the minimum number of valves. The set I am describing this month has been specially designed for use in "dead" spots, so that satisfactory telephone reproduction can be obtained from stations which are not heard at all in such cases. It will not work a loud speaker, even from the local station, but it "reaches out" in an astonishing manner, is quite reasonably selective and very simply controlled. For loud speaker work, any

of the one or two valve amplifiers described in THE WIRELESS CONSTRUCTOR from time to time, can be added, although generally if you want a set to work a loud speaker, it is just as well to build one incorporating the necessary note magnifying stages.

The circuit is given in Fig. 1, from which the more experienced reader will see that the set contains one high-frequency valve coupled by the tuned anode method to the detector valve, and neutrodyne to check the tendency to self-oscillation by the method first described by Mr. A. D. Cowper, M.Sc. It incorporates my own modification of the Cowper circuit using plug-in units of special design usually known in the trade as "neutrodyne units." The special feature of the receiver is the use of a low-loss coil with a semi-aperiodic coupling in the aerial circuit. This gives both selectivity and good signal strength.
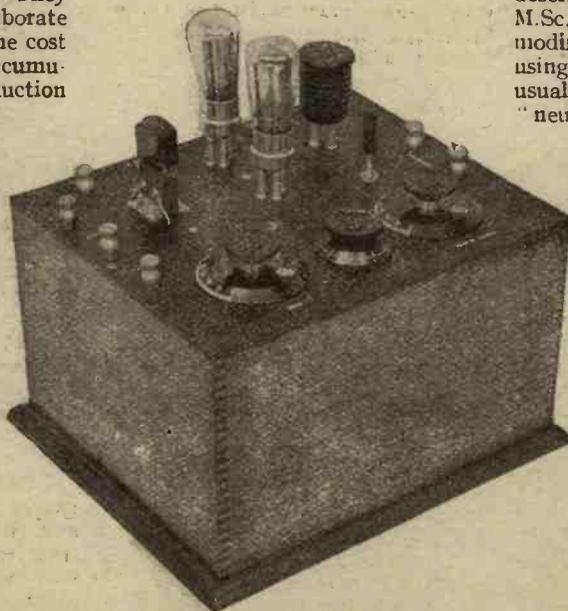
### Parts Required

The constructional work is very simple, all components being mounted on one 12 x 10 in. panel of suitable guaranteed material. I have used a Peto-Scott panel, but any of the guaranteed ebonite or Radion panels will do equally well. The other components required are as follows. The actual makes used are named, but other good makes can



The box is fairly deep owing to the length of the low-loss coil.



be substituted without loss of efficiency:—

One square law variable condenser .0005 $\mu$ F (Bowyer-Lowe).

One square law variable condenser .0003 $\mu$ F (Bowyer-Lowe).

One low-loss coil former with grooved supports with sixteen threads to the inch (Collinson's Precision Screw Co.). This should be 6 in. long by 3 in. diameter, and can be obtained ready made and wound from the firm mentioned.

Nine terminals.

One dual filament resistance for bright or dull emitters (McMichael).

Three sets of valve sockets.

One neutrodyne condenser (Gambrell).

One socket for plug-in coil (Magnum).

One shorting plug for same.

One .0003 $\mu$ F condenser with clip for leak (Dorwood.)

One 2-meg. leak (Dubilier).

One fixed condenser with clips .001 $\mu$ F (McMichael).


Radio Press Panel Transfers.

Suitable cabinet.
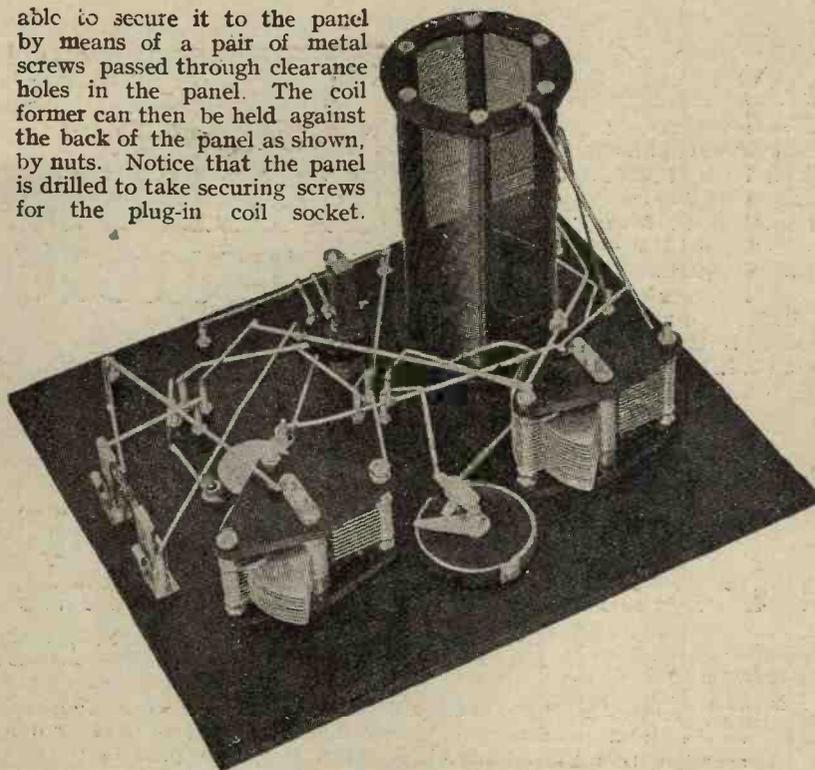
#### Constructional Work

You can obtain the low-loss coil former either ready wound or unwound. In either case it should be wound with 90 turns No. 22 enamelled copper wire in the grooves. At the 18th turn from one end make a tapping (quite a simple matter if you scrape the wire free of enamel at that point), and solder on a lead to it. The coil former has two holes drilled in the end by which you will be

able to secure it to the panel by means of a pair of metal screws passed through clearance holes in the panel. The coil former can then be held against the back of the panel as shown, by nuts. Notice that the panel is drilled to take securing screws for the plug-in coil socket.



A general view of the wiring, showing the connections to the coil.


This socket is necessary for adding the loading coil when it is desired to listen to 5XX. When wound as shown, with the turns indicated, the tuning range of the set will be from about 250 metres to well over 600. When it is desired to hear 5XX the short-

circuiting plug is detached from the panel and a No. 100 coil plugged in. This coil then comes in series with the low-loss coil. The aerial connection is now changed and taken to the end of this coil nearest the grid. A terminal is provided for this purpose so that the change-over can be rapidly effected.

On the shorter waves, with some aerials it may be found that the minimum wavelength is too high. If this is so, take off about fifteen turns from the coil at the end nearest the panel. The wiring diagram (free blue print) shows all connections clearly, and I would particularly direct your attention to the connections to the coil itself and to the soldering lugs of the condenser and grid leak mounting.
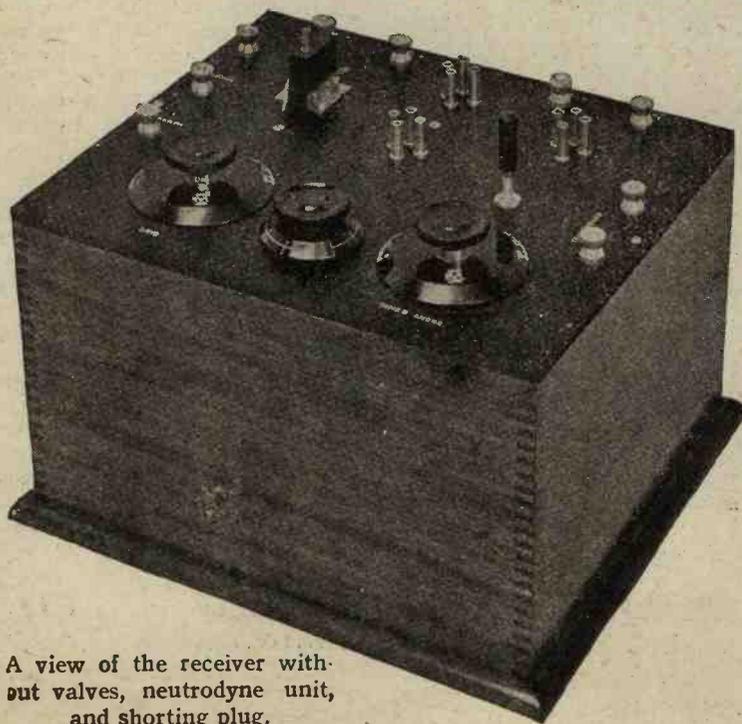
#### Neutrodyne Unit

In addition to the components named you will need for the broadcast band a plug-in neutrodyne unit, which can be of any of the well-known makes. The filament resistance controls both valves simultaneously, for which reason it is necessary to have two similar valves. Two of the general purpose valves will serve excellently here, whether they are bright or dull emitters. The filament resistance itself acts as an on-and-off switch, and a particular note should be made of the best working position when it is found.



A view of the receiver with out valves, neutrodyne unit, and shorting plug.

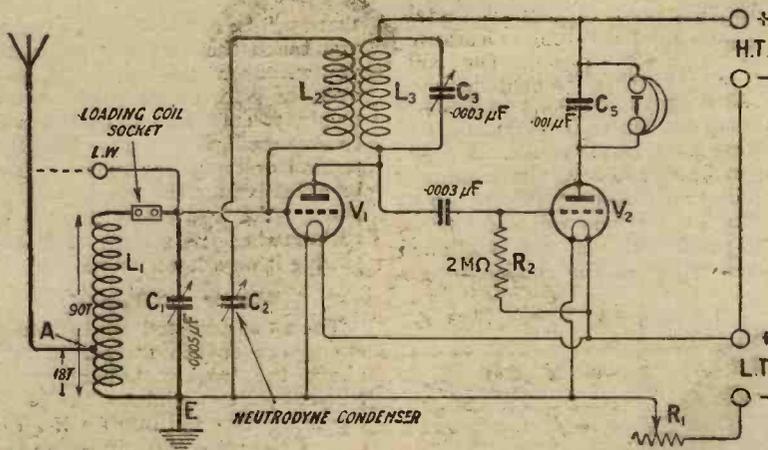


Fig. 1.—The aerial is joined to terminal L.W., and a coil is inserted in the socket, when it is desired to receive 5XX.

**Testing Out**

If you have no other set using batteries you will have to obtain either an accumulator or dry cells to supply the filament current. I would strongly recommend the use of an accumulator in preference to

dry cells even with the dullest of dull emitters. Your dealer will recommend a suitable accumulator for the particular kind of valve you buy. A high-tension battery of, say, 60 volts with tapings will be required for the anode supply

current, or, better still, use one of the many good high-tension accumulators now available.

**Adjusting the Neurodyne**

If you are not used to operating a set using the Cowper neurodyne method, you should read the following instructions carefully before attempting to listen in on this set. They are simple, but if you do not follow them, you may cause considerable annoyance to your neighbours, whereas properly carried out, the set will remain stable, and is not likely to give trouble.

First of all, conduct the tests either before or after broadcasting hours, so that your preliminary experiments do not upset your neighbours. Connect your aerial and earth, put the short-circuiting plug in position, turn your filament resistance to the off position, place two valves in their sockets and the neurodyne unit in its socket, and connect the L.T. battery to the terminals marked. Gradually turn the filament resistance on, and see whether the brightness is increased



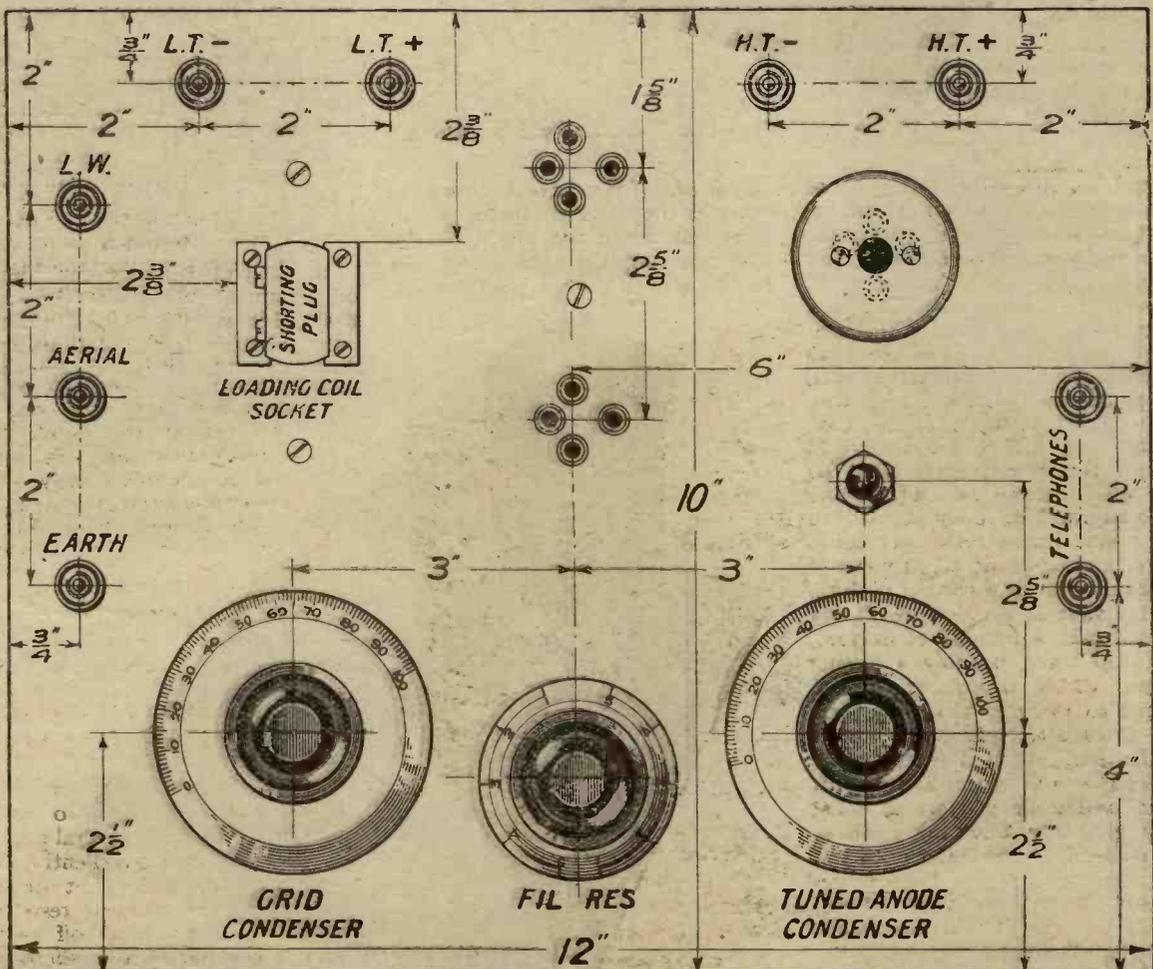


Fig. 2.—A half-size drawing of the panel layout, giving the drilling centres. Full-size Blueprint No. C.1021A may be obtained, price 1/6 post free.

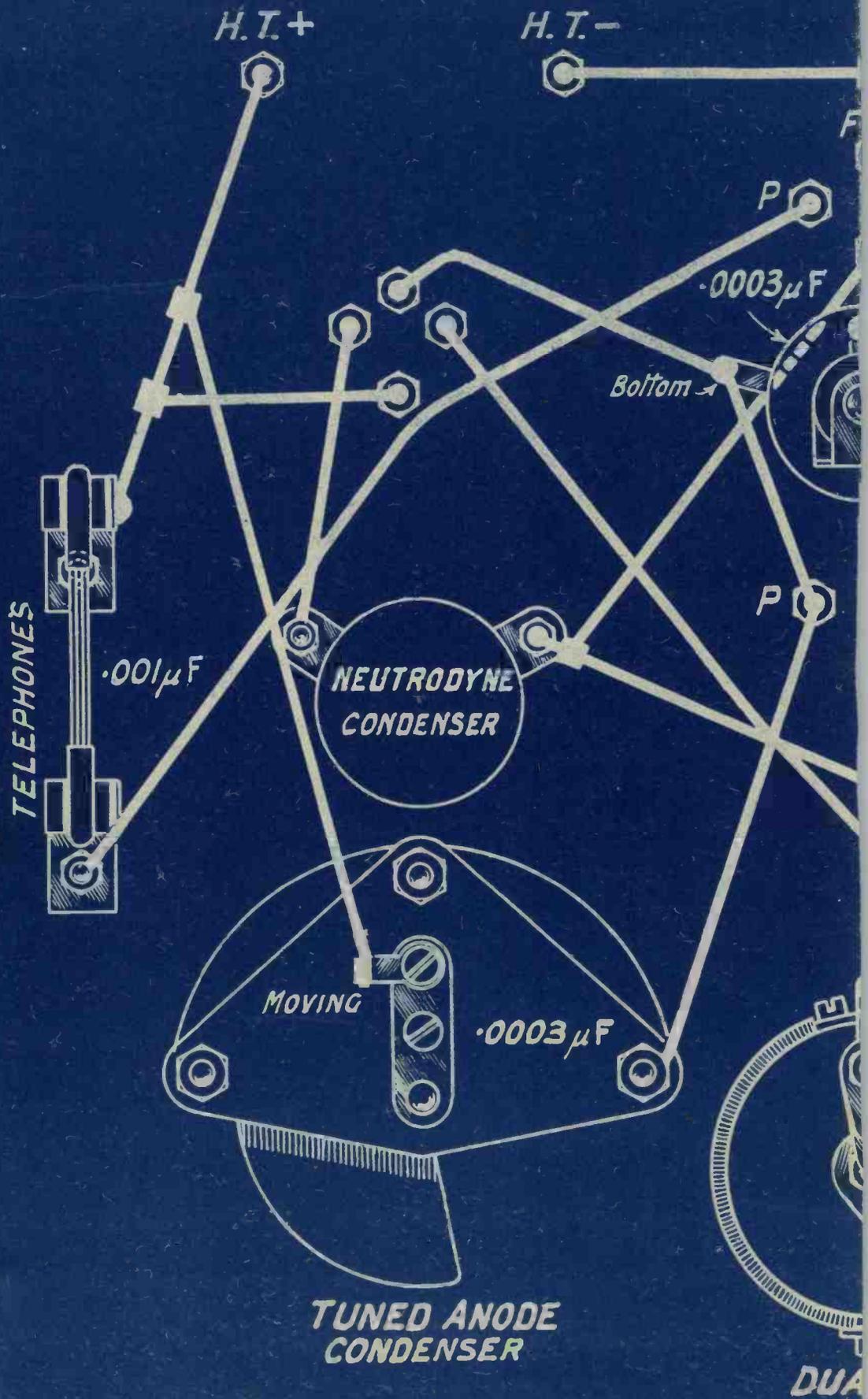THE WIRELESS CONSTRUCTOR" 2-VALVE NEUTRODYNE RECEIVER. B.P. No C1021B



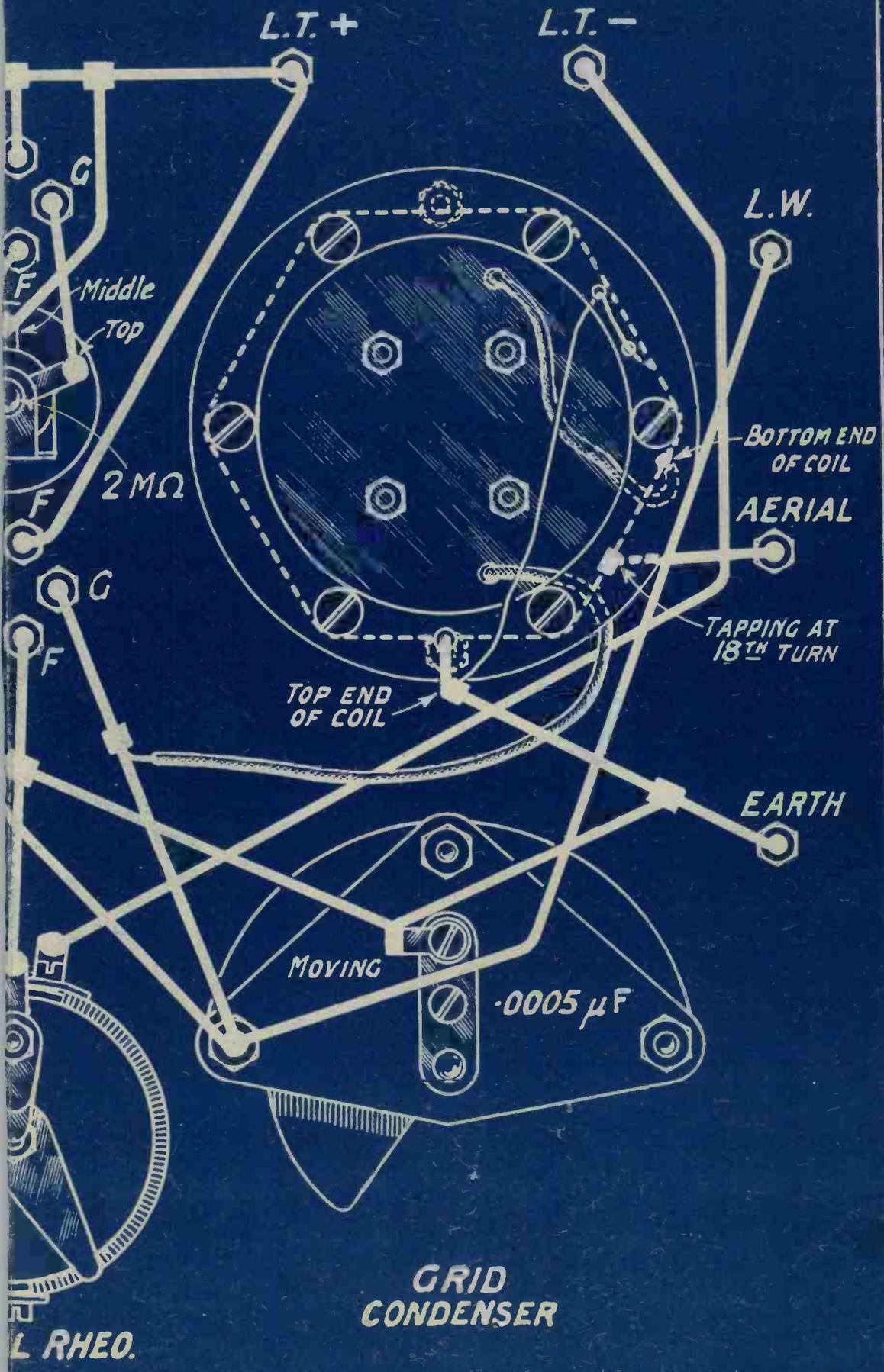

RADIO PRESS LTD.  
 BUSH HOUSE, STRAND, W.C.2.

Price 1/6.

W.C. VOL I. No 12.

or decreased as you turn the knob one way or the other. If you are using bright emitters you will need to turn the filament resistance about three-quarters of the way

A further slight turn will check this completely.

#### Test for Oscillation

Now turn your grid circuit tuning condenser to about 10, and swing your anode condenser again to make sure that you have checked oscillation. Repeat this at about 30 or 40, and you will find that at no point will you get oscillation when either of the condensers are

there will be a loud click both when you touch this terminal and when you withdraw your finger. If, however, in spite of all these adjustments, you still find yourself unable to stop oscillation, reduce the high-tension voltage slightly, as it may be excessive for the valves you are using. You can easily do this by withdrawing the wander plug and placing it on a lower value.


#### Wavelength Range

The set so adjusted will tune from about 250 or 260 metres to well above the broadcast band. To receive 5XX withdraw the short circuiting plug and insert a No. 100 coil, at the same time replacing the neutrodyne unit with a similar unit of the 5XX wave-band. You will probably find it necessary to re-neutralise the set for 5XX, which is done in a moment, by turning the knob slightly one way or the other. Notice, too, that for the reception of 5XX the aerial must be connected to the uppermost of the three terminals on the left, and not to the middle terminal, as is the case for the ordinary broadcast wavelengths.

When you are experienced, you can use the neutrodyne condenser as a delicate reaction control, although I do not advise you to do this until you are accustomed to using the set in its fully stabilised condition.
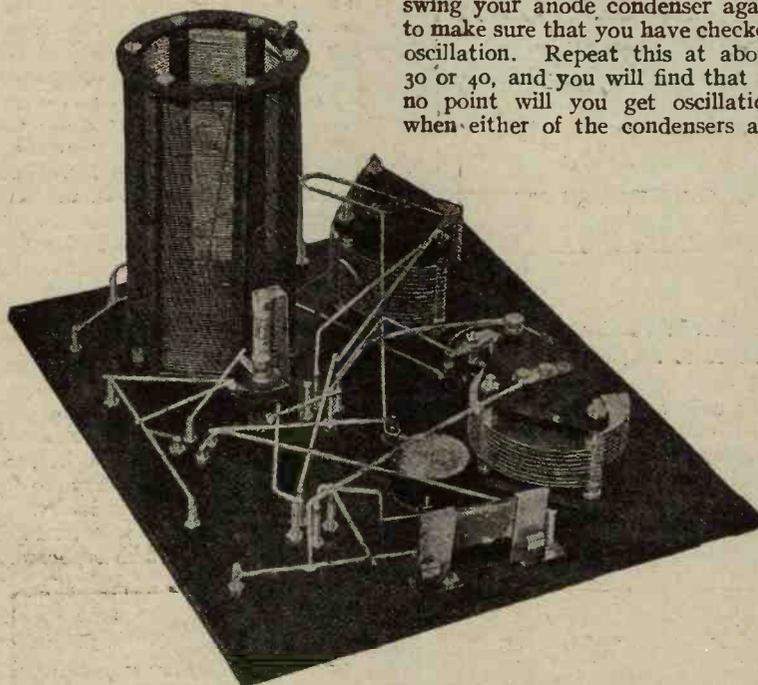
#### Results


In difficult summer conditions, on a number of tests at different times, this set brought in after dark, all of the main B.B.C. stations, and during daytime two or three other than the local station. Radio-Paris  
(Concluded on the following page.)



Showing connections to the neutrodyne condenser and valve sockets.

round, if not a little more. If you are using dull emitters, about the first half of the first segment of the dual rheostat will be needed. Now turn the valves off, and connect up the high-tension battery and telephones. The knob of the neutrodyne condenser should be turned in an anti-clockwise direction until its plates are at the widest separation—that is to say, until the knob is full out. Now set your grid circuit tuning condenser (that on the left) to about 20, and, leaving it so adjusted for the moment, turn the anode tuning condenser backwards and forwards, when you will probably hear at a certain position on the scale (a position which will extend over a number of degrees) a "plop" and possibly a hissing sound, which, if you are accustomed to using wireless sets, you will at once recognise as a sign of oscillation. Turn the condenser backwards and forwards over this band, and while you are so doing very gradually turn the knob of the neutrodyne condenser until you find the width of the band is decreased. Continue your adjustments of the knob, meanwhile swinging the condenser until the band has narrowed so much that there is barely a degree of the condenser which will show oscillation.

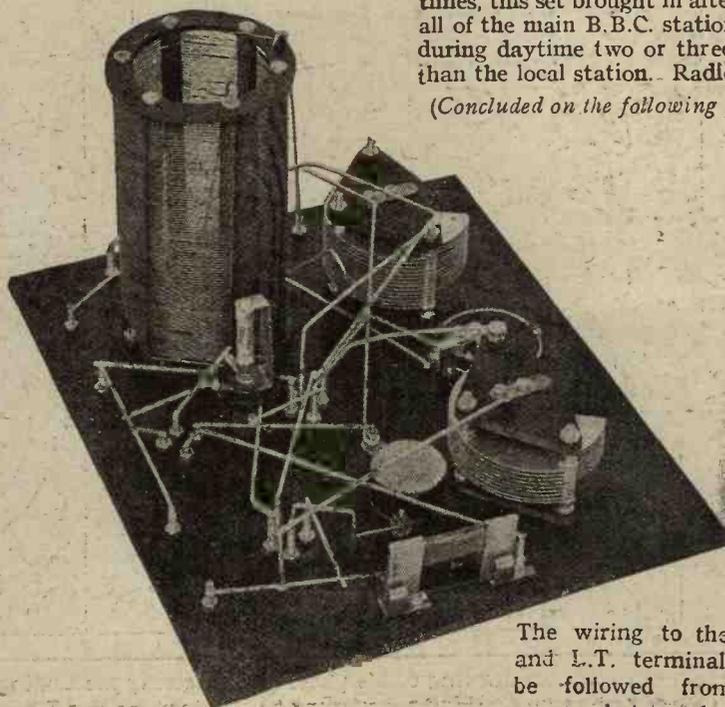adjusted. If you have doubts as to whether the set is oscillating or not, wet your finger and tap it on the uppermost of the three terminals on the left. If the set is oscillating,



The wiring to the H.T. and L.T. terminals may be followed from this photograph.

## Deputy Director of Research to Radio Press, Ltd.

### APPOINTMENT OF CAPTAIN H. L. CROWTHER, M.Sc.

READERS of THE WIRELESS CONSTRUCTOR will have seen, no doubt, our advertisement regarding the vacancy for a Deputy Director of Research for the new Radio Press Laboratories at Elstree, this post carrying a minimum salary of £1,700 per annum. The appointment has just been filled, the successful applicant being Captain H. L. Crowther, M.Sc., who, curiously enough, has just been appointed to the same

1891, and studied at the University of Birmingham when Sir Oliver Lodge was Principal. His special subjects were physics, mathematics, engineering and chemistry, and in 1912 he received the B.Sc., with Honours, and later obtained the degree M.Sc. for research work. Before the War he held an important scholarship for research work, while from as far back as 1911 he was a prominent amateur wireless experimenter, his transmitting and

Captain Crowther is an expert on valves, and is a member of the Valve Committee of the Radio Research Board. He has also served on the Wireless Board. A number of his inventions were extensively used during the War, and many, of course, are still in use. For these he has received awards from the Air Inventions Board.

The appointment of Captain Crowther will give a further indication of the great importance we attach to the new laboratories which will serve the Radio Press journals.

### Receiving in "Dead" Spots

*(Concluded from the previous page)*

and a German station were also heard in daylight and, of course, after dark numerous Continental stations came in at excellent telephone strength. The use of fairly loosely coupled semi-a-periodic aerial coupling cuts down a good deal of the interference which frequently comes from atmospheric and from spark jamming in those cases where the listener is situated close to the sea shore. For those who require still simpler sets to construct, the low-loss coil can be omitted entirely, and the socket for the loading coil used for a plug-in coil of the shorter wavelength band. This will also give good results, but you will not get the selectivity obtainable with the arrangement indicated.



Capt. H. L. Crowther, M.Sc., the newly-appointed Deputy Director of Research.

position as that held by Dr. Robinson (our Director of Research) under the Air Ministry.

Captain Crowther is at present in charge of the Wireless Research and Design Laboratories of the Royal Air Force, and it is a coincidence that the two successive holders of this position should have been appointed to the Elstree Laboratories. Dr. Robinson is now with us, of course, and Captain Crowther will join the Company about September 15.

Captain Crowther was born in

receiving station being probably one of the best known in the country. In 1914 he joined a Special Wireless Corps, and at the beginning of 1915 received a commission in the Royal Naval Air Service. He was later transferred to the wireless experimental staff at Eastchurch for the development of wireless in aircraft. For the last eleven years Captain Crowther has been engaged entirely on radio research and design work for the Royal Air Force, and has now risen to the highest position available to him.

## " WIRELESS "

THE ONE-WORD WEEKLY


No. 1 OUT TO-DAY  
(September 15th)

DO  
NOT  
FAIL  
TO BUY  
A COPY  
NOW

2<sup>D</sup>. PRICE 2<sup>D</sup>.
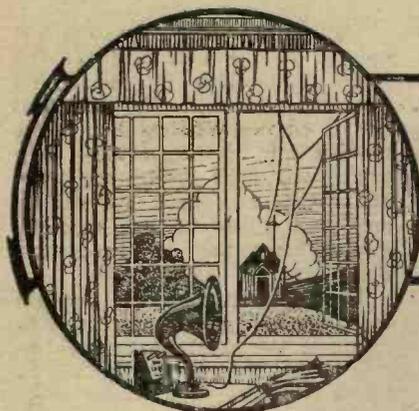
#### ERRATUM

Owing to a printer's error, the price given in the advertisement of Messrs. Gambrell Bros., Ltd., in our last issue was incorrect, and should have been as shown in their advertisement on page 1068.



## What Two Readers Think of the "Twin-Valve" Receiver

*Originally described in the January issue of this magazine, complete details of this receiver are now available in Radio Press Envelope No. 10*

SIR,—Having made up the Twin-Valve Set as described by Mr. John Scott-Taggart in the January issue of THE WIRELESS CONSTRUCTOR, I wish to congratulate him on evolving such a fine circuit, as the results obtainable are remarkable. I have followed the design to the letter, the only alteration being an R.I. transformer in place of the Success, the primary and secondary connections for which I find the same. Results obtained may interest you. The set was completed just a few minutes before 2LO closed down, and the volume obtainable from this station was tremendous. Using an Ultra loud-speaker, music could be heard all over the house. Madrid was the next station received, and was comfortably audible in a large room on the loud-speaker.

The next day I received Belfast, this being the only B.B.C. station working in the afternoon, also 5NO.

The next morning at 1.30 a.m. I tuned in WGY, which station was received at about R6 on phones and audible 6 ft. from the loud-speaker. Subsequently I received KDKA on 326 metres. One other station, 5AF, on 425 metres, has been heard, but so far I have not been able to identify where this transmission came from, although the announcer spoke English.

Thanking you once again for this valuable circuit, by far the best of many I have tried.—Yours faithfully,

J. H. ROSS.

Isleworth, Middlesex.

\* \* \*

SIR,—I think you may be interested to hear the results obtained with the "Twin-Valve Reflex Receiver," described in the January number of THE WIRELESS CONSTRUCTOR by Mr. John Scott-Taggart. It is a remarkably sensitive set, and receives 5XX without aerial or earth. In this case the aerial was connected

to earth outside the house, about 10 ft. away from the set. The reception was at moderate phone strength using a 200 coil in the aerial and a 150 for reaction, reversed.

On an indoor aerial consisting of 20 ft. of twin flex running along a passage, 5XX comes in at comfortable loud-speaker strength, and London, Radio-Paris and Newcastle quite loud on the phones.

castle, Bournemouth, Radio-Paris and Petit Parisien are received at good loud-speaker strength.

All other main stations and relays come in easily on the phones, and, of course, dozens of Continental ones. I am also agreeably surprised to find that the set is almost as easy to handle on the shorter waves as on the long ones. I have had a great number of amateurs on wave-lengths varying from 125 to 300



Much to the relief of the insurance companies, with whom he was insured for £100,000 (and also a separate insurance for another £10,000) during his recent visit to America, Mr. Percy W. Harris has now returned to his editorial chair at Bush House. He has, since his return, been engaged in preparing a remarkable series of articles for the new weekly paper "Wireless" which he is editing and the first number of which is published to-day (September 15).


With an outdoor aerial 100 ft. long and about 26 ft. average height, the following stations are obtained with great regularity:—5XX, too loud on the loud-speaker (a Brown H2) to be comfortable, and easily heard all over the house (I usually detune to a moderate strength); London, New-

metres. I am delighted with the receiver and feel that it is only right to let you know how satisfied I am.

Wishing your excellent publications every success.—Yours faithfully,

HAROLD C. LEE.

Herne Bay.

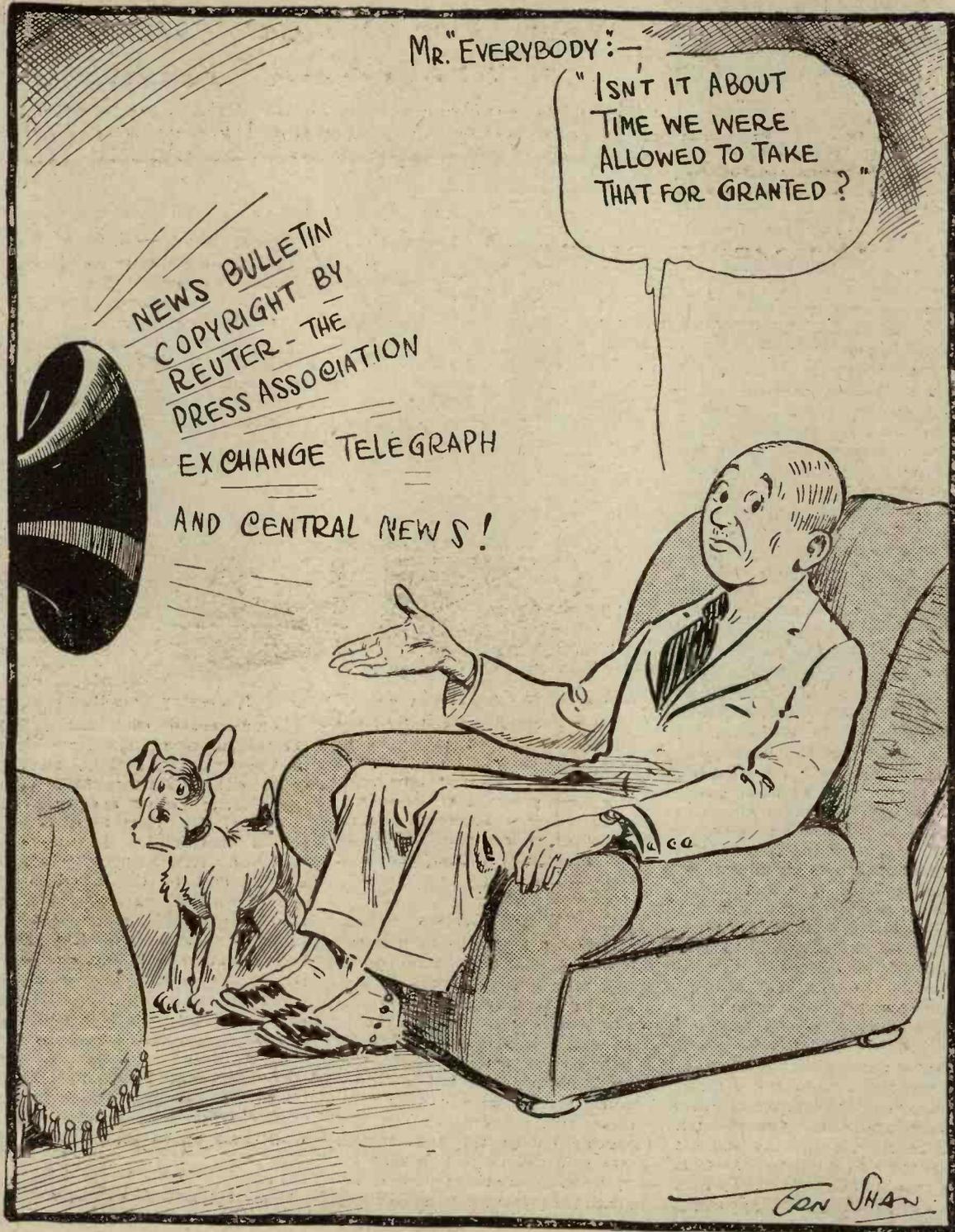

What do you think about it?

# POSSIBILITIES OF SECRET BROADCASTING

By

**MAJOR JAMES ROBINSON,**  
D.Sc., Ph.D., F.Inst.P.

DIRECTOR OF RESEARCH  
TO RADIO PRESS LTD.



**A** COMPANY has recently been formed for the purpose of Secret Broadcasting. The aims of this company are to have a system of transmitting wireless programmes which can only be received by people who are in possession of apparatus and information which will enable them to receive such programmes, and thus to found a healthy commercial undertaking. The present methods of broadcasting make reception of the programmes open to all. The object of secret broadcasting is to place a lock on the programmes which can only be opened by a special key which will have to be bought. This raises the very interesting problem of national policy as to whether it is in the best interests of the community to depart from the present system of monopoly. The discussion of this problem will be very long drawn out, and will be entered into by both technical and non-technical people. It is intended, to give some idea as to whether it is technically possible to have a system of secret broadcasting.

## A Limiting Factor

A large number of patents have been granted for systems of secret broadcasting; and some of them are very ingenious. The object is to make it exceptionally difficult for anyone who is not in possession of knowledge of the methods used to construct or adjust apparatus to receive the programmes. It can safely be said that any system proposed up to the present could be disentangled by the most highly skilled engineers, but by making a system sufficiently complicated and difficult, very few would trouble to attempt to solve the various secret

devices. Again, if a system were of such complication that it required very highly skilled engineers to discover it, the effect on the commercial side of a secret broadcasting company would be negligible. It should be remembered, however, that what is complicated to-day may become commonplace and simple to-morrow.

## "Wired Wireless"

There are proposals to transmit programmes along electric power lines, and it is very possible that broadcasting may develop in this way, though not to the complete detriment of the present form of wireless broadcasting. Such proposals, however, do not assist towards secret broadcasting, for unless special complications are introduced into the transmission system, it will be just as easy for anyone to receive these programmes as with the present wireless methods provided the electric power supply is installed in one's house. Again, if some uncommon form of radiation is used, such as for instance very short wireless waves of, say, one-tenth of a metre wavelength, secret broadcasting would not be effected.

## Necessary Conditions

Some special complications in the transmission system, and thus in the receiving system, are required either with wireless, or with the electric power lines, or else special electric lines must be installed merely for broadcasting purposes. Restricting ourselves to wireless and to the allied problem of transmission along existing electric power lines by systems usually called wired wireless, there is no doubt as to the technical possibility of introducing sufficient complications into the transmitting and receiving apparatus as to make broadcasting secret except to the most highly skilled engineers. It is obvious that it will be much more difficult to maintain the receiving apparatus in good working order with these added complications.

## Methods Available

The methods which have been proposed fall generally into the following groups:—

1. Methods which use more than one wavelength for transmission, or which vary the wavelength irregularly.
2. Methods which introduce other noises into the transmission

which can be removed by special devices at the receiving end.

3. Methods which completely change the form of sounds during the transmission so as to be unintelligible with ordinary receiving apparatus. This is done by transmitting a note of frequency 1,000 as a note of some other frequency.

4. Combinations of some or all of the other three methods.

It is impossible here to describe every method which has been proposed, but a number of examples will be given.

**Changing Wavelength Method**

A number of methods for secret broadcasting have been proposed where the wavelength is changed at the transmitting station and at the receiving stations in the same way and at the same time. This

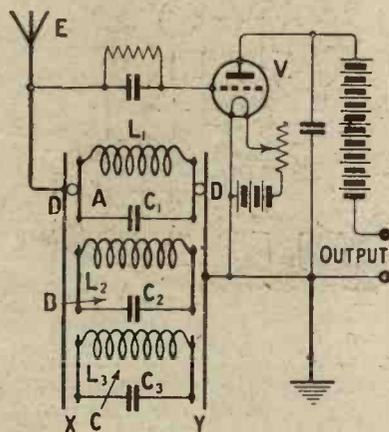


Fig. 1.—Illustrating the principle of the Anstey system.

involves the difficult feat of synchronism, but although difficult it is quite possible of achievement. Some of the methods involve a number of fixed wavelengths to which the transmitter and receivers are tuned, and a switch at each station to change the wavelengths at the same instant, the duration of transmission on each wavelength and the order of occurrence of the wavelengths being known only to the people who have paid for the information. Other methods involve a continuous variation of wavelength, the changes at the transmitter and all the receivers being effected at the same rate and in the same way. In these methods the rate of change of wavelength can be made regular or irregular by the use of cam devices or by the use of variable condensers which are made to rotate at a uniform rate, but the plates of which are cut in some irregular manner.

A method of changing the wave-

length in steps will be briefly described. This is the invention of R. W. Anstey, and is interesting in addition as it brings in the features of the second group, transmitting objectionable noises on one of the wavelengths not in use. The object of this is that it is easy for anyone to discover the wavelengths in use, but not so easy to find out the order in which they are used. Thus any eavesdropper may obtain a small part of the programmes, but for most of the time he will not be able to avoid these noises.

**Two Transmissions**

Two transmitters are required for this system, both capable of transmitting on three wavelengths the same for each. One transmitter is used for sending out the programmes, and the other for sending out noises, the two always working on different wavelengths. Suppose the wavelengths are 380, 400 and 420 metres respectively, the order in which these are used is different for the two, thus, when the programme is on 380 the noise may be on 420, when the programme is on 400 the noise may be on 380, and so on. In addition, each transmitter has a special switch which will be described shortly.

Each receiver is also in two parts, one part with three separate circuits, and the other for a special purpose.

**Switching Arrangements**

In Fig. 1 is shown a diagram of a simple valve receiving circuit, with the three tuned circuits A, B and C connected through a special switch XY to the grid circuit. In these switches there are metal balls D to join the outer portions to the inner portions, which are in three parts, one part joined to each circuit. It will be seen that the position of the balls determines which circuit is being used.

The switches consist of inclined planes (Fig. 2) down which the metal balls D can roll. Provided all switches are identical and are inclined at the same angle to the horizontal, the balls, if again identical, will roll down in the same time. All that is now required is for all the balls at all stations, including the transmitting station, to commence rolling at the same time. It is for this purpose that there must be another receiving circuit.

**Synchronism**

A central station is arranged to transmit short powerful signals at

regular intervals which are picked up by the special receiving circuits. These signals are made to operate a relay which turns a ratchet wheel one tooth at a time. This wheel is arranged to carry a number of balls, and on being moved one tooth, one ball is set rolling down the inclined plane. Special arrangements are also made for the balls to be brought back into the toothed wheel. In this way a ball is set rolling at the same time at all receiving stations and also at the transmitting station.

It will be obvious from this description that secret broadcasting can be effected. The technical difficulties are not slight, and the initial adjustment of a receiving station and the maintenance of it will involve much more expense than in the case of ordinary broadcast reception. It will be difficult for any unauthorised person to hear programmes perfectly, and his difficulties can be increased considerably by changing the order of the wavelengths, and the lengths of each transmission on each wavelength from time to time.

A great disadvantage of this system is that three separate wavelengths are used, this taking up too

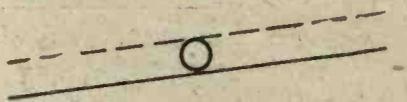


Fig. 2.—The method of synchronisation adopted in the Anstey system depends upon the rolling of identical balls down similarly inclined paths. (See D in Fig. 1.)

large a band of wavelengths when there are so many calls on wavelengths for various purposes.

**Second Method**

An illustration of the second group of methods has already been given in the foregoing description of Anstey's system. A much simpler way than his of effecting the introduction of objectionable noises at the transmitting station and of removing them at each authorised receiving station, is described in a British patent of the Marconi Co. (No. 198,368). In this case a normal form of telephony transmission is employed, and the objectionable noise is introduced into the microphone circuit. Thus there is transmitted the usual telephony intermingled with a noise so as to make it impossible or at least unpleasant to receive a programme when using ordinary receiving apparatus. All that is required, however, is a special

filter at the receiving station to take out the disturbing noise. This may have a frequency above that most commonly employed in speech or music, say, 5,000. At the receiving station a "low pass filter" is required which will allow all frequencies below 5,000 to pass but which rejects all frequencies above. Again, the disturbance may have a frequency below those common in speech and music, say, 25. In this case a high pass filter to reject all frequencies below 25, and to allow all frequencies above to pass, is required. Similarly the disturbing noise may have a frequency inside the audible range, when another type of filter circuit

can be listened to without much trouble.

**Speech Inversion**

The third group of methods is very ingenious, depending on the device of actually changing the speech or music frequencies for transmission. The simplest method of doing this is to invert the speech frequencies. Speech and music consist of an arrangement of different frequencies from about 25 to about 10,000, the frequencies being of different intensities, usually being more than one frequency at any time. Each sound has a particular combination of frequencies, each being of a definite intensity. For instance, middle C in music has a

frequencies, and this consists of the frequencies, 2,256, 2,512, 2,768, 3,024, etc. Now, if we can reject the upper side band, which is possible by the use of a low pass filter, we are left with the lower side band, which is a combination of frequencies entirely different from that of our original middle C of the piano. This combination of frequencies will not be recognisable as a note of the piano at all, and if it is used to modulate a carrier wave it will be completely unintelligible when received on the ordinary broadcast receiver. However, at the receiving station it is possible to obtain the original piano note in the following manner. The process of modulation is

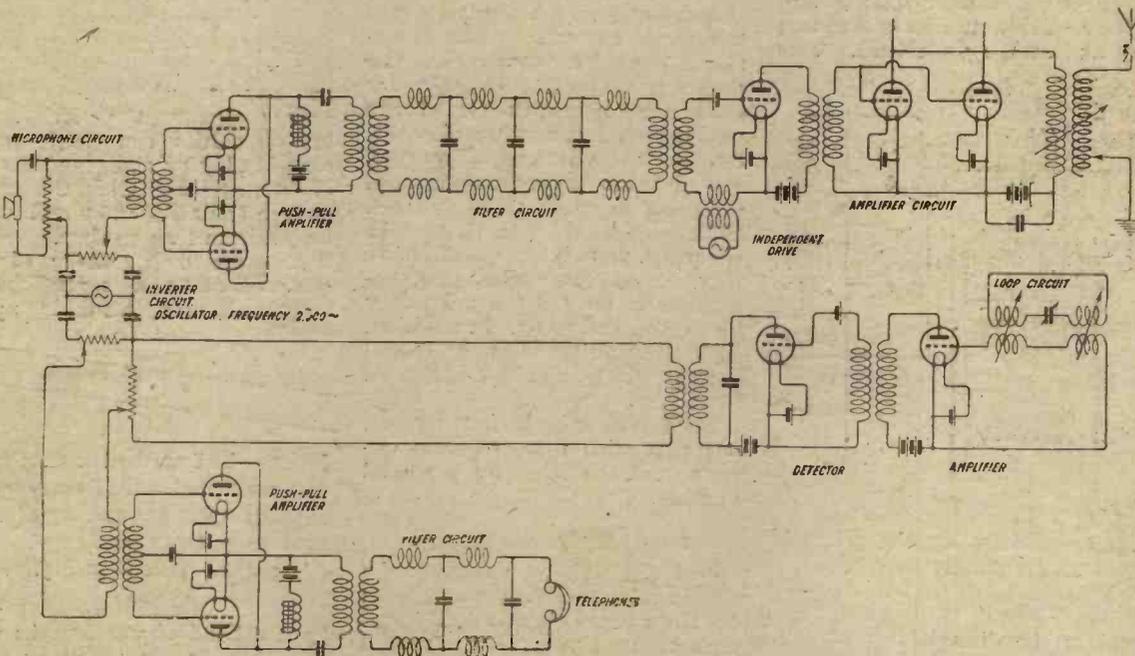


Fig. 3.—The Western Electric Company's system makes use of a "speech inversion" arrangement.

must be used to eliminate a narrow band of frequencies including that of the disturbance.

**Additional Apparatus**

With such a system of secret broadcasting, all that is required in addition to the ordinary receiving apparatus is a number of filter circuits, so that the correct filter can be used from time to time. It will be necessary with this system to change the frequency of the disturbance periodically, as the complications introduced are not so serious as in the first case described. This type of transmission has, however, the advantage that only one wavelength is required for each broadcasting station. Further than this, the receiving apparatus is very flexible, and stations on various wavelengths

frequency of 256. When struck on the piano, other frequencies accompany it, called harmonics, which are 2, 3, 4, &c., times the fundamental. These harmonics have not the same intensity. We thus have frequencies, 256, 512, 768, 1,024, etc., present in middle C struck on the piano. Now suppose we have a continuous wave of, say, 2,000 frequency and modulate this by our middle C. The following frequencies will result: 2,000 less 256; 2,000 less 512, etc., i.e., 1,744, 1,488, 1,232, 976, &c., which is called a side band resulting from the difference in frequencies of the continuous wave and the tone frequencies.

**Sideband Suppression**

There is also another side band resulting from the sum of the

reversed, and the received frequencies are used to modulate a continuous wave of 2,000. Again two side bands result, the lower one being 2000 less each of the frequencies which results in our original combination of 256, 512, 768, 1,024, etc. The upper side band consists of 3,744, 3,488, 3,232, 2,976, etc. If we can eliminate this upper side band we are left with our original piano middle C.

This example illustrates the principle of the inversion of speech or music. The inversion gives an entirely different series of frequencies for transmission, and with ordinary receiving apparatus a jumble of sounds would be heard.

This principle has been proposed by the Western Electric Company for secret broadcasting purposes. Inversion is, of course, the simplest

possible form. In this form it would be comparatively easy for many listeners to build additions to their ordinary receiving sets to re-invert the inverted speech. Numerous complications can be added to the simple method of inversion. One method is to divide

**Probabilities**

Sufficient descriptions of a few systems for secret broadcasting have been given to show that it is technically possible to transmit programmes which can only be received by listeners with the correct receiving apparatus.

and of the programmes, will be very high. Thus from every point of view a scheme of secret broadcasting will be much more costly for the subscriber than the present system. Many people would be entirely shut out from the benefits of broadcasting purely from the question of expenditure. The influence on crystal users would be particularly bad, and the introduction of secret broadcasting would make crystal sets things of the past. The people in this country would never tolerate any tendencies to make broadcasting a luxury for the few. It is essential to keep it democratic.

**Wavelengths Available**

Another very serious point is the question of the number of wavelengths available. There are so many claims on the facilities of wireless that it is absolutely essential to exercise the strictest control in the allocation of wavelengths. Were one company allowed to commence a system of secret broadcasting, other companies would wish to introduce their special systems, and in a short time there would be a jumble of wavelengths, particularly as some systems of secret broadcasting require more than one wavelength.

**Present System Economical**

On the other hand, the present



One of the temporary buildings being erected for the Radio Press laboratories at Elstree.

the acoustic band of frequencies into a number of parts and to invert each part. The essential band of frequencies lies between 25 and 5,000. This might be divided into the three bands, 25 to 150, 150 to 900, and 900 to 5,000, and each band inverted in turn. The divisions into bands of frequencies can be effected by the use of the filters already referred to. In this case it is a much more complicated matter to re-invert the separate bands and to combine them to be equivalent to the original speech or music.

A still further complication can be introduced, which is to divide the acoustic frequency range into bands, and to mix up those bands after inversion.

**The Hammond System**

Another system of secret broadcasting has been proposed by John Hayes Hammond. This involves the use of a carrier wave of comparatively short wavelength, which is modulated by a supersonic frequency. The telephony modulations are applied to the supersonic modulations; this itself makes it more difficult to receive telephony. Much greater secrecy can be obtained by varying the frequency of the supersonic modulation, and if this were applied for the purposes of secret broadcasting the supersonic frequency would be varied periodically or continuously, according to a pre-arranged plan.

**Will it be Tolerated?**

Broadcasting is meant for the man in the street, and he is likely to ask "whether secret broadcasting is in his interests."


Many objections to any scheme



Mr. Scott-Taggart (pointing) and Dr. Robinson inspecting the concrete foundations for one of the buildings at Elstree.

of secret broadcasting are apparent from the preceding description. The cost of the listener's initial installation will be high, and, of course, also the weekly expenditure on keeping the apparatus in good working order. Again, the expenditure of a secret broadcasting company, in order to keep all subscribers informed of the particular codes or keys as they change periodically,

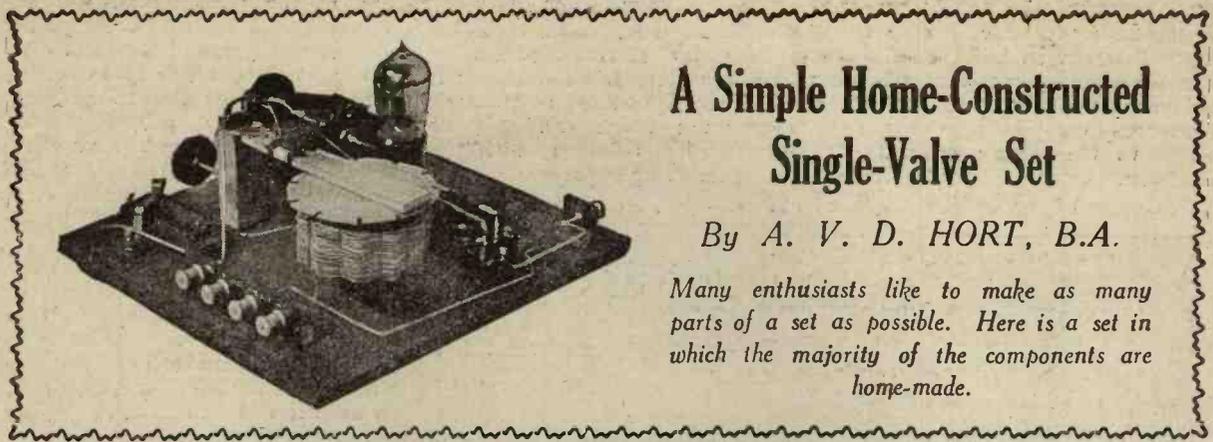broadcasting system is economical in the use of wavelengths, although the system might be made even more economical. Thus, though secret broadcasting is technically possible, there are so many disadvantages, from the listener's point of view, as well as nationally, that there is very little prospect of such systems being substituted for our present one.



# A Simple Home-Constructed Single-Valve Set

By A. V. D. HORT, B.A.

Many enthusiasts like to make as many parts of a set as possible. Here is a set in which the majority of the components are home-made.

RECEIVERS in which the components used are mounted on a board are attractive in many ways, when appearance is not a serious consideration. Cabinets and large ebonite panels are dispensed with, thereby reducing considerably the expense involved in construction, while there is no reason why a receiver mounted on an open board should not be fully as efficient in operation as a cabinet

coils is incorporated, which gives what is in effect practically a "vernier" movement of the moving coil. At the same time, if the valve is accidentally set into a state of oscillation, the reaction coil can be lifted well away from the aerial coil in a moment, so that the minimum of interference is caused to others. The constructional work involved in making this coil-holder is extremely simple, and no elaborate tools are required for constructing this or any other part of the receiver.

These components are set up in clips on a small ebonite panel, by which means they are easily attached to the baseboard.

Seven 4 B.A. terminals.

One valve-holder for board mounting, with connections to the sockets brought out through the sides of the holder.

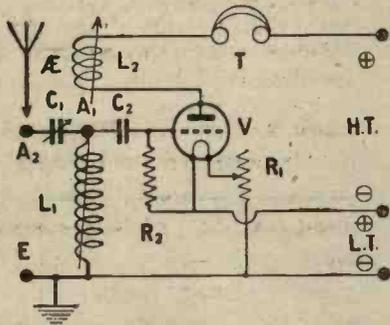


Fig. 1.—The condenser  $C_1$  may be used in series or parallel with  $L_1$ .

receiver designed to be a handsome piece of furniture for the drawing-room as well as an electrically sound instrument. Additional advantages from the point of view of the beginner or experimenter are that the wiring of the circuit is apparent at a glance, and that alterations in the connections can be easily carried out, since every part of the receiver is readily accessible.

### The Circuit

The circuit used in the receiver to be described, as will be seen from the diagram, Fig. 1, is that of a single detector valve, with reaction on to the aerial. As this method of obtaining reaction effects is capable of causing considerable annoyance to other listeners if carelessly handled, a form of control of the degree of coupling between the reaction and aerial

### Bought Components

While constructional details and diagrams are given for making several of the parts of the set, it is recommended that certain components be bought ready made, as more satisfactory results are likely to be achieved by this means. The purchased components should be of good quality, since they can then be relied on to function properly in this receiver; also they will be available to give further good service if it is subsequently decided to incorporate them in a more elaborate set.

The components to buy are as follows:—

One .0005  $\mu$ F variable condenser with ebonite end plates. This may be either the square-law or standard pattern. The one used in the set shown was one which the writer happened to have by him.

One .0003  $\mu$ F fixed condenser (L. McMichael, Ltd.).

One 2 megohm leak (L. McMichael, Ltd.).

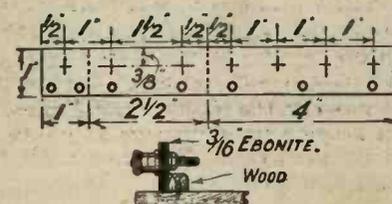


Fig. 2.—The terminal strips are made from one piece of ebonite.

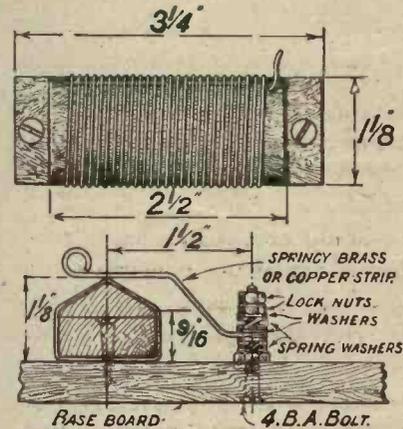


Fig. 3.—Details of the filament resistance.

The other parts which will be required are:—

One board, 10 in.  $\times$  10 in.  $\times$  1/2 in. That used by the writer is the bottom of an old Fullerphone case, which is impregnated with damp-resisting material.

Ebonite strip, 7 1/2 in.  $\times$  1 in.  $\times$  3/8 in. 2 ozs. of 26 S.W.G. d.c.c. copper wire.

4 yards of 24 S.W.G. bare Eureka resistance wire. This is for use with bright emitter valves and a 6-volt accumulator. If dull emitter .06 valves and a 4-volt battery are to be used, 3 yards of 34 S.W.G. wire will be required.

3 in. of 4 B.A. screwed rod.  
One 4 B.A. ebonite knob.  
Strip of stiff brass 2 1/2 in.  $\times$  3/8 in.  
Piece of brass 1 in.  $\times$  1/2 in.  $\times$  1/8 in.  
One small brass hinge, and 3 small brass angle brackets.

Various bolts, screws, odd pieces of wood, etc.

# LISSENIUM

## Is Daventry interfering with you?

ARE YOU FINDING DAVENTRY A SOURCE OF INTERFERENCE?  
DOES IT PREVENT YOU TUNING IN RADIO-PARIS?  
IS IT EVEN SO NEAR AS TO INTERFERE ON THE LOWER  
WAVELENGTHS?

The remedy is to increase the selectivity of your receiver. You will naturally wish to do so with as little alteration as possible to your existing receiver and without complicating the tuning.

Do you find it a problem? The solution is the use of a  
**LISSENAGON X COIL**

In many receivers a LISSENAGON X COIL can be used to increase the selectivity without any alteration to internal wiring or additional parts. Simply plug a suitable LISSENAGON X COIL into the aerial coil holder in place of the usual coil and connect the aerial to one of the terminals on the side of the coil; mount instead of to the usual terminal. Try both terminals on the coil and use the one which is found the better. See that the earth is connected to the socket of the coil plug. Tuning is carried out as usual with the aerial tuning condenser.

LISSENAGON X COILS can also be used in the H.F. circuit and give remarkably sharp tuning; usually it is only necessary to alter one connection



### LISSENAGON X COILS

No. 50	-	-	-	6/-
No. 60	-	-	-	6/4
No. 75	-	-	-	6/4
No. 250	-	-	-	9/9

*Interesting Leaflet describing the uses of LISSENAGON X COILS will be sent free on request to all readers of this magazine*

in order to obtain much greater selectivity than with a standard coil.

LISSENAGON X COILS are particularly suitable for use in Neutrodyne and Reinartz Circuits.

LISSENAGON X COILS possess all the characteristics which have made standard Lissenagon Coils so much demanded by all experimenters—maximum inductance, minimum self-capacity, lowest possible H.F. resistance and great air space between windings. Although the tappings of the LISSENAGON X COILS make them suitable for special purposes they are, in other respects, similar to standard coils and can be plugged in instead of them in any circuit without any alteration of any kind.

Hold a LISSENAGON COIL to the light—see the great air space right through it

# Lissen Limited

LISSENIUM WORKS

30-32 FRIARS LANE, RICHMOND, SURREY

'Phone: Richmond 2285 (4 lines).

'Grams: "Lissenium, London."


**LISSEN PARTS—WELL THOUGHT OUT, THEN WELL MADE**

# Brandes Audio Transformer

successful engineering research achieves  
greater volume and clearer tone

Brandes engineers have long been engaged in a close study of radio acoustics. There can be no angle of thought or experiment which has not been investigated in their efforts to obtain perfect reproduction of voice or music. Consequently, all Brandes radio equipment for bringing the receiver to life has unique constructional principles which mean vast improvements. Acoustics is the science of sound. Radio acoustics is the science of transforming electrical impulse into audible sound, and with the knowledge of seventeen years' research in this direction Brandes have come near to perfection in the reproduction of radio transmission of sound. The new *Audio Transformer* as a step to purity and greater volume is a definite achievement.

Any good Dealer stocks Brandes

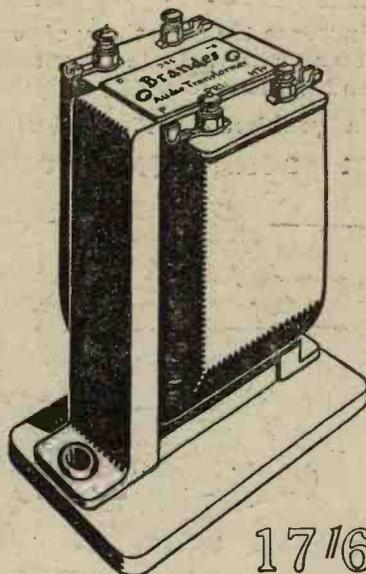

1716

Ratio: 1 to 5

The Brandes *Audio Transformer* has been developed along sound engineering lines, the main objects in view being a high amplification of applied voltage, together with a straight line amplification-frequency curve. That is to say, for a given input voltage, the amplification is constant over a wide band of frequencies, and thus resonance eliminated. Comparative tests have authentically established a greater and more uniform relative amplification as against existing transformers.

The Unit is well protected mechanically and the shielding is such that the Transformers may be placed close together without any interaction. It is an ideal first stage Transformer and is equally suitable for second stage work.


Ask your Dealer for the *Audio Transformer*

# Brandes

Experts in radio acoustics since 1908

Brandes Limited, 296, Regent St., W.1. Works: Slough, Bucks.

## Three other famous Brandes products

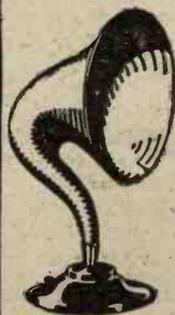

**The Table-Talker**  
Re-designed goose-neck horn which produces clear, more rounded and mellow tones. Constructed of special material which defeats any suggestion of harshness or metallic resonance. The adjustment lever, located at the rear of the base, controls the volume and sensitivity. 18 ins. high, diameter of bell 10 ins. Strongly built and attractive in appearance. Splendid value at moderate price 30/-



**Matched Tone Headphones**  
Every pair of Brandes phones is matched in tone by a special apparatus so that the two receivers produce exactly the same sound at the same instant. Comfortable and light in weight with clutch on head-band giving perfect adjustment to any head. Included in the leading types of completely equipped receiving sets - - - 20/-



**The Brandola**  
Special constructional features ensure greatest volume with minimum current input and exceptional clarity over full frequency range. Adjustable semi-goose-neck horn of patent non-resonant material, electroplated fittings and polished walnut plinth. 26 ins. high 12 in. bell 90/-

**Constructional Details**

Turning now to the actual construction of the set, the ebonite strip which is to carry the terminals may first be marked out, a sharp-pointed scriber being used to fix


used, 50 turns being put on, and the ends of the winding brought out to opposite sides of the coil. For use with this size of aerial coil a 60-turn reaction coil is wound in single basket form on a thin

coil movement should be clear from the photographs and sketches. The block of wood to which the moving arm is hinged is secured to the baseboard with a brass angle bracket; in addition, a long wood screw passes up through the baseboard into its lower end. A  $\frac{1}{4}$  in. hole is drilled through the block as indicated, to give ample clearance for the threaded control rod. When the whole assembly is complete, the point where the end of this control rod touches the bent brass strip attached to the moving arm should be marked, and a small hole drilled half through the strip to act as a guide for the rod. It may be noted that if a slightly coarser control of reaction is desired, a 2 B.A. threaded rod may be substituted for that shown, the brass bearing piece being tapped to suit.

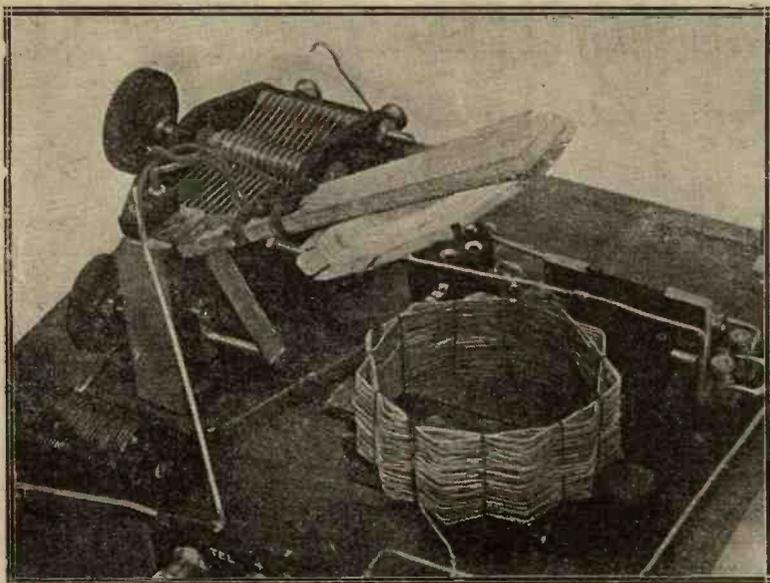**Reaction Coil**

The reaction coil is attached to the wooden arm with short screws; the aerial coil is tied to a strip of wood and screwed down on a block of wood mounted on the baseboard; this coil should be placed so that it is concentric with and close to the reaction coil, when the latter is lowered to the horizontal position.

The former for the filament resistance, which should be of hard wood, preferably treated with a coat of shellac varnish before use, is cut to the shape shown in Fig. 3. The wire is to be wound on this former as tightly as possible. A



A view of the set showing the reaction coil mounting and how its position is altered.

the positions of the terminals and screw holes. When the whole strip has been marked out and drilled in accordance with the diagram, Fig. 2, it should be divided up into sections as indicated. Each of these sections is now fastened with wood screws to a strip of wood of similar length and of the approximate dimensions shown, after which it is secured to the baseboard by means of screws through the wooden strips. The single terminal section and the pair are for the aerial first position, and the second position and earth respectively. The four-terminal section provides for the L.T. and H.T. batteries and the telephones. Next the grid condenser and leak on their ebonite panel are secured in position; the valve-holder is mounted with its grid terminal as close as possible to the common connection of the condenser and leak.

**Condenser and Coils**

The variable condenser is mounted with the spindle horizontal by bolting two small brass angle brackets to the edge of its top plate, and screwing these down to the baseboard.

We now come to the construction of the coils and their mountings. The aerial coil shown is of the basket-weave type, wound to a diameter of 3 in. on 11 pegs in a board; 26 S.W.G. d.c.c. wire is

card former. These turn numbers may need slight variation for different aerial systems and individual requirements, and more turns on the reaction coil may be found necessary with inefficient aerials; the mistake of using too

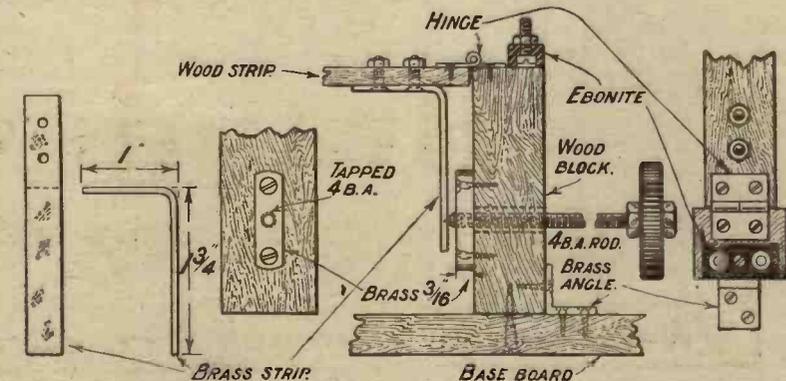


Fig. 4.—Showing how the coil stand is made. The ebonite knob, when screwed toward the upright, loosens the coupling between the coils,

many turns on this coil should, however, be guarded against, since under such conditions the receiver may become unstable and liable to flop over into oscillation without smooth regeneration when the coupling between the two coils is tightened.

**Assembly**

The method of assembling the various parts of the reaction

convenient method of doing this is to secure one end of the wire to one end of the former, by drilling a small hole through one corner and passing the end of the wire through it twice, the other end of the wire being attached to a nail firmly fixed in the wall or gripped in a vice. Then, keeping a constant tension on the wire, turn the former over and over in

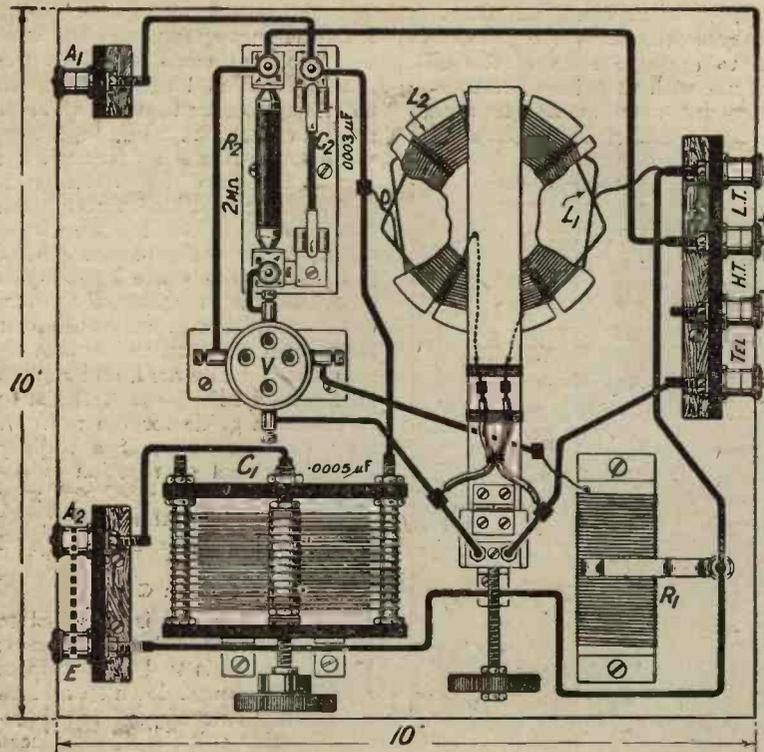


Fig. 5.—When all parts have been mounted in position, wiring is carried out as shown.

the hands while moving slowly forwards; the wire should bite well into the corners of the former, to prevent subsequent slipping of the turns; the finishing end is secured as before,  $\frac{1}{2}$  in. of wire being left over for making connection. The former is now screwed to the baseboard, the loose end being placed at the end furthest from the edge of the board. The contact arm should be bent to shape so that it will press firmly on the turns of wire when mounted on its pivot; spring washers on each side of it on the pivot assist in maintaining a good electrical contact at this point. When the arm has been mounted two small screws are inserted, one at each end of the former, to act as stop pins; the screw nearest the edge of the board should leave room for the arm to be moved into an "off" position, out of contact with the resistance wire.

**Wiring**

Short lengths of thin flex are used to connect the reaction coil to the two insulated bolts provided as terminating points on the top of the wood block supporting the movement; from these terminating points rigid wires go to the anode connection of the valve-holder and one of the telephone terminals. The ends of the aerial coil winding are soldered to the wire leading from the grid condenser to the fixed plates of the tuning con-


denser, and to the L.T. negative terminal respectively. The ends of the reaction coil winding should be only temporarily connected to the flex leads, until by a test on actual signals the correct method of connection has been ascertained. Assuming that these tests have been satisfactorily completed, the batteries and telephones may be connected to their appropriate terminals, and the aerial and earth leads attached, the reaction coil

being lifted right away from the aerial coil before switching on the filament current. If no signals are heard when the tuning condenser is rotated over its whole scale, move the aerial to the alternative terminal and try again. When signals are heard, slowly lower the reaction coil; if there is an increase in signal strength, the connections to the flex leads of this coil are correct, and they should be soldered and taped over; if, however, the opposite effect is observed, the connections should be reversed.

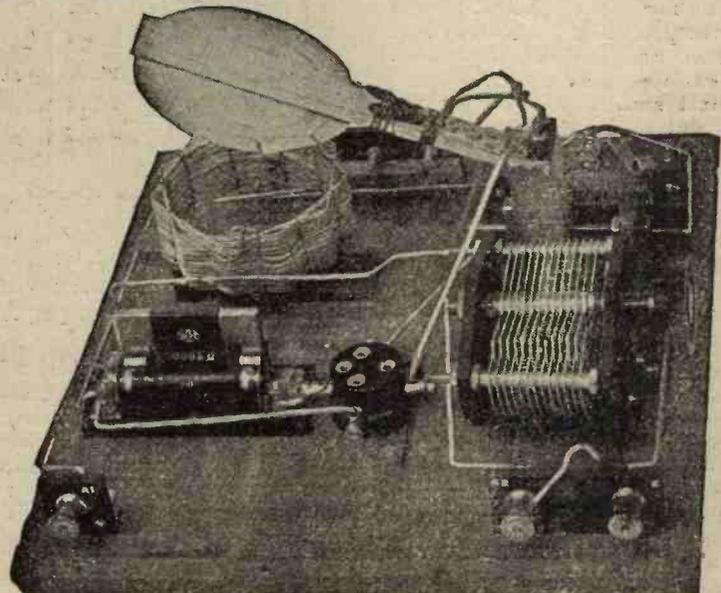**Test Report**

Constant aerial tuning may be used by the insertion of a fixed condenser of  $.0001 \mu F$  capacity between the aerial lead and terminal  $A_1$  or  $A_2$ ; a convenient method is to attach a fixed condenser permanently to the aerial lead, with a short length of flex to connect its other side to the required terminal. If any difficulty is experienced with the smooth control of reaction, a fixed condenser of  $.001$  or  $.002 \mu F$  may be joined across the telephones.

On test on a high though poorly situated aerial in south-west London with an A.R.D.F. valve and 45 volts H.T., 2L.O's transmission was of course received at full strength. Birmingham and Radio Toulouse also came in well, with the 2L.O transmission as a faint background. Belfast and Frankfort-on-Main were clear, though naturally not very strong, and with careful setting of the reaction adjustment and the assistance of a wavemeter Rome on 425 metres was tuned in sufficiently well to be identified. Some other stations were audible, but could not be identified.



A view showing the grid leak and condenser and aerial circuit terminals.



Folks meet a really good Condenser!

THAT'S me! The Efficient Watmel, radio men call me. Efficient—it's my middle name, and you'll say it is when you hear the improvement I make in the results from your radio. Read my test report. Something to be proud of, isn't it? I possess all the good points you look for in a Fixed Condenser and a few more besides. If you're interested in better condenser efficiency—visit your dealer and ask for me. Closer acquaintance will prove to you my sterling qualities.

Watmel Test Report.

1. Mica Insulation up to 2,000 volts.
2. Complete Condenser up to 1,000 volts.
3. Capacity checked.
4. Insulation up to 500 volts After Final Assembly.
5. Final Capacity Test PASSED OUT 100% EFFICIENT.

Prices.

Capacities for Standard Grid-Condensers.  
 '00005 to '0005 - 2/6 each.  
 Standard Fixed Condensers.  
 '002, '001 - 2/6 each.  
 '0025, '001 - 3/6 each.  
 Combined Grid Leak and Condenser is . . . 3/- each

The Watmel Wireless Co., Ltd.  
 332a, GOSWELL ROAD - LONDON, E.C.1



Representative for Lancashire and Cheshire—  
 Mr. J. B. LEVÉE, 23, Hartley Street, Levenshulme, MANCHESTER.

“So we left the middle out”  
 says CLIXIE!



“CLIXIE”

“Has it ever occurred to you,” asks CLIXIE, “that the ordinary wire lead absorbs no end of the energy it's supposed to conduct?”

“Realising this, my people have produced a conductor that sticks to its job and really does conduct. Radio Condit is a tiny copper tube, burnished inside and out. Since the middle of the wire is useless, Radio Condit is wire with the middle left out. Accordingly its H.F. resistance is cut down to the minimum for its weight.

“With the minimum metal, it provides the maximum of highly polished conducting surface. Lateral surgings are completely eliminated.

“Radio Condit is the H.F. conductor you've been looking for for ages.”

RADIO CONDIT  
 The H.F. Conductor

Tinned in 24-inch lengths (equivalent to 16 S.W.G.) in packets of 6 lengths . . . . . 2/- per pkt.

Obtainable from all Wireless Dealers or direct from the Patentees.

Are you well connected?  
 Try CLIX!

AUTOVEYORS LTD., 84, Victoria Street, LONDON, S.W.1




COMPONENTS

—for better results

Granted you have carefully adjusted your receiver to perfect balance we ask you to concentrate your experience—critical as it may be—and judge for yourself the merit of the Super Success. It gives you tonal purity—shorn of the tone-destroying mush, which till now was accepted as an irremediable evil in low frequency amplification



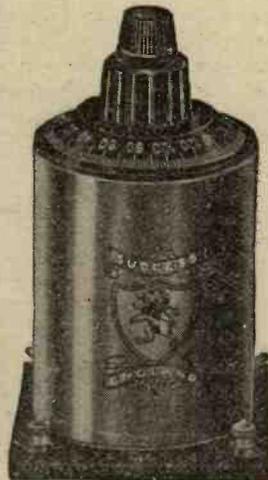THE SUPER SUCCESS  
 (All Black) L.F.  
 Transformer  
 21/-  
 THE SUPER SUCCESS  
 L.F. Transformer  
 For Second Stage  
 21/-



“SUCCESS”  
 OSCILLATOR  
 UNIT

Price 21/-

Covers a waveband of 250 to 550 metres; a very efficient component

The “Success”  
 Superforma

The outstanding feature of the “Success” Superforma is the incorporation of a ‘0003 Variable Condenser as an integral part of the unit. The fact that it is tunable is a consideration which enables the experimenter to balance up the stages for himself, after the set is built, and to tune out interference. That the “Success” Superforma is tunable considerably increases the selectivity of the receiver, gives greater amplification and generally improves the efficiency of any Super Heterodyne Receiver employing the type of Transformer balanced by the manufacturer. After finally balancing up the Superforma, by turning the small knob, the tuning condenser may be locked in position

“SUCCESS” SUPERFORMA, Price 30/-

SEE US ON  
 STAND NO. 23  
 N.A.R.M.A.T.  
 EXHIBITION  
 ALBERT HALL

Trade applications to:—

BEARD & FITCH, LTD.  
 34, AYLESBURY STREET, LONDON E.C.1

Telephone: Clerkenwell 8941

North of England Branch: 1, DEAN STREET, PICCADILLY, MANCHESTER  
 Telephone: Central 8240

Barclays Ad.

# Burndept specialise in wireless

A COMPANY manufacturing wireless apparatus as a side-line can never obtain the success for its productions as one specialising solely in the subject. The birth of Burndept coincided with the inception of domestic wireless. The Company has specialised in wireless apparatus manufacture from its foundation, until to-day the word Burndept stands for the world's best in wireless goods. Because Burndept are specialists, they are equipped in the best possible manner for the production of the world's finest wireless apparatus. Our much repeated slogan, "The Burndept range includes everything for radio reception, from components to complete installations," is no idle boast, but simply a plain statement of fact. We may also say that there is a Burndept set for each pocket. The building-up of such a comprehensive range as ours is the outcome of much patient research and development and represents the combined effort of many brains.

At the Blackheath Works, a special department is devoted to the study of radio in all its aspects. The equipment of this laboratory is so complete that there is hardly a problem which cannot be tackled by scientific means. Every piece of apparatus is rigorously examined and tried out before it is produced in bulk and every stage of manufacture is carefully supervised. Thorough testing ensures that finished sets or components are perfect when packed. If difficulties arise, Burndept Service-after-Purchase ensures your protection in the form of a generous guarantee. Write for our latest catalogue.


**LOOK OUT FOR THE  
BURNDEPT  
SUPER VALVE  
ON SALE SHORTLY**

*"The Valve with a guarantee"*

**HEAD OFFICE :** - - Aldine House  
Bedford Street, Strand, London, W.C.2  
*Tel. : Gerrard 9072. Grams : Burndept, Westrand, London*  
**BRANCHES at :** Birmingham, Brighton,  
Bristol, Cardiff, Exeter, Glasgow, Leeds, Liver-  
pool, Manchester, Newcastle, Northampton,  
and Nottingham. *Agents throughout the World*

**BURNDEPT**

**WIRELESS LIMITED**

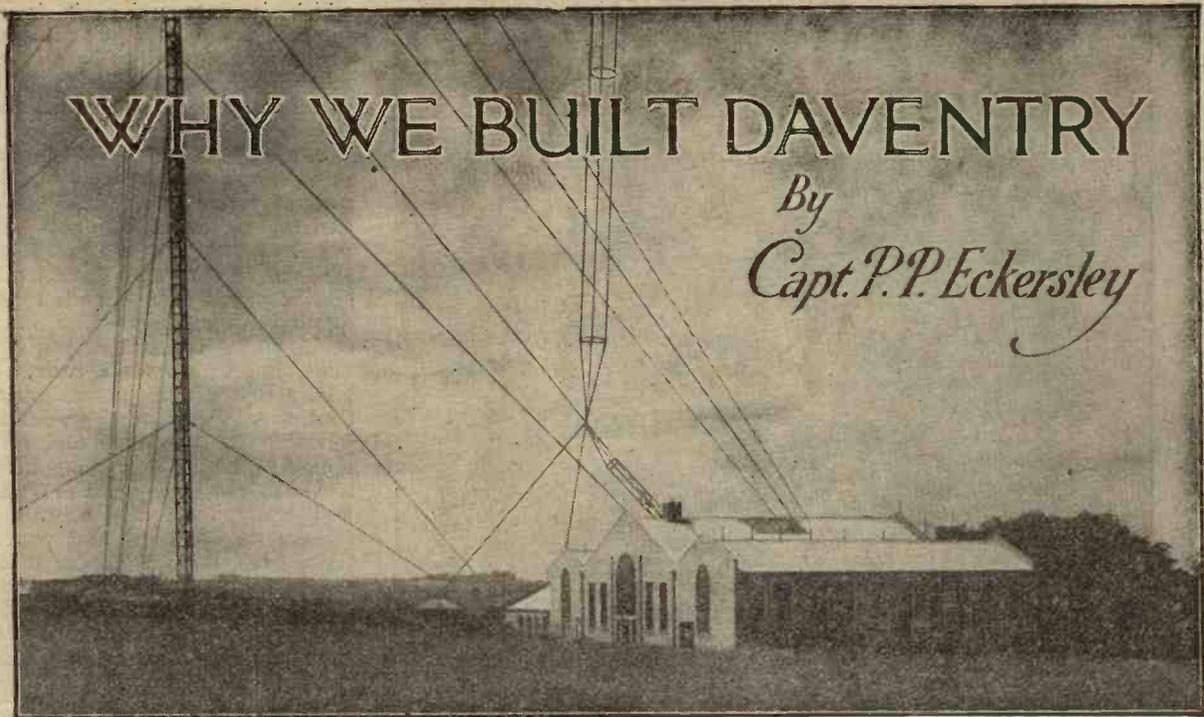

# WHY WE BUILT DAVENTRY

By  
*Capt. P. P. Eckersley*

IT is a fact that 85 per cent. of the population of the British Isles can receive broadcasting on a crystal set. This as a bald statement may possibly seem interesting, but not particularly wonderful. On the other hand, it probably gains added weight when it is realised that this record is unsurpassed in any other country—in fact, is hardly approached by other broadcasting organisations which have attempted to make listening a part of the population's daily life.

Then, again, it may be questioned, why this insistence upon a piece of apparatus that, while it has the merit of cheapness, is after all, in the minds of many, practically obsolescent?

## Cheap Listening

In stating this fact that 85 per cent. of the population of these isles can receive broadcast on a crystal, we as a broadcasting company in no way wish to put forward the crystal set as the be-all and end-all of listening, although it must be admitted that such a set as a criterion of judgment is probably unsurpassed.

The statement means far more than this, however. It means that, in the first place, persons with shallow purses can afford to indulge in the delights of listening; it means, secondly—and possibly this is more important—that people who have the money to employ

valve sets may be quite certain that one programme, at least, will be available without the annoying interruptions that mar enjoyment when listening to more distant and less robust signals.

The crystal area—which, of course, means the area in which crystal reception may be enjoyed—is an area wherein it is quite certain that nothing else, except the programme, may be heard; unless, indeed, some foolish and misguided person with no knowledge of the art tries to make himself a set, and causes oscillation and interferes with the enjoyment of others.

## A Public Service

It is, perhaps, interesting to study the way in which this ideal of universal crystal reception—and it surely is an ideal—has been obtained. The British Broadcasting Company was, in the first place, under contract with the Postmaster-General to erect eight main stations. It did so, but interpreting its functions in terms not simply of fulfilling a contract, but more of becoming a real public service controlled in the interests of the public, and the public only, it sought to give a greater democratisation of the art than was implied in the original contract.


Thus it was in 1924 that, to serve the denser areas of population not contained in the crystal areas incident to these eight main stations, eleven relay stations were erected.

Main stations and relay stations together gave, at any rate to all the densely populated areas, the ideal service; but still there remained the country user—the listener, after all, who deserves possibly more consideration than his cousin in town, because in the country, as we all well know, there are fewer distractions and therefore more need for the benefits of broadcasting.
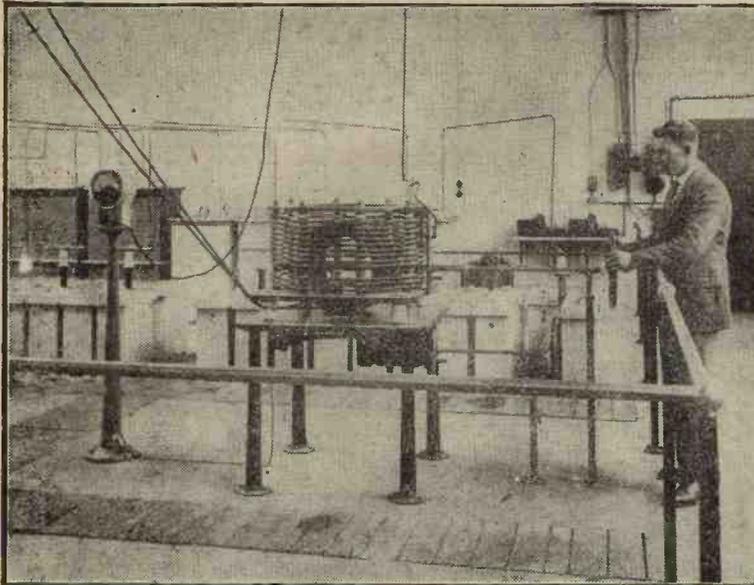
## Chelmsford

It was in the summer of 1924 that, to supplement our relay station policy, the high power experiments were begun. The Broadcasting Company erected at Chelmsford, therefore, a station of higher power than any used for regular service throughout the world, designed in the main to give the London programme to the country user who, as before mentioned, was probably outside the range of main or relay stations.

The wavelength of 1,600 metres which was chosen for the experiments perhaps needs some justification. We realise very fully that the design of the ubiquitous receiving set is considerably complicated by necessitating inductance or capacity values eight times that of the average 400 metre set. The wavelength was chosen, however, not without due thought. In these islands, in the first place, we have a great "jamming" problem. The narrow waters contain more shipping and more ship signalling than



A view of the aerial tuning coils and aerial ammeter. The latter reads up to 120 amperes!

in any other part of the world, as the listeners in Kent and Sussex will agree. It was necessary to choose either a power so great as to overcome the jamming very nearly on the same wavelength, or a wavelength far removed from the source of interference. A combination of these two factors gave us an ensurance that the jamming problem would die, and thus a good reason can be advanced for the 1,600 metre wavelength on the score of jamming alone.

**Fading on Short Waves**

There is a second point, however. Short waves, as we well know, are subject to all sorts of vagaries. Fading at long distances is a pronounced phenomenon which, so far, is susceptible of no real cure. Shielding by local hills has been known to play a considerable part, and to introduce blind spots in all sorts of country places, and the power needed to overcome some vagaries is out of all proportion to the gain that might be experienced. It is possible that with 50 kilowatts power some results might have been achieved and the jamming problem might have been overcome (the latter is doubtful), but the interference between the high power and existing broadcasting stations experienced with the average unselective receiving set used by the average listener would have been considerable, even though the station were located far away from the centres of broadcasting.


**Advantages of the 1,600 metre Wave**

The long wave is less susceptible, then, to these troubles of fading

and shielding. It has a daylight to night-time ratio of signal strength

which is near unity, it is not jammed nor does it jam; in fact, Chelmsford proved to be a stable, reliable source of broadcast, thanks to its long wave and to its high power.


The success of the Chelmsford experiments led us to seek permission from the Postmaster-General to crystallise our high-power policy in a permanent station. After some considerable sacrifices, which were made by the fighting services and others, it was decided that the station might be built, but there was a restriction laid as to the siting of the station. Chelmsford caused considerable jamming to Air Force and other signalling, and it was thought that it was necessary to put the station well away from the centres of training in the south-east part of these islands. An arbitrary line was drawn, therefore, between the mouth of the Severn and the mouth of the Wash, and we were told that the station could not be situated south of this line. Daventry was thus chosen as

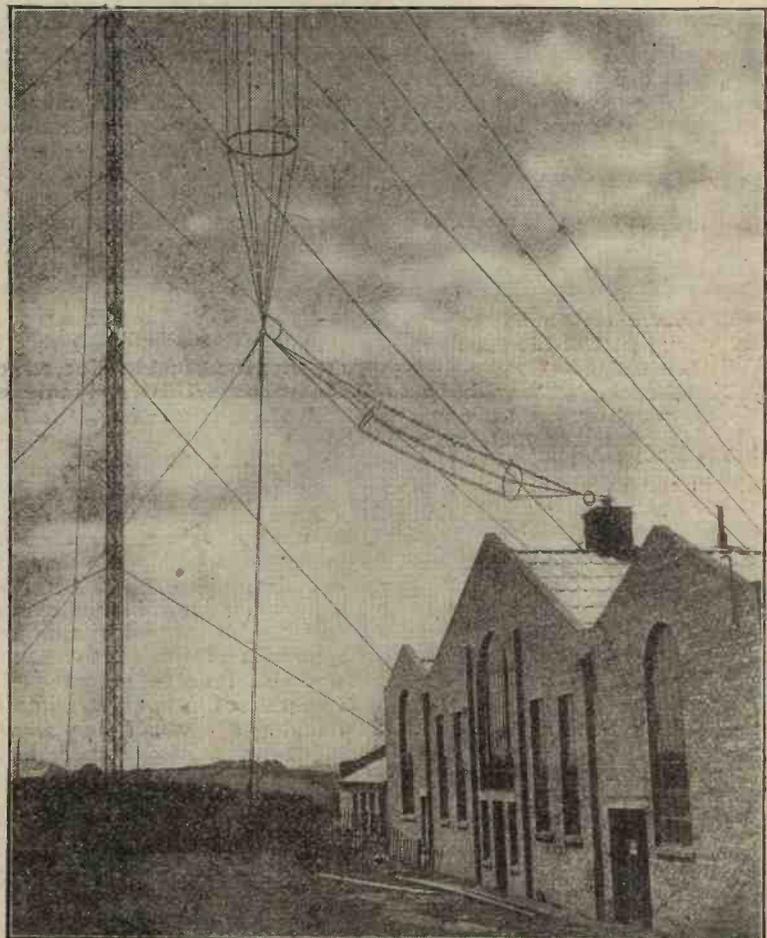

This photograph gives a very good idea of the lead-in arrangements at the high-power station.
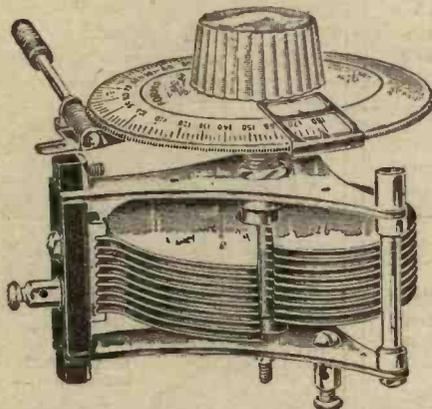
# FAMOUS FORMO PRODUCTIONS

THE NEW FORMO-DENSOR STRAIGHT WAVE, ULTRA LOW LOSS with 200-1 FINE TUNING RECORDING DIAL



0003μF 0005μF  
**FORMO-DENSOR**  
complete with  
**FINE TUNING RECORDING DIAL**  
17/6

**FORMO-DENSOR**  
without Dial  
10/6

**FINE TUNING RECORDING DIAL**  
separately  
7/6

## SEPARATES STATIONS WITH HAIR-SPLITTING EXACTITUDE

*A Condenser of Advanced Design, Suitable alike for Laboratory and General Use, and for Super-Het., Neutrodyne and other Circuits designed for Super-Selectivity*

**GROUNDING ROTOR, INDEPENDENT SKELETON FRAME, JEWELLERS' METAL VANES, NO HAND CAPACITY, STATIONS LOGGED ON THE DIAL**

## The FORMO PERFECTION L.F. TRANSFORMER



Full, Rich, Mellow Reproduction of Voice or Music, with the Utmost Fidelity.

ITS STRONGEST APPEAL IS TO THE MOST CRITICAL  
**ONE GUINEA**  
30,000 Turns of Wire

*Correctly proportioned between the windings. On a core composed of the exact amount of iron.*

## THE EVER POPULAR FORMO SHROUD D MODEL

12,500 Turns

10/6 Formerly 18/-

This transformer is increasing in favour by leaps and bounds, and, at the new price of 10/6, is undeniably the utmost value in Radio that money can buy. It is giving honest and faithful service to thousands of listeners in every quarter of the globe.

ILLUSTRATED DESCRIPTIVE LEAFLETS ON REQUEST


**THE FORMO COMPANY**  
(ARTHUR PREEN & CO., Ltd.)

**CROWN WORKS**

Cricklewood, London, N.W.2



# Get Yesly Tuning for CONCENTRATION

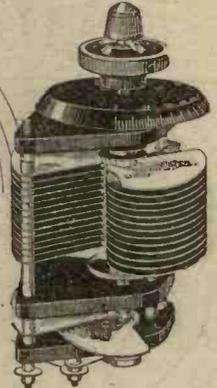

Ask for Leaflet C2.

Clean cut signals are the direct results of accurate tuning. 50% to 100% improvement in the volume of reception can be obtained with improved tuning apparatus.

With YESLY TUNING each individual station can be isolated so as to obtain the full strength of its signals without interruption.

The accuracy required for this concentration tuning is THE feature of the

## YESLY SQUARE LAW VARIABLE CONDENSER

### NOTE

- (1) The first-class GENERAL FINISH
- (2) The pure EBONITE highly polished plates.
- (3) The coiled SPRING MOVING contacts
- (4) The ONE HOLE FIXING with embedded nut to eliminate all backlash and spindle play.
- (5) The special panel pin to prevent bodily rotation.
- (6) The ROBUST CONSTRUCTION
- (7) The MODERATE PRICES

## BETTER TUNING GREATER VOLUME

	Plain	Vernier
001	11/6	15/-
0005	10/6	14/-
0003	10/-	13/-
00025	9/6	12/6
001	9/-	12/-



## Perfect Control

A touch of the throttle, the clutch or the steering wheel, and what a world of difference it can make in the running of a car. The whole of the power obedient to the slightest change in control. Radio Valves throb to the pulse of power. They obey the commands of your Rheostats with startling exactness.

THE "YESLY" VELVET TOUCH Rheostat embodies a smooth running contact shoe which results in wonderful flexibility of control. The moulded bakelite and polished nickel case gives great mechanical strength and a sure protection from the loss of efficiency due to dust. The shaft is 1/4 in. in diameter and turns in a bearing one full inch in length. This is only ONE feature to ensure strength and safety in control.

Obtainable from your local dealer. If you have any difficulty write direct to—

**ENGINEERING SUPPLIES, LTD.**

235, Blackfriars Road, London, S.E., England

All genuine "Yesly" Components are packed in blue boxes.

6 ohms resistance each 6/6

30 ohms resistance each 7/-


YESLY Potentiometers: 400 ohms resistance each 8/-

The highest possible standard in Aerial tuning demands YESLY COMPONENTS

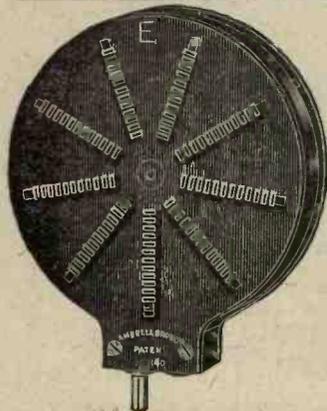
## LOOK FOR THE NAME




A Well Known Fact  
**GAMBRELL PRODUCTIONS**  
 Give Maximum Efficiency



Gambrell Efficiency Coils.

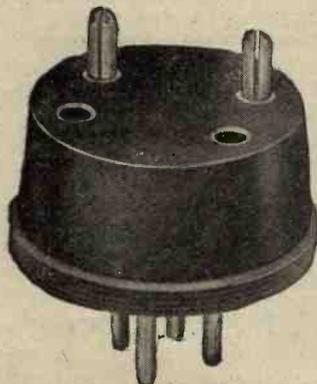

Gambrell Transadapta. Pat. pending

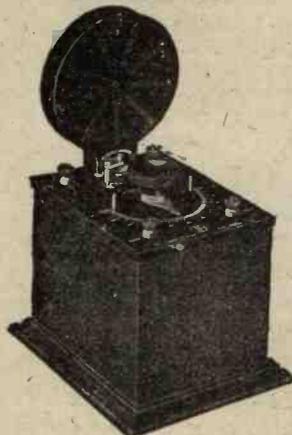

Gambrell Wavemeter.

**The FAMOUS GAMBRELL "EFFICIENCY" COILS**  
 Give greatest selectivity of tuning and have the lowest self-capacity and H.F. Resistance of any coil yet produced. Supplied in all wavelengths. Prices 5/9 to 19/- each.

**The GAMBRELL TRANSADAPTA**  
 One of the most recently designed components whose object is to cut out those highly inefficient fine wire H.F. Transformers by using air-spaced coils of maximum efficiency. Price 6/6.

**The GAMBRELL WAVEMETER**  
 Calibrated against N.P.L. standards and supplied with Coils and Chart. (Type C) Complete, price £4 10s. 50-500 metres. Additional ranges 20 to 7,000 metres if required.

**The GAMBRELL ANTI-CAPACITY SWITCHES**  
 Designed to give absolutely reliable contacts, negligible capacity between the blades and perfect insulation. Price, 2-way, 7/-; 4-way, 9/6.


**The GAMBRELL ORIGINAL NEUTRODYNE CONDENSER**  
 The original Neutrodyne Condenser which was first designed by Gambrell Bros. Limited. Thousands are in use and giving the utmost satisfaction. Price 5/6.

**The GAMBRELL L.F. INTERVALVE TRANSFORMER**  
 Is unsurpassable for purity of reproduction and volume. Stage I, 27/6; Stage II, 27/6.

*PUT THE BEST IN YOUR SET  
 AND GET THE BEST OUT OF IT*

Specify Gambrell Components  
*If any difficulty in obtaining locally, write direct*  
 Write for full particulars of components designed to give maximum efficiency


The Sign  of Efficiency

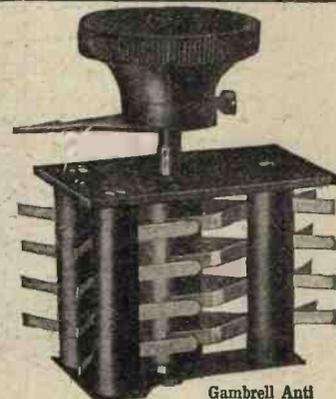

Gambrell Anti Capacity Switch.



Gambrell Neutrodyne Condenser.

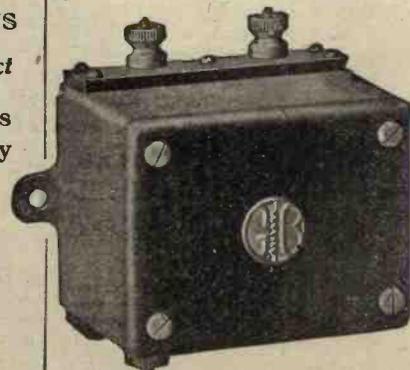

Gambrell L.F. Intervolve Transformer.

**GAMBRELL BROS., LTD.**

76, VICTORIA STREET, LONDON, S.W.1. 'Phone: Victoria 9938.

*Barclays Ad.*



A general view of the interior of the station. The valve panels are seen in the middle background, while the aerial tuning arrangements are on the right.

the permanent quarters of our high-power station.

The site was chosen somewhat against our will, because we realised that those spark-jammed territories around the area of Kent and Essex would be in worse case than they were when Chelmsford was operating. Our choice for the site to combine a certain amount more land in the 100-mile crystal area than was given by Chelmsford was somewhere, it might have been, 40 miles north-west of London, but, as mentioned before, the Government had to decide otherwise.

#### Results at Daventry

Results with the Daventry station show that our guarantee of 100 miles crystal range has been fulfilled, and if the reader would take the trouble to get a map of England and draw a circle of 100 miles round Daventry, he will find that very little of the area included contains sea. The station, as far as taking into account the maximum number of listeners, is probably very favourably placed. Complaints, however, come from the area of Chelmsford, where one has heard of a loud-speaker in series with an aerial, without anything else, which has been known to get results. Naturally, this would be so because, obviously, the strength of signal must be considerably diminished with so great a relative removal of the station. An East Kent listener is badly placed, because much of the area so severely jammed by the shipping is left outside a crystal area, and we must take thought as to how to cure the troubles incident to reception in that area.

The high power station, which one may say without exaggeration is the keystone of British broadcasting, puts the final touch to our

crystal policy, which again is synonymous with our ideal of the complete democratisation of wireless listening.

#### The Next Move


The question may be asked, having built Daventry, and having explained the reasons for its building, what is next to do? The writer has been subject to a considerable amount of criticism, because he has stated that in his own opinion distant listening can never be a finality of enjoyment for the *hoi polloi*, but is rather an ephemera of wireless. This is only a personal opinion, and as such can carry as much or as little weight as the reader desires.

It is obvious that wireless listening has great potentialities in putting us, in our own houses, in touch

with foreign lands, and with different programmes that suit our taste better, but I am not sure whether the future will not see alternative programmes given from as robust a source as are the single programmes of to-day, and our ideals must be towards giving not only 90 per cent. of the population the possibility of receiving a programme on a crystal set, but more, giving 100 per cent. of our population the possibility of receiving a choice of programmes on a crystal set.

To link up Europe with many valves, and incidentally many dots and dashes, and many X's, too, would not appear to be the be-all and end-all of broadcasting. Would it not be better when, by exploring all the possibilities of the wire and wireless link, the same conditions that at present apply to Britain will apply to the whole of Europe—indeed, to the whole of the world, and is the day so far distant when one may see printed in the *Radio Times* "S.B. to Europe," or "S.B. from Britain?"

If there are some, perhaps, who do not wish to listen to foreign concerts, they will still have the British alternative. Until the flexibility of the whole is such that a man in his own home, with an apparatus that need not cost him more than a cheap cigarette case, will be able, by the turning of a simple single knob, to annihilate space and tour in foreign lands, with less trouble than it takes at present to walk round his own village, broadcasting will not have achieved finality. In the meanwhile we have built Daventry. I trust you will all realise why.

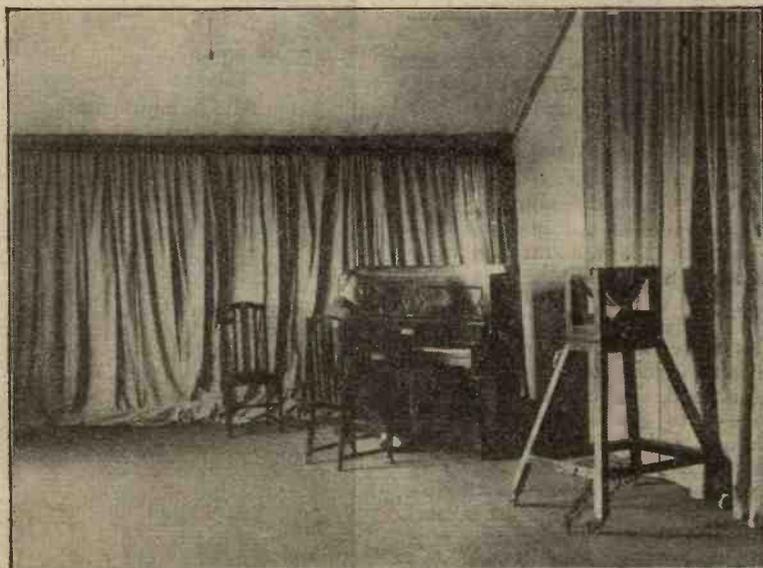

The studio at Daventry, which will be used occasionally. The majority of the transmissions will, however, be relayed from distant studios.



## On the Verge of New Developments

By JOHN SCOTT-TAGGART,  
F.Inst.P., A.M.I.E.E.,  
Technical and Managing Director of  
Radio Press, Ltd.

**H**AVE wireless receiver designs improved during the last six months, or even during the last year? This is a question I have been pondering over during the last month or two, and I have felt that undoubtedly the improvements, such as have been made, have not been on a large, or large enough, scale.

"Getting distance" is still a matter of considerable difficulty, and the importance of selectivity in relation to increasing the range of receivers is a matter which also has not received the attention it should.

### Range

The range of a receiver does not merely depend upon the amplification obtainable, but on the ratio between the desired signals and interfering signals or noises. Almost every experimenter has, at some time or another, obtained signals from very long distances, and he would probably find, if he kept a close record, that many of the cases of excellent reception were on occasions when the amount of interference was negligible.

Special cases, particularly, are those where, say, only one B.B.C. station is working and the others have closed down, or when some special experimental transmission is taking place outside the normal hours. On such occasions excellent reception is often obtained, and this is because the amount of interference is negligible.

### Interference

As more and more broadcasting stations are erected in this country and abroad, the tendency for interference to be experienced will increase, and the present situation, bad as it is, will become worse, unless technical developments on the receiving side improve simultaneously.

As a matter of fact, if receiving stations are made more selective, even at the expense of signal strength, greater ranges can now be

accomplished, but in the immediate future sets will be designed which will attain the greater selectivity without sacrificing signal strength; on the other hand, the very methods which improve selectivity will simultaneously improve signal strength. These methods will include the cutting down of losses in different parts of the receiving circuit, and the originating of new circuits for the special purpose we have in mind.

### Work at Elstree

Very important work is now proceeding in the new laboratories which are being erected at Elstree by the Radio Press, two buildings being already in use. It is realised that in order to further progress in the required direction it is essential for us to have laboratories of our own in which experts will be devoting the whole of their time to the practical problems which affect the wireless constructor and

experimenter. New readers will, no doubt, be surprised to hear of the great enterprise which has been undertaken on behalf of the Radio Press journals, but the step has become necessary if the readers of these journals are to have placed before them progressive designs and accurate information.


In many directions American sets are superior to British receivers. In the September double number of *Modern Wireless*, Major James Robinson, D.Sc., Ph.D., F.Inst.P. (who has taken charge of the new Radio Press laboratories, after resigning from the service of the Air Ministry, where he was engaged as Director of Radio Research and Design Work), explains the various directions in which development is likely to take place, and readers of *THE WIRELESS CONSTRUCTOR* will undoubtedly in the very near future derive the fullest benefit from the work at present being carried out at Elstree.



The Orchestra at 5SC, the Glasgow Station. On the right is seen Mr. Isaac Losowsky, the conductor.

# INTRODUCING

*A  
New  
Standard of  
Excellence*

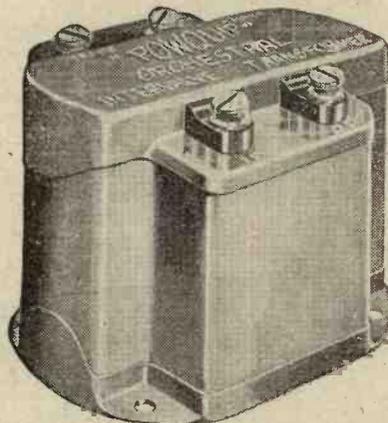

Price 31/6

The

**"POWQUIP"**  
INTERVAL TRANSFORMER  
**ORCHESTRAL**

The  
**POWER EQUIPMENT**  
COMPANY LIMITED

KINGSBURY WORKS, THE HYDE,  
HENDON, LONDON. N.W. 9.

Amplification ..  
Absolutely Uniform  
and Considerably  
increased.

Every Instrumental  
note both high &  
low distinguishable

Voice reproduction  
Absolutely  
Natural.

Guaranteed  
12 Months.  
No distortion....

Shrouded with  
Electrolitic  
Copper.

Bobbin of pure  
Vulcanized  
Rubber.

Terminals moulded  
in bobbin flange  
No loose wires.

Nearly three miles  
of wire used in  
Construction.

**SOLVING  
AN  
AERIAL  
DIFFICULTY  
A NOVEL  
SINGLE-VALVER**

By  
C.P. Allinson



COME multi-valve, go multi-valve, the humble one-valve set still retains its popularity; and even among the most advanced experimenters few will probably be found who do not possess a favourite "single-valver." Do not think that this is merely kept on a shelf as a relic of old times, far from it—it is used regularly and with affection.

When single-circuit tuning is employed many put their trust in parallel tuning; others, however, swear by series, and this is no doubt due to varying conditions obtaining with different aerial-earth systems. The best results, however, may frequently be obtained by using both together, but this results in an extra control requiring adjustment.

**Obtaining the Advantages of Both Methods**

The receiver described in this article employs both, and yet it retains the advantage of having only one tuning control by the use of a dual condenser, one portion of which acts as a series condenser and the other as parallel tuning condenser.

It is thus possible to combine the advantages of both systems of tuning without extra complication, excellent selectivity being obtained, and although it is not claimed that greater signal strength will be obtained, the completed receiver will be found very efficient.

**Coils and Valve Enclosed**

As will be seen from the illustrations, the set presents a handsome appearance with its moulded top and base, and its simplicity will readily be appreciated. Standard modern practice has been followed

in its design by enclosing both coils and valve within the cabinet, so protecting them from any possible chance of damage from idle fingers or too energetic dusters.


All the panel mounting components are of the one-hole fixing type, thus reducing the amount of constructional work to a minimum,

The tuning condenser, a double  $.00025\mu\text{F}$ , gives an excellent wavelength range and enables all B.B.C. stations to be received without the necessity for changing the tuning coil, and the coil holder used has the moving coil controlled by a worm and pinion which gives a very fine adjustment, allowing of close control of reaction.

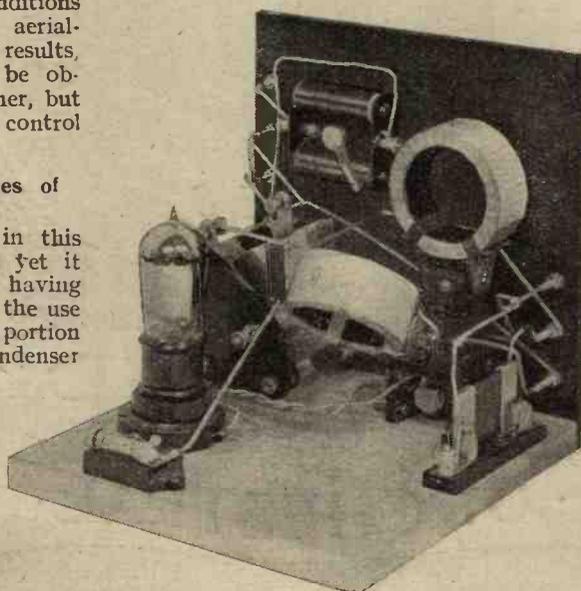**Extra Fixed Condenser**

A clip-in type of fixed condenser is provided, so that should it be found necessary, a small condenser may be connected in parallel with the portion of the dual condenser which is connected in series with the aerial. This is shown as  $C_1$  in the theoretical circuit diagram (Fig. 1). Further, two aerial terminals allow the two halves of the tuning condenser to be connected in parallel for long-wave reception, or where it is desired to use only parallel tuning, as well as the combined series-parallel arrangement.

The clip-in type of grid leak is employed, and, of course, different values of leak should be tried. Not only does this allow of the



The valve and coils, being behind the panel, are protected from accidental damage.

and the receiver can be completed in a short space of time. The photographs taken from behind the panel indicate the simple wiring scheme and how the components are mounted in relation to each other.

best results being obtained, as different values of leak suit different valves, but also if an incorrect grid leak is used smooth control of reaction may be difficult or unattainable. It is most important that back-lash be absent in

the reaction control or distant stations will not be received at their fullest strength, if at all.

The dual filament resistance fitted to this receiver allows either bright or dull emitter valves to be used and is a refinement well worth any extra expense that may be entailed. Similarly the shock-absorbing valve holder employed

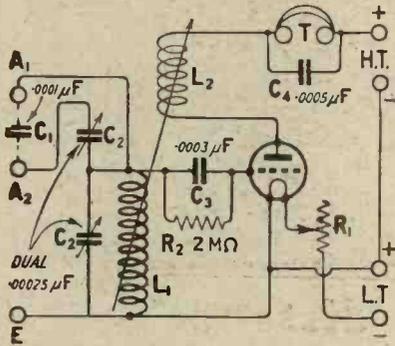


Fig. 1.—Note that the two sets of moving plates of the dual condenser are joined to terminal A<sub>1</sub>.

not only eliminates ringing noises being heard when microphonic valves are in use, but also with valves that do not suffer from this trait protects them from damage from shock or serious vibration.

**Extension Handle Needed**

As the scheme of connections used with this receiver makes it necessary to connect the moving spindle of the tuning condenser to the grid of the valve an extension handle has been fitted so as to avoid any possibilities of hand-capacity effects affecting the tuning. This, however, is easily made, and its use certainly conduces to facility in tuning-in weak and distant transmissions.

**Components**

I give below a complete list of the components required to construct this receiver, and so that those who wish to may duplicate it exactly, I also give the makers' names. You will want:—

- One ebonite panel, 8 in. x 8 in. x 1/4 in. (Paragon).
- One cabinet with loose base-board, 8 in. deep (Agar).
- One dual .00025 μF square law condenser (Jackson Bros.).
- One panel mounting coil-holder (J. & P.).
- One dual filament resistance (Radio Instruments, Ltd.).
- One "Anti-phonic" valve-holder (Burndep't Wireless, Ltd.).
- One fixed condenser, .0005 μF;

one fixed condenser, .0003 μF, and one 2 MΩ grid leak (Dubilier).

One clip-in condenser with mounting, .0001 μF (L. McMichael, Ltd.).

One piece of ebonite rod for extension handle 3 1/2 in. long by 3/4 in. diameter, and an inch of 2 B.A. screwed rod (Burne-Jones & Co., Ltd.).

Nine W.O. type terminals, nickelled.

Quantity square tinned copper wire 16 gauge, and a short length of flex for connecting up.

A short length of Glazite.  
One set of Radio Press Panel Transfers.

**Preparing the Panel**

The first proceeding is to prepare the ebonite panel for drilling. If guaranteed ebonite is used this will merely consist of marking it out according to the panel lay-out, shown in Fig. 2. If, however, there is any doubt as to the surface insulation of the panel used, both sides should be thoroughly rubbed down with No. 0 glasspaper to remove the surface skin. A square, a rule and a scribe are all that is required to mark out the panel, but a pair of dividers will be found useful. Fig. 2 gives all the necessary details and dimensions, and having marked out the panel, centre-punch all points at which holes have to

be drilled. There will then be little risk of the drill wandering and spoiling the job. All holes of the same size may be drilled first, and it is a good scheme to put a small drill through before drilling the large holes. This will then act as a pilot for the big drill and conduces to accurate work.

**Transfers**

Next apply the panel transfers, and should it have been necessary to prepare the panel by rubbing it down, the front surface should be rubbed over with a rag and a trace of vaseline to restore the black colour.

As there are only three components to mount on the panel, this will soon be done, after which the terminals will be fixed. Fasten the panel to the base-board with three 1/2-in. No. 3 countersunk wood screws and mount the components that go on this base-board. It may here be noted that the .0005 μF fixed condenser (C<sub>4</sub>) that is connected across the telephone terminals is held in place by means of the wiring and will, therefore, not be placed in position till that is done.

**Wiring**

The wiring may now be commenced, and it is advisable if the constructor has the required skill


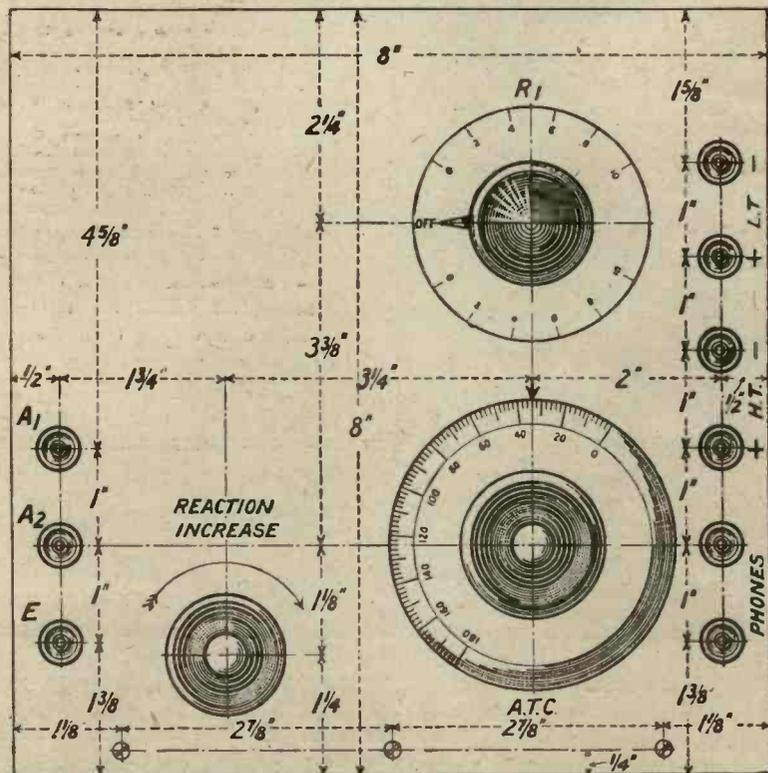


Fig. 2.—A half-size drawing of the vertical panel, showing terminal markings.

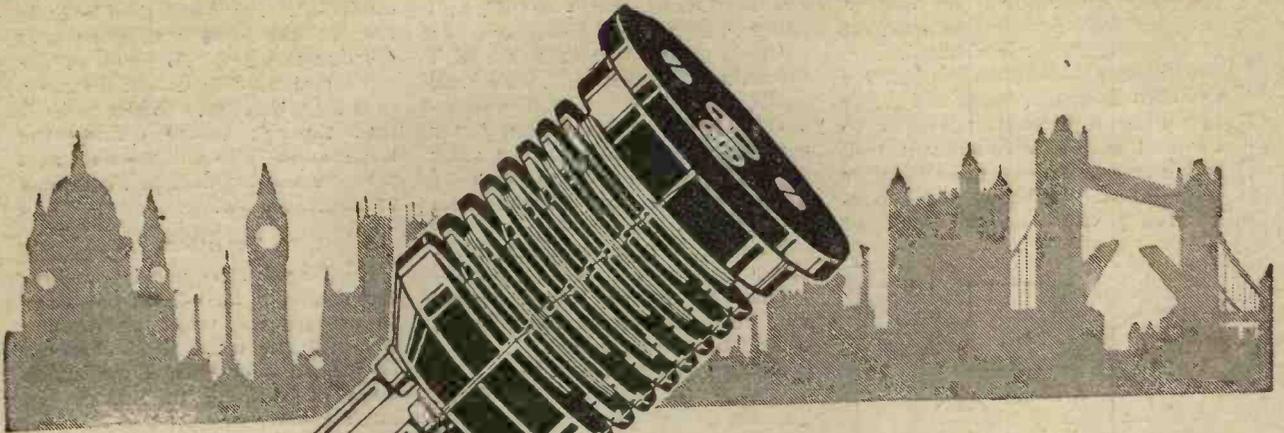

## Selectivity and distance

**L**OOK at the shape of a McMichael **MB** H.F. Transformer, observe the divisions carrying the windings, note the staggered slots conveying the leads.

*The reason, elimination of losses.  
The result, greater selectivity and reception of distant stations hitherto unobtainable.*



## H.F. TRANSFORMERS

Supplied in six ranges of wavelengths, covering from 80 to 7,000 metres.

No. 0	80 to 150 metres	10/-	No. 2	550 to 1,200 metres	10/-
No. 1	150 " 300 "	10/-	No. 3	1,100 " 3,000 "	10/-
No. 2	300 " 600 "	10/-	No. 4	2,500 " 7,000 "	10/-

A6, Neurodyne Unit (Broadcast Wavelength) .. .. each 10/-  
A7, Supersonic Unit .. .. each 12/6

No. 3 Transformer is suitable as a Neurodyne Unit for 5XX  
The Complete set in handsome case, Nos 00-4 .. .. 60/-

*Any number of each transformer can be supplied matched at NO extra charge, if requested at the time of ordering.*

OBTAINABLE FROM ALL DEALERS.

**"The Transformer that made High Frequency Amplification popular."**

Your dealer can also supply you with the two latest **MB** Components, the **MB** H.F. Reactor Unit and the **MB** H.F. Damper. Both are auxiliaries of the **MB** Transformer.

*For full details of these write for 16-page booklet on High Frequency Amplification and Allied Neurodyne and Supersonic (Super-Heterodyne) Reception.*



Works :—  
WEXHAM ROAD, SLOUGH  
Phone : SLOUGH 199

# L.M<sup>C</sup>MICHAEL LTD

Manufacturers of Wireless and Scientific Apparatus

Head Office:— HASTINGS HOUSE, NORFOLK STREET, STRAND, LONDON, W.C. 2. Phone: CENTRAL 8272/3  
TELEGRAPHIC ADDRESS: RADIETHER, ESTRAND, LONDON CABLE ADDRESS: RADIETHER, LONDON

London Showrooms :—  
179, STRAND, W.C. 2.  
Phone: CENTRAL 6988

Barclays Ad

to solder all connections. If the wiring diagram (Fig. 3) is followed, no difficulty need be experienced. The two I.T. leads should first be done with Glazite, the remainder being done in any convenient order, finishing up, however, with the three leads going to the fixed condenser  $C_4$ , namely, two from the telephone terminals and one from the reaction coil. Care should be taken to see that the connecting wires to the coil-holder allow sufficient clearance not only for the two coils  $L_1$  and  $L_2$  to be plugged in, but also for the reaction coil to swing without fouling any of them. The positions of the wires shown in the wiring diagram permit of the largest commercial coils being used.

The extension handle is made by drilling and tapping a 2 B.A. hole in each end of the ebonite rod. One end has a short length of 2 B.A. screwed rod inserted, on which the knob is fixed, the other end screws on the condenser spindle and fixes the dial in position.

**Valve and Accumulator**

The receiver is now ready for test. First insert two coils, say, a 50 for  $L_1$  and 35 for  $L_2$ , and the valve in the holder, attach the leads to I.T. - and I.T. +, taking these to the respective terminals of the I.T. battery. With bright emitters taking 3.5 volts a four-volt accumulator will do, though a six-volt one can be used. Valves of the dull emitter type passing .06 amps may be used either with a dry battery giving three volts, or with a four-volt accumulator. In the former case the bright part of the filament resistance may be used, with the latter the "dull." Instructions will, however, generally be given by the makers as to the correct I.T. battery to use. Turn on the valve by means of the correct winding of the filament resistance and note whether it is burning correctly. In the case of dull emitters this may be rather difficult to determine, as the bulb has usually been "gettered" in order to give a high degree of vacuum; it is usually possible, however, to see if the filament is burning, by looking straight down on the pip of the valve, or failing this, by means of a small piece of looking-glass held at the base of the valve, so as to reflect any light coming downwards out of the valve.

If all is in order, connect the phones and the H.T. battery, plugging in only six volts first in case a short circuit has occurred at some point. If the brightness of the valve does not change, the correct

value of H.T. may then be plugged in according to the maker's instructions, or if the valve has already been in use, according to the value you will have found best.

The next proceeding is to ascertain that the reaction coil is cor-

rectly connected. Gradually approach  $L_2$  to  $L_1$  by turning the knob controlling the moving coil in a clock-wise direction, and at a certain point a plop or click should be heard, after which a faint hissing or rushing sound is

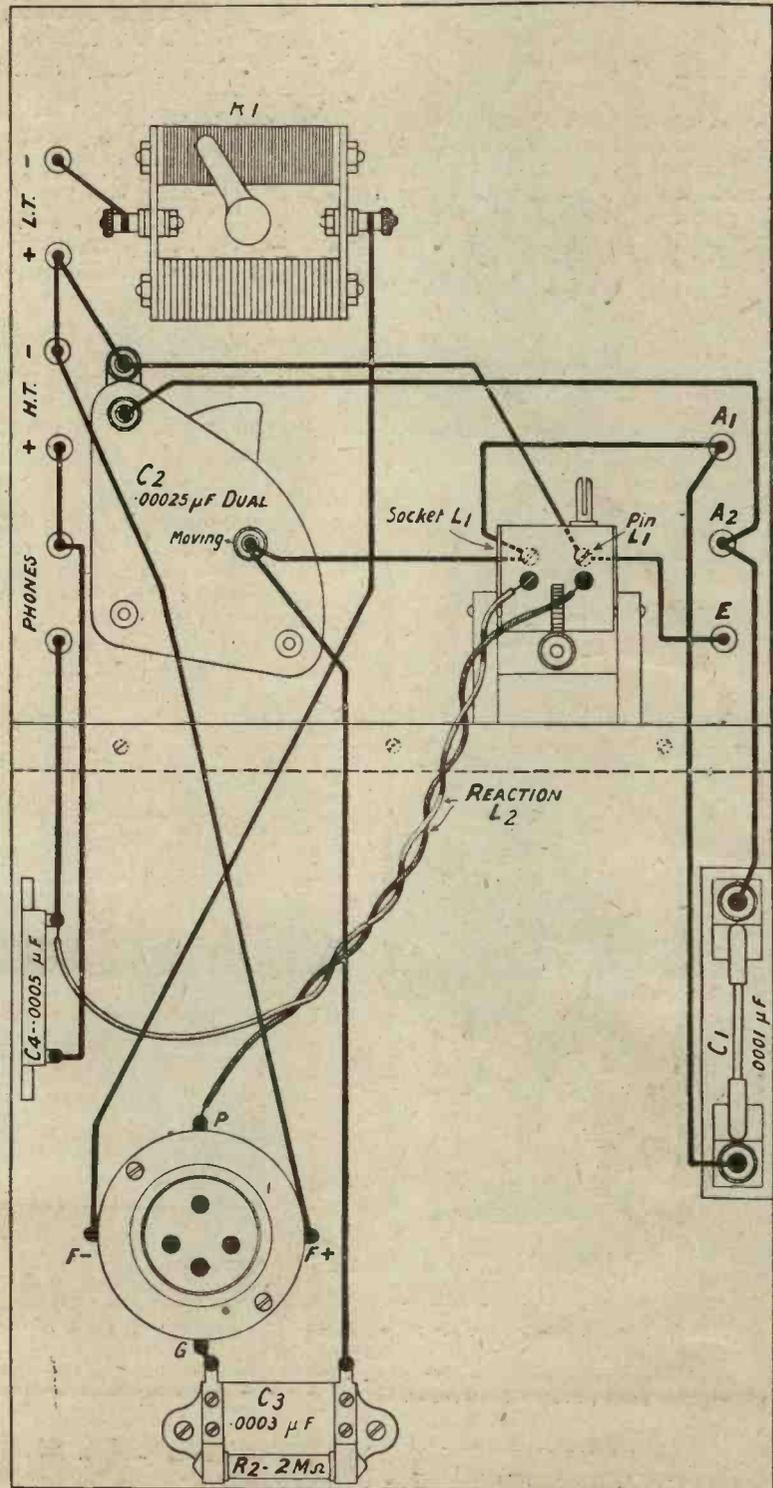


Fig. 3.—The connections given should be carefully followed. Note that the dotted connections on the coil-holder are those to the aerial coil, the reaction leads being shown in full.

# See Stand 33

ALBERT HALL


## L. F. TRANSFORMERS

All-Purpose Model. Specially designed to serve as first and second stage. In brown metal case, which excludes moisture.


Cat. No. 5152. Price 15/-

De Luxe Model. Constructed with one primary winding, with a secondary winding on either side; therefore minimum of self-capacity with greater amplification, which remains constant over a wide band of frequencies. Black metal case.

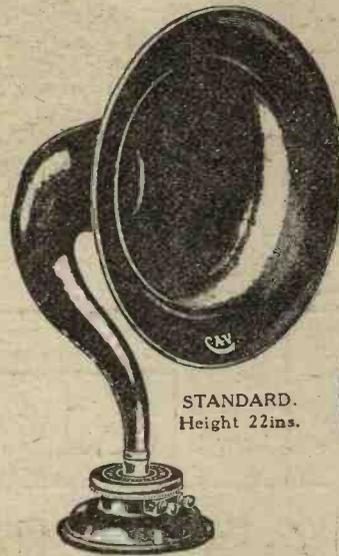
Cat. No. 5150 High Ratio (first stage) Price 27/6  
 5151 Low Ratio (second stage)



STANDARD.  
Height 22ins.

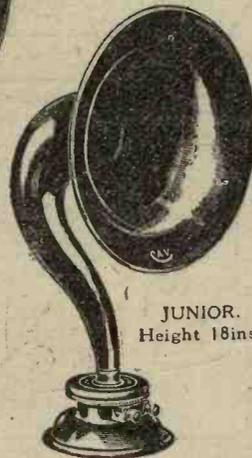

JUNIOR.  
Height 18ins.

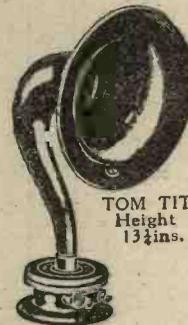

TOM TIT.  
Height 13 1/2 ins.

## LOUD SPEAKERS

For purity of tone they stand alone.

STANDARD—2000 ohms.

Black Satin Enamel. Cat.

No. 5016 - - - - - 90/-

New Reduced Price

120 ohms. Cat. No. 5026  
New Reduced Price 90/-

4000 ohms. Cat. No. 5021  
New Reduced Price 100/-

JUNIOR—2000 ohms.  
Black Satin Enamel. Cat.

No. 5007 - - - - - 55/-


TOM TIT—2000 ohms.

Black Crystalline. Cat.

No. 5001 - - - - - 27/6  
New Reduced Price
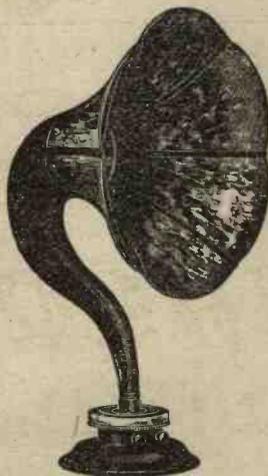
## HORNLESS LOUD SPEAKER

This has been designed for those requiring an instrument to harmonise with the furnishing of a room. It is compactly encased in a richly polished mahogany cabinet, 15 1/2" long, 9 1/2" wide, 9" high. Although comparatively small, it is equal in efficiency to our other types—has excellent tonal qualities and good volume. Cat. No. 5040. Price 105/-



## ALTERNATIVE TYPE OF HORN.

For those requiring a non-metallic horn, we can supply our speakers with imitation tortoise-shell flare as illustrated.

(2000 ohms.)

STANDARD. Cat. No. 5017 5:5:0

JUNIOR. Cat. No. 5008 3:5:0

TOM-TIT. Cat. No. 5003 1:10:0



## GRAMOPHONE ATTACHMENT

By utilising the tone-arm of a gramophone for the acoustic amplification of radio reception, a very effective Loud Speaker is provided. This attachment readily replaces the sound-box and produces excellent results.

Cat. No. 5210 2000 ohms Price 25/-

## USE "ACTON" ACCUMULATORS


A new range of low-tension Accumulators composed of separate 2-volt units. Produced at Acton in one of the finest equipped accumulator plants in the world. Note the following prices:—

Ign. Cap.	2-volt.	4-volt.	6-volt.
40 amps.	11/-	22/-	32/6
60 amps.	13/6	27/6	40/-
80 amps.	16/-	32/-	48/-
100 amps.	18/6	37/6	56/-

## H.T. 3. The Wonder Wireless Battery.

Outlasts dozens of dry cells and gives better results. Fully charged 60/-



# For these New C.A.V. Productions

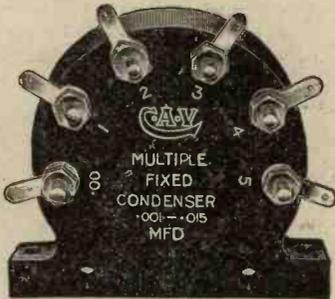

### MULTIPLE FIXED CONDENSER

This has been specially designed to enable a selection of fixed capacities being obtained from one instrument. By connecting up the indicated capacities in parallel as required, any range can be used to suit the individual set.

Cat. No.	Price.
5190 .001 to .015 M.F.	5/-
5191 .0001 to .0015 M.F.	

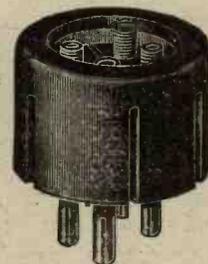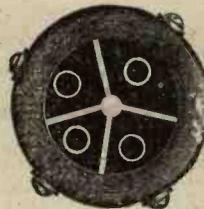

### A.C.A.V. VALVE HOLDERS


Of unique design, the A.C.A.V. Valve Holders are unequalled for their achievement of Anti-Capacity and Anti-Vibration results. For adapting to existing valve sockets, it is fitted with split pins as illustrated, whilst it can also be supplied for screw fixing.

Cat. No.	Price.
5200 A.C.A.V. Valve Holder	4/6
5201 A.C.A.V. Valve Holder Adaptor	5/-

### FILAMENT RHEOSTAT


With helical worked arm and interchangeable resistance unit. Very smooth and silent action. By means of a patented construction, the rotation of the contactor causes the resistance unit to revolve with it, thus ensuring smooth and silent action. The resistance unit can be instantly detached when required, to change from bright to dull emitter valves.

Cat. No.	Price.
5220 7 ohms resistance	5/-
5221 30 " "	

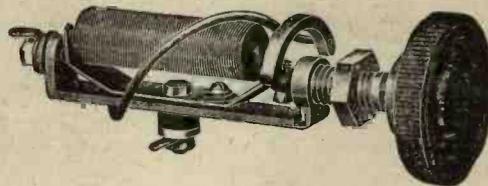
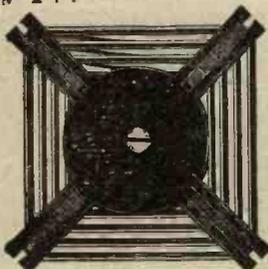
### TUNING COILS

With winding totally enclosed, these coils are wound with bare wire on a bakelite former. The illustration below shows the method of interior construction and indicates clearly the ample air space between windings. All coils have the same external dimensions—4" x 1".



Cat. No.	Approx W/L.	Price.
5180	250—400	6/9
5181	350—600	6/9
5182	450—900	8/-
5183	1000—1650	9/6

MANUFACTURERS OF MOTOR CAR ELECTRICAL EQUIPMENT



BY APPOINTMENT TO H.M. THE KING.

# Choice

If your aim is to reproduce the original sounds transmitted without distortion, make your next set with components bearing the C.A.V. initials—

### THE WORLD'S BEST.

If unable to visit the Albert Hall, write for copy of our complete Radio Catalogue.

**C.A. Vandervell & Co. Ltd.**  
WARPLE WAY ACTON LONDON, W.3

heard in the headphones. This indicates that the receiver is oscillating and that the reaction coil is correctly connected. If this does not occur reverse the leads going to  $L_2$  and try again. It is most important that this point be got right, otherwise it will be impossible to receive anything but the local station.

#### Some Preliminary Tests

The aerial and earth leads may now be connected under their respective terminals; unless there is any particular reason why it would be preferred to use parallel tuning, these will be  $A_2$  and E, by which the benefit of using both series and parallel tuning is obtained. Before connecting the set up to the aerial, the reaction coil should, of course, be swung well away from the aerial coil. If broadcasting is not in progress it would now be advisable to test for oscillation control. Bring the reaction coil up as before and the set should go smoothly into oscillation; if, however, it goes with a plock or loud plonk, different values of H.T. should be tried, small adjustments of filament current made, and lastly different values of grid leak substituted.

#### Coil Sizes

When broadcasting is in progress, find out which coil brings in your local station at the correct condenser setting; that is, if it is a relay with a wavelength of about 300 metres, it should come in at a low condenser reading; if Aberdeen, at the top of the scale. Suitable values for the coils to use will probably be a 50 or 75 for the aerial coil when series tuning is being employed as well as parallel, and a 35 or 50 for reaction. With some aerials it may be found that a 50 does not go quite as high as Aberdeen, and a 75 as low as Cardiff, or some of the relay stations working on a lower wavelength; in this case an intermediate size such as a 60, which is obtainable in several makes, will probably be found suitable.

#### Reception of 5XX


For Daventry the aerial may be connected to  $A_1$ , and  $A_2$  and E be connected together and to earth. This will give parallel tuning with both sections of the dual condenser connected in parallel; a suitable size for the aerial coil  $L_1$  will be a 150, with a 75 or 100 for reaction.

With a "stiff" aerial larger reaction coils than those mentioned may, of course, be necessary.
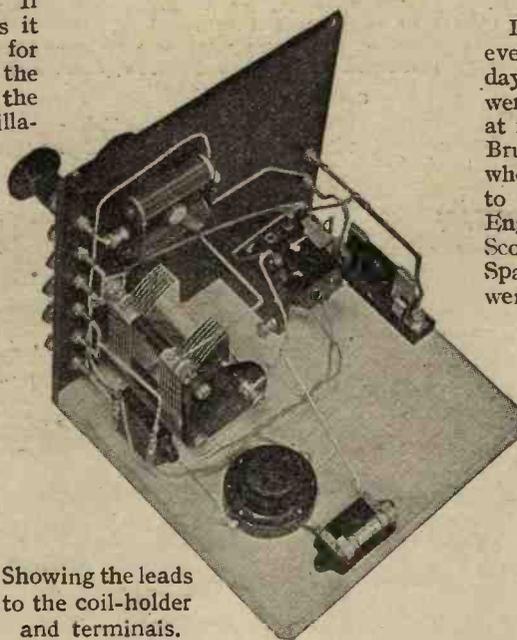
#### Searching for Distant Stations

Other stations may now be searched for by bringing the receiver into its most sensitive condition, namely, by bringing it to the point just short of oscillation, when carrier waves will be picked up as a slight hiss. If, however, whistling noises are heard which change in note only when the condenser dial is turned, the receiver is oscillating and the reaction coupling should be loosened at once, as you may be causing considerable annoyance to other set users.

A little practice will soon show you how to handle this set and get



Showing the leads to the coil-holder and terminals.

the best out of it, and it will be found surprising what large distances in reception can be covered with a single valve. If any drop in signal strength is noted when the condenser is nearly all out, it will be advisable to clip in a  $.0001\mu\text{F}$ , or even in some cases a  $.0002\mu\text{F}$  condenser in the mount fixed near the aerial terminals. This connects a small condenser in parallel with the series portion of the dual condenser, for if the value of this is too low sufficient energy from the aerial may not reach the tuned circuit  $L_1$ ,  $C_2$ , to operate the valve or to produce any but weak signals.

#### Test Report

When tested on the writer's aerial a very convenient size of aerial coil was found to be a No.

60, while a Gambrell B also was satisfactory. It was possible to cover the whole of the broadcast wavelengths with either of these coils, and even with the latter coil it was possible to get down below 200 metres, while its top range was just on the 600 metric mark. This was without using  $C_1$ , the clip-in condenser by means of which the series portion of the tuning condenser may be augmented, and the aerial being connected to  $A_2$ .

#### Coils for Daventry

For Daventry and Radio-Paris a 200 coil for  $L_1$  with 100 reaction will be found the correct size when using series tuning. With the aerial at  $A_1$ , and earth to E and  $A_2$  joined, a 150 for  $L_1$  will be large enough.


#### Stations Heard

During a short test in the early evening, when it was still full daylight, three B.B.C. stations were received without difficulty at fair strength in the phones, and Brussels, too, was strong, while when it got dark it was possible to tune in station after station, English (both main and relay), Scotch, French, German, Belgian, Spanish, etc. Over twenty stations were picked up in half-an-hour, notwithstanding serious interference from 2LO working at full blast within about three miles. Even a wave-trap does not completely eliminate this station's transmission, and it comes through on anything lower than 5NO or higher than Petit Parisien. Several stations that were heard could not be identified as they were working on wavelengths not given. They may possibly be new stations, or else old ones that have wandered away from their true wavelength. In view of the poor conditions obtaining at the writer's station (a mansion overshadows the whole of the aerial), results are very good indeed with this receiver, and many an interesting hour can be spent with it doing a little "aether searching."

#### THE WIRELESS EXHIBITION

Visitors to the Wireless Exhibition at the Albert Hall (Sept. 12th-23rd) should not fail to see the Radio Press stands, Nos. 51 and 52. Members of the industry should also make a point of visiting Stand No. 73, which is allotted to "The Wireless Dealer," the new trade journal of Radio Press, Ltd.
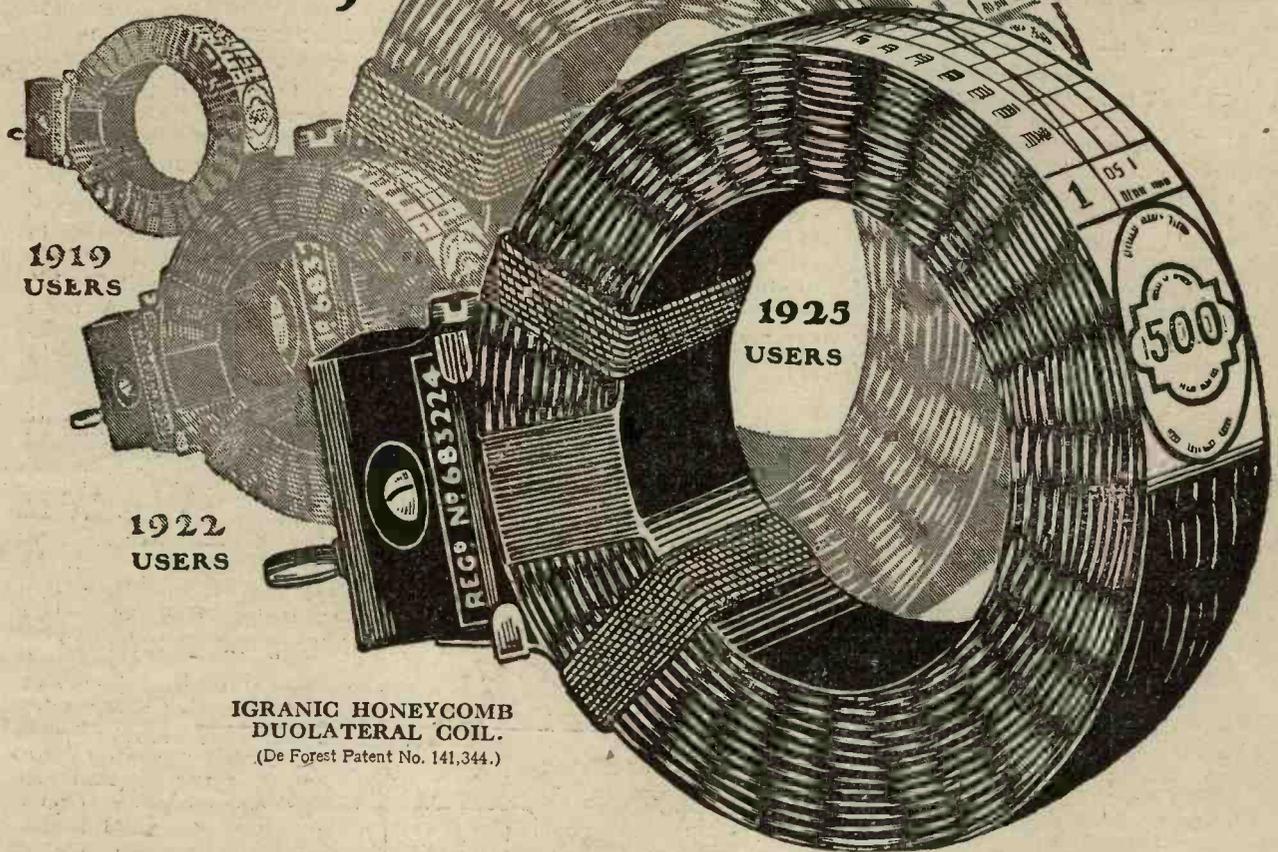
# The test of ever-growing popularity proves the merit of IGRANIC Radio Devices



IGRANIC HONEYCOMB  
DUOLATERAL COIL.  
(De Forest Patent No. 141,344.)

The public's appreciation of the Honeycomb Coil—the Igranich leader—typifies the favour with which all *Igranich Radio Devices* are regarded by discriminating wireless enthusiasts.

It is remarkable enough that the demand for *Igranich Radio Devices* should keep pace with the rapidly increasing body of the radio

public; but it is indeed a noteworthy testimony to the inherent merit of these Radio Devices that the percentage of *Igranich users increases* even more rapidly as, year by year, Igranich merit proves itself to experienced wireless enthusiasts.

The reputation built up by the world-famous Igranich Honeycomb Coil is ably sustained by the other Radio Devices—all of which measure up to the high Igranich standard.

If at any time you wish to have any information about Igranich Components write to Research Department U684 Igranich Electric Co., Ltd., Bedford.

**IGRANIC RADIO DEVICES include:**

Variable Condensers, Fixed Condensers, Filament Rheostats, Intervalve Transformers, Variable Grid-Leaks, Variometers, Vario-couplers, Coil-holders, Potentiometers, Vernier Tuning Devices, Switches, etc., etc.

All carry the IGRANIC guarantee

Write for **COMPANY** List U 684



149 Queen Victoria Street  
LONDON

Works: BEDFORD

Branches:

BIRMINGHAM	LEEDS
CARDIFF	MANCHESTER
GLASGOW	NEWCASTLE

# Experimenting with the Low - Loss Reinartz Receiver

By G. P. KENDALL, B.Sc., Staff Editor

*Some further notes upon the interesting receiver described in our last issue*

**L**AST month exigencies of space compelled me to compress the account of the operation and general use of the low-loss Reinartz receiver into the absolute minimum of words, and a number of points were of necessity omitted altogether.

The question of the method of arranging the set for reception of 5XX<sub>2</sub>, for example, requires further amplification. To receive the 1,600 metre wave station, the shorting plug is removed from the aerial circuit loading coil socket, and replaced by a coil of size No. 150. The choke coil now becomes the reaction coil in an ordinary single valve circuit, and the adjustment of the angle between these two coils should enable sufficiently strong reaction effects to be produced to enable 5XX to be heard at quite good strength. The right-hand condenser will also serve to adjust reaction on this wavelength, provided that the choke coil is not too large. For example, a 150 or 200 coil should now be used in the choke coil socket, to give the most convenient adjustment with the majority of valves. When such an angle between the coils has been found that by placing the reaction condenser at zero, the set does not oscillate, but begins to do so as the reaction condenser is increased to, say, half scale reading, both the coil sockets can be finally screwed down upon the baseboard.

## Size of Choke Coil

The size of choke coil to use upon the ordinary broadcast band is largely a matter of expediency, but in general the larger this coil the better. Certainly, nothing smaller than a No. 150 should be used. A No. 300 is a desirable size, and the type employed should be such as possesses only a small self-capacity, in other words, a "good" type of coil should be employed.

The actual operation of the receiver is a matter which I should imagine most of the builders of the set will by now have grasped. It should, perhaps, be emphasised that the methods of obtaining the necessary fine adjustments of tuning and reaction respectively are for the first the vernier con-

denser, and for the second the variable grid leak. This latter I find to give an exceedingly fine and smooth control, and this is of considerable importance in receiving weak signals. The procedure should be to find out at what particular value the grid leak should be set to give a smooth and gradual passage into oscillation by means of the reaction condenser, and then final adjustment of reaction should be made when required by slight movements on either side of this grid leak setting.

## Wavelength Range

The wavelength range given by the coil is a matter in which individual preference must play a certain part, and it will be remembered that I said that the number of turns for this coil should be about 65. This is the actual

perience, to make a tapping at, say, the 50th turn upon the coil, and provide some means of attaching the lead which normally goes to the upper end of the winding to this tapping point instead. This is very easily done if the lead in question is made of a short piece of flex, carrying upon its end a Burndept tapping clip. A point should then be scraped bare upon the 50th turn, and to this a short piece of tinned copper wire should be soldered, with an end projecting about half an inch, so as to afford a good grip for the clip. The lead can then be very readily transferred from the end of the coil to the tapping point as required.

## Selectivity

We now come to the question of the adjustment of the degree of selectivity given by the receiver,


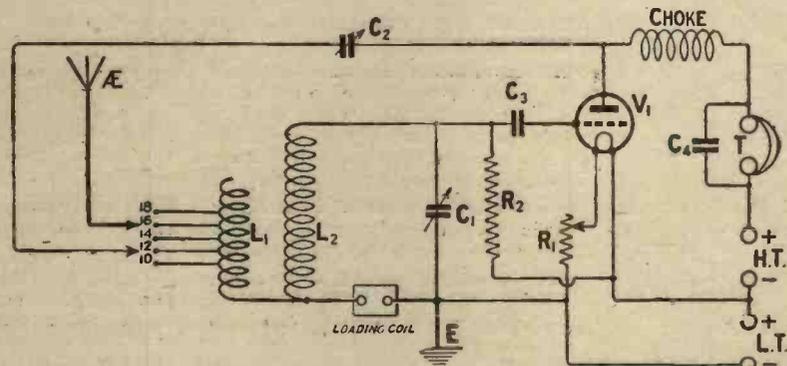


Fig. 1.—The revised circuit, showing the tapping points on the aerial-reaction coil.

number in my own set, and the wavelength range which it gives is from 302 to 634 metres. This, of course, omits certain stations below 300 metres, such as Brussels, which the constructor may desire to hear. I do not recommend in the case of this particular set that the number of turns upon the coil should be reduced so that it should cover such a band as, for instance, 250 to 500 metres, since if this is done a certain sacrifice of signal strength in receiving the longer wave stations will result.

A better method is, in my ex-

and here a little alteration to our coil will be necessary. This alteration merely consists in preparing some tapping points upon the aerial and reaction winding, which it will be remembered is composed of double cotton-covered wire. What is to be done is to take a pen-knife, and to prise up slightly a point in the 10th, 12th, 14th, 16th and 18th turns, counting downwards as the coil stands upon the base board. At each of these raised portions the wire is then scraped bare, and a short piece of tinned copper wire is soldered on, the result being shown in one of the

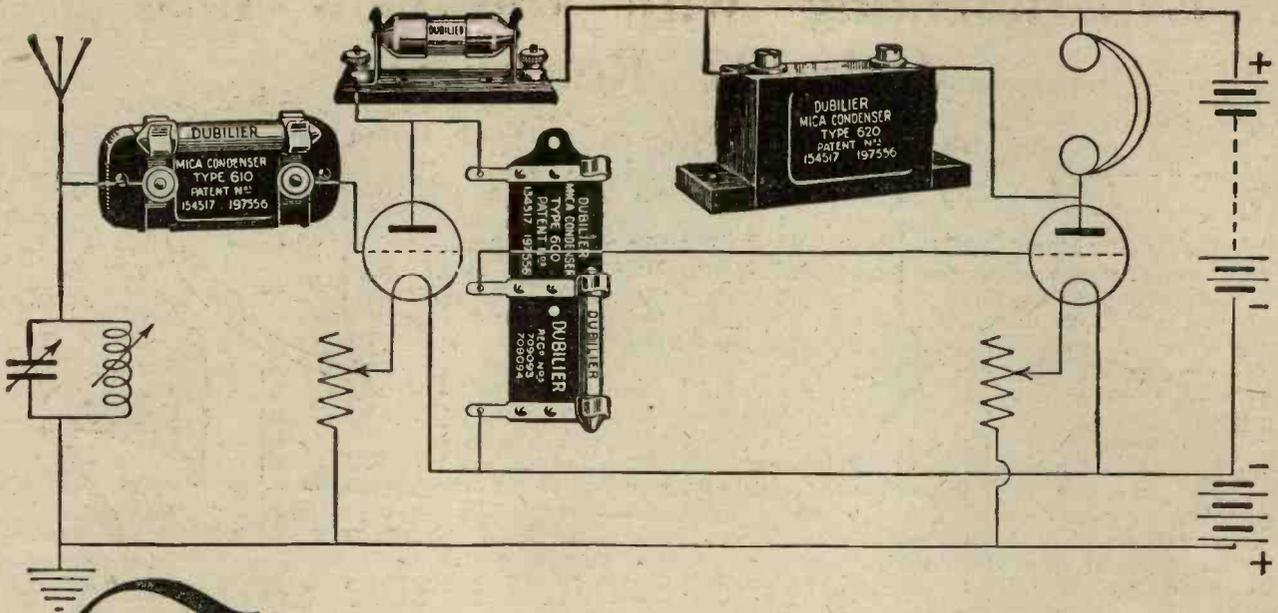

# Further Small Matters-

**T**HE components illustrated above are small but important. They are the highly specialised products of a notable firm—one which, among other things, was responsible for the introduction of Mica Condensers. Further, these components are characterised by the now well-known Dubilier standards of neatness and finish in construction and reliability in operation.

There is the Type 600 Dubilier Mica Condenser, for example:— a fixed condenser whose capacity is guaranteed by us to be accurate within close limits that are not often met with elsewhere.


A new Dubilier Grid-Leak Attachment is sold for use with it, and is illustrated above. It enables a Grid Leak to be inserted direct between the Grid and L.T. leads simply by clipping in, making use of one of the condenser clips and the clip on the attachment.

The Dubilier Anode Resistance, again, designed for extreme stability in operation, is tested during manufacture to 200 volts, and is absolutely reliable.

The new Dubilier Type 610 Mica Condenser is also shown. It was dealt with in a previous advertisement of this series—“Little Things that Matter.” It is suitable for use everywhere in receiving circuits, and is provided with screw terminals and detachable Grid Leak Clips.

For specialised products such as these, it is always easier and better to specify—

Mica Condenser, Type 600 (Also Type 600A for vertical panel mounting).	0.0001—0.0009 mfd...2/6
	0.001—0.006 mfd...3/-
Mica Condenser, Type 610 (with Grid Leak clips) (Also Type 620 for panel mounting).	0.0001—0.0009 mfd...3/-
	0.001—0.009 mfd...3/6
	0.01 mfd. .... 4/-
	0.011—0.015 mfd. ...4/6
Grid Leak Attachment, Gd. (for use with Type 600).	
Anode Resistance complete with holder 20,000—100,000 ohms. 5/6	
Grid Leak 0.5, 1, 2, 3, 4 & 5 megohms. 2/6	

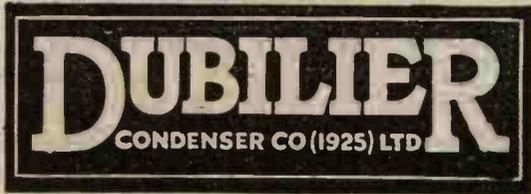


ADVERTISEMENT OF THE DUBILIER CONDENSER CO. (1925), LTD., DUOON WORKS, VICTORIA ROAD, NORTH ACTON, LONDON, W.3

TELEPHONE: CHISWICK 2941-2-4.  
E.P.S. 108

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.

BRITISH THROUGHOUT

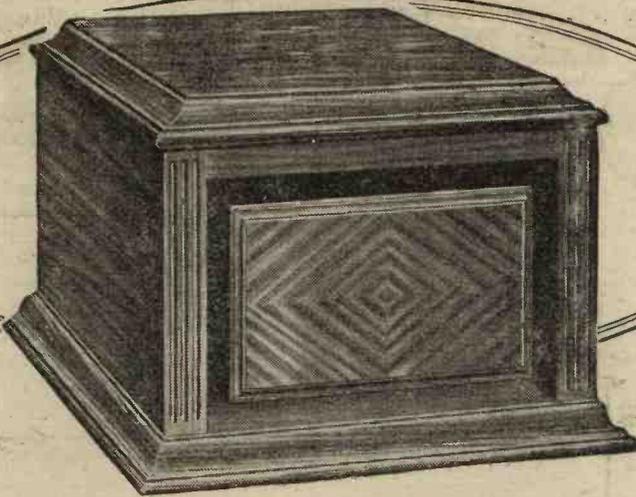

**The New HQ**

A handsome new Loud Speaker possessing the same beauty of outline as the luxurious Q-type whilst retaining the full volume and sensitiveness of the well-known H1. Can be supplied either in a rich brown colour or a glossy black. Polished mahogany base with nickelled fittings. A superb instrument which will charm everyone with its exceptional fidelity of reproduction. Height 20 in £6  
4000 ohms.  
Also in 120 and 2000 ohms.



**The New A-type**

At last we have been able to produce the new Brown A-type headphones at the sensational price of 30/-. The same famous tuned reed movement is used. At such a low price you cannot afford to be without a pair of genuine Brown A-type Headphones—famous throughout the world. 30/-

Brown Featherweight Headphones sold everywhere at 20/- per pair (4000 ohms resistance).

**Standard Brown Loud Speakers**

H2.	120 ohms	£2 5 0
	2000 ohms	£2 8 0
	4000 ohms	£2 10 0
H1.	120 ohms	£5 5 0
	2000 ohms	£5 8 0
	4000 ohms	£5 10 0
Q type in all resistances £15 15 0		



**The New H3**

A new Loud Speaker embodying all the well-known Brown features. Although only 15 inches high it gives the same superb tone as the larger H1 and is equally clear on speech and music. No other Loud Speaker on the market within several pounds of its price can give such a fine volume as the H3. £3  
In all resistances.



**The New H4**

We are proud of being able to offer a real Brown Loud Speaker—British throughout, and a replica in every detail of the larger models—at the amazingly low price of 30/-. Small in size but big in performance it is wonderful value for money. 2000 ohms. 30/-  
Height 10 inches.

**The New Crystavox**

The new and improved horn now fitted to the Crystavox will enable this Loud Speaker to give an exceptional volume of sound direct from a Crystal Set without the use of valves. The powerful Daventry Station will permit thousands of Crystal Set users to get Loud Speaker results direct from a Crystavox. £6

As pleasing to the eye as to the ear  
—this elegant Brown Cabinet Loud Speaker marks a new era in design

IT has been left to the manufacturers of the first Wireless Loud Speaker to produce the first British Cabinet Loud Speaker. The handsome Instrument illustrated above is a welcome relief to some of the more usual type of Loud Speakers. Beautifully finished in a rich rosewood shade and made of the best mahogany, it will undoubtedly achieve a very wide measure of popularity.

The same superb volume and purity of tone so characteristic of the Brown will be found in this new Cabinet model. If you have been prejudiced against the use of Loud Speakers—either on account of their appearance or their performance—your last objection has now been removed.

For supreme beauty of outline, clarity of tone and ample volume, the new Brown Cabinet Loud Speakers stands alone. Supplied in all resistances. £6/6/0


S. G. Brown, Ltd., N. Acton, London, W.3

Showrooms: 19 Mortimer Street, W.1. 15 Moorfields, Liverpool. 67 High Street, Southampton.

Depots (Wholesale only): 13 Bushy Park, Bristol. 5 Wilson's Court, Newcastle-on-Tyne.

**Brown**

HEADPHONES AND LOUD SPEAKERS

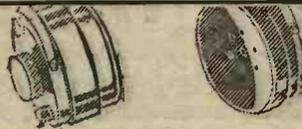

small sketches accompanying these notes. To any one of these tapping points it is then possible to attach a Burndept clip carrying a lead, and we shall require two of these clips in addition to the one already mentioned.

It is desirable to be able to vary the number of reaction turns independently of those used for coupling the aerial circuit to the secondary winding, and to do this it is necessary to remove the lead which previously ran from one side of the reaction condenser to the

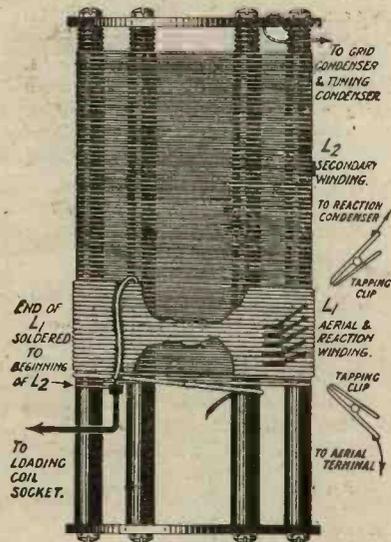


Fig. 2.—Details of the coil showing addition of tapping points.

aerial terminal. Simply unsolder the end which was at first attached to the aerial terminal, and leave this wire sticking out in the air. To the loose end thereby produced solder about 4 in. of flex, whose other end is to carry one of the tapping clips. This clip is then attached to one of the tapping points which have been made, and it will probably be found that almost the full number of turns can be used with advantage, a reduction to, say, 16 turns sometimes being a slight improvement.

To the aerial terminal should now be soldered another short length of flex, again carrying a tapping clip upon its end, and this may be attached to one of the tapping points which we have made, in order to vary the number of turns in use in the aerial circuit. This last adjustment is by far the most important one in the whole set, and a little care and patience should be devoted to it. In general, the smaller the number of turns

used in the aerial circuit the sharper will be the tuning of the set, and the less the interference from the local station, but if this reduction is carried too far the signal strength of the distant stations will suffer.

**Reduction of Aerial Turns**

In my own set I find that, if the number of turns in the aerial circuit is reduced to 10, signal strength is just perceptibly beginning to suffer, but tuning has become remarkably sharp and the distant stations are exceedingly pleasing to listen to, on account of the absence of general spark jamming and the other casual sources of interference which do so much to mar long-distance reception. This, perhaps, is a matter for individual taste, and many people may prefer to have somewhat greater signal strength with a little more jamming.

**A Wavetrap**

The tuning is so sharpened by a reduction of turns in the aerial circuit that interference by a local broadcasting station is very much reduced, but, in cases where such local interference is severe, I would strongly advise the reader to try the type of wavetrap developed by Mr. Cowper for this circuit, and with which I have had really remarkable results. Using a large and high aerial only about seven miles from the new 2LO station, with the aid of this wavetrap I find that, with this particular circuit, the interference problem is perfectly solved, since 2LO simply

vanishes off the dial, and there is no perceptible alteration in the signal strength of the distant stations, although their settings upon the dial are changed by the inclusion of the wavetrap. With the trap in use, I have heard Bournemouth without the slightest sound from London, and this without any difficulty or delicacy of adjustment. One simply sets the wavetrap, once and for all, and then proceeds to forget all about it and search for the distant stations in the ordinary manner. The effect is much as though 2LO had closed down and


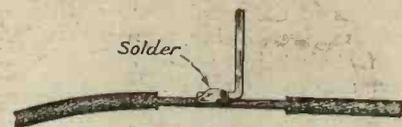


Fig. 3.—How the tapping points are made.

left one free to hunt for distant signals.

The addition of such a wavetrap is an exceedingly simple matter, and all that is required is a variable condenser of .0005μF and a coil in a socket. Connect these two in series, that is to say, take a wire from the moving plates of the condenser to one side of the coil holder. From the other side of the coil holder then take a wire to the earth terminal of the receiver, and from the fixed plates of the condenser take a wire to the aerial terminal of the receiver. Aerial

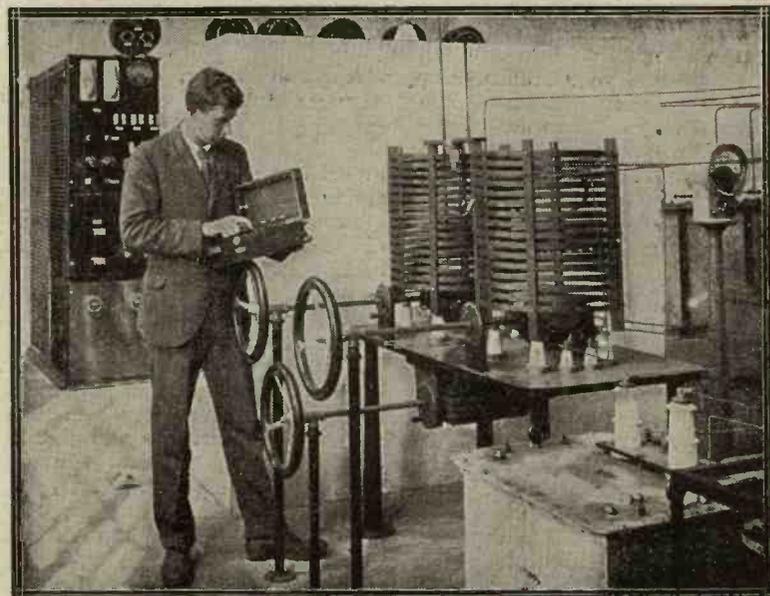

The new high-power station at Daventry. One of the engineers is here seen checking up the wavelength by means of a wave meter which he is holding.

and earth are connected as usual and the procedure is as follows: Set the dial of the receiver to a tuning adjustment which is fairly close, although not actually upon, that of your local station. Then insert a fairly large coil, say, a No. 75 or a Gambrell "C.", in the coil socket on the wavetrapp arrangement and proceed to turn the wavetrapp condenser very slowly until you find a point at which the signals from your local station fade down practically to nothing and upon either side of which they reappear. Having done this, simply proceed to search for the other stations in the usual manner with your receiver, being prepared for the fact that their settings will now have altered somewhat.

#### Size of Trap Coil

I have found this trap invariably successful whatever size coil is used in the socket which I have mentioned—that is to say, any size of coil which covers the wavelength will practically eliminate the local station, but there is definitely a best size so far as the reduction of the alteration in the settings of the different stations is concerned. On my own aerial and earth with the receiver which we are considering the effect of a rather small coil in the wavetrapp with a consequently large reading of the wavetrapp condenser is completely to upset the wavelength range of the Reinartz receiver. With such a circuit in operation the set will only tune down to about 380 metres, but this I have remedied by the use of a much larger coil and a smaller condenser setting in the trap circuit. The wavelength range is then very little affected.

The number of turns included in the aerial circuit by means of the appropriate tapping clip also affects this matter of range.

#### Wavetrapp Coil

The coil used in the wavetrapp must necessarily be one of low high-frequency resistance—that is to say, it must be a "good" coil. I have found the Gambrell "C" satisfactory, and, those who may care to wind their own coil instead of obtaining a number of plug-in coils to try, may do so by winding 80 turns upon a 3 in. diameter ebonite tube, preferably of No. 20 d.c.c. wire. This should be thoroughly dried, and kept dry. A tapping should be taken along this coil every ten turns after 50 turns have been wound on—that is to say, at 50, 60 and 70 turns. A little adjustment will then enable one to find out the best

number of turns to include in the circuit with the wavetrapp condenser.

#### Results

Before leaving the subject, it may perhaps be useful to give a fuller idea of the results which have been obtained with the original receiver. When I first finished the set I was decidedly disappointed with the results, since it was first tested early in August, when reception conditions were at their worst and most summery. Comparison with an ordinary plug-in coil single-valve set, however, soon showed that the low-loss Reinartz was in



Mr. Kolin Hagen, the chief announcer at WGY, whose voice is familiar to many British listeners.

actual fact giving remarkably good results.

Since that time, of course, conditions have very much improved, and upon trying out the set on a recent evening when wavetrapp experiments were being carried on, I succeeded in obtaining clear and distinct signals from every one of the main B.B.C. stations, with the exception of Cardiff, which was not separable from London with the wavetrapp arrangement available. Of the stations heard upon this occasion, Bournemouth, Birmingham, Newcastle and Belfast were really loud. Munster, Hamburg, the School of Posts and Telegraphs (Paris), Madrid, and three unidentified German stations were all also heard at quite good strength.

### Results with the Twin-Valve Receiver

(Radio Press Envelope No. 10)

SIR,—I think you might be interested to hear of my results with the "Twin Valve" described by Mr. John Scott-Taggart in THE WIRELESS CONSTRUCTOR for January.

Results are the finest that myself and scores of friends have ever heard, the aerial being about 80 ft. long and average height about 35 ft. single.

All stations in England come in, Birmingham and Bournemouth while 2LO is working, the latter (Bournemouth) on Sterling "Dinkie," perfectly audible at about 7-8 ft. on speech, while music is quite loud. Sunday nights between 5.30 and 8.30 most of the French and German stations are quite audible in the phones. Three Sundays ago conditions must have been very good, or else I was particularly lucky, as Hamburg, broadcasting opera, was heard by all the members of my family on the loud speaker, sitting about 3 ft. away. I have now had sufficient time to judge the capabilities of this set, and I doubt whether there is a more efficient type of set on the market made by an amateur.

London is painfully loud on the speaker, and the set has to be detuned.

I hope this letter will be of some interest, and if only those howlers would give up those "super" sets and build one such as the "Twin Valve" I think there would be more peace during broadcast hours and better results.—Yours faithfully,

E. W. SHEPHERD.

Upton Manor, E.

P.S.—This is no first-set effusion, as I have made four sets from *Modern Wireless* and THE WIRELESS CONSTRUCTOR.

**"WIRELESS"**

THE ONE-WORD WEEKLY

Edited by

PERCY W. HARRIS, M.I.R.E.

THE POPULAR WEEKLY

AT THE POPULAR PRICE

2<sup>D</sup>.

Everywhere

2<sup>D</sup>.

# An Entirely New Wireless Condenser

## GECOPHONE

### LOW LOSS-SLOW MOTION VARIABLE CONDENSER



THE large control knob, rotating in the same direction as the dial, easily allows the most delicate adjustments to be made.



THE patent reduction mechanism, giving micrometer adjustment without backlash. Dead silent, velvety movement in operation.

THE GECOPHONE Low-Loss Slow-Motion Variable Condenser will supersede the old-type condenser wherever valve sets are used. The result of close and protracted research into the essentials of *ideal* condenser design, it is entirely new in conception, and gives to tuning an amazing degree of ease, certainty and selectivity.


Wireless enthusiasts everywhere will discover in the new GECOPHONE Condenser the knowledge—not previously accessible—of what faultless tuning can be.

The GECOPHONE Low-Loss Slow-Motion Variable Condenser provides micrometer adjustment without backlash. Minimum capacity is uniquely low, hand-capacity eliminated, and dielectric losses are the smallest possible. The condenser is adapted for one-hole fixing, and can be mounted on a metal panel—without insulation.

Sold by all GECOPHONE service depots, wireless dealers and stores.



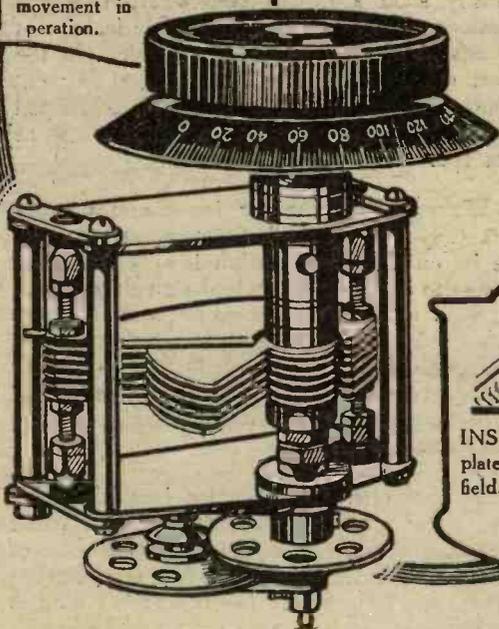INSULATION of fixed plates outside electrostatic field. This reduces losses to a minimum.



#### PRICES

·0002 mfd	...	...	22/-		·0003 mfd	...	...	24/-
·00025 mfd	...	...	23/-		·0005 mfd	...	...	27/6
·001 mfd	...	...	...		...	...	...	32/6

(Manufacturers — wholesale only)

THE GENERAL ELECTRIC Co., Ltd.

Head Office: Magnet House, Kingsway, London, W.C.2

# THE WUNCELL

## —a centenarian among Valves!

OUR morning mail would be exceptional if it did not contain at least one letter from some enthusiastic Cossor user commenting upon the long life of his valve. Among our most treasured possessions are these hundreds of letters—each one of which has been written spontaneously to express the writer's keen approval of the satisfactory service he has received.

Typical among them is the following from Mr. H. Hayward, of 9 Daisy Gardens, Dagenham, Essex. He writes as follows :

*"On looking through one of your ads. in 'Modern Wireless' a few days ago, and noticing the claims of some of your users, I think I ought to bring to your notice the performance of one of your valves. I bought this in July 1923, and after using it practically 4 hours per night on the average, and more so during week-ends, it has just given up the ghost. I reckon the life of this valve at about 4000 hours. Can anyone beat this? I won't say any more!"*

But if the Cossor bright emitter is reckoned to possess a long working life, then truly the Wuncell Dull Emitter is a centenarian among valves. Here is a valve which is fitted with an entirely new type of filament—one which can be obtained in no other valve.

A filament which, instead of being whittled down to an exceptional thinness to obtain low current consumption, is actually *built up layer upon layer* until it is practically as stout as that used in a bright emitter valve. A filament which, mounted in arch formation and further secured at its centre by a third support, will readily withstand all the shocks and abuses of everyday use. A filament, moreover, that owing to its unique method of manufacture gives off an intensely powerful electron stream when barely glowing.

Ally such a wonderful filament to the Cossor construction and you'll readily appreciate why the Wuncell gives a standard of performance which has not yet been approached by any other valve.

The essential features of every Cossor Valve—irrespective of type—are its hood-shaped Grid and Anode and its arched filament. As every wireless enthusiast knows, the action of the 3-electrode valve depends upon an effective use being made of the electron stream given off by the heated filament. Previous to the introduction of the Cossor this had always been done by means of a spiral grid and a tubular anode. But obviously such a design suffers from severe limitations on account of considerable leakage of electrons from each end of the anode. In the Cossor, on the other hand, the arched filament is almost totally enclosed by the hood-shaped Grid and Anode, and few, if any, of the electrons can escape.

The Wuncell Dull Emitter incorporates every salient Cossor feature. It functions at 1·8 volts, while its current consumption is only ·3 amp.—so low as to enable the standard six-volt accumulator, with its cells connected in parallel, to last six times as long as with bright emitter valves. The man changing over to Wuncells from ordinary valves, therefore, gets an additional *five weeks' Broadcasting free of cost* every time he has his accumulator charged.

So that, not only do you get a long-life valve when you choose the Wuncell, but you effect tremendous economies as well. In the face of such incontrovertible facts can you delay buying Wuncells any longer? In two types: W1 for use as a Detector or L.F. amplifier, and W2 (with red top) for use as a high-frequency amplifier. 14/- each from all Wireless Dealers

**A. C. COSSOR LTD.—Highbury Grove, London, N.5**  
**MANUFACTURERS OF COSSOR AND WUNCELL VALVES**

## Appointment of Mr. J. H. REYNER, B.Sc., A.C.G.I., D.I.C., to the Staff of Radio Press, Ltd.



A recent portrait of Mr. Reyner.

**I**N connection with the development of our Research Laboratories at Elstree, we have considerable pleasure in introducing to our readers Mr. J. H. Reyner, who recently joined the staff of Radio Press, Ltd.

Mr. Reyner, although comparatively young, is possessed of high qualifications, his career at the City and Guilds (Engineering) College being a record of successes.

On entering college he went straight into the second year, at the end of which time he obtained the John Samuel Scholarship for the best student of the year.

At the conclusion of the third-year course he obtained the Associateship of the City and Guilds Institute (A.C.G.I.), and again headed the list of successful candidates, thereby gaining the Unwin Scholarship. He further achieved the distinction of gaining the Henrici Medal for the best student in Mathematics.

He followed this up with a fourth-year course in research

work, under Professor G. W. O. Howe, on Radio Telegraphy and Telephony, at the conclusion of which he was awarded the Diploma of the Imperial College (D.I.C.).

During the same year he also obtained the B.Sc. Honours degree of the University of London, the special subjects being Electrical Engineering and Mathematics. Perhaps, Mr. Reyner's qualifications can best be appreciated from the following extract from an official college document: "This brilliant record is nearly, if not quite, unique in the annals of the college."

### Experience in the Post Office

Since leaving college in 1920 Mr. Reyner has been engaged with the Post Office Engineering Department. He has been responsible for the design of receiving equipment at the various coast and other stations controlled by the Post Office.

This work has been of a varied nature, involving the design and

construction of all types of receiving apparatus from simple "one knob" sets up to multivalve highly selective equipment. In the course of the work he has obtained practical experience of the use of transmitting and receiving apparatus in all parts of the country.


He has further been responsible for the design of complete receiving stations which have been erected under his supervision, including, in some measure, the Direction Finding Service, which is now being rapidly developed, so that he has been able to keep well in the forefront of developments in wireless reception.

Mr. Reyner has already obtained considerable experience in the preparation of articles of interest to the radio public, and has, in fact, written two books on the subject. One of these, "Modern Radio Communication," is fast becoming accepted as the standard low-priced textbook on wireless.

The second book, entitled "Radio Engineering," is a very valuable collection of data, which embraces every phase of the science, and was published by Radio Press, Ltd., on September 1.

Mathematics, as such, are of little interest to the average reader. Mr. Reyner, however, while intimately conversant with the more technical and mathematical aspects of radio, is an expert in the art of investigating problems from a theoretical and practical standpoint, and subsequently placing the results obtained in a very simple form, easily understood by the non-technical public.

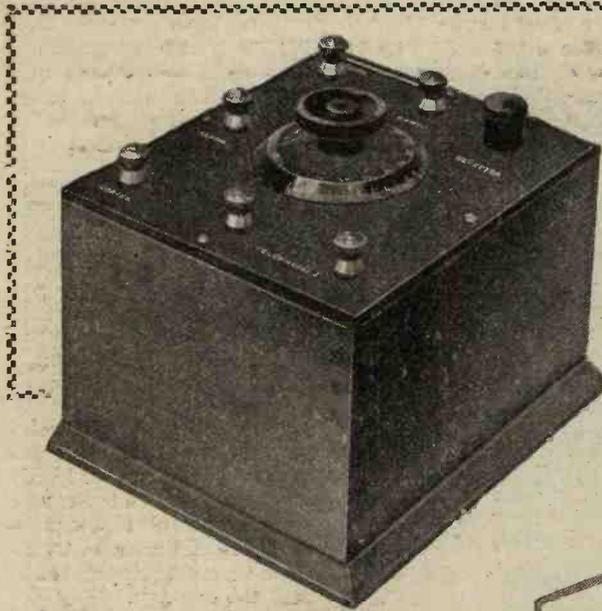Our readers may, therefore, look forward to a series of most helpful articles from Mr. Reyner's pen, many of which will be the result of research work carried out at our new laboratories, and of which a large proportion will indicate, from theoretical considerations, the most fruitful lines of experiment on any given subject.



## How to Build a Variometer-Tuned Crystal Set

By PERCY W. HARRIS,  
M.I.R.E., Editor

*Variometers have not attained great popularity on account of limited tuning ranges, but with the introduction of a new type this difficulty is overcome, and the set described will be made by many readers*

made so short as to reach the 300 metre to any wavelength from 300 to 500 metres. It is difficult for a single variometer, unless it is very

WHEN the British Broadcasting Company's stations were first erected, and before the long wave station at Chelmsford came into operation, variometers were quite popular for tuning crystal sets. For the benefit of new readers who are not acquainted with all wireless terms, it may be stated that a variometer consists of two coils of wire, one of which can be rotated either within or close to the other, the tuning effect being such that it varies as the angular relation of the two coils varies, giving a progressive increase of wavelength tuning between the two limits of the scale. The disadvantage of variometers is, however, that they will not generally cover a very wide range of tuning, so that when the 5XX station was started it was found to be beyond the tuning range of the average variometer receiver.

Another problem arose when the wavelengths of relay stations were

A view of the wiring. Note in particular the connections to the variometer.

mark, for then it was necessary for a successful commercial receiver to be able to tune

efficiently designed, to cover this range with all aerials. Variometers are more sensitive to changes of aerial than most other tuning systems, owing to the great influence of the aerial capacity.



### Reception of 5XX

The variometer crystal set described in this article, however, is free from any of the faults mentioned. By the use of two fixed condensers it can be adapted to almost any aerial and will, in addition, receive 5XX satisfactorily. The appearance is neat, and as no loading coil is required, the space occupied by the complete receiver is less than is often the case. The photograph will show the construction clearly, and the wiring diagram will show you how simple it is to join up. The component parts are few, and are as follows:—

One Dubilier Mansbridge variometer.

Six terminals.

One panel of ebonite or other

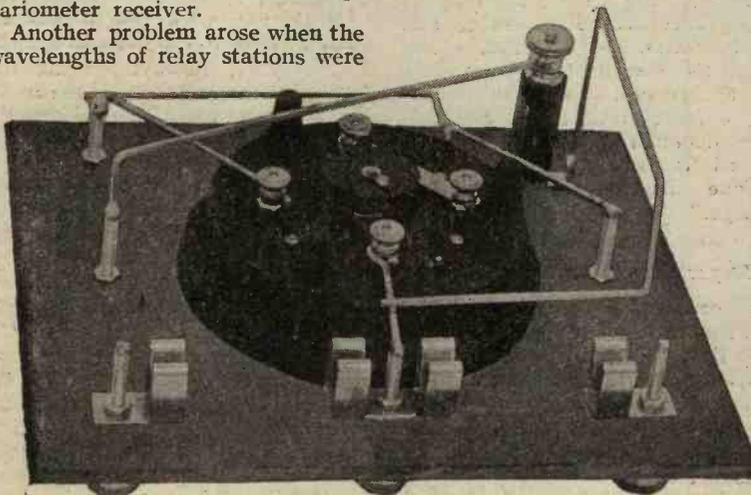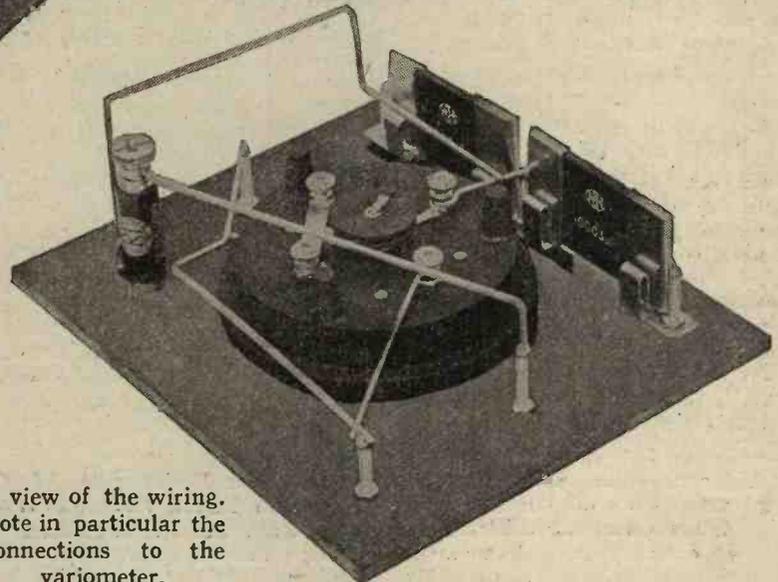

This view shows the connection to the crystal detector and fixed condenser clips.

suitable insulating material, 7 in. by 6 in.

One fixed condenser with clips, .0003  $\mu$ F (McMichael).

One fixed condenser with clips, .002  $\mu$ F (McMichael).

One crystal detector for back of panel mounting (R.I. Permanent).

Suitable box.

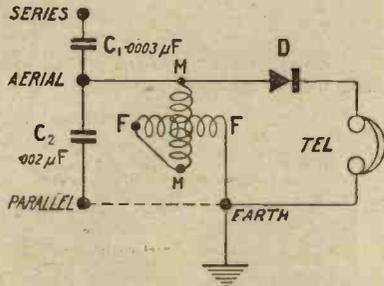


Fig. 1.—The dotted connection is only made when it is desired to receive 5XX.

**Radio Press Panel Transfers**

In the package of the variometer you will find a paper template, which will show you exactly where to drill the holes in the ebonite panel for mounting. It will also tell you the drill sizes. Two screws are provided with the variometer for fixing to the panel, and you will notice that there are two strips to join the terminals at the back. Only one of these strips should be used in this set in the way


shown. The permanent detector is of the "one-hole fixing" variety, and is provided with a cover for the adjusting knob. Once a suitable setting of this crystal has been found it can be left for very long periods, if not indefinitely, and should not be changed without good reason.

**Condenser Clips**

Notice particularly the position of the clips for holding the fixed condensers. Two of these clips are made to overlap, so that the two holes are superimposed. A terminal is passed through these holes, and locked into position with a lock-nut. Be careful to place the two fixed condensers in their correct positions. Wiring up is so arranged as to be simple and short.

The set is very easy to use, and you will soon find the best tuning positions. If you have a very long aerial and the wavelength you desire to receive is on the shorter end of the B.B.C. scale, connect the aerial to the lowest terminal on the front left-hand side of the receiver, and leave the two upper terminals open. The earth is always joined to terminal E. Try, also, connecting the aerial to the middle left-hand terminal instead of the lowest. You will probably receive good signals on both of these arrangements, the only difference being the position on the tuning scale. One of these arrangements will probably be better than the

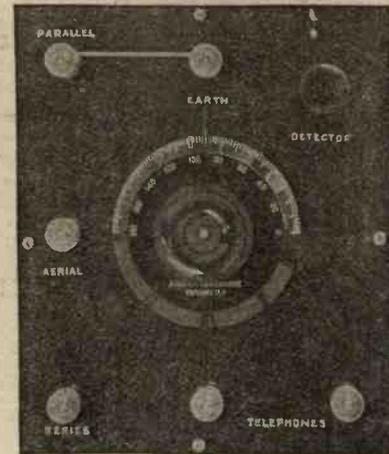other for your particular aerial, and once you have found it, adhere to this for your local station. To receive 5XX, it is merely necessary to place the aerial connection on the middle terminal, and to join the terminal marked "Parallel" to the terminal "Earth." You will



A straight-on view of the panel.

then find 5XX on the upper end of the scale.

**Extra 'Phones**

If you desire to use more than one pair of telephones in this set, you can easily do so. For two pairs place one tag of each pair of telephones under each telephone terminal, and join the other two tags with a connector.

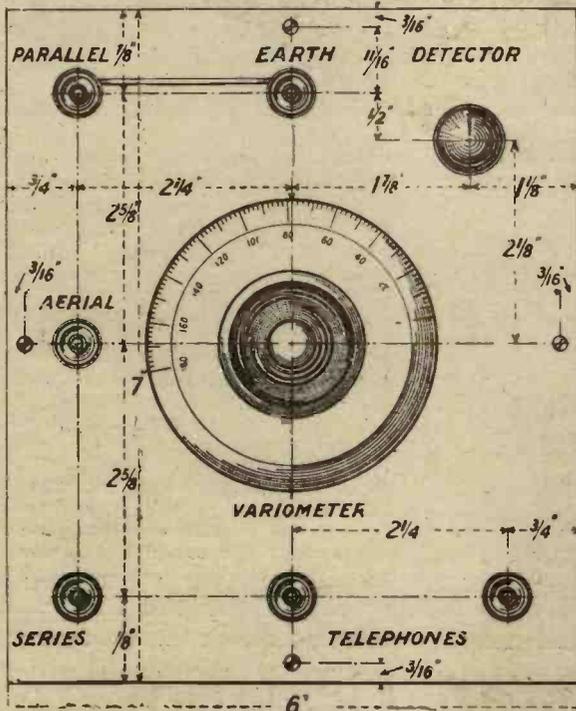


Fig. 2.—How to drill your panel. A drilling template is supplied with the variometer.



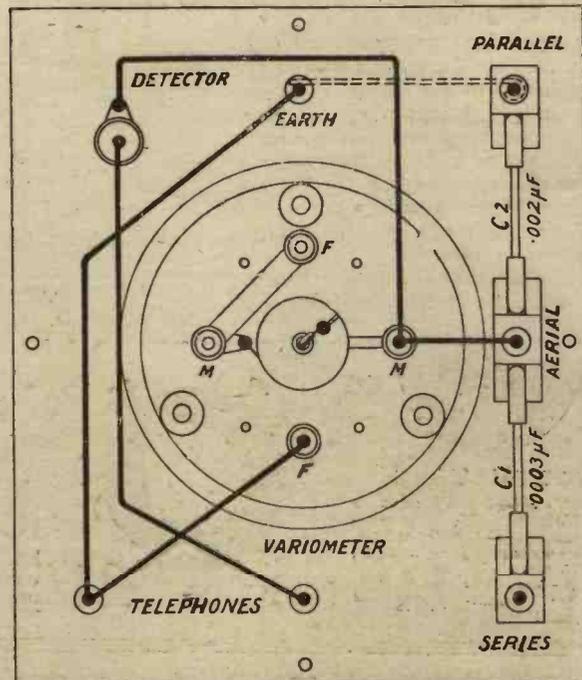


Fig. 3.—The wiring is carried out like this. The dotted connection indicates the strap on the face of the panel.

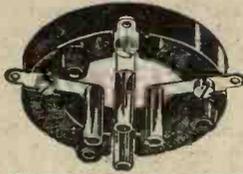

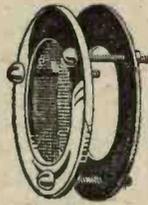
**"ANTIPONG" VALVE HOLDER**

Low loss, anti-capacity and shock absorbing, this holder prevents all microphonic noises in Dull Emitter Valves and reduces inter-electrode capacity to a minimum. Valve legs are surrounded by air and attached by Phosphor Bronze springs to a bakelite ring that will not melt under soldering iron. Universal fitting, with screws for baseboard or panel mounting **3/-**



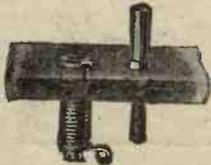
**VALVE WINDOWS**

Superior appearance and finish. Made of heavily nickel-plated brass. Outside diam. 1 1/2 in., gauze covered opening, 1 in. Rounded edges. Supplied complete with backing plate and all screws, etc. **9d.**



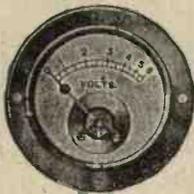**COIL PLUG AND SOCKET**

Three types made. One for baseboard mounting with top connection; another mounted on circular ebonite flange for use on Wood Panels and Cabinets; a third consisting of plug and socket only for panel mounting. Baseboard or Flange Type, 2/6 each. Panel Mounting Type **9d.**



**VOLTMETERS**

Reasonably priced instruments for Panel Mounting. Specially made for sets using Dull Emitter Valves. Current consumption at 3 volts, only .045 amps. Instrument fits hole 2 1/2 in. diam. Beautifully finished **14/-**

**ALL WORTHY OF YOUR SKILL**

Every ounce of thought and care you put into building your sets is backed up and encouraged by the sheer responsiveness of Bowyer-Lowe Tested Components.

We expect you to demand from them a high standard of performance. They are made carefully, tested stringently, so that they will give you results which exceed your anticipation.

Every Bowyer-Lowe Product is fully guaranteed for one year, and dealers who stock these Products know they are desired to interpret that guarantee generously.

Make up your mind to use these trustworthy parts in all your sets this year.

**SEND for a COMPLETE CATALOGUE**


of all Bowyer-Lowe Components. It is free for your request on a postcard. Within it you will find much useful data, and information that will help you to get the maximum satisfaction from every set you make.

**BOWYER-LOWE**  
CO., LTD. LETCHWORTH



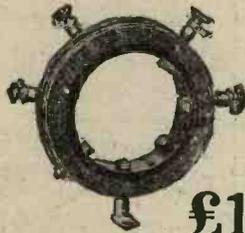
**SUPER-HET. TRANSFORMERS**

Built expressly for use with British Valves. These Transformers give unusually high amplification with purity of signals. Amateurs who have made the Seven Valve Receiver described in the brochure accompanying the Transformers say it surpasses any they have heard in selectivity and freedom from noisy background. The complete set of Transformers, individually matched and tested **£4**



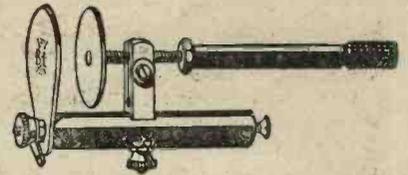
**OSCILLATOR-COUPLER**

MODEL II, a late development of Super-Het. design. Operates on direct coupled system without a pick up coil. More sensitive than older types of coupler. Covers 260 to 550 metres when tuned with Bowyer-Lowe '0005 Square Law Condenser. **£1**



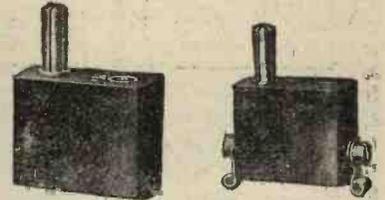**NEUTRODYNE CONDENSERS**

Designed for use in Neutrodyne circuits, this instrument has also proved exceedingly valuable as a vernier when used in parallel with a larger condenser. It is invaluable in Super-Het. circuits. Fitted in panel with single screw and 3/16 in. hole for spindle **5/-**




**SHORT CIRCUITING AND TRANSFER PLUGS**

These components are very useful where it is desired to short circuit a reaction coil or to transfer connections from a coil holder to some other part of a circuit. Made of best ebonite, highly polished, and solid brass.

Short Circuiting Plug **1/6**

Transfer Plug **2/-**

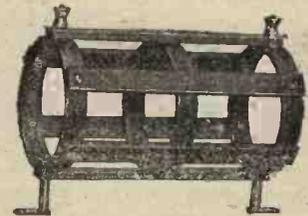

**LOW LOSS COIL FORMERS**

Skeleton Formers should always be used to ensure efficiency, especially on short wavelengths. The series made by Bowyer-Lowe covers most needs of the amateur for both reception and transmission.

3 1/2 diam. by 6 in. long 5/- 4 1/2 diam. by 8 in. long 8/6  
4 1/2 " " 4 in. " 6/- 4 1/2 " " 10 in. " 10/-  
4 1/2 " " 6 in. " 7/6 For A B C Wavetrap 2/6

**A BALL-BEARING CONDENSER**

If you have not had particulars of the new Condenser made by the Bowyer-Lowe Co., you should write for descriptive leaflet at once. The FOUR-SQUARE Condenser has balanced vanes, soldered in position and mounted on ball bearings. Each condenser has four available capacities, and its losses are appreciably lower than has ever previously been possible. Enquire about this instrument to-day.

Wireless Exhibition, Albert Hall, Sept. 12-23

**Bowyer-Lowe Tested Components**

RADIO WORKS

[Wireless Exhibition, Albert Hall, Sept. 12 to 23]

LETCWORTH



# MR GUMPLETHORPE

## Builds His Set

By "BROADCASTER"



IT is quite a long time now since I told you anything of the adventures of Mr. Gumplethorpe, but that does not mean to say that he has not had any. Far from it. Life with Mr. Gumplethorpe since he took up wireless has been one long adventure. He knows now quite a lot about this great science. He has discovered (practically) something about voltage by placing his fingers inadvertently upon the output terminals of a set using a power valve; he knows what a difference aerial height makes, having fallen from both a high mast and a low one; he knows all about the effects of deep and shallow

details of every set designed, and at one time had thoughts of making them all. As, however, he started rather late it occurred to him that he would never be able to catch up, and he did not like the prospect of being about two years behind. After much consideration and cogitation he narrowed down his selections to two. The choice lay between the "Flannelly Four" and the "Fan's Own Frantic Six," both of which were designed, and produced by Mr. Hercy Parris in his happiest moments. Has it ever occurred to you to notice what beautiful names Mr. Parris chooses for his sets? Some time ago he produced one with a name so touching that no one could read it or speak it without a tear in his eye and a catch in his throat. This was the "Old Folks'" Receiver. Just say "old" to yourself, and you will find that you simply cannot help picturing granfer and grandma, toothless and bent but still smiling, sitting by the fire with the headphones on. Granfer smokes his pipe, and chuckles and slaps his thigh every now and then, whilst grandma is so carried away by what she hears that she quite forgets to turn the heel of the sock which she is knitting for granfer, and makes the foot about a yard and a half long.

rather smaller housekeeping cheque each week? Mrs. Gumplethorpe said that she could not. Mr. Gumplethorpe said that she must. And she did. In hard times when business is bad the only thing to do is to take up a hobby, and immerse yourself in it, so as to take your mind off worries. Mr. Gumplethorpe explained all about this to Mrs. Gumplethorpe, and proved to her most ingeniously that he was really economising tremendously by spending money like water upon valves and condensers and rheostats and grid leaks and coils and B.A. thingmejigs. He explained, too, when he arrived home evening after evening bearing his purchases in a taxi that it was quite impos-



He has discovered something about voltage!

earths, having dug the holes for both; he knows what it is to live at the rate of £10,000,000 a year, having blown up five valves in a fraction of a second through a misunderstanding about the high-tension leads. His knowledge, then, has increased by leaps and bounds since we last met him. But until quite recently he had never undertaken anything very ambitious in the way of building a set. His earlier efforts were what he called hook-ups, though to the casual observer they looked as if he had forgotten to do up most of the hooks. He did his wiring, too, in the cat's-cradle, Clapham Junction, Hampton Court Maze, or go-as-you-please style. But all this kind of thing is now passed. After a long and strenuous apprenticeship Mr. Gumplethorpe decided last week that the time was ripe for him to make something that was really worth calling a receiving set.

### His Choice

As an earnest student of Radio Press publications he drank in the

Economy!  
But to return to Mr. Gumplethorpe. The Flannelly Four appealed to him very much, since with only four valves he could not do in more than thirty-four shillings' worth at a time should he happen to make any mistake with the high-tension connections. On the other hand, Mr. Gumplethorpe does like to have a set with some juice behind it, so that he can let the loud speaker rip when he wants to. It took him some time to make up his mind, but eventually he fixed upon the Fan's Own Frantic Six. And now began a very sad time for Mrs. Gumplethorpe. He began to suggest to her that times were rather hard, what with rates and taxes and one thing and another, and could not she possibly do with a



The "Old Folks'" Receiver.

sible for him to travel by trams or buses or tubes or trains, because they always made him worry so. Mrs. Gumplethorpe wanted the drawing-room repapered. Mr. Gumplethorpe said that the old paper would do quite well, and that anyhow it was no good putting on a new one, because if they did it would be just his luck to splash his accumulator all over it or do something awful of that kind. He said that he always felt uncomfortable when there were new papers and things of that sort about for real comfort give him old paper, old paint, an old carpet, old furniture, because then you felt that you could do what you liked, and had not always to be thinking about the awful things that might happen if you were not careful. Having been shorn of her housekeeping money, Mrs. Gumplethorpe cut down the menu considerably. Mr. Gumplethorpe strongly approved of this manifestation of economy, and showed his approval by lunching in the City and dining at his club.

# Important Announcement!

ONE of the most decisive and beneficial steps ever taken in the history of British Wireless has been accomplished by a collaboration between the world-renowned manufacturers of Mullard Valves and Philips Glowlampworks Ltd., the famous lamp and valve makers in Holland.

This outstanding collaboration secures for the British Wireless Industry—

- (1) The stoppage of all imported foreign valves into Great Britain, Northern Ireland or the Irish Free State by Messrs. Philips, the largest exporters of Radio Valves to this country.

This will mean an immediate call for **INCREASED BRITISH PRODUCTION** to meet the demands of the home market, thus producing **MORE WORK FOR BRITISH LABOUR!**

- (2) The exclusive use in Great Britain by the Mullard Radio Valve Co. Ltd. of all Philips Patents and improved manufacturing processes relating to the specialised manufacture of Radio Valves.

This means that all Mullard Valves will be produced under the combined valuable Philips and Mullard Patents and will be manufactured in Great Britain, thereby providing an enormous increase in the employment of skilled and unskilled British Labour.

- (3) The use of all machinery designs of Messrs. Philips by the Mullard Co. in connection with the manufacture of Radio Valves. These designs are extremely valuable and are exclusive for use in England to the Mullard Co.

The advantage of the very latest designs in machinery cannot be overrated. The delicate and highly-skilled work of valve manufacture will be improved and increased by the use of this modern plant, and there will be

**AMPLE SUPPLIES OF MASTER VALVES FOR EVERYBODY.**

- (4) The combined efforts of both the Mullard and Philips technical experts to obtain from experiments and research in their extensive laboratories all radio valve developments from time to time.

This means that Mullard Valves will carry the superior advantages of thorough research and contain the most advanced designs for **PERFECT RADIO RECEPTION.**

This gift of service to the British Wireless Industry will consolidate and preserve the high standard in the productions of Great Britain and further the endeavour for the improved

**EXCELLENCE OF BRITISH BROADCASTING.**

The Radio Public of this country will be the first to recognise the wonderful advantages of this Master Collaboration particularly when it means

**MORE WORK FOR BRITISH LABOUR AND BETTER RADIO VALVES**

*Support British Endeavour and*  
**BUY BRITISH GOODS**



# Mullard

## THE · MASTER · VALVE



Advt.—The Mullard Wireless Service Co., Ltd., 45, Nightingale Lane, Balham, London, S.W.12

# Mullard Master Research

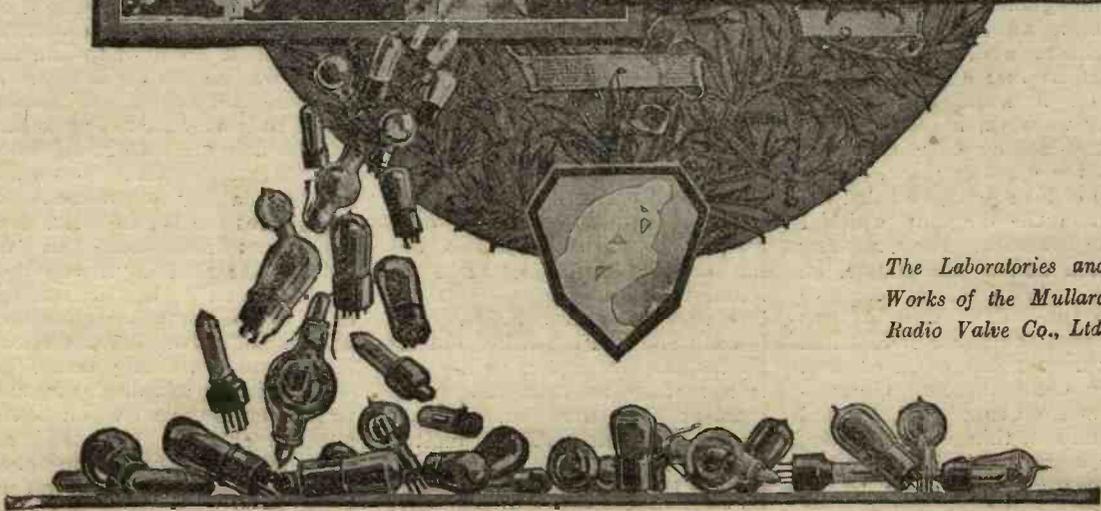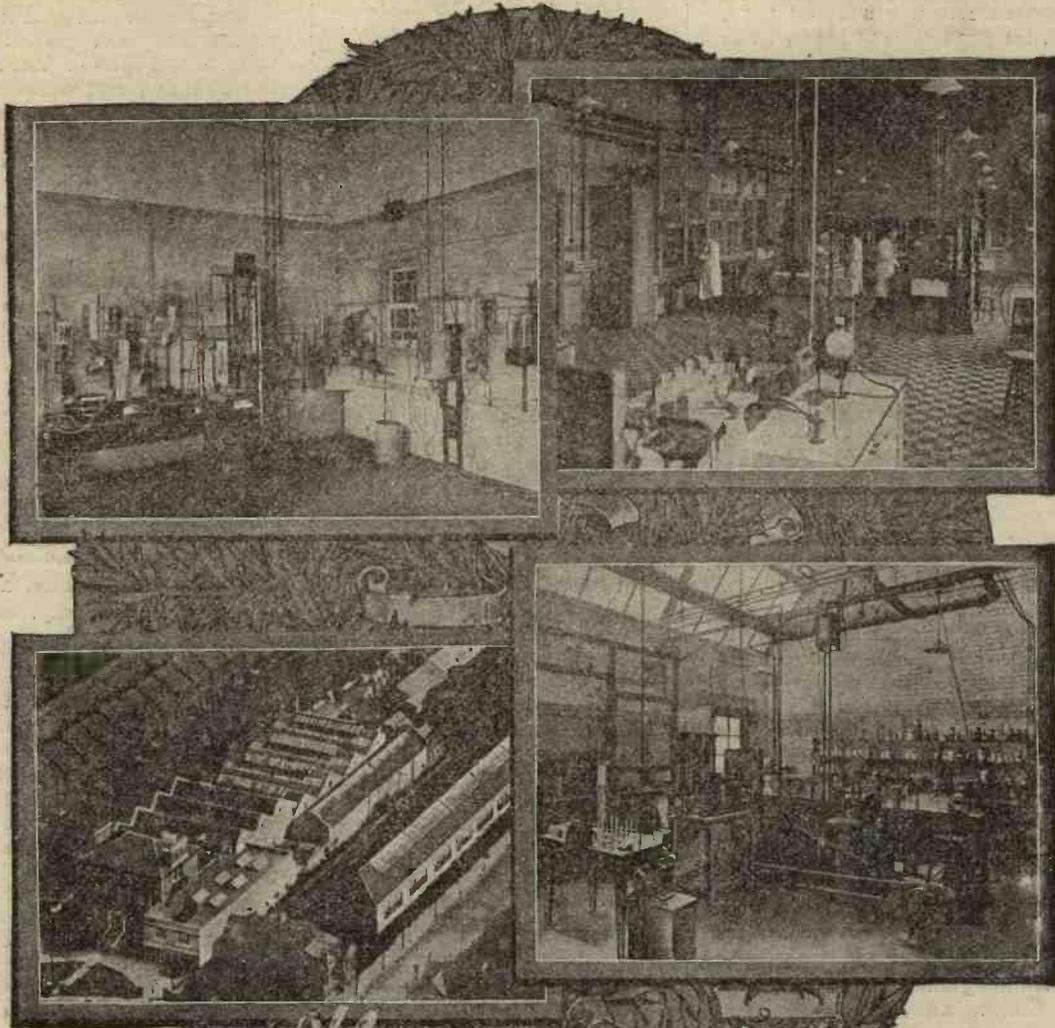


*The Laboratories and  
Works of the Mullard  
Radio Valve Co., Ltd.*

Advt.—The Mullard Wireless Service Co., Ltd., 45, Nightingale Lane, Balham, London, S.W.12

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.

Meanwhile, the store of gadgets that he was collecting in his study was growing vastly as the days came and went. In every chair, upon the writing-desk, and the table and the floor and the mantel-piece and the window-sill, and even in the coal-scuttle, which, being empty since it was summer time, formed a good storing place, there were parcels and boxes, and crates and paper bags and all sorts of things. He began the work of construction by tidying up his writing-table. This was quite easily done by placing its contents upon the floor. To the top of it he fixed his vice with four stout screws. The screws were rather long and he had forgotten all about the drawers underneath. To open one of them he now has to remove the vice, but he does not mind little things of this kind. Such was the array of

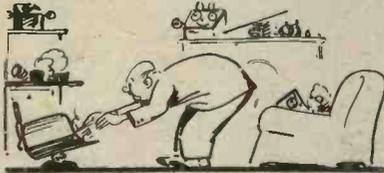

Even the coal-scuttle . . .

tools that he purchased that he felt that he could tackle every single job himself with every hope of making a real success of it.

#### Squaring the Panel


The first business was to square up the shiny ebonite panel that he had brought home with him. For some reason unknown at present, no small wireless shop is ever able either to square a panel or to cut it to the correct measurements. When he ran his brand-new setsquare over the ebonite, Mr. Gumblethorpe was horrified to find that it was a long way out. Measurements with a ruler showed him that he had a great deal to worry off it somehow. Setting manfully to work, he selected the straightest-looking edge and used that as the starting point. With the help of his square, he ruled the line AB in the diagram, which I give you herewith. Next, making use of AB and of the square, he ruled BC. With BC as reference line, he ruled CD. Careful tests showed that the figure ABCD had by no means right-angled corners. Nothing daunted, Mr. Gumblethorpe went on ruling DE, EF and FG. And still things did not look as they ought to, so he continued until eventually he came to X. As it was a panel and not a point that he required, Mr. Gumblethorpe took the ebonite next morning to a clever friend, who said that he

would do the job in two twos, whatever that may be. When Mr. Gumblethorpe called for it that evening it was quite ready.
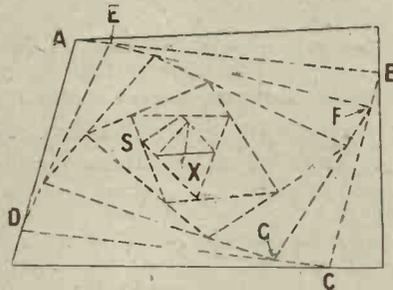
#### Another Friend

When he measured it out he found that it was  $\frac{1}{2}$  in. longer at the top edge than at the bottom. He therefore took it round to a second friend, who was even cleverer than the first. He said that he would do it in a jiffy. When he finished it the two long edges were of equal length, but the short ones were not. Mr. Gumblethorpe smiled a little sadly and took it round to a third friend, who said that he would do it in two ticks. Mr. Gumblethorpe said that he hoped that that was something different from two twos and a jiffy, since he had had some of these. When the third friend had finished all four sides were of different lengths. When it came back from a fifth friend it had five sides instead of four, and the sixth brought it back to four once more, but, as he was a disciple of Einstein's, all his straight lines had bends in them. The tenth really expert friend finished the job and got the panel perfectly square, but, as by this time it measured only 3 in. by  $2\frac{1}{2}$  in., it was hardly big enough for the job.

"After all," said Mr. Gumblethorpe, to himself, "squaring up a panel is no part of home set construction. I will get a big firm



How the panel was "squared."

to send me along one that is guaranteed correct." And he did. When it turned up, he at once tackled the job of marking it out for drilling purposes. But he found that his setsquare was not long enough for the job, so he sent it back and had it marked out for him, since this, again, as he said, is not really an essential part of amateur construction. Centre punching is quite a different matter. Some people have difficulty in getting the point of the punch on to the intersection of the cross lines and holding it steady there whilst the hammer delivers its blow. It occurred to Mr. Gumble-

thorpe that the usual method of holding the punch by its barrel between the thumb and forefinger of the left hand was a poor one, and simply made for inaccurate marking out. Grasping the punch between the fingers and the palm of his hand he placed its point in the right position, and held it perfectly steady by pressing hard upon its top with his thumb. Then he raised the hammer, and smote shrewdly. Then he decided that centre punching was a waste of time, and that one had much better get it done by somebody else.

When the panel returned, centre punched, Mr. Gumblethorpe leapt to the task of drilling; but as there were about nineteen  $\frac{3}{8}$ -inch holes to drill, and his left thumb was still giving him trouble, he took it



He raised the hammer and smote shrewdly.

round to the garage to be drilled. Fixing the components upon the panel or baseboard is a job that anybody can do once the drilling has been done. "Very well," said Mr. Gumblethorpe, after he had rammed the screwdriver into his still seedy thumb, "let anybody do it." So the handyman at the garage got that job, too.

Our hero decided that he would reserve his strength for the job of wiring. When he had covered the set and his table and the carpet an inch thick in flux and little blobs of solder, and still had not made the first joint, it occurred to him that wiring was no job for a man. He therefore borrowed his neighbour's very handy son, promising him five bob for doing the work, but warning him not to attempt to do it in two-twos, a jiffy or two ticks. So speedy was the lad that Mr. Gumblethorpe's home-made set was finished the next day. It refused to work, and he despatched it at once to the Test Department to have it put right. When it returns in thorough working order, Mr. Gumblethorpe will display proudly to his friends the set which he constructed entirely by himself, and when those boys of his brag about things that they make he will just point to it, and say, "When you can make as good a set as your father, my lads, you will be entitled to talk a bit."

# 6,500 NAUTICAL MILES on Loud Speaker!

REGULAR AND CONSISTENT PERFORMANCE


The Times, Los Angeles, California  
on Loud Speaker in Scotland

## Duodyne

"... As mentioned in my previous letter to you, wonderful results are still regularly and consistently received on my Duodyne V at home. The latest result to hand, the writer being at sea, is, up to August 3rd, the loud speaker reception of KFI, Radio Central, and KHJ, THE TIMES, PACKARD MOTOR-CAR BUILDING, LOS ANGELES, CALIFORNIA. Time of reception, 05.15 G.m.t. to 05.50 approx. G.m.t. Loud speaker medium strength, signals then weakened, but excellent phone reception was possible from Los Angeles until 06.30 G.m.t., which is 7.30 a.m. standard time and full daylight. Other stations heard were WTAM, WJL (special test?), KGO and XAD, two latter stations unknown—possibly American. The above-mentioned results were obtained on the ordinary £18 18 0 Model of your manufacture.

Hope I am not boring you with this long account of results, but anyone wishing to receive long-distance broadcasting—specify the Duodyne V, and extreme satisfaction and many hours of enjoyment will result.


F.V., s/s—"

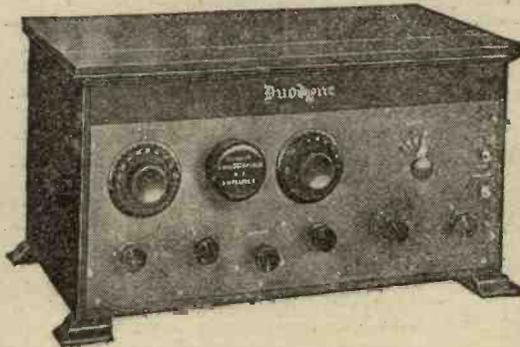

Prices range  
from  
**£7 10 0**

SEND FOR  
1925/1926  
CATALOGUE

## TWO ESSENTIALS OF DUODYNE RECEPTION

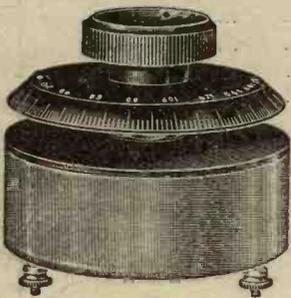

### Curtis Variable Mica Condenser.

Eliminates the many defects in the existing type of Condenser. This Condenser gives a square law reading. In operation there is no backlash, since its precision gives "dead beat" action.

Essential for the perfect reception in all circuits; indispensable for Super Heterodynes.

·001 Mfd.; ·0005 Mfd.;  
·00025 Mfd.

Price 12/6

### BUILD YOUR OWN DUODYNE

Hints to Home Constructors contains:

1. Curtis diagrams for 3 and 5 valves.
2. Simplified layout and wiring charts for 3 and 5 valves.
3. Instructions for operation.
4. Complete schedule of all material required.

Price 1/6


Send for 1925/26  
List of all the  
PETER CURTIS  
PRODUCTIONS

### PETER CURTIS LTD.

75, CAMDEN ROAD  
LONDON, N.W.1

Telephone: North 3112.

Telegrams: Paracurietx.

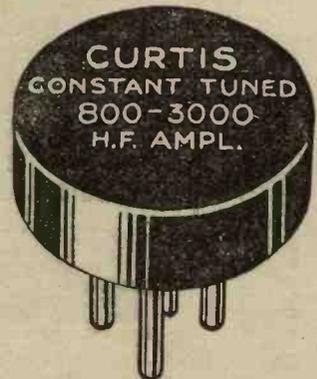

The universal High-Frequency coupling for distortionless reception at maximum radio efficiency.

PRICES:

- Type A, 250 to 800 metres, 15/-
- Type B, 800 to 3,000 metres, 17/6
- Type C, 2,000 to 7,000 metres, 18/6

Stocked for Plug-in or Board Mounting.

Type C is specially designed for the aperiodic stages in the Long Wave Amplifier of Super Heterodyne Receivers.



# Then—and Now

In olden days important news was "broadcast" through the medium of beacon fires on hilltops. This and other old-fashioned methods have been superseded by radio, but the significance of the beacon—a light visible, through its high position, to all—still remains. The high quality of **MH** COMPONENTS is making itself known to an ever-widening circle of radio enthusiasts.

## HERE ARE SIX REASONS

why you should use **MH** Filament Rheostats  
Once you have used them, you will find many others

(i.) They are wire wound, therefore their value does not alter from day to day or hour to hour. A certain setting on the dial always gives the same control.


(ii.) The wire is wound on a former in such a manner that it will not loosen with use.

(iii.) The winding will safely carry the required current without overheating.


(iv.) The moving contact is smooth and silent in operation. In the dual type it is transferred from the fine to the heavy winding by a metal bridge piece. This gives indication to the touch of the position of the slider, a safety device of considerable utility.

(v.) It is only necessary to drill a single hole to mount any one of these rheostats, and each is supplied with an engraved dial.

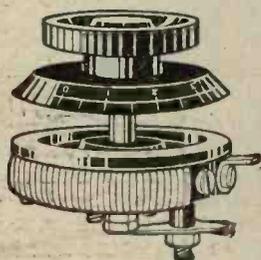
(vi.) The fact that they are **MH** Components is sufficient guarantee that they will give you long and dependable service.



**MH** Bright Rheostat

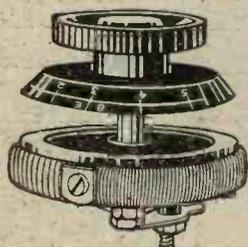

**MH** Dual Rheostat

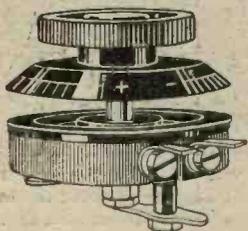

**MH** Potentiometer

<b>Bright Emitter Filament Rheostat</b> ... ..	5/6 each
<b>Dull Emitter Filament Rheostat</b> ... ..	6/6 each
<b>Dual Type</b> (for either Bright or Dull Emitters) ... ..	7/6 each
<b>Triple Rheostat</b> ... ..	22/6 each

### Control with precision by using a **MH** Potentiometer

If it is desired accurately to adjust the grid potential of a valve, a potentiometer is indispensable. Its moving contact must, however, be constant and quiet in operation or all advantages accruing from its use are lost. Also its resistance must be high or a heavy drain is put on the L.T. filament supply.

The **MH** Potentiometer which has a resistance of 300 ohms is an instrument every wireless enthusiast should possess. Every detail in design and manufacture has been carefully considered, and it can be relied upon to give satisfactory service.

Potentiometer for panel mounting (as illustrated) Price 7/6 each

VISIT THE **MH** STAND No. 6 AT THE  
N.A.R.M.A.T. EXHIBITION, ROYAL  
ALBERT HALL, Sept. 12th to 23rd, 1925

# L.M<sup>c</sup>MICHAEL LTD

Manufacturers of Wireless and  
Scientific Apparatus

Head Office:  
HASTINGS HOUSE, NORFOLK ST.  
STRAND - LONDON - W.C.2

Showrooms:  
179, STRAND, LONDON, W.C.2  
Works: SLOUGH, BUCKS.

# What are these Kilocycles ?

By J. H. REYNER, B.Sc., A.C.G.I., D.I.C.  
Staff Editor

**T**HERE has recently been considerable discussion on the use of kilocycles instead of metres in wireless nomenclature, and the question therefore arises as to what kilocycles are, and why they should be used.

## Should Pillion Riding on Kilocycles be Permitted?

The office boy, who is a keen motorist (on paper) was very perturbed about this new development, and enquired anxiously as to the seating capacity of these new machines. He was obviously greatly relieved when I explained that a kilocycle was not a motor vehicle, but a unit of frequency.

As a matter of fact, a kilocycle is 1,000 cycles or alternations.

## Frequency

An alternating current is one in which the current periodically changes its direction, flowing first one way and then the other. The number of complete reversals which take place in any one second is called the frequency, and is referred to in terms of the number of "cycles" or alternations per second.

## Wireless Currents

The currents in a wireless circuit (such as is used for broadcasting) reverse their direction many hundreds of thousands of times in one second, so that in this case the frequency is a very large number.

For example, the frequency of Newcastle's carrier wave (403 metres) is 743.950 cycles per second.

In order to deal with such frequencies the kilocycle is used (1 k.c. = 1,000 cycles), and 5NO's frequency is then 744 kilocycles per second (to the nearest kilocycle).

The frequency should, strictly speaking, be specified in kilocycles per second, but for convenience it is often referred to simply as so many kilocycles.

## Wavelength

When these high-frequency currents flow in a wireless aerial a series of disturbances are set up in the aether. These disturbances,

or pulses, follow one another in rapid succession, there being one pulse for every complete alternation or cycle.

Now the pulses which are set up by this means travel outwards through space with the velocity of light (299,800,000 metres per second approximately), and it is this succession of pulses, travelling at this tremendous speed, which constitutes an electro-magnetic wave and ultimately affects the receiver.


It will be clear that when the second pulse is produced the first will already have travelled some

distance. This distance is termed the *wavelength* of the electro-magnetic wave.

## Wavelength Classification

In the early days, when wireless phenomena were first investigated, the wavelengths of the disturbances produced were very short (one or two metres only). Moreover, as the phenomena obtained were similar to those of light, which is nearly always referred to in terms of wavelength, wireless waves were also classified in terms of their wavelength.

The need for this has now ceased,

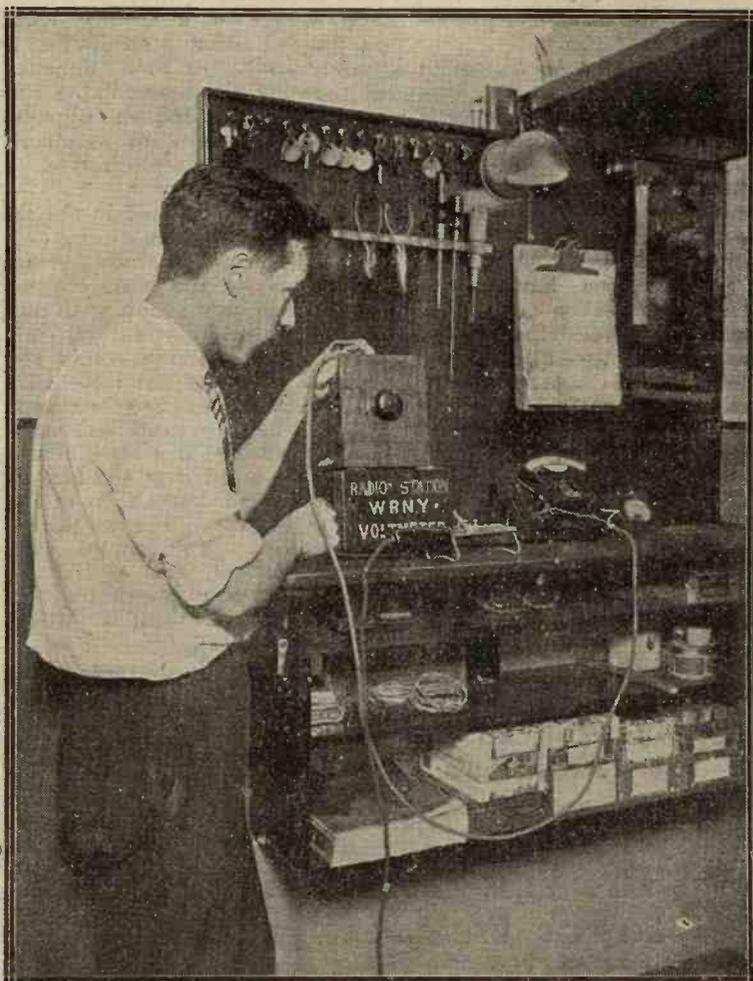

At WRNY, the Radio News Broadcasting Station in New York, everything is ready at hand for instant use. We see here the tool rack in the repair department,

and, in fact, the use of wavelengths means very little.

**Use of Frequency Preferable**

There are many reasons why the use of frequency is to be preferred to the continued classification of stations by wavelength.

The tuning circuits employed must be designed to tune to the same frequency as that of the pulses in the wave being received. It is true that charts and formulæ have been provided enabling the results to be expressed in terms of wavelength direct, but these are only derived from the frequency calculations. Any calculation other than that of simple tuning properties has to be carried out in terms of frequencies.

**Interference**

Another important point is the interference between two stations. There is a limit to the frequency difference between any two stations below which the stations will interfere by heterodyning each other with a receiver of the maximum permissible selectivity.

This means that each station requires a definite band of frequency (which in the case of a telephony station is about 10,000 cycles per second).

If the stations are classified in terms of wavelengths it is not easy to see at a glance whether the frequency separation is adequate; e.g., two stations having frequencies of 750 and 800 k.c. will not interfere. The wavelengths radiated by these stations would be 400 and 375 metres approximately, giving a 25 metre difference.

Two stations 1,600 and 1,625 metres apart, however, would have frequencies of 187.5 and 184.6 kilocycles. These are only 2.9 k.c. apart—i.e., 2,900 cycles—so that the stations would interfere. Hence the wavelength separation required between two stations is not constant.

**A Cycle a Day Keeps the Doctor Away**

There are many other arguments for the use of frequency rather than wavelength, but space forbids further discussion of the subject.

Suffice it to remark that, as Herodotus said (or would have done if he had lived to-day), "A cycle a day keeps the doctor away."

For the future, therefore, references will, where convenient, be given in terms of kilocycles as well as metres.

**A Few Hints and Tips**

By W. H. BERRY

A COMMON method of rejuvenating the plates of not too badly sulphated cells is to send them for an extra long charge at a slightly lower charging rate than normal. This is greatly facilitated in its function of reducing the accumulated sulphate if some sodium sulphate (commonly known as Glauber's Salt) is added to the electrolyte.

Where a crystal used in the set is of the type which requires a very light pressure of the whisker on its surface for the most efficient results, it is very annoying to find that the slightest vibration, such as a person walking across the room or a jar on the table with one's elbow, upsets the adjustment. This can be very easily and satisfactorily avoided if a little muslin cap be stretched over the face of the crystal and drawn tight at the back of the cup. The whisker is then moved into contact with the surface of the crystal as usual, but now penetrates the muslin, the fine mesh of which

prevents the whisker from being jerked.

Frequently after wiring and soldering a panel thin layers of flux will remain spread over the adjacent surfaces. These must be cleaned if no leakage is to result. It is very useful in such cases to keep a small bottle of benzene or methylated spirit, together with a small paintbrush, such as is sold for water-colour work on paper, costing about 2d. This enables inaccessible positions such as exist between valve pins and coil sockets to be thoroughly cleaned.

If a perfectly safe flux which does not corrode is required, and where joints are made with the intention of lasting good and clean for some time, it is a good way to use the solder known as hard solder used in conjunction with a flux of resin dissolved in methylated spirit. A useful paste flux for any purpose of soldering is made thus by dissolving resin in methylated spirit.

We frequently find difficulty in deciding the polarity of two leads, and unless we are possessed of pole-finding paper or some other commercial pole-finding apparatus we usually resort to trial and error. This is unsatisfactory and may be expensive. A certain and cheap pole-finder is to bare the surface of a potato by cutting off a piece of skin. If now the two wires be touched to the surface of the potato a green stain will be clearly seen where only one of the wires has come into contact. This is the positive pole.

Crystals may usually be re-sensitised by giving them an alum bath. About a dessertspoonful of alum should be put into about a wineglassful of water. This should be left overnight, and in the morning there should still be a little alum left. If this is not so, a little more alum should be added. When the water has dissolved as much alum as it can and still a little remains we then know we have what is termed a "saturated solution." The crystal should be placed in this solution and left for from 10 to 20 minutes. Now lift out with a pair of tweezers (on no account using your fingers) and put to dry in some cool, dry position. When completely dry the crystal will have turned dull where previously it was bright. This is no deterrent, as it is only a thin layer of alum which has now covered the crystal surface. The crystal can now be used and will be found to be re-sensitised.

**" WIRELESS "**

THE ONE - WORD WEEKLY

The best that money can buy or brains can produce

2<sup>d</sup>.

at all bookstalls

2<sup>d</sup>.

*A New  
B.T.H. Production  
that will make  
all the difference  
to your set*



If your loud speaker does not give uniformly good reproduction of all notes, tones, instruments and voices, the trouble can probably be eliminated by the use of the new B.T.H. Transformer. Its chief characteristics are:

**HIGH AND CONSTANT AMPLIFICATION** over a wide range of frequencies. (See curve below.)

**PERFECT REPRODUCTION**, free from distortion, with maximum volume and absolute purity of tone.

**NEGLIGIBLE LOSSES**—the result of careful design and workmanship.

**UNIFORM RESULTS** ensured by the use of a single spool of moulded composition to contain all windings. Separate spacers not employed.

**TOTALLY ENCLOSED** and thus protected from moisture, dirt and mechanical damage.



**LARGE CORE**, perfectly jointed, eliminates stray fields and renders screening unnecessary.

**B.T.H.  
Low Frequency Transformer**


Made in two ratios  
4:1 and 2:1

PRICE 25<sup>1</sup>/<sub>2</sub> ea.

*Insist on B.T.H.—the Best of all.*

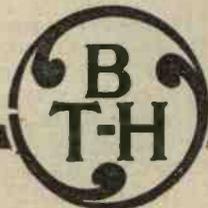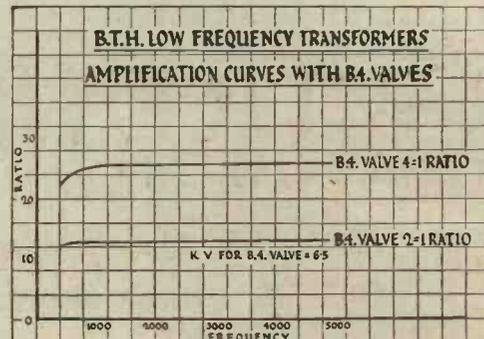

A BRITISH SUBMARINE

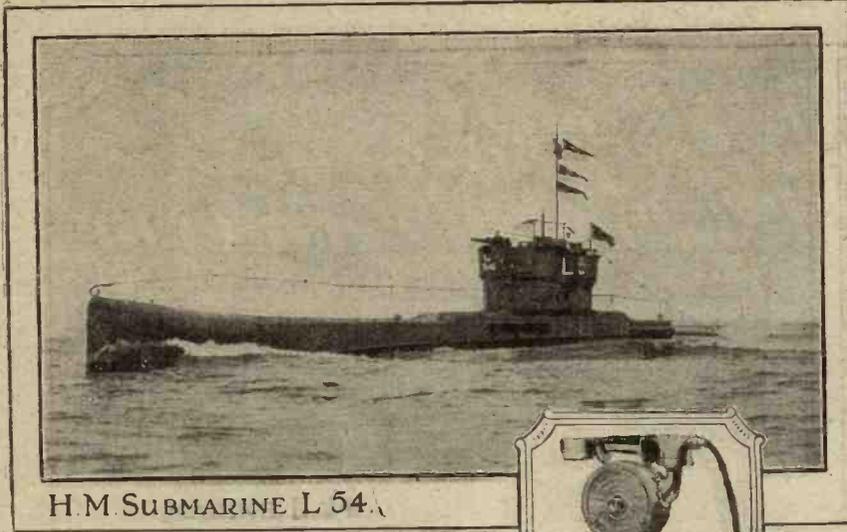

H.M. SUBMARINE L 54.

# On Land and Sea

Loud Speaking Telephone Apparatus manufactured by **THE HOUSE OF GRAHAM** is used throughout the British Navy and adopted by many Foreign Governments, as also by leading Shipping Companies in all quarters of the Globe.

With over thirty years' pre-eminence in every field of Loud Speaker application, the utility, technical efficiency and reliability of Graham instruments are conclusively demonstrated.


Just as the most exacting requirements of Naval and Maritime experts have been adequately met by production to meticulously accurate standards, so the present-day needs of Radio reception have been fully satisfied in the evolution of the **AMPLION** Loud Speaker.

## A Product of The House of Graham


Recognised as the World's Standard Wireless Loud Speaker.

Obtainable from **AMPLION STOCKISTS** and Wireless Dealers everywhere.

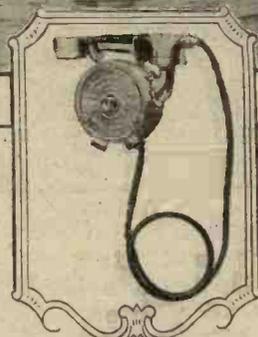**ALFRED GRAHAM & CO. (E. A. GRAHAM)**  
St. Andrew's Works, Crofton Park, London, S.E.4  
Demonstrations given during business hours at—  
West End Showrooms 25 & 26, Savile Row, W.1  
Suburban Showrooms 79-82, High Street, Clapham, S.W.4  
Scottish Depot 101, St. Vincent Street, Glasgow




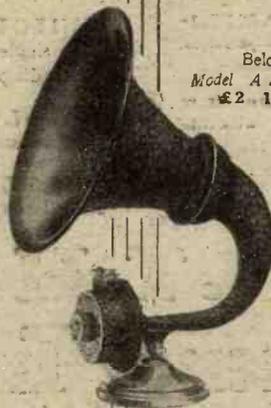Above.  
A typical Graham Patent Loud Speaking Naval Telephone as fitted in British Submarines.



Below.  
Model A R 111 at  
£2 10 0

# AMPLION

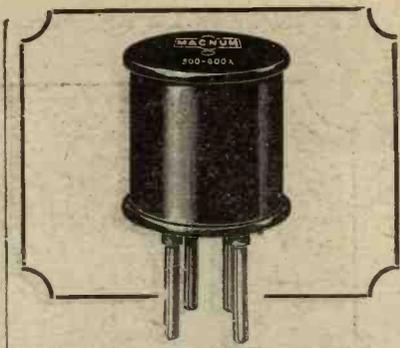


## MAGNUM H.F. TRANSFORMERS

Highest efficiency—but no increase in price

WAVELENGTH RANGE With '0003 CONDENSER			
Metres		Metres	
No. 0 ..	150—300	No. 1 ..	300—600
*No. 0A ..	250—525	No. 2 ..	550—1200
*Special Neutrodyne Unit for Broadest Range		No. 3 ..	1100—3000
		No. 4 ..	2500—7000

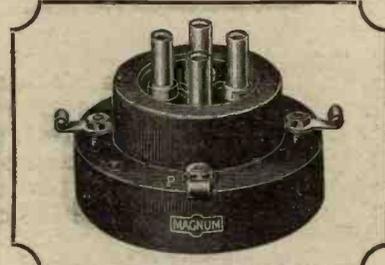PRICE 7/- EACH  
Guaranteed Matched 14/- per pair



## MAGNUM VIBRO VALVE HOLDER

Non-Microphonic, Anti Capacity, No Loss. As used in several Radio Press Sets .. 5/- each

- 2-VALVE LOW LOSS NEUTRODYNE As described in this Issue by Mr. Percy W. Harris
- 1 Collinson Low loss Coil Former .. 5/6
  - 1 Magnum Neutrodyne Unit .. 7/-
  - 1 Magnum Coil Holder with feet .. 1/9
  - 9 Terminals Lacquered and complete .. 1/6
  - 1 Square Law Variable Condenser '0003 8/9
  - 1 '0005 10/6
  - 1 Magnum Neutrodyne Condenser .. 4/6
  - 1 McMichael Fixed Cond. and Clips '001 1/9
  - 1 Dorwood '0003 2/6
  - 1 Dubilier Grid Leak 2 Meg. .... 2/6
  - 12 Valve Sockets Lacquered and complete 1/6
  - 1 McMichael Dual Rheostat .. 7/6
  - 4 yards No. 16 Sq. Sec. T.C. Wire .. 6
  - 1 set Radio Press Transfers. .... 6
- £2/16/3

Polished Mahogany Cabinet 12x10x7 .. 13/-  
Ebonite Panel Drilled 12x10x7 .. 10/9  
NOTE..Where a complete set of components are purchased together, a Marconi Royalty of 12/6 per valve holder is payable.

**SUPER-HETERODYNES.** - Build your own set with Magnaformers. Price £5 per outfit, including 1 Interchangeable Oscillator Coupler and 5 Interfrequency Transformers Of our own design and manufacture. 34 stations on the loud-speaker—mostly during daylight. These wonderful results were obtained on the Magnadyne Super-Het. Send stamp for lists and set of leaflets dealing with Radio Press Circuits, also the Magnadyne Super-Het.

**KENDALL CROSS FORMER.** Low-loss Price 3/- each—With plug and adaptor 3/9 each

**TAPPED ANODE COIL** for the **SIMPLICITY-3** (Radio Press Envelope No. 3). Also the **T.A.T. CIRCUIT** designed by Mr. J. Scott-Taggart. Price 3/- each

**WAVE TRAP FORMER** for A B C WAVE-TRAP (Radio Press Envelope No. 6) Price 5/6 each

**BURNE-JONES & CO., Ltd.**  
Magnum House  
296, Borough High St., London, S.E.1  
Telephone HOP 6257  
Telegrams: "Burjomag, Sedist, London"  
Cables: "Burjomag, London"  
TRADE ENQUIRIES INVITED



# Correspondence

**"A NEW CRYSTAL-VALVE CIRCUIT."**

SIR,—I am writing to report that I have constructed a receiver with the "New Crystal-Valve Circuit" described by Mr. John Scott-Taggart in the March issue of THE WIRELESS CONSTRUCTOR.

I have built one or two single valve receivers from this journal, but I have never before used a circuit which gives such excellent results as this one.

It was stated that the circuit would probably work a loud speaker up to five miles, but, as you will observe, I live at New Southgate (which is about seven or eight miles from 2LO), and I obtain perfect loud speaker reception. I am using a Cossor bright emitter valve and a Sterling "Dinkie" loud speaker. The coils are 25 aerial and 120 reaction.

Last Thursday (August 13th) I was listening to the first edition of "Radio Radiance," and the signals were so pure and loud that it was just as though I was in the studio. Such results as I have obtained with only one valve are both surprising and satisfying.

Hoping this letter may be of assistance to other readers and wishing every success to THE WIRELESS CONSTRUCTOR,

Yours faithfully,  
H. E. MARCHANT.

New Southgate.

**THE "FAMILY TWO."**

SIR,—Knowing that letters of appreciation are always welcome, I feel I ought to let you know how satisfied I am with the "Family Two" Loud-speaker Set, which I made up from Mr. Percy Harris's instructions in the March issue. It is certainly the ideal set for the local station. Using two D.E.R.'s off a 2-volt accumulator, with a Dulcivox loud speaker, the volume is quite sufficient for a room of about 16 ft. by 12 ft., and the purity of tone is remarkable. Except for slight crystal adjustment, the set is never touched, and is always reliable. I have no hesitation in recommending anyone who wishes to build an economical set for

broadcasting only to select the "Family Two," providing they are within the correct range.

Yours faithfully,  
WM. DUNCAN.

Sydenham, S.E.26.

**THE "SHORT-WIRE" VALVE PANEL.**


SIR,—A few months ago I made up the "Short-Wire" valve panel described by Mr. A. S. Clark in the January issue of THE WIRELESS CONSTRUCTOR and the corresponding tuner described in the April issue, and the good results have prompted me to write this letter. To-day a friend lent me a Sterling "Baby" loud speaker, and the set worked it loud enough to be clearly

heard in an average-sized room. I can also get Liverpool, Leeds-Bradford, Stoke and Daventry comfortably in the 'phones, and I have heard Birmingham, Newcastle, Belfast, London, Bournemouth and Brussels at various times.

I am situated about 2½ miles from the Manchester station, and the aerial consists of four wires stretched across a bedroom, so I think the results speak wonders for the set. I am only fifteen years old, and have followed the lay-out exactly, but have used different parts. Many thanks for designing such a wonderful set.

Yours faithfully,  
H. WALTON.

Manchester.

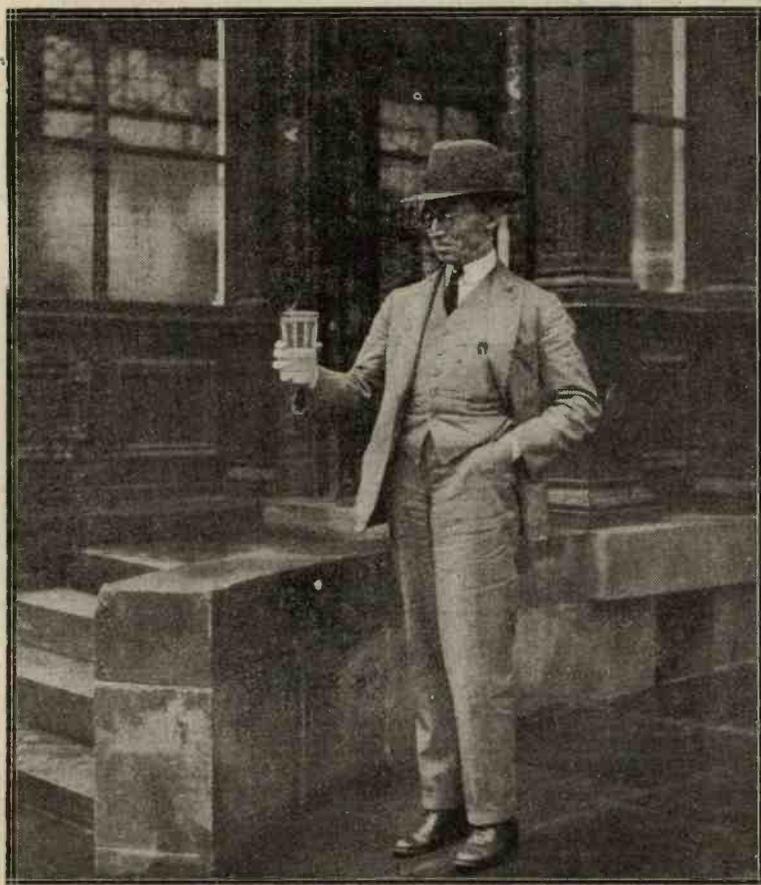

John Henry, the famous comedian, is here seen partaking of the sulphur waters at Harrogate.

K. RAYMOND

ALL GOODS POST FREE U.K. except where stated. Foreign orders over £10 post free. otherwise please send ample for post, etc. OPEN ALL DAY SATURDAY.

SEE FULL ADDRESS ON OPPOSITE PAGE

Table listing various electronic components such as Accumulators, Edison Bell, GOSWELL, BURDEPT, and others with their respective prices.

Table listing various electronic components such as Edison Bell, GOSWELL, BURDEPT, and others with their respective prices.

Table listing various electronic components such as IGRANIC, MAGNUM, POLAR, and others with their respective prices.

Table listing various electronic components such as SUCCESS, SHIPTON, SUNDRIES, and others with their respective prices.

Table listing various electronic components such as L.F. TRANSFORMERS, SUCCESS, SHIPTON, and others with their respective prices.

Table listing various electronic components such as L.F. TRANSFORMERS, SUCCESS, SHIPTON, and others with their respective prices.

Delivery given at the earliest possible moment but no responsibility accepted for manufacturer's delays, lock-outs, strikes, or any cause over which I have no control. All orders accepted on condition, place of payment, 7, Grape Street, W.C.2.

Delivery given at the earliest possible moment but no responsibility accepted for manufacturer's delays, lock-outs, strikes, or any cause over which I have no control. All orders accepted on condition, place of payment, 7, Grape Street, W.C.2.

Delivery given at the earliest possible moment but no responsibility accepted for manufacturer's delays, lock-outs, strikes, or any cause over which I have no control. All orders accepted on condition, place of payment, 7, Grape Street, W.C.2.

Delivery given at the earliest possible moment but no responsibility accepted for manufacturer's delays, lock-outs, strikes, or any cause over which I have no control. All orders accepted on condition, place of payment, 7, Grape Street, W.C.2.

Delivery given at the earliest possible moment but no responsibility accepted for manufacturer's delays, lock-outs, strikes, or any cause over which I have no control. All orders accepted on condition, place of payment, 7, Grape Street, W.C.2.

Delivery given at the earliest possible moment but no responsibility accepted for manufacturer's delays, lock-outs, strikes, or any cause over which I have no control. All orders accepted on condition, place of payment, 7, Grape Street, W.C.2.

K. RAYMOND


7, Grape St., Shaftesbury Ave., W.C.2

Fall address other page

If you spend 25/- (Retail) Your PANEL DRILLED FREE.

Send POSTCARD for particulars of our 5/- phones.
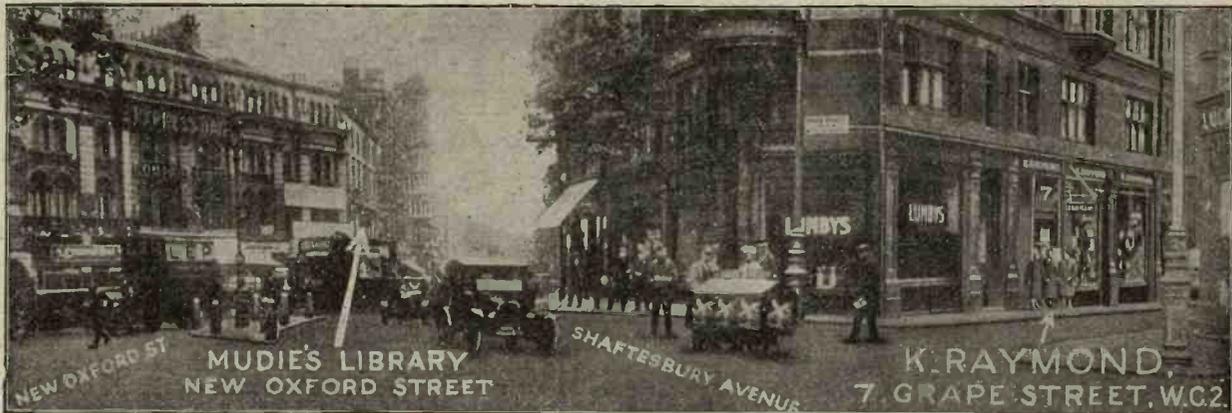
# 7. GRAPE STREET. SHAFTESBURY AVENUE. W.C.2



**K. RAYMOND**  
PLEASE NOTE →  
THIS IS THE HOUSE FOR  
HIGHEST QUALITY  
COMPONENTS.

This is the **New Oxford Street End** of Shaftesbury Avenue, Grape St. is between Mudie's Library and New Princes Theatre. It is **One** minute's walk from **Tottenham Court Rd. Tube**. **3** minutes' walk from **Holborn Tube**. **2** minutes' walk from **Palace Theatre, Cambridge Circus**. **1** minute **Museum Tube**.

**HOURS OF BUSINESS**  
Daily 9 a.m. to 8 p.m.  
Sundays, 11 to 1.  
Open all day Saturday  
Two shops, one al-  
ways open.  
Telephone (private  
line) Gerrard 2821.

OPEN ALL DAY SATURDAY


**SECOND-HAND GOODS.**  
Patronise the live firm!  
I will accept in part pay-  
ment for new goods (or  
purchase if so desired) any  
articles you have no use  
for.  
This is a stunning offer, so  
don't forget to take ad-  
vantage of it.  
Make out your list of what  
you have to sell, and I will  
offer you best prices. This  
applies to post or callers.

**Very Important — Space  
costs MONEY.** To avail  
yourself of our very  
special offers which mean  
**POUNDS** to you, just  
send us a postcard with  
your name and address  
and our lists follow im-  
mediately.

**VERY IMPORTANT.**  
This list is a fairly com-  
prehensive one, but if you  
will make out your re-  
quirements, giving goods  
actually wanted, makers'  
names, etc.,  
I will Quote You Lowest  
possible inclusive Prices.


VALVES.	POST PRICES
To encourage you to use British Valves I am willing to purchase one burnt-out valve for each valve you purchase.	3/6 EBONITE stock sizes.
Prices given range from 1/3 to 4/- according to valve you buy.	8 x 6 .. 2/- 9 x 6 .. 2/3 10 x 9 .. 3/6 12 x 9 .. 5/- 12 x 12 .. 6/6 14 x 10 .. 6/6
	Cut to size 1/1. per sq. inch.

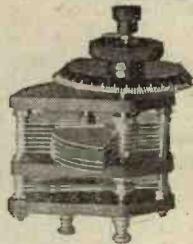**RAYMOND'S VARIABLE CONDENSERS**  
SQUARE LAW LOW LOSS.  
ONE HOLE FIXING.  
EBONITE ENDS.



	With Vernier	Without Vernier
.001	8/6	7/6
.0005	7/6	5/9
.0003	7/-	5/3

Including knob and dial.  
Post 3d. set.

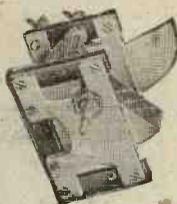

**ORMOND "AMERICAN"**  
Square Law Low Loss.  
Skeleton Ends, Knob  
and Dial.  
.001, 9/-; .0005, 8/-  
.0003, 7/6; .00025, 6/6  
With Vernier, 1/6 each  
extra.  
Post 3d. set.

JACKSON BROS. "J.B."	Square Law with vernier	ORMOND "No. 3" Ebonite Ends.
.001 .. 9/6	.001 .. 12/6	Sq. law with vernier .001 .. 10/6
.0005 .. 8/-	.0005 .. 11/6	.0005 .. 9/6
.0003 .. 7/6	.0003 .. 11/3	.0003 .. 9/-
.00025 .. 6/6	.00025 .. 11/3	Also without vernier, 1/6 each less.
J.B. "No. 1" .. 8/6	.0005 .. 7/-	All with knob & dial
Standard (0003) .. 5/9	.0003 .. 5/-	
ALL with knob and dial.	Post free.	

**WARNING**

A certain firm in the vicinity of my address is copying my advertisement in detail, in my opinion it is an attempt to mislead the public. Will customers' carefully note the name

**K. RAYMOND**

on premises to ensure their getting the actual goods advertised both for quality and price. **NO USE COMPLAINING WHEN IT'S TOO LATE.**

**K. RAYMOND**  
**7, GRAPE STREET, Shaftesbury Avenue.**  
(Full Address above.) W.C.2

**These two Columns CALLERS ONLY**  
ALL POST ORDERS FROM OTHER COLUMNS.

Terminals, Nut and Washer W.O. Phone, Pillar	1d	Panel Swoches.	
Extra Large ditto	3 for 4d	Nickel DPDT, 1/-	SPDT, 10d.
Nickel, 2d. each	doz. 1.6	Telefunken, Adjustable phones, 4,000 ohms, guaranteed genuine.	14/11 pr.
Valve Sockets	2 for 1d	ERICSSON EV (Continental), 4,000 ohms, per pair, 10/6.	
Valve Pins and Nuts	2 a 1d	N. & K. Genuine, 4,000 ohms, 12/11	
2, 4, 6, BA Nuts	6 a 1d	Davenport, 1,800 Ohms 1/4, 1.3, 1.6	
2 or 4 BA Washers	12 a 1d	Ledion New Model	2/-
2 BA Rod, best	foot 2d	Ledion New Model	3/6
4 BA Rod, best	foot 2d	2-way Coil Stands	2/2, 2.3, 1/11
Spade Tags	6 a 1d	3 way Coil Stands	4/6, 3/3
Soldering "Nickel"	3 a 1d	2 way Cam Vernier	4/6, 3/3
Screwed Spades	3 for 1d	2 way Gear	4/6
Screwed Pins	9 for 1d	3 way Geared	5/11
Battery Clips	5 for 2d	Bhaw's Genuine Herizite	8d.
Copper Foil, 6 in.	foot 3d	Wonder Aerial, 49 strands.	
Large Bleeding	yard 2d	100 ft. best, quality 3-2nd qual. 1.6	
Screw Wander Plugs	pair 4d	DCC Wire, 1lb. reels. Best English.	
Extra Quality Plugs	pair 4d	18 .. 9d. 20 .. 9d.	
Red and Black ditto, 12 yards	1d	22 .. 10d. 24 .. 11d.	
'Phone Connectors	2 a 1d	26 .. 1 .. 28 .. 1.1.	
Spade Terminals (red or black)	1d		
Plug and Socket red or black	1d		
Flush Pane Sockets, with 2 nuts	1d		
Twin Flex, 12 yards	1/5		
Ribbon Aerial, 100 ft.	1/3		
'Phone Cords, 6 ft. rubber ins.	1/6		
Loud Speaker Cords, 20 ft.	2/11		
Ditto, 12 ft.	1/11		
Valve Templates	2d		
Ribbon Aerial, 100 ft.	1/3		
7/22 Hard Drawn, 100 ft.	1/10		
Adhesive Tape	5d and 3d		
Empire Tape, doz. yds.	6d		
Breast Drills, with double pinion cut gears.	4/6		
Valve Windows	6/1		
Ormond Machine Screws stocked	8d		
Enclosed Detector	1/-		
Ditto Large Brass	1/3		
Ditto, Terminal Fitting	1/3		
Ditto, Half Opal	1/6		
Ditto, Half Opal Nickel	1/6		
Ditto, Micrometer	1/6		
Micrometer, trigger movement	2/-		
Climax Earth Tubes	5/-		
'Opera' Earth Tubes	2/1		
Twin Silk Flex Miniature, 6 yds.	6d		
'Phone Connector Boards	1/11		
Brownie ditto	3/6		
Ebonite Coil Plugs, plain	4d		
Ditto, wedge	6d		
Fitted Fibre	7d		
Edison Bell	11d		
Basket Holders	8d. 10d.		
Spice and Plug	9d		
Bus Bar Square.			
1/16 in. 12 ft., 6d.	18 gauge 5d.		
Ins. Hooks	2 for 1d.		
Ditto, Staples	6 a 1d.		
Variometer, 220-650 metres	1/8		
Lea-1-in. 10 yds.	1/-		
Extra Heavy.	yd. 2d. 3d.		
Coil Formers, with handle	1/6		
Crystal Set, Sloping Cabinet fitted for 5XX, Leatherette Case, guaranteed a perfect instrument	9/6		
Twin Bell Wire	yd. 2d.		
DCC, JEC Bell Wire	10 yds. 5d.		
DPDT China Base, 1/3.	SPDT 10d.		

ABOVE TWO COLUMNS FOR CALLERS

# No. 1 of Important Radio Press Weekly

## OUT SEPTEMBER 15th

Some preliminary details regarding "WIRELESS," the one-word weekly

ALL readers of THE WIRELESS CONSTRUCTOR will, no doubt, be interested to hear that the Radio Press, Limited, are bringing out on Tuesday, September 15th, an entirely new periodical, which will be entitled *Wireless*, the price of which paper will be 2d. (two pence).

The effect of the production of a 2d. weekly paper by the Radio Press will be to create the greatest interest throughout the world of wireless. Hitherto, the Radio Press have not catered for the wide public interested in wireless by means of a weekly paper. Although they possess *Wireless Weekly*, a 6d. periodical having a high-class circulation and appealing to the more technical section of the public, they have never attempted, as yet, to compete with the cheaper weekly wireless papers, or to cater for the large public which buys no technical wireless paper at all.

Practically all WIRELESS CONSTRUCTOR readers buy, in addition, a weekly paper of a popular character. Many of these have said to us: "Why cannot Radio Press, with all their resources, experience and staff, produce a weekly paper on broad popular lines at a cheap price?"

They are now going to, and on Tuesday, September 15th, you will find on every bookstall and in every newsagent's shop a copy of *Wireless*—meant for you to buy.

For 2d. weekly you will receive remarkable value—value which you could never get unless a great wireless publishing organisation were behind the paper. The new Radio Press laboratories are now in operation; two of the buildings are up and several new brilliant engineers have been engaged, as

announced elsewhere in this issue.

The organisation of the Radio Press has been strengthened enormously by the great Elstree enterprise and by the acquisition of new engineers who will write for the Radio Press journals.

The contributors to *Wireless* will include the most able writers in the country, including, apart from the laboratory staff, all the well-known Radio Press authors, and also outside contributors of outstanding ability.

Mr. Percy W. Harris paid a special visit to the United States

with information which will undoubtedly change, in large measure, the whole trend of apparatus design. He knew exactly what to look for and made very careful comparisons and investigations.

He frankly admits that American sets are, generally speaking, far in advance of British designs, and he is going to tell his story, week by week, commencing with No. 1 of *Wireless*.

These articles, if they appeared in THE WIRELESS CONSTRUCTOR would take months to complete, but by publishing them weekly the whole extremely valuable information he

has gained will be completely available to the wireless public in time to derive the fullest benefit during the winter.

Mr. John Scott-Taggart, F.Inst.P., A.M.I.E.E., will be contributing, at intervals, to *Wireless*, and in No. 1 will appear an article by him of intense interest to all who have built, or read of, the ST.100 receiver. Since this was first designed, in the summer of 1923, great strides have been made as re-

gards general design and circuit improvement. The new ST.100 has been built in the Radio Press laboratories, under the direction of Mr. Scott-Taggart, and full details will be given in the first issue of *Wireless*.

A striking article of universal interest will appear under the name of Major James Robinson, D.Sc., Ph.D., F.Inst.P., Council P.S.L., and there will be innumerable other features of extreme interest.

Suffice it to say that the best that money can buy, or brains can produce, will find its place in No. 1 and in subsequent issues.

The price, 2d., is so small for the value which will be given that only the fullest support by readers and

### AN ANNOUNCEMENT REGARDING

The New Radio Press Paper entitled

# "WIRELESS"

THE ONE-WORD WEEKLY.

Edited by PERCY W. HARRIS, M.I.R.E.


Editor-in-Chief: JOHN SCOTT-TAGGART, M.C., F.Inst.P., A.M.I.E.E.

Research Editor: MAJOR JAMES ROBINSON, D.Sc., Ph.D., F.Inst.P.

## No. 1 Out Sept. 15th

in order to obtain the very latest information regarding American radio designs. We have heard so much about the superiority of American radio apparatus, its greater range and its greater selectivity, that we felt it essential to investigate the position at first hand, and Mr. Harris has returned with data and information of extraordinary value and importance. Many articles have appeared, dealing with American methods, written by semi-technical and non-technical authors. Mr. Harris, however, has enjoyed, for several years, a very high reputation in this country as a designer of wireless sets, and he has returned

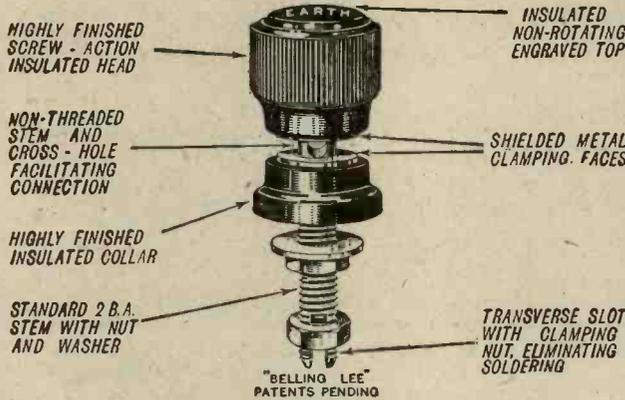
# "BELLING LEE" INDICATING TERMINALS INSULATED TYPE



ALL METAL PARTS HEAVILY NICKELLED.  
INSULATED PARTS OF GENUINE POLISHED BLACK BAKELITE.  
Price: 9d. each
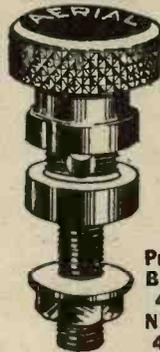
## INDICATING TERMINALS Metal Type

Stocks of all varieties are held as follows:  
Aerial, Earth, Phones +, Phones -,  
L.T. +, L.T. -, H.T. +, H.T. -,  
Input +, Input -, Output +, Out-  
put -, L.S. +, L.S. -, Grid +, Grid -,  
A.T.I., Reaction, Ap. Aerial, H.T.:  
Medium and Blanks.



Price:  
Brass 4d.  
Nickel 4½d.

PATENTED

Internal  
Metal  
Chuck to  
grip 14 to  
44 gauge  
wire or  
flex:




Price:  
Plug 4d.  
Socket 2d.  
Indicating  
Ring 1d.



## PLUG & SOCKET TERMINALS (M.K. PATENT)

1. Give seven points of contact.
2. Have no loose parts.
3. Soldering lug on socket; will also grip a sub-connector.
4. Indicating rings are dome-shaped.
5. All metal parts are nickelled.

## DIAL INDICATORS

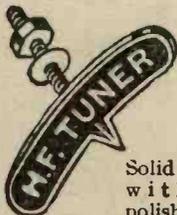

Solid cast metal, with raised, polished letters showing white on a black background. Single hole fixing, complete with nut. Stocked in Tuner, Filament, Reaction, Aerial, Anode, H.P. Tuner, Secondary, Reflector.

Price - 6d. each

Every high-class dealer stocks them, but in case of difficulty send to:

BELLING & LEE, Ltd., Queensway Works, Ponder's End, Middlesex.

## SUB-CONNECTORS

Eliminate Soldering

Perfect connection; lowest possible self-capacity; low resistance; connection changed in an instant. Tapped to screw on to 2, 4, 5 and 6 B.A. threads; also T connectors for joining wires.



Price 1d. each



He never gets  
let down now!

## THAT "BOUND-TO-COME" SORT OF FEELING!

You know it, and I know it, and one day it will come! No current—no wireless!

There's only one satisfactory solution—always have your accumulator ready charged, and when you think of chargers remember there is only one that will give complete satisfaction.

The **PHILIPS RECTIFIER** works off any A.C. supply, requires no supervision whatever, works silently, and automatically regulates the current supply.

There are no objectionable chemicals, no buzzing noises, and you have in fact a most reliable battery feeder with an extraordinarily low running cost.

**SIMPLE, CONVENIENT, EFFICIENT. IT CHARGES WHILE YOU SLEEP.**

Write for leaflet W.O., free on application.

Trade enquiries invited.



# PHILIPS RECTIFIER

Adot. Philips Lamps Ltd., 60, Wilson Street, London, E.C.2

R.L.

trade alike would justify it. If it were produced by any other organisation than the Radio Press, the surprise exhibited would not be so great, but the great welcome which the preliminary announcements of this paper have received indicate that there will be a huge demand on publication.

Mr. Percy W. Harris will be the Editor of *Wireless*, and Mr. John Scott-Taggart will be Editor-in-Chief. It will be whole-heartedly a Radio Press production, and the entire organisation of the company is going to make it the greatest and most successful enterprise they have yet undertaken.

*Wireless* will be in a class by itself; although eminently readable and interesting, and of lighter character than some of the other Radio Press periodicals, the same soundness as regards technical facts and policy will be there. The stamp of the Radio Press will appear on every page, and this is what will make the new paper different from any existing wireless weekly.

September 15th will be a red-letter day, not merely for the Radio Press, but for those masses of expectant readers who have had to buy some other weekly simply because the Radio Press have had nothing suitable to offer them.

We are out for an entirely new public, but we are confident that the readers of our monthly periodicals will, to their own advantage, become supporters of *Wireless*—the new Radio Press weekly.

ENGLISH ARTISTS AT WRNY.



The Volga Trio, who are well known to the 2LO audience, are here seen broadcasting from the Radio News Station in New York. Ivan, the Cellist, is only eleven years old.



FOR CLARITY—VOLUME—DISTANCE

Look into the workshops of radio amateurs, into the laboratories of radio engineers. Observe the radio battery equipment in the homes you visit. Everywhere you will find

Columbia

The No. 4780 60 VOLT HIGH CAPACITY BATTERY is by far the most satisfactory plate battery you can use. The extra large sized cells used in the construction of the battery not only supply sufficient power for the finest reception, but give an unusually long service life as well. The heavy spring clips ensure quick and secure connections.

PRICE 22/6 NET

Columbia

Radio "A" Dry Cells

ESPECIALLY DESIGNED FOR WIRELESS and suitable for use with all types of dull emitter valves, the Radio "A" is the most reliable and efficient filament heating unit manufactured,

PRICE 2/6 NET.




Send for our new FREE BOOKLET "K"

—33 pages of valuable information pertaining to care and operation of your batteries.

No. 4770 45 VOLT EXTRA HEAVY DUTY are specially recommended for "Fada" and other neotrodyne circuits

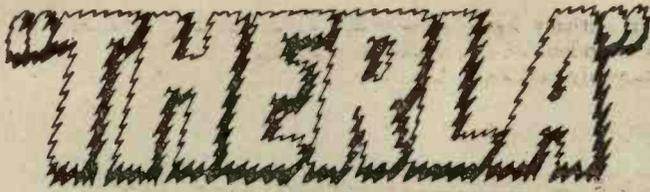ADVERTISEMENT OF J. R. MORRIS, 15, KINGSWAY, LONDON, W.C.2



REG. N° 457042

### Now introduce a better Grid Leak

THE Theria Grid Leak is a definite improvement on other products of its kind. There are good reasons to support this claim.

First: Theria Grid Leaks are made by a special protected process. Second: They are guaranteed to be accurate. Each individual one is tested by Faraday House, and

the material is the very best obtainable. Third: A moisture-proof mounting ensures that resistance is permanently maintained. The resistance element contains no India ink or pencil markings, thereby ensuring a constant and noiseless leak. Try out the Theria Grid Leak in your set—the improved results will surprise you.

Size 250,000 ohms	} Price 1/9
500,000 "	
1,000,000 "	
" 1 megohms	
" 2 "	
" 3 "	Grid Condenser and Leak 3.

The Theria Fixed Condenser is also tested for capacity by Faraday House and guaranteed Grid Condenser with Clips 1, 3.

Price '0001 to '0015.
mid. 1/3 each.
'002 mfd. to '006 mfd. 2/- each.



Sole Distributors:

Telephone: Regent 1140.

SEL-EZI WIRELESS SUPPLY CO., LTD 6, GREEK STREET, LONDON, W.1 and 20, OLD HAYMARKET LIVERPOOL



## GUARANTEED EBONITE PANELS BEST BY TEST

"Insulation resistance—virtual infinity;  
Surface resistivity—virtual infinity;  
Electric strength—to Admiralty specification."

### See N.P.L. Test Report


#### WARNING.

The contract price for raw rubber in December, 1924, was approximately 1/3 per lb.; the price on July 1st, 1925, rose to 3/3 per lb.; and on July 20th, 1925, the price rose still further to 4/6½ per lb. We have determined—

1. To maintain our Quality;
2. To continue to give our guarantee of "Entire freedom from all deleterious fillings and impurities";
3. And Guarantee every panel sold in our Sealed Carton under our Trade Mark to be "exactly similar in specification and quality to the Ebonite tested by the National Physical Laboratory on the 6th May, 1925."

We are, therefore, reluctantly compelled to alter our prices from month to month in proportion to the rise or fall in the price of raw rubber.

## 60 STANDARD SIZES SEE LISTS

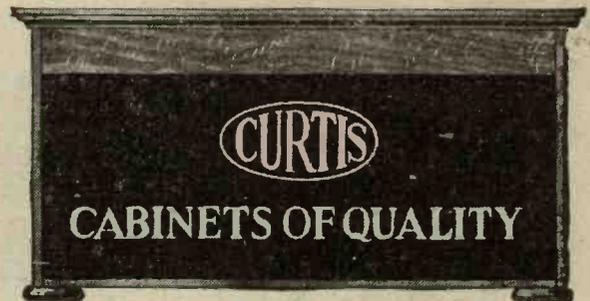

### CABINETS OF QUALITY


#### TO SUIT PANEL SIZES OF

Length	Height	Price s. d.
10 ins. x	7 to 9 ins. . . . .	27 6
12 " x	7 to 9 " . . . . .	32 6
16 " x	7 to 9 " . . . . .	37 6
18 " x	7 to 9 " . . . . .	42 6
20 " x	7 to 9 " . . . . .	47 6
24 " x	7 to 9 " . . . . .	52 6
30 " x	7 to 9 " . . . . .	60 6
36 " x	7 to 9 " . . . . .	65 6

All above cabinets 9 ins. deep inside. Prices include sliding base-board fitted to panel. Panel extra.

**PETER CURTIS, LTD.**  
75, CAMDEN ROAD, N.W.1  
Telegrams—Paracurtex. Telephone—North 3112

## A New Battery OF OUTSTANDING MERITS

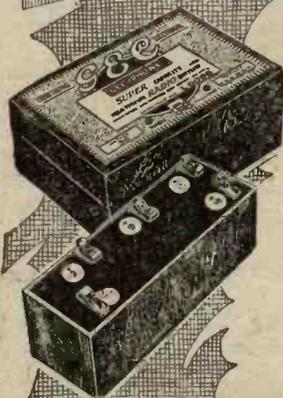

The new GECOPHONE Super Capacity H.T. Radio Batteries are the latest development in British Battery manufacture and have been specially designed to meet the needs of users of valve sets who desire to improve reception and to eliminate the annoyance of frequent renewals and the "sizzling" hitherto experienced.

**LONG LIFE**—4 to 5 times as long as others.

**LARGE CAPACITY.**

**SILENCE IN USE.**

THESE MERITS ARE WORTH YOUR CONSIDERATION.

ASK YOUR DEALER ABOUT THEM.




Super Capacity, High Tension RADIO BATTERIES

Prices from 7/6 to 27/6

Sold by Wireless and Electrical Dealers everywhere

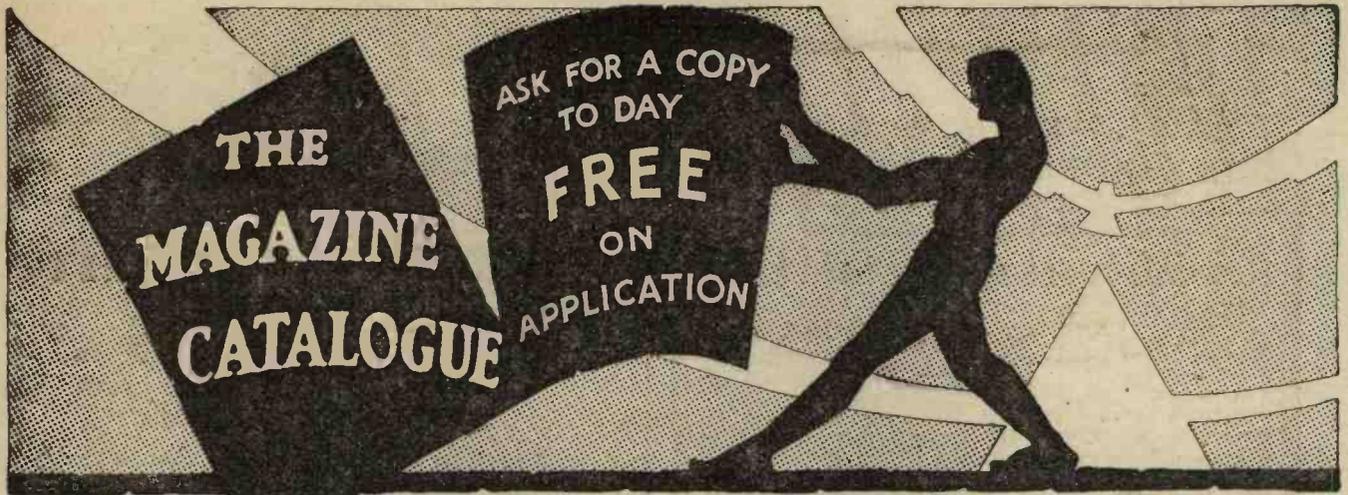Manufacturers: Th. General Electric Co., Ltd., Magnet House, Kingsway, W.C.



# CLIMAX RADIO

## UP-TO-DATE

Yesterday—to-day—and to-morrow. The experiences of yesterday in the light of the knowledge of to-day point clearly to the practices of to-morrow.—See the "Climax Magazine Catalogue."

**THE CLIMAX RADIO EARTH.** (Prov. Pat. 17653).—The low loss direct tubular earth. Far better than the old-fashioned water-pipe or gas-pipe earth. Provided with flanges which break up the earth around the tube, thereby preventing any rocking of the tube in the ground. In addition, the surface projections provide water courses, making perfect electrical contact. Ready for use. Easily fitted. Maximum efficiency. Length approx. 30 ins. Price, 5/-.

Prof. A. M. Row  
on  
"THE POSSIBILITY  
OF TELEVISION."

W. B. Medlam, B.Sc.  
A.M.I.E.E.  
on  
"Building a  
superheterodyne"

Articles on "Building a  
Wireless Set," "Upkeep of a  
Crystal Set," "These Micro-  
phonic Noises," "Dodging  
the Aerial," and many others

Full details  
of all the new  
CLIMAX RADIO  
COMPONENTS and SETS

**THE NEW CLIMAX AERIAL INSULATOR** (Regd. Design No. 708718)—Stands four times the flash over voltage. Far less capacity to earth. Will stand a direct pull of hundreds of pounds. Entirely non-hygroscopic. Cannot absorb moisture even if fractured. Insulates perfectly during rainfall. Self-cleaning on all surfaces. Price per pair 1/-

**THE CLIMAX INSULATED SHOCK ABSORBER SET.**—Comprising set of four Climax low-loss aerial insulators and two Climax aerial shock-absorbers, 3/- per box.

If you believe in metal—and who does not?—use exclusively Climax Rheostats and Potentiometers. They are wire wound on metal cooling cores with vitreous enamel insulation.

Price—Climax Rheostats, 6 ohm pattern for one, two or three bright valves 3/- each  
Climax Rheostats, 30 ohm pattern, Universal pattern for D.E. or Bright Valves, 4/- each  
Climax Potentiometers, 300 ohm pattern 5/- each

**CLIMAX RESISTANCE CAPACITY UNIT FOR L.F. AMPLIFICATION.**—A new convenient design of Resistance Capacity coupling unit embodying the Climax fixed Mica Condenser, the Climax Wire Wound Anode Resistance and the Climax New System Grid Leak. Each item is readily replaceable and interchangeable so that the discriminating user has complete freedom of control. Price 12/6



**THE CLIMAX ANTI-MICROPHONIC VALVE SOCKETS.**—No larger than the old-fashioned solid sockets. Readily fitted to any existing panel. They fit flush with the panel and give a particularly attractive appearance, and protect the valve from accidental damage. Fitted with the Climax patented hour-glass spring contacts. The valve floats on metal springs. Perfect electrical contact. Set of four Climax Anti-microphonic Valve Sockets, per box 2/-.

**CLIMAX FIXED MICA CONDENSERS.**—Manufactured of the finest mica, having extremely high insulation resistance and the lowest possible dielectric losses. Fitted with substantial terminals and mounted in vitreous porcelain containers of the highest grade. Guaranteed accurate within 5 per cent.


Price: .0001 mfd. to .0009 mfd. 2/- ea.  
.001 mfd. to .006 mfd. 2/6 ea.

**THE CLIMAX POPULAR L.F. TRANSFORMER.**—A highly efficient transformer for general low frequency amplification. Specially designed to give uniform amplification over the widest possible range of frequencies. Reproduction of speech and musical notes is therefore exceptionally good and pure. Price 17/6

Insist on the name "CLIMAX," refuse substitutes. If substitutes are offered, send you order direct to us together with P.O. and we will send the goods by return.
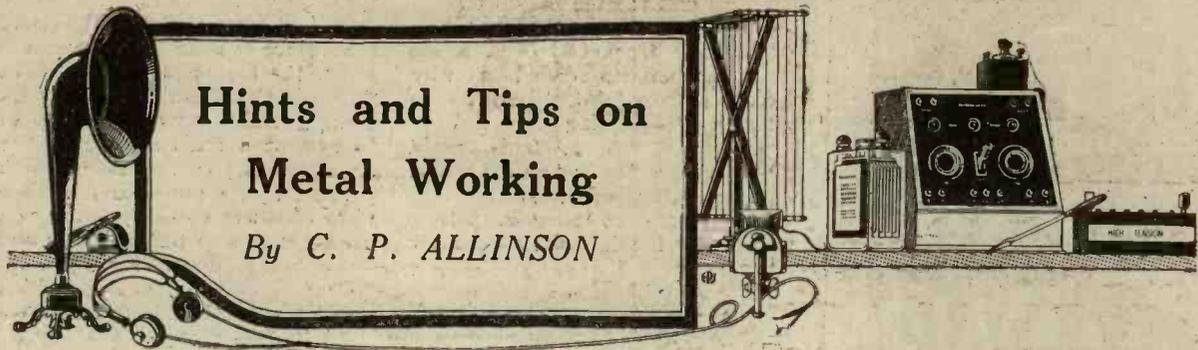
### CLIMAX RADIO ELECTRIC LIMITED

Head Office and Works **QUILL WORKS, PUTNEY, LONDON, S.W.15** Telephone—Putney 2599  
All Communications to Head Office  
Showrooms • **257, HIGH HOLBORN, LONDON, W.O.1** Telephone—Holborn 2538



## Hints and Tips on Metal Working

By C. P. ALLINSON

**T**HE wireless amateur who makes his own apparatus may frequently be called upon to make special parts for himself out of brass or copper, and a few hints on how to set about such work are given here.

The first point to consider is that relating to cutting these metals. A hacksaw is generally used, and the teeth of the blade should be coarse, otherwise they will clog up easily, and, of course, no lubricant should be used. Thin sheet may be cut with a pair of shears, but if so thick that the hacksaw has to be used, the work should be held in the vice so that there is no "spring" in it. The portion being cut should, therefore,

be within an eighth of an inch of the jaws of the vice, and it may have to be shifted after every three or four cuts. If this is not done it will be found that the hacksaw blade is soon minus teeth.


### Cutting Sheet Metal

Another method of cutting sheet metal that is just too heavy to be cut by a pair of "snips" is to place it on a metal plate (a piece of iron or mild steel  $\frac{1}{2}$  in. thick, or the back of the vice will do), and having marked the outline of the piece required, to go all round it with a sharp-edged cold-steel chisel and a hammer. It may be necessary to go round two or three times before the metal is cut through,

and enough metal should be left outside the marking line to allow the piece to be trimmed up afterwards with a file.

When thick metal is being worked and an irregularly-shaped piece is required, or when a slot or large hole has to be cut in it, the best procedure is to drill a series of holes round the marking line, run the holes together with a small cross-cut chisel, and file up to shape. The cut edge has now to be finished off, and it should therefore be filed to within about  $\frac{1}{64}$  in. of the marked line. A handy size file for this is a 9 in. second cut, or even a coarse cut may be used. The surface, if discoloured or rough, may also be
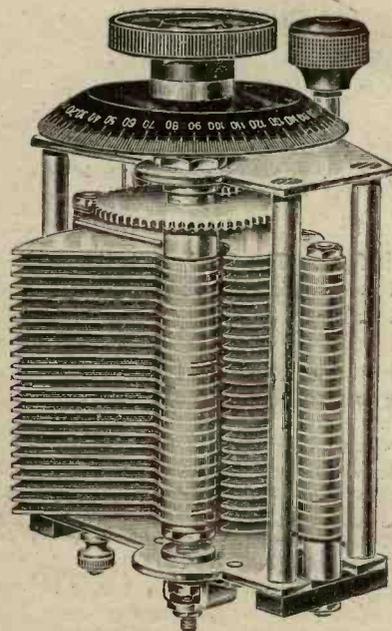
## For modern radio conditions prefer condensers of modern design



**W**ITH the rapidly congesting broadcast wave-band selectivity acquires a new significance.


The reception of distant signals is complicated by the opening of Broadcast stations on nearby wavelengths and considerable interference is experienced. These are the modern conditions with which every experimenter is faced.

Little relief from interference can be expected except when super-sensitive circuits are utilised—the tuning of which logically demands extreme low loss. This then is the modern practice—low loss, selectivity follows in logical sequence.

The new J.B. Low Loss Tuning Condensers illustrated here conform to modern design and embody principles which make for extreme low loss. The N.P.L. report that the .0005 mfd. J.B. Low Loss has a loss of .02 ohms—absolutely negligible wherever the instrument may be used.

LOW LOSS		LOW LOSS	
		Geared Vernier	
.001 ..	13/-	.001 ..	17/6
.00075 ..	11/9	.00075 ..	16/3
.0005 ..	10/6	.0005 ..	15/-
.0003 ..	9/-	.0003 ..	13/6
.00025 ..	8/9	.00025 ..	13/3
.0002 ..	8/6	.0002 ..	14/-
.0001 ..	8/3	.0001 ..	12/9

British and Foreign Patents Pending.

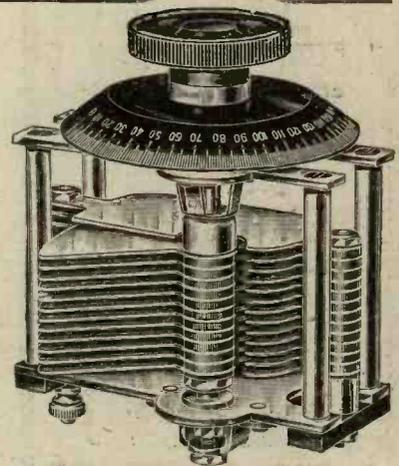

Other outstanding distinctions include:—  
Losses absolutely negligible (.02 ohms at a million cycles .0005 mfd.)  
Plates rigidly supported at two points.  
Pigtail connection.  
Earthed Rotor and Frame (giving perfect freedom from hand capacity).  
Minimum solid dielectric.  
Ingenuously designed frame (giving exceptional rigidity).  
Metal end plates. Conforming to modern practice. Minimum capacity scarcely affected.  
Correct Square Law.

If your dealer cannot supply, send direct  
Post: One 6d.; Two 9d.; Three 1/-.

**JACKSON BROS**  
8, POLAND ST- OXFORD ST  
LONDON - W.1.  
(First Floor)  
Telephone: GERRARD 7414

**ULTRA**  
REGISTERED TRADE MARK



27/6

Ask your Dealer for it

“Ultra” Loud Speakers are unsurpassable for sensitivity, clear and perfect reproduction.

These qualities are only to be found in “Ultra” products.

Traders, write now for our Illustrated Pamphlet to

**Messrs. E. E. Rosen & CO.**

661-663, Harrow Road  
LONDON, N.W.10

Telephone WILLESDEN 4544

**ULTRA**  
REGISTERED TRADE MARK

filed up, and the file should receive frequent dressings of chalk and be cleaned frequently with a file card (sometimes called a wire brush or scratch-file), so as to prevent it clogging up, and to give a good surface. This should be done especially when a fine-cut file is being used, such as a smooth or dead smooth. If a coarse-cut file has been used for

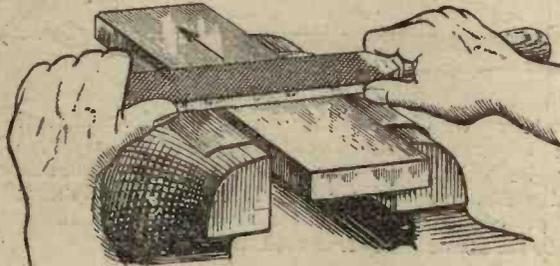


Fig. 1.—This method of “draw-filing” gives the metal a good finish.

the first trimming, a second cut should be used next, and after this a smooth, and if required, a dead smooth last of all. The surface may finally be “drawfiled” to give it really high-class finish. This is done by grasping the file by both ends, one in each hand, and drawing it across the work, backwards and forwards, at right angles to the length of the file. The sketch shows more clearly how this is done. Care must be taken to keep the file clean, as if the cut gets clogged in the least degree scratches will be left on the work.

**Flat Surfaces**

Great care must be exercised when filing flat surfaces to, keep them not only flat but square. Skill with a file is only acquired by practice, but you should not let yourself be discouraged by the workshop saying that “it takes a man five years to learn to file flat!”

**Cutting Tubing**

When you have to cut brass or copper tube a little care is required, and it should not be cut right through, or the hacksaw teeth will suffer. Take several cuts, rotating the tube thirty or forty degrees after every cut, till it is through everywhere except in one place;

the piece wanted can then be easily separated from the stock. Should the surface be so rough as to require filing, the file must be rocked, as shown in the illustration, the work being turned thirty or forty degrees to present a fresh surface to the file after every cut. Finally, a high polish may be given to it with a piece of emery cloth by tearing off a long strip and pulling it up and down rapidly over the work, which should be held in a vice.

It should here be noted that when working with any soft metal, such as copper or brass, it should never be put in the vice without a pair of jaw guards being used. These are made of sheet lead about  $\frac{1}{4}$  in. or  $\frac{3}{8}$  in. thick, bent over

the jaws of the vice so as to prevent pieces of soft metal being marked by the jaws.

**Lacquering**

Should it be desired to lacquer the finished piece of metal, this is preferably done hot. The work should be carefully cleaned with a drop of petrol or turpentine to remove all grease from the surface, and then heated above a gas flame till it is about blood heat. The lacquer is then applied with

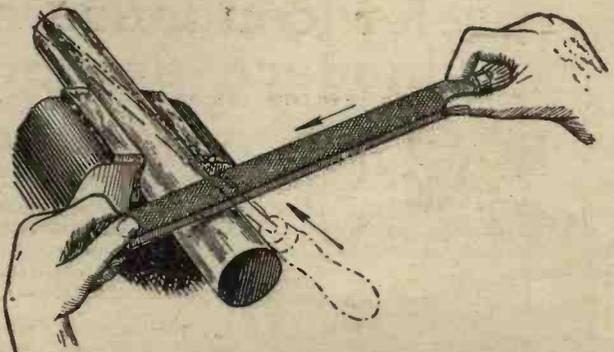


Fig. 2.—How tubing is filed. The file is rocked to and fro, while the tube is turned round during working.

a very fine brush and the piece hung up to dry. Where a rich lacquer colouring is required several coats may be given till the desired shade is reached, each further coat being applied only when the previous one is quite hard.

**Riveting**

A job that frequently has to be tackled is to join two pieces of metal, and the method to be



**Verb. Sap.**

**W**E have tried practically every transformer on the market and your transformers certainly are by far the best, both for ordinary use and for Power Amplification and, what is very important, they are the most convenient for mounting.

"Their chief advantages over others are strength, clearness of speech and music, and entire absence of howling even when placed very close to each other.

"In the hands of amateurs, they should also be splendid for their freedom from self-capacity effects."

In these words a prominent West London Wireless Firm gives its unsolicited opinion of the M-L Low Frequency Transformer. Their satisfaction can easily be shared by you—M-L Transformers only cost 25/- each, and the name "M-L Wireless" appears conspicuously on the container.


The 1:6 ratio is used for amplification after a crystal rectifier. The 1:4 ratio is used for single stage L-F Amplification. The 1:2:6 and 1:4 ratios are used respectively in the first and second stages of two-stage amplification.

**S. SMITH & SONS (M.A) LTD.**  
 179-185, Great Portland Street, London, W.1  
 Telephone: Langham 2323    Telegrams: "Speedamet, Telew, London"  
 Also at Birmingham, Manchester, Glasgow and Belfast.

**S. SMITH & SONS (M.A) LTD**

E.P.S.2.


**Quality**  
 RADIO  
**COMPONENTS**

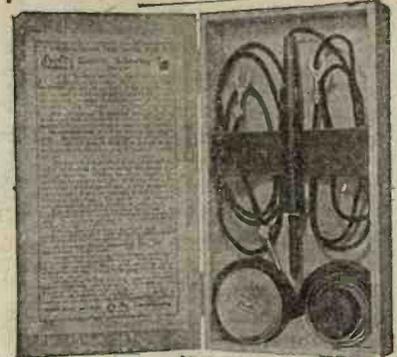

**SOLDERING**

simplified by this new invention, which works from any wireless accumulator with a carbon soldering bit. No gas, fire or lamp needed. Everything necessary, including Flux and Solder, in stout wooden box, for 5/6.

Postage 3d.

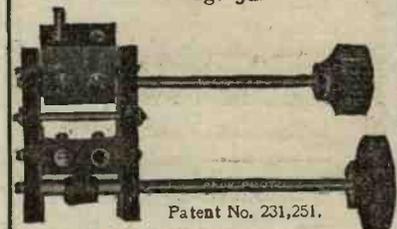

Patent No. 231,251.

**Quality** Cam-Vernier  
 RADIO Coil Holder


Price 9/-, on base 1/- extra. With Reaction Reverse and Shorting Switch incorporated, 12/6

Postage 4d.

**BOX SPANNERS for B.A. NUTS**

2, 4, 5 and 6 B.A. Price 1/- each.

Postage 3d.

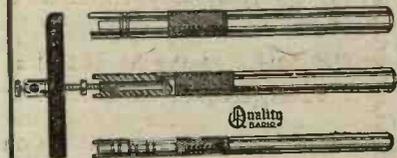

If your dealer has not got them, we send post free if you mention his name and address

**GOSWELL**  
 ENGINEERING CO. LTD.

95, WHITE LION STREET, LONDON, N.1  
 Liberal Trade Terms. Phone: North 3051

employed will depend on circumstances, such as whether they are large or small pieces, thick or thin, whether a flat surface is a *sine qua non*, etc., etc. Three methods that may be used are riveting, bolting or soldering (sometimes



Fig. 3.—Two forms of rivet, namely cup-head and countersunk-head, respectively.

called sweating) them together. Many amateurs are rather shy of riveting, but once it has been tried and accomplished its terrors will be found to be greatly over-estimated. Two forms of rivets are shown in Fig. 3 at "a" and "b," which are cup-headed and countersunk respectively. The method to be followed in riveting is as follows: Suppose the two pieces of metal (Fig. 5) are to be joined, with an overlap between the edges AC and BD. Determine the amount of overlap that is to be allowed (this should be about twice the thickness of the metal) and scribe a line on one of them showing where the edge of the other is to come. We will suppose that three rivets are going to be used at the points marked in the figure. Larger pieces might, of course, require more rivets, according to



Fig. 4.—Rivets may be filed flush to preserve a neat appearance.

what use the finished piece is to be put and how strong the finished job has to be. The rivets used are to be countersunk so that a smooth surface will result. The size of rivet will again depend on the weight of the work, and we will take them as being  $\frac{1}{8}$  in. rivets, which is a fairly useful all-round size.

**Drilling the Rivet Holes**

The pieces of metal are clamped together with the edge of the one piece along the scribed line on the other, and three  $\frac{1}{8}$  in. holes are drilled right through with a small brace and twist drill. Both sides are then countersunk with a  $\frac{1}{8}$  in. drill, but if cup-headed rivets are used, only one side need be countersunk, and even that is not necessary if the surface does not have

to be flat on that side. The rivets are now driven through the holes and they should project about  $\frac{1}{8}$  in. on the other side. The work is then placed on a heavy piece of metal, such as the jaws of a vice, with the head of the rivets downwards and the projecting end of the rivet hammered over with the ball of a ball-pene hammer. The hammer should be "pulled" slightly so as to spread the metal, and if the rivet is being countersunk it should be hammered well in to the countersink. This will make a good strong joint, and when countersunk rivets are used both sides can be filed flush so as to

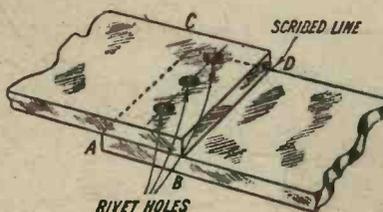


Fig. 5.—Illustrating the procedure when two pieces of metal are to be riveted.

make a neat job, and the rivets will be barely visible. A section of such a joint is shown in Fig. 4, and will help to make this clear.

**Another Method**

Another method is to fix the two pieces together with screws. In this case the holes through the one piece of metal will be clearance holes, and those in the other tapping holes tapped out with the correct thread for the screws that are to be used to hold the two pieces of metal together. The screws are put in tightly with a screwdriver, and the projecting ends may be burred over with a hammer so as to prevent their slacking off. Alternative methods are to employ thin lock nuts or to file off the ends of the screws on the side that they project and make a number of centre punch marks round the edge of the screws so as to prevent



Fig. 6.—Screws may be used as rivets.

them from turning. If a lock-nut is used you can do away with the need to tap the holes in the one piece of metal and the nut can be prevented from slacking back either

by the burring or centre punch method. A little shellac varnish applied to the threads of a screw will also prevent it getting loose.

**Drilling Brass**

We may now consider the question of drilling and tapping brass or copper. No lubricant should be used, except a little "monkey juice," as the workshop mechanic calls it, otherwise saliva. This may be applied if the drill or tap runs hot. The chief thing is that the drill should be sharp, or else it will push its way through instead of drilling, it will get excessively hot and may lose its temper. Also when the drill comes through there will be a nasty burred edge which has to be filed off. For those who are used to sharpening drills it may be stated that the correct angle for the cutting edge is 59 degrees and that the clearance required when drilling brass is greater than that required for working with mild steel or iron. When drilling thin brass or copper sheet it should be clamped between


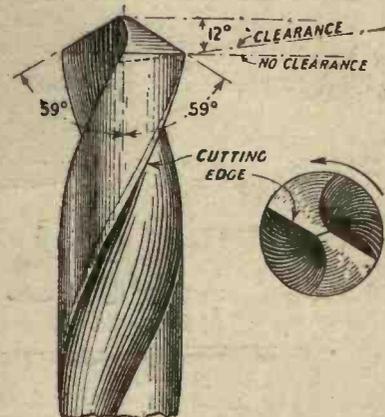


Fig. 7.—Showing the clearance and cutting angles for drilling brass and copper.

a couple of pieces of wood, so that it cannot move and the drill revolved rapidly with fairly light pressure, otherwise the metal may tear.

Drills and taps in brass should be run at a fairly high speed, if possible, but when tapping a hole by hand care should be taken to see that the tap enters straight, or else the tap may jam and break, or the thread you are trying to cut may be entirely stripped. When tapping copper it may be found advisable to remove the tap after every few cuts and clear it, as the copper is so soft that it may clog the cutting edges of the tap and tear the metal, thus stripping the thread.

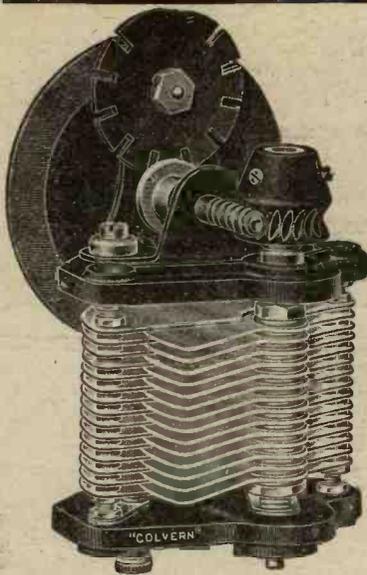

Little experience is necessary upon any such super-sensitive circuits as the short wave side of the Super-Heterodyne or capacity-reaction circuits to self-demonstrate that distant work is an impossible pastime without a mechanical fine tuning device operating on the condenser

**It's when you want to calibrate—**

your receiver to dead accuracy that the Colvern Selector proves its superiority as a fine tuning device.

Every other vernier device can only be calibrated with certainty to a degree interval. Obviously, any smaller interval must be imaginary and its relocation arbitrary.

Home Constructors are aware that a vernier knob provides only slow motion—the dial or indicator continuing to travel at the same rate as the moving vanes.

The Colvern Selector is a geared condenser and embodies a system of fine tuning control which permits the definite and accurate location of any pre-determined calibration. The dial is divided over the full circle and provides 360 degrees value for each rotation of the index.

**COLVERN  
SELECTOR  
LOW LOSS  
GEARED CONDENSER**

**COLLINSON PRECISION SCREW CO., LTD.**  
Provost Works, Macdonald Road, Walthamstow, E.17  
Telephone: Walthamstow 532

Barclays Ad.

By this system ten complete turns of the dial reduces a one degree interval to the equivalent of 1/36000th part of the variable capacity.

In point of fact, the Colvern enables you to tune to a degree of accuracy that is 20 times greater than ordinary vernier adjustment. It is an instrument which will give the precise tuning essential to perfect reception, whether of local broadcast or weak distant transmission.

- The Colvern Selector Low Loss—  
Reading to 1/36000th of capacity  
Capacity 0005 mfd. . . . . £1 1 0  
    " 0003 mfd. . . . . 1 0 0
- Type F without gear attachment—  
Capacity 0005 mfd. . . . . 15 0  
    " 0003 mfd. . . . . 14 0
- One hole fixing. Other capacities if required.

Descriptive Folder upon request.

Your dealer also sells

- The Colvern Independent Vernier  
—a very effective instrument . . . 2 6
- The Colvern Low Loss Coil Former  
—with the threaded supporting rods. Reduces the self-capacity of a coil to the lowest yet . . . 6 0



**5/6  
COMPLETE  
WITH  
CRYSTAL**

**Harlie  
SUPER-SENSITIVE  
DETECTOR**

The irritating business of finding a good spot on your crystal is over for ever the moment you fix a "Harlie-Detector"—the world's best rectifier for crystal and reflex circuits.

This wonderful little invention combines the most sensitive crystal yet produced with an entirely new and vastly superior method of contact.

In the "Harlie" the crystal rotates whilst the "catwhisker" remains stationary. The contact is never broken and is always at the exact delicate tension required for perfect reception.

By simply turning the knob the best spot is instantly found. It can be done in the dark as easily as in the light and adjusting does not interrupt reception.

It can be fitted to your set in a few moments. When required, a new crystal can be inserted in an instant without any soldering or irksome adjustment.

A clinching argument in favour of the "Harlie-Detector" is that it has been adopted by the MARCONI INTERNATIONAL MARINE COMMUNICATION CO., LTD.

If your Dealer does not get stock send to us—TO-DAY

HARLIE BROS., 36, WILTON ROAD, LONDON, E.8

Dear Sirs,


I enclose herewith 5/6 for one HARLIE-DETECTOR to be sent to me post free on the understanding that my money will be refunded, without question, if I return the Detector undamaged within ten days.

Name .....


Address..... 10

Merrill Service

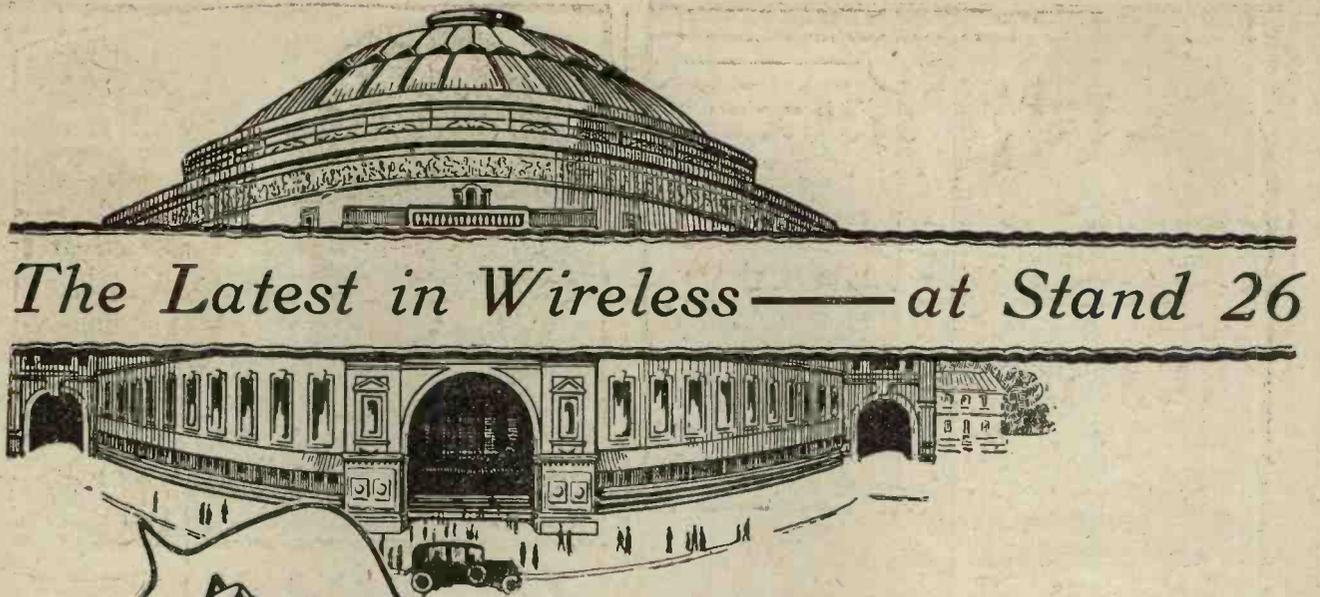**For the latest, most efficient  
AMERICAN COMPONENTS**  
write to the leading British Stockists  
**THE BRIGHTON RADIO STORES**  
who offer a highly organized mail order service,  
vast stocks, and a courteous reply to your  
enquiries.  
Mail us your requirements to-day  
**THE BRIGHTON RADIO STORES**  
(Super Heterodyne Specialists),  
**163, Western Road, BRIGHTON**



*The Latest in Wireless* — at Stand 26

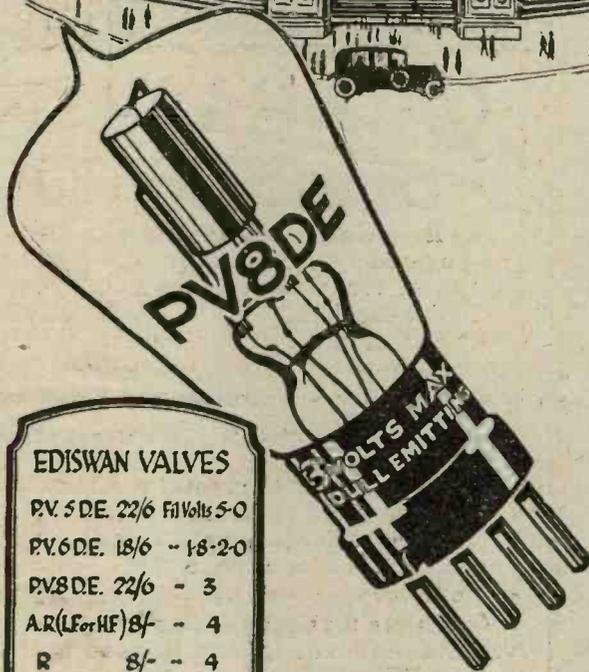

EDISWAN VALVES	
PV. 5 DE.	22/6 Fil Volts 5-0
PV. 6 DE.	18/6 - 18-20
PV. 8 DE.	22/6 - 3
AR (L For HF)	8/- - 4
R	8/- - 4
AR DE (L For HF)	14/- - 18-20
AR 26	16/6 - 25-3

**E**VERYTHING to ensure perfect reception . . . at the Ediswan Stand. Come and see it!

Come and see the latest in Sets and Loud Speakers, in Components, in Valves, all embodying some novel feature to assist flawless reception, some feature exclusive to Ediswan.

And bring your Wireless problems with you. The Ediswan Experts can solve them for you!

# EDISWAN

*"The Latest in Wireless"*

N.A.R.M.A.T. WIRELESS EXHIBITION, SEPT. 12th—23rd, 1925  
 ROYAL ALBERT HALL  
 STAND NO. 26

THE EDISON SWAN ELECTRIC CO. LTD.  
 123, QUEEN VICTORIA STREET, LONDON, E.C.4



The new SERVICE

# SQUARE-LAW LOW-LOSS FINE TUNING CONDENSER

(PATENT PENDING)

(FOR COARSE AND FINE TUNING)

Exceptionally fine tuning can be obtained by the  
**100-1 Reduction Gear**

SALIENT FEATURES:

1.—Exceptionally Fine Tuning obtained by the 100 to 1 Reduction Gear. "Service" Condensers are made with the highest ratio geared adjustment ever developed for fine tuning.

2.—Low Wave Stations can be easily separated, the special shaped vanes giving straight line frequency variation.


3.—Hand Capacity effects are eliminated by means of a special device which completely insulates the hand spindles from the working Vanes.

4.—Brass Vanes soldered together to minimise resistance losses. Vanes have direct No Loss metallic paths to their terminals.

5.—Frictional and erratic contacts entirely dispensed with.

6.—Numerous other Low Loss features in the design of "Service" Condenser.

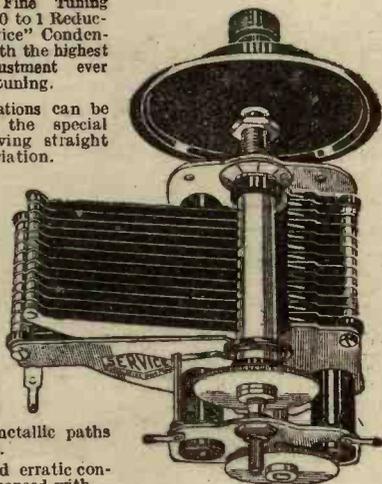7.—Sound Constructional job mechanically and electrically efficient.



PRICES:


001 mfd. 25/- 0005 mfd. 20/- 0003 mfd. 18/6 0002 mfd. 17/6

Obtainable at all Radio Stores

The World-Famous  
"SERVICE"  
Crystal Detector

"The Best Detector on the Market." It is dustproof, and has a Patent Micrometer Adjustment, therefore rendering it absolutely unaffected by vibration, and enabling the cat-whisker to be regulated to any requirement. It is without doubt the Best Value obtainable.

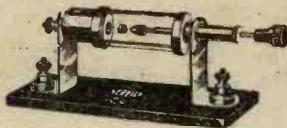
Best Nickel-plated Finish.  
Retail Price 2/6 (panel mounting); 2/9 (mounted on ebonite base).



A free sample of the New "SERVICE" Long Distance Crystal supplied with each Detector

Sole Producers:—

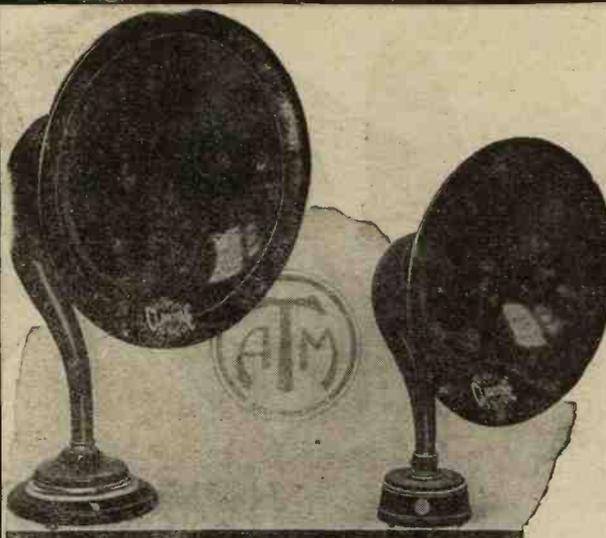**The Service Radio Co., Ltd.**  
67 Church Street, St-ke Newington, London, N.16



# CLARITONE LOUD SPEAKERS

enable you to appreciate the pleasure of perfect reception and to obtain that sweet purity of tone so dear to all music lovers. They stand unequalled in quality and service, and are recognised as a true example of faithful sound reproduction.

New Fixed Prices for Season 1925-26

## SENIOR MODEL CLARITONE

2,000 ohms - W 290 £5:0:0  
120 ohms - W 291

## JUNIOR MODEL CLARITONE

2,000 ohms - W 295  
120 ohms - W 296

£2 : 15 : 0

## CLARITONE HEADPHONES

20/-



Supplied by all reputable dealers

SOLE AGENTS:

## The ASHLEY WIRELESS TELEPHONE COMPANY

69 RENSCHAW STREET, LIVERPOOL

Telephone—4628 ROYAL      Telegrams—ROTARY, LIVERPOOL

London and Southern Counties:  
PETTIGREW and MERRIMAN  
122 Tooley Street, London, S.E.1

# It's here!

## THE NEW SUPER FULSTOP CONDENSER

—the greatest advance in variable condenser construction since the introduction of wireless.

Fifteen months ago the Fulstop Variable Condenser superseded all other condensers. It possessed two entirely new features—it was geared and it abolished absolutely hand capacity effects. The new Super Fulstop Condenser is as far in advance of the old Fulstop as that was in advance of ordinary variable condensers. This is why.


The new Super Fulstop Condenser is fitted with dual gearing. It has two operating knobs. One has a gear ratio of 2-1 and is used for first adjustment. The second—a small vernier knob—is geared 125 to 1 and is used for final critical tuning.

The dial is graduated round the whole circumference from 0 to 100. These graduations are again divided, giving 200 actual readings. Each reading is capable of an infinite number of adjustments by means of the vernier gearing.

The clockwork multigear is made by watchmakers for the sake of accuracy and is quite free from backlash.

It is a no-loss Condenser, is perfectly square law and has brass vanes.

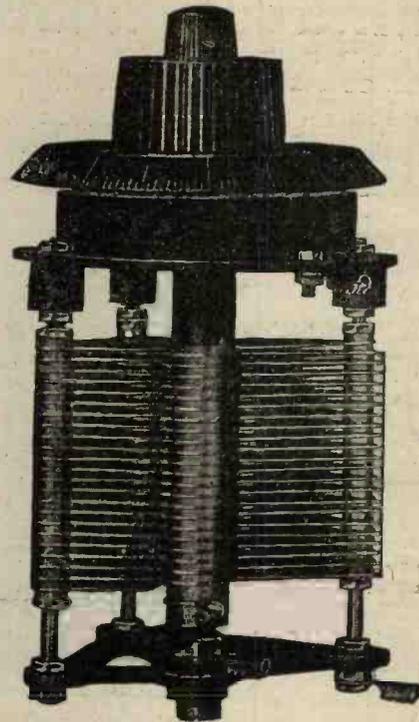It is the superlative Condenser, and is positively unapproached by any other variable Condenser made.



**GUARANTEED TO ABOLISH HAND CAPACITY EFFECTS**

Made in 3 models.

**SUPER FULSTOP.**

·00025	...	...	...	25/6d.
·0005	...	...	...	28/6d.
·001	...	...	...	30/6d.

The Standard Fulstop, geared 2 to 1, is still in great demand. We also make the Plain Fulstop without gears

**Prices**

STANDARD FULSTOP		PLAIN FULSTOP (no gears)	
·0002	- - 9 6d.	- -	8 3d.
·0003	- - 10/3d.	- -	8/9d.
·0005	- - 11/3d.	- -	9/6d.
·001	- - 13 6d.	- -	11 6d.

Send for full descriptive leaflet free.

There are three Models, and all are guaranteed for twelve months.

Protected throughout the world.

If any difficulty in obtaining write us and we will send direct post free.

**Fulstop**  
VARIABLE CONDENSER

**J. H. NAYLOR LIMITED, WIGAN**

**NO MATTER what CIRCUIT  
YOU DESIRE to CONSTRUCT**

you will find we carry a full range stock of requisite parts, of the best possible quality for the:—

NEUTRODYNE, SUPER-HET-  
ERODYNE, MICRODYNE,  
TROPADYNE, ULTRADYNE,

and all the latest reflex Circuits. Do not fail to inspect the latest in Positive Low Loss Condensers, the most efficient matched Transformers, special minute Panel Switches, Geared Vernier Dials, 80-1, &c.

*Write at once for our Catalogue,  
post free by mentioning this paper*

**DAYZITE, LTD.**

18-19 LISLE STREET, LONDON, W.C.2

Phone: 4577 Regent.


Telegrams: "Titles, Westrand"



One-hole Fixing and  
Wiring

(Proc. Patent)

**VERNIER  
COIL - HOLDER**

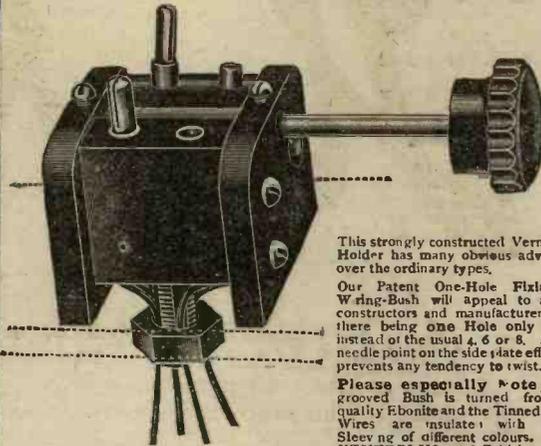

This strongly constructed Vernier Coil Holder has many obvious advantages over the ordinary types.

Our Patent One-Hole Fixing and Wiring-Bush will appeal to amateur constructors and manufacturers alike, there being one Hole only to drill instead of the usual 4, 6 or 8. A small needle point on the side plate effectively prevents any tendency to twist.

Please especially note: The grooved Bush is turned from best quality Ebonite and the Tinned Copper Wires are insulated with Rubber Sleeve of different colours. IT IS ETHERPLUS—and British made.

Under panel connections, one hole for both fixing and wiring. Adjustable vernier roller. Perfect contact without flexible or moving wires.

W/17 (Single) at 1/4 each  
W/52/2 (Two-way) at 6/6 each  
W/53/3 (Three-way) at 8/6 each

From all Dealers or direct from

**M·AND·AW** 9-15, WHITECROSS ST., LONDON, E.C.1  
Full Illustrated Catalogue of "Etherplus +"  
Components FREE on application.

**SPECIAL NOTICE.**

REVISED PRICES OF THE WORLD-FAMOUS

CLARKE'S  
**"ATLAS"**  
LOW LOSS COILS

PATENT N° 215053

Coil Nos.	25	30	35	40	50	60	75	100	150	200
Prices	4/3	4/3	4/3	4/5	4/6	4/10	4/10	6/3	7/0	8/0
Coil Nos.	250	300	400	500	600	750	1000	1250	1500	
Prices	8/6	9/0	10/0	10/3	11/0	12/6	13/9	15/6	17/6	

*Ask your Dealer for Revised Lists.*

The best—as the whole world's finding—is the coil with the twin-wire winding

*Sole Manufacturers:*

**H. Clarke & Co. (Manchester) Ltd., Atlas Works, Old Trafford, Manchester**

BRITISH  
MADE

# Six Sixty

B. B. C.  
STAMPED

14/-

FILAMENT  
VOLTS 1.5-2

FILAMENT  
CURRENT  
3 amps

If your local dealer cannot supply, write direct to us. If possible please give dealer's name and address.



The Best Dull Emitter

**G**REAT volume is not usually associated with small current consumption.

But every user of the "Six Sixty" knows that in its patented MOLYBDENUM THORIUM COVERED FILAMENT, volume with economy is achieved as in no other valve, either bright or dull emitter.

Make it your next valve purchase.

Our folders, descriptive of the unique filament of the "Six Sixty" and giving users testimonies of recent achievements, merit your perusal. Send a post card to-day to—

**ELECTRON**  
C<sup>o</sup> LTD

TRIUMPH HOUSE  
189 REGENT STREET, LONDON, W.1  
Phone: Regent 5336

Testimony that tells


Grangetown, Yorks  
I wanted a good Valve as Detector. I purchased the "Six Sixty" Valve, and when I put it on the Set as a detector I got MANCHESTER, LONDON, ABERDEEN and NEWCASTLE, all on the LOU SPEAKER, a thing I never had had before. NEWCASTLE was deafening on the Loud Speaker, and a great many stations came swarming in on the phones.—J.C.M

## YOUR SET COULD BE IMPROVED

BY INCORPORATING

**BURWOOD**

All Metal Parts Nickel-Plated.

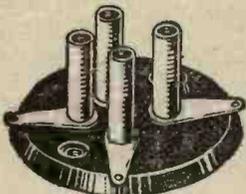

FINEST EBONITE.  
SAY NO! to Substitutes.

MINIMUM CAPACITY  
VALVE HOLDERS


Acknowledged an exceptionally efficient holder for BASEBOARD mounting, and a TRUE fitting. A QUALITY component at a reasonable price.

Neatly boxed & fully guaranteed. 1/3  
From all dealers or post free

**BURWOOD (CONCESSIONAIRES)**  
Ltd.

Great Queen Street, London,  
W.C.2

## DORWOOD CONSTRUCTOR'S GAUGE

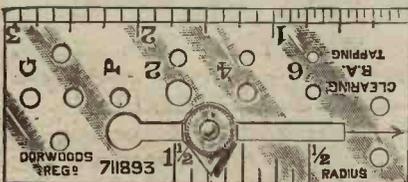

REGISTERED.  
BRITISH MADE

1/9

FROM YOUR DEALER,  
OR POST FREE FROM  
MAKERS.

NOTHING gives your panel more character and finish than neat accurate setting out of the parts. The Dorwood Gauge is indispensable to constructors. It comprises a Valve template, contact Stud Spacer to any radius, B.A. tapping and clearing drill gauges, 3 In. Rule and Square. Made in hard plate, silvered and finely engraved.

Sole Makers—

**DORWOODS, 274a, Kentish Town Road, London, N.W.5**

## Good News for every Crystal user

THE LEADING NATURAL  
GALENA CRYSTAL

**Gil-Ray**

is now reduced  
in price to—

1/-

Increased output and most advantageous contracts for supplies of galena, enables "Gil-Ray," the famous Crystal, formerly sold at 1/6, to become available to every listener, in all parts of Great Britain, at the price of 1/-.

You now obtain, at the price of an unobtainable and unguaranteed, inferior crystal, a high-grade Crystal with a definite guarantee of complete sensitiveness.

**GIL-RAY CRYSTAL** is natural—not synthetic, nor sensitised galena. Every piece is tested and sold under a guarantee of replacement if not found satisfactory.

Look for the buff Tin—containing liberal piece of Gil-Ray, full directions and guarantee slip.

Sold by all Wireless Dealers.

In case of difficulty, send P.O. 1/-, with Dealer's name, to:

**GIL-RAY TRADING CORPORATION**  
LTD.  
Sicilian House, LONDON, W.C.1  
Phone: Museum 3206



THE PANEL DE LUXE



**G**OOD news travels apace—and it is not surprising, therefore, to find that wireless enthusiasts are gladly paying the few shillings extra for Radion Panels. Already they have realised that at a very small extra cost they can insure against surface leakage and all the deadly ills to which cheap ebonite is prone.


**R**adion is available in 21 different sizes in black and mahogany. Radion can also be supplied in any special size. Black 1d. per square inch, mahogany 1½d. per square inch.

# RADION Trade Mark

American Hard Rubber Company (Britain) Ltd.

Head Office: 13a Fore Street, London, E.C. 2  
 Depots: 120 Wellington Street, Glasgow.  
 116 Snow Hill, Birmingham.  
 Irish Agents: 8 Corporation Street, Belfast

Gilbert Ad. 3318

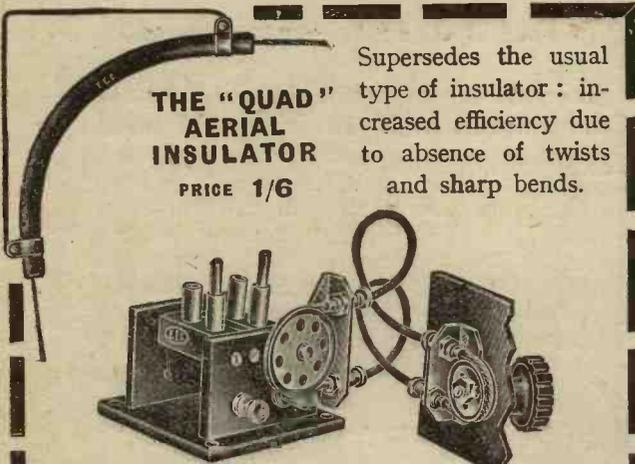

**THE "QUAD" AERIAL INSULATOR**  
 PRICE 1/6

Supersedes the usual type of insulator: increased efficiency due to absence of twists and sharp bends.

**THE "REMOCON" COIL STAND WITH REMOTE CONTROL.** Enables the stand to be mounted in any position irrespective of the control knob. Gives exceedingly fine adjustment with absence of back-lash.  
 PRICE, complete with 12 in. flexible controls, 12/6



**"DEXTRAUDION" VALVES** will increase the efficiency of your set


Order from this advertisement or write for new 44 page Radio Catalogue, post free if you mention "The Wireless Constructor."

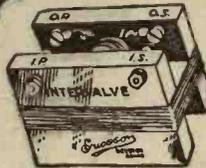**ECONOMIC ELECTRIC, LIMITED.**


Registered Offices: 10 Fitzroy Square, W.1  
 Showrooms: 303 Euston Road, N.W.1  
 Branch Works: Twickenham



**THE ERICSSON Dual Rheostat** found under every advanced amateur's panel. For any type of valve—bright or dull filament—works like silk.  
 Price 8/6



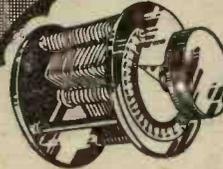Ericsson Transformers are perfect examples of the instrument maker's art. Give clear distortionless amplification in any circuit.  
 Ratios—1:2, 1:4.  
 Price 17/6



Tested condensers like Ericsson's are the last word in accuracy. Stout vanes, accurate spacing, sturdy workmanship, low losses.  
 .0005, 10/6  
 .001, 12/6



A new Ericsson line—a fine wave trap for tuning out powerful "locals," invaluable in DX work.  
 Price 60/-

The More you know about Wireless the better you'll like these components

**A**CCURACY—dead accuracy is the key-note of ERICSSON TESTED PARTS. Condensers, Transformers, Rheostats, Coil-holders, etc., etc., all have to pass a pretty stiff laboratory test at our Beeston Works before the market sees them.


All the DX fans are using Ericsson Tested Parts, for it's on long-distance work that good components pull their weight.

Write to-day for our splendid illustrated lists. Ask for particulars of our receivers, crystal and valve, headphones, loud-speakers, etc. Agents everywhere.

THE BRITISH  
**L. M. ERICSSON MFG. CO. LTD.**  
 67-73, KINGSWAY  
 LONDON, W.C.2

**Ericsson** (BRITISH)  
**TESTED PARTS**

# PILOT RECEIVERS

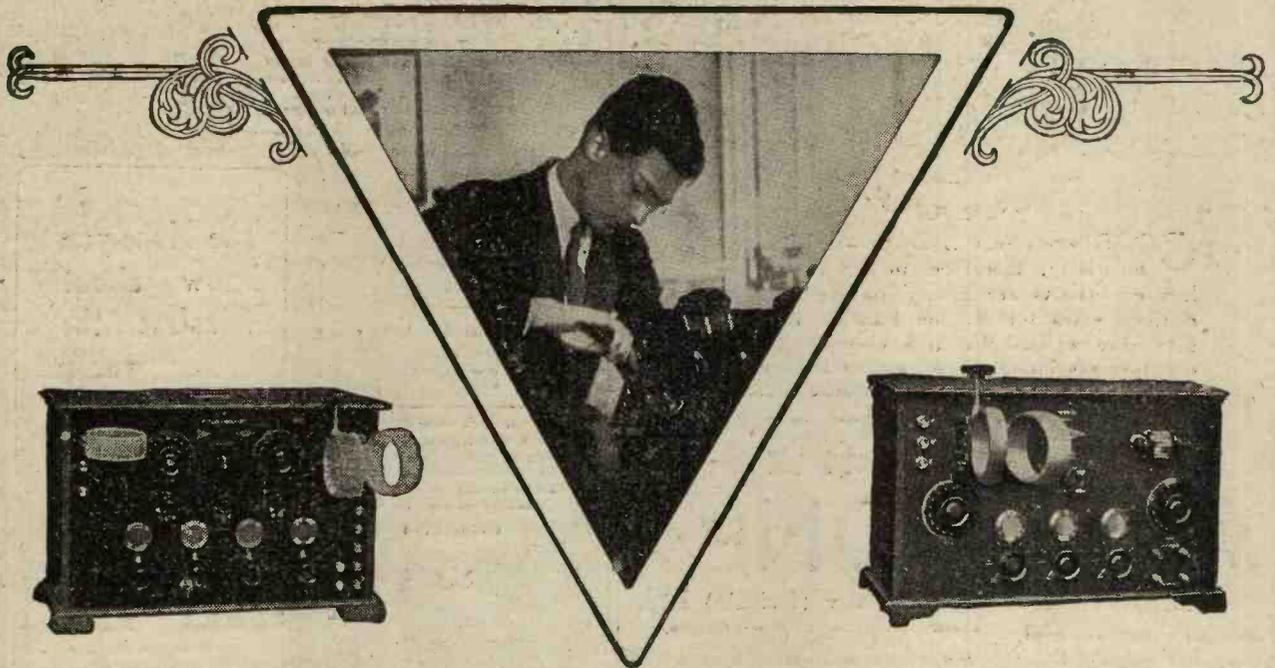

This new—and better—way guarantees you  
success in Set-building

**T**HOUSANDS of wireless enthusiasts at this moment are asking themselves this question: Shall I buy a ready-made Set or build one myself and save the difference? Many of them have already successfully built themselves Crystal Sets, but—and here their lack of confidence shows itself—they are afraid to tackle the building of a good Valve Receiver.

Now here is where the Pilot System of Simplified Set-building is proving itself to be the greatest and most helpful innovation of the season. No one can fail to get perfect results the first time with a Pilot Set. Even if you have never built a Set before we will still guarantee you complete success. The reason is not hard to seek.

Every Pilot Receiver combines efficiency with simplicity. Its panel is supplied cut to size, neatly engraved and accurately drilled. Every tested component

fits snugly into its position either on the panel or on the baseboard. The full complement of screws, terminals, nuts and bolts is supplied—nothing is missing and there is nothing more to buy. A most complete wiring diagram shows the position of each component and terminal and how it should be connected up. Everything has been done, in fact, to make the building of any Pilot Set the job of a few hours with no tools but a pair of pliers, a screwdriver, and a soldering iron.

The purchase of a Pilot Receiver in parts for home assembly carries with it a guarantee of complete satisfaction or money refunded in full. An expert Service Department is available for testing and correcting any instrument not giving satisfactory results. Why hesitate any longer? Just send 3d. for a copy of the Pilot Chart giving particulars of more than 30 splendid Pilot Receivers available in parts for home assembly.


#### List of Pilot Sets

All Concert de luxe  
Simplicity 3-valve  
3-valve Dual  
4-valve Family  
Transatlantic Five  
Anglo-American Six  
7-valve T.A.T.  
S.T. 100, etc. etc.

Illustrated Catalogue of Wireless Components (48 pages) 3d.

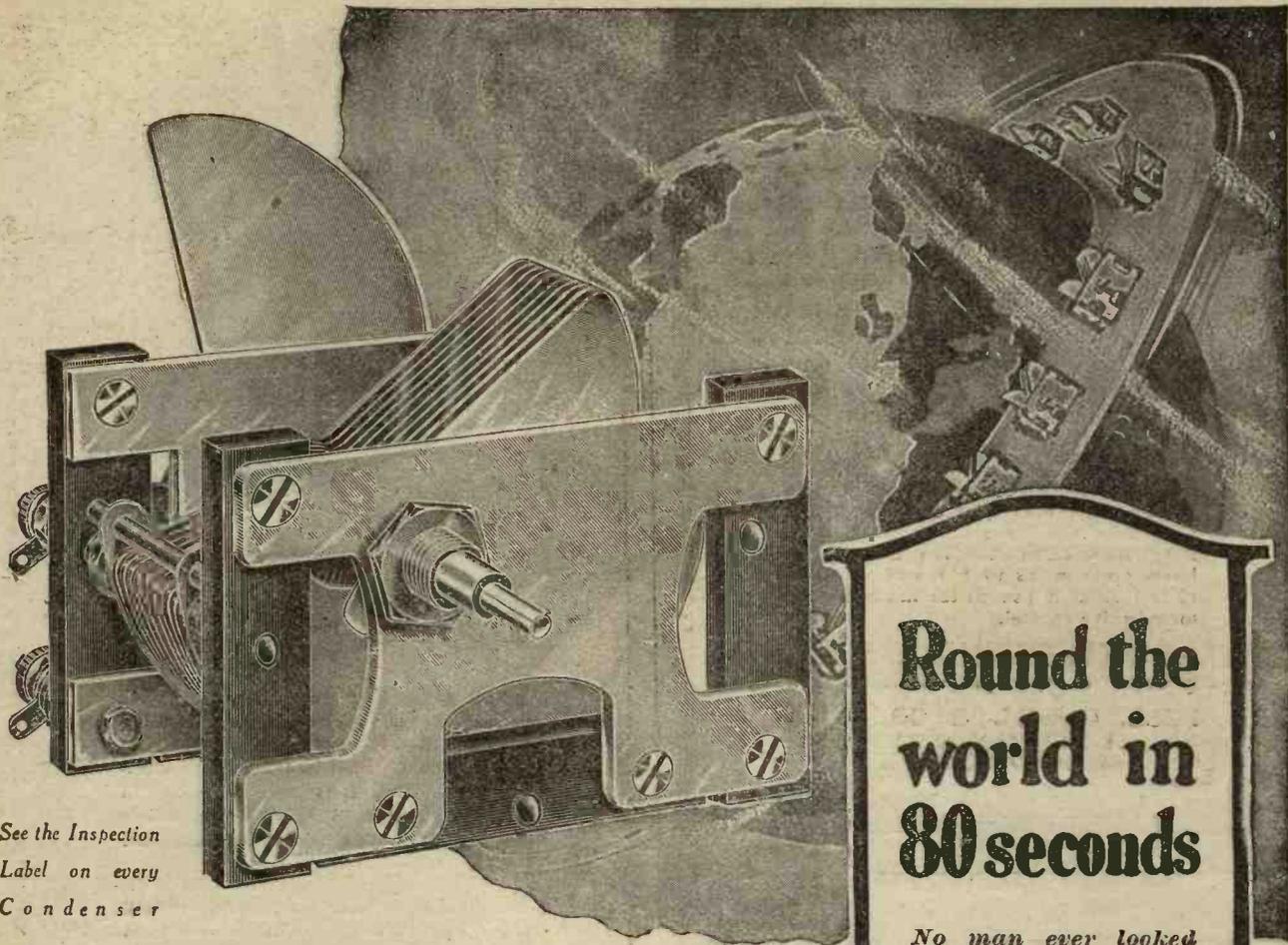**PETO-SCOTT CO. LTD. HEAD OFFICES: 77 CITY RD., E.C.1**

BRANCHES: 62 High Holborn, London, W.C.1. Walthamstow: 230 Wood Street.  
Plymouth: 4 Bank of England Place. Liverpool: 4 Manchester Street.



See the Inspection Label on every Condenser

## Ormond Low Loss Condenser

### SQUARE LAW

A new departure in British Condenser design, giving the following advantages:—

1. Practically negligible losses.
2. One-hole fixing—one  $\frac{3}{8}$ " diam. hole is needed to fix this condenser to panel.
3. Rigid construction—cannot warp; end plates of stout aluminium, perfectly flat.
4. Fixed vanes supported by  $\frac{1}{4}$ " ebonite strips.
5. Smooth action, spindle tension is maintained by a specially designed friction washer.
6. Moving vanes and end plates are at earth potential.
7. One-piece knob and dial—supplied loose. Secured by 4B.A. Set Screw.

This condenser is fitted with optional soldering Tags, or Terminals, and can be supplied with or without Vernier as desired.

Supplied in the following sizes:

Size	Price with Vernier	Price without Vernier
·00025 ...	8/-	6/6
·0003 ...	9/-	7/6
·0005 ...	9/6	8/-
·001 ...	10/6	9/-

Write for our new (1925) Catalogue and trade terms—

We specialise in turning brass and Steel Screws and Machined Parts and Accessories of all descriptions.



Complete with Knob and Dial.

All Cheques and Postal Orders should be crossed and made payable to "The Ormond Engineering Co."

199-205 Pentonville Road, King's Cross, London, N.1

Telephone—Clerkenwell 9344, 5 & 6

Telegrams: "Ormondengi, Kinross"

Factory—WHISKIN STREET, CLERKENWELL, E.C.1


25 YEARS' BRITISH MANUFACTURING EXPERIENCE

# Round the world in 80 seconds

No man ever looked into the future more accurately than Jules Verne. Yet even he did not foresee the day, now with us, when amateurs can tune in to stations all round the world with a speed that reduces the trip from 80 days to nearer 80 seconds.

The scientific achievements of to-day are possible owing to the genius of modern invention and engineering craftsmanship.

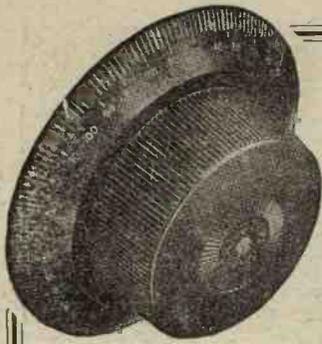Notable examples are provided by Ormond Products, the outcome of 25 years' British Manufacturing Experience.



*Make your Set*  
**Micro-Selective**

**B**E able to get those elusive DX stations readily, clear and loud. Simply replace your dials with Pelican UNIVERNIERS

without otherwise altering your set, or drilling the panel, and then see what a marvellous difference it will make to your tuning.

*It does away with Vernier Condensers*


Buy good plain condensers and fit with Pelican Univernier dials. The Pelican Univernier will make the finest receiver 100% more efficient. The large single knob gives a 12 to 1 reduction. The 12 to 1 ratio is proved the most efficient for selective control.

**Pelican UNIVERNIER complete, 6/-** at your dealer or post paid on receipt of P.O.

**PELL, CAHILL & CO., LTD.**  
64 NEWMAN STREET  
LONDON, W.1

Telephone:  
Museum 9236

Telegrams:  
Pelcarad, Wesdo, London

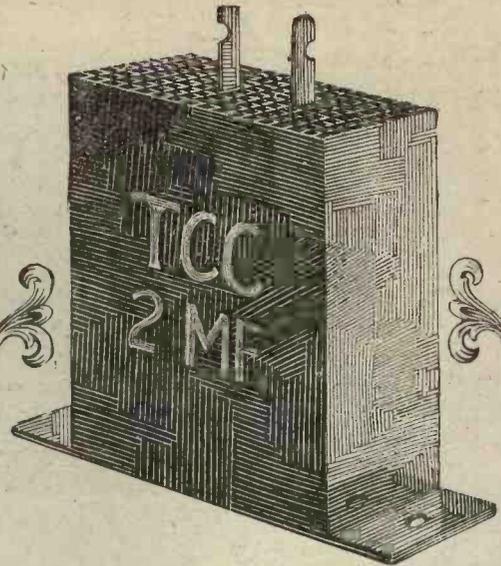

**1905 - 1925**

**F**OR more than twenty years T.C.C. Mansbridge Condensers have been the standard fixed condensers for all electrical requirements. First in telegraphy—afterwards in wireless telegraphy—now in Broadcast reception, their dependability and accuracy have always earned unstinted praise.

Among all your wireless friends you will never have known one who has ever been disappointed with a T.C.C. Mansbridge Condenser. And, after all, this feeling of supreme confidence is a great thing. It means that you can accept a T.C.C. Mansbridge Condenser, place it in the circuit, and know that its capacity is exactly as marked and that it cannot possibly short circuit. The most frequent and rigorous tests that can be devised safeguard both of these points for you.

But not all green condensers are T.C.C., and not all condensers produced to imitate the T.C.C. are of the genuine Mansbridge pattern. In fact, very few of them are. But you are always safe if you see the letters T.C.C. stamped on the side of the case.

**T.C.C.**  
**Mansbridge**  
**Condensers**

In all values from all Dealers

Telegraph Condenser Co. Ltd.  
Mortlake Road, Kew

**Have you entered for the "Sylverex" Radio Crystal Prize Scheme?**

The Competition is simple—you merely put twelve B.B.C. "turns" in order of popularity. And every competitor receives a prize, the chief prizes going to those competitors giving the nearest to the correct list according to total voting; the other competitors all receive Consolation Prizes

Ask your Wireless Dealer for Full Details—or send a Postcard to Sylverex Ltd. (Dept. D), 25, Victoria Street, London, S.W.1

*Sylverex is a natural Crystal and is a revelation in sensitiveness. It is subjected to the fullest tests of any crystal on the market, and as a consequence is fully guaranteed.*



Price  
**2/-**

Entrants for the Sylverex Prize Scheme are asked to write down the following list of "turns" in their order of popularity. Put down first which item you consider most popular; then the item you consider second in popularity, and so on. Write only the items listed here. Prizes will be awarded to those entries most nearly in accordance with the total voting of all competitors

- Covent Garden Opera
- Symphony Orchestra
- The Children's Hour
- The Savoy Bands
- The Wireless Drama
- "Celebrity" Speeches
- Sports Talk
- Humorous Entertainers
- De Groot and Piccadilly Orchestra
- Concert Parties
- "Star" Musicians and Vocalists
- News and Weather Reports

Your list of items must be written on the plain side (back) of the printed directions slip enclosed with each packet of Sylverex Crystal

**£200**  
in Cash Prizes  
1st Prize - £100 Cash  
2nd Prize - £50 Cash  
3rd Prize - £25 Cash  
50 Prizes of 10/- each

Numerous additional prizes, consisting of Valve Sets, Crystal Sets, Loud Speakers, etc., and thousands of Consolation Prizes of copies of popular published songs

**ELECTRADIX RADIOS**

The increasing scope of wireless apparatus has necessitated a wide increase in our already large and comprehensive stock in London. Our new July edition of our famous Catalogue of Radio Bargains now contains 800 illustrations of radio sets, components, and electrical instruments of great interest. Many of these are unobtainable elsewhere and our prices are the very lowest. The experimenter on short waves, the expert transmitter or the crystal novice will all find it advantageous to have a copy of "The CATALOGUE that SAVES YOU POUNDS". Its scope ranges from 5s. pair of British Headphones or a 12s. 6d. Milliammeter to a 30,000 volt Generator, and covers all requirements. If you cannot call and inspect goods in our showrooms between 9 a.m. and 6 p.m. it will pay you to send 4d. for our Catalogue at once. Goods promptly dispatched all over the world.

**LESLIE TIXON & COMPANY,**  
9, Colonial Avenue, Minories, E.1.  
Phone: Avenue 4168. Teleg: (Electradix Ad.)  
Colonial Avenue is the first on left down the Minories from Fenchurch Street or Aldgate Underground Station.

*Barclays Advt.*

Maymore **ELECTRIC SOLDERING IRON** for Wireless Constructors

British made & Guaranteed 6 months

Gives easier, neater and better solder joints than any other method. Small overall diameter allows user to reach all connections. Always keep correct temperature with it without sawing for heating. Consumes no more current than an ordinary lamp.

**10/6**

Post free

Complete with Lamp Adapter. Stock voltages 100/110, 200/220, 230/250. Any other voltage supplied.

**GOODWINS M. A. Ltd.**  
24 Edmund St., Birmingham

**PACENT RADIO ESSENTIALS**

Finest U.S.A. Products  
**EVERY CONSTRUCTOR NEEDS THEM**

<b>RHEOSTAT</b>	4s 10 or 3s	
<b>PLUG</b>	2s	
<b>JACK OPENING</b>	2s 3	<b>DONT</b>
<b>D.C.</b>	2s 9	<b>IMPROVISE</b>
<b>GRID LEAK</b>	1s 6	<b>PACENTISE</b>

DEALERS OR  
**RADIO & ELECTRICAL ACCESSORIES, CO.**  
14, Endwood Court Road, Handsworth, Bham

You cannot get a better **SERVICE**

than that offered by  
**WALTER E. REYNOLDS**  
Wireless Apparatus Manufacturer

4 South Street, Fenton, STAFFS  
ASK FOR QUOTATIONS AND LISTS

TRADE **DECKO** MARK

**BASEBOARD VALVEHOLDER**  
SAFETY SOCKETS. CAP REDUCE TO THE ABSOLUTE MINIMUM.  
OBTAINABLE FROM ALL THE BEST DEALERS.

**A.F. BULGIN & CO.**  
9-11 CURSITOR ST.  
CHANCERY LANE, E.C.4.

PRICE 2/3 EACH IN CARTONS.

**EBONITE BUSHES**

FOR MOUNTING ON WOOD PERFECT INSULATION

Orders under 1/- send 1/4d. postage.

NUMBER 1 2 3 4 5  
Size of Hole 4BA, 2BA, 1/4", 5/16", 3/8"

**DAREX** Price each: 1d, 1d, 1/4d, 2d, 2d.


RADIO Co., Standard Works, Forest Hill, S.E.23.

**COUPON**

Questions and Answers

This Coupon must be accompanied with a 2/6 P. O. and stamped addressed envelope.

"WIRELESS CONSTRUCTOR" Oct. 1925

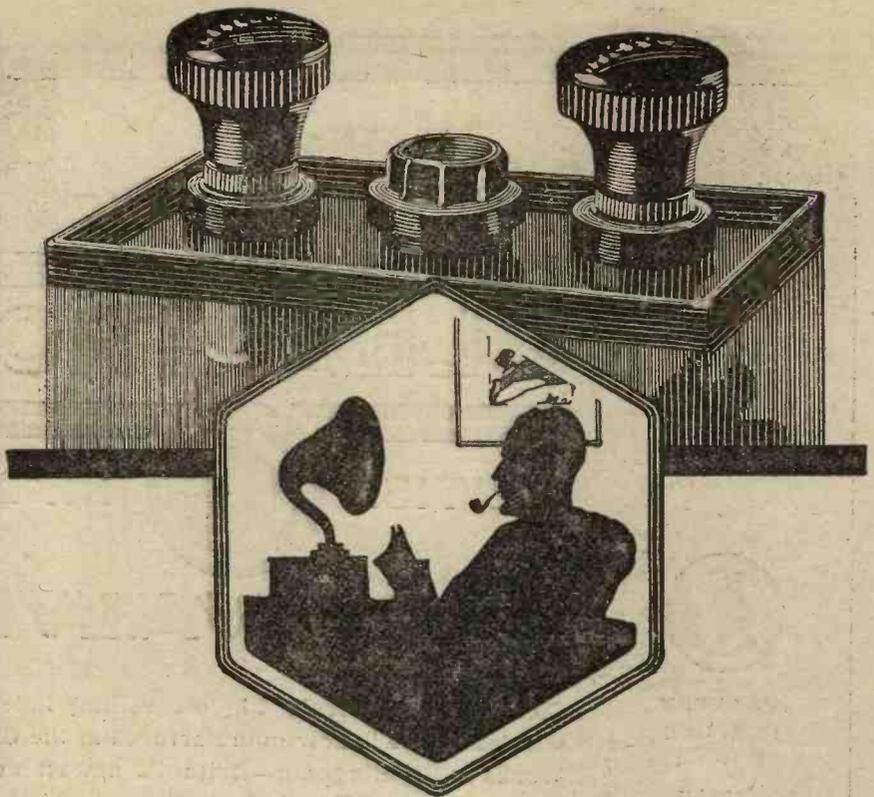

For economy's sake you'll choose this Oldham

A **CHEAP** accumulator is about the most expensive thing you can buy. Not only will it have a short life, but it will require much more frequent recharging. And should it stand idle for any length of time much of its charge will disappear.

Oldham accumulators are built to give long service. Not only does this mean long life—it means also the ability to hold a charge for a much greater period. Their secret of success lies in their plates. All Oldham plates are made under the exclusive Special Activation Process—a method of plate making which automatically guarantees an exceptionally tough plate, capable of readily withstanding sulphation and buckling.

Examine an Oldham at your Dealer's. Note its strong case made from the best celluloid it is possible to obtain. If you have had experience with the leaky, flimsy cases of cheap accumulators you'll be glad to handle an Oldham and to see its immense strength.

You will also observe that its large filler cap screws into the top and that no acid can leak out. Its terminals, too, are of generous diameter, one being red and the other black to indicate polarity.

Altogether this Oldham Accumulator is splendidly made and well worth the moderate price asked for it. Available in a wide range of capacities in 2-volt units at all first-class Wireless Dealers.

**OLDHAM & SONS LTD., DENTON, MANCHESTER**  
London: Hazlitt House, Southampton Buildings, W.C.2  
Glasgow: 120 Wellington Street

Special Activation Process

**OLDHAM**

ACCUMULATORS

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.

*Introducing*

# CLEARTRON

BRITISH  MADE

## RADIO VALVES



AN EVERY  
PURPOSE  
POWER  
VALVE

### C.T. 25

Fl. Volts .....5  
Fl. Current  
0.25 amp.  
Anode Volts 30-150  
Anode Impedance  
10,000  
Amplification  
Factor 9

15/-

FOR  
RESISTANCE  
CAPACITY  
COUPLED  
AMPLIFIER

### C.T. 25B

Fl. Volts .....5  
Fl. Current  
0.25 amp.  
Anode Volts 90-200  
Anode Impedance  
20,000  
Amplification  
Factor 20  
Power Amp.  
Factor 20  
Supplied English or  
American Bases.

15/-

Cleartron—America's biggest selling independent wireless valve is now manufactured at the Cleartron Works in Birmingham—Britain's newest and most recently equipped radio factory.

CLEARTRON VALVES possess UNUSUAL RECEPTION QUALITIES through which they have achieved their great reputation and sale in America.

VASTLY INCREASED VOLUME  
FAR GREATER DISTANCE  
OPERATIC PURITY OF TONE  
KEENER SELECTIVITY

*Sold under an IRONCLAD GUARANTEE*

## POSITIVE PERFORMANCE OR INSTANT REPLACEMENT

Full technical data on request or sample valves sent post free, together with our Ironclad Guarantee, on receipt of remittance and name of nearest Dealer.

## CLEARTRON RADIO LIMITED

1, CHARING CROSS, LONDON, S.W.1

Phones: AND BIRMINGHAM Grams:  
REGENT 2231/2 "CLEARTRON, WESTRAND, LONDON"



AN EVERY  
PURPOSE  
VOLUME  
VALVE

### C.T. 08

Fl. Volts .....3  
Fl. Current  
0.08 amp.  
Anode Volts 30-150  
Anode Impedance  
17,500  
Amplification  
Factor 8.75

12/6

AN EVERY  
PURPOSE  
VOLUME  
VALVE

### C.T. 15

Fl. Volts .....1.8  
Fl. Current  
0.15 amp.  
Anode Volts 30-160  
Anode Impedance  
20,000  
Amplification  
Factor 10

12/6

ALSO  
CLEARTRON  
VALVES FOR  
AMERICAN  
SETS & KITS

### C.T. 199 (Dry Cells)

C.T. 201a  
(Accumulators)

15/- EACH



PLUGS AND JACKS 3/- pair; Dewar Switch 3 way 12 point, 2/8; Mansbridge Condensers, 2 mfd., 2/-; Modulation Transformers, 5/- All Ex-W.D.

Post Free.

A. ROBERTS & CO., 42, Bedford Hill, Balham, S.W.12

TRADE DECKO MARK

**DIAL INDICATORS**

SIMPLY DRILL ONE HOLE AND FIX AT ANY POINT OF DIAL, BEAUTIFUL THE PANEL. OBTAINABLE FROM ALL THE BEST DEALERS.

**A.F. BULGIN & CO.**

9-11 CURSITOR ST., CHANCERY LANE E.C.4.

Price 9/- per pair

The Home for Your Wireless Set!


MORRIS SOLID OAK STANDARD CABINET WITH LOCKS,

to lock up any set and batteries with panel up to 36" x 18"

Sent on approval Trade supplied

Price carriage paid and packing free:  
22" wide inside £4 15  
25" " " £5 0  
36" " " £8 0

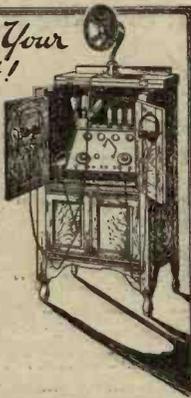MAKERIMPORT CO.  
(Dept. 20)  
54, Lord Street, LIVERPOOL



**SM**  
SUPER PARTS




**SILVER MARSHALL**  
210 and 211 transformers are known as the finest intermediate transformers ever produced. They were an important feature of the receiver built entirely of S-M Parts that won the grand sweepstake prize at the recent American Radio Show. They are also used by experts in the new Super-Autodyne, Laboratory and All-Wave Super-Heterodyne Receivers.

S-M. Kit, consisting of two 210 and one 211, together with one 101 Oscillator Coupler, List Price, £8 18s. 9d.

Send for reprints of articles and our 36pp. Radio Catalogue, enclosing 6d. in stamps to cover cost of postage.

R. A. ROTHERMEL, LTD.,  
24-26, Maddox Street, London, W. 1.  
Telephone: Mayfair 578

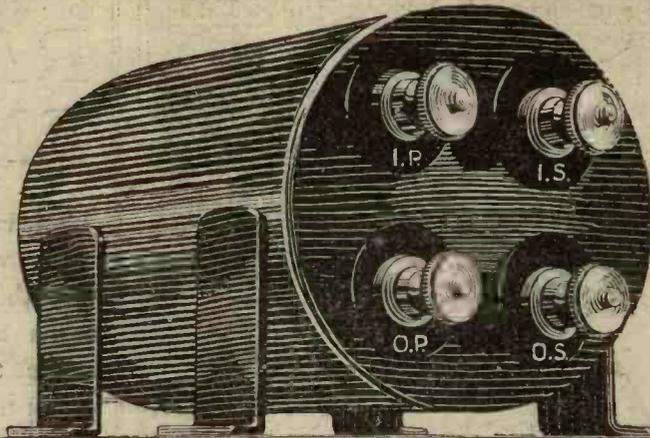Announcement of Portable Utilities Co. Ltd., Fisher St., W.C.1



## Eureka introduces three new models:

FOR the past two years Eureka has been accepted as the finest Transformer that money can buy. It has always been selected by those to whom quality of reproduction is the first essential. Owing to its unique principles of construction and the immense amount of fine copper wire involved, it is of necessity high-priced. As a result, although coveted by every discriminating amateur, not everyone can afford to buy it.

Six months' work in our extensive laboratories has now enabled us to reproduce for the first time in the new Eureka Baby Grand a worthy competitor of the famous Concert Grand. The same quality of workmanship—the same freedom from breakdown—the same high-grade materials—the same purity of tone—still the same Eureka but in a smaller size.

No longer is it necessary for you to accept an inferior substitute because the Concert Grand is beyond your means—choose the Eureka Baby Grand and you are guaranteed the same Eureka standard of quality.

### Everyone can now afford the Eureka

**Eureka Baby Grand. No. 1**  
A new and inexpensive first stage Transformer embodying all the well-proved Eureka principles. Unconditionally guaranteed. Price 15/-.

**Eureka Baby Grand. No. 2**  
Specially designed to follow the Baby Grand No. 1 when two stages of I.f. amplification are wanted. Unconditionally guaranteed. Price 15/-.

**Eureka Reflex Transformer**  
The first Transformer ever to be placed on the market as being specially designed for reflex work. This fine quality instrument will give considerably more volume in a

reflex circuit than any standard transformer. Unconditionally guaranteed. Price 15/-.

**Eureka Concert Grand**


The well-known Eureka Transformer selected by experienced radio engineers for its wonderful amplification with a complete absence of distortion. Unconditionally guaranteed. Price 25/-.

**Eureka No. 2**

Specially designed for use as a second stage transformer with the Concert Grand. Unconditionally guaranteed. Price 21/-.

Don't experiment—specify Eureka

# EUREKA

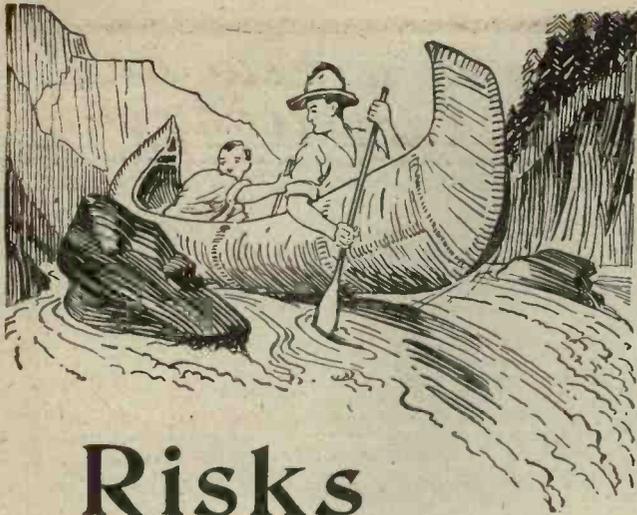

# Risks

**W**HY take risks when buying radio components? A moment's care will mean hours of better reception. Know what you're buying.—For instance—.


The VICTORIA LOW LOSS CONDENSER is an instrument that has merited the expressed approval of radio men all over the country. There is nothing better.

### OBSERVE THESE POINTS OF SUPERIORITY

Fixed and moving vanes designed to give perfect square law reading. Ball bearings. Vanes insulated by ebonite supports outside the electrostatic field. Sturdily constructed, yet presenting a pleasing appearance with highly finished aluminium end plates, nickelled supports and brass vanes. A really first class condenser, particularly ideal for short wavelengths.
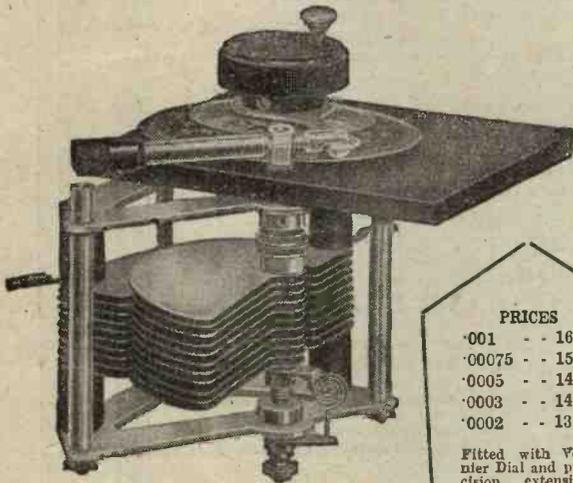
### The VICTORIA VERNIER DIAL

Single Plate Verniers are of the past: the only universally recognised method to-day is a micrometer variation of the whole condenser. You can obtain this by using the "VICTORIA" VERNIER DIAL, which has a ratio of 300 to 1, obtained by a precision screw motion. No gears, therefore no back lash. Coarse and fine tuning provided for. Suitable for use with any standard condenser or variometer. Price 4/3.



For purposes of illustration, section of panel is not shown in correct position.

**W**E said: "Whenever a better condenser is produced the 'Victoria' will make it." Here is one.

PRICES	
·001	- - 16/-
·0075	- - 15/8
·0005	- - 14/9
·0003	- - 14/-
·0002	- - 13/8

Fitted with Vernier Dial and precision extension handle as illustrated! 2/6 extra on prices quoted above From Your Dealer

**VICTORIA ELECTRICAL (Manchester) LTD.**  
 VICTORIA WORKS, OAKFIELD ROAD,  
 ALTRINCHAM, CHESHIRE

# RADIO PRESS ENVELOPES

Each envelope contains complete instructions written by eminent radio experts, and this, together with elaborate illustrations and wiring diagrams, enables the novice to build a set with all the confidence of a practised hand, resulting in complete satisfaction.

No.		Price	Post Free
1	HOW TO BUILD AN ST.100 RECEIVER ... By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	1/6	1/9
2	HOW TO BUILD THE "FAMILY" 4- VALVE RECEIVER ... .. By Percy W. Harris, M.I.R.E.	2/6	2/9
3	HOW TO BUILD THE "SIMPLICITY" 3- VALVE SET ... .. By G. P. Kendall, B.Sc.	2/6	2/9
4	HOW TO BUILD THE ALL-CONCERT DE LUXE RECEIVER ... .. By Percy W. Harris, M.I.R.E.	2/6	2/9
5	HOW TO BUILD THE OMNI RECEIVER By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	2/6	2/9
6	HOW TO BUILD THE ABC WAVE TRAP By G. P. Kendall, B.Sc.	1/6	1/9
7	HOW TO BUILD A 2-VALVE AMPLIFIER DE LUXE ... .. By Herbert K. Simpson.	1/6	1/9
8	HOW TO MAKE A 1-VALVE REFLEX RECEIVER ... .. By Herbert K. Simpson.	1/6	1/9
9	HOW TO BUILD AN EFFICIENT SINGLE- VALVE SET ... .. By Herbert K. Simpson.	1/6	1/9
10	HOW TO MAKE THE TWIN-VALVE LOUD SPEAKER RECEIVER ... .. By John Scott-Taggart, F.Inst.P., A.M.I.E.E.	2/6	2/9
11	AN ADAPTABLE CRYSTAL SET AND HOW TO BUILD IT ... .. By Percy W. Harris, M.I.R.E.	1/6	1/9


All the above can be obtained from Wireless dealers, booksellers, bookstalls, or direct from Dept. W., Radio Press, Ltd.

For prompt and sure delivery when ordering direct from Radio Press, Ltd., please write your name in BLOCK LETTERS.

**RADIO PRESS, LTD.**  
 BUSH HOUSE, STRAND, LONDON, W.C.2
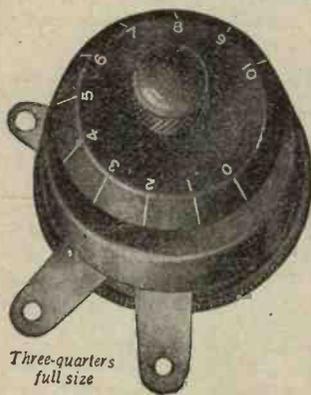
# "FULSTOP" COMPONENTS

In addition to the famous Fulstop Condensers we make the following:



Three-quarters full size



Actual size

## Fulstop Variable Grid Leak.

At last. A variable grid leak that is **CONSTANT** and **ACCURATE** in its performance, as well as in its reading. It is supplied complete with dial graduated from 0 to 10. In addition, it incorporates the famous Fulstop Patents, and is guaranteed to be free from hand-capacity effects.

PRICE 7/6

## Fulstop Fixed Grid Leaks

(1, 2 & 3 megs.)

Patented, and guaranteed to be **ACCURATE** and remain so. The element is an entirely new departure, and has distinct advantages over any other.

PRICE 2/- each

If any difficulty in obtaining, write us and we will send direct, post free.

**J. H. NAYLOR, Ltd., WIGAN**

*Here is a new and better connecting wire!*

"GLAZITE," the coloured connecting wire, marks a new era in the construction of wireless sets. It dispenses entirely with insulating sleeving and gives perfect insulation with a minimum of trouble. The back-of-panel short becomes an impossibility, expensive valves may be saved, and the appearance of the set is enhanced.

Furthermore, "Glazite" is flame-proof and damp-proof. It consists of tinned copper wire, first covered with cotton, and then with a special glazed covering which has exceptional insulating qualities.

The more complicated the circuit the more important it is to use "Glazite" in different colours.

Supplied in four colours—red, blue, yellow and black. 10-ft. coils (1/18 S.W.G.), price 1/2 per coil, 2-ft. lengths (1/16 S.W.G.), 4 lengths in an envelope. assorted colours, price 1/- per packet.



Our mark is a  guarantee of quality

## The LONDON ELECTRIC WIRE CO. AND SMITHS LTD.

(Makers of Electric Wire for over forty years)


Playhouse Yard, Golden Lane, London, E.C.1

Telegrams: "Electric, London."

Telephone: Clerkenwell 1388, 1389, 1390, 1391.



## A Loose Contact

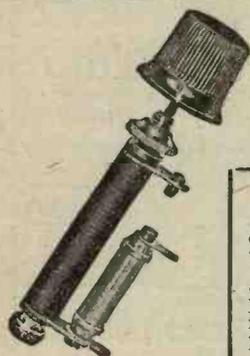

A loose contact in a receiver may give rise to loud crackling noises. The usual carbon compression type of variable grid leak consists of pellets or particles of carbon or impregnated material in more or less loose contact with each other. How can they be expected to be silent or constant in operation?

Only in the "Bretwood" variable grid leak is absolute constancy in action obtained.

The homogeneous mastic employed ensures this. One of the most difficult faults to trace is that arising from a poor grid leak. If you fit a "Bretwood" you just know it's right.

PRICE 3/-

Postage 2d.

With Condenser (as illustrated)

4/6

Postage 3d.

WIRELESS



SPECIALITIES

Obtainable from most Wireless Dealers  
**BRETWOOD LIMITED**  
12-18, London Mews, Maple St., London, W.

Barclays Ad.

**"FAMA" DUTCH VALVES**  
CHEAPEST & BEST

<b>AMPLIFIER</b>	<b>4/6</b>	<b>POWER (DOUBLE GRID)</b>	<b>8/6</b>
Fil. Volts 3-8 to 4 Anode „ 30 to 100 Amps. 0.5 Post Free		Fil. Volts 4 to 6 Anode „ 100 to 250 Post Free Amps. 0.3 The Loud Speaker.	
<b>DETECTOR</b>	<b>4/6</b>	<b>0-06 D.E.</b>	<b>9/6</b>
Fil. Volts 3-8 to 4 Anode „ 20 to 60 Amps. 0.5 Post Free		Fil. Volts 1.8 to 3 Anode „ 20 to 100 Post Free Amps. 0.06 The Dry Cell Valve	

**EXTRA LIBERAL TRADE DISCOUNTS**  
Keenest Quotations to the Trade for all Wireless Components. Write for Price List  
**H. D. ZEALANDER & CO.**  
Phone, Avenue 1482 ST. JOHN'S HOUSE, 124-127, MINORIES, LONDON, E.1

**INSIST UPON**



**H. T. BATTERIES**  
**L. F. TRANSFORMERS**  
and  
**AHEMO HEADPHONES**

**MERCHANTS & AGENCIES Ltd.**

38, Gt. Russell Street, London, W.C.1. Phone: Museum 6634/5

**TWO GOOD THINGS**

**THE RADIAX LOUD SPEAKER**

A British made instrument combining several good points. Perfect in tonal quality, it is extremely sensitive to small power, yet capable of dealing with large volume very successfully. For the moderate price, there is no loudspeaker possessing similar capabilities to compare with the Radiax.

(18 1/2" high with a 10" trumpet)

Permanently Guaranteed PRICE 45/-

**THE RADIAX BABY**

POSSESSES all the features of the RADIAX LOUD SPEAKER and is an instrument that gives best results always.

(12" high)

Permanently Guaranteed PRICE 22/6



—to be seen at the  
**Royal Albert Hall**



**RADIAX LOW LOSS COILS**

If you desire improved tuning, volume and selectivity, insist on Radiax Coils. Each one is engraved with trade mark and size. They are strong, all the turns are bonded together, and they are of reasonable size. Packed in individual containers.

No. 25 1/6 No. 75 2/3 No. 200 4/3  
.. 35 1/9 .. 100 2/9 .. 250 4/9  
.. 50 2/- .. 150 3/- .. 300 5/3

Unmounted coils 9d. each less.  
Set of nine mounted, 27s.

THESE are but two of many equally interesting Radiax Products which you must see or write for full information.



**RADIAX LTD.** 44, RADIO HOUSE  
Tottenham Court Road  
LONDON, W.1

Barclays Ad.

**INSIST UPON SHIPTON'S PRODUCTS AT YOUR DEALERS**

- 7 ohm Rheostat with fuse 3/-
- 30 " " 3/-
- 60 " " 3/-
- Potentiometer 600 ohm 4/6
- Variable gridleak 3/-
- Patent combined aerial & earth switch 3/6



**PRODUCTS**

Don't choose radio components indiscriminately. Buy wisely—Shipton's. Using Shipton Components in your radio receiver, you make certain of best possible results at all times.

Other Shipton Products in preparation

**E. SHIPTON & CO., LTD.**

37 TOTTERDEAN STREET, WESTMINSTER, S.W.1  
Phone: Victoria 8111. Grams: Bentfones, Parl.  
Also at 14, KING ST., COVENT GARDEN, W.C.2


Barclays Ad.

**SOLDERED JOINTS SUPERSEDED!**

You can easily connect up the most complicated set entirely without use of solder, with the

**PATENT**

**"KRISCROS" CONNECTORS**

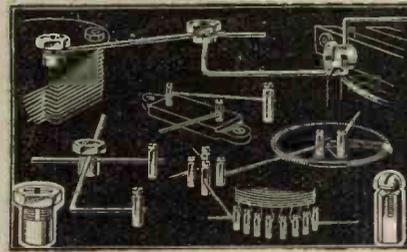


Strong and perfect joints. Used by Mr. Percy W. Harris and other leading experts. A "Kriscros" for every standard thread. No Solder. Prices: 1/6 to 3/- per doz. Send for List.

**Kriscros Co., 50, Gray's Inn Road, W.C.1**

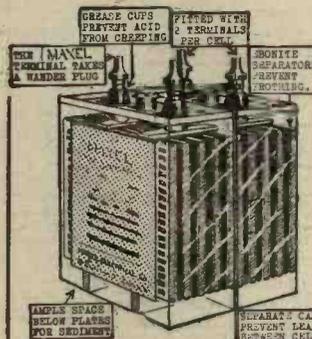**The New MAXEL Accumulator**

Specially designed for Wireless GUARANTEED TWELVE MONTHS.

If you live too far away to call and see the Battery Mail your Order to us for the size you want. We will willingly return your money if you are disappointed.



	AMPS.			
	40	60	80	110
2 VOLT ..	7/6	9/6	11/6	14/-
4 VOLT ..	15/-	18/6	22/-	25/6
6 VOLT ..	22/6	27/-	32/6	37/6

Packing 1/- extra per battery.

60 volt H.T. Batteries 7/6 post free

**MAXEL ELECTRICAL CO.** 28, Clipstone Street, Great Portland Street, W.1

Telephone: MUSEUM 704

**TUNING**

Keen as a Razor!



Successful reception of distant radio demands the utmost tuning accuracy. Every radio enthusiast of experience appreciates this fact which accounts for so many having incorporated the Microhm Vernier Condenser into their receivers. They have proved it to be an instrument capable of sharp and accurate tuning always, with the greatest ease of adjustment. Until you have fitted the Microhm into your set, you cannot know what fine tuning really is. For a negligible outlay you can greatly improve upon present results. Remember it must be the—


**MICROHM VERNIER CONDENSER**

For use in parallel with aerial and anode tuning condensers. Indispensable for "Neutrodynes."

**MICROHM ENGINEERING CO.** VARSITY WORKS, COLLEGE ST., LONDON, E.9  
Phone: CL180LD 2887  
Scottish Agents: KEITH & IRWIN, 35, Robertson Street, Glasgow, G.2

Barclays 1816

# The "4 Point" Condenser

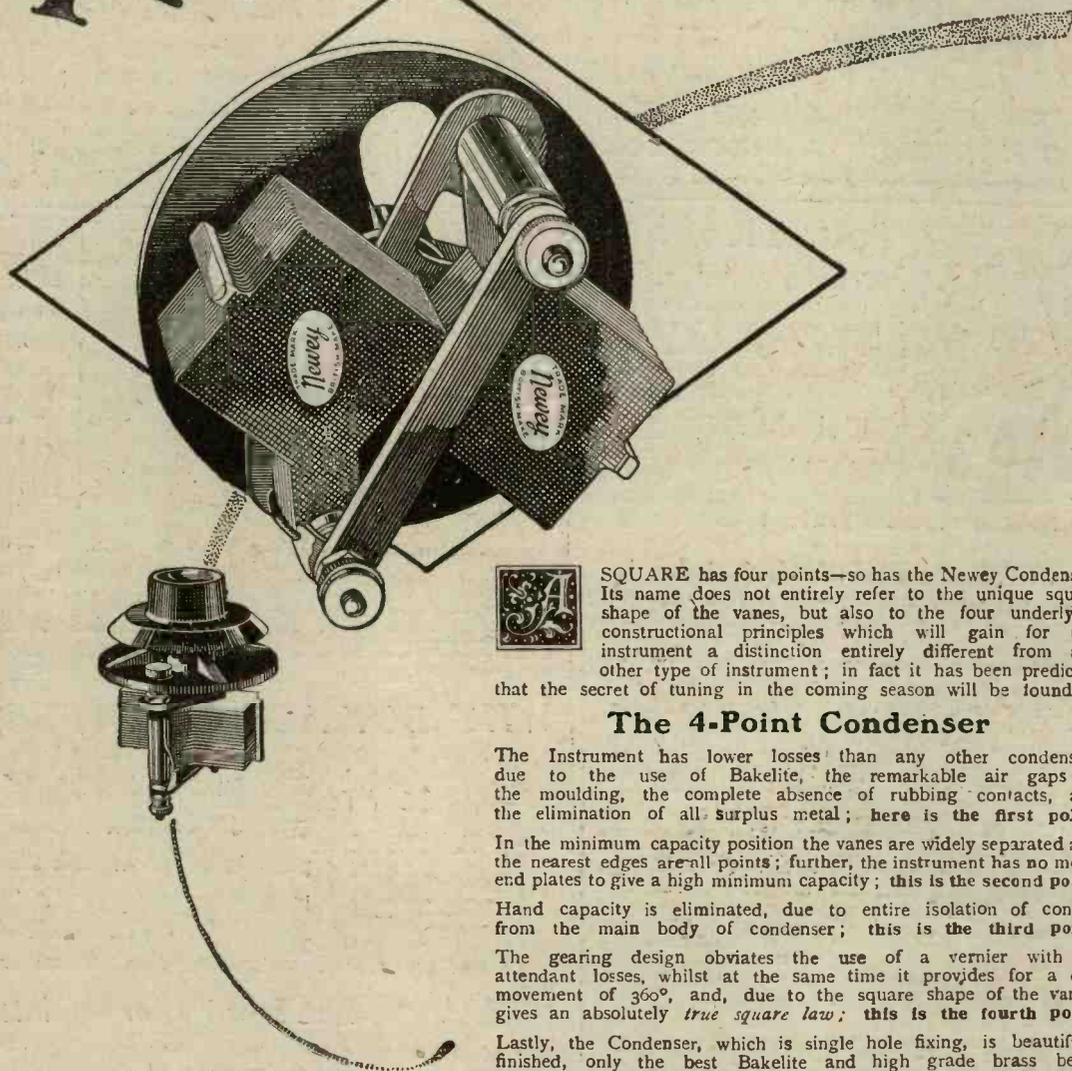

SQUARE has four points—so has the Newey Condenser. Its name does not entirely refer to the unique square shape of the vanes, but also to the four underlying constructional principles which will gain for this instrument a distinction entirely different from any other type of instrument; in fact it has been predicted that the secret of tuning in the coming season will be found in

## The 4-Point Condenser

The Instrument has lower losses than any other condenser, due to the use of Bakelite, the remarkable air gaps in the moulding, the complete absence of rubbing contacts, and the elimination of all surplus metal; **here is the first point.**

In the minimum capacity position the vanes are widely separated and the nearest edges are all points; further, the instrument has no metal end plates to give a high minimum capacity; **this is the second point.**

Hand capacity is eliminated, due to entire isolation of control from the main body of condenser; **this is the third point.**

The gearing design obviates the use of a vernier with its attendant losses, whilst at the same time it provides for a dial movement of 360°, and, due to the square shape of the vanes, gives an absolutely *true square law*; **this is the fourth point.**

Lastly, the Condenser, which is single hole fixing, is beautifully finished, only the best Bakelite and high grade brass being used, and it bears the Newey British Hall Mark of Excellence.



POINT  
CONDENSER

# Newey's

Write for Leaflet W.C. free on application

Sole Distributors: P. & M., Ltd.  
Tooley Street London, S.E.1

USE NEWAY SNAP TERMINALS

# The Bronel Permanent Detector

THE BRONEL PERMANENT DETECTOR IS ABSOLUTELY & DEFINITELY PERMANENT

THERE IS NOTHING TO ADJUST AND IT IS ALWAYS SET



**5/-** Get one! to-day!

FITTED with adjustable screw which gives 1/4" extension, thus allowing it to be fitted to existing clips.

AS used in the Crystal-valve Set described in July issue of *The Wireless Constructor*.

**5 YEARS SOLID GUARANTEE**

From all Wireless Dealers or post free from—

**Wm. R. BOWMAN LTD.**

**47, MARK LANE LONDON, E.C.3**



## You, also, can increase your salary

"After 17 years with a London engineering firm, I was receiving only £4 10s. od. a week, but becoming an I.C.S. student in Civil Engineering, I quickly got an appointment at £1,000 a year, which steadily increased to £2,500!"

Many thousands of such messages from grateful students

have been received by the International Correspondence Schools, the originators of

### SPARE TIME STUDY BY POST

The I.C.S. Diploma is known, valued, respected, in every country. It is an insurance against unemployment, and wins prosperity and happiness for its owners.

SIR HAROLD BOWDEN, MANAGING DIRECTOR OF THE RALEIGH CYCLE CO., LTD., NOTTINGHAM, says:—

"The Diploma of the I.C.S. in the hands of an ambitious man can carry him far, as it has carried thousands. To possess this qualification is proof of a sound, thorough, and specialised education in the subject representing that man's vocation."

The I.C.S. originated spare-time technical training by post 34 years ago, and is by far the largest institution of its kind in the world. It has teaching centres in eleven countries, and students in fifty.

Write to-day for full information as to how the I.C.S. can help you in your chosen vocation. There are 300 I.C.S. Courses, of which the following are the most important groups:—

- |                     |                            |                     |
|---------------------|----------------------------|---------------------|
| Advertising         | Engineering (all branches) | Professional Exams. |
| Architecture        | French and Spanish         | Salesmanship        |
| Building            | General Education          | Showcard Writing    |
| Commercial Art      | Market Gardening           | Textiles            |
| Commercial Training | Plumbing                   | Window Dressing     |
| Draughtsmanship     |                            | Woodworking         |

**International Correspondence Schools, Ltd.,**  
172, International Buildings, Kingsway, London, W.C.2.

**CABINETS CASEWORK CABINETS**

**WRITE AT ONCE** for our illustrated list of 100 varieties of cabinets or radio sets, including many described in "MODERN WIRELESS," "WIRELESS WEEKLY," and "WIRELESS CONSTRUCTOR," etc., or 'phone Clerkenwell 6903.

NAME.....  
ADDRESS.....

Write in Block Letters Please

Cut along here and post in unsealed envelope bearing 1d. stamp,  
**TRADE ENQUIRIES ESPECIALLY INVITED.**

**CARRINGTON MANUFACTURING CO., LTD.**  
18/20, Normans Buildings, Mitchell St., Central St., E.C.1

**The last word in EFFICIENCY and ELEGANCE.**

"Scientific" NON-METALLIC HORNS.

Two of our latest models.

No.	Approx. Ht. Flare	PRICE	Post
508	24" 14"	15/6	1/9
517	— 14"	15/6	1/9

Trade Inquiries Invited.

**SCIENTIFIC SUPPLY STORES,**  
126, NEWINGTON CAUSEWAY, LONDON, S.E.1.

Branches: 80, Newington Causeway, S.E.1; 7, St. George's Circus, S.E.1; 16, Manette St., Charing Cross Rd., W.1; 291, Edgware Rd., W.2; 81, Church Rd., Upper Norwood, S.E.23.

555  
508  
Phone:  
HOP 4177

**NO CURRENT?**

**LIGHT YOUR HOUSE**

**CHARGE BATTERIES**

with

**REGALITE**

Lighting and Charging Plant

**FROM £65**

Complete with Batteries, etc.

**A. E. MORRISON & SON, Gartree Street, LEICESTER**

## WHY BUY ACCUMULATORS?

AVAIL yourself of our real Hire Service. Punctual weekly or fortnightly deliveries of Rotax Wireless Accumulators (Greater London Area) from 2/6 per quarter. If you have your own accumulators, let us maintain them. Always clean, and fully charged. We guarantee satisfaction.

*If you add depreciation to the expense and inconvenience of having your own accumulators unskillfully recharged, & cost you considerably more than our inclusive Hire Service.*

**RADIO DOCTOR AT YOUR SERVICE**

If your set gives poor reception, our Wireless Specialist will call at your house and examine it for a small fee (Greater London Area) and if necessary estimate for repairs or reconstruction.

**RADIO SERVICE CO., 105A, TORRIANO AVENUE, KENTISH TOWN, N.W.5**

### REAL SERVICE—Hire or Maintenance

WRITE FOR FOLDER "Z-9" 'PHONE—NORTH 4161, 4162

## SUPER SETS and ACCURACY

For efficient results, absolute accurate capacity and low loss are essential. You must therefore fit THE

**Dorwood Precision Condensers**

which are guaranteed by our work's laboratory test. The only grid condenser having a three point connection.

The DORWOOD has often been used in sets described in Radio Press publications. This is another guarantee of its efficiency.

**GET DORWOOD PRECISION CONDENSERS** direct from us if your dealer cannot supply at once, post free at list prices as follows:—

**PRICES:**

Capacities '0001 to '0009 MF. with or without Grid Leak Clip	2/6
.. '001 to '006	3/-
.. above '006 to '01	4/8

Sole Manufacturers **HERBERT BOWYER & CO.** 1a, Ralley Mews, Leverton Street, LONDON, N.W.5

**TRADE DECKO MARK**  
 HEAVY GAUGE  
**VALVE WINDOWS**  
 MAKE & FINISH OF THE HIGHEST  
 QUALITY, FOR SETS OF DISTINCTION.  
 OBTAINABLE FROM ALL THE BEST DEALERS.



PRICE 6/- EACH  
 R.P. 7/6 OR BLACK  
 IN PACKETS

**A.F. BULGIN & CO.**  
 9-11 CURSITOR ST.  
 CHANCERY LANE E.C.4.

**"F.A.R." L.F.**  
**F.A.R. Transformer**  
 (SHROUDED)  
**RATIO 5 to 1. 15/-**  
 Of all Dealers or  
**M. BOBIN, 21 Warwick Lane, London, E.C.**  
 Telephone: Central 4872.

**DOMINION TIMBERS**  
 Remarkable success of our special WEMBLEY OFFERS to AMATEUR WOOD WORKERS. The demand has been ENORMOUS, and there are already HUNDREDS of SATISFIED USERS OF


**AUSTRALIAN SILKY OAK**  
 the most wonderful figured wood known. During Wembley we offer this and many other EMPIRE WOODS at GREATLY REDUCED PRICES. Specially selected for WIRELESS BOXES, FRETWORK, and all classes of AMATEUR CABINET WORK. All thicknesses planed ready for use. Guaranteed bone dry and free from knots, etc. Write now for WEMBLEY DISCOUNT LIST, or we will send our useful sample parcel of six different woods (two pieces 9 ins. x 8 ins. and four smaller pieces) in all 1 1/2 sq. ft. for absolute cost price, 1/3 post free. Only one parcel allowed each applicant.

**EMPIRE TIMBER CO. (Dept. B.E.E.)**  
 101, Dewsbury Road, Dollis Hill, N.W.10

**2-VALVE AMPLIFIER, 35/-**  
 1-Valve Amplifier, 20/- both perfect as new; Valves 4/8 each; smart Headphones 7/6 pair; new 4-Volt Accumulator, celluloid case, 13/-; new 40-Volt H.T. Battery, guaranteed 6/-; 2-Valve All-Station Set, £4. Approval willingly

**G. Taylor, 57, Studley Rd., Stockwell, London**

**MOUNTS IN MORE WAYS than any other**

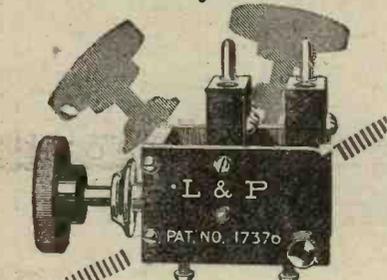

**The L. & P. Universal Vernier Coil Holder**

gives the finest control of coupling ever achieved.

Designed for "one-hole" panel mounting. Easily fitted back or front of panel. The action of the moving coil-holder is on the worm and pinion principle together with a special patented spring which balances the weight of the moving coil.

This combination gives a smoothness and delicacy of control not to be experienced with any other device what-so-ever. Every part of the workmanship is superb. All metal heavily plated. Only PURE ebonyite used - no mouldings.

This device will make all the difference between "getting" a distant station and just missing it.

Do not buy a coil holder of any kind until you have had our list. Mention name of dealer when writing.

**LONDON & PROVINCIAL RADIO COMPANY LTD.,**  
 27, Colne Lane, Colne, Lancs.

**WIRELESS EXHIBITION**  
 ALBERT HALL,  
 SEPT.  
 12 TO 23



**THE FINEST UPHOLSTERY VALUE IN THE WORLD**

**Do let's send for this Charming Suite!**

**T**HE sooner you install Berkeley Upholstery in your home the sooner you will realise that luxurious comfort and rest which make home a haven of joy and peace from the world's troubles.

Handsome in appearance, so soundly constructed that it will last for years, Berkeley Upholstery is unrivalled for value and has gained a reputation for comfort and reliability which time steadily increases.

**Specification & Construction of Berkeley Upholstery**

**FRAME:** Made from specially selected well-seasoned birch, all joints perfectly dowelled and fitted. **SPRINGS:** Made in our own Works from the finest steel-copper rustless wire, which retain their resiliency after years of constant use. **WEBBING:** Best Scotch make that has been tested up to an enormous strain before use. **UPHOLSTERY:** By our system the whole of the springs in the seat, back and front edge are entirely free in action, with the result that they respond to every movement of the body, thus assuring complete comfort and repose. Finest fibre stuffing. **COVERING:** Tapestries, cretonnes, etc., of your own selection.



*Any piece of the Berkeley Lounge Suite supplied separately if desired.*

**The Berkeley Chesterfield**

is a handsome lounge with an adjustable let down end. This adjustable end is absolutely reliable and its strength is such that when extended it can be used as an extra seat. Extreme length with end let down, 6ft.

**CASH PRICE**

**£10** or 30/- with order and 6 payments of 30/- monthly.

**The Berkeley Wing Model**

has large well-upholstered wings and is higher in the back than the Berkeley giving extra comfort and protection from draughts.

**CASH PRICE**

**£5** or 15/- with order and 6 payments of 15/- monthly.

**The Berkeley**

has the largest sale of any Easy Chair in the world.

**CASH PRICE**

**85/-** or 15/- with order and 5 payments of 15/- monthly.

**WRITE TO-DAY for Patterns of Coverings POST FREE**

The **Berkeley** Regd. **LOUNGE SUITE**

Comprises: Berkeley Chesterfield, Berkeley Wing Model and the famous Berkeley Easy Chair.

**GUARANTEE** — Sold on the Money-Back Principle Delivered Free in England and Wales (Scotland extra)

**H. J. SEARLE & SON, LTD.,**  
 (Dept. WC) 70-78, OLD KENT RD., LONDON, S.E.1  
 Showrooms: 133, Victoria Street, Westminster, London, S.W.1 and THE ARCADE, CROYDON.



Cash Price for Complete Suite

**£18:10:0**

or 19:10:0 50/- with order & balance 50/- m'thy

# 3/4 an Ounce!

approximately is what you pay for GENERAL RADIOPHONES.

If you are buying weight, they are the most expensive you can buy.

If you are buying result, they are easily the cheapest. Which do you want—a pound of dissatisfaction or seven ounces of sensitivity?

Do you want a sore head—or comfort? Sore ears — or Matched tone? Any Phone — or **GENERAL RADIOPHONES**



They carry the General Radio Guarantee.

Price 20/-


**"THE BIG THREE"**  
FAMOUS FOR EFFICIENCY

*General Radio*

**"GENERAL RADIO" ON A BROADCAST RECEIVER OR COMPONENT MEANS THAT IT IS GUARANTEED TO GIVE PERFECT SATISFACTION.**

**GENERAL RADIO COMPANY LIMITED**  
RADIO HOUSE, 335, REGENT ST., LONDON, W. 1
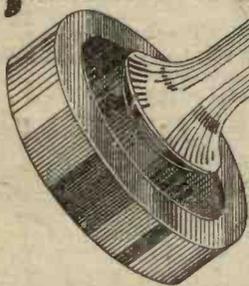
## just a ball, a metal plate — and no cats-whisker —



Abolish your Crystal and cats-whisker and adopt this trouble-free method of detection. Not a permanent detector, but a readily adjustable one, with a zinc ball making contact with a smooth plate coated with mineral compounds.

—and the volume of pure production is extraordinary

Kathoxyd consists of a smooth metal plate in a brass mount, which fits your Crystal cup. It is supplied with two contacts—one a ball of zinc iron, for local-station use, the other a fine graphite point for long-distance work. Each contact is readily fixed, in place of your ordinary catswhisker.


## METAL PLATE Kathoxyd RADIO DETECTOR CRYSTAL

Supplied in sealed boxes, containing one Kathoxyd Element, one Ball Contact and one Long-distance Contact ... Price **1/6**

From all Wireless Dealers.  
Wholesale from all reputable Factors. All enquiries welcomed by:—  
**KATHOXYD, LTD., 41, High Holborn, London, W.C. 1.**

If unobtainable locally, send 2/6 when the Crystal will be sent by return post. Visit us at the Albert Hall Exhibition, our Stand being situated in the Gallery, and is No. G7.
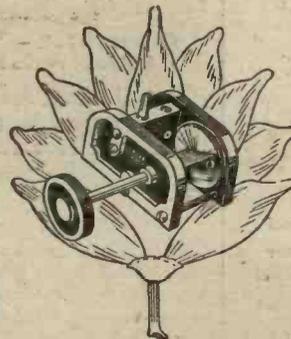
## FIT THE "LOTUS" COIL-HOLDER and Realise What Perfect Reception means




THE "LOTUS" cut geared Vernier Coil-Holders are fitted with Vernier movement actuated by three sets of encased precision cut gears representing a reduction of 8 to 1.

**MOVING BLOCK CANNOT FALL**

Made from Bake-lite Mouldings with Nickel-Plated Parts

Retail Selling Prices:

Two-Way - 7/-  
Three-Way 10/6

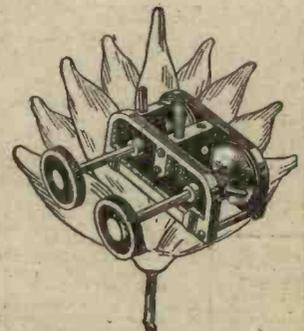

**GARNETT, WHITELEY & CO., LTD.**  
Lotus Works, Broadgreen Road - LIVERPOOL

— ANNOUNCEMENT —

# A New Wireless Loud speaker

A NEW invention of the Western Electric Company that will be placed on the market on October 1st, 1925.

The "Kone" Loud Speaker, as its name implies, has been evolved by the Scientific application of two cones, with the result that absolutely faithful reproduction is assured of every musical note, and complete freedom from the objectionable guttural tones associated with most Loud Speakers of the horn type.

*ORDER YOURS NOW AND SAVE DISAPPOINTMENT.*


**Western Electric Company Limited,**  
CONNAUGHT HOUSE, ALDWYCH, LONDON.

*Central 7345 (10 lines).*


WORKS: North Woolwich, New Southgate, Bexley Heath, Hendon. BRANCHES: Glasgow, Leeds, Birmingham, Manchester, Newcastle, Cardiff, Southampton, Liverpool, Dublin, etc.



SIDE VIEW.

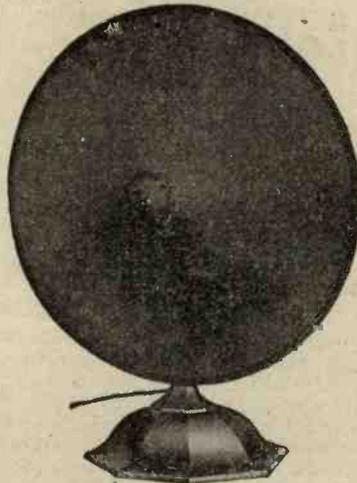

FACE VIEW.

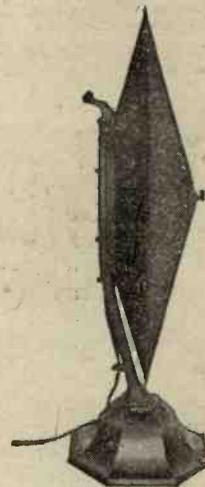


SIDE VIEW.

## Western Electric KONE LOUD SPEAKER



PRICE £6 - 6 - 0

*Unrivalled  
Tone.*

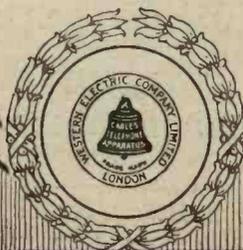

*Perfect  
Reproduction*

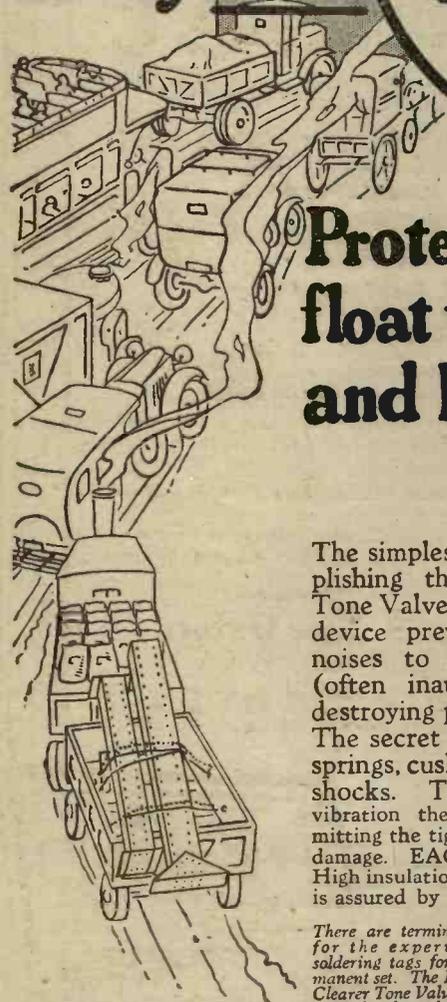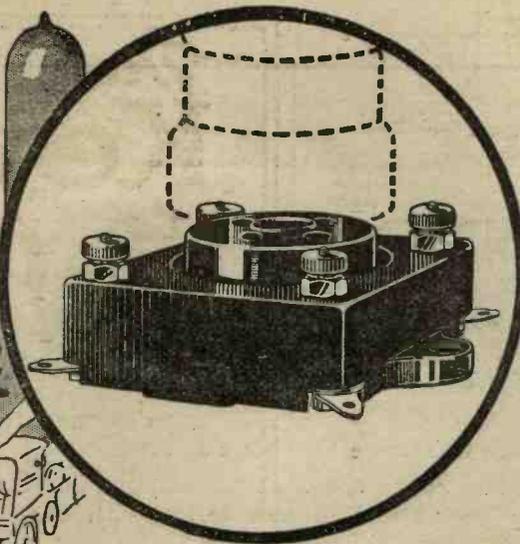**Vibration-distant shocks - they are always here**



**Protect your valves - float them on springs and kill noise in the filament!**

The simplest, most efficient method of accomplishing this is to use a Benjamin Clearer Tone Valve Holder. This new shock-absorbing device prevents the transmission of outside noises to the filament. Outside vibrations (often inaudible to the ear, yet invariably destroying pure tone) are completely dissipated. The secret lies in the four delicately adjusted springs, cushioning the valve against all external shocks. Though responding to the slightest vibration these springs are immeasurably strong, permitting the tightest valve to be inserted without fear of damage. **EACH SPRING HAS ONE TURN ONLY.** High insulation, low capacity and great mechanical strength is assured by using Bakelite for the body of the holder.

There are terminal connections for the experimenter and soldering tags for the permanent set. The Benjamin Clearer Tone Valve Holder is easily cleaned—little or no dust can collect in the sockets.

The springs themselves, as shown in the lower of the two diagrams, form the valve pin sockets. No soldered


joints—all one solid metal piece from tag to valve leg. No flexible wire connections. The spring supports are not affected by stiff bus bar wiring. For Good Reception with Dull Emitter Valves Benjamin Clearer Tone Anti-Microphonic Valve Holders are absolutely essential.

**2/9**  
Each.

Sectional View of Holder



Detail of Spring Feature

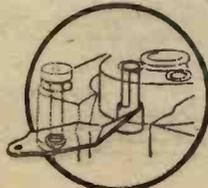

**BRITISH BENJAMIN MADE CLEARER TONE VALVE HOLDER**

Patents (ANTI-MICROPHONIC) Pending

From your Dealer or direct from:

**THE BENJAMIN ELECTRIC LIMITED**  
Brantwood Works, Tariff Road, Tottenham, N.17.

The Benjamin Battery Switch gives perfect current control, 2/- each.

**Buy Experience**

Radio Press Books are the condensed experience of many years' research, written by experts in a manner that brings complete satisfaction. They are comprehensive in the variety of subjects covered, as a glance below will tell.

**RADIO PRESS BOOKS**

	Post	Price.	Free.
	9d.	11d.	
1 Wireless for All ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>			
2 Simplified Wireless ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>	1/-	1/2	
3 How to Make Your Own Broadcast Receiver ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>	1/6	1/8	
4 How to Erect your Wireless Aerial ... <i>By E. Mittell, A.M.I.E.E.</i>	1/-	1/2	
5 The Construction of Wireless Receiving Apparatus ... <i>By P. D. Myers</i>	1/6	1/8	
6 The Construction of Crystal Receivers ... <i>By Alan L. M. Douglas</i>	1/6	1/8	
7 How to Make a "Unit" Wireless Receiver ... <i>By E. Redpath</i>	2/6	2/8	
8 Pictorial Wireless Circuits ... <i>By Oswald J. Rankin</i>	1/6	1/8	
9 Wireless Valves Simply Explained ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>	2/6	2/8	
10 Practical Wireless Valve Circuits ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>	2/6	2/8	
12 Radio Valves and How to Use Them ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>	2/6	2/8	
13 500 Wireless Questions Answered ... <i>By G. P. Kendall, B.Sc., and E. Redpath</i>	2/6	2/8	
14 12 Tested Wireless Sets ... <i>By Percy W. Harris, M.I.R.E.</i>	2/0	2/8	
15 More Practical Valve Circuits ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>	3/6	3/10	
16 Home-Built Wireless Components	2/6	2/8	
17 Wireless Sets for Home Constructors ... <i>By E. Redpath</i>	2/6	2/8	
18 Tuning Coils and How to Wind Them ... <i>By G. P. Kendall, B.Sc.</i>	1/8	1/8	
21 Six Simple Sets ... <i>By Stanley G. Rattee, M.I.R.E.</i>	1/6	1/8	
22 Switches in Wireless Circuits ... <i>By Oswald J. Rankin</i>	1/6	1/8	
24 Wireless Faults and How to Find Them ... <i>By R. W. Hallows, M.A.</i>	1/6	1/3	
Elementary Text Book on Wireless Vacuum Tubes ... <i>By John Scott-Taggart, F.Inst.P., A.M.I.E.E.</i>	10/-	10/6	
Radio Engineering ... <i>By J. H. Keyner, B.Sc. (Hons.), A.C.G.I., D.I.C.</i>	15/-	15/9	

Radio Press Books are obtainable from all Bookstalls, Newsagents, your local Wireless Dealer, or direct from Dept. W., Radio Press, Ltd. For prompt and sure delivery when ordering direct from Radio Press, Ltd., please write your name and address in **BLOCK LETTERS**


**RADIO PRESS, LTD.**  
Bush House, Strand, London, W.C.2

Barclays Ad.

TWO NEW

# UTILITY

COMPONENTS

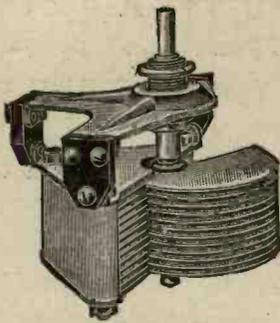

## THE UTILITY VALVE-SWITCH UNIT

This component, which combines a switch, rheostat, and a low-loss valve holder, enables a valve to be switched in or out of action whilst at the same time preserving absolute continuity of the circuit. The filament can be controlled as usual with the rheostat, the valve being switched on and off by means of the switch. It is one-hole fixing and is fitted with an engraved dial showing ON and OFF positions.

Price 8/6

## THE UTILITY LOW-LOSS CONDENSER

This instrument has been designed to meet the demand for a condenser that is really low loss. One end plate has been dispensed with and all insulation has been placed outside the electro-static field.

The bearing of the Centre Spindle is of unusual length and "end play" has been entirely eliminated. The condenser is fitted with a dust cover and is one-hole fixing.


## THE UTILITY VERNIER DIAL

Designed especially for use with the above condenser on a new geared principle which gives both direct and Vernier adjustment, with a reduction ratio of 50 to 1. Backlash has been entirely eliminated.

Prices of the "Utility" Low Loss Condenser.

Capacity	Ref. No.	Price
.001	W. 159	14/6
.002	W. 160	12/6
.003	W. 161	10/6
.0025	W. 162	9/6
.002	W. 163	9/-

Vernier Adjustment 5/- extra.

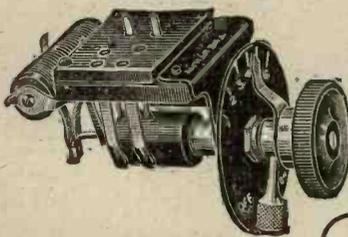

**WILKINS & WRIGHT, UTILITY WORKS**  
KENYON STREET - BIRMINGHAM

Telephone: Central 2334.

Telegraphic Address: "Utility, B'gham."

Barclays Ad.

# Radion Valve Prices are still the lowest

For Guaranteed British — Made Valves.

If you have any difficulty in being served, don't be "put off." We will be pleased to give your orders prompt attention.



FREE!

This book, free on request, gives useful information and curves of RADION VALVES. Write to-day.

## Radion D.E. '06

A wonderful, efficient 3-volt "very dull" filament valve.

In two types: H.F. & L.F.

## Radion D.E. '34

A 2-volt dull emitter of fine performance.

In two types: H.F. & L.F.

## Radion G.P.

A 4-volt bright valve that only consumes '48 amp.

## Radion Pyramid

(1) Valve The power

Valve do

lux. Can be used with largest loud speaker

without valve distortion. Filament robust;

works at low temperature, ensuring long life

Special construction gives highest efficiency

and mechanical strength. Fil. volts 5.5; Fil.

amps. 34; Anode volts 50-100; Neg. Grid-

Bias 3.9. Also supplied with 4 v. fil. if desired.

From United Dealers or Direct Post Free.

Don't let any dealer try to sell you something

dearer. There are no better valves; our curves

PROVE IT. Buy RADIONS and save money.

## New VALVE REPAIR Prices

We are the only British firm of valve manu-

facturers who will repair valves for you. (We

can successfully repair practically every make.)

## BRIGHT EMITTERS 5/-

## DULL EMITTERS 7/6

from service dealers or post free from us.

Power valves at half the cost of British stand-

ard current prices for the same type when new.



**RADIONS LTD., BOLLINGTON, Near MACCLESFIELD**

# The Key to your Crystal Set

The name denotes its work

Start the season well with a

# DETEX Crystal

A "DETEX" detects even the faintest signals which you never hear at all with ordinary crystals.

A genuine testimony—of which we receive many.

"Since I purchased a 'DETEX' Crystal I have put it to most rigorous tests with really wonderful results. In fact the 'DETEX' is the best crystal I have ever tested."

C. R. Taylor, B.Sc. Eng., A.M.I.Mech.E.

Obtainable from all radio dealers—or send P.O. for 1/6 (post free) for this product of science and nature.

Sole Producers:

**DETEX, 59, New Oxford Street LONDON, W.C.1**

**CAUTION** Be sure you get genuine "DETEX" in the scientific rod transparent box and that the gold seal is unbroken.

# 1/6 EACH

of all the best radio dealers

WHOLESALE AGENTS:

London:

Houghtons, Ltd., Ensign House, 83/9, High Holborn; Sun Electrical Co., Ltd., 118, Charing Cross Road; Manufacturers Accessories Co., Ltd., 86, Great Eastern Street; Brown Brothers Ltd., 22, Gt. Eastern Street, London, E.C.2 and Associated Companies.

Birmingham, Northampton and Leicester: Cooke & Whitfield Wireless, Ltd., 24, St. Paul's Sq., Birmingham.

Manchester: Garnett's, Islington Grove Works, Salford.


Leeds: Ellison & Hillman, 123, Albion Street.

Bradford: Thos. Dyson, 79, Manchester Road.

Newcastle-on-Tyne: Steven, Ltd., 67, Newgate Street.

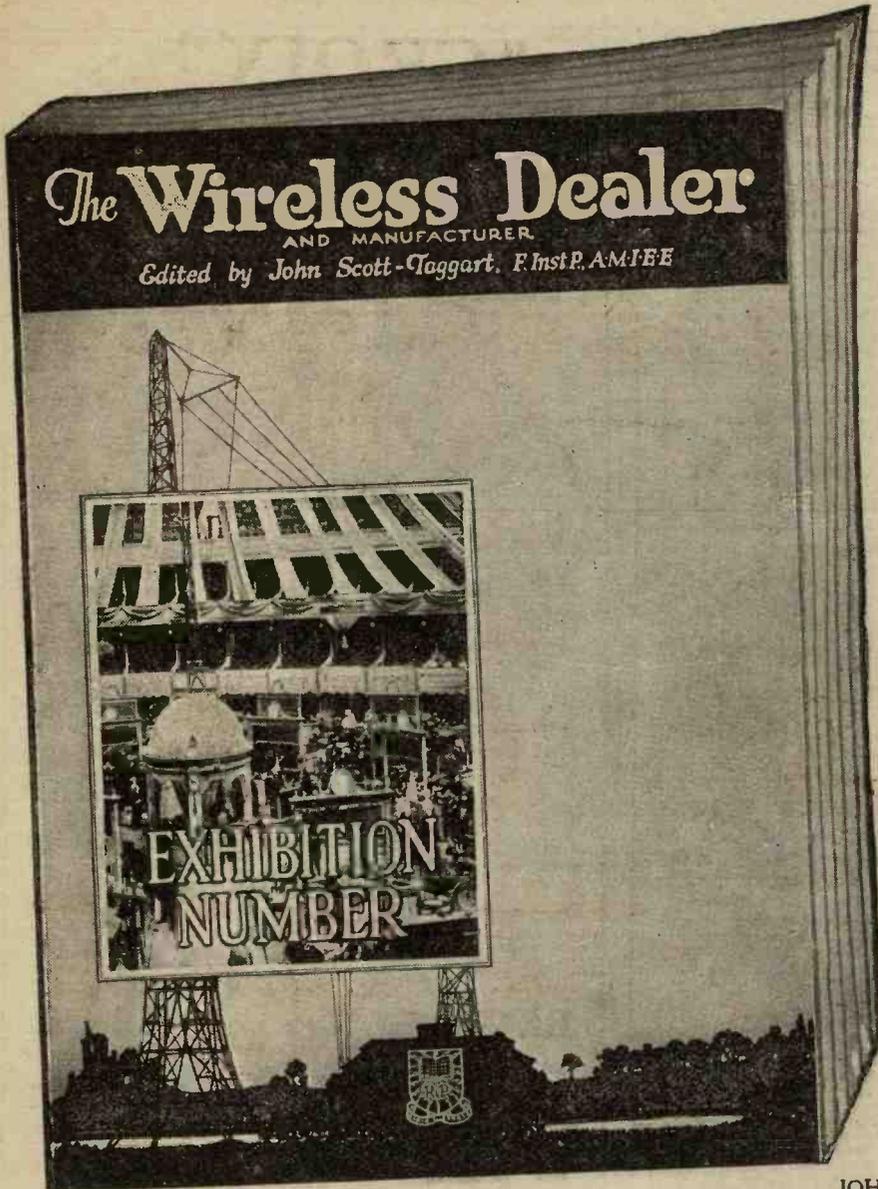Sheffield: Sheffield Radio, 30, Trippet Lane.





# NO. 1 EXHIBITION NUMBER

Just /  
Published  
!

Send your  
Subscription  
Now for

## The WIRELESS DEALER

and MANUFACTURER

EDITED BY

JOHN SCOTT-TAGGART, M.C., F.Inst.P., A.M.I.E.E.

**T**HE first number of this new Radio Press Trade Monthly appears at a time when sales interest is intense and will prove of exceptional value to retailer and manufacturer. Reports issued from the new Radio Press Test Laboratories, under the supervision of Major James Robinson, D.Sc., Ph.D., F.Inst., and published in "THE WIRELESS DEALER," give the radio retailer valuable information as to what is likely to be demanded by the public.

To be up to the times and abreast of all new developments in radio, you must be a subscriber to "THE WIRELESS DEALER." Copies can only be obtained by entering a subscription. It is not available to the public, and therefore not on sale at Bookstalls.

Kindly complete the form below, and post, together with remittance of 7/6 (10/- abroad) ensuring the receipt of copies for twelve months from No. 1.

### SUBSCRIPTION ORDER FORM

To RADIO PRESS, LTD., Sales Dept.  
Bush House, Strand, London, W.C.2.

Please enter my name for a twelve month's subscription to "THE WIRELESS DEALER" commencing with No. 1, September 12th, 1925. Enclosed is remittance of 7/6 (10/- abroad).

NAME.....

ADDRESS .....



# DON'T BLAME THE SET!



Nine times out of ten there is a fault in the circuit which can be put right in a minute or two with the aid of FLUXITE.

Solder all joints with FLUXITE, and they cease to be joints, but become one unbroken piece of metal. No chance of leakage there!

It's so easy, too. A child could do it. No wireless enthusiast should dream of making joints any other way.

Ask your Ironmonger or Hardware Dealer to show you the neat little

## FLUXITE SOLDERING SET

It is perfectly simple to use, and will last for years in constant use. It contains a special "small space" Soldering Iron with non-heating metal handle, a Pocket Blow-lamp, FLUXITE, solder, etc., and full instructions. Price 7/6. Write to us should you be unable to obtain it.

Price 7/6



## FLUXITE SIMPLIFIES SOLDERING

All Hardware and Ironmongery Stores sell FLUXITE in tins, price 8d., 1/4 & 2 8.

Buy a Tin To-day!  
FLUXITE, LTD. (Dept. 330), West Lane Works, Rotherhithe, S.E.15

ANOTHER USE FOR FLUXITE  
Hardening Tools & Case Hardening  
ASK FOR LEAFLET on improved methods



## "WE HAVE FOUND NO OTHER UNIT IN EUROPE"

E.M.C. Filament Dimmer.  
0.5 ohms 3/4    0.20 ohms 4/-  
0.10 ohms 3/6    0.30 ohms 4/3

E.M.C. Grid Leak.  
2.5 Meg. 3/6    5-10 Meg. 4/-  
Recommended by P.W.  
for Unidyne Circuits.

E.M.C. Special Anode Resistance for Super-Selective Circuit.—5,000-15,000 ohms 4/-  
Spare Cartridges, 1/6 each.  
New York City, May 16, 1925.

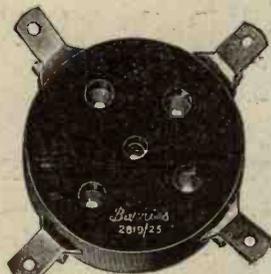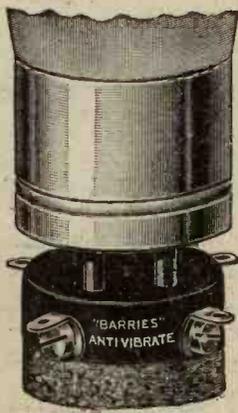American Inventors say:  
"We wish to compliment you upon the design of your variable resistance unit for use in the Filter Tuner or Super-Selective Circuit, as it has been called in England. Smooth and delicate control is essential in this important part of the circuit, and we have found no other unit in Europe which performs this function so well."  
(Signed) PAUL MCGINNIS,  
J. F. J. MAHER.



BARRIE'S ANTI-VIBRATE VALVE-HOLDER, 1/6 each.

BARRIE'S LOW CAPACITY VALVE-HOLDER, 1/3 each.

Write at once for Leaflet No. 84.

ENTERPRISE MANUFACTURING Co., Ltd.

Electric House, Grape Street, London, W.C.2

# "CROIX"


The World's greatest  
**TRANSFORMERS**  
over 500,000 in use



one year's guarantee

RATIO 5/1  
9/6

RATIO 5/1  
9/6

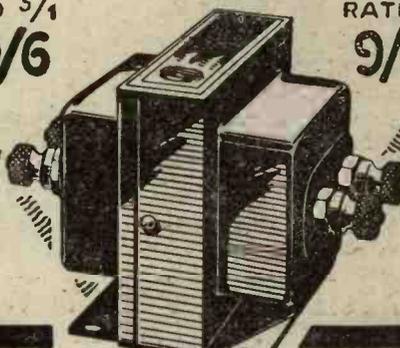

an opinion.

POPULAR WIRELESS, of May 9th, said:

"The 'Croix' Transformers are excellently made little components, and on test they behaved exceptionally well and much better than we should have expected in view of the low price at which they are sold—9/6 each. Amplification was good and distortion not appreciable throughout the whole range of audible frequencies."

The GLASGOW WEEKLY HERALD, March 7th, said:

"The 'Croix' Transformer gave good, undistorted amplification and has satisfied every test."

### WARNING—"Croix" Transformers

This is to give notice that genuine "Croix" Transformers will in future be boxed in white boxes, with the Trade Mark "Croix" stamped in black and gold on each end, and will be numbered individually. No other Transformers are genuine or are guaranteed by us, and the Trade and Public are warned against them.

FROM ALL WIRELESS DEALERS.

SOLE DISTRIBUTORS, United Kingdom:

THE WHOLESALE WIRELESS CO.

103, FARRINGDON ROAD, LONDON, E.C.

Colonies and Dominions:

A. VANDAM, CAXTON HOUSE,  
WESTMINSTER LONDON, S.W.



JOHN SCOTT-TAGGART, M.C.  
F. Inst. P., A.M.I.E.E.  
(Editor-in-Chief of all Radio Press  
Publications.)

---

---

# “WIRE

## THE ONE

---

---

*No. 1 Out Today!*


Editor: PERCY W. HARRIS, M.I.R.E.

Technical Director: JOHN SCOTT-TAGGART, M.C.,  
F.INST.P., A.M.I.E.E.

Research Editor: MAJOR JAMES ROBINSON, D.Sc.,  
PH.D., F.INST.P.

The great new Radio Press weekly is now on sale. 400,000 copies have been printed to meet a phenomenal demand. They will soon go! To avoid disappointment buy your copy early.

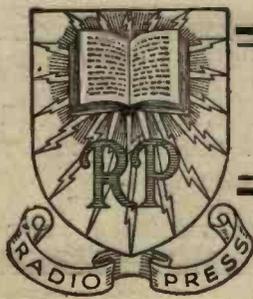The Advertising Campaign for “WIRELESS” includes a whole page in the “Daily Mail” and pages in different other publications.



---

---

# BUY YOUR

---

---

RADIO PRESS LIMITED, BUSH

# LESS"

## WORD WEEKLY



PERCY W. HARRIS, M.I.R.E.  
(Editorial Manager of Radio Press, Ltd.)

# 2<sup>d</sup>. AT ALL Bookstalls

### ARTICLES IN No. 1 BY :—

Percy W. Harris, M.I.R.E. (On American and British Receiver designs compared.)

John Scott-Taggart, M.C., F.Inst.P., A.M.I.E.E. (A New ST. 100 Receiver.)

Major James Robinson, D.Sc., Ph.D., F.Inst.P.

Capt. H. L. Crowther, M.Sc.

R. W. Hallows, M.A.

J. H. Reyner, B.Sc. (Hons.),  
A.C.G.I., D.I.C.

G. P. Kendall, B.Sc.

E. H. Chapman, M.A., D.Sc.

A. D. Cowper, M.Sc.

D. J. S. Hartt, B.Sc.

A. Johnson-Randall.

John W. Barber.

Stanley G. Rattee, M.I.R.E.

C. P. Allinson.

and certain eminent authors whose names we do not at this stage desire to disclose.

# COPY TO-DAY

## HOUSE, STRAND, LONDON, W.C.2



Index to Advertisers

	PAGE		PAGE		PAGE
American Hard Rubber Co. ...	1119	Electron Co., Ltd. ...	1118	Newey Bros., Ltd. ...	1129
Ashley Wireless Telephone Co. ...	1115	Empire Timber Co. ...	1131	Oldham Accumulators ...	1125
Autoveyors, Ltd. ...	1063	Engineering Supplies ...	1067	Ormond Engineering Co. ...	1121
Beard and Fitch, Ltd. ...	1063	Enterprise Mfg. Co., Ltd. ...	1137	Pell, Cahill and Co. ...	1122
Belling and Lee ...	1105	Falk, Stadelmann and Co. ...	Cover iii	Peto-Scott Co. ...	1120
Benjamin Electric, Ltd. ...	1134	Fluxite ...	1137	Philips Lamps, Ltd. ...	1105
Bobin (M.) ...	1131	Forno Co. ...	1067	Portable Utilities Co., Ltd. ...	1125
Bowman (Wm.), Ltd. ...	1130	Gambrell Bros. ...	1068	Power Equipment Co., Ltd. ...	1071
Bowyer-Lowe Co. ...	1090	Garnett, Whiteley and Co. ...	1132	Radio and Elec. Accessories Co. ...	1123
Bowyer & Co. (H.) ...	1130	General Electric Co., Ltd. ...	1085, 1107	Radio Instruments, Ltd. ...	Cover iv
Brandes, Ltd. ...	1060	General Radio Co. ...	1132	Radio Stocks ...	1140
Bretwood, Ltd. ...	1127	Gent and Co. ...	1140	Radions, Ltd. ...	1135
Brighton Radio Stores ...	1113	Gilray Radio Co. ...	1118	Radiax, Ltd. ...	1128
British L. M. Ericsson Mfg. Co., Ltd. ...	1119	Goodwin's Motor Agency ...	1123	Raymond (K.) ...	1102, 1103
B.T.-H. Co., Ltd. ...	1099	Goswell Engineering Co. ...	1111	Real Service Co. ...	1130
Brown (S. G.), Ltd. ...	1082	Graham (A.) and Co. ...	1100	Reynolds (Walter E.) ...	1123
Bulgin (A. F.) and Co. ...	1123, 1125, 1131	Harlie Bros. ...	1113	Rosen (Ed.) and Co. ...	1110
Burndept, Ltd. ...	1064	Igranic Electric Co. ...	1079	Rothermel (R.A.) ...	1125
Burne-Jones and Co. ...	1100	International Correspondence Sch. ...	1130	Scientific Supply Stores ...	1130
Burwood-Concessionaires ...	1118	Jackson Brothers ...	1109	Searle (H. J.) and Son ...	1131
Carrington Mfg. Co. ...	1130	Kathoxyd ...	1132	"Sel-Ezi" Wireless Co. ...	1107
Clarke (H.) and Co. ...	1045, 1117	Kriscross Co. ...	1128	Service Radio Co., Ltd. ...	1115
Cleartron Radio, Ltd. ...	1124	Lissen, Ltd. ...	1059	Shipton (E.) and Co., Ltd. ...	1128
Climax Patents, Ltd. ...	1108	London and Provincial Radio Co., Ltd. ...	1131	Smith (S.) and Sons (M.A.), Ltd. ...	1111
Collinson's Precision Screw Co., Ltd. ...	1113	London Elec. Wire Co. ...	1127	Sterling Telephone & Elec. Co., Ltd. ...	1046
Cossor (A. C.), Ltd. ...	1086	McMichael (L.), Ltd. ...	1074, 1096	Sylvex ...	1122
Curtis (Peter); Ltd. ...	1095, 1107	Makerimport Co. ...	1125	Taylor (C.) ...	1131
Darex ...	1123	Mandaw ...	1117	Telegraph Condenser Co. ...	1122
Dayzite, Ltd. ...	1117	Mazel Electrical Co. ...	1128	Vandam (A.) ...	1137
Detex Co. ...	1135	Merchants and Agencies, Ltd. ...	1128	Vandervell (C. A.) and Co. ...	1076, 1077
Dixon (L.) and Co. ...	1123	Michrom Engineering Co. ...	1128	Victoria Electrical Co. (M/c.), Ltd. ...	1126
Dorwoods ...	1118	Morris (J. R.) ...	1106	Watmel Wireless Co. ...	1063
Dubilier Condenser Co., Ltd. ...	1081	Morrison (A. E.) and Son ...	1130	Western Electric Co., Ltd. ...	1133
Economic Elec., Ltd. ...	1119	Mullard Radio Valve Co., Ltd. ...	1092, 1093	Wholesale Wireless Co., The ...	1137
Edison Swan Elec. Co., Ltd. ...	1114	Naylor (J. H.), Ltd. ...	1116, 1127	Wilkins and Wright, Ltd. ...	1135
				Williams, Ellis and Co. ...	1140
				Zealand (H. D.) ...	1128

**RADIO STOCKS (B. HAINE) PROPRIETOR**

**89, NEWMAN STREET, OXFORD STREET, LONDON, W.1**

Telephone: MUSEUM 3205.

Ask for New Catalogue for **EVERYTHING WIRELESS**

WE SPECIALISE IN:

<b>TERMINALS and BRASS PARTS</b>	Best Quality and Finish - Precision Work - Lowest Prices
<b>"OCTOPUS" MANSBRIDGE CONDENSERS</b>	"The Best by Test"
<b>"PERFECT" VERNIER COIL HOLDER</b>	Which is Really The Perfect Co. I Holder

**SETS OF PARTS FOR ANY AND EVERY CIRCUIT**

**THE "SECURITY" VALVE HOLDER**  
(Prov. Pat. No. 2187/25).

PRICE  
**1/-**  
NETT

**ANTI-CAPACITY**

**PROTECTS THE VALVE**

METAL DRILLING  
TEMPLATE Included.



**OBTAINABLE FROM ALL RETAILERS & FACTORS.**

Advert. of  
**Williams, Ellis & Co., London.**

Charm your friends with a pleasing performance —

install the

**"TANGENT" Type "D" RADIOMATIC 2-VALVE — £7-0-0**

Try it on Daventry with Loud Speaker—even 100 miles away

If not in his stock, all good dealers can obtain by return

**GENT & CO., LTD.**  
(Estd. 1872)

Paraday Works  
**LEICESTER**

London: 25 Victoria Street, S.W.1  
Newcastle-on-Tyne: "Tangent House," Blackett Street



# EFESCA

## Regenerative AERIAL TUNER



The Efesca Regenerative Aerial Tuner is the natural development of the extremely convenient series of Efesca One-Hole Tapped Coils. It is a specially designed form of Tapped Aerial Coil incorporating Aerial Reactance in a self-contained Unit. Reaction is effected by means of a rotor revolving in a separately wound section of the Aerial Coil thereby effecting maximum and uniform reaction over the whole wave band covered by the coil. Wavelength range 150 to 2,600 metres in conjunction with a .0005 variable condenser in parallel. Price complete with Split Switch, Knob, Pointer and Scale, 32/- each.

Other components in the Efesca Series of One-Hole Fixing Tapped Coils, are the H.F. Transformer and Anode Tuner (described and illustrated here), Aerial Tuner and the H.F. Reactance Coil.

Home Constructors can employ these units with every confidence and will find that the task of assembling is greatly simplified and the completed set will have a finish that is unobtainable by the use of conventional components. Furthermore no coils or external tuning accessories are required.



**EFESCA H.F. TRANSFORMER.** Wavelength range 150-2,500 metres, complete as illustration, wound on ebonite former, 21/- . Ditto, employing Grid Leak and .0003 Condenser, 25/- .

**EFESCA TUNED ANODE**  
An alternative method to H.F. Transformer Coupling. Must be used in conjunction with a variable Condenser of .0003 to .0005 mfd. Wavelength range 150 to 2,600 metres. 21/- each.




## EFESCA COMPONENTS

Write for Catalogue No 559 describing and illustrating EFESCA Components and EFESCAPHONE Receiving Sets

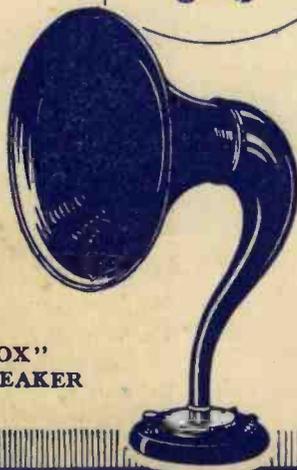**FALK STADELMANN & Co., Ltd.**

83/93, Farringdon Road, London, E.C.1

Also at Glasgow, Manchester and Birmingham




**EFESCA  
"PURAVOX"  
LOUD SPEAKER**



**EFESCA  
HEADPHONES**

# WHY THE **R.I.** CURVE IS RIGHT

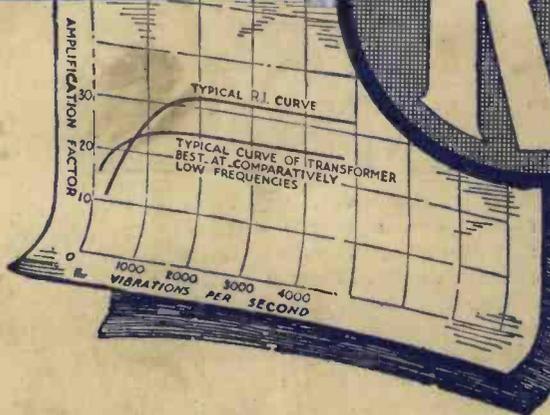

## *The Amplification that Preserves the Overtones*

The real personality of any artist lies in the overtones that are additional to the fundamental note waves. These overtones vary in frequency from one thousand to several thousand cycles per second, whereas the frequency of the fundamental notes generally varies between 250-1,200 per second.

A transformer that is designed to amplify the fundamental frequencies only, gives characterless reproduction resulting from the elimination of the smaller but nevertheless all-important overtone frequencies. The increased amplification necessary to bring out these minute vibrations is shown by the curve of the R.I. Transformer.

The immediate increase above the frequency of 1,000 is the reason why the R.I. curve is right.

The problem of the overtones has called for extensive and thorough research and the solution that maintains lifelike character in reproduction is the World's Transformer.

**THE R.I. TRANSFORMER**



**25/-**

Write for R.I. Catalogue, free on application.

Visit our Stand No. 36 at the All-British Wireless Exhibition, Albert Hall, September 12th—September 23rd

Advt. R.I. Ltd., 12, Hyde Street, New Oxford Street, London, W.C.1