

Rudolf F. Graf

Encyclopedia of

# ELECTRONIC CIRCUITS

Volume 3

# Contents

---

<b>1</b>	<b>Active Antennas</b>	<b>1</b>
<b>2</b>	<b>Alarm and Security Circuits</b>	<b>3</b>
<b>3</b>	<b>Amplifiers</b>	<b>10</b>
<b>4</b>	<b>Analog-to-Digital Converters</b>	<b>22</b>
<b>5</b>	<b>Annunciator</b>	<b>27</b>
<b>6</b>	<b>Attenuators</b>	<b>29</b>
<b>7</b>	<b>Audio Amplifiers</b>	<b>32</b>
<b>8</b>	<b>Automotive Circuits</b>	<b>40</b>
<b>9</b>	<b>Battery Chargers</b>	<b>53</b>
<b>10</b>	<b>Battery Monitors</b>	<b>60</b>
<b>11</b>	<b>Bridge Circuits</b>	<b>68</b>
<b>12</b>	<b>Burst Generators</b>	<b>72</b>
<b>13</b>	<b>Capacitance Meters</b>	<b>75</b>
<b>14</b>	<b>Carrier-Current Circuits</b>	<b>78</b>
<b>15</b>	<b>Clock Circuits</b>	<b>83</b>

<b>16</b>	<b>Comparators</b>	<b>86</b>
<b>17</b>	<b>Compressor/Expander Circuits</b>	<b>91</b>
<b>18</b>	<b>Computer Circuits</b>	<b>96</b>
<b>19</b>	<b>Converters</b>	<b>109</b>
<b>20</b>	<b>Counters</b>	<b>123</b>
<b>21</b>	<b>Crystal Oscillators</b>	<b>131</b>
<b>22</b>	<b>Decoders</b>	<b>141</b>
<b>23</b>	<b>Delay Circuits</b>	<b>146</b>
<b>24</b>	<b>Demodulator</b>	<b>149</b>
<b>25</b>	<b>Detectors</b>	<b>151</b>
<b>26</b>	<b>Digital-to-Analog Converters</b>	<b>163</b>
<b>27</b>	<b>Display Circuits</b>	<b>170</b>
<b>28</b>	<b>Drive Circuits</b>	<b>172</b>
<b>29</b>	<b>Fiber Optics Circuits</b>	<b>176</b>
<b>30</b>	<b>Field-Strength Meters</b>	<b>182</b>
<b>31</b>	<b>Filter Circuits</b>	<b>184</b>
<b>32</b>	<b>Flashers and Blinkers</b>	<b>193</b>
<b>33</b>	<b>Flow Detector</b>	<b>202</b>
<b>34</b>	<b>Fluid and Moisture Detectors</b>	<b>204</b>
<b>35</b>	<b>Followers</b>	<b>211</b>
<b>36</b>	<b>Frequency Multipliers and Dividers</b>	<b>213</b>
<b>37</b>	<b>Frequency-to-Voltage Converter</b>	<b>219</b>
<b>38</b>	<b>Function Generators</b>	<b>221</b>
<b>39</b>	<b>Games</b>	<b>243</b>
<b>40</b>	<b>Gas and Smoke Detectors</b>	<b>246</b>
<b>41</b>	<b>Hall-Effect Circuits</b>	<b>254</b>
<b>42</b>	<b>High-Frequency Amplifiers</b>	<b>259</b>
<b>43</b>	<b>Humidity Sensor</b>	<b>266</b>
<b>44</b>	<b>Indicators</b>	<b>268</b>
<b>45</b>	<b>Infrared Circuits</b>	<b>271</b>
<b>46</b>	<b>Instrumentation Amplifiers</b>	<b>278</b>

<b>47</b>	<b>Integrator Circuits</b>	<b>285</b>
<b>48</b>	<b>Intercom Circuits</b>	<b>287</b>
<b>49</b>	<b>Inverters</b>	<b>293</b>
<b>50</b>	<b>Lamp-Control Circuits</b>	<b>299</b>
<b>51</b>	<b>Laser Circuits</b>	<b>309</b>
<b>52</b>	<b>Light-Controlled Circuits</b>	<b>312</b>
<b>53</b>	<b>Limiters</b>	<b>320</b>
<b>54</b>	<b>LVDT Circuit</b>	<b>323</b>
<b>55</b>	<b>Mathematical Circuits</b>	<b>325</b>
<b>56</b>	<b>Measuring and Test Circuits</b>	<b>328</b>
<b>57</b>	<b>Medical Electronics Circuits</b>	<b>349</b>
<b>58</b>	<b>Metronome</b>	<b>353</b>
<b>59</b>	<b>Miscellaneous Treasures</b>	<b>355</b>
<b>60</b>	<b>Mixers</b>	<b>367</b>
<b>61</b>	<b>Modulators</b>	<b>371</b>
<b>62</b>	<b>Motor-Control Circuits</b>	<b>378</b>
<b>63</b>	<b>Multiplexers</b>	<b>391</b>
<b>64</b>	<b>Noise Reduction Circuits</b>	<b>398</b>
<b>65</b>	<b>Notch Filters</b>	<b>402</b>
<b>66</b>	<b>Operational Amplifiers</b>	<b>405</b>
<b>67</b>	<b>Optically Coupled Circuits</b>	<b>407</b>
<b>68</b>	<b>Oscillators</b>	<b>420</b>
<b>69</b>	<b>Oscilloscope Circuits</b>	<b>433</b>
<b>70</b>	<b>Phase Detectors</b>	<b>440</b>
<b>71</b>	<b>Photography-Related Circuits</b>	<b>443</b>
<b>72</b>	<b>Power Amplifiers</b>	<b>450</b>
<b>73</b>	<b>Fixed Power Supplies</b>	<b>457</b>
<b>74</b>	<b>High-Voltage Power Supplies</b>	<b>478</b>
<b>75</b>	<b>Variable Power Supplies</b>	<b>487</b>
<b>76</b>	<b>Power Supply Monitors</b>	<b>493</b>
<b>77</b>	<b>Probes</b>	<b>496</b>

<b>78</b>	<b>Programmable Amplifiers</b>	<b>504</b>
<b>79</b>	<b>Protection Circuits</b>	<b>509</b>
<b>80</b>	<b>Proximity Sensors</b>	<b>514</b>
<b>81</b>	<b>Pulse Generators</b>	<b>519</b>
<b>82</b>	<b>Ramp Generators</b>	<b>525</b>
<b>83</b>	<b>Receivers</b>	<b>528</b>
<b>84</b>	<b>Rectifier Circuits</b>	<b>536</b>
<b>85</b>	<b>Resistance/Continuity Meters</b>	<b>538</b>
<b>86</b>	<b>Rf Amplifiers</b>	<b>541</b>
<b>87</b>	<b>Sample-and-Hold Circuits</b>	<b>548</b>
<b>88</b>	<b>Signal Injectors</b>	<b>554</b>
<b>89</b>	<b>Sine-Wave Oscillators</b>	<b>556</b>
<b>90</b>	<b>Sirens, Warblers, and Wailers</b>	<b>560</b>
<b>91</b>	<b>Solid-State Relay Circuits</b>	<b>569</b>
<b>92</b>	<b>Solenoid Drivers</b>	<b>571</b>
<b>93</b>	<b>Sound Effects Circuits</b>	<b>574</b>
<b>94</b>	<b>Sound-Operated Circuits</b>	<b>579</b>
<b>95</b>	<b>Splitters</b>	<b>581</b>
<b>96</b>	<b>Square-Wave Generators</b>	<b>583</b>
<b>97</b>	<b>Staircase Generators</b>	<b>586</b>
<b>98</b>	<b>Strobe Circuit</b>	<b>589</b>
<b>99</b>	<b>Switching Circuits</b>	<b>591</b>
<b>100</b>	<b>Tachometer Circuits</b>	<b>595</b>
<b>101</b>	<b>Tape-Recorder Circuits</b>	<b>599</b>
<b>102</b>	<b>Telephone-Related Circuits</b>	<b>602</b>
<b>103</b>	<b>Temperature Controls</b>	<b>623</b>
<b>104</b>	<b>Temperature Sensors</b>	<b>629</b>
<b>105</b>	<b>Temperature-to-Time Converters</b>	<b>632</b>
<b>106</b>	<b>Tesla Coils</b>	<b>634</b>
<b>107</b>	<b>Thermometer Circuits</b>	<b>637</b>
<b>108</b>	<b>Tilt Meter</b>	<b>644</b>

<b>109</b>	Time Delay Circuits	<b>647</b>
<b>110</b>	Timers	<b>650</b>
<b>111</b>	Tone Control Circuits	<b>656</b>
<b>112</b>	Touch-Switch Circuits	<b>661</b>
<b>113</b>	Tracking Circuits	<b>666</b>
<b>114</b>	Transducer Amplifiers	<b>669</b>
<b>115</b>	Transmitters	<b>674</b>
<b>116</b>	Tremolo Circuits	<b>692</b>
<b>117</b>	Ultrasonics	<b>696</b>
<b>118</b>	Video Amplifiers	<b>708</b>
<b>119</b>	Video Circuits	<b>713</b>
<b>120</b>	Voice Circuits	<b>729</b>
<b>121</b>	Voltage-Controlled Oscillators	<b>735</b>
<b>122</b>	Voltage Converters	<b>742</b>
<b>123</b>	Voltage-to-Frequency Converters	<b>749</b>
<b>124</b>	Voltage Meters/Monitors/Indicators	<b>758</b>
<b>125</b>	Voltage References	<b>773</b>
<b>126</b>	Window Detectors/Comparators/Discriminators	<b>776</b>
	Sources	<b>781</b>
	Index	<b>801</b>

To Sheryl Melissa,  
a budding scholar  
From Popsi

## Preface

---

Volume III of *The Encyclopedia of Electronic Circuits* adds about 1,000 new circuits to the ready-to-use files that were established by the publication of volumes I and II of this set of circuits encyclopedias.

These three volumes now offer an invaluable storehouse of about 3,000 carefully arranged and categorized, easy-to-access circuits. Volume IV is scheduled for publication in 1992.

Once again it gives me great pleasure to extend my gratitude to William Sheets for his comments and contributions, and to Mrs. Stella Dillon for her virtuoso performance on the word processor.

# 1

## Active Antennas

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Active Antenna  
Active Antenna



## 2


# Alarm and Security Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Auto Alarm  
One-Chip Burglar Alarm  
Semiconductor Fail-Safe Alarm  
Single-IC Auto Alarm  
Burglar Alarm  
Burglar Alarm

## AUTO ALARM

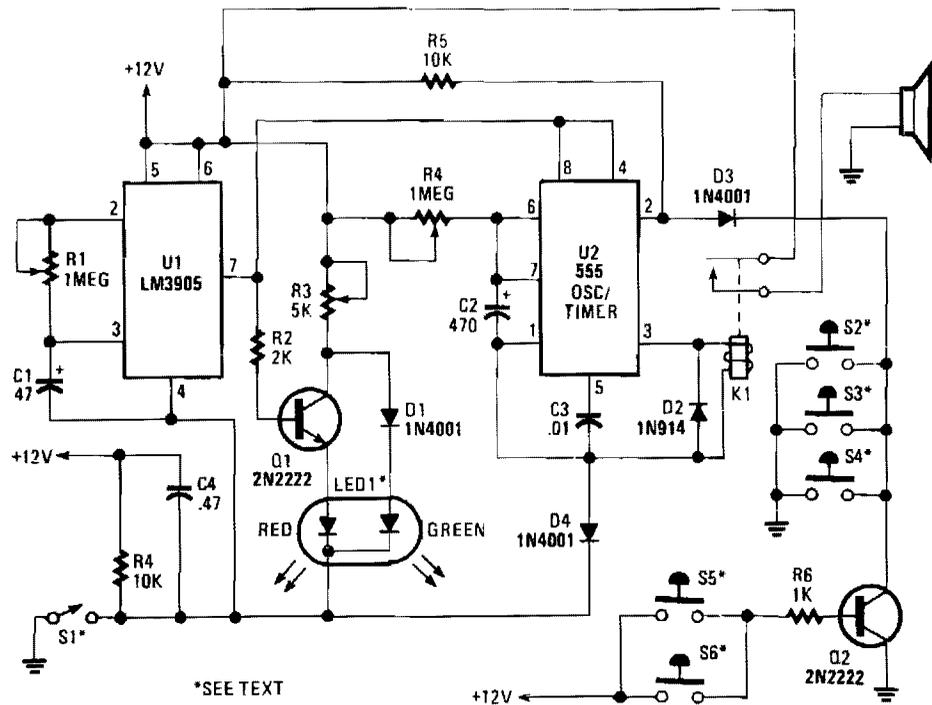

POPULAR ELECTRONICS


Fig. 2-1

In operation, the alarm circuit allows a 0–47 second time delay, as determined by the R1/C1 combination, after the switch is armed to allow the vehicle's motion sensor to settle down. This allows you time to get a bag of groceries out of the trunk and not have the hassle of juggling the groceries and the key switch at once.

During the time delay, half of LED1, which is actually a single, bi-colored, three-legged common cathode device, lights green. At the same time, pins 8 and 4 of U2 (a 555 oscillator/timer) are held low by U1 (a 3905 oscillator/timer), causing the alarm to remain silent. Once the delay is over, LED1 turns red, indicating that the circuit is armed.


At that point, a ground at pin 2 of U2 forces pin 3 of U2 high, closing the contacts of K1 and sounding the siren for a time duration determined by R4 and C2. Once the time has elapsed, pin 3 is pulled low, K1 opens, and the circuit is again ready to go. The circuit can be manually reset by the simple expedient of opening and closing the key switch. Potentiometer R3 controls the LED's illumination intensity. Diode D1 ensures that the green segment of LED1 is fully extinguished when Q1 is turned on—which turns the LED to red. Resistors R4 and R5 must be connected to the +V bus, not to pin 7 of U1, otherwise U2 will mysteriously trigger itself each time the initial delay ends.

## ONE-CHIP BURGLAR ALARM

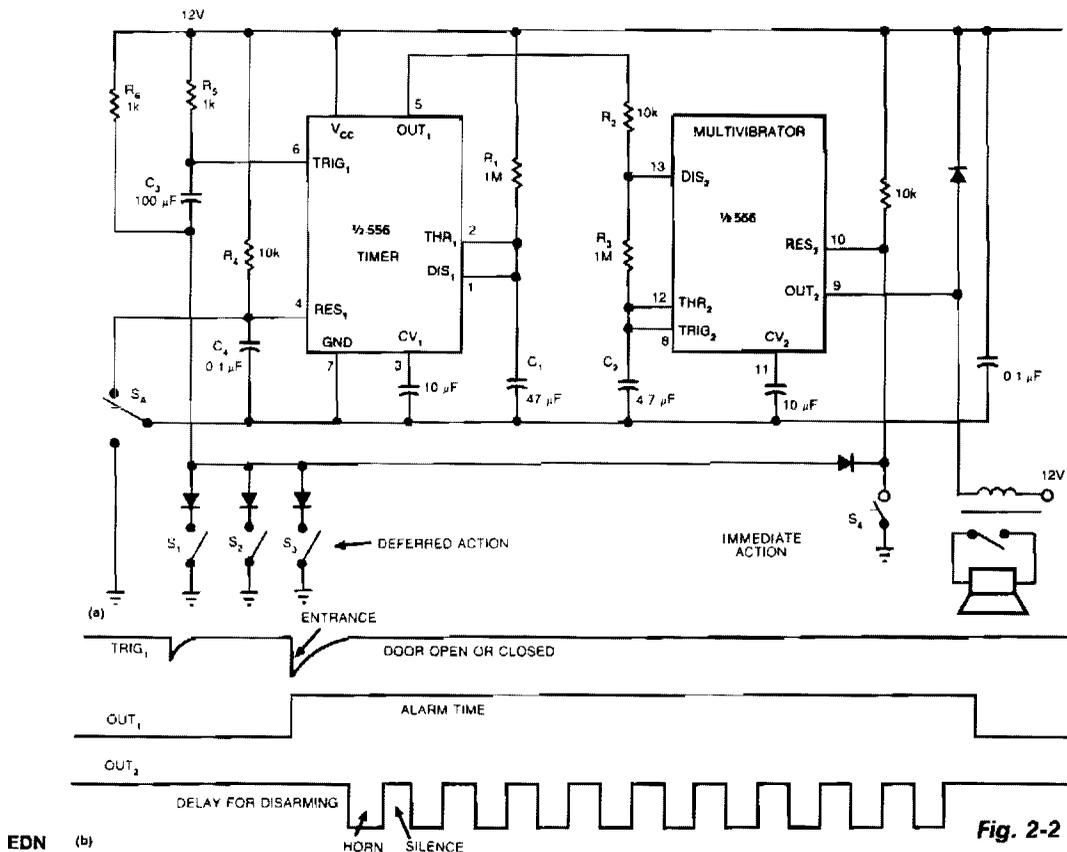

The single-chip, burglar-alarm circuit shown uses a dual 556 timer, draws 10 mA of standby current, and generates a pulsing alarm signal that conserves battery energy. Once activated, the alarm will remain on, independent of the subsequent state of any of the sensors. The sensors support both deferred and immediate-action modes. You can attach this circuit to your car's internal lighting circuitry using a single wire and a relay. To arm this circuit, you open your car door and close switch SA. The switch discharges capacitor C4 and holds the timer (one half of the 556 IC) in a reset state to prevent false triggering while you're arming the circuit. When you close your car door, the circuit enters a standby mode. If the door is then reopened, the sensors apply a negative-going pulse to trigger 1. Output 1 then increases, enabling the alarm for  $1.1R_1C_1$  seconds. Output 1's high state triggers the multivibrator, the other half of the 556, which begins to cycle after a delay equal to  $1.1(R_2 + R_3)C_2$  seconds. As long as the timer's output stays high, the multivibrator will continue to cycle, turning the horn off and on at 3.3-second intervals. During the interval between time that the timer's output increases and the time that the multivibrator's output decreases, you can disarm this circuit using switch SA. To prevent false triggering caused by switch contacts, at S1, S2, and S3, that may bounce when closing the door, make the  $R_6C_3$  time constant as large as possible. In addition, capacitors C1 and C2 should be tantalum types and should exhibit leakage of less than  $1\ \mu\text{A}$  at room temperature.

## SEMICONDUCTOR FAIL-SAFE ALARM

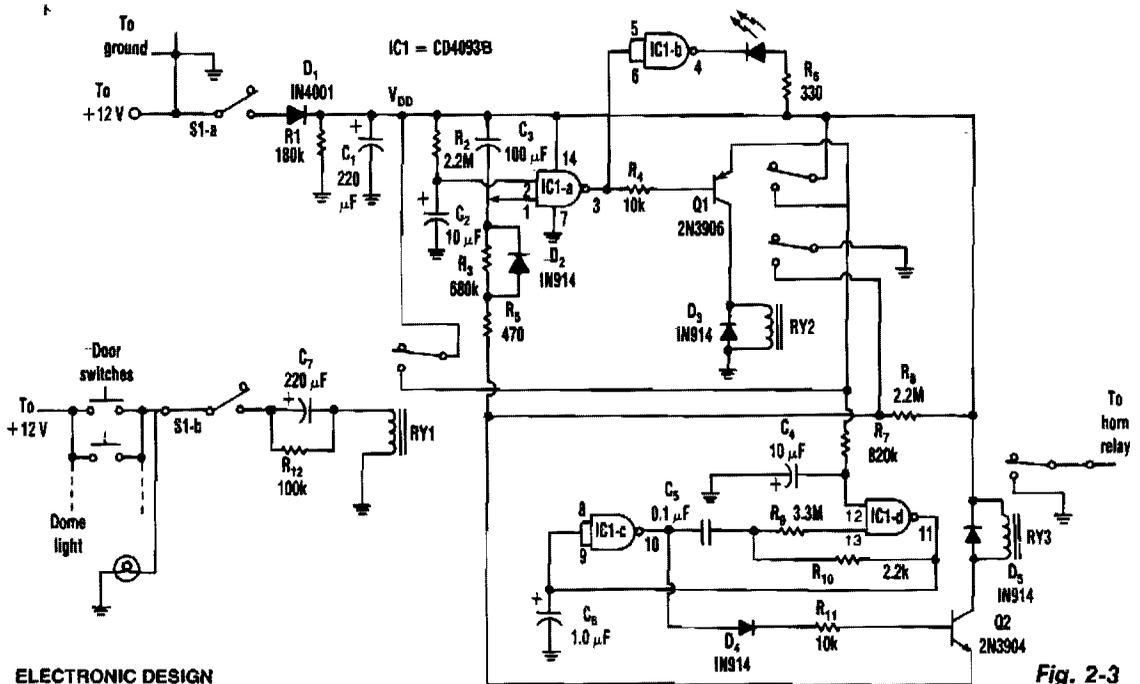

False alarms produced by semiconductor failure are impossible with this burglar-alarm circuit equipped with relays. What's more, the circuit is virtually immune to false triggering. With a standby current of less than 0.1 mA, the circuit offers all the features an alarm needs: entry and exit delays, a timed alarm period, and automatic reset after an intrusion.

One CMOS CD4093B quad NAND gate, IC1, supplies both logic and analog timing functions with the aid of Schmitt-trigger switching action. Relays make the circuit fail-safe in the alarm-active mode, even when the semiconductors fail. The relays are 12-V, with coil resistances of 250  $\Omega$  or more.

Closing switch S1 initiates circuit operation. Capacitor C2 begins charging through resistor R2 and arming indicator LED1 lights. When pin 2 of IC1a reaches its switching point, its output decreases, extinguishing LED1 and indicating that the exit delay has ended. That output also drives the base of Q1 low, so that if the emitter circuit completes to the  $V_{DD}$  line, Q1 conducts. The circuit is now armed, and current drain drops to less than 0.1 mA.



When the vehicle is entered, relay RY1 contacts close momentarily, completing the emitter circuit of Q1 and causing the RY2 contacts to close. Charging C4 through R7 determines the entry-delay period. If the system isn't turned off by opening S1 during this period, the oscillator circuit of IC1c and IC1d activates, and a rapid on/off horn-honking cycle kicks on with the aid of Q2 and RY3.

The alarm cycle ends after about a minute, when C2 charges through R3 to the threshold voltage of IC1a at pin 1. This voltage resets the timing circuit, readying it for another entry/alarm cycle.

RY1 is connected for vehicles that use door switches connected to +12 V. For vehicles that use grounding door switches, the bottom of the RY1 coil should connect to +12 V instead of ground. In the latter case, the polarity of C7 should be reversed.

For home use, the R3C3 time constant should be increased to give a longer alarm.

## SINGLE-IC AUTO ALARM

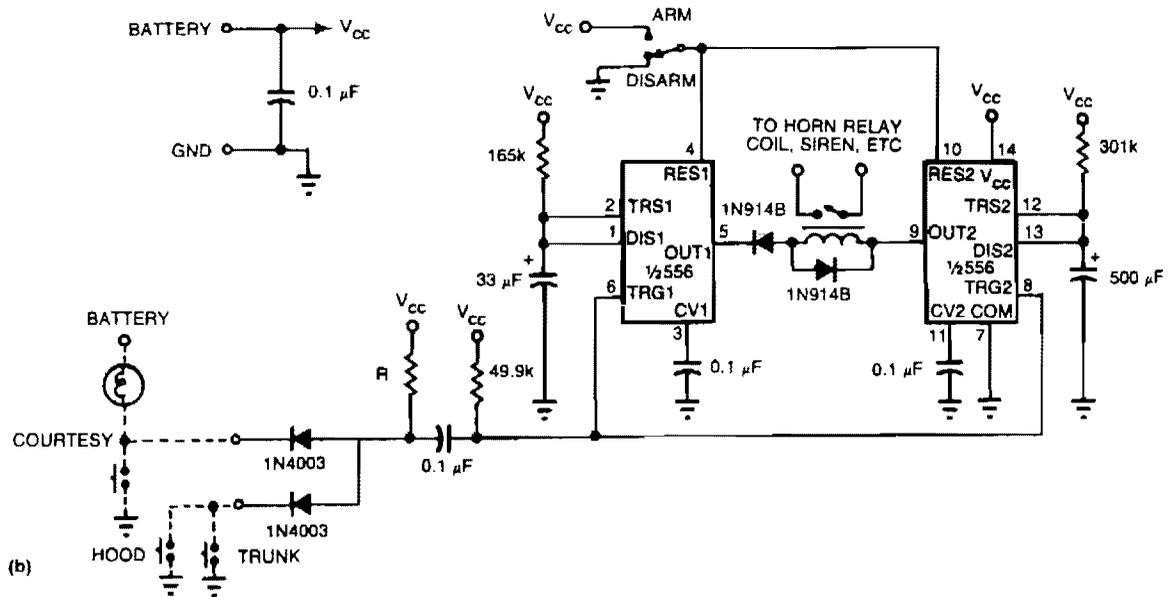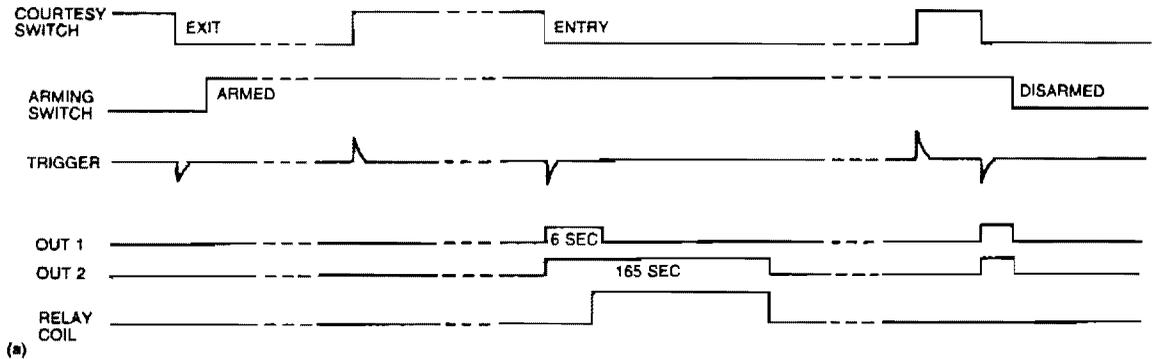


EDN

Fig. 2-4

See (a) for the timing information for the alarm circuit in (b). When leaving your vehicle, flip the arming switch and close the door to arm the device. Subsequent opening of an entrance triggers both timers. After the expiration of the entry delay timer, the alarm sounds for a time determined by the second timer. The value of  $R$  should be less than  $1\text{ K}\Omega$ . If you use an incandescent lamp instead of a resistor, you get an extra function—an open-entrance indicator. By keeping the resistance low, you avoid false tripping should water collect under the hood. If your door switch connects the courtesy light to 12 V rather than ground, use a single transistor as an inverter at the input.

## BURGLAR ALARM

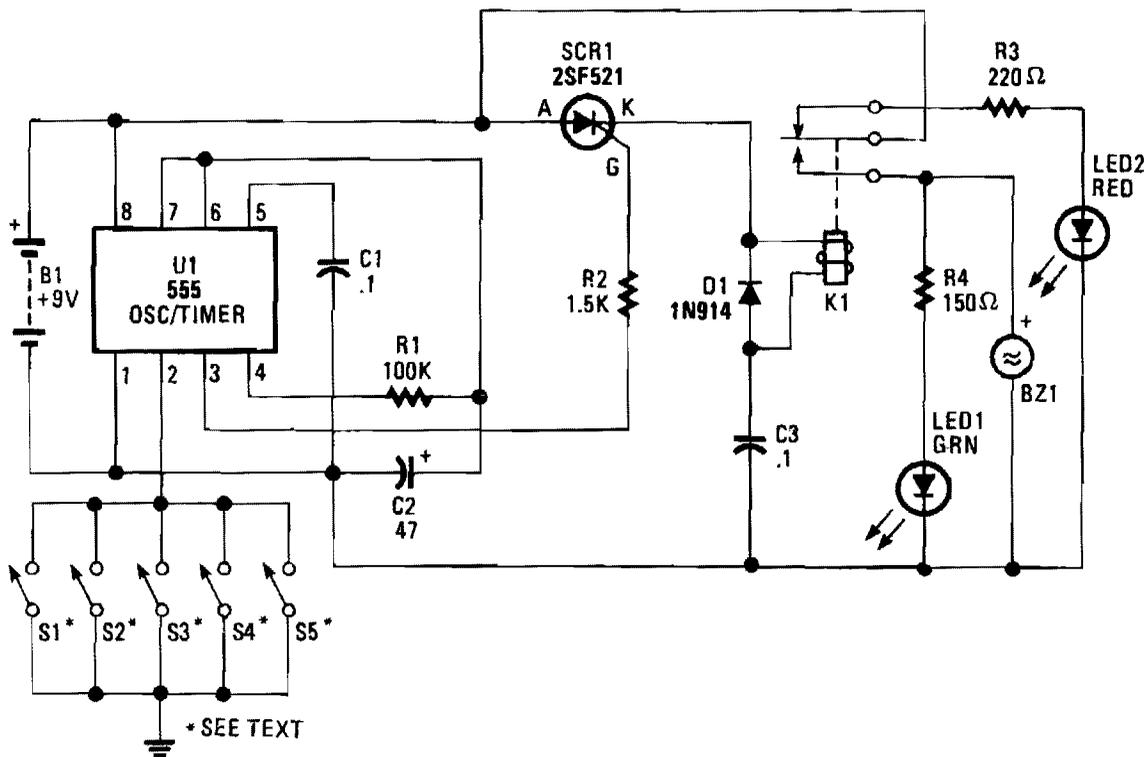

POPULAR ELECTRONICS


Fig. 2-5

The heart of the circuit is a 555 oscillator/timer, U1, configured for monostable operation. The output of U1 at pin 3 is tied to the gate of SCR1. As long as S1 – S5, which are connected to the trigger input of U1, are open, the circuit remains in the ready state, and does not trigger SCR1 into conduction. Because the relay is not energized, battery current is routed through the relay's normally-closed terminal and through current-limiting resistor R3 to LED2, causing it to light.

However, when one of the switches (S1 – S5) is closed, grounding U1 pin 2, the output of U1 at pin 3 increases, activating SCR1. That energizes the relay, pulling the wiper of K1 to the normally-open terminal, causing LED1 to light and BZ1 to sound.

The duration of the output is determined by the RC time-constant circuit, formed by R1 and C1. Resistor R2 regulates the output of U1 to a safe value for the gate of SCR1. Switches S1 – S5 are to doors, windows, etc. A switch can be connected in series with B1 to activate and deactivate the alarm circuit when it's not needed.

# BURGLAR ALARM

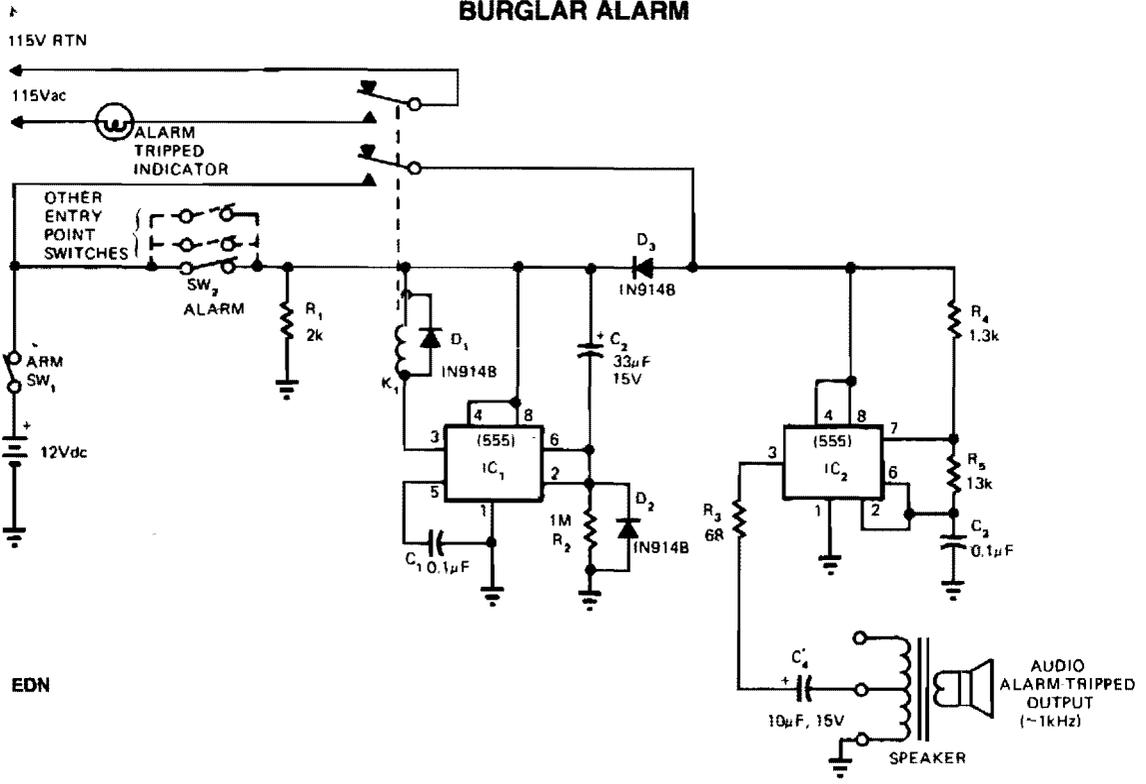

EDN

Fig. 2-6

This circuit cannot be shut off for 10 to 60 seconds—even if the trip condition is immediately removed. It draws no standby power from the battery and is self-resetting.

# 3


## Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Input/Output Buffer Amplifier for Analog Multiplexers	Polarity-Reversing Low-Power Amplifier
Absolute-Value Norton Amplifier	Summing Amplifier
Intrinsically Safe Protected Op Amp	Ac-Coupled Dynamic Amplifier
$\pm 15$ -V Chopper Amplifier	Forward-Current Booster
Composite Amplifier	Dc-Stabilized Fast Amplifier
Cascaded Amplifier	Write Amplifier
Inverting Amplifier	Low-Noise Photodiode Amplifier
Noninverting Amplifier	Voltage-Follower Amplifier for Signal-Supply Operation
Differential Amplifier	Current-Shunt Amplifier
Active Clamp-Limiting Amplifier	Constant-Bandwidth Amplifier
Wide-Band AGC Amplifier	
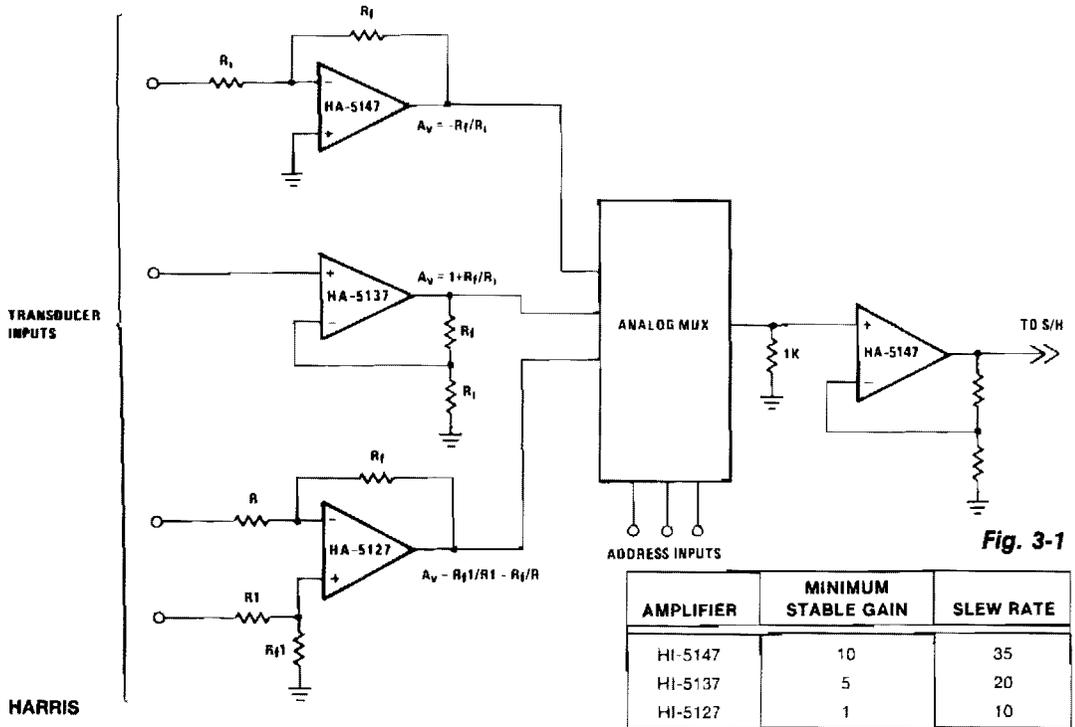
## INPUT/OUTPUT BUFFER AMPLIFIER FOR ANALOG MULTIPLEXERS




The precision input characteristics of the HA-5147 help simplify system *error budgets*, while its speed and drive capabilities provide fast charging of the multiplexer's output capacitance. This speed eliminates an increased multiplexer acquisition time, which can be induced by more limited amplifiers. The HA-5147 accurately transfers information to the next stage while effectively reducing any loading effects on the multiplexer's output.

## ABSOLUTE VALUE NORTON AMPLIFIER

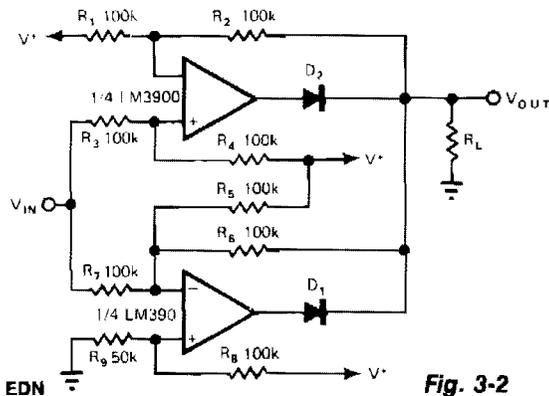

The noninverting amplifier has a gain of  $R_2/R_3$  (1 in this case) and produces a voltage of  $V_{out}$  during a positive excursion of  $V_{in}$  with respect to ground. The inverting amplifier accommodates the negative excursions of  $V_{in}$ ; its gain is given by  $-R_6/R_7$ , which equals  $-1$  to maintain symmetry with the noninverting amplifier.  $R_9$  provides adjustment for the symmetry, supply variations, and offsets. Even though the circuit operates on a single supply,  $V_{in}$  can go negative to the same extent that it goes positive.

## INTRINSICALLY SAFE PROTECTED OP AMP

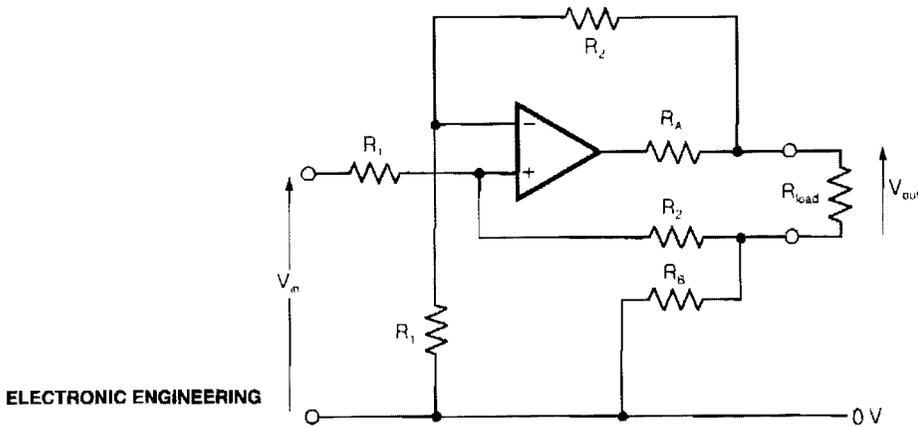

**Fig. 3-3**

In intrinsically safe applications, it is sometimes necessary to separate sections of circuitry by resistors which limit current under fault conditions. The circuit shown provides an accurate analogue output with effectively zero output impedance, despite having resistors in series with the output. The output voltage is given by:


$$V_{out} = \frac{V_{in} R_2}{R_1}$$

which is independent of  $R_A$  and  $R_B$ . The values of  $R_A$  and  $R_B$  should be chosen to achieve the desired current limiting, but note that a proportion of the voltage given at the op-amp output will be dropped across these resistors. This limits the output swing at the load to approximately:

$$\frac{V_S R_{load}}{R_A + R_B + R_{load}}$$

where:  $V_S$  = voltage swing at the op-amp output. Any type of op amp would be suitable.


## ± 15-V CHOPPER AMPLIFIER

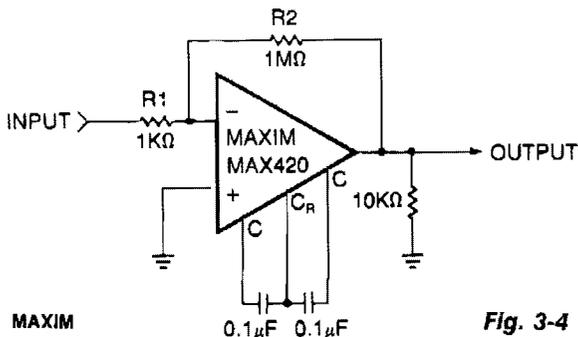

**Fig. 3-4**

This simple circuit is a gain-of-1000 inverting amplifier. It will amplify submillivolt signals up to signal levels suitable for further processing. In almost all system applications, it is best to use as much gain as possible in the MAX420, thus minimizing the effects of later-stage offsets. For example, if circuitry following the MAX420 has an offset of 5 mV, the additional offset referred back to the MAX420 input (gain = 1000) will be 5 μV, doubling the system's offset error.

### COMPOSITE AMPLIFIER

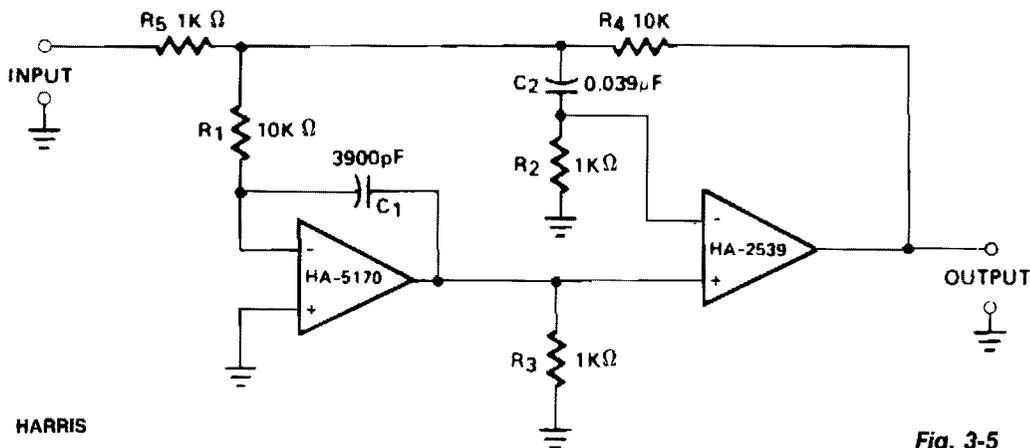

HARRIS

Fig. 3-5


A composite configuration greatly reduces dc errors without compromising the high-speed, wideband characteristics of HA-2539. The HA-2540 could also be used, but with slightly lower speeds and bandwidth response.

The HA-2539 amplifies signals above 40 kHz which are fed forward via C2; R2 and R5 set the voltage gain at  $-10$ . The slew rate of this circuit was measured at  $350 \text{ V}/\mu\text{s}$ . Settling time to a 0.1% level for a 10-V output step is under 150 ns and the gain bandwidth product is 300 MHz.

The HA-5170 amplifies signals below 40 kHz, as set by C1 and R1, and controls the dc input characteristics such as offset voltage, drift, and bias currents of the composite amplifier. Therefore, it has an offset voltage of  $100 \mu\text{V}$ , drift of  $2 \mu\text{V}/^\circ\text{C}$ , and bias currents in the 20-pA range. The offset voltage can be externally nulled by connecting a 20-K $\Omega$  pot to pins 1 and 5, with the wiper tied to the negative supply. The dc gains of the HA-5170 and HA-2539 are cascaded; this means that the dc gain of the composite amplifier is well over 160 dB.

The excellent ac and dc performance of this composite amplifier is complemented by its low noise performance,  $0.5\text{-}\mu\text{V}$  rms from 0.1 Hz to 100 Hz. It is very useful in high-speed data acquisition systems.

### CASCADED AMPLIFIER

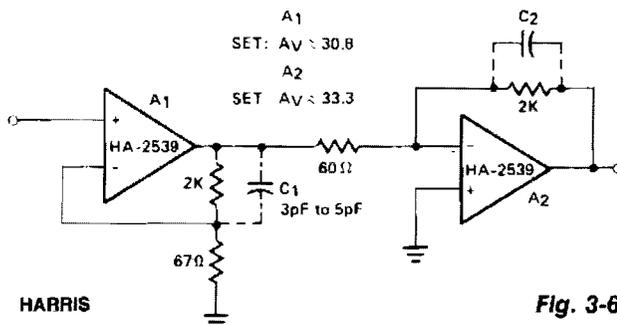

HARRIS

Fig. 3-6

Cascaded amplifier sections are used to extend bandwidth and increase gain. Using two HA-2539 devices, this circuit is capable of 60-dB gain at 20 MHz.

### INVERTING AMPLIFIER

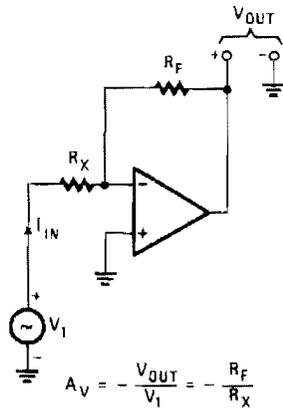


Fig. 3-7

HANDS-ON ELECTRONICS

### NONINVERTING AMPLIFIER


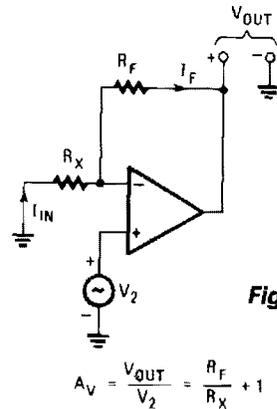


Fig. 3-8

HANDS-ON ELECTRONICS

### DIFFERENTIAL AMPLIFIER

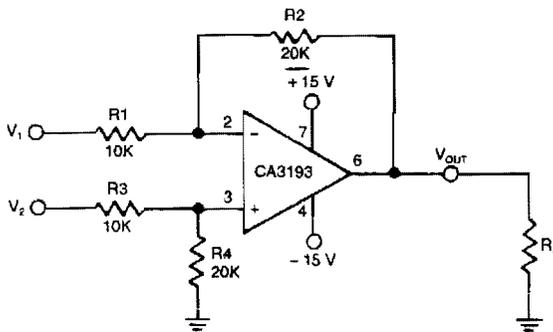

ALL RESISTANCE VALUES ARE IN OHMS

$$V_{OUT} = V_2 \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) - V_1 \left( \frac{R_2}{R_1} \right)$$

$$\text{IF } R_4 = R_2, R_3 = R_1 \text{ AND } \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$\text{THEN } V_{OUT} = (V_2 - V_1) \left( \frac{R_2}{R_1} \right)$$

$$\text{FOR VALUES ABOVE } V_{OUT} = (V_2 - V_1)$$

IF  $A_V$  IS TO BE MADE 1 AND IF  $R_1 = R_3 = R_4 = R$   
WITH  $R_2 = 0.999R$  (0.1% MISMATCH IN  $R_2$ )


THEN  $V_{OCM} = 0.0005 V_{IN}$  OR CMRR = 66 dB  
THUS, THE CMRR OF THIS CIRCUIT IS LIMITED BY  
THE MATCHING OR MISMATCHING OF THIS NETWORK  
RATHER THAN THE AMPLIFIER

This differential amplifier uses a CA3193 BiMOS op amp. This classical, differential input-to-signal-ended output converter when used with low-resistance signal source will maintain level of CMRR, if  $R_1 = R_3 + R_4$ .

Fig. 3-9

GE/RCA


## ACTIVE CLAMP-LIMITING AMPLIFIER

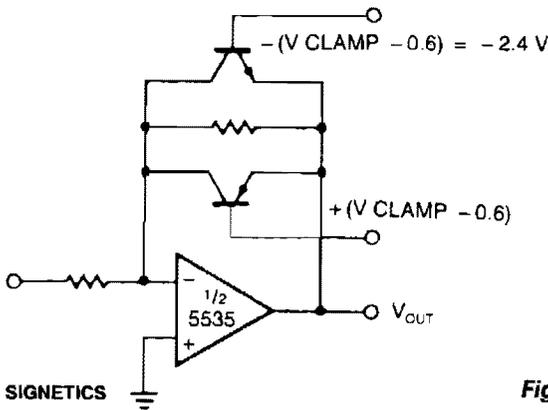

The modified inverting amplifier uses an active clamp to limit the output swing with precision. Allowance must be made for the  $V_{BE}$  of the transistors. The swing is limited by the base-emitter breakdown of the transistors. A simple circuit uses two back-to-back zener diodes across the feedback resistor, but tends to give less precise limiting and cannot be easily controlled.

Fig. 3-10

## WIDE-BAND AGC AMPLIFIER

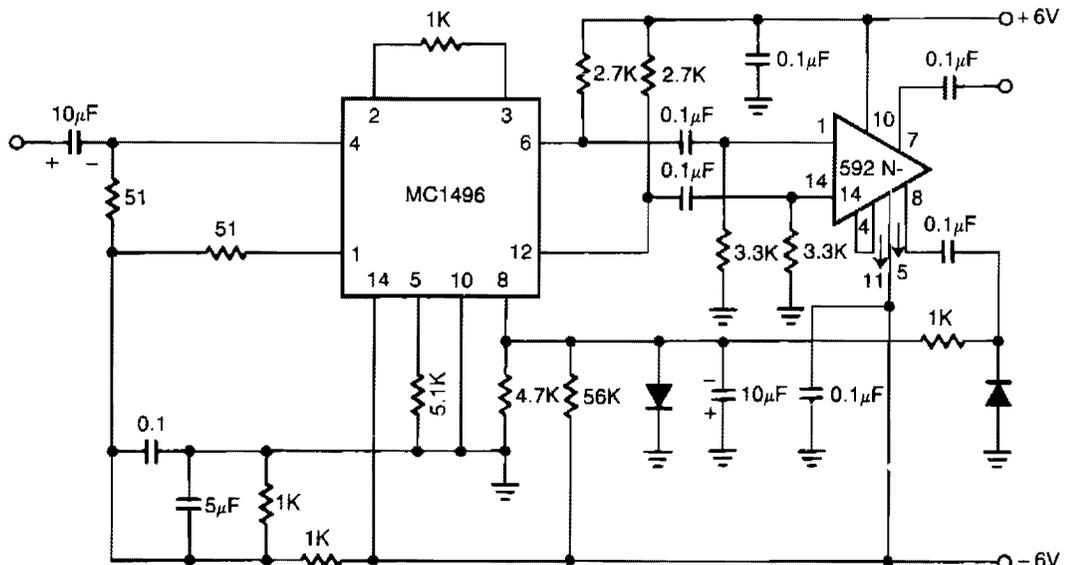

NOTE:  
ALL RESISTOR VALUES ARE IN OHMS

SIGNETICS

Fig. 3-11

The NE592 is connected in conjunction with a MC1496 balanced modulator to form an excellent automatic gain control system. The signal is fed to the signal input of the MC1496 and rc-coupled to the NE592. Unbalancing the carrier input of the MC1496 causes the signal to pass through unattenuated. Rectifying and filtering one of the NE592 outputs produces a dc signal which is proportional to the ac signal amplitude. After filtering, this control signal is applied to the MC1496, causing its gain to change.

### POLARITY-REVERSING LOW-POWER AMPLIFIER


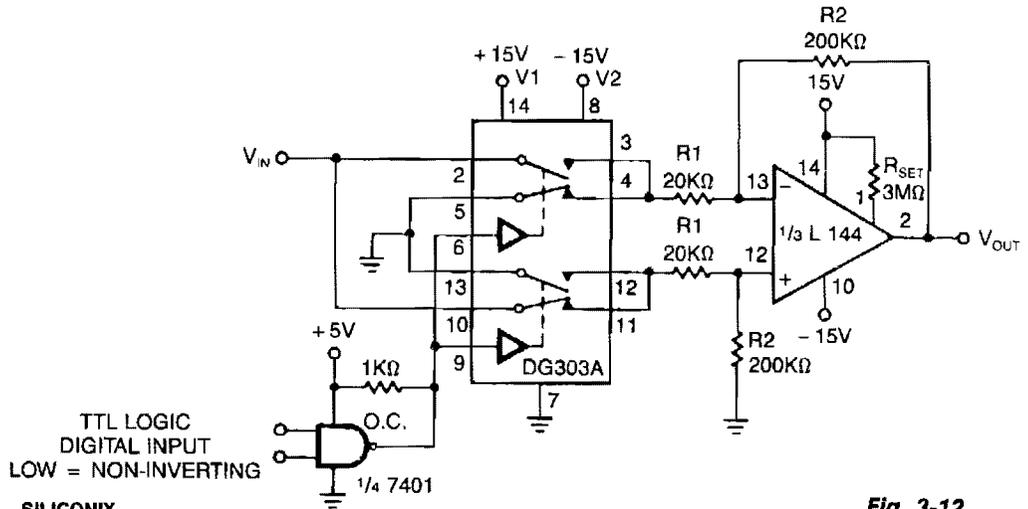


Fig. 3-12

### SUMMING AMPLIFIER

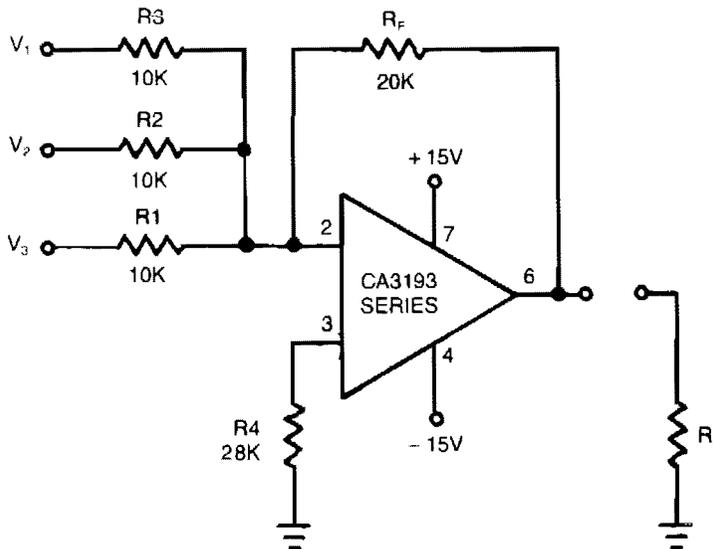

$$V_{OUT} = - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$

$$V_{OUT} = - (2V_1 + 2V_2 + 2V_3)$$


GE/RCA

ALL RESISTANCE VALUES ARE IN OHMS

Fig. 3-13


This circuit uses a CA3193 BiMOS op amp. Because input noise of the amplifier is increased by  $R_F/R_1//R_2//R_3$ , and the gain that a single input will amplify is the gain of only one of the input channels ( $R_F/R_1$ ), for good noise performance, use the smallest number of inputs.

## AC-COUPLED DYNAMIC AMPLIFIER

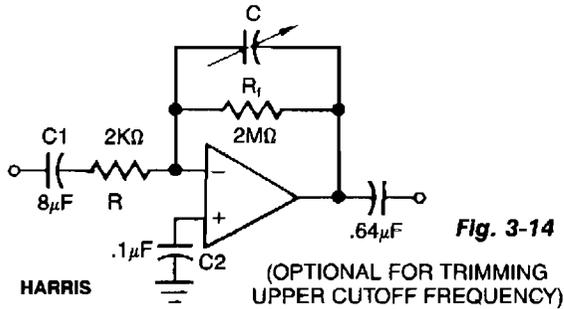

This circuit acts as a bandpass filter with gain and would be most useful for biomedical instrumentation. Low-frequency cutoff is set at 10 Hz while the high-frequency breakpoint is given by the open-loop rolloff characteristic of the HA-5141/42/44. In this case, the  $A_{VCL} = 60$  dB where the rolloff occurs at approximately 300 Hz. This corner frequency may be trimmed by inserting a capacitor in parallel with  $R_f$ .

## FORWARD-CURRENT BOOSTER

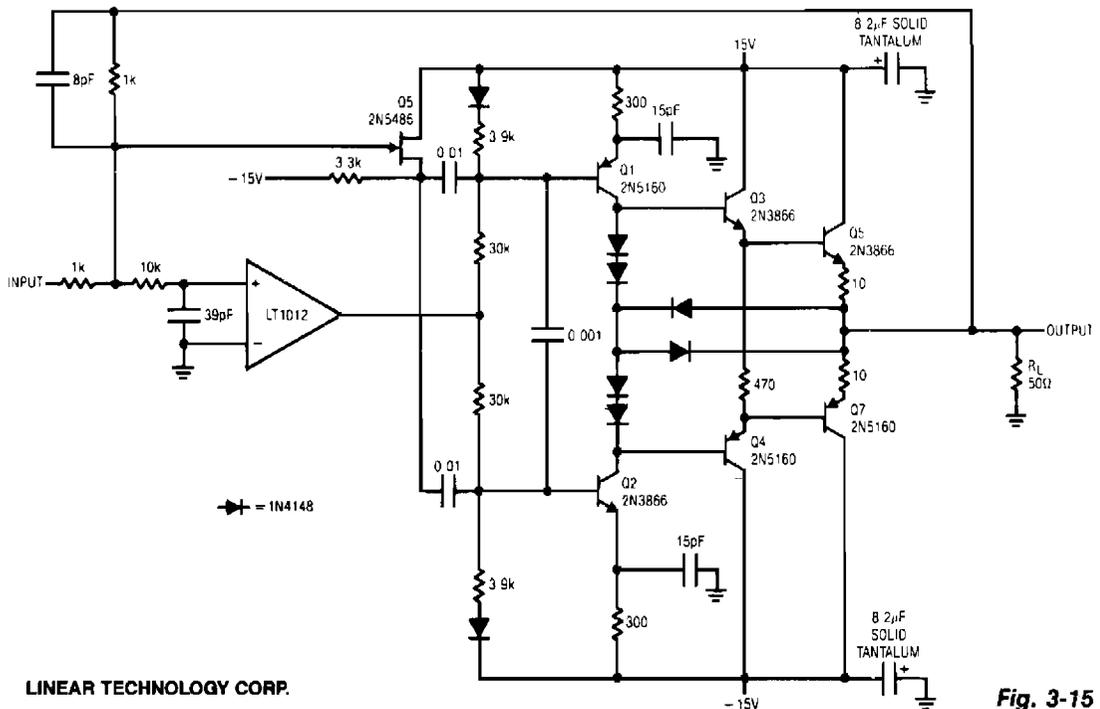

The LT1012 corrects dc errors in the booster stage, and does not set high-frequency signals. Fast signals are fed directly to the stage via Q5 and the 0.01- $\mu$ F coupling capacitors. Dc and low-frequency signals drive the stage via the op-amp's output. The output stage consists of current sources, Q1 and Q2, driving the Q3-Q5 and Q4-Q7 complementary emitter follows. The diode network at the output steers drive away from the transistor bases when output current exceeds 250 mA, providing fast short-circuit protection. The circuit's high frequency summing node is the junction of the 1-K and 10-K resistors at the LT1012. The 10 K/39 pF pair filters high frequencies, permitting accurate dc summation at the LT1012's positive input. This current-boosted amplifier has a slew rate in excess of 1000 V/ $\mu$ s, a full power bandwidth of 7.5 MHz and a 3-dB point of 14 MHz.

## DC-STABILIZED FAST AMPLIFIER

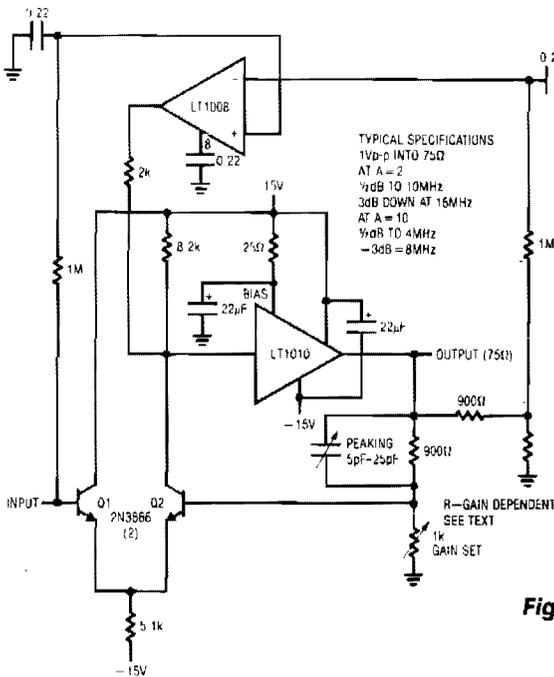


Fig. 3-16

LINEAR TECHNOLOGY CORP.

This amplifier functions over a wide range of gains, typically 1-10. It combines the LT1008 based dc stabilizing loop. Q1 and Q2 form a differential stage which single-ends into the LT1010. The circuit delivers 1 V pk-pk into a typical 75-Ω video load. At  $A = 2$ , the gain is within 0.5 dB to 10 MHz with the -3-dB point occurring at 16 MHz. At  $A = 10$ , the gain is flat ( $\pm 0.5$  dB to 4 MHz) with a -3-dB point at 8 MHz. The peaking adjustment should be optimized under loaded output conditions. This is a simple stage for fast applications where relatively low output swing is required. Its 1 V pk-pk output works nicely for video circuits. A possible problem is the relatively high bias current, typically 10  $\mu$ A. Additional swing is possible, but more circuitry is needed.

## WRITE AMPLIFIER


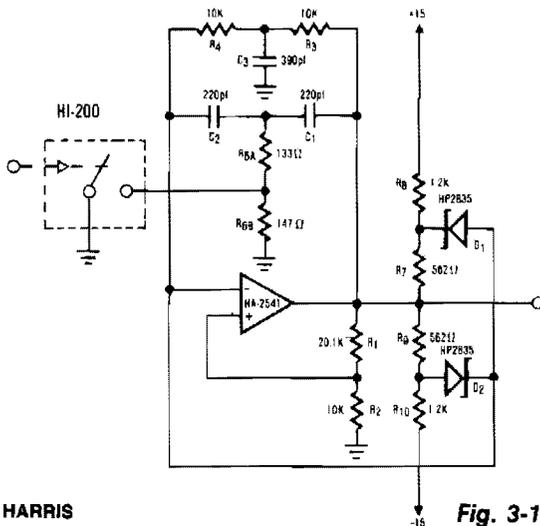


Fig. 3-17

HARRIS

The proliferation of industrial and computerized equipment containing programmable memory has increased the need for reliable recording media. The magnetic tape medium is presently one of the most widely used methods. The primary component of any magnetic recording mechanism is the write mechanism. The concept of the write generator is very basic. The digital input causes both a change in the output amplitude, as well as a change in frequency. This type of operation is accomplished by altering the value of a resistor in the standard twin-tee oscillator. A HI-201 analog switch was used to facilitate the switching action. The effect of the external components on the feedback network requires R6A and R6B to be much smaller than would normally have been expected when using the twin-tee feedback scheme.

## LOW-NOISE PHOTODIODE AMPLIFIER

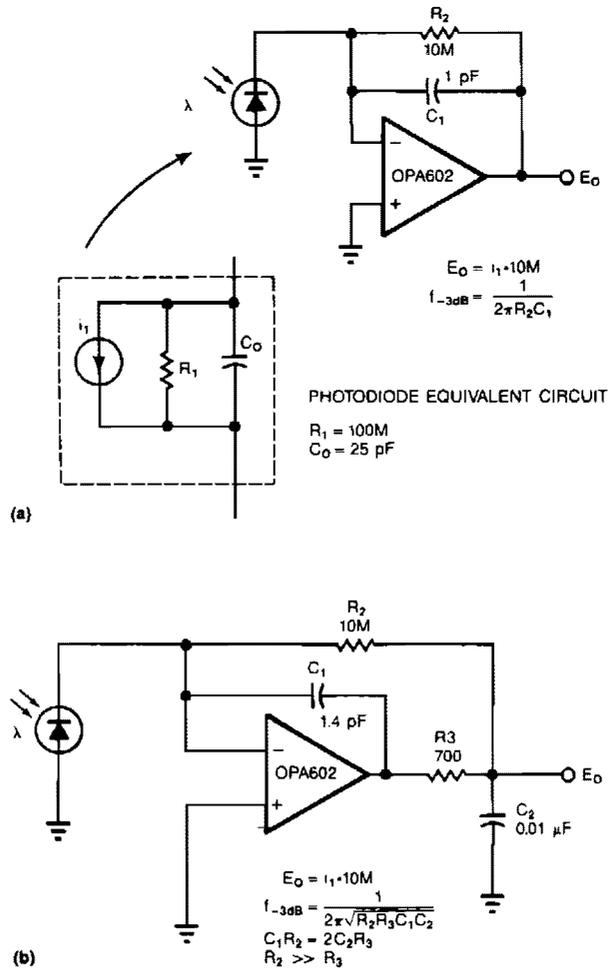


**Fig. 3-18**

Adding two passive components to a standard photodiode amplifier reduces noise. Without the modification, the shunt capacitance of the photodiode reacting with the relatively large feedback resistor of the transimpedance (current-to-voltage) amplifier, creates excessive noise gain.

The improved circuit, Fig. 3-18b, adds a second pole, formed by R3 and C2. The modifications reduce noise by a factor of 3. Because the pole is within the feedback loop, the amplifier maintains its low output impedance. If you place the pole outside the feedback loop, you have to add an additional buffer, which would increase noise and dc error.

The signal bandwidth of both circuits is 16 kHz. In the standard circuit (Fig. 3-18a), the 1-pF stray capacitance in the feedback loop forms a single 16-kHz pole. The improved circuit has the same bandwidth as the first, but exhibits a 2-pole response.
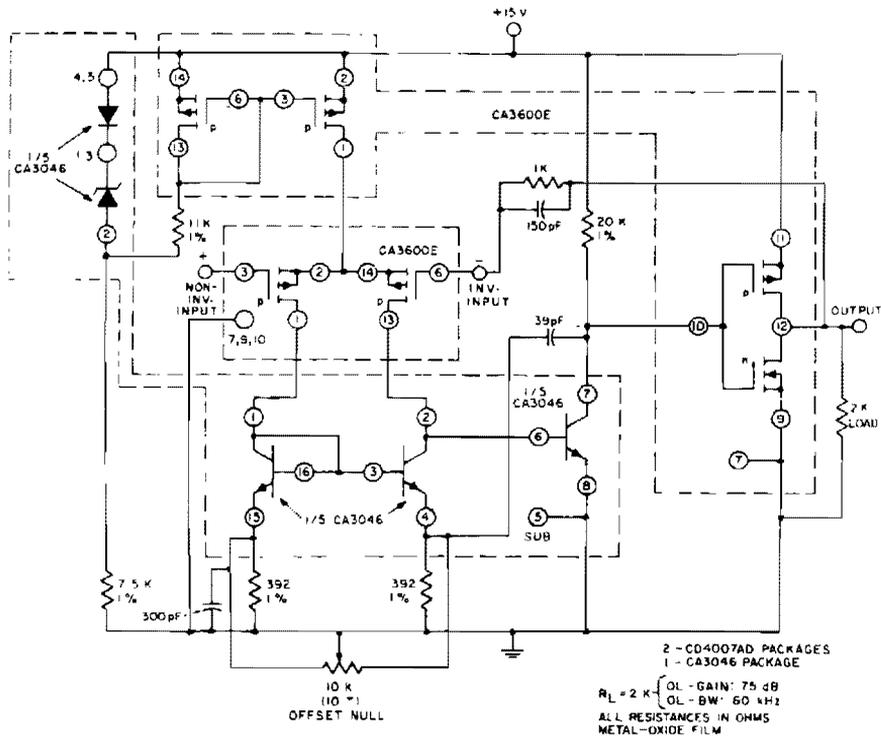
## VOLTAGE-FOLLOWER AMPLIFIER FOR SIGNAL-SUPPLY OPERATION




INTERSIL

Fig. 3-19


This unity-gain follower amplifier has a CMOS p-channel input, an npn second-gain stage, and a CMOS inverter output. The IC building blocks are two CA3600E's (CMOS transistor pairs) and a CA3046 npn transistor array. A zener-regulated leg provides bias for a 400- $\mu\text{A}$  p-channel source, feeding the input stage, which is terminated in an npn current mirror. The amplifier voltage-offset is nulled with the 10-K $\Omega$  balance potentiometer. The second-stage current level is established by the 20-K $\Omega$  load, and is selected to approximately the first-stage current level, to assure similar positive and negative slew rates. The CMOS inverter portion forms the final output stage and is terminated in a 2-K $\Omega$  load, a typical value used with monolithic op amps. Voltage gain is affected by the choice of load resistance value. The output stage of this amplifier is easily driven to within 1 mV of the negative supply voltage.

## CURRENT-SHUNT AMPLIFIER

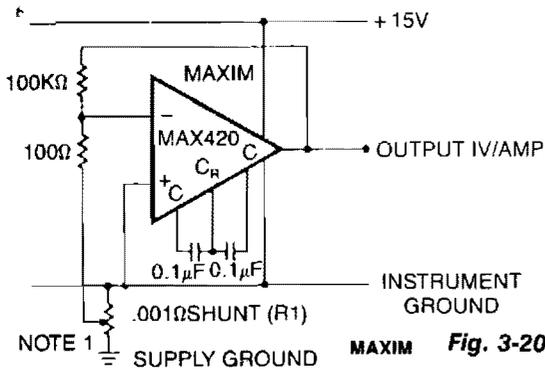

This circuit measures the power-supply current of a circuit without really having a current-shunt resistor: R1 is only 3 cm of #20 gauge copper wire. A length of the power distribution wiring can be used for R1. The MAX420's CMVR includes its own negative power supply; therefore, it can both be powered by and measure current in the ground line.

## CONSTANT-BANDWIDTH AMPLIFIER

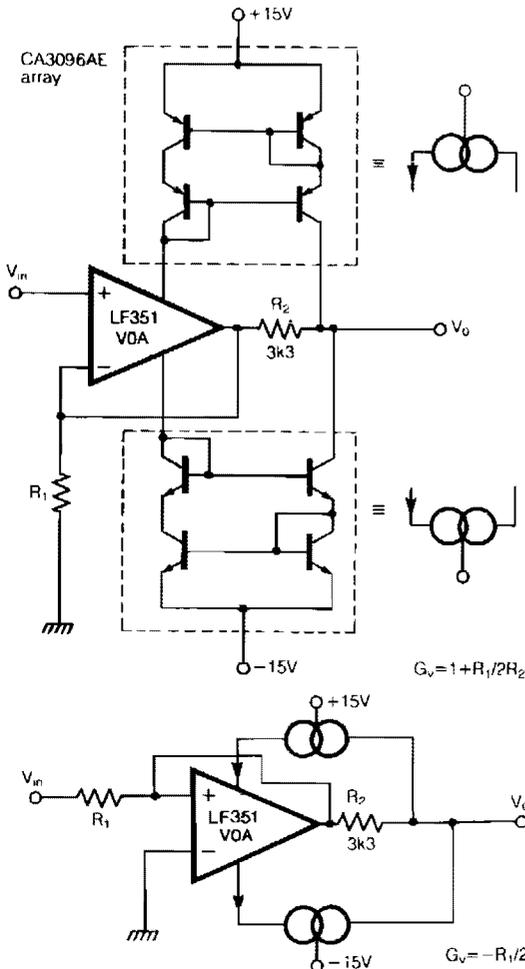

The traditional restriction of constant gain-bandwidth products for a voltage amplifier can be overcome by employing feedback around a current amplifier. Two current mirrors, constructed from transistors in a CA3096AE array, effectively turn the LF351 op amp into a current amplifier. Feedback is then applied by using R2 and R1, turning the whole circuit into a feedback voltage amplifier with a noninverting gain of  $G$  of  $1 + R_1/2R_2$ .

Using the values shown, a constant bandwidth of 3.5 MHz is obtained for all voltage gains up to and beyond 100 at 10 V pk-pk output, equivalent to a gain-bandwidth product of 350 MHz from an op amp with an advertised unity gain-bandwidth of 10 MHz. An inverting gain configuration is also possible (see Fig. 2) where  $G = R_1/2R_2$ . Slewing rates are significantly improved by this approach; even a 741 can manage 100 V  $\mu$ s under these conditions since its output is a virtual earth. However, because the new configurations use current feedback to achieve bandwidth independence, an output buffer should be added for circuits where a significant output current is required.

Fig. 3-21

ELECTRONIC ENGINEERING

# 4


## Analog-to-Digital Converters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Switched-Capacitor ADC  
Tracking ADC  
ADC  
Half-Flash ADC


## SWITCHED-CAPACITOR ADC

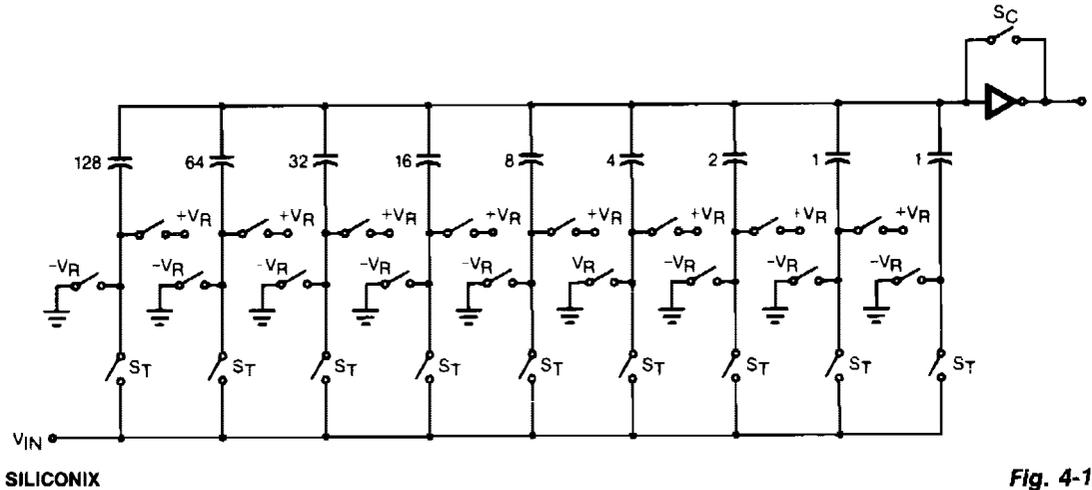

The CMOS comparator in the successive-approximation system determines each bit by examining the charge on a series of binary-weighted capacitors. In the first phase of the conversion process, the analog input is sampled by closing switch  $SC$  and all  $ST$  switches, and by simultaneously charging all the capacitors to the input voltage.

In the next phase of the conversion process, all  $ST$  and  $SC$  switches are opened and the comparator begins identifying bits by identifying the charge on each capacitor relative to the reference voltage. In the switching sequence, all 8 capacitors are examined separately until all 8 bits are identified, and then the charge-convert sequence is repeated. In the first step of the conversion phase, the comparator looks at the first capacitor (binary weight = 128). One pole of the capacitor is switched to the reference voltage, and the equivalent poles of all the other capacitors on the ladder are switched to ground. If the voltage at the summing node is greater than the trip point of the comparator—approximately  $1/2$  the reference voltage, a bit is placed in the output register, and the 128-weight capacitor is switched to ground. If the voltage at the summing node is less than the trip point of the comparator, this 128-weight capacitor remains connected to the reference input through the remainder of the capacitor-sampling (bit-counting) process. The process is repeated for the 64-weight capacitor, the 32-weight capacitor, and so forth down the line, until all bits are tested. With each step of the capacitor-sampling process, the initial charge is redistributed among the capacitors. The conversion process is successive-approximation, but relies on charge shifting rather than a successive-approximation register—and reference  $d/a$ —to count and weigh the bits from MSB to LSB.

## TRACKING ADC

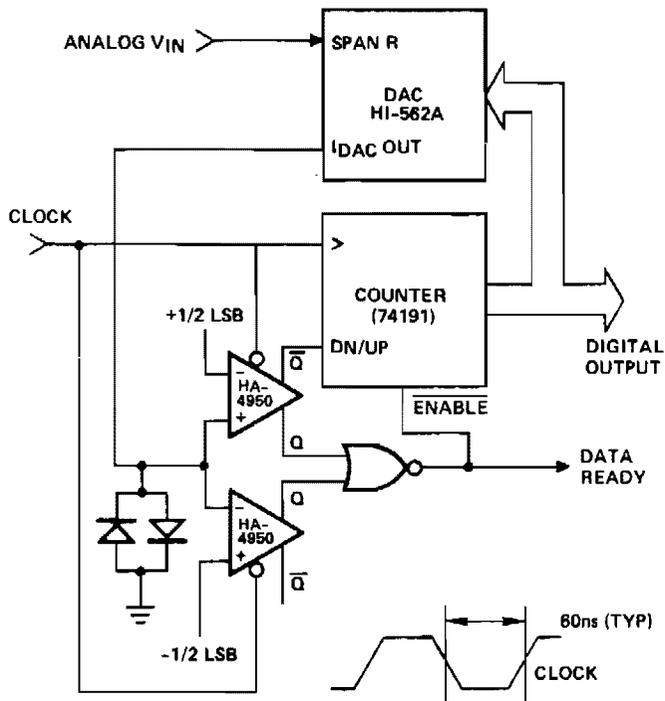


HARRIS

Fig. 4-2

The analog input is fed into the span resistor of a DAC. The analog input voltage range is selectable in the same way as the output voltage range of the DAC. The net current flow through the ladder termination resistance; i.e.,  $2\text{ K}\Omega$  for HI-562A; produces an error voltage at the DAC output. This error voltage is compared with  $\frac{1}{2}$  LSB by a comparator. When the error voltage is within  $\pm\frac{1}{2}$  LSB range, the  $Q$  output of the comparators are both low, which stops the counter and gives a data ready signal to indicate that the digital output is correct. If the error exceeds the  $\pm\frac{1}{2}$  LSB range, the counter is enabled and driven in an up or down direction depending on the polarity of the error voltage.


The digital output changes state only when there is a significant change in the analog input. When monitoring a slowly varying input, it is necessary to read the digital output only after a change has taken place. The data ready signal could be used to trigger a flip-flop to indicate the condition and reset it after readout. The main disadvantage of the tracking ADC is the time required to initially acquire a signal; for a 12-bit ADC, it could be up to 4096 clock periods. The input signal usually must be filtered so that its rate of change does not exceed the tracking range of the ADC—1 LSB per clock period.

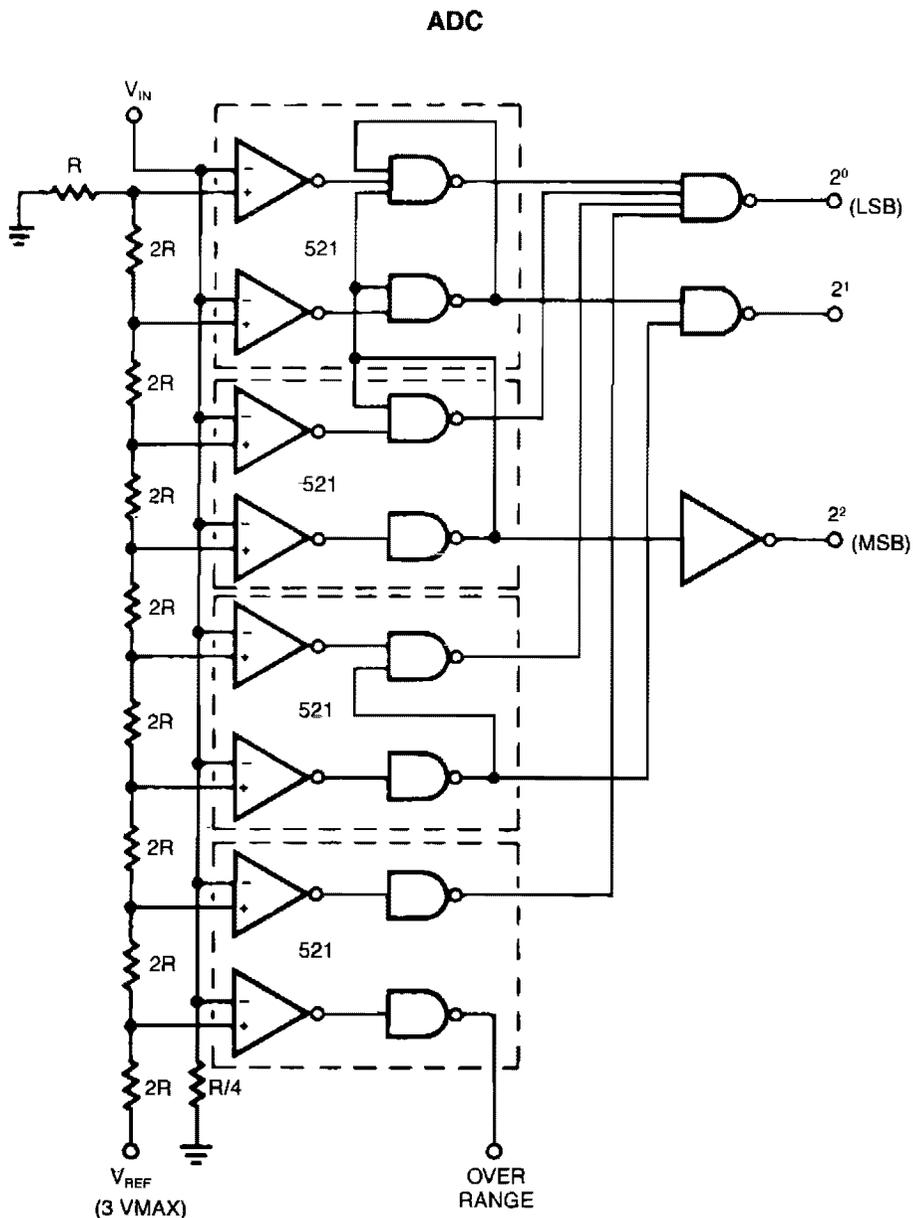

**SIGNETICS**

**Fig. 4-3**

Conversion speed of this design is the sum of the delay through the comparator and the decoding gates. Reference voltages for each bit are developed from a precision resistor ladder network. Values of  $R$  and  $2R$  are chosen so that the threshold is  $1/2$  of the least significant bit. This assures maximum accuracy of  $\pm 1/2$  bit. The individual strobe line and duality features of the NE521 greatly reduced the cost and complexity of the design.

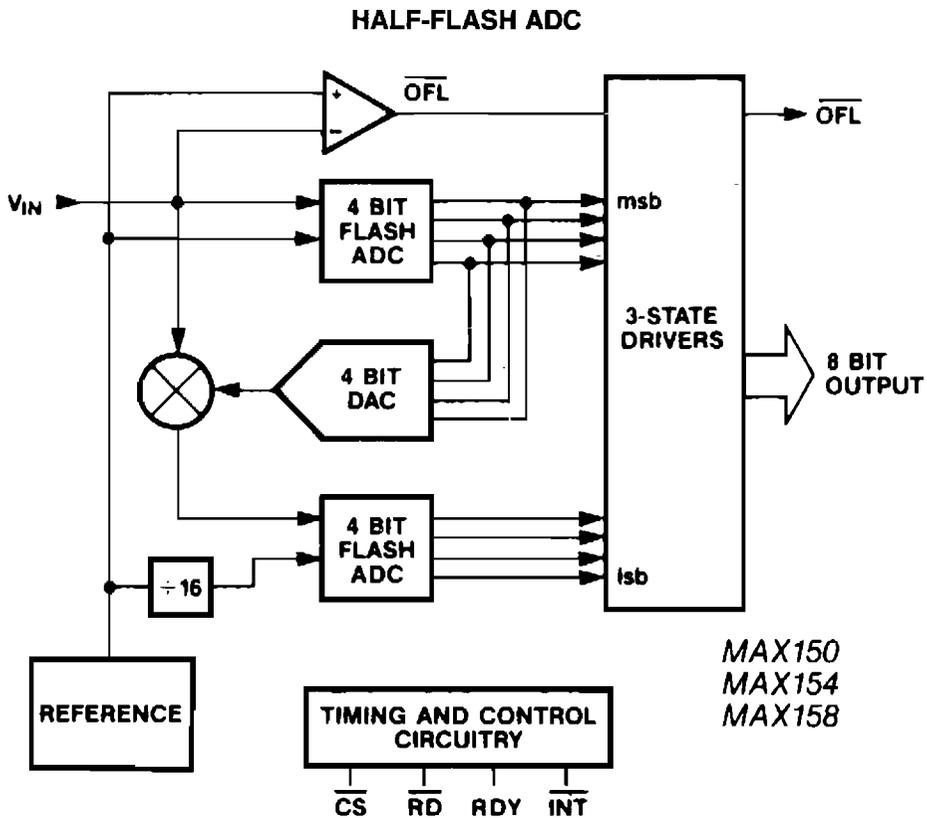

MAXIM

**Fig. 4-4**

An a/d conversion technique which combines some of the speed advantages of flash conversion with the circuitry savings of successive approximation is termed *half-flash*. In an 8-bit, half-flash converter, two 4-bit flash a/d sections are combined. The upper flash a/d compares the input signal to the reference and generates the upper 4 data bits. This data goes to an internal DAC, whose output is subtracted from the analog input. Then, the difference can be measured by the second flash a/d, which provides the lower 4 data bits.

# 5


## Annunciator

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Transformerless Tone Annunciator

## TRANSFORMERLESS TONE ANNUNCIATOR

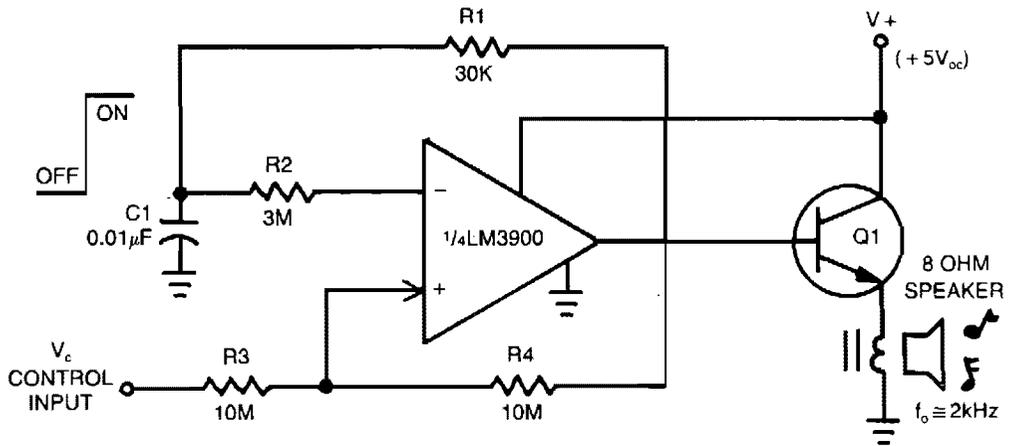

EDN

Fig. 5-1

This circuit does not require an output transformer or an output coupling capacitor; the annunciator can easily be turned on or off by a control input voltage driving a 10-M $\Omega$  input resistor,  $R3$ . For a smaller acoustic output, replace output transistor,  $Q1$ , with a 100- $\Omega$  resistor, while also raising the voice coil impedance to 100  $\Omega$ , to prevent loading of the IC.

# 6


## Attenuators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Digitally Programmable Attenuator  
Programmable Attenuator  
Voltage-Controlled Attenuator


## DIGITALLY PROGRAMMABLE ATTENUATOR

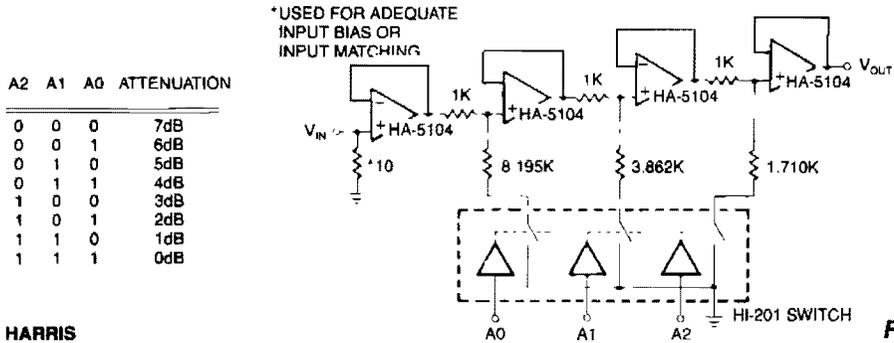

HARRIS

The first stage is a simple buffer used to isolate the signal source from the attenuator stages to follow. Each of the subsequent stages is preceded by a voltage divider formed by two resistors and CMOS switch. Provided that the CMOS switch for each stage is closed, the drive signal will be attenuated according to the basic voltage divider relationship at each stage. In the event a switch is open, nearly all of the signal strength will be passed to the next stage through the 1-KΩ resistor. The amplifiers act as buffers for divider networks and reduce the interaction between stages. Eight levels of attenuation are possible with the circuit as illustrated, but more stages could be added. Each divider network must be closely matched to the resistor ratios shown or the level of attenuation will not match the levels in the logic chart.

## PROGRAMMABLE ATTENUATOR

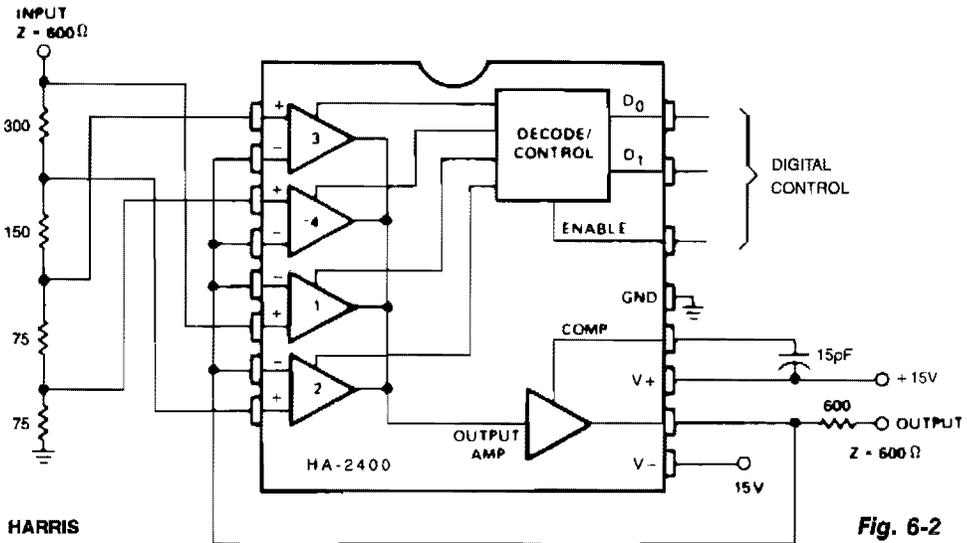

HARRIS

This circuit performs the function of dividing the input signal by a selected constant (1, 2, 4, 8, etc.). While T, Z, or L sections could be used in the input attenuator, this is not necessary since the amplifier loading is negligible and a constant input impedance is maintained. The circuit is thus much simpler and more accurate than the usual method of constructing a constant impedance ladder, and switching sections in and out with analog switches. Two identical circuits can be used to attenuate a balanced line.

## VOLTAGE-CONTROLLED ATTENUATOR

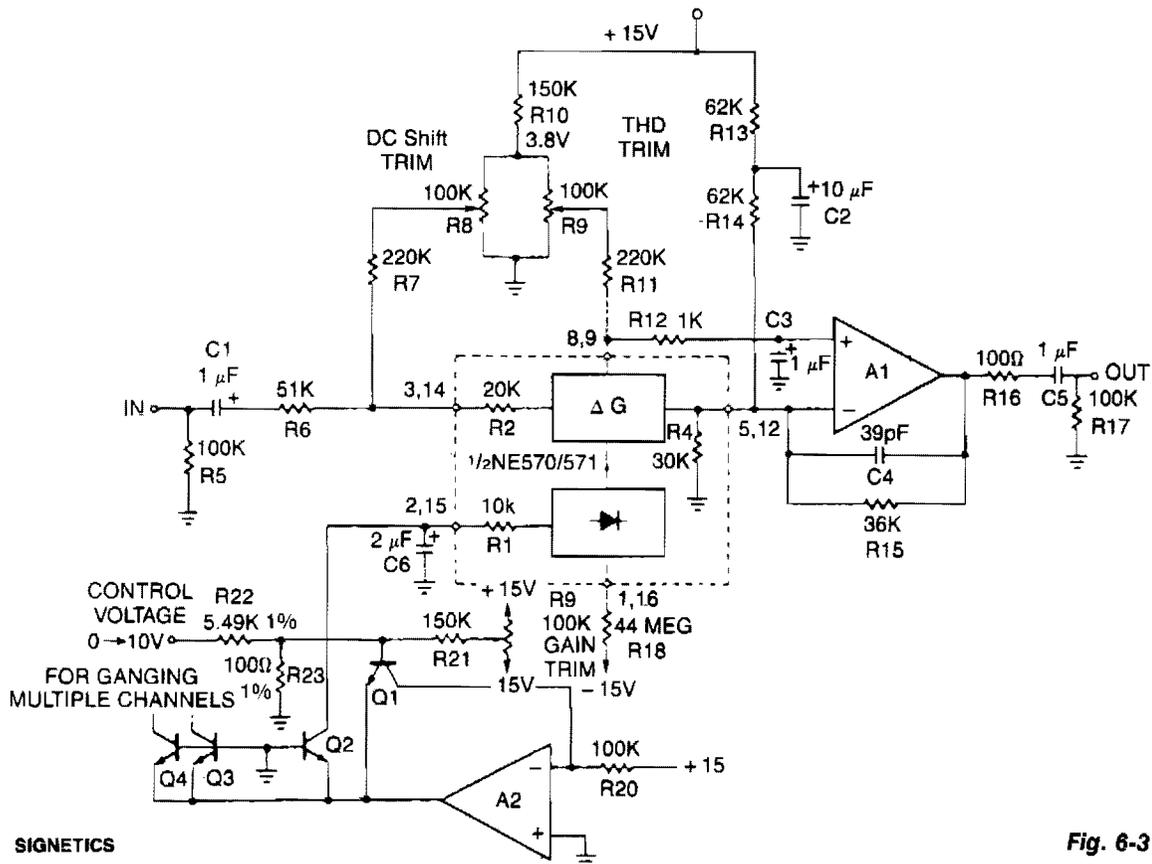


Fig. 6-3

This typical circuit uses an external op amp for better performance and an exponential converter to get a control characteristic of  $-6 \text{ dB/V}$ . Trim networks are shown to null out distortion and dc shift, and to fine trim the gain to  $0 \text{ dB}$  with  $0 \text{ V}$  of control voltage.

# 7


## Audio Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

AGC with Squelch Control	Magnetic Phono Preamplifier
Gain-Controlled Stereo Amplifier	RIAA Preamplifier
Microphone Amplifier	Professional Audio NAB Tape
Audio Circuit Bridge Load Drive	Playback Preamplifier
20-dB Audio Booster	Mini-Stereo
Micro-Size Amplifier	Speaker Amplifier for Hand-Held
Audio Amplifier	Transceivers
Line-Operated Amplifier	TV Audio Amplifier

## AGC WITH SQUELCH CONTROL

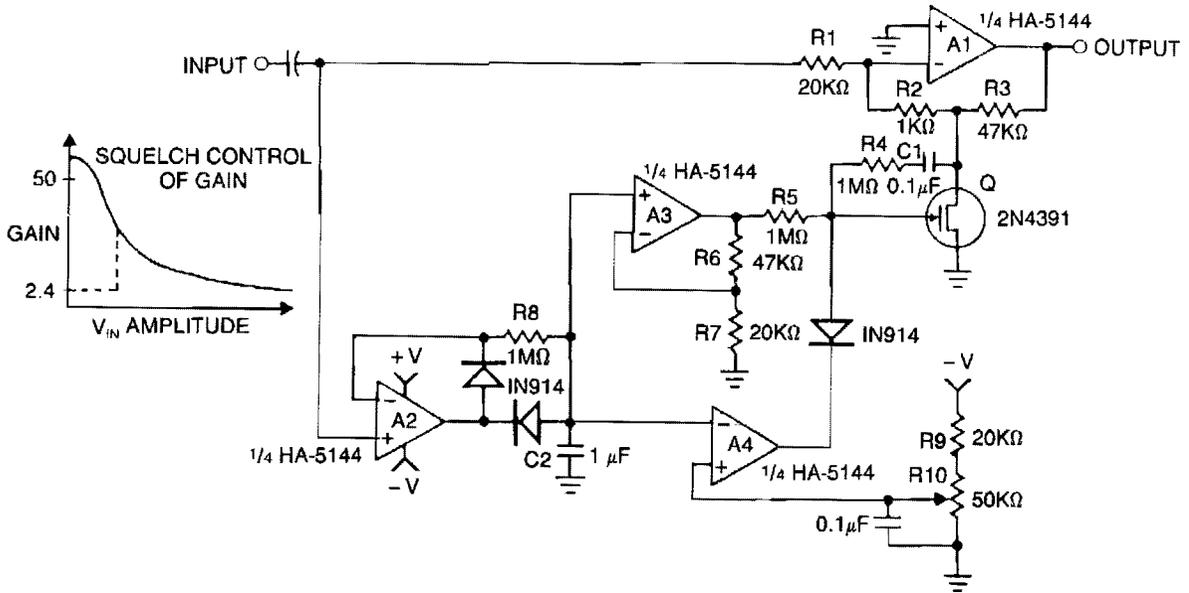


HARRIS

Fig. 7-1

Automatic gain control is a very useful feature in a number of audio amplifier circuits: tape recorders, telephone speaker phones, communication systems and PA systems. This circuit consists of a HA-5144 quad op amp and a FET transistor used as a voltage-controlled resistor to implement an AGC circuit with squelch control. The squelch function helps eliminate noise in communications systems when no signal is present and allows remote hands-free operation of tape recorder systems. Amplifier A1 is placed in an inverting-gain *T* configuration in order to provide a fairly wide gain range and a small signal level across the FET. The small signal level and the addition of resistors R5 and R6 help reduce nonlinearities and distortion. Amplifier A2 acts as a negative peak detector to keep track of signal amplitude. Amplifier A3 can be used to amplify this peak signal if the cutoff voltage of the FET is higher than desired. Amplifier A4 acts as a comparator in the squelch control section of the circuit. When the signal level falls below the voltage set by R10, the gate of the FET is pulled low—turning it off completely—and reducing the gain to 2.4. The output A4 can also be used as a control signal in applications, such as a hands-free tape recorder system.


## GAIN-CONTROLLED STEREO AMPLIFIER

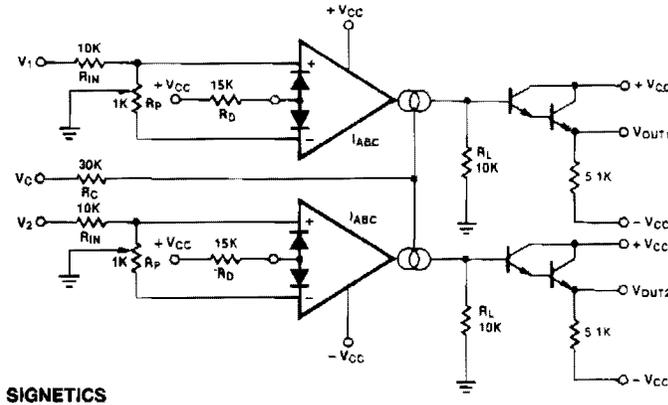

SIGNETICS

Fig. 7-2

## MICROPHONE AMPLIFIER

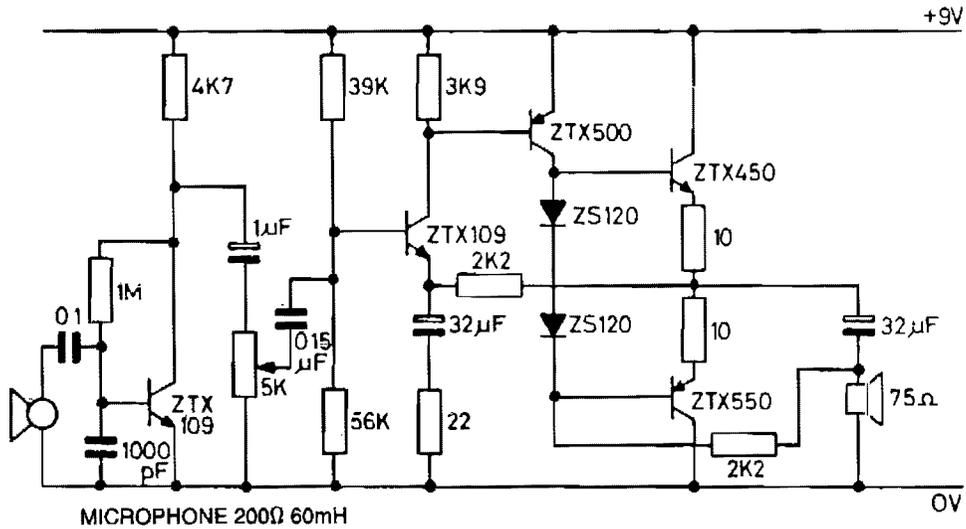

ZeTeX, formerly FERRANTI

Fig. 7-3

This circuit features the ZTX450/ZTX550 transistors in a push-pull output stage. The following readings were taken at maximum volume:

Input: 0.4 mV rms

Output: 1.8 V rms

Voltage gain: 4500


Max. output before distortion: 2.25 V rms – supply current = 3.5 mA

Zero output-supply current: 3.5 mA

Wattage: 0.034 W

Frequency response: 250 Hz to 28 kHz


## AUDIO CIRCUIT BRIDGE LOAD DRIVE

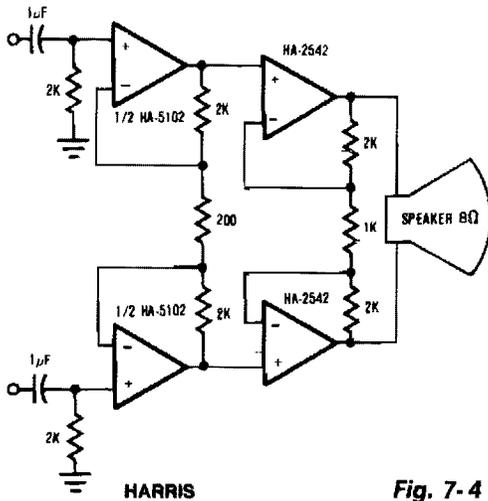

**Fig. 7-4**

This circuit shows a method which increases the power capability of a drive system for audio speakers. Two HA-2542s are used to operate on half cycles only, which greatly increases their power handling capability. Bridging the speaker, as shown, makes 200 mA of output current available to drive the load. The HA-5102 is used as an ac-coupled, low noise preamplifier, which drives the bridge circuit.


## 20-dB AUDIO BOOSTER

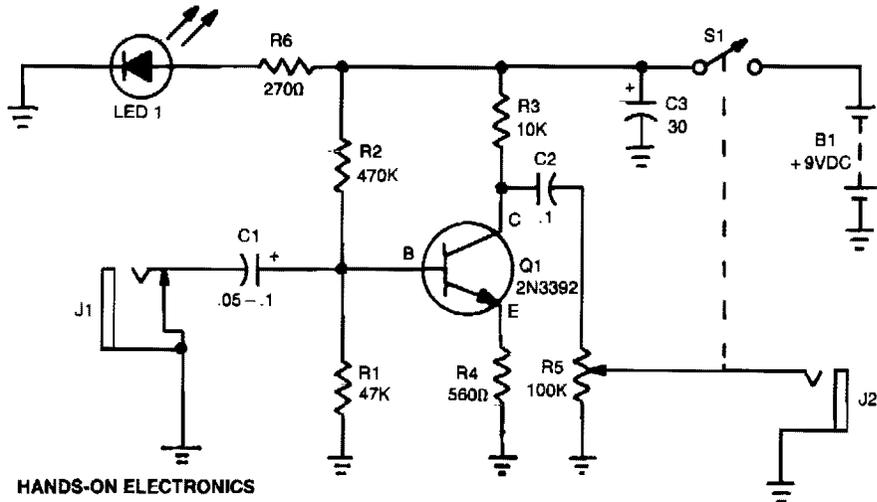

**Fig. 7-5**

The amplifier's gain is nominally 20 dB. Its frequency response is determined primarily by the value of just a few components—primarily C1 and R1. The values in the schematic diagram provide a response of  $\pm 3.0$  dB from about 120 to over 20,000 Hz. Actually, the frequency response is flat from about 170 to well over 20,000 Hz; it's the low end that deviates from a flat frequency response. The low end's rolloff is primarily a function of capacitor C1, since R1's resistive value is fixed. If C1's value is changed to 0.1  $\mu$ F, the low end's corner frequency—the frequency at which the low end rolloff starts—is reduced to about 70 Hz. If you need an even deeper low end rolloff, change C1 to a 1.0- $\mu$ F capacitor. If it's an electrolytic type, make certain that it's installed into the circuit with the correct polarity—with the positive terminal connected to Q1's base terminal.

## MICRO-SIZED AMPLIFIER

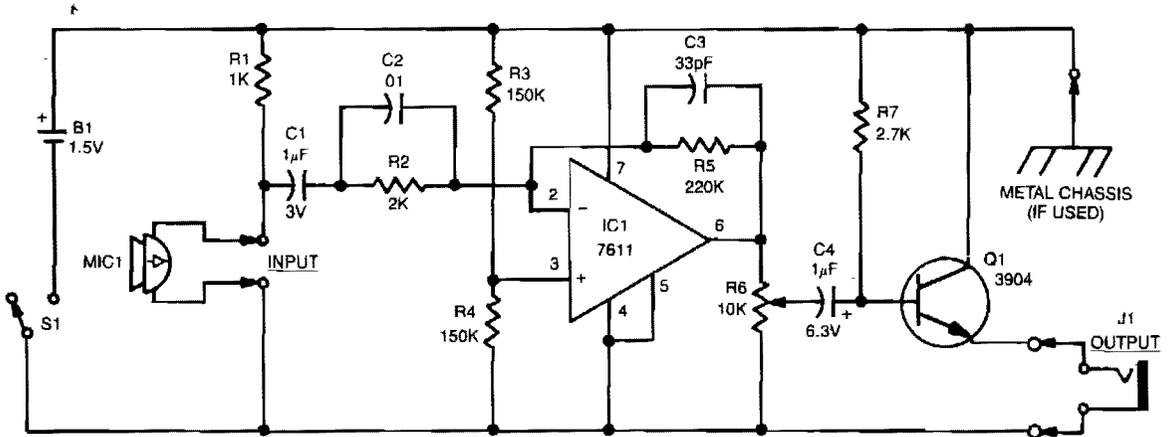


Reprinted with permission from Radio-Electronics Magazine, August 1988. Copyright Gernsback Publications, Inc., 1988.

Fig. 7-6

Sound detected by electret microphone MIC1 is fed to IC1's input through resistor R2, and capacitors C1 and C2. Resistors R2 and R5 determine the overall stage gain, while C2 partially determines the amplifier's frequency response. To ensure proper operation, use a single-ended power supply. R3 and R4 simulate a null condition equal to half the power supply's voltage at IC1's noninverting input. The output of IC1 is transferred to emitter-follower amplifier Q1 via volume control R6. The high-Z-in/low-Z-out characteristic of the emitter-follower matches the moderately high-impedance output of IC1 to a low-impedance headphone load.

## AUDIO AMPLIFIER

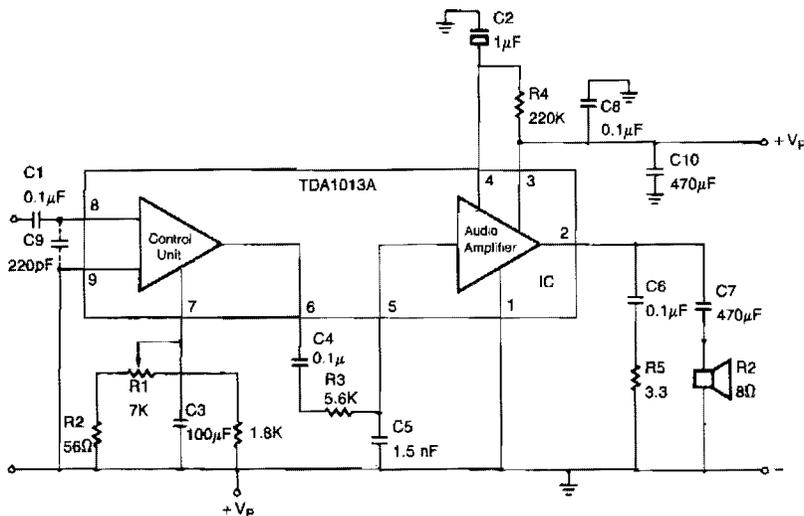


SIGNETICS

Fig. 7-7

C9 is necessary to filter-out rf input interferences. R3 in combination with C5 is used to limit the af frequency bandwidth. The 470-μF power supply decoupling capacitor is C10.

## LINE-OPERATED AMPLIFIER

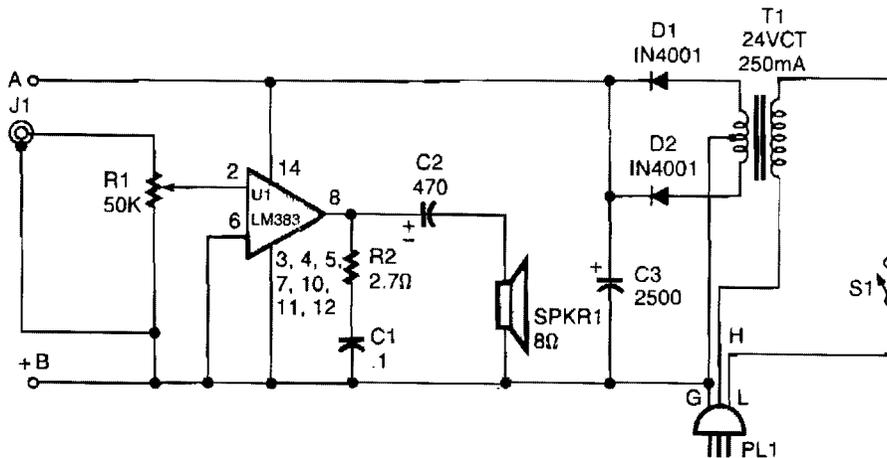


POPULAR ELECTRONICS

Fig. 7-8

T1 isolates the unit from the line, and has a 24-V, center-tapped secondary. The output of the transformer is rectified by diodes D1 and D2 and filtered by capacitor C3 to provide 15 to 18 Vdc. The LM383 has built-in protection against speaker shorts.

## MAGNETIC PHONO PREAMPLIFIER

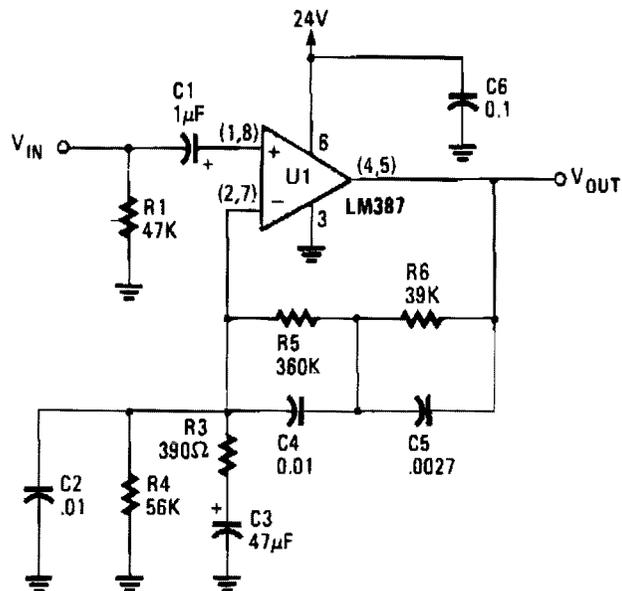

POPULAR ELECTRONICS

Fig. 7-9

### RIAA PREAMPLIFIER

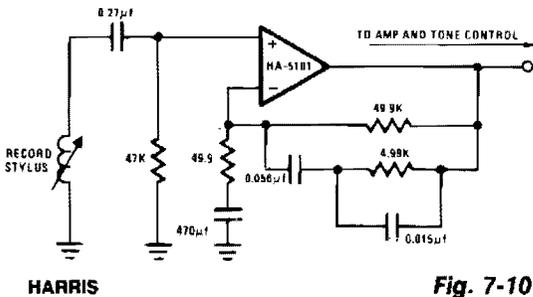


Fig. 7-10

The circuit essentially provides low-frequency boost below 318 Hz and high-frequency attenuation above 3150 Hz. Recent modifications to the response standard include a 31.5-Hz peak gain region to reduce dc-oriented distortion from external vibration.

### PROFESSIONAL AUDIO NAB TAPE PLAYBACK PREAMPLIFIER

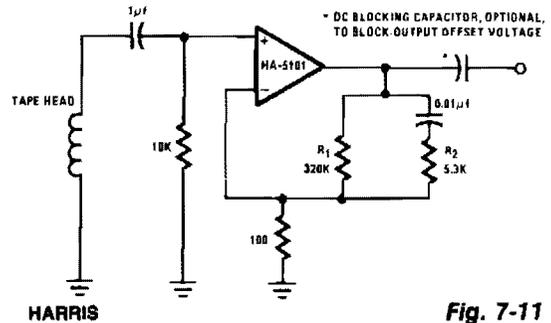


Fig. 7-11

The preamplifier is configured to provide low-frequency boost to 50 Hz, flat response to 3 kHz, and high-frequency attenuation above 3 kHz. Compensation for variations in tape and tape head performance can be achieved by trimming R1 and R2.

### MINI-STEREO


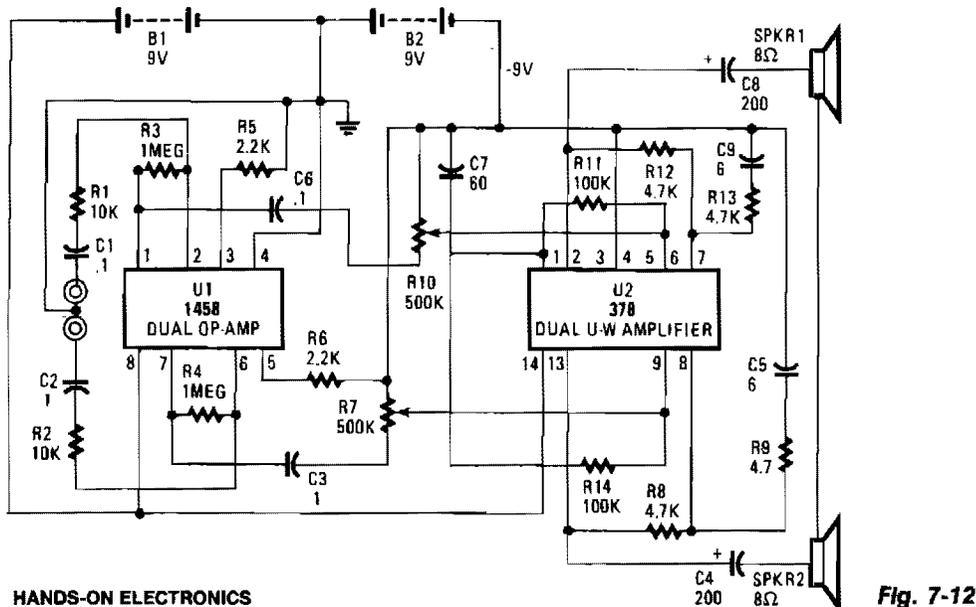


Fig. 7-12


This circuit is built around two chips: the MC1458 dual op amp, configured as a preamplifier, and the LM378 dual 4-watt amplifier. The gain of the preamp is given by  $R3/R1$  for one side and  $R4/R2$  for the other side, which is about 100. That gain can be varied by increasing the ratios. The left and right channel inputs are applied to pins 2 and 6. The left and right outputs of U1 at pins 7 and 2 are coupled through C5/R10 and C3/R6, respectively, to U2 to drive the two 8-Ω loudspeakers.
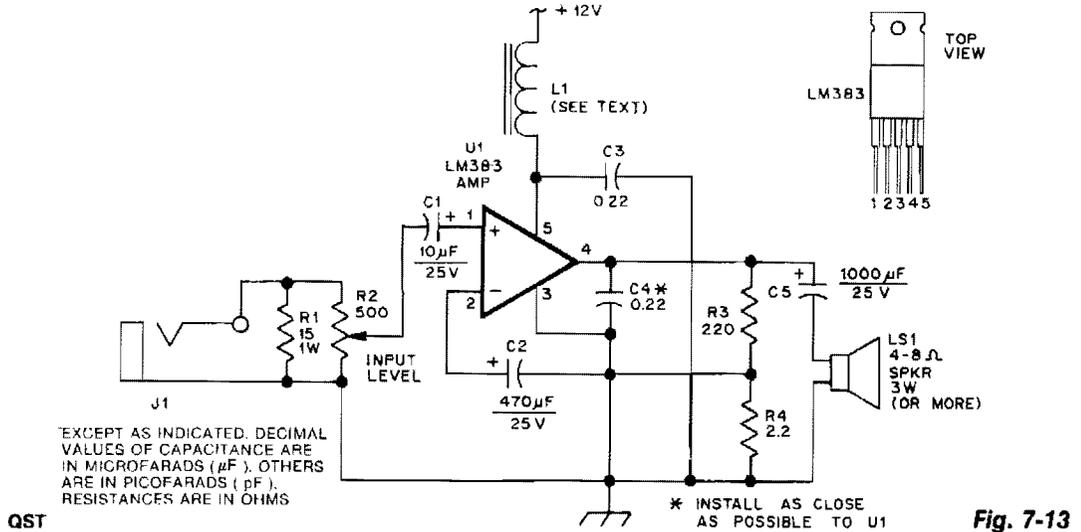
## SPEAKER AMPLIFIER FOR HAND-HELD TRANSCEIVERS



The LM383 is an audio-power amplifier that is capable of producing up to 8 W of audio output. R1 is essentially a load resistor for the hand-held transceiver's audio output. R2 can be composed of two fixed resistors in a 10:1 divider arrangement, but using a potentiometer makes it easy to set the amplifier's maximum gain. When powered from a vehicle's electrical system, the amplifier's +12V power source requires filter L1 to eliminate alternator whine. The LM383 can be mounted directly on the heatsink because the mounting tab is at ground potential.

## TV AUDIO AMPLIFIER

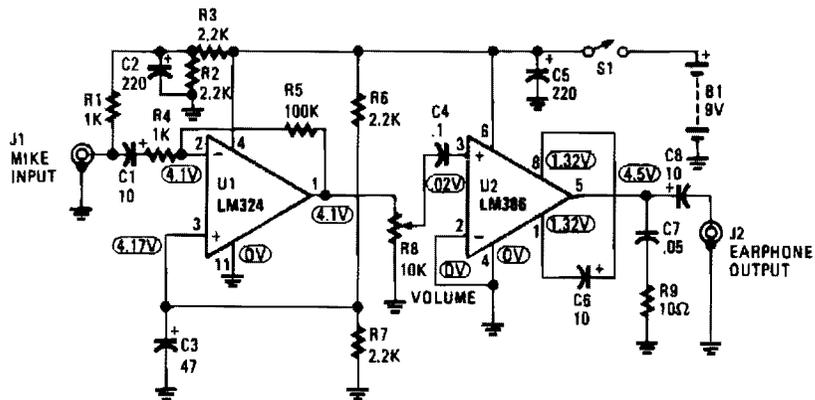

HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

Fig. 7-14

The amplifier picks up the TV's audio output signal and amplifies it to drive a set of earphones for private listening. It is built around an LM324 quad op amp and an LM386 low-power audio amplifier. The circuit uses an inexpensive electret microphone element as the pick-up and a set of earphones as the output device.

# 8


## Automotive Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Automobile Ignition Substitute	Tachometer with Set Point
Courtesy Light Delay Switch	Automobile Voltage Regulator
Lights-On Reminder	Directional Signals Monitor
Automobile Locator	Automatic Headlight Delay
Read-Head Preamplifier	Back-Up Beeper
Delayed Extra Brake Light	Electronic Car Horn
Digital Tach/Dwell Meter	Courtesy Light Extender
Automobile Air Conditioner	Flashing Third Brake Light
Smart Clutch	Headlight Alarm
Door Ajar Monitor	

## AUTOMOBILE IGNITION SUBSTITUTE

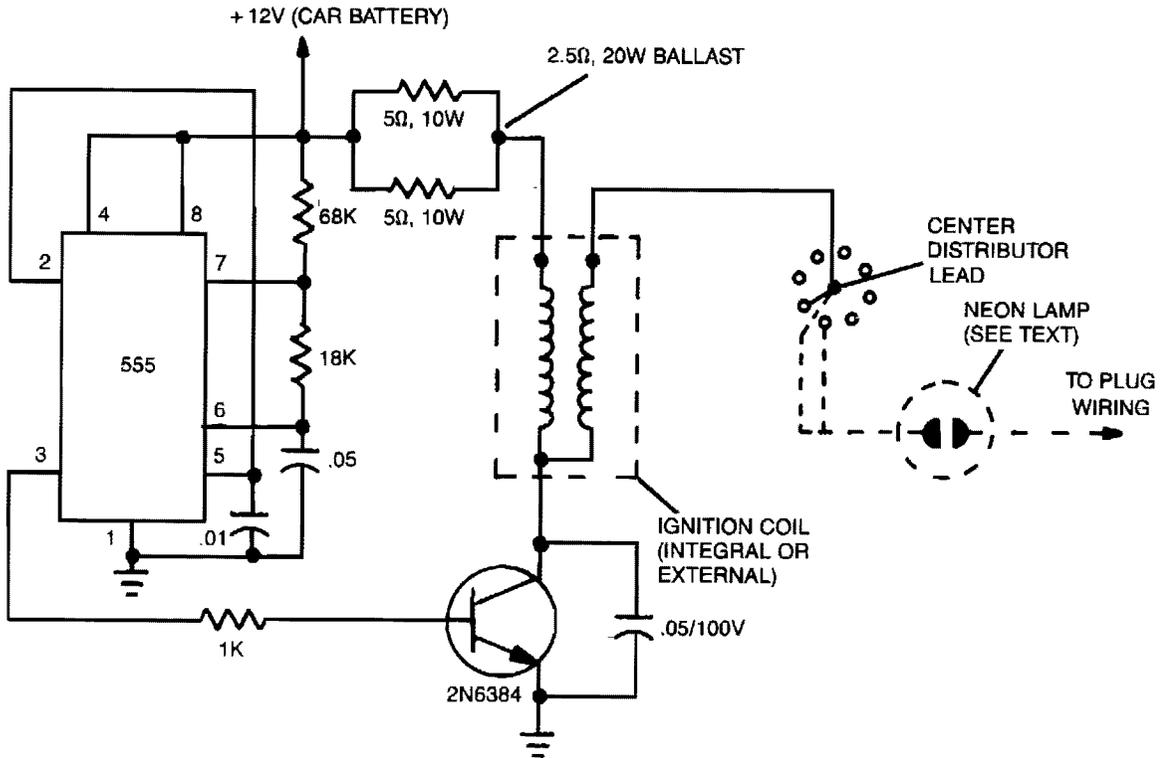

GERNSBACK PUBLICATIONS INC.

**Fig. 8-1**


The ignition substitute provides a constant power source for the ignition coil. Its frequency, 0.5–1.0 kHz, is that used by an 8-cylinder engine with an idling speed of 650 RPM, and the unit provides a rapid spark at a 17% duty cycle, while staying within the power dissipation limits of the components.

The circuit consists of a 555 timer IC configured as an astable free-running multivibrator that is used to drive a high-current npn transistor, such as a 2N6384. The transistor should be heavily heatsinked because it might be drawing several amps over quite a long period of time.

The coil ballast can be from 0.68 to 6.5  $\Omega$ , depending on what's available. The 2.5- $\Omega$ , 20-W ballast shown works well. All the other resistors can be either 1/4- or 1/2-W devices, and the capacitor, between pins 1 and 5 of the 555, can range from 0.01 to 0.05  $\mu\text{F}$ . Do not omit the 100-V, 0.05- $\mu\text{F}$  capacitor across the transistor; it prevents voltage spikes from damaging the device.

Although designed for an 8-cylinder engine, this device can be used with other types. In addition, a neon bulb can be added to the circuit to verify the presence of a spark.

### COURTESY LIGHT DELAY SWITCH

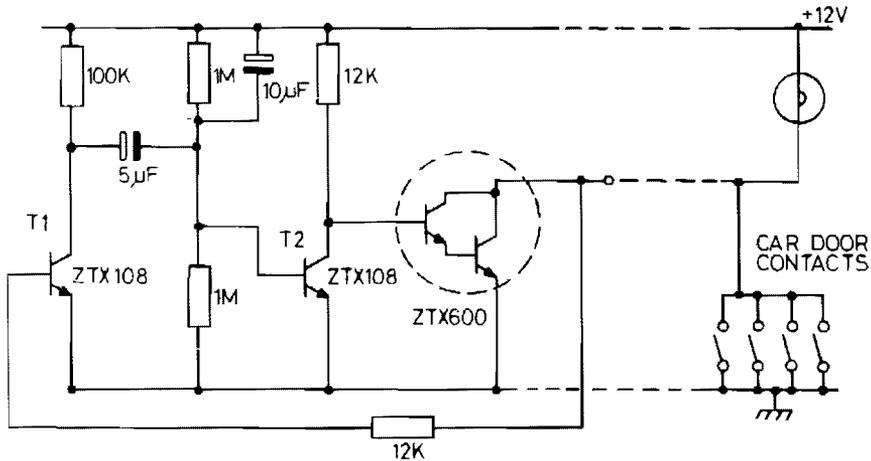


ZeTeX, formerly FERRANTI

Fig. 8-2

This circuit holds on the internal light for approximately one minute after the car doors are closed. When the door contacts open, a + VE pulse is applied to the base of T1. This transistor turns on, turning off T2 and charging the 10- $\mu$ F capacitor. T3 turns on, holding on the internal light. The capacitor takes one minute to discharge when the circuit reverts to its original state.

### LIGHTS-ON REMINDER

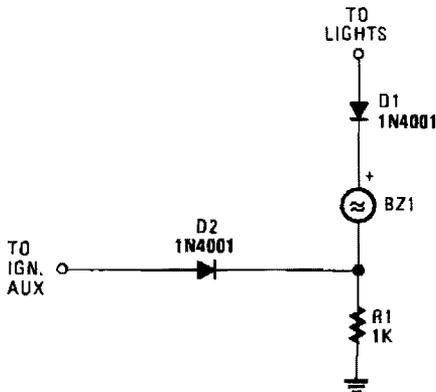


With both the ignition and the car lights on, piezo transducer BZ1 draws no current and remains silent. With only the ignition on, diode D1 is reverse-biased and so prevents current flow through BZ1.

However, when the lights are on and the ignition is off, the transducer becomes energized and sounds to alert you to turn the lights off. With the ignition off and the lights on, D2 is reverse-biased, preventing current from flowing to the ignition. Resistor R1 prevents a short circuit when the ignition is on.


POPULAR ELECTRONICS

Fig. 8-3

## AUTOMOBILE LOCATER

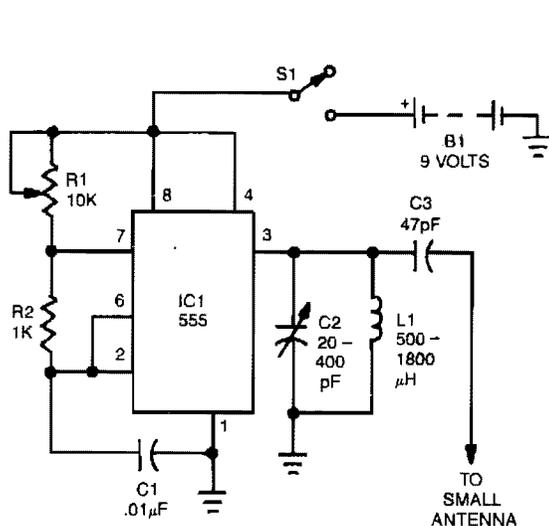

**Fig. 8-4a**

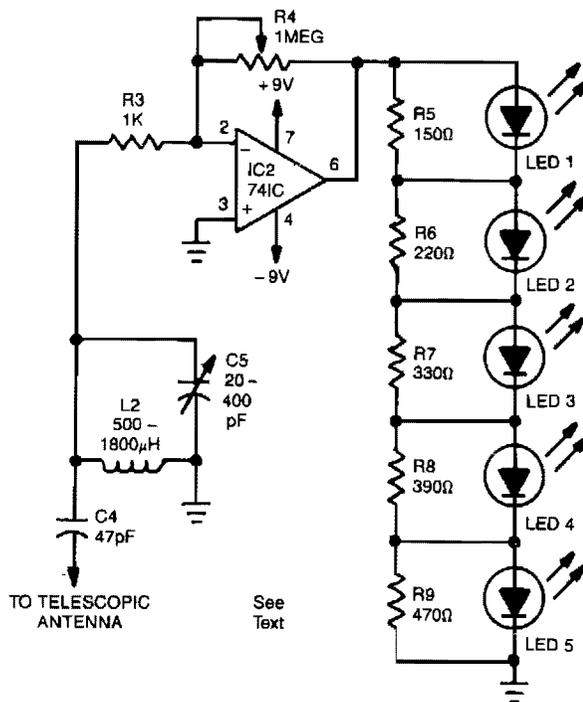


**Fig. 8-4b**

**GERNSBACK PUBLICATIONS INC.**

This locator is made up of two parts. The first is an rf oscillator, whose circuit is shown in Fig. 8-4a. The second is a sensitive receiver shown in Fig. 8-4b. The heart of the oscillator is a 555 timer IC. Tank circuit C2 and L1 is used to tune the transmitter. The antenna is coupled to the transmitter through C3. A telescopic antenna or a length of hookup wire will work quite well. At the receiver, the incoming signal is tuned by C5 and L2 before being passed on to the 741 IC. The five LEDs are used to indicate signal strength, they light up in order (1 to 5) as the signal gets stronger.

After the devices are built, the receiver and transmitter will need to be tuned. Tune the transmitter until all of the receiver's LEDs light. Separate the receiver and the transmitter—the farther apart they are the better—and adjust R4 until you get a maximum strength reading only when the receiver's antenna is pointed directly at the transmitter. Place the transmitter on the dashboard and completely extend the antenna. To find your car, just extend the telescope antenna to its full length and hold it parallel to the ground. Point the antenna to your far left, then swing it to your far right. Do that until you find in which direction the strongest signal lies, as indicated by the LEDs. The antenna will be pointing at your car.

## READ-HEAD PREAMPLIFIER

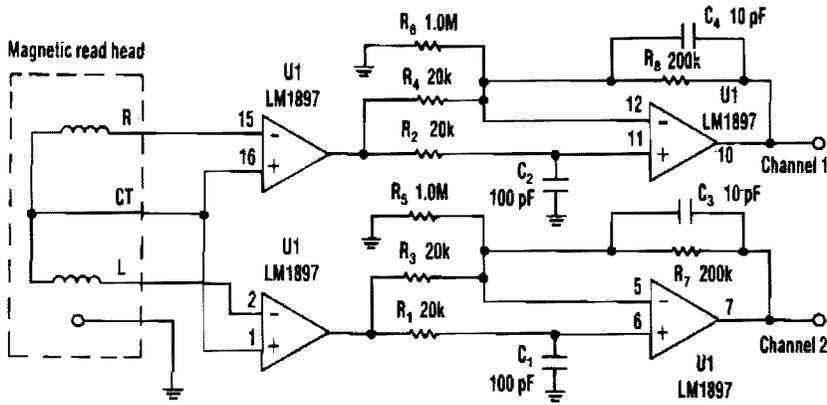


ELECTRONIC DESIGN

Fig. 8-5

Choosing dc rather than ac coupling can reduce much of the noise associated with preamplifiers for a magnetic reading head, particularly in the low frequencies. The LM1897 eliminates the need for the capacitor that usually ac couples the read head to the preamplifier input. The read head itself has a small resistance, typically  $50 \Omega$ , and so is less prone to noise pickup. Moreover, the LM1897 has a low-bias current; merely  $2 \mu A$  as a worst case. Such a low-bias current flowing through the head's low resistance generates very little noise. Accordingly, even with a gain of 25, the first stage of the preamplifier circuit produces little noise.

## DELAYED EXTRA BRAKE LIGHT

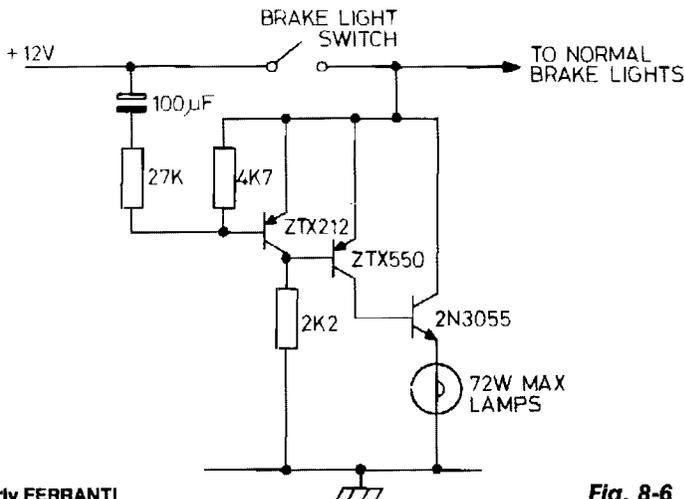


ZeTeX, formerly FERRANTI

Fig. 8-6

Operating the brake pedal of the car brings on the normal brake lights and then, after a delay, the extra lights are turned on. A bimetal strip in series with the lights would make them flash.

## DIGITAL TACH/DWELL METER

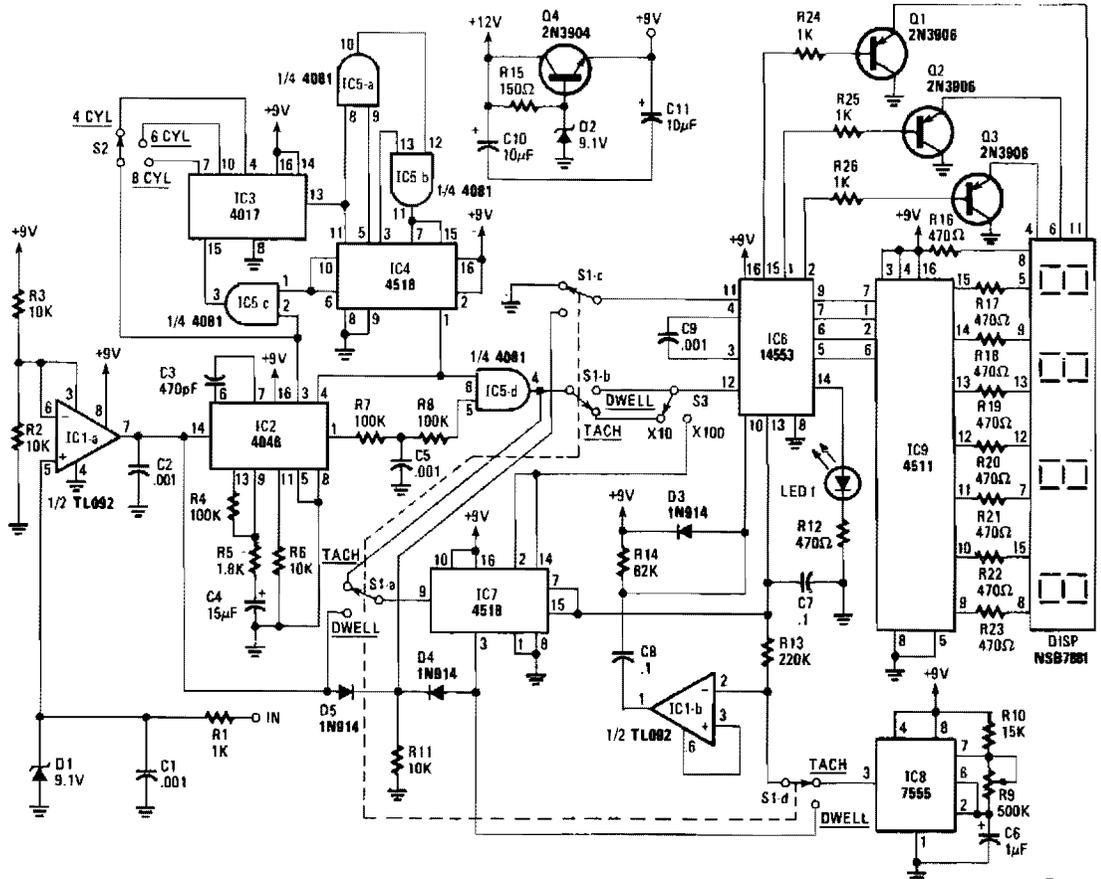


Reprinted with permission from Radio-Electronics Magazine, July 1985. Copyright Gernsback Publications, Inc., 1985.

**Fig. 8-7**

The heart of the circuit is IC2, a 4046 micropower phase-locked loop (PLL). The incoming signals are fed to the PLL after being buffered by IC1a and its associated components. The frequency of the incoming signal is multiplied by either 90, 60, or 45, depending on the setting of the cylinder select switch, S2. That switch selects the proper output from counters IC3 and IC4, which are set to divide the output frequency of the PLL by those amounts, and then send the divided output back to the comparator to the PLL to keep it locked on to the input signal. The phase pulses output at pin 4 of IC2, then go through an AND gate IC5d—which only passes the signals if the PLL is locked on to an input signal, preventing stray readings—and then to the input of IC6. When in the tach mode, IC6 counts the number of pulses present at pin 12, during the timing interval generated by IC8 and the associated circuitry of IC1b. Because of the varied multiplication rate for the different cylinder selections—90, 60, and 45 for 4, 6, and 8 cylinders, respectively, the time interval is always constant at  $\frac{1}{3}$  of a second. The time interval is adjusted with R9, a 500-K $\Omega$  potentiometer; it is the only adjustment in the circuit.

In the high-tach (TACH 1 or  $\times 100$ ) range of 0–9990 rpm, the output of IC2 is routed by switches S1a and S3 through IC7, a divide-by-ten counter, which increases the count range tenfold. In the low-tach (TACH 2 or  $\times 10$ ) range of 0–999 rpm, the counter is bypassed.
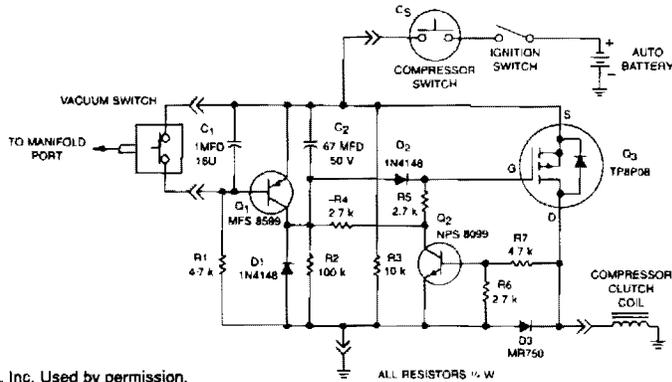
## AUTOMOBILE AIR CONDITIONER SMART CLUTCH




Copyright of Motorola, Inc. Used by permission.

**Fig. 8-8**

This circuit disables the air conditioner compressor when additional engine power is required. It does so by monitoring the engine vacuum at the intake manifold. If the vacuum drops to 40% of its normal level, the compressor clutch is disabled, removing the air conditioner load from the engine. After the engine returns to normal vacuum level, there is a 6 second delay before the compressor clutch is enabled and the air conditioner is reactivated. This allows 6 seconds of extra power, about 500 ft at 60 MPH, which increases the safety margin when passing another vehicle. Loss of cooling is minimal because the air conditioner fan is not interrupted. When the engine is accelerated, manifold vacuum drops and vacuum switch VS opens to 40% of the normal manifold pressure. This causes Q1 to turn on, discharging C2 and turning off Q3 via diode D2. When Q3 turns off, so does Q2. When the engine reaches its normal operating vacuum, VS closes and Q1 turns off, allowing C2 to charge for 6 seconds until Q3 turns on again.


## DOOR AJAR MONITOR

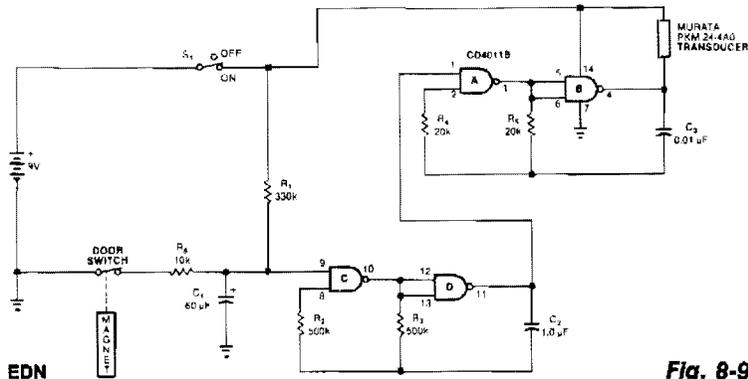

**Fig. 8-9**

The monitor senses an ajar door and, if the situation isn't corrected within 20 seconds, sounds a beeping alarm. The circuit is controlled by a magnetic reed switch and magnet on the door. With the door closed, the switch is closed and the alarm is disarmed. Opening the door opens switch, C1 starts charging up through R1. Approximately 20 seconds later, the voltage at pin 9 is high enough to turn on the oscillator formed from C, D, R2, R3, and C2. That pulses the piezoelectric transducer's 3-kHz oscillator. For lower standby drain on the battery, change R1 to 66 M $\Omega$  and C1 to 1 mF (film).

## TACHOMETER WITH SET POINT

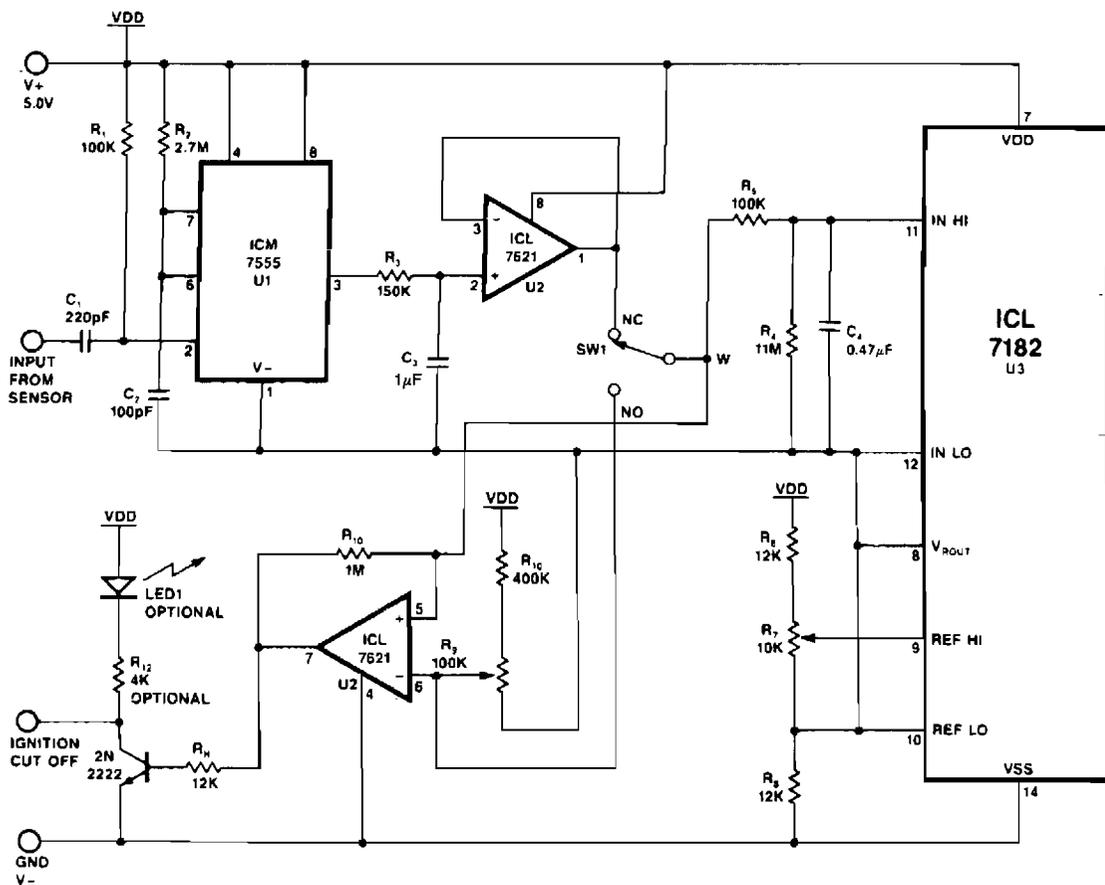

$$\frac{V_O}{V_{IN}} = \frac{1/RC}{S + 1/R_3C_3}$$

$$f_c = \frac{1}{2\pi R_3C_3}$$

SW1 Momentary  
Switch SPST

$V_{IN} = 264 \text{ mV @ 5000 RPM}$   
4 Stroke VB


RPM	Hz	Period
600	10	100 ms
1000	16.7	60 ms
5000	83	12 ms
10,000	166.7	6 ms

No. of Cylinders	Events Per Cycle	Strokes Per Cycle
1	0.5	4
4	2	4
6	3	4
8	4	4

INTERSIL

Fig. 8-10

## AUTOMOBILE VOLTAGE REGULATOR

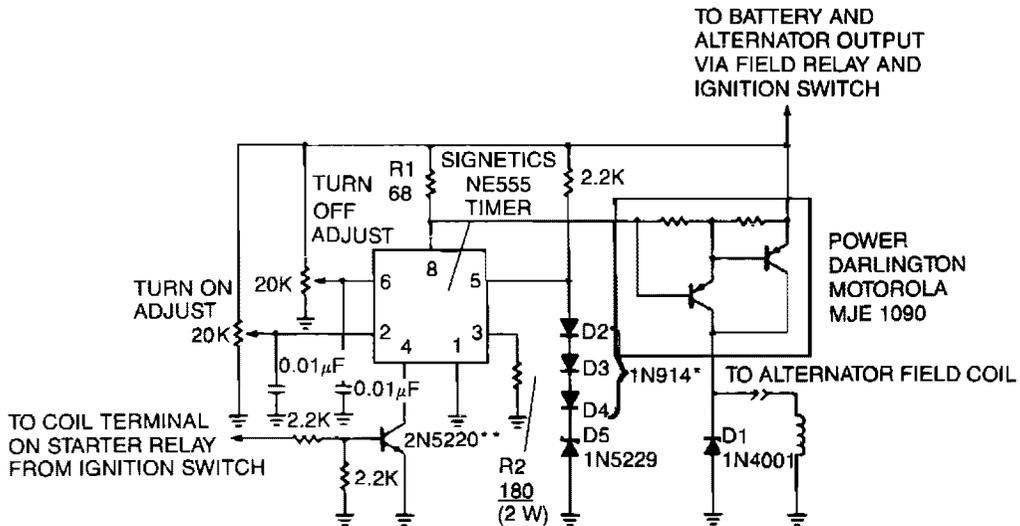

**NOTES:**


- \* Can be any general purpose Silicon diode or 1N4157 device.
  - \*\*Can be any general purpose Silicon transistor.
- All resistor values are in ohms.

**SIGNETICS**

**Fig. 8-11**

A monolithic 555-type timer is the heart of this simple automobile voltage regulator. When the timer is off so that its output at pin 3 is low, the power Darlington transistor pair is off. If battery voltage becomes too low, less than 14.4 V in this case, the timer turns on and the Darlington pair conducts.

## DIRECTIONAL SIGNALS MONITOR

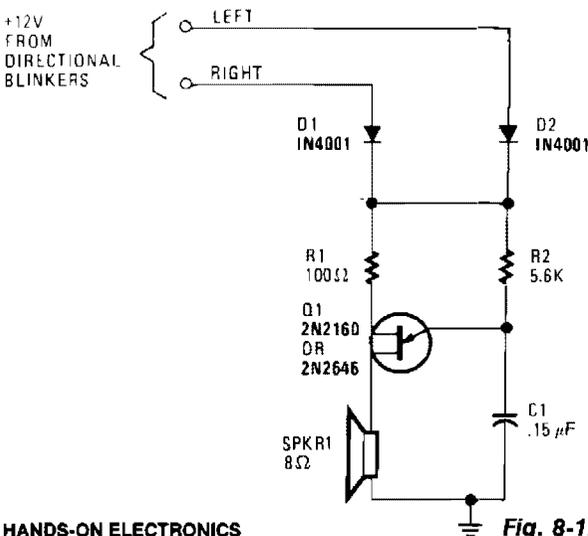


A unijunction transistor audio oscillator drives a small speaker. The oscillator's frequency is determined by resistor R2 and capacitor C2. The operating voltage is supplied from the car's turn-signal circuit(s) through D1 and D2. The diodes conduct current from the blinker circuit that is energized, and prevent stray current flow to the other blinker circuit.

**Fig. 8-12**

**HANDS-ON ELECTRONICS**

## AUTOMATIC HEADLIGHT DELAY

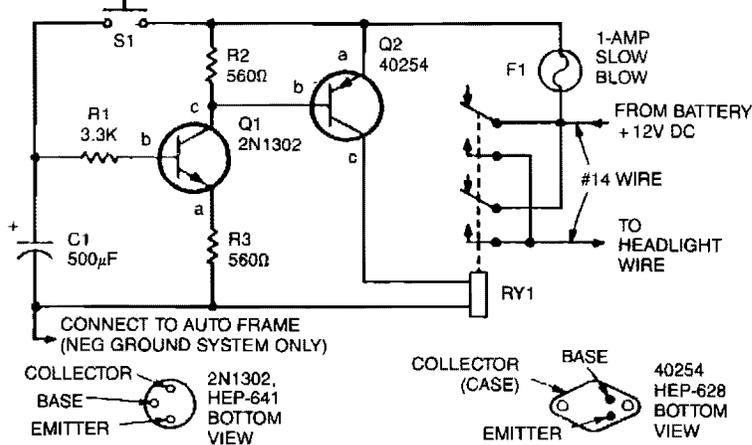

- C1—500  $\mu$ F electrolytic capacitor, 15 VDC or better  
 Q1—NPN transistor, 2N1302, HEP-641  
 Q2—PNP transistor, RCA 40254, HEP-628  
 R1—3,300-ohm, 1/2-watt resistor  
 R2, R3—560-ohm, 1/2-watt resistor  
 RY1—Relay, DPDT, 10-amp contacts, 12 VDC coil resistance at least 100-ohms, Potter and Brumfield type MR11D or equiv.


- S1—SPST pushbutton switch, normally open (time-start switch)  
 Misc—3 1/4-in.  $\times$  2 1/8-in.  $\times$  1 5/8-in. case, 1-amp SB fuse with pigtail leads, #14 wire, hook-up wire, printed circuit material, hardware, solder, etc.

TAB BOOKS

Fig. 8-13

When the driver depresses pushbutton switch S1, timing capacitor C1 charges to 12 V and turns on transistor Q1, which drives power transistor Q2 into conduction. This, in turn, energizes the relay which has its contacts connected in parallel with the headlight switch. The relay will stay energized until C1 discharges to the Q1 turn-off level. The lights-on period is determined by the value of C1, R1, and the characteristics of transistor Q1. With values chosen on the schematic, about 60 light-on seconds are provided.

## BACK-UP BEEPER

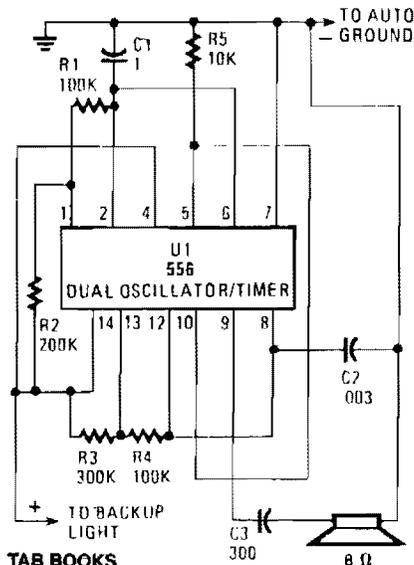


TAB BOOKS

Fig. 8-14

Put the car in reverse and the circuit provides a loud, audible beep at the rate of about one per second (1 Hz). Half of U1, a 556 dual oscillator/timer, is used as a slow-pulse oscillator with a rate of about 1 Hz. Components R2, R1, and C1 form the long time constant. You can calculate on time by  $t = .7 (R1 + R2) C1$  or 1.15 seconds. The off time is shorter than the on time, at .77 second. Enabling pin 4 (reset) is held high to keep the oscillator free-running when voltage is applied to pin 14. The output at pin 5 is coupled to pin 10 of U1 enabling oscillator 2. Oscillator 2 of U1 produces an audio output of about 1 kHz, as determined by C2, R3, and R4. Pin 10 (reset) of oscillator 2 is connected to the pin 5 output of oscillator 1. So when pin 5 becomes positive, the oscillator beeps a short pulsed tone of 1 kHz.

## ELECTRONIC CAR HORN

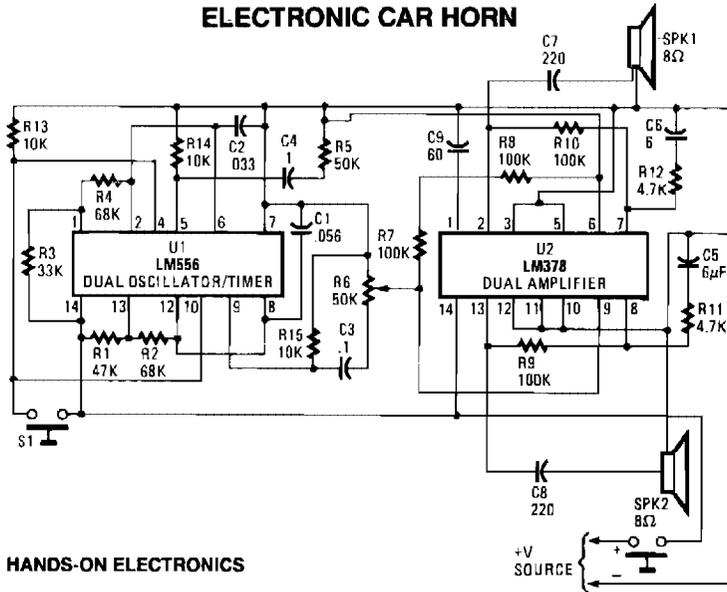


HANDS-ON ELECTRONICS

**Fig. 8-15**

An LM556 dual oscillator/timer, U1, configured as a two-tone oscillator drives U2, a dual 4-watt amplifier. One of the oscillators, pins 1 to 6, contained in U1 produces the upper frequency signal of about 200 Hz, while the second oscillator, pins 8 to 13, provides the lower frequency signal of about 140 Hz. Increase or decrease the frequencies by changing the values of C2 and C3. U1's outputs, pins 9 and 5, are connected to separate potentiometers to provide control over volume and balance. Each half of U2 produces 4 W of audio that is delivered to two 8-Ω loudspeakers via capacitors C7 and C8.

## COURTESY LIGHT EXTENDER

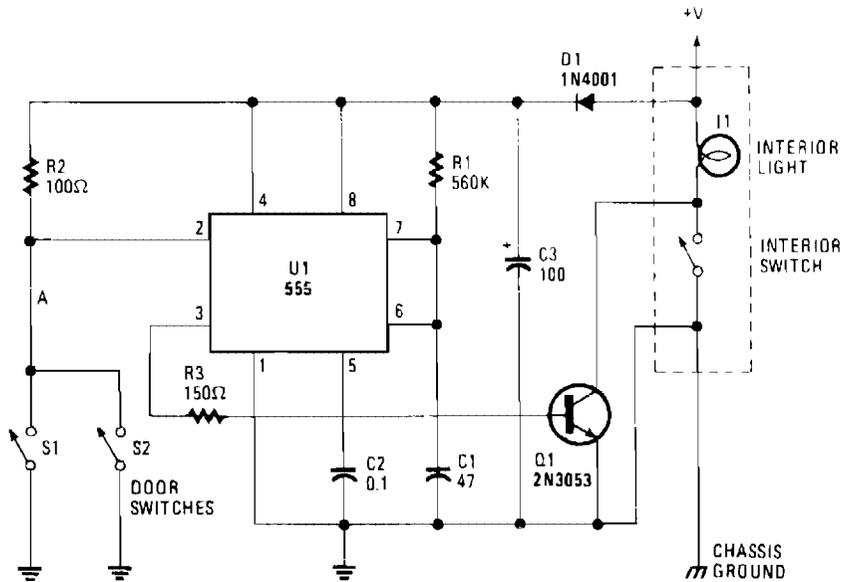


HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

**Fig. 8-16**

## COURTESY LIGHT EXTENDER (Cont.)

The circuit keeps the courtesy light on for 30 seconds after you close the door. The lead from the door switch is removed and connected to the 555 circuit. The 555 is arranged in a monostable mode, and is triggered by the door switches. The output drives Q1, which is connected across the interior light switch. The interior light is turned on for 30 seconds after the door is opened. If the door(s) are held open for longer than 30 seconds, it will not reset until after the doors are closed. In that case, the lights go out immediately.

## FLASHING THIRD BRAKE LIGHT

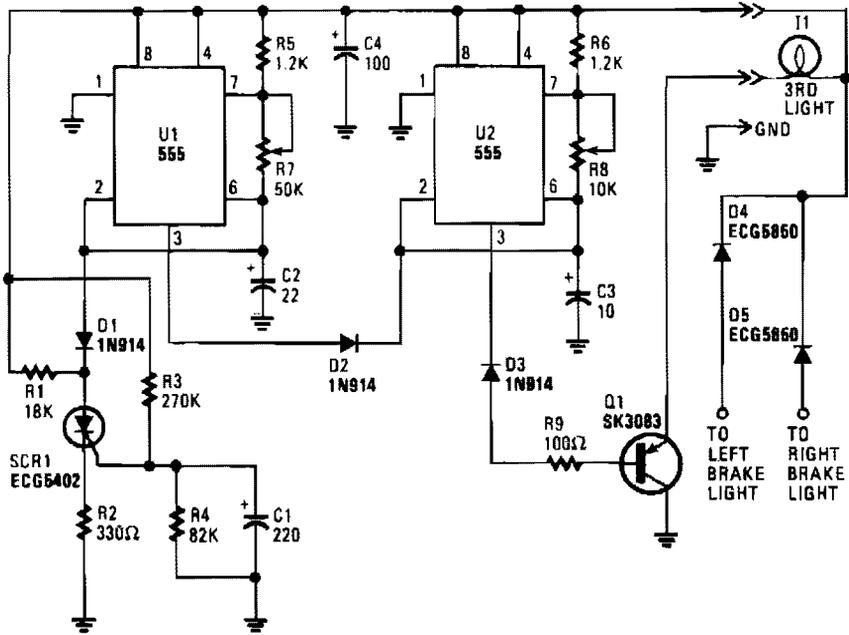

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 8-17

When power is first applied, three things happen: light-driving transistor Q1 is switched on due to a low output from U2 pin 3; timer U1 begins its timing cycle, with the output, pin 3, becoming high, inhibiting U2's trigger, pin 2, via D2; and charge current begins to move through R3 and R4 to C1.

When U1's output becomes low, the inhibiting bias on U2 pin 2 is removed, so U2 begins to oscillate, flashing the third light via Q1, at a rate determined by R8, R6, and C3. That oscillation continues until the gate-threshold voltage of SCR1 is reached, causing it to fire and pull U1's trigger, pin 2, low.

With its trigger low, U1's output is forced high, disabling U2's triggering. With triggering inhibited, U2's output switches to a low state, which makes Q1 conduct, turning on I1 until the brakes are released. Of course, removing power from the circuit resets SCR1, but the rc network consisting of R4 and C1 will not discharge immediately and will trigger SCR1 earlier. So, frequent brake use means fewer flashes.

## HEADLIGHT ALARM

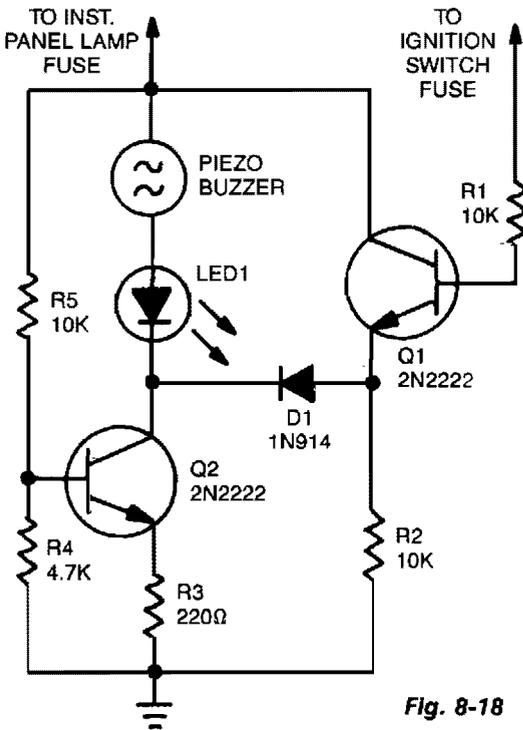


Fig. 8-18

The base of Q1 is connected to the car's ignition circuit. One side of the piezoelectric buzzer is connected to the instrument-panel light fuse. When the headlights are off, no current reaches the buzzer, and therefore nothing happens. What happens when the headlights are on depends on the state of the ignition switch. When the ignition switch is on, transistors Q1 and Q2 are biased on, removing the buzzer and the LED from the circuit. When the ignition switch is turned off, but the headlight switch remains on; transistor Q1 is turned off, but transistor Q2 continues to be biased on. The result is that the voltage is sufficient to sound the buzzer loudly and light the LED. Turning off the headlight switch will end the commotion quickly.

Reprinted with permission from Radio-Electronics Magazine, April 1987. Copyright Gernsback Publications, Inc., 1987.

# 9



## Battery Chargers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

PUT Battery Charger	UJT Battery Charger
Lead/Acid Battery Charger	Portable NiCad Battery Charger
Lead/Acid Low-Battery Detector	Universal Battery Charger
Universal Battery Charger	Low-Battery Warning

## PUT BATTERY CHARGER

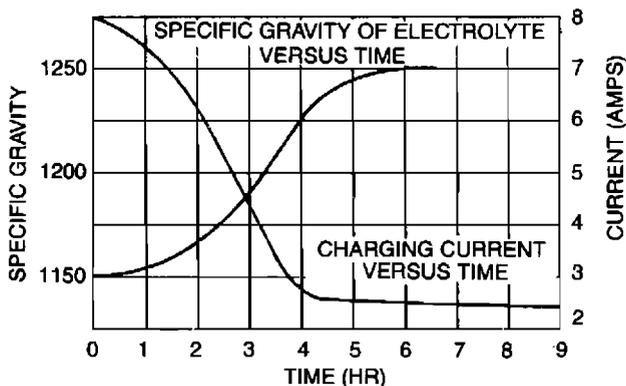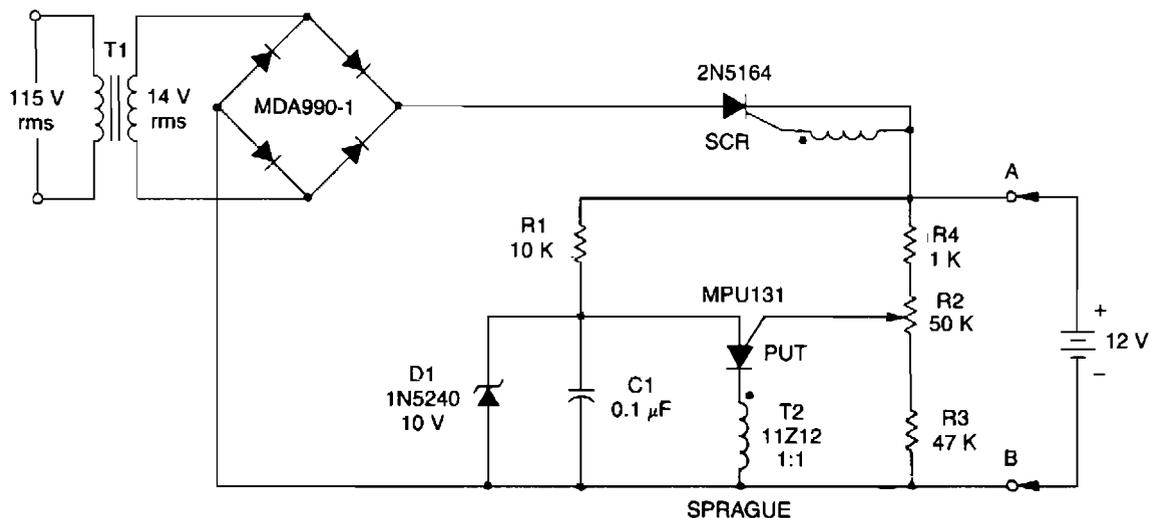


Copyright of Motorola, Inc. Used by permission.

**Fig. 9-1**

A short-circuit-proof battery charger will provide an average charging current of about 8 A to a 12-V lead/acid storage battery. The charger circuit has an additional advantage; it will not function nor will it be damaged by improperly connecting the battery to the circuit. With 115 V at the input, the circuit commences to function when the battery is properly attached. The battery provides the current to charge the timing capacitor C1 used in the PUT relaxation oscillator. When C1 charges to the peak point voltage of the PUT, the PUT fires turning the SCR on, which in turn applies charging current to the battery. As the battery charges, the battery voltage increases slightly which increases the peak point voltage of the PUT. This means that C1 has to charge to a slightly higher voltage to fire the PUT. The voltage on C1 increases until the zener voltage of D1 is reached, which clamps the voltage on C1, and thus prevents the PUT oscillator from oscillating and charging ceases. The maximum battery voltage is set by potentiometer R2 which sets the peak point firing voltage of the PUT. In the circuit shown, the charging voltage can be set from 10 V to 14 V—the lower limit being set by D1 and the upper limit by T1.

## LEAD/ACID BATTERY CHARGER

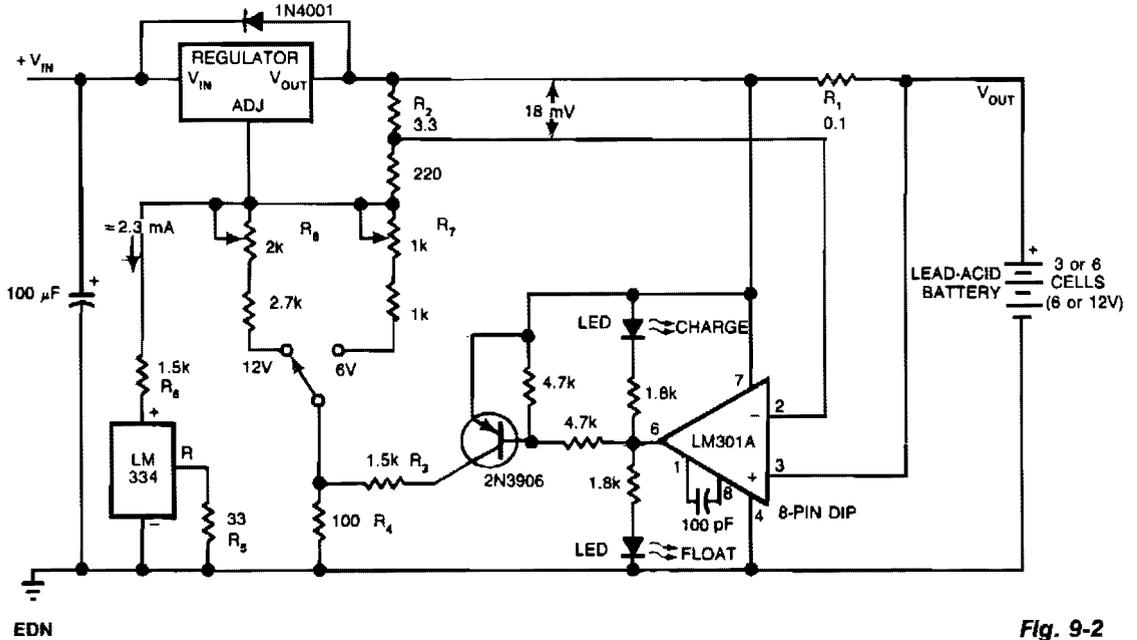


This circuit furnishes an initial voltage of 2.5 V per cell at 25°C to rapidly charge a battery. The charging current decreases as the battery charges, and when the current drops to 180 mA, the charging circuit reduces the output voltage to 2.35 V per cell, leaving the battery in a fully charged state. This lower voltage prevents the battery from overcharging, which would shorten its life.

The LM301A compares the voltage drop across R1 with an 18 mV reference set by R2. The comparator's output controls the voltage regulator, forcing it to produce the lower float voltage when the battery-charging current, passing through R1, drops below 180 mA. The 150 mV difference between the charge and float voltages is set by the ratio of R3 to R4. The LEDs show the state of the circuit.

Temperature compensation helps prevent overcharging, particularly when a battery undergoes wide temperature changes while being charged. The LM334 temperature sensor should be placed near or on the battery to decrease the charging voltage by 4 mV/°C for each cell. Because batteries need more temperature compensation at lower temperatures, change R5 to 30 Ω for a tc of -5 mV/°C per cell if application will see temperatures below -20°C.

The charger's input voltage must be filtered dc that is at least 3 V higher than the maximum required output voltage: approximately 2.5 V per cell. Choose a regulator for the maximum current needed: LM371 for 2 A, LM350 for 4 A, or LM338 for 8 A. At 25°C and with no output load, adjust R7 for a  $V_{OUT}$  of 7.05 V, and adjust R8 for a  $V_{OUT}$  of 14.1 V.


## LEAD/ACID LOW-BATTERY DETECTOR

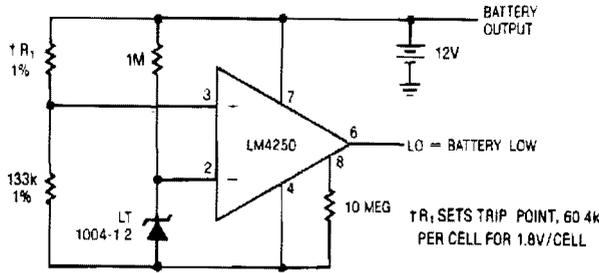

LINEAR TECHNOLOGY CORP.

Fig. 9-3


## UNIVERSAL BATTERY CHARGER

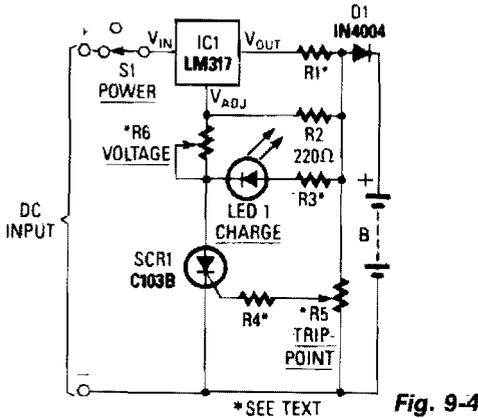

Reprinted with permission from Radio-Electronics Magazine, July 1988.  
 Copyright Gernsback Publications, Inc. 1986.

When power is applied to the circuit, SCR1 is off, so there is no bias-current path to ground; thus, LM317 acts as a current regulator. The LM317 is connected to the battery through steering diode D1, limiting resistor R1, and bias resistor R2. The steering diode prevents the battery from discharging through the LED and the SCR when power is removed from the circuit. As the battery charges, the voltage across trip-point potentiometer R5 rises, and at some point, turns on the SCR. Then, current from the regulator can flow to ground, so the regulator now functions in the voltage mode. When the SCR turns on, it also provides LED1 with a path to ground through R3. So, when LED1 is on, the circuit is in the voltage-regulating mode; when LED1 is off, the circuit is in the current-regulating mode.

## UJT BATTERY CHARGER

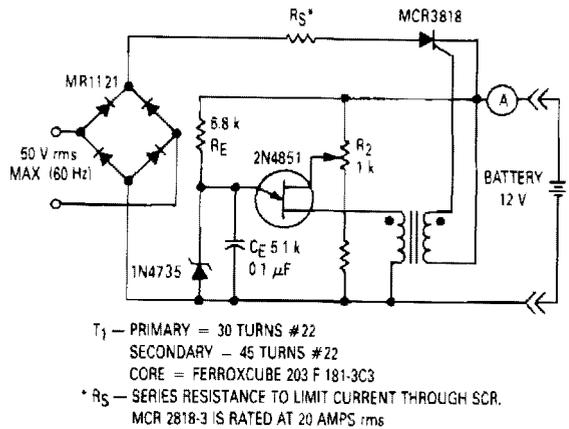


Copyright of Motorola, Inc. Used by permission.

Fig. 9-5

This circuit will not work unless the battery to be charged is connected with proper polarity. The battery voltage controls the charger and when the battery is fully charged, the charger will not supply current to the battery. The battery charging current is obtained through the SCR when it is triggered into the conducting state by the UJT relaxation oscillator. The oscillator is only activated when the battery voltage is low.  $V_{B2B1}$  of the UJT is derived from the voltage of the battery to be charged, and since  $V_P = V_D = V_{B2B1}$ ; the higher  $V_{B2B1}$ , the higher  $V_P$ . When  $V_P$  exceeds the breakdown voltage of the zener diode Z1, the UJT will cease to fire and the SCR will not conduct. This indicates that the battery has attained its desired charge as set by R2.

## PORTABLE NICAD BATTERY CHARGER

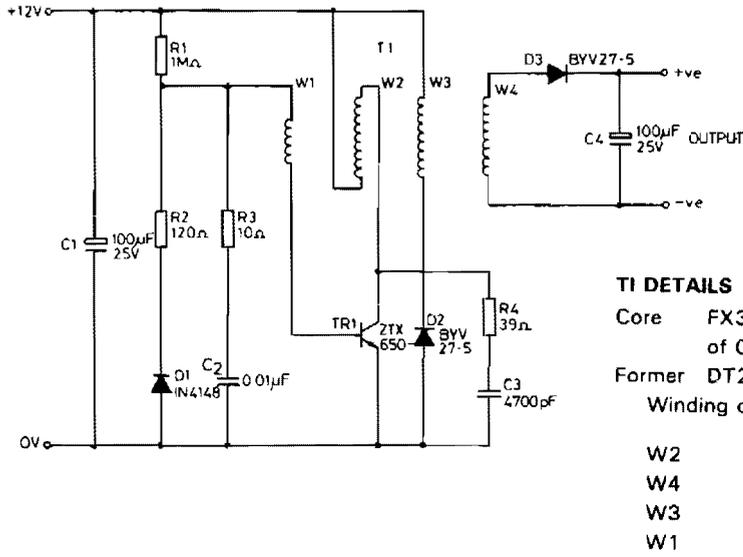


Z<sub>e</sub>TeX, formerly FERRANTI

*Fig. 9-6*

This circuit was designed to charge NiCad battery packs in the range of 4.8 to 15.6 V from a convenient remote power source, such as an automobile battery. When power is first applied to the circuit, a small bias current supplied by R1 via winding W1, starts to turn on the transistor TR1. This forces a voltage across W2 and the positive feedback given by the coupling of W1 and W2 causes the transistor to turn hard on, applying the full supply across W2. The base drive voltage induced across W1 makes the junction between R1 and R2 become negative with respect to the 0-V supply, forward-biasing diode D1 to provide the necessary base current to hold TR1 on.

With the transistor on, a magnetizing current builds up in W2, which eventually saturates the ferrite core of transformer T1. This results in a sudden increase on the collector current flowing through TR1, causing its collector-emitter voltage to rise, and thus reducing the voltage across W2. The current flowing in W2 forces the collector voltage of the TR1 to swing positive until restricted by transformer output loading. R<sub>c</sub> network R4 and C3 limits the turn off transient TR1. R3 and C2 maintain the loop gain of the circuit when diode D1 is not conducting.

## UNIVERSAL BATTERY CHARGER

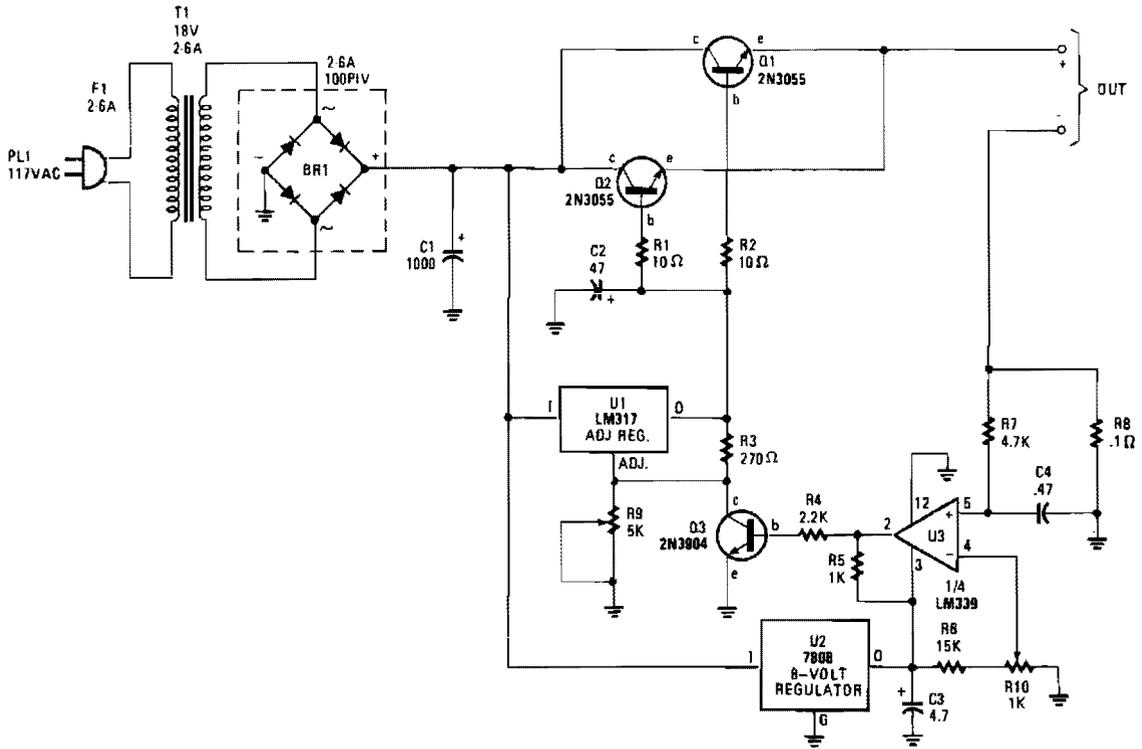

POPULAR ELECTRONICS

Fig. 9-7


The charger's output voltage is adjustable and regulated, and has an adjustable constant-current charging circuit that makes it easy to use with most NiCad batteries. The charger can charge a single cell or a number of series-connected cells up to a maximum of 18 V.

Power transistors Q1 and Q2 are connected as series regulators to control the battery charger's output voltage and charge-current rate. An LM317 adjustable voltage regulator supplies the drive signal to the bases of power transistors Q1 and Q2. Potentiometer R9 sets the output-voltage level. A current-sampling resistor, R8 (a 0.1-Ω, 5-W unit), is connected between the negative output lead and circuit ground. For each amp of charging that flows through R8, a 100 mV output is developed across it. The voltage developed across R8 is fed to one input of comparator U3. The other input of the comparator is connected to variable resistor R10.

As the charging voltage across the battery begins to drop, the current through R8 decreases. Then the voltage feeding pin 5 of U3 decreases, and the comparator output follows, turning Q3 back off, which completes the signal's circular path to regulate the battery's charging current.

The charging current can be set by adjusting R10 for the desired current. The circuit's output voltage is set by R9.

## LOW-BATTERY WARNING

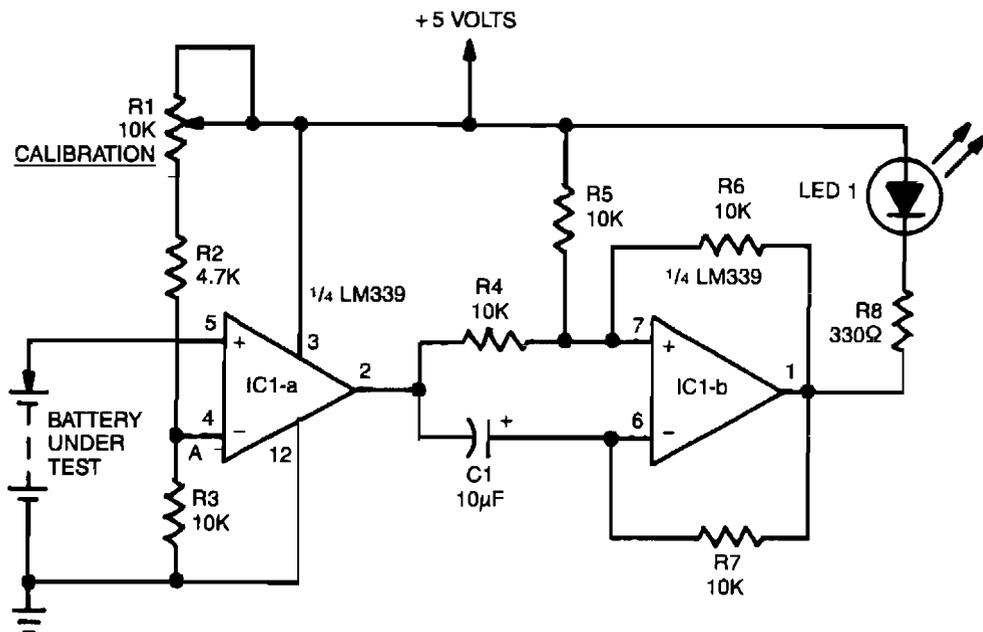

GERNSBACK PUBLICATIONS INC.

**Fig. 9-8**

A voltage divider consisting of R1, R2, and R3 is used to set the input reference voltage below which the batteries are to be replaced. That reference voltage, at point A, is varied by R1. With the voltage divider shown in Fig. 9-7, a range of 2 to 3.5 V is possible. When the battery voltage drops below that at point A, the output of IC1a,  $\frac{1}{4}$  of a LM339 quad comparator, switches from high to low. That triggers IC1b, which is configured as an astable multivibrator. Feedback resistors R6 and R7, coupled with capacitor C1, determine the time constant of the multivibrator. The output from IC1b is connected to LED1 through dropping resistor R8. With the circuit values as shown, the LED will flash at a rate of 3 Hz. Although this circuit was designed specifically to monitor RAM back-up batteries, it can of course be modified for use in just about any application where the condition of a battery must be found.

# 10

## Battery Monitors

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Quickly Deactivating Battery Sensor	NiCad-Battery Analyzer
Automatic Shutoff for Battery-Powered Projects	Low-Battery Protector
NiCad-Battery Protection Circuit	Low-Battery Warning/Disconnecter
9-V Battery Life Extender	Battery Capacity Tester
Auto Battery Alternator Monitor	Battery Splitter
Low-Battery Detector	Electric Vehicle Battery Saver

## QUICKLY DEACTIVATING BATTERY SENSOR

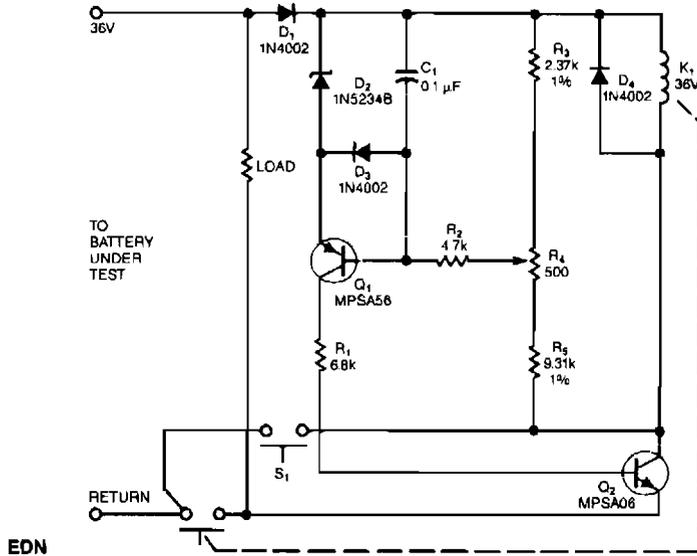


Fig. 10-1

The sensing circuit rapidly disconnects the battery voltage and load whenever the voltage drops below a preset threshold. One-way operation prevents the circuit from reconnecting the load if the voltage should then rise above the threshold. C1 ensures that the circuit doesn't activate while making connections to the battery; if you accidentally reverse these connections, D1 will block the turn on the relay.

After you connect the battery, nothing happens until you depress pushbutton switch S1, which allows relay K1 to energize. When you release S1, the relay remains on only if the battery voltage is above the minimum level. You preset this threshold—to 31.5 V when testing 36-V batteries, for example—using R4. Q1 begins to turn off as the battery voltage drops. Once the threshold level is reached, Q2 also begins to turn off, and its rising collector voltage provides positive feedback to the base of Q1, accelerating the turn off. When Q2 turns off, the relay drops out, disconnecting the battery from its load.

## AUTOMATIC SHUTOFF FOR BATTERY-POWERED PROJECTS


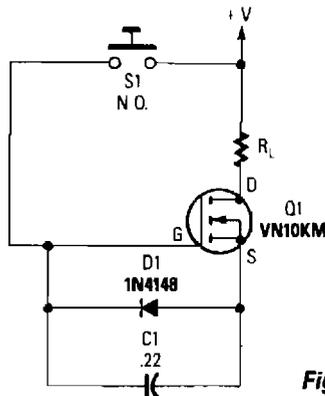


Fig. 10-2

When S1 is depressed, C1 begins to charge to the supply voltage. That places a forward bias on the gate of Q1 turning it on and supplying current to load resistor RL. When the charge on C1 leaks off, the transistor shuts off, cutting off current to the load. That load could be anything from a transistor radio to a child's toy. Transistor Q1, available from Radio Shack as part No. 276-2070, is rated at 0.5 A at 60 Vdc. With a supply voltage of 9 Vdc and with C1 rated at 0.22  $\mu$ F, a delay of about one minute is produced; with C1 rated at 10  $\mu$ F, the delay is about an hour.

## NICAD-BATTERY PROTECTION CIRCUIT

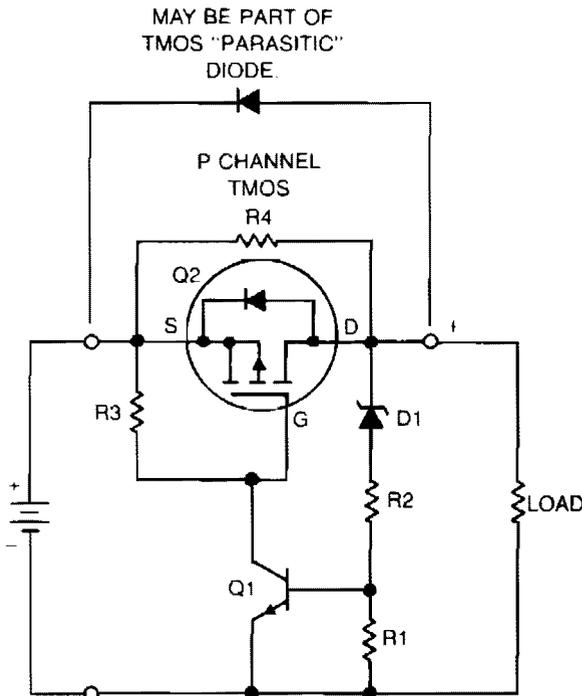

Copyright of Motorola, Inc. Used by permission.


Fig. 10-3

If a NiCad battery is discharged to a point at which the lowest capacity cell becomes fully discharged and reverses polarity, that cell will usually short internally and become unusable. To prevent this type of damage, this circuit detects a one-cell drop of 1.25 V and turns the load off before cell reversal can occur.

Low-current zener or other voltage sensor D1 and resistors R1 and R2 establish a reference level for transistor Q1. These resistors bias the zener to a few microamperes above its "knee." Therefore, if battery voltage falls more than 1.25 V, Q1 turns off, turning off Q2, and disconnecting the load. After the load is disconnected, if the battery returns to nominal voltage, the high value of resistor shunting Q2 provides enough output voltage to reset the voltage sensor and turn Q2 back on. If desirable, shunt diode D2 or the parasitic diode of the TMOS device, if suitable, allows the battery to be charged from the load terminals.

The protection circuit presents a shunt current of only 10 mA at nominal battery voltage, which is low relative to the internal leakage of the batteries.

## 9-V BATTERY LIFE EXTENDER

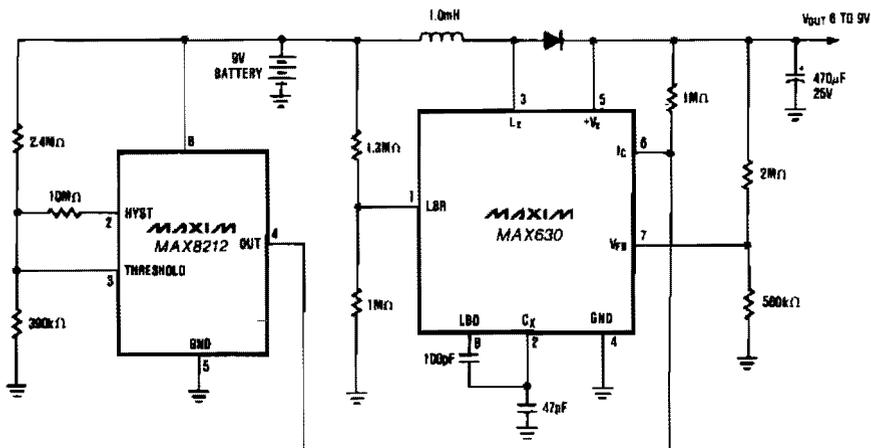

MAXIM

Fig. 10-4







## BATTERY CAPACITY TESTER


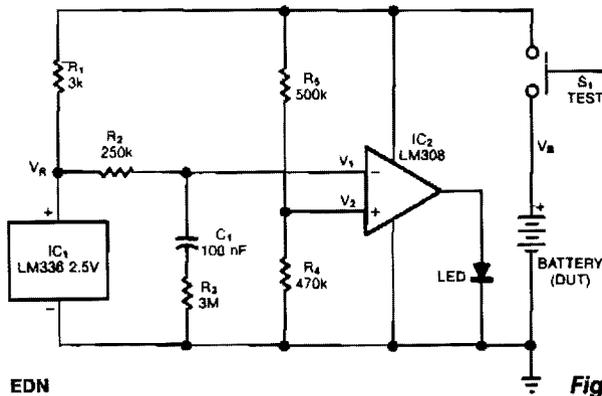


Fig. 10-10

The test circuit gives an indication of the capacity remaining in a battery. By noting the time in seconds that the LED remains on after you depress the test switch S1. The circuit has proven reliable in testing NiCad-, carbon-, and alkaline-type batteries. Closing S1 activates the circuit by applying voltage from the battery under test. Voltage  $V_1$  jumps to a value  $V_0 = V_R R_3 / (R_2 + R_3)$  when the switch closes and then increases with a time constant  $T = C_1 (R_2 + R_3)$ . The divider  $R_4/R_5$  fixes  $V_2$ . The reference circuit IC1 sets  $V_R$  to approximately 2.5 V. The op-amp's output remains high (LED on) until  $V_1$  rises to the level of  $V_2$ , when the LED turns off. Calculate the on-time  $t_{ON}$  as follows:

$$t_{ON} = T \ln \frac{V_R - V_0}{V_R - V_2}$$

## BATTERY SPLITTER

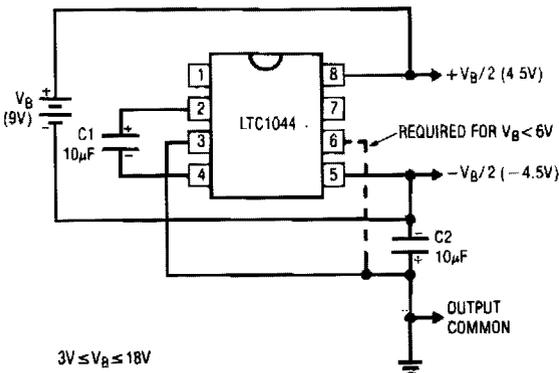


LINEAR TECHNOLOGY

Fig. 10-11

A common need in many systems is to obtain positive and negative supplies from a single battery. Where current requirements are small, the circuit shown is a simple solution. It provides symmetrical  $\pm$  output voltages, both equal to one half the input voltage. The output voltages are referenced to pin 3, output common. If the input voltage between pin 8 and pin 5 exceeds 6 V, pin 6 should also be connected to pin 3, as shown by the dashed line. Higher current requirements are served by an LT1010 buffer. The splitter circuit can source or sink up to  $\pm 150$  mA with only 5 mA quiescent current. The output capacitor, C2, can be made as large as necessary to absorb current transients. An input capacitor is also used on the buffer to avoid high frequency instability that can be caused by high source impedance.

## ELECTRIC VEHICLE BATTERY SAVER

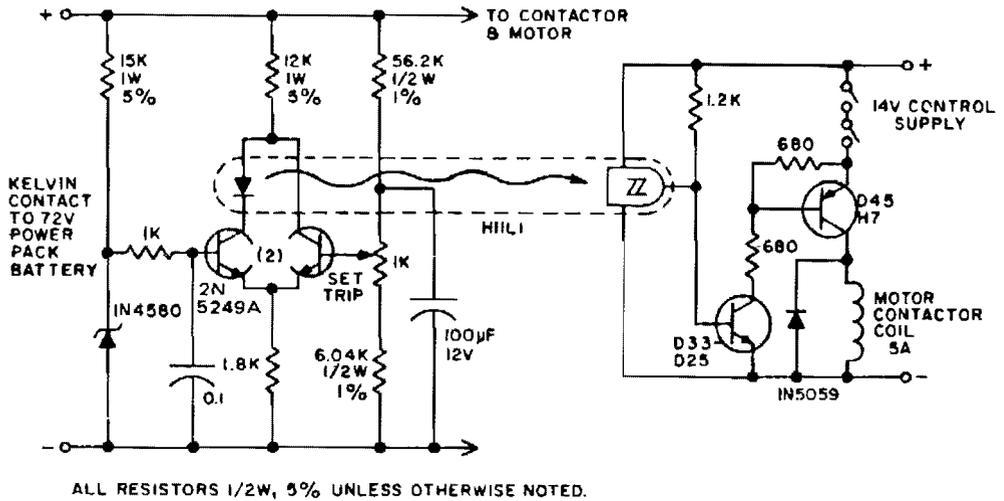

GE

**Fig. 10-12**

The battery life and operating cost of an electric vehicle is severely affected by overdischarge of the battery. This circuit provides both warning and shutdown. An electronic switch is placed in series with the propulsion motor contactor coil. Three modes of operation are possible:

- When the propulsion power pack voltage is above the 63-V trip point, the electronic switch has no effect on operation
- When the propulsion power pack no load voltage is below 63 V, power will not be supplied to the propulsion motor since the electronic switch will prevent contactor operation
- When the propulsion power pack loaded voltage drops below 63 V, the contactor will close and open because of the electronic switch. The *bucking operation* indicates to the operator need to charge the batteries

# 11

## Bridge Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Auto-Zeroing Scale  
Accurate Null/Variable Gain Circuit  
Remote Sensor Loop Transmitter  
Bridge Transducer Amplifier  
Strain Gauge Signal Conditioner with  
Bridge Excitation

## AUTO-ZEROING SCALE

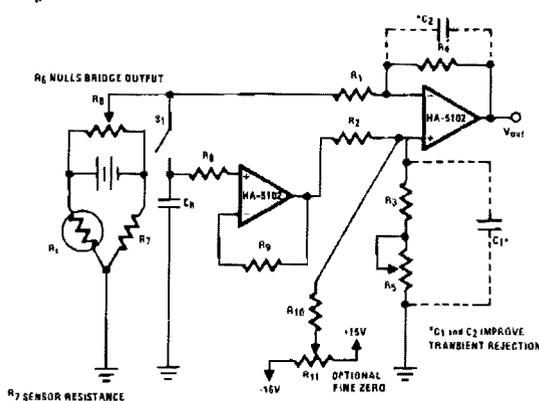


Fig. 11-1


HARRIS

Electronic scales have come into wide use and the HA-510X, as a very low noise device, can improve such designs. This circuit uses a strain-gauge sensing element as part of a resistive Wien-bridge. An auto-zero circuit is also incorporated into this design by including a sample-and-hold network.

The bridge signal drives the inverting input of a

differentially configured HA-5102. The noninverting input is driven by the other half of the HA-5102 used as a buffer for the holding capacitor, *CH*. This second amplifier and its capacitor *CH* form the sampling circuit used for automatic output zeroing. The 20-K $\Omega$  resistor between the holding capacitor *CH* and the input terminal, reduces the drain from the bias currents. A second resistor *RG* is used in the feedback loop to balance the effect of *R8*. If *R7* is approximately equal to the resistance of the strain gauge, the input signal from the bridge can be roughly nulled with *R6*. With very close matching of the ratio *R4/R1* to *R3/R2*, the output offset can be nulled by closing *S1*. This will charge *CH* and provide a 0-V difference to the inputs of the second amplifier, which results in a 0-V output. In this manner, the output of the strain gauge can be indirectly zeroed. *R10* and potentiometer *R11* provide an additional mechanism for fine tuning *V<sub>OUT</sub>*, but they can also increase offset voltage away from the zero point. *C1* and *C2* reduce the circuit's susceptibility to noise and transients.

## ACCURATE NULL/VARIABLE GAIN CIRCUIT

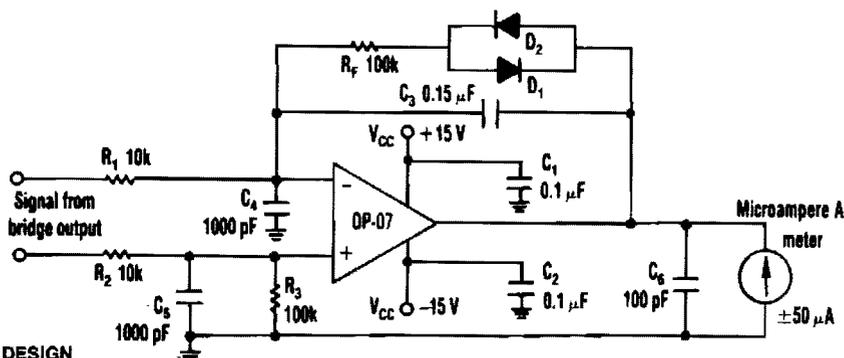


ELECTRONIC DESIGN

Fig. 11-2

The circuit can use any general-purpose, low-offset, low-drift op amp, such as the OP-07. The differential signal from the bridge feeds an amplifier that drives an ordinary, rugged  $\pm 50\text{-}\mu\text{A}$  meter. Near the null point, however, the drastically reduced signal level from the bridge requires very high gain to achieve a high null resolution. To provide the variable-gain feature, the op amp's feedback path needs a dynamic resistance that increases as the input signal drops. Two common signal diodes, *D1* and *D2*, in an antiparallel configuration in the feedback path supply function for all positive and negative inputs. To stabilize the op amp circuit at high gain, capacitors *C3*, *C5*, and *C6* reduce response to high frequencies; capacitors *C1* and *C2* bypass the amplifier's power supplies.

## REMOTE SENSOR LOOP TRANSMITTER

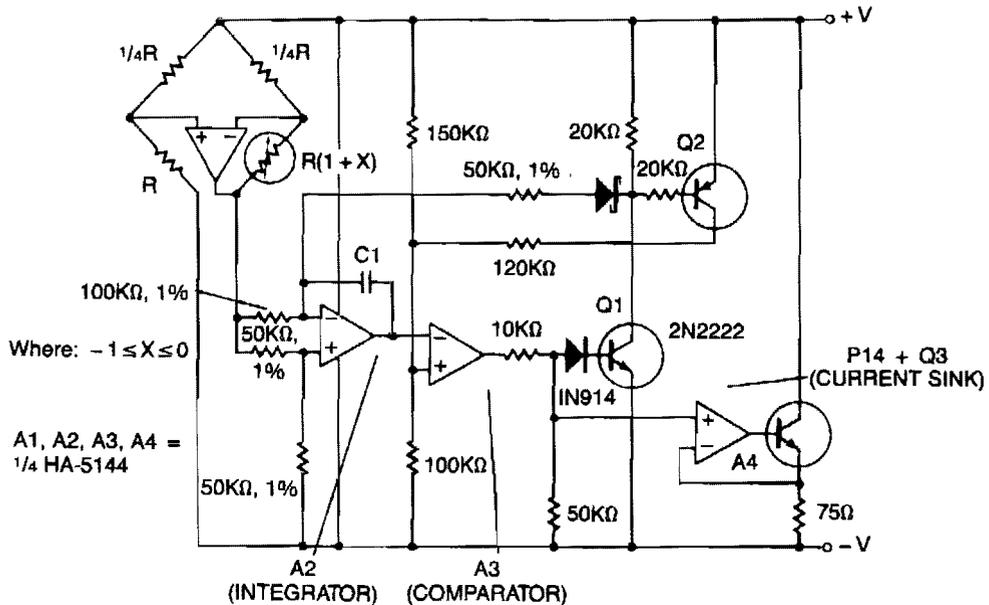


HARRIS

Fig. 11-3

This circuit shows amplifier A1 as a sensor amplifier in a bridge configuration. Amplifiers A2 and A3 are configured as a voltage to frequency converter and A4 is used as the transmitter. This entire sensor/transmitter can be powered directly from a 4 to 20 mA current loop.

The bridge configuration produces a linear output with respect to the changes in resistance of the sensor. The voltage at the output of A1 causes the integrator output A2 to ramp down until it crosses the comparator threshold voltage of A3. A3 turns on Q1 and Q2. A1 causes the output of A2 to ramp up at a rate nearly equal to its negative slope, while Q2 provides hysteresis for the comparator. In addition, Q1 and Q2 help eliminate changes in power supply loop voltage. Amplifier A4 and Q3 are configured as a constant current sink which turns on when the comparator current increases. The resulting increase in loop current transmits the frequency of the V/F converter back to the control circuitry.

## BRIDGE TRANSDUCER AMPLIFIER

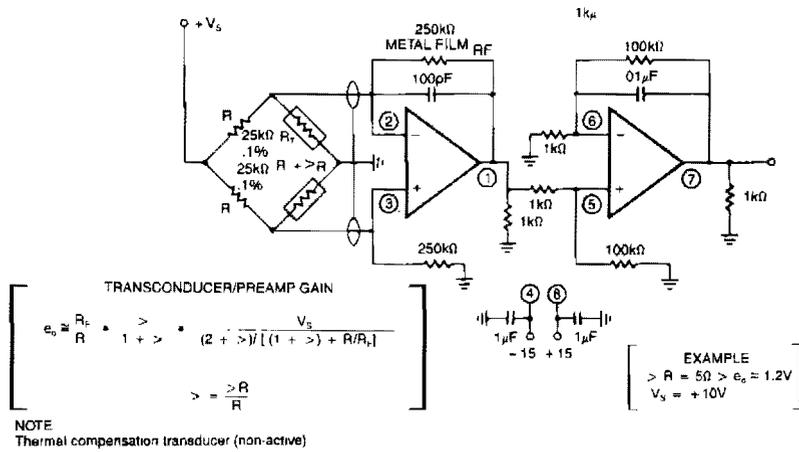


**SIGNETICS**

**Fig. 11-4**

In applications involving strain gauges, accelerometers, and thermal sensors, a bridge transducer is often used. Frequently, the sensor elements are high resistance units requiring equally high bridge resistance for good sensitivity. This type of circuit then demands an amplifier with high input impedance, low bias current and low drift. The circuit shown represents a possible solution to these general requirements.

## STRAIN GAUGE SIGNAL CONDITIONER WITH BRIDGE EXCITATION

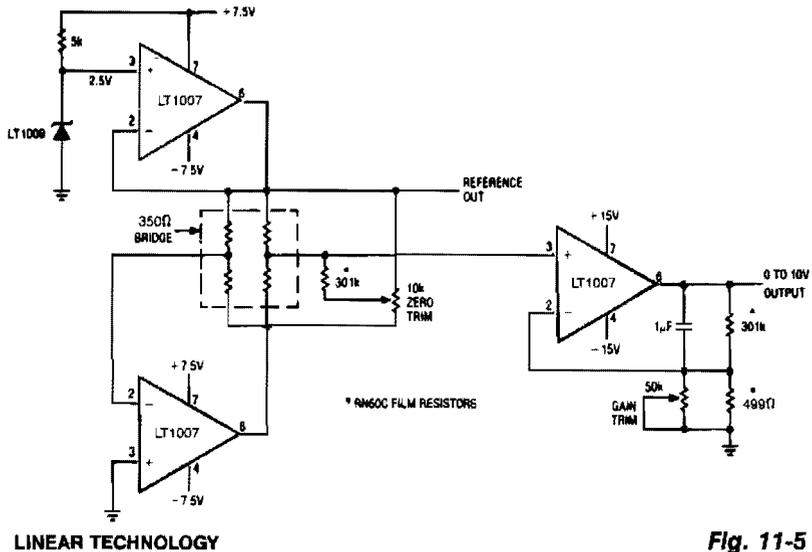

**Fig. 11-5**

The LT1007 is capable of providing excitation current directly to bias the 350-Ω bridge at 5 V. With only 5 V across the bridge, as opposed to the usual 10 V, total power dissipation and bridge warm-up drift is reduced. The bridge output signal is halved, but the LT1007 can amplify the reduced signal accurately.

# 12


## Burst Generators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Portable Rf Burst Generator  
Tone Burst Generator for European Repeaters

## PORTABLE RF BURST GENERATOR

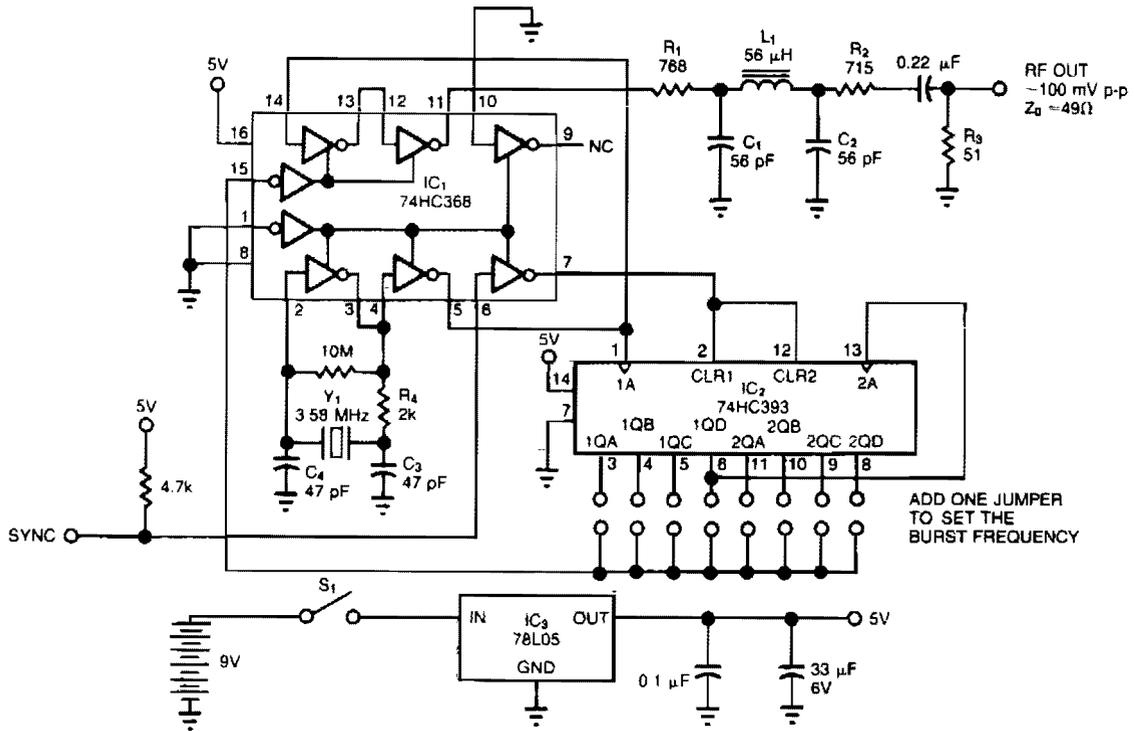


EDN

Fig. 12-1

The circuit generates low-level rf bursts having frequencies as high as 10 MHz, thus permitting field testing of high frequency receivers. A jumper-selectable binary fraction ( $1/2$  to  $1/256$  of the Y1 crystal frequency) gates the output rf signal. Output amplitude (open circuit) is approximately 100 mV; output impedance is approximately 49  $\Omega$ . The rf source is a clock oscillator based on a 3.58-MHz, color-burst crystal and two inverting buffers. The oscillator drives two cascaded 4-bit binary counters, IC2, and the sync signal resets the counters with a logic-high pulse—logic low at the counters. Select the desired output frequency by adding a jumper to one of the counter's eight output lines, which provides an enable signal for the two 3-state output buffers. The square-wave output at IC1, pin 11, is attenuated by R1, R2, and R3 to fix the output resistance at approximately 49  $\Omega$ . Resistor R3 is the only critical component; for clean gating, isolate it from the rest of the circuit.
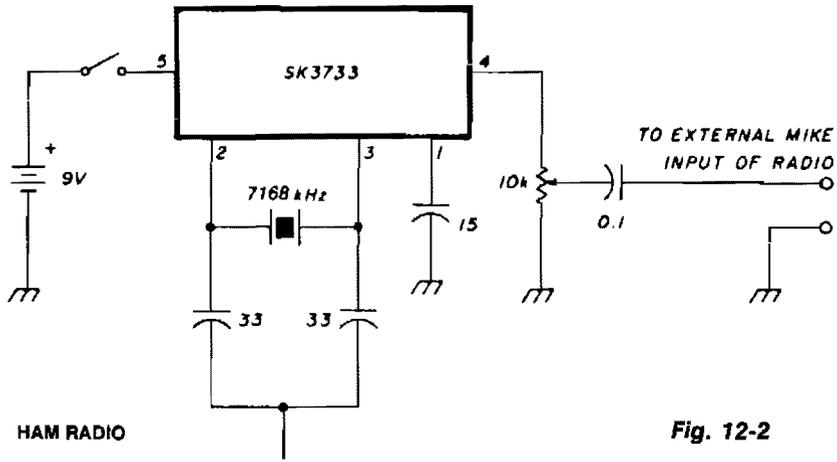
## TONE BURST GENERATOR FOR EUROPEAN REPEATERS



Most European repeaters must be brought up with a 1750-Hz tone. The SK3733 (also known as an ECG1197) IC contains a crystal oscillator and is divided by -256, 1024, 2048, and 4096. A 7168-kHz crystal is used; the divide-by-4096 output produces a 1750-Hz signal.

# 13


## Capacitance Meters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

3<sup>1</sup>/<sub>2</sub>-Digit A/D Capacitance Meter  
Capacitance Meter
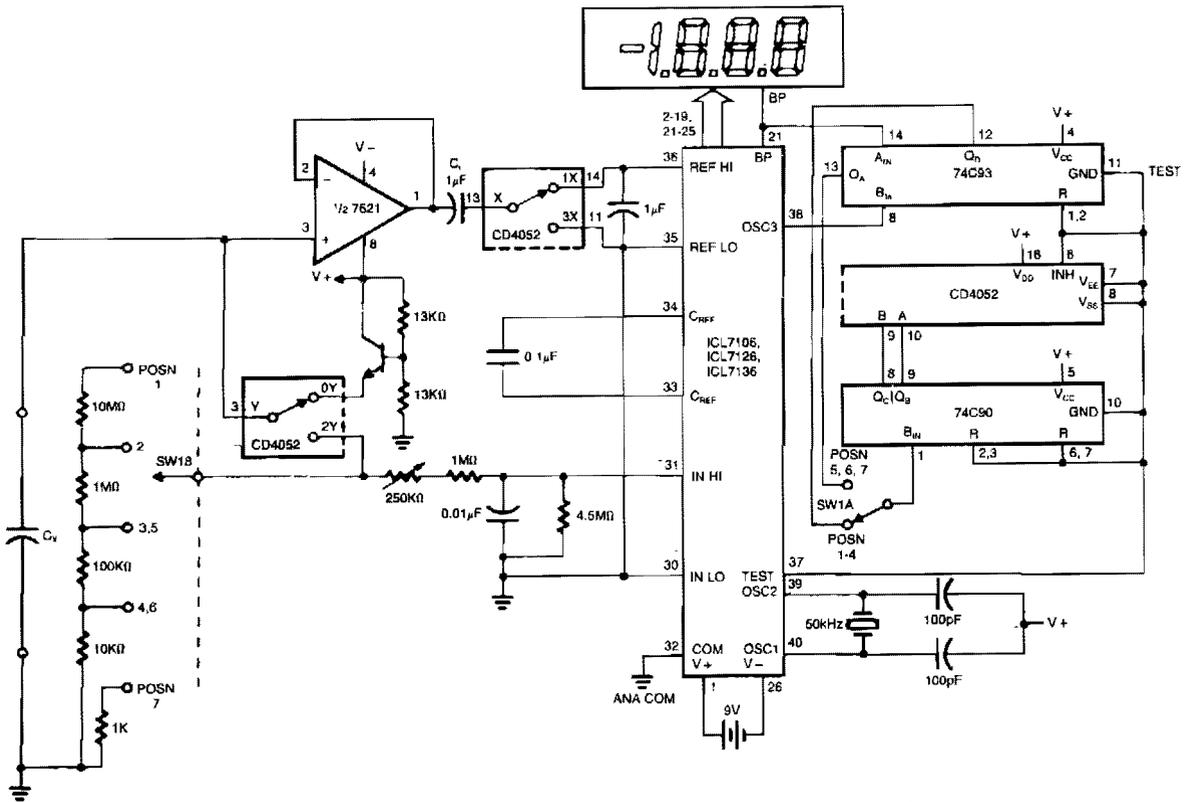
### 3<sup>1</sup>/<sub>2</sub>-DIGIT A/D CAPACITANCE METER



	Switch 1A	Switch 1B	Max C	Counter/Switch Phases	
1	10MΩ	6KHz	20μF	0Y	00
2	1MΩ	6KHz	2nF	1Y	01
3	100KΩ	6KHz	20nF	2Y	10
4	10KΩ	6KHz	0.2μF	3X	11
5	100KΩ	80Hz	2μF		
6	10KΩ	80Hz	20μF		
7	1KΩ	80Hz	200μF		

0668-26


INTERSIL

Fig. 13-1

The circuit charges and discharges a capacitor at a crystal-controlled rate, and stores on a sample-and-difference amplifier the change in voltage achieved. The current that flows during the discharge cycle is averaged, and ratiometrically measured in the a/d using the voltage change as a reference. Range switching is done by changing the cycle rate and current metering resistor. The cycle rate is synchronized with the conversion rate of the a/d by using the externally divided internal oscillator and the internally divided back plane signals. For convenience in timing, the switching cycle takes 5 counter states, although only four switch configurations are used. Capacitances up to 200 μF can be measured, and the resolution on the lowest range is down to 0.1 pF.

The zero integrator time can be set initially at 1/3 to 1/2, the minimum auto-zero time, but if an optimum adjustment is required, look at the comparator output with a scope under worst-case overload conditions. The output of the delay timer should stay low until after the comparator has come off the rail, and is in the linear region (usually fairly noisy).

## CAPACITANCE METER

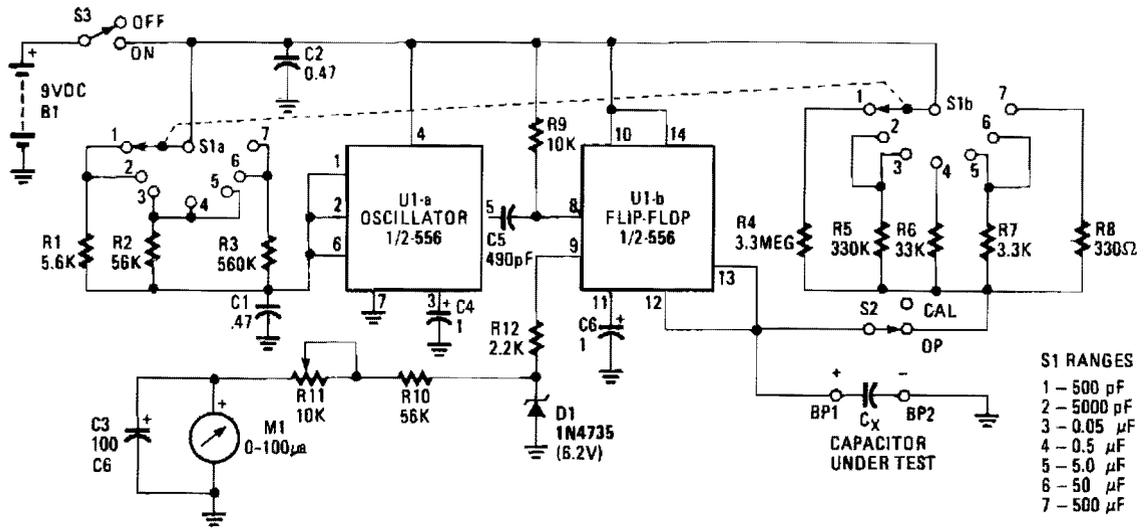

HANDS-ON ELECTRONICS

**Fig. 13-2**

U1a is an oscillator and U1b the measurement part of the circuit. It converts unknown capacity into a pulse-width modulated signal the same way an automotive dwell meter works. The meter is linear so the fraction or percentage of time that the output is high is directly proportional to the unknown capacitance (CX in the schematic). Meter M1 reads the average voltage of those pulses since its mechanical frequency response is low compared to the oscillator frequency of U1a.

# 14


## Carrier-Current Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Carrier-Current Audio Transmitter  
Carrier-Current FM Receiver  
Carrier-Current AM Receiver  
Power-Line Modem

## CARRIER-CURRENT AUDIO TRANSMITTER

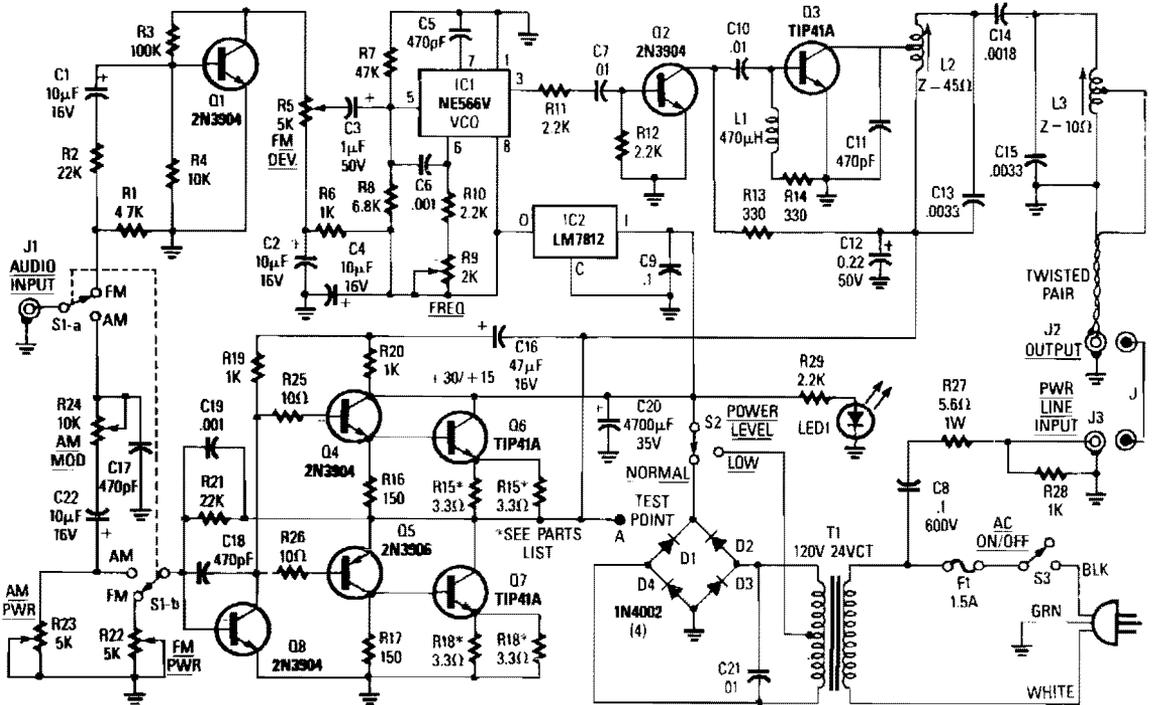

Reprinted with permission from Radio-Electronics Magazine, January 1989. Copyright Gernsback Publications, Inc., 1989.


**Fig. 14-1**

The decision to use either AM, narrowband FM (less than 15 kHz), or wideband FM (greater than 30 kHz) depends on the application. For the transmission of music, FM is better because it has greater noise immunity. For speech or other noncritical applications, AM may be satisfactory. Our transmitter permits either mode by switch selection.

Audio is fed from S1a to either the FM or AM circuitry. Starting with the FM section, amplifier Q1 accepts an audio signal in the 10 Hz to 20 kHz range of about 0.5 V peak-to-peak. The audio gain is adjusted via R5 to provide up to 60 kHz deviation of voltage-controlled oscillator IC1 which is set to nominally 280 kHz. IC1 and Q1 are supplied with a regulated 12 V from IC2. A square-wave signal from IC1 pin 3 drives Q2, and Q2 drives the output amplifier Q3. A coupling network is used to match the nominal 45-Ω output impedance of Q3 to the 10-Ω ac line impedance.

In the AM mode, audio is coupled to Q8 via R24 and then amplified again by transistors Q4 to Q7. The normally stable dc voltage at test point A is thereby varied at an audio rate. Because Q2 and Q3 obtain their dc  $V_{CC}$  from test point A, the VCO carrier input to Q2 is amplitude modulated by the varying  $V_{CC}$  amplitude. That produces an amplitude-modulated output from the transmitter. Careful setting of carrier level R23 and audio level R24 provides up to 100% modulation. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.

## CARRIER-CURRENT FM RECEIVER

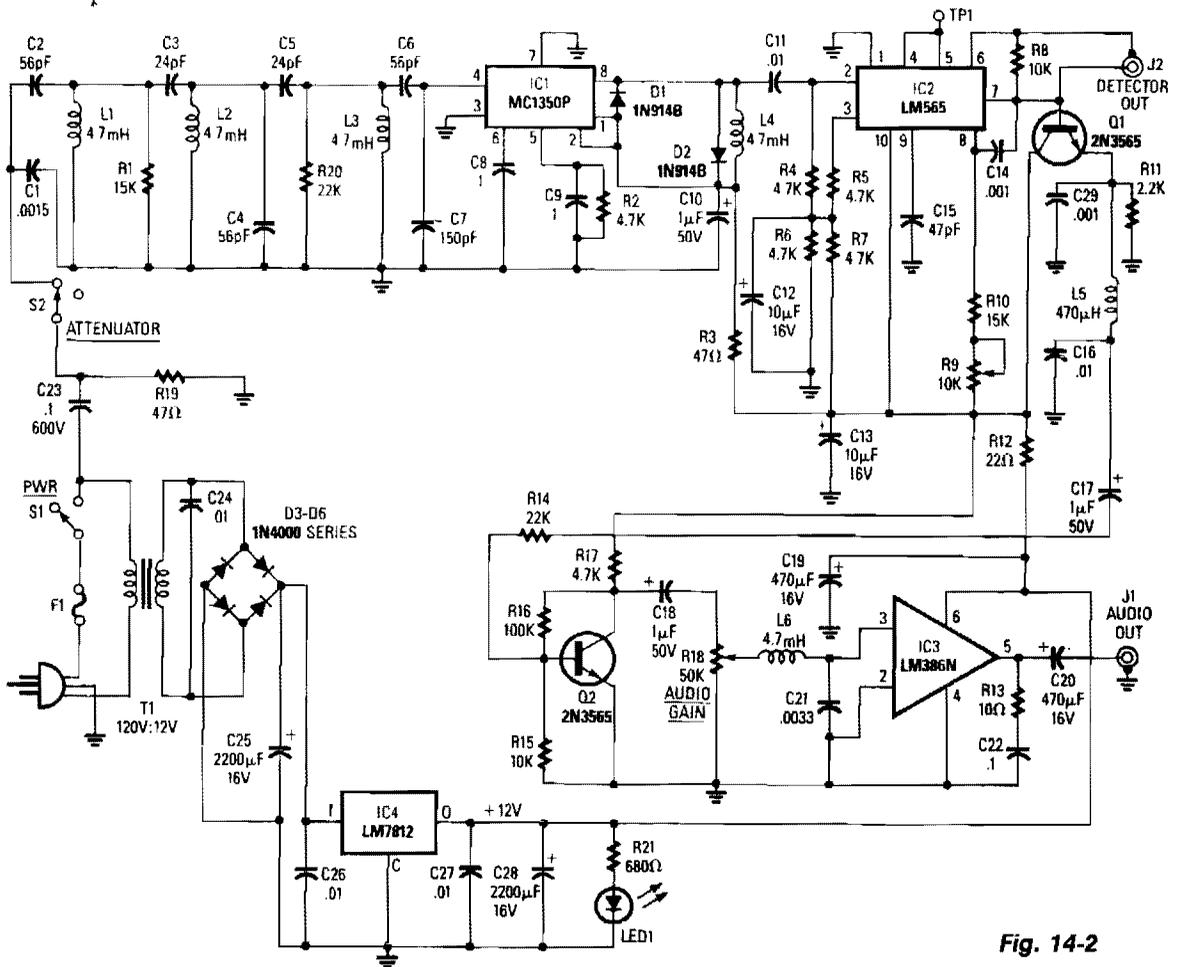


**Fig. 14-2**

Reprinted with permission from Radio-Electronics Magazine, February 1989. Copyright Gernsback Publications, Inc., 1989.

Input signals from the power line are coupled through C23 and R19 to the input filter network. C23 must be rated at 600 volts. Switch S2 is used as an attenuator. Components C2 through C7, L1 through L3, R1, and R20 form a triple-tuned bandpass filter having a passband from 220–340 kHz. Signals from the filter are fed to an MC1350P gain block IC, which is used as a tuned rf amplifier.

IC2, the LM565 PLL, is used as an FM demodulator. Pins 8 and 9 are connected to an internal VCO and components R9, R10, and C15 set the VCO's free running frequency. The VCO signal and the input signal from pin 2 are compared in the phase detector. The output from the phase detector is internally amplified, and then appears at pin 7. The output at pin 7 is a replica of the original modulation on the FM input signal to the receiver; the output at pin 7 is therefore the recovered audio. C17 and R14 couple audio to the base of Q2, which, in conjunction with R15, R16, R17, and C18, form an audio amplifier that brings the recovered audio up to around 1 V peak-to-peak. The signal is then fed into an LM386N audio amplifier, which can deliver up to 1/2 W of audio, coupled via C20, to any standard 8-Ω external speaker. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.

## CARRIER-CURRENT AM RECEIVER

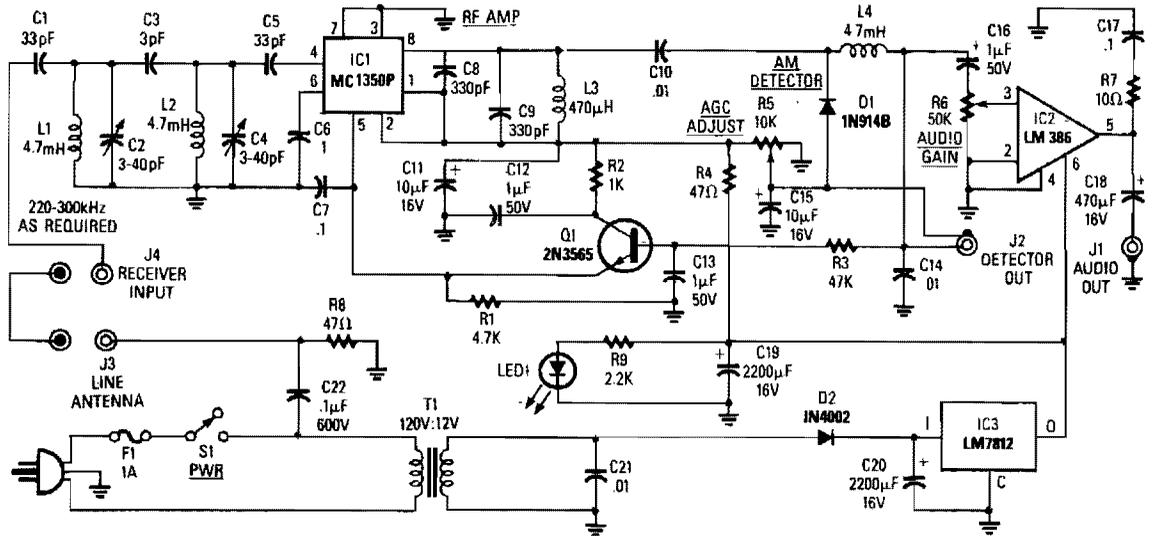

Reprinted with permission from Radio-Electronics Magazine, February 1989. Copyright Gernsback Publications, Inc., 1989.


**Fig. 14-3**

The AM Tuned Radio Frequency (TRF) receiver, has a sensitivity of about 1 mV at the input for an audio output of  $\frac{1}{2}$  W. Capacitor C22 couples audio signals from the power line to the PC board—it must be rated at 600 Vdc. R8 will cause F1 to blow, if C22 shorts. The signal from C22 goes to a tuned network (C1 through C5, L1, and L2) that has a 20-kHz bandwidth, which allows only the desired signal to pass through.

IC1 is a *gain block* i-f chip that has AGC capability and approximately 60 dB of gain. Components C8, C9, and L3, which are placed across the output of IC1, are broadly resonant around 280 kHz. C10 couples rf to detector-diode D1, which is used as an envelope detector.

The detector output is taken from C14, which sets the upper frequency limit at about 10 kHz or so. By reducing the value of C14, high frequency response can be obtained. The detector output is connected to an external jack. Audio components are fed to audio-gain control R6, through C16 to IC2, an audio amplifier. C18 couples up to  $\frac{1}{2}$  watt of audio to an external speaker. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.

## POWER-LINE MODEM

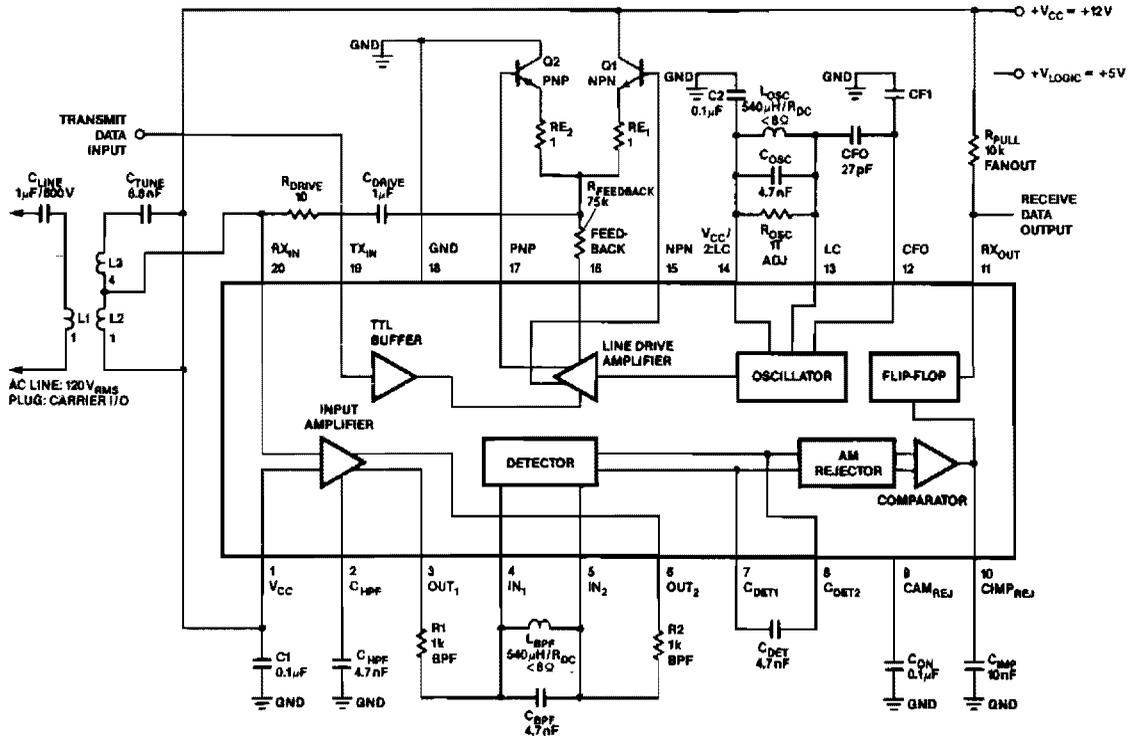

SIGNETICS

Fig. 14-4

In the 100-kHz application from left to right, the coupling network feeds into the receiver section on the bottom of the chip. (The external components are summarized later.) The receive data output is pulled up via  $R_{PULL} = 10\text{ K}\Omega$ . A minimum current of 10 mA sets the voltage drop across  $R_{PULL}$ . Another voltage supply,  $V_{LOGIC}$ , is shown if the user wants to have the output sent at TTL levels. Across the top is the transmitter section; going from right to left, the oscillator network, the class AB output stage (note feedback resistor  $R_{FEEDBACK}$ ) and the drive section. The LC values on the oscillator network should match those on the bandpass filter in the receiver. The drive stage feeds into the coupling network and back into the receive section. This enables the on-chip collision detection with listen-while-talking capability. This effect can be cancelled, although the transmitter will still be connected to the receiver.

# 15


## Clock Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Digital Clock with Alarm  
Oscillator/Clock Generator  
Single Op Amp Clock  
Wide-Frequency TTL Clock

### DIGITAL CLOCK WITH ALARM

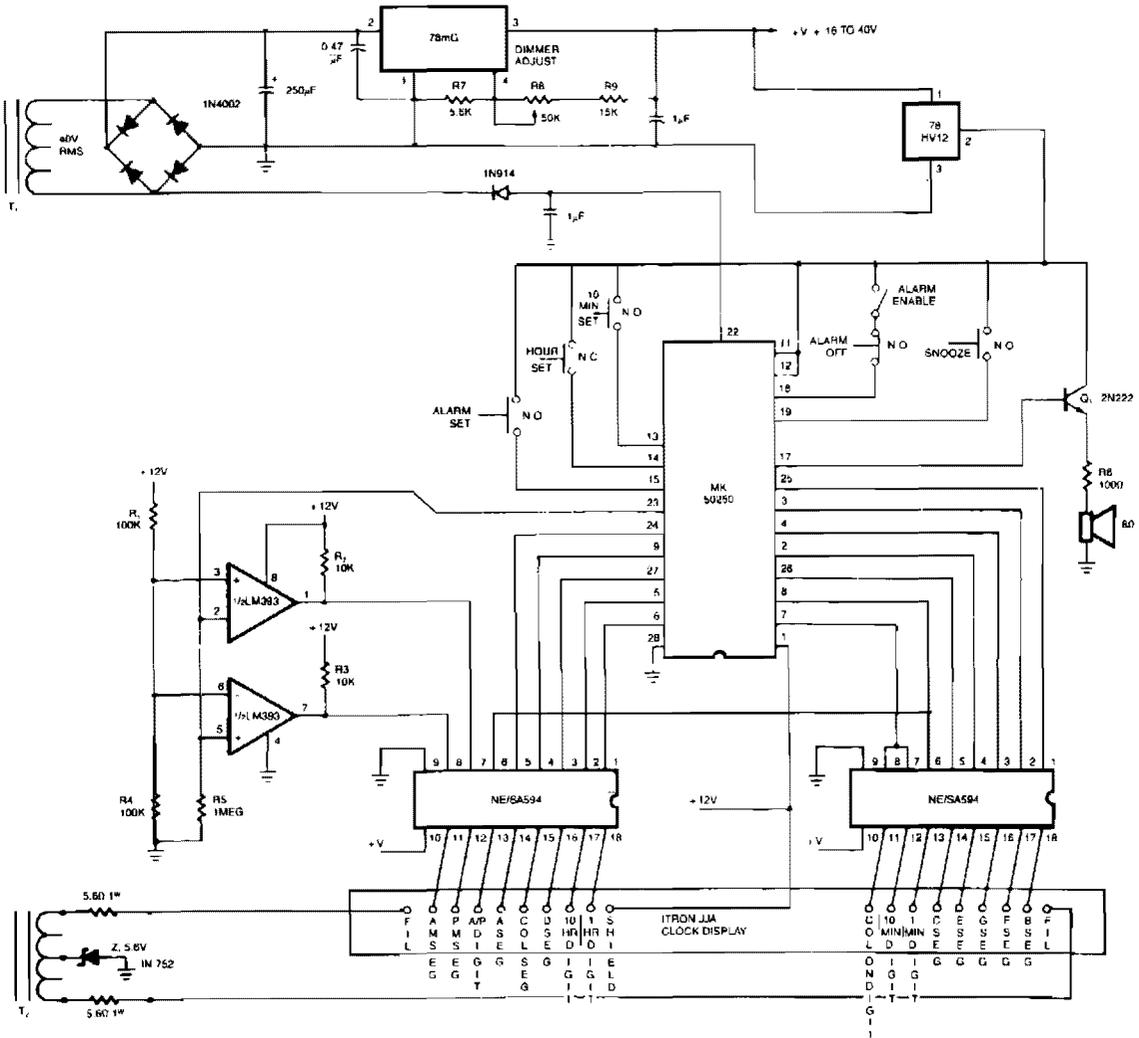

## OSCILLATOR/CLOCK GENERATOR

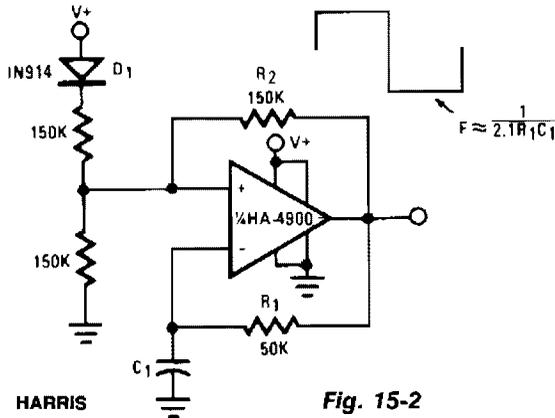


Fig. 15-2

This self-starting fixed-frequency oscillator circuit gives excellent frequency stability. R1 and C1 comprise the frequency-determining network, while R2 provides the regenerative feedback. Diode D1 enhances the stability by compensating for the difference between  $V_{OH}$  and  $V_{SUPPLY}$ . In applications where a precision clock generator up to 100 kHz is required, such as in automatic test equipment, C1 might be replaced by a crystal.

## SINGLE OP AMP CLOCK


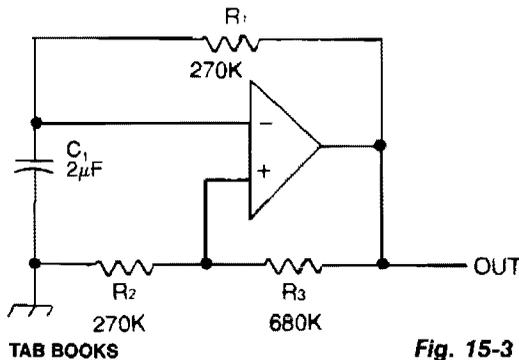


Fig. 15-3

Capacitor C1 is charged through timing resistor R1 when the clock output is high. When C1 reaches the upper threshold voltage, the output signal decreases, and then C1 discharges through R1 until its voltage reaches the lower threshold point. When this happens, the output increases again and the cycle repeats itself. Using the parts values shown results in a frequency of 1 Hz. The output frequency can be adjusted by trimming the value of R1 slightly.

## WIDE-FREQUENCY TTL CLOCK

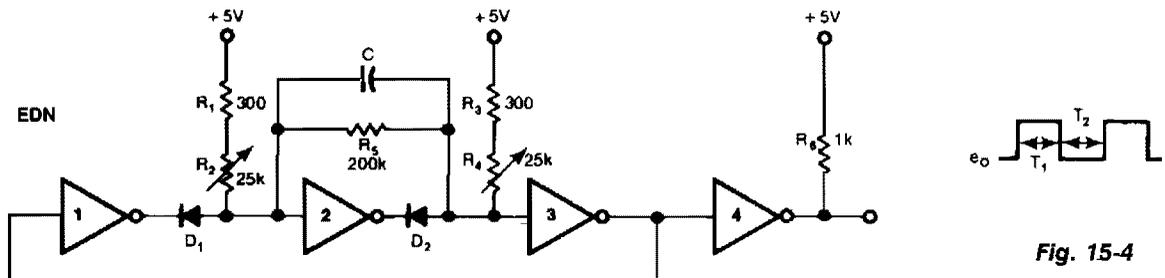

This free-running TTL square-wave oscillator has a variable frequency output over a 20:1 range or better through use of four of the six inverters in an SN7404 chip and the additional components shown. Frequency of oscillation is determined by the capacitor and the settings of potentiometers R2 and R4; the first pot controls width T1 and the second controls width T2 of the square-wave output. These adjustments are not completely independent.

# 16

## Comparators


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Window Comparator  
Microvolt Comparator with Hysteresis  
Comparator/Latch  
Frequency-Detecting Comparator  
Precision Comparator with Balanced Outputs  
and Variable Offset

Dual Limit Microvolt Comparator  
Window Comparator  
Four-Channel Comparator

## WINDOW COMPARATOR

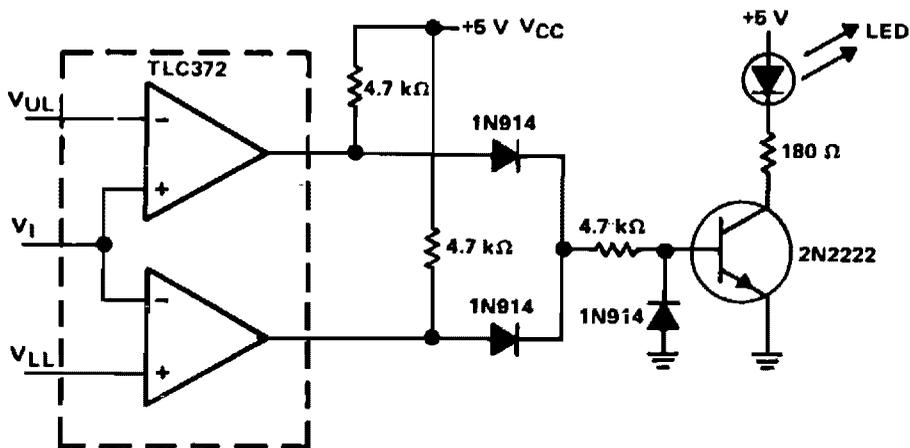

Window Comparator with LED Indicator

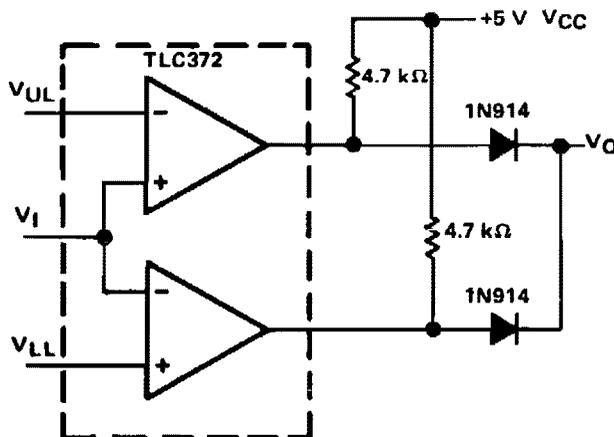


Basic Window Comparator

Fig. 16-1

Reprinted by permission of Texas Instruments.

A window detector is a specialized comparator circuit designed to detect the presence of a voltage between two prescribed limits; that is, within a voltage *window*. This circuit is implemented by logically combining the outputs of two single-ended comparators by the 1N914 diodes. When the input voltage is between the upper limit,  $V_{UL}$ , and the lower limit,  $V_{LL}$ , the output voltage is zero; otherwise it equals a logic high level. The output of this circuit can be used to drive a logic gate, LED driver, or relay driver circuit. The circuit shown in Fig. 16-1 shows a 2N2222 npn transistor being driven by the window comparator. When the input voltage to the window comparator is outside the range set by the  $V_{UL}$  and  $V_{LL}$  inputs, the output changes to positive, which turns on the transistor and lights the LED indicator.

## MICROVOLT COMPARATOR WITH HYSTERESIS

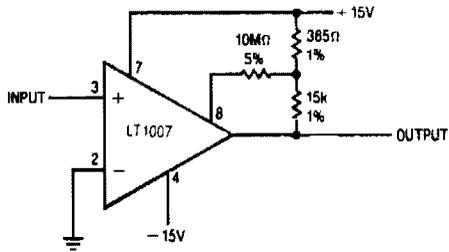


LINEAR TECHNOLOGY

Fig. 16-2

Positive feedback to one of the nulling terminals creates approximately  $5 \mu\text{V}$  of hysteresis. The output can sink 16 mA; the input offset voltage is typically changed less than  $5 \mu\text{V}$  because of the feedback.

## COMPARATOR/LATCH

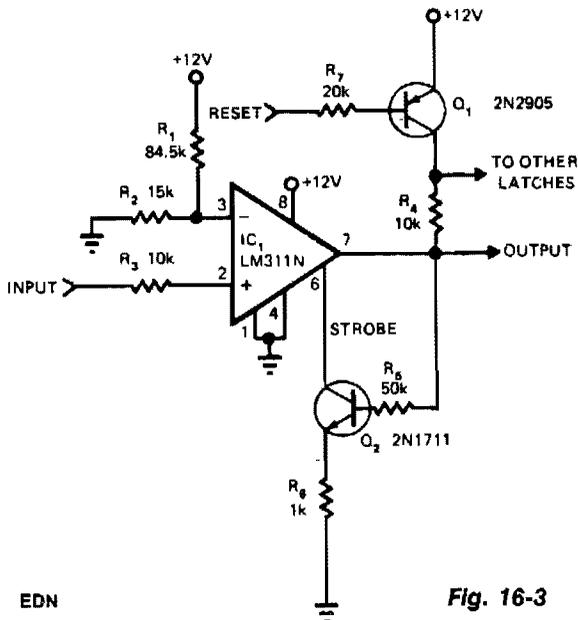


EDN

Fig. 16-3

The primary advantage of this circuit, when compared to other comparators, is its ability to latch after the input has reached a predetermined threshold level. When the input exceeds the threshold level, the LM311N output increases. This transition enables the strobe input, preventing the output from falling low. A high-level voltage on the reset input will turn off Q1, thereby removing the supply voltage from the open collector output of the LM311N. With no supply to the strobe input, the latch condition is removed and the output is again allowed to follow the input excursions. The LM311N will operate with a wide variety of supply voltage levels, ranging from dual  $\pm 15\text{ V}$  to a single 5 V level that provides compatibility with digital IC logic. If more than one latch is used with a common reset, all the pull-up resistors may be connected to Q1's collector.

## FREQUENCY-DETECTING COMPARATOR

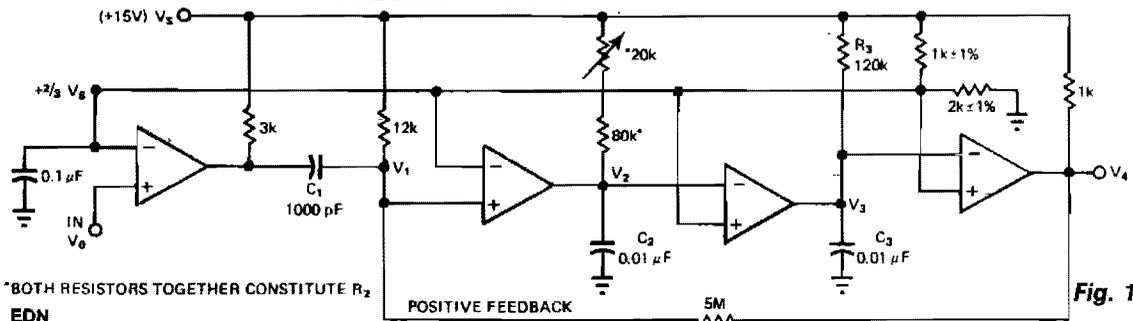

\*BOTH RESISTORS TOGETHER CONSTITUTE  $R_2$   
EDN

Fig. 16-4



## WINDOW COMPARATOR

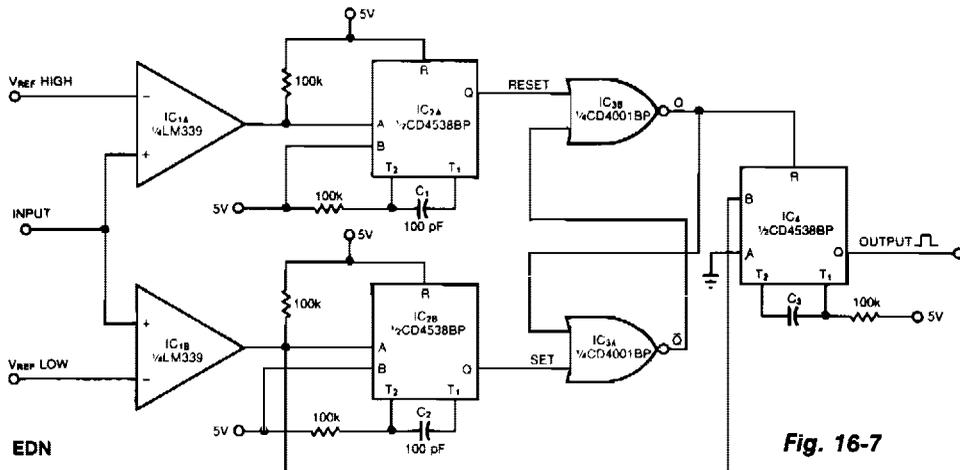


Fig. 16-7

This window comparator generates an output pulse for each event that occurs within a specified window. That is, each output pulse signifies an input voltage pulse or level change that exceeds  $V_{REFLOW}$ , but not  $V_{REFHIGH}$ . The monostable multivibrators, IC2A and IC2B, produce a 10- $\mu$ s pulse at their Q output in response to a rising edge at their A input. Comparator IC1B produces a rising edge when the input exceeds  $V_{REFLOW}$ , and comparator IC2A produces a rising edge when the input exceeds  $V_{REFHIGH}$ . The NOR gates, IC3A and IC3B, form a bistable latch whose Q output, when low, disables IC4. IC4, unless disabled, produces output pulses in response to falling edges at the IC1B comparator output. You set the width of these pulses by selecting the value of C3. The circuit can handle an input waveform containing 0 to 2 V amplitudes and 10-Hz to 10-kHz frequency components.

## FOUR-CHANNEL COMPARATOR

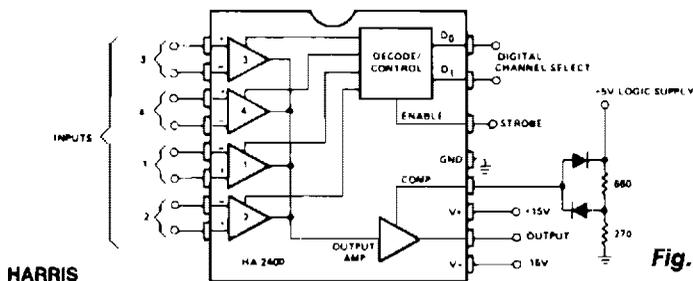


Fig. 16-8

When operated as an open loop without compensation, the HA-2400 becomes a comparator with four selectable input channels. The clamping network at the compensation pin limits the output voltage to allow DTL or TTL digital circuits to be driven with a fanout of up to ten loads.

The circuit can be used to compare several signals against each other or against fixed references; or a single signal can be compared against several references. A window comparator, which assures that a signal is within a voltage range, can be formed by monitoring the output polarity, while rapidly switching between two channels with different reference inputs and the same signal input.

# 17


## Compressor/Expander Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Low-Voltage Compander  
Hi-Fi Compressor with Pre-Emphasis  
Variable Slope Compressor/Expander  
Hi-Fi Expander with De-Emphasis

## LOW-VOLTAGE COMPANDER

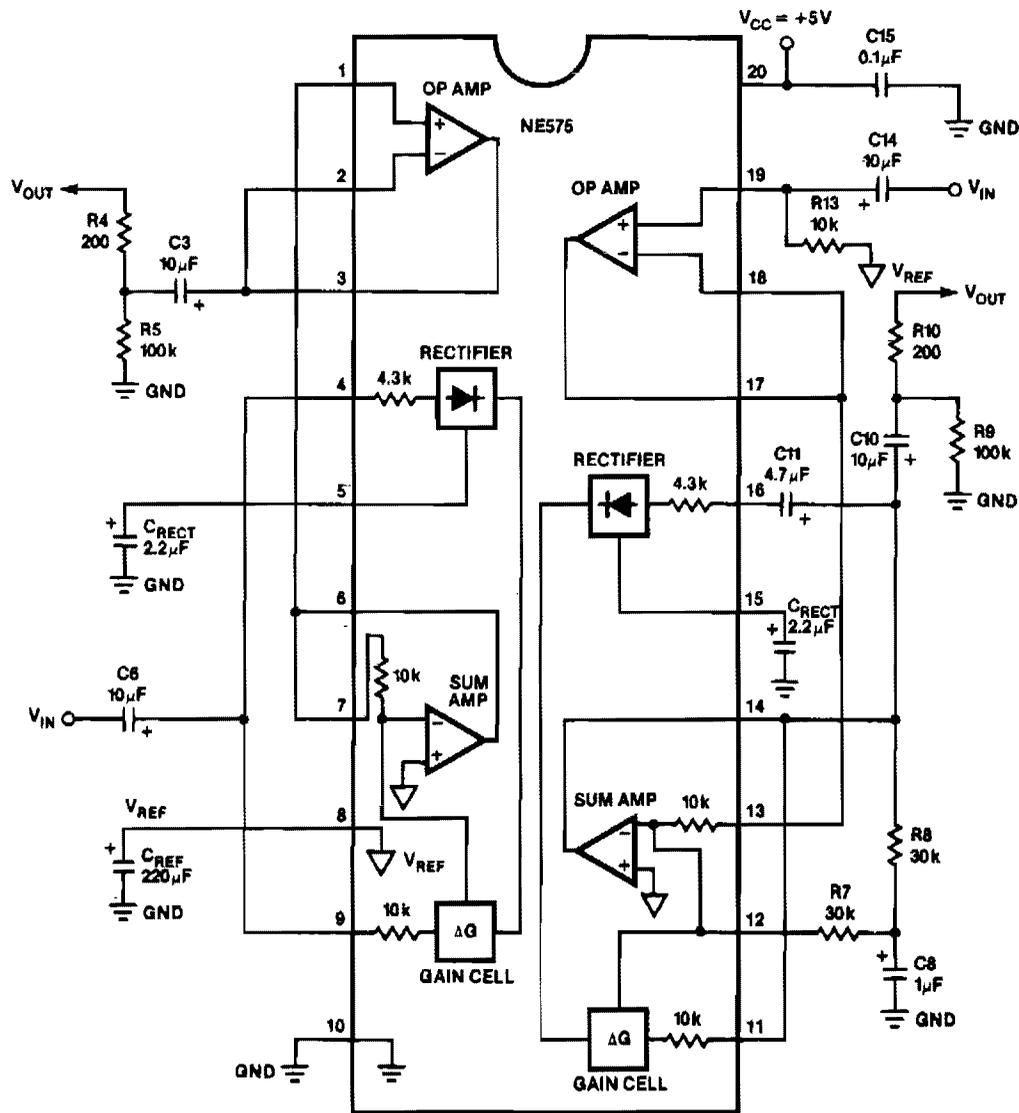


**NOTE:**  
 Left channel in expander mode; right channel in compressor mode.  
 For additional information, call the factory.

**SIGNETICS**

**Fig. 17-1**

The NE575 is a dual-gain control circuit designed for low voltage applications. The NE575's channel 1 is an expander, while channel 2 can be configured either for expander, compressor, or automatic level controller (ALC) applications.

## HI-FI COMPRESSOR WITH PRE-EMPHASIS

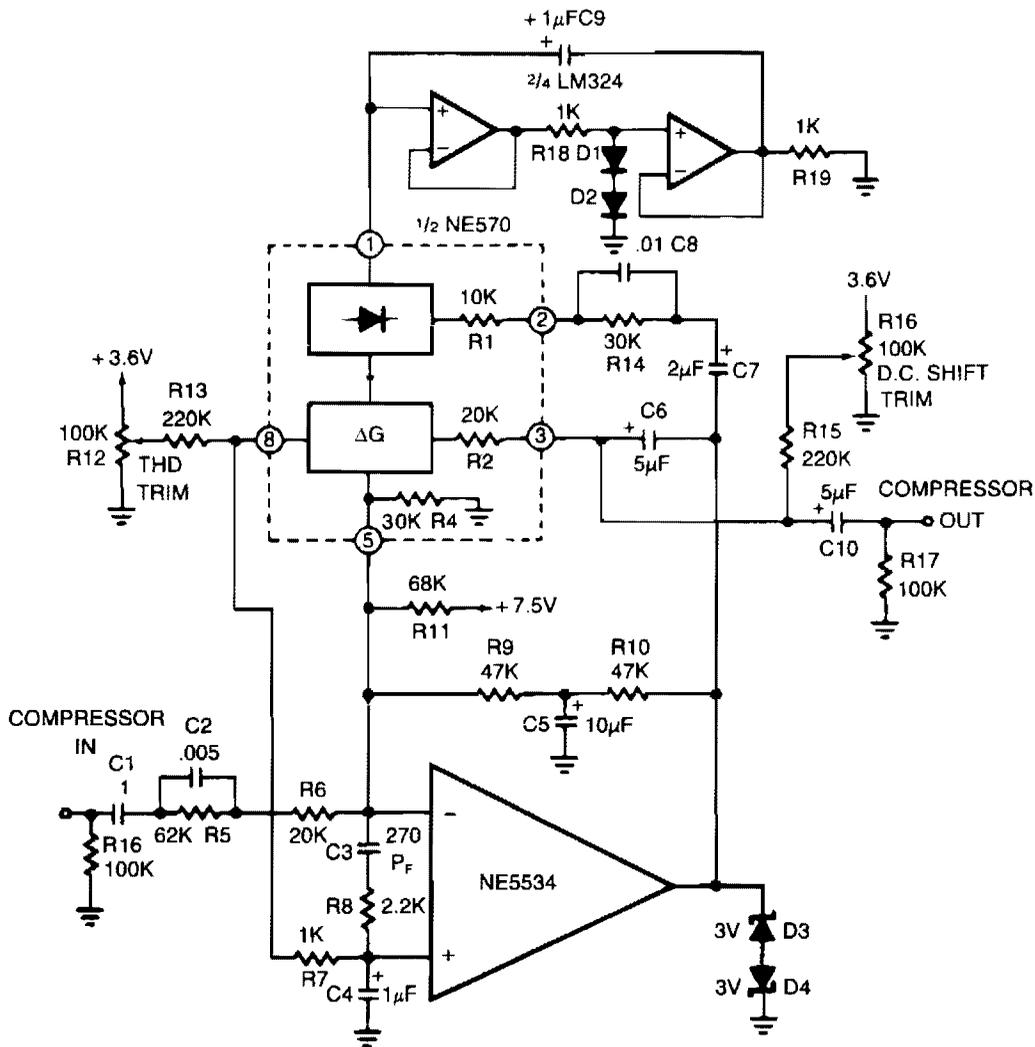


SIGNETICS

Fig. 17-2

The compressor contains a high-frequency, pre-emphasis circuit (C2, R5, and C8, R14), which helps solve this problem. Matching de-emphasis on the expander is required. More complex designs could make the pre-emphasis variable.

## VARIABLE SLOPE COMPRESSOR/EXPANDER

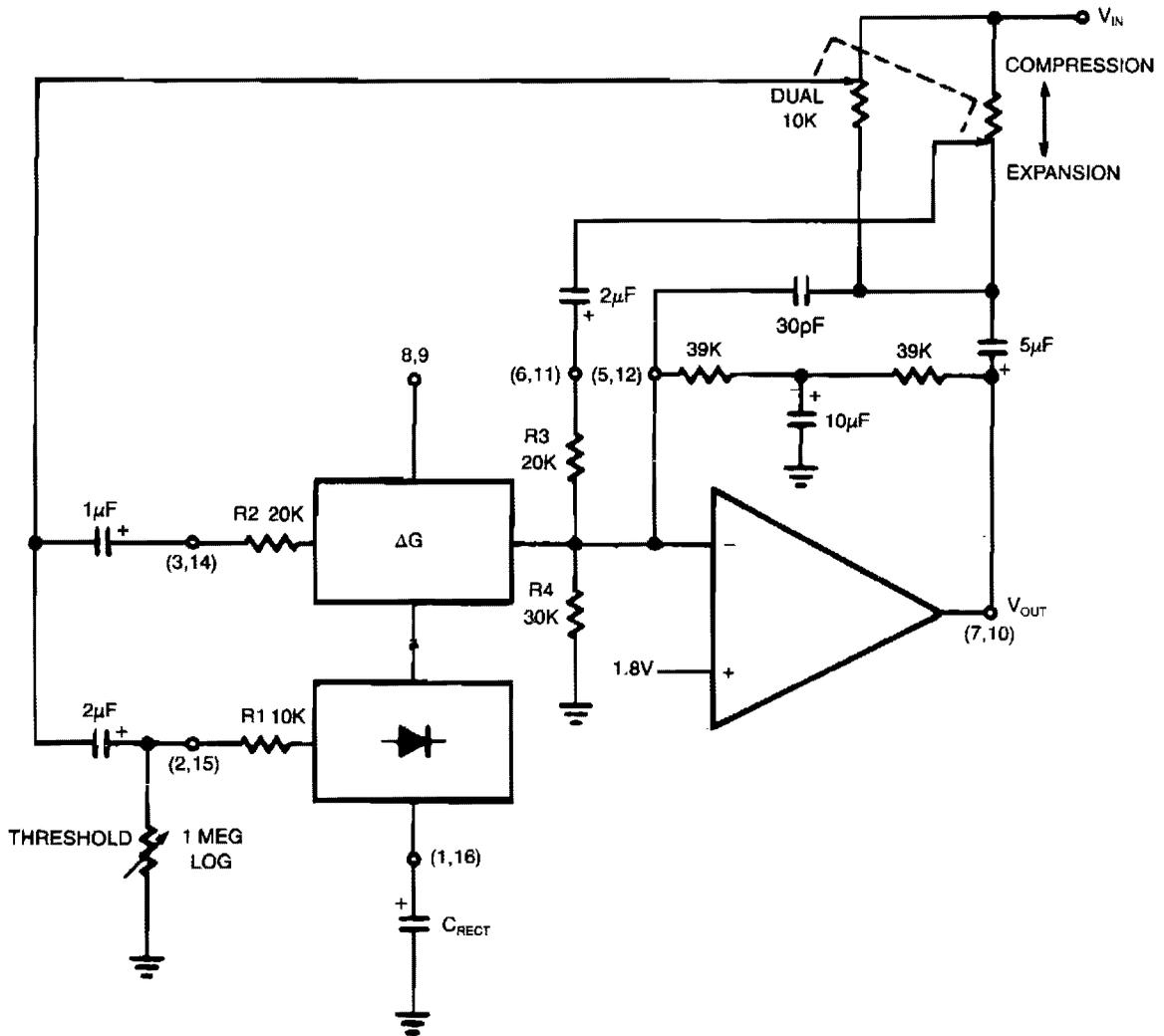


SIGNETICS

Fig. 17-3

Compression and expansion ratios other than 2:1 can be achieved by the circuit shown. Rotation of the dual potentiometer causes the circuit hook-up to change from a basic compressor to a basic expander. In the center of rotation, the circuit is 1:1, has neither compression nor expansion. The (input) output transfer characteristic is thus continuously variable from 2:1 compression to 1:2 expansion. If a fixed compression or expansion ratio is desired, proper selection of fixed resistors can be used instead of the potentiometer. The optional threshold resistor will make the compression or expansion ratio deviate towards 1:1 at low levels. A wide variety of (input) output characteristics can be created with this circuit.

## HI-FI EXPANDER WITH DE-EMPHASIS

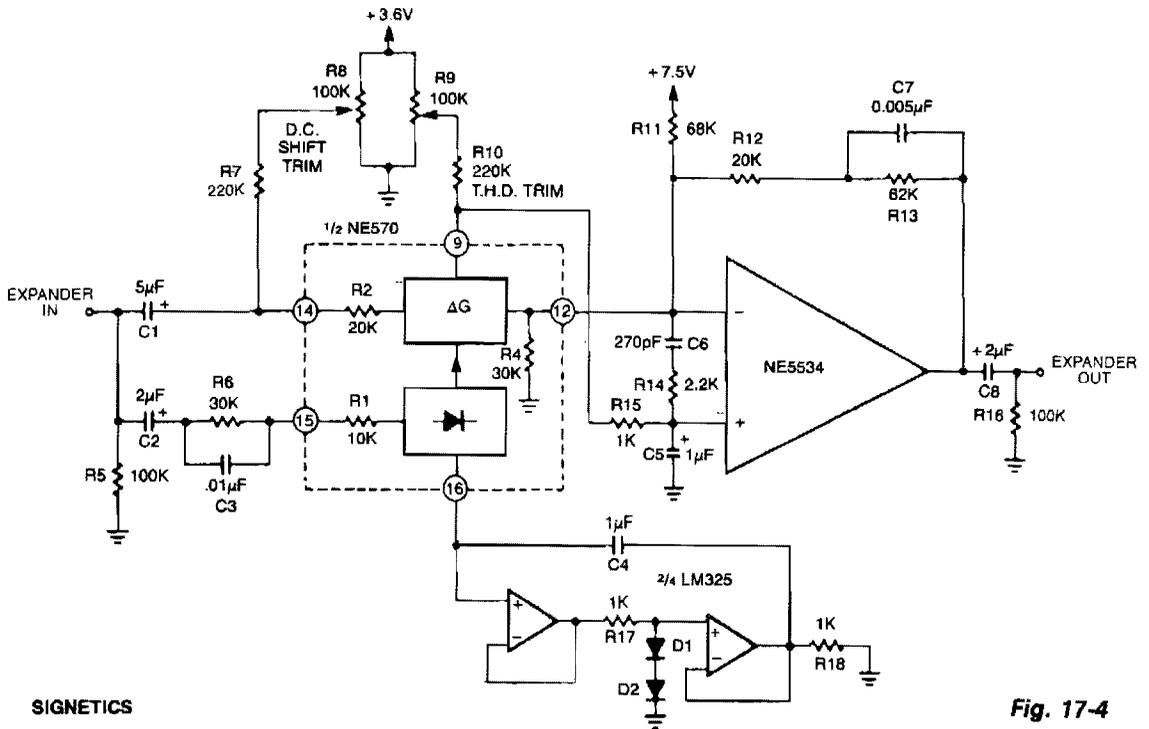

The expander to complement the compressor is shown. An external op amp is used for high slew rate. Both the compressor and expander have unity gain levels of 0 dB. Trim networks are shown for distortion (THD) and dc shift. The distortion trim should be done first, with an input of 0 dB at 10 kHz. The dc shift should be adjusted for minimum envelope bounce with tone bursts. When applied to consumer tape recorders, the subjective performance of this system is excellent.

# 18


## Computer Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Automatic RS-232 Datasector	RS-232C LED Circuit
Interface to 680X, 650X, and 8080 Families	Spare Flip-Flop Inverter
RGB Blue Box	Coprocessor Socket Debugger
5V-Powered EEPROM Pulse Generator	20-MHz-to-NuBus Clock Phase Lock
One-of-Eight Channel Transmission System	XOR Gate Up/Down Converter
Microprocessor-Controlled Analog Signal Attenuator	Eight-Digit Microprocessor Display
Multiple Input Detector	Logic Line Monitor
RS-232-to-CMOS Line Receiver	Long Delay Line for Logic Signals

## AUTOMATIC RS-232 DATASELECTOR

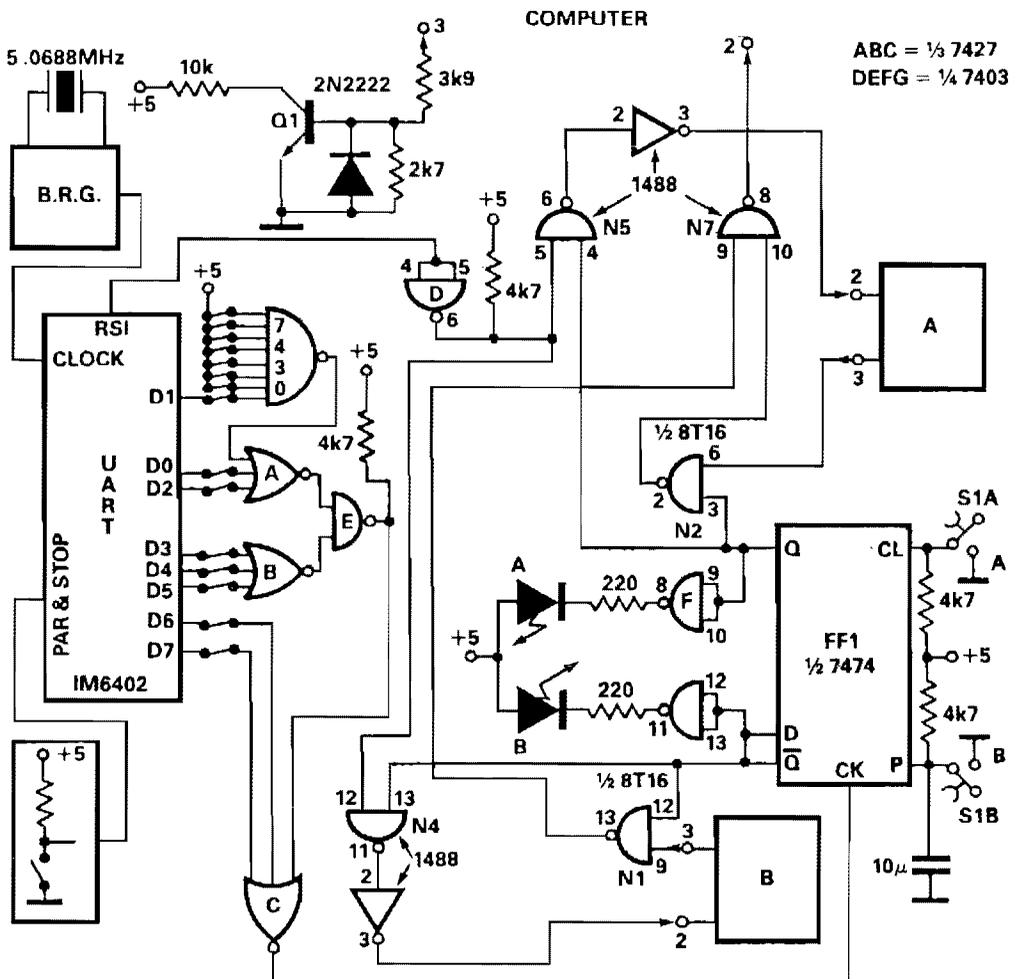

ELECTRONIC ENGINEERING

Fig. 18-1

With this datas selector, only one RS-232 port is used to connect two RS-232 devices (i.e., printer, plotter, etc.) with a mini- or microcomputer. The operation is very simple. Power on will reset FFI ( $Q_{FFI} = \text{Low}$ ), which enables gates N1, N5, and N7. Now communication between computer and device B is possible. Detection of the switch command, i.e., Control B character = CHR\$(2), selectable with wire-wrap pins, on the parallel outputs of the UART (IM 6402 or equivalent) will set:  $Q_{FFI} = \text{High}$ . Gates N2, N5, and N7 are open, so device A is connected with the computer until Control B character is detected again.

Transistor Q1 converts RS-232 levels to TTL levels while two LEDs indicate whether device A or B is linked. The baud-rate generator provides the  $16 \times$  clock needed for the UART. Any baud rate ranging from 50 to 19200 can be selected. Manual control of the selector is available with toggleswitch S1.

## INTERFACE TO 680X, 650X, AND 8080 FAMILIES

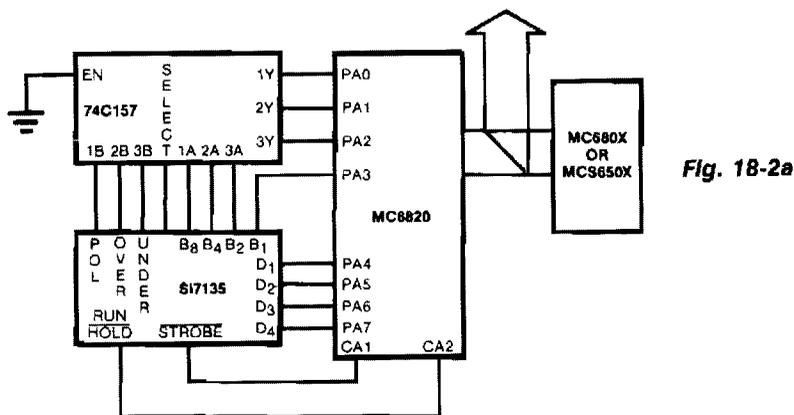


Fig. 18-2a

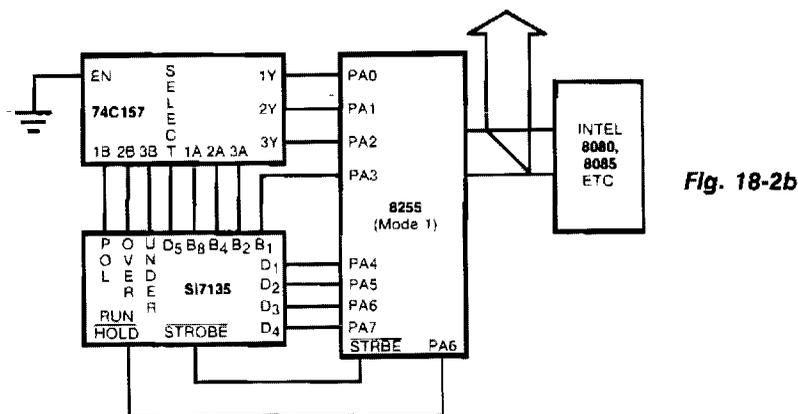


Fig. 18-2b

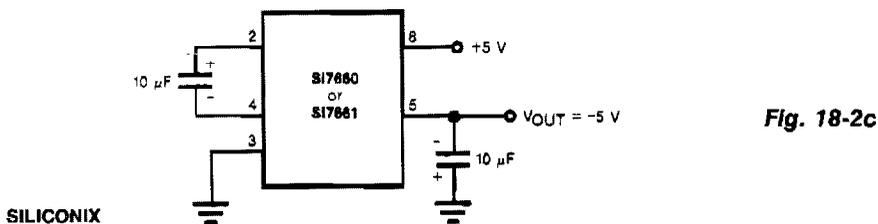


Fig. 18-2c

SILICONIX

Circuits to interface the Si7135 directly with two popular microprocessors are shown in Figs. 18-2a and b. The 8080/8048 and the MC6800 families with 8-bit words need to have polarity, overrange, and underrange multiplexed onto the digit 5 word. In each case, the microprocessor can instruct the ADC when to begin a measurement and when to hold this measurement. The Si7135 is designed to work from  $\pm 5$  V supplies. However, if a negative supply is not available, it can be generated using 2 capacitors, and an inexpensive Si7660 or Si7661 IC, as shown in Fig. 18-2c.

## RGB BLUE BOX


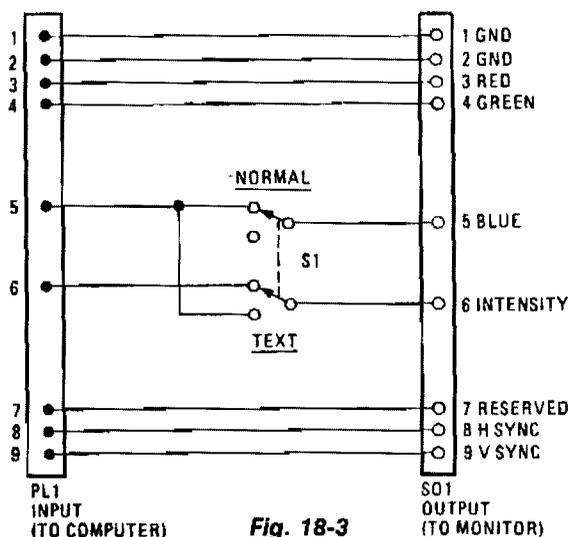


Fig. 18-3

HANDS-ON-ELECTRONICS/POPULAR ELECTRONICS

The RGB blue box turns your PC's RGB-monitor screen blue at the flip of a switch. That is, it makes your computer display bright white text on a blue background, instead of the usual low-intensity white on black. The RGB blue box connects between your IBM PC color graphics adapter, or equivalent, and your RGB color monitor. By flipping a switch, you choose between two modes. One mode passes the signal from the PC to the monitor unaltered; the other transforms it to make text more readable. The monitor has four TTL-level inputs—red, green, blue, and intensity—and it interprets disconnected wires as on. That's why the screen turns white if you disconnect the monitor from the computer, and blue if you disconnect only the blue line. Instead of just discarding the blue signal, the blue box reroutes it to the intensity input. As a result, most of the text colors come out intensified.

## 5V-POWERED EEPROM PULSE GENERATOR

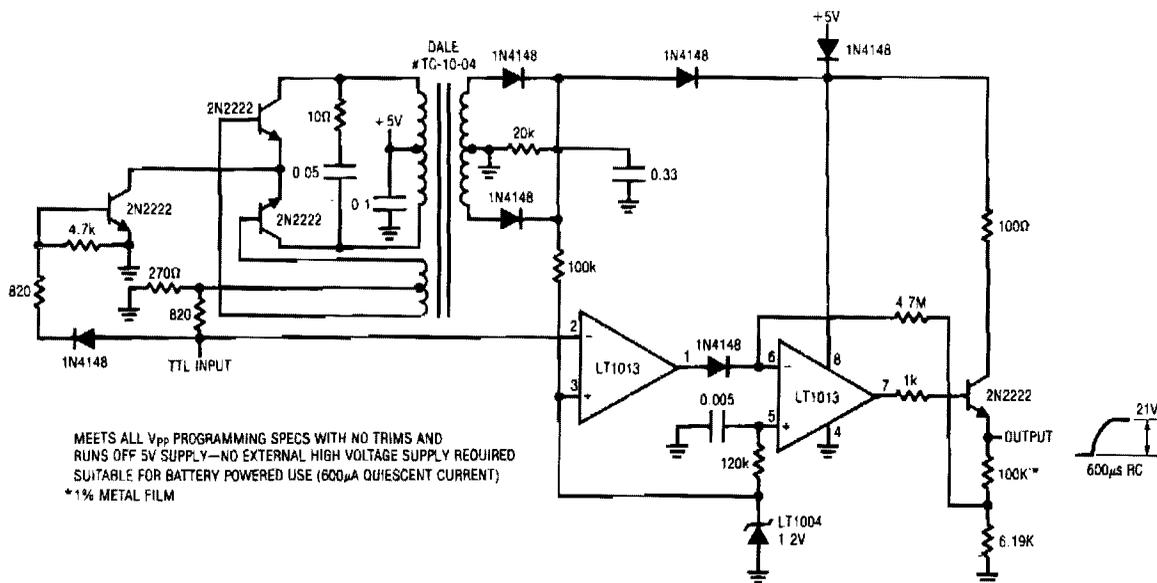


MEETS ALL  $V_{pp}$  PROGRAMMING SPECS WITH NO TRIMS AND RUNS OFF 5V SUPPLY—NO EXTERNAL HIGH VOLTAGE SUPPLY REQUIRED SUITABLE FOR BATTERY POWERED USE (600μA QUIESCENT CURRENT)  
\*1% METAL FILM


LINEAR TECHNOLOGY CORP.

Fig. 18-4
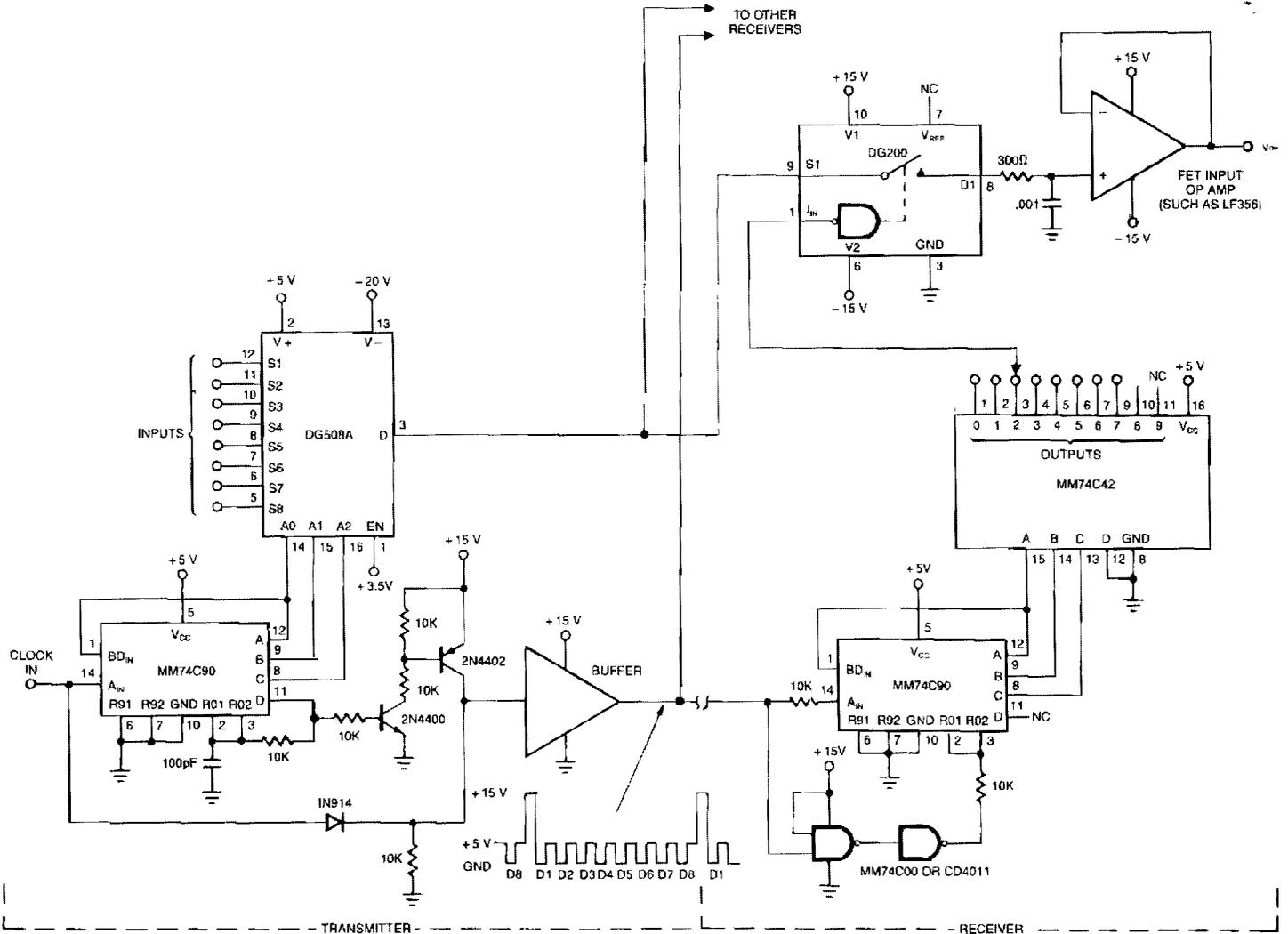
# ONE-OF-EIGHT CHANNEL TRANSMISSION SYSTEM



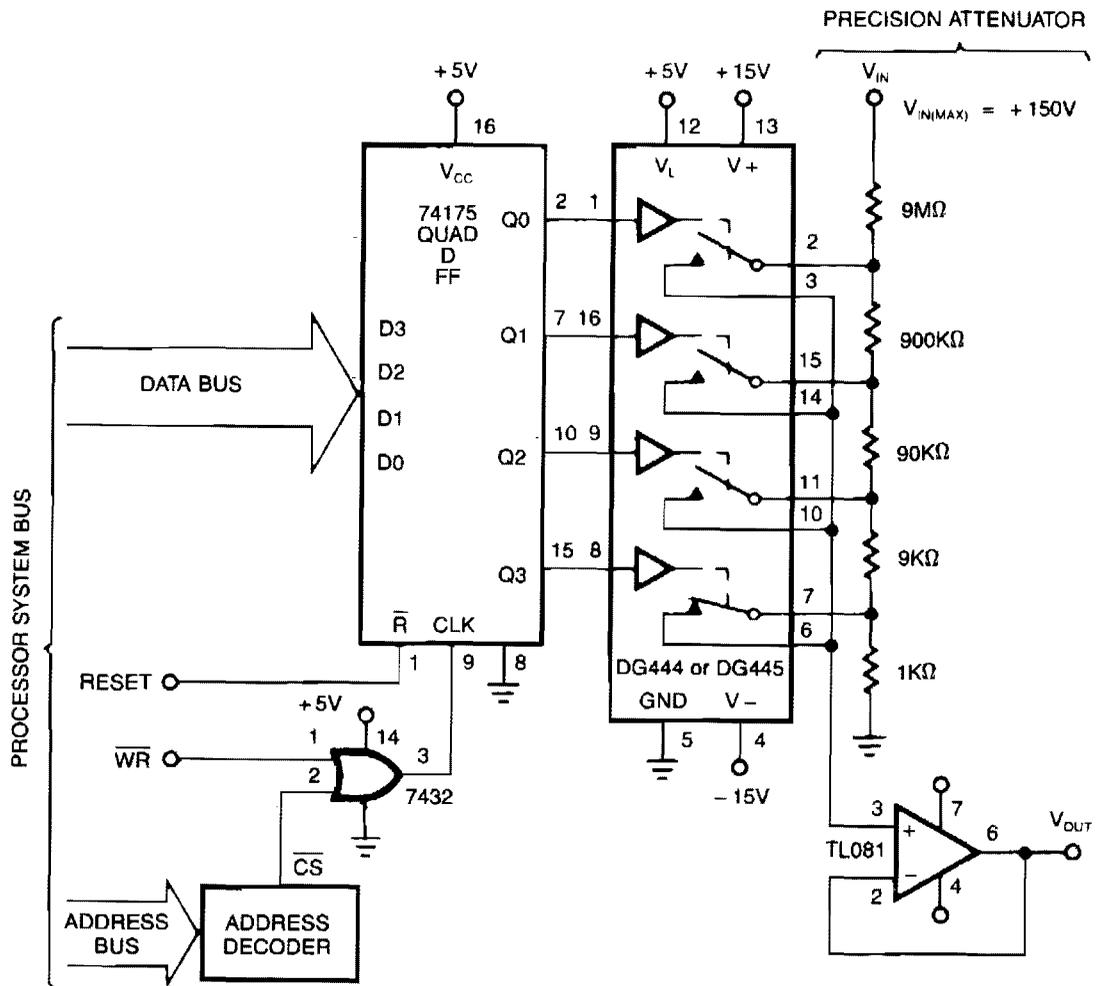
# MICROPROCESSOR-CONTROLLED ANALOG SIGNAL ATTENUATOR



SILICONIX

Fig. 18-6

## MULTIPLE INPUT DETECTOR

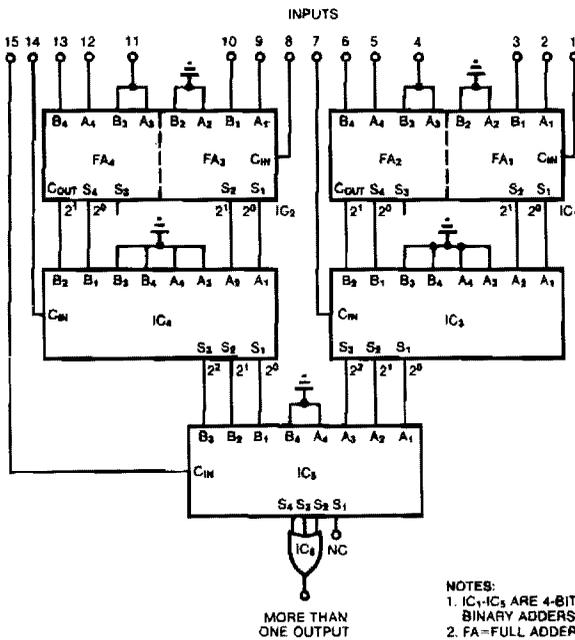


This circuit determines whether more than one input in a group of digital inputs is active. It provides a digital measure of the number of active inputs, and it allows you to establish a threshold for majority-decision applications. That is, whether the number of active inputs is more than, less than, or equal to a value between 1 and 15. You can monitor more inputs by cascading the adders.

Each binary adder, IC1 and IC2, forms two full adders (FAs). Each FA monitors three input lines and generates a 2-bit output representing the number of inputs active. IC3 and IC4, by summing the outputs of two FAs plus an input line, individually measure how many in a group of seven inputs are active. Similarly, by monitoring the 3-bit outputs of IC3 and IC4 plus one input, IC5 measures how many in the group of 15 are active. The OR gate, IC6, simply indicates whether more than one input is active.

EDN

**Fig. 18-7**

## RS-232-TO-CMOS LINE RECEIVER

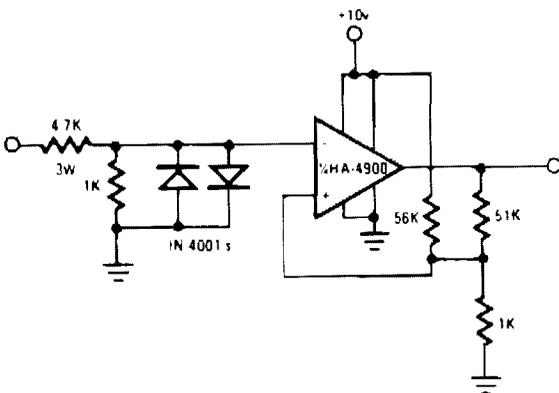

This RS-232 type line receiver to drive CMOS logic uses a Schmitt-trigger feedback network to give about 1-V input hysteresis for added noise immunity. A possible problem in an interface which connects two pieces of equipment, each plugged into a different ac receptacle, is that the power line voltage might appear at the receiver input when the interface connection is made or broken. The two diodes and a 3-W input resistor will protect the inputs under these conditions.

HARRIS

**Fig. 18-8**

## RS-232C LED CIRCUIT


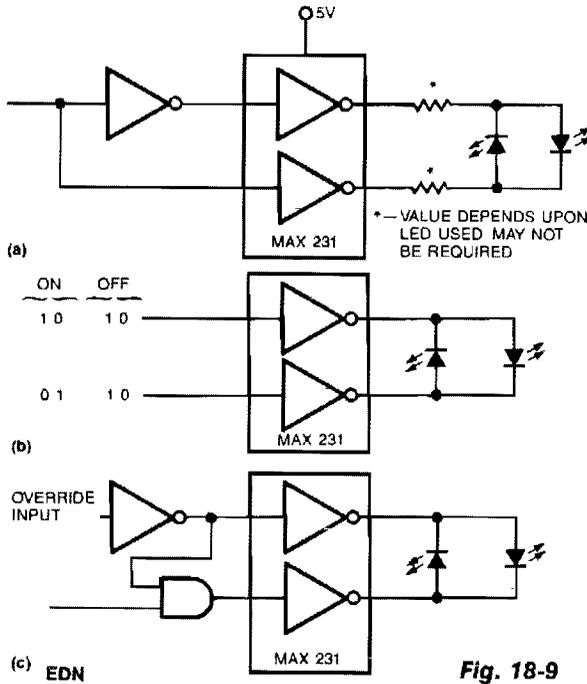


Fig. 18-9

Use a pair of Maxim's 5V-powered MAX231 RS-232C transmitters as drivers to obtain a 2-color LED. The transmitters require only a single-ended, 5-V input to generate  $\pm 10$  V internally. Their outputs are short-circuit-proof and can supply as much as 10 mA—enough to drive most LEDs. Depending on which LED you select, their current-limiting feature might also eliminate the need for external series resistors. Using the simple circuits, you can implement a variety of functions.

## SPARE FLIP-FLOP INVERTER

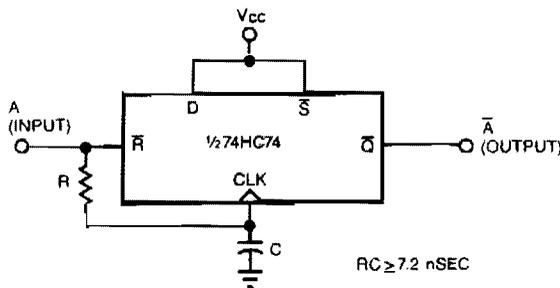


EDN

Fig. 18-10

The circuit uses one-half of a dual D flip-flop as an inverter. When the input decreases, the flip-flop resets, and its  $Q$  output increases. When the input increases, the reset line is released and  $Q$  gets clocked low. The  $rc$  delay between applying the input signal to the flip-flop's reset input and its clock input enables clocking the flip-flop on the input's positive edge. A 74HC74 dual D flip-flop, for example, requires a minimum recovery time of 5 ns after releasing the reset input before strobing its clock input. Therefore, spec'ing  $rc$  at greater than 7.5 ns provides adequate margin. The slight slowing of the clock edge presents no problem, because the clock input's maximum allowable rise time is a much longer 500 ns. To prevent skewing of the output's symmetry, limit the maximum input frequency to less than 10 MHz.

## COPROCESSOR SOCKET DEBUGGER

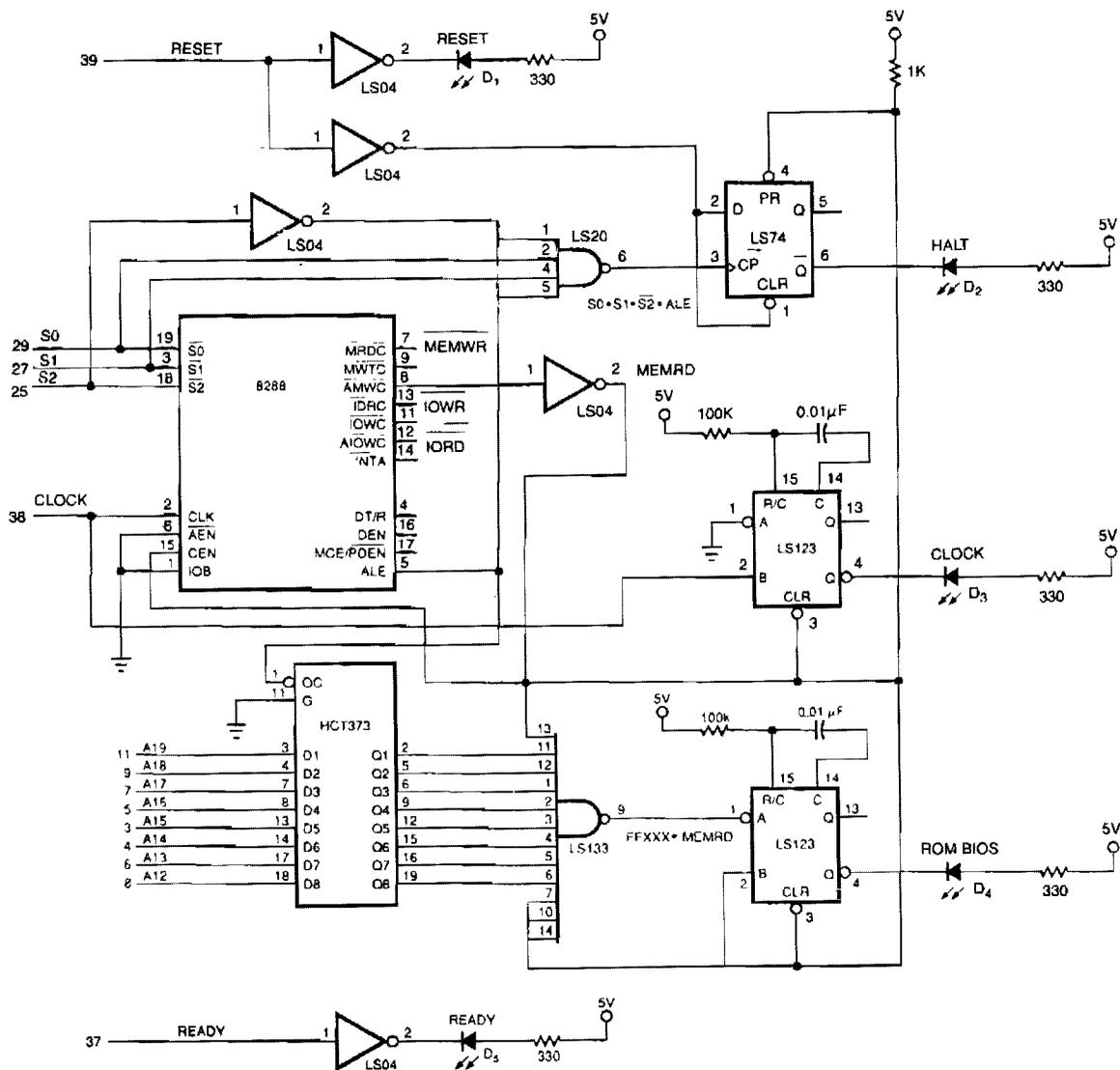

**Fig. 18-11**

The IBM PC debugger plugs into the PC's math-coprocessor socket. The 8288 bus controller, IC1, regenerates control signals from the processor's status signals, S0, S1, and S2. Reset LED D1 lights if reset is active and holding the processor. Clock status LED D3 indicates that the processor is receiving a toggling clock signal. The address-decode logic detects when the processor is doing a jump-on-reset to the PC's BIOS ROM's power-on; self-test then detects a fatal error and halts the processor.

## 20-MHz-TO-NUBUS CLOCK PHASE LOCK


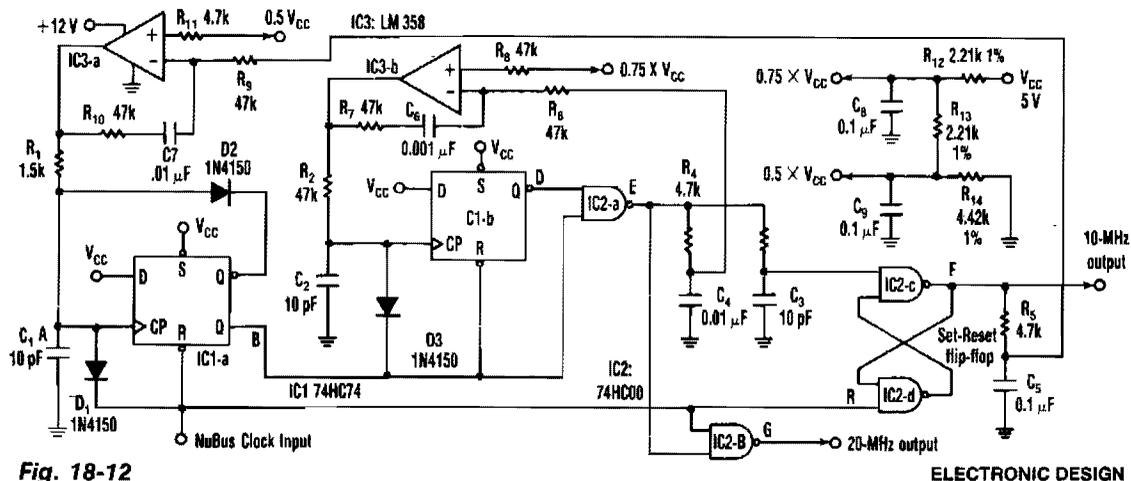


Fig. 18-12

ELECTRONIC DESIGN

The 20-MHz clock phase-locks to Apple's Mac II 10-MHz NuBus clock. It uses a simple, inexpensive CMOS circuitry to generate 10- and 20-MHz square waves. The output duty cycle settings are insensitive to  $V_{CC}$  variations. The input to the circuit is a NuBus clock signal with specifications that call for a 75 percent duty cycle at 10 MHz—a square wave that's high for 75 ns and low for the remaining 25 ns. To generate the 20-MHz signal, the circuit produces a 25-ns negative-going pulse, delayed 50 ns from the falling edge of the 10-MHz NuBus clock input at point E. NORing that pulse with the NuBus clock produces the 20-MHz clock at point G. Finally, applying the 25-ns pulse to the set input of a set-reset input, results in a 10-MHz square wave at F.

## XOR GATE UP/DOWN COUNTER

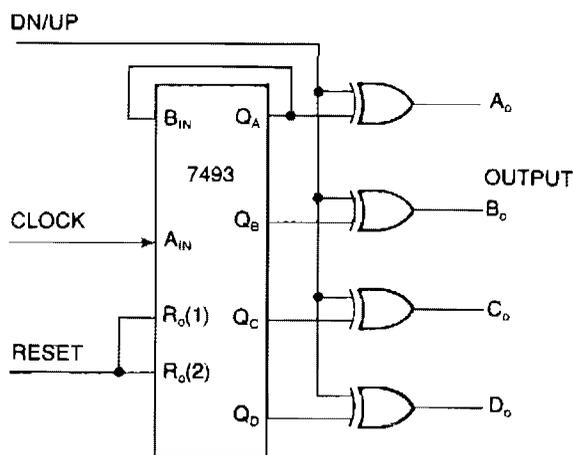

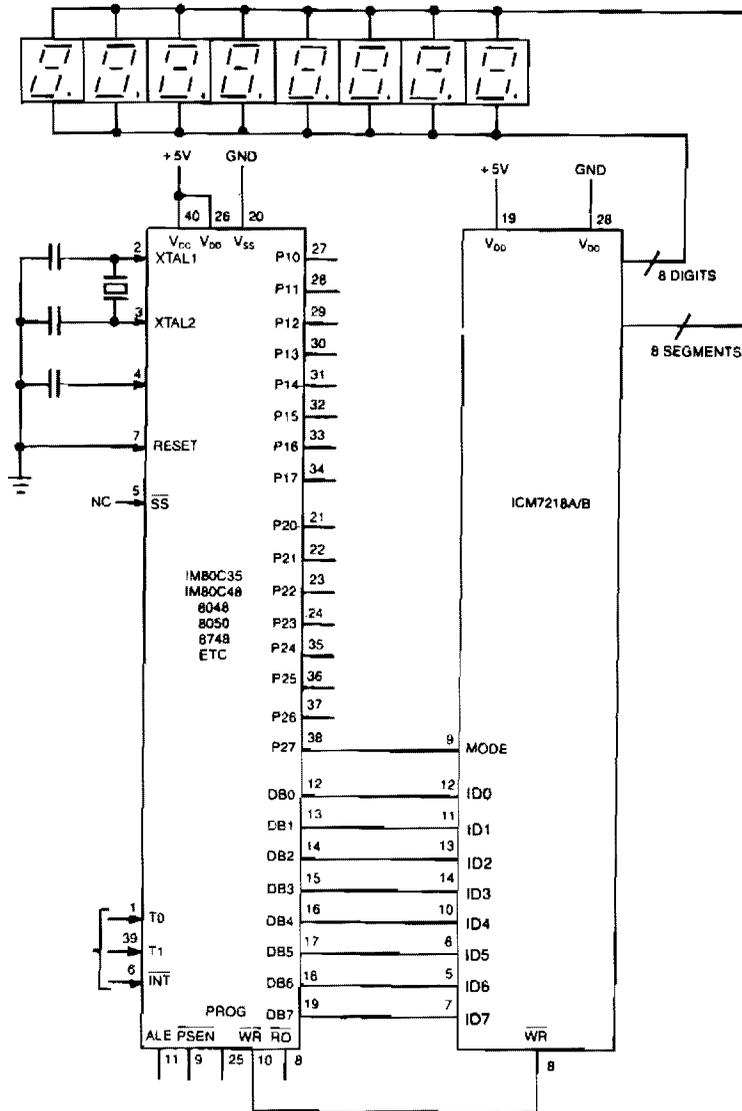
EDN

Fig. 18-13

One can transform an ordinary binary counter, such as a 7493, into an up/down counter with mode control by adding XOR gates 7486 to the counter's outputs. The circuit counts up when the DN/UP line is low and down when the DN/UP line is high.

To use the 7493 counter to count out its maximum count length of 0–15, connect the  $Q_A$  output to the  $B_{IN}$  input and apply clock pulses to the  $A_{IN}$  input. The reset input, when high, inhibits the count inputs and simultaneously returns the outputs  $A_o$  through  $D_o$  to low in the up-count mode or 15 in the down-count mode. For normal counting, the reset input must be low. One can easily cascade this counter by feeding the  $Q_D$  line to the clock input of a succeeding counter.

## EIGHT-DIGIT MICROPROCESSOR DISPLAY

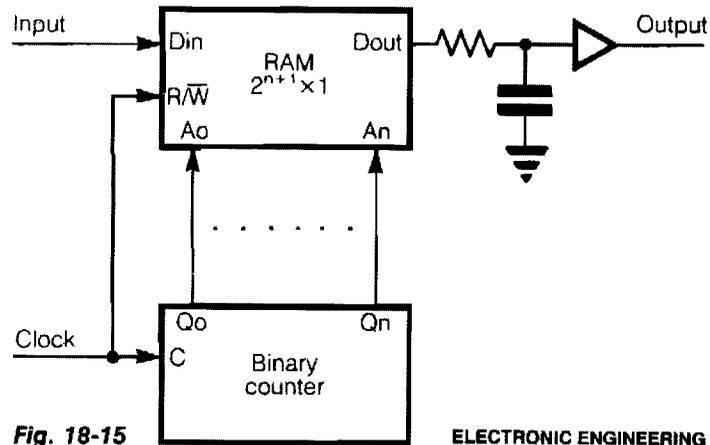


**Fig. 18-14**

INTERSIL

Display interface uses the ICM7218A/B with an 8048 family microcontroller. The 8-bit data bus (DB0/DB7 – ID0/ID7) transfers control and data information to the 7218 display interface on successive WRITE pulses. The mode input pins on the microcontroller. When mode is high, a control word is transferred; when mode is low, data is transferred. Sequential locations in the 8-byte static memory are automatically loaded on each successive WRITE pulse. After eight WRITE pulses have occurred, further pulses are ignored until a new control word is transferred.

## LONG DELAY LINE FOR LOGIC SIGNALS



**Fig. 18-15**

**ELECTRONIC ENGINEERING**

An extremely long delay of logic signal can be accomplished with this circuit. The logic signals to be delayed are applied to the  $D_{IN}$  of RAM. Address lines  $A_0, A_1, \dots, A_n$  are connected to outputs  $Q_0, Q_1, \dots, Q_n$  of a binary counter. Clock input of counter and  $R/\bar{W}$  input of RAM are joined together. However, it is sometimes necessary to put an inverter between those inputs, depending on the RAM and counter employed in line. In the first half of clock interval, content on outputs of counter is increased for 1 and content of chosen memory cell is read; in the second half of the clock interval, new content from  $D_{IN}$  in the same memory cell is written. When full cycles of counting reaches the same memory cell, again we can read, in the first half of the clock interval of the following counting cycles, the chosen content. Delay time is:

$$T_d = 2^{n+1} \cdot t_{cl}$$

If clock frequency is not a multiple of input signal frequency, distortion of input signal is proportioned to the clock period. But if the clock frequency is a multiple of input signal frequency, there is no distortion. If we use RAM organized according to  $2^{n+1} \times 4$  with separated data inputs and data outputs, we can have four parallel long delay lines. The resistor, capacitor, and buffer on  $D_{OUT}$  of RAM are used to save output signal in writing time, when output of RAM becomes high impedance.

## LOGIC LINE MONITOR

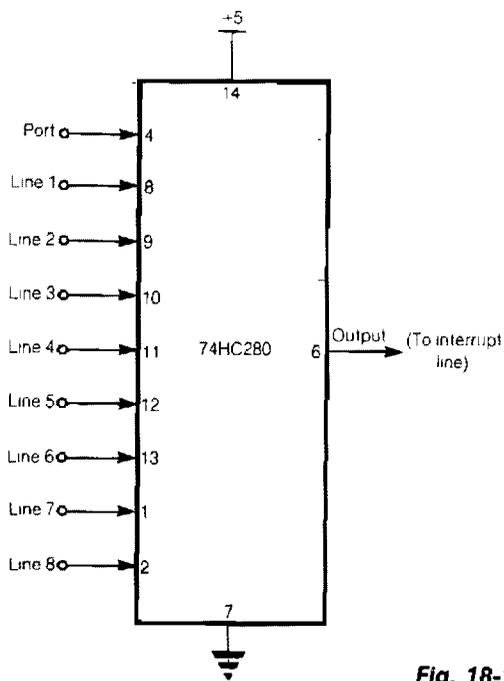


Fig. 18-16

This circuit requires only one CMOS IC, which is available in a 14-pin surface-mount package. The figure shows the logic lines going to a standard 9-bit parity comparator chip. This device is conventionally used in data transmission and recording applications to provide a means of error-detection by comparing the received eight- or nine-bit words with their corresponding parity bits. If the sum of the one's in a received word is odd but the odd-parity bit is low, then that word is known to be in error and requires retransmission.

When one of the logic lines decreases, the output of the parity comparator decreases, generating a *wake-up* interrupt to the microprocessor. The ninth line comes from a port on the microprocessor and is toggled to reset the output signal high again, ready for the next logic change.

# 19

## Converters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

10 Hz-to-10 kHz V/F Converter

Low-Frequency Converter

Positive-to-Negative Converter

Buck/Boost Converter

4 – 18 MHz Converter

Shortwave Converter

Isolated +15 V Dc-Dc Converter

Voltage Ratio-to-Frequency Converter

50-MHz Thermal Rms-to-Dc Converter

Pulse Width-to-Voltage Converter

Step Up/Down Dc-Dc Converter

Square-to-Sine Wave Converter

Pulse Height-to-Width Converter


PIN Photodiode-to-Frequency Converter

Zero  $I_B$  Error V/I Converter

Regulated Dc-Dc Converter

Pulse Train-to-Sinusoid Converter


# 10 Hz-TO-10kHz V/F CONVERTER

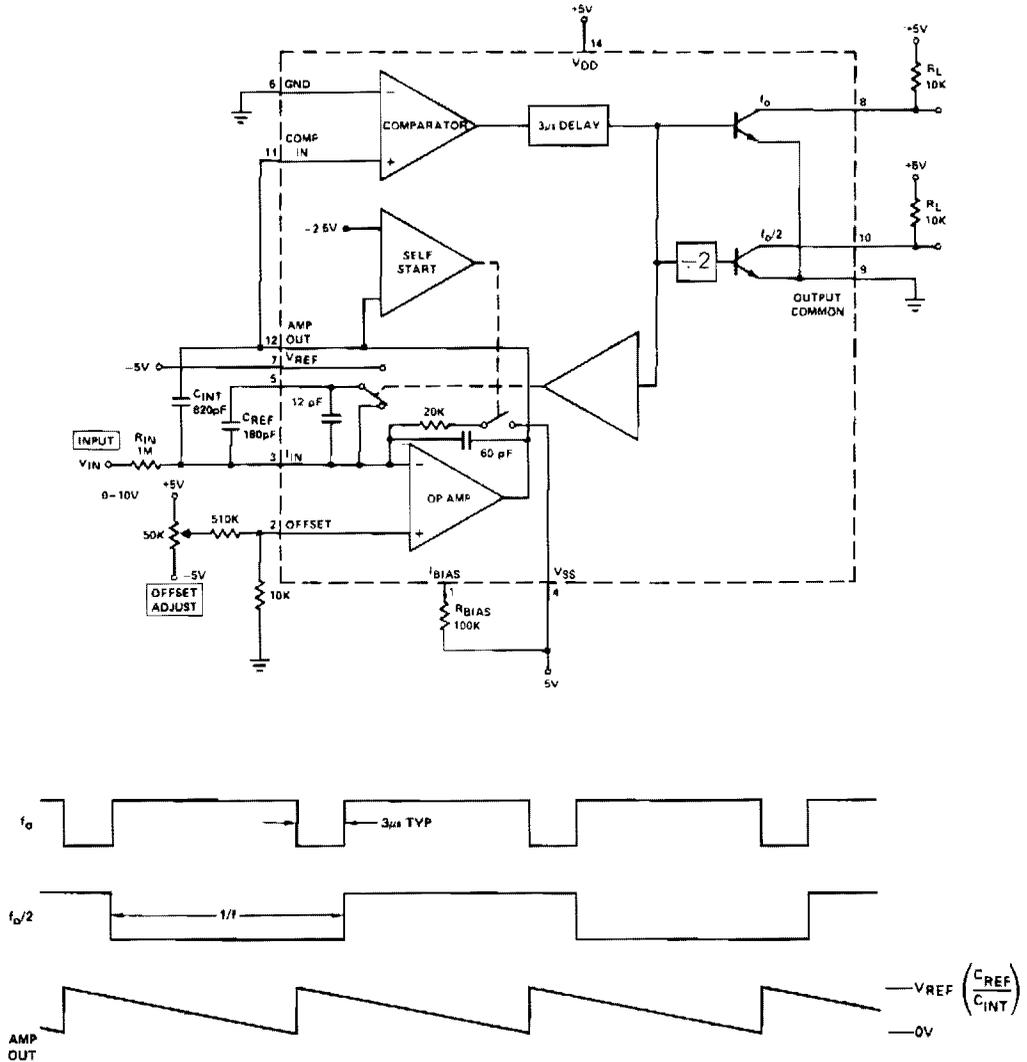

## Notes:

1. To adjust  $f_{min}$ , set  $V_{IN} = 10$  mV and adjust the 50 k offset for 10 Hz out.
2. To adjust  $f_{max}$ , set  $V_{IN} = 10$  V and adjust  $R_{IN}$  or  $V_{REF}$  for 10 kHz out.
3. To increase  $f_{OUT MAX}$  to 100 kHz change  $C_{REF}$  to 27 pF and  $C_{INT}$  to 75 pF.
4. For high performance applications use high stability components for  $R_{IN}$ ,  $C_{REF}$ ,  $V_{REF}$  (metal film resistors and glass film capacitors). Also separate the output ground (Pin 9) from the input ground (Pin 6).

## LOW-FREQUENCY CONVERTER

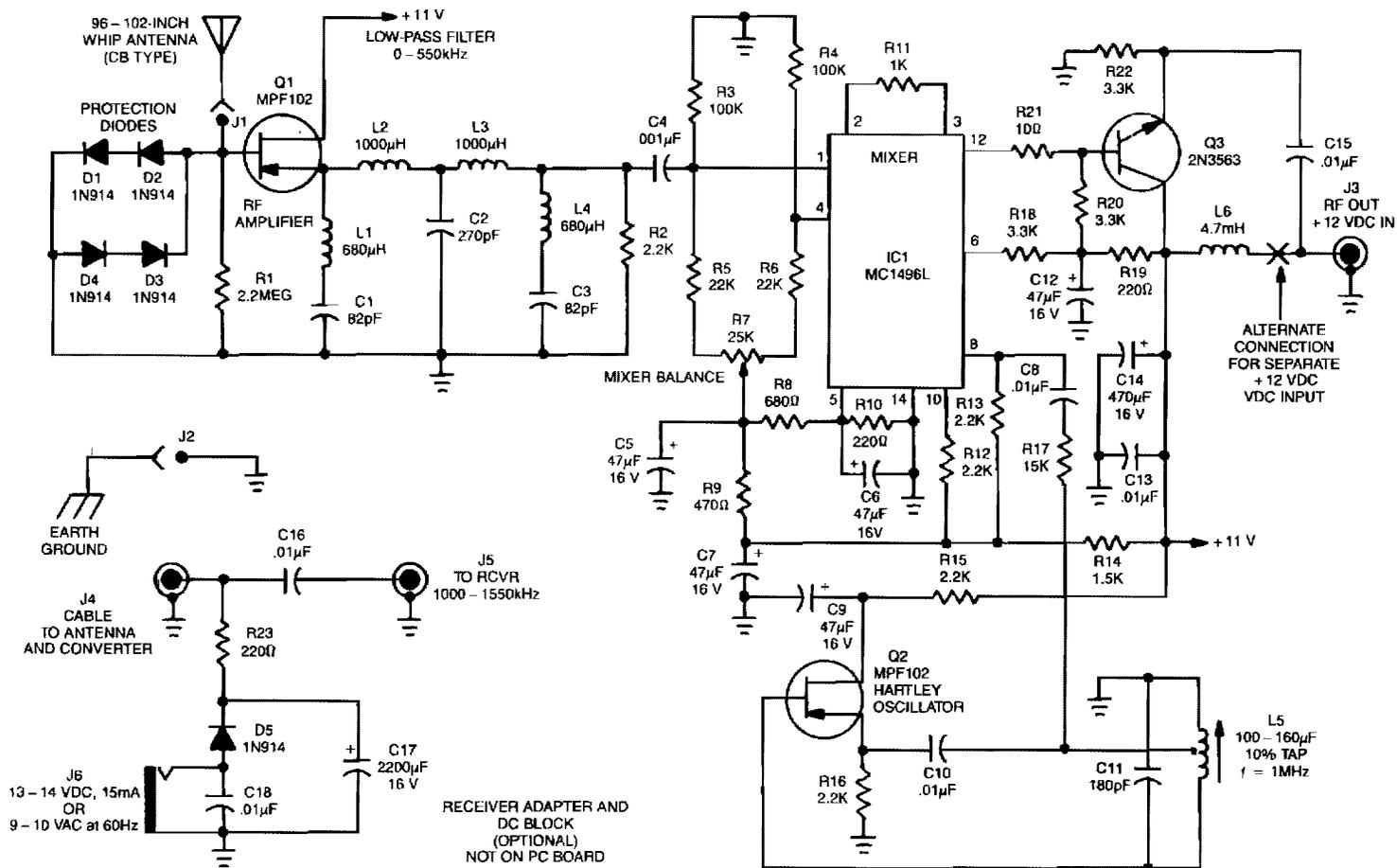

Reprinted with permission from Radio-Electronics Magazine, September 1989. Copyright Gernsback Publications, Inc., 1989.

**Fig. 19-2**


## LOW-FREQUENCY CONVERTER (Cont.)

Among the signals below 550 kHz are maritime mobile, distress, radio beacons, aircraft weather, European Longwave-AM broadcast, and point-to-point communications. The low-frequency converter converts the 10 to 500 kHz LW range to a 1010 to 1550 kHz MW range, by adding 1000 kHz to all received signals. Radio calibration is unnecessary because signals are received at the AM-radio's dial setting, plus 1 MHz; a 100-kHz signal is received at 1100 kHz, a 335-kHz signal at 1335 kHz, etc. The low-frequency signals are fed to IC1, a doubly-balanced mixer.

Transistor Q2 and associated circuitry form a Hartley 1000-kHz local oscillator, which is coupled from Q2's drain, through C8, to IC1 pin 8. Signals in the 10 – 550 kHz range are converted to 1010 – 1550 kHz. The mixer heterodynes the incoming low-frequency signal and local-oscillator signal. Transistor Q3 reduces IC1's high-output impedance to about 100  $\Omega$  to match most receiver inputs. Capacitor C15 couples the 1010 – 1550 kHz frequencies from Q3's emitter to output jack J3, while blocking any dc bias.


Inductor L6 couples the dc voltage that's carried in the rf signal cable from the rcvr/dc adaptor. The dc voltage and rf signals don't interfere with one another; that saves running a separate power-supply wire, which simplifies installation at a remote location. Capacitors C14 and C13 provide dc supply filtering. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.

## POSITIVE-TO-NEGATIVE CONVERTER

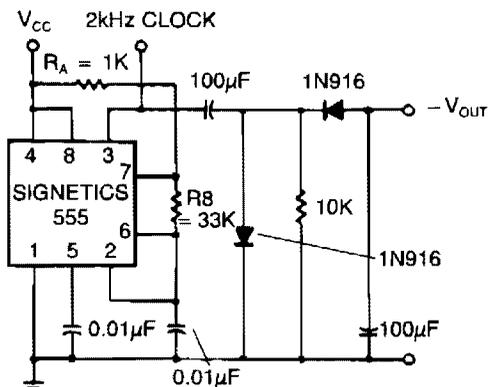


NOTE:  
All resistor values are in ohms

(a) POSITIVE-TO-NEGATIVE CONVERTER

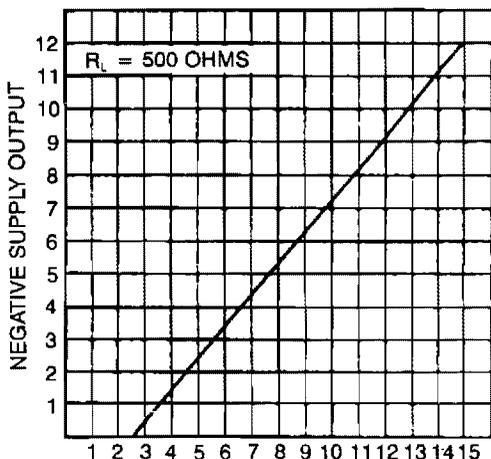

(b) POSITIVE SUPPLY
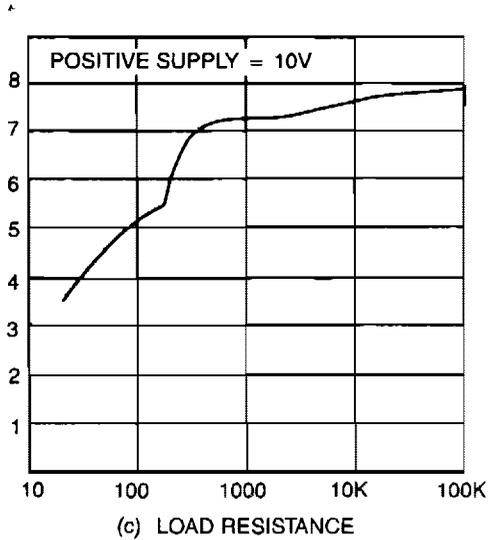
## POSITIVE-TO-NEGATIVE CONVERTER (Cont.)




The transformerless dc-dc converter derives a negative supply voltage from a positive. As a bonus, the circuit also generates a clock signal. The negative output voltage tracks the dc-input voltage linearity (a), but its magnitude is about 3 V lower. Application of a 500-Ω load, (b), causes 10% change from the no-load value.

SIGNETICS

Fig. 19-3

## BUCK/BOOST CONVERTER

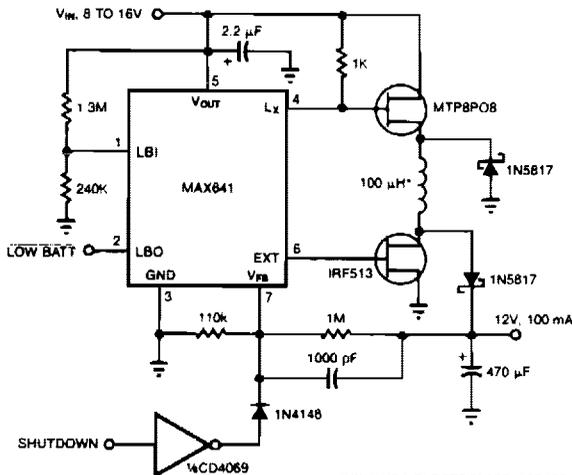

This converter can accommodate wide input-voltage swings, such as the 8 to 15-V swing typical of a 12-V sealed lead/acid battery. The low battery output indicates when input voltage drops below 8 V. Pulling shutdown turns off the circuit.

MAXIM

Fig. 19-4

### 4 - 18 MHz CONVERTER


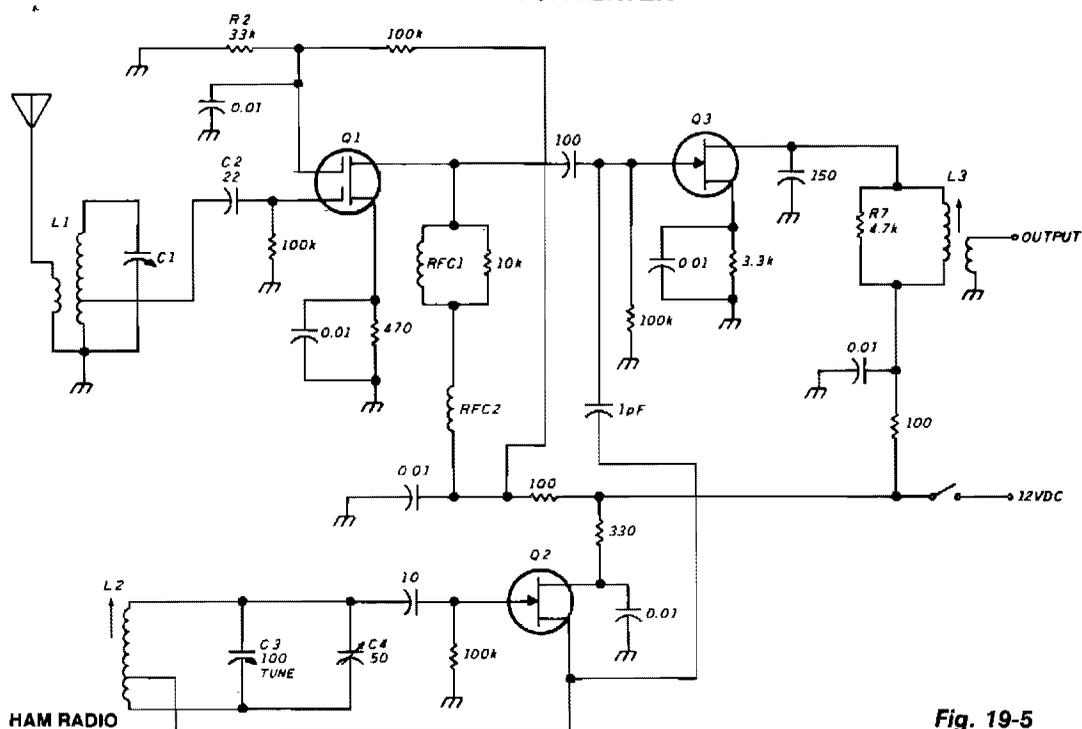


Fig. 19-5

The unit consists of rf amplifier Q1, local oscillator Q2, and mixer Q3. The two bands are covered without a bandswitch by using an i-f or 3.5 MHz. The oscillator range is 7.5 to 14.5 MHz. Incoming signals from 4 to 11 MHz are mixed with the oscillator to produce the 3.5-MHz i-f. Signals from 11 to 18 MHz are mixed with the oscillator to also produce an i-f of 3.5 MHz. At any one oscillator frequency, the two incoming signals are 7 MHz apart. Rf amplifier input C1/L1 comprises a high-Q, lightly loaded, tuned circuit; this is essential for good band separation.

### SHORTWAVE CONVERTER

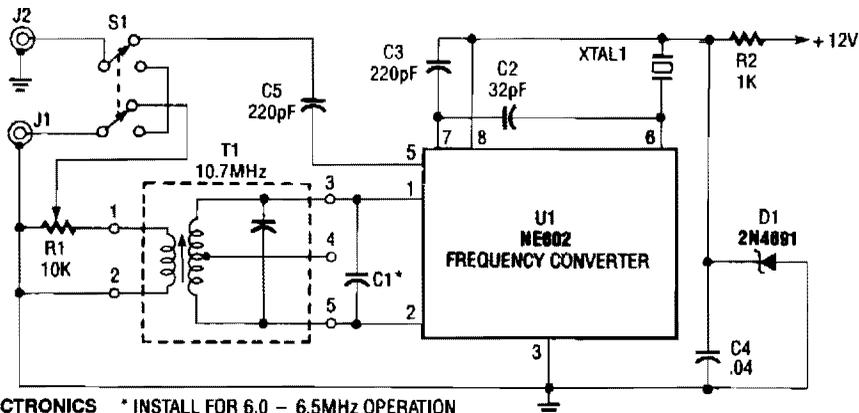


POPULAR ELECTRONICS \* INSTALL FOR 6.0 - 6.5MHz OPERATION

Fig. 19-6

## SHORTWAVE CONVERTER (Cont.)

The NE602, U1, contains oscillator and mixer stages. The mixer combines the oscillator signal with the input rf signal to produce signals whose frequencies are the sum and difference of the input frequencies. For example, a 7.5-MHz signal is picked up by the antenna and mixes with the 8.5-MHz oscillator frequency. The difference between those two signals is 1 MHz—right in the center of your AM dial. Transformer T1 is a 10.7-MHz i-f transformer.

## ISOLATED +15 V DC-DC CONVERTER

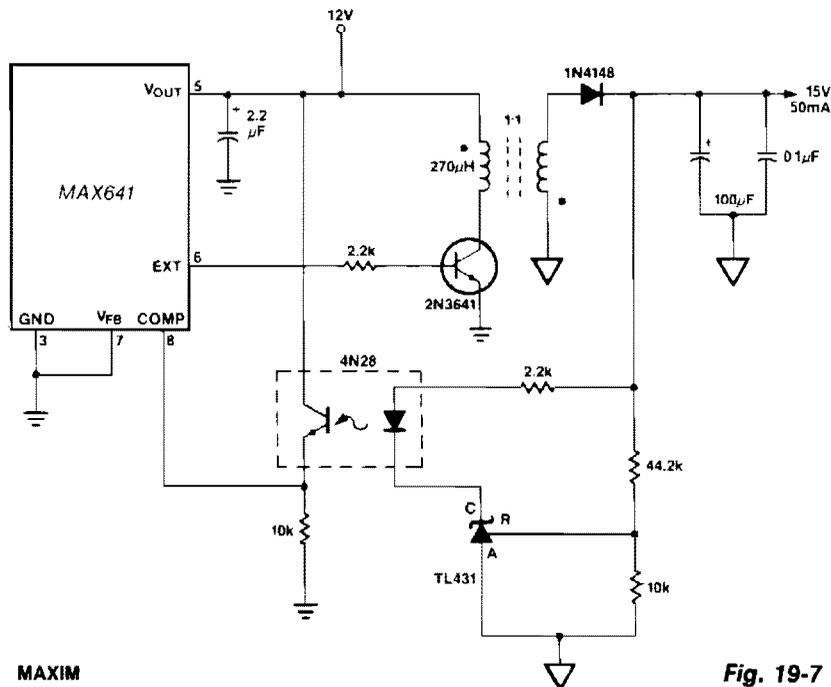


MAXIM

Fig. 19-7

In this circuit, a TL431 shunt-regulator is used to sense the output voltage. The TL431 drives the LED of a 4N28 optocoupler which provides feedback to the MAX641 while maintaining isolation between the input, +12 V, and the output, +15 V. In this circuit, the +15 V output is fully regulated with respect to both line and load changes.

## VOLTAGE RATIO-TO-FREQUENCY CONVERTER

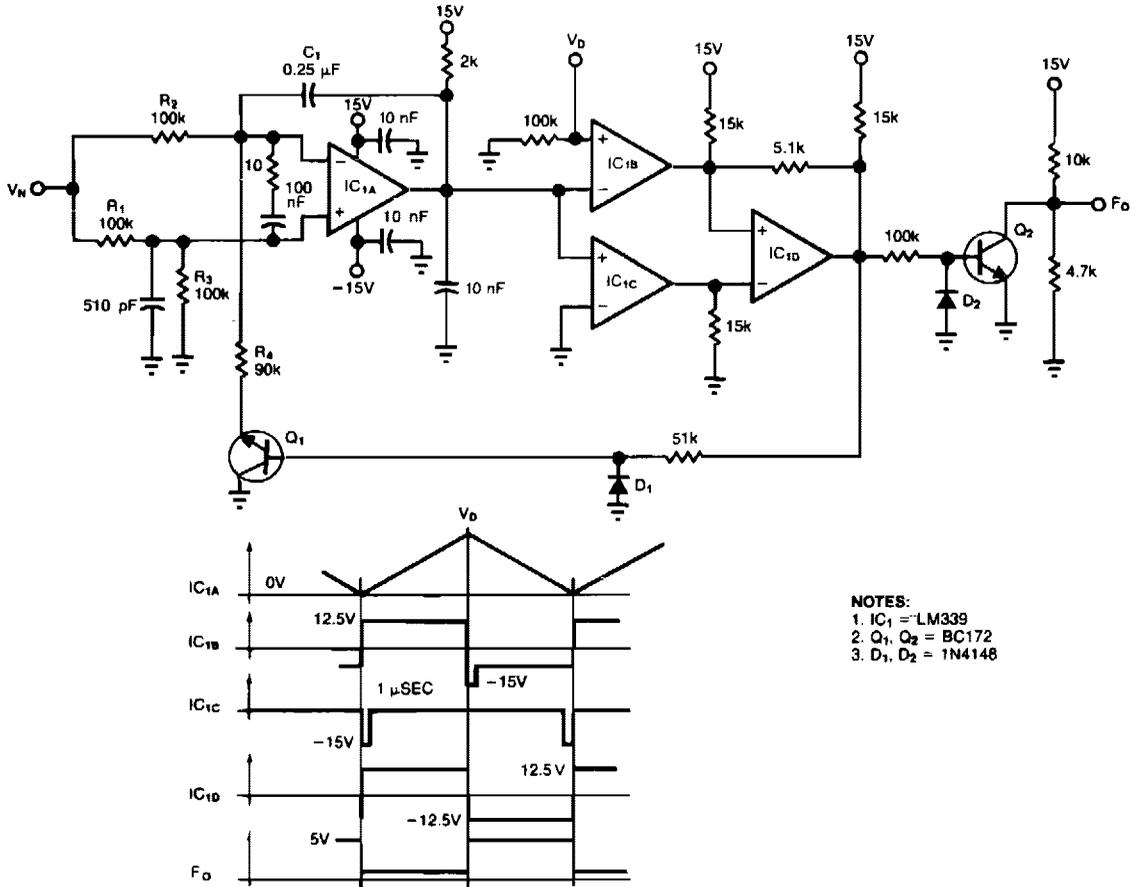


EDN

Fig. 19-8

The circuit accepts two positive-voltage inputs  $V_N$  and  $V_D$  and provides a TTL-compatible output pulse train whose repetition rate is proportional to the ratio  $V_N/V_D$ . Full-scale output frequency is about 100 Hz, and linearity error is below 0.5 percent. The output  $F_o$  equals  $KV_N/V_D$ , where  $K = 1/(4R_2C_1)$  provided  $R_1 = R_3$ . Op amp  $IC_{1A}$  alternately integrates  $V_N/2$  and  $-V_N/2$ , producing a sawtooth output that ramps between the  $V_D$  level and ground. When transistor  $Q_1$  is on, for example,  $IC_{1A}$  integrates  $-V_N/2$  until its output equals  $V_D$ . At that time, the  $IC_{1B}$  comparator switches low, causing  $IC_{1D}$ 's bistable output to go low, which turns off  $Q_1$ .  $IC_{1A}$ 's output then ramps in the negative direction. When the output reaches 0 V, the  $IC_{1C}$  comparator switches,  $Q_1$  turns on, and the cycle repeats. Transistor  $Q_2$  converts the  $IC_{1D}$  output to TTL-compatible output logic levels. Setting  $V_D$  to 1.00 V yields a linear voltage-to-frequency converter ( $F_o = KV_N$ ), and setting  $V_N$  to 1.00 V yields a reciprocal voltage-to-frequency converter ( $F_o = KV_D$ ).

## 50-MHz THERMAL RMS-TO-DC CONVERTER

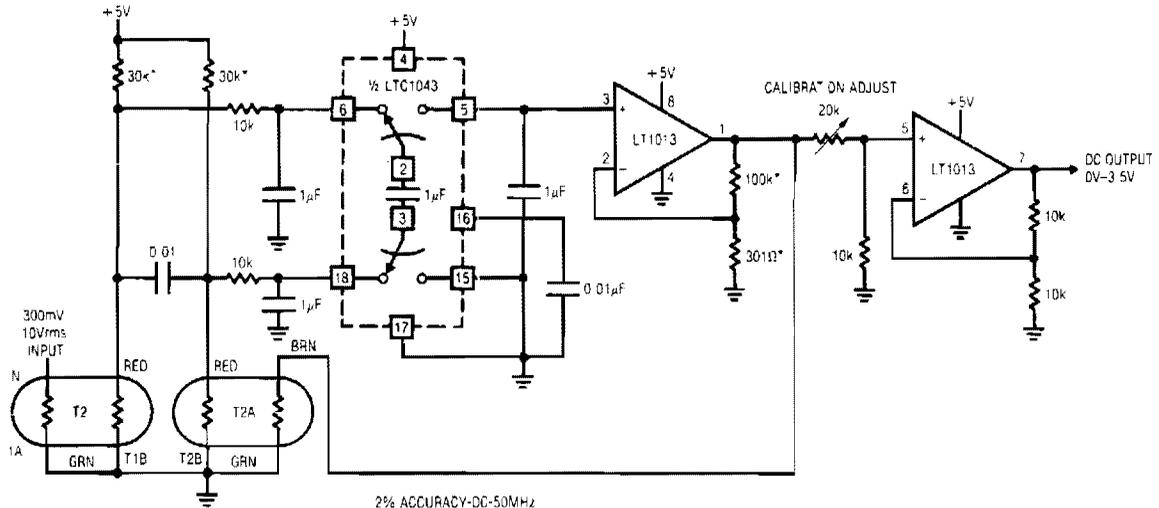


2% ACCURACY-DC-50MHz  
 100:1 CREST FACTOR CAPABILITY  
 T1-T2 = YELLOW SPRINGS INST. CO. THERMISTOR COMPOSITE  
 ENCLOSE T1 AND T2 IN STYROFOAM

\* 1% RESISTOR

LINEAR TECHNOLOGY CORP.

Fig. 19-9

## PULSE WIDTH-TO-VOLTAGE CONVERTER

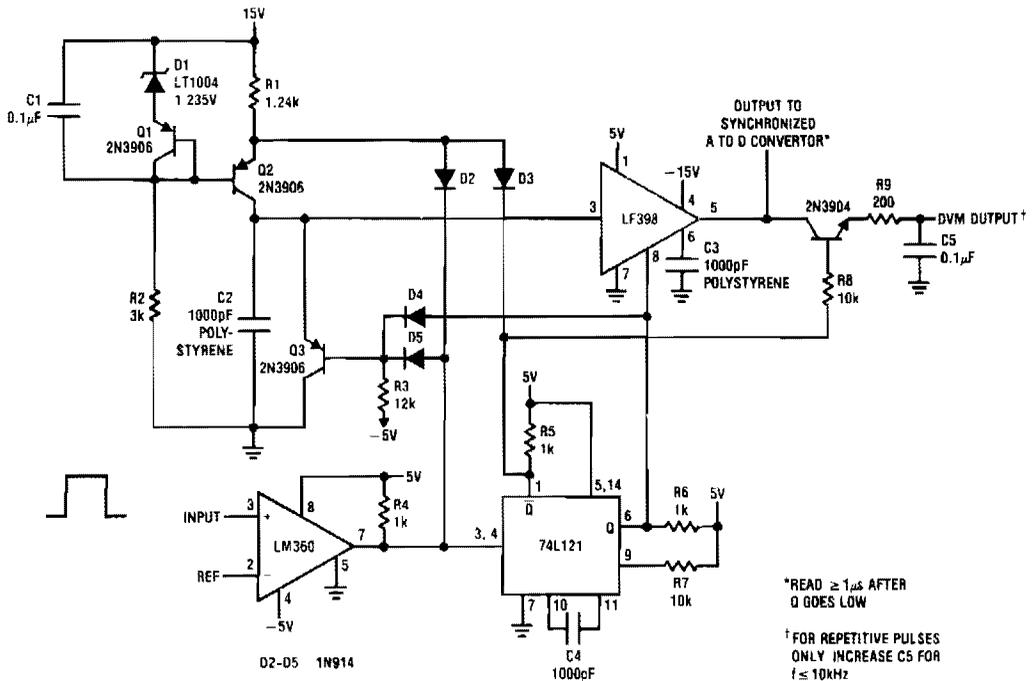

\* READ  $\geq 1\mu s$  AFTER Q GOES LOW

† FOR REPETITIVE PULSES ONLY INCREASE C5 FOR  $f \leq 10kHz$

LINEAR TECHNOLOGY CORP.

Fig. 19-10

## STEP UP/DOWN DC-DC CONVERTER

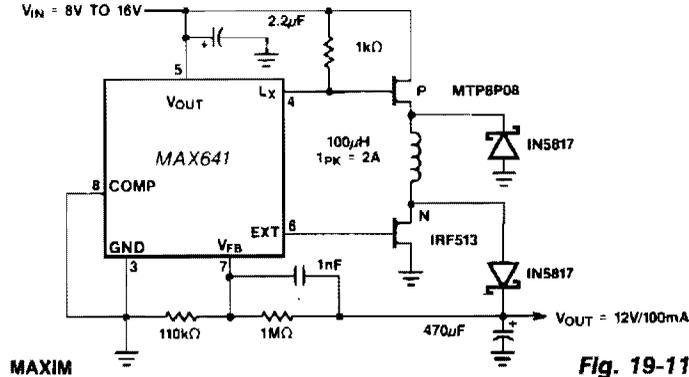


Fig. 19-11

Positive output step-up and step-down dc-dc converters have a common limitation in that neither can handle input voltages that are both greater than or less than the output. For example, when converting a 12-V sealed lead/acid battery to a regulated +12 V output, the battery voltage might vary from a high of 15 V down to 10 V.

By using a MAX641 to drive separate P- and N-channel MOSFETs, both ends of the inductor are switched to allow noninverting buck/boost operation. A second advantage of the circuit over most boost-only designs is that the output goes to 0 V when shutdown is activated. Inefficiency is a drawback because two MOSFETs and two diodes increase the losses in the charge and discharge path of the inductor. The circuit delivers +12 V at 100 mA at 70 percent efficiency with an 8-V input.

## SQUARE-TO-SINE WAVE CONVERTER


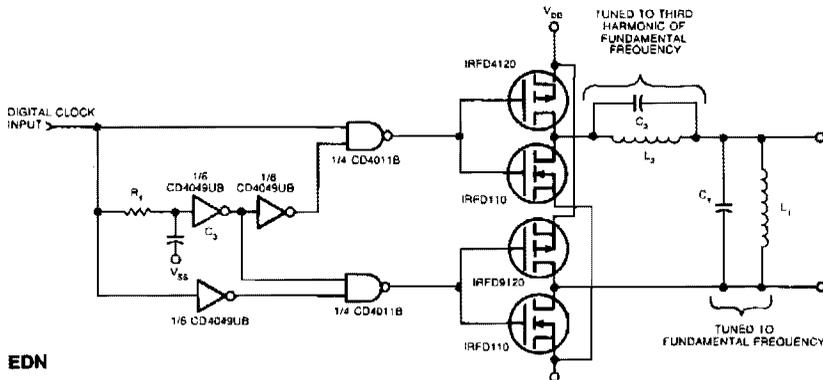


Fig. 19-12

Two pairs of MOSFETs form a bridge that alternately switches current in opposite directions. Two parallel-resonant LC circuits complete the converter. The  $L_1/C_1$  combination is resonant at the fundamental frequency; the  $L_2/C_2$  combination is resonant at the clock frequency's third harmonic and acts as a trap.  $T_1$  and  $C_3$  ensure that both halves of the MOSFET bridge are never on at the same time by providing a common delay to the gate drive of each half. Select the values of  $R_1$  and  $C_3$  to yield a time constant that's less than 5% of the clock's period. You can add an output amplifier for additional buffering and conditioning of the circuit's sine-wave output.

## PULSE HEIGHT-TO-WIDTH CONVERTER

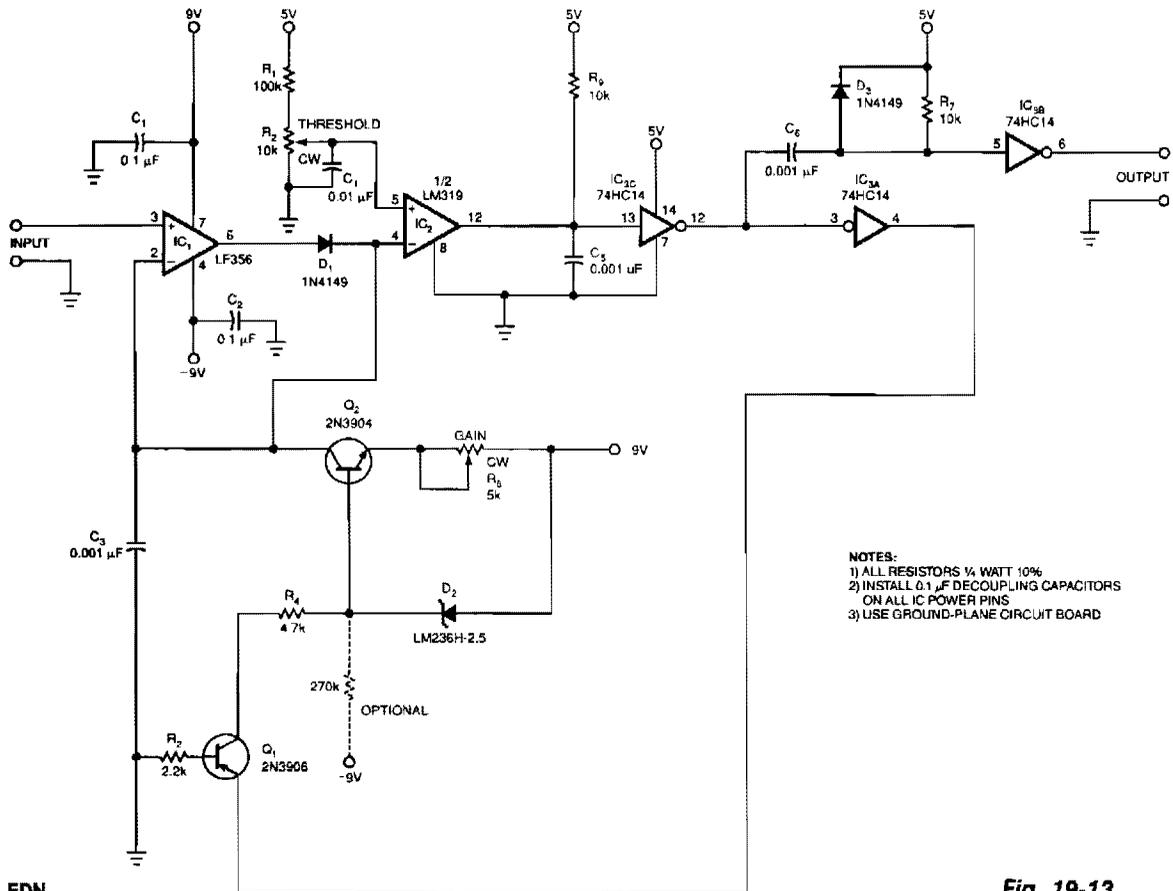

**Fig. 19-13**

The output-pulse width from the circuit is a linear function of the input pulse's height. You can set the circuit's input threshold to discriminate against low-level pulses, while fixed components limit the circuit's maximum output-pulse width.

With a 270-KΩ resistor connected from the -9 V supply to the base lead of Q2, this circuit can handle input pulses separated by 20 μs for correct operation. The turn-off time of zener diode D2 sets the lower limit for the input-pulse repetition rate.

IC1, D1, and C3 detect the peak of the input pulse. The comparator IC2, triggers at your preset threshold. The RC delay network, R9 and C5, hold off inverter IC3's changing state until the completion of peak detection. After IC3A changes state, Q1 turns on and then turns on Q2, a constant-current source.


Constant-current source Q1 then discharges C3, the peak-detecting capacitor. When C3 has discharged below IC2's threshold, IC2's output decreases, as do pins 6 and 4 of IC3. The output-pulse width is a function of this discharge time, which you can adjust with R6. C6 and R7 control the maximum output-pulse width, which is 8 μs max.

EDN





## PULSE TRAIN-TO-SINUSOID CONVERTER

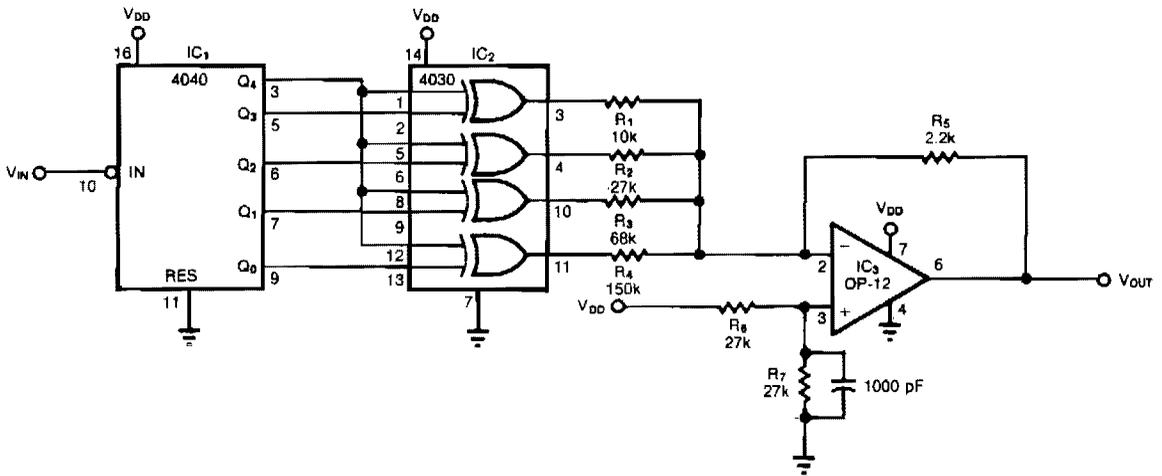

EDN

**Fig. 19-17**

The circuit lets you convert a serial pulse stream or sinusoidal input to a sinusoidal output at  $1/32$  the frequency. By varying the frequency of  $V_{IN}$ , you can achieve an output range of  $10^7:1$ —from about 100 kHz to less than 0.01 Hz. The output resembles that of a 5-bit d/a converter operating on parallel digital data.

Counter IC1 generates binary codes that repeatedly scan the range from 00000 to 11111. The output amplifier adds the corresponding XOR gate outputs,  $V_{DD}$  or ground, weighted by the values of input resistors R1 through R4. The 16 counter codes 00000 to 01111, for instance, pass unchanged to the XOR gate outputs, and cause  $V_{OUT}$  to step through the half-sinusoidal cycle for maximum amplitude to minimum amplitude.

Counter output Q4 becomes high for the next 16 codes, causing the XOR gates to invert the Q0 through Q3 outputs. As a result,  $V_{OUT}$  steps through the remaining half cycle from minimum to maximum amplitude. The counter then rolls over and initiates the next cycle. You can change the R1 through R4 values to obtain other  $V_{OUT}$  waveforms.  $V_{DD}$  should be at least 12 V to assure maximum-frequency operation from IC1 to IC2.

# 20


## Counters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Low-Cost Frequency Counter	Low-Power Wide-Range Programmable Counter
Up/Down Counter/Extreme Count	40-MHz Universal Counter
Freezer	Frequency Counter Preamp
10-MHz Frequency Counter	1.2-GHz Frequency Counter


## LOW-COST FREQUENCY COUNTER

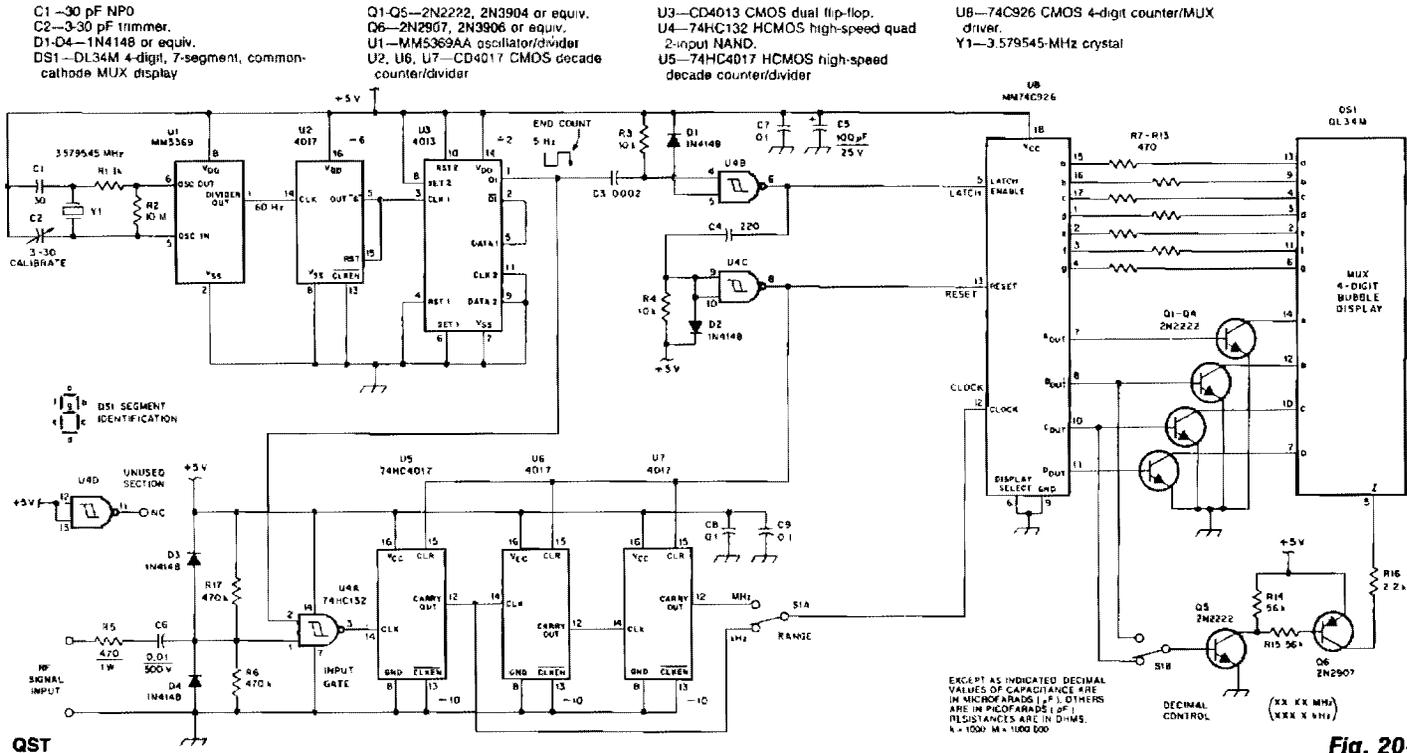

This counter uses a four-digit display, but with a flip of the range switch, it can display frequencies from 1 to 40 MHz, with a resolution of 100 Hz. The MM74C926 CMOS IC contains a four-digit decimal counter that can latch a given count and then use this information to drive a 7-segment, common-cathode multiplexed (MUX) display. The block diagram and schematic show the operation of the counter. Crystal-controlled timer U1 through U3 produces a 5-Hz square wave used for timing the frequency count. Y1 is a TV color-burst crystal operating in a reliable circuit that controls the oscillator frequency. U1 acts as the oscillator and also divides the fundamental operating frequency of 3.579545 MHz to produce a square-wave output of 60 Hz. U2 divides the 60-Hz output of U1 by six. In turn, the 10-Hz output of U2 is divided by two in U3, a dual flip-flop, to produce the 5-Hz pulse.

A quad, two-input, Schmitt-triggered NAND U4 is used for gating the rf-signal input and for generating the counter control pulses—Section U4D is unused. The 5-Hz output pulse of U3 is applied to the rf-signal input gate at U4A pin 2. When the timer output signal is low, the gate is closed.

## UP/DOWN COUNTER/EXTREME COUNT FREEZER

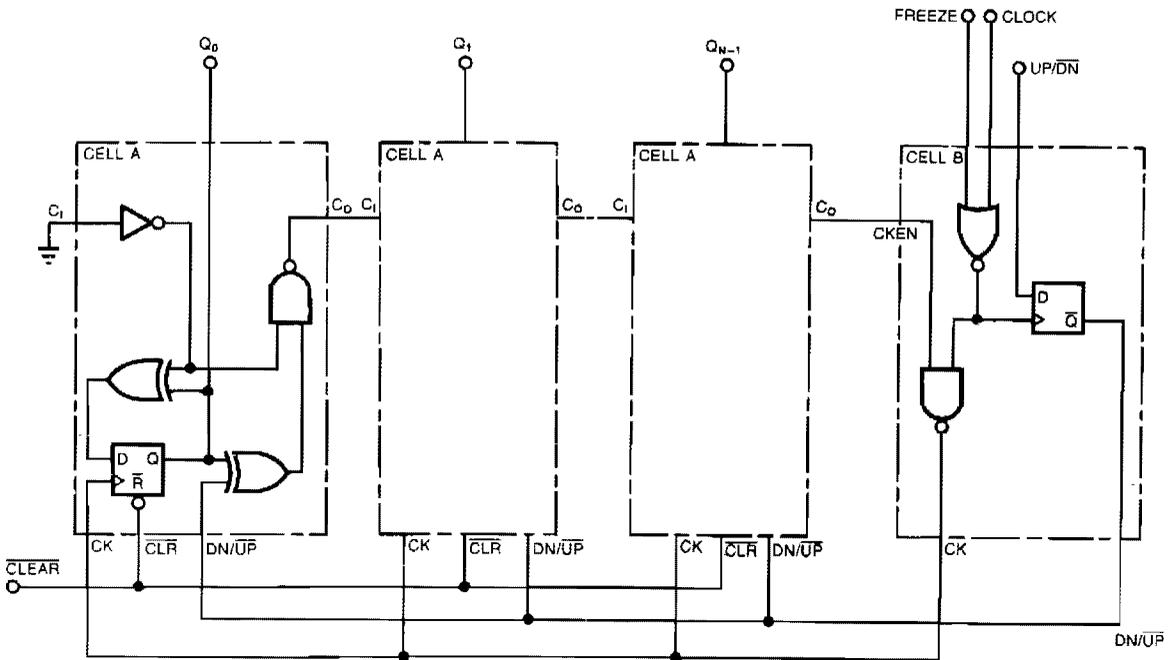

**STATE TABLE**

FREEZE	UP/DN	CLOCK	CURRENT STATE	NEXT STATE
			$Q_{N-1} \dots Q_0$	$Q_{N-1} \dots Q_0$
L	H		11...10	11...11
L	H		11...11	11...11
L	L		00...01	00...00
L	L		00...00	00...00
H	X	X	$Q_X$	$Q_X$


EDN

**Fig. 20-2**

The discrete-gate up/down-counter design has the unusual property of freezing, or saturating, when it reaches its lowest count in the down-count mode or its highest count in the count-up mode instead of rolling over and resetting as do most counters. This property proves especially useful in position-control systems. For example, you wouldn't want a robot's arm to slowly move to full extension as the counter counts up and then have it suddenly slam back to its rest position when the counter resets to zero.

You can cascade as many of the A cells as you need because the counter's outputs are synchronous. The B cell accepts the carry bit from the most significant bit's A cell and provides the clock control that stops the counter. Make sure that the freeze input to the B cell doesn't get asserted when the clock input is low; otherwise, the counter might make an extra count.

## 10-MHz FREQUENCY COUNTER

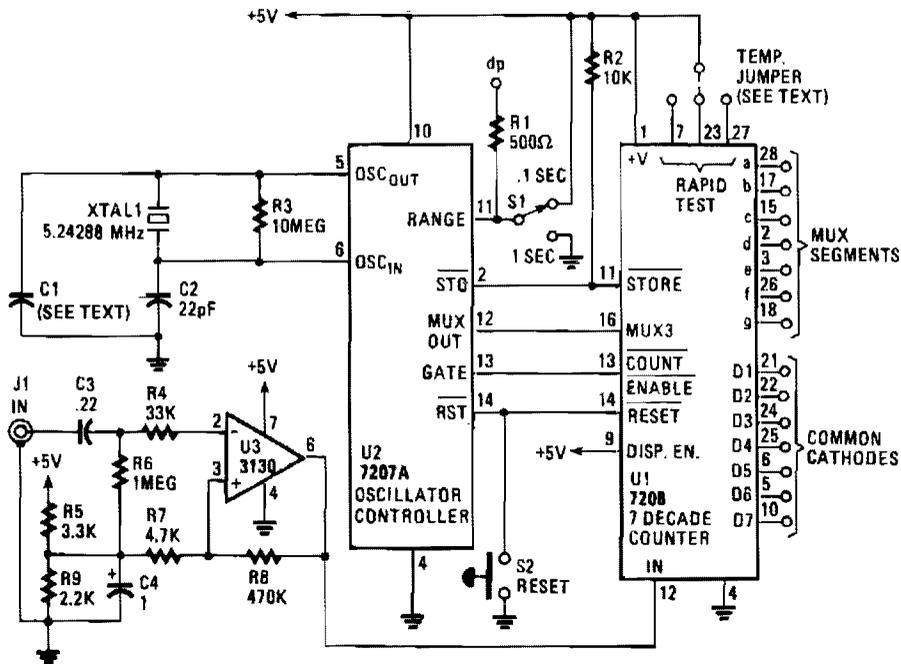


HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

Fig. 20-3

The circuit consists of ICM7208 seven-decade counter U1, ICM7207A oscillator controller U2, and CA3130 biFET op amp U3. IC U1 counts input signals, decodes them to 7-segment format, and outputs signals that are used to drive a 7-digit display. IC U2 provides the timing for U1, while U3 conditions the input to U1. The 5.24288-MHz crystal frequency is divided by U2 to produce a 1280-MHz multiplexing signal at pin 12 of U2. That signal is input to U1 at pin 16 and used to scan the display digits in sequence.
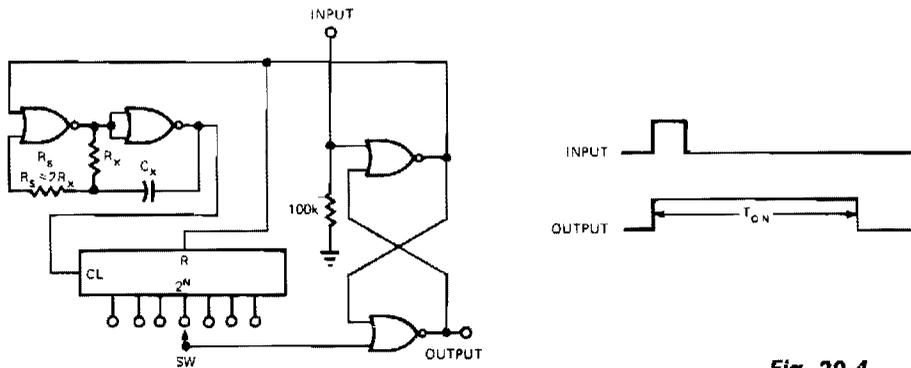
## LOW-POWER WIDE-RANGE PROGRAMMABLE COUNTER



EDN


Fig. 20-4

## LOW-POWER WIDE-RANGE PROGRAMMABLE COUNTER (Cont.)

This CMOS circuit can be used as a 1-shot time delay switch and general-purpose timer. The circuit consists of a gated oscillator and a latch made from one CD4001 quad 2-input NOR gate as shown and a CD4020 14-stage counter.  $T_{ON}$  is a function of the oscillator frequency from the  $R_X C_X$  and the proper  $2^N$  output from the counter. A pulse applied to the latch will "enable" the oscillator and counter. The latch output will remain high until the  $2^N$  count resets the latch and disables the oscillator and counter. The circuit provides  $\mu s$  to hour interval timing. The extraordinarily long periods available from the CMOS oscillator, combined with the 14-stage counter, make this range possible. Further decoding is required for variations finer than a power of two.
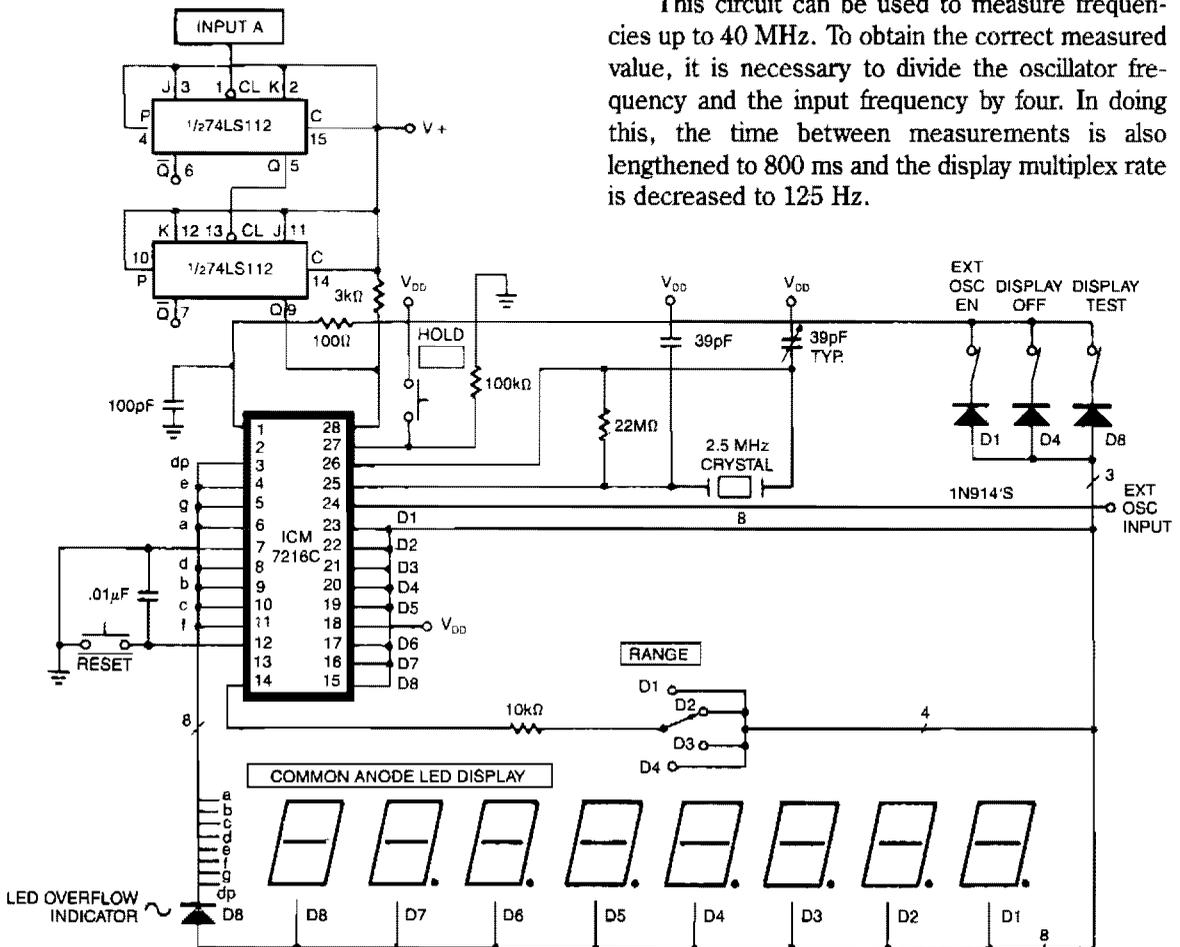
### 40-MHz UNIVERSAL COUNTER


This circuit can be used to measure frequencies up to 40 MHz. To obtain the correct measured value, it is necessary to divide the oscillator frequency and the input frequency by four. In doing this, the time between measurements is also lengthened to 800 ms and the display multiplex rate is decreased to 125 Hz.



INTERSIL

Fig. 20-5

## FREQUENCY-COUNTER PREAMP

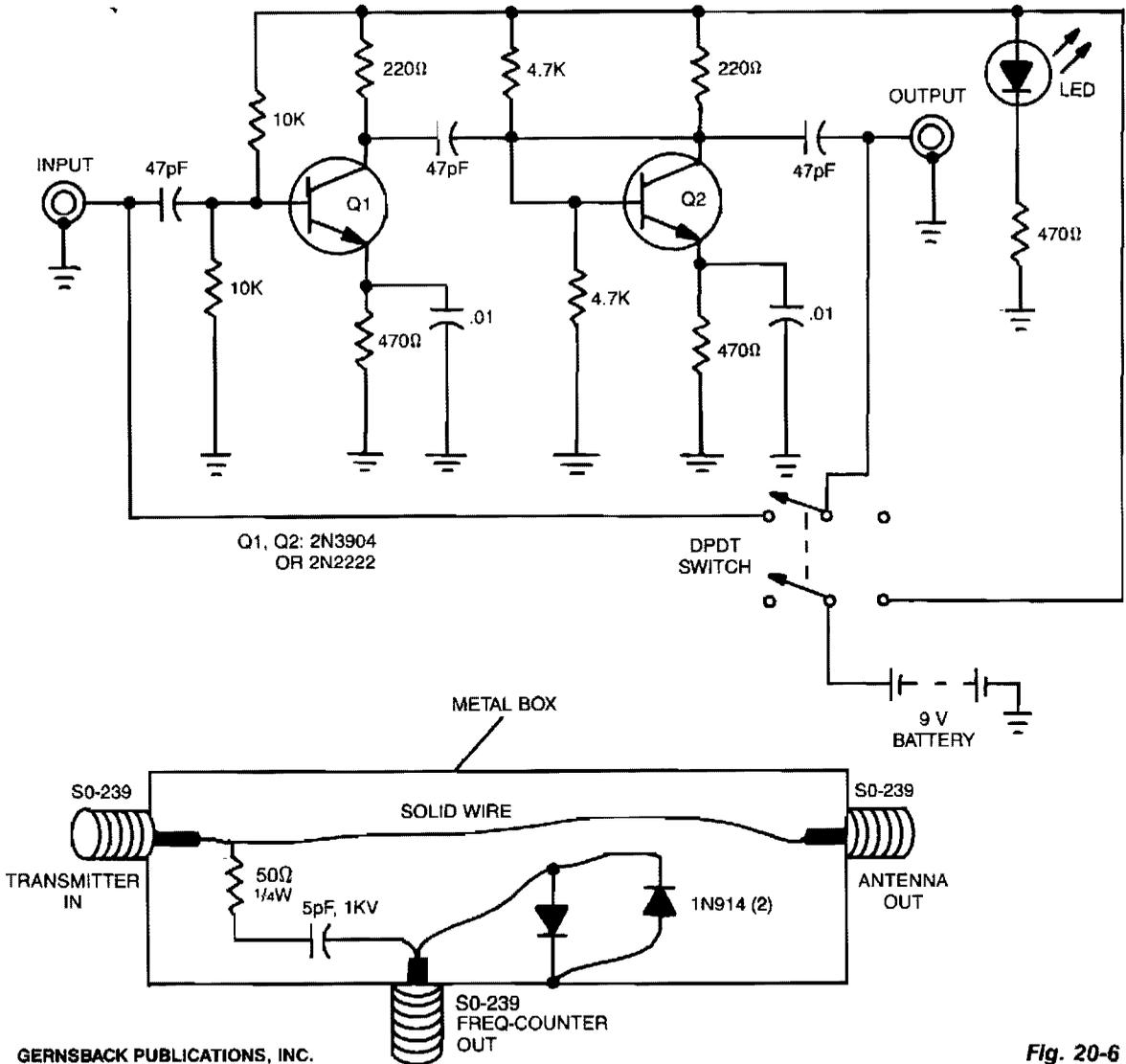


GERNSBACK PUBLICATIONS, INC.

**Fig. 20-6**

By using the preamplifier with a short length of shielded cable and clip leads, signals that generally could not generate a readout, generate precise and stable readouts on the counter. The DPDT switch is used to bypass the circuit when amplification is not needed. The preamplifier can also be used for other purposes. For example, the unit was also tested as a receiver preamplifier and increased received signal strength about 6 S-units at 30 MHz. A line tap can be used to measure the frequency directly at the output of a transmitter. The entire circuit for that consists of two diodes, one resistor, and one capacitor. The line tap simply picks a low-amplitude signal for measurement by the frequency counter. The tap can be connected to transmitters with an output power of between 1 and 250 W.

## 1.2-GHz FREQUENCY COUNTER

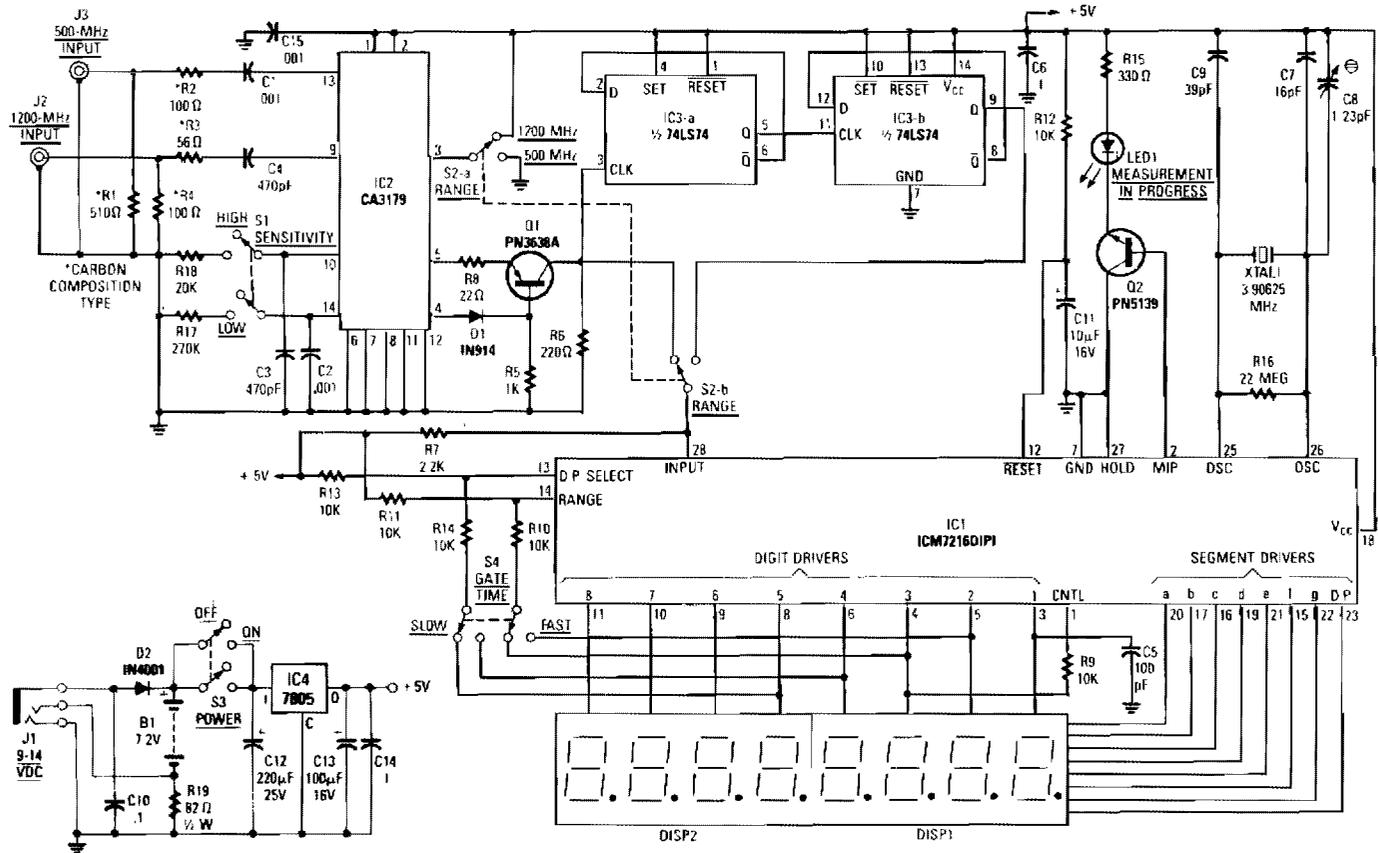

Reprinted with permission from Radio-Electronics Magazine, 1987, R-E Experimenters Handbook  
 Copyright Gernsback Publications, Inc., 1987.

**Fig. 20-7**

## 1.2-GHz FREQUENCY COUNTER (Cont.)

The output of the CA3179 is fed through the D1/Q1 circuit. Those components serve to boost the 1-V output of the CA3179 to a standard TTL level. Then, depending on the position of range switch S2b, the signal is passed directly to the 7216, or through the divide-by-four circuit built from the two D flip-flops in IC3.

The other half of the range switch S2a controls the voltage at pin 3 of the CA3179. When pin 3 is high, the signal applied to pin 9 is fed through an extra internal divide-by-four stage before it is amplified and output on pins 4 and 5. When pin 3 is low, the signal on pin 13 is simply processed for output without being divided internally.

A 3.90625-MHz crystal provides the time base; the crystal yields a fast gate time of 0.256 second. The displayed frequency equals the input frequency divided by 1000 in the fast mode. In slow mode, gate time is 2.56 seconds. The displayed frequency equals the input frequency divided by 100 in the slow mode.

Switch S4, gate time, performs two functions. First it selects the appropriate gate time according to which digit output of IC1 the range input is connected to. Another of the 7216's inputs is also controlled by S4: the dp select input. The decimal point of the digit output to which that pin is connected will be the one that lights up. The correct decimal point illuminates, according to the position of S4, to provide a reading in MHz.

---

# 21

## Crystal Oscillators


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Fundamental-Frequency Crystal Oscillator	Two-Gate Quartz Oscillator
Easy Start-Up Crystal Oscillator	Crystal-Controlled Reflection Oscillator
Crystal Timebase	Temperature-Compensated Crystal Oscillator
Low-Frequency Pierce Oscillator	20-MHz VHF Crystal Oscillator
1-MHz Pierce Oscillators	Marker Generator
Simple CMOS Crystal Oscillators	100-MHz VHF Crystal Oscillator
Voltage-Controlled Crystal Oscillator	50-MHz VHF Crystal Oscillator



## CRYSTAL TIMEBASE

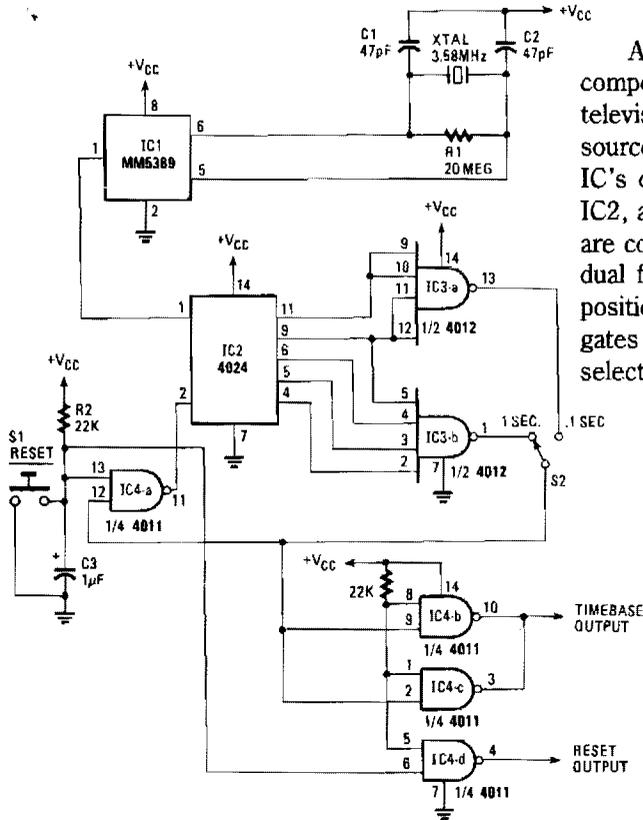

An on-board oscillator and a 17-stage divider compose IC1. By connecting a standard 3.58-MHz, television color-burst crystal as shown, an accurate source of 60-Hz squarewaves is generated at the IC's output, pin 1. Those pulses are then fed to IC2, a 4024 seven-stage ripple counter. Its outputs are connected to different gates in IC3, which is a dual four-input NAND gate. Depending on which position pulse-select switch S2 is on, one of those gates will provide an output/reset pulse of the selected width.

Fig. 21-3

Reprinted with permission from Radio-Electronics Magazine, February 1986. Copyright Gernsback Publications, Inc., 1986.

## LOW-FREQUENCY PIERCE OSCILLATOR


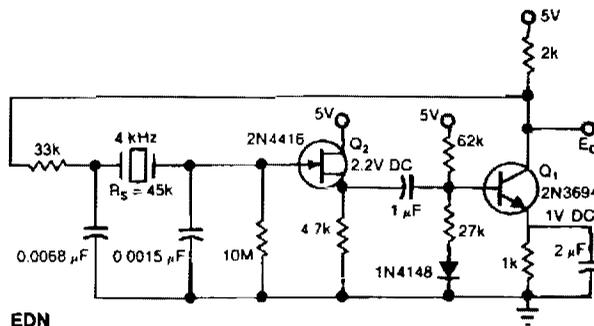


Fig. 21-4


The Pierce circuit oscillates at 4 kHz. At low frequencies, the crystal's internal series resistance  $R_S$  is quite high (45 K at 4 kHz). Therefore, an FET-based source follower is included to prevent Q1 from loading the crystal output.

## 1-MHZ PIERCE OSCILLATORS

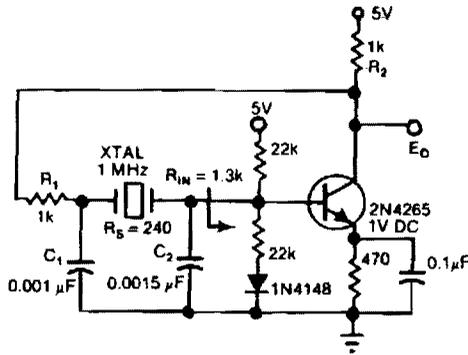

(a)

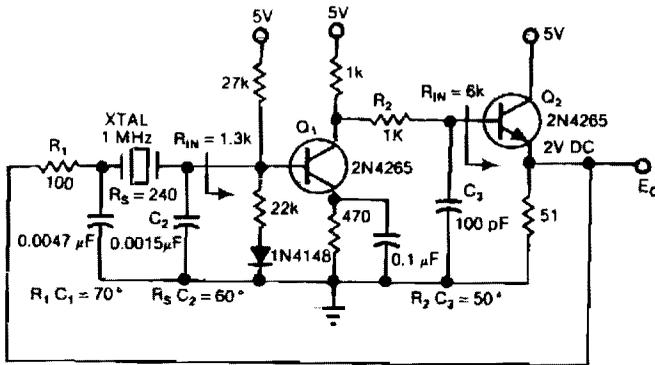Simple network design is a key feature of the Pierce circuit, as these 1-MHz oscillators illustrate. Operating the crystal slightly above resonance (Fig. 21-5a) requires only one high-gain transistor stage. Operating it exactly at series resonance (Fig. 21-5b) requires an extra RC phase lag and two transistors which can have lower gain.



(b) EDN

Fig. 21-5

## SIMPLE CMOS CRYSTAL OSCILLATOR


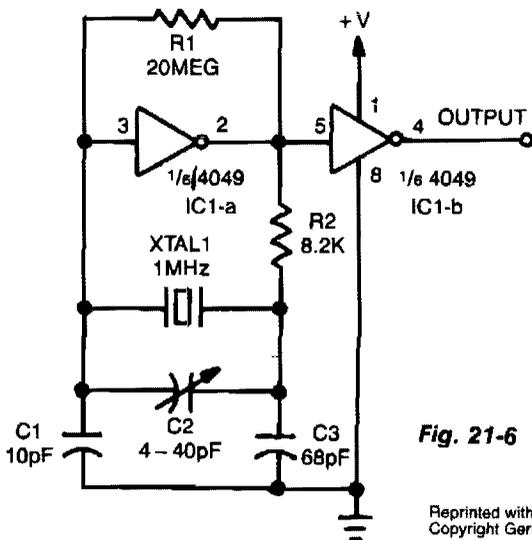


Fig. 21-6

The circuit is an inverter set up as a linear amplifier. Adding the crystal and capacitors to the feedback path, we turn the amplifier into an oscillator and force it to oscillate at, or least very near, the crystal's resonant frequency. Trimmer capacitor C2 adjusts the actual operating frequency of the circuit. The crystal should be a parallel-resonant type; maximum frequency will depend partly on supply voltage, but it should be possible to go to at least 1 MHz.

Reprinted with permission from Radio-Electronics Magazine February 1987. Copyright Gernsback Publications, Inc., 1987.

## VOLTAGE-CONTROLLED CRYSTAL OSCILLATOR

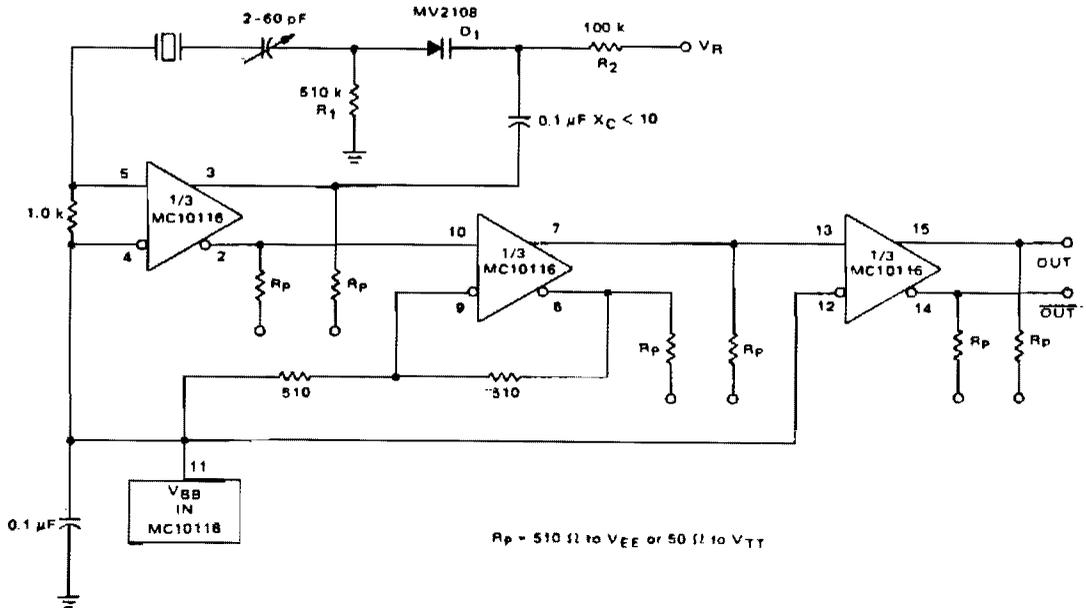


NOMINAL FREQUENCY	DEVIATION	
	+PPM	-PPM
MHz		
1.0000	57.0	48.0
1.8432	95.5	80.3
10.000	197.4	202.8
15.000	325.4	322.9

Copyright of Motorola, Inc. Used by permission.

**Fig. 21-7**

A voltage-variable capacitance tuning diode is placed in series with the crystal feedback path. Changing the voltage on  $V_R$  varies the tuning diode capacitance and tunes the oscillator. The 510-K $\Omega$  resistor,  $R_1$ , establishes a reference voltage for  $V_R$ —ground is used in this example. A 100-K $\Omega$  resistor,  $R_2$ , isolates the tuning voltage from the feedback loop and 0.1- $\mu$ F capacitor  $C_2$  provides ac coupling to the tuning diode. The circuit operates over a tuning range of 0 to 25 V. It is possible to change the tuning range from 0 to 25 V by reversing the tuning diode  $D_1$ . Center frequency is set with the 2–60 pf trimmer capacitor. Deviation on either side of center is a function of the crystal frequency. The table in Fig. 21-7 shows measured deviation in parts per million for several tested crystals.

## TWO-GATE QUARTZ OSCILLATOR

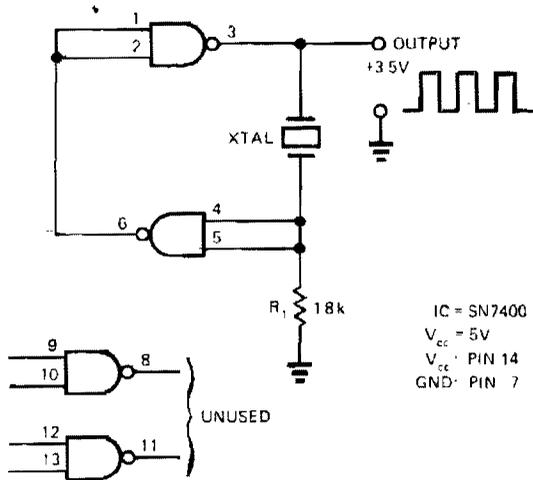


A SN7400 quartz crystal and a resistor provide a square-wave output of approximately 3.5 V. The circuit operates reliably at frequencies from 120 kHz to 4 MHz.

Fig. 21-8

EDN
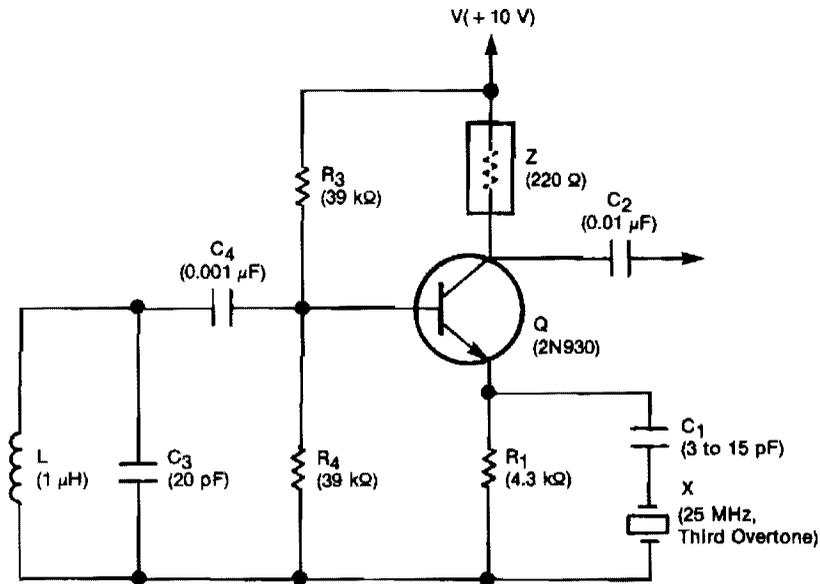
## CRYSTAL-CONTROLLED REFLECTION OSCILLATOR




NASA

OSCILLATOR

Fig. 21-9

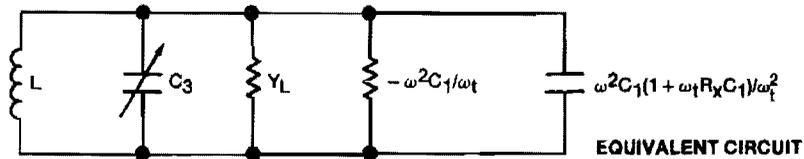
## CRYSTAL-CONTROLLED REFLECTION OSCILLATOR (Cont.)



This unit is easily tunable and stable, consumes little power, and costs less than other types of oscillators that operate at the same frequencies. This unusual combination of features is made possible by a design concept that includes operation of the transistor well beyond the 3 dB frequency of its current-versus-frequency curve. The concept takes advantage of newly available crystals that resonate at frequencies up to about 1 GHz.

The emitter of transistor Q is connected with variable capacitor C1 and series-resonant crystal X. The emitter is also connected to ground through bias resistor R1. The base is connected to the parallel combination of inductor L and capacitor C3 through dc-blocking capacitor and C4 and is forward biased with respect to the emitter by resistors R3 and R4. Impedance Z could be the 220- $\Omega$  resistor shown or any small impedance that enables the extraction of the output signal through coupling capacitor C2. If Z is a tuned circuit, it is tuned to the frequency of the crystal.
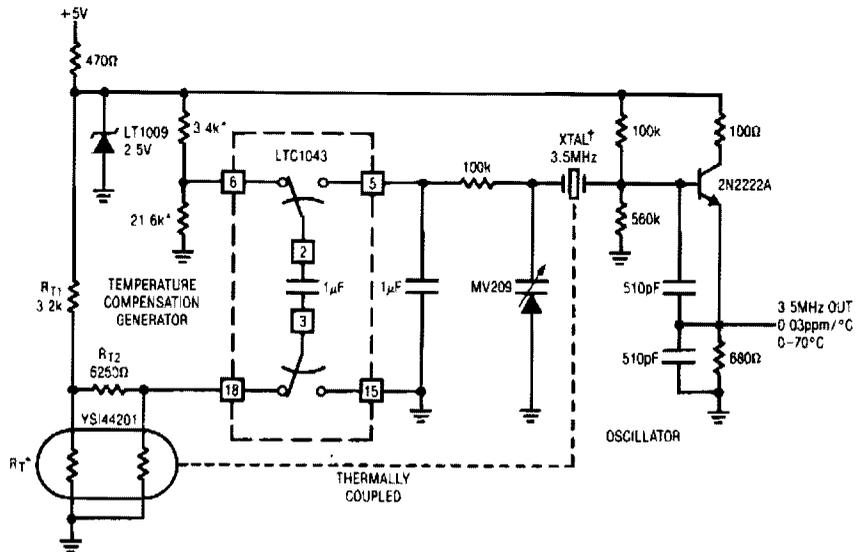
## TEMPERATURE-COMPENSATED CRYSTAL OSCILLATOR




LINEAR TECHNOLOGY CORP.

Fig. 21-10

This circuit uses LTC1043 to differentiate between a temperature sensing network and a dc reference. The single-ended output biases a varactor-tuned crystal oscillator to compensate drift. The varactor crystal network has high dc impedance, eliminating the need for an LTC1043 output amplifier.


## 20-MHz VHF CRYSTAL OSCILLATOR

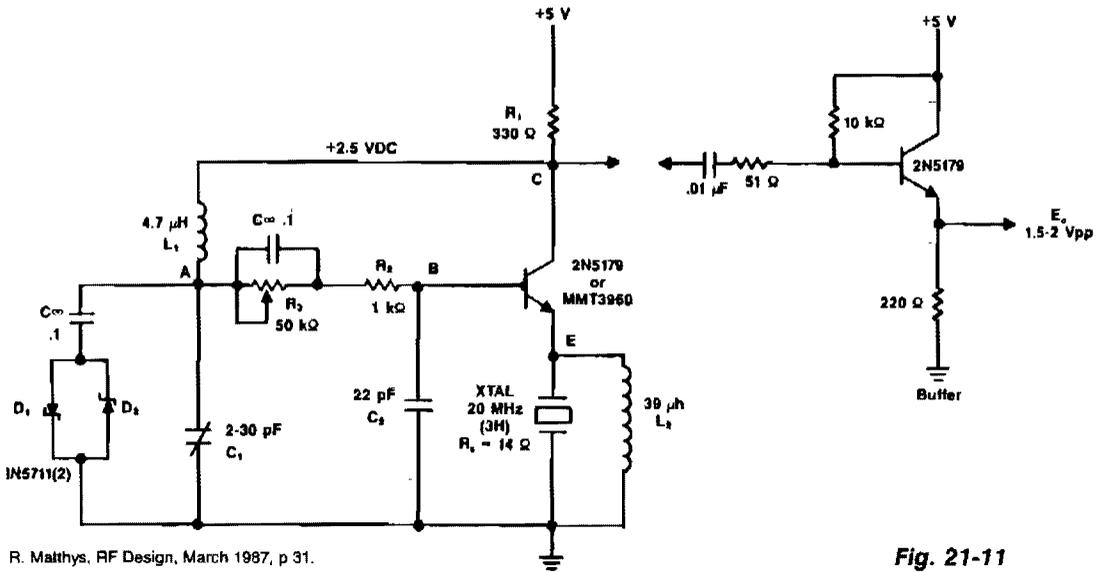

**Fig. 21-11**

A typical circuit at 20 MHz is shown. The crystal, which has an internal series resistance  $R_S$  of 14  $\Omega$ , oscillates at its third harmonic. The diode clamp D1 and D2 provides a constant amplitude control. The transistor operates continuously in a linear mode over a complete cycle of oscillation, and reflects a reasonably constant load across the crystal at all times.

## MARKER GENERATOR

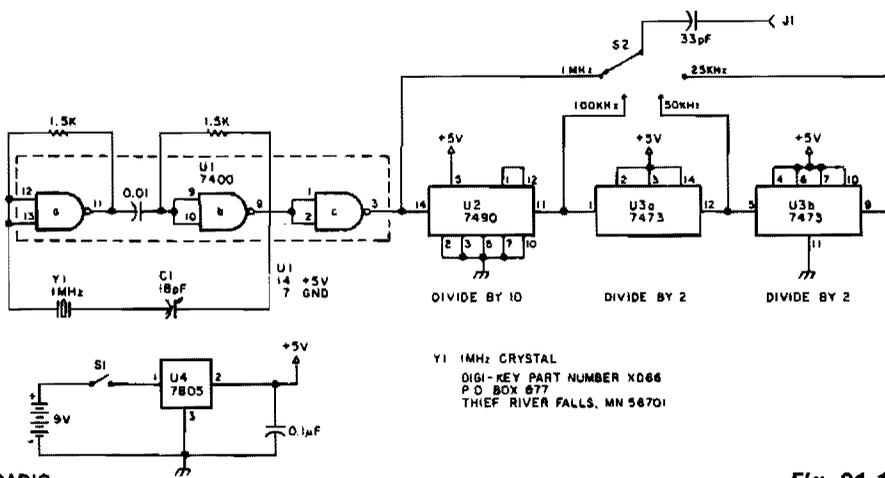


**Fig. 21-12**
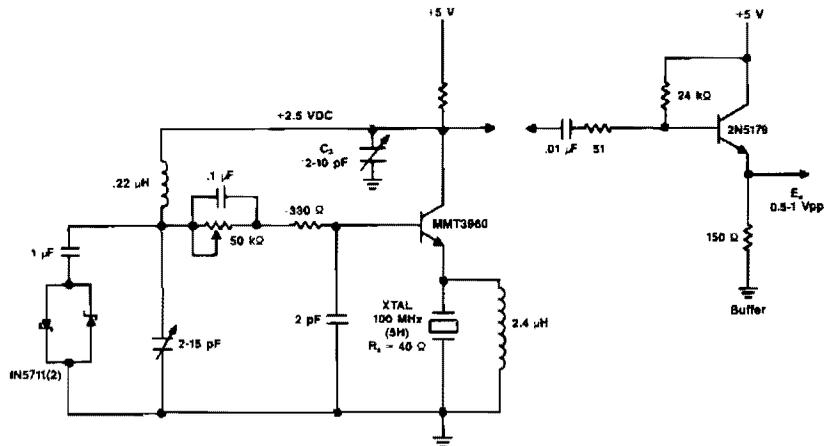
## MARKER GENERATOR (Cont.)

The oscillator section uses three sections of a 7400 quad NAND gate integrated circuit. The 1-MHz signal from the oscillator is fed into a 7490 decade counter configured to divide by ten, providing the 100-kHz signal. To obtain the 50 and 25 kHz outputs, the 100-kHz signal is further divided by 7473 dual J-K flip-flop. The first half of the 7473 divides the 100-kHz signal by two, yielding the 50 kHz signal. The second half of the 7473 again divides by two, giving the 25 kHz signal. S2 selects the output, a square wave, rich in harmonics. The generator can be powered from any convenient 6 to 12 Vdc source. A 7805 fixed-voltage regulator supplies the regulated voltage for the oscillator and the divider chips. The generator described here is powered by a 9-V transistor radio battery.

### 100-MHz VHF CRYSTAL OSCILLATOR




R. Matthys, RF Design, March 1987, p. 31.

Fig. 21-13

Figure 21-13 shows a 100-MHz oscillator operating on the fifth harmonic. Again to maintain the transistor's gain, note the increase in the collector's load resistance  $R_1$  because of the increase in the quartz crystal's internal series resistance  $R_s$ .  $C_3$  is needed at frequencies above 50 MHz to tune out the shunting effect of  $L_1$  on  $R_1$ , to maintain a high load resistance for the transistor and get enough gain for oscillation. The equivalent series  $R_L C_L$  load across the crystal is  $8.2 \Omega$  ( $R_L$ ) and  $200 \text{ pF}$  ( $C_L$ ).

## 50-MHz VHF CRYSTAL OSCILLATOR

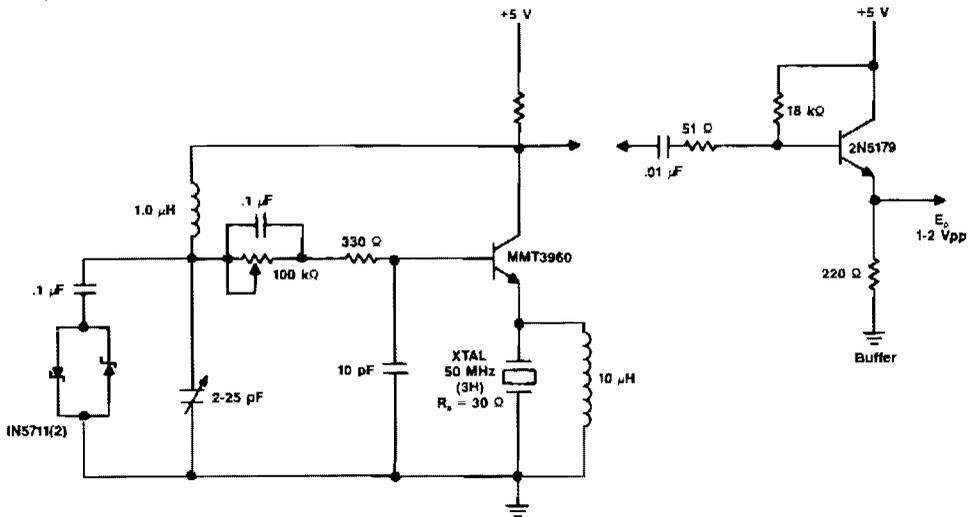

R. Matthys, RF Design, March 1987, p. 31.

**Fig. 21-14**

Figure 21-14 shows a 50-MHz oscillator operating on a third harmonic. The collector's load resistor  $R_L$  has been increased because the quartz crystal's internal series resistance  $R_S$  increases with frequency in the VHF range. The crystal's internal series resistance  $R_S$  is  $30\ \Omega$ , and the transistor's minimum current gain  $H_{FE}$  is 100. Using the same technique as for the 20 MHz oscillator, the external series  $R_L C_L$  equivalent load seen by the 50 MHz crystal is  $5.6\ \Omega$  ( $R_L$ ) and  $1000\ \text{pF}$  ( $C_L$ ).

# 22


## Decoders

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Second-Audio Program Adapter  
Tone Decoder  
Encoder/Decoder  
Direction Detector/Decoder  
Sound-Activated Decoder

## SECOND-AUDIO PROGRAM ADAPTER

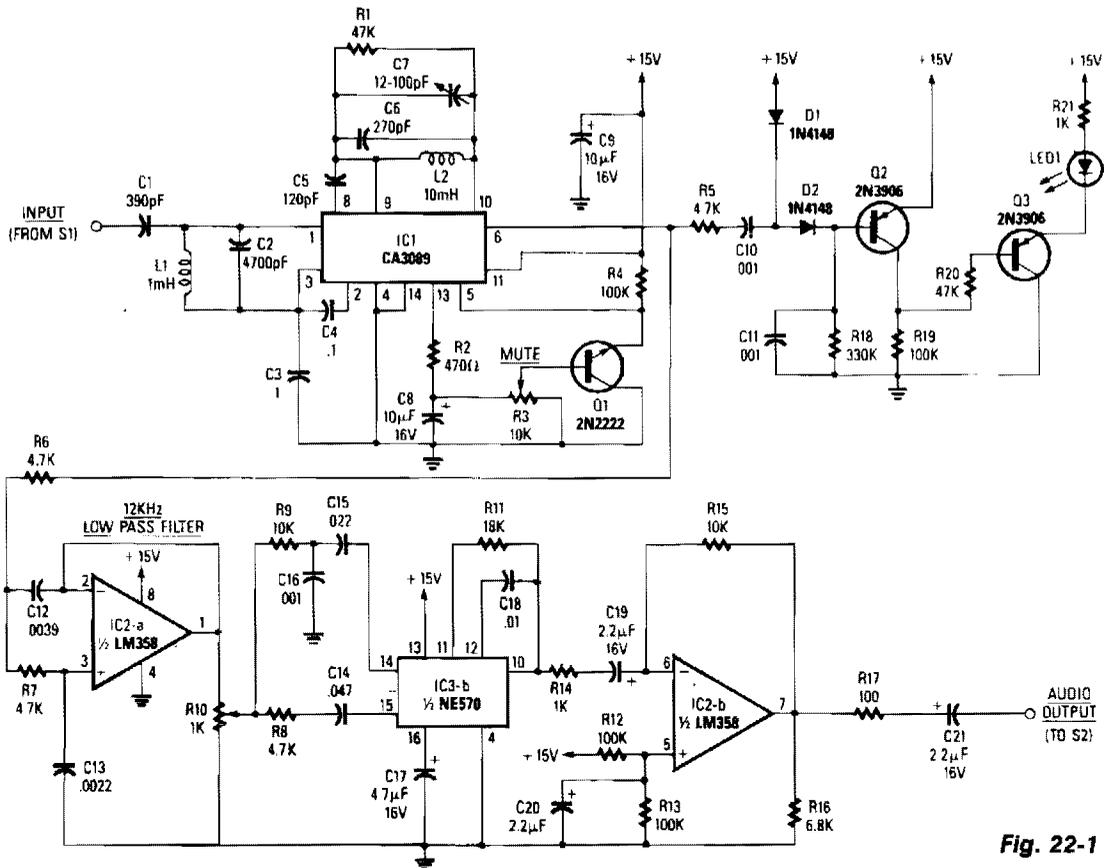

**Fig. 22-1**

Reprinted with permission from Radio-Electronics Magazine 1989, R-E Experimenters Handbook Copyright Gernsback Publications, Inc., 1989.

The baseband-audio input comes from the pole of switch S1 in the stereo decoder, and is coupled to IC1 (a CA3089) via a 78.6 kHz bandpass filter that consists of capacitors C1 and C2, and inductor L1. IC1 is a combination i-f amplifier and quadrature detector normally used for FM radio systems operating within an i-f of 10.7 MHz. The device works equally well at 78.6 kHz. Capacitors C6 and C7, and inductor L2 tune the detector section to 78.6 kHz, while C5 provides the necessary 90-degree phase shift for proper quadrature detector operation. The output voltage at pin 13 of IC1 is proportional to the level of the incoming signal. When the voltage at the wiper of potentiometer R3 reaches a predetermined threshold level, Q1 conducts, grounding pin 5 of IC1, enabling IC1's mute function.


Detected audio output from pin 6 of IC1 goes to IC2a, which is configured as a 12-kHz, -12 dB per octave, low-pass filter. The output of IC2a appears across potentiometer R10, which provides a means of adjusting the drive level into IC3b, the 2:1 compander.

## SECOND-AUDIO PROGRAM ADAPTER (Cont.)

Audio from the wiper of R10 is split into two paths: a high-pass filter (C14 and R8) provides a path to the rectifier input of the compander, and a bandpass filter (R9, C16, and C15) that feeds the audio input of the compander. A fixed 390- $\mu$ s de-emphasis network is formed by C18 and R11 in conjunction with IC3b. Corrected audio appears at pin 10 of IC3b and is coupled to IC2b, and output buffer amplifier.

Audio from pin 6 of IC1 is also coupled to an audio high-pass filter, R5 and C10, and fed to an audio rectifier, D1, D2, and C11. When a SAP signal is detected by IC1, it is rectified by D1 and D2; the resultant dc charges C11. An increasing positive voltage at the base of Q2 causes its current flow to decrease, so the voltage at Q2's collector also decreases. That in turn causes the base voltage of Q3 to drop, which causes Q3 to conduct, thereby lighting the LED.

### TONE DECODER

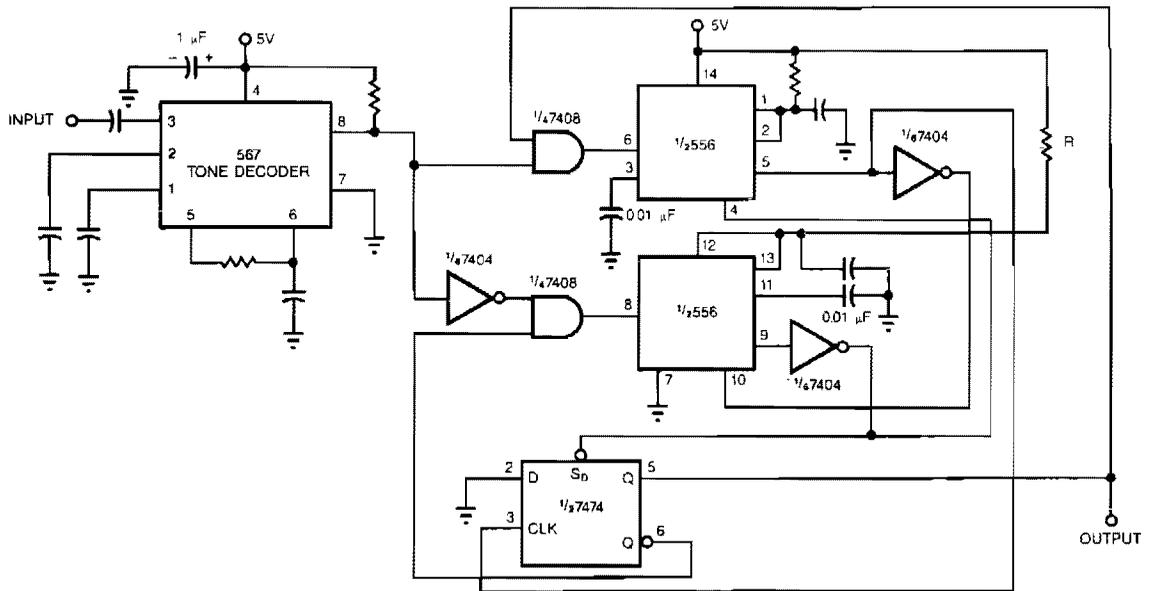

HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

Fig. 22-2

Adding a pair of one shots to the output of a 567 tone decoder renders it less sensitive to out-of-band signals and noise. Without the one shots, the 567 is prone to spurious output chatter. Other protection schemes, such as feeding back outputs or using an input filter, do not work as well as the one shots. The output of the 567 is high in the absence of a tone and becomes low when it detects a tone. The tone decoder triggers a one shot via an AND gate. The one shot's period is set to slightly less than the duration of a tone burst.

When the output of the tone decoder decreases, it triggers the second one shot. The second one shot's period is set to slightly less than the interval between tone bursts. The flip-flop enables and disables the inputs to one shots so that spurious outputs from the tone decoder do not affect the output.

## ENCODER/DECODER

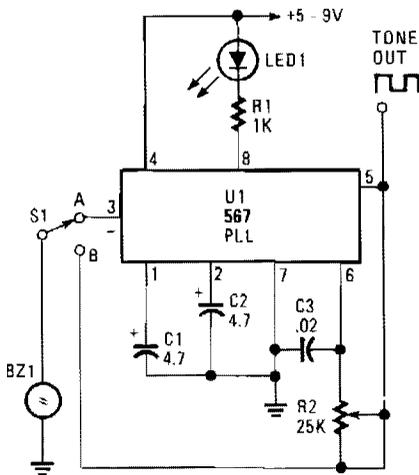


Fig. 22-3

The transducer circuit can be operated as either a tone encoder or decoder by changing the position of S1. The operating frequency of that dual-purpose circuit is determined by C3 and R2. Capacitors C1 and C2 are not critical and can be of almost any value between 1 and 5 mf. When the circuit is receiving an on-frequency signal, LED1 lights. Although a two wire piezo transducer with a resonance frequency of 2500 Hz was used in the circuit, any piezo unit should work—as long as the values of C3 and R2 are selected to tune to the transducer's operating frequency.

With power on and S1 in the B position, adjust R2 for the loudest tone output. The circuit should be tuned to the resonance frequency of the transducer. In that position, the circuit can be used as an acoustical or tone signal encoder. Next, switch to the A position and aim an on-frequency audible tone toward the transducer; the LED should light, indicating a decoded signal.

## DIRECTION DETECTOR DECODER

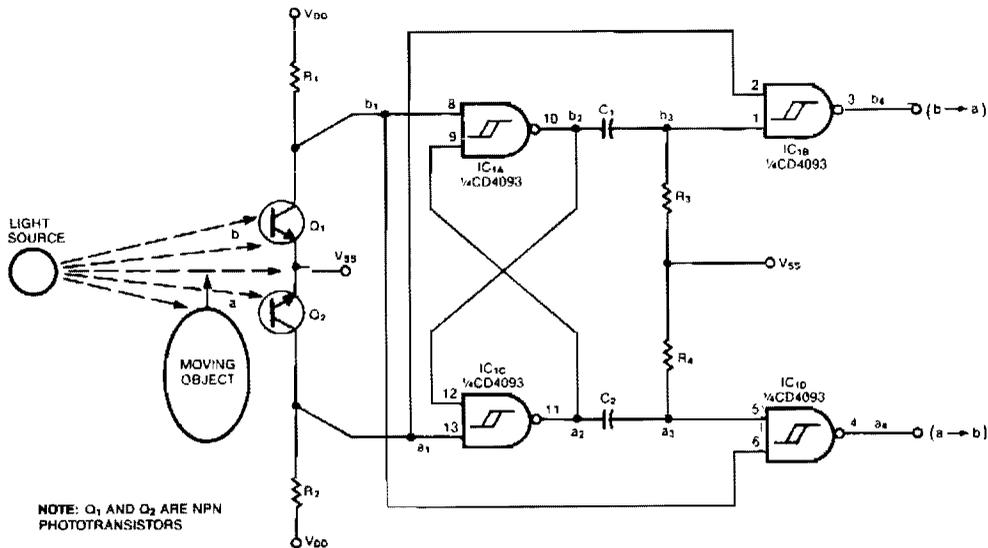


Fig. 22-4

## DIRECTION DETECTOR DECODER (Cont.)

\* This circuit, which was developed to monitor the traffic of bumblebees in and out of the hive, differentiates a-to-b motion from b-to-b motion. When used with an optical decoder, the circuit distinguishes clockwise from counterclockwise rotation and provides a resolution of one output pulse per quadrature cycle.

Q1 and Q2 are mounted so that a moving object first blocks one phototransistor, then both, then the other. Depending on the direction in which the object is moving, either IC1B or IC1D emits a negative pulse when the moving object blocks the second sensor. An object can get as far as condition 3 and retreat without producing an output pulse; that is, the circuit ignores any probing or jittery motion. If an object gets as far as condition 4, however, a retreat will produce an opposite-direction pulse.

The time constants R3C1 and R4C2 set the output pulse width. A 100 K $\Omega$ /100pF combination, for example, produces 10- $\mu$ s pulses. Select a value for pullup resistors R1 and R2 from the 10 K to 100 K $\Omega$  range, according to the sensitivity your application requires.

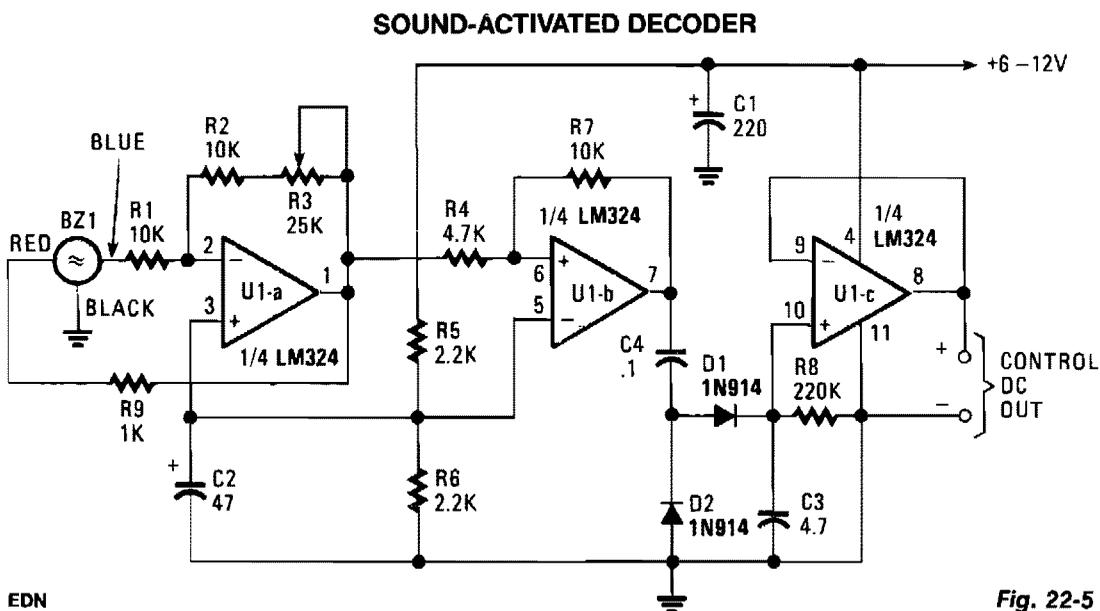


Fig. 22-5

The piezo transducer operates as a sound-pickup device as well as a frequency-selective filter. By controlling the gain of the op amps, the oscillator can be transformed into a sensitive and frequency-selective tone-decoder circuit. With the gain of U1a set just below the point of self oscillation, the transducer becomes sensitive to acoustically coupled audio tones that occur at or near its resonant frequency.

The circuit's output can be used to activate optocouplers, drive relay circuits, or to control almost any dc-operated circuit. The dc signal at the output of U1c varies with 0 to over 6 V, depending on the input-signal level. One unusual application for the sound-activated decoder would be in extremely high-noise environments, where normal broadband microphone pickup would be useless. Because piezo transducers respond only to frequencies within a very narrow bandwidth, little if any of the noise would get through the transducer.

# 23


## Delay Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Leading-Edge Delay  
Pulse Delay with Dual-Edge Trigger  
Adjustable Delay

## LEADING-EDGE DELAY

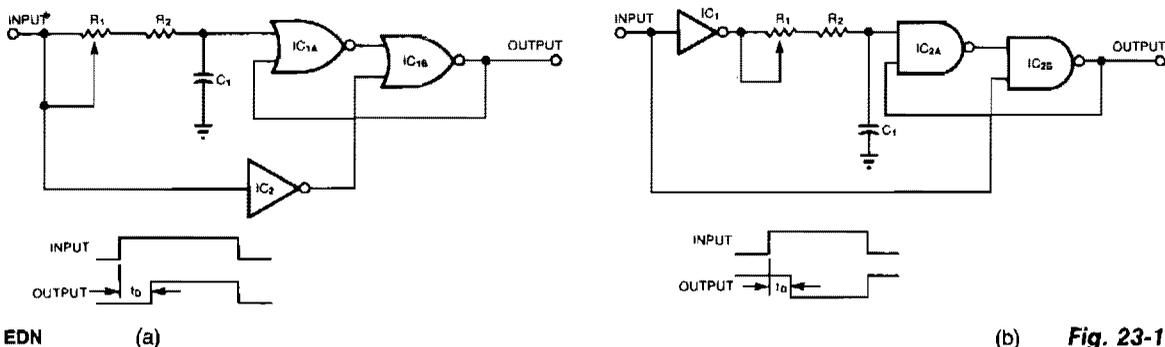


Circuit (a) lets you delay the leading edge of a positive pulse while leaving the trailing edge almost unaffected. A positive input transition, inverted by IC2, has no effect on IC1B. However, when the positive transition reaches IC1A, (delayed by the adjustable network of R1, R2, and C1), it toggles both NOR gates, initiating the output pulse. When the input decreases IC1B follows suit, delayed only by the propagation through itself and IC2. Circuit (b) produces an inverted output pulse. Inverter IC1 serves as a buffer for the signal source—an advantage when driving a low-impedance (short-delay) network. Moreover, only the propagation delay of IC2B separates the output's trailing edge from that of the input. You can configure circuit (a) to handle negative pulses by using NAND instead of NOR gates. Similarly, circuit (b) will produce a delayed positive pulse in response to negative input pulse, if you substitute NOR gates for NAND gates.

## PULSE DELAY WITH DUAL-EDGE TRIGGER

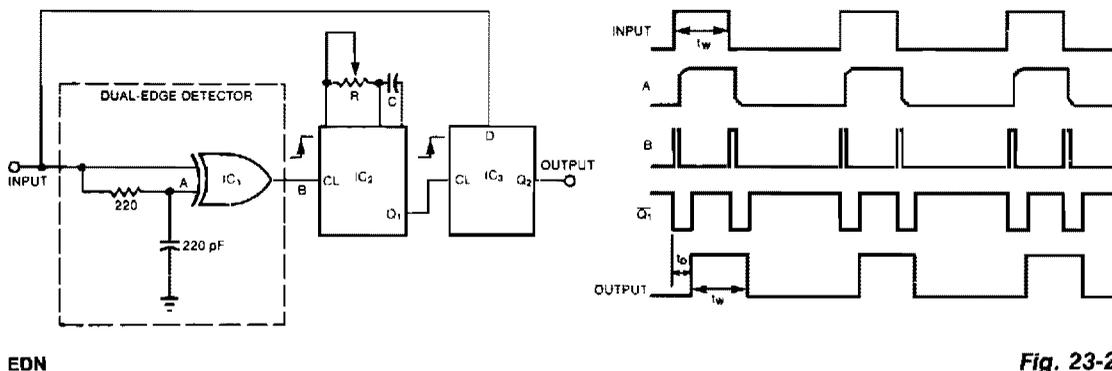

A single monostable multivibrator delays a pulse train by a variable amount; nonetheless, this amount can be no less than the minimum allowed pulse width  $t_w$ . The exclusive-OR gate, IC1, generates a short pulse following every leading or falling edge of the input waveform. These pulses cause one-shot IC2 to produce a negative-going pulse with a duration equal to the desired time delay  $t_p$ , which you set by adjusting potentiometer R. Flip-flop IC3 then creates a delayed replica of the input pulse by latching the Q1 output of IC2 between positive-going transitions. You can independently control the output-pulse duration by cascading a second one shot with the first.

## ADJUSTABLE DELAY

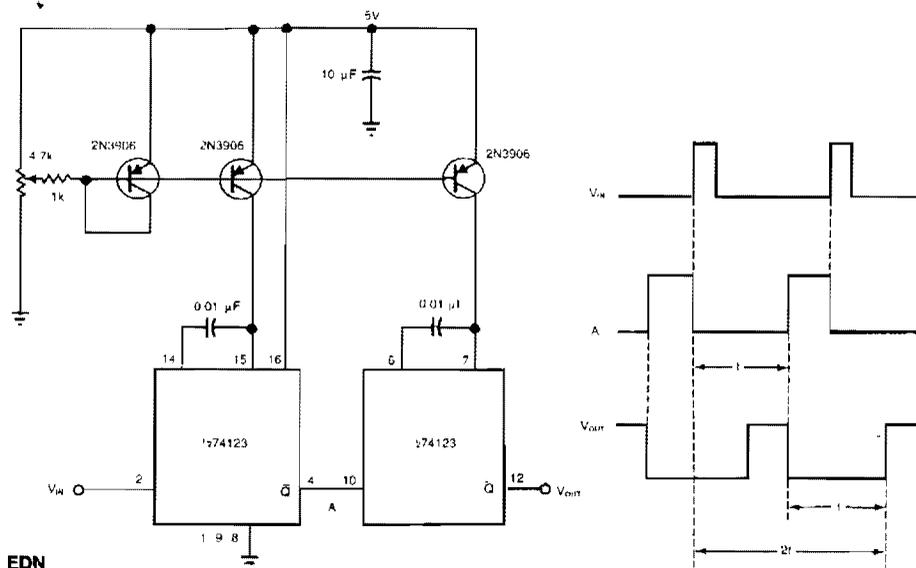

**Fig. 23-3**

You can obtain well over  $360^\circ$  of phase delay by cascading two monostable multivibrators. In a typical configuration, a single monostable multivibrator is used to introduce delay in a pulse train; the multivibrator triggers on each incoming pulse, provided it resets in time for the next pulse. Yet even when it resets in time, the single monostable multivibrator provides a maximum phase delay of less than  $360^\circ$ . However, with the cascaded-multivibrator approach, you can achieve  $650^\circ$  of phase delay by using an input-pulse spacing of  $200 \mu\text{s}$  for example, with the component values shown. Every input pulse will trigger the circuit while you adjust the phase delay throughout its available range. The first multivibrator triggers the second one, whose reset marks the total delay time ( $2t$ ). Each introduces a delay of  $t \mu\text{s}$ , based on  $0.01\text{-}\mu\text{F}$  timing capacitors and equal charging currents from the three-transistor, dual-current source. The two multivibrator arrangement allows the first multivibrator to reset in time to be triggered by the next input pulse. Also, the variation of  $t$  is linear with the potentiometer setting.

# 24


## Demodulator

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

565 SCA Demodulator

## 565 SCA DEMODULATOR

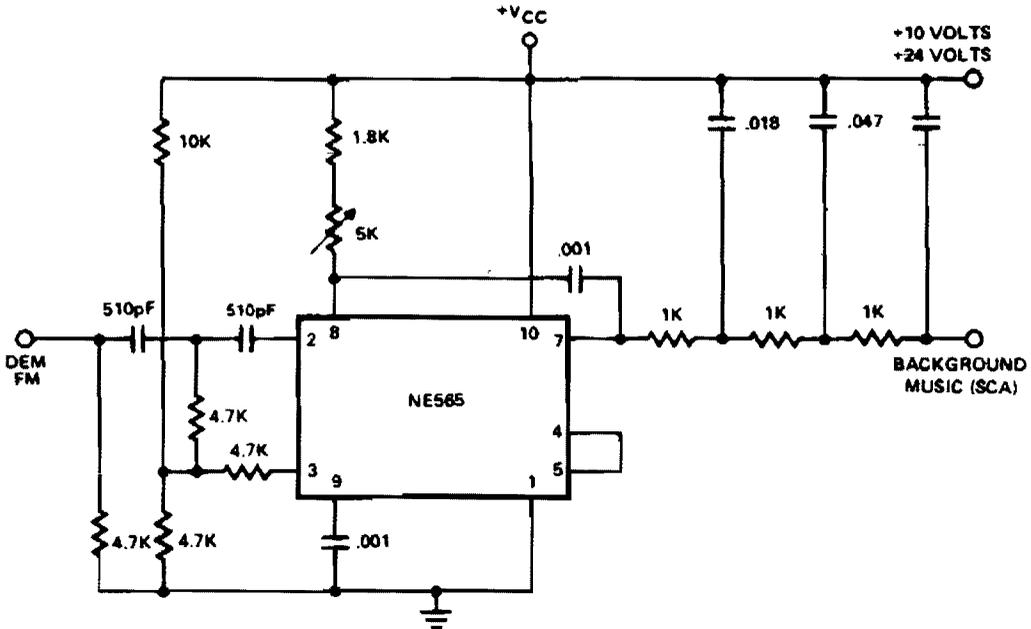

SIGNETICS

Fig. 24-1

This application involves demodulation of a frequency-modulated subcarrier of the main channel. This popular example uses the PLL to recover the SCA (Subsidiary Carrier Authorization or storecast music) signal from the combined signal of many commercial FM broadcast stations. The SCA signal is a 67 kHz frequency-modulated subcarrier which puts it above the frequency spectrum of the normal stereo or monaural FM program material. By connecting the circuit to a point between the FM discriminator and the deemphasis filter of an FM receiver and tuning the receiver to a station which broadcasts an SCA signal, you can obtain hours of commercial-free background music.

# 25


## Detectors

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Wide-Range Peak Detector	Precision Threshold Detector
Schmitt Trigger	Out-Of-Bounds Pulse-Width Detector
Analog Peak Detector with Digital Hold	Digital Frequency Detector
500-Hz Tone Detector	Missing-Pulse Detector
Audio Decibel Level Detector with Meter Driver	Digital Peak Detector
Precision Envelope Detector	High-Bandwidth Peak Detector
Frequency-Boundary Detector	Wide-Bandwidth Peak Detector
Low-Drift Peak Detector	
Edge Detector	
Null Detector	

## WIDE-RANGE PEAK DETECTOR

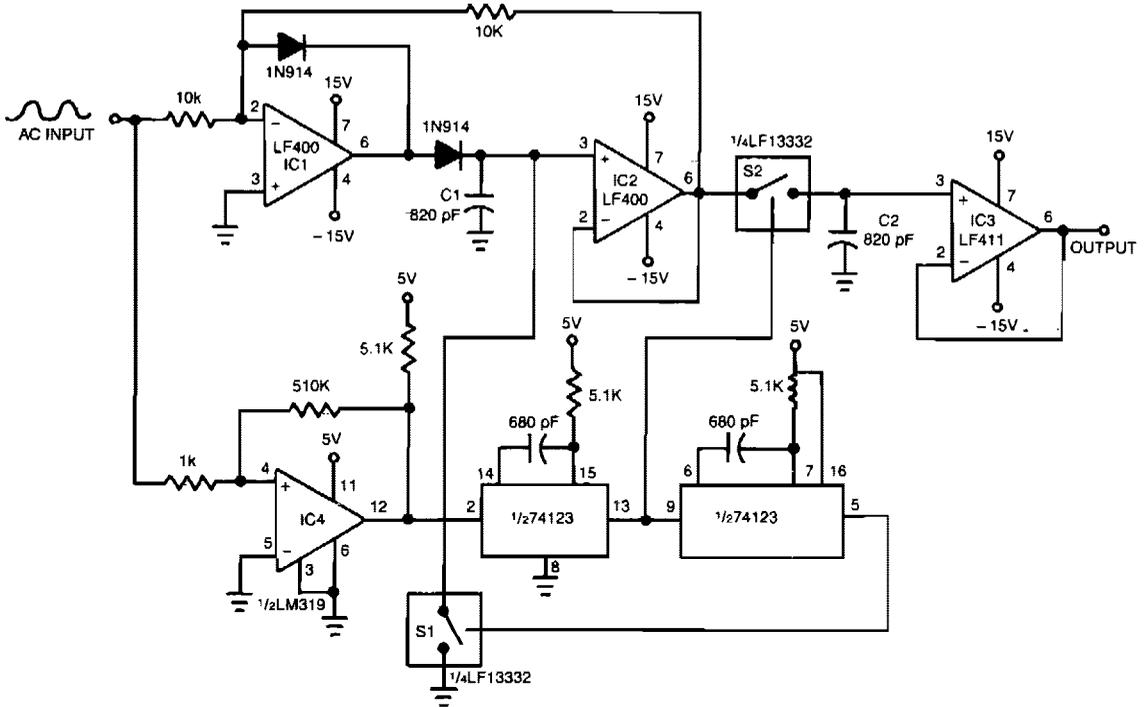


EDN

**Fig. 25-1**

IC1 and IC2 form an inverting half-wave precision-rectifier/peak-detector circuit. Negative input-signal, swings with peaks larger than the voltage on C1, cause this capacitor to charge to the new peak voltage. The capacitor holds this voltage until a larger signal peak arrives. When the input swings high, comparator IC4 detects the zero crossing and triggers the one-shot multivibrator. The one shot closes FET switch S2, thereby causing C2 to charge to the peak voltage held on C1, during the previous half cycle. The second one shot then produces a pulse that causes FET switch S1 to discharge C1. If the next negative signal-input peak is different from the previous one, the circuit captures it and it appears at IC3's output during the next half cycle. The peak detector thus resets itself once every input-waveform cycle. Note that the zero crossings are necessary to trigger the switches; therefore, the circuit is usable only with ac signals.

## SCHMITT TRIGGER

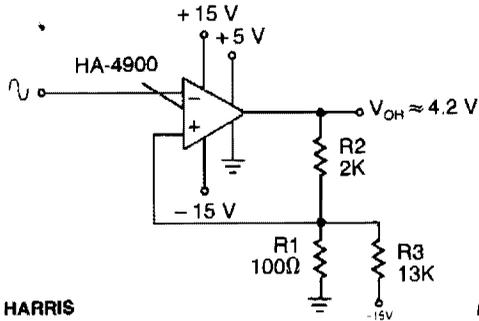


HARRIS

Fig. 25-2

This circuit has a 100-mV hysteresis which can be used in applications where very fast transition times are required at the output, even though the signal input is very slow. The hysteresis loop also reduces false triggering because of noise in the input.
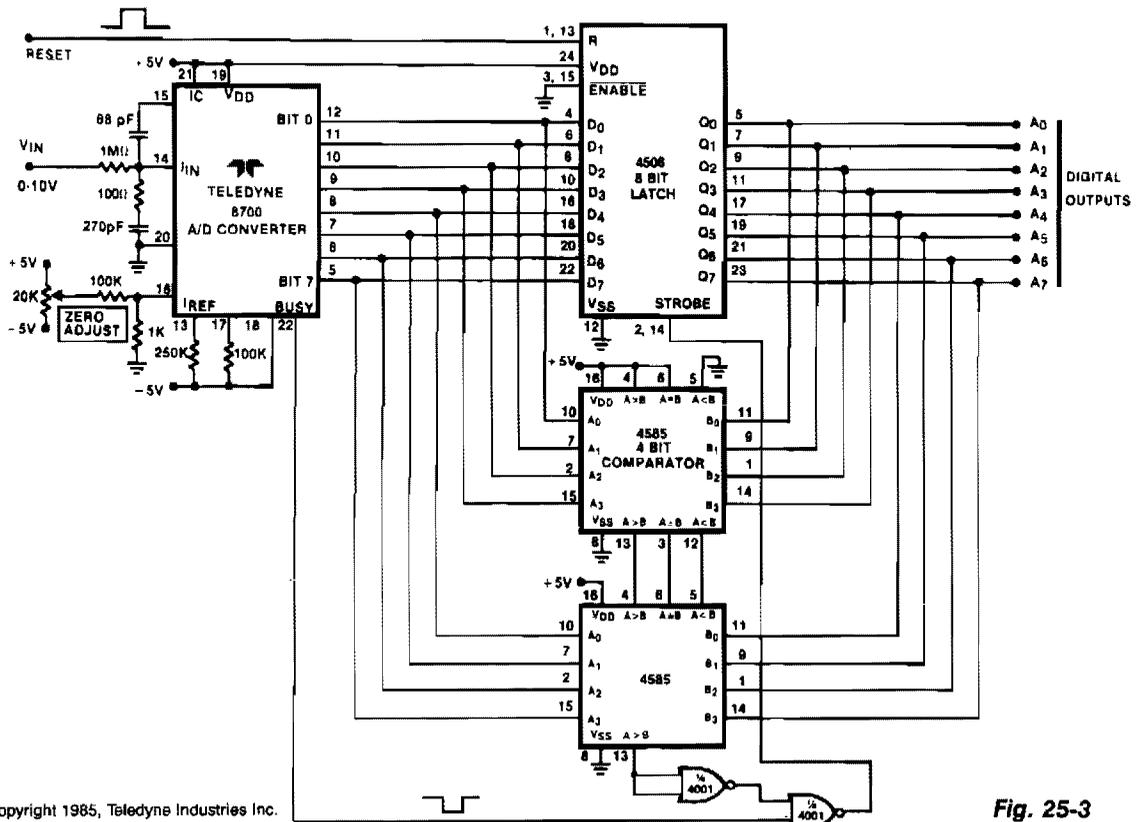
## ANALOG PEAK DETECTOR WITH DIGITAL HOLD




Copyright 1985, Teledyne Industries Inc.


Fig. 25-3

Analog peak detection is accomplished by repeatedly measuring the input signal with an a/d converter and comparing the current reading with the previous reading. If the current reading is larger than the previous, the current reading is stored in the latch and becomes the new peak value. Since the peak is stored in a CMOS latch, the peak can be stored indefinitely.

## 500-HZ TONE DETECTOR

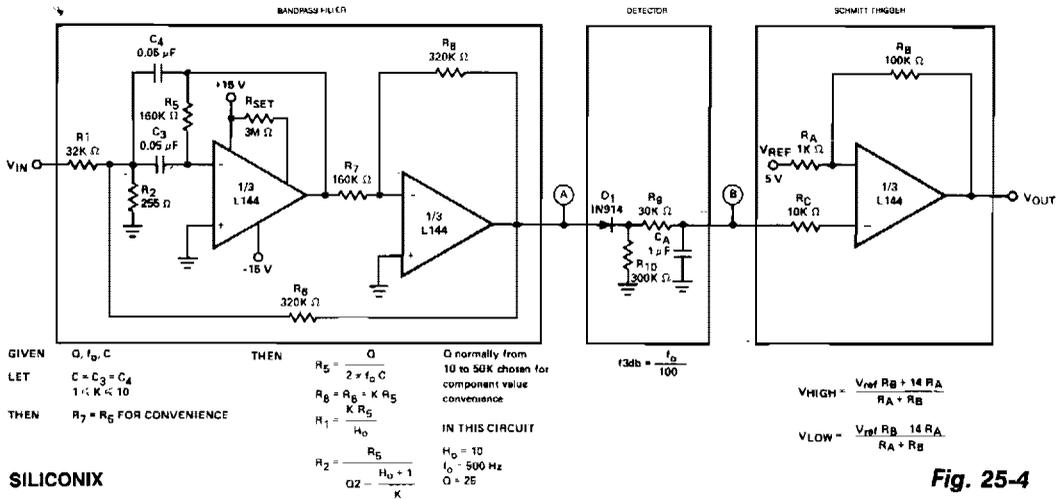
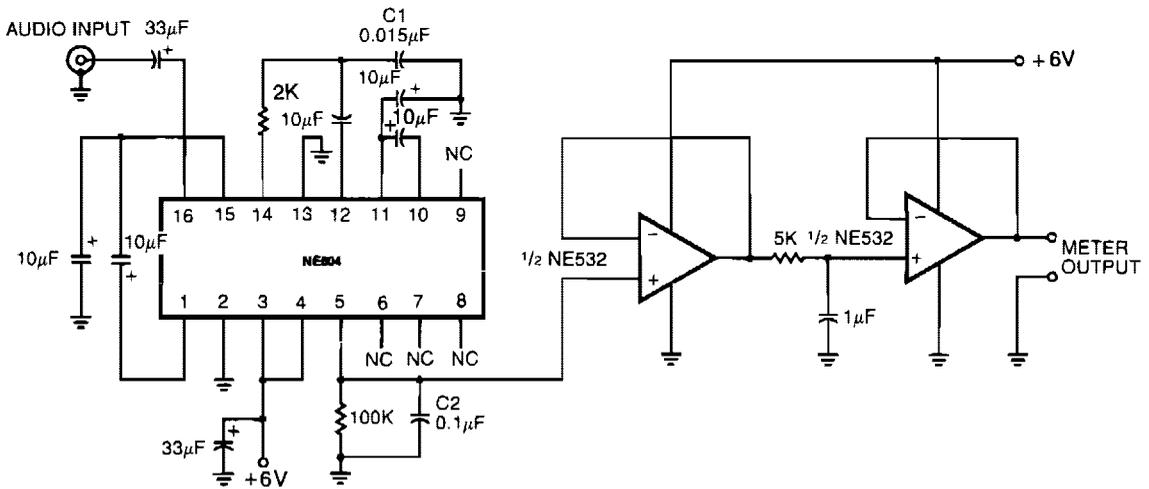
## AUDIO DECIBEL LEVEL DETECTOR WITH METER DRIVER




**SIGNETICS**

**Fig. 25-5**

This circuit draws very little power, less than 5 mA with a single 6-V power supply, making it ideal for portable battery-operated equipment. The small size and low power consumption belie the 90-dB dynamic range and 10.5- $\mu\text{V}$  sensitivity. Dc output voltage proportional to the  $\log_{10}$  of the input signal level. Thus, a standard 0-5 voltmeter can be linearly calibrated in decibels over a single 80-dB range. The circuit is within 1.5-dB tolerance over the 80-dB range for audio frequencies from 100 Hz to 10 kHz. Higher audio levels can be measured by placing an attenuator ahead of the input capacitor.

## PRECISION ENVELOPE DETECTOR

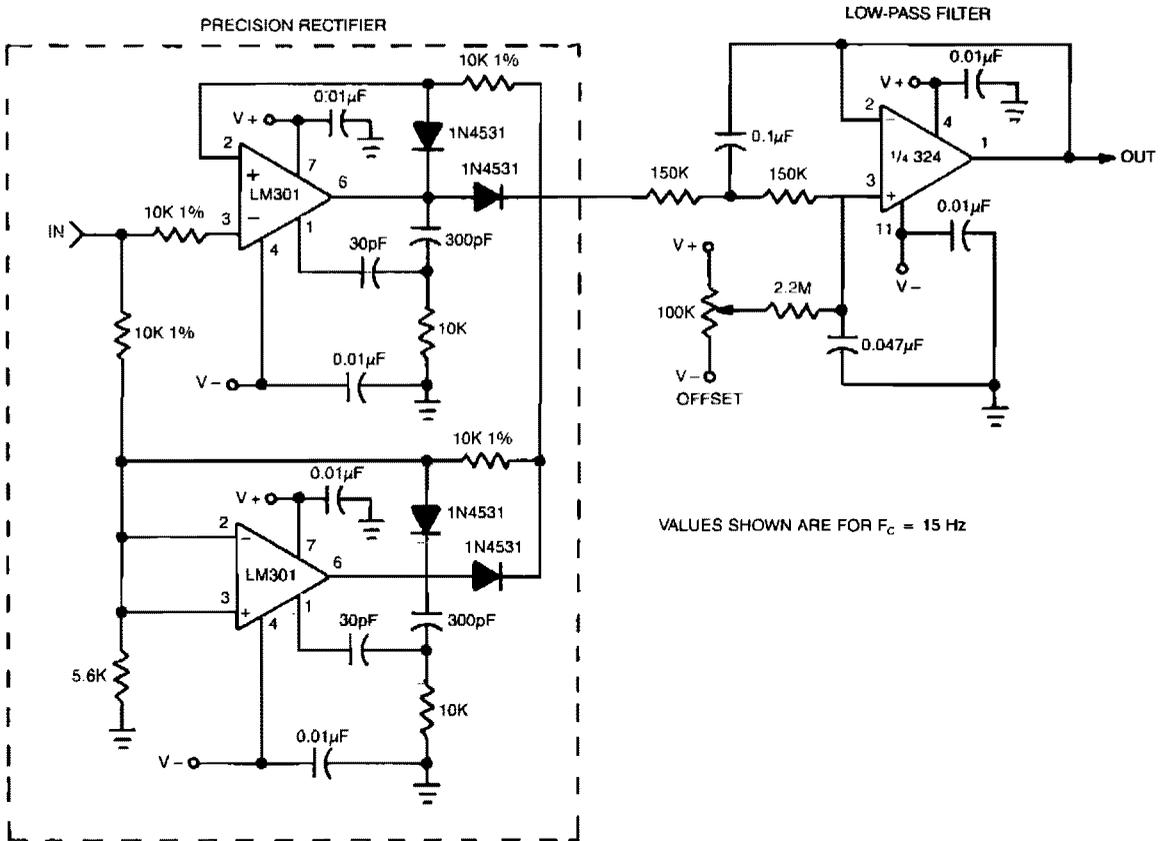

EDN


**Fig. 25-6**

This circuit is useful for signal-processing sonar data recorded on an instrumentation-quality analog tape recorder. The envelope detector utilizes ready available parts, and furnishes accuracy beyond 100 kHz. Two LM301 op amps connected as precision absolute-value circuits use 2-pole frequency compensation for increased slew rate. And one section of an LM324 quad op amp connected in a Butterworth LPF configuration subjects the rectifier's output to a low-pass filter.

$$f_c = 1/2\pi RC_1$$

$$C_2 = (1/2) C_1$$

## FREQUENCY-BOUNDARY DETECTOR

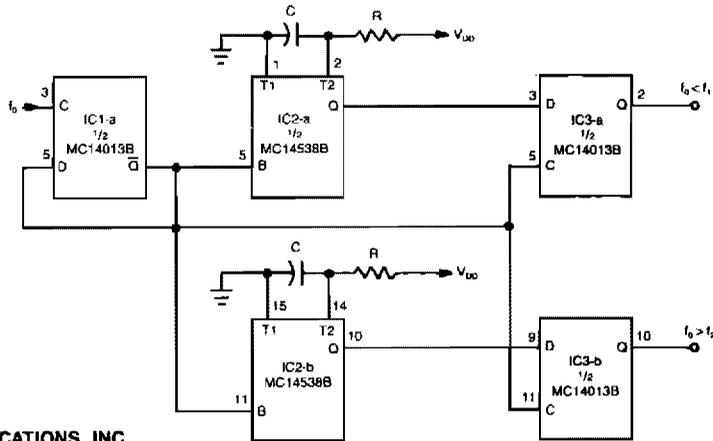


GERNSBACK PUBLICATIONS, INC.

Fig. 25-7

The circuit can be used to tell whether or not an input signal is within a certain frequency range. The device consists of three ICs, a dual monostable multivibrator, and two dual D-type flip-flops. The signal whose frequency is in question is fed to the clock input of one of the flip-flops. The  $Q$  output of that flip-flop (IC1a) is cross coupled to its data input so that it acts like a divide-by-two counter. The trailing edge of the  $Q$  output is used to trigger the one shots formed by IC2. The upper- and lower-frequency boundaries are determined by the two sections of IC2; the dual precision monostable multivibrator and their external rc networks. The upper-frequency boundary,  $f_1$ , is set by the output of IC2a, and the lower-frequency boundary,  $f_2$ , is set by the output of IC2b.

The frequency of the input to the circuit can be anywhere from dc to 100 kHz. The states of the outputs of IC2, which determine the upper- and lower-frequency boundaries, are latched by IC3a and IC3b respectively. The output of IC3a will be high only when the input frequency is less than that of the output of IC2a,  $f_1$ . The output of IC3b will be high only when the frequency of the input is greater than that of the output of IC2b,  $f_2$ .

## LOW-DRIFT PEAK DETECTOR

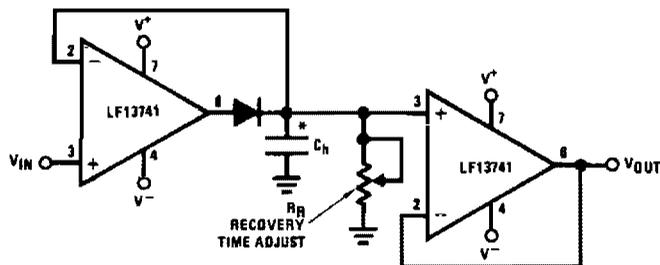



NATIONAL SEMICONDUCTOR CORP.

\*Low leakage capacitor

Fig. 25-8

This circuit uses op amp U1 to compensate for the offset in peak detector diode D1. Across  $C_h$  is the exact peak voltage; U2 is used as a voltage follower to read this voltage.

## EDGE DETECTOR

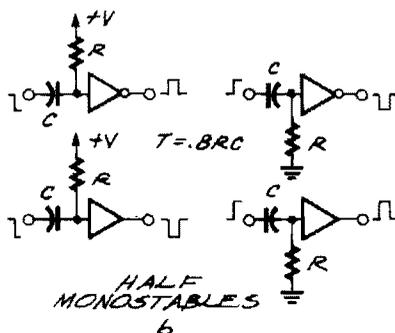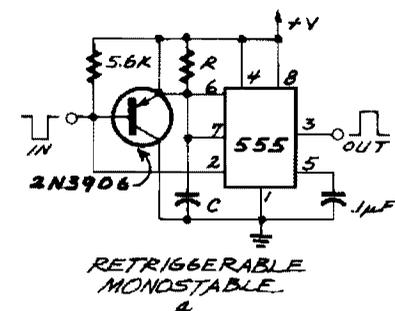


The 555 is a monostable that *wants* a negative-going trigger. If the pulse you're feeding it with is positive-going, you can run it through an inverter made up of either an inverting gate or, if you're tight on space, a single transistor. Both ways are shown. The circuits shown in Fig. 25-9b are edge detectors as well, and are usually referred to as half monostables, since they can't be used in every application. The width of the output pulse is determined by the RC value, but there are a few rules governing their use:

- The input pulse has to be wider than the output pulse
- The input pulse can't be glitchy
- The circuit can't be retriggered faster than the RC time

Reprinted with permission from Radio-Electronics Magazine, March 1989. Copyright Gernsback Publications, Inc., 1989.

Fig. 25-9

## PRECISION THRESHOLD DETECTOR

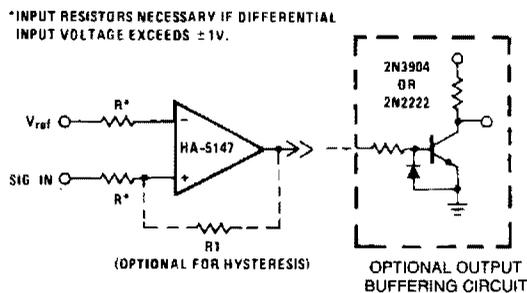


This circuit requires low noise, low and stable offset voltages, high open loop gain, and high speed. These requirements are met by the HA-5147. The standard variations of this circuit can easily be implemented using the HA-5147. For example, hysteresis can be generated by adding R1 to provide small amounts of positive feedback. The circuit becomes a pulse width modulator if  $V_{ref}$  and the input signal are left to vary. Although the output drive capability of this device is excellent, the optional buffering circuit can be used to drive heavier loads, preventing loading effects on the amplifier.

HARRIS

Fig. 25-10

## OUT-OF-BOUNDS PULSE-WIDTH DETECTOR

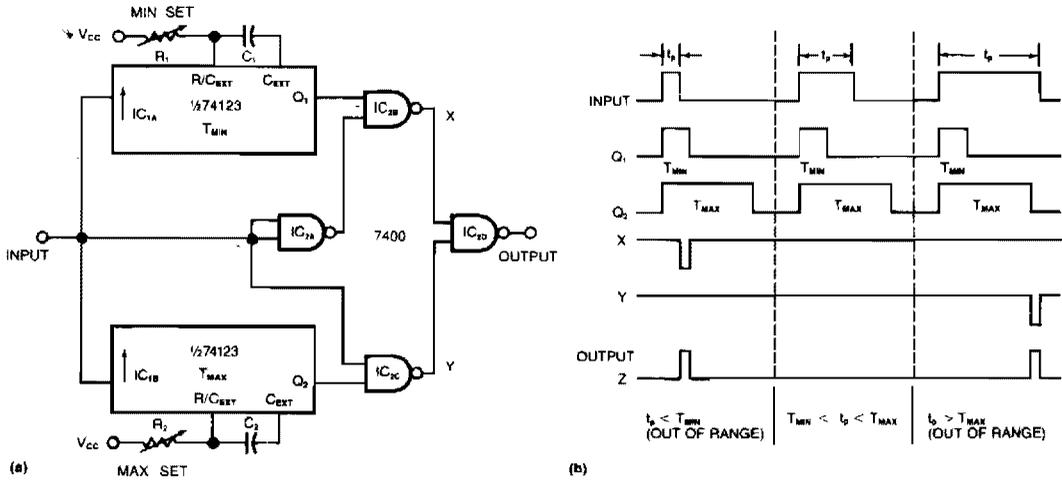


EDN

Fig. 25-11

Requiring only two ICs to monitor a train of positive pulses, this circuit produces a single positive output pulse for each input pulse whose duration is either too long or too short. You specify the minimum and maximum limits by adjusting the trimming potentiometers, R1 and R2. You can set the value of the acceptable pulse width from approximately 50 ns to 10  $\mu$ s, for a 74123 monostable multivibrator. The leading edge of an input pulse triggers one shots IC1A and IC1B as you can see from the timing diagram. Each NAND-gate output is high unless either or both inputs are low, so outputs X and Y are high unless the circuit encounters an out-of-range pulse. IC2D then gates a negative pulse from IC2B or IC2C to produce the circuit's positive output pulse.

## DIGITAL FREQUENCY DETECTOR

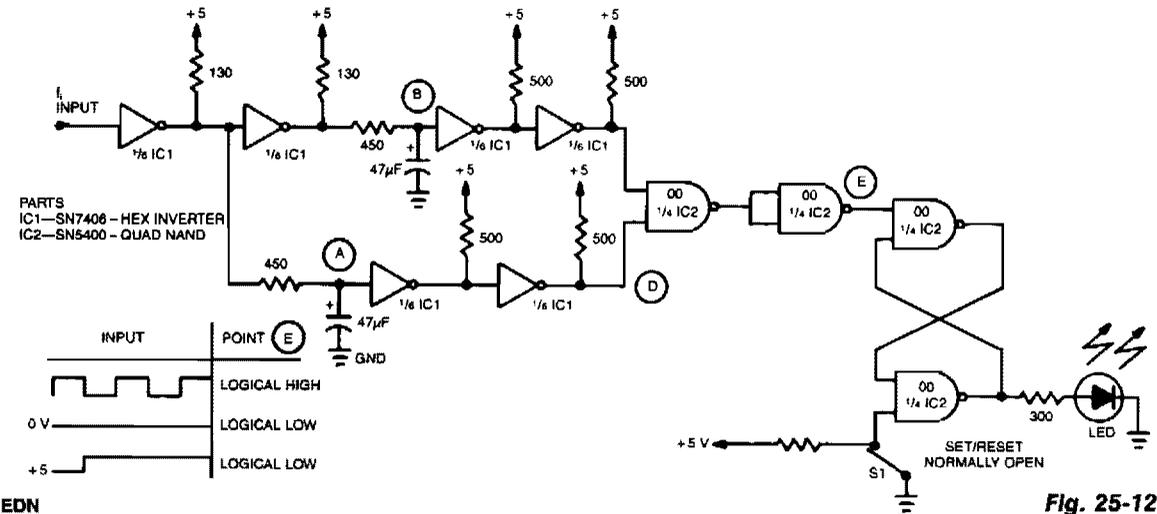


EDN

Fig. 25-12

## DIGITAL FREQUENCY DETECTOR (Cont.)

A simple inverter and NAND gate can be connected to yield a highly compact and reliable digital frequency detector. This circuit can detect frequencies up to 3 MHz with 50% duty cycles. When a frequency,  $f_i$ , appears at the input, points A and B detect a logical high dc level. Thereupon point E increases the latch sets and the LED lights. If the input frequency is absent and if the voltage is either at a constant high or low level, points A and B will be complementary and point E will decrease. This will reset the latch and extinguish the LED.

### MISSING-PULSE DETECTOR

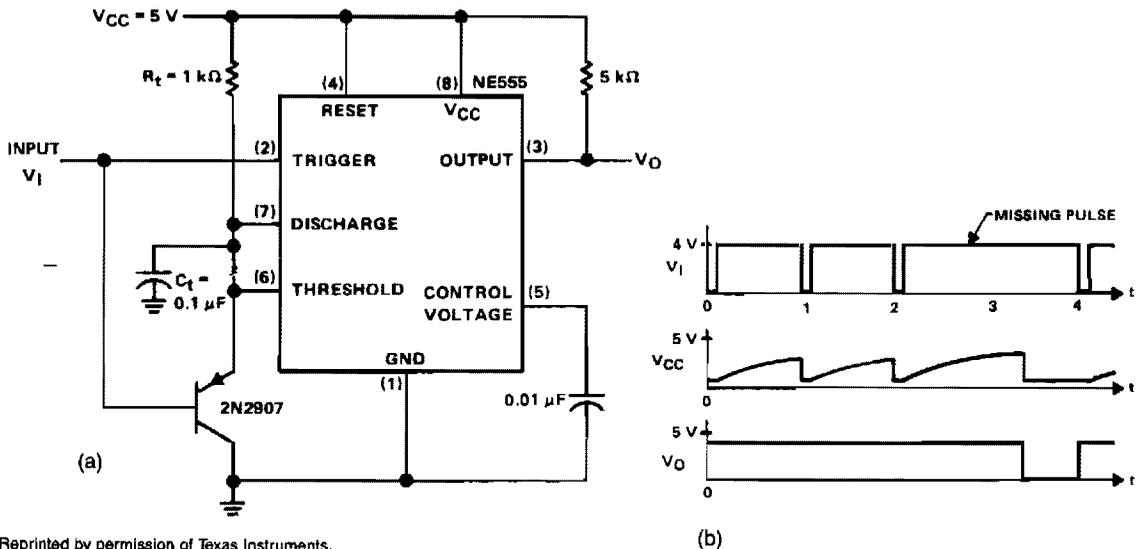


Reprinted by permission of Texas Instruments.

Fig. 25-13

This circuit will detect a missing pulse or abnormally long spacing between consecutive pulses in a train of pulses. The timer is connected in the monostable mode. The time delay should be set slightly longer than the timing of the input pulses. The timing interval of the monostable circuit is continuously retriggered by the input pulse train,  $V_I$ . The pulse spacing is less than the timing interval, which prevents  $V_C$  from rising high enough to end the timing cycle. A longer pulse spacing, a missing pulse, or a terminated pulse train will permit the timing interval to be completed. This will generate an output pulse,  $V_O$  as illustrated in Fig. 25-3b. The output remains high on pin 3 until a missing pulse is detected at which time the output decreases.

The NE555 monostable circuit should be running slightly slower, lower in frequency, than the frequency to be analyzed. Also, the input cannot be more than twice this free-running frequency or it would retrigger before the timeout and the output would remain in the low state continuously. The circuit operates in the monostable mode at about 8 kHz, so pulse trains of 8 to 16 kHz can be observed.

# DIGITAL PEAK DETECTOR

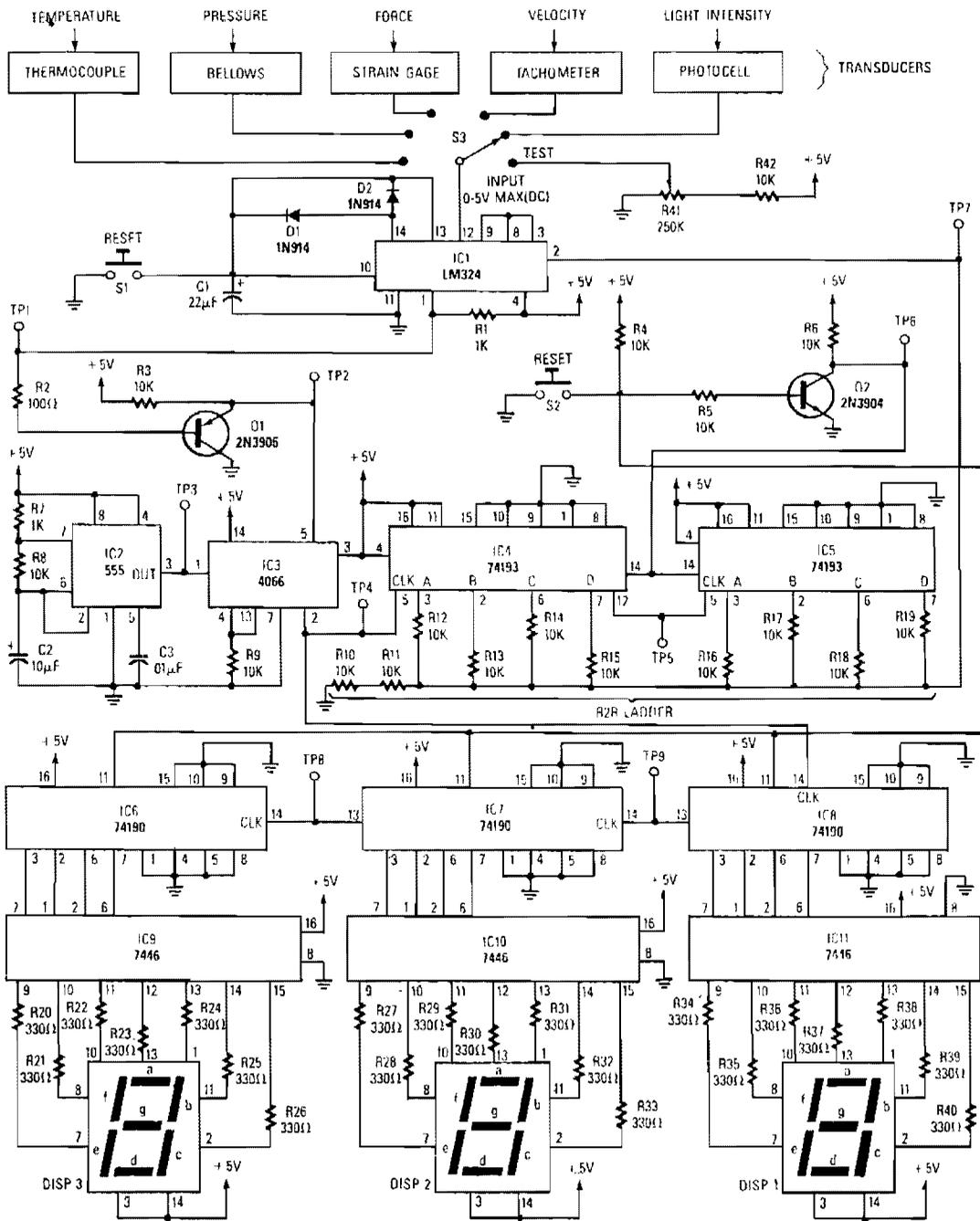


Reprinted with permission from Radio-Electronics Magazine, April 1989. Copyright Gernsback Publications, Inc., 1989.

**Fig. 25-14**

## DIGITAL PEAK DETECTOR CONT.

The peak detector tracks and holds, using the charge-storing ability of a capacitor, the highest output voltage from a transducer. Initially, the voltage on the inverting input of the comparator is at ground level. As a small voltage (0–5 V) is captured by the peak detector and presented to the comparator's noninverting input, the output will swing high, which asserts the bilateral switch; clock pulses now pass through the switch to clock both the BCD and binary counters. The outputs of the binary counters are connected to an R2R ladder network, which functions as a digital-to-analog converter. As the binary count increases, the R2R ladder voltage also increases until it reaches a point slightly above the voltage of the peak detector; at that instant, the comparator output swings low, which disables the bilateral switch and stops the counters. The number displayed on the 7-segment LED's will represent a value equivalent to the transducer's output.


## HIGH-BANDWIDTH PEAK DETECTOR

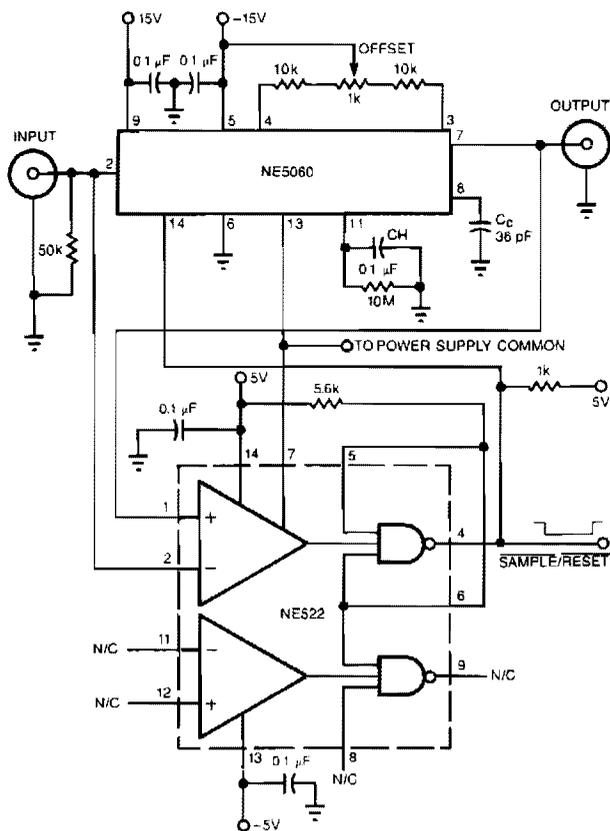

The high-speed peak detector uses a highly accurate, fast s/h amplifier controlled by a high-speed comparator. The s/h amplifier holds the peak voltage, until the comparator switches the amp to its sample mode, to capture a new, higher voltage level. The circuit handles all common-wave shapes and exhibits 5% accuracy from 50 Hz to 2 MHz.

The comparator's output decreases when the input signal exceeds the value of the currently held output. This transition puts the s/h amplifier into sample mode. Once the output reaches the value of the input, or the input signal falls below the output's level, the comparator's output increases; the high output brings the s/h amplifier back to the hold mode, thereby holding the peak value of the input signal. Reset the circuit by lowering the value of pin 4 of the NE522 comparator, which in turn allows the NE5060 s/h amplifier to acquire the input. The NE522 comparator has an open-collector output.

## NULL DETECTOR

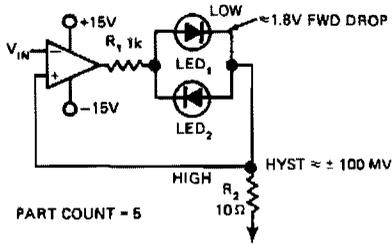


EDN

Fig. 25-16

In this indicating comparator circuit,  $R_2$  sets the hysteresis. If the 741 saturates at  $\pm 12$  V, the current in  $R_1$  will be approximately  $\pm 10$  mA if 0.1 V hysteresis is desired. Then  $0.1 \text{ V}/10 \text{ mA} = 10\Omega = R_2$ .

## WIDE-BANDWIDTH PEAK DETECTOR

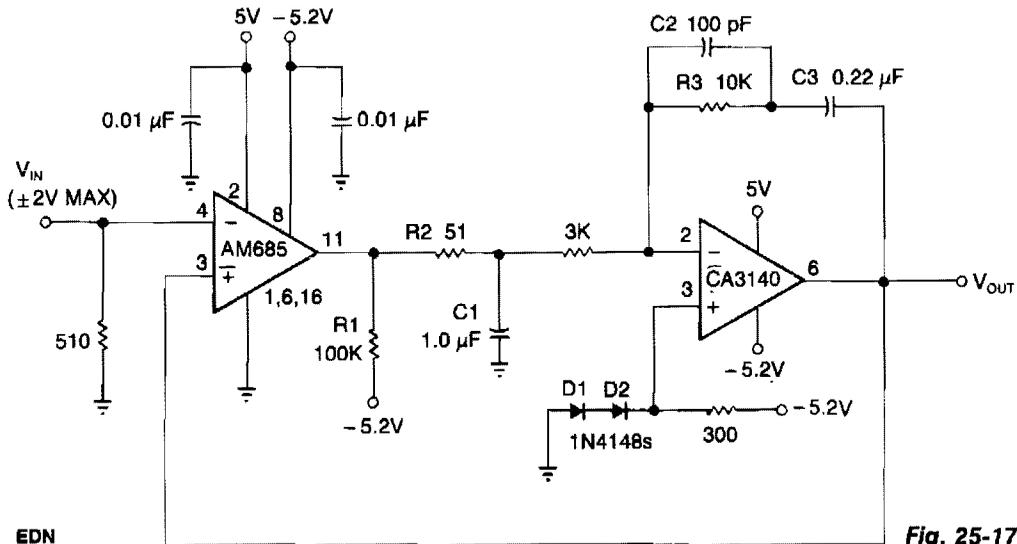

EDN

Fig. 25-17

This circuit can detect the positive peaks for signal frequencies higher than 5 MHz. It yields  $\pm 1\%$  accuracy for 400 mV to 4 V pk-pk signal amplitudes on sine, square, and triangular waveforms. The Am685 comparator output increases whenever  $V_{IN}$  is a greater negative voltage than  $V_{OUT}$ ; the high comparator output, in turn, charges  $C_1$  in a positive direction. The CA3140 op amp amplifies the  $C_1$  voltage with respect to the ECL-switching-threshold voltage ( $-1.3$  V) developed by diodes  $D_1$  and  $D_2$ . For repetitive waveforms, each cycle boosts  $V_{OUT}$  until it equals the peak input value. The peak-detection process is aided by the comparator's open-emitter output, which allows  $C_1$  to charge rapidly through  $R_2$ , but to discharge slowly through  $R_2$  and  $R_1$ . Reducing the value of  $C_1$  shortens system-response times. Although the circuit can't detect negative-going peaks, it can be modified to measure the pk-pk value of bipolar signals that are symmetric about ground. To do so, divide  $V_{OUT}$  by 2 using two 1-K $\Omega$  resistors and feed the comparator  $V_{OUT}/2$  rather than  $V_{OUT}$ .

## 26

# Digital-to-Analog Converters


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Digital-to-Analog Converters  
Four-Channel D/A Output Amplifier  
12-Bit Binary 2s Complement D/A  
Conversion System  
9-Bit CMOS D/A Converter  
Multiplying D/A Converter  
Positive Peak Detector

## DIGITAL-TO-ANALOG CONVERTERS

10 Bit, 4 Quadrant Multiplying DAC  
(Offset Binary Coding)

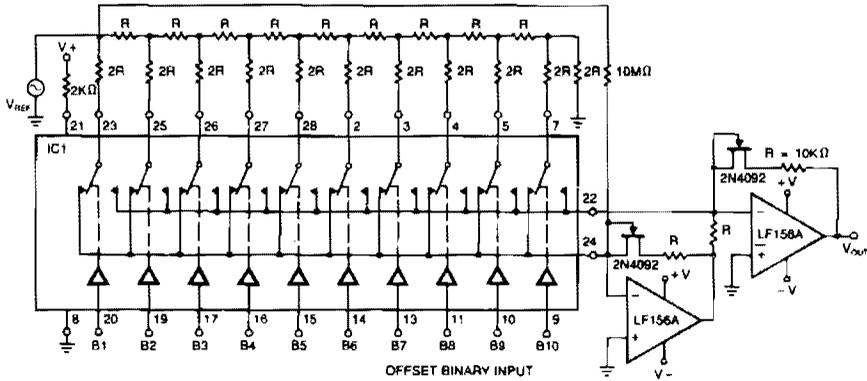


IC1: use five of either DG403, DG413, or DG423

Bipolar (Offset Binary) Operation

DIGITAL INPUT	ANALOG OUTPUT
1 1 1 1 1 1 1 1 1 1	$-V_{REF} (1 - 2^{-9})$
1 0 0 0 0 0 0 0 0 1	$-V_{REF} (2^{-9})$
1 0 0 0 0 0 0 0 0 0	0
0 1 1 1 1 1 1 1 1 1	$V_{REF} (2^{-9})$
0 0 0 0 0 0 0 0 0 1	$V_{REF} (1 - 2^{-9})$
0 0 0 0 0 0 0 0 0 0	$V_{REF}$

NOTE: 1 LSB =  $2^{-9} V_{REF}$   
\*Complementing B1 (MSB) will give 2's complement coding.

4 Bit Multiplying Current Switch D/A

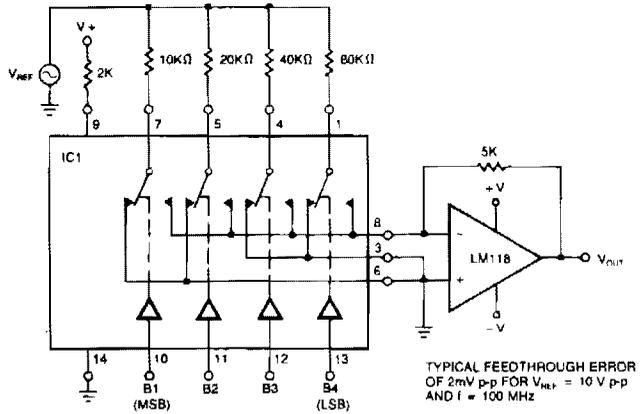

IC1: use two of either DG403, DG413, or DG423

TYPICAL FEEDTHROUGH ERROR  
OF 2mV p-p FOR  $V_{REF} = 10V$  p-p  
AND  $f = 100$  MHz


**SILICONIX**

**Fig. 26-1**

The following applications circuits are intended to illustrate the following points:

- A 2-KΩ resistor should be in series with  $V+$  to limit supply current with negative ringing of the bit inputs
- Temperature compensation for  $R_{DS(on)}$  can be provided in the feedback path of the op amp
- Bipolar reference voltages can be used in all configurations


# FOUR-CHANNEL D/A OUTPUT AMPLIFIER

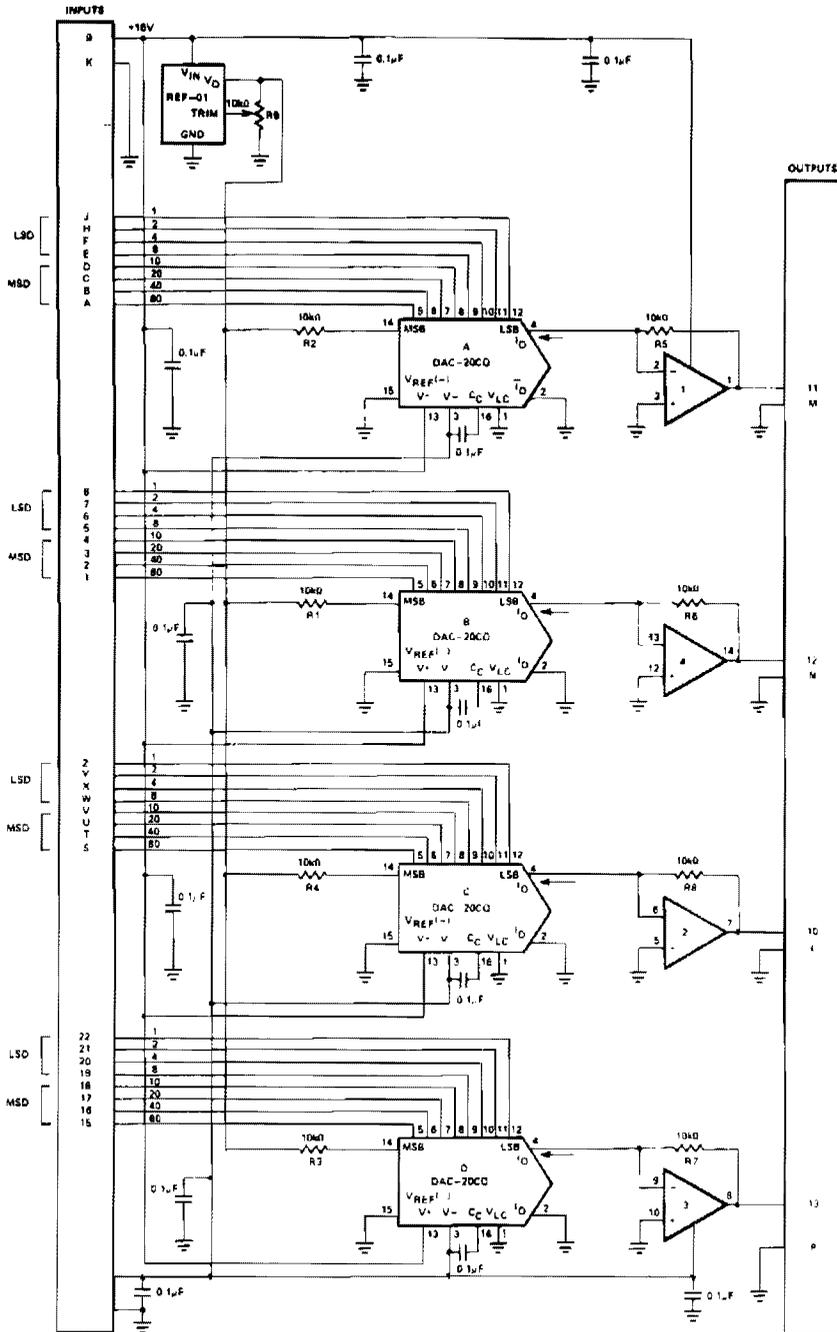

PRECISION MONOLITHICS INC.

Fig. 26-2
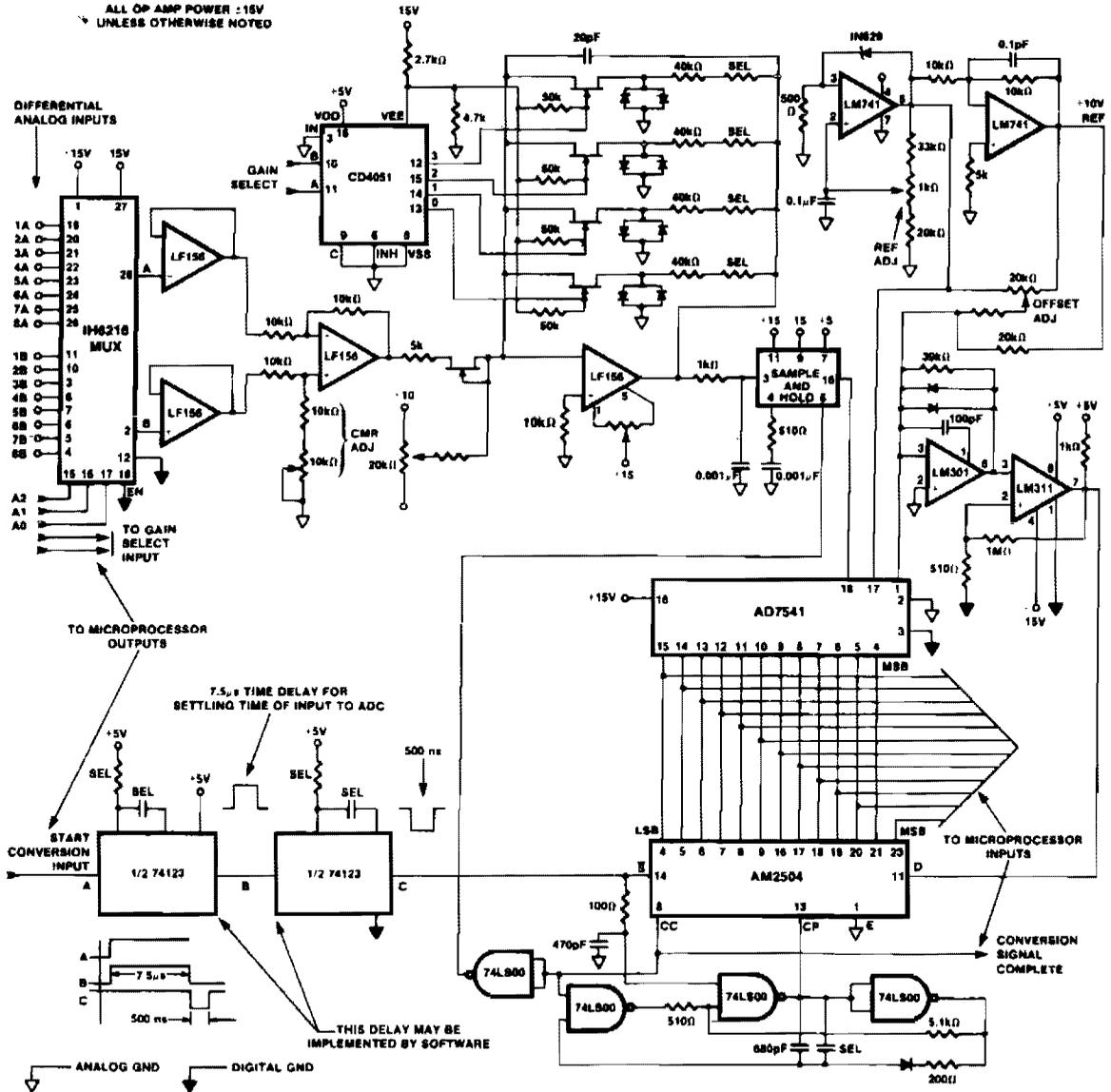
## 12-BIT BINARY 2<sup>s</sup> COMPLEMENT D/A CONVERSION SYSTEM




INTERSIL

Fig. 26-3

The front end of the DAC is configured differentially using dual eight-input IC multiplexer 1H6216 and three LM156 op amps. Following the differential amplifier is the programmable gain stage discussed earlier, with a low-pass filter on the output feeding the IH5110 sample and hold amplifier. The output of the IH5110 is connected to the comparator input, - input LM301, through the internal 10-KΩ feedback resistor of the 7541 multiplying d/a converter. The AD7541, along with a ±10-V reference and successive approximation logic, make up the 2's complement a/d converter.

## 9-BIT CMOS D/A CONVERTER

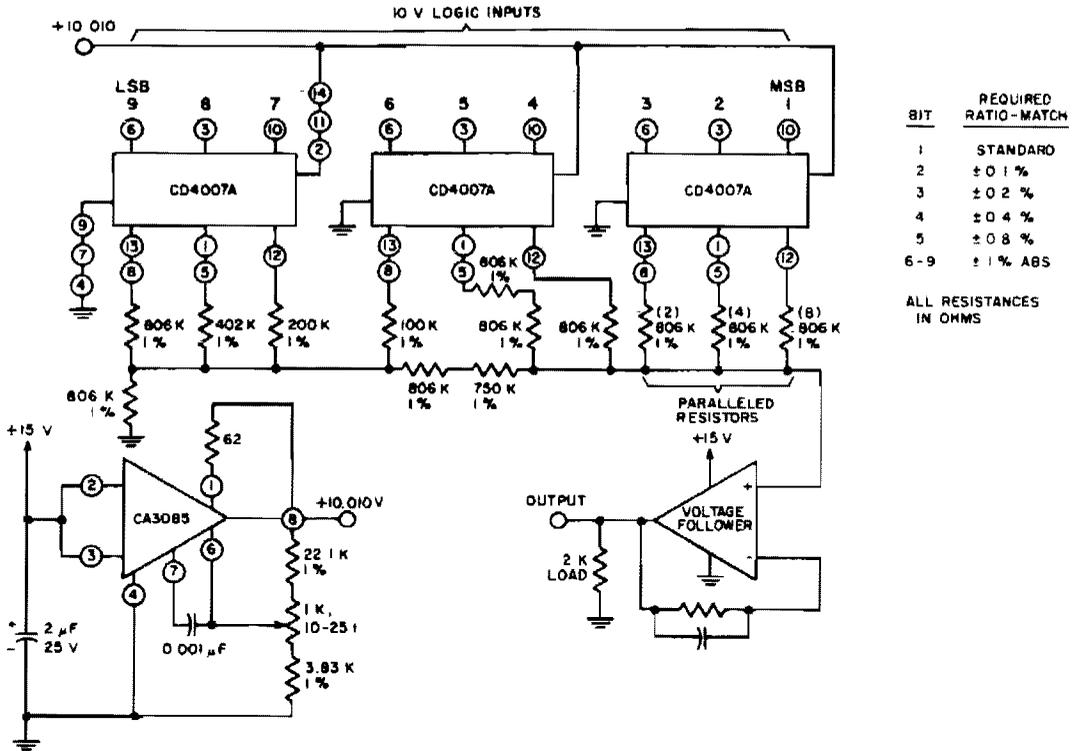


INTERSIL

Fig. 26-4

Three CD4007A IC packages perform the switch function using a 10-V logic level. A single 15-V supply provides a positive bus for the follower amplifier and feeds the CA3085 voltage regulator. The scale adjust function is provided by the regulator output control, which is set to a nominal 10 V in this system. The line-voltage regulation (approximately 0.2%) permits 9-bit accuracy to be maintained with a variation of several volts in the supply. System power consumption ranges between 70 and 200 mW; a major portion is dissipated in the load resistor and op amp. The regulated supply provides a maximum current of 440  $\mu$ A of which 370  $\mu$ A flows through the scale adjusting. The resistor ladder is composed of 1% tolerance metal-oxide film resistors. The ratio match between resistance values is in the order of 2%. The follower amplifier has the offset adjustment nulled at approximately a 1 V output level.

## MULTIPLYING D/A CONVERTER

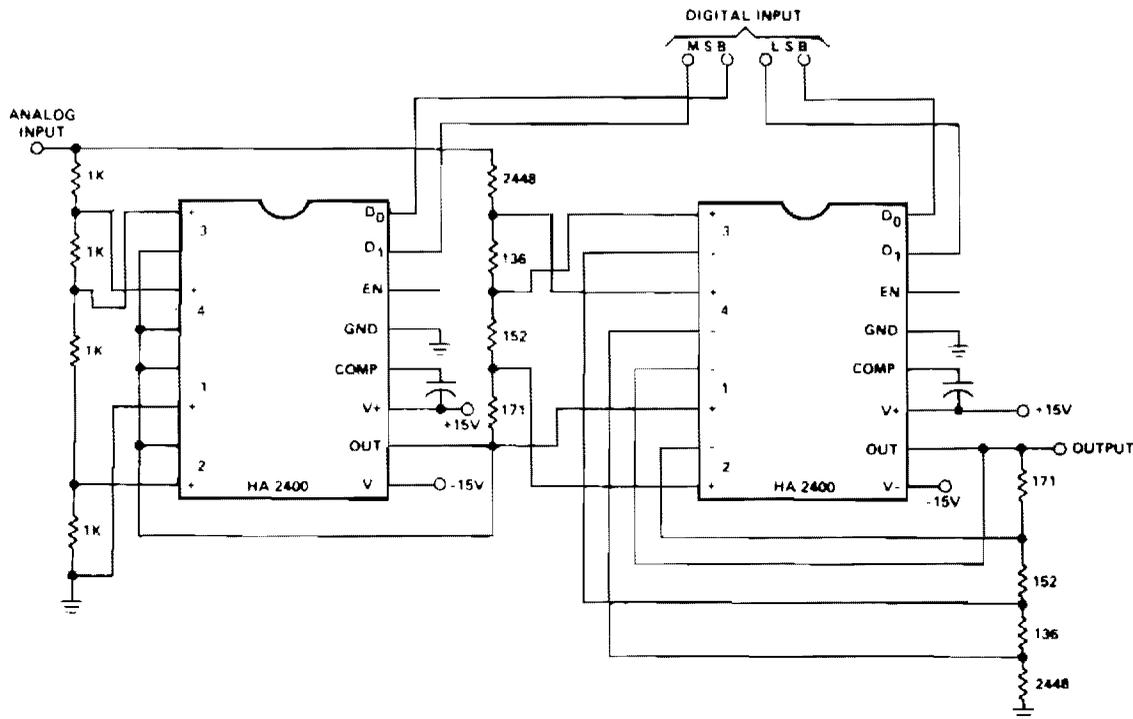

HARRIS


Fig. 26-5

The circuit performs the function:

$$V_{OUT} = V_{IN} \times \frac{N}{16}$$

where  $N$  is the binary number from 0 to 15 formed by the digital input. If the analog input is a fixed dc reference, the circuit is a conventional 4-bit D to ac signal, in which case the output is the product of the analog signal and the digital signal. The circuit on the left is a programmable attenuator with weights of 0,  $1/4$ ,  $1/2$ , or  $3/4$ . The circuit on the right is a noninverting adder, which adds weights to the first output of 0,  $1/16$ ,  $1/8$ , or  $3/16$ . If four quadrant multiplication is required, place a phase selector circuit in series with either the analog input or output. The  $D_0$  input of that stage becomes the + or - sign bit of the digital input.

## POSITIVE PEAK DETECTOR

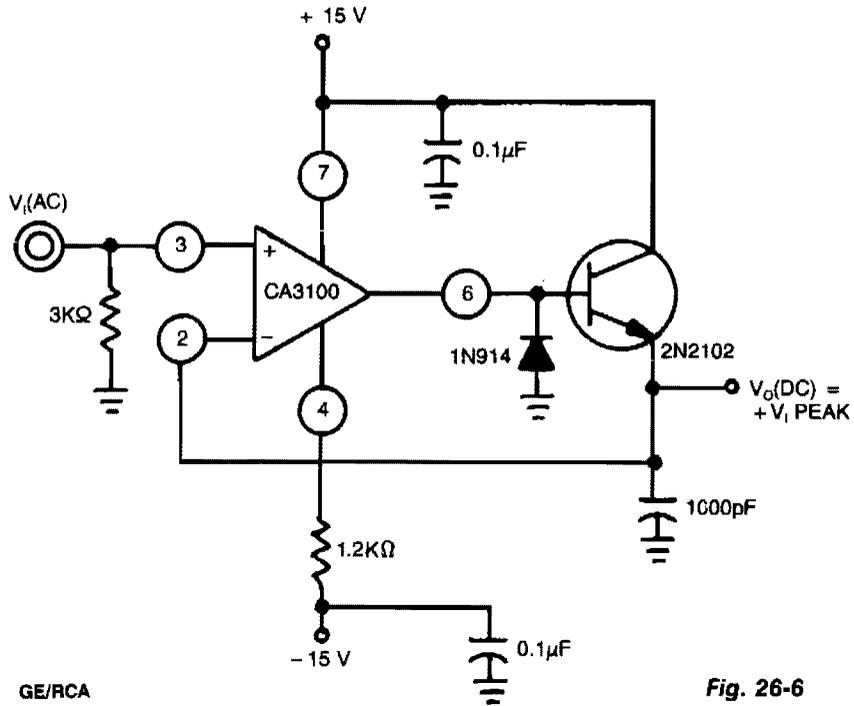

This peak detector uses a CA3100 BiMOS op amp as a wide-band noninverting amplifier to provide essentially constant gain for a wide range of input frequencies. The 1N914 clips the negative half of  $V_{IN}$  ( $R_4/R_3$ ) ( $R_5$ ). A 500- $\mu$ A load current is constant for all load values and the output reflects only positive input peaks.

# 27


## Display Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Two-Variable LED Matrix Display

## TWO-VARIABLE LED MATRIX DISPLAY

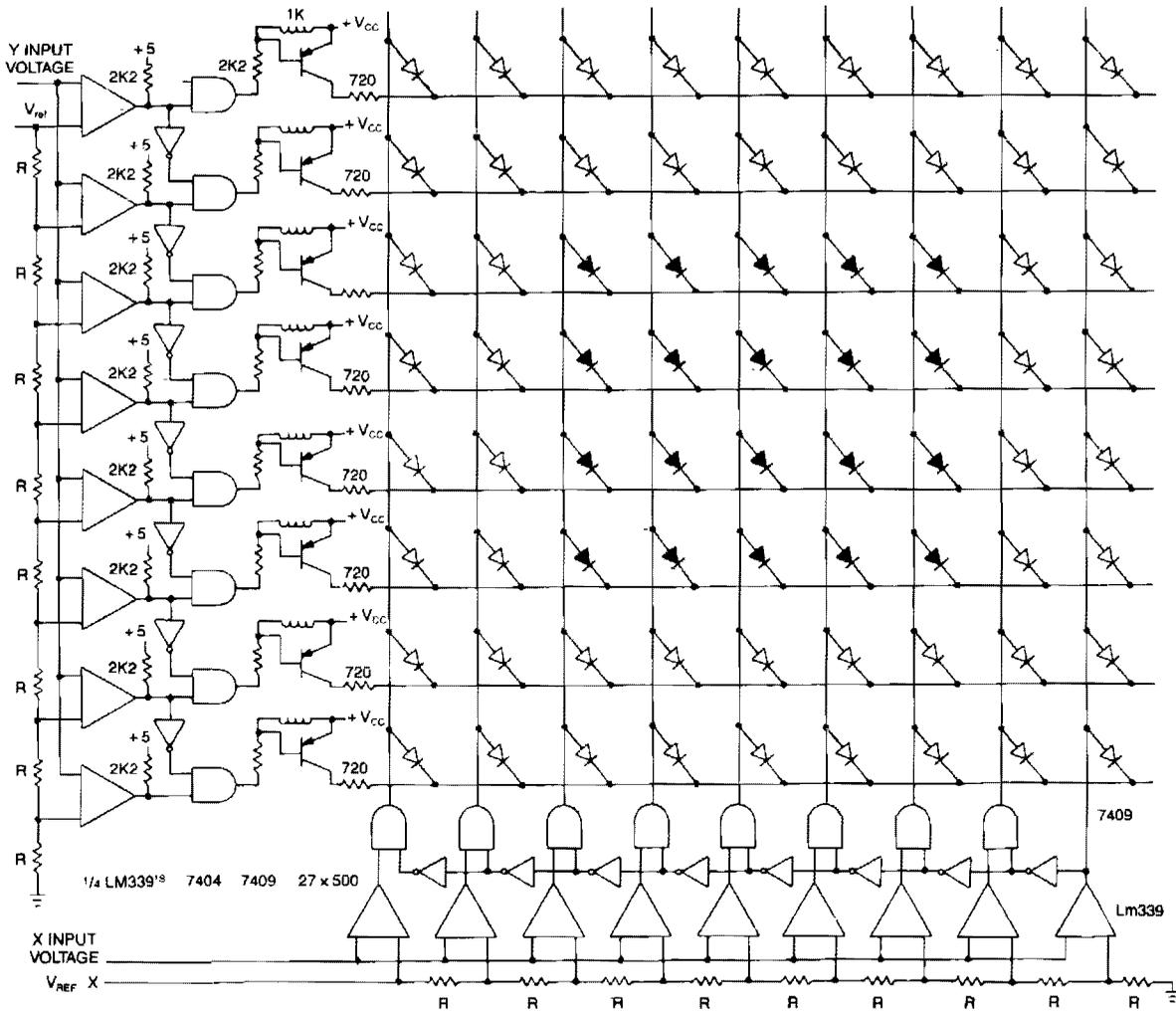

This matrix can show the values of two variables, for example, frequency and voltage. The display is a graph made from a matrix of LEDs. The LEDs on each axis are color coded, red for *out of tolerance* and green for *in*, forming a red band around the inner green rectangle. The two input voltages proportional to the functions being measured are presented to the two columns of comparators. The other comparator input is a reference voltage derived from resistor ladder R<sub>1</sub> to R<sub>x</sub>. The output of each row of comparators is processed with an inverted and an AND gate to allow only one active output for any input value. The LED at the intersection of the active drives shows the relationship of the two inputs. The advantage of this display is the ease in reading, modification, and also its small size. All comparators are LM339 quads.

# 28

## Drive Circuits


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Practical Current-Limiting Coil Driver  
Line-Synchronized Driver  
Low-Power RS-232C Driver  
Totem-Pole Driver with Bootstrapping

## PRACTICAL CURRENT-LIMITING COIL DRIVER

R - SEE TEXT

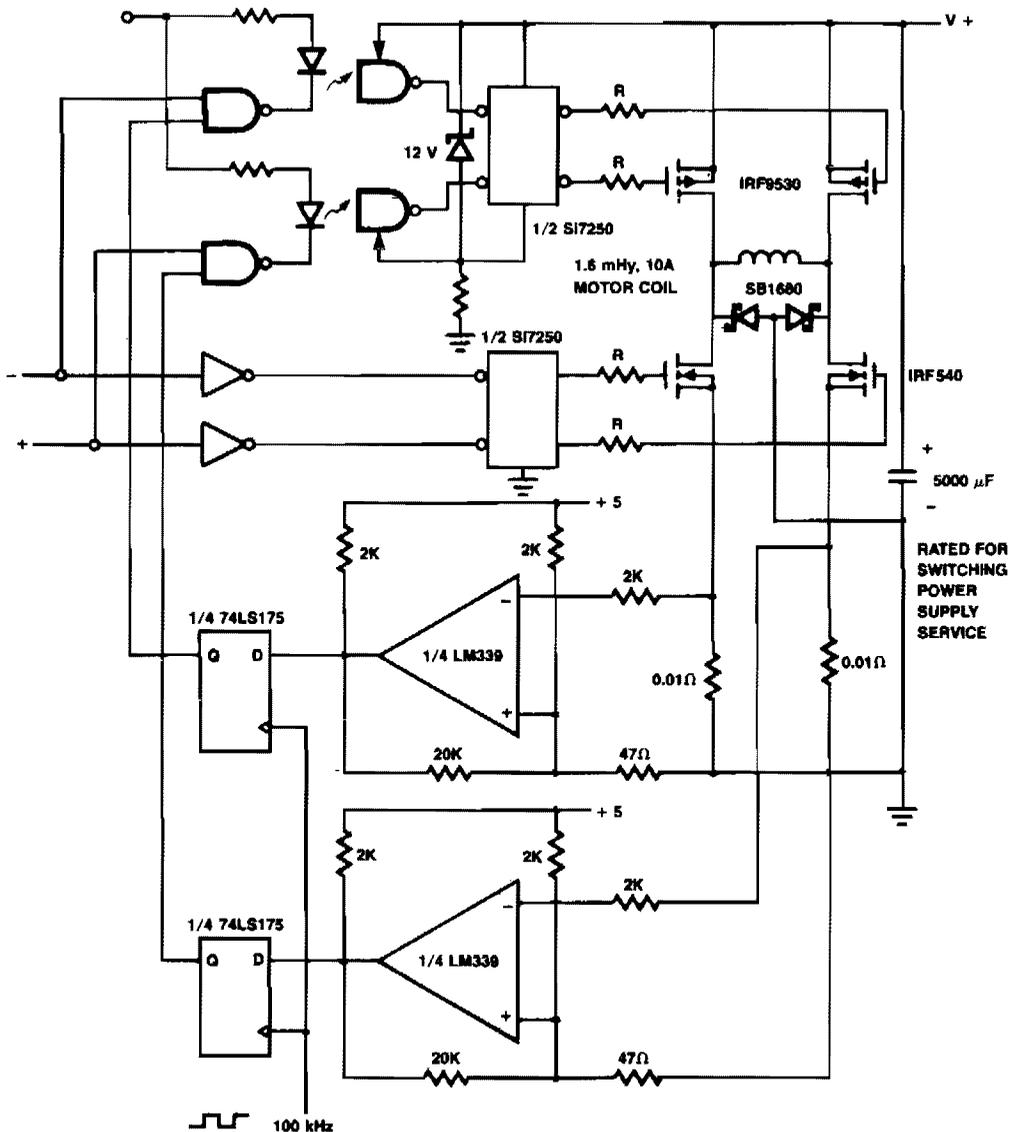


SILICONIX

Fig. 28-1

The p-channel devices are switched off by current sensors when the coil current reaches 10 A. The operation is similar to that of a switching-type power supply. The Schottky diodes and resistors are for spike protection.

### LINE-SYNCHRONIZED DRIVER

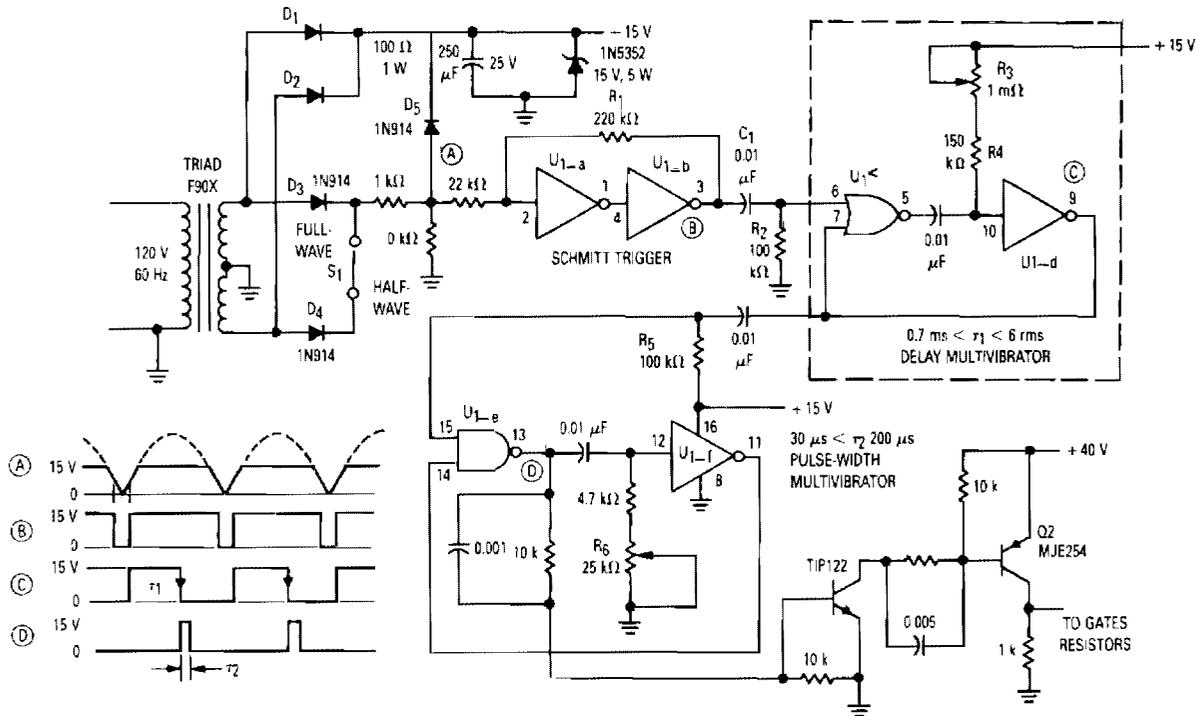

Copyright of Motorola, Inc. Used by permission.

Fig. 28-2

The gate drive that phase controls the four parallel SCRs is accomplished with complementary MOS hex gate MC14572 and two bipolar transistors. This adjustable line-synchronized driver permits SCR conduction from near zero to 180 degrees. A Schmitt trigger clocks a delay monostable multivibrator that is followed by a pulse-width monostable multivibrator. Line synchronization is achieved through the half-wave section of the secondary winding of the full-wave, center-tapped transformer. This winding also supplies power to the circuit through rectifiers D1 and D2.



# 29

## Fiber Optics Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Fiber Optic Transmitter  
Digital Fiber Optic Receiver  
50-Mb/s Fiber Optic LED Driver  
Fiber Optic Link  
Low-Cost 100-M Baud Fiber Optic Receiver  
50-Mb/s Fiber Optic Receiver

## FIBER OPTIC TRANSMITTER

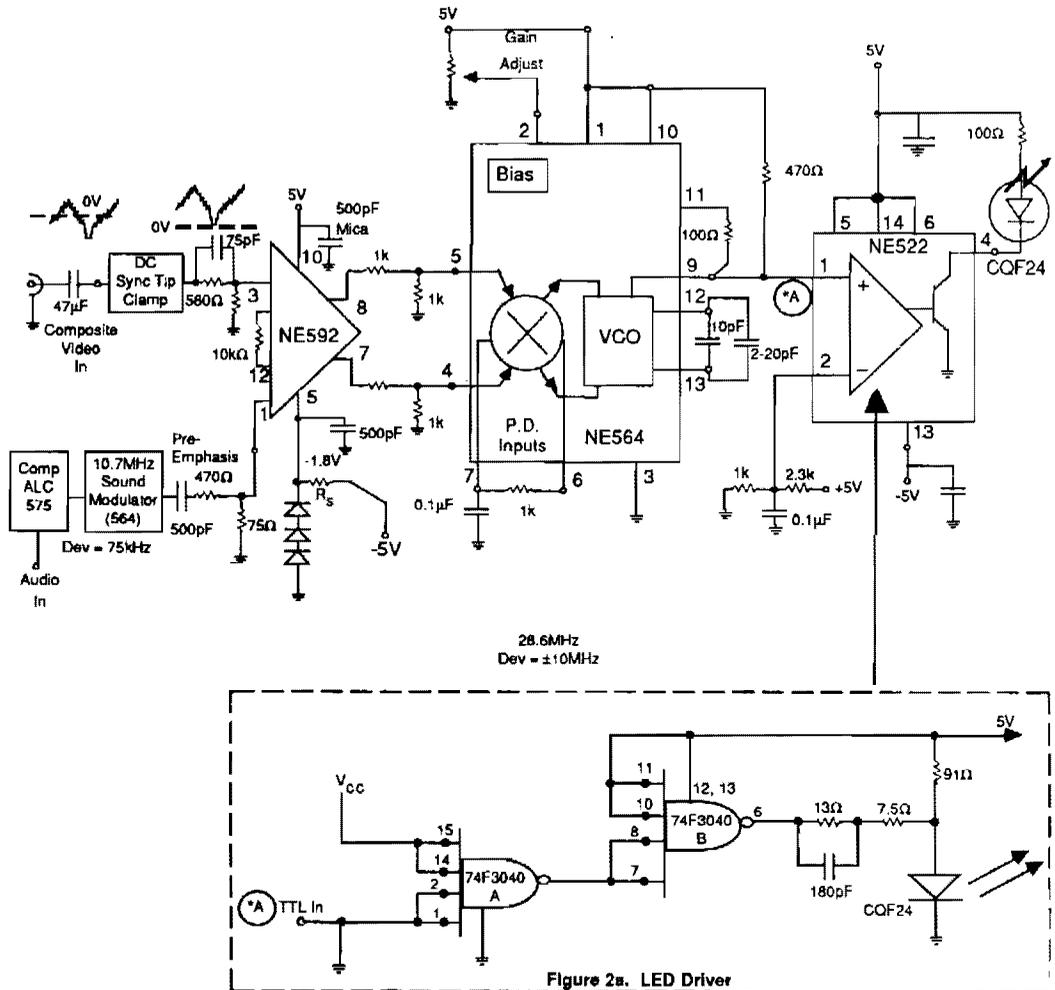


Figure 2s. LED Driver


\* Note: An alternate LED driver which uses the 74F3040 line driver was incorporated in this particular application example. The 74F3040 has a higher current rating, but not the variable threshold capabilities of the NE522. The LED diode is operated in the saturated on-off mode for best signal to noise.

SIGNETICS

Fig. 29-1

This receiver circuit consists of wideband differential amplifier NE592, VCO NE564 and LED driver NE522—the high-speed comparator. The video signal is ac coupled into the modulator preamplifier and followed by a sync tip clamp to provide dc restoration on the composite video signal and to prevent variation of modulation deviation with varying picture content. A video signal level of 250 to 300 mV peak is required to maintain optimum picture modulation. Frequency compensation (preemphasis) is inserted in the form of a passive rc lead network at the input to the NE592 differential amplifier. The main FM modulator consists of an NE564 used only as a linear wideband VCO, but the other sections of the device are not used. Differential dc coupling to the VCO terminals is attained via the loop filter terminals, pins 4 and 5.

## DIGITAL FIBER OPTIC RECEIVER

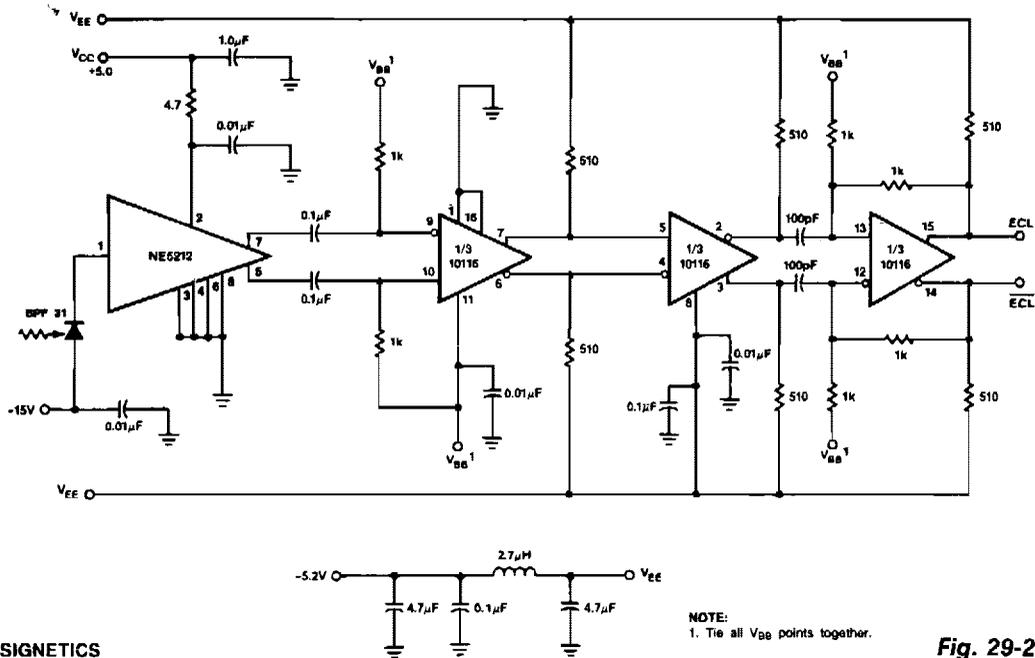


SIGNETICS

**Fig. 29-2**

This receiver uses the NE5212, the Signetics 10116 ECL line receiver, and the Phillips/Ampere BPF31 pin diode. The circuit is a capacitor-coupled receiver and utilizes positive feedback in the last stage to provide the hysteresis. The amount of hysteresis can be tailored to the individual application by changing the values of the feedback resistors to maintain the desired balance between noise immunity and sensitivity. At room temperature, the circuit operates at 50-M baud with a BER of 10E-10 and over the automotive temperature range at 40-M baud with a BER of 10E-9. Higher speed experimental diodes have been used to operate this circuit at 220-M baud with a BER of 10E-10.

## 50-Mb/s FIBER OPTIC LED DRIVER

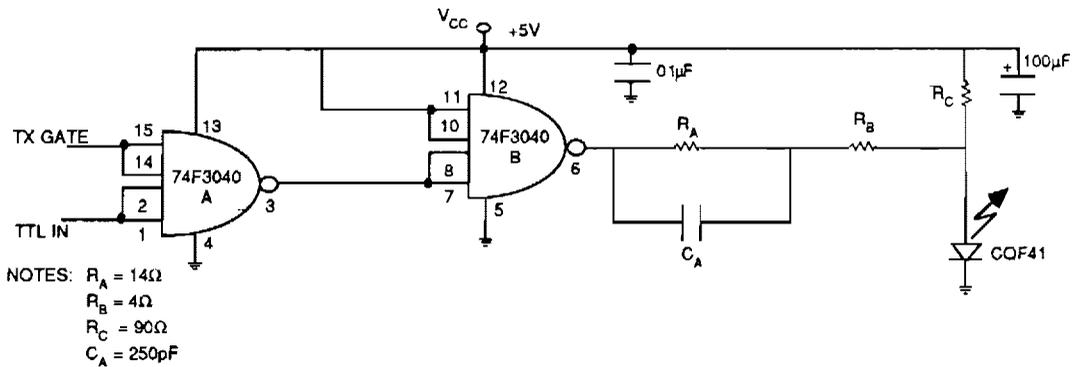


SIGNETICS

**Fig. 29-3**

## 50-Mb/s FIBER OPTIC LED DRIVER (Cont.)

The pull-up transistor of the totem-pole output is used to turn on the LED and the pull-down transistor is used to turn off the LED. The lower impedance and higher current handling capability of the saturated pull-down transistor is used as an effective method of transferring the charge from the LED's anode to ground as its dynamic resistance increases during turn-off. The slightly higher output impedance of the pull-up stage ensures that the LED is not over peaked during the less difficult turn-on transition. This asymmetric current handling capability of the output stage with its variable impedance substantially reduces the pulse-width distortion and long-tailed response. As the signal propagates through two NAND gates, each transition passes through the high-to-low and low-to-high transition once, normalizing the total propagation delay through the circuit.

### FIBER OPTIC LINK

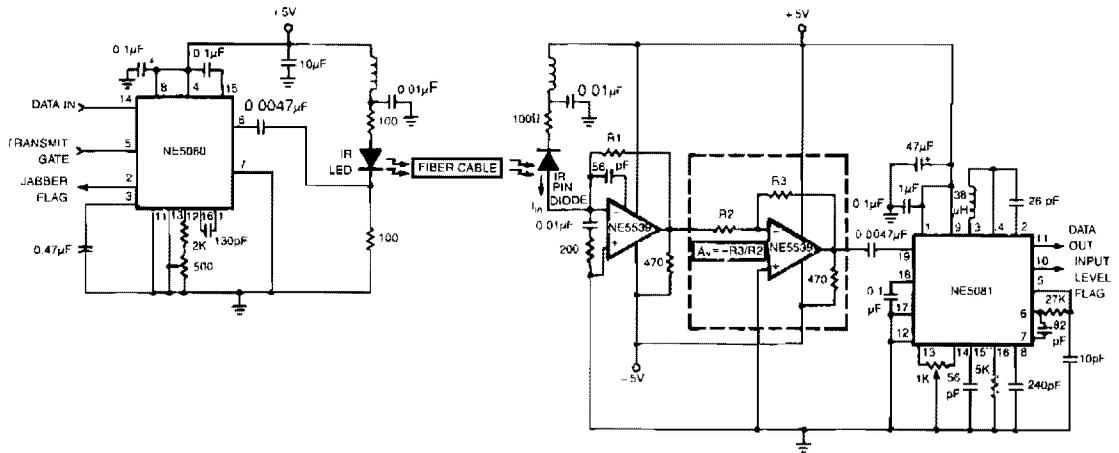


SIGNETICS

Fig. 29-4

The circuit shows a simplex fiber link between the NE5080 transmitter and the NE5081 receiver. The components shown are for a center frequency of 5 MHz, although this frequency can be increased to 20 MHz with proper selection of external component values. The NE5539 has a 530-MHz unity gain bandwidth which could limit maximum operating frequencies in some systems. Since the NE5081 can adequately accept signals below 10 mV at 5-MHz carrier, the gain stage within the dashed lines can be eliminated if the attenuation in the link is low. If the gain stage is used, be mindful of the bandwidth trade-off at higher gains. Refer to the NE5539 data sheet for details.
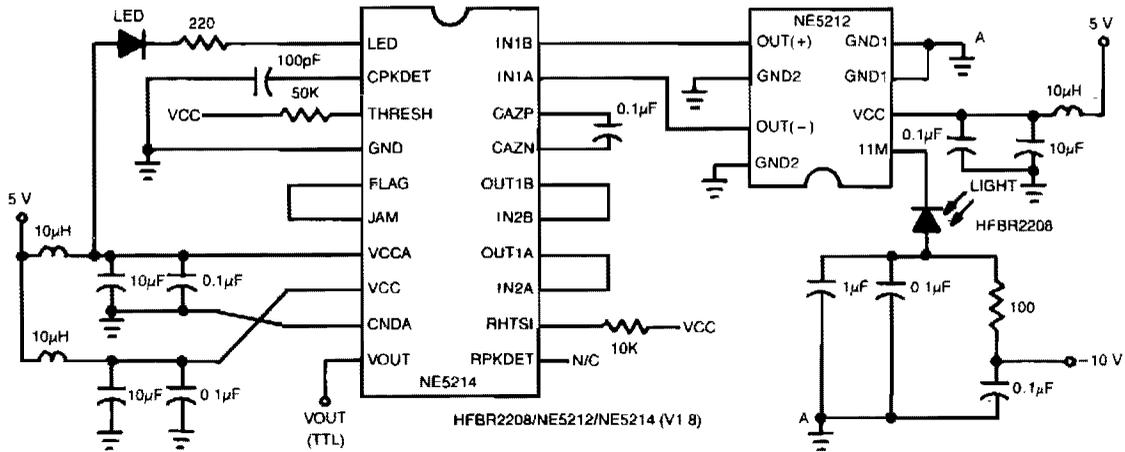
## LOW-COST 100-M BAUD FIBER OPTIC RECEIVER




SIGNETICS

Fig. 29-5

This two-chip receiver with minimum external component count has been designed for low-cost fiber optic applications to 100-M baud (50 MHz). The receiver is divided into pre- and postamplifier ICs for increased stability. The preamplifier IC features low noise with a differential transresistance design. The postamplifier IC incorporates an auto-zeroed first stage with noise shaping, high-gain symmetrical-limiting amplifier, and a matched rise/fall time TTL output buffer. A wide-band full-wave rectifier functions as a link-status indicator. To ensure stability, a surface mount, small outline (SO), package is used. The received signal in the  $-35$  dBm optical (average) to  $-9$  dBm range is converted into a small unipolar current by the pin diode. The pin diode then feeds its signal current to a preamplifier, such as the NE5212. The preamplifier output is fed to a high-gain limiting amplifier, simply known as the post amp.

The NE5214/NE5217 postamplifiers are low-cost ICs that provide up to 60 dB of gain at 50 MHz to bring mV level signals up to TTL levels. The postamplifier IC incorporates an auto-zeroed first stage with noise shaping, a high-gain symmetrical-limiting amplifier, and a matched rise/fall time TTL output buffer. A secondary amplifier chain functions as a link-status indicator.

## 50-Mb/s FIBER OPTIC RECEIVER

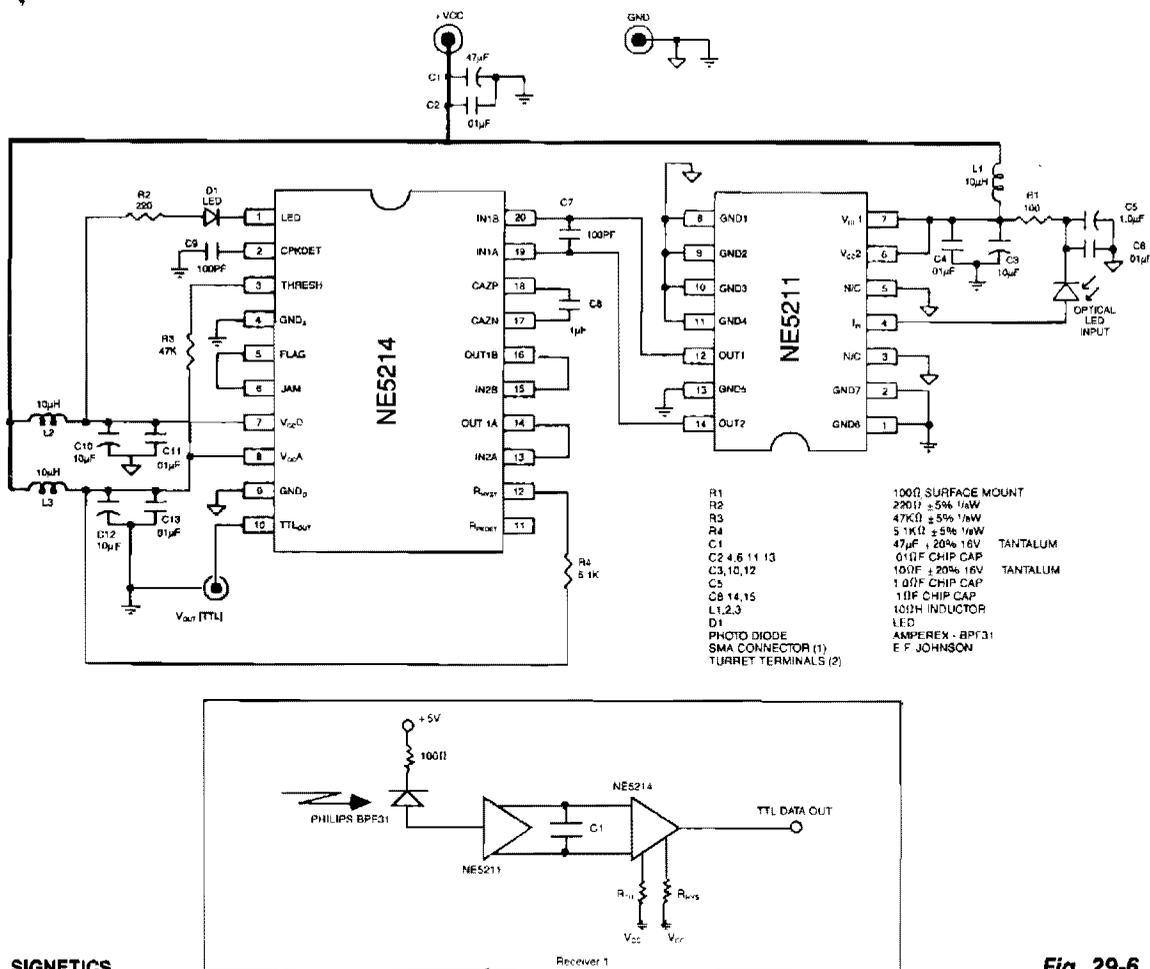

SIGNETICS

Fig. 29-6

The optical signal is coupled to the pin diode. Current flowing in the diode also flows into the input of the NE5211 preamplifier. The preamplifier is a fixed-gain block that has a 28-KΩ differential transimpedance and does a single-ended to differential conversion. With the signal in differential form, greater noise immunity is assured. The second stage, or postamplifier NE5214, includes a gain block, auto-zero detection, and limiting. The auto-zero circuit allows dc coupling of the preamplifier and the postamplifier and cancels the signal dependent offset because of the optical-to-electrical conversion. The auto-zero capacitor must be 1000 pF or greater for proper operation. The peak detector has an external threshold adjustment,  $R_{TH}$ , allowing the system designer to tailor the threshold to the individual's need. Hysteresis included to minimize jitter introduced by the peak detector, and an external resistor,  $R_{HYS}$ , is used to set the amount of hysteresis desired. The output stage provides a single-ended TTL data signal with matched rise and fall times to minimize duty-cycle distortion.

# 30


## Field-Strength Meters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Sensitive Field-Strength Meter  
Field-Strength Meter


## SENSITIVE FIELD-STRENGTH METER

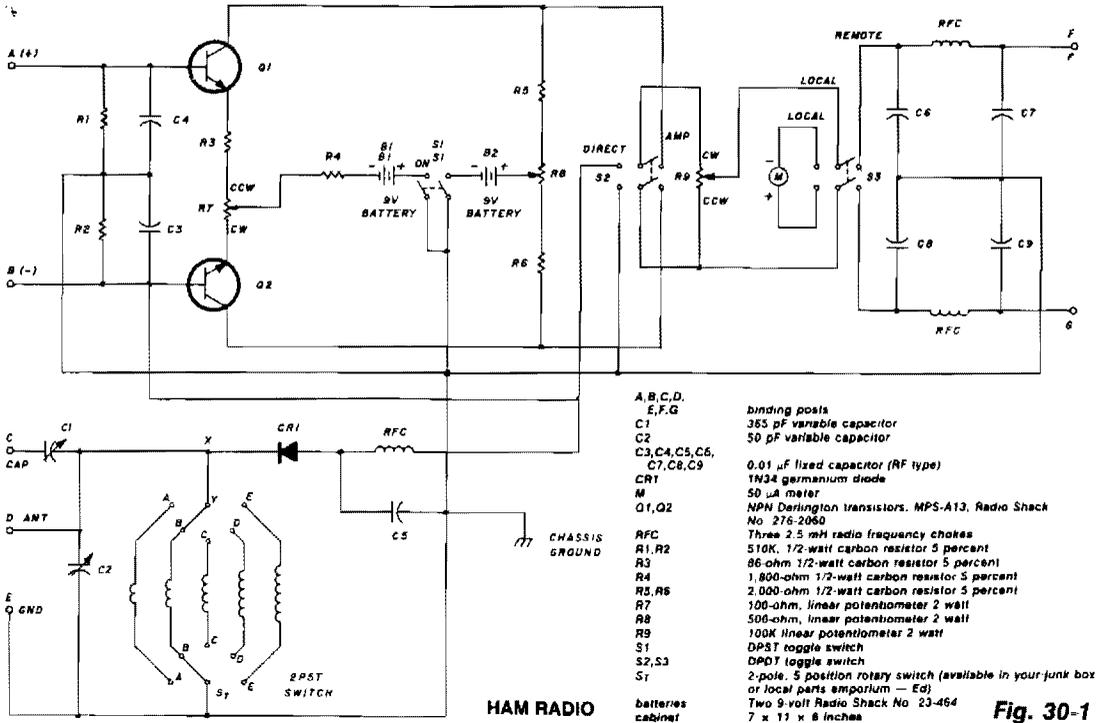

**Fig. 30-1**

The two-pole, five-position switch, coils and 365-pF variable capacitor cover a range from 1.5 to 30 MHz. The amplifier uses Darlington npn transistors whose high beta, 5000, provides high sensitivity with S1 used as the amplifier on/off switch. Switch S2 in the left position allows the output of the 1N34 diode to be fed directly into the 50-μA meter (M) for direct reading. When S2 is in the right position, the amplifier is switched into the circuit. Switch S3 is for local or remote monitoring. At full gain setting, the input signal is adjusted to give a full-scale reading of 50 mA on the meter. Then with the amplifier switched out of the circuit, the meter reading drops down to about 0.5 mA. A 2.5-mH rf choke and capacitors C3, C4, and C5 effectively keep rf out of the amplifier circuit.

## FIELD-STRENGTH METER

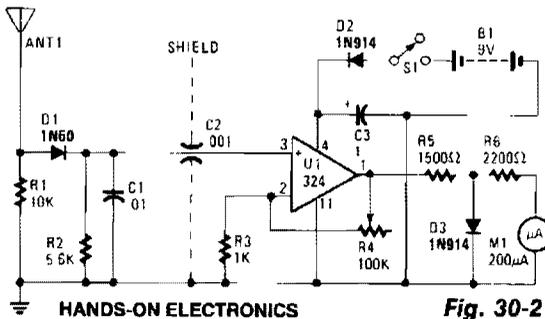

**Fig. 30-2**

The untuned, but amplified FSM can almost sense that mythical flea's whisper—from 3 through 148 MHz no less—and yet, is so immune to overload that the meter pointer won't pin. The key to the circuit is the amplifier, a 324 quad op amp, of which only one section is used. It's designed for a single-ended power supply, will provide at least 20-dB dc gain, and the output current is self-limiting. The pointer can't be pinned.

# 31

## Filter Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Programmable Active Filters  
Biquad Audio Filter  
Low-Power Active Filter with Digitally  
    Selectable Center Frequency  
Glitch-Free Turbo Circuit  
Voltage-Controlled Filter  
Second-Order Biquad Bandpass Filter  
Noisy Signal Filter  
State-Variable Active Filter

Scratch Filter  
Dynamic Noise Filter  
State-Variable Filter with Multiple  
    Filtering Outputs  
Typical Active Bandpass Filter  
Sixth-Order Elliptic High-Pass Filter  
Fourth-Order Chebyshev High-Pass Filter  
Fourth-Order Chebyshev Bandpass Filter  
Rumble Filter

## PROGRAMMABLE ACTIVE FILTERS


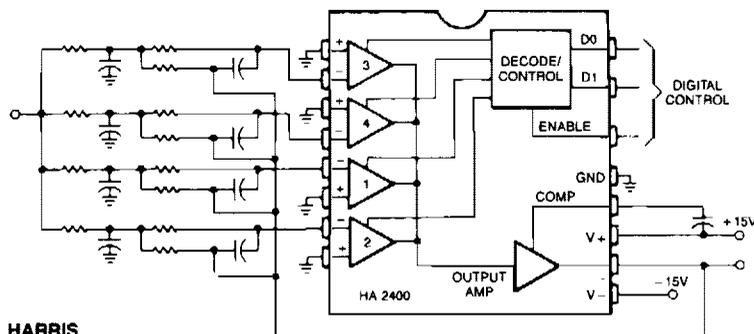


Fig. 31-1

This is a second-order, low-pass filter with programmable cutoff frequency. This circuit should be driven from a low-source impedance since there are paths from the output to the input through the unselected networks. Virtually any filter function which can be constructed with a conventional op amp can be made programmable with the HA-2400.

A useful variation would be to wire one channel as a unity gain amplifier, so that one could select the unfiltered signal, or the same signal filtered in various manners. These could be cascaded to provide a wide variety of programmable filter functions.

## BIQUAD AUDIO FILTER

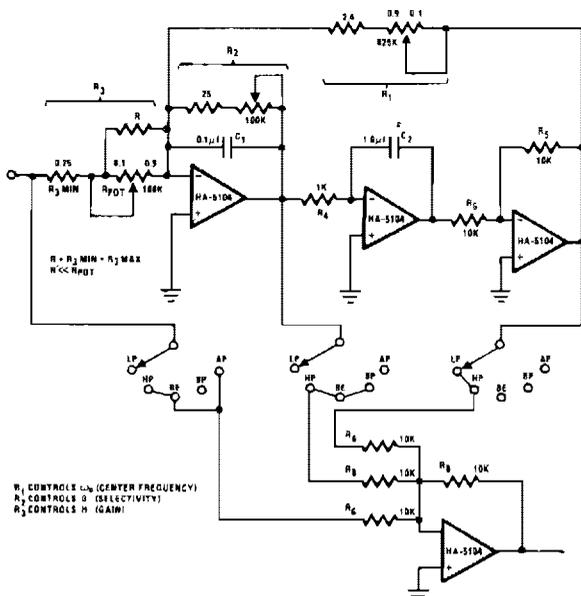

$R_1$  CONTROLS  $\omega_0$  (CENTER FREQUENCY)  
 $R_2$  CONTROLS  $Q$  (SELECTIVITY)  
 $R_3$  CONTROLS  $H$  (GAIN)

The biquad offers a universal filter with  $\omega_0$ ,  $Q$  and gain 'orthogonally' tuned


This universal filter offers low-pass, high-pass, bandpass, band elimination, and all-pass functions. The Biquad consists of two successive integration stages followed by an inverting stage. The entire group has a feedback loop from the front to the back consisting of  $R_1$  which is chiefly responsible for controlling the center frequency,  $\omega_0$ . The first stage of integration is a *poor* integrator because  $R_2$  limits the range of integration.  $R_2$  and  $C$  form the time constant of the first stage integrator with  $R_3$  influencing gain  $H$  almost directly. The band-pass function is taken after the first stage with the low-pass function taken after the third stage. The remaining filter operations are generated by various combinations of three stages.

The Biquad is orthogonally tuned, meaning that  $\omega_0$ ,  $Q$ , and gain  $H$  can all be independently adjusted. The component values known will allow  $\omega_0$  to range from 40 Hz to 20 kHz. The other component values give an adequate range of operation to allow for virtually universal filtering in the audio region.  $\omega_0$ ,  $Q$ , and gain  $H$  can all be independently adjusted by tuning  $R_1$  through  $R_3$  in succession.

HARRIS

Fig. 31-2

## LOW-POWER ACTIVE FILTER WITH DIGITALLY SELECTABLE CENTER FREQUENCY

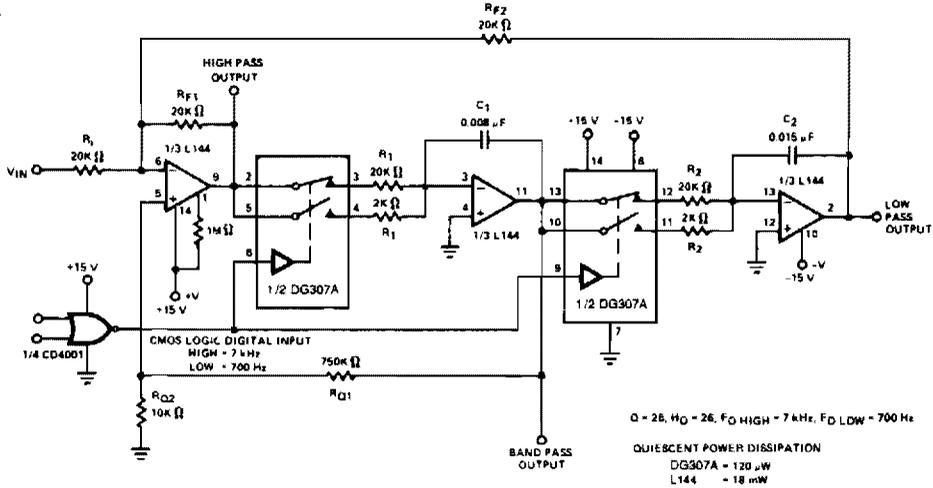

**Table 1**

**Design Procedure for the State Variable Active Filter**  
 Given:  $f_0$  (Resonant Frequency),  
 $H_0$  (Gain at the Resonant Frequency) and  $Q_0$

**STANDARD DESIGN**  
 (Assumes Infinite Op-Amp Gain)

1. CHOOSE  $C_1 = C_2 = C$ , A CONVENIENT VALUE
2. LET  $R_1 = R_2 = R$
3. THEN  $R = \frac{1}{2\pi \times f_0 \times C}$
4. CHOOSE  $R_{11} = R_{12} = KR$ ,  
 WHERE  $R_{11}, R_{12} =$  A CONVENIENT VALUE

$$\text{AND } K = \frac{H_0}{Q_0}$$

IF  $H_0$  IS UNIMPORTANT (i.e., GAIN CAN BE ADDED BEFORE AND/OR AFTER THE FILTER), CHOOSE  $K = 1$

5. LET  $R_{Q1} =$  A CONVENIENT VALUE

6. THEN  $R_{Q2} = \frac{R_{Q1}}{(2 + K) \times Q_0 - 1}$

A ( $f_0$ ) = THE NOMINAL OP AMP GAIN AT THE RESONANT FREQUENCY.


GBWP = THE NOMINAL GAIN-BANDWIDTH PRODUCT OF THE OPERATIONAL AMPLIFIER

SILICONIX

**Fig. 31-3**

The switchable center frequency active filter allows a decade change in center frequency.

## GLITCH-FREE TURBO CIRCUIT

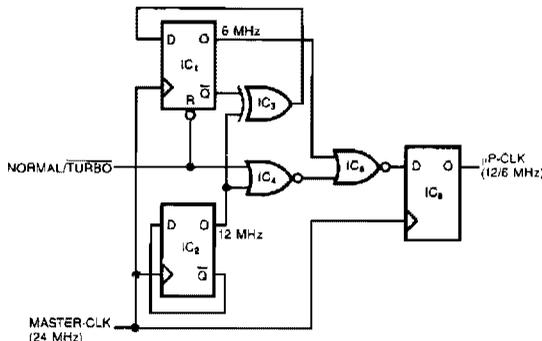

**Fig. 31-4**

This simple circuit generates a dual-speed clock for personal computers. The circuit synchronizes your asynchronous switch inputs with the master clock to provide glitch-free transitions from one clock speed to the other. The dual-speed clock allows some programs to run at the higher clock speed in order to execute more quickly. Other programs—for example, programs that use loops for timing—can still run at the lower speed as necessary. The circuit will work with any master-clock

EDN


## GLITCH-FREE TURBO CIRCUIT (Cont.)

frequency that meets the flip-flops' minimum-pulse-width specs.

The two D two flip-flops, IC1 and IC2, and an XOR gate, IC3, form a binary divider that develops the 6- and 12-MHz clocks. When the NT signal is low, the reset pin forces the 6-MHz output low. On the other hand, when the NT signal is high, IC3

blocks the 12-MHz output. Therefore, only one of the two clock signals passes through IC3 and gets clocked into IC6. Because the master-clk signal clocks IC6, asynchronous switching of the NT signal can't generate an output pulse shorter than 41  $\mu$ s ( $1/24$  MHz). Also, the synchronization eliminates glitches.

## VOLTAGE-CONTROLLED FILTER

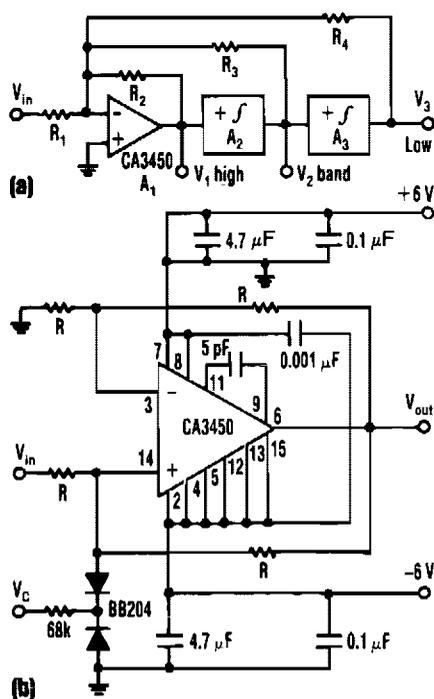

ELECTRONIC DESIGN

Fig. 31-5

The control voltage  $V_C$  easily sets the cutoff frequency  $\omega_o$  of this state-variable filter to any desired value, from about 1.7 MHz up to 5 MHz, with a BB 204 varicap and  $R = 100$  K $\Omega$ .  $V_C$  can range from 0 to 28 V. This range changes the capacitance of the varicap from about 4 to 12 pF.


The circuit consists of input summing circuit A1 and two noninverting integrators, A2 and A3. Both the integrators and the summing-amplifier circuits use CA3450 op amps. With them, cutoff frequencies up to 200 MHz are possible.

The circuit's cutoff frequency, its  $Q$ -factor, and gain  $G$  are simply:

$$\omega_o = 2/CR, \quad Q = R_3/R_4, \\ \text{and } G = R_4/R_1$$

For a given value for  $R_4$ , say 10 K $\Omega$ ,  $Q$  depends only upon the resistance of  $R_3$ . The  $Q$  can be any value, even 100, independently of both  $\omega_o$  and  $G$ . Similarly, the gain then depends only on the resistance of  $R_1$  and can also be set as high as 100.

## SECOND-ORDER BIQUAD BANDPASS FILTER

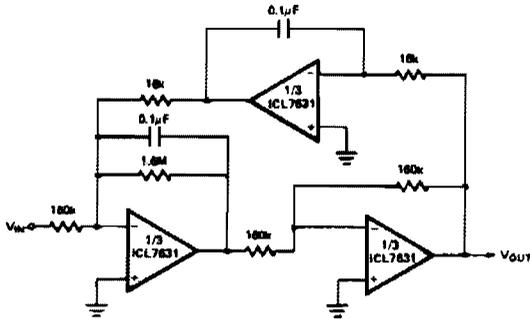


INTERSIL

Fig. 31-6

Note that  $I_Q$  on each amplifier might be different.  $A_{VCL} = 10$ ,  $Q = 100$ ,  $f_o = 100$  Hz.

## NOISY SIGNALS FILTER

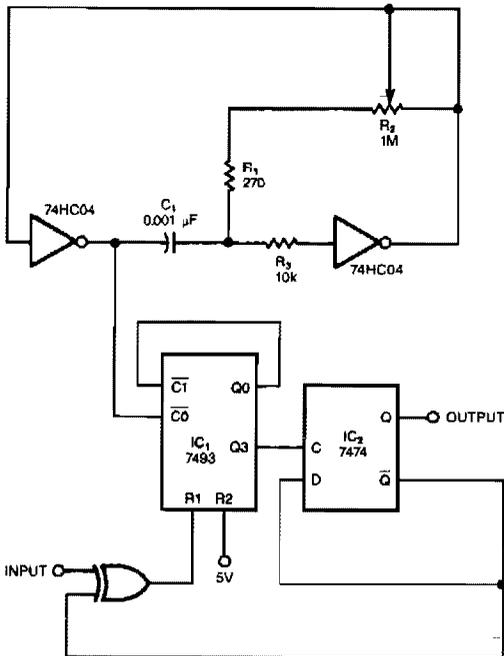


EDN

Fig. 31-7

This circuit filters noise, such as glitches and contact bounce, from digital signals. You can easily adjust the circuit for a wide range of noise frequencies. The circuit's output changes state only if the input differs from the output long enough for the counter to count eight cycles. If the input changes before the counter reaches its maximum count, the counter resets without clocking the output of flip-flop, IC2. You use R2 to set the frequency of the two-inverter CMOS oscillator, which clocks the counter. Simply adjust the oscillator such that its period is one-eighth that of the noise you want to eliminate.

## STATE-VARIABLE ACTIVE FILTER

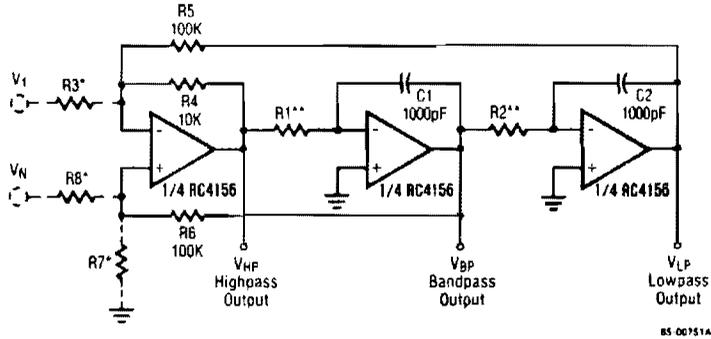

\*Input connections are chosen for inverting or non-inverting response. Values of R3, R7, R8 determine gain and Q.

\*\*Values of R1 and R2 determine natural frequency.


Reprinted with permission from Raytheon Co., Semiconductor Div.

**Fig. 31-8**

A generalized circuit diagram of the two-pole state-variable active filter is shown. The state-variable filter can be inverting or noninverting and can simultaneously provide three outputs: low-pass, bandpass, and high-pass. A notch filter can be realized by adding one summing op amp.

In the state-variable filter circuit, one amplifier performs a summing function and the other two act as integrators. The choice of passive component values is arbitrary, but must be consistent with the amplifier operating range and input signal characteristics. The values shown for C1, C2, R4, R5, and R6 are arbitrary. Preselecting their values will simplify the filter tuning procedures, but other values can be used if necessary.


## SCRATCH FILTER

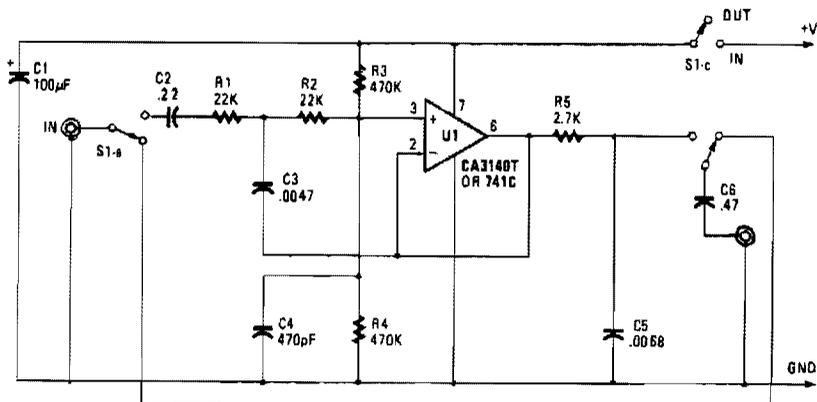

POPULAR ELECTRONICS

**Fig. 31-9**


## DYNAMIC NOISE FILTER

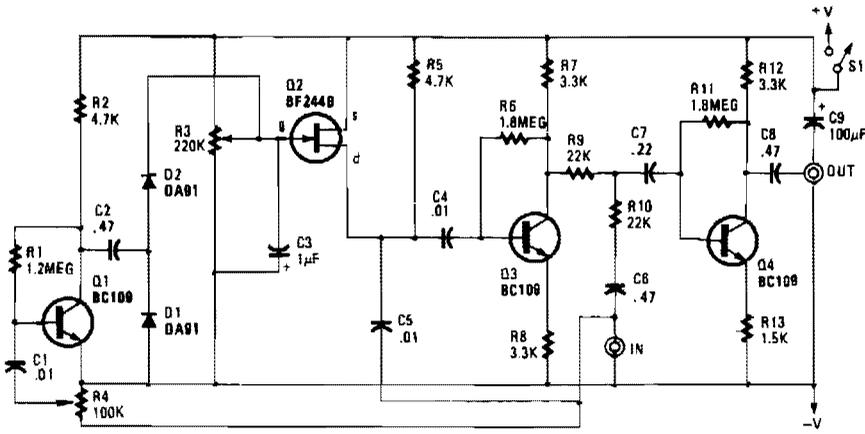

POPULAR ELECTRONICS

Fig. 31-10

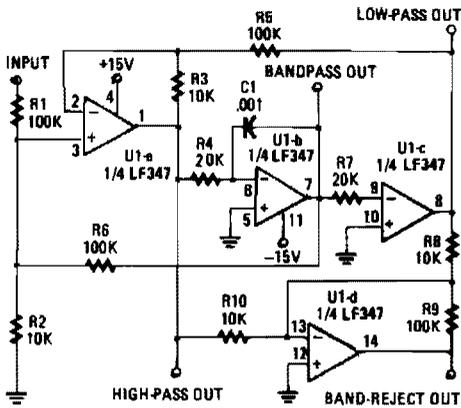
## STATE-VARIABLE FILTER WITH MULTIPLE FILTERING OUTPUTS



POPULAR ELECTRONICS

Fig. 31-11


## TYPICAL ACTIVE BANDPASS FILTER

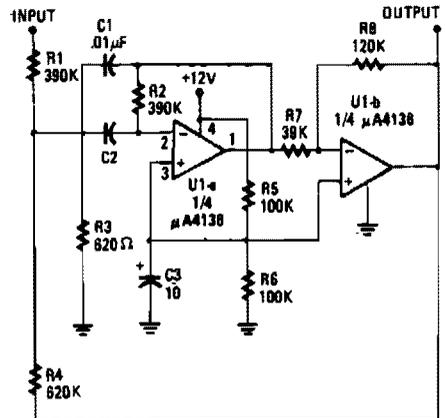

POPULAR ELECTRONICS

Fig. 31-12

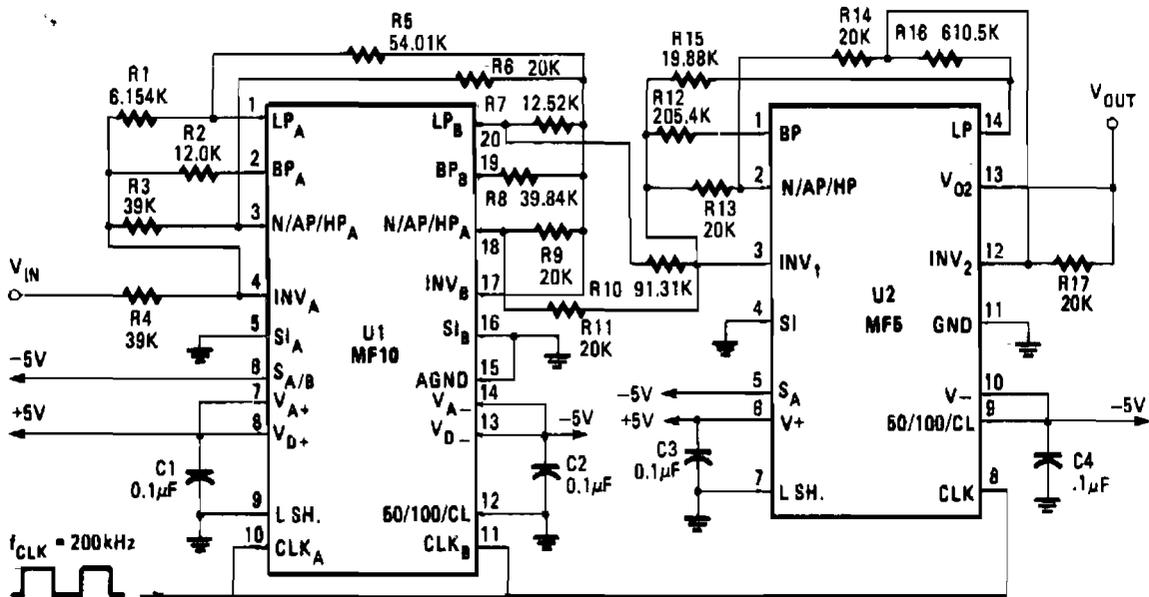
### SIXTH-ORDER ELLIPTIC HIGH-PASS FILTER



POPULAR ELECTRONICS

Fig. 31-13

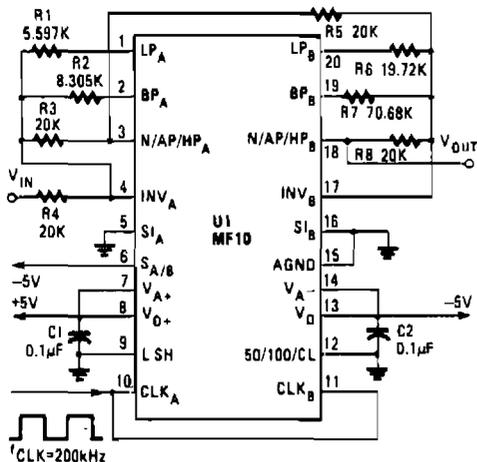
### FOURTH-ORDER CHEBYSHEV HIGH-PASS FILTER



POPULAR ELECTRONICS

Fig. 31-14

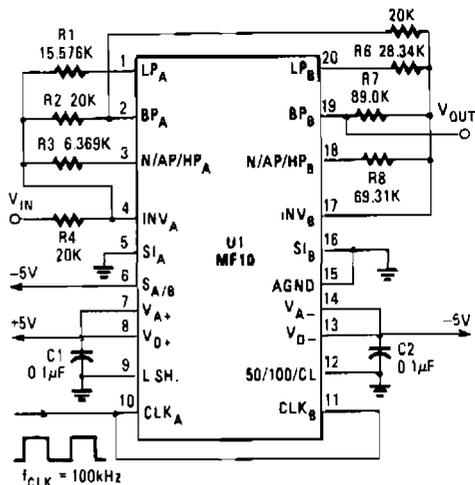
### FOURTH-ORDER CHEBYSHEV BANDPASS FILTER



POPULAR ELECTRONICS

Fig. 31-15

# RUMBLE FILTER

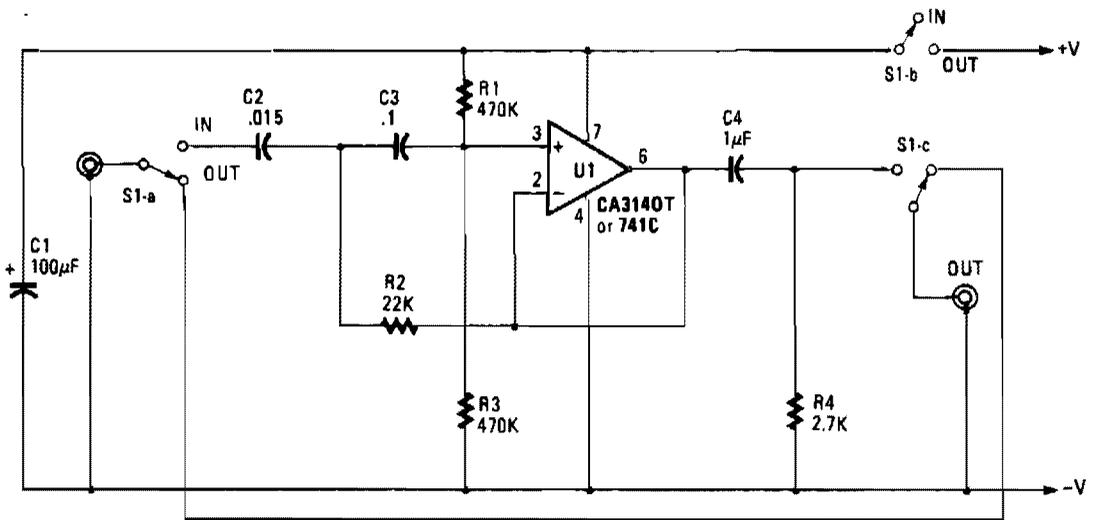

POPULAR ELECTRONICS

Fig. 31-16

# 32


## Flashers and Blinkers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Ring-Around LED Flasher	Five-Lamp Neon Flasher
Three-Year LED Flasher	Alternating LED Flasher
SCR Ring Counter	CMOS Flasher
Astable Multivibrator	60-W Flashing Light
Ac Flasher	Two-State Neon Oscillator
Single-Lamp Flasher	Alternating LED Flasher
SCR Chasher	Transistor Flasher
SCR Flasher	Minimum Component Flasher
Incandescent Light Flasher	Lamp Flasher

## RING-AROUND LED FLASHER

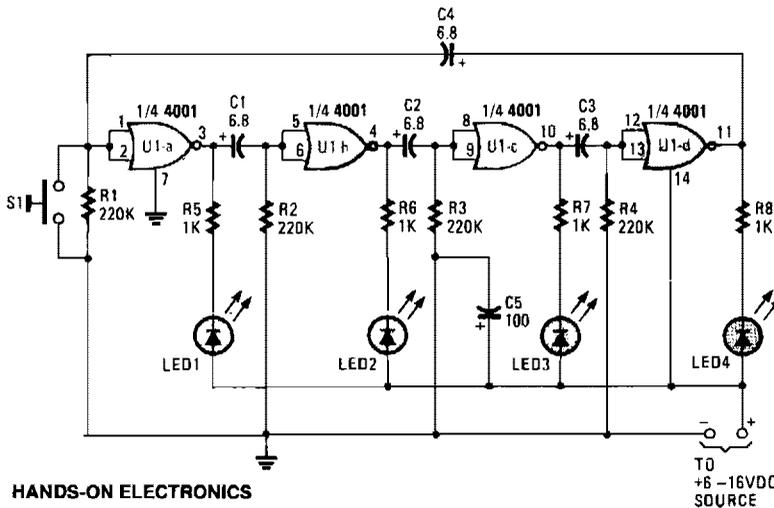

When power is first turned on, two of the LEDs are on and the other two remain off until the timing cycle reverses. The LEDs flash in pairs, but by pressing and holding S1 closed until only one of the LEDs is on, and then releasing it, the four LEDs can be made to flash in sequential order. The number of LEDs flashing in a sequential ring can be easily increased to eight by adding another 4001 quad NOR gate. Just repeat the circuit and connect the additional circuit in series with the first—input to output—as an extension of the first circuit. When power is connected to the eight-LED flasher circuit, four LEDs will turn on at once and then flash off as the four remaining LEDs come on. As before, just press S1 and hold closed until all but one LED turns off; then the LEDs will begin their sequential march in a circle. You can connect as many circuits in series as you like.


## THREE-YEAR LED FLASHER

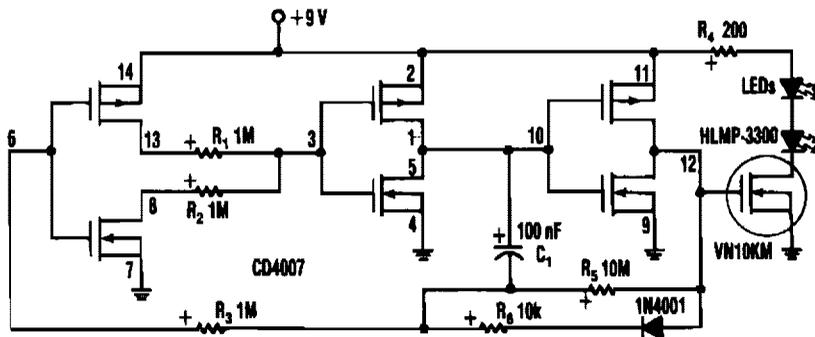

### THREE-YEAR LED FLASHER (Cont.)

Inserting two 1-M $\Omega$  resistors, R1 and R2, in the output stage of one of the circuit's inverters limits the current needed by the oscillator to no more than a few  $\mu$ A. This circuit includes a CD4007 package, which has three CMOS inverters. It forms a standard three-inverter oscillator. Resistors R1 and R2, in series with separate drains on inverter pins 8 and 13, limit the oscillator's supply current. Capacitor C1 and resistors R5 set the off time of the oscillator, C1; R6 sets the on time. A VN10KM small-power FET, current-limited by R4, drives two HLMP-3300 LEDs. The LEDs consume about 20 mA for 1 ms. Their average current determines battery life. Since the LEDs in the circuit flash at 1 Hz, the average current drain is about 1/1000 of 20 mA, or 20  $\mu$ A. A 9-V battery should last about three years at the current drain—essentially the shelf life of an alkaline battery.

### SCR RING COUNTER

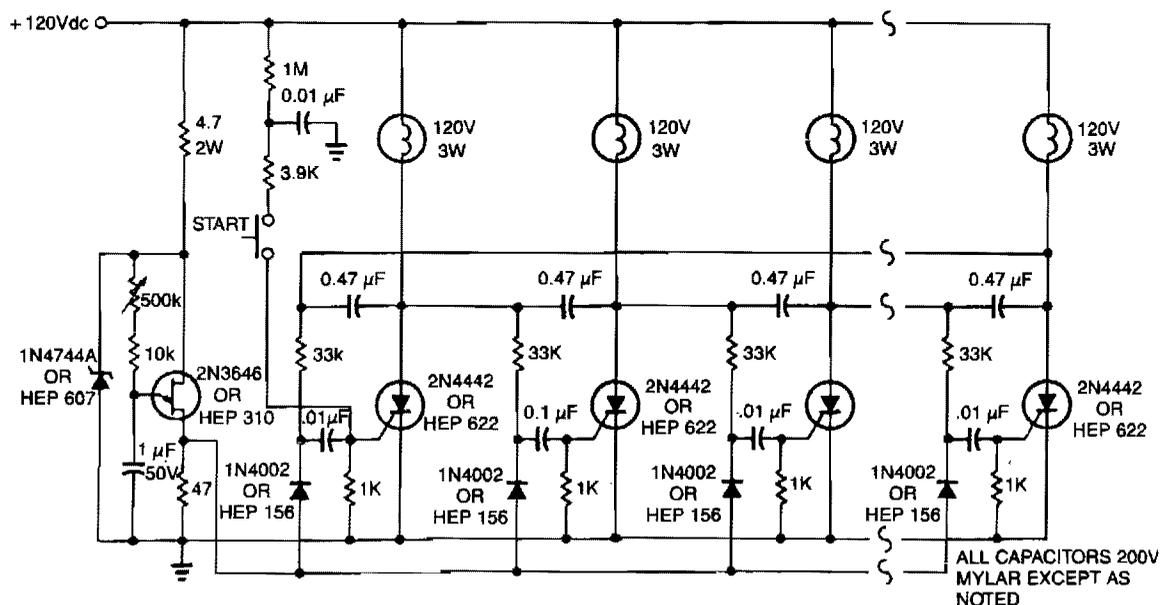


EDN

Fig. 32-3

One lamp at a time is lit in the string to give the appearance of a moving point of light.

## ASTABLE MULTIVIBRATOR

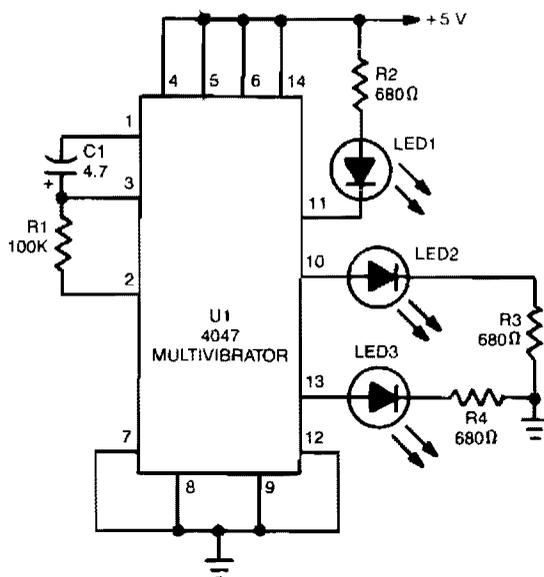


The 4047 is configured as a free-running, astable-multivibrator (oscillator) circuit. That configuration, offers three different outputs. The output pulses at the  $Q$  and  $\bar{Q}$  output (pins 10 and 11, respectively) are the same as in the previous two circuits. The third output at pin 13 pulses twice as often as the outputs at 10 and 11. So, the circuit can be used to simultaneously provide both positive- and negative-trigger signals since the  $Q$  and  $\bar{Q}$  output are never in the same state, and a clock frequency. Thus, the 4047 can replace both a simple oscillator (the 555, for instance) and a flip-flop in some applications.

POPULAR ELECTRONICS

Fig. 32-4

## AC FLASHER

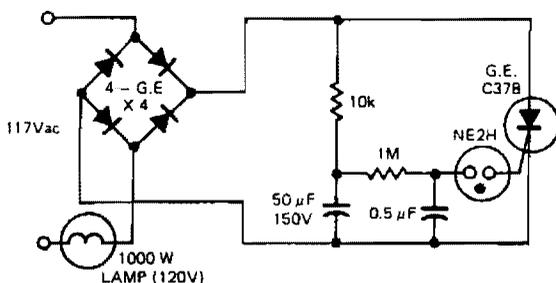


EDN

Fig. 32-5

This ac line-operated flasher uses an SCR and is capable of flashing a large lamp. Flashing rate is determined by the 10-K $\Omega$  resistor and the 50-mF capacitor. Increasing or decreasing the value of the capacitor has a corresponding effect on the flash rate.

## SINGLE-LAMP FLASHER

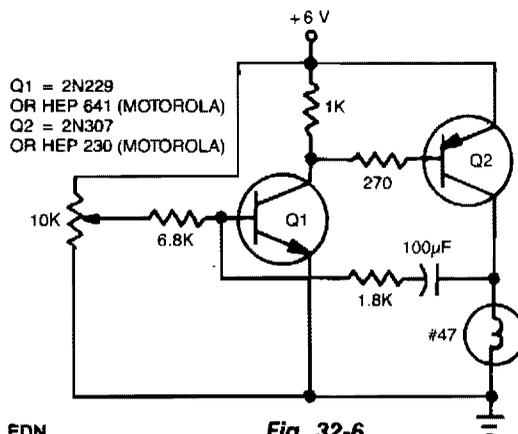


EDN

Fig. 32-6

The flash rate is controlled by a complementary multivibrator consisting of an npn and a pnp transistor.

### SCR CHASER

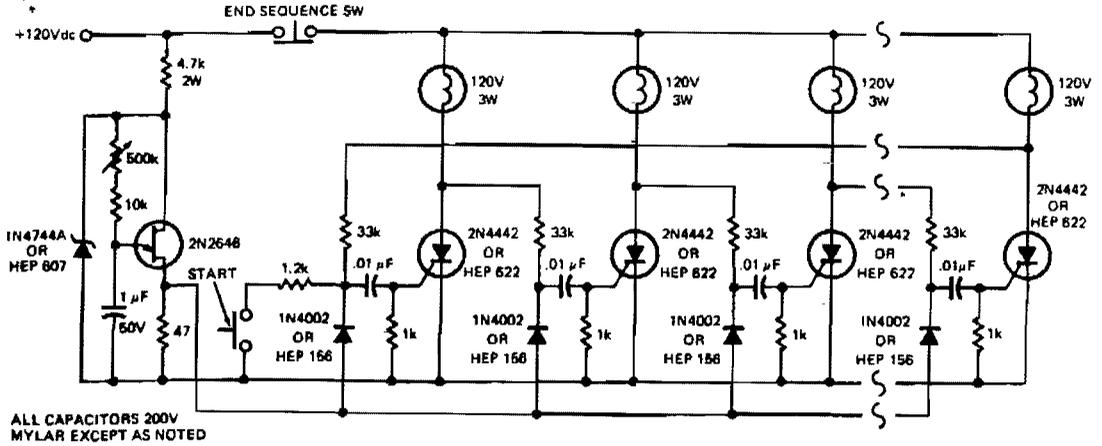


EDN

Fig. 32-7

Each lamp lights in succession to give the appearance of a growing column.

### SCR FLASHER

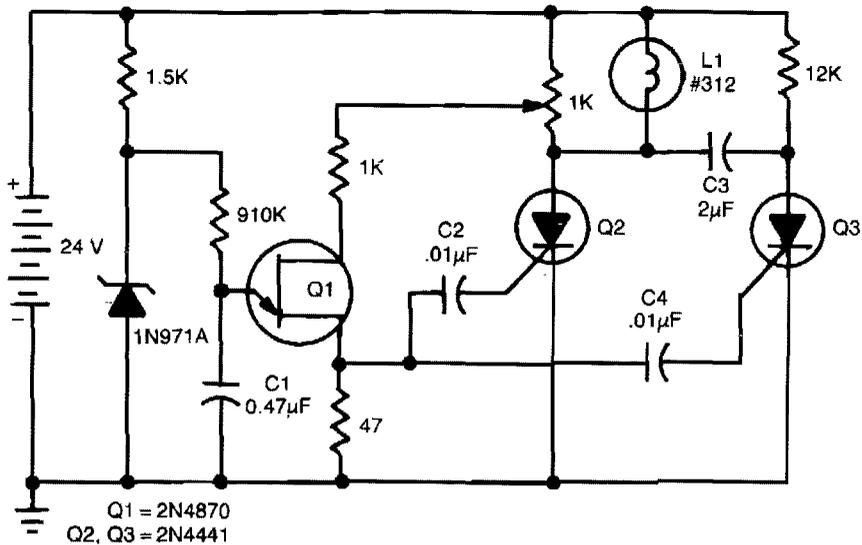

EDN

Fig. 32-8

This dc flasher uses two SCRs and a unijunction oscillator clock to set the flash rate, which can be varied by changing the value of C1.

### INCANDESCENT LIGHT FLASHER


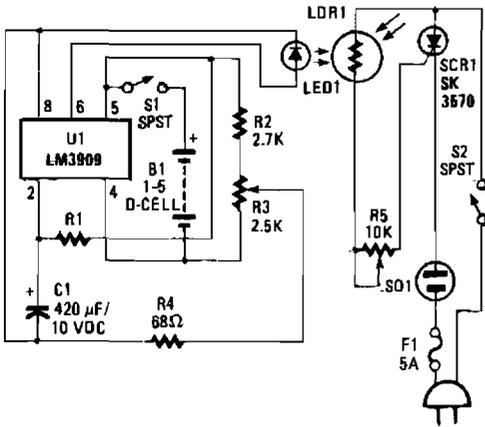


Fig. 32-9

POPULAR ELECTRONICS

### FIVE-LAMP NEON FLASHER

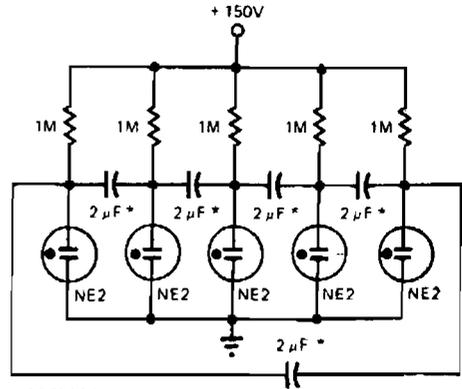

\*200V MYLAR

EDN

Fig. 32-10

In this circuit, the number of lamps can be increased almost without limit.

### ALTERNATING LED FLASHER

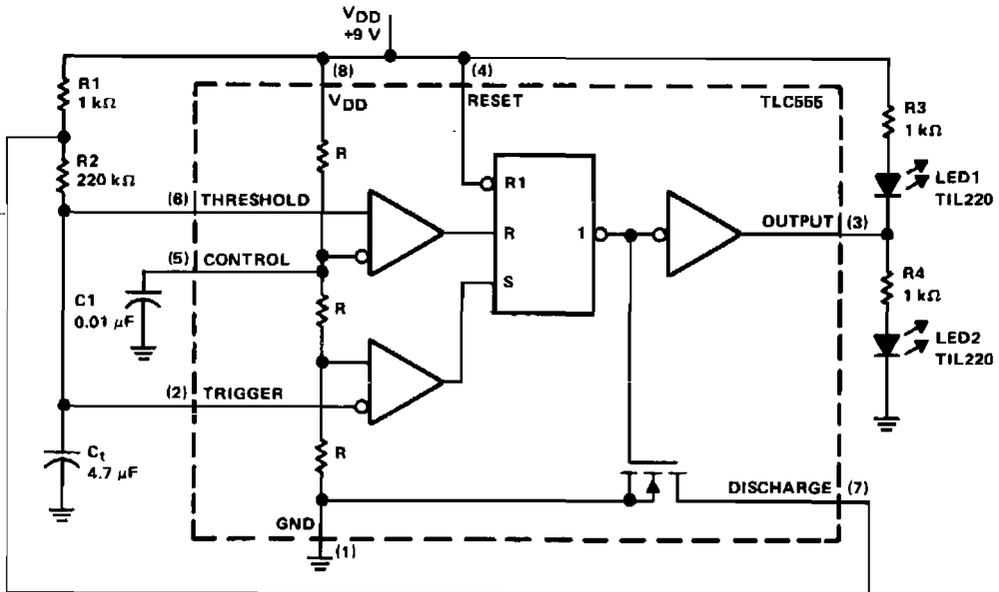


Fig. 32-11


Reprinted by permission of Texas Instruments.

## ALTERNATING LED FLASHER (Cont.)

The timing components are R1, R2, and C1. C1 is a bypass capacitor used to reduce the effects of noise. At start-up, the voltage across C1 is less than the trigger level voltage ( $1/3 V_{DD}$ ), causing the timer to be triggered via pin 2. The output of the timer at pin 3 increases, turning LED1 off, LED2 on, the discharge transistor at pin 7 off, and allowing C1 to charge through resistors R1 and R2. When capacitor C1 charges to the upper threshold voltage ( $2/3 V_{DD}$ ), the flip-flop is reset and the output at pin 3 decreases. LED1 is turned on, LED2 is turned off, and capacitor C1 discharges through resistor R2 and the discharge transistor. When the voltage at pin 2 reaches  $1/3 V_{DD}$ , the lower threshold or trigger level, the timer triggers again and the cycle is repeated.

The totem-pole output at pin 3 is a square wave with a duty cycle of about 50%. The output alternately turns on each LED at slightly less than one blink per second. If the unit is battery operated, the TLC555 uses minimum current to produce this function. With a 9-V battery, the circuit draws 5 mA (no load) and 15 mA when turning on an LED. Most of the on current is for the LED.

## CMOS FLASHER

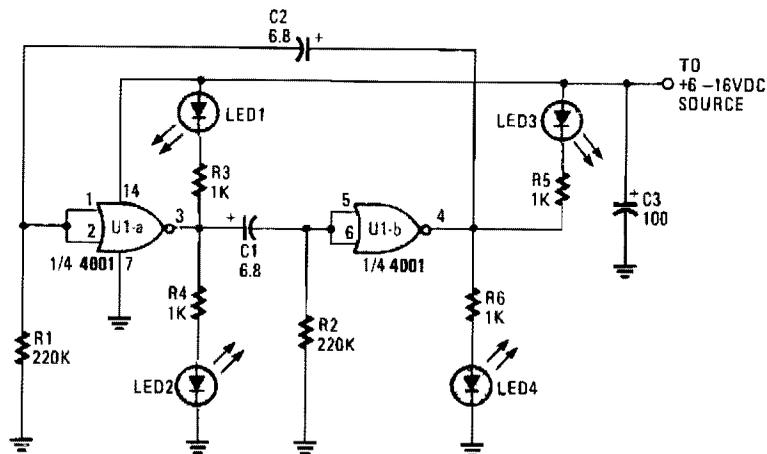


HANDS-ON ELECTRONICS

Fig. 32-12

Uses a low cost CMOS IC to turn four LEDs on and off at a rate that is set by the values of R1, R2, C1, and C2. The pulse rate for the component values given for R1 and R2 is about one cycle every four seconds. By lowering the values of R1 and R2 to 220 K $\Omega$ , the pulse rate increases to 1 Hz. The LEDs flash in pairs, with LED1 and LED4 turning together for one half of the time period, while LED2 and LED3 are on for the other half. The on/off duration of each pair of LEDs can be increased or decreased by changing the value of one of coupling capacitors C1 or C2. Increasing either capacitor's value by a factor of 10 will also increase the ON time of a pair of the LEDs for about the same factor.

### 60-W FLASHING LIGHT

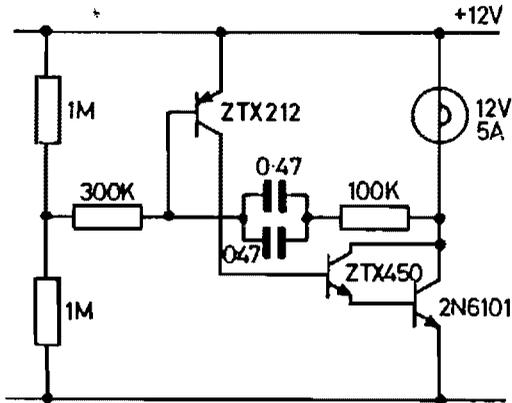


ZeTeX, formerly FERRANTI

Fig. 32-13

The 2N6101 transistor should be mounted on a small heatsink. The 300-KΩ resistor controls the off period and might need to be adjusted if transistor gains are high. The 100-KΩ resistor controls the on period.

### ALTERNATING LED FLASHER

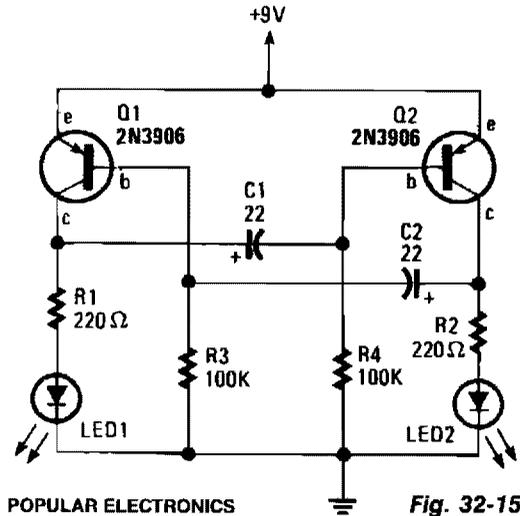


POPULAR ELECTRONICS

Fig. 32-15

The alternating LED flasher is simply a two-transistor oscillator with LEDs connected to the collector of each transistor, so that they light in time with the circuit's oscillations.

### TWO-STATE NEON OSCILLATOR

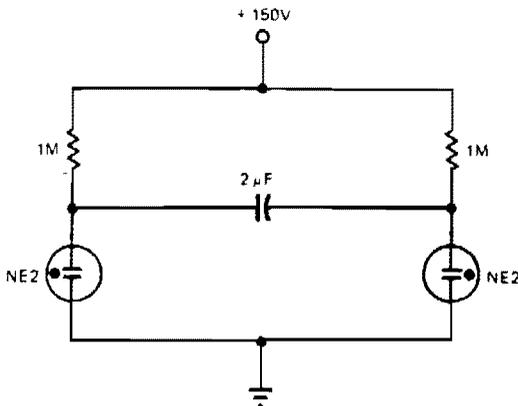


\* 200V MYLAR

EDN

Fig. 32-14

The number of lamps is easily increased in this oscillator.

### TRANSISTOR FLASHER

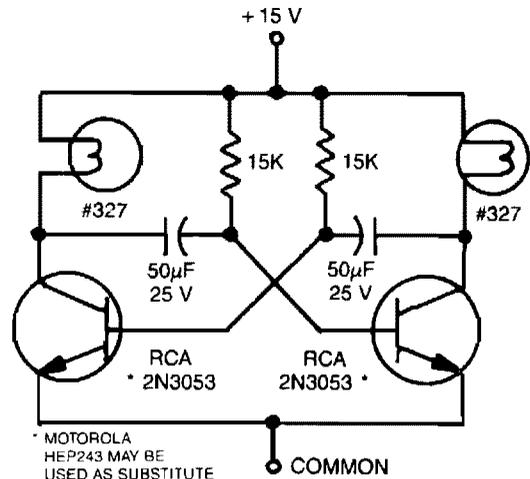


\* MOTOROLA  
HEP243 MAY BE  
USED AS SUBSTITUTE

EDN

Fig. 32-16

This astable multivibrator uses incandescent lamps in place of collector load resistors. The lamps flash on and off alternately.

### MINIMUM COMPONENT FLASHER

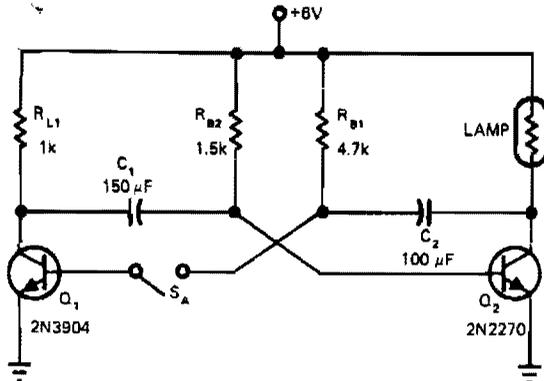

ELECTRONIC DESIGN

Fig. 32-17

Opening  $S_A$ , changes the indicator lamp from flashing to steady-lit condition. The 6-V incandescent lamp on the collector of  $Q_2$  requires about 0.3 A. A 1-K $\Omega$  load resistor limits  $Q_1$ 's collector current to about 6 mA. The circuit is, therefore, asymmetrical with respect to the on currents of the transistors, allowing use of a much smaller transistor for  $Q_1$  than for  $Q_2$ .

### LAMP FLASHER

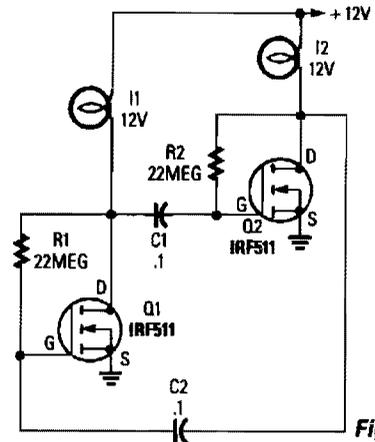


Fig. 32-18

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

The circuit is built around two power FETs, which are configured as a simple astable multivibrator to alternately switch the two lamps on and off. The rc values given sets the flash rate to about  $1/3$  Hz. By varying either the resistor or capacitor values, almost any flash rate can be obtained. Increase either  $C_1$  and  $C_2$ , or  $R_1$  and  $R_2$ , and the flash rate slows. Decrease them and the rate increases.

# 33


## Flow Detector

---


The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Low Flow-Rate Thermal Flowmeter


## LOW FLOW-RATE THERMAL FLOWMETER

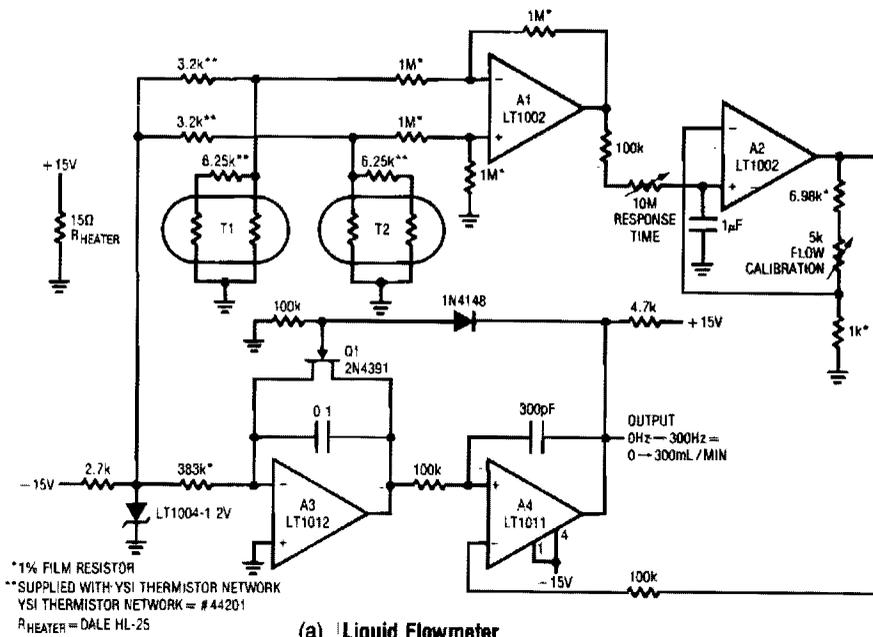

(a) Liquid Flowmeter

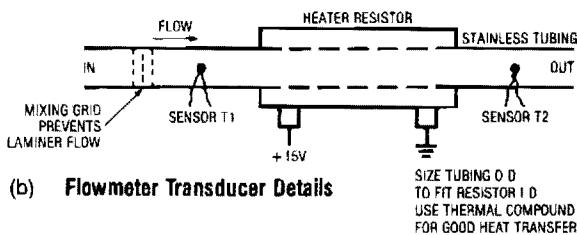

(b) Flowmeter Transducer Details

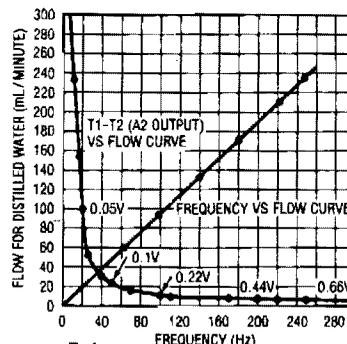

(c) Flowmeter Response Data

LINEAR TECHNOLOGY CORP.

Fig. 33-1

This design measures the differential temperature between two sensors. Sensor T1, located before the heater resistor, assumes the fluid's temperature before it is heated by the resistor. Sensor T2 picks up the temperature rise induced into the fluid by the resistor's heating. The sensor's difference signal appears at A1's output. A2 amplifies this difference with a time constant set by the 10 MΩ adjustment. Fig. 33-1c shows A2's output versus flow rate. The function has an inverse relationship. A3 and A4 linearize this relationship, while simultaneously providing a frequency output. A3 functions as an integrator that is biased from the LT1004 and the 338-KΩ input resistor. Its output is compared to A2's output at A4. Large inputs from A2 force the integrator to run for a long time before A4 can increase, turning on Q1 and resetting A3. For small inputs from A2, A3 does not have to integrate long before resetting action occurs. Thus, the configuration oscillates at a frequency which is inversely proportional to A2's output voltage. Since this voltage is inversely related to flow rate, the oscillation frequency linearly corresponds to flow rate.

# 34


## Fluid and Moisture Detectors

---


The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

- Fluid-Level Control
- Flood Alarm or Temperature Monitor
- Water-Level Sensor and Control
- Dual Liquid-Level Detector
- Soil Moisture Meter
- Liquid-Level Checker
- Liquid-Level Monitor

## FLUID-LEVEL CONTROL

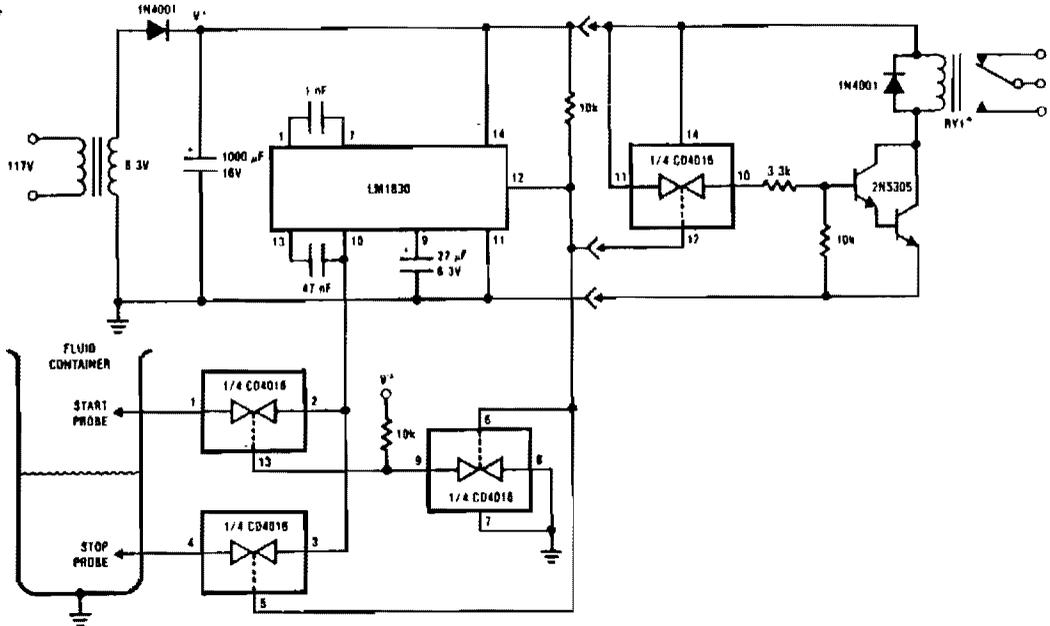

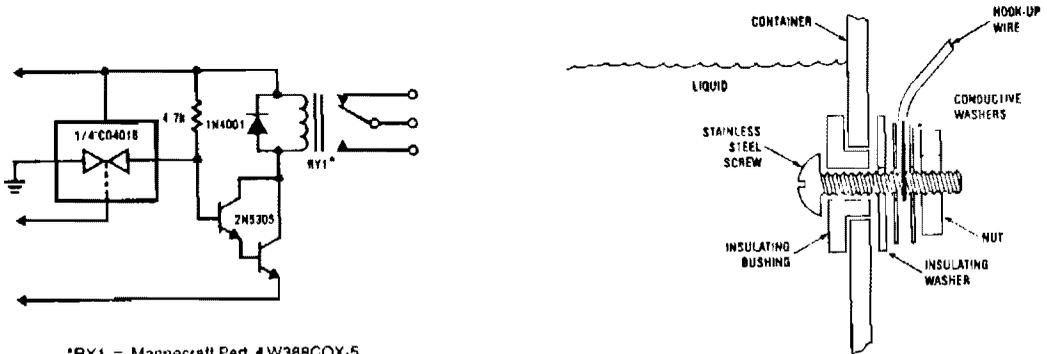"Emptying" Processes are Controlled with this Circuit



\*RV1 - Magnecraft Part # W388COX-5

**FIGURE 1(b). Filling Processes are Implemented with this Output Circuit and Relabeled Probes**


**NATIONAL SEMICONDUCTOR CORP.**

A sealing compound applied externally protects hook-up wire and prevents leaks

**Typical Probe Installation Fig. 34-1**

This circuit is designed to detect the presence or absence of aqueous fluids. An ac signal generated on-chip is passed through two probes within the fluid. A detector determines the presence of the fluid by using the probes in a voltage divider circuit and measuring the signal level across the probes. An ac signal is used to prevent plating or dissolving of the probes as occurs when a dc signal is used. A pin is available for connecting an external resistance in cases where the fluid impedance is not compatible with the internal 13-KΩ divider resistance.


## FLOOD ALARM OR TEMPERATURE MONITOR

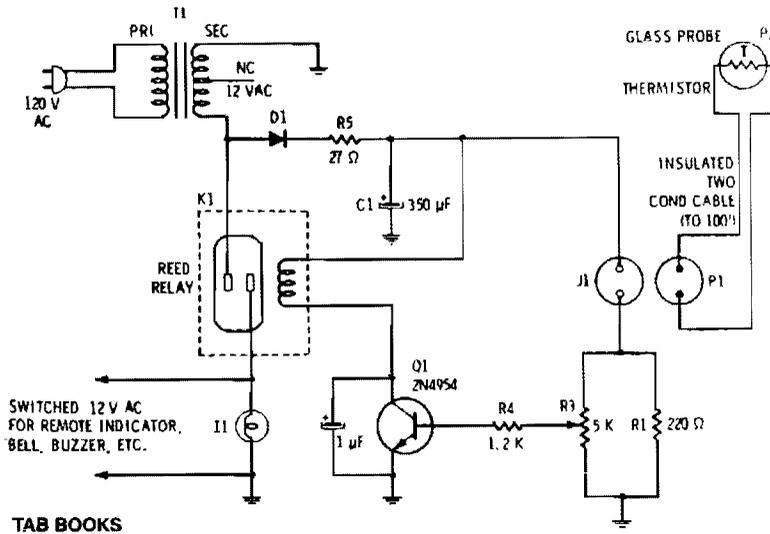

**Fig. 34-2**

Filtered 15 Vdc is applied to a series circuit consisting of thermistor R2 and parallel combination of resistors R1 and R3. Transistor Q1 acts as a switch whose state is determined by the setting of potentiometer R3, which is first set so just enough current flows into the base to switch on when the thermistor is in contact with air. When the resistance of the thermistor decreases, the voltage at the base of Q1 rises. When the base current reaches the preset level, the transistor conducts and passes current through the reed relay coil, closing the reed relay contacts. Current at the base of transistor Q1 is determined by the environment into which the thermistor is inserted.

## WATER-LEVEL SENSOR AND CONTROL

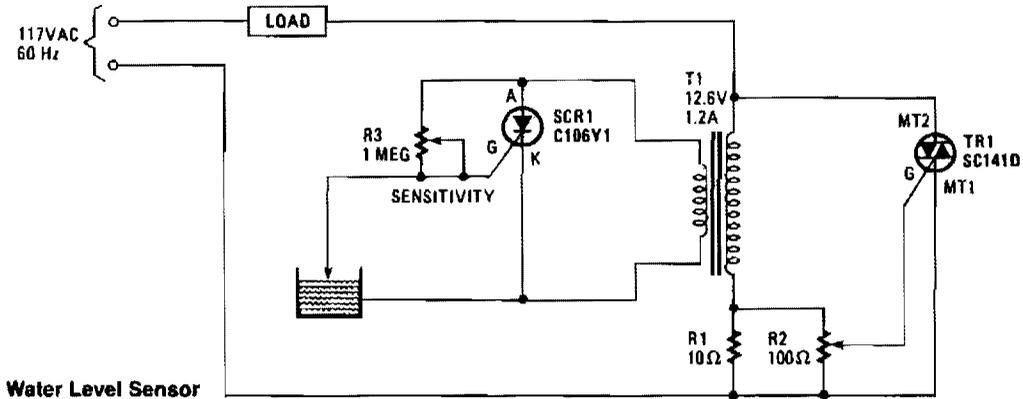


HANDS-ON ELECTRONICS

**Fig. 34-3**

## WATER-LEVEL SENSOR AND CONTROL (CONT.)

When the water level is low, the probe is out of the water and SCR1 is triggered on. It conducts and imposes a heavy load on transformer T1's secondary winding. That load is reflected back into the primary, gating triac TR1 on, which energizes the load. If the load is an electric valve in the water-supply line, it will open and remain open until the water rises and touches the probe; this shorts SCR1's gate and cathode, thereby turning off the SCR1, which effectively open-circuits the secondary. That open-circuit condition, when reflected back to the primary winding, removes the triac's trigger signal, thereby turning the water off.

### DUAL LIQUID-LEVEL DETECTOR

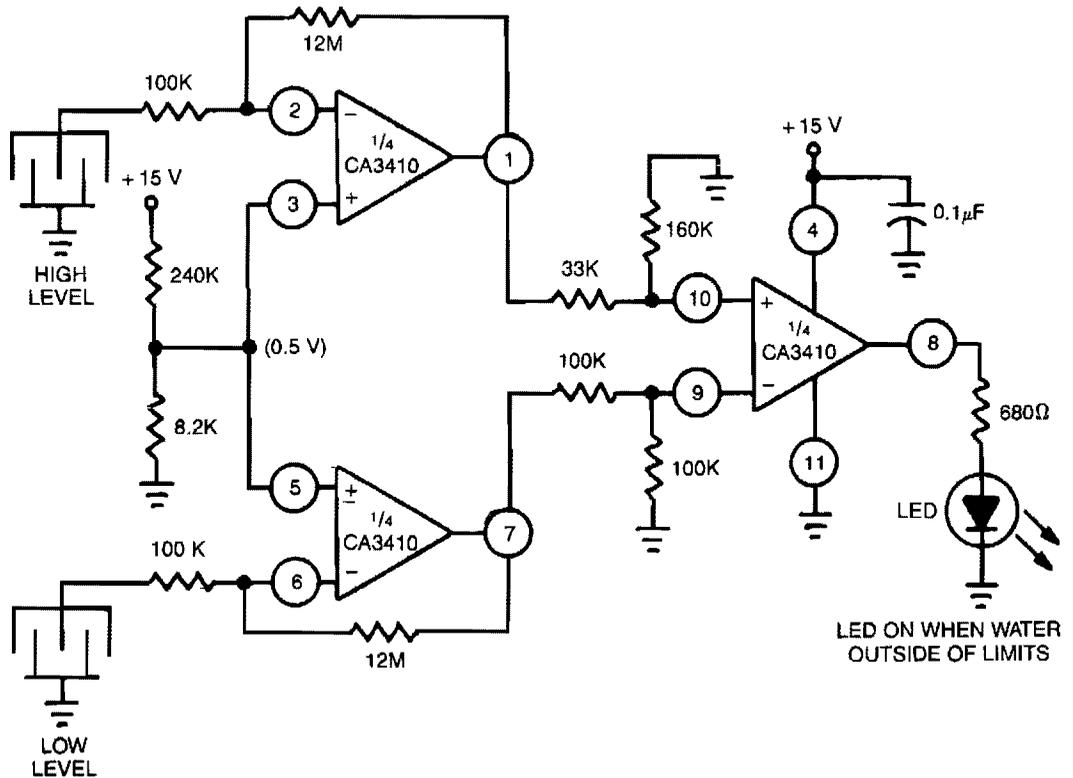


GE/RCA

Fig. 34-4

Uses CA3410 quad BiMOS op amp to sense small currents. Because the op amp's input current is low, a current of only  $1 \mu\text{A}$  passing through the sensor will change the converter's output by as much as 10 to 12 V.

## SOIL-MOISTURE METER

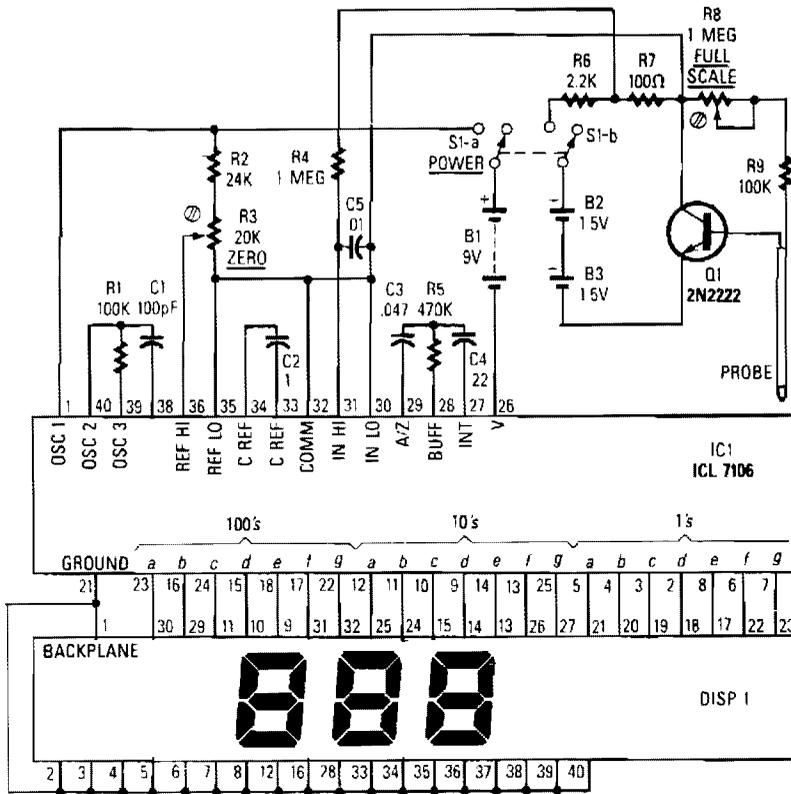

**Fig. 34-5**


Reprinted with permission from Radio-Electronics Magazine, June, 1988. Copyright Gernsback Publications, Inc., 1988.

IC1, an Intersil ICL7106, contains an a/d converter, a 3<sup>1</sup>/<sub>2</sub>-digit LCD driver, a clock, a voltage reference, seven segment decoders, and display drivers. A similar part, the ICL7107, can be used to drive seven segment LEDs. The probe body is a five-inch length of light-weight aluminum tubing. The leads from the circuit are connected to the body and tip of the probe. The sensor functions as a variable resistor that varies Q1's base current, hence its collector current. The varying collector current produces a varying voltage across 100 Ω resistor R7, and that voltage is what IC1 converts for display.

The LCD consumes about 25 μA, and IC1 consumes under 2 mA, so the circuit will run for a long time when it is powered by a standard 9-V battery. Current drain of the two 1.5-V AA cells is also very low: under 300 μA.

To calibrate, rotate R3 to the center of its range. Then place the end of the probe into a glass of water and adjust R8 for a reading of 100. When you remove the probe from the water, the LCD should indicate 000. You might have to adjust R3 slightly for the display to indicate 000. If so, readjust R8 with the probe immersed. Check for a reading of 000 again with probe out of water.

## LIQUID-LEVEL CHECKER

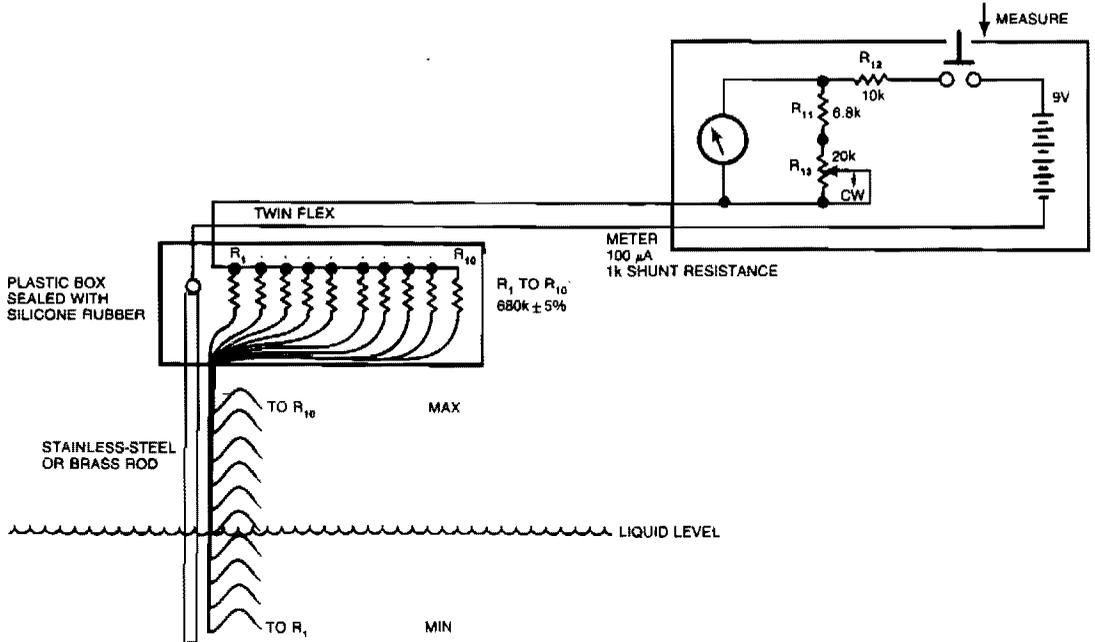


EDN

**Fig. 34-6**

Although many circuits use the varying-capacitance method for checking liquid levels, this simple resistive circuit is much easier to construct. Even a tank of a liquid, such as water, has sufficient conductive salts in solution for this method to work. The probe uses a metal rod that supports 10 insulated wires, which have stripped ends pointing down. As the level of liquid rises, resistors R1 through R10 are successively brought into circuit, each drawing an extra 10  $\mu\text{A}$  through the meter. Shunt resistors R11 and R13 calibrate the meter for a full-scale reading when the tank is full. Resistor R12 limits the current through the meter. If tank isn't rectangular—ie, if the volume of the liquid it contains isn't directly proportional to the liquid's depth—space the resistors accordingly or use a nonlinear progression of resistor values and retain constant resistor spacing.

## LIQUID-LEVEL MONITOR

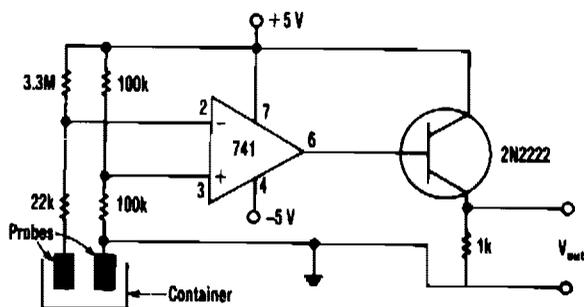

ELECTRONIC DESIGN

Fig. 34-7

This monitor uses a common 741 amp configured as a comparator and a low cost nontransistor as an output driver. With no liquid detected, a voltage of about 2.92 V is present in the op amp's inverting input at pin 2. The 100-K $\Omega$  resistors establish a reference voltage of +2.5 V at the non-inverting input at pin 3 of the op amp. Under those conditions, the op amp's output is -3.56 V, which keeps the 2N2222 transistor turned off and the voltage across its 1-K $\Omega$  output load resistor at 0 V. When liquid reaches the probes, the 3.3-M $\Omega$  and 22-K $\Omega$  resistor circuit conductively connects to ground. When enough current, about 1.4  $\mu$ A, flows through the liquid, the small 30 mV drop developed across the 22-K $\Omega$  resistor drives the op amp to deliver an output voltage of about 4.42 V. This voltage then drives a 2N2222 transistor into saturation, which generates a voltage drop of about 3.86 V across its 1-K $\Omega$  output load resistor.

# 35


## Followers

---


The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

High-Frequency Inverting Follower  
High-Frequency Noninverting Follower  
Simple Follower  
Voltage Follower


## HIGH-FREQUENCY INVERTING FOLLOWER

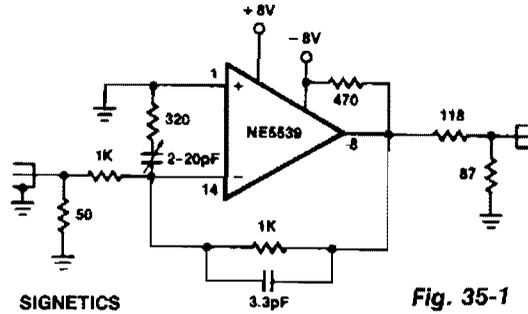


## HIGH-FREQUENCY NONINVERTING FOLLOWER

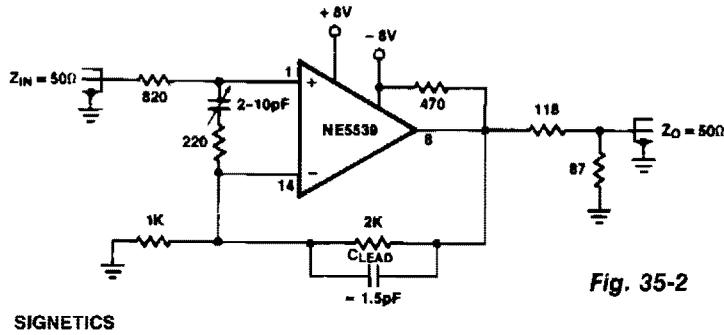

## SIMPLE FOLLOWER

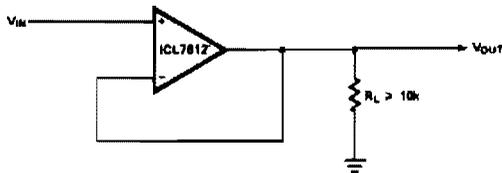

## VOLTAGE FOLLOWER

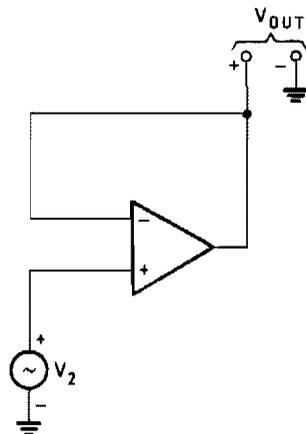

# 36



## Frequency Multipliers and Dividers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Pulse-Width Multiplier  
Frequency Doubler  
Digital Frequency Doubler  
Divide-by- $1\frac{1}{2}$  Counter Divider  
Odd-Number Counter Divider  
Single-Chip Frequency Doubler

## PULSE-WIDTH MULTIPLIER

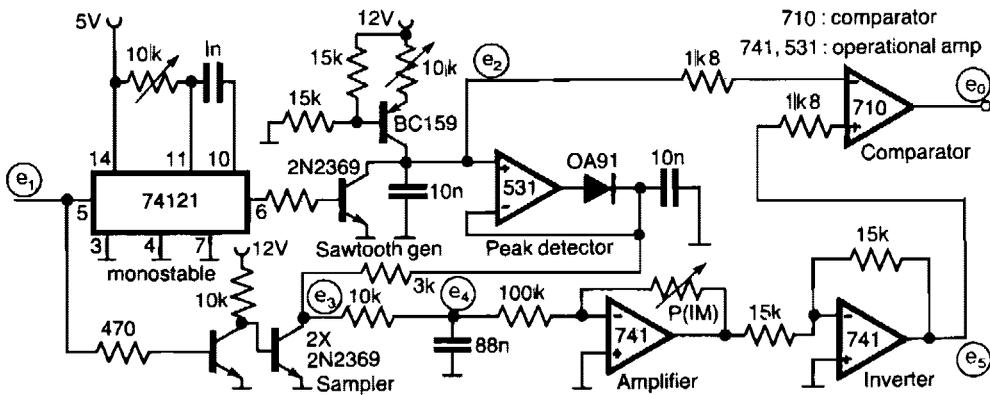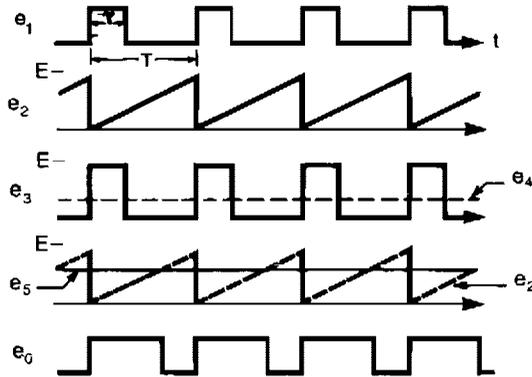


ELECTRONIC ENGINEERING

Fig. 36-1

This circuit for multiplying the width of incoming pulses by a factor greater or less than unity is simple to build and has the feature that the multiplying factor can be selected by adjusting one potentiometer only. The multiplying factor is determined by setting the potentiometer in the feedback of the 741 amplifier. The input pulses  $e_1$ , width  $T$  and repetition period  $T$  is used to trigger a sawtooth generator at its rising edges to produce the waveform  $e_2$  having a peak value of  $E$  volts. This peak value is then sampled by the input pulses to generate the pulse train  $e_3$  having an average value of  $e_4 (= ET/T)$  which is proportional to  $T$  and independent on  $T$ . The dc voltage  $e_4$  is amplified by a factor  $k$  and compared with sawtooth waveform  $e_2$  giving output pulses of duration  $kT$ . The circuit is capable of operating over the frequency range 10 kHz – 100 kHz. Note that  $k$  should be chosen less than  $T/T$  to ensure accurate pulse-width multiplication.

## FREQUENCY DOUBLER

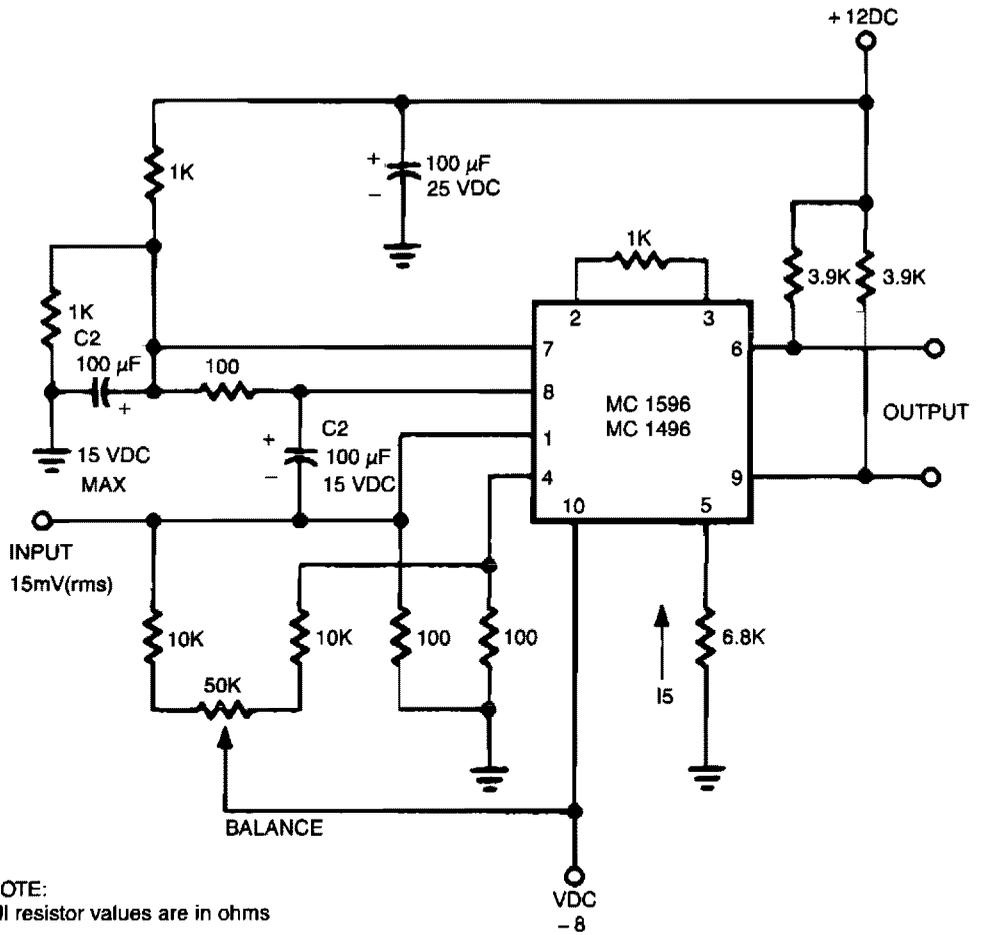


**SIGNETICS**

**Fig. 36-2**

The output contains the sum component, which is twice the frequency of the input, since both input signals are the same frequency.

## DIGITAL FREQUENCY DOUBLER

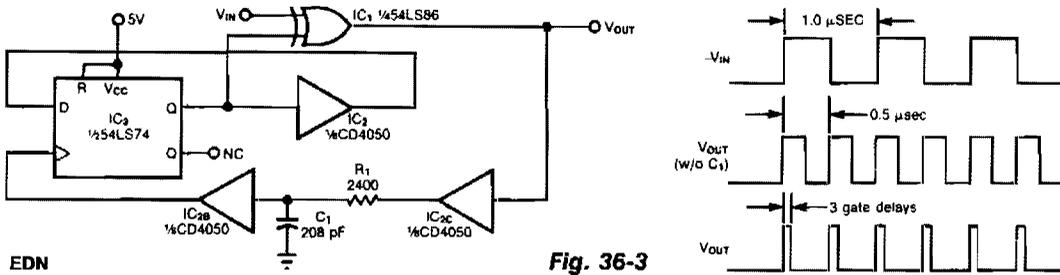


**Fig. 36-3**

The circuit doubles the frequency of a digital signal by operating on both signal edges. Each transition causes exclusive-OR gate IC1 to produce a pulse, which clocks flip-flop IC3 after propagating through buffers IC2C and IC2B. If you remove capacitor C1, the circuit produces narrow output pulses. By including C1, you can obtain a desired duty cycle for a given input frequency  $f_{IN}$ . The C1 value for an approximate 50% duty cycle is:

$$C1 = \frac{1}{2R_1 f_{IN}}$$

## DIVIDE-BY-1½ CIRCUIT

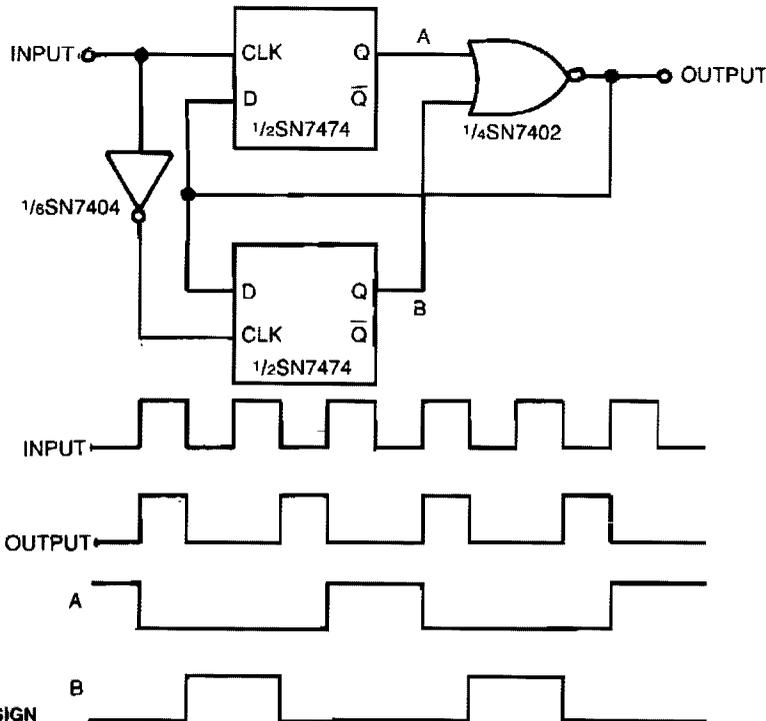


**Fig. 36-4**
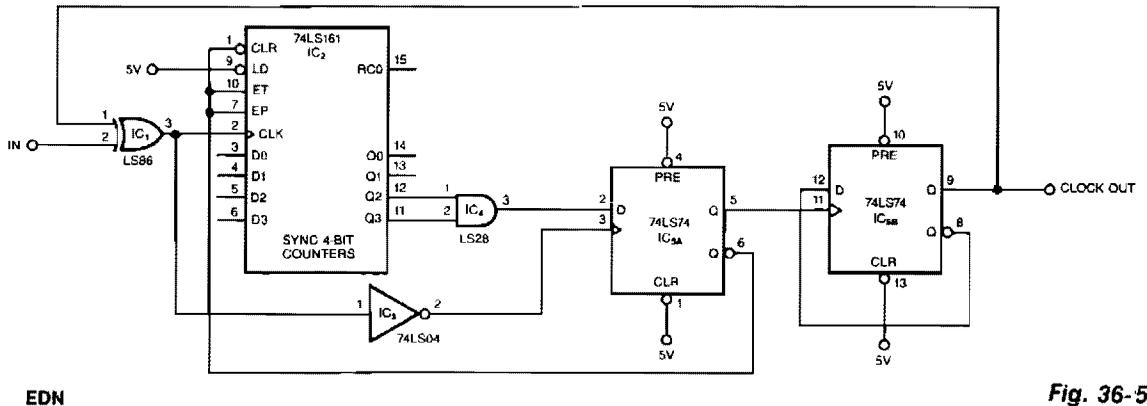
## DIVIDE-BY-1<sup>1</sup>/<sub>2</sub> CIRCUIT (CONT.)

An input signal drives both SN7474 D-type flip-flops, which are positive edge-triggered devices. A low-to-high input signal transition triggers the A flip-flop, while a high-to-low input signal transition triggers the B flip-flop via the SN7404 inverter. Either flip-flop in the high state will cause the output to decrease via the SN7402 NOR gate. This in turn disables the opposite flip-flop from going to the high state. The flip-flop in the high state remains there for one clock period, then it is clocked low. With both flip-flops low, the output increases, enabling the opposite flip-flop to be clocked high one-half clock cycle later. This alternate enabling and disabling action of the flip-flops results in a divide-by-1<sup>1</sup>/<sub>2</sub> function. That is, three clock pulses in, produce two evenly spaced clock pulses out. The circuit has no lock-up states and no inherent glitches. Replacing the NOR gate with an SN7400 NAND gate inverts the A, B, and output signals. By adding simple binary or BCD counters, counting chains, such as divide-by-3, -6, -12, -24, -15, -30, etc., can be generated using the divide-by-1<sup>1</sup>/<sub>2</sub> circuit as a basis.

## ODD-NUMBER COUNTER DIVIDER




EDN

Fig. 36-5

This circuit, shown symmetrically, divides an input by virtually any odd number. The circuit counts  $n + 1/2$  clocks twice to achieve the desired divisor. By selecting the proper  $n$ , which is the decoded output of the LS161 counter, you can obtain divisors from 3 to 31. The circuit, as shown, divides by 25; you can obtain higher divisors by cascading additional LS161 counters. The counter and IC5A form the  $n + 1/2$  counter. Once the counter reaches the decoded count,  $n$ , IC5A ticks off an additional  $1/2$  clock, which clears the counter and puts it in hold. Additionally, IC5A clocks IC5B, which changes the clock phasing through the XOR gate, IC1. The next edge of the input clocks IC5A, which reenables the counter to start counting for an additional  $n + 1/2$  cycles. Although the circuit has been tested at 16 MHz, a worst-case timing analysis reveals that the maximum input frequency is between 7 and 8 MHz.

## SINGLE-CHIP FREQUENCY DOUBLER

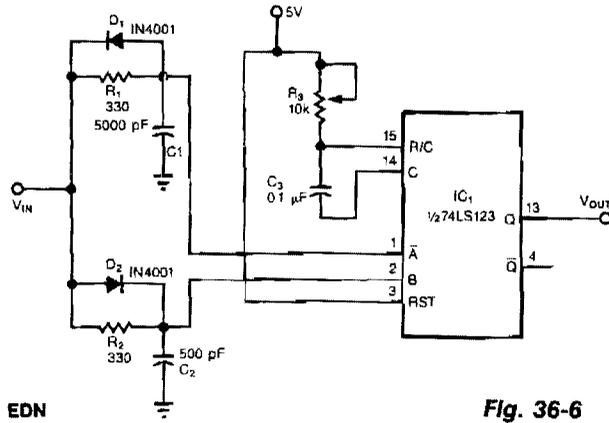

**Fig. 36-6**

The frequency doubler uses only one IC. Like other doublers, this circuit uses both the rising and falling edges of the input signals to produce digital pulses, thus effectively doubling the input's frequency.

Without the rc networks at IC<sub>1</sub> inputs, IC<sub>1</sub> would not produce any output pulses. However, the rc networks delay one edge with respect to the other. The A input lags the B input for positive-going edges, and the B input lags the A input for negative-going ones. You can vary the output duty cycle from 0 to 100% by varying R<sub>3</sub>. IC<sub>1</sub>'s minimum output pulse width defines the maximum frequency of this circuit.


# 37

## Frequency-to-Voltage Converters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

## FREQUENCY-TO-VOLTAGE CONVERTER

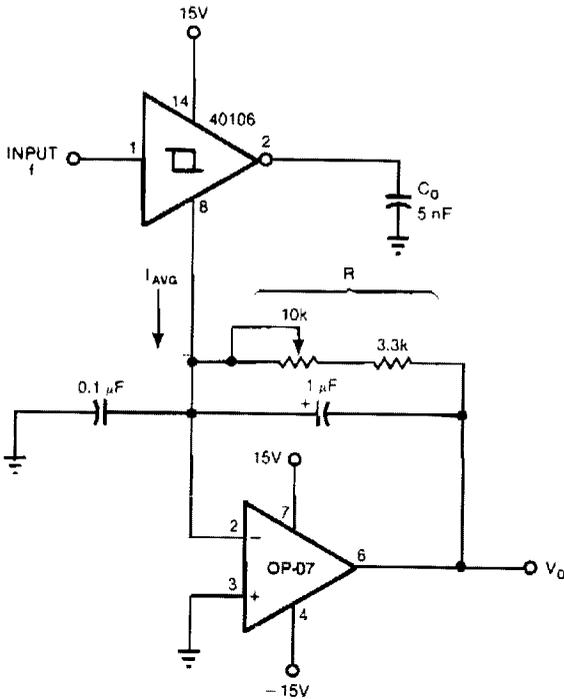

Six components can configure a circuit whose output voltage is proportional to its input frequency. The average current ( $I_{AVG}$  from the 40106 Schmitt trigger inverter's ground pin 8) is linearly dependent on the frequency at which  $C_0$  is discharged into the op amp's summing junction. The op amp forces this current to flow through the 13.33-K $\Omega$  feedback resistor, producing a corresponding voltage drop. This frequency-to-voltage converter yields 0 to -10 V output with 0 to 10 kHz input frequencies.

EDN

Fig. 37-1

# 38


## Function Generators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Precision One Shot	Two-Function Signal Generator
Linear Triangle-Wave Timer	Triangle Generator
Four-Output Waveform Generator	Monostable Operator
Function Generator	Programmable-Frequency Free-Running
Classic Op Amp Astable Multivibrator	Multivibrator
Programmable Triangle-/Square-Wave	Function Generator
Generator	Programmable-Frequency Astable
Noninteger Programmable Pulse Divider	Linear-Ramp Monostable
XOR Gate Complementary Signal Generator	Low-Frequency Multivibrator
Low-Cost FSK Generator	Retriggerable One Shot
Harmonics Generator	Astable Multivibrator
Low-Frequency FM Generators	Single-Control Function Generator
Positive-Triggered Monostable	Triangle-/Square-Wave Generator
Precision Audio Waveform Generator	Variable Duty Cycle Timer
Monostable Multivibrator	Basic Function Generator
Versatile $2\phi$ Pulse Generator	Wide-Range Tunable Function Generator
Fixed-Frequency Generator	Sawtooth and Pulse Generator
Single-Supply Multivibrator	Precise Triangle/Square-Wave Generator
Easily Tuned Sine-/Square-Wave Oscillator	Wide-Range Triangle/Square-Wave Generator
Astable	


## PRECISION ONE SHOT

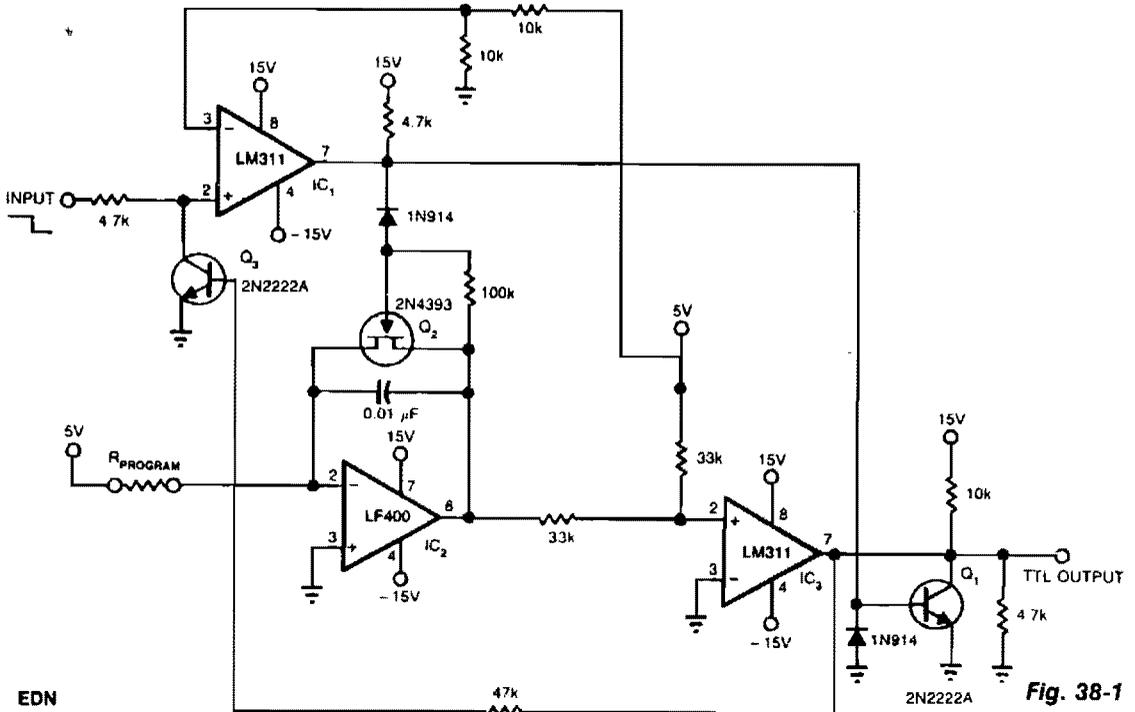

**Fig. 38-1**

If you need a wide-range, resistor-programmable monostable multivibrator, you can program the circuit for pulse widths from  $1 \mu\text{s}$  to  $10\text{s}$ — $10^7:1$  range. A high-to-low transition at the input causes IC1's output to switch low, thereby turning off Q1 and Q2. With the latter transistor turned off, IC3's output increases and the output of IC2 begins to ramp toward the negative supply level at a rate determined by the  $0.01\text{-}\mu\text{F}$  capacitor and the programming resistor. When IC2's output voltage reaches  $-5\text{V}$ , IC3's output switches low. If you anticipate input pulses shorter than the desired output pulses, Q3 is necessary. This transistor keeps IC1's input low while an output pulse is present, thereby preventing inadvertent resetting of the one shot.


## LINEAR TRIANGLE-WAVE TIMER

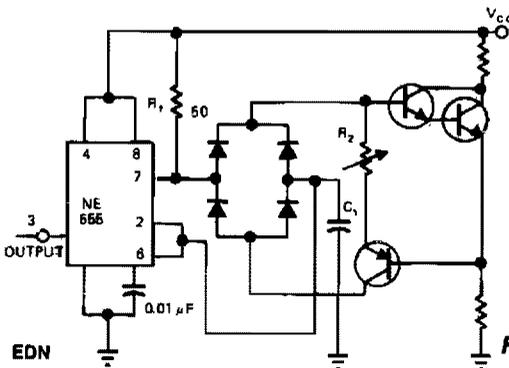


**Fig. 38-2**

Using one current source for the charge and discharge path in this circuit ensures identical rise and fall times at the capacitor terminal. A Darlington pair ensures identical biasing of the IC during the charge and discharge cycles. The period of the triangle wave is:  $T \approx 0.46V_{CC}/R_2$ .  $V_{CC}$  must be at least  $8\text{V}$  to maintain linearity. At the output at pin 3 of the IC timer, a 50% duty-cycle square wave, frequency tunable by  $R_2$  alone, appears.

## FOUR-OUTPUT WAVEFORM GENERATOR

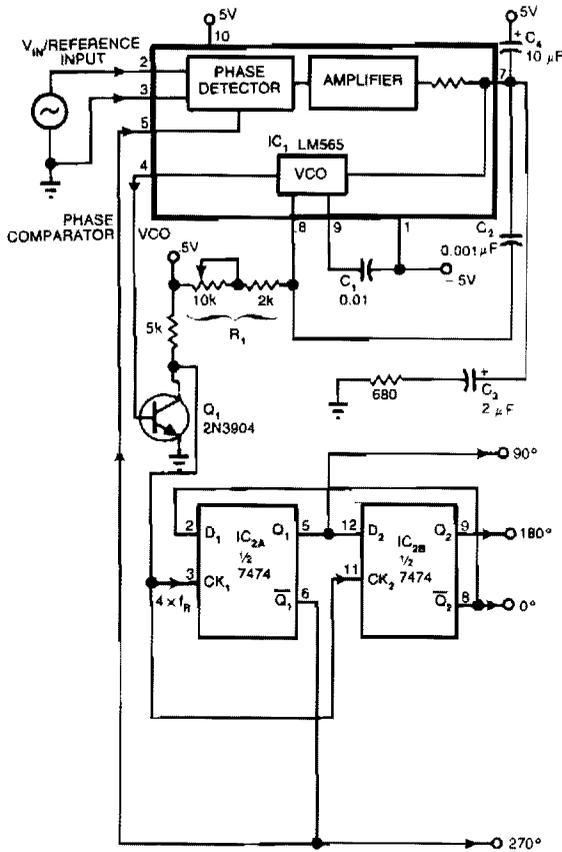

(A)

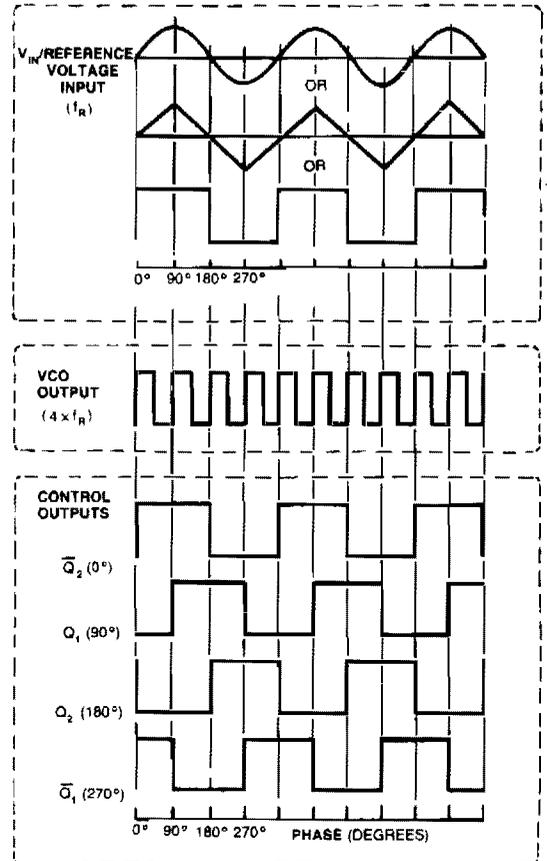

(B)

EDN

**Fig. 38-3**

Many applications require control signals that have phase shifts with reference to an input signal. Circuit accepts a sine, square, or triangular wave as an input reference signal and produces square-wave outputs with 0°, 90°, 180°, and 270° phase shifts with respect to the input. Figure 38-3B shows the input and output waveforms. The circuit contains two ICs: an LM565 phase-locked loop and a 7474 dual-D positive edge-triggered flip-flop. R1 and C1 set the free-running frequency of the LM565's VCO. You should adjust R1 so that the frequency is approximately four times that of the input reference signal. The LM565 responds to input signals greater than 10 mV pk-pk; 3 V pk-pk is the chip's maximum allowable input level. Q1 matches the LM565's output to the flip-flops' inputs. The flip-flops' outputs provide the TTL-compatible square-wave signals with 0°, 90°, 180°, and 270° phase shift with reference to the input signal.

## FUNCTION GENERATOR


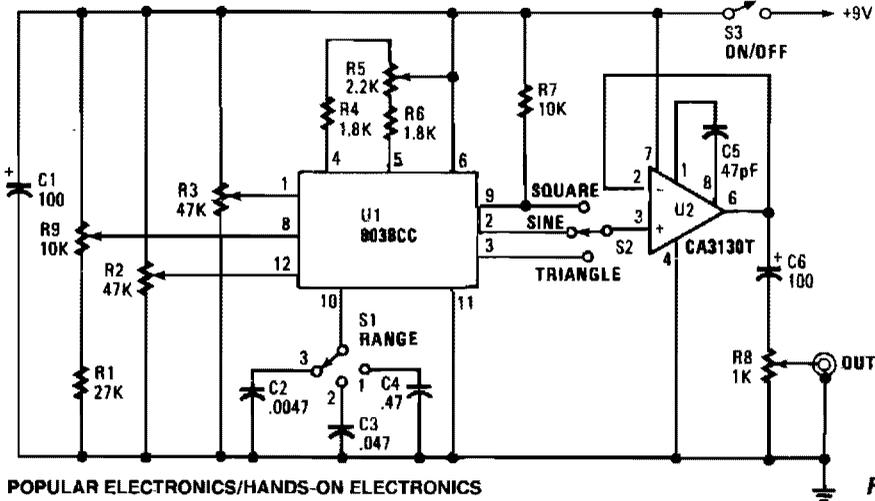


Fig. 38-4

This circuit can output sine, square, and triangular signals of from 15 Hz to 25 kHz in three ranges. The circuit is built around an 8038 function generator that produces the triangular- and square-wave outputs directly from an oscillator. The triangular output is then processed to develop the sine wave. While that method doesn't provide a sufficiently low level of distortion to let you make distortion measurements on audio gear, the degree of purity is high enough for frequency-response tests and a lot of other audio analysis. Three switched capacitors, C2 to C4, set the circuit's frequency range via switch S1. Variable resistor R9 and resistor R1 provide the voltage for controlling the charge and discharge rates of the timing capacitor selected. Resistors R4 to R6 control the charge and discharge currents. Resistor R5 can be adjusted to provide a 1.1 mark/space ratio.

## CLASSIC OP AMP ASTABLE MULTIVIBRATOR

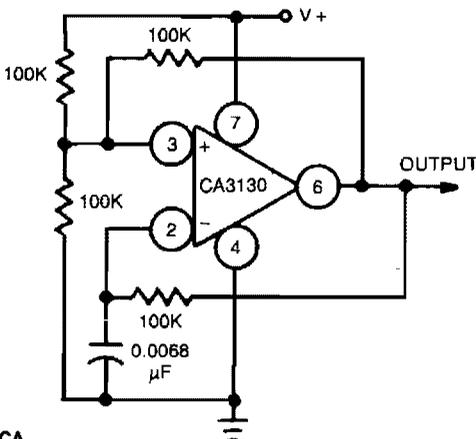


Uses CA3130 BiMOS op amp that operates at a frequency of 1 kHz. With rail-to-rail output swing, frequency is independent of supply voltage, device, and temperature. Only the temperature coefficient of  $R_T$  and  $C_T$  enters into circuit stability.

GE/RCA

ALL RESISTANCE VALUES ARE IN OHMS

Fig. 38-5

## PROGRAMMABLE TRIANGLE-/SQUARE-WAVE GENERATOR

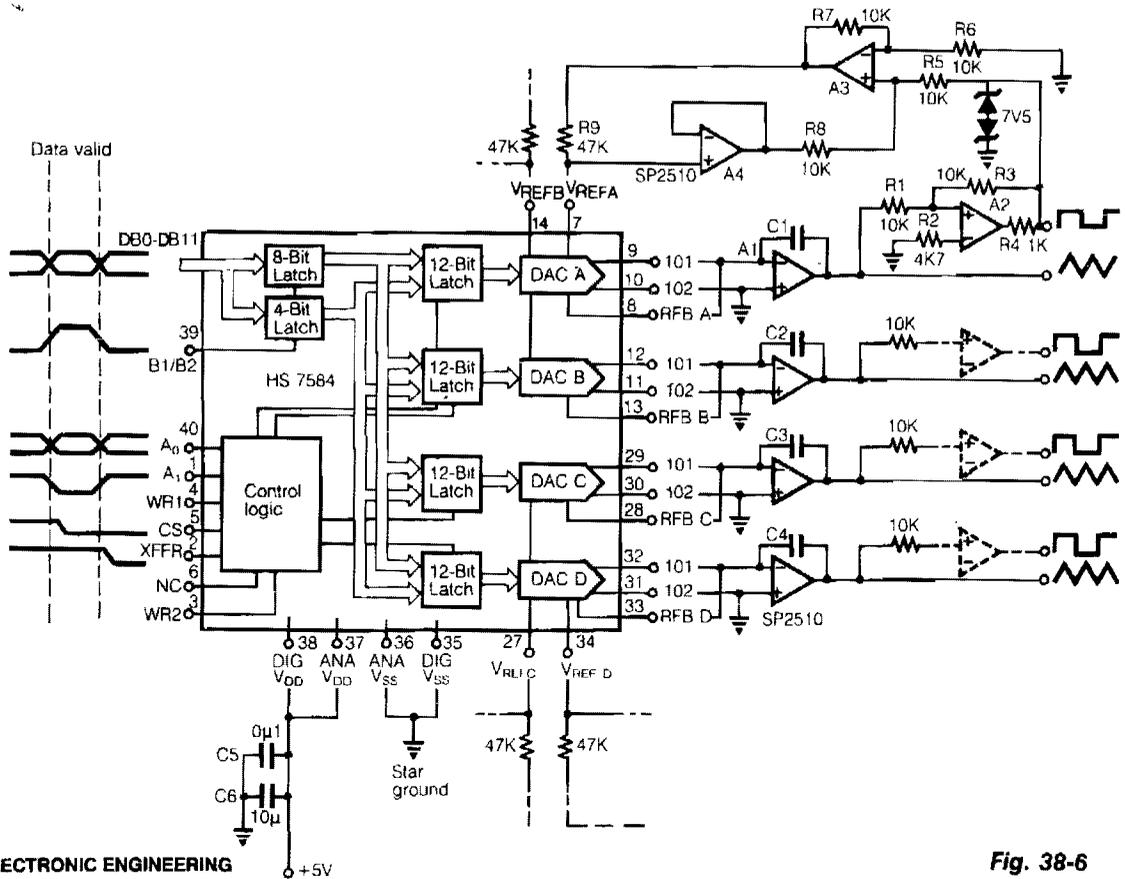

**Fig. 38-6**


The programmable multiple output generator provides the control signals for data converter ATE. Major performance criteria are simple, interfaces to a number of microprocessor systems, low power consumption, stable output timing relationships combined with a minimum of board space. For schematic simplicity only, one output circuit is shown in full.

The monolithic HS7584 provides four current output DAC's with four quadrant multiplication, individual reference input and a feedback resistor. The digitally controlled integrator's frequency is determined by:

$$f = \frac{\text{Digital Input}}{4 R C}$$

$C$  is the value of  $C1$  to  $C4$  and  $R$  is the resistance of the DAC. With the four DACs on a single chip, the resistance matching is good, which results in stable timing relationships of the generator outputs. The output of the comparator  $A2$  determines whether the constant current source provided by  $A3$  and  $A4$  is positive or negative.


## NONINTEGER PROGRAMMABLE PULSE DIVIDER

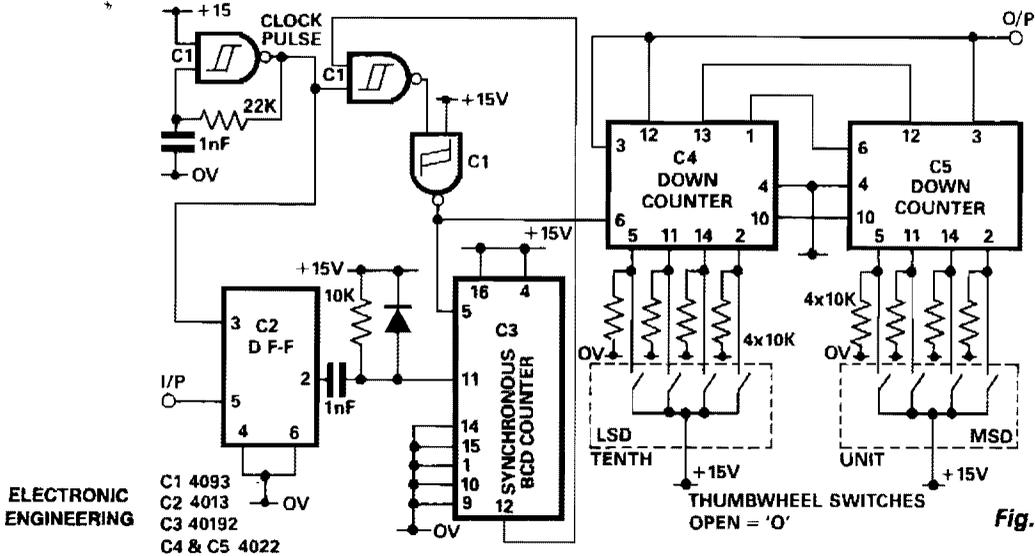

**Fig. 38-7**

The purpose of D-type flip-flop IC2 is to synchronize the input signal with the clock pulse. When the clock pulse changes from low to high and the input is high, IC2 output is high. Subsequently, IC3 resets to zero and starts counting up. Until the counter counts to ten, the counter is inhibited. Thus, the number of pulses of the output of IC3 is ten times input pulse. The designed frequency of the clock pulse must be ten times higher than the maximum frequency of the input. IC4 and IC5 are cascaded to form a two decade programmable down counter. Since the number of pulses appearing at the input of the down counter is ten times the input to the divider, the effective range of the divisor for this divider is 0.1 to 9.9.

## XOR GATE COMPLEMENTARY SIGNALS GENERATOR

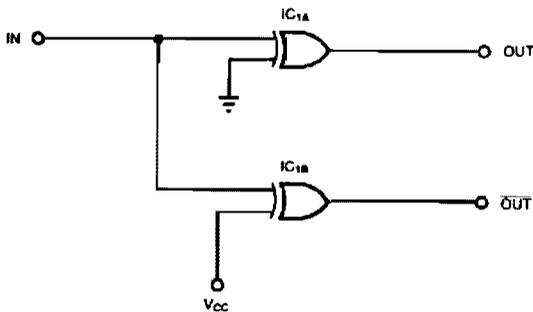


**Fig. 38-8**

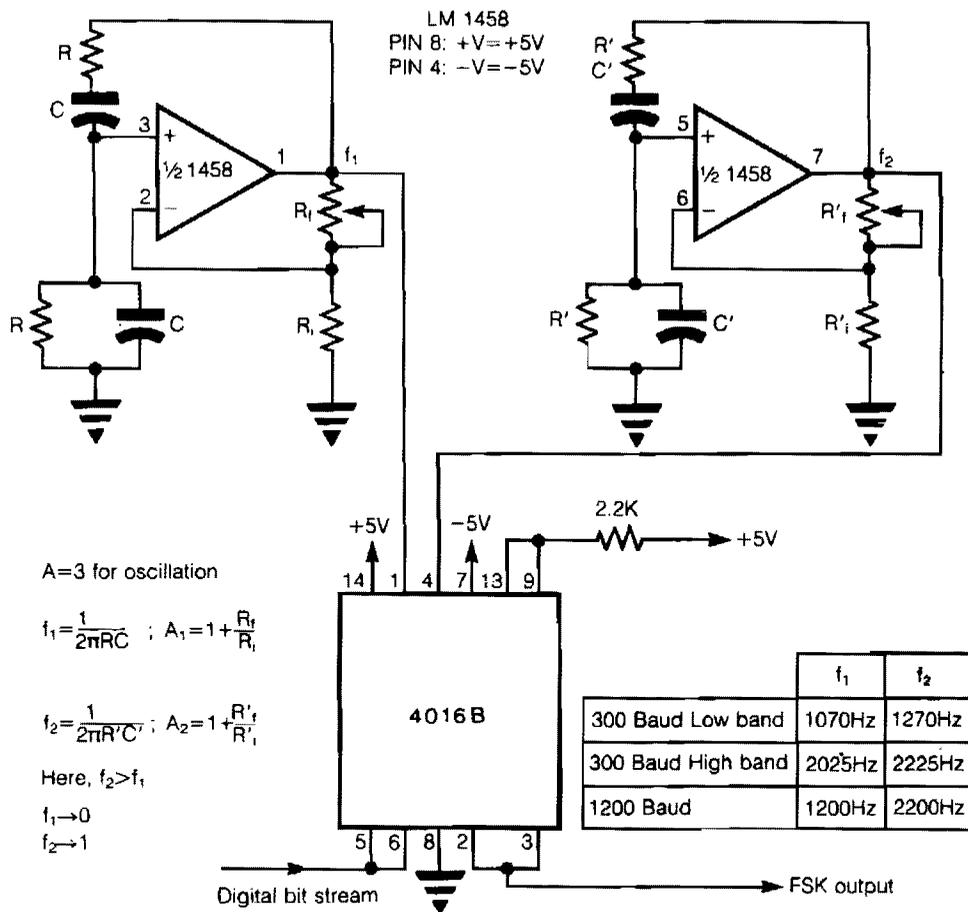EDN

Some applications, such as driving three-state buffers for data multiplexers or for biphasic clocks in high-speed systems, require complementary signals having a small-time skew and nearly simultaneous transitions. Here, XOR gates function as both inverting and noninverting gates. For CMOS systems, practically any type of XOR gate will work. However, the advanced-CMOS logic (ACL) families have the greatest drive capability, the shortest gate delays, and the tightest manufacturing tolerances. For TTL systems, compatible CMOS types such as the ACT or S/AS86 families are preferable. Do not use low-power TTL versions (LS or ALS), because they have large propagation delay differences when one XOR gate is inverting and the other is noninverting.

## LOW-COST FSK GENERATOR



ELECTRONIC ENGINEERING

**Fig. 38-9**

In FSK, two discrete frequencies are used to represent the binary digits 0 and 1. The heart of the circuit consists of two Wien-bridge oscillators built using a dual op amp LM 1458, for the two frequencies. The two frequencies are enabled corresponding to digital data using two switches in SCL 4016. The control lines of these switches are logically inverted with respect to each other using one of the switches in SCL 4016 as an inverter, so as to enable only one oscillator output at a time. The digital bit stream is used to control the analog switches as shown. Since the switching frequency limit of SCL 4016 is 40 MHz, high-data rates can be easily accommodated. This method comes in handy when expensive FSK generator chips are not readily available; also, the components used in this circuit are easily available off the shelf and are quite cheap.

## HARMONICS GENERATOR

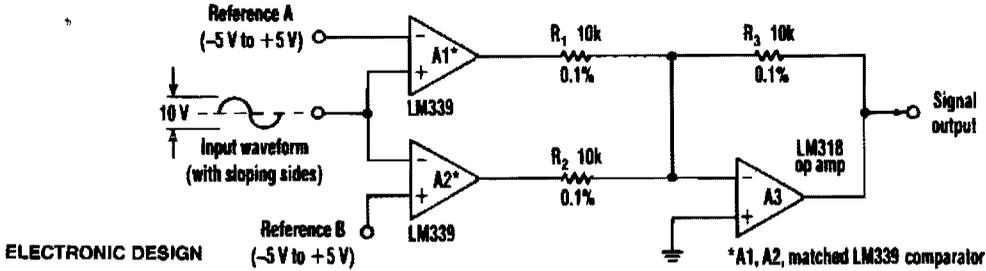


Fig. 38-10

ELECTRONIC DESIGN

Two comparators and a summing amplifier that generate differential harmonic spectra comprise a simple frequency multiplier. The resulting circuit can extract harmonics from a sine, triangle, sawtooth, or any other sloped-sided waveform.

With a sloped-input waveform, a comparator produces an output pulse width that's proportional to the input amplitude plus a reference voltage. Changing the reference can vary the pulse width from 0 to 100%. As the pulse width changes, the harmonic spectrum changes, but two comparators combined in the adder eliminate harmonics, depending on the duty cycle. For example, a 50% pulse will lack all the even-numbered harmonics. Similarly, a 25% duty-cycle pulse will be missing multiples of the fourth harmonic and deliver the second, sixth, and tenth harmonics. Accordingly, the circuit generates multiples of the input frequency that might not have existed in the input waveform. Adjusting the references can create virtually any harmonic.

Because comparators A1 and A2 supply differential inputs to the added A3, the adder cancels out equal harmonics. Therefore, both A1 and A2 should have identical ac characteristics, and A3 should have good common-mode rejection and a high slew rate. In particular, R1, R2, and R3 should match within 0.1%. Of course, the accuracy of the circuit depends heavily on the amplitude stability of the input.

## LOW-FREQUENCY FM GENERATORS

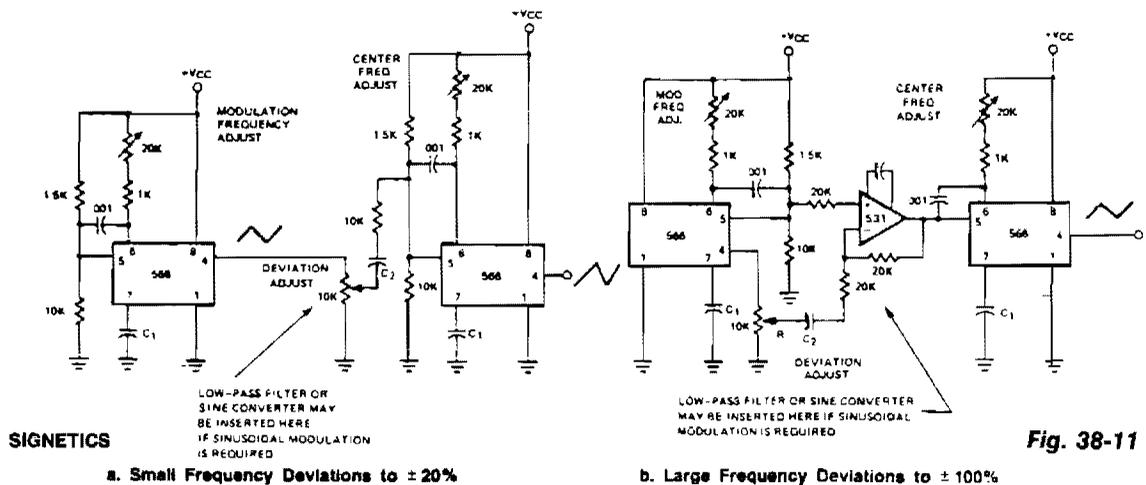


Fig. 38-11


a. Small Frequency Deviations to  $\pm 20\%$

b. Large Frequency Deviations to  $\pm 100\%$

## LOW-FREQUENCY FM GENERATORS (Cont.)

Here are two FM generators for low frequency, less than 0.5 MHz center frequency, applications. Each uses a 566 function generator as a modulation generator and a second 566 as the carrier generator. Capacitor C1 selects the modulation frequency adjustment range and C1 selects the center frequency. Capacitor C2 is a coupling capacitor which only needs to be large enough to avoid distorting the modulating waveform. If a frequency sweep in only one direction is required, the 566 ramp generators given in this section can be used to drive the center generator.

### POSITIVE-TRIGGERED MONOSTABLE

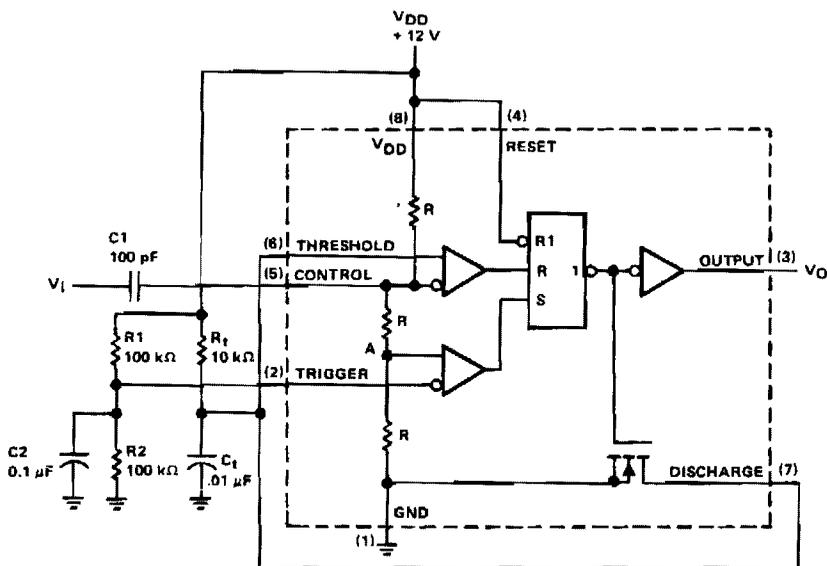


Reprinted by permission of Texas Instruments.

Fig. 38-12

A positive-going trigger pulse can be used to start the timing cycle with the circuit shown. In this design, trigger input pin 2 is biased to 6 V ( $1/2 V_{DD}$ ) by divider R1 and R2. Control input pin 5 is biased to 8 V ( $2/3 V_{DD}$ ) by the internal divider circuit. With no trigger voltage applied, point A is at 4 V ( $1/3 V_{DD}$ ). To turn the timer on, the voltage at point A has to be greater than the 6 V present on pin 2. Positive 5-V trigger pulse  $V_i$  applied to the control input pin 5 is ac coupled through capacitor C1, adding the trigger voltage to the 8 V already on pin 5; this results in 13 V with respect to ground. The output pulse width is determined by the values of  $R_t$  and  $C_t$ .

When voltage at point A is increased to 6.5 V, which is greater than the 6 V on pin 2, the timer cycle is initialized. The output of timer pin 3 increases, turning off discharge transistor pin 7 and allowing  $C_t$  to charge through resistor  $R_t$ . When capacitor  $C_t$  charges to the upper threshold voltage of 8 V ( $2/3 V_{DD}$ ), the flip-flop is reset and output pin 3 decreases. Capacitor  $C_t$  then discharges through the discharge transistor. The timer is not triggered again until another trigger pulse is applied to control input pin 5.


## PRECISION AUDIO WAVEFORM GENERATOR

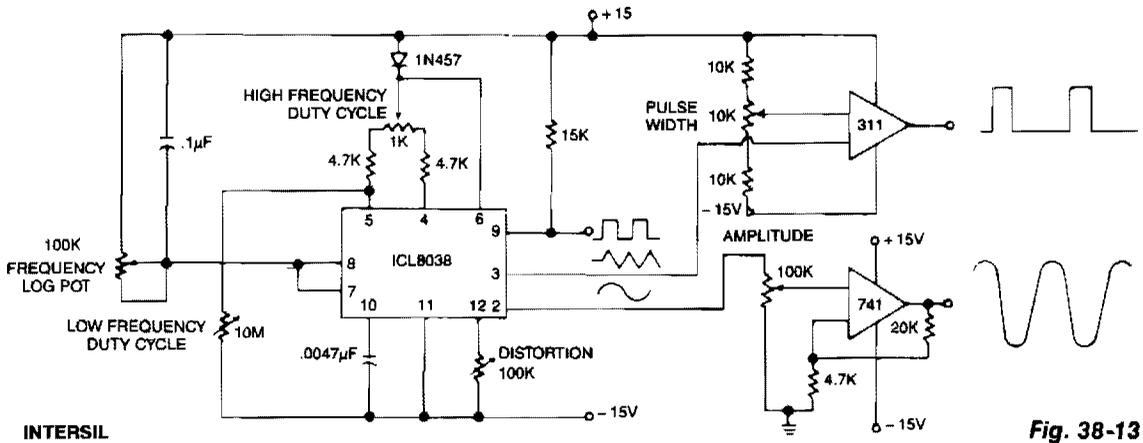

**Fig. 38-13**

This circuit generates sinusoidal, square, and triangle waveforms simultaneously. Set the frequency to a particular value or vary it, as shown above. An op amp can be added for extra drive capability and simplified amplitude adjustment. A simple comparator, slicing the triangle waveform, provides continuous duty cycle adjustment at a constant frequency.

## MONOSTABLE MULTIVIBRATOR

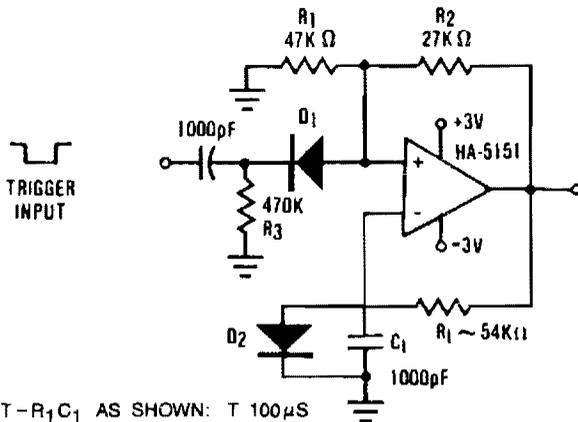

T -  $R_1 C_1$  AS SHOWN: T 100  $\mu$ S

HARRIS

**Fig. 38-14**

The circuit illustrates the usefulness of the HA-5151 as a battery-powered monostable. In this circuit, the ratio is set to .632, which allows the time constant equation to be reduced to:

$$T = R_1 C_1$$

D2 is used to force the output to a defined state by clamping the negative input at +0.6 V. Triggering is set by C1, R3, and D2. An applied trigger pulls the positive input below the clamp voltage, +0.6 V, which causes the output to change state. This state is held because the negative input cannot follow the change because of  $R_1 \cdot C_1$ . This particular circuit has an output pulse width set at approximately 100  $\mu$ s. Use of potentiometers for  $R_1$  and variable capacitors for  $C_1$  will allow for a wide variation in  $T$ .

## VERSATILE 2 $\phi$ PULSE GENERATOR

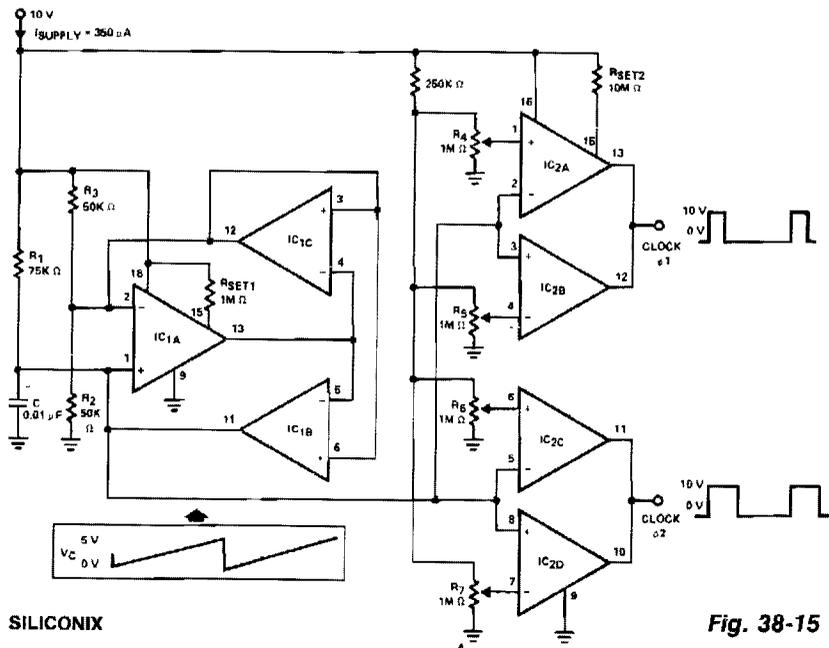


Fig. 38-15

## FIXED-FREQUENCY GENERATOR

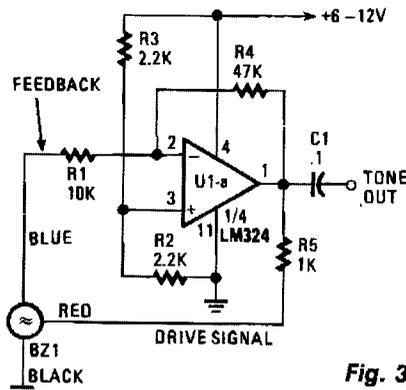


Fig. 38-16

HANDS-ON ELECTRONICS/POPULAR ELECTRONICS


A single op amp, one fourth of an LM324 quad op amp, is configured as a standard inverting amplifier. At power up, a positive voltage is applied to the noninverting input of U1, via R3, forcing its output high. That high output travels along three paths. The first path is the tone output. Along the second path, by way of R5, that high is used as the drive

signal for BZ1. In the third path, the high output of U1 is fed back, via R4, to the inverting input of U1. That forces U1's output to go low. And that low, when fed back to the inverting input of U1, causes the op amp output again to a high, and the cycle repeats itself. As configured, U1 provides a voltage gain of 4.7 (gain =  $R4/R1$ ).

The outer ring of the piezo element is usually connected to the circuit ground. The large inner circle serves as the driven area, and the small elongated section supplies the feedback signal. Resistor R5 sets BZ1's output-volume level. That level can be increased by decreasing R5 for example, to 470  $\Omega$ . To decrease the volume, increase R5 to about 2.2 K $\Omega$ , or so.


Resistors R2 and R3 set the bias for op amp U1's positive input pin 3 to half of the supply-voltage level. That allows for a maximum voltage swing at U1's output. Although a quad op amp is specified, almost-any similar low cost single or dual op amp will work for U1a.

## SINGLE-SUPPLY MULTIVIBRATOR

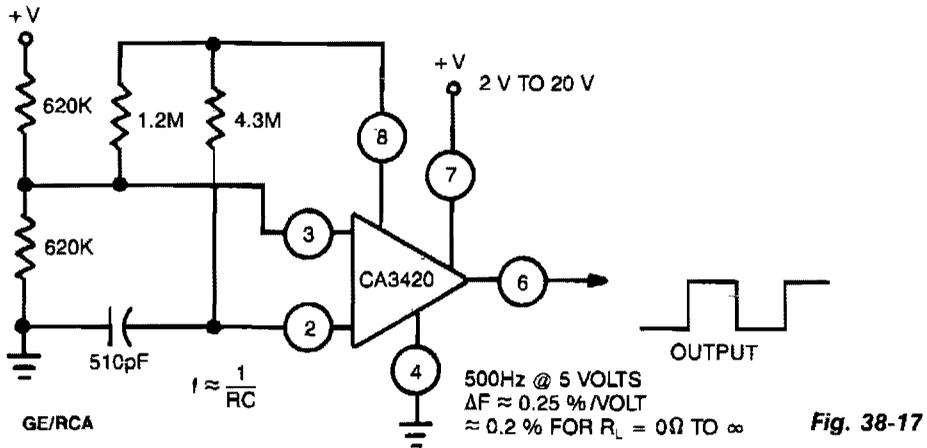

This multivibrator uses a CA3420 BiMOS op amp to provide improved frequency stability. The output frequency remains essentially independent of supply voltage. Because of the inherent buffering action of pin 6, frequency shift is approximately 0.2% when  $R_L$  varies between zero  $\Omega$  to infinity.
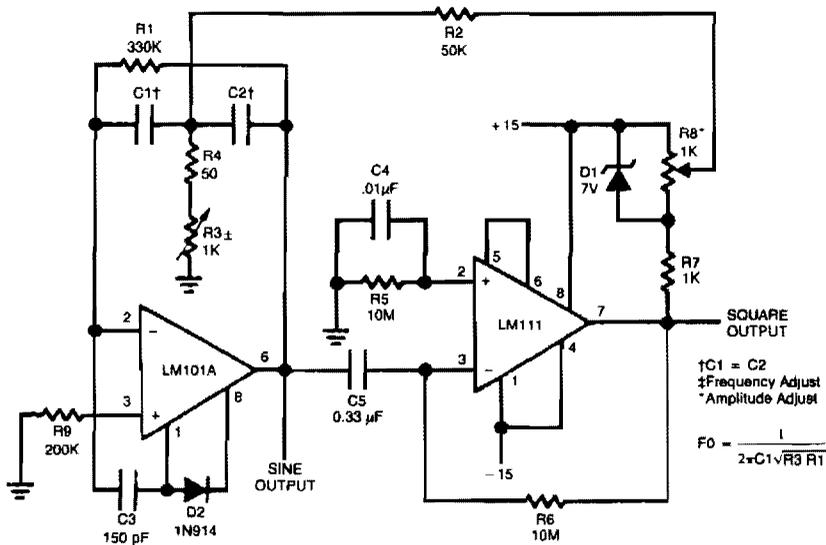
## EASILY TUNED SINE-WAVE/SQUARE-WAVE OSCILLATOR



NATIONAL SEMICONDUCTOR CORP.


**Fig. 38-18**

## EASILY TUNED SINE-WAVE / SQUARE-WAVE OSCILLATOR (Cont.)


The circuit will provide both a sine- and square-wave output for frequencies from below 20 Hz to above 20 kHz. The frequency of oscillation is easily tuned by varying a single resistor. This is a considerable advantage over Wien-Bridge circuits where two elements must be tuned simultaneously to change frequency. Also, the output amplitude is relatively stable when the frequency is changed. An amp is used as a tuned circuit, driven by square wave from a voltage comparator. The frequency is controlled by R1, R2, C1, C2, and R3, with R3 used for tuning. Tuning the filter does not affect its gain or bandwidth, so the output amplitude does not change with frequency.

A comparator is fed with the sine-wave output to obtain a square wave. The square wave is then fed back to the input of the tuned circuit to cause oscillation. Zener diode, D1, stabilizes the amplitude of the square wave fed back to the filter input. Starting is insured by R6 and C5 which provide dc negative feedback around the comparator. This keeps the comparator in the active region. Distortion ranges between 0.75% and 2% depending on the setting of R3. Although greater tuning range can be accomplished by increasing the size of R3 beyond 1 K $\Omega$ , distortion becomes excessive. Decreasing R3 lower than 50  $\Omega$  can make the filter oscillate by itself.

### ASTABLE

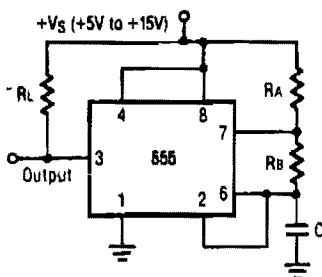

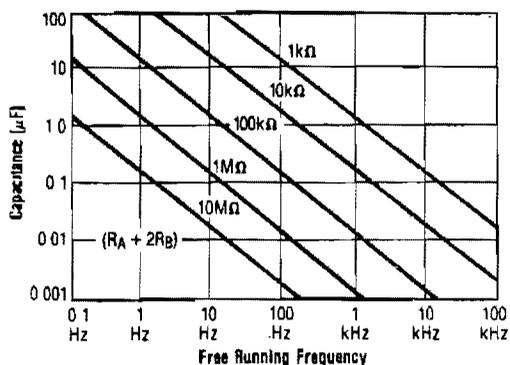
Free Running Frequency vs.  $R_A$ ,  $R_B$  and  $C$



Reprinted with permission from Raytheon Co., Semiconductor Division.


Fig. 38-19

## TWO-FUNCTION SIGNAL GENERATOR

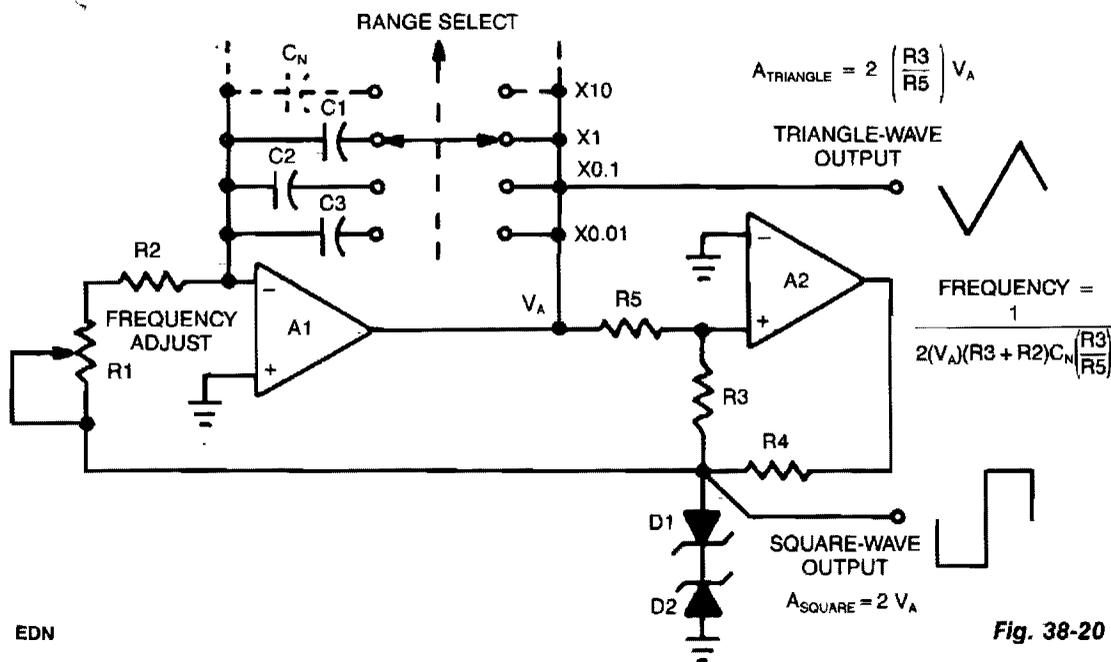


You can continuously vary the frequencies of the triangle and square waves produced by this circuit over a full decade. If  $R5 = R3$ , the amplitude of the two waveforms will be equal ( $A_{\text{SQUARE}} = A_{\text{TRIANGLE}}$ ).

## TRIANGLE GENERATOR

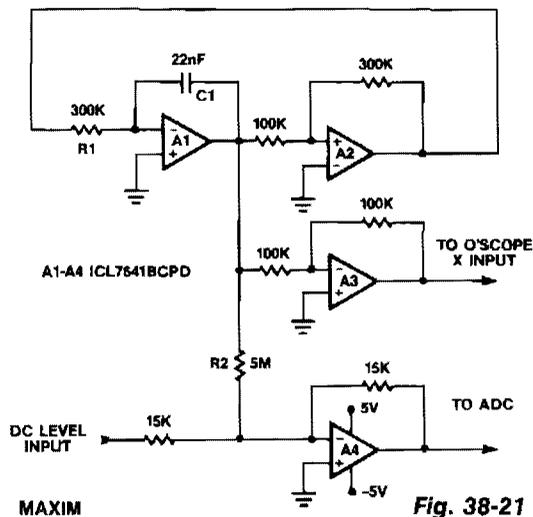


This circuit generates a symmetrical, 10-mV pk-pk triangle waveform which is summed with a dc level and connected to the a/d analog input for noise/DNL testing. The dc level input offsets the triangle waveform over the input range of the ADC. The 10-mV amplitude amounts to an 8 LSB span for a 12-bit, 5-V, full-scale ADC.

## MONOSTABLE OPERATION

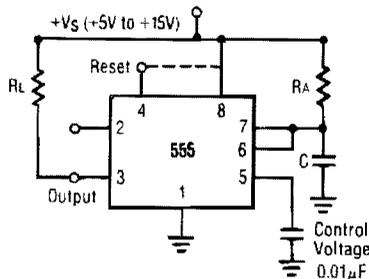

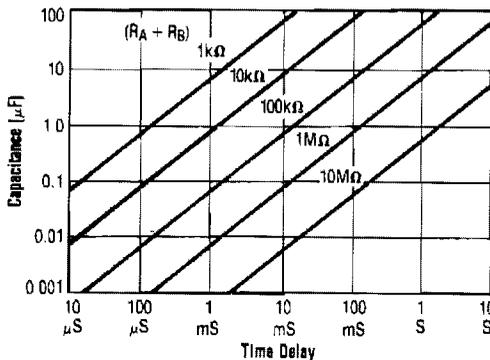**Time Delay vs.  $R_A$ ,  $R_B$  and  $C$**




Reprinted with permission from Raytheon Co., Semiconductor Division.

**Fig. 38-22**

In this mode, the timer functions as a one shot. The external capacitor is initially held discharged by a transistor internal to the timer. Applying a negative trigger pulse to pin 2 sets the flip-flop, driving the output high, and releasing the short circuit across the external capacitor. The voltage across the capacitor increases with the time constant  $\tau = R_A C$  to  $\frac{2}{3} V_S$ , where the comparator resets the flip-flop and discharges the external capacitor. The output is now in the low state.

Circuit triggering takes place when the negative-going trigger pulse reaches  $\frac{1}{3} V_S$ ; the circuit stays in the output high state until the set time elapses. The time the output remains in the high state is  $1.1 R_A C$  and can be determined by the graph. A negative pulse applied to pin 4 (reset) during the timing cycle will discharge the external capacitor and start the cycle over again beginning on the positive-going edge of the reset pulse. If reset function is not used, pin 4 should be connected to  $V_S$  to avoid false resetting.
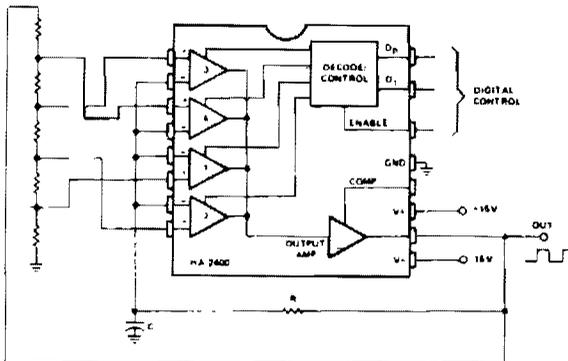
## PROGRAMMABLE-FREQUENCY, FREE-RUNNING MULTIVIBRATOR




HARRIS

**Fig. 38-23**

This is the simplest of any programmable oscillator circuit, since only one stable timing capacitor is required. The output square wave is about 25 V pk-pk, and has rise and fall times of about  $0.5 \mu\text{s}$ . If a programmable attenuator circuit is placed between the output and the divider network, 16 frequencies can be produced with two HA-200's and still only one timing capacitor.

## FUNCTION GENERATOR

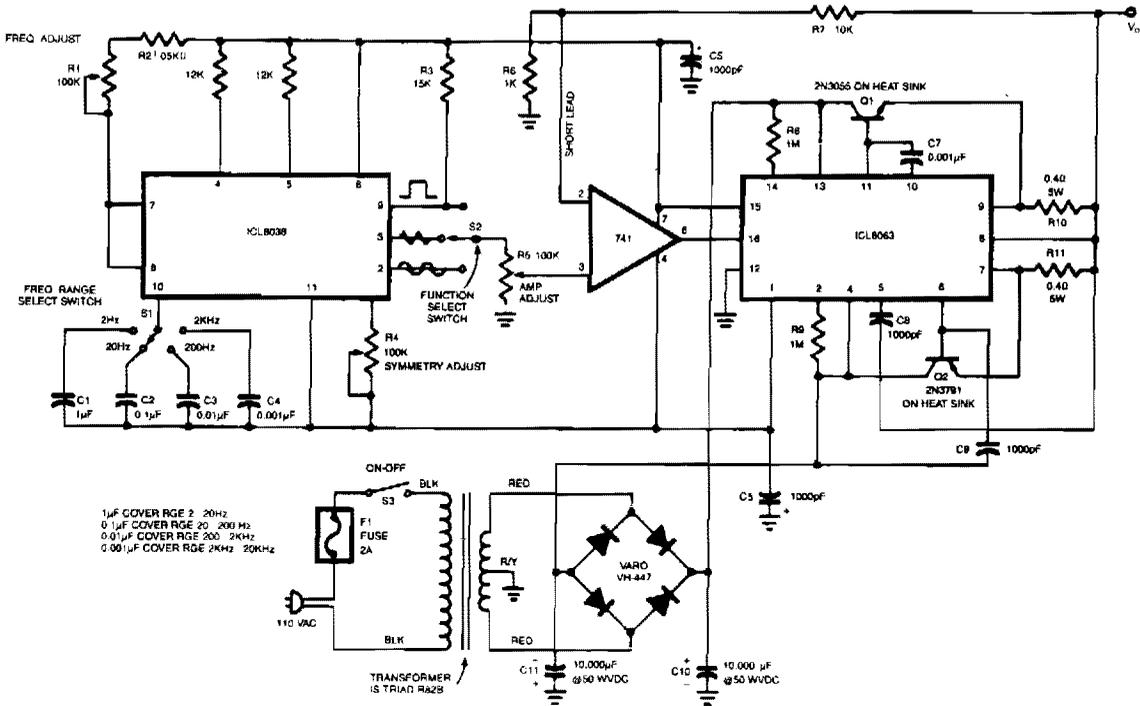


INTERSIL

Fig. 38-24

This generator will supply sine, triangular, and square waves from 2 Hz to 20 kHz. This complete test instrument can be plugged into a standard 110 Vac line for power.  $V_{OUT}$  will be up to  $\pm 25$  V (50 V pk-pk across loads as small as 10  $\Omega$  (about 2.5 A maximum output current).

Capacitor working voltages should be greater than 50 Vdc and all resistors should be  $\frac{1}{2}$  W, unless otherwise indicated. The interconnecting leads from the 741 pins 2 and 3 to their respective resistors should be kept short, less than 2 inches if possible; longer leads might result in oscillation. Full output swing is possible to about 5 kHz; after that the output begins to taper off because of the slew rate of the 741, until at 20 kHz the output swing will be about  $20 V_{pp} \pm 10$  V. This problem can be remedied by simply using an op amp with a higher slew rate, such as the LF356.

### PROGRAMMABLE-FREQUENCY ASTABLE

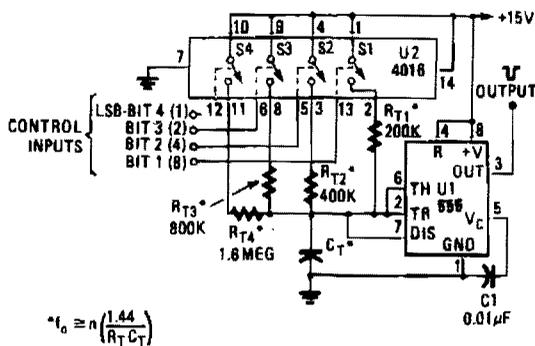


$$*f_o \approx n \left( \frac{1.44}{R_T C_T} \right)$$

WHERE,  
 n is DIGITAL INPUT WORD:  $1 < n < 15$   
 (AS SHOWN, WITH BASE  $R_T$  OF 1.8 MEG,  $100 \text{ Hz} < f_o < 1500 \text{ Hz}$ ).

POPULAR ELECTRONICS

Fig. 38-25

### LINEAR-RAMP MONOSTABLE

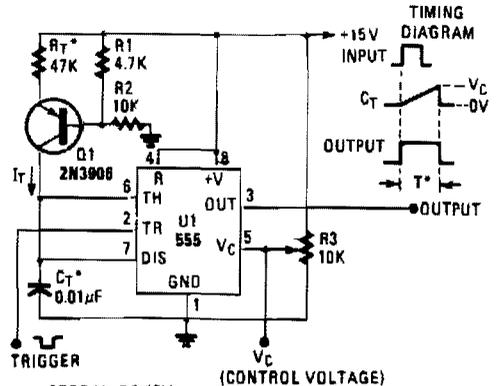


\*FOR  $V+$  OF 15V:  
 $T = \frac{V_C C_T}{I_T} \approx \frac{4.2}{R_T} T \approx 0.24 V_C R_T C_T$   
 (AS SHOWN,  $T_{MAX} \approx 1 \text{ MS}$  WITH  $V_C = 10V$ .)

HANDS-ON ELECTRONICS

Fig. 38-26

### LOW-FREQUENCY MULTIVIBRATOR

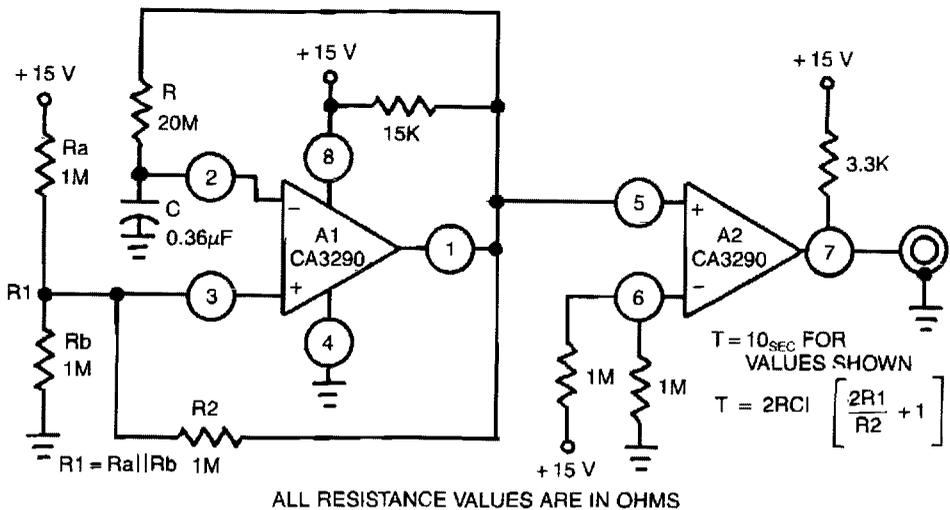


GE/RCA

Fig. 38-27

This circuit uses half the CA3290 BiMOS dual voltage comparator as conventional multivibrator. The second half maintains frequency against effects of output loading. Large values of timing resistor, R1, assure long time delays with low-leakage capacitors.

### RETRIGGERABLE ONE SHOT

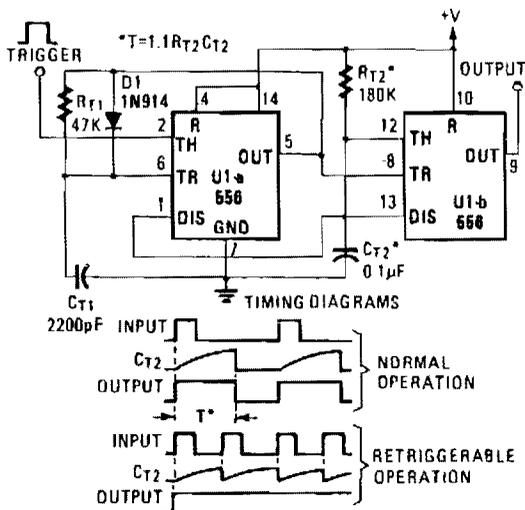

HANDS-ON ELECTRONICS

Fig. 38-28

### ASTABLE MULTIVIBRATOR

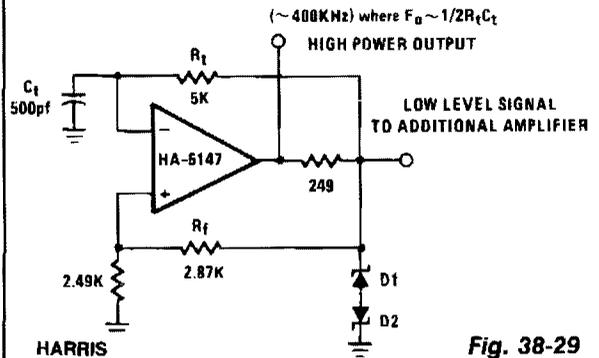


Fig. 38-29

The power bandwidth of the HA-5147 extends the circuit's frequency range to approximately 500 kHz.  $R_f$  can be made adjustable to vary the frequency if desired. Any timing errors because of  $V_{OS}$  or  $I_{bias}$  have been minimized by the precision characteristics of the HA-5147. D1 and D2, if used, should be matched to prevent additional timing errors. These clamping diodes can be omitted by tying  $R_f$  and positive feedback resistor  $R_f$  directly to the output.

### SINGLE-CONTROL FUNCTION GENERATOR

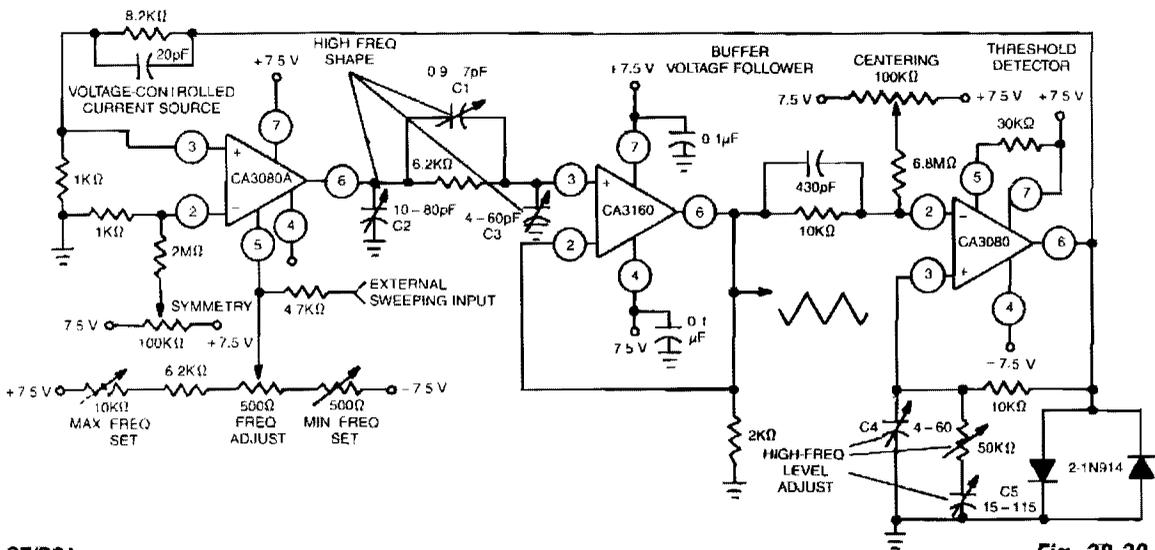



Fig. 38-30

GE/RCA

## SINGLE-CONTROL FUNCTION GENERATOR (Cont.)

This function generator, with an adjustment range in excess of 1,000,000 to 1, uses a CA3160 BiMOS op amp as a voltage follower, a CA3080 OTA as a high-speed comparator, and a CA3080 as a programmable-current source. Three variable capacitors, C1, C2, and C3 shape the triangular signal between 500 kHz and 1 MHz. Capacitors C4 and C5, and the trimmer potentiometer in series with C5, maintain essentially constant ( $\pm 10\%$ ) amplitude to 1 MHz.

### TRIANGLE-/SQUARE-WAVE GENERATOR

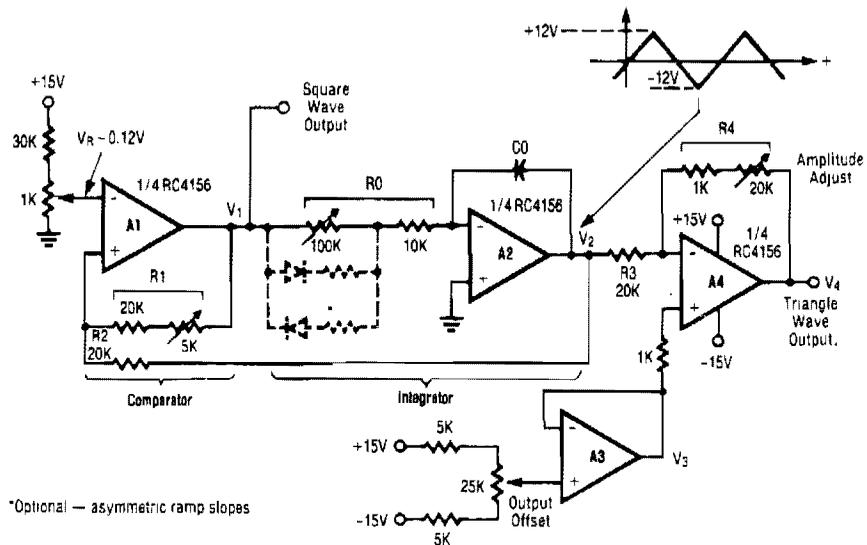


Reprinted with permission from Raytheon Co., Semiconductor Division.

Fig. 38-31

This circuit uses a positive-feedback loop closed around a combined comparator and integrator. When power is applied, the output of the comparator will switch to one of two states, to the maximum positive or maximum negative voltage. This applies a peak input signal to the integrator, and the integrator output will ramp either down or up, opposite of the input signal. When the integrator output, which is connected to the comparator input, reaches a threshold set by R1 and R2, the comparator will switch to the opposite polarity. This cycle will repeat endlessly, the integrator charging positive then negative, and the comparator switching in a square-wave fashion.




## WIDE-RANGE TUNABLE FUNCTION GENERATOR

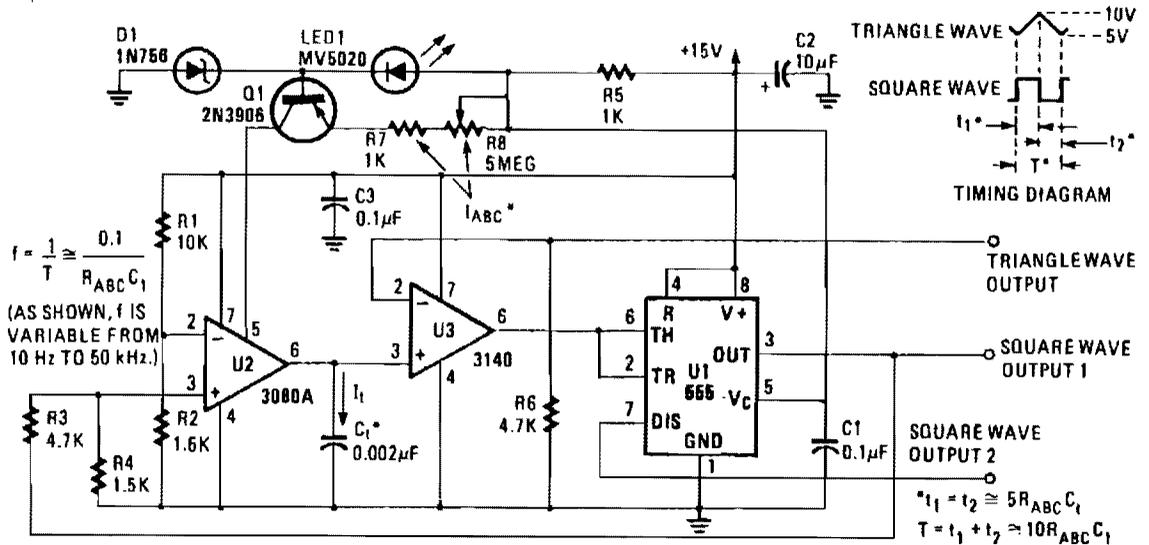

HANDS-ON ELECTRONICS

Fig. 38-34

## SAWTOOTH AND PULSE GENERATOR

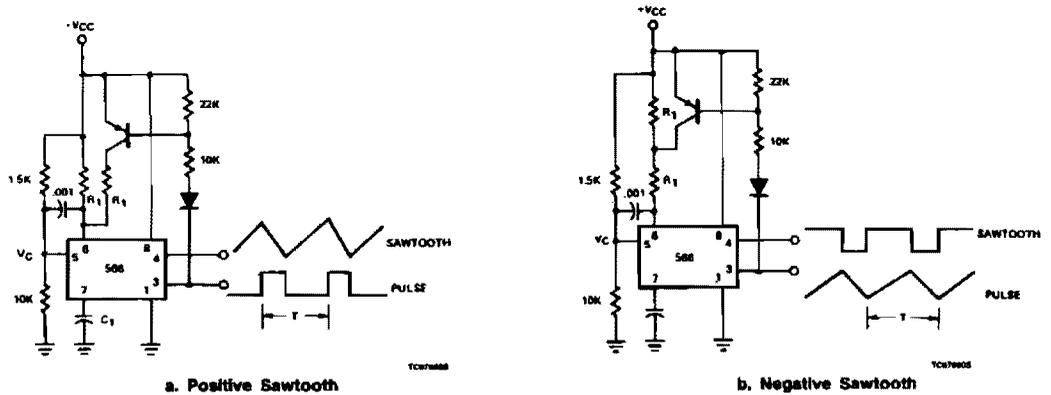

SIGNETICS


Fig. 38-35

The pin 3 output of the 556 can be used to provide different charge and discharge currents for  $C_1$  so that a sawtooth output is available at pin 4 and a pulse at pin 3. The pnp transistor should be well saturated to preserve good temperature stability. The charge and discharge times can be estimated by using the formula:

$$T = \frac{R_T C_1 V_{CC}}{5(V_{CC} - V_C)}$$

where  $R_T$  is the combined resistance between pin 6 and  $V_{CC}$  for the interval considered.
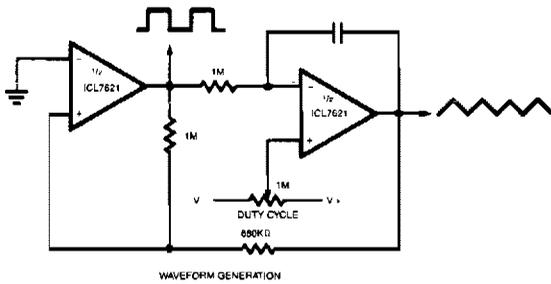
### PRECISE TRIANGLE-/ SQUARE-WAVE GENERATOR




INTERSIL

Fig. 38-36

Since the output range swings exactly from rail to rail, frequency and duty cycle are virtually independent of power supply variations.
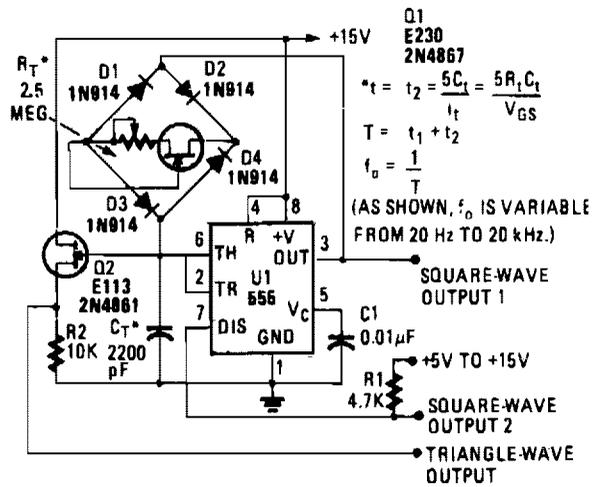
### WIDE-RANGE TRIANGLE-/ SQUARE-WAVE GENERATOR



HANDS-ON ELECTRONICS

Fig. 38-37

# 39

## Games

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Coin Flipper  
Who's First  
Electronic Dice

## COIN FLIPPER


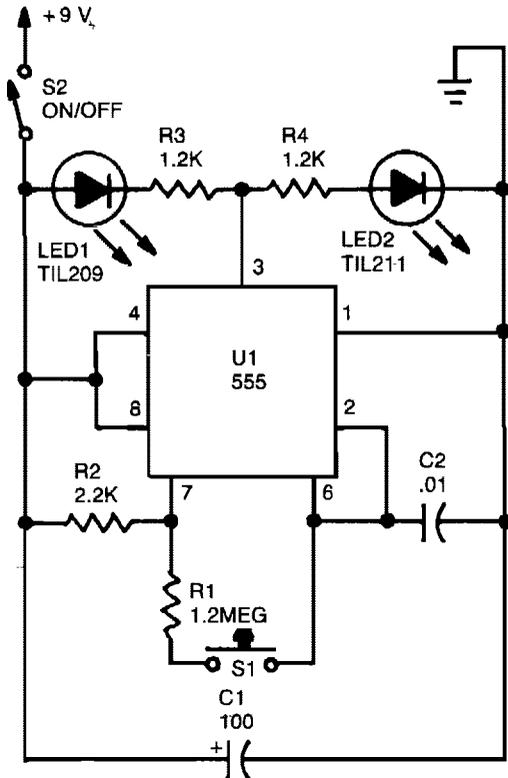


Fig. 39-1

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

## WHO'S FIRST

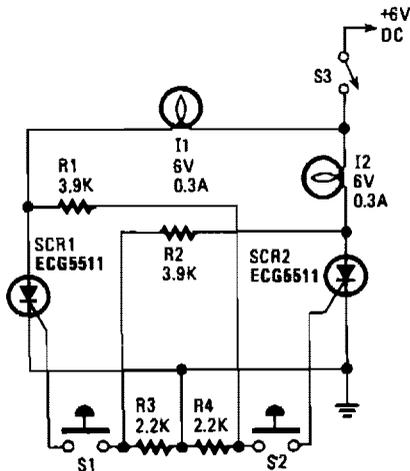


POPULAR ELECTRONICS

Fig. 39-2

The circuit is basically a 555 astable circuit that divides two LEDs, LED1 and LED2. LED2 is switched on when the output of U1 is high, and LED1 is activated when its output is low. When U1 oscillates, LED1 and LED2 switch on alternately as the output of U1 switches from state to state. Resistor R1's value is high in comparison to R2, so the waveform at the output is a square wave with a mark/space ratio of nearly one-to-one. When you release S1, you break the circuit and U1 latches whatever the output state happens to be at the time.

Using two SCRs, this control circuit is designed to lock out the other SCR when one has been triggered, so only one lamp will light. Indicator lamp I1 is controlled by SCR1. The operator simply presses switch S1. Lamp I2 is similarly controlled by S2 and SCR2. With both switches open, neither lamp is lit. The result is insufficient gate current to trigger SCR2 into conduction, so lamp I2 does not light. If S2 is pressed first, the reverse situation occurs. Once one of the SCRs is activated, it is necessary to open S3 to turn the light off.

## ELECTRONIC DICE

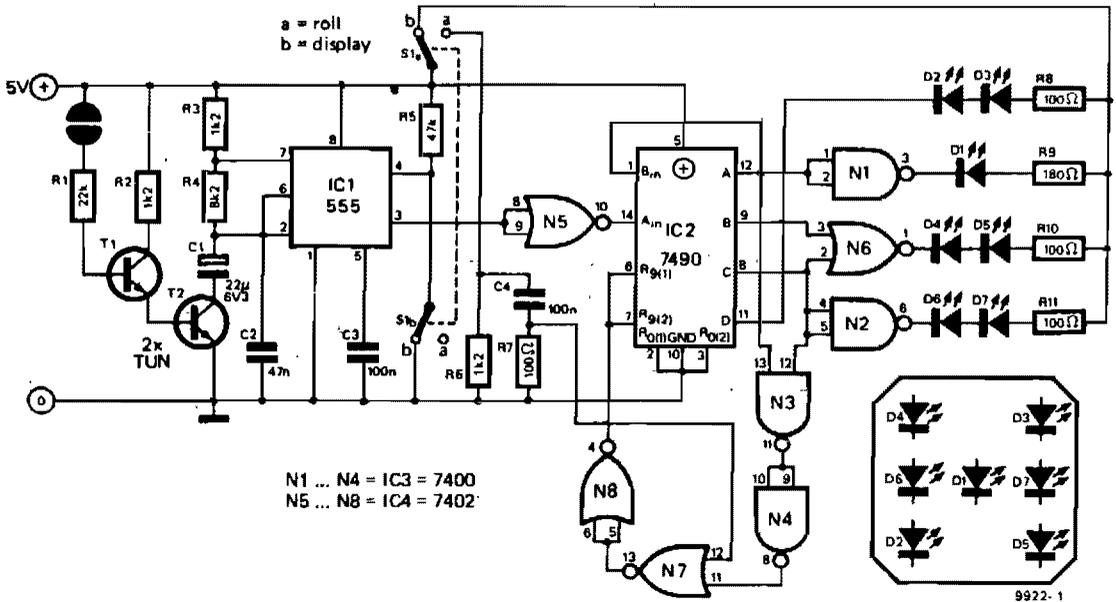

ELEKTOR

Fig. 39-3

The basic die circuit is given. A 555 timer, IC1, is connected as an astable multivibrator. This feeds clock pulses to divide-by-six counter IC2 the outputs of which are decoded by gates N1 to N6 to drive an array of LEDs in the familiar die pattern. When switch S1 is in position b, the reset input of IC1 decreases and the oscillator is inhibited. Power is fed to the LEDs via S1b so that the display is activated. When the die is *rolled* by switching S1 to position a, the display is blanked. C4 is connected to positive supply via S1a, producing a short pulse which resets IC2 via N7 and N8. The reset input of IC1 is pulled high via R5, so the multivibrator begins to oscillate and feeds clock pulses to IC2 via N5. When S1 is switched back to position a, the multivibrator is again inhibited. Then, the counter stops and power is applied to the LEDs which display the value of the *throw*.

# 40


## Gas and Smoke Detectors

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Smoke Detector	Gas/Smoke Detector
Furnace Exhaust Gas Temperature	Smoke Detector
Monitor with Low-Supply Detection	Smoke Detector
Methane Concentration Detector with	Gas/Smoke Detector
Linearized Output	SCR Smoke Alarm
Smoke/Gas/Vapor Detector	

## SMOKE DETECTOR

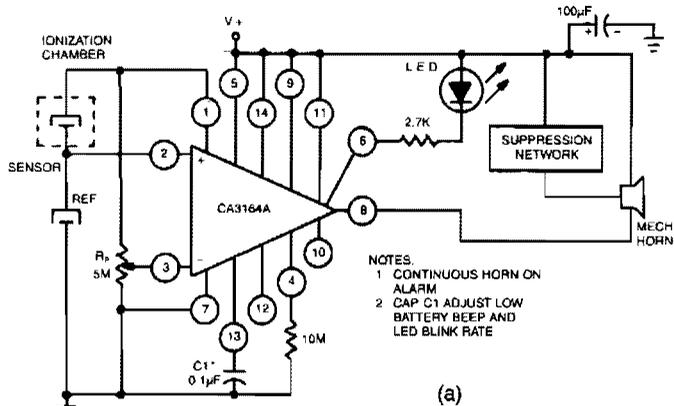

\* POLYCARBONATE OR EQUIVALENT INSULATION RESISTANCE > 10GΩ APPROX 1 nA LEAKAGE

ALL RESISTANCE VALUES ARE IN OHMS

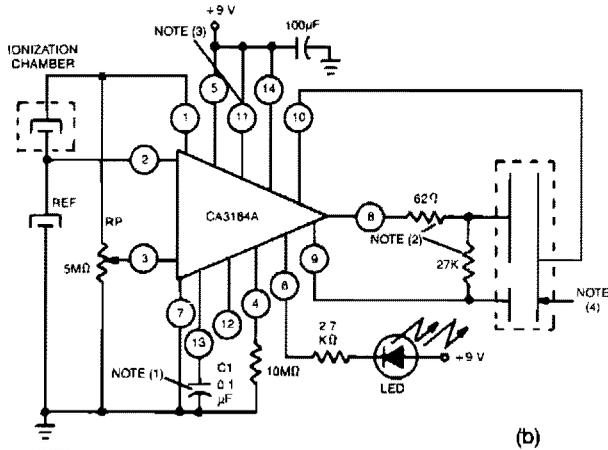

### NOTES


- (1) POLYCARBONATE OR EQUIVALENT INSULATION RESISTANCE > 10GΩ APPROXIMATELY 1 nA LEAKAGE
- (2) C1 ADJUSTS LOW BATTERY BEEP AND LED BLINK RATE
- (3) RESISTOR VALUES MAY VARY DEPENDING UPON THE PIEZO ELECTRIC HORN USED
- (4) CONTINUOUS HORN-ON ALARM AS SHOWN. FOR INTERMITTENT HORN SOUND, RETURN PIN 11 TO GROUND THROUGH 3.9 MΩ RESISTOR
- (5) TYPICAL PIEZO HORNS.  
GULTON #101FB  
LINDEN LABORATORIES #70048

GE/RCA


**Fig. 40-1**

Use CA3164A BiMOS detector/alarm system. For operation as smoke detector with electromechanical horn (Fig. 40-1a), the output of driver at terminal 8 is used. Large npn transistor Q3, with an active pull-up and transistor Q2 provide over 300 mA of drive current. For operation as a smoke detector with a piezoelectric horn (Fig. 40-1b), the circuit requires output from a second inverting amplifier at terminal 10, as well as the output from terminal 8.
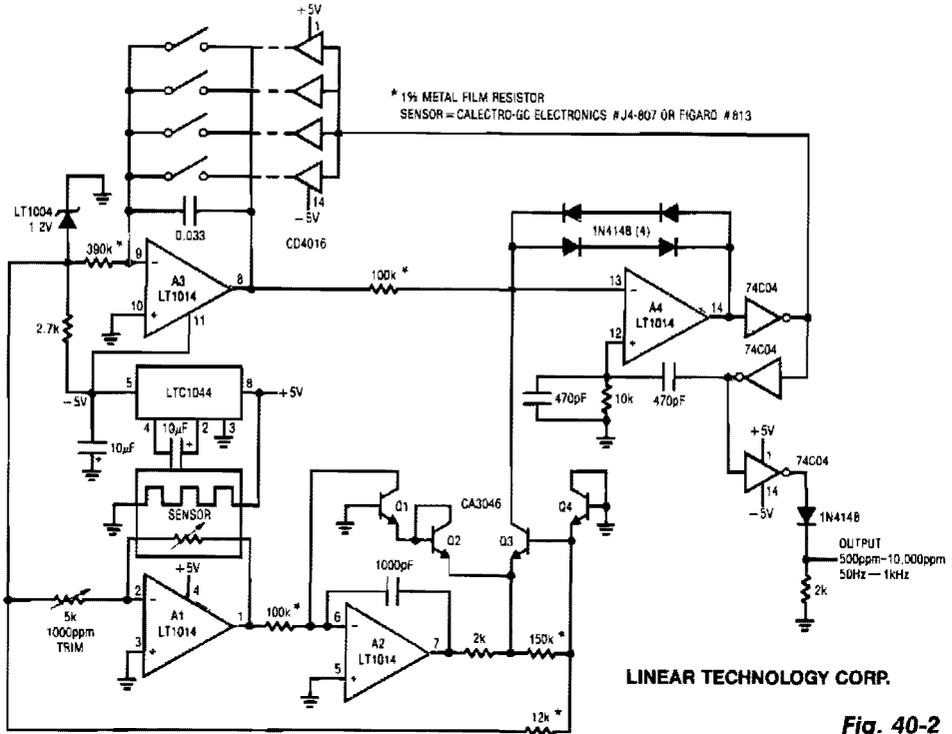
# METHANE CONCENTRATION DETECTOR WITH LINEARIZED OUTPUT




# SMOKE/GAS/VAPOR DETECTOR

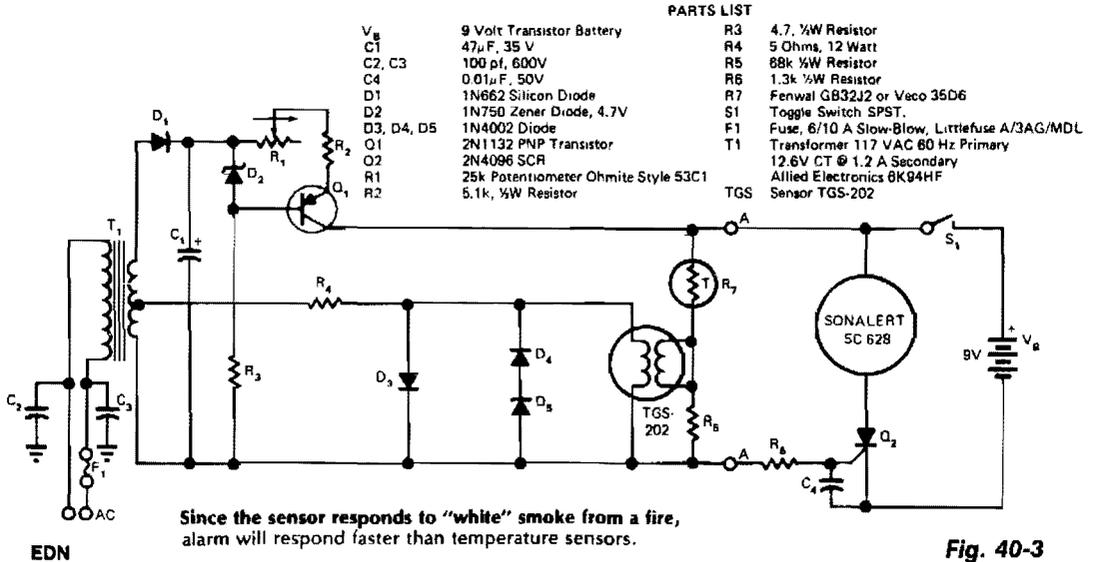

## SMOKE/GAS/VAPOR DETECTOR (Cont.)

Transformer T1 supplies power to the heater of the sensor. Since the sensor is fairly sensitive to heater voltage, diodes D3, D4, and D5 regulate the heater voltage. T1, together with D1 and C2, forms a dc power supply, whose current is regulated by Q1 and adjusted by R1. The constant current from Q1 feeds a variable resistance, consisting of thermistor R7 and the parallel combination of R5 and the sensor resistance. When a hazard causes the voltage at A-A to drop, the net voltage at the SCR gate turns positive, triggering the SCR on and operating the alarm. The alarm draws a small amount of current, so the battery will last a long time. Switch S1 turns off the alarm and resets the SCR.

### GAS/SMOKE DETECTOR

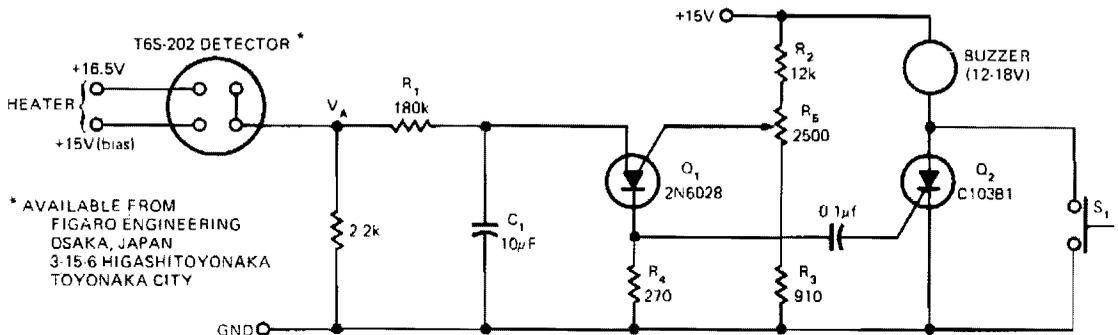


\* AVAILABLE FROM  
FIGARO ENGINEERING  
OSAKA, JAPAN  
3-15-6 HIGASHI TOYONAKA  
TOYONAKA CITY

EDN

Fig. 40-4

The sensor is based on the selective absorption of hydrocarbons by an n-type metal-oxide surface. The heater in the device serves to burn off the hydrocarbons once smoke or gas is no longer present in the immediate area; hence, the device is reusable. When initially turned on, a 15 minute warm-up period is required to reach equilibrium ( $V_A \cong 0.6$  V) in a hydrocarbon-free environment. When gas or smoke is introduced near the sensor,  $V_A$  will quickly rise (rate and final equilibrium depend on the type of gas and concentration) and trigger Q1, a programmable unijunction transistor. The voltage pulse generated across R4 triggers Q2, sounding the buzzer until S1 resets the unit. R1 and C1 give a time delay to prevent small transient waves of smoke, such as from a cigarette, from triggering the alarm. Triggering threshold is set by R5, R2, and R3; with the components shown, between 50 and 200 ppm of hydrocarbons can be easily detected. Since it is somewhat sensitive to heater voltage, a regulated supply should be used. Power requirements are 1.5 V at 500 mA for the heater and 15 V at 30 mA, depending on type of buzzer, for the bias supply.
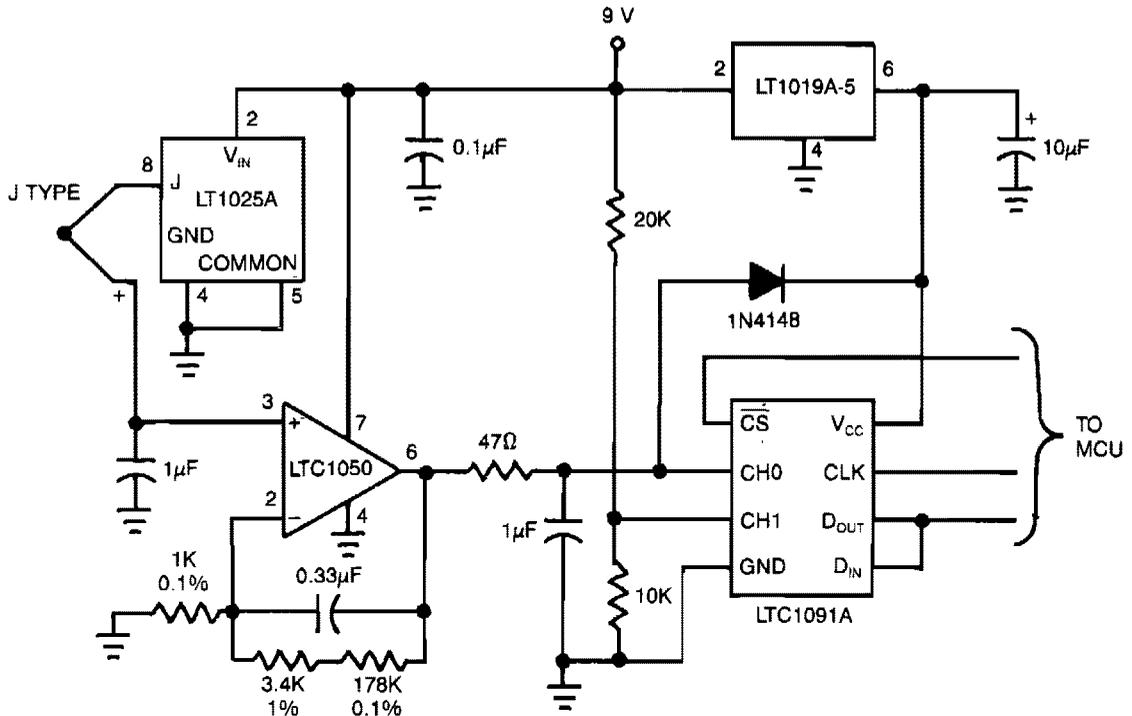
## FURNACE EXHAUST GAS TEMPERATURE MONITOR WITH LOW SUPPLY DETECTION




LINEAR TECHNOLOGY DESIGN NOTES

Fig. 40-5

This circuit can be used to measure exhaust gas temperature in a furnace. The 10-bit LTC1091A gives 0.5°C resolution over a 0°C to 500°C range. The LTC1050 amplifies and filters the thermocouple signal, the LT1025A provides cold junction compensation and the LT1019A provides an accurate reference. The J-type thermocouple characteristic is linearized digitally inside the MCU. Linear interpolation between known temperature points spaced 30°C apart introduces less than 0.1°C error. The 20-K/10 KΩ divider on CH1 of the LTC1091 provides low supply voltage detection. Remote location is easy, with data transferred from the MCU to the LTC1091 via the three-wire serial part.

## SMOKE DETECTOR

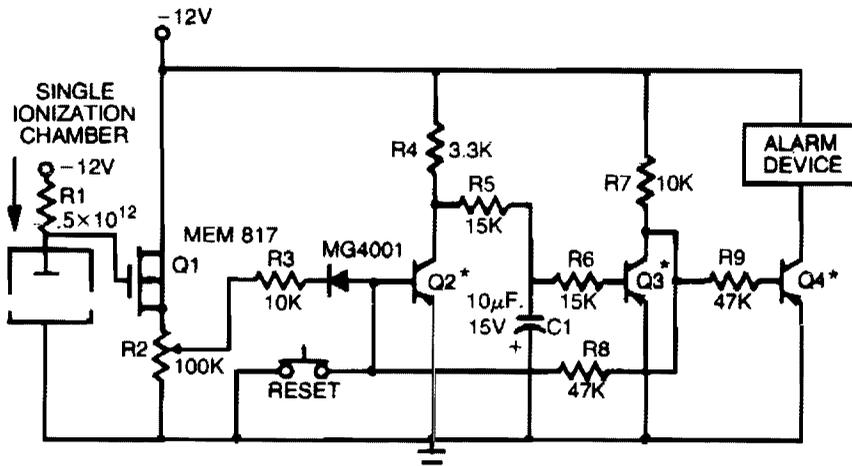


GENERAL INSTRUMENT MICROELECTRONICS

\*2N6076 or equivalent

Fig. 40-6

This smoke detector uses a MEM 817 p-channel enhancement mode MOSFET as its buffer amplifier. Operation of the sensor is based on a decrease in the current when smoke enters the chamber, thereby causing a negative voltage excursion at the gate of the buffer MOSFET. Quiescent voltage values at the output of the chamber vary from about  $-4\text{ V}$  to  $-6\text{ V}$ , and detection of smoke will result in an excursion of about  $-4\text{ V}$ . The MOSFET is connected as a source follower.


## SCR SMOKE ALARM

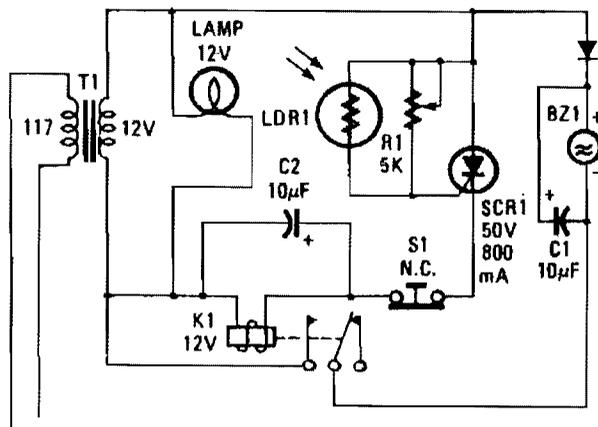

POPULAR ELECTRONICS

Fig. 40-7

## GAS/SMOKE DETECTOR

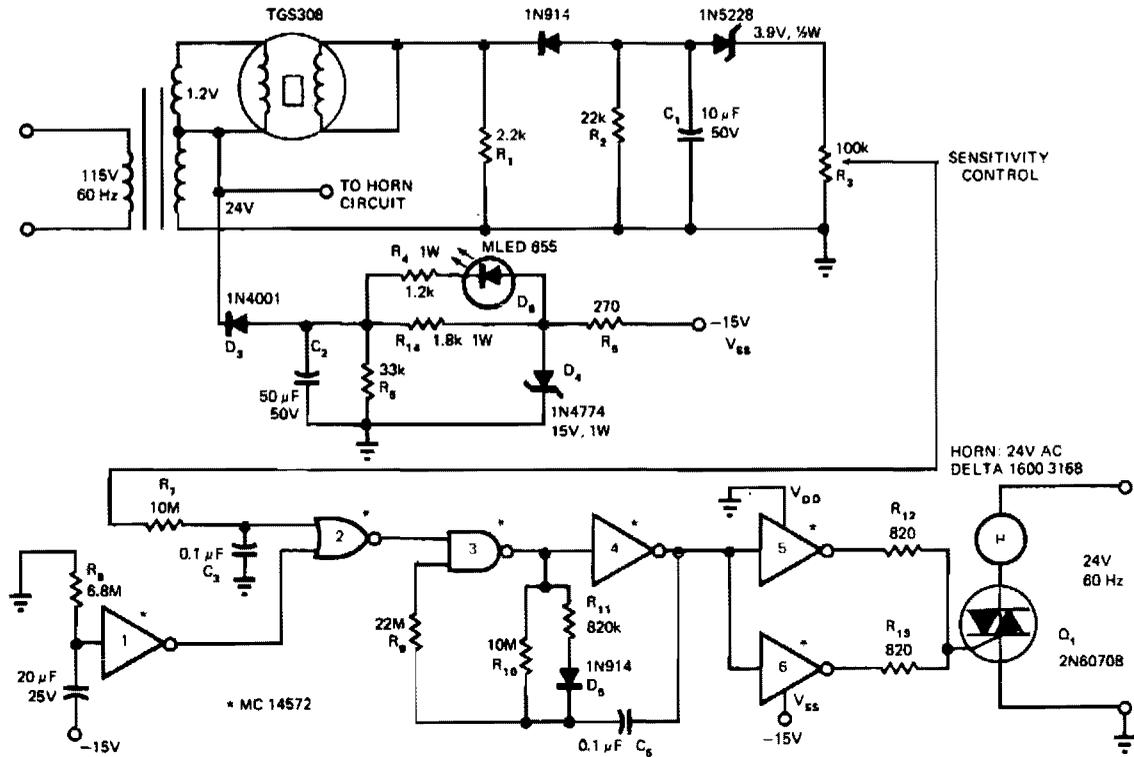


EDN

Fig. 40-8

In the presence of smoke or gas, the ac output voltage increases and becomes rectified, filtered and zener-diode coupled (D2 for thresholding) to sensitivity control R3. Under no gas condition, the output equals approximately 0 V (high). When gas is present, the output will be a negative value (low) sufficient to overcome the threshold of McMOS gate 2 and D2. The circuit shown uses a TGS 308 sensor, a general-purpose gas detector that is not sensitive to smoke or carbon monoxide. If smoke is the primary element to be detected, use the TGS 202 sensor. The two sensors are basically identical; the main differences lie in the heater voltage and the required warm up time delay. The TGS requires a 1.2 V heater and a 2 minute delay, whereas the TGS 202 requires 1.5 V and 5 minutes, respectively.

The system uses a McMOS gated oscillator directly interfacing with a triac-controlled ac horn. Using the MC14572 HEX functional gate, four inverters, one two-input NAND gate and one two-input NOR gate, the circuit provides the complete gas/smoke detector logic functions time delay, gated astable multivibrator control and buffers operation. The 24-Vac horn produces an 85/90-dB sound level output at a distance of 10 ft. Controlled by the astable multivibrator, the horn generates a pulsating alarm—a signal that may be advantageous over a continuous one in some noise environments.

## SMOKE DETECTOR

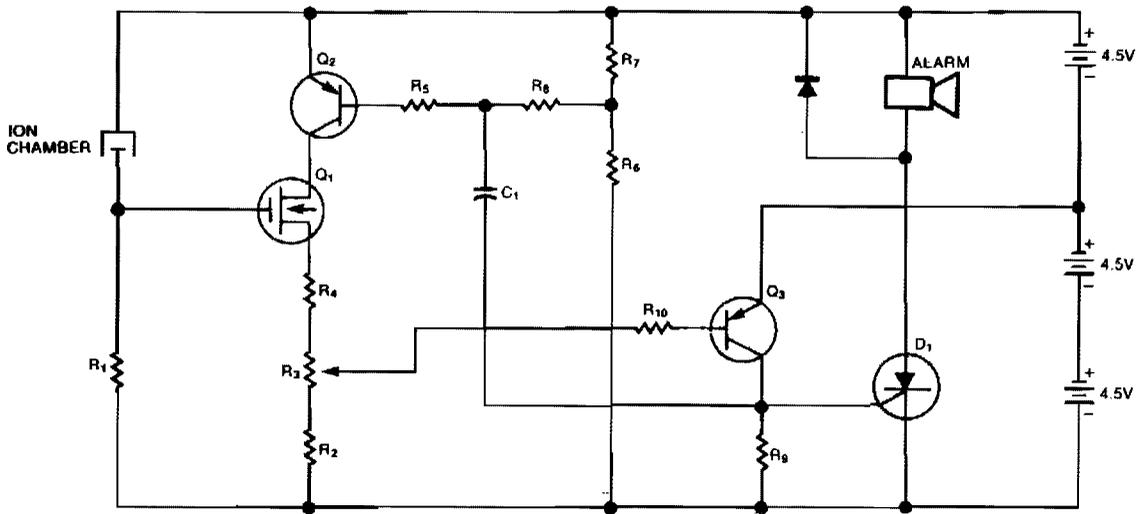

EDN

Fig. 40-9

This circuit comes from U.S. Patent 3,778,800, granted to BRK Electronics in Aurora, IL. The circuit provides a smoke detector with an alarm for both smoke and low batteries. The R6/R7 voltage divider monitors the battery and will turn Q2 and Q1 off when the battery voltage falls too low. The smoke-detector chamber will also cut Q1 off when it senses smoke. Q1 via Q3, triggers SCR D1 and sounds the alarm. Capacitor C1 provides feedback that causes the alarm to sound intermittently. The smoke detector and low-battery circuits sound the alarm at two different rates.

# 41


## Hall-Effect Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Current Monitor  
Security Door Ajar Alarm  
Hall-Effect Switches  
Hall-Effect Compass

## CURRENT MONITOR

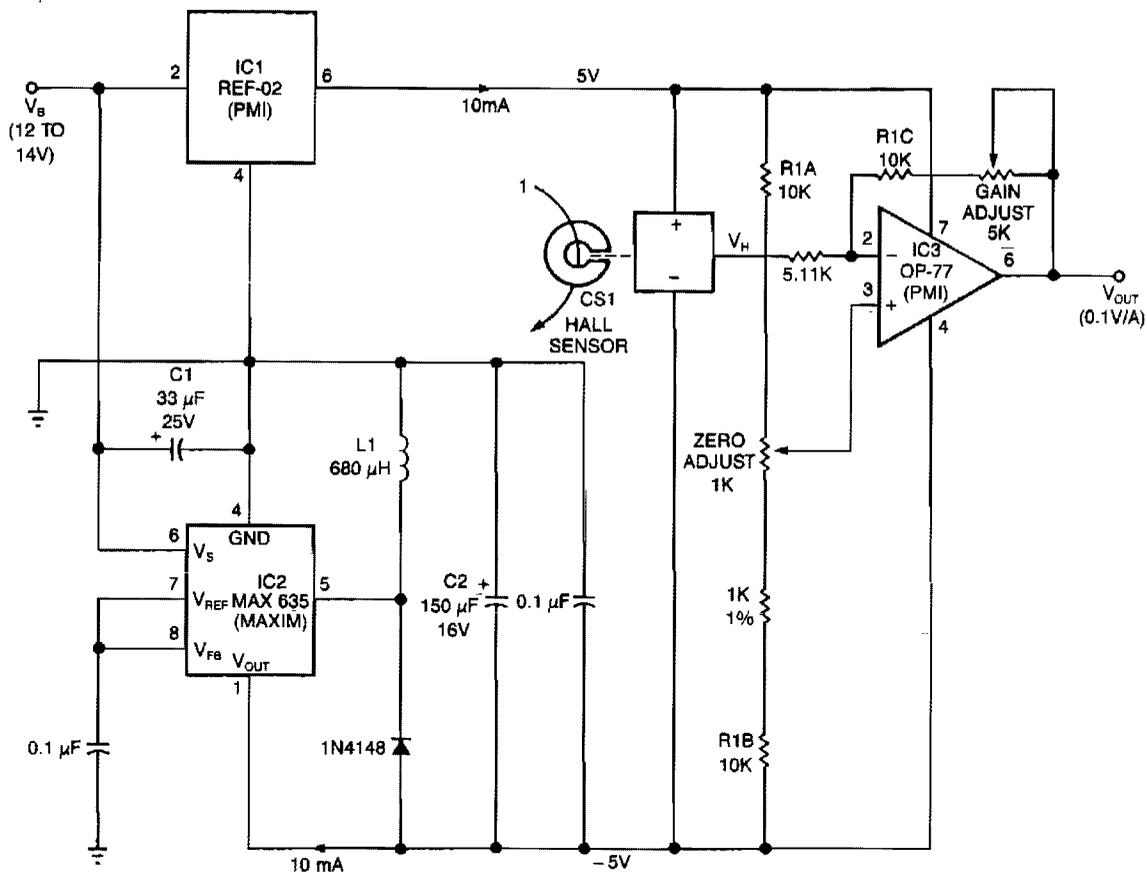

**NOTES:**

1. C1 AND C2 ARE 199D TANTALEX CAPACITORS FROM SPRAGUE
2. L1 IS A 6860-23 INDUCTOR FROM CADDELL-BURNS
3. R1A, R1B, AND R1C ARE PART OF A THIN-FILM RESISTOR NETWORK SUCH AS THE CADDOCK T914-10K.
4. CS1 IS A HALL-EFFECT CURRENT SENSOR (CSLA1CD) FROM MICROSWITCH.


EDN

**Fig. 41-1**

This circuit uses a Hall-effect sensor, consisting of an IC that resides in a small gap in a flux-collector toroid, to measure dc current in the range of 0 to 40 A. You wrap the current-carrying wire through the toroid; the Hall voltage  $V_H$  is then linearly proportional to current  $I$ . The current drain from  $V_B$  is less than 30 mA.

To monitor an automobile alternator's output current, for example, connect the car battery between the circuit's  $V_B$  terminal and ground, and wrap one turn of wire through the toroid. Or, you could wrap 10 turns—if they fit—to measure 1 A full scale. When  $I = 0$  V current sensor  $CS_1$ 's  $V_H$  output equals one-half of its 10 V bias voltage. Because regulators IC1 and IC2 provide a bipolar bias voltage,  $V_H$  and  $V_{OUT}$  are zero when  $I$  is zero; you can then adjust the output gain and offset to scale  $V_{OUT}$  at 1 V per 10 A.

## SECURITY DOOR AJAR ALARM

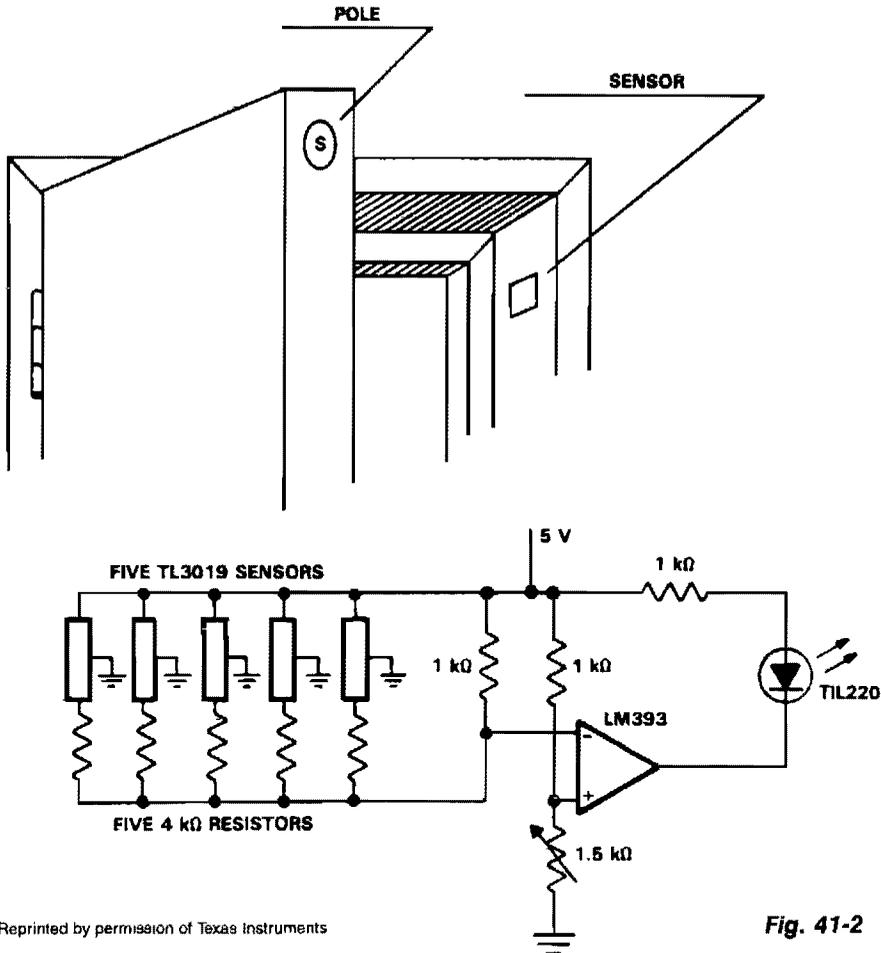


Reprinted by permission of Texas Instruments

Fig. 41-2

In operation, the TL3019 device will activate, or become low, when a south pole of a magnet comes near the chip face of the device. The example shows five doors. Each door has a magnet embedded in its edge with the south pole facing the outer surface. At the point where the magnet is positioned with the door closed, a TL3019 sensor is placed in the door jamb. With the door closed, the Hall devices will be in a logic low state. This design has five doors and uses five TL3019 devices. Each TL3019 has a 4-K $\Omega$  resistor in series and all door sensor and resistor sets are in parallel and connected to the inverting input of an LM393 comparator. With all doors closed, the effective resistance will be about 800  $\Omega$  and produce 2.2 V at the inverting input. The noninverting input goes to a voltage divider network which sets the reference voltage. The 1.5-K $\Omega$  potentiometer is adjusted so the indicator goes out with all doors closed. This will cause 2.35 V to appear at the noninverting input of the comparator. When a door opens, the voltage at the inverting input will go to 2.5 V which is greater than  $V_{REF}$ , and the LED will light. A large number of doors and windows can be monitored with this type of circuit. Also, it could be expanded to add an audible alarm in addition to the visual LED.

## HALL-EFFECT SWITCHES

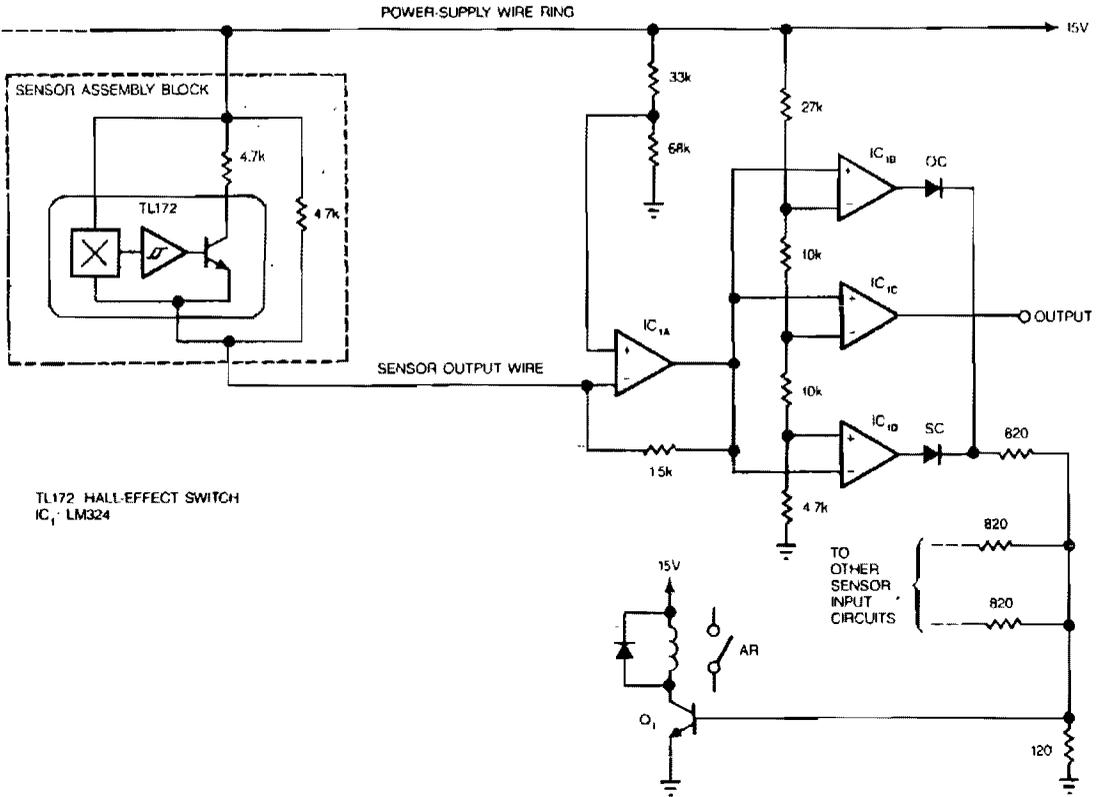

EDN

Fig. 41-3

Hall-effect switches have several advantages over mechanical and optically coupled switches. They're insensitive to environmental light and dirt, they don't bind, and they don't sustain mechanical wear. Their major drawback is that they require three wires per device. The circuit shown, however, reduces this wire count to  $N + 1$  wires for  $N$  devices.

Amplifier **IC<sub>1A</sub>** is configured as a current-to-voltage converter. It senses the sensor assembly's output current. When the Hall-effect switch is actuated, the sensor's output current increases to twice its quiescent value. Amplifier **IC<sub>1B</sub>**, configured as a comparator, detects this increase. The comparator's output decreases when the Hall-effect switch turns on.

The circuit also contains a fault-detection function. If any sensor output wire is open, its corresponding LED will turn on. If the power-supply line opens, several LEDs will turn on. A short circuit will also turn an LED on. Every time an LED turns on, **Q<sub>1</sub>** turns on and the alarm relay is actuated.

---

## HALL-EFFECT COMPASS

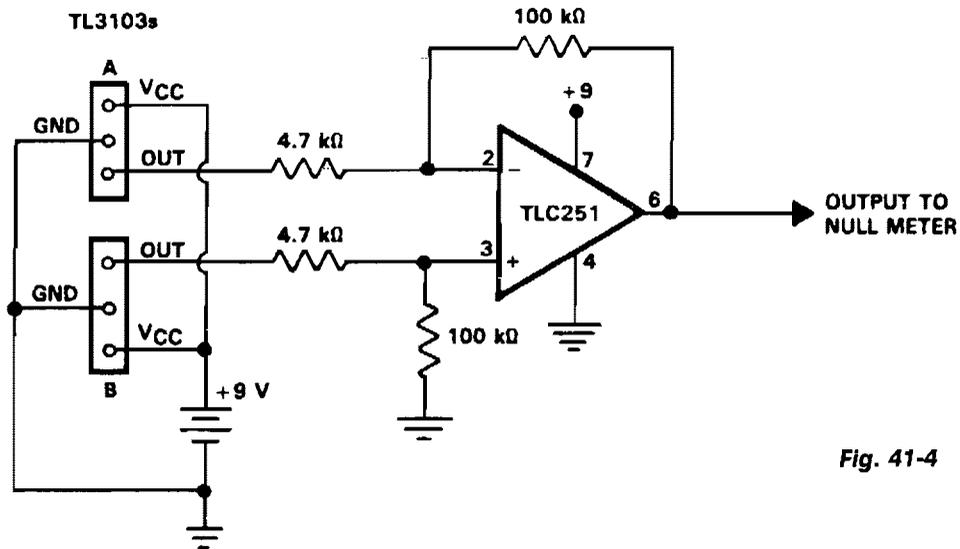


Fig. 41-4

Reprinted by permission of Texas Instruments.

The TL3103 linear Hall-effect device can be used as a compass. By definition, the north pole of a magnet is the pole that is attracted by the magnetic north pole of the earth. The north pole of a magnet repels the north-seeking pole of a compass. By convention, lines of flux emanate from the north pole of a magnet and enter the south pole. The circuit of the compass is shown. By using two TL3103 devices instead of one, we achieve twice the sensi-

tivity. With each device facing the opposite direction, device A would have a positive output while the output of device B would be negative with respect to the zero magnetic field level. This gives a differential signal to apply to the TLC251 op amp. The op amp is connected as a difference amplifier with a gain of 20. Its output is applied to a null meter or a bridge balance indicator circuit.

# 42

## High-Frequency Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

2 – 30 MHz 140-W (PEP) Amateur  
Radio Linear Amplifier

80-W (PEP) 3 – 30 MHz 12.5 – 13.6 V  
Amplifier

29-MHz Amplifier

28-dB Noninverting Amplifier


Wideband UHF Amplifier with  
High-Performance FETs

Broadcast Band Rf Amplifier

Miniature Wideband Amplifier

Wideband 500 kHz – 1 GHz Hybrid  
Amplifier
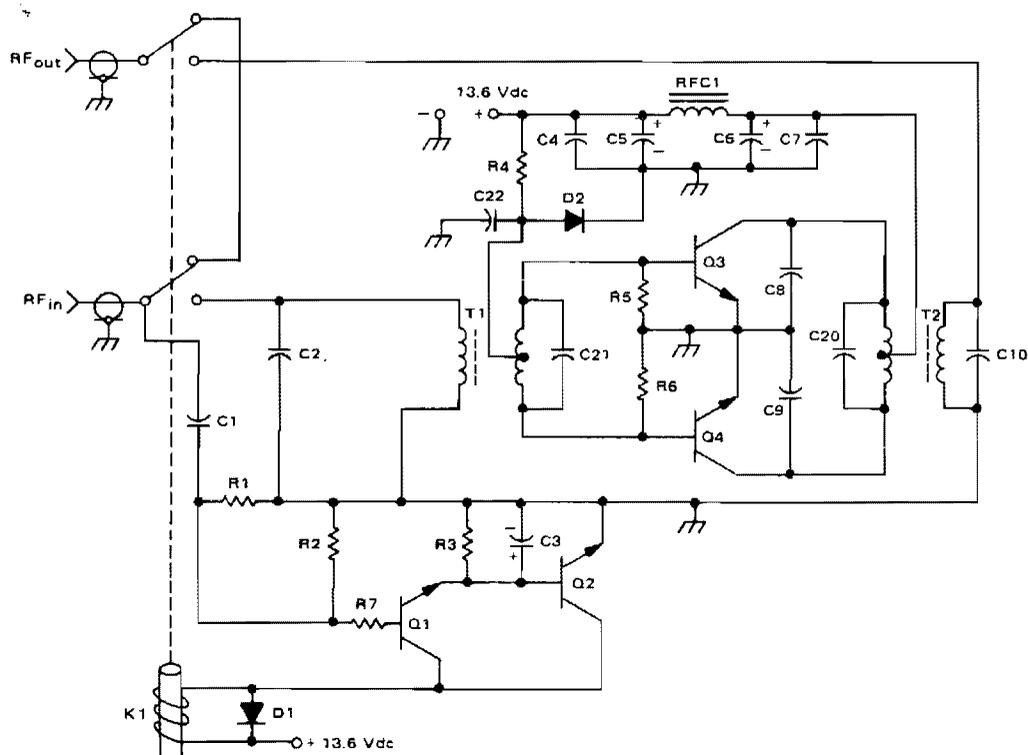
## 2 – 30 MHz 140-W (PEP) AMATEUR RADIO LINEAR AMPLIFIER




- |       |  |        |  |
|-------|--|--------|--|
| C1    | = 33 pF Dipped Mica  | R7     | = 100 $\Omega$ 1/4 W Resistor                            |
| C2    | = 18 pF Dipped Mica  | RFC1   | = 9 Ferrocube Beads on #18 AWG Wire                      |
| C3    | = 10 $\mu$ F 35 Vdc for AM operation,<br>100 $\mu$ F 35 Vdc for SSB operation. | D1     | = 1N4001   |
| C4    | = .1 $\mu$ F Erie  | D2     | = 1N4997   |
| C5    | = 10 $\mu$ F 35 Vdc Electrolytic   | Q1, Q2 | = 2N4401   |
| C6    | = 1 $\mu$ F Tantalum   | Q3, 4  | = MRF454   |
| C7    | = .001 $\mu$ F Erie Disc   | T1, T2 | = 16:1 Transformers                                      |
| C8, 9 | = 330 pF Dipped Mica   | C20    | = 910 pF Dipped Mica                                     |
| R1    | = 100 k $\Omega$ 1/4 W Resistor  | C21    | = 1100 pF Dipped Mica                                    |
| R2, 3 | = 10 k $\Omega$ 1/4 W Resistor   | C10    | = 24 pF Dipped Mica                                      |
| R4    | = 33 $\Omega$ 5 W Wire Wound Resistor  | C22    | = 500 $\mu$ F 3 Vdc Electrolytic                         |
| R5, 6 | = 10 $\Omega$ 1/2 W Resistor   | K1     | = Potter & Brumfield<br>KT11A 12 Vdc Relay or Equivalent |

Copyright of Motorola, Inc. Used by permission.

**Fig. 42-1**

The amplifier operates across the 2 – 30 MHz band with relatively flat gain response and reaches gain saturation at approximately 210 W of output power. Both input and output transformers are 4:1 turns ratio (16:1 impedance ratio) to achieve low input SWR across the specified band and a high saturation capability. When using this design, it is important to interconnect the ground plane on the bottom of the board to the top, especially at the emitters of the MRF454s.
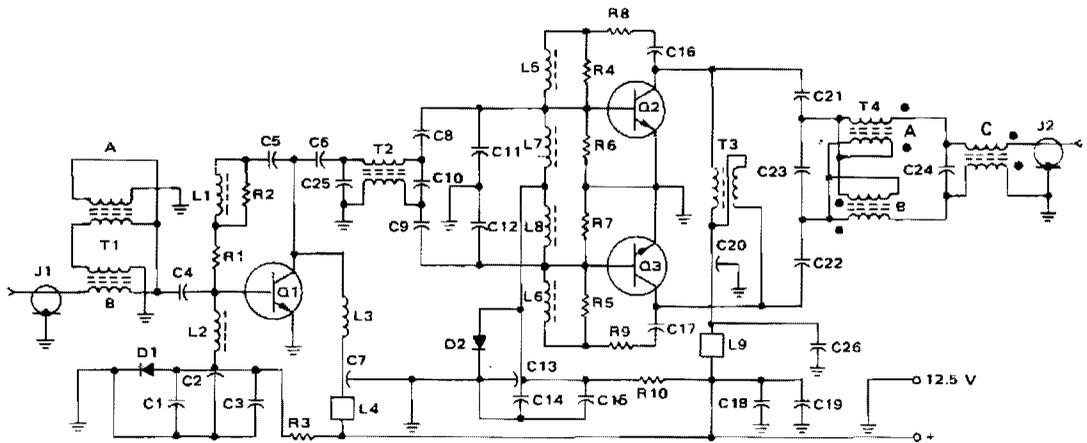
## 80-W (PEP) 3 – 30 MHz 12.5 – 13.6 V AMPLIFIER



- C1, C14, C18 – 0.1  $\mu\text{F}$  ceramic.
- C2, C7, C13, C20 – 0.001  $\mu\text{F}$  feed through.
- C3 – 100  $\mu\text{F}/3\text{V}$
- C4, C6 – 0.033  $\mu\text{F}$  mylar
- C5 – 0.0047  $\mu\text{F}$  mylar.
- C8, C9 – 0.015 and 0.033  $\mu\text{F}$  mylars in parallel
- C10 – 470 pF mica.
- C11, C12 – 560 pF mica.
- C15 – 1000  $\mu\text{F}/3\text{V}$
- C16, C17 – 0.015  $\mu\text{F}$  mylar
- C19 – 10 pF 15 V
- C21, C22 – two 0.068  $\mu\text{F}$  mylars in parallel.
- C23 – 330 pF mica
- C24 – 39 pF mica
- C25 – 680 pF mica
- C26 – .01  $\mu\text{F}$  ceramic

- R1, R6, R7 – 10  $\Omega$ , 1/2 W carbon
- R2 – 51  $\Omega$ , 1/2 W carbon
- R3 – 240  $\Omega$ , 1 W wire W
- R4, R5 – 18  $\Omega$ , 1 W carbon
- RB, R9 – 27  $\Omega$ , 2 W carbon
- R10 – 33  $\Omega$ , 6 W wire W

- L1 – 0.22  $\mu\text{H}$  molded choke
- L2, L7, L8 – 10  $\mu\text{H}$  molded choke
- L5, L6 – 0.15  $\mu\text{H}$
- L3 – 25 t, #26 wire, wound on a 100  $\Omega$ , 2 W resistor. (1.0  $\mu\text{H}$ )
- L4, L9 – 3 ferrite beads each.

T1 – 2 twisted pairs of #26 wire, 8 twists per inch. A = 4 turns, B = 8 turns. Core - Stack pole 57-9322-11, Indiana General F627-8Q1 or equivalent

T2 – 2 twisted pairs of #24 wire, 8 twists per inch, 6 turns. (Core as above.)

T3 – 2 twisted pairs of #20 wire, 6 twists per inch, 4 turns. (Core as above.)

T4 – A and B = 2 twisted pairs of #24 wire, 8 twists per inch, 5 turns each. C = 1 twisted pair of #24 wire, 8 turns. Core - Stack pole 57-9074-11, Indiana General F624-19Q1 or equivalent

Q1 – 2N6367  
Q2, Q3 – 2N6368

D1 – 1N4001  
D2 – 1N4997


J1, J2 – BNC connectors

Copyright of Motorola, Inc. Used by permission.

**Fig. 42-2**

This amplifier utilizes a 2N6367 and a pair of 2N6368 transistors. The 2N6367 transistor is employed as a driver and is specified for up to 9 W (PEP) output. In the amplifier design the driver must supply on 5 W (PEP) at 30 MHz with a resulting IMD performance of about  $-37$  to  $-38$  dB. At lower operating frequencies, drive requirements drop to the 2 – 3 W (PEP) range and IMD performance improves to better than 40 dB. Two 2N6368 transistors are employed in the final stage of the transmitter design in a push-pull configuration. These devices are rated at 40 W (PEP) and  $-30$  dB maximum IMD, although  $-35$  dB performance is more typical for narrowband operation. Without frequency compensation, the completed amplifier can deliver 90 W (PEP) in the 25 – 30 MHz band with IMD performance down  $-30$  dB. If only the power amplifier stage is frequency compensated, 95 W (PEP) can be obtained at 6 – 10 MHz.


## 29-MHz AMPLIFIER

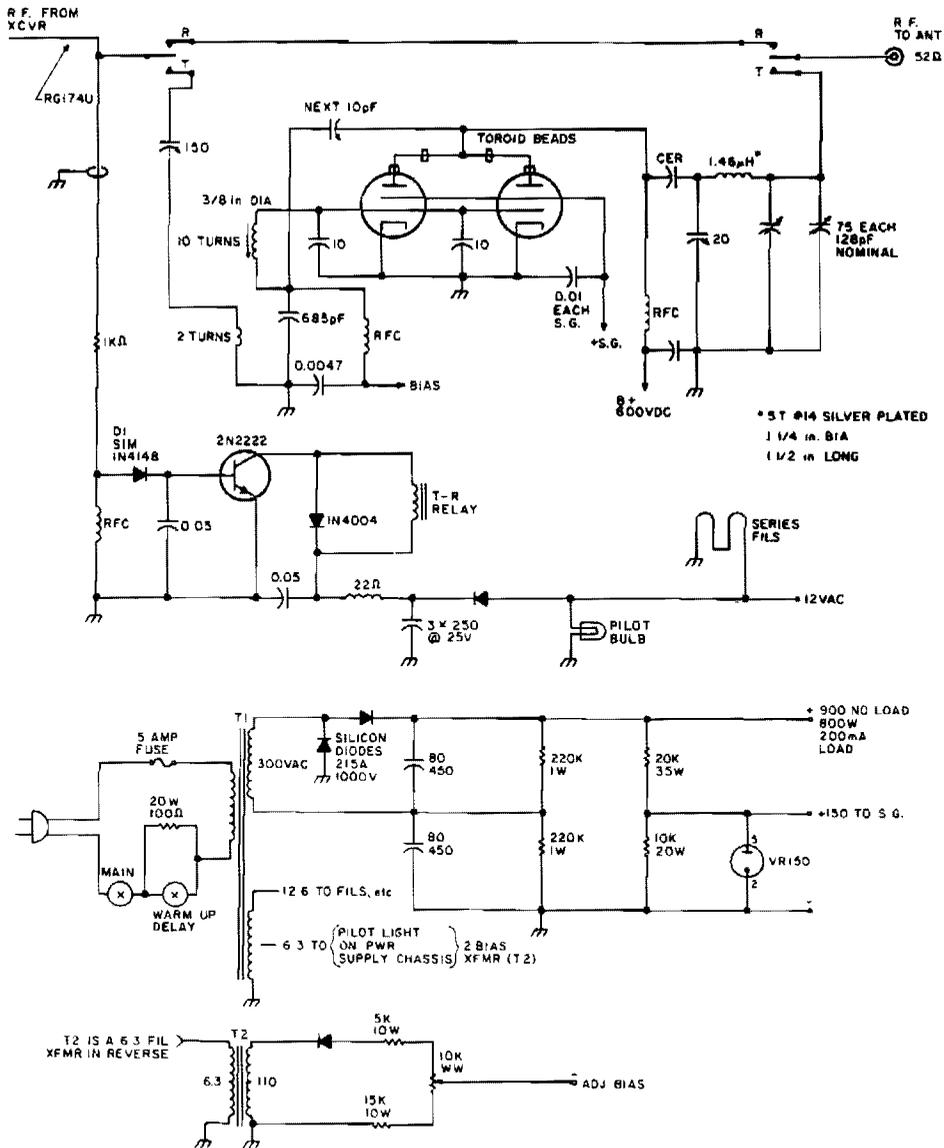

**Fig. 42-3**

The only adjustments that require close attention are input, output, and neutralization. The 150-pF capacitor in the input line compensates for impedance mismatch. You tune for maximum signal transfer from exiter to final with an in-line meter or external field strength meter. The final is a conventional pi network. When neutralized, the plate current dip should be at about the same setting of the 20-pF plate capacitor as maximum output. Adjust bias to let tubes idle at about 30 mA.

## 28-dB NONINVERTING AMPLIFIER

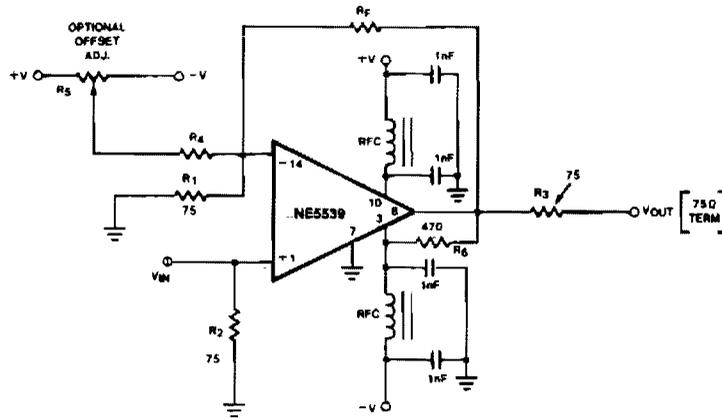

TC087405


**NOTES:**

- R<sub>1</sub> = 75Ω 5% CARBON
- R<sub>2</sub> = 75Ω 5% CARBON
- R<sub>3</sub> = 75Ω 5% CARBON
- R<sub>4</sub> = 38k 5% CARBON

- R<sub>5</sub> = 20k TRIMPOT (CERMET)
- R<sub>F</sub> = 1.5k (28dB GAIN)
- R<sub>6</sub> = 470Ω 5% CARBON


- RFC 3T # 26 BUSS WIRE ON FERROXCUBE VK 200 09/3B CORE
- BYPASS CAPACITORS 1nF CERAMIC (MEPCO OR EQUIV.)

**Top Plane Copper<sup>1</sup>  
(Component Side)**

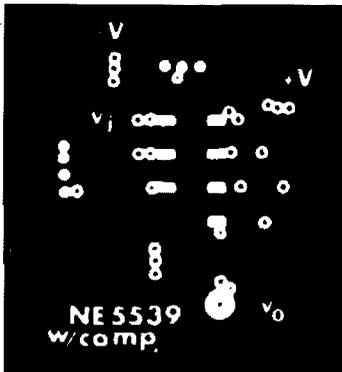


DF089105

**Component Side  
(Component Layout)**

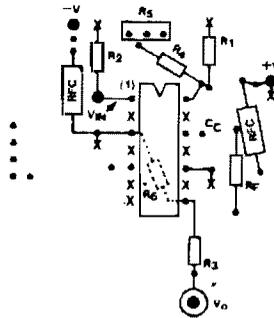

DF089205

**Bottom Plane  
Copper<sup>1</sup>**

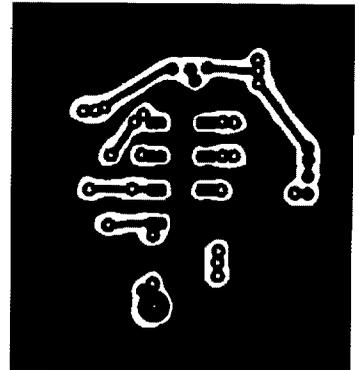

DF089305

**NOTES:**

- (X) indicates ground connection to top plane.
- \*R<sub>5</sub> is on bottom side

**NOTE:**


- <sup>1</sup> Bond edges of top and bottom ground plane copper.

**SIGNETICS**

**Fig. 42-4**

The physical circuit layout is extremely critical. Breadboarding is not recommended. A double-sided copper-clad printed circuit board will result in more favorable system operation.
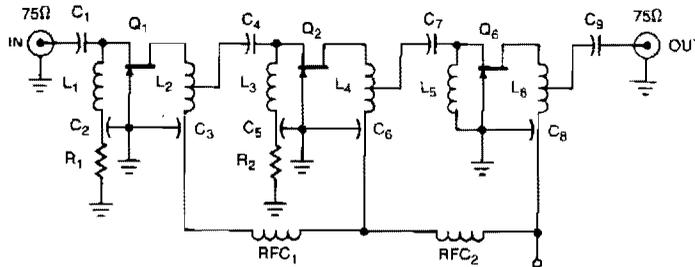
## WIDEBAND UHF AMPLIFIER WITH HIGH-PERFORMANCE FETS




$C_1, C_4, C_7, C_9 = 68 \text{ pF}$        $L_1, L_3, L_5 = 120 \text{ nH}$        $V_D = +20\text{V}$   
 $C_2, C_5 = 500 \text{ pF}$              $L_2, L_4, L_6 = 222 \text{ nH}$   
 $C_3, C_6, C_8 = 1000 \text{ pF}$        $\text{RFC}_1, \text{RFC}_2 = 2.2 \text{ nH}$   
 $Q_1, Q_2, Q_3 = \text{Siliconix U310}$      $R_1, R_2 = 51\Omega$

**SILICONIX**

**Fig. 42-5**

The amplifier circuit is designed for a 225 MHz center frequency, 1 dB bandwidth of 50 MHz, low-input VSWR in a 75-Ω system, and 24 dB gain. Three stages of U310 FETs are used, in a straight-forward design.

## BROADCAST BAND RF AMPLIFIER

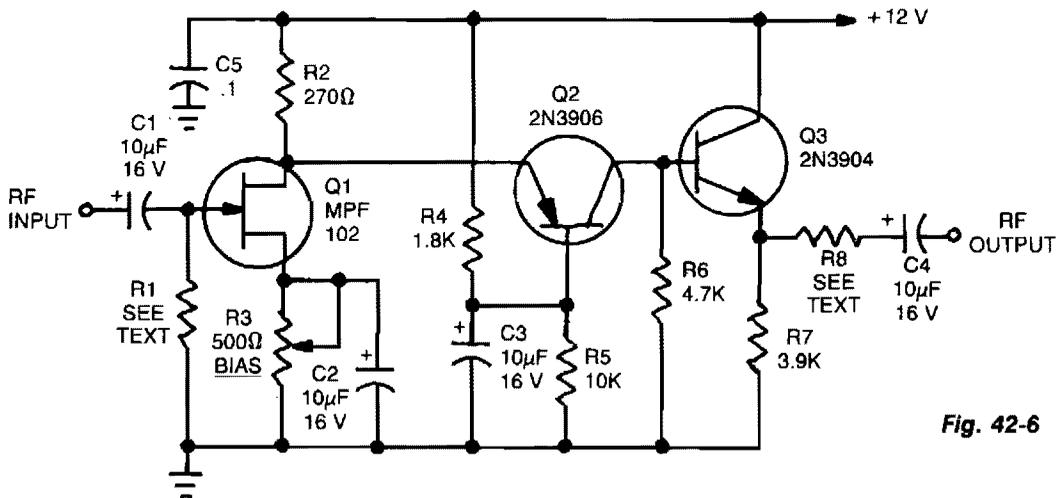


**Fig. 42-6**

Reprinted with permission of Radio-Electronics Magazine, 1989 R-E Experimenters Handbook. Copyright Gernsback Publications, Inc., 1989.

The circuit has a frequency response ranging from 100 Hz to 3 MHz; gain is about 30 dB. Field-effect transistor Q1 is configured in the common-source self-biased mode. Optional resistor R1 allows you to set the input impedance to any desired value; commonly, it will be 50 Ω.

The signal is then direct coupled to Q2, a common-base circuit that isolates the input and output stages and provides the amplifier's exceptional stability. Last, Q3 functions as an emitter follower, to provide low output impedance at about 50 Ω. If you need higher output impedance, include resistor R8. It will affect impedance according to this formula:  $R8 \approx R_{OUT} - 50$ . Otherwise, connect output capacitor C4 directly to the emitter of Q3.

## MINIATURE WIDEBAND AMPLIFIER

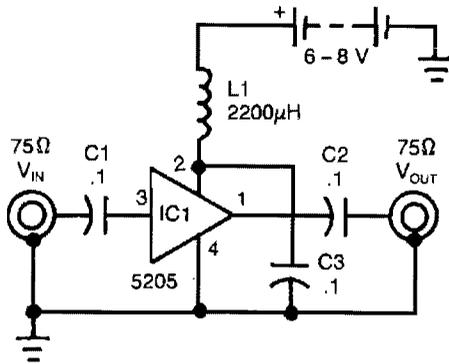


Reprinted with permission from Radio-Electronics Magazine, 1989 R-E Experimenters Handbook. Copyright Gernsback Publications, Inc., 1989.

Fig. 42-7

This wideband amplifier uses only five components. External signals enter pin 3 of IC1 via ac coupling capacitor C1. Following amplification, the boosted signals from IC1 pin 1 are coupled to the output by capacitor C2. Capacitor C3 decouples the dc power supply, while rf current is isolated from the power supply by rf choke L1.

The NE5205's low current consumption of 25 mA at 6 Vdc makes battery-powered operation a reality. Although the device is rated for a 6 to 8 V power supply, 6 V is recommended for normal operation. From 6 V an internal bias of 3.3 V results, which permits a 1.4 V pk-pk output swing for video applications.
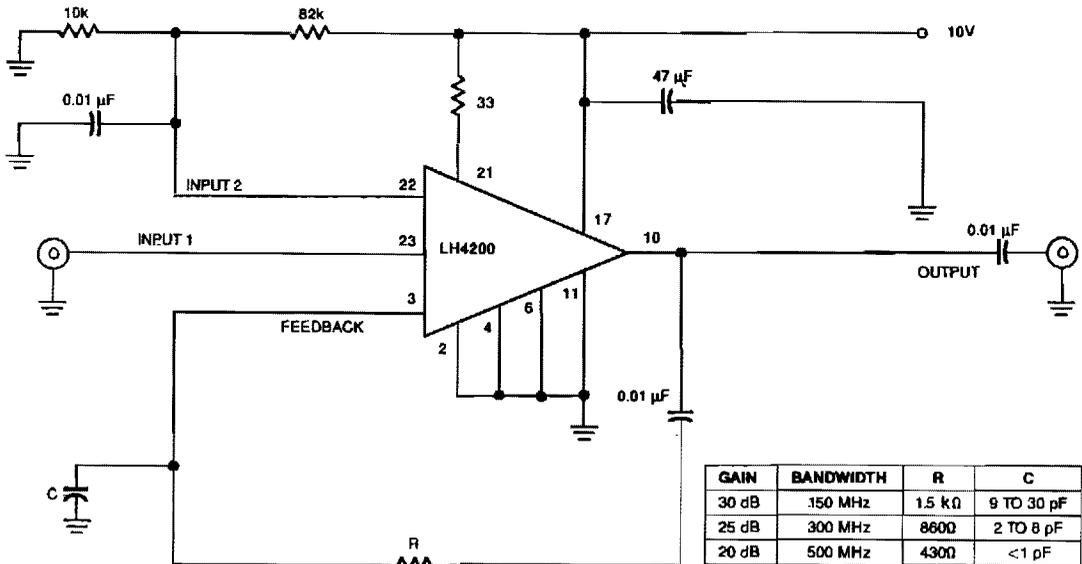
## WIDEBAND 500 kHz – 1 GHz HYBRID AMPLIFIER



EDN

Fig. 42-8

The amplifier's input stage is a dual-gate GaAs FET, which provides low input capacitance and high transconductance. The dual-gate structure accepts the signal on input 1. Input 2 controls the gain of the amplifier. The amplifier has a third input for use in series feedback. The output feeds back to pin 3 via a single resistor, which controls the overall power gain of the amplifier. At 10 MHz, the output is capable of delivering 12 dBm into a 50-Ω load with 1 dB of signal compression. The ac-coupled amplifier has a gain of 37 dB at 100 MHz and 3 dB at 1 GHz.

# 43


## Humidity Sensor

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Low-Cost Humidity Sensor

## LOW-COST HUMIDITY SENSOR

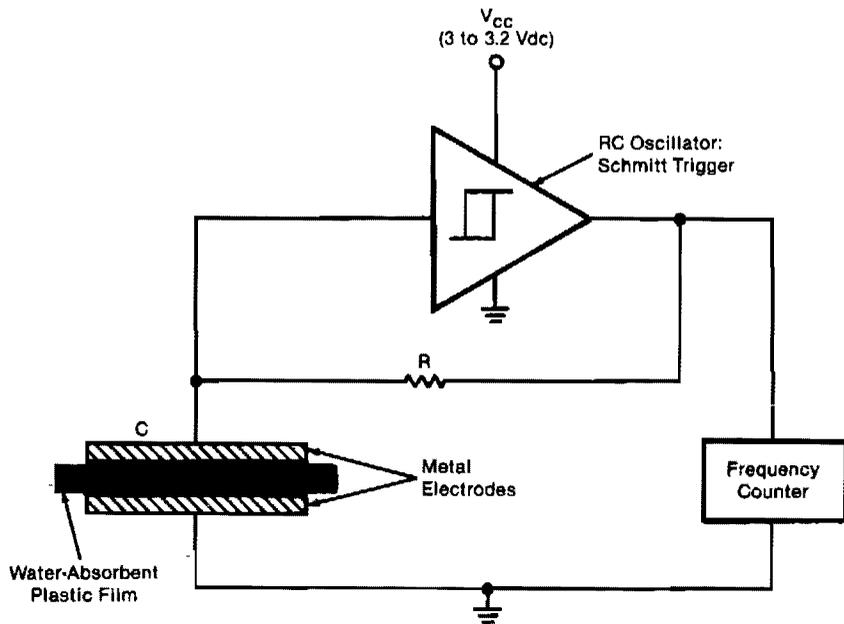

NASA TECH BRIEFS

Fig. 43-1

The sensor is an RC oscillator in which a water-absorbent plastic film is the insulator in the capacitive element. The capacitance of the film increases with the amount of water it absorbs from the air, and thus reduces the oscillation frequency. A frequency counter produces a digital output that represents the change in frequency and hence the change in relative humidity. The sensor can be used to measure humidity in the atmosphere, in the soil, and in industrial gases, for example. A Schmitt-trigger-type IC is connected to the capacitor, which consists of a film of a commercially produced sulfonated fluorocarbon polymer, 2 in. (5.08 cm) square, sandwiched between perforated metal plates. The oscillation frequency decreases almost linearly from about 100 to 16 kHz as the relative humidity increases from about 20 to 76%.

# 44


## Indicators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Stereo Indicator  
On-the-Air Indicator  
Receiver Signal Alarm  
Rf-Actuated Relay  
Visual-Level Indicator

## STEREO INDICATOR

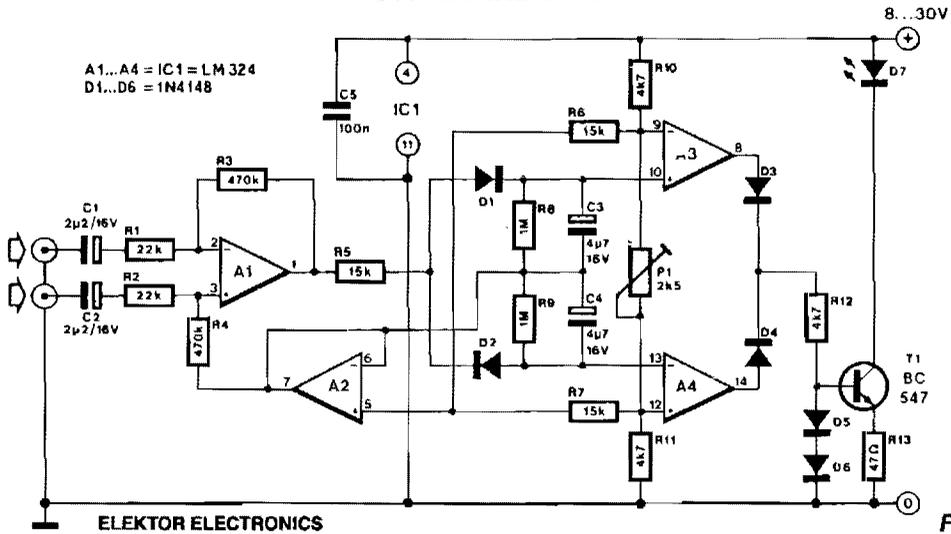


**Fig. 44-1**

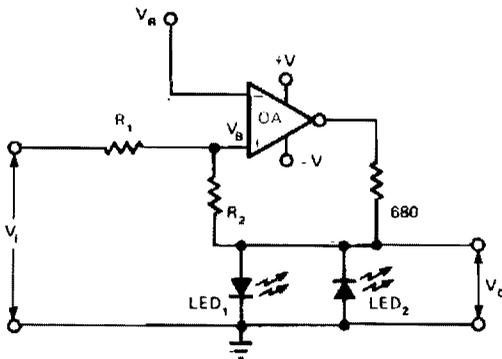On most FM tuners, the stereo indicator lights upon detection of the 19-kHz pilot tone. However, this doesn't mean that the program is actually stereophonic, since the pilot tone is often transmitted with mono programs also. A similar situation exists on stereo amplifiers, where the stereo LED is simply controlled from the mono/stereo switch.

The LED-based stereo indicator described here lights only when a true stereo signal is fed to the inputs. Differential amplifier A1 raises the difference between the L and R input signals. When these are equal, the output of A1 remains at the same potential as the output of A2, which forms a virtual ground rail at half the supply voltage. When A1 detects a difference between the L and R input signals, it supplies a positive or negative voltage with respect to the virtual ground rail, and so causes C3 to be charged via D1 or C4 via D2. Comparator A3/A4 switches on the LED driver via OR circuit D3/D4. The input signal level should not be less than 100 mV to compensate for the drop across D1 or D2. The sensitivity of the stereo indicator is adjustable with P1.

## VISUAL LEVEL INDICATOR



EDN

**Fig. 44-2**

This indicator is basically a switch with hysteresis characteristics. If the input voltage momentarily (or permanently) exceeds the most positive reference level, LED1 is switched on. If, on the other hand, the voltage falls below the negative, or least positive, reference level, LED1 will be switched off and LED2 switched on. The output voltage,  $V_o$  is clamped either to the diode voltage  $V_{D1}$ , or  $V_{D2}$  depending on which LED is conducting. For  $V_o$  to be positive,  $V_B$  has to be positive with respect to the reference voltage  $V_R$ ; for  $V_o$  to be negative,  $V_B$  has to be negative with respect to  $V_R$ .

### RECEIVER SIGNAL ALARM

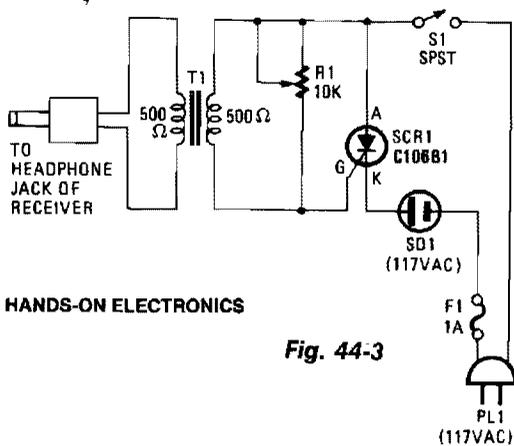


Fig. 44-3

### RF-ACTUATED RELAY

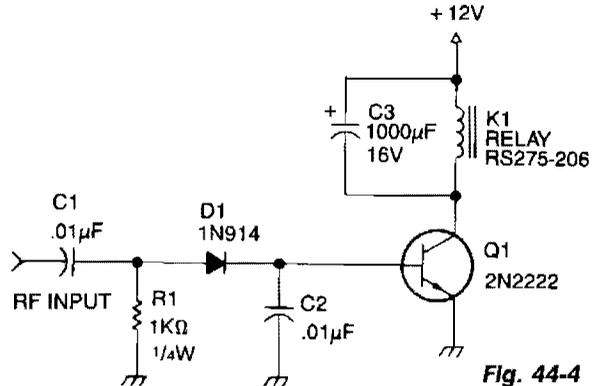


Fig. 44-4

Automatic antenna switching or rf power indication can be achieved with this circuit. Relay will key with less than 150 mW drive on 2 m.

### ON-THE-AIR INDICATOR

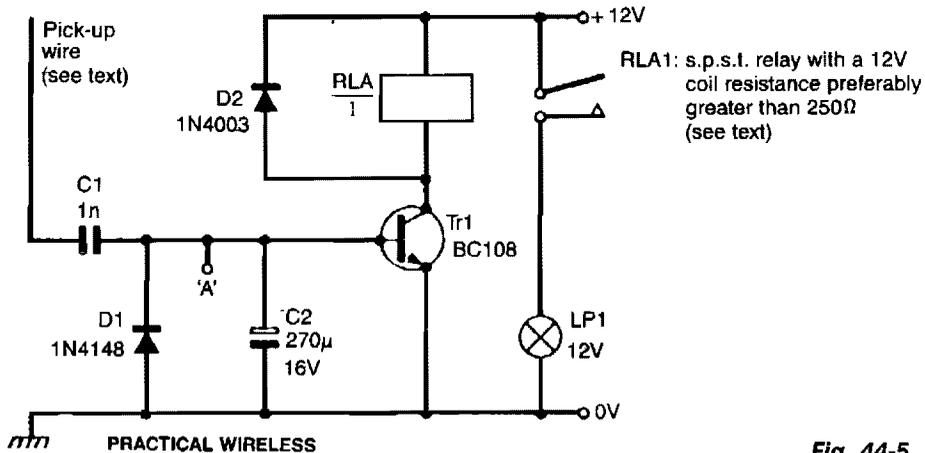


Fig. 44-5

The circuit is a simple rf-actuated switch which will respond to any strong field in the region of the pickup wire. The length of the wire will depend on how much coupling is needed, but a 250-mm length wrapped around the outside of the coaxial cable feeding the antenna should suffice for most power levels. If only one band is used, the wire can be made a resonant length—495 mm for 144 MHz band operation for example. When rf energy is picked up by the device, diode D1 will conduct on the negative half-cycles, but will be cut off on the positive half-cycles. The result will be a net positive voltage at the base of transistor Tr1, forward biasing it into conduction. On ssb and cw transmissions, where the transmission is not continuous, that bias would be constantly varying and the relay RLA would chatter. However, capacitor C2 holds the bias voltage steady until a long gap in transmissions occurs.

# 45

## Infrared Circuits


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Infrared Wireless Speaker System  
Long-Range Object Detector  
IR Receiver  
IR Transmitter

Digital IR Transmitter  
Simple IR Detector  
Infrared Transmitter  
Infrared Transmitter

## INFRARED WIRELESS SPEAKER SYSTEM

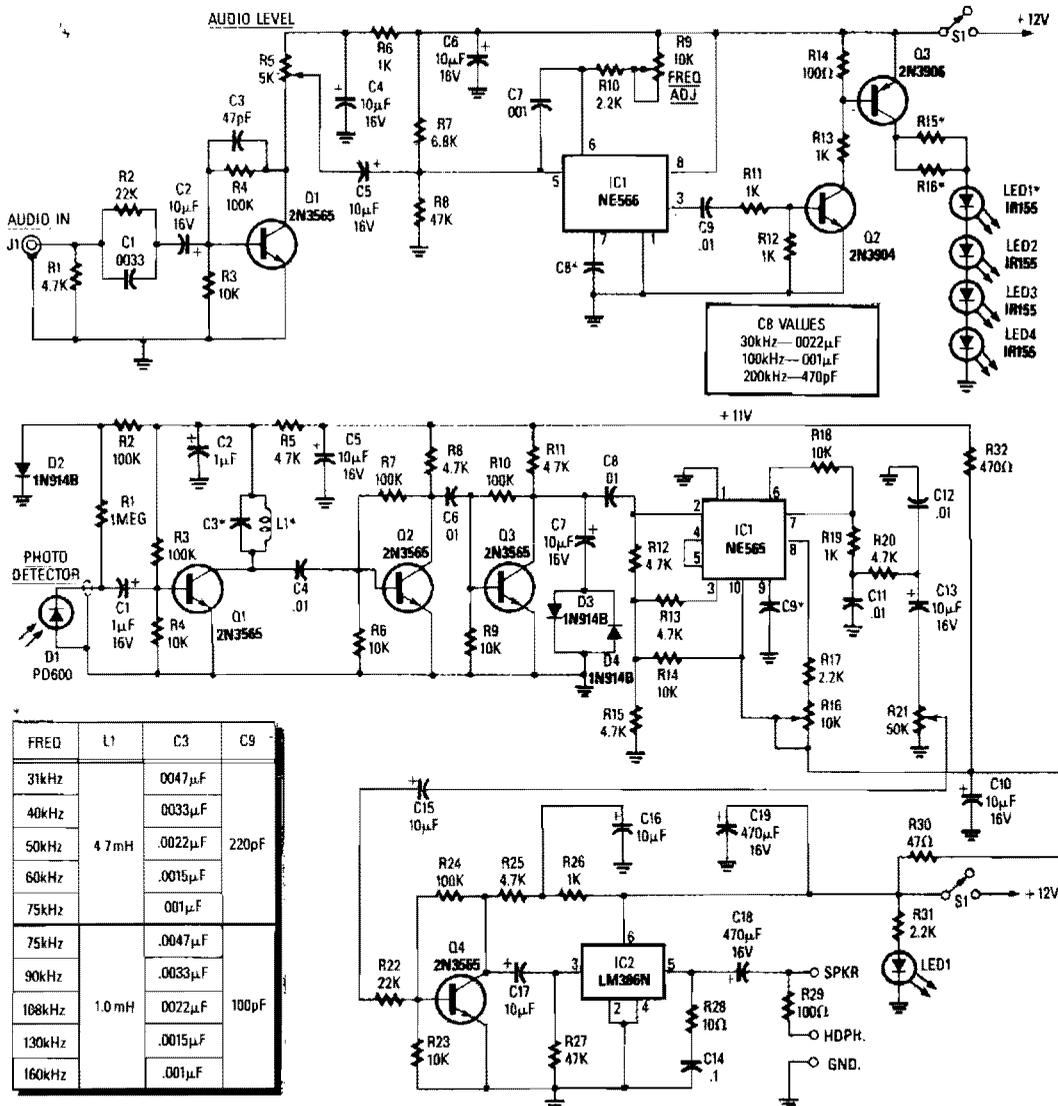


Reprinted with permission from Radio-Electronics Magazine, August 1988. Copyright Gernsback Publications, Inc., 1988.

**Fig. 45-1**

Although the IR region is free from radio interference, it is subject to interference from incandescent lamps, fluorescent lamps, stray reflections, and other sources.

A simple way to overcome that problem is to create a *carrier* by chopping the IR radiation at a rate of 100 kHz. The audio then modulates the carrier by modulating the chopping rate. A receiver then detects the IR beam as a 100-kHz FM signal. The only disadvantage is that instead of a simple audio amplifier, a high-gain FM receiver is necessary. However, with the ICs that are now available, an FM receiver is easy to build, and contains little more circuitry than a high-gain audio amplifier. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.

## LONG-RANGE OBJECT DETECTOR

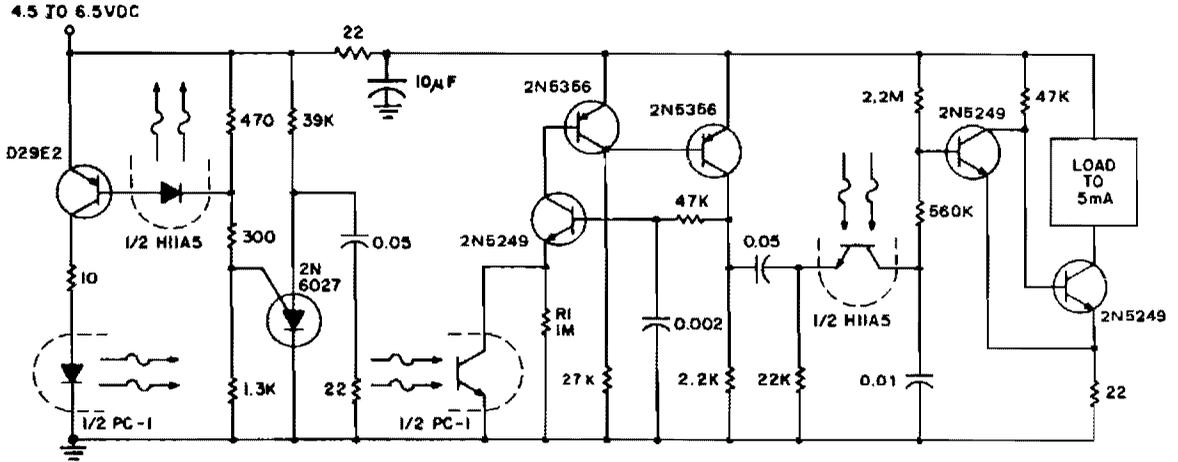

PC-1 SELECTION	TRANSMISSION RANGE	REFLECTIVE RANGE
H23A1	5"	1"
LED56 and L14Q1	12"	3"
LED56 and L14G1	18"	4 1/2"
LED55C and L14Q1	32"	8"
1N6266 and L14G3	48"	12"
F5D1 and L14G3	80"	20"
F5D1 and L14P2	200"	50"


GE

When long ranges must be worked with IR light sources, and when high system reliability is required, pulsed-mode operation of the IR is required. Additional reliability of operation is attained by synchronously detecting the photodetector current, as this circuit does. PC-1 is an IR and phototransistor pair which detect the presence of an object blocking the transmission of light from the IR to the phototransistor. Relatively long-distance transmission is obtained by pulsing the IR, with about 10- $\mu$ s pulses, at a 2-ms period, to 350 mA via the 2N6027 oscillator. The phototransistor current is amplified by the 2N5249 and 2N5356 amplifier to further increase distance and allows use of the H11A5, also pulsed by the 2N6027, as a synchronous detector, providing a fail-safe, noise immune signal to the 2N5249 pair forming a Schmitt-trigger output.

This design was built for battery operation, with long battery life a primary consideration. Note that another stage of amplification driving the IR can boost the range limited by the IR  $V_F$ , by 5 to 10 times. A higher supply voltage for the IR can double this range.

Today, optoelectronics are mostly used to transmit electronic information over light beams. These applications range from the use of optocouplers transmitting information between IC logic circuits and power circuits, between power lines and signal circuits, between telephone lines and control circuitry, to the pulse-modulated systems which transmit information through air or fiber optics over relatively great distances.


## IR RECEIVER

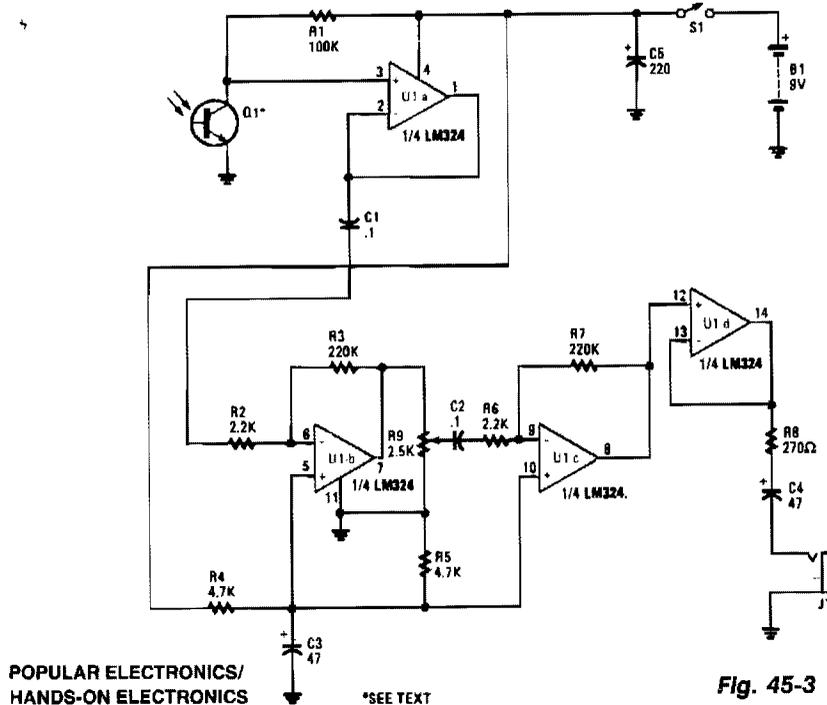

**Fig. 45-3**

Infrared emissions detected by Q1 are fed through U1a to U1b, which amplifies the signal by a factor of 100. The amplified output of U1b is fed to U1c through R9, C2, and R6. Potentiometer R9 serves as a volume control. With R9 set to pass the maximum signal, U1c provides a gain of 100, for a total system gain of 10,000 dB. The output of U1c is connected to voltage follower circuit U1d to better match and drive headphones that can be plugged into J1.

## IR TRANSMITTER

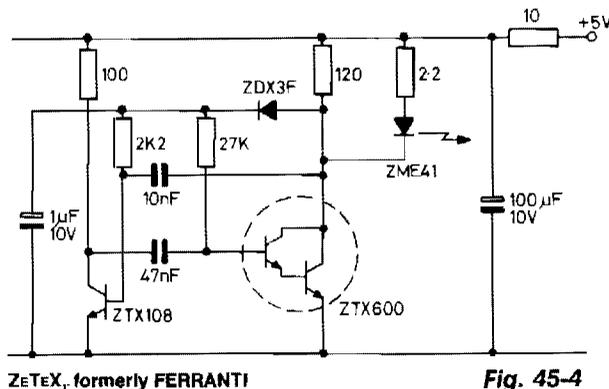


**Fig. 45-4**
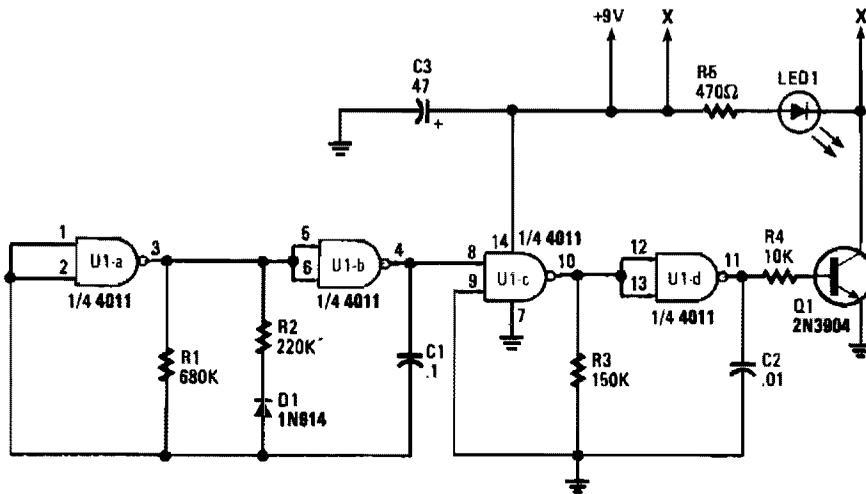
## IR TRANSMITTER (Cont.)

The transmitter consists of an oscillator which drives a high output IR emitting diode. The oscillator is a sure start multivibrator circuit that provides an output of 15 to 1000 mark to space ratio at a frequency of 1 kHz. This large mark to space ratio allows the IR diode to be operated at a high peak current, provided by the ZTX600 Darlington transistor, to maximize the transmitter range. A decoupling network is included in the power supply lead to isolate it from any logic circuitry using the same 5-V power supply source. The transmitter supply current is approximately 65 mA.

### DIGITAL IR TRANSMITTER



POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 45-5



Gates U1a and U1b are configured as a low-frequency oscillator. The output waveform at pin 11 is nonsymmetrical with the positive portion of the signal, making up only 20% of the time period.

Diode D1, a 1N914 general-purpose unit, together with C1, R1, and R2, determine the on time for the positive portion of the output waveform. The off, or negative portion of the output waveform, depends mainly on the values of R1 and C1. The operating frequency of that oscillator is about 11 Hz. The second oscillator consists of U1c and U1d, which outputs an almost symmetrical waveform at a frequency of about 400 Hz. The output of the first oscillator U1a/U1b is fed to pin 8 of U1c to key the second oscillator U1c/U1d on and off at about 11 Hz, with the on time limited to about 20% of the time period (about 15 ms).

The output waveform of the second oscillator is fed to the base of Q1, which is used to drive the IR diode LED1 in short bursts. Pulsing LED1 helps to save battery power, and also allows each circuit to be given its own special sound footprint.

By changing any of the values of R1, R2, R3, C1, or C2, the sound footprint can be varied. As the component values are increased, the oscillator's frequency goes down, and as the values are decreased, the frequency goes up.

## SIMPLE IR DETECTOR

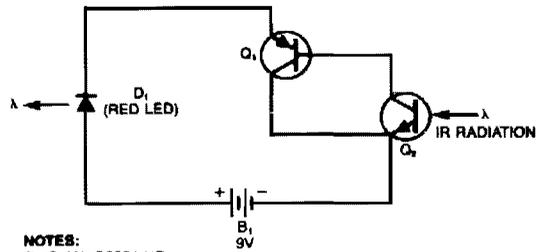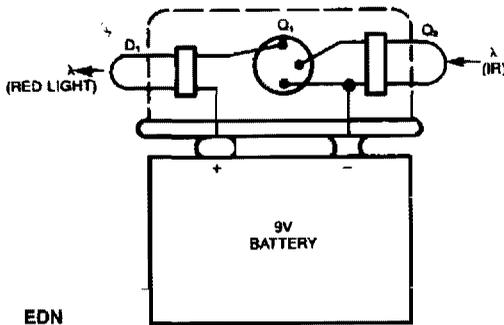


**NOTES:**  
 D<sub>1</sub> IS AN ID5531-UR  
 Q<sub>1</sub> IS A 2N3638  
 Q<sub>2</sub> IS A TRW 802

**Fig. 45-6**


This simple IR detector turns on a real LED when Q2 is exposed to invisible IR radiation found in fiber-optics systems, position sensors, and TV remote-control units. The device can be built on top of a 9-V battery and held in place with RTV. Its power dissipation is virtually zero, unless IR radiation or high ambient light is present. Normal fluorescent lighting is not a problem, but if necessary add an IR filter to the Q2 detector to exclude ambient light. Exposing the detector to a strong light or IR source gives a quick check of the battery and the red LED.

## INFRARED TRANSMITTER

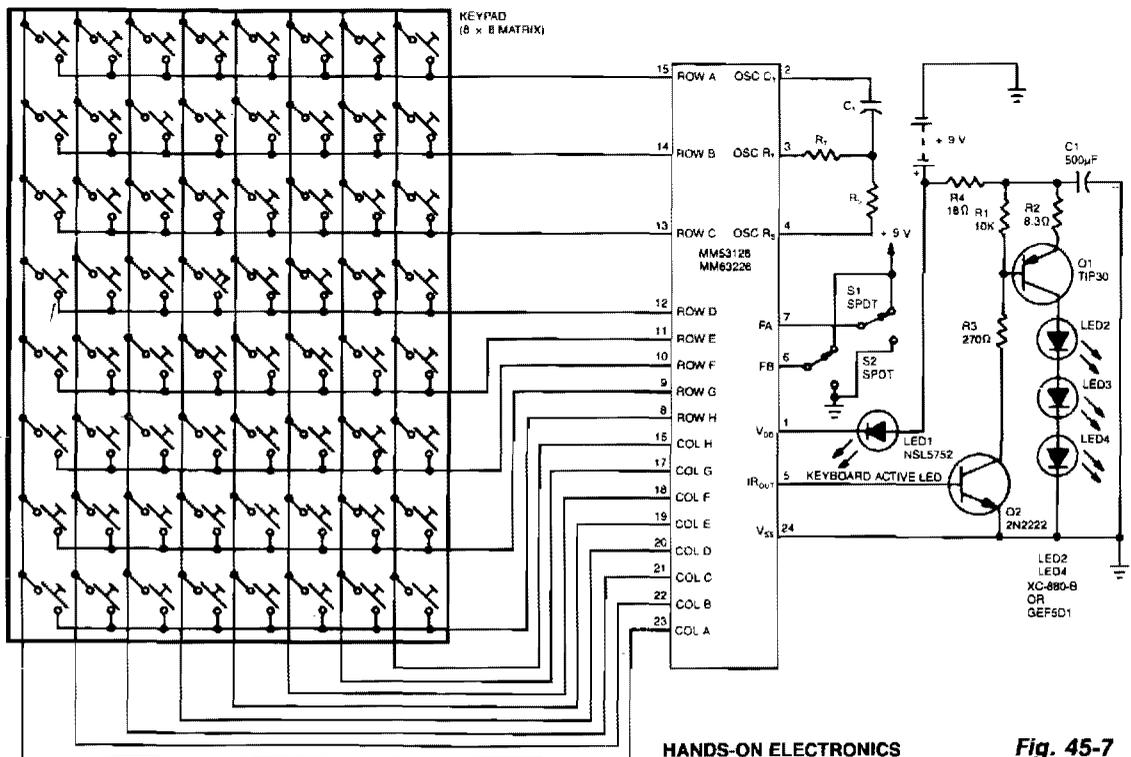

**Fig. 45-7**

# INFRARED TRANSMITTER

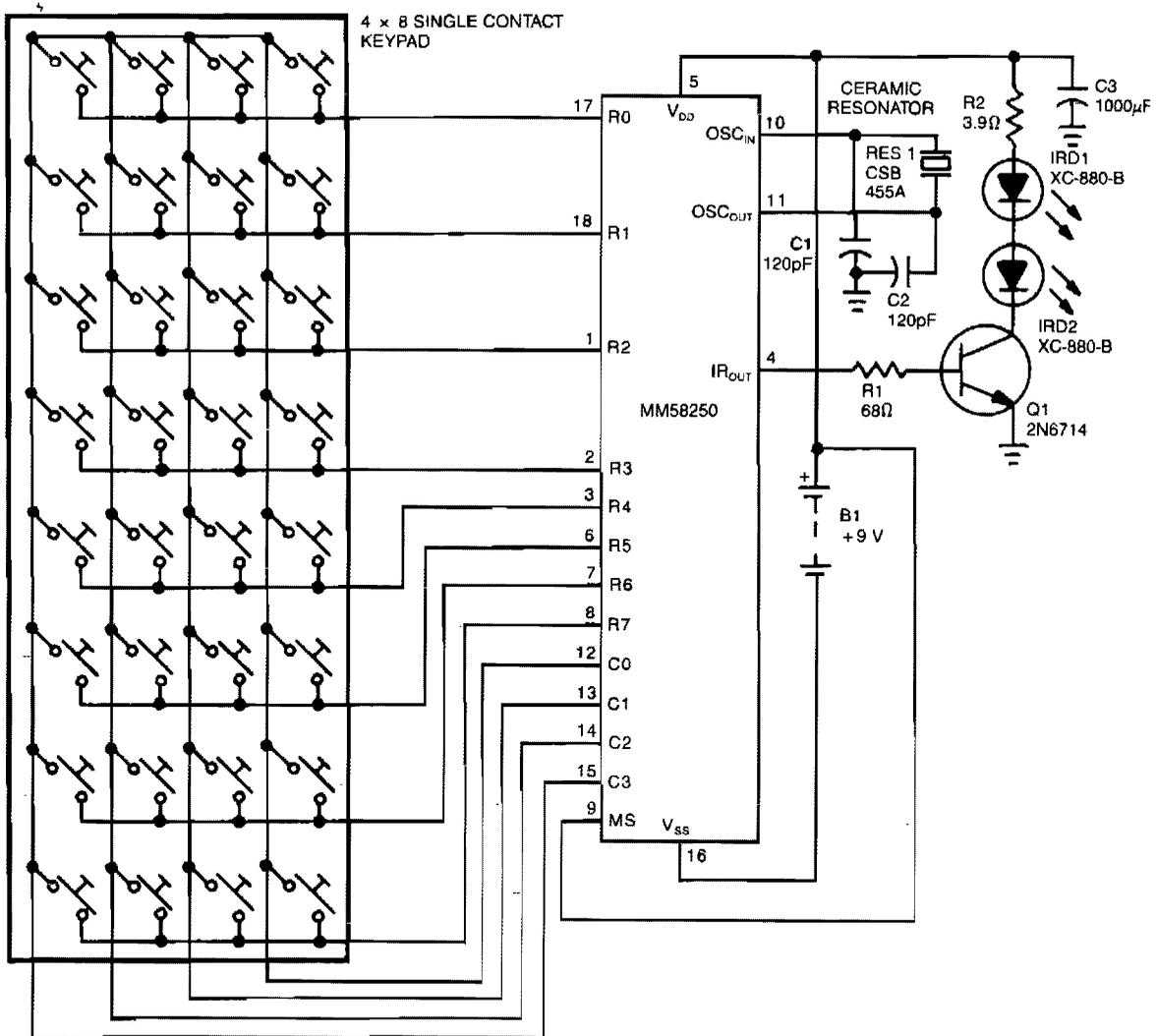

POPULAR ELECTRONICS

Fig. 45-8

# 46

## Instrumentation Amplifiers


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Ultra-Precision Instrumentation Amplifier  
Strain Guage Instrumentation Amplifier  
Instrumentation Amplifier  
Wideband Instrumentation Amplifier

Biomedical Instrumentation Differential Amplifier  
Differential Instrumentation Amplifier  
Thermocouple Preamplifier  
Low-Power Instrumentation Amplifier
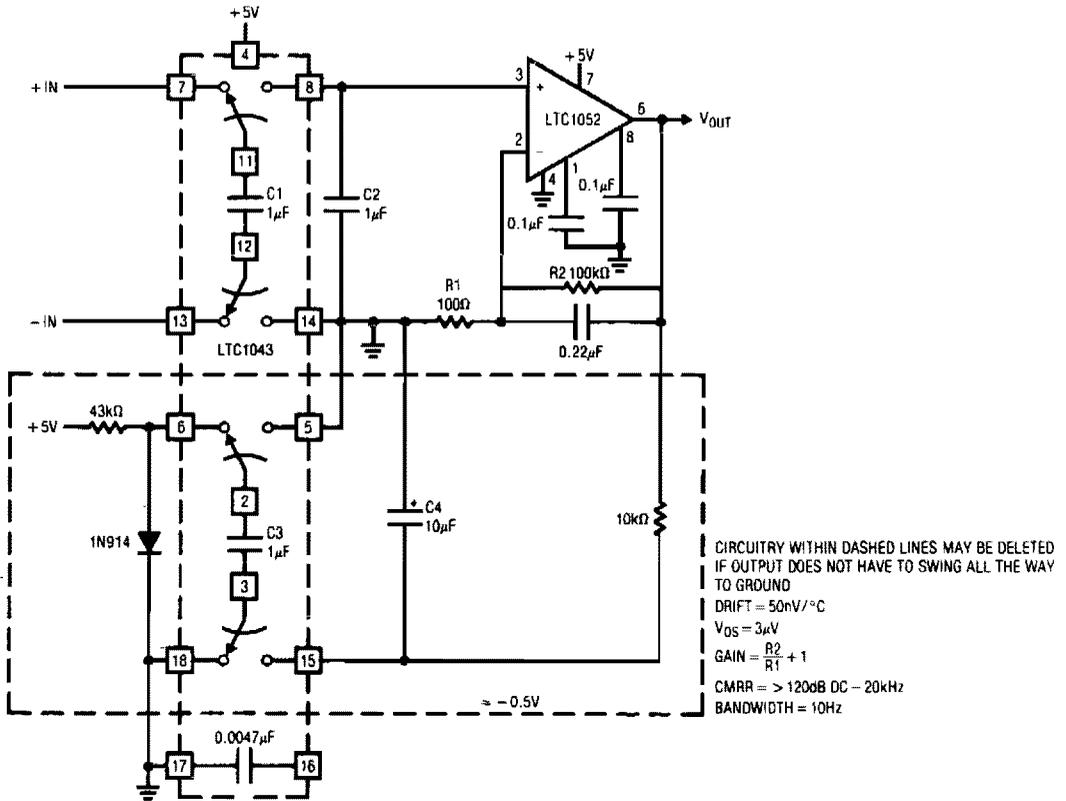
## ULTRA-PRECISION INSTRUMENTATION AMPLIFIER



LINEAR TECHNOLOGY

**Fig. 46-1**

This circuit will run from a single 5 V power supply. The LTC1043 switched-capacitor instrumentation building block provides a differential-to-single-ended transition using a flying-capacitor technique. C1 alternately samples the differential input signal and charges ground referred C2 with this information. The LTC1052 measures the voltage across C2 and provides the circuit's output. Gain is set by the ratio of the amplifier's feedback resistors. Normally, the LTC1052's output stage can swing within 15 mV of ground. If operation all the way to zero is required, the circuit shown in dashed lines can be employed. This configuration uses the remaining LTC1043 section to generate a small negative voltage by inverting the diode drop. This potential drives the 10-K $\Omega$ , pull-down resistor, forcing the LTC1052's output into class A operation for voltages near zero. Note that the circuit's switched-capacitor front-end forms a sampled-data filter allowing the common-mode rejection ratio to remain high, even with increasing frequency. The 0.0047 $\mu F$  unit sets front-end switching frequency at a few hundred Hz.

## STRAIN GAUGE INSTRUMENTATION AMPLIFIER

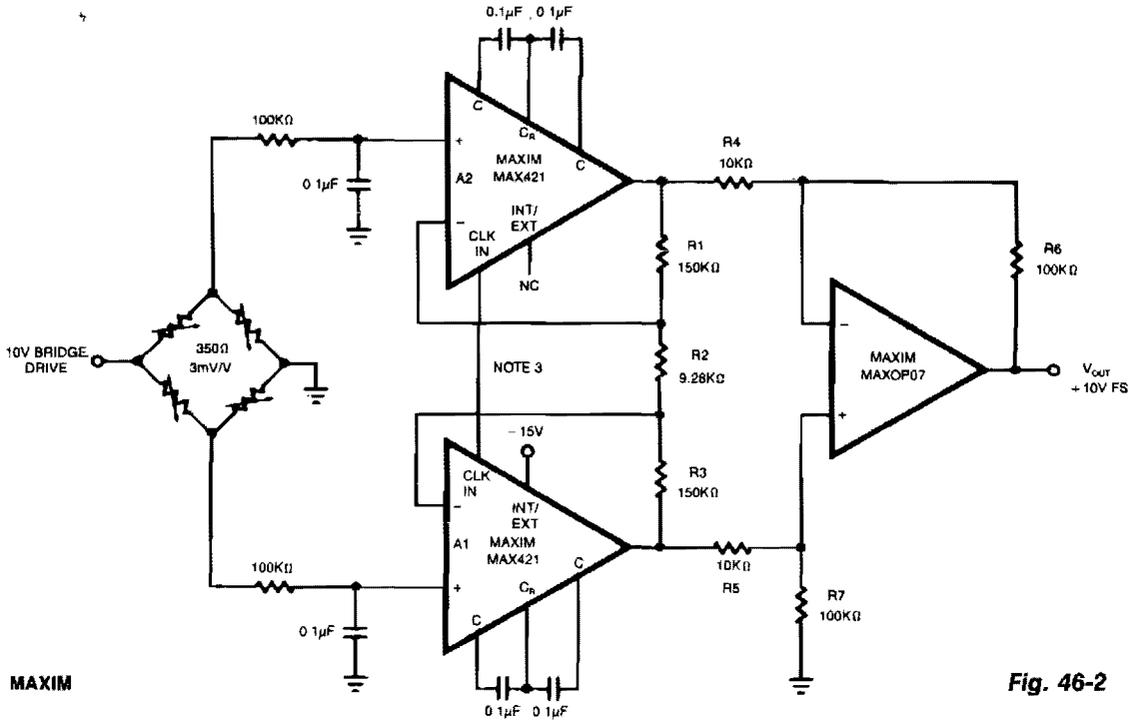


Fig. 46-2

This circuit has an overall gain of 320. More gain can easily be obtained by lowering the value of R2. Untrimmed  $V_{OS}$  is 10  $\mu\text{V}$ , and  $V_{OS}$  tempco is less than 0.1  $\mu\text{V}/^\circ\text{C}$ . In many circuits, the OP07 can be omitted, with the two MAX421 differential outputs connected directly to the differential inputs of an integrating a/d.

## INSTRUMENTATION AMPLIFIER


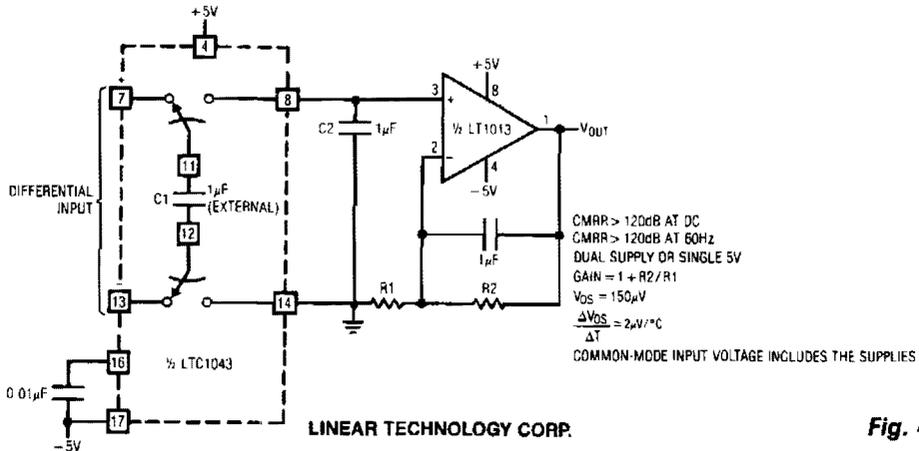


Fig. 46-3

## INSTRUMENTATION AMPLIFIER (Cont.)

LTC1043 and LT1013 dual op amps are used to create a dual instrumentation amplifier using just two packages. A single DPDT section converts the differential input to a ground-referred single-ended signal at the LT1013's input. With the input switches closed, C1 acquires the input signal. When the input switches open, C2's switches close and C2 receives charge. Continuous clocking forces C2's voltage to equal the difference between the circuit's inputs. The 0.01- $\mu$ F capacitor at pin 16 sets the switching frequency at 500 Hz. Common-mode voltages are rejected by over 120 dB and drift is low.

### WIDEBAND INSTRUMENTATION AMPLIFIER

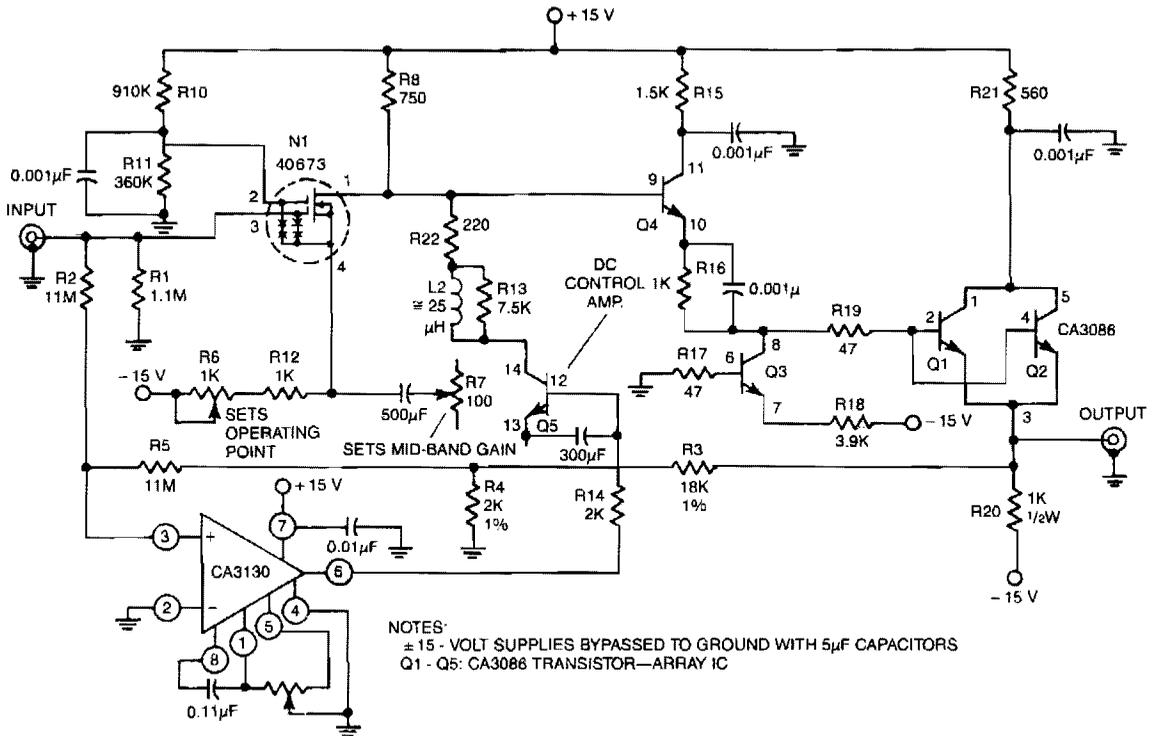


GE/RCA

Fig. 46-4

Has an input resistance of 1-M $\Omega$ , a bandwidth from dc to about 35 MHz, and a gain of 10 times. Low-frequency gain is provided by a CA3130 BiMOS op amp operated as a single-supply amplifier. High-frequency gain is provided by a 40673 dual-gate MOSFET. The entire amplifier is nulled by shorting the input to ground and adjusting R9 for zero dc output voltage.
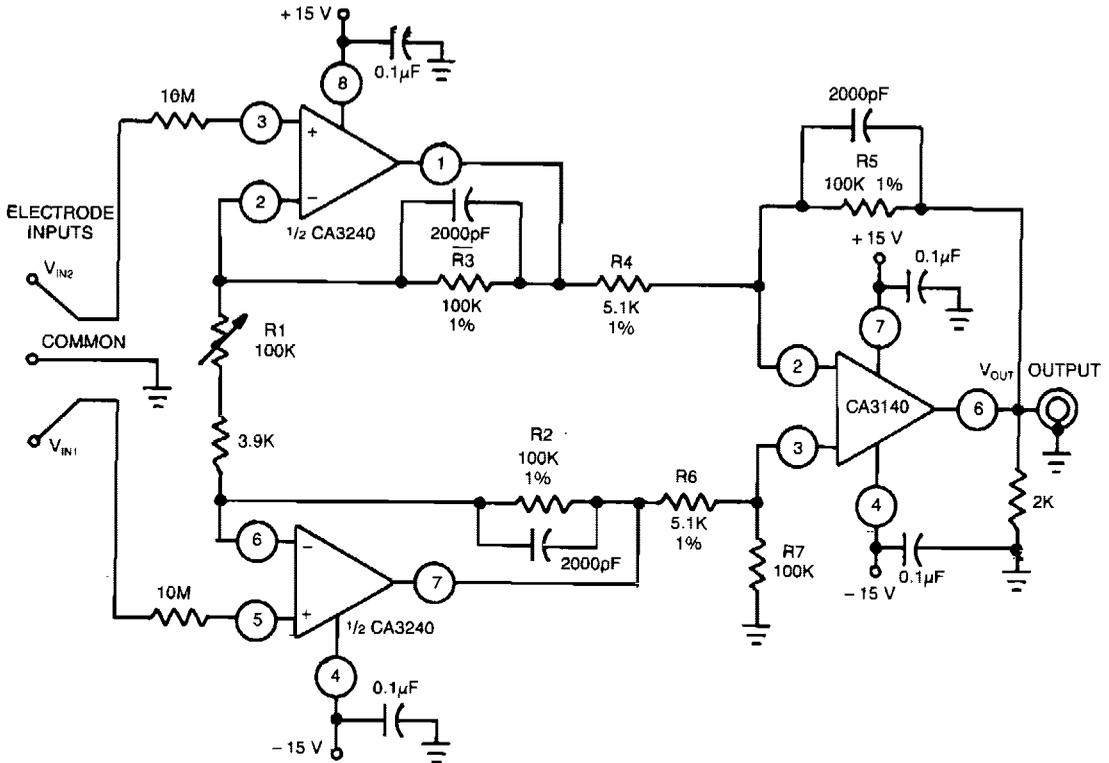
## BIOMEDICAL INSTRUMENTATION DIFFERENTIAL AMPLIFIER




GE/RCA

Fig. 46-5

This differential amplifier uses the isolated high-impedance inputs of the CA3420 BiMOS op amp. Because the CA3240's input current is only 50 pA maximum, 10-MΩ resistors can be used in series with the input probes to limit the current to 2 μA under a fault condition.
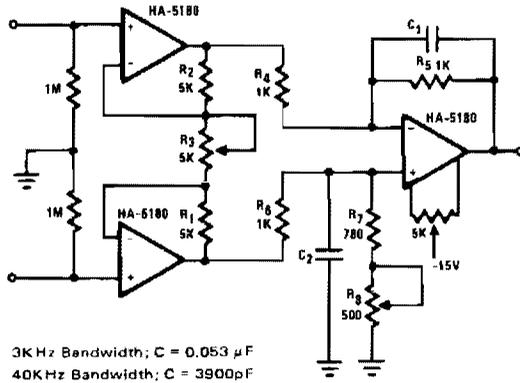
## DIFFERENTIAL INSTRUMENTATION AMPLIFIER




HARRIS

Fig. 46-6

This circuit relies on extremely high input impedance for effective operation. The HA-5180 with its JFET input stage, performs well as a pre-amplifier. The standard three amplifier configuration is used with very close matching of the resistor ratios  $R5/R4$  and  $(R7 + R8)/R6$ , to insure high common-mode rejection (CMR). The gain is controlled through  $R3$  and is equal to  $2R1/R3$ . Additional gain can be had by increasing the ratios  $R5/R4$  and  $(R7 + R8)/R6$ . The capacitors  $C1$  and  $C2$  improve the ac response by limiting the effects of transients and noise. Two suggested values are given for maximum transient suppression at frequencies of interest. Some of the faster DVM's are operating at peak sampling frequency of 3-kHz, hence the 4-kHz, low-pass time constant. The 40-kHz, low-pass time constant for ac voltage ranges is an arbitrary choice, but should be chosen to match the bandwidth of the other components in the system.  $C1$  and  $C2$  might however, reduce CMR for ac signals if not closely matched. Input impedances have also been added to provide adequate dc bias currents for the HA-5180 when open-circuited.

## THERMOCOUPLE PREAMPLIFIER

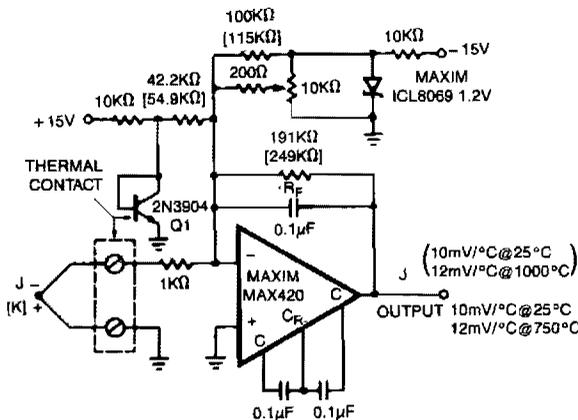


MAXIM

Fig. 46-7

The MAX420 is operated at a gain of 191 to convert the  $52 \mu\text{V}/^{\circ}\text{C}$  output of the type J thermocouple to a  $10 \text{ mV}/^{\circ}\text{C}$  signal. The  $-2.2 \text{ mV}/^{\circ}\text{C}$  tempco of the 2N3904 is added into the summing junction with a gain of 42.2 to provide cold-junction compensation. The ICL8069 is used to remove the offset caused by the 600-mV initial voltage of the 2N3904. Adjust the 10-K $\Omega$  trimpot for the proper reading with the 2N3904 and isothermal connection block at a temperature near the center of the circuit's operating range. Use the component values shown in parentheses when using a type K thermocouple.

## LOW-POWER INSTRUMENTATION AMPLIFIER

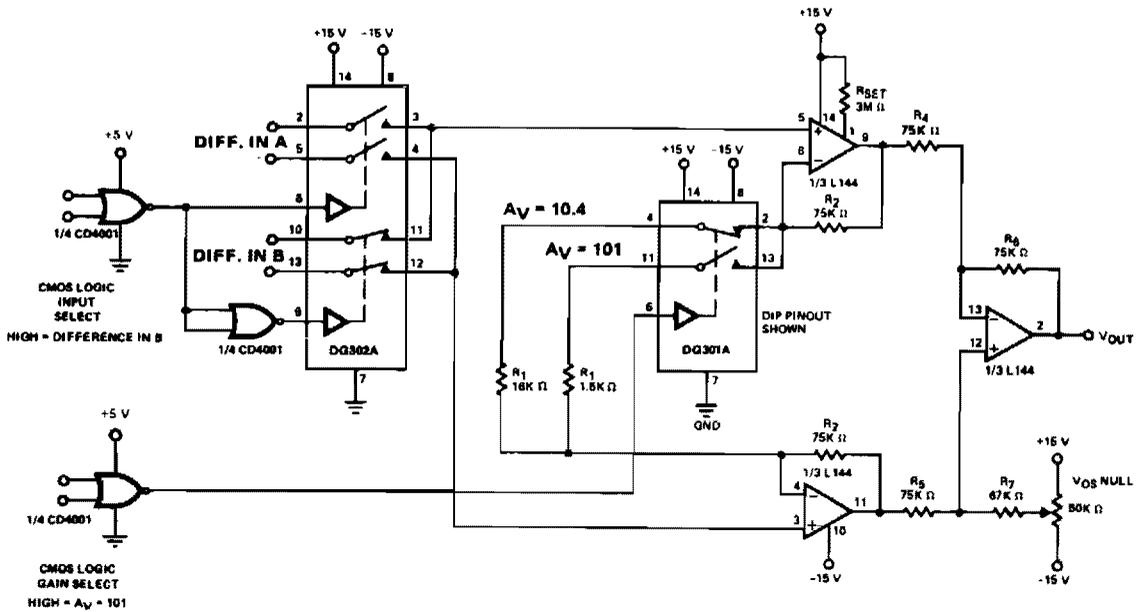

RSET programs L144 power dissipation, gain-bandwidth product. Refer to AN73-6 and the L144 data sheet.

Voltage gain of the instrumentation amplifier is:

$$A_v = 1 + \frac{2R_2}{R_1} \quad (\text{In the circuit shown, } A_{V1} = 10.4, A_{V2} = 101)$$

SILICONIX

**Fig. 46-8**

# 47

## Integrator Circuits


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Resetable Integrator

Integrator with Programmable Reset Level

## RESETTABLE INTEGRATOR

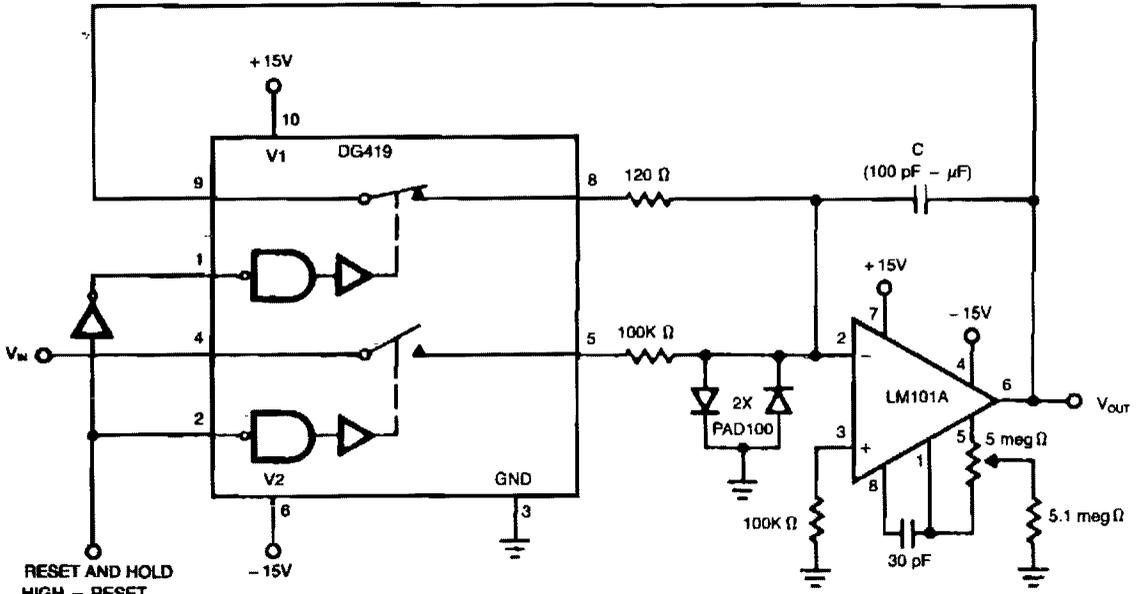


RESET AND HOLD  
HIGH = RESET

NOTE: PIN CONNECTIONS SHOWN ARE FOR METAL CAN PACKAGE  
SILICONIX

$$V_o = \frac{1}{C} \int_{t_1}^{t_2} V_{in} dt \quad (C \text{ in } \mu\text{F}) \quad \text{Fig. 47-1}$$

The low  $r_{DS(on)}$  and high peak current capability of the DG419 makes it ideal for discharging an integrator capacitor. A high logic input pulse disconnects the integrator from the analog input and discharges the capacitor. When the logic input lowers, the integrator is triggered. D1 and D2 prevent the capacitor from charging to over 15 V.
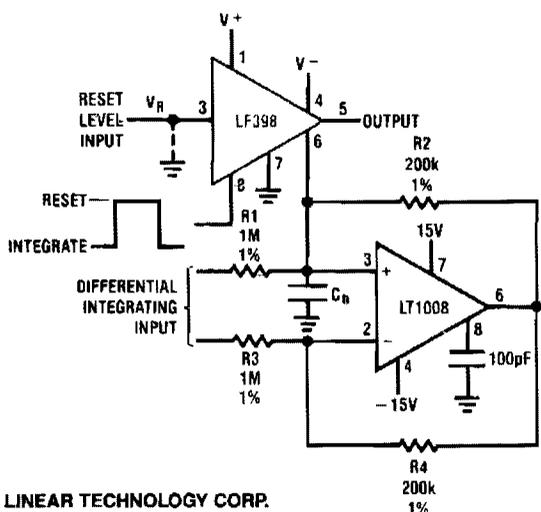
## INTEGRATOR WITH PROGRAMMABLE RESET LEVEL



$$V_{OUT} (\text{HOLD MODE}) = \left[ \frac{1}{(R1)C_n} \int_0^t V_{IND} dt \right] + [V_R]$$

LINEAR TECHNOLOGY CORP.

Fig. 47-2

# 48


## Intercom Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Personal Pocket Pager  
Bidirectional Intercom System  
Intercom  
Hands-Off Intercom  
Two-Way Intercom


## PERSONAL POCKET PAGER

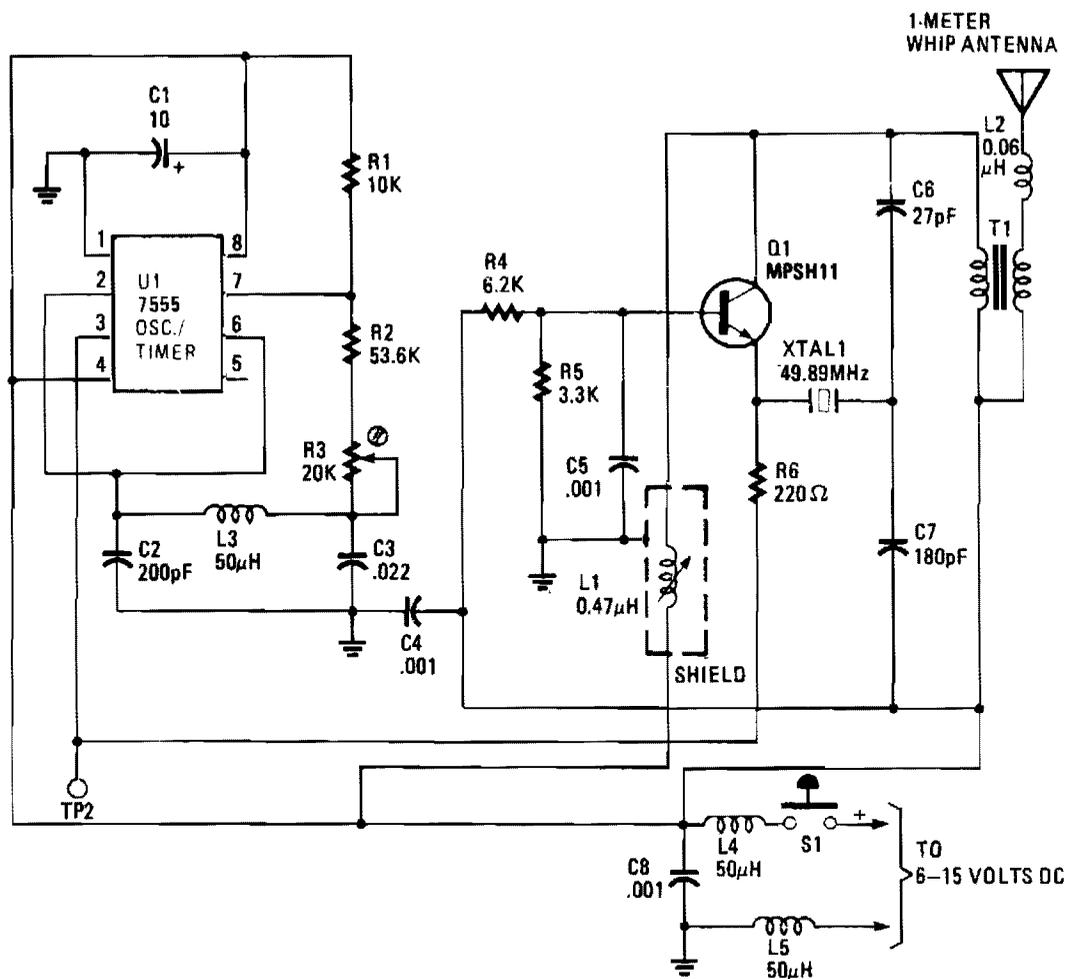


HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

Fig. 48-1

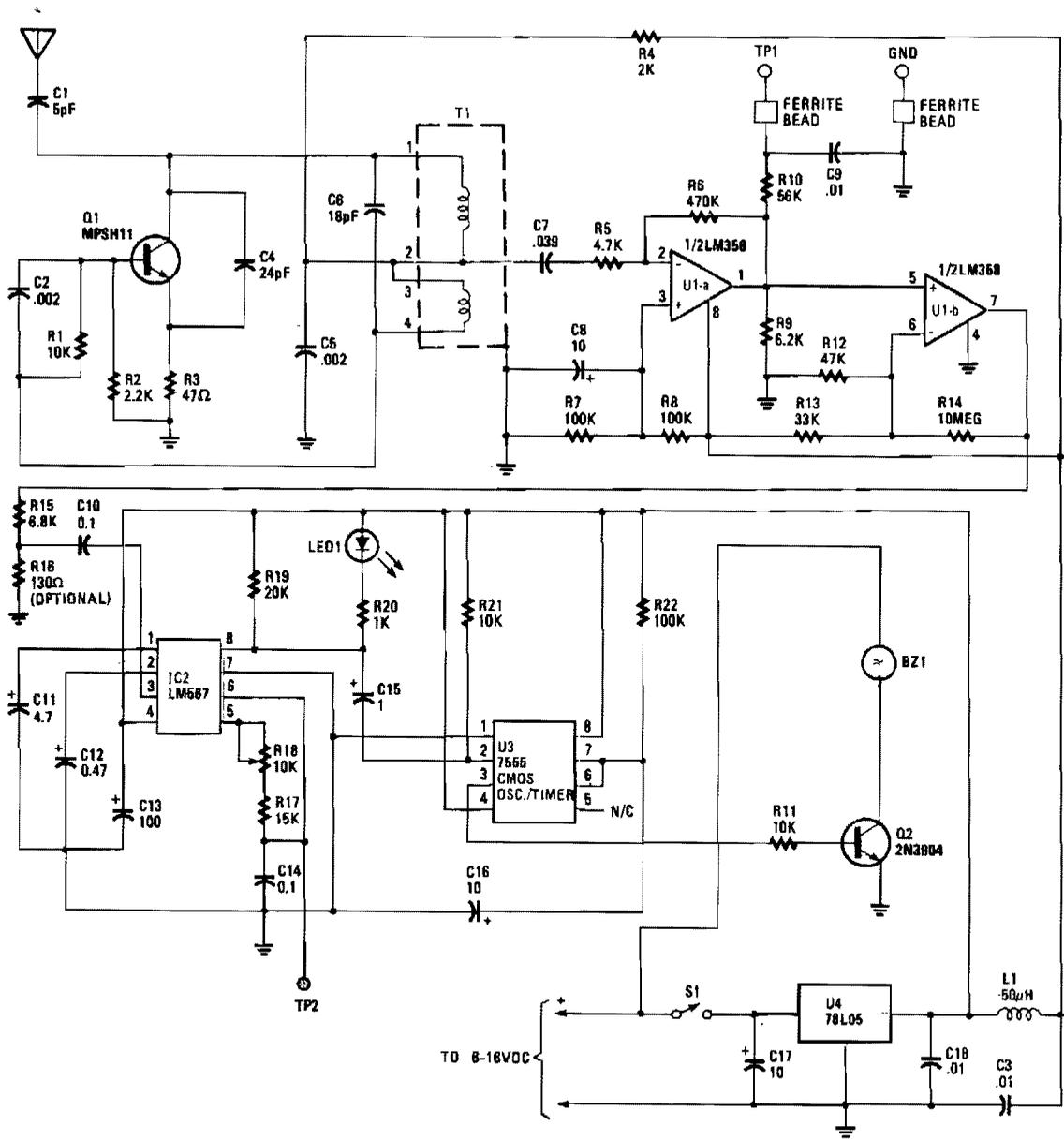When activated, the transmitter sends out a 49.890-MHz, AM rf carrier. The receiver detects, amplifies, and decodes the rf signal, which, in turn, activates a piezo buzzer. The receiver is small enough to carry in a pocket or sit on your workbench. The transmitter is also small and fits easily into a pocket for quick access.



## BIDIRECTIONAL INTERCOM SYSTEM

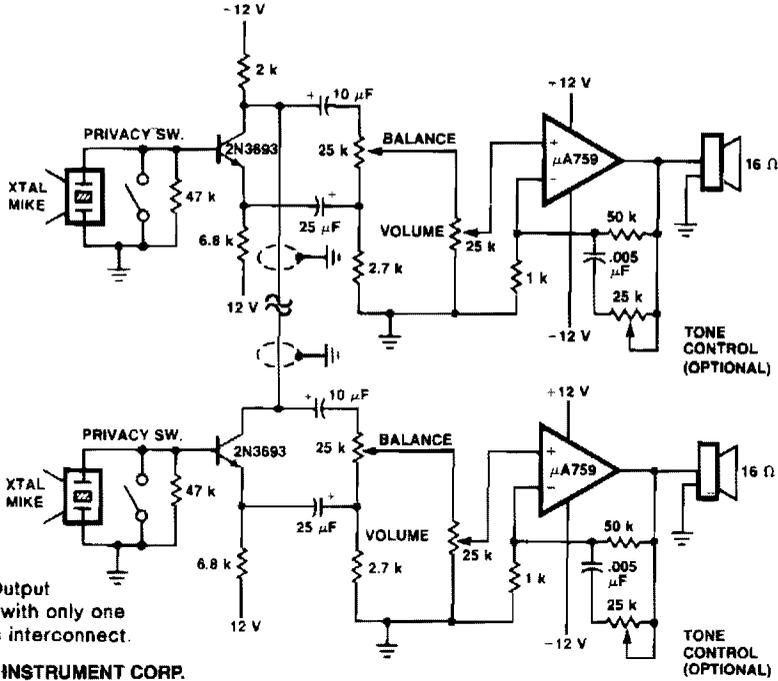

### Features

- Circuit Simplicity
- 1 Watt of Audio Output
- Duplex operation with only one two-wire cable as interconnect.

FAIRCHILD CAMERA & INSTRUMENT CORP.

Fig. 48-2

This system uses  $\mu A759$  audio IC devices and a common connection between the preamps as an interconnect. Either mike can drive either speaker. Duplex operation is possible with only one cable (two wires).

## INTERCOM

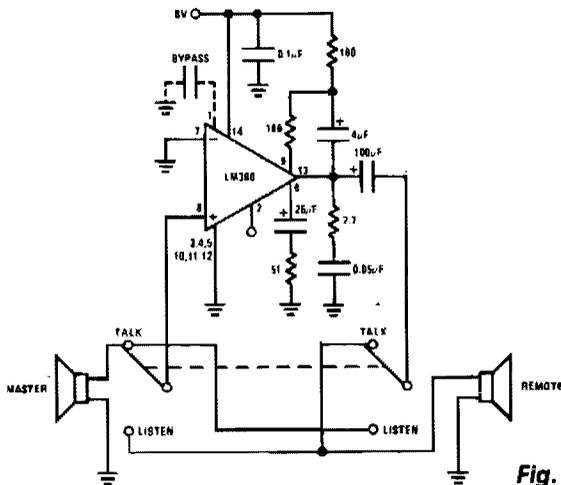



Fig. 48-3

This intercom uses a single audio IC as a two-way amplifier, and the speakers as microphones. A single 6-V supply provides adequate audio volume.

NATIONAL SEMICONDUCTOR CORP.



## TWO-WAY INTERCOM

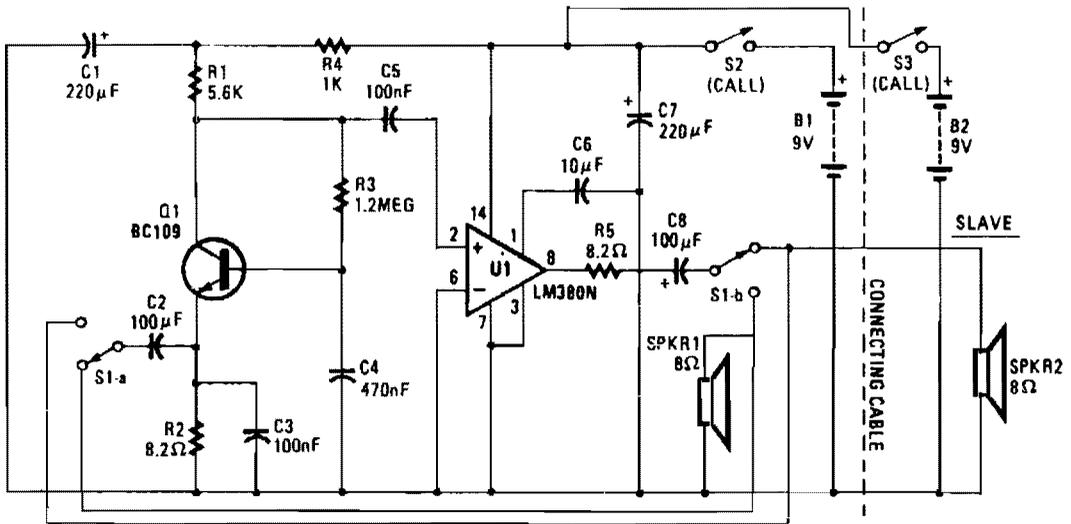

POPULAR ELECTRONICS

Fig. 48-5

# 49


## Inverters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

12 Vdc-to-117 Vac at 60 Hz Power Inverter  
Power MOSFET Inverter  
Medium Power Inverter  
Complementary Output Variable Frequency  
Inverter  
Precision Voltage Inverter  
Power Inverter

## 12 VDC-TO-117 VAC AT 60 Hz POWER INVERTER

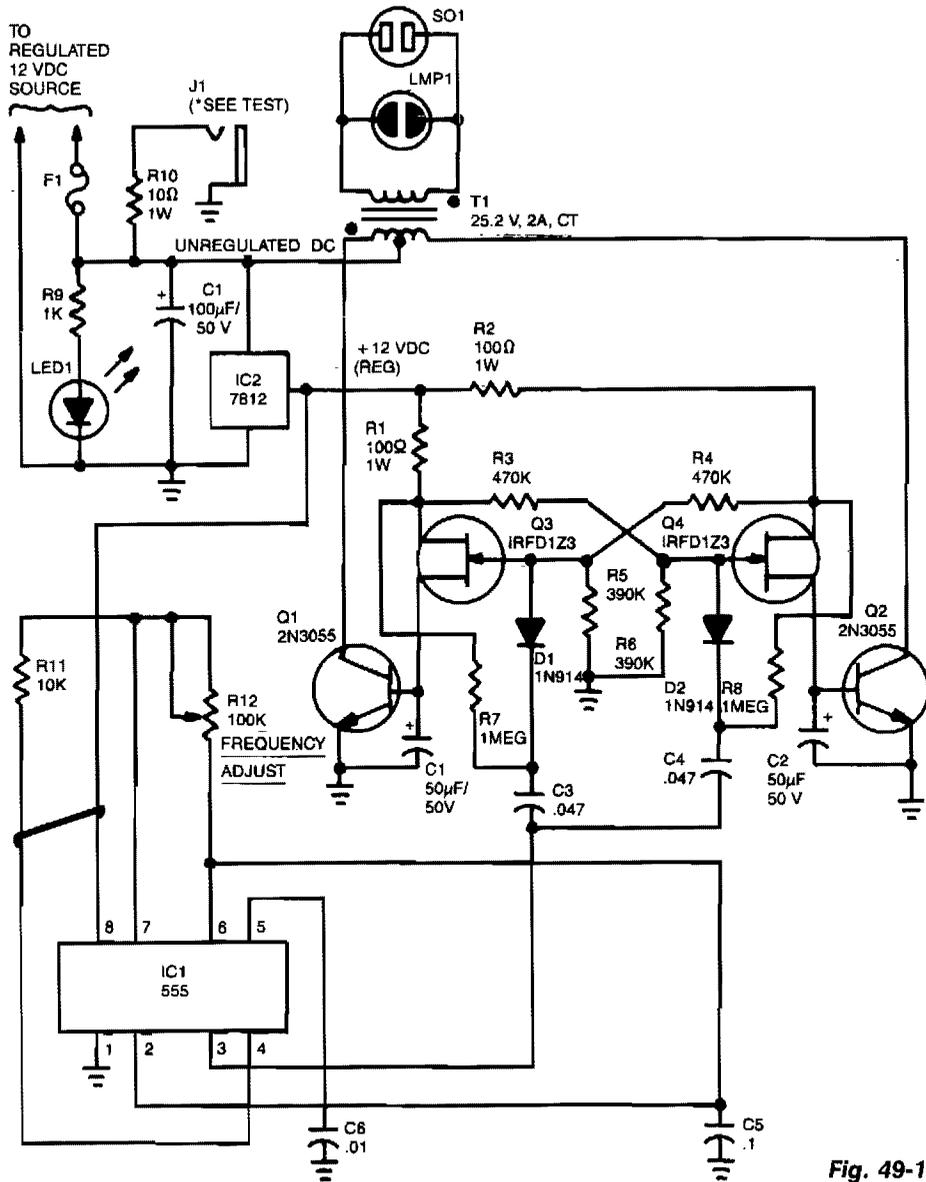

**Fig. 49-1**

Reprinted with permission from Radio-Electronics Magazine, 1987 R-E Experimenters Handbook. Copyright Gernsback Publications, Inc., 1987.


## 12 VDC-TO-117 VAC AT 60 Hz POWER INVERTER (Cont.)

Capacitor C5 and potentiometer R12 determine the frequency of the output signal at pin 3 of IC1, the 555 oscillator. The output signal is differentiated by C3 and C4 before it's input to the base of power transistors Q1 and Q2 via diodes D1 and D2, respectively. The signal from IC1 is adjusted to 120 Hz, because the flip-flop formed by transistors Q3 and Q4 divides the frequency by 2.

When Q3 is on, the base of Q1 is connected via R1 to the regulated 12-V supply. Then, when the flip-flop changes states, Q4 is turned on and the base of Q2 connected to the 12-V supply through R2. The 100 mA base current allows Q1 and Q2 to alternately conduct through their respective halves to the transformer's secondary winding.

To eliminate switching transients caused by the rapid switching of Q3 and Q4, capacitors C1 and C2 filter the inputs to the base of Q1 and Q2 respectively. Power for the unit comes from an automobile's 12-V system or from a storage battery. The power is regulated by IC2, a 7812 regulator. LED1, connected across the 12-V input, can be used to indicate whether power is being fed to the circuit. The neon pilot lamp, LMP1, shows a presence or absence of output power.

### POWER MOSFET INVERTER

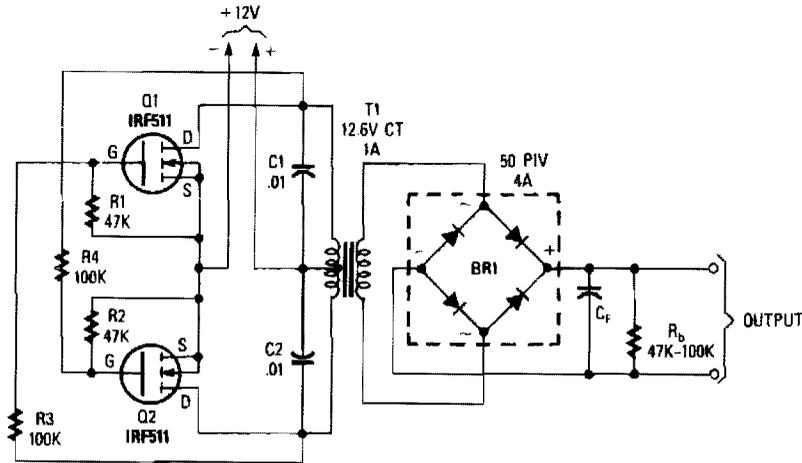


POPULAR ELECTRONICS

Fig. 49-2

This inverter can deliver high-voltage ac or dc, with a rectifier and filter, up to several hundred volts. The secondary and primary of T1—a 12.6 to 440 V power transformer, respectively—are reversed; e.g., the primary becomes the secondary and the secondary becomes the primary. Transistors Q1 and Q2 can be any power FET. Be sure to heat sink Q1 and Q2. Capacitors C1 and C2 are used as spike suppressors.

## MEDIUM POWER INVERTER

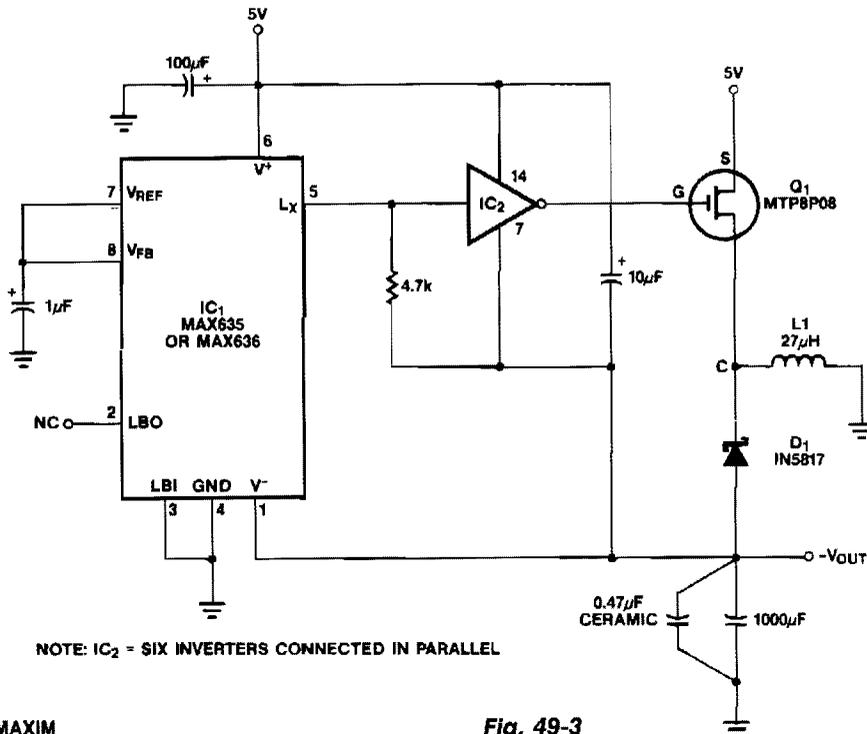

MAXIM


Fig. 49-3

In this circuit, a CMOS inverter, such as the CD4069, is used to convert the open drain  $L_x$  output to a signal suitable for driving the gate of an external P MOSFET. The MTP8P03 has a gate threshold voltage of 2.0 V to 4.5 V, so it will have a relatively high resistance if driven with only 5 V of gate drive. To increase the gate drive voltage, and thereby increase efficiency and power handling capability, the negative supply pin of the CMOS inverter is connected to the negative output, rather than to ground. Once the circuit is started, the P MOSFET gate drive swings from +5 V to  $-V_{OUT}$ . At start up, the  $-V_{OUT}$  is one Schottky diode drop above ground and the gate drive to the power MOSFET is slightly less than 5 V. The output should be only lightly loaded to ensure start up, since the output power capability of the circuit is very low until  $-V_{OUT}$  is a couple of volts.

This circuit generates complementary output signals from 50 to 240 Hz. Digital timing control ensures a separation of 10 to 15° between the fall time of one output and the rise time of the complementary output.

The digital portion of inverter U1 to U4 controls the drive to Q1 and Q2, both MTE60N20 TMOS devices. These devices are turned on alternately with 11.25° separation between complementary outputs. A +12-V supply for CMOS gates U1 to U4 is developed by T1, D3, D4, C7, and U6. The power supply for the TMOS frequency generator is derived from the diode bridge, U5, and capacitor C7; it is applied to the center tap of T2.
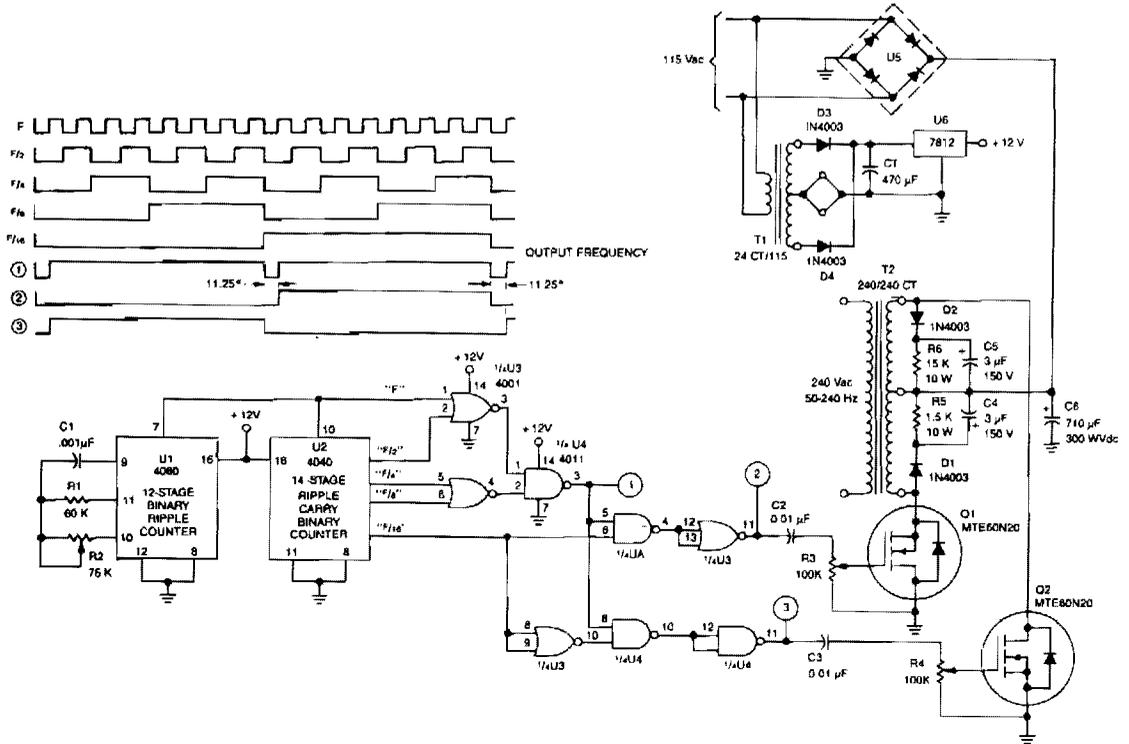
## COMPLEMENTARY OUTPUT VARIABLE FREQUENCY INVERTER




Copyright of Motorola, Inc. Used by permission.

**Fig. 49-4**

U1 is a 4060 12-stage binary ripple counter that is used as a free-running oscillator; its frequency of oscillation is:  $1/2.2 C1R2$ . The output of U1 is applied to U2, a 14-stage binary ripple counter that provides square-wave outputs of  $1/2$ ,  $1/4$ ,  $1/8$ , and  $1/16$  of the clock frequency. These signals are combined in U3 and U4 to provide a complementary drive for Q1 and Q2.

Outputs from U3 and U4 are ac-coupled to Q1 and Q2 via C2 and C4, respectively. R3 and R4 adjust the gate drive to Q1 and Q2. Q1 and Q2 alternately draw current through opposing sides of the primary to synthesize an ac input voltage at a given frequency. Only one side of the primary of T2 is driven at one time, so maximum power output is half of the transformer rating.

### PRECISION VOLTAGE INVERTER

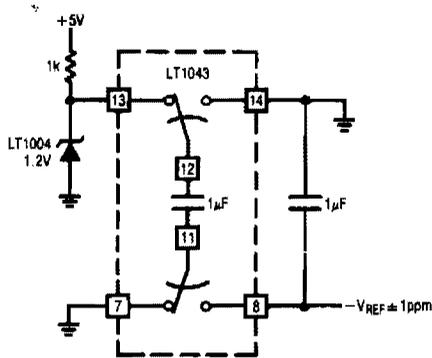


LINEAR TECHNOLOGY CORP.

Fig. 49-5

This circuit allows a reference to be inverted with 1 ppm accuracy, features high input impedance, and requires no trimming.

### POWER INVERTER

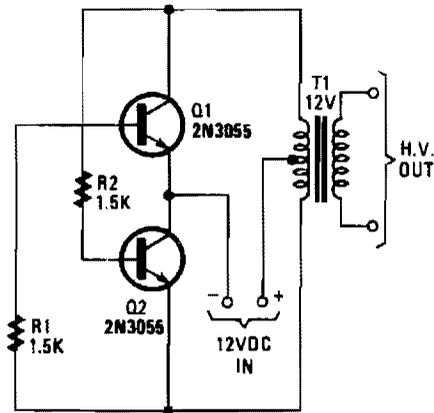

POPULAR ELECTRONICS

Fig. 49-6

The transformer can be any 6.3 or 12.6 V type. Apply the 12-Vdc input so the positive goes to the transformer's center tap and the negative goes to the two transistor emitters. Any bridge-type rectifier and filter can be used at the output, if you need dc.

# 50


## Lamp-Control Circuits

---



The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Halogen Lamp Dimmer	Solid-State Light Dissolver
Pseudorandom Sequencer	Line-Voltage Operated Automatic Night Light
Light Modulator	8-W Fluorescent Lamp Inverter
Lamp Life Extender	Pulse-Width Modulation Lamp Brightness Controller
Phase Control	Constant Brightness Control
Triac Light Dimmer	
800-W Soft-Start Light Dimmer	


## HALOGEN LAMP DIMMER

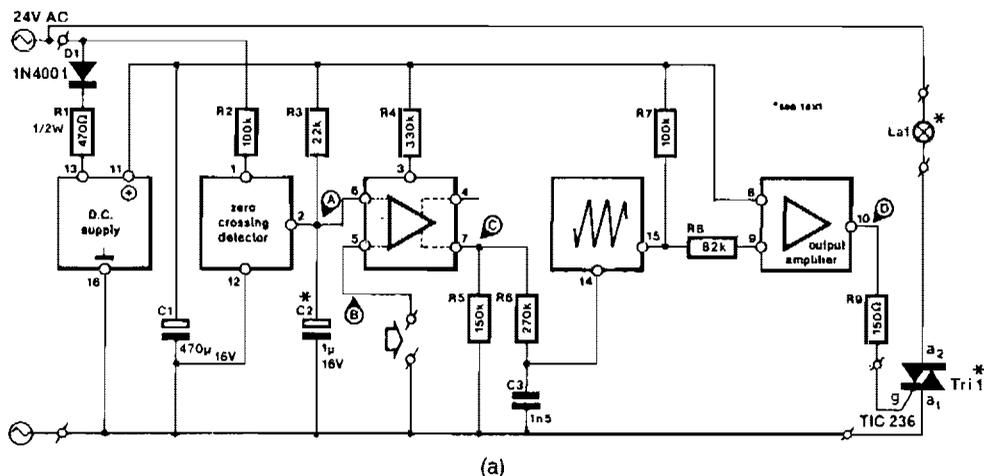

□ = IC1 = TCA 280 A

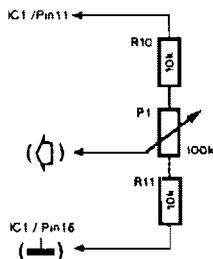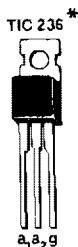

(b)

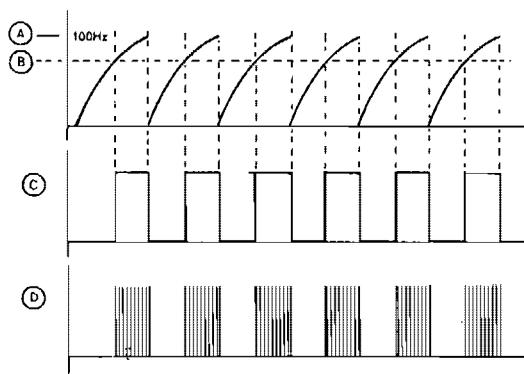

(c)


ELEKTOR ELECTRONICS

Fig. 50-1

This circuit is suitable for fitting into slide projectors without a dimmer facility as with 24-Vac fed halogen lamps. With a few small alterations, it can also be used for dimming 12-V halogen lamps, but not those in a car, because these are fed from a dc source. The circuit shown in Fig. 50-1a is intended for operation from a 24-Vac supply, and can handle a lamp load of up to 150 W. For loads up to 250 W, the TIC236 should be replaced by a TIC246.

Figure 50-1b shows detail of the connection of a potentiometer to the intensity control input of the TCA280A. Voltage divider R10-P1-R11 is fitted externally and can be fed from the stabilized voltage available at pin 11 of IC1. The minimum and maximum intensities of the lamp are determined by R10 and R11, respectively.

## PSEUDORANDOM SEQUENCER

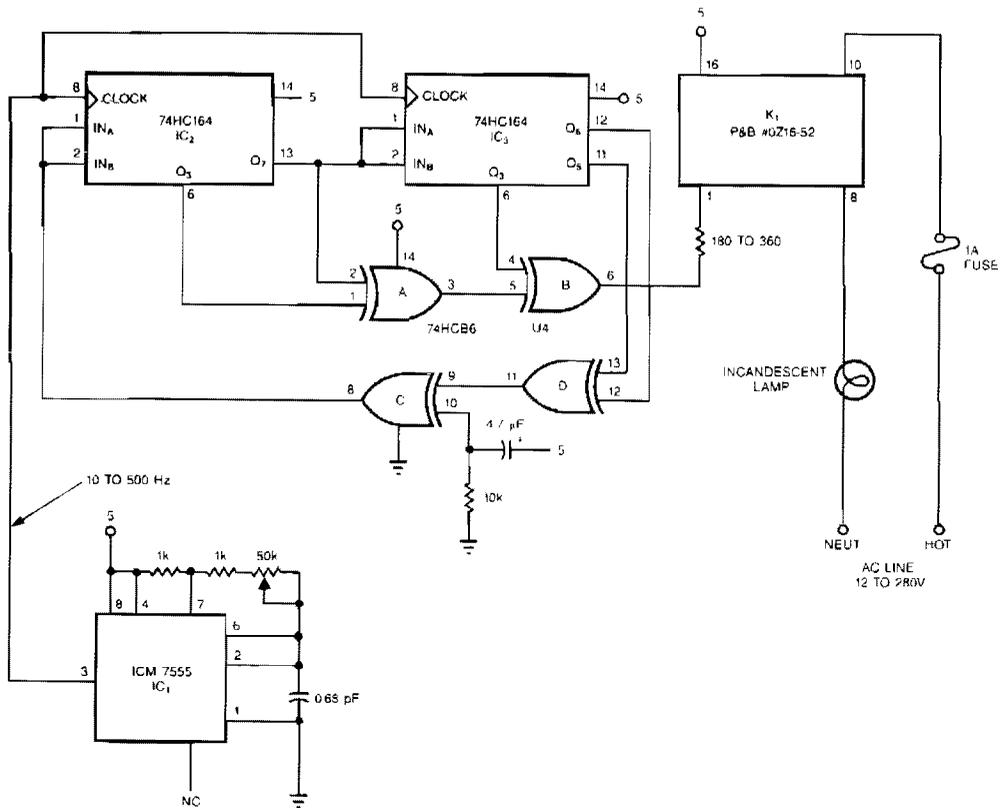


EDN

**Fig. 50-2**

This pseudorandom sequencer drives a solid-state relay. If you power a low-wattage lamp from the relay, the lamp will appear to flicker like a candle's flame in the wind; using higher-wattage lamps allows you to simulate the blaze of a fireplace or campfire. You can enhance the effect by using three or more such circuits to power an array of lamps.

The circuit is comprised of an oscillator IC1 and a 15-stage, pseudorandom sequencer, IC2 through IC4. The sequencer produces a serial bit stream that repeats only every 32, 767 bits. Feedback from the sequencer's stages 14 and 15 go through IC4D and back to the serial input of IC2. Note the rc network feeding IC4C; the network feeds a positive pulse into the sequencer to ensure that it won't get stuck with all zeros at power-up. The leftover XOR gates IC4A and IC4B further scramble the pattern. The serial stream from IC4B drives a solid-state relay that features zero-voltage switching and can handle loads as high as 1 A at 12 to 280 Vac.

## LIGHT MODULATOR

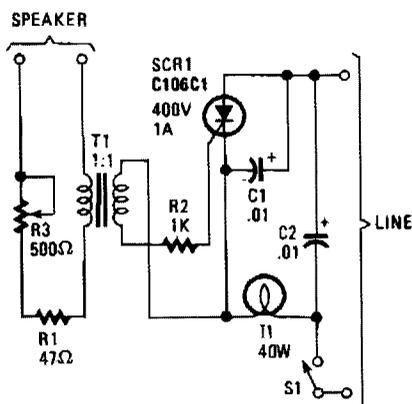


The lights seem to dance in time with the music. Line-voltage lamps of about 40 to 100 W do nicely. The current for the lamp is from an SCR. When low-level audio is present across T1, SCR1 is not triggered into conduction. A louder signal, however, triggers the SCR so that the lamp lights and follows the sounds. Since SCR1 is operated by an alternating current, the rectifier moves out of the avalanche condition when the gate current is low. Potentiometer R3 lets you adjust the power reaching transformer T1, so that with normal operating volume, SCR1 triggers again and again, except during quiet passages.

HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

Fig. 50-3

## LAMP LIFE EXTENDER

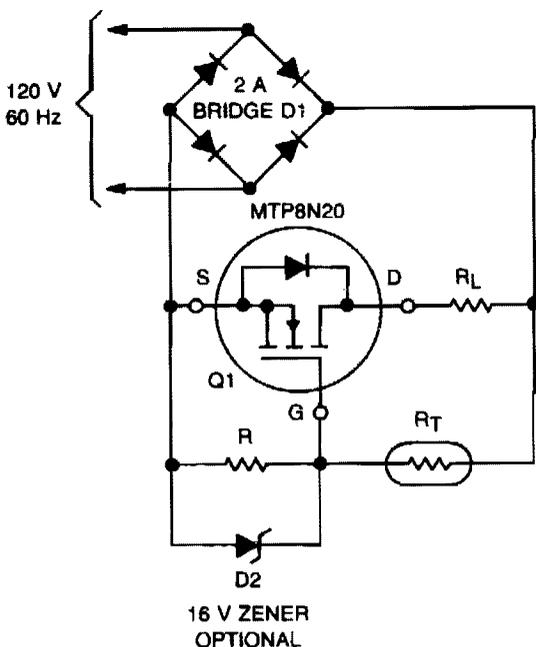

Lamp life can be extended by improving the conditions under which its filament is operated. This includes eliminating the inrush overcurrent surge and reducing the mechanical stress (vibration) on the filament caused by an ac source.

The circuit shown controls the inrush current to the lamp without the 10 to 15 times-rated current stage that normally occurs when power is applied to a cold lamp. It does so by adjusting the inrush current over time to the inverse of the value normally experienced.


$R_L$  is a standard tungsten lamp in the range of 15 to 250 W,  $R$  is 10- $\Omega$  and  $R_T$  is a negative temperature coefficient resistance that is initially 1.65 M $\Omega$  and decreases, by self-heating, to 150 K $\Omega$  in approximately 0.5 s. Use of the TMOS device allows high  $\Omega$  values for  $R$  and  $R_T$ , keeping drive power at a negligible level.

This circuit has a number of advantages: very low power dissipation, long life, low-cost components, no significant effect on lamp ratings, negligible effect on efficiency, negligible RFI, and it can be used in hazardous environments.

Copyright of Motorola, Inc. Used by permission.

Fig. 50-4

## PHASE CONTROL

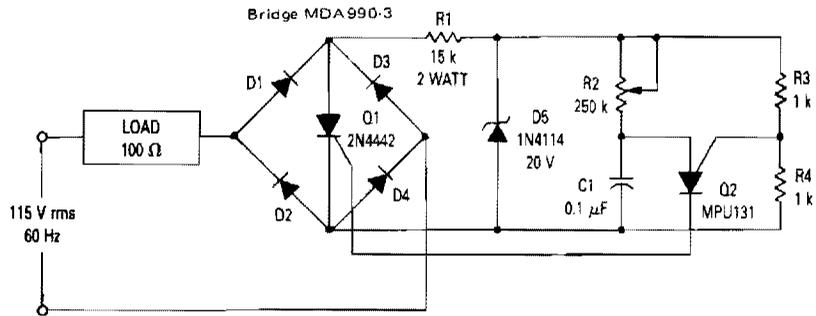


Copyright of Motorola, Inc. Used by permission.

**Fig. 50-5**

This circuit uses a PUT for phase control of an SCR. The relaxation oscillator formed by Q2 provides conduction control of Q1 from 1 to 7.8 ms or  $21.6^\circ$  to  $168.5^\circ$ . This constitutes control of over 97% of the power available to the load. Only one SCR is needed to provide phase control for both the positive and negative portion of the sine wave by putting the SCR across the bridge—composed of diodes D1 through D4.

## TRIAC LIGHT DIMMER

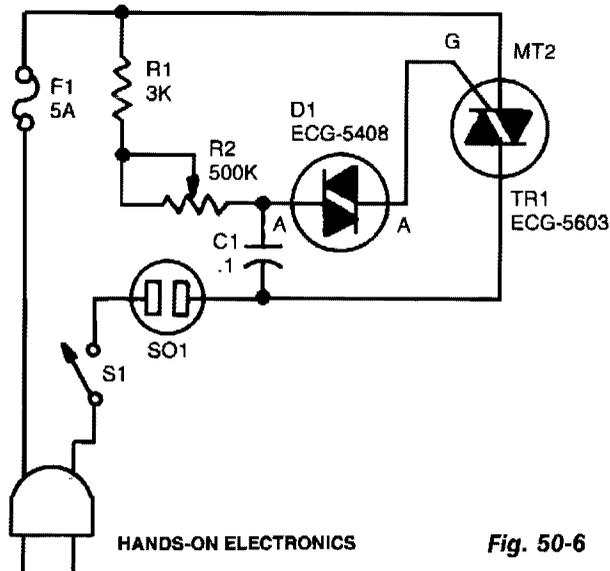

HANDS-ON ELECTRONICS


**Fig. 50-6**



## SOLID-STATE LIGHT DISSOLVER (Cont.)

The dimming action is controlled by varying the amount of current passed through triac Q4 and, thus, the lamp plugged into ac receptacle SO1. Unijunction transistor Q3 operates as a relaxation oscillator whose output pulse frequency depends on how fast capacitor C2 recharges after firing. Transistors Q1 and Q2 furnish the charging current, with the R3/C1 and R1/R2/C1 time-constant networks controlling the turn-on and turn-off times. Inside IC1 is a LED, a detector, and a small triac. In circuit, the low-level pulses coming from Q3 make the LED in IC1 emit short bursts of light that are picked up and converted into electrical current pulses by the internal detector. This small current triggers the internal triac, which then outputs the pulses to the gate of power triac Q4, triggering it on so that it delivers current to the lamp. Potentiometer R4 serves as a master control of the pulse rate and provides both manual control and a limit in the brightness of the lamp plugged into SO1. Momentarily pressing S2 causes the lamp to instantly turn on. Choke L1 suppresses any spikes produced by the power triac and limits interference with AM radio reception. No safeguards against interference need to be made for FM and TV reception, since these media are immune to this type of noise.

## PHASE CONTROL

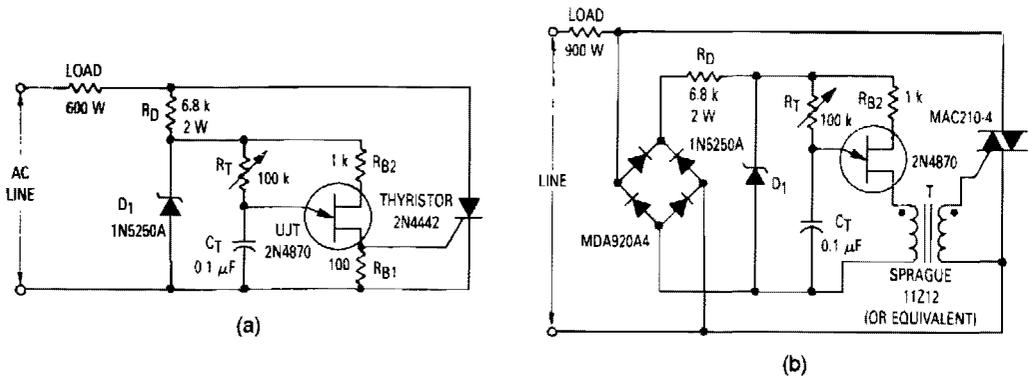


Copyright of Motorola, Inc. Used by permission.

Fig. 50-9

The most elementary application is a half-wave control circuit. The thyristor is acting both as a power control device and as a rectifier, providing variable power to the load during the positive half cycle and no power to the load during the negative half cycle. The circuit is designed to be a two terminal control which can be inserted in place of a switch. If full-wave power is desired as the upper extreme of this control, a switch can be added which will short circuit the SCR when  $R_T$  is turned to its maximum power position. Full-wave control might be realized by the addition of a bridge rectifier, a pulse transformer, and by changing the thyristor from an SCR to a TRIAC, shown in Fig 50-9b. In this circuit,  $R_{B1}$  is not necessary since the pulse transformer isolates the thyristor gate from the steady-state UJT current. Occasionally, a circuit is required to provide constant output voltage regardless of line voltage changes. Adding potentiometer P1 to the circuits will provide an approximate solution to this problem. The potentiometer is adjusted to provide reasonably constant output over the desired range of line voltage.

## LINE-VOLTAGE OPERATED AUTOMATIC NIGHT LIGHT

SUGGESTED TRIAC	LAMP WATTAGE MAXIMUM	
	120V	220V
SC141D	400W	800W
SC146D	550W	1100W
SC161D	750W	1500W
SC280D	1200W	2500W
SC265D	2000W	4000W

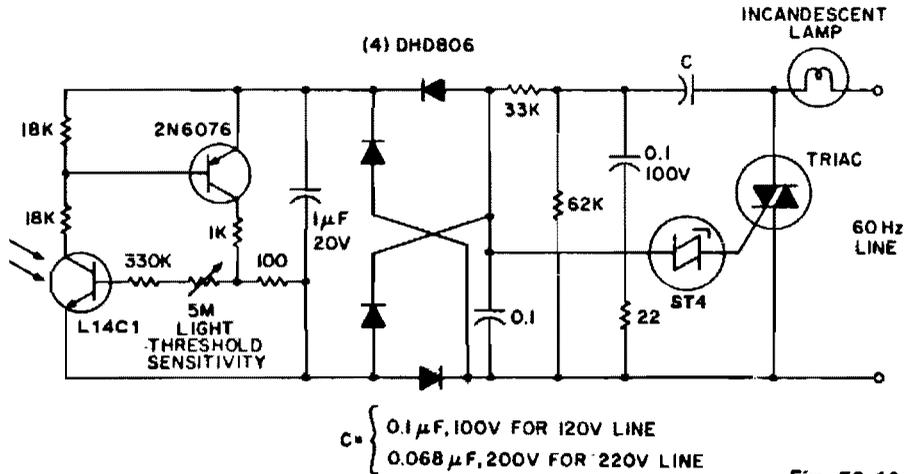

GE

Fig. 50-10

This circuit has stable threshold characteristics from its dependence on the photo diode current in the L14C1 to generate a base emitter voltage drop across the sensitivity setting resistor. The double phase shift network supplying voltage to the ST-4 trigger insures triac triggering at line voltage phase angles small enough to minimize RFI problems with a lamp load. This eliminates the need for a large, expensive inductor, contains the dV/dt snubber network, and utilizes lower voltage capacitors than the snubber of rfi suppression network normally used. The addition of a programmable unijunction timer can modify this circuit to turn the lamp on for a fixed time interval each time its environment gets dark. Only the additions to the previous circuit are shown in the interest of simplicity. When power is applied to the lamp, the 2N6028 timer starts. Upon completion of the time interval, the H11C3 is triggered and turns off the lamp by preventing the ST-4 from triggering the triac. The SCR of the H11C3 will stay on until the L14C1 is illuminated and allows the 2N6076 to commutate it off. Because of capacitor leakage currents, temperature variations and component tolerances, the time delay may vary considerably from nominal values.

## 8-W FLUORESCENT LAMP INVERTER


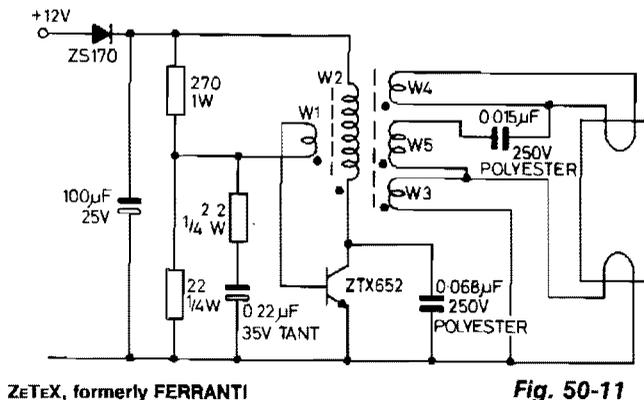


Fig. 50-11

## 8-W FLUORESCENT LAMP INVERTER (Cont.)

This circuit has been designed to drive an 8-W fluorescent lamp from a 12-V source using an inexpensive inverter based on the ZTX652 transistor. The inverter will operate from supplies in the range of 10 to 16.5 V, thus making it suitable for use in on-charge systems such as caravanettes as well as periodically charged systems, such as camping lights, outhouse lights, etc. Other features of the inverter are an inaudible 20-kHz oscillator and reverse polarity protection.
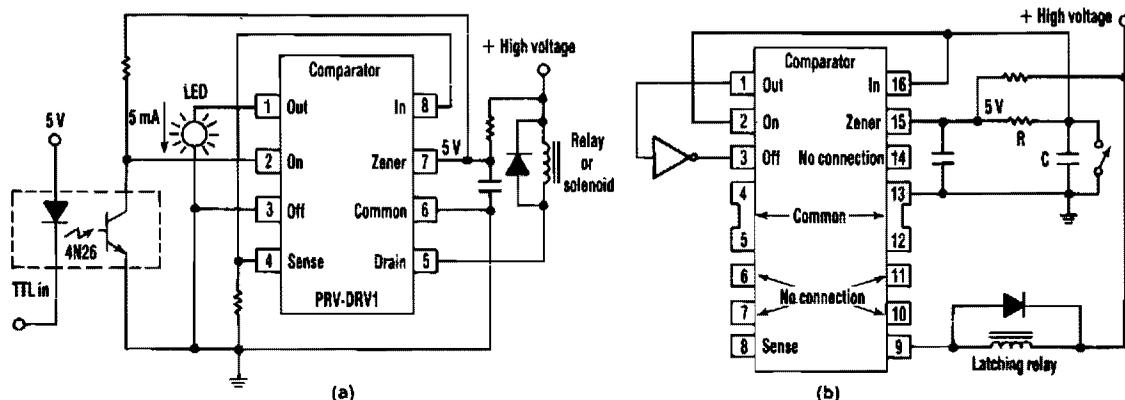
### PULSE-WIDTH MODULATION LAMP BRIGHTNESS CONTROLLER




ELECTRONIC DESIGN

Fig. 50-12

At half brightness, the lamp current is pulsed on and off (Fig. 50-12b) by the voltage developed across the resistor and capacitor at the current-sense output. Lamp current is sensed by the current-sense output. A simple pulse-width modulation lamp-brightness control circuit can also be built with the device. When the device powers up, the sense output is low, pulling the comparator output and the on input low, and turning the FET switch on. When the switch is on, current from the sense output charges the capacitor in the rc timing network to the 200-mV comparator threshold voltage. The comparator trips, turning the switch off. The charge then leaks off the capacitor, its voltage drops below 100 mV, and the FET is again turned on. The average current through the load is basically a function of the resistor value. The pulse-width modulation frequency on the other hand, is a function of the capacitor value.

## CONSTANT BRIGHTNESS CONTROL

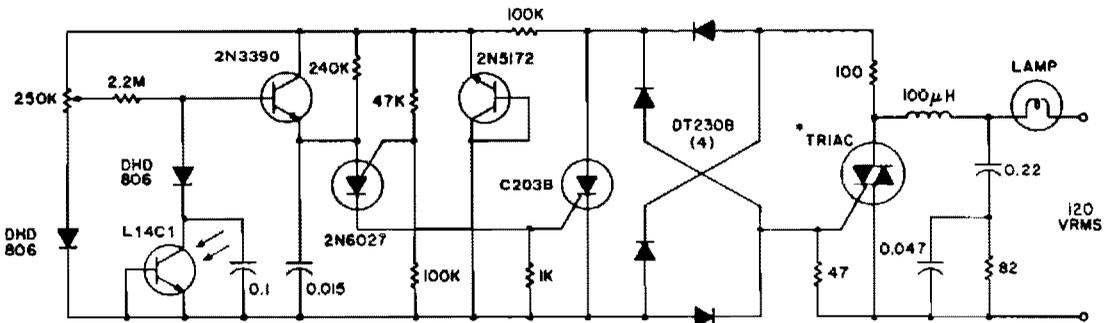

\*The triac is matched to the lamp per chart

SUGGESTED TRIAC	LAMP WATTAGE MAXIMUM	
	120V	220V
SC141D	400W	800W
SC146D	550W	1100W
SC151D	750W	1500W
SC260D	1200W	2500W
SC265D	2000W	4000W

GE

**Fig. 50-13**

An automatic control maintains a lamp at a constant brightness over a wide range of supply voltages. This circuit utilizes the consistency of photodiode response to control the phase angle of power line voltage applied to the lamp and can vary the power between that available and  $\approx 30\%$  of available. This provides a candlepower range from 100% to less than 10% of nominal lamp output. The 100- $\mu$ H choke, resistor, and capacitors form an rlc filter network that is used to eliminate conducted RFI.

# 51


## Laser Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Visible Red Continuous Laser Gun  
Laser Diode Pulsers

## VISIBLE RED CONTINUOUS LASER GUN

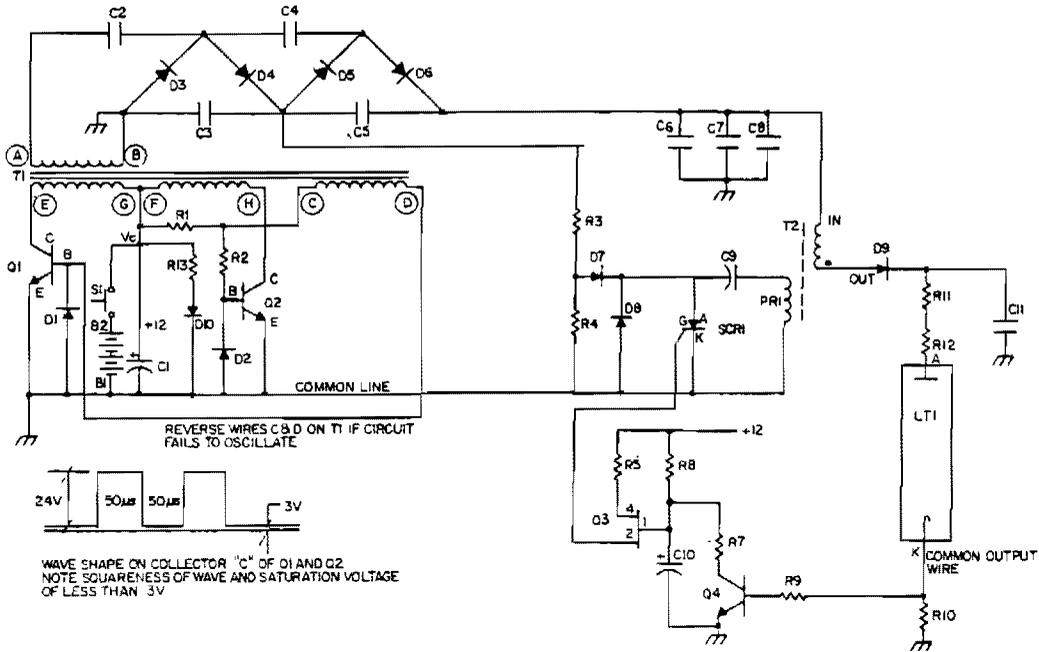


TAB BOOKS

**Fig. 51-1**

Q1 and Q2 switch the primary windings of transformer T1 via a square wave at a frequency determined by its magnetic properties. Diodes D1 and D2 provide base return paths for the feedback current of Q1 and Q2. The output winding of T1 is connected to a multiple section voltage multiplier. That multiplier consists of capacitors C1 through C5 and diodes D3 through D6. Resistors R3 and R4 divide the 800 V taken off at the junction of C3, and C5 for charging the dump capacitor C9 in the ignitor circuit. The ignitor, consisting of the T2 pulse transformer and capacitor discharge circuitry, provides the high-voltage dc pulse to ignite the laser the SCR1 dumping the energy of capacitor C9 into the primary of T2. The high-voltage pulses in capacitor C11 through rectifier diode D9. When C11 is charged to a LT1, ignition takes place and a current now flows that is sufficient to sustain itself at the lower voltage output of the voltage multiplier section. The path for this sustaining current is through the secondary of T2 and ballast resistors R11 and R12. The ignitor circuit is now deactivated by the clamping of Q3 emitter via Q4 being turned on by the voltage drop occurring across R10. This voltage drop will only occur when the laser tube is ignited and causes the SCR1 to cease firing; otherwise, the ignitor circuit would continue to operate, unnecessarily drawing on the limited power available.

## LASER DIODE PULSERS

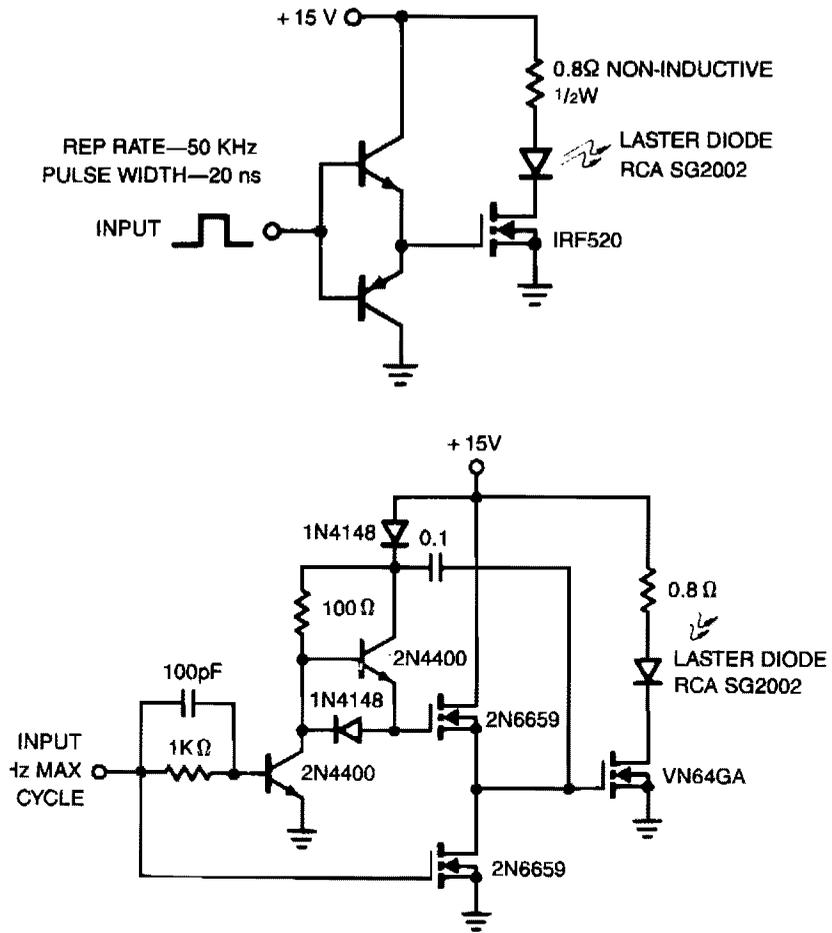

SILICONIX

Fig. 51-2

The laser diode pulser is a simple drive circuit capable of driving the laser diode with 10-A, 20-ns pulses. For a 0.1% duty cycle, the repetition rate will be 50 kHz. A complementary emitter follower is used as a driver. Switching speed is determined by the  $f_T$  of the bipolar transistors used and the impedance of the drive source. A faster drive circuit is shown. It can supply higher peak gate current to switch the IRF520 very quickly. This circuit uses a MOSPOWER totem-pole stage to drive the high power switch. The upper MOSFET is driven by a bootstrap circuit. Typical switching times for this circuit are about 10 ns for both turn-on and turn-off.

# 52


## Light-Controlled Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Flame Monitor	Lighted Display and Brightness Control
Low-Light Level Drop Detector	Warning Light and Marker Light
Light-Controlled Lamp Switch	Light-Controlled One-Shot Timer
Optical Sensor-to-TTL Interface	Solar-Triggered Switch
Light-Sensitive Audio Oscillator	Sun Tracker
Light Level Detector	Photoelectric Ac Power Switch


## FLAME MONITOR

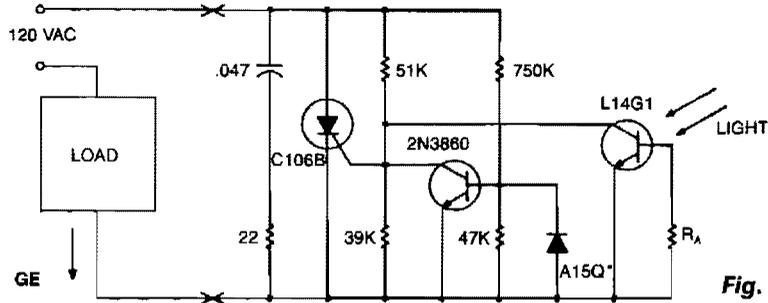

**Fig. 52-1**

Monitoring a flame and directly switching a 120-V load is easily accomplished using the L14G1 for point sources of light. For light sources which subtend over  $10^\circ$  of arc, the L14C1 should be used and the illumination levels raised by a factor of 5. This circuit provides zero voltage switching to eliminate phase controlling.

## LOW-LIGHT LEVEL DROP DETECTOR

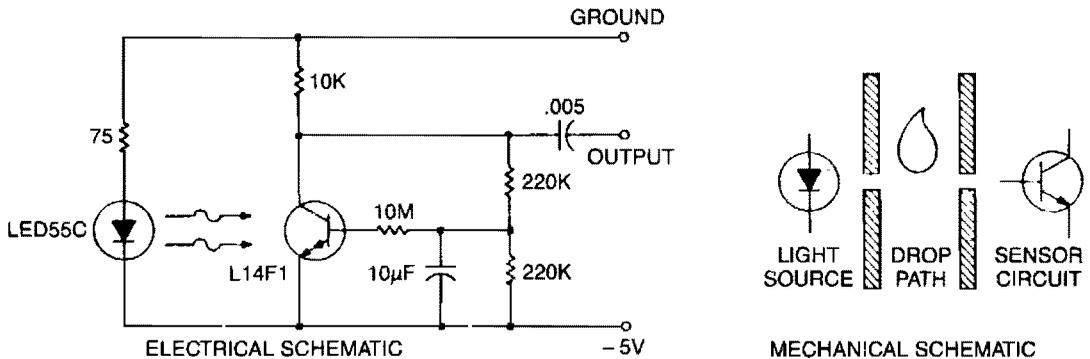

GE

**Fig. 52-2**

This self-biasing configuration is useful any time small changes in light level must be detected, for example, when monitoring very low flow rates by counting drops of fluid. In this bias method, the photodarlington is dc bias stabilized by feedback from the collector, compensating for different photodarlington gains and LED outputs. The  $10\text{-}\mu\text{F}$  capacitor integrates the collector voltage feedback, and the  $10\text{-M}\Omega$  resistor provides a high base-source impedance to minimize effects on optical performance. The detector drop causes a momentary decrease in light reaching the chip, which causes collector voltage to momentarily rise, generating an output signal. The initial light bias is small because of output power constraints on the LED and mechanical spacing system constraints. The change in light level is a fraction of this initial bias because of stray light paths and drop translucence. The high sensitivity of the photodarlington allows acceptable output signal levels when biased in this manner. This compares with unacceptable signal levels and bias point stability when biased conventionally, i.e., base open and signal output across the collector bias resistor.

## LIGHT-CONTROLLED LAMP SWITCH


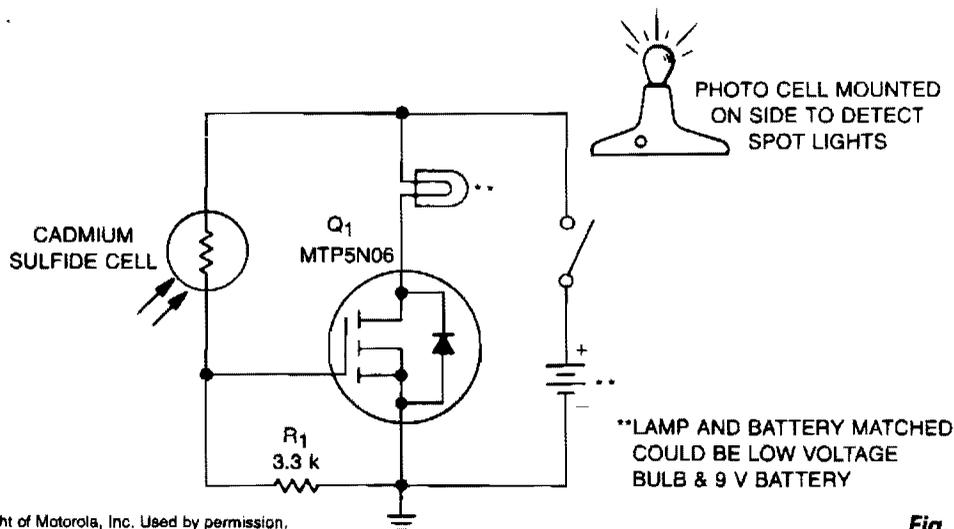


Fig. 52-3

A school drama needed lamps that automatically turned on and off when spot lights did the same. Lamp switching had to be wireless, durable, dependable, simple and inexpensive.

With stage and spot lights off, very little light falls on the CdS photocell, so its internal resistance is several megohms and R1 keeps the gate of Q1 at nearly zero volts, which keeps it off. When a spot or stage light hits the photocell, its resistance drops to several hundred ohms, raising Q1's gate voltage, which turns it on and applies power to the lamp.

## OPTICAL SENSOR-TO-TTL INTERFACE

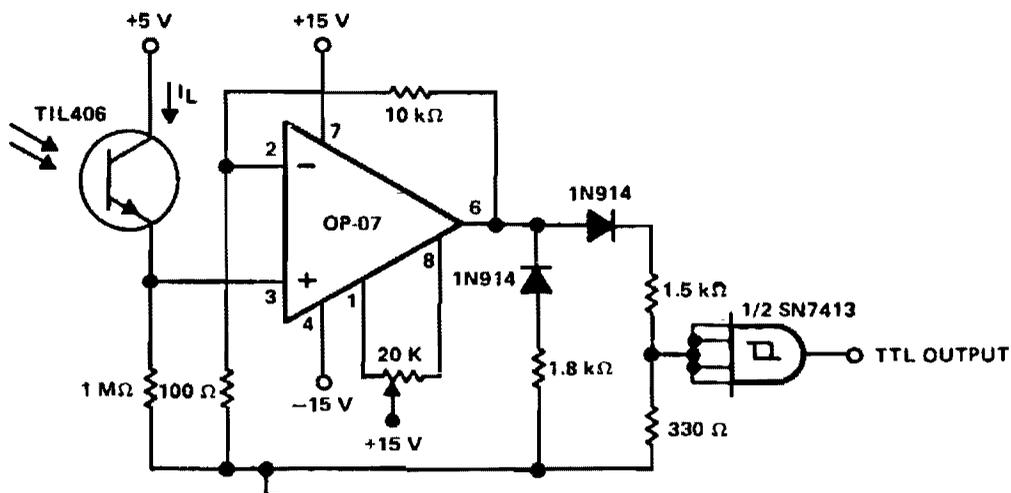


Reprinted by permission of Texas Instruments.

Fig. 52-4

## OPTICAL SENSOR-TO-TTL INTERFACE (Cont.)

This circuit is designed to detect a low light level at the sensor, amplify the signal, and provide a TTL-level output. When the optical sensor detects low-level light, on condition, its output is small and must be amplified. An amp with very low input bias current and high input resistance must be used to detect the on condition. When sensor TIL406 is in the on condition, its output is assumed to be 250 nA (allowing a safety margin). This results in a 250-mV signal being applied to the noninverting input of amplifier OP-07. Because of the circuit configuration, the OP-07 provides a gain of 100 and its output is in positive saturation. The OP-07 output level is applied to a loading network that provides the basic TTL level.

### LIGHT-SENSITIVE AUDIO OSCILLATOR

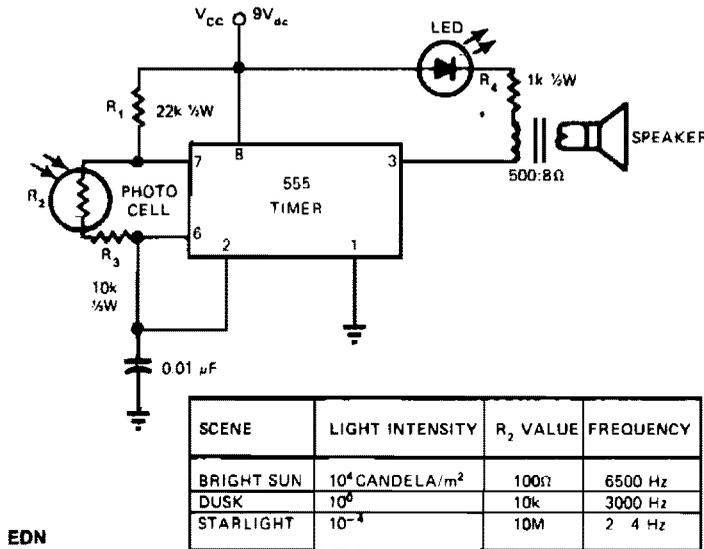


**Fig. 52-5**

This circuit's frequency of oscillation increases directly with light intensity. The greater the light intensity, the higher the frequency of the oscillator. The 555 timer operates in the astable oscillator mode where frequency and duty cycle are controlled by two resistors and one capacitor. The capacitor charges through R1 and R2, and discharges through R2, a standard photo cell. Resistor R3 limits the upper frequency of oscillation to the audio range. The lower range of approximately 1 pps is set by the value of R2, approximately 10-MΩ, with the photo cell almost totally dark.

A loudspeaker provides audio output, and an LED is used as a pilot light that flashes when the frequency falls below about 10 to 12 Hz. Extremely sensitive, especially on the dark end of the photocell resistance range, the unit can detect lightning many miles away, providing a rapid frequency increase with each flash of lightning. When used with a flashlight at night, the device becomes a simple optical radar for the blind, showing angular direction to a light-reflecting object, as well as height and distance to the object when hand scanned back and forth.


This light-sensitive audio oscillator can also serve as an audible horizontal level device by noting the position of a liquid bubble illuminated by a light source. Thus, you can sense fluid levels as well as the vibration state of a fluid surface level.

## LIGHT LEVEL DETECTOR

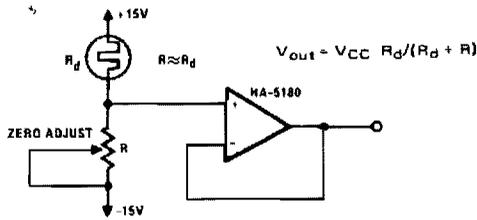

Cadmium Sulfide cells control two light detection circuits

(A)

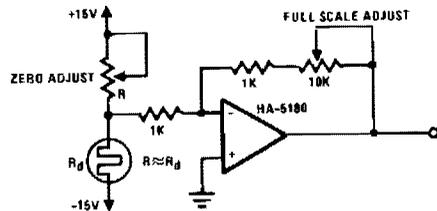

Cadmium Sulfide cells control two light detection circuits


(B)

HARRIS

Fig. 52-6

If  $R$ , the sensor matching resistor, is equal to the "dark" resistance of the cadmium sulfide cell, the amplifier output will range from 0 to  $\approx 2$  as the light level ranges from "dark" to "bright." The circuit in Fig. B operates similarly, but use the standard noninverting configuration instead of the voltage-follower configuration; this allows for variable gain. Although the "dark" resistance of the cadmium sulfide cell is only  $\approx 7 \text{ K}\Omega$ , the principles of operation apply to other types of detectors which require the high-input impedance of the HA-5180 for reasonable linearity and useability.

## LIGHTED DISPLAY BRIGHTNESS CONTROL

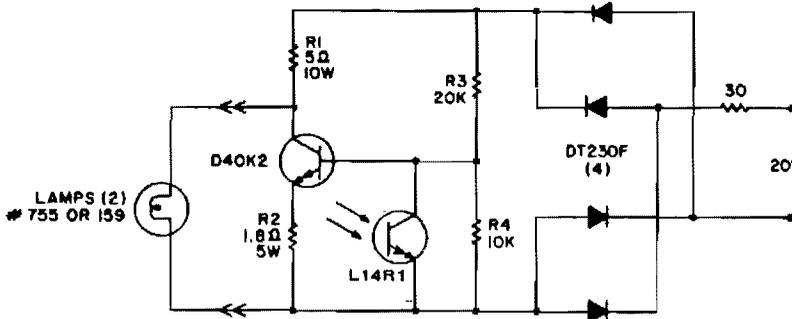


GE

Fig. 52-7


This circuit provides a very low cost method of controlling light levels. Circuit power is obtained from a relatively high source impedance transformer or motor windings, normally used to drive the low-voltage lamps used in these functions. It should be noted that the bias resistors are optimized for the 20-V, 30- $\Omega$  source, and they must be recalculated for other sources. The L14R1 is placed to receive the same ambient illumination as the display and should be shielded from the light of the display lamps. The illumination level of lighted displays should be lowered as the room ambient light dims, to avoid undesirable or unpleasant visual effects.



### SOLAR-TRIGGERED SWITCH

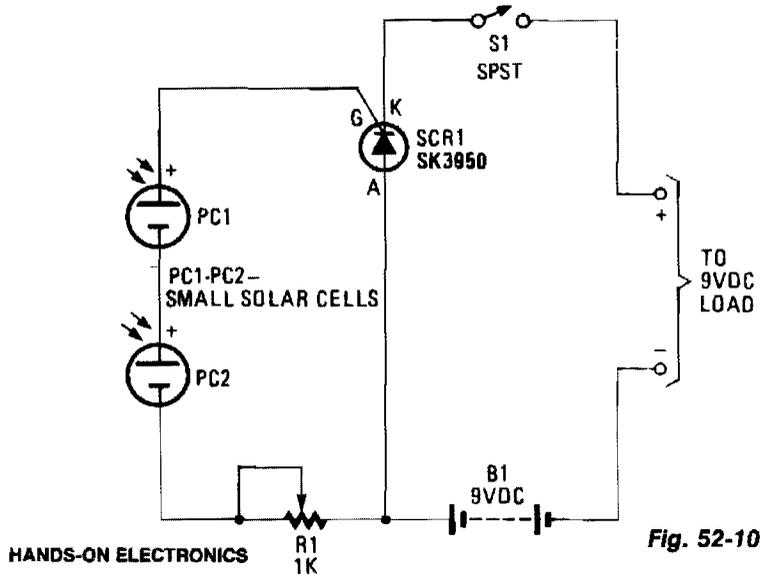

### SUN TRACKER

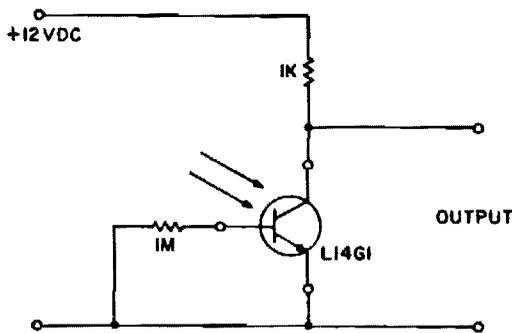


GE  
Electrical



Mechanical  
Fig. 52-11

In solar cell array applications and solar instrumentation, it is desirable to monitor the approximate position of the sun to allow efficient automatic alignment. The L14G1 lens can provide about  $15^\circ$  of accuracy in a simple level sensing circuit, and a full hemisphere can be monitored with about 150 phototransistors. The sun provides  $\approx 80 \text{ mW/cm}^2$  to the L14G1 when on the centerline. This will keep the output down to  $\leq 0.5 \text{ V}$  for  $\theta \leq 7.5^\circ$ . The sky provides  $\approx 0.5 \text{ mW/cm}^2$  to the L14G1 and will keep the output greater than  $10 \text{ V}$  when viewed. White clouds viewed from above can lower this voltage to  $\approx 5 \text{ V}$  on some devices. This circuit can directly drive TTL logic by using the 5-V supply and changing the load resistor to  $430 \Omega$ . Different bright objects can also be located with the same type of circuitry simply by adjusting the resistor values to provide the desired sensitivity.

## PHOTOELECTRIC AC POWER SWITCH

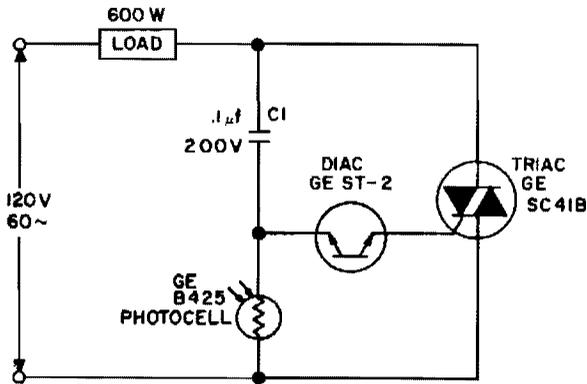

For a dark photocell, high resistance, the voltage across the diac rises rapidly with the line voltage due to the current through C1, triggering the diac early in the cycle. When the photocell resistance is less than about  $2000 \Omega$ , the drop across it is limited to less than the diac triggering voltage, and the load power is shut off.

GE

Fig. 52-12

# 53


## Limiters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Noise Limiter  
Dynamic Noise Reduction Circuit  
Output Limiter

## NOISE LIMITER

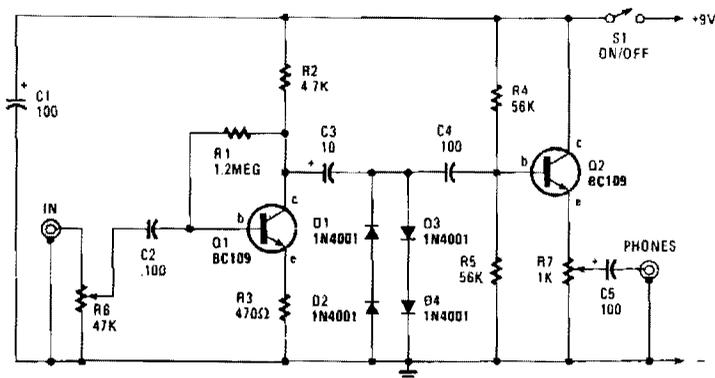


HANDS-ON ELECTRONICS

**Fig. 53-1**

This circuit is fed from the earphone jack of your receiver and goes to limiter control R6 and is then amplified by Q1: a common-emitter stage that has a voltage gain of only about 10, because of the negative feedback introduced by R3. The output of Q1 is fed to a simple clipping circuit, consisting of diodes D1 through D4. The diodes, connected in pairs, act like Zeners with an avalanche rating of about 1 V. The two pairs are connected opposite in polarity to each other, so that the audio signal is clipped at about 1 V. The signal is then coupled to the output socket through an emitter-follower buffer stage built around Q2 and an output attenuator control R7.


## DYNAMIC NOISE REDUCTION CIRCUIT

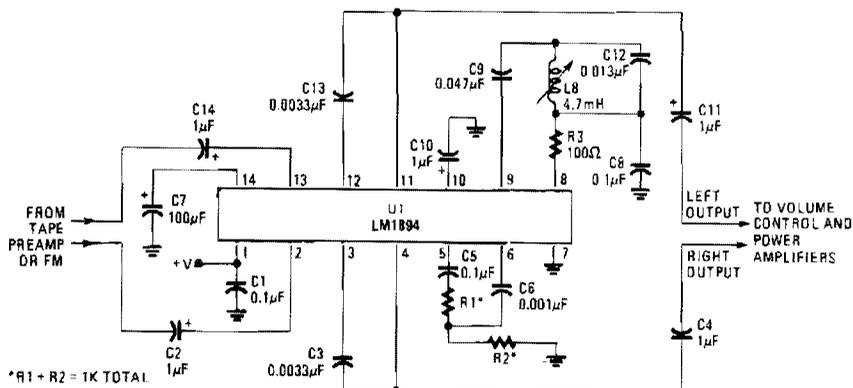

POPULAR ELECTRONICS

**Fig. 53-2**

## OUTPUT LIMITER

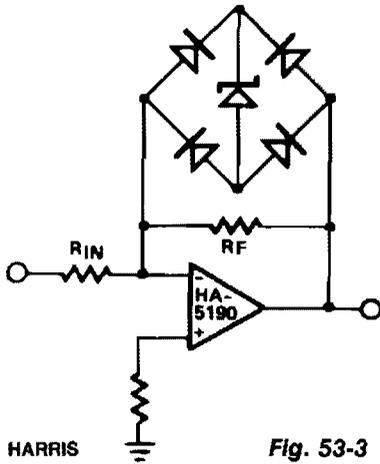

HA-5190 is rated for  $\pm 5$  V output swing, and saturates at  $\pm 7$  V. As with most op amps, recovery from output saturation is slow compared to the amplifier's normal response time. Some form of limiting, either of the input signal or in the feedback path, is desirable if saturation might occur. The circuit illustrates a feedback limiter, where gain is reduced if the output exceeds  $\pm (V_Z + 2V_f)$ . A 5-V zener with a sharp knee characteristic is recommended.

HARRIS

Fig. 53-3

# 54


## LVDT Circuit

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

LVDT Driver Demodulator

## LVDT DRIVER DEMODULATOR

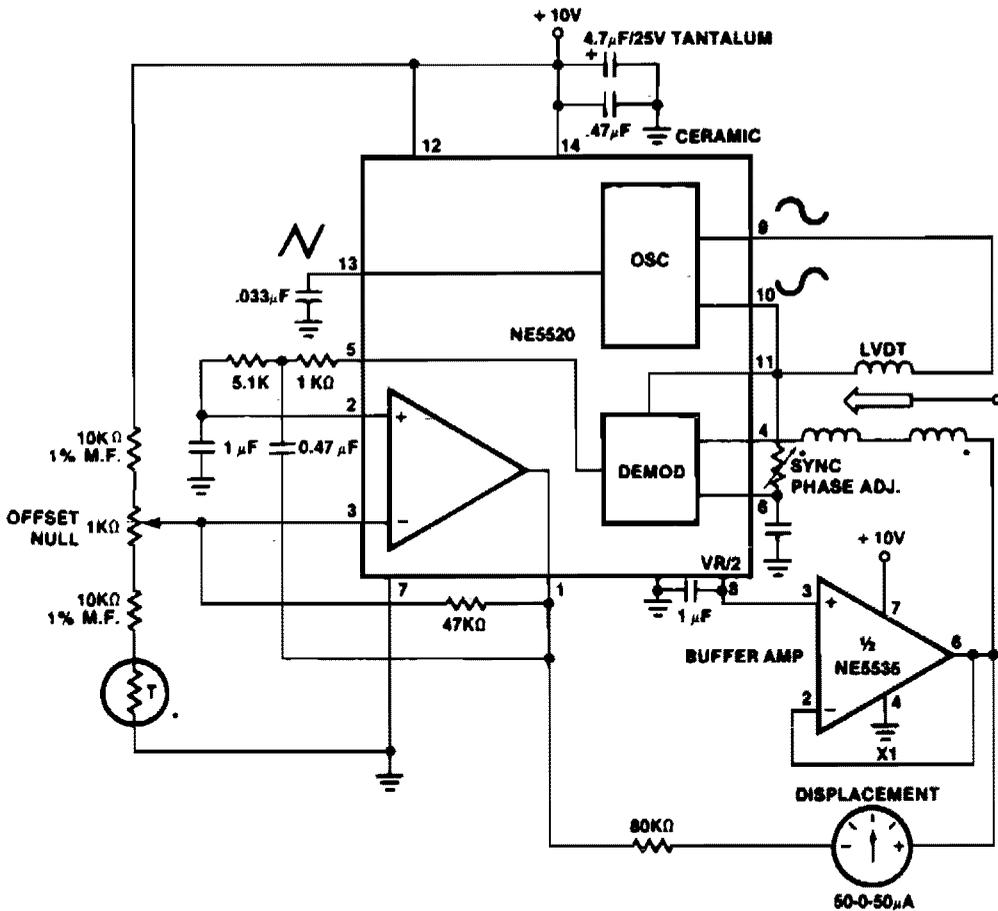

SIGNETICS

Fig. 54-1

A very simple motion transducer can be constructed using the circuit shown. The output is biased to one-half the supply voltage. This requires special interface circuitry for the signal readout. One simple method is to use a zero center meter in a bridge configuration. Displacement now can be measured as a positive or negative meter reading. Readout sensitivity is a function of the particular LVDT and of the gain of the error amplifier. Dc offsets can be nulled by using a simple offset adjustment circuit as indicated.

# 55

## Mathematical Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Divide/Multiply with Only One Trim

Adder

Subtractor



### ADDER

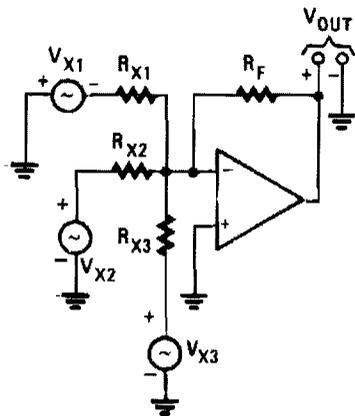


$$V_{OUT} = - \frac{R_F}{R_X} (V_{X1} + V_{X2} + V_{X3})$$

$$(R_{X1} = R_{X2} = R_{X3})$$

HANDS-ON ELECTRONICS

Fig. 55-2

### SUBTRACTOR

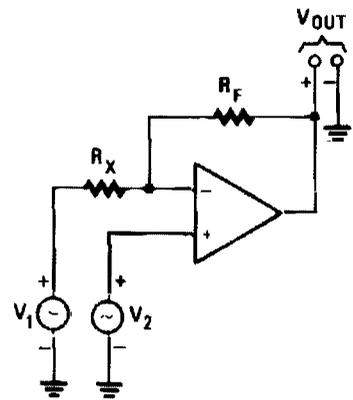

$$V_{OUT} = V_2 + \frac{R_F}{R_X} (V_2 - V_1)$$

HANDS-ON ELECTRONICS

Fig. 55-3

# 56


## Measuring and Test Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Duty Cycle Monitor	Motor Hour Meter
3-in-1 Test Set	Stud Finder
Stereo Power Meter	Low-Power Magnetic Current Sensor
Wide-Range Rf Power Meter	Line-Current Monitor
LED Peak Meter	S Meter
Lc Checker	Hot-Wire Anemometer
Tachometer and Direction-of-Rotation Circuit	Audible Logic Tester
Very Short Pulse-Width Measurer	SCR Tester
QRP SWR Bridge	Digital Frequency Meter
Electrostatic Detector	Low-Current Measurement System
Current Monitor and Alarm	Simple Continuity Tester
Picoammeter Circuit	Sound-Level Meter
Paper Sheet Discriminator for Printing and Copying Machines	LED Panel Meter
Precision Frequency Counter/Tachometer	Optical Pick-Up Tachometer
	Peak-dB Meter


## DUTY CYCLE MONITOR

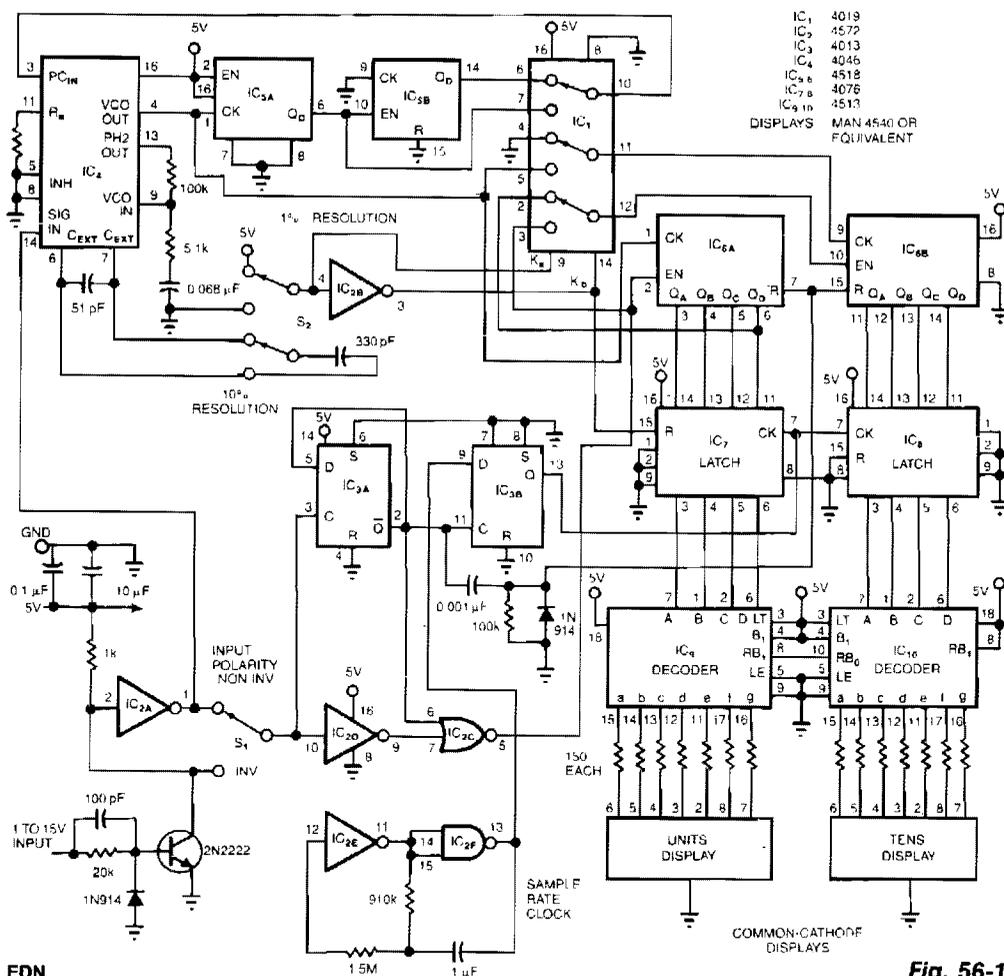

**Fig. 56-1**

The circuit monitors and displays a digital signal's duty cycle and provides accuracy as high as  $\pm 1\%$ . Using switch S2, you can choose a frequency range of either 250 Hz to 2.5 kHz at  $\pm 1\%$  accuracy or 2 kHz to 50 kHz at  $\pm 10\%$  accuracy. The common-cathode display gives the signal's duty-cycle percentage. Phase-locked loop IC4 and counters IC5A and IC5B multiply the input frequency by a factor of either 10 or 100, depending on switch S2's setting. IC6A and IC6B count this multiplied frequency during the incoming signal's mark interval. IC7 and IC8 then latch this count and display it at the clock's sample rate. For example, if you select a 1% resolution, when the signal's mark period is 40% of the total period, the circuit will enable the counter comprising IC6A and IC6B for 40 counts. To obtain space-interval sampling, you can reverse the input polarity using switch S1. IC2A samples the input signal's period and enables gate IC2C and resets the counter. IC2E and IC2F form the sample-rate clock; IC3B synchronizes the clock's output with the input, so that the circuit can update latches IC7 and IC8.

### 3-IN-1 TEST SET

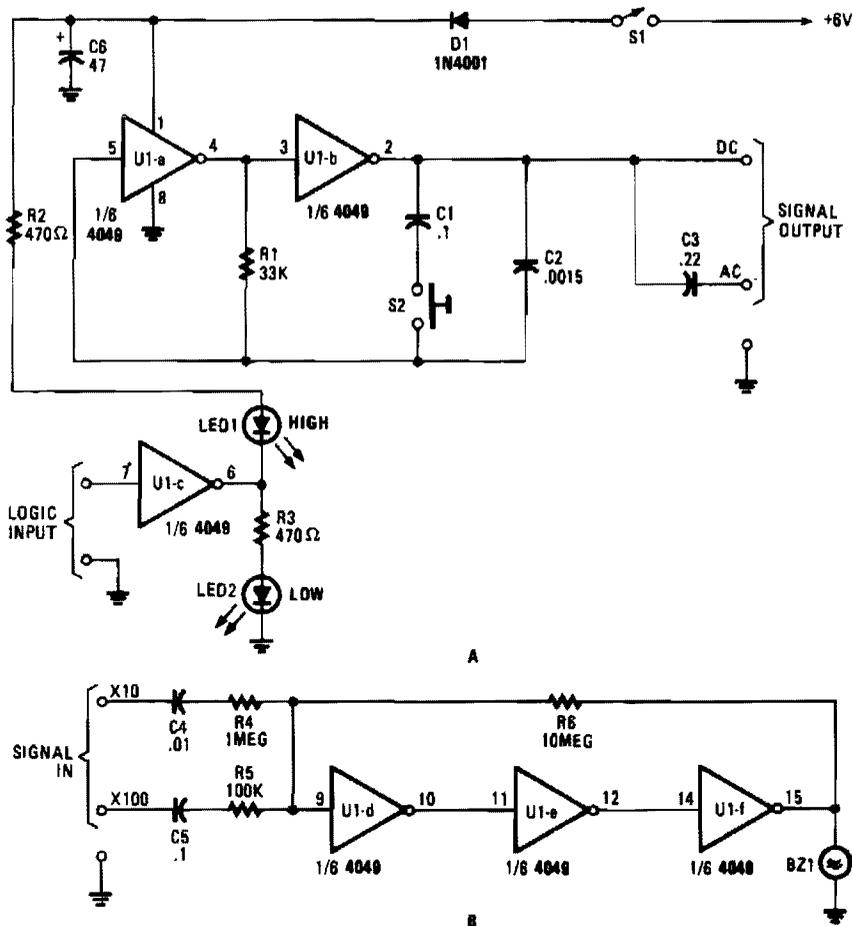

POPULAR ELECTRONICS


Fig. 56-2

This circuit is designed around a 4049 hex inverter/buffer. Two inverters are used in a dual-frequency signal-injector circuit, another inverter is used as a logic probe, and the remaining three inverters are used as a sensitive dual-input, audio-signal tracer.

The signal-injector portion gates are configured as a two-frequency, pulse-generator circuit. Under normal conditions, the generator's output frequency is around 10 kHz, but when S2 is closed, the output frequency drops to about 100 Hz. The logic-probe portion is made up of U1c, the output of the inverter decreases. The low output of U1c reverse biases LED2, so it remains off. That low output also forward biases LED1, causing it to light. But when a logic low presented U1c's input, the situation is reversed, so LED2 lights and LED1 darkens.

The audio-signal tracer portion is made up of the three remaining inverters which are configured as a linear audio amplifier to increase the input signal level by a factor of 10 or 100. The amplified output signal feeds a miniature piezo element of audible detection.

## STEREO POWER METER

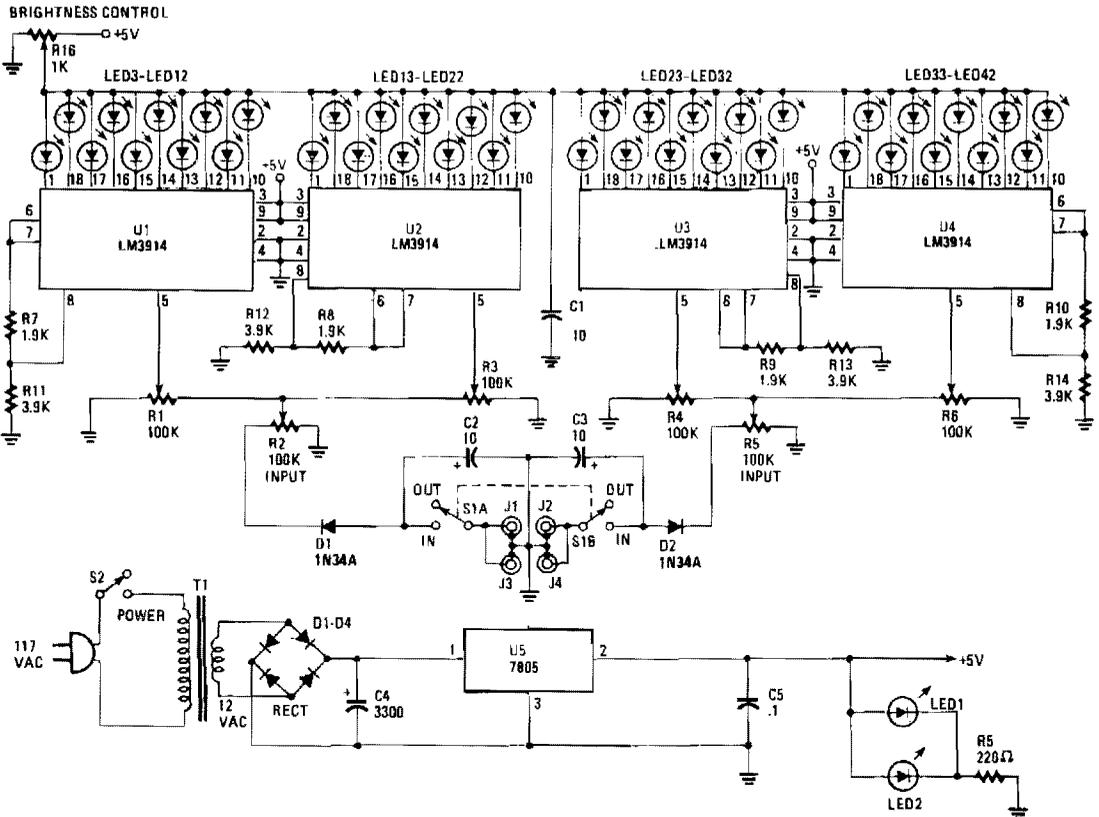


HANDS-ON ELECTRONICS

Fig. 56-3

The Stereo Power Meter is made up of two identical circuits and a power supply. Each circuit contains two LM3914 display chips which contain 10 voltage comparators, a 10-step voltage divider, a reference-voltage source, and a mode-select circuit that selects a bar or dot display via a logic input at pin 9. The brightness of the LEDs is controlled by the 1900- $\Omega$  resistors and the reference voltage is controlled by the 3900- $\Omega$  resistors. The 10-step voltage divider within the chips is connected between the reference voltage and ground. Since each step of the voltage divider is separated by a 1-K $\Omega$  resistor, each comparator senses a voltage 10% greater than the preceding comparator. The signal is applied to pin 5, which is buffered through a resistor-diode network and then amplified as it passes to each of the 10 comparators. Each LED is grounded through the comparators as the input signal voltage matches the reference voltage. That results in one to 10 LEDs illuminating as the signal voltage increases.

## WIDE-RANGE RF POWER METER

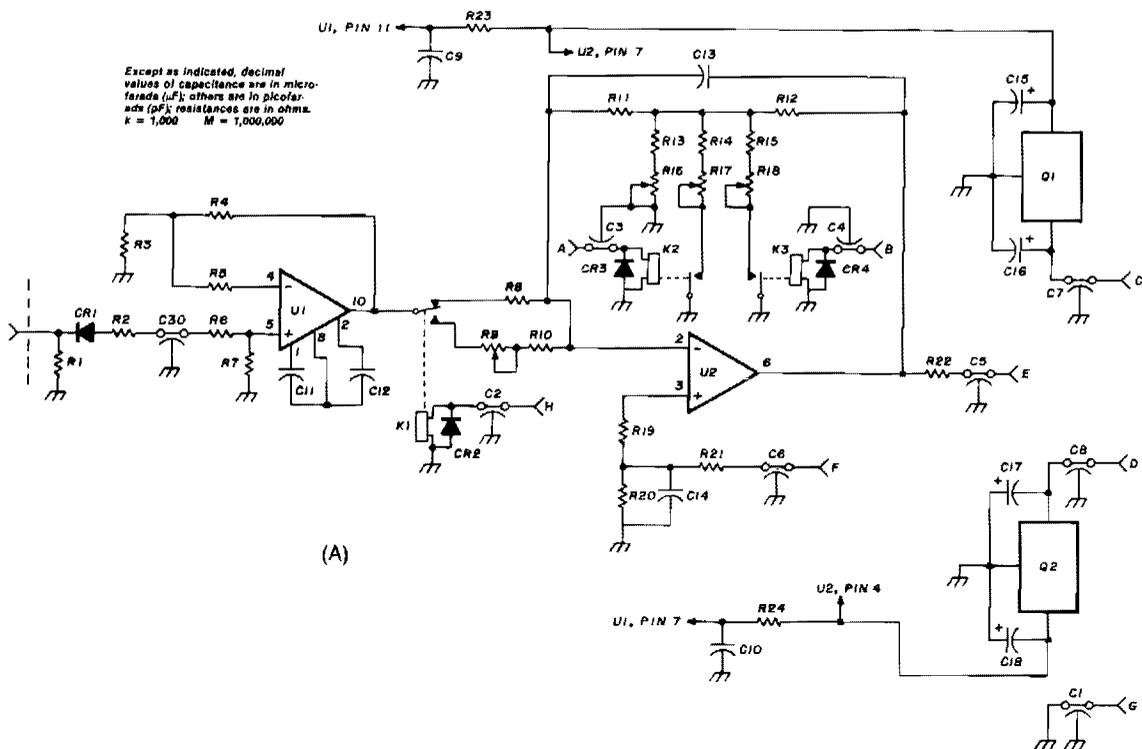

Except as indicated, decimal values of capacitance are in microfarads ( $\mu\text{F}$ ); others are in picofarads (pF); resistances are in ohms.  $k = 1,000$   $M = 1,000,000$

(A)

table 1. RF power meter and power supply parts list

C1 thru C8	1000 pF feedthru (Ehe, Cambion)
C9,10,15,18	1 $\mu\text{F}$ 10wvdc tantalum
C11-12	0.1 $\mu\text{F}$ metalized film
C13	500 pF disc
C14	0.01 $\mu\text{F}$ disc ceramic
C16,17	2.2 $\mu\text{F}$ 25 wvdc tantalum
C19,21	100 $\mu\text{F}$ 15 wvdc electrolytic
C20	500 $\mu\text{F}$ 15 wvdc electrolytic
C22,23	0.01 $\mu\text{F}$ disc
C30	100pF chip capacitor
CR1	HSCH-3486 Hewlett-Packard
CR2,3,4,9,10	1N914 or equivalent
CR5,6,7,8	1N4003 or equivalent
K1	SPDT reed Magnecraft W172-DIP5 (internal diode — CR2 not used)
K2,3,4,5	SPST reed EAC EAC Z610-ND
M1	1 mA DC meter with dB scale
Q1,4	78L05 regulator
Q2	79L05 regulator
Q3	78L12 regulator
R1,2	50 ohm 1/8 watt carbon film

All resistors 1% metal film 1/4 watt


R3,6,14,22	7k
R5,7	100k
R10	120k
R4	150k
R8,19	4.99k
R11,12	20k
R13	2.74k
R15	165 ohm

All resistors 5% carbon film 1/4 watt

R20	100 ohm
R21	1 megohm
R23, 24	10 ohm
R27	1.5k
R9	50k Panasonic CEG54 trimpot
R16	500 ohm Panasonic CEG52 trimpot
R17	200 ohm Panasonic CEG22 trimpot
R18	100 ohm Panasonic CEG12 trimpot
R25,26	10k potentiometer


S1	DP6T rotary switch
T1, T2	6.3 VAC transformers
U1	ICL76508CPD Intersil
U2	LM11CLH National
Box	CU-124 BUD
Chassis	9 1/2 x 5 x 2 chassis BUD Ac-403

## WIDE-RANGE RF POWER METER (Cont.)

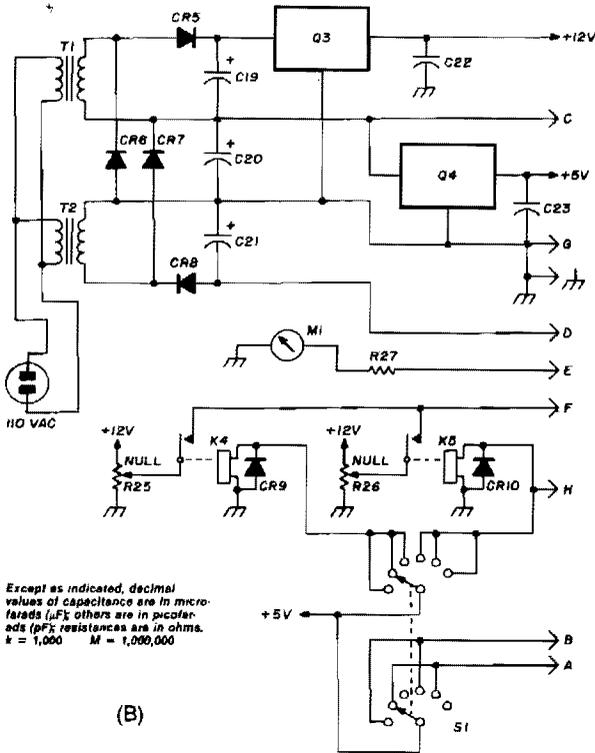

The Hewlett-Packard HSCH-3486 zero-bias Schottky diode is used as the detector. To avoid using a modulation method of detection, a chopper-stabilized op amp is used. The chopper op amp basically converts the input dc voltage to ac, amplifies it, and converts it back to dc. Amplifying the dc output from the detector 150 times with a chopper op amp puts the signal at a level that simpler op amps, such as the LM11, can handle. Offset voltages in the amplifier are nulled with two pots, one for the high range and one for the lower three ranges.

## LED PEAKMETER

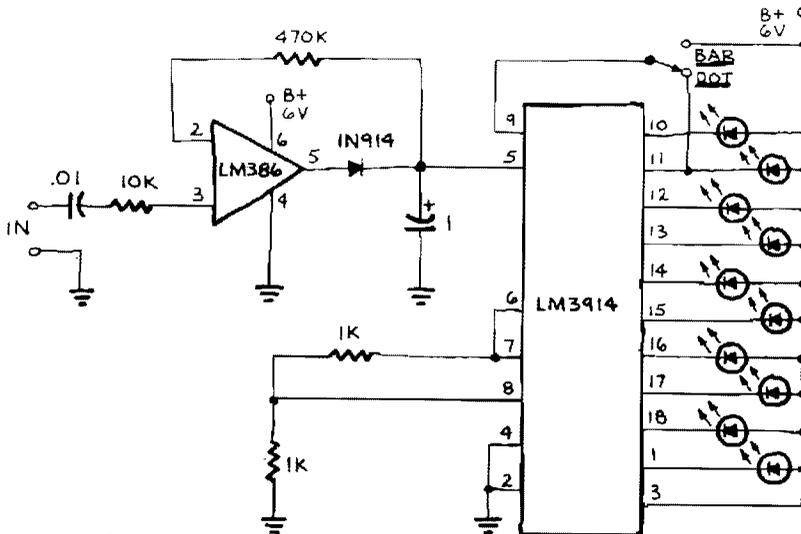

## LED PEAKMETER (Cont.)

The circuit includes a peak detector that immediately drives the readout to any new higher signal level and slowly lowers it after the signal drops to zero. The readout is a moving dot or expanding bar display. The circuit can be expanded for a longer bar readout. Tapping five or more LED peakmeters into a frequency equalizer or series of audio filters should give a unique result. The bottom LED remains on with no signal at the input, thus providing a pilot light for the unit.


## LC CHECKER

The circuit is based on the *grid-dip* or *absorption effect*, which occurs when a parallel resonant circuit is coupled to an oscillator of the same frequency. Q1 operates in a conventional Colpitts oscillator circuit at a fixed frequency of approximately 4 MHz. A meter connected in series with the transistor's base-bias resistor serves as the dip or absorption indicator.

The variable measuring circuit consists of C1, C2, and L2 and is connected to panel terminals as shown. L2 is loosely coupled to L1 in the oscillator circuit. This measuring circuit is tuned to the oscillator frequency with variable capacitor C2 set at full capacitance. When power is applied to the oscillator, the meter shows a dip caused by power absorption from the measuring circuit.

Connecting an unknown capacitor across the test terminals lowers the resonant frequency of the measuring circuit. To restore resonance, tune capacitor C2 lower in capacitance. The meter will dip again when you reach this point. Determine the capacitance across the test terminals by calibrating the dial settings of C2.

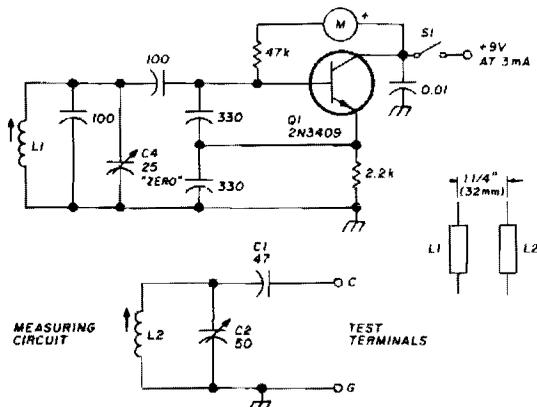Capacitor C4, a small variable trimmer in the oscillator circuit, compensates for drift or other variations and is normally set at half capacitance. The capacitor is a panel control, labeled zero, and it is used to set the oscillator exactly at the dip point when C2 is set at maximum capacitance. This corresponds to zero on the calibration scale.




L1- 30T NO. 28E CLOSE-WOUND ON 3/8" (10mm) SLUG-TUNED FORM. APPROX 7 $\mu$ H.  
L2- 50T. SAME AS L1. APPROX. 30 $\mu$ H  
Q1- 2N3904 OR SIMILAR  
M- 0 TO 100 OR 0 TO 200 $\mu$ A.  
S1- SPST TOGGLE OR SLIDE SWITCH

Fig. 56-6

HAM RADIO
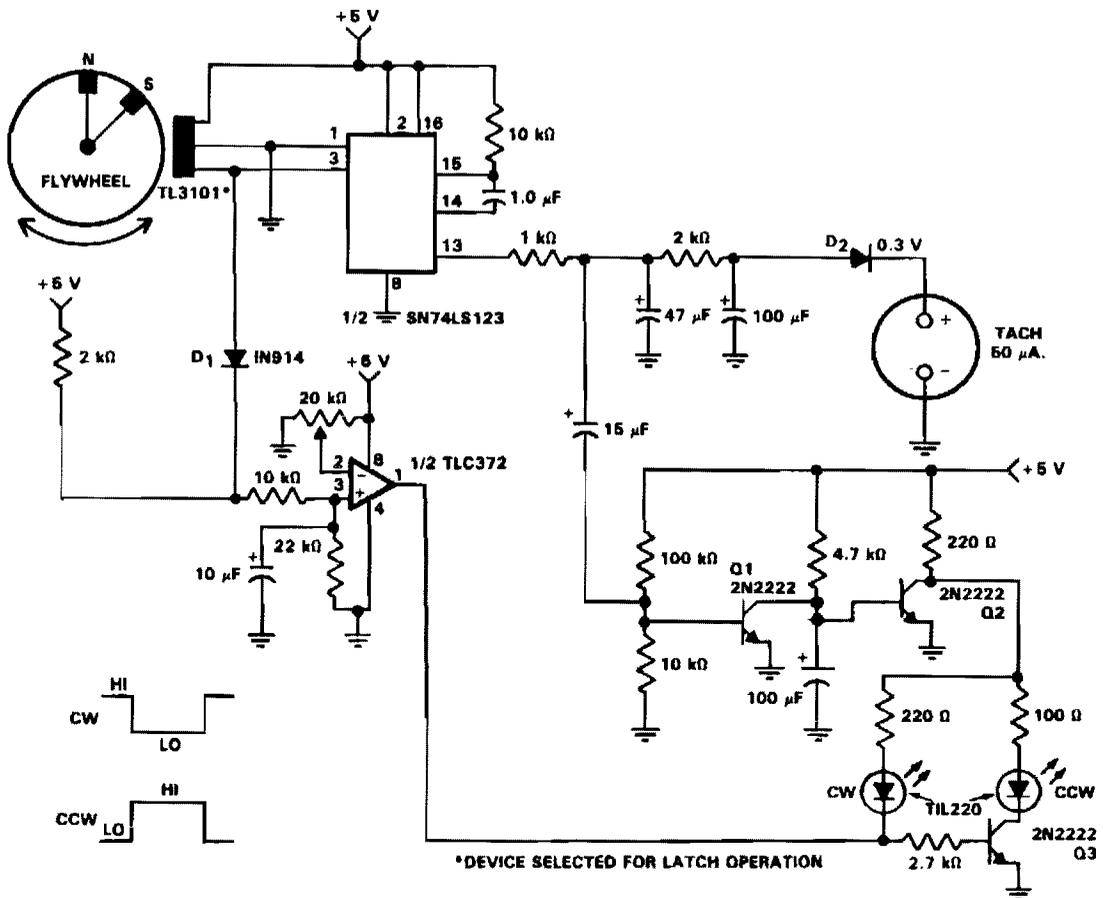
## TACHOMETER AND DIRECTION-OF-ROTATION CIRCUIT




Reprinted by permission of Texas Instruments

Fig. 56-7

In machine and equipment design, some applications require measurement of both the shaft speed and the direction of rotation. Fig. 56-4 shows the circuit of a tachometer, which also indicates the direction of rotation. The flywheel has two magnets embedded in the outer rim about  $45^\circ$  apart. One magnet has the north pole toward the outside and the other magnet has the south pole toward the outside rim of the flywheel. Because of the magnet spacing, a short on pulse is produced by the TL3101 in one direction and a long on pulse in the other direction. A 0–50  $\mu\text{A}$  meter is used to monitor the flywheel speed while the LEDs indicate the direction of rotation. The direction-of-rotation circuit can be divided into three parts:

- TLC372 device for input conditioning and reference adjustment.
- Two 2N2222 transistors which apply the  $V_{CC}$  to the two LEDs when needed.
- The two TIL220 LEDs which indicate clockwise (CW) or counterclockwise (CCW) direction of rotation.


## VERY SHORT PULSE-WIDTH MEASURER

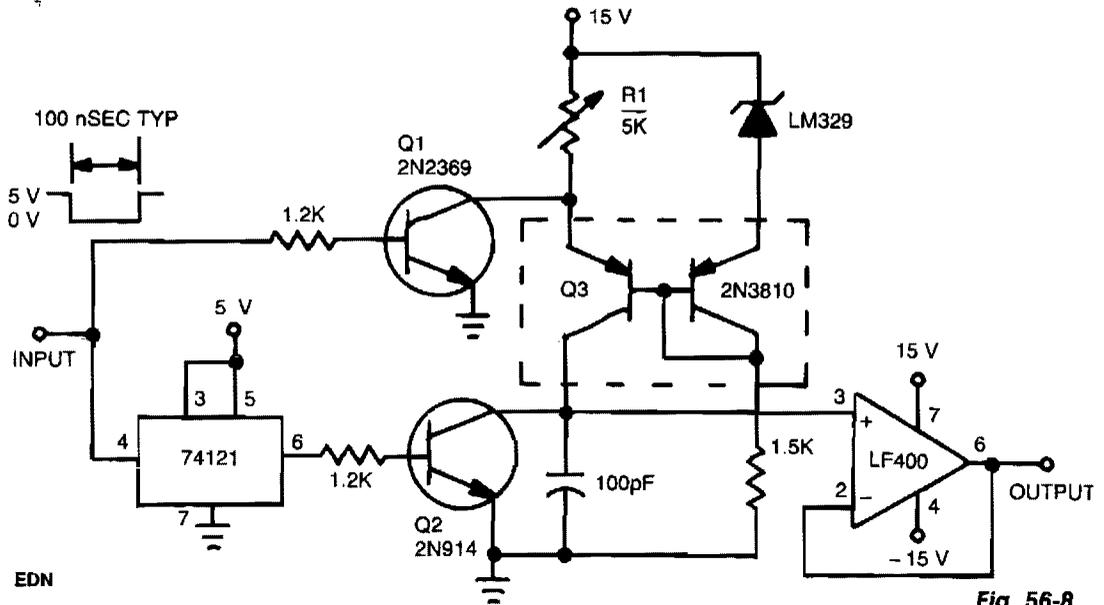

**Fig. 56-8**

This circuit operates by charging a small capacitor from a constant-current source when the pulse to be measured is present. Dual pnp transistor Q3 is the current source; its output current equals the LM329 reference voltage divided by the resistance of potentiometer R1. When the input is high with no pulse present, Q1 keeps the current source turned off. When the pulse begins and the input decreases, Q1 turns off and the monostable multivibrator generates a short pulse. The pulse from the multivibrator turns on Q2, removing any residual charge from the 100-pF capacitor. Q2 then turns off, and the capacitor begins to charge linearly from the current source. When the input pulse ends, the current source turns off, and the voltage on the capacitor is proportional to the pulse width.

## QRP SWR BRIDGE

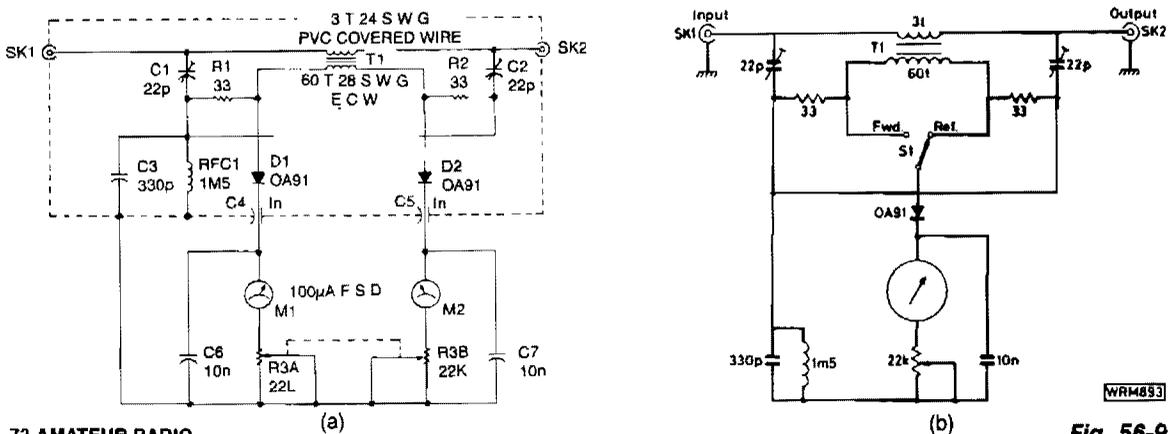


73 AMATEUR RADIO

**Fig. 56-9**

## QRP SWR BRIDGE (Cont.)

The design shown is a simple unit for QRP operation on all authorized frequencies up to 30 MHz, based on a toroidal transformer T1. The secondary winding of T1 samples a small amount of rf power, both forward and reflected, which is divided by the bridge circuit and rectified by diodes D1 and D2. Forward and reflected readings are obtained simultaneously on the two meters M1 and M2, and the bridge is matched and balanced at the required load impedance by C1 and C2. See Fig. 56-9b for an alternative, less expensive, single meter version. The bridge also measure forward power.

## ELECTROSTATIC DETECTOR


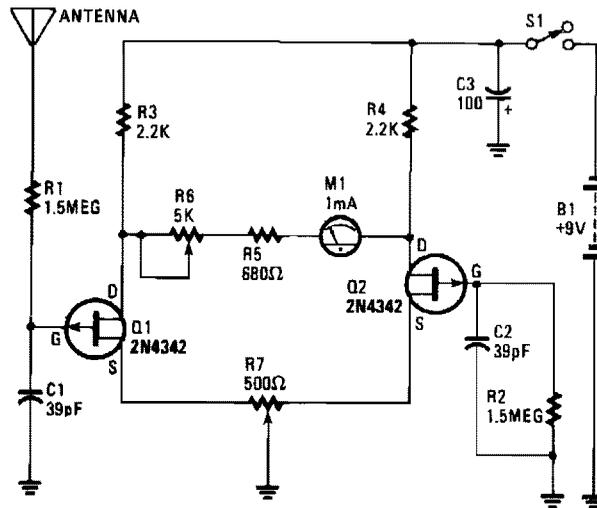


HANDS-ON ELECTRONICS

Fig. 56-10

The heart of the electrostatic detector is the two junction FETs Q1 and Q2 connected in a balanced-bridge circuit. The gate input of Q1 is connected to the wire pick-up antenna, while Q2's gate is tied to the circuit's common ground through R2. That type of bridge circuit offers excellent temperature stability; therefore, Q1 is allowed to operate in an open-gate configuration. Potentiometer R7 is used to balance the bridge circuit, and R6 sets the maximum meter swing. Capacitors C1 and C2 help to reduce the 60-Hz pickup and add to the short-term stability of the circuit.


## CURRENT MONITOR AND ALARM

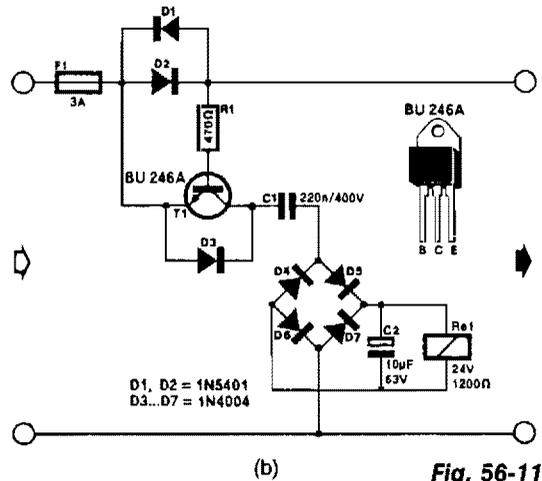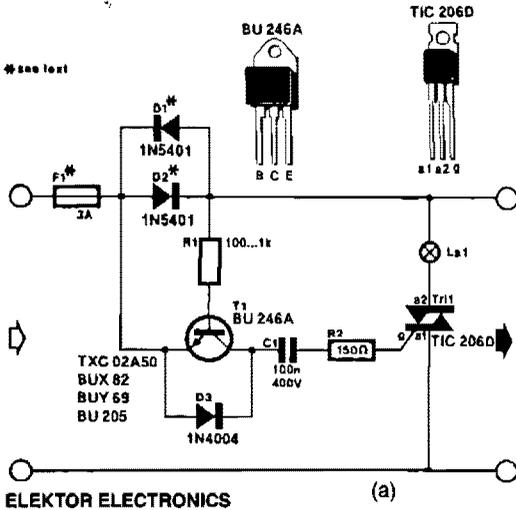

The circuit in Fig. 56-11a lights the signal lamp upon detecting a line current consumption of more than 5 mA, and handles currents of several amperes with appropriate diodes fitted in the D1 and D2 positions. Transistor T1 is switched on when the drop across D1/D2 exceeds a certain level. Diodes from the well-known 1N400x series can be used for currents of up to 1 A, while 1N540x types are rated for up to 3 A. Fuse F1 should suit the particular application.

The circuit in Fig. 56-11b is a current-triggered alarm. Rectifier bridge D4 through D7 can only provide the coil voltage for Rel when the current through D1/D2 exceeds a certain level, because then series capacitor C1 passes the alternating main current. Capacitor C1 needs to suit the sensitivity of the relay coil. This is readily effected by connecting capacitors in parallel until the coil voltage is high enough for the relay to operate reliably.

## PICOAMMETER CIRCUIT

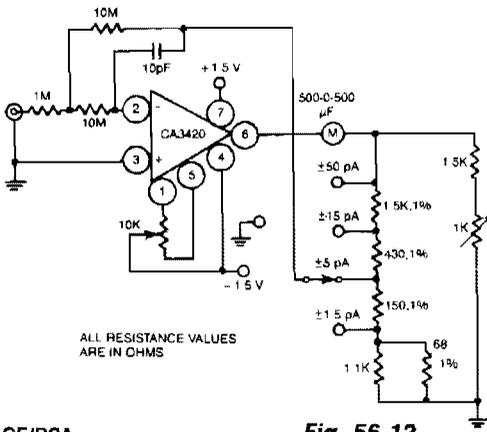

This circuit uses the exceptionally low input current 0.1 pA of the CA3420 BiMOS op amp. With only a single 10-MΩ resistor, the circuit covers the range from  $\pm 50$  pA to a maximum full-scale sensitivity of  $\pm 1.5$  pA.

## PAPER SHEET DISCRIMINATOR FOR PRINTING AND COPYING MACHINES


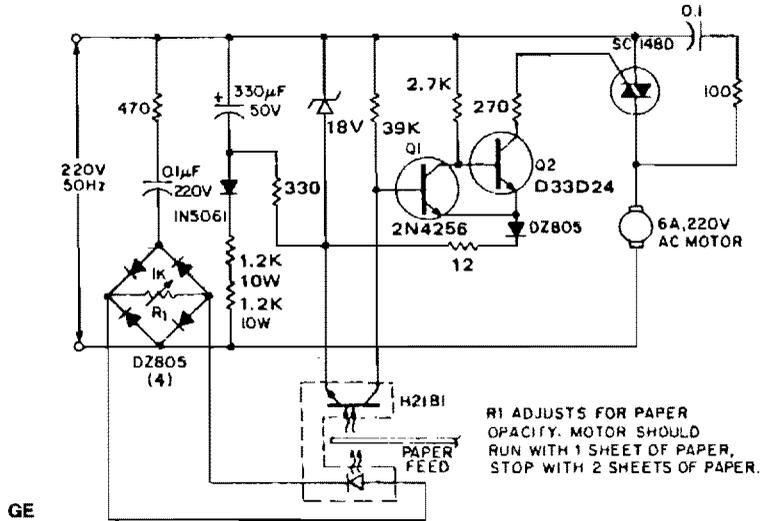


Fig. 56-13


The circuit outputs power to the drive motor when one or no sheets are being fed, but interrupts motor power when two or more superimposed sheets pass through the optodetector slot. The optodetector can be either an H2aB darlington interruptor module or an H23B matched emitter-detector pair. The output from the optodarlington is coupled to a Schmitt trigger, comprising transistors Q1 and Q2 for noise immunity and minor paper opacity variation immunity. When the Schmitt is on, gate current is applied to the SC148D output device. The dc power supply for the detector and Schmitt is a simple rc diode half-wave configuration chosen for its low cost (fewer diodes and no transformers) and minimum bulk. While such a supply is directly coupled to the power triac, this is precluded by current drain considerations (50 mA dc for the gate drive alone). Note that direct coupling of the Schmitt to the output triacs is preferred, since RFI is virtually eliminated with the quasi-dc gate drive.

## STUD FINDER

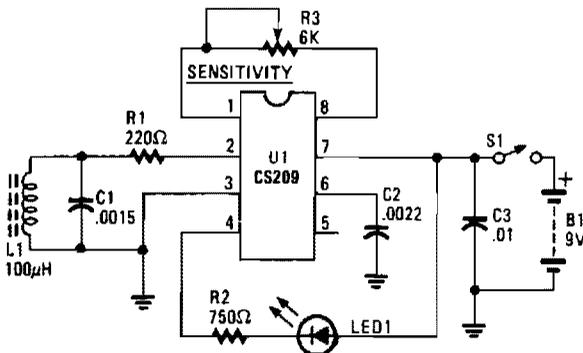

The CS209 is designed to detect the presence or proximity of magnetic metals. It has an internal oscillator that, along with its external lc resonant circuit, provides oscillations whose amplitude is dependent upon the  $Q$  of the lc network. Close proximity to magnetic material reduces the  $Q$  of the tuned circuit, thus the oscillations tend to decrease in amplitude. The decrease in amplitude is detected and used in turn on LED1, indicating the presence of a magnetic material (i.e., nail or screw).


## PRECISION FREQUENCY COUNTER/TACHOMETER

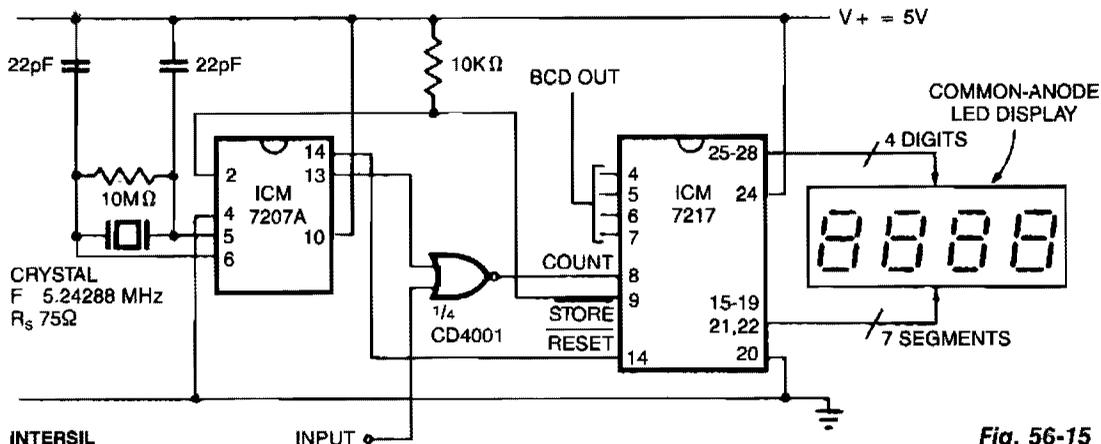

**Fig. 56-15**

In this configuration, the display reads hertz directly. With pin 11 of the ICM7207A connected to  $V_{DD}$ , the gating time will be 0.1 second; this will display tens of hertz as the least significant digit. For shorter gating times, an ICM7207 can be used with a 6.5536-MHz crystal, giving a 0.01 second gating with pin 11 connected to  $V_{DD}$ , and a 0.1 second gating with pin 11 open.


## MOTOR HOUR METER

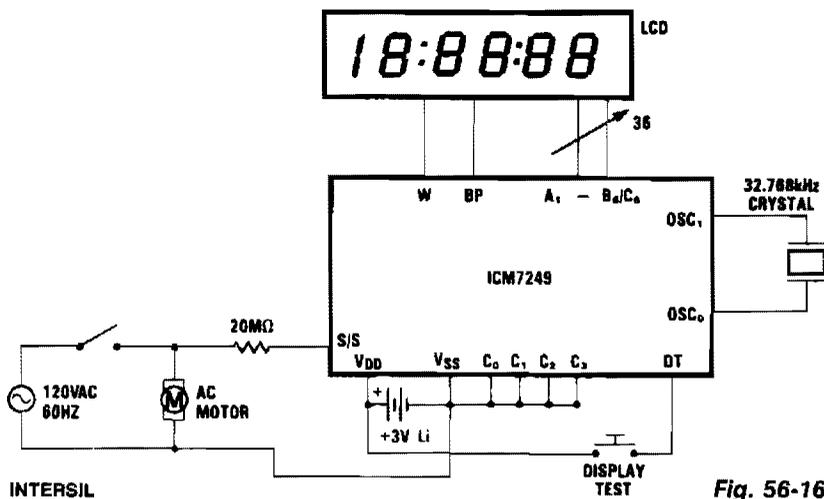

**Fig. 56-16**

In this application, the ICM7249 is configured as an hours-in-use meter and shows how many whole hours of line voltage have been applied. The 20-M $\Omega$  resistor and high-pass filtering allow ac line activation of the S/S input. This configuration, which is powered by a 3-V lithium cell, will operate continuously for 2½ years. Without the display, which only needs to be connected when a reading is required, the span of operation is extended to 10 years.

## LOW-POWER MAGNETIC CURRENT SENSOR

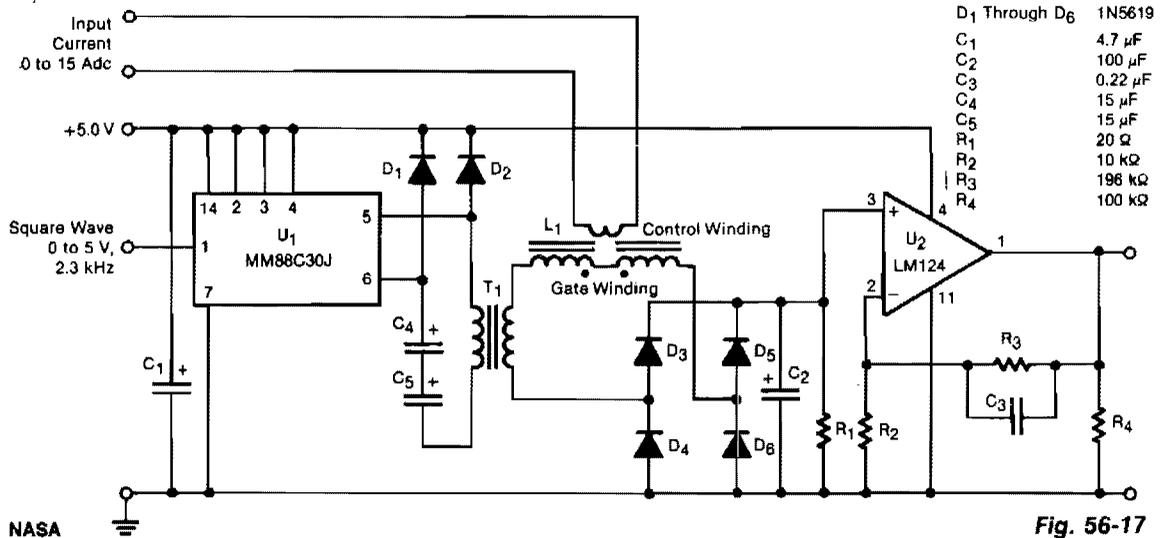

**Fig. 56-17**


A transducer senses a direct current magnetically, providing isolation between the input and the output. The detecting-and-isolating element is a saturable reactor, in which the input current, to be measured, passes through a one-turn control coil. The transducer provides an output of 0 to 3 Vdc, an input current of 0 to 15 Adc, and consumes 22 mW at 10 Adc input.

Line driver U1 excites the saturable reactor L1 by feeding a 2.3-kHz square wave through transformer T1. The output of L1 is rectified by the bridge rectifier composed of diodes D3 through D6, then amplified by op amp U2, which has a gain of 20.

Diodes D1 and D2 commutate the reactive current fed back to the primary of T1 from L1. Without these diodes, large reactive voltage spikes on the primary would waste power and could destroy U1. Filter capacitor C1 stores the energy fed back through D1 and D2.

To minimize core losses, the core of T1 is made of an alloy of 80% nickel and 20% iron. To minimize capacitance, the primary and secondary windings are interleaved and progressively wound 350°. The primary and secondary windings consist of 408 and 660 turns, respectively, of #34 wire.

## LINE-CURRENT MONITOR

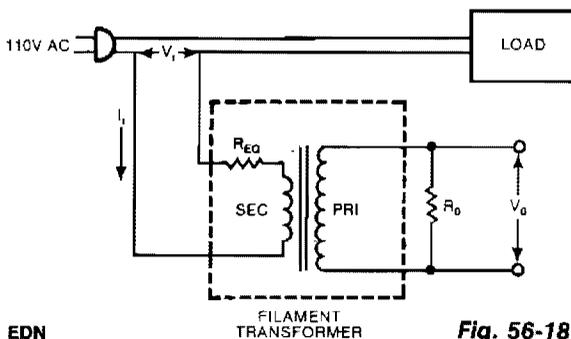

**Fig. 56-18**

A low-cost filament transformer provides a linear indication of the load current in an ac line. This method causes a slight series voltage drop over a wide range of load currents.

EDN

## S METER

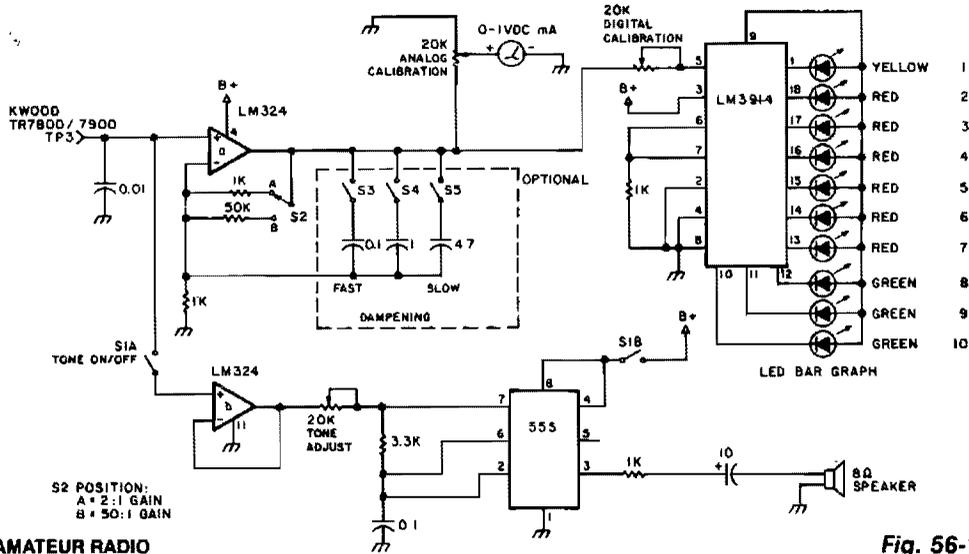


Fig. 56-19

This design is for an external signal strength meter that is analog, digital, and audible for mobile transmitter hunters. The S meter also incorporates a gain circuit. The digital LED bar graph display has a very fast response time. The 3.3-K $\Omega$  resistor near LM3914 can be replaced with a 5-K pot to control LED brightness. The S2A position gives a 2:1 gain and the S2B position gives about a 50:1 gain. The calibration pots control the amount of meter action relative to the gain. The optional dampening circuit is used for the averaging of a transmitted signal that has modulated power or when a dip on the voice peaks occur. The capacitors can be switched one by one or switched into a very slow response using 5.8  $\mu$ F total capacitance.

## HOT-WIRE ANEMOMETER


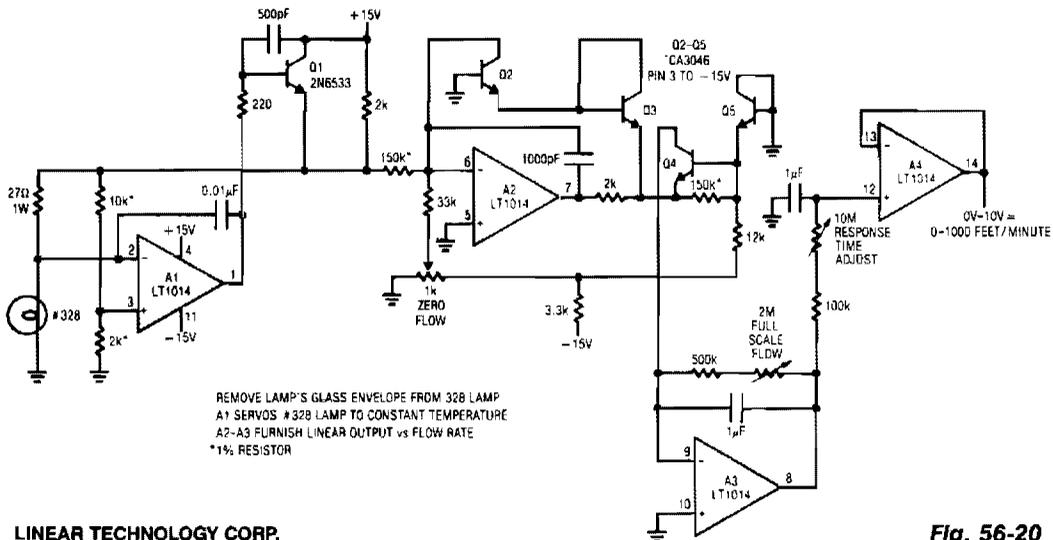


Fig. 56-20

## AUDIBLE LOGIC TESTER

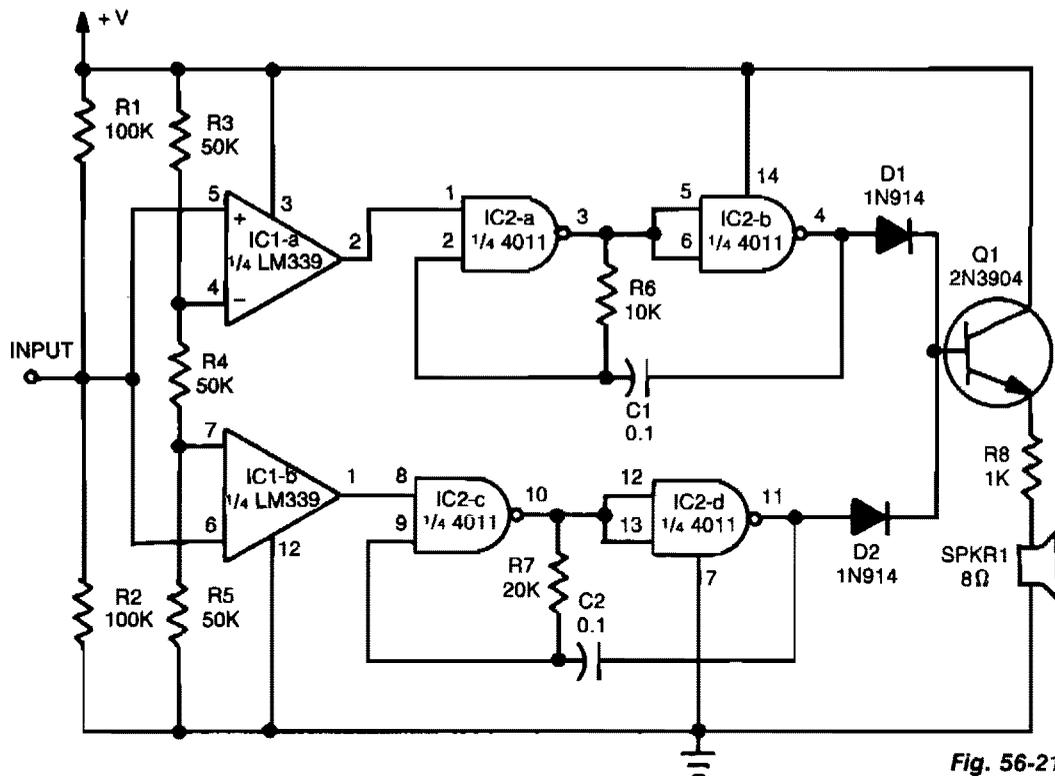


**Fig. 56-21**

Reprinted with permission from Radio-Electronics Magazine, September 1987. Copyright Gernsback Publications, Inc., 1987.

This tester provides an audible indication of the logic level of the signal presented to its input. A logic high is indicated by a high tone, a logic low is indicated by a low tone, and oscillation is indicated by an alternating tone. The input is high impedance, so it will not load down the circuit under test. The tester can be used to troubleshoot TTL or CMOS logic. The input consists of two sections of an LM339 quad comparator. IC1a increases when the input voltage exceeds 67% of the supply voltage. The other comparator increases when the input drops below 33% of the supply.

The tone generators consist of two gated astable multivibrators. The generator built around IC2a and IC2b produces the high tone. The one built around IC2c and IC2d produces the low tone. Two diodes, D1 and D2, isolate the tone-generator outputs. Transistor Q1 is used to drive a low-impedance speaker.

## SCR TESTER

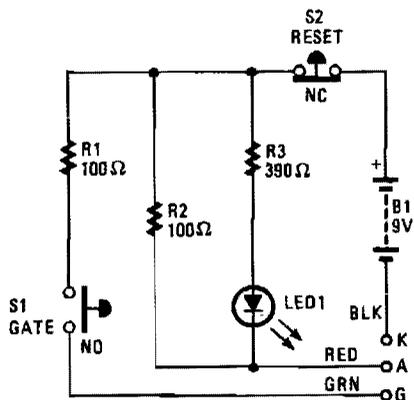

HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

Fig. 56-22

The DUT's (Device Under Test) cathode, anode, and gate are connected to the unit's K, A, and G terminals, respectively. Pressing switch S1 feeds a gate current to the DUT, which triggers it on. Resistor R1 limits the gate current to the appropriate level. Resistor R3 limits the current through the LED to about 20 mA, which, with the current through R2, results in a latching current of about 110 mA. The LED is used to monitor the latching current. If the DUT is good, once the gate is triggered with S1, the LED will remain lit, indicating that the device is conducting. To end the test, turn off the device by interrupting the latching current flow using switch S2. The LED should turn off and remain off. The preceding procedure will work with SCRs and triacs. To check LEDs and other diodes, connect the anode and cathode leads to the anode and cathode of the diode; LED1 should light. When the leads are reversed, the LED should remain off.

## DIGITAL FREQUENCY METER


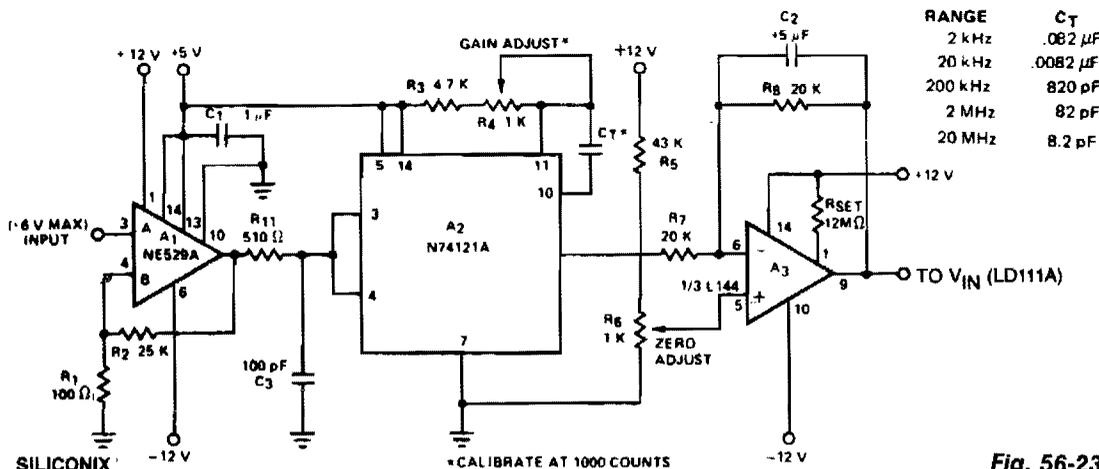


Fig. 56-23

The circuit converts frequency to voltage by taking the average dc value of the pulses from the 74121 monostable multivibrator. The one shot is triggered by the positive-going ac signal at the input of the 529 comparator. The amplifier acts as a dc filter, and also provides zeroing. This circuit will maintain an accuracy of 2% over 5 decades of range. The input signal to the comparator should be greater than 0.1 V pk-pk, and less than 12 V pk-pk for proper operation.

## LOW-CURRENT MEASUREMENT SYSTEM

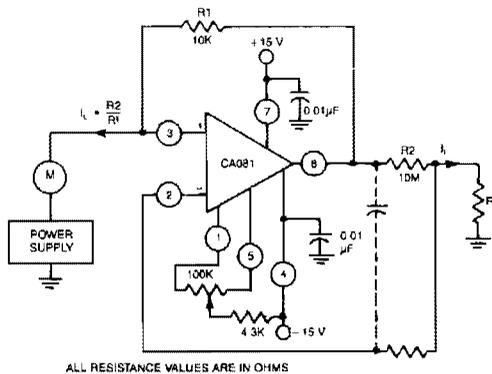


GE/RCA

Fig. 56-24

This circuit uses a CA018 BiMOS op amp. Low current, supplied at input potential as power supply to load resistor  $R_L$ , is increased by  $R_2/R_1$ , when load current  $I_L$  is monitored by power supply meter M. Thus, if  $I_L$  is 100 nA, with values shown,  $I_L$  presented to supply will be 100  $\mu$ A.

## SIMPLE CONTINUITY TESTER

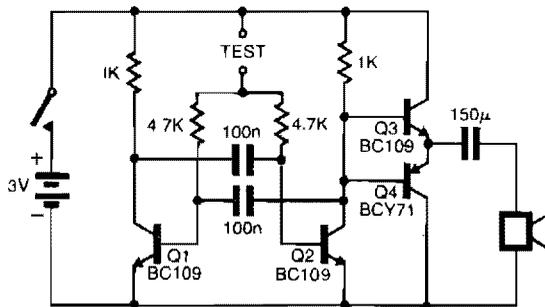


ELECTRONIC ENGINEERING

Fig. 56-25

The pitch of the tone is dependent upon the resistance under test. The tester will respond to resistances of hundreds of kilohms, yet it is possible to distinguish differences of just tens of ohms in low-resistance circuits. Q1 and Q2 form a multivibrator, the frequency of which is influenced by the resistance between the test points. The output stage, Q3 and Q4, will drive a small loudspeaker or a telephone earpiece. The unit is powered by a 3-V battery, and draws very little current when not in use.

## SOUND-LEVEL METER

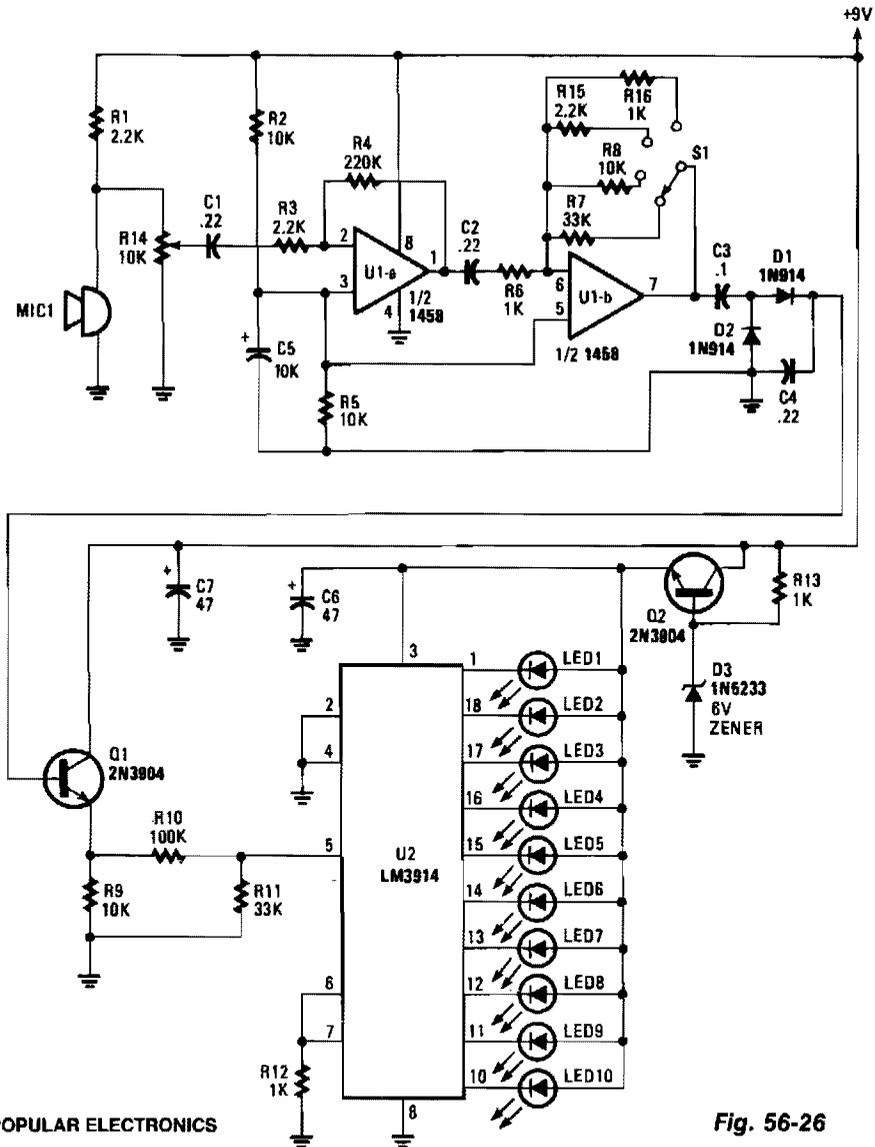

POPULAR ELECTRONICS


Fig. 56-26

Sounds are picked up by MIC1 and fed to the input of the first op amp. The signal is then fed to the input of second op amp U1b, where it is boosted again by a factor of between 1 and 33, depending upon the setting of range switch S1.

With the range switch set in the A position, R6 is 1 K $\Omega$  and R7 is 33 K $\Omega$ , so that stage has a gain of 33. In the B position, the gain is 10  $\Omega$ ; in the C position, the gain is 22  $\Omega$ ; and in the D position the gain is 1  $\Omega$ .


As the signal voltage fed to the input of U2 at pin 5 varies, one of ten LEDs will light to correspond with the input-voltage level. At the input's lowest operating level, U2 produces an output at pin 1, causing LED1 to light. The highest input level presented to the input of U2, about 1.2 V, causes LED10 to turn on.

## LED PANEL METER

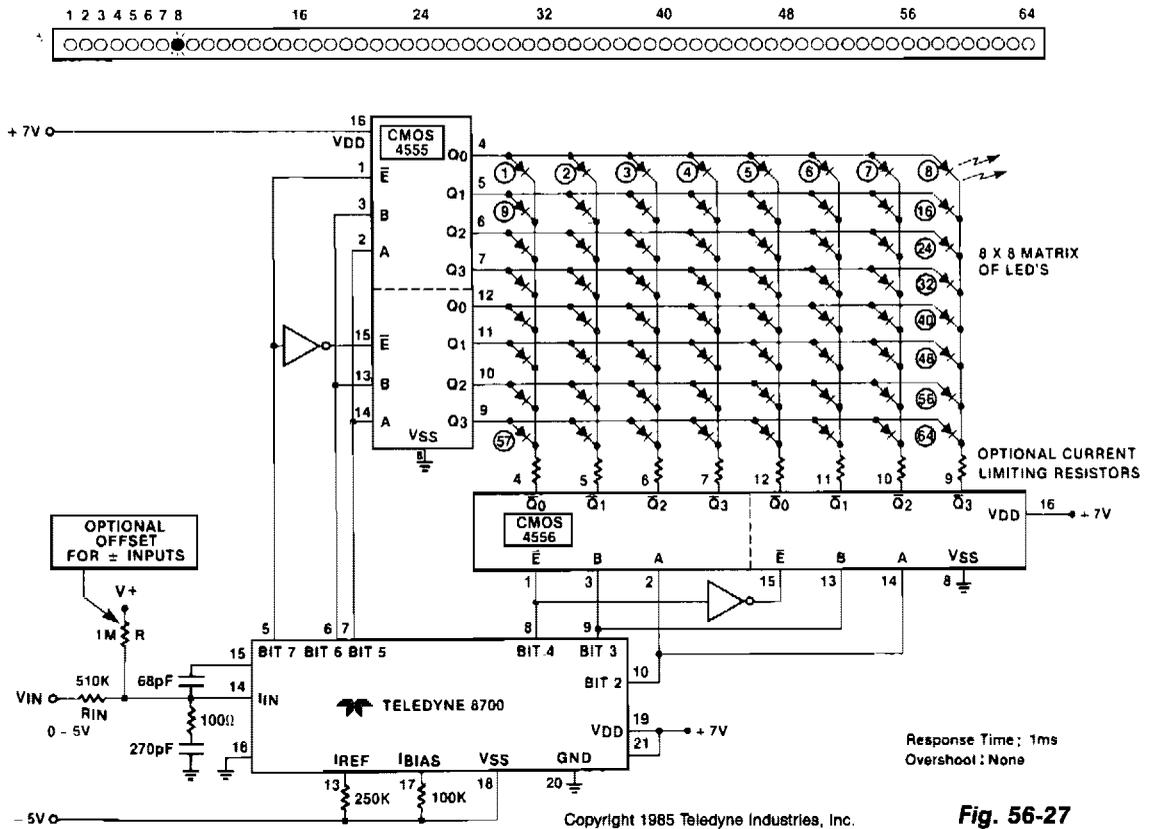


**Fig. 56-27**

## OPTICAL PICK-UP TACHOMETER

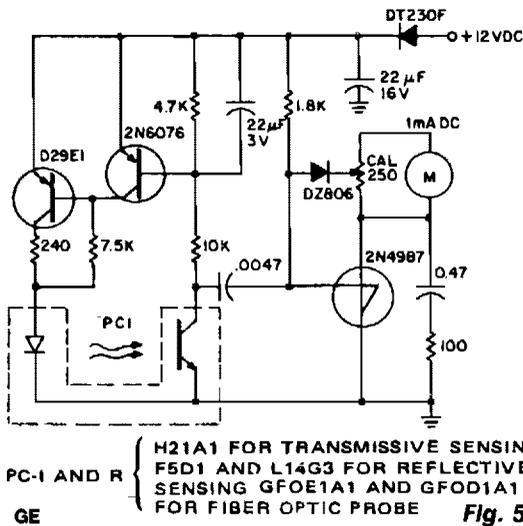

Remote, noncontact, measurement of the speed of rotating objects is the purpose of this simple circuit. Linearity and accuracy are extremely high and normally limited by the milliammeter used and the initial calibration. This circuit is configured to count the leading edge of light pulses and to ignore normal ambient light levels. It is designed for portable operation since the tachometer is not sensitive to supply voltage within the supply voltage tolerance. Full scale at the maximum sensitivity of the calibration resistance is read at about 300 light pulses per second. A digital voltmeter can be used, on the 100-mV full-scale range, in place of the milliammeter. Shunt its input with a 100- $\Omega$  resistor in parallel with a 100- $\mu$ F capacitor. This rc network replaces the filtering supplied by the analog meter.

## PEAK-dB METER

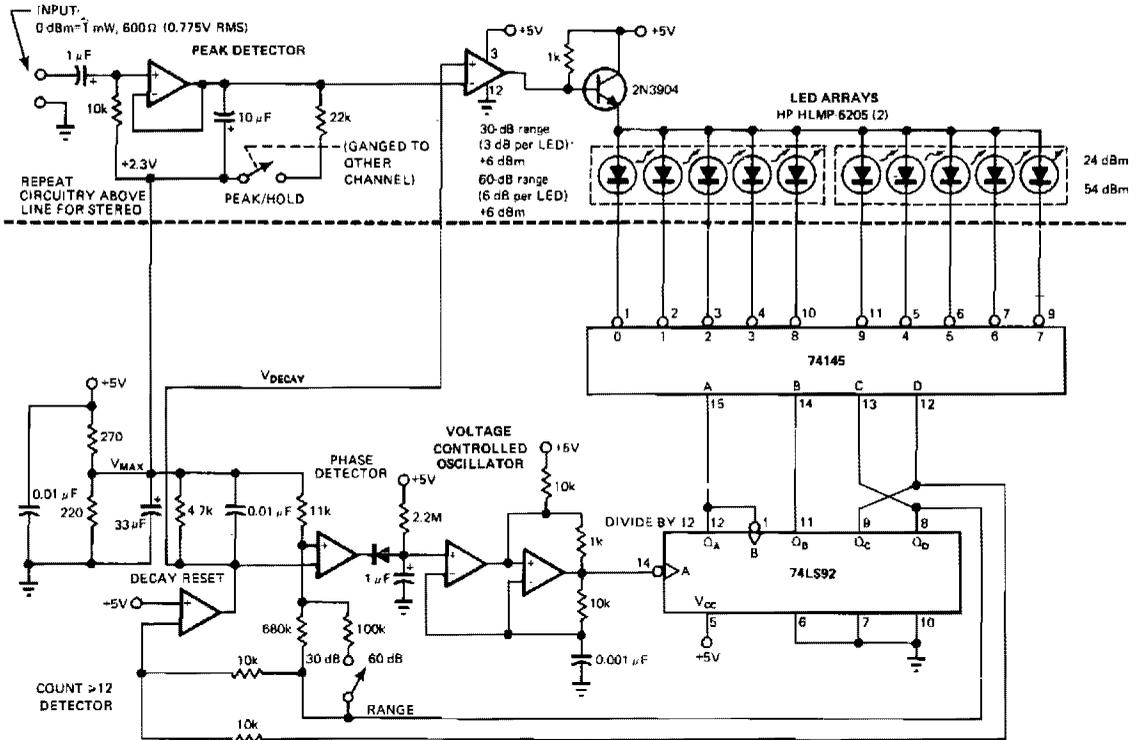

EDN

Fig. 56-29

This circuit compares a rectified input,  $V_{IN}$ , with a voltage that decays exponentially across a 4.7-KΩ resistor and a 0.01-μF capacitor. Comparing the exponentially decaying voltage with the rectified input provides a peak-level indication that requires no adjustment. A phase-locked loop controls the scan rate so that each LED represents 6 dB in the 30 dB range.

# 57


## Medical Electronics Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Three-Chip EKG Simulator  
Breath Monitor  
Stimulus Isolator  
Constant-Current Stimulator

## THREE-CHIP EKG SIMULATOR

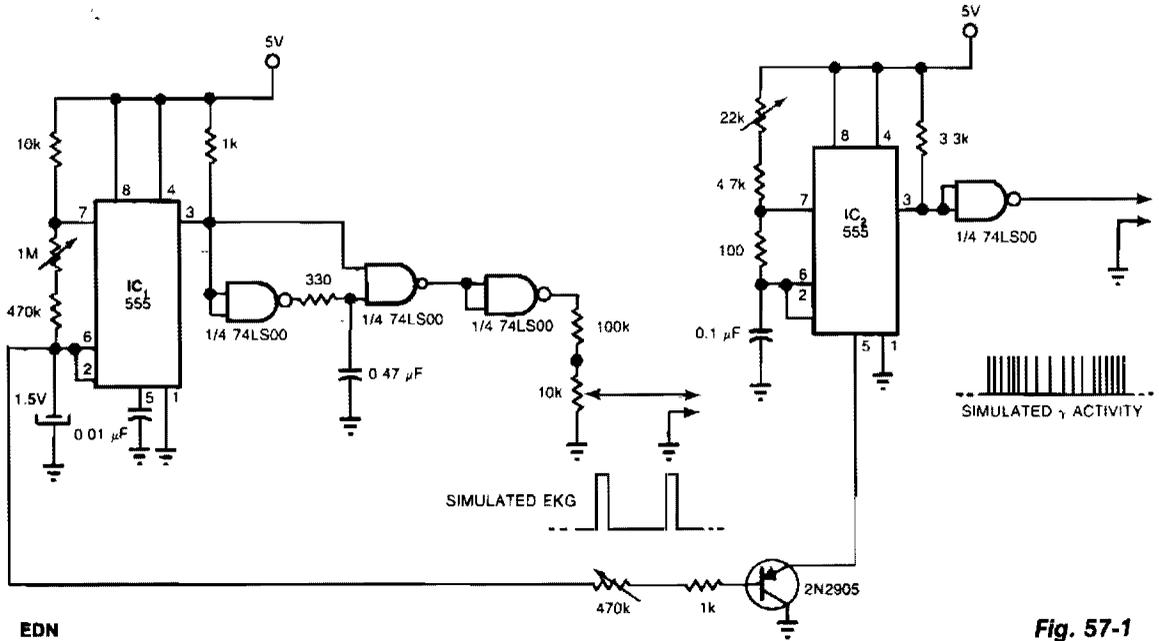

Two 555s and a quad NAND-gate IC can simulate an electrocardiograph signal and a  $\gamma$ -wave radioisotope signal for applications in nuclear medicine. This circuit synchronizes the radioisotope signal to the EKG signal. You can use the circuit's outputs to test, for example, microprocessor-based software that calculates the left ventricular ejection fraction before you use the software in clinical applications. IC1, a 555 timer, provides a positive-going pulse train that simulates an EKG signal. A 10-K $\Omega$  potentiometer provides frequency adjustment. The other 555 timer, configured as a pulse-position modulator, provides the simulated  $\gamma$ -wave activity.

## BREATH MONITOR

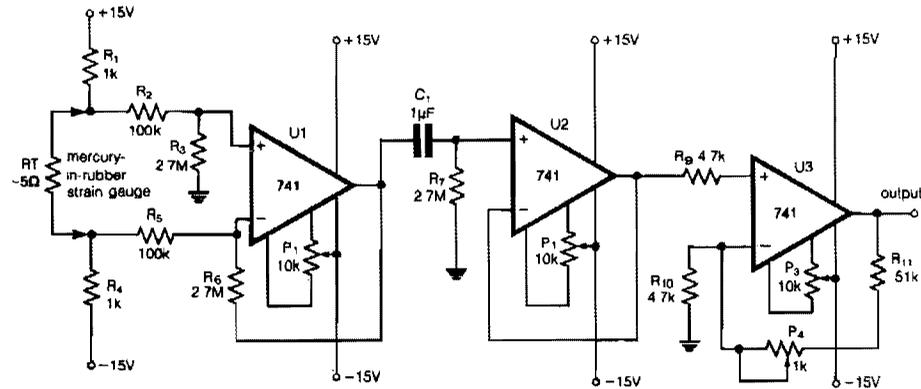

**ELECTRONIC ENGINEERING**

**Fig. 57-2**





**58**


# **Metronome**

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Downbeat-Emphasized Electronic Metronome
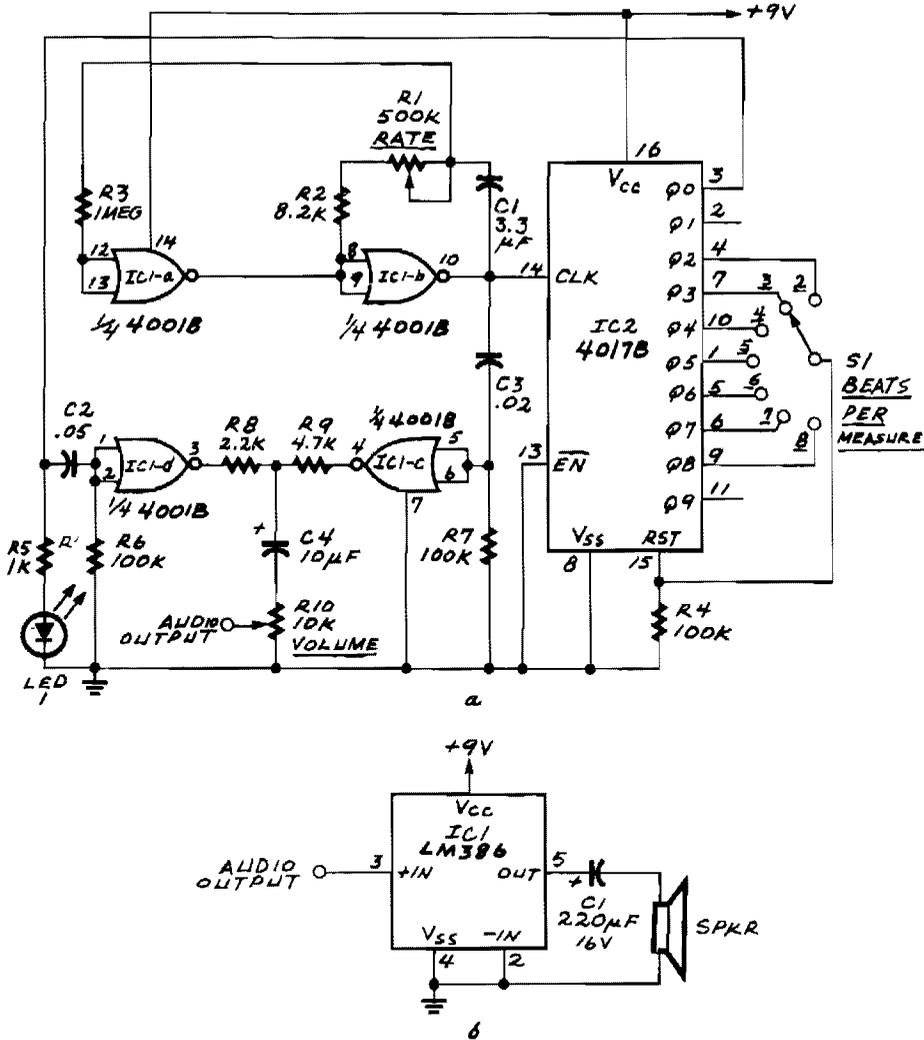
## DOWNBEAT-EMPHASIZED ELECTRONIC METRONOME



Reprinted with permission from Radio-Electronics magazine, December 1985. Copyright Gernsback Publications, Inc., 1985.

**Fig. 58-1**

IC1a and IC1b form an astable multivibrator. The astable's signal is fed to IC1c, also to the clock input of IC2, a 4017B decade counter. That IC's Q0 through Q9 outputs become high one at a time for each successive clock pulse received at pin 14. Switch S1 feeds one of those outputs to the 4017B's reset input. Whenever the selected output becomes high, the 4017B restarts its counting cycle; that determines the number of beats per measure. The network composed of C2 and R6 sharpens the downbeat pulse, and the network composed of C3 and R7 sharpens the free-running pulses. By making C2 larger than C3, the downbeat receives greater emphasis.

# 59


## Miscellaneous Treasures

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Closed-Loop Tracer	Simple Low-Cost Rf Switch
Pulse Amplitude Discriminator	Burst Power Control
Tracer Receiver	Flame Ignitor
Central Image Cancellor	Bar Code Scanner
Bug Tracer	50-MHz Trigger
Breath Alert Alcohol Tester	Air-Motion Detector
Automatic Electronic Music	Bug Detector
Positive Input/Negative Output Charge Pump	Door Opener
Acid Rain Monitor	

## CLOSED-LOOP TRACER

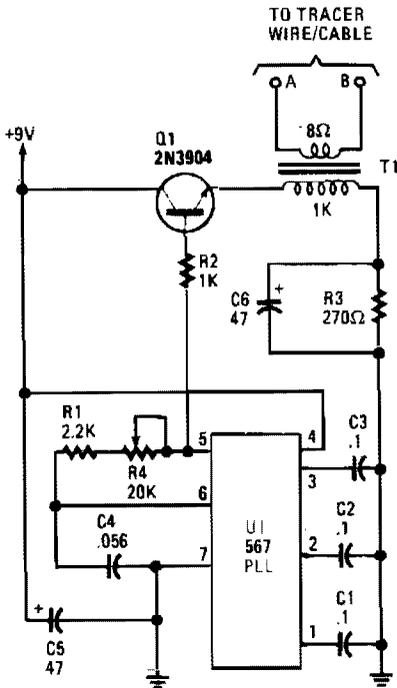

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 59-1

The tracer, consisting of both a transmitter and receiver, is designed to follow a closed-loop wire or cable system. It follows an induced voltage path created by feeding a low-current, audio-frequency signal through the cable. When the pick-up coils come within close proximity of the current-carrying cable, a small voltage is generated in each coil, and that induced voltage is then processed by the receiver's circuitry.

The circuit is built around a 567 phase-locked loop (PLL) configured as a variable-frequency, audio-generator circuit, which is designed to produce a square-wave output at pin 5. Potentiometer R4 allows the oscillator to be easily tuned to the receiver's frequency. Transistor Q1 isolates the oscillator from the load and matches the impedance of the primary of T1. Resistor R3 limits current flow through Q1. The low-impedance secondary of T1 supplies the cable drive signal.

## PULSE AMPLITUDE DISCRIMINATOR


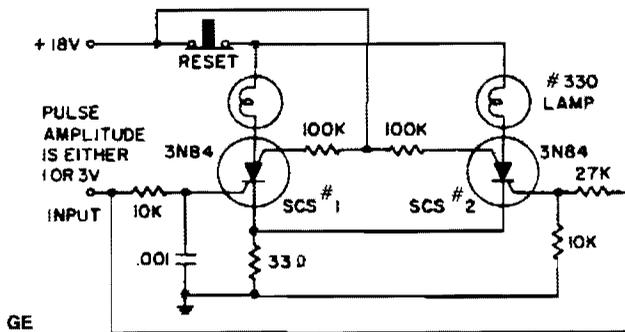


Fig. 59-2

A 1-V amplitude pulse triggers SCS1, but has insufficient amplitude to trigger SCS2. A 3-V input pulse is delayed in reaching SCS1 by the 10-KΩ and .001-μF integrating network. Instead, it triggers SCS2, then raises the common emitter voltage to prevent SCS1 from triggering. The 100-KΩ resistors suppress the rate effect.

## TRACER RECEIVER

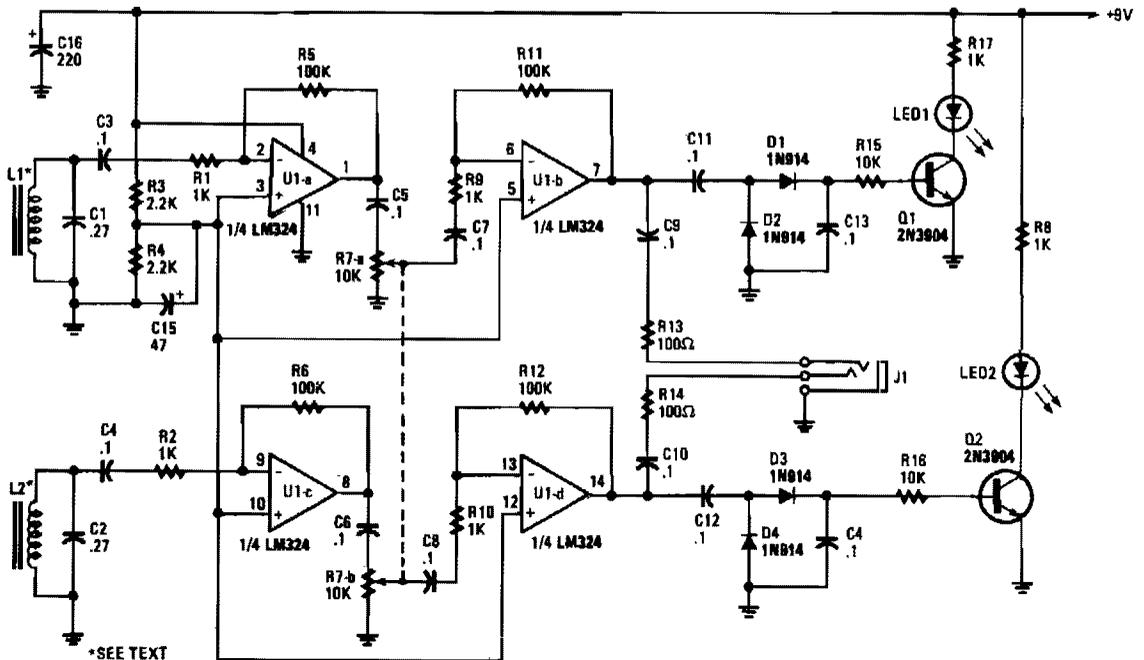

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 59-3

The tracer receiver is a stereo audio amplifier/detector circuit operating near 1 kHz. Inductors L1 and L2—hand-wound coils, consisting of 200 turns of #26 wire on 2-inch ferrite cores—are tuned to the operating frequency of the amplifier/detector. The received signal strength of each individual receiver is indicated by an LED. The audio output of the receiver is fed to a stereo headphone. That dual-receiver scheme helps in locating and tracking the hidden wire or cable by giving a directional output that indicates the cable's path.

The 1-kHz signal is picked up by L1 and coupled to the input of op amp U1a, which provides a gain of about 100 dB. The output of op amp U1a is fed through volume-control potentiometer R7 to the input of U1b, which magnifies the already amplified signal 100 times more. That puts the maximum gain of the receiver at about 10,000 dB. The output of U1b follows two paths: in the first path, the signal is coupled through C9 and R13 to J1, and is used to drive one half of a stereo headphone.


In the other path, the signal is fed through a voltage doubling/detector circuit—consisting of D1, D2, C11, and C13—that converts the amplified 1-kHz signal to the dc voltage that's used to drive Q1. When Q1 is turned on, LED1 lights, indicating a received signal.

## CENTRAL IMAGE CANCELLER

The circuit allows you to eliminate the vocal portion of an audio signal, while leaving the instrumental portion. The circuit mixes two channels that must be  $180^\circ$  out of phase, so the signals that form the center-stereo image is canceled out. Those signals usually appear in phase. Resistor R3 biases the noninverting input of U1 from a center tap formed by resistors R1 and R4, and capacitor C3. Resistor R4, capacitor C3, and potentiometer R6 form a negative-feedback circuit that establishes the closed-loop voltage gain of U1 at unity. The signal is inverted between the input and output.

Signals applied to the right input are coupled to the noninverting input of U1 through C4 and attenuating resistor R5. Resistors R3 and R5 make up a 6 dB attenuator, so once again, there is unity voltage gain between the input and the output. However, the right input signal is not inverted.

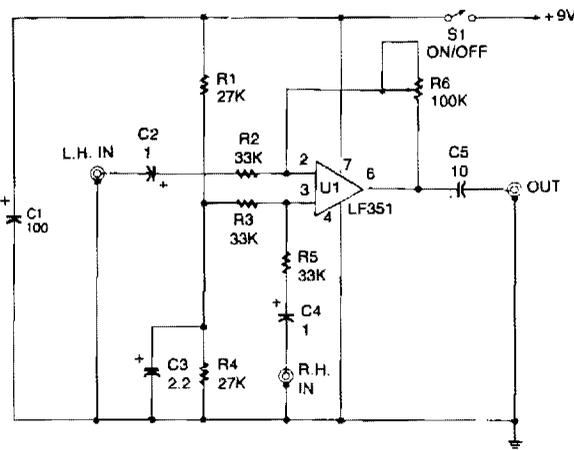Therefore, a signal appearing at both inputs is phased out by the circuit and will not appear at the output. Even if the two input signals are at slightly different levels because of different source impedances, you can still adjust for full cancellation by carefully tweaking R6.




POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 59-4
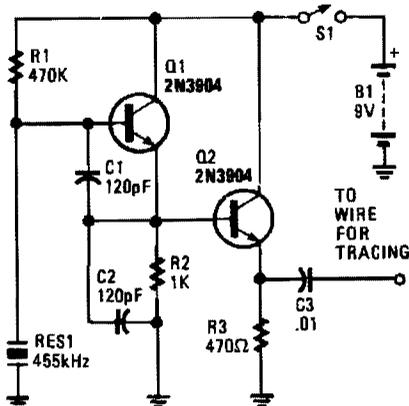
## BUG TRACER

The bug tracer is made up of a simple rf-injector circuit consisting of Q1 and Q2, and a pocket-size, AM broadcast receiver. The two-transistor rf-injector circuit supplies a constant rf signal to one end of a cable. Then the AM receiver is used as a detector, allowing you to trace the wire to its source.

Transistor Q1, along with piezoelectric ceramic resonator RES1, make up a simple rf oscillator that operates either at or near the AM-radio, 455-kHz, i-f frequency. That means that the second or third harmonic signal can easily be picked up by the receiver. Transistor Q2 is connected to an emitter-follower circuit to protect the oscillator from output loading; that helps to stabilize the output frequency and signal level.




POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 59-5




## ELECTRONIC MUSIC

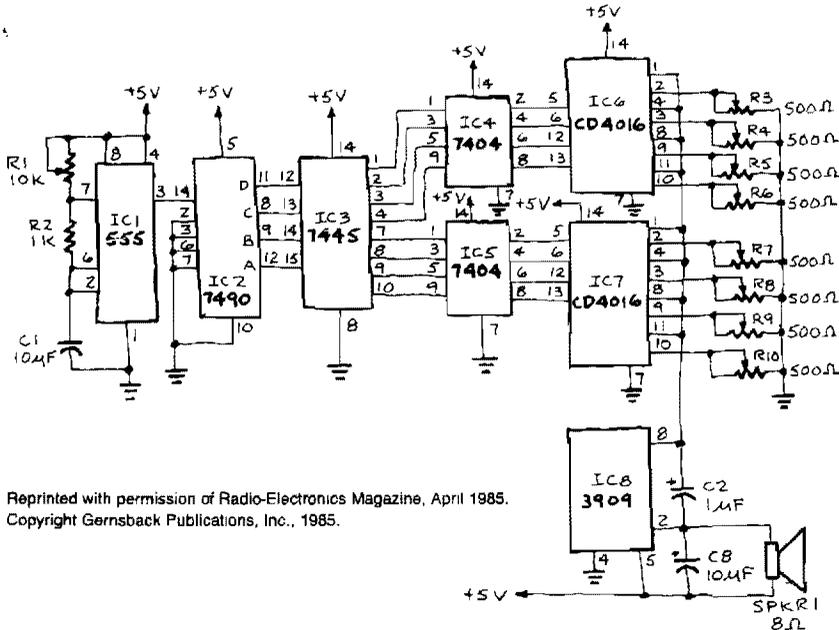

**Fig. 59-7**

IC1, a 555 timer, is set up as an astable multivibrator to produce the signal that triggers IC2, a 7490 decade counter. That IC, in turn, produces a BCD output that is fed to IC3, a 7445 BCD-to-decimal decoder/driver. IC3's output is inverted by two hex inverters, IC4 and IC5. The outputs of IC4 and IC5 are inputted to control pins on IC6 and IC7, CD4016 CMOS quad bilateral switches. As those switches open and close, different resistances (as set by potentiometers R3 through R10) are inserted into the sound-generating circuit made from IC8. The frequency at the outputs of IC6 and IC7 are adjusted to various rates, using potentiometers R3 through R10, to produce the desired tones. Capacitors can be placed in series with the potentiometers to produce a sloping sound instead of a straight tone. The negative-going output signals of IC6 and IC7 are fed through a common bus to pin 8 of IC8.
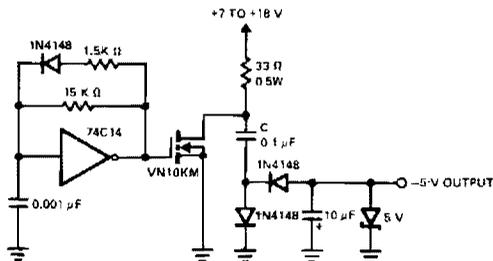
## POSITIVE INPUT/NEGATIVE OUTPUT CHARGE PUMP




SILICONIX

**Fig. 59-8**

A charge pump is a simple means of generating a low-power voltage supply of opposite polarity from the main supply. The 74C14 IC is a self-oscillating driver for the MOSFET power switch. It produces a pulse width of  $6.5 \mu\text{s}$  at a repetition frequency of 100 kHz. When the MOSFET device is off, capacitor C is charged to the positive supply. When the power through the MOSFET switches on, C delivers a negative voltage through the series diode to the output. The zener serves as a dissipative regulator. Because the MOSFET switches fast, operation at high frequencies allows the capacitors in the system to be small.

## ACID RAIN MONITOR

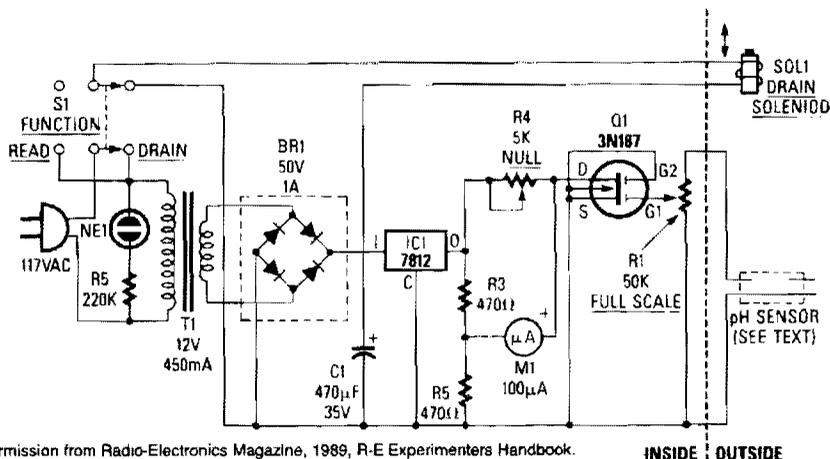


Reprinted with permission from Radio-Electronics Magazine, 1989, R-E Experimenters Handbook.  
Copyright Gernsback Publications, Inc., 1989.

**Fig. 59-9**

A simple bridge rectifier and a 12-V regulator powers the MOSFET sensing circuit. The unregulated output of the bridge rectifier operates the drain solenoid via switch S1. The sensor itself is built from two electrodes: one made of copper, the other of lead. In combination with the liquid trapped by the sensor, the electrodes form a miniature lead/acid cell whose output is amplified by MOSFET Q1. The maximum output produced by our prototype cell was about 50  $\mu$ A.

MOSFET Q1 serves as the fourth leg of a Wheatstone bridge. When sensed acidity causes the sensor to generate a voltage, Q1 turns on slightly, so its drain-to-source resistance decreases. That resistance variation causes an imbalance in the bridge, and that imbalance is indicated by meter M1.

## SIMPLE LOW-COST RF SWITCH

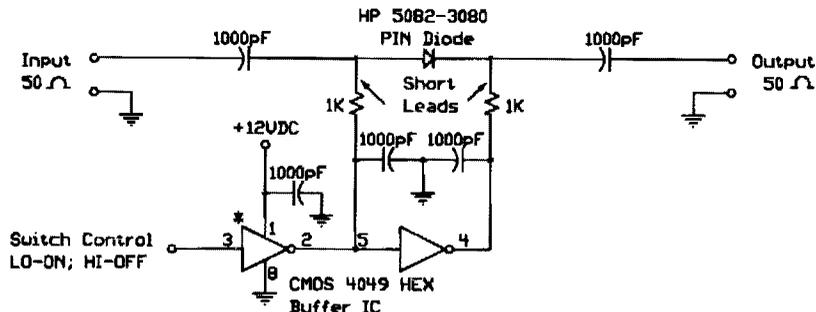

T. Harris, RF Design, July 1988, p. 53.

\* This gate is needed only if CMOS driver is not present

**Fig. 59-10**

When the digital logic level at the control input is low, the PIN diode is forward-biased by the CMOS gates. The two 1-K $\Omega$  bias resistors limit this current to the PIN diode's safe forward current limit. In this state, the switch is on. When the control input is high, the diode is reverse-biased and the switch is off. This switch is well-suited for electronically steered antenna arrays, multiple path switching, and other applications requiring small, low-cost rf switches. This particular design was used in a four-pole rotary switch for a Doppler-shift radio direction-finder operating at 144 MHz.

## BURST POWER CONTROL

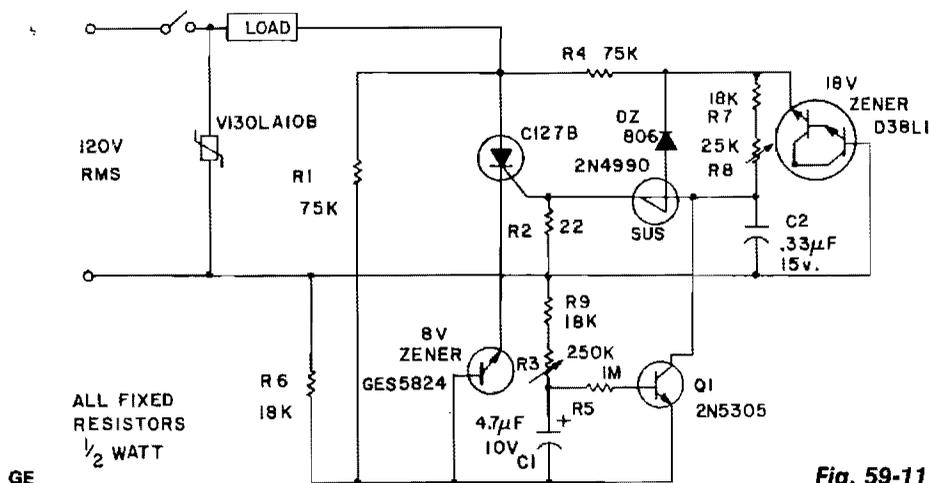


Fig. 59-11

Industrial applications sometimes require that power be only briefly applied to a load following the closure of a switch, such as a microswitch or foot switch. The load could be a heating element for use in sealing plastic bags, a dc motor that is indexed or stepped with each application of power, or a dc solenoid which is to be energized for a brief time—for example, a staple gun.

The phase angle at which the SCR triggers on is determined by the charging rate of C2 through R7 and potentiometer R8. When the breakover voltage of the gate triggering device, a silicon unilateral switch, is reached, the SCR turns on. The average dc voltage to the load is determined by the setting of R8.

## FLAME IGNITOR


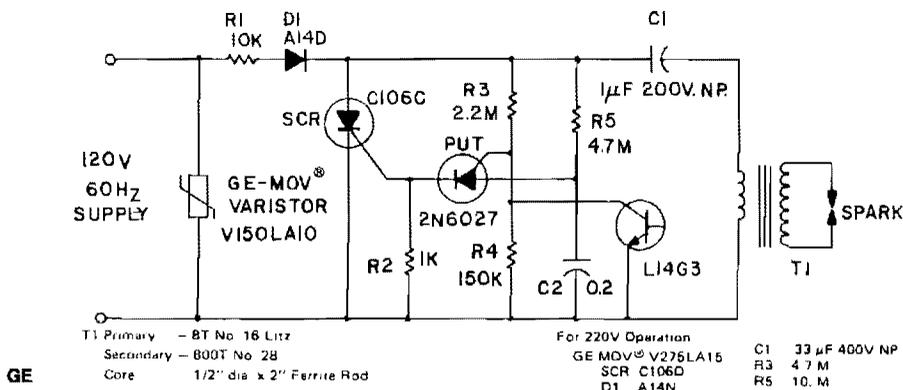


Fig. 59-12

The spark developed by the circuit is suitable for a gas ignitor. Capacitor C1 is charged through R1 and D1 toward peak line voltage. C2 is simultaneously being charged at a slower rate through R5. When the charge on C2 is sufficient to trigger the PUT, the SCR is triggered on, providing a rapid discharge path for C1 through the transformer primary. The SCR is triggered about 20 times per second with the component values shown. The L14G3 serves as a flame sensor. When ignition is achieved and sensed by the photodetector, the low  $V_{CE}$  prevents further SCR triggering.

## BAR-CODE SCANNER

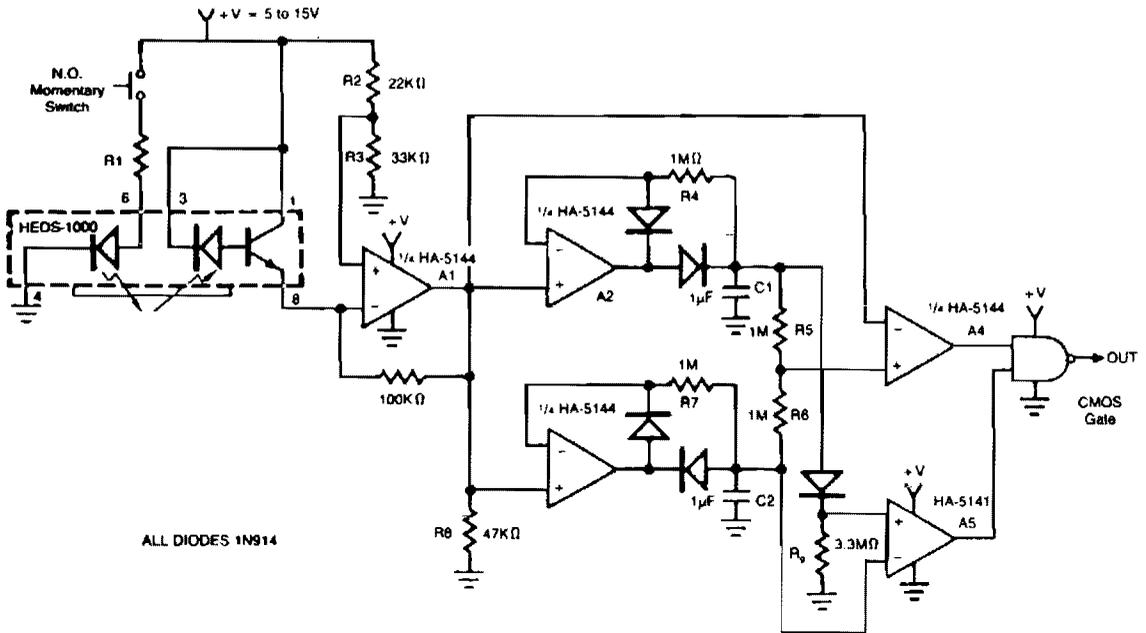


HARRIS

Fig. 59-13

The circuit illustrates a method of interfacing a HEDS-1000 emitter-detector pair with a HA-5144 for use as a bar-code scanner circuit. The HA-5144 is used as an amplifier system which converts the bar and space widths of the printed bar code into a pulse-width modulated digital signal. Amplifier A1 is used to amplify the current output of the detector. The output of A1 is passed to two precision peak-detector circuits which detect the positive and negative peaks of the received signal. Amplifier A4 is used as a comparator whose reference is maintained at the midpoint of the peak-to-peak signal by resistors R5 and R6. This provides a more accurate edge detection and less ambiguity in bar width. Amplifier A5 is used as an optional noise gate which only allows data to pass through the gate when the peak-to-peak modulation signal is larger than one diode drop. This circuit is operated by a single supply voltage with low-power consumption which makes it ideal for battery-operated data entry systems.

## 50-MHZ TRIGGER

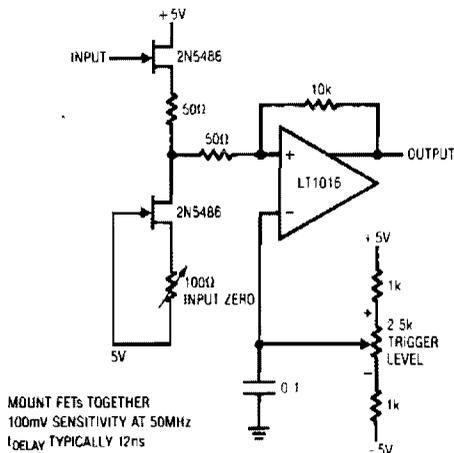


LINEAR TECHNOLOGY CORP.

Fig. 59-14

This has a stable trigger 100 mV sensitivity at 50 MHz. The FETs comprise a simple high-speed buffer and the LT1016 compares the buffer's output to the potential at the trigger level potentiometer, which can be of either polarity. The 10-KΩ resistor provides hysteresis, eliminating "chattering" caused by noisy input signals. To calibrate this circuit, ground the input and adjust the input zero control for 0 V at Q2's drain terminal.

## AIR-MOTION DETECTOR

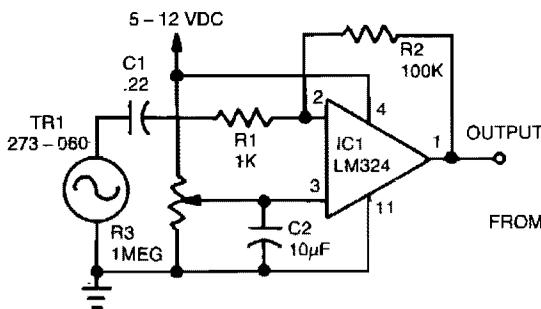

GERNSBACK PUBLICATIONS, INC.


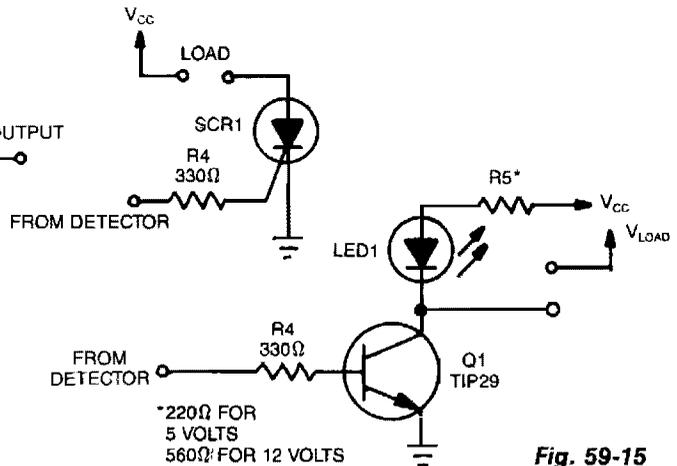


Fig. 59-15

When a current of air hits the piezo element, a small signal is generated and is fed through C1 and R1 to inverting input pin 2 of one section of the LM324. That causes output pin 1 to increase. Resistor R3 is used to adjust the sensitivity of the detector. The circuit can be set so high as to detect the wave of a hand or so low that blowing on the element as hard as you can will produce no output. Resistor R2 is used to adjust the level of the output voltage at pin 1.

The detector circuit can be used in various control applications. For example, an SCR can be used to control 117-Vac loads as shown. Also, an npn transistor, such as a TIP29, can be used to control loads as shown.

## BUG DETECTOR

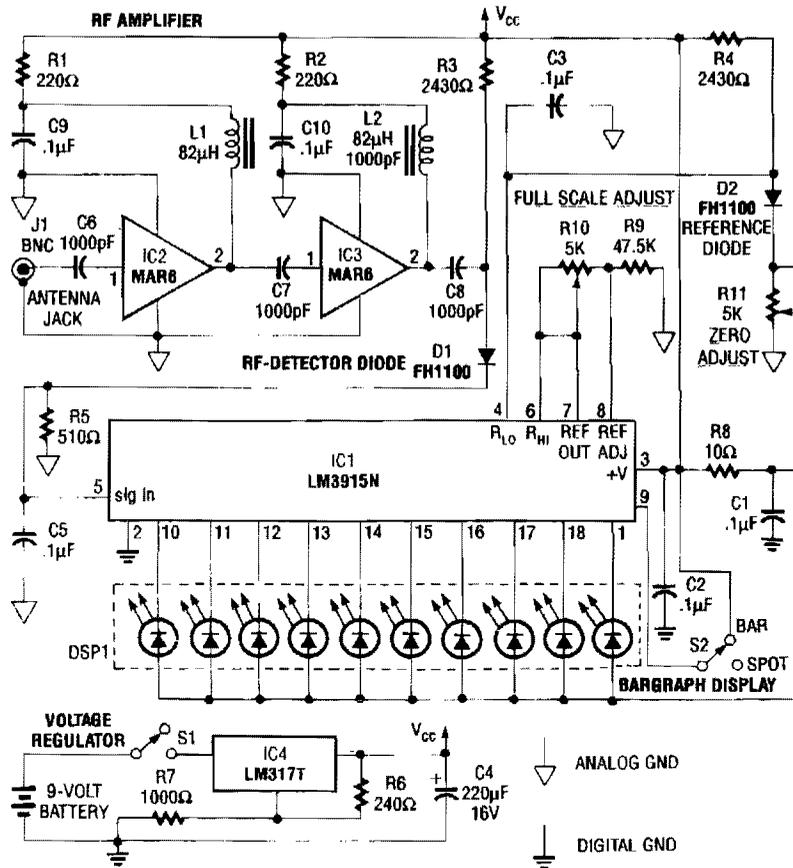


**Fig. 59-16**

Reprinted with permission from Radio-Electronics Magazine, June 1989. Copyright Gernsback Publications, Inc., 1989.

This rf detector can locate low-power transmitters (bugs) that are hidden from sight. It can sense the presence of a 1-mW transmitter at 20 feet, which is sensitive enough to detect the tiniest bug. As you bring the rf detector closer to the bug, more and more segments of its LED bar-graph display light, which aids in direction finding.

The front end has a two-stage wideband rf amplifier, and a forward-biased hot-carrier diode for a detector. After detection, the signal is filtered and fed to IC1, an LM3915N bar-graph driver having a logarithmic output. Each successive LED segment represents a 3-dB step.

## DOOR OPENER

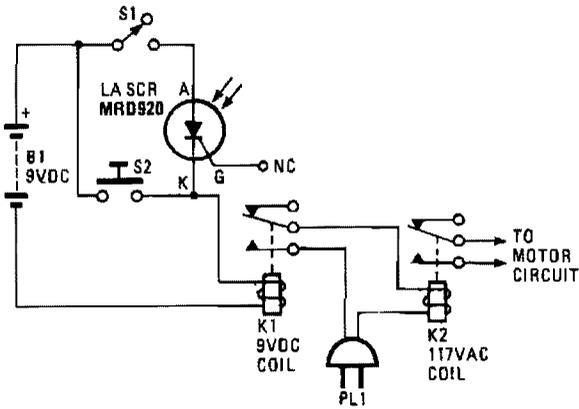

The door opener derives its power from a 9-V battery. A momentary-contact switch, S2, is provided in the event that manual opening and closing is required. Relay K1 is a 9-V type and relay K2 is a 117-Vac latching-type, which automatically latches with the first burst of current and opens on the second burst. The gate lead of the LASCR is not used; a light source triggers the LASCR unit into conduction, causing current to flow in the coil of the relay. That, in turn, causes K1's contacts to close, thereby energizing K2 (closing its contacts), and operating the garage door motor.

HANDS-ON ELECTRONICS

Fig. 59-17

# 60


## Mixers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Signal Combiner  
Simple Mixer  
Input-Buffered Mixer  
Four-Channel Mixer  
Universal Mixer Stage

## SIGNAL COMBINER

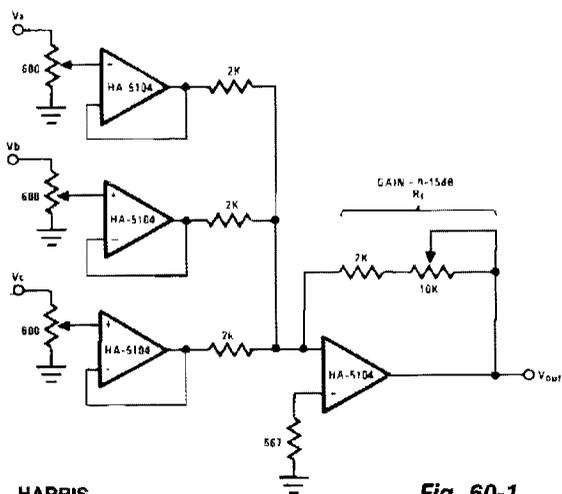


HARRIS

Fig. 60-1

This circuit uses buffer stages to prevent channel crosstalk back through the mixer resistor network. The potentiometers used for each stage allow for convenient signal strength adjustment, while maintaining input impedance matching at the 600- $\Omega$  audio standard. The feedback resistor  $R_f$  will permit the output signal gain to be as high as 15 dB.

## SIMPLE MIXER

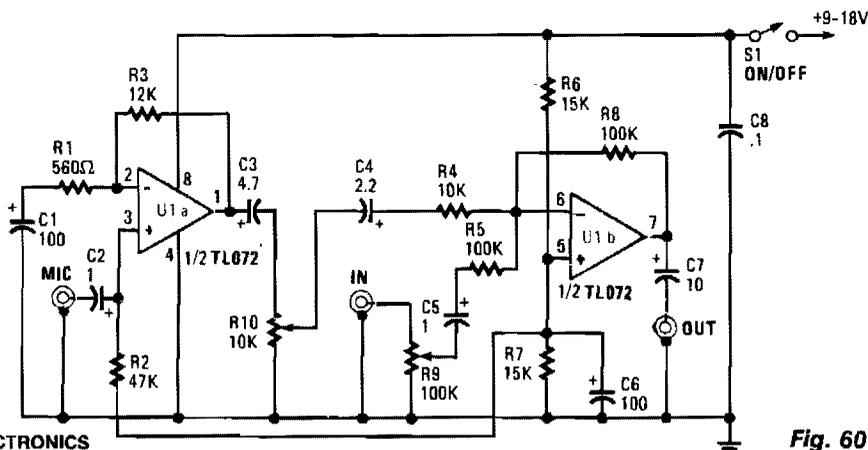


POPULAR ELECTRONICS

Fig. 60-2

This mixer is built around a TL072 dual BiFET op amp with a JFET input stage, and can be powered from a single-ended 9- to 18-V power supply. The microphone input is capacitively coupled to the noninverting input of U1a.

Resistors R1 and R3 set the voltage gain at about 26 dB and serve as a negative feedback network for U1a. Capacitors C1 through C3 are dc-blocking capacitors. Most high-impedance microphones have outputs of a few mV. Often, a preamp stage just isn't enough, so the microphone signal is given a boost of about 20 dB in the mixer. The noninverting input of U1b is biased to half the supply voltage by R6, R7, and C6. Resistors R5 and R8 make up the negative-feedback network and set the voltage gain of U1b at unity. Capacitor C5 is for dc blocking at this input.

## INPUT-BUFFERED MIXER

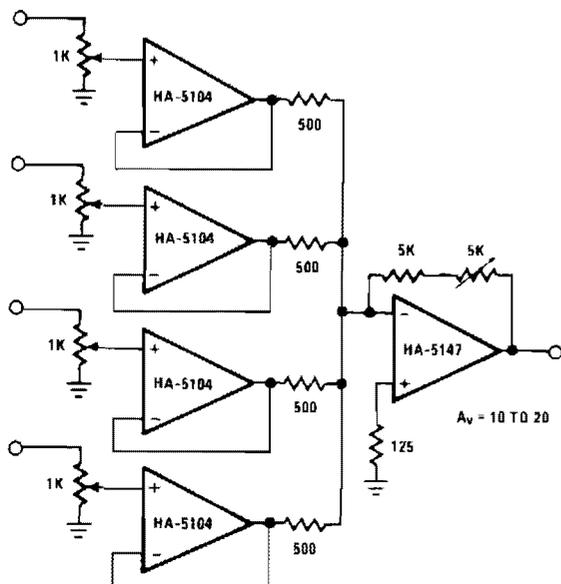


HARRIS

Fig. 60-3

A high signal-to-noise ratio is important in signal construction and combination. The HA-5147 aids in lowering overall system noise and thereby raises system sensitivity. The signal combination circuit incorporates input buffering with several other features to form a relatively efficient mixer stage with a minimum of channel crosstalk. The potentiometer used for each channel allows for both variable input levels and a constant impedance for the driving source. The buffers serve mainly to prevent reverse crosstalk back through the resistor network. This buffering allows for the combination of varying strength signals without reverse contamination. The gain of the final stage is set at a minimum of 10 and can be adjusted to as much as 20. This allows a great amount of flexibility when combining a vast array of input signals.


## FOUR-CHANNEL MIXER

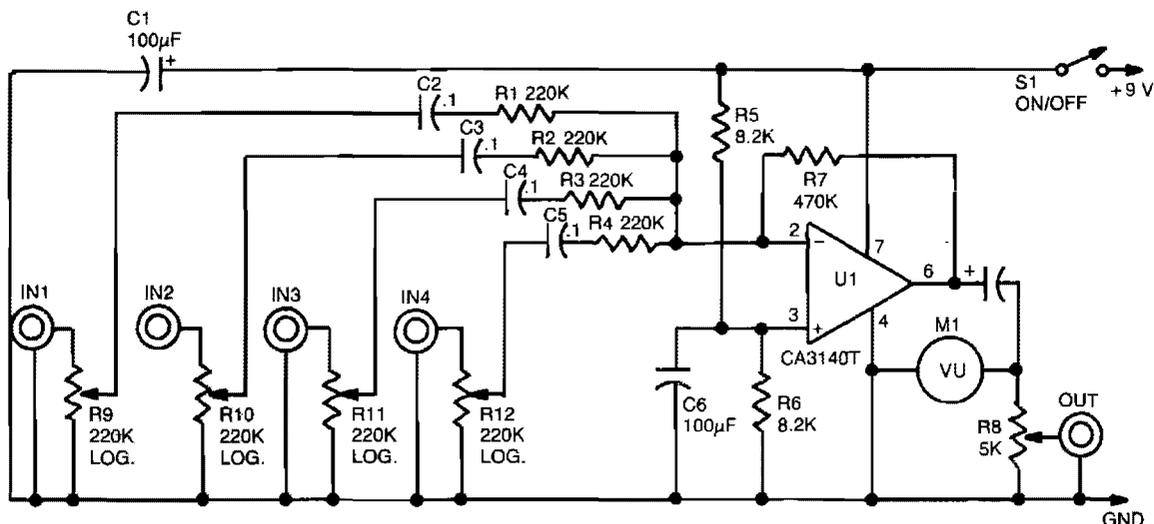

POPULAR ELECTRONICS

Fig. 60-4

## UNIVERSAL MIXER STAGE

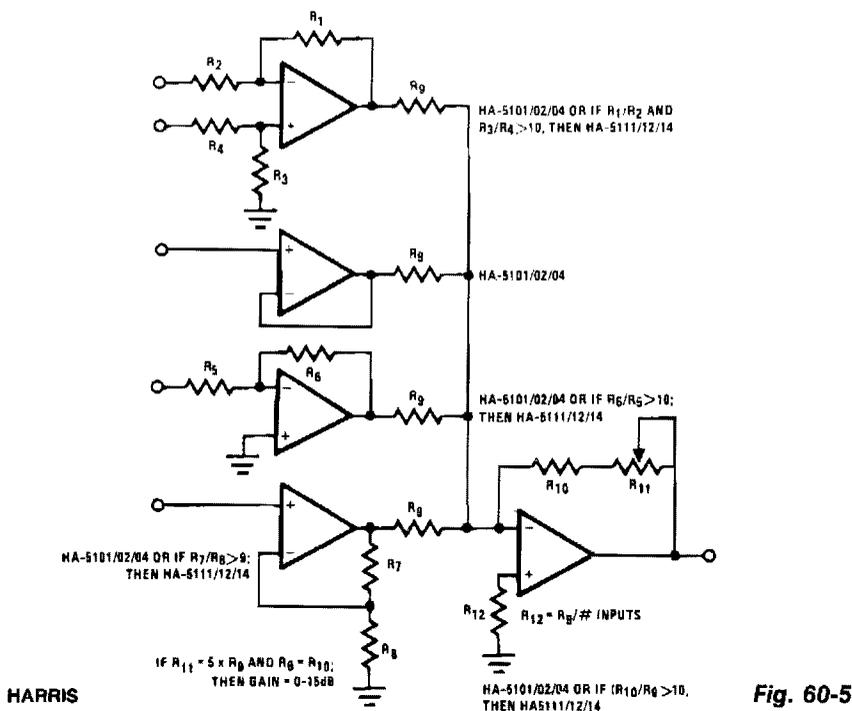

This circuit illustrates some possible buffer combinations. These include a differential input stage, a voltage follower as well as both noninverting and inverting stages. The allowable resistor ratios and recommended device types are also included. One restriction applies to this type of mixer network in which  $R_9$  is greater than  $2.4 \text{ K}\Omega$ . This limits the worst case output current for each of the input buffers to less than 10 mA.

# 61


## Modulators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Rf Modulator	Pulse-Position Modulator
Modulator	Pulse-Width Modulator
SAW Oscillator Modulator	Balanced Modulator
Rf Modulator	Double-Sideband Suppressed-Carrier
Modulation Monitor	Modulator


## RF MODULATOR

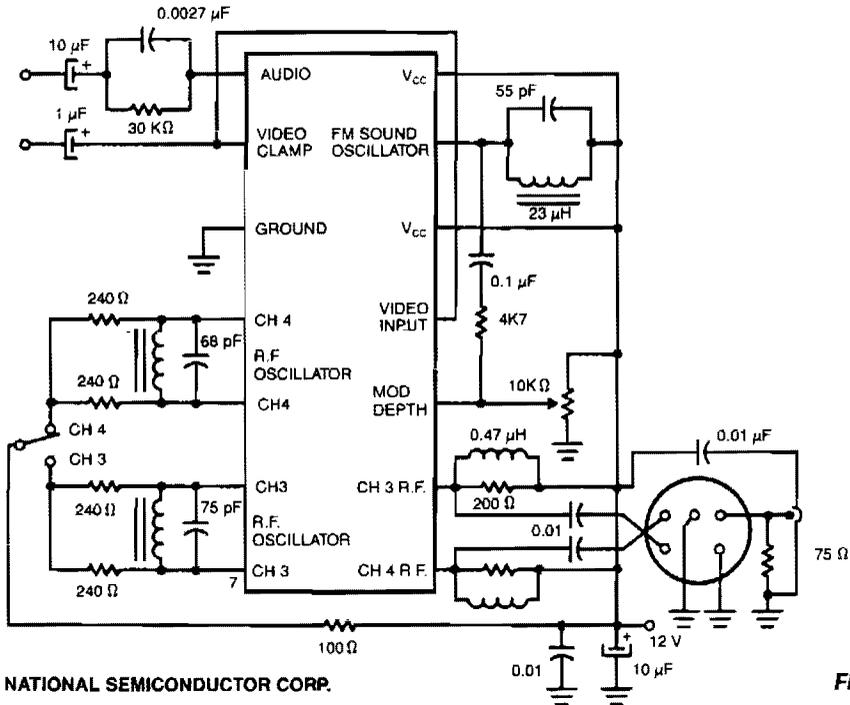

**Fig. 61-1**

Two IC rf modulators convert a suitable baseband video and audio signal up to a low VHF modulated carrier—Channel 2 through 6 in the U.S., and 1 through 3 in Japan—the LM1889 and the LM2889. Both ICs are identical regarding the rf modulation function, including pin outs, and can provide either of two rf carriers with dc switch selection of the desired carrier frequency. The LM1889 includes a crystal-controlled chroma subcarrier oscillator and balanced modulator for encoding R through Y or U and V color difference signals. A sound intercarrier frequency ic oscillator is modulated using an external varactor diode. The LM2889 replaces the chroma subcarrier function of the LM1889 with a video dc restoration clamp and an internal frequency-modulated sound intercarrier oscillator.

## MODULATOR

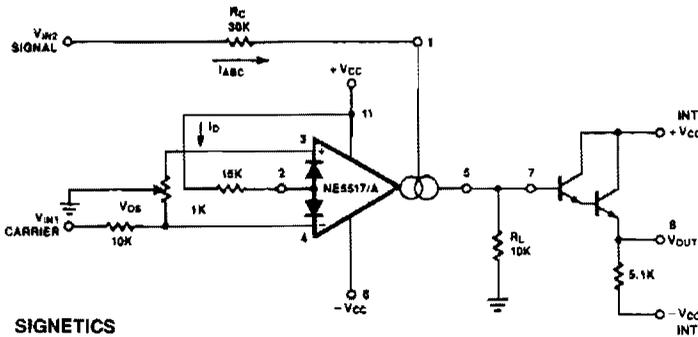


**Fig. 61-2**
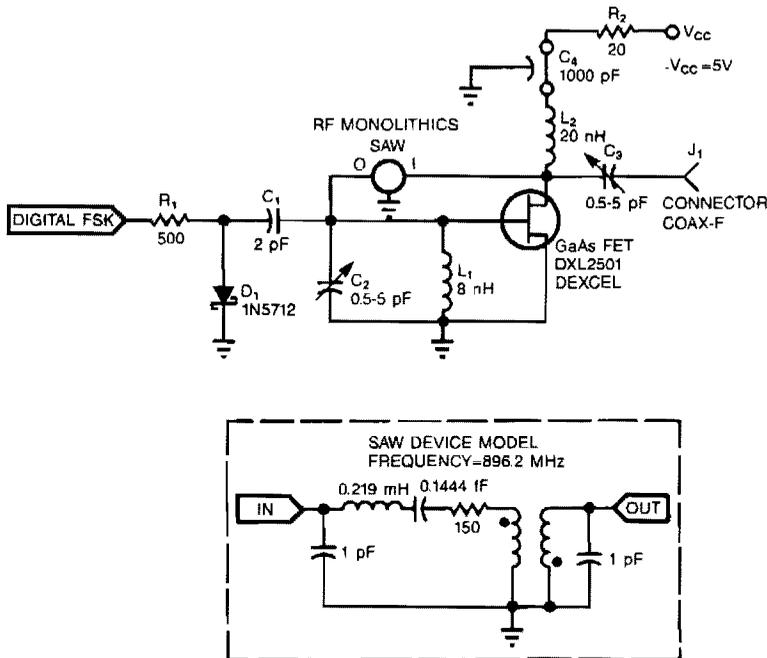
## MODULATOR (Cont.)

Because the transconductance of an operational transconductance amplifier is directly proportional to  $I_{ABC}$ , the amplification of a signal can be controlled easily. The output current is the product from transconductance  $\times$  input voltage. The circuit is effective up to approximately 200 kHz. Modulation of 99% is easy to achieve.

### SAW OSCILLATOR MODULATOR



ELECTRONIC DESIGN


Fig. 61-3

Adding a diode, a resistor, and a capacitor to the SAW (surface-acoustic-wave) oscillator allows you to use the oscillator in FSK (frequency-shift-keying) applications. D1, R1, and C1 form a simple diode switch in which D1 shunts C1 to ground. When the digital FSK input to R1 is low, D1 is off, and the small junction capacitance of D1 couples C1 to ground. A high FSK signal causes current to flow through R1 and D1. D1's dynamic impedance is small when it is in forward conduction. Therefore, C1 sees a lower impedance path to ground. Thus, the FSK input effectively switches C1 in and out of the oscillator's circuit.

When C1 is in the circuit—digital FSK is high—it pulls the frequency of the circuit slightly lower because of the additional phase shift C1 introduces at the GaAs FET gate terminal (available from: Dexcel, Div. of Gould, Santa Clara, CA). The SAW device (available from: RF Monolithics, Dallas, TX) restricts the amount of frequency shifting—usually less than 20 ppm for a high-Q SAW device.

The oscillator shown produces a center frequency of 896.2 MHz with an FSK deviation of 17 kHz when you drive the FSK input with a 0 to 5 V signal. The frequency also depends on L1 and C2.

## RF MODULATOR

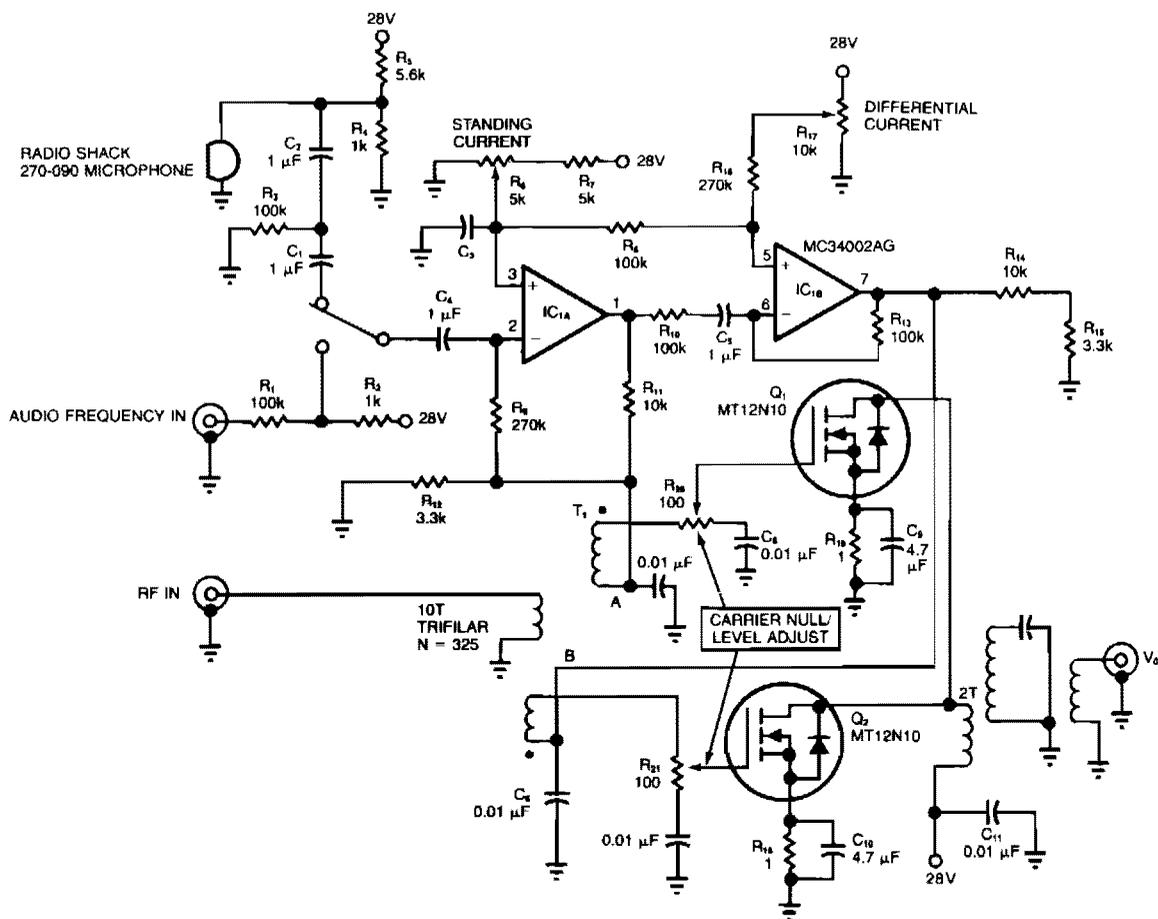


EDN

Fig. 61-4

Because power MOSFETs offer high power gain at both audio and radio frequencies, they are useful in many areas of radio-circuit design. For rf applications, a MOSFET's large safe operating area,  $V_{DS}$  vs  $I_D$ , protects it against damage from reflected rf energy. As a modulator, a MOSFET's transfer linearity aids fidelity. In the suppressed-carrier modulator, an rf signal is applied to the primary of transformer T1, whose secondaries provide equal-amplitude, opposite-phase rf drive signals to output FETs Q1 and Q2. Output  $V_o$  is zero when no audio-frequency signals are present, because the opposite-phase rf signals from Q1 and Q2 cancel. When audio-frequency signals appear at nodes A and B, you obtain a modulated rf output ( $V_o$ ). Source resistors R18 and R19 improve the dc stability and low-frequency gain. A phase inverter, based on the dual op amp IC1A and IC1B, generates the out-of-phase, equal-amplitude, audio-frequency modulation signals.

## MODULATION MONITOR

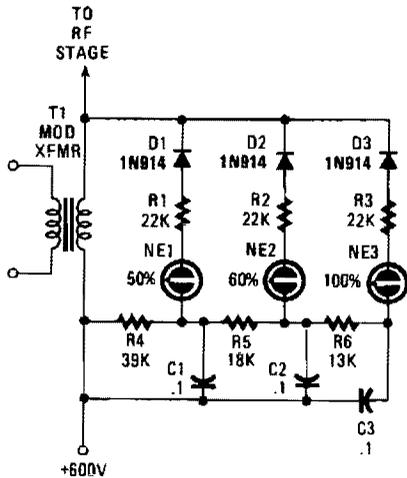


POPULAR ELECTRONICS


Fig. 61-5

Switching diodes are used to fire the neon lamps when negative-peak modulation hits 50, 60, and 100%. To use the circuit, keep an eye on the lamps. You should attempt to keep the 50% lamp firing all the time, the 60% lamp should be on as much as possible, but try to prevent the 100% lamp from lighting.

## PULSE-POSITION MODULATOR

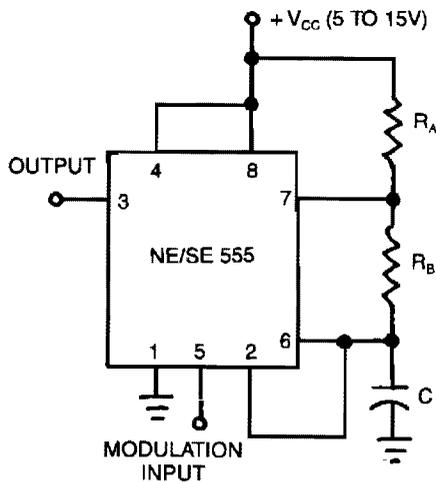

a. Schematic Diagram

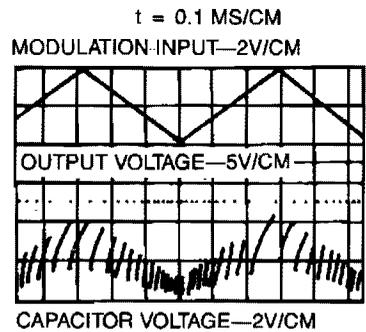

$$R_A = 3K\Omega \quad R_B = 500\Omega \quad C = .01\mu F$$


b. Expected Waveform

SIGNETICS


Fig. 61-6

This application uses the timer connected for astable (free-running) operation, with a modulating signal again applied to the control voltage terminal. The pulse position varies with the modulating signal, since the threshold voltage and the time delay is varied.

## PULSE-WIDTH MODULATOR

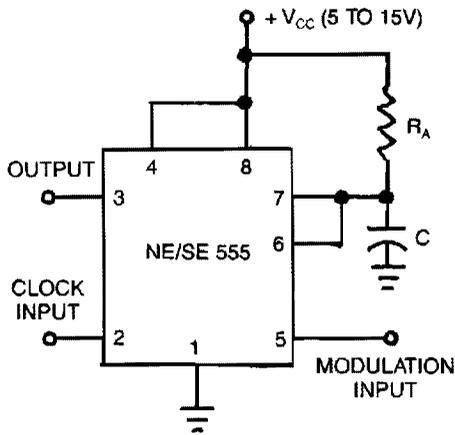

a. Device Schematic

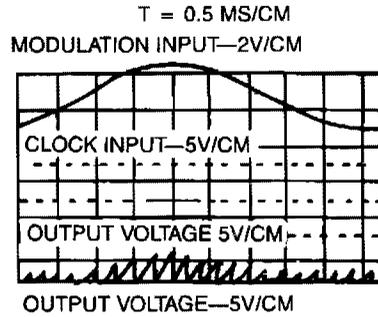


b. Expected Waveforms

### SIGNETICS

Fig. 61-7

In this application, the timer is connected in the monostable mode. The circuit is triggered with a continuous pulse train and the threshold voltage is modulated by the signal applied to the control voltage terminal at pin 5. This has the effect of modulating the pulse width as the control voltage varies. The figure shows the actual waveform generated with this circuit.

## BALANCED MODULATOR

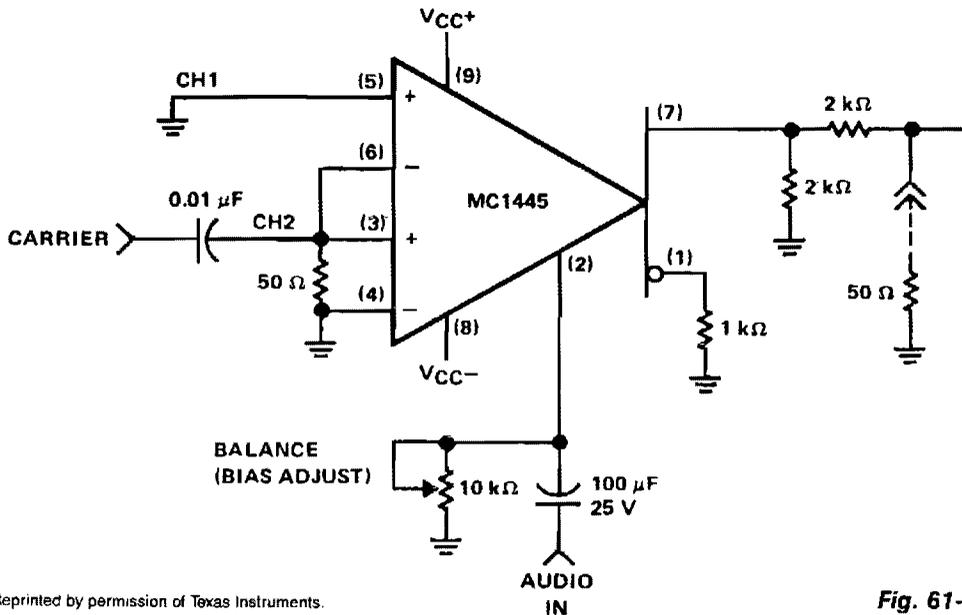


Reprinted by permission of Texas Instruments.

Fig. 61-8

## BALANCED MODULATOR (Cont.)

When the carrier level is adequate to switch the cross-coupled pair of differential amplifiers, the modulation signal, which has been applied to the gate, will be switched at the carrier rate, between the collector loads. When switching occurs, it will result in the modulation being multiplied by a symmetrical switching function. If the modulation gate remains in the linear region, only the first harmonic will be present. To balance the MC1445 modulator, equal gain must be achieved in the two separate channels. To remain in the linear region, the modulation input must be restricted to approximately 200 mV pk-pk. Because the gate bias point is sensitive to the amount of carrier suppression, a high-resolution, 10-turn potentiometer should be used.
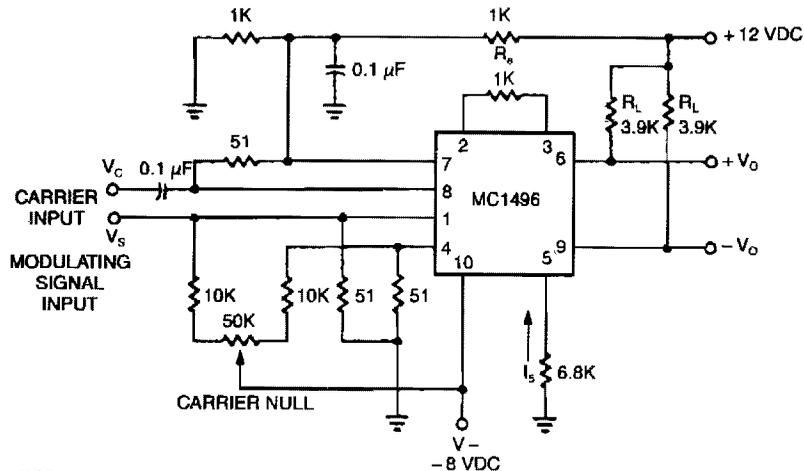
## DOUBLE-SIDEBAND SUPPRESSED-CARRIER MODULATOR



NOTE:  
All resistor values are in ohms

SIGNETICS

Fig. 61-9

The basic current allows no carrier to be present in the output. By adding offsets to the carrier differential pairs, controlled amounts of carrier appear at the output. The amplitude becomes a function of the modulation signal—AM modulation.

# 62

## Motor-Control Circuits


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

PWM Servo Amplifier  
PWM Speed Control and  
Energy-Recovering Brake  
Start-and-Run Motor Circuit  
Automatic Fan-Speed Controller  
Efficient Switching Controller  
Closed-Loop Motor-Speed Control  
Servo System Controller  
Switched-Mode Motor-Speed  
Controller  
Tachless Motor-Speed Controller

Constant-Speed Motor Driver  
Dc Motor Drive with Fixed Speed  
Control  
Bridge-Type Ac Servo Amplifier  
Speed-Controlled Reversible Dc  
Motor Drive  
PWM Motor Controller  
Stepping Motor Drive  
High-Efficiency Motor-Speed  
Controller

## PWM SERVO AMPLIFIER

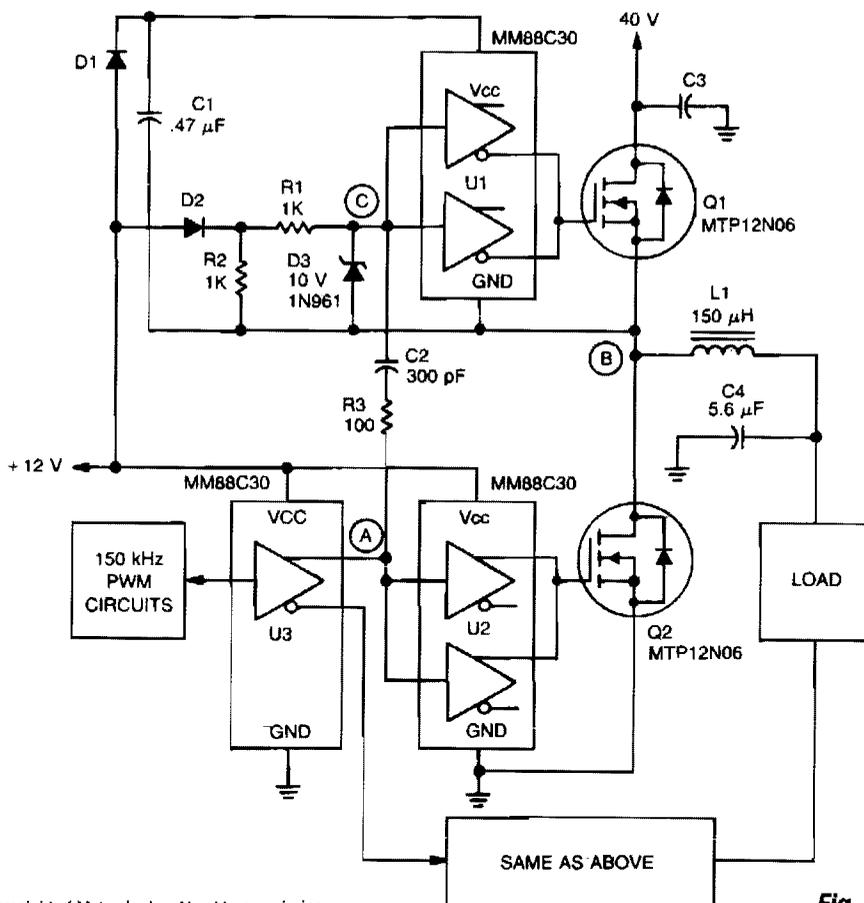


Copyright of Motorola, Inc. Used by permission.

Fig. 62-1

A major feature of the PWM servo amplifier is elimination of a pulse transformer. A 150 kHz pulse-width modulated signal is applied to U3, with its complementary outputs applied to identical circuits to drive the load. When point A increases, Q2 is on and point B is at ground potential. The  $V_{CC}$  for U1 is maintained through D1, and Q1 is held off by D2. When point A decreases, Q2 turns off, point C is pulled low by C2, which turns Q1 on. The time constant for R1, R3, and C2 can hold Q1 on just long enough to allow the voltage at point B to start rising. As point B rises, it charges C2 by forward biasing D3, maintaining point C high with respect to U1, and keeping Q1 turned on.

With point B at 40 V, D2 is off and point C is held low by R1 and R2, and  $V_{CC}$  for U1 is maintained by the charge on C1. When point A increases again, Q2 again turns on, C2 pushes point C high, and turns Q1 off long enough to allow the voltage at point B to start falling. C2 is now discharged by reverse-biased D3, which keeps point C high with respect to U1, and keeps Q1 off. Once point B reaches ground potential, D1 again turns on, recharging C1, and maintaining  $V_{CC}$  to U1. D2 also turns on and keeps Q1 off.
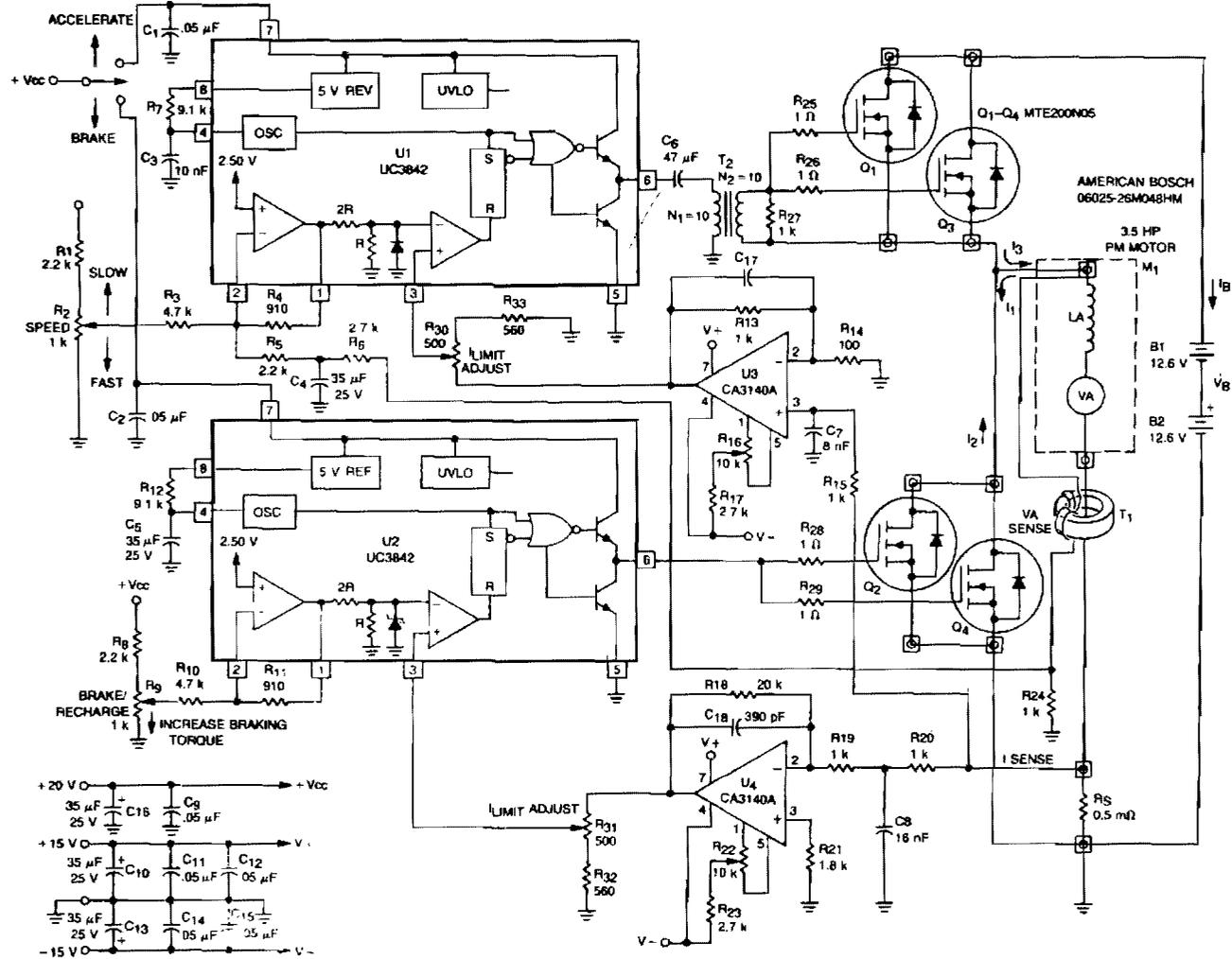
## PWM SPEED CONTROL AND ENERGY-RECOVERING BRAKE



Copyright of Motorola, Inc. Used by permission.

Fig. 62-2

This circuit uses the main drive motor as a generator/brake to recover the battery charge during vehicle braking. When this is done, it can increase the overall range and efficiency of an electric vehicle.

In the accelerate mode, Q1 through Q3 receive gate pulses from U1, an on-line, current-mode, PWM controller IC. Assuming negligible effects of  $R$ , when Q1 through Q3 turn on, current  $I_1$  builds up through the motor at a rate of:

$$dI_1 = V_B - V_A$$

where:  $V_A$  = Battery voltage  
 $V_B$  = Motor's back EMF  
 $L_A$  = Motor inductance in henries

Motor current and torque continue to rise until the voltage on the  $I_{SENSE}$  line is greater than  $I_{RESET}$ , as determined by the speed potentiometer. At this time, Q1 through Q3 are switched off, current  $I_2$  begins to flow and decreases at a rate of:

$$\frac{dI_2}{dt} = \frac{V_A}{L_A}$$

until the next clock period begins.

As vehicle braking occurs, accelerate PWM IC U1 is switched off and braking PWM IC U2 and Q2 through Q4 are switched on. During this time, the back EMF source voltage causes current  $I_3$  to begin to flow at the rate of:

$$\frac{dI_3}{dt} = \frac{V_A}{L_A}$$

The current  $I_3$  continues to rise until  $I_{SENSE}$  is greater than  $I_{RESET}$ . Now, Q2 through Q4 are switched off and  $I_B$  is forced to flow back into the storage battery, thus energy is recovered.

The braking torque produced by the motor is proportional to the average reverse current that flows through the motor on the duty cycle of Q2 through Q4. The braking force can continue until:

$$V_A = 0$$

For reliable performance, voltage supplies should be independent of the main battery voltage.



## AUTOMATIC FAN SPEED CONTROLLER (Cont.)

The controller circuit can reduce a fan's noise, power consumption, and wear, particularly in the presence of a low, fluctuating ambient temperature. Mount a temperature sensor in the fan's airstream, and the circuit will adjust the fan speed as necessary to maintain a relatively constant sensor temperature. Input components R1 and C1 integrate the input square wave, producing a quasitriangular wave at the non-inverting input of op amp IC1A. At this inverting input is a reference voltage that decreases as temperature increases. The two-terminal sensor produces  $1 \mu\text{A}/^\circ\text{K}$ . The result is a rectangular wave at the output of IC1A with a duty cycle proportional to absolute temperature. Thus, a rise in temperature triggers a counteracting cooling effect by delivering more power to the fan. To calibrate the system with the sensor at room temperature, simply adjust R2 for a 50% duty cycle at  $V_1$ . The fan will switch off at approximately  $0^\circ\text{C}$  and will be fully on at  $44^\circ\text{C}$ .

## EFFICIENT SWITCHING CONTROLLER


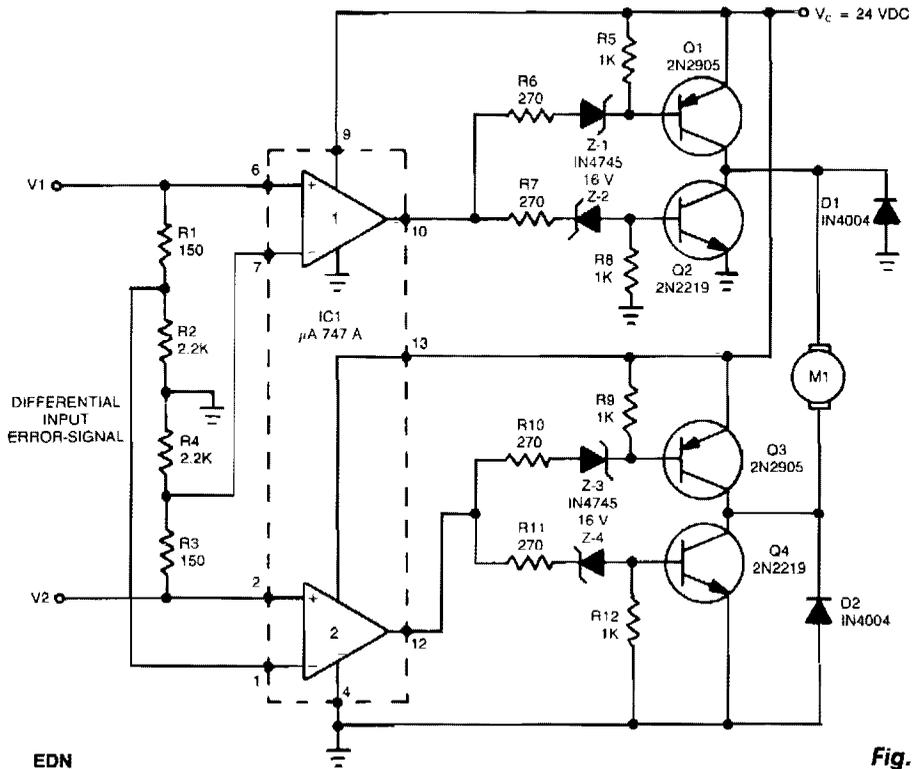


Fig. 62-5

This high-performance switching controller for a low-power dc servo motor uses a symmetrical complementary-transistor bridge. The bridge acts as a reversing switch between the motor and a single-ended power supply. Since the transistors operate either fully on or completely off, except during a very short transition period, much less heat is dissipated than in linear-amplifier circuits. Damping is provided by the circuit's inherent dynamic braking. Since either maximum or zero voltage is applied to the motor, the dynamic response is faster than that of linear servo drives.

## SERVO SYSTEM CONTROLLER

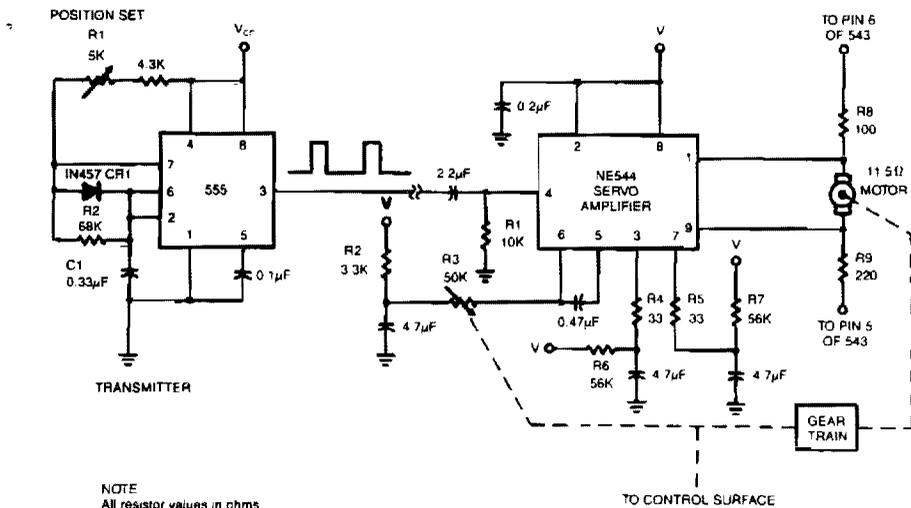


SIGNETICS

Fig. 62-6

To control a servo motor remotely, the 555 needs only six extra components.

## SWITCHED-MODE MOTOR-SPEED CONTROLLER

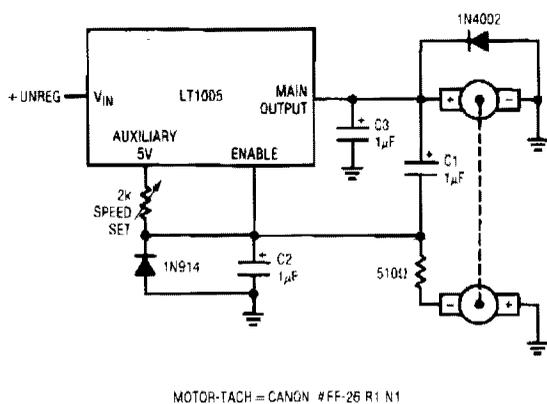


LINEAR TECHNOLOGY CORP.

Fig. 62-7

This circuit uses a tachometer to generate a feedback signal which is compared to a reference signal supplied by the auxiliary output. When power is applied, the tachometer output is zero and the regulator output comes on, forcing current into the motor. As motor rotation increases, the negative tachometer output pulls the enable pin toward ground. When the enable pin's threshold voltage is reached, the regulator output decreases and the motor slows. C1 provides positive feedback, ensuring clean transitions. In this fashion, the motor's speed is servo-controlled at a point determined by the 2-KΩ potentiometer setting. The regulator free-runs at whatever frequency and duty cycle are required to maintain the enable pin at its threshold. The loop bandwidth and stability are set by C2 and C3. The 1N914 diode prevents the negative output tachometer from pulling the enable pin below ground, and the 1N4002 commutates the motor's negative flyback pulse.

## CLOSED-LOOP MOTOR-SPEED CONTROL

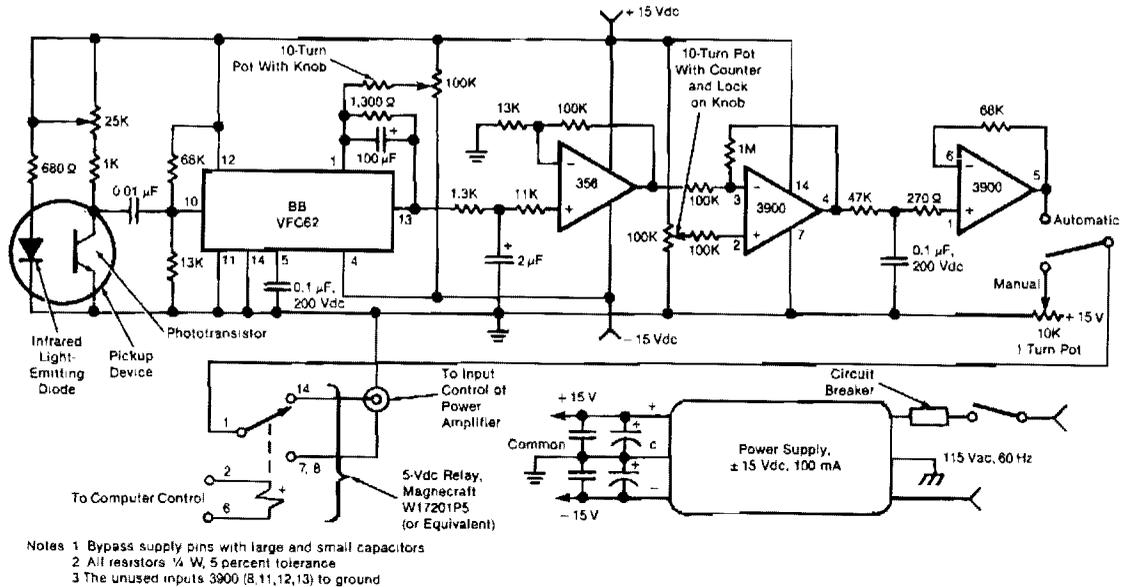

**Fig. 62-8**


NASA

This electronic motor-speed control circuit is designed to operate in an electrically noisy environment. The circuit includes an optoelectronic pickup device, which is placed inside the motor housing to provide a speed feedback signal. The circuit automatically maintains the speed of the motor at the commanded value.

The pickup device contains an infrared LED and a phototransistor. The radiation from the diode is chopped into pulses by the motor fan blades, which are detected by the phototransistor. The train of pulses from the phototransistor is fed to a frequency-to-voltage converter, the output of which is a voltage proportional to the speed of the motor. This voltage is low-pass filtered, amplified, and compared with a manually-adjustable control voltage that represents the commanded speed.


The difference between the speed-measurement and speed-command signals is amplified and fed as a control voltage to an external power amplifier that drives the motor. A selector switch at the output of the final amplifier of this circuit also enables the operator to bypass the circuit and manually set the control voltage for the external amplifier.

## TACHLESS MOTOR-SPEED CONTROLLER

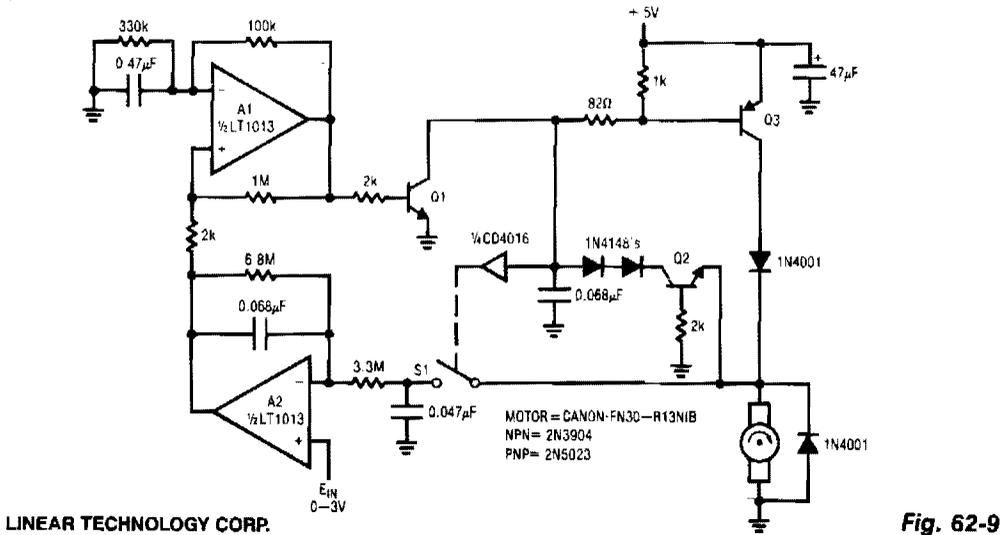

This circuit is particularly applicable to digitally-controlled systems in robotic and X-Y positioning applications. By functioning from the 5-V logic supply, it eliminates additional motor-drive supplies. The *tachless* feedback saves additional space and cost. The circuit senses the motor's back EMF to determine its speed. The difference between the speed and a set point is used to close a sampled loop around the motor. A1 generates a pulse train. When A1's output is high, Q1 is biased, and Q3 drives the motor's ungrounded terminal. When A1 decreases, Q3 turns off and the motor's back EMF appears after the inductive flyback ceases. During this period, S1's input is turned on, and the 0.047- $\mu$ F capacitor acquires the back EMF's value. A2 compares this value with the set point and the amplified difference (trace D) changes A1's duty cycle, controlling the motor speed.

## CONSTANT-SPEED MOTOR DRIVER

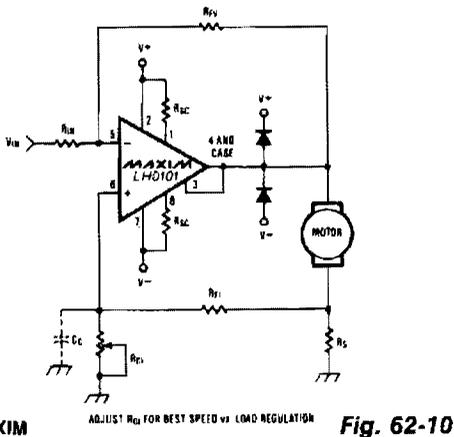

When the torque load on the motor increases, its current increases. This current increase is sensed across  $R_s$ , and positive feedback is applied to the noninverting terminal of the LH0101, thereby increasing the motor voltage to compensate for the increased torque load. With the proper amount of positive feedback, the motor-speed variation can be kept below 1% from no load to full load.

## DC MOTOR DRIVE WITH FIXED SPEED CONTROL


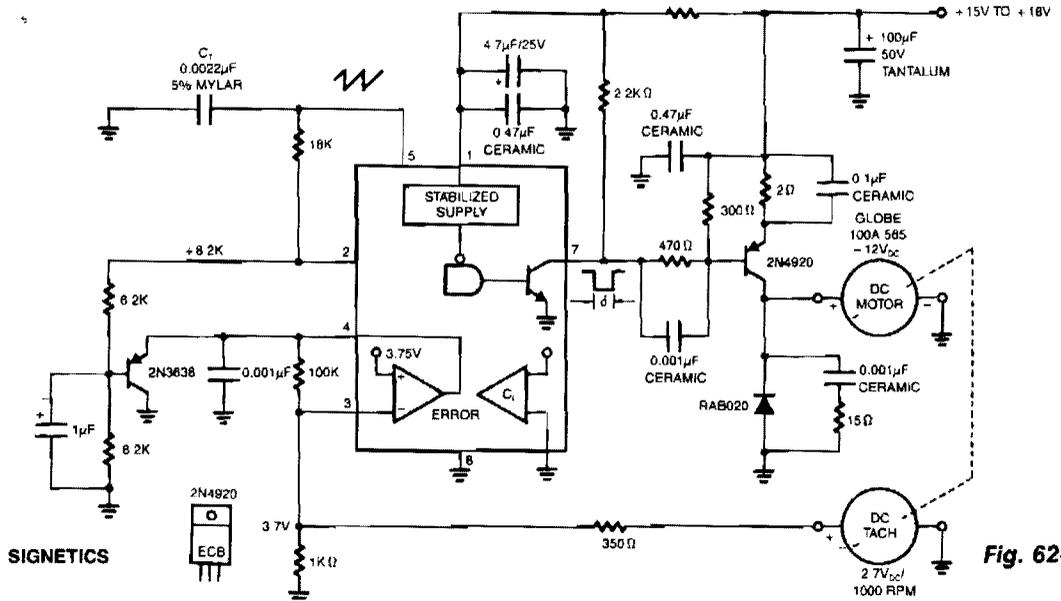


Fig. 62-11


The NE5561 provides pulse-proportional drive and speed control based on dc tachometer feedback. This simple switching circuit consists of transistor 2N4920 pnp with a commutation diode used to deliver programmed pulse energy to the motor. A frequency of approximately 20 kHz is used to eliminate audio noise. The dc tach delivers 2.7 V/1000 RPM. Negative feedback occurs when this voltage is applied to the error amplifier of the NE5561. The duty cycle varies directly with load torque demand. The no-load current is  $\approx 0.3$  A and full load is 0.6 A.

## BRIDGE-TYPE AC SERVO AMPLIFIER

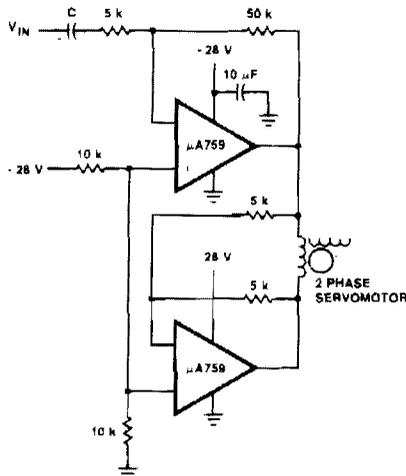

This motor driver circuit uses a  $\mu$ A759 power amplifier to drive a two-phase servomotor.

## SPEED-CONTROLLED REVERSIBLE DC MOTOR DRIVE

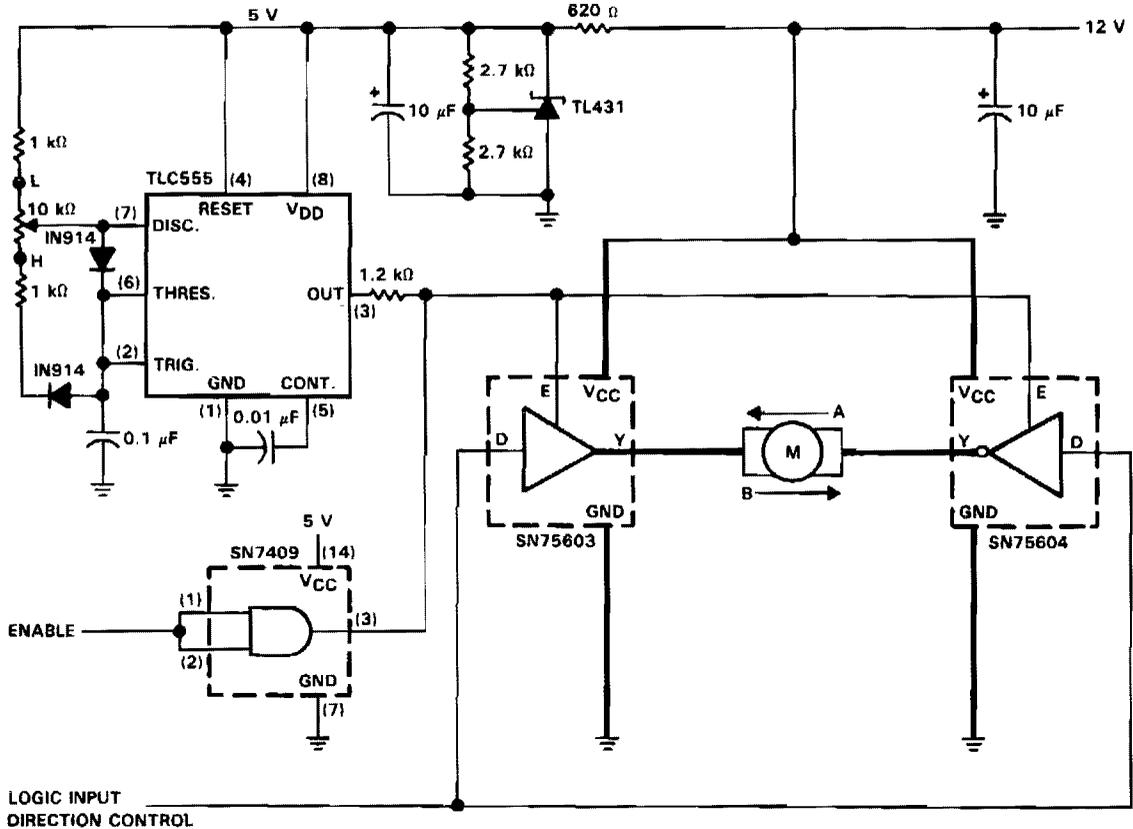

**Fig. 62-13**

Reprinted by permission of Texas Instruments.

The figure illustrates a reversible dc motor drive application with adjustable speed control. The D inputs for these drivers are complementary and can be tied together and driven from the same logic control for bidirectional motor drive. The enables are tied together and driven by a pulse-width-modulated generator providing on duty cycles of 10 to 90% for speed control. A separate enable control is provided through an SN7409 logic gate. See the truth table for this motor controller application.

Definitions for the terms used in the truth table are as follows:

- EN Enable
- DC Direction control
- SP.C Speed control
- A Direction of current—right to left
- B Direction of current—left to right
- H Logic 1 voltage level
- L Logic 0 voltage level
- N Speed control set for narrow pulse width
- W Speed control set for wide pulse width
- X Irrelevant

**Truth Table for Motor Control Circuit**

EN	DC	SP.C	MOTOR DIRECTION	MOTOR SPEED
L	X	X	OFF	OFF
H	L	N	A	SLOW
H	L	W	A	FAST
H	H	N	B	SLOW
H	H	W	B	FAST

## PWM MOTOR CONTROLLER

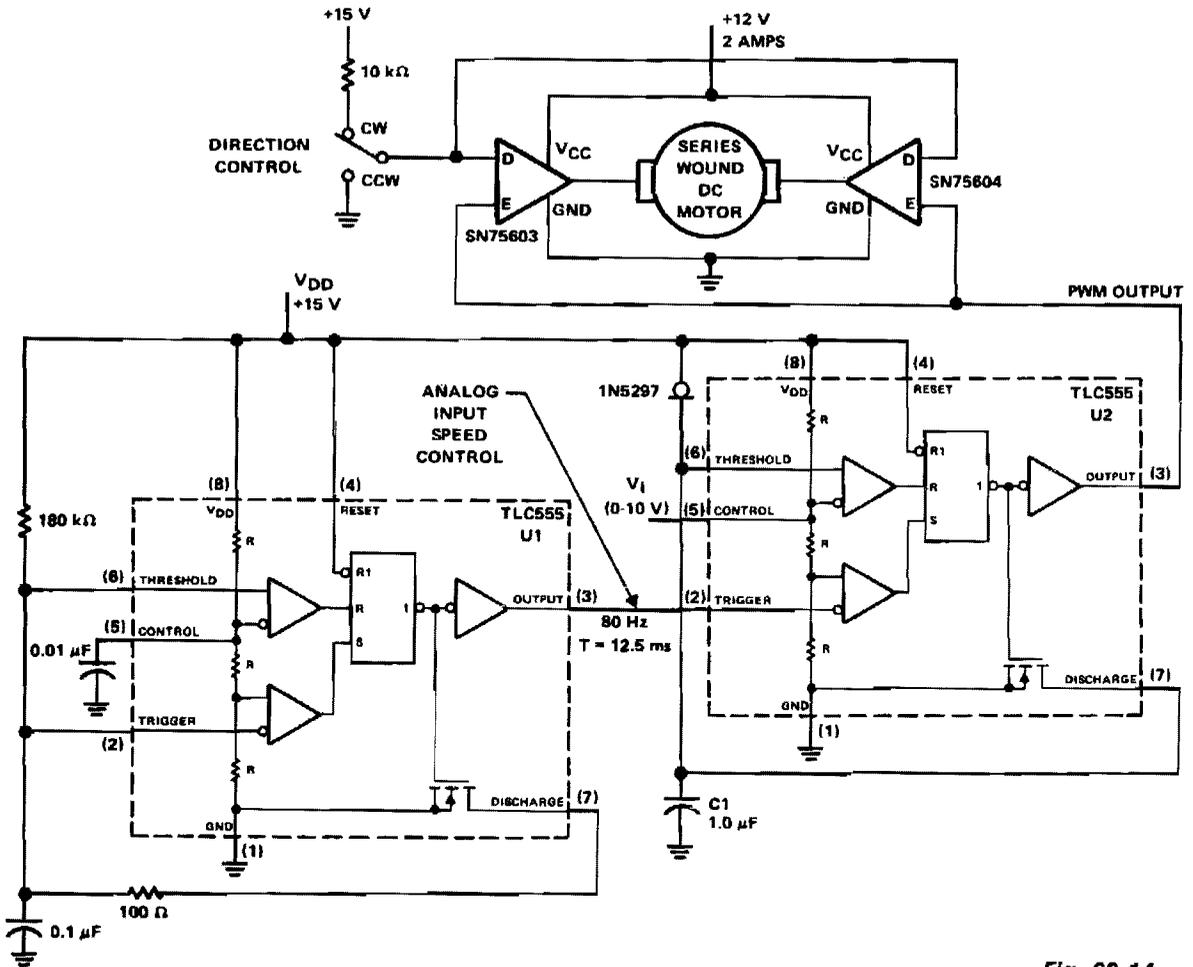


Fig. 62-14


Reprinted by permission of Texas Instruments.

The PWM controller uses complementary half-H peripheral drivers SN75603 and SN75604, with totem-pole outputs rated at 40 V and 2.0 A. These drivers effectively place the motor in a full-bridge configuration, which has the ability to provide bidirectional control.

Timer U1 operates in the astable mode at a frequency of 80 Hz. The 100-Ω discharge resistor results in an 8-μs trigger pulse which is coupled to the trigger input of timer U2. Timer U2 serves as the PWM generator. Capacitor C1 is charged linearly with a constant current of 1 mA from the 1N5297, which is an FET current-regulator diode.

Motor speed is controlled by feeding a dc voltage of 0 to 10 V to control input pin 5 of U2. As the control voltage increases, the width of the output pulse pin 3 also increases. These pulses control the on/off time of the two motor drivers. The trigger pulse width of timer U1 limits the minimum possible duty cycle from U2.

## STEPPING MOTOR DRIVE

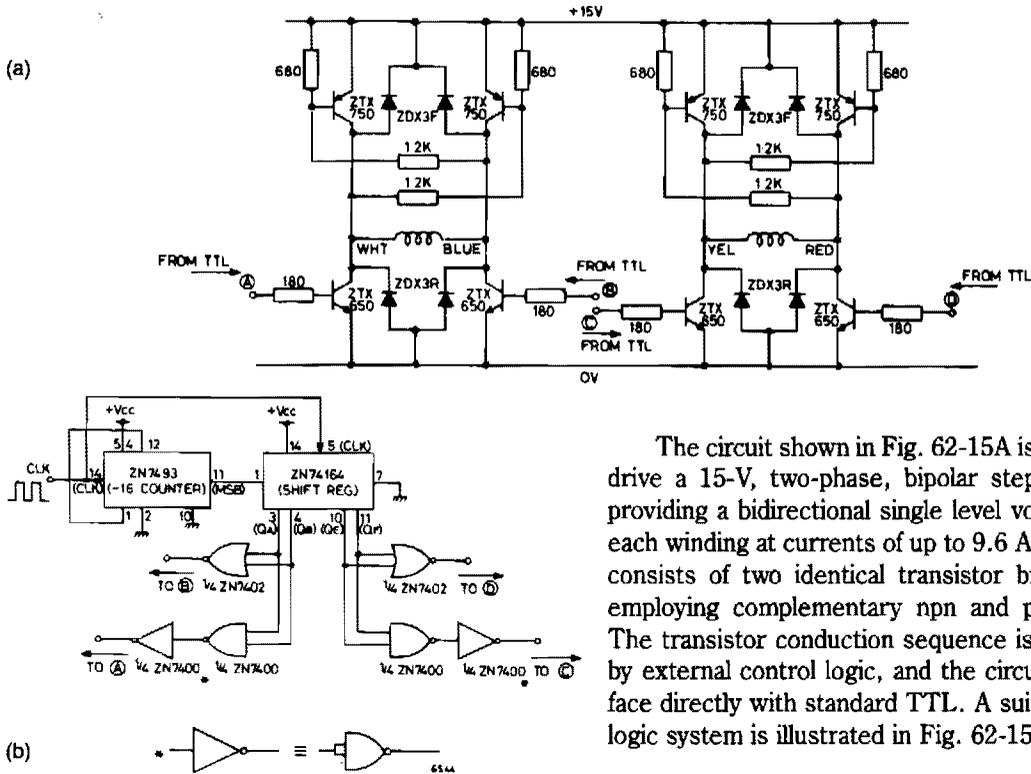


The circuit shown in Fig. 62-15A is designed to drive a 15-V, two-phase, bipolar stepping motor, providing a bidirectional single level voltage across each winding at currents of up to 9.6 A. The circuit consists of two identical transistor bridge stages employing complementary npn and pnp devices. The transistor conduction sequence is determined by external control logic, and the circuit will interface directly with standard TTL. A suitable control system is illustrated in Fig. 62-15B.

ZeTeX, formerly FERRANTI

Fig. 62-15
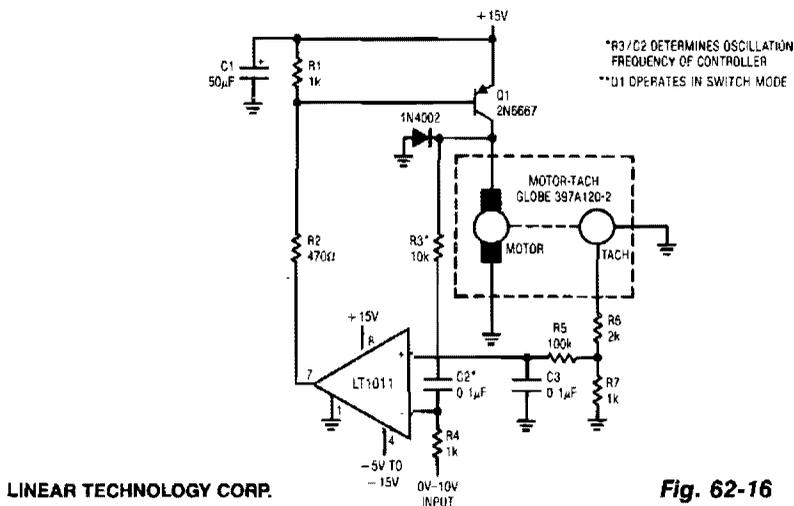
## HIGH-EFFICIENCY MOTOR-SPEED CONTROLLER



# 63

## Multiplexers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Two-Level Multiplexer

1-of-15 Cascaded Video MUX


Low-Cost Four-Channel Multiplexer  
Demultiplexer

One-of-Eight Channel Transmission  
System

Three-Channel Multiplexer with  
Sample-and-Hold

Analog Multiplexer with  
Buffered Input and Output

# TWO-LEVEL MULTIPLEXER

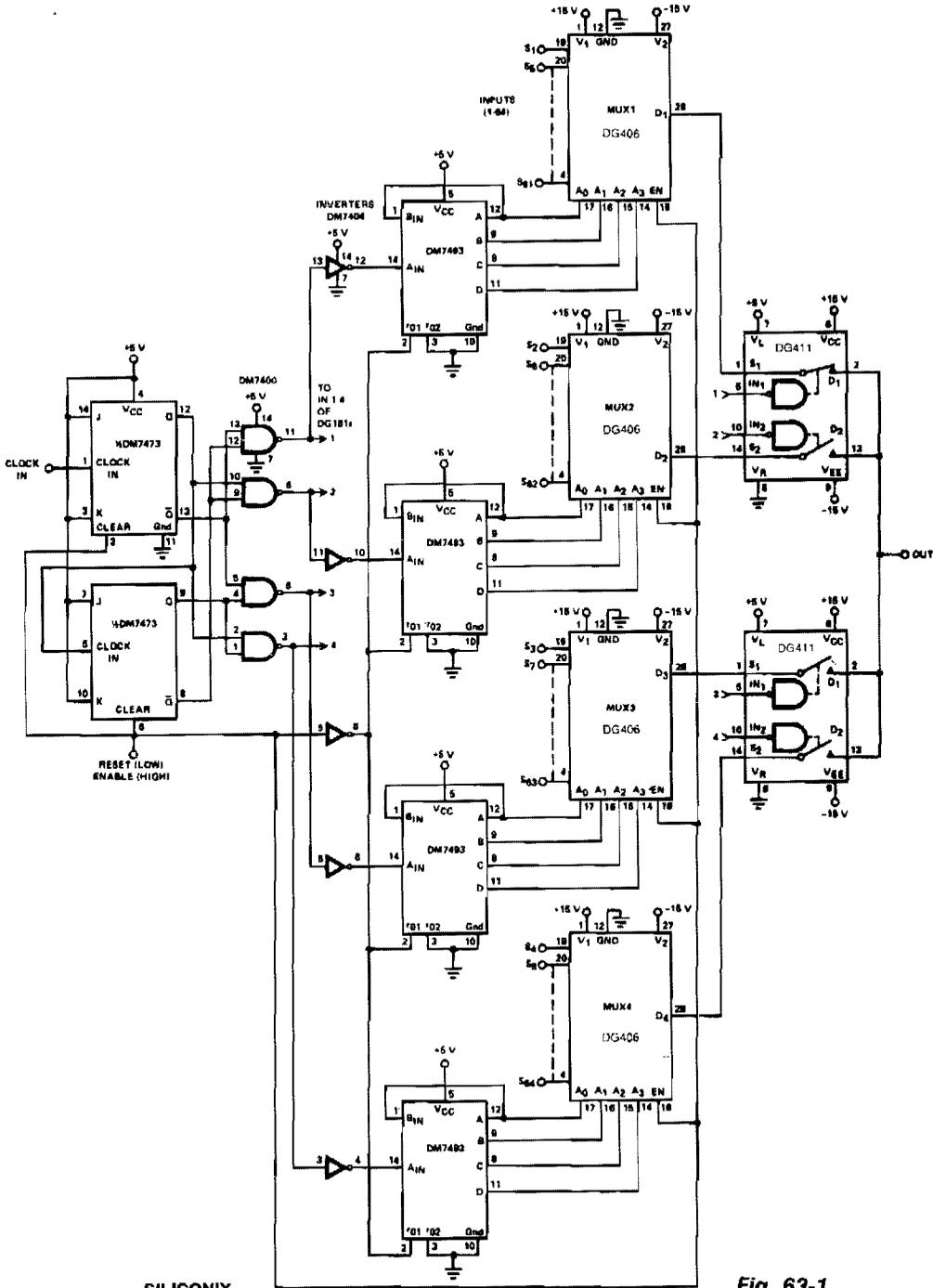


SILICONIX

Fig. 63-1

## TWO-LEVEL MULTIPLEXER (Cont.)

When a large number of channels are multiplexed, the outputs of two or more multiplexers can be connected together and each multiplexer sequentially enabled. In the inhibit mode, the multiplexer draws less power and its output and inputs act as open circuits. Theoretically, an infinite number of channels can be accommodated in this way; in practice, the accumulated output capacitance and leakage of many paralleled multiplexers limits the speed and accuracy of the system. A much better method is the two-level multiplex system. The two-level system has a bank of high-speed switches at the output which sequentially switch between the four DG406s. Each DG406 is able to switch during the time the other three are being interrogated. The DG406s contribute leakage and capacitance at the output only, when they are switched on by the DG411— $1/4$  of the time. The two-level multiplex system is very useful in communications links, high-speed interfacing with comparators, or wherever a large number of channels must be multiplexed at high speeds.

### 1-OF-15 CASCADED VIDEO MUX

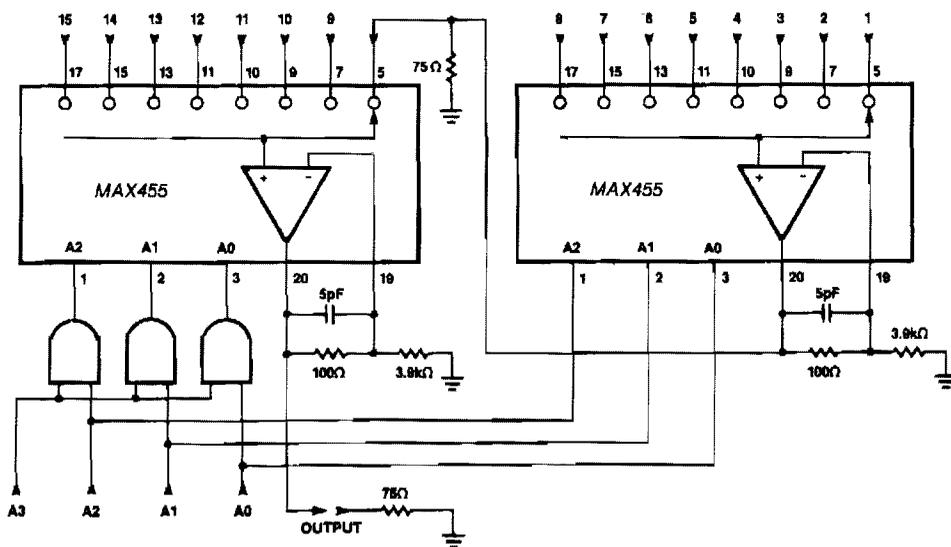


MAXIM

Fig. 63-2

Two MAX455s can be cascaded to form a 1 of 15 video MUX by connecting the output of one MUX to one of the input channels of a second MUX. Although the two devices are usually close to one another, the output of the first MUX should be terminated to preserve its bandwidth.


## LOW-COST FOUR-CHANNEL MULTIPLEXER

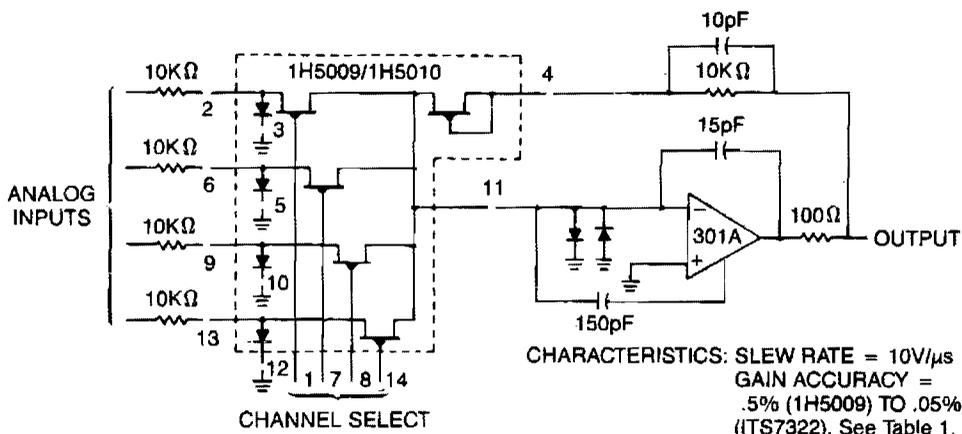

INTERSIL

Fig. 63-3

## DEMULTIPLEXER

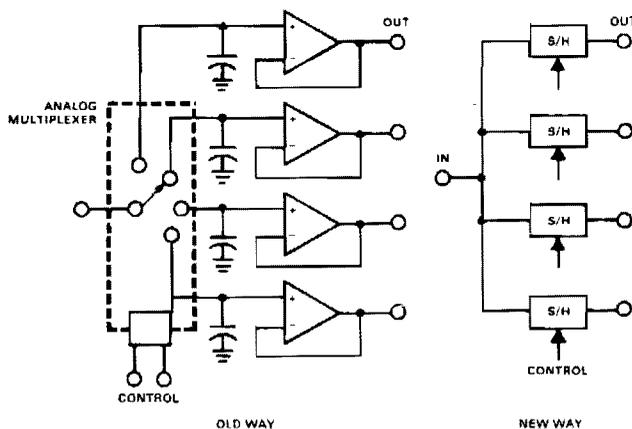


SILICONIX

Fig. 63-4

This circuit reconstructs and separates analog signals which have been time-division multiplexed. The conventional method, shown on the left, has several restrictions, particularly when a short dwell time and a long, accurate hold time is required. The capacitors must charge from a low-impedance source through the resistance and current-limiting characteristics of the multiplexer. When holding, the high-impedance lines are relatively long and subject to noise pickup and leakage. When FET input buffer amplifiers are used for low leakage applications, severe temperature offset errors are often introduced.



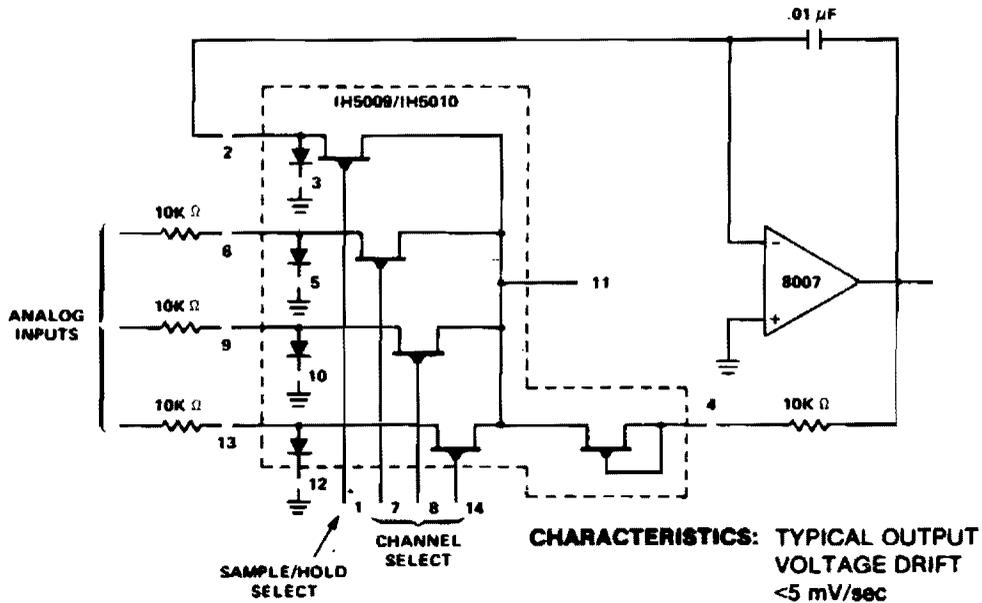
### THREE-CHANNEL MULTIPLEXER WITH SAMPLE-AND-HOLD



INTERSIL

Fig. 63-6
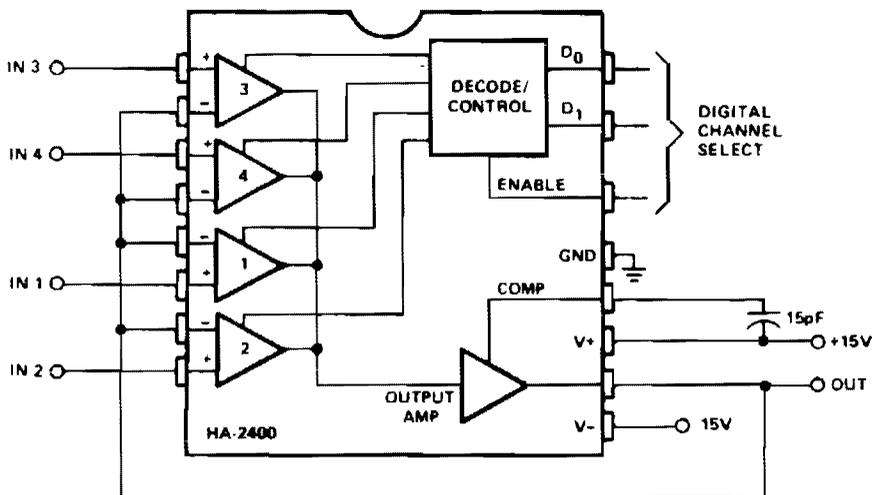
### ANALOG MULTIPLEXER WITH BUFFERED INPUT AND OUTPUT



HARRIS

Fig. 63-7

## **ANALOG MULTIPLEXER WITH BUFFERED INPUT AND OUTPUT (Cont.)**

This circuit is used for analog signal selection or time division multiplexing. As shown, the feedback signal places the selected amplifier channel in a voltage follower (noninverting unity gain) configuration, and provides very high input impedance and low output impedance. The single package replaces four input buffer amplifiers, four analog switches with decoding, and one output buffer amplifier. For low-level input signals, gain can be added to one or more channels by connecting the (-) inputs to a voltage divider between output and ground. The bandwidth is approximately 8 MHz, and the output will slew from one level to another at about 15.0 V per  $\mu$ s.

Expansion to multiplex 5 to 12 channels can be accomplished by connecting the compensation pins of two or three devices together, and using the output of only one of the devices. The enable input on the unselected devices must be low.

Expansion to 16 or more channels is accomplished easily by connecting outputs of four 4-channel multiplexers to the inputs of another 4-channel multiplexer. Differential signals can be handled by two identical multiplexers addressed in parallel. Inverting amplifier configurations can also be used, but the feedback resistors might cause crosstalk from the output to unselected inputs.

---

# 64


## Noise Reduction Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Dolby B/C Noise Reduction System  
Dolby B Noise Reduction Circuit in Encode Mode  
Dolby B Noise Reduction Circuit in Decode Code

## DOLBY B/C NOISE REDUCTION SYSTEM

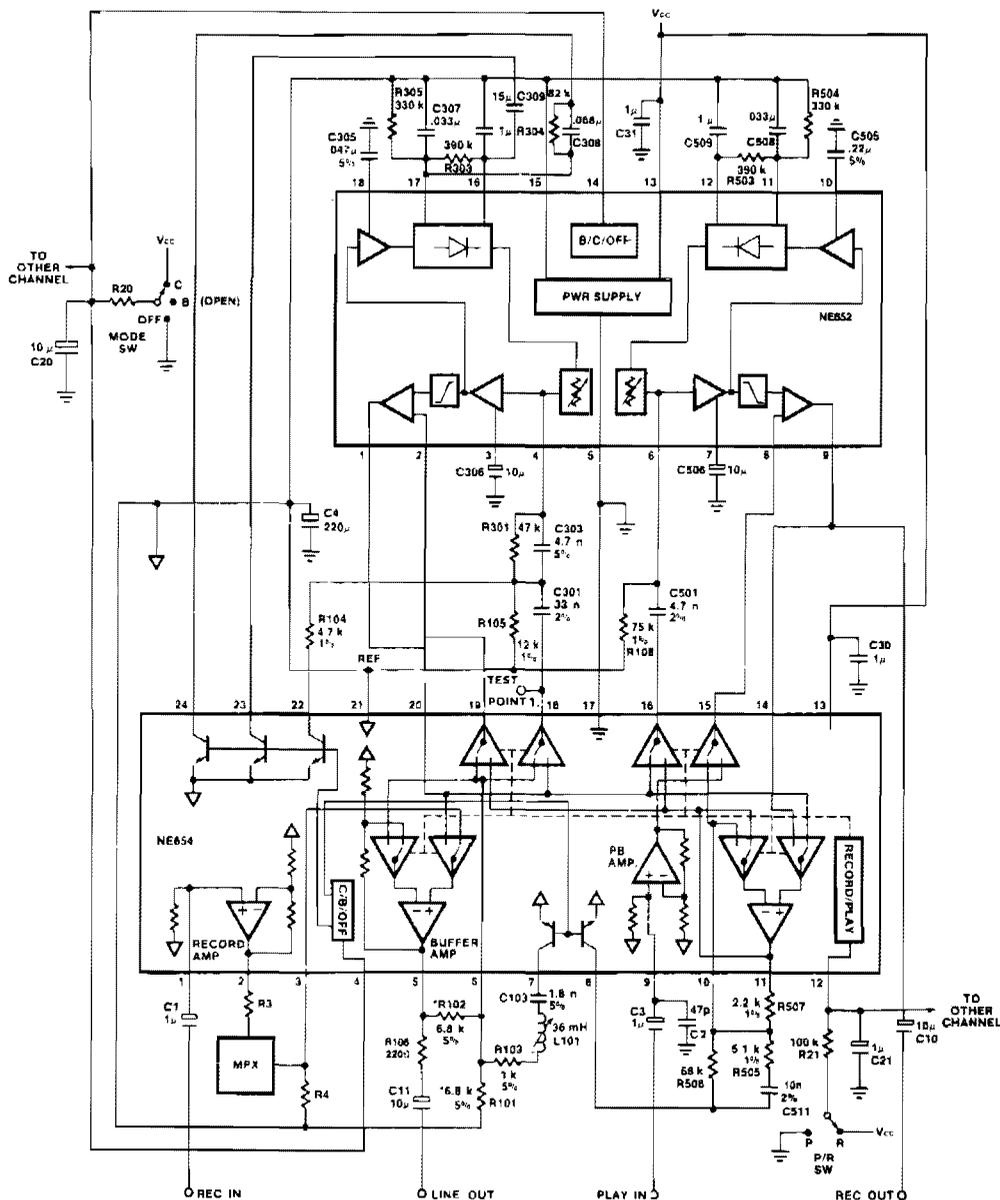


**NOTES:**

1. \*Line output programming resistors
2. Split supply operation and coupling capacitors are optional
3. Time constant for mode switch is optional.
4. Applications info is for reference only. Final design configuration/values are found in relevant Dolby Labs Bulletins and Licensee manuals
5. R20 value is equal to 6.8KΩ divided by "N" where "N" equals the number of switched channels
6. R106 is recommended for large capacitive loads on line out
7. Switches shown in REC position

**SIGNETICS**

**Fig. 64-1**

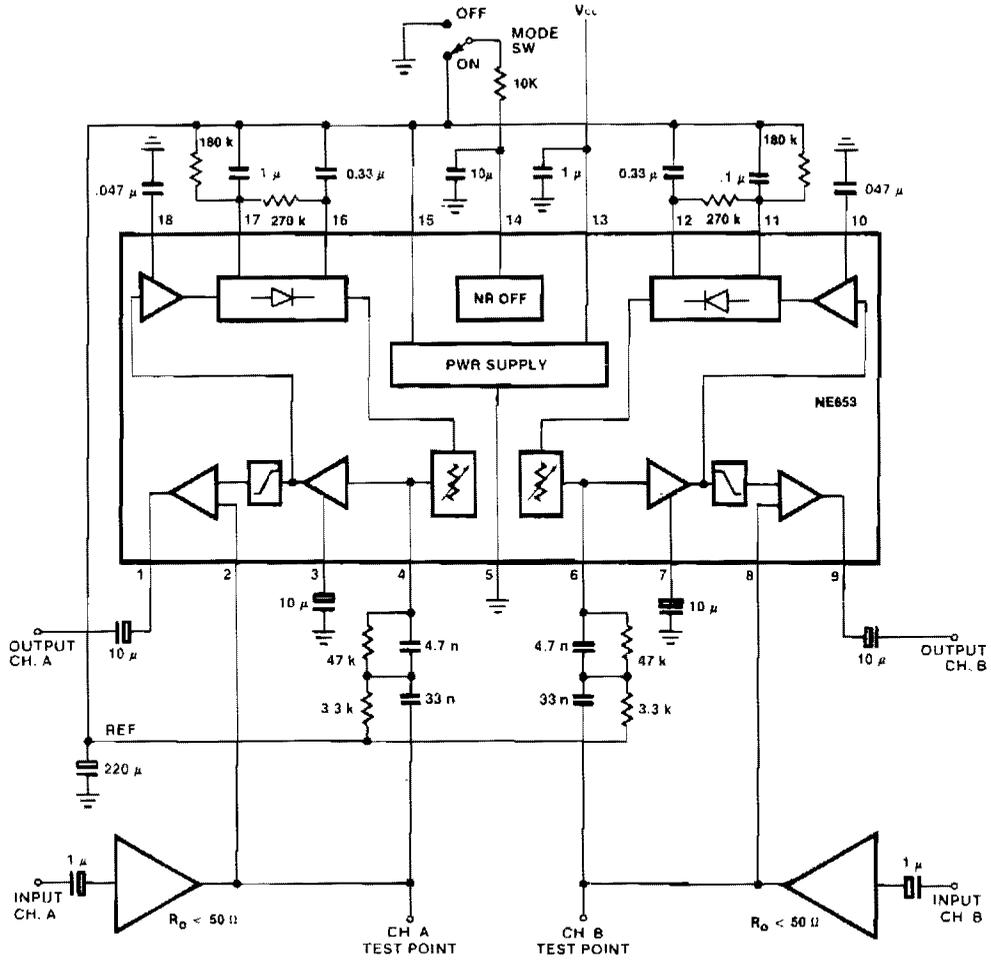
## DOLBY B NOISE REDUCTION CIRCUIT IN ENCODE MODE



SIGNETICS

Fig. 64-2
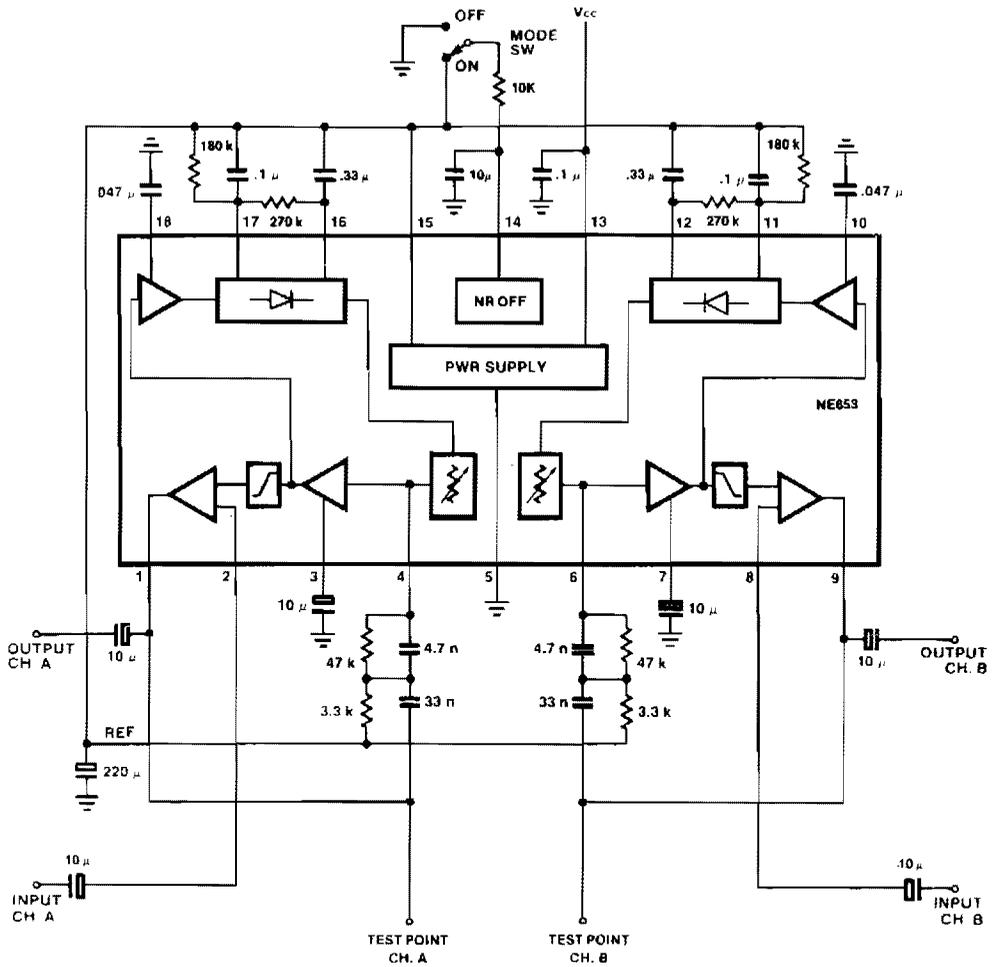
## DOLBY B NOISE REDUCTION CIRCUIT IN DECODE MODE



SIGNETICS

Fig. 64-3

# 65


## Notch Filters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Twin-T Notch Filter  
High- $Q$  Notch Filter

## TWIN-T NOTCH FILTER

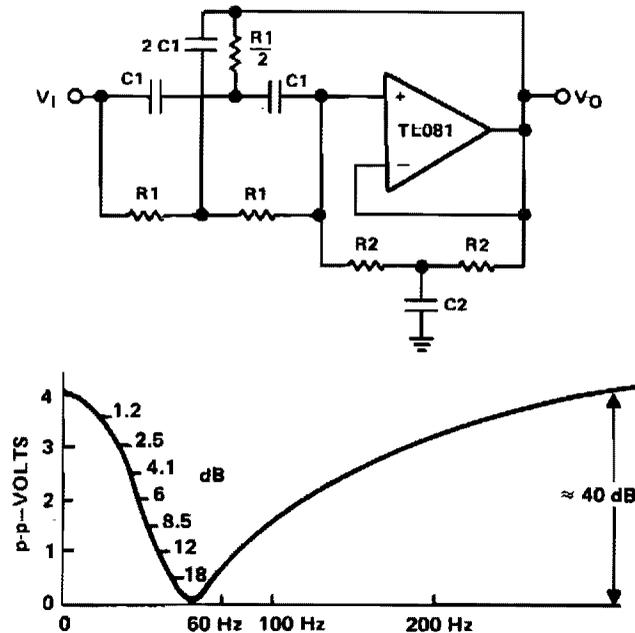

60-Hz Twin-T Notch Filter Response

Fig. 65-1

Reprinted by permission of Texas Instruments.

This filter is used to reject or block a frequency or band of frequencies. These filters are often designed into audio and instrumentation systems to eliminate a single frequency, such as 60 Hz. Commercial grade components with 5% - 10% tolerance produce a null depth of at least 30 to 40 dB. When a twin-T network is combined with a TL081 op amp in a circuit, an active filter can be implemented. The added resistor capacitor network, R2 and C2, work effectively in parallel with the original twin-T network, on the input of the filter. These networks set the  $Q$  of the filter. The op amp is basically connected as a unity-gain voltage follower. The  $Q$  is found from:



$$Q = \frac{R_2}{2R_1} = \frac{C_1}{C_2}$$

For a 60-Hz notch filter with a  $Q$  of 5, it is usually best to pick the C1 capacitor value and calculate the resistor R1. Let C1 = 0.22  $\mu$ F. Then:

$$\begin{aligned} R_1 &= 12 \text{ K}\Omega \\ R_2 &= 120 \text{ K}\Omega \\ C_2 &= 0.047 \text{ }\mu\text{F} \end{aligned}$$

Standard 5% resistors and 10% capacitors produce a notch depth of about 40 dB, as shown in the frequency response curve.

## HIGH-Q NOTCH FILTER

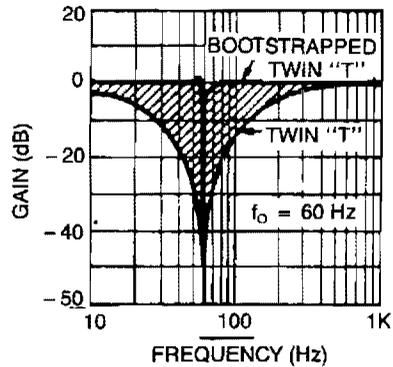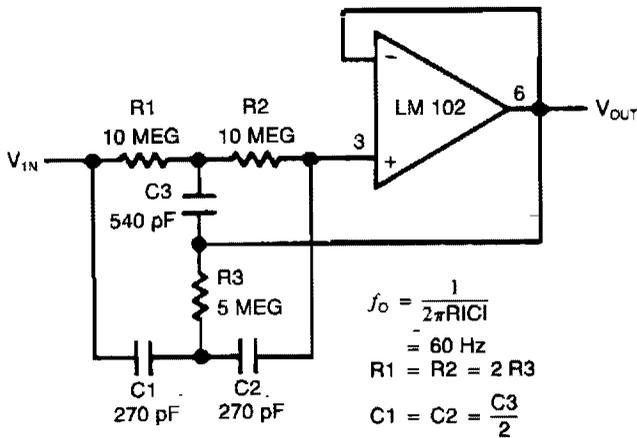

Response of High and Low Q Notch Filter

NATIONAL SEMICONDUCTOR CORP.

**Fig. 65-2**

This circuit shows a twin-T network connected to an LM102 to form a high-Q, 60-Hz notch filter. The junction of R3 and C3 which is normally connected to ground, is bootstrapped to the output of the follower. Because the output of the follower is a very low impedance, neither the depth nor the frequency of the notch change; however, the *Q* is raised in proportion to the amount of signal fed back to R3 and C3. Shown is the response of a normal twin-T and the response with the follower added.

**66**



# **Operational Amplifiers**

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Operational Amplifiers

## OPERATIONAL AMPLIFIERS

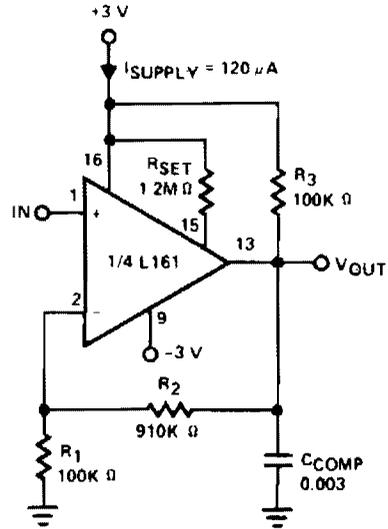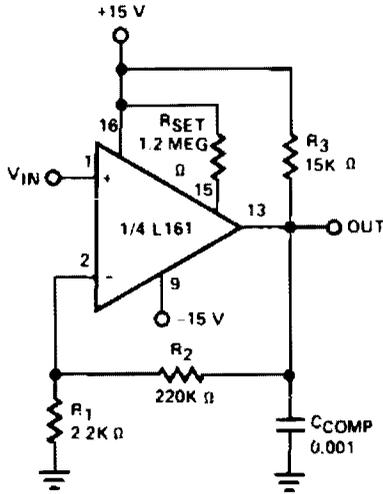


The L161 as a X100 Operational Amplifier

(A)

A Micropower X10 Op Amp

(B)

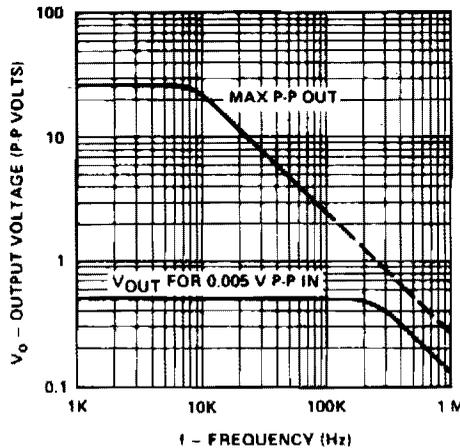

**Frequency Response and Maximum Output  
for the X100 Op Amp**

SILICONIX

Fig. 66-1

This is a single gain-of-100 amplifier with a gain-bandwidth product of 20 MHz! The primary limitation in the performance is the low slew rate ( $0.3 \text{ V}/\mu\text{s}$ ) imposed by  $I_{OH}$  charging  $C_{COMP}$ . The effects of slew rate and compensation are shown. A lower gain amplifier requires a larger  $C_{COMP}$ , which in turn further reduces slew rate. For this reason, it might actually be advantageous in certain areas to lower the gain by placing a resistive divider at the input rather than raising  $R_f$ . Figure 66-1B shows a  $700\text{-}\mu\text{W}$ , X10 op amp whose slew rate is  $0.02 \text{ V}/\mu\text{s}$  and is 3 dB down at 100 kHz.

# 67


## Optically-Coupled Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

High-Voltage Ac Switcher	Optical CMOS Coupler
Solid-State Zero-Voltage Switchers (ZVS)	Line-Current Detector
Triggering SCR Series	Line-Operated Power Outage Light
Normally Closed Half-Wave ZVS Contact Circuit	Optical TTL Coupler
Normally Open and Normally Closed Dc Solid-State Relays	Zero-Voltage Switching, Solid-State Relay with Antiparallel SCR Output
Indicator Lamp Driver	Dc Latching Relay
Ambient-Light-Ignoring Optical Sensor	Ac Relay
	Photodiode Source Follower


## HIGH-VOLTAGE AC SWITCHER

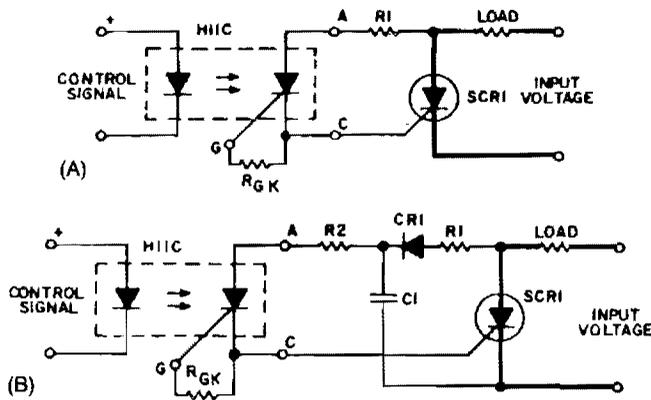

A basic circuit to trigger an SCR is shown in Fig. 67-1A. This circuit has the disadvantage that the blocking voltage of the photon-coupler output device determines the circuit-blocking voltage, irrespective of higher main SCR capability.

Adding capacitor C1 to the circuit, as shown in Fig. 67-1B, will reduce the  $dV/dt$  seen by the photon-coupler output device. The energy stored in C1, when discharged into the gate of SCR1, will improve the  $di/dt$  capability of the main SCR.

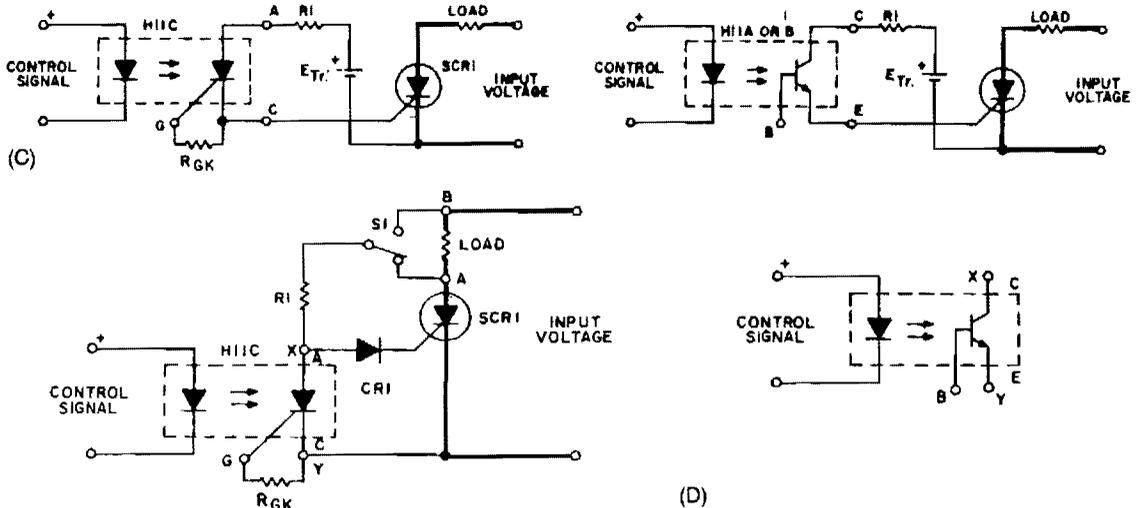Using a separate power supply for the coupler adds flexibility to the trigger circuit; it removes the limitation of the blocking power voltage capability of the photon-coupler output device. The flexibility adds cost and more than one power supply might be necessary for multiple SCRs if no common reference points are available.




Photon Coupler With SCR – Output

Photon Coupler With Transistor Output  
(connect in place of SCR coupler)

## HIGH-VOLTAGE AC SWITCHER (Cont.)

In Fig. 67-1C, R1 can be connected to Point A, which will remove the voltage from the coupler after SCR1 is triggered, or to Point B so that the coupler output will always be biased by input voltage. The former is preferred since it decreases the power dissipation in R1. A more practical form of SCR triggering is shown in Fig. 67-1F. Trigger energy is obtained from the anode supply and stored in C1. Coupler voltage is limited by the zener voltage. This approach permits switching of higher voltages than the blocking voltage capability of the output device of the photon coupler. To reduce the power losses in R1 and to obtain shorter time constants for charging C1, the zener diode is used instead of a resistor.

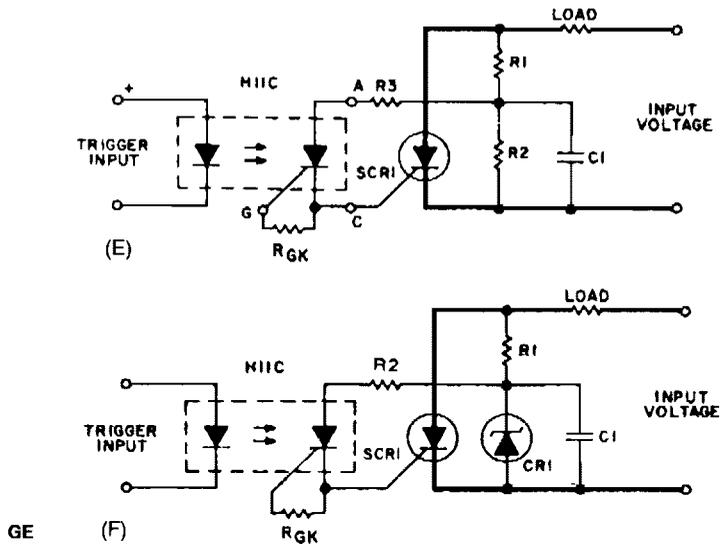

**Fig. 67-1**


A guide for selecting the component values would consist of the following steps:

- Choose C1 in a range of 0.05 to 1  $\mu$ F. The maximum value might be limited by the recharging time constant  $(R_L + R_1) C_1$  while the minimum value will be set by the minimum pulse width required to ensure SCR latching.
- R2 is determined from peak gate current limits, if applicable, and minimum pulse width requirements.
- Select a zener diode. A 25-V zener is a practical value, since this will meet the usual gate requirement of 20 V and 20  $\Omega$ . This diode will also eliminate spurious triggering because of voltage transients.
- Photon coupler triggering is ideal for the SCR's driving inductive loads. By ensuring that the LASCR latches on, it can supply gate current to SCR1 until it stays on.
- Component values for dc voltage are easily computed from the following formulae:

$$R_1 = \frac{E_{IN} - V_Z}{I_G}$$

where:  $V$  = zener voltage  
 $P_{(R1)} = I_G \cdot (E_{IN} - V_Z)$   
 $P_{(ZENER)} = I_G \cdot V_Z$
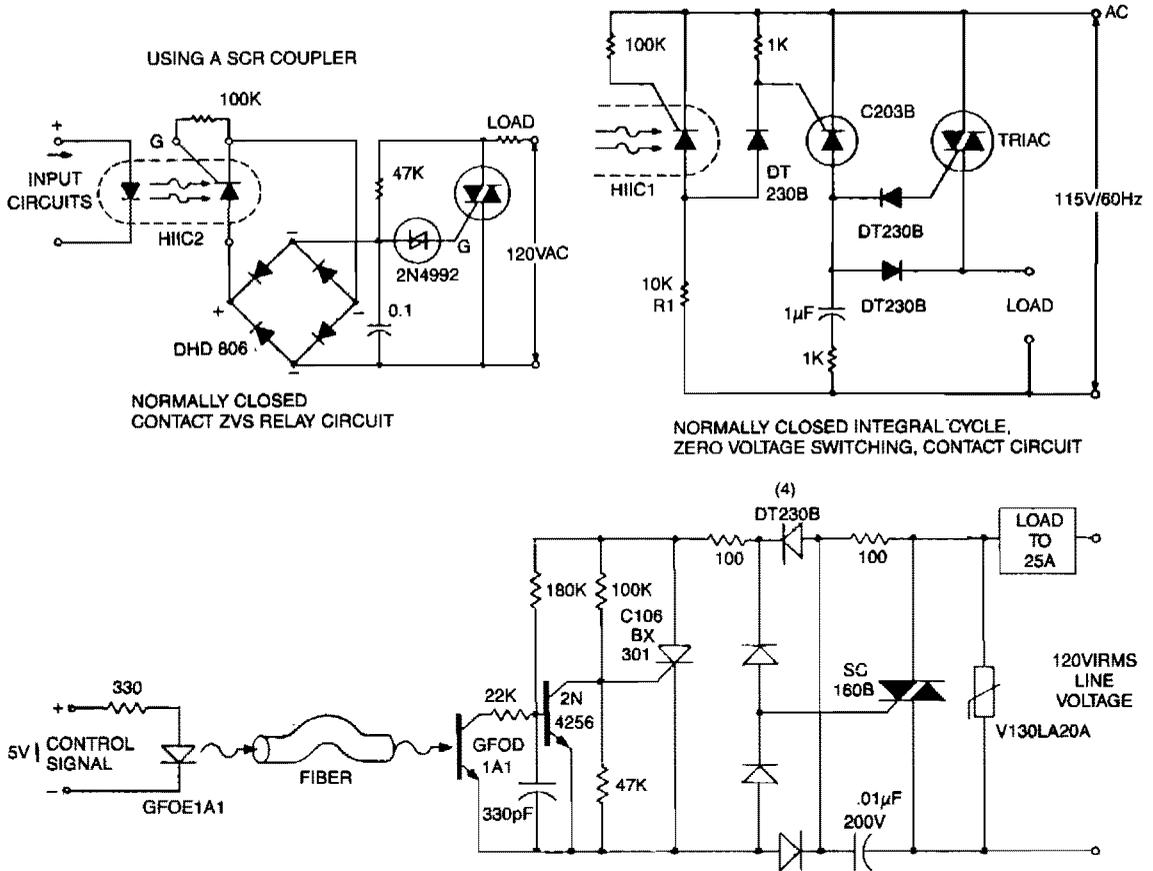
## SOLID-STATE ZERO-VOLTAGE SWITCHING (ZVS) CIRCUITS



GE



25A FIBER OPTIC ZVS AC SOLID STATE RELAY

Fig. 67-2

This circuit is effective for lamp and heater loads. Some circuits driving reactive loads require integral cycling and zero-voltage switching—when an identical number of positive and negative half cycles of voltage are applied to the load during a power period. The circuit, although not strictly a relay because of the three-terminal power connection, performs the integral cycle ZVS function when interfaced with the previous coil circuits.

Fiber optics offers advantages in power control systems. Electrical signals do not flow along the non-conducting fiber, minimizing shock hazard to both operator and equipment. EMI/RFI pick up on the fiber is nonexistent—although high gain receiver circuits might require shielding, eliminating noise pick-up errors caused by sources along the cable route. Both ac and dc power systems can be controlled by fiber optics using techniques similar to the optoisolator solid-state relay. Triac triggering is accomplished through the C106BX301, a low gate trigger current SCR, switching line voltage derived current to the triac gate via the full-wave rectifier bridge. The primary difference between fiber optics solid-state relay circuits and optoisolator circuits is the gain; photo currents are much smaller.

## TRIGGERING SCR SERIES

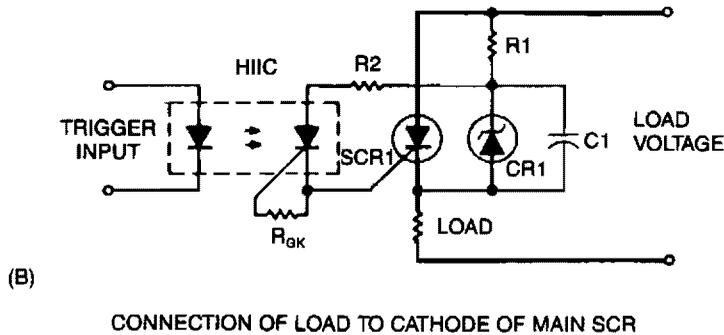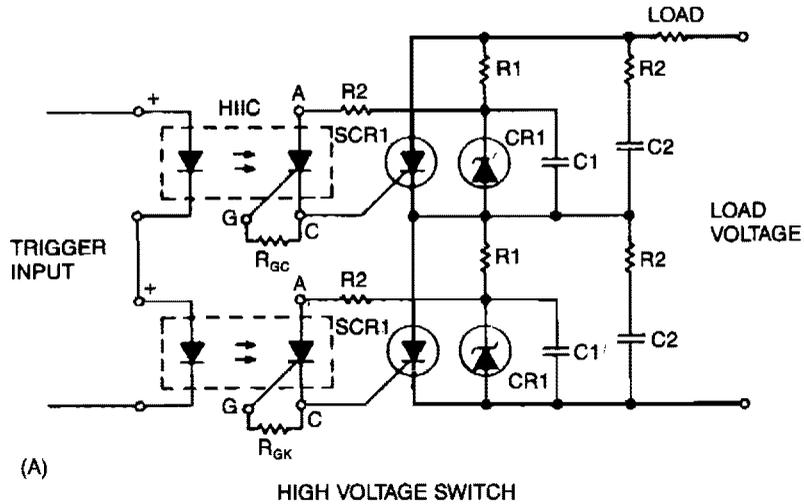

GE

**Fig. 67-3**

Snubber circuit R2C2, as shown, might be necessary since R1 and C1 are tailored for optimized triggering and not for  $dV/dt$  protection. Fiber-optic pairs can be used with discrete SCRs to switch thousands of volts. A photon coupler with a transistor output will limit the trigger-pulse amplitude and rise time because of CTR and saturation effects. Using the H11C1, the rise time of the input pulse to the photon coupler is not critical, and its amplitude is limited only by the H11C1 turn-on sensitivity. The load can also be connected to the cathode as illustrated in Fig. 67-3B.

## NORMALLY CLOSED HALF-WAVE ZVS CONTACT CIRCUIT

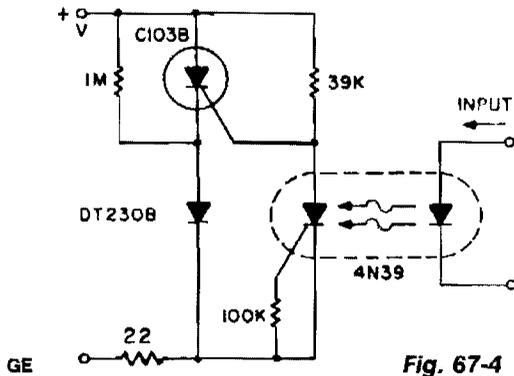


Fig. 67-4

A normally closed contact circuit that provides zero-voltage switching is designed around the 4N39 SCR optocoupler. The circuit illustrates the method of modifying the normally open contact circuit by using the photo SCR to hold off the trigger SCR.

## NORMALLY OPEN AND NORMALLY CLOSED DC SOLID-STATE RELAYS


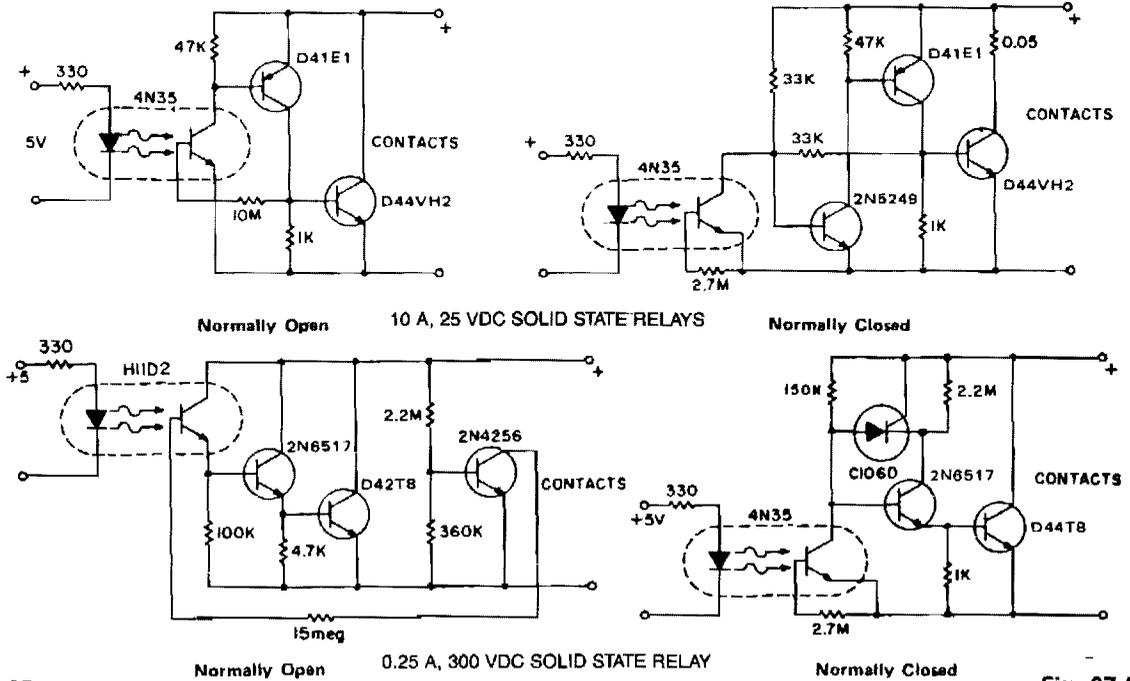


Fig. 67-5

The phototransistor and photodarlington couplers act as dc relays in saturated switching at currents up to 5 mA and 50 mA, respectively. When higher currents or higher voltage capabilities are required, additional devices are required to buffer or amplify the photocoupler output. The addition of hysteresis to provide fast switching and stable pick-up and drop-out points can be easily implemented simultaneously. These circuits provide several approaches to implement the dc relay function and serve as practical, cost-effective examples.


## INDICATOR LAMP DRIVER

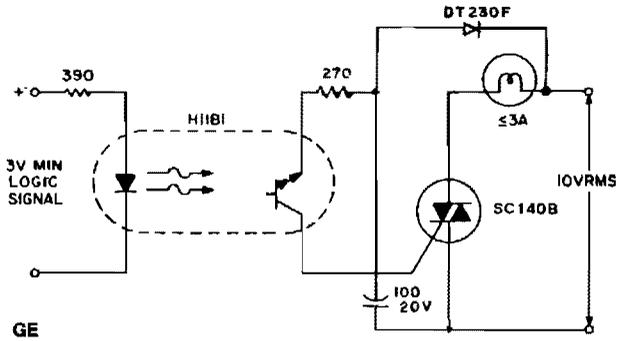

**Fig. 67-6**

A simple solid-state relay circuit drives the 10-Vac telephone indicator lamps from logic circuitry, while maintaining complete isolation between the 10-V line and the logic circuit.

## AMBIENT-LIGHT-IGNORING OPTICAL SENSOR

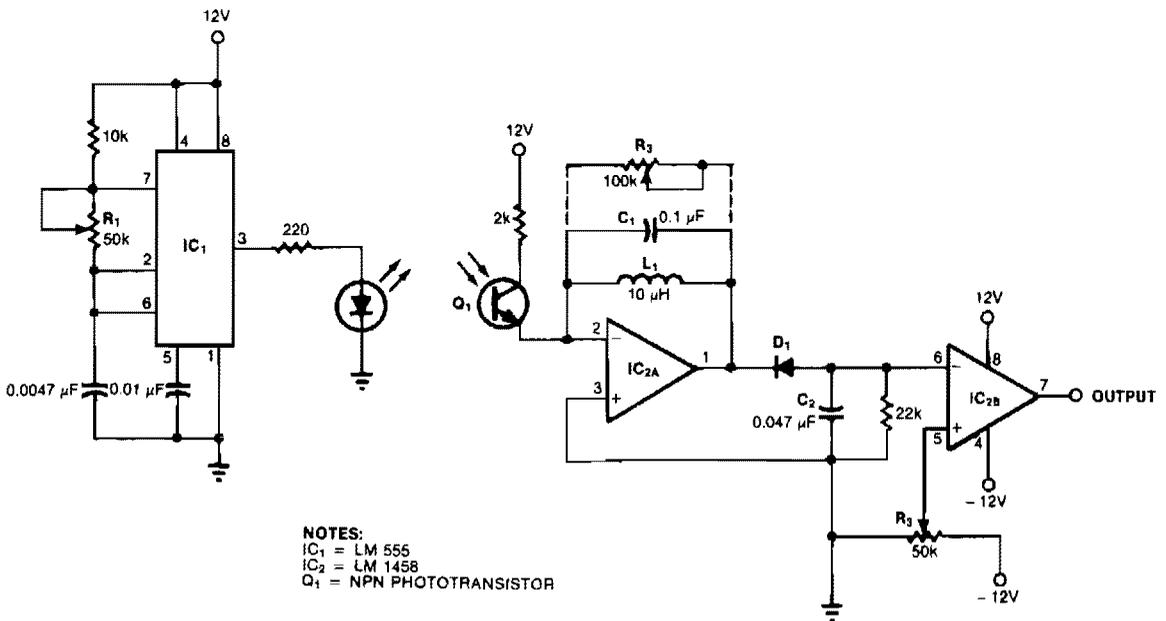


EDN

**Fig. 67-7**

A resonance-tuned narrow-band amplifier reduces this optical object detector's sensitivity to stray light. C1 and L1 in IC2A's feedback loop cause the op amp to pass only those frequencies at or near the LED's 5-kHz modulation rate. IC2B's output increases when the received signal is sufficient to drop the negative voltage across C2 below the reference set by R2.

## OPTICAL CMOS COUPLER

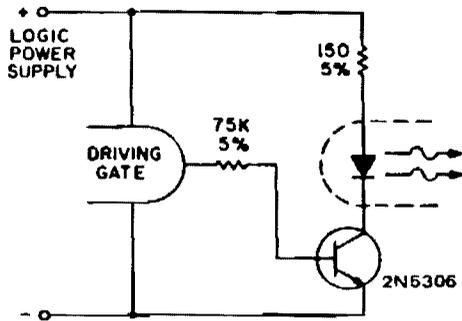


GE

Fig. 67-8

Since standard CMOS logic operates down to 3-V supply voltages and is specified as low as  $30\ \mu\text{A}$  maximum current sinking/sourcing capability, it is necessary to use a buffer transistor to provide the


required current to the IRED if CMOS is to drive the optocoupler. As in the case of the low output TTL families, the H74A output can drive a multiplicity of CMOS gate inputs or a standard TTL input given the proper bias of the IRED. A one-logic stage drives the IRED on. This circuit will provide worst-case drive criteria to the IRED for logic supply voltages from 3 to 10 V, although lower power dissipation can be obtained by using higher value resistors for high supply voltages. If this is desired, the worst-case drive must be supplied to the IRED with minimum supply voltage, minimum temperature and maximum resistor tolerances, gate saturation resistance, and transistor saturation voltages applied. For the H74 devices, minimum IRED current at worst-case conditions, zero logic state output of the driving gate, is 6.5 mA and the H11L1 is 1.6 mA.

## LINE-CURRENT DETECTOR

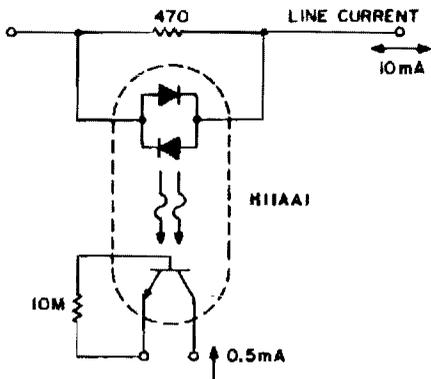

POLARITY INSENSITIVE LINE CURRENT DETECTOR

GE

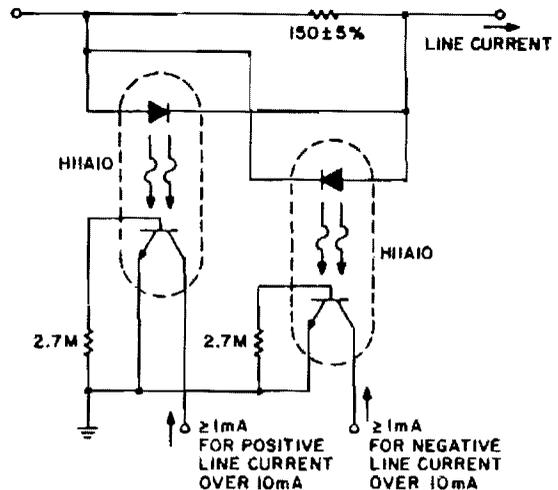


POLARITY INDICATING LINE CURRENT DETECTOR

Fig. 67-9

## LINE-CURRENT DETECTOR (Cont.)

Detection of line-current flow and indicating the flow to an electrically remote point is required in line status monitoring at a variety of points in the telephone system and auxiliary systems. The line should be minimally unbalanced or loaded by the monitor circuit, and relatively high levels of 60-Hz induced voltages must be ignored. The H11AA1 allows line currents of either polarity to be sensed without discrimination and will ignore noise up to approximately 2.5 mA. In applications where greater noise immunity or polarity-sensitive line-current detection is required, the H11A10 threshold coupler can be used. This phototransistor coupler is specified to provide a minimum 10% current transfer ratio at a defined input current, while leaking less than 50  $\mu\text{A}$  at half that input current over the full  $-55^\circ\text{C}$  to  $+100^\circ\text{C}$  temperature range. The input current range, at which the coupler is on, is programmable by a single resistor from 5 to 10 mA.

## LINE-OPERATED POWER OUTAGE LIGHT

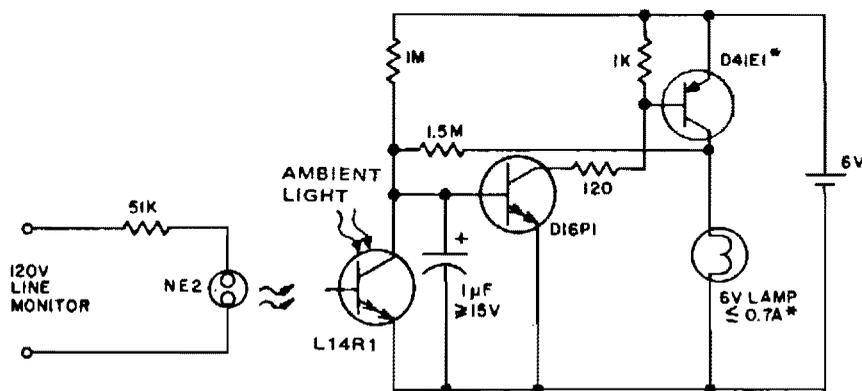


GE


Fig. 67-10

This circuit provides emergency lighting during a power outage. The phototransistor should be positioned to maximize coupling of both neon light and ambient light into the pellet, without allowing self-illumination from the 6-V lamp. Many circuits of this type also use line voltage to charge the battery.

## OPTICAL TTL COUPLER

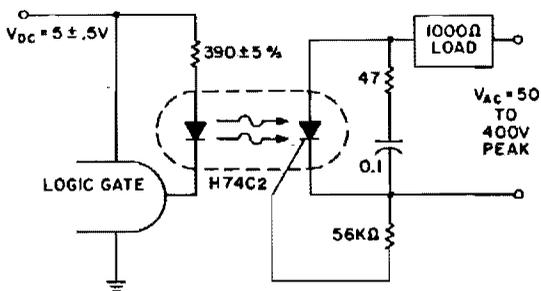

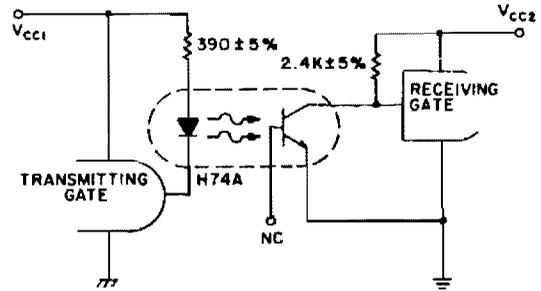LOGIC TO POWER COUPLING H74C2 BIAS CIRCUIT



LOGIC TO LOGIC COUPLERS H74A1 BIAS CIRCUIT

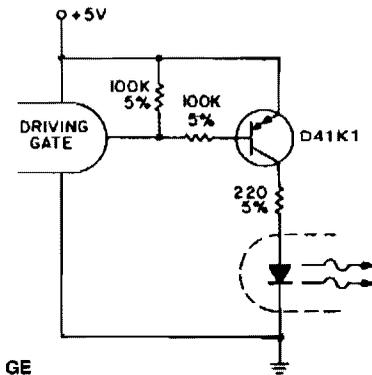


Fig. 67-11

IRED DRIVE FROM LOW POWER, MSI AND LSI TTL

For higher speed applications, up to 1-MHz NRZ, the Schmitt-trigger output H11L series optoisolator provides many features. The 1.6-mA drive current allows fan-in circuitry to drive the IRED, while the 5-V, 270-Ω sink capability and 100-ns transition times of the output add to the logic coupling flexibility.

## ZERO-VOLTAGE SWITCHING, SOLID-STATE RELAY WITH ANTIPARALLEL SCR OUTPUT


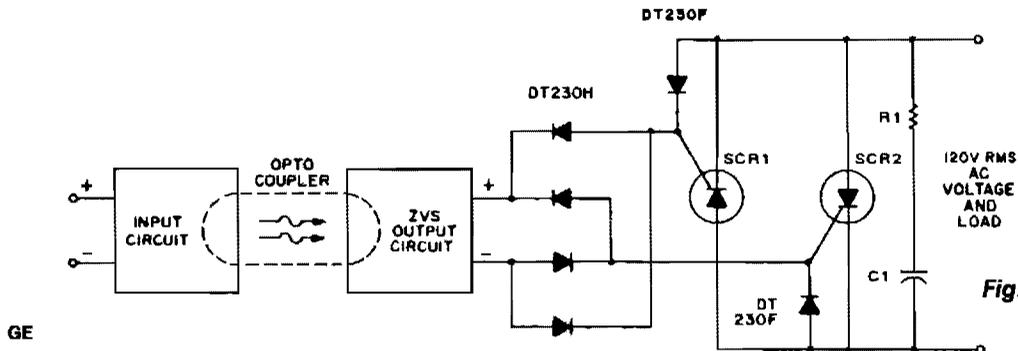


Fig. 67-12

A higher line voltage can be used if the diode, varistor, ZVS, and power thyristor settings are at compatible levels. For applications beyond triac current ratings, antiparallel SCRs might be triggered by the ZVS network.

## DC LATCHING RELAY

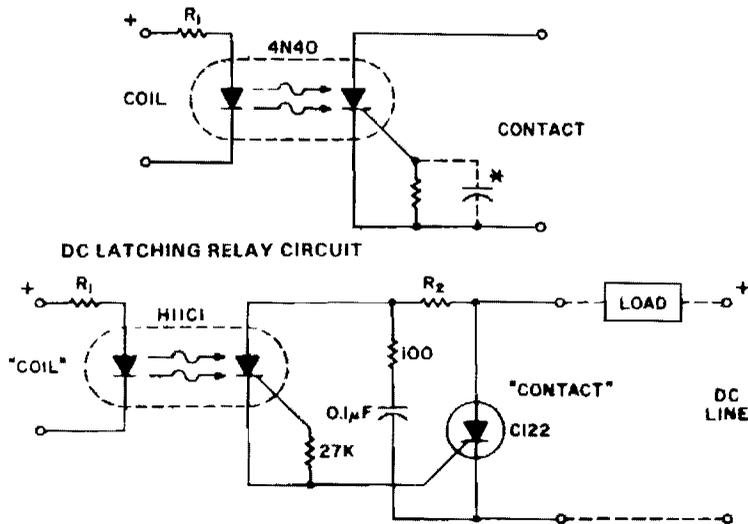

<b>COIL VOLTAGE</b>	6	12	24	48	120	V
<b>R1 VALUE</b>	470	1.1K	2.4K	4.7K	12K	Ω

<b>LINE VOLTAGE</b>	12	24	48	120	V
<b>C122 PART</b>	U	F	A	B	D
<b>R2 VALUE</b>	200	470	1K	2.2K	Ω

**NO HEAT SINK RATINGS AT  $T_A \leq 50^\circ$**

<b>I CONTACT, MAX.</b>	<b>PULSE WIDTH</b>	<b>DUTY CYCLE</b>
0.67 A	D.C.	100%
4.0 A	160 msec.	12%
8.0 A	160 msec.	3%
12 A	160 msec.	1%
15 A	160 msec.	0.3%


FOR HEAT SINK RATINGS  
SEE C122 SPECIFICATION  
SHEET NUMBER 150.35 AND  
APPLICATION NOTE NUMBER  
200.55

GE

**Fig. 67-13**

The H11C supplies the dc latching relay function and reverse polarity blocking, for currents up to 300 mA, depending on ambient temperature. For dc use, the gate cathode resistor can be supplemented by a capacitor to minimize transient and  $dV/dt$  sensitivity. For pulsating dc operation, the capacitor value must be designated to either retrigger the SCR at the application of the next pulse or prevent retriggering at the next power pulse. If not, random or undesired operation might occur. For higher current contacts, the H11C can be used to trigger an SCR capable of handling the current, as illustrated.

## AC RELAY

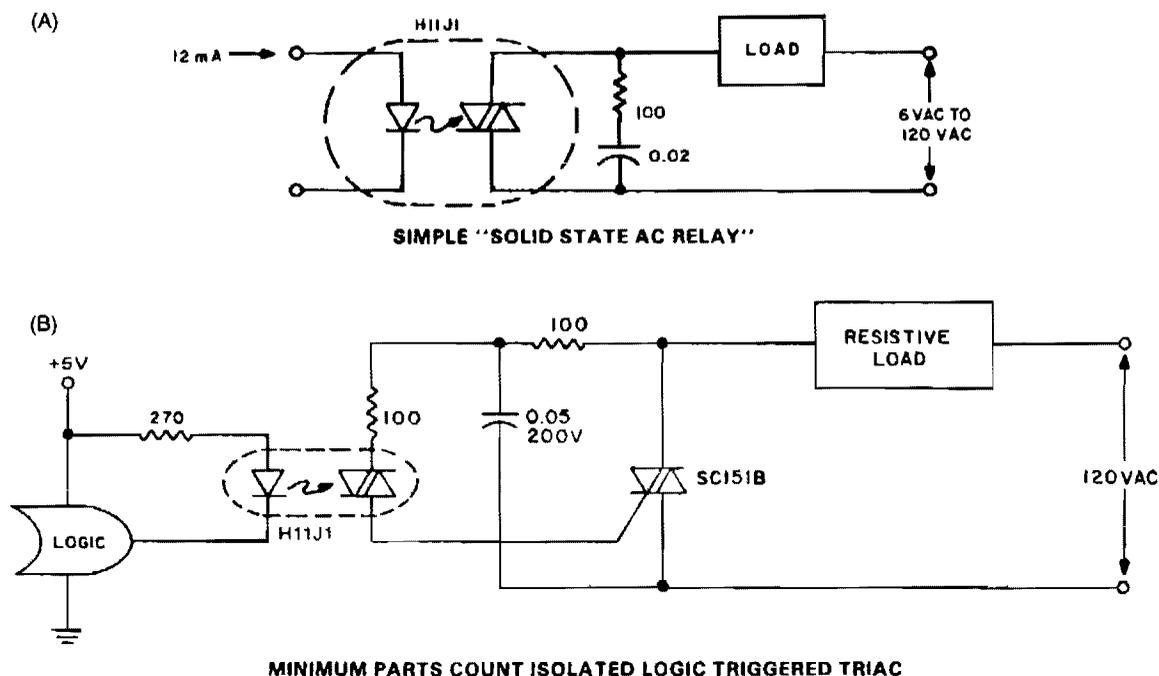

GE


**Fig. 67-14**

When zero voltage switching is not required, methods of providing this function are illustrated. The lowest parts count version of a solid-state relay is an optoisolator, the triac driver H11J. Unfortunately, the ability of the H11J to drive a load on a 60-Hz line is severely limited by its power dissipation and the dynamic characteristics of the detector. These factors limit applications to 30–50 mA resistive loads on 120 Vac, and slightly higher values at lower voltages. These values are compatible with neon-lamp drive, pilot, and indicator incandescent bulbs; low voltage control circuits, such as furnace and bell circuits, if  $dV/dt$  are sufficient; but less than benign loads require a discrete triac.

The H11J1 triac trigger optocoupler potentially allows a simple power switching circuit utilizing only the triac, a resistor, and the optocoupler. This configuration will be sensitive to high values of  $dV/dt$  and noise on normal power-line voltages, leading to the need for the configuration shown in Fig. 67-14B, where the triac snubber acts as a filter for line voltage to the optocoupler.

Since the snubber is not usually used for resistive loads, the cost effectiveness of the circuit is compromised somewhat. Even with this disadvantage, the labor, board space, and inventory of parts savings of this circuit prove it cost-optimized for isolated logic control of power-line switching. In applications where transient voltages on the power line are prevalent, provisions should be made to protect the H11J1 from breakover triggering.

## PHOTODIODE SOURCE FOLLOWER

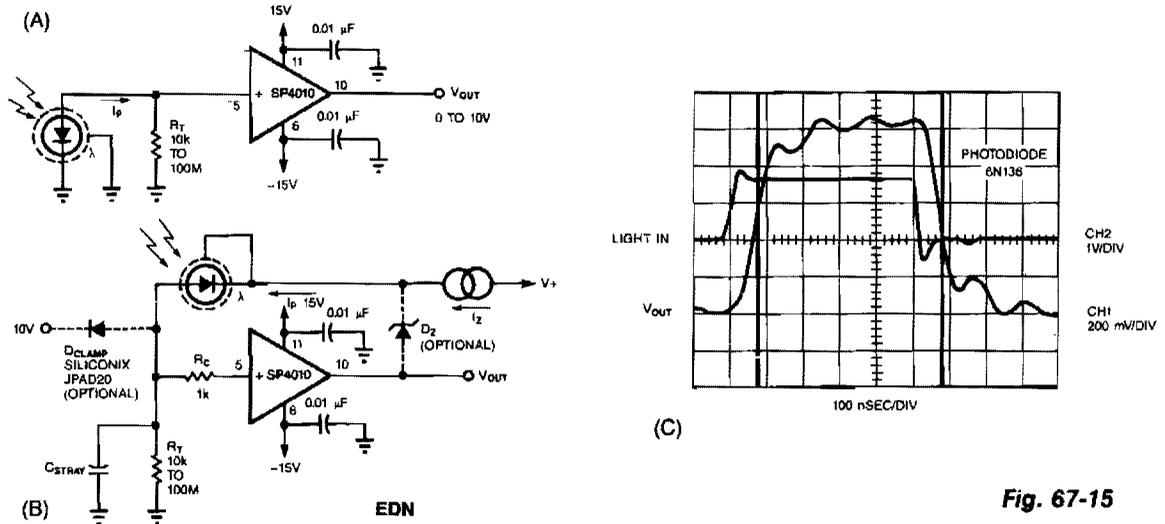

**Fig. 67-15**

A common method of transforming the output current of a photodiode into a voltage signal, paralleling the photodiode with a high-value load resistor, produces a nonlinear response. Also the combination of the load's transresistance,  $R_T$ , and the photodiode's junction capacitance,  $C_J$ , slows the circuit's response time. Figure 67-11B shows virtually the same components as Fig. 67-11A rearranged to maximize the inherent speed and linearity of the photodiode. The SP4010 (available from Hybrid Systems, Billerica, MA) is a unity voltage-gain buffer with a JFET input, 60-MHz 3-dB bandwidth, and 18-bit, 0.0004% linearity over a  $\pm 10$  V input range.

In the circuit of Fig. 67-11B, the photodiode sees a constant voltage across its terminals, which is essential for linear photodiode outputs. The optional zener diode,  $D_Z$ , sets a reverse bias at the photodiode for lower junction capacitance and higher speed. If you don't use  $D_Z$ , be sure to connect the feedback loop. An optional diode,  $D_{CLAMP}$ , limits the output in case of unexpected light bursts, but results in increased dark-current leakage and lower speed. The buffered output of the circuit equals the photodiode current times the transresistance,  $R_T$ . Figure 67-11C shows the circuit's response to a fast light pulse.

# 68



## Oscillators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Discrete Sequence Oscillator	Audio Oscillator
Fixed-Frequency Variable Duty-Cycle Oscillator	Low-Frequency Oscillator
RLC Oscillator	Quadrature Oscillator
HC-Based Oscillators	Wien-Bridge Oscillator
Programmable-Frequency Sine-Wave Oscillator	CMOS Oscillator
Variable Wien-Bridge Oscillator	XOR-Gate Oscillator
Wide-Range Oscillator	SCR Relaxation Oscillator
HCV/HCT-Based Oscillator	CMOS Oscillator
50% Duty-Cycle Oscillator	Code-Practice Oscillator
High-Frequency Oscillator	Precision Voltage-Controlled Oscillator
Last-Cycle Completing Gated Oscillator	5-V Oscillator
	Low-Voltage Wien-Bridge Oscillator

## DISCRETE SEQUENCE OSCILLATOR

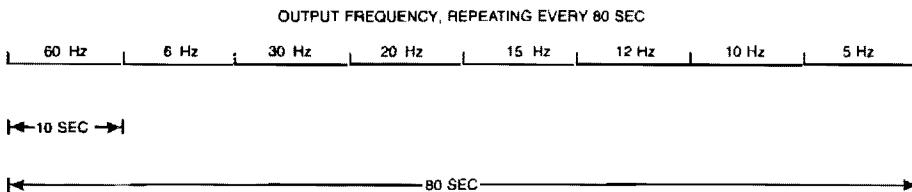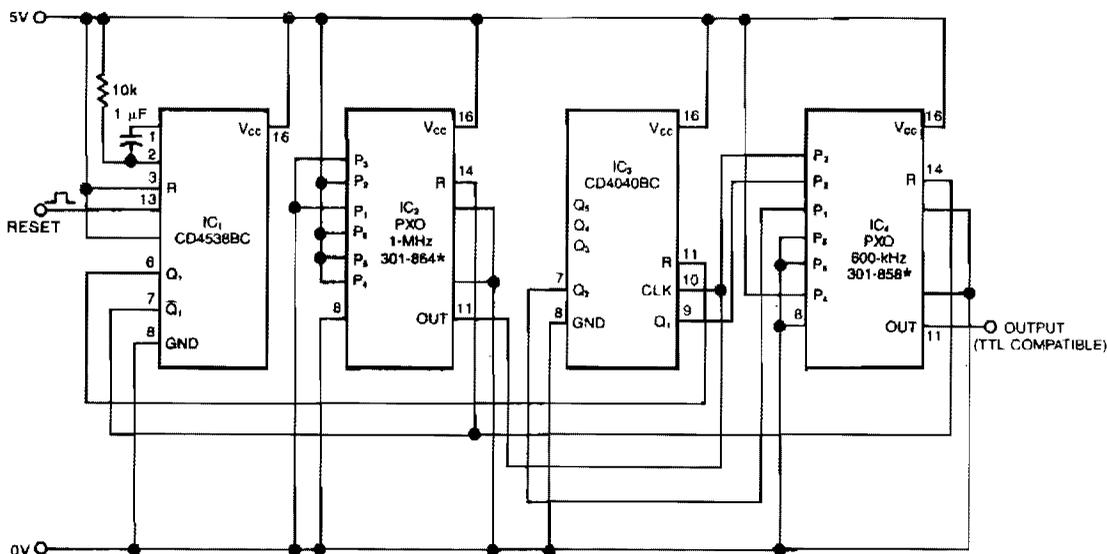

\*INTERFACE QUARTZ DEVICES LTD, CREWKERNE, SOMERSET, UK

EDN


**Fig. 68-1**

The swept-frequency oscillator offers an inexpensive source of discrete frequencies for use in testing digital circuits. In this configuration, the circuit generates an 80-second sequence of eight frequencies, dwelling for 10 seconds on each frequency. You can change the dwell time or the number of frequencies. Frequencies can range from 0.005 Hz to 1 MHz.

The programmable crystal oscillators, PXOs, IC2 and IC4 can each generate 57 frequencies in response to an 8-bit external code. IC2 contains a 1-MHz crystal and produces a 0.05-Hz output. IC4 contains a 600-kHz crystal; its output changes in response to the combined outputs of the 12-stage binary counter IC3 (Q1 and Q2) and the PXO IC2.

To generate more frequencies, you can use one or more of IC3's outputs, (Q3, Q4, Q5) to drive one or more of IC4's inputs (P4, P5, P6). Similarly, you can rewire IC2 or drive it with other logic to control the duration of each frequency. IC1, a monostable multivibrator, provides a system reset. It initiates the sequence shown, beginning at 60 Hz, in response to a positive pulse.
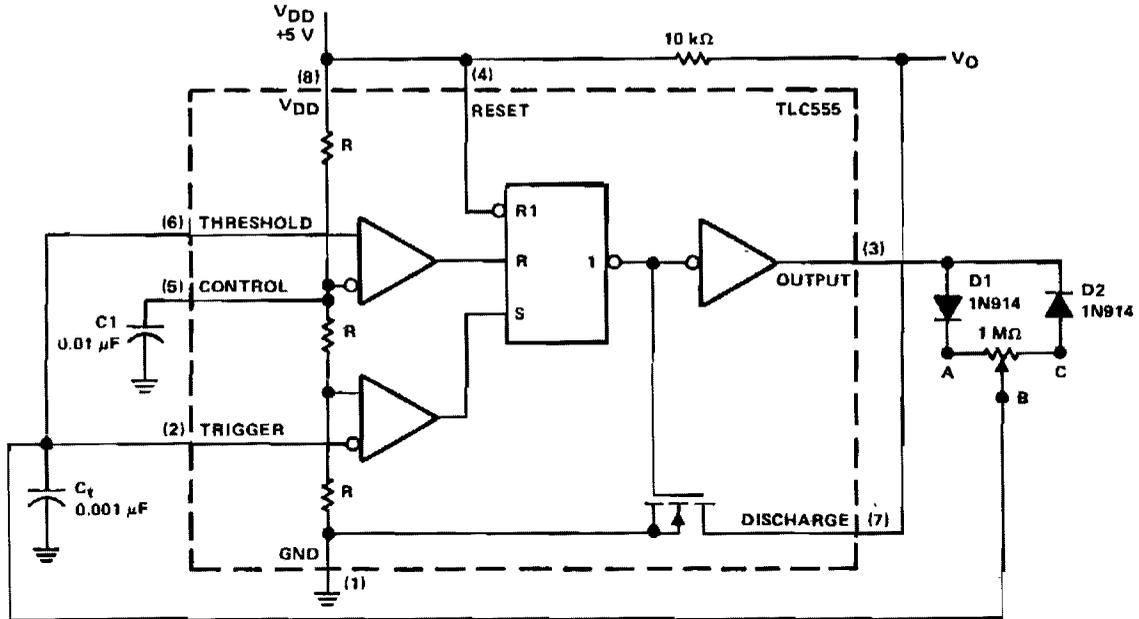
## FIXED-FREQUENCY VARIABLE DUTY-CYCLE OSCILLATOR




Reprinted by permission of Texas Instruments.

**Fig. 68-2**

In a basic astable timer, configuration timing periods  $t_1$  and  $t_2$  are not controlled independently. The lack of control makes it difficult to maintain a constant period,  $T$ , if either  $t_1$  or  $t_2$  is varied. In this circuit, charge  $R_{AB}$  and discharge  $R_{BC}$  resistances are determined by the position of common wiper B of the potentiometer. So, it is possible to adjust the duty-cycle by adjusting  $t_1$  and  $t_2$  proportionately, without changing period  $T$ .


At start-up, the voltage across  $C_1$  is less than the trigger level voltage ( $1/2 V_{DD}$ ), causing the timer to be triggered via pin 2. The output of the timer at pin 3 increases, turning off the discharge transistor at pin 7 and allowing  $C_1$  to charge through diode D1 and resistance  $R_{AB}$ . When capacitor  $C_1$  charges to upper threshold voltage  $2/3 V_{DD}$ , the flip-flop is reset and the output at pin 3 decreases. Capacitor  $C_1$  then discharges through diode D2 and resistor  $R_{BC}$ . When the voltage at pin 2 reaches  $1/3 V_{DD}$ , the lower threshold or trigger level, the timer triggers again and the cycle is repeated. In this circuit, the oscillator frequency remains fixed and the duty cycle is adjustable from less than 0.5% to greater than 99.5%.

## RLC OSCILLATOR

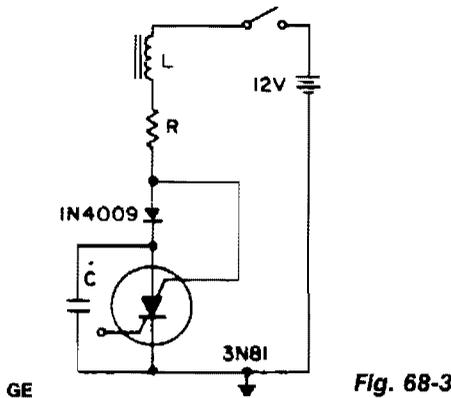

A positive transient, such as the power switch closing, charges  $C$  through  $L$  to a voltage above the supply voltage, if  $Q$  is sufficient. When the current reverses, the diode blocks and triggers the SCS. As the capacitor discharges, the anode gate approaches ground potential, depriving the anode of holding current. This turns off the SCS, and  $C$  charges to repeat the cycle.


## HC-BASED OSCILLATORS

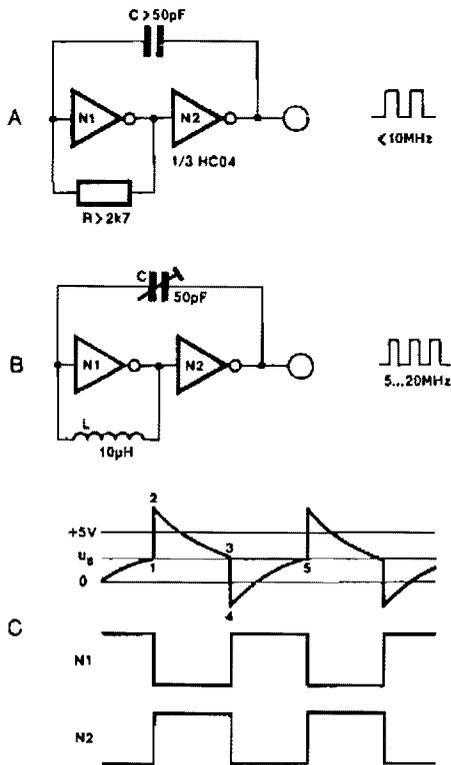

Two inverters, one resistor, and one capacitor are all that is required to make a HC(T)-based oscillator that gives reliable operation up to about 10 MHz. The use of two HC inverters produces a fairly symmetrical rectangular output signal. In the same circuit, HCT inverters give a duty factor of about 25%, rather than about 50%, since the toggle point of an HC and an HCT inverter is  $1/2 V_{CC}$ , and slightly less than 2 V, respectively. If the oscillator is to operate above 10 MHz, the resistor is replaced with a small inductor, as shown in Fig. 68-4B.


The output frequency of the circuit in Fig. 68-4A is given as about  $1/1.8rc$ , and can be made variable by connecting a 100-K $\Omega$  potentiometer in series with  $R$ . The solution adopted for the oscillator in Fig. 68-4B is even simpler:  $C$  is a 50-pF trimmer capacitor.
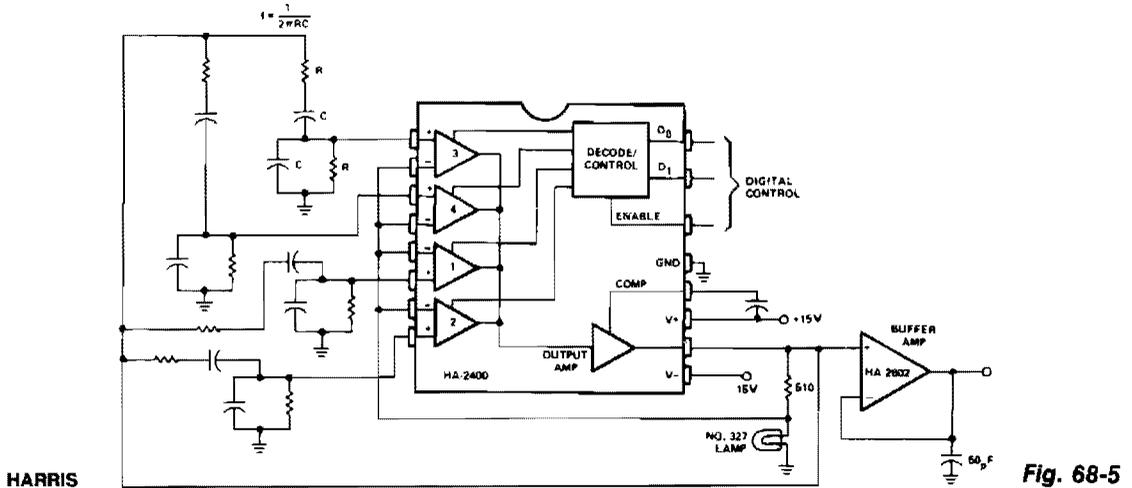
## PROGRAMMABLE-FREQUENCY SINE-WAVE OSCILLATOR



This Wien-bridge oscillator is very popular for signal generators, since it is easily turned over a wide frequency range, and has a very low distortion sine-wave output. The frequency determining networks can be designed from about 10 Hz to greater than 1 MHz; the output level is about 6.0-V rms. By substituting a programmable attenuator for the buffer amplifier, a very versatile sine-wave source for automatic testing, etc. can be constructed.

## VARIABLE WIEN-BRIDGE OSCILLATOR

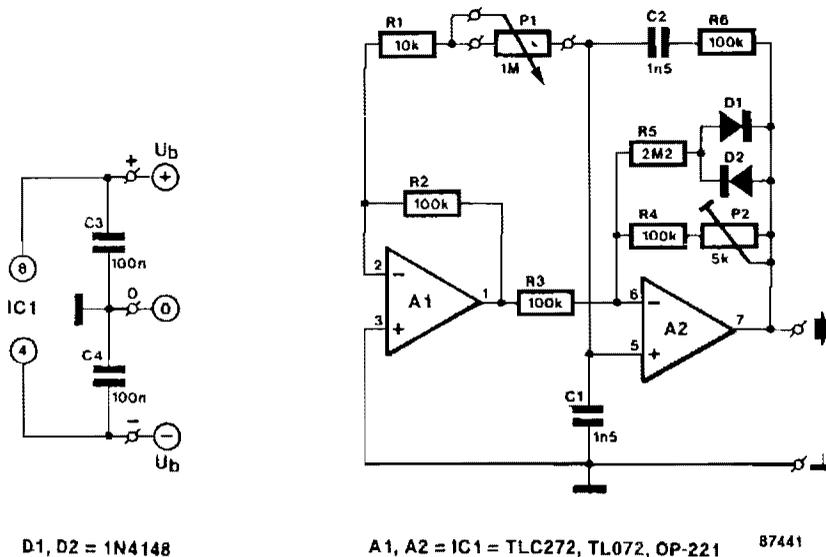

ELEKTOR ELECTRONICS

**Fig. 68-6**

## VARIABLE WIEN-BRIDGE OSCILLATOR (Cont.)

A Wien-bridge oscillator can be made variable by using two frequency-determining parts that are varied simultaneously at high tracking accuracy. High-quality tracking potentiometers or variable capacitors are, however, expensive and difficult to obtain. To avoid having to use such a component, this oscillator was designed to operate with a single potentiometer. The output frequency,  $f_o$ , is calculated from:


$$f_o = 1/(2nRC \nu a)$$

where:

$$R = R_2 = R_3 = R_4 = R_6, C = C_1 = C_2, \text{ and } a = (P_1 + R_1)R$$

With preset P2 you can adjust the overall amplification so that the output-signal has a reasonably stable amplitude, 3.5  $V_{PP}$  max., over the entire frequency range. The stated components allow the frequency to be adjusted between 350 Hz and 3.5 kHz.

## WIDE-RANGE OSCILLATOR

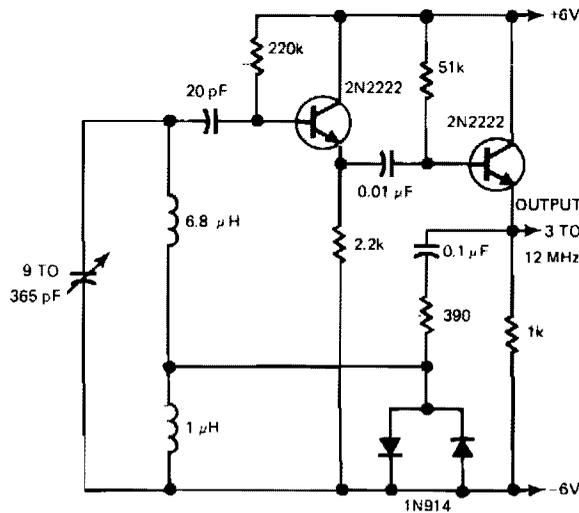

EDN

Fig. 68-7

The gain control allows the oscillator to maintain essentially constant output over its range. The circuit functions over 160 kHz to 12 MHz with essentially constant amplitude.

## HCU/HCT-BASED OSCILLATOR

ELEKTOR ELECTRONICS

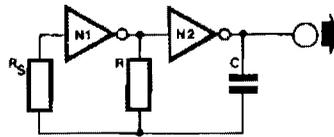


Fig. 68-8

N1, N2 = 1/3 IC1 = 74HCT04, 74HCU04

When frequency stability is not of prime importance, a simple, yet reliable, digital clock oscillator can be made with the aid of relatively few components. High-speed CMOS (HCU/HCT) inverters or gates with an inverter function are eminently suitable to make such oscillators, thanks to their low power consumption, good output signal definition, and extensive frequency range.


The circuit as shown uses two inverters in a 74HCT04 or 74HCU04. The basic design equations are:

$$\text{For HCU: } f=1/T; \quad T=2.2 RC; \quad V_{CC} \text{ 6 V; } \quad I_c=13 \text{ mA}$$

$$\text{For HCT: } f=1/T; \quad T=2.4 RC; \quad V_{CC} \text{ 5.5 V; } \quad I_c=2.2 \text{ mA}$$

With  $R_S$  and  $R$  calculated for a given frequency and value of  $C$ , both resistors can be realized as pre-sets to enable precise setting of the output frequency and the duty factor. Do not forget, however, to fit small series resistors in series with the pre-sets, in observance of the minimum values for  $R$  and  $R_S$  as given in the design equations. The values quoted for  $I_c$  are only valid if the inputs of the remaining gates are grounded.

## 50% DUTY-CYCLE OSCILLATOR

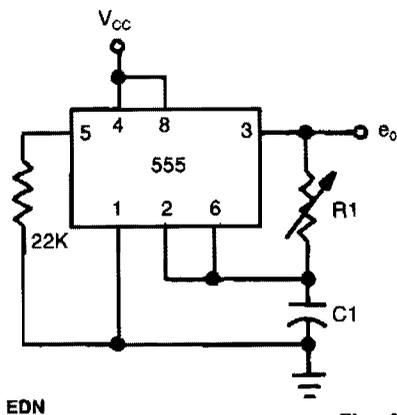


EDN

Fig. 68-9

Frequency of oscillation depends on the  $R1/C1$  time constant and allows frequency adjustment by varying  $R1$ .

## HIGH-FREQUENCY OSCILLATOR

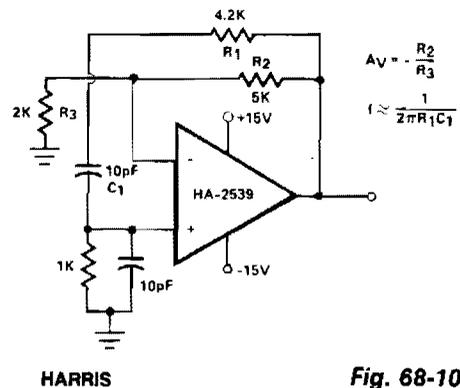


HARRIS

Fig. 68-10

Intended primarily as a building block for a QRP transmitter, this 20-MHz oscillator delivered a clean 6-V, pk-pk signal into a 100-Ω load.


## LAST-CYCLE COMPLETING GATED OSCILLATOR

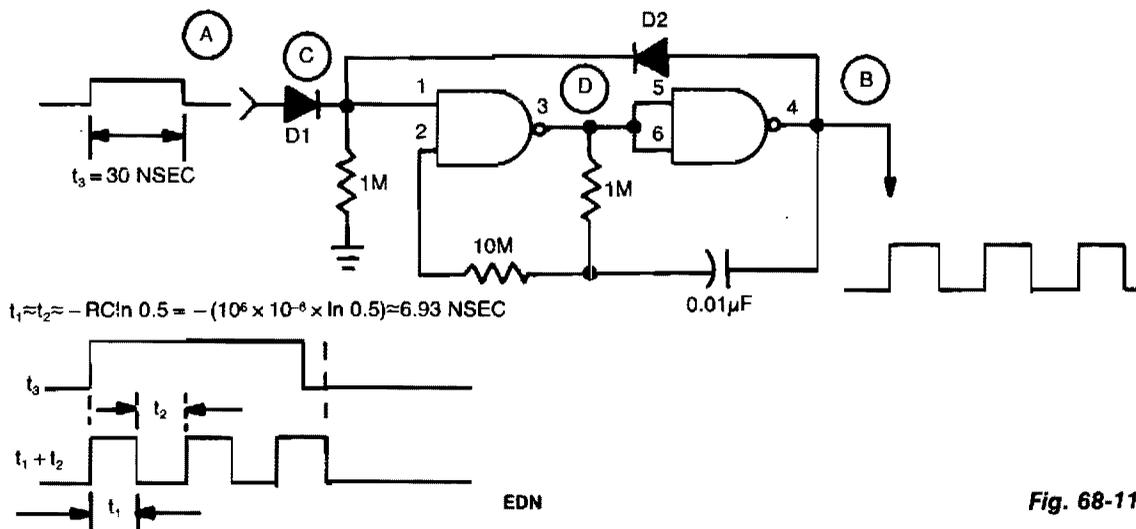

**Fig. 68-11**

Regenerative feedback at C enables the oscillator to complete its timing cycle, rather than immediately shutting it off. The IC used was a CD4011AE, although an equivalent will work.

## AUDIO OSCILLATOR

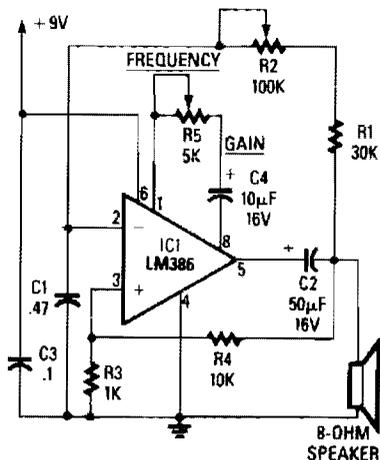


Reprinted with permission of Radio-Electronics Magazine, August 1986.  
Copyright Gernsback Publications, Inc., 1986.

**Fig. 68-12**

The circuit's frequency of oscillation is  $f = 2.8 / [C_1 \times (R_1 + R_2)]$ . Using the values shown, the output frequency can be varied from 60 Hz to 20 kHz by rotating potentiometer R2.

A portion of IC1's output voltage is fed to its noninverting input at pin 3. The voltage serves as a reference for capacitor C1, which is connected to the noninverting input at pin 2 of the IC. That capacitor continually charges and discharges around the reference voltage, and the result is a square-wave output. Capacitor C2 decouples the output.

## LOW-FREQUENCY OSCILLATOR

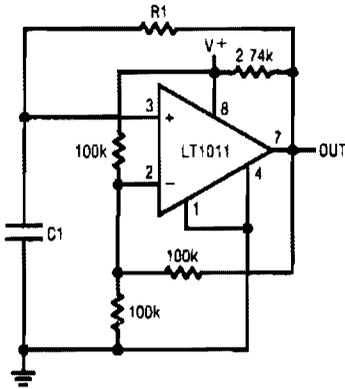


This simple rc oscillator uses a medium-speed comparator with hysteresis and feedback through  $R_1$  and  $C_1$  as timing elements. The frequency of oscillation is, at least theoretically, independent from the power supply voltage. If the comparator swings to the supply rails, if the pull-up resistor is much smaller than the resistor  $R_h$ , and if the propagation delay is negligible compared to the rc time constant, the oscillation frequency is:

$$f_{osc} = \frac{0.72}{R_1 C_1}$$

LINEAR TECHNOLOGY CORP.

Fig. 68-13


## QUADRATURE OSCILLATOR

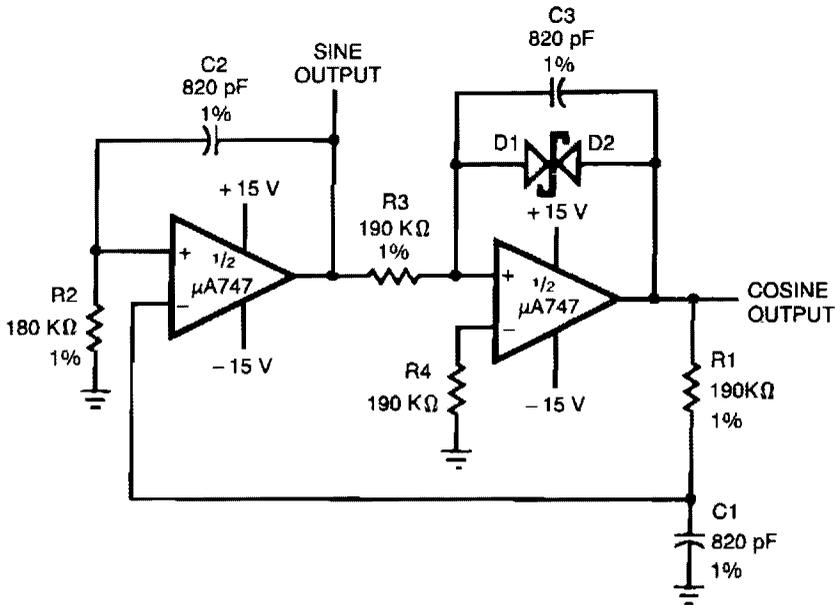

FAIRCHILD CAMERA AND INSTRUMENT

Fig. 68-14

### WIEN-BRIDGE OSCILLATOR

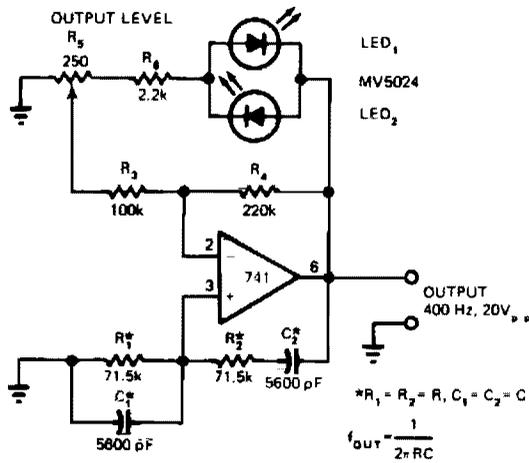


EDN

Fig. 68-15

LEDs function as both pilot lamps and as an AGC (automatic gain control) in this unconventional amplitude-stabilized oscillator.

### CMOS OSCILLATOR

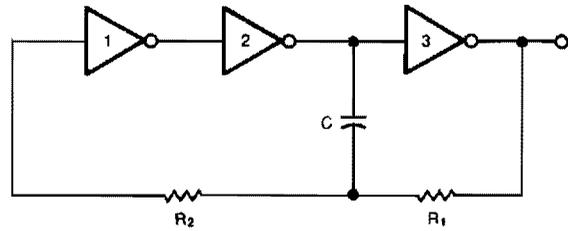


EDN

Fig. 68-16

This circuit is guaranteed to oscillate at a frequency of about  $2.2/(R_1 \times C)$  if  $R_2$  is greater than  $R_1$ . You can reduce the number of gates further if you replace gates 1 and 2 with a noninverting gate.

### XOR-GATE OSCILLATOR

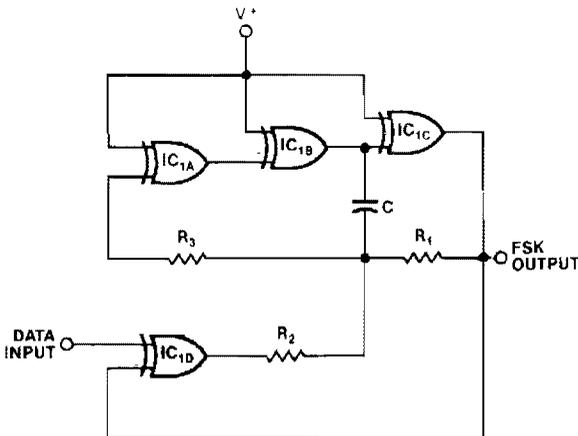

NOTES:  
 IC<sub>1</sub> = CD4070B  
 $R_1 \geq 15k$   
 $R_2, R_3 \geq 3R_1$   
 $f_o = \frac{1}{2R_1C}$   
 $V^+ = 5 \text{ TO } 15V$

EDN

Fig. 68-17

An exclusive-OR gate, IC1D, turns a simple CMOS oscillator into an FSK generator. When the data input increases, IC1D inverts, and negative feedback through  $R_2$  lowers the circuit's output frequency. A low input results in positive feedback and a higher output frequency.  $R_1$  and  $C$  set the oscillator's frequency range, and  $R_2$  determines the circuit's frequency shift. To ensure frequency stability, make  $R_3$  much greater than  $R_1$  and use a high-quality feedback capacitor. The three gates constituting the oscillator itself need not be exclusive-OR types; use any CMOS inverter.

## SCR RELAXATION OSCILLATOR

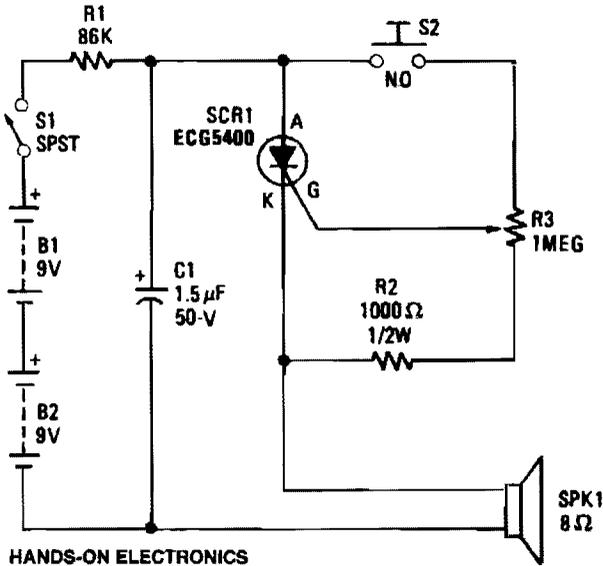


Fig. 68-18

## CMOS OSCILLATOR

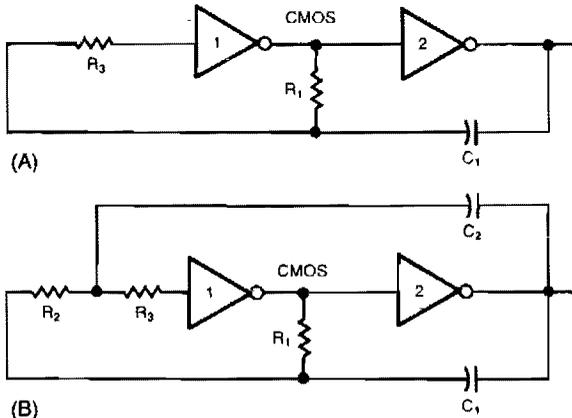


Fig. 68-19

EDN

The common clock oscillator in Fig. 68-19A has two small problems: It might not, in fact, oscillate if the transition regions of its two gates differ. If it does oscillate, it might sometimes oscillate at a slightly lower frequency than its equation predicts because of the finite gain of the first gate. If the cir-

cuit does work, oscillation occurs usually because both gates are in the package and, therefore, have logic thresholds only a few millivolts apart.

The circuit in Fig. 68-19B resolves both problems by adding a resistor and a capacitor. The  $R_2/C_2$  network provides hysteresis, thus delaying the onset of gate 1's transition until  $C_1$  has enough voltage to move gate 1 securely through its transition region. When gate 1 is finally in its transition region,  $C_2$  provides positive feedback, thus rapidly moving gate 1 out of its transition region.

The equations for the oscillator in Fig. 68-19B are:

$$R_2 = 10R_1$$

$$R_3 = 10R_2$$

$$C_1 = 100C_2$$

$$f \cong \frac{1}{1.2R_1C_1}$$

## CODE-PRACTICE OSCILLATOR


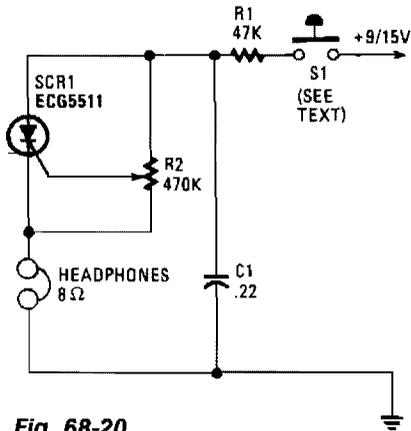


Fig. 68-20

Capacitor C1 charges through resistor R1, and when the gate level established by potentiometer R2 is high enough, the SCR is triggered. Current flows through the SCR and earphones, discharging C1. The anode voltage and current drop to a low level, so the SCR stops conducting and the cycle is repeated. Resistor R2 lets the gate potential across C1 be adjusted, which charges the frequency or tone. Use a pair of 8-Ω headphones. The telegraph key goes right into the B+ line, 9-V battery.

HANDS-ON ELECTRONICS/  
POPULAR ELECTRONICS
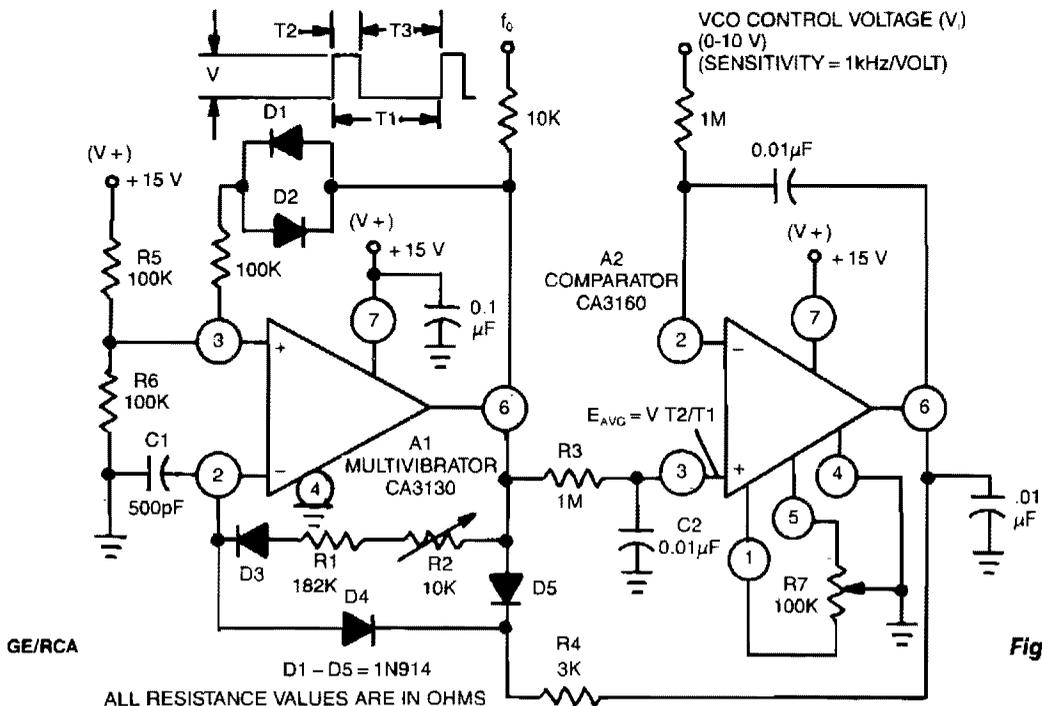
## PRECISION VOLTAGE-CONTROLLED OSCILLATOR




GE/RCA

D1 - D5 = 1N914  
ALL RESISTANCE VALUES ARE IN OHMS

Fig. 68-21

This circuit uses a CA3130 BiMOS op amp as a multivibrator and CA3160 BiMOS op amp as a comparator. The oscillator has a sensitivity of 1 kHz/V, with a tracking error in the order of 0.02%, and a temperature coefficient of 0.01%/°C.

## 5-V OSCILLATOR

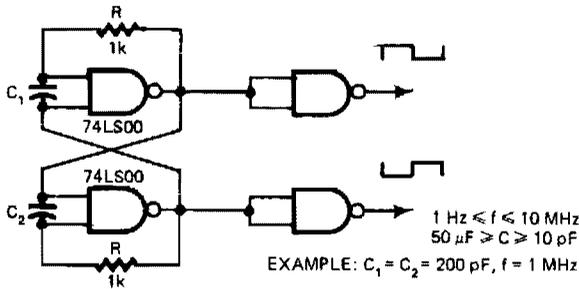

Consistently self-starting and yet capable of operating from over 1 Hz to 10 MHz, this low-cost oscillator requires only five components. Calculate the period of oscillation by using this relationship:  $P = 5 \times 10^3 C \text{ sec}$  when  $C = C_1 = C_2$ . By changing the ratio of  $C_1$  to  $C_2$ , the duty cycle can be as low as 20%.

EDN

Fig. 68-22

## LOW-VOLTAGE WIEN-BRIDGE OSCILLATOR

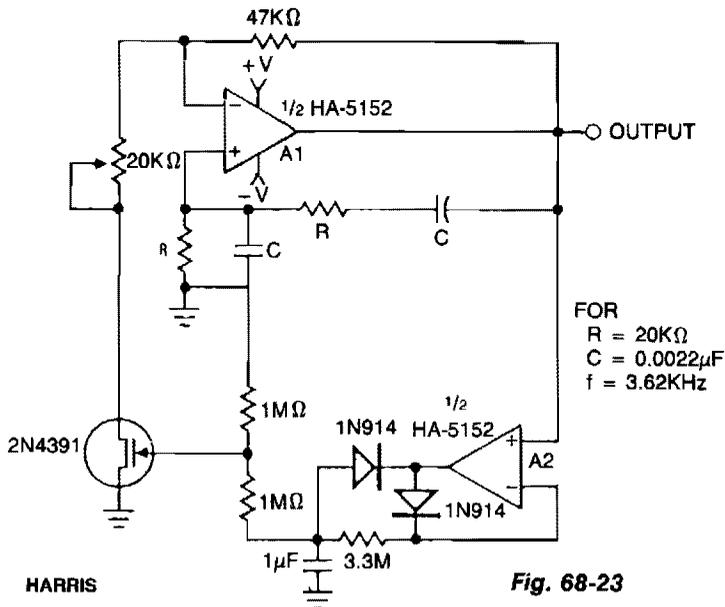


Fig. 68-23

This circuit utilizes an HA-5152 dual op amp and FET to produce a low-voltage, low-power, Wien-bridge sine-wave oscillator. Resistors  $R$  and capacitors  $C$  control the frequency of oscillation; the FET, used as a voltage-controlled resistor, maintains the gain of A1 exactly 3 dB to sustain oscillation. The 20-K $\Omega$  pot can be used to vary the signal amplitude. The HA-5152 has the capability to operate from  $\pm 1.5\text{-V}$  supplies. This circuit will produce a low-distortion sine-wave output while drawing only 400  $\mu\text{A}$  of supply current.

# 69



## Oscilloscope Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Scope Extender	Oscilloscope Preamplifier
Eight-Channel Voltage Display	Oscilloscope/Counter Preamplifier
Oscilloscope Calibrator	Oscilloscope-Triggered Sweep
Scope Sensitivity Amplifier	CRO Doubler
Add-On Scope Multiplexer	

## SCOPE EXTENDER

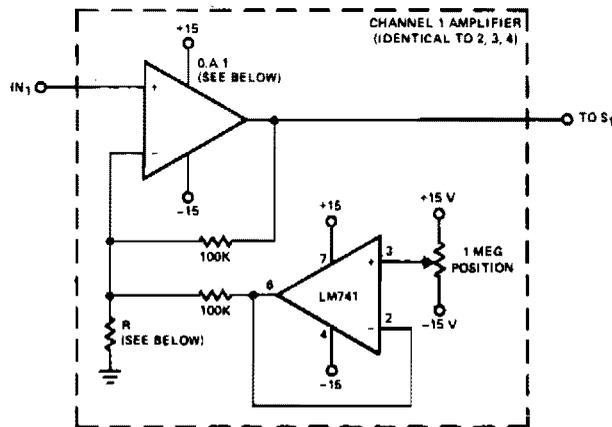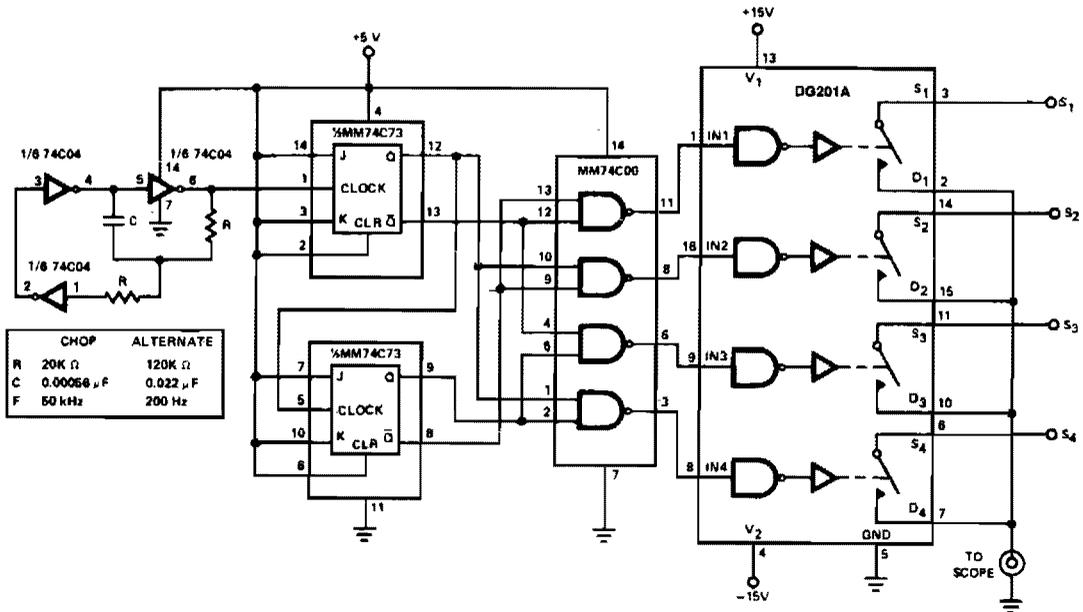


0. A. 1 IS OP AMP WITH SUITABLE BANDWIDTH, SLEW RATE, ETC., FOR DESIRED SIGNALS  
 R IS ADDED FOR EXTRA GAIN ACCORDING TO FORMULA VOLTAGE GAIN =  $2 + \frac{100K}{R}$

SILICONIX

**Fig. 69-1**

The adapter allows four inputs to be displayed simultaneously on a single trace scope. For low-frequency signals, less than 500 Hz, the adapter is used in the *chop* mode at a frequency of 50 kHz. The clock can be run faster, but switching glitches and the actual switching time of the DG201A limit the maximum frequency to 200 kHz. High frequencies are best viewed in the alternate mode, with a clock frequency of 200 Hz. When the clock is below 100 Hz, trace flicker becomes objectionable. One of the four inputs is used to trigger the horizontal trace of the scope.

## EIGHT-CHANNEL VOLTAGE DISPLAY

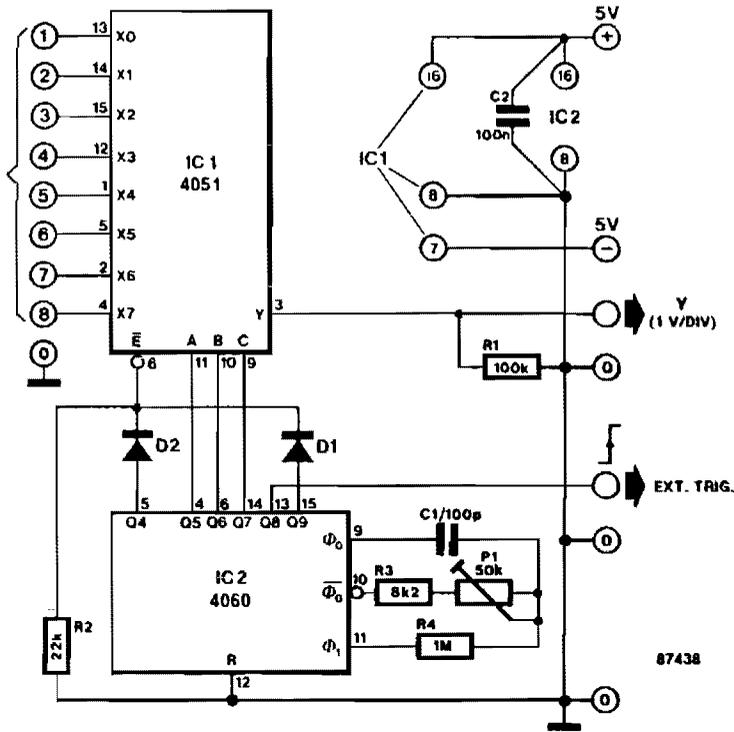

ELEKTOR ELECTRONICS


Fig. 69-2

This circuit turns a common oscilloscope into a versatile eight-channel display for direct voltages. The trend of each of the eight input levels is readily observed, albeit that the attainable resolution is not very high.

The circuit diagram shows the use of an eight-channel analog multiplexer IC1, which is the electronic version of an eight-way rotary switch with contacts X0 through X7 and pole Y. The relevant channel is selected by applying a binary code to the A-B-C inputs. For example, binary code 011 (A-B-C) enables channel 7 (X6 Y). The A-B-C inputs of IC1 are driven from three successive outputs of binary counter IC2, which is set to oscillate at about 50 kHz with the aid of P1. Since the counter is not reset, the binary state of outputs Q5, Q6, and Q7 steps from 0 to 7 in a cyclic manner. Each of the direct voltages at input terminals 1 to 8 is therefore briefly connected to the Y input of the oscilloscope. All eight input levels can be seen simultaneously by setting the timebase of the scope, in accordance with the time it takes the counter to output states 0 through 7, on outputs Q5, Q6, and Q7.

The timebase on the scope should be set to 0.5 ms/div, and triggering should occur on the positive edge of the external signal. Set the vertical sensitivity to 1 V/div. The input range of this circuit is from -4 V to +4 V; connected channels are terminated in about 100 K $\Omega$ .

## OSCILLOSCOPE CALIBRATOR

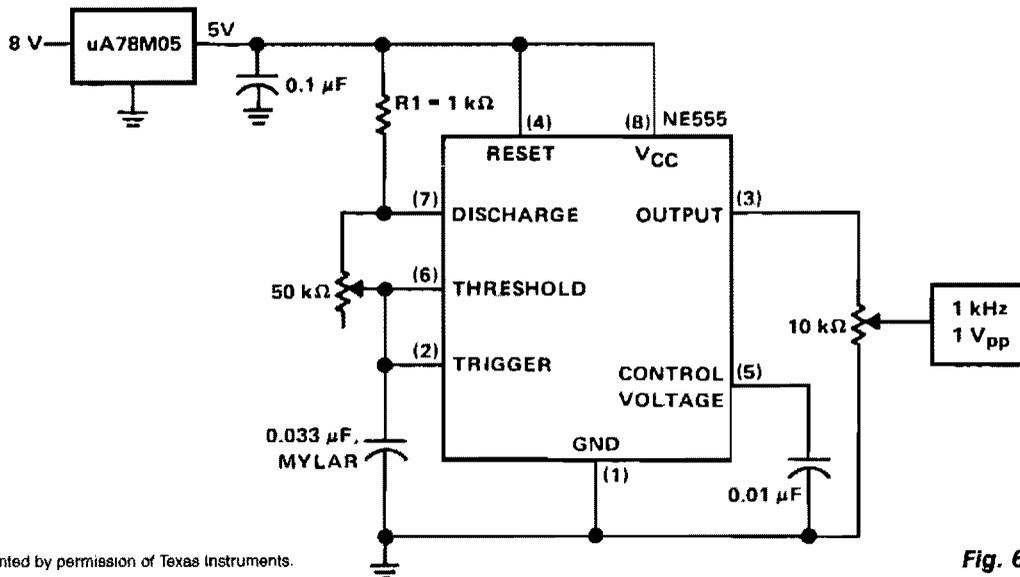


Reprinted by permission of Texas Instruments.

**Fig. 69-3**

The calibrator can be used to check the accuracy of a time-base generator, as well as to calibrate the input level of amplifiers. The calibrator consists of an NE555 connected in the astable mode. The oscillator is set to exactly 1 kHz by adjusting potentiometer P1 while the output at pin 3 is being monitored against a known frequency standard or frequency counter. The output level, likewise, is monitored from potentiometer P2's center arm to ground with a standard instrument. P2 is adjusted for 1 V pk-pk at the calibrator output terminal. During operation, the calibrator output terminal will produce a 1-kHz, square-wave signal at 1 V pk-pk with about 50% duty cycle. For long-term oscillator frequency stability, C1 should be a low-leakage mylar capacitor.


## SCOPE SENSITIVITY AMPLIFIER

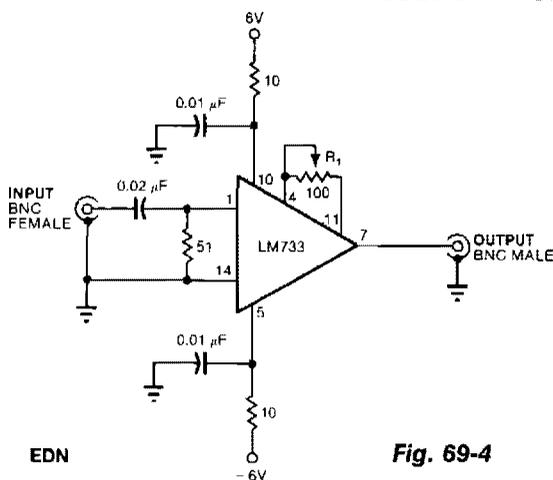

**Fig. 69-4**

This circuit provides  $20 \pm 0.1$  dB voltage gain from 0.5 to 25 MHz and  $\pm 3$  dB from 70 kHz to 55 MHz. An LM733 video amplifier furnishes a low input-noise spec, 10- $\mu$ V typical, measured over a 15.7-MHz bandwidth. The scale factor of the instrument can be preserved by using a trimmer R1 or a selected precision resistor, to set the circuit's voltage gain to exactly 100.

## ADD-ON SCOPE MULTIPLEXER

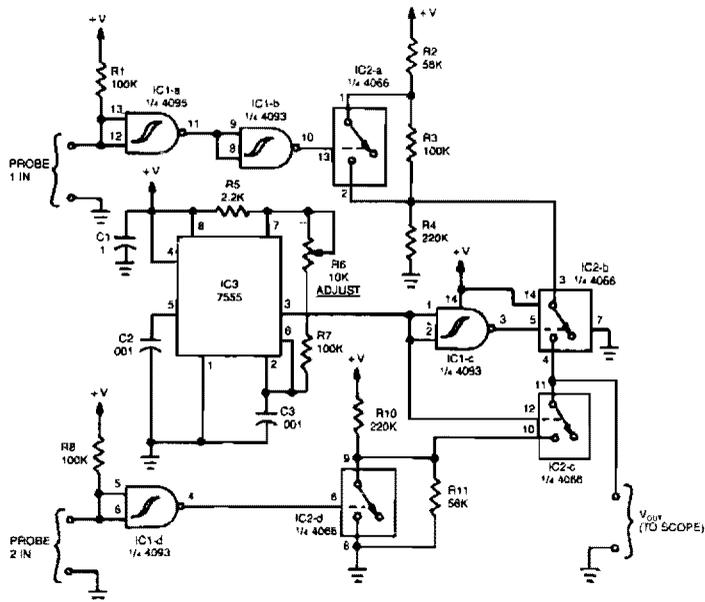


**Fig. 69-5**

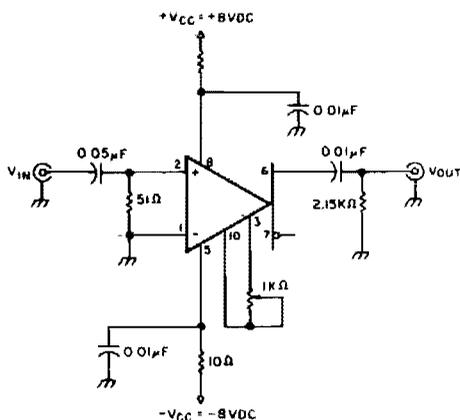Reprinted with permission of Radio-Electronics Magazine, October 1984. Copyright Gernsback Publications, Inc., 1984.

The operation of the unit revolves around three ICs: a 4093 quad NAND Schmitt trigger, a 4066 quad analog switch, and a 7555 timer. When a high is fed to probe 1 in, it is inverted to IC1a and once again by IC1b, so that the input to IC2a is high. That high causes the *switch contacts* in IC2a to close. With the *contacts* closed, a high-level output is presented to the input of IC2b. The high output is fed to probe 2 in. That signal is then inverted by IC1d and routed to IC2d, causing its *contacts* to open, and the unit to output a logic-level high. The output of IC2d is then fed to IC2c.


## OSCILLOSCOPE PREAMPLIFIER



This circuit provides about 20 dB voltage gain with a frequency range from 0.5 to 50 MHz. You can extend the low-frequency response of this circuit by increasing the value of the 0.05- $\mu\text{F}$  capacitor—or try removing the capacitor. This circuit delivers a particularly small level of input noise, measured at approximately 20  $\mu\text{V}$  over a bandwidth range of 15 MHz.

Calibrate the gain by adjusting the gain potentiometer connected between pins 3 and 10, then adjust the 1-K $\Omega$  trimmer potentiometer for an exact voltage gain of 10; this helps preserve the scale factor of the oscilloscope.

## OSCILLOSCOPE/COUNTER PREAMPLIFIER

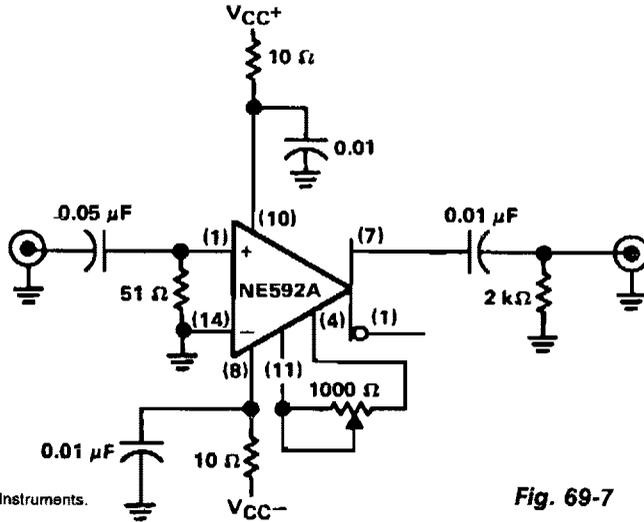

Reprinted by permission of Texas Instruments.

Fig. 69-7

The circuit will provide a  $20 \pm 0.1$  dB voltage gain from 500 kHz to 50 MHz. The low-frequency response of the amplifier can be extended by increasing the value of the  $0.05\text{-}\mu\text{F}$  capacitor connected in series with the input terminal. This circuit will yield an input-noise level of approximately  $10\ \mu\text{V}$  over a 15.7-MHz bandwidth. The gain can be calibrated by adjusting the potentiometer connected between pins 4 and 11. The 1-K $\Omega$  potentiometer can be adjusted for an exact voltage gain of 10. This preserves the scale factor of the instrument.

## OSCILLOSCOPE-TRIGGERED SWEEP


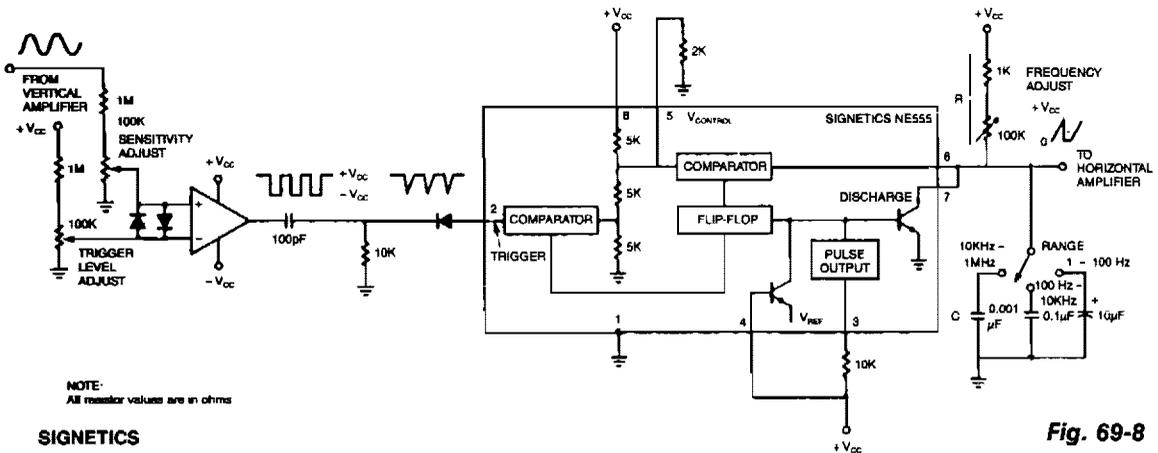


Fig. 69-8


The circuit's input op amp triggers the timer, sets its flip-flop and cuts off its discharge transistor so that capacitor C can charge. When capacitor voltage reaches the timer's control voltage of  $0.33 V_{CC}$ , the flip-flop resets and the transistor conducts, discharging the capacitor. Greater linearity can be achieved by substituting a constant-current source for frequency adjust resistor R.

## CRO DOUBLER

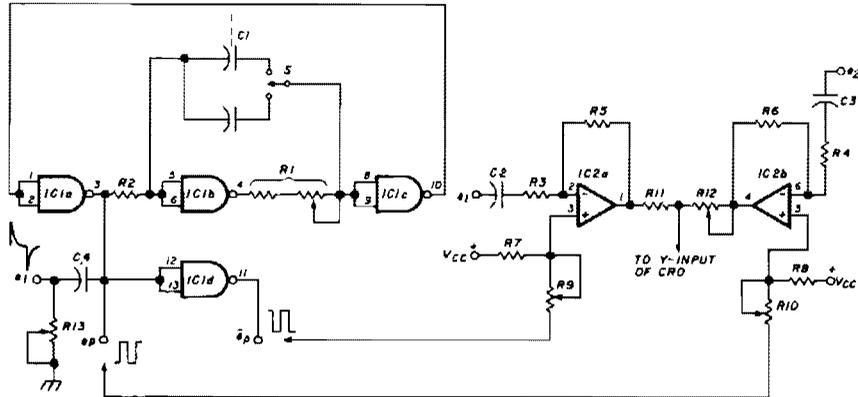


Parts List (fig. 1)

IC1	4011	R3	20k
IC2	LM358	R4	20k
C1	0.001 $\mu$ F	R5	200k
	0.01 $\mu$ F	R6	200k
	0.1 $\mu$ F	R7	50k
	1.0 $\mu$ F	R8	50k
	10 $\mu$ F	R9	50k pot
C2	25 $\mu$ F	R10	50k pot
C3	25 $\mu$ F	R11	100 ohm
C4	0.001 $\mu$ F	R12	300 ohm pot
R1	500-ohm + 50-k pot	R13	50k pot
R2	500 ohm	Vcc	5 volts
		S	multipole switch


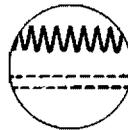


$R_{12} < R_{11}$

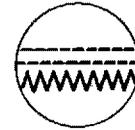

$R_{12} > R_{11}$

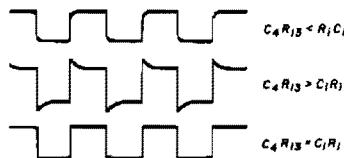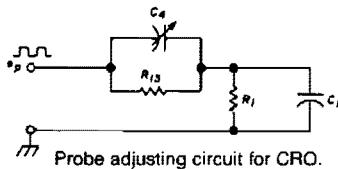Oscillograms of the displayed input signals  $e_1$  (sine wave) and  $e_2$  (square wave).



Displayed square waves on CRO screen.

**Fig. 69-9**

### HAM RADIO

IC1a, IC1b, and IC1c of the quad two-input NAND gate 4011 are connected as an astable multivibrator; IC1d is connected as an inverter. Terminals 3 and 11 of the 4011 produce square waves with opposite phases. The square waves,  $e_p$ , at the output of IC1a, passing through differentiator C4R13, then form positive and negative pulses,  $e_1$ . The dual op amps of the LM358 are used as two gated amplifiers for signals  $e_1$  and  $e_2$  and fed through terminals 2 and 6, to be displayed simultaneously on the CRO screen.

The two opposite-phase square waves  $\bar{e}_p$  and  $e_p$  are used to gate IC2a and IC2b at terminals 3 and 5 of the LM358, respectively. Resistances R9 and R10 are preadjusted so that one op amp is driven to saturation while the other works normally as an amplifier. Thus, they will amplify signals  $e_1$  and  $e_2$  alternately, and two separate traces will be displayed on the screen. Resistance R12 can be varied to adjust the vertical separation of the two traces.

Select a suitable value for C1 with switch S, and adjust the pot of R1. The frequency of square waves can be varied from 1 to  $10^6$  cps. This process is necessary for stabilizing the waveforms displayed on the screen. A common supply of 6 V is used in the circuit.

# 70


## Phase Detectors

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Phase Selector/Phase Detector/  
Synchronous Rectifier/Balanced Modulator  
Phase Sequence Detector  
Phase Detector
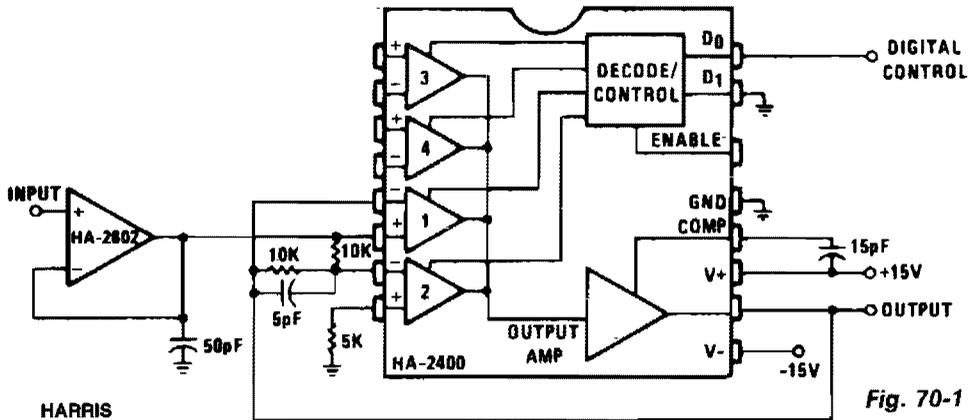
## PHASE SELECTOR/PHASE DETECTOR/ SYNCHRONOUS RECTIFIER/BALANCED MODULATOR




This circuit passes the input signal at unity gain, either unchanged or inverted, depending on the digital control input. A buffered input is shown, since low-source impedance is essential. Gain can be added by modifications to the feedback networks. Signals up to 100 kHz can be handled with 20.0-V pk-pk, output. The circuit becomes a phase detector when driving the digital control input with a reference phase at the same frequency as the input signal; the average dc output is proportional to the phase difference, with 0 V at +90°. By connecting the output to a comparator, which in turn drives the digital control, a synchronous full-wave rectifier is formed. With a low-frequency input signal and a high-frequency digital control signal, a balanced (suppressed carrier) modulator is formed.

## PHASE-SEQUENCE DETECTOR

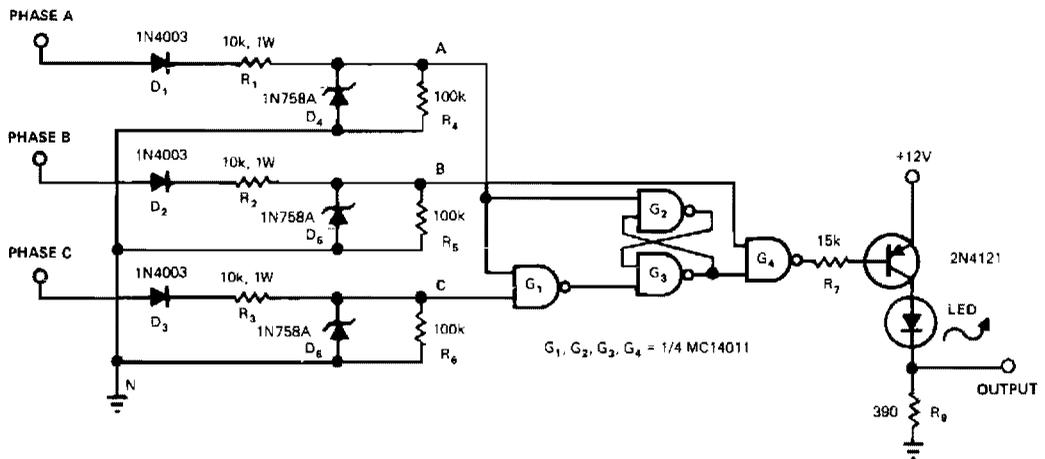

EDN

## PHASE DETECTOR

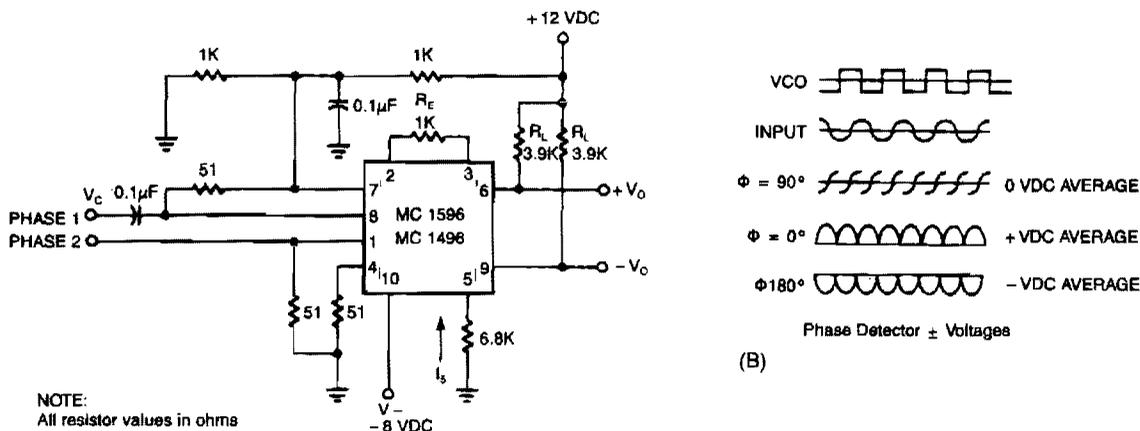

(A)

**Fig. 70-3**

### SIGNETICS

The output of the detector contains a term related to the cosine of the phase angle. Two signals of equal frequency are applied to the inputs. The frequencies are multiplied together, producing the sum and difference frequencies. Equal frequencies cause the difference component to become dc, while the undesired sum component is filtered out. The dc component is related to the phase angle by the graph of Fig. 70-2B. At  $90^\circ$ , the cosine becomes zero, while being at maximum positive or maximum negative at  $0^\circ$  and  $180^\circ$ , respectively. The advantage of using the balanced modulator over other types of phase comparators is the excellent conversion-linearity. This configuration also provides a conversion gain, rather than a loss for greater resolution. Used in conjunction with a phase-locked loop, for instance, the balanced modulator provides a very low-distortion FM demodulator.

Correct phase sequences (ABC, BCA, or CAB) produce trains of output pulses and illuminate the LED. The output stays low and the LED remains dark for incorrect sequences (BAC, ACB, or CBA) or for phase loss (phase A, B, or C missing).

# 71


## Photography-Related Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Slide-Show Timer  
Camera Alarm Trigger  
Darkroom Enlarger Timer  
Flash Meter  
Slave Photographic Xenon Flash Trigger  
Slide Timer  
Electronic Photoflash

## SLIDE-SHOW TIMER

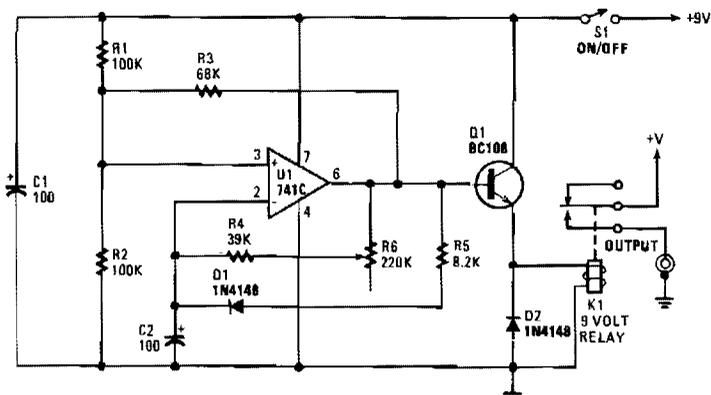

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 71-1


You can set the interval from about 5–30 seconds. A relay operates the slide-change mechanism. Op amp U1 forms a sort of Schmitt trigger. Resistors R1 and R2 bias the noninverting input at pin 3 of U1 to half the supply voltage. Feedback resistor R3 increases or reduces the bias to pin 3, depending on whether the output of U1 is high or low.

When power is first applied to the circuit, C2 has a zero charge and the inverting input of the op amp is at a lower voltage than its noninverting input. When the output of U1 is high, C2 begins to charge through R5 and D1. It takes about one second for the charge on C2 to reach the same voltage as that at the noninverting input of U1. At that time, the output of U1 begins a negative swing.

Because of the positive feedback through R3, the voltage at the noninverting input is reduced and the output becomes more negative. The voltage at the noninverting input is about  $\frac{1}{4}$  of the supply voltage, and C2 begins to discharge through the resistor bank. The timing is controlled by R6.

The resulting pulses are fed to the base of Q1, configured as an emitter-following buffer stage, which is used to activate relay K1. Transistor Q1 is necessary because op amps usually have an output current in the 20-mA range, which is too low to activate the relay.

## CAMERA ALARM TRIGGER

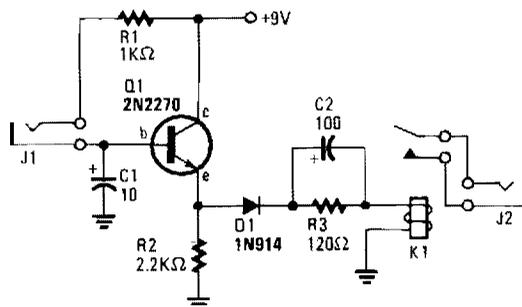


HANDS-ON ELECTRONICS

Fig. 71-2

## CAMERA ALARM TRIGGER (Cont.)

Transistor Q1 remains off until the magnetic switch connected to J1 closes. When that happens, the 9 V is connected through R1 to Q1'S base. Q1 turns on, thereby charging C2 through relay K1, which causes K1's contacts to close. Since the contacts connect via J2 to the remote control jack in the camera, which in turn connects to the camera's shutter release, the closure of K1's contacts will cause the camera's shutter to trigger. After C2 charges, K1 opens because current through its coil ceases; the camera won't take another picture. If Q1 turns off because the magnetic switch on the window or gate opens, C2 discharges and the circuit is ready for another cycle. As long as Q1 remains on, C2 stays charged and prevents K1 from triggering more photos. Capacitor C1 bypasses spurious magnetic switch noises from physical phenomena, such as a rattling window or a gate shaking in the wind, thus reducing the likelihood of an unwanted picture. Resistor R2 biases Q1 and dampens K1/C2 oscillations which might cause contact bounce. Diode D1 prevents C2 from discharging through K1; the relay coil isn't polarity conscious and C2 discharging through it would trigger an unwanted picture.

## DARKROOM ENLARGER TIMER

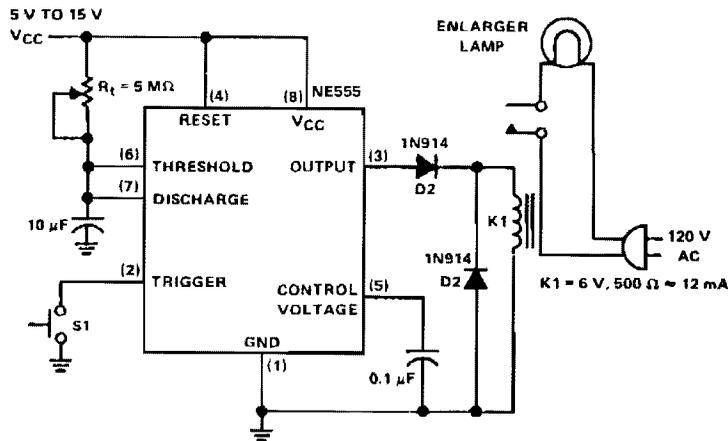


Reprinted by permission of Texas Instruments.

Fig. 71-3

The NE555 circuit is a basic one-shot timer with a relay connected between the output and ground. It is triggered with the normally open momentary contact switch, which when operated, grounds the trigger input at pin 2. This causes a high output to energize K1 which closes the normally open contacts in the lamp circuit. They remain closed during the timing interval, then open at time out. Timing is controlled by a 5-MΩ potentiometer,  $R_t$ . All timer-driven relay circuits should use a reverse clamping diode, such as D1, across the coil. The purpose of diode D2 is to prevent a timer output latch-up condition in the presence of reverse spikes across the relay.

With the rc time constant shown, the full-scale time is about 1 minute. A scale for the 5-MΩ potentiometer shaft position can be made and calibrated in seconds. Longer or shorter full-scale times can be achieved by changing the values of the rc timing components.

## FLASH METER

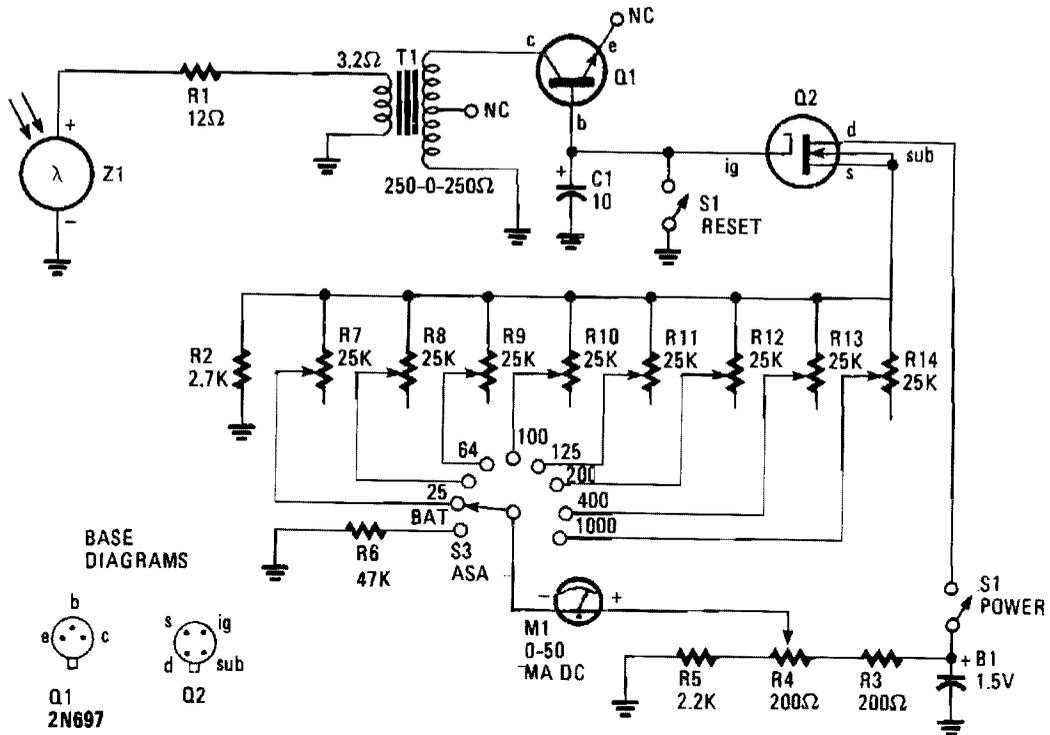


HANDS-ON ELECTRONICS

Fig. 71-4

Insulated-gate, field-effect transistor (IGFET), Q2 and silicon photo cell Z1 form the heart of this circuit. Transformer T1 is an audio-output type, but it's reversed in the circuit. A sudden flash from a photo-flash unit detected by Z1 sends a voltage pulse through the low-impedance winding of T1 via R1. That voltage pulse is stepped-up in T1's 500-Ω, primary winding before being rectified by Q1. Transistor Q1 is used as a diode; its emitter lead was snipped off close to the case. Q1 then charges C1 to a value proportional to the amplitude of the electrical pulse generated by the light from a flash unit.

Capacitor C1 controls the current flowing through Q2, which has a very high-input impedance. The current through Q2 is read by meter M1, a 0-50 μA dc unit, which has been calibrated in f-stops. The extremely high internal resistances of Q1 and Q2 will allow C1 to retain its charge for several minutes; this is more than enough time for you to take your reading of M1. The charge on C1 is shorted to ground and returned to 0 V by depressing reset button S1. The flashmate is ready to read the next photoflash. Trim potentiometers, R7 through R14, are adjusted to values which will yield correct readings for corresponding film sensitivities, or exposure indexes.

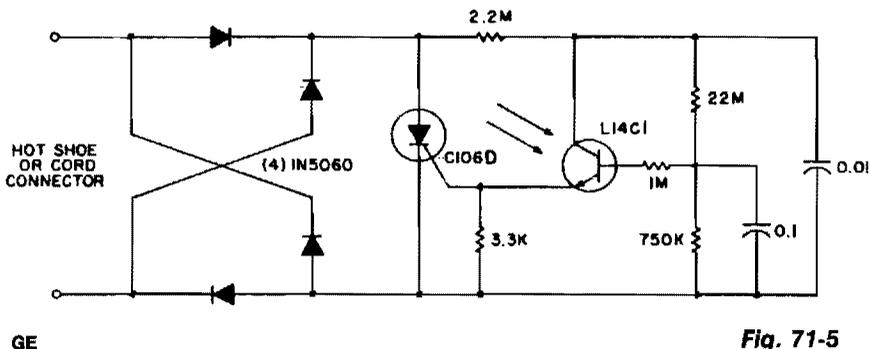
## SLAVE PHOTOGRAPHIC XENON FLASH TRIGGER



This circuit is used for remote photographic flash units that flash at the same time as the flash attached to the camera. This circuit is designed to the trigger cord or *hot shoe* connection of a commercial portable flash unit and triggers the unit from the light produced by the light of the flash unit attached to the camera. This provides remote operation without the need for wires or cables between the various units. The flash trigger unit should be connected to the slave flash before turning the flash on to prevent a  $dV/dt$  triggered flash on connection. The L14C1 phototransistor has a wide, almost cosine viewing angle, so alignment is not critical. If a very sensitive, more directional remote trigger unit is desired, the circuit can be modified using an L14G2 lensed phototransistor as the sensor.

The lens on this transistor provides a viewing angle of approximately  $10^\circ$  and gives over a 10 to 1 improvement in light sensitivity (3 to 1 range improvement). Note that the phototransistor is connected in a self-biasing circuit which is relatively insensitive to slow-changing ambient light, and yet discharges the  $0.01\text{-}\mu\text{F}$  capacitor into the C106D gate when illuminated by a photo flash. For a physically smaller size, the C106D can be replaced by a C205D, if the duty cycle is reduced appropriately.

## SLIDE TIMER

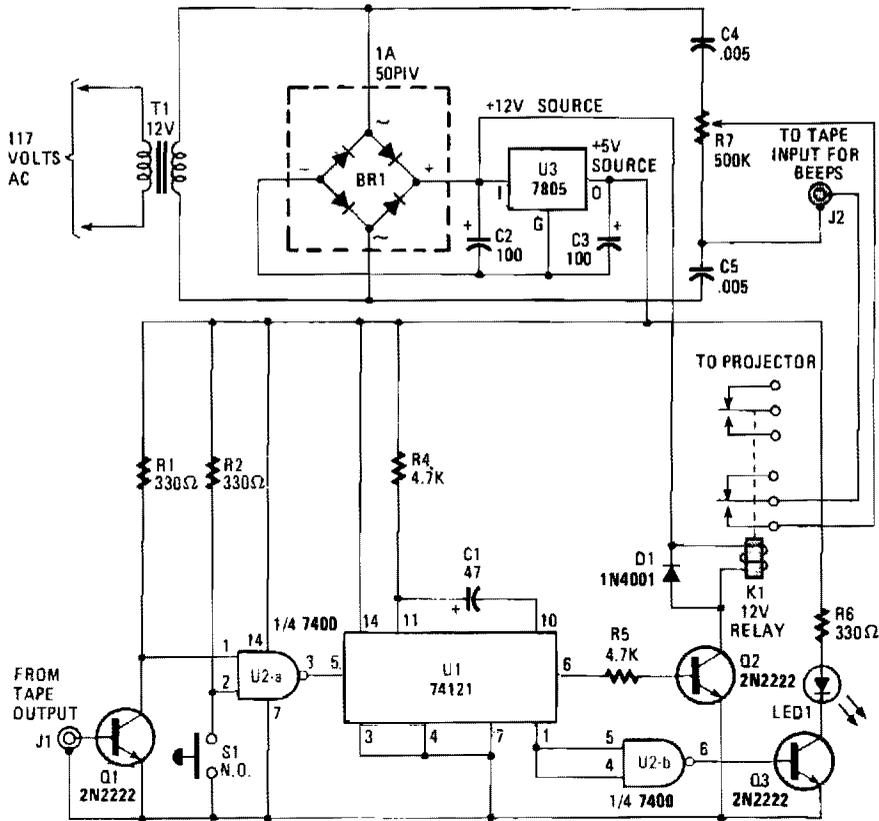

POPULAR ELECTRONICS

Fig. 71-6

This circuit will record commentary and/or music on one track of a tape and put the beeps that change the slides on another track. Gate U2a is used to trigger U1, which is configured as a timer when a pulse is received from either the tape input or via pushbutton switch S1. Timer U2 outputs one pulse for every input pulse received, no matter how long S1 is depressed.

The Q output of U2 at pin 1 is fed to U2b, which is set up as an inverter. When pin 1 of U1 becomes low, Q3 is activated, lighting LED1. The Q output of U1 at pin 6 is tied to the base of Q2, through R5, so that when pin 6 becomes high, Q2 is turned on. When Q2 is turned on, relay K1 is energized, and a signal is fed to the tape input through J2. The second set of contacts of K1 are used to trigger the projector.

Power for the circuit is provided by a 7805 regulator. The unregulated 12 V output of BR1 is used to power the relay. The 12-V relay needs to have two sets of contacts as shown: to advance the projector, and to supply the beeps when recording. The LED indicates projector advance.

To record the beeps, connect beeper jack J2 to the input of the tape recorder and connect the controller to the projector-advance plug. The 60-Hz line frequency is used to produce beeps that are recorded on half of the stereo tape. The other track is used for commentary. The beeper output is controlled via 500-KΩ potentiometer R6.



# 72


## Power Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

50-W Audio Power Amplifier	Audio Power Amplifier
Output-Stage Power Booster	6-W Power Amplifier with Preamp
Portable Amplifier	Hybrid Power Amplifier
Class-D Power Amplifier	20-W Audio Amplifier

## 50-W AUDIO POWER AMPLIFIER

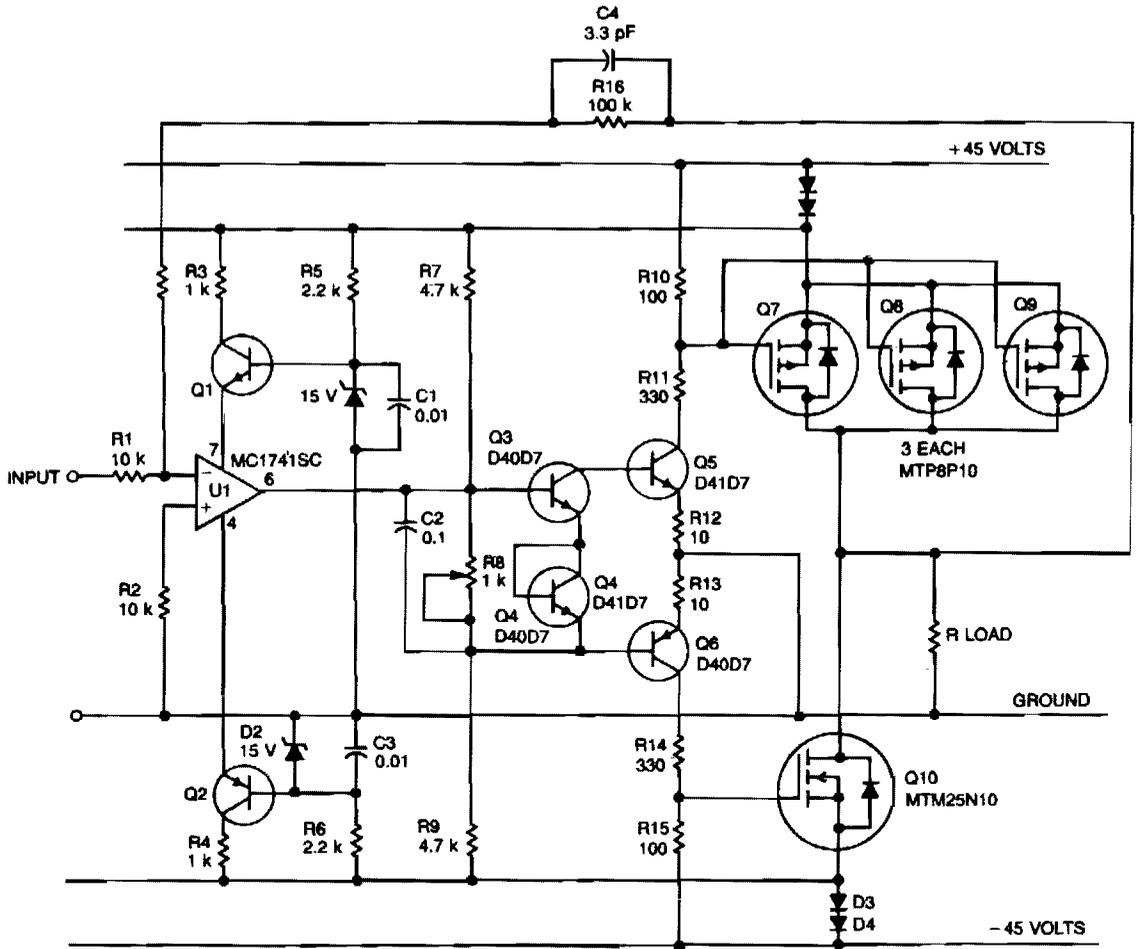

Copyright of Motorola, Inc. Used by permission.


**Fig. 72-1**

This audio amplifier design approach employs TMOS Power FETs operating in a complementary common-source configuration. They are biased to cutoff, then turn on very quickly when a signal is applied. The advantage of this approach is that the output stage is very stable from a thermal point of view.

U1 is a high slew-rate amp that drives Q3, Q4, and Q6 (operating class AB) providing level transition for the output stage consisting of Q7, Q8, Q9, and Q10. The positive temperature coefficient of the TMOS device enables parallel operation of Q7, Q8, and Q9 and provides a higher power *complementary* device for Q10. These TMOS Power FETs must be driven from a low-source impedance of 100  $\Omega$ , in order to actually obtain high turn-on speeds.



## CLASS-D POWER AMPLIFIER

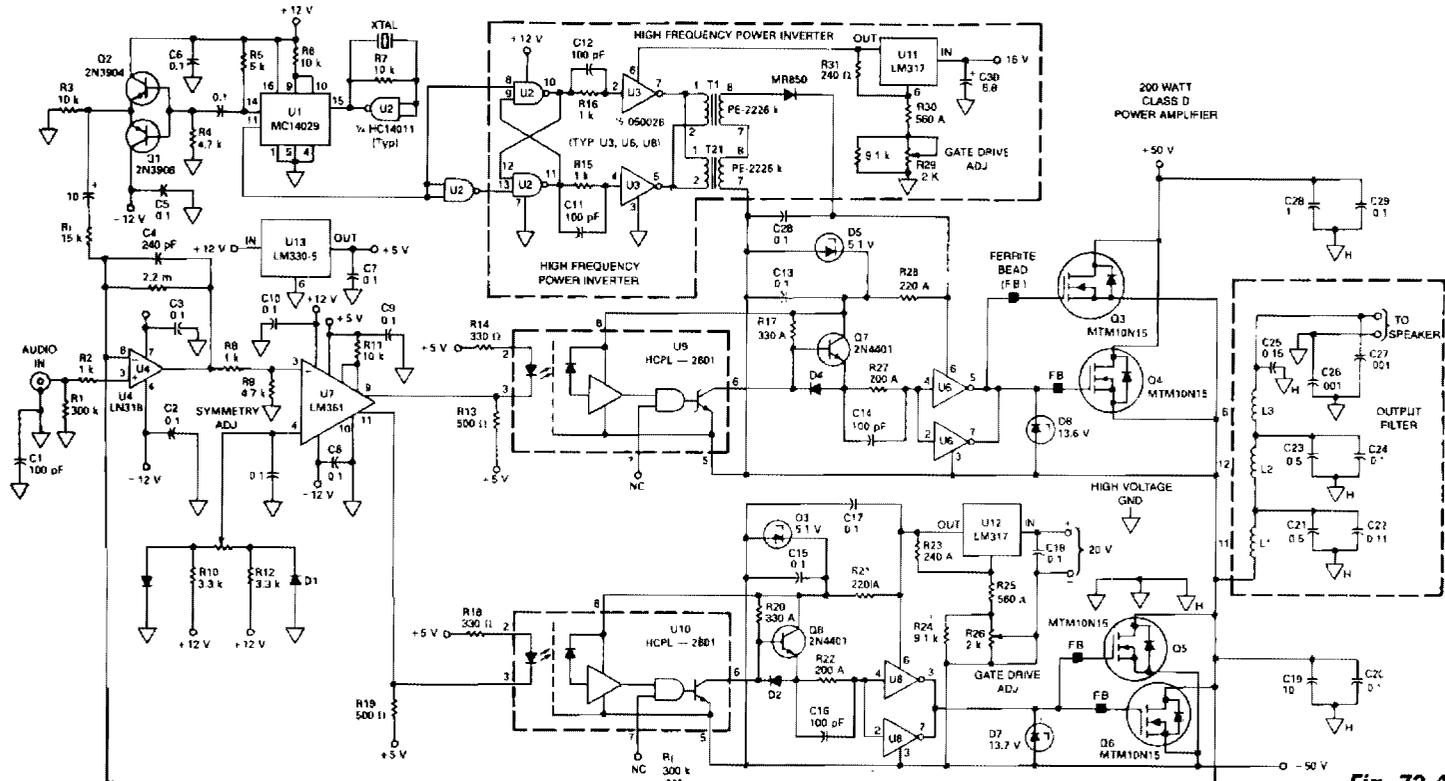

**Fig. 72-4**


Copyright of Motorola, Inc. Used by permission.

In this circuit, a 2-MHz clock is divided by eight in U1, providing a stable 250-kHz carrier. Q1 and Q2 buffer the clock and provide a low-impedance drive for op amp U4, which is a high-gain amplifier and integrator. U4 accepts audio inputs and converts the 250-kHz square wave into a triangular wave. The summed audio and triangular-wave signal is applied to the input of comparator U7, where it is compared with a dc reference to produce a pulse-width modulated signal at the output of U7.

The output devices switch between the +50 V and -50 V rails in a complementary fashion, driving the output filter that is a sixth-order Butterworth low-pass type, which demodulates the audio and attenuates the carrier and high frequency components. Feedback is provided  $R_7$ ; amplifier gain is  $R_7/R_1$ .

Specifications: 200 W continuous power into a 4- $\Omega$  load; 20 to 20 kHz frequency response +0.5, -1.0 dB at 200 W; THD, IMD 0.5% at 200 W; 1.5-V rms input for rated output; 69 dB S/N ratio, A weighting; 6.6-V ms slew rate.

## AUDIO POWER AMPLIFIER

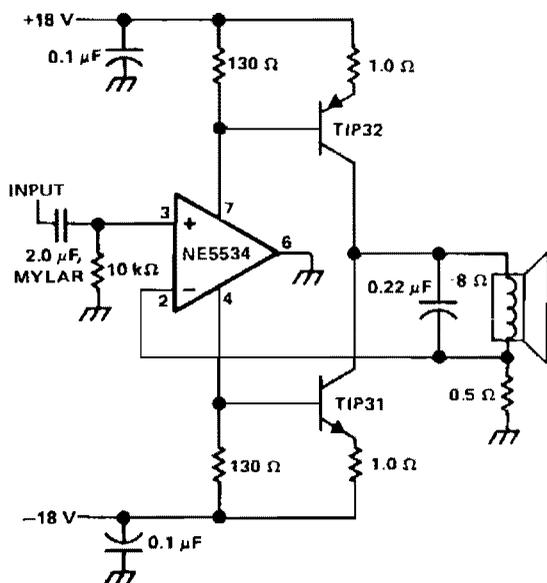

Reprinted by permission of Texas Instruments.

Fig. 72-5

The single speaker amplifier circuit uses current feedback, rather than the more popular voltage feedback. The feedback loop is from the junction of the speaker terminal and a 0.5-Ω resistor, to the inverting input of the NE5534. When the input to the amplifier is positive, the power supply supplies current through the TIP32 and the load to ground. Conversely, with a negative input, the TIP31 supplies current through the load to ground. The gain is set to about 15 (gain =  $\text{SPKR } 8 \Omega / 0.5 \Omega$  feedback). The 0.22-μF capacitor across the speaker rolls off its response beyond the frequencies of interest. Using the 0.22-μF capacitor specified, the amplifier current output is 3 dB down at 90 kHz where the speaker impedance is about 20 Ω. To set the recommended class A output collector current, adjust the value of either 130-Ω resistor. An output current of 50 to 100 mA will provide a good operating midpoint between the best crossover distortion and power dissipation.

## 6-W AUDIO AMPLIFIER WITH PREAMP


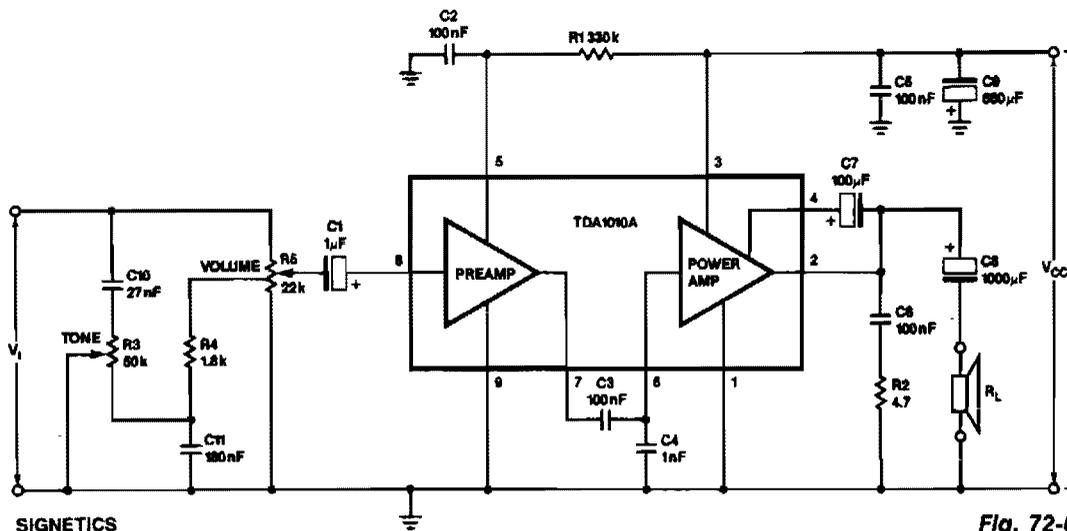


Fig. 72-6

This monolithic IC, class-B, audio amplifier circuit is a 6-W car radio amplifier for use with 4-Ω and 2-Ω load impedances.

## HYBRID POWER AMPLIFIER

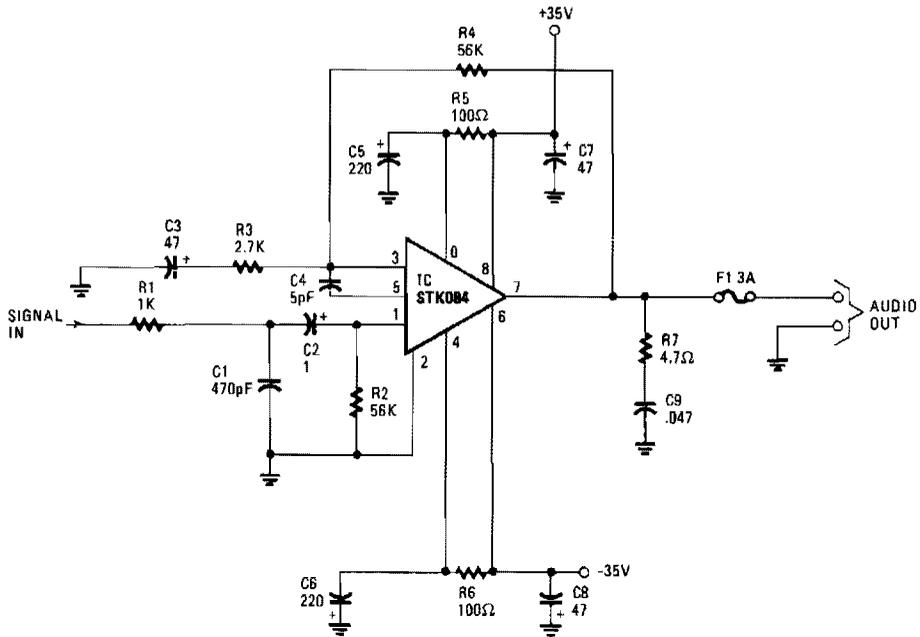


HANDS-ON ELECTRONICS

Fig. 72-7

The input is ac coupled to the amplifier through C2, which blocks dc signals that might also be present at the input. The R1/C1 combination forms a low-pass filter, which eliminates unwanted high-frequency signals by bypassing them to ground when they appear at the circuit input, which has an impedance of about 52  $\Omega$ . The gain of the amplifier is set at about 26 dB by resistors R3 and R4. The R5/C5/C7 combination on the positive supply and its counterpart R6/C6/C8 on the negative supply provides power-supply decoupling. R7 and C9 together prevent oscillation at the output of the amplifier. From that point, the amplifier's output signal is direct coupled to the speaker through a 3-A fuse, F1. The dc output of the amplifier at pin 7 is 0 V, so no dc current flows through the speaker. Should there be a catastrophic failure of the output stage, fuse F1, which should be a fast-acting type, prevents dc from flowing through the speaker.

## 20-W AUDIO AMPLIFIER

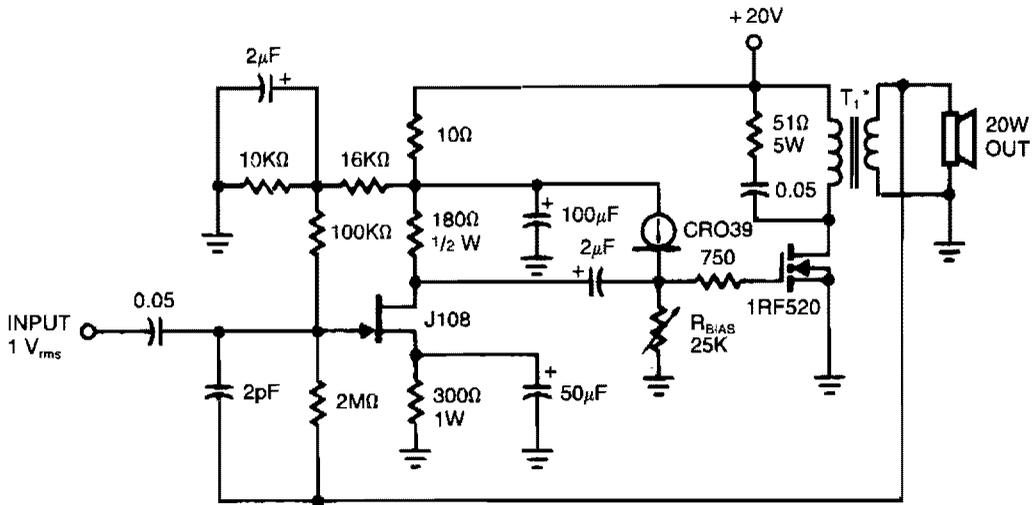

ALL RESISTORS 1/4 WATT, UNLESS NOTED  
\* TRIAD TY67A

SILICONIX

Fig. 72-8

This amplifier delivers 20 W into an 8-Ω load using a single IRF520 driving a transformer coupled output stage. This circuit is similar to the audio output stage used in many inexpensive radios and phonographs. Distortion is less than 5% at 10 W, using very little feedback (3%), with the IRF520 biased at 3 A.

# 73

## Fixed Power Supplies

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

- |                                   |  |
|-----------------------------------|--|
| Switching Power Supply            | Voltage-Controlled Current Source with |
| Low-Cost Low-Dropout Linear       | Grounded Source and Load               |
| Regulator                         | Charge Pool Power Supply               |
| Voltage Doubler                   | Bilateral Current Source               |
| Isolated Feedback Power Supply    | Power Converter                        |
| Hand-Held Transceiver Dc Adapter  | Positive Regulator with PNP Boost      |
| Low-Dropout 5-V Regulator         | Low Forward-Drop Rectifier Circuit     |
| Dual-Tracking Regulator           | Safe Constant-Current Source           |
| + 15 V 1-A Regulated Power Supply | Low-Cost 3-A Switching Regulator       |
| - 15 V 1-A Regulated Power Supply | 50-W Off-Line Switching Power Supply   |
| 12-Vdc Battery-Operated 120-Vac   | Efficient Negative Voltage Regulator   |
| Power Source                      | 5 V-to-Isolated 5 V at 20 mA Converter |
| Simple Power Supply               | Positive Regulator with NPN and        |
| General-Purpose Power Supply      | PNP Boost                              |
| Low-Power Inverter                | High-Current Inductorless Switching    |
| Three-Rail Power Supply           | Regulator                              |
| Programmable Power Supply         | Slow Turn-On 15-V Regulator            |
| Triac-Controlled Voltage Doubler  | Ac Voltage Regulator                   |
| High-Stability 10-V Regulator     | Uninterruptable +5 V Supply            |

## SWITCHING POWER SUPPLY


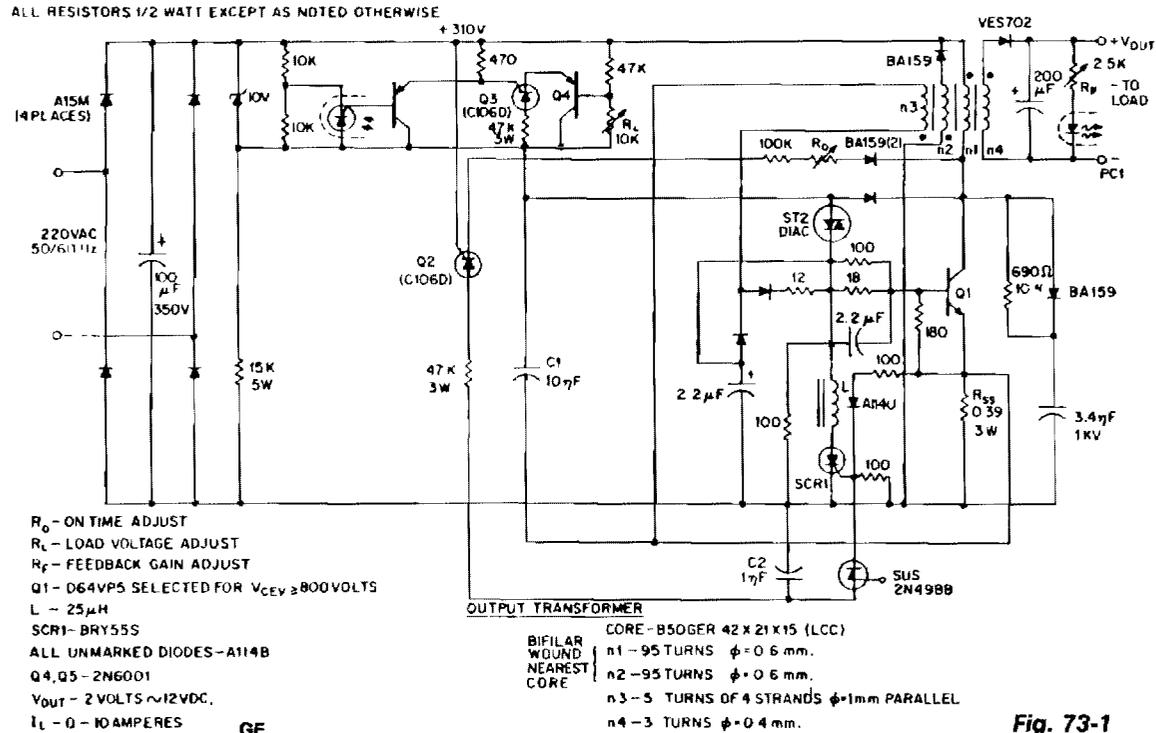


Fig. 73-1

This low-voltage high-current output, switching dc power supply is running off the 220-Vac input. In this circuit, an ST2 diac relaxation oscillator, Q3, C1, and the diac, initiates conduction of the output switching transistor Q1, the on-time of which is maintained constant by a separate timing/commutation network consisting of Q2, C2, SUS, and SCR 1. The output voltage, consequently, is dependent on the duty cycle. To compensate for unwanted variations of output voltage because of input voltage or load resistance fluctuations, an H11C wired as a linear-model unilateral PNP transistor in a stable differential amplifier configuration is connected into the galvanically isolated negative-feedback loop. The loop determines the duty cycle and hence the output voltage. Of further interest in this circuit is the use of several low-current, high-voltage, 400V  $V_{DRM}$  thyristors (Q2, Q3,) which are also used as pnp remote-base transistors. Short-circuit protection is assured by coupling Q1 collector-current feedback into the turn-off circuitry via  $R_{SS}$ .

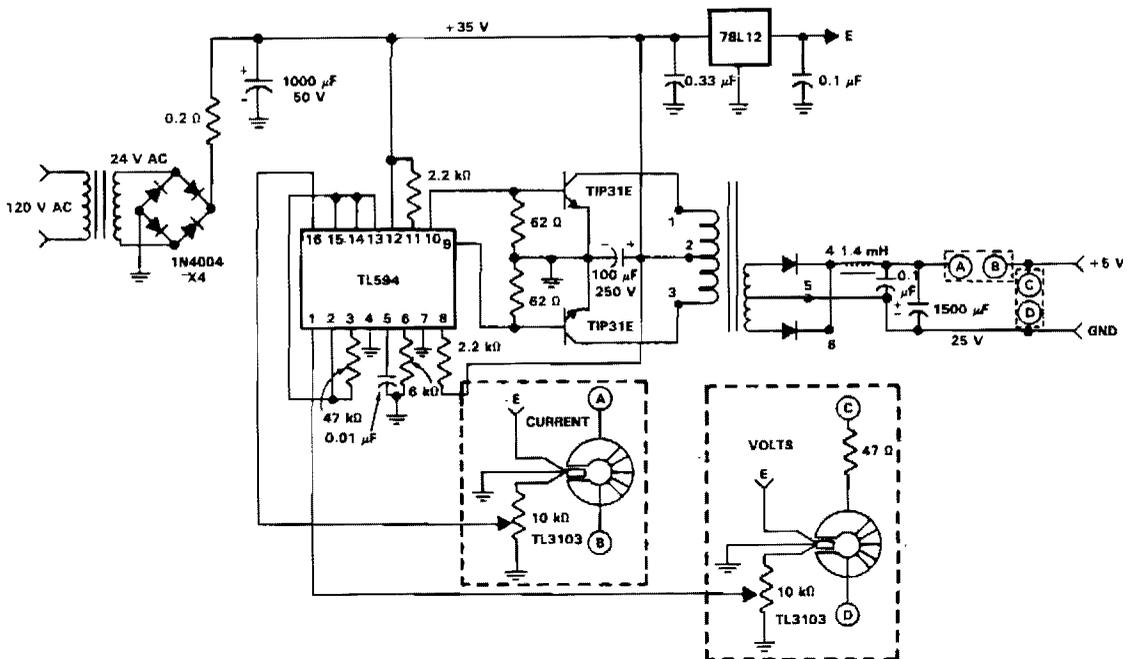

## ISOLATED FEEDBACK POWER SUPPLY




Reprinted by permission of Texas Instruments.

**Fig. 73-4**


Figure 73-4 is a power supply circuit using the isolated feedback capabilities of the TL3103 for both current and voltage sensing. This supply is powered from the ac power line and has an output of 5 V at 1.5 A. Both output voltage and current are sensed and the error voltages are applied to the error amplifiers of the TL594 PWM control IC. The 24-V transformer produces about 35 V at the 1000- $\mu$ F filter capacitor. The 20-kHz switching frequency is set by the 6-K $\Omega$  resistor and the 0.01- $\mu$ F capacitor on pins 6 and 5, respectively. The TL594 is set for push-pull operation by typing pin 13 high. The 5-V reference on pin 14 is tied to pin 15, which is the reference or the current error amplifier. The 5-V reference is also tied to pin 2 which is the reference for the output voltage error amplifier. The output voltage and current limit are set by adjustment of the 10-K $\Omega$  pots in the TL3103 error-sensing circuits. A pair of TIP31E npn transistors are used as switching transistors in a push-pull circuit.

## HAND-HELD TRANSCEIVER DC ADAPTER

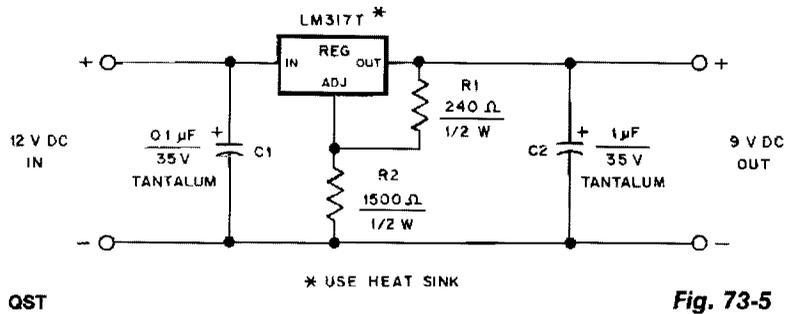

This dc adapter provides a regulated 9-V source for operating a Kenwood TR-2500 hand-held transceiver in the car. The LM317T's mounting tab is electrically connected to its output pin, so take this into account as you construct your version of the adapter. The LM317T regulator dissipates 2 or 3 W in this application, so mount it on a 1- $\times$ -2-inch piece of 1/8-inch-thick aluminum heatsink.

## LOW-DROPOUT 5 V REGULATOR

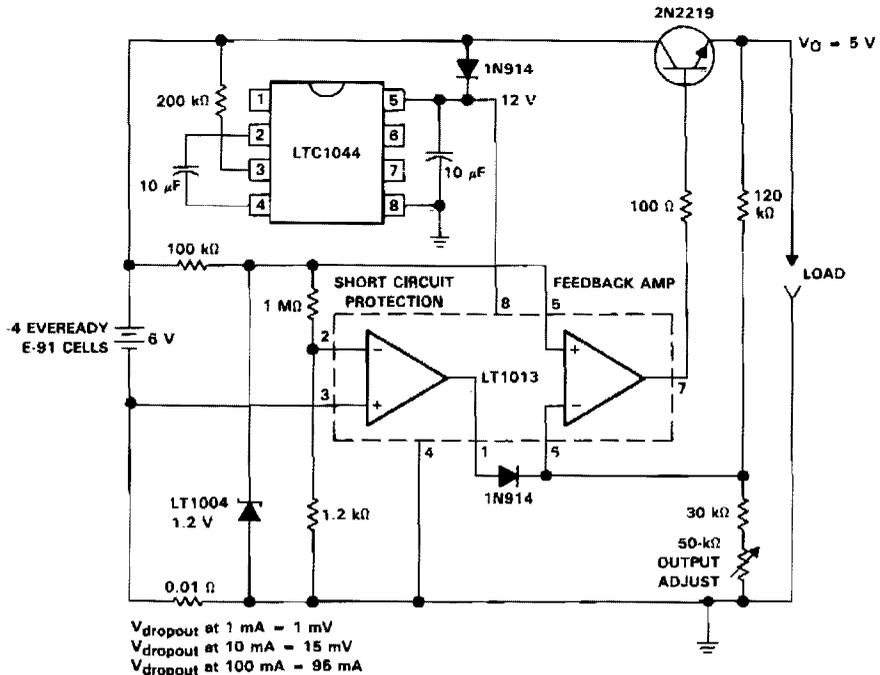

Reprinted by permission of Texas Instruments.

Fig. 73-6

## DUAL-TRACKING REGULATOR

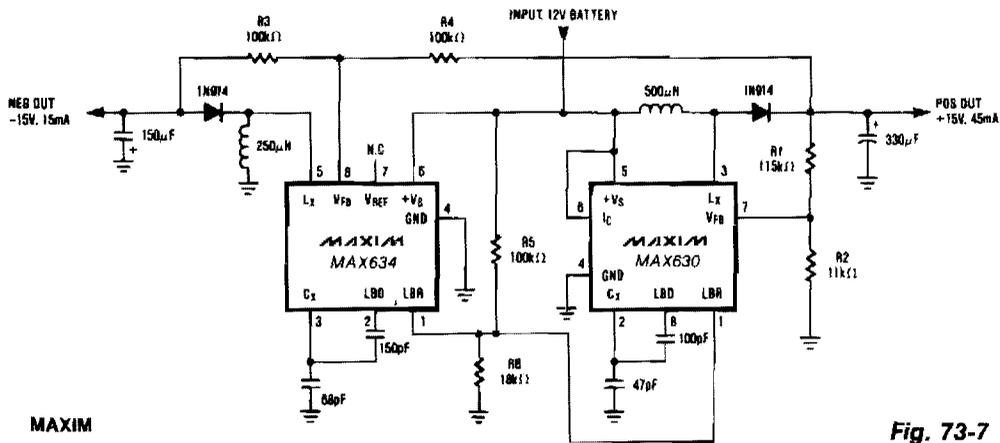


Fig. 73-7

A MAX634 inverting regulator is combined with a MAX630 to provide a dual tracking  $\pm 15$  output from a 12-V battery. The reference for the  $-15$  V output is derived from the positive output via  $R_3$  and  $R_4$ . Both regulators are set to maximize output power at low battery voltages by reducing the oscillator frequency, via LBR, when  $V_{BATT}$  falls to 8.5 V.

## + 15 V 1-A REGULATED POWER SUPPLY


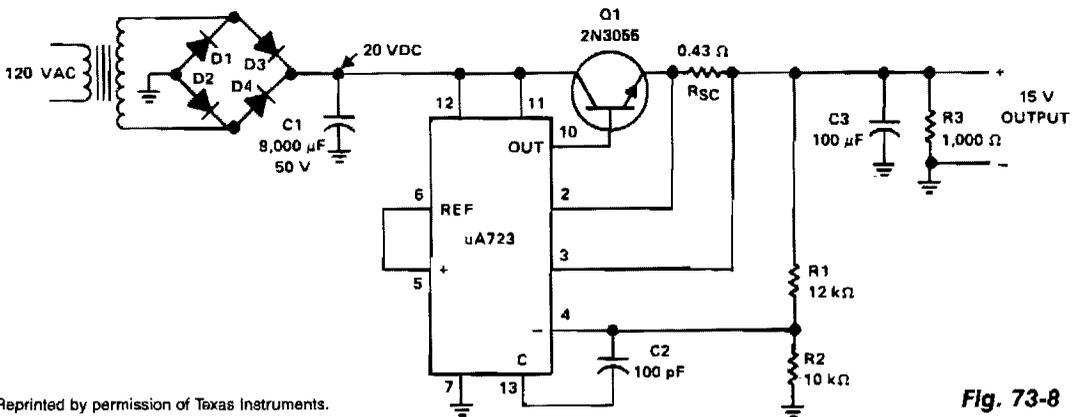


Fig. 73-8

The supply receives +20 Vdc from the rectifier/filter section. This is applied to pins 11 and 12 of the  $\mu$ A723, as well as to the collector of the 2N3055 series-pass transistor. The output voltage is sampled through  $R_1$  and  $R_2$ , providing about 7 V with respect to ground at pin 4. The reference terminal at pin 6 is tied directly to pin 5, the noninverting input of the error amplifier. For fine trimming the output voltage, a potentiometer can be installed between  $R_1$  and  $R_2$ . A 100-pF capacitor from pin 13 to pin 4 furnishes gain compensation for the amplifier.

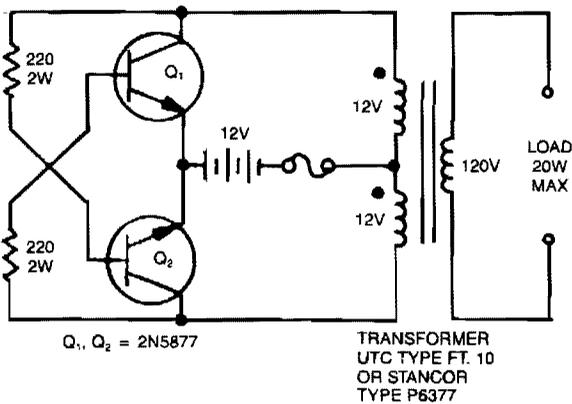

## 12-VDC BATTERY-OPERATED 120-VAC POWER SOURCE




EDN

Fig. 73-10

If Q<sub>1</sub> is faster and has a higher gain than Q<sub>2</sub>, it will turn on first when you apply the input power and will hold Q<sub>2</sub> off. Load current and transformer magnetizing current then flows in the upper half of the primary winding, and auto transformer action supplies the base drive until the transformer saturates. When that action occurs, Q<sub>1</sub> loses its base drive. As it turns off, the transformer voltages reverse, turning Q<sub>2</sub> on and repeating the cycle. The output frequency depends on the transformer iron and input voltage, but not on the load. The frequency will generally range between 50 to 60 Hz with a 60-Hz transformer and car battery or equivalent source. The output voltage depends on turns ratio and the difference between input voltage and transistor saturation voltage. For higher power, use larger transformers and transistors. This type of inverter normally is used in radios, phonographs, hand tools, shavers, and small fluorescent lamps. It will not work with reactive loads (motors) or loads with high inrush currents, such as coffee pots, frying pans, and heaters.

A simple 120 V; 24 V, center-tapped control transformer and four additional components can do the job. This circuit outputs a clean 200 V pk-pk square wave at 60 Hz and can supply up to 20 W. The circuit is self-starting and free-running.

## SIMPLE POWER SUPPLY

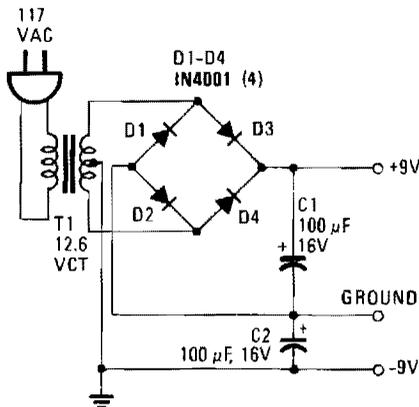


HANDS-ON ELECTRONICS

Fig. 73-11

This power supply delivers plus and minus 9 V to replace two 9-V batteries. The rectifier circuit is actually two separate full-wave rectifiers fed from the secondary of the transformer. One full-wave rectifier is composed of diodes D1 and D2, which develop +9 V, and the other is composed of D3 and D4, which develop -9 V.

Each diode from every pair rectifies 6.3 Vac, half the secondary voltage, and charges the associated filter capacitor to the peak value of the ac waveform,  $6.3 \times 1.414 = 8.9$  V. Each diode should have a PIV, Peak Inverse Voltage, rating that is at least twice the peak voltage from the transformer,  $2 \times 8.9 = 18$  V. The 1N4001 has a PIV of 50 V.

## GENERAL-PURPOSE POWER SUPPLY

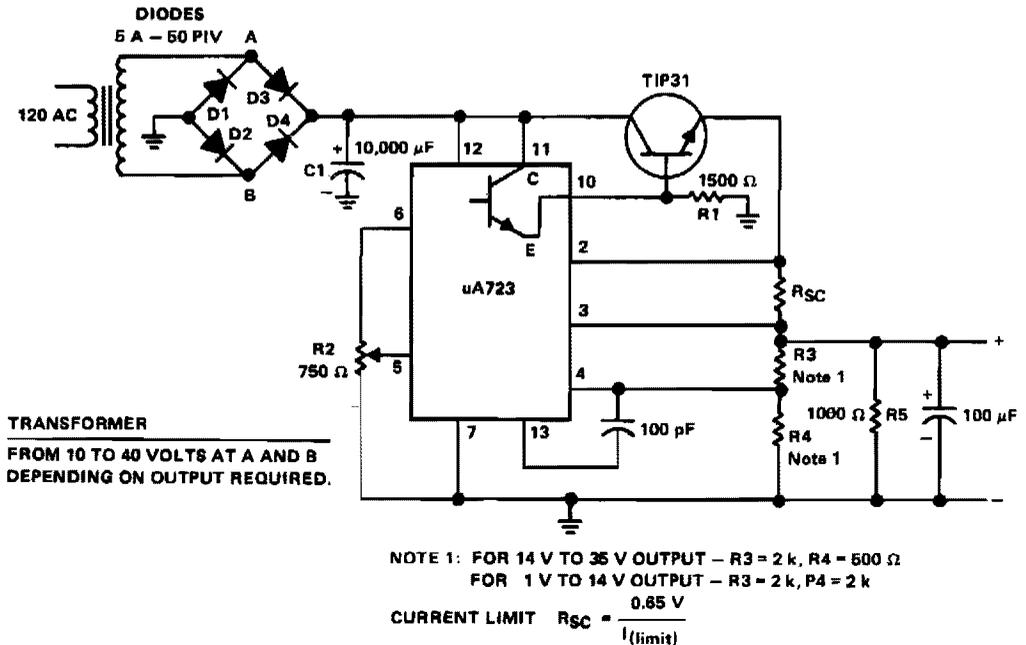

Reprinted by permission of Texas Instruments.

**Fig. 73-12**

The supply 6-66 can be used for supply output voltages from 1 to 35 V. The line transformer should be selected to give about 1.4 times the desired output voltage from the positive side of filter capacitor C1 to ground. Potentiometer R2 sets the output voltage to the desired value by adjusting the reference input.  $R_{SC}$  is the current limit set resistor. Its value is calculated as:

$$R_{SC} = \frac{0.65 \text{ V}}{I_L}$$

For example, if the maximum current output is to be 1 A,  $R_{SC} = 0.65/1.0 = 0.65 \Omega$ . The 1-K $\Omega$  resistor,  $R_S$ , is a light-loaded resistor designed to improve the no-load stability of the supply.

## LOW-POWER INVERTER

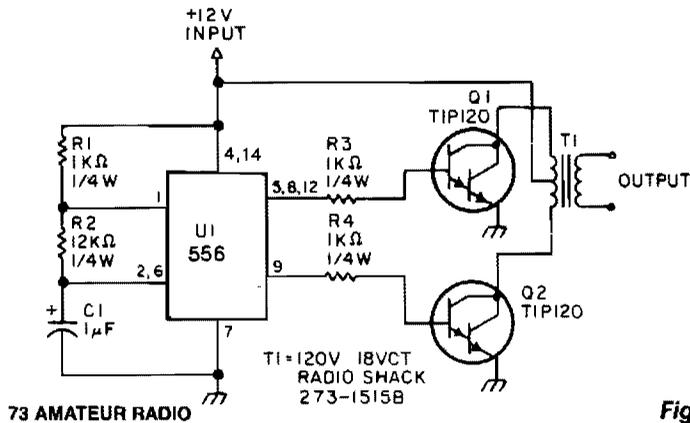


Fig. 73-13

This low-power inverter uses only 9 parts and turns 10 to 16 Vdc into 60-Hz, 115-V square-wave power to operate ac equipment up to 25 W. The first section of the 556 timer chip is wired as an astable oscillator with R2 and C1 setting the frequency. The output is available at pin 5. The second section is wired as a phase inverter. That output is available at pin 9. Resistors R3 and R4 keep output transistors Q1 and Q2 from loading down the oscillator. The two transistors drive the transformer push-pull fashion. When one transistor is biased-on, the other is cut-off. The transformer is a 120 V/18 VCT unit that is connected backwards, so that it steps the voltage up rather than down. Oscillator circuit U1, R1, R2, and C1 operates from about 4 to 16 V with a very stable output.

## THREE-RAIL POWER SUPPLY


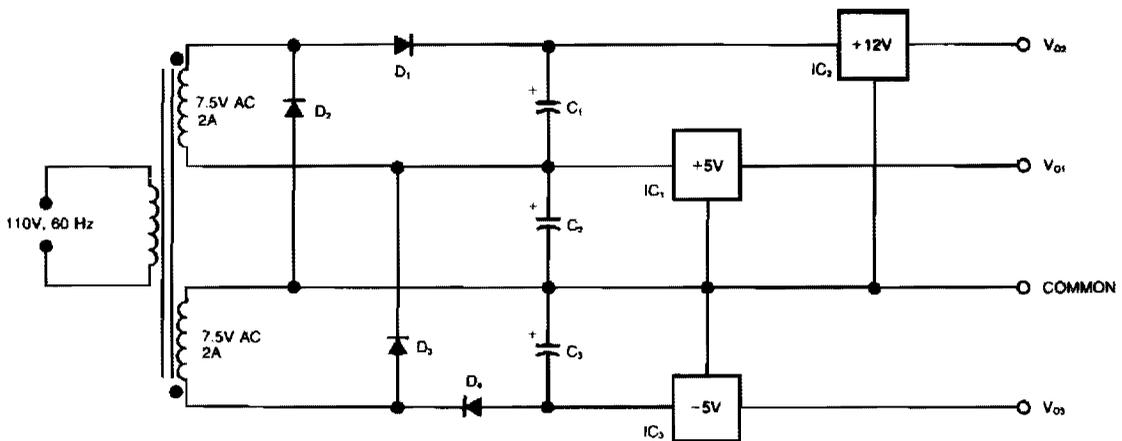


Fig. 73-14

## THREE-RAIL POWER SUPPLY (Cont.)

This circuit generates three supply voltages using a minimum of components. Diodes D2 and D3 perform full-wave rectification, alternately charging capacitor C2 on both halves of the ac cycle. On the other hand, diode D1 with capacitor C1, and diode D4 with capacitor C3 each perform half-wave rectification. The full- and half-wave rectification arrangement is satisfactory for modest supply currents drawn from  $-5$  and  $+12$ -V regulators IC3 and IC2. You can use this circuit as an auxiliary supply in an up-based instrument, for example, and avoid the less attractive alternatives of buying a custom-wound transformer, building a more complex supply, or using a secondary winding, say 18 Vac, and wasting power in the 5-V regulators.

## PROGRAMMABLE POWER SUPPLY

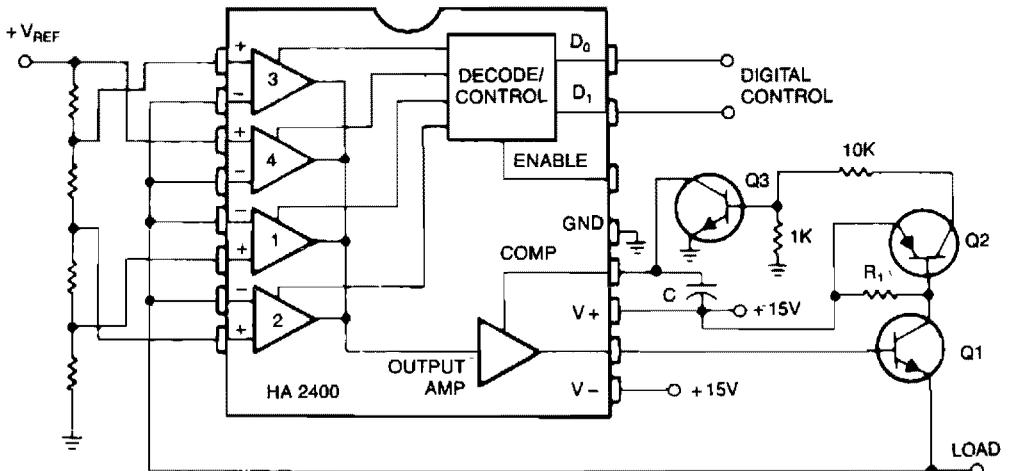


HARRIS

Fig. 73-15

Many systems require one or more relatively low-current voltage sources which can be programmed to a few predetermined levels. The circuit shown above produces positive output levels, but could be modified for negative or bipolar outputs. Q1 is the series regulator transistor, selected for the required current and power capability. R1, Q2, and Q3 form an optional short circuit protection circuit, with R1 chosen to drop about 0.7 V at the maximum output current. The compensation capacitor, C, should be chosen to keep the overshoot, when switching, to an acceptable level.


### TRIAC-CONTROLLED VOLTAGE DOUBLER

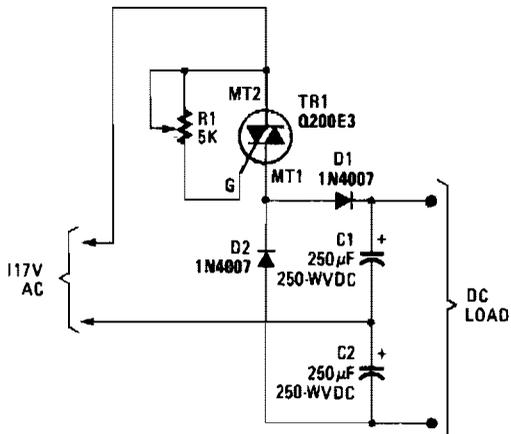

HANDS-ON ELECTRONICS

Fig. 73-16


### HIGH STABILITY 10-V REGULATOR

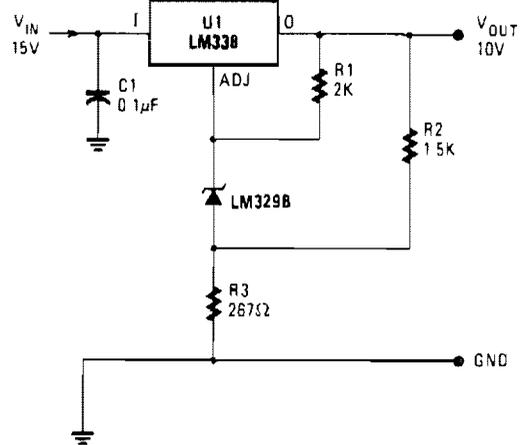

POPULAR ELECTRONICS

Fig. 73-17
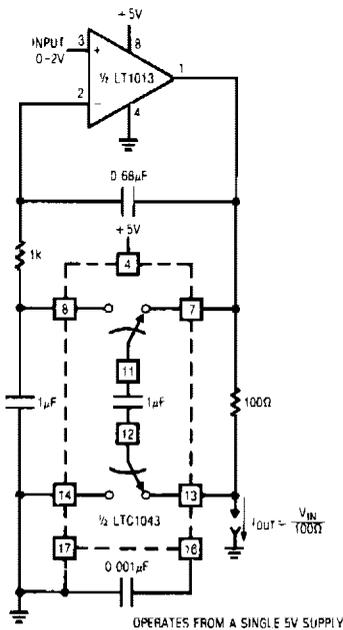
### VOLTAGE-CONTROLLED CURRENT SOURCE WITH GROUNDED SOURCE AND LOAD




LINEAR TECHNOLOGY CORP.

Fig. 73-18

This is a simple, precise voltage-controlled current source. Bipolar supplies will permit bipolar output. Configurations featuring a grounded voltage-control source and a grounded load are usually more complex and depend upon several components for stability. In this circuit, accuracy and stability almost entirely depend upon the 100-Ω shunt.

## CHARGE POOL POWER SUPPLY

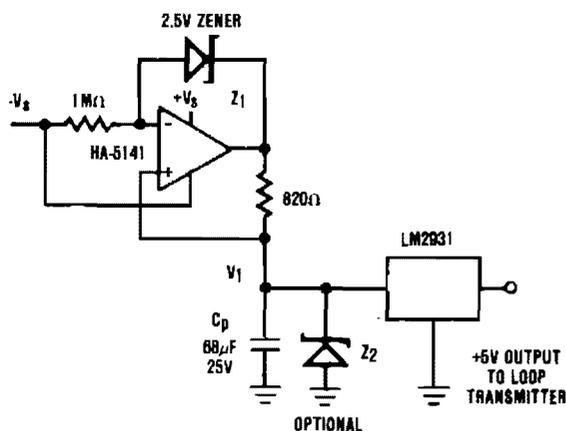

HARRIS


Fig. 73-19

It is usually desirable to have the remote transmitter of a 4 to 20 mA current loop system powered directly from the transmission line. In some cases, this is not possible because of the high-power requirements set by the remote sensor/transmitter

system. In these cases, an alternative to the separate power supply is still possible. If the remote transmitter can be operated in a pulsed mode where it is active only long enough to perform its function, then a charge pool power supply can still allow the transmitter to be powered directly by the current loop. In this circuit, constant current  $I_1$  is supplied to the charge pool capacitor,  $C_P$ , by the HA-5141 (where  $I_1 = 3 \text{ mA}$ ). The voltage  $V_1$  continues to rise until the output of the HA-5141 approaches  $+V_s$  or the optional voltage limiting provided by Z2. The LM2931 voltage regulator supplies the transmitter with a stable +5 V supply from the charge collected by  $C_P$ . Available power supply current is determined by the duration, allowable voltage droop on  $C_P$ , and required repetition rate. For example, if  $V_1$  is allowed to droop 4.4 V and the duration of operation is 1 ms, the available power supply current is approximately:

$$= C_P \frac{dV_1}{dt} = 68\mu\text{F} \times \frac{4.4 \text{ V}}{1 \text{ ms}} = 30 \text{ mA}$$

## BILATERAL CURRENT SOURCE

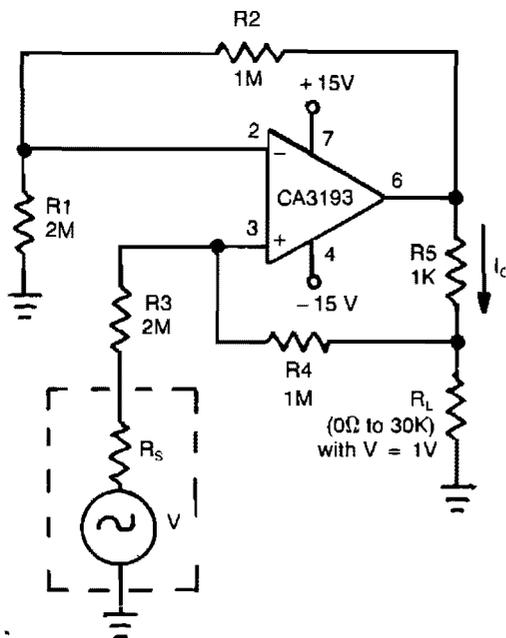

ALL RESISTORS ARE 1%  
ALL RESISTANCE VALUES ARE IN OHMS  
IF  $R_1 = R_3$  AND  $R_2 \approx R_4 + R_5$  THEN

$I_L$  IS INDEPENDENT OF VARIATIONS IN  $R_L$   
FOR  $R_L$  VALUES OF  $0\Omega$  TO  $30\text{K}\Omega$  WITH  $V = 1\text{V}$


$$I_L = \frac{V R_4}{R_3 R_5} = \frac{V \cdot 1\text{M}}{(2\text{M})(1\text{K})} = \frac{V}{2\text{K}} = 500\mu\text{A}$$

GE/RCA


Fig. 73-20

This circuit uses a CA3193 precision op amp to deliver a current independent of variations in  $R_L$ . With  $R_1$  set equal to  $R_3$ , and  $R_2$  approximately equal to  $R_4 + R_5$ , the output current,  $I_L$ , is:  $V_{IN} (R_4)/(R_3) (R_5)$ . 500- $\mu\text{A}$  load current is constant for load values from 0 to 3  $\Omega$ .


## POWER CONVERTER

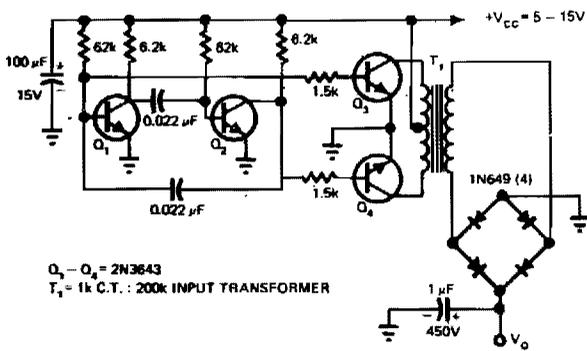

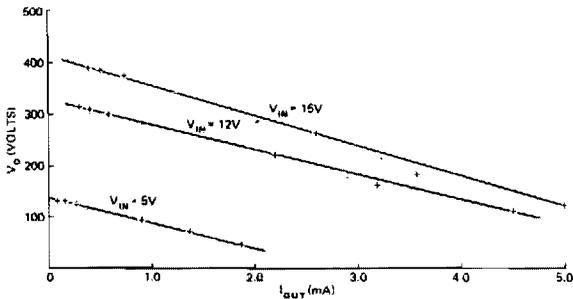$Q_1 - Q_2 = 2N3643$   
 $T_1 = 1k C.T. : 200k INPUT TRANSFORMER$



INPUT AND OUTPUT PARAMETERS FOR LOW COST POWER CONVERTER						
$V_{IN} = 5V$						
$R_L$ (OHMS)	$V_O$ (VOLTS)	$I_O$ (mA)	$I_{IN}$ (mA)	$P_O$ (W)	$P_{IN}$ (W)	EFF (%)
0	160	0	22	0	0.11	—
1 M	130	0.13	25	0.017	0.125	14
750k	130	0.17	26	0.022	0.130	17
510k	125	0.25	27	0.031	0.135	23
100k	90	0.90	42	0.081	0.210	39
51k	70	1.37	60	0.096	0.300	32
24k	45	1.88	60	0.085	0.300	38
$V_{IN} = 12V$						
$R_L$ (OHMS)	$V_O$ (VOLTS)	$I_O$ (mA)	$I_{IN}$ (mA)	$P_O$ (W)	$P_{IN}$ (W)	EFF (%)
0	415	0	60	0	0.720	—
1 M	315	0.32	65	0.10	0.78	13
750k	310	0.41	65	0.13	0.78	17
510k	300	0.59	70	0.18	0.84	21
100k	220	2.20	100	0.48	1.20	40
51k	165	3.24	120	0.54	1.44	38
24k	110	4.58	140	0.50	1.68	30
$V_{IN} = 15V$						
$R_L$ (OHMS)	$V_O$ (VOLTS)	$I_O$ (mA)	$I_{IN}$ (mA)	$P_O$ (W)	$P_{IN}$ (W)	EFF (%)
0	520	0	80	0	1.2	—
1 M	390	0.39	80	0.15	1.2	13
750k	385	0.51	85	0.196	1.28	15
510k	375	0.74	90	0.28	1.35	21
100k	260	2.6	120	0.68	1.8	38
51k	180	3.57	140	0.65	2.1	31
24k	120	5.0	160	0.60	2.4	25

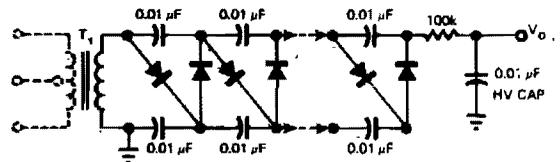


- ADD ADDITIONAL STAGES AS REQUIRED
- DIODES ARE 1N649 OR EQUIVALENT
- CAPACITORS ARE CERAMIC DISC 1 kV

EDN

Fig. 73-21

This circuit consists of an astable multivibrator driving a push-pull pair of transistors into the transformer primary. The multivibrator frequency should equal 1 or 2 kHz. For higher dc voltages, voltage multipliers on the secondary circuit have been used successfully to generate 10 kV from a 40-stage multiplier like the one shown.

## POSITIVE REGULATOR WITH PNP BOOST

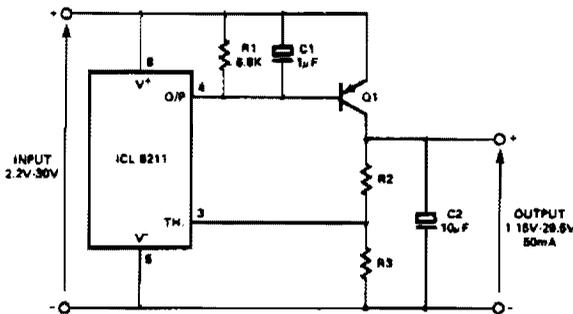

INTERSIL

**Fig. 73-22**


The IC8211 provides the voltage reference and regulator amplifier, while Q1 is the series pass transistor. R1 defines the output current of the IC8211, while C1 and C2 provide loop stability and also act to suppress feedthrough of input transients to the output supply. R2 and R3 determine the output voltage as follows:

output supply. R2 and R3 determine the output voltage as follows:

$$V_{OUT} = 1.5 \times \frac{R_2 + R_3}{R_3}$$

In addition, the values of R2 and R3 are chosen to provide a small amount of standing current in Q1, which gives additional stability margin to the circuit. Where accurate setting of the output voltage is required, either R2 or R3 can be made adjustable. If R2 is made adjustable, the output voltage will vary linearly with the shaft angle; however, if the potentiometer wiper was to open the circuit, the output voltage would rise. In general, therefore, it is better to make R3 adjustable, since this gives fail-safe operation.

## LOW FORWARD-DROP RECTIFIER CIRCUIT

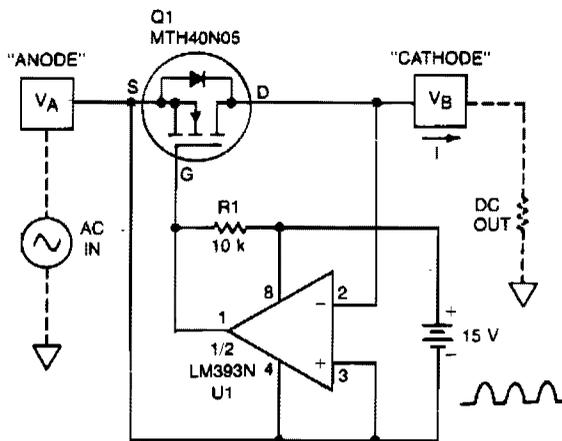


Copyright of Motorola, Inc. Used by permission.

**Fig. 73-23**

A TMOS power FET, Q1, and an LM393 comparator provide a high-efficiency rectifier circuit. When  $V_A$  exceeds  $V_B$ , U1's output becomes high and Q1 conducts. Conversely, when  $V_B$  exceeds  $V_A$ , the comparator output becomes low and Q1 does not conduct.

The forward drop is determined by Q1's on resistance and current  $I$ . The MTH40N05 has an on resistance of  $0.028 \Omega$ ; for  $I = 10 \text{ A}$ , the forward drop is less than  $0.3 \text{ V}$ . Typically, the best Schottky diodes do not even begin conducting below a few hundred mV.

### SAFE CONSTANT-CURRENT SOURCE

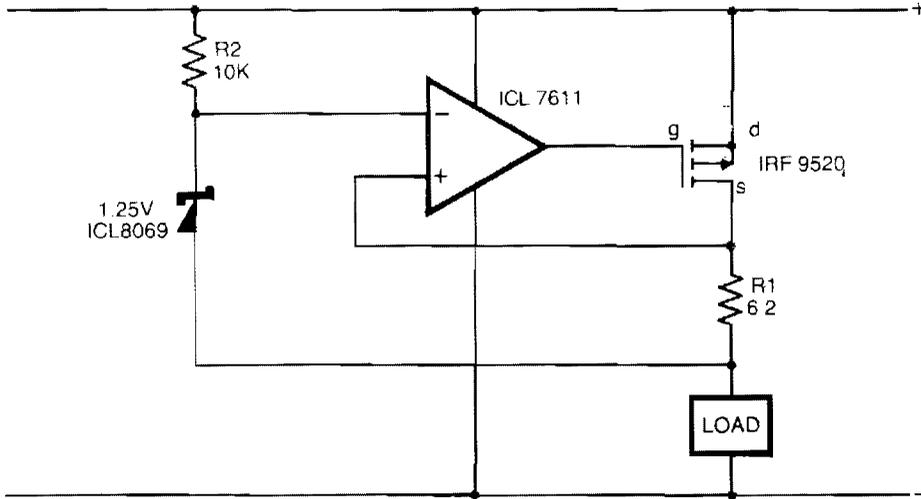


ELECTRONIC ENGINEERING

Fig. 73-24

In the circuit shown, a CMOS op amp controls the current through a p-channel HEXFET power transistor to maintain a constant voltage across R1. The current is given by:  $I = V_{REF}/R1$ . The advantages of this configuration are: (a) in the event of a component failure, the load current is limited by R1; and (b) the overhead voltage needed by the op amp and the HEXFET is extremely low.


### LOW-COST 3-A SWITCHING REGULATOR

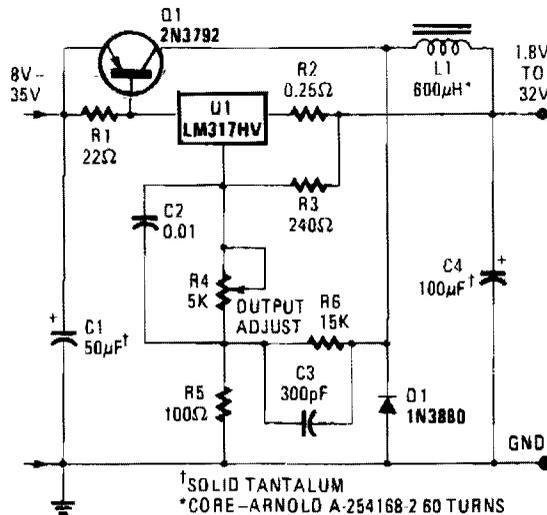

POPULAR ELECTRONICS

Fig. 73-25

## 50-W OFF-LINE SWITCHING POWER SUPPLY

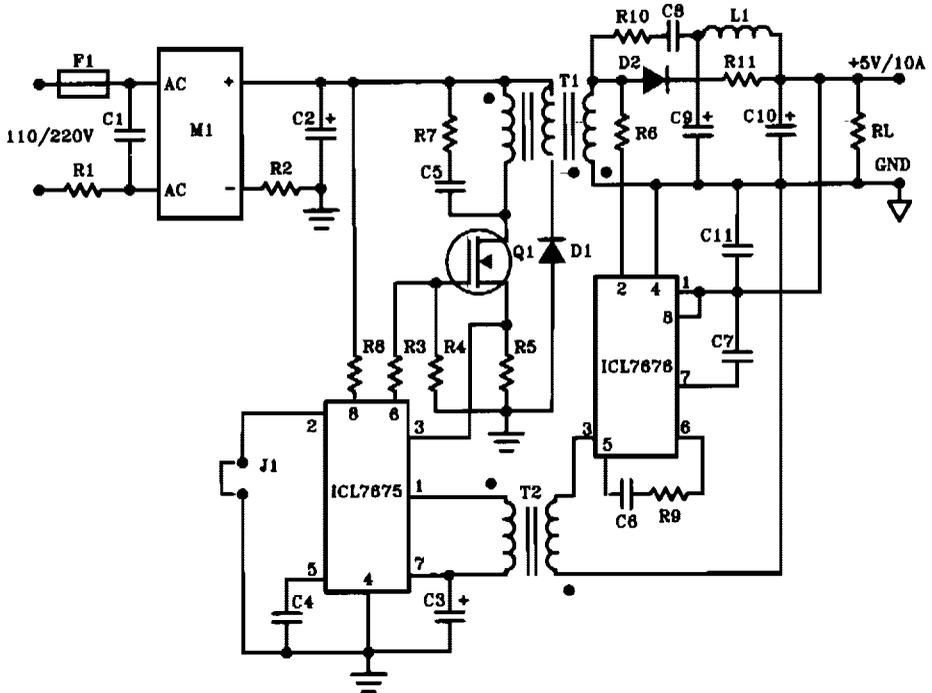

**Component Values Table**


C1	0.022 $\mu$ F/400V	R1	100 $\Omega$ at 25°C	L1	25 $\mu$ H
C2	470 $\mu$ F/250V	R2	1 $\Omega$ /1W	D1	1N4937
C3	470 $\mu$ F/16V	R3	10 $\Omega$ /0.25W	D2	MBR1035
C4	220 pF/100V	R4	100 k $\Omega$ /0.25W	T1	L <sub>p</sub> = 9 mH, n = 1:15
C5	470 pF/500V	R5	0.33 $\Omega$ /1W	T2	50 $\mu$ H, n = 1:3
C6	2200 pF/500V	R6	10 k $\Omega$ /0.25W	F1	Fuse 1 A/SB
C7	270 pF/500V	R7	390 $\Omega$ /2W	M1	Diode Bridge
C8	39 pF/500V	R8	22 k $\Omega$ /10W	Q1	BUZ80A/IXTP4N80 (220VAC)
C9	11,000 $\mu$ F/6.3V	R9	68 $\Omega$ /0.25W	Q1	GE 1RF823 (110VAC)
C10	10 $\mu$ F/16V	R10	10 $\Omega$ /0.5W		
C11	0.047 $\mu$ F/10V	R11	3.3 $\Omega$ /0.5W		
		RL	5 $\Omega$ /10W		

INTERSIL

Fig. 73-26

The schematic shows a 50-W power supply with a 5-V 10-A output. It is a flyback converter operating in the continuous mode. The circuit features a primary side and secondary side controller will full-protection from fault conditions such as overcurrent. After the fault condition has been removed, the power supply will enter the soft-start cycle before recommencing normal operation.

## EFFICIENT NEGATIVE VOLTAGE REGULATOR

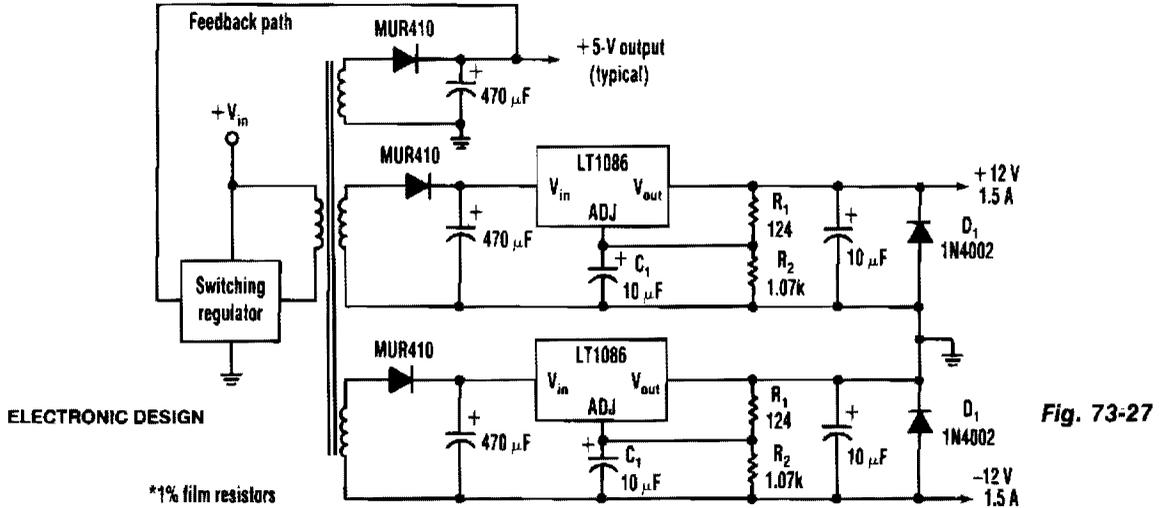


One way to provide good negative-voltage regulation is with a low-dropout positive-voltage regulator operating from a well-isolated secondary winding of switch-mode circuit transformer. The technique works with any positive-voltage regulator, although highest efficiency occurs with low-dropout types.

Under all loading conditions, the minimum voltage difference between the regulator  $V_{IN}$  and  $V_{OUT}$  pins must be at least 1.5 V, the LT1086's low-dropout voltage. If this requirement isn't met, the output falls out of regulation. Two programming resistors,  $R_1$  and  $R_2$ , set the output voltage to 12 V, and the LT1086's servo the voltage between the output and its adjusting (ADJ) terminals to 1.25 V. Capacitor  $C_1$  improves ripple rejection, and protection diode  $D_1$  eliminates common-load problems.

Since a secondary winding is galvanically isolated, a regulator's 12 V output can be referenced to ground. Therefore, in the case of a negative-voltage output, the positive-voltage terminal of the regulator connects to ground, and the -12 V output comes off the anode of  $D_1$ . The  $V_{IN}$  terminal floats at 1.5 V or more above ground.

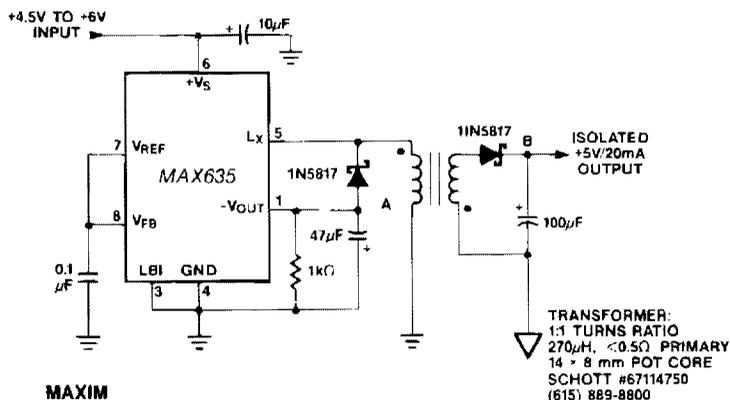
## 5 V-TO-ISOLATED 5 V AT 20 MA CONVERTER



## 5-V-TO-ISOLATED 5 V AT 20 MA CONVERTER (Cont.)

In this circuit, a negative output voltage dc-dc converter generates a  $-5\text{ V}$  output at pin A. In order to generate  $-5\text{ V}$  at point A, the primary of the transformer must fly back to a diode drop more negative than  $-5\text{ V}$ . If the transformer has a tightly coupled 1/1 turns ratio, there will be a  $5\text{ V}$  plus a diode drop across the secondary. The 1N5817 rectifies this secondary voltage to generate an isolated  $5\text{-V}$  output. The isolated output is not fully regulated since only the  $-5\text{ V}$  at point A is sensed by the MAX635.
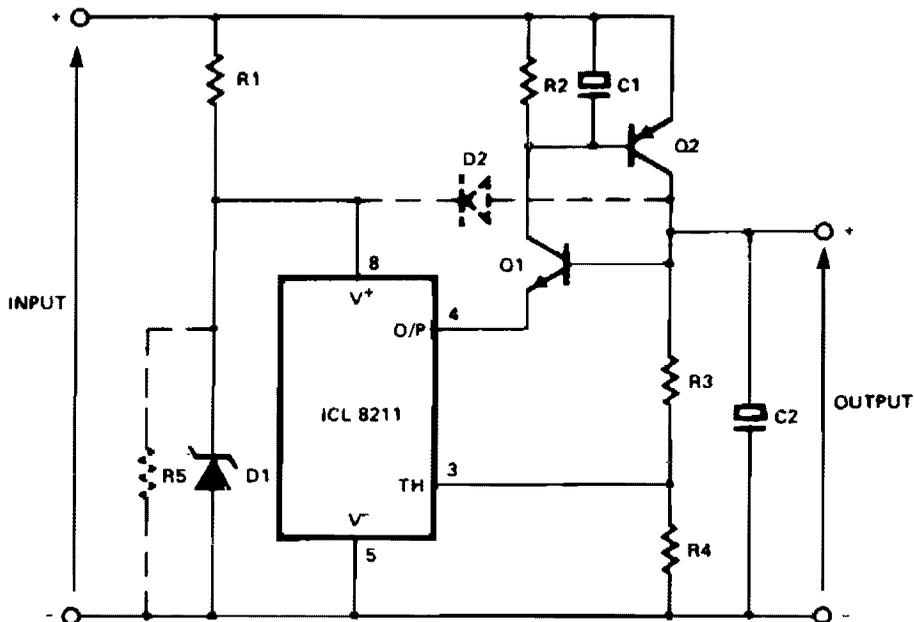
### POSITIVE REGULATOR WITH NPN AND PNP BOOST




INTERSIL

Fig. 73-29

In the circuit, Q1 and Q2 are connected in the classic SCR or thyristor configuration. Where higher input voltages or minimum component count are required, the circuit for thyristor boost can be used. The thyristor is running in a linear mode with its cathode as the control terminal and its gate as the output terminal. This is known as the remote base configuration.
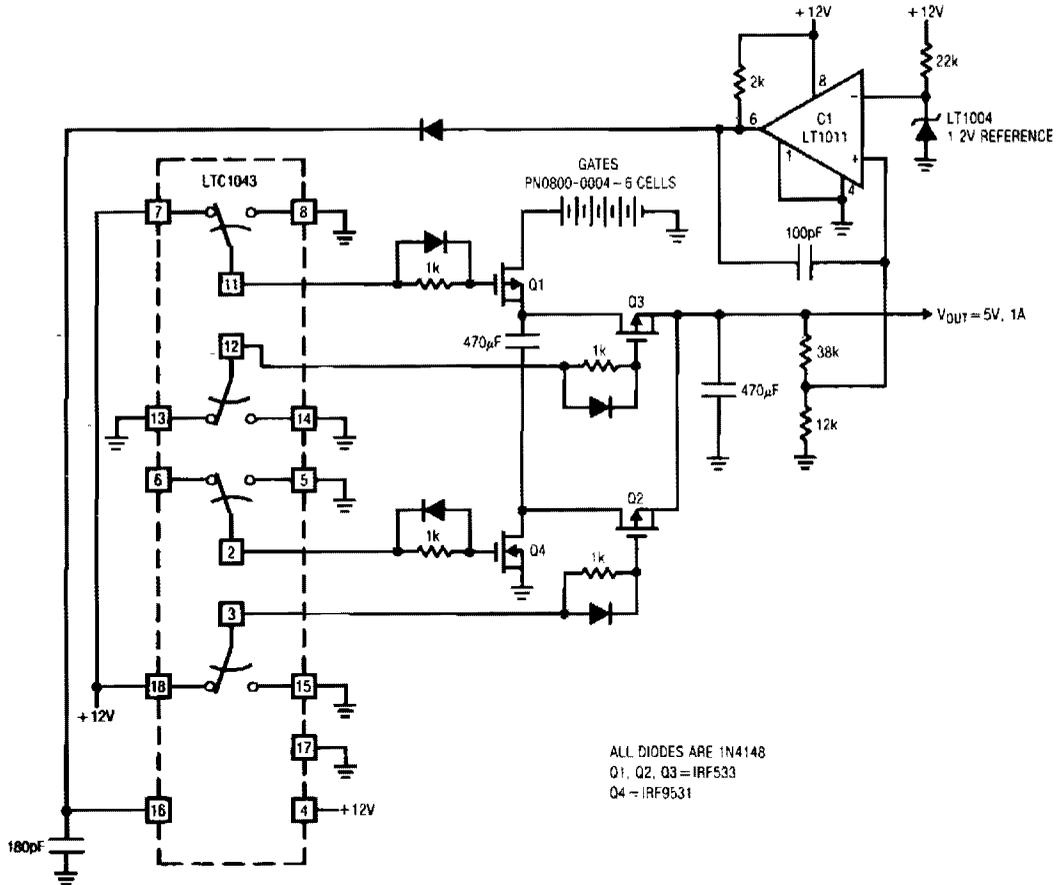
## HIGH-CURRENT INDUCTORLESS, SWITCHING REGULATOR




LINEAR TECHNOLOGY CORP.

**Fig. 73-30**

The LTC10432 switched-capacitor building block provides nonoverlapping complementary drive to the Q1 to Q4 power MOSFETs. The MOSFETs are arranged so that C1 and C2 are alternately placed in series and then parallel. During the series phase, the +12 V battery's current flows through both capacitors, charging them, and furnishing load current. During the parallel phase, both capacitors deliver current to the load. Q1 and Q2 receive similar drive from pins 3 and 11. The diode-resistor networks provide additional nonoverlapping drive characteristics, preventing simultaneous drive to the series-parallel phase switches. Normally, the output would be one-half of the supply voltage, but C1 and its associated components close a feedback loop, forcing the output to 5 V. With the circuit in the series phase, the output heads rapidly positive. When the output exceeds 5 V, C1 trips, forcing the LTC1043 oscillator pin, trace D, high; this truncates the LTC1043's triangular-wave oscillator cycle. The circuit is forced into the parallel phase and the output coasts down slowly, until the next LTC1043 clock cycle begins. C1's output diode prevents the triangle down-slope from being affected and the 100-pF capacitor provides sharp transitions. The loop regulates the output to 5 V by feedback controlling the turn-off point of the series phase.


### SLOW TURN-ON 15 V REGULATOR

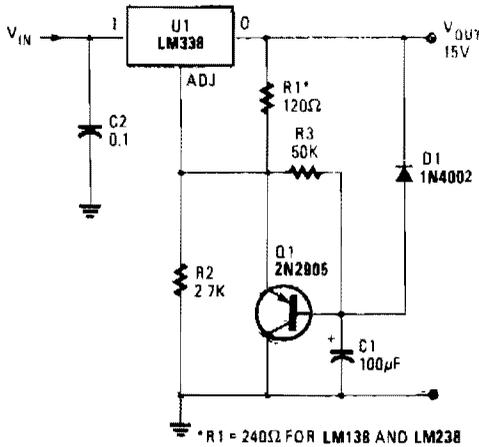

POPULAR ELECTRONICS

Fig. 73-31

### AC VOLTAGE REGULATOR

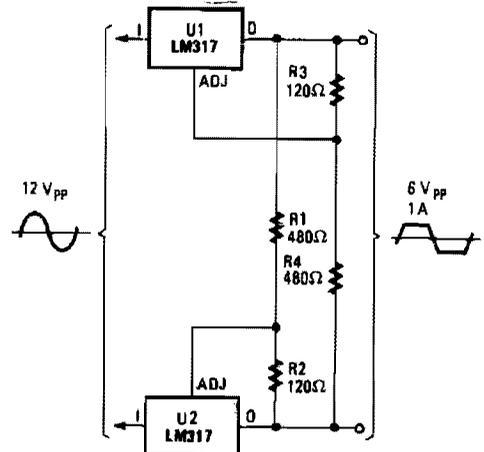

POPULAR ELECTRONICS

Fig. 73-32

### UNINTERRUPTABLE +5 V SUPPLY

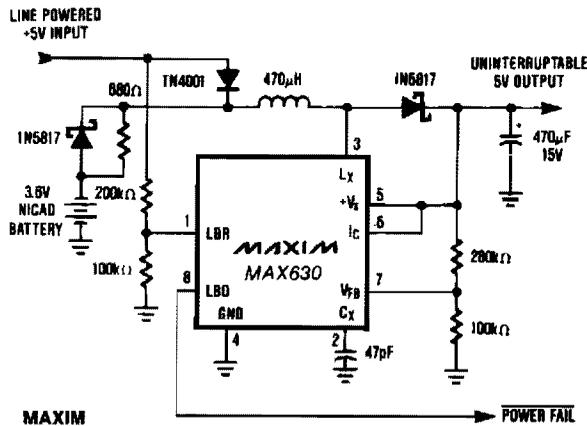


Fig. 73-33

This circuit provides a continuous supply of regulated +5 V, with automatic switch-over between line power and battery backup. When the line-powered input voltage is a +5 V, it provides 4.4 V to the MAX630 and trickle charges the battery. If the line-powered input falls below the battery voltage, the 3.6 V battery supplies power to the MAX630, which boosts the battery voltage up to +5 V, thus maintaining a continuous supply to the uninterruptable +5 V bus. Since the +5 V output is always supplied through the MAX630, there are no power spikes or glitches during power transfer. The MAX630's low-battery detector monitors the line-powered +5 V, and the LBD output can be used to shut down unnecessary sections of the system during power failures. Alternatively, the low-battery detector could monitor the NiCad battery voltage and provide warning of power loss when the battery is nearly discharged. Unlike battery backup systems that use 9-V batteries, this circuit does not need +12 or +15 V to recharge the battery. Consequently, it can be used to provide +5 V backup on modules or circuit cards which only have 5 V available.

# 74

## High-Voltage Power Supplies

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Arc-Jet Power Supply and Starting  
Circuit

Preregulated High-Voltage Supply

High-Voltage Bucking Regulator

High-Voltage Dc Generator

Battery-Powered High-Voltage  
Generator

Optoisolated High-Voltage Driver

Simple High-Voltage Supply


High-Voltage Inverter

High-Voltage Regulator

Capacitor-Discharge High-Voltage  
Generator

Remotely Adjustable Solid-State  
High-Voltage Supply
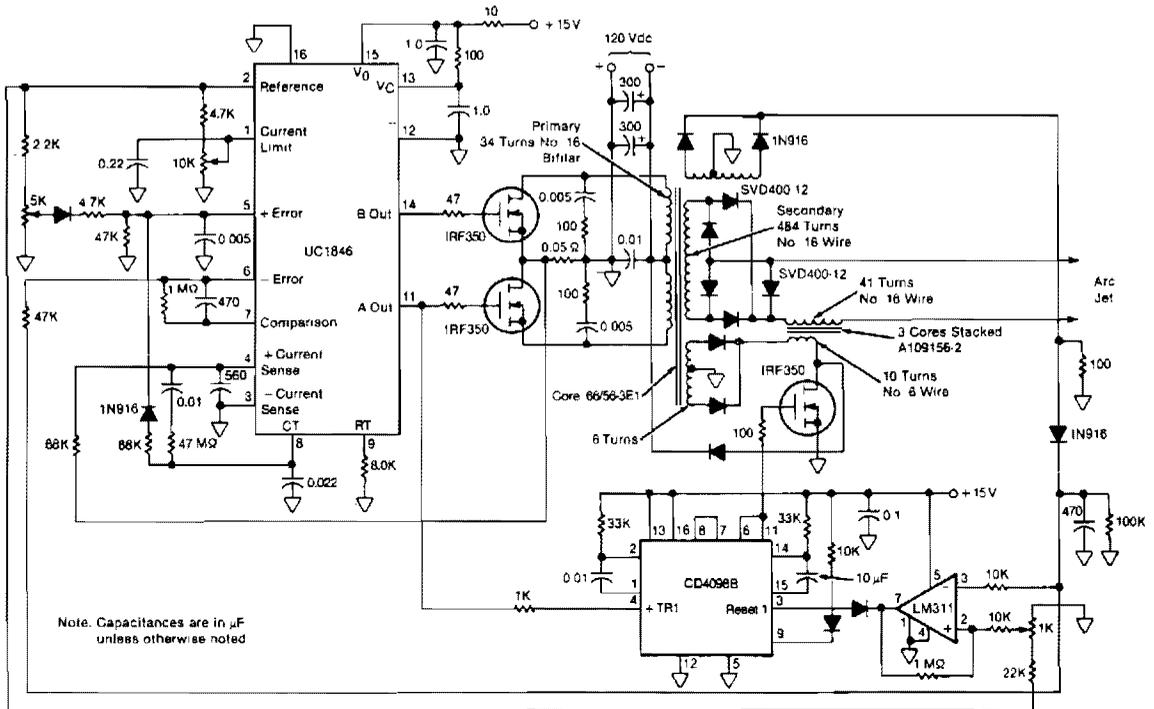
## ARC-JET POWER SUPPLY AND STARTING CIRCUIT




NASA TECH BRIEFS

**Fig. 74-1**

This circuit for starting arc jets and controlling them in steady operation is capable of high power efficiency and can be constructed in a lightweight form. The design comprises a pulse-width-modulated power converter, which is configured in a closed control loop for fast current control. The series averaging inductor maintains nearly constant current during rapid voltage changes, and thereby allows time for the fast-response regulator to adjust its pulse width to accommodate load-voltage changes. The output averaging inductor doubles as the high-voltage pulse transformer for ignition. The starting circuit operates according to the same principle as that of an automobile ignition coil. When the current is interrupted by a transistor switch, the inductor magnetic field collapses, and a high-voltage pulse is produced. The pulse is initiated every 0.25 second until arc current is detected, then the pulser is automatically turned off.

## PREREGULATED HIGH-VOLTAGE SUPPLY

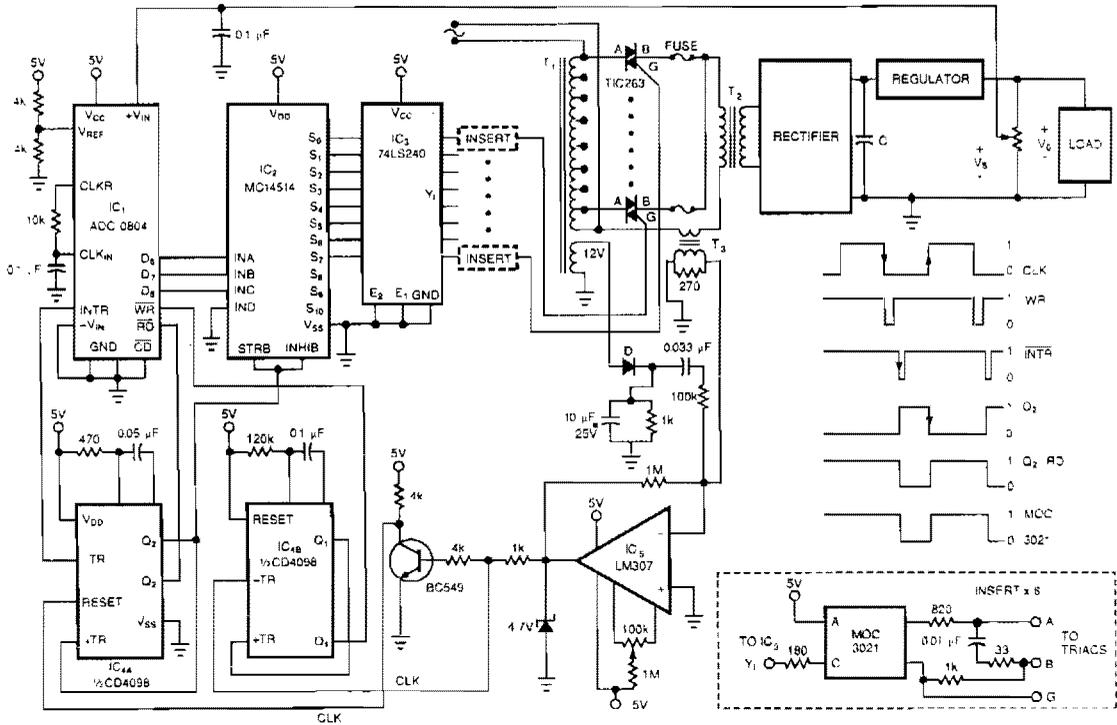

EDN

Fig. 74-2


One of the control circuit's triacs selects the tap on main transformer T1, which provides the proper, preregulated voltage to the secondary regulator. T2 and its associated components comprise the secondary regulator.

The ADC 0804, IC1, digitizes a voltage-feedback signal from the secondary regulator's output. The MC14514 demultiplexer, IC2, decodes the digitizer's output. IC2, in turn, drives T1's optoisolated triacs via the 74LS240 driver chip, IC3, and associated optoisolators.

Transformer T3 samples the circuit's current output. The auxiliary, 12 V winding on T1 ensures no-load starting. The combination of op amp IC5 and the inverting transistor, Q1, square this current signal. The output of Q1 is the CLK signal, which triggers one-half of the one shot, IC4A, to begin the circuit's A/D conversion. The one shots' periods are set to time out within 1/2 cycle of the ac input.

Upon completion of its A/D conversion, IC1's INTR output triggers the other half of the one shot, IC4B, which enables the converter's data outputs. The rising edge of the CLK signal resets the one shot and latches the new conversion value into IC2. The latch, associated driver, and optoisolator trigger a selected triac according to the latest value of the voltage-feedback signal, V<sub>o</sub>.

## HIGH-VOLTAGE BUCKING REGULATOR

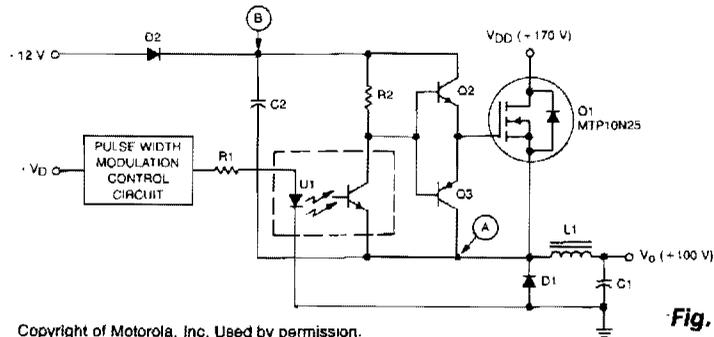

Copyright of Motorola, Inc. Used by permission.


**Fig. 74-3**

This circuit is basically the classic bucking regulator, except it uses a TMOS N-channel power FET for the chopper and creates its own supply for the gate control.

The unique aspect of this circuit is how it generates a separate supply for the gate circuit, which must be greater than  $V_{DD}$ . When power is applied, C2 charges, through D2, to +12 V. At this time, Q1 is off and the voltage at point A is just below zero. When the pulse-modulated signal is applied, the optoisolator transistors, Q2 and Q3, supply a signal to Q1 that turns it on. The voltage at point A then goes to  $V_{DD}$ , C2 back-biases D2, and the voltage at point B becomes 12 V above  $V_{DD}$ .

After Q1 is turned on, current starts to flow through L1 into C1, increasing until Q1 turns off. The current still wants to flow through L1, so the voltage at point A moves toward negative infinity, but is clamped by D1 to just below zero. Current flows less and less into C1, until Q1 turns on again. Q2 and Q3 drive Q1's gate between the voltages at point A and B, which is always a 12 V swing, so  $V_{GS}$  max. is never exceeded. For proper operation, the 12-V supply has to be established before the pulse-width modulator signal is applied.


## HIGH-VOLTAGE DC GENERATOR

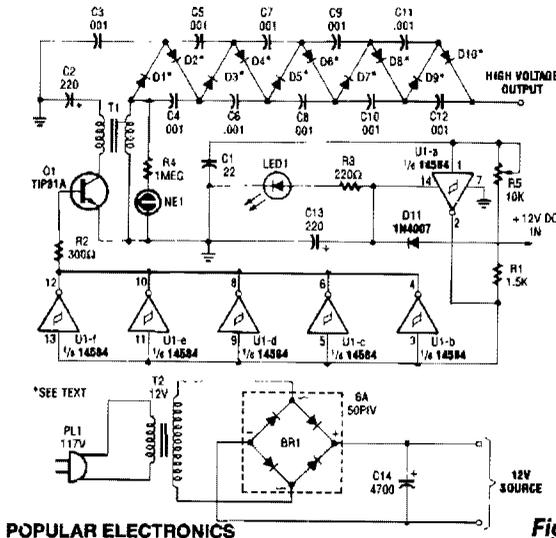

This circuit is fed from a 12-Vdc power supply. The input to the circuit is then amplified to provide a 10,000-Vdc output. The output of the up-converter is then fed into a 10 stage, high-voltage multiplier to produce an output of 10,000 Vdc.

**Fig. 74-4**
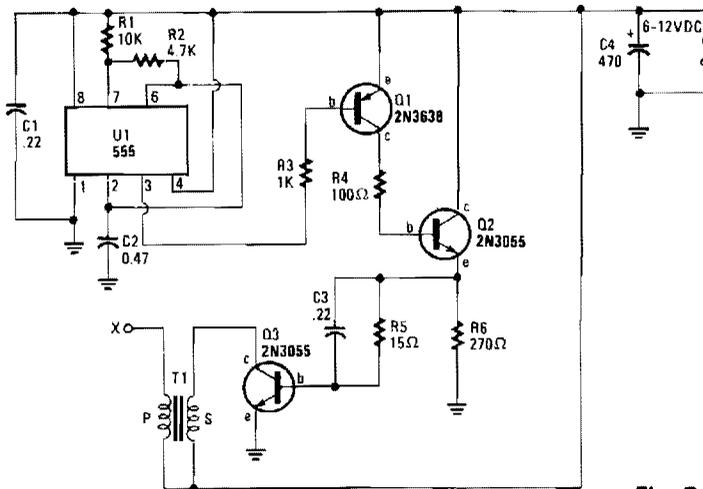
## BATTERY-POWERED HIGH-VOLTAGE GENERATOR




HANDS-ON ELECTRONICS

T1 = Auto Ignition Coil

Fig. 74-5

Output voltage great enough to jump a 1-inch gap can be obtained from a 12-V power source. A 555 timer IC is connected as an astable multivibrator that produces a narrow negative pulse at pin 3. The pulse turns Q1 on for the duration of the time period. The collector of Q1 is direct-coupled to the base of the power transistor Q2, turning it on during the same time period. The emitter of Q2 is direct-coupled through current limiting resistor R5 to the base of the power transistor. Q3 switches on, producing a minimum resistance between the collector and emitter. The high-current pulse going through the primary of high-voltage transformer T1 generates a very high pulse voltage at its secondary output terminal (labeled X). The pulse frequency is determined by the values of R1, R2, and C2. The values given in the parts list were chosen to give the best possible performance when an auto-ignition coil is used for T1.

## OPTOISOLATED HIGH-VOLTAGE DRIVER

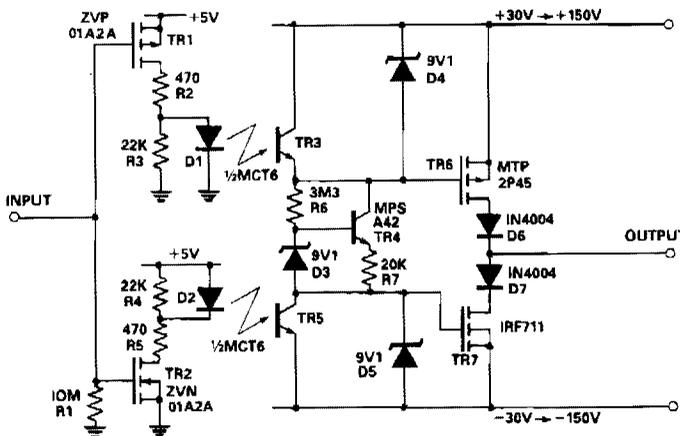

ELECTRONIC ENGINEERING


Fig. 74-6

## OPTOISOLATED HIGH-VOLTAGE DRIVER (Cont.)

This circuit takes as an input a signal from a 5-V CMOS logic circuit and outputs a high voltage of the same polarity. The high-voltage supply can be varied from  $\pm 30$  V to  $\pm 150$  V without the need to change circuit components. The input voltage is applied to the gates of transistors TR1 and TR2.

TR3 is optically coupled to D1 as is TR5 to D2. R5 limits the current through D2, while R3 and R4 reduce the effects of leakage current. The light transmitted by D1 turns TR3 on and discharges the gate-source capacitance of TR6, which turns TR6 off. At the same time, TR5 is off and a constant current produced by R6, R7, D3, and TR4 charges the gate-sourced capacitance of TR7, thus turning TR7 on. With TR7 on and TR6 off, the output is pulled close to the lower supply rail. When the input is high, TR1 is off and TR2 is on. Therefore, D2 conducts, which turns on TR5. With TR3 off and TR5 on, TR6 turns on and TR7 off. The output is pulled towards the higher supply rail.

## SIMPLE HIGH-VOLTAGE SUPPLY

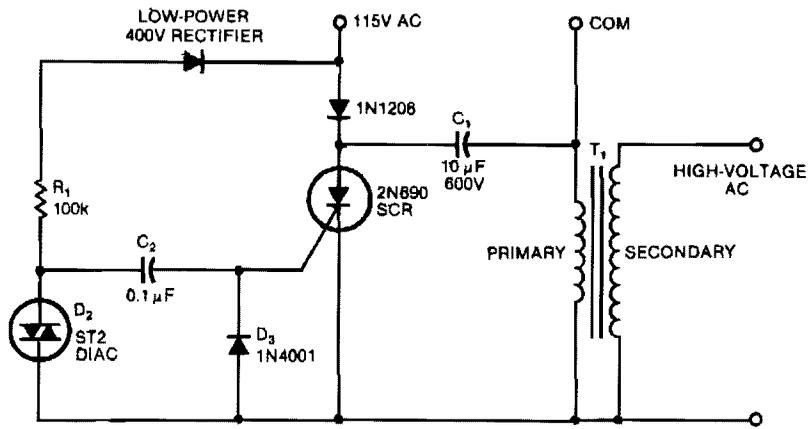

### NOTES:


$T_1 = 8$  mH AT 5A DC, 1:230 TO 1:500  
TURNS RATIO, 0.45 $\Omega$  PRIMARY.  
RESISTANCE, 10-k $\Omega$  SECONDARY.  
RESISTANCE AUTOMOBILE  
IGNITION COIL  
 $C_1 = 10$ - $\mu$ F, 600 WV DC, OIL-FILLED  
PAPER CAPACITOR

EDN

Fig. 74-7

This circuit can generate high-voltage pulses with an inexpensive auto ignition coil. Add a rectifier on the output and the circuit produces high-voltage dc. The circuit's input is 115 Vac. During the input's positive half cycle, energy is stored in capacitor C1, which is charged via diode D1 and the primary winding of transformer T1, the coil. The SCR and its trigger circuitry are inactive during this period. During the input's negative half cycle, energy is stored in capacitor C2 until diac D2 reaches its trigger voltage, whereupon D2 conducts abruptly and C2 releases its energy into the SCR's gate. The SCR then discharges C1 into the transformer's primary and ceases to conduct. This store-and-release cycle repeats on the line's positive and negative half cycles, producing high-voltage pulses at the transformer's secondary.

## HIGH-VOLTAGE INVERTER

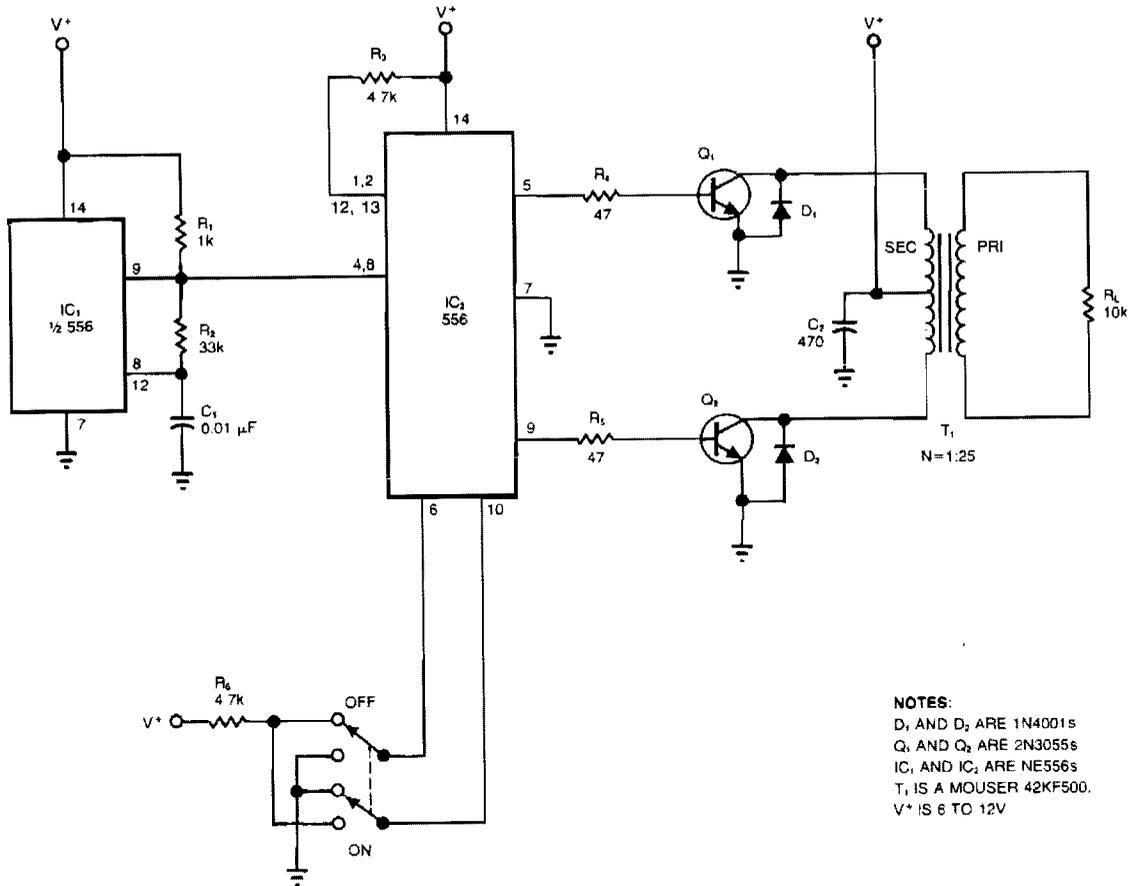

**NOTES:**


- D<sub>1</sub> AND D<sub>2</sub> ARE 1N4001s
- Q<sub>1</sub> AND Q<sub>2</sub> ARE 2N3055s
- IC<sub>1</sub> AND IC<sub>2</sub> ARE NE556s
- T<sub>1</sub> IS A MOUSER 42KF500.
- V<sup>+</sup> IS 6 TO 12V

EDN

**Fig. 74-8**

The circuit converts a dc voltage ( $V^+$ ) to a high-amplitude square wave in the audio-frequency range. The dual timer, IC<sub>2</sub>, provides an inexpensive alternative to the traditional transformer for providing complementary base drive to the power transistors, Q<sub>1</sub> and Q<sub>2</sub>. You can convert a 6 to 12 V battery output, for example, to an ac amplitude, which is limited primarily by the power rating of transformer T<sub>1</sub>. Connect timer IC<sub>1</sub> as an oscillator to provide a symmetrical square-wave drive to both inputs of IC<sub>2</sub>. The timing components, R<sub>2</sub> and C<sub>1</sub>, produce a 2.2-kHz output frequency. By connecting half of IC<sub>2</sub> in the inverting mode and the other half in noninverting mode, the timer's outputs alternately drive the two transistors. You can operate the audio-output transformer, T<sub>1</sub>, as a step-up transformer by connecting it backwards—using the output winding as an input. The transformer delivers an output voltage across  $R_L$  of  $4 \times N \times V^+$  V pk-pk, where  $N$  is the transformer turns ratio. For the circuit shown, the output swing is  $100 \times V^+$  V pk-pk.

## HIGH-VOLTAGE REGULATOR

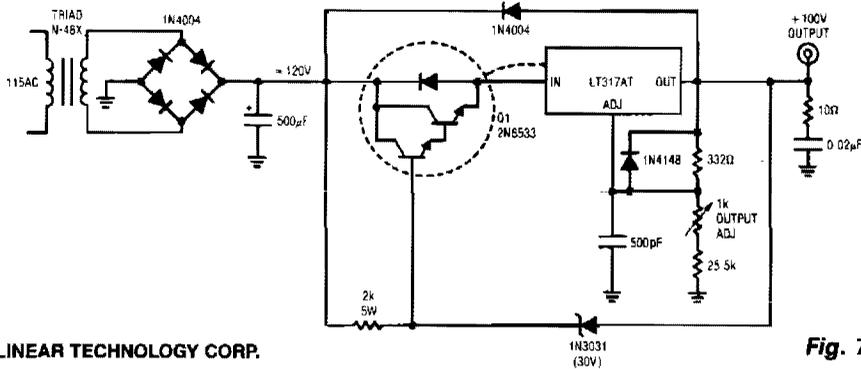

LINEAR TECHNOLOGY CORP.

Fig. 74-9

The regulator delivers 100-V at 100 mA and withstands shorts to ground. Even at 100 V output, the LT317A functions in the normal mode, maintaining 1.2 V between its output and adjustment pin. Under these conditions, the 30-V zener is off and Q1 conducts. When an output short occurs, the zener conducts, forcing Q1's base to 30 V. This causes Q1's emitter to clamp  $2 V_{BE}$ s below  $V_Z$ , well within the  $V_{IN}-V_{OUT}$  rating of the regulator. Under these conditions, Q1, a high-voltage device, sustains 90 V- $V_{CE}$  at whatever current the transformer specified saturates at 130 mA, while Q1 safely dissipates 12 W. If Q1 and the LT317A are thermally coupled, the regulator will soon go into thermal shutdown and oscillation will commence. This action will continue, protecting the load and the regulator as long as the output remains shorted. The 500-pF capacitor and the 10  $\Omega$ /0.02  $\mu$ F damper aid transient response and the diodes provide safe discharge paths for the capacitors.

## CAPACITOR-DISCHARGE HIGH-VOLTAGE GENERATOR

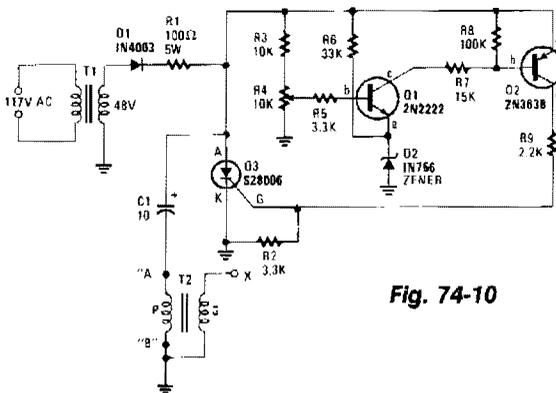


Fig. 74-10

HANDS-ON ELECTRONICS

Stepdown transformer T1 drops the incoming line voltage to approximately 48 Vac which is rectified by diode D1; the resultant dc charges capacitor

C1—through current limiting resistor R1—to a voltage level preset by R4. When the voltage on R4's wiper reaches about 8.6 V, Q1 begins to turn on, drawing current through R7 and the base-emitter junction of Q2. Q2 turns on and supplies a positive voltage to the gate of silicon-controlled rectifier Q3. The positive gate voltage causes Q3 to conduct, thereby discharging C1 through the primary winding of step-up transformer T2, which results in a high-voltage arc at output terminal X. The voltage developed at T2's output is determined by the value of C1, the voltage across C1, and the turns ratio of transformer T2. The frequency or pulse rate of the high voltage is determined by the resistance of T1's primary and secondary windings, the value of R1, and the value of C1. The lower the value of each item, the higher the output pulse rate; the peak output voltage will only remain unchanged if C1's value remains unchanged.



# 75

## Variable Power Supplies

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

100-kHz Multiple-Output Switching  
Power Supply

3 – 30 V Universal Power Supply Module  
Regulator/Current Source

Low-Power Switching Regulator  
Variable Voltage Regulator  
Tracking Preregulator  
Adjustable 10-A Regulator

## 100-KHz MULTIPLE-OUTPUT SWITCHING POWER SUPPLY

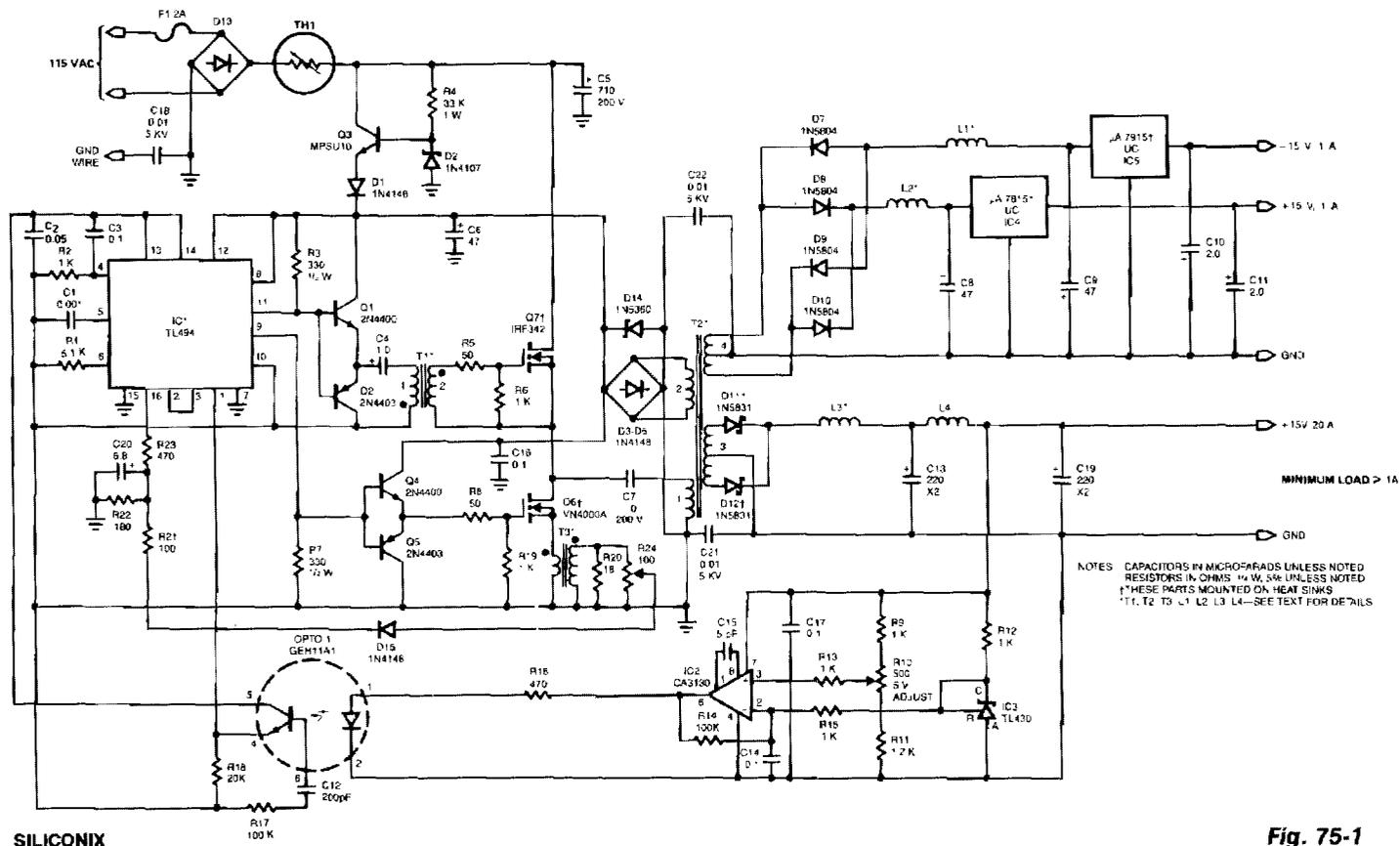


Fig. 75-1

The power supply uses two VN4000A 400-V MOSPOWER FETs in a half-bridge power switch configuration. Outputs available are +5 V at 20 A and  $\pm 15$  V (or  $\pm 12$  V) at 1 A. Since linear three-terminal regulators are used for the low-current outputs, either  $\pm 12$  V or  $\pm 15$  V can be made available with a simple change in the transformer secondary windings. A TL494 switching regulator IC provides pulse-width modulation control and drive signals for the power supply. The upper MOSPOWER FET, Q7, in the power switch stage is driven by a simple transformer drive circuit. The lower MOS, Q6, since it is ground referenced, is directly driven from the control IC.

### 3 – 30 V UNIVERSAL POWER SUPPLY MODULE

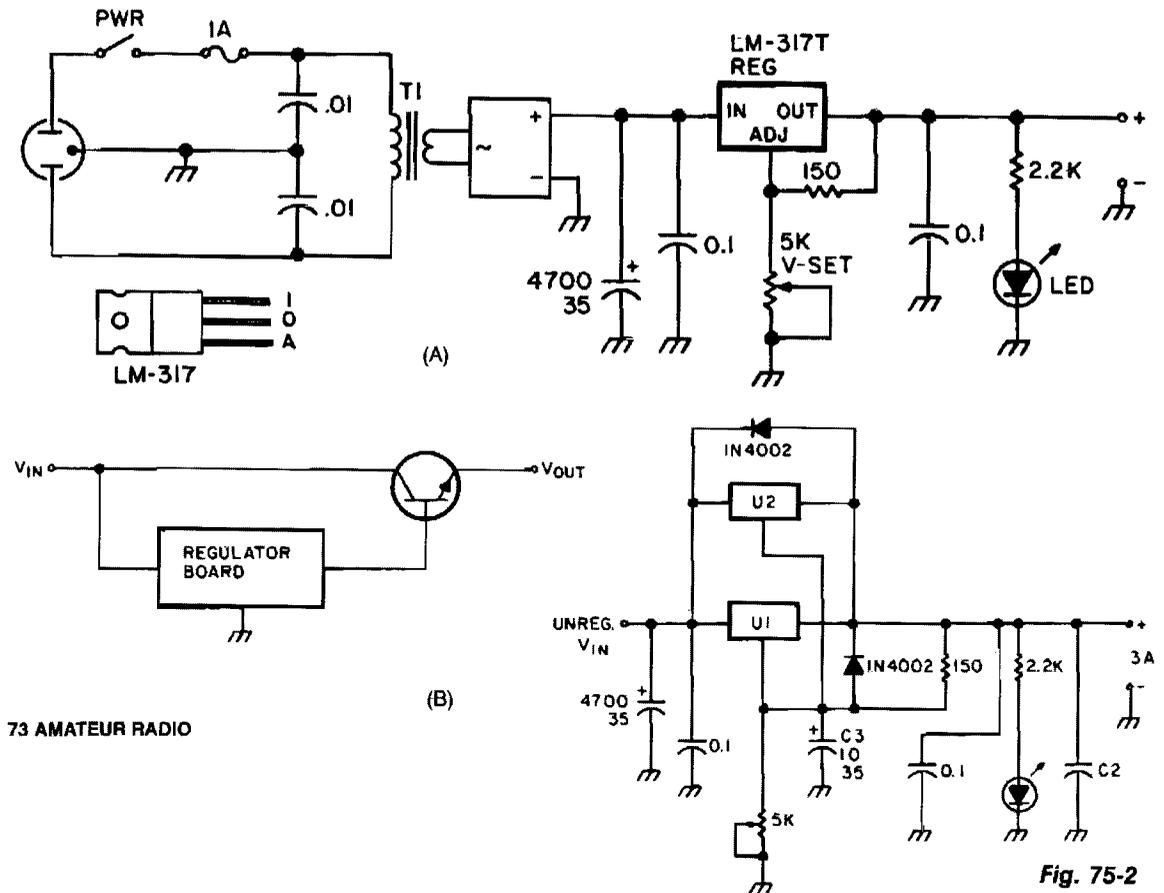


Fig. 75-2

U1, an LM317 adjustable regulator provides short-circuit protection and automatic current limiting at 1.5 A. The input voltage to the regulator is supplied by DB1, a 4-A 100 PIV full-wave bridge rectifier. Capacitor C1 provides initial filtering. U1 provides additional electronic filtering as part of the regulating function. The output level of the regulator is set by trim-pot R1. Bypass capacitors on the input and output of U1 prevent high-frequency oscillation. The current rating of the transformer must be at least 1.8 times the rated continuous-duty output of the supply. This means that a 1.5-A supply should use a 2.7-A transformer. For light or intermittent loads, a smaller 2.0-A transformer should suffice.


Wiring a second LM317, U2, in parallel with U1 is a quick and clean way to increase the current-limiting threshold to 3 A without sacrificing short-circuit protection. When more than 3 A is required, the regulator module can be used to drive the base of one or more pass-transistors (see Fig. 75-2B).



## LOW-POWER SWITCHING REGULATOR (Cont.)

A simple battery-powered switching regulator provides 5 V out from a 9-V source with 80% efficiency and 50 mA output capability. When Q1 is on, its collector voltage rises, forcing current through the inductor. The output voltage rises, causing A1's output to rise. Q1 cuts off and the output decays through the load. The 100-pF capacitor ensures clean switching. The cycle repeats when the output drops low enough for A1 to turn on Q1. The 1- $\mu$ F capacitor ensures low battery impedance at high frequencies, preventing sag during switching.

## VARIABLE VOLTAGE REGULATOR

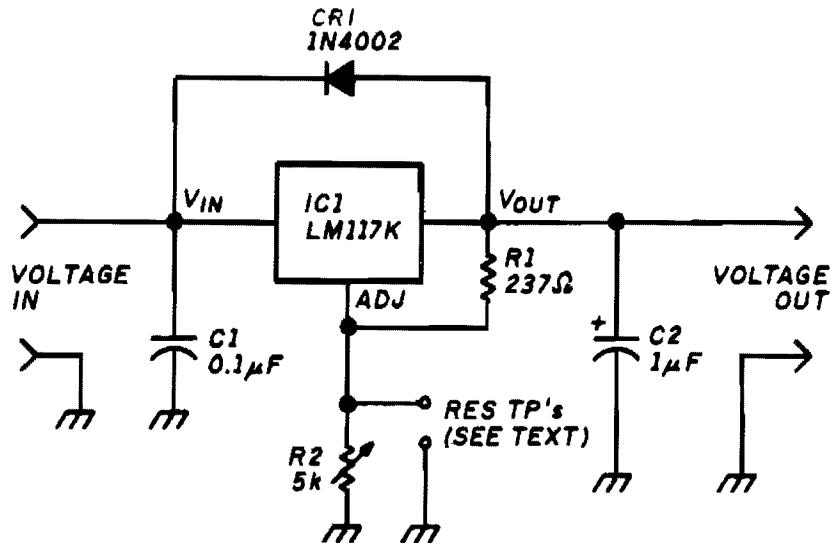


HAM RADIO

Fig. 75-5

The variable voltage regulator lets you adjust the output voltage of a fixed dc power supply between 1.2 and 37 Vdc, and will supply the output current in excess of 1.5 A. The circuit incorporates an LM117K three-terminal adjustable output positive voltage regulator in a TO-3 can. Thermal overload protection and short-circuit current-limiting constant with temperature are included in the package. Capacitor C1 reduces sensitivity to input line impedance, and C2 reduces excessive ringing. Diode CR1 prevents C2 from discharging through the IC during an output short.


### TRACKING PREREGULATOR

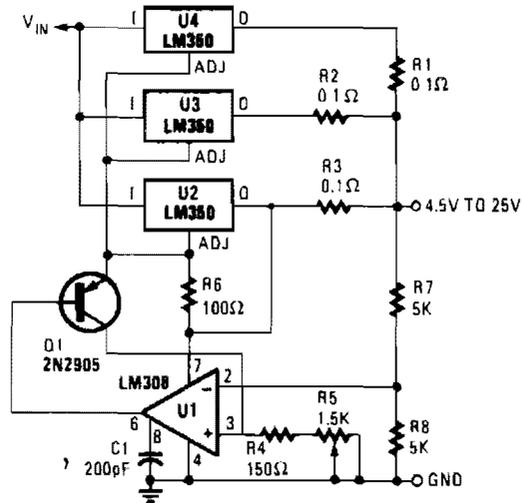

POPULAR ELECTRONICS

Fig. 75-6

### ADJUSTABLE 10-A REGULATOR

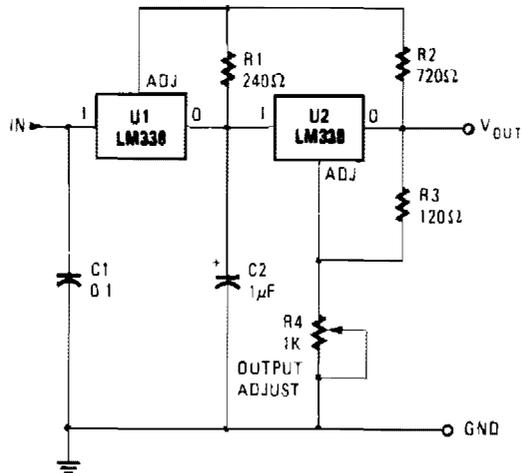

POPULAR ELECTRONICS

Fig. 75-7

# 76


## Power Supply Monitors

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Power-Supply Balance Indicator  
Single-Supply Fault Monitor


## POWER-SUPPLY BALANCE INDICATOR

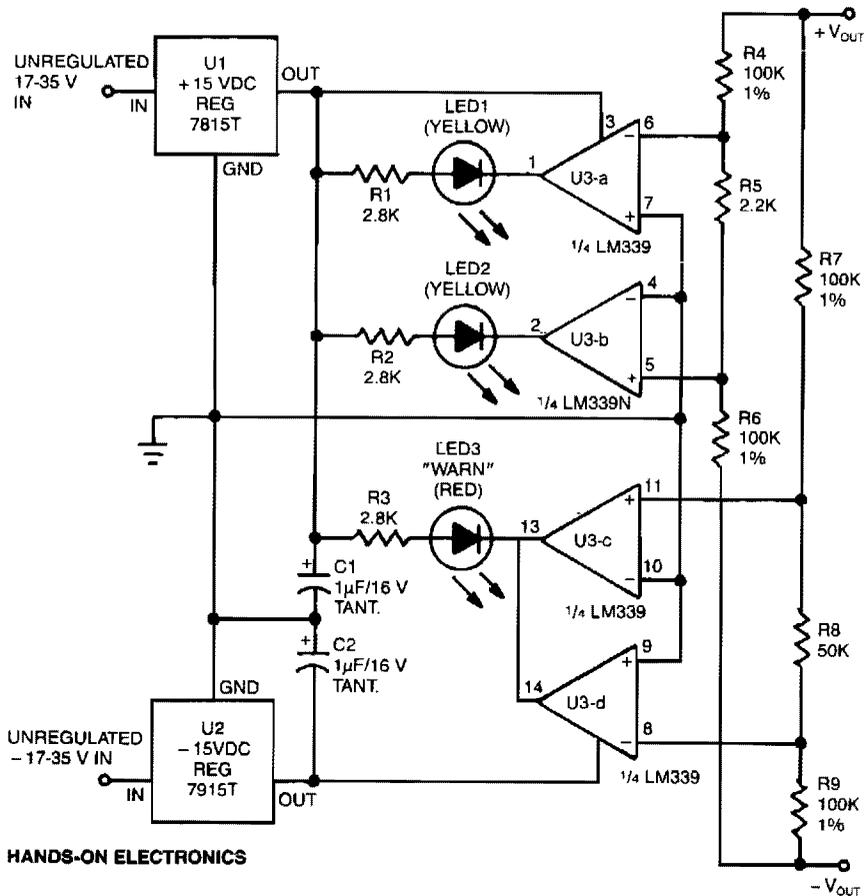

**Fig. 76-1**

This circuit uses two comparator pairs from an LM339N quad comparator; one pair drives the yellow positive (+) and negative (-) indicators, the other jointly drives the red warn LED3. The circuit draws its power from the unregulated portion of the power supply. The four comparators get their switching inputs from two parallel resistor-divider strings. Both strings have their ends tied between the power supply's positive and negative output terminals. The first string, consisting of R4, R5, and R6, divides the input voltage in half, with output taps at 0.5%. The other string, made up of R7, R8, and R9, also divides the input voltage in half, with taps at +10%. The 0.5% R4/R5/R6 string drives the two comparators controlling the positive and negative indicators (LED1 and LED2). Their inputs are crossed so that LED2 does not fire until the positive supply is at least 0.5% higher than the negative; the positive indicator does not go off until the negative supply is at least 0.5% higher than the positive—in relative levels. That overlap permits both LEDs to be on when the two supplies are in 1% or better balance. The +10T R7/R8/R9 string drives the other two comparators, which control the warn indicator. If either side of the supply is 10% or more higher than the other, one of the two comparators will switch its output low and light the red LED3—the LM339N has open-collector outputs, allowing such wired OR connections. The inputs are not crossed, as with the other comparator pair, so there is a band in the middle where neither comparators output is low and the LED remains off.

## SINGLE-SUPPLY FAULT MONITOR

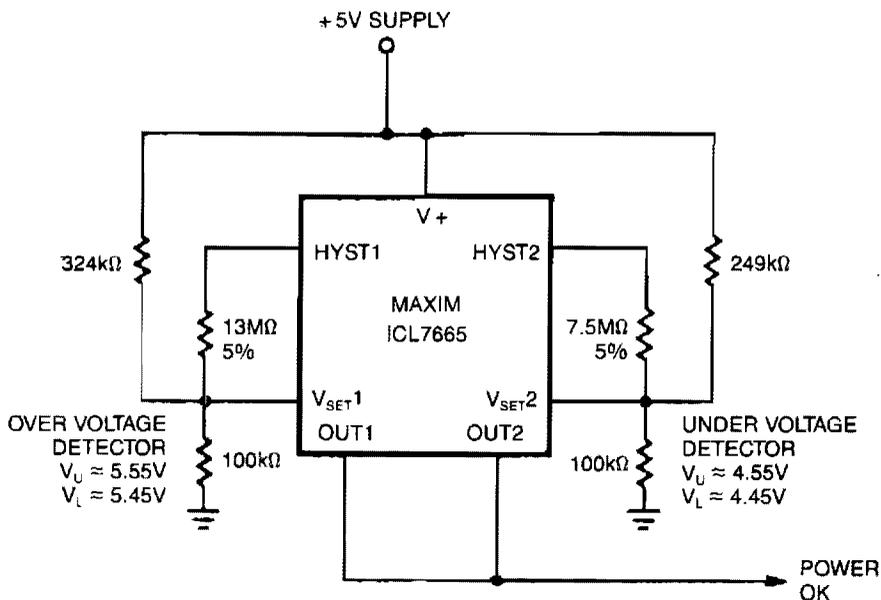

MAXIM

Fig. 76-2

This circuit shows a typical over/under-voltage fault monitor for a single supply. The upper trip points, controlling OUT 1, are centered on 5.5 V with 100 mV of hysteresis ( $V_U = 5.55$  V,  $V_L = 5.45$  V); and the lower trip points, controlling OUT 2, are centered on 4.5 V, also with 100 mV of hysteresis. OUT 1 and OUT 2 are connected together in a wired OR configuration to generate a *power OK* signal.

# 77

## Probes

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Digital Logic Probe	Battery-Powered Ground-Noise Probe
Low Input Capacitance Buffer	FET Probe
Rf Probe	pH Probe and Detector
CMOS Universal Logic Probe	Stabilized Low Input Capacitance
4 ~ 220 V Test Probe	Buffer
	Rf Probe

## DIGITAL LOGIC PROBE

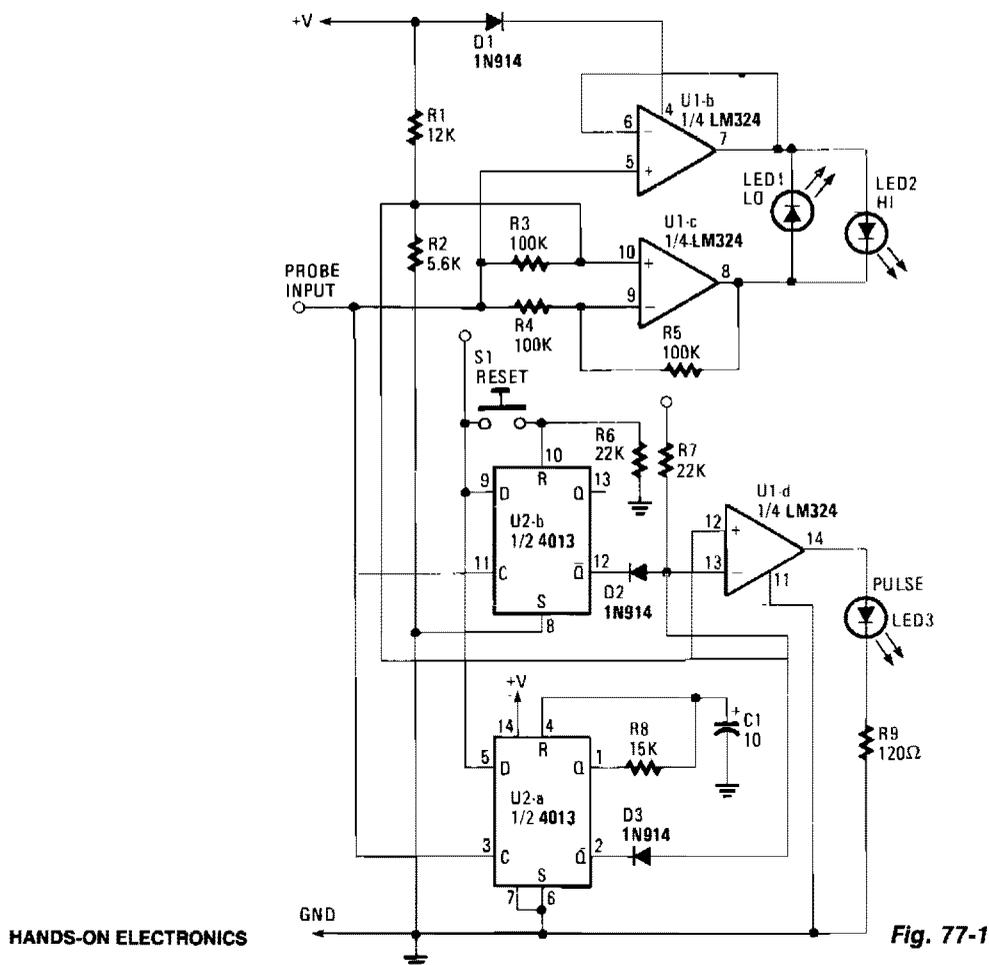



Fig. 77-1

The probe relies on the power supply of the CUT (circuit-under-test). The input to the probe, at probe tip, is fed along two paths. One path flows to the clock inputs of U2a and U2b. The other path feeds both the inverting input of U1c, which is set up as an inverting-mode integrator, and the noninverting input of U1b, which is configured as a noninverting unity-gain amplifier, in a logic-low state.

That low, below the reference set at pin 10, causes U1b's output at pin 7 to become high. With U1b outputting low and U1c outputting high, LED1 is forward-biased, and lights. LED2, reverse-biased, remains dark. Suppose that the logic level on the same pin becomes high. That high is applied to pin 5 of U1b, causing its output to be high. LED2 is now forward-biased and lights, while LED1 is reverse-biased and becomes dark.

Assume that a clock frequency is sensed at the probe input; LED1 and LED2 alternately light, and depending on the frequency of the signal, can appear constantly lit. That frequency, which is also applied to the clock input of both flip-flops, causes the Q outputs of U2a and U2b to simultaneously alternate between high and low. Each time that the Q outputs of the two flip-flops decrease, the output of U1d increases, lighting LED3, indicating that a pulse stream has been detected.


## LOW INPUT CAPACITANCE BUFFER

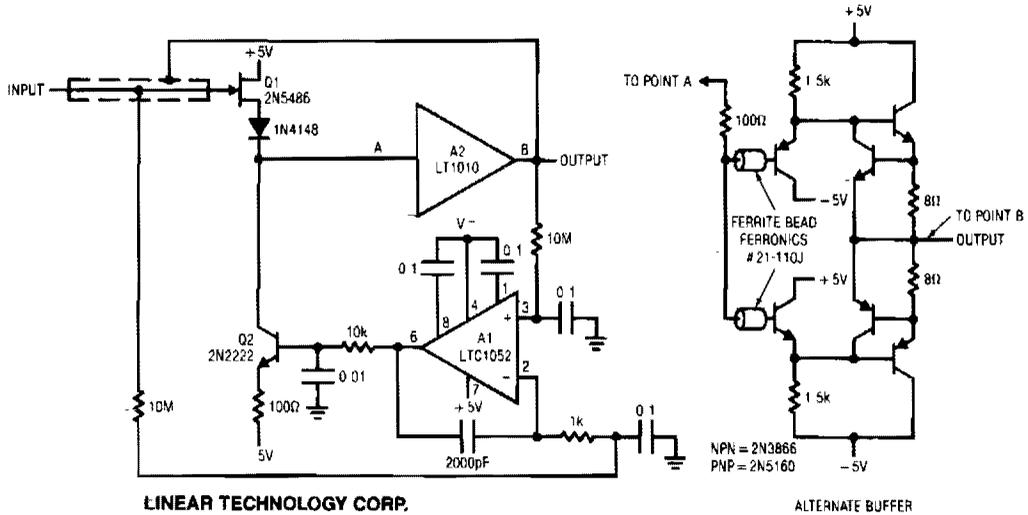

**Fig. 77-2**

Q1 and Q2 constitute a simple, high-speed FET input buffer. Q1 functions as a source follower, with the Q2 current-source load setting the drain-source channel current. The LT1010 buffer provides output drive capability for cables or whatever load is required. The LTC1052 stabilizes the circuit by comparing the filtered circuit output to a similarly filtered version of the input signal. The amplified difference between these signals is used to set Q2's bias, and hence Q1's channel current. This forces Q1's  $V_{GS}$  to whatever voltage is required to match the circuit's input and output potentials. The diode in Q1's source line ensures that the gate never forward biases and the 2000-pF capacitor at A1 provides stable loop compensation. The rc network in A1's output prevents it from seeing high-speed edges coupled through Q2's collector-base junction. A2's output is also fed back to the shield around Q1's gate lead, bootstrapping the circuit's effective input capacitance to less than 1 pF.


## RF PROBE

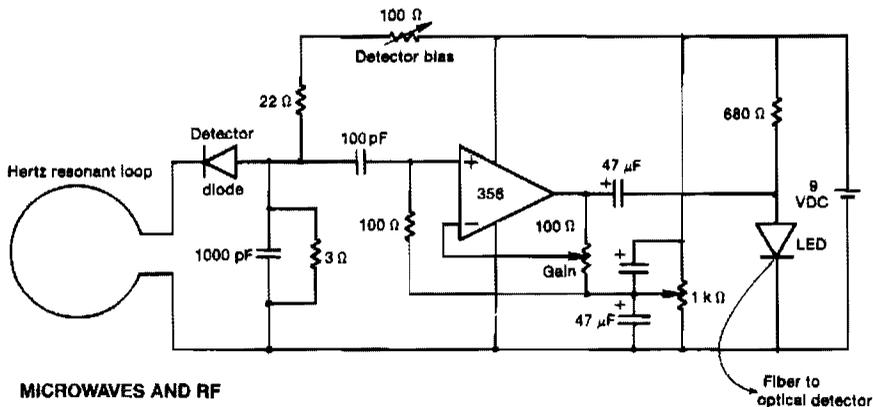

**Fig. 77-3**



## BATTERY-POWERED GROUND-NOISE PROBE

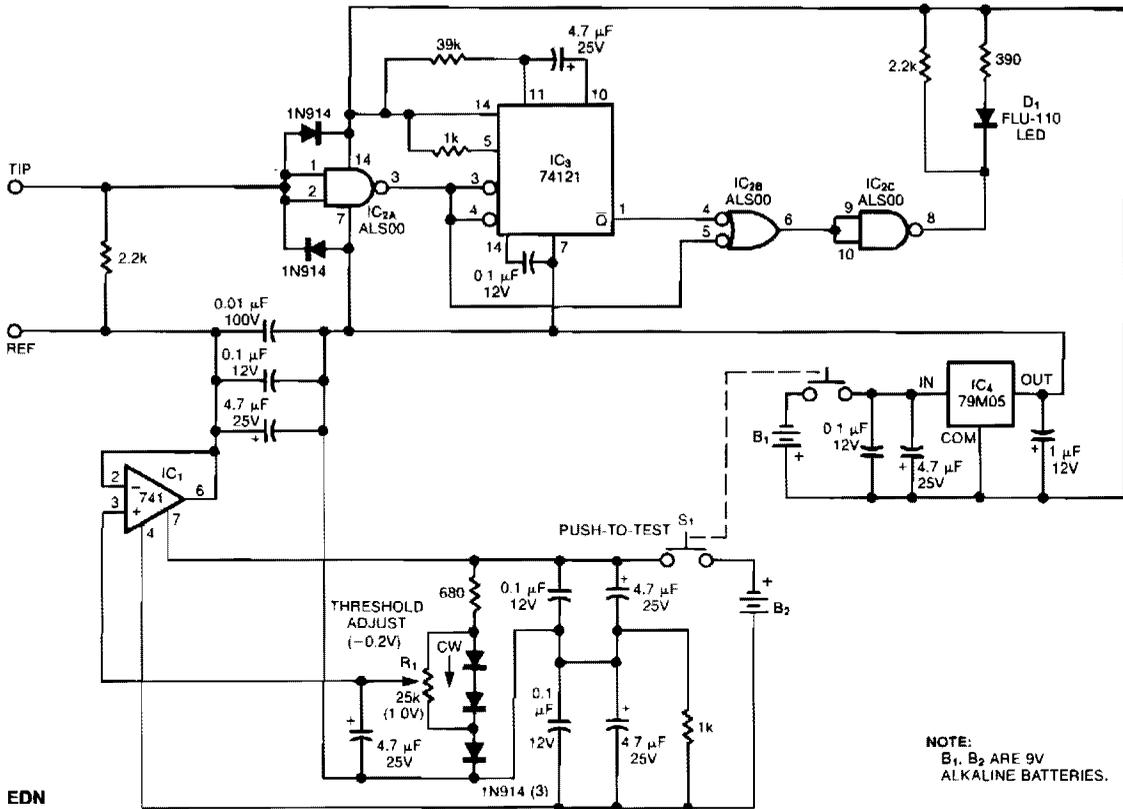

NOTE:  
B<sub>1</sub>, B<sub>2</sub> ARE 9V  
ALKALINE BATTERIES.

Fig. 77-6

Oscilloscope measurements of ground noise can be unreliable because noise can enter your circuit via the scope's three-pronged power plug. You can avoid this problem by using the ground-noise tester shown. Powered by two 9-V batteries, the circuit dissipates power only while push-to-test switch S1 is depressed. Noise pulses that reach IC2A's switching threshold of about 1.5 to 1.8 V create a logic transition that triggers the monostable multivibrator IC3, which stretches the pulse to produce a visible blink from LED D1. You set the noise reference level by adjusting threshold-adjust potentiometer R1, which lets the circuit respond to minimum pulse amplitudes ranging from about 0 to 1 V. For convenience, you can use a one-turn potentiometer for R1 and calibrate the dial by applying an adjustable dc voltage, monitored by an accurate voltmeter.

## FET PROBE

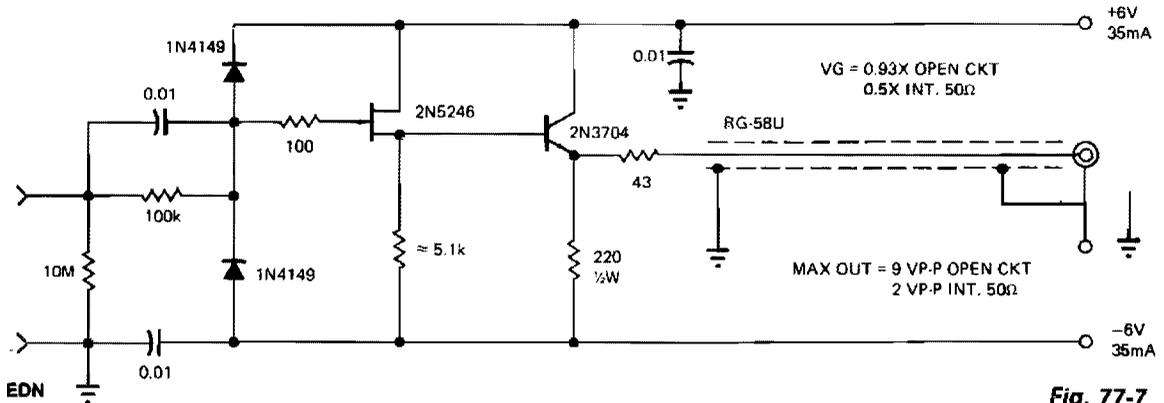


Fig. 77-7

This FET probe has an input impedance of  $10\text{ M}\Omega$  shunted by  $8\text{ pF}$ . Eliminating the protective diodes reduces this impedance to about  $4\text{ pF}$ . The frequency response of the probe extends from dc to  $20\text{ MHz}$  ( $-1\text{ dB}$ ), although higher frequency operation is possible through optimized construction and use of a UHF-type transistor. Zero dc offset at the output is achieved by selecting a combination of a 2N5246 and source resistor that yields a gate-source bias equal to the  $V_{BE}$  of the 2N3704 at approximately  $0\text{ V}$ . At medium frequencies, the probe can be used unterminated for near-unity gain; for optimum impedance converter probe high-frequency response, the cable must be terminated into  $50\text{ }\Omega$ . The voltage gain, when properly terminated, is precisely  $0.5 X$ .

## pH PROBE AND DETECTOR


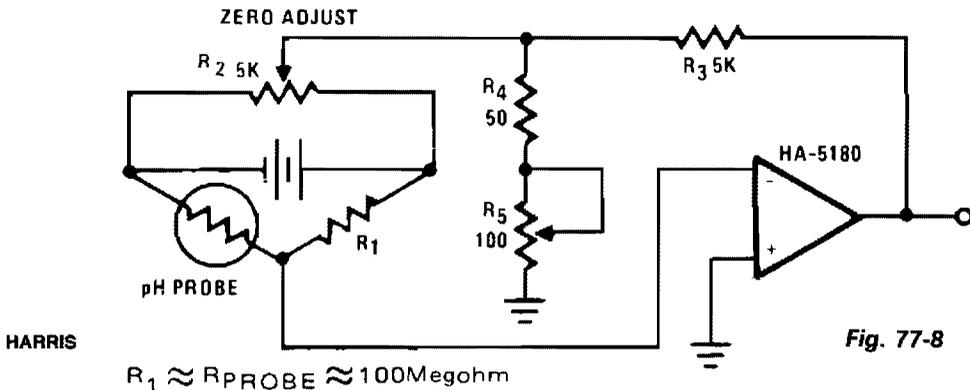


Fig. 77-8

The greatest sensitivity is achieved if  $R_1$  is approximately equal to the probe resistance. The circuit can be *zeroed* with  $R_2$ , while the full-scale voltage is controlled by  $R_5$ . The correlation between pH and output voltage might not be linear, which would necessitate a shaping circuit. A calibration scheme, using solutions of known pH, might prove adequate and more reliable over a period of time because of probe variance.


## STABILIZED LOW-INPUT CAPACITANCE BUFFER

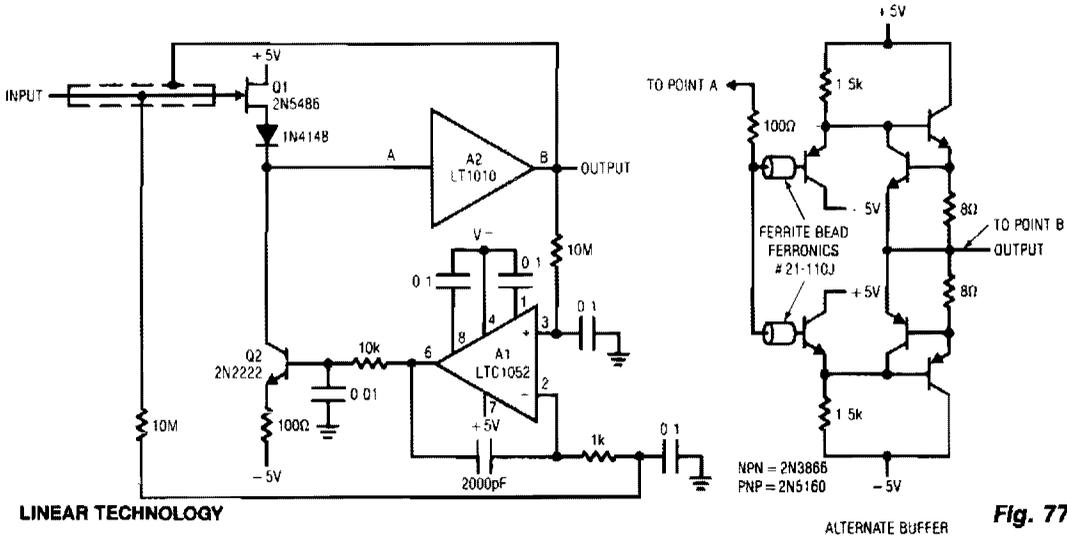

**Fig. 77-9**

Q1 and Q2 constitute a simple, high-speed FET input buffer. Q1 functions as a source follower, with the Q2 current source load setting the drain-source channel current. The LT1010 buffer provides output drive capability for cables or whatever load is required. Normally, this open-loop configuration would be quite drifty because there is no dc feedback. The LTC1052 contributes this function to stabilize the circuit. It does this by comparing the filtered circuit output to a similarly filtered version of the input signal. The amplified difference between these signals is used to set Q2's bias, and hence Q1's channel current. Q1's source line ensures that the gate never forward biases, and the 2000 pF capacitor at A1 provides stable loop compensation. The rc network in A1's output prevents it from seeing high-speed edges coupled through Q2's collector-base junction. A2's output is also fed back to the shield around Q1's gate lead, bootstrapping the circuit's effective input capacitance down to less than 1 pF.

### RF PROBE

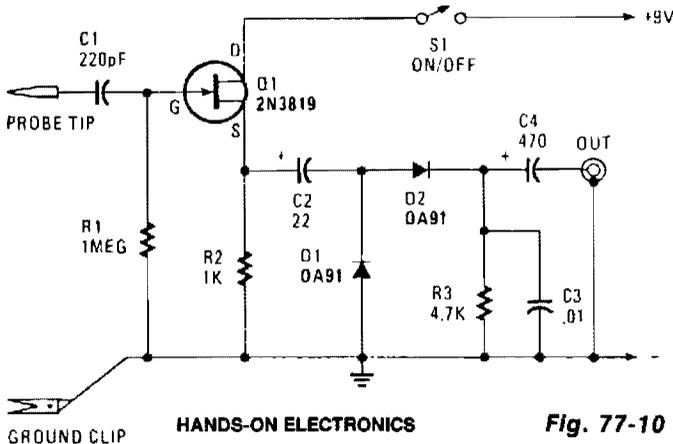

**Fig. 77-10**

## RF PROBE (Cont.)

Transistor Q1—configured as a source-follower buffer stage, offering a bit under unity voltage gain—gives the unit a high-impedance input of about  $1\text{ M}\Omega$  shunted by about  $10\text{ pF}$ , which keeps only minimal loading on the equipment being tested. C1 serves as input dc blocking capacitor. The Q1 output is coupled by C2 to a simple AM detector circuit made up of D1, D2, R3 and C3. Capacitor C4 provides output dc blocking. Total current consumption should be somewhere around  $1\text{ mA}$ . The circuit responds to frequencies from  $100\text{ kHz}$  to well over  $50\text{ MHz}$ .

---

# 78

## Programmable Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Inverting Programmable-Gain Amplifier

Noninverting Programmable Gain Amplifier


Wide Range Digitally Controlled Variable-Gain  
Amplifier

Digitally Programmable Precision Amplifier

Programmable-Gain Differential-Input Amplifier

Programmable Amplifier

## INVERTING PROGRAMMABLE-GAIN AMPLIFIER

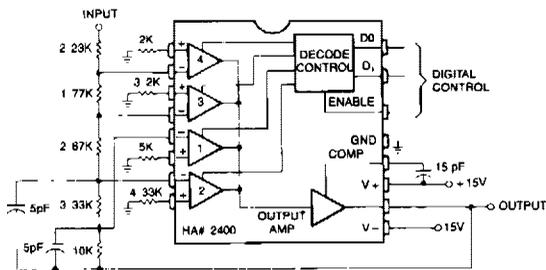


HARRIS

Fig. 78-1

This circuit can be programmed for a gain of 0, -1, -2, -4, or -8. This could also be accomplished with one input resistor and one feedback resistor per channel in the conventional manner, but this would require eight resistors, rather than five.
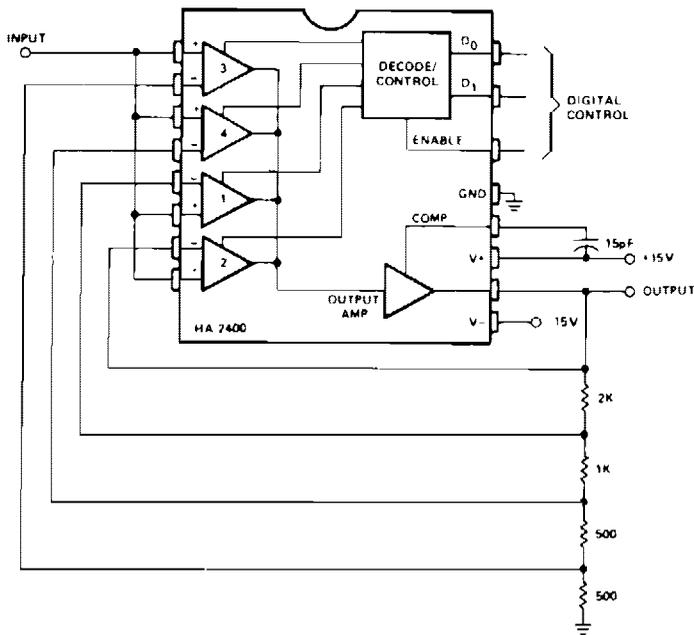
## NONINVERTING PROGRAMMABLE GAIN AMPLIFIER




HARRIS

Fig. 78-2

This is a noninverting amplifier configuration with feedback resistors chosen to produce a gain of 0, 1, 2, 4, or 8, depending on the digital control inputs. Comparators at the output could be used for automatic gain selection for auto-ranging meters, etc.
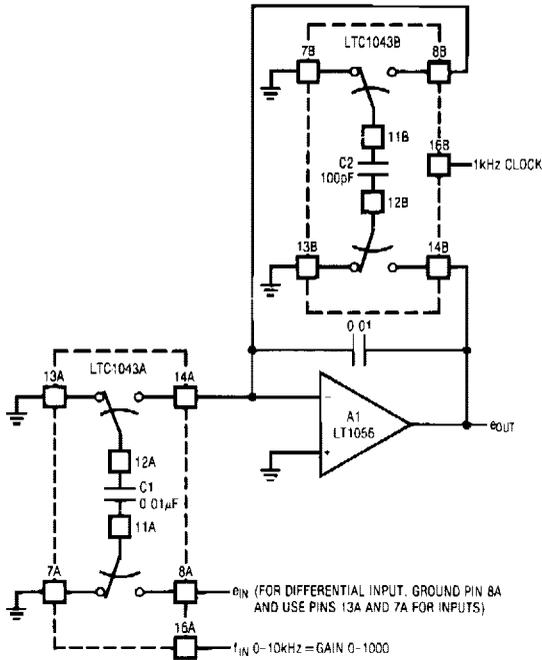
## WIDE RANGE DIGITALLY CONTROLLED VARIABLE-GAIN AMPLIFIER




LINEAR TECHNOLOGY CORP.

Fig. 78-3

The circuit uses the LTC1043 in a variable gain amplifier which features continuously variable gain, gain stability of 20 ppm/°C, and single-ended or differential inputs. The circuit uses two separate LTC1043s. LTC1043B is continuously clocked by a 1-kHz source, which could also be processor supplied. Both LTC1043s function as the sampled data equivalent of a resistor within the bandwidth set by A1's 0.01- $\mu$ F value and the switched-capacitor equivalent feedback resistor. The time-averaged current delivered to the summing point by LTC1043A is a function of the 0.01- $\mu$ F capacitor's input-derived voltage and the commutation frequency at pin 16. Low-commutation frequencies result in small time-averaged current values, and require a large input resistor. Higher frequencies require an equivalent small input resistor.
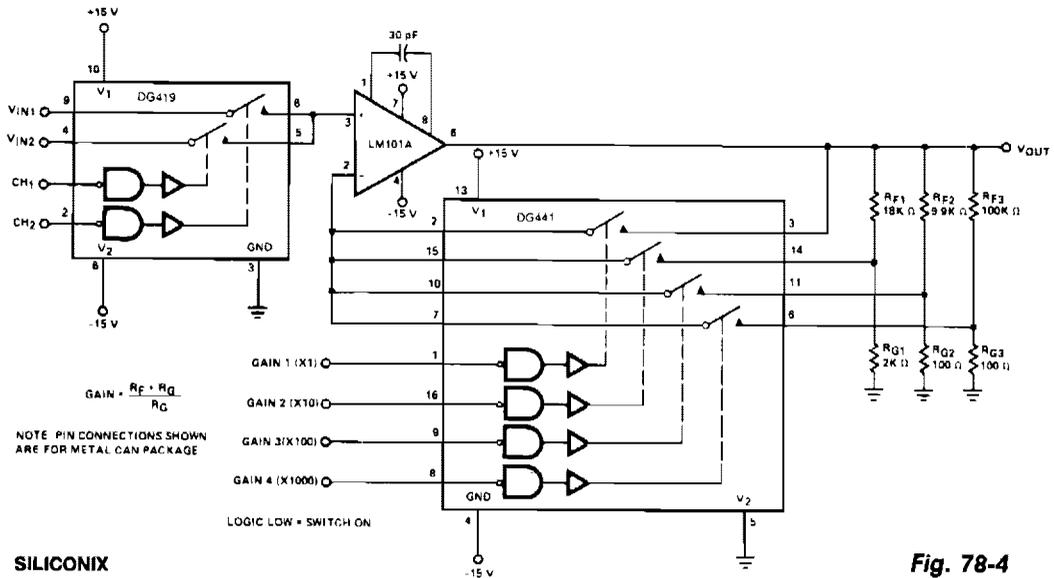
## DIGITALLY PROGRAMMABLE PRECISION AMPLIFIER




SILICONIX

Fig. 78-4

## DIGITALLY PROGRAMMABLE PRECISION AMPLIFIER (Cont.)

The DG419 *looks* into the high input impedance of the op amp, so the effects of  $R_{DS(on)}$  are negligible. The DG441 is also connected in series with  $R_{IN}$  and is not included in the feedback dividers, thus contributing negligible error to the overall gain. Because the DG419 and DG441 can handle  $\pm 15$  V, the unity gain follower connection, X1, is capable of the full op-amp output range of  $\pm 12$  V.
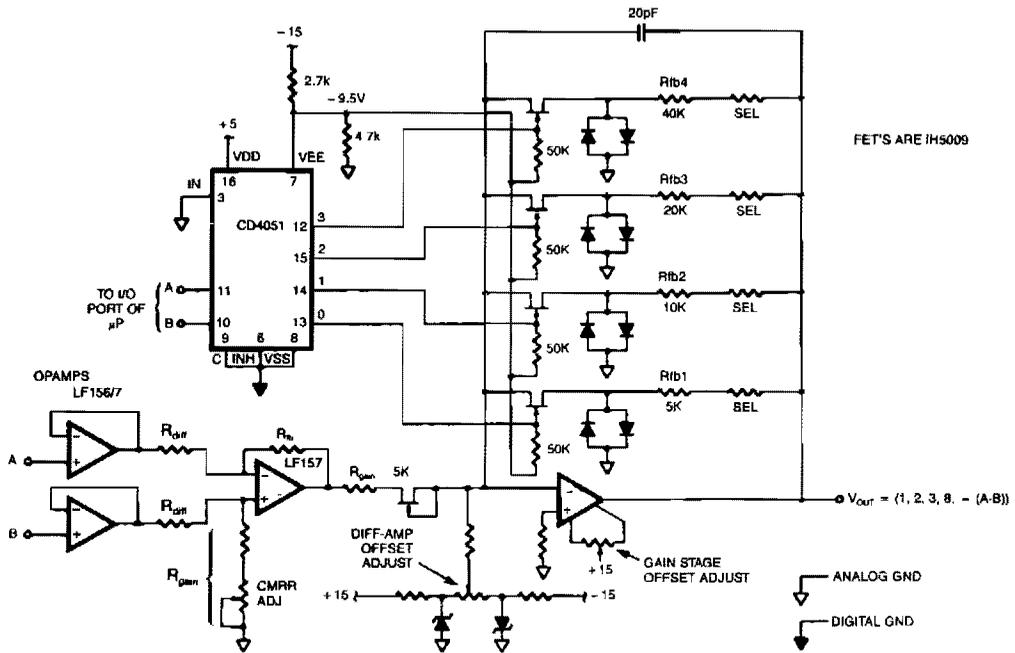
### PROGRAMMABLE-GAIN DIFFERENTIAL-INPUT AMPLIFIER




INTERSIL

b	a	Gain
0	0	X1
0	1	X2
1	0	X4
1	1	X8

Fig. 78-5

This programmable gain circuit employs a CD4051 CMOS Analog Multiplexer as a two to four line decoder, with appropriate FET drive for switching between feedback resistors to program the gain to any one of four values.

## PROGRAMMABLE AMPLIFIER

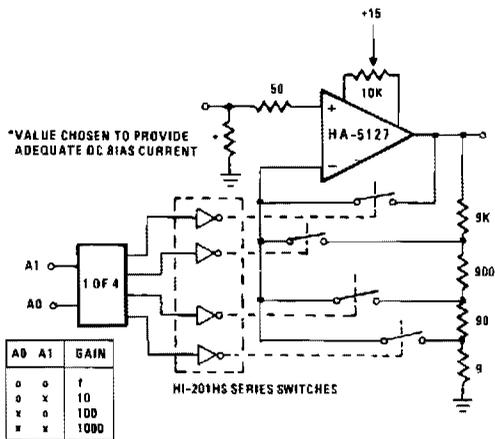

HARRIS

**Fig. 78-6**

Often a circuit will be called upon to perform several functions. In these situations, the variable gain configuration of this circuit could be quite useful. This programmable gain stage depends on CMOS analog switches to alter the amount of feedback, and thereby, the gain of the stage. Placement of the switching elements inside the relatively low-current area of the feedback loop, minimizes the effects of bias currents and switch resistance on the calculated gain of the stage. Voltage spikes can occur during the switching process, resulting in temporarily reduced gain because of the make-before-break operation of the switches. This gain loss can be minimized by providing a separate voltage divider network for each level of gain.

# 79


## Protection Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Electric Crowbars  
Ac Power-Line Connections Monitor  
Line-Voltage Monitor  
Power-Failure Alarm  
Ac Circuit Breaker  
Fast Overvoltage Protector

## ELECTRIC CROWBARS

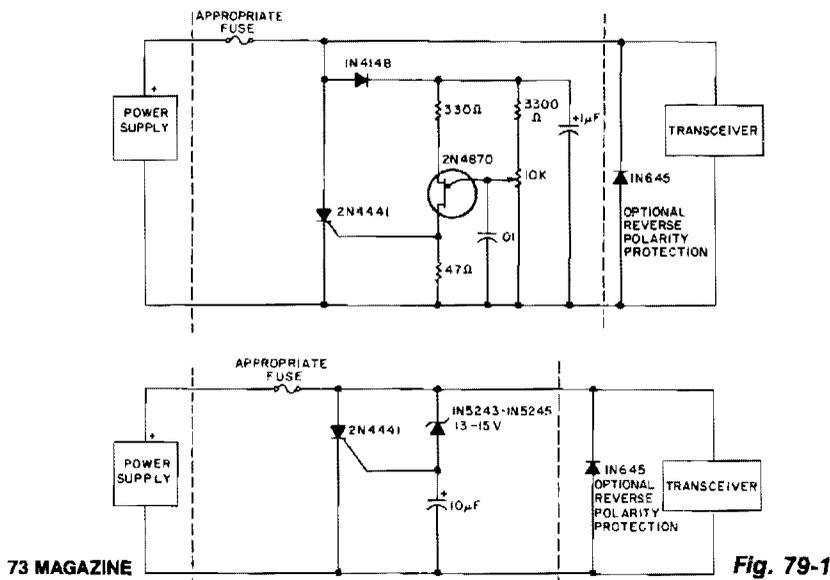


To avoid grief when using 12-V power supplies with mobile transceivers, especially when there is a short-circuit failure of the series pass transistor, crowbar circuits provide protection by clamping the power line and blowing the fuse within microseconds of an overvoltage condition. It is a good idea to incorporate the crowbar directly into the transceiver. The main difference between the two circuits is that less complex circuit B depends on component tolerances for the exact trigger level, while the circuit A includes a unijunction trigger to permit precise setting of the operating point.

## AC POWER-LINE CONNECTIONS MONITOR

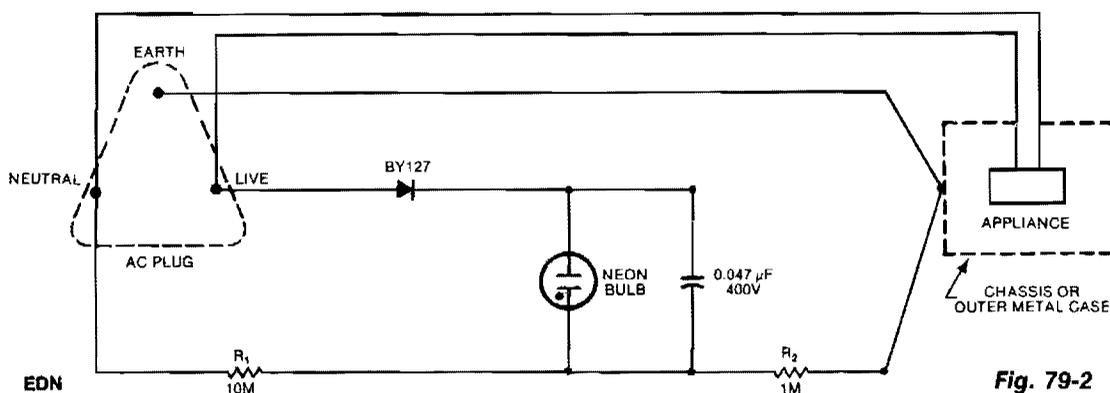

A continuous glow signifies that everything is normal; a blinking or extinguished neon bulb indicates a broken earth-ground connection, or interchanged neutral and live wires.

## LINE-VOLTAGE MONITOR

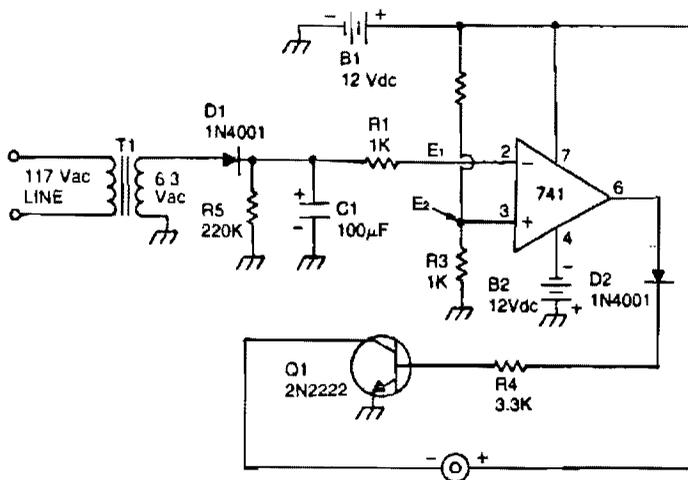


TAB BOOKS

MALLORY  
SONALERT\*

Fig. 79-3

This circuit uses a type 741 op amp as a voltage comparator. One input of the 741 is connected to a reference voltage (a 12-V battery) through a resistor voltage divider. The potential at the noninverting input of the 741 is approximately 3 V. The inverting input of the op amp comparator is connected to the output of a line-operated 8-V power supply. When the ac power main fails, T1 will no longer be energized, so the charge stored in capacitor C1 will begin to discharge through resistor R5. When the capacitor voltage drops below the reference voltage of 3 V, the output of the comparator becomes high. This output condition will forward bias transistor Q1, causing the Sonalert to sound the alarm. The time constant of the R5/C1 combination is 22 seconds—long enough to prevent noise from triggering the alarm.

## POWER-FAILURE ALARM

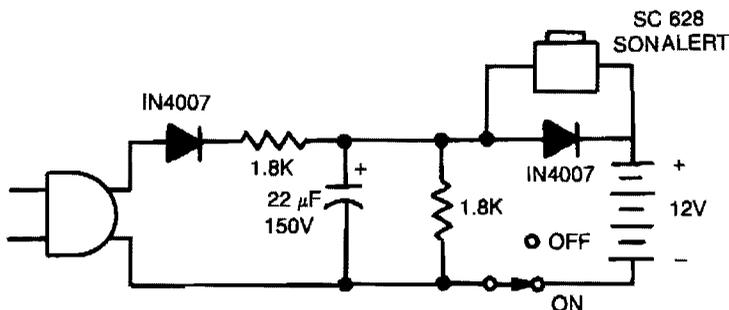


Reprinted with permission of William Sheets.

Fig. 79-4

With power ac off, the alarm sounds when S1 is closed on. The 12-V battery is kept charged when the circuit is plugged in and the switch is left on.


## AC CIRCUIT BREAKER

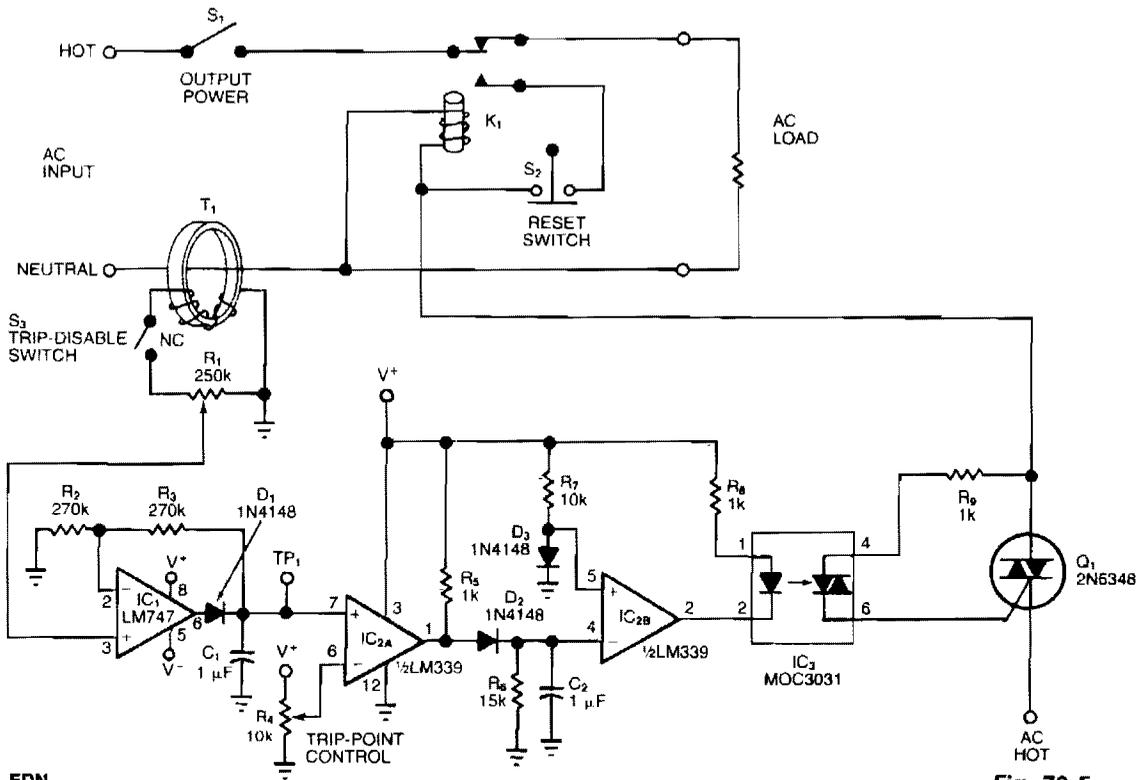

**Fig. 79-5**

The adjustable circuit breaker responds in 0.02 s under all conditions—provided you select a fast relay for K1. For moderate overload conditions, it's preferable to use the fuse or the fast-acting breaker. Toroid transformer T1 senses ac load current and produces an ac signal at the wiper of R1, when switch S3 is closed. Diode D1 rectifies this signal to produce a positive voltage at test point TP1. Because R1 allows you to calibrate this voltage, the circuit accommodates a variety of current-sense transformers. To calibrate the trip threshold, apply the maximum expected overload and adjust R1 until the TP1 voltage is 0.7 V below the positive saturation level for IC1. Then adjust R4 for the desired trip point. To reset the circuit breaker after it has tripped, open S1 or S2.

## FAST OVERVOLTAGE PROTECTOR

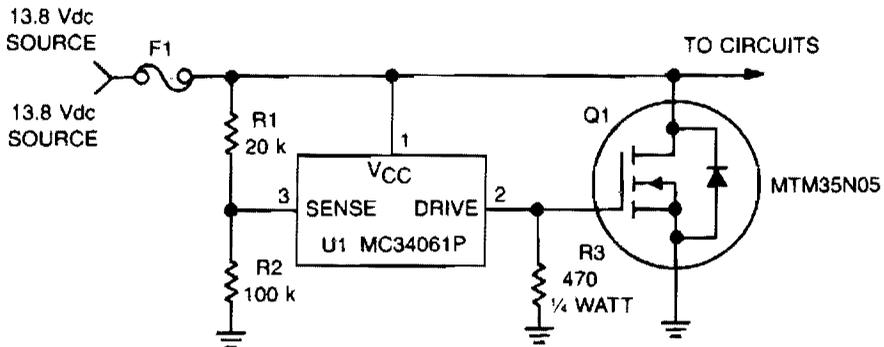

Copyright of Motorola, Inc. Used by permission.

**Fig. 79-6**

This circuit protects expensive portable equipment against all types of improper hookups and environmental hazards that could cause an overvoltage condition. It operates very quickly and does not latchup, that is, it recovers when the overvoltage condition is removed. In contrast, SCR overvoltage circuits can latch and do not recover, unless the power is removed.

Here, U1 senses an overvoltage condition when the drop across R1 exceeds 2.5 V. This causes U1 to apply a positive signal to the gate of Q1, turning it on and shorting the line going to the external circuits. Fuse 1 opens if the transient condition lasts long enough to exceed the  $i^2t$  rating.

# 80


## Proximity Sensors

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Capacitive Sensor Alarm  
UHF Movement Detector  
Proximity Switch  
SCR Proximity Alarm  
Proximity Sensor

## CAPACITIVE SENSOR ALARM

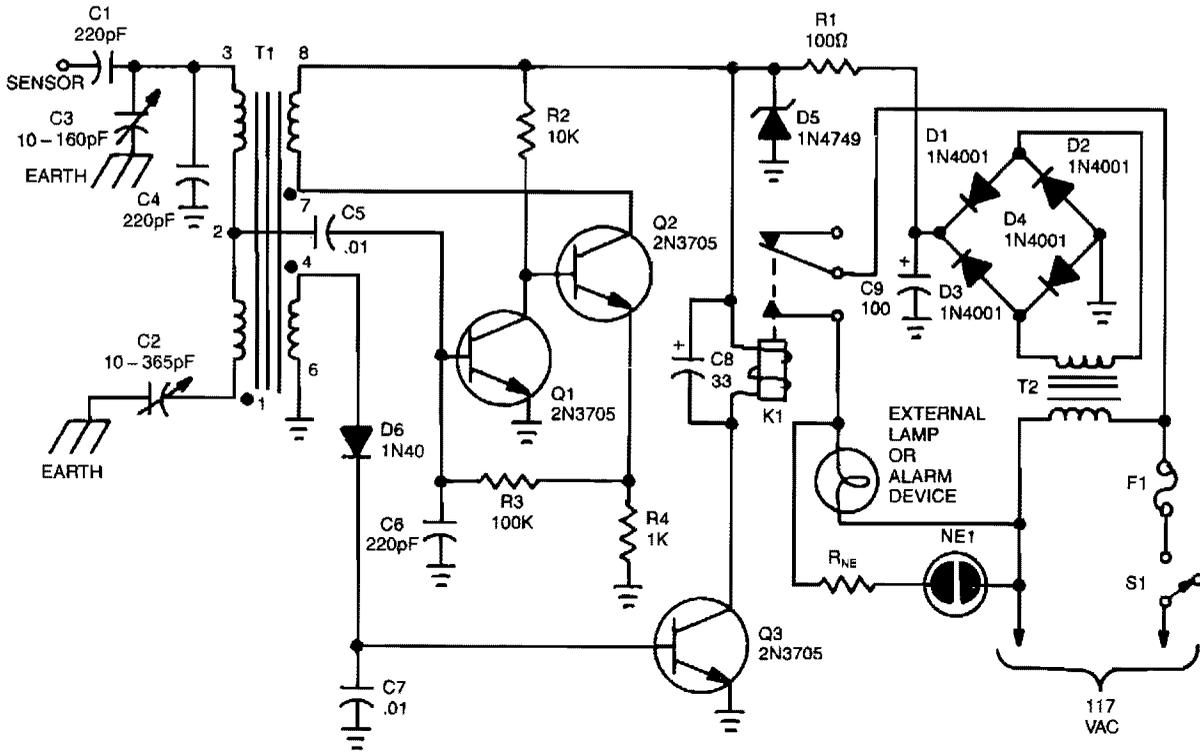


**Fig. 80-1**

The unit is constructed around a balanced-bridge circuit, using both capacitance and inductance. The bridge consists of capacitors C2 and C3, and the center-tapped winding of T1. One end of the bridge is coupled to ground by C4, while capacitance changes are introduced through C1. A small capacitance change unbalances the bridge and produces an ac signal at the base of Q1. Transistors Q1 and Q2 are connected to form a modified-Darlington amplifier. The collector load for Q2 is a separate winding of T1 that is connected out-of-phase with the incoming ac signal. That produces a large, distorted signal each time the bridge is unbalanced.

The distorted signal is taken from the bridge circuit by a third winding of transformer T1. That signal is then rectified by D6 and applied as a dc signal to the base of Q3. The applied signal energizes the relay, K1, as soon as the unbalanced condition occurs, and the relay drops out as soon as the circuit balance is restored. Of course, for normal alarm use, the relay should be made self-latching, so that the alarm condition remains in effect until the system is reset.

An audible alarm, such as a bell or klaxon horn, can be operated from the relay. If a silent alarm is needed, a light bulb can be used. Transformer T1 can be purchased as part #6182 from: Pulse Engineering, P.O. Box 12235, San Diego, CA 92112.

## UHF MOVEMENT DETECTOR

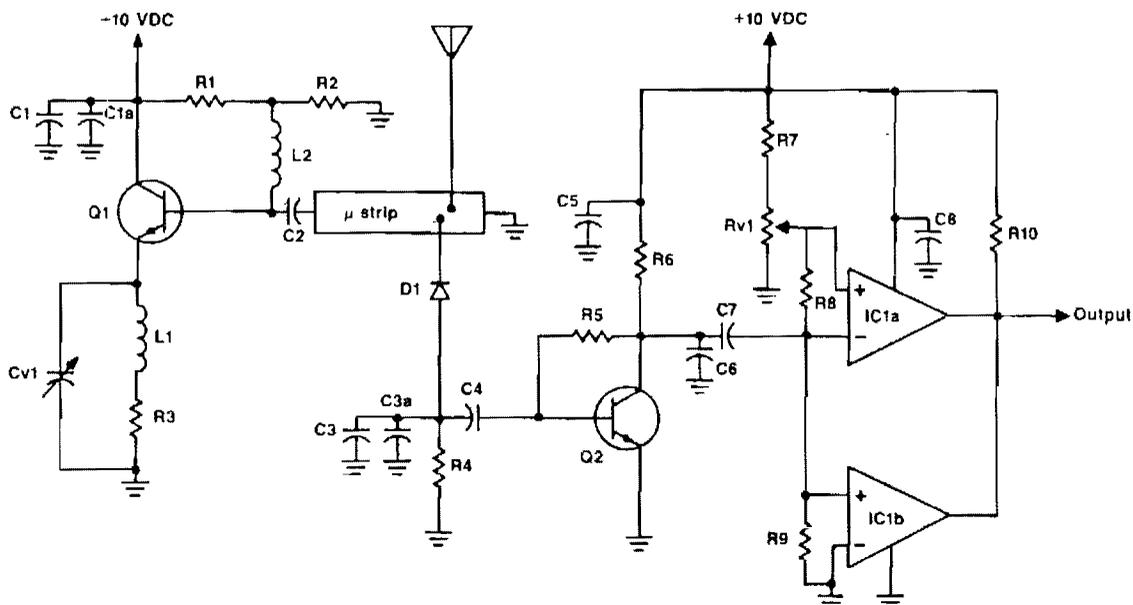

### Parts List

R1	3.9 k	C1	1 nF	D1	ISS97 or other Schottky type
R2, 4	1 k	C1a	470 uF	O1	MRF961
R3	100	C2	47 nF	Q2	BC548
R5	2.2 M	C3a	1 uF	Cv1	2-7 pF miniature
R6	68 k	C4	22 uF	IC1	LM339 comparator
R7	100 k	C5, 8	100 uF	L1	5 turns 0.86 mm wire on 35 mm core
R8, 9, 10	22 k	C6	100 nF	L2	4 turns 0.86 mm wire on 35 mm core
Rv1	1 k	C7	10 uF		

D. Huisman, RF Design, December 1986, p. 41.

**Fig. 80-2**

The oscillator is a standard UHF design which delivers about 10 mW at 1.2 GHz. R1 and R2 bias the base of Q1 to 1.2 V via L2. Collector current is set by R3 to about 30 mA. C2 couples the base of Q1 to the stripline circuit. Tuning is provided by CV1, and C1 plus C1a decouple the collector. R2 and R3 are not decoupled, since this could cause instability.

Q2 is a simple one-transistor amplifier. C4 and C7 reduce gain below 1.5 and above 100 Hz; the remaining band of frequencies is amplified and passed on to the level detector. Two comparators of IC1 provide level detection. The trigger voltage is set by R7, Rv1, R8, and R9; it is adjustable from 8 to 60 mV by Rv1.

Positive voltage swings above the trigger level cause the IC1a output to become low, while negative swings cause IC1b to become low. C8 decouples IC1 from the power supply, and R10 is a pull-up resistor for the open collector output of IC1.

## PROXIMITY SWITCH

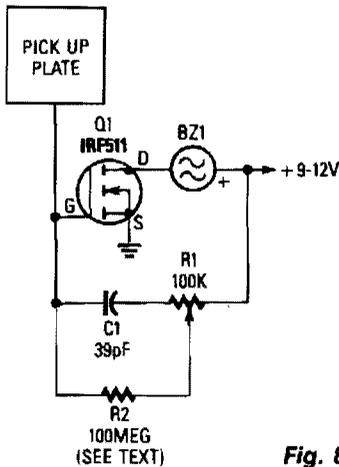



Fig. 80-3

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

A 3- $\times$ -3-inch piece of circuit board, or similar size metal object which functions as the pick-up sensor, is connected to the gate of Q1. A 100-M $\Omega$  resistor, R2, isolates Q1's gate from R1, allowing the input impedance to remain very high. If a 100-M $\Omega$  resistor cannot be located, just tie five 22-M $\Omega$  resistors in series and use that combination for R2. In fact, R2 can be made even higher in value for added sensitivity.

Potentiometer R1 is adjusted to where the piezo buzzer just begins to sound off and then carefully backs off to where the sound ceases. Experimenting with the setting of R1 will help in obtaining the best sensitivity adjustment for the circuit. Resistor R1 can be set to where the pick-up must be contacted to set off the alarm sounder. A relay or other current-hungry component can take the place of the piezo sounder to control most any external circuit.

## SCR PROXIMITY ALARM

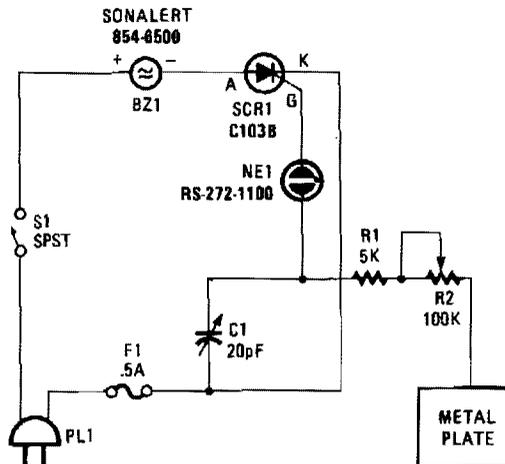

HANDS-ON ELECTRONICS

Fig. 80-4

## PROXIMITY SENSOR

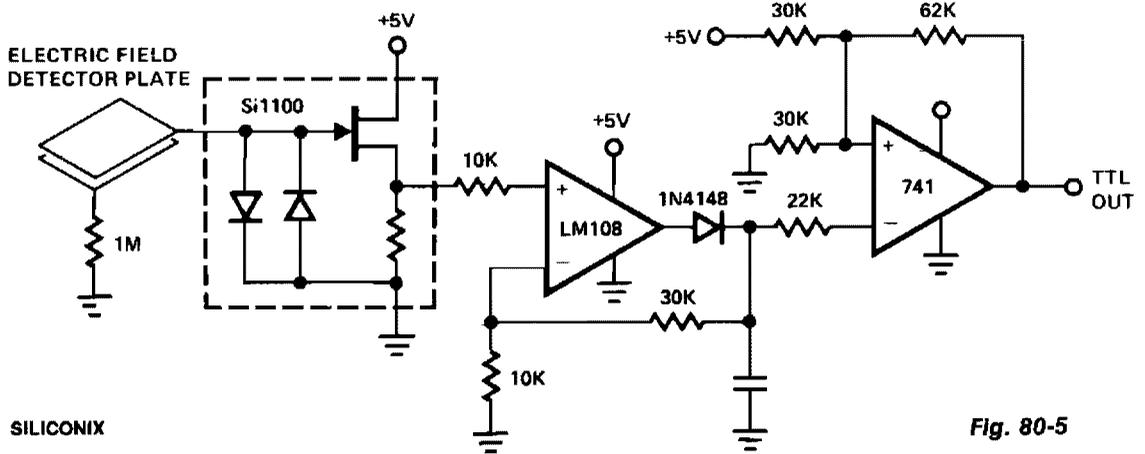


Fig. 80-5

The Si1100 series circuit input is connected to a capacitive field sensor—possibly a piece of double-sided circuit board. Any induced voltage change on the plate is fed to the input of the peak detector section of the op-amp circuit. The Schmitt trigger monitors the voltage across the capacitor and changes its output state when the capacitor voltage crossed the 2.5-trigger point. The output from the Schmitt trigger switches between 0 and 5 V and is microprocessor compatible for sensor applications, such as computer-controlled intruder alarms.

# 82


## Ramp Generators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

- Logic Pulser
- 300-V Pulse Generator
- Very Low Duty-Cycle Pulse Generator
- Wide-Ranging Pulser
- CMOS Short-Pulse Generator
- Voltage Controller/Pulse-Width Generator

## LOGIC PULSER

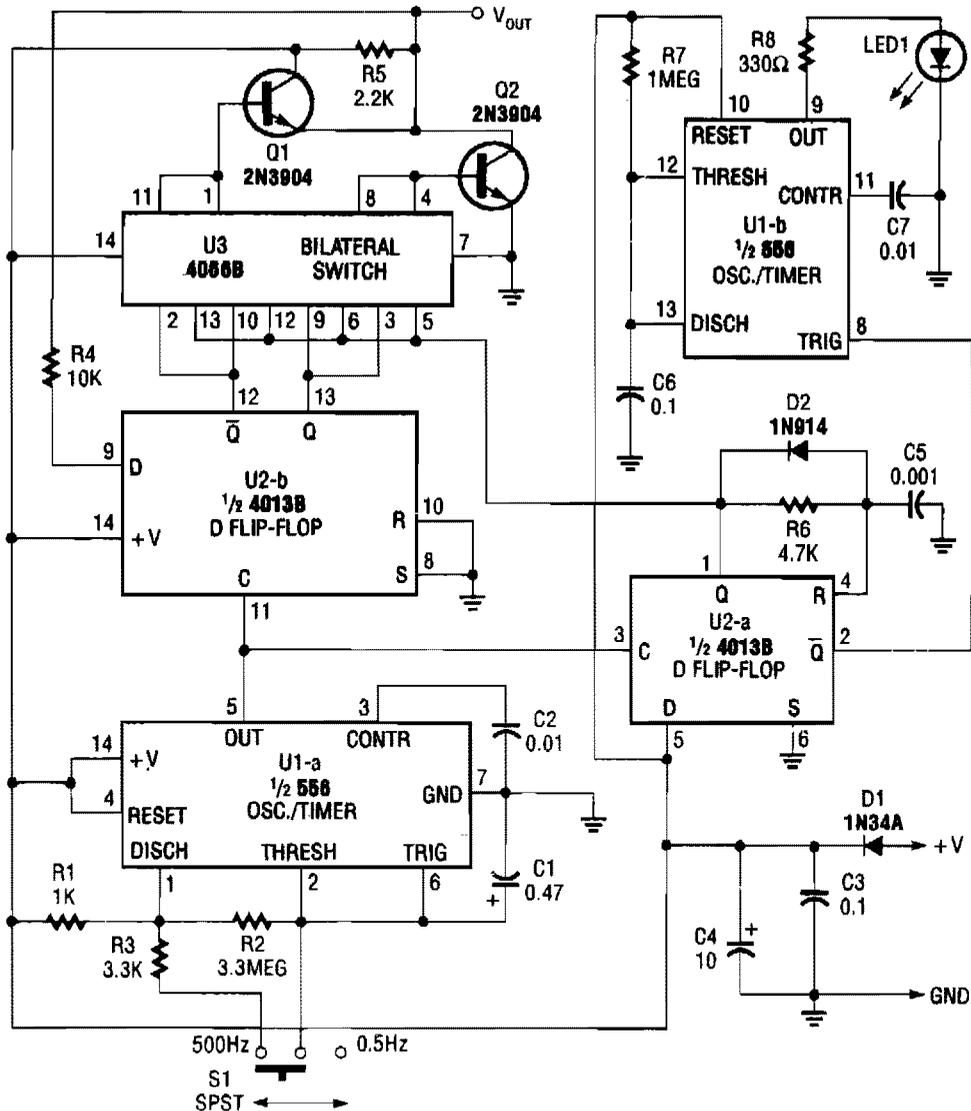

**Fig. 81-1**

POPULAR ELECTRONICS

The pulser generates pulses at a user-selected frequency of 0.5 or 500 Hz, with a pulse width of about 5 ms. If the input to be pulsed is already being driven high or low by another output, the pulser automatically pulses the input to the opposite logic state. The pulser is powered by the circuit under test, and operates from supplies of from +5 to +15 Vdc.



## WIDE-RANGING PULSER

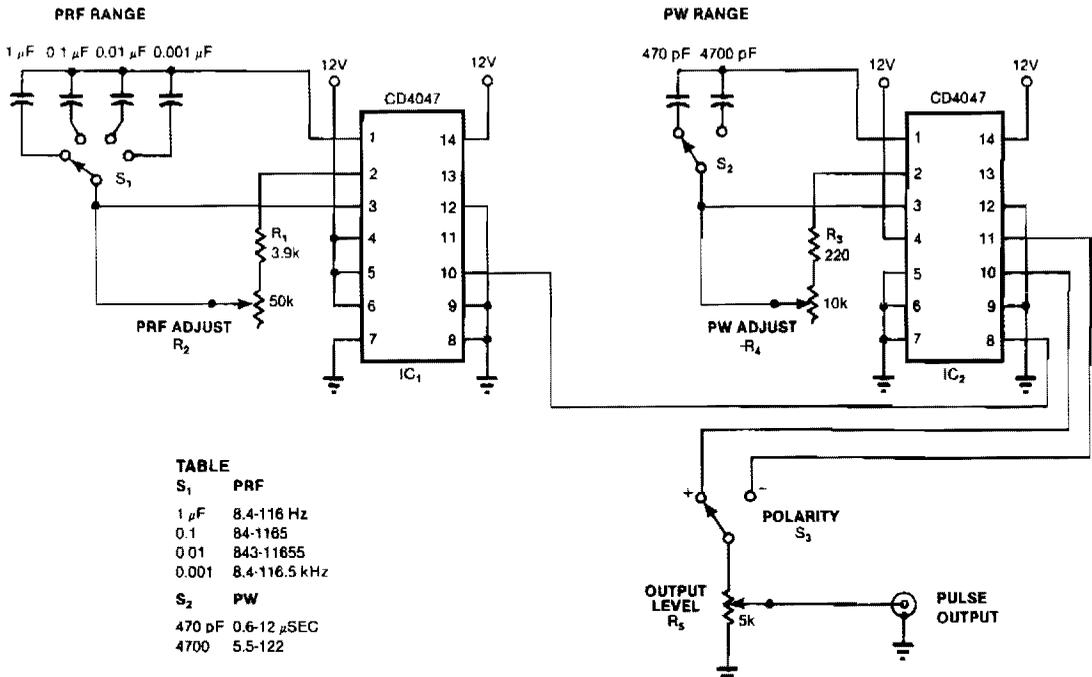



TABLE	
S <sub>1</sub>	PRF
1 μF	8.4-116 Hz
0.1	84-1165
0.01	843-11655
0.001	8.4-116.5 kHz
S <sub>2</sub>	PW
470 pF	0.6-12 μSEC
4700	5.5-122

EDN

Fig. 81-4

An output pulse's characteristics depend upon two multivibrator's timing components. IC1's free-running astable-mode frequency sets the pulse's prf, whereas the pulse's width comes from IC2's monostable operation.

## CMOS SHORT - PULSE GENERATOR

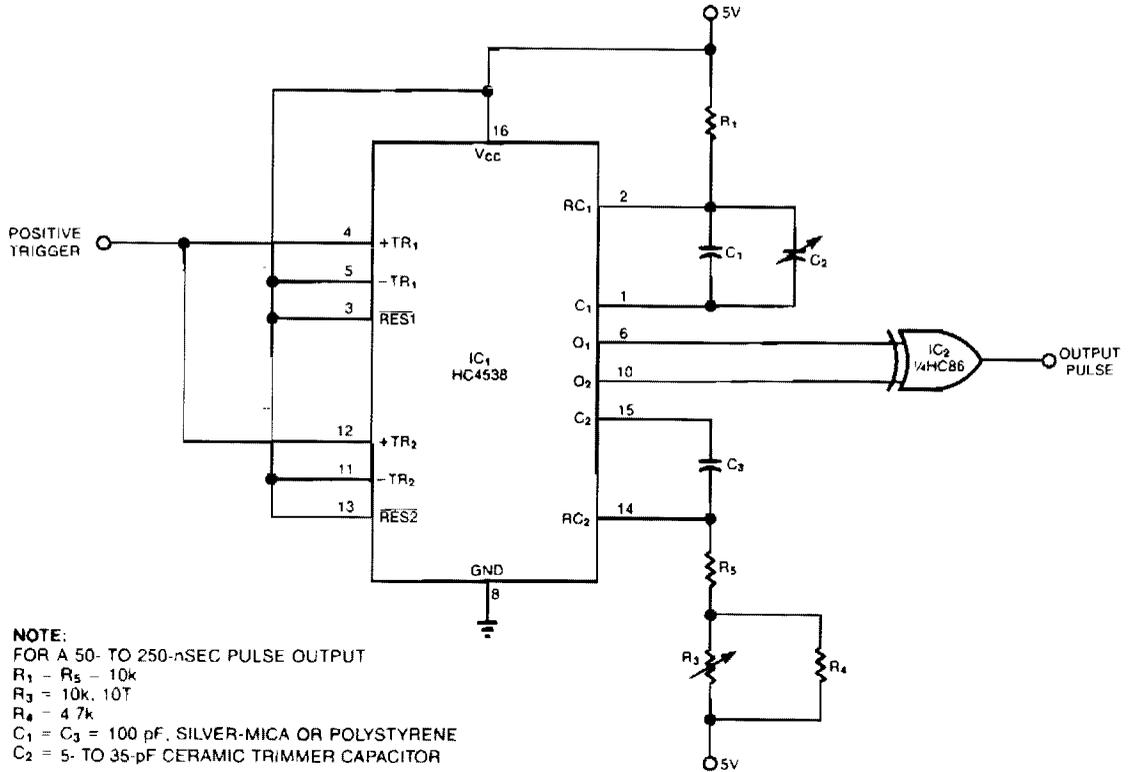


EDN

Fig. 81-5

Comprising two low-power, CMOS chips, the pulse generator produces a precise pulse width in the 50 to 500 ns range. IC1 is a dual monostable multivibrator (one shot) in which each positive trigger pulse initiates simultaneous positive output pulses at pins 6 and 10. In response, XOR gate IC2 produces a positive pulse whose duration is equal to the difference between the two input-pulse durations. Section 1 of the one shot generates an approximate 1- $\mu$ s reference pulse—shorter pulses are more susceptible to manufacturing variations caused by parasitic layout capacitance. Variable capacitor C2 lets you adjust this pulse width. Section 2 of the one shot generates a variable-length pulse; you adjust its width by using potentiometer R3. Resistors R4 and R5 set the output pulse's maximum and minimum width, respectively. Because the XOR gate's rise and fall times are about 20 ns for reasonable values of load capacitance, you should calibrate the circuit using C2 for a minimum output-width of 50 ns.
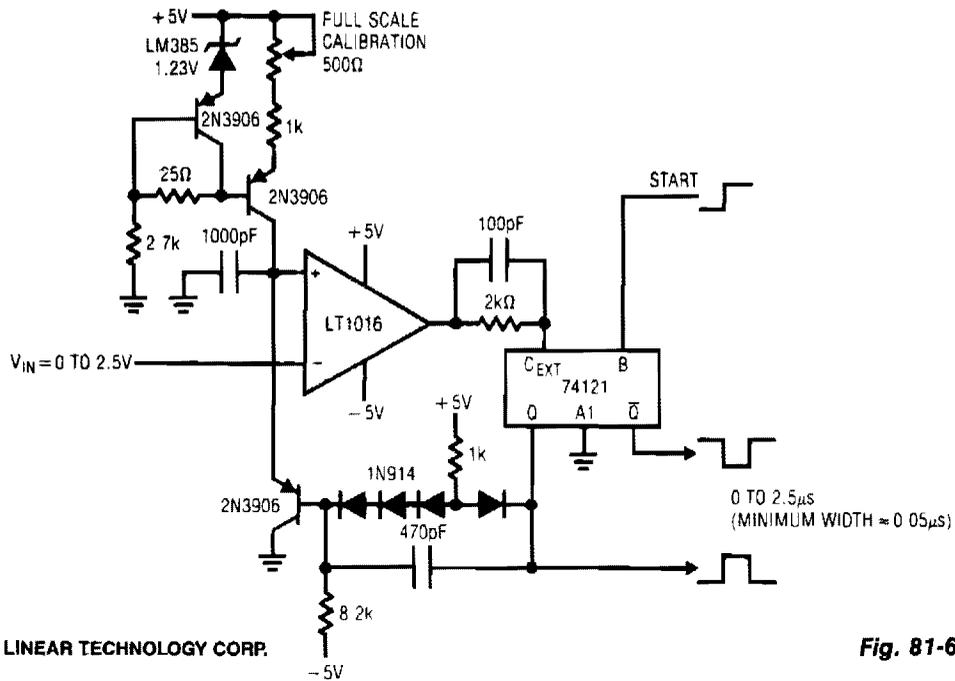
## VOLTAGE CONTROLLER/PULSE-WIDTH GENERATOR



LINEAR TECHNOLOGY CORP.

Fig. 81-6

# 82

## Ramp Generators


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Accurate Ramp Generator

Integrator/Ramp Generator with Initial Condition Reset

## ACCURATE RAMP GENERATOR

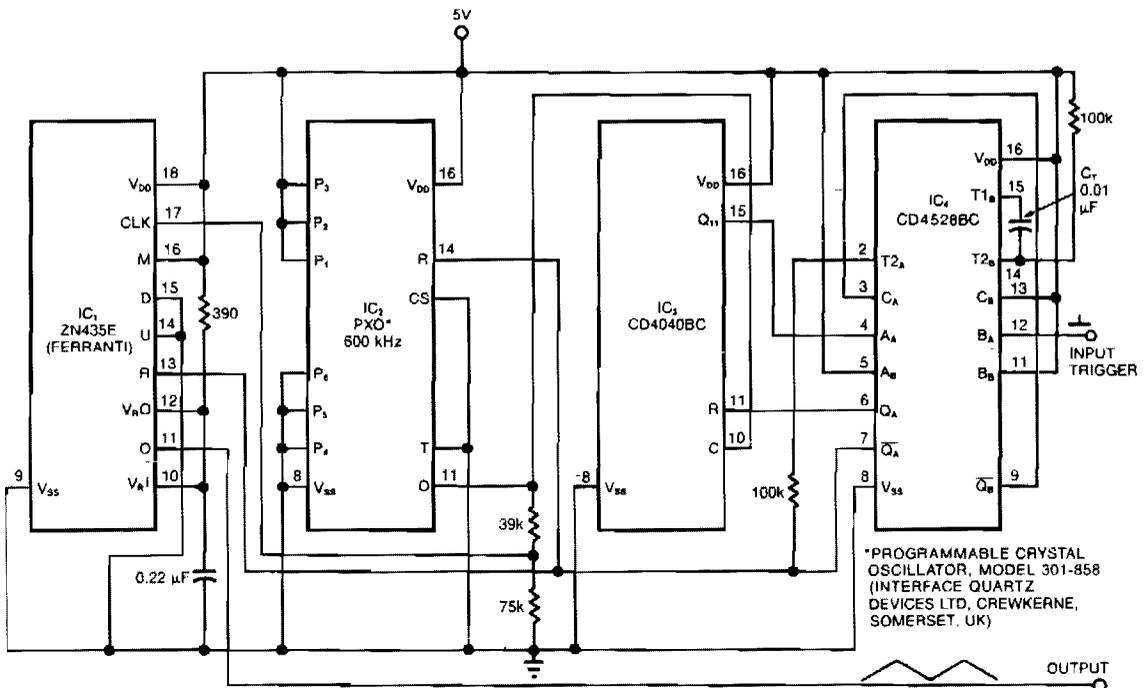


EDN

Fig. 82-1

The ramp generator, an inexpensive alternative to commercial function generators, provides a more linear and repeatable output than conventional analog integrators. The circuit provides a triangle waveform in burst mode; in this case, two cycles of 10.24 ms each per input trigger pulse. IC4 is a dual monostable multivibrator (one shot) in which the A side is configured as a latch (see *Multivibrator IC performs extra tasks*, EDN, September 6, 1984, p. 232). The rising edge of each input pulse triggers the B side, producing at pin 9 an output pulse whose duration depends on the timing capacitor's,  $C_T$ , value—A 0.01- $\mu$ F value gives a 500  $\mu$ s pulse. This output provides a reset to the A side latch. While the latch is reset with  $Q_A$  high,  $\bar{Q}_A$  low, the other three ICs are active. The P1 through P6 connections, as shown, set oscillator IC2's frequency to 50 kHz at pin 11.

Counter IC3 counts upward. The output at pin 11 of multifunction converter IC1 ramps up to full-scale, reverses, ramps down to zero, and then repeats this sequence of events. As this output completes its second cycle, IC3 reaches a count of 1024, causing the Q11 output to become high and toggle the IC4 latch. The resulting change of state on  $Q_A$  and  $\bar{Q}_A$  resets the other three ICs, terminating further activity until the arrival of the next input trigger pulse. IC2 is included for its synchronous-reset capability, and it therefore drives the internal clock of IC1, which cannot be synchronously reset. Still IC2 can be omitted in some applications. The circuit operates from a 5-V supply. You can modify the output by changing IC2's frequency and IC3's output connection.

## INTEGRATOR/RAMP GENERATOR WITH INITIAL CONDITION RESET

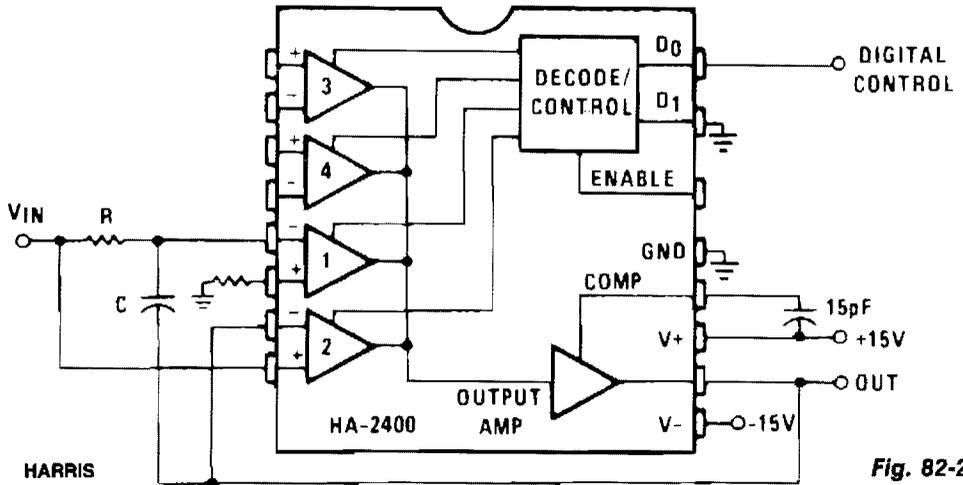

**Fig. 82-2**

Channel 1 is wired as a conventional integrator, and channel 2 as a voltage follower. When channel 2 is switched on, the output will follow  $V_{IN}$  and  $C$  will discharge to maintain 0 V across it. When channel 1 is then switched on, the output will initially be at the instantaneous value of  $V_{IN}$ , and then will commence integrating towards the opposite polarity. This circuit is particularly suitable for timing ramp generation using a fixed dc input. Many variations, such as building programmable time constant integrators, are possible.

# 83

## Receivers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

AM Radio	FSK Data Receiver
FM Tuner	Simple Ham-Band Receiver
FM MPX/SCA Receiver	Digital Data Line Receiver
Narrow-Band FM Receiver	Integrated AM Receiver
Low-Cost Line Receiver	

## AM RADIO

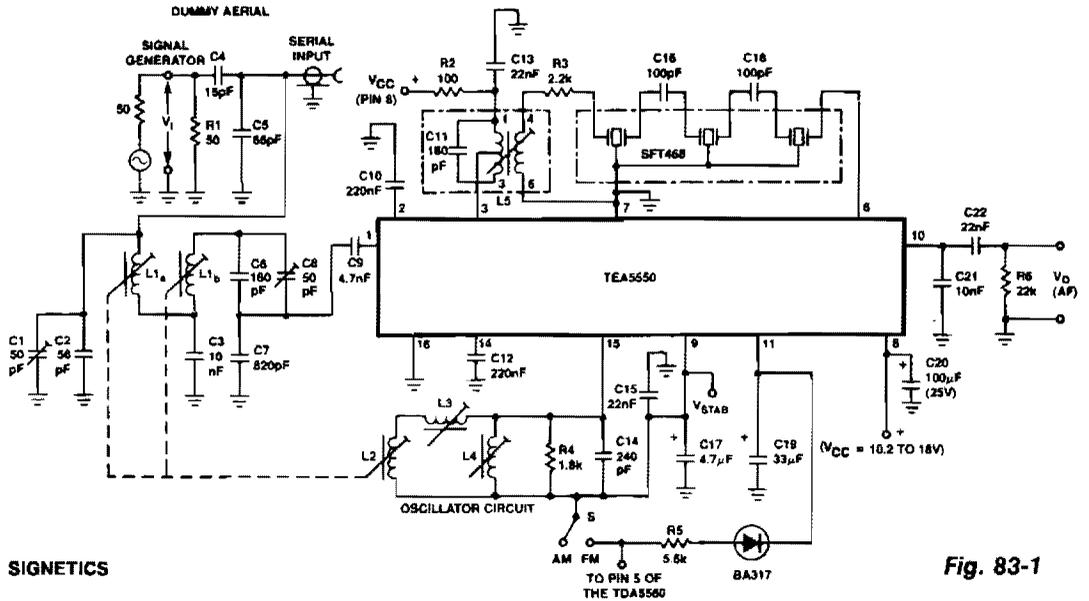


Fig. 83-1

### SIGNETICS


#### NOTES:

- Coil data  
 L1<sub>a</sub>, L1<sub>b</sub>, L2 = Tuning coils; ALPS unit MMK (HEI) (for coil connections see Figure 7)  
 L3 = Trimming coil (4.7μH), catalog number 3122 138 27460  
 L4 = Padding coil (200μH), catalog number 3111 118 23510  
 L5 = IF coil, catalog number 3122 138 91481

S is AM/FM switch, for printed circuit board see Figures 7 and 8

This circuit diagram is for a double-tuned, AM-channel, in-car radio receiver using the TEA5550.

## FM TUNER

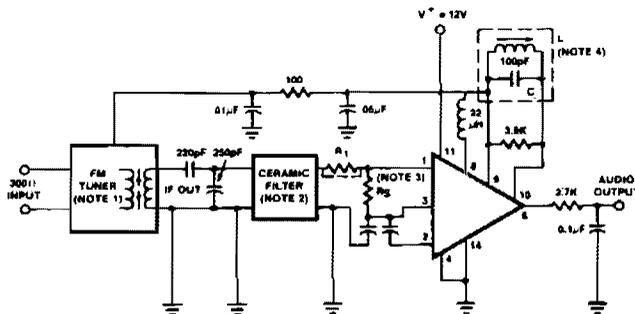

#### NOTES:

- All resistor values are typical and in ohms  
 1. Waller 4SN3FC or equivalent.  
 2. Murata SFG 10.7mA or equivalent.  
 3. R<sub>2</sub> will affect stability depending on circuit layout. To increase stability R<sub>2</sub> is decreased. Range of R<sub>2</sub> is 330  
 4. L tunes with 100pF (C) at 10.7MHz Q<sub>0</sub> unloaded ≈ 75 (G.I. EX27825 or equivalent).

Performance data at f<sub>0</sub> = 96MHz, f<sub>MOD</sub> = 400Hz, deviation = ± 74kHz.

1.74kHz.


-30dB limiting sensitivity  
 20dB quieting sensitivity  
 30dB quieting sensitivity

2μV (antenna level)  
 1μV (antenna level)  
 1.5μV (antenna level)

### SIGNETICS


Fig. 83-2

# FM MPX/SCA RECEIVER

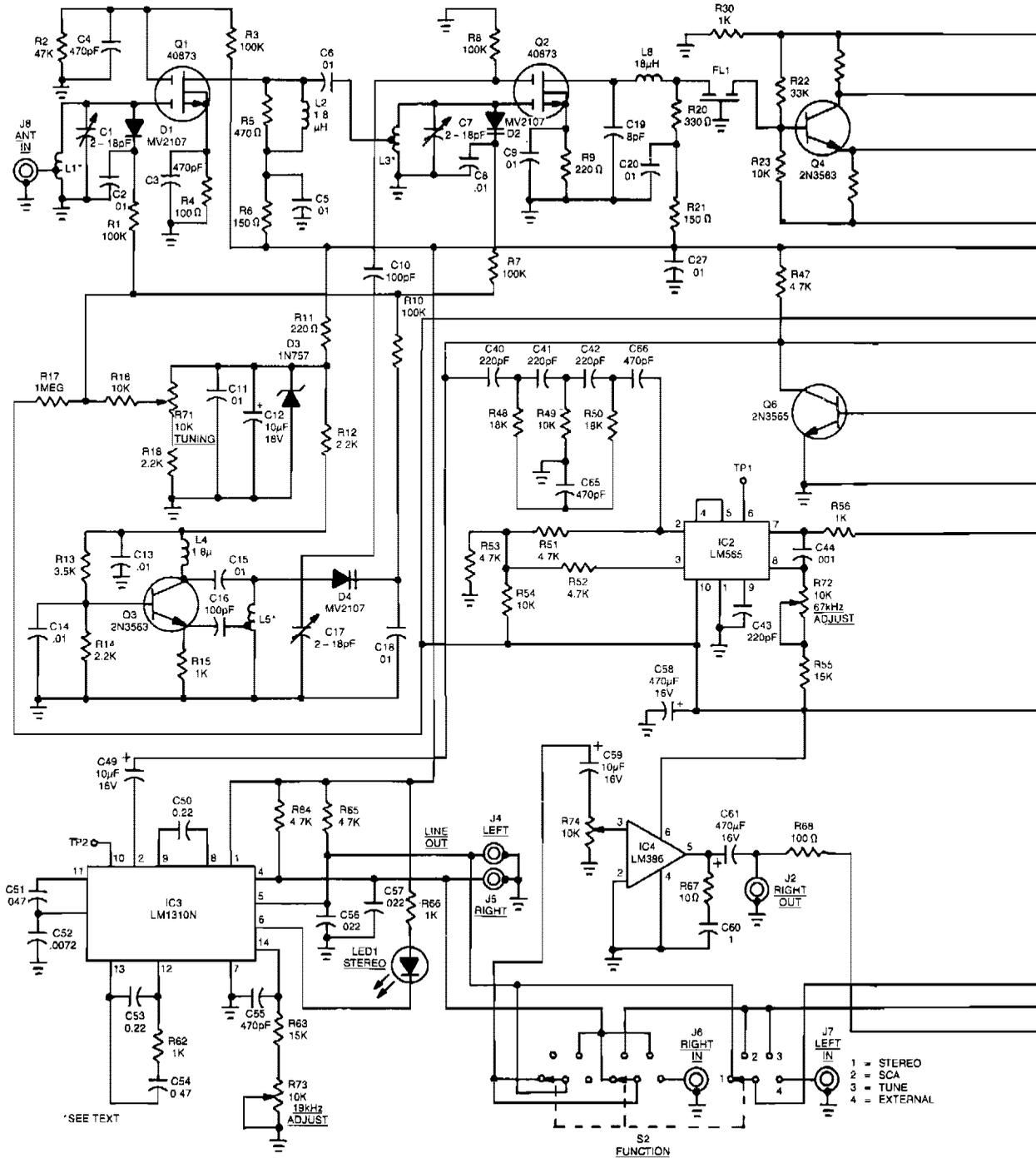


\*Reprinted with permission from Radio-Electronics Magazine, August 1987. Copyright Gernsback Publications, Inc., 1987.

Fig. 83-3

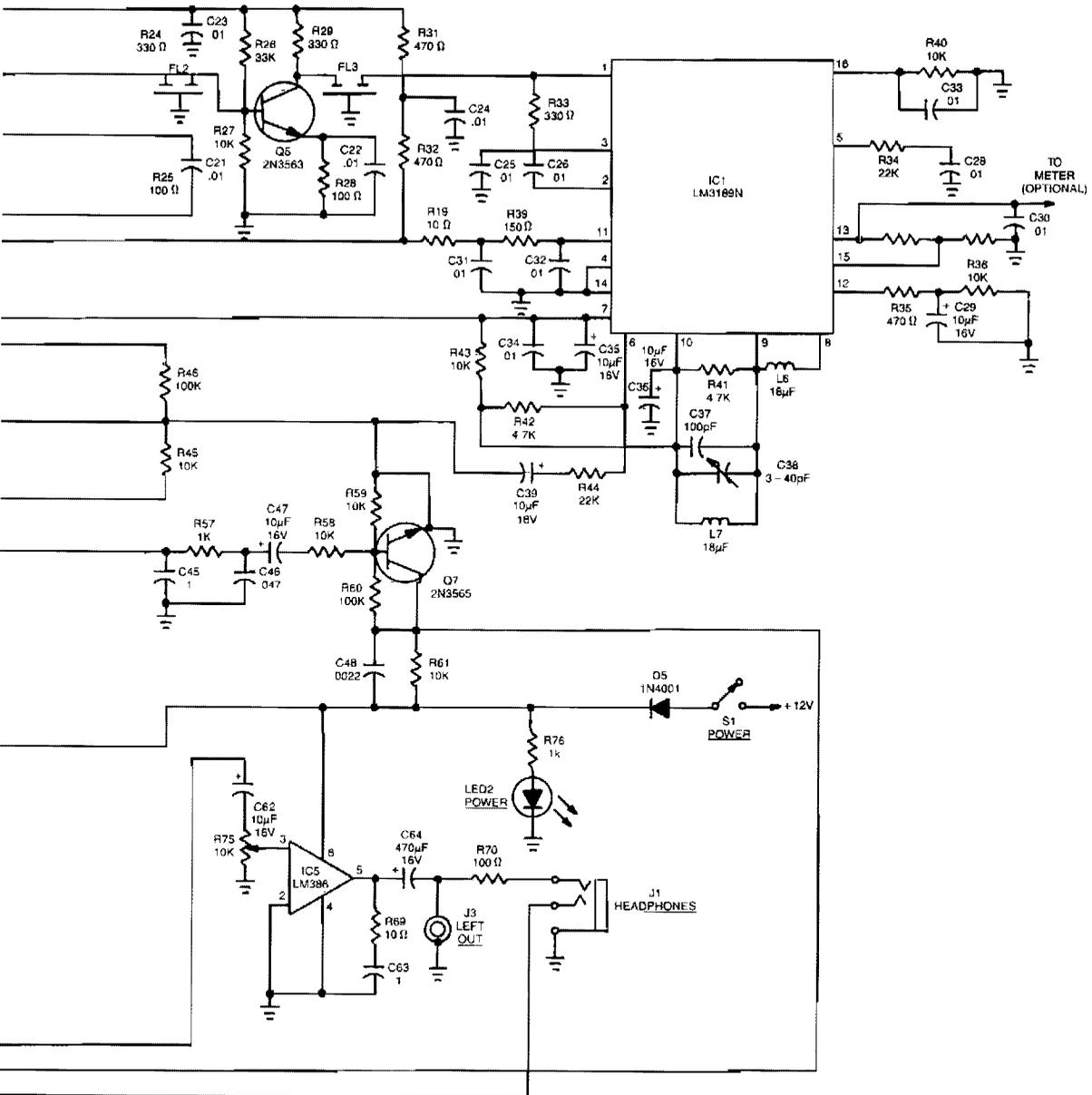

This receiver is capable of better than  $1.5 \mu$  VIHF sensitivity and uses MOSFET front-end circuitry with varactors to eliminate conventional bulky tuning capacitors. It also features high dynamic range, ceramic i-f filters requiring no alignment, and a quadrature-type detector with excellent limiting and AM rejection capability. The receiver operates from nominal 12-V supply. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.


## NARROW-BAND FM RECEIVER

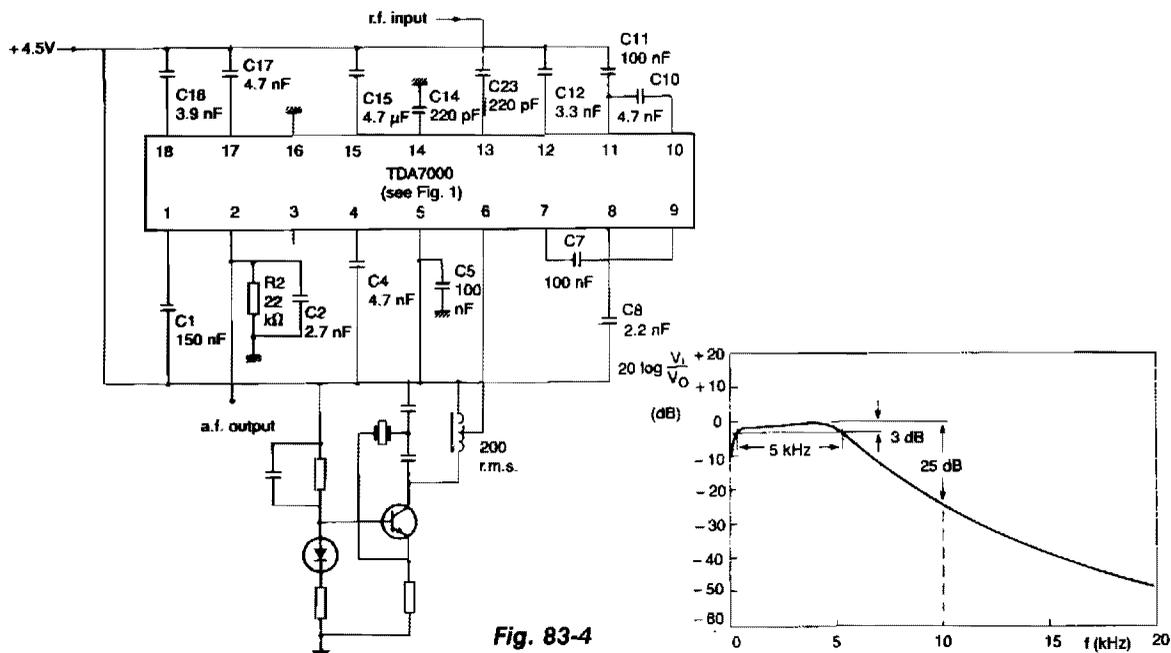

**Fig. 83-4**

The local oscillator is crystal-controlled and the i-f swing is hardly compressed. The deviation of the transmitted carrier frequency, because of modulation, must therefore be limited to prevent severe distortion of the demodulated audio signal. The component values result in an i-f of 4.5 kHz and an i-f bandwidth of 5 kHz. If the i-f is multiplied by  $N$ , the values of capacitors C17 and C18 in the all-pass filters, and the values of filter capacitors C7, C8, C10, C11, and C12 must be multiplied by  $1/N$ . For improved i-f selectivity to achieve greater adjacent channel attenuation, second-order networks can be used in place of C10 and C11.

## LOW-COST LINE RECEIVER

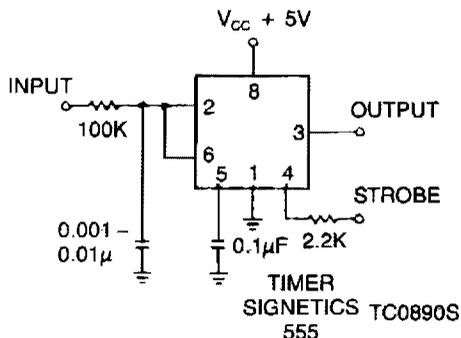


This timer makes an excellent line receiver for control applications involving relatively slow electromechanical devices. It can work without special drivers over single, unshielded lines.

NOTE:  
ALL RESISTOR VALUES ARE IN OHMS.

SINETICS

**Fig. 83-5**

## FSK DATA RECEIVER

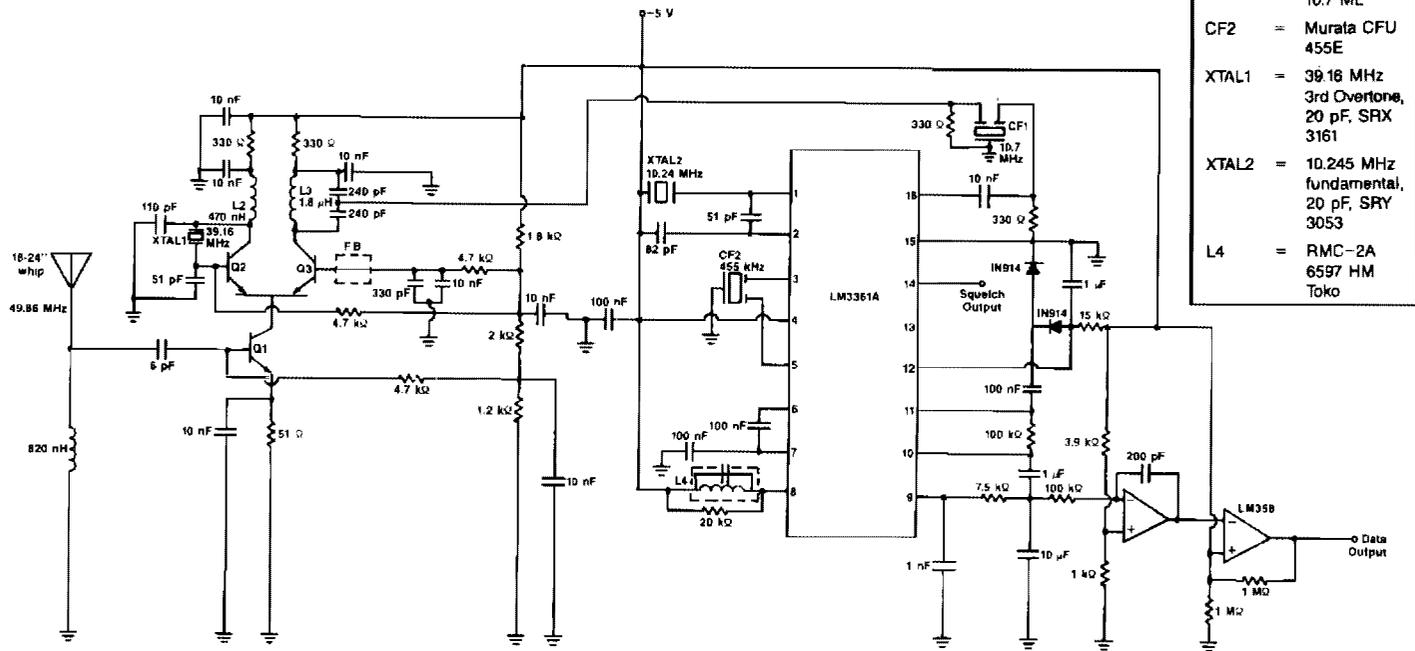


Parts List	
Q <sub>1,2,3</sub>	= MPSH 20
CF1	= Murata SFE 10.7 ML
CF2	= Murata CFU 455E
XTAL1	= 39.16 MHz 3rd Overtone, 20 pF, SRX 3161
XTAL2	= 10.245 MHz fundamental, 20 pF, SRY 3053
L4	= RMC-2A 6597 HM Toko

M. Lee, "A Simple FSK Data Receiver," RF Design, March 1987, p. 46.

Fig. 83-6


The various signal frequencies are obtained for an incoming carrier centered at 49.86 MHz. The receiver employs double conversion, with *i*-fs at 10.7 MHz and 455 kHz. Ceramic filters are used in both *i*-fs for selectivity and reduced-coil count. A quadrature detector is used to recover the baseband data, and an integrator and Schmitt trigger are used to filter the demodulated output. Also included is a squelch circuit that functions as a status line, and the open-collector output switches high when a signal is received. The LM3361A functions as the 2nd LO, 2nd mixer, limiting *i*-f, quadrature detector, and squelch; yet, it consumes less than 4 mA from a 5-V logic supply. The entire receiver requires approximately 10 mA.

## SIMPLE HAM-BAND RECEIVER

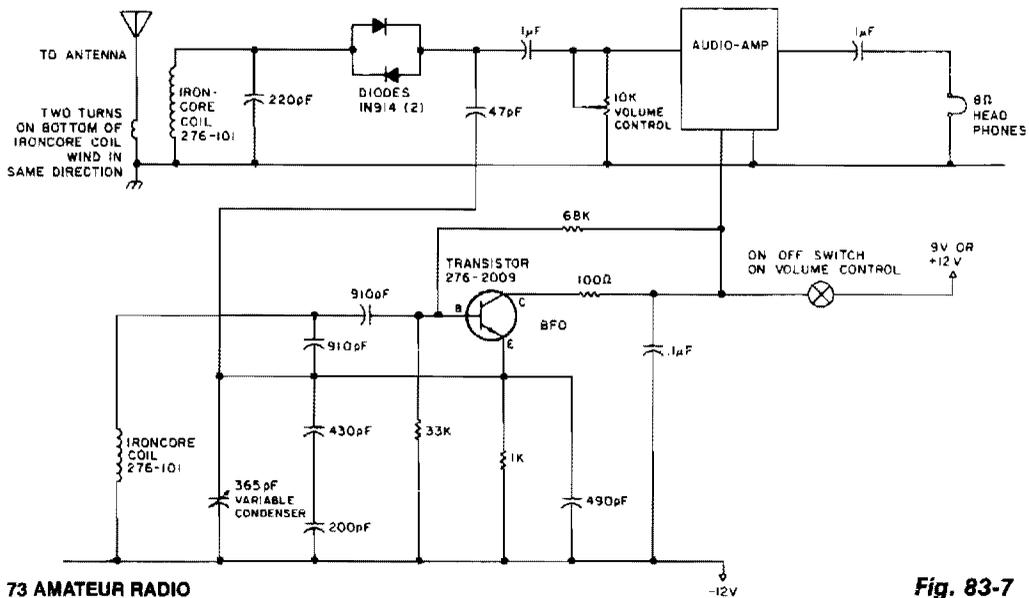


This circuit is configured for the 80m band. The 365-pF, broadcast-band variable capacitor should have a vernier drive with a six-to-one ratio, which makes tuning easier by separating the stations on the dial. A good antenna and ground are also recommended. The Radio Shack iron-core chokes (276-101), used in the bfo part of the circuit, can be calibrated by listening for the bfo signal in a calibrated receiver.

## DIGITAL DATA LINE RECEIVER

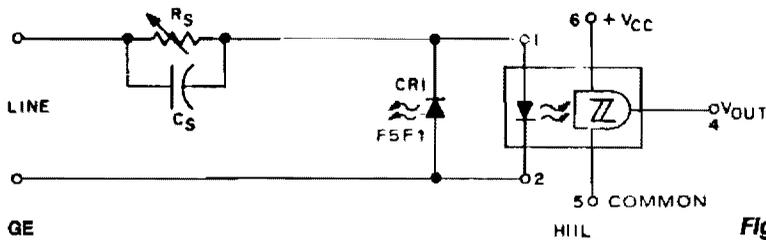

When digital data is transmitted over long lines (longer than 1 meter), proper transfer is often disturbed by the parasitic effects of ground level shifts and ground loops, as well as by extraneous noise picked up along the way. An optocoupler, such as the H11L, combining galvanic isolation to minimize ground loop currents and their concomitant common-mode voltages, with predictable switching levels to enhance noise immunity, can significantly reduce erratic behavior. Resistor  $R_S$  is programmed for the desired switching threshold,  $C_S$  is an optional speed-up capacitor, and CR1 is an LED used as a simple diode to provide perfect line balance and a discharge path for  $C_S$  if the speed-up capacitor is used.

## INTEGRATED AM RECEIVER

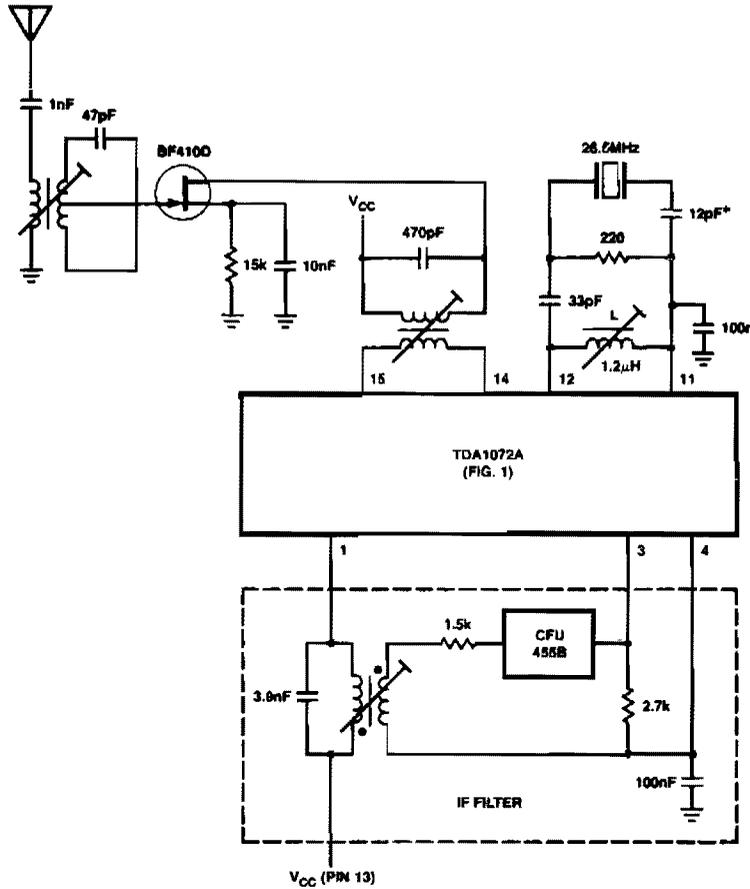

**NOTE:**  
A crystal Oscillator is used so that a narrow-band hybrid IF filter can be used.

**SIGNETICS**

**Fig. 83-9**

This circuit has aerial and local oscillator circuits for a 27-MHz receiver for remote control of garage doors, projectors, curtains, etc.

# 84


## Rectifier Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Precision Full-Wave Rectifier  
Diodeless Precision Rectifier

## PRECISION FULL-WAVE RECTIFIER

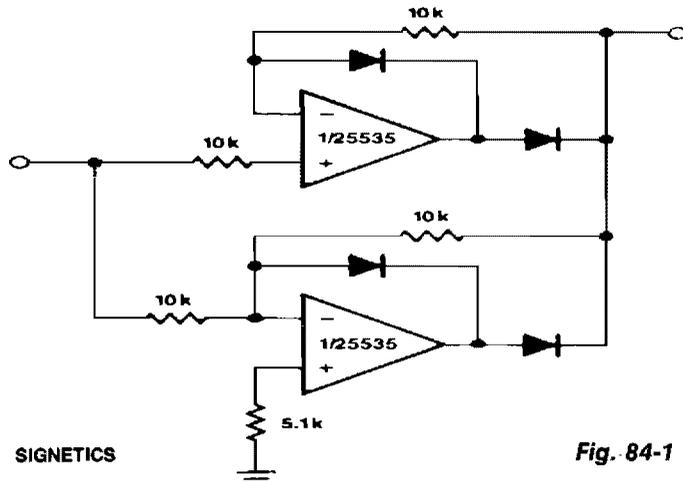

This circuit provides accurate full-wave rectification. The output impedance is low for both input polarities, and the errors are small at all signal levels. Note that the output will not sink heavy currents, except a small amount through the 10-K $\Omega$  resistors. Therefore, the load applied should be referenced to ground or a negative voltage. The reversal of all diode polarities will reverse the polarity of the output. Since the outputs of the amplifiers must slew through two diode drops when the input polarity changes, the 741-type devices give 5% distortion at about 300 Hz.

## DIODELESS PRECISION RECTIFIER

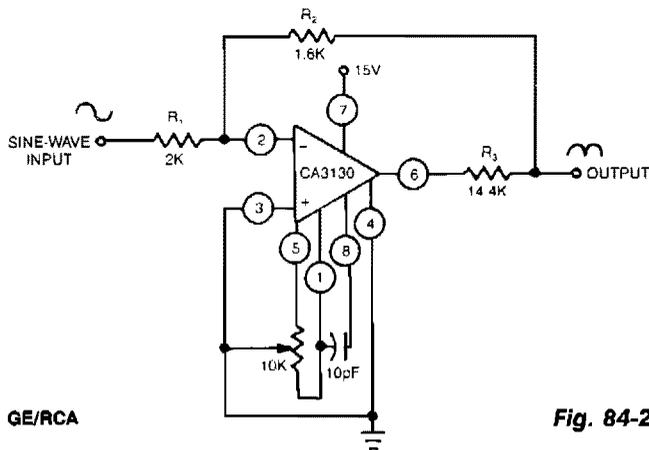

A CA3130 BiMOS op amp, acts as an attenuator for positive inputs and as a conventional op amp for negative signals. With 1-V rms input and a circuit gain of 0.8, its frequency response is  $-1\%$  at 60 kHz and  $-1$  dB at 300 kHz.

# 85


## Resistance/Continuity Meters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Cable Tester  
Continuity Tester  
Linear Ohmmeter


# CABLE TESTER

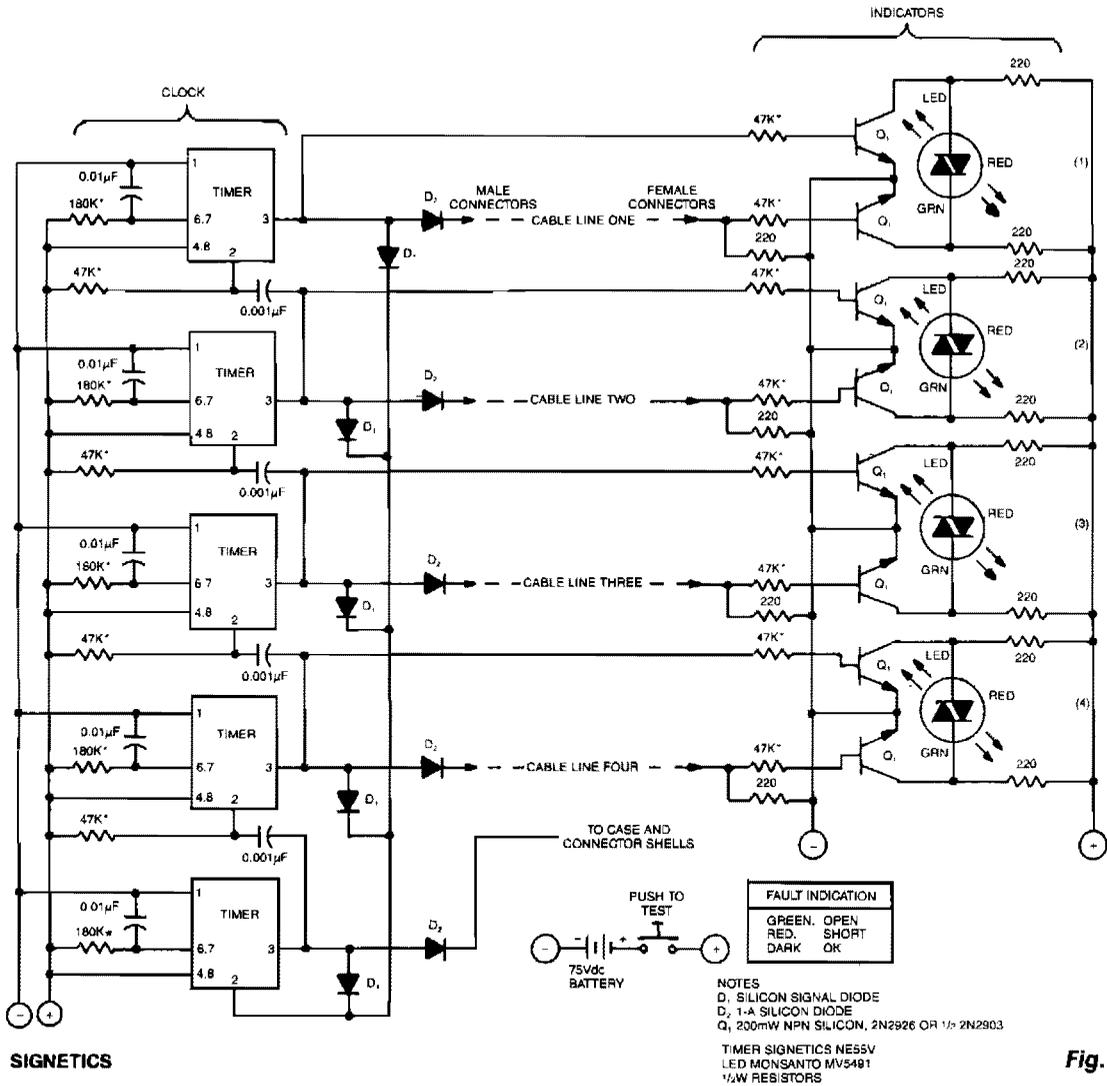

**Fig. 85-1**

This compact tester checks cables for open-circuit or short-circuit conditions. A differential transistor pair at one end of each cable line remains balanced as long as the same clock pulse generated by timer IC appears at both ends of the line. A clock pulse, just at the clock end of the line, lights a green LED, and a clock pulse, only at the other end, lights a red LED.

## CONTINUITY TESTER

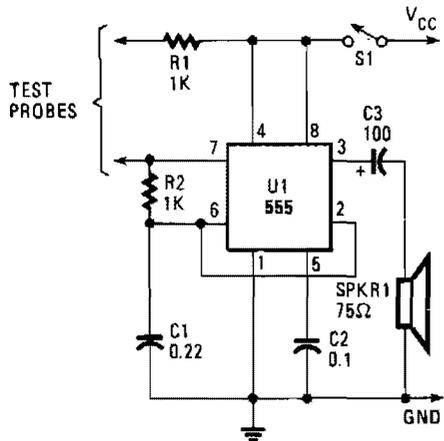


The continuity tester feeds a voltage through the positive probe to the circuit-under-test, while the negative probe serves as the return line. Voltage that returns to the tester through the negative probe triggers the circuit, giving an audible indication of continuity.

HANDS-ON ELECTRONICS/POPULAR ELECTRONICS

Fig. 85-2

## LINEAR OHMMETER

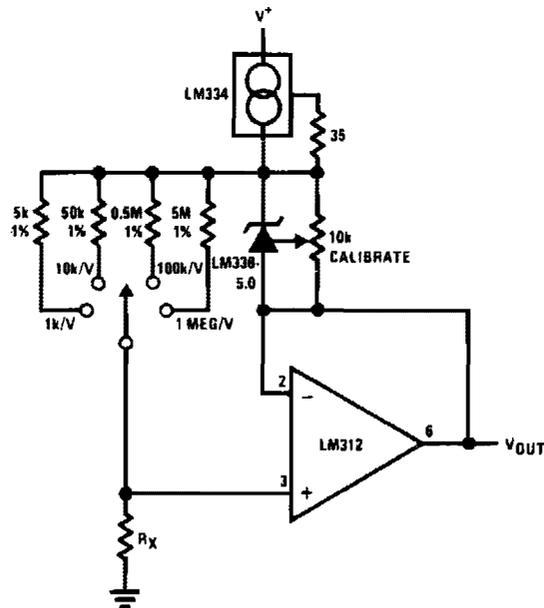

NATIONAL SEMICONDUCTOR CORP.

Fig. 85-3

# 86

## Rf Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

1296-MHz Solid-State Power Amplifier  
10 dB-Gain Amplifier  
2 – 30 MHz Amplifier  
450-MHz Common-Gate Amplifier  
Rf Wideband Adjustable AGC Amplifier

1-MHz Meter-Driver Amplifier  
5-W 150-MHz Amplifier  
UHF-TV Preamplifier  
60-W 225 – 400 MHz Amplifier

## 1296-MHZ SOLID-STATE POWER AMPLIFIER

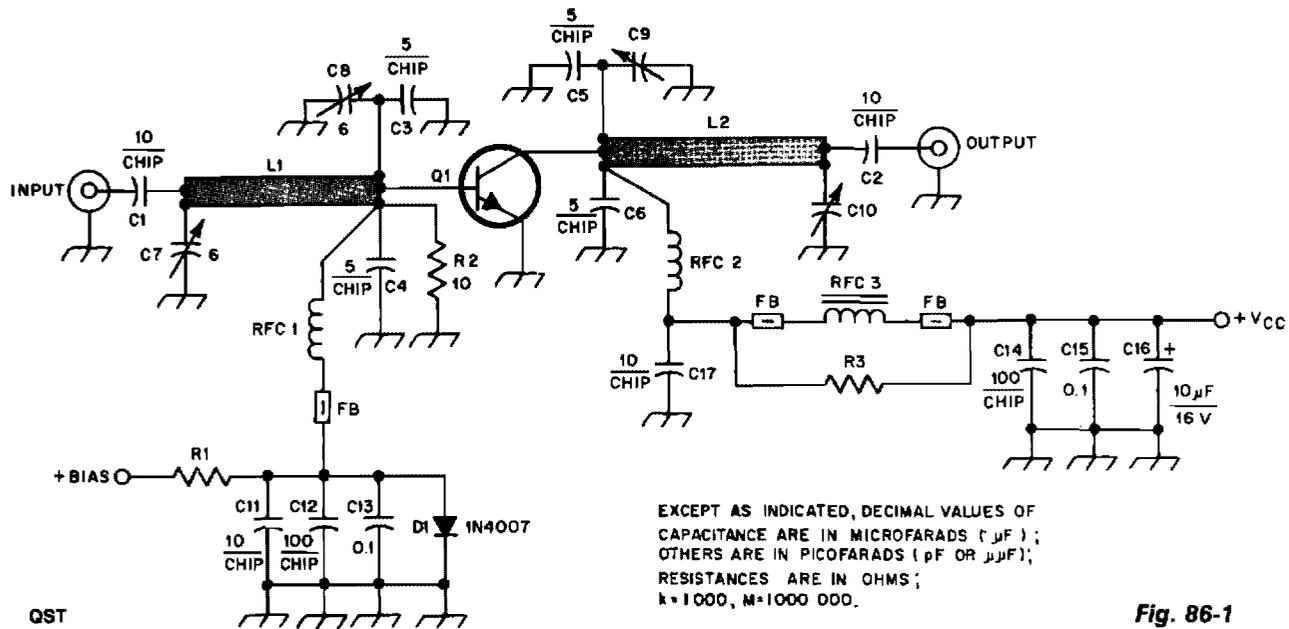


Fig. 86-1

Fig. 1—Schematic diagram of the NEL1306 and NEL1320 1296-MHz solid-state power amplifiers. The schematic is identical for both versions. Component values are the same except as noted.

C1, C2, C11, C17—10-pF chip capacitor.

C3, C4, C5, C6—3.6- to 5.0-pF chip capacitor.

C7, C8—1.8- to 6.0-pF miniature trimmer capacitor (Mouser 24AA070 or equiv. See text).

C9, C10—Same as C7 and C8 for the NEL1306 amplifier. For the NEL1320 version, 0.8- to 10-pF piston trimmers are used (Johanson 5200 series or equiv.).

C12, C14—100-pF chip capacitor.

C13, C15—0.1- $\mu\text{F}$  disc ceramic capacitor.

C16—10- $\mu\text{F}$  electrolytic capacitor.

D1—1N4007 diode.

L1, L2—30-ohm microstrip line,  $\frac{1}{4}$ -wavelength long (see text).

Q1—NEC NEL130681-12 (8 W) or NEL132081-12 (18 W) transistor.

R1—82- to 100- $\Omega$  resistor, 2-W minimum. Vary for specified idling current.

R2—10- $\Omega$ ,  $\frac{1}{4}$ -W carbon-composition resistor with "zero" lead length. See text.

R3—15- $\Omega$ , 1-W carbon-composition resistor.


RFC1—3t no. 24 wire, 0.125 inch ID, spaced 1 wire diam.

RFC2—1t no. 24 wire, 0.125 inch ID, spaced 1 wire diam.



RFC3—1- $\mu\text{H}$  RF choke; 18t no. 24 enam. close-spaced on a T50-10 toroid core.

The design incorporates 30- $\Omega$ ,  $\frac{1}{4}\lambda$  microstrip lines on the input and output. C3, C4, C7, and C8, along with L1, form a pi network that matches the low-input impedance of the device to 50  $\Omega$ . C5, C6, C9, C10, and 30- $\Omega$  transmission line L2 form an output pi network that maximizes power transfer to 50  $\Omega$ . C10 is not always necessary, depending on variations among devices and circuit-board material. Bias is provided by R1, R2, and D1. R1 can be optimized, if desired, to adjust the collector idling current.

## 10 dB-GAIN AMPLIFIER

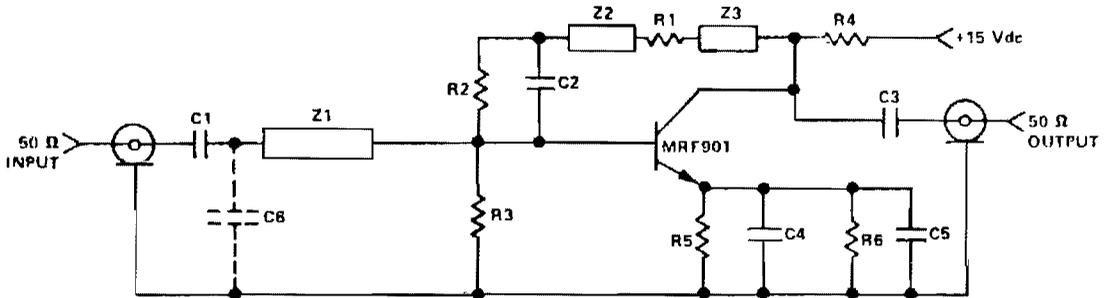

- |                                     |                                       |   |
|-------------------------------------|---------------------------------------|---|
| C1-C3 - 2200 pF chip capacitor      | Z3 - 0.3" × 0.125" microstrip line    | R4 - 560Ω carbon resistor   |
| C4, C5 - 6.5 pF chip capacitor      | R1 - 200Ω 1/8" W, ±5% carbon resistor | R5, R6 - 15Ω ±5% chip resistor  |
| C6 - Optional 2.1 pF chip capacitor | R2 - 4.3kΩ carbon resistor            | Substrate - 1 oz. copper, double-sided glass Teflon® board 0.0625" thick, ε ≈ 2.5 |
| Z1 - 0.3" × 0.125" microstrip line  | R3 - 680Ω carbon resistor             |   |
| Z2 - 0.15" × 0.125" microstrip line |                                       |   |

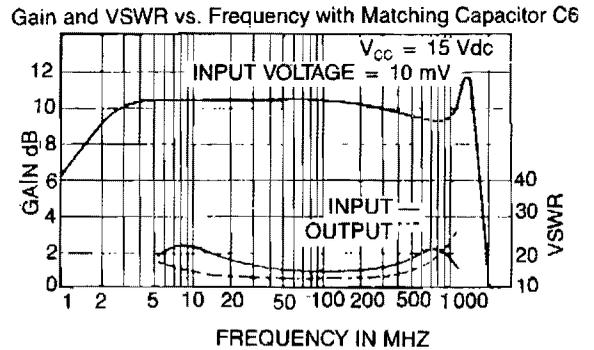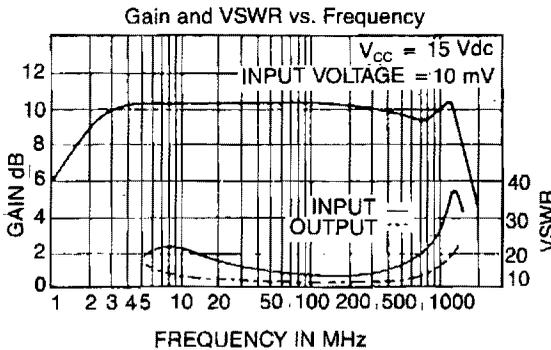


Copyright of Motorola, Inc. Used by permission.

**Fig. 86-2**

This circuit design is a class A amplifier employing both ac and dc feedback. Bias is stabilized at 15 mA of the collector current using dc feedback from the collector. The ac feedback, from collector to base, and in each of the partially bypassed emitter circuits, compensates for the increase in device gain with decreasing frequency, yielding a flat response over a maximum bandwidth. The amplifier shows a nominal 10-dB power gain from 3 MHz to 1.4 GHz. With only a minimum matching network used at the amplifier input, the input VSWR remains less than 2.5:1 to approximately 1 GHz, while the output VSWR stays under 2:1. Note that a slight degradation in gain flatness and output VSWR occurs with the addition of C6. A more elaborate network design would probably optimize impedance matching, while maintaining gain flatness.

## 2-30 MHz AMPLIFIER

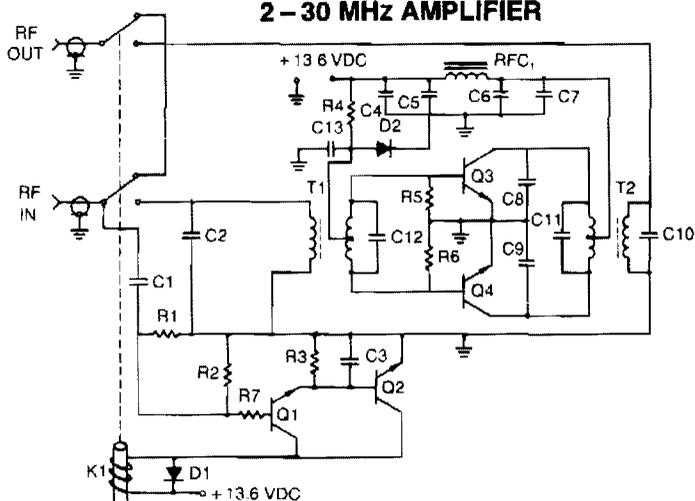


- |   |  |
|---|--|
| C1—33 pF dipped mica  | R—100 K $\Omega$ , 0.25 W                              |
| C2—18 pF dipped mica  | R2—10 K $\Omega$ , 0.25 W                              |
| C3—10 $\mu$ F, 35 VDC for AM operation<br>100 $\mu$ F, 35 VDC for SSB operation | R3—10 K $\Omega$ , 0.25 W                              |
| C4—0.1 $\mu$ F Erie   | R4—33 $\Omega$ , 5 W wirewound                         |
| C5—10 $\mu$ F, 35 VDC electrolytic  | R5, R6—10 $\Omega$ , 0.5 W                             |
| C6—1 $\mu$ F tantalum   | R7—100 $\Omega$ , 0.25 W                               |
| C7—0.001 $\mu$ F Erie disk  | RFC1—9 ferrocube beads on No. 18 AWG wire              |
| C8, C9—330 pF dipped mica   | D1—1N4001  |
| C10—24 pF dipped mica   | D2—1N4997  |
| C11—910 pF dipped mica  | Q1, Q2—2N4401  |
| C12—1100 pF dipped mica   | Q3, Q4—MRF454  |
| C13—500 $\mu$ F, 3 VDC electrolytic   | T1, T2—16:1 transformers                               |
|   | K1—Potter & Brumfield KT11A 12 VDC relay or equivalent |

MICROWAVES AND RF

Fig. 86-3

This amplifier provides 140-W PEP nominal output power when supplied with input levels as low as 3 W. Both input and output transformers have a 4:1 turn ratio and a 16:1 impedance ratio to achieve low input VSWR across the band with high-saturation capability.

## 450-MHz COMMON-GATE AMPLIFIER

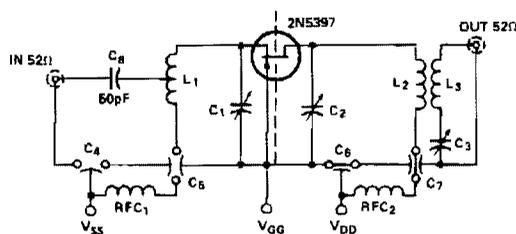

- C1, C2, C3 — 0.8–12 pF Johnson type 2950  
 C4, C5, C6, C7, — 1000 pF Allen-Bradley type 335D  
 RFC 1,2 — 0.16  $\mu$ H Delevan type 1537-00  
 L1—1.5" long; #18 copper  
 L2—1.2" long; #18 copper  
 L3—2.0" long; #22 copper enamel, loosely coupled  
 to L2, 0.75" spacing

V<sub>DD</sub> = 10V  
 I<sub>D</sub> = 10mA  
 NF Typ 3.2dB  
 G<sub>ps</sub> Typ 10dB

This is a low noise, 3-dB typical NF, amplifier with about 10-dB gain at 450–470 MHz for VHF two-way applications.

Copyright 1981, Teledyne Industries, Inc.

Fig. 86-4

## RF WIDEBAND ADJUSTABLE AGC AMPLIFIER

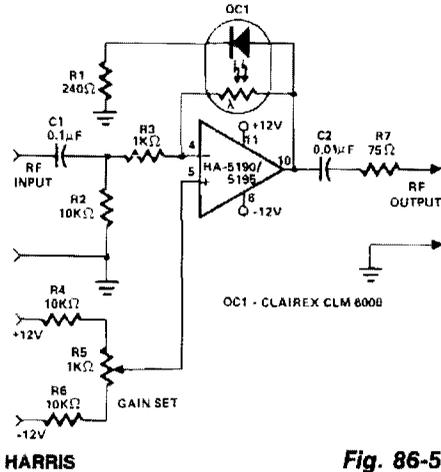


Fig. 86-5

This circuit functions as a wideband adjustable AGC amplifier. With an effective bandwidth of approximately 10 MHz, it is capable of handling rf input signal frequencies from 3.2 to 10 MHz at levels ranging from 40 mV up to 3 V pk-pk.

AGC action is achieved by using optocoupler/isolator OC1 as part of the gain control-feedback loop. In operation, the positive peaks of the ampli-

fied output signal drive the OC1 LED into a conducting state. Since the resistance of the OC1 photosensitive element is inversely proportional to light intensity, the higher the signal level, the lower the feedback resistance to the op amp inverting input. The greater negative feedback lowers stage gain. Any changes in gain occur smoothly because the inherent memory characteristic of the photoresistor acts to integrate the peak signal inputs. In practice, the stage gain is adjusted automatically to where the output signal positive peaks are approximately one diode drop above ground.

Gain set control R5 applies a fixed dc bias to the op amp noninverting input, thus establishing the steady state-zero input signal current through the OC1 LED and determining the signal level at which AGC action begins.

The effective AGC range depends on a number of factors, including individual device characteristics, the nature of the rf drive signal, the initial setting for R5, et al. Theoretically, the AGC range can be as high as 4000:1 for a perfect op amp because the OC1 photoresistor can vary in value from 1 MΩ with the LED dark to 250 Ω with the LED fully on.

## 1-MHZ METER-DRIVER AMPLIFIER


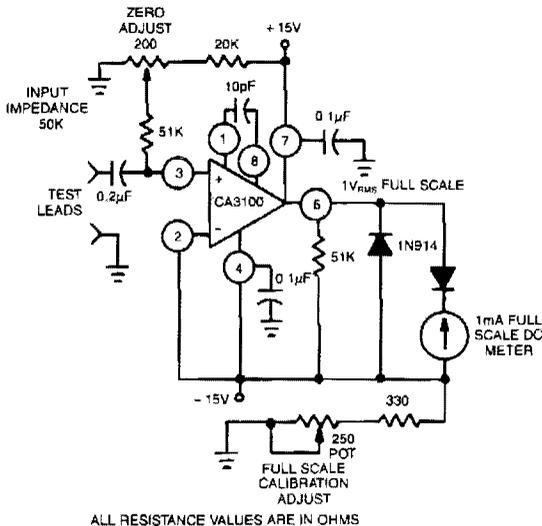


Fig. 86-6

This circuit uses the CA3100 BiMOS op amp to drive a 1-mA meter movement to full scale with 1-V rms input.

### 5-W 150-MHz AMPLIFIER

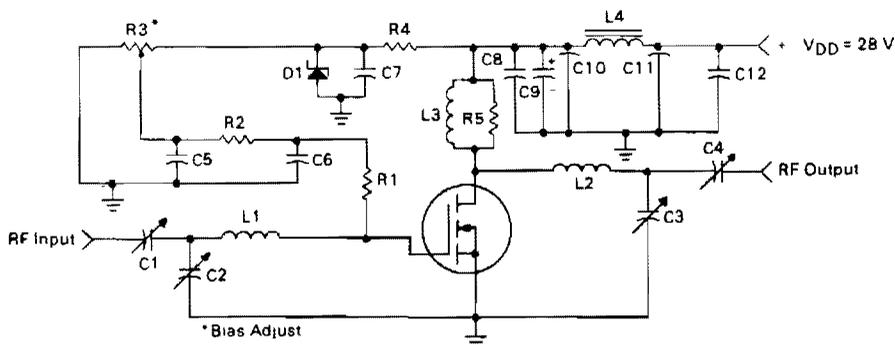

- C1, C4 — Arco 406, 15–115 pF
- C2 — Arco 403, 3–35 pF
- C3 — Arco 402, 1.5–20 pF
- C5, C6, C7, C8, C12 — 0.1  $\mu$ F Erie Redcap
- C9 — 10  $\mu$ F, 50 V
- C10, C11 — 880 pF Feedthru
- D1 — 1N5925A Motorola Zener
- L1 — 3 Turns, 0.310" ID, #18 AWG Enamel, 0.2" Long
- L2 — 3-1/2 Turns, 0.310" ID, #18 AWG Enamel, 0.25" Long

- L3 — 20 Turns, #20 AWG Enamel Wound on R5
- L4 — Ferroxcube VK-200 — 19/4B
- R1 — 68  $\Omega$ , 1.0 W Thin Film
- R2 — 10 k $\Omega$ , 1/4 W
- R3 — 10 Turns, 10 k $\Omega$  Beckman Instruments 8108
- R4 — 1.8 k $\Omega$ , 1/2 W
- R5 — 1.0 M $\Omega$ , 2.0 W Carbon
- Board — G10, 62 mils

Copyright of Motorola, Inc. Used by permission.

Fig. 86-7

This circuit utilizes the MRF123 T MOS power FET. The MRF134 is a very high gain FET that is potentially unstable at both VHF and UHF frequencies. Note that a 68- $\Omega$  input loading resistor has been utilized to enhance stability. This amplifier has a gain of 14 dB and a drain efficiency of 55%.

### UHF-TV PREAMPLIFIER


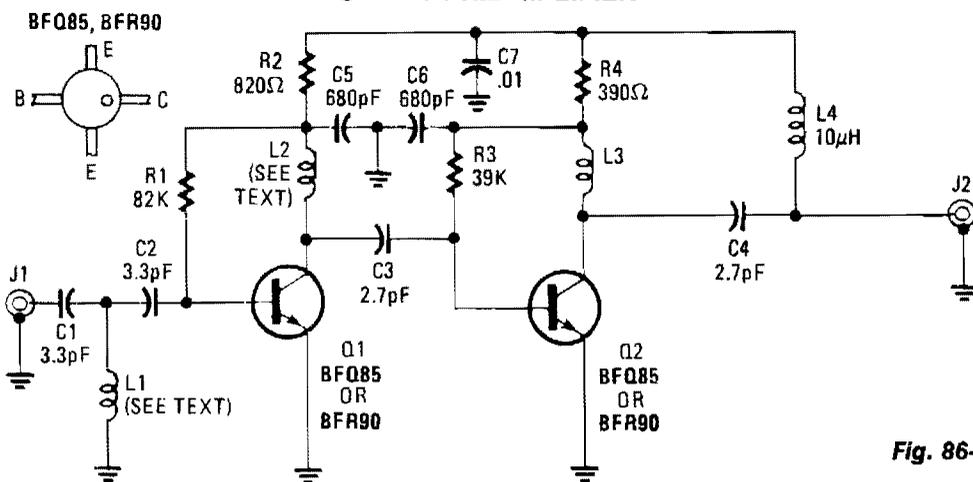


Fig. 86-8

Reprinted with permission from Radio-Electronics Magazine, March 1982. Copyright Gernsback Publications, Inc., 1982.

An inexpensive, antenna-mounted, UHF-TV preamplifier can add more than 25 dB of gain. The first stage of the preamp is biased for optimum noise, the second stage for optimum gain. L1, L2 strip line  $\approx \lambda/8$  part of PC board.

## 60-W 225 – 400 MHz AMPLIFIER

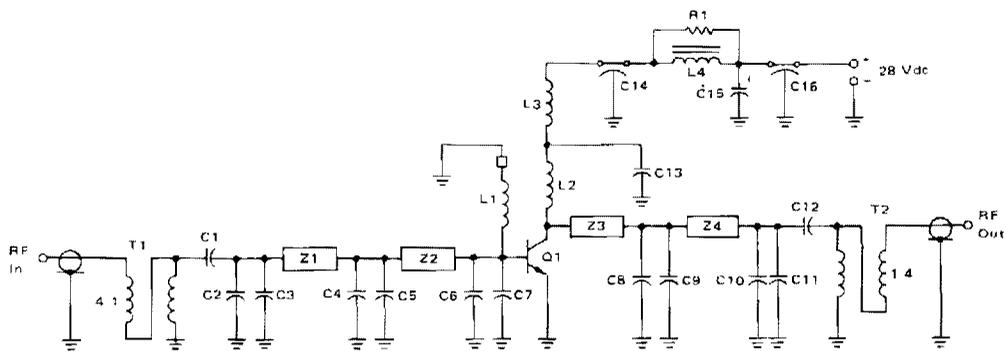


- C1 – 63 pF Chip
- C2, C8 – 27 pF Chip
- C3 – 24 pF Chip
- C4 – 15 pF Chip
- C5, C9 – 30 pF Chip
- C6, C7 – 50 pF Chip
- C10 – 10 pF Chip
- C11 – 5.1 pF Chip
- C12 – 150 pF Chip
- C13 – 270 pF Chip
- C14, C16 – 680 pF Feedthru
- C15 – 1.0  $\mu$ F 50 V Tantalum

- All Chip Capacitors are 100 mil TDK ACl Co.  
Style FC282 BAG
- L1 – 0.15  $\mu$ H Molded Choke with Ferroxcube
  - Bead #56 590 65/4B on ground end of coil
  - L2 – 1 Turn #22 AWG, 1/8" ID
  - L3 – 0.15  $\mu$ H Molded Choke
  - L4 – Ferroxcube VK 200 19/4B
  - Q1 – 2N6439
  - R1 – 10  $\Omega$  2 Watt
  - T1, T2 – 25  $\Omega$  Subminiature Coax (Type UT25)
  - 2.25 inches (57.15 mm) long


- Z1 – Microstrip Line  
800 mils L X 225 mils W  
20.32 mm L X 5.715 mm W
- Z2 – Microstrip Line  
200 mils L X 225 mils W  
5.08 mm L X 5.715 mm W
- Z3, Z4 – Microstrip Line  
550 mils L X 125 mils W  
13.97 mm L X 3.175 mm W
- Board – 0.031" (0.787 mm) Glass Teflon  
 $\epsilon_r = 2.56$

### 2N6439 60 Watt Building Block 225 – 400 MHz


#### SCHEMATIC REPRESENTATION

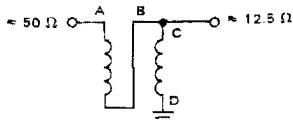

#### ASSEMBLY AND PICTORIAL

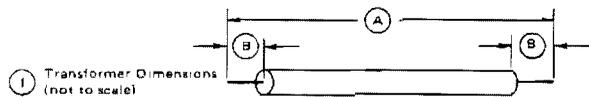

- (A) – 2.25 inches (5.715 cm)
- (B) – 0.1875 inch (0.476 cm)

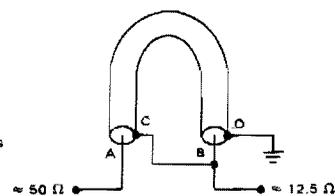

**Fig. 86-9**

Copyright of Motorola, Inc. Used by permission.

### **Construction Details of the 4:1 Unbalanced to Unbalanced Transformers**

This 60-W, 28-V broadband amplifier covers the 225–400 MHz military communications band. The amplifier may be used singly as a 60-W output stage in a 225–400 MHz transmitter, or by using two of these amplifiers combined with quadrature couplers, a 100-W output amplifier stage can be constructed. The circuit is designed to be driven from a 50- $\Omega$  source and work into a nominal 50- $\Omega$  load. The input network consists of two microstrip L-sections composed of Z1, Z2, and C2 through C6. C1 serves as a dc-blocking capacitor. A 4:1 impedance ratio coaxial transformer T1 completes the input matching network. L1 and a ferrite bead serve as a base decoupling choke. The output circuit consists of shunt inductor L2 at the collector, followed by two microstrip L-sections composed of Z3, Z4, and C8 through C11. C12 serves as a dc blocking capacitor, and is followed by another 4:1 impedance ratio coaxial transformer. Collector decoupling is accomplished through the use of L3, L4, C14, C15, C16, and R1.


## Sample-and-Hold Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Sample-and-Hold	Sample-and-Hold
Basic Track-and-Hold/ Sample-and-Hold	Track-and-Hold/ Sample-and-Hold
High-Speed Sample-and-Hold	Inverting Sample-and-Hold
Filtered Sample-and-Hold	Sample-and-Hold
Sample-and-Hold	

## SAMPLE-AND-HOLD

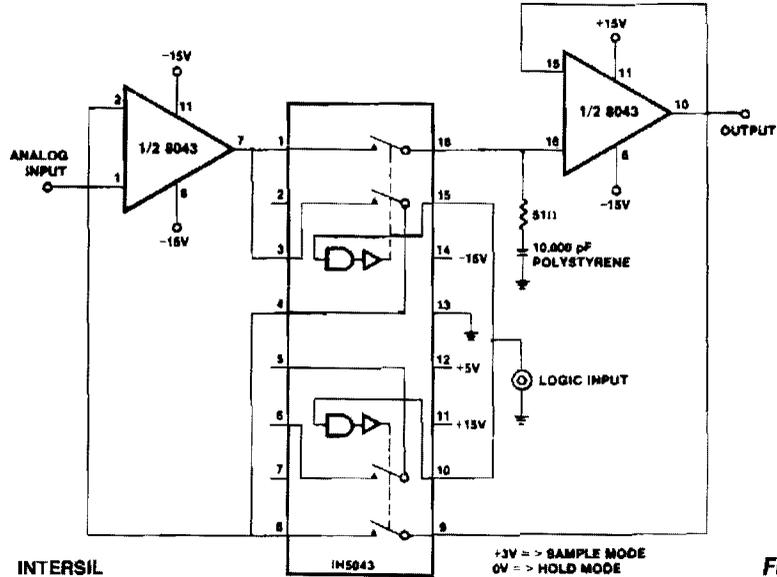


**Fig. 87-1**

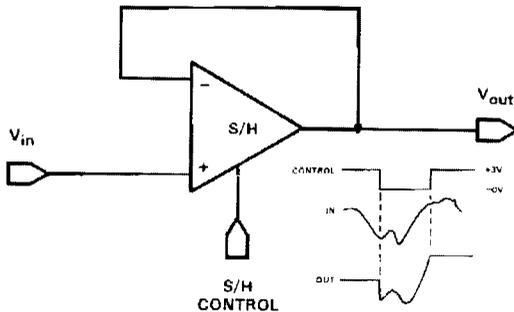Two important properties of the 8043 are used to advantage in this circuit. The low input bias currents give rise to slow output decay rates (droop) in the hold mode, while the high slew rate at  $6 \text{ V}/\mu\text{s}$  improves the tracking speed and the response time of the circuit. The upper waveform is the input  $10 \text{ V}/\text{div}$ , the lower waveform the output  $5 \text{ V}/\text{div}$ . The logic input is high.

The center waveform is the analog input, a ramp moving at about  $67 \text{ V}/\text{ms}$ , the lower waveform is the logic input to the sample-and-hold; a logic 1 initiates the sample mode. The upper waveform is the output, displaced by about one scope division  $2 \text{ V}$  from the input to avoid superimposing traces. The hold mode, during which the output remains constant, is clearly visible. At the beginning of a sample period, the output takes about  $8 \mu\text{s}$  to catch up with the input, after which it tracks, until the next hold period.

## BASIC TRACK-AND-HOLD/SAMPLE-AND-HOLD



HARRIS

**Fig. 87-2**

Feedback is the same as a conventional op-amp voltage follower which yields a unity-gain, noninverting output. This hookup also has a very high input impedance. The only difference between a track-and-hold and a sample-and-hold is the time period during which the switch is closed. In track-and-hold operation, the switch is closed for a relatively long period; the output signal might change appreciably and would hold the level present at the instant the switch is opened. In sample-and-hold operation, the switch is closed only for the time necessary to fully charge the holding capacitor.

## HIGH-SPEED SAMPLE-AND-HOLD


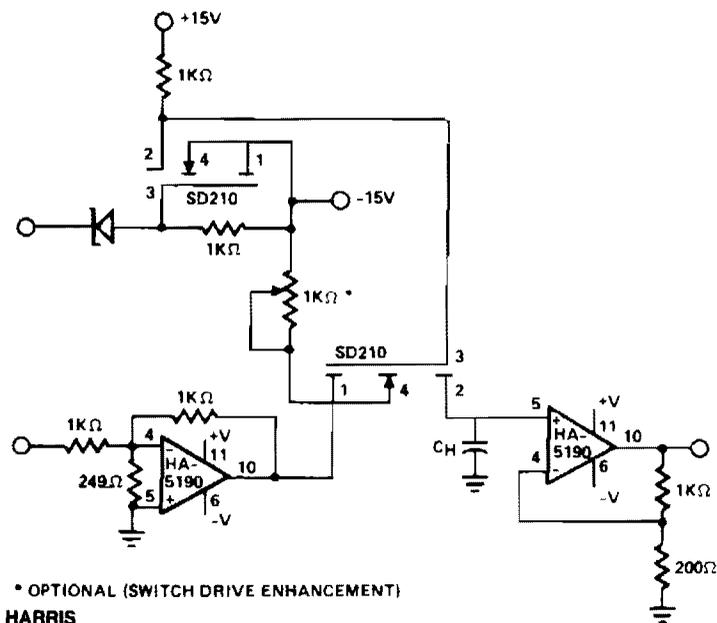


Fig. 87-3

This circuit uses the speed and drive capability of the HA-5190 coupled with two high-speed DMOS FET switches. The input amplifier is allowed to operate at a gain of  $-5$ , although the overall circuit gain is unity. Acquisition times of less than  $100\text{ ns}$  to  $0.1\%$  of a  $1\text{-V}$  input step are possible. Drift current can be appreciably reduced by using FET input buffers on the output stage of the sample-and-hold.

## FILTERED SAMPLE-AND-HOLD

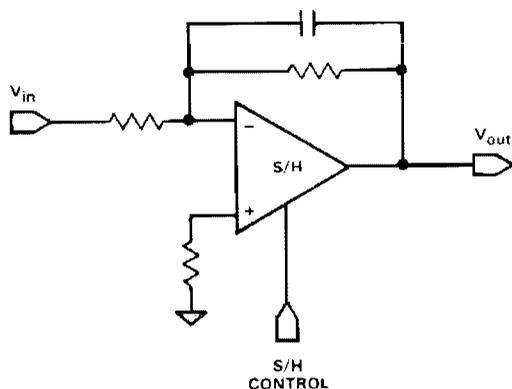


It is often required that a signal be filtered prior to sampling. This can be accomplished with only one device. Use any of the inverting and noninverting filters that can be built with op amps. However, it is necessary that the sampling switch be closed for a sufficient time for the filter to settle when active filter types are connected around the device.

HARRIS

Fig. 87-4

## SAMPLE-AND-HOLD

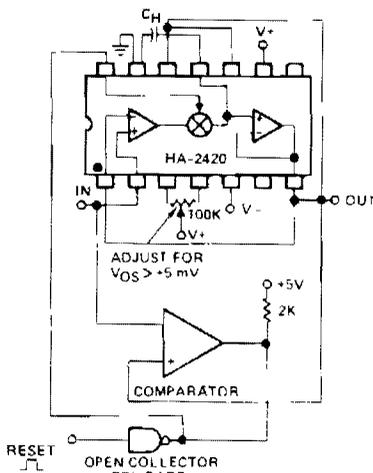


HARRIS

Fig. 87-5

The sample-and-hold function has often been accomplished with separate analog switches and op amps. These designs always involve performance tradeoffs between acquisition time, charge injection, and droop rate. The HA-242-/2425 monolithic sample-and-hold, has many better tradeoffs, and usually a lower total cost than the other approaches. The switching element is a complementary bipolar circuit with feedback, which allows high charging currents of 30 mA, a low charge injection of 10 pC, and an ultra-low off leakage current of 5 pA; a combination that is not approached in any other electronic switch. These factors make it also superior as an integrator reset switch, or as a precision peak detector.

## SAMPLE-AND-HOLD

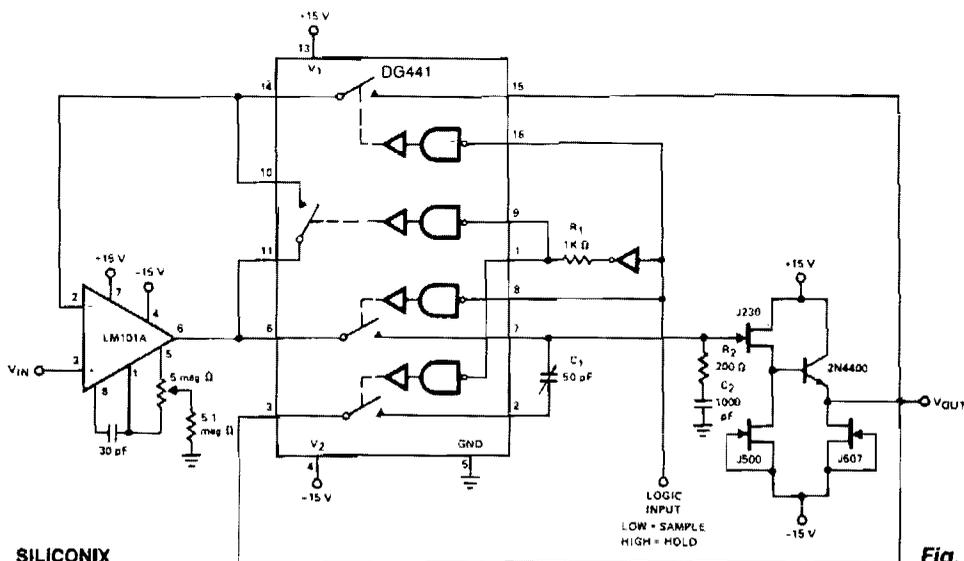


SILICONIX

Fig. 87-6


The LM101A provides gain and buffers the input from storage capacitor C2. R2 adds a zero in the open loop response to compensate for the pole caused by the switch resistance and C2, improving the closed-loop stability. R1 provides a slight delay in the digital drive to pins 1 and 9. C1 provides cancellation of coupled charge, keeping the sample-and-hold offset below 5 mV over the analog signal range of -10 through +10 V. Aperture time is typically 1  $\mu$ s, the switching time of the DG441. Acquisition time is 25  $\mu$ s, but this can be improved by using a faster slewing op amp. Droop rate is typically less than 5 mV/s at 25°C.

## TRACK-AND-HOLD/SAMPLE-AND-HOLD

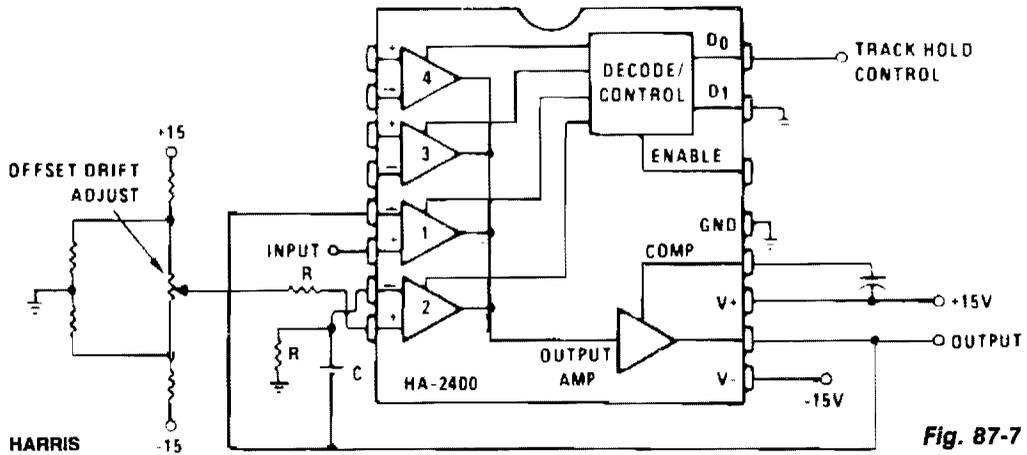

Channel 1 is wired as a voltage follower and is turned on during the track/sample time. If the product of  $R \times C$  is sufficiently short compared to the period of maximum output frequency, or sample time;  $C$  will charge to the output level. Channel 2 is an integrator with zero input signal. When channel 2 is then turned on, the output will remain at the voltage across  $C$ .

## INVERTING SAMPLE-AND-HOLD

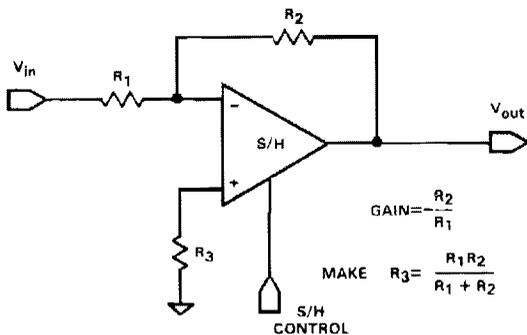


This illustrates another application in which the hookup versatility of a sample-and-hold often eliminates the need for a separate op amp and a sample-and-hold module. This hookup will have a somewhat higher input-to-output feedthrough during hold than the noninverting connection, since the output impedance is an open-loop value during hold. The feedthrough will

$$\frac{V_{IN} R_0}{R_1 + R_2 + R_0}$$

HARRIS

Fig. 87-8

## SAMPLE-AND-HOLD

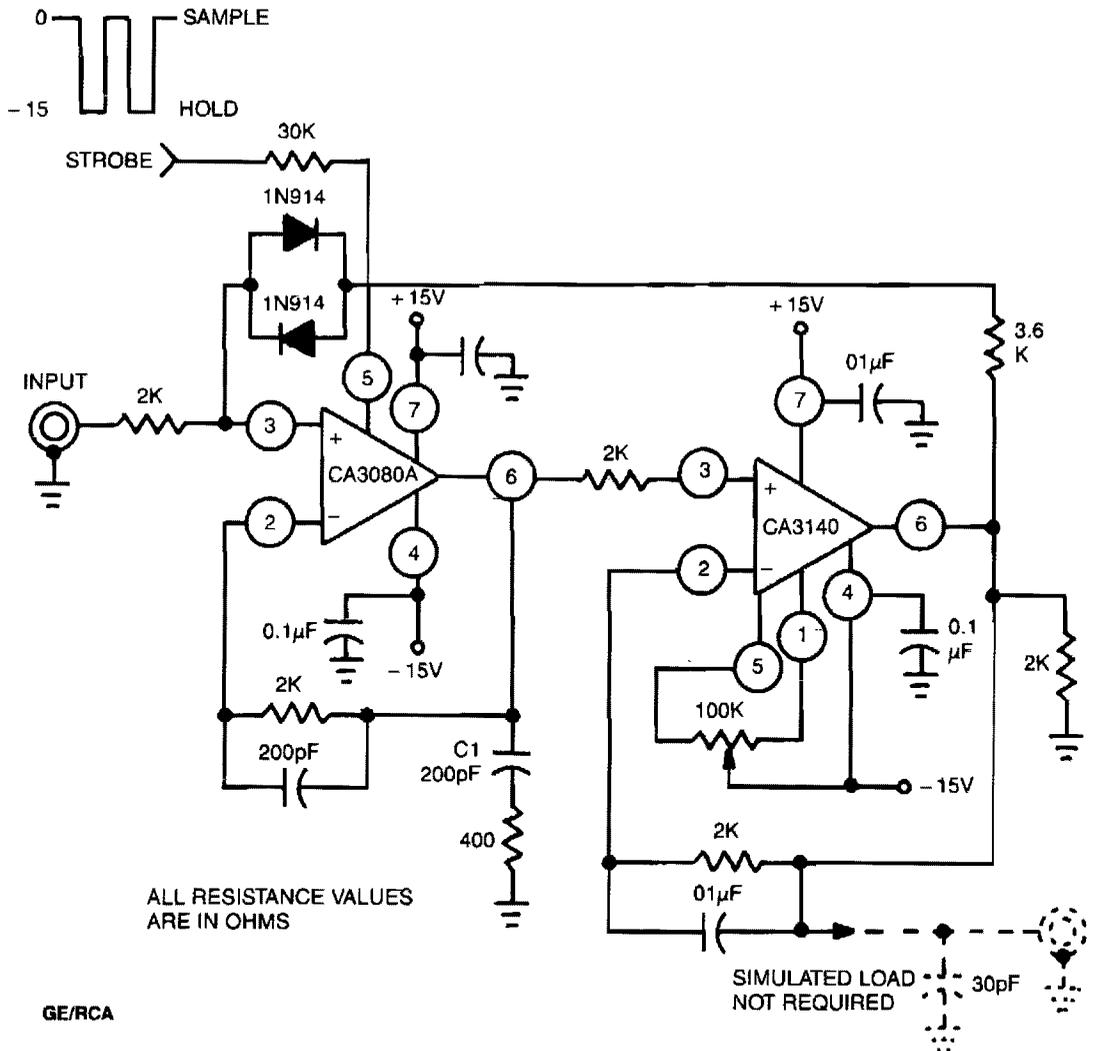

GE/RCA

Fig. 87-9

This circuit uses a CA3140 BiMOS op amp as the readout amplifier for the storage capacitor C1, and a CA3080A variable op amp as input buffer amplifier and low feedthrough transmission switch. Offset nulling is accomplished with the CA3140.

**88**


## **Signal Injectors**

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Signal Injector  
Signal Injector

## SIGNAL INJECTOR

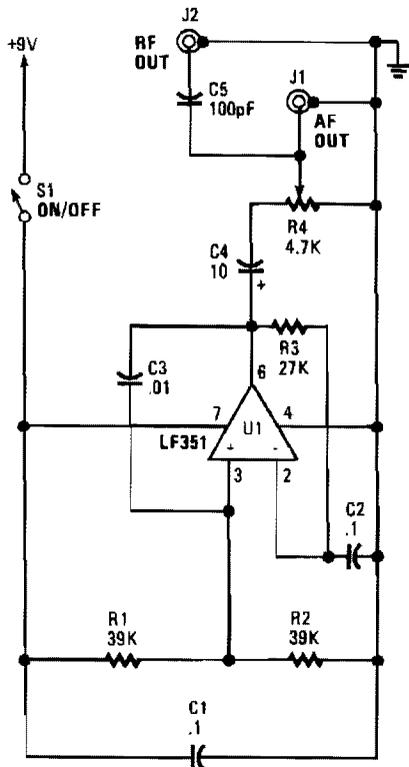


POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 88-1

This unit is a single oscillator built around an LF351 JFET-input op amp. Resistors R1 and R2 bias the noninverting input while R3 biases the inverting input from the output. This layout provides 100% negative feedback, but the decoupling caused by C2 gives reduced feedback and high-voltage gain when dealing with audio frequencies. The fundamental operating frequency is about 800 Hz. Potentiometer R4 is the output-level control. To use it start at the speaker. If no tone is heard, move back to the amplifier input, and listen for the tone. Still if no tone is heard, continue backtracking from the output to the input, covering all stages in between. The stage where the signal is lost is the one that is not operating.

## SIGNAL INJECTOR

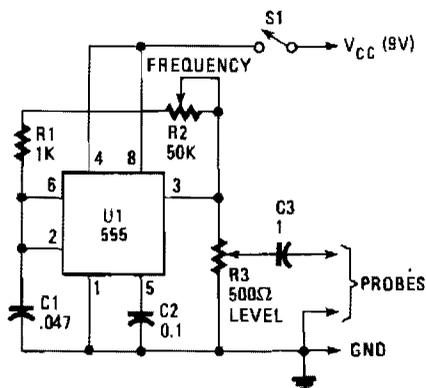

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 88-2

The unit provides a square-wave output that is rich in harmonic content. The circuit's output frequency can be varied from 50 Hz to 15 kHz. The heart of the circuit is a 555 astable connected in its equal mark/space mode. The frequency is controlled by potentiometer R2 and capacitor C1. Resistor R3 controls the output level with the output ac-coupled through C3.

# 89



## Sine-Wave Oscillators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Low-Distortion Thermally Stabilized  
Wien-Bridge Oscillator  
Single-Supply Wien-Bridge Oscillator  
Super-Low-Distortion Variable Sine-Wave Oscillator  
Audio Generator
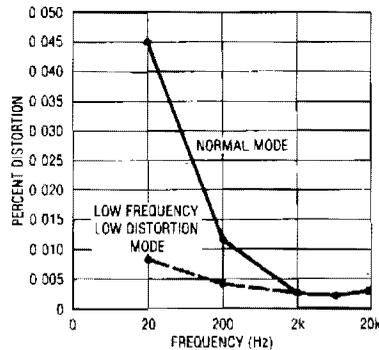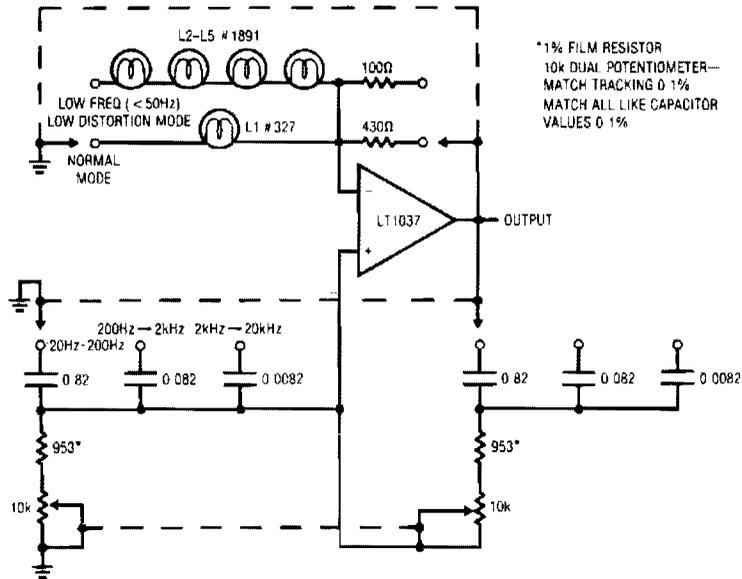
## LOW-DISTORTION THERMALLY STABILIZED WIEN-BRIDGE OSCILLATOR




**Oscillator Distortion vs Frequency**

LINEAR TECHNOLOGY CORP.

**Fig. 89-1**

A variable Wien bridge provides frequency tuning from 20 Hz to 20 kHz. Gain control comes from the positive temperature coefficient of the lamp. When power is applied, the lamp is at a low resistance value, the gain is high, and oscillation amplitude builds. The lamp's gain-regulating behavior is flat within 0.25 dB over the 20 Hz – 20 kHz range of the circuit. Distortion is below 0.003%. At low frequencies, the thermal time constant of the small normal-mode lamp begins to introduce distortion levels about 0.01%. This is because of *hunting* when the oscillator's frequency approaches the lamp's thermal time constant. This effect can be eliminated, at the expense of reduced output amplitude and longer amplitude settling time, by switching to the low-frequency, low-distortion mode. The four large lamps give a longer thermal time constant, and distortion is reduced.

## SINGLE-SUPPLY WIEN-BRIDGE OSCILLATOR

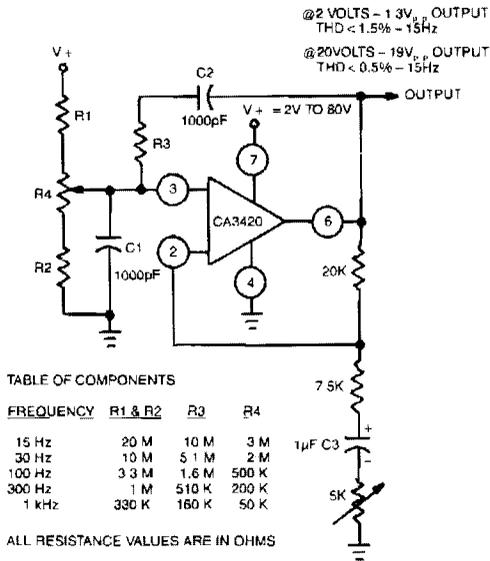


The adjustment of R4 contributes to the comparatively symmetrical output transfer characteristic of the CA3420 BiMOS op amp. To extend the lower operating frequency, remove C3 and use a dual supply.

GE/RCA

Fig. 89-2

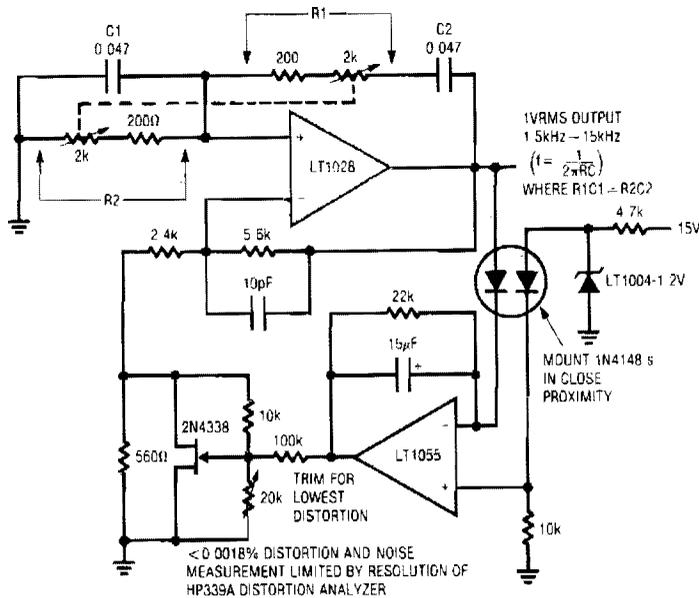
## SUPER-LOW-DISTORTION VARIABLE SINE-WAVE OSCILLATOR



LINEAR TECHNOLOGY CORP.

Fig. 89-3

## AUDIO GENERATOR

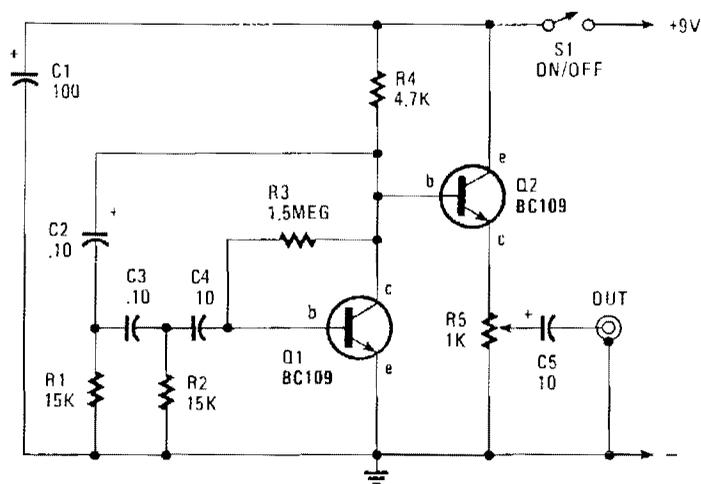

HANDS-ON ELECTRONICS

Fig. 89-4

This circuit produces a sinusoidal output of about 8 V pk-pk, which can be varied down to zero, at about 500 Hz. The signal is generated by a phase-shift oscillator.

# 90


## Sirens, Warblers, and Wailers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Electronic Bagpipe	Super Sound Generator
Two-Tone Siren	Hee-Haw Siren
Yelping Siren	Electronic Siren
Programmable-Frequency	555 Beep Transformer
Adjustable-Rate Siren	Siren
The Wailing Siren	Two-State Siren
Linear IC Siren	Steam Train with Whistle

## ELECTRONIC BAGPIPE

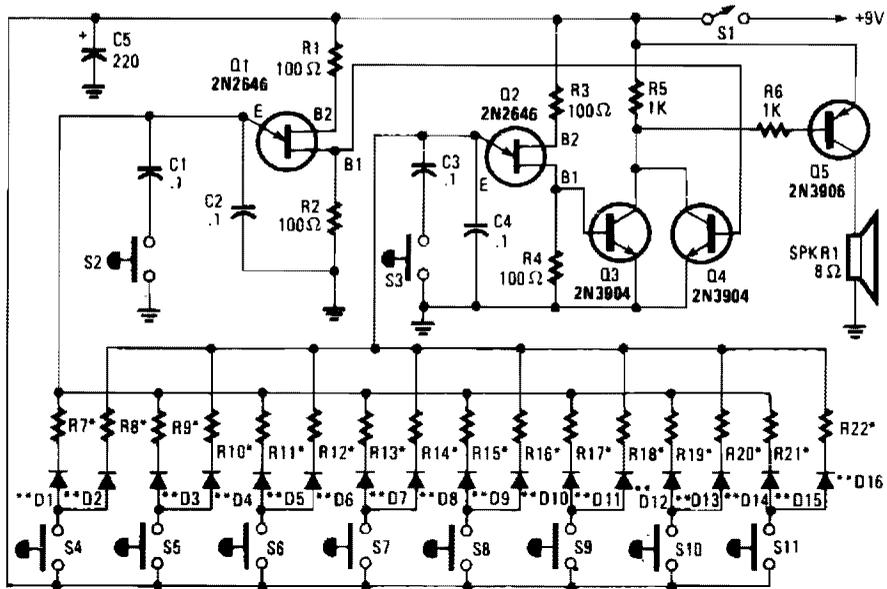

\* SEE TEXT  
 \*\*D1-D16 ARE 1N914


POPULAR ELECTRONICS

Fig. 90-1

This circuit mimics the dual-tone drone sound that's produced by the unusual wind instrument. Uni-junction transistors Q1 and Q2 are connected in similar audio-oscillator circuits. Each of the oscillator frequencies is determined by one of the two resistors selected by one of the pushbutton switches, S4 through S11. The odd-numbered resistors in R7 to R21, determine the frequency for the Q1 oscillator circuit and the even-numbered resistors in R8 through R22, determine the frequency for Q2's circuit.

When S4 is pressed, the positive supply is connected to both R7 and R8 through isolation diodes D1 and D2, causing both oscillators to operate. A narrow, fast-rising positive pulse is developed at B1 of both Q1 and Q2 for each cycle of operation. Transistors Q3 and Q4 serve as a simple audio mixer, which is used to combine the pulses from each oscillator. The mixed signal at the collectors of Q3 and Q4 is coupled through R6 to the base of Q5, which amplifies and drives an 8-Ω speaker, SPKR1. Switches, S2 and S3 are used to reduce the oscillator's frequency by about 50% when closed, to produce a new group of tones.

## TWO-TONE SIREN

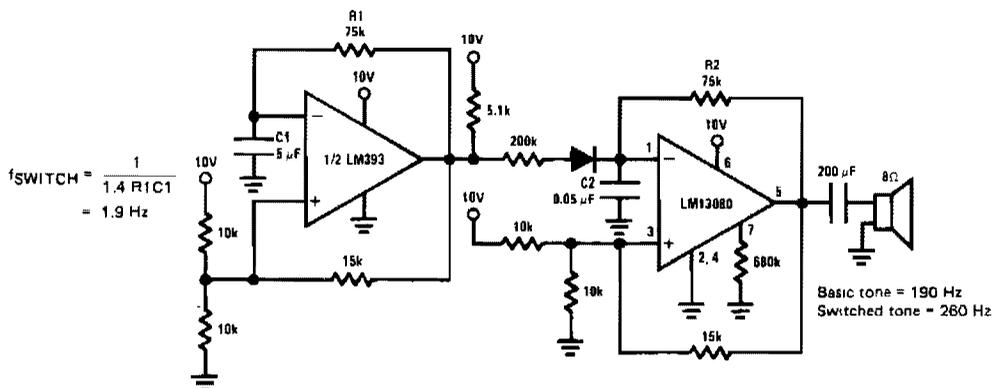


NATIONAL SEMICONDUCTOR

Fig. 90-2

This siren provides a constant audio output, but alternates between two separate tones. The LM13080 is set to oscillate at one basic frequency; this frequency is changed by adding a 200-K $\Omega$  charging resistor in parallel with the feedback resistor, R2.

## YELPING SIREN

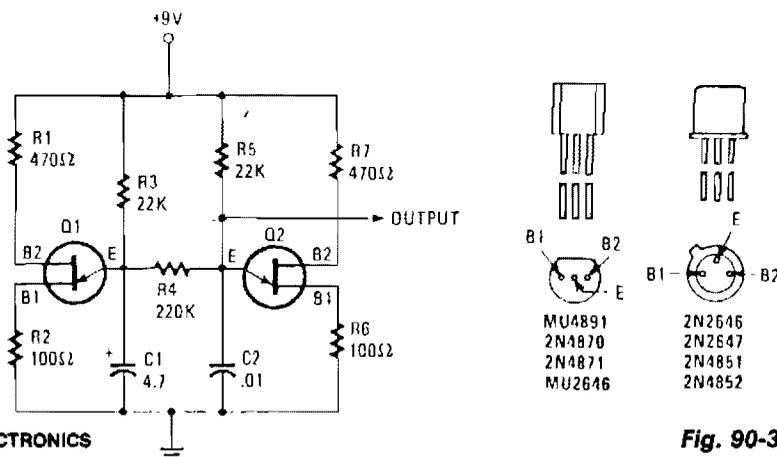


HANDS-ON ELECTRONICS

Fig. 90-3

Unijunction transistors Q1 and Q2 are both connected as relaxation-type, sawtooth oscillators. Transistor Q1 is the low-frequency control oscillator and Q2 is the tone generator. Sawtooth waveforms are produced at the emitter terminals. Without R4 connecting the two emitters, each oscillator operates independently, with its frequency determined mainly by the RC time constant. With the values shown, Q1 operates from 1. to 1.5 Hz and Q2 operates from 400 to 500 Hz. When R4 is connected between the two emitters, it couples the low-frequency sawtooth from Q1 directly across capacitor C2. That coupling causes the frequency of the tone generator to increase, along with the rise in sawtooth voltage from Q1. The tone generator's frequency drops to its lower design value when C1 discharges and produces the falling edge of the sawtooth.
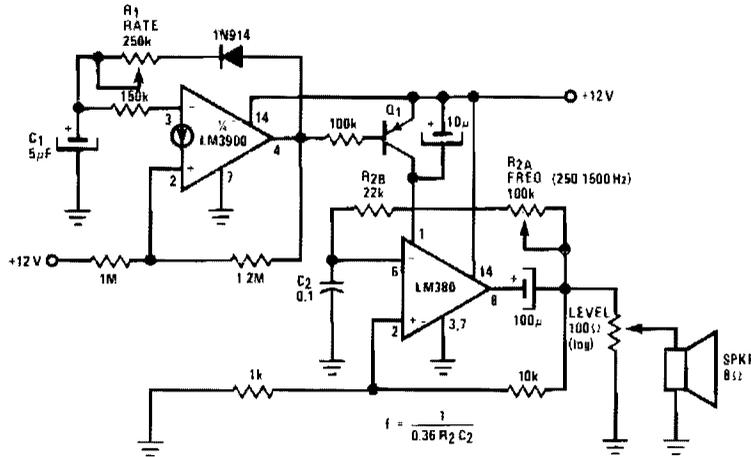
## PROGRAMMABLE-FREQUENCY ADJUSTABLE-RATE SIREN




NATIONAL SEMICONDUCTOR CORP.

Fig. 90-4

The LM380 operates as an astable oscillator with the frequency determined by  $R2/C2$ . Adding  $Q1$  and driving its base, with the output of an LM3900 wired as a second astable oscillator, acts to gate the output of the LM380 on and off, at a rate fixed by  $R1/C1$ .

## THE WAILING SIREN

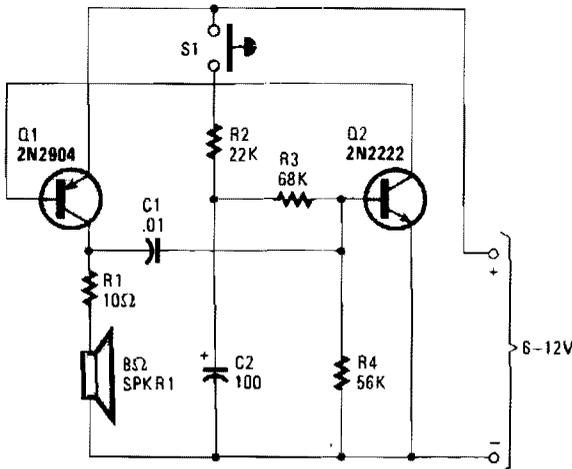


HANDS-ON ELECTRONICS

Fig. 90-5

Transistors  $Q1$  and  $Q2$ , with feedback provided via  $C1$  from the collector of  $Q1$  to the base of  $Q2$ , forms a voltage-controlled oscillator (VCO). De-

pending on the voltage applied to  $Q2$ 's base, the VCO frequency ranges from around 60 Hz to 7.5 kHz. The instantaneous voltage applied to the base of  $Q2$  is determined by the values of  $C2$ ,  $R2$ ,  $R3$ , and  $R4$ . When pushbutton switch  $S1$  is closed,  $C2$  charges fairly rapidly to the maximum supply voltage through  $R2$ , a 22-K $\Omega$  fixed resistor. That causes the siren sound to rise rapidly to its highest frequency. When the button is released, the capacitor discharges through  $R3$  and  $R4$  with a combined resistance of 124 K $\Omega$ , causing the siren sound to decay from a high-pitched wail to a low growl. If you want to experiment with the pitch of the sound at its highest frequency, try different values for  $C1$ . Increase its value for lower notes, and decrease it for higher ones. Different values for  $R2$  will change the attack time. A 100-K $\Omega$  resistor provides equal attack and decay times. The way you handle the pushbutton varies the effect.

## LINEAR IC SIREN

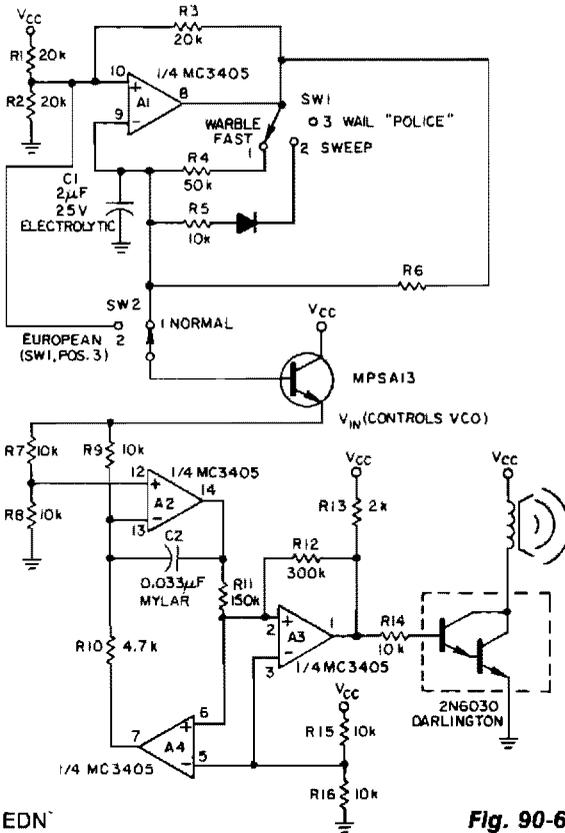

A low-frequency, op-amp oscillator and a VCO, both configured from a single MC3405 dual op amp and dual comparator, are the major components in a siren circuit that can be made to produce various warbles and wails, or serve as an audio sweep generator. The only other active components needed are an MPS A13 small-signal transistor and a 2N6030 power Darlington transistor.

Fig. 90-6

## SUPER SOUND GENERATOR


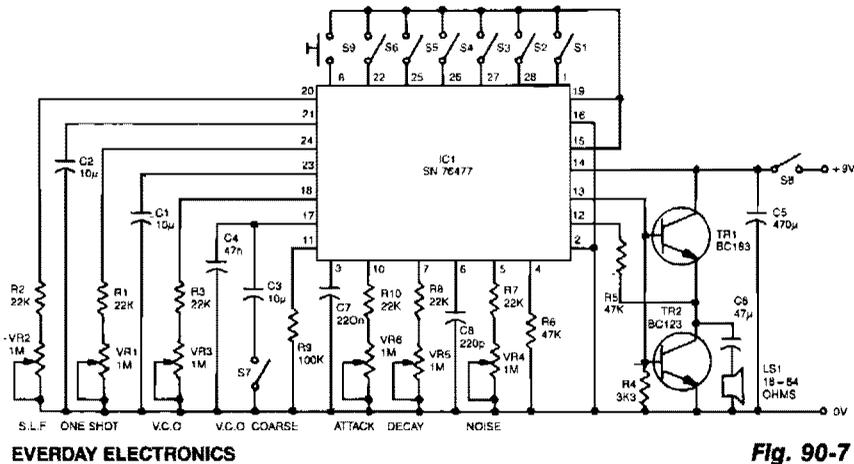


Fig. 90-7

## SUPER SOUND GENERATOR (Cont.)

Six preset controls and seven selector switches enable a vast range of different sounds to be produced and altered at will. Such sounds as steam trains chuffing, helicopters flying, bird chirping, and machine guns firing are possible, as well as the usual police sirens, phaser guns, and bomb explosions. The circuit incorporates an amplifier giving 150-mW output into a small loudspeaker. Alternatively, a separate amplifier system can be used for disco effects, car alarms, etc. Continuous or one-shot sounds are possible. For one-shot sounds, a push-button switch is provided, which can also be used to turn continuous sounds on and off. A single IC, SN76477, provides all of the sound generation circuits.

### HEE-HAW SIREN

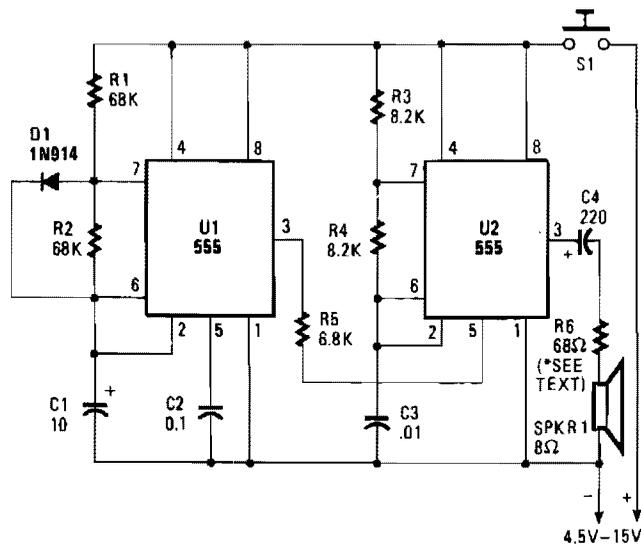

HANDS-ON ELECTRONICS

Fig. 90-8

A pair of timer IC's are the heart of a circuit that simulates the warbling hee-haw of a British police siren. One of the 555 timers, U2, is wired as an astable multivibrator operating at about 900 Hz. The other, U1, operates at approximately 1 Hz. Its output at pin 3 is a square wave with a 50% duty cycle—on and off cycles of about 0.5 second each. The output of U1 is applied to pin 5, the control-voltage terminal of U2. The frequency of the 555 timer IC is relatively independent of supply voltage, but can be varied over a fairly wide range by applying a variable voltage between pin 5 and ground. When U1's output becomes high, U2 operates at about 800 kHz. That switching between two frequencies produces the warbling hee-haw signal.

## ELECTRONIC SIREN

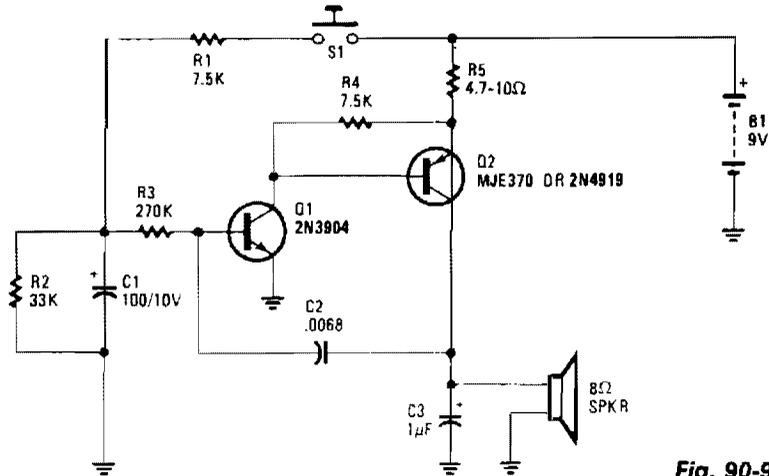


Fig. 90-9

Reprinted with permission from Radio-Electronics Magazine, December 1981. Copyright Gernsback Publications, Inc., 1981.

The wailing sound of a siren is generated by a VFO consisting of Q1 and Q2. Capacitor C2 provides the feedback for the oscillator. The frequency of the oscillator is varied by the voltage applied to the base of Q1 through R3. When switch S1 is closed, capacitor C1 charges, thus increasing the oscillator frequency. When S1 is released, capacitor C1 discharges, and the oscillator frequency decreases. Capacitor C3 limits the maximum oscillator frequency. The average battery current drain is about 15 mA.

## 555 BEEP TRANSFORMER


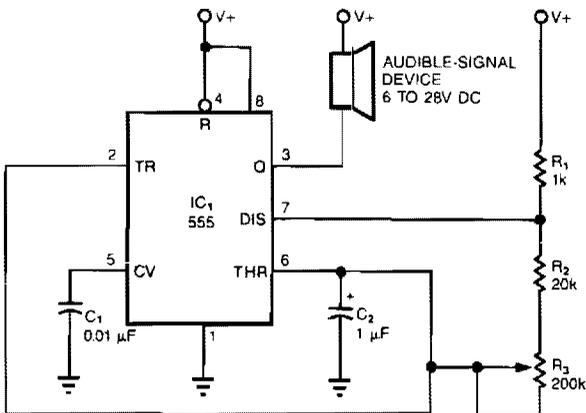


Fig. 90-10

The simple circuit transforms the steady beep of an audible-signal device, such as a Mallory sonalert, into a distinctive warble or chirp. The value of C2 determines just what tone color you'll get. With the 1- $\mu$ F value shown, the circuit produces a warble similar to the ring tone of an inexpensive phone. A 10- $\mu$ F value produces a chirp similar to a truck's back-up alarm. One elaboration of this circuit would be to use the second section of a 555 timer to drive a piezoelectric transducer instead of a sonalert; that modification would vary the tone's pitch, as well as the chirp rate.


### SIREN

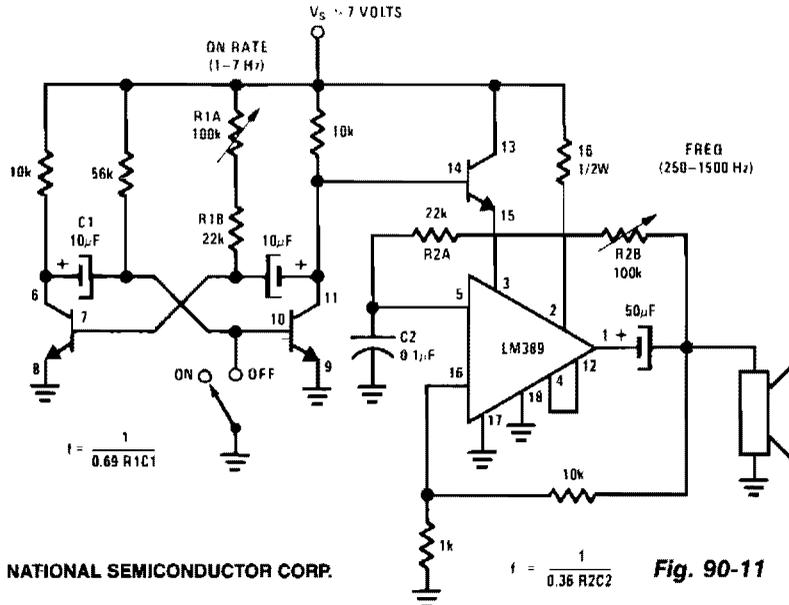

NATIONAL SEMICONDUCTOR CORP.

This circuit uses one of the LM389 transistors to gate the power amplifier on and off by applying the muting technique. The other transistors form a cross-coupled multivibrator circuit that controls the rate of the square-wave oscillator. The power amplifier is used as the square-wave oscillator with individual frequency adjust provided by potentiometer R2B.


### TWO-STATE SIREN

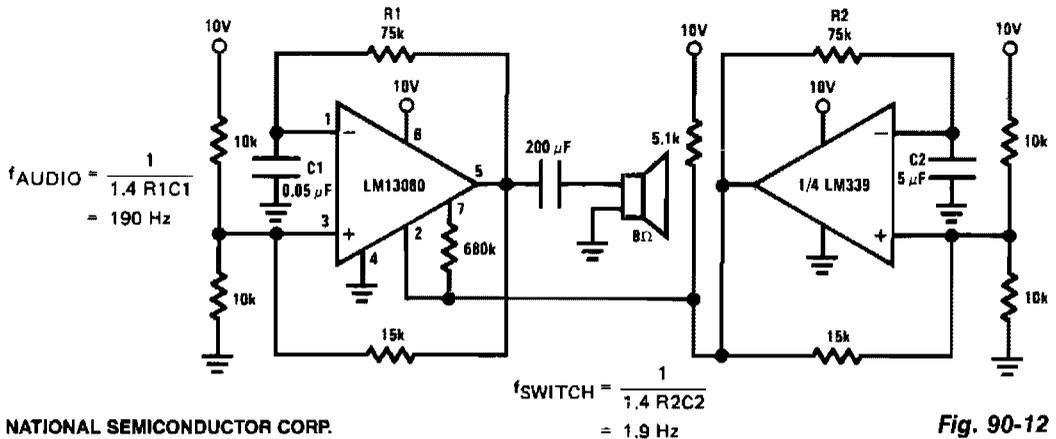

NATIONAL SEMICONDUCTOR CORP.

This is a two-state or on/off-type siren where the LM13080 oscillates at an audio frequency and drives an 8-Ω speaker. The LM339 acts as a switch which controls the audio burst rate.

## STEAM TRAIN WITH WHISTLE

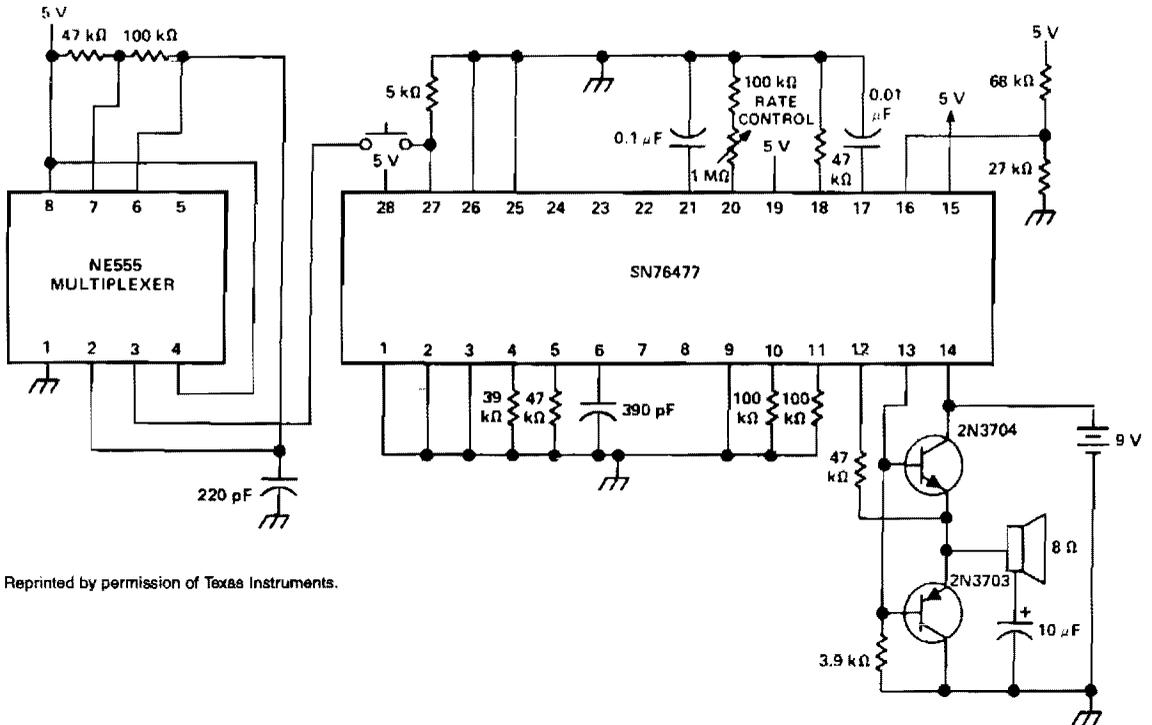

Reprinted by permission of Texas Instruments.

**Fig. 90-13**

# 91


## Solid-State Relay Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

*Ac Solid-State Relays*

## AC SOLID-STATE RELAYS

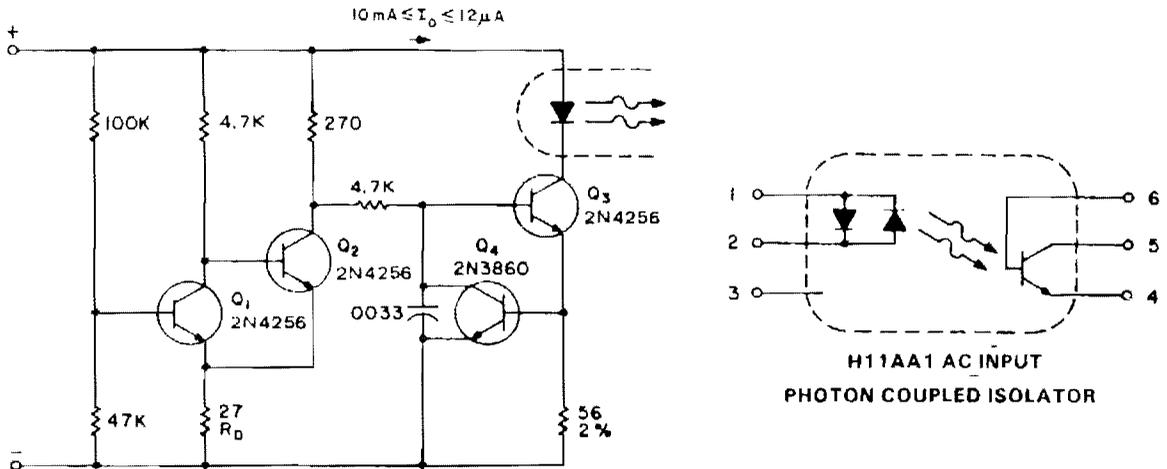

GE

**Fig. 91-1**

In the case where analog signals are being used as the logic control, hysteresis from a Schmitt-trigger input can be used to prevent half-wave power output. The circuit operation is as follows: at low input voltages, Q1 is biased in the off state. Q2 conducts and biases Q3, and the IRED turns off. When the base of Q1 reaches the biasing voltage of 0.6 V, plus the drop across  $R_D$ , Q1 turns on. Q3 is then supplied base drive, and the solid-state relay input will be activated. The combination of Q3 and Q4 acts as a constant-current source to the IRED. In order to turn-off Q3, the base drive must be reduced to pull it out of saturation. Because Q2 is in the off-state as the signal is reduced, Q1 will now stay on to a base bias-voltage lowered by the change in the drop across  $R_D$ . With these values, the highest turn-off voltage is 1.0 V, while turn-on will be at less than the 4.1 V supplied to the circuit.

For ac or bipolar input signals, there are several possible connections. If only positive signals are set to activate the relay, a diode, such as the A14, can be connected in parallel to protect the IRED from reverse voltage damage, since its specified peak reverse voltage capability is approximately 3 V. If ac signals are being used, or if activation is to be polarity insensitive, a H11AA coupler, which contains two LEDs in antiparallel connection, can be used. For high-input voltage designs, or for any easy means of converting a dc input relay to ac, a full-wave diode bridge can be used to bias the IRED.

92

## Solenoid Drivers

---


The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Power-Consumption Limiter

12-V Latch

Hold-Current Limiter

## POWER-CONSUMPTION LIMITER

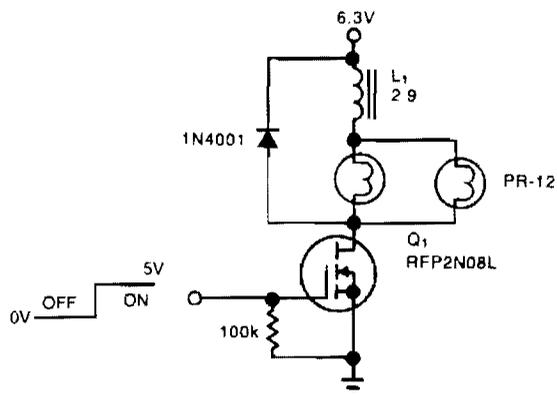

EDN


Fig. 92-1

A simple solenoid driver uses incandescent lamp filaments as on-indicators to limit power consumption. High magnetic reluctance (opposition to flux) in the coil of an armature-driven device, such as a solenoid or relay, calls for a surge of activation current, followed by a lower dc level to remain on,

since surge to on-current ratio is typically 5:1. The cold filament allows a surge of coil-activation current to pass through; as the filament heats up, it throttles the current to a more reasonable hold value. The solenoid driver circuit offers these features:

- 5-V logic swings turn the power-MOSFET switch, Q1, fully on and off.
- Two low-cost flashlight lamps, in parallel, handle the peak current. Because their dc current is only 50% of peak and because they operate at 60% of their rated voltage, the lamps have an operating life of 12,000 hours. Further, the lamp filaments' positive temperature coefficients raise each filament's resistance. This rise in resistance eliminates current-hogging problems and provides short-circuit protection.
- The steady-state on-current is 700 mA, vs. 1700 mA without the lamps.
- A 4.6-V min supply rating allows battery operation.

## 12-V LATCH

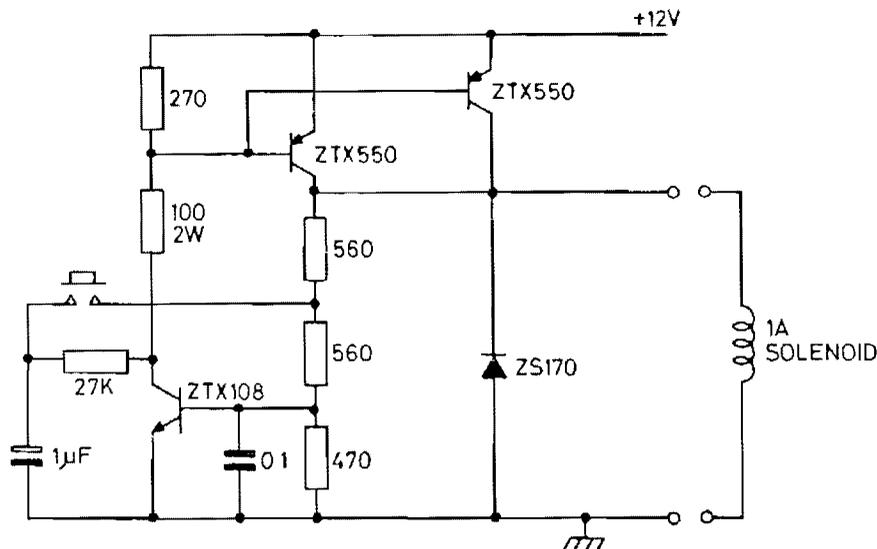


ZetEX, formerly FERRANTI

Fig. 92-2

## 12-V LATCH (Cont.)

This circuit controls a solenoid by the operation of a single push-button switch. The circuit will supply loads of over 1 A and can be operated up to a maximum speed of once every 0.6 second. When power is first applied to the circuit, the solenoid will always start in its off position. Other features of the circuit are its automatic turn-off, if the load is shorted, and its virtually zero-power consumption when off.

### HOLD-CURRENT LIMITER

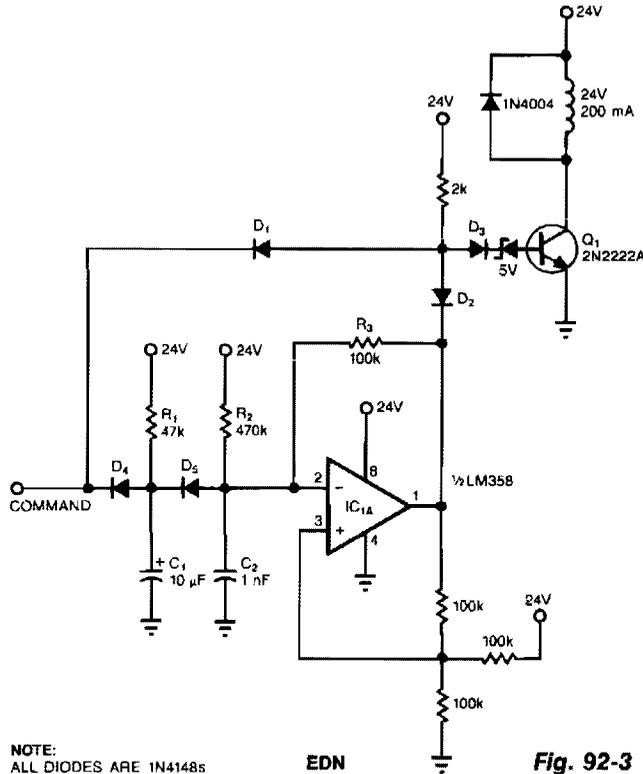

NOTE:  
ALL DIODES ARE 1N4148s

EDN

Fig. 92-3

In many applications, a solenoid driver must first briefly supply a large amount of pull-in current, which quickly actuates the solenoid. Thereafter, the driver must supply a much lower holding current to avoid burning the solenoid out. To avoid using the customary, cumbersome, large capacitors or power-wasting resistors, you can use the switch technique.

As long as the input to the circuit is low, diode D1 holds Q1 off; a low input also prevents the op-amp circuit from oscillating. When the input reaches 24 V, Q1 switches on and pulls in the solenoid. Concurrently, D4 is back-biased, and C1 begins charging up. When C1 charges up, the op-amp circuit begins to oscillate, switching Q1 on and off.

The time constant defined by R1 and C1 determines the length of the period during which the solenoid receives full power. R3 and C2 set the oscillator's frequency, and R2 sets the oscillator's duty cycle. The hold current is directly proportional to the duty cycle. For the components shown, the full-power period is 300 ms, the oscillator's frequency is 3 kHz, and its duty cycle is 50%.

# 93


## Sound Effects

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Sound-Effects Generator  
Fuzz Box  
Chug-Chug  
Electronic Bird Chirper  
Race-Car Motor/Crash

## SOUND-EFFECTS GENERATOR

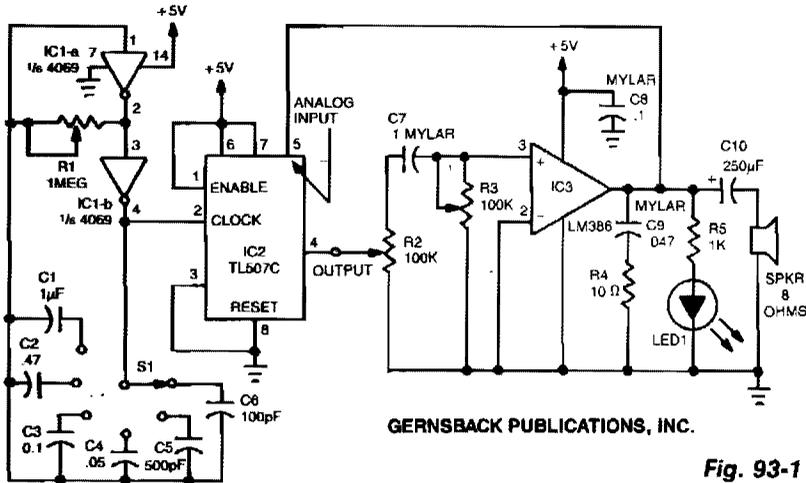


**Fig. 93-1**

A variable clock-pulse generator is made up of two sections of IC1 (a 4069 CMOS hex inverter), R1, S1, and capacitors C1 through C6. By adjusting R1 and switching one of the capacitors into the circuit, the clock's pulse rate can be varied over a wide range.

The TL507C converts analog signals—in this case the output of IC3, an LM386 audio amplifier—into digital signals. The conversion is accomplished using the single-slope method; it involves comparing an internally generated ramp signal to the analog input signal and a 200-mV reference voltage.

The square-wave output from the a/d converter is fed to IC3 through a network consisting of R2, R3, and C7. Resistor R2 controls the amplitude of the pulses. Resistor R3 and capacitor C7 form a variable tone-control filter and a differentiator circuit that converts a square wave into a spiked waveform. That waveform is amplified by IC3, and the resulting output is fed back into the analog input of IC2, as well as to an 8-Ω speaker. By adjusting R1 and selecting one of the six capacitors with S1—thus varying the clock frequency—and by varying R2 and R3, you can produce many sounds.

## FUZZ BOX

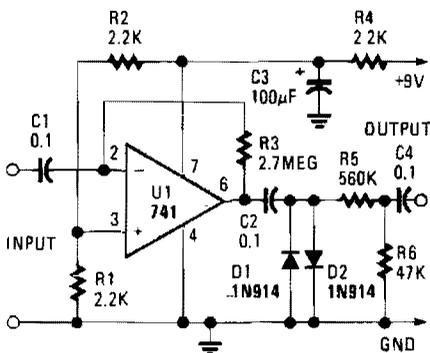


HANDS-ON ELECTRONICS

**Fig. 93-2**

The 741's maximum gain of 20,000 is pushed to nearly 3 million dB, and therefore distorts the output. That distortion provides the fuzz sound. The level is dropped by clipping the two diodes.

## CHUG-CHUG

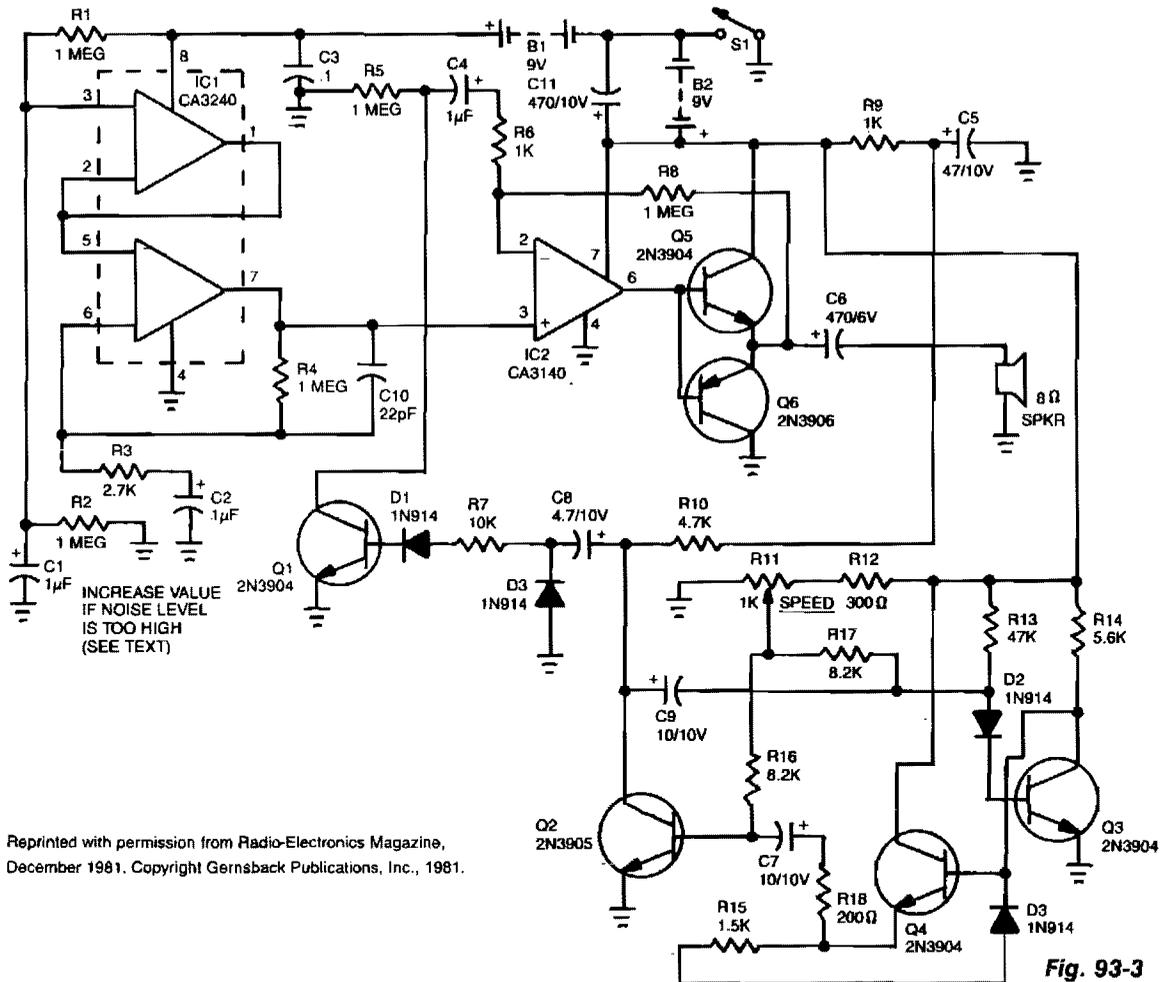


Reprinted with permission from Radio-Electronics Magazine, December 1981. Copyright Gernsback Publications, Inc., 1981.

Fig. 93-3

A CA3240 dual MOSFET-input device is used as a white-noise source. Op amp IC2 is used as a driver stage for the push-pull output stage formed by Q5 and Q6. Transistors Q2, Q3, and Q4 form a variable-frequency multivibrator. R11, the speed control, is used to control the multivibrator's frequency. The output is differentiated by C8 and applied to modulator transistor Q1, through D1 and R7. Transistor Q1 modulates the gain of the output amplifier stage by changing the impedance to ground, through R6 and C4. When the multivibrator's frequency is reduced using R11, C8 discharges slowly, creating a sound similar to escaping steam from a stopped locomotive.

To find the proper value for R3, short Q1's collector to ground. Then, increase the value of R3 until the current drain from the power supply is less than 60 mA. Then remove the short from Q1. To see if the device is operating properly, close switch S1 and reduce the resistance of R11. Wait 10 seconds, then rotate R11 slowly. You should hear a sound similar to a steam locomotive picking up speed.

## ELECTRONIC BIRD CHIRPER

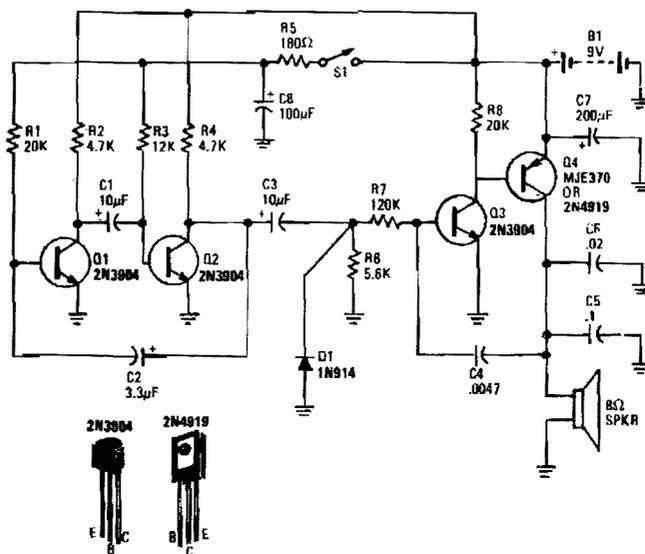

**Fig. 93-4**

Reprinted with permission from Radio-Electronics Magazine, December 1981. Copyright Gernsback Publications, Inc., 1981.

Transistors Q1 and Q2 form the two halves of a free-running multivibrator whose frequency is determined by the voltage across C8. That capacitor is charged and discharged by closing and opening switch S1. Transistors Q3 and Q4 make up a VFO. The output of the free-running multivibrator frequency modulates the Q3/Q4 oscillator, causing the chirping bird sound. The number of chirps per second is determined by the frequency of the Q1/Q2 multivibrator, which also varies. The pitch of the chirps is determined by C5 and C6.



# 94


## Sound-Operated Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Sound-Activated Switch  
Voice-Operated Switch

### SOUND-ACTIVATED SWITCH

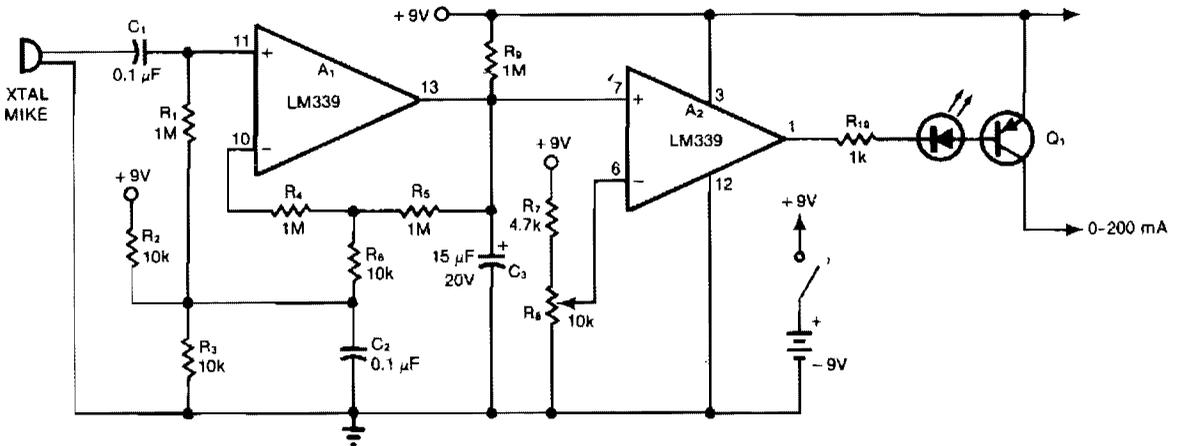


EDN

Fig. 94-1

A1 and A2 are two sections of a quad comparator. The first, A1, functions as an amplifier and detector. Resistors R5 and R6 set the gain at 100; the output of A1 is an open collector to negative-peak-rectify the output with a decay time constant determined by R9 and C3. This dc output is then compared with the reference level selected by R8. A2 triggers switch Q1, and an LED inserted in the base drive of Q1 gives visual indication of switch closure. The standby battery drain is 2 mA. Use potentiometer R8 to select the desired sensitivity.

### VOICE-OPERATED SWITCH

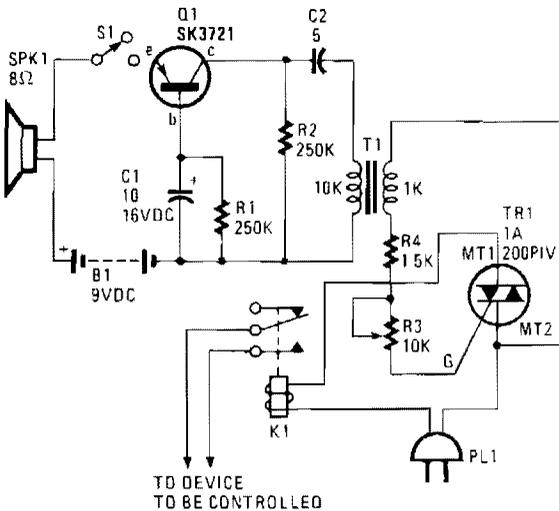

The sound picked up by SPKR1, which acts as a microphone, is fed to transistor amplifier Q1. The output of Q1 is applied across coupling transformer T1 and is used to drive the gate circuit of Triac TR1. TR1 is used to lend a latching effect to the action of the relay.

HANDS-ON ELECTRONICS

Fig. 94-2

# 95


## Splitters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Wideband Signal Splitter  
Precision Phase Splitter

## WIDEBAND SIGNAL SPLITTER

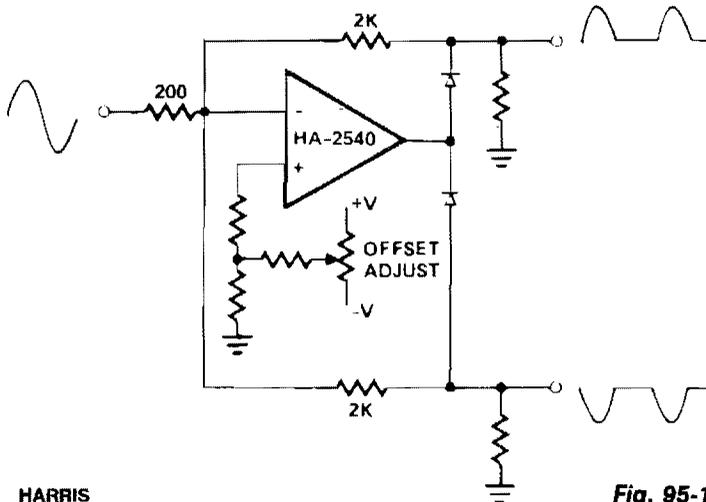


HARRIS

Fig. 95-1

With one HA-2539 or HA-2540 and two low-capacitance switching diodes, signals exceeding 10 MHz can be separated. This circuit is most useful for full-wave rectification, AM detection, or sync generation.

## PRECISION PHASE SPLITTER

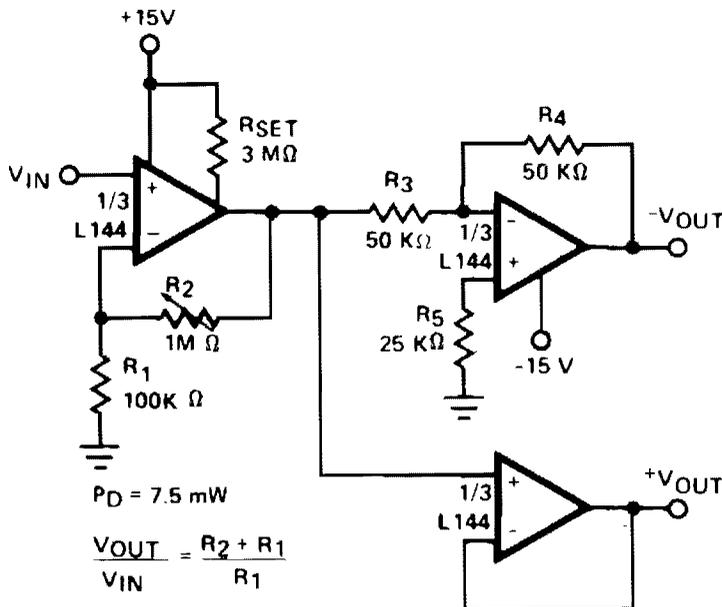

SILICONIX

Fig. 95-2

**96**


## **Square-Wave Generators**

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Square-Wave Pulse Extractor  
Nearly 50% Duty-Cycle Multivibrator  
High-Current Oscillator  
Quadrature-Output Oscillator

## SQUARE-WAVE PULSE EXTRACTOR

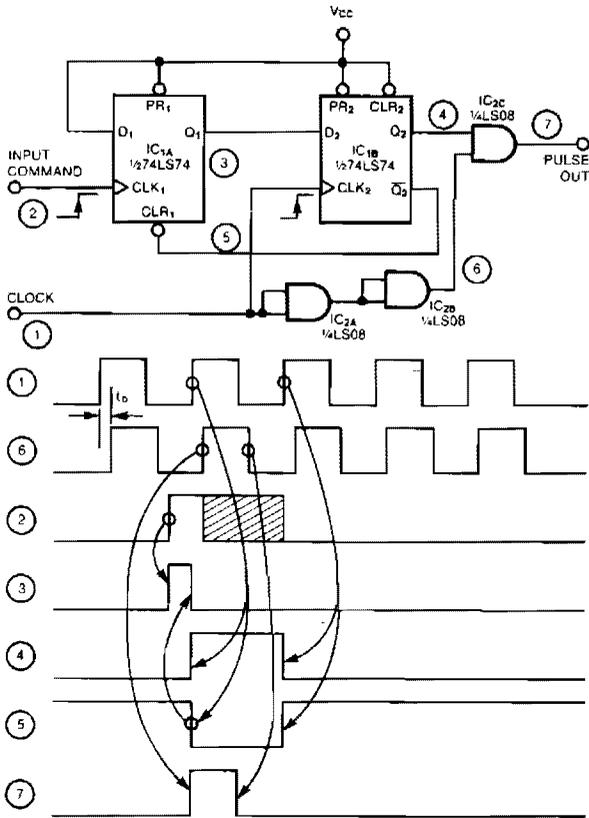


EDN

Fig. 96-1

This circuit traps a single positive pulse from a square-wave train. Following the rising edge of an input command, the pulse-out signal emits a replica of one positive pulse of the clock signal simultaneous with the clock signal's next rising edge. The input command signal sets the Q1 output of flip-flop IC1A. Consequently, the next rising edge of the clock signal sets the Q2 output of IC1B, which allows AND gate IC2C to pass the clock signal's next positive pulse. AND gates IC2A and IC2B prevent the generation of brief output glitches by delaying the clock signal by  $t_D$  seconds (two propagation delays).

## NEARLY 50% DUTY-CYCLE MULTIVIBRATOR

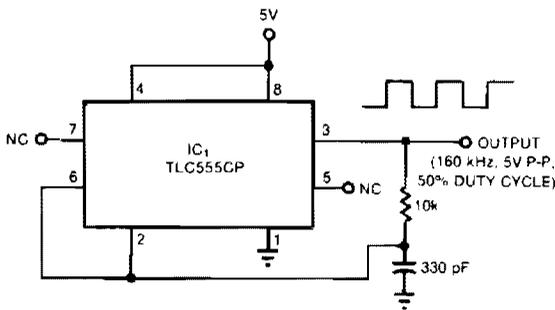


EDN

Fig. 96-2

Three factors contribute to the output symmetry. The capacitor charges and discharges through the same external resistor. An internal resistive divider sets accurate switching thresholds within the chip, the bipolar types use dividers, as well. Most importantly, IC1's CMOS output stage switches fully between ground and  $V_{CC}$ , avoiding the errors from asymmetry that are often found in a TTL timer's output. The IC's internal switching-threshold tolerances can cause a deviation of several percent from the desired 50% duty cycle. To meet a tighter specification, you might have to select from a group of ICs.

## HIGH-CURRENT OSCILLATOR

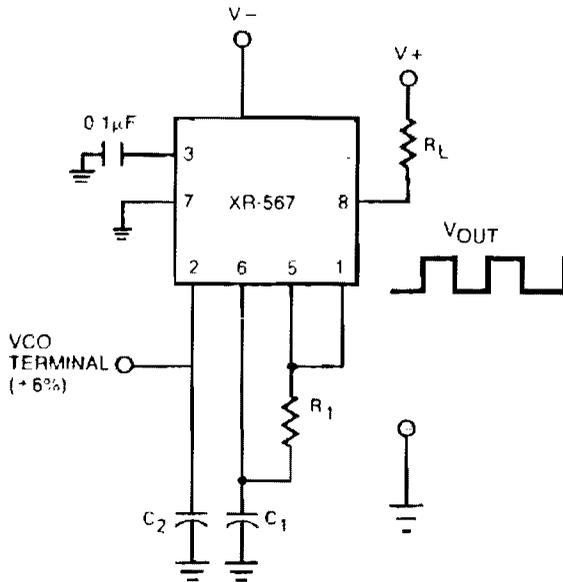


The oscillator output of the XR-567 can be amplified using the output amplifier and high-current logic output available at pin 8. In this manner, the circuit can switch 100-mA load currents without sacrificing oscillator stability. The oscillator frequency can be modulated over  $\pm 6\%$  in frequency by applying a control voltage of pin 2.

EXAR

Fig. 96-3

## QUADRATURE-OUTPUTS OSCILLATOR

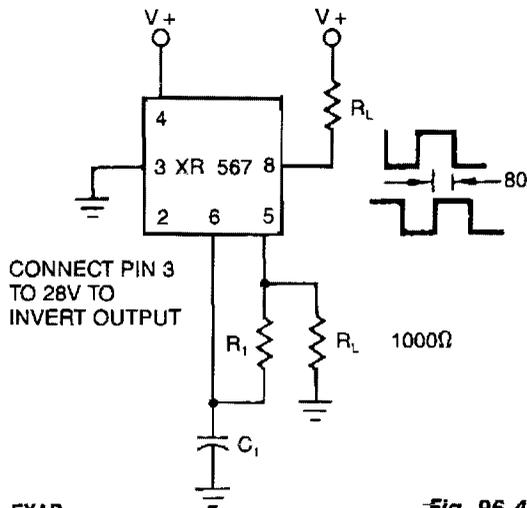

The XR-567 functions as a precision oscillator with two separate square-wave outputs at pins 5 and 8, that are at nearly quadrature phase with each other. Because of the internal biasing arrangement, the actual phase shift between the two outputs is typically 80%.

EXAR

Fig. 96-4

# 97


## Staircase Generators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

*μ*A2240 Staircase Generators  
Staircase Generator

## UA2240 STAIRCASE GENERATOR

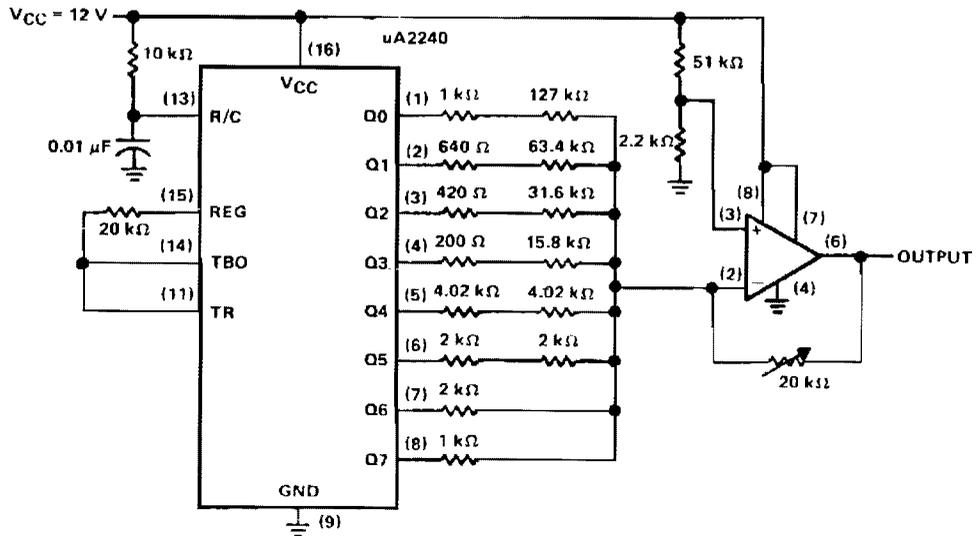


Reprinted by permission of Texas Instruments.

**Fig. 97-1**

The uA2240 timer/counter, combined with a precision resistor ladder network and an op amp, form the staircase generator. In the astable mode, once a trigger pulse is applied, the uA2240 operates continuously until it receives a reset pulse. The trigger input at pin 11 is tied to the time base output at pin 14, resulting in automatic starting and continuous operation. The frequency of the time-base oscillator, TBO, is set by the time constants  $R_1$  and  $C_1$  ( $f = 1/R_1C_1$ ). For this example, a 10-K $\Omega$  resistor and a 0.01- $\mu$ F capacitor form the timing network.

The counter outputs are connected to a precision resistor ladder network with binary-weighted resistors. The current sink through the resistors connected to the counter outputs correspond to the count number. For example, the current sink at Q7, the most significant bit, is 128 times the current sink at Q0, the least significant bit. As the count is generated by the uA2240 eight-bit counter, the current sink through each active binary-weighted resistor decreases the positive output of the op amp in discrete steps. The feedback potentiometer is set at a nominal 10 K $\Omega$  to supply a maximum output voltage range. An input of 12 V allows a 10-V output swing. With a 0.5-V input reference on pin 3 of the TCL271, the output will change from 10.46 V maximum, in 256 steps of 38.9 mV per step, to a 0.5 V minimum. Each step has a pulse duration of 100  $\mu$ s and an amplitude decrease of 38.9 mV. The waveform output is repeated until a reset is applied to the uA2240.

## STAIRCASE GENERATOR

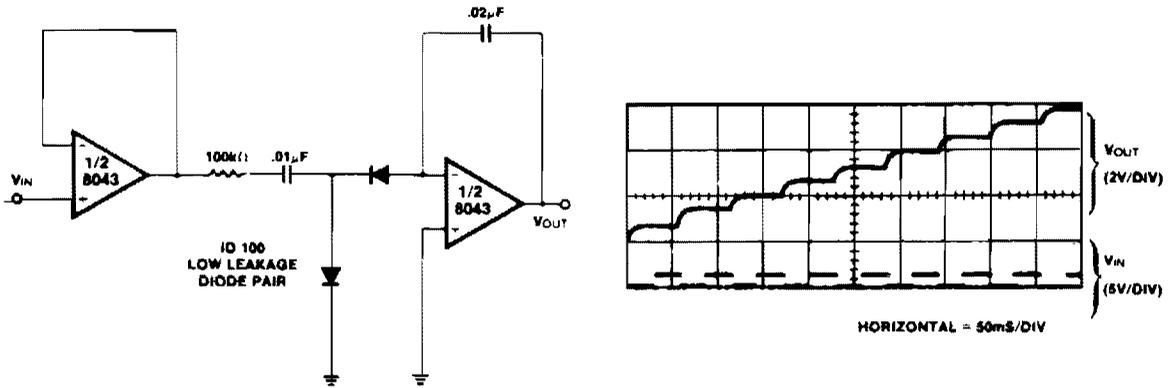

INTERSIL

Fig. 97-2

This circuit is a high-input impedance version of the so-called *diode pump* or *staircase generator*. Note that charge transfer takes place at the negative-going edge of the input signal. The most common application for staircase generators is in low-cost counters. By resetting the capacitor when the output reaches a predetermined level, the circuit can be made to count reliably up to a maximum of about 10.

**98**


## **Strobe Circuit**

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Variable Strobe Light

## VARIABLE STROBE LIGHT

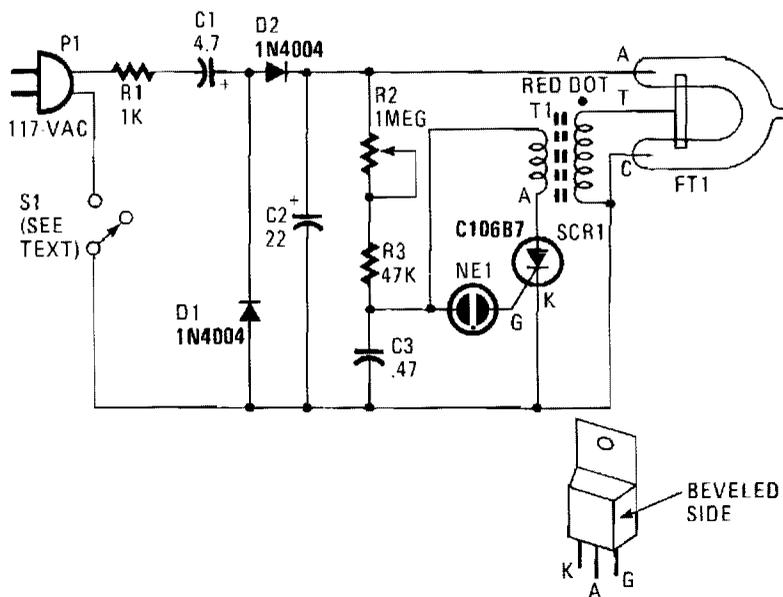

HANDS-ON ELECTRONICS

**Fig. 98-1**

In this strobe-light, two circuits are needed; one circuit charges a capacitor placing 320 Vdc between the cathode and anode of the flashtube. The other circuit provides bursts of approximately 4000 V to trigger the flashtube into conduction. The voltage-doubler works by summing two equal voltages in series, which results in a doubling of the voltage. The 4000 V needed to trigger the flashtube is provided by transformer T1—a voltage step-up transformer that develops 4000 V across its secondary coil when current flows in the primary coil. Silicon-controlled rectifier SCR1 controls the current flow in the primary coil of T1. When SCR1 conducts, current flows suddenly in the primary coil and 4000 Vac spikes appear across the secondary coil. For conduction, SCR1 needs a negative and positive voltage on the cathode and anode, respectively, and a positive voltage on the gate. It is the function of components R2, R3, C3, and NE1 to provide that positive gate voltage and turn on SCR1. Potentiometer R2, resistor R3, and capacitor C3 form an rc timing circuit. Control of charging time of C3 is accomplished by varying that resistance in the circuit. When the voltage on C3 reaches the firing voltage of the neon bulb, it causes NE1 to conduct, thus placing a positive voltage, from C3, on the gate of SCR1. The SCR now turns on and C3 discharges through SCR1 and the primary coil of T1. The 4000 V that is developed across the secondary coil of T1 fires the xenon tube, causing a bright flash. The whole process then repeats itself with C3 charging up, NE1 firing to short out SCR1, and T1 developing 4000 V to trigger the xenon flashtube.

# 99

## Switching Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Rf Power Switch  
Switch Debouncer  
SCR-Replacing Latching Switch  
One-MOSPOWER FET Analog Switch  
On/Off Inverters

## RF POWER SWITCH

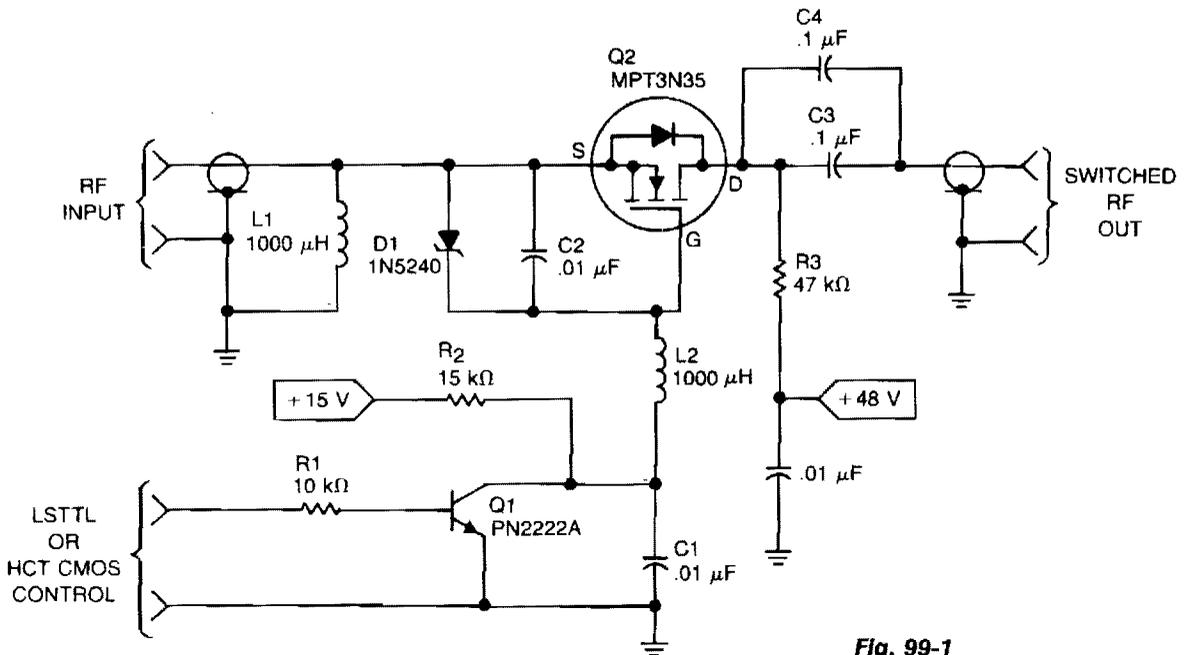


Fig. 99-1

Copyright of Motorola, Inc. Used by permission.

This rf power switch operates at 1.7 MHz with a 50-V source and load. Its on loss is 0.2 dB and its off isolation is 30 dB. It provides 40-W PEP, 45  $V_{PEAK}$  and 0.9  $A_{PEAK}$ . The control input can come from CMOS, TTL, LS, etc., to turn on Q1, which turns on Q2, a TMOS MPT3N35.

## SWITCH DEBOUNCER


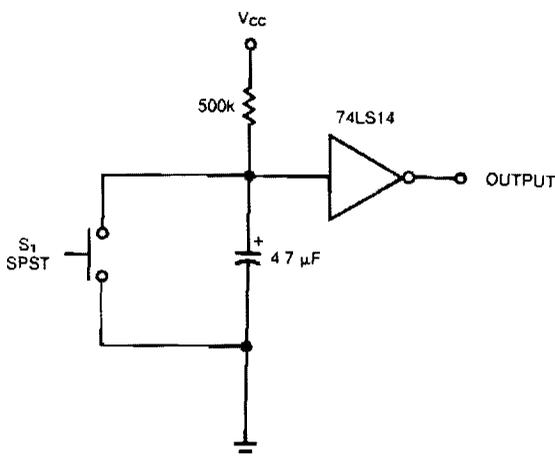


Fig. 99-2

TTL inverter 74LS14 has an internal 16-K $\Omega$ , pull-up resistor that pulls the gate input high when the switch is open. As you close the switch, the 4.7- $\mu$ F capacitor discharges on the first contact. If the switch contacts bounce open, the internal resistor limits the capacitor's recharge to a rate sufficiently slow to prevent an undesired gate transition before the contacts again close. Note that the circuit correctly debounces the switch for both opening and closing. If you add an external pull-up resistor, you can use a CMOS Schmitt-trigger gate, 74HC14, and a smaller, 0.1- $\mu$ F, capacitor.

EDN

## SCR-REPLACING LATCHING SWITCH

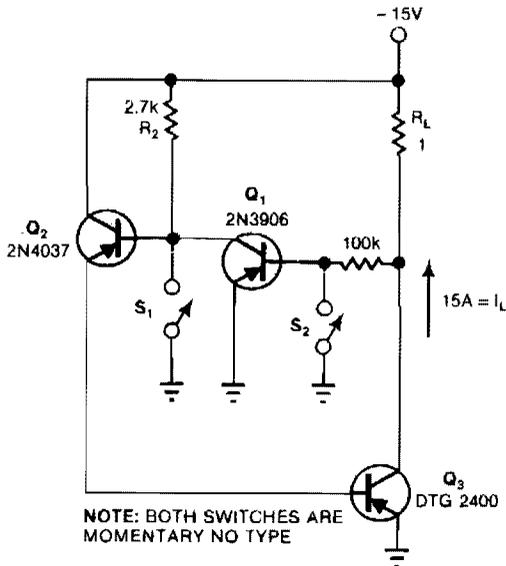


EDN

Fig. 99-3

This circuit provides the turn-on characteristics of an SCR, but turns off with ease. The switch is comprised of three transistors with descending current ratings: Q3 has a high-current rating and Q2 has a medium rating. The current,  $I_L$ , to be switched is 15 A. Momentarily depressing S2 removes Q1's base drive, turning Q1 off and allowing Q2 to turn on. Q2 then drives the base-emitter junction of Q3, turning Q3 on. Q3's collector-emitter voltage, which serves as Q1's base drive, is essentially zero, keeping Q1 off. To turn Q3 off, depress S1; this action momentarily shunts Q2's base current to ground, reversing the chain of events that turned Q3 on.

## ONE-MOSPOWER FET ANALOG SWITCH

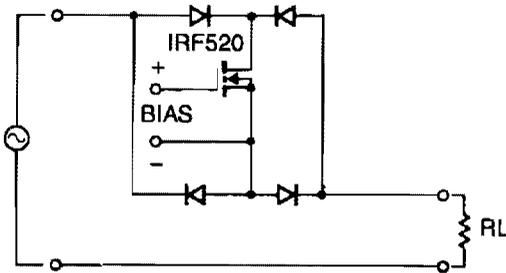


SILICONIX

Fig. 99-4

Using four diodes in an array allows using only one MOSPOWER transistor for analog switching. The current flow is controlled by keeping the source-base connection of the MOSFET towards the load. Be sure to use diodes capable of handling the load current and a transistor whose breakdown voltage specification exceeds the peak analog voltage anticipated. Operationally, by increasing the gate-to-source bias voltage, the MOSFET turns on. For applications other than either full-on or full-off, care must be taken not to exceed the dissipation of the MOSPOWER transistor. A suitable heatsink cannot be overstressed in such applications.

## ON/OFF INVERTERS

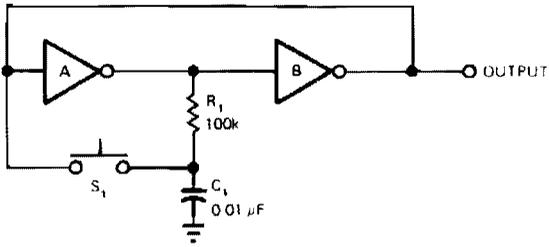

EDN

**Fig. 99-5**

Each time the switch closes, the voltage on  $C_1$  causes inverter A to change state, with positive feedback from inverter B. Resistor  $R_1$  delays the charging and discharging of  $C_1$ , making the circuit virtually immune to contact bounce. The circuit works with either CMOS or TTL gates. The values of  $R_1$  and  $C_1$  are not critical and can be increased for greater contact bounce protection, if needed. Recommended ranges are 10 K to 1 M $\Omega$  for  $R_1$ , and 0.01 to 1.0  $\mu\text{F}$  for  $C_1$ .

# 100

## Tachometer Circuits


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Low-Frequency Tachometer  
Tachometer  
Calibrated Tachometer



## TACHOMETER

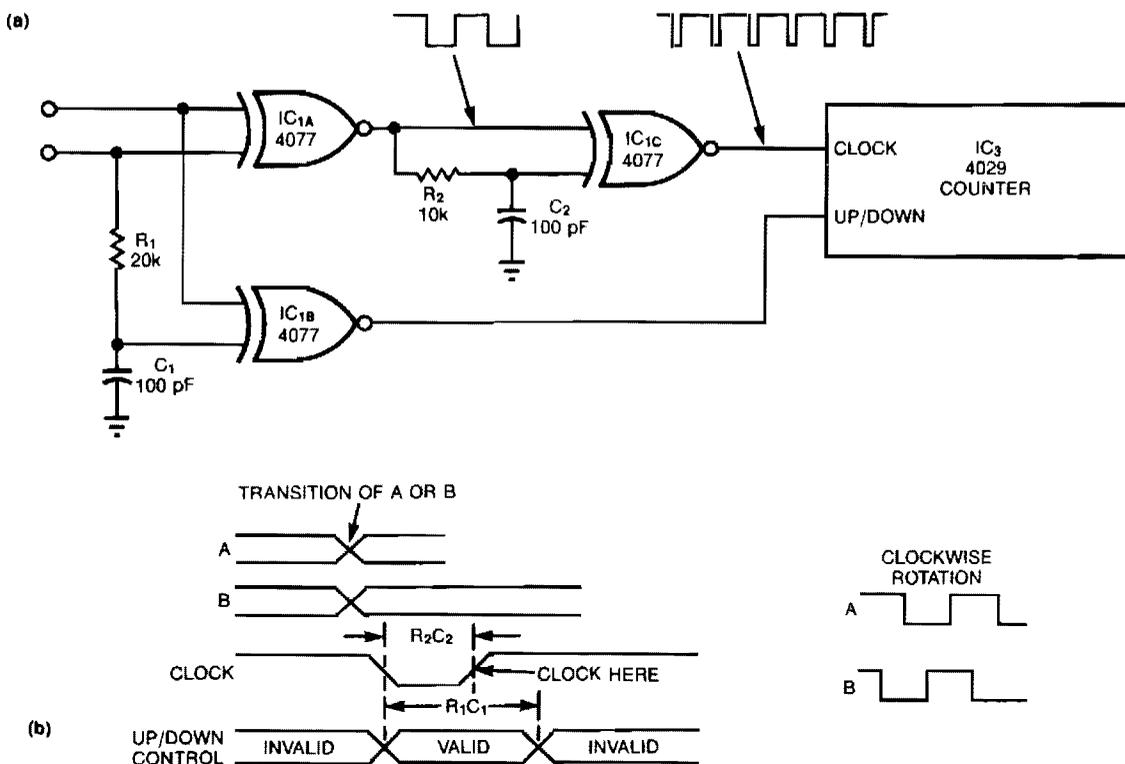

EDN


Fig. 100-2

A standard shaft encoder's *A* and *B* ports generate square waves with the same frequency as the shaft turns. The phase of *A* will lead or lag that of *B* by  $90^\circ$ , depending on the direction of rotation. To obtain maximum resolution, the tachometer circuit must count every change of the state for the *A* and *B* signals. Each such change causes a change of state at IC1A's output, followed by a  $1\text{-}\mu\text{s}$  negative pulse at the output of IC1C. These clock pulses' positive (trailing) edges cause the counter to count up or down, according to the direction of shaft rotation.

You should set the  $R_1C_1$  time constant, so that it is approximately twice that of the  $R_2C_2$  product, to ensure adequate setup and hold times for the up/down signal with respect to the positive clock edges. IC1C supports this timing requirement by producing clock pulses of similar duration for either positive or negative transitions or IC1A.

The exclusive-NOR logic of IC1B generates the correct polarity of the up/down signal when necessary, at the positive clock edges, by combining the *A* value with the *B* value just prior to a transition of *A* or *B*.  $C_1$  provides memory by sorting the *B* value voltage for about  $2\ \mu\text{s}$ . The maximum frequency for *A* or *B* is approximately  $(4R_1C_1)^{-1}$ .

## CALIBRATED TACHOMETER

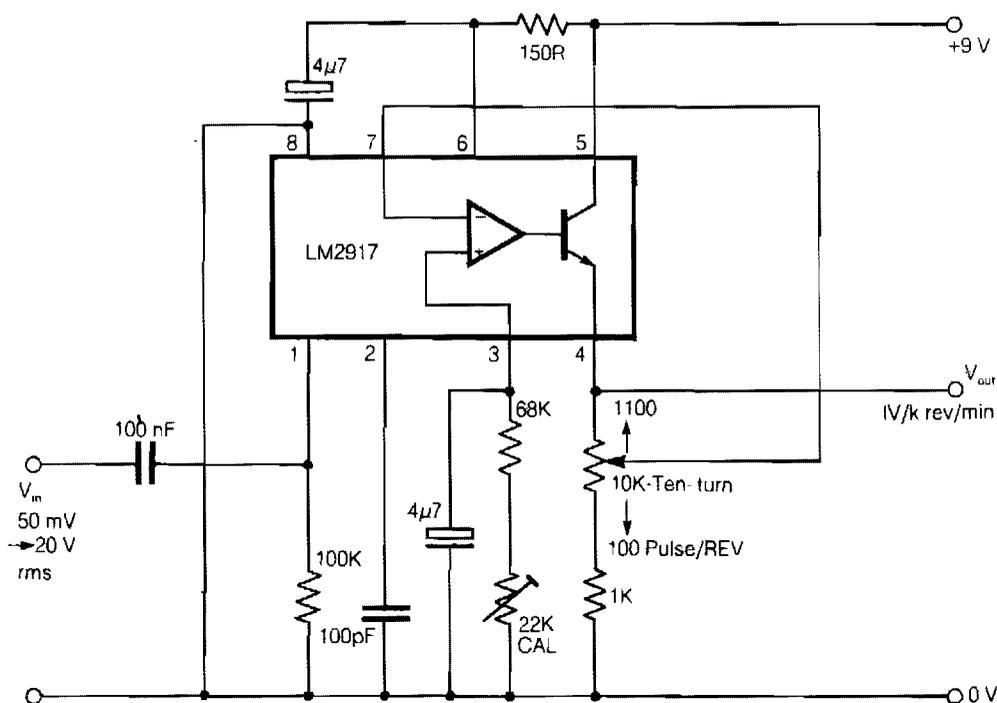

ELECTRONIC ENGINEERING

**Fig. 100-3**

Here is a simple tachometer circuit for use with a hand-held DVM or portable chart recorder. A novel feature is that the source frequency pulse/rev rate can be directly set on a ten-turn potentiometer to provide a convenient calibration of one V per 1000 rev/min. This is particularly useful when measuring a shaft or engine speed by sensing gear teeth.

The circuit uses an LM2917 IC which is specifically designed for tachometer applications. The ten-turn potentiometer, which provides the pulse/rev setting, is suitably configured in the output amplifier feedback path. The pulse/rev range is 100 to 1100, so the potentiometer dial mechanism should be set to start at 100 to provide direct calibration.

The IC's internal 7.5-V zener provides stable operation from a 9-V battery. The tachometer accepts an input signal between 50 mv and 20 V rms and has an upper speed limit of 6000 rev/min with the component values shown.

# 101


## Tape-Recorder Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Extended-Play Circuit  
Sound-Activated Switch  
Sound-Activated Tape Switch

## EXTENDED-PLAY CIRCUIT

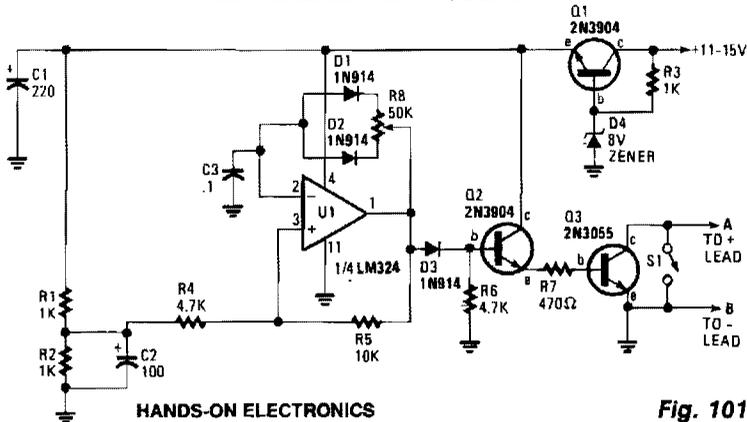


**Fig. 101-1**

A single op amp—one of four contained in the popular LM324—is operating in a variable pulsewidth, free-running squarewave oscillator circuit, with its timed output driving two transistors that control the on/off cycle of the tape-drive motor.

The oscillator's positive feedback path holds the secret to the successful operation of the variable on/off timing signal. The two diodes and pulsewidth potentiometer R8 allows the setting of the on and off time, without affecting the oscillator's operating frequency. One diode allows only the discharge current to flow through it and the section of R8 that it's connected to. The other diode, and its portion of R8, sets the charge time for the timing capacitor, C3. Since the recorder's speed is controlled by the precise off/on timing of the oscillator, a simple voltage-regulator circuit (Q1, R3, and D4) is included.

Connecting the speed control to most cassette recorders is a simple matter of digging into the recorder and disconnecting either of the motor's power leads, the ground or common side might be best, and connecting the recorder through a length of small, shielded cable to the control circuit. In some recorders, a remote input jack is furnished to remotely turn on and off the recorder. Before going in and modifying a recorder with a remote jack, try connecting the circuit to the external remote input.


## SOUND-ACTIVATED SWITCH

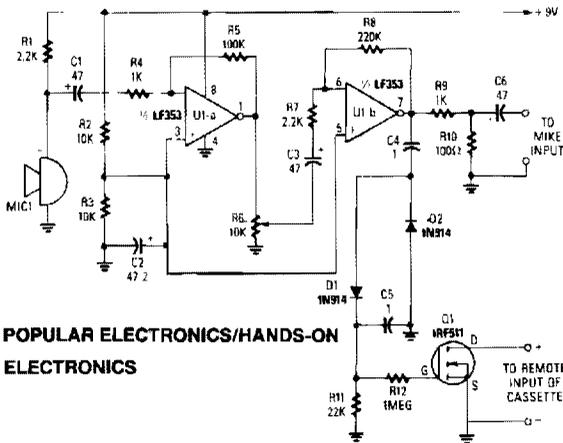

**Fig. 101-2**

A sensitive electret microphone picks up the sound and feeds the signal to a two-stage amplifier circuit, consisting of U1a and U1b. The amplified output of U1b is fed to a voltage-doubler circuit (comprised of D1, D2, C4, and C5). The output of the doubler is input to the gate of Q1. When the dc voltage reaches the gate's threshold level, Q1 switches on, starting the recorder. Resistor R6 sets the circuit's sensitivity and should be experimented with to obtain the optimum adjustment.

## SOUND-ACTIVATED TAPE SWITCH

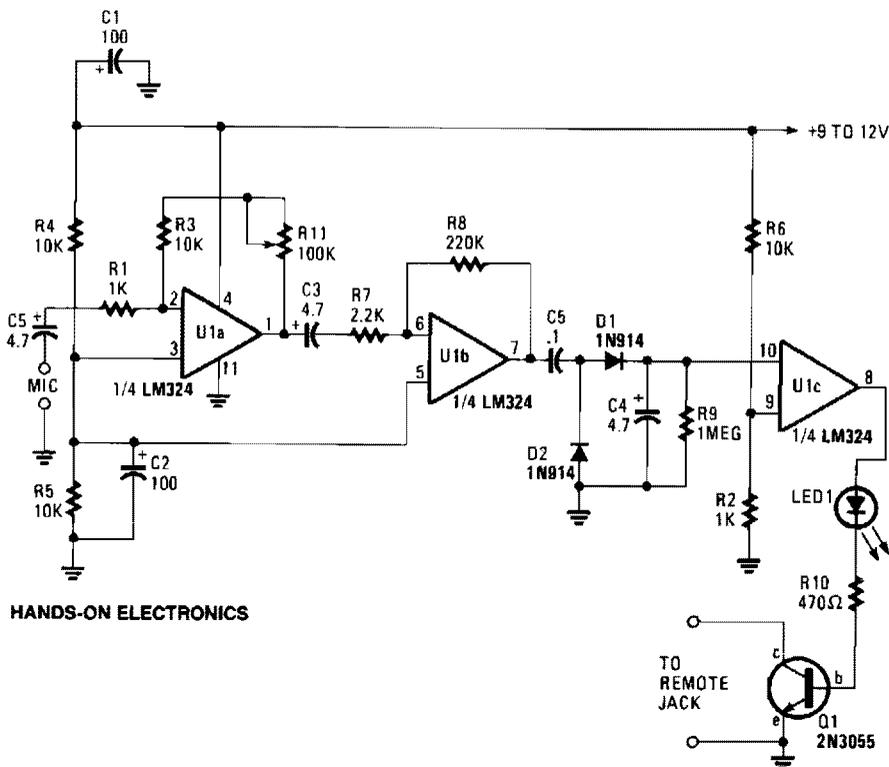

**Fig. 101-3**

This circuit can cause a cassette recorder to automatically turn on and record when a sound or noise is present. Another use, is when the sound-activated switch is used to turn on a cassette player so that it operates as a burglar-alarm detector and sounder. Op amps U1a and U1b are connected in tandem to amplify the sounds picked up by the detector's mike. The amplified audio voltage, output at pin 7 of U1b, is fed to a voltage-doubler circuit, consisting of D1 and D2. The elevated voltage from the doubler circuit is input to the positive input of op amp U1c, which is operating as a simple comparator circuit. The other input of U1c is connected to a voltage divider that sets the switching point for the dc signal voltage, to turn on when the signal level is greater than about 1.5 V. As the comparator switches on, its output at pin 8 becomes positive and supplies a forward bias to turn on D3 and Q1, which in turn, starts the recorder. The rc combination of C4/R9 sets the cassette's run time after the input sound has ceased, preventing the recorder from chopping-up or turning-off between closely spaced sounds or words picked up by the mike. The delay time is roughly 6 to 8 seconds. R11 sets the circuit's gain. Connect a low-impedance cassette mike to the amplifier's input, and connect the output of Q1 to the cassette's remote input or to the internal input and set the recorder to the record position. Talk and adjust the amplifier's gain with R11 for the desired sensitivity.

# 102


## Telephone-Related Circuits

---


The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Single-Chip Pulse/Tone Dialer	Telephone Handset Encoder
Telephone-Controlled Night Light	Dial Pulse Indicator
Hands-Free Telephone	Telephone Sound Level Meter Monitor
Electronic Telephone Set with Redial	Remote Telephone Ringer
Ringer Relay	Telephone Speech Activity Detector
Tone-Dialing Telephone	Duplex Line Amplifier
Telephone Repeater	Phone Recorder
Speakerphone	Line-Activated Solid-State Switch
Series Telephone Connection	Cassette Interface
Simple Touchtone™ Generator	Ring Detector
Pulse-Dialing Telephone	Wireless Telephone Eavesdropper
Optically Interfaced Ring Detector	Telephone Amplifier
Parallel Telephone Connection	Telephone Tap
Add-On Telephone Hold Button	

## SINGLE-CHIP PULSE/TONE DIALER

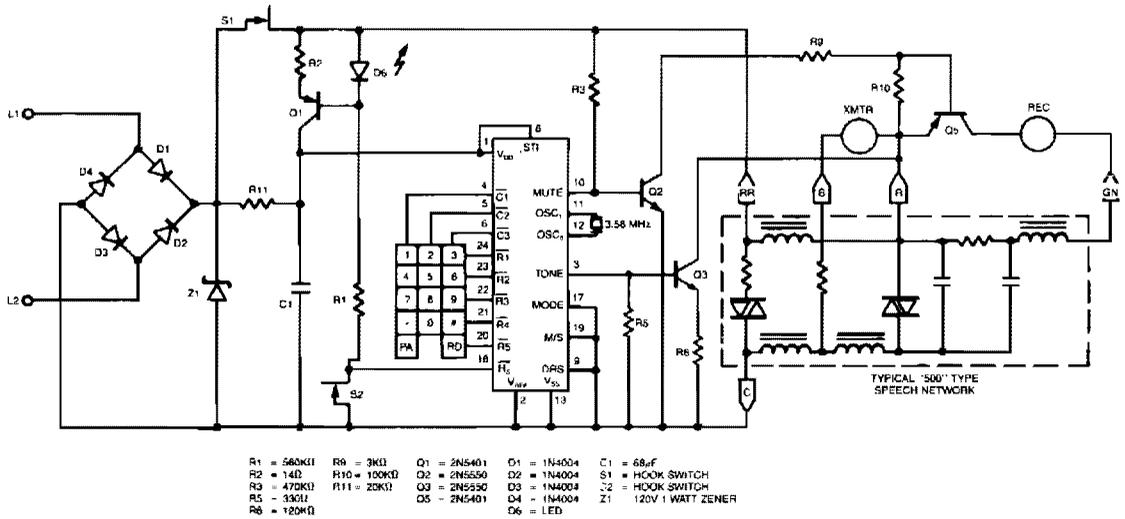

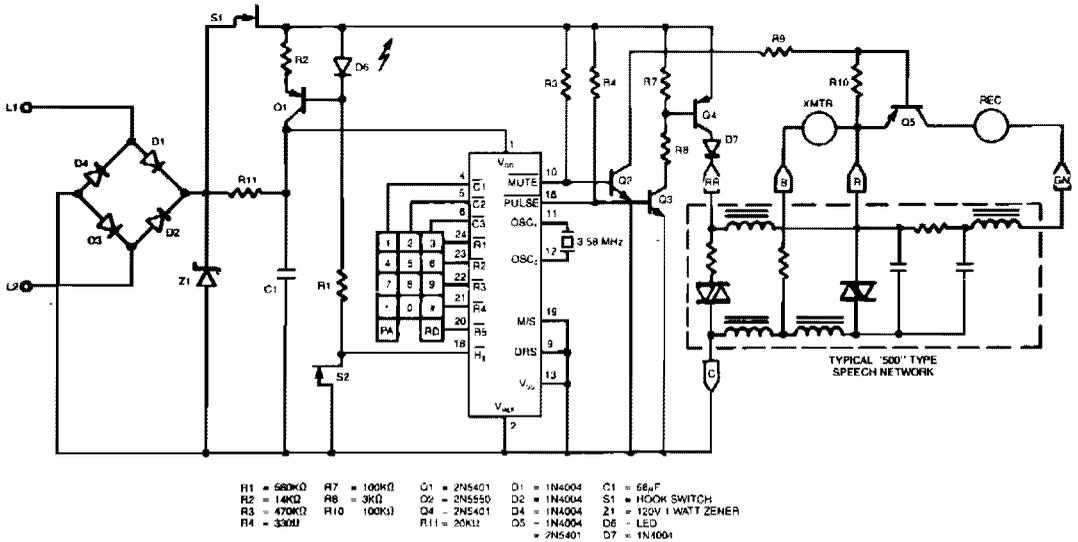**Typical Tone Dialing Application Circuit**




**Typical Pulse Dialing Application Circuit**

**Fig. 102-1**

EXAR

The XR-T5990 single-chip pulse/tone Dialer is a silicon gate CMOS circuit which performs both pulse and tone functions. It is designed to operate directly from the telephone line or on a separate small power supply. A 17-digit buffer is provided for redial feature.

## TELEPHONE-CONTROLLED NIGHT LIGHT

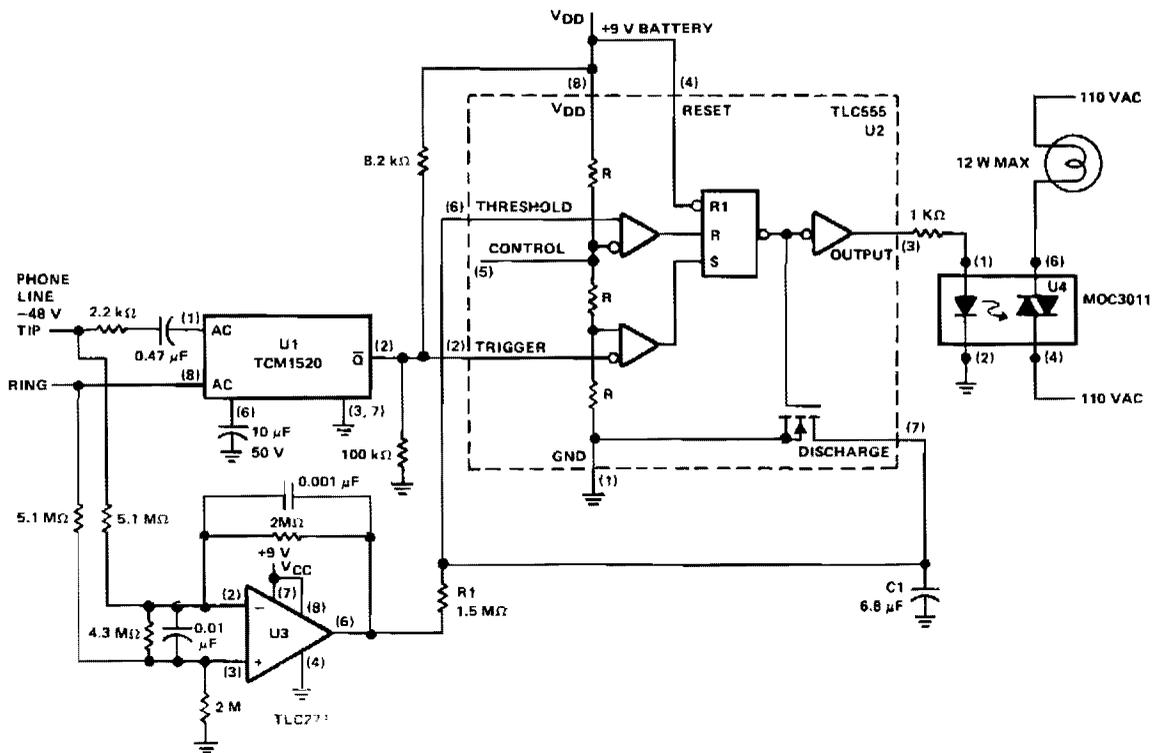


Reprinted by permission of Texas Instruments.

**Fig. 102-2**

When the telephone rings, or when the handset is lifted, the night light is turned on and remains on while the conversation takes place. When the handset is replaced in the cradle, the light remains on for about 11 s. During standby conditions, the  $-28\text{ Vdc}$  bias on the phone line maintains the output of U3 in a high state. When the ac ring signal is applied to the phone line, it is processed by the ring detector U1, producing a negative output pulse at pin 2 for each ring. These pulses trigger U2, causing its output to become high and the discharge transistor to turn off. The high output of U2 activates optoisolator U4, which turns on the night light. Each ring retriggers the timer and discharges C1, preventing it from reaching the  $\frac{2}{3} V_{DD}$  threshold level. Thus, the night light will remain on while the phone is ringing and for about 11 s after the last ring. After 11 s, C1 will be charged to the U2 threshold level ( $\frac{2}{3} V_{DD}$ ) resulting in the U2 output returning to a low level and its discharge output turning on, discharging C1. The lamp will turn off if the phone is not answered.

When the phone is answered, a 1-K $\Omega$  load is placed across the phone. This removes the differential input to op amp U3, causing its output to become low, and capacitor C1 starts discharging through R1. As long as the voltage across C1 remains low, timer U2 cannot start its cycle and the lamp will remain on. When the phone is hung up, the low impedance is removed from the phone line and the differential voltage across the line causes the U3 output to become high. This allows C1 to start charging, initiating the timing that will turn off the night light.

## HANDS-FREE TELEPHONE

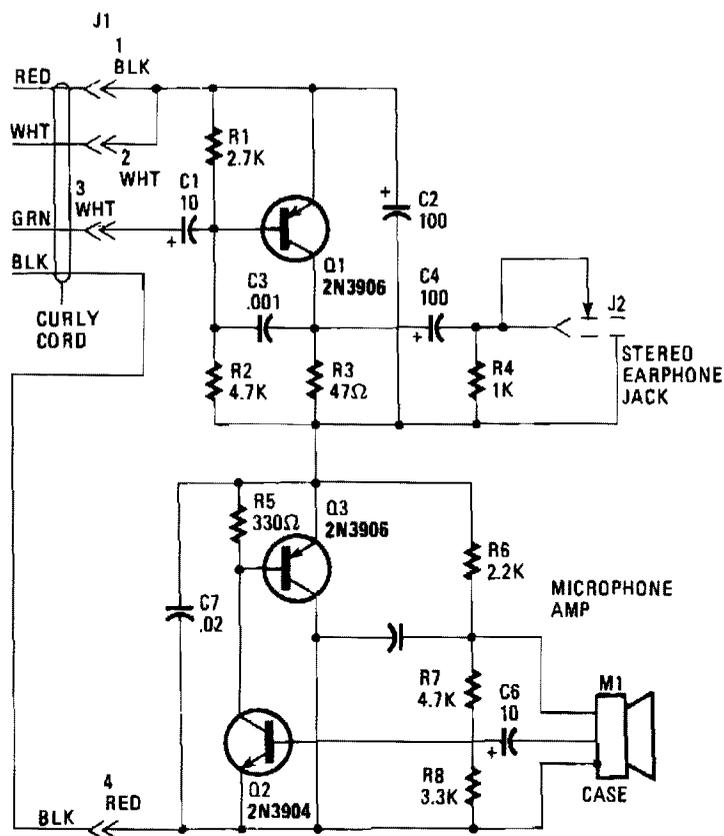


HANDS-ON ELECTRONICS

Fig. 102-3

Transistor Q1 of the headset amplifier circuit amplifies the 30 mV signal, that would have gone to the earphones, to .5 V, which sufficiently drives the stereo earphones. Capacitor C1 blocks any dc current from shorting back into the telephone base. Capacitor C2 provides the very important ac signal short around the amplifier. Capacitor C3 provides high-frequency rolloff characteristics and prevents the amplifier from oscillating. Capacitor C4 is a dc block to the 35- $\Omega$  impedance of the stereo earphones, and resistor R4 bleeds off any charge build up to prevent a popping sound when the stereo earphones are plugged into the mini-earphone jack J2. The headset amplifier has only about 2 Vdc across it. The microphone amplifier circuit is composed of transistors Q2 and Q3 in an inverted-Darlington configuration.

Another, and perhaps easier, way to understand the operation of this circuit is to consider Q3 as an emitter-follower stage. The electret microphone has a built-in FET IC amplifier that needs at least 3 V at 0.4 mA of clean supply power in order to provide an output impedance of 200 to 800  $\Omega$ . Resistors R6 and C5 provide that clean dc power to the FET IC and also provide the bias to Q2 without an ac feedback, which would have reduced Q2's gain. Capacitor C6 blocks the output dc bias from the FET IC.

## ELECTRONIC TELEPHONE SET WITH REDIAL

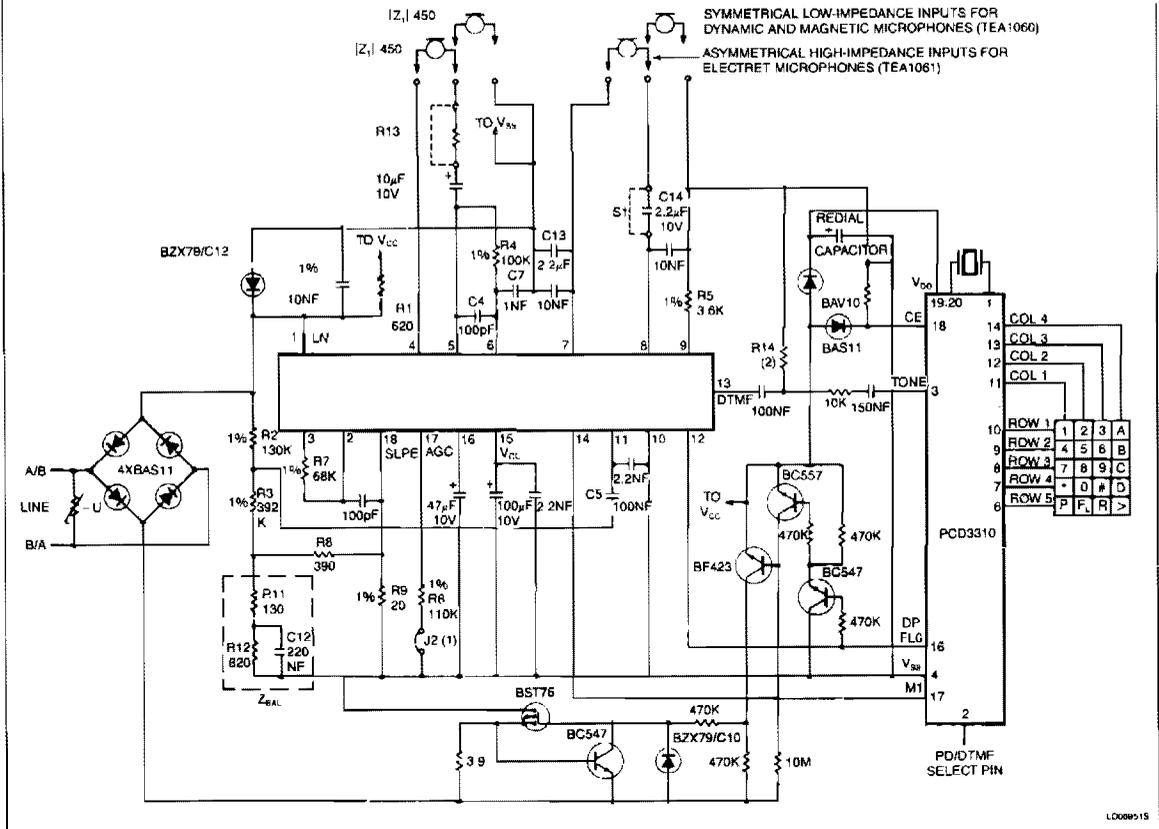

LD089515


**NOTES:**

- 1 Automatic line compension obtained by connecting R6 to V<sub>SS</sub>
- 2 The value of resistor R14 is determined by the required level at LN and the DTMF gain of the TEA1060

**SIGNETICS**

**Fig. 102-4**


## RINGER RELAY

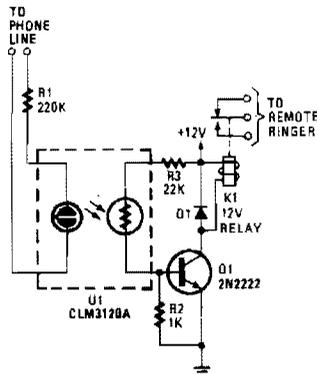

When the phone rings, the ring signal from the telephone company lights a neon lamp within a CLM3120 optocoupler. That causes a drop in the resistance of the CdS cell output of the device, turning on transistor Q1. When Q1 turns on, relay K1 is energized. The circuit should be connected in series with the lamp that is to be activated.

**Fig. 102-5**


## TONE-DIALING TELEPHONE

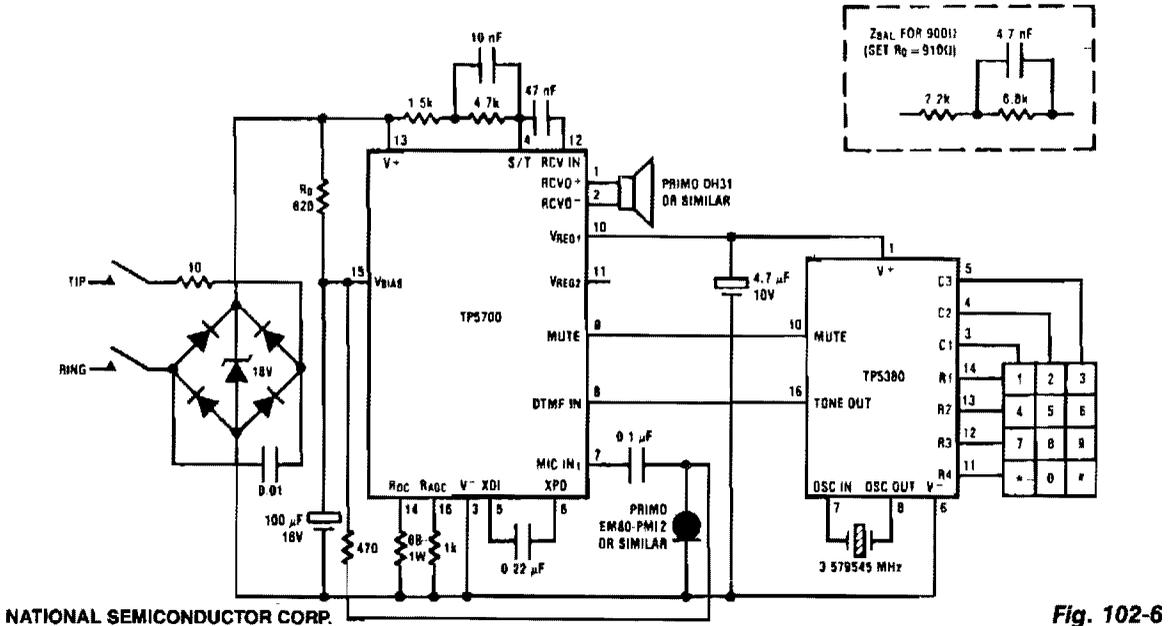

**Fig. 102-6**


This circuit shows the TP5700 directly interfacing to a low-voltage DTMF generator.  $V_{REG1}$  supplies the necessary 2-V minimum bias to enable the TP5380 to sense key closures and pull its mute output high.  $V_{REG1}$  then switches to a 3-V regulated output to sustain the tone dialer during tone generation. The TP5700 DTMF input incorporates the necessary load resistor to  $V-$  and provides gain, plus AGC action, to compensate for loop length. A muted tone level is heard in the receiver. For DTMF generators with a higher output level than the TP5380, a resistive potentiometer should be added to reduce the level at the speech circuit DTMF input.

## TELEPHONE REPEATER

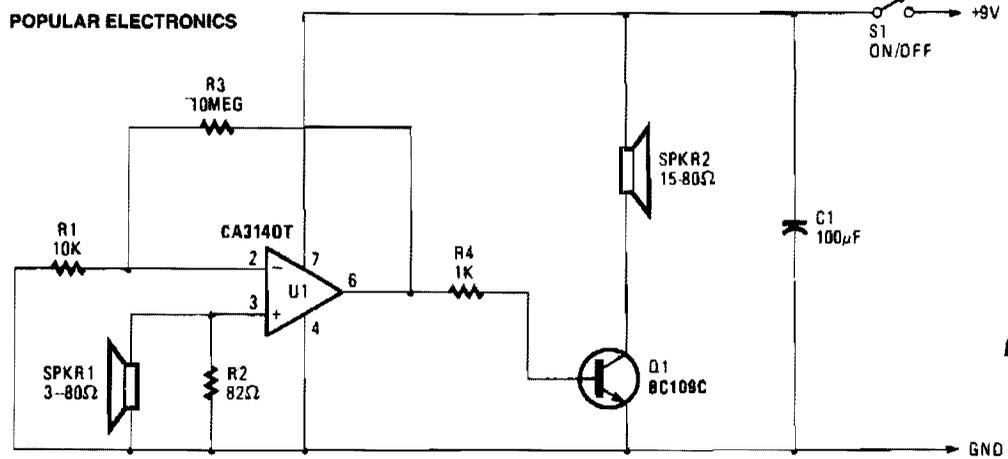

**Fig. 102-7**

## SPEAKERPHONE

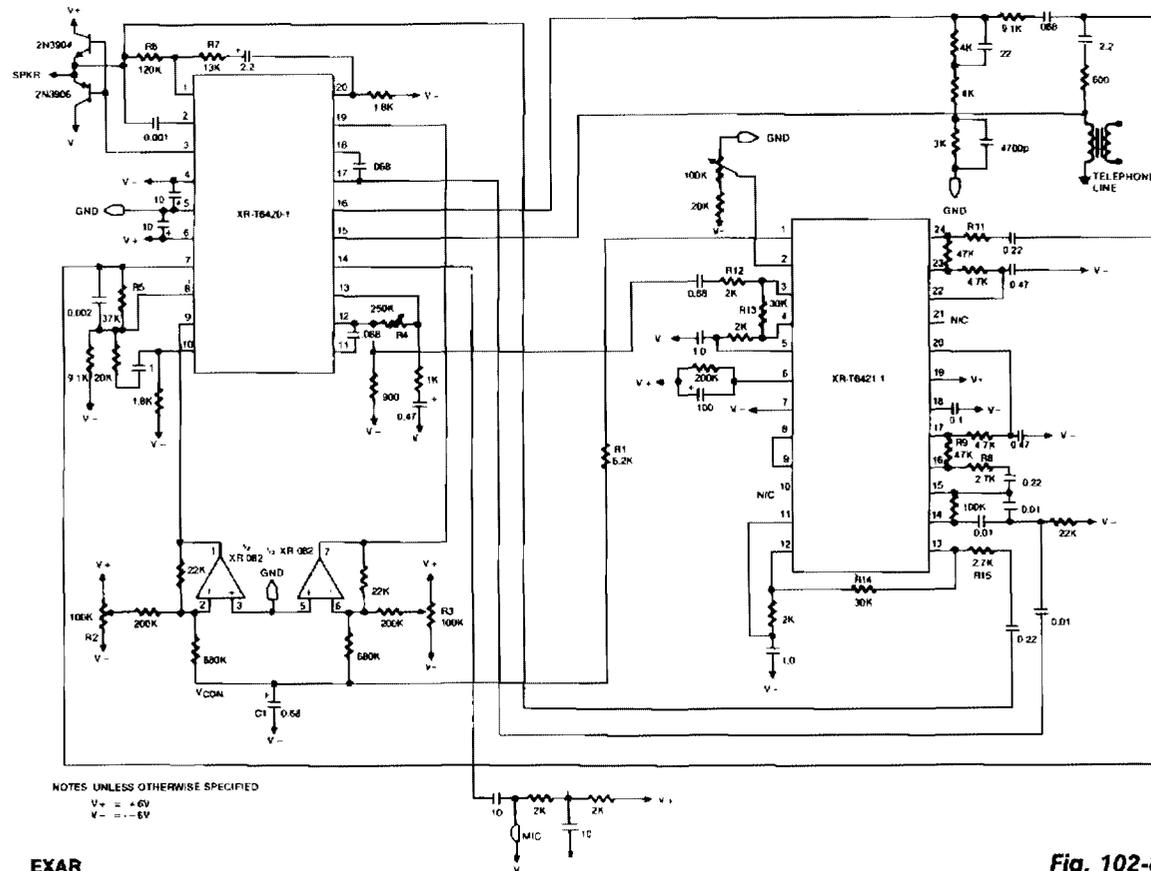

This circuit consists of two audio channels, a control circuit, and a hybrid interface circuit. The gain of each audio channel is controlled by the control circuitry, with the use of a voltage controlled amplifier (VCA). The inputs to the control circuit are obtained from each of the audio channels. The hybrid interface circuit performs three important functions. First, it couples the  $T_X$  channel signal to the telephone line. Second, it couples the signal on the telephone line to the  $R_X$  channels. And, finally, it cancels a majority of the  $T_X$  signal that can couple into the  $R_X$  channel. The amount of  $T_X$  signal that appears on the  $R_X$  channel is called sidetone.

## SERIES TELEPHONE CONNECTION


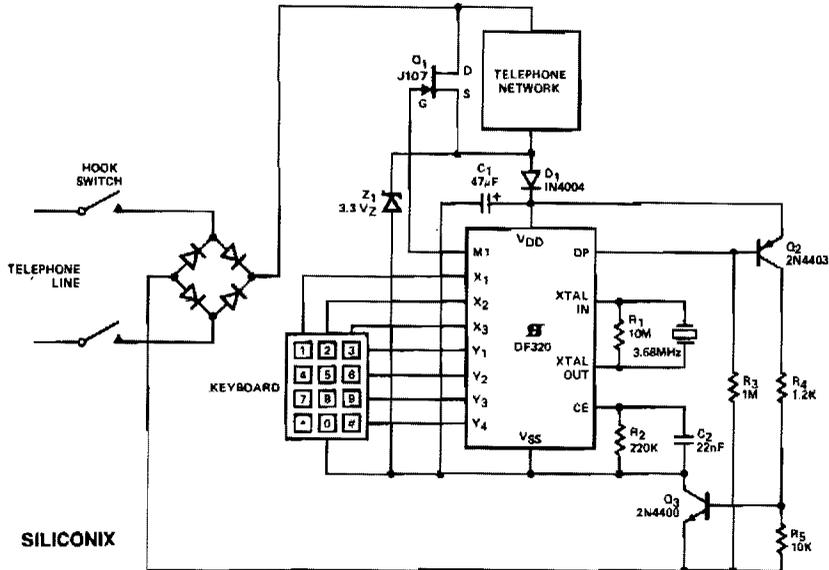


Fig. 102-9

Here is a simple method of series connection into the telephone set suitable for PABX or short line applications. When the telephone handset is lifted, C1 is charged via D1 to  $(V_{Z1} - 0.7)$  V and DF320 power on reset occurs. When the first keyed digit is recognized, M1 goes to logic 1, muting the telephone network by switching on the low on resistance JFET Q1, and maximizing the line-loop current for impulsing. Impulsing occurs through DP switching Q2, and hence Q3 turns off. Rapid discharge of C1 through Z1 is prevented during line break by blocking diode D1. When dialing is complete, the circuit returns to the static standby condition, and Q1 is switched off. The circuit reset, during a line interruption by the cradle switch, is for the parallel connection mode.

## SIMPLE TOUCHTONE™ GENERATOR

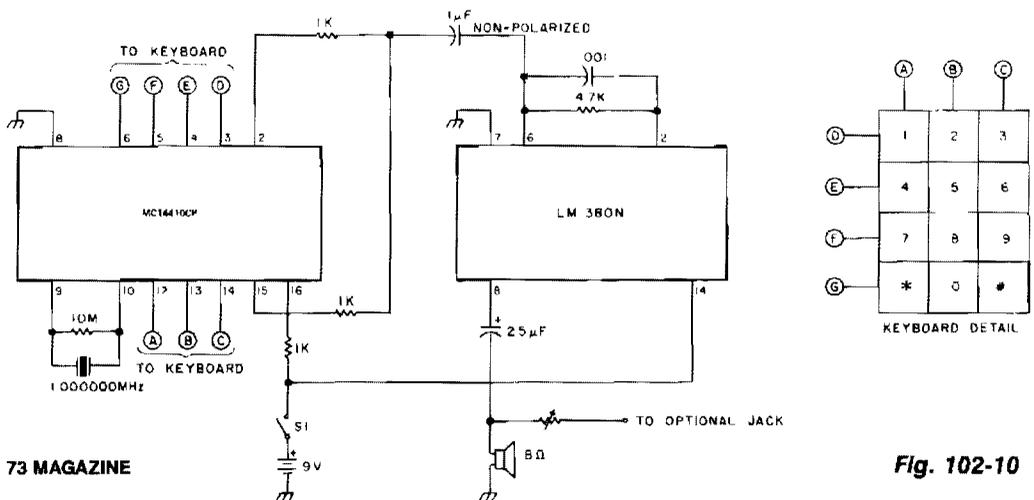


73 MAGAZINE

Fig. 102-10

## SIMPLE TOUCHTONE™ GENERATOR (Cont.)

The oscillator is a Motorola MC14410CP chip using a 1-MHz crystal. The chip generates both the high and low tones, feeding the energy to the amplifier through 1-K resistors and the 1- $\mu$ F capacitor. Values for the output resistors can vary from a few hundred  $\Omega$  to about 60 K $\Omega$ . The value of the resistor shunting the crystal can vary from about 3 to 15 M $\Omega$ . The amplifier consists of an LM-380N.

### PULSE-DIALING TELEPHONE

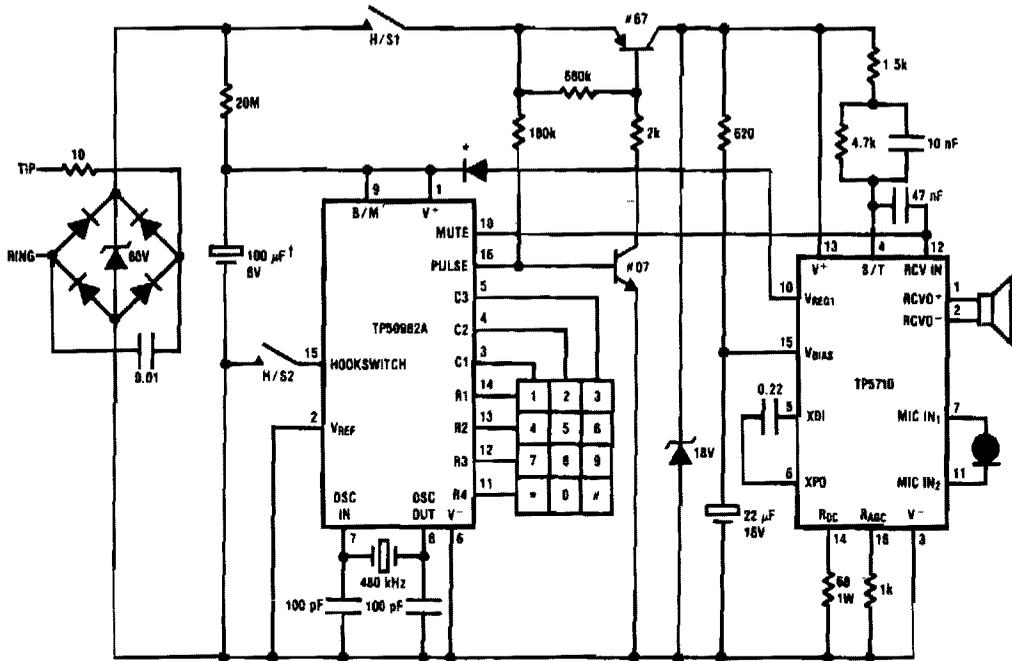

\* Select as necessary to suit mic sensitivity


† Low leakage type

NATIONAL SEMICONDUCTOR CORP.

Fig. 102-11

The TP5700 or TP5710 can reduce the number of components required to build a pulse-dialing telephone, as shown. The usual current source can be eliminated by using the  $V_{REG1}$  output to power a TP50982A low-voltage (1.7 V) pulse dialer via a blocking diode. A low forward-voltage drop diode such as a Schottky type is necessary because  $V_{REG1}$  is used in its nonregulated mode and its output voltage might fall to 2 V on a 20-mA loop. A 100- $\mu$ F decoupling capacitor is required to hold up the pulse dialer supply voltage during dialing. This capacitor will take about one second to charge up when the telephone is first connected to the line, but thereafter, the 20-M $\Omega$  resistor, required to retain the last-number dialed memory, will keep this capacitor charged. Partial muting is obtained by directly connecting the N-channel open-drain mute output of the pulse dialer to the RCV in pin on the speech circuit. A fully muted pulse dialer design requires the use of a shunt-mode dialer, such as the TP50981A or TP50985A.

## OPTICALLY INTERFACED RING DETECTOR

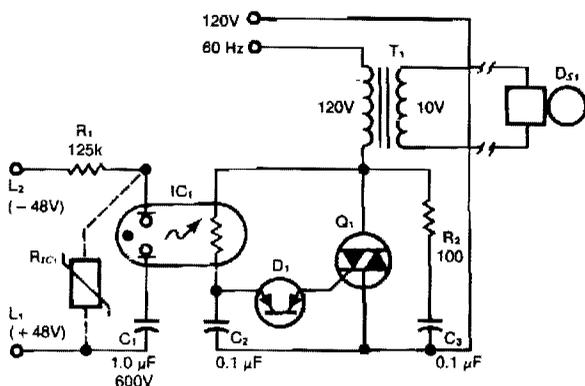


This ring detector, utilizing a neon-LDR (light-dependent resistor) optocoupler, simplifies interfacing with telephone lines.

EDN

Fig. 102-12

## PARALLEL TELEPHONE CONNECTION

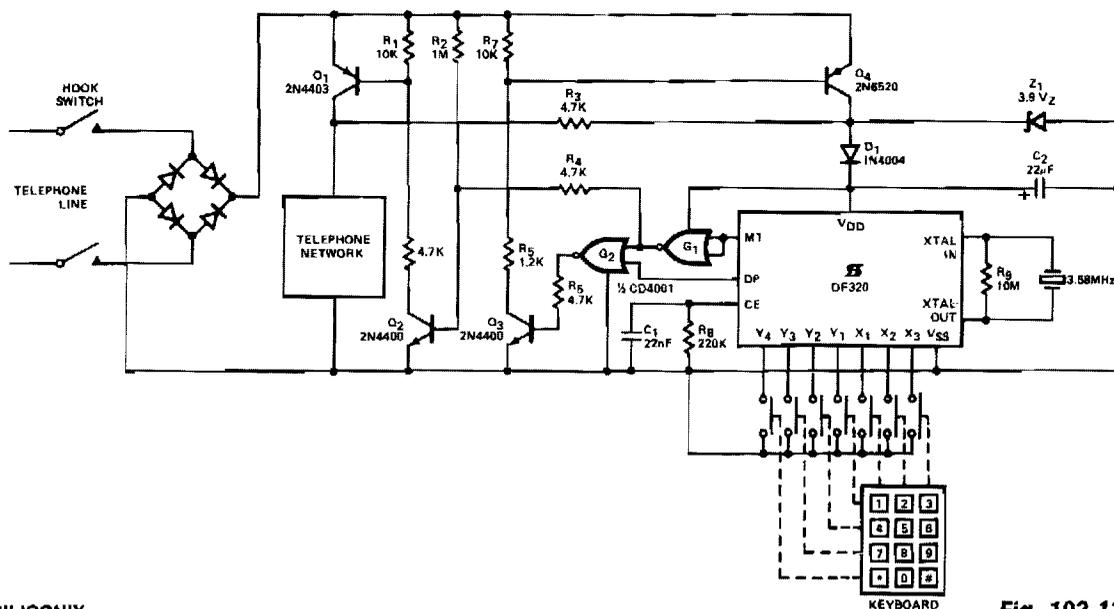

SILICONIX


Fig. 102-13

When the handset is lifted and power is applied to the circuit, Q2 is fed base current through R2, which in turn drives Q1. C2 is charged via R3 in series with D1 to  $(V_{Z1} - 0.7)$  V. When the minimum operating  $V_{DD}$  voltage is reached, power on reset occurs via the rc network of C1 and R8. Q2 is maintained in the on condition by G1, while Q3, and hence Q4, are held off by G2. The DF320 network appears in parallel with the telephone as an impedance more than 10 K $\Omega$  in the standby condition with the telephone

## PARALLEL TELEPHONE CONNECTION (Cont.)

network connected in circuit through Q1. On recognition of the first keyed digit, the DF320 clock is started. M1 then goes to logic 1 causing Q2 and Q1 to turn off, and Q3 and Q4 to turn on. Hence, the majority of the line loop current now flows through Q4 and Z1. When impulsing occurs, Q3 and Q4 are turned off by DP acting on G2. Line loop current is then reduced to approximately 50  $\mu\text{A}$  taken through R2, R4, and G2 in series. When dialing in, complete M1 goes to logic 0, causing the telephone network to be reconnected. The DF320 then returns to the static standby condition. If the line loop is interrupted by the cradle switch during dialing, impulsing will continue until C2 discharges to a voltage, such that R8 pulls CE to logic 0, causing the DF320 to reset. The diode bridge protects the network from line polarity reversal.

## ADD-ON TELEPHONE HOLD BUTTON

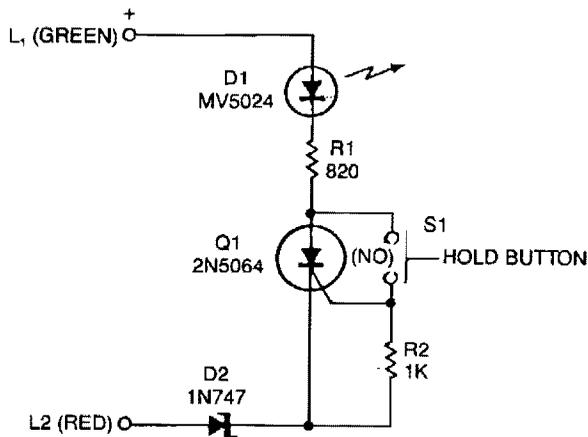

EDN

Fig. 102-14

A sensitive-gate SCR provides a line-holding current of 20 to 40 mA, depending on loop resistance. It also lights an LED to give the user a positive indication that the telephone line is on hold. The 20 to 40 mA should prove sufficient to hold the majority of lines, but it might require increasing—by decreasing the size of R1—in individual instances. When any receiver in the same loop is lifted, the low impedance of the off-hook telephone set shunts holding current away from the SCR, thereby releasing the line and extinguishing the LED. Zener diode D2 ensures that the line-holding current drops below the SCR's minimum conduction current. If the calling party tires of waiting on hold and hangs up, the release of the central-office relays from the calling side also releases the line from the hold mode.

## TELEPHONE HANDSET ENCODER

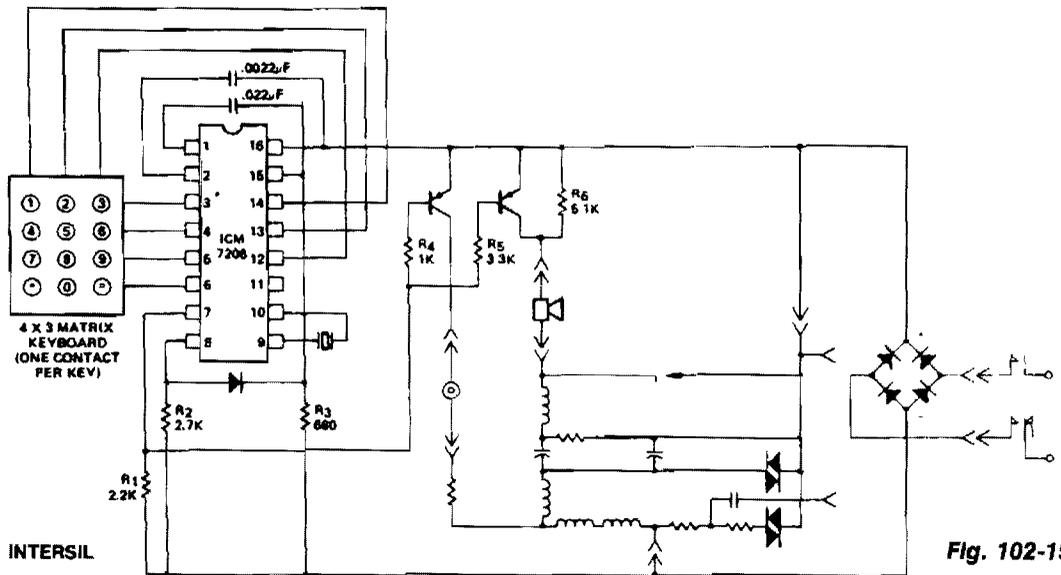


Fig. 102-15

This encoder uses a single contact per key keyboard and provides all other switching functions electronically. The diode connected between terminals 8 and 15 prevents the output from going more than 1 V negative with respect to the negative supply  $V_{SS}$ . The circuit operates over the supply voltage range from 3.5 V to 15 V on the device side of the bridge rectifier. Transients as high as 100 V will not cause system failure, although the encoder will not operate correctly under these conditions. Correct operation will resume immediately after the transient is removed. The output voltage of the synthesized sine wave is almost directly proportional to the supply voltage ( $V_{DD} - V_{SS}$ ) and will increase with the increase of supply voltage between terminals 8 and 16, after which the output voltage remains constant.

## DIAL PULSE INDICATOR


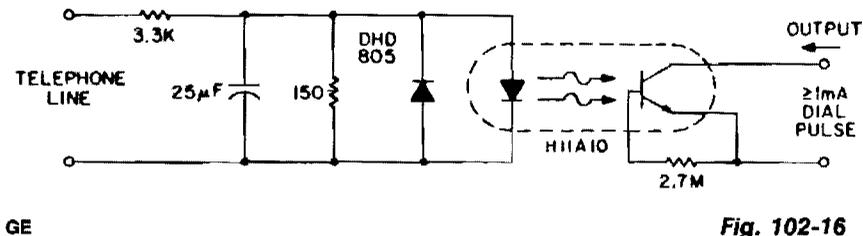


Fig. 102-16

This indicator senses the switching on and off of the 48-Vdc line voltage and transmits the pulses to logic circuitry. An H11A10 threshold coupler, with capacitor filtering, gives a simple circuit which can provide dial pulse indication, and yet reject high levels of induced 60-Hz noise. The DHD805 provides reverse bias protection for the LED during transient over-voltage situations. The capacitive filtering removes less than 10 ms of the leading edge of a 40-V dial pulse, while providing rejection of up to 25-V rms at 60 Hz.


## TELEPHONE SOUND LEVEL METER MONITOR

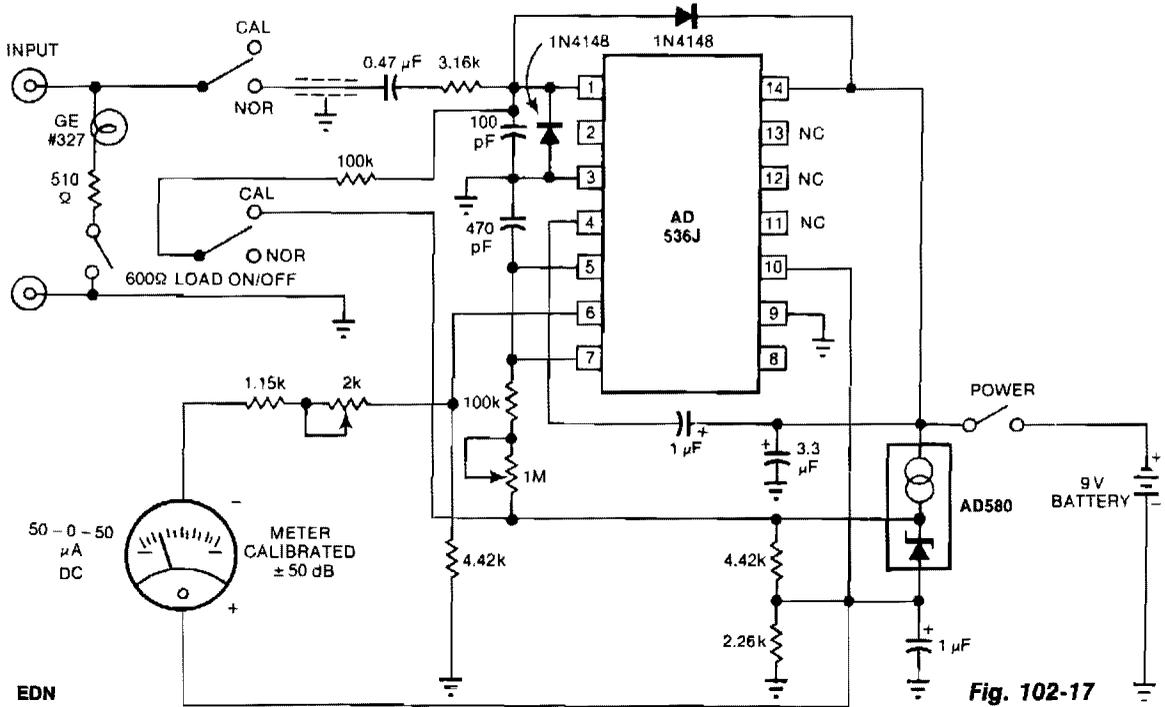

**Fig. 102-17**

The telephone-line decibel meter and line-voltage sensor shown lets you accurately monitor and adjust telephone sound levels. The 600-Ω resistor properly terminates the line. Power drain from the 9-V battery is 2 mA, and the meter provides ±30 dB range.

## REMOTE TELEPHONE RINGER

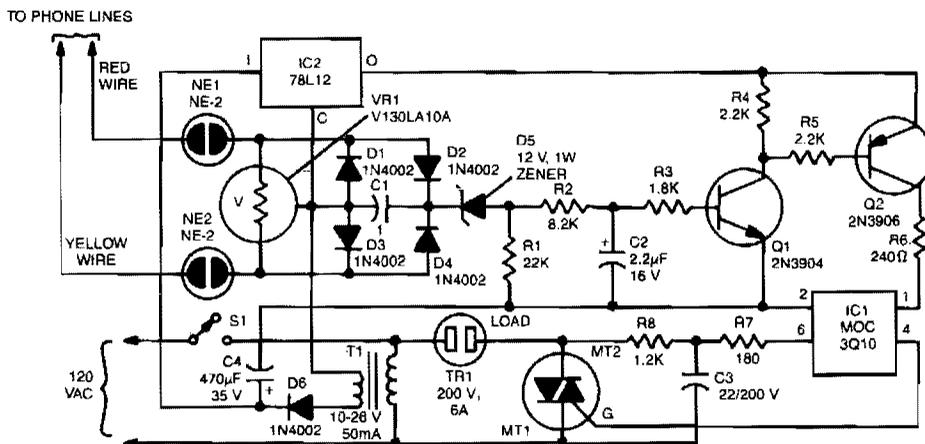


**Fig. 102-18**

Reprinted with permission of Radio-Electronics Magazine, October 1983. Copyright Gernsback Publications, Inc., 1983.

## REMOTE TELEPHONE RINGER (Cont.)

The two neon bulbs will light when more than 100 V is across the ringing circuit. The bulbs provide line isolation between the unit and the telephone line. Finally, they act as a voltage divider for the bridge rectifier made up of D1 through D4. That voltage divider creates a positive voltage that is then applied through D5, is filtered by R2, R3, and C2, and causes Q1 and Q2 to conduct. When that happens, triac TR1 is fired through the optical coupler IC1; this turns on the triac, which applies 110 Vac to the load.

## TELEPHONE SPEECH ACTIVITY DETECTOR

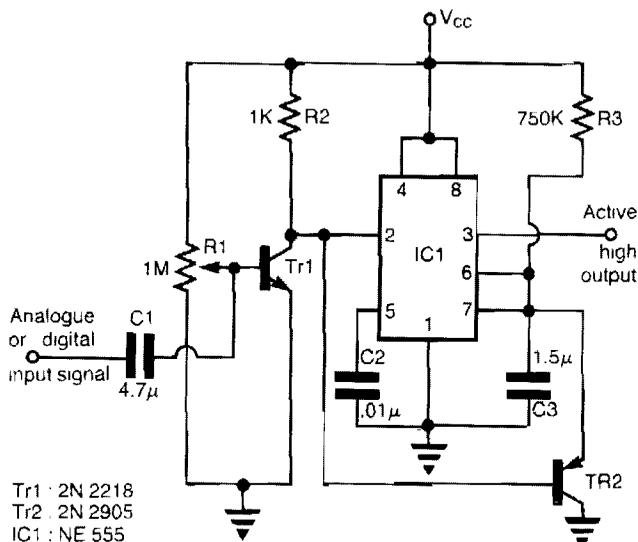

Tr1 : 2N 2218  
Tr2 : 2N 2905  
IC1 : NE 555

ELECTRONIC ENGINEERING

Fig. 102-19

This circuit can be used in telephone lines for speech activity detection purposes. This detection is very useful in the case of half-duplex conversation between two stations—in the case of simultaneous transmission of voice and data over the same pair of cables by the method of interspersed data on voice traffic, and also in echo suppressor devices. The circuit consists of a class-A amplifier to amplify the weak analog signals (25–400 mV). The IC1 which follows, is connected as a retriggerable monostable multivibrator with the TR2 discharging the timing capacitor C3, if the pulse train reaches the trigger input 2 of IC1 with period less than the time:  $T_{HIGH} = 1.1 R3C3$ . The output 3 of IC1 is active on when an analog or digital signal is presented at the output, and it drops to a low level,  $T_{HIGH}$ , seconds after the input signal has ceased to exist.

## DUPLEX LINE AMPLIFIER


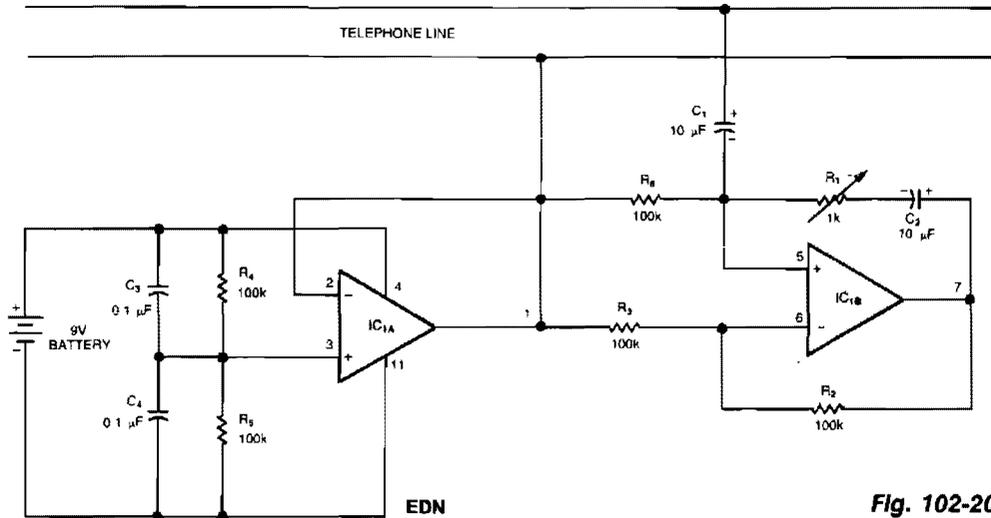


Fig. 102-20

This circuit is a bidirectional amplifier that can amplify both signals of a duplex telephone conversation. It uses the principle of negative resistance. Obviously, such an amplifier could easily be unstable; however, you can adjust R1 for maximum amplification and the circuit will remain stable. The LM324 op amps can be replaced with op amps that would distort less, such as the LM1558, LF412, LF353, or LF442.

## PHONE RECORDER

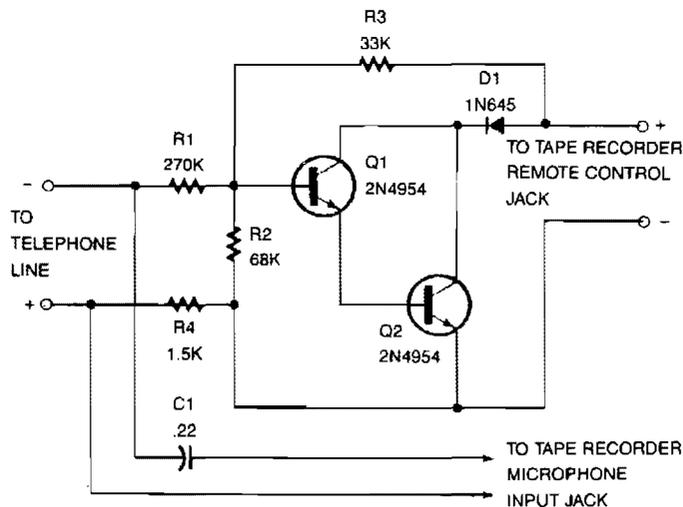


HANDS-ON ELECTRONICS

Fig. 102-21

## PHONE RECORDER (Cont.)

This recorder can be connected to the telephone lines just about any place, and no external power source is needed. The tape recorder's switch terminals are applied to a pair of transistors, connected as Darlingtontons, that are used to turn the recorder on and off. When the telephone is off-hook there's usually about 50 Vdc across the phone that's divided over R1, R2, and R4, so that Q1's base is negative enough to keep the recorder off. Pick up the receiver, and the voltage drops to 5 V. That leaves not quite-enough voltage on Q1's base to keep that transistor at cutoff, so the recorder begins. Remember to keep your recorder's switch in the on position, and depending on how many people use the telephone, remember to rewind or change tapes occasionally!

## LINE-ACTIVATED SOLID-STATE SWITCH

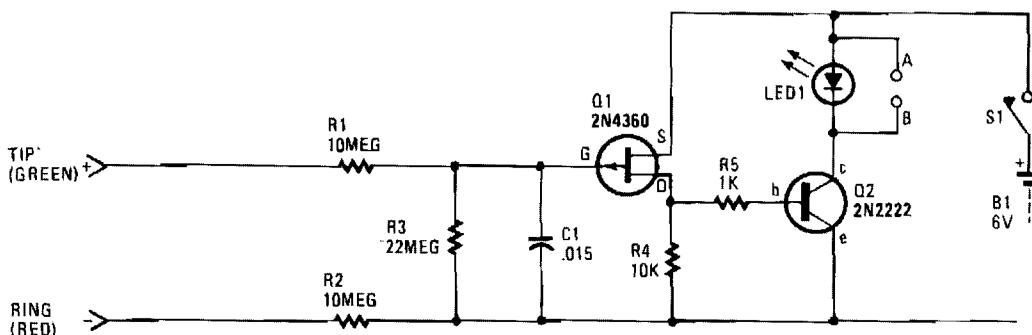

HANDS-ON ELECTRONICS


Fig. 102-22

Each and every time a phone on the same line or calling number is taken off-hook, the circuit will be activated to control an external electronic circuit. If several extension telephones are used on one phone line, the circuit can be useful as a *busy* indicator. LED1 contains a special flashing red LED that makes an excellent indicator for a *busy* circuit condition.

The solid-state switch can be used for several other phone-activated applications, such as automatically turning on a cassette recorder, starting a phone-use timer or counter, etc. A small relay can be connected at points A and B, in place of LED1, to control external circuits. A 117-Vac-to-6-Vdc plug-in power supply can be substituted for the battery to keep the operating cost at a minimum.

The 48-Vdc, on-hook, phone-line voltage keeps Q1 in the cut-off condition, allowing no current to flow through resistor R4, hence Q2 remains off. Resistors R1 and R2 keep the solid-state switch circuit from causing any problems with the telephone's central-office equipment. When a phone is taken off-hook, the line voltage (tip to ring) drops to 10 V or less, which forces Q1 to turn on; this, in turn, causes Q2 to trigger LED1, or a relay which might be used in lieu of LED1.

## CASSETTE INTERFACE

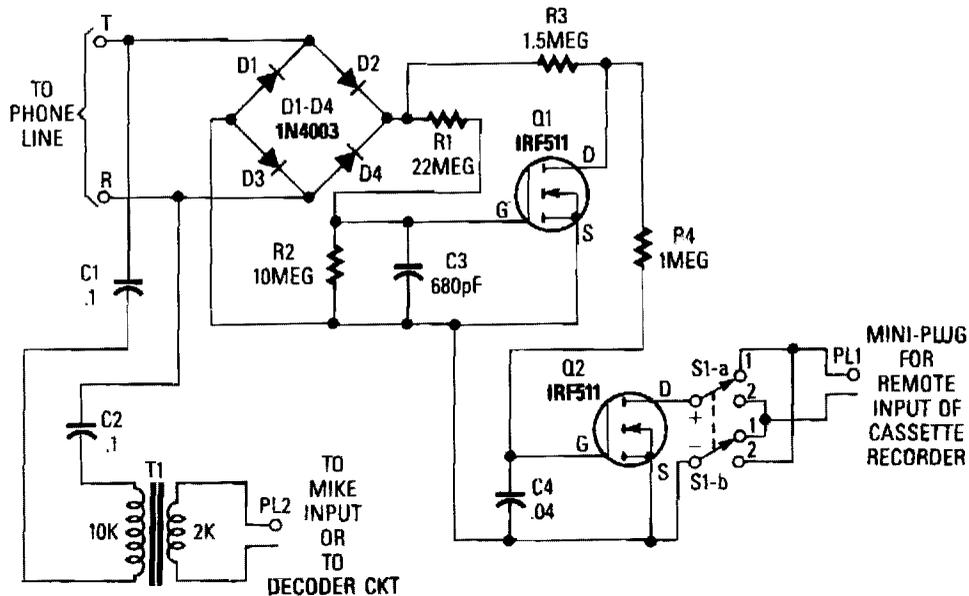

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 102-23





Q1 and Q2 are used to form the basis of an interface circuit for attaching a cassette recorder to the phone line. The circuit does not require a power supply because operating power is drawn from the telephone line itself. The incoming signal is fed across a bridge-rectifier circuit, consisting of diodes D1 through D4.

When the phone is on hook, the voltage at the output of the bridge at the R1/R3 junction is near 48 V. That voltage is fed across a voltage divider consisting of R1 and R2. The voltage at the junction formed by R1 and R2 is fed to the gate of Q1, turning it on. That pulls the drain of Q1 low. Since the gate of Q2 is connected to the drain of Q1, the bias applied to the gate of Q2 is low, holding it in the OFF state.

When the answering machine responds to a call or a phone is taken off hook, the voltage across the phone lines drops below 10 V, causing Q1 to turn off. At that point, the voltage at Q1's drain rises, turning Q2 on. The remote input of the cassette is connected to Q2's drain and source through S1, and a miniature plug is connected to the remote input jack.

Switch S1 must be in a position so that the positive lead of the recorder's remote input connects, through switch position 1, to Q2's drain and the negative input to Q2's source. Switch S1 provides a convenient way to reverse the circuit's trigger output without having to unsolder and resolder leads. The phone's audio is coupled through C1, C2, and T1 to the microphone input of the cassette recorder.

# RING DETECTOR

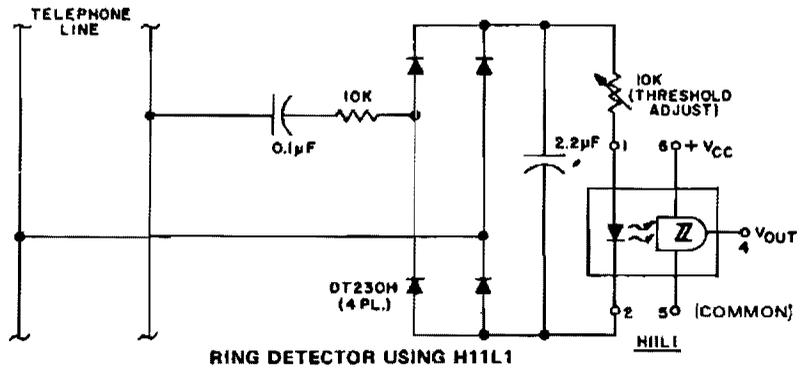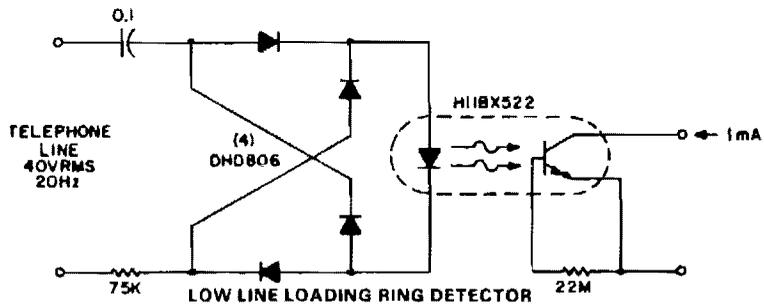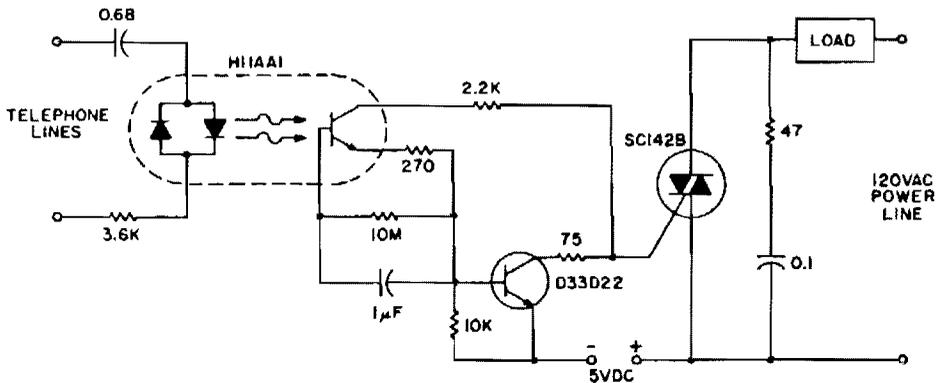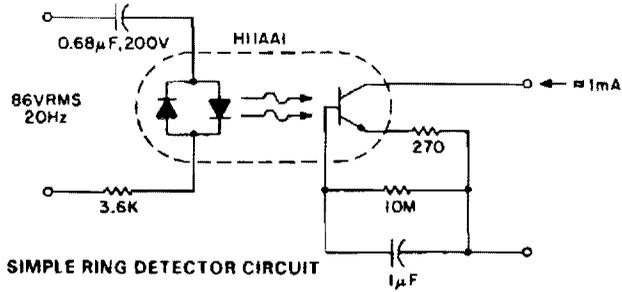

GE


Fig. 102-24

## RING DETECTOR (Cont.)

This circuit detects the 20 Hz,  $\approx$  86-V rms ring signal on telephone lines and initiates action in an electrically isolated circuit. Typical applications would include automatic answering equipment, and interconnect/interface and key systems. The circuits illustrated are *bare bones* circuits designed to illustrate concepts. They might not eliminate the ac/dc ring differentiation, 60-Hz noise rejection, dial tap rejection, and other effects that must be considered in field application. The first ring detector is the simplest and provides about 1-mA signal for a 7-mA line loading for  $1/10$  sec after the start of the ring signal. The time delay capacitor provides a degree of dial tap and click suppression, as well as filtering out the zero crossing of the 20-Hz wave. This circuit provides the basis for a simple example, a ring extender that operates lamps and buzzers from the 120-V, 60-Hz power line, while maintaining positive isolation between the telephone line and the power line. Use of the isolated tab triac simplifies heat sinking by removing the constraint of isolating the triac heatsink from the chassis. Lower line current loading is required in many ring detector applications. This can be provided by using the H11BX522 photo-Darlington optocoupler, which is specified to provide a 1-mA output from a 0.5-mA input through the  $-25^{\circ}\text{C}$  to  $+50^{\circ}\text{C}$  temperature range.

The next circuit allows ring detection down to a 40-V rms ring signal while providing 60-Hz rejection to about 20-V rms. Zero-crossing filtering can be accomplished either at the input bridge rectifier or at the output. Dependable ring detection demands that the circuit responds only to ring signals, rejecting spurious noise of similar amplitude, such as dialing transients. The configuration shown relies on the fact that ring signals are composed of continuous frequency bursts, whereas dialing transients are much lower in repetition rate. The dc bridge-filter combination at the H11L input has a time constant; it cannot react to widely spaced dialing transients, but will detect the presence of relatively long duration bursts, causing the H11L to activate the downstream interconnect circuits at a precisely defined threshold.

## WIRELESS TELEPHONE EAVESDROPPER

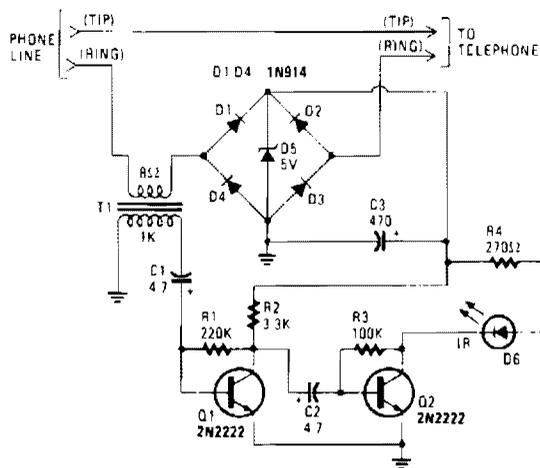


HANDS-ON ELECTRONICS

Fig. 102-25

The IR transmitter connects to a telephone circuit, and transmits both sides of all telephone conversations to any line-of-sight location, within 40 feet. No power is taken from the central office, as long as all phones remain on-hook. The current flows through the phone and back to the central office, thereby keying their equipment. We tap into the telephone line by connecting the IR transmitter circuit in series with either the tip or ring. When the telephone is off-hook, current will flow through the diode bridge polarity protector and supply the power for the IR transmitter. The phone's audio information is taken off the line by transformer T1. The 1000- $\Omega$  winding of the transformer connects to a two-stage transistor audio amplifier/modulator. A 2000- $\Omega$  potentiometer could be added to the input of the two-stage amplifier to control the modulation level, and another potentiometer could be added in place of R3 to adjust the IR's idle current.

## TELEPHONE AMPLIFIER

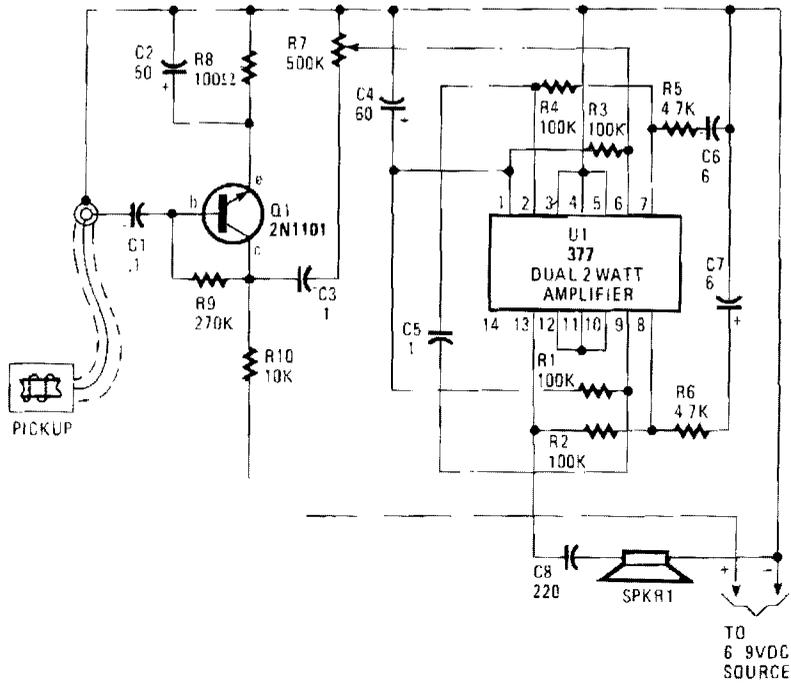


TAB BOOKS

Fig. 102-26

Audio from the telephone is inductively coupled to the base of Q1, which is used as a preamp. The preamp provides a gain of about 75 dB, to boost the input signal from about 4 mV to about 300 mV pk-pk. If you use a higher gain transistor, increase the value of R9 to produce a Q point, measured from minus to the collector of Q1, of one-half the supply voltage. The Q1 output signal is coupled through C3 to R7, which serves as a volume or drive-level control, to U1, a dual, 2 w amplifier connected in cascade. Pins 1 through 7 serve as a driver for the final amplifier, pins 8 through 13. Compensation and balance is accomplished by components R1 through R6 and C4, C6, and C7. Pins 3 through 5, and 10 through 12 should be tied to the negative supply rail.

---

## TELEPHONE TAP

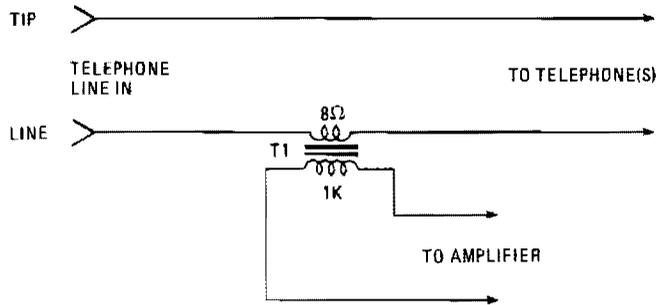

HANDS-ON ELECTRONICS

*Fig. 102-27*

Amplify or record a telephone call with the simple circuit shown. The 8-Ω secondary winding of a miniature transistor output transformer is connected in series with either of the telephone lines. The 1000-Ω primary winding can feed either a cassette recorder or an audio amplifier.

---

# 103


## Temperature Controls

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Zero-Point Switching Temperature Control  
Servo-Sensed Heater Protector  
Temperature Controller  
Proportional Temperature Controller  
Piezoelectric Fan-Based Temperature Controller  
Electronic Heat Sniffer


## ZERO-POINT SWITCHING TEMPERATURE CONTROL

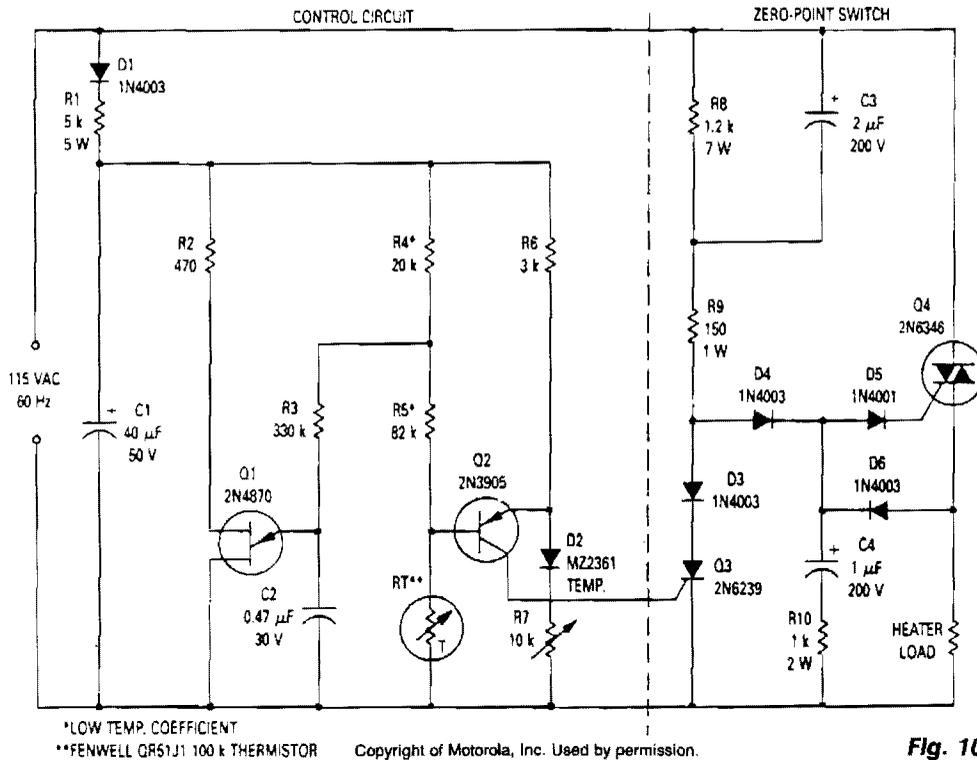

**Fig. 103-1**

This modulated triac zero-point switching circuit controls heater loads operating from 115 Vac. Circuit operation is best described by splitting the circuit into two parts. The circuit at right is the zero-point switch; to the left is the proportional control for the zero-point switch.

## SERVO-SENSED HEATER PROTECTOR

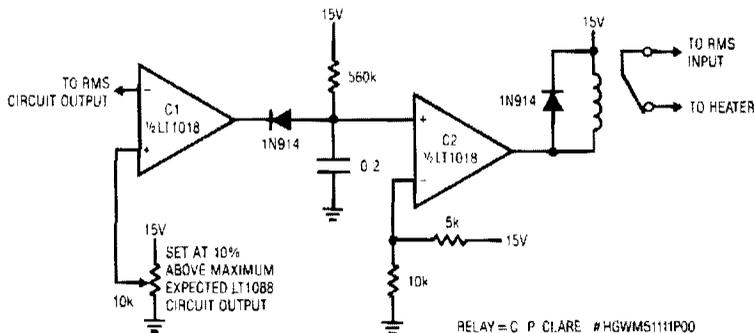


LINEAR TECHNOLOGY TECH.

**Fig. 103-2**



## PROPORTIONAL TEMPERATURE CONTROLLER

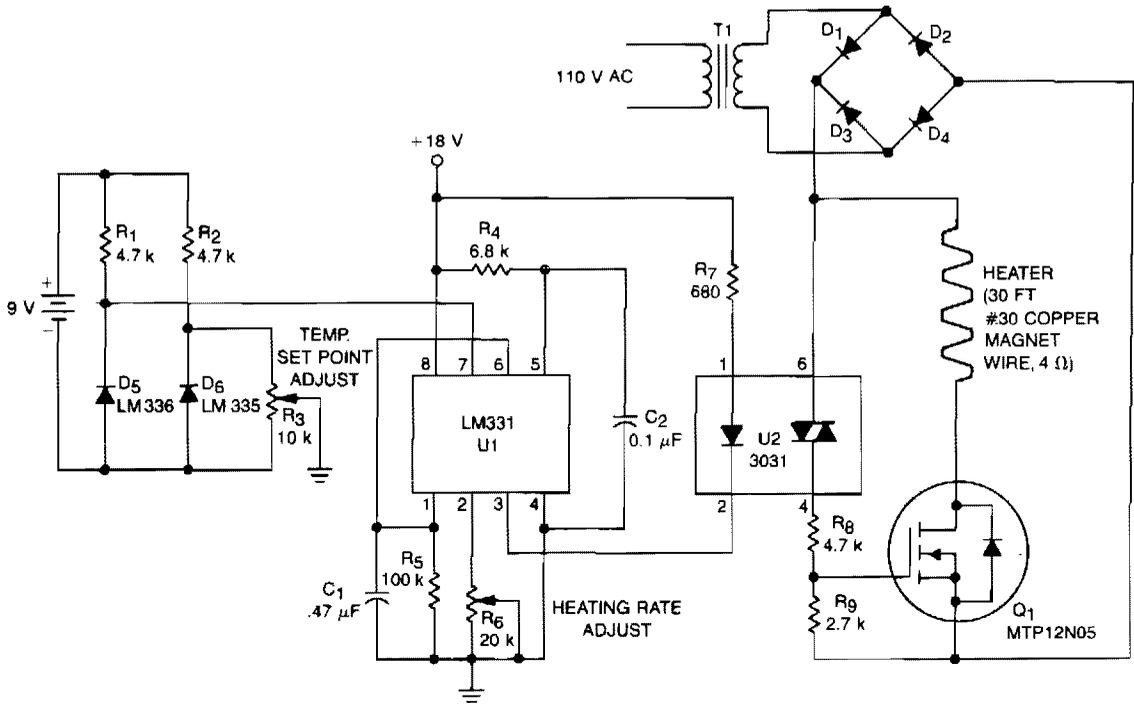


Copyright of Motorola, Inc. Used by permission.

**Fig. 103-4**

This temperature controller operates as a *pulse snatching* device, which allows it to run at its own speed and turn on at the zero crossing of the line frequency. Zero crossing turn-on reduces the generation of line noise transients. TMOS Power FET, Q1, is used to turn on a heater.


Temperature sensor D6 provides a dc voltage proportional to temperature that is applied to voltage-to-frequency converter U1. Output from U1 is a pulse train proportional to temperature offset that is applied to the input of triac optoisolator U2. The anode supply for the triac is a 28 V pk-pk, full-wave rectified sine wave. The optoisolator ORs the pulse train from U1 with the zero crossing of U2's anode supply, supplying a gate turn on signal for Q1. Therefore, TMOS power FET Q1 can only turn the heater on at the zero crossing of the applied sine wave. The maximum temperature, limited by the sensor and the insulation of the wire, is 130°C for the components shown.
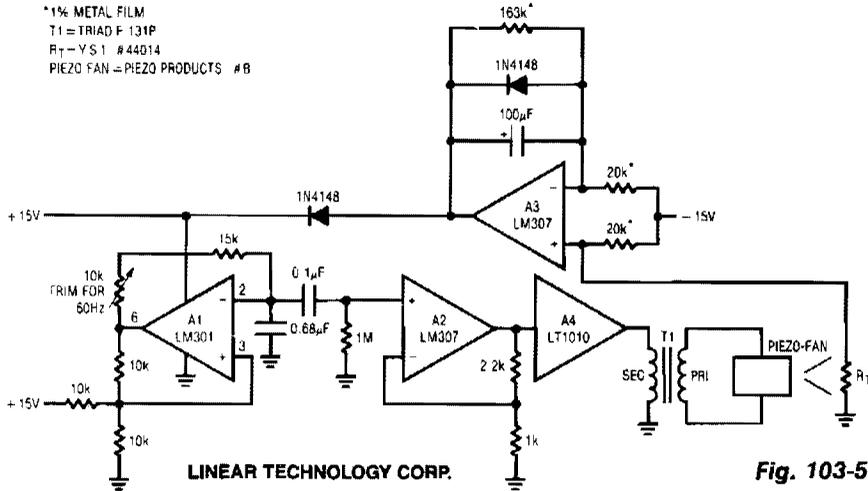
## PIEZOELECTRIC FAN-BASED TEMPERATURE CONTROLLER



The fan employed is one of the new electrostatic type which is very reliable, because it contains no wearing parts. These devices require high-voltage drive. When power is applied, the thermistor, located in the fan's exhaust stream, is at a high value. This value unbalances the A3 amplifier driven bridge. A1 receives no power and the fan does not run. As the instrument enclosure warms, the thermistor value decreases until A3 begins to oscillate. A2 provides isolation and gain, and A4 drives the transformer to generate high voltage for the fan. In this fashion, the loop acts to maintain a stable instrument temperature by controlling the fan's exhaust rate. The 100- $\mu$ F time constant across the error amplifier pins is typical of such configurations. Fast time constants will produce audibly annoying *hunting* in the servo. Optimal values for this time constant and gain depend upon the thermal and airflow characteristics of the enclosure being controlled.

## ELECTRONIC HEAT SNIFFER

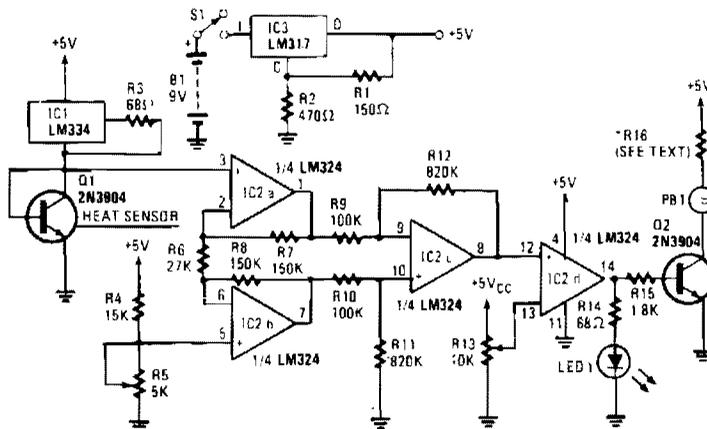

Reprinted with permission from Radio-Electronics Magazine, May 1985. Copyright Gernsback Publications, Inc., 1985.

Fig. 103-6

## ELECTRONIC HEAT SNIFFER (Cont.)

Sensing element Q1 is a 2N3904 general-purpose npn transistor, although any general-purpose npn unit in a TO-92 style case will do. IC1, an LM334, supplies Q1 with a constant current that is independent of temperature. An LM324 quad op amp, IC2, forms a high input-impedance differential amplifier (IC2a, IC2b, and IC2c) with a gain of about 99. IC2d is used as a voltage comparator. When Q1 senses a rise or fall in temperature, the base-to-emitter voltage decreases. That decrease in voltage causes the input to IC2a at pin 3 to deviate from the reference voltage that's fed to IC2b at pin 5, which is set by potentiometers R5. The difference between the input and the reference is amplified by IC2c. That amplified voltage is fed to IC2d where it is compared to a control voltage set by potentiometer R13. The setting of R13 determines the threshold and is set at a point that's equal to the ambient temperature. The output of IC2d at pin 14 is fed to the base of transistor Q2. When the output of IC2d is high, LED1 lights and Q2 turns on. With Q2 turned on, a ground path through the transistor is provided for buzzer PB1.

The circuit can be built on perforated construction board using point-to-point wiring. All components, except Q1, are mounted on the board. Transistor Q1 is mounted at the tip of the heat-sensing probe.

---

# 104


## Temperature Sensors

---


The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Thermocouple Multiplex System  
0 – 63°C Temperature Sensor  
Isolated Temperature Sensor

## THERMOCOUPLE MULTIPLEX SYSTEM

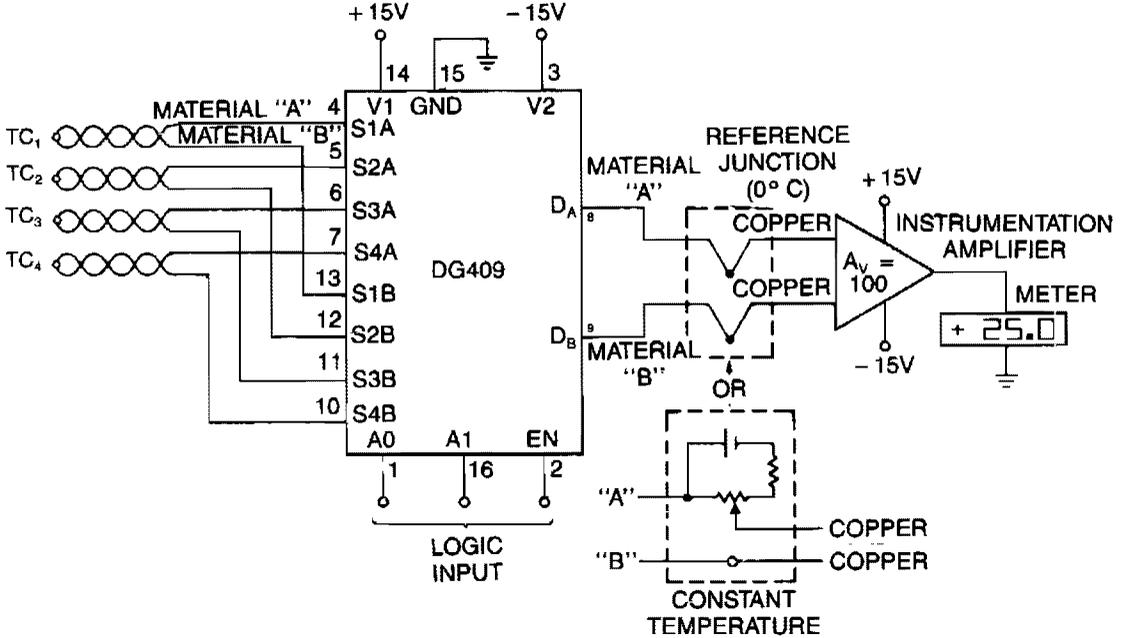

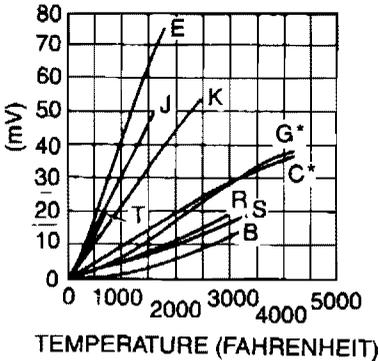Output Voltage vs. Temperature of Several Common Thermocouples



### ANSI SYMBOL

- T Copper vs Constantan
- E Chromel vs Constantan
- J Iron vs Constantan
- K Chromel vs Alumel
- G\* Tungsten vs Tungsten 26% Rhenium
- C\* Tungsten 5% Rhenium vs Tungsten 26% Rhenium
- R Platinum vs Platinum 13% Rhodium
- S Platinum vs Platinum 10% Rhodium
- B Platinum 6% Rhodium vs Platinum 30% Rhodium

\*Not ANSI Symbol

Used with permission of Omega Engineering, Inc., Stamford, Conn., 06907

SILICONIX

Fig. 104-1

To decouple the sensors from the meter amplifier, either a reference junction at 0°C or a bucking voltage set at room temperature may be used. The latter method is simpler, but is sensitive to changes in ambient temperature. The table above shows the output voltage vs temperature of several common types of thermocouples.



# 105


## Temperature-to-Time Converters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Two Simple Temperature-to-Time Converters
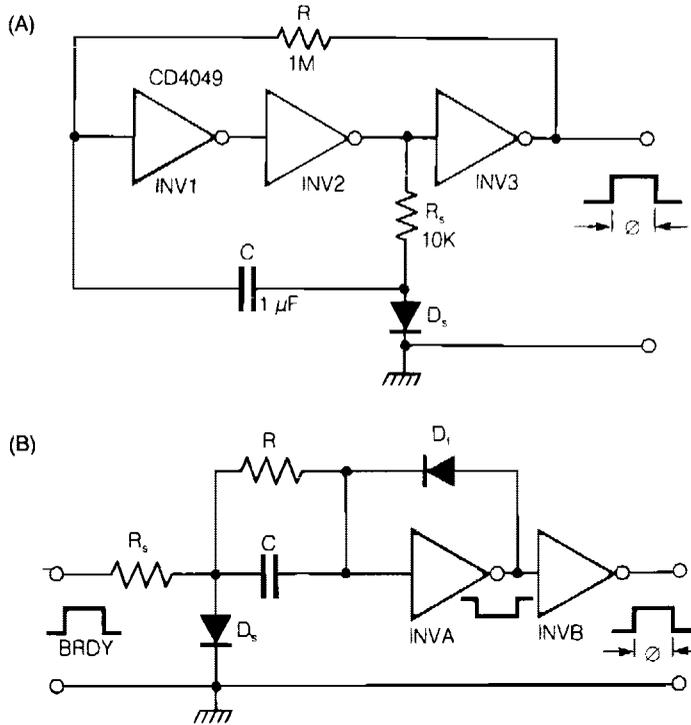
## TWO SIMPLE TEMPERATURE-TO-TIME CONVERTERS



ELECTRONIC ENGINEERING

Fig. 105-1

Both of these converters use CMOS inverters. Figure 105-1A shows a free-running circuit having both the pulse duration and pulse pause dependent on temperature of the diode  $D_s$ . It can be used where a synchronization between the converter and something else is not required.

Figure 105-1B shows a one shot circuit that produces a pulse with its duration dependent of temperature of diode  $D_s$ . The additional diode  $D_f$  should have inverse current low enough to not influence the discharging process in the network  $rc$  when the INVA output is low. A silicon component or a GaAsP LED can be used.

The converter is intended for a digital system producing a RADY pulse which disappears after the conversion process is ended. The pulse duration is approximately:

$$= 2RC \frac{V_D}{V_{DD}}$$

where  $V_D$  is the sensor diode forward voltage and  $V_{DD}$  is the supply voltage of the CMOS chip.

Resistance  $R$  must be much higher than  $R_s$ . A  $0.1\text{-}\mu\text{F}$  capacitor can be applied in parallel with  $D_s$ , if necessary, to repulse stray pickup and noise in a long cable. The circuits described can be used with a temperature sensitive resistor instead of the diode  $D_s$ .

# 106


## Tesla Coils

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Simple Tesla Coil  
Tesla Coil

## SIMPLE TESLA COIL

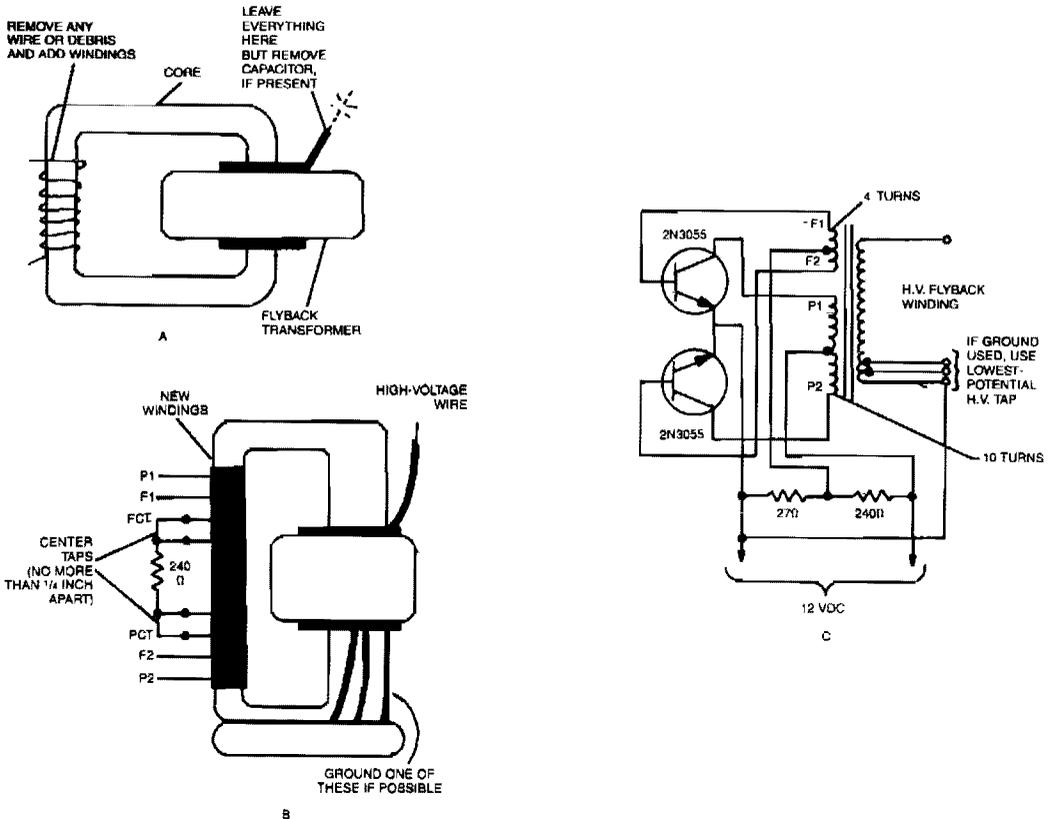

GERNSBACK PUBLICATIONS INC.

Fig. 106-1

The Tesla coil described here can generate 25,000 V. So, even though the output current is low, be **very careful!** The main component is a flyback transformer from a discarded TV.


A new primary winding is needed. Begin by winding 5 turns of #18 wire on the core. Then, twist a loop in the wire, and finish by winding five more turns. Wrap with electrical tape, but leave the loop exposed.

A four-turn winding must be wound over the ten-turn winding that you've just finished. That is done the same way. First wind two turns of # 18 wire, then make a loop, and finish by winding two more turns. Again, wrap the new winding with electrical tape, leaving the loop exposed.

When the windings are finished, the two loops shouldn't be more than 1/4-inch apart, but take care that they do not touch. Connect a 240-Ω resistor between the two loops. The modified transformer now should look like the one shown. Connect the transformer as shown. The 27-Ω resistor and two transistors should be mounted on a heatsink and must be insulated from it.

The output of the high-voltage winding should begin to oscillate as soon as the circuit is connected to a 12-Vdc power supply. If it does not, reverse the connections to the base leads of the transistors. In normal operation, you should be able to draw 1-inch sparks from the high-voltage lead using an insulated screwdriver.

## TESLA COIL

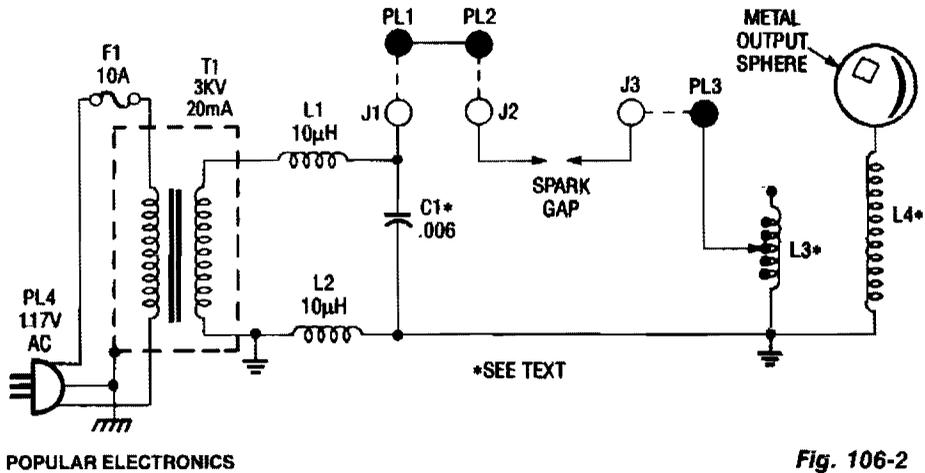

POPULAR ELECTRONICS

Fig. 106-2

Power is fed to transformer T1, a small neon-sign transformer, which steps the voltage up to about 3000 Vac. The stepped-up output of T1 is fed through L1 and L2 and across C1, causing the capacitor to charge until enough power is stored in the unit to produce an arc across the spark gap. The spark gap, which momentarily connects C1 and L3 in parallel, determines the amount of current transferred between C1 and L3.

The arcing across the spark gap sends a series of high-voltage pulses through L3, giving a sort of oscillated effect. The energy fed through L3 is transferred to L4 via the magnetic coupling between the two coils. Because of the turn ratio that exists between L3 and L4, an even higher voltage is produced across L4. Coil L4 steps up the voltage, which collects on the top-capacitance sphere. There, it causes an avalanche breakdown of the surrounding air, giving off a luminous discharge.

The rotary spark gap is a simple add-on circuit for the Tesla Coil, consisting of a variable dc power supply and a small, 5000-rpm, dc motor. The circuit allows you to vary the output of the Tesla coil by adjusting the rotating speed of the motor. A rotary gap is far more efficient than a stationary gap, because the stationary gap could cut-out and require readjustment.

# 107

## Thermometer Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Differential Thermometer  
Temperature-Reporting Digital Thermometer  
Electronic Thermometer  
Temperature Measuring Add-On for DMM  
Digital Voltmeter


Implantable Ingestible Electronic  
Thermometer  
Simple Linear Thermometer  
Thermometer Adapter



## TEMPERATURE-REPORTING DIGITAL THERMOMETER (Cont.)

The ROMs or PROMs must have the correct code for converting the data from the NE5037—used as address for the ROMs or PROMs—to the appropriate segment driver codes. The displayed amount could easily be converted to degrees Fahrenheit, °F, by the controller of (0 – 63° temperature sensor) or through the (P) ROMs. When doing this, a third (hundreds) digit (P)ROM and display will be needed for displaying temperatures above 99°F. An expensive clock can be made from NAND gates or inverters as shown.

### ELECTRONIC THERMOMETER

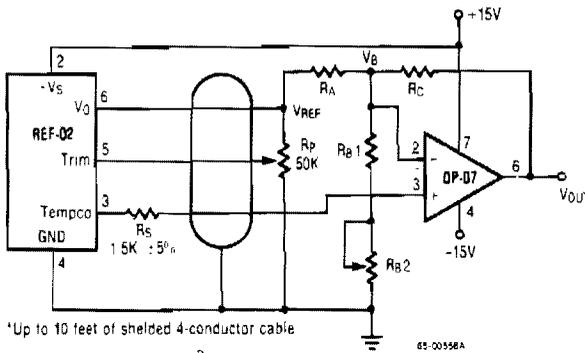

TCVOUT Slope(s)	Resistor Values		
	10mV/°C	100mV/°C	10mV/°F
Temperature Range	-55°C to +125°C	-55°C to +125°C	-65°F to +257°F
Output Voltage Range	-0.55V to +1.25V	-5.5V to -12.5V	-0.67V to +2.57V
Zero Scale	0V at 0°C	0V at 0°C	0V at 0°F
RA (±1% Resistor)	9.09KΩ	15KΩ	8.25KΩ
RB1 (±1% Resistor)	1.5KΩ	1.82KΩ	1.0KΩ
RB2 (Potentiometer)	200Ω	500Ω	200Ω
RC (±1% Resistor)	5.11KΩ	84.5KΩ	7.5KΩ

**Fig. 107-3**

\*Up to 10 feet of shielded 4-conductor cable

$$T_C V_{OUT} = (21 \text{ mV}/^\circ\text{C}) \left( 1 - \frac{R_C}{R_B} \right)$$

$$V_0 = \left( 4 \frac{R_C}{R_A} - \frac{R_C}{R_B} \right) V_{TEMPCO} - \left( \frac{R_C}{R_A} \right) (10 \text{ V})$$


Reprinted with permission from Raytheon Co., Semiconductor Division.

This circuit uses the +5 V reference output and the op amp to level shift and amplify the 2.1 mV/°C Tempco output into a voltage signal dependent on the ambient temperature. Different scaling can be obtained by selecting appropriate resistors from the table giving output slopes calibrated in degrees Celsius or degrees Fahrenheit. To calibrate, first measure the voltage on the Tempco pin,  $V_{TEMPCO}$ , and the ambient room temperature,  $T_A$  in °C. Put those values into the following equation:

$$\frac{V_{TEMPCO} \text{ (in mV)}}{(S) (T_A + 273)}$$

Where  $S$  = Scale factor for your circuit selected from the table in mV. Then turn the circuit power off, short  $V_{OUT}$  at pin 6 of the REF-02 to ground, and while applying exactly 100.00 mV to the op amp output, adjust  $R_{B2}$  to that  $V_B = (X) (100 \text{ mV})$ . Now remove the short and the 100-mV source, reapply circuit power and adjust  $R_P$  so that the op-amp output voltage equals  $(T_A) (S)$ . The system is now exactly calibrated.

## TEMPERATURE MEASURING ADD-ON FOR DMM DIGITAL VOLTMETER

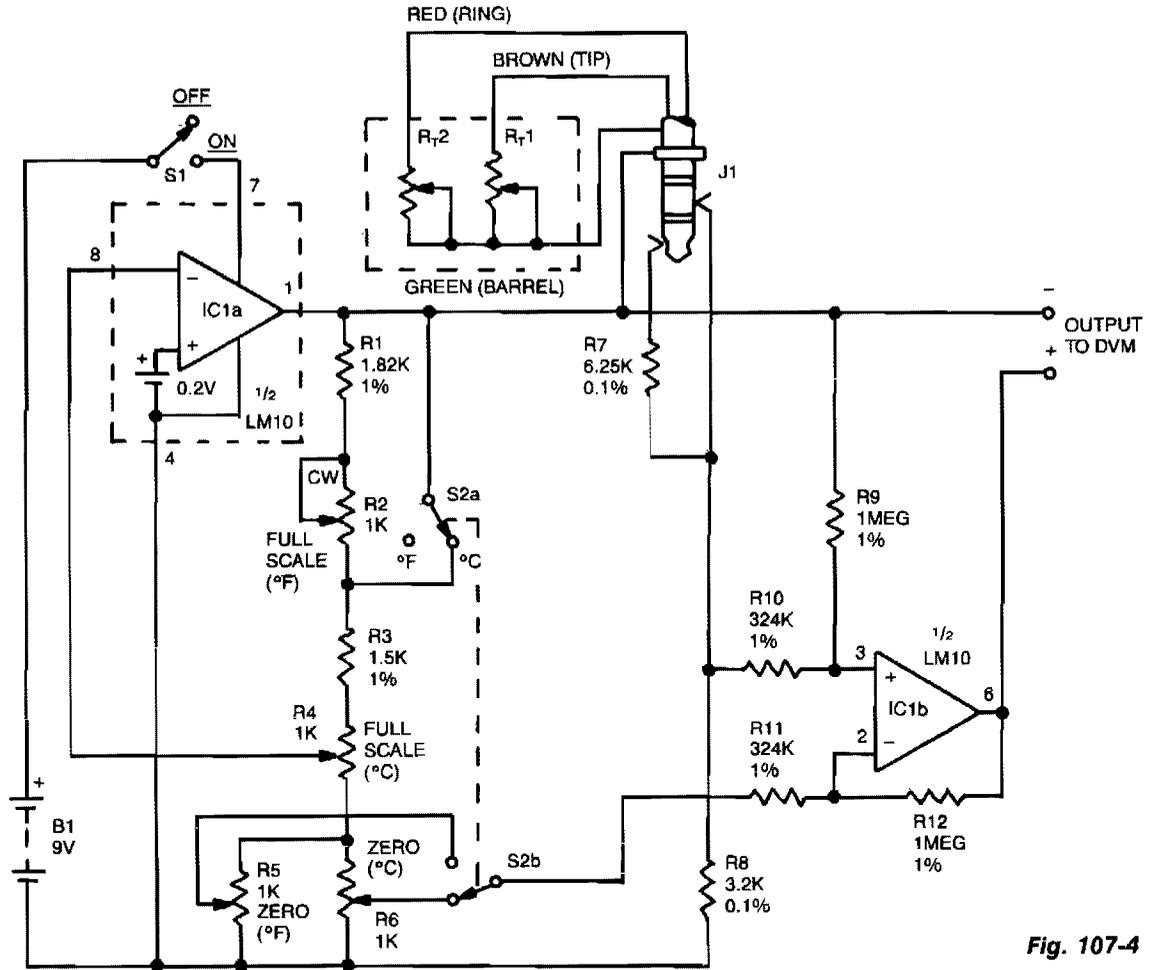


**Fig. 107-4**

The DVM-to-temperature adapter is built around a single IC, National's LM10. That micropower IC contains a stable 0.2 V reference, a reference amplifier and a general-purpose op amp. The circuit is designed for a linear temperature range of 0 to 100°C (32 to 212°F). The 0.2-V reference and reference amplifier provide a stable, fixed-excitation voltage to the Wheatstone bridge. The voltage is determined by a feedback network consisting of R1 through R6. Switch S2a configures the feedback to increase the voltage from 0.6 V on the Celsius range to 1.08 V on the Fahrenheit range. These differences compensate for the fact that one degree Fahrenheit produces a smaller resistance change than does one degree Celsius.

Resistors R1 through R16 also form the fixed leg of the Wheatstone bridge, nulling the bridge output at zero degrees. Since 0°C is different from 0°F, S2b is used to select the appropriate offset.

The LM10's op amp, along with R9 through R12, form a differential amplifier that boosts the bridge output to 10 mV per degree. Since a single supply is used, and since the output must be able to swing both positive and negative, the output is referenced to the bridge supply voltage, rather than to the common supply.
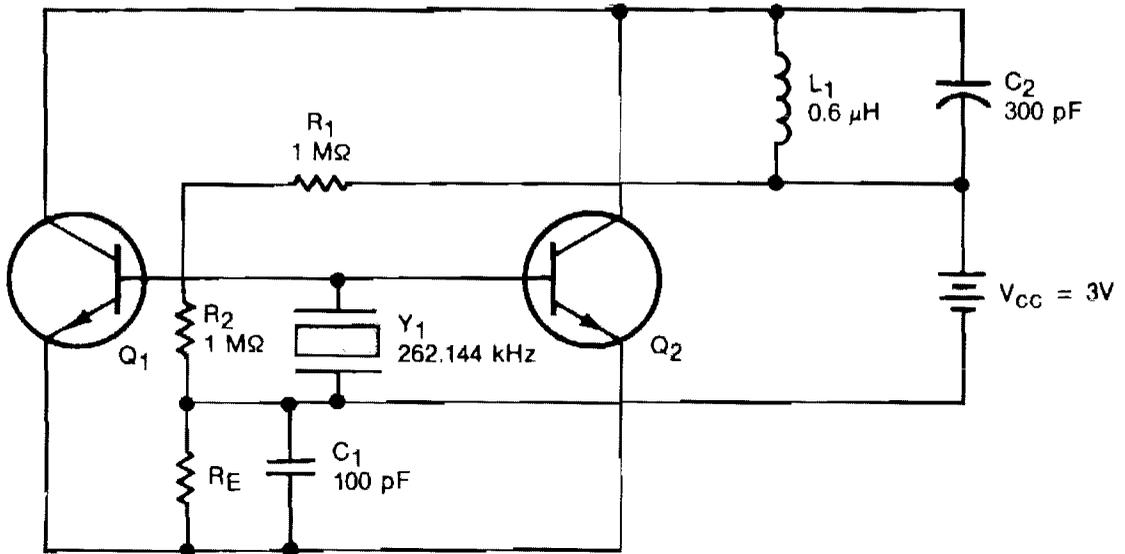
## IMPLANTABLE INGESTIBLE ELECTRONIC THERMOMETER




- NOTES: 1.  $Q_1$  and  $Q_2$  are MAT-02 bipolar npn transistors.  
2.  $R_E = 20$  to  $40$  k $\Omega$ .

NASA

Fig. 107-5

This oscillator circuit includes a quartz crystal that has a nominal resonant frequency of 262,144 Hz and is cut in the orientation that gives a large linear coefficient of frequency variation with the temperature. In this type of circuit, the oscillation frequency is controlled primarily by the crystal—as long as the gain-bandwidth product is at least four times the frequency. In this case, the chosen component values yield a gain-bandwidth product of 1 MHz. Inductor  $L_1$  can be made very small: 100 to 200 turns with a diameter of 0.18 in. (4.8 mm) and a length of 0.5 in. (12.7 mm). Although the figure shows two transistors in parallel, one could be used to reduce power consumption or three could be used to boost the output. The general oscillator circuit can be used to measure temperatures from  $-10$  to  $+140^\circ\text{C}$ . A unit made for use in the human body from about  $30$  to  $40^\circ\text{C}$  operates at  $262,144 \pm 50$  Hz with a frequency stability of 0.1 Hz and a temperature coefficient of 9 Hz/ $^\circ\text{C}$ .

## SIMPLE LINEAR THERMOMETER

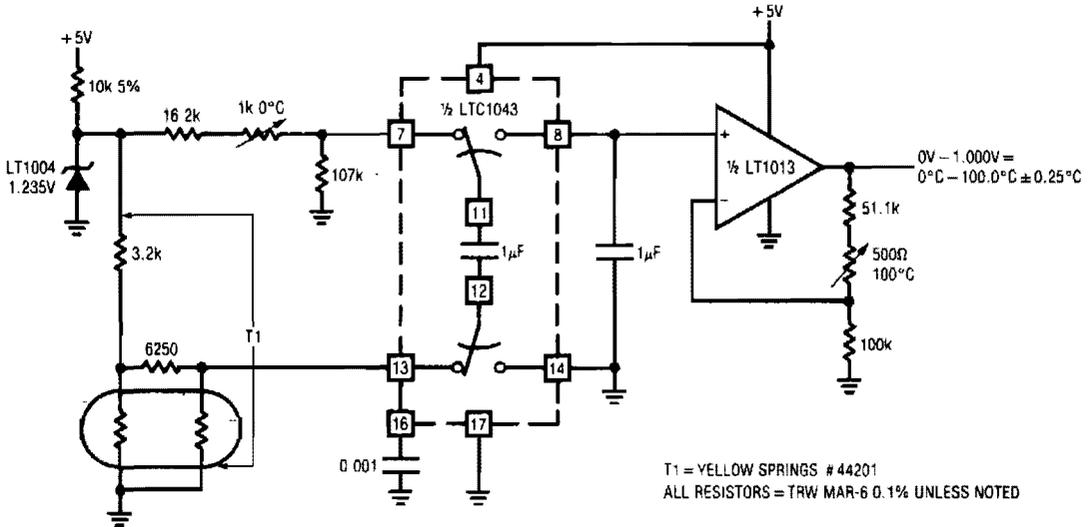


LINEAR TECHNOLOGY CORP.

**Fig. 107-6**

The thermistor network specified eliminates the need for a linearity trim—at the expense of accuracy and operational range.

## THERMOMETER ADAPTER

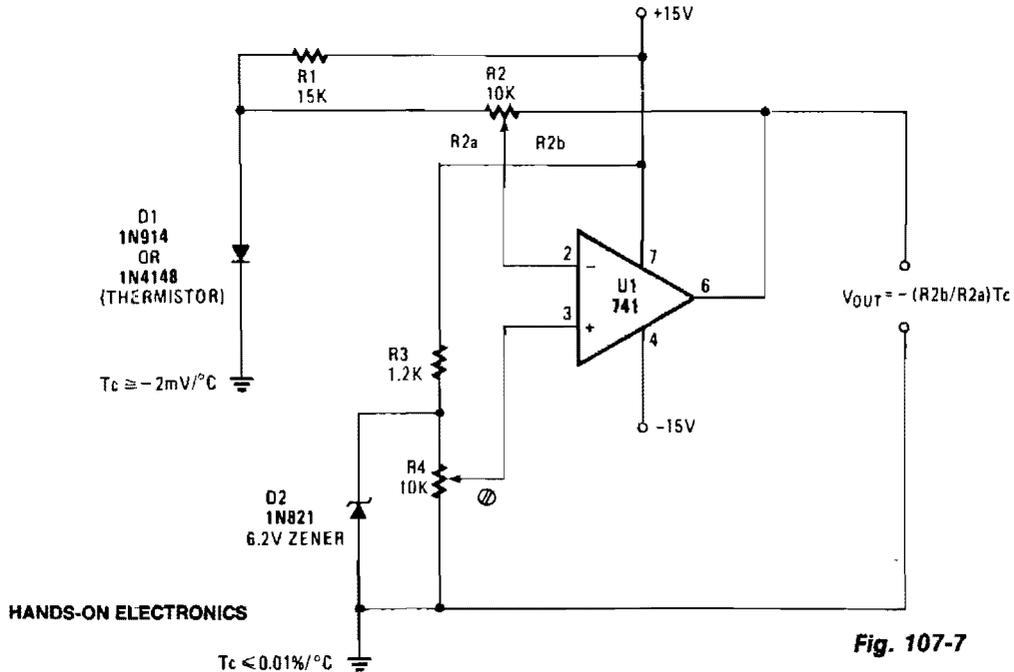

**Fig. 107-7**

## THERMOMETER ADAPTER (Cont.)

A simple op amp and silicon diode are the heart of the temperature-to-voltage converter that will permit you to use an ordinary voltmeter—either analog or digital—to measure temperature. User adjustments make it possible for a reading of either 10 mV or 100 mV to represent 1°F or C.

Temperature sensor D1 is a 1N4148 silicon diode. It has a temperature coefficient of  $-2 \text{ mV}/^\circ\text{C}$ . U1, a 741 op amp, is connected as a differential amplifier. A voltage divider consisting of R3 and Zener diode D2 provides a 6.2 V reference voltage. D2 is shunted by potentiometer R4, so that the offset can be adjusted to align the output voltage with either the Celsius or Fahrenheit scale, as desired.

Gain control R2 is adjusted so the output of the op amp is in the scale or voltage range of the meter being used. R4, the offset adjust control, is then adjusted so the output voltage represents either degrees F or C. The thermometer adapter can be calibrated by adjusting R4 while the probe sensor is at a known temperature.

---

# 108

## Tilt Meter

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Digitizer

# DIGITIZER


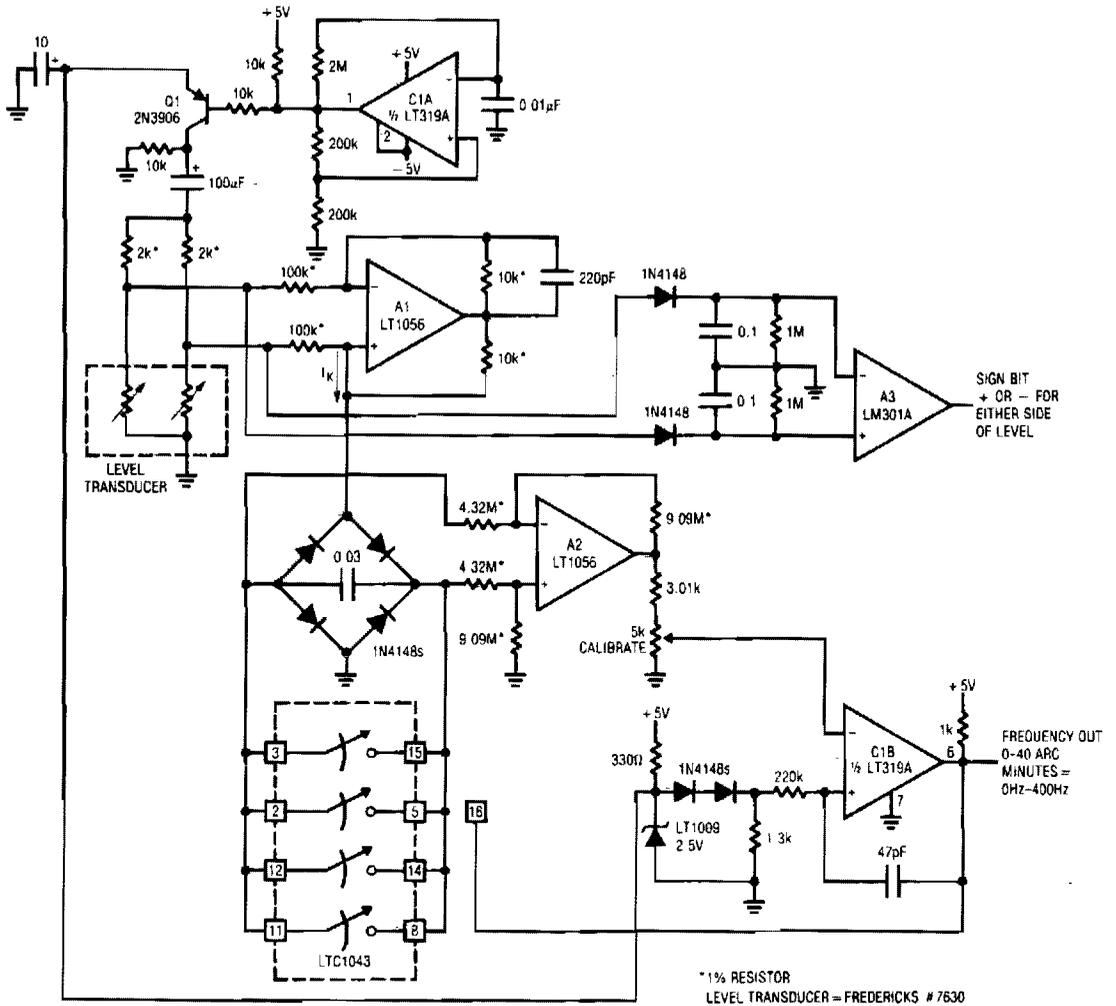


Fig. 108-1(a)

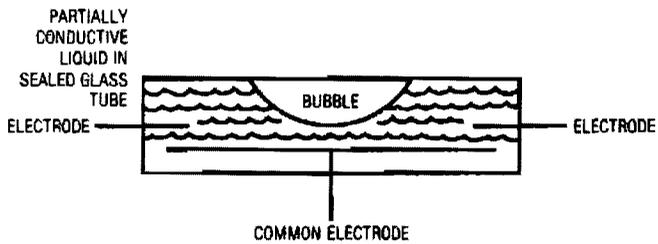

LINEAR TECHNOLOGY

Fig. 108-1(b)

## Bubble Based Level Transducer

## DIGITIZER (Cont.)

If the tube is level with respect to gravity, the bubble resides in the tube's center and the electrode resistances to common are identical. As the tube shifts away from level, the resistances increase and decrease proportionally. Transducers of this type must be excited with an ac waveform to avoid damage to the partially conductive liquid inside the tube.

The level transducer is configured with a pair of 2-K $\Omega$  resistors to form a bridge. The required ac bridge excitation is developed at C1A, configured as a multivibrator. C1 biases Q1, which switches the LT1009's 2.5-V potential through the 100- $\mu$ F capacitor to provide the ac bridge drive. The bridge differential output ac signal is converted to a current by A1, operating as a Howland current pump. This current, whose polarity reverses as bridge drive polarity switches, is rectified by the diode bridge. Thus, the 0.03- $\mu$ F capacitor receives unipolar charge. A2, running at a differential gain of 2, senses the voltage across the capacitor and presents its single-ended output to C1B. When the voltage across the 0.03- $\mu$ F capacitor becomes high enough, C1B's output becomes high, turning on the paralleled sections of the LTC1043 switch. This discharges the capacitor. The 47-pF capacitor provides enough ac feedback around C1B to allow a complete zero reset for the capacitor. When the ac feedback ceases, C1B's output decreases and the LTC1043 switch goes off. The 0.03- $\mu$ F unit again receives constant current charging and the entire cycle repeats. The frequency of this oscillation is determined by the magnitude of the constant current delivered to the bridge-capacitor configuration. This current's magnitude is determined by the transducer bridge's offset, which is level related.

---

# 109


## Time-Delay Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Electronic Time Delay  
Timing Threshold and Load Driver  
Simple Time Delay

## ELECTRONIC TIME DELAY

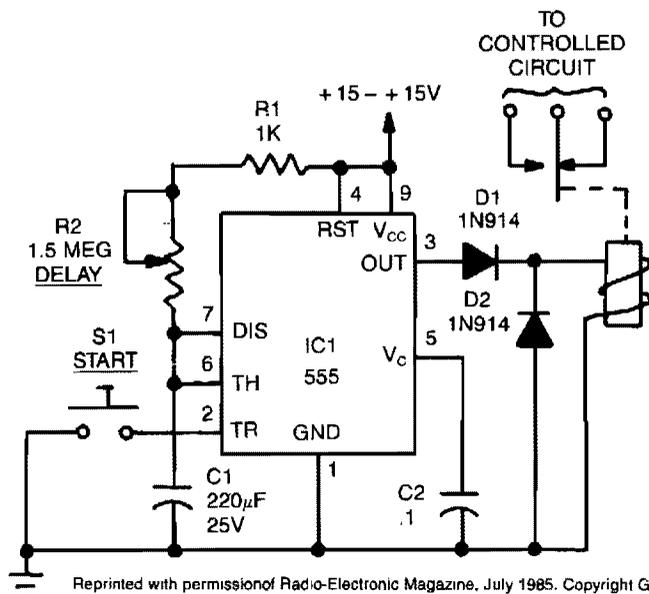


**Fig. 109-1**

Reprinted with permission of Radio-Electronic Magazine, July 1985. Copyright Gernsback Publications, Inc., 1985.

The time delay,  $T$ , in seconds is:  $T = 1.1 \times C1 \times (R1 + R2)$ . The resistances are in megohms and capacitances in microfarads. The sum of  $R1$  and  $R2$  should not be less than  $1000 \Omega$  nor higher than  $20 M\Omega$ . Pressing  $S1$  starts the timing cycle. A low-going pulse, instead of  $S1$  can also be used to initiate the timing cycle. With the values shown and allowing for the tolerances of the  $200\text{-}\mu\text{F}$  capacitor, the delay will range from 4 minutes and 50 seconds to 7 minutes and 26 seconds. The output terminal, pin 3, of 555, is normally low and switches high during the timing cycle. The output can either sink or source currents up to 200 mA. Therefore, a load such as a relay coil can be connected between pin 3 and  $V_{CC}$  or between pin 3 and ground, depending on circuit requirements. When the relay is connected between pin 3 and ground, it is normally de-energized so it is energized only during the timing cycle. Connecting the relay to ground will save power and allow the IC to run cool.


## TIMING THRESHOLD AND LOAD DRIVER

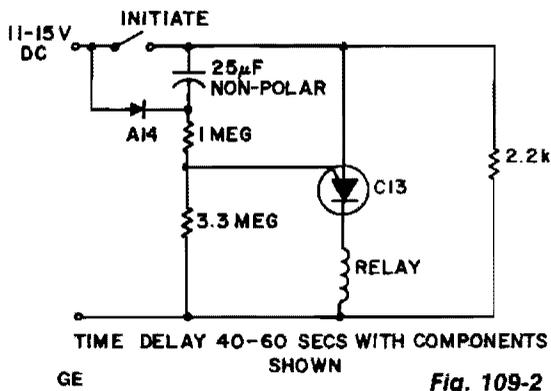

**Fig. 109-2**

Power is applied to the circuit with the initiate switch open. The  $25\text{-}\mu\text{F}$  capacitor charges through the A14, or equivalent, diode and  $2.2\text{-K}\Omega$  resistor to full supply voltage. When the initiate switch is closed, the low side of the capacitor is suddenly raised to +12 V. This raises the diode side of the capacitor to approximately +24 V. The capacitor immediately begins discharging through the series-connected 1 and  $3.3\text{-M}\Omega$  resistors. Eventually, the C13 gate becomes forward biased, the device turns, and it applies power to the relay. The delay is virtually independent of supply voltage.

## SIMPLE TIME DELAY

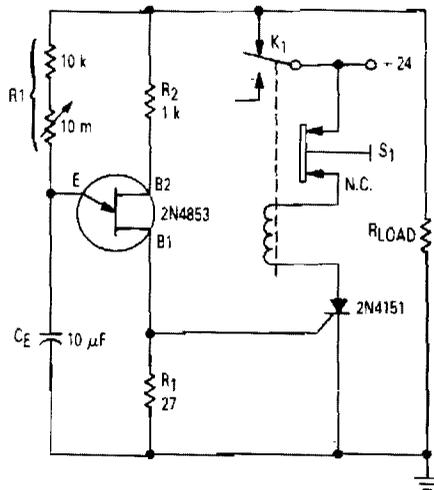

Copyright of Motorola, Inc. Used by permission.

Fig. 109-3

After the first cycle, the relay will normally be energized. When normally closed pushbutton S<sub>1</sub> is activated, the SCR turns off, the relay is de-energized, and power is applied to the relaxation oscillator and the load. After a time delay varying from less than a second to approximately 2.5 minutes, as determined by the setting of the 10-MΩ potentiometer, the unijunction will fire and turn on the SCR. The relay will energize until power is removed from the oscillator and the load, and will stay energized until button S<sub>1</sub> is pushed again. The UJT trigger output from base 1 directly drives the gate of the SCR. However, where isolation between the UJT trigger or any other type of trigger and the thyristor power circuit is required, then a simple pulse transformer, interfacing the two elements, will suffice.

# 110

## Timers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Sequential Timer  
CMOS Precision Programmable  
Laboratory Timer  
Long-Time Timer  
One-Shot Timer  
Three-Minute Timer

## SEQUENTIAL TIMER


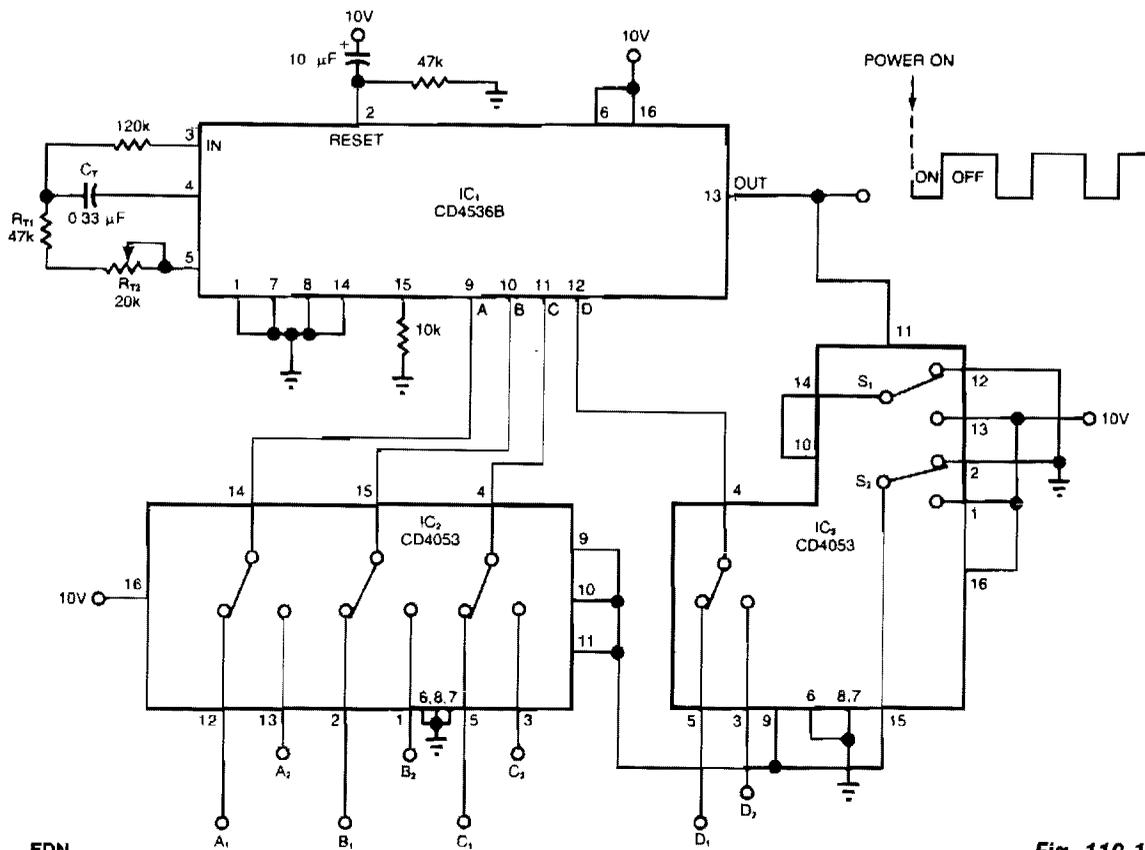


Fig. 110-1

The timer circuit shown gives independent control of the output's on and off intervals, which can range from 0.055 seconds to 30 minutes, relatively unaffected by power-line transients. IC<sub>1</sub> is a CMOS programmable-timer chip that includes 24 ripple-binary counter stages; the first eight are bypassed when logic 1 is applied to pin 6. Then, a 4-bit input code at pins A, B, C, and D connects one of the 16 remaining stages to the output at pin 13. The chip includes an oscillator whose timing components are  $C_T$ ,  $R_{T1}$ , and  $R_{T2}$ . For this example, you adjust  $R_{T2}$  for an internal period  $T_{IN}$  of 54.9 ms (18.2 Hz). Then, the output on or off interval is:  $T_{OUT} = T_{IN} 2^{N-1}$ , where  $N$  is the number of counter stages in the internal divider chain (See Fig. 110-3). IC<sub>2</sub> and IC<sub>3</sub> are CMOS triple-spdT analog switches that connect one BCD code ( $A_1 - D_1$ ) for the on interval and another ( $A_2 - D_2$ ) for the off interval. You can apply the codes using manual toggle switches or programmable latches. When power is first applied, the switches are in the positions shown, which applies  $A_1 - D_1$  to IC<sub>1</sub> and generates the on interval. When the output changes state, all the switches change position and initiate the off interval by applying  $A_2 - D_2$  to IC<sub>1</sub>. The cycle then repeats. To eliminate race conditions, switches S<sub>1</sub> and S<sub>2</sub> of IC<sub>3</sub> operate in sequence before the remaining four switches operate in parallel. To start the output sequence with an off instead of an on interval, connect a power-on-set signal at pin 1 instead of the power-on-reset signal at pin 2.
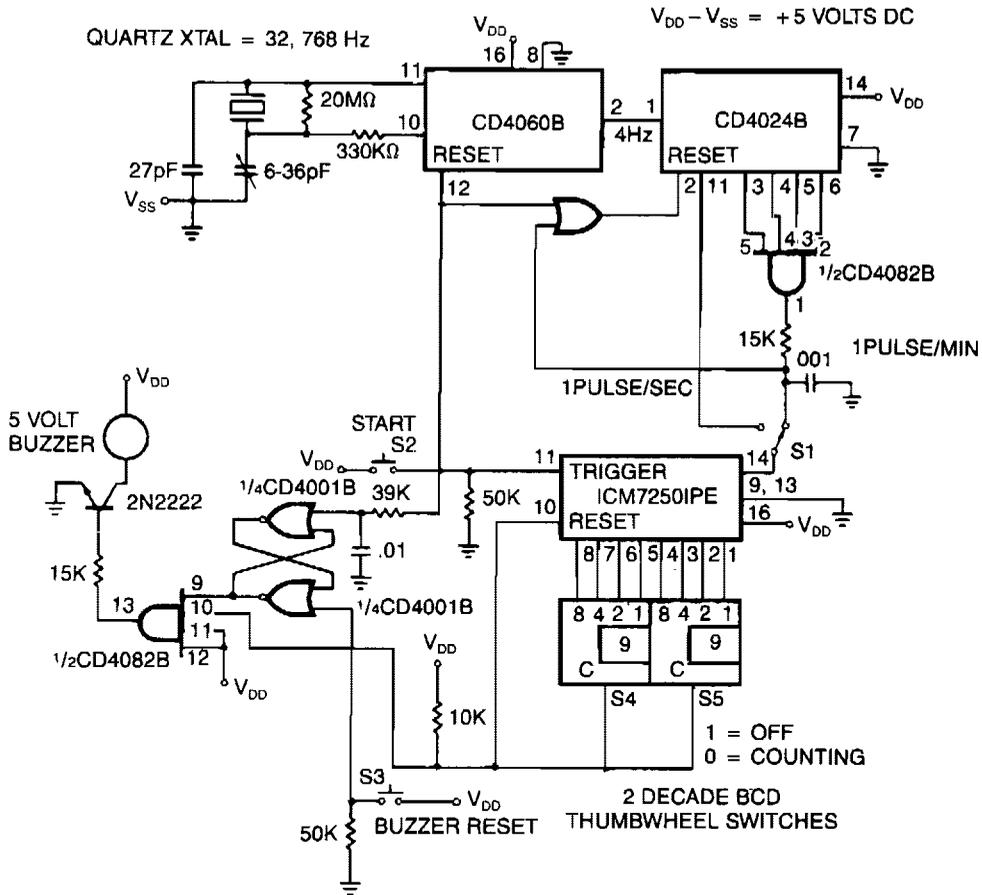
## CMOS PRECISION PROGRAMMABLE LABORATORY TIMER



INTERSIL

Fig. 110-2

The time base is first selected with S1 set for seconds or minutes, then units 0–99 are selected on the two thumbwheel switches S4 and S5. Finally, switch S2 is depressed to start the timer. Simultaneously, the quartz crystal-controlled divider circuits are reset, the ICM7250 is triggered and counting begins. The ICM7250 counts until the preprogrammed value is reached, then, the value is reset, pin 10 of the CD4082B is enabled, and the buzzer is turned on. Pressing S3 turns the buzzer off.

## LONG-TIME TIMER

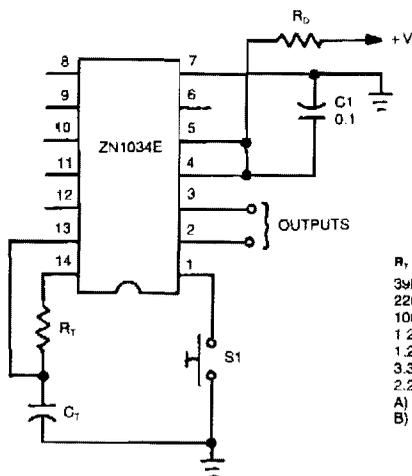
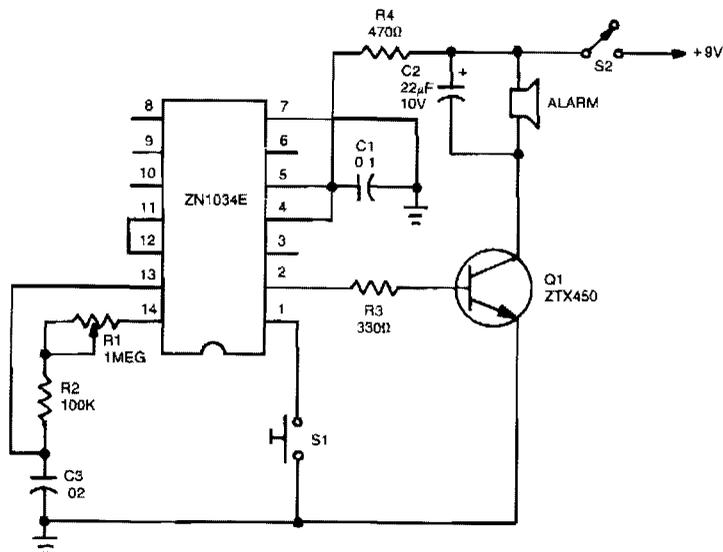


TABLE 1— $R_T$  AND  $C_T$  VALUES

Timing elements		Timed period	
$R_T$ (ohms)	$C_T$ ( $\mu$ F)	A	B
39K	0.01	1 sec	2.92 sec
220K	0.1	1 min	2.75 min
100K	1.0	5 min	12.5 min
1.2 Meg	1.0	55 min	2.5 hrs
1.2 Meg	10	9.1 hrs	25 hrs
3.3 Meg	10	1 day	2.8 days
2.2 Meg	100	1 week	19 days


A) Pins 11 and 12 tied together  
 B) 300K resistor connected between pins 11 and 12

**Fig. 110-3**

Reprinted with permission from Radio-Electronics Magazine May 1987. Copyright Gernsback Publications, Inc., 1987

When used as a stand-alone device, ZN1034E from Ferranti can provide timed intervals ranging from 1 second to 19 days, although the rc time constant is only 220 seconds. The ZN1034E includes an internal voltage regulator, an oscillator, and a 12-stage binary counter. The total delay time provided by the counter is 4095 times the oscillator period. The control logic times-out after 4095 cycles of the oscillator, and delivers high and low output pulses at pins 2 and 3. The output at pin 3 is normally high and decreases at the end of the timed interval. The complementary output at pin 2 is normally low and becomes high at the end of the timed interval. The timing period is initiated by momentarily grounding pin 1. Timing resistor  $R_T$  consists of two resistors, R1 and R2, in series. Because R1 has a fixed value of 100 K $\Omega$ , the total range of  $R_T$  is 100 K to 1.1 M $\Omega$ .

## ONE-SHOT TIMER

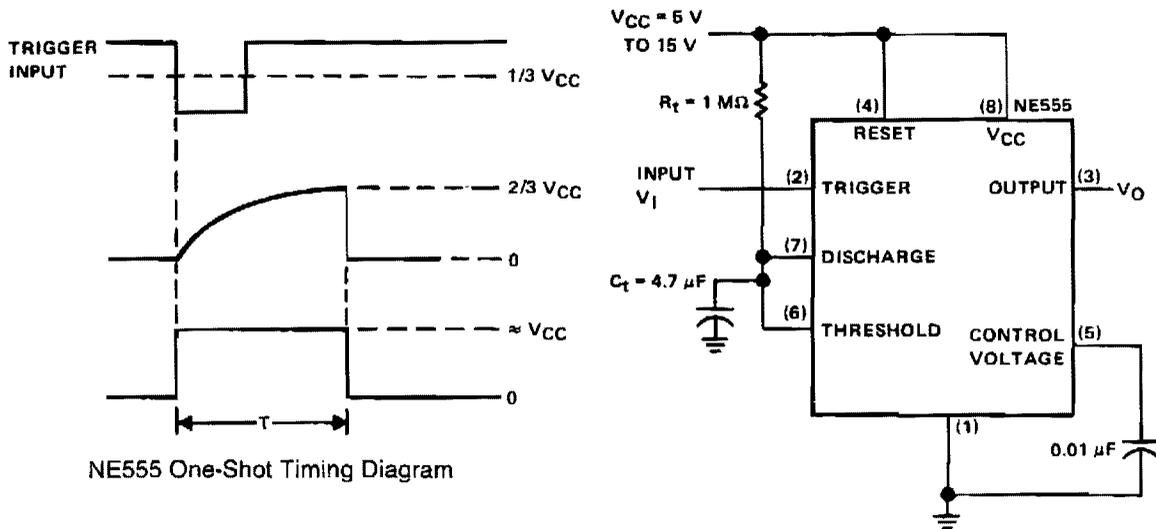


Reprinted by permission of Texas Instruments.

Fig. 110-4

This simple circuit consists of only two timing components  $R_T$  and  $C_T$ , the NE555, and bypass capacitor  $C_2$ . While not essential for operation,  $C_2$  is recommended for noise immunity. During standby, the trigger input terminal is held higher than  $1/3 V_{CC}$  and the output is low. When a trigger pulse appears with a level less than  $1/3 V_{CC}$ , the timer is triggered and the timing cycle starts. The output rises to a high level near  $V_{CC}$ , and at the same time,  $C_T$  begins to charge toward  $V_{CC}$ . When the  $C_T$  voltage crosses  $2/3 V_{CC}$ , the timing period ends with the output falling to zero, and the circuit is ready for another input trigger. Because of the internal latching mechanism, the timer will always time out when triggered, regardless of any subsequent noise, such as bounce, on the trigger input. For this reason, the circuit can also be used as a bounceless switch by using a shorter  $rc$  time constant. A  $100\text{-K}\Omega$  resistor for  $R_T$  and a  $1\text{-}\mu\text{F}$  capacitor for  $C_T$  would give a clean, 0.1 s output pulse when used as a bounceless switch.

## THREE-MINUTE TIMER

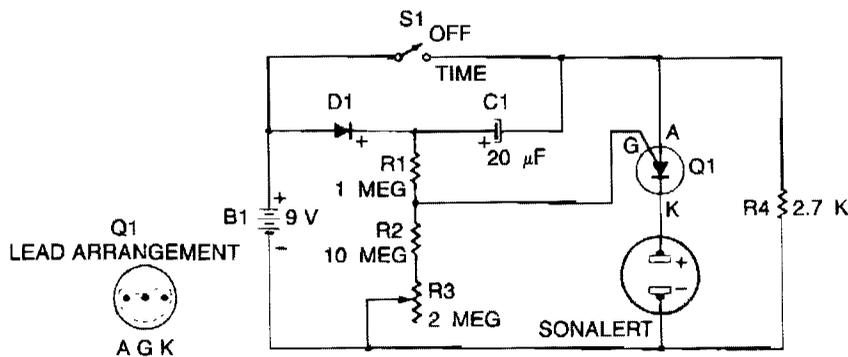

TAB BOOKS

Fig. 110-5

### **THREE-MINUTE TIMER (Cont.)**

When S1 is off, C1 charges to within 0.5 V of the battery voltage through diode D1 and resistor R4. When S1 is closed, the anode of the PUT rises to the positive supply voltage. The PUT does not conduct, because battery voltage appears in series with the charge stored on C1, which raises the gate of the PUT to a level positive with respect to the anode. The timer relies on the discharge of capacitor C1 through resistors R1, R2, R3, and R4. Once C1 is at zero volts, the PUT will turn on battery voltage to the SonaAlert and cause it to sound.

---

111



## Tone Control Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

IC Preamplifier/Tone Control  
Ten-Band Octave Equalizer  
Three-Band Active Tone Control  
Wien-Bridge Filters  
Rumble/Scratch Filter

## IC PREAMPLIFIER/TONE CONTROL

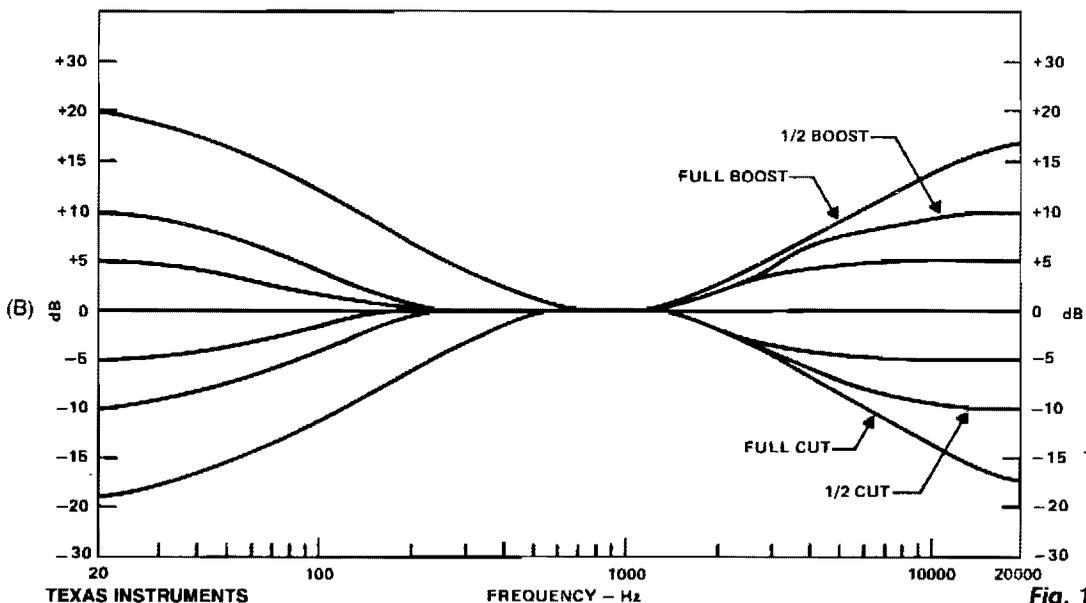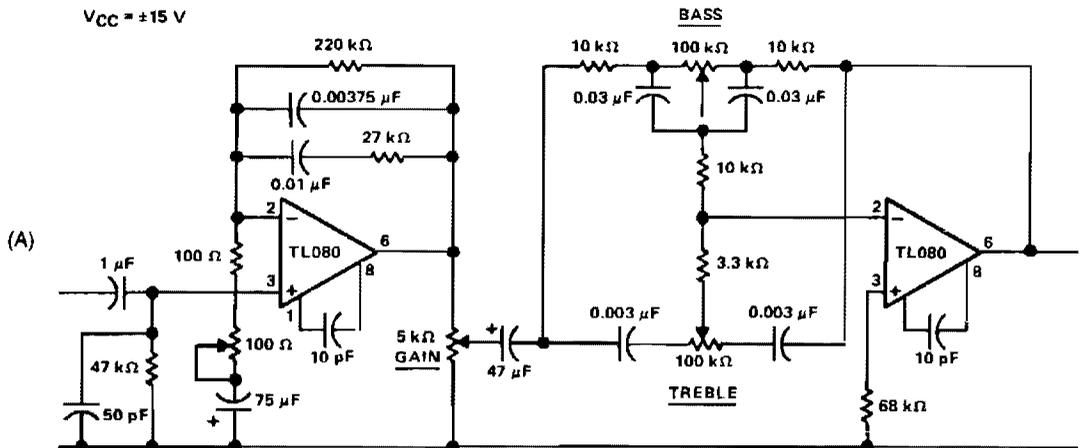

**Fig. 111-1**

The circuit is a form of the so-called “Americanized” version of the Baxandall negative-feedback tone control. At very low frequencies, the reactance of the capacitor is large enough that they might be considered open circuits, and the gain is controlled by the bass potentiometer. At low to middle frequencies, the reactance of the 0.03- $\mu\text{F}$  capacitors decreases at the rate of 6 dB/octave, and is in parallel with the 200-K $\Omega$  potentiometer; so the effective impedance is reduced correspondingly, thereby reducing the gain. This process continues until the 10-K $\Omega$  resistors, which are in series with the bass pot, become dominant and the gain levels off at unity. The action of treble circuit is smaller and becomes effective when the reactance of the 0.003- $\mu\text{F}$  capacitors becomes minimal. This complete tone control is in the negative feedback loop of the TL080. Figure B shows the bass and treble tone control response.

## TEN-BAND OCTAVE EQUALIZER


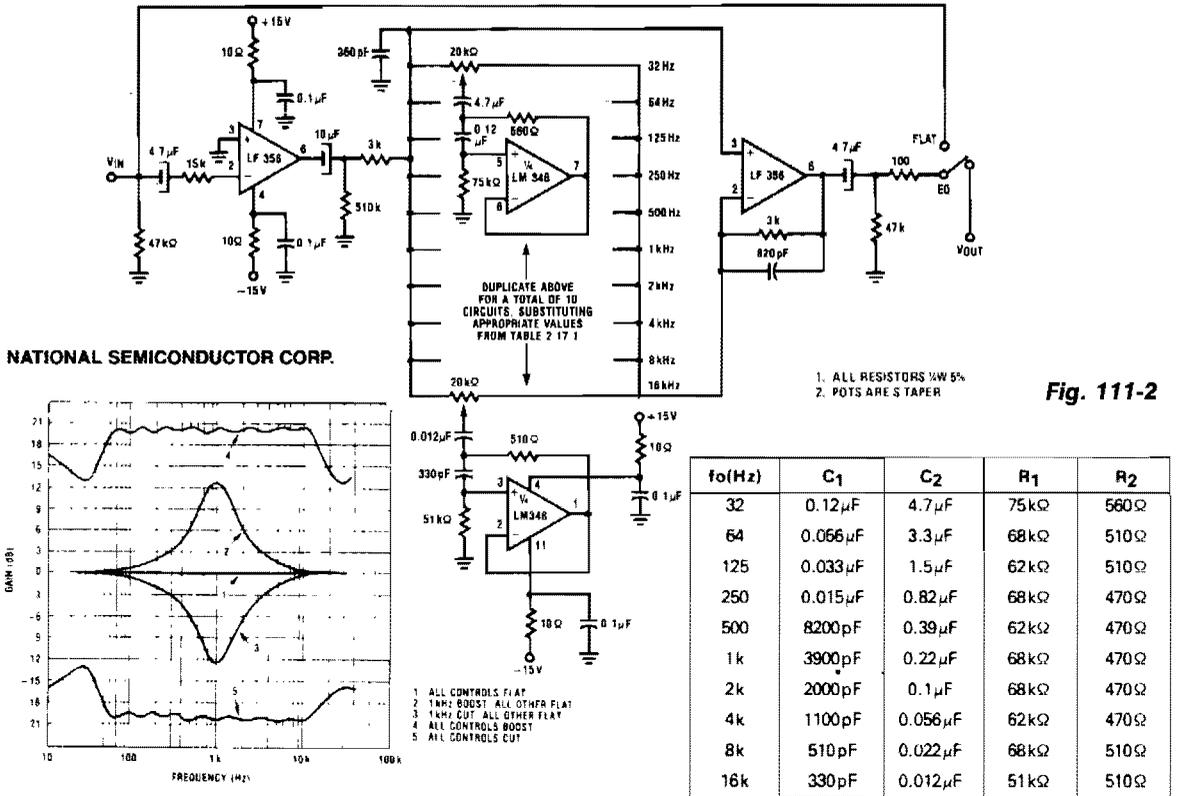




Fig. 111-2

A series of active rf filters using National LM348IC comprises a ten-band graphic equalizer. C1, C2, R1, and R2 should be at least 10% with 5% preferred tolerances.

## THREE-BAND ACTIVE TONE CONTROL

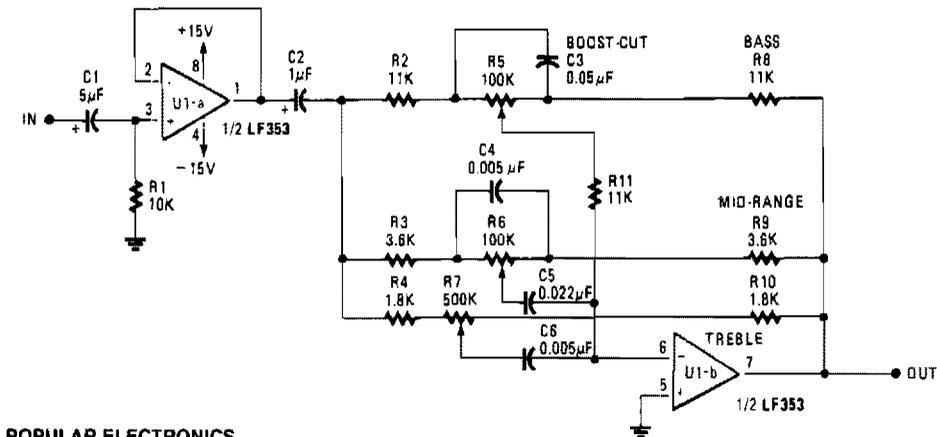

## WIEN-BRIDGE FILTER

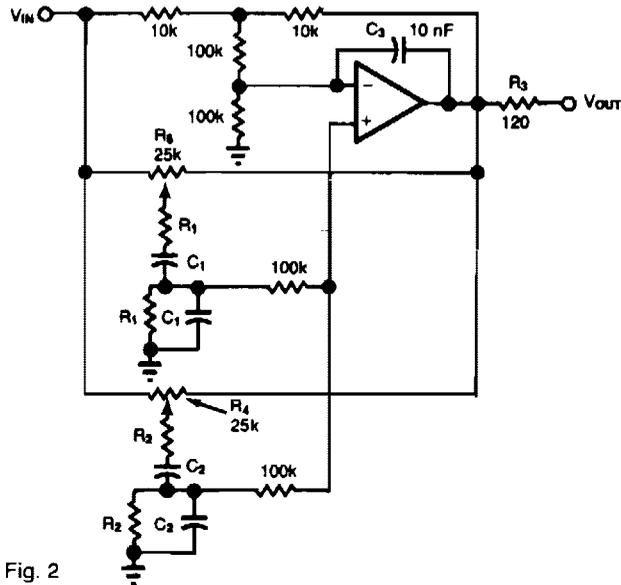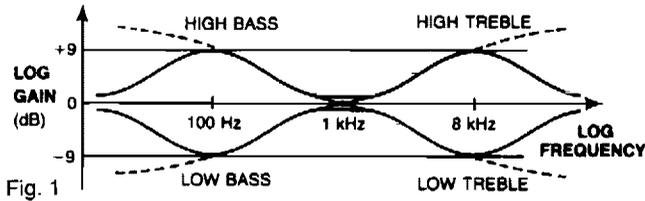

EDN

Fig. 111-4

Most audio tone controls affect midband gain, and they often create booming or hissing sounds when activated. You can avoid these problems by using a dual Wien-bridge filter to provide independent control of the treble and bass frequencies.


Experiments with equalizers indicate that the optimum center frequencies are about 100 Hz and 8 kHz. Using the relation  $f = (2\pi RC)^{-1}$ , set the Fig. 1 values accordingly:

$$100 \text{ Hz: } R1 = 15 \text{ K}\Omega; C1 = 0.1 \mu\text{F}$$

$$8 \text{ kHz: } R2 = 16 \text{ K}\Omega; C2 = 1.3 \text{ nF}$$

R3 and C3 provide stability. You obtain a  $\pm 9$  dB variation of treble and bass by adjusting potentiometers R4 and R5, respectively. The filter's frequency response is shown in Fig. 2.

## RUMBLE/SCRATCH FILTER

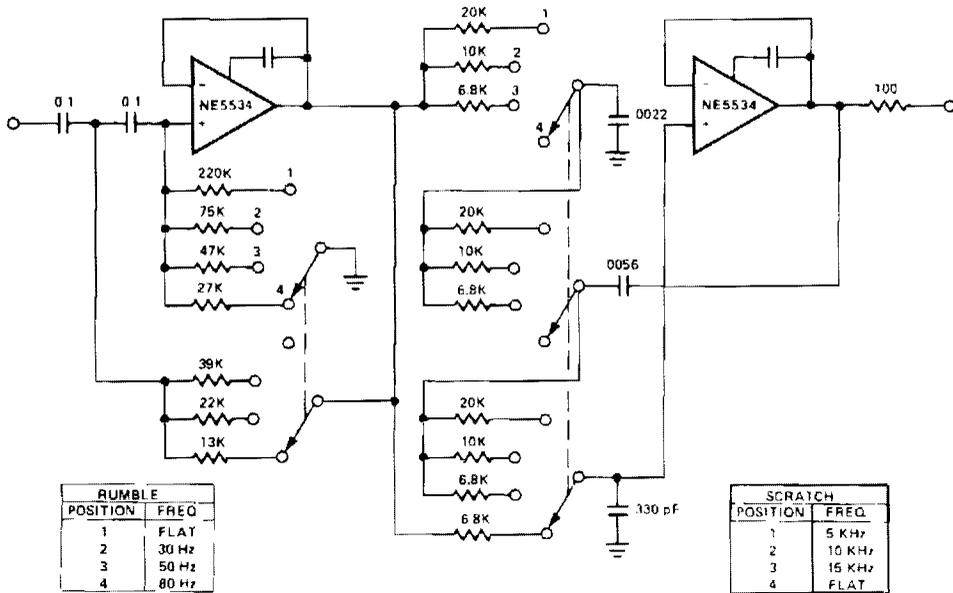

All resistor values are in ohms

**SIGNETICS**

**Fig. 111-5**

This is a variable bandpass amplifier with adjustable low- and high-frequency cutoffs.

# 112


## Touch-Switch Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Negative-Triggered Touch Circuit	Line Hum Touch Switch
Positive-Triggered Touch Circuit	Touch Switch
Digital Touch On/Off Switch	Touch Switch
Two-Terminal Touch Switch	Touch Switch
Touch On/Off Electronic Switch	

## NEGATIVE-TRIGGERED TOUCH CIRCUIT

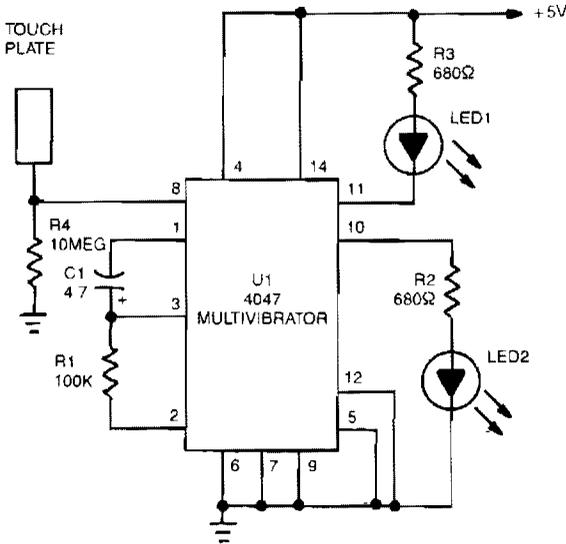


POPULAR ELECTRONICS

Fig. 112-1

The 4047 is configured as a monostable multivibrator circuit or one shot that is set up to trigger on a negative-transition of the signal applied to its pin 6 input. The multivibrator's on time is determined by the values of R1 and C1. Although R1 is shown to be a 100-K unit, its value can be anything between 10 K and 1 MΩ. Capacitor C1 can be a nonpolarized capacitor with any practical value above 100 pF. By making R4's value extremely high, the circuit can be used as a touch-triggered one-shot multivibrator. If the value of R4 is reduced to a much lower value, such as 10 KΩ, the circuit can be triggered with a negative pulse through 0.1-μF capacitor connected to pin 6. With a 100-KΩ resistor for R1, and a 4.7-μF electrolytic capacitor for C1, the circuit's on time is about 0.6 second. When R1 is increased to 470 KΩ, the on time of the circuit is increased to over 6 seconds.

## POSITIVE-TRIGGERED TOUCH CIRCUIT

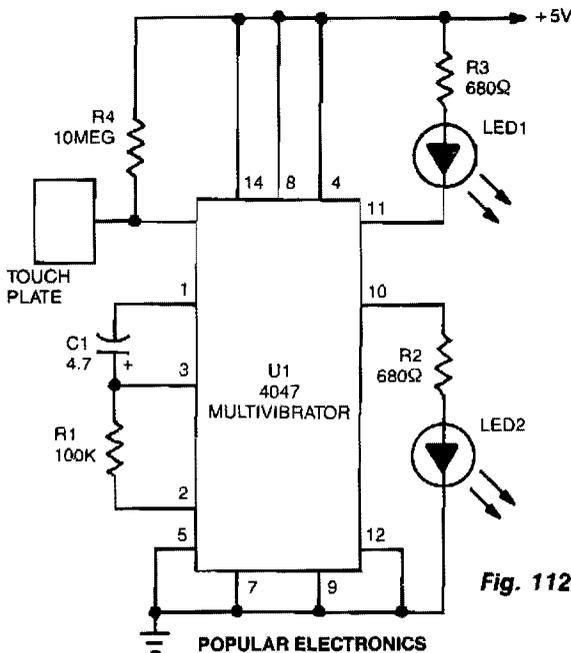


POPULAR ELECTRONICS

Fig. 112-2

LED1 and LED2 indicators turn on and remain on, each time the circuit is triggered. During the timing cycle, U1's Q output at pin 10 becomes positive when the Q output at pin 11 becomes negative. The two LEDs can be removed and the Q and Q outputs at pins 10 and 11, respectively, can be used to trigger some other circuit.

## DIGITAL TOUCH ON/OFF SWITCH

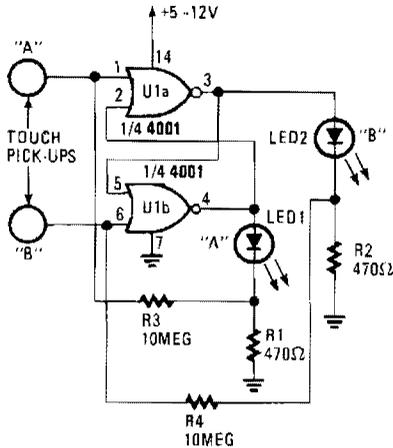


HANDS-ON ELECTRONICS

Fig. 112-3

Only one LED can be on when the circuit is at rest. Which LED is illuminated is determined by the touch pick-up that last had human contact. Pickup terminal A controls the on condition of LED1, and terminal B controls the on condition of LED2. A 4001 quad two-input NOR gate is connected in an anti-bounce latching circuit that is activated by touching a pickup.

## TWO-TERMINAL TOUCH SWITCH

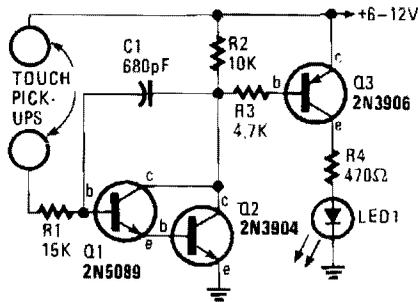


HANDS-ON ELECTRONICS

Fig. 112-4

This circuit requires the bridging of two circuits to activate the electronic switch. That circuit does not require a 60-Hz field to operate and can be battery or ac powered. The two-pickup terminals can be made from most any clean metal; they should be about the size of a penny. The input circuitry of the two-terminal touch switch is a high-gain Darlington amplifier that multiplies the small bridging current to a value of sufficient magnitude to turn on Q3, supplying power to LED1. If a quick on and off switching time is desired, the value of C1 should be very small; if a long on-time period is required, the value of C1 can be increased.

## TOUCH ON/OFF ELECTRONIC SWITCH

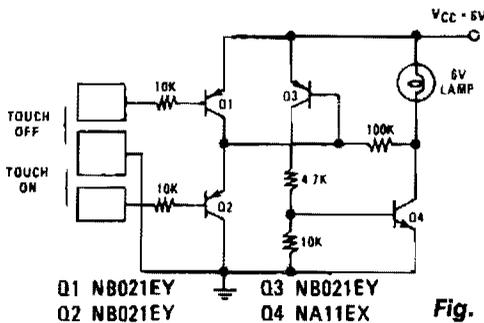

Q1 NB021EY  
Q2 NB021EY


Q3 NB021EY  
Q4 NA11EX

Fig. 112-5

Transistors Q1 and Q2 control latch Q3 and Q4 to switch on the lamp. A high resistance from touching the electrode biases Q1 or Q2 on, setting or resetting the latch.

NATIONAL SEMICONDUCTOR CORP.

## LINE-HUM TOUCH SWITCH

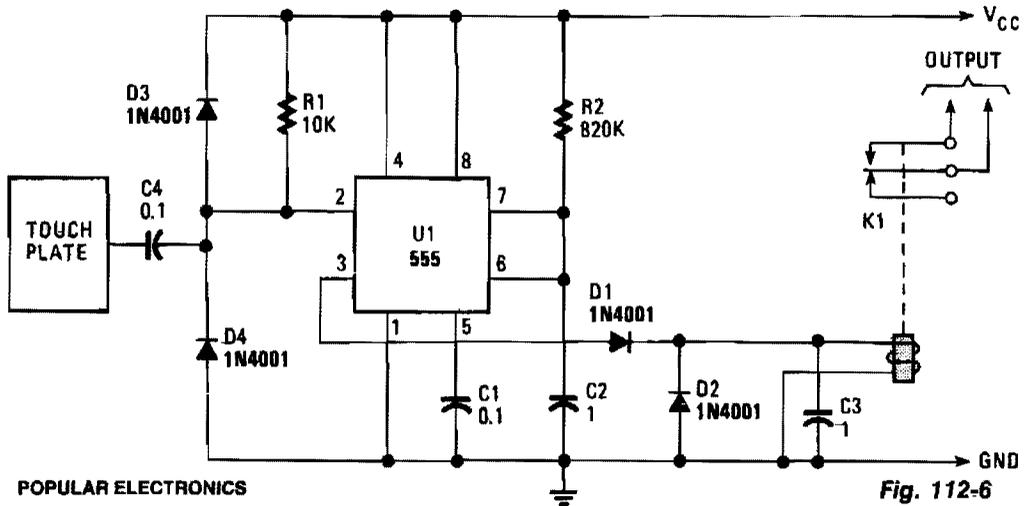


POPULAR ELECTRONICS

Fig. 112-6

The monostable period is set for about 1 second, as is the usual case. The induced line hum comes through C2, providing a continuous string of trigger pulses. The output becomes low for about 10 ms per second as the monostable times out and then retriggers. Diode D1 and capacitor C3 buffer the relay so it doesn't chatter on those 10-ms pulses. Resistor R2 sets the sensitivity.

The relay energizes when the plate is touched and de-energizes, up to one second after the finger is removed. The delay is a function of when the monostable last retriggered.

## TOUCH SWITCH

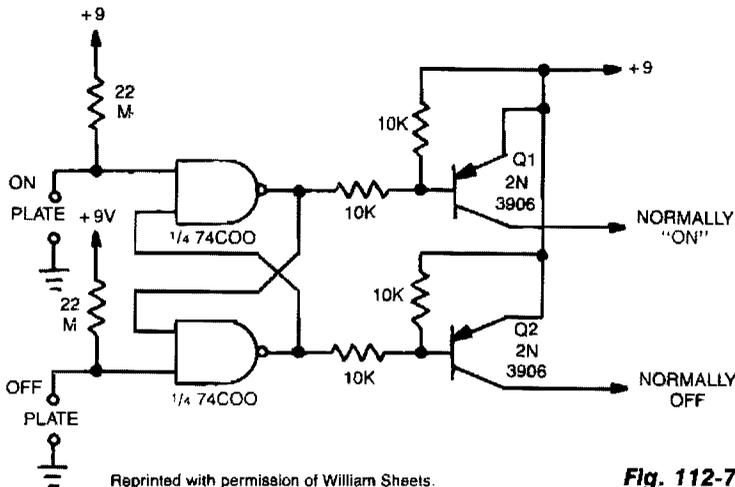


Reprinted with permission of William Sheets.

Fig. 112-7

When the plate is touched, the gate input becomes low, changing the state of the latch. Q1 and Q2 give alternate N-on—N-off outputs.

## TOUCH SWITCH

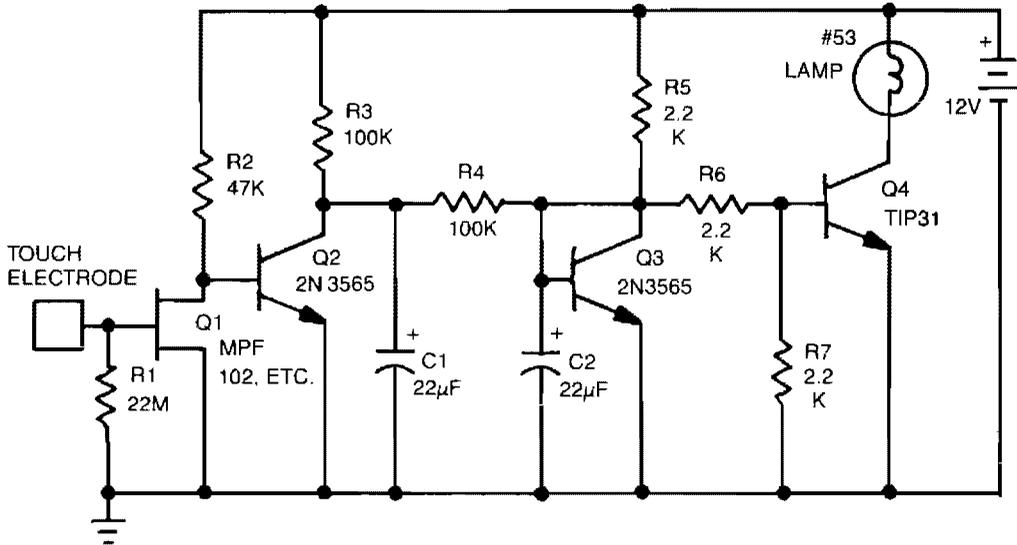


Reprinted with permission of William Sheets.

**Fig. 112-8**

This touch-actuated switch stays on as long as you keep your finger on the touch plate. R1 sets the input impedance to a high 22 MΩ. Q1 picks up stray signals coupled through your body to the touch plate and amplifies them to turn on Q2, which turns on lamp drivers Q3 and Q4. Lamp I1 is any small 12-V lamp, such as a No. 53—12 V 120 mA. R4 and C1 add a small amount of hysteresis (delay) to keep the light from constantly flickering. A relay can be used for I1.

## TOUCH SWITCH

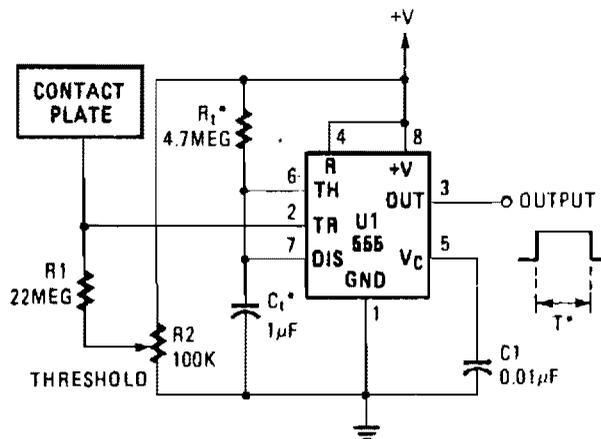

$$*T = 1.1R_1C_t$$

(CHOOSE  $R_1$  AND  $C_t$  FOR PULSE WIDTH GREATER THAN ANTICIPATED CONTACT TIME.)

**Fig. 112-9**

# 113


## Tracking Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Track and Hold  
Positive and Negative Voltage  
Reference Tracker  
Signal Track and Hold

## TRACK AND HOLD

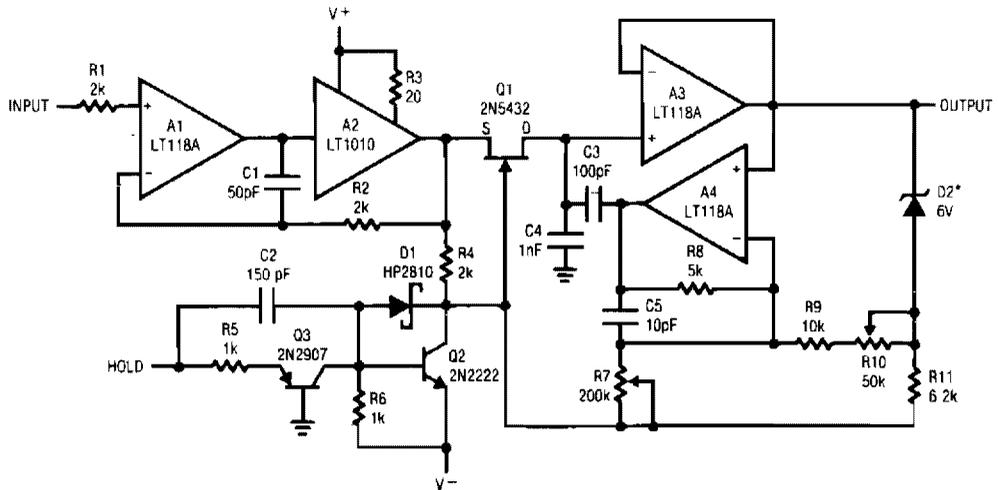

LINEAR TECHNOLOGY CORP.


\*2N2369 EMITTER BASE JUNCTION

Fig. 113-1

The 5-MHz track and hold shown here has a 400-kHz power bandwidth driving  $\pm 10$  V. A buffered input follower drives the hold capacitor, C4, through Q1, a low resistance FET switch. The positive hold command is supplied by TTL logic, with Q3 level shifting to the switch driver, Q2. The output is buffered by A3. When the gate is driven to V- for hold, it pulls the charge out of the hold capacitor. A compensating charge is put into the hold capacitor through C3. The step into hold is made independent of the input level with R7, and adjusted to zero with R10.

Since internal dissipation can be quite high when driving fast signals into a capacitive load, using a buffer in a power package is recommended. Raising the buffer quiescent current to 40 mA with R3 improves frequency response.
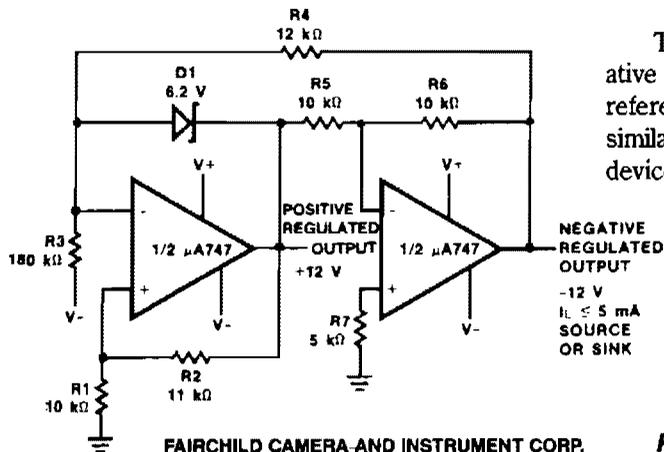
## POSITIVE AND NEGATIVE VOLTAGE REFERENCE TRACKER



FAIRCHILD CAMERA AND INSTRUMENT CORP.


Fig. 113-2

This reference uses an op amp to derive a negative output voltage that tracks with the positive reference voltage. A  $\mu A747$  dual op amp, or any similar device such as an LM1458 or two  $\mu A741$  devices, can be used.


$$\text{Positive Output} = V_{D1} \times \frac{R1 + R2}{R2}$$

$$\text{Negative Output} = -\text{Positive Output} \times \frac{R6}{R5}$$

## SIGNAL TRACK AND HOLD

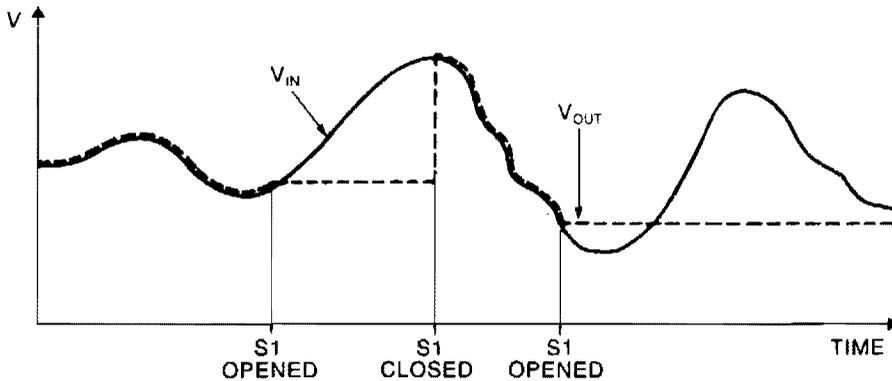

ML101B OR ANY LOW-LEVEL SWITCHING FET

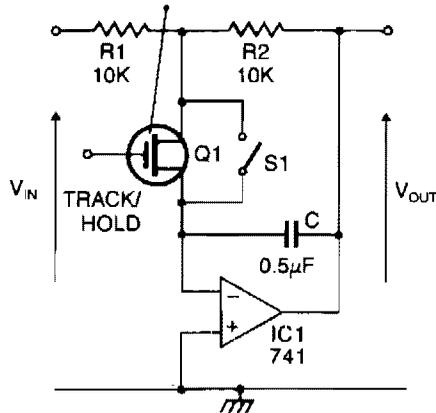

ELECTRONICS TODAY INTERNATIONAL

Fig. 113-3

When the switch is closed or the FET is conducting, the circuit behaves as an inverting amplifier with a gain of  $R2/R1$ . Since the inverting terminal of the op amp is a virtual ground, the capacitor is kept charged to the output voltage by the op amp. When the switch is opened and the FET is nonconducting, the voltage at the output is held constant by the capacitor, the current demands of the next stage are met by the op amp. The value of  $C$  should be chosen so that its impedance at the operating frequency is large compared to  $R1$  and  $R2$ .

# 114

## Transducer Amplifiers


---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Differential-to-Single-Ended Voltage  
Amplifier  
Equalized Preamp for Magnetic Phono  
Cartridges  
Photodiode Amplifier

Tape Playback Amplifier  
NAB Record Preamplifier  
Magnetic Phono Preamplifier  
Two-Pole NAB-Type Preamp  
Flat-Response Tape Amplifier
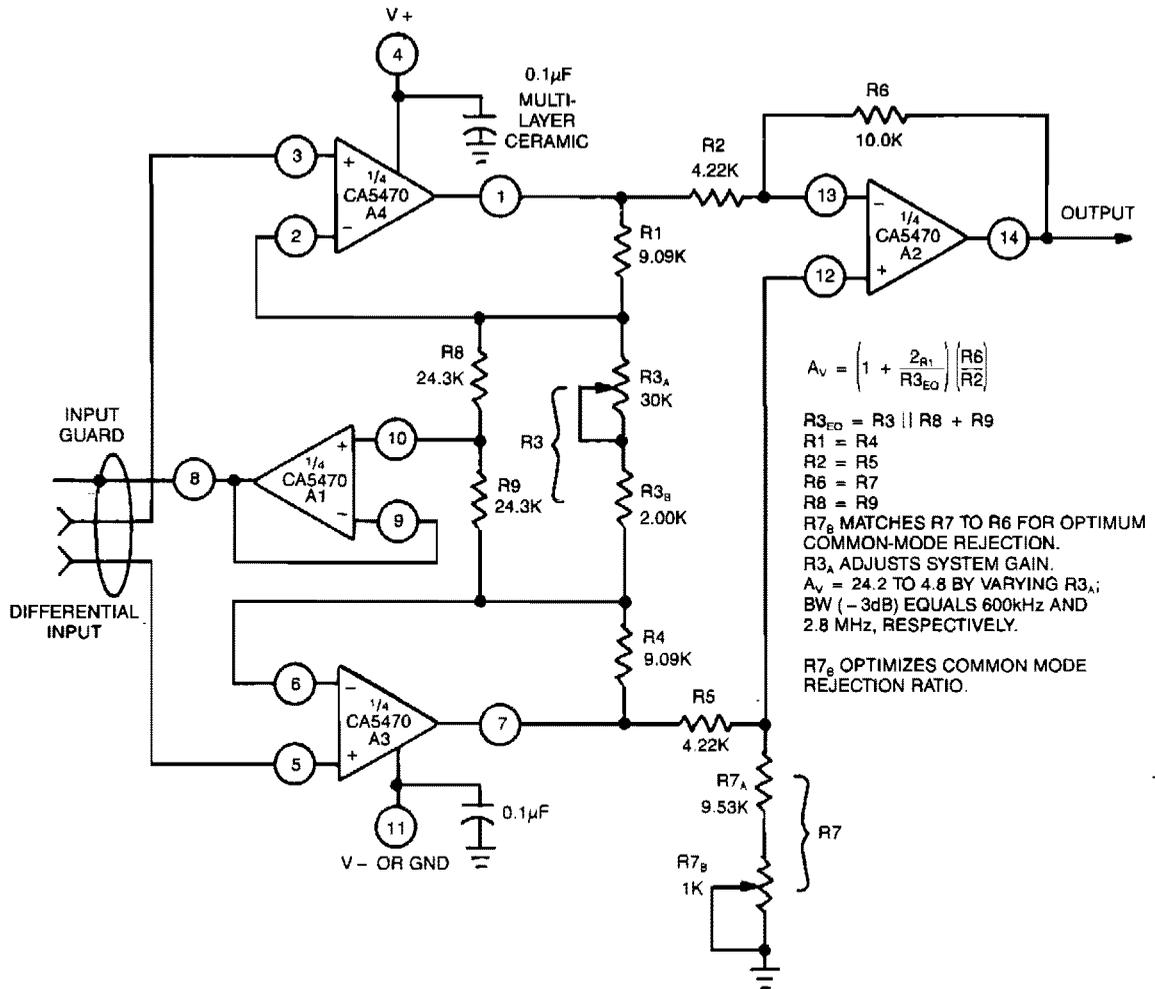
## DIFFERENTIAL-TO-SINGLE-ENDED VOLTAGE AMPLIFIER




GE/RCA

Fig. 114-1

This circuit uses a CA5470 quad microprocessor BiMOS-E op amp. Amplifiers A1 and A2 are employed as a cross-coupled differential input and differential output preamp stage and A3 provides input guard-banding. Amplifier A4 converts the differential outputs of A1 and A2 to a single-ended output.
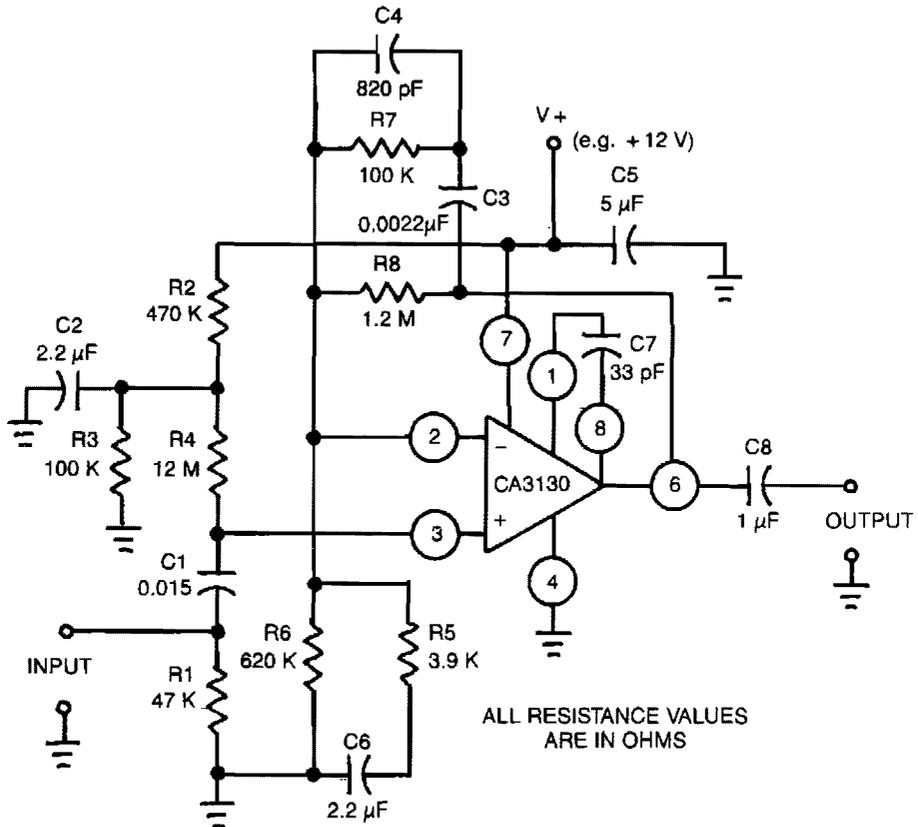
## EQUALIZED PREAMP FOR MAGNETIC PHONOGRAPH CARTRIDGES




GE/RCA

Fig. 114-2

This circuit uses a CA3130 BiMOS op amp. Amplifier is *equalized* to RIAA playback frequency-response specifications. The circuit is useful as preamplifier following a magnetic tapehead.



### NAB RECORD PREAMPLIFIER

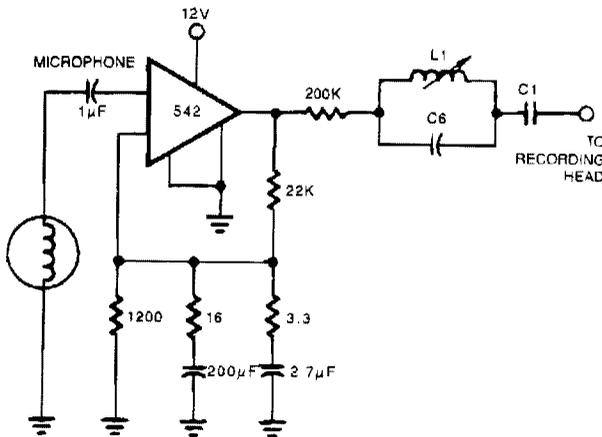


NOTE  
All resistor values are in Ω

SIGNETICS

Fig. 114-5


### TWO-POLE NAB-TYPE PREAMP

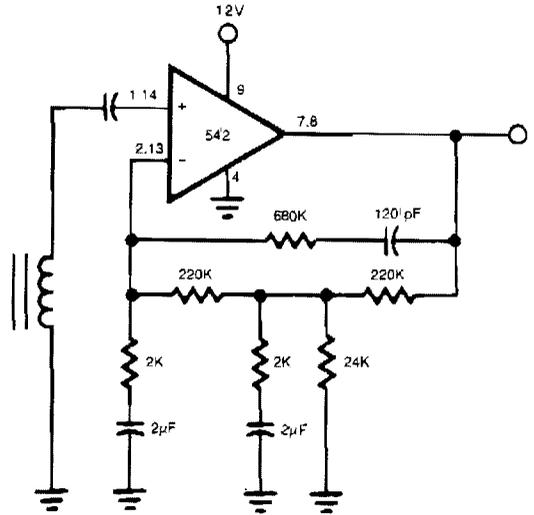

SIGNETICS

Fig. 114-7

### MAGNETIC PHONO PREAMPLIFIER

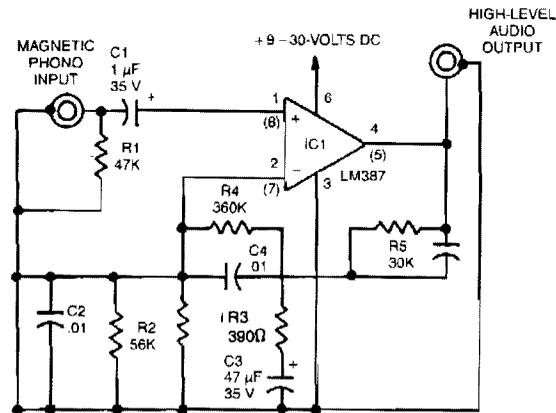


Reprinted with permission of Radio-Electronics Magazine, March 1986.  
Copyright Gernsback Publications, Inc., 1986.

Fig. 114-6

This simple stereo amplifier uses a National LM387IC. The pin numbers in parentheses are for one channel, and those not in parentheses are for the other channel. The supply voltage can be +9 to +30 Vdc at about 10 mA. The output voltage swing is about  $V_{CC} - 2$  V pk-pk. The preamp should be able to deliver at least 5 V.

### FLAT-RESPONSE TAPE AMPLIFIER

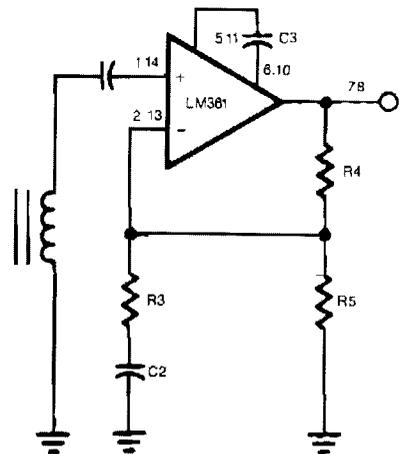

SIGNETICS

Fig. 114-8

# 115


## Transmitters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

80-M Amateur Radio Transmitter	Beacon Transmitter
TV Transmitter	40-M CW Transmitter
FM Voice Transmitter	VHF Modulator
1-W CW Transmitter	Wireless FM Microphone
Low-Cost Half-Duplex Information Transmission Link	902-MHz CW Transmitter
FM Snooper	One-Transistor FM Transmitter
VHF Tone Transmitter	FM Multiplex Transmitter
Low-Frequency Transmitter	QRP CW Transceiver
Wireless FM Microphone	Wireless FM Microphone

## 80-M AMATEUR RADIO TRANSMITTER

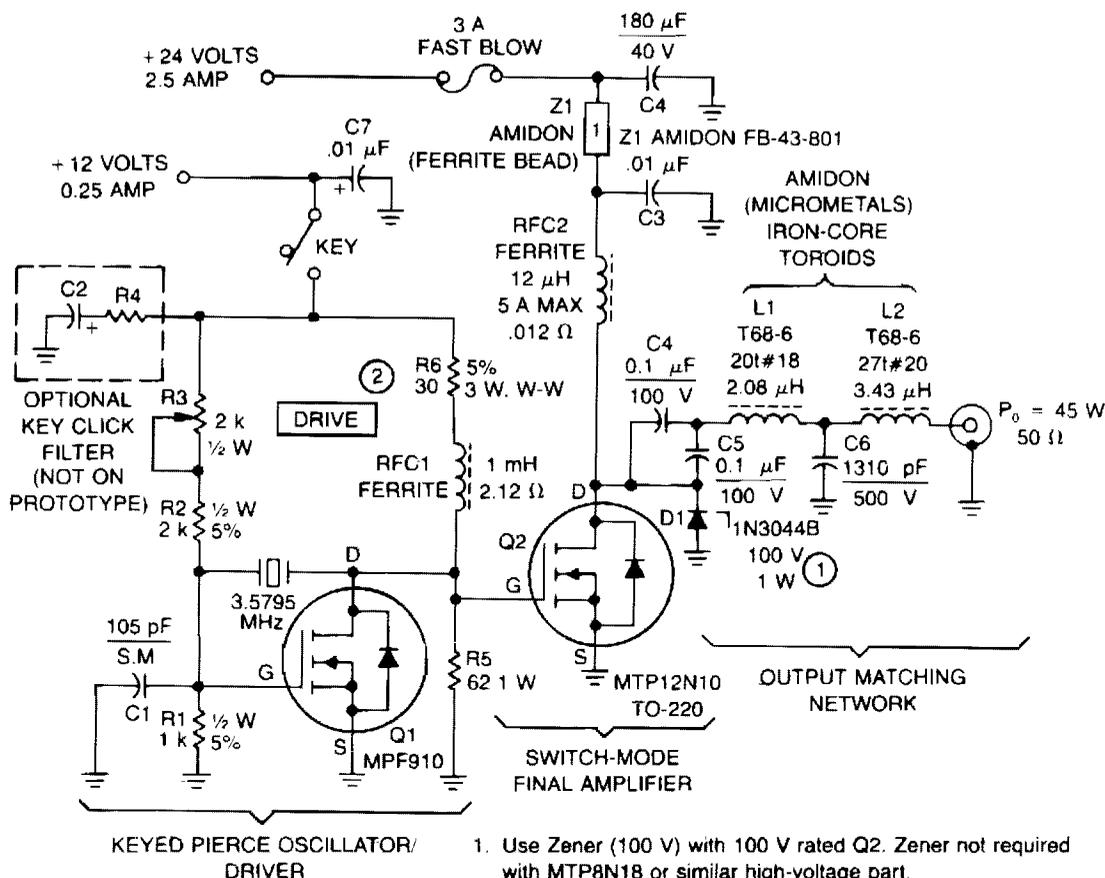

1. Use Zener (100 V) with 100 V rated Q2. Zener not required with MTP8N18 or similar high-voltage part.
2. Adjust DRIVE for minimum oscillation delay on keying.

Copyright of Motorola, Inc. Used by permission.


**Fig. 115-1**

This transmitter consists of a keyed crystal oscillator/driver and a high efficiency final, each with a TMOS Power FET as the active element. The total parts cost less than \$20, and no special construction skills or circuit boards are required.


The Pierce oscillator is unique because the high  $C_{RSS}$  of the final amplifier power FET, 700–1200 pF, is used as part of the capacitive feedback network. In fact, the oscillator will not work without Q2 installed. The MPF910 is a good choice for this circuit because the transistor is capable of driving the final amplifier in a switching mode, while still retaining enough gain for oscillation. To minimize cost, a readily-available color burst TV crystal is used as the frequency-determining element for Q1.

An unusual 84% output efficiency is possible with this transmitter. Such high efficiency is achieved because of the TMOS power FET's characteristics, along with modification of the usual algorithm for determining output matching.

## TV TRANSMITTER

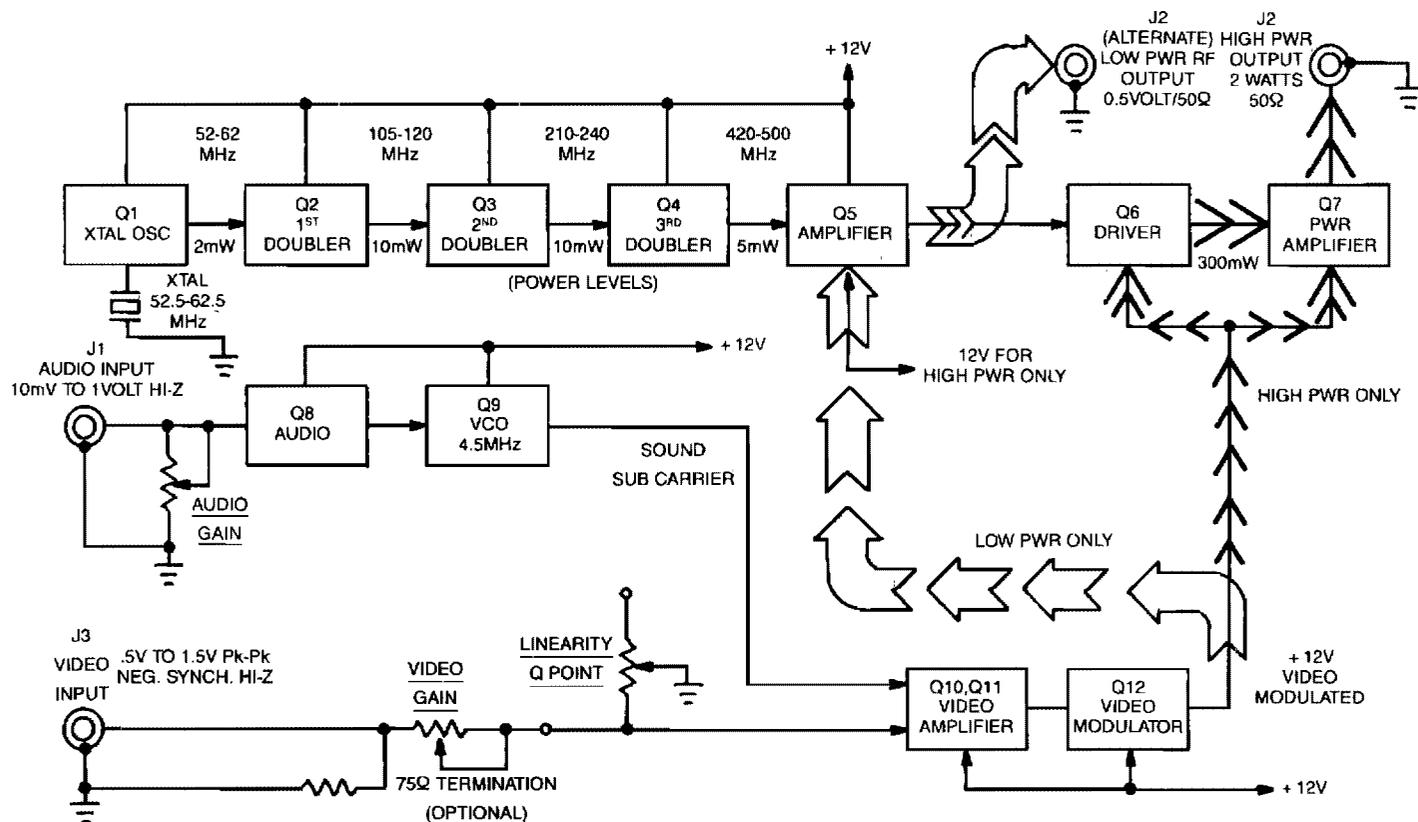

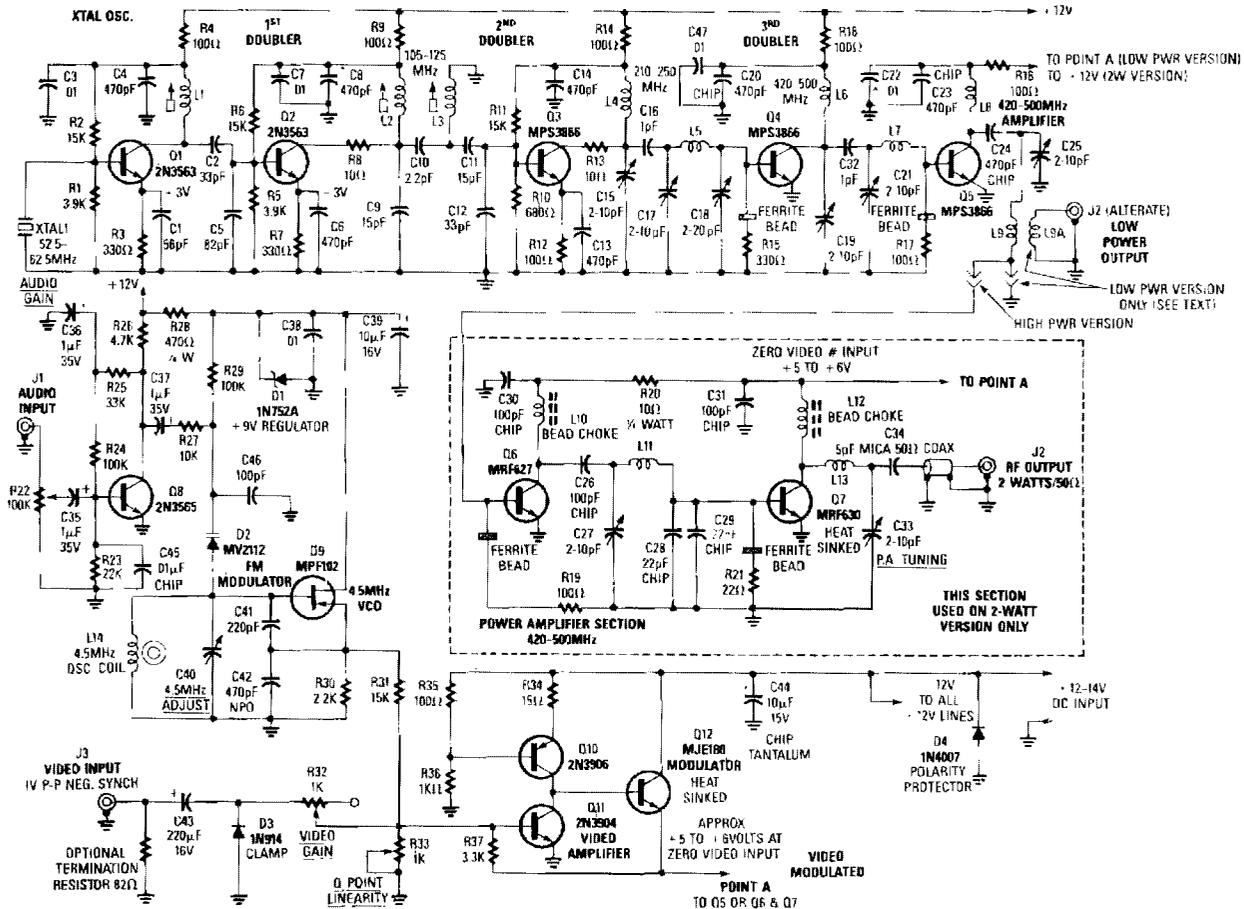This transmitter is capable of two levels of rf power. For low-power wireless video, like in a house or office, where simultaneous monitoring of program material is desirable without cumbersome hookups, 1 – 30 mW is available. For longer ranges up to several miles, as in amateur (ham) TV, security, and surveillance purposes, 2 W into a 50-Ω load is available.




Reprinted with permission from Radio-Electronics Magazine, June 1989. Copyright Gernsback Publications, Inc., 1989.

Fig. 115-2

The video-link transmitter accepts color and B/W video, and audio inputs from VCRs, camcorders, small TV cameras, and microphones. The unit runs on a nominal 12 Vdc and draws 100 mA in the low-power version, or 500 mA in the 2-W version. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.
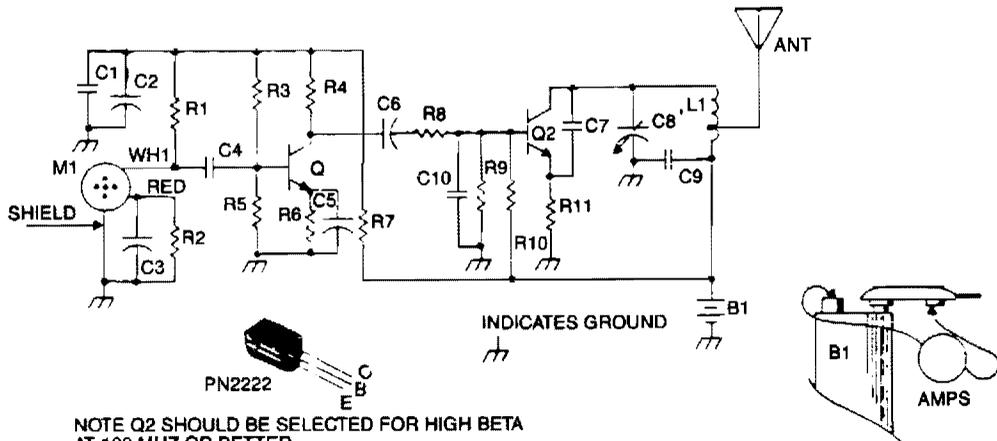
## FM VOICE TRANSMITTER

C1, C2 AND R7-DO NOT USE UNLESS  
FEED BACK INSTABILITY OCCURS  
NOT SHOWN ON FIG. 20-2




NOTE Q2 SHOULD BE SELECTED FOR HIGH BETA  
AT 100 MHZ OR BETTER

TAB BOOKS

Fig. 115-3

This is a sensitive, mini-powered FM transmitter consisting of an rf oscillator section interfaced with a high-sensitivity wide passband audio amplifier and capacitance microphone with built-in FET that modulates the base of the rf oscillator transistor. The setting of C8 determines the desired operating frequency—in the standard FM broadcast band, tuned to favor the high end up to 110 MHz. Capacitor C7 supplies the necessary feedback voltage developed across R11 in the emitter circuit of Q2, sustaining an oscillating condition. Resistors R9 and R10 provide the necessary bias of the base-emitter junction for proper operation, and capacitor C10 bypasses any rf to ground fed through to the base circuit. C9 provides an rf return path for the tank circuit of L1 and C8, while blocking the dc supply voltage fed to the collector of Q2. The speech voltage developed across R1 by M1 is capacitively coupled by C4 to the base of Q1. A signal voltage developed across R4 is capacity-coupled through C6 to the base of Q2 through R8. R7 and R8, along with C1 and C2, decouple the oscillator and audio circuits.

## 1-W CW TRANSMITTER

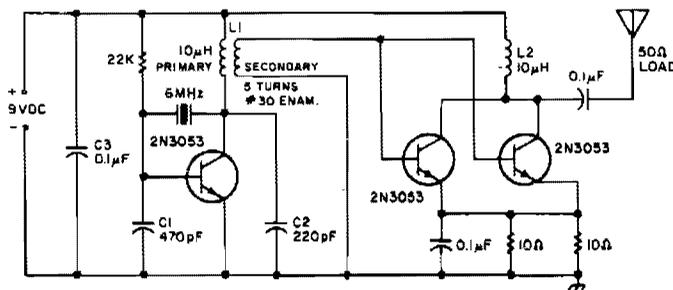

73 AMATEUR RADIO


Fig. 115-4


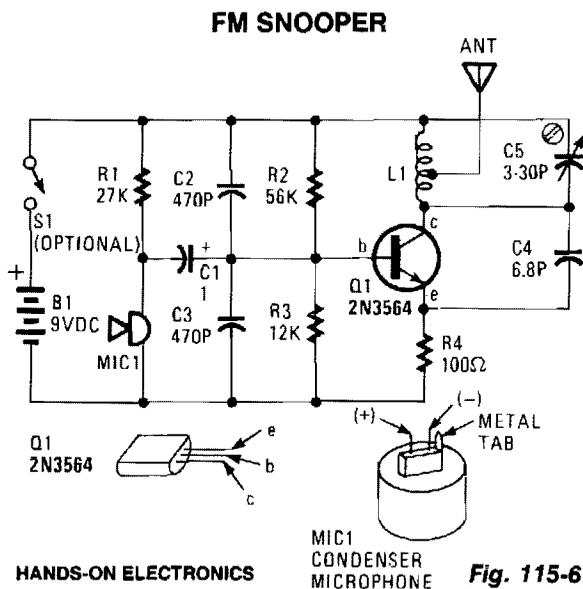
## LOW-COST HALF-DUPLEX INFORMATION TRANSMISSION LINK (Cont.)

In a half-duplex system, information can flow in both directions, but only one direction at any given time. The conventional method of building a half-duplex link requires a separate emitter and detector, connected with directional couplers, at each end of the fiber. The GFOE1A series of infrared emitting diodes are highly efficient, long-lived emitters, which are also sensitive to the 940 nm infrared they produce. Biased as a photodiode, they exhibit a sensitivity of about 30 nA per  $\mu\text{W}$  irradiation at 940 nm. In a suitable bias and switching logic network, they form the basis for a half-duplex information link. A half-duplex link, illustrating the emitter-detector operation of the GFOE1A1, is shown.

This schematic represents a full, general purpose system, including: approximately 50-dB compliance range with 1-V rms output, passive receive, voice-activated switching logic, 100 Hz to 50 kHz frequency response, and inexpensive components and hardware. The system is simple, inexpensive, and can be upgraded to provide more capability through use of higher gain bandwidth amplifier stages. Conversely, performance and cost can be lowered simply by removing undesired features.



The FM Snooper is an FM transmitter that radiates a continuous wave whose frequency is altered according to the sound waves striking the microphone. An ordinary FM broadcast receiver detects the transmitter's output carrier. When 9-V battery, B1, is connected, a brief surge of current flows from the collector to the emitter of Q1, causing an alternating current, shock oscillation in the resonant LC circuit, to flow back and forth between L1 and C5. So, by varying the value of C5, you can tune the oscillations to the exact frequency desired.

Although tuning capacitor C5 accounts for the major part of the tuning capacitance, the capacitance between the base and the collector of Q1 has a small, but noticeable, effect on the oscillation frequency. That capacitance, which is known as the *junction capacitance*, is not a fixed value, but instead varies when the voltage on the base of the transistor varies. Sound waves striking the microphone induce a voltage that varies in time with the sound. That voltage is applied via C1 to the base of Q1, thereby frequency modulating the transmitter.

## VHF TONE TRANSMITTER

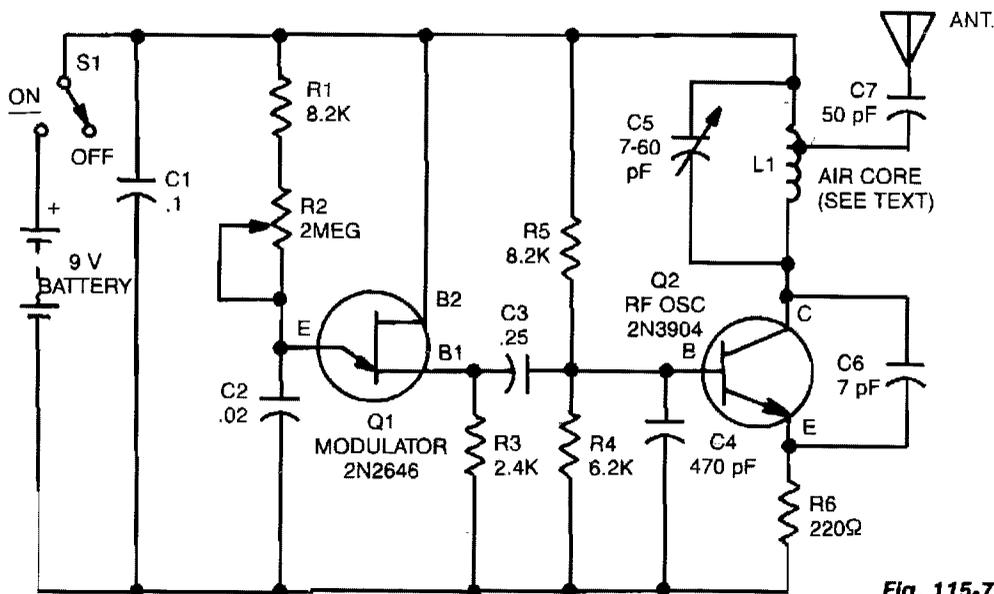


Fig. 115-7

Reprinted with permission of Radio-Electronics Magazine, 1987 R-E Experimenters Handbook. Copyright Gernsback Publications, Inc., 1987.


The range of this transmitter is about 50 feet with a short whip antenna. The tone generator, is made up of a unijunction transistor, Q1, and R1, R2, R3, and C2. Transistor Q1 pulses on and off at a rate determined by the time constant of R1 and R2, together with the capacitance of C2 and the B1-emitter junction of Q1. Trimmer potentiometer R2 determines the frequency of the tone generated and allows a range of approximately 100 Hz to over 5 kHz.

Transistor Q2 is the rf oscillator. Its frequency is set by tuned circuits consisting of L1, C5, C6, and the interelectrode capacitance of Q2. The values shown will give a tuning range of about 55 to 108 MHz. Capacitor C6 provides positive feedback from the emitter to the collector of Q2, for oscillation. The audio tone generated by Q1 is applied to the base of Q2, causing the collector current to vary at the frequency of the tone, yielding an amplitude-modulated (AM) signal. This, in turn, varies Q2's collector-to-emitter capacitance, which makes up part of the tuned circuit, and causes the output frequency to vary similarly, producing a frequency-modulated (FM) signal, as well. The rf signal is coupled to the antenna through capacitor C7.

Coil L1 consists of five turns of #18 bare wire, close-wound on a piece of 1/4-inch wooden dowel. The length of the winding is about 1/4 inch. One end of capacitor C7 is soldered to the coil, one turn away from the 9-V supply end, and the other capacitor end is connected to the antenna. To adjust the vertical height and linearity of a TV set, place the tone transmitter near the set and use R2 to select the number of horizontal bars to be displayed. Once the picture is steady and the bars are sharp, adjust the set's vertical controls, so that all the bars are of the same height and are evenly spaced.

The fact that both AM and FM signals are generated makes it possible to use this circuit to check almost any receiver within the transmitter's frequency range. A TV set's sound section (discriminator) will reject the AM portion of the signal, but its video section will respond to it. Similarly, the TV sound section and FM receivers will respond to the FM signal produced.

## LOW-FREQUENCY TRANSMITTER

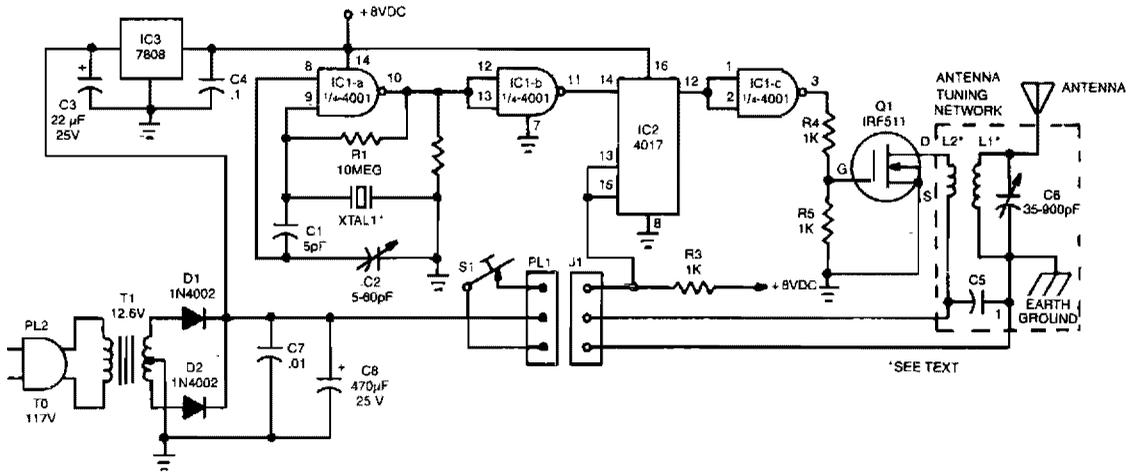


Reprinted with permission of Radio-Electronics Magazine, September 1989. Copyright Gernsback Publications, Inc., 1989.

**Fig. 115-8**

The crystal oscillator, which uses two sections of IC1, a 4001 quad 2-input NOR gate, is a standard and reliable design. The oscillator's 1.85-MHz, square-wave output feeds IC2, a 4017 divide-by-10 counter. The count enable and reset terminals, pins 13 and 15, are normally held high by resistor R3, and the counter is activated by bringing those pins low by closing telegraph key S1—an arrangement that guarantees that the final state of IC2 pin 12 is always high. The high on IC2 pin 12 is inverted by a third section of the 4001, IC1c, to prevent dc current flow through power amplifier Q1 during key-up periods.

## WIRELESS FM MICROPHONE

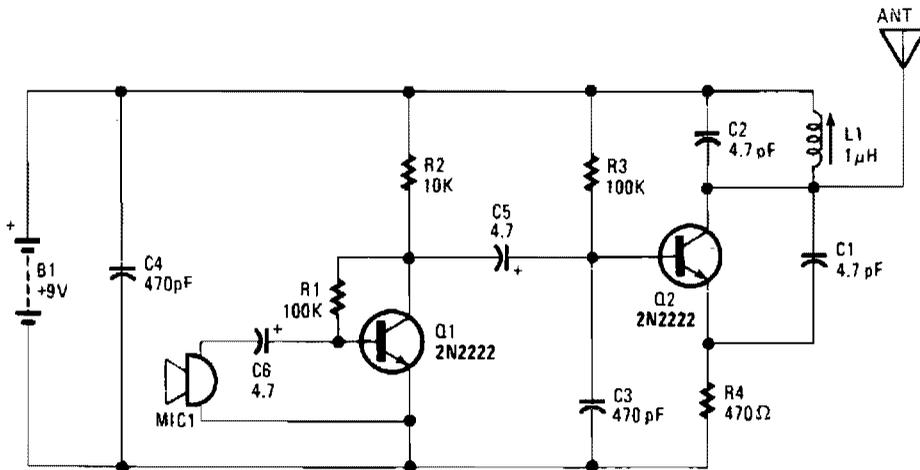


POPULAR ELECTRONICS

**Fig. 115-9**

## WIRELESS FM MICROPHONE (Cont.)

Transistor Q1 acts as an amplifier for condenser microphone MIC1. The output of Q1 is applied to the base of transistor Q2 through a  $4.7\text{-}\mu\text{F}$  capacitor. C2 and L1 form an LC tank circuit, which is used to set the frequency at which the transmitter operates. Coil L1 is a variable inductor, centered a bit below  $1\ \mu\text{H}$ , that is used to adjust the modulating frequency of the circuit. Capacitors C1 and C2 are  $4.7\ \text{pF}$  units. A lower value can be used to raise the circuit's operating frequency. The microphone and Q1 provide a varying voltage at the base of Q2, with the output of Q2 applied to the LC tank circuit. That causes a modulating action in the tank circuit that, when applied to the antenna, a short piece of wire 6- to 8-inches long, will provide a good, clear FM signal somewhere in the range of 88 to 95 MHz with a range of about 100 feet.

## BEACON TRANSMITTER

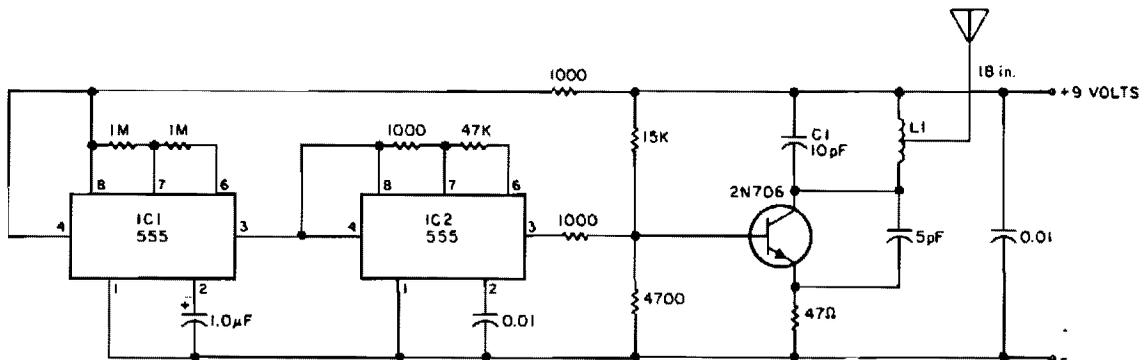

73 AMATEUR RADIO

Fig. 115-10

This transmitter can be used for transmitter hunts, for remote key finding, or for radio telemetry in model rockets. It can be tuned to the two meter band or other VHF bands by changing C1 and L1. L1 is four turns of #20 enameled wire airwound, 0.25 inch in diameter (use a drill bit), 0.2 inch long, center-tapped. The antenna can be 18 inches of any type of wire. IC2 functions as an audio oscillator that is turned on and off by IC1 about once per second. The range of the transmitter is several hundred yards.

### 40-M CW TRANSCEIVER


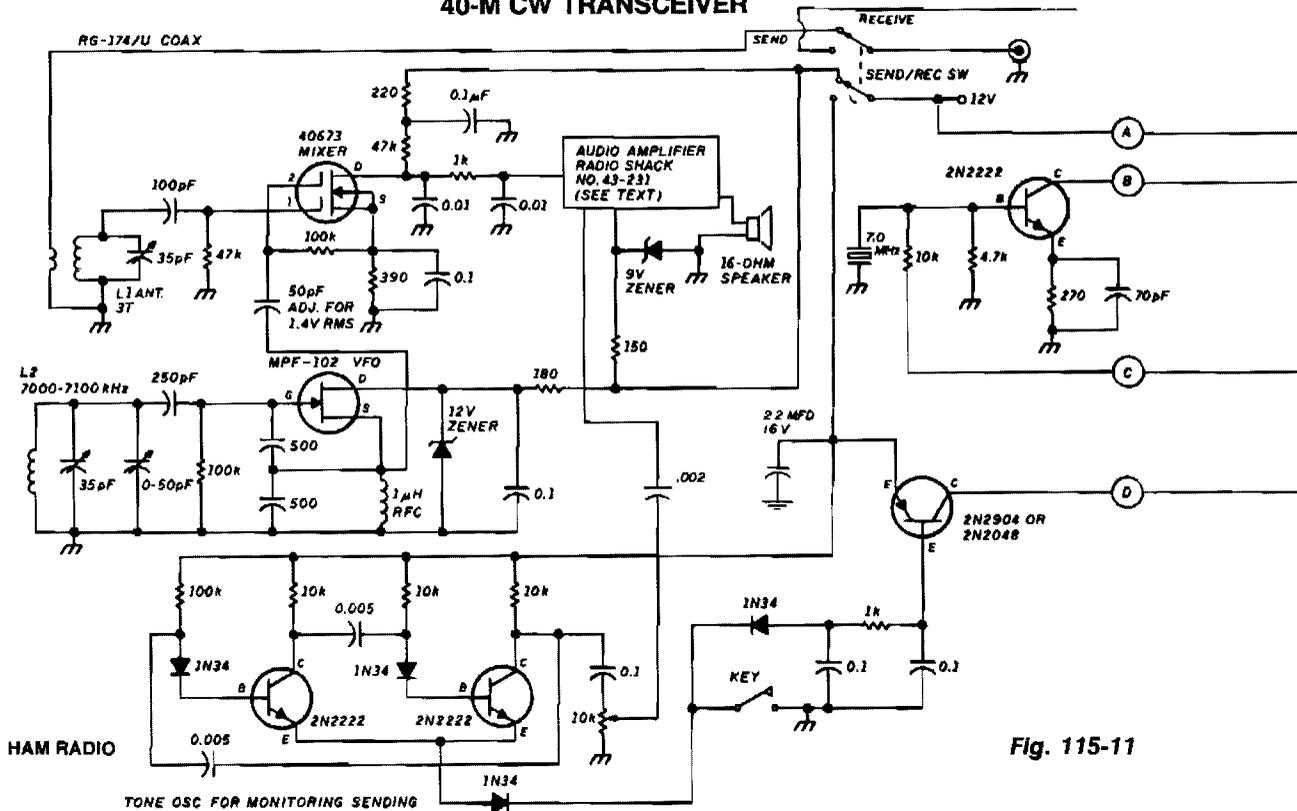


Fig. 115-11

### VHF MODULATOR

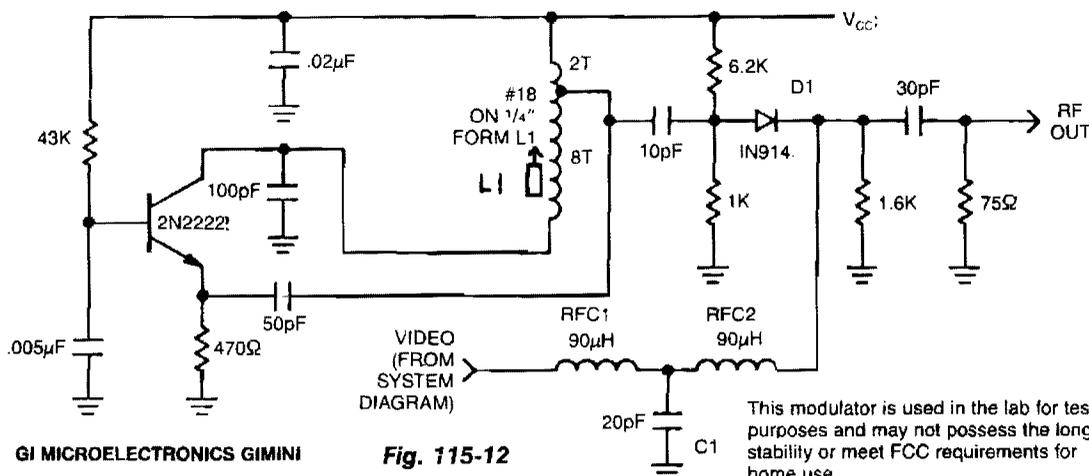


GI MICROELECTRONICS GIMINI

Fig. 115-12


This modulator is used in the lab for test purposes and may not possess the long-term stability or meet FCC requirements for home use.

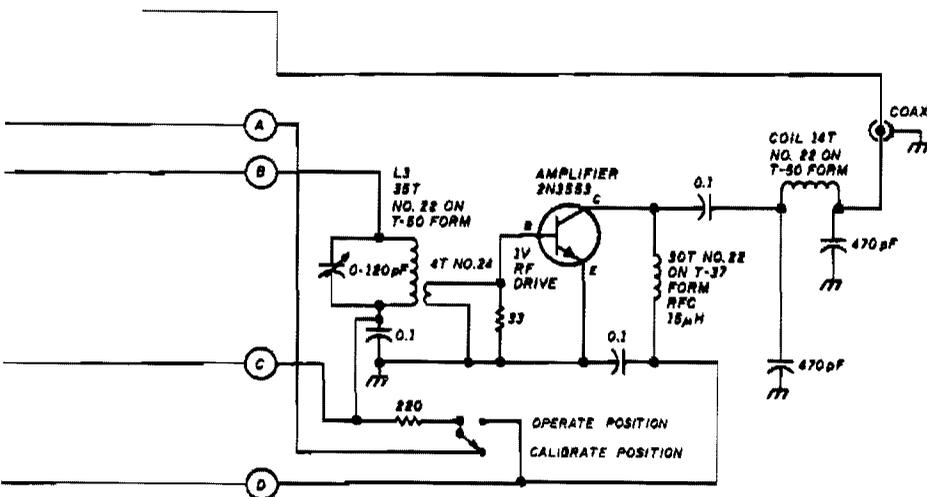This circuit uses an oscillator (2N2222) and a diode D1 as a nonlinear mixer. The frequency is set by a slug in L1. RFC1, C1, and RFC2 form a low-pass filter to pass video and block rf from the video source.



The unit consists of a direct conversion receiver and 1-W transmitter. The direct conversion receiver VFO is tuned just off frequency from the incoming signal. This difference in frequency produces a clean, strong, and solid audio tone signal. Detect the resonant frequency of the transmitter VFO by using the GDO as a field-strength meter.

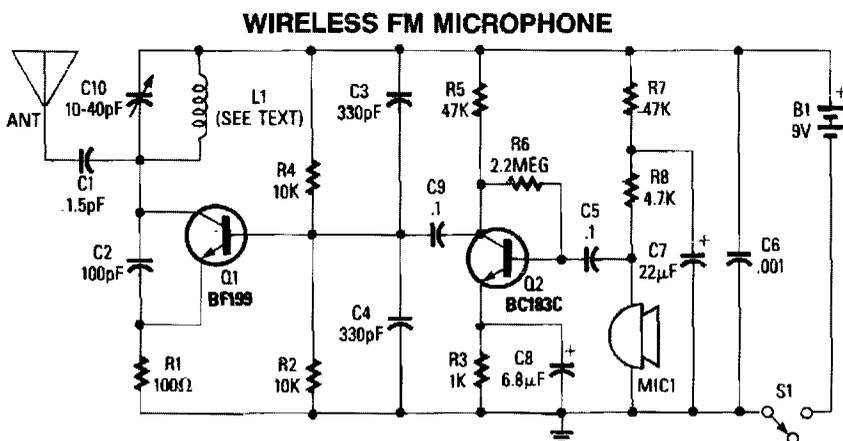Because of the large capacitance in the Colpitts VFO, the tuning coil will have fewer turns than the mixer coil. Use the capacitance shown for the VFO gate to ground and to the coil. It will effect the frequency and output. You'll need 1.4-V rms on pin 2 of the mixer to get a good signal from the VFO. The 1000-Ω resistor and 0.01-μF capacitors act as an rf filter from the mixer output.



Reprinted with permission from Radio Electronics Magazine, March 1989. Copyright Gernsback Publications, Inc., 1989.

Fig. 115-13

Adjustable capacitor C10, and coil L1 form a tank circuit that, in combination with Q1, C2, and R1, oscillates at a frequency on the FM band. The center frequency is set by adjusting C10. An electret microphone, M1, picks up an audio signal that is amplified by transistor Q2. The audio signal is coupled via C9 to Q1, which frequency modulates the tank circuit. The signal is then radiated from the antenna. The circuit can operate from 9–12 Vdc.

## 902-MHz CW TRANSMITTER

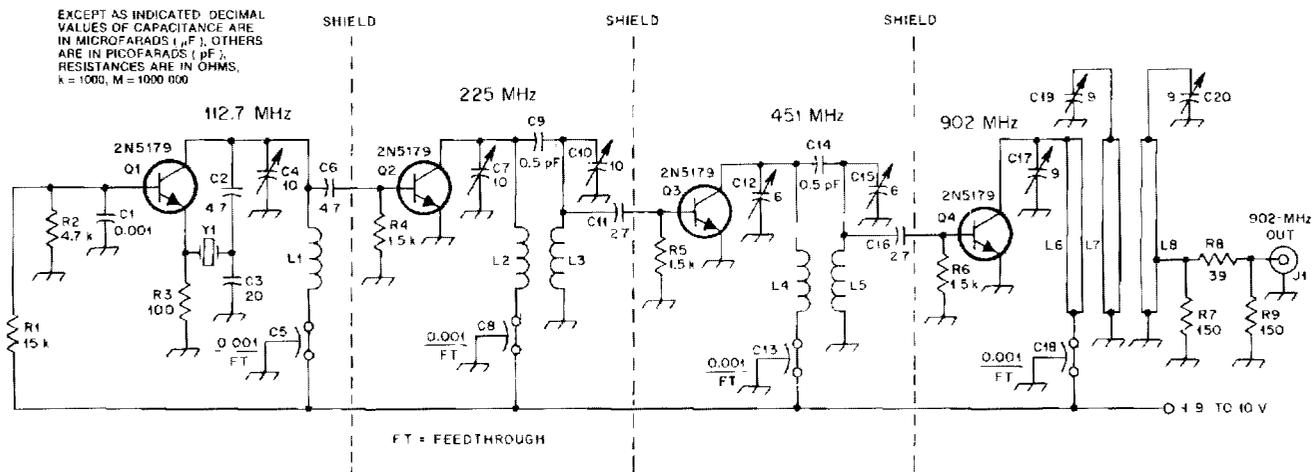


Fig 2—Schematic diagram of the exciter. Resistors are  $\frac{1}{4}$ -W carbon composition. Capacitors are 50-V epoxy-coated ceramic types unless otherwise noted.

C4, C7, C10—1.5-15 pF miniature air-variable capacitor (Trim-tronics 10-1120-25015-000 or equiv).

C5, C8, C13, C18—470- to 1000-pF ceramic feedthrough capacitor, solder-in type preferred.

C9, C14—0.5-pF "gimmick" capacitor (see text).

C12, C15—1.6 pF miniature air-variable capacitor (Trim-tronics 10-1120-25006-000 or equiv).

## QST

C17, C19, C20—0.6-9 pF ceramic piston trimmer capacitor (Voltronics EQT9 or equiv).

J1—Chassis-mount female BNC connector (UG-1094 or equiv).

L1—5t no. 22 tinned wire, 0.228-in ID (no. 1 drill), spaced 1 wire dia.

L2, L3—4t no. 18 tinned wire,  $\frac{1}{4}$ -in ID, spaced 1 wire dia.

L4, L5—2t no. 18 tinned wire,  $\frac{1}{4}$ -in ID,

spaced 1 wire dia.

L6, L7, L8—Inductor made from copper strap, 1-in long  $\times$   $\frac{1}{8}$ -in wide. See text and Fig 3 for details.


Q1-Q4—2N5179 transistor.

Y1—Fifth-overtone crystal, 80.545 MHz, or seventh-overtone crystal, 112.763 MHz, HC-25 holder, series resonant, 0.005% (avail from JAN Crystals, 2400 Crystal Dr, Ft Meyers, FL 33906 tel 800-237-3063).

Fig. 115-14

The oscillator, Q1, is a standard overtone circuit. A fifth-overtone crystal, 80.545 MHz, is operated on the seventh overtone, 112.763 MHz. C6 couples the output of the oscillator to Q2, which operates as a doubler to 225.5 MHz. A double-tuned circuit using C7, L2, L3, C10 is used in the collector of Q2 to reduce the level of the 112-MHz oscillator signal. The output of Q2 is capacitively coupled at C11 to the base of Q3. The double-tuned circuit in the collector of Q3 with C12, L4, L5, C15, is tuned to 451 MHz. A small capacitance, 2.7 pF, couples the 451-MHz signal to the base of another 2N5179, Q4, which doubles the signal to 902 MHz. The output of the 902-MHz doubler has a triple-tuned circuit using C17, L6, C19, L7, C20, L8 in its collector.

## A ONE-TRANSISTOR FM TRANSMITTER

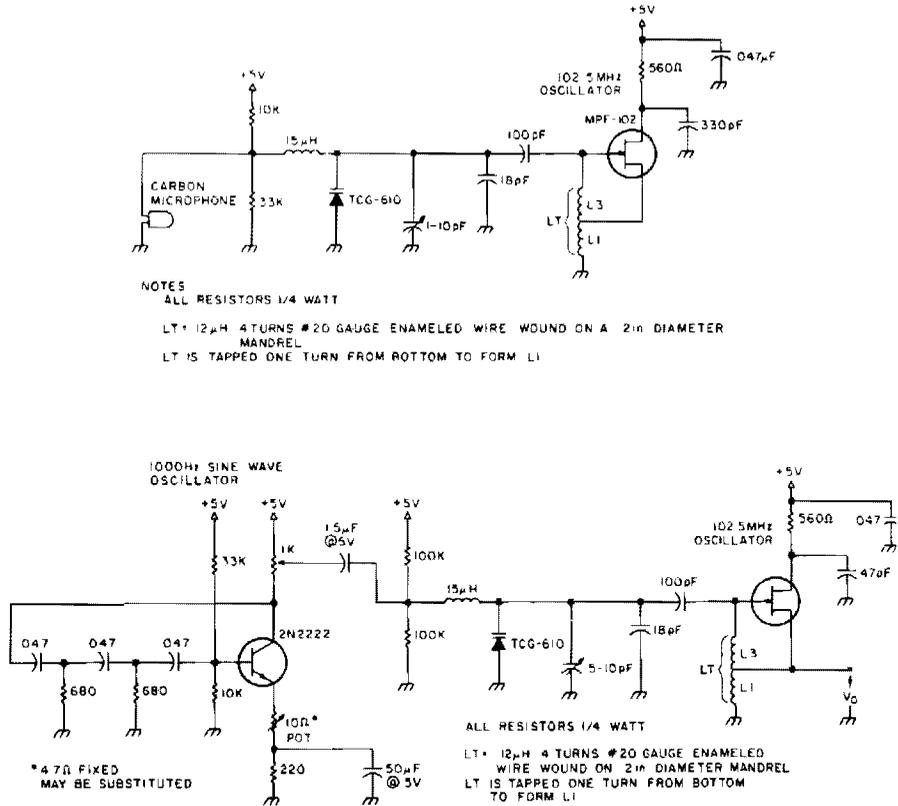


73 AMATEUR RADIO

Fig. 115-15


The 2N2222 circuitry is a three-element, phase-shift oscillator circuit, designed to yield a 1,000-Hz sine wave. The 1,000-Hz sine wave is then applied to the TCG-610 varactor diode, 6 pF at 4 V, which changes the tank capacitance, thus varying the rf oscillator frequency at a 1,000-Hz rate. The 1,000-Ω potentiometer in the collector circuit can be adjusted to enable the desired frequency modulation level.

The Hartley rf oscillator, designed around a readily available MPF-102 JFET, has an output that should be relatively stable if it is enclosed in a metal box, thus minimizing changes in tank capacitance. The completed transmitter has a range of 30 feet when not enclosed—without an antenna.

## FM MULTIPLEX TRANSMITTER


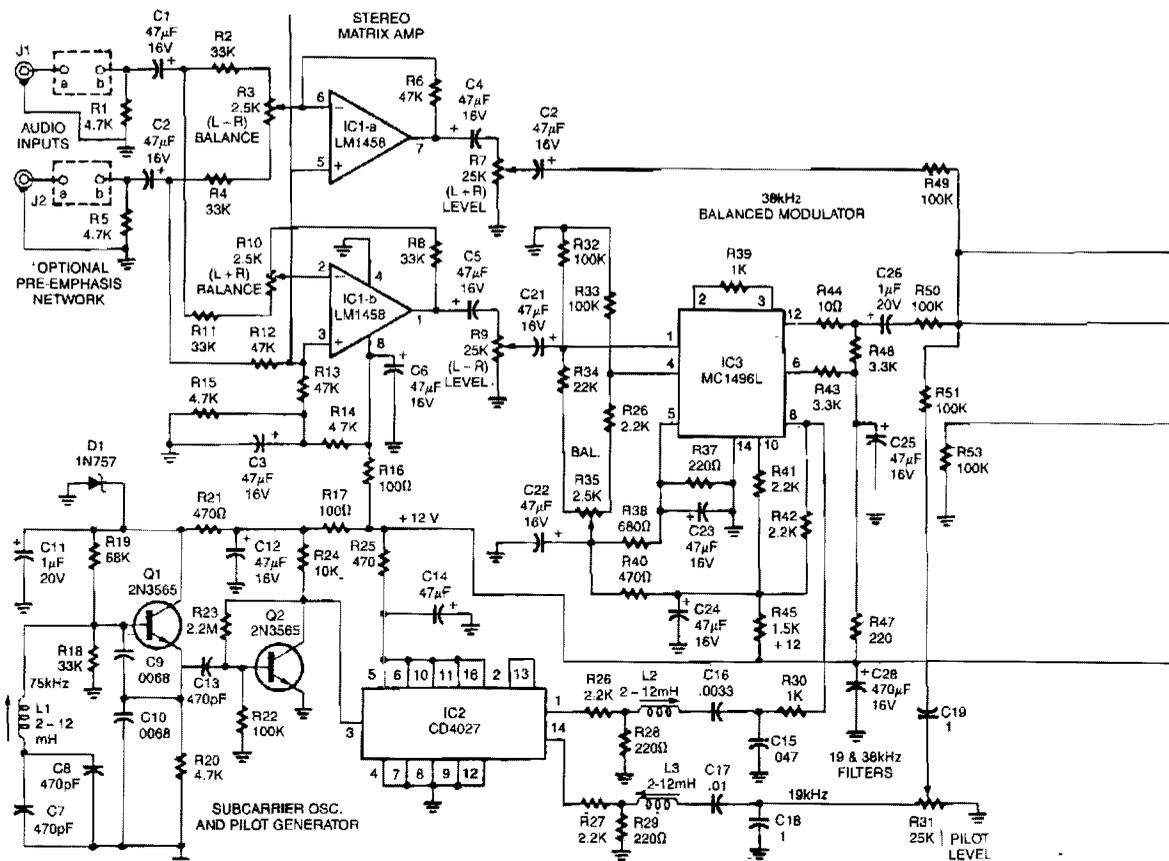


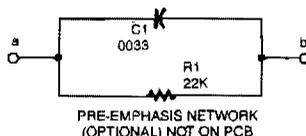THIS STEREO FM TRANSMITTER is capable of transmitting a stereo signal up to a hundred feet.



THIS PRE-EMPHASIS NETWORK can be added to the audio inputs of the MPX transmitter, if necessary.

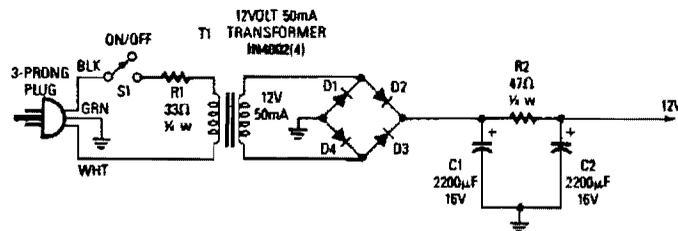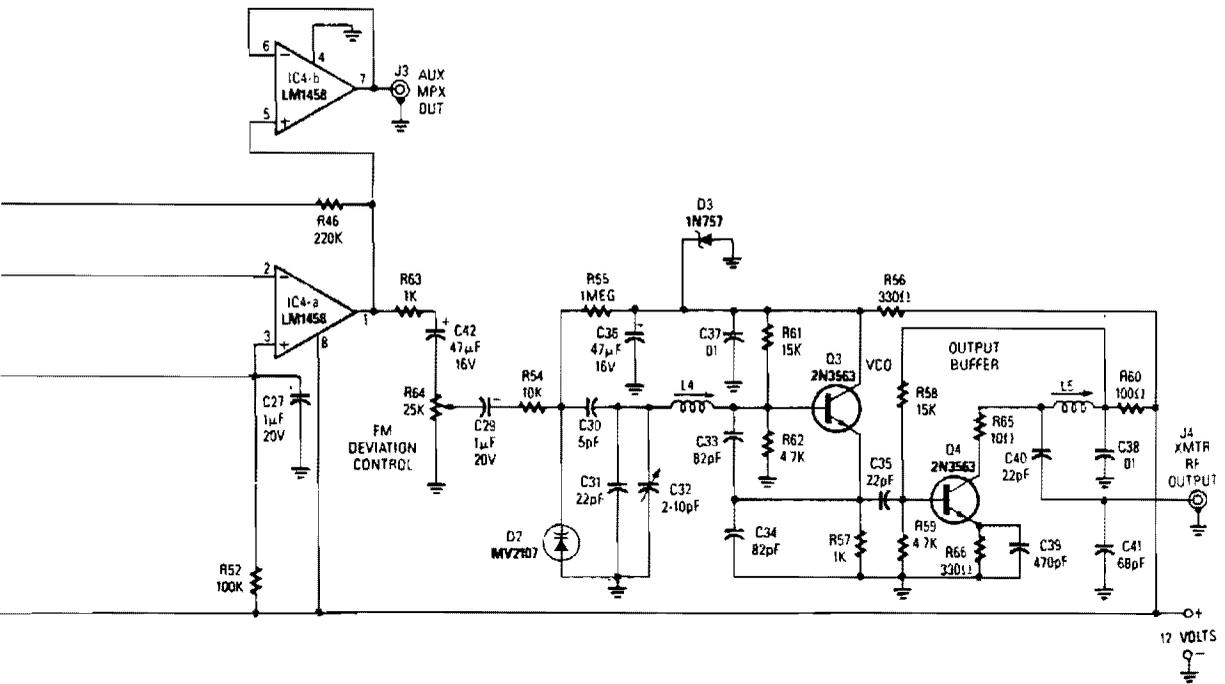Reprinted with permission from Radio-Electronics Magazine, March 1988. Copyright Gernsback Publications, Inc., 1988.



THIS POWER SUPPLY can be used if you do not want to power the transmitter with batteries.

This transmitter has a range of up to 100 feet. It generates a complete multiplex stereo signal and is useful for cordless headphone applications in which an inexpensive socket stereo receiver can be used. It can also be used as an FM multiplex generator for receiver alignments. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.

# QRP CW TRANSCEIVER

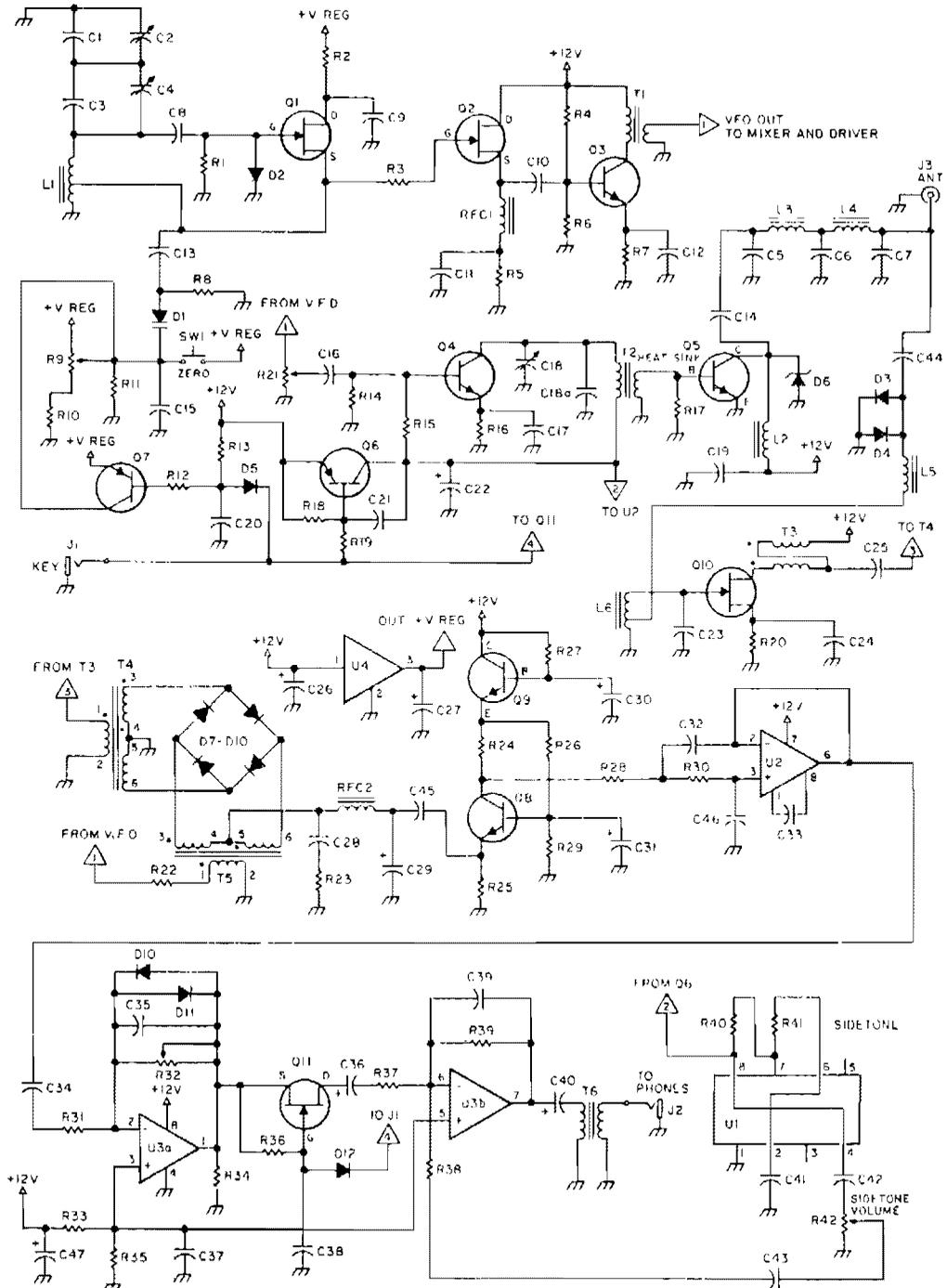



Fig. 115-17

## QRP CW TRANSCEIVER (Cont.)

This is a 3-W, single-circuit board, VFO-controlled CW transceiver for 40 or 30 meters, featuring a direct-conversion receiver with audio filtering, Receiver Incremental Tuning (RIT), and speaker level audio volume. The transmit frequency is generated by Q1 and its associated components in the VFO. The buffer, Q2, isolates the oscillator from the other circuitry to help keep the VFO stable. Q3 builds up the signal to a more usable level. The driver, Q4, amplifies the signal. The final, Q5, amplifies it to the 3-W level.

Key the transmitter by turning the power to the driver on and off, using Q6 as a switching transistor. Select the frequency by varying the tuning capacitor, C2. The VFO frequency feeds into the diode-ring mixer, and is mixed with the incoming 7- or 10-MHz signal. The *difference*, or *produce*, is the audio frequency. The post-mixer circuitry amplifies the audio signal to speaker level: Q8 preamplifies the signal a little, U2 is an audio filter that attenuates the audio signals above about 700 Hz, and U3 amplifies the signal from the audio filter to listening level.

## WIRELESS FM MICROPHONE

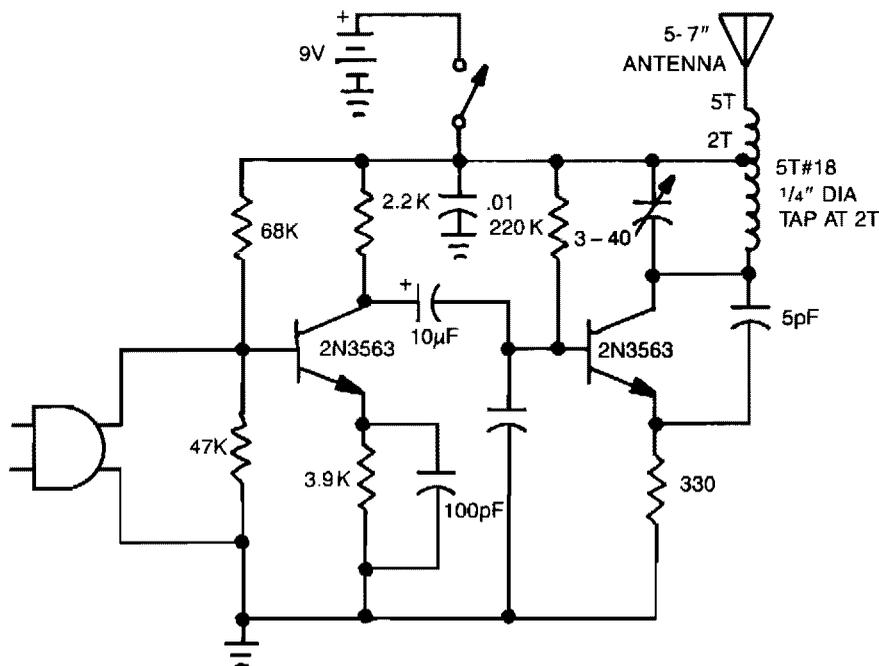

Reprinted with permission of William Sheets.

Fig. 115-18

Use standard rf wiring precautions. The best speech clarity is obtained by using an electret microphone. For music reproduction, substitute a dynamic mike element.

# 116

## Tremolo Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.


Tremolo  
Tremolo  
Electronic Tremolo  
Tremolo



## TREMOLO (Cont.)

A phase shift oscillator using the LM324 operates at an adjustable rate, 5–10 Hz, set by the speed pot. A portion of the oscillator output is taken from the depth pot and used to modulate the on resistance of two 1N914 diodes operating as voltage controlled attenuators. Care must be taken to restrict the incoming signal level to less than 0.6 V pk-pk, or undesirable clipping will occur.

### ELECTRONIC TREMOLO

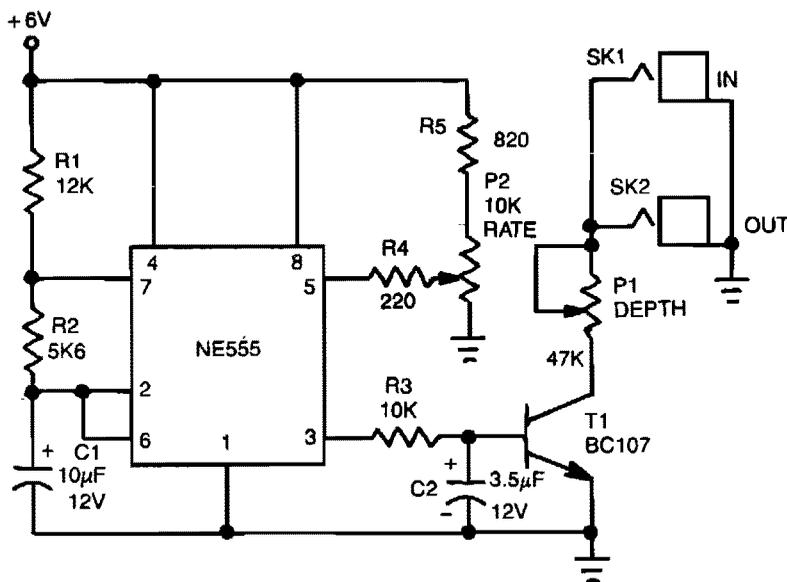


ELECTRONIC ENGINEERING

Fig. 116-3

The tremolo effect is generated by a repeating volume change at a rate usually between 1 and 15 Hz. The timer produces a low frequency square wave that is smoothed by a simple rc integrator. This varying signal modulates the signal input from the instrument. Transistor T1 is used as a voltage controlled resistor. The output of the circuit is connected in parallel to the output of the instrument. Potentiometer P1 provides depth control by adjusting the amplitude of the modulating waveform applied to the instrument. The rate control frequency is set by potentiometer P2.

## TREMOLO

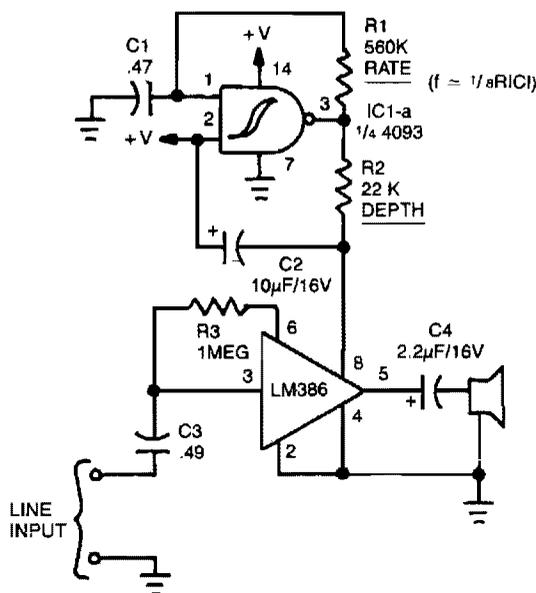

Reprinted with permission of Radio-Electronics Magazine, September 1985.  
 Copyright Gernsback Publications, Inc., 1985.

**Fig. 116-4**

This simple circuit can color the sound coming from your audio system. Clocking for the circuit is provided by an oscillator built from one quarter of a 4093 quad NAND Schmitt trigger. With the component values shown, it will run at about 5 Hz. The clock frequency is fed to the gain control, pin 8, of an LM386 amplifier. Tremolo is produced by varying the amplifier gain. A trimmer potentiometer can be put in series with R1, to easily experiment with different rates. To experiment, make R1 about 100-K $\Omega$  and use a 1-M $\Omega$  trimmer. That allows frequencies from about 2 to 20 Hz to pass. Resistor R2 is the depth control. It controls the degree of tremolo. To adjust, put a trimmer in series with R2. Make R2 a 5-K $\Omega$  unit and use a 50-K $\Omega$  trimmer. Since the tremolo clock uses the gain-control pin of the amplifier, change the value of capacitor C4 in order to change the gain of the amplifier. Make C4 larger to increase the gain or smaller to decrease it. But, don't go any lower than 0.1  $\mu$ F because you'll be cutting into the bottom-end frequency response.

# 117


## Ultrasonics

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Ranging System	120-kHz 500-W Induction Heater
Ultrasonic Receiver	Ultrasonic Transceiver
Ultrasonic Pest-Repeller	Ultrasonic Receiver
20-kHz Arc Welding Inverter	Ultrasonic-Pulsed Pest Controller
Ultrasonic Transceiver	Ultrasonic Pest Controller
Sonar Transducer/Switch	

## RANGING SYSTEM

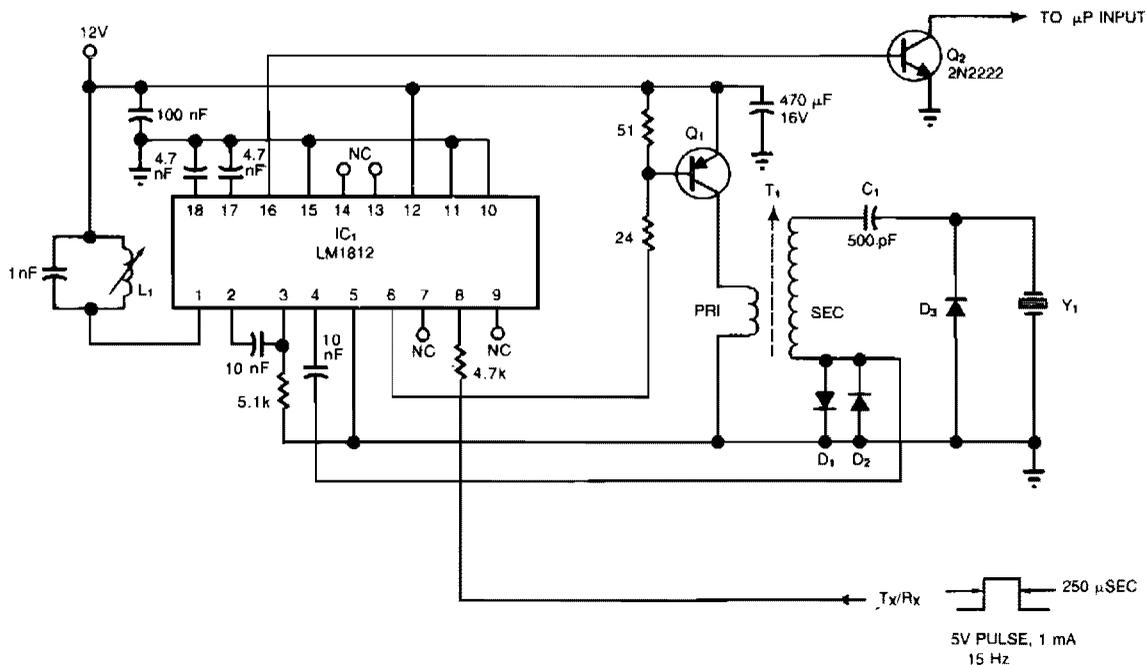

PART	PARTS LIST DESCRIPTION	MANUFACTURER
L <sub>1</sub>	15.8 mH ADJUSTABLE #CLN-2A900HM	TOKO AMERICA (SKOKIE, IL)
T <sub>1</sub>	PRIMARY 8 TURNS #24* SECONDARY 110 TURNS #30* POTCORE RM8P-A630-3B7 BOBBIN RM8 PCB1-4 CLIPS 991-393-00	FERROXCUBE (SAUGERTIES, NY)
X <sub>1</sub>	TRANSDUCER	POLAROID (CAMBRIDGE, MA)
Q <sub>1</sub>	D45C6 I <sub>c</sub> = 5A MIN, V <sub>CEO</sub> = 40V MIN	NATIONAL SEMICONDUCTOR (SANTA CLARA, CA)


\*IF MACHINE WOUND, SLIGHTLY LARGER WIRE SIZES MAY BE USED.

EDN

**Fig. 117-1**

Combine an electrostatic transducer with an ultrasonic transceiver IC to build a ranging system that senses objects at distances from 4 inches to more than 30 feet. Transducer Y1's broadband characteristic simplifies tuning. The secondary of T1 resonates with the 500-pF capacitor C1 at a frequency between 50 and 60 kHz. You tune L1 to this frequency by using an oscilloscope to note the maximum echo sensitivity at pin 1. Step-up transformer T1 provides 150-V bias for the transducer.

## ULTRASONIC RECEIVER

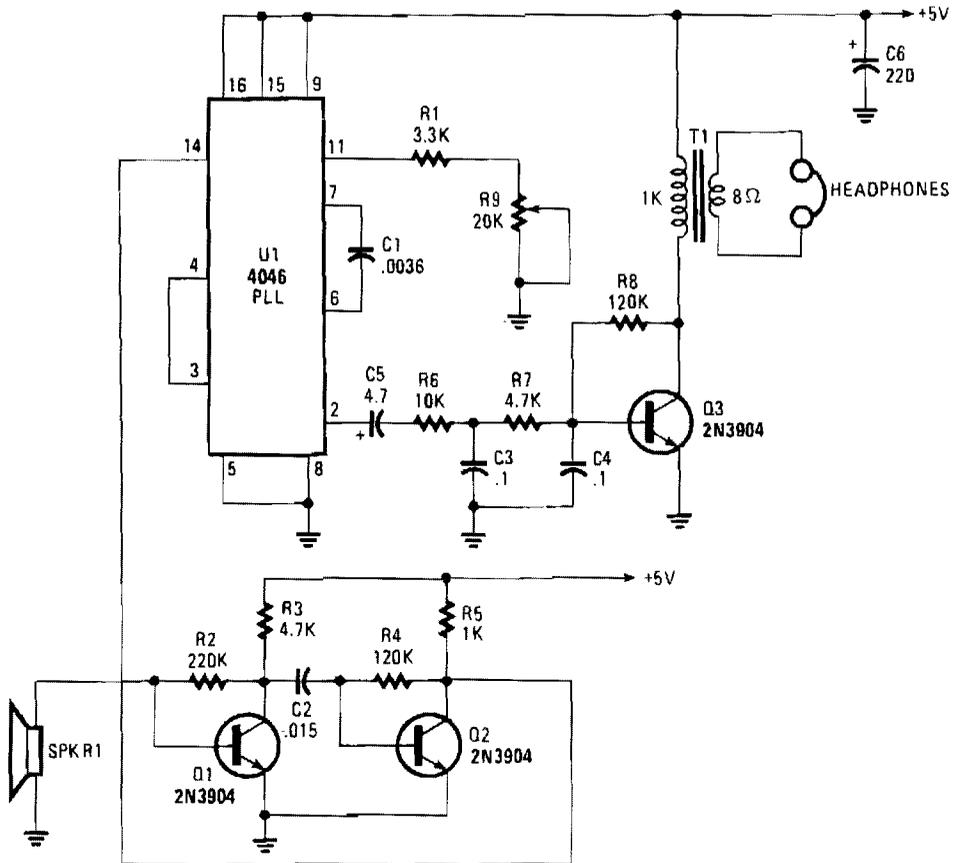


POPULAR ELECTRONICS

**Fig. 117-2**

The 4046 PPL is used as the heart of a tunable ultrasonic receiver that can be used to locate unheard ultrasonic sounds. The receiver might also be used, along with a simple ultrasonic generator, to send and receive Morse code. The incoming ultrasonic signal is picked up by piezo speaker SPKR1, and amplified by transistors Q1 and Q2. The output is fed to the phase comparator input of U1 at pin 14. The chip's interval VCO is tuned by turning potentiometer R9.

If a 20-kHz signal is picked up by SPKR1 and the VCO is tuned to produce a 19-kHz signal the difference output at pin 2 will be 1 kHz. That 1-kHz signal is amplified by Q3 and coupled through T1 to a pair of headphones. If the received frequency increases to 22 kHz, a 3-kHz tone is heard in the headphones. With the values given in the parts list for C1, R1, and R9, the VCO can be tuned from 12 to well over 42 kHz, which should cover just about anything the piezo sensor can respond to.

## ULTRASONIC PEST-REPELLER

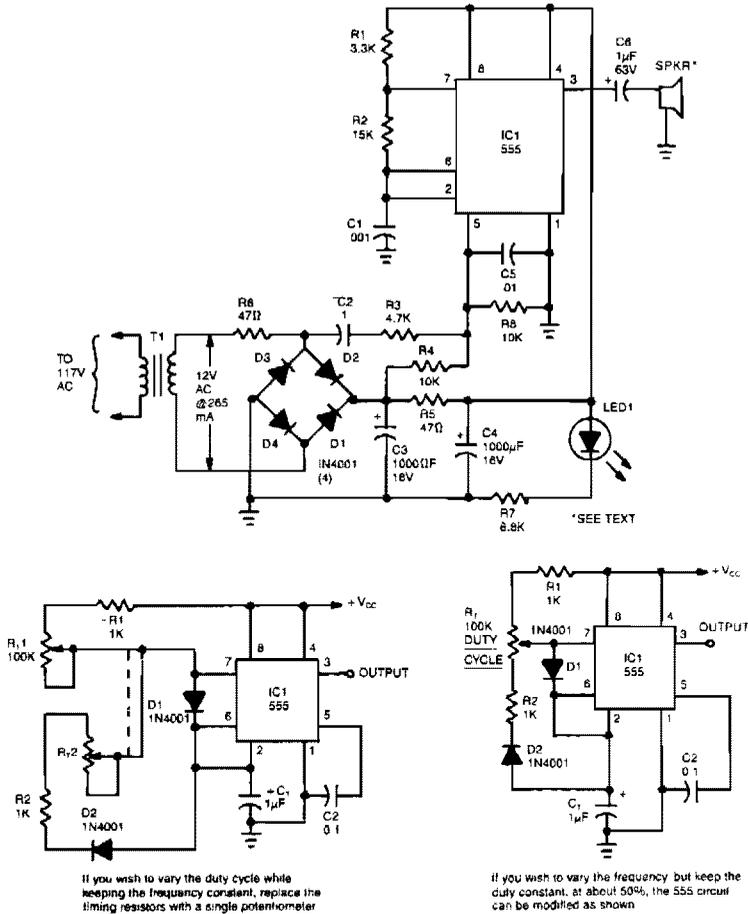

Reprinted with permission from Radio-Electronics Magazine, R-E Experimenters Handbook. Copyright Gernsback Publications, Inc.

**Fig. 117-3**

This circuit is a 555 timer IC connected as a square-wave generator. Its base frequency is approximately 45 kHz, as determined by the values of R1, R2, and C1. The 45-kHz carrier is frequency modulated by a modified trapezoidal voltage waveform applied to pin 5 of the 555 timer. That modulating voltage is developed by a network consisting of C2, R3, and R4 connected across one leg of the bridge rectifier. The sweep is approximately 20 kHz on each side of the base frequency. The speaker is a 2-inch piezoelectric tweeter.

## 20-kHz ARC WELDING INVERTER

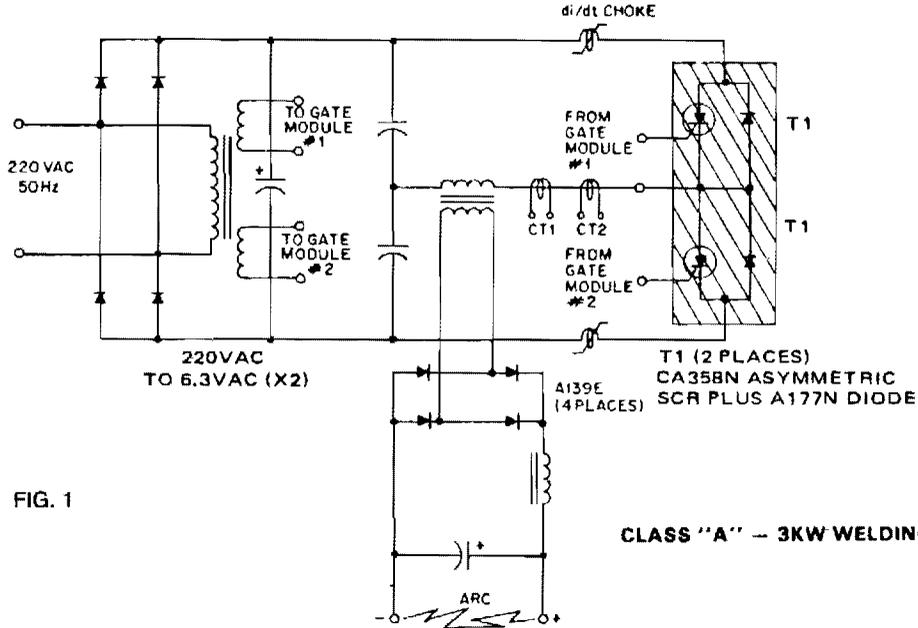


FIG. 1

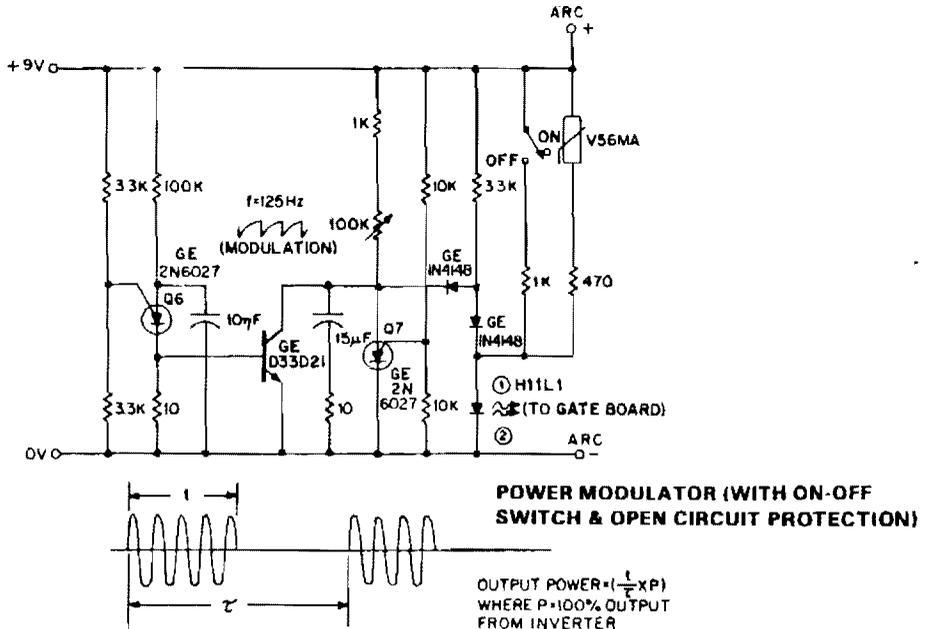



FIG. 2

The Class A series resonant inverter portrayed is well-known and respected for its high efficiency, low cost, and small size, provided that operating frequency is greater than about 3 kHz. The disadvantages are, at least in high power versions, the difficulty in effecting smooth RFI-free output voltage modulation





## SONAR TRANSDUCER/SWITCH

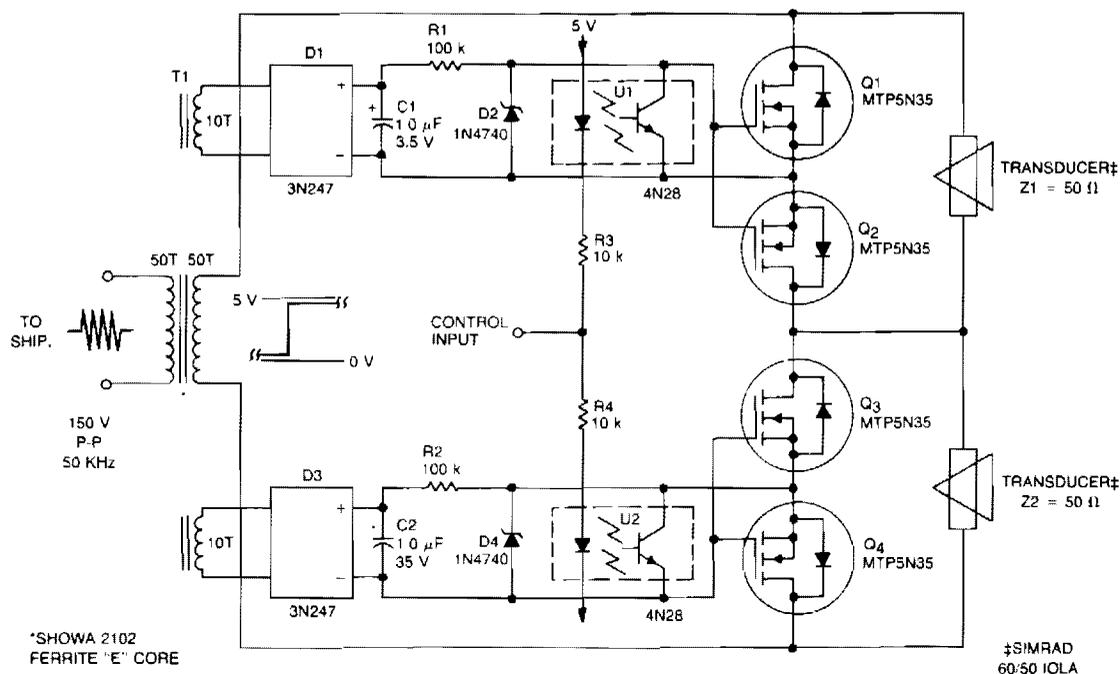

Copyright of Motorola, Inc. Used by permission.


**Fig. 117-6**

This submersible sonar positioning apparatus generally consists of dual-opposed ultrasonic transducers, alternately excited, with return signals processed and displayed for observation and measurement. Typical transmitter frequencies range from 50 to 200 kHz and pulse widths can be varied from 0.3 to 5 ms, depending on depth and resolution requirements.

The input to the transducer/switch is transformer T1 which provides isolation and impedance matching. The turn ratio of the secondary windings depends on the peak-to-peak amplitude of the transmitter output into the specified load. The transmitted pulse that appears on the secondary winding charges capacitors C1 and C2 through bridge rectifiers D1 and D3. Zener diodes D2 and D4 limit the TMOS gate bias to 12 V; R1 and R2 limit the discharge current from C1 and C2.

The square-wave control input is applied to opto-isolators U1 and U2 through resistors R3 and R4. If the control input is 0 V, U1 is activated; when it changes to +5 V, U2 is activated. When U1 is activated, it saturates and reduces the gate bias to zero, turning Q1 and Q2 off. Q3 and Q4 remain on, effectively shunting transducer Z2. When U2 is activated, it saturates and reduces the bias to zero, turning Q3 and Q4 off. Q1 and Q2 remain on, effectively shunting transducer Z1.

## 120-kHz 500-W INDUCTION HEATER

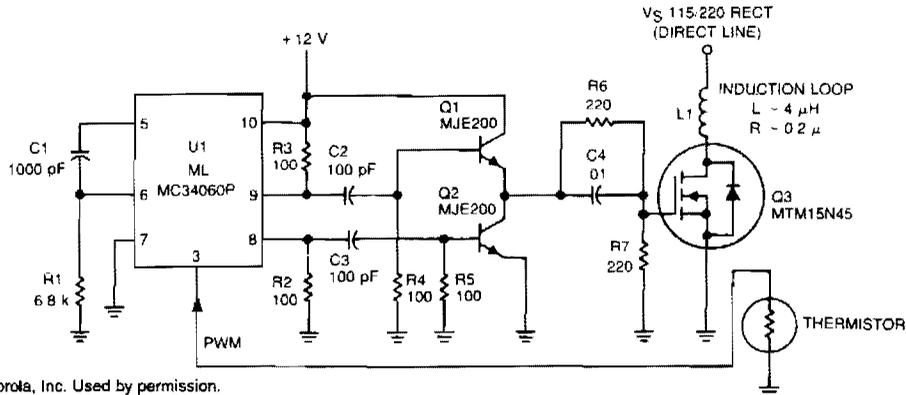


Copyright of Motorola, Inc. Used by permission.

Fig. 117-7

Variable width pulses with fast rise times are provided by U1, and MC34060 operating at 120 kHz, the optimum frequency for heating aluminum alloy containers. The pulse width is modulated by sensing the temperature of the target with a thermistor, using its negative temperature coefficient to change pulse duration. The MC34060 produces output pulses that are ac-coupled to push-pull MJE200 transistors Q1 and Q2. This IC provides the current needed to ensure fast switching for MTM15N45 TMOS power FET Q3.

The estimated efficiency is 80%, based on switching losses and an  $R_{ON}$  of 0.4  $\Omega$  (max). The MTM15N45, with maximum ratings of 15 A and 450 V, was chosen because the induction heater might be operated from either 115 or 220 V sources. A modest heatsink is required because 100 W is dissipated in the power FETs at a full output power of 500 W.

## ULTRASONIC TRANSCIVER

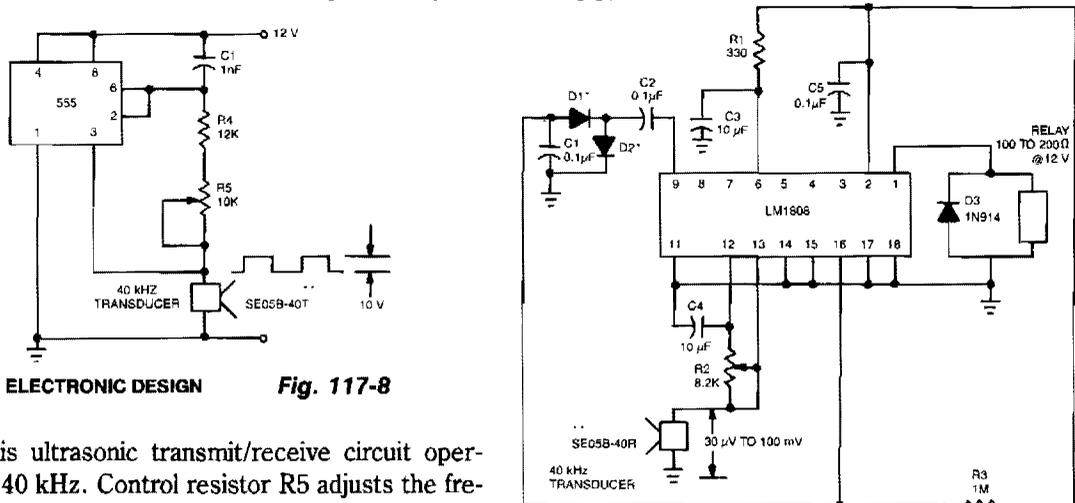


ELECTRONIC DESIGN Fig. 117-8

This ultrasonic transmit/receive circuit operates at 40 kHz. Control resistor R5 adjusts the frequency for best performance with the transducers used.

\*SEE TEXT  
 \*\*AVAILABLE FROM HALL ELECTRONICS,  
 AVONDALE RD., LEYTON, LONDON, E17 8JG

## ULTRASONIC RECEIVER

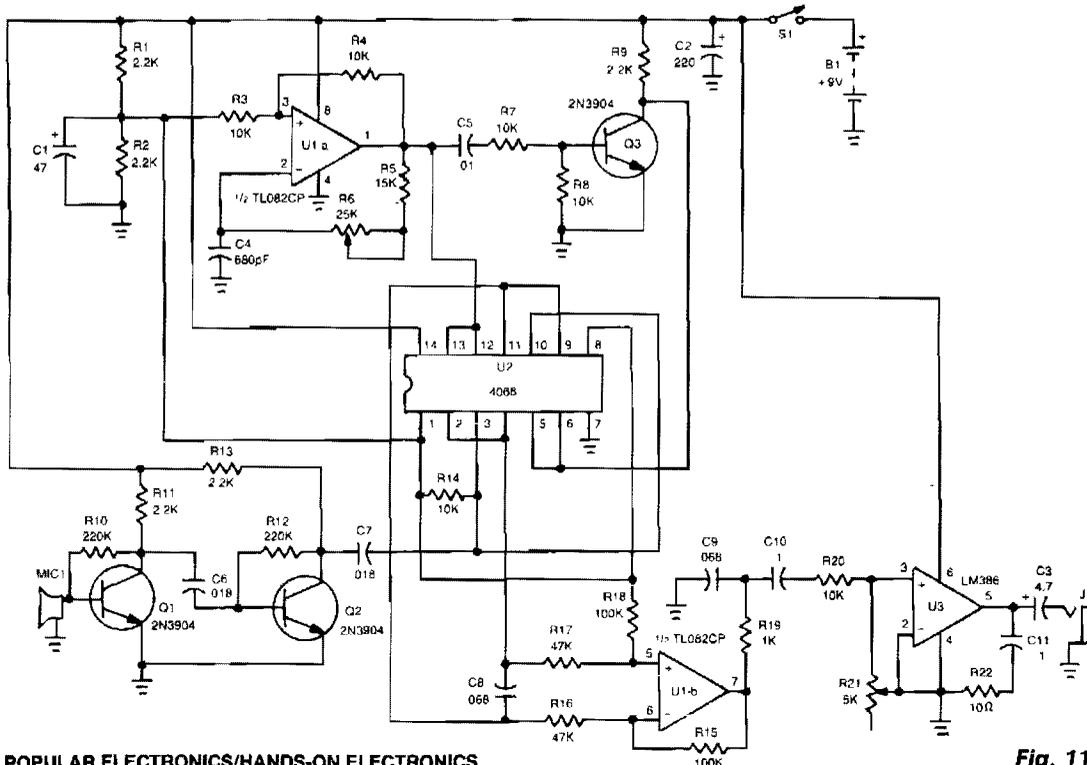

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS

Fig. 117-9


The piezo speaker, MIC1, picks up the incoming ultrasonic signal and feeds it to the base of Q1. The two-transistor booster amplifier, Q1 and Q2, raises the signal to a level that is sufficient to drive one input of this most unusual mixer circuit.

Integrated circuit U2, a quad bilateral switch, functions as an extremely clean balanced-mixer circuit for the superheterodyne receiver. Integrated circuit U1a, 1/2 of a dual op amp, is connected in a variable-frequency square-wave oscillator circuit. Resistors R5, R6, and capacitor C4 determine the frequency and tuning range of the oscillator.

The oscillator's square-wave output is fed along two paths. In one path, the output of U1a is input to pins 12 and 13 of U2. In the other path, the signal is fed to the base of Q3, which is configured as an inverter. The inverter outputs a signal that is 180° out-of-phase with the input signal. The inverted output of Q3 is then fed to U2 at pins 5 and 6. There, the two input signals, the ultrasonic input from MIC1 and the oscillator output, are mixed. The mixing of the ultrasonic input and the square-wave signal produces an audible product that is fed to the input of a differential amplifier, U1b, the second half of the dual op amp, which has a voltage gain of two. The output of U1b at pin 7 is filtered by R19 and C9 to remove the high-frequency content of the mixed signal.

Only the difference frequency is important; the sum frequency, the incoming ultrasonic signal added to the oscillator frequency, is too high for the human ear to hear. The sum frequency is removed by R19 and C9 to produce a clean output signal to feed power-amplifier U3. Resistor R21 functions as the circuit's volume control.

## ULTRASONIC-PULSED PEST CONTROLLER

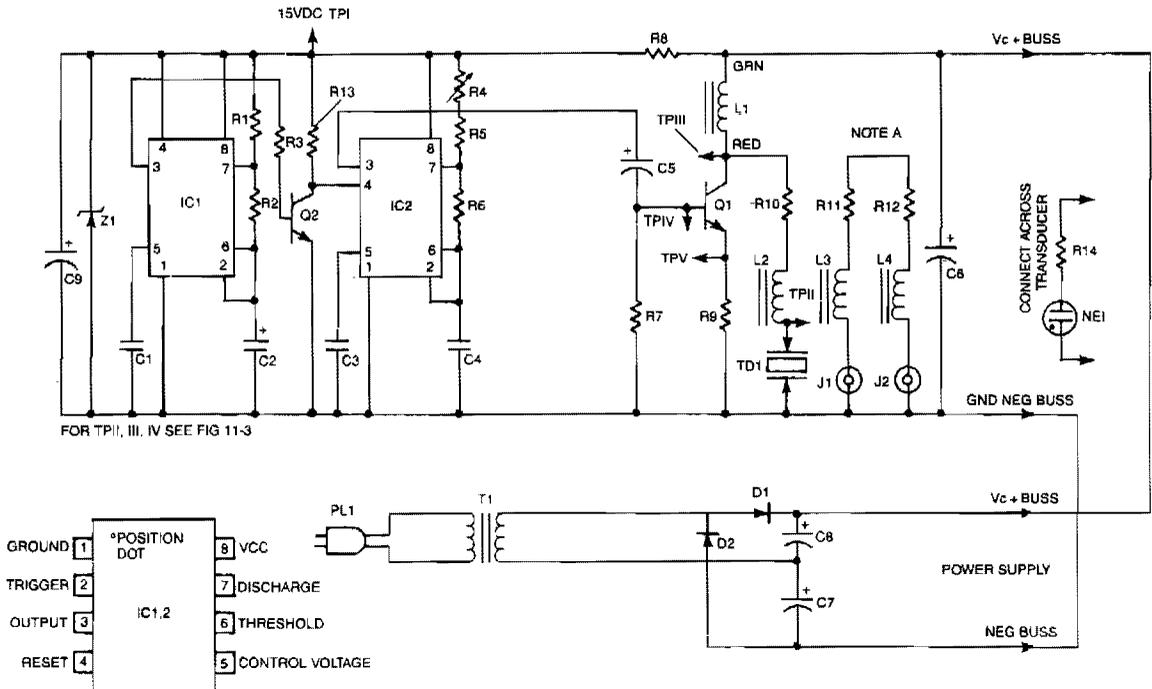

Note a-R11, L3, J1 and R12, L4, J2 are for extra station transducers. Each station should be a similar cabinet with transducer mounted as shown in Fig. 11-3. Use of interconnecting cable strain reliefs, jack or whatever, left up to builder. Station transducers connected same as TD1.


Use sleeving or tubing on any interconnecting wires that are potentially close to one another or on wire jump bridges. Use component leads wherever possible.

### TAB BOOKS

Fig. 117-10

IC2 forms a stable oscillator whose frequency and pulse width is determined by the values of R4, R5, R6, and C4. R4 is made adjustable for precise frequency setting. The output of IC2 is pin 3, which is capacitively coupled to the base of Q1. L1 acts as a high-impedance choke to the signal, while allowing the collector of Q1 to be dc-biased. Q1 amplifies the positive pulses from IC2 and step drives the series resonant combination of L2 and TD1. Resistor R10 serves to broaden the response of this resonant circuit. L2 and the inherent capacity of the transducer, TD1, forms a resonant circuit at around 23 kHz. It is usually found that most rodents are bothered when the signal is pulsed with the off exceeding the on time. This timing is accomplished via timer IC1 and timer inverter Q2. IC1 is free running and its periods are determined by R1, R2, and C2 to be approximately two seconds off and two seconds on. The periods are inverted via Q2 and used to gate pin 4 of IC2, the frequency oscillator, turning it on for two seconds and off for three seconds. The power supply is a conventional voltage doubler with a zener regulator for the oscillator voltages.

## ULTRASONIC PEST CONTROLLER

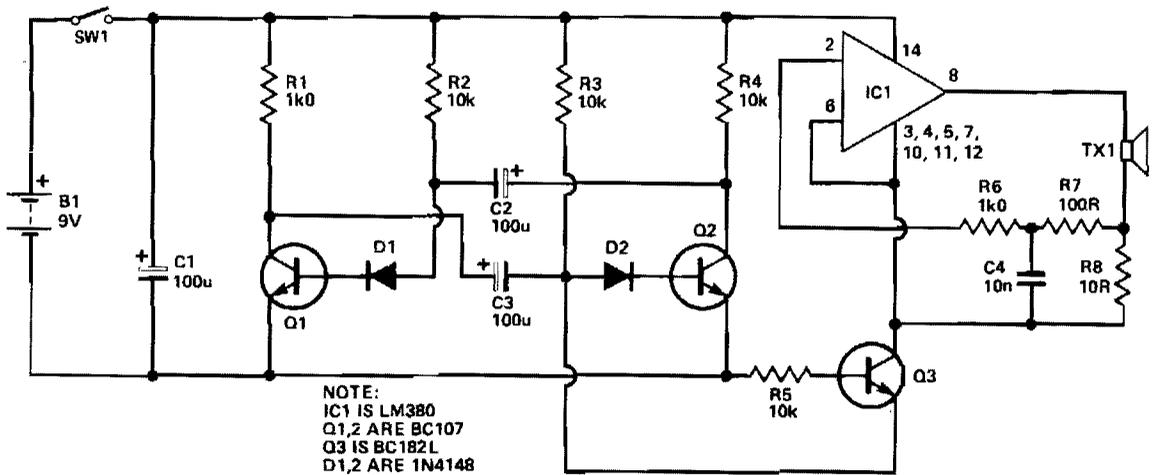

ELECTRONICS TODAY INTERNATIONAL

Fig. 117-11

This circuit consists of two basic parts: an oscillator tuned to 40 kHz, and a voltage doubler with pulse generator. The pulses are about 10 ms long and occur 2–3 per s to reduce battery drain and increase the annoyance factor for a cat, dog, hedgehog, etc. The voltage doubling action increases the available output power for any given battery voltage.

# 118


## Video Amplifiers

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

- RGB Video Amplifier
- Video Line Driving Amplifier
- Summing Amplifier/Clamping Circuit
- Dc Gain-Controlled Video Amplifier
- 75- $\Omega$  Video Pulse Amplifier
- Video Gain Block
- Low-Distortion Video Buffer


## RGB VIDEO AMPLIFIER

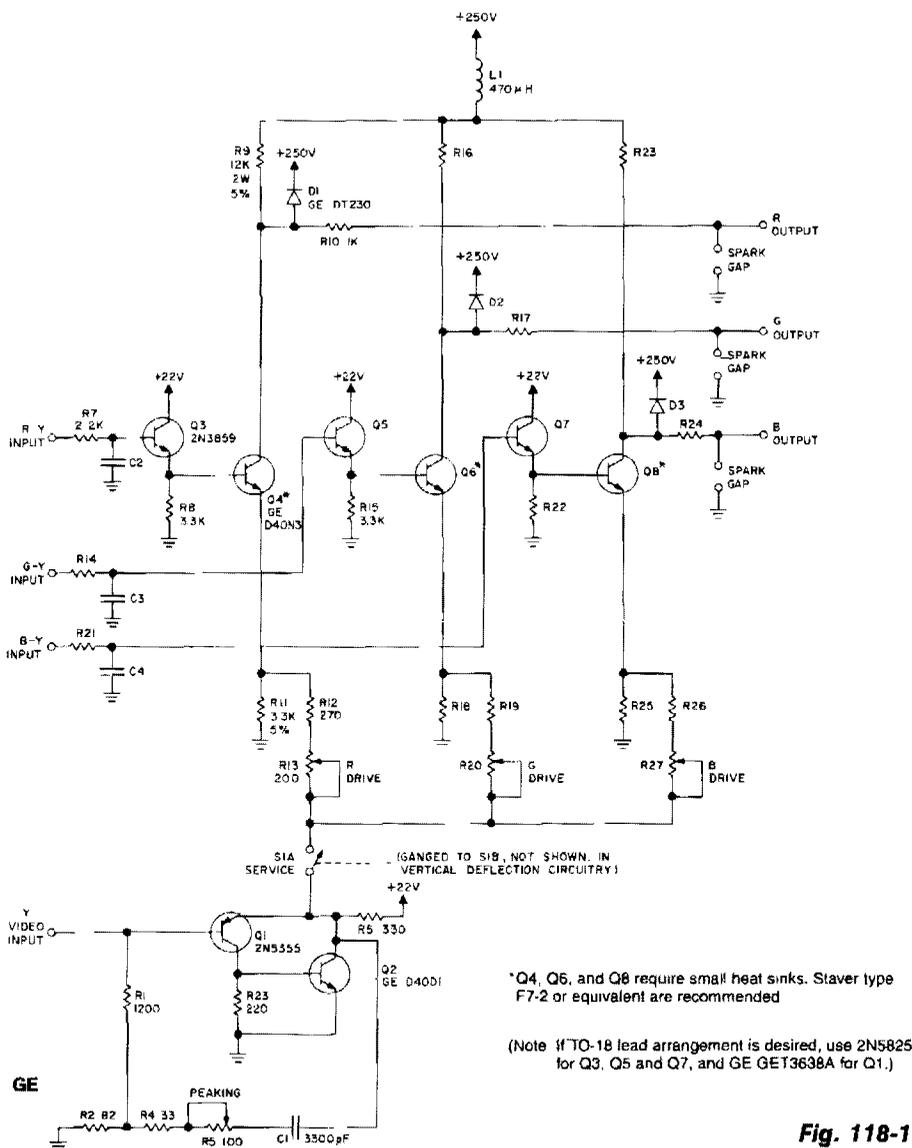

**Fig. 118-1**

Transistors Q1 and Q2 and their associated components provide: a low-impedance output with the necessary power to drive the output stages, give increased gain to high frequencies, and peaking the video for enhanced transient response. Emitter followers Q3, Q5, and Q7 provides low-impedance drive to output stages, Q4, Q6, and Q8. The output stages, with the color difference signals applied to their bases and the luminance signals to their emitters, perform matrixing. The matrixing results in composite output information, to the picture tube, which contains both luminance and chroma information.

## VIDEO LINE DRIVING AMPLIFIER

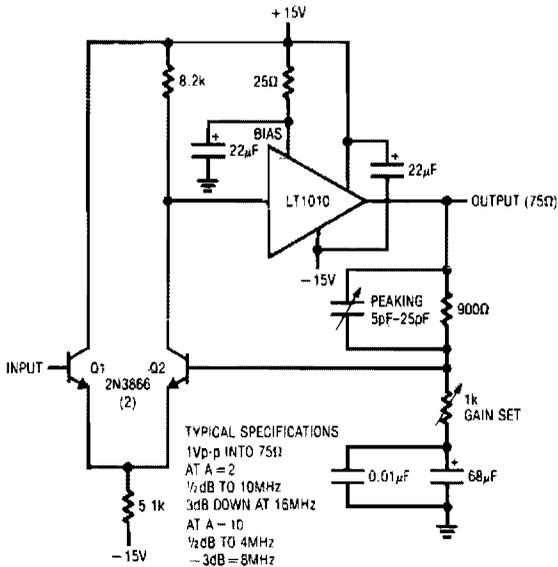


Q1 and Q2 form a differential stage which single-ends into the LT1010. The capacitively terminated feedback divider gives the circuit a dc gain of 1, while allowing ac gains up to 10. Using a 20-Ω bias resistor, the circuit delivers 1 V pk-pk into a typical 75-Ω video load. For applications sensitive to NTSC requirements, dropping the bias resistor value will aid performance. At  $A = 2$ , the gain is within 0.5 dB to 10 MHz and the -3 dB point occurs at 16 MHz. At  $A = 10$ , the gain is flat, within  $\pm 0.5$  dB to 4 MHz, and the -3 dB point occurs at 8 MHz. The peaking adjustment should be optimized under loaded output conditions.

LINEAR TECHNOLOGY CORP.

Fig. 118-2

## SUMMING AMPLIFIER/CLAMPING CIRCUIT

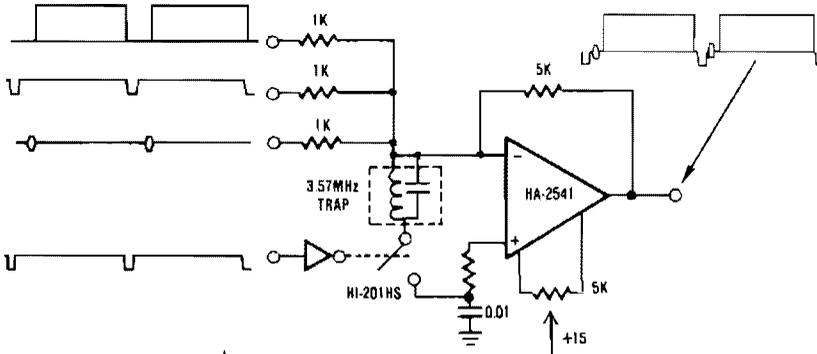


HARRIS

Fig. 118-3

This circuit is a traditional summing amplifier configuration with the addition of the dc clamping circuit. The operation is quite simple; each component—synchronization, color burst, picture information, etc.—of the composite video signal is applied to its own input terminal of the amplifier. These signals combine algebraically and form the composite signal at the output. The clamping circuit, if used, restores the 0-V reference of the composite signal.

## DC GAIN-CONTROLLED VIDEO AMPLIFIER

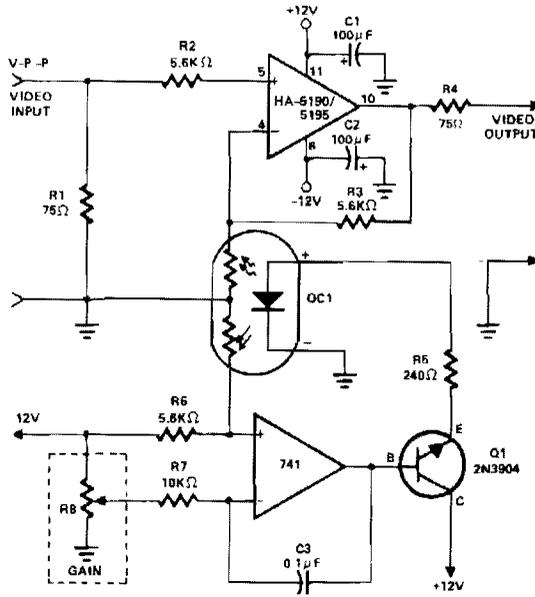

HARRIS

OC1-CLAIREX CLM 8500/2  
C1, C2 - TANTALUM TYPES


Fig. 118-4

This amplifier employs a cascaded op amp integrator and transistor buffer, Q1, to drive the gain control element. Except for a simple modification, the HA-5190/5195 stage is connected as a conventional noninverting op amp, and includes input and output impedance matching resistors R1 and R4,

respectively, series stabilization resistor R2, and power supply bypass capacitors C1 and C2. The circuit differs from standard designs in that the gain control network includes a photoresistor, part of OC1. The optocoupler/isolator OC1 contains two matched photoresistors, both activated by a common LED. The effective resistances offered by these devices are inversely proportional to the light emitted by the LED. One photoresistor is part, with R3, of the HA-5190/5195 gain network, while the other forms a voltage-divider with R6 to control the bias applied to the integrator noninverting terminal.

In operation, the dc voltage supplied by gain control R8 is applied to the integrator inverting input terminal through input resistor R7. Depending on the relative magnitude of the control voltage, the integrator output will either charge or discharge C3. This change in output, amplified by Q1, controls the current supplied to the OC1 LED through series limiting resistor R5. The action continues until the voltage applied to the integrator noninverting input by the R6—photoresistor gain network is changing, adjusting the op amp stage gain. As the control voltage at R8 is readjusted, the OC1 photoresistances track these changes, automatically readjusting the op amp in accordance with the new control voltage setting.

## 75-Ω VIDEO PULSE AMPLIFIER

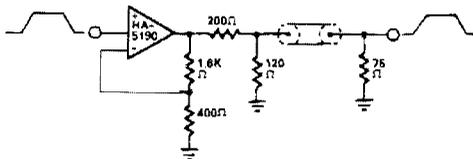


HARRIS

Fig. 118-5

HA-5190 can drive the 75-Ω coaxial cable with signals up to 2.5 V pk-pk without the need for current boosting. In this circuit, the overall gain is approximately unity because of the impedance matching network.

## VIDEO GAIN BLOCK

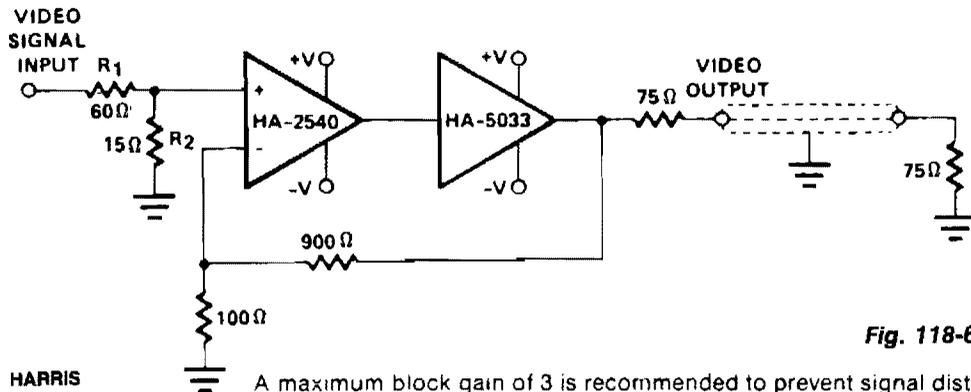

A maximum block gain of 3 is recommended to prevent signal distortion.

This configuration utilizes the wide bandwidth and speed of HA-2540, plus the output capability of HA-5033. Stabilization circuitry is avoided by operating HA-2540 at a closed loop gain of 10, while maintaining an overall block gain of unity. However, gain of the block can be varied using the equation:


$$\frac{V_{OUT}}{V_{IN}} = 5 \frac{R2}{(R1 + R2)}$$

where  $R1 + R2 = 75 \Omega$

A maximum block gain of 3 is recommended to prevent signal distortion.

This circuit was tested for differential phase and differential gain using a Tektronix 520A vector scope and a Tektronix 146 video signal generator. Both differential phase and differential gain were too small to be measured.

## LOW-DISTORTION VIDEO BUFFER

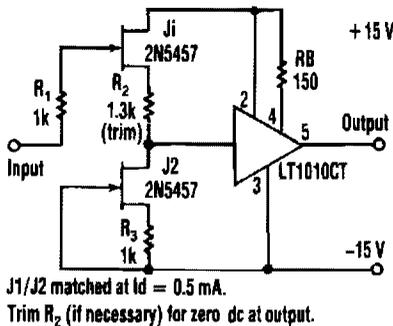

J1/J2 matched at  $I_d = 0.5 \text{ mA}$ .  
Trim  $R_2$  (if necessary) for zero dc at output.

Fig. 118-7

This buffer amplifier's overall harmonic distortion is a low 0.01% or less at 3-V rms output into a 500-Ω load with no overall feedback. The LT1010CT offers a 100 V/μs slew rate, a 20 MHz video bandwidth, and 100 mA of output. A pair of JFETs, J1 and J2 are preselected for a nominal

match at the bias level of the linearized source-follower input stage, at about 0.5 mA. The source-bias resistor,  $R_2$ , of J1 is somewhat larger than  $R_3$  so that it can drop a larger voltage and cancel the LT1010CT's offset. J1 and J2 provide an untrimmed dc offset of  $\pm 50 \text{ mV}$  or less. Swapping J1 and J2 or trimming the  $R_2$  value can give a finer match.

The circuit's overall harmonic distortion is low: 0.01% or less at 3-V rms output into a 500-Ω load with no overall feedback. The circuit's response to a  $\pm 5 \text{ V}$ , 10 kHz square-wave input, band-limited to 1 μs, has no overshoot. If needed, setting bias resistor  $R_B$  lower can accommodate even steeper input-signal slopes and drive lower impedance loads with high linearity. The main trade-off for both objectives is more power dissipation. A secondary trade-off is the need for retrimming the source-bias resistor,  $R_2$ .

# 119

## Video Circuits



---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.



RGB-Composite Converter  
Single-Supply Wide-Range Sync Separator  
Chroma Demodulator with RGB Matrix  
Composite-Video Signal Text Adder  
PAL/NTSC Decoder with RGB Inputs  
Wireless Video Camera Link  
Video Switch with Very High Off Isolation  
Video Palette

Picture Fixer/Inverter  
Video Dc Restorer  
Color TV Crosshatch Generator  
General Purpose Video Switch  
Video Signal Clamp  
Automatic Video Switch  
High-Performance Video Switch

## RGB-COMPOSITE CONVERTER

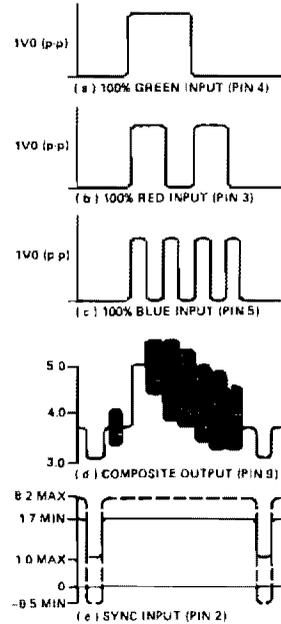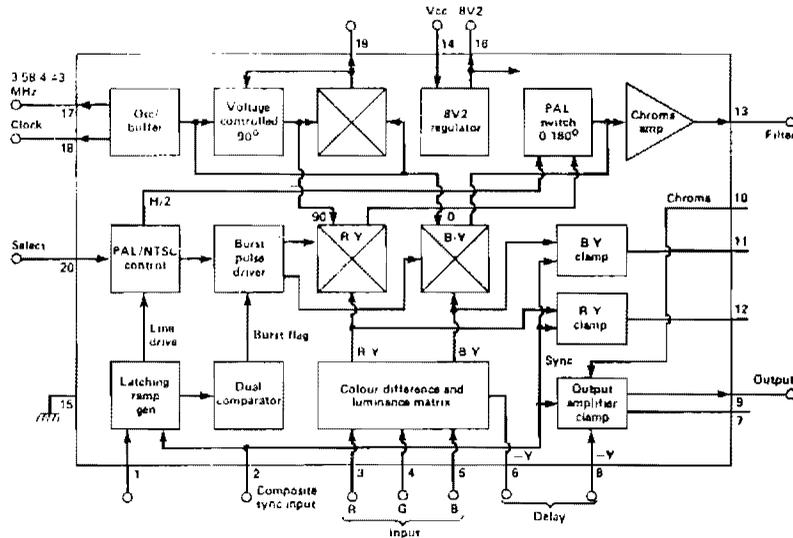

BLOCK DIAGRAM OF THE MC1377P ENCODER IC.

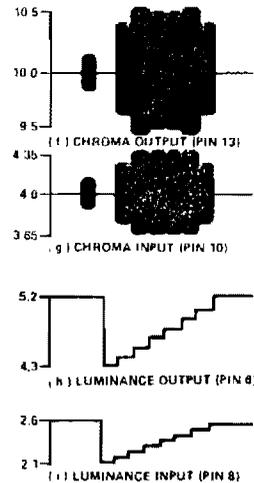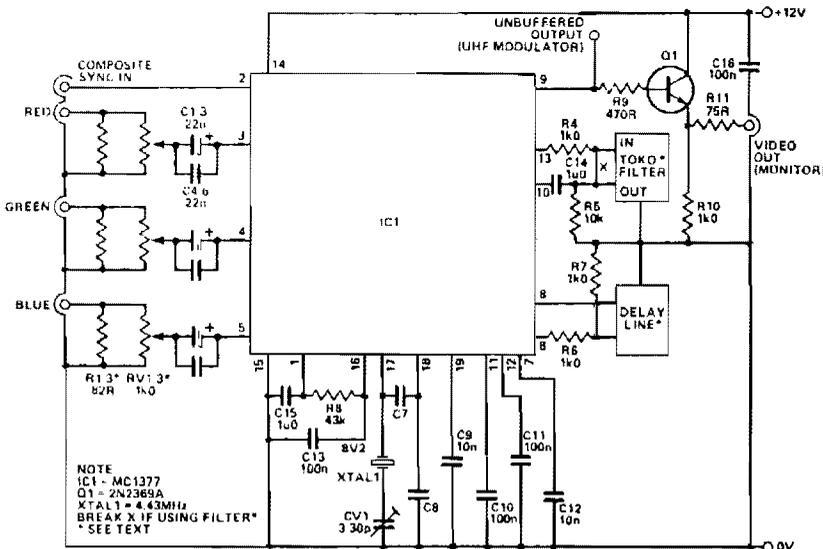

CIRCUIT DIAGRAM OF THE CONVERTER.

The signals that should appear at the test points around the chip.

### ELECTRONICS DIGEST

Fig. 119-1


The incoming RGB inputs are terminated with resistors R1, R2, and R3 and potentiometers RV1, RV2, and RV3. These provide input impedances of approximately 75  $\Omega$ . The presets should be adjusted to provide a maximum input of 1 V pk-pk into the MC1377. The inputs are ac-coupled into the encoder; the large value capacitor is required for the 60 Hz field component.

## RGB-COMPOSITE CONVERTER (Cont.)

The Colpitts oscillator for the color burst is formed around pins 17 and 18. About 0.5 V pk-pk should appear on pin 17 and 0.25 V rms into pin 18 with the oscillator components removed. The incoming composite sync signal at pin 2 should be negative-going. The device will accept CMOS and TTL directly. If it is necessary to ac-couple the sync, then a pull-up to 8.2 V is required—a regulated 8.2 V is provided on pin 16.

From the composite sync input, the MC1377 generates a ramp which it uses to provide the burst gate pulse. The slope of this ramp can be varied by a potentiometer on pin 1. However, a preset value, shown as 43 K $\Omega$ , is usually sufficient. The chrominance filter should be fitted between pins 13 and 10. If the filter is not used, a compensatory potential divider should be fitted (both are shown). We used a prealigned Toko bandpass filter centered on 4.43 MHz. If the chroma filter is fitted, the delay through it, 400 ns, has to be compensated for by a luminance delay line between pins 6 and 8. This line is shorted out if the filter is not fitted. The composite video output from the IC is buffered to provide a low-impedance drive for a monitor, or it can be applied directly to a UHF modulator commonly used in computers.
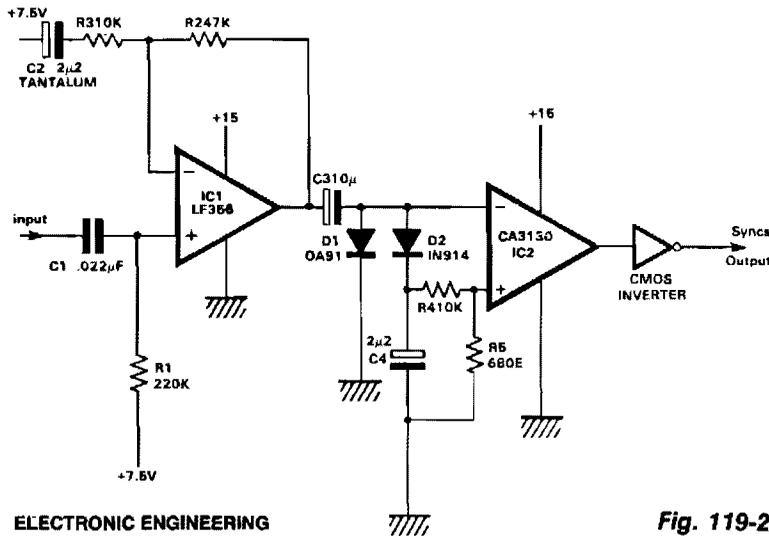
### SINGLE-SUPPLY WIDE-RANGE SYNC SEPARATOR



ELECTRONIC ENGINEERING

Fig. 119-2

This circuit extracts the sync pulses from a video signal over a wide range of amplitudes and operates a single +15 V supply. IC1 buffers and amplifies the incoming signal and applies it via C3 to the peak detector, consisting of D2 and C4. It is also applied to one input of a comparator, IC2. The other input of IC2 is set at a voltage corresponding to about 0.065 of the peak video amplitude, by the divider R4/R5. The trigger points of IC2 are set near the bottom of the sync pulses which help prevent spurious noise. These resistors also leak across C4, so they must be chosen as a compromise between excessive ripple and speed of response to falling signal levels. The IC2 output swings between 0 and 15 V and is conveniently CMOS compatible, but further buffering is advisable, hence the CMOS inverter. Maximum input amplitude is set by saturating IC1's output. The minimum acceptable level is set by the forward voltage drop of the dc restoring clamp D1, which should be either a germanium (as shown) or a Schottky diode.

## CHROMA DEMODULATOR WITH RGB MATRIX

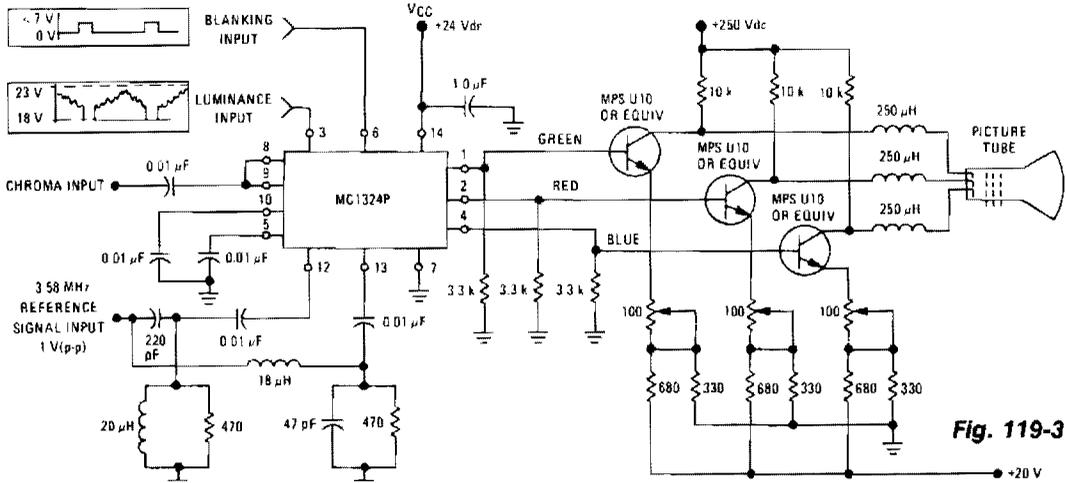


Fig. 119-3

Copyright of Motorola, Inc. Used by permission

A typical application is given above to indicate the requirements and output functions of this chroma demodulator.

The MC1324 provides chroma demodulation recovering recoding the R, G, and B signals to drive video amps for each color difference signal. The luminance signal and chrominance signal are matrixed to get the R, G, and B signals.

## COMPOSITE-VIDEO SIGNAL TEXT ADDER


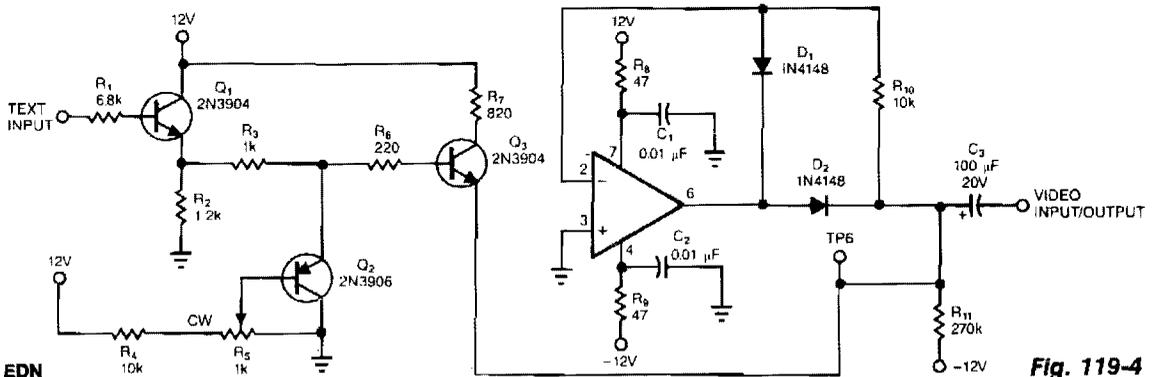


Fig. 119-4

This circuit shows a simple way to add text information to a composite-video signal that might be floating at some indeterminate dc level. The text generator and composite-video source must have the same sync signal. The video-input and -output signals share the same terminal. C3 couples the video signal to the output of a rectifier circuit that is based on a subvideo-speed op amp. A faster op amp would clamp on individual sync pulses rather than on the video waveform's average value, as is desired. R11 serves as a pull-down resistor and feedback resistor R10 ensures that TP6 remains at ground level. Emitter follower Q1 buffers the text signal, and R5 serves as a gain control. A simple clamp circuit, Q2, is sufficient for regulating amplitude, because the text signal contains no gray-scale levels. Q3 couples the text signal into the op-amp clamp circuit.

### PAL/NTSC DECODER WITH RGB INPUTS

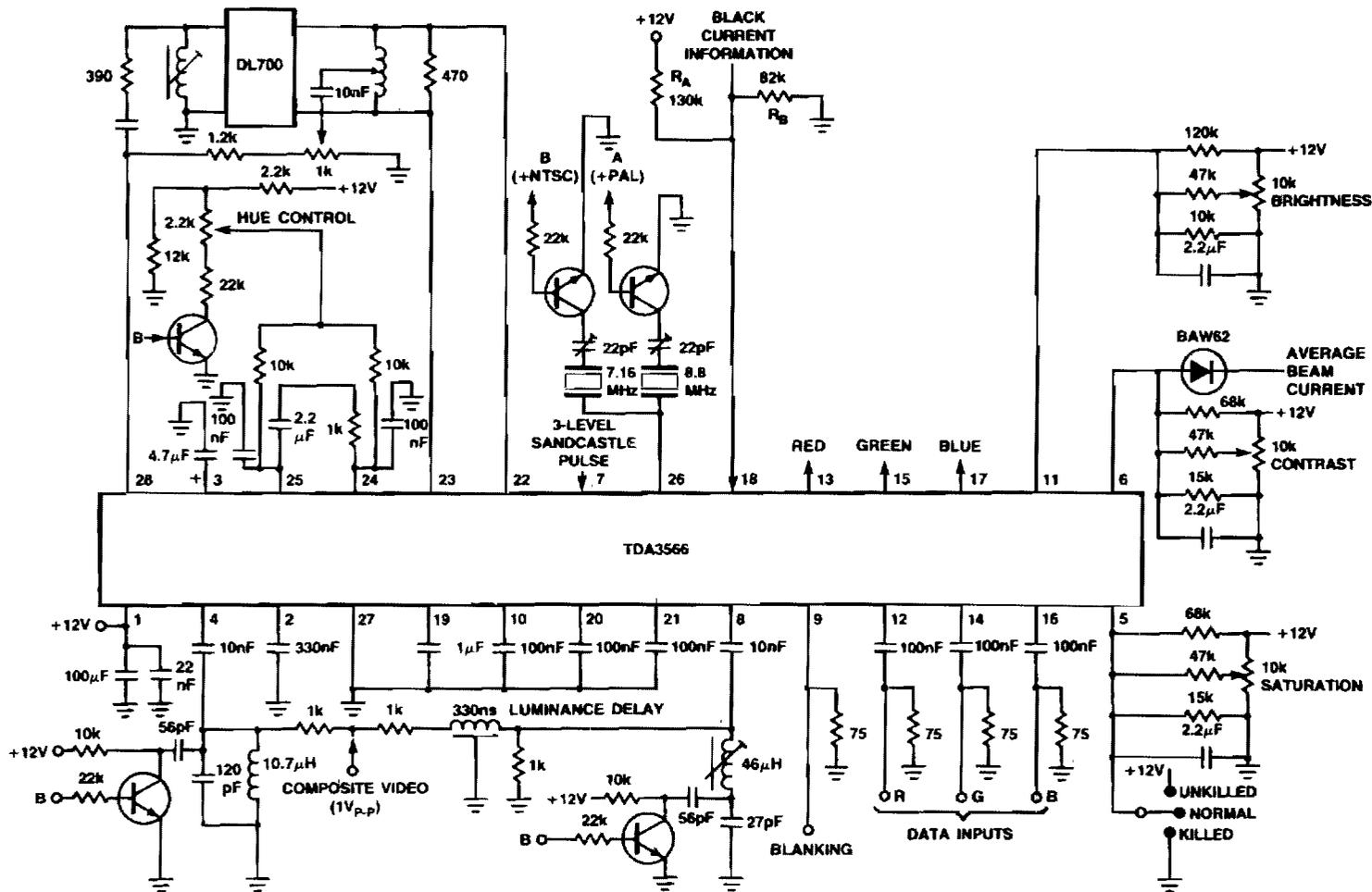


SIGNETICS

This circuit shows the TDA3566 for a PAL/NTSC Decoder.

Fig. 119-5

## WIRELESS VIDEO CAMERA LINK

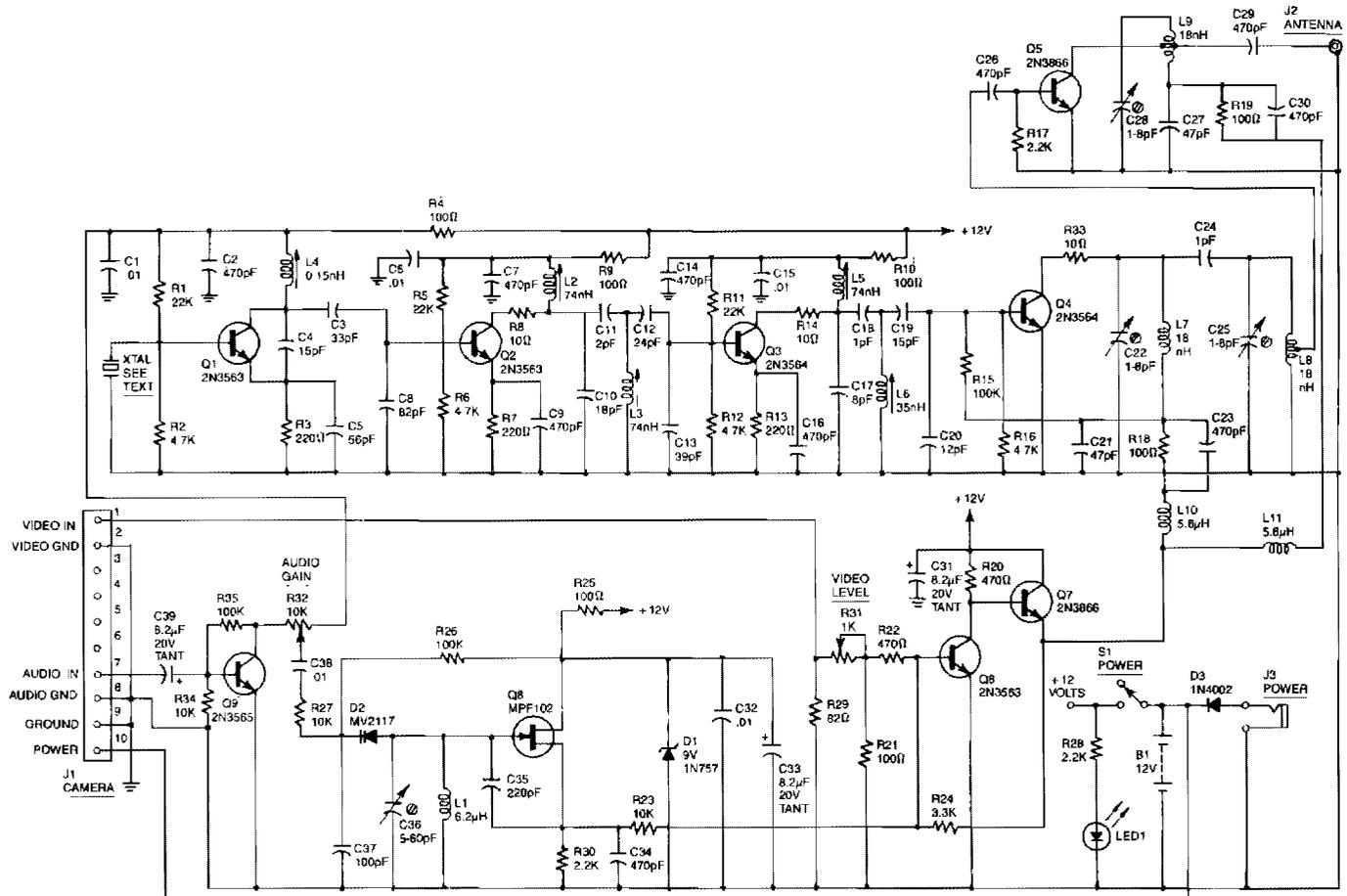


Reprinted with permission from Radio-Electronics Magazine, February 1966. Copyright Gernsback Publications, Inc., 1966.

Fig. 119-6


## WIRELESS VIDEO CAMERA LINK (Cont.)


This high-performance video-camera link transmits signals from your video camera to your VCR, or from your VCR to TVs throughout your home. The first stage of the rf chain is a crystal-controlled oscillator, Q1, with a frequency of 60 to 65 MHz, which is one-eighth of the final output frequency. The oscillator produces a signal of about +6 dBm (4 mW) that drives three stages of frequency doublers. The combined action of those doublers multiplies the input frequency by eight for a final output frequency of (nominally) 500 MHz. Double-tuned circuits are used between each stage to help reduce spurious outputs that might cause unwanted interference. The video input signal from your VCR, video camera, etc. drives a video modulator, Q6 and Q7, that adds the video signal to the +12 V line supplying power to the final doubler, Q4, and the output amplifier, Q5. That method of modulation is similar to the way a conventional AM-radio transmitter is modulated. The video modulator has a nominal bandwidth of five MHz. The audio input is applied to Q8, which operates as a VCO running at a nominal frequency of 4.5 MHz to produce the modulated sound carrier. For simplicity, Q8 is a free-running oscillator, since the  $\pm 25$  kHz frequency deviation that is required would be very difficult to produce at that frequency with a crystal-controlled oscillator. Besides, most TV sound systems will accept a  $\pm 10$  kHz error in the sound-carrier frequency without producing undue distortion, and that greatly simplifies the circuitry required. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.
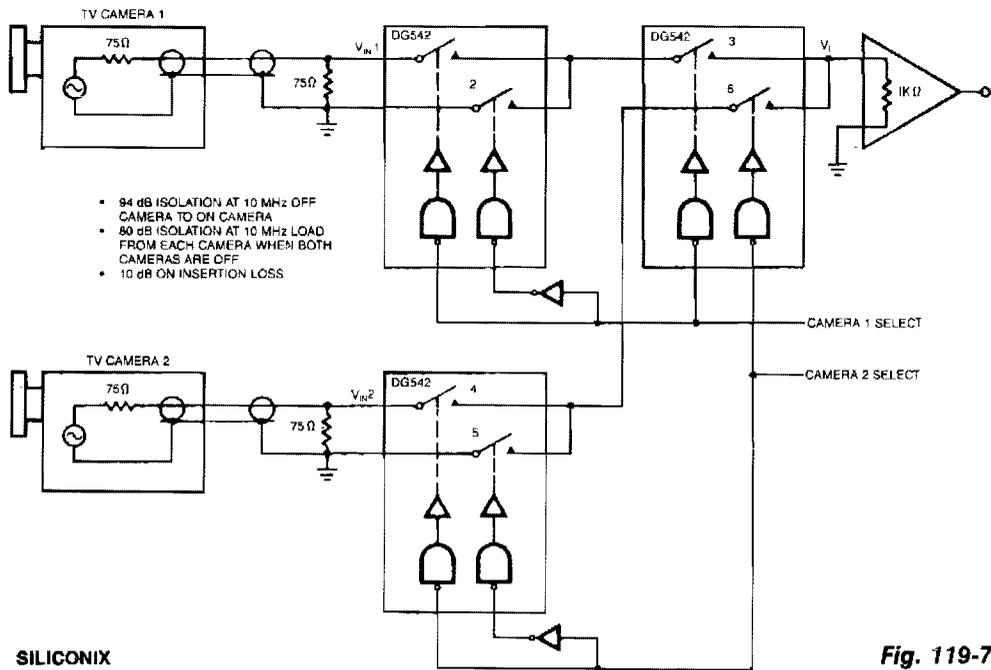
### VIDEO SWITCH WITH VERY HIGH OFF ISOLATION



## VIDEO PALETTE

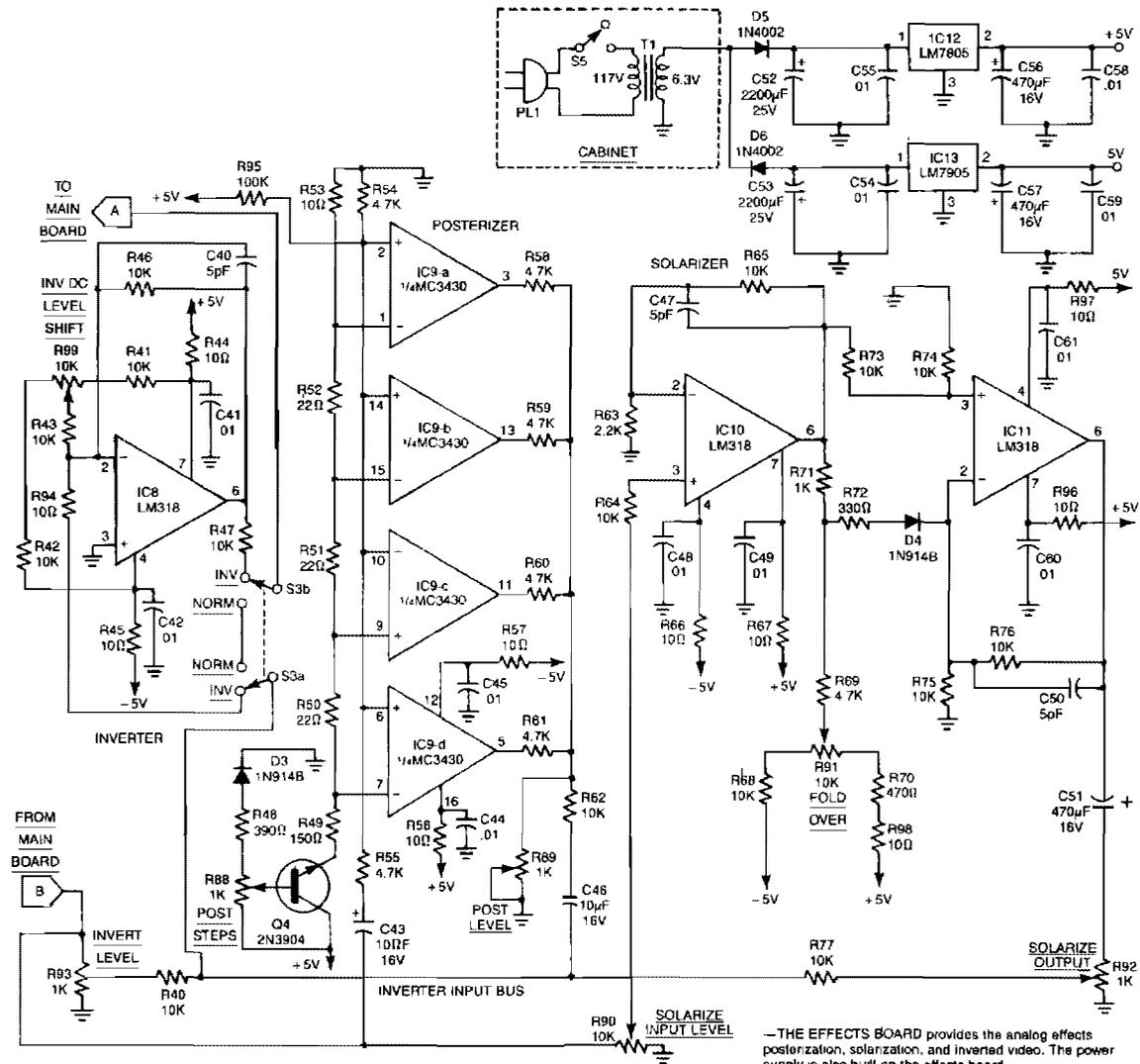

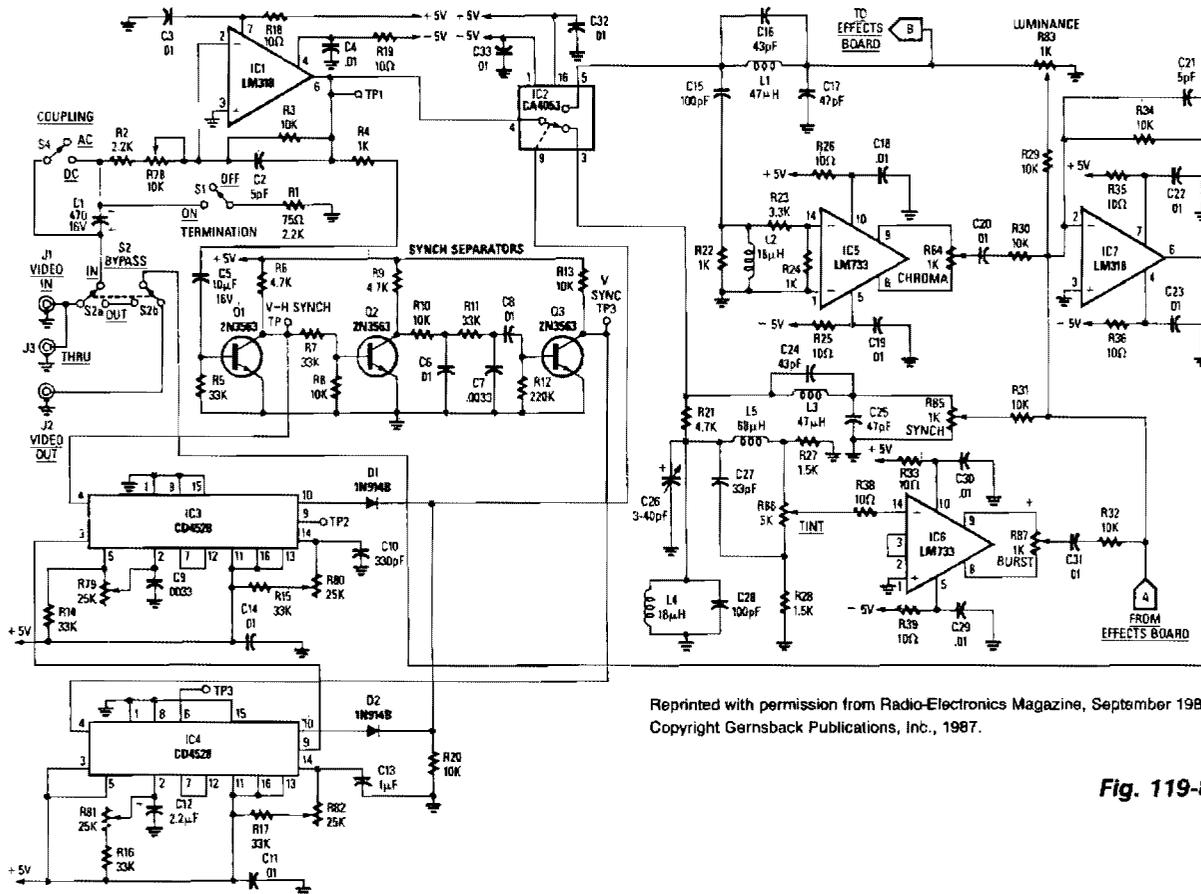


Reprinted with permission from Radio-Electronics Magazine, September 1987. Copyright Gernsback Publications, Inc., 1987.

Fig. 119-8

This system consists of two parts. The main board dissects the video signal and provides independent level control for burst, chroma, luminance, and sync signals, as well as phase and polarity. The video signal is reassembled in the output in corrected or modified format as required by the user. The effects board produces luminance inversion or can generate discrete luminance steps (posterization) or a nonlinear gray scale (solarization) to achieve simulation of photographic effects commonly seen in various special-effect photographic processes. The kit is available from North Country Radio, P.O. Box 53, Wykagyl Station, NY 10804.

## PICTURE FIXER/INVERTER

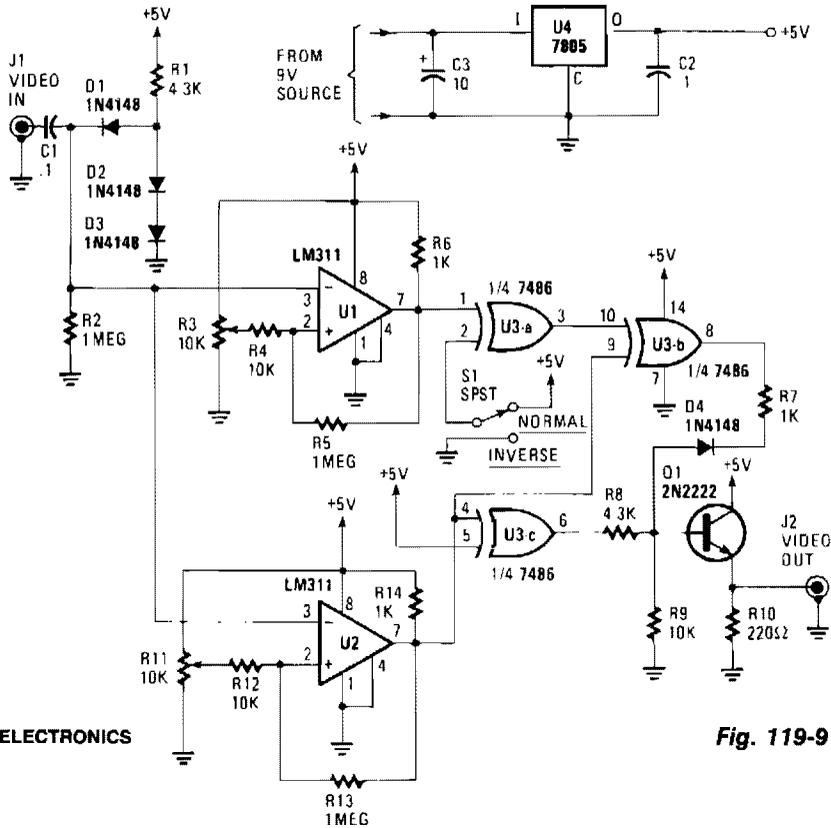

HANDS-ON ELECTRONICS

Fig. 119-9



The circuit will accept a video signal, separate the sync pulses, invert the video, and add new video to the old sync pulses.

The video signal is brought in through J1 and applied to a clamping circuit consisting of C1, D1, D2, D3, R1, and R2. The clamp circuit forces all of the sync pulses to align with the same dc voltage level. With the video voltage clamped, the trip points of the comparators that follow can be set with trimmer resistors R3 and R11. The resistors will not have to be readjusted. One comparator, U1, is adjusted to change states with a change in either video or sync-pulse levels. The other comparator, U2, is adjusted to trip on changes of sync-pulse levels only.

The output of U1 now consists of a logic level, 0 to +5 V, signal that contains both sync pulses and video. The composite signal is coupled to an EXCLUSIVE-OR gate, U3a, where it is either inverted or not inverted, depending upon the position of switch NORM/REV S1. The output, at pin 3 of U3a, is next sent to U3b. There the composite signal is combined with the sync-pulse only signal from U2. The EXCLUSIVE-OR action of U3b cancels out the sync pulses, leaving only video at the IC's output.

Since the sync pulses are inverted as they pass through U2, they must be inverted once more before being combined with the video signal. That final inversion is performed by U3c, and that device's output is combined with that of U3b via D4, R7, R8, and R9. The newly combined signal is buffered by emitter-follower Q1, and sent to the outside world via J2. The circuit can be powered by a 9- to 12-V wall-mount power supply. The supply voltage is regulated down to 5 V by U4.

## VIDEO DC RESTORER

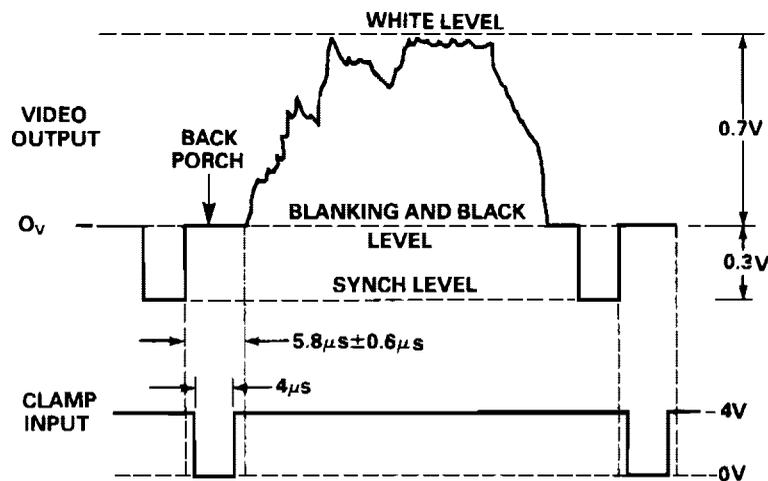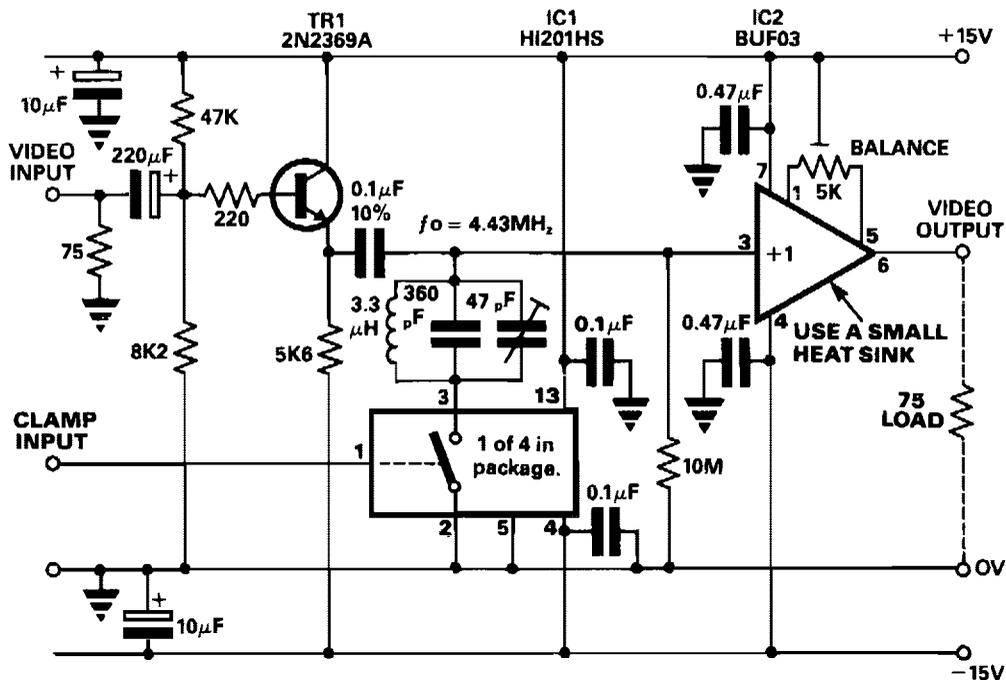


ELECTRONIC ENGINEERING

Fig. 119-10


The main requirement for efficient dc restoration is to provide a short time-constant during the clamp period, with a long time-constant during the active line time. The switch within the Harris HI201HS has an on resistance of  $30\ \Omega$  and the PMI buffer, BUF03, has an input resistance of  $50\ M\Omega$ . The tuned circuit presents a high impedance at the 4.43-MHz color subcarrier frequency so that the color-burst signal is retained if the video signal contains this information.

## COLOR VIDEO AMPLIFIER

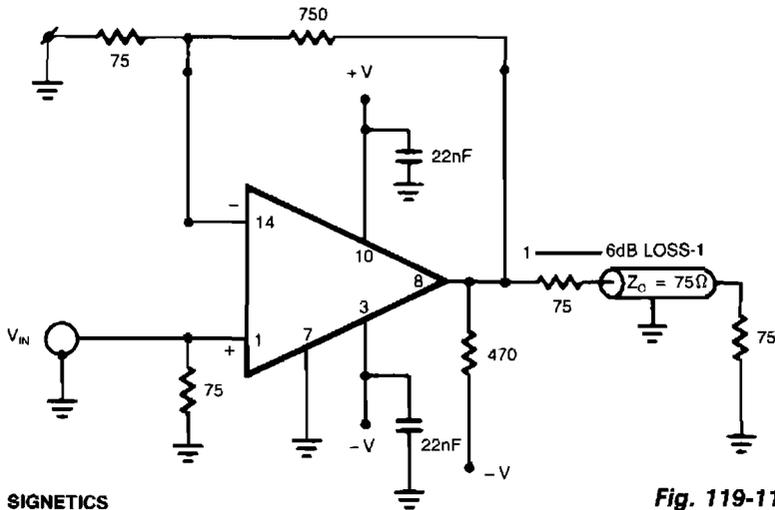

The NE5539 wideband op amp is easily adapted for use as a color video amplifier. The gain varies less than 0.5% from the bottom to the top of the staircase. The maximum differential phase is approximately  $+0.1^\circ$ . The amplifier circuit was optimized for a 75- $\Omega$  input and output termination impedance for a gain of approximately 10 (20 dB).


## COLOR TV CROSSHATCH GENERATOR

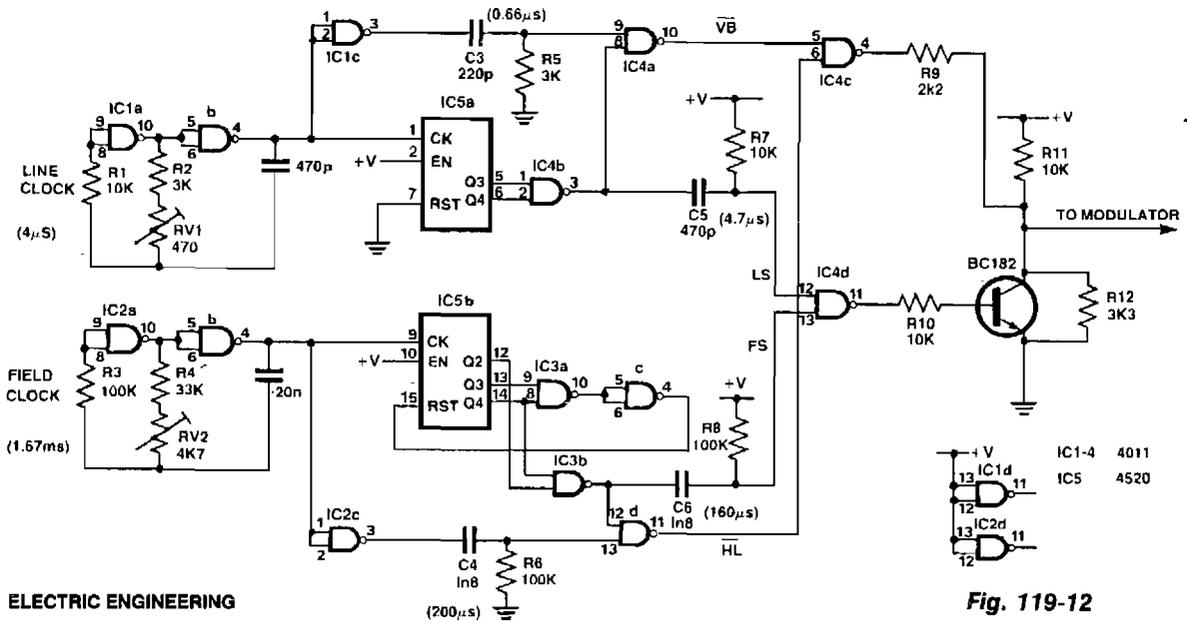

## COLOR TV CROSSHATCH GENERATOR (Cont.)

This circuit provides a simple, low-cost crosshatch generator for convergence and geometry adjustments on color TVs. The generator is driven by two clocks, one for the horizontal drive, IC1ab, and one for the vertical drive, IC2ab. The clock outputs are applied to the two binary counters contained in IC5 which generate the line and field sync pulses and respective blanking periods. Line clock pulses, buffered by IC1c, are differentiated by C3/R5 to produce the vertical bars. These bars are gated by IC4a which suppresses the bars during the line blanking period produced by the coincidence of Q3, Q4 outputs of IC5a, detected by IC4b. This output is also differentiated by C5/R7 to produce the line sync pulse, *LS*. A similar process is used to generate horizontal lines and the field sync, except that in order to give the correct aspect ratio, the count of IC5b is reset at 12, coincidence of Q3 and Q4. In coincidence of Q2, Q4 is used to generate the sync pulse *FS* and the blanking period. The line and field sync pulses, *LS* and *FS*, are combined in IC4d.

## GENERAL PURPOSE VIDEO SWITCH

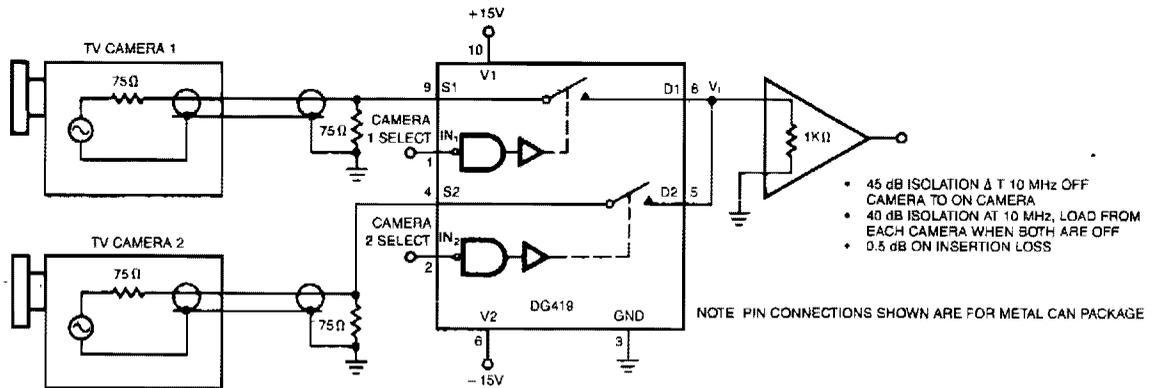


SILICONIX

Fig. 119-13

The circuit shown provides 40-dB isolation at 6 MHz and is good for general purpose video switching.

## VIDEO SIGNAL CLAMP

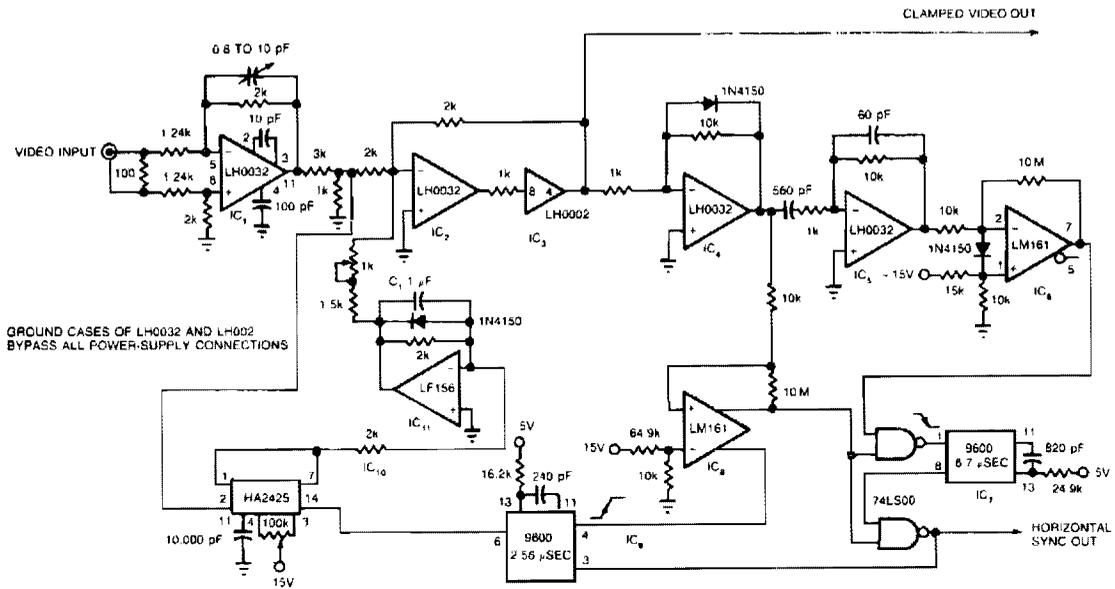


EDN

Fig. 119-14

The circuit uses a track-and-hold amplifier in a closed-loop configuration to clamp the back-porch voltage of a standard video waveform to 0 V. The circuit's outputs include a clamped composite-video signal and a TTL-level horizontal-blanking pulse. Differential input buffer IC1 and the summing amplifier IC2 isolate the input video signal. Clipper IC4 removes the video signal, leaving only the synchronization information. Differentiator IC5 detects the edges of the horizontal blanking pulses and produces pulses that correspond to the leading and trailing edges of the horizontal blanking pulses. IC6 clips these pulses and converts them to a TTL level. IC7 uses these clipped pulses to generate a TTL-level window that, when combined with the horizontal pulse generated by IC8, forms a TTL representation of the original horizontal pulse. This representation is synchronized to the input waveform. IC9 uses the trailing edge of this reconstructed waveform to generate the track pulse for track-and-hold amplifier IC10. IC11 filters IC10's dc output and, after gain adjustment, feeds it back to IC2's summing node.

## AUTOMATIC VIDEO SWITCH

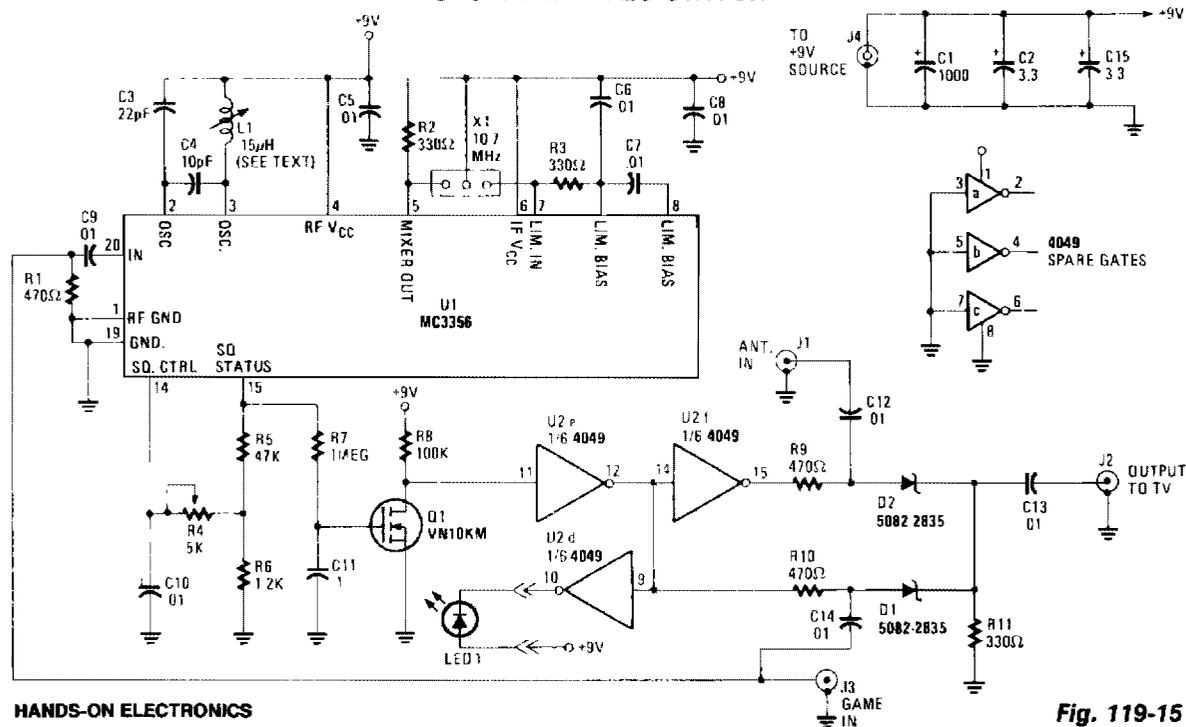


HANDS-ON ELECTRONICS

Fig. 119-15

Turn on a game, computer, videodisc player, or whatever, and its output takes priority over the antenna-derived signal—the antenna is disconnected and the alternate source is fed to the monitor. When the alternate video source is no longer detected, the switch automatically reconnects the antenna. When the rf carrier is detected, a high logic output appears at pin 15 of U1—squelch status. The signal is then buffered to VMOS FET Q1. This FET can drive CMOS inverter/buffer U2, can be an *open-drain* output to drive a relay, or can convert to a 5 V logic level. When pin 15 of U1 becomes high, Q1 turns on, pulling pin 11 of U2e low; in turn, pin 12 becomes high. The output of U2e is fed to U2f, forcing its output, at pin 15, low. When the signal at U2 pin 12 is high, D1 is biased on, allowing the signal at J3 to flow through C14, D1, and out to J2 through C13. When the signal at J3 is removed, U1 pin 15 decreases. That decrease causes U2 pin 12 to decrease and U2 pin 15 to increase. When the signal at U2 pin 15 is high, it biases D2 on, allowing the signals at J1 to flow through C12, D2, and out to J2 through C13.

## HIGH-PERFORMANCE VIDEO SWITCH

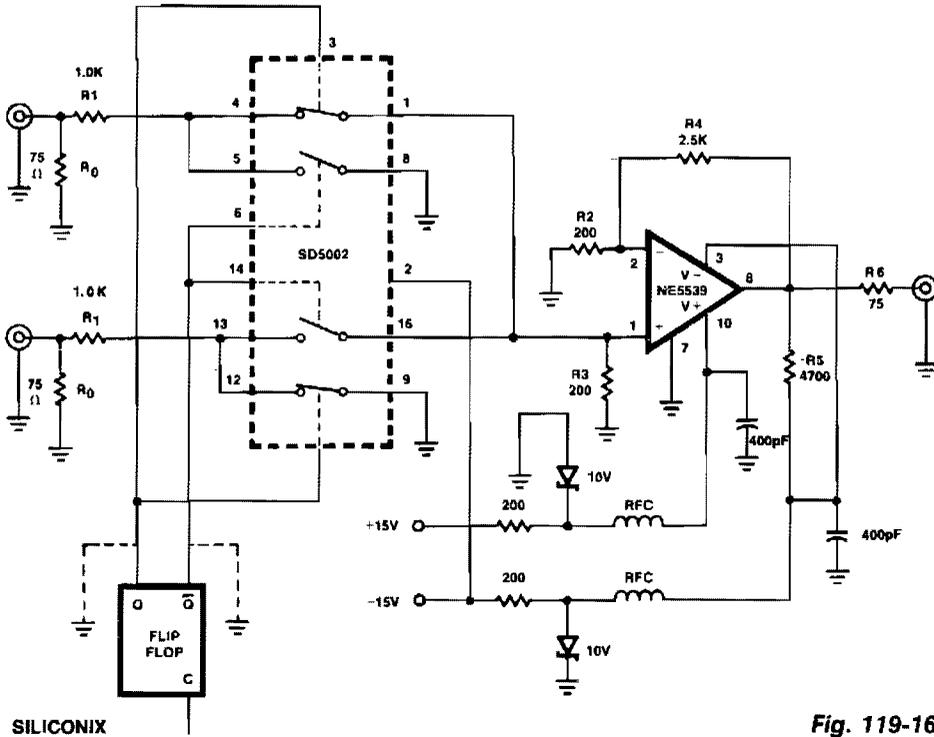

**Fig. 119-16**

This figure shows a one-of-two switch with a summing amplifier. The video source's line can be terminated either externally or internally to switch R0. With this termination resistor, a load change of less than 1 Ω will be *seen* by the source when the switch changes state. For this reason, input isolation amplifiers are not necessary. R4 can be varied to control circuit gain, but should never be less than 1400 Ω since the NE5539 is internally compensated for gain values greater than seven. A value of approximately 2500 Ω for R4 will set circuit gain to near unity. Additionally, the circuit output impedance is set by R6, and R5 sets the output dc offset to near zero.

# 120


## Voice Circuits

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Ac Line-Voltage Announcer  
Dialed Phone Number Vocalizer  
Computer Speech Synthesizer  
Allophone Generator  
Electronic Voice Substitute

## AC LINE-VOLTAGE ANNOUNCER

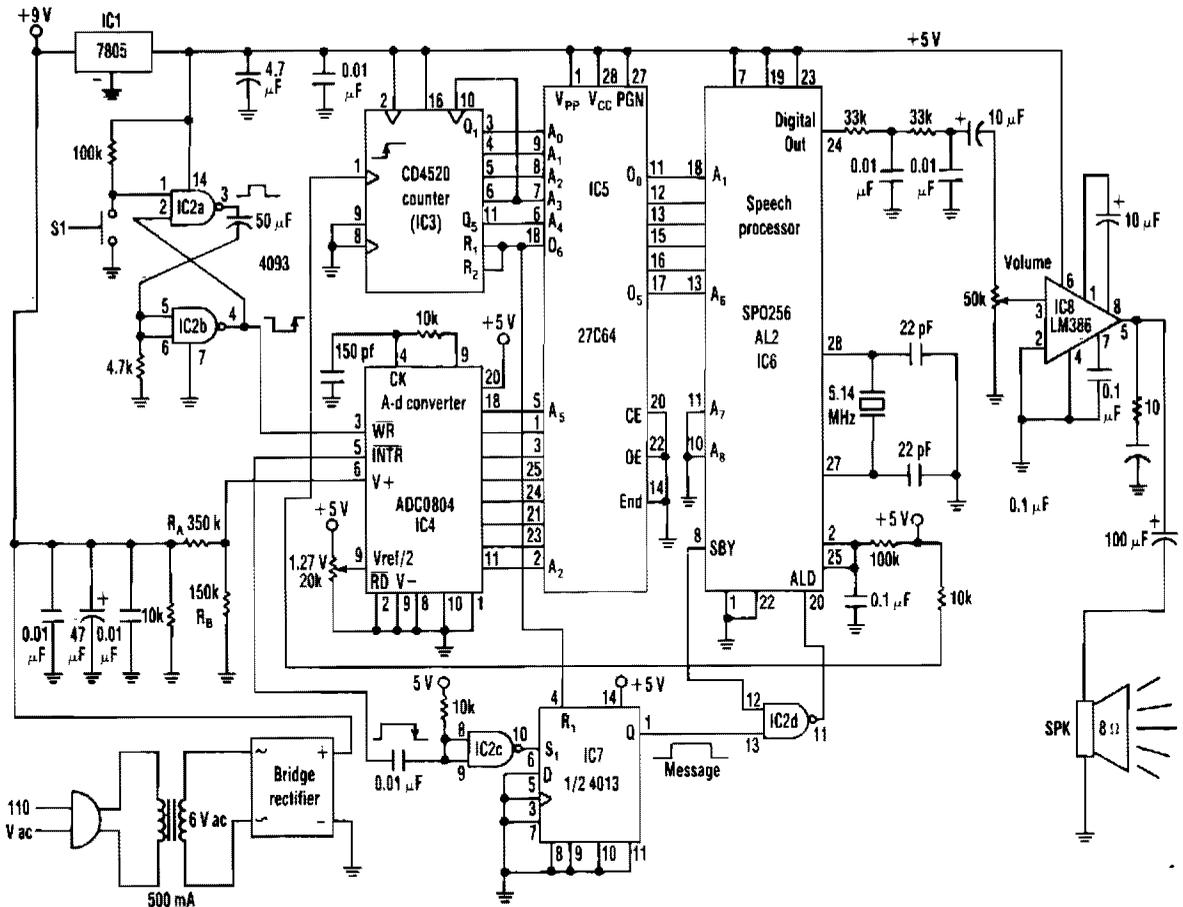


ELECTRONIC DESIGN

Fig. 120-1

The range of this ac-voltage monitor is 100 to 140 Vac, with a resolution of 1 V. The speech processor interprets an 8-bit binary input code from an analog-to-digital converter. The processor's pulse-code-modulated output then passes through a filter and an amplifier before driving the circuit's speaker to vocalize the corresponding number. Each time switch S1 is pressed, the speech-processor program enunciates the monitored voltage readings from 100 to 140 V, depending on the code at the input of a 27C64 EPROM.

The voltage-monitoring circuit consists of a bridge rectifier, filter capacitors, and a 10-KΩ load resistor. A divider,  $R_A$  and  $R_B$ , limits the input voltage to a maximum 2.55 V. The a/d converter, IC4, then sends the voltage reading to the 27C64 EPROM, IC5. Pressing S1 sends a negative transient pulse to the write, WR, input of the a/d converter, IC4, which initiates a 100-µs conversion process.

## DIALED PHONE NUMBER VOCALIZER

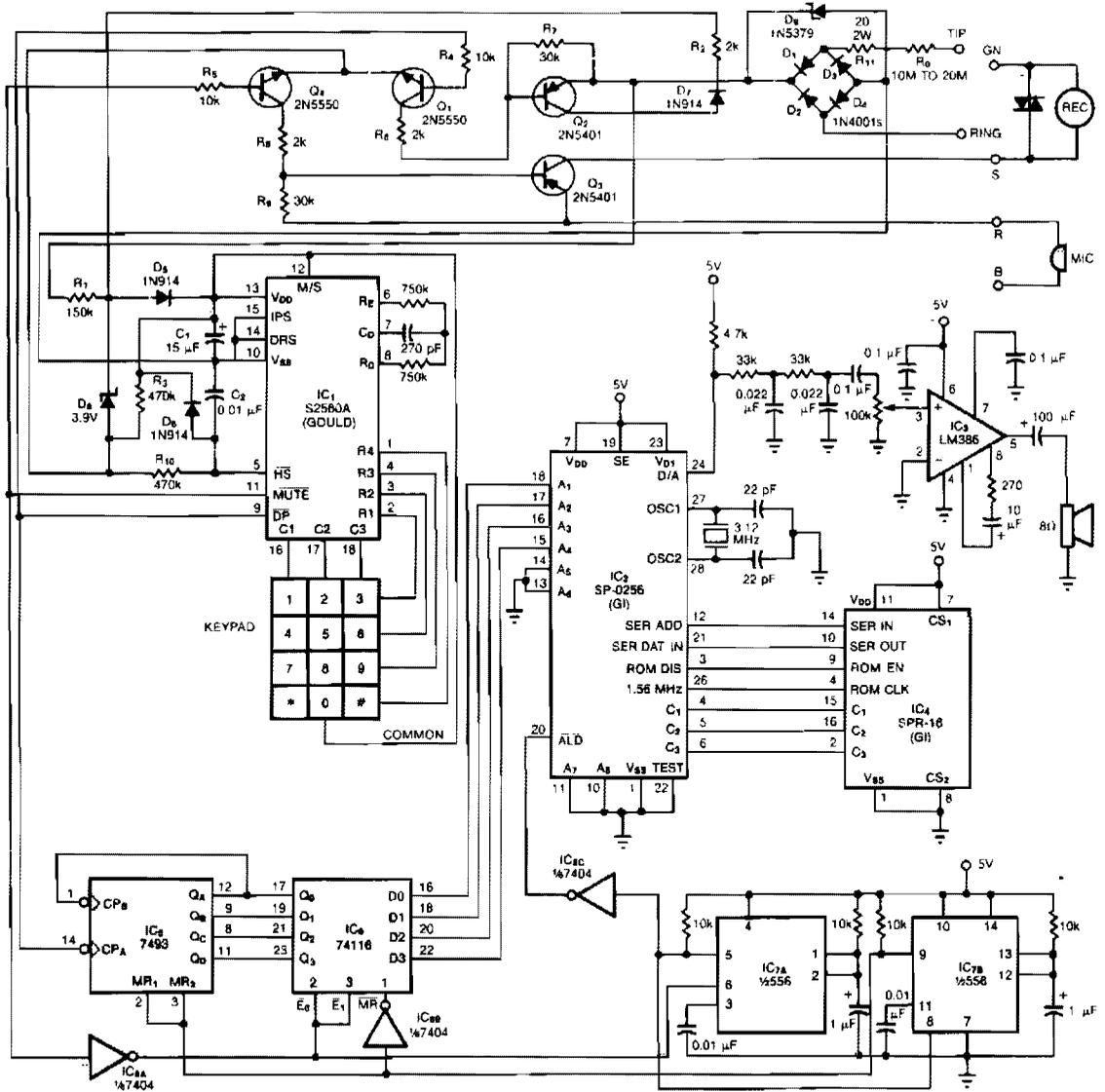


EDN

Fig. 120-2

By vocalizing the numbers and symbols of its keypad, the phone provides an audible confirmation that is useful to the blind. The serial-interface, 2 K-byte  $\times$  8-bit ROM (IC4) stores programmed sequences of instructions that are executed by the speech-processor chip IC2—manufactured by the General Instrument Corp. When you depress a key, tone-dialing chip IC1 issues the corresponding number of pulses at its DP output. Counter IC5 totals the pulses, and IC6 latches the resulting 4-bit digital word. This word, converted to serial format by IC2, becomes an address that selects a block of memory within IC4.

## COMPUTER SPEECH SYNTHESIZER

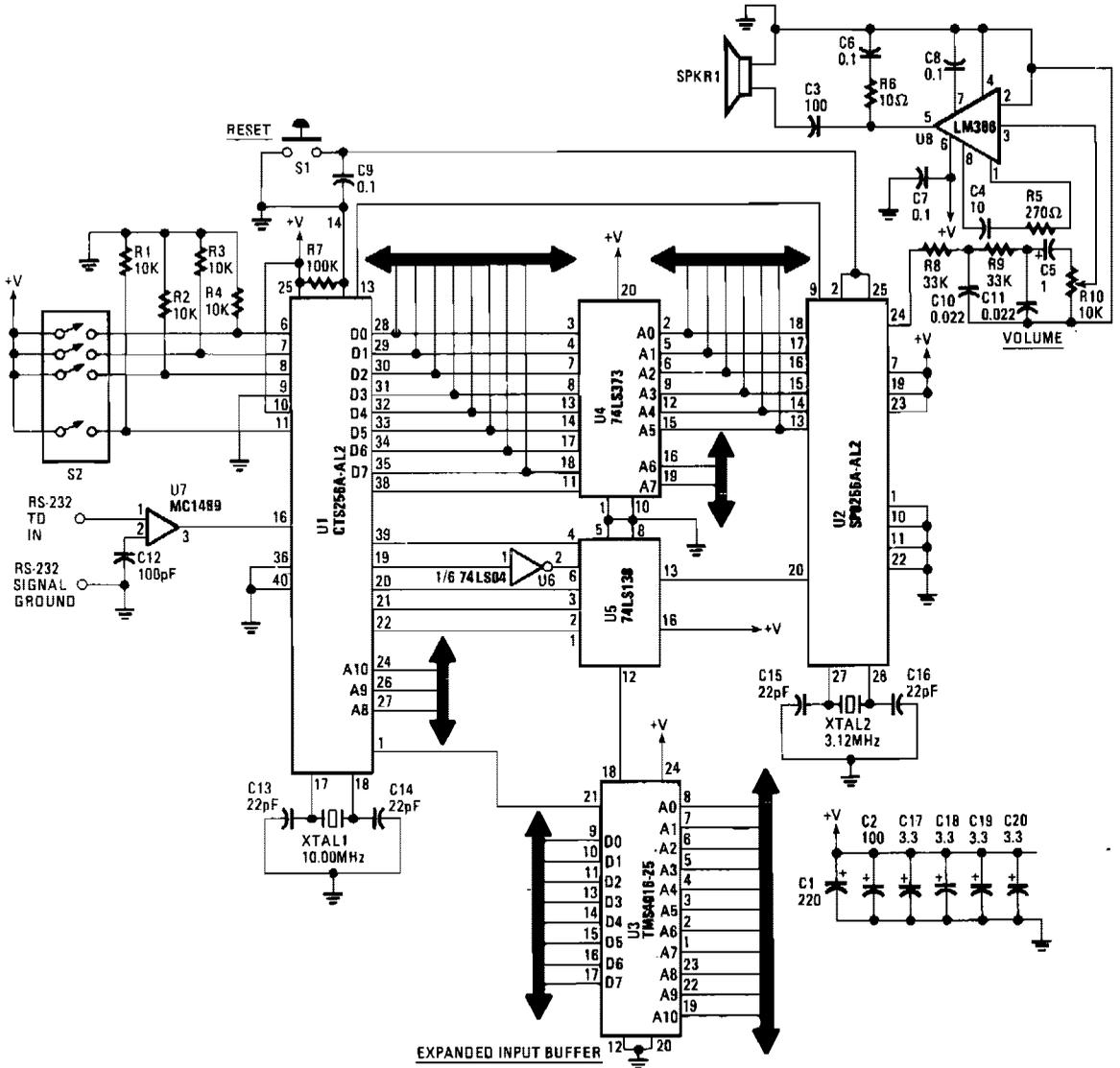

HANDS-ON ELECTRONICS


Fig. 120-3

This text-to-speech converter is built around the SPO256-AL2 speech processor and the CT6256-AL2 text-to-speech converter chips—manufactured by General Instruments. The circuit is set up to receive standard ASCII code from virtually any microcomputer or dumb terminal that is equipped with an RS-232 port—such as a serial-printer or modem port. If a microcomputer is used, the synthesizer can be activated from a terminal-emulator of any communications program, or from any programming language such as BASIC.

## COMPUTER SPEECH SYNTHESIZER (Cont.)

The serial input from the RS-232 port enters the circuit through U7, the MC1489 RS-232 receiver chip, and is converted from an RS-232 level to a TTL-level signal. The CTS256-AL2 chip, U1, then converts the ASCII characters into allophone codes and sends those codes to U3, the TMS4016 external-RAM chip. The codes are then transferred to the SPO256-AL2, U2, through the 74LS373 octal latch, U4. Finally, the SPO256-AL2 sends out an audio signal to the LM386 audio amplifier, U8, through some high-pass filtering, and on to the speaker. The 74LS138d, U5, and the 74LS04, U6, provide control logic.

### ALLOPHONE GENERATOR

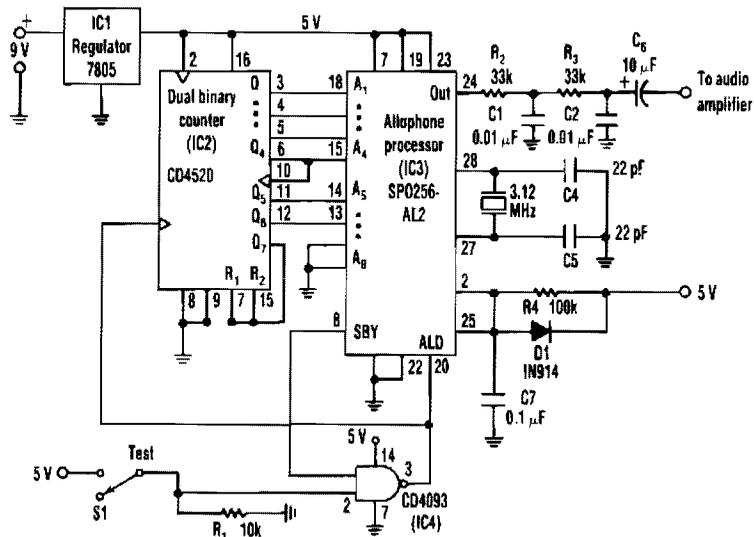


ELECTRONIC DESIGN

Fig. 120-4

The circuit, a general-purpose system with many uses, vocalizes 59 allophones contained in the speech processor. After filtering and amplification, its pulse-code-modulated output can drive an 8- $\Omega$  speaker. The processor's address pins, A1 to A6, define 64 speech-entry points.

Closing the test switch to the NAND gate lowers its output, thereby loading an address and triggering the ALD input for an allophone cycle. The CD4520 dual binary counter, IC2, counts from 0 to 63 in binary code until its Q7 output resets it on the number 64 count. To generate a phrase, just add an EPROM between IC2 and IC3 that contains a program for a predetermined sequence of allophones.

## ELECTRONIC VOICE SUBSTITUTE

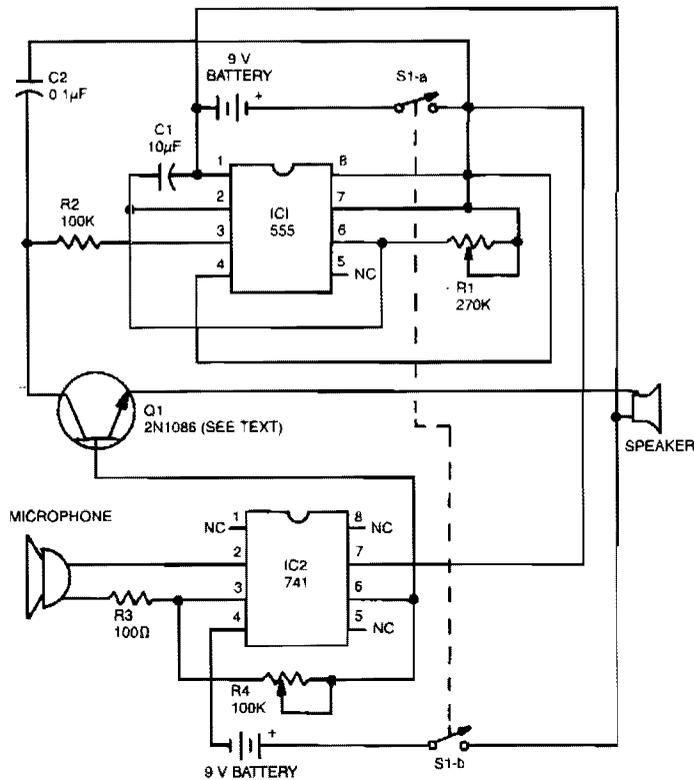

GERNSBACK PUBLICATIONS INC.

Fig. 120-5

The 555 acts as the tone generator configured in the astable mode. Its pin 3, square-wave output is transformed into a triangle wave by R1 and C2. The *voice's* pitch is controlled by R1. Transistor Q1 can be 2N1086, 2N1091, or any other equivalent npn germanium type. Sounds are amplified by the 741, and the IC's output drives the transistor to saturation. When the transistor is in the saturated state, the triangle wave is able to reach the speaker, and your new *voice* can be heard.

# 121

## Voltage-Controlled Oscillators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Balanced TMOS VCO

Waveform Generator/Stable VCO

Variable-Capacitance Diode-Sparked VCO

Logarithmic Sweep VCO


Supply Voltage Splitter

3–5 V Regulated Output Converter

VCO

Simple VCO

## BALANCED TMOS VCO

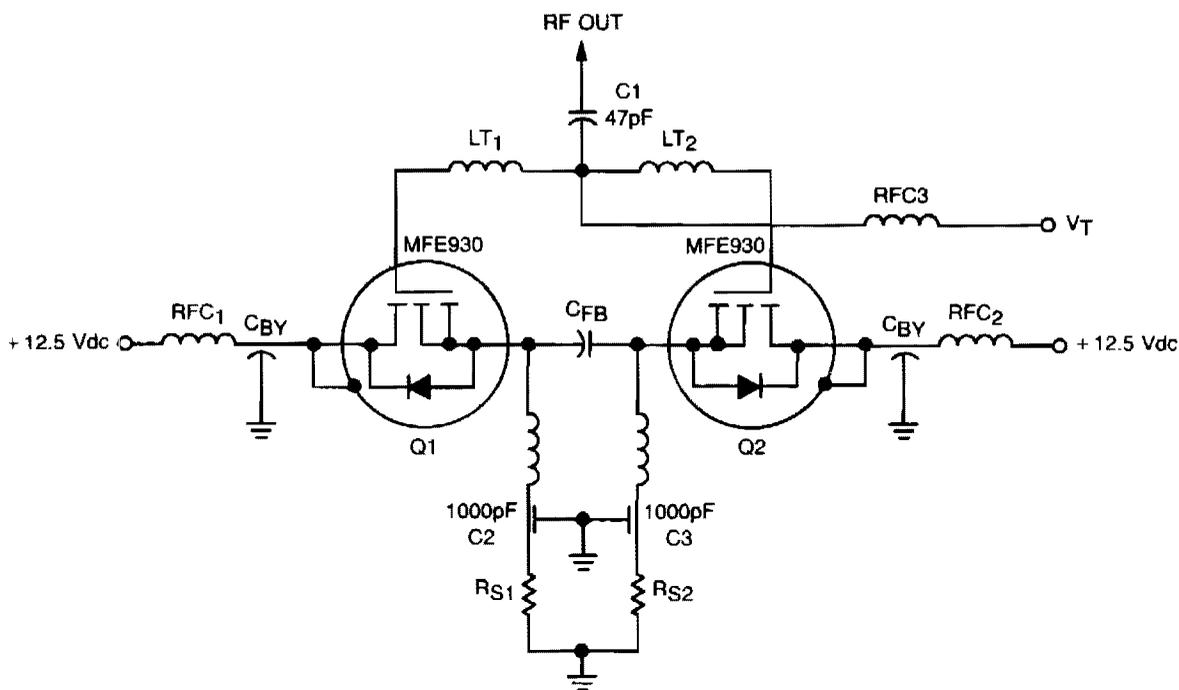

Copyright of Motorola, Inc. Used by permission.

Fig. 121-1

This TMOS VCO operates in push-pull to produce 4 W at 70 MHz. It consists of two MFE930 TMOS devices in a balanced VCO that generally provide better linearity than the single-ended types. Varactors are not used because the design takes advantage of the large change in *Miller* capacitance,  $C_{RSS}$ , that is available in TMOS gate structures.


In the balanced VCO, the fundamental ( $f_O$ ) and/or twice the fundamental ( $2f_O$ ) can be coupled from the circuit at separate nodes. This makes the balanced oscillator very useful in phase-locked loops. The fundamental:

$$f_O = \frac{1}{2} (L_F C_{RSS})^{-1/2}$$

where:

$$L_F = 0.68 \mu\text{H}$$

## WAVEFORM GENERATOR/STABLE VCO

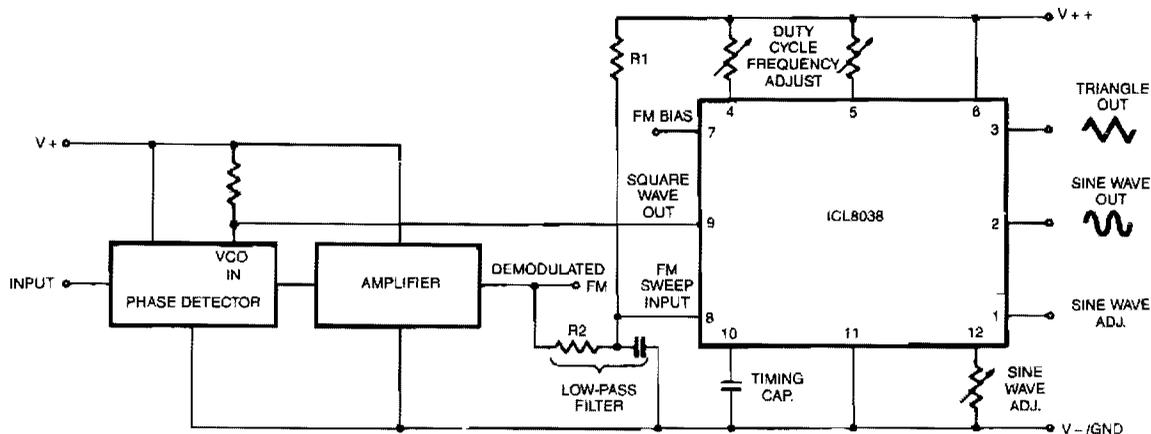


INTERSIL

**Fig. 121-2**

In this circuit, a waveform generator is used as a stable VCO in a Phase-Locked Loop (PLL).
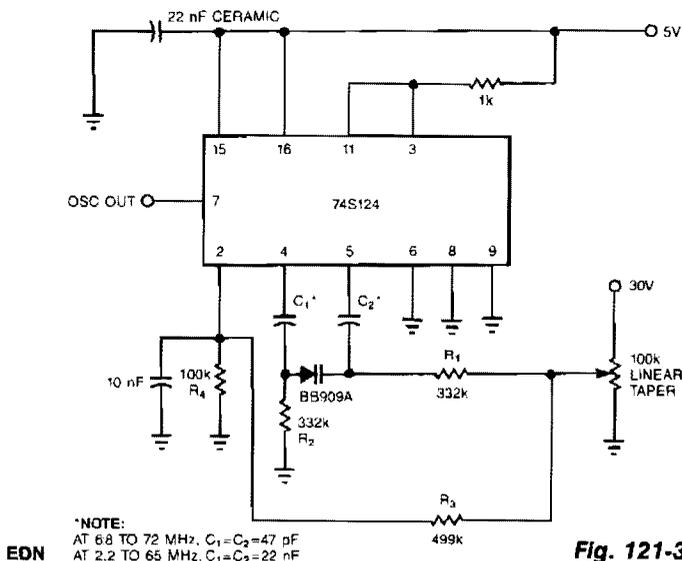
## VARIABLE-CAPACITANCE DIODE-SPARKED VCO



EDN

**Fig. 121-3**

You can transform a 74S124 multivibrator into a wideband VCO by replacing its conventional fixed capacitor with a variable-capacitance diode. The only disadvantage of this scheme is the 30-V biasing voltage that the diode requires. Capacitors  $C_1$  and  $C_2$  couple the Philips BB909A variable-capacitance diode to the 74S124.  $R_1$  and  $R_2$  are large enough to isolate ground and control voltages from the timing capacitors. Resistors  $R_3$  and  $R_4$  form a voltage divider for the 74S124's control input.

## LOGARITHMIC SWEEP VCO


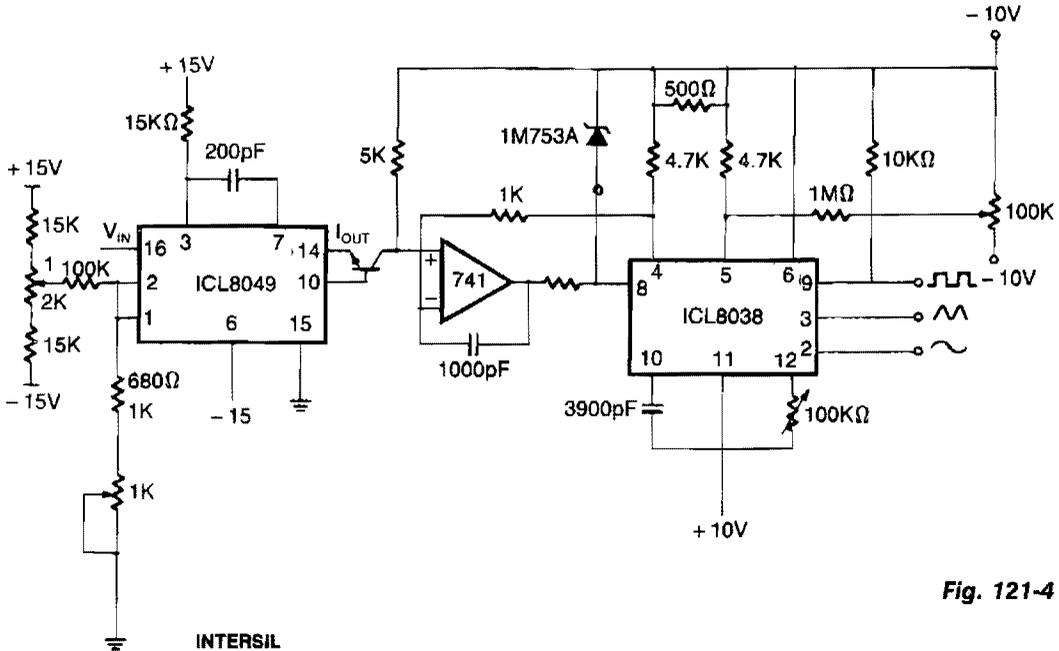


Fig. 121-4

This circuit uses the output of the ICL8049 to control the frequency of the ICL3038 waveform generator; the 741 op amp is used to linearize the voltage-frequency response. The input voltage to the 8049 can be, for example, from the horizontal sweep signal of an oscilloscope; the output of the 8038 will then sweep logarithmically across the audio range. By feeding this to the equipment being measured and detecting the output, a standard frequency response can be obtained. If the output is fed through an ICL8048 before being displayed, a standard bode plot results.

## SUPPLY VOLTAGE SPLITTER

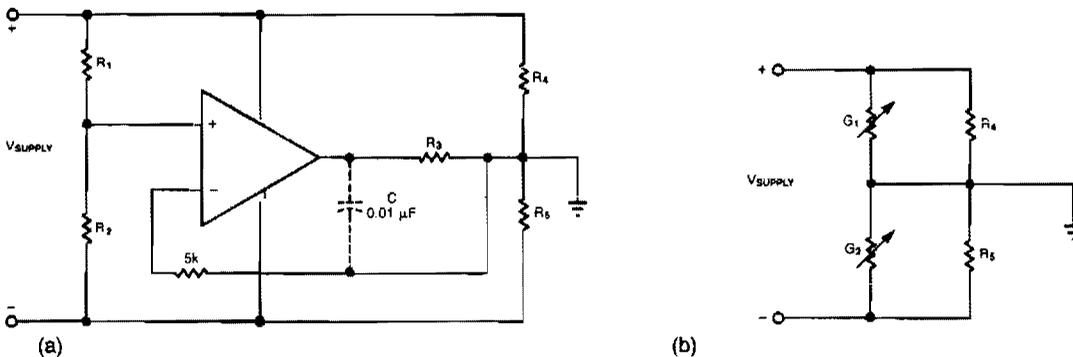


EDN

Fig. 121-5

## SUPPLY VOLTAGE SPLITTER (Cont.)

This simple circuit can convert a single supply voltage, such as a battery, into a bipolar supply. Sense resistors R1 and R2 establish relative magnitudes for the resulting positive and negative voltages. Their rail-to-rail value, of course, equals  $V_{SUPPLY}$ . R4 and R5 represent the load impedances. For example, equal-value sense resistors produce  $1/2 V_{SUPPLY}$  across each of the load resistors, R4 and R5. The op amp maintains these equal voltages by sinking or sourcing current through R3; the op amp's action is equivalent to that of variable conductances G1 and G2 in shunt with each load resistor. Choose a value for R3 so that the largest voltage across it, the greatest load-current mismatch, won't exceed the op amp's output-voltage capability for the application. You can add a buffer amplifier at the op amp's output to provide greater load currents. If you need bypass capacitors across the load resistors as well, connect a capacitor (dashed lines) to ensure that the amplifier remains stable.



## 3 - 5 V REGULATED OUTPUT CONVERTER

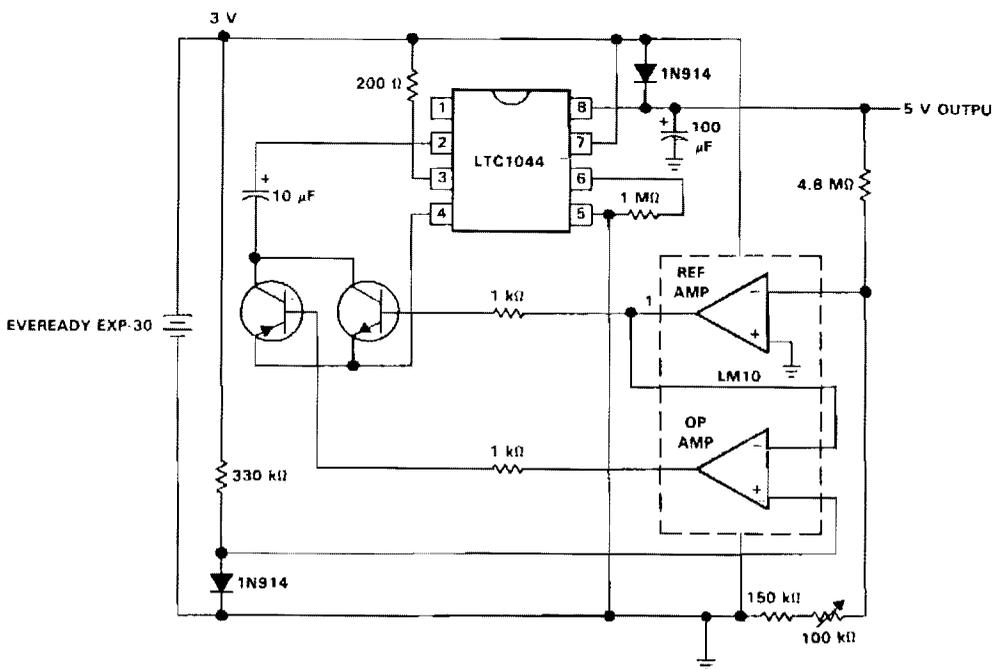

Reprinted by permission of Texas Instruments.

Fig. 121-6

## VCO

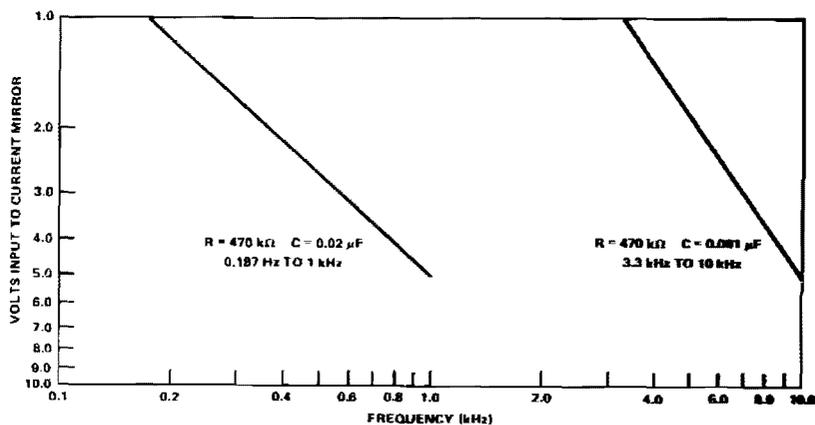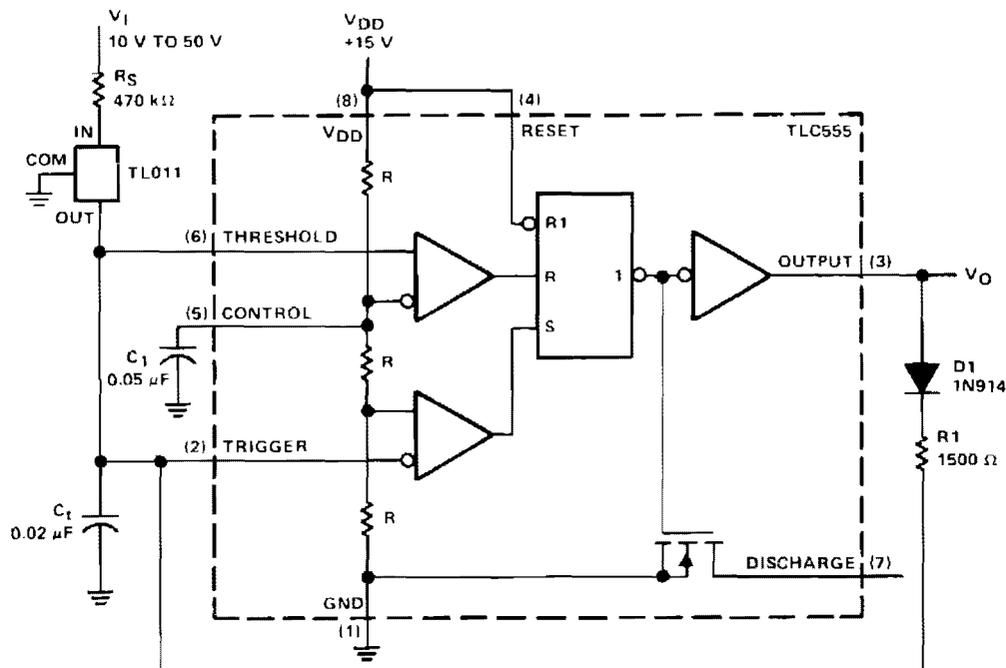

Voltage-Controlled Oscillator Frequency vs Voltage


Reprinted by permission of Texas Instruments.

Fig. 121-7

At startup, the voltage in the trigger input at pin 2 is less than the trigger level voltage,  $\frac{1}{3} V_{DD}$ , causing the timer to be triggered via pin 2. The output of the timer at pin 3 becomes high, allowing capacitor  $C_t$  to charge very rapidly through diode  $D_1$  and resistor  $R_1$ .

When capacitor  $C_t$  charges to the upper threshold voltage  $\frac{2}{3} V_{DD}$ , the flip-flop is reset, the output at pin 3 decreases, and capacitor  $C_t$  discharges through the current mirror, TL011. When the voltage at pin 2 reaches  $\frac{1}{3} V_{DD}$ , the lower threshold or trigger level, the timer triggers again and the cycle is repeated.

## SIMPLE VCO

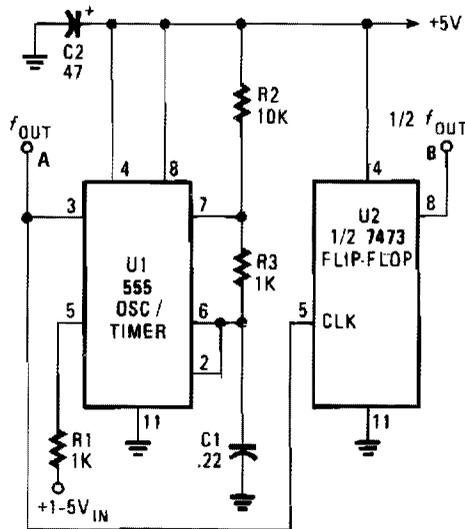

POPULAR ELECTRONICS

Fig. 121-8

The output frequency of the VCO, U1, varies inversely with the input voltage. With a 1-V input, the oscillator output frequency is about 1500 Hz; with a 5-V input, the output frequency drops to around 300 Hz. The output frequency range of U1 can be altered by varying the values of C1, R2, and R3. Increasing the value of any of those three components will lower the oscillator frequency, and decreasing any of those values will raise the frequency. Output-waveform symmetry suffers since the frequency varies from one extreme to the other. At the highest frequency, the waveform is almost equally divided. But when the frequency drops, the output of the circuit turns into a narrow pulse. If a symmetrical waveform is required, add the second IC, U2, half of a 7473P dual TTL J-K flip-flop, to the oscillator circuit. The signal frequency output by U2 is  $1/2$  of the input.

# 122

## Voltage Converters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Unipolar-to-Dual Supply Converter

Efficient Supply Splitter

High-Efficiency Flyback Voltage Converter

3 – 25 V Dc-Dc Converter

Regulated  $15-V_{OUT}$  6-V Driven Converter


1.5-W Offline Converter

Dual Output  $\pm 12$  or  $\pm 15$  V Dc-Dc Converter

12-to-6 V Converter

Self-Oscillating Flyback Converter

## UNIPOLAR-TO-DUAL SUPPLY CONVERTER

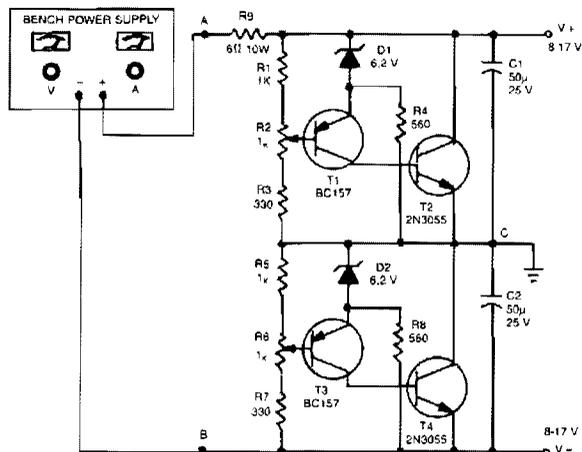


The outputs in this circuit are independently variable and can be loaded unsymmetrically. The output voltage remains constant, irrespective of load and changes. By varying potentiometers R2 or R6, the output voltages can be conveniently set. Outputs can be varied between 8 and 17 V, so that the standard  $\pm 9$ ,  $\pm 12$ , and  $\pm 15$  V settings can be made. This converter is designed for a maximum load current of 1 A and the output impedance of both supplies of  $0.35 \Omega$ . This circuit is not protected against shortcircuits, but uses the protection provided by the dc input source. This circuit is ideal for biasing operation amplifier circuits.

ELECTRONIC ENGINEERING

Fig. 122-1

## EFFICIENT SUPPLY SPLITTER

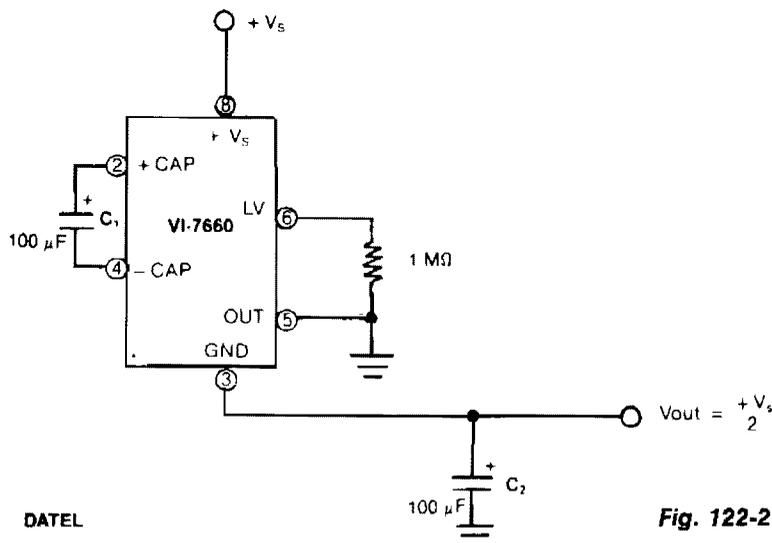


DATEL

Fig. 122-2

In this application, the VI-7660 is connected as a voltage splitter. Note that the *normal* output pin is connected to ground and the *normal* ground pin is used as the output. The switches that allow the charge pumping are bidirectional; therefore, charge transfer can be performed in reverse. The  $1\text{-}M\Omega$  resistor is used to avoid start-up problems by forcing the internal regulator on. An application for this circuit would be driving low-voltage,  $\pm 7.5$  Vdc, circuits from  $\pm 15$  Vdc supplies, or low-voltage logic from 9 to 12 V batteries.
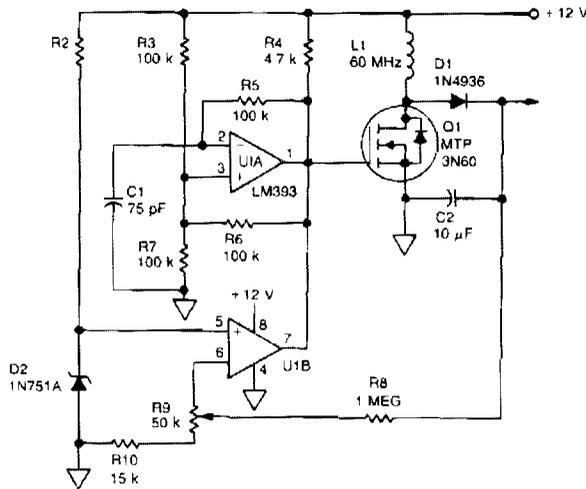
## HIGH-EFFICIENCY FLYBACK VOLTAGE CONVERTER



Copyright of Motorola, Inc. Used by permission.


Fig. 122-3

U1 is a dual voltage comparator with open collector outputs. The A side is an oscillator operating at 100 kHz, and the B side is part of the regulation circuit that compares a fraction of the output voltage to a reference generated by zener diode D2.

The output of U1A is applied directly to the gate of Q1. During the positive half-cycle of the Q1 gate voltage, energy is stored in L1; in the negative half, the energy is discharged into C2. A portion of the output voltage is fed back to U1B to provide regulation. The output voltage is adjustable by changing feedback potentiometer R9.

Using the component values shown will produce a nominal 300-V output from a 12-V source. However, the circuit maximum output voltage is limited by R10; a lower value for R10 yields a higher output voltage. The output voltage is also limited by the breakdown of values Q1, L1, D1, and C2.


## 3 - 25 V DC-DC CONVERTER

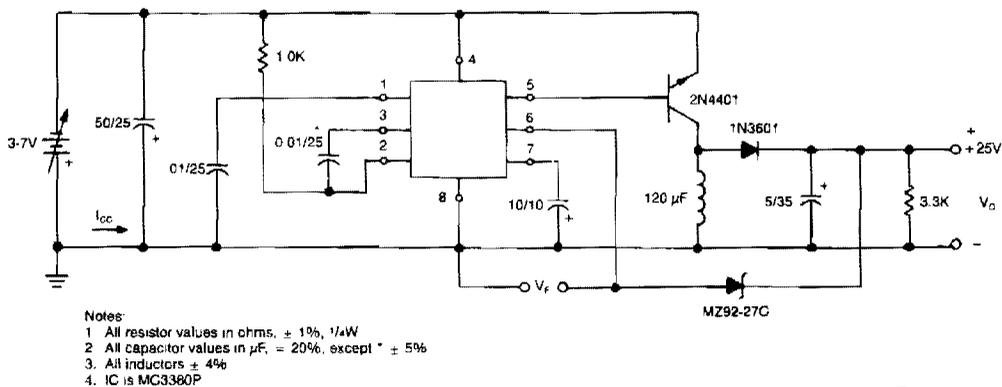

Copyright of Motorola, Inc. Used by permission.

Fig. 122-4
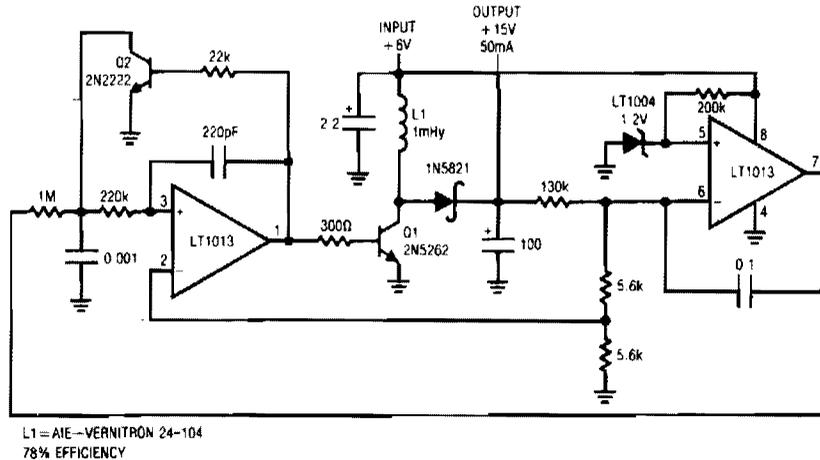
## REGULATED 15-V<sub>OUT</sub> 6-V DRIVEN CONVERTER



LINEAR TECHNOLOGY CORP.


Fig. 122-5

This converter delivers up to 50 mA from a 6-V battery with 78% efficiency. This flyback converter functions by feedback-controlling the frequency of inductive flyback events. The inductor's output, rectified and filtered to dc, biases the feedback loop to establish a stable output. If the converter's output is below the loop setpoint, A2's inputs unbalance and current is fed through the 1-MΩ resistor at A1. This ramps the 1000-pF value positive. When this ramp exceeds the 0.5-V potential at A1's positive input, the amplifier switches high. Q2 turns on, discharging the capacitor to ground. Simultaneously, regenerative feedback through the 200-pF value causes a positive-going pulse at A1's positive input, sustaining A1's positive output. Q1 comes on, allowing inductor, L1, current to flow. When A1's feedback pulse decays, its output becomes low, turning off Q1. Q1's collector is pulled high by the inductor's flyback and the energy is stored in the 100-μF capacitor. The capacitor's voltage, which is the circuit output, is sampled by A2 to close a loop around A1/Q1. This loop forces A1 to oscillate at whatever frequency is required to maintain the 15-V output.

In-phase transformer windings for the drain and gate of TMOS power FET Q1 cause the circuit to oscillate. Oscillation starts when the feedback coupling capacitor, C1, is charged from the supply line via a large resistance; R2 and R3 limit the collector current to Q2. During *pump-up*, the on time is terminated by Q2, which senses the ramped source current of Q1. C1 is charged on alternate half-cycles by Q2 and forward-biased by zener D2.

When the regulated level is reached, forward bias is applied to Q2, terminating the on time earlier at a lower peak current. When this occurs, the frequency increases in inverse proportion to current, but the energy per cycle decreases in proportion to current squared. Therefore, the total power coupled through the transformer to the secondary is decreased.


## 1.5-W OFFLINE CONVERTER

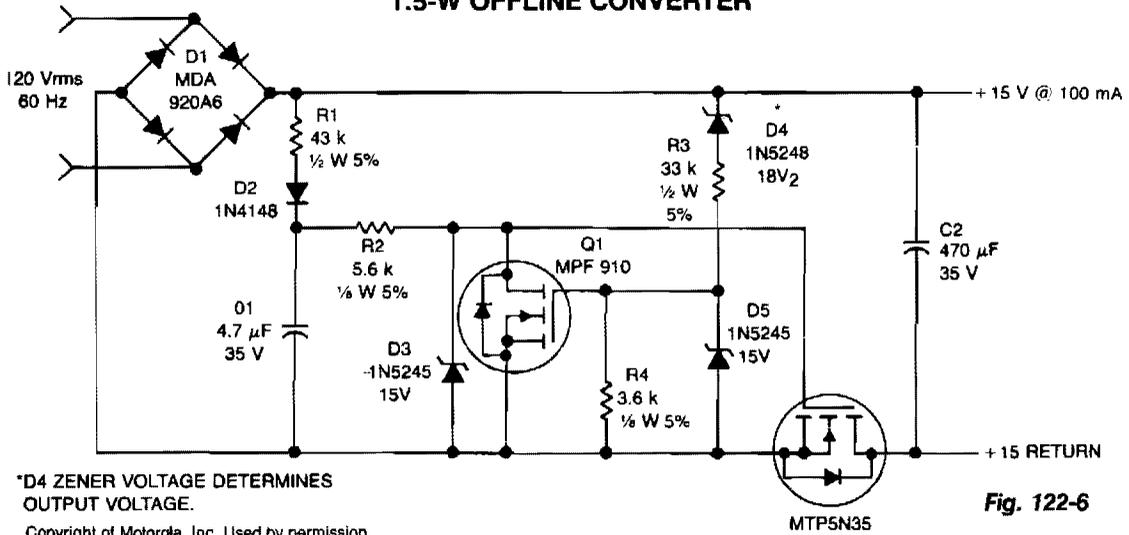

This nonisolated, unregulated, minimum component converter fills the void between low-power zener regulation and the higher power use of a 60-Hz input transformer. It is intended for use wherever a nonisolated supply can be used safely.

The circuit operates by conducting only during the low-voltage portion of the rectified sine wave. R1 and D2 charge C1 to approximately 20 V, which is maintained by Q1. This voltage is applied to the gate of Q2, turning it on. When the rectified output voltage exceeds the zener voltage of D4, Q1 turns on, shunting the gate of Q2 to ground, turning it off.

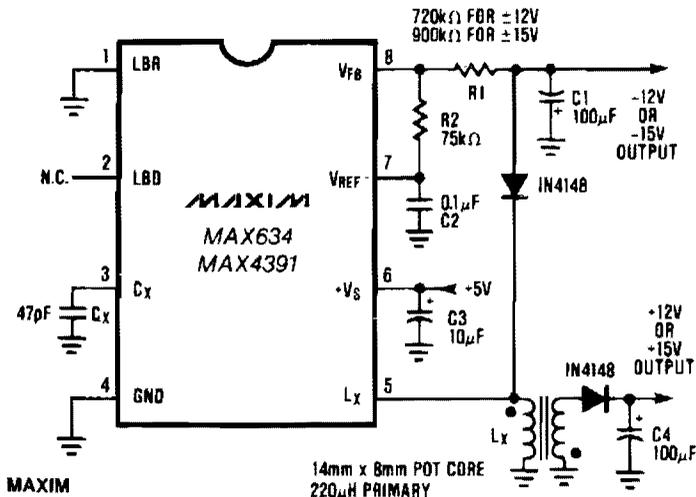
## DUAL OUTPUT $\pm 12$ OR $\pm 15$ V DC-DC CONVERTER



## DUAL OUTPUT $\pm 12$ OR $\pm 15$ V DC-DC CONVERTER (Cont.)

The buck-boost configuration of the MAX634 is well suited for dual output dc-dc converters. Only a second winding on the inductor is needed. Typically, this second winding is bifilar—primary and secondary are wound simultaneously using two wires in parallel. The inductor core is usually a toroid or a pot core. The negative output voltage is fully regulated by the MAX634. The positive voltage is semiregulated, and will vary slightly with load changes on either the positive or negative outputs.

### 12-TO-16 V CONVERTER

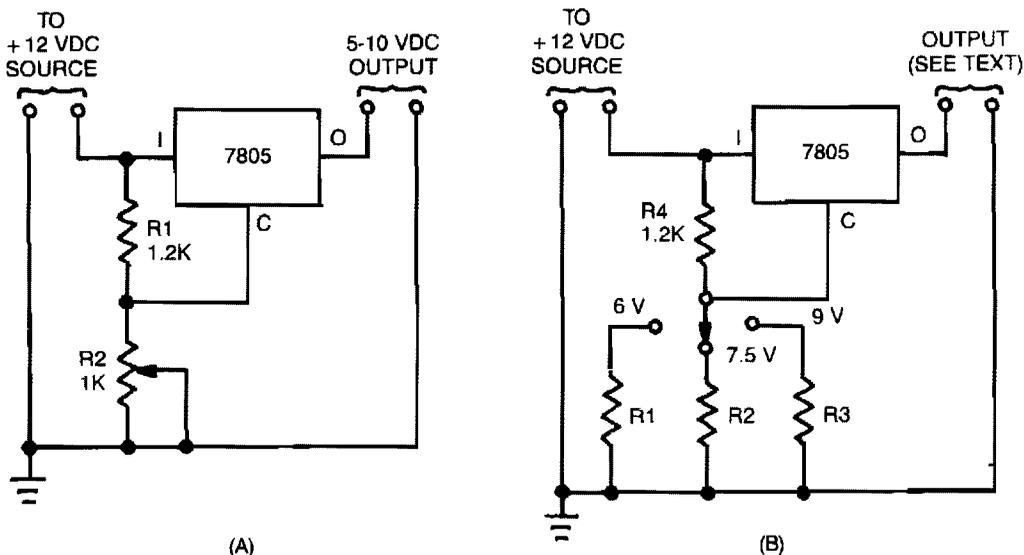


Reprinted with permission of Radio-Electronics Magazine, April 1985. Copyright Gernsback Publications, Inc., 1985.

Fig. 122-8

Many devices operate from a car's 12-V electrical system. Some require 12 V; others require some lesser voltage. An automobile battery's output can vary from 12 to 13.8 V under normal circumstances. The load requirements of the device might vary. This circuit maintains a constant voltage regardless of how those factors change. Simple circuit, A, uses a 7805 voltage regulator. In addition to a constant output, this IC provides overload and short-circuit protection. That unit is a 5-V, 1-A regulator, but when placed in circuit B, it can provide other voltages as well. When the arm of potentiometer R1 is moved toward ground, the output varies from 5 to about 10 V.
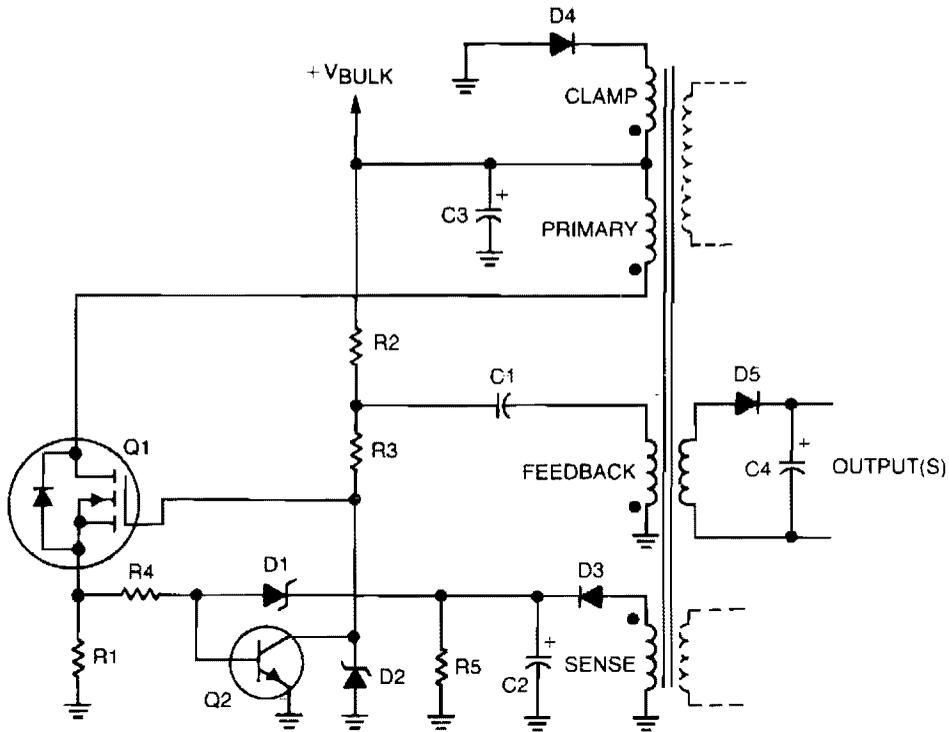
## SELF-OSCILLATING FLYBACK-SWITCHING CONVERTER



Copyright of Motorola, Inc. Used by permission.

Fig. 122-9

Regulation is provided by taking the rectified output of the sense winding and applying it as a bias to the base of Q2 via zener D1. The collector of Q2 then removes drive from the gate of Q1. Therefore, if the output voltage should increase, Q2 removes the drive to Q1 earlier, shortening the on time, and the output voltage will remain the same. Dc outputs are obtained by merely rectifying and filtering secondary windings, as done by D5 and C4.

# 123

## Voltage-to-Frequency Converters

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

1 Hz-to-30 MHz Voltage-to-Frequency  
Converter

Differential-Input Voltage-to-Frequency  
Converter

Low-Cost Voltage-to-Frequency Converter

Wide-Range Voltage-to-Frequency Converter

5 kHz-to-2 MHz Voltage-to-Frequency  
Converter

Preserved Input Voltage-to-Frequency  
Converter

1 Hz-to-10 MHz Voltage-to-Frequency  
Converter


Voltage-to-Frequency Converter

1 Hz-to-1.25 MHz Voltage-to-Frequency .  
Converter

Accurate Voltage-to-Frequency Converter  
Voltage-to-Frequency Converter


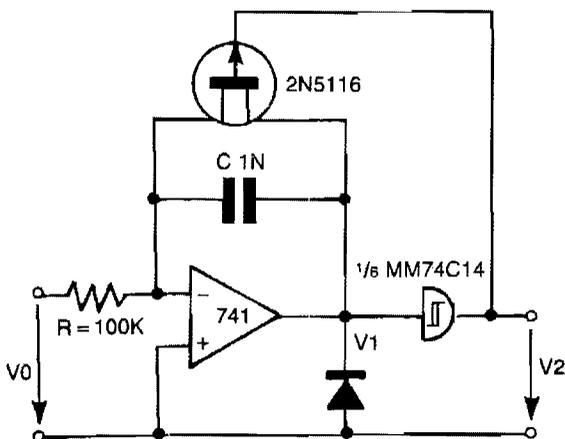
## LOW-COST VOLTAGE-TO-FREQUENCY CONVERTER




ELECTRONIC ENGINEERING

Fig. 123-3

The 741 op amp integrator signal is fed into the Schmitt trigger input of an inverter. When the signal reaches the magnitude of the positive-going threshold voltage, the output of the inverter is switched to zero. The inverter output controls the FET switch directly. For a gate voltage of zero, the FET channel turns on to low resistance and the capacitor is discharged. The discharge current depends on the on resistance of the FET. When the capacitor C1 is discharged to the negative-going threshold level of the inverter, the inverter output is switched to  $\pm 12$  V. This switch causes the FET channel to be switched off, and the discharging process is switched into a charging process again. Using the components shown, an output frequency of about 10 kHz with 0.1% linearity can be obtained.
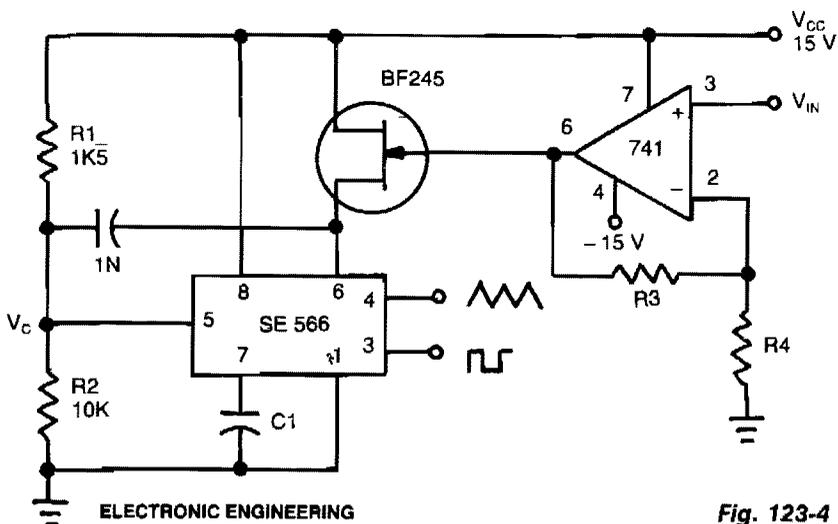
## WIDE-RANGE VOLTAGE-TO-FREQUENCY CONVERTER



ELECTRONIC ENGINEERING

Fig. 123-4

This circuit is based upon the change of frequency of the function generator with the input voltage  $V_{IN}$ . Generally, the frequency depends upon the capacitance and resistor connected to pin 6. This resistor is replaced by the FET. The frequency range is adjustable by changing the input voltage,  $V_{IN}$ ; the converter will give a range of 10 Hz to 1 MHz.



## PRESERVED INPUT VOLTAGE-TO-FREQUENCY CONVERTER

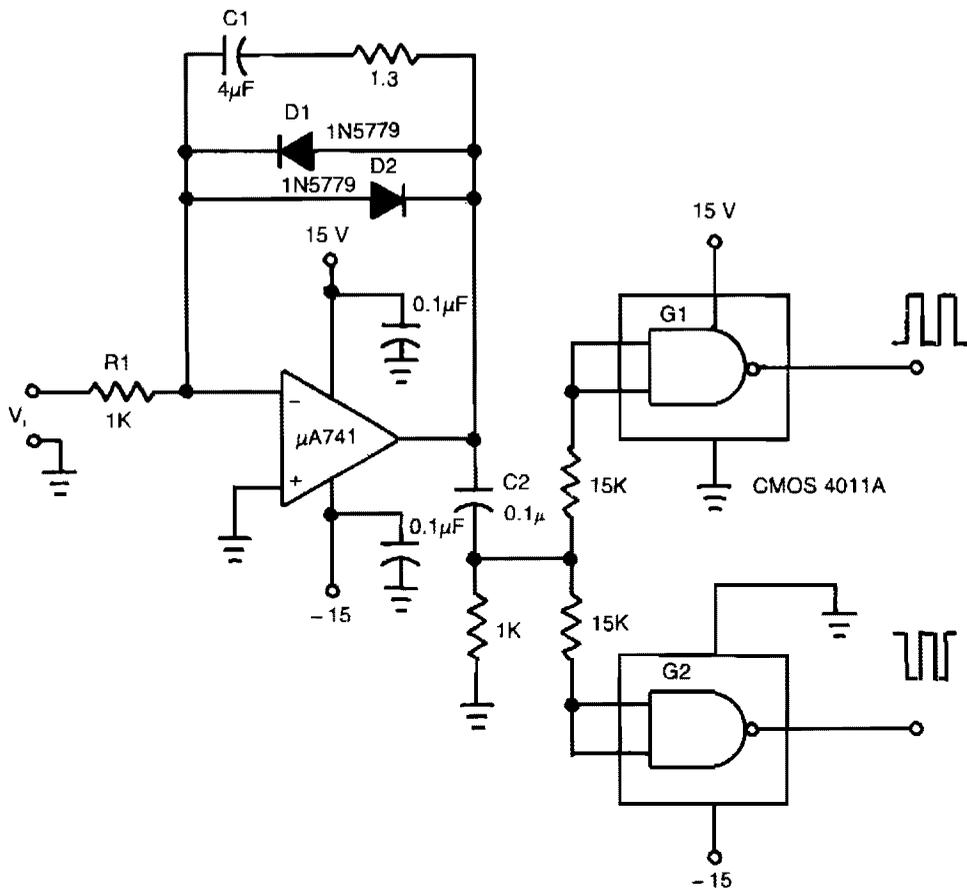



Fig. 123-7

### ELECTRONIC DESIGN

The input voltage,  $V_1$ , causes  $C_1$  to charge and produce a ramp voltage at the output of the 741 op amp. Diodes  $D_1$  and  $D_2$  are four-layer devices. When the voltage across  $C_1$  reaches the breakover voltage of either diode, the diode conducts to discharge  $C_1$  rapidly and the op amp output goes abruptly to zero. This rapid discharge action applies a narrow pulse to  $G_1$  and  $G_2$ . Positive discharge pulses produced by a positive  $V_1$  are coupled to the output only through  $G_1$ , while negative pulses are coupled only through  $G_2$ .

Because of the forward breakover current of diodes  $D_1$  and  $D_2$ , the circuit won't operate below a minimum input voltage. An increase of  $R_1$  increases this minimum voltage and reduces the circuit's dynamic range. The minimum input voltage with  $R_1$  at  $1\text{ K}\Omega$  is in the range of 10 to 50 mV. This input dead zone, when input signal  $V_1$  is near zero is desirable in applications that require a signal to exceed a certain level before an output is generated.

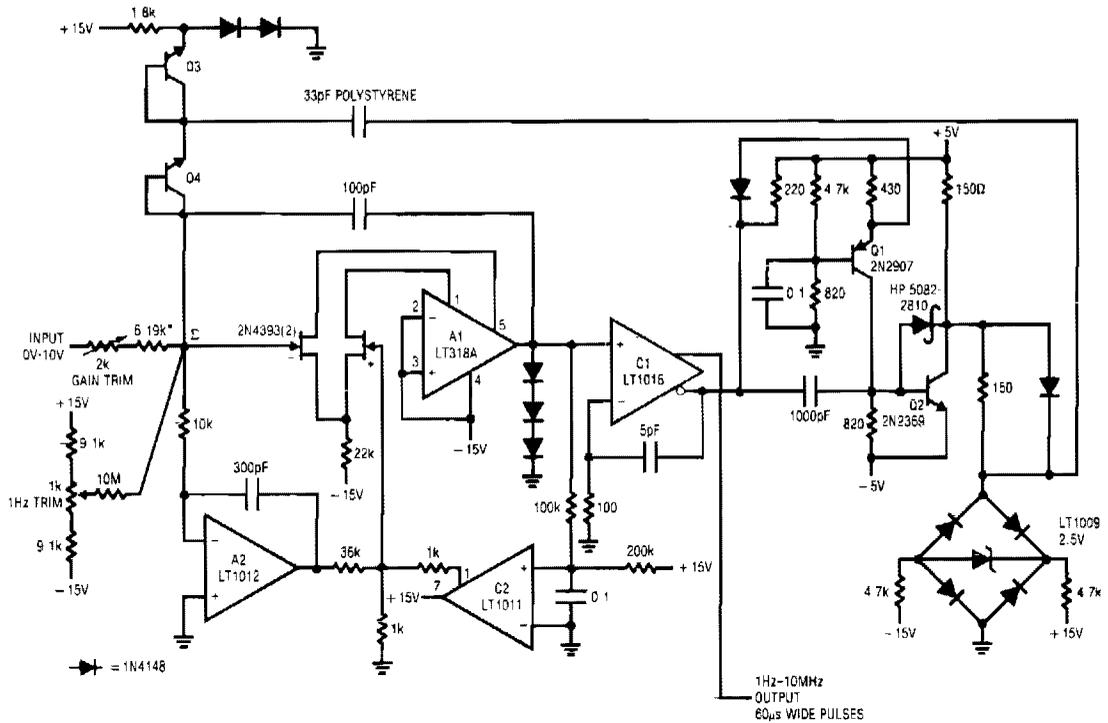
## 1 Hz-TO-10 MHz VOLTAGE-TO FREQUENCY CONVERTER



LINEAR TECHNOLOGY CORP.

**Fig. 123-8**

## VOLTAGE-TO-FREQUENCY CONVERTER

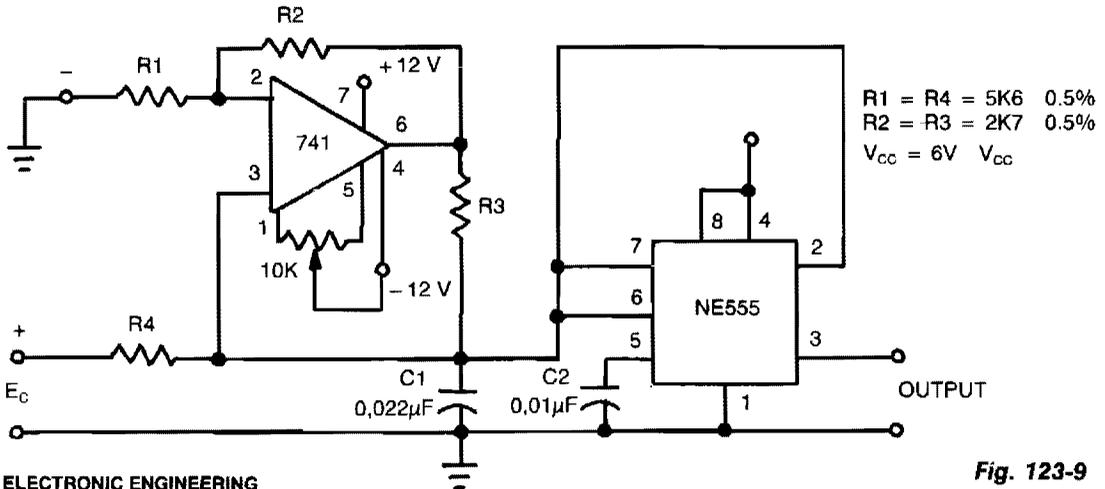


**Fig. 123-9**
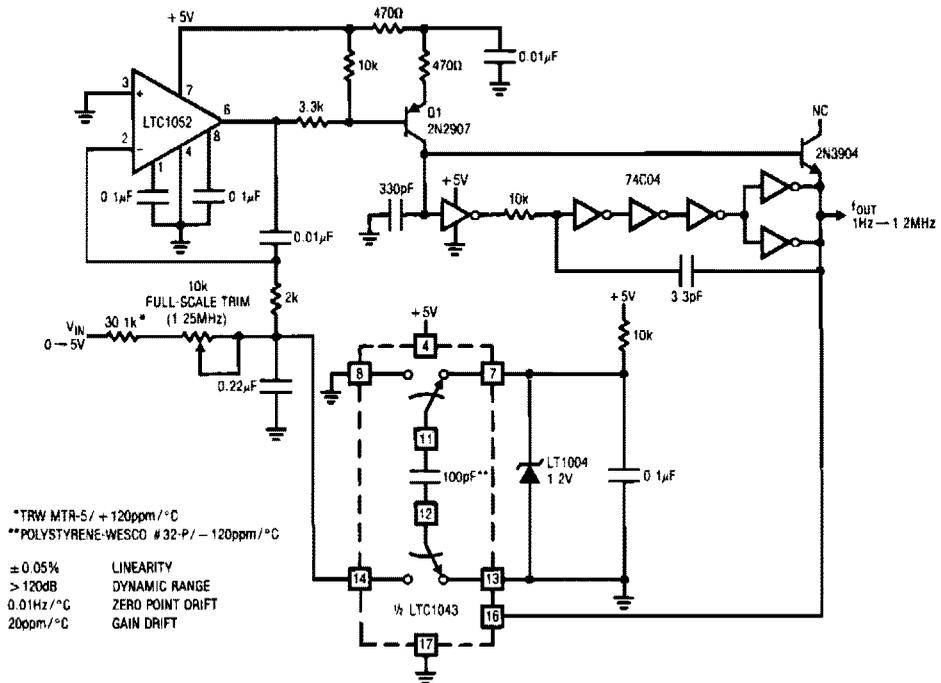
## VOLTAGE-TO-FREQUENCY CONVERTER (Cont.)

This circuit can accept positive or negative or differential control voltages. The output frequency is zero when the control voltage is zero. The 741 op amp forms a current source controlled by the voltage  $E_C$  to charge the timing capacitor C1 linearly. NE555 is connected in the astable mode, so that the capacitor charges and discharges between  $1/3 V_{CC}$  and  $2/3 V_{CC}$ . The offset is adjusted by the 10-K potentiometer so that the frequency is zero when the input is zero. For the component values shown:  $f \approx 4.2 E_C$  kHz. If two dc voltages are applied to the ends of R1 and R4, the output frequency will be proportional to the difference between the two voltages.

### 1 HZ-TO-1.25 MHZ VOLTAGE-TO-FREQUENCY CONVERTER




LINEAR TECHNOLOGY CORP.


Fig. 123-10

This stabilized voltage-to-frequency converter features 1 Hz – 1.25 MHz operation, 0.05% linearity, and a temperature coefficient of typically 20 ppm/°C. This circuit runs from a single 5-V supply. The converter uses a charge feedback scheme to allow the LTC1052 to close a loop around the entire circuit, instead of simply controlling the offset. This approach enhances linearity and stability, but introduces the loop's settling time into the overall voltage-to-frequency step-response characteristic.
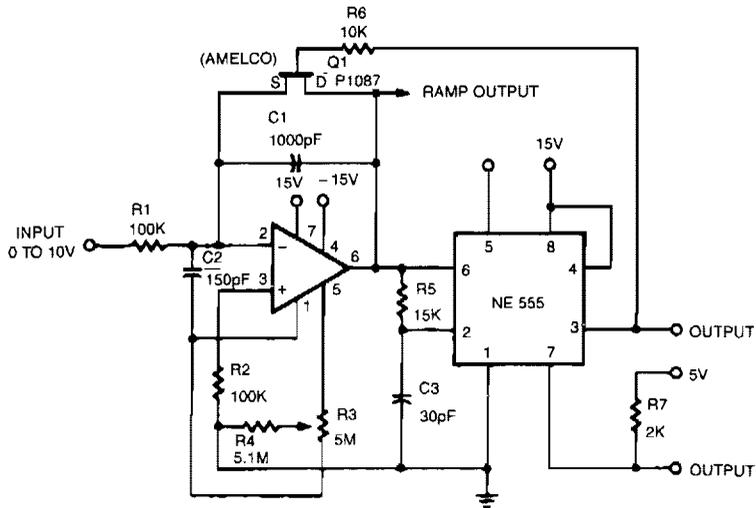
## ACCURATE VOLTAGE-TO-FREQUENCY CONVERTER



(a)

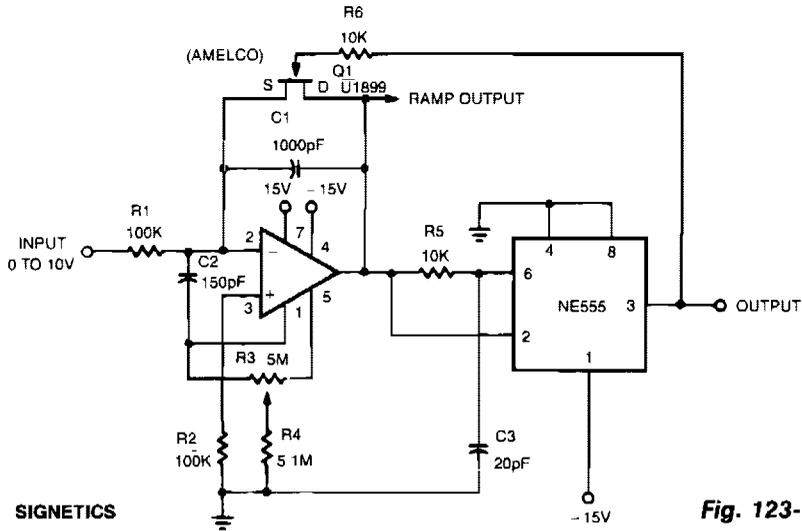

(b)


**SIGNETICS**

**Fig. 123-11**

NOTE:  
ALL RESISTOR VALUES IN OHMS

This linear voltage-to-frequency converter, a, achieves good linearity over 0 to -10 V. Its mirror image, b, provides the same linearity over 0 to +10 V, but it is not DTL/TTL compatible.

## VOLTAGE-TO-FREQUENCY CONVERTER

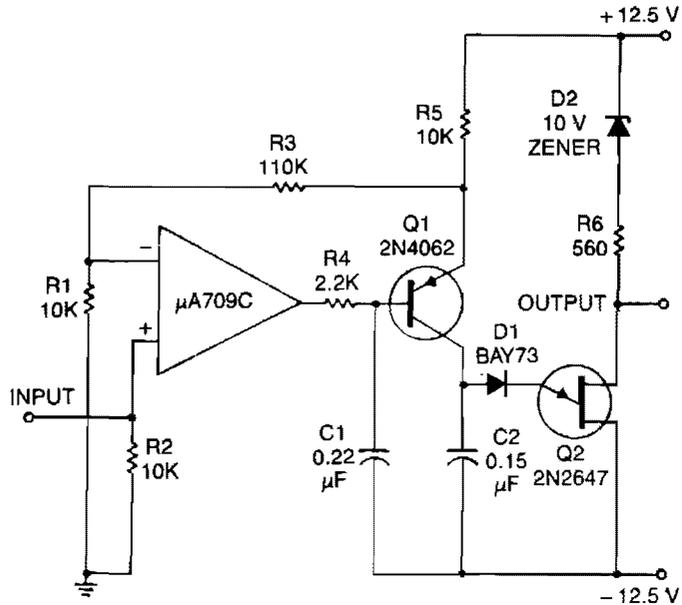

ELECTRONIC DESIGN

Fig. 123-12

This circuit consists of a UJT oscillator in which the timing charge capacitor  $C_2$  is linearly dependent on the input signal voltage. The charging current is set by the voltage across resistor  $R_5$ , which is accurately controlled by the amplifier.

# 124


## Voltage Meters/Monitors/Indicators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Voltage-Level Indicator	Voltage Monitor
4 <sup>1/2</sup> -Digit DVM	Audio Millivoltmeter
Full-Scale Four-Decade 3 <sup>1/2</sup> -Digit DVM	High-Input Resistance Voltmeter
Over/Under Voltage Monitor	Frequency Counter
High Input Resistance Dc Voltmeter	Audio Millivoltmeter
Dc Voltmeter	Low-Voltage Indicator
Voltage Freezer	FET Voltmeter
Multiplexed Common-Cathode LED-Display ADC	Simplified Voltage-Level Sensor
Ac Voltmeter	Peak Program Detector
FET Voltmeter	Wide-Range AC Voltmeter
Sensitive Rf Voltmeter	Visible Voltage Indicator

## VOLTAGE-LEVEL INDICATOR

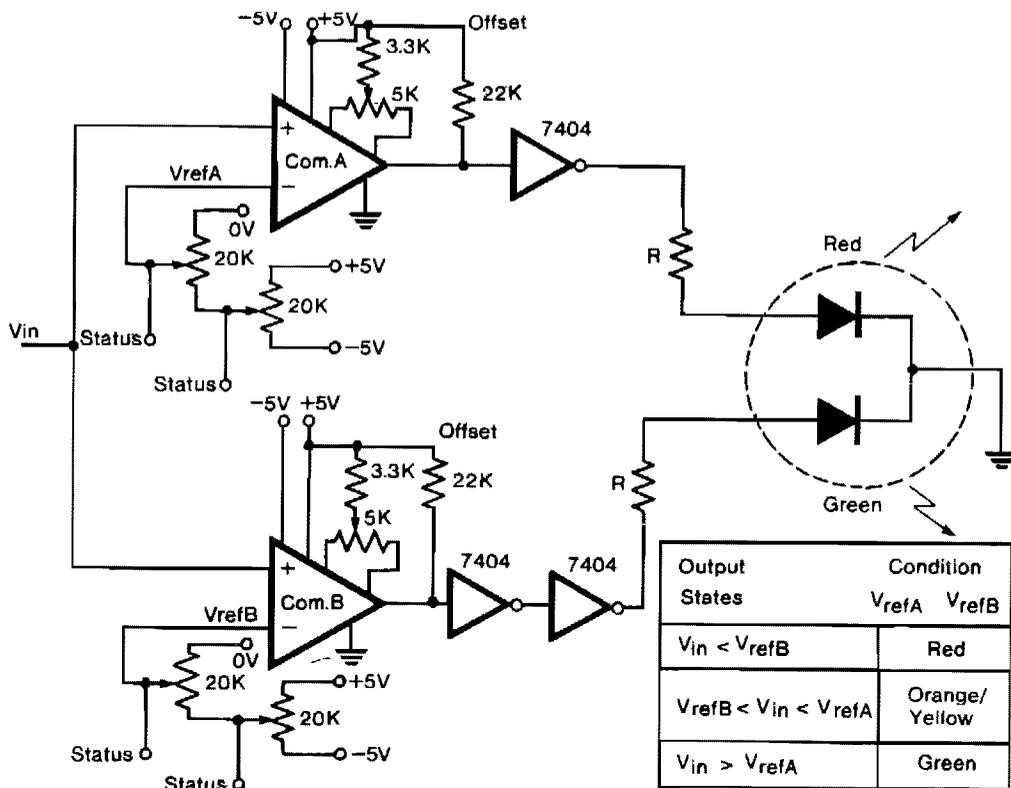


ELECTRONIC ENGINEERING

Fig. 124-1

A tricolor LED, acts as the visual indicator of the voltage level. The voltage to be measured is connected to the two comparators in parallel. The first 20-KΩ trimmer defines a voltage between  $\pm 5$  V and this becomes the full-scale value of the reference voltage. The second trimmer is a fine adjustment to give any reference voltage between 0 V and the full-scale voltage. Thus, it is possible to select both positive and negative reference voltages. During the initialization procedure, a voltage, equal to the reference voltage of each comparator, is connected to the input terminal, and the offset balance potentiometer is adjusted to give a reading between the high and low output voltage levels. The inverter following comp A ensures that, whatever the input voltage, at least one diode is lit. The two inverters following comp B leave the voltage largely unchanged, but provide the current necessary to illuminate the diode. The value of the resistance should be chosen so that the current through any single diode does not exceed the specified limit, usually 30 mA. The LED contains a red and a green diode with a common cathode. When both diodes are lit, a third color, orange, is emitted. With  $V_{refA}$  greater than  $V_{refB}$ , the output states given in the diagram apply.

## 4<sup>1</sup>/<sub>2</sub>-DIGIT DVM

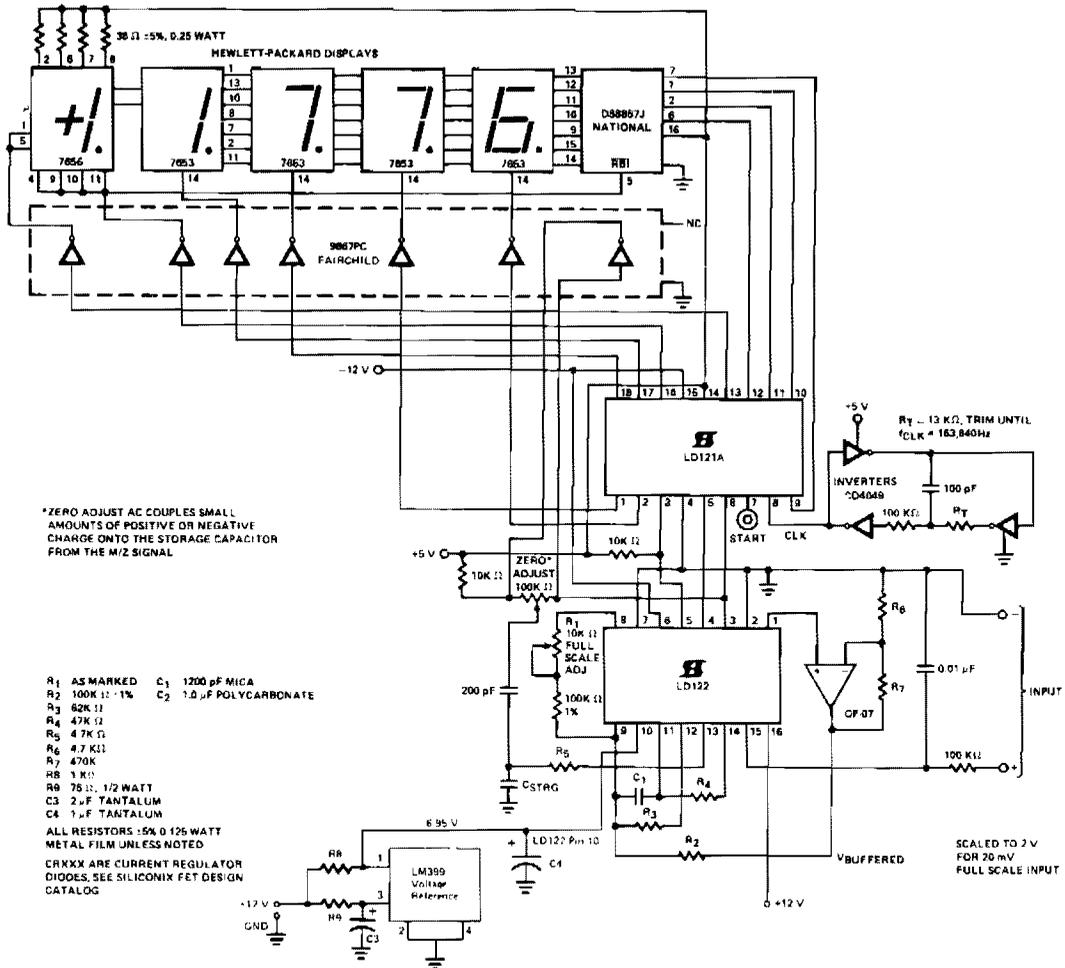


SILICONIX

Fig. 124-2

- 1- $\mu$ V resolution
- Overrange blinking
- 0-19.999 mV input voltages
- Zero adjust-to-null offset introduced by PC board leakage and the comparator.
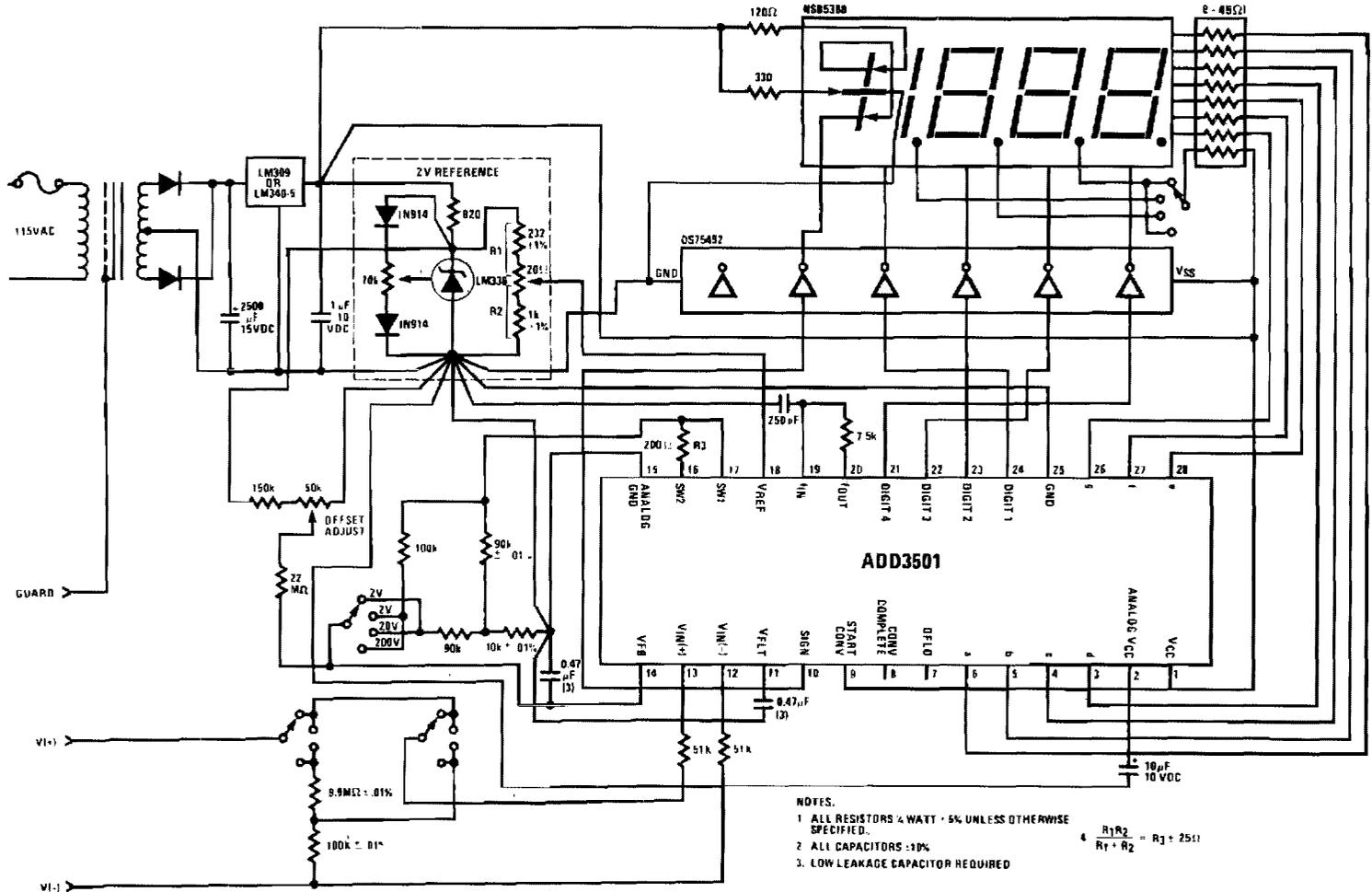
## FULL-SCALE FOUR-DECADE 3 1/2-DIGIT DVM




NATIONAL SEMICONDUCTOR CORP.

Fig. 124-3


This DVM circuit uses a National ADD3501 DVM chip and an LM336 reference IC to create a simple DVM with relatively few components. When making a single range panel meter, the range switching components can be left out, as required.

## OVER/UNDER VOLTAGE MONITOR

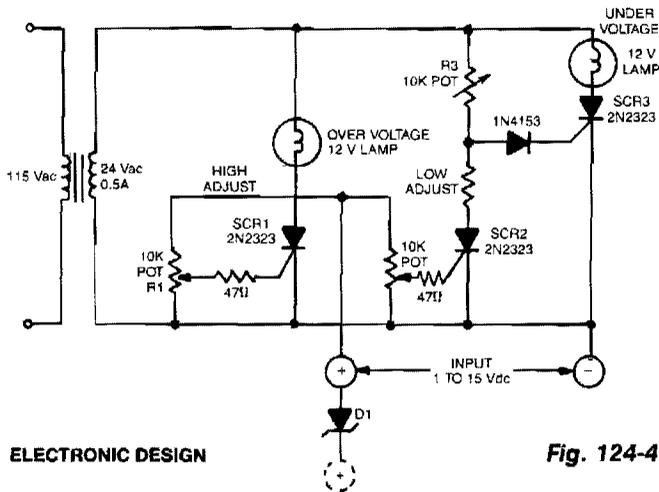

Any potential from 1 to 15 V can be monitored with this circuit. Two lamps alert any undesirable variation. The voltage differential from lamp turn-on to turn-off is about 0.2 V at any setting. High and low set points are independent of each other. The SCRs used in the circuit should be the sensitive gate type. R3 must be experimentally determined for the particular series of SCRs used. This is done by adjusting R3 to the point where the undervoltage lamp turns on when no signal is present at the SCR2 gate. Any 15-V segment can be monitored by putting the zener diode, D1, in series with the positive input lead. The low set-point voltage will then be the zener voltage plus 0.8 V.


## HIGH INPUT RESISTANCE DC VOLTMETER

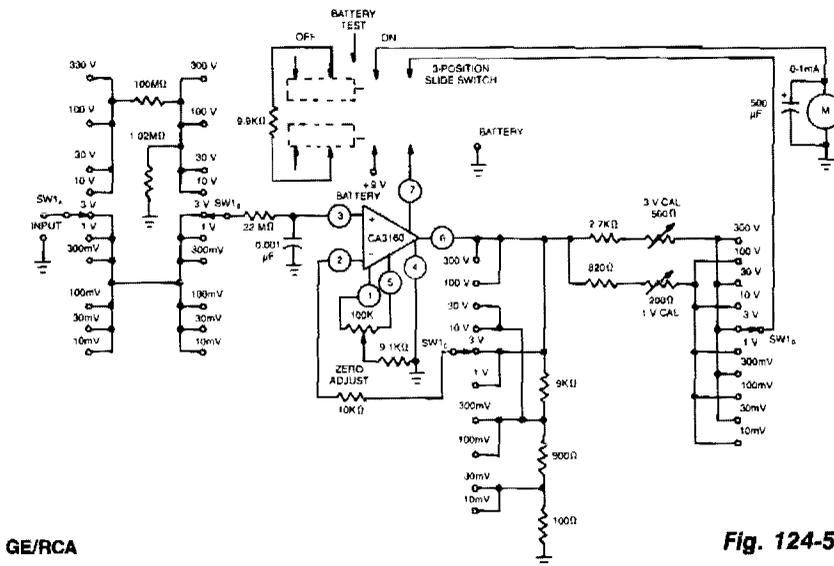

## HIGH INPUT RESISTANCE DC VOLTMETER (Cont.)

This voltmeter exploits a number of the CA3160 BiMOS op amp's useful characteristics. The available voltage ranges from 10 mV to 300 V. Powered by a single 8.4-V mercury battery, this circuit, with zero input, consumes approximately 500  $\mu$ A. Thus, at full-scale input, the total supply current will increase by 1000  $\mu$ A.

### DC VOLTMETER

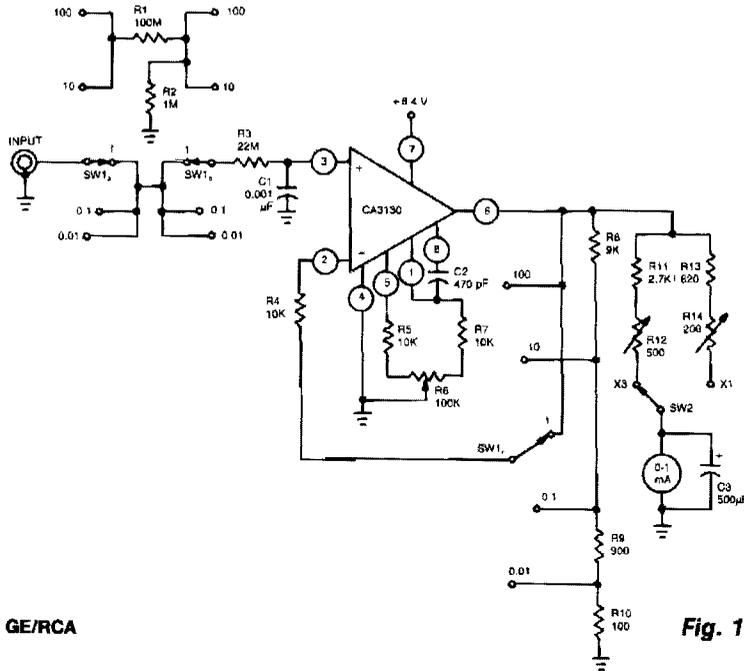

GE/RCA

Fig. 124-6

This dc voltmeter, with high input resistance, uses a CA3130 BiMOS op amp and measures voltages from 10 mV to 300 V. Resistors R12 and R14 are used individually to calibrate the meter for full-scale deflection. Potentiometer R6 is used to null the op amp and meter on the 10-mV range by shorting the input terminals, then adjusting R6 for the first indication of upscale meter deflection.

### VOLTAGE FREEZER

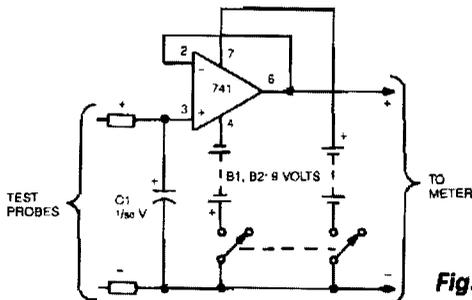


Fig. 124-7


This circuit reads and stores voltages, thus freezing the meter reading even after the probes are removed. The op amp is configured as a unity-gain voltage follower, with C1 situated at the input to store the voltage. For better performance, use an LF13741 or a TL081 op amp in place of the 741. These two are JFET devices and offer a much higher input impedance than the 741.

Reprinted with permission of Radio-Electronics Magazine, November 1982.





## SENSITIVE RF VOLTMETER

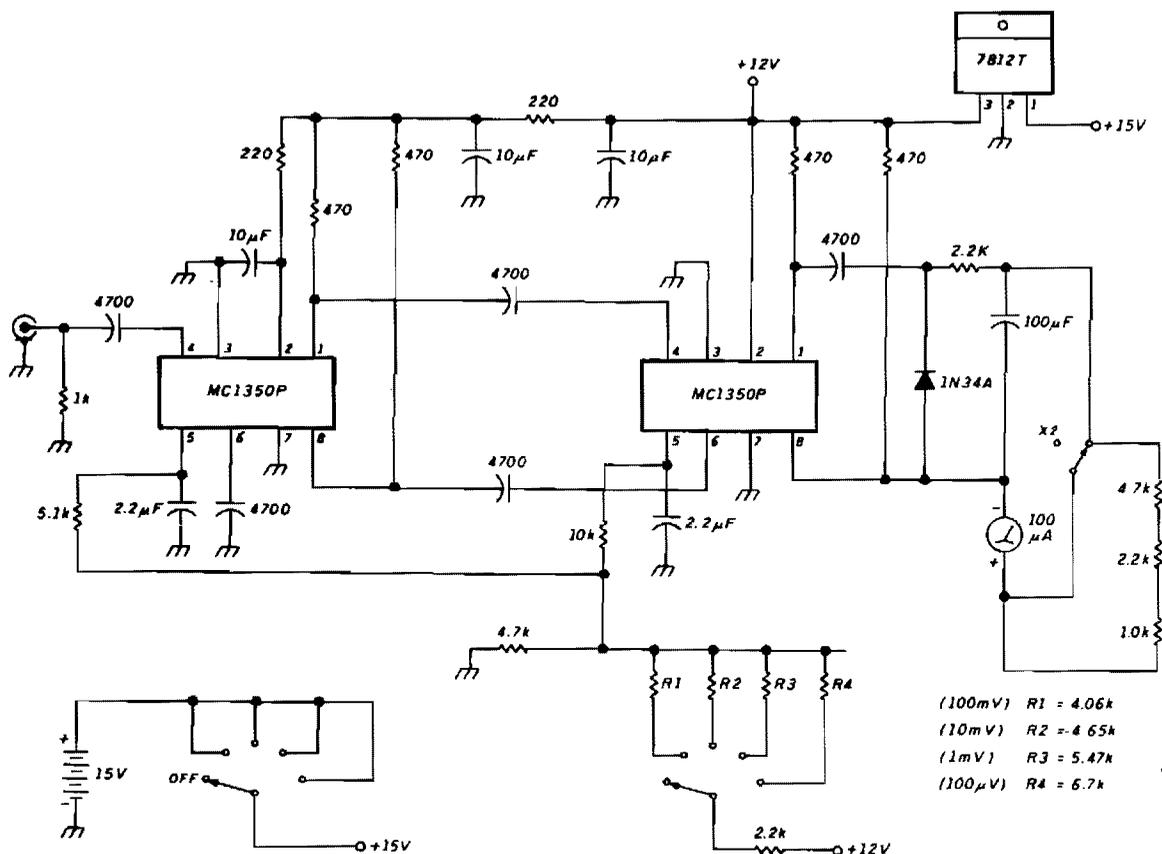


HAM RADIO

Fig. 124-11

This schematic shows a peak-reading diode voltmeter driven by two stages of amplification. A 100- $\mu$ F capacitor provides a fairly large time constant, which results in satisfactory meter damping. The limited differential output voltage coupled with an overdamped meter prevents most *needle pinning* when you select an incorrect range position, or make other errors. An SPST toggle switch selects additional series resistance. This X2 function gives some more overlap of the sensitivity ranges. The resistance values shown are correct for use with a 100- $\mu$ A meter with 1500- $\Omega$  internal resistance.

## VOLTAGE MONITOR

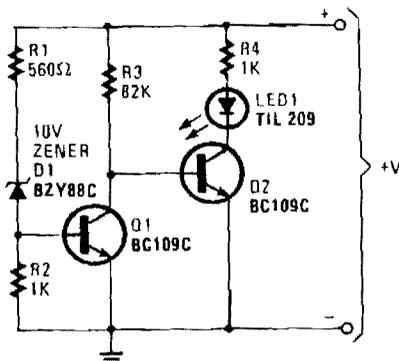


HANDS-ON ELECTRONICS

Fig. 124-12

If the battery voltage exceeds about 11 V, current flows through R1, D1, and R2. The voltage produced as a result of current flow through R2 is sufficient to bias transistor Q1 into conduction. That places the collector voltage of Q1 virtually at ground. Therefore, Q2, driven from the collector of Q1, is cut off, LED1 and current-limiting resistor R4 are connected in the collector circuit of Q2. With Q2 in the cut-off state, the LED does not light. Should Q1's base voltage drop below approximately 0.6 V, Q1 turns off, biasing Q2 on and illuminating LED1 to indicate that the battery voltage has fallen below the 11 V threshold level.

## AUDIO MILLIVOLTMETER

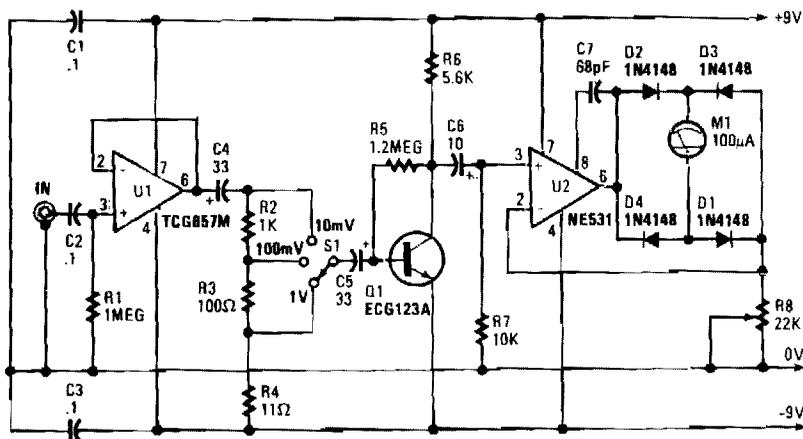

POPULAR ELECTRONICS/HANDS-ON ELECTRONICS


Fig. 124-13

Capacitor C4 couples the output of U1 to a simple attenuator, which is used to provide a loss of 0 dB, 20 dB, or 40 dB, depending on the setting of range switch S1. The circuit's sensitivity is 10-V rms for full-scale deflection, so the attenuator gives additional ranges of 100-mV and 1-V rms. The attenuator output is connected through capacitor C5 to common-emitter amplifier Q1, which has a high-voltage gain of 40 dB.

To get linear scaling on the meter, we have to use an active-rectifier circuit built around U2. That IC is connected so that its noninverting input is biased to the 0-V bus via R7. Capacitor C6 couples the output of Q1 to the noninverting input of U2; C7 is the compensation capacitor for U2.

The voltage gain of U2 is set by the difference in resistance between the output and the inverting input, and between the inverting input and the ground bus. One resistance is made up of the diode-bridge rectifier D1 through D4, the other by resistor R8. This circuit has a nearly flat frequency response to about 200 kHz.


## HIGH-INPUT RESISTANCE VOLTMETER

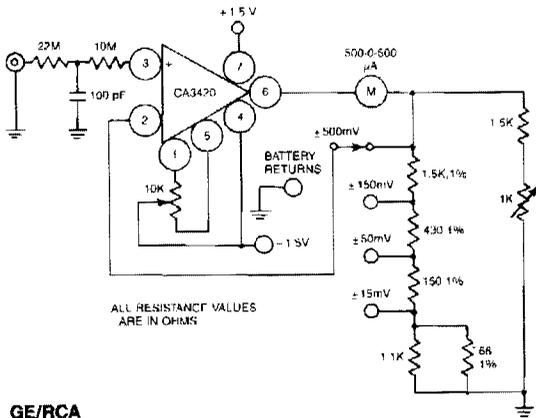

A resistance of 1,000,000  $\text{M}\Omega$  takes advantage of the high input impedance of the CA3420 BiMOS op amp. Only two 1.5-V AA-type penlite batteries are required for use. Full-scale deflection is  $\pm 500$  mV,  $\pm 150$  mV, and  $\pm 15$  mV.

Fig. 124-14

## FREQUENCY COUNTER

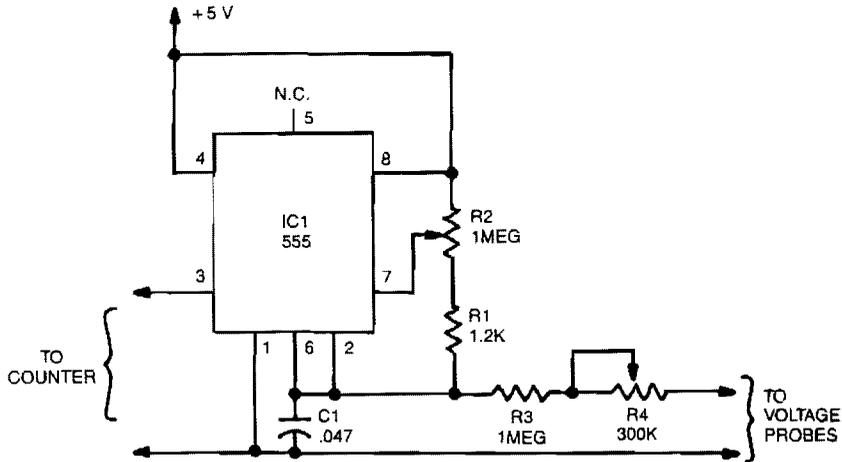


Reprinted with permission of Gernsback Publications Inc.

Fig. 124-15

The output frequency from IC pin 3 is determined by the voltage input to pin 6. A standard frequency counter can be used to measure voltages directly over a limited range from 0 to 5 V. In this circuit, the 555 is wired as an astable multivibrator. Resistor R2 determines the output frequency when the input to the circuit (the voltage measured by the voltage probes) is zero. R4 is a scaling resistor that adjusts the output frequency so that a change in the input voltage of 1 V will result in a change in the output frequency of 10 Hz. That will happen when the combined resistance of R3 and R4 is 1.2  $\text{M}\Omega$ . To calibrate short the voltage probes together, adjust R2 until the reading on the frequency counter changes to 00 Hz. Then, use the voltage probes to measure an accurate 5-V source and adjust R4 until the frequency counter reads 50 Hz.


## AUDIO MILLIVOLTMETER

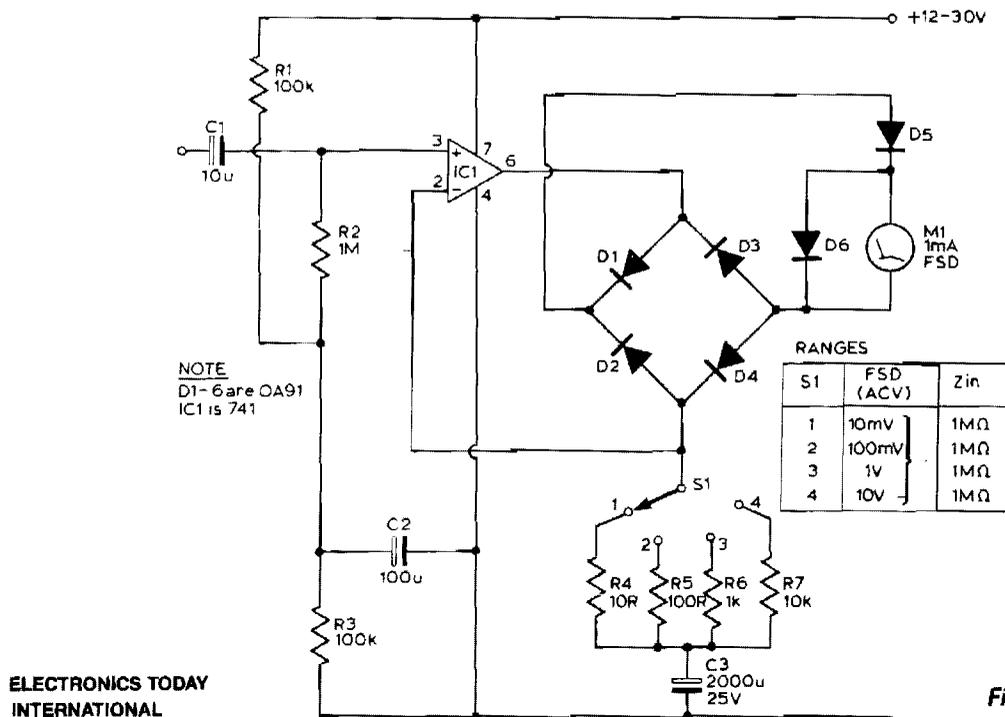

**Fig. 124-16**

This circuit has a flat response from 8 Hz to 50 kHz at -3 db on the 10-mV range. The upper limit remains the same on the less sensitive ranges, but the lower frequency limit covers under 1 Hz.

## LOW-VOLTAGE INDICATOR

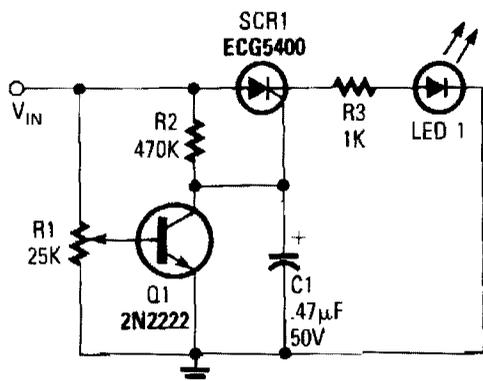

**Fig. 124-17**

Input terminal  $V_{IN}$  is connected to the +V line of the circuit that the indicator is to monitor, and the grounds of both circuits are connected together. The position of potentiometer R1's wiper determines Q1's base voltage. As long as the transistor gets enough bias voltage to remain on, the low voltage at the collector will keep the SCR from firing. As the battery voltage starts to fall, the transistor's base voltage will fall as well. When Q1 turns off ( $V_{IN}$  drops), the collector voltage increases. That voltage provides enough gate drive to turn on the SCR, which turns on the LED. The LED could also be a buzzer or almost any other type of warning device.

Reprinted with permission of Radio-Electronics Magazine, January 1986. Copyright Gernsback Publications, Inc., 1986.

## FET VOLTMETER

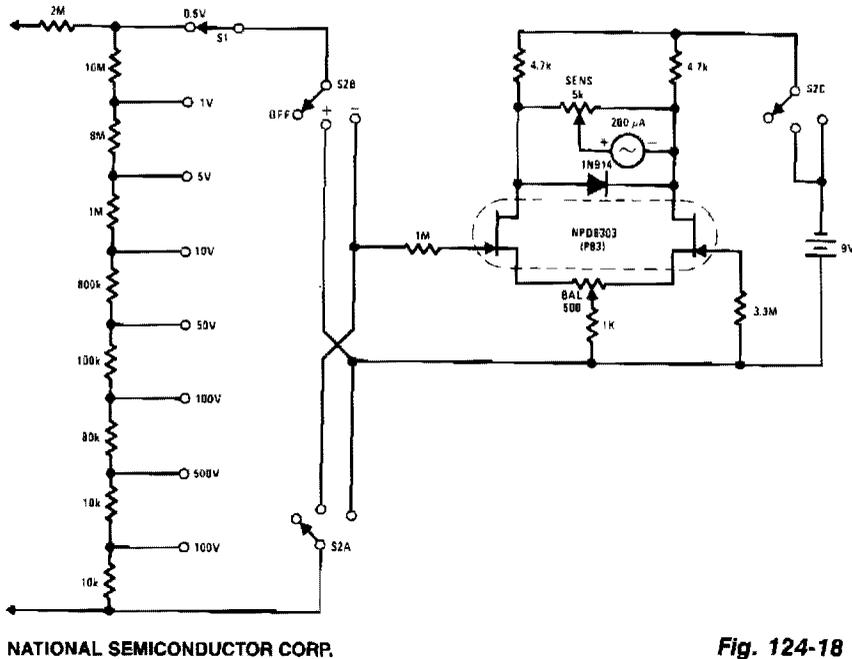


Fig. 124-18

This FETVM replaces the function of the VTVM and rids the instrument of the usual line cord. In addition, FET drift rates are far superior to vacuum tube circuits, allowing a 0.5 V full-scale range which is impractical with most vacuum tubes. The low leakage, low noise NPD8303 is ideal for this application.

## SIMPLIFIED VOLTAGE-LEVEL SENSOR

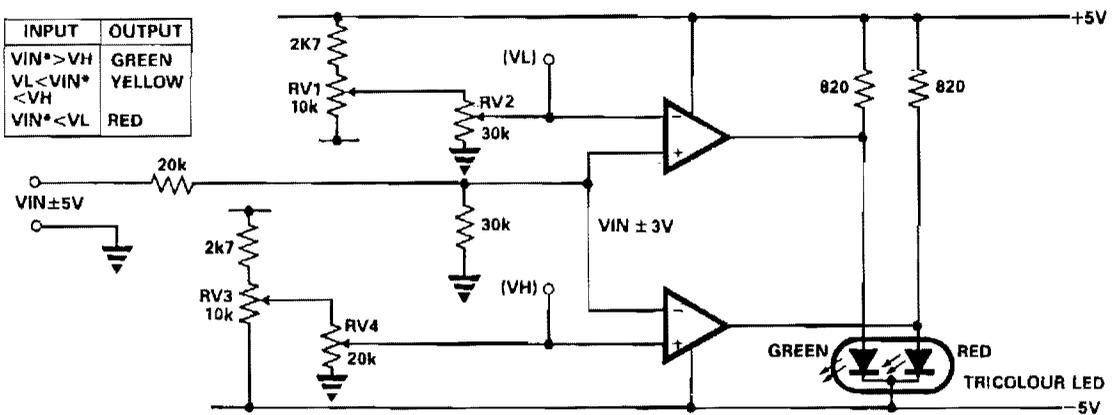


Fig. 124-19


## SIMPLIFIED VOLTAGE-LEVEL SENSOR (Cont.)

This circuit uses only one IC, either 1, LM393 dual comparator or 1/2, LM339 quad comparator. RV1 and RV3 set the full scale reference voltage, and RV2 and RV4 set the switching thresholds to a value between 0 V and the full-scale reference. The change in input voltage needed to fully switch the output state is less than 0.05 mV (typical).

An alternative is:

INPUT	OUTPUT
$V_{IN}, V_H$	red
$V_H, V_{IN}, V_L$	yellow
$V_{IN}, V_L$	green

## PEAK PROGRAM DETECTOR

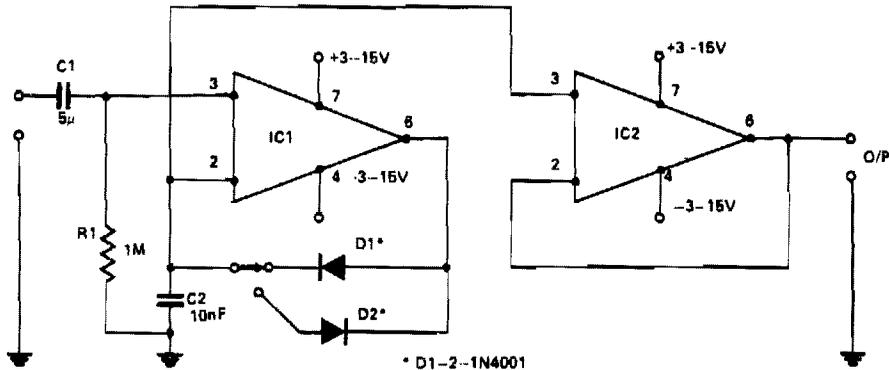


ELECTRONICS TODAY INTERNATIONAL

Fig. 124-20

This circuit will allow a multimeter to display the positive or negative peaks of an incoming signal. A 741, IC1, is used in the noninverting mode with R1 defining the input impedance. D1 or D2 will conduct on a positive or negative peak, charging C2 until the inverting input is at the same dc level as the incoming peak. This level will maintain the voltage until a higher peak is detected, then this will be stored by C2. Another 741, IC2, prevents loading by the multimeter. Connected in the noninverting mode as a unity gain buffer, output impedance is less than 1 Ω. This circuit has a useful frequency response from 10 Hz to 100 kHz at ±1 dB. High linearity is ensured by placing the diodes in the feedback loop of IC1, effectively compensating for the 0.6 V bias that these components require.

## WIDE-RANGE AC VOLTMETER

NATIONAL SEMICONDUCTOR CORP.

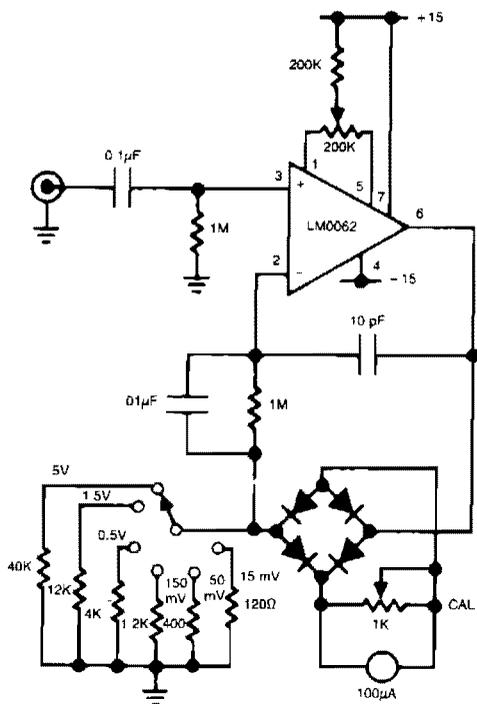

In this circuit, a diode bridge is used as a meter rectifier. The offset voltage is compensated for by the op amp, since the bridge is in the feedback network.

Fig. 124-21

## VISIBLE VOLTAGE INDICATOR

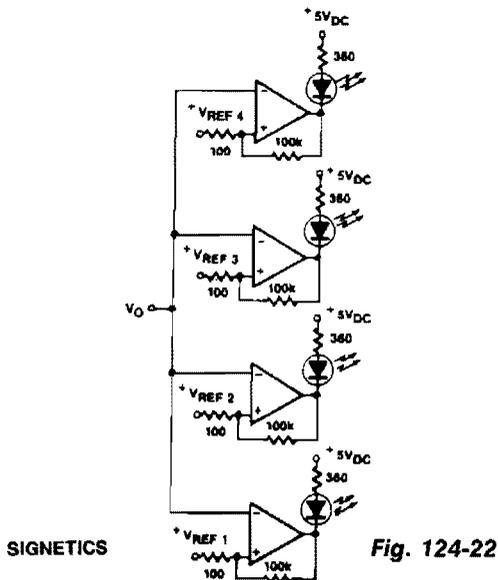


Fig. 124-22

# 125


## Voltage References

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Bipolar Reference Source  
Expanded-Scale Analog Meter  
Digitally Controlled Voltage Reference

## BIPOLAR REFERENCE SOURCE

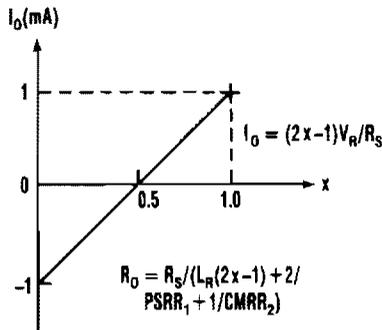

ELECTRONIC DESIGN


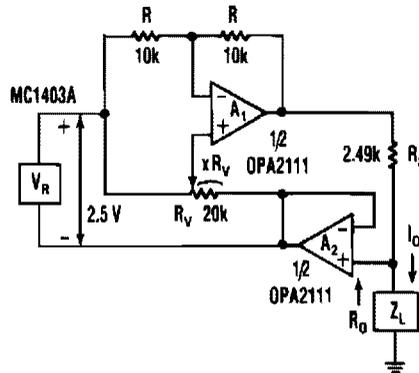


Fig. 125-1

This current source has continuous control of the magnitude and polarity of its amplifier gain and needs only one voltage reference. The circuit includes reference  $V_R$ , voltage-amplifier circuit A1 with gain-setting resistor  $R_S$ , and bootstrap-follower amplifier A2. The bootstrapping converts the circuit to a current source and allows the load to be grounded. Any voltage developed across load  $Z_L$  feeds back to the reference and voltage amplifier, making their functions immune to that voltage. Then the current-source circuitry floats, instead of the load.

The voltage reference is connected to both the inverting and noninverting inputs of A1; this provides a balanced combination of positive and negative gain. The inverting connection has equal feedback resistors,  $R$ , for a gain of  $-1$ , and the noninverting connection varies according to the fractional setting,  $X$ , of potentiometer  $R_V$ .  $X$  controls the noninverting gain and adjusting it counters the effect of some of the inverting gain. The value of  $X$  is the portion of  $R_V$ 's resistance from the noninverting input of A1 to the temporarily grounded output of A2. Between potentiometer extremes, the current varies with  $X \pm 1$  mA.

## EXPANDED-SCALE ANALOG METER

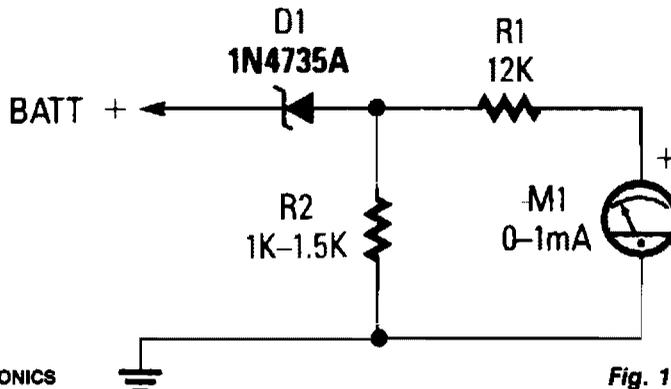


POPULAR ELECTRONICS

Fig. 125-2

The circuit consists of 0–1 mA meter M1, 6.2-V zener diode D1, and 12-K $\Omega$ , 1% resistor R1. R2 is included in the circuit as a load resistor for the zener diode. The value of R2 isn't critical; use a value of 1000 to 1500  $\Omega$ . The meter reads from 6 to 18 volts, which is perfect for checking a car's charging system.
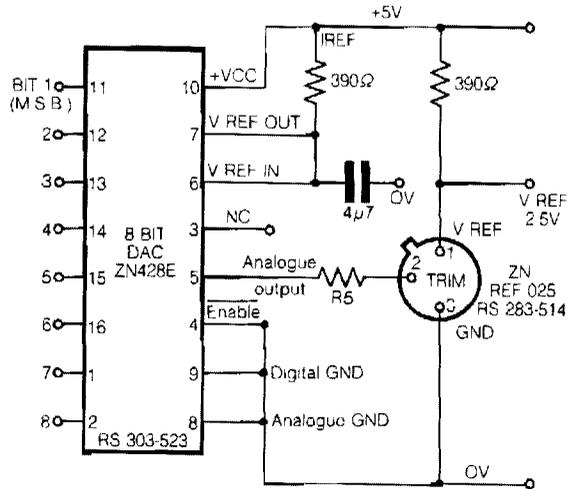
## DIGITALLY-CONTROLLED VOLTAGE REFERENCE



ELECTRONIC ENGINEERING

Fig. 125-3

This circuit shows a simple method of achieving a voltage reference which can be trimmed using an 8-bit DAC with an on-chip voltage reference. The analogue output from the DAC drives the trim pin of the ZNREF025 via a resistor,  $R_S$ . When  $R_S = 0$ , this circuit will produce a trim range exceeding  $\pm 5\%$  of the nominal reference voltage. When  $R_S$  is greater than zero, the trim range is reduced. It was found that after dividing the trim range by two, the needed value for  $R_S$  was approximately  $1\text{ M}\Omega$ .

The reference voltage of the ZNREF025 can be set to an accuracy determined by the trim range of the device itself and the accuracy of the DAC. Increasing  $R_S$  reduces the percentage trim range and hence increases the effective voltage resolution. Other voltage references from the ZNREF series can be used with this circuit if other voltages are required. This voltage reference can be used to set the value of  $V_{REF}$  to a much tighter tolerance, than the data sheet specification of  $\pm 1\%$ , in a much wider range of operating conditions. Applications could include any system with automatic self-calibration of instrumentation, such as in electronic weighing scales.

# 126


## Window Detectors/ Comparators/Discriminators

---

The sources of the following circuits are contained in the Sources section beginning on page 782. The figure number contained in the box of each circuit correlates to the sources entry in the Sources section.

Digital Frequency Window	Window Detector
Window Detector	Simple Window Detector
Window Detector	Multiple Aperature Window
Window Detector	Detector

## DIGITAL FREQUENCY WINDOW

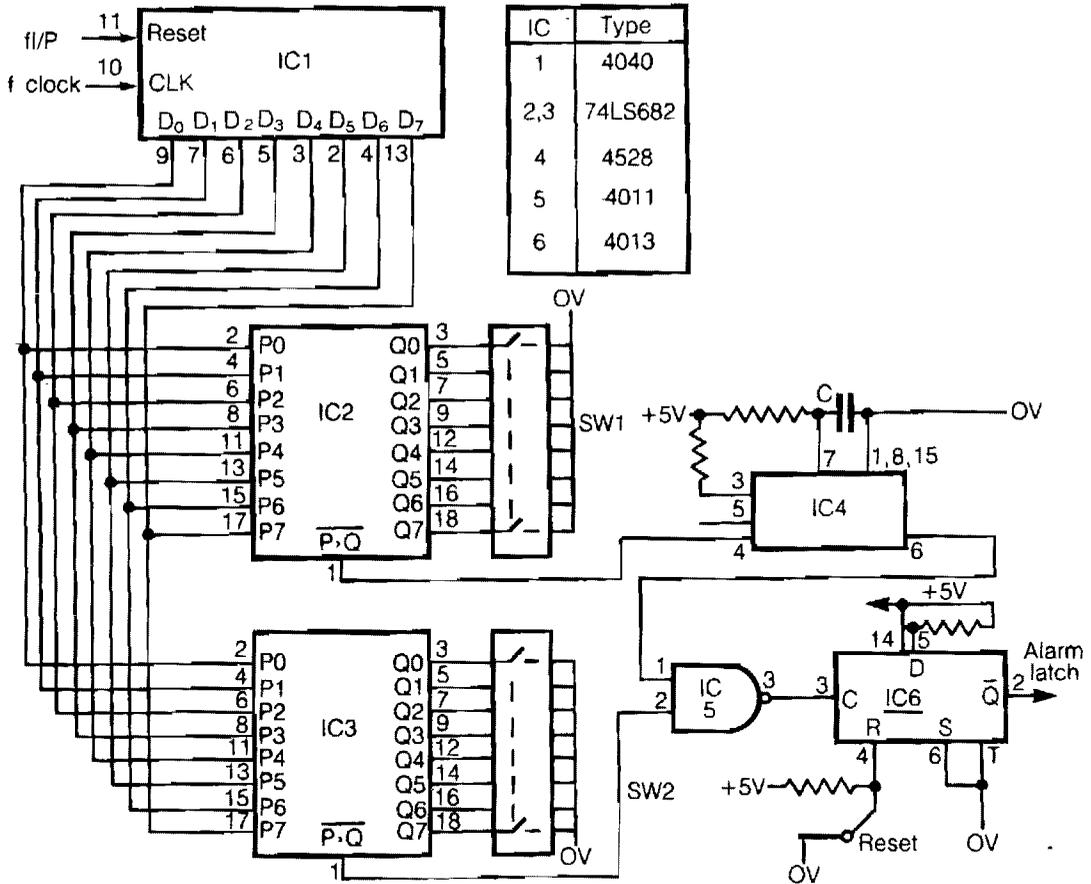


ELECTRONIC ENGINEERING

Fig. 126-1



This circuit detects frequency variation above or below preset limits. IC1 is a binary counter clocked at  $F_{CLK}$ . The outputs are compared with switch preset values by IC2 and IC3. The input signal, which must be a positive-going pulse, is used to reset IC1. The *P greater than Q* output of the comparators is at logic 0 for input frequencies below the preset values. Above the preset count, a pulse train is output.

IC2, detects a low input by supplying the pulse train to a retriggerable monostable, IC4. When the input frequency falls below the preset value in SW1, the monostable is no longer triggered and its output falls to logic 0. IC3 detects the frequency high state SW2, and outputs directly when this occurs. The outputs from both comparators can then be latched as shown, using IC5 and IC6. The clock frequency is related to input and switch values:  $\text{switch value} = F_{CLK}/\text{input}$ . The time constant of IC4 is not critical, but must obviously exceed the maximum input pulse period.

## WINDOW DETECTOR

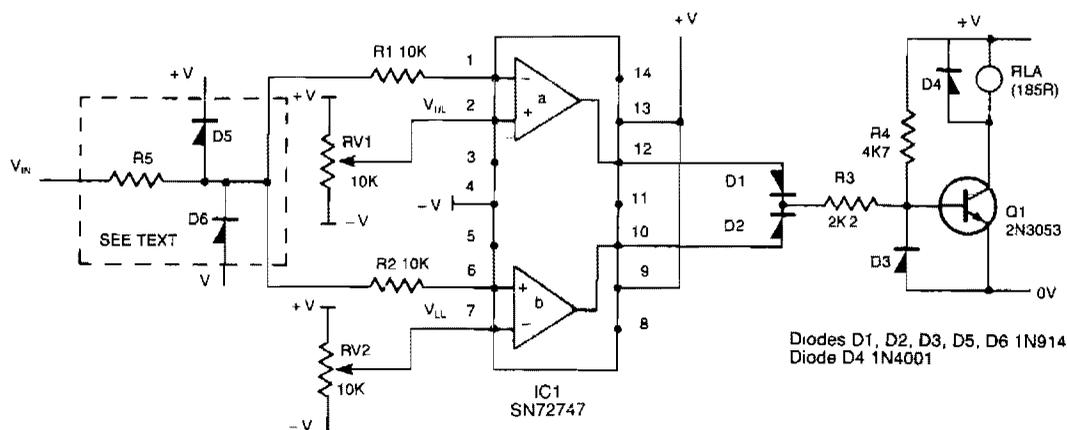

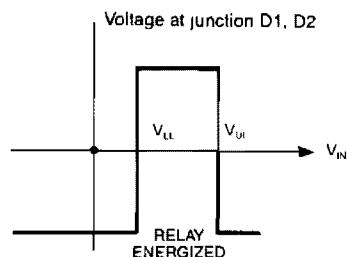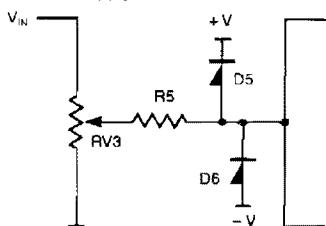Modification for trigger points  
outside supply rails




ELECTRONICS TODAY INTERNATIONAL

Fig. 126-2

This circuit de-energizes a normally energized relay if the input voltage goes above or below two individually set voltages. The transistor driving the relay is normally turned on by R4, so the relay is normally energized. If the cathode of D1 or D2 is taken negative, Q1 will turn off and the relay will de-energize. The IC is a 72747 dual op amp used without feedback, so the full gain of about 100dB is available. The amplifier output will thus swing from full positive to full negative for a few mV change at the input. The relay is therefore only energized if  $V_{IN}$  is between  $V_{UL}$  and  $V_{LL}$ . The two limits can be set anywhere between the supply rails, but obviously  $V_{UL}$  must be more positive than  $V_{LL}$ . If  $V_{IN}$  can go outside the supply rails, D5, D6, and R5 should be added to prevent damage to IC1. If  $V_{UL}$  and  $V_{LL}$  are required to be outside the supply rails,  $V_{IN}$  can be reduced by RV3. The supplies can be any value, providing that the voltage across them is not more than 30 V.

## WINDOW DETECTOR

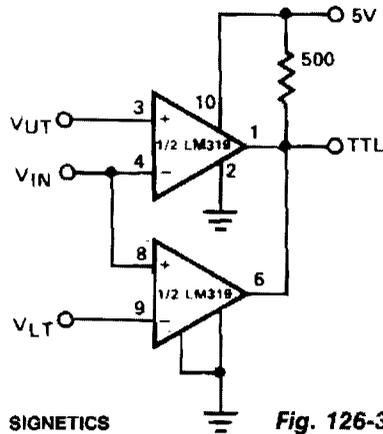


$V_{OUT} = 5V$  for  $V_{LT} < V_{IN} < V_{UT}$   
 $V_{OUT} = 0$  for  $V_{IN} < V_{LT}$  or  $V_{IN} > V_{UT}$

SIGNETICS

Fig. 126-3

## WINDOW DETECTOR

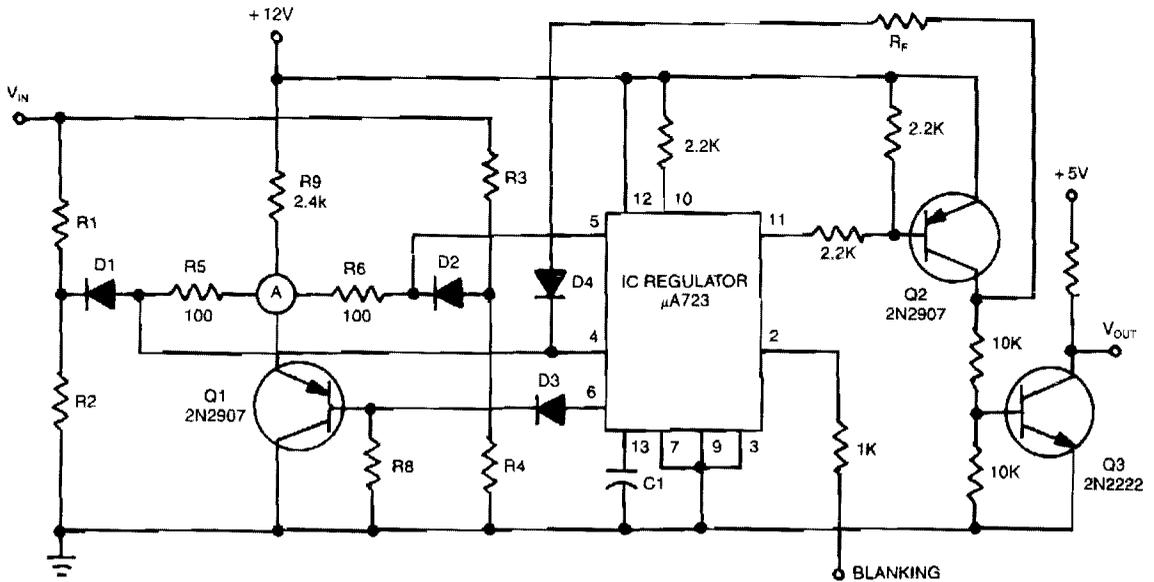


EDN

Fig. 126-4

The detector circuit compares the output voltage of two separate voltage dividers with a fixed reference voltage. The resultant absolute error signal is amplified and converted to a logic signal that is TTL compatible.

## WINDOW DETECTOR


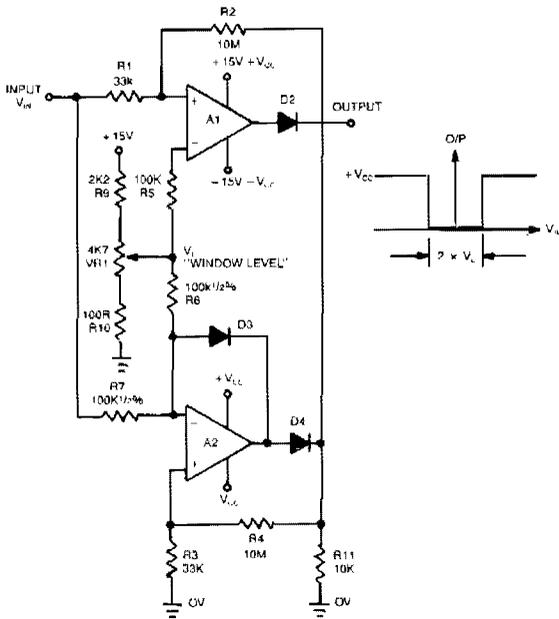


This novel window detector uses only two op amps. The width of the window can be changed by the 4.7-K $\Omega$  potentiometer.

ELECTRONIC ENGINEERING

Fig. 126-5

## SIMPLE WINDOW DETECTOR

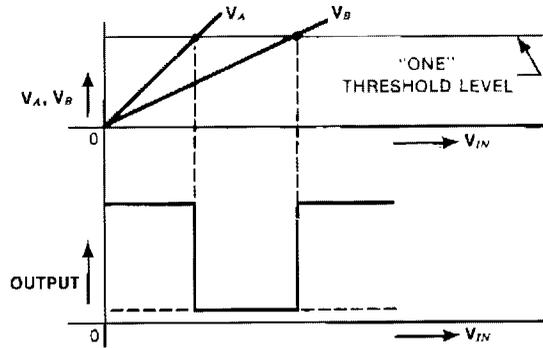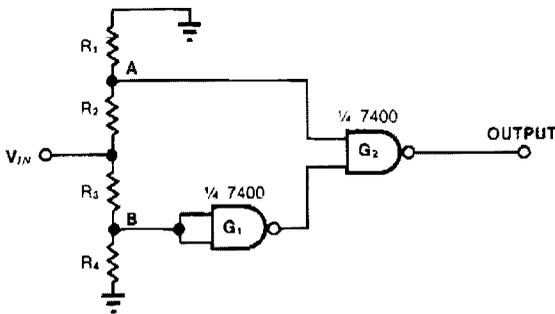


EDN

Fig. 126-6

This simple window detector uses only half of a 7400 quad NAND gate plus four resistors, chosen so that the voltage at point A exceeds the voltage at point B for any input voltage. With no input applied or when  $V_{IN}$  is at ground, the output of gate  $G1$  is one; hence  $G2$ 's output is also one. As the input voltage increases,  $V_A$  rises faster than  $V_B$ . When  $V_A$  reaches an acceptable one level, the circuit's output drops to zero. As the input continues to increase,  $V_B$  rises to an acceptable level, changing the output of  $G2$  to one.
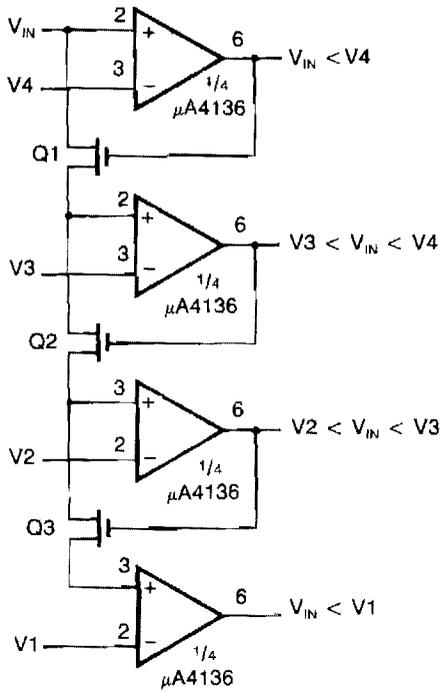
## MULTIPLE APERTURE WINDOW DISCRIMINATOR



The circuit shown here uses  $\mu\text{A}4136$  comparators and FETs Q1 through Q3.

FAIRCHILD CAMERA AND INSTRUMENT CORP.

Fig. 126-7

# Sources Index

## Chapter 1

Fig. 1-1. Radio-Electronics, 2/89, p.51.

Fig. 1-2. QST, 2/86, p.22.

## Chapter 2

Fig. 2-1. Popular Electronics, 8/89, p. 24.

Fig. 2-2. Reprinted from EDN, 5/16/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 2-3. Reprinted with permission from Electronic Design. Copyright 1988, Penton Publishing.

Fig. 2-4. Reprinted from EDN, 9/20/84, Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 2-5. Popular Electronics, 8/89, p. 22.

Fig. 2-6. Reprinted from EDN, 12/74, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 3

Fig. 3-1. Harris, Analog Product Data Book, 1988, p.10-167.

Fig. 3-2. Reprinted from EDN, 1/79, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 3-3. Electronic Engineering, Applied Ideas, 9/88, p. 25.

Fig. 3-4. Maxim, Maxim Advantage, p. 44.

Fig. 3-5. Harris, Analog Product Data Book, 1988, p. 10-95.

Fig. 3-6. Harris, Analog Product Data Book, 1988, p. 10-96.

Fig. 3-7. Hands-on Electronics, Fact Card No. 29.

Fig. 3-8. Hands-on Electronics, Fact Card No. 29.

Fig. 3-9. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 13.

Fig. 3-10. Signetics, 1987 Linear Data Manual Vol 2: Industrial, 11/6/86, p. 4-136.

Fig. 3-11. Signetics, 1987 Linear Data Manual Vol 2: Industrial, 2/87, p. 4-243.

Fig. 3-12. Siliconix, Integrated Circuits Data Book, 1988, p. 13-166.

Fig. 3-13. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 13.

- Fig. 3-14. Harris, Analog Product Data Book, 1988, p. 10-110.
- Fig. 3-15. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN18-3.
- Fig. 3-16. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN21-5.
- Fig. 3-17. Harris, Analog Product Data Book, 1988, p. 10-150.
- Fig. 3-18. Reprinted from EDN, 9/1/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 3-19. Intersil, Applications Handbook, 1988, p. 3-181.
- Fig. 3-20. Maxim, Maxim Advantage, p. 44.
- Fig. 3-21. Electronic Engineering, 9/88/ p. 28.

## Chapter 4

- Fig. 4-1. Siliconix, Integrated Circuits Data Book, 1988, p. 6-148.
- Fig. 4-2. Harris, Analog Product Data Book, 1988, p. 10-48.
- Fig. 4-3. Signetics, 1987 Linear Data Manual Vol 2: Industrial, 2/87, p. 5-311.
- Fig. 4-4. Maxim, Seminar Applications Book, 1988/89, p. 38.

## Chapter 5

- Fig. 5-1. Reprinted from EDN, 4/77, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 6

- Fig. 6-1. Harris, Analog Product Data Book, 1988, p. 10-173.
- Fig. 6-2. Harris, Analog Product Data Book, 1988, p. 10-13.
- Fig. 6-3. Signetics, RF Communications Handbook, 1989, p. 2-14 and 2-15.

## Chapter 7

- Fig. 7-1. Harris, Analog Product Data Book, 1988, p. 10-108.
- Fig. 7-2. Signetics, Analog Data Manual, 1983, p. 10-20.
- Fig. 7-3. ZeTeX (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-153.
- Fig. 7-4. Harris, Analog Product Data Book, 1988, p. 10-161.
- Fig. 7-5. Hands-On Electronics, Summer 1984, p. 74
- Fig. 7-6. Radio-Electronics, 8/88, p. 33.
- Fig. 7-7. Signetics, RF Communications Handbook, 1989, p. 1-61 and 1-62.

- Fig. 7-8. Popular Electronics, 7/89, p. 26.
- Fig. 7-9. Popular Electronics, Fact Card No. 110.
- Fig. 7-10. Harris, Analog Product Data Book, 1988, p. 10-174.
- Fig. 7-11. Harris, Analog Product Data Book, 1988, p. 10-174.
- Fig. 7-12. Hands-On Electronics, 5/87, p. 96.
- Fig. 7-13. QST, 1/89, p. 20.
- Fig. 7-14. Hands-On Electronics/Popular Electronics, 11/88, p. 39.

## Chapter 8

- Fig. 8-1. Gernsback Publications Inc., 42 New Ideas, 1984, p. 9.
- Fig. 8-2. ZeTeX (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-158.
- Fig. 8-3. Popular Electronics, 8/89, p. 22.
- Fig. 8-4. Gernsback Publications Inc. 42 New Ideas, 1985, p. 28.
- Fig. 8-5. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.
- Fig. 8-6. ZeTeX, (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-155.
- Fig. 8-7. Radio-Electronics, 7/85, p. 55.
- Fig. 8-8. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 3.
- Fig. 8-9. Reprinted from EDN, 8/81, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 8-10. Intersil, Component Data Catalog, 1987, p. 2-108.
- Fig. 8-11. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-67.
- Fig. 8-12. Hands-On Electronics, 9-10/86, p. 27.
- Fig. 8-13. TAB Books, The Giant Book of Easy-to-Build Electronic Projects, 1982, p. 186.
- Fig. 8-14. TAB Books, 101 Sound, Light, and Power IC Projects, 1986, p. 139.
- Fig. 8-15. Hands-On Electronics, 5/87, p. 95.
- Fig. 16. Hands-On Electronics/Popular Electronics, 12/88, p. 25.
- Fig. 8-17. Popular Electronics/Hands-On Electronics, 3/89, p. 36.
- Fig. 8-18. Radio-Electronics, 4/87, p. 67.

## Chapter 9

- Fig. 9-1. Motorola, Motorola Thyristor Device Data, Series A 1985, p. 1-6-54.
- Fig. 9-2. Reprinted from EDN, 7/21/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 9-3. Linear Technology Corp., Linear Databook, 1986, p. 4-15.

Fig. 9-4. Radio-Electronics, 7/86, p. 67.

Fig. 9-5. Motorola, Motorola Thyristor Device Data, Series A 1985, p. 1-6-46.

Fig. 9-6. ZeTeX (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-164.

Fig. 9-7. Popular Electronics, 7/89, p. 81.

Fig. 9-8. Gernsback Publications, Inc., 42 New Ideas, 1984, p. 9.

## Chapter 10

Fig. 10-1. Reprinted from EDN, 7/21/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 10-2. Popular Electronics/Hands-On Electronics, 5/89, p. 25.

Fig. 10-3. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 5.

Fig. 10-4. Maxim, 1986 Power Supply Circuits, p. 26.

Fig. 10-5. Hands-On Electronics, Spring 1985, p. 49.

Fig. 10-6. National Semiconductor Corp., 1984 Linear Supplement Databook, p. S2-7.

Fig. 10-7. Reprinted from EDN, 9/5/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 10-8. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 6.

Fig. 10-9. Maxim, 1986 Power Supply Circuits, p. 121.

Fig. 10-10. Reprinted from EDN, 1/8/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 10-11. Linear Technology, Application Note 8, p. 2.

Fig. 10-12. GE, Optoelectronics, Third Edition, Ch. 6, p. 148.

## Chapter 11

Fig. 11-1. Harris, Analog Product Data Book, 1988, p. 10-183.

Fig. 11-2. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.

Fig. 11-3. Harris, Analog Product Data Book, 1988, p. 10-106.

Fig. 11-4. Signetics, 1987 Linear Data Manual Vol 2: Industrial, 2/87, p. 4-78.

Fig. 11-5. Linear Technology, 1986 Linear Databook, p. 2-45.

## Chapter 12

Fig. 12-1. Reprinted from EDN, 7/10/86, © 1989

Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 12-2. Ham Radio, 7/86, p. 88.

## Chapter 13

Fig. 13-1. Intersil, Applications Handbook, 1988, p. 3-138.

Fig. 13-2. Hands-On Electronics, Fall 1984, p. 68

## Chapter 14

Fig. 14-1. Radio-Electronics, 1/89, p. 55.

Fig. 14-2. Radio-Electronics, 2/89, p. 55

Fig. 14-3. Radio-Electronics, 2/89, p. 55

Fig. 14-4. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 5-36.

## Chapter 15

Fig. 15-1. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 12/2/86, p. 6-78.

Fig. 15-2. Harris, Analog Product Data Book, 1988, p. 2-106.

Fig. 15-3. TAB Books, 44 Electronics Projects for the Darkroom, p. 101.

Fig. 15-4. Reprinted from EDN, 10/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 16

Fig. 16-1. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 3-46 and 3-47.

Fig. 16-2. Linear Technology, 1986 Linear Databook, p. 2-44.

Fig. 16-3. Reprinted from EDN, 4/75, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 16-4. Reprinted from EDN, 4/79, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 16-5. National Semiconductor Corp., 1984 Linear Supplement Databook, p. S1-42.

Fig. 16-6. Linear Technology, 1986 Linear Databook, p. 2-29.

Fig. 16-7. Reprinted from EDN, 2/18/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 16-8. Harris, Analog Product Data Book, 1988, p. 10-16.

## Chapter 17

Fig. 17-1. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 4-373 and 4-375.

Fig. 17-2. Signetics, RF Communications Handbook, 1989, p. 2-17 and 2-18.

- Fig. 17-3. Signetics, RF Communications Handbook, 1989, p. 2-15 and 2-16.  
 Fig. 17-4. Signetics, RF Communications Handbook, 1989, p. 2-17 and 2-18.

## Chapter 18

- Fig. 18-1. Electronic Engineering, Applied Ideas, 4/86, p. 33.  
 Fig. 18-2. Siliconix, Integrated Circuits Data Book, 1988, p. 6-40 and 6-41.  
 Fig. 18-3. Hands-On Electronics/Popular Electronics, 11/88, p. 43.  
 Fig. 18-4. Linear Technology Corp., Linear Databook, 1986, p. 2-98.  
 Fig. 18-5. Siliconix, Integrated Circuits Data Book, 1988, p. 13-200.  
 Fig. 18-6. Siliconix, Integrated Circuits Data Book, 1988, p. 5-140.  
 Fig. 18-7. Reprinted from EDN, 4/28/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 18-8. Harris, Analog Product Data Book, 1988, 2-106.  
 Fig. 18-9. Reprinted from EDN, 10/27/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 18-10. Reprinted from EDN, 9/1/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 18-11. Reprinted from EDN, 6/22/89, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 18-12. Reprinted with permission from Electronic Design. Copyright 1988, Penton Publishing.  
 Fig. 18-13. Reprinted from EDN, 9/1/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 18-14. Intersil, Component Data Catalog, 1987, p. 13-22.  
 Fig. 18-15. Electronic Engineering, Applied Ideas, 10/88, p. 37.  
 Fig. 18-16. Electronic Engineering, Applied Ideas, 12/88, p. 22.

## Chapter 19

- Fig. 19-1. Teledyne Semiconductor, Data Acquisition IC Handbook, 1985, p. 9-7.  
 Fig. 19-2. Radio Electronics, 9/89, p. 47.  
 Fig. 19-3. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-65.

- Fig. 19-4. Maxim, Seminar Applications Book, 1988/89, p. 149.  
 Fig. 19-5. Ham Radio, 5/89, p. 26.  
 Fig. 19-6. Popular Electronics, 10/89, p. 42.  
 Fig. 19-7. Maxim, Seminar Applications Book, 1988/89, p. 83.  
 Fig. 19-8. Reprinted from EDN, 10/2/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 19-9. Linear Technology Corp., Linear Databook, 1986, p. 8-13.  
 Fig. 19-10. Linear Technology Corp., Linear Databook, 1986, p. 8-43.  
 Fig. 19-11. Maxim, Seminar Applications Book, 1988/89, p. 78.  
 Fig. 19-12. Reprinted from EDN, 3/7/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 19-13. Reprinted from EDN, 8/17/89, © Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 19-14. Linear Technology Corp., Linear Databook, 1986, p. 2-112.  
 Fig. 19-15. Reprinted from EDN, 10/1/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 19-16. Reprinted from EDN, 3/3/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 19-17. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-62.

## Chapter 20

- Fig. 20-1. QST, 2/89, p. 21.  
 Fig. 20-2. Reprinted from EDN, 11/10/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 20-3. Hands-On Electronics / Popular Electronics, 1/89, p. 59.  
 Fig. 20-4. Reprinted from EDN, 3/74, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 20-5. Intersil, Component Data Catalog, 1987, p. 14-49.  
 Fig. 20-6. Gernsback Publications Inc., 42 New Ideas, 1984, p. 18.  
 Fig. 20-7. R-E Experimenters Handbook, 1987, p. 151.

## Chapter 21

- Fig. 21-1. Motorola, MECL System Design Handbook, 1983, p. 226.  
 Fig. 21-2. Reprinted from EDN, 2/78, © 1989 Cahners

- Publishing Co., a division of Reed Publishing USA.
- Fig. 21-3. Radio-Electronics, 2/86, p. 46.
- Fig. 21-4. Reprinted from EDN, 6/83, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 21-5. Reprinted from EDN, 6/83, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 21-6. Radio-Electronics, 2/87, p. 96.
- Fig. 21-7. Motorola, MECL System Design Handbook, 1983, p. 228.
- Fig. 21-8. Reprinted from EDN, 5/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 21-9. NASA Tech Briefs, 8/89, p. 20.
- Fig. 21-10. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-14.
- Fig. 21-11. RF Design, 3/87, p. 31.
- Fig. 21-12. 73 Amateur Radio, 1/89, p. 35.
- Fig. 21-13. RF Design, 3/87, p. 31.
- Fig. 21-14. RF Design, 3/87, p. 31.

## Chapter 22

- Fig. 22-1. R-E Experiments Handbook, 1989, p. 23.
- Fig. 22-2. Hands-On Electronics / Popular Electronics, 1/89, p. 97.
- Fig. 22-3. Reprinted from EDN, 7/21/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 22-4. Hands-On Electronics / Popular Electronics, 1/89, p. 84.
- Fig. 22-5. Reprinted from EDN, 9/29/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 23

- Fig. 23-1. Reprinted from EDN, 10/29/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 23-2. Reprinted from EDN, 3/4/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 23-3. Reprinted from EDN, 10/3/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 24

- Fig. 24-1. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 4-303.

## Chapter 25

- Fig. 25-1. Reprinted from EDN, 3/21/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

- Fig. 25-2. Harris, Analog Product Data Book, 1988, p. 2-106.
- Fig. 25-3. Teledyne Semiconductor, Data Acquisitions IC Handbook, 1985, p. 15-15.
- Fig. 25-4. Siliconix, Integrated Circuits Data Book, 3/85, p.5-8.
- Fig. 25-5. Signetics, RF Communications Handbook, 1989, p. 3-22.
- Fig. 25-6. Reprinted from EDN, 1/20/79, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 25-7. Gernsback Publications Inc., 42 New Ideas, 1984, p. 6.
- Fig. 25-8. National Semiconductor Corp., Linear Databook, 1982, p. 3-97.
- Fig. 25-9. Radio-Electronics, 3/89, p. 12.
- Fig. 25-10. Harris, Analog Product Data Book, 1988, p. 10-167.
- Fig. 25-11. Reprinted from EDN, 9/19/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 25-12. Reprinted from EDN, 4/76, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 25-13. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-11 and 7-12.
- Fig. 25-14. Radio Electronics, 4/89, p. 60.
- Fig. 25-15. Reprinted from EDN, 12/8/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 25-16. Reprinted from EDN, 2/20/76, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 25-17. Reprinted from EDN, 10/17/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 26

- Fig. 26-1. Siliconix, Integrated Circuits Data Book, 3/85, p. 4-15.
- Fig. 26-2. Precision Monolithics Inc., 1981 Full Line Catalog, p. 6-85.
- Fig. 26-3. Intersil, Applications Handbook, 1988, p. 2-38.
- Fig. 26-4. Intersil, Applications Handbook, 1988, p. 3-183.
- Fig. 26-5. Harris, Analog Product Data Book, 1988, p. 10-17.
- Fig. 26-6. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 12.

## Chapter 27

Fig. 27-1. Electronic Engineering, 12/78, p. 31.

## Chapter 28

Fig. 28-1. Siliconix, Mospower Applications Handbook, p. 6-161.

Fig. 28-2. Motorola, Motorola Thyristor Device Data, Series A, 1985, p.1-5-27.

Fig. 28-3. Reprinted from EDN, 7/10/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 28-4. Siliconix, Integrated Circuits Data Book, 3/85, p. 1-11.

## Chapter 29

Fig.29-1. Signetics, Fiber-Optic Communication Data and Applications, 1988, p. 5-3.

Fig. 29-2. Signetics, Fiber-Optic Communication Data and Applications, 1988, p. 3-63 and 3-64.

Fig. 29-3. Signetics, Fiber-Optic Communication Data and Applications, 1988, p. 2-3 and 2-4.

Fig. 29-4. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 5-56 and 5-58.

Fig. 29-5. Signetics, Fiber-Optic Communication Data and Applications, 1988, p. 3-3.

Fig. 29-6. Signetics, Fiber-Optic Communication Data and Applications, 1988, p. 3-7 and 3-9.

## Chapter 30

Fig. 30-1. Ham Radio, 1/85, p. 51.

Fig. 30-2. Hands-On Electronics, 8/87, p. 65.

## Chapter 31

Fig. 31-1. Siliconix, Integrated Circuits Data Book, 1988, p. 13-181.

Fig. 31-2. Reprinted from EDN, 9/29/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 31-3. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing,

Fig. 31-4. Harris, Analog Product Data Book, 1988, p. 10-16.

Fig. 31-5. Harris, Analog Product Data Book, 1988, p. 10-175.

Fig. 31-6. Intersil, Component Data Catalog, 1987, p. 7-45.

Fig. 31-7. Reprinted from EDN, 3/16/89, © 1989

Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 31-8. Raytheon, Linear and Integrated Circuits, 1989, p. 4-189.

Fig. 31-9. Popular Electronics, Fact Card No. 101.

Fig. 31-10. Popular Electronics, Fact Card No. 104.

Fig. 31-11. Popular Electronics, Fact Card No. 59.

Fig. 31-12. Popular Electronics, Fact Card No. 59.

Fig. 31-13. Popular Electronics, Fact Card No. 117.

Fig. 31-14. Popular Electronics, Fact Card No. 117.

Fig. 31-15. Popular Electronics, Fact Card No. 117.

Fig. 31-16. Popular Electronics, Fact Card No. 101.

## Chapter 32

Fig. 32-1. Hands-On Electronics, 3/87, p. 97.

Fig. 32-2. Ideas for Design.

Fig. 32-3. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-4. Popular Electronics, 9/89, p. 88.

Fig. 32-5. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-6. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-7. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-8. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-9. Popular Electronics, Fact Card No. 65.

Fig. 32-10. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-17.

Fig. 32-11. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-12. Hands-On Electronics, 3/87, p. 97.

Fig. 32-13. ZeTeX, (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-153.

Fig. 32-14. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-15. Popular Electronics, 9/89, p. 23.

Fig. 32-16. Reprinted from EDN, 7/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-17. Reprinted from EDN, 9/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 32-18. Popular Electronics/Hands-On Electronics, 5/89, p. 86.

## Chapter 33

Fig.33-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN5-5.

## Chapter 34

34-1. National Semiconductor Corp., Linear Applications Databook, p. 1079.

- Fig. 34-2. Radio-Electronics, 6/88, p. 49.  
 Fig. 34-3. TAB Books, The Build-It Book of Electronic Projects, p. 18.  
 Fig. 34-4. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 23.  
 Fig. 34-5. Hands-On Electronics, 9-10/86, p. 24.  
 Fig. 34-6. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.  
 Fig. 34-7. Reprinted from EDN, 2/21/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

### Chapter 35

- Fig. 35-1. Signetics, RF Communications Handbook, 1989, p. 1-33.  
 Fig. 35-2. Signetics, RF Communications Handbook, 1989, p. 1-33.  
 Fig. 35-3. Intersil, Component Data Catalog, 1987, p. 7-44.  
 Fig. 35-4. Hands-On Electronics, Fact Card No. 29.

### Chapter 36

- Fig. 36-1. Electronic Engineering, 9/87, p. 27.  
 Fig. 36-2. Reprinted from EDN, 5/26/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 36-3. Reprinted from EDN, 2/77, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 36-4. Reprinted from EDN, 6/8/89, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 36-5. Signetics, RF Communications Handbook, 1989, p. 4-10 and 4-11.  
 Fig. 36-6. Reprinted from EDN, 11/24/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

### Chapter 37

- Fig. 37-1. Reprinted from EDN, 5/83, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

### Chapter 38

- Fig. 38-1. Reprinted from EDN, 3/21/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 38-2. Reprinted from EDN, 11/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 38-3. Reprinted from EDN, 12/13/84, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

- Fig. 38-4. Popular Electronics/Hands-On Electronics, 4/89, p. 23.  
 Fig. 38-5. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 7.  
 Fig. 38-6. Electronic Engineering, 9/88, p. 34.  
 Fig. 38-7. Electronic Engineering, 9/86, p. 34.  
 Fig. 38-8. Reprinted from EDN, 4/14/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 38-9. Electronic Engineering, 4/88, p. 33.  
 Fig. 38-10. Reprinted from EDN, 5/26/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 38-11. GE/RCA BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 8.  
 Fig. 38-12. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.  
 Fig. 38-13. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 4-312.  
 Fig. 38-14. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-18.  
 Fig. 38-15. Intersil, 1978 Databook.  
 Fig. 38-16. Harris, Analog Product Data Book, 1988, p. 10-109.  
 Fig. 38-17. Siliconix, Integrated Circuits Data Book, 1981, p. 8-51.  
 Fig. 38-18. Hands-On Electronics/Popular Electronics, 1/89, p. 84.  
 Fig. 38-19. GE/RCA BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 9.  
 Fig. 38-20. National Semiconductor Corp., Linear Applications Databook, p. 1118.  
 Fig. 38-21. Raytheon, Linear and Integrated Circuit, 1984, p. 12-8.  
 Fig. 38-22. Reprinted from EDN, 6/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 38-23. Maxim, Seminar Applications Book, 1988/89, p. 45.  
 Fig. 38-24. Raytheon, Linear and Integrated Circuits, 1984, p. 12-7.  
 Fig. 38-25. Harris, Analog Product Data Book, 1988, p. 10-15.  
 Fig. 38-26. Intersil, Component Data Catalog, 1987, p. 7-104.  
 Fig. 38-27. Popular Electronics, Fact Card No. 98.  
 Fig. 38-28. Hands-On Electronics, Fact Card No. 86.  
 Fig. 38-29. Harris, Analog Product Data Book, 1988, p. 10-168.  
 Fig. 38-30. Hands-On Electronics, Fact Card No. 86.  
 Fig. 38-31. Raytheon, Linear and Integrated Circuits,

1989, p. 4-188.

Fig. 38-32. GE/RCA BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 8.

Fig. 38-33. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 9.

Fig. 38-34. Hands-On Electronics, Fact Card No. 89.

Fig. 38-35. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 4-311.

Fig. 38-36. Intersil, Component Data Catalog, 1987, p. 7-44.

Fig. 38-37. Hands-On Electronics, Fact Card No. 89.

## Chapter 39

Fig. 39-1. Popular Electronics/Hands-On Electronics, 3/89, p. 24.

Fig. 39-2. Popular Electronics, 6/89, p. 27.

Fig. 39-3. Elektor, 6/78, p. 6-18.

## Chapter 40

Fig. 40-1. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 27.

Fig. 40-2. Linear Technology Corp., Linear Databook, 1986, p. 2-99.

Fig. 40-3. Reprinted from EDN, 8/75, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 40-4. Reprinted from EDN, 9/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 40-5. Linear Technology Design Notes, 3/89, Number 5.

Fig. 40-6. General Instrument Microelectronics, Application Note 1601, p. 3.

Fig. 40-7. Reprinted from EDN, 2/76, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 40-8. Popular Electronics, Fact Card No. 65.

Fig. 40-9. Reprinted from EDN, 10/30/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 41

Fig. 41-1. Reprinted from EDN, 7/7/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 41-2. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 12-9.

Fig. 41-3. Reprinted from EDN, 7/11/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 41-4. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 12-8.

## Chapter 42

Fig. 42-1. Motorola, RF Data Manual, 1986, p. 6-226.

Fig. 42-2. Motorola, RF Data Manual, 1986, p. 6-85.

Fig. 42-3. 73 Amateur Radio, 3/89, p. 66.

Fig. 42-4. Signetics, RF Communications Handbook, 1989, p. 1-31.

Fig. 42-5. Siliconix, Small-Signal FET Data Book, 1989, p. 4-158, 4-159, and 9-42.

Fig. 42-6. R-E Experiments Handbook, 1989, p. 156.

Fig. 42-7. R-E Experiments Handbook, 1989, p. 33.

Fig. 42-8. Reprinted from EDN, 1/7/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 43

Fig. 43-1. NASA, NASA Tech Briefs, p. 55.

## Chapter 44

Fig. 44-1. Elektor Electronics, 7-8/87 Supplement, p. 36.

Fig. 44-2. Reprinted from EDN, 5/74, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 44-3. Hands-On Electronics, Fact Card No. 57.

Fig. 44-4. 73 Magazine, 10/83, p. 53.

Fig. 44-5. Practical Wireless, 5/85, p. 37.

## Chapter 45

Fig. 45-1. Radio-Electronics, 8/88, p. 37.

Fig. 45-2. GE, optoelectronics, Third Edition, Ch. 6, p. 115.

Fig. 45-3. Popular Electronics/Hands-On Electronics, 4/89, p. 83.

Fig. 45-4. ZeTeX (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-155.

Fig. 45-5. Popular Electronics/Hands-On Electronics, 4/89, p. 82.

Fig. 45-6. Reprinted from EDN, 11/13/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 45-7. Hands-On Electronics, Fact Card No. 83.

Fig. 45-8. Popular Electronics, Fact Card No. 94.

Fig. 45-9. Hands-On Electronics, Fact Card No. 83.

## Chapter 46

Fig. 46-1. Linear Technology, Application Note 9, p. 6.

Fig. 46-2. Maxim, Maxim Advantage, p. 45.

Fig. 46-3. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-2.

Fig. 46-4. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 19.

- Fig. 46-5. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 15.  
 Fig. 46-6. Harris, Analog Product Data Book, 1988, p. 10-181.  
 Fig. 46-7. Maxim, Maxim Advantage, p. 45.  
 Fig. 46-8. Siliconix, Integrated Circuits Data Book, 1988, p. 5-172.

## Chapter 47

- Fig. 47-1. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-64.  
 Fig. 47-2. Linear Technology Corp., Linear Databook, 1986, p. 8-40.

## Chapter 48

- Fig. 48-1. Fairchild Camera & Instrument Corp., Linear Databook, 1982, p. 4-88.  
 Fig. 48-2. National Semiconductor Corp., Linear Databook, 1982, p. 10-63.  
 Fig. 48-3. Hands-On Electronics/Popular Electronics, 1/89, p. 39.  
 Fig. 48-4. Hands-On Electronics/Popular Electronics, 11/88, p. 39.  
 Fig. 48-5. Popular Electronics, Fact Card No. 59.

## Chapter 49

- Fig. 49-1. R-E Experimenters Handbook, 1987, p. 129.  
 Fig. 49-2. Popular Electronics, 6/89, p. 25.  
 Fig. 49-3. Maxim, Seminar Applications Book, 1988/89, p. 81.  
 Fig. 49-4. Motorola, Motorola TMOS Power FET Design Ideas, p. 35.  
 Fig. 49-5. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-14.  
 Fig. 49-6. Popular Electronics, 10/89, p.26.

## Chapter 50

- Fig. 50-1. Elektor Electronics, 7-8/87 Supplement, p. 55.  
 Fig. 50-2. Reprinted from EDN, 10/27/88, © Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 50-3. Hands-On Electronics/Popular Electronics, 1/89, p. 27.  
 Fig. 50-4. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 22.  
 Fig. 50-5. Motorola, Motorola Thyristor Device Data, Series A, 1985, p. 1-6-54.  
 Fig. 50-6. Hands-On Electronics, Fact Card No. 37.  
 Fig. 50-7. Motorola, Motorola Thyristor Device Data, Series A, 1985, p. 1-6-48.

- Fig. 50-8. Modern Electronics, 11/85, p. 44.  
 Fig. 50-9. Motorola, Motorola Thyristor Device Data, Series A, 1985, p. 1-6-10.  
 Fig. 50-10. GE, Optoelectronics, Third Edition, Ch. 6, p. 106.  
 Fig. 50-11. ZeTeX (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-158.  
 Fig. 50-12. Reprinted with permission from Electronic Design, Copyright 1989, Penton Publishing.  
 Fig. 50-13. GE, Optoelectronics, Third Edition, Ch. 6, p. 110.

## Chapter 51

- Fig. 51-1. TAB Books, Build Your Own Laser, Phaser, Ion Ray Gun, 1983, p. 13.  
 Fig. 51-2. Siliconix, Mospower Applications Handbook, p. 6-184.

## Chapter 52

- Fig. 52-1. GE, Optoelectronics, Third Edition, Ch. 6, p. 109.  
 Fig. 52-2. GE, Optoelectronics, Third Edition, Ch. 6, p. 112.  
 Fig. 52-3. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 19.  
 Fig. 52-4. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 3-3 and 3-4.  
 Fig. 52-5. Reprinted from EDN, August 1976, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 52-6. Harris, Analog Product Data Book, 1988, p. 10-182.  
 Fig. 52-7. GE, Optoelectronics, Third Edition, Ch. 6, p. 109.  
 Fig. 52-8. GE, Optoelectronics, Third Edition, Ch. 6, p. 107.  
 Fig. 52-9. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 7.  
 Fig. 52-10. Hands-On Electronics, Fact Card No. 57.  
 Fig. 52-11. GE, Optoelectronics, Third Edition, Ch. 6, p. 108.  
 Fig. 52-12. GE, Application Note 200.35, p. 15.

## Chapter 53

- Fig. 53-1. Hands-On Electronics, 9/87, p. 96.  
 Fig. 53-2. Popular Electronics, Fact Card No. 113.  
 Fig. 53.3 Harris, Analog Product Data Book, 1988, p. 10-54.

## Chapter 54

- Fig. 54-1. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 5-350 and 5-352.

## Chapter 55

- Fig. 55-1. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.  
Fig. 55-2. Hands-On Electronics, Fact Card No. 29.  
Fig. 55-3. Hands-On Electronics, Fact Card No. 29.

## Chapter 56

- Fig. 56-1. Reprinted from EDN, 5/2/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 56-2. Popular Electronics, 10/89, p. 104.  
Fig. 56-3. Hands-On Electronics, Winter 1985, p. 31.  
Fig. 56-4. Ham Radio, 4/86, p. 24.  
Fig. 56-5. Gernsback Publications Inc., 42 New Ideas, 1984, p. 24.  
Fig. 56-6. Ham Radio, 12/88, p. 19.  
Fig. 56-7. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 12-5.  
Fig. 56-8. Reprinted from EDN, 3/23/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 56-9. 73 Amateur Radio, 6/89, p. 44.  
Fig. 56-10. Hands-On Electronics, 2/87, p. 92.  
Fig. 56-11. Elektor Electronics, 7-8/87 Supplement, p. 23.  
Fig. 56-12. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 20.  
Fig. 56-13. GE, Optoelectronics, Third Edition, Ch. 6, p. 111.  
Fig. 56-14. Hands-On Electronics, 7-8/86, p. 51.  
Fig. 56-15. Intersil, Component Data Catalog, 1987, p. 14-70.  
Fig. 56-16. Intersil, Component Data Catalog, 1987, p. 14-121.  
Fig. 56-17. NASA, NASA Tech Briefs, 1/89, p. 19.  
Fig. 56-18. Reprinted from EDN, 5/83, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 56-19. 73 Amateur Radio, 8/88, p. 24.  
Fig. 56-20. Linear Technology Corp., Linear Databook, 1986, p. 2-96.  
Fig. 56-21. Radio-Electronics, 9/87, p. 32.  
Fig. 56-22. Hands-On Electronics/Popular Electronics, 12/88, p. 61.  
Fig. 56-23. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-137.  
Fig. 56-24. GE/RCA BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 12.  
Fig. 56-25. Electronic Engineering, 11/86, p. 34.  
Fig. 56-26. Popular Electronics, 10/89, p. 84.  
Fig. 56-27. Teledyne Semiconductor, Data Acquisition

IC Handbook, 1985, p. 15-11.

Fig. 56-28. GE, Optoelectronics, Third Edition, Ch. 6, p. 112.

Fig. 56-29. Reprinted from EDN, 3/79, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 57

- Fig. 57-1. Reprinted from EDN, 3/7/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 57-2. Electronic Engineering, Applied Ideas, 5/88, p. 25.  
Fig. 57-3. Signetics. 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-63.  
Fig. 57-4. Reprinted from EDN, 9/15/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 58

- Fig. 58-1. Radio-Electronics, 12/85, p. 38.

## Chapter 59

- Fig. 59-1. Popular Electronics/Hands-On Electronics, 3/89, p. 82.  
Fig. 59-2. GE, Application Note 90.16, p. 25.  
Fig. 59-3. Popular Electronics/Hands-On Electronics, 3/89, p. 83.  
Fig. 59-4. Popular Electronics/Hands-On Electronics, 4/89, p. 22.  
Fig. 59-5. Popular Electronics/Hands-On Electronics, 3/89, p. 82.  
Fig. 59-6. Radio-Electronics, 10/88, p. 51.  
Fig. 59-7. Radio-Electronics, 4/85, p. 40.  
Fig. 59-8. Siliconix, Small-Signal FET Data Book, 1989, p. 6-69 and 6-70.  
Fig. 59-9. R-E Experimenter's Handbook, 1989, p. 41.  
Fig. 59-10. RF Design, 7/89, p. 53.  
Fig. 59-11. GE, Application Note 200.85, p. 16.  
Fig. 59-12. GE, Application Note 200.85, p. 19.  
Fig. 59-13. Harris, Analog Product Data Book, 1988, p. 10-109.  
Fig. 59-14. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN13-24.  
Fig. 59-15. Gernsback Publications Inc., 44 New Ideas, 1985, p. 2.  
Fig. 59-16. Radio-Electronics, 6/89, p. 42.  
Fig. 59-17. Hands-On Electronics, 3/87, p. 26.

## Chapter 60

- Fig. 61-1. National Semiconductor Corp., Linear Applications Databook, p. 1028.

- Fig. 60-2. Popular Electronics, 7/89, p. 23.  
 Fig. 60-3. Harris, Analog Product Data Book, 1988, p. 10-170.  
 Fig. 60-4. Popular Electronics, Fact Card No. 107.  
 Fig. 60-5. Harris, Analog Product Data Book, 1988, p. 10-176.

## Chapter 61

- Fig. 61-1. Reprinted from EDN, 11/28/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 61-2. Signetics, 1987 Linear Data Manual Vol.2: Industrial, 10/10/86, p. 4-260.  
 Fig. 61-3. Electronic Design, 11/24/88, p. 222.  
 Fig. 61-4. Reprinted from EDN, 11/28/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 61-5. Popular Electronics, 10/89, p. 23.  
 Fig. 61-6. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-59.  
 Fig. 61-7. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/78, p. 7-59.  
 Fig. 61-8. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 4-3.  
 Fig. 61-9. Signetics, RF Communications Handbook, 1989, p. 4-9.

## Chapter 62

- Fig. 62-1. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 53.  
 Fig. 62-2. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 29.  
 Fig. 62-3. Reprinted with permission from Electronic Design. Copyright 1988, Penton Publishing.  
 Fig. 62-4. Reprinted from EDN, 8/20/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 62-5. Reprinted from EDN, 3/77, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 62-6. Signetics, 1987 Linear Data Manual Vol.2: Industrial, 2/87, p. 7-63.  
 Fig. 62-7. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN1-7.  
 Fig. 62-8. NASA, NASA Tech Briefs, 2/89, p. 26.  
 Fig. 62-9. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN11-7.  
 Fig. 62-10. Maxim, Maxim Advantage, p. 47.  
 Fig. 62-11. Signetics, 1987 Linear Data Manual Vol.2: Industrial, 2/87, p. 8-94 and 8-95.  
 Fig. 62-12. Fairchild Camera and Instrument Corp., Linear Databook, 1982, p. 4-89.

- Fig. 62-13. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 10-22.  
 Fig. 62-14. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-22.  
 Fig. 62-15. ZeTeX (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-162.  
 Fig. 62-16. Linear Technology Corp., Linear Databook, 1986, p. 5-15.

## Chapter 63

- Fig. 63-1. Siliconix, Integrated Circuits Data Book, 1988, p. 13-203.  
 Fig. 63-2. Maxim, Seminar Applications Book, 1988/89, p. 61.  
 Fig. 63-3. Intersil, Applications Handbook, 1988, p. 5-6.  
 Fig. 63-4. Siliconix, Integrated Circuits Data Book, 1988, p. 13-200.  
 Fig. 63-5. Harris, Analog Product Data Book, 1988, p. 10-23.  
 Fig. 63-6. Intersil, Applications Handbook, 1988, p. 5-6.  
 Fig. 63-7. Harris, Analog Product Data Book, 1988, p. 10-12.

## Chapter 64

- Fig. 64-1. Signetics, Analog Data Manual, 1983, p. 4-26.  
 Fig. 64-2. Signetics, Analog Data Manual, 1983, p. 4-32.  
 Fig. 64-3. Signetics, Analog Data Manual, 1983, p. 4-33.

## Chapter 65

- Fig. 65-1. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 3-10 and 3-11.  
 Fig. 65-2. National Semiconductor Corp., Linear Applications, p. 1083.

## Chapter 66

- Fig. 66-1. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-211.

## Chapter 67

- Fig. 67-1. GE, Optoelectronics, Third Edition, Ch. 6, p. 141.  
 Fig. 67-2. GE, Optoelectronics, Third Edition, Ch. 6, p. 135.  
 Fig. 67-3. GE, Optoelectronics, Third Edition, Ch. 6, p. 144.  
 Fig. 67-4. GE, Optoelectronics, Third Edition, Ch. 6, p. 134.  
 Fig. 67-5. GE, Optoelectronics, Third Edition, Ch. 6, p. 147.

- Fig. 67-6. GE, Optoelectronics, Third Edition, Ch. 6, p. 127.
- Fig. 67-7. Reprinted from EDN, 1/82, © 1989 Cahner Publishing Co., a division of Reed Publishing USA.
- Fig. 67-8. GE, Optoelectronics, Third Edition, Ch. 6, p. 123.
- Fig. 67-9. GE, Optoelectronics, Third Edition, Ch. 6, p. 126.
- Fig. 67-10. GE, Optoelectronics, Third Edition, Ch. 6, p. 108.
- Fig. 67-11. GE, Optoelectronics, Third Edition, Ch. 6, p. 122.
- Fig. 67-12. GE, Optoelectronics, Third Edition, Ch. 6, p. 135.
- Fig. 67-13. GE, Optoelectronics, Third Edition, Ch. 6, p. 145.
- Fig. 67-14. GE, Optoelectronics, Third Edition, Ch. 6, p. 138.
- Fig. 67-15. Reprinted from EDN, 11/10/88, © 1989 Cahner Publishing Co., a division of Reed Publishing USA.

## Chapter 68

- Fig. 68-1. Reprinted from EDN, 8/7/86, © 1989 Cahner Publishing Co., a division of Reed Publishing USA.
- Fig. 68-2. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-17.
- Fig. 68-3. GE, Application Note 90.16, p. 27.
- Fig. 68-4. Elektor Electronics, 7-8/87 Supplement, p. 36.
- Fig. 68-5. Harris, Analog Product Data Book, 1988, p. 10-15.
- Fig. 68-6. Elektor Electronics, 7-8/87 Supplement, p. 63.
- Fig. 68-7. Reprinted from EDN, 1/79, © 1989 Cahner Publishing Co., a division of Reed Publishing USA.
- Fig. 68-8. Elektor Electronics, 7-8/87 Supplement, p. 59.
- Fig. 68-9. Reprinted from EDN, 7/74, © 1989 Cahners Publishing Co., A division of Reed Publishing USA.
- Fig. 68-10. Harris, Analog Product Data Book, 1988, p. 10-97.
- Fig. 68-11. Reprinted from EDN, 1/77, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 68-12. Radio-Electronics, 8/86, p. 83.
- Fig. 68-13. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN20-11.
- Fig. 68-14. Fairchild Camera and Instrument, Linear Databook, 1982, p. 4-71.
- Fig. 68-15. Reprinted from EDN, 8/76, © 1989 Cahners

- Publishing Co., a division of Reed Publishing USA.
- Fig. 68-16. Reprinted from EDN, 5/11/89, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 68-17. Reprinted from EDN, 4/82, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 68-18. Hands-On Electronics, Fact Card No. 49.
- Fig. 68-19. Reprinted from EDN, 2/2/89 © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 68-20. Hands-On Electronics/Popular Electronics, 1/89, p. 26.
- Fig. 68-21. GE/RCA, BiMOS Operational Amplifier Circuit Ideas, 1987, p. 9.
- Fig. 68-22. Reprinted from EDN, 1/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 68-23. Harris, Analog Product Data Book, 1988, p. 10-108.

## Chapter 69

- Fig. 69-1. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-62.
- Fig. 69-2. Elektor Electronics, 7-8/87 Supplement, p. 50.
- Fig. 69-3. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-13.
- Fig. 69-4. Reprinted from EDN, 3/82, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 69-5. Radio-Electronics, 10/84, p. 32.
- Fig. 69-6. 73 Amateur Radio, 8/88, p. 47.
- Fig. 69-7. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 4-2.
- Fig. 69-8. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-62.
- Fig. 69-9. Ham Radio, 12/88, p. 26.

## Chapter 70

- Fig. 70-1. Harris, Analog Product Data Book, 1988, p. 10-14.
- Fig. 70-2. Reprinted from EDN, 8/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 70-3. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 4-67 and 4-68.

## Chapter 71

- Fig. 71-1. Popular Electronics/Hands-On Electronics, 4/89, p. 26.
- Fig. 71-2. Hands-On Electronics, 1/87, p. 101.
- Fig. 71-3. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-14.
- Fig. 71-4. Hands-On Electronics, 11/87, p. 32.

- Fig. 71-5. GE, Optoelectronics, Third Edition, Ch. 6, p. 105.  
 Fig. 71-6. Popular Electronics, 9/89, p. 22.  
 Fig. 71-7. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 24.

## Chapter 72

- Fig. 72-1. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 1.  
 Fig. 72-2. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 25.  
 Fig. 72-3. Popular Electronics.  
 Fig. 72-4. Motorola, Motorola Power FET Design Ideas, 1985, p. 2.  
 Fig. 72-5. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 3-14.  
 Fig. 72-6. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/6/86, p. 7-246.  
 Fig. 72-7. Hands-On Electronics, 7-8/86, p. 43.  
 Fig. 72-8. Siliconix, Mospower Applications Handbook, p. 6-180.

## Chapter 73

- Fig. 73-1. GE, Optoelectronics, Third Edition, Ch. 6, p. 152.  
 Fig. 73-2. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 38.  
 Fig. 73-3. 73 Amateur Radio, 6/89, p. 61.  
 Fig. 73-4. Texas Instruments, Linear and Interface Circuits Applications, 1987, p. 12-5.  
 Fig. 73-5. QST, 6/88, p. 48.  
 Fig. 73-6. Texas Instruments, Linear Circuits Data Book, 1989, p. 2-74.  
 Fig. 73-7. Maxim, 1986 Power Supply Circuits, p. 27.  
 Fig. 73-8. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 6-36.  
 Fig. 73-9. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 6-36.  
 Fig. 73-10. Reprinted from EDN, 5/5/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 73-11. Hands-On Electronics, 7-8/86.  
 Fig. 73-12. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 6-34.  
 Fig. 73-13. 73 Amateur Radio, 5/88, p. 90.  
 Fig. 73-14. Reprinted from EDN, 7/7/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 73-15. Harris, Analog Product Data Book, 1988, p. 10-16.  
 Fig. 73-16. Hands-On Electronics, Fact Card No. 49.

- Fig. 73-17. Popular Electronics, Fact Card No. 100.  
 Fig. 73-18. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-13.  
 Fig. 73-19. Harris, Analog Product Data Book, 1988, p. 10-107.  
 Fig. 73-20. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 12.  
 Fig. 73-21. Reprinted from EDN, 4/20/77, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 73-22. Intersil, Applications Handbook, 1988, p. 6-17.  
 Fig. 73-23. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 14.  
 Fig. 73-24. Electronic Engineering, 2/87, p. 44.  
 Fig. 73-25. Popular Electronics, Fact Card No. 100.  
 Fig. 73-26. Intersil, Applications Handbook, 1988, p. 6-70.  
 Fig. 73-27. Reprinted with permission from Electronic Design. Copyright 1988, Penton Publishing.  
 Fig. 73-28. Maxim, Seminar Applications Book, 1988/89, p. 83.  
 Fig. 73-29. Intersil, Applications Handbook, 1988, p. 6-18.  
 Fig. 73-30. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-15.  
 Fig. 73-31. Popular Electronics, Fact Card No. 100.  
 Fig. 73-32. Popular Electronics, Fact Card No. 95.  
 Fig. 73-33. Maxim, 1986 power Supply Circuits, p. 26.

## Chapter 74

- Fig. 74-1. NASA, NASA Tech Briefs, 1/88, p. 22.  
 Fig. 74-2. Reprinted from EDN 6/22/89, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 74-3. Motorola, Motorola, TMOS Power FET Design Ideas, 1985, p. 40.  
 Fig. 74-4. Popular Electronics, 10/89, p. 37.  
 Fig. 74-5. Hands-On Electronics, 12/86, p. 93.  
 Fig. 74-6. Electronic Engineering, Applied Ideas, 3/86, p. 33.  
 Fig. 74-7. Reprinted from EDN, 9/15/82 and 1/6/83, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 79-8. Reprinted from EDN, 10/17/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 74-9. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN2-7.  
 Fig. 74-10. NASA, NASA Tech Briefs, Summer 1985, p. 48.

Fig. 74-11. Hands-On Electronics, 12/86, p. 92.

## Chapter 75

Fig. 75-1. Siliconix, Mospower Applications Handbook, p. 6-62.

Fig. 75-2. 73 Amateur Radio, 4/88, p. 20.

Fig. 75-3. Reprinted from EDN, 12/8/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 75-4. Linear Technology Corp., Linear Application Handbook, 1987, p. AN8-4.

Fig. 75-5. Ham Radio, 7/89, p. 20.

Fig. 75-6. Popular Electronics, Fact Card No. 100.

Fig. 75-7. Popular Electronics, Fact Card No. 95.

## Chapter 76

Fig. 76-1. Hands-On Electronics, 1-2/86, p. 96.

Fig. 76-2. Maxim, 1986 Power Supply Circuits, p. 120.

## Chapter 77

Fig. 77-1. Hands-On Electronics, 12/87, p. 73.

Fig. 77-2. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN9-9.

Fig. 77-3. Microwaves and RF, 3/86, p. 143.

Fig. 77-4. Reprinted from EDN, 6/72, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 77-5. Reprinted from EDN, 7/7/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 77-6. Reprinted from EDN, 10/16/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 77-7. Reprinted from EDN, 3/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 77-8. Harris, Analog Product Data Book, 1988, p. 10-182.

Fig. 77-9. Linear Technology Corp., Application Note 9, p. 9.

Fig. 77-10. Hands-On Electronics, 9/87, p. 96.

## Chapter 78

Fig. 78-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-5.

Fig. 78-2. Siliconix, Integrated Circuits Data Book, 1988, p. 5-128.

Fig. 78-3. Intersil, Applications Handbook, 1988, p. 2-34.

Fig. 78-4. Harris, Analog Product Data Book, 1988, p. 10-13.

Fig. 78-5. Harris, Analog Product Data Book, 1988, p. 10-13.

Fig. 78-6. Harris, Analog Product Data Book, 1988, p. 10-169.

## Chapter 79

Fig. 79-1. 73 Magazine, 7/77, p. 35.

Fig. 79-2. Reprinted from EDN, 4/83, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 79-3. TAB Books, 104 Weekend Electronics Projects, p. 70.

Fig. 79-4. Contributed by William Sheets.

Fig. 79-5. Reprinted from EDN, 6/12/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 79-6. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 16.

## Chapter 80

Fig. 80-1. Hands-On Electronics, 7/87, p. 47.

Fig. 80-2. RF Design, 12/86, p. 41.

Fig. 80-3. Popular Electronics/Hands-On Electronics, 5/89, p. 85.

Fig. 80-4. Hands-On Electronics, Fact Card No. 57.

Fig. 80-5. Siliconix, Small-Signal FET Data Book, 1/86, p. 7-28.

## Chapter 81

Fig. 81-1. Popular Electronics, 9/89, p. 41.

Fig. 81-2. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 15.

Fig. 81-3. Reprinted from EDN, 11/10/88, © Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 81-4. Reprinted from EDN, 5/82, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 81-5. Reprinted from EDN, 11/27/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 81-6. Linear Technology Corp., Linear Databook, 1986, p. 5-33.

## Chapter 82

Fig. 82-1. Reprinted from EDN, 11/13/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 82-2. Harris, Analog Product Data Book, 1988, p. 10-14.

## Chapter 83

Fig. 83-1. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/14/86, p. 7-33.

Fig. 83-2. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 11/14/86, p. 4-115.

Fig. 83-3. Radio-Electronics, 8/87, p. 39.

Fig. 83-4. Signetics, RF Communications Handbook,

- 1989, p. 3-80 and 3-81.  
 Fig. 83-5. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-66 and 7-67.  
 Fig. 83-6. RF Design, 3/87, p. 46.  
 Fig. 83-7. 73 Amateur Radio, 10.86, p. 54.  
 Fig. 83-8. GE, Optoelectronics, Third Edition, Ch. 6, p. 128.  
 Fig. 83-9. Hands-On Electronics/Popular Electronics, 1/89, p. 35.  
 Fig. 83-10. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 7-25.

### Chapter 84

- Fig. 84-1. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/6/86, p. 4-137.  
 Fig. 84-2. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 17.

### Chapter 85

- Fig. 85-1. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-66 and 7-67.  
 Fig. 85-2. Hands-On Electronics/Popular Electronics, 12/88, p. 24.  
 Fig. 85-3. National Semiconductor Corp., Voltage Regulator Handbook, p. 10-59.

### Chapter 86

- Fig. 86-1. QST, 9/85, p. 41.  
 Fig. 86-2. Motorola, RF Data Manual, 1986, p. 6-221.  
 Fig. 86-3. Microwaves and RF, 9/85, p. 191.  
 Fig. 86-4. Teledyne Semiconductor, Data and Design Manual, 1981, p. 11-178.  
 Fig. 86-5. Harris, Analog Product Data Book, 1988, p. 10-58.  
 Fig. 86-6. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 20.  
 Fig. 86-7. Motorola, RF Data Manual, 1986, p. 6-182.  
 Fig. 86-8. Radio-Electronics, 3/82, p. 59.  
 Fig. 86-9. Motorola, RF Data Manual, 1986, p. 6-236.

### Chapter 87

- Fig. 87-1. Intersil, Component Data Catalog, p. 7-96.  
 Fig. 87-2. Harris, Analog Product Data Book, 1988, p. 10-22.  
 Fig. 87-3. Harris, Analog Product Data Book, 1988, p. 10-54.  
 Fig. 87-4. Harris, Analog Product Data Book, 1988, p. 10-22.  
 Fig. 87-5. Harris, Analog Product Data Book, 1988, p. 10-37.

- Fig. 87-6. Siliconix, Integrated Circuits Data Book, 1988, 5-127.  
 Fig. 87-7. Harris, Analog Product Data Book, 1988, p. 10-14.  
 Fig. 87-8. Harris, Analog Product Data Book, 1988, p. 10-22.  
 Fig. 87-9. GE/RCA, BiMOS Operational Amplifier Circuit Ideas, 1987, p. 13.

### Chapter 88

- Fig. 88-1. Popular Electronics/Hands-On Electronics, 3/89, p. 24.  
 Fig. 88-2. Popular Electronics/Hands-On Electronics, 12/88, p. 26.

### Chapter 89

- Fig. 89-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN5-7.  
 Fig. 89-2. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 7.  
 Fig. 89-3. Linear Technology Corp., Linear Databook Supplement, 1988, p. S2-34.  
 Fig. 89-4. Hands-On Electronics, 9/87, p. 97.

### Chapter 90

- Fig. 90-1. Popular Electronics, 10/89, p. 84.  
 Fig. 90-2. National Semiconductor, Linear Databook, 1982, p. 3-289.  
 Fig. 90-3. Hands-On Electronics, Spring 1985, p. 35.  
 Fig. 90-4. National Semiconductor Corp., Audio/Radio Handbook, 1980, p. 4-29.  
 Fig. 90-5. Hands-On Electronics, 5-6/86, p. 86.  
 Fig. 90-6. Reprinted from EDN, 8/4/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 90-7. Everyday Electronics, 5/88, p. 292.  
 Fig. 90-8. Hands-On Electronics, Winter 1985, p. 72.  
 Fig. 90-9. Radio-Electronics, 12/81, p. 53.  
 Fig. 90-10. Reprinted with permission from Electronic Design. Copyright 1980, Penton Publishing.  
 Fig. 90-11. National Semiconductor Corp., Audio/Radio Handbook, 1980, p. 4-39.  
 Fig. 90-12. National Semiconductor Corp., Linear Databook, 1982, p. 3-289.  
 Fig. 90-13. Texas Instruments, Complex Sound Generator Bulletin No. DL-S 12612, p. 15.

### Chapter 91

- Fig. 91-1. GE, Optoelectronics, Third Edition, Ch. 6, p. 131.

## Chapter 92

- Fig. 92-1. Reprinted from EDN, 4/17/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 92-2. ZeTeX (formerly Ferranti), Technical Handbook Super E-Line Transistors, 1987, p. SE-154.
- Fig. 92-3. Reprinted from EDN, 12/8/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 93

- Fig. 93-1. Gernsback Publications Inc., 42 New Ideas, 1984, p. 4.
- Fig. 93-2. Hands-On Electronics, 11/87, p. 92.
- Fig. 93-3. Radio-Electronics, 12/81, p. 54.
- Fig. 93-4. Radio-Electronics, 12/81, p. 53.
- Fig. 93-5. Texas Instruments, Complex Sound Generator Bulletin No. DL-S 12612, p. 11.

## Chapter 94

- Fig. 94-1. Reprinted from EDN, 8/5/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 94-2. Hands-On Electronics, 3/87, p. 26.

## Chapter 95

- Fig. 95-1. Harris, Analog Product Data Book, 1988, p. 10-97.
- Fig. 95-2. Siliconix, Integrated Circuits Data Book, 3/85, p. 5-8.

## Chapter 96

- Fig. 96-1. Reprinted from EDN, 4/30/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 96-2. Reprinted from EDN, 5/28/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 96-3. Exar, Telecommunications Databook, 1986, p. 9-24.
- Fig. 96-4. Exar, Telecommunications Databook, 1986, p. 9-24.

## Chapter 97

- Fig. 97-1. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-28.
- Fig. 97-2. Intersil, Component Data Catalog, 1987, p. 7-96.

## Chapter 98

- Fig. 98-1. Hands-On Electronics, 2/87, p. 65.

## Chapter 99

- Fig. 99-1. Motorola, TMOS Power FET Design Ideas, 1985, p. 48.
- Fig. 99-2. Reprinted from EDN, 2/18/88, Cahner Publishing Co., a division of Reed Publishing USA.
- Fig. 99-3. Reprinted from EDN, 5/79, © 1989 Cahner Publishing Co., a division of Reed Publishing USA.
- Fig. 99-4. Siliconix, Mospower Applications Handbook, p. 6-185.
- Fig. 99-5. Reprinted from EDN, 6/76, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

## Chapter 100

- Fig. 100-1. Reprinted from EDN, 3/3/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 100-2. Reprinted from EDN, 5/26, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 100-3. Electronic Engineering, Applied Ideas, 11/88, p. 28.

## Chapter 101

- Fig. 101-1. Hands-On Electronics, 11/87, p. 84.
- Fig. 101-2. Popular Electronics/Hands-On Electronics, 5/89, p. 87.
- Fig. 101-3. Hands-On Electronics, 11/87, p. 85.

## Chapter 102

- Fig. 102-1. Exar, Telecommunications Databook, 1986, p. 4-2.
- Fig. 102-2. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-23.
- Fig. 102-3. Hands-On Electronics, Winter 1985, p. 49.
- Fig. 102-4. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 12/2/86, p. 6-23.
- Fig. 102-5. Popular Electronics, 9/89, p. 27.
- Fig. 102-6. National Semiconductor Corp., 1984 Linear Supplement Databook, p. S13-15.
- Fig. 102-7. Popular Electronics, Fact Card No. 104.
- Fig. 102-8. Exar, Telecommunications Databook, 1986, p. 11-61.
- Fig. 102-9. Siliconix, Integrated Circuits Data Book, 3/85, p. 7-12.
- Fig. 102-10. 73 Magazine, 10.78, p. 78.
- Fig. 102-11. National Semiconductor Corp., 1984 Linear Supplement Databook, p. S13-16.
- Fig. 102-12. Reprinted from EDN, 8/78, © 1989

Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 102-13. Siliconix, Integrated Circuits Data Book, 3/85, p. 7-11.

Fig. 102-14. Reprinted from EDN, 10/20/79, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 102-15. Intersil, Databook 1987, p. 7-8.

Fig. 102-16. GE, Optoelectronics, Third Edition, Ch. 6, p. 128.

Fig. 102-17. Reprinted from EDN, 8/79, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 102-18. Radio-Electronics, 10/83, p. 56.

Fig. 102-19. Electronic Engineering, 2/87, p. 40.

Fig. 102-20. Reprinted from EDN, 4/27/89, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 102-21. Hands-On Electronics, 10/87, p. 95.

Fig. 102-22. Hands-On Electronics, 9-10/86, p. 88.

Fig. 102-23. Popular Electronics/Hands-On Electronics, 5/89, p. 86.

Fig. 102-24. GE, Optoelectronics, Third Edition, Ch. 6, p. 124.

Fig. 102-25. Hands-On Electronics, 7-8/86, p. 87.

Fig. 102-26. TAB Books, 101 Sound, Light, and Power IC Projects.

Fig. 102-27. Hands-On Electronics, 9-10/86, p. 105.

### **Chapter 103**

Fig. 103-1. Motorola, Motorola Thyristor Device Data, Series A 1985, p. 1-6-60.

Fig. 103-2. Linear Technology Corp., Application Note 22, p. 10.

Fig. 103-3. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN5-1.

Fig. 103-4. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 24.

Fig. 103-5. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN4-7.

Fig. 103-6. Radio-Electronics, 5/85, p. 110.

### **Chapter 104**

Fig. 104-1. Siliconix, Integrated Circuits Data Book, 1988, p. 13-204.

Fig. 104-2. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/14/86, p. 5-58.

Fig. 104-3. Linear Technology Corp., Linear Databook, 1986, p. 8-43.

### **Chapter 105**

Fig. 105-1. Electronic Engineering, Applied Ideas, 11/88, p. 28.

### **Chapter 106**

Fig. 106-1. Gernsback Publications Inc., 42 New Ideas, 1984, p. 18.

Fig. 106-2. Popular Electronics, 8/89, p. 29.

### **Chapter 107**

Fig. 107-1. TAB Books, 44 Electronics Projects for the Darkroom.

Fig. 107-2. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/14/86, p. 5-58.

Fig. 107-3. Raytheon, Linear and Integrated Circuits, 1989, p. 8-16.

Fig. 107-4. R-E Experimenters Handbook, 1987, p. 11.

Fig. 107-5. NASA, NASA Tech Briefs, 10/87, p. 34.

Fig. 107-6. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN3-14.

Fig. 107-7. Hands-On Electronics, 9-10/86, p. 32.

### **Chapter 108**

Fig. 108-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN7-12.

### **Chapter 109**

Fig. 109-1. Radio-Electronics, 7/85, p. 16.

Fig. 109-2. GE, Semiconductor Data Handbook, Second Edition, p. 905.

Fig. 109-3. Motorola, Motorola Thyristor Device Data, Series A 1985, p. 1-6-43.

### **Chapter 110**

Fig. 110-1. Reprinted from EDN, 9/13/86, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.

Fig. 110-2. Intersil, Databook 1987, p. 7-101.

Fig. 110-3. Radio-Electronics, 5/87, p. 129.

Fig. 110-4. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 7-13.

Fig. 110-5. TAB Books, The Build-It Book of Electronic Projects, p. 32.

### **Chapter 111**

Fig. 111-1. Texas Instruments, Linear and Interface Circuits Applications, 1985, Vol. 1, p. 3-11 and 3-12.

Fig. 111-2. National Semiconductor Corp., Audio/Radio Handbook, 1980, p. 2-61.

- Fig. 111-3. Popular Electronics, Fact Card No. 113.  
 Fig. 111-4. Reprinted from EDN, 7/7/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 111-5. Signetics, Analog Data Manual, 1983, p. 10-93.

## Chapter 112

- Fig. 112-1. Popular Electronics, 9/89, p. 88.  
 Fig. 112-2. Popular Electronics, 9/89, p. 88.  
 Fig. 112-3. Hands-On Electronics, 9/87, p. 89.  
 Fig. 112-4. Hands-On Electronics, 9/87, p. 89.  
 Fig. 112-5. National Semiconductor Corp., Transistor Databook, 1982, p. 7-11.  
 Fig. 112-6. Popular Electronics, 7/89, p. 25.  
 Fig. 112-7. Contributed by William Sheets.  
 Fig. 112-8. Contributed by William Sheets.  
 Fig. 112-9. Hands-On Electronics, Fact Card No. 86.

## Chapter 113

- Fig. 113-1. Linear Technology Corp., 1986 Linear Databook, p. 2-69.  
 Fig. 113-2. Fairchild Camera and Instrument Corp., Linear Databook, 1982, p. 4-71.  
 Fig. 113-3. Electronics Today International, 10/75, p. 64.

## Chapter 114

- Fig. 114-1. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 18.  
 Fig. 114-2. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 21.  
 Fig. 114-3. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 19.  
 Fig. 114-4. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 7-173.  
 Fig. 114-5. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 7-173.  
 Fig. 114-6. Radio-Electronics, 3/86, p. 8.  
 Fig. 114-7. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 7-173.  
 Fig. 114-8. Signetics, 1987 Linear Data Manual Vol. 1: Communications, 2/87, p. 7-173.

## Chapter 115

- Fig. 115-1. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 44.  
 Fig. 115-2. Radio-Electronics, 6/89, p. 45.  
 Fig. 115-3. TAB Books, Build Your Own Laser, Phaser, Ion Ray Gun, 1983, p. 292.

- Fig. 115-4. 73 Amateur Radio, 1/87, p. 46.  
 Fig. 115-5. GE, Optoelectronics, Third Edition, Ch. 6, p. 118.  
 Fig. 115-6. Hands-On Electronics, 11/87, p. 44.  
 Fig. 115-7. R-E Experimenters Handbook, 1987, p. 161.  
 Fig. 115-8. Radio-Electronics, 9/89, p. 43.  
 Fig. 115-9. Popular Electronics, 8/89, p. 27.  
 Fig. 115-10. 73 Amateur Radio, 3/88, p. 96.  
 Fig. 115-11. Ham Radio, 9/89, p. 56.  
 Fig. 115-12. GI Microelectronics Gemini, TV Games Section 4B, p. 22.  
 Fig. 115-13. Radio-Electronics, 3/89, p. 43.  
 Fig. 115-14. QST, 3/86, p. 32.  
 Fig. 115-15. 73 Amateur Radio, 1/87, p. 48.  
 Fig. 115-16. Radio-Electronics, 3/88, p. 54.  
 Fig. 115-17. 73 Amateur Radio, 6/89, p. 20.  
 Fig. 115-18. Contributed by William Sheets.

## Chapter 116

- Fig. 116-1. TAB Books, 101 Sound, Light, and Power IC Projects.  
 Fig. 116-2. National Semiconductor Corp., Audio/Radio Handbook, 1980, p. 5-11.  
 Fig. 116-3. Electronic Engineering, 1/79, p. 27.  
 Fig. 116-4. Radio-Electronics, 9/85, p. 96.

## Chapter 117

- Fig. 117-1. Reprinted from EDN, 4/3/86, ©1989 Cahners Publishing Co., a division of Reed Publishing USA.  
 Fig. 117-2. Popular Electronics, 9/89, p. 102.  
 Fig. 117-3. R-E Experimenters Handbook, p. 92.  
 Fig. 117-4. GE, Optoelectronics, Third Edition, Ch. 6, p. 149.  
 Fig. 117-5. National Semiconductor Corp., Linear Applications Databook, p. 1083.  
 Fig. 117-6. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 26.  
 Fig. 117-7. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 25.  
 Fig. 117-8. Reprinted with permission from Electronic Design. Copyright 1975, Penton Publishing.  
 Fig. 117-9. Popular Electronics/Hands-On Electronics, 2/89, p. 46.  
 Fig. 117-10. TAB Books, Build Your Own Laser, Phaser, Ion Ray Gun, 1983, p. 170.  
 Fig. 117-11. Electronics Today International, 2/82, p. 89.

## Chapter 118

- Fig. 118-1. GE, Application Note 90.88, p. 7.  
Fig. 118-2. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN4-3.  
Fig. 118-3. Harris, Analog Product Data Book, 1988, p. 10-149.  
Fig. 118-4. Harris, Analog Product Data Book, 1988, p. 10-58.  
Fig. 118-5. Harris, Analog Product Data Book, 1988, p. 10-54.  
Fig. 118-6. Harris, Analog Product Data Book, 1988, p. 10-96.  
Fig. 118-7. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.

## Chapter 119

- Fig. 119-1. Electronics Digest, Spring 1988, p. 63.  
Fig. 119-2. Electronic Engineering, 5/84, p. 36.  
Fig. 119-3. Motorola, Linear Integrated, Circuits, p. 5-37.  
Fig. 119-4. Reprinted from EDN, 8/18/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 119-5. Signetics, Linear Data Manual Vol. 3: Video, p. 10-58.  
Fig. 119-6. Radio-Electronics, 2/86, p. 51.  
Fig. 119-7. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-67.  
Fig. 119-8. Radio-Electronics, 9/87, p. 41.  
Fig. 119-9. Hands-On Electronics, Winter 1985, p. 44.  
Fig. 119-10. Electronic Engineering, 8/86, p. 32.  
Fig. 119-11. Signetics Linear Data Manual Vol. 3: Video, p. 11-95.  
Fig. 119-12. Electronic Engineering, 7/84, p. 27.  
Fig. 119-13. Siliconix, Integrated Circuits Data Book, 3/85, p. 10-66.  
Fig. 119-14. Reprinted from EDN, 5/16/85, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 119-15. Hands-On Electronics, 7-8/86, p. 78.  
Fig. 119-16. Siliconix, Small-Signal FET Data Book, 1/86, p. 7-101.

## Chapter 120

- Fig. 120-1. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.  
Fig. 120-2. Reprinted from EDN, 1/7/88, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 120-3. Hands-On Electronics, 10/88, p. 30.

- Fig. 120-4. Reprinted with permission from Electronic Design. Copyright 1988, Penton Publishing.  
Fig. 120-5. Gernsback Publications Inc., 42 New Ideas, 1984, p. 16.

## Chapter 121

- Fig. 121-1. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 47.  
Fig. 121-2. Intersil, Component Data Catalog, 1987, p. 6-29.  
Fig. 121-3. Reprinted from EDN, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 121-4. Intersil, Applications Handbook, 1988, p. 6-6.  
Fig. 121-5. Reprinted from EDN, 10/1/87, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.  
Fig. 121-6. Texas Instruments, Linear and Interface Circuit Applications, 1985, p. 7-19.  
Fig. 121-7. Texas Instruments, Linear Circuits Data Book, 1989, p. 2-73.  
Fig. 121-8. Popular Electronics, 10/89, p. 105.

## Chapter 122

- Fig. 122-1. Electronic Engineering, 11/76, p. 23.  
Fig. 122-2. Datel, Data Conversion Components, p. 6-18.  
Fig. 122-3. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 41.  
Fig. 122-4. Motorola, Linear Integrated Circuits, p. 5-145.  
Fig. 122-5. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN8-9.  
Fig. 122-6. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 39.  
Fig. 122-7. Maxim, 1986 Power Supply circuits, p. 44.  
Fig. 122-8. Radio-Electronics, 4/85, p. 80.  
Fig. 122-9. Motorola, Motorola TMOS Power FET Design Ideas, 1985, p. 36.

## Chapter 123

- Fig. 123-1. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN9-14.  
Fig. 123-2. Analog Devices, Data Acquisition Databook, 1982, p. 6-27.  
Fig. 123-3. Electronic Engineering, 12/75, p. 11.  
Fig. 123-4. Electronic Engineering, 7/76, p. 23.  
Fig. 123-5. Reprinted with permission from Electronic Design. Copyright 1975, Penton Publishing.

- Fig. 123-6. Linear Technology Corp., Linear Databook, 1986, p. 5-79.
- Fig. 123-7. Reprinted with permission from Electronic Design. Copyright 1975, Penton Publishing.
- Fig. 123-8. Linear Technology Corp., Linear Databook, 1986, p. 5-33.
- Fig. 123-9. Electronic Engineering, 10/77, p. 17.
- Fig. 123-10. Linear Technology Corp., Linear Applications Handbook, 1987, p. AN9-13.
- Fig. 123-11. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 2/87, p. 7-63.
- Fig. 123-12. Reprinted with permission from Electronic Design. Copyright 1967, Penton Publishing.

## Chapter 124

- Fig. 124-1. Electronic Engineering, 10/84, p. 41.
- Fig. 124-2. Siliconix, Integrated Circuits Data Book, 3/85, p. 3-21.
- Fig. 124-3. National Semiconductor Corp., CMOS Databook, 1981, p. 3-41.
- Fig. 124-4. Reprinted with permission from Electronic Design. Copyright 1970, Penton Publishing.
- Fig. 124-5. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 16.
- Fig. 124-6. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 16.
- Fig. 124-7. Radio-Electronics, 11/82, p. 92.
- Fig. 124-8. Teledyne, Teledyne Semiconductor Databook, p. 9.
- Fig. 124-9. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 15.
- Fig. 124-10. TAB Books, Third Book of Electronic Projects, p. 37.
- Fig. 124-11. Ham Radio, 7/89, p. 62.
- Fig. 124-12. Hands-On Electronics, 4/87, p. 93.
- Fig. 124-13. Popular Electronics/Hands-On Electronics, 4/89, p. 25.

- Fig. 124-14. GE/RCA, BiMOS Operational Amplifiers Circuit Ideas, 1987, p. 11.
- Fig. 124-15. Gernsback Publications Inc., 44 New Ideas, 1985, p. 8.
- Fig. 124-16. Electronics Today International, 10/78, p. 95.
- Fig. 124-17. Radio-Electronics, 1/86, p. 104.
- Fig. 124-18. National Semiconductor Corp., Transistor Databook, 1982, p. 7-26.
- Fig. 124-19. Electronic Engineering, 9/85, p. 25.
- Fig. 124-20. Electronics Today International, 6/76, p. 42.
- Fig. 124-21. National Semiconductor Corp., Linear Databook, 1982, p. 362.
- Fig. 124-22. Signetics, 1987 Linear Data Manual Vol. 2: Industrial, 11/14/86, p. 5-269.

## Chapter 125

- Fig. 125-1. Reprinted with permission from Electronic Design. Copyright 1989, Penton Publishing.
- Fig. 125-2. Popular Electronics, 6/89, p. 22.
- Fig. 125-3. Electronic Engineering, Applied Ideas, 3/89, p. 32.

## Chapter 126

- Fig. 126-1. Electronic Engineering, 7/88, p. 27.
- Fig. 126-2. Electronics Today International, 6/76, p. 40.
- Fig. 126-3. Signetics, Analog Data Manual, 1982, p. 8-10.
- Fig. 126-4. Reprinted from EDN, 5/73, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 126-5. Electronic Engineering, 1/83, p. 31.
- Fig. 126-6. Reprinted from EDN, 8/20/78, © 1989 Cahners Publishing Co., a division of Reed Publishing USA.
- Fig. 126-7. Fairchild Camera and Instrument Corp., Linear Databook, 1982, p. 4-180.

# Index

Numbers preceded by a 'I,' 'II,' 'III,' or 'IV' are from *Encyclopedia of Electronic Circuits* Vol. I, II, III, or IV, respectively.

## A

- absolute-value amplifier, I-31
- absolute-value circuit, I-37, IV-274
- absolute-value full wave rectifier, II-528
- absolute-value Norton amplifier, III-11
- ac bridge circuit, II-81
- ac flasher, III-196
- ac linear coupler, analog, II-412
- ac motor
  - control for, II-375
  - three-phase driver, II-383
  - two-phase driver, II-382
- ac sequential flasher, II-238
- ac switcher, high-voltage optically coupled, III-408
- ac timer, .2 to 10 seconds, adjustable, II-681
- ac-coupled amplifiers, dynamic, III-17
- ac/dc indicator, IV-214
- ac-to-dc converter, I-165
  - fixed power supplies, IV-395
  - full-wave, IV-120
  - high-impedance precision rectifier, I-164
- acid rain monitor, II-245, III-361
- acoustic-sound receiver/transmitter, IV-311
- active antennas, III-1-2, IV-1-4
  - basic designs, IV-3
  - wideband rod, IV-4
  - with gain, IV-2
- active clamp-limiting amplifiers, III-15
- active crossover networks, I-172-173
- active filters (*see also* filter circuits)
  - band reject, II-401
  - bandpass, II-221, II-223, III-190
  - digitally tuned low power, II-218
  - five pole, I-279
  - high-pass, second-order, I-297
  - low-pass, digitally selected break frequency, II-216
  - low-power, digitally selectable center frequency, III-186
  - low-power, digitally tuned, I-279
  - programmable, III-185
  - RC, up to 150 kHz, I-294
  - state-variable, III-189
  - ten-band graphic equalizer using, II-684
  - three-amplifier, I-289
  - tunable, I-294
  - universal, II-214
  - variable bandwidth bandpass, I-286
- active integrator, inverting buffer, II-299
- adapters
  - dc transceiver, hand-held, III-461
  - program, second-audio, III-142
  - traveller's shaver, I-495
- adder, III-327
- AGC, II-17
- AGC amplifiers
  - AGC system for CA3028 IF amplifier, IV-458
  - rf, wideband adjustable, III-545
  - squelch control, III-33
  - wideband, III-15
- air conditioner, auto, smart clutch for, III-46
- air flow detector, I-235, II-242, III-364
- air flow meter (*see* anemometer)
- air-pressure change detector, IV-144
- air-motion detector, III-364
- airplane propeller sound effect, II-592
- alarms (*see also* detectors; indicators; monitors; sensors; sirens), III-3-9, IV-84-87

- alarms (*cont.*)
- auto burglar, II-2, I-3, III-4, I-7, I-10, IV-53
  - auto burglar, CMOS low-current design, IV-56
  - auto burglar, horn as loudspeaker, IV-54
  - auto burglar, single-IC design, IV-55
  - auto burglar, single-IC, III-7
  - auto-arming automotive alarm, IV-50
  - automatic turn-off after 8-minute delay, automotive, IV-52
  - automatic turn-off with delay, IV-54
  - blow fuse, I-10
  - boat, I-9
  - burglar, III-8, III-9, IV-86
  - burglar, latching circuit, I-8, I-12
  - burglar, NC and NO switches, IV-87
  - burglar, NC switches, IV-87
  - burglar, one-chip, III-5
  - burglar, self-latching, IV-85
  - burglar, timed shutoff, IV-85
  - camera triggered, III-444
  - capacitive sensor, III-515
  - current monitor and, III-338
  - differential voltage or current, II-3
  - digital clock circuit with, III-84
  - door-ajar, II-284
  - door-ajar, Hall-effect circuit, III-256
  - doorbell, rain, I-443
  - fail-safe, semiconductor, III-6
  - field disturbance, II-507
  - flasher, bar display, I-252
  - flood, III-206, I-390, IV-188
  - freezer meltdown, I-13
  - headlights-on, III-52
  - high/low limit, I-151
  - home-security system, IV-87
  - ice formation, II-58
  - infrared wireless security system, IV-222-223
  - low-battery disconnect and, III-65
  - low-battery warning, III-59
  - low volts, II-493
  - mains-failure indicator, IV-216
  - motion-actuated car, I-9
  - motion-actuated motorcycle, I-9
  - multiple circuit for, II-2
  - one-chip, III-5
  - photoelectric, II-4, II-319
  - piezoelectric, I-12
  - power failure, III-511, I-581, I-582
  - printer-error, IV-106
  - proximity, II-506, III-517
  - pulsed-tone, I-11
  - purse-snatcher, capacitance operated, I-134
  - rain, I-442, I-443, IV-189
  - road ice, II-57
  - security, I-4
  - self-arming, I-2
  - shutoff, automatic, I-4
  - signal-reception, receivers, III-270
  - smoke, photoelectric, line-operated, I-596
  - smoke, SCR, III-251
  - solar powered, I-13
  - sonic defenders, IV-324
  - speed, I-95
  - Star Trek red alert, II-577
  - strobe flasher alarm, IV-180
  - tamperproof burglar, I-8
  - temperature, II-643
  - temperature, light, radiation sensitive, II-4
  - timer, II-674
  - trouble tone alert, II-3
  - varying-frequency warning, II-579
  - wailing, II-572
  - warbling, II-573
  - watchdog timer/alarm, IV-584
  - water-leakage, IV-190
  - water level, I-389
  - allophone generator, III-733
  - alternators
    - battery-alternator monitor, automotive, III-63
  - AM demodulator, II-160
  - AM microphone, wireless, I-679
  - AM radio, I-544
  - AM radio
    - AM car-radio to short-wave radio converter, IV-500
    - broadcast-band signal generator, IV-302
    - envelope detector, IV-142
    - modulation monitor, IV-299
    - power amplifier for, I-77
    - receivers, III-529, IV-455
    - receivers, carrier-current, III-81
    - receivers, integrated, III-535
  - AM/FM
    - clock radio, II-543, III-1
    - squelch circuit for, II-547, III-1
  - amateur radio
    - linear amp, 2-30 MHz 140-W, III-260
    - receiver, III-534
    - signal-identifier, programmable, IV-326
    - transmitter, 80-M, III-675
  - ambience amplifier, rear speaker, II-458
  - ammeter, I-201
    - nano, I-202
    - pico, II-154, I-202
    - pico, circuit for, II-157
    - pico, guarded input circuit, II-156
    - six decade range, II-153, II-156
  - amplifiers, II-5-22, III-10-21
    - 1 watt/2.3 GHz, II-540
    - 2 to 6 W, with preamp, II-451
    - 25-watt, II-452
    - 30 MHz, I-567
    - 40 dB gain design, IV-36
    - 60 MHz, I-567
    - 135-175 MHz, I-564
    - absolute value, I-31
    - ac servo, bridge type, III-387
    - AGC, II-17
    - AGC, squelch control, III-33
    - AGC, wide-band, III-15
    - adjustable-gain, noninverting, I-91
    - ambience, rear speaker, II-458
    - amateur radio, linear, 2-30 MHz, 140W, I-555
    - AM radio power, I-77
    - attenuator, digitally controlled, I-53
    - audio (*see* audio amplifiers)
    - audio converter, two-wire to four-wire, II-14
    - audio limiter, low-distortion, II-15
    - audio power amplifiers, IV-28-33
    - audio signal amplifiers, IV-34-42
    - auto fade circuit for, II-42
    - automatic level control for, II-20
    - automotive audio amplifier, IV-66
    - balance, II-46
    - balance, loudness control, II-47, II-395
    - balancing circuit, inverting, I-33
    - bass tone control, stereo phonograph, I-670
    - bridge, I-74
    - bridge, 4W, I-79
    - bridge, 16 W, I-82
    - bridge, ac servo, I-458
    - bridge, audio power, I-81
    - bridge, high-impedance, I-353
    - bridge transducer, III-71, II-84, I-351
    - broadband, low-noise, I-562
    - broadband, PEP, 160W, I-556
    - broadband/linear, PEP, 80W, I-557
    - buffer, 10x, I-128
    - buffer, 100x, I-128
    - buffer, ac, single-supply, I-126
    - buffer, battery-powered, standard cell, I-351
    - buffer, rf amplifiers with modulator, IV-490
    - buffer, sinewave output, I-126
    - buffer, unity-gain, stable design, II-6
    - cascade, III-13
    - cascade, 80 MHz, I-567
    - cascode, rf amplifiers, IV-488
    - CD4049 audio signal amplifiers, IV-40
    - chopper,  $\pm$  15V, III-12
    - chopper channel, I-350

chopper stabilized, II-7  
 clamp-limiting, active, III-15  
 color video, I-34, III-724  
 common-source, 450 MHz, I-568  
 common-source, low power, II-84  
 complementary-symmetry, I-78  
 composite, II-8, III-13  
 compressor/amplifier, low-distortion, IV-24  
 constant-bandwidth, III-21  
 current-shunt, III-21  
 current collector head, II-11, II-295  
 current-to-voltage, high-speed, I-35  
 dc servo, I-457  
 dc-stabilized, fast action, III-18  
 dc-to-video log, I-38  
 detector, MC1330/MC1352, television IF, I-688  
 differential, III-14, I-38  
 differential, high-impedance, I-27, I-354  
 differential, high-input high-impedance, II-19  
 differential, instrumentation, I-347, III-283  
 differential, instrumentation, biomedical, III-282  
 differential, programmable gain, III-507  
 differential, two op amp bridge type, II-83  
 dynamic, ac-coupled, III-17  
 electrometer, overload protected, II-155  
 FET input, II-7  
 flat response, I-92, III-673  
 forward-current booster, III-17  
 four-quadrant photo-conductive detector, I-359  
 gain, 10-dB, III-543  
 gain-controlled, III-34  
 gate, I-36  
 guitars, matching audio signal amplifiers, IV-38  
 hi-fi compander, II-12  
 hi-fi expander, II-13  
 high-frequency, III-259-265  
 high-impedance/high gain/high-frequency, I-41  
 high-impedance/low capacitance, I-691  
 IF (*see* IF amplifiers)  
 input/output buffer for analog multiplexers, III-11  
 instrumentation, I-346, I-348, I-349, I-352, I-354, III-278-284, IV-229-234  
 instrumentation, differential, high-gain, I-353  
 instrumentation, high-impedance, low-drift, I-355  
 instrumentation, high-speed, I-354  
 instrumentation, low-signal/high-impedance, I-350  
 instrumentation, precision FET input, I-355  
 instrumentation, triple op-amp design, I-347  
 instrumentation, variable gain, differential input, I-349  
 instrumentation, very high-impedance, I-354  
 inverting, I-42, II-41, III-14  
 inverting, ac, high-gain, I-92  
 inverting, gain of 2, lag-lead compensation, UHF, I-566  
 inverting, power, I-79  
 inverting, unity gain, I-80  
 isolation, capacitive load, I-34  
 isolation, level-shifting, I-348  
 isolation, medical telemetry, I-352  
 isolation, rf, II-547  
 JFET bipolar cascade video, I-692  
 line amplifier, universal design, IV-39  
 linear, CMOS inverter in, II-11  
 line-operated, III-37  
 line-type, duplex, telephone, III-616  
 load line protected, 75W audio, I-73  
 logarithmic, II-8  
 logic (*see* logic amplifier)  
 log ratio, I-42  
 loudness control, II-46  
 low-noise design, IV-37  
 low-level video detector circuit, I-687  
 medical telemetry, isolation, I-352  
 meter-driver, rf, 1-MHz, III-545  
 micro-powered, high-input/high-impedance, 20 dB, II-44  
 micro-sized, III-36  
 microphone, III-34, I-87  
 microphone, electronically balanced input, I-86  
 microwave, IV-315-319  
 monostable, II-268  
 neutralized common source, 100 MHz/400MHz, I-565  
 neutralized common source, 200 MHz, I-568  
 noninverting, I-32, I-33, I-41, III-14  
 noninverting, ac power, I-79  
 noninverting, single-supply, I-75  
 noninverting, split-supply, I-75  
 Norton, absolute value, III-11  
 op amp (*see also* operational amplifiers)  
 op amp, x10, I-37  
 op amp, x100, I-37  
 op amp, clamping circuit, II-22  
 op amp, intrinsically safe-protected, III-12  
 oscilloscope sensitivity, III-436  
 output, four-channel D/A, III-165  
 phono, I-80, I-81  
 phono, magnetic pickup, I-89  
 photodiode, I-361, II-324, III-672  
 photodiode, low-noise, III-19  
 playback, tape, III-672  
 polarity-reversing low-power, III-16  
 power (*see also* power amps), II-46, II-451, III-450-456  
 power, 10-W, I-76  
 power, 12-W, low distortion, I-76  
 power, 90-W, safe area protection, II-459  
 power, GaAsFET with single supply, II-10  
 power, rf power, 600 W, I-559  
 pre-amps (*see* pre-amplifiers)  
 precision, I-40  
 programmable, II-334, III-504-508  
 programmable gain, weighted resistors, II-9  
 pulse-width proportional controller circuit, II-21  
 push-pull, PEP, 100W, 420-450 MHz, I-554  
 PWM servo, III-379  
 reference voltage, I-36  
 remote, I-91  
 rf (*see* rf amplifiers)  
 sample and hold, high-speed, I-587  
 sample and hold, infinite range, II-558  
 selectable input, programmable gain, I-32  
 servo, 400 Hz, II-386  
 servo motor, I-452  
 servo motor drive, II-384  
 signal distribution, I-39  
 sound-activated, gain-controlled amp, IV-528  
 sound mixer, II-37  
 speaker, hand-held transceivers, III-39  
 speaker, overload protector for, II-16  
 speech compressor, II-15  
 standard cell, saturated, II-296  
 stereo, Av/200, I-77  
 stereo, gain control, II-9  
 summing, I-37, III-16  
 summing, fast action, I-36  
 summing, precision design, I-36  
 switching power, I-33  
 tape playback, I-92, IV-36  
 tape recording, I-90  
 telephone, III-621, IV-555, IV-560

- amplifiers (*cont.*)
- thermocouple, I-654, III-14
  - thermocouple, cold junction compensation, II-649
  - thermocouple, high-stability, I-355
  - transducer, I-86, III-669-673
  - transformerless, 6W 8-ohm output, I-75
  - transistorized, basic design, I-85
  - transistorized, headphone, II-43
  - tremolo circuit, voltage-controlled, I-598
  - tube amplifier, high-voltage isolation, IV-426
  - TV audio, III-39
  - two-meter, 5W output, I-567
  - two-meter, 10W power, I-562
  - UHF, I-565
  - UHF, wideband, high-performance FET, I-560
  - unity gain, I-27
  - unity gain, ultra-high Z, ac, II-7
  - VHF, single-device, 80W/50-ohm, I-558
  - video, I-692, III-708-712
  - video, FET cascade, I-691
  - video, loop-through amplifier, IV-616
  - voice activated switch, I-608
  - voltage, differential-to-single-ended, III-670
  - voltage-controlled, IV-20
  - voltage-follower, signal-supply operation, III-20
  - voltage-controlled (*see* voltage-controlled amplifiers)
  - volume, II-46
  - walkman, II-456
  - weighted-resistor programmable gain, precision design, II-9
  - wideband (*see* wideband amplifiers)
  - wide frequency range, III-262
  - write, III-18
  - amplitude modulator, low distortion low level, II-370
  - analog counter circuit, II-137
  - analog delay line, echo and reverb effects, IV-21
  - analog multiplexers
    - buffered input/output, III-396
    - single-trace to four-trace scope converter, II-431
  - analog multiplier, II-392
    - 0/01 percent, II-392
  - analog-to-digital buffer, high-speed 6-bit, I-127
  - analog-to-digital converters, II-23-31, III-22-26, IV-5-6
    - 3-bit, high-speed, I-50
    - 8-bit, I-44, I-46
  - 8-bit successive approximation, I-47
  - 10-bit, II-28
  - 10-bit serial output, II-27
  - 12-bit, high-speed, II-29
  - 16-bit, II-26
  - board design, IV-6
  - capacitance meter, 3<sup>1</sup>/<sub>2</sub> digit, III-76
  - cyclic, II-30
  - differential input system, II-31
  - fast precision, I-49
  - four-digit (10,000 count), II-25
  - half-flash, III-26
  - IC, low cost, I-50
  - LCD 3.5-digit display, I-49
  - logarithmic, three-decade, I-48
  - precision design, I-49
  - successive approximation, I-45, II-24, II-30
  - switched-capacitor, III-23
  - three-IC, low-cost, I-50
  - tracking, III-24
  - video converter, IV-610-611
  - analyzer, gas, II-281
  - AND gate, I-395
    - large fan-in, I-395
  - anemometers
    - hot-wire, III-342
    - thermally based, II-241
  - angle-of-rotation detector, II-283
  - annunciators, II-32-34, III-27-28, IV-710
    - ac line-voltage, III-730
    - bell, electronic, IV-9
    - chime circuit, low-cost, II-33
    - door buzzer, IV-8
    - door buzzer, electronic, IV-8
    - electronic bell, II-33
    - large fan-in, I-395
    - SCR circuit, self-interrupting load, IV-9
    - sliding tone doorbell, II-34
    - two-door annunciator, IV-10
  - answering machines, beeper, IV-559
  - antennas, IV-11-14
    - active, III-1-2
    - active antenna, wideband rod, IV-4
    - active antenna, with gain, IV-2
    - active antennas, IV-1-4
    - loop, 3.5 MHz, IV-12-13
    - selector switch, IV-538-539
    - tuner, 1-to-30 MHz, IV-14
  - antitheft device, I-7
  - arc lamp, 25W, power supply for, II-476
  - arc welding inverter, ultrasonic, 20 KHz, III-700
  - arc-jet power supply, starting circuit, III-479
  - astable flip-flop with starter, II-239
  - astable multivibrators, II-269, II-510, III-196, III-233, III-238
    - op amp, III-224
    - programmable-frequency, III-237
    - square wave generation with, II-597
  - attendance counter, II-138
  - attenuators, III-29-31
    - analog signals, microprocessor-controlled, III-101
    - digitally programmable, III-30
    - digitally selectable, precision design, I-52
    - programmable, I-53, III-30
    - programmable (1 to 0.00001), I-53
    - rf, IV-322
    - variable, I-52
    - voltage-controlled, II-18, III-31
  - audio amplifiers, III-32-39
    - AGC, squelch control, III-33
    - automotive stereo systems, high-power, IV-66
    - balance indicator, IV-215
    - Baxandall tone-control, IV-588
    - booster, 20 dB, III-35
    - circuit bridge load drive, III-35
    - complementary-symmetry, I-78
    - distribution, I-39, II-39
    - fixed power supplies,  $\pm$  35 V ac, IV-398
    - fixed power supplies,  $\pm$  35 V, 5 A, mobile, IV-407
    - high-slew rate power op amp, I-82
    - gain-controlled, stereo, III-34
    - line-operated, III-37
    - load line protection, 75W, I-73
    - low-power, II-454
    - micro-sized, III-36
    - microphone, III-34
    - mini-stereo, III-38
    - pre-amp, NAB tape playback, professional, III-38
    - pre-amp, phono, magnetic, III-37
    - pre-amp, RIAA, III-38
    - Q-multiplier, II-20
    - signal, II-41-47
    - speaker, hand-held transceivers, III-39
    - television type, III-39
    - tone control, II-686
    - ultra-high gain, I-87
    - volume indicator, IV-212
  - audio circuits
    - audio-rf signal tracer probe, I-527
    - automatic gain control, II-17
    - booster, II-455, III-35
    - biquad filter, III-185
    - bridge load drive, III-35
    - carrier-current transmitter, III-79
    - clipper, precise, II-394
    - compressor, II-44

- continuity tester, I-550
- converter, two-wire to four-wire, II-14
- distribution amplifier, II-39, I-39
- filters (*see* audio filters)
- frequency meter, I-311
- generators (*see* sound generators)
- LED bar peak program meter display, I-254
- limiter, low distortion, II-15
- millivoltmeter, III-767, III-769
- mixers (*see* mixers)
- notch filter, II-400
- power meter, I-488
- Q multiplier, II-20
- sine wave generator, II-564
- squelch, II-394
- switching/mixing, silent, I-59
- waveform generators, precision, III-230
- audio effects circuits (*see* sound generators)
- audio equalizer, IV-18
- audio fader, IV-17
- audio filters
  - analyzer circuit, IV-309
  - biquad filter, III-185
  - notch filter, II-400
  - tunable, IV-169
- audio generators (*see* sound generators)
- audio-operated circuits (*see* sound-operated circuits)
- audio oscillators, I-64, II-24, III-427, IV-374, IV-375
  - 20Hz to 20kHz, variable, I-727
  - light-sensitive, III-315
  - sine wave, II-562
- audio power amplifier, II-451, III-454, IV-28-33
  - 20-W, III-456
  - 50-W, III-451
  - 6-W, with preamp, III-454
- audio amplifier, IV-32
- audio amplifier, 8-W, IV-32
- bridge, I-81
- bull horn, IV-31
- general-purpose, 5 W, ac power supply, IV-30
- op amp, simple design, IV-33
- receiver audio circuit, IV-31
- stereo amp, 12-V/20-W, IV-29
- audio scramblers, IV-25-27
  - voice scrambler/descrambler, IV-26
  - voice scrambler/disguiser, IV-27
- audio signal amplifiers, II-41-47, IV-34-42
  - 40 dB gain design, IV-36
  - audio compressor, II-44
  - auto fade, II-42
- balance, II-46
- balance and loudness amplifier, II-47
- CD4049 design, IV-40
- electric guitar, matching amplifier, IV-38
- line amplifier, universal design, IV-39
- loudness, II-46
- low-noise design, IV-37
- microphone preamp, II-45
- micropower high-input-impedance 20-dB amplifier, II-44
- power, II-46
- preamplifier, 1000x, low-noise design, IV-37
- preamplifier, general-purpose design, IV-42
- preamplifier, impedance-matching, IV-37
- preamplifier, low-noise, IV-41
- preamplifier, magnetic phono cartridges, IV-35
- preamplifier, microphone, IV-37, IV-42
- preamplifier, microphone, low-impedance, IV-41
- preamplifier, phono, low-noise, IV-36
- preamplifier, phono, magnetic, ultra-low-noise, IV-36
- stereo preamplifier, II-43, II-45
- tape playback amplifiers, IV-36
- transistor headphone amplifier, II-43
- volume, II-46
- audio-frequency doubler, IV-16-17
- audio/video switcher circuit, IV-540-541
- auto-advance projector, II-444
- autodrum sound effect, II-591
- auto-fade circuit, II-42
- auto-flasher, I-299
- auto-zeroing scale bridge circuits, III-69
- automotive circuits, II-48-63, III-40-52, IV-43-67
  - alarms, automatic-arming, IV-50
  - alarms, automatic turn-off after 8-minute delay, IV-52
  - alarms, automatic turn-off with delay, IV-54
  - alarms, CMOS design, low-current, IV-56
  - alarms, horn as loudspeaker, IV-54
  - alarm, motion actuated, I-9
  - alarms, single-IC design, IV-55
  - air conditioner smart clutch, III-46
  - AM-radio to short-wave radio converter, IV-500
  - analog expanded-scale meter, IV-46
  - audio-amplifier, high-power, IV-66
  - automatic headlight dimmer, II-63
- automobile locator, III-43
- automotive exhaust emissions analyzer, II-51
- back-up beeper, III-49, IV-51, IV-56
- bar-graph voltmeter, II-54
- battery charger, ni-cad, I-115
- battery condition checker, I-108
- battery current analyzer, I-104
- battery monitor, I-106
- battery supply circuit,  $\pm 15$  V and 5 V, IV-391
- battery-alternator monitor, III-63
- brake lights, delayed extra, III-44
- brake lights, flashing third, III-51
- brake light, night-safety light for parked cars, IV-61
- brake light, third brake light, IV-60
- burglar alarm, I-3, I-7, I-10, II-2, III-4, III-7, IV-53
- cassette-recorder power circuit, IV-548
- courtesy light delay switch, III-42
- courtesy light extender, III-50
- delayed-action windshield wiper control, II-55
- digi-tach, II-61
- directional signals monitor, III-48
- door ajar monitor, III-46
- electric vehicles, battery saver, III-67
- electrical tester, IV-45
- electronic circuits, IV-63-67
- fog light controller with delay, IV-59
- fuel gauge, digital readout, IV-46
- exhaust-gas emissions analyzer, II-51
- garage stop light, II-53
- glow plug driver, II-52
- headlight alarm, I-109, III-52
- headlight automatic-off controller, IV-61
- headlight delay circuit, II-59, III-49
- headlight dimmer, II-57
- high-speed warning device, I-101
- horn, III-50
- ice formation alarm, II-58
- ignition circuit, electronic ignition, IV-65
- ignition cut-off, IV-53
- ignition substitute, III-41
- ignition timing light, II-60
- immobilizer, II-50
- intermittent windshield wiper with dynamic braking, II-49
- light circuits, IV-57-62
- lights-on warning, II-55, III-42, IV-58, IV-60, IV-62
- night-safety light for parked cars, IV-61
- oil-pressure gauge, digital readout, IV-44, IV-47

automotive circuits (*cont.*)

PTC thermistor automotive temperature indicator, II-56  
radio, receiver for, II-525  
read-head pre-amplifier, III-44  
road ice alarm, II-57  
security system, I-5, IV-49-56  
tachometer, set point, III-47  
tachometer/dwell meter, III-45  
temperature gauge, digital readout, IV-48  
temperature indicator, PTC thermistor, II-56  
turn signals, sequential flasher, II-109, III-1  
vacuum gauge, digital readout, IV-45  
voltage gauge, IV-47  
voltage regulator, III-48, IV-67  
voltmeter, bargraph, I-99  
water-temperature gauge, IV-44  
wiper control, II-55, II-62  
wiper delay, solid-state, IV-64  
wiper interval controller, IV-67

## B

B-field measurer, IV-272  
back-biased GaAs LED light sensor, II-321  
back-EMF PM motor speed control, II-379  
backup-light beeper, automotive, IV-51, IV-56  
bagpipe sound effect, IV-521  
balance indicator, audio amplifiers, IV-215  
balancer, stereo, I-619  
barricade flasher, I-299  
battery charge/discharge indicator, I-122  
battery charger, automatic shut-off, II-113  
balance amplifiers, III-46  
  loudness control, II-47, II-395  
balance indicator, bridge circuit, II-82  
bandpass filters (*see also* filter circuits), II-222  
  0.1 to 10 Hz bandpass, I-296  
  160 Hz, I-296  
  active, II-221, II-223, III-190  
  active, with 60dB gain, I-284  
  active, 1 kHz, I-284  
  active, 20 kHz, I-297  
  active, variable bandwidth, I-286  
  biquad, RC active, I-285  
  biquad, second-order, III-188  
  Chebyshev, fourth-order, III-191  
  high Q, I-287  
  MFB, multichannel tone decoder, I-288  
  multiple feedback, I-285, II-224  
  multiple feedback, 1.0 kHz, I-297  
  notch, II-223  
  Sallen-Key, 500 Hz, I-291  
  second-order biquad, III-188  
  state variable, I-290  
  tunable, IV-171  
band reject filters, active (*see also* filter circuits), II-401  
bang-bang power controllers, IV-389  
bar-code scanner, III-363  
bar-expanded scale meter, II-186  
bar graphs  
  ac signal indicator, II-187  
  voltmeter, II-54  
  voltmeter, automotive, I-99  
barometer, IV-273  
bass tuners, II-362  
  12 V, I-111  
  200 mA-hour, 12V ni-cad, I-114  
  automatic shutoff for, I-113  
batteries  
  fixed power supply, 12-VDC/120-VAC, III-464  
  high-voltage generator, III-482  
  zapper, simple ni-cad, I-116  
battery chargers, I-113, II-64, II-69, III-53-59, IV-68-72  
  12-V charger, IV-70  
battery-life extender, lead-acid batteries, IV-72  
  constant-voltage, current limited charger, I-115  
  control for 12V, I-112  
  current limited 6V, I-118, IV-70  
  gel cell, II-66  
  lead/acid, III-55  
  lithium, II-67  
  low-battery detector, lead-acid, III-56  
  low-battery warning, III-59  
  low-cost trickle for 12V storage, I-117  
  mobile battery charger, +12-Vdc, IV-71  
  ni-cad, I-118  
  ni-cad, portable, III-57, IV-69  
  ni-cad, temperature-sensing charger, IV-77  
  ni-cad, zapper, II-66  
  power supply and, 14V, III-4A, II-73  
  PUT, III-54  
  regulator, I-117  
  simpli-cad, I-112  
  solar cell, II-71  
  thermally controlled ni-cad, II-68  
  UJT, III-56  
  universal, III-56, III-58  
  versatile design, II-72  
  voltage detector relay, II-76

  wind powered, II-70  
  zapper, simple ni-cad, I-116  
battery monitors, I-106, II-74-79, III-60-67, IV-73-80  
  analyzer, ni-cad batteries, III-64  
  automatic shutoff, battery-powered projects, III-61  
  battery saver, electric vehicles, III-67  
  battery-life extender, 9 V, III-62  
  battery life-extender, disconnect switch, IV-75  
  capacity tester, III-66  
  condition checker, I-108, I-121  
  converter, dc-to-dc +3-to-+5 V, IV-119  
  disconnect switch, life-extender circuit, IV-75  
  dynamic, constant current load fuel cell/battery tester, II-75  
  internal resistance tester, IV-74  
  level indicator, II-124  
  lithium battery, state of charge indicator, II-78  
  low-battery detector, III-63, IV-76  
  low-battery indicator, I-124, II-77, IV-80  
  low-battery protector, III-65  
  low-battery warning/disconnect, III-65  
  protection circuit, ni-cad batteries, III-62  
  sensor, quick-deactivating, III-61  
  splitter, III-66  
  status indicator, II-77  
  step-up switching regulator for 6V, II-78  
  temperature-sensing battery charger, ni-cad batteries, IV-77  
  test circuit, IV-78  
  test circuit, ni-cad batteries, IV-79  
  threshold indicator, I-124  
  undervoltage indicator for, I-123  
  voltage, II-79  
  voltage detector relay in, II-76  
  voltage gauge, automotive battery, IV-47  
  voltage indicator, solid-state, I-120  
  voltage measuring regulator, IV-77  
  voltage monitor, II-79  
  voltage monitor, HTS, I-122  
  voltage-level indicator, IV-80  
battery-life extender, 9 V, III-62, IV-75  
battery-operated equipment  
  ac power control switch, battery-triggered, IV-387  
  automatic shutoff, III-61  
  automotive battery supply,  $\pm 15$  V and 5 V, IV-391  
  automotive cassette-deck power

- circuit, IV-548
- bipolar power supply for, II-475
- buffer amplifier for standard cell, I-351
- fence charger, II-202
- flasher, high powered, II-229
- lantern circuit, I-380
- light, capacitance operated, I-131
- On indicator, IV-217
- undervoltage indicator for, I-123
- warning light, II-320
- Baxandall tone-control audio amplifier, IV-588
- BCD-to-analog converter, I-160
- BCD-to-parallel converter, multiplexed, I-169
- beacon transmitter, III-683
- beep transformer, III-555, III-566
- beepers
  - back-up, automotive circuits, III-49
  - repeater, I-19
- bells
  - electronic, II-33, IV-9
  - electronic phone, I-636
- benchtop power supply, II-472
- bicycle speedometer, IV-271, IV-282
- bilateral current source, III-469
- binary counter, II-135
- biomedical instrumentation differential amplifier, III-282
- bipolar dc-dc converter with no inductor, II-132
- bipolar power supply, II-475
- bipolar voltage reference source, III-774
- biquad audio filter, I-292-293, III-185
- second-order bandpass, III-188
- RC active bandpass, I-285
- bird-chirp sound effect, II-588, III-577
- bistable multivibrator, touch-triggered, I-133
- bit grabber, computer circuits, IV-105
- blinkers (*see* flashers and blinkers)
- blown-fuse alarm, I-10
- boiler control, I-638
- bongos, electronic, II-587
- boosters
  - 12ns, II-97
  - audio, III-35, II-455
  - booster/buffer for reference current boost, IV-425
  - electronic, high-speed, II-96
  - forward-current, III-17
  - LED, I-307
  - power booster, op-amp design, IV-358
  - rf amplifiers, broadcast band booster, IV-487
  - shortwave FET, I-561
- bootstrapping, cable, I-34
- brake lights
  - extra, delayed, III-44
  - flashing, extra, III-51
- brake, PWM speed control/energy recovering, III-380
- breakers
  - 12ns, II-97
  - high-speed electronic, II-96
- breaker power dwell meter, I-102
- breakout box, buffer, II-120
- breath alert alcohol tester, III-359
- breath monitor, III-350
- bridge balance indicator, II-82
- bridge circuits, I-552, II-80-85, III-68-71, IV-81-83
  - ac, II-81
  - ac servo amplifier with, III-387
  - accurate null/variable gain circuit, III-69
  - air-flow sensing thermistor bridge, IV-82
  - auto-zeroing scale, III-69
  - balance indicator, II-82
  - bridge transducer amplifier, III-71
  - crystal-controlled bridge oscillator, IV-127
  - differential amplifier, two op-amp, II-83
  - inductance bridge, IV-83
  - load driver, audio circuits, III-35
  - low power common source amplifier, II-84
  - one-power supply design, IV-83
  - QRP SWR, III-336
  - rectifier, fixed power supplies, IV-398
  - remote sensor loop transmitter, III-70
  - strain gauge signal conditioner, II-85, III-71
  - transducer, amplifier for, II-84
  - Wien bridge, variable oscillator, III-424
  - Wien-bridge filter, III-659
  - Wien-bridge oscillator, III-429
  - Wien-bridge oscillator, low-distortion, thermally stable, III-557
  - Wien-bridge oscillator, low-voltage, III-432
  - Wien-bridge oscillator, single-supply, III-558
- brightness controls, III-308
  - LED, I-250
  - low loss, I-377
- broadband communications
  - ac active rectifier, IV-271
- broadcast-band rf amplifier, II-546, III-264
- buck converter, 5V/0.5A, I-494
- buck/boost converter, III-113
- bucking regulator, high-voltages, III-481
- buffers, IV-88-90
  - ac, single-supply, high-speed, I-127-128
  - ADC input, high-resolution, I-127
  - A/D, 6-bit, high-speed, I-127
  - booster/buffer for reference current boost, IV-425
  - capacitance, stabilized low-input, III-502
  - input/output, for analog multiplexers, III-11
  - inverting bistable buffer, IV-90
  - oscillator buffers, IV-89
  - precision-increasing design, IV-89
  - rf amplifiers, buffer amplifier with modulator, IV-490
  - stable, high-impedance, I-128
  - unity gain, stable, good speed and high-input impedance, II-6
  - video, low-distortion, III-712
  - wideband, high-impedance/low-capacitance I-127
- buffer amplifiers
  - 10x, I-128
  - 100x, I-128
  - ac, single-supply, I-126
  - battery-powered, standard cell, I-351
  - sinewave output, I-126
  - unity-gain, stable design, II-6
- buffered breakout box, II-120
- bug detector, III-365
- bug tracer, III-358
- bull horn, II-453, IV-31
- burglar alarms (*see* alarms)
- burst generators (*see also* function generators; sound generators; waveform generators), II-86-90, III-72-74
  - multi-, square waveform, II-88
  - rf, portable, III-73
  - single timer IC square wave, II-89
  - single-tone, II-87
  - strobe-tone, I-725, II-90
  - tone, II-90
  - tone burst, European repeaters, III-74
- burst power control, III-362
- bus interface, eight bit uP, II-114
- Butler oscillators
  - aperiodic, I-196
  - common base, I-191
  - emitter follower, II-190-191, II-194
- Butterworth filter, high-pass, fourth-order, I-280
- buzzers
  - door buzzer, IV-8

buzzers (*cont.*)

- continuous tone 2kHz, I-11
- gated 2kHz, I-12

## C

- cable bootstrapping, I-34
- cable tester, III-539
- calibrated circuit, DVM auto, I-714
- calibrated tachometer, III-598
- calibration standard, precision, I-406
- calibrators
  - crystal, 100 kHz, I-185
  - electrolytic-capacitor reforming circuit, IV-276
  - ESR measurer, IV-279
  - oscilloscope, II-433, III-436
  - portable, I-644
  - square-wave, 5 V, I-423
  - tester, IV-265
  - wave-shaping circuits, high slew rates, IV-650
- cameras (*see* photography-related circuits; television-related circuits; video circuits)
- canceller, central image, III-358
- capacitance buffers
  - low-input, III-498
  - low-input, stabilized, III-502
- capacitance meters, I-400, II-91-94, III-75-77
  - A/D, three-and-a-half digit, III-76
  - capacitance-to-voltage, II-92
  - digital, II-94
- capacitance multiplier, I-416, II-200
- capacitance relay, I-130
- capacitance switched light, I-132
- capacitance-to-pulse width converter, II-126
- capacitance-to-voltage meter, II-92
- capacitor discharge
  - high-voltage generator, III-485
  - ignition system, II-103
- capacity tester, battery, III-66
- car port, automatic light controller, II-308
- cars (*see* automotive circuits)
- carrier-current circuits, III-78-82, IV-91-93
  - AM receiver, III-81
  - audio transmitter, III-79
  - data receiver, IV-93
  - data transmitter, IV-92
  - FM receiver, III-80
  - intercom, I-146
  - power-line modem, III-82
  - receiver, I-143
  - receiver, single transistor, I-145
  - receiver, IC, I-146
  - remote control, I-146
  - transmitter, I-144
  - transmitter, integrated circuit, I-145
- carrier-operated relay (COR), IV-461
- carrier system receiver, I-141
- carrier transmitter with on/off 200kHz line, I-142
- cascaded amplifier, III-13
- cassette bias oscillator, II-426
- cassette interface, telephone, III-618
- cassette-recorders (*see* tape-recorder circuits)
- centigrade thermometer, I-655, II-648, II-662
- central image canceller, III-358
- charge pool power supply, III-469
- charge pumps
  - positive input/negative output, I-418, III-360
  - regulated for fixed power supplies, IV-396
- chargers (*see* battery charger)
- chase circuit, I-326, III-197
- Chebyshev filters (*see also* filter circuits)
  - bandpass, fourth-order, III-191
  - fifth-order multiple feedback low-pass, II-219
  - high-pass, fourth-order, III-191
- chime circuit, low-cost, II-33
- chopper amplifier, I-350, II-7, III-12
- checkers
  - buzz box continuity and coil, I-551
  - car battery condition, I-108
  - crystal, I-178, I-186
  - zener diode, I-406
- chroma demodulator with RGB matrix, III-716
- chug-chug sound generator, III-576
- circuit breakers (*see also* protection circuits)
  - 12ns, II-97
  - ac, III-512
  - high-speed electronic, II-96
  - trip circuit, IV-423
- circuit protection (*see* protection circuits)
- clamp-on-current probe compensator, II-501
- clamp-limiting amplifiers, active, III-15
- clamping circuits
  - video signal, III-726
  - video summing amplifier and, III-710
- class-D power amplifier, III-453
- clippers, II-394, IV-648
  - audio-powered noise, II-396
  - audio clipper/limiter, IV-355
  - zener-design, fast and symmetrical, IV-329
- clock circuits, II-100-102, III-83-85
  - 60Hz clock pulse generator, II-102
  - adjustable TTL, I-614
  - comparator, I-156
  - crystal oscillators, micropower design, IV-122
  - digital, with alarm, III-84
  - gas discharge displays, 12-hour, I-253
  - oscillator/clock generator, III-85
  - phase lock, 20-Mhz to Nubus, III-105
  - run-down clock for games, IV-205
  - sensor touch switch and clock, IV-591
  - single op amp, III-85
  - source, clock source, I-729
  - three-phase from reference, II-101
  - TTL, wide-frequency, III-85
  - Z80 computer, II-121
- clock generators
  - oscillator, I-615, III-85
  - precision, I-193
  - pulse generator, 60 Hz, II-102
- clock radio, I-542
  - AM/FM, I-543
- CMOS circuits
  - 555 astable true rail to rail square wave generator, II-596
  - 9-bit, III-167
  - coupler, optical, III-414
  - crystal oscillator, III-134
  - data acquisition system, II-117
  - flasher, III-199
  - inverter, linear amplifier from, II-11
  - mixer, I-57
  - optical coupler, III-414
  - oscillator, III-429, III-430
  - short-pulse generator, III-523
  - timer, programmable, precision, III-652
  - touch switch, I-137
  - universal logic probe, III-499
- coaxial cable, five-transistor pulse booster, II-191
- Cockcroft-Walton cascaded voltage doubler, IV-635
- code-practice oscillator, I-15, I-20, I-22, II-428-431, IV-373, IV-375, IV-376
- coil drivers, current-limiting, III-173
- coin flipper circuit, III-244
- color amplifier, video, III-724
- color-bar generator, IV-614
- color organ, II-583, II-584
- color video amplifier, I-34
- Colpitts crystal oscillator, I-194, I-572, II-147
  - 1-to-20 MHz, IV-123
  - frequency checker, IV-301

- harmonic, I-189-190
- two-frequency, IV-127
- combination locks
  - electronic, II-196
  - electronic, three-dial, II-195
- commutator, four-channel, II-364
- companders (*see* compressor/expander circuits)
- comparators, I-157, II-103-112, III-86-90
  - demonstration circuit, II-109
  - diode feedback, I-150
  - display and, II-105
  - double-ended limit, I-156, II-105
  - dual limit, I-151
  - four-channel, III-90
  - frequency, II-109
  - frequency-detecting, III-88
  - high-impedance, I-157
  - high-input impedance window comparator, II-108
  - high-low level comparator with one op amp, II-108
  - latch and, III-88
  - LED frequency, II-110
  - limit, II-104, I-156
  - low-power, less than 10uV hysteresis, II-104
  - microvolt, dual limit, III-89
  - microvolt, with hysteresis, III-88
  - monostable using, II-268
  - opposite polarity input voltage, I-155
  - oscillator, tunable signal, I-69
  - power supply overvoltage, glitch detection with, II-107
  - precision, balanced input/variable offset, III-89
  - precision, photodiode, I-360, I-384
  - time-out, I-153
  - TTL-compatible Schmitt trigger, II-111
  - three-input and gate comparator, op-amp design, IV-363
  - variable hysteresis, I-149
  - voltage comparator, IV-659
  - voltage monitor, II-104
  - window, I-152, I-154, II-106, III-87, III-90, III-776-781, IV-656-658
  - with hysteresis, I-157
  - with hysteresis, inverting, I-154
  - with hysteresis, noninverting, I-153
- compass
  - digital design, IV-147
  - Hall-effect, III-258
- compensator, clamp-on-current probe, II-501
- composite amplifier, II-8, III-13
- composite-video signal text adder, III-716
- compressor/expander circuits, III-91-95, IV-94-97
  - amplifier/compressor, low-distortion, IV-24
  - audio, II-44
  - audio compressor/audio-band splitter, IV-95
  - clock circuit, I-156
  - guitar, sound-effect circuit, IV-519
  - hi-fi, II-12, II-13
  - hi-fi, de-emphasis, III-95
  - hi-fi, pre-emphasis, III-93
  - low-voltage, III-92
  - protector circuit, IV-351
  - speech, II-2
  - universal design, IV-96-97
  - variable slope, III-94
- computalarm, I-2
- computer circuits (*see also* interfaces), II-113-122, III-96-108, IV-98-109
  - analog signal attenuator, III-101
  - alarm, I-2
  - ASCII triplex LCD, 8048/IM80C48
    - 8-char/16-seg, II-116
  - bit grabber, IV-105
  - buffered breakout box, II-120
  - bus interface, 8-bit uP, II-114
  - clock phase lock, 20-Mhz-to-Nubus, III-105
  - CMOS data acquisition system, II-117
  - CPU interface, one-shot design, IV-239
  - data separator for floppy disks, II-122
  - deglitcher, IV-109
  - display, eight-digit, III-106
  - dual 8051s execute in lock-step circuit, IV-99
  - EEPROM pulse generator, 5V-powered, III-99
  - eight-channel mux/demux system, II-115
  - eight-digit microprocessor display, III-106
  - flip-flop inverter, spare, III-103
  - high-speed data acquisition system, II-118
  - interface, 680x, 650x, 8080 families, III-98
  - interval timer, programmable, II-678
  - keyboard matrix interface, IV-240
  - line protectors, 3 uP I/O, IV-101
  - logic-level translators, IV-242
  - logic line monitor, III-108
  - long delay line, logic signals, III-107
  - memory/protector power supply monitor, IV-425
  - memory saving power supply for, II-486
- microprocessor selected pulse width control, II-116
- multiple inputs detector, III-102
- one-of-eight channel transmission system, III-100
- oscilloscope digital-levels, IV-108
- power supply watchdog, II-494
- pulse width control, II-116
- printer-error alarm, IV-106
- reset protection, IV-100
- reset switch, child-proof, IV-107
- RGB blue box, III-99
- RS-232 dataselector, automatic, III-97
- RS-232C line-driven CMOS circuits, IV-104
- RS-232-to-CMOS line receiver, III-102
- RS-232C LED circuit, III-103
- short-circuit sensor, remote data lines, IV-102
- signal attenuator, analog, microprocessor-controlled, III-101
- socket debugger, coprocessor, III-104
- speech synthesizer, III-732
- stalled-output detector, IV-109
- switch debouncer, IV-105
- switch debouncer, auto-repeat, IV-106
- triac array driver, II-410
- uninterruptible power supply, II-462
- Vpp generator for EPROMs, II-114
- XOR gate, IV-107
- XOR gate up/down counter, III-105
- Z-80 bus monitor/debugger, IV-103
- Z80 clock, II-121
- contact switch, I-136
- continuity testers, II-533, II-535, III-345, III-538-540, IV-287, IV-289, IV-296
  - audible, adjustable, II-536
  - cable tester, III-539
  - latching design, IV-295
  - PCB, II-342, II-535
- contrast meters, II-447
  - automatic, I-472
- control circuits (*see also* alarms; detectors; indicators; monitors; motor control circuits; sensors), III-378-390
- ac servo amplifier, bridge-type, III-387
- boiler, I-638
- brightness, low-loss, I-377
- fan speed, III-382
- feedback speed, I-447
- floodlamp power, I-373
- fluid level, I-387

- control circuits (*cont.*)  
 full-wave SCR, I-375  
 heater, I-639  
 hi-fi tone, high-Z input, I-676  
 high-power, sensitive contacts for, I-371  
 LED brightness, I-250  
 light-level, I-380  
 light-level, 860 W limited-range low-cost, I-376  
 light-level, brightness, low-loss, I-377  
 liquid level, I-388  
 model train and/or car, I-453, I-455  
 motor controllers (*see* motor control circuits)  
 on/off, I-665  
 phase control, hysteresis-free, I-373  
 power tool torque, I-458  
 sensitive contact, high power, I-371  
 servo system, III-384  
 single-setpoint temperature, I-641  
 speed control (*see* speed controllers)  
 switching, III-383  
 temperature, I-641-643  
 temperature-sensitive heater, I-640  
 three-phase power-factor, II-388  
 tone control (*see* tone controls)  
 voltage-control, pulse generator and, III-524  
 water-level sensing, I-389  
 windshield wiper, I-105
- conversion and converters, I-503, II-123-132, III-109-122, IV-110-120  
 3-5 V regulated output, III-739  
 4-18 MHz, III-114  
 4-to-20-mA current loop, IV-111  
 5V-to-isolated 5V at 20mA, III-474  
 5V/0.5A buck, I-494  
 9-to-5 V converter, IV-119  
 12 V- to 9-, 7.5-, or 6-V, I-508  
 12-to-16 V, III-747  
 +50V feed forward switch mode, I-495  
 +50 V push-pull switched mode, I-494  
 100 MHz, II-130  
 100 V/10.25 A switch mode, I-501  
 ac-to-dc, I-165  
 ac-to-dc, high-impedance precision rectifier, I-164  
 analog-to-digital (*see* analog-to-digital conversion)  
 ATV rf receiver/converter, IV-420  
 MHz, low-noise, IV-496, IV-497  
 BCD-to-analog, I-160  
 BCD-to-parallel, multiplexed, I-169  
 buck/boost, III-113  
 calculator-to-stopwatch, I-153  
 capacitance-to-pulse width, II-126  
 current-to-frequency, IV-113  
 current-to-frequency, wide-range, I-164  
 current-to-voltage, I-162, I-165  
 current-to-voltage, grounded bias and sensor, II-126  
 current-to-voltage, photodiode, II-128  
 dc-dc, 3-25 V, III-744, IV-118  
 dc-to-dc, +3-to- +5 V battery, IV-119  
 dc-to-dc, 1-to-5 V, IV-119  
 dc-to-dc, bipolar, no inductor, II-132  
 dc-to-dc, fixed 3- to 15-V supplies, IV-400  
 dc-to-dc, isolated +15V, III-115  
 dc-to-dc, push-pull, 400 V, 60 W, I-210  
 dc-to-dc, regulating, I-210, I-211, II-125, III-121  
 dc-to-dc, step up-step down, III-118  
 digital-to-analog (*see* digital-to-analog conversion)  
 fixed power supply, III-470  
 flyback, I-211  
 flyback, self oscillating, I-170, II-128  
 flyback, voltage, high-efficiency, III-744  
 frequency, I-159  
 frequency-to-voltage (*see* frequency-to-voltage conversion)  
 high-to-low impedance, I-41  
 intermittent converter, power-saving design, IV-112  
 light intensity-to-frequency, I-167  
 logarithmic, fast-action, I-169  
 low-frequency, III-111  
 ohms-to-volts, I-168  
 oscilloscope, I-471  
 period-to-voltage, IV-115  
 pico-ampere, 70 voltage with gain, I-170  
 PIN photodiode-to-frequency, III-120  
 polarity, I-166  
 positive-to-negative, III-112, III-113  
 peak-to-peak, ac-dc, precision, II-127  
 pulse height-to-width, III-119  
 pulse train-to-sinusoid, III-122  
 pulse width-to-voltage, III-117  
 radio beacon converter, IV-495  
 rectangular-to-triangular waveform, IV-116-117  
 regulated 15-Vout 6-V driven, III-745  
 resistance-to-voltage, I-161-162  
 RGB-composite video signals, III-714  
 RMS-to-dc, II-129, I-167  
 RMS-to-dc, 50-MHz thermal, III-117  
 RGB-to-NTSC, IV-611  
 sawtooth wave converter, IV-114  
 shortwave, III-114  
 simple LF, I-546  
 sine-to-square wave, I-170, IV-120  
 square-to-sine wave, III-118  
 square-to-triangle wave, TTL, II-125  
 temperature-to-frequency, I-168  
 temperature-to-time, III-632-633  
 triangle-to-sine wave, II-127  
 TTL-to-MOS logic, II-125, I-170  
 two-wire to four-wire audio, II-14  
 unipolar-to-dual voltage supply, III-743  
 video, a/d and d/a, IV-610-611  
 video, RGB-to-NTSC, IV-611  
 VLF, I-547  
 VLF, rf converter, IV-497  
 voltage ratio-to-frequency, III-116  
 voltage, III-742-748, III-742  
 voltage, negative voltage, uP-controlled, IV-117  
 voltage, offline, 1.5-W, III-746  
 voltage-to-current, I-166, II-124, III-110, IV-118  
 voltage-to-current, power, I-163  
 voltage-to-current, zero IB error, III-120  
 voltage-to-frequency (*see* voltage-to-frequency conversion)  
 voltage-to-pulse duration, II-124  
 WWV-to-SW rf converter, IV-499  
 coprocessor socket debugger, III-104  
 countdown timer, II-680  
 counters, II-133-139, III-123-130  
 analog circuit, II-137  
 attendance, II-138  
 binary, II-135  
 divide-by-N, CMOS programmable, I-257  
 divide-by- $\pi$ , 1+ GHz, IV-155  
 divide-by-odd-number, IV-153  
 frequency, III-340, III-768, IV-300  
 frequency, 1.2 GHz, III-129  
 frequency, 10-MHz, III-126  
 frequency, 100 MHz, periodic, II-136  
 frequency, low-cost, III-124  
 frequency, preamp, III-128  
 frequency, tachometer and, I-310  
 geiger, I-536-537  
 microfarad counter, IV-275  
 odd-number divider and, III-217  
 preamplifier, oscilloscope, III-438  
 precision frequency, I-253  
 programmable, low-power wide-range, III-126  
 ring, 20 kHz, II-135  
 ring, incandescent lamp, I-301  
 ring, low cost, I-301  
 ring, low-power pulse circuit, IV-437

- ring, SCR, III-195
- ring, variable timing, II-134
- time base, function generators, 1 Hz, IV-201
- universal, 10 MHz, I-255, II-139
- universal, 40-MHz, III-127
- up/down, 8-digit, II-134
- up/down, extreme count freezer, III-125
- up/down, XOR gate, III-105
- couplers
  - linear, ac analog, II-412
  - linear, analog, II-413
  - linear, dc, II-411
  - optical, CMOS design, III-414
  - optical, TTL design, III-416
  - photon, II-412
  - transmitter oscilloscope for CB signals, I-473
- courtesy light delay/extender, I-98, III-42, III-50
- CRO doubler, III-439
- cross-fader, II-312
- cross-hatch generator, color TV, III-724
- crossover networks, II-35
  - 5V, I-518
  - ac/dc lines, electronic, I-515
  - active, I-172
  - active, asymmetrical third order Butterworth, I-173
  - electronic circuit for, II-36
- crowbars, I-516
  - electric, III-510
  - electronic, II-99
  - SCR, II-496
- crystal oscillators (*see also* oscillators),
  - I-180, I-183-185, I-195, I-198, II-140-151, III-131-140, IV-121-128
  - 1-to-20 MHz, TTL design, IV-127
  - 1-to-4 MHz, CMOS design, IV-125
  - 10 MHz, II-141
  - 10-to-150 kHz, IV-125
  - 10-to-80 MHz, IV-125
  - 50-to-150 MHz, IV-126
  - 96 MHz, I-179
  - 150-to-30,000 kHz, IV-126
  - 330 MHz, IV-125
  - aperiodic, parallel-mode, I-196
  - bridge, crystal-controlled, IV-127
  - Butler oscillator, I-182
  - calibrator, 100 kHz, I-185, IV-124
  - ceramic, 10 MHz, varactor tuned, II-141
  - clock, micropower design, IV-122
  - CMOS, I-187, III-134
  - CMOS, 1-to-4 MHz, IV-125
  - Colpitts, II-147
  - Colpitts, 1-to-20 MHz, IV-123
  - Colpitts, frequency checker, IV-301
  - Colpitts, two-frequency, IV-127
  - crystal-controlled oscillator as, II-147
  - crystal-stabilized IC timer for subharmonic frequencies, II-151
  - crystal tester, I-178, I-186, II-151
  - doubler and, I-184
  - easy start-up, III-132
  - FET, 1 MHz, II-144
  - fundamental-frequency, III-132
  - high-frequency, I-175, II-148
  - high-frequency signal generator as, II-150
  - IC-compatible, II-145
  - LO for SSB transmitter controlled by, II-142
  - low-frequency, I-184, II-146
  - low-frequency, 10 kHz to 150 kHz, II-146
  - low-noise, II-145
  - OF-1 HI oscillator, international, I-197
  - OF-1 LO oscillator, international, I-189
  - overtone, I-176, I-180, I-183, II-146
  - overtone, 100 MHz, IV-124
  - marker generator, III-138
  - mercury cell crystal-controlled oscillator as, II-149
  - overtone, I-176, I-177, I-180, I-186, III-146
  - Pierce, II-144
  - Pierce, 1-MHz, III-134
  - Pierce, JFET, I-198
  - Pierce, low-frequency, III-133
  - quartz, two-gate, III-136
  - reflection oscillator, crystal-controlled, III-136
  - Schmitt trigger, I-181
  - signal source controlled by, II-143
  - sine-wave oscillator, I-198
  - stable low frequency, I-198
  - standard, 1 MHz, I-197
  - temperature-compensated, I-187, III-137
  - temperature-compensated, 5V driven, low-power, II-142
  - third-overtone, I-186, IV-123
  - time base, economical design, IV-128
  - TTL design, I-179
  - TTL design, 1-to-20 MHz, IV-127
  - TTL-compatible, I-197
  - transistorized, I-188
  - tube-type, I-192
  - VHF, 20-MHz, III-138
  - VHF, 50-MHz, III-140
  - VHF, 100-MHz, III-139
  - voltage-controlled, III-135, IV-124
- crystal switching, overtone oscillator with, I-183
- current analyzer, auto battery, I-104
- current booster, I-30, I-35
- current collector head amplifier, II-11, II-295
- current loop, 4-to-20-mA converter, IV-111
- current meters and monitors, I-203, II-152-157, III-338
  - ac current indicator, IV-290
  - current sensing in supply rails, II-153
  - electrometer amplifier with overload protection, II-155
  - Hall-effect circuit, III-255
  - Hall-sensor, IV-284
  - high-gain current sensor, IV-291
  - pico ammeter, II-154, II-157
  - pico ammeter, guarded input, II-156
  - range ammeter, six-decade, II-153, II-156
- current readout, rf, I-22
- current sensing, supply rails, II-153
- current sink, I-206
  - 1 mA for fixed power supplies, IV-402
  - voltage-controlled, IV-629
- current sources, I-205, I-697
  - 0-to-200-nA, IV-327
  - bilateral, III-469, I-694-695
  - bipolar, inverting, I-697
  - bipolar, noninverting, I-695
  - constant, I-697, III-472
  - fixed power supplies, bootstrapped amp, IV-406
  - fixed power supplies, differential-input, fast-acting, IV-405
  - low-current source, fixed power supplies, IV-399
  - precision, I-205
  - precision, 1mA to 1mA, I-206
  - regulator, variable power supply, III-490
  - variable power supplies, voltage-programmable, IV-420
  - voltage-controlled, grounded source/load, III-468
- current-loop controller, SCR design, IV-387
- current-shunt amplifiers, III-21
- current-to-frequency converter, IV-113
  - wide range, I-164
- current-to-voltage amplifier, high-speed, I-35
- current-to-voltage converter, I-162, I-165
  - grounded bias and sensor in, II-126
  - photodiode, II-128
- curve tracer
  - diodes, IV-274
  - FET, I-397
- CW radio communications

CW radio communications (*cont.*)

filter, razor sharp, II-219  
keying circuits, IV-244  
offset indicator, IV-213  
SSB/CW product detector, IV-139  
transceiver, 5 W, 80-meter, IV-602  
transmitter, 1-W, III-678  
transmitter, 40-M, III-684  
transmitter, 902-MHz, III-686  
transmitter, HF low-power, IV-601  
transmitter, QRP, III-690  
cyclic A/D converter, II-30

## D

darkroom equipment (*see* photography-related circuits)  
Darlington regulator, variable power supplies, IV-421  
data-manipulation circuits, IV-129-133  
acquisition circuits, CMOS system, II-117  
acquisition circuits, four-channel, I-421  
acquisition circuits, high-speed system, II-118  
analog-signal transmission isolator, IV-133  
data-acquisition systems, IV-131  
link, IR type, I-341  
prescaler, low-frequency, IV-132  
read-type circuit, 5 MHz, phase-encoded, II-365  
receiver/message demuxer, three-wire, IV-130  
selector, RS-232, III-97  
separator, floppy disk, II-122  
data transmission  
receiver, carrier-current circuit design, IV-93  
transmitter, carrier-current circuit design, IV-92  
dc adapter/transceiver, hand-held, III-461  
dc generators, high-voltage, III-481  
dc restorer, video, III-723  
dc servo drive, bipolar control input, II-385  
dc static switch, II-367  
dc-to-dc converters, IV-118  
1-to-5 V, IV-119  
3-25 V, III-744  
bipolar, no inductor, II-132  
dual output  $\pm$  12-15 V, III-746  
fixed power supplies, 3-to-15 V, IV-400  
isolated +15 V, III-115  
push-pull, 400 V, 60 W, I-210

regulated, I-210, I-211, II-125, III-121  
step up/step down, III-118  
dc-to-dc SMPS variable power supply, II-480  
debouncer, III-592, IV-105  
auto-repeat, IV-106  
flip-flop, IV-108  
debugger, coprocessor sockets, III-104  
decibel level detector, audio, with meter driver, III-154  
decoders, II-162, III-141-145  
10.8 MHz FSK, I-214  
24-percent bandwidth tone, I-215  
direction detector, III-144  
dual-tone, I-215  
encoder and, III-144  
frequency division multiplex stereo, II-169  
PAL/NTSC, with RGB input, III-717  
radio control receiver, I-574  
SCA, I-214, III-166, III-170  
second-audio program adapter, III-142  
sound-activated, III-145  
stereo TV, II-167  
time division multiplex stereo, II-168  
tone alert, I-213  
tone dial, I-631  
tone dial sequence, I-630  
tone, I-231, III-143  
tone, dual time constant, II-166  
tone, relay output, I-213  
video, NTSC-to-RGB, IV-613  
weather-alert detector/decoder, IV-140  
deglitcher circuit, computer circuits, IV-109  
delay circuits/ delay units, III-146-148  
adjustable, III-148  
door chimes, I-218  
headlights, I-107, II-59  
leading-edge, III-147  
long duration time, I-217, I-220  
precision solid state, I-664  
pulse, dual-edge trigger, III-147  
time delay, constant-current charging, II-668  
time delay, simple design, I-668, II-220  
windshield wiper delay, I-97, II-55  
delay line, analog, echo and reverb effects, IV-21  
delayed pulse generator, II-509  
delay relay, ultra-precise long time, II-211  
demodulators, II-158-160, III-149-150  
5V FM, I-233

12V FM, I-233  
565 SCA, III-150  
AM, II-160  
chroma, with RGB matrix, III-716  
FM, II-161  
FM, narrow-band, carrier detect, II-159  
linear variable differential transformer driver, I-403  
LVDT circuit, III-323-324, III-323  
LVDT driver, II-337  
stereo, II-159  
telemetry, I-229  
demonstration comparator circuit, II-109  
demultiplexer, III-394  
descramblers, II-162  
gated pulse, II-165  
outband, II-164  
sine wave, II-163  
derived center-channel stereo system, IV-23  
detect-and-hold circuit, peak, I-585  
detection switch, adjustable light, I-362  
detectors (*see also* alarms; control circuits; indicators; monitors; sensors), II-171-178, III-151-162, IV-134-145  
air flow, I-235, II-240-242  
air motion, I-222, III-364  
air-pressure change, IV-144  
amplifier, four quadrant photoconductive, I-359  
angle of rotation, II-283  
bug, III-365  
controller circuit, IV-142  
decibel level, audio, with meter driver, III-154  
direction detector, thermally operated, IV-135  
double-ended limit, I-230, I-233  
duty-cycle, IV-144  
edge, III-157, I-226  
electrostatic, III-337  
envelope detector, III-155  
envelope detector, AM signals, IV-142  
envelope detector, low-level diodes, IV-141  
flame, III-313  
flow, III-202-203  
flow, low-rate thermal, III-203  
fluid and moisture, II-243, II-248, III-204-210, IV-184-191  
frequency limit, II-177  
frequency window, III-777  
frequency, digital, III-158  
frequency-boundary, III-156

gas, II-278, III-246-253  
 gas and smoke, I-332  
 gas and vapor, II-279  
 ground-fault Hall detector, IV-208-209  
 high-frequency peak, II-175  
 high-speed peak, I-232  
 IC product detector, IV-143  
 infrared, II-289, III-276, IV-224  
 IR, long-range objects, III-273  
 level, II-174  
 level, with hysteresis, I-235  
 lie detector, IV-206  
 light detector, IV-369  
 light interruption, I-364  
 light level, III-316  
 light level, level drop, III-313  
 line-current, optically coupled, III-414  
 liquid level, I-388, I-390  
 low-level video, video IF amplifier, I-687-689  
 low-line loading ring, I-634  
 low-voltage, I-224  
 magnet, permanent-magnet detector, IV-281  
 magnetic transducer, I-233  
 MC1330/MC1352 television IF amplifier, I-688  
 metal, II-350-352, IV-137  
 missing pulse, I-232, III-159  
 moisture, I-442  
 motion, IV-341-346  
 motion, UHF, III-516  
 multiple-input, computer circuit, III-102  
 negative peak, I-234  
 nuclear particle, I-537  
 null, I-148, III-162  
 peak program, III-771  
 peak, II-174, II-175, IV-138, IV-143  
 peak, analog, with digital hold, III-153  
 peak, digital, III-160  
 peak, high-bandwidth, III-161  
 peak, low-drift, III-156  
 peak, negative, I-225  
 peak, op amp, IV-145  
 peak, positive, III-169  
 peak, wide-bandwidth, III-162  
 peak, wide-range, III-152  
 peak voltage, precision, I-226  
 people-detector, infrared-activated, IV-225  
 pH level, probe and, III-501  
 phase, III-440-442  
 phase, 10-bit accuracy, II-176  
 photodiode level, precision, I-365  
 positive peak, I-225, I-235  
 power loss, II-175  
 product, I-223, I-861  
 proximity, I-344, II-135, II-136, IV-341-346  
 pulse coincidence, II-178  
 pulse sequence, II-172  
 pulse-width, out-of-bounds, III-158  
 radar (*see* radar detector)  
 radiation (*see* radiation detector)  
 resistance ratio, II-342  
 rf, II-500, IV-139  
 rf detector probe, IV-433  
 Schmitt trigger, III-153  
 smoke, II-278, III-246-253, IV-140  
 smoke, ionization chamber, I-332-333  
 smoke, operated ionization type, I-596  
 smoke, photoelectric, I-595  
 speech activity on phone lines, II-617, III-615  
 SSB/CW product detectors, IV-139  
 stalled computer-output detector, IV-109  
 static detector, IV-276  
 telephone ring, III-619, IV-564  
 telephone ring, optically interfaced, III-611  
 threshold, precision, III-157  
 tone, 500-Hz, III-154  
 toxic gas, II-280  
 true rms, I-228  
 TV sound IF/FM IF amplifier with quadrature, I-690  
 two-sheets in printer detector, IV-136  
 ultra-low drift peak, I-227  
 undervoltage detector, IV-138  
 video, low-level video IF amplifier, I-687-689  
 voltage level, I-8, II-172  
 weather-alert decoder, IV-140  
 window, I-235, III-776-781, IV-658  
 zero crossing, I-732, I-733, II-173  
 zero crossing, with temperature sensor, I-733  
 deviation meter, IV-303  
 dial pulse indicator, telephone, III-613  
 dialers, telephone  
   pulse-dialing telephone, III-610  
   pulse/tone, single-chip, III-603  
   telephone-line powered repertory, I-633  
   tone-dialing telephone, III-607  
 dice, electronic, I-325, III-245, IV-207  
 differential amplifiers, I-38, III-14  
   high-impedance, I-27, I-354  
   high-input high-impedance, II-19  
   instrumentation, I-347, III-283  
   instrumentation, biomedical, III-282  
   programmable gain, III-507  
   two op amp bridge type, II-83  
 differential analog switch, I-622  
 differential capacitance measurement circuit, II-665  
 differential hold, I-589, II-365  
 differential multiplexers  
   demultiplexer/, I-425  
   wide band, I-428  
 differential thermometer, II-661, III-638  
 differential voltage or current alarm, II-3  
 differentiators, I-423  
   negative-edge, I-419  
   positive-edge, I-420  
 digital-capacitance meter, II-94  
 digital-IC, tone probe for testing, II-504  
 digital-frequency meter, III-344  
 digital-logic probe, III-497  
 digital audio tape (DAT)  
   dithering circuit, IV-23  
 digital multimeter (DMM)  
   high-resistance-measuring, IV-291  
 digital oscillator, resistance controlled, II-426  
 digital transmission isolator, II-414  
 digital voltmeters (DVM)  
   3.5-digit, common anode display, I-713  
   3.5-digit, full-scale, four-decade, III-761  
   3.75-digit, I-711  
   4.5-digit, III-760  
   4.5-digit, LCD display, I-717  
   auto-calibrate circuit, I-714  
   automatic nulling, I-712  
   interface and temperature sensor, II-647  
 digital-to-analog converters, I-241, II-179-181, III-163-169  
 0-to -5V output, resistor terminated, I-239  
 3-digit, BCD, I-239  
 8-bit, I-240-241  
 8-bit, high-speed, I-240  
 8-bit, output current to voltage, I-243  
 8-bit to 12-bit, two, II-180  
 9-bit, CMOS, III-167  
 10-bit, I-238  
 10-bit, 4-quad, offset binary coding, multiplying, I-241  
 +10V full scale bipolar, I-242  
 +10V full scale unipolar, I-244  
 12-bit, binary two's complement, III-166

- digital-to-analog converters (*cont.*)
  - 12-bit, precision, I-242
  - 12-bit, variable step size, II-181
  - 14-bit binary, I-237
  - 16-bit binary, I-243
  - fast voltage output, I-238
  - high-speed voltage output, I-244
  - multiplying, III-168
  - output amplifier, four-channel, III-165
  - video converter, IV-610-611
- digitizer, tilt meter, III-644-646
- dimmers (*see* lights/light-activated and controlled circuits)
- diode emitter driver, pulsed infrared, II-292
- diode tester, II-343, III-402
  - go/no-go, I-401
  - zener diodes, I-406
- diode-matching circuit, IV-280
- dip meters, I-247, II-182-183
  - basic grid, I-247
  - dual gate IGFET, I-246
  - little dipper, II-183
  - varicap tuned FET, I-246
- diplexer/mixer, IV-335
- direction detector, thermally operated, IV-135
- direction detector decoder, III-144
- direction finders, IV-146-149
  - compass, digital design, IV-147
  - radio-signal direction finder, IV-148-149
- direction-of-rotation circuit, III-335
- directional-signals monitor, auto, III-48
- disco strobe light, II-610
- discrete current booster, II-30
- discrete sequence oscillator, III-421
- discriminators
  - multiple-aperture, window, III-781
  - pulse amplitude, III-356
  - pulse width, II-227
  - window, III-776-781
- display circuits, II-184-188, III-170-171
  - $3^{1/2}$  digit DVM common anode, II-713
  - 60 dB dot mode, II-252
  - audio, LED bar peak program meter, II-254
  - bar-graph indicator, ac signals, II-187
  - brightness control, III-316
  - comparator and, II-105
  - exclamation point, II-254
  - expanded scale meter, dot or bar, II-186
  - LED bar graph driver, II-188
  - LED matrix, two-variable, III-171
  - oscilloscope, eight-channel voltage, III-435
  - dissolver, lamp, solid-state, III-304
- distribution circuits, II-35
- distribution amplifiers
  - audio, I-39, II-39
  - signal, I-39
- dividers, IV-150-156
  - 1 + GHz divide-by- $n$  counter, IV-155
  - 7490-divided-by- $n$  circuits, IV-154
  - binary chain, I-258
  - counter, divide-by-odd-number, IV-153
  - divide-by-2-or-3 circuit, IV-154
  - divide-by- $n + 1/2$  circuit, IV-156
  - frequency, I-258, II-254, III-213-218
  - frequency divider, clock input, IV-151
  - frequency, decade, I-259
  - frequency, divide-by- $1^{1/2}$ , III-216
  - frequency, low frequency, II-253
  - frequency divider, programmable, IV-152-153
  - mathematical, one trim, III-326
  - odd-number counter and, III-217
  - pulse, non-integer programmable, II-511, III-226
- Dolby noise reduction circuits, III-399
- decode mode, III-401
- encode mode, III-400
- door bells/chimes, I-218, I-443, IV-8
  - buzzer, two-door, IV-10
  - musical-tone, IV-522
  - rain alarm, I-443
  - single-chip design, IV-524
  - sliding tone, II-34
- door-open alarm, II-284, III-46
  - Hall-effect circuit, III-256
- door opener, III-366
- dot-expanded scale meter, II-186
- double-sideband suppressed-carrier modulator, III-377
- double-sideband suppressed-carrier rf, II-366
- doublers
  - 0 to 1MHz, II-252
  - 150 to 300 MHz, I-314
  - audio-frequency doubler, IV-16-17
  - broadband frequency, I-313
  - CRO, oscilloscope, III-439
  - crystal oscillator, I-184
  - frequency, I-313, III-215
  - frequency, digital, III-216
  - frequency, GASFET design, IV-324
  - frequency, single-chip, III-218
  - low-frequency, I-314
  - voltage, III-459
  - voltage, triac-controlled, III-468
- downbeat-emphasized metronome, III-353-354
- drivers and drive circuits, I-260, II-189
  - 193, III-172-175, IV-157-160
  - 50 ohm, I-262
- bar-graph driver, transistorized, IV-213
- BIFET cable, I-264
- bridge loads, audio circuits, III-35
- capacitive load, I-263
- coaxial cable, I-266, I-560
- coaxial cable, five-transistor pulse boost, II-191
- coil, current-limiting, III-173
- CRT deflection yoke, I-265
- demodulator, linear variable differential transformer, I-403
- fiber optic, 50-Mb/s, III-178
- flash slave, I-483
- glow plug, II-52
- high-impedance meter, I-265
- instrumentation meter, II-296
- lamp, I-380
  - lamp, flip-flop independent, IV-160
  - lamp, low-frequency flasher/relay, I-300
  - lamp, optically coupled, III-413
  - lamp, short-circuit proof, II-310
- laser diode, high-speed, I-263
- LED, bar graph, II-188
- LED, emitter/follower, IV-159
- line signals, 600-ohm balanced, II-192
- line, I-262
- line, 50-ohm transmission, II-192
- line, full rail excursions in, II-190
- line-synchronized, III-174
- load, timing threshold, III-648
- LVDT demodulator and, II-337, III-323-324
- meter-driver rf amplifier, 1-MHz, III-545
- microprocessor triac array, II-410
- motor drivers (*see* motor control, drivers)
- multiplexer, high-speed line, I-264
- neon lamp, I-379
- op amp power driver, IV-158-159
- optoisolated, high-voltage, III-482
- power driver, op amp, IV-158-159
- pulsed infrared diode emitter, II-292
- relay, I-264
  - relay, delay and controls closure time, II-530
  - relay, with strobe, I-266
- RS-232C, low-power, III-175
- shift register, I-418
- solenoid, I-265, III-571-573
- SSB, low distortion 1.6 to 30MH, II-538
- stepping motor, II-376
- totem-pole, with bootstrapping, III-175
- two-phase motor, I-456

VCO driver, op-amp design, IV-362  
 drop-voltage recovery for long-line systems, IV-328  
 drum sound effect, II-591  
 dual-tone decoding, II-620  
 dual-tracking regulator, III-462  
 duplex line amplifier, III-616  
 duty-cycle detector, IV-144  
 duty-cycle meter, IV-275  
 duty-cycle monitor, III-329  
 duty-cycle multivibrator, 50-percent, III-584  
 duty-cycle oscillators  
 50-percent, III-426  
 variable, fixed-frequency, III-422  
 dwell meters  
 breaker point, I-102  
 digital, III-45

## E

eavesdropper, telephone, wireless, III-620  
 echo effect, analog delay line, IV-21  
 edge detector, I-266, III-157  
 EEPROM pulse generator, 5V-powered, III-99  
 EKG simulator, three-chip, III-350  
 elapsed-time timer, II-680  
 electric-fence charger, II-202  
 electric-vehicle battery saver, III-67  
 electrolytic-capacitor reforming circuit, IV-276  
 electrometer, IV-277  
 electrometer amplifier, overload protected, II-155  
 electronic dice, IV-207  
 electronic locks, II-194-197, IV-161-163  
 combination, I-583, II-196  
 digital entry lock, IV-162  
 keyless design, IV-163  
 three-dial combination, II-195  
 electronic music, III-360  
 electronic roulette, II-276, IV-205  
 electronic ship siren, II-576  
 electronic switch, push on/off, II-359  
 electronic theremin, II-655  
 electronic thermometer, II-660  
 electronic wake-up call, II-324  
 electrostatic detector, III-337  
 emergency lantern/flasher, I-308  
 emergency light, I-378, IV-250  
 emissions analyzer, automotive exhaust, II-51  
 emulators, II-198-200  
 capacitance multiplier, II-200  
 JFET ac coupled integrator, II-200  
 resistor multiplier, II-199  
 simulated inductor, II-199

encoders  
 decoder and, III-14  
 telephone handset tone dial, I-634, III-613  
 tone, I-67, I-629  
 tone, two-wire, II-364  
 engine tachometer, I-94  
 enlarger timer, II-446, III-445  
 envelope detectors, III-155  
 AM signals, IV-142  
 low-level diodes, IV-141  
 envelope generator/modulator, musical, IV-22  
 EPROM, Vpp generator for, II-114  
 equalizers, I-671, IV-18  
 ten-band, graphic, active filter in, II-684  
 ten-band, octave, III-658  
 equipment-on reminder, I-121  
 exhaust emissions analyzer, II-51  
 expanded-scale meters  
 analog, III-774  
 dot or bar, II-186  
 expander circuits (*see* compressor/expander circuits)  
 extended-play circuit, tape-recorders, III-600  
 extractor, square-wave pulse, III-584

## F

555 timer  
 astable, low duty cycle, II-267  
 beep transformer, III-566  
 integrator to multiply, II-669  
 RC audio oscillator from, II-567  
 square wave generator using, II-595  
 fader, audio fader, IV-17  
 fail-safe semiconductor alarm, III-6  
 fans  
 infrared heat-controlled fan, IV-226  
 speed controller, automatic, III-382  
 Fahrenheit thermometer, I-658  
 fault monitor, single-supply, III-495  
 fax/telephone switch, remote-controlled, IV-552-553  
 feedback oscillator, I-67  
 fence charger, II-201-203  
 battery-powered, II-202  
 electric, II-202  
 solid-state, II-203  
 FET circuits  
 dual-trace scope switch, II-432  
 input amplifier, II-7  
 probe, III-501  
 voltmeter, III-765, III-770  
 fiber optics, II-204-207, III-176-181  
 driver, LED, 50-Mb/s, III-178  
 interface for, II-207  
 link, I-268, I-269, I-270, III-179

motor control, dc, II-206  
 receiver, 10 MHz, II-205  
 receiver, 50-Mb/s, III-181  
 receiver, digital, III-178  
 receiver, high-sensitivity, 30nW, I-270  
 receiver, low-cost, 100-M baud rate, III-180  
 receiver, low-sensitivity, 300nW, I-271  
 receiver, very-high sensitivity, low speed, 3nW, I-269  
 repeater, I-270  
 speed control, II-206  
 transmitter, III-177  
 field disturbance sensor/alarm, II-507  
 field-strength meters, II-208-212, III-182-183, IV-164-166  
 1.5-150 MHz, I-275  
 adjustable sensitivity indicator, I-274  
 high-sensitivity, II-211  
 LF or HF, II-212  
 microwave, low-cost, I-273  
 rf sniffer, II-210  
 sensitive, I-274, III-183  
 signal-strength meter, IV-166  
 transmission indicator, II-211  
 tuned, I-276  
 UHF fields, IV-165  
 untuned, I-276  
 filter circuits, II-213-224, III-184-192, IV-167-177  
 active (*see* active filters)  
 antialiasing/sync-compensation, IV-173  
 audio, biquad, III-185  
 audio, tunable, IV-169  
 bandpass (*see* bandpass filters)  
 band-reject, active, II-401  
 biquad, I-292-293  
 biquad, audio, III-185  
 biquad, RC active bandpass, I-285  
 bridge filter, twin-T, programmable, II-221  
 Butterworth, high-pass, fourth-order, I-280  
 Chebyshev (*see* Chebyshev filters)  
 CW, razor-sharp, II-219  
 full wave rectifier and averaging, I-229  
 high-pass (*see* high-pass filters)  
 low-pass (*see* low-pass filters)  
 networks of, I-291  
 noise, dynamic, III-190  
 noisy signals, III-188  
 notch (*see* notch filters)  
 programmable, twin-T bridge, II-221  
 rejection, I-283  
 ripple suppressor, IV-175

- filter circuits (*cont.*)
  - rumble, III-192, IV-175
  - rumble, LM387 in, I-297
  - rumble filter, turntable, IV-170
  - rumble/scratch, III-660
  - Sallen-Key, 500 Hz bandpass, I-291
  - Sallen-key, low-pass, active, IV-177
  - Sallen-Key, low-pass, equal component, I-292
  - Sallen-Key, low-pass, second order, I-289
  - scratch, III-189, IV-175
  - scratch, LM287 in, I-297
  - speech, bandpass, 300 Hz 3kHz, I-295
  - speech filter, second-order, 300-to-3,400 Hz, IV-174
  - speech filter, two-section, 300-to-3,000 Hz, IV-174
  - state-variable, II-215
  - state-variable, multiple outputs, III-190
  - state-variable, second-order, 1kHz, Q/10, I-293
  - state-variable, universal, I-290
  - turbo, glitch free, III-186
  - twin-T bridge filter, II-221
  - Wien-bridge, III-659
  - voltage-controlled, III-187
  - voltage-controlled, 1,000:1 tuning, IV-176
- fixed power supplies, III-457-477, IV-390-408
  - 12-VDC battery-operated 120-VAC, III-464
  - +24 V, 1.5 A supply from +12 V source, IV-401
  - 15 V isolated to 2,500 V supply, IV-407
  - audio amplifier supply,  $\pm 35$  V ac, IV-398
  - audio amplifier supply,  $\pm 35$  V, 5 A, mobile, IV-407
  - automotive battery supply,  $\pm 15$  V and 5 V, IV-391
  - auxiliary supply, IV-394
  - bias/reference applications, auxiliary negative dc supply, IV-404
  - bilateral current source, III-469
  - bridge rectifier, IV-398
  - charge pool, III-469
  - charge pump, regulated, IV-396
  - constant-current source, safe, III-472
  - converter, III-470
  - converter, 5V-to-isolated 5V at 20mA, III-474
  - converter, ac-to-dc, IV-395
  - converter, dc-to-dc, 3-to-15 V, IV-400
  - current sink, 1 mA, IV-402
  - current source, bootstrapped amp, IV-406
  - current source, differential-input, fast-acting, IV-405
  - dc adapter/transceiver, hand-held, III-461
  - dual-tracking regulator, III-462
  - GASFET power supply, IV-405
  - general-purpose, III-465
  - inverter, 12 V input, IV-395
  - isolated feedback, III-460
  - LCD display power supply, IV-392, IV-403
  - linear regulator, low cost, low dropout, III-459
  - low-current source, IV-399
  - low-power inverter, III-466
  - negative rail, GET, with CMOS gates, IV-408
  - negative supply from +12 V source, IV-401
  - negative voltage from positive supply, IV-397
  - output stabilizer, IV-393
  - portable-radio 3 V power supply, IV-397
  - positive and negative voltage power supplies, IV-402
  - pnp regulator, zener increases voltage output, II-484
  - programmable, III-467
  - rectifier, bridge rectifier, IV-398
  - rectifier, low forward-drop, III-471
  - regulated 1 A, 12 V, IV-401
  - regulated +15V 1-A, III-462
  - regulated -15V 1-A, III-463
  - regulator, 15V slow turn-on, III-477
  - regulator, positive with PNP boost, III-471
  - regulator, positive, with NPN/PNP boost, III-475
  - regulator, switching, 3-A, III-472
  - regulator, switching, high-current inductorless, III-476
  - ripple suppressor, IV-396
  - RTTY machine current supply, IV-400
  - stabilizer, CMOS diode network, IV-406
  - switching, III-458
  - switching, 5- and  $\pm 12$  V, ac-powered, IV-404
  - switching, 50-W off-line, III-473
  - switching, positive and negative voltage, IV-403
  - switching regulator, 3 A, IV-408
  - three-rail, III-466
  - uninterruptible +5V, III-477
  - voltage doubler, III-459
  - voltage doubler, triac-controlled, III-468
  - voltage regulator, 10V, high stability, III-468
  - voltage regulator, 5-V low-dropout, III-461
  - voltage regulator, ac, III-477
  - voltage regulator, negative, III-474
  - voltage-controlled current source/grounded source/load, III-468
  - fixed-frequency generator, III-231
  - flame ignitor, III-362
  - flame monitor, III-313
  - flash/flashbulb circuits (*see* photography-related circuits)
  - flashers and blinkers (*see also* photography-related circuits), I-304, II-225, III-193-210, IV-178-183
    - 1.5 V, minimum power, I-308
    - 1 kW flip-flop, II-234
    - 1A lamp, I-306
    - 2 kW, photoelectric control in, II-232
    - 3V, I-306
    - ac, III-196
    - alternating, I-307, II-227
    - astable multivibrator, III-196
    - auto, I-299
    - automatic safety, I-302
    - automotive turn signal, sequential, I-109
    - bar display with alarm, I-252
    - barricade, I-299
    - boat, I-299
    - CMOS, III-199
    - dc, adjustable on/off timer, I-305
    - dual LED CMOS, I-302
    - electronic, II-228
    - emergency lantern, I-308
    - fast-action, I-306
    - flash light, 60-W, III-200
    - flicker light, IV-183
    - flip-flop, I-299
    - four-parallel LED, I-307
    - high efficiency parallel circuit, I-308
    - high-voltage, safe, I-307
    - high-power battery operated, II-229
    - incandescent bulb, III-198, I-306
    - LED, IV-181
    - LED, alternating, III-198, III-200
    - LED, control circuit, IV-183
    - LED, multivibrator design, IV-182
    - LED, PUT used in, II-239
    - LED, ring-around, III-194
    - LED flasher, sequential, reversible-direction, IV-182
    - LED, three-year, III-194
    - LED, UJT used in, II-231
    - low-current consumption, II-231

low-voltage, I-305, II-226  
 miniature transistorized, II-227  
 minimum-component, III-201  
 neon, I-303  
 neon, five-lamp, III-198  
 neon, two-state oscillator, III-200  
 neon, tube, I-304  
 oscillator and, high drive, II-235  
 oscillator and, low frequency, II-234  
 photographic slave-flash trigger, SCR design, IV-380, IV-382  
 photographic time-delay flash trigger, IV-380  
 relay driver, low-frequency lamp, I-300  
 SCR design, II-230, III-197  
 SCR chaser, III-197  
 SCR relaxation, II-230  
 SCR ring counter, III-195  
 sequential, II-233, IV-181  
 sequential, ac, II-238  
 sequencer, pseudorandom simulated, IV-179  
 single-lamp, III-196  
 strobe alarm, IV-180  
 telephone, II-629, IV-558, IV-559, IV-561  
 telephone-message flasher, IV-556  
 transistorized, III-200, I-303  
 transistorized, table of, II-236  
 variable, I-308  
 xenon light, IV-180

**flashlight finder, I-300**

**flip-flops**  
 astable, with starter, II-239  
 debouncer switch, IV-108  
 flasher circuit, 1 kW, use of, II-234  
 inverter, III-103  
 SCR, II-367  
 wave-shaping circuits, S/R, IV-651

**flood alarm, I-390, III-206, IV-188**

**flow detectors, II-240-242, III-202-203**  
 air, II-242  
 low-rate thermal, III-203  
 thermally based anemometer, II-241

**flowmeter, liquid, II-248**

**fluid and moisture detectors, I-388, I-390, I-442, II-243-248, III-204-210, IV-184-191**  
 acid rain monitor, II-245  
 checker, III-209  
 control, I-388, III-206  
 cryogenic fluid-level sensor, I-386  
 dual, III-207  
 flood alarm, III-206, IV-188  
 fluid-level control, III-205  
 full-bathtub indicator, IV-187  
 full-cup detector for the blind, IV-189  
 indicator, II-244

liquid flow meter, II-248  
 liquid-level checker, III-209  
 liquid-level monitor, III-210  
 liquid-level sensor, IV-186  
 liquid-level, dual, III-207  
 moisture detector, IV-188  
 monitor, III-210  
 plant water, II-245, II-248  
 pump controller, single-chip, II-247  
 rain alarm, IV-189  
 rain warning bleeper, II-244  
 sensor and control, II-246  
 soil moisture, III-208  
 temperature monitor, II-643, III-206  
 water-leak alarm, IV-190  
 water-level, III-206, IV-186, IV-191  
 water-level, indicator, II-244  
 water-level, sensing and control, II-246, IV-190  
 windshield-washer level, I-107

**fluid-level controller, I-387, III-205**

**fluorescent display, vacuum, II-185**

**fluorescent lamps**  
 high-voltage power supplies, cold-cathode design, IV-411  
 inverter, 8-W, III-306

**flyback converters, I-211**  
 self oscillating, I-170, II-128, III-748  
 voltage, high-efficiency, III-744

**flyback regulator, off-line, II-481**

**FM transmissions**  
 5 V, I-233  
 12 V, I-233  
 clock radio, AM/FM, I-543  
 demodulators, I-544, II-161  
 IF amplifier with quadrature detector, TV sound IF, I-690  
 generators, low-frequency, III-228  
 radio, I-545  
 receivers, carrier-current circuit, III-80  
 receivers, MPX/SCA receiver, III-530  
 receivers, narrow-band, III-532  
 receivers optical receiver/transmitter, 50 kHz, I-361  
 receivers, zero center indicator, I-338  
 snooper, III-680  
 speakers, remote, carrier-current system, I-140  
 squelch circuit for AM, I-547  
 stereo demodulation system, I-544  
 transmitters, I-681  
 transmitters, infrared, voice-modulated pulse, IV-228  
 transmitters, multiplex, III-688  
 transmitters, one-transistor, III-687  
 transmitters, optical, 50 kHz center frequency, II-417  
 transmitters, optical receiver/transmitter, 50 kHz, I-361  
 transmitters, optical (PRM), I-367  
 transmitters, voice, III-678  
 tuner, I-231, III-529  
 wireless microphone, III-682, III-685, III-691

**FM/AM clock radio, I-543**

**fog-light controller, automotive, IV-59**

**foldback current, HV regulator limiting, II-478**

**followers, III-211-212**  
 inverting, high-frequency, III-212  
 noninverting, high-frequency, III-212  
 source, photodiode, III-419  
 unity gain, I-27  
 voltage, III-212

**forward-current booster, III-17**

**free-running multivibrators**  
 100 kHz, I-465  
 programmable-frequency, III-235

**free-running oscillators, I-531**  
 square wave, I-615

**freezer, voltage, III-763**

**freezer-meltdown alarm, I-13**

**frequency comparators, II-109**  
 LED, II-110

**frequency control, telephone, II-623**

**frequency converter, I-159**

**frequency counters, III-340, III-768, IV-300**  
 1.2 GHz, III-129  
 10-MHz, III-126  
 100 MHz, period and, II-136  
 low-cost, III-124  
 preamp, III-128  
 precision, I-253  
 tachometer and, I-310

**frequency detectors, II-177, III-158**  
 boundary detector, III-156  
 comparator, III-88

**frequency dividers, I-258, II-251, II-254**  
 clock input, IV-151  
 decade, I-259  
 low, II-253  
 programmable, IV-152-153  
 staircase generator and, I-730

**frequency-division multiplex stereo decoder, II-169**

**frequency doublers, I-313**  
 broadband, I-313  
 GASFET design, IV-324

**frequency generators, fixed-frequency, III-231**

**frequency indicators, beat, I-336**

**frequency inverters, variable frequency, complementary output, III-297**

- frequency meters, II-249-250, IV-282  
 audio, I-311  
 linear, I-310  
 low cost, II-250  
 power, II-250  
 power-line, I-311
- frequency multipliers/dividers, II-251, III-213-218  
 counter, odd-number, III-217  
 divide-by-1<sup>1</sup>/<sub>2</sub>, III-216  
 doubler, III-215  
 doubler, digital, III-216  
 doubler, to 1MHz, II-252  
 doubler, single-chip, III-218  
 nonselective tripler, II-252  
 pulse-width, III-214
- frequency-boundary detector, III-156  
 frequency-detecting comparator, III-88  
 frequency oscillator, tunable, II-425  
 frequency-ratio monitoring circuit, IV-202
- frequency-shift key (FSK) communications  
 data receiver, III-533  
 decoder, 10.8 MHz, I-214  
 generator, low-cost design, III-227  
 keying circuits, IV-245
- frequency synthesizer, programmable  
 voltage controlled, II-265
- frequency-to-voltage converter, I-318, II-255-257, III-219-220  
 dc, 10kHz, I-316  
 digital meter, I-317  
 optocoupler input, IV-193  
 sample-and-hold circuit, IV-194  
 single-supply design, IV-195  
 zener regulated, I-317
- fuel gauge, automotive, IV-46
- full-wave rectifiers, IV-328, IV-650  
 absolute value, II-528  
 precision, I-234, III-537
- function generators (*see also* burst generators; sound generators; waveform generators), I-729, II-271, III-221-242, III-258-274, IV-196-202  
 555 astable, low duty cycle, II-267  
 astable multivibrator, II-269, III-233, III-238  
 astable multivibrator, op amp, III-224  
 astable multivibrator, programmable-frequency, III-237  
 audio function generator, IV-197  
 clock generator, I-193  
 clock generator/oscillator, I-615  
 complementary signals, XOR gate, III-226  
 DAC controlled, I-722  
 emitter-coupled RC oscillator, II-266
- fixed-frequency, III-231  
 FM, low-frequency, III-228
- free-running multivibrator, programmable-frequency, III-235
- frequency-ratio monitoring circuit, IV-202
- frequency synthesizer, programmable  
 voltage controlled, II-265
- FSK, low-cost, III-227
- harmonics, III-228
- linear ramp, II-270
- linear triangle/square wave VCO, II-263
- monostable operation, III-235
- monostable multivibrator, III-230
- monostable multivibrator, linear-ramp, III-237
- monostable multivibrator, positive-triggered, III-229
- monostable multivibrator, video amplifier and comparator, II-268
- multiplying pulse width circuit, II-264
- multivibrator, low-frequency, III-237
- multivibrator, single-supply, III-232
- nonlinear potentiometer outputs, IV-198
- one-shot, precision, III-222
- one-shot, retriggerable, III-238
- oscillator/amplifier, wide frequency range, II-262
- potentiometer-position V/F converter, IV-200
- precise wave, II-274
- programmed, I-724
- pulse divider, noninteger, programmable, III-226
- pulse train, IV-202
- pulse, 2-ohm, III-231
- quad op amp, four simultaneous synchronized waveforms, II-259
- ramp, variable reset level, II-267
- sawtooth and pulse, III-241
- signal, two-function, III-234
- sine/cosine (0.1-10 kHz), II-260
- single supply, II-273
- sine-wave/square-wave oscillator, tunable, III-232
- single-control, III-238
- timebase, 1 Hz, for readout and counter applications, IV-201
- time-delay generator, I-217-218
- triangle-square wave, programmable, III-225
- triangle-wave, III-234
- triangle-wave timer, linear, III-222
- triangle-wave/square-wave, III-239
- triangle-wave/square-wave, precision, III-242
- triangle-wave/square-wave, wide-range, III-242
- tunable, wide-range, III-241
- UJT monostable circuit insensitive to changing bias voltage, II-268
- variable duty cycle timer output, III-240
- voltage controlled high-speed one shot, II-266
- waveform, II-269, II-272
- waveform, four-output, III-223
- white noise generator, IV-201
- funk box, II-593
- furnace exhaust gas/smoke detector, temp monitor/low supply detection, III-248
- fuzz box, III-575
- fuzz sound effect, II-590

## G

- GaAsFET amplifier, power, with single supply, II-10
- gain block, video, III-712
- gain control, automatic, audio, II-17
- gain-controlled stereo amplifier, II-9, III-34
- game feeder controller, II-360
- game roller, I-326
- games, II-275-277, III-243-245, IV-203-207  
 coin flipper, III-244  
 electronic dice, III-245, IV-207  
 electronic roulette, II-276, IV-205  
 lie detector, II-277, IV-206  
 reaction timer, IV-204  
 run-down clock/sound generator, IV-205  
 Wheel-of-Fortune, IV-206  
 who's first, III-244
- garage stop light, II-53
- gas analyzer, II-281
- gas/smoke detectors (*see also* smoke alarms and detectors), II-278-279, III-246-253, III-246  
 analyzer and, II-281  
 furnace exhaust, temp monitor/low-supply detection, III-248  
 methane concentration, linearized output, III-250  
 toxic, II-280  
 SCR, III-251  
 smoke/gas/vapor detector, III-250
- GASPET fixed power supplies, IV-405
- gated oscillator, last-cycle completing, III-427
- gated-pulse descrambler, II-165
- gates  
 programmable, I-394  
 XOR gate, IV-107

geiger counters, I-536-537  
   high-voltage supply, II-489  
   pocket-sized, II-514  
 gel cell charger, II-66  
 generators, electric-power  
   corona-wind generator, IV-633  
   high-voltage generator, IV-413  
   high-voltage generator, battery-powered, III-482  
   high-voltage generator, capacitor-discharge, III-485  
   high-voltage generator, dc voltage, III-481  
   high-voltage generator, negative-ions, IV-634  
   high-voltage generator, ultra-high voltages, II-488  
 glitch-detector, comparator, II-107  
 glow plug driver, II-52  
 graphic equalizer, ten-band, active filter in, II-684  
 grid-dip meter, bandswitched, IV-298  
 ground tester, II-345  
 ground-fault Hall detector, IV-208-209  
 ground-noise probe, battery-powered, III-500  
 guitars  
   compressor, sound-effect circuit, IV-519  
   matching audio signal amplifiers, IV-38  
   treble boost for, II-683  
   tuner, II-362  
 gun, laser, visible red and continuous, III-310

## H

half-duplex information transmission link, III-679  
 half-flash analog-to-digital converters, III-26  
 half-wave ac phase controlled circuit, I-377  
 half-wave rectifiers, I-230, III-528, IV-325  
   fast, I-228  
 Hall-effect circuits, II-282-284, III-254-258  
   angle of rotation detector, II-283  
   compass, III-258  
   current monitor, III-255, IV-284  
   door open alarm, II-284  
   ground-fault detector, IV-208-209  
   security door-ajar alarm, III-256  
   switches using, III-257, IV-539  
 halogen lamps, dimmer for, III-300  
 handtalkies, I-19  
   two-meter preamplifier for, I-19

hands-free telephone, III-605  
 hands-off intercom, III-291  
 handset encoder, telephone, III-613  
 harmonic generators, I-24, III-228, IV-649  
 Hartley oscillator, I-571  
 HC-based oscillators, III-423  
 HCU/HTC-based oscillator, III-426  
 headlight alarm, III-52  
 headlight delay unit, I-107, III-49  
 headlight dimmer, II-63  
 headphones, amplifier for, II-43  
 heart rate monitor, II-348, II-349  
 heat sniffer, electronic, III-627  
 heater, induction, ultrasonic, 120-KHz 500-W, III-704  
 heater controls, I-639  
   element controller, II-642  
   protector circuit\*, servo-sensed, III-624  
   temperature sensitive, I-640  
 hee-haw siren, II-578, III-565  
 hi-fi circuits  
   comparer, II-12  
   compressor, pre-emphasis and, III-93  
   expander, II-13  
   expander, de-emphasis, III-95  
   tone control circuit, high Z input, I-676  
 high-frequency amplifiers, III-259-265  
   29-MHz, III-262  
   3-30 MHz, 80-W, 12.5-13.6 V, III-261  
   amateur radio, linear, 2-30 MHz 140-W, III-260  
   noninverting, 28-dB, III-263  
   RF, broadcast band, III-264  
   UHF, wideband with high-performance FETs, III-264  
   wideband, hybrid, 500 kHz-1GHz, III-265  
   wideband, miniature, III-265  
 high-frequency oscillator, III-426  
   crystal, I-175, II-148  
 high-frequency peak detector, II-175  
 high-frequency signal generator, II-150  
 high-input-high-impedance amplifiers, II-19, II-44  
 high-pass filters, I-296  
   active, I-296  
   active, second-order, I-297  
   Butterworth, fourth-order, I-280  
   Chebyshev, fourth-order, III-191  
   fourth-order, 100-Hz, IV-174  
   second-order, 100-Hz, IV-175  
   sixth-order elliptical, III-191  
   wideband two-pole, II-215  
 high-voltage power supplies (*see also* generators, electrical power), II-

487-490, III-486, IV-409-413  
 10,000 V dc supply, IV-633  
 arc-jet power supply, starting circuit, III-479  
 battery-powered generator, III-482  
 bucking regulator, III-481  
 dc generator, III-481  
 fluorescent-lamp supply, cold-cathode design, IV-411  
 geiger counter supply, II-489  
 generators (*see* generators, electrical power)  
   inverter, III-484  
   inverter, 40 W, 120 V ac, IV-410-411  
   negative-ion generator, IV-634  
   optoisolated driver, III-482  
   preregulated, III-480  
   pulse supply, IV-412  
   regulator, III-485  
   regulator, foldback-current limiting, II-478  
   solid-state, remote adjustable, III-486  
   strobe power supply, IV-413  
   tube amplifier, high-volt isolation, IV-426  
   ultra high-voltage generator, II-488  
 hobby circuits (*see* model and hobby circuits)  
 hold button, telephone, 612, II-628  
 home security systems, IV-87  
   lights-on warning, IV-250  
   monitor, I-6  
 horn, auto, electronic, III-50  
 hot-wire anemometer, III-342  
 hour/time delay sampling circuit, II-668  
 Howland current pump, II-648  
 humidity sensor, II-285-287, III-266-267  
 HV regulator, foldback current limiting, II-478  
 hybrid power amplifier, III-455

**I**  
 IC product detectors, IV-143  
 IC timer, crystal-stabilized, subharmonic frequencies for, II-151  
 ice alarm, automotive, II-57  
 ice formation alarm, II-58  
 ice warning and lights reminder, I-106  
 ICOM IC-2A battery charger, II-65  
 IF amplifiers, I-690, IV-459  
   AGC system, IV-458  
   AGC system, CA3028-amplifiers, IV-458  
   preamp, IV-460  
   preamp, 30-MHz, IV-460  
   receiver, IV-459  
   two-stage, 60 MHz, I-563

ignition circuit, electronic, automotive, IV-65

ignition cut-off circuit, automotive, IV-53

ignition substitute, automotive, III-41

ignition system, capacitor discharger, I-103

ignition timing light, II-60

ignitor, III-362

illumination stabilizer, machine vision, II-306

image canceller, III-358

immobilizer, II-50

impedance converter, high to low, I-41

incandescent light flasher, III-198

indicators (*see also* alarms; control circuits; detectors; monitors; sensors), III-268-270, IV-210-218

ac-current indicator, IV-290

ac-power indicator, LED display, IV-214

ac/dc indicator, IV-214

alarm and, I-337

automotive-temperature indicator, PTC thermistor, II-56

balance indicator, IV-215

bar-graph driver, transistorized, IV-213

battery charge/discharge, I-122

battery condition, I-121

battery level, I-124

battery threshold, I-124

battery voltage, solid-state, I-120

beat frequency, I-336

CW offset indicator, IV-213

dial pulse, III-613

field-strength (*see* field-strength meters)

in-use indicator, telephone, II-629

infrared detector, low-noise, II-289

lamp driver, optically coupled, III-413

level, three-step, I-336

low-battery, I-124

low-voltage, III-769

mains-failure indicator, IV-216

On indicator, IV-217

on-the-air, III-270

overspeed, I-108

overvoltage/undervoltage, I-150

peak level, I-402

phase sequence, I-476

receiver-signal alarm, III-270

rf output, IV-299

rf-actuated relay, III-270

simulated, I-417

sound sensor, IV-218

stereo-reception, III-269

SWR warning, I-22

telephone, in-use indicator, II-629, IV-560, IV-563

telephone, off-hook, I-633

temperature indicator, IV-570

transmitter-output indicator, IV-218

undervoltage, battery operated equipment, I-123

visual modulation, I-430

visual level, III-269

voltage, III-758-772

voltage, visible, I-338, III-772

voltage-level, I-718, III-759

voltage-level, five step, I-337

voltage-level, ten-step, I-335

volume indicator, audio amplifier, IV-212

VU meter, LED display, IV-211

zero center, FM receivers, I-338

in-use indicator, telephone, II-629

induction heater, ultrasonic, 120-KHz 500-W, III-704

inductors

active, I-417

simulated, II-199

infrared circuits, II-288-292, III-271-277, IV-219-228

data link, I-341

detector, III-276, IV-224

detector, low-noise, II-289

emitter drive, pulsed, II-292

fan controller, IV-226

laser rifle, invisible pulsed, II-291

loudspeaker link, remote, I-343

low-noise detector for, II-289

object detector, long-range, III-273

people-detector, IV-225

proximity switch, infrared-activated, IV-345

receivers, I-342, II-292, III-274, IV-220-221

receivers, remote-control, I-342

remote controller, IV-224

remote-control tester, IV-228

remote-extender, IV-227

transmitter, I-343, II-289, II-290, III-274, III-276, III-277, IV-226-227

transmitter, digital, III-275

transmitter, remote-control, I-342

transmitter, voice-modulated pulse FM, IV-228

wireless speaker system, III-272

injectors

three-in-one set: logic probe, signal tracer, injector, IV-429

injector-tracers, I-522

single, II-500

signal, I-521

input selectors, audio, low distortion, II-38

input/output buffer, analog multiplexers, III-11

instrumentation amplifiers, I-346, I-348, I-349, I-352, II-293-295, III-278-284, IV-229-234

$\pm 100$  V common mode range, III-294

current collector head amplifier, II-295

differential, I-347, I-354, III-283

differential, biomedical, III-282

differential, high-gain, I-353

differential, input, I-354

differential, variable gain, I-349

extended common-mode design, IV-234

high-impedance low drift, I-355

high-speed, I-354

low-drift/low-noise dc amplifier, IV-232

low-signal level/high-impedance, I-350

low-power, III-284

meter driver, II-296

preamp, oscilloscope, IV-230-231

re-amp, thermocouple, III-283

precision FET input, I-355

saturated standard cell amplifier, II-296

strain gauge, III-280

triple op amp, I-347

ultra-precision, III-279

variable gain, differential input, I-349

very high-impedance, I-354

wideband, III-281

instrumentation meter driver, II-296

integrators, II-297-300, III-285-286

active, inverting buffer, II-299

JFET ac coupled, II-200

gamma ray pulse, I-536

long time, II-300

low drift, I-423

noninverting, improved, II-298

photocurrent, II-326

programmable reset level, III-286

ramp generator, initial condition reset, III-327

resettable, III-286

intercoms, I-415, II-301-303, III-287-292

bidirectional, III-290

carrier current, I-146

hands-off, III-291

party-line, II-303

pocket pager, III-288

telephone-intercoms, IV-557

two-way, III-292

two-wire design, IV-235-237

interfaces (*see also* computer circuits), IV-238-242

680x, 650x, 8080 families, III-98

- cassette-to-telephone, III-618
  - CPU interface, one-shot design, IV-239
  - DVM, temperature sensor and, II-647
  - FET driver, low-level power FET, IV-241
  - fiber optic, II-207
  - keyboard matrix interface, IV-240
  - logic-level translators, IV-242
  - optical sensor-to-TTL, III-314
  - process control, precision, I-30
  - tape recorder, II-614
  - interrupter, ground fault, I-580
  - interval timer, low-power, microprocessor programmable, II-678
  - inverters, III-293-298
    - dc-to-dc/ac, I-208
    - fast, I-422
    - fixed power supplies, 12 V input, IV-395
    - flip-flop, III-103
    - fluorescent lamp, 8-W, III-306
    - high-voltage, III-484
    - high-voltage power supplies, 40 W, 120 V ac, IV-410-411
    - low-power, fixed power supplies, III-466
    - on/off switch, III-594
    - picture, video circuits, III-722
    - power, III-298
    - power, 12 VDC-to-117 VAC at 60 Hz, III-294
    - power, medium, III-296
    - power, MOSFET, III-295
    - rectifier/inverter, programmable op-amp design, IV-364
    - ultrasonic, arc welding, 20 KHz, III-700
    - variable frequency, complementary output, III-297
    - voltage, precision, III-298
  - inverting amplifiers, I-41-42, III-14
    - balancing circuit in, I-33
    - low power, digitally selectable gain, II-333
    - power amplifier, I-79
    - programmable-gain, III-505
    - unity gain amplifier, I-80
    - wideband unity gain, I-35
  - inverting buffers, active integrator using, II-299
  - inverting comparators, hysteresis in, I-154
  - inverting followers, high-frequency, III-212
  - isolated feedback power supply, III-460
  - isolation amplifiers
    - capacitive load, I-34
    - level shifter, I-348
    - medical telemetry, I-352
    - rf, II-547
  - isolation and zero voltage switching logic, II-415
  - isolators
    - analog data-signal transmission, IV-133
    - digital transmission, II-414
    - stimulus, III-351
- J**
- JFET ac coupled integrator, III-200
- K**
- Kelvin thermometer, I-655
    - zero adjust, III-661
  - keying circuits, IV-243-245
    - automatic operation, II-15
    - automatic TTL morse code, I-25
    - CW keyer, IV-244
    - electronic, I-20
    - frequency-shift keyer, IV-245
    - negative key line keyer, IV-244
- L**
- lamp-control circuits (*see* lights/light-activated and controlled circuits)
  - laser circuits (*see also* lights/light-activated and controlled circuits; optical circuits), II-313-317, III-309-311
    - diode sensor, IV-321
    - discharge current stabilizer, II-316
    - gun, visible red, III-310
    - light detector, II-314
    - power supply, IV-636
    - pulsers, laser diode, III-311, I-416
    - receiver, IV-368
    - rifle, invisible IR pulsed, II-291
  - latches
    - 12-V, solenoid driver, III-572
    - comparator and, III-88
  - latching relays, dc, optically coupled, III-417
  - latching switches
    - double touchbutton, I-138
    - SCR-replacing, III-593
  - LCD display, fixed power supply, IV-392, IV-403
  - lead-acid batteries
    - battery chargers, III-55
    - life-extender and charger, IV-72
    - low-battery detector, III-56
  - leading-edge delay circuit, III-147
  - LED circuits
    - ac-power indicator, IV-214
    - alternating flasher, III-198, III-200
    - bar graph driver, II-188
    - driver, emitter/follower, IV-159
    - flasher, IV-181
    - flasher, control circuit, IV-183
    - flasher, multivibrator design, IV-182
    - flasher, PUT, II-239
    - flasher, sequential, reversible-direction, IV-182
    - flasher, UJT, II-231
    - frequency comparator, II-110
    - matrix display, two-variable, III-171
    - millivoltmeter readout, IV-294
    - multiplexed common-cathode display ADC, III-764
    - panel meter, III-347
    - peakmeter, III-333
    - ring-around flasher, III-194
    - RS-232C, computer circuit, III-103
    - three-year flasher, III-194
    - voltmeter, IV-286
    - VU meter, IV-211
  - level, electronic, II-666, IV-329
  - level controllers/indicators/monitors, II-174
    - alarm, water, I-389
    - audio, automatic, II-20
    - cryogenic fluid, I-386
    - fluid, I-387
    - hysteresis in, I-235
    - liquid, I-388, I-389, I-390
    - meter, LED bar/dot, I-251
    - peak, I-402
    - sound, I-403
    - three-step, I-336
    - visual, III-269
    - warning, audio output, low, I-391
    - warning, high-level, I-387
    - water, I-389
  - level shifter, negative-to-positive supply, I-394
  - LF or HF field strength meter, II-212
  - LF receiver, IV-451
  - lie detector, II-277, IV-206
  - lights/light-activated and controlled circuits (*see also* laser circuits; optical circuits), II-304-312, II-318-331, III-312-319
  - 860 W limited-range light control, I-376
  - ambient-light cancellization circuit, II-328
  - audio oscillator, light-sensitive, III-315
  - battery-powered light, capacitance operated, I-131
  - brightness control, lighted displays, III-316
  - carport light, automatic, II-308

- lights/light-activated and controlled circuits (*cont.*)
- chaser lights, sequential activation, IV-251, IV-252
- Christmas light driver, IV-254
- complementary, I-372
- controller, IV-252
- cross fader, II-312
- detectors, detection switch, adjustable, I-362
- dimmer, I-369, II-309, IV-247, IV-249
- dimmer, 800 W, II-309
- dimmer, dc lamp, II-307
- dimmer, four-quadrant, IV-248-249
- dimmer, halogen lamps, III-300
- dimmer, headlight, II-57, II-63
- dimmer, low-cost, I-373
- dimmer, soft-start, 800-W, I-376, III-304
- dimmer, tandem, II-312
- dimmer, triac, I-375, II-310, III-303
- dissolver, solid-state, III-304
- drivers, I-380
- drivers, flip-flop independent design, IV-160
- drivers, indicator-lamps, optical coupling, III-413
- drivers, neon lamps, I-379
- drivers, short-circuit-proof, II-310
- emergency light, I-378, I-581, II-320, III-317, III-415, IV-250
- flame monitor, III-313
- fluorescent-lamp high-voltage power supplies, cold-cathode design, IV-411
- indicator-lamp driver, optically coupled, III-413
- interruption detector, I-364
- inverter, fluorescent, 8-W, III-306
- level controller, I-380
- level detector, I-367, III-316
- level detector, low-light level drop detector, III-313
- life-extender for lightbulbs, III-302
- light-bulb changer, "automatic" design, IV-253
- lights-on warning, IV-58, IV-62, IV-250
- light-seeking robot, II-325
- logic circuit, I-393
- machine vision illumination stabilizer, II-306
- marker light, III-317
- meters, light-meters, I-382, I-383
- modulator, III-302
- monostable photocell, self-adjust trigger, II-329
- mooring light, automatic, II-323
- night light, automatic, I-360, III-306
- night light, telephone-controlled, III-604
- on/off relay, I-366
- on/off reminder, automotive lights, I-109
- on/off reminder, with ice alarm, I-106
- one-shot timer, III-317
- phase control, II-303, II-305
- photo alarm, II-319
- photocell, monostable, self-adjust trigger, II-329
- photocurrent integrator, II-326
- photodiode sensor amplifier, II-324
- photoelectric controller, IV-369
- photoelectric switches, II-321, II-326, III-319
- projector-lamp voltage regulator, II-305
- power outage light, line-operated, III-415
- pulse-generation interruption, I-357
- relay, on/off, I-366
- remote-controller, I-370
- robot, eyes, II-327
- robot, light-seeking robot, II-325
- sensor, ambient-light ignoring, III-413
- sensor, back-biased GaAs LED, II-321
- sensor, logarithmic, I-366
- sensor, optical sensor-to-TTL interface, III-314
- sequencer, pseudorandom, III-301
- short-circuit proof lamp driver, II-310
- signal conditioner, photodiode design, II-330
- sound-controlled lights, I-609
- speed controller, IV-247
- strobe, high-voltage power supplies, IV-413
- strobe, variable, III-589-590
- sun tracker, III-318
- switch, II-320, III-314
- switch, capacitance switch, I-132
- switch, light-controlled, II-320, III-314
- switch, photoelectric, II-321, II-326, III-319
- switch, solar triggered, III-318
- switch, zero-point triac, II-311
- tarry light, I-579
- telephone in-use light, II-625
- three-way light control, IV-251
- touch lamp, three-way, IV-247
- triac switch, inductive load, IV-253
- turn-off circuit, SCR capacitor design, IV-254
- twilight-triggered circuit, II-322
- voltage regulator for projection lamp, II-305
- wake-up call light, II-324
- warning lights, II-320, III-317
- light-seeking robot, II-325
- lights-on warning, automotive, II-55, III-42
- limit alarm, high/low, I-151
- limit comparator, I-156, III-106
  - double ended, I-156, II-105
- limit detectors
  - double ended, I-230, I-233
  - micropower double ended, I-155
- limiters, III-320-322, IV-255-257
  - audio, low distortion, II-15
  - audio clipper/limiter, IV-355
  - dynamic noise reduction circuit, III-321
  - hold-current, solenoid driver, III-573
  - noise, III-321, II-395
  - one-zener design, IV-257
  - output, III-322
  - power-consumption, III-572
  - transmit-time limiter/timer, IV-580
  - voltage limiter, adjustable, IV-256
- line amplifier
  - duplex, telephone, III-616
  - universal design, IV-39
- line drivers
  - 50-ohm transmission, II-192
  - 600-ohm balanced, II-192
  - full rail excursions, II-190
  - high output 600-ohm, II-193
  - video amplifier, III-710
- line-dropout detector, II-98
- line-frequency square wave generator, II-599
- line receivers
  - digital data, III-534
  - low-cost, III-532
- line-sync, noise immune 60 Hz, II-367-
- line-current detector, optically coupled, III-414
- line-current monitor, III-341
- line-hum touch switch, III-664
- line-synchronized driver circuit, III-174
- line-voltage announcer, ac, III-730
- line-voltage monitor, III-511
- linear amplifiers
  - 2-30MHz, 140W PEP amateur radio, I-555
  - 100 W PEP 420-450 MHz push-pull, I-554
  - 160 W PEP broadband, I-556
  - amateur radio, 2-30 MHz 140-W, III-260
  - CMOS inverter, II-11
  - rf amplifiers, 6-m, 100 W, IV-480-481
  - rf amplifiers, 903 MHz, IV-484-485
  - rf amplifiers, ATV, 10-to-15 W, IV-481

- linear couplers
    - analog, II-413
    - analog ac, II-412
    - dc, II-411
  - linear IC siren, III-564
  - linear optocoupler, instrumentation, II-417
  - linear ramp generator, II-270
  - linear regulators
    - fixed power supply, low dropout low cost, III-459
    - radiation-hardened 125A, II-468
  - link, fiber optic, III-179
  - liquid flowmeter, II-248
  - liquid-level detectors (*see* fluid and moisture detectors)
  - lithium batteries
    - charger for, II-67
    - state of charge indicator for, II-78
  - little dipper dip meter, II-183
  - locator, lo-parts treasure, I-409
  - locks, electronic, II-194-197, IV-161-163
    - combination, I-583, II-196
    - digital entry lock, IV-162
    - keyless design, IV-163
    - three-dial combination, II-195
  - locomotive whistle, II-589
  - logarithmic amplifiers, I-29, I-35, II-8
    - dc to video, I-38
    - log-ratio amplifier, I-42
  - logarithmic converter, fast, I-169
  - logarithmic light sensor, I-366
  - logarithmic sweep VCO, III-738
  - logic/logic circuits
    - audible pulses, II-345
    - four-state, single LED indicator, II-361
    - isolation and zero voltage switching, II-415
    - light-activated, I-393
    - line monitor, III-108
    - overvoltage protection, I-517
    - probes (*see* logic probes)
    - pulse generator for logic-trouble-shooting, IV-436
    - pulsar, III-520
    - signals, long delay line for, III-107
    - tester, audible, III-343
    - tester, TTL, I-527
    - translators, logic-level translators, IV-242
  - logic amplifiers, II-332-335
    - low power binary, to 10n gain low frequency, II-333
    - low power inverting, digitally selectable gain, II-333
    - low power noninverting, digitally selectable input and gain, II-334
    - precision, digitally programmable input and gain, II-335
    - programmable amplifier, II-334
  - logic converter, TTL to MOS, I-170
  - logic level shifter, negative-to-positive supply, I-394
  - logic probes, I-520, I-525, I-526, IV-430-431, IV-434
    - CMOS, I-523, I-526, III-499
    - digital, III-497
    - four-way operation, IV-432
    - memory-tester, installed, I-525
    - single-IC design, IV-433
    - three-in-one test set: probe, signal tracer, injector, IV-429
  - long-duration timer, PUT, II-675
  - long-range object detector, III-273
  - long-term electronic timer, II-672
  - long-time integrator, II-300
  - long-time timer, III-653
  - loop antenna, 3.5 MHz, IV-12-13
  - loop transmitter, remote sensors, III-70
  - loop-thru video amplifier, IV-616
  - loudness amplifier, II-46
  - loudness control, balance amplifier with, II-395
  - loudspeaker coupling circuit, I-78
  - low-current measurement system, III-345
  - low-distortion audio limiter, II-15
  - low-distortion input selector for audio use, II-38
  - low-distortion low level amplitude modulator, II-370
  - low-distortion sine wave oscillator, II-561
  - low-frequency oscillators, III-428
    - crystal, I-184, II-146
    - oscillator/flasher, II-234
    - Pierce oscillator, III-133
    - TTL oscillator, II-595
  - low-pass filters, I-287
    - active, digitally selected break frequency, II-216
    - Chebyshev, fifth-order, multi-feed-back, II-219
    - pole-active, I-295
    - fast-response, fast settling, IV-168-169
    - fast-settling, precision, II-220
    - precision, fast settling, II-220
    - Sallen-Key, 10 kHz, I-279
    - Sallen-key, active, IV-177
    - Sallen-Key, equal component, I-292
  - low-voltage alarm/indicator, II-493, III-769
  - low-voltage power disconnecter, II-97
  - LVDI circuits, II-336-339, III-323-324
  - driver demodulator, II-337
  - signal conditioner, II-338
- ## M
- machine vision, illumination stabilizer for, II-306
  - magnetic current low-power sensor, III-341
  - magnetic phono preamplifier, I-91
  - magnetic pickup phone preamplifier, I-89
  - magnetometer, II-341
  - magnets, permanent-magnet detector, IV-281
  - mains-failure indicator, IV-216
  - marker generator, III-138
  - marker light, III-317
  - mathematical circuits, III-325-327, IV-258-263
    - adder, III-327
    - adder, binary, fast-action, IV-260-261
    - divide/multiply, one trim, III-326
    - multiplier, precise commutating amp, IV-262-263
    - slope integrator, programmable, IV-259
    - subtractor, III-327
  - measurement/test circuits (*see also* detectors; indicators; meters), II-340, III-328-348, IV-264-311
    - 3-in-1 test set, III-330
    - absolute-value circuit, IV-274
    - acoustic-sound receiver, IV-311
    - acoustic-sound transmitter, IV-311
    - anemometer/, hot-wire, III-342
    - audible logic tester, III-343
    - automotive electrical tester, IV-45
    - B-field measurer, IV-272
    - barometer, IV-273
    - battery internal-resistance, IV-74
    - battery tester, IV-78
    - battery tester, ni-cad batteries, IV-79
    - breath alert alcohol tester, III-359
    - broadband ac active rectifier, IV-271
    - cable tester, III-539
    - capacitor tester, IV-265
    - capacitor-ESR measurer, IV-279
    - continuity tester, I-550, I-551, II-342, III-345, III-540, IV-287, IV-289, IV-296
    - continuity tester, latching, IV-295
    - crystal tester, II-151
    - current indicator, ac current, IV-290
    - current monitor, Hall-sensor, IV-284
    - current monitor/alarm, III-338
    - current sensor, high-gain, IV-291
    - deviation meter, IV-303
    - digital frequency meter, III-344

measurement/test circuits (*cont.*)  
   digital multimeter (DMM), high-resistance measuring, IV-291  
   diode, I-402, II-343  
   direction-of-rotation circuit, III-335  
   diode-curve tracer, IV-274  
   diode-matching circuit, IV-280  
   duty-cycle measurer, IV-265  
   duty-cycle meter, IV-275  
   duty-cycle monitor, III-329  
   E, T, and R measurement/test circuits, IV-283-296  
   electrolytic-capacitor reforming circuit, IV-276  
   electrometer, IV-277  
   electrostatic detector, III-337  
   filter analyzer, audio filters, IV-309  
   frequency checker, crystal oscillator, precision design, IV-301  
   frequency counter, III-340, IV-300  
   frequency meter, IV-282  
   frequency shift keyer tone generator, I-723  
   go/no-go, diode, I-401  
   go/no-go, dual-limit, I-157  
   grid-dip meter, bandswitched, IV-298  
   ground, I-580, II-345  
   injectors, IV-429  
   high-frequency and rf, IV-297-303  
   LC checker, III-334  
   LED panel meter, III-347  
   line-current monitor, III-341  
   logic probes (*see* logic probes)  
   logic-pulses, slow pulse test, II-345  
   low-current measurement, III-345  
   low-ohms adapter, IV-290  
   magnet, permanent-magnet detector, IV-281  
   magnetic current sensor, low-power, III-341  
   magnetic-field meter, IV-266  
   magnetometer, II-341  
   measuring gauge, linear variable differential transformer, I-404  
   meter tester, IV-270  
   microammeter, dc, four-range, IV-292  
   microfarad counter, IV-275  
   millivoltmeter, dc, IV-295  
   millivoltmeter, four-range, IV-289  
   millivoltmeter, LED readout, IV-294  
   modulation monitor, IV-299  
   mono audio-level meter, IV-310  
   motion sensor, unidirectional, II-346  
   motor hour, III-340  
   multiconductor-cable tester, IV-288  
   multimeter shunt, IV-293  
   noise generator, IV-308  
   ohmmeter, linear, III-540  
   ohmmeter, linear-scale, five-range, IV-290  
   oscilloscope adapter, four-trace, IV-267  
   paper sheet discriminator, copying machines, III-339  
   peak-dB meter, III-348  
   peakmeter, LED, III-333  
   phase difference from 0 to 180 degrees, II-344  
   phase meter, digital VOM, IV-277  
   picoammeter, III-338  
   power gain, 60 MHz, I-489  
   power supply test load, constant-current, IV-424  
   probes, 4-to-220 V, III-499  
   pulse-width, very short, III-336  
   QRP SWR bridge, III-336  
   remote-control infrared device, IV-228  
   resistance measurement, synchronous system, IV-285  
   resistance ratio detector, II-342  
   resistance/continuity meters, III-538-540  
   rf output indicator, IV-299  
   rf power, wide-range, III-332  
   SCR tester, III-344  
   shutter, I-485  
   signal generator, AM broadcast-band, IV-302  
   signal generator, AM/IF, 455 kHz, IV-301  
   signal strength (S), III-342  
   signal tracer, IV-429  
   sound-level meter, III-346, IV-305, IV-307  
   sound-test circuits (*see also* sound generators), IV-304  
   speedometer, bike, IV-271, IV-282  
   static detector, IV-276  
   stereo audio-level meter, IV-310  
   stereo audio-power meter, IV-306  
   stereo power meter, III-331  
   stud finder, III-339  
   SWR meter, IV-269  
   tachometer, III-335, III-340  
   tachometer, optical pick-up, III-347  
   tachometer, analog readout, IV-280  
   tachometer, digital readout, IV-278  
   tachometer, digital, IV-268-269  
   temperature measurement, transistorized, IV-572  
   test probe, 4-220 V, III-499  
   thermometers, III-637-643  
   three-in-one set, logic probe, signal tracer, injector, IV-429  
   three-phase tester, II-440  
   transistor, I-401, IV-281  
   TTL logic, I-527  
   universal test probe, IV-431  
   UHF source dipper, IV-299  
   voltmeter, digital LED readout, IV-286  
   VOM, phase meter, digital readout, IV-277  
   VOR signal simulator, IV-273  
   water-level measurement circuit, IV-191  
   wavemeter, tuned RF, IV-302  
   wideband test amplifier, IV-303  
   wire tracer, II-343  
   zener, I-400  
 medical electronic circuits, II-347-349, III-349-352  
   biomedical instrumentation differential amp, III-282  
   breath monitor, III-350  
   EKG simulator, three-chip, III-350  
   heart rate monitor, II-348, II-349  
   preamplifier for, II-349  
   stimulator, constant-current, III-352  
   stimulus isolator, III-351  
   thermometer, implantable/ingestible, III-641  
 melody generator, single-chip design, IV-520  
 memory-related circuits  
   EEPROM pulse generator, 5V-powered, III-99  
   memory protector/power supply monitor, IV-425  
   memory-saving power supply, II-486  
 metal detectors, II-350-352, IV-137  
 micropower, I-408  
 meters (*see also* measurement/test circuits)  
   ac voltmeters, III-765  
   analog, expanded-scale, IV-46  
   analog, expanded-scale, voltage reference, III-774  
   anemometer/, hot-wire, III-342  
   audio frequency, I-311  
   audio millivolt, III-767, III-769  
   audio power, I-488  
   automatic contrast, I-479  
   basic grid dip, I-247  
   breaker point dwell, I-102  
   capacitance, I-400  
   dc voltmeter, III-763  
   dc voltmeter, high-input resistance, III-762  
   deviation meter, IV-303  
   digital frequency, III-344  
   digital multimeter (DMM), high-resistance measuring, IV-291  
   dip, I-247  
   dip, dual-gate IGFET in, I-246

dosage rate, I-534  
 duty-cycle meter, IV-275  
 electrometer, IV-277  
 extended range VU, I-715, III-487  
 FET voltmeter, III-765, III-770  
 field-strength meters (*see* field-strength meters)  
 flash exposure, I-484, III-446  
 frequency meter, IV-282  
 grid-dip meter, bandswitched, IV-298  
 LED bar/dot level, I-251  
 LED panel, III-347  
 light, I-383  
 linear frequency, I-310  
 linear light, I-382  
 logarithmic light, I-382  
 magnetic-field meter, IV-266  
 meter-driver rf amplifier, 1-MHz, III-545  
 microammeter, dc, four-range, IV-292  
 microwave field strength, I-273  
 millivoltmeter, dc, IV-295  
 millivoltmeter, four-range, IV-289  
 millivoltmeter, LED readout, IV-294  
 mono audio-level meter, IV-310  
 motor hour, III-340  
 multimeter shunt, IV-293  
 ohmmeter, linear, III-540  
 ohmmeters, linear-scale, five-range, IV-290  
 peak decibels, III-348  
 peak, LED, III-333  
 pH, I-399  
 phase, I-406  
 picoammeter, III-338  
 power line frequency, I-311  
 power, I-489  
 resistance/continuity, III-538-540  
 rf power, I-16  
 rf power, wide-range, III-332  
 rf voltmeter, III-766  
 signal strength (S), III-342, IV-166  
 soil moisture, III-208  
 sound-level meter, IV-305, IV-307  
 sound level, telephone, III-614  
 sound level, III-346  
 speedometer, bicycle, IV-271, IV-282  
 stereo audio-level meter, IV-310  
 stereo audio-power meter, IV-306  
 stereo balance, I-618-619  
 stereo power, III-331  
 suppressed zero, I-716  
 SWR power, I-16, IV-269  
 tachometer, III-335, III-340, III-347  
 tachometer, analog readout, IV-280  
 tachometer, digital readout, IV-278  
 temperature, I-647  
 tester, IV-270  
 thermometers, III-637-643  
 tilt meter, III-644-646  
 varicap tuned FET DIP, I-246  
 vibration, I-404  
 voltage, III-758-77  
 voltmeters, ac wide-range, III-772  
 voltmeters, digital, 3.5-digit, full-scale four-decade, III-761  
 voltmeters, digital, 4.5-digit, III-760  
 voltmeters, high-input resistance, III-768  
 VOM field strength, I-276  
 VOM/phase meter, digital readout, IV-277  
 wavemeter, tuned RF, IV-302  
 methane concentration detector, linearized output, III-250  
 metronomes, I-413, II-353-355, III-353-354, IV-312-314  
 ac-line operated unijunction, II-355  
 accentuated beat, I-411  
 downbeat-emphasized, III-353-354  
 electronic, IV-313  
 low-power design, IV-313  
 novel design, IV-314  
 sight and sound, I-412  
 simple, II-354  
 version II, II-355  
 microammeter, dc, four-range, IV-292  
 microcontroller, musical organ, preprogrammed single-chip, I-600  
 micro-sized amplifiers, III-36  
 microphone circuits  
   amplifiers for, I-87, III-34  
   amplifiers for, electronic balanced input, I-86  
   FM wireless, III-682, III-685, III-691  
   mixer, II-37  
   preamp for, II-45, IV-37, IV-42  
   preamp, low-impedance design, IV-41  
   preamp for, low-noise transformerless balanced, I-88  
   preamp for, tone control in, I-675, II-687  
   wireless, IV-652-654  
   wireless AM, I-679  
 microprocessors (*see* computer circuits)  
 microvolt comparators  
   dual limit, III-89  
   hysteresis-including, III-88  
 microvolt probe, II-499  
 microwave amplifier circuits, IV-315-319  
   5.7 GHz, IV-317  
   bias supply for preamp, IV-318  
   preamplifier, 2.3 GHz, IV-316  
   preamplifier, 3.4 GHz, IV-316  
   preamplifier, single-stage, 10 GHz, IV-317  
   preamplifiers, bias supply, IV-318  
   preamplifiers, two-stage, 10 GHz, IV-319  
 Miller oscillator, I-193  
 millivoltmeters (*see also* meters; voltmeters)  
   ac, I-716  
   audio, III-767, III-769  
   high-input impedance, I-715  
 mini-stereo audio amplifiers, III-38  
 mixers, III-367-370, IV-330-336  
   1-MHz, I-427  
   audio, I-23, II-35, IV-335  
   audio, one-transistor design, I-59  
   CMOS, I-57  
   common-source, I-427  
   digital mixer, IV-334  
   diplexer, IV-335  
   doubly balanced, I-427  
   dynamic audio mixer, IV-331  
   four-channel, I-60, III-369, IV-333  
   four-channel, four-track, II-40  
   four-channel, high level, I-56  
   four-input, stereo, I-55  
   four-input, unity-gain, IV-334  
   HF transceiver/mixer, IV-457  
   hybrid, I-60  
   input-buffered, III-369  
   microphone, II-37  
   multiplexer, I-427  
   one-transistor design, I-59  
   passive, I-58  
   preamplifier with tone control, I-58  
   signal combiner, III-368  
   silent audio switching, I-59  
   sound amplifier and, II-37  
   stereo mixer, pan controls, IV-332  
   unity-gain, four-input, IV-334  
   utility-design mixer, IV-336  
   universal stage, III-370  
   video, high-performance operation, IV-609  
 mobile equipment, 8-amp regulated power supply, II-461  
 model and hobby circuits, IV-337-340  
   controller, model-train and/or slot-car, IV-338-340  
 model rocket launcher, II-358  
 modems, power-line, carrier-current circuit, III-82  
 modulated light beam circuit, ambient light effect cancellization with, II-328  
 modulated readback systems, disc/tape phase, I-89  
 modulation indicator/monitor, I-430  
   CB, I-431

modulators, I-437, II-368-372, III-371-377  
   + 12V dc single supply, balanced, I-437  
   AM, I-438  
   amplitude, low-distortion low level, II-370  
   balanced, III-376  
   balanced, phase detector-selector/sync rectifier, III-441  
   double-sideband suppressed-carrier, III-377  
   linear pulse-width, I-437  
   monitor for, III-375  
   musical envelope generator, I-601  
   pulse-position, I-435, III-375  
   pulse-width, I-435, I-436, I-438-440, III-376, IV-326  
   rf, I-436, III-372, III-374  
   rf, double sideband, suppressed carrier, II-369  
   saw oscillator, III-373  
   TTL oscillator for television display, II-372  
   TV, I-439, II-433, II-434  
   VHF, I-440, III-684  
   video, I-437, II-371, II-372  
 moisture detector (*see* fluid and moisture detectors)  
 monitors (*see also* alarms; control circuits; detectors; indicators; sensors), III-378-390  
   acid rain, III-361  
   battery, III-60-67  
   battery-alternator, automotive, III-63  
   blinking phone light, II-624  
   breath monitor, III-350  
   current, alarm and, III-338  
   directional signals, auto, III-48  
   door-ajar, automotive circuits, III-46  
   duty cycle, III-329  
   flames, III-313  
   home security system, I-6  
   line-current, III-341  
   line-voltage, III-511  
   logic line, III-108  
   modulation, III-375  
   overvoltage, III-762  
   power monitor, SCR design, IV-385  
   power-supply monitors (*see* power-supply monitors)  
   power-line connections, ac, III-510  
   precision battery voltage, HTS, I-122  
   receiver, II-526  
   sound level, telephone, III-614  
   telephone status, optoisolator in, I-625  
   telephone, remote, II-626  
   thermal monitor, IV-569  
   undervoltage, III-762  
   voltage, III-767  
   voltage, III-758-772  
 monostable circuit, I-464, II-460  
 monostable multivibrators, I-465, III-230, III-235  
   input lockout, I-464  
   linear-ramp, III-237  
   positive-triggered, III-229  
 monostable photocell, self-adjust trigger, II-329  
 monostable TTL, I-464  
 monostable UJT, I-463  
 mooring light, automatic, II-323  
 MOSFETs  
   power control switch, IV-386  
   power inverter, III-295  
 mosquito repelling circuit, I-684  
 motion sensors  
   acoustic Doppler motion detector, IV-343  
   auto alarm, I-9  
   low-current-drain design, IV-342-343  
   motorcycle alarm, I-9  
   UHF, III-516, IV-344  
   unidirectional, II-346  
 motor control circuits, IV-347-353  
   400 Hz servo amplifier, II-386  
   ac motors, II-375  
   bidirectional proportional, II-374  
   compressor protector, IV-351  
   direction control, dc motors, I-452  
   direction control, series-wound motors, I-448  
   direction control, shunt-wound motors, I-456  
   direction control, stepper motor, IV-350  
   driver control, ac, three-phase, II-383  
   driver control, ac, two-phase, II-382  
   driver control, constant-speed, III-386  
   driver control, dc, fixed speed, III-387  
   driver control, dc, servo, bipolar control input, II-385  
   driver control, dc, speed-controlled reversible, III-388  
   driver control, N-phase motor, II-382  
   driver control, reversing, dc control signals, II-381  
   driver control, servo motor amplifier, I-452, II-384  
   driver control, stepper motors, III-390  
   driver control, stepper motor, half-step, IV-349  
   driver control, stepper motor, quar-  
   ter-step, IV-350  
   driver control, two-phase, II-456  
   fiber-optic, dc, variable, II-206  
   hours-in-use meter, III-340  
   induction motor, I-454  
   load-dependent, universal motor, I-451  
   mini-drill control, IV-348  
   power brake, ac, II-451  
   power-factor controller, three-phase, II-388  
   PWM motor controller, III-389  
   PWM servo amplifier, III-379  
   PWM speed control, II-376  
   PWM speed control/energy-recovering brake, III-380  
   self-timing control, built-in, universal motor, I-451  
   servo motor amplifier, I-452, II-384  
   speed control (*see* speed controllers)  
   start-and-run motor circuit, III-382  
   stepper motors, half-step, IV-349  
   stepper motors, quarter-step, IV-350  
   stepper motors, speed and direction, IV-350  
   tachometer feedback control, II-378  
   tachometer feedback control, closed loop, II-390  
 motorcycle alarm, motion actuated, II-9  
 multiburst generator, square waveform, II-88  
 multimeters, shunt, IV-293  
 multiple-input detector, III-102  
 multiplexed common-cathode LED-display ADC, III-764  
 multiplexers, III-391-397  
   1-of-8 channel transmission system, III-395  
   analog, II-392  
   analog, 0/01-percent, II-392  
   analog, buffered input and output, III-396  
   analog, input/output buffer for, III-11  
   analog, single- to four-trace converter, II-431  
   capacitance, II-200, II-416  
   dc-, III-394  
   four-channel, low-cost, III-394  
   frequency, III-213-218  
   mathematical, one trim, III-326  
   oscilloscopes, add-on, III-437  
   pulse-width, III-214  
   resistor, II-199  
   sample-and-hold, three-channel, III-396  
   two-level, III-392  
   video, 1-of-15 cascaded, III-393  
   wideband differential, II-428  
 multipliers, low-frequency multiplier, IV-325

multiplying D/A converter, III-168  
 multiplying pulse width circuit, II-264  
 multivibrators  
   100 kHa free running, II-485  
   astable, I-461, II-269, II-510, III-196, III-224, III-233, III-238  
   astable, digital-control, II-462  
   astable, dual, II-463  
   astable, programmable-frequency, III-237  
   bistable, II-465  
   bistable, touch-triggered, I-133  
   car battery, II-106  
   CB modulation, II-431  
   current, II-203  
   duty-cycle, 50-percent, III-584  
   free-running, programmable-frequency, III-235  
   low-frequency, III-237  
   low-voltage, II-123  
   modulation, II-430  
   monostable, II-465, III-229, III-230, III-235, III-237  
   monostable, input lock-out, II-464  
   one-shot, II-465  
   oscilloscope, II-474  
   single-supply, III-232  
   sound level, II-403  
   square-wave generators, IV-536  
   telephone line, II-628  
   wideband radiation, II-535  
 music circuits (*see* sound generators)  
 musical envelope generator/modulator, IV-22  
 mux/demux systems  
   differential, I-425  
   eight-channel, I-426, II-115

## N

N-phase motor drive, III-382  
 NAB preamps  
   record, III-673  
   two-pole, III-673  
 NAB tape playback pre-amp, III-38  
 nano ammeter, I-202  
 narrow-band FM demodulator, carrier detect in, II-159  
 negative-ion generator, IV-634  
 neon flashers  
   five-lamp, III-198  
   two-state oscillator, III-200  
 networks  
   filter, I-291  
   speech, telephone, II-633  
 ni-cad batteries  
   analyzer for, III-64  
   charger, I-112, I-116, III-57  
   charger, 12 v, 200 mA per hour, I-114

charger, current and voltage limiting, I-114  
 charger, fast-acting, I-118  
 charger, portable, IV-69  
 charger, temperature-sensing, IV-77  
 charger, thermally controlled, II-68  
 packs, automotive charger for, I-115  
 protection circuit, III-62  
 test circuit, IV-79  
 zappers, I-6, II-68  
 night lights (*see* lights/light-activated and controlled circuits)  
 noise generators (*see* sound generators)  
 noise reduction circuits, II-393-396, III-398-401, IV-354-356  
   audio clipper/limiter, IV-355  
   audio shunt noise limiter, IV-355  
   audio squelch, II-394  
   balance amplifier with loudness control, II-395  
   blanker, IV-356  
   clipper, II-394  
   clipper, audio-powered, III-396  
   Dolby B, decode mode, III-401  
   Dolby B, encode mode, III-400  
   Dolby B/C, III-399  
   dynamic noise reduction, III-321  
   filter, III-188  
   filter, dynamic filter, III-190  
   limiter, II-395, III-321  
 noninverting amplifiers, I-41, III-14  
   adjustable gain, I-91  
   comparator with hysteresis in, I-153  
   high-frequency, 28-dB, III-263  
   hysteresis in, I-153  
   low power, digitally selectable input and gain, II-334  
   power, I-79  
   programmable-gain, III-505  
   single supply, I-74  
   split supply, I-75  
 noninverting integrator, improved design, II-298  
 noninverting voltage followers, I-33  
   high-frequency, III-212  
 nonselective frequency tripler, transistor saturation, II-252  
 Norton amplifier, absolute value, III-11  
 notch filters (*see also* filter circuits), I-283, II-397-403, III-402-404  
   4.5 MHz, I-282  
   550 Hz, II-399  
   1800 Hz, II-398  
   active band reject, II-401  
   adjustable Q, II-398  
   audio, II-400  
   bandpass and, II-223  
   high-Q, III-404  
   selectable bandwidth, I-281

three-amplifier design, I-281  
 tunable, II-399, II-402  
 tunable, passive-bridged differentiator, II-403  
 tunable, hum-suppressing, I-280  
 tunable, op amp, II-400  
 twin-T, III-403  
 Wien bridge, II-402  
 NTSC-to-RGB video decoder, IV-613  
 null circuit, variable gain, accurate, III-69  
 null detector, I-148, III-162

## O

ohmmeters, I-549  
   linear, III-540  
   linear scale, I-549  
   linear-scale, five-range, IV-290  
 ohms-to-volts converter, I-168  
 oil-pressure gauge, automotive, IV-44, IV-47  
 on/off inverter, III-594  
 on/off touch switches, II-691, III-663  
 one-of-eight channel transmission system, III-100  
 one-shot function generators, I-465  
   digitally controlled, I-720  
   precision, III-222  
   retriggerable, III-238  
 one-shot timers, III-654  
   light-controlled, III-317  
   voltage-controlled high-speed, II-266  
 op amps, II-404-406, III-405-406, IV-357-364  
   x10, I-37  
   x100, I-37  
   astable multivibrator, III-224  
   audio amplifier, IV-33  
   bidirectional compound op amp, IV-361  
   clamping for, II-22  
   clock circuit using, III-85  
   comparator, three-input and gate comparator, IV-363  
   compound op-amp, IV-364  
   feedback-stabilized amplifier, IV-360  
   gain-controlled op amp, IV-361  
   intrinsically safe protected, III-12  
   inverter/rectifier, programmable, IV-364  
   on/off switch, transistorized, IV-546  
   power booster, IV-358  
   power driver circuit, IV-158-159  
   quad, simultaneous waveform generator using, II-259  
   single potentiometer to adjust gain over bipolar range, II-406  
   swing rail-ray, LM324, IV-363

- op amps (*cont.*)
    - tunable notch filter with, II-400
    - variable gain and sign, II-405
    - VCO driver, IV-362
    - video op amp circuits, IV-615
  - optical circuits (*see also* lasers; lights/light-activated and controlled circuits), II-407-419, IV-365-369
  - 50 kHz center frequency FM transmitter, II-417
  - ac relay, III-418
  - ac relay using two photon couplers, II-412
  - ac switcher, high-voltage, III-408
  - ambient light ignoring optical sensor, III-413
  - CMOS coupler, III-414
  - communication system, II-416
  - dc linear coupler, II-411
  - dc latching relay, III-417
  - digital transmission isolator, II-414
  - high-sensitivity, NO, two-terminal zero voltage switch, II-414
  - indicator lamp driver, III-413
  - integrated solid state relay, II-408
  - interruption sensor, IV-366
  - isolation and zero voltage switching logic, II-415
  - light-detector, IV-369
  - line-current detector, III-414
  - linear ac analog coupler, II-412
  - linear analog coupler, II-413
  - linear optocoupler for instrumentation, II-417
  - microprocessor triac array driver, II-410
  - optoisolator relay circuit, IV-475
  - paper tape reader, II-414
  - photoelectric light controller, IV-369
  - power outage light, line-operated, III-415
  - probe, IV-369
  - receiver, 50 kHz FM optical transmitter, II-418
  - receiver, light receiver, IV-367
  - receiver, optical or laser light, IV-368
  - relays, dc solid-state, open/closed, III-412
  - source follower, photodiode, III-419
  - stable optocoupler, II-409
  - telephone ring detector, III-611
  - transmitter, light transmitter, IV-368
  - triggering SCR series, III-411
  - TTL coupler, optical, III-416
  - zero-voltage switching, closed half-wave, III-412
  - zero-voltage switching, solid-state, III-410
  - zero-voltage switching, solid-state relay, III-416
- optical communication system, I-358, II-416
  - optical pyrometer, I-654
  - optical receiver, I-364, II-418
  - optical Schmitt trigger, I-362
  - optical sensor, ambient light ignoring, III-413
  - optical sensor-to-TTL interface, III-314
  - optical transmitters, I-363
    - FM (PRM), I-367
  - optocouplers
    - linear, instrumentation, II-417
    - stable, II-409
  - optoisolators, IV-475
    - driver, high-voltage, III-482
    - telephone status monitor using, I-626
  - OR gate, I-395
  - organ, musical, I-415
    - preprogrammed single chip microcontroller for, I-600
    - stylus, I-420
  - oscillators, II-420-429, III-420-432, IV-370-377
    - 1 kHz, II-427
    - 1.0 MHz, I-571
    - 2MHz, II-571
    - 5-V, III-432
    - 50 kHz, I-727
    - 400 MHz, I-571
    - 500 MHz, I-570
    - 800 Hz, I-68
    - adjustable over 10:1 range, II-423
    - astable, I-462
    - audio, I-245, III-427, IV-374, IV-375
    - audio, light-sensitive, III-315
    - beat-frequency audio generator, IV-371
    - buffer circuits, IV-89
    - Butler, aperiodic, I-196
    - Butler, common base, I-191
    - Butler, emitter follower, II-190-191, II-194
    - cassette bias, II-426
    - clock generator, I-615, III-85
    - CMOS, I-615
    - CMOS, 1 MHz to 4MHz, I-199
    - CMOS, crystal, I-187
    - code practice, I-15, I-20, I-22, II-428, III-431, IV-373, IV-375, IV-376
    - Colpitts, I-194, I-572, II-147
    - Colpitts, harmonic, I-189-190
    - crystal (*see* crystal oscillators)
    - double frequency output, I-314
    - discrete sequence, III-421
    - duty-cycle, 50-percent, III-426
    - emitter-coupled, big loop, II-422
    - emitter-coupled, RC, II-266
    - exponential digitally controlled, I-728
    - feedback, I-67
    - flasher and, high drive, II-235
    - flasher and, low frequency, II-234
    - free-running, I-531
    - free-running, square wave, I-615
    - frequency doubled output from, II-596
    - gated, I-728
    - gated, last-cycle completing, III-427
    - Hartley, I-571
    - hc-based, III-423
    - HCU/HCT-based, III-426
    - high-current, square-wave generator, III-585
    - high-frequency, III-426
    - high-frequency, crystal, I-175, II-148
    - load-switching, 100 mA, I-730
    - low-distortion, I-570
    - low-duty-cycle pulse circuit, IV-439
    - low-frequency, III-428
    - low-frequency, crystal, I-184, II-146
    - low-frequency, TTL, II-595
    - low-noise crystal, II-145
    - Miller, I-193
    - neon flasher, two-state, III-200
    - one-second, 1 kHz, II-423
    - one-shot, voltage-controlled high-speed, II-266
    - overtone, 50 MHz to 100 MHz, I-181
    - overtone, crystal, I-176, I-180, II-146, IV-123
    - overtone, crystal switching, I-183
    - overtone, fifth overtone, I-182
    - phase-locked, 20-MHz, IV-374
    - Pierce, I-195
    - Pierce, crystal, II-144
    - Pierce, harmonic, I-199, II-192
    - quadrature, III-428
    - quadrature-output, I-729
    - quadrature-output, square-wave generator, III-585
    - R/C, I-612
    - reflection, crystal-controlled, III-136
    - relaxation, IV-376
    - relaxation, SCR, III-430
    - resistance-controlled digital, II-426
    - rf (*see also* rf oscillator), II-550, I-572
    - rf-genie, II-421
    - rf-powered sidetone, I-24
    - RLC, III-423
    - sawtooth wave, modulator, III-373
    - Schmitt trigger crystal, I-181
    - sine-wave (*see* sine-wave oscillators)
    - sine-wave/square wave, easily tuned, I-65
    - sine-wave/square-wave, tunable, III-232
    - single op amp, I-529
    - square-wave, II-597, I-613-614, II-

616, IV-532, IV-533  
square-wave, 0.5 Hz, I-616  
square-wave, 1kHz, I-612  
start-stop oscillator pulse circuit, IV-438  
switching, 20 ns, I-729  
temperature-compensated, low power 5v-driven, II-142  
temperature-stable, II-427  
temperature-compensated crystal, I-187  
timer, 500 timer, I-531  
tone-burst, decoder and, I-726  
transmitter and, 27 MHz and 49 MHz rf, I-680  
triangle/square wave, I-616, II-422  
TTL, I-179, I-613  
TTL, 1MHz to 10MHz, I-178  
TTL, television display using, II-372  
TTL-compatible crystal, I-197  
tube type crystal, I-192  
tunable frequency, II-425  
tunable single comparator, I-69  
varactor tuned 10 MHz ceramic resonator, II-141  
variable, II-421  
variable, audio, 20Hz to 20kHz, II-727  
variable, four-decade, single control for, II-424  
variable, wide range, II-429  
variable-duty cycle, fixed-frequency, III-422  
voltage-controlled (*see* voltage-controlled oscillators)  
wide-frequency range, II-262  
wide-range, I-69, III-425  
wide-range, variable, I-730  
Wien-bridge (*see* Wien-bridge oscillators)  
XOR-gate, III-429  
yelp, II-577

oscilloscopes, II-430-433, III-433-439  
analog multiplexer, single- to four-trace scope converter, II-431  
beam splitter, I-474  
calibrator, II-433, III-436  
converter, I-471  
CRO doubler, III-439  
eight-channel voltage display, III-435  
extender, III-434  
FET dual-trace switch for, II-432  
four-trace oscilloscope adapter, IV-267  
monitor, I-474  
multiplexer, add-on, III-437  
preamplifier, III-437  
preamplifier, counter, III-438  
preamplifier, instrumentation amplifiers, IV-230-231

sensitivity amplifier, III-436  
triggered sweep, III-438  
voltage-level dual readout, IV-108  
outband descrambler, II-164  
out-of-bounds pulse-width detector, III-158  
output limiter, III-322  
output-gating circuit, photomultiplier, II-516  
output-stage booster, III-452  
over/under temperature monitor, dual output, II-646  
overload protector, speaker, II-16  
overspeed indicator, I-108  
overtone crystal oscillators, II-146  
50 MHz to 100 MHz, I-181  
100 MHz, IV-124  
crystal, I-176, I-180, II-146  
crystal switching, I-183  
fifth overtone, I-182  
third-overtone oscillator, IV-123  
overvoltage detection and protection, IV-389  
comparator to detect, II-107  
monitor for, III-762  
protection circuit, II-96, II-496, III-513  
undervoltage and, indicator, I-150

## P

pager, pocket-size, III-288  
PAL/NTSC decoder, RGB input, III-717  
palette, video, III-720  
panning circuit, two-channel, I-57  
paper-sheet discriminator, copying machines, III-339  
paper-tape reader, II-414  
parallel connections, telephone, III-611  
party-line intercom, II-303  
passive bridge, differentiator tunable notch filter, II-403  
passive mixer, II-58  
PCB continuity tester, II-342  
peak decibel meter, III-348  
peak detectors, II-174, II-175, II-434-436, IV-138, IV-143  
analog, with digital hold, III-153  
digital, III-160  
high-bandwidth, III-161  
high-frequency, II-175  
high-speed, I-232  
low-drift, III-156  
negative, I-225, I-234  
op amp, IV-145  
positive, I-225, I-235, II-435, III-169  
ultra-low drift, I-227  
voltage, precision, I-226  
wide-bandwidth, III-162  
wide-range, III-152

peak meter, LED, III-333  
peak program detector, III-771  
peak-to-peak converter, precision ac/dc, II-127  
people-detector, infrared-activated, IV-225  
period counter, 100 MHz, frequency and, II-136  
period-to-voltage converter, IV-115  
pest-repeller, ultrasonic, III-699, III-706, III-707, IV-605-606  
pH meter, I-399  
pH probe, I-399, III-501  
phase detectors, III-440-442  
10-bit accuracy, II-176  
phase selector/sync rectifier/balanced modulator, III-441  
phase sequence, III-441  
phase difference, 0- to 180-degree, II-344  
phase indicator, II-439  
phase meter, I-406  
digital VOM, IV-277  
phase selector, detector/sync rectifier/balanced modulator, III-441  
phase sequence circuits, II-437-442  
detector, II-439, II-441, II-442, III-441  
indicator, I-476, II-439  
rc circuit, phase sequence reversal detection, II-438  
reversal, rc circuit to detect, II-438  
three-phase tester, II-440  
phase shifters, IV-647  
0-180 degree, I-477  
0-360 degree, I-477  
single transistor, I-476  
phase splitter, precision, III-582  
phase tracking, three-phase square wave generator, II-598  
phasor gun, I-606, IV-523  
phono amplifiers, I-80-81  
magnetic pickup, I-89  
stereo, bass tone control, I-670  
phono preamps, I-91  
equalized, III-671  
LM382, I-90  
low-noise design, IV-36  
magnetic, I-91, III-37  
magnetic, ultra-low-noise, IV-36  
photo-conductive detector amplifier, four quadrant, I-359  
photo memory switch for ac power control, I-363  
photo stop action, I-481  
photocell, monostable, self-adjust trigger, II-329  
photocurrent integrator, II-326  
photodiode circuits  
amplifier, III-672

- photodiode circuits amplifier (*cont.*)  
 amplifier, low-noise, III-19  
 current-to-voltage converter, II-128  
 sensor amplifier, II-324  
 amplifier, I-361  
 comparator, precision, I-360  
 level detector, precision, I-365  
 PIN, thermally stabilized signal conditioner with, II-330  
 PIN-to-frequency converters, III-120  
 source follower, III-419  
 photoelectric circuits  
 ac power switch, III-319  
 alarm system, II-4  
 controlled flasher, II-232  
 light controller, IV-369  
 smoke alarm, line operated, I-596  
 smoke detector, I-595  
 switch, II-321  
 switch, synchronous, II-326  
 photoflash, electronic, III-449  
 photography-related circuits, II-443-449, III-443-449, IV-378-382  
 auto-advance projector, II-444  
 camera alarm trigger, III-444  
 camera trip circuit, IV-381  
 contrast meter, II-447  
 darkroom enlarger timer, III-445  
 electronic flash trigger, II-448  
 enlarger timer, II-446  
 exposure meter, I-484  
 flash meter, III-446  
 flash slave driver, I-483  
 flash trigger, electronic, II-448  
 flash trigger, remote, I-484  
 flash trigger, sound-triggered, II-449  
 flash trigger, xenon flash, III-447  
 photo-event timer, IV-379  
 photoflash, electronic, III-449  
 shutter speed tester, II-445  
 slave-flash unit trigger, SCR design, IV-380, IV-382  
 slide projector auto advance, IV-381  
 slide timer, III-448  
 slide-show timer, III-444  
 sound trigger for flash unit, II-449, IV-382  
 time-delay flash trigger, IV-380  
 timer, I-485  
 xenon flash trigger, slave, III-447  
 photomultiplier output-gating circuit, II-516  
 picoammeters, I-202, II-154, III-338  
 circuit for, II-157  
 guarded input circuit, II-156  
 picture fixer/inverter, III-722  
 Pierce crystal oscillator, I-195, II-144  
 1-MHz, III-134  
 harmonic, I-199, II-192  
 low-frequency, III-133  
 piezoelectric alarm, I-12  
 piezoelectric fan-based temperature controller, III-627  
 PIN photodiode-to-frequency converters, III-120  
 pink noise generator, I-468  
 plant watering gauge, II-248  
 plant watering monitor, II-245  
 plant waterer, I-443  
 playback amplifier, tape, I-77  
 PLL/BC receiver, II-526  
 pocket pager, III-288  
 polarity converter, I-166  
 polarity-protection relay, IV-427  
 polarity-reversing amplifiers, low-power, III-16  
 portable-radio 3 V fixed power supplies, IV-397  
 position indicator/controller, tape recorder, II-615  
 positive input/negative output charge pump, III-360  
 positive peak detector, II-435  
 positive regulator, NPN/PNP boost, III-475  
 power amps, II-450-459, III-450-456  
 2- to 6-watt audio amplifier with preamp, II-451  
 10 W, I-76  
 12 W low distortion, I-76  
 25 W, II-452  
 90 W, safe area protection, II-459  
 am radio, I-77  
 audio, II-451, III-454, IV-28-33  
 audio, 20-W, III-456  
 audio, 50-W, III-451  
 audio, 6-W, with preamp, III-454  
 audio, booster, II-455  
 bridge audio, I-81  
 bull horn, II-453  
 class-D, III-453  
 hybrid, III-455  
 inverting, I-79  
 low-distortion, 12 W, I-76  
 low-power audio, II-454  
 noninverting, I-79  
 noninverting, ac, I-79  
 output-stage booster, III-452  
 portable, III-452  
 rear speaker ambience amplifier, II-458  
 rf, 1296-MHz solid state, III-542  
 rf, 5W, II-542  
 switching, I-33  
 two-meter 10 W, I-562  
 walkman amplifier, II-456  
 power booster, I-28, I-33  
 power control, burst, III-362  
 power disconnecter, low-voltage, II-97  
 power factor controller, three-phase, II-388  
 power failure alarm, I-581-582  
 power gain test circuit, 60 MHz, I-489  
 power inverters, III-298  
 12 VDC-to-117 VAC at 60 Hz, III-294  
 medium, III-296  
 MOSFET, III-295  
 power loss detector, II-175  
 power meters, I-489  
 audio, I-488  
 frequency and, II-250  
 rf, I-16  
 SWR, I-16  
 power op amp/audio amp, high slew rate, I-82  
 power outage light, line-operated, III-415  
 power pack for battery operated devices, I-509  
 power protection circuit, I-515  
 power reference, 0-to-20 V, I-694  
 power supplies, II-460-486, III-464  
 5V including momentary backup, II-464  
 5V, 0.5A, I-491  
 8-amp regulated, mobile equipment operation, II-461  
 10 A regulator, current and thermal protection, II-474  
 12-14 V regulated 3A, II-480  
 90 V rms voltage regulator with PUT, II-479  
 500 kHz switching inverter for 12V, II-474  
 2,000 V low-current supply, IV-636-637  
 adjustable current limit and output voltage, I-505  
 arc lamp, 25W, II-476  
 arc-jet, starting circuit, III-479  
 backup supply, drop-in main-actuated, IV-424  
 balance indicator, III-494  
 battery charger and, 14V, 4A, II-73  
 bench top, II-472  
 benchtop, dual output, I-505  
 bipolar, battery instruments, II-475  
 charge pool, III-469  
 dc-to-dc SMPS variable 18V to 30 V out at 0.2A, II-480  
 dual polarity, I-497  
 fault monitor, single-supply, III-495  
 fixed power supplies (*see* fixed power supplies)  
 general-purpose, III-465  
 glitches in, comparator to detect, II-107

- high-voltage (*see* high-voltage power supplies)
- increases zener diode power rating, II-485
- isolated feedback, III-460
- laser power supply, voltage multiplier circuits, IV-636
- low-ripple, I-500
- low-volts alarm, II-493
- memory save on power-down, II-486
- micropower bandgap reference, II-470
- microprocessor power supply watchdog, II-494
- monitors (*see* power-supply monitors)
- off-line flyback regulator, II-481
- overvoltage protection circuit, II-496
- overvoltages in, comparator to detect, II-107
- power-switching circuit, II-466
- programmable, III-467
- protection circuit, II-497
- protection circuit, fast acting, I-518
- push-pull, 400V/60W, II-473
- radiation-hardened 125A linear regulator, II-468
- regulated, +15V I-A, III-462
- regulated, -15V I-A, III-463
- regulated, split, I-492
- SCR preregulator for, II-482
- single supply voltage regulator, II-471
- split, I-512
- stand-by, non-volatile CMOS RAMs, II-477
- switching, II-470, III-458
- switching, 50-W off-line, III-473
- switching, variable, 100-KHz multiple-output, III-488
- three-rail, III-466
- uninterruptible, +5V, III-477
- uninterruptible, personal computer, II-462
- variable (*see* variable power supplies)
- voltage regulator, II-484
- power-consumption limiters, III-572
- power-control circuits, IV-383-389
  - ac switch, battery-triggered, IV-387
  - bang-bang controllers, IV-389
  - current-loop control, SCR design, IV-387
  - high-side switches, 5 V supplies, IV-384, IV-385
  - monitor, SCR design, IV-385
  - MOSFET switch, IV-386
  - overvoltage protector, IV-389
  - power controller, universal design, IV-388
  - pushbutton switch, IV-388
- power-down protection
  - alarm, III-511
  - memory save power supply for, II-486
  - protection circuit, II-98
- power-line connections monitor, ac, III-510
- power-line modem, III-82
- power-on reset, II-366
- power-supply monitors, II-491-497, III-493-495, IV-422-427
  - backup supply, drop-in main-activated, IV-424
  - balance monitor, III-494
  - booster/buffer, boosts reference current, IV-425
  - circuit breaker, trip circuit, IV-423
  - fault monitor, single-supply, III-495
  - memory protector/supply monitor, IV-425
  - polarity-protection relay, IV-427
  - test load, constant-current, IV-424
  - triac for ac-voltage control, IV-426
  - tube amplifier, high-voltage isolation, IV-426
  - voltage sensor, IV-423
- power-switching circuit, II-466
  - complementary ac, I-379
- power/frequency meter, II-250
- preamplifiers, I-41
  - 6-meter, 20 dB gain and low NF, II-543
  - 1000x, low-noise design, IV-37
  - audio amplifier, 2- to 6-watt, II-451
  - audio amplifier, 6-W and, III-454
  - equalized, for magnetic phono cartridges, III-671
  - frequency counter, III-128
  - general purpose, I-84
  - general-purpose design, audio signal amplifiers, IV-42
  - handtalkies, two-meter, I-19
  - IF, 30 MHz, IV-460
  - impedance-matching, IV-37
  - LM382 phono, I-91
  - low-noise, IV-41
  - low-noise 30MHz, I-561
  - low-noise transformerless balanced microphone, I-88
  - magnetic phono, I-91, III-673, IV-35
  - medical instrument, II-349
  - microphone, II-45, IV-37, IV-42
  - microphone, low-impedance, IV-41
  - microphone, tone control for, II-687
  - microphone, transformerless, unbalanced input, I-88
  - microwave, 2.3 GHz, IV-316
  - microwave, 3.4 GHz, IV-316
  - microwave, bias supply, IV-318
  - microwave, single-stage, 10 GHz, IV-317
- microwave, two-stage, 10 GHz, IV-319
- NAB, tape playback, professional, III-38
- NAB, record, III-673
- NAB, two-pole, III-673
- oscilloscope, III-437
- oscilloscope, instrumentation amplifiers, IV-230-231
- oscilloscope/counter, III-438
- phono, I-91
- phono, low-noise, IV-36
- phono, magnetic, ultra-low-noise, IV-36
- phono, magnetic, III-37
- read-head, automotive circuits, III-44
- RIAA, III-38
- RIAA/NAB compensation, I-92
- stereo, II-43, II-45
- tape, I-90
- thermocouple instrumentation amplifier, III-283
- tone control, I-675
- tone control, high-level, II-688
- tone control, IC, I-673, III-657
- tone control, mixer, I-58
- UHF-TV, III-546
- ultra-low leakage, I-38, II-7
- VHF, I-560
- precision amplifier, I-40
  - digitally programmable input and gain, II-335
- preregulators
  - high-voltage power supplies, III-480
  - tracking, III-492
- prescaler, data circuits, low-frequency, IV-132
- prescaler probe, amplifying, 650 MHz, II-502
- preselectors
  - rf amplifiers, JFET, IV-485
  - rf amplifiers, JFET, double-tuned, IV-483
  - rf amplifiers, varactor-tuned, IV-488
- printer-error alarm, computer circuits, IV-106
- printers
  - printer-error alarm, IV-106
  - two-sheets in printer detector, IV-136
- probes, II-498-504, III-496-503, IV-428-434
  - 100 K megaohm dc, I-524
  - ac hot wire, I-581
  - audible TTL, I-524
  - audio-rf signal tracer, I-527
  - capacitance buffer, low-input, III-498
  - capacitance buffer, stabilized low-input, III-502

probes (*cont.*)

clamp-on-current compensator, II-501  
CMOS logic, I-523  
FET, III-501  
general purpose rf detector, II-500  
ground-noise, battery-powered, III-500  
logic probes (*see* logic probes)  
microvolt, II-499  
optical light probe, IV-369  
pH, I-399, III-501  
prescaler, 650 MHz amplifying, II-502  
rf, I-523, III-498, III-502, IV-433  
single injector-tracer, II-500  
test, 4-220V, III-499  
three-in-one test set: logic probe, signal tracer, injector, IV-429  
tone, digital IC testing, II-504  
universal test probe, IV-431  
process control interface, I-30  
processor, CW signal, I-18  
product detector, I-223  
programmable amplifiers, II-334, III-504-508  
differential-input, programmable gain, III-507  
inverting, programmable-gain, III-505  
noninverting, programmable-gain, III-505  
precision, digital control, III-506  
precision, digitally programmable, III-506  
programmable-gain, selectable input, I-32  
variable-gain, wide-range digital control, III-506  
projectors (*see* photography-related circuits)  
proportional temperature controller, III-626  
protection circuits, II-95-99, III-509-513  
12ns circuit breaker, II-97  
automatic power down, II-98  
circuit breaker, ac, III-512  
circuit breaker, electronic, high-speed, II-96  
compressor protector, IV-351  
crowbars, electronic, II-99, III-510  
heater protector, servo-sensed, III-624  
line protectors, computer I/O, 3  $\mu$ P, IV-101  
line dropout detector, II-98  
line-voltage monitor, III-511  
low-voltage power disconnect, II-97  
overvoltage, II-96, IV-389

overvoltage, fast, III-513  
overvoltage, logic, I-517  
polarity-protection relay for power supplies, IV-427  
power-down, II-98  
power-failure alarm, III-511  
power-line connections monitor, ac, III-510  
power supply, II-497, I-518  
reset-protection for computers, IV-100  
proximity sensors, I-135-136, I-344, II-505-507, III-514-518, IV-341-346  
alarm for, II-506  
capacitive, III-515  
field disturbance sensor/alarm, II-507  
infrared-reflection switch, IV-345  
relay-output, IV-345  
SCR alarm, III-517  
self-biased, changing field, I-135  
switch, III-517  
UHF movement detector, III-516  
pseudorandom sequencer, III-301  
pulse circuits, IV-435-440  
amplitude discriminator, III-356  
coincidence detector, II-178  
counter, ring counter, low-power, IV-437  
delay, dual-edge trigger, III-147  
detector, missing-pulse, III-159  
divider, non-integer programmable, III-226, II-511  
extractor, square-wave, III-584  
generator, 555-circuit, IV-439  
generator, delayed-pulse generator, IV-440  
generator, free-running, IV-438  
generator, logic troubleshooting applications, IV-436  
generator, transistorized design, IV-437  
height-to-width converters, III-119  
oscillator, fast, low duty-cycle, IV-439  
oscillator, start-stop, stable design, IV-438  
pulse train-to-sinusoid converters, III-122  
sequence detector, II-172  
stretcher, IV-440  
stretcher, negative pulse stretcher, IV-436  
stretcher, positive pulse stretcher, IV-438  
pulse generators, II-508-511  
2-ohm, III-231  
300-V, III-521  
astable multivibrator, II-510  
clock, 60Hz, II-102  
CMOS short-pulse, III-523  
delayed, II-509

EEPROM, 5V-powered, III-99  
interrupting pulse-generation, I-357  
logic, III-520  
programmable, I-529  
sawtooth-wave generator and, III-241  
single, II-175  
two-phase pulse, I-532  
unijunction transistor design, I-530  
very low duty-cycle, III-521  
voltage-controller and, III-524  
wide-ranging, III-522  
pulse supply, high-voltage power supplies, IV-412  
pulse-dialing telephone, III-610  
pulse-position modulator, III-375  
pulse-width-to-voltage converters, III-117  
pulse-width modulators (PWM), IV-326  
brightness controller, III-307  
control, microprocessor selected, II-116  
modulator, III-376  
motor speed control, II-376, III-389  
multiplier circuit, II-264, III-214  
out-of-bounds detector, III-158  
proportional-controller circuit, II-21  
servo amplifier, III-379  
speed control/energy-recovering brake, III-380  
very short, measurement circuit, III-336  
pulse/tone dialer, single-chip, III-603  
pulsers, laser diode, III-311  
pump circuits  
controller, single chip, II-247  
positive input/negative output charge, I-418  
push switch, on/off, electronic, II-359  
push-pull power supply, 400V/60W, II-473  
pushbutton power control switch, IV-388  
PUT battery chargers, III-54  
PUT long-duration timer, II-675  
pyrometer, optical, I-654

## Q

Q-multipliers  
audio, II-20  
transistorized, I-566  
QRP CW transmitter, III-690  
QRP SWR bridge, III-336  
quad op amp, simultaneous waveform generator using, II-259  
quadrature oscillators, III-428  
square-wave generator, III-585  
quartz crystal oscillator, two-gate, III-136

quick-deactivating battery sensor, III-61

## R

- race-car motor/crash sound generator, III-578
- radar detectors, II-518-520, IV-441-442 one-chip, II-519
- radiation detectors, II-512-517 alarm, II-4 micropower, II-513 monitor, wideband, I-535 photomultiplier output-gating circuit, II-516 pocket-sized Geiger counter, II-514 radiation-hardened 125A linear regulator, II-468
- radio
- AM car-radio to short-wave radio converter, IV-500
  - AM demodulator, II-160
  - AM radio, power amplifier, I-77
  - AM radio, receivers, III-81, III-529, III-535
  - AM/FM, clock radio, I-543
  - AM/FM, squelch circuit, II-547, III-1
  - amateur radio, III-260, III-534, III-675
  - automotive, receiver for, II-525
  - clock, I-542
  - direction finder, radio signals, IV-148-149
  - FM (*see* FM transmissions)
  - portable-radio 3 V fixed power supplies, IV-397
  - radio beacon converter, IV-495
  - receiver, AM radio, IV-455
  - receiver, old-time design, IV-453
  - receiver, reflex radio receiver, IV-452
  - receiver, short-wave receiver, IV-454
  - receiver, TRF radio receiver, IV-452
- radio beacon converter, IV-495
- radio-control circuits
- audio oscillator, II-567, III-555
  - motor speed controller, I-576
  - phase sequence reversal by, II-438
  - oscillator, emitter-coupled, II-266
  - receiver/decoder, I-574
  - single-SCR design, II-361
- radioactivity (*see* radiation detectors)
- rain warning beeper, I-244, IV-189
- RAM, non-volatile CMOS, stand-by power supply, II-477
- ramp generators, I-540, II-521-523, III-525-527, IV-443-447 accurate, III-526 integrator, initial condition reset, III-527
- linear, II-270
- variable reset level, II-267
  - voltage-controlled, II-523
- ranging system, ultrasonic, III-697
- reaction timer, IV-204
- read-head pre-amplifier, automotive circuits, III-44
- readback system, disc/tape phase modulated, I-89
- readout, rf current, I-22
- receiver audio circuit, IV-31
- receivers and receiving circuits (*see also* transceivers; transmitters), II-524-526, III-528-535, IV-448-461
- 50kHz FM optical transmitter, I-361
  - acoustic-sound receiver, IV-311
  - AGC system for CA3028 IF amplifier, IV-458
  - AM, III-529, IV-455
  - AM, carrier-current circuit, III-81
  - AM, integrated, III-535
  - analog, I-545
  - ATV rf receiver/converter, 420 MHz, low-noise, IV-496, IV-497
  - car radio, capacitive diode tuning/electronic MW/LW switching, II-525
  - carrier current, I-143, I-146
  - carrier current, single transistor, I-145
  - carrier system, I-141
  - carrier-operated relay (COR), IV-461
  - CMOS line, I-546
  - data receiver/message demuxer, three-wire design, IV-130
  - fiber optic, 10 MHz, II-205
  - fiber optic, 50-Mb/s, III-181
  - fiber optic, digital, III-178
  - fiber optic, high-sensitivity, 30nW, I-270
  - fiber optic, low-cost, 100-M baud rate, III-180
  - fiber optic, low-sensitivity, 300nW, I-271
  - fiber optic, very high-sensitivity, low speed 3nW, I-269
  - FM, carrier-current circuit, III-80
  - FM, MPX/SCA, III-530
  - FM, narrow-band, III-532
  - FM, tuner, III-529
  - FM, zero center indicator, I-338
  - FSK data, III-533
  - ham-band, III-534
  - IF amplifier, IV-459
  - IF amplifier, preamp, 30 MHz, IV-460
  - IF amplifier/receiver, IV-459
  - infrared, I-342, II-292, III-274, IV-220-221
  - laser, IV-368
  - LF receiver, IV-451
  - line-type, digital data, III-534
  - line-type, low-cost, III-532
  - monitor for, II-526
  - optical, I-364, II-418
  - optical light receiver, IV-367, IV-368
  - PLL/BC, II-526
  - pulse-frequency modulated, IV-453
  - radio control, decoder and, I-574
  - radio receiver, AM, IV-455
  - radio receiver, old-time design, IV-453
  - radio receiver, reflex, IV-452
  - radio receiver, TRF, IV-452
  - regenerative receiver, one-transistor design, IV-449
  - RS-232 to CMOS, III-102
  - short-wave receiver, IV-454
  - signal-reception alarm, III-270
  - superheterodyne receiver, 3.5-to-10 MHz, IV-450-451
  - tracer, III-357
  - transceiver/mixer, HF, IV-457
  - ultrasonic, III-698, III-705
  - zero center indicator for FM, I-338
- recording amplifier, I-90
- recording devices (*see* tape-recorder circuits)
- rectangular-to-triangular waveform converter, IV-116-117
- rectifiers, II-527-528, III-536-537
- absolute value, ideal full wave, II-528
  - averaging filter, I-229
  - bridge rectifier, fixed power supplies, IV-398
  - broadband ac active, IV-271
  - diodeless, precision, III-537
  - full-wave, I-234, III-537, IV-328, IV-650
  - half-wave, I-230, II-528, IV-325
  - half-wave, fast, I-228
  - high-impedance precision, for ac/dc converter, I-164
  - inverter/rectifier, programmable op-amp design, IV-364
  - low forward-drop, III-471
  - precision, I-422
  - synchronous, phase detector-selector/balanced modulator, III-441
- redial, electronic telephone set with, III-606
- reference voltages, I-695, III-773-775
- $\pm 10V$ , I-696
  - $\pm 3V$ , I-696
  - $\pm 5V$ , I-696
  - 0- to 20 V power, I-694, I-699
- amplifier, I-36
- bipolar output, precision, I-698

- reference voltages (*cont.*)
  - dual tracking voltage, precision, I-698
  - high-stability, I-696
  - low-noise buffered, precision, I-698
  - low-power regulator, I-695
  - micropower 10 V, precision, I-697
  - square wave voltage, precision, I-696
  - standard cell replacement, precision, I-699
  - variable-voltage reference source, IV-327
- reference clock, three phase clock
  - from, II-101
- reference supply, low-voltage adjustable, I-695
- reflection oscillator, crystal-controlled, III-136
- reflectometer, I-16
- regenerative receiver, one-transistor design, IV-449
- registers, shift, I-380, II-366
  - driver, I-418
- regulated power supplies
  - 8-amp, II-461
  - 12 to 14V at 3 A, II-480
  - + 15V 1-A, III-462
  - 15V 1-A, III-463
  - split power supplies, I-492
- regulators (*see voltage regulators*)
- rejection filter, I-283
- relaxation oscillator, III-430, IV-376
- relays, II-529-532, IV-471-475
  - ac, optically coupled, III-418
  - ac, photon coupler in, II-412
  - ac, solid-state latching, IV-472
  - audio operated, I-608
  - bidirectional switch, IV-472
  - capacitance, I-130
  - carrier operated, I-575
  - carrier-operated relay (COR), IV-461
  - dc latching, optically coupled, III-417
  - delay-off circuit, IV-473
  - driver, delay and controls closure time, II-530
  - light-beam operated on/off, I-366
  - monostable relay, low-consumption design, IV-473
  - optically coupled, ac, III-418
  - optically coupled, dc latching, III-417
  - optoisolator, IV-475
  - polarity-protection for power supplies, IV-427
  - rf-actuated, III-270
  - ringer, telephone, III-606
  - solid-state, III-569-570, IV-474
  - solid-state, 10 A 25 Vdc, I-623
  - solid-state, ac, III-570
  - solid-state, ac, latching, IV-472
  - solid-state, dc, normally open/closed, III-412
  - solid-state, integrated, II-408
  - solid-state, light-isolated, I-365
  - solid-state, ZVS, antiparallel SCR output, III-416
  - sound actuated, I-576, I-610
  - telephone, I-631
  - time delayed, I-663
  - time delayed, ultra-precise, I-219
  - tone actuated, I-576
  - TR circuit, II-532
  - triac, contact protection, II-531
- remote control devices
  - amplifier, I-99
  - carrier, current, I-146
  - drop-voltage recovery for long-line systems, IV-328
  - extender, infrared, IV-227
  - fax/telephone switch, IV-552-553
  - infrared circuit, IV-224
  - lamp or appliance, I-370
  - loudspeaker via IR link, I-343
  - on/off switch, I-577
  - ringer, telephone, III-614
  - sensor, temperature transducer, I-649
  - servo system, I-575
  - telephone monitor, II-626
  - temperature sensor, II-654
  - tester, infrared, IV-228
  - thermometer, II-659
  - transmitter/receiver, IR, I-342
  - video switch, IV-619-621
- repeaters
  - European-type, tone burst generator for, III-74
  - fiber optic link, I-270
  - telephone, III-607
- repeater beeper, I-19
- reset buttons
  - child-proof computer reset, IV-107
  - power-on, II-366
  - protection circuit for computer, IV-100
- resistance/continuity meters, II-533, III-538-540
  - cable tester, III-539
  - continuity tester, III-540
  - ohmmeter, linear, III-540
  - resistance-ratio detector, II-342
  - single chip checker, II-534
- resistance measurement, low parts count ratiometric, I-550
- resistance-to-voltage converter, I-161-162
- resistor multiplier, II-199
- resonator oscillator, varactor tuned 10 MHz ceramic, II-141
- restorer, video dc, III-723
- reverb effect, analog delay line, IV-21
- reverb system, stereo, I-602, I-606
- reversing motor drive, dc control signal, II-381
- rf amplifiers, II-537-549, III-542-547, IV-476-493
  - 1 W, 2.3 GHz, II-540
  - 10 W, 225-400 MHz, II-548
  - 10 dB-gain, III-543
  - 2- to 30 MHz, III-544
  - 4 W amp for 900 MHz, IV-477
  - 5 W 150-MHz, III-546
  - 5 W power, II-542
  - 6-meter kilowatt, II-545
  - 6-meter preamp, 20dB gain and low NF, II-543
  - 60 W 225-400 MHz, III-547
  - 125 W, 150 MHz, II-544
  - 500 MHz, IV-491
  - 1,296 MHz, IV-486
  - 1,500 W, IV-478-479
  - AGC, wideband adjustable, III-545
  - broadcast-band, III-264, II-546
  - broadcast-band booster, IV-487
  - buffer amplifier with modulator, IV-490
  - cascode amplifier, IV-488
  - common-gate, 450-MHz, III-544
  - isolation amplifier, II-547
  - linear amplifier, 903 MHz, IV-484-485
  - linear amplifier, 6-m, 100 W, IV-480-481
  - linear amplifier, ATV, 10-to-15 W, IV-481
  - low distortion 1.6 to 30MHz SSB driver, II-538
  - meter-driver, 1-MHz, III-545
  - MOSFET rf-amp stage, dual-gate, IV-489
  - power, 600 W, I-559
  - power amp, 1296-MHz solid-state, III-542
  - preselector, JFET, IV-485
  - preselector, JFET, double-tuned, IV-483
  - preselector, varactor-tuned, IV-488
  - UHF-TV preamp, III-546
  - UHF TV-line amplifier, IV-482, IV-483
  - wideband amplifier, IV-479, IV-489, IV-490
  - wideband amplifier, HF, IV-492
  - wideband amplifier, JFET, IV-493
  - wideband amplifier, MOSFET, IV-492
  - wideband amplifier, two-CA3100 op

- amp design, IV-491
- rf circuits
  - attenuator, IV-322
  - burst generators, portable, III-73
  - converters, IV-494-501
  - converters, ATV receiver/converter, 420 MHz, low-noise, IV-496, IV-497
  - converters, radio beacon converter, IV-495
  - converters, receiver frequency-converter stage, IV-499
  - converters, SW converter for AM car radio, IV-500
  - converters, two-meter, IV-498
  - converters, up-converter, TVRO subcarrier reception, IV-501
  - converters, VLF converter, IV-497
  - converters, WWV-to-SW converter, IV-499
  - converters, receiving converter, 220 MHz, IV-500
  - current readout, I-22
  - detector, II-500
  - detector probe, IV-433
  - genie, II-421
  - measurement/test circuits, IV-297-303
  - modulators, I-436, III-372, III-374
  - modulators, double sideband suppressed carrier, II-369
  - oscillators, I-550-551, I-572
  - oscillators, 5 MHz VFO, II-551
  - oscillators, transmitter and, 27MHz and 49MHz, I-680
  - output indicator, IV-299
  - power meter, I-16
  - power meter, sidetone oscillator, I-24
  - power meter, switch, III-592
  - power meter, wide-range, III-332
  - probe, I-523, III-498, III-502
  - signal tracer probe, audio, I-527
  - sniffer, II-210
  - switch, low-cost, III-361
  - VHF/UHF diode switch, IV-544
  - voltmeter, I-405, III-766
- RGB video amplifier, III-709
- RGB-composite video signal converter, III-714
- RGB-to-NTSC converter, IV-611
- ring counters
  - 20 kHz, II-135
  - incandescent lamps, I-301
  - low cost, I-301
  - pulse circuit, low-power, IV-437
- SCR, III-195
- variable timing, II-134
- ring detectors

- low line loading, I-634
- telephone, II-623, III-619
- telephone, auto-answer, I-635
- telephone, optically interfaced, III-611
- ring-around flasher, LED, III-194
- ringers, telephone, I-628, IV-556
  - extension-phone ringer, IV-561
  - high isolation, II-625
  - multi-tone, remote programmable, II-634
  - musical, II-619
  - piezoelectric, I-636
  - plug-in, remote, II-627
  - relay, III-606
  - remote, II-627, III-614, IV-562
  - silencer, IV-557
  - tone, I-627, I-628, II-630, II-631
- ripple suppressor, IV-175
  - fixed power supplies, IV-396
- RLC oscillator, III-423
- rms-to-dc converter, I-167, II-129
  - thermal, 50-MHz, III-117
- road ice alarm, II-57
- robots
  - eyes for, II-327
  - light-seeking, II-325
- rocket launcher, II-358
- rotation detector, II-283
- roulette, electronic, II-276, IV-205
- RS-232 interface
  - CMOS-to, line receiver, III-102
  - datasector, automatic, III-97
  - drive circuit, low-power, III-175
  - LED circuit, III-103
  - line-driven CMOS circuits, IV-104
- RS flip-flop, I-395
- RTD signal conditioners
  - 5V powered linearized platinum, II-650
  - precision, linearized platinum, II-639
- RTTY machines, fixed current supply, IV-400
- rumble filters, I-297, III-192, III-660, IV-170, IV-175

## S

- S meter, III-342
- safe area protection, power amplifier with, III-459
- safety flare, II-608
- Sallen-Key filters
  - 500 Hz bandpass, I-291
  - low-pass, active, IV-177
  - low-pass, equal component, I-292
  - low-pass, second order, I-289
- sample-and-hold circuits, I-590, II-552-

- 559, III-548-553, IV-502-503
- x 1000, I-589
- charge-compensated, II-559
- fast and precise, II-556
- filtered, III-550
- frequency-to-voltage conversion, IV-194
- high-accuracy, I-590
- high-performance, II-557
- high-speed amplifier, I-587
- high-speed, I-587-588, I-590, III-550
- infinite, II-558
- inverting, III-552
- JFET, I-586
- low-drift, I-586
- offset adjustment for, I-588
- three-channel multiplexer with, III-396
- track-and-hold, III-552
- track-and-hold, basic, III-549
- sampling circuit, hour time delay, II-668
- saturated standard cell amplifier, II-296
- sawtooth waves
  - converter, IV-114
  - generator, digital design, IV-444, IV-446
  - oscillator modulator, III-373
  - pulse generator and, III-241
- SCA decoder, I-214, II-166, II-170
- SCA demodulator, II-150, III-565
- scale, digital weight, I-398
- scaler, inverse, I-422
- scanner, bar codes, III-363
- Schmitt triggers, I-593, III-153
- crystal oscillator, I-181
- programmable hysteresis, I-592
- TTL-compatible, II-111
- without hysteresis, I-592

SCR circuits

- annunciator, self-interrupting load, IV-9
- chaser, III-197
- crowbar, II-496
- flasher, III-197
- flip-flop, II-367
- gas/smoke detector, III-251
- preregulator, II-482

proximity alarm, III-517

- radio control using, II-361
- relaxation flasher, II-230
- relaxation oscillator, III-430
- ring counter, III-195
- tester, III-344
- time delay circuit with, II-670
- triggering series, optically coupled, III-411

scramblers, audio (*see also* sound generators; voice-activated circuits), IV-25-27

- scramblers, audio (*cont.*)  
 telephone, II-618  
 voice scrambler/descrambler, IV-26  
 voice scrambler/disguiser, IV-27
- scratch filters, III-189, IV-175  
 LM287 in, I-297
- second-audio program adapter, III-142
- security circuits, I-4, III-3-9  
 automotive security system, I-5, IV-49-56  
 home system, I-6, IV-87  
 infrared, wireless, IV-222-223
- sense-of-slope tilt meter, II-664
- sensors (*see also* alarms; control circuits; detectors; indicators; monitors)  
 0-50 C, four-channel temperature, I-648  
 air-flow sensor, thermistor bridge, IV-82  
 ambient light ignoring optical, III-413  
 capacitive, alarm for, III-515  
 cryogenic fluid level, I-386  
 differential temperature, I-655  
 humidity, II-285-287, III-266-267  
 IC temperature, I-649  
 isolated temperature, I-651  
 light level, I-367  
 light, back-biased GaAs LED, II-321  
 logarithmic light, I-366  
 magnetic current, low-power, III-341  
 motion, IV-341-346  
 motion, unidirectional, II-346  
 nanoampere, 100 megohm input impedance, I-203  
 optical interruption sensor, IV-366  
 photodiode amplifier for, II-324  
 precision temperature transducer with remote, I-649  
 proximity, II-505, III-514-518, IV-341-346  
 remote, loop transmitter for, III-70  
 remote temperature, I-654  
 self-biased proximity, detected changing field, I-135  
 short-circuit sensor, computer remote data lines, IV-102  
 simple differential temperature, I-654  
 temperature (*see also* temperature sensor), II-645, I-648, I-657  
 temperature, III-629-631, III-629  
 voltage regulators, LM317 design, IV-466  
 voltage sensor, power supplies, IV-423  
 voltage-level, III-770  
 water level, I-389  
 zero crossing detector with temperature, I-733
- sequence indicator, phase, I-476
- sequencer, pseudorandom, III-301
- sequential flasher, II-233  
 ac, II-238  
 automotive turn signals, I-109  
 sequential timer, III-651
- series connectors, telephone, III-609
- servo amplifiers  
 400 Hz, II-386  
 bridge type ac, I-458  
 dc, I-457
- servo motor drive amplifier, II-384
- servo systems  
 controller, III-384  
 remote control, I-575
- shaper, sine wave, II-561
- shift registers, I-380, II-366  
 driver for, I-418
- shifter, phase (*see* phase shifter)
- ship siren, electronic, II-576
- short-circuit proof lamp driver, II-310
- shortwave transmissions  
 converters, III-114  
 converter, AM car radio, IV-500  
 FET booster, I-561  
 receiver, IV-454
- short-circuit sensor, computer remote data lines, IV-102
- shunt, multimeter shunt, IV-293
- shutoff, automatic, battery-powered projects, III-61
- shutter speed tester, II-445
- sidetone oscillator, rf-powered, I-24
- signal amplifiers, audio, IV-34-42
- signal attenuator, analog, microprocessor-controlled, III-101
- signal combiner, III-368
- signal conditioners, IV-649  
 5V powered linearized platinum RTD, II-650  
 bridge circuit, strain gauge, II-85  
 linearized RTD, precision design, II-639  
 LVDT, II-338  
 thermally stabilized PIN photodiode, II-330
- signal distribution amplifier, I-39
- signal generators (*see also* function generators; sound generators; waveform generators)  
 AM broadcast-band, IV-302  
 AM/IF, 455 kHz, IV-301  
 high-frequency, II-150  
 square-wave, III-583-585  
 staircase, III-586-588  
 two-function, III-234
- signal injectors, III-554-555
- signal sources, crystal-controlled, II-143
- signal tracer, three-in-one set: logic probe, signal tracer, injector, IV-429
- signal-strength meters, III-342, IV-166
- signal-supply, voltage-follower amplifiers, III-20
- simulated inductor, II-199
- simulators  
 EKG, three-chip, III-350  
 VOR signals, IV-273
- sine-to-square wave converter, IV-120
- sine-wave descrambler, II-163
- sine-wave generators, square-wave and, tunable oscillator, III-232
- sine-wave oscillators, I-65, II-560-570, III-556-559, III-560, IV-504-513  
 555 used as RC audio oscillator, II-567  
 adjustable, II-568  
 audio, II-562  
 audio, generator, III-559  
 audio, simple generator for, II-564  
 generator, IV-505  
 generator, LC sine-wave, IV-507  
 generator, LF, IV-512  
 generator, pure sine-wave, IV-506  
 generator, VLF audio tone, IV-508  
 generators, 60 Hz, IV-507  
 LC oscillator, low-frequency, IV-509  
 low distortion, II-561  
 one-IC audio generator, II-569  
 phase-shift, audio ranging, IV-510  
 programmable-frequency, III-424  
 relaxation, modified UJT for clean audio sinusoids, II-566  
 sine wave shaper, II-561  
 sine/square wave TTL oscillator, IV-512  
 two-tone generator, II-570  
 two-transistor design, IV-508  
 variable, super low-distortion, III-558  
 very-low distortion design, IV-509  
 Wien bridge, I-66, I-70, II-566, IV-511  
 Wien bridge, CMOS chip in, II-568  
 Wien-bridge, low-distortion, thermal stable, III-557  
 Wien-bridge, single-supply, III-558  
 Wien-bridge, three-decade 15 Hz to 15 kHz, IV-510  
 Wien-bridge, very-low distortion, IV-513
- sine-wave output buffer amplifier, I-126
- sine-wave to square-wave converter, I-170
- sine/cosine generator, 0.1 to 10 kHz, II-260
- sine/square wave oscillators, I-65  
 easily tuned, I-65  
 TTL design, IV-512

- tunable, III-232
- single-pulse generator, II-175
- single-sideband (SSB) communications
  - CW/SSB product detector, IV-139
  - driver, low distortion 1.6 to 30MHz, II-538
  - generators, IV-323
  - transmitter, crystal-controlled LO for, II-142
- sirens (*see also* alarms; sound generators), I-606, II-571, III-560-568
- alarm using, II-572, II-573, IV-514-517
- 7400, II-575
- adjustable-rate programmable-frequency, III-563
- electronic, III-566, IV-515, IV-517
- generator for, II-572
- hee-haw, III-565, II-578
- high power, II-578
- linear IC, III-564
- low-cost design, IV-516
- multifunction system for, II-574
- ship, electronic, II-576
- sonic defender, IV-324
- Star Trek red alert, II-577
- tone generator, II-573
- toy, II-575
- TTL gates in, II-576
- two-state, III-567
- two-tone, III-562
- varying frequency warning alarm, II-579
- wailing, III-563
- warble-tone siren, 6 W, IV-516
- warble-tone siren, alternate tone, IV-515
- whooper, IV-517
- yelp oscillator, II-577, III-562
- slave-flash trigger, IV-380, IV-382
- slide timer, III-448
- slide-show timer, III-444
- sliding tone doorbell, II-34
- smart clutch, auto air conditioner, III-46
- smoke alarms and detectors, II-278, III-246-253
  - gas, I-332
  - ionization chamber, I-332-333
  - line-operated, IV-140
  - operated ionization type, I-596
  - photoelectric, I-595, I-596
- sniffers (*see also* detectors; monitors)
  - heat, electronic, III-627
  - rf, II-210
- snooper, FM, III-680
- socket debugger, coprocessor, III-104
- soldering station, IR-controlled, IV-225
- soil moisture meter, III-208
- solar-powered battery charger, II-71
- solar-triggered switch, III-318
- solenoid drivers, III-571-573
  - 12-V latch, III-572
  - hold-current limiter, III-573
  - power-consumption limiter, III-572
- solid-state devices
  - ac relay, III-570
  - electric fence charger, II-203
  - high-voltage supply, remote adjustable, III-486
  - relays, III-569-570
  - stepping switch, II-612
  - switch, line-activated, telephone, III-617
- sonic defender, IV-324
- sound-activated circuits (*see* sound-operated circuits)
- sound generators (*see also* burst generators; function generators; sirens; waveform generators), I-605, II-585-593, III-559-568, III-575, IV-15-24, IV-518-524
  - amplifier, voltage-controlled, IV-20
  - amplifier/compressor, low-distortion, IV-24
  - allophone, III-733
  - audio tone generator, VLF, IV-508
  - autodrum, II-591
  - bagpipes, electronic, III-561, IV-521
  - beat-frequency, IV-371
  - bird chirp, I-605, II-588, III-577
  - bongos, II-587
  - chime generator, II-604
  - chime generator, single-chip design, IV-524
  - chug-chug, III-576
  - dial tone, I-629, III-609
  - ditherizing circuit, digital audio use, IV-23
  - doorbell, musical tones, IV-522
  - doubler, audio-frequency doubler, IV-16-17
  - echo and reverb, analog delay line, IV-21
  - electronic, III-360
  - envelope generator/modulator, II-601
  - equalizer, IV-18
  - fader, IV-17
  - frequency-shift keyer, tone-generator test circuit, I-723
  - funk box, II-593
  - fuzz box, III-575
  - guitar compressor, IV-519
  - harmonic generator, I-24, IV-649
  - high-frequency signal, III-150
  - hold for telephone, II-623
  - melody generator, single-chip design, IV-520
- music maker circuit, IV-521
- musical chimes, I-640
- musical envelope, modulator, I-601, IV-22
- noise generators, I-467, I-468, I-469, IV-308
- octave-shifter for musical effects, IV-523
- one-IC design, II-569
- phasor sound generator, IV-523
- pink noise, I-468
- portable, I-625
- race-car motor/crash, III-578
- run-down clock for games, IV-205
- sound effects, III-574-578
- steam locomotive whistle, II-589, III-568
- steam train/prop plane, II-592
- stereo system, derived center-channel, IV-23
- super, III-564
- synthesizer, II-599
- telephone call-tone generator, IV-562
- telephone ringer, II-619
- tone generator, burst, I-604
- tone generator, portable design, I-625
- Touchtone dial-tone, telephone, III-609
- train chuffer, II-588
- tremolo circuits, III-692-695, IV-589
- twang-twang, II-592
- two-tone, II-570
- ultrasonic sound source, IV-605
- unusual fuzz, II-590
- warbling tone, II-573
- white noise, IV-201
- very-low frequency, I-64
- vocal eliminator, IV-19
- voice circuits, III-729-734
- waa-waa circuit, II-590
- white noise, IV-201
- sound-level meters, III-346, IV-305, IV-307
  - meter/monitor, telephone, III-614
- sound-operated circuits (*see also* ultrasonic circuits; voice-operated circuits), II-580-584, III-579-580, IV-525-528
  - amplifier, gain-controlled, IV-528
  - color organ, II-583, II-584
  - decoder, III-145
  - flash triggers, I-481, II-449, IV-382
  - lights, I-609
  - noise clipper, I-396
  - relay, I-608, I-610
  - switch, II-581, III-580, III-600, III-601, IV-526-527
  - switch, ac, II-581

- sound-operated circuits (*cont.*)
  - switch, two-way, I-610
  - switch, voice-operated, III-580
  - switch, voice-activated, microphone-controlled, IV-527
  - speech activity detector, telephone, III-615
  - voice-operated switch, III-580
  - vox box, II-582
- sources (*see* current sources; voltage sources)
- source follower, photodiode, III-419
- SPDT switch, ac-static, II-612
- space war, I-606
- speaker systems
  - FM carrier current remote, I-140
  - hand-held transceiver amplifiers, III-39
  - overload protector for, II-16
  - wireless, IR, III-272
- speakerphone, II-611, III-608
- speech-activity detector, II-617, III-619
- speech compressor, II-15
- speech filter
  - 300 Hz-3kHz bandpass, I-295
  - second-order, 300-to-3,400 Hz, IV-174
  - two-section, 300-to-3,000 Hz, IV-174
- speech network, II-633
- speed alarm, I-95
- speed controllers, I-450, I-453, II-378, II-379, II-455
  - back EMF PM, II-379
  - cassette-deck motor speed calibrator, IV-353
  - closed-loop, III-385
  - fans, automatic, III-382
  - dc motors, I-452, I-454, III-377, III-380
  - dc motor, direction control and, I-452
  - dc variable, fiber optic, II-206
  - feedback, I-447
  - fixed, III-387
  - high-efficiency, III-390
  - high-torque motor, I-449
  - light-activated/controlled, IV-247
  - load-dependent, I-451
  - model trains and/or cars, I-455, IV-338-340
  - motor, I-450, I-453
  - motor, dc, reversible, driver and, III-388
  - motor, high-efficiency, III-390
  - PWM, II-376
  - PWM, energy-recovering brake, III-380
  - radio-controlled, I-576
  - series-wound motors, I-448, II-456
  - shunt-wound motors, II-456
- stepper motors, direction and speed control, IV-350
- switched-mode, III-384
- tachless, III-386
- tachometer, II-378, II-389
- tachometerless, IV-349
- tools and appliances, I-446
- universal motors, I-457
- universal motors, load-dependent, II-451
- speed warning device, I-96, I-101
- speedometers, bicycle, IV-271, IV-282
- splitters, III-581-582
  - battery, III-66
  - phase, precision, III-582
  - precision phase, I-477
  - voltage, III-738, III-743
  - wideband, III-582
- squarer, precision, I-615
- square-wave generators, II-594-600, III-583-585, IV-529-536
  - 1 kHz, IV-536
  - 2 MHz using two TTL gates, II-598
  - 555 timer, II-595
  - astable circuit, IV-534
  - astable multivibrator, II-597
  - CMOS 555 astable, true rail-to-rail, II-596
  - duty-cycle multivibrator, III-50-percent, III-584
  - four-decade design, IV-535
  - high-current oscillator, III-585
  - line frequency, II-599
  - low-frequency TTL oscillator, II-595
  - multiburst generator, II-88
  - multivibrator, IV-536
  - oscillator, II-597, IV-532, IV-533
  - oscillator, with frequency doubled output, II-596
  - phase-tracking, three-phase, II-598
  - pulse extractor, III-584
  - quadrature-outputs oscillator, III-585
  - sine-wave, tunable oscillator, III-232
  - three-phase, II-600
  - tone-burst generator, single timer IC, II-89
  - triangle-wave, III-239
  - triangle-wave, precision, III-242
  - triangle-wave, programmable, III-225
  - triangle-wave, wide-range, III-242
  - TTL, LSTTL, CMOS designs, IV-530-532
  - variable duty-cycle, IV-533
  - variable-frequency, IV-535
- square-wave oscillators, I-613-614, II-597, II-616, IV-532, IV-533
  - 0.5 Hz, I-616
  - 1kHz, I-612
- square-to-sine wave converters, III-118
- squelch circuits, II-394
  - AM/FM, I-547
  - voice-activated circuits, IV-624
- squib firing circuits, II-357
- stabilizer
  - fixed power supplies, CMOS diode network, IV-406
  - fixed power supplies, output stabilizer, IV-393
- staircase generators, (*see also* waveform generators), II-601-602, III-586-588, IV-443-447
  - UA2240, III-587
- stand-by power supply, non-volatile CMOS RAMs, II-477
- standard, precision calibration, I-406
- standard-cell amplifier, saturated, II-296
- standing wave ratio (SWR) meter, IV-269
  - power meter, I-16
  - QRP bridge, III-336
  - warning indicator, I-22
- Star Trek red alert siren, II-577
- start-and-run motor circuit, III-382
- state-of-charge indicator, lithium battery, II-78
- state-variable filters, II-215, III-189
  - multiple outputs, III-190
  - second-order, 1kHz, Q/10, I-293
  - universal, I-290
- steam locomotive sound effects, II-589, II-592, III-568
- static detector, IV-276
- step-up switching regulator, 6V battery, II-78
- step-up/step-down dc-dc converters, III-118
- stepping motor driver, II-376, III-390
- stepping switch, solid state, II-612
- stereo circuits
  - amplifier, 12-V/20-W, IV-29
  - amplifier, Av/200, I-77
  - amplifier, bass tone control, I-670
  - audio-level meter, IV-310
  - audio-power meter, IV-306
  - balance circuit, II-603-605
  - balance meter, II-605, I-618-619
  - balance tester, II-604
  - decoder, frequency division multiplex, II-169
  - decoder, time division multiplex, II-18
  - decoder, TV-stereo, II-167
  - demodulator, II-159
  - demodulator, FM, I-544
  - derived center-channel system, IV-23
  - mixer, four-input, I-55
  - power meter, III-331

preamplifier, II-43, II-45  
 reception indicator, III-269  
 reverb systems, I-602, I-606  
 reverb systems, gain control in, II-9  
 TV-stereo decoder, II-167  
 stimulator, constant-current, III-352  
 stimulus isolator, III-351  
 stop light, garage, II-53  
 strain gauges  
   bridge excitation, III-71  
   bridge signal conditioner, II-85  
   instrumentation amplifier, III-280  
 strobe circuits, II-606-610  
   disco-, II-610  
   high-voltage power supplies, IV-413  
   safety flare, II-608  
   simple, II-607  
   tone burst generator, II-90  
   trip switch, sound activated, I-483  
   variable strobe, III-589-590  
 stud finder, III-339  
 subharmonic frequencies, crystal-stabilized IC timer, II-151  
 subtractor circuit, III-327  
 successive-approximation A/D converter, II-24, II-30  
 summing amplifiers, III-16  
   precision design, I-36  
   video, clamping circuit and, III-710  
 sun tracker, III-318  
 superheterodyne receiver, 3.5-to-10 MHz, IV-450-451  
 supply rails, current sensing in, II-153  
 suppressed-carrier, double-sideband, modulator, III-377  
 sweep generators  
   10.7 MHz, I-472  
   add-on triggered, I-472  
   oscilloscope-triggered, III-438  
 switches and switching circuits, II-611-612, III-591-594, IV-537  
   ac switch, battery-triggered, IV-387  
   analog, buffered, DTL-TTL-controlled, I-621  
   analog, differential, I-622  
   analog, high-toggle/high-frequency, I-621  
   analog, one MOSPOWER FET, III-593  
   antenna selector, electronic, IV-538-539  
   audio/video switcher circuit, IV-540-541  
   auto-repeat switch, bounce-free, IV-545  
   bidirectional relay switch, IV-472  
   bistable switch, mechanically controlled, IV-545  
   contact, I-136  
   dc static, II-367  
   debouncer, III-592  
   debouncer, computer switches, IV-105  
   debouncer, computer switches, auto-repeat, IV-106  
   debouncer, computer switches, flip-flop, IV-108  
   delay, auto courtesy light, III-42  
   DTL-TTL controlled buffered analog, I-621  
   fax/telephone switch, IV-552-553  
   FET dual-trace (oscilloscope), II-432  
   Hall-effect, III-257, IV-539  
   high-frequency, I-622  
   high-side power control switch, 5 V supply, IV-384, IV-385  
   infrared-activated, IV-345  
   latching, SCR-replacing, III-593  
   light-operated, II-320, III-314  
   light-operated, adjustable, I-362  
   MOSFET power control switch, IV-386  
   on/off inverter, III-594  
   on/off switch, IV-543  
   on/off switch, transistorized op-amp on/off switch, IV-546  
   optically coupled, high-voltage ac, III-408  
   optically coupled, zero-voltage, solid-state, III-410  
   over-temperature switch, IV-571  
   photocell memory, ac power control, I-363  
   photoelectric, II-321  
   photoelectric, ac power, II-326  
   photoelectric, synchronous, II-326  
   proximity, III-517  
   push on/off, II-359  
   pushbutton power control switch, IV-388  
   remote, on/off, I-577  
   remote, ring extender, I-630  
   rf, low-cost, III-361  
   rf, power switch, III-592  
   satellite TV audio switcher, IV-543  
   solar-triggered, III-318  
   solid-state stepping, II-612  
   sonar transducer/, III-703  
   sound-activated, II-581, III-580, III-600, III-601, IV-526-527  
   sound-activated, two-way, I-610  
   speed, I-104  
   SPDT, ac-static, II-612  
   switching controller, III-383  
   temperature control, low-power, zero-voltage, II-640  
   tone switch, narrowband, IV-542  
   touch switches (*see* touch switches)  
   touchomatic, II-693  
   triac, inductive load, IV-253  
   triac, zero point, II-311  
   triac, zero voltage, I-623  
   two-channel, I-623  
   ultrasonic, I-683  
   under-temperature switch, IV-570  
   VHF/UHF diode rf switch, IV-544  
   video, IV-618-621  
   video, automatic, III-727  
   video, general purpose, III-725  
   video, high-performance, III-728  
   video, very-high off isolation, III-719  
   voice-operated, I-608, III-580  
   voice-operated, microphone-controlled, IV-527  
   zero crossing, I-732  
   zero point, I-373, II-311  
   zero-voltage switching, closed contact half-wave, III-412  
   zero-voltage switching, solid-state, optically coupled, III-410  
   zero-voltage switching, triac design, I-623  
 switched-mode power supplies, II-470, III-458  
   50 W, off-line, III-473  
   100 kHz, multiple-output, III-488  
   converter, +50V push pull, I-494  
 switched light, capacitance, I-132  
 switching inverter, 500 kHz, 12 V systems, II-474  
 switching power amplifier, I-33  
 switching regulators  
   3 A, III-472  
   5 V, 6 A, 25 uHz, separate ultra-stable reference, I-497  
   6 A variable output, I-513  
   200 kHz, I-491  
   application circuit, 3W, I-492  
   fixed power supplies, 3 A, IV-408  
   high-current inductorless, III-476  
   low-power, III-490  
   multiple output MPU, I-513  
   positive, I-498  
   step-down, I-493  
   step-up, 6V battery, II-78  
 switching/mixing, silent audio, I-59  
 sync separators  
   single-supply wide-range, III-715  
   video circuits, IV-616  
 synthesizers  
   four-channel, I-603  
   frequency, programmable voltage-controlled, II-265  
   music, I-599

**T**  
 tachometers, I-100, I-102, II-175, III-335, III-340, III-595-598

- tachometers (*cont.*)
- analog readout, IV-280
  - calibrated, III-598
  - closed-loop, feedback control, II-390
  - digital, II-61, III-45, IV-268-269, IV-278
  - frequency counter, I-310
  - gasoline engine, I-94
  - low-frequency, III-596
  - minimum component, I-405
  - motor speed control, II-378, II-389
  - optical pick-up, III-347
  - set point, III-47
- tandem dimmer, II-312
- tap, telephone, III-622
- tape-recorder circuits, I-21, I-419, III-599-601, IV-547-548
- amplifier, I-90
  - amplifier, playback mode, IV-36
  - audio-powered controller, IV-548
  - automatic tape-recording switch, I-21, II-21
  - automotive-battery power circuit, IV-548
  - cassette-deck motor speed calibrator, IV-353
  - extended-play circuit, III-600
  - flat-response amplifier, III-673
  - interface for, II-614
  - playback amplifier, III-672, IV-36
  - position indicator/controller, II-615
  - preamplifier, I-90
  - sound-activated switch, III-600, III-601
  - starter switch, telephone-activated, I-632
  - telephone-activated starter switch, I-632, II-622, III-616
  - telephone-to-cassette interface, III-618
- telemetry demodulator, I-229
- telephone-related circuits, II-616-635, III-602-622, IV-549-564
- amplifier, III-621, IV-560
  - answering machine beeper, IV-559
  - auto answer and ring indicator, I-635
  - automatic recording device, II-622
  - blinking phone light monitor, II-624, II-629
  - call-tone generator, IV-562
  - cassette interface, III-618
  - decoder, touch-tone, IV-555
  - dial pulse indicator, III-613
  - diald-phone number vocalizer, III-731
  - dialer, pulse/tone, single-chip, III-603
  - dual tone decoding, II-620
  - duplex audio link, IV-554
  - duplex line amplifier, III-616
  - eavesdropper, wireless, III-620
  - fax-machine switch, remote-controlled, IV-552-553
  - flasher, phone-message, IV-556
  - flasher, tell-a-bell, IV-558
  - flasher, visual ring indicator, IV-559, IV-561
  - frequency and volume controller, II-623
  - hands-free telephone, III-605
  - handset encoder, I-634, III-613
  - hold button, II-628, III-612
  - in-use indicator, II-629, IV-560, IV-563
  - intercom, IV-557
  - light for, II-625
  - line interface, autopatch, I-635
  - line monitor, I-628
  - message-taker, IV-563
  - musical hold, II-623
  - musical ringer, II-619
  - night light, telephone controlled, III-604
  - off-hook indicator, I-633
  - optoisolator status monitor, I-626
  - parallel connection, III-611
  - piezoelectric ringer, I-636
  - power switch, ac, IV-550
  - pulse-dialing, III-610
  - recording calls, I-632, III-616
  - recording calls, auto-record switch, IV-558
  - recording calls, telemonitor, IV-553
  - redial, III-606
  - relay, I-631
  - remote monitor for, II-626
  - repeater, III-607
  - repertory dialer, line powered, I-633
  - ring detector, II-623, III-619, IV-564
  - ring detector, optically interfaced, III-611
  - ringers, IV-556
  - ringers, extension-phone ringer, IV-561
  - ringers, high isolation, II-625
  - ringers, multi-tone, remote programmable, II-634
  - ringers, musical, II-619
  - ringers, piezoelectric, I-636
  - ringers, plug-in, remote, II-627
  - ringers, relay, III-606
  - ringers, remote, II-627, III-614, IV-562
  - ringers, tone, I-627, I-628, II-630, II-631
  - scrambler, II-618
  - series connection, III-609
  - silencer, IV-557
  - sound level meter monitor, III-614
  - speaker amplifier, IV-555
  - speakerphone, II-632, III-608
  - speech activity detector, II-617, III-615
  - speech network, II-633
  - status monitor using optoisolator, I-626
  - switch, solid-state, line-activated, III-617
  - tap, III-622
  - tape-recorder starter controlled by, I-632
  - toll-totalizer, IV-551
  - tone-dialing, III-607
  - tone ringers, I-627, I-628, II-630, II-631
  - Touchtone generator, III-609
  - touch-tone decoder, IV-555
  - vocalizer, diald-phone number, III-731
- television-related circuits (*see also* video circuits)
- amplifier, audio, III-39
  - amplifier, IF detector, MC130/MC1352, I-688
  - amplifier, IF/FM IF, quadrature, I-690
  - amplifier, RF, UHF TV-line amplifier, IV-482, IV-483
  - audio/video switcher circuit, IV-540-541
  - automatic turn-off, I-577
  - cross-hatch generator, III-724
  - data interface, TTL oscillator, II-372
  - decoder, stereo TV, II-167
  - IF detector, amplifier, MC130/MC1352, I-688
  - modulators, I-439, II-433, II-434
  - preamplifier, UHF, III-546
  - rf up-converter for TVRO subcarrier reception, IV-501
  - satellite TV audio switcher, IV-543
  - stereo-sound decoder, II-167
  - transmitter, III-676
  - transmitter, amateur TV, IV-599
- temperature-related circuits (*see also* thermometers), IV-565-572
- alarms, II-4, II-643
  - alarms, adjustable threshold, II-644
  - automotive temperature indicator, II-56, IV-48
  - automotive water-temperature gauge, IV-44
  - Centigrade thermometer, II-648
  - control circuits, I-641-643, II-636-644, III-623-628, IV-567
  - control circuits, defrost cycle, IV-566
  - control circuits, heater element, II-642

control circuits, heater protector, servo-sensed, III-624

control circuits, heat sniffer, electronic, III-627

control circuits, liquid-level monitor, II-643

control circuits, low-power, zero-voltage switch, II-640

control circuits, piezoelectric fan-based, III-627

control circuits, proportional, III-626

control circuits, signal conditioners, II-639

control circuits, single setpoint, I-641

control circuits, thermocoupled, IV-567

control circuits, zero-point switching, III-624

converters, temperature-to-frequency, I-646, I-168, I-656, II-651-653

converters, temperature-to-time, III-632-633

defrost cycle and control, IV-566

heater control, I-640, II-642, III-624

heat sniffer, III-627

hi/lo sensor, II-650

indicator, IV-570

indicator, automotive temperature, PTC thermistor, II-56

measuring circuit, digital, II-653

measuring sensor, transistorized, IV-572

meter, I-647

monitor, III-206

monitor, thermal monitor, IV-569

oscillators, crystal, temperature-compensated, I-187

oscillators, temperature-stable, II-427

over-temperature switch, IV-571

over/under sensor, dual output, II-646

remote sensors, I-649, I-654

sensors, I-648, I-657, II-645-650, III-629-631, IV-568-572

sensors, 0-50-degree C four channel, I-648

sensors, 0-63 degrees C, III-631

sensors, 5 V powered linearized platinum RTD signal conditioner, II-650

sensors, automotive-temperature indicator, PTC thermistor, II-56

sensors, Centigrade thermometer, II-648

sensors, coefficient resistor, positive, I-657

sensors, differential, I-654, I-655

sensors, over/under, dual output, II-646

sensors, DVM interface, II-647

sensors, hi/lo, II-650

sensors, integrated circuit, I-649

sensors, isolated, I-651, III-631

sensors, remote, I-654

sensors, thermal monitor, IV-569

sensors, thermocouple amplifier, cold junction compensation, II-649

sensors, thermocouple multiplex system, III-630

sensors, zero-crossing detector, I-733

signal conditioners, II-639

thermocouple amplifier, cold junction compensation, II-649

thermocouple control, IV-567

thermocouple multiplex system, III-630

transducer, temperature-to-frequency, linear, I-646

transducer, temperature-transducer with remote sensor, I-649

under-temperature switch, IV-570

zero-crossing detector, I-733

temperature-to-frequency converter, I-168, I-656, II-651-653

temperature-to-frequency transducer, linear, I-646

temperature-to-time converters, III-632-633

ten-band graphic equalizer, active filter, II-684

Tesla coils, III-634-636

test circuits (*see* measurement/test circuits)

text adder, composite-video signal, III-716

theremins, II-654-656

digital, II-656

electronic, II-655

thermal flowmeter, low-rate flow, III-203

thermocouple circuits

digital thermometer using, II-658

multiplex, temperature sensor system, III-630

pre-amp using, III-283

thermometer, centigrade calibrated, I-650

thermocouple amplifiers, I-654, II-14

cold junction compensation, II-649

high stability, I-355

thermometers, II-657-662, III-637-643, IV-573-577

0-50 degree F, I-656

0-100 degree C, I-656

adapter, III-642

add-on for DMM digital voltmeter, III-640

centigrade, I-655, II-648, II-662

centigrade, calibrated, I-650

centigrade, ground-referred, I-657

differential, I-652, II-661, III-638

digital, I-651, I-658

digital, temperature-reporting, III-638

digital, thermocouple, II-658

digital,  $\mu$ P controlled, I-650

electronic, II-660, III-639, IV-575, IV-576

Fahrenheit, I-658

Fahrenheit, ground-referred, I-656

high-accuracy design, IV-577

implantable/ingestible, III-641

kelvin, zero adjust, I-653, II-661

kelvin, ground-referred, I-655

linear, III-642, IV-574

low-power, I-655

meter, trimmed output, I-655

remote, II-659

single-dc supply, IV-575

variable offset, I-652

thermostats

electronic, remote ac, two-wire, I-639

electronic, three-wire, I-640

three-in-one test set, III-330

three-minute timer, III-654

three-rail power supply, III-466

threshold detectors, precision, III-157

tilt meter, II-663-666, III-644-646

differential capacitance measurement circuit, II-665

sense-of-slope, II-664

ultra-simple level, II-666

time base

crystal oscillator, III-133, IV-128

function generators, 1 Hz, for read-out and counter applications, IV-201

time delays, I-668, II-220, II-667-670, III-647-649

circuit, precision solid state, I-664

constant current charging, II-668

electronic, III-648

generator, I-218

hour sampling circuit, II-668

integrator to multiply 555 timers, low-cost, II-669

long-duration, I-220

relay, I-663

relay, ultra precise long, I-219

timing threshold and load driver, III-648

two-SCR design, II-670

time division multiplex stereo decoder, II-168

- timers, I-666, I-668, II-671-681, III-650-655, IV-578-586
- 0.1 to 90 second, I-663
  - 741 timer, I-667
  - adjustable, IV-585
  - adjustable ac .2 to 10 seconds, II-681
  - alarm, II-674
  - appliance-cutoff timer, IV-583
  - CMOS, programmable precision, III-652
  - circuit, II-675
  - darkroom, I-480
  - elapsed time/counter timer, II-680
  - electronic egg, I-665
  - IC, crystal-stabilized, II-151
  - interval, programmable, II-678
  - interval, programmable, thumbwheel, I-660
  - long-delay, PUT, I-219
  - long-duration, PUT, II-675
  - long-duration, time delay, IV-585
  - long-interval, programmable, IV-581, IV-582
  - long-interval, RC, I-667
  - long-term electronic, II-672
  - long-time, III-653
  - mains-powered, IV-579
  - one-shot, III-654
  - photographic, I-485
  - photographic, darkroom enlarger, III-445
  - photographic, photo-event timer, IV-379
  - reaction timer, game circuit, IV-204
  - SCR design, IV-583
  - sequential, I-661-662, I-663, III-651
  - sequential UJT, I-662
  - slide-show, III-444
  - slides, photographic, III-448
  - solid-state, industrial applications, I-664
  - ten-minute ID timer, IV-584
  - three-minute, III-654
  - thumbwheel-type, programmable interval, I-660
  - time-out circuit, IV-586
  - transmit-time limiter, IV-580
  - triangle-wave generator, linear, III-222
  - variable duty-cycle output, III-240
  - voltage-controlled, programmable, II-676
  - washer, I-668
  - watchdog timer/alarm, IV-584
- timing light, ignition, II-60
- timing threshold and load driver, III-648
- tone alert decoder, I-213
- tone annunciator, transformerless, III-27-28
- tone burst generators, I-604, II-90
- European repeaters, III-74
- tone controls (*see also* sound generators), I-677, II-682-689, III-656-660, IV-587-589
- active bass and treble, with buffer, I-674
  - active control, IV-588
  - audio amplifier, II-686
  - Baxandall tone-control audio amplifier, IV-588
  - equalizer, ten-band octave, III-658
  - equalizer, ten-band graphic, active filter, II-684
  - guitar treble booster, II-683
  - high-quality, I-675
  - high-z input, hi fi, I-676
  - microphone preamp, I-675, II-687
  - mixer preamp, I-58
  - passive circuit, II-689
  - preamplifier, high-level, II-688
  - preamplifier, IC, I-673, III-657
  - preamplifier, microphone, I-675, II-687
  - preamplifier, mixer, I-58
  - rumble/scratch filter, III-660
  - three-band active, I-676, III-658
  - three-channel, I-672
  - tremolo circuit, IV-589
  - Wien-bridge filter, III-659
- tone decoders, I-231, III-143
- dual time constant, II-166
  - 24 percent bandwidth, I-215
  - relay output, I-213
  - tone-dial decoder, I-631
- tone detectors, 500-Hz, III-154
- tone-dial decoder, I-630, I-631
- tone-dial encoder, I-629
- tone-dial generator, I-629
- tone-dialing telephone, III-607
- tone encoder, I-67
- subaudible, I-23
  - tone-dial encoder, I-629
  - two-wire, II-364
- tone generators (*see* sound generators)
- tone probe, digital IC testing with, II-504
- tone ringer, telephone, II-630, II-631
- totem-pole driver, bootstrapping, III-175
- touch circuit, I-137
- touch switches, I-131, I-135-136, II-690-693, III-661-665, IV-590-594
- CMOS, I-137
  - bistable multivibrator, touch-triggered, I-133
  - double-button latching, I-138
  - hum-detecting touch sensor, IV-594
  - lamp control, three-way, IV-247
  - low-current, I-132
  - On/Off, II-691, III-663, IV-593
  - line-hum, III-664
  - momentary operation, I-133
  - negative-triggered, III-662
  - positive-triggered, III-662
  - sensor switch and clock, IV-591
  - time-on touch switch, IV-594
  - touchomatic, II-693
  - two-terminal, III-663
- Touchtone generator, telephone, III-609
- toxic gas detector, II-280
- toy siren, II-575
- TR circuit, II-532
- tracers
- audio reference signal, probe, I-527
  - bug, III-358
  - closed-loop, III-356
  - receiver, III-357
- track-and-hold circuits, III-667
- sample-and-hold circuit, III-549, III-552
  - signal, III-668
- tracking circuits, III-666-668
- positive/negative voltage reference, III-667
  - preregulator, III-492
  - track-and-hold, III-667
  - track-and-hold, signal, III-668
- train chuffer sound effect, II-588
- transceivers (*see also* receivers; transmitters), IV-595-603
- CE, 20-m, IV-596-598
  - CW, 5 W, 80-meter, IV-602
  - hand-held, dc adapter, III-461
  - hand-held, speaker amplifiers, III-39
  - HF transceiver/mixer, IV-457
  - ultrasonic, III-702, III-704
- transducer amplifiers, III-669-673
- flat-response, tape, III-673
  - NAB preamp, record, III-673
  - NAB preamp, two-pole, III-673
  - photodiode amplifier, III-672
  - preamp, magnetic phono, III-671, III-673
  - tape playback, III-672
  - voltage, differential-to-single-ended, III-670
- transducers, I-86
- bridge type, amplifier, II-84, III-71
  - detector, magnetic transducer, I-233
  - sonar, switch and, III-703
  - temperature, remote sensor, I-649
- transistors and transistorized circuits
- flashers, II-236, III-200
  - frequency tripler, nonselective, saturated, II-252
  - headphone amplifier, II-43

- on/off switch for op amp, IV-546
  - pulse generator, IV-437
  - sorter, I-401
  - tester, I-401, TV-281
  - transmission indicator, II-211
  - transmitters (*see also* receivers; transceivers), III-674-691, IV-595-603
    - 2-meter, IV-600-601
    - acoustic-sound transmitter, IV-311
    - amateur radio, 80-M, III-675
    - amateur TV, IV-599
    - beacon, III-683, IV-603
    - broadcast, 1-to-2 MHz, I-680
    - carrier current, I-144, I-145, III-79
    - computer circuit, 1-of-8 channel, III-100
    - CW, 1 W, III-678
    - CW, 10 W, one-tube, I-681
    - CW, 40 M, III-684
    - CW, 902 MHz, III-686
    - CW, HF low-power, IV-601
    - CW, QRP, III-690
    - fiber optic, III-177
    - FM, I-681
    - FM, infrared, voice-modulated pulse, IV-228
    - FM, multiplex, III-688
    - FM, one-transistor, III-687
    - FM, (PRM) optical, I-367
    - FM, snoopier, III-680
    - FM, voice, III-678
    - FM, wireless microphone, III-682, III-685, III-691
    - half-duplex information transmission link, low-cost, III-679
    - HF, low-power, IV-598
    - infrared, I-343, II-289, II-290, III-277, IV-226-227
    - infrared, digital, III-275
    - infrared, FM, voice-modulated pulse, IV-228
    - infrared, remote control with receiver, I-342
    - line-carrier, with on/off, 200 kHz, I-142
    - low-frequency, III-682
    - multiplexed, 1-of-8 channel, III-395
    - negative key-line keyer, IV-244
    - optical, I-363, IV-368
    - optical, FM, 50 kHz center frequency, II-417
    - optical, receiver for, II-418
    - oscillator and, 27 and 49 MHz, I-680
    - output indicator, IV-218
    - remote sensors, loop-type, III-70
    - television, III-676
    - ultrasonic, 40 kHz, I-685
    - VHF, modulator, III-684
    - VHF, tone, III-681
  - treasure locator, lo-parts, I-409
  - treble booster, guitar, II-683
  - tremolo circuits, I-59, III-692-695, IV-589
    - voltage-controlled amplifier, I-598
  - triac circuits
    - ac-voltage controller, IV-426
    - contact protection, II-531
    - dimmer switch, II-310, III-303
    - dimmer switch, 800W, I-375
    - drive interface, direct dc, I-266
    - microprocessor array, II-410
    - relay-contact protection with, II-531
    - switch, inductive load, IV-253
    - trigger, I-421
    - voltage doubler, III-468
    - zero point switch, II-311
    - zero voltage, I-623
  - triangle-to-sine converter, II-127
  - triangle/square wave oscillator, II-422
  - triangle-wave generators, III-234
    - square-wave, III-225, III-239
    - square-wave, precision, III-242
    - square-wave, wide-range, III-242
    - timer, linear, III-222
  - trickle charger, 12 V battery, I-117
  - triggers
    - 50-MHz, III-364
    - camera alarm, III-444
    - flash, photography, xenon flash, III-447
    - optical Schmitt, I-362
    - oscilloscope-triggered sweep, III-438
    - remote flash, I-484
    - SCR series, optically coupled, III-411
    - sound/light flash, I-482
    - triac, I-421
  - triggered sweep, add-on, I-472
  - tripler, nonselective, transistor saturation, II-252
  - trouble tone alert, II-3
  - TTL circuits
    - clock, wide-frequency, III-85
    - coupler, optical, III-416
    - gates, siren using, II-576
    - Morse code keyer, II-25
    - square wave to triangle wave converter, II-125
    - TTL to MOS logic converter, II-125
  - TTL oscillators, I-179, I-613
    - 1MHz to 10MHz, I-178
    - television display using, II-372
    - crystal, I-197
    - sine/square wave oscillator, IV-512
  - tube amplifier, high-voltage isolation, IV-426
  - tuners
    - antenna tuner, 1-to-30 MHz, IV-14
    - FM, I-231
    - guitar and bass, II-362
    - turbo circuits, glitch free, III-186
    - twang-twang circuit, II-592
    - twilight-triggered circuit, II-322
    - twin-T notch filters, III-403
    - two-state siren, III-567
    - two-tone generator, II-570
    - two-tone siren, III-562
    - two-way intercom, III-292
    - two's complement, D/A conversion system, binary, 12-bit, III-166
- ## U
- UA2240 staircase generator, III-587
  - UHF transmissions
    - field-strength meters, IV-165
    - rf amplifiers, UHF TV-line amplifier, IV-482, IV-483
    - source dipper, IV-299
    - TV preamplifier, III-546
    - VHF/UHF rf diode switch, IV-544
    - wideband amplifier, high performance FETs, III-264
  - UJT circuits
    - battery chargers, III-56
    - metronome, II-355
    - monostable circuit, bias voltage change insensitive, II-268
  - ultrasonic circuits (*see also* sound-operated circuits), III-696-707, IV-604-606
    - arc welding inverter, 20 KHz, III-700
    - induction heater, 120-KHz 500-W, III-704
    - pest-controller, III-706, III-707
    - pest-repeller, I-684, II-685, III-699, IV-605-606
    - ranging system, III-697
    - receiver, III-698, III-705
    - sonar transducer/switch, III-703
    - sound source, IV-605
    - switch, I-683
    - transceiver, III-702, III-704
    - transmitter, I-685
  - undervoltage detector, IV-138
  - undervoltage monitor, III-762
  - uninterruptible power supply, II-462 + 5V, III-477
  - unity-gain amplifiers
    - inverting, I-80
    - inverting, wideband, I-35
    - ultra high Z, ac, II-7
  - unity-gain buffer
    - stable, with good speed and high-input impedance, II-6
  - unity-gain follower, I-27
  - universal counters
    - 10 MHz, II-139

- universal counters (*cont.*)
  - 40-MHz, III-127
- universal mixer stage, III-370
- universal power supply, 3-30V, III-489
- up/down counter, extreme count freezer, III-125
- V**
- vacuum fluorescent display circuit, II-185
- vacuum gauge, automotive, IV-45
- vapor detector, II-279
- varactor-tuned 10 MHz ceramic resonator oscillator, II-141
- variable current source, 100 mA to 2A, II-471
- variable duty-cycle oscillator, fixed-frequency, III-422
- variable-frequency inverter, complementary output, III-297
- variable-gain amplifier, voltage-controlled, I-28-29
- variable-gain and sign op amp, II-405
- variable-gain circuit, accurate null and, III-69
- variable oscillators, II-421
  - audio, 20Hz to 20kHz, II-727
  - four-decade, single control for, II-424
  - sine-wave oscillator, super low-distortion, III-558
  - wide range, II-429
- variable power supplies, III-487-492, IV-414-421
  - adjustable 10-A regulator, III-492
  - current source, voltage-programmable, IV-420
  - dc supply, SCR variable, IV-418
  - dc supply, step variable, IV-418
  - dual universal supply, 0-to-50 V, 5 A, IV-416-417
  - regulated supply, 2.5 A, 1.25-to-25 V regulator, Darlington, IV-421
  - regulator, variable, 0-to-50 V, IV-421
  - regulator/current source, III-490
  - switch-selected fixed-voltage supply, IV-419
  - switching regulator, low-power, III-490
  - switching, 100-KHz multiple-output, III-488
  - tracking preregulator, III-492
  - transformerless supply, IV-420
  - universal 3-30V, III-489
  - variable current source, 100mA to 2A, II-471
  - voltage regulator, III-491
- vehicles (*see* automotive circuits)
- VFO, 5 MHz, II-551
- VHF transmissions
  - crystal oscillator, 20-MHz, III-138
  - crystal oscillator, 50-MHz, III-140
  - crystal oscillator, 100-MHz, III-139
  - modulator, I-440, III-684
  - tone transmitter, III-681
  - VHF/UHF diode rf switch, IV-544
- video amplifiers, III-708-712
  - 75-ohm video pulse, III-711
  - buffer, low-distortion, III-712
  - color, I-34, III-724
  - dc gain-control, III-711
  - FET cascade, I-691
  - gain block, III-712
  - IF, low-level video detector circuit, I-689, II-687
  - JFET bipolar cascade, I-692
  - line driving, III-710
  - log amplifier, I-38
  - RGB, III-709
  - summing, clamping circuit and, III-710
- video circuits (*see also* television-related circuits), III-713-728, IV-607-621
  - audio/video switcher circuit, IV-540-541
  - camera-image tracker, analog voltage, IV-608-609
  - camera link, wireless, III-718
  - chroma demodulator with RGB matrix, III-716
  - color amplifier, III-724
  - color-bar generator, IV-614
  - composite-video signal text adder, III-716
  - converter, RGB-to-NTSC, IV-611
  - converter, video a/d and d/a, IV-610-611
  - cross-hatch generator, color TV, III-724
  - dc restorer, III-723
  - decoder, NTSC-to-RGB, IV-613
  - high-performance video switch, III-728
  - line pulse extractor, IV-612
  - loop-thru amplifier, IV-616
  - mixer, high-performance video mixer, IV-609
  - modulators, I-437, II-371, II-372
  - monitors, RGB, blue box, III-99
  - monochrome-pattern generator, IV-617
  - multiplexer, cascaded, 1-of-15, III-393
  - PAL/NTSC decoder with RGB input, III-717
  - palette, III-720
  - picture fixer/inverter, III-722
  - RGB-composite converter, III-714
  - signal clamp, III-726
  - switching circuits, IV-618-621
  - switching circuits, remote selection switch, IV-619
  - switching circuits, remote-controlled switch, IV-619-621
  - sync separator, IV-616
  - sync separator, single-supply wide-range, III-715
  - video op amp circuits, IV-615
  - video switch, automatic, III-727
  - video switch, general purpose, III-725
  - video switch, very-high off isolation, III-719
  - wireless camera link, III-71
- vocal eliminator, IV-19
- voice scrambler/descrambler, IV-26
- voice scrambler/disguiser, IV-27
- voice substitute, electronic, III-734
- voice-activated circuits (*see also* sound-operated circuits), III-729-734, IV-622-624
- ac line-voltage announcer, III-730
- allophone generator, III-733
- amplifier/switch, I-608
- computer speech synthesizer, III-732
- dialed phone number vocalizer, III-731
- scanner voice squelch, IV-624
- switch, III-580
- switch, microphone-controlled, IV-527
- switch/amplifier, I-608
- voice substitute, electronic, III-734
- VOX circuit, IV-623
- voltage amplifiers
  - differential-to-single-ended, III-670
  - reference, I-36
- voltage-controlled amplifier, I-31, I-598
- attenuator for, II-18
- tremolo circuit, I-598
- variable gain, I-28-29
- voltage-controlled filter, III-187
- 1,000:1 tuning, IV-176
- voltage-controlled high-speed one shot, II-266
- voltage-controlled ramp generator, II-523
- voltage-controlled resistor, I-422
- voltage-controlled timer, programmable, II-676
- voltage-controlled amplifier, IV-20
- tremolo circuit or, I-598
- voltage-controlled oscillators, I-702-704, II-702, III-735, IV-625-630
- 3-5 V regulated output converter, III-739
- 10Hz to 10kHz, I-701, III-735-741

555-VCO, IV-627  
 audio-frequency VCO, IV-626  
 crystal oscillator, III-135, IV-124  
 current sink, voltage-controlled, IV-629  
 driver, op-amp design, IV-362  
 linear, I-701, IV-628  
 linear triangle/square wave, II-263  
 logarithmic sweep, III-738  
 precision, I-702, III-431  
 restricted-range, IV-627  
 stable, IV-372-373  
 supply voltage splitter, III-738  
 three-decade, I-703  
 TMOS, balanced, III-736  
 two-decade, high-frequency, I-704  
 varactorless, IV-630  
 variable-capacitance diode-sparked, III-737  
 VHF oscillator, voltage-tuned, IV-628  
 waveform generator, III-737  
 wide-range, IV-629  
 wide-range, biphasic, IV-629  
 wide-range, gate, IV-627  
 voltage-controller, pulse generator, III-524  
 voltage converters, III-742-748  
   12-to-16 V, III-747  
   dc-to-dc, 3-25 V, III-744  
   dc-to-dc, dual output  $\pm$  12-15 V, III-746  
   flyback, high-efficiency, III-744  
   flyback-switching, self-oscillating, III-748  
   negative voltage,  $\mu$ P-controlled, IV-117  
   offline, 1.5-W, III-746  
   regulated 15-Vout 6-V driven, III-745  
   splitter, III-743  
   unipolar-to-dual supply, III-743  
 voltage detector relay, battery charger, II-76  
 voltage followers, I-40, III-212  
   fast, I-34  
   noninverting, I-33  
   signal-supply operation, amplifier, III-20  
 voltage inverters, precision, III-298  
 voltage meters/monitors/indicators, III-758-772  
   ac voltmeter, III-765  
   ac voltmeter, wide-range, III-772  
   audio millivoltmeter, III-767, III-769  
   automotive battery voltage gauge, IV-47  
   battery-voltage measuring regulator, IV-77  
   comparator and, II-104  
   dc voltmeter, III-763  
   dc voltmeter, resistance, high-input, III-762  
   DVM, 3.5-digit, full-scale 4-decade, III-761  
   DVM, 4.5-digit, III-760  
   FET voltmeter, III-765, III-770  
   five-step level detector, I-337  
   frequency counter, III-768  
   high-input resistance voltmeter, III-768  
   HTS, precision, I-122  
   level detectors, I-338, II-172, III-759, III-770  
   low-voltage indicator, III-769  
   multiplexed common-cathode LED ADC, III-764  
   over/under monitor, III-762  
   peak program detector, III-771  
   rf voltmeter, III-766  
   solid-state battery, I-120  
   ten-step level detector, I-335  
   visible, I-338, III-772  
   voltage freezer, III-763  
 voltage multipliers, IV-631-637  
   2,000 V low-current supply, IV-636-637  
   10,000 V dc supply, IV-633  
   corona wind generator, IV-633  
   doublers, III-459, IV-635  
   doubler, cascaded, Cockcroft-Walton, IV-635  
   doublers, triac-controlled, III-468  
   laser power supply, IV-636  
   negative-ion generator, high-voltage, IV-634  
   tripler, low-current, IV-637  
 voltage ratio-to-frequency converter, III-116  
 voltage references, III-773-775  
   bipolar source, III-774  
   digitally controlled, III-775  
   expanded-scale analog meter, III-774  
   positive/negative, tracker for, III-667  
   variable-voltage reference source, IV-327  
 voltage regulators, I-501, I-511, II-484  
   0- to 10-V at 3A, adjustable, I-511  
   0- to 22-V, I-510  
   0- to 30-V, I-510  
   5 V, low-dropout, III-461  
   5 V, 1 A, I-500  
   6 A, variable output switching, I-513  
   10 A, I-510  
   10 A, adjustable, III-492  
   10 V, high stability, III-468  
   15 V, 1 A, remote sense, I-499  
   15 V, slow turn-on, III-477  
   -15 V negative, I-499  
   45 V, 1 A switching, I-499  
   100 Vrms, I-496  
   ac, III-477  
   adjustable output, I-506, I-512  
   automotive circuits, III-48, IV-67  
   battery charging, I-117  
   buckling, high-voltage, III-481  
   common hot-lead regulator, IV-467  
   constant voltage/constant current, I-508  
   current and thermal protection, 10 amp, II-474  
   dual-tracking, III-462  
   efficiency-improving switching, IV-464  
   fixed pnp, zener diode increases output, II-484  
   fixed-current regulator, IV-467  
   fixed-voltages, IV-462-467  
   flyback, off-line, II-481  
   high- or low-input regulator, IV-466  
   high-stability, I-499  
   high-stability, 1 A, I-502  
   high-stability, 10 V, III-468  
   high-voltage, III-485  
   high-voltage, foldback-current limiting, II-478  
   high-voltage, precision, I-509  
   low-dropout, 5-V, III-461  
   low-voltage, I-502, I-511  
   linear, low-dropout, III-459  
   linear, radiation-hardened 125 A, II-468  
   mobile, I-498  
   negative, III-474, IV-465  
   negative, -15 V, I-499  
   negative, floating, I-498  
   negative, switching, I-498  
   negative, voltage, I-499  
   negative, floating, I-498  
   positive, switching, I-498  
   positive, with NPN/PNP boost, III-475  
   positive, with PNP boost, III-471  
   pre-, SCR, II-482  
   pre-, tracking, III-492  
   projection lamp, II-305  
   PUT, 90 V rms, II-479  
   remote shutdown, I-510  
   negative, IV-465  
   sensor, LM317 regulator sensing, IV-466  
   short-circuit protection, low-voltage, I-502  
   single-ended, I-493  
   single-supply, II-471  
   slow turn-on 15 V, I-499  
   switch-mode, IV-463  
   switching, 3-A, III-472  
   switching, 3 W, application circuit, I-492

voltage regulators (*cont.*)  
 switching, 5 V, 6 A 25kHz, separate  
 ultrastable reference, I-497  
 switching, 6 A, variable output, I-513  
 switching, 200 kHz, I-491  
 switching, multiple output, for use  
 with MPU, I-513  
 switching, step down, I-493  
 switching, high-current inductorless,  
 III-476  
 switching, low-power, III-490  
 variable, III-491, IV-468-470  
 variable, current source, III-490  
 zener design, programmable, IV-470

voltage sources  
 millivolt, zenerless, I-696  
 programmable, I-694

voltage splitter, III-738

voltage-to-current converter, I-166, II-  
 124, III-110, IV-118  
 power, I-163  
 zero IB error, III-120

voltage-to-frequency converters, I-707,  
 III-749-757, IV-638-642  
 1 Hz-to-10MHz, III-754  
 1 Hz-to-30 MHz, III-750  
 1Hz-to-1.25 MHz, III-755  
 5 KHz-to-2MHz, III-752  
 10Hz to 10 kHz, I-706, III-110  
 accurate, III-756  
 differential-input, III-750  
 function generators, potentiometer-  
 position, IV-200  
 low-cost, III-751  
 low-frequency converter, IV-641  
 negative input, I-708  
 optocoupler, IV-642  
 positive input, I-707  
 precision, II-131  
 preserved input, III-753  
 ultraprecision, I-708  
 wide-range, III-751, III-752

voltage-to-pulse duration converter, II-  
 124

voltmeters  
 3<sup>1</sup>/<sub>2</sub> digit, I-710  
 3<sup>1</sup>/<sub>2</sub> digital true rms ac, I-713  
 5-digit, III-760  
 ac, III-765  
 ac, wide-range, III-772  
 add-on thermometer for, III-640  
 bar-graph, I-99, II-54  
 dc, III-763  
 dc, high-input resistance, III-762  
 digital, III-4  
 digital, 3.5-digit, full-scale, four-  
 decade, III-761  
 digital, LED readout, IV-286  
 FET, I-714, III-765, III-770

high-input resistance, III-768  
 millivoltmeters (*see* millivoltmeters)  
 rf, I-405, III-766  
 wide-band ac, I-716

voltohmmeter, phase meter, digital  
 readout, IV-277

volume amplifier, II-46

volume control circuits, IV-643-645  
 telephone, II-623

volume indicator, audio amplifier, IV-  
 212

VOR signal simulator, IV-273

vox box, II-582, IV-623

Vpp generator, EPROM, II-114

VU meters  
 extended range, II-487, I-715  
 LED display, IV-211

## W

waa-waa circuit, II-590

wailers (*see* alarms; sirens)

wake-up call, electronic, II-324

walkman amplifier, II-456

warblers (*see* alarms; sirens)

warning devices  
 auto lights-on warning, II-55  
 high-level, I-387  
 high-speed, I-101  
 light, III-317  
 light, battery-powered, II-320  
 low-level, audio output, I-391  
 speed, I-96  
 varying-frequency alarm, II-579

water-level sensors (*see* fluid and  
 moisture detectors)

water-temperature gauge, automotive,  
 IV-44

wattmeter, I-17

wave-shaping circuits (*see also* wave-  
 form generators), IV-646-651  
 capacitor for high slew rates, IV-650  
 clipper, glitch-free, IV-648  
 flip-flop, S/R, IV-651  
 harmonic generator, IV-649  
 phase shifter, IV-647  
 rectifier, full-wave, IV-650  
 signal conditioner, IV-649

waveform generators (*see also* burst  
 generators; function generators;  
 sound generators; square-wave  
 generators; wave-shaping circuits),  
 II-269, II-272  
 audio, precision, III-230  
 four-output, III-223  
 harmonic generator, IV-649  
 high-speed generator, I-723  
 precise, II-274  
 ramp generators, IV-443-447

sawtooth generator, digital, IV-444,  
 IV-446

sine-wave, IV-505, IV-506  
 sine-wave, 60 Hz, IV-507  
 sine-wave, audio, II-564  
 sine-wave, LC, IV-507  
 sine-wave, LF, IV-512  
 sine-wave oscillator, audio, III-559  
 staircase generators, IV-443-447  
 staircase generator/frequency  
 divider, I-730  
 stepped waveforms, IV-447  
 triangle and square waveform, I-726  
 VCO and, III-737

wavemeter, tuned RF, IV-302

weather-alert decoder, IV-140

weight scale, digital, II-398

Wheel-of-Fortune game, IV-206

whistle, steam locomotive, II-589, III-  
 568

who's first game circuit, III-244

wide-range oscillators, I-69, III-425  
 variable, I-730

wide-range peak detectors, III-152  
 hybrid, 500 kHz-1 GHz, III-265  
 instrumentation, III-281  
 miniature, III-265  
 UHF amplifiers, high-performance  
 FETs, III-264

wideband amplifiers  
 low-noise/low drift, I-38  
 two-stage, I-689  
 rf, IV-489, IV-490, IV-491  
 rf, HF, IV-492  
 rf, JFET, IV-493  
 rf, MOSFET, IV-492  
 rf, two-CA3100 op amp design, IV-  
 491  
 unity gain inverting, I-35

wideband signal splitter, III-582

wideband two-pole high pass filter, II-  
 215

Wien-bridge filter, III-659  
 notch filter, II-402

Wien-bridge oscillators, I-62-63, I-70,  
 III-429, IV-371, IV-377, IV-511  
 CMOS chip in, II-568  
 low-distortion, thermally stable, III-  
 557  
 low-voltage, III-432  
 sine wave, I-66, I-70, II-566  
 sine-wave, three-decade, IV-510  
 sine-wave, very-low distortion, IV-  
 513  
 single-supply, III-558  
 variable, III-424

wind-powered battery charger, II-70

windicator, I-330

window circuits, II-106, III-90, III-776-

781, IV-655-659  
comparator, IV-658  
comparator, low-cost design, IV-656-657  
comparator, voltage comparator, IV-659  
detector, IV-658  
digital frequency window, III-777  
discriminator, multiple-aperture, III-781  
generator, IV-657  
high-input-impedance, II-108  
windshield wiper circuits  
control circuit, I-103, I-105, II-62  
delay circuit, II-55  
delay circuit, solid-state, IV-64  
hesitation control unit, I-105  
intermittent, dynamic braking, II-49  
interval controller, IV-67  
slow-sweep control, II-55  
windshield washer fluid watcher, I-107  
wire tracer, II-343

wireless microphones (*see* micro-phones), IV-652  
wireless speaker system, IR, III-272  
write amplifiers, III-18

## X

xenon flash trigger, slave, III-447  
XOR gates, IV-107  
complementary signals generator, III-226  
oscillator, III-429  
up/down counter, III-105

## Y

yelp oscillator/siren, II-577, III-562

## Z

Z80 clock, II-121

zappers, battery, II-64  
ni-cad battery, II-66  
ni-cad battery, version II, II-68  
zener diodes  
clipper, fast and symmetrical, IV-329  
increasing power rating, I-496, II-485  
limiter using one-zener design, IV-257  
tester, I-400  
variable, I-507  
voltage regulator, programmable, IV-470  
zero-crossing detector, II-173  
zero meter, suppressed, I-716  
zero-point switches  
temperature control, III-624  
triac, II-311  
zero-voltage switches  
closed contact half-wave, III-412  
solid-state, optically coupled, III-410  
solid-state, relay, antiparallel SCR output, III-416