

MAKING A NOVEL LINEN SPEAKER

W. JAMES ON THE NEWEST AERIAL CIRCUITS

Amateur Wireless


Every
Thursday 3^d

and
Radiovision

Vol. XVII. No. 442

Saturday, November 29, 1930

The SEARCHER SHORT WAVE TWO

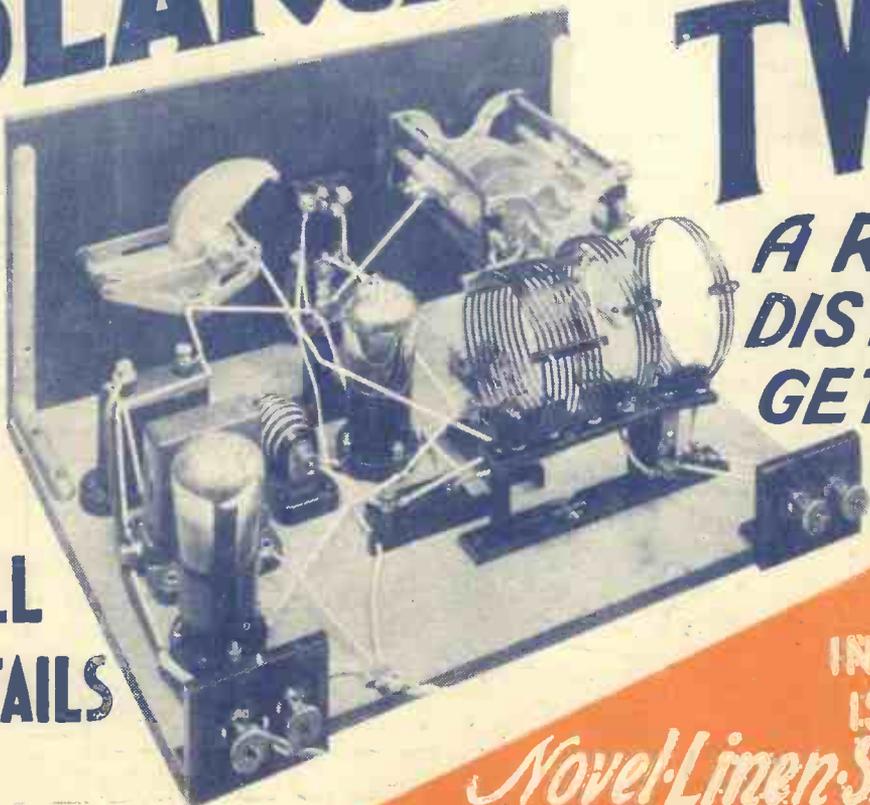

**A REAL
DISTANCE
GETTER**

**FULL
DETAILS**

**ALSO
IN THIS
ISSUE**

Novel-Linen-Speaker

THE WIZARD OF WIRELESS.



The LEWCOS DUAL WAVE COIL

The LEWCOS DUAL WAVE COIL

Although the days of wizardry are past, there are still scientifically constructed instruments capable of feats which incline us to believe that they are the work of those old-time magicians of which we read.

In this category come the Lewcos Dual-wave Coils, which are the direct result of a demand for highly efficient, though selective, coils covering both the medium (235-550 m.) and long (1,000-2,000 m.) wave-bands. These coils are of the radiating type, and are mounted on bases fitted with the standard six terminals and push-pull switching mechanism, so that the wave-band required is selected by a single operation of the push-pull rod. Write for fully descriptive leaflet Ref. R.65

The fine materials and high-class workmanship used in the manufacture of the Lewcos H.F. Choke make it supreme. The terminals are placed one at the top and the other at the base of the coil to eliminate the risk of additional self-capacity in the wiring of the receiver.

"Its design places it in the front rank of high-class components," writes Industrial Progress (International), Ltd., of Bristol.

A fully descriptive leaflet, Ref. R.33, giving tested values, will be sent on request.



The LEWCOS H.F. CHOKE



GLAZITE is 6d. Per 10 ft. Coil and is Not Genuine Unless Made by LEWCOS.

THE LONDON ELECTRIC WIRE COMPANY AND SMITHS LIMITED
CHURCH ROAD, LEYTON, LONDON, E.10

LEWCOS



RADIO PRODUCTS


Write for Lewcos free sheet of blue prints of four suggested circuits utilizing Lewcos components. Please quote reference R70.

Stocks held at the following Branches:

- BELFAST
- BIRMINGHAM
- CARDIFF
- DUBLIN
- GLASGOW
- LEEDS
- LIVERPOOL
- LONDON
- MANCHESTER
- NEWCASTLE
- NOTTINGHAM

Please Mention "A.W." When Corresponding with Advertisers

The test of TIME

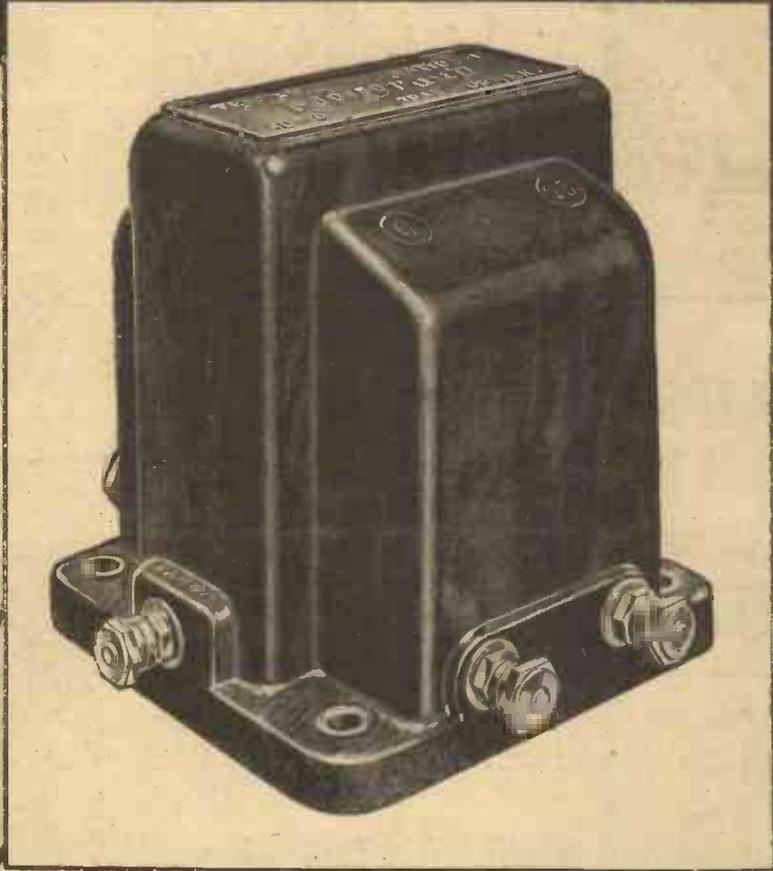

The "ACE" TRANSFORMER has been specially designed for inclusion in all Portable Sets and where space is limited. Similar finish to the "Radiogrand." Price each 8/6. Made in ratios 3-1 and 5-1.

TELSEN "RADIOGRAND" TRANSFORMER. Note new Earth Terminal, invaluable in two-transformer-coupled sets. Built for permanent efficiency. Ratios 3-1 and 5-1. Price each 12/6. Super Ratio 7-1. Price 17/6.

THE TEST OF TIME —BUILT TO LAST

Telsen transformers have held a reputation unique in the radio transformer industry since the inception of broadcasting. This pre-eminent position has been gained through their sound designs, accurate workmanship—and ultimate "Lasting Efficiency."

Telsen transformers have still further increased that reputation by embodying many new and exclusive features, which give reproduction throughout the entire musical score—giving radio that is living.

Despite all these new features, the prices of Telsen transformers still remain the same. They have thus withstood the test of time against all comers.

TELSEN ELECTRIC CO., LTD., BIRMINGHAM

TELSEN

TRANSFORMERS

A Ltd. of Telsen Electric Co., Ltd., Birmingham

Advertisers Appreciate Mention of "A.W." with Your Order

"ARROW TWO" COILS
Each **3/6**
RELIABLE

"JAMES' SCREENED GRID 3" COILS
Each **7/6**
EFFICIENT

"MUSIC MONITOR" COILS
Each **7/6**
SPECIFIED


"CHALLENGE FOUR" DUAL RANGE COILS
Each **10/6**
ALWAYS USE

WEARITE COMPONENTS

SEND FOR ILLUSTRATED LISTS
WRIGHT & WEAIRE, LTD.
 740, High Road, Tottenham, London, N.17

Phone: Tottenham 3847-8

SPECIFIED BY EXPERTS

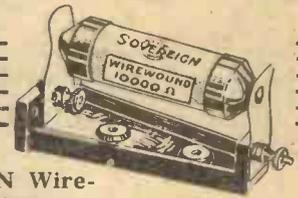

SOVEREIGN Wire-wound Resistances are invariably specified by experts who want consistency and reliability when constructing Mains Eliminators. Every Resistance is guaranteed within 5% of its stated value and is astatically wound. Send for pamphlet giving safe load current carrying capacity of every Resistance. Any one supplied without Bakelite holder and metal clips at 1/- less than list prices.

Tell us if your dealer does not stock what you want. We will gladly give you the name and address of the nearest stockist.


VALUES

ohms	each
1,000/3,000	5/-
4,000 40,000	4/-
50,000	5/-
60,000	6/-
75,000	7/-
100,000	8/-

OTHER NOTABLE SOVEREIGN PRODUCTS:—Volume Controls, Potentiometers, Rheostats, Wave Traps, Dual-range and Screen-grid Coils, H. F. Chokes, Compression-type Condensers, etc.



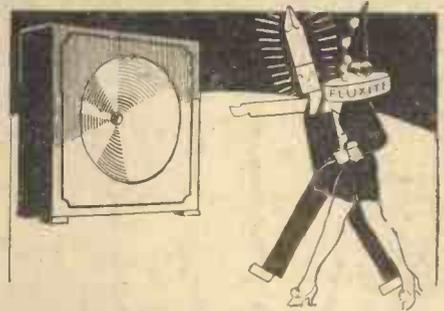SOVEREIGN PRODUCTS, LTD., 52 54 Rosebery Avenue, London, E.C.1.




"We're Fluxite and Solder—The reliable pair, Famous for Soldering, Known everywhere! If there's trouble with Wireless, Loud-Speaker—or Set, just call US to help you—You'll be glad that we met."

See that Fluxite and Solder are always by you—in the house, garage, workshop—anywhere where simple, speedy soldering is needed. They cost so little but will make scores of everyday articles last years longer! For Pots, Pans, Silver and Brassware; RADIO: odd jobs in the garage—there's always something useful for Fluxite and Solder to do.

ANOTHER USE FOR FLUXITE. Hardening Tools and Case Hardening. Ask for Leaflet on improved method **FLUXITE SOLDERING SET.** Simple to use and lasts for years in constant use. Contains special 'small-space' soldering iron with non-heating metal handle; pocket blow-lamp, Fluxite, Solder, etc; and full instructions.

All Hardware and Ironmongery Stores sell Fluxite in tins, 8d., 1/4 and 2/8.

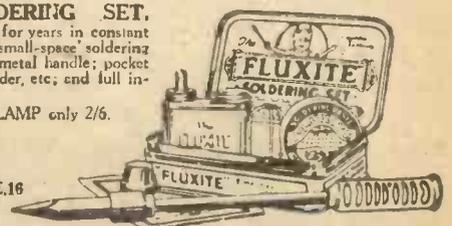COMPLETE 7/6, or LAMP only 2/6.
FLUXITE LTD.,
 (Dept. 323)
 ROTHERHITHE, S.E.16



ALL MECHANICS WILL HAVE
FLUXITE
 IT SIMPLIFIES ALL SOLDERING

TESTS EVERYTHING



**VALVES
FILAMENT · ·
ANODE & GRID
COMPONENTS
AND CIRCUITS
H.T. AND L.T.
MILLIAMPS
Everything!**

The All-in-One Radiometer gives you a definite answer to every question you put to it. It will tell you, at once, whether a valve is "good" or "dud." If your batteries are failing it will show you just where you stand, giving you

the exact output in volts and milliamps. Mains Units, too, can be tested. When you build your new set you can test every component, every inch of wiring—before you switch on. You will never burn out a valve if you check over first with the All-in-One. It is calibrated to give an accurate reading, is as simple to understand as an alarm clock and is built to last. Let it solve your problems—let it save you money. Ask for our booklet or write direct to Pifco Ltd., Pifco House, High St., Manchester


12/6

OBTAINABLE FROM ALL GOOD WIRELESS DEALERS.

**PIFCO
ALL IN ONE
RADIOMETER**

P4


LITTLE STORIES OF GREAT MOMENTS

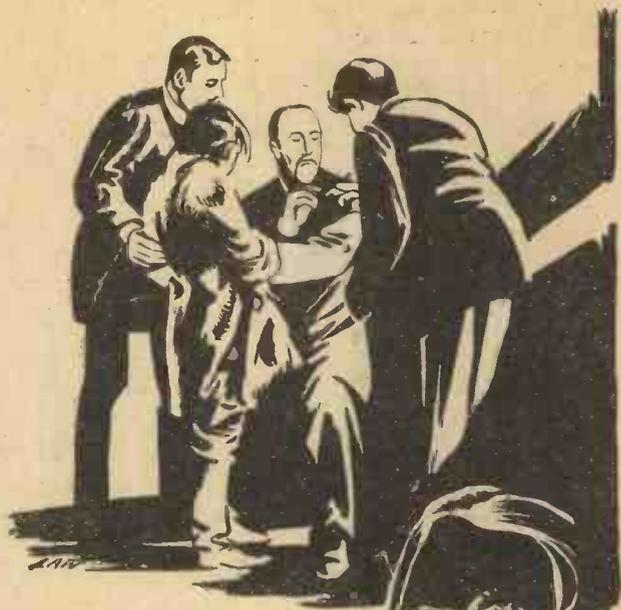

**"I dare
not
do it!"**

When a young shepherd boy, bitten by a mad dog, was brought to him for inoculation, Louis Pasteur, the great French scientist, was tormented by indecision. Should he put his life's work to the test? Would it save—or end—the boy's life? He decided, the boy was saved, and long years spent in doing one thing and doing it well, were rewarded with success.

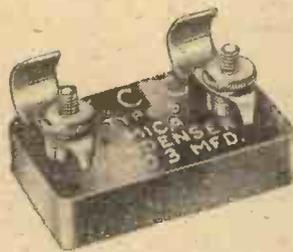It is this same spirit of "doing one thing and doing it well" which has, for years, been behind all T.C.C. endeavour. That is why T.C.C. have never made anything but Condensers, and why T.C.C. Condensers are unmatched—for accuracy and dependability. The T.C.C. .0003 mfd. Flat type Mica Condenser is shown here. Price 1/3.



**T.C.C.
CONDENSERS**

TELEGRAPH CONDENSER CO., LTD., N. ACTON, W.3.


© 6781

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

Seven point suspension

definitely prevents filament vibration

the primary cause
of microphonic noises

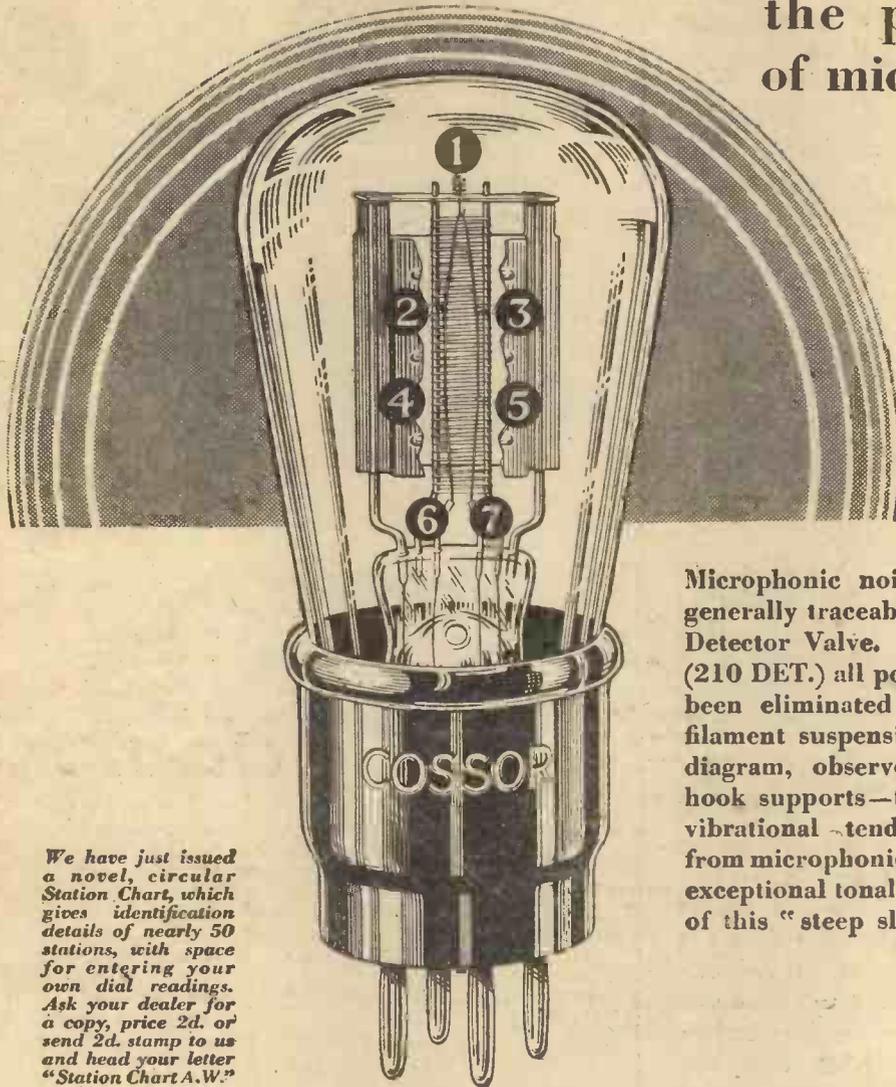

We have just issued a novel, circular Station Chart, which gives identification details of nearly 50 stations, with space for entering your own dial readings. Ask your dealer for a copy, price 2d. or send 2d. stamp to us and head your letter "Station Chart A.W."

Cossor 210 DET., 2 volts, .1 amp.
Impedance 13,000. Amplification Factor 15. Mutual Conductance 1.15 m.a./v.
Normal working Anode Voltage 90-150. Price **8/6**

Microphonic noises in a Receiving Set are generally traceable to filament vibration in the Detector Valve. In the new Cossor Detector (210 DET.) all possibility of this vibration has been eliminated by the special seven point filament suspension employed. Examine the diagram, observe the four extra insulated hook supports—these effectively damp out all vibrational tendencies. Complete freedom from microphonic noises and great volume with exceptional tonal purity are ensured by the use of this "steep slope" Cossor Detector Valve.

THE NEW
COSSOR
DETECTOR VALVE

DEFINITELY FREE FROM MICROPHONIC NOISES


A. C. Cossor, Ltd., Highbury Grove, London, N.5

Advertisers Appreciate Mention of "A.W." with Your Order



Amateur Wireless

and
Radiovision

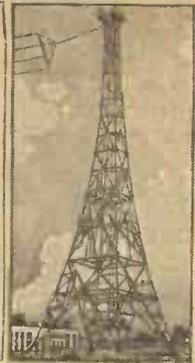

EDITOR:
BERNARD E. JONES.

TECHNICAL EDITOR:
J. H. REYNER, B.Sc., A.M.I.E.E.

RESEARCH CONSULTANT:
W. JAMES.

ASSISTANT EDITOR:
H. CORBISHLEY.

THE LEADING RADIO WEEKLY FOR THE
CONSTRUCTOR, LISTENER & EXPERIMENTER.

NEWS · & · GOSSIP · OF THE · WEEK

NEXT WEEK— OUR CHRISTMAS NUMBER

CHRISTMAS is close at hand, and next week's issue of AMATEUR WIRELESS is our Special Christmas Number, which will make you think deeply about Christmas holidays, Christmas festivities, and (last, but not least) Christmas radio! Make sure, at the newsagent's, of getting your copy of this bumper number, for it will sell like hot cakes: a coloured cover, and seventy-six pages chock full of helpful, constructional, and entertaining features; bigger than ever—but the usual price, 3d.

SPONSORED PROGRAMMES AGAIN

THE topic of sponsored programmes is on everybody's lips, and as it seems inevitable that advertising programmes of some form will come in time, it is a good

thing that the listening public is now thinking deeply about it. Don't overlook the fact that there can be two kinds of sponsored programme: one the occasional big effort of an advertiser to whom cost means nothing, when he will put over an "all-star" programme, and the other the average effort of small firms, who can only afford to give broadcast matter inferior to that now offered by the B.B.C. We do want the big effort, because it will mean a type of programme which the B.B.C. could never hope to afford; but we don't want sponsored programmes which are no better than State-provided programmes. There are plenty of British firms who could afford to give fine programmes.

A CONSIDERED OPINION

THIS logical idea was well expressed by the Editor of AMATEUR WIRELESS

PRINCIPAL CONTENTS

	Page
News and Gossip	821
A Novel Linen-diaphragm Speaker	823
The Newest Aerial Circuits ...	825
A Home-made Pick-up	826
On Your Wavelength	829
The ABC of Low-frequency Amplification	831
All About B.B.C. Auditions ...	832
Without Fear or Favour	835
The "Searcher Short-wave 2" ...	836
In My Wireless Den	840
The Varley Junior Two	842
Is Resistance-coupling Out of Date?	844
We Test for You	846


when, in a leading article in the October issue of *Wireless Magazine*, he said: "Anybody with brains and money ought to be able, just for one hour, to put out a better show than the B.B.C. can in the nature of things put out continuously. . . . Sponsored programmes might be the spiced morsels in the regular plain but nourishing menu, and would add a new zest to listening."

ANNOUNCERS' SALARIES

WHAT salary do American announcers receive? When the question was submitted to the National Broadcasting Company, a representative said: "The announcers' regular pay is nothing to speak of. It's the commercials he gets that count. For example, when Graham McNamee announces a commercial programme, he gets £50, in addition to his salary, and during the winter he usually has at least four commercial programmes a week."

IN AUSTRALIA

IF imitation really is the sincerest form of flattery, then AMATEUR WIRELESS is flattered! A popular Australian contemporary was interested in the special article which was published in AMATEUR WIRELESS No. 427, telling how it is possible to telephone from a sixty-mile-an-hour express train. As, no doubt, the article was considered of great interest also to Australian amateurs, it was reprinted word for word

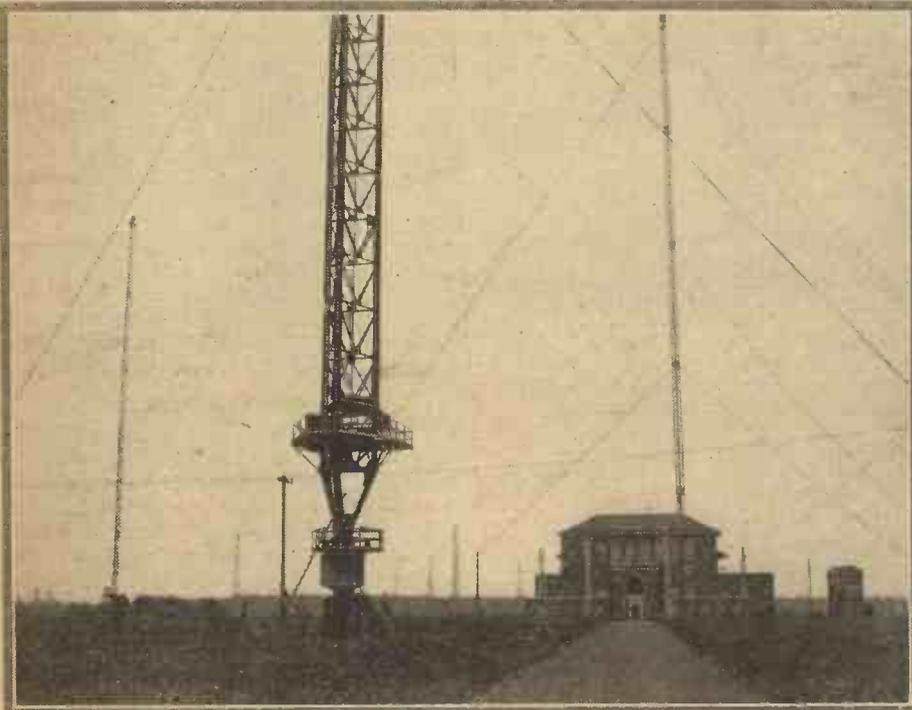

Down at the base. A new glimpse of Rugby, with one of the giant 820-ft. masts in the foreground. Rugby is the transmitter for the P.O. transatlantic telephone, and a short-wave transmitter is sometimes used

NEWS · & · GOSSIP · OF THE · WEEK

—Continued

under a different title. It is unfortunate that no acknowledgment of AMATEUR WIRELESS was made, but, then, our Australian readers who saw the article in AMATEUR WIRELESS some three months before it appeared in the Australian magazine will have no doubt as to the origination of the information.

A BRITISH PRODUCER FOR CANADA

TYRONE GUTHRIE, author of *The Squirrel's Cage*, has been engaged by the Radio Department of the Canadian National Railways to produce a number of plays specially written for the microphone. The close co-operation of the B.B.C. has been granted, and the technique which has been perfected in our studios will be closely followed. The plays will be presented either in Montreal or Toronto, and will be broadcast simultaneously by all the C.N.R. stations.

SIGN, PLEASE!

UPON entering an exhibition held recently in New York, visitors were somewhat surprised to hear a voice, coming

Simpson wireless station he broadcast a request for some of the latest dance records. His "musical S.O.S." was picked up by the Canadian National Telegraphs' operator at Edmonton, who purchased a selection and dispatched them by aeroplane. The trapper had his records within two days. Before wireless and aerial transport the records would have been out of date long before delivery.

B.B.C.'s INTERVAL SIGNAL

AS soon as the apparatus is delivered, which should be within the next two or three weeks, B.B.C. stations will introduce an interval signal. This will resemble the ticking of a clock, similar to the sound made by several Continental stations during their intervals. But it should be made clear that the B.B.C.'s interval signal is not intended as a means of identifying the station, but to reassure listeners who have switched on during a blank period in the programme that their sets are working correctly. The interval signal will generally be broadcast when a programme falls short of its scheduled time. Where the interval is more than five minutes, piano music will

famous artiste's broadcast. After some false starts the piano was hoisted, one of the men exclaiming: "Well, Bill, I hope it goes alright over the air." Another replied: "I wish it would go on air; save us some (blank) trouble!"

END OF STUDIO OPERA

FOLLOWING the announcement (on page 852) of the new Covent Garden Opera scheme it seems that Broadcast opera from studios will soon be a thing of the past, apart from occasional broadcasts of new settings of old works appropriate to studios. The B.B.C. has long felt that opera broadcasts at its best from the actual opera house. The scheme assures the continuance and extension of the Covent Garden seasons, combining increased opportunities for the public to attend first-class performances of grand opera with adequate provision for those who, unable to attend the performances, are anxious to hear the broadcasts in their own houses.

ABOUT DICK SHEPPARD


FOLLOWING Mr. Maxwell Light's deputy talk on asthma last Sunday, in which he mentioned that the Reverend Dick Sheppard was unable to give the talk owing to a crippling attack of asthma, hundreds of anxious inquiries were received from listeners. The B.B.C. wishes to reassure them that Dick Sheppard's indisposition was only temporary, although extremely exhausting, as asthma sufferers will appreciate. It is hoped that this favourite divine will soon broadcast again

A. J. ALAN AGAIN

ANOTHER inimitable story will be broadcast by A. J. Alan on December 1 from the National and on December 2 from the Regional. The title of the story is "The Well." It is related that, while listening to a rehearsal of this story, at A. J. Alan's house, an amusing affair took place. It appears that A. J. Alan was "broadcasting" his story, by speaking into a microphone situated in a different room from whence the loud-speaker reproduction appeared. Finishing "The Well," he went on to tell a story about a man who had a pet fish that used to follow him about until one day it was accidentally drowned, but before he had finished speaking through the medium of the loud-speaker he appeared in person before his astonished audience. They had been listening to the reproduction of a gramophone record!

A GOOD SPORT

WHEN Walford Hyden arrived in the B.B.C. studio to conduct his Chinese scena during a recent vaudeville programme he found that one of the singers had been taken ill. Noticing another artiste standing by for another item in the programme, Hyden said: "Do you sing?" "A little," was the reply. "Right. Will you help me out?" "Let's have a look at it." So they tried over the number on the piano. "Fine! By the way, who are you?" "Melville Gideon." "Well, you're a good sport!" We wonder how many listeners to this particular item realised that only a "good sport" saved it.

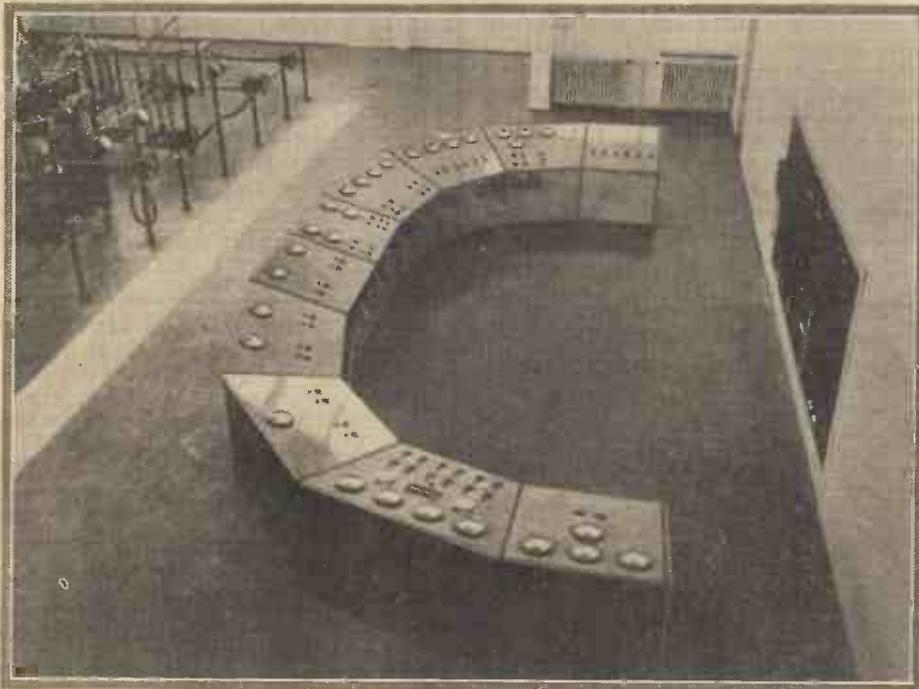

The control room of the new German high-power Regional station at Stuttgart. This "bird's eye" view of the control desk gives an idea of the large number of tuning controls and adjustments which have to be made in a transmitter, and it is interesting to compare this with the two simple control desks at Brookmans Park

apparently from nowhere, inviting them to sign their names in the book! When each visitor entered the exhibition he interrupted a beam of light directed on to a photo-electric cell, and thus automatically set a gramophone in motion, which was connected through an amplifier to a hidden speaker.


JAZZ RECORDS BY RADIO

RECENTLY a trapper, stationed at the Hudson Bay post at Fort Simpson, 700 miles north of Edmonton, decided that new records for his portable gramophone would be welcome. Through the Fort

be broadcast in the usual way. We think that, while the B.B.C. is doing an interval signal they might as well have thought of something more distinctive, in order that foreign listeners could identify and distinguish between the various B.B.C. stations.

OUTSIDE SAVOY HILL

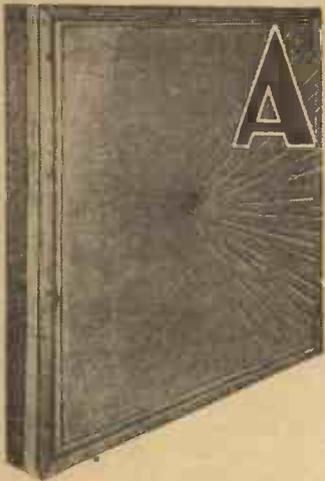PASSING through the portals of the B.B.C.'s Headquarters at Savoy Hill the other day, an AMATEUR WIRELESS correspondent noticed four struggling and perspiring men heaving up a grand piano to one of the studios, in preparation for a



A NOVEL LINEN-DIAPHRAGM SPEAKER

In the past we have described many linen-diaphragm loud-speakers all of which have been highly efficient. That described in this article, designed by W. A. HATCH, has several novel features and we place it before our readers with every assurance that it will give excellent results

THE big advantage of the linen speaker is that it enables amateurs to get high-quality reproduction at low cost. Furthermore, the amount of constructional work involved in the building of a linen speaker is so small that anyone capable of using ordinary wood-working tools should have no difficulty in making a very satisfactory job.

Moving-coil and dynamic speakers have their respective advantages, and the home construction of the former type, at least, is within the bounds of possibility. What deters amateurs, though, is the prospect of having to wind large "pot" coils, construct delicate moving-coil formers, and carry out rather tricky work at the diaphragm apex.

No such difficulties have to be contended with in the construction of a linen

diaphragm speaker. Readers who have previously made up linen speakers will know that the principle of operation depends on the stretching of a linen sheet, rendered taut by "doping" with some cellulose compound, so that the natural period of vibration is shifted to a point of no importance on the frequency scale.


With some instruments the tension on the diaphragm is obtained by means of a smaller diaphragm, also of doped linen, the two being joined at their apexes. In other designs the smaller diaphragm has been dispensed with and the tension obtained by means of a run of stranded Bowden wire stretched tightly on the framework at the

back and joined at its mid point to the apex of the diaphragm.


The degree of success obtained with a linen speaker depends very largely on correct tensioning. If the method of tensioning is not properly arranged, or if the dope used is of an inferior quality, not capable of tensioning the linen strands, then the diaphragm will be flabby and will not transmit sound vibrations over a useful portion of its area.

The new design of linen speaker shown here employs a novel method of tensioning.

(Continued on next page)

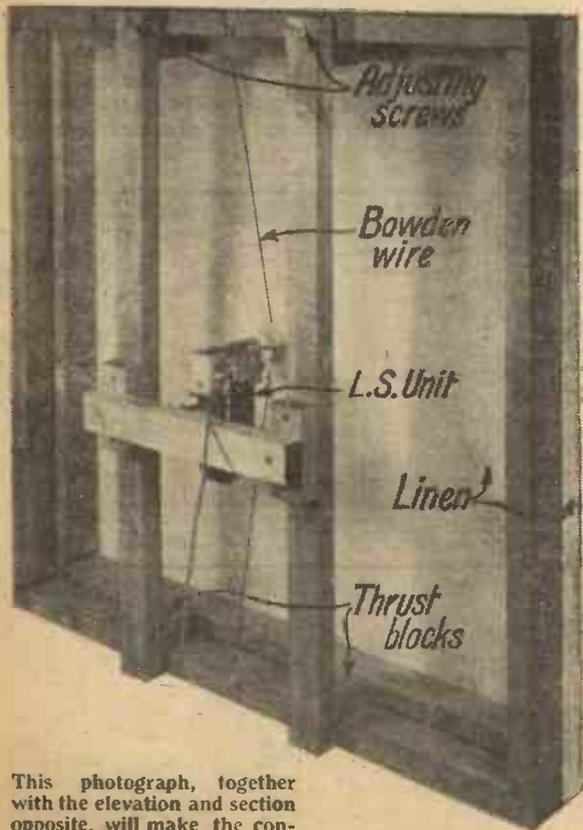

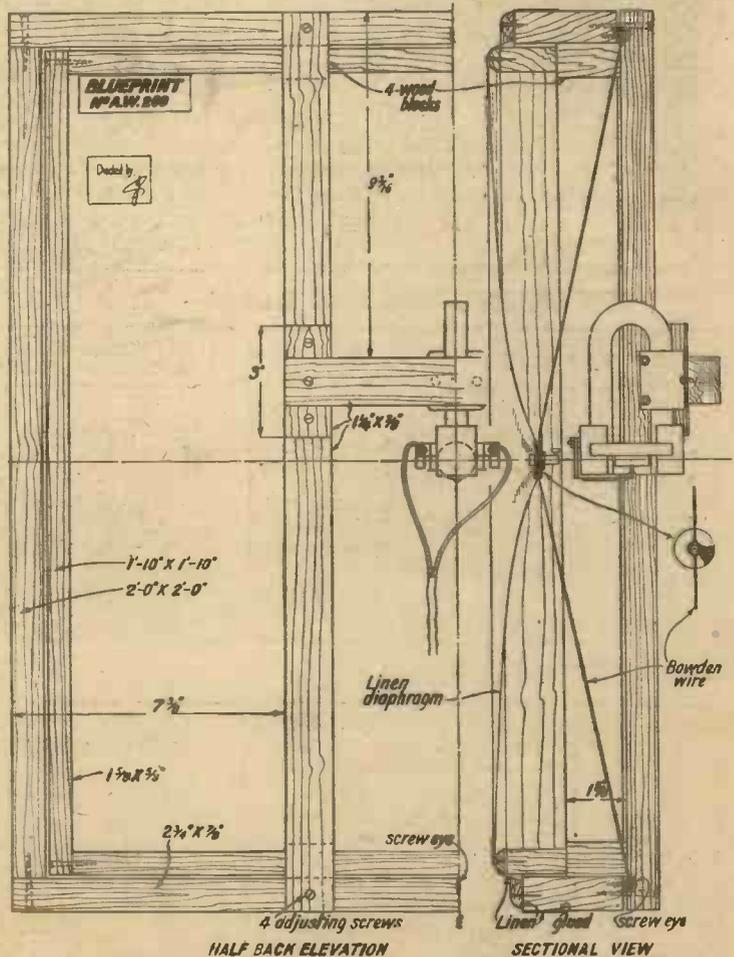This photograph, together with the elevation and section opposite, will make the construction quite clear



A full-size blueprint of this drawing is available, price 1/-

"A NOVEL LINEN-DIAPHRAGM SPEAKER"

(Continued from preceding page)

It is still necessary to use the proper dope in order to get good results. No method of stretching can compensate for imperfect tensioning, by the dope, of the individual strands of the linen. In this new speaker the Bowden wire system of tensioning the diaphragm is employed, and the novelty consists in the way in which the diaphragm is stretched at its outer edges.

Examination of the constructional diagram given here shows that the linen



The novel tensioning system can clearly be seen in this photograph

diaphragm, which is firmly secured to a rectangular wooden frame, is stretched by means of an inner frame pressing against the edges of the diaphragm and forcing it outwards.

The centre of the diaphragm is held by means of Bowden wire to the outer frame. The wire used for this tensioning must have a considerable tensile strength, for if it is affected by the constant strain on it then the speaker will be constantly

needing adjustment and the diaphragm tensioning screws will need frequent attention. It is important, also, that the wire used for tensioning should not vibrate of its own accord, for were it to do so a resonance would be set up which would nullify the good frequency characteristic of a tightly-stretched diaphragm.

Bowden wire is very suitable; use the kind covered with a protective compound, which has a deadening effect on any resonance which the stranded wire alone may exhibit.

The Linen

Practically any type of unit may be employed, but naturally only the best results can be expected with a driving mechanism capable of standing to quite a considerable amount of volume, and at that point showing no signs of overloading.

Complete kits of materials for making up this speaker can be obtained from specialists in linen speaker construction; the Kone-Dope Co., for example. If you are purchasing your own linen, then take care to get material of good quality, which will not burst its threads when the tensioning is being carried out.

Good quality Irish handkerchief linen is the proper material to use. It is unfair to expect good results from a diaphragm made up from poor linen.

The Framework

The frames can be constructed of any good hard wood and all measurements can be obtained from the accompanying drawing, which shows the speaker frames in part section. The outer frame is used as the support for the linen and the smaller frame is used for tensioning. It will be seen that the diaphragm is attached along its edges to the larger diaphragm with glue, and is further secured by means of stout beading, which should be screwed in place when the diaphragm has been stretched, evenly but not at drum tightness, across the frame.

The Bowden wire is secured at its ends by small screw eyes, the ends of the wire being twisted over and soldered. The connection to the chuck in the centre of the diaphragm can be made either by dividing the strands and pushing the chuck through, or, alternatively, a special chuck, supplied complete with the Bowden wire fixing, and which can be obtained from most wireless dealers, can be employed.

Doping

Doping and stretching should be carried out alternatively as with previous linen speakers. The final stretching should be carried out while the diaphragm is still wet with dope. As the fixing screws of the smaller diaphragm are tightened, the diaphragm is forced outwards, so increasing the tension on the Bowden wire. When the diaphragm is dry, it should be then at drum tightness and should emit a "plonk" when tapped with the finger.



With some of the special linen diaphragms supplied by kit manufacturers, the tightening can be carried out simply by damping the diaphragm with water. When it dries, the tension of the threads is increased.

When fixing the unit to the diaphragm, take care to get the driving rod exactly central with the chuck in the centre of the diaphragm. If there is any eccentric strain on the driving rod, then the working of the unit may be upset, and in any case the diaphragm and driving mechanism will be acoustically damped by this side strain.


The unit must be very firmly secured to its supporting batten and the driving rod must be firmly attached to the chuck. Any looseness at either of these points may set up a disturbing chatter.

Constructors who want to make quite sure of getting good results and of eliminating any constructional difficulties should get the blueprint, which can be obtained, price 1s., post free, from the Blueprint Department of AMATEUR WIRELESS, 58-61 Fetter Lane, London, E.C.4.


MR. FLEX WANTS HIS LOG BOOK--

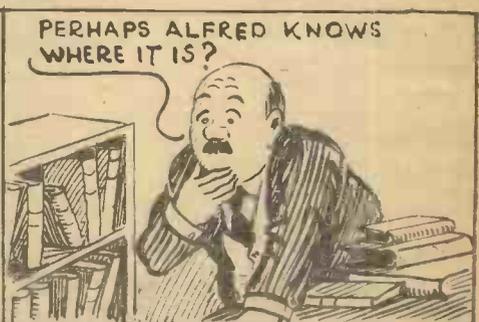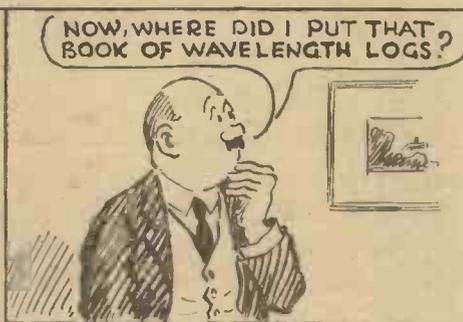

AND GETS ALFRED'S

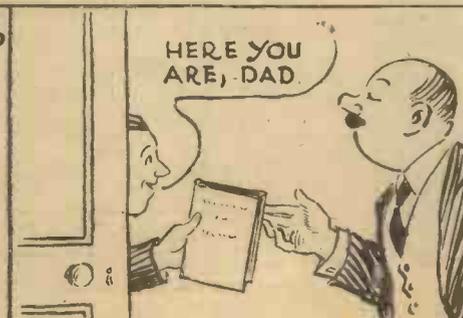

The NEWEST AERIAL CIRCUITS

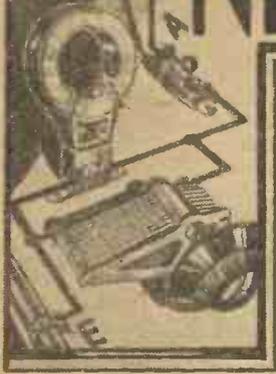

Some notes on the best methods of obtaining selective tuning

By W JAMES

At last it is being realised that from the local station we may receive several volts across the aerial tuning coil. Voltages

To adjust the coupling of the pair of coils for the best results at every wavelength and to keep the circuits in tune demanded a little patience. Nowadays the smallest number of controls must be used, and so the old method is not used.

Instead, we try and fix a value of coupling which will be fairly good over the whole tuning range. Sometimes we use a magnetic coupling and sometimes a condenser coupling, while it is quite possible to use a mixture of both.

In the coupled circuit having a magnetic coupling we may fit a small coil L (Fig. 4), and shield the pair of tuning coils.

With similar coils and tuning condensers one knob tuning is practicable. The only difficulty is that if the size of L is made most satisfactory at 500 metres, the circuit is too tightly coupled at 200 metres and broad tuning results. If, on the other hand, the coupling is fixed at 200 metres, the circuit as a whole is far too sharp at 500 metres.

We can of course, obtain an average result by setting the circuit at, say, 350 metres, depending upon the kind of coils used and how their resistances vary with wavelength.

Condenser Coupling

When a condenser is used as the coupling, as in Fig. 5, the reverse tuning characteristics are obtained.

method is suitable. The best value for the coupling condenser c depends upon the wavelength range being covered and the characteristics of the coils. A usual value with 2-in. coils of No. 26 or No. 28 wire, covering 200 to 550 metres, is .015 microfarad.

With a larger value the tuning is sharper, and if a lower capacity is used, the aerial circuit tunes more broadly. Thus there is room here for experiment and it might even pay to have a second condenser to switch in over part of the tuning range in order to secure the finest results.

Filter Circuits


Aerial filter circuits are greatly used in American sets, and as a rule they have good characteristics. They must of course, be carefully set up or the two circuits will not tune properly.

With the two condensers and coils matched, we have to adjust on the one hand for the effective capacity of the aerial and on the other hand for the capacity of the valve and its holder, to which must be added the wiring.

It is obvious that if, with both tuning condensers set at zero, the total capacities of the circuits are alike, the circuits will tune properly, because at any point over the range the capacity in both circuits is equal.

of 6 are common, given an outdoor aerial and a good coil.

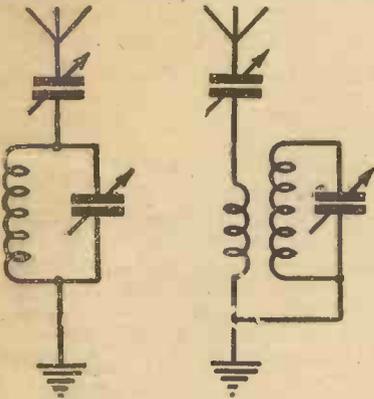Relatively few people receive so great a voltage, but even a volt or two is enough to upset many screen-grid valves. These valves, as normally used, simply will not deal properly with signals of a volt or more.



Figs. 1 and 2. These are two usual aerial circuits but neither is very selective

The result is that distortion is introduced in the very first stage of the set and the tuning is made flat.

Volume Control

With a correct volume control we could avoid these difficulties to an extent, but the best practice is first to select the signal and then to magnify it. With this arrangement the screen-grid valve is not likely to be overloaded and broad tuning and distortion are, therefore, minimised.

The usual aerial circuit, Fig. 1, or perhaps Fig. 2, is really not very selective. You may have a good coil and tuning condenser, but the fact remains that the shape of the tuning curve is not really satisfactory.

The local station comes through even when the circuit is tuned, perhaps, 40 or 50 metres off. It is, therefore, magnified along with the signal to which the circuit is actually tuned and interference results.

In the early days of broadcasting we used to employ two-circuit tuners (Fig. 3). The position of one coil relative to the other could be altered. We used a two- or three-way coil holder and plug-in coils, and pretty good selectivity was obtained—actually much better than with some of our present-day arrangements.

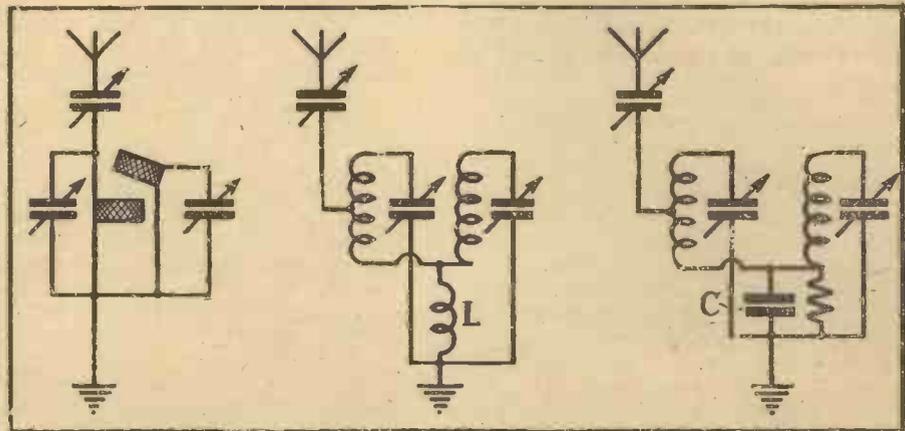


Fig. 3. An early double-tuner arrangement. Fig. 4. A coupled circuit with magnetic coupling. Fig. 5. A coupled circuit with condenser coupling

tics are obtained. Thus, if we set the condenser for the best results at 500 metres, the tuning is probably too sharp at 200 metres. We must remember, however, that an ordinary tuned circuit tunes more broadly at the lower wavelengths. It is, therefore, possible that the combined tuning of a set may be perfectly satisfactory and, so long as the characteristics of the aerial circuit are reasonably good, the

Perhaps the easiest way of testing is with a meter in the anode circuit of the detector valve. With a leaky-grid detector the meter will read less current when a signal is tuned in, and when the anode-bend method of detection is used the current increases with a signal.


Tune to the local station first and adjust the pre-set condenser in the aerial circuit
(Continued at foot of next page)

A HOME-MADE PICK-UP

MOST amateurs have all the necessary "ingredients" for the making of an excellent pick-up lying among the junk in their possession, only waiting to be assembled and put into commission.

For the pivot bar use the third contact stud (5BA this time to reduce weight) and, after cutting to the correct length to pass between the pivot points, slightly counter-sink both ends dead centre.

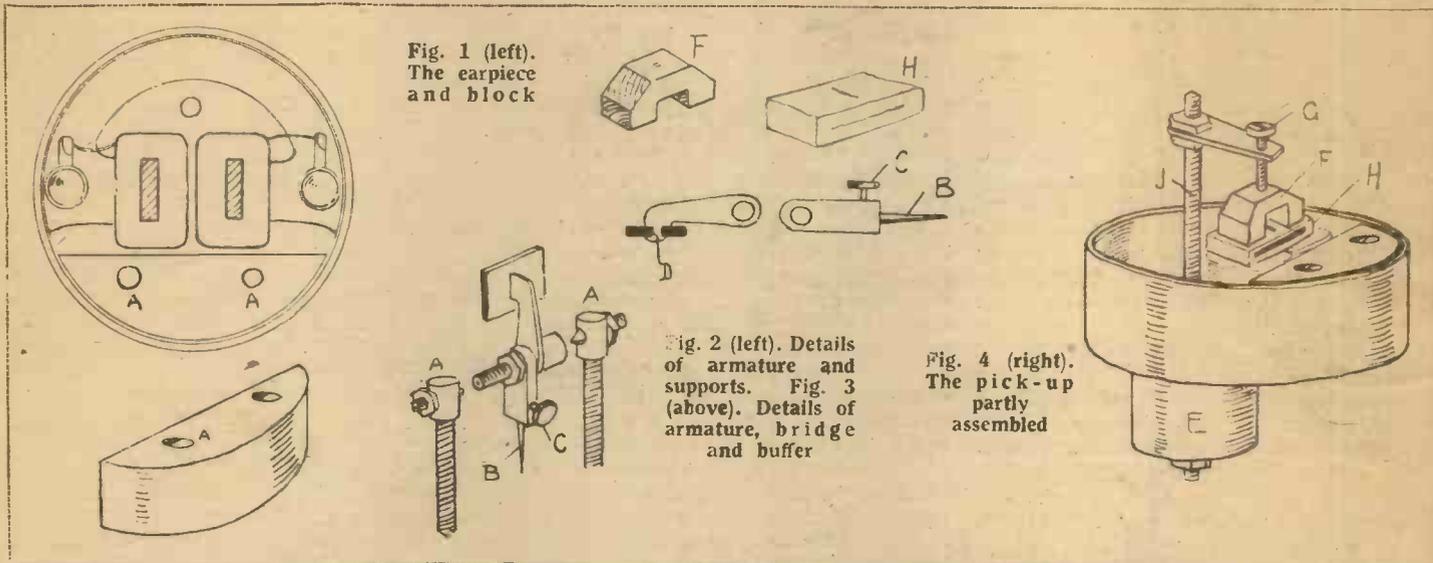20 gauge, cut to cover both pole pieces and drilled in the centre to take the brass tag (D). Take a little care in assembling these parts in order to get the armature exactly over the pole pieces and parallel



You will need nothing but a single ear-piece from a pair of headphones, three contact studs, some small pieces of wood, brass and iron, a piece of rubber sponge, and a few odd screws and nuts.

The principle used in the pick-up to be described is that used on the ordinary gramophone sound-box, the only alteration being the substitution of the light iron armature for the mica diaphragm.

Detach the earpiece and remove the cap and diaphragm. You will find that, apart from the pole pieces in the centre, one-half of the aluminium casing is unoccupied. Cut a piece of hard wood to fit snugly into this space (Fig. 1), the level of the small platform thus formed being brought to the height of the pole pieces. This block forms the anchorage of the mechanism operating the small armature.

Through both block and casing drill two 4BA clearance holes to accommodate two 4BA contact studs (A) about 3/4 in. apart and parallel with the pole pieces. After tapping a 6BA thread through their heads (Fig. 2), insert the two contact studs and pull down tightly by means of nuts behind the casing, taking care to have the threaded holes in direct line. Two 6BA screws pointed at one end, and complete with lock nuts, are now inserted, points inwards, and we have everything in readiness for the moving parts.

Now study Fig. 2, and it will be seen that, while the brass needle holder has to be of sufficient substance to take both the hole for the needle (B) and that for the anchor screw (C), the small bar carrying

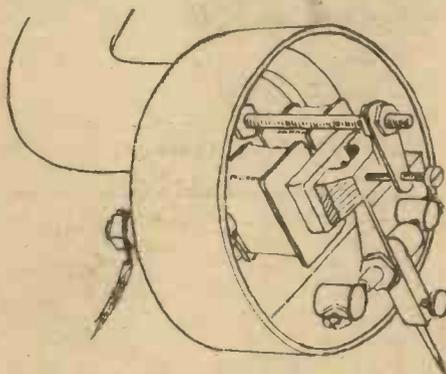


Fig. 5. The complete pick-up

the armature is much lighter, as it is here we have to keep down the weight. This bar must be of such a length that the armature shall be immediately over the two pole pieces (Fig. 4). File the end of the brass bar as shown in Fig. 3, leaving a small tag (D) for riveting on the armature. Both bars are now drilled to fit on to the pivot bar and screwed up tightly.

The armature is of soft iron, about

to their surface when about 1/8 in. away from them.

If the movement is now assembled at the pivot points it will be found that, while the whole mechanism works freely, there is nothing to prevent the armature leaving the magnets. This must be kept close, at the same time leaving play for the movement to operate.

Here we kill two birds with one stone, by fixing a piece of 4BA rod through the other half of the casing J, one end holding a wooden boss E for inserting into the tone arm of the gramophone, while the other end holds the movement in place.

For this I have used a wooden bridge F, the size of the armature, held in place by an adjustable 6BA screw G in a small brass plate at the top of the rod. This bridge, which must clear any moving part, presses on a rubber sponge buffer H, and as the sponge is cut to envelop the iron it will be seen that not only is the movement held in place, but that a most useful damping adjustment can be made at the screw G. Cut the rubber sponge with a sharp chisel.

The pick-up is now complete and, provided all nuts are well tightened up to prevent undue rattle, you can fix the unit to your gramophone and connect up to your set.

C. H. SPARKE.

"THE NEWEST AERIAL CIRCUITS"

(Continued from preceding page)

Afterwards, tune to a fairly strong distant station and once more adjust the pre-set condenser to obtain good tuning.

A point to note now is that with the setting of the pre-set condenser found in this way the signal strength may not be the maximum. To try this, increase the capacity of the pre-set condenser a little

and also that of the trimming condenser connected across the second tuning condenser, that is, the one joined to the grid of the valve. In this way the circuits will be kept in tune and the strength of the signal will be varied.

It is most important that the tuned circuits be properly ganged, and this can hardly be carried out unless a system is used. To adjust the trimming condensers without method will only end in confusion,

and I believe the poor results sometimes obtained from a filter circuit are due solely to the circuits not being carefully ganged.

The Scottish Orchestra is again to broadcast a number of its concerts during the season. The arrangement includes the stipulation that a certain number of contemporary Scottish works will figure on the programmes



For all round service in a domestic receiver, the combination of a screened grid high frequency amplifying valve, a detector and a pentode output valve cannot be bettered. In a correctly designed receiver, these three valves give results definitely superior to the best 5-valve set of a few seasons ago, from the point of view of range, sensitivity and quality—and for a

very much lower expenditure of both low and high tension current.

Such a combination, even in the hands of the merest novice, should render possible the reception, at good speaker strength, of a reasonable number of foreign transmissions as well as the local stations.

The following types should be employed in a screened grid, detector and pentode combination:—

L.T. Supply	Mullard Screened Grid	Mullard Detector	Mullard Pentode
2-volt accumulator	P.M.12	P.M. 2DX	P.M.22
4-volt accumulator	P.M.14	P.M. 4DX	P.M.24
6-volt accumulator	P.M.16	P.M. 6D	P.M.26
A.C. Main	S.4V or S.4VA	354V.	P.M.24 or P.M.24A

Mullard

THE · MASTER · VALVE

Advt. : The Mullard Wireless Service Co., Ltd., Mullard House, Charing Cross Road, London, W.C.2

Don't Forget to Say That You Saw it in "A.W."



STARTLING!!

IN **29/6** OAK

**how much it does
how little it costs**

Whatever the power, this amazing Ormond Loudspeaker will handle it with an ability unexcelled by any other speaker of its class. From deepest bass to highest treble—throughout the whole musical range—perfect! It is by far the most wonderful value ever given and it's **ORMOND.**

Fitted with the famous Ormond "Four Pole Adjustable Loudspeaker Unit," and a cone of specially selected material and mounted in handsome figured Oak Cabinet.

**The
ORMOND
"Popular"
LOUDSPEAKER**



**For
PUNCH
POWER
& PURITY**

THE
**ORMOND
ENGINEERING
CO., LTD.,
ORMOND HOUSE,
Rosebury Avenue,
LONDON, E.C.1.**

Telephone:
Clerkenwell 5334/5/6 and
9344/5/6
Telegrams:
"Ormondengi, Smith."

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

Oh Your Wavlenek!

THE LOUD-SPEAKER TRIUMPHS

THE loud-speaker is gaining ground everywhere. Not so very long ago, musicians, especially those with "extremist" minds, looked upon the loud-speaker and broadcasting with suspicion and distrust. Sir Thomas Beecham said most unpleasant things about them. But the time has come when it is, in many cases, more satisfactory musically to sit at home and listen to a concert on a good loud-speaker than it is to go to the concert-hall. While it must be admitted that the loud-speaker does not put over the personal contact and personality of the artistes at the concert-hall, this drawback of not being able to see what is happening at the other end is frequently advantageous. Some of the finest vocalists, choirs, and orchestras are not very pleasing to look upon; and, again, many instrumentalists obtain effect—and subsequent applause—by means of physical flourishes and facial contortions.

HANDSOME CONDUCTORS

THE question of appearances works both ways, of course. Orchestral conductors are invariably aided by their personal appearance and the dignity which is inspired by command. Sir Thomas Beecham, Sir Hamilton Harty, Sir Henry Wood and others are good to look upon and fascinating to watch. But in watching them control their large orchestras, the eye is again taking the mind away from something which should be exclusively for the ear. When listening to the orchestra on a good loud-speaker, one is hearing it under conditions which permit concentration on the music itself, and, with the microphone placed ideally for picking up every instrument, the listener at home is frequently much better off than brother listener in the actual hall.

ABSORPTION

THE performance of a receiver in a town is usually much less satisfactory than the performance of the same receiver on an equally good (or bad) aerial in the suburbs or country. Quite apart from the question of local station interference, static and other noises, H.F. pick-up from distant stations is appreciably less. This is due to the screening effects and absorption of buildings, especially those with girders and metal frameworks.

RETAILED RADIO

THE plan of having a central receiving station and sending the radio programmes to subscribers by telephone line is spreading. There is a class of listener who does not want to be bothered with a receiving set however simple, and there are cases where acute local interference from trams, electric signs and the like make radio reception practically impossible. For these listeners the local broadcast suppliers are catering, and they provide their subscribers with a loud-speaker and switch; a

broadcast programme is always on the line, in the same way as the distribution of broadcast music was made at the Radio Exhibition. Blackpool is the latest town to have such a central receiving station, and I hear that very fine results are being obtained. But if this practice spreads, the B.B.C. would do well to extend a little tactful aid to their self-appointed retailers. Badly designed receivers, with inadequate power stages and incorrect feeding of land lines will cause disappointment. The B.B.C. has done a great deal of work in this particular field, and the circulation of the design of their super Olympia receiver would protect listeners who wish to make use of this new kind of service. It should be added that a broadcast licence has to be taken out for each radio line used, so that the B.B.C. will lose nothing by the increasing use of "retailed radio."

FAULTY CONDENSER EFFECTS

THE most effective remedy for a broken condenser, of course, is to replace it with another one. The symptoms in a grid circuit, are no signals and failure to oscillate. It is perhaps a good thing when one finds a receiver not working properly to suspect some of the fixed condensers, perhaps replacing them with other ones in order to see if this clears up the difficulty. If the trouble still remains, of course, the condenser can be assumed to be O.K., but if there is a defect, then the substitution of another condenser will often cure the fault and save a good deal of bother.

"DUD" COMPONENTS

I WONDER if components to-day are really as reliable as we think they are. In the early days of wireless we often expected a component to be faulty. The wise birds would test all their parts before putting them in a set. To-day, owing to the great improvements which have been made, not only in methods of manufacture, but in the testing adopted by the manufacturers, before the products are sent out, we are inclined to take all components at their face value.

Nevertheless, cases do arise where trouble is experienced due to actual defects, and because of the state of mind into which we have allowed ourselves to be lulled, these defects are much more difficult to detect. Let me quote an instance which occurred only the other day when I was experimenting with a hook-up containing quite a number of valves. I was, in fact, trying out a little idea of my own. The preliminary experiments had worked out so well that I

thought that it would perhaps be better if I built up the components more or less properly to avoid lots of straggly leads. This, by the way, is often a useful thing to do, partly because it shows definitely whether the effects being obtained are really due to the causes you imagine. If the same result is obtained when the set is wired up properly, then everything is in order, but if the results are much worse than they were in the hook-up stage, it shows that unsuspected effects were coming into play before, and one must, therefore, go back and find out what these effects were. It is only by proceeding in this manner that one can really determine whether any particular new stunt is of any value or not.

CAUGHT NAPPING

HOWEVER, when I built the arrangement up for the second time I found the results not just worse than they were before, but practically hopeless. I could get nothing through except the local station, and try as I would, the old liveliness had completely vanished. I searched everywhere for a cause, but I could hardly believe that the mere alteration of the layout had completely destroyed what had originally seemed a very promising hook-up. After considerable playing about I suddenly found that the grid condenser in my detector was not a condenser at all, but a piece of bakelite without any inside. I do not mean to say that there were no condenser plates at all, but that there was a complete disconnection internally. Replacement of this condenser certainly improved matters, but it did not altogether overcome the difficulty, and I therefore had to resume my search. Strange as it may seem I subsequently found *another* fixed condenser in exactly the same condition. Two completely broken fixed condensers in one hook-up is rather an extraordinary state of affairs, and I must admit that it was the first time it had happened in my experience for some considerable period. At the same time I have had trouble with fixed condensers before, which goes to show that, particularly in these days of cheap construction, errors in assembling may creep in, and defective components may pass the test bench.

OUTWARD APPEARANCES

I HEAR a certain amount of criticism levelled from time to time against the designers of sets for their apparent lack of artistic inspiration in the matter of "externals." Certainly many of the sets now on the market do strike a dead-level of mediocrity as regards outward shape and size. This is a drawback to those—especially the ladies—who feel that an obvious "box of tricks" is somewhat out of place in the living-room. In the case of loud-speakers, designers seem to be able to give their imagination freer rein. One can buy a speaker disguised as a hanging picture or wall-plaque, or even as a lampshade.

A SPECIAL CHRISTMAS NUMBER NEXT WEEK

Watch for the full-coloured cover

USUAL PRICE, 3d.

:: :: **On Your Wavelength! (continued)** :: ::

But a set is always the same old brick-shaped piece of work. I know of more than one instance where a harassed paterfamilias has been compelled by "she who must be obeyed" to hide the wretched thing behind a screen, out of sight. Only by doing so could he preserve the harmony of the furniture, of the B.B.C., and of domestic life. Now, perhaps, the manufacturers will sit up and take notice.

SPLENDID CONDITIONS

At the time of writing, conditions for receiving foreign stations are, and have been for some days, just about as good as I have known them at the time of year. The receiving set seems absolutely alive, and if you have one decent stage of high-frequency amplification, there is hardly a tick on the dials that doesn't bring in something. Atmospheric are conspicuous by their absence, except at rare moments, and there is undoubtedly far less morse interference on the broadcast band than there was even a year ago. This is generally speaking, for there are evenings when spark morse is a perfect nuisance for considerable periods. The other night our old friend, FFB, using the flattest tuning that I have ever come across, was messing up the patch of the broadcast band which contains some of the best received European stations. Sometimes, too, sparks spoil one's reception of Budapest and Vienna.

SOME NEW STATIONS

There are some fine new stations in operation on the broadcast band just now which the DX-minded reader should certainly look out for. Two of the best are Genoa and Strasbourg. Genoa has been working lately on a wavelength of about 312 metres—just above Cardiff—and he comes in with something like the punch of Turin. Strasbourg is supposed to have a wavelength of 346 metres, but when I found him the other night he was operating above 370 metres. You cannot mistake Strasbourg, for all announcements are made first by a woman in French and then by a man in German. Both Genoa and Strasbourg are at work on Sunday evenings during the close time of the home stations, and you shouldn't, therefore, have much difficulty in finding them. Strasbourg is a PTT station. Genoa, like Turin, relays the Milan programmes. These, by the way, are jolly good, particularly on Sundays.

WHAT A PIONEER SAYS

An exceedingly interesting article by Sir Ambrose Fleming, the inventor of the diode valve, appeared the other day in one of the lay papers. The subject was the progress of wireless in 1930. Sir Ambrose dealt first of all with

the big improvements in selectivity that had been made, and referred particularly to the Stenode, in which he sees the solution of one of the greatest problems of television. With ordinary receiving gear and sideband ideas of wireless, one of the difficulties about television is that the transmission of any but the smallest image will necessitate the use of a channel from five to ten times as wide as that allowed to any broadcasting station under the present wavelength plan. With the Stenode no trouble results, and large images can be transmitted and received without there being any interference with stations working on frequencies as near as 5 kilocycles on either side of the television station.

A VALVE SUGGESTION

I WAS wondering the other day whether it would not pay valve makers to grade their products. You will see what I am driving at in a moment. Supposing that you are buying a fixed condenser by a first-rate firm, you will probably purchase one of ordinary quality whose capacity is guaranteed to be within 5 per cent. of the stated

value. Standard quality fixed resistances, again, are guaranteed accurate to within 5 per cent. Thus, if you pay five shillings for a wire-wound 50,000-ohm resistance made by a reputable firm, you know that its value lies between 47,500 and 52,500 ohms—limits which are quite near enough for ordinary purposes. But if you want a condenser or a resistance accurate to 2 per cent., or even 1 per cent., you can obtain these by paying a little extra for them.

Now for valves. I would like to see these classed in much the same way. The tolerances allowed in the impedance, amplification factor, and mutual conductance by valve makers' test departments are small. They are on a par with the 5-per-cent. accuracy of resistances. In the ordinary way, the very slight differences between one valve and another of the same make and type are so small that they do not affect the working of a receiving set. But in very sensitive high-frequency circuits, or in low-frequency circuits designed for special purposes, one does sometimes require valves either to match one another or to show none but the most minute divergencies from standard curves and figures.

What I would like to see, then, is a standard-grade valve sold at the present price, or perhaps a little less, and a precision valve of guaranteed close accuracy sold at, say 25 per cent. more.


TROUBLE-SAVING

I BELIEVE that the precision grading of valves would pay makers well, and it could be quite easily carried out. It would mean simply that in the test department any valve which showed characteristics identical with the standard, or only minutely different from it, would pass into the precision class, whilst others with slightly greater variations would be graded as of standard quality. This kind of thing would be a very great saving of time and trouble to experimenters who wanted to match valves accurately. As matters are, it is often a lengthy and fiddling business to do so—and an expensive one. You must have a pretty large stock of valves and you have to go through them with the utmost care until you find a pair that are identical or almost so. Matched valves are becoming more and more in demand, since, in the search for quality, push-pull low-frequency amplification is constantly adding to its adherents, and the push-pull method of detection has now many devotees. I am quite sure that there would be a useful and a growing market for precision valves.

THERMION.

OUR CHRISTMAS NUMBER!

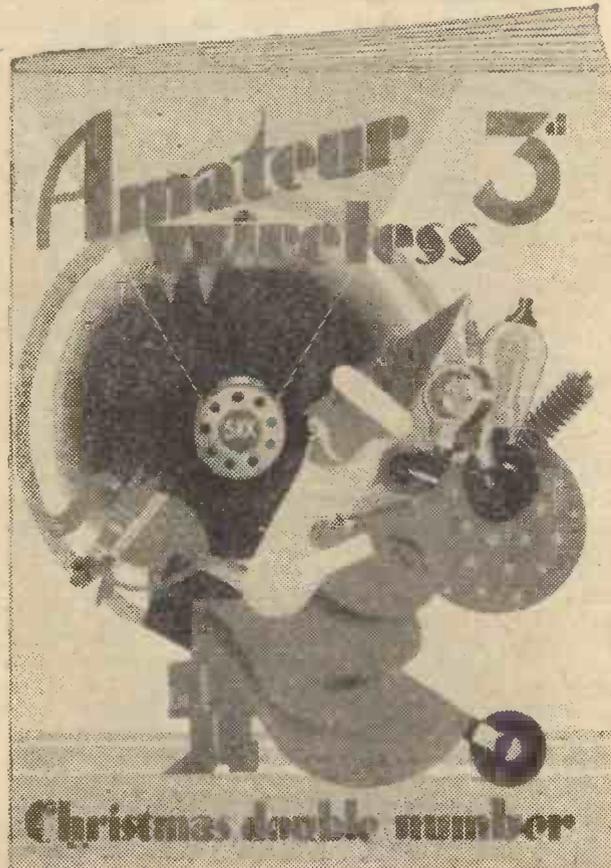WATCH FOR THIS COVER IN FULL COLOURS NEXT WEEK



ORDER YOUR COPY NOW - - USUAL PRICE, 3?
A BUMPER ISSUE, 76 PAGES

Wireless on slow trains in Italy is being installed on the line between Rome and Turin. Earphones will be available to passengers at a small charge.

THE HOW AND WHY OF RADIO

XI—THE ABC OF LOW-FREQUENCY AMPLIFICATION

If you are a beginner in wireless, now is your chance to gain a clear conception of its theory and practice. In this series of articles, specially prepared for the beginner, no previous knowledge of wireless is assumed. It is intended to deal with every aspect of the subject and the whole series will endow the beginner with sufficient knowledge to enable him to derive the greatest possible interest from the fascinating hobby of wireless

BETWEEN the detector and the output valve an intermediate valve is nearly always required. This is because the low-frequency voltage, separated by the detector from the high frequency of transmission, is not big enough to load the power valve,

valves, let me emphasise two guiding rules. Firstly, we must ensure an even response curve. That is a technical way of saying that we must make sure that the output from the low-frequency amplifier is of the same form as the input, differing only in amplitude. At the input the high notes, middle register, and low notes will bear a certain relative prominence to one another. This same relative make-up of the musical scale should appear at the output. The job of low-frequency amplification is to amplify, not to modify. Sometimes the input is not pure, in that certain notes are unduly prominent. Only then can low-frequency amplification be allowed to distort the input, in order to overcome some initial and undesirable emphasis.

Just what is this anode impedance? It may be the primary of a transformer, a choke winding, or a non-inductive high resistance, depending on whether transformer, choke-capacity, or resistance-capacity coupling is employed. The transformer is by far the most used low-frequency amplifying coupling. Its simple connections, with the two valves it is coupling together, are shown by Fig. 1:

The primary winding forms the anode impedance of the valve preceding it. If the valve has an impedance of 20,000 ohms, the primary of the transformer should have an impedance of not less than 60,000 ohms, at a stated frequency. Here the beginner will again find a snag in relating theory with practice, for the transformers on the market are seldom accompanied by any useful data. Only a general rule can be observed to conform with the impedance

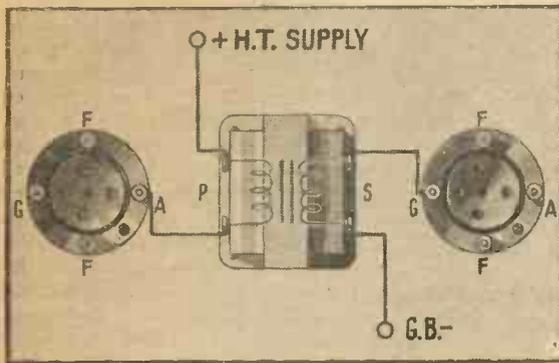


Fig. 1. Transformer coupling is the most commonly used type

which cannot, therefore, operate the loud-speaker.

Yet a study of the average three-valve set of to-day will not, at first, show the presence of a low-frequency valve. The first valve may be the high-frequency amplifier, the second the detector, and the third the power valve. Where, then, is the low-frequency valve?

The answer is that the detector and the power valve, in addition to their main functions, also work as low-frequency amplifiers. So much so that, with a suitable coupling between the detector and power valves, a further valve for the express

secondly, to obtain even amplification, an observance of the impedance rule. The impedance in the anode circuit of the low-frequency valve must be not less than twice the impedance of the valve itself. Now the great difficulty about this rule is hardly ever referred to, but I intend to put beginners on their guard. It is all very well to say the impedance of the anode circuit must be twice that of the valve, but just what is the impedance of the valve under working conditions?

No amateur has any way of answering that question. The impedance of the valve is usually measured at zero grid volts and 100 anode volts. Assuming that the anode voltage actually applied to the valve is about 100 volts, one must think of the altered conditions brought about by the bias on the grid, often very different in value from the zero volts determining the nominal impedance of the valve.

In practice, the impedance of the valve is usually something greater than the value given in the maker's list of characteristics. By making the anode impedance three times the impedance of the valve, one can usually be sure that the impedance requirement for good quality is being observed.

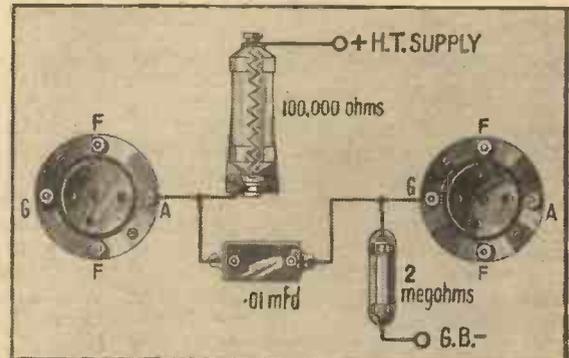


Fig. 3. Resistance-capacity is popular and possesses many advantages

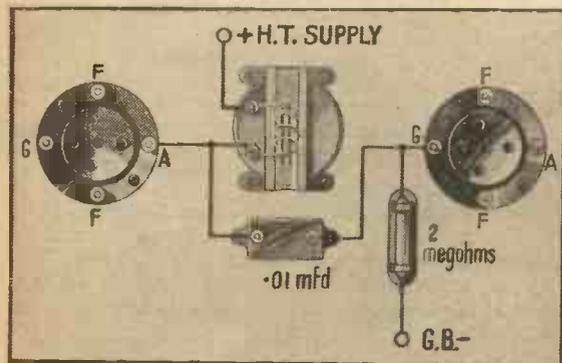


Fig. 2. The choke-capacity method does not give a voltage step-up

purpose of low-frequency amplification is often not wanted.

Before we talk about the different methods of coupling together low-frequency

ratio requirement.

This rule is based on a limitation common to all transformers, namely, that only a certain amount of wire can be used for the secondary, beyond which very bad effects are produced. So when a high ratio of secondary to primary turns is wanted, the primary is reduced, instead of increasing the secondary. The fewer the primary turns, other things being equal, the lower the impedance of the primary. So if a high-ratio transformer is used, in order to gain a big step-up in voltage, it is wise to choose a medium-impedance valve, say 20,000 ohms. A low-ratio transformer is more likely to have a high-impedance primary than one with a high ratio. But with a good low-ratio transformer one can use a much higher impedance valve. And since a high-impedance valve usually has a high amplification factor, it greatly offsets the disadvantage of the low ratio.

(Continued at foot of next page)

ALL ABOUT B.B.C. AUDITIONS

By SAVOY HILLER

THERE are, of course, several varieties of auditions at the B.B.C.—vaudeville, dramatic, instrumental, musical comedy, operatic and concert, and even talks.

Each of these sections is run by a different department and each body of officials responsible for auditions is allowed to use its own method of procedure.

Let us take vaudeville, for example. The B.B.C. is only too willing to give every applicant an audition, but such applicant must have what is known on the music hall stage as "an act."

It is not a bit of good just saying, "Oh, I sing comic songs," or, "My partner and I do cross-talk" your work must have been properly rehearsed and arranged into a five-, ten-, or fifteen-minute item.

Originality Necessary

Once you can show that you have got something like this, the B.B.C. will at once give you an audition, and if you do well, you are more than likely to get dates.

Of course, it is not easy for a new "act" to, shall I say, get away with it, because to be successful you must have something about you which is different to anyone else. Imitation, although the sincerest form of flattery, is no use. You must remember that the B.B.C. has the services of a great many stars already.

As an example: suppose you are a guitar player—well, it is not a bit of good just being a good player. You must have originality or personality or new method to "put it over." You see, the B.B.C. already has Mario de Pietro and his guitar playing is just about the best in the country.

Vaudeville auditions are run under the following system. A studio is connected via the microphone to a listening room in



Auditions are usually given in either No. 4 or No. 8 studios. This is a photograph of No. 8

another part of the building, where sit one or two experts. As soon as everything is ready, the first "turn" is shown in and another official in the studio announces to the listeners that, "No. 1—a comedian—will sing."

Judged on Capability

During and after No. 1's performance, the listening experts make notes independently of each other for comparison later.

After No. 1 comes No. 2—a xylophone player, for instance—and so on for perhaps a dozen different tests.

You see, the advantage of the listening room is that the auditors, as we might call them, never see the artistes, so that everyone is judged by their broadcasting capabilities only, appearance, bad or good, not entering into it at all. As well as making notes on performances, the listening experts also each jot down their opinion as to an artiste's worth in guineas, so that when the verdicts are compared later, the booking manager can get some idea as to what amount to offer them.

I am sorry to say, however, that the percentage of successful auditions is depressingly low. Last year only one per cent. passed the tests.

Dramatic auditions, or auditions for play-acting are also conducted by means of a listening room. In this case candidates are required to read a few lines from a chosen play, recite a little poetry, do some-

thing from Shakespeare (this is optional), and give a reading from a daily newspaper. If, of course, they should know languages or dialects, they are allowed to render a passage or two from these, also.

A Committee of Experts

Now that the B.B.C. has a repertory company for plays, however, there is not much call for outside talent in dramatic work.

Vocal and instrumental auditions for orchestral, concert and operatic work are held by a committee of experts and in the listening room there are often as many as eight or nine persons "taking" an audition.

The biggest bug-bear in vocal auditions is, of course, "wobble," or more technically, "vibrato," and any one with the slightest trace of it has little chance of success.

Of course, hundreds of artistes who have not passed these tests are still wondering why, because the B.B.C. never gives a reason for failure, being content with the words: "We regret to inform you that your voice was not considered suitable for our 'medium' (microphone)," or something equally non-committal, but in my opinion, and I have attended many auditions at Savoy Hill, in the capacity of spectator of course, the B.B.C. system represents fairness itself; and as for the studio officials who conduct the tests in the studios, they are the last word in courtesy.

"THE A B C OF LOW-FREQUENCY AMPLIFICATION"

(Continued from preceding page)

In the choke-capacity method of coupling there is no step-up in voltage. The overall amplification of a stage of choke-capacity coupling, as shown by Fig. 2, cannot be greater than the amplification of the first valve, and in practice is always less. Variations in this method of coupling provide for a step-up in voltage by tapping the choke coil. This system is now seldom used, but the third form of coupling, shown by Fig. 3, is still a good second to transformer coupling. This is the resistance-

capacity coupling, widely adopted to ensure good-quality amplification. But that was before the existing high-quality transformers were available.

In resistance-capacity coupling it is easy to conform with the impedance rule already mentioned, because there is no difficulty in making a high resistance free from unwanted capacity effects. The value of the resistance should be not less than three times the valve impedance. And that value determines the value of the coupling condenser and grid leak.

We have so far been dealing with the low-frequency valve preceding the coupling, but we must end these notes by a reminder

that the power valve following the coupling is also a low-frequency amplifier, subject to the same impedance rule as applied to the preceding valve. In the anode circuit of the power valve is the loud-speaker. Its impedance should be greater than the impedance of the valve, or at any rate not less.

Sometimes the impedance of the loud-speaker differs so much from the impedance of the power valve that the two can only be reconciled by using an output transformer, the primary matching the valve impedance and the secondary matching the impedance of the loud-speaker.

HOTSPOT.

THREE NEW MARCONI VALVES!

COMPLETING A WONDERFUL 2-VOLT SERIES!

S2/c

A new screen grid valve which at last provides, in perfectly blended unison, every feature required in the ideal H.F. amplifier. Marconi S2/c combines a very high amplification factor with very moderate impedance; enormous magnification is thus easily obtainable in any receiver; at the same time the minute self capacity ensures perfect stability. Rigidly constructed and unvarying in characteristics, S2/c will set new standards in successful H.F. amplification **20/-**

L2/b

Remarkably high mutual conductance—1.55 MA/volt—excellent amplification combined with particularly fine reproduction—these are outstanding points in the performance of Marconi L2/b, a new 2-volt low frequency and general purpose valve of exceptional efficiency. L2/b is a sensitive heavy duty detector, and a supreme initial L.F. amplifier; its low impedance permits of perfect reproduction with transformer coupling, the very high stage gain greatly increasing the overall efficiency of any receiver. **8/6**

P2/b

A new 2-volt super power valve of amazing efficiency with characteristics superior to those of any equivalent 6-volt type—truly a crowning achievement of Marconi research! Marconi P2/b successfully unites a high amplification factor with the low impedance of only 1,850 ohms, a figure ideally suited to the average cone or moving coil speaker. Exceptionally steep slope renders it the foremost output valve for every battery operated receiver in which ample volume, pure tone and strict economy in current must combine for perfect reception. **13/6**

CHARACTERISTICS.	S2/c.	L2/b.	P2/b.
Amp. Factor	330	15.5	6.5
Impedance	300,000	10,000	1,850
Mut. Conductance	1.1	1.55	3.5
Fil. Volts	2.0	2.0	2.0
Fil. Amps.	0.15	0.1	0.2
H.T. Volts—(max.)	150	150	150
Price	20/-	8/6	13/6

USE

MARCONI VALVES

The Valves the *G. Marconi* Experts use!





WEEKLY PRODUCTION-

**- 2,500,000 CELLS
FOR PERTRIX BATTERIES**



The Best Proof
of the Quality of
Pertrix Batteries
is the number we
:: :: sell :: ::

PERTRIX
NON-SAL-AMMONIAC
DRY BATTERIES

*Pertrix Limited,
Britannia House, 233 Shaftesbury Avenue,
London, W.C.2
Works: Redditch*

"The batteries you can trust"

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

A Weekly Programme Criticism—By SYDNEY A. MOSELEY.

Without Fear or Favour



THE RIDGEWAY PARADES

THE TALKS

AN extraordinary speech by Mr. Ridgeway, throwing bouquets at the B.B.C. through the B.B.C. microphone, concluded a series of mediocre productions. But Mr. Ridgeway apparently seems to be proud of them. Look how they were announced: "The Ridgeway Parade," "Including additional number by Philip Ridgeway," "Devised, written, and produced by Philip Ridgeway." But all this was not enough, apparently. Mr. Holt Marvel must come in to his aid.

As I say, the funniest part of the production was the speech, which apparently was not censored. Reminded me of the sort of thing that goes on on the boards, where hysteria seems to be part of the show. "I love you all, my lovely audience!"

The next series of talks, "Electricity in Our Bodies," by Mr. Bryan H. C. Matthews, bids fair to be interesting. Certainly the first one was arresting, if a bit gruesome.

The St. George Singers may be good; but, oh, the dreary stuff they sang!

In the National programme I noticed that from 7 o'clock to 7.30 there was a talk on new novels, and when that was finished another talk until 7.45. This hardly seems to be a good arrangement.

Two good speakers, however, are Professor Ernest Barker, who spoke on "What is Liberty?" and Dr. J. B. Orr, who began a series on "The Future Supply of Animal Products."

In regard to this last talk, supposing you had not read it was being relayed from Aberdeen, would you have guessed it?

Holt Marvel is one of the most energetic and enterprising young men I know, but I think he will admit that *Give Me New York* is not the best of his productions. I really do not think it was worth £2 a minute. Why does not Mr. Marvel put over his musical plays based on the music of famous masters? At Savoy Hill, however, they tell me that his numbers in any show are the best. And they ought to know!

I prefer the playing of the Luton Red Cross Band to their singing even as Persians. It didn't sound much like "A

Persian Market," but rather like Club Row.

I think we are getting to the climax of the annoyance of hearing Cockney singing during dance-band music. The latest 'orrible example was during the relay of Jack Kerr and his band from Birmingham. Apart from the fact that there was an "extra special request," there was another song about "seeing you dye by dye." I admit that "dye by dye" sounds better than merely "day by day"; but, then, this is contrary to the teaching of the B.B.C. official pronunciation, which in a moment of weakness I vowed to accept.

I ought to make mention of *Brigade Exchange* since we are likely to have more war plays. Now, I submit that *All Quiet on the Western Front* and *Journey's End* told us the worst about war, and therefore a play like *Brigade Exchange* sounds rather tame. The little gadgets which were meant to freeze our blood had all been heard before.

But I notice in this play a tendency to use a method (probably it was the same man) which is merely shouting—or no doubt the producer would prefer to use the word "declaim"—imagining that this is dramatic emphasis when it is merely irritating confusion.



Lissenden's idea of Archie Pitt

"GIVE ME NEW YORK"

DANCE BAND PLAYING

I may be wrong, but the same sort of man shouted in the same way in other productions, and I wish they would cut it out.

By careful manipulation I switched on Midland Regional to hear an operatic programme from *Faust* by the Birmingham Grand Opera Society, but I am afraid the singing of Siebel rather broke one of the important tenets of the B.B.C. regarding *tremula*, and put me completely off.

"The 1914-1918 Chronicle" was beautiful in conception, even if now and then the renderings seemed to be too sombre. It was a privilege to hear the best work from some of our best writers.

I have often paid tribute to Joseph Lewis and his orchestra, and therefore I congratulate him, and London, on his promotion.

Certainly the B.B.C. are getting away with it with their new symphony orchestra.


I paid another visit to the Queen's Hall. Although the programme was full of Bach, there was not a slackening of interest among the audience from beginning to end. Sir Henry Wood conducted, and, watching him, I thought: "How well this man is wearing!" When you are sitting in the hall, thinking back twenty-five years, when you saw him on the same platform, it makes you feel rather old!

I listened, too, to the Sunday concert, and I think that both listeners and those who saw the concert are equally fortunate.

I still seem to be out of luck whenever I switch on to the Saturday 1 till 2 o'clock programmes. What I heard last Saturday was a sort of jazzy riot, and in the past one had been accustomed to quiet music of the better sort.

And, by the way, the announcer in closing down corrected himself when he said the orchestra was "conducted by" Joseph Muscant. "Directed by" was his corrected expression.

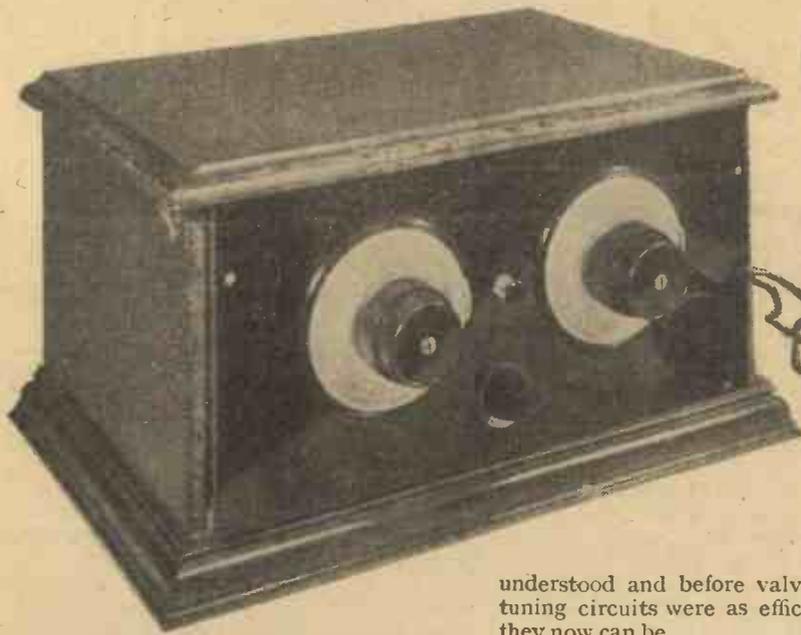Can anyone explain the difference between these terms beyond the possibility that ordinary orchestras have conductors and grand orchestras directors?



The SEARCHLIGHT

By
THE "A.W."
TECHNICAL
STAFF

If you have not previously contemplated listening on the short waves, then now is the time to do so.

Short-wave reception conditions vary from time to time, just like their broadcast band counterparts, and all regular short-wave listeners are agreed at the moment that the present time of year is productive of a whole crop of short-wave stations easily receivable on simple sets at good speaker strength. Do not be deterred by friends who tell you that short-wave listening is beset by technical difficulties, that the results are not worth while, and that you will have to spend a deal of time in listening with phones.

These things are relics of a day when short-wave reception was not properly


understood and before valves and tuning circuits were as efficient as they now can be.

It is quite possible to convert your present broadcast-band set to short-wave reception, but that is not always the most efficient way of going about the job. After all, there is little difference between making up a special set for short-wave reception and the construction of an adaptor unit to make your present set workable on the short waves. Both necessitate new parts and both are used with existing batteries and valves. You can use the valves, high- and low-tension, and grid-bias batteries, speaker, aerial, and earth as are employed for broadcast-band reception.

The set is arranged on straightforward and conventional lines, with a panel supporting the main controls, and a baseboard.

Two valves only are used, for it is felt that for a straightforward short-wave receiver to be used by the average man there is no need to go to the expense and difficulty of fitting a screen grid valve preceding the detector.

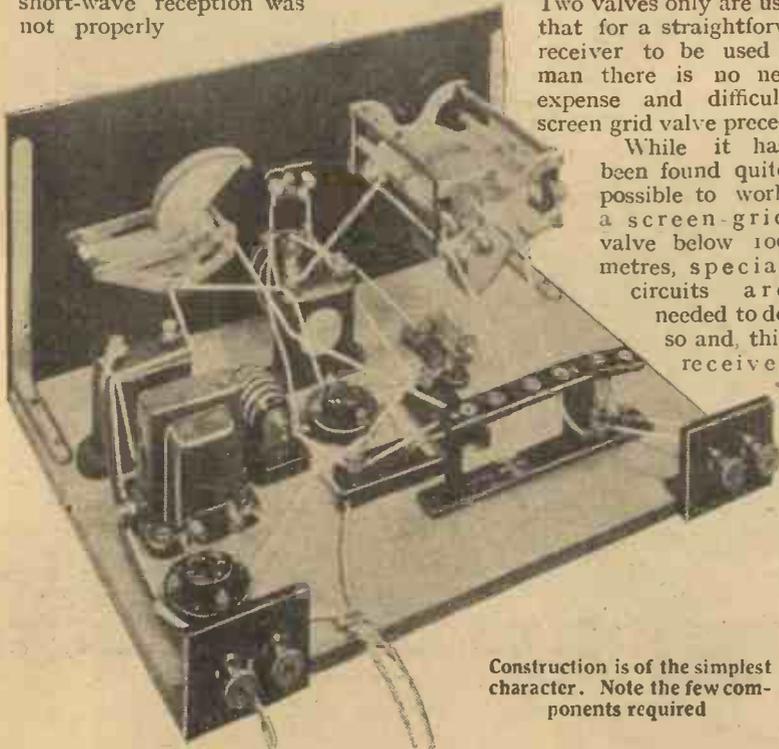While it has been found quite possible to work a screen-grid valve below 100 metres, special circuits are needed to do so and, this receiver



Construction is of the simplest character. Note the few components required

being mainly as a standby for occasional short-wave listening, the use of an expensive screen-grid stage would not be justified. For this set you just use your ordinary detector and power valves.

Do not think, however, that any feature has been overlooked which would

appeal to the technical folk well acquainted with short-wave working. On the contrary, the AMATEUR WIRELESS Technical Staff has taken a deal of pains to make this two-valve short-wave set a real success and to ensure that it can be worked by novices and experts alike.

Novel Features

Short-wave connoisseurs will appreciate a novel idea which has been incorporated in the tuning circuit. If you have previously used a short-wave set, you will have noticed that, when searching below 50 metres or so, some condensers give rise to crackling noises in the speaker when the slightest variation in capacity is made. This makes tuning very difficult, of course, and rather unpleasant. Poorly-made condensers exhibit this fault on all short-wave reception, while others do not give trouble until the wavelengths below 50 metres, or thereabouts, are tried; but on

THE COMPONENTS AND THE CIRCUIT

Ebonite panel, 14 in. by 7 in. (Becol, Trelleborg).

.00015-mfd. short-wave condenser (Cylidon).

Special .0002-mfd. reaction condenser (J.B., Lissen, Igranic, Read-Rad, Dubilier, Burton, Polar, Formo).

Two slow-motion dials (Utility type W.181, Ormond, Igranic, Astra).

400-ohm panel-mounting potentiometer (Lissen, Igranic, Rotor, Varley).

On-off filament switch (Read-Rad, Bulgin, Junit, Benjamin, Lotus, Lissen, Igranic).

Two anti-microphonic valve holders (Lotus, Telsen, Benjamin, Igranic, W.B., Clix, Wearite, Burton).

2-mfd. fixed condenser (Lissen, T.C.C., Igranic, Dubilier, Formo).

1-mfd. fixed condenser (Lissen, T.C.C., Dubilier, Igranic, Formo).

High-frequency choke (Burton, Igranic, Lewcos, R.I., Lissen, Wearite, Varley, Telsen).

Two .0001-mfd. fixed condensers

(Lissen, Telsen, Dubilier, T.C.C., Watmel, Formo, Igranic).

3-megohm grid leak (Dubilier, Lissen, Rotor, Igranic).

Grid-leak holder (Lissen, Bulgin, Wearite, Graham-Farish).

Short-wave inductance unit (Eddy-stone type 585).

Low-frequency transformer (Telsen, Aes, Lissen, Igranic, Burton, R.I., Lotus, Varley).

15,000-ohm spaghetti resistance (Bulgin).

Two terminal blocks (Junit, Lissen, Belling-Lee).

Four terminals, marked: A, E, L.S.+, L.S.— (Eelex, Belling-Lee, Clix, Igranic, Burton).

Four wander plugs, marked: H.T.—, H.T.+, G.B.—, G.B.— (Clix, Belling-Lee, Eelex, Burton, Igranic).

Pair panel brackets (Bulgin, Keystone, Read-Rad).

Glazite for wiring.

Rubber-covered flex (Lewcos).

SEARCHER SHORT-WAVE TWO

There is no need to have anything elaborate for short-wave reception, and a glance down any official list of below 100-metre stations shows what a galaxy of transmissions there is now on the ether, and which is at the disposal of any amateur who is enterprising enough to make up a simple set for this special work.

as a guide to show the centres for the tuning and reaction condensers, the filament on-off switch, and the potentiometer.

Do not mount these parts until the panel has been firmly fixed at right angles to the baseboard. Panel brackets are used in order to keep the panel rigidly at right angles, for any loose movement in a short-wave set is apt

25 metres and below it is safe to say that practically every condenser gives rise to these noises—not an inherent fault in the component itself, but one due to the fact that at these very high frequencies the slightest variation of capacity caused by the movement of a pigtail connection, or by a resistance change caused by the movements of the condenser, gives rise to crackling noises.

point, and the use of a dropping resistance in series with the detector anode; this is a sure guard against threshold howl.

You need have no worry on the score of expense, for the parts needed are few. A full list of components is given in an accompanying table.

You are advised to get the full-size blueprint which is available for this receiver, price, 1s., post free, from the Blueprint Department, AMATEUR WIRELESS, 58-61 Fetter Lane, London, E.C.4, for accurate layout is of paramount importance in a "wavelets" set. The blueprint, which is full size, makes it easy for any constructor to follow the layout exactly.

You will see from the photographs that the layout of the set is well spaced. Care should be taken not to crowd the parts together, and the arrangement of the parts on the baseboard should be followed with meticulous care.

to make tuning difficult. For this reason the wiring should be carefully done and all the joints made so that a good electrical and mechanical connection is provided.

Rigid wire is used for making connections, except to those points to which the battery flexes are taken. The 15,000-ohm dropping resistance in the detector anode circuit is one of the new flexible resistances, and this is connected directly between high-tension positive terminal and one of the terminals on the 2-microfarad by-pass condenser. This condenser, by the way, should not be mounted until connections have been made to the low-frequency terminals, for otherwise a little difficulty will be experienced in soldering to the transformer terminal tags.

Make sure that you connect the coil supporting strip exactly as shown by the layout diagram. A special method of connections has been employed to work in conjunction with the novel condenser tuning arrangement.

In the set shown by the photographs the point-to-point wiring system has been adopted and soldered connections have been made. The point-to-point system is very

Special Tuning Arrangements

A special dual condenser is used in this short-wave set and a novel method of connection prevents this from giving rise to "atmospherics." You will see that the two sets of fixed vanes (the condenser has dual sections) are taken to the tuning points of the circuit and that the variation of capacity is produced solely by the movement of the two sections of the moving vanes.


A little thought will thus show that variation of capacity is produced not by any moving part in connection with the outside circuit, and there is, therefore, nothing to cause noisy working. Even when this set is worked down on 15 metres the condenser control is quite silent.

Other little features which will appeal to knowledgeable short-wave enthusiasts are the inclusion of a grid-leak potentiometer, which gives a nice control of oscillation and keeps the detector at its proper working

Easy Construction


Constructional work has been simplified by the use of flex connections for the high-tension, low-tension, and grid-bias batteries. Terminal strips are used only for the aerial and earth and the output to the speaker.

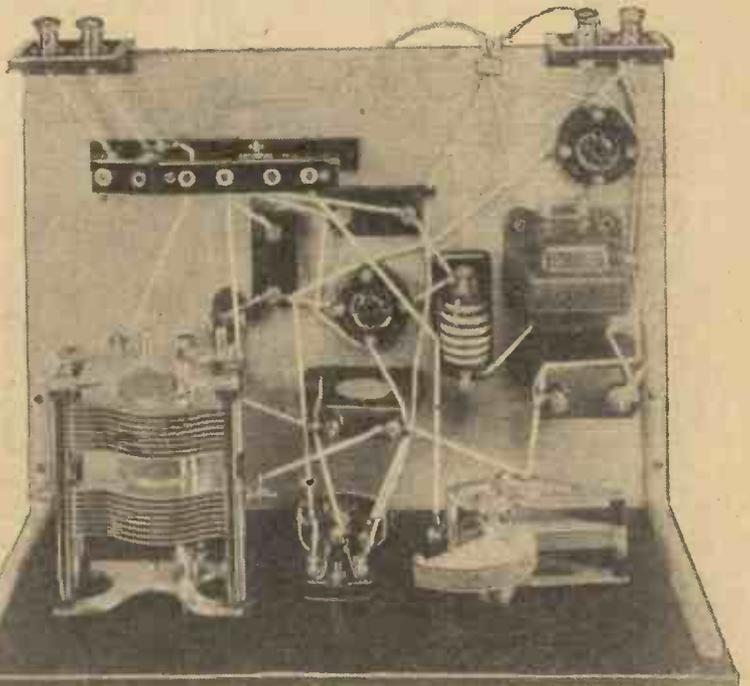Panel drilling is quite a simple job, and the blueprint should be used



This plan view shows the easy wiring; compare it with the layout diagram on the next page

OF THE "SEARCHER SHORT-WAVE TWO"

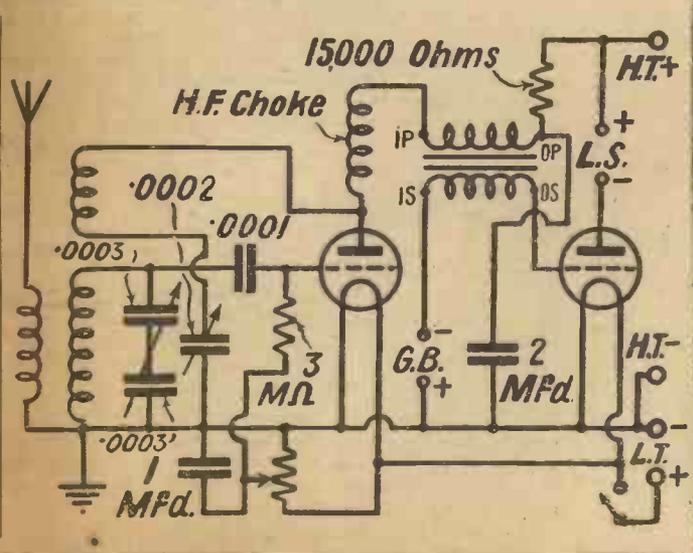

convenient in this particular receiver, for it makes for short, direct connections and a minimum of internal capacity in the set. The appearance may not be so pleasing to the eye as that obtained by the square-corner system, but then we are out for the maximum of efficiency and "prettiness" must be a secondary consideration.

It should be unnecessary to emphasise the importance of making a test of the wiring when all the leads have been connected. There is nothing very difficult about this, the scheme of connections being so simple.



Suitable Valves

So far as valves are concerned, you will, in practically every case, find that standard detector and power valves are quite suitable, but if you are buying special valves for the set, then you will find the following recommendations helpful. The detector valve may be chosen from the following :

Two volts : Mullard PM2DX, Cossor 210HF, Dario Univ., Marconi HL210,

"THE SEARCHER SHORT-WAVE TWO"

(Continued from preceding page)

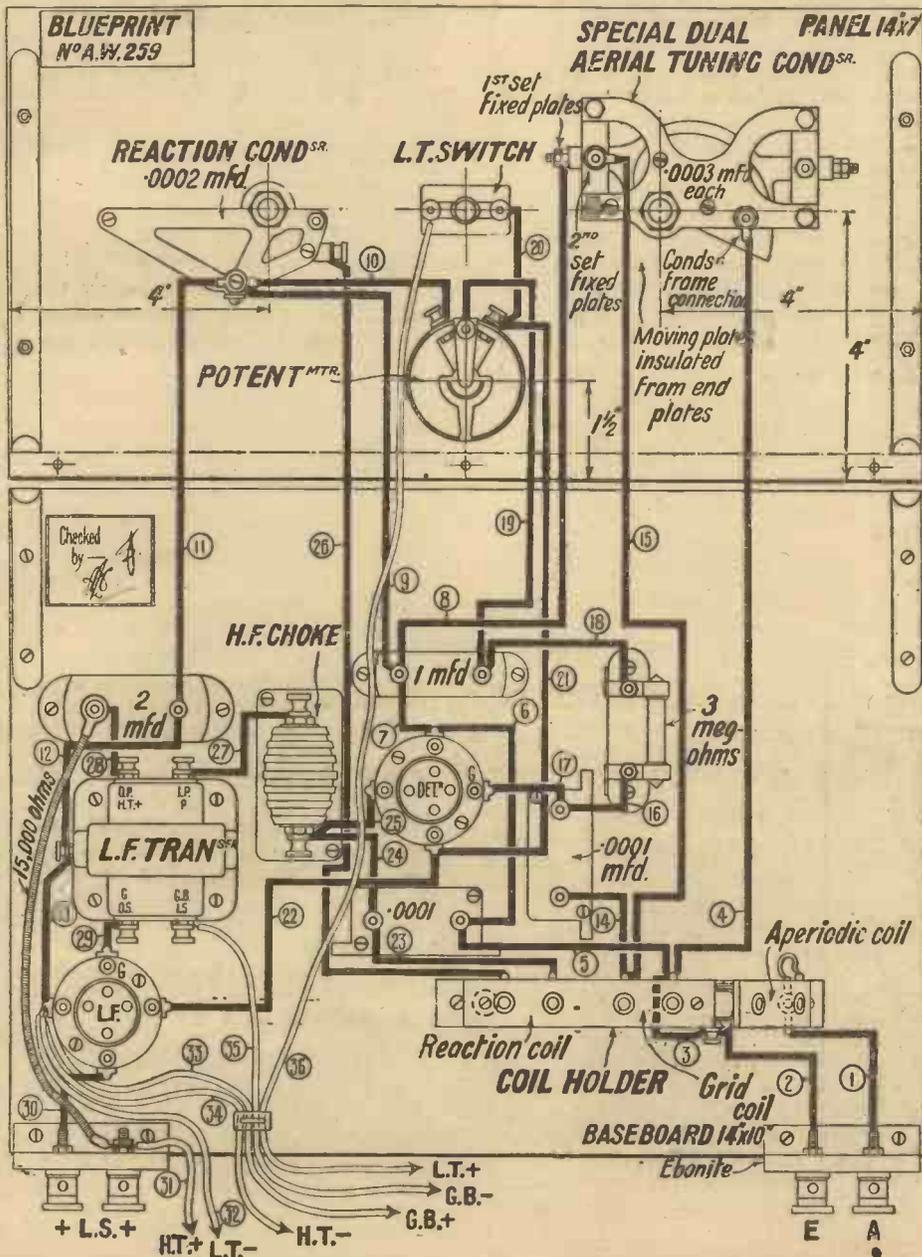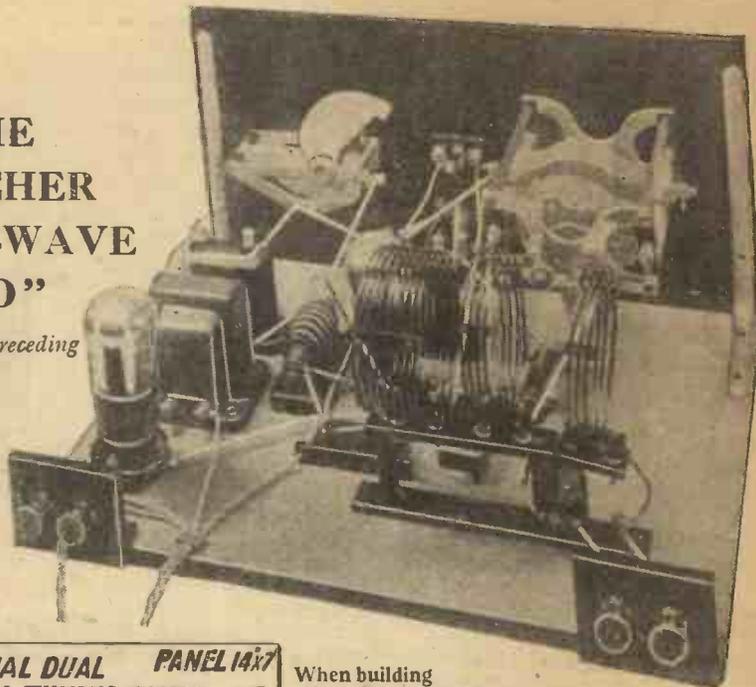

The layout and wiring diagram. A full-size blueprint is available, price 1/-

When building a short-wave set the tried layout should be followed closely if the best results are to be obtained

Osram HL210, Six-Sixty 210HF, Mazda HL210, Lissen HL210. Four volts : Mullard PM3, Six-Sixty 4075HF, Osram HL410, Marconi HL410, Dario Univ., Cossor 410HF. Six volts : Mullard PM5X, Cossor 610HF, Marconi HL610, Osram HL610, Mazda HL607.

The power valve need not be of the super type, for it will not have to deal with large grid swings, and the following power valves will be quite suitable and will not consume an excessive amount of high tension :

Two volts : Mullard PM2, Cossor 220P, Dario SP, Marconi P2, Osram P2, Six-Sixty 220P, Mazda P220A, Lissen P220. Four volts : Mullard PM4, Cossor 410P, Dario SP, Marconi P410, Osram P410, Six-Sixty 410P. Six volts : Cossor 610P, Marconi P610, Osram P610, Six-Sixty 610P, Mullard PM6.

Proper use of the coils plays an important part in getting good results. With the standard Eddystone coils used it will be found that the lowest range, from 14 to approximately 31 metres, is covered by a 3-turn coil in the aerial socket, a similar coil in the grid socket, and a 2-turn coil in the reaction socket. The next range, from 25 to approximately 52 metres, is covered by a 3- or 6-turn coil in the aerial socket, a 6-turn coil in the grid socket, and a 3-turn coil in the reaction socket. A range of 46 to about 98 metres is covered by a 6-turn coil in the aerial socket, a 15-turn grid coil, and a 5-turn reaction coil.

There should be no difficulty in obtaining reaction. Various settings of the potentiometer and of the aerial coil with respect to the adjustment of the grid coil should be tried. If there is any tendency to motorboat when the reaction condenser is adjusted, then a new setting of the potentiometer arm should be tried.

The high-tension voltage may also be adjusted, but, generally speaking, it will be found that good results will be obtained with 100 or 120 volts, and 7 or 9 volts should be applied to the grid-bias plugs.

MEASURE THE PRICE OF YOUR BATTERY BY THE MONTHS OF ITS LIFE — THE QUALITY OF ITS CURRENT AND THE ABUNDANCE OF ITS POWER



**60
VOLT
7'11**

WHEN you get a high tension battery for radio that lasts so long that you forget the date you bought it—when that battery delivers pure clean current that will keep every note of music, every word of song so distinct and loud—when the power of that battery is so abundant that your loudspeaker was never so loud before—and when the output from that battery is obtained at a cost acknowledged to be the lowest cost known per unit of output, can you expect to get more from any battery?

In a Lissen Battery you get the advantage of all this abundant power, all this clarity of tone in your loudspeaker, and all this economy of current cost. No battery will do more for you than a Lissen Battery, and it will take a long search to find one that will do anything like so much.

100 v. 12/11

Also made in all sizes, all capacities, all voltages to suit your needs.

You can secure all the advantages of a Lissen Battery by asking by name for a "Lissen New Process Battery" and showing you are firm about it by the way you say "Lissen." Obtainable at 10,000 radio dealers.



IT PAYS TO BUY LISSEN—THE POWER THAT LASTS

THE REASON FOR THE SUPERIORITY OF THE LISSEN BATTERY

Big cells—a process and chemical combination known only to Lissen, which packs those cells with the largest oxygen content found in any battery—giving a stamina and a resistance to volt drop over such prolonged periods of time that the battery seems everlasting, and yielding only pure power all the time.

LISSEN LIMITED, Worple Road, Isleworth, Middlesex

You will Help Yourself and Help Us by Mentioning "A.W." to Advertisers

IN MY WIRELESS DEN



WEEKLY TIPS—
CONSTRUCTIONAL AND THEORETICAL

By W. JAMES.

A Coil Puzzle

THE point often crops up as to whether it is better to connect the long and medium wavelength coils in parallel or to short-circuit the long-wave part when tuning over the medium waves.

Actually, sometimes one method is better than the other, and it seems to depend upon the position of the coils and their shape and size. A long-wave coil when short-circuited may have a natural wavelength within the medium wavelength band. And if the long- and medium-wave coils are fairly near together the effect may be to reduce materially the strength of the signals.

When the coils are not too close together and are astatically wound, the chances of one circuit affecting the other are remote. At the same time, curious effects are produced by slight couplings. When experimenting, one should try joining the coils first in series and then in parallel, for a rule cannot be given. Some good dual-range coils have been made with the windings arranged both in series and in parallel, and, let me add, some bad ones as well.

All-metal Sets

The practice of using a metal base or of covering the baseboard with copper foil for shielding purposes seems to be on the increase. Valve holders and other parts are screwed down in the usual way, and the point that these parts were probably designed for a wooden baseboard is overlooked.

The result is that live contacts often lie very near the earthed metal, and on occasions a contact is actually made. Valve holders, for instance, sometimes have terminal screws which only just clear. In tightening down wires the screws may work down a little, when contacts will be formed.

It is a good plan when in doubt to place a sheet of insulating material below the valve holders, so as to avoid the chance of this fault occurring. Care is also needed with some other parts.

Coils, for example, may have contacts beneath them with only just enough clearance. Screw heads should therefore be examined, and if they seem too near the lower surface of the base, the precaution of using a sheet of insulating material should be taken.

Those Cheap Transformers

Cheap transformers, having but few


turns of wire in their primary coils, often will pass a surprisingly large current before saturation of the core commences.

This means that a fairly low-impedance valve may be used with them. The quality of the reproduction may, therefore, be fair, but you should not forget that when poor quality iron stampings are used there may be more or less bad distortion.

Whether this is noticed depends upon the rest of the set and the loud-speaker. There may be so much distortion elsewhere in the set that transformer distortion is not noticeable. With small sets the last valve may be so overloaded that other distortions are of no great account.

From D.C. to A.C.

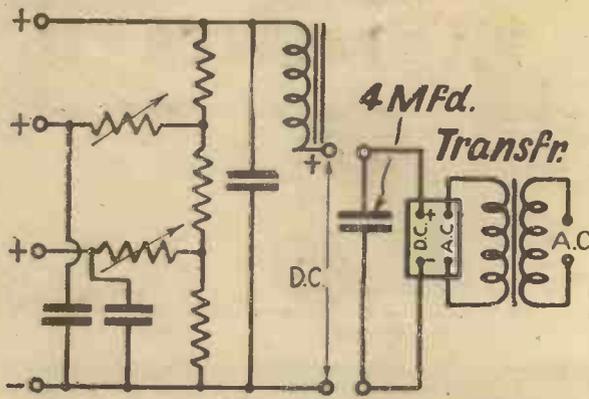There are one or two difficulties in the way of changing over a direct-current mains unit to alternating current.



This is the circuit of a typical mains eliminator

DO YOU KNOW—

that in a mains-driven set there are two advantages in having a choke or transformer output for the speaker? One is that the speaker is insulated from the mains current and the other is that the smoothing and elimination of hum are materially improved.

that if the reaction control of your set is tricky, you might try fitting a differential condenser in place of the plain two-vane type? Differential reaction control does not upset tuning to the same extent as plain control.

that if your mains eliminator hums and you do not want to interfere with the connections then you might try putting a 2-microfarad condenser across the mains input wires? The condenser should be capable of standing up to the full mains voltage.

It is not safe simply to connect a transformer and rectifier unit to the D.C. unit, for the reason that the D.C. unit may have unsuitable parts.

Thus, in some types a potentiometer is fitted, as indicated in the accompanying diagram. This will pass a fair current—perhaps too much for the rectifier. Then, again, the choke may have a very high resistance, this not being of great importance when the D.C. voltage is relatively high.

When the output from the A.C. part is limited, however, the choke may too seriously restrict the supply to the set. A by-pass condenser should be provided across the output from the rectifier and the potentiometer ought to be removed if it passes more than a few milliamperes. As a rule, the D.C. unit should be re-built for the best results and proper anode resistance and condenser filters be added.

Your Aerial


I have often wondered whether the size of the wire used as the aerial is of great importance, and now I am inclined to believe that this is perhaps the least important feature of the aerial circuit.

Most of the resistance seems to be localised in the earth. Many people use earth tubes and neglect them, so that the actual earth-circuit resistance is pretty high. A copper-wire aerial of not smaller than, say, No. 24 gauge seems satisfactory with average tuning coils and earths.

There seems no electrical advantage in using stranded wire or very thick wires unless, of course, a highly efficient aerial and earth circuit is being constructed. The mistake usually made is in the earth circuit. A wire wrapped round a pipe seems to suit many people; but, really, is not good. A clip which grips a pipe going to earth is much better.

The outstanding feature of the day's music from Midland Regional on December 10 is a programme of works by British composers by the studio orchestra.

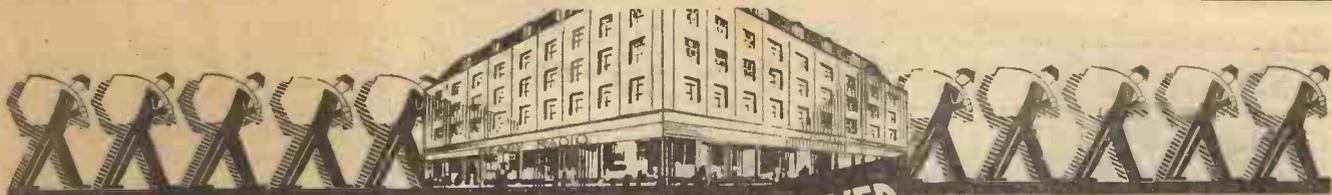"The Kingdom," by Sir Edward Elgar, will be given at the first concert for the season of the Cardiff Musical Society in the Park Hall, Cardiff, on December 7. The coming season is the forty-third of the society's existence, and for the third year the National Orchestra of Wales will take part in the concerts.



TROUBLE-FREE SET BUILDING **USE READY RADIO APPROVED NON-SOLDERING KITS ONLY.** **USE "JIFFILINKS" FOR WIRING-UP**

"CHALLENGE THREE"

- KIT A** less valves and cabinet £6:1:9
or 12 equal monthly payments of 11/3
- KIT B** with valves less cabinet £8:0:9
or 12 equal monthly payments of 14/9
- KIT C** with valves and cabinet £9:5:9
or 12 equal monthly payments of 17/-

"CHALLENGE FOUR"

- KIT A** less valves and cabinet £8:6:9
or 12 equal monthly payments of 15/3
- KIT B** with valves less cabinet £11:5:9
or 12 equal monthly payments of 20/9
- KIT C** with valves and cabinet £12:18:3
or 12 equal monthly payments of 23/9

N.K. FARRAND INDUCTOR SPEAKER

Unit and Chassis complete, ready mounted. The finest permanent magnet Speaker on the market—quality of reproduction equal to moving coil. Price £3.10.0 or 12 equal monthly payments of 6/5

THE GAMBRELL "NOVOTONE"

TYPE J. Cash £3.3.0 or 11/-
6 equal monthly payments of 11/-

THE GAMBRELL "RADIO-NOVOGRAM"

Supplied in OAK cabinet for DIRECT current. Cash 62 Gns. or 12 equal monthly payments of £5.19.3
FOR ALTERNATING CURRENT 70 Gns. or 12 equal monthly payments of £6.14.9

TO OVERSEAS CUSTOMERS
All your goods are very carefully packed for export and insured, all charges forward.

You can buy any RECEIVER, EQUIPMENT or SETS OF PARTS from READY RADIO by EASY PAYMENTS

READ THIS—

9, Ullswater St., Liverpool, 8/11/30
To Ready Radio, Ltd.
Sirs,—Just a few lines to thank you for your prompt attention and splendid packing of goods which I received last Saturday. I wrote one firm asking for these goods and only received a reply after waiting three weeks, so goodness knows when the components would have been dispatched. But now, thanks to your prompt attention, I have got my set working (THE "MAGIC" FOUR), and it is a credit for the good components you sell. Later, I shall be wanting some long-range coils, so you may depend on my order coming to Ready Radio.
(Signed) ERNEST CRUMBE.

SEND FOR A COPY OF OUR 1931 ILLUSTRATED CATALOGUE, PRICE 1/., POST FREE. A COMPLETE ENCYCLOPEDIA OF MODERN SETS, SPEAKERS, COMPONENTS AND ACCESSORIES.

Ready Radio
159, BOROUGH HIGH STREET,
LONDON BRIDGE, S.E.1.
Telephone: Hop 5555 (Private Exchange) Telegrams: READIRAD, SEDIST.

"EKCO" ALL-ELECTRIC 3-VALVE RECEIVER

(Model 313 for A.C. or D.C. Mains). Entirely self-contained—No aerial or battery required. S.G., DETECTOR and POWER. A.C. or D.C. Cash £22:10:0 or 12 equal monthly payments of £2.1.0

"EKCO" ALL-ELECTRIC 2-VALVE RECEIVER

(Model 312 for A.C. or D.C. Mains). DETECTOR and PENTODE. A.C. or D.C. Cash £14:10:0 or 12 equal monthly payments of £1.6.6

COSSOR "EMPIRE MELODY MAKER"

Complete Kit including valves and cabinet. Cash £6:17:6 or 12 equal monthly payments of 12/6

MULLARD 1931 "ORGOLA" 3-VALVE KIT

S.G., DETECTOR & POWER. Complete Kit including valves and cabinet. Cash £8:0:0 or 12 equal monthly payments of 14/9

MULLARD 1931 "ORGOLA" 4-VALVE KIT

2 S.G., DETECTOR and PENTODE. Complete Kit including Valves and Cabinet. Cash £13:12:6 or 12 equal monthly payments of £1.4.9


1931 OSRAM "MUSIC MAGNET FOUR"

2 S.G., DETECTOR and POWER. Complete Kit including Valves and Cabinet. Cash £11:15:0 Or 12 equal monthly payments of £1.1.3

TO INLAND CUSTOMERS
Your goods are dispatched post free or carriage paid.

Immediate Dispatch

Cash or Easy Payments

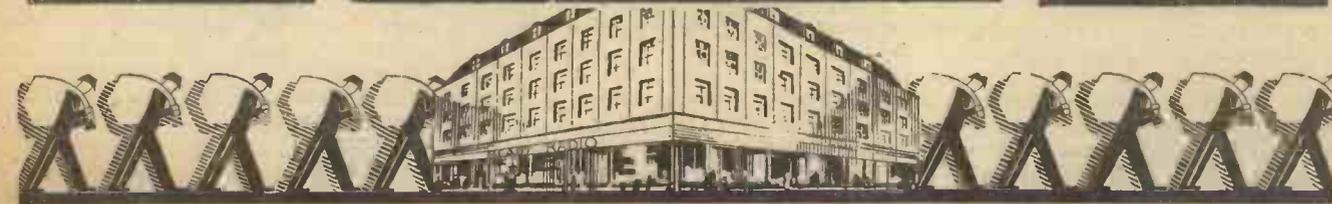

ADVERT, OF READY RADIO (R.R. Ltd.), 159 BOROUGH HIGH STREET, LONDON, S.E.1

Advertisers Appreciate Mention of "A.W." with Your Order

SETS OF DISTINCTION

The VARLEY JUNIOR TWO

Makers : Varley Ltd.

Price : 15 gns.



AMONG the host of two-valve all-electric sets of the season, the Varley Junior Two is outstanding. Its rather high price needs some justification in these hard times. Well, in my opinion, the performance justifies the extra guinea or so. There will always be people, no matter how hard the times, who insist on something a little better than the average.

Like all Varley sets, this two-valver is good to look at. The makers must have a fine aesthetic sense. And a good idea of the housewife's outlook when the mere male goes to buy a set. I have authentic experience of sets turned down by the lady of the house on account of poor cabinet work.

Very Attractive

The picture shows how modern is the conception of the cabinet work of the Varley set. I can add that the burr-walnut finish is extremely attractive. In fact, the fine appearance of the set alone justifies the price asked.

The controls are, naturally, simple and few in number. In the centre of the front of the cabinet is a slow-motion tuning dial, with an operating knob mounted below. To the left of the tuner is a handy knob for controlling reaction. I am glad to see this knob is plainly engraved "reaction" and that an arrow indicates the direction for turning the knob to increase reaction. Likewise the knob on the right of the tuner is engraved to show that when the knob is moved to the left the medium waves are in tune and when moved to the right the long waves. This is undoubtedly a fine set for family use.

The top half of the back of the cabinet can be removed, by undoing two screws, to get at the valves and mains connections. A look round the interior showed an unsparring use of the very best material. An extremely large tuning coil for the medium waves was noted with interest. As far away from it as possible I noted the long-wave coil. Both look highly efficient, as indeed they are.

In an accessible position is the mains transformer, with three plug sockets marked 200 v., 220 v., and 240 v., to make the set suitable for all A.C. supplies between 200 and 250 volts. The detector valve and the power valve are fitted close together at one side of the cabinet. The rectifying valve for deriving the high-tension from the supply is fitted near the mains transformer.

The terminal strip just below the remov-

able back is unusually free from confusion. The two loud-speaker terminals are at the left and the earth terminal at the extreme right. Near this is the socket for gramophone pick-up, and further to the left are four aerial terminals, providing for every conceivable length of aerial.

The makers have wisely fitted small fuses in each of the two mains connections. And I see a small packet of spare fuse wire is thoughtfully pinned inside near the mains transformer. There is a negligible chance of the fuse being wanted, but the makers are taking no chances.

Now the reader will want to know what sort of results can be expected from this set. Firstly, I would like to emphasise that this is more than a set; it is a very fine gramophone amplifier as well. The facilities for amplifying records are the same in this two as in the Varley and other threes, where the high-frequency amplifier is cut out of circuit for gramo-radio work. I tried the Varley Junior as a gramophone amplifier, using a B.T.H. pick-up and a Ferranti permanent-magnet moving-coil loud-speaker. The quality was wonderful.


On the radio side this fine quality is well maintained, the two Brookman's Park stations coming through with great clarity. The first thing I established was the selectivity, a property that is just as important in a two-valver as in a larger set. At worst, the set must be able to separate the two Regional programmes, so that each can be clearly heard without an obligato from the other. At best, the set will do this without sacrificing volume. And that is where the very fine tuning coils of the Varley set distinguish themselves. The following readings speak for themselves:—

The National London station was tuned in at maximum strength at 31 degrees on the dial. It was entirely inaudible at 33 and 27, indicating a spread of only 6 degrees. The Regional London station was at its maximum at 56 degrees and had gone at 65 and 45, a spread of 20 degrees. For this test I was using the No. 1 aerial terminal, which gives the greatest volume and the least selectivity.

As the aerial was a full 70 feet long, I consider the set behaved extremely well. And by changing over to No. 2 aerial terminal the tuning was made razor sharp, without much loss of volume. The tests show that this little set is inherently selective and that local regional stations can be separated without loss of signal strength.

A Good Trier

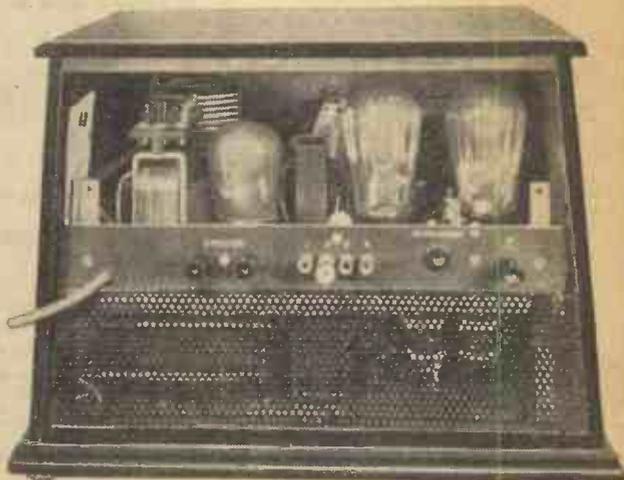The Varley Junior is also a good trier; in addition to the Midland Regional at 93 on the dial, a good loud-speaker signal, I located fourteen strong carrier waves of



The internal arrangements of the Varley Junior Two are particularly neat: note the accessibility of the valves and the efficient disposition of the mains apparatus

foreign stations. Rome at 81 was almost as strong as the Midland. Toulouse, Cologne and Nürnberg were also quite strong.

On the long waves the set works well. Daventry at 75 was very strong. Huizen at 95 could just be called a loud-speaker signal, while Eiffel Tower at 62 was easily heard at good strength and quite clear of Daventry.

So although intended as a local set, the Varley Junior can, in the hands of an operator who understands the funny ways of reaction, bring in not a few foreigners.

This set is made for D.C. and A.C. mains. Two separate models are listed. My notes refer to the A.C. set. The D.C. model is a guinea more.

SET TESTER.

A light orchestral programme will be given by the National Orchestra of Wales from the Cardiff studio on December 8.

GREATEST RADIO SENSATION

NEW 3-VALVE SET OBTAINS OVER 50 STATIONS ON LOUD SPEAKER WITH DAVENTRY 5GB WORKING

This is the new Northampton Plating Co. Super Selective 3-Valve Loud Speaker set, which is now offered to the public. After months of careful research a circuit has been designed superior in selectivity to a screen-grid set, and yet remarkably simple. It can be used, not only for cutting out the local station, but for other disturbances such as Morse. It is the simplest, cheapest, and most selective in the world. No soldering required or coil changing. Experts have declared it absolutely unique. Over fifty stations have been obtained on loud speaker with aerial 20 feet high using cheap valves, including Cardiff, Paris, Madrid, Manchester, Stuttgart, Toulouse, Hamburg, Glasgow, Frankfurt, Rome, Langenberg, Berlin, Brussels, Hilversum, Kalundborg, Konigswusterhausen, Radio Paris. These were obtained 3 miles from Daventry while 5GB was working. Thousands of novices with no knowledge of wireless have built the old Northampton Plating Co. Super 2 and 3 in all parts of the world, and have been astounded by the results even with cheap components, but the new Super Selective 3 makes other sets old fashioned, and marks the greatest improvement in valve sets for years. Orders have poured in from all parts of the world, including America, Turkey, Gold Coast, and Nigeria. In order to give everyone the opportunity of testing out the new circuit, two 6d. Blueprints, one for new Super Selective 2 and one for Super Selective 3 Valve, will be supplied for 3d. each.

NEW SUPER 4-VALVE PORTABLE SEPARATES TWO BROOKMANS PARK STATIONS UNDER THE AERIALS

This is the latest model circuit by the Northampton Plating Co. offered to the public for the first time. It has been specially designed to satisfy the requirements of the new regional stations. Owing to its wonderful selectivity, it requires no wavetrap and obtains under favourable conditions a large number of Continental stations at loud-speaker strength, including Toulouse, Hilversum, Eiffel Tower, Konigswusterhausen, and Radio Paris. At less than half the price of a high-class portable set, it is acknowledged under severe technical tests to be far superior. In order to show what marvellous results can be obtained the set was placed between two aerials at the entrance to Brookmans Park, and the two programmes were easily separated. The set was also taken on a 1,000-mile motor tour over England and Wales. On the south coast and east coast many stations were easily obtained on loud-speaker at good strength. Even in Wales, where reception is difficult, excellent results were also obtained. In order that everyone may be able to construct this unique portable set, a full-size shilling Blueprint, with details and instructions, can be obtained from Northampton Plating Co. for 6d. Letters must be fully stamped: NAME AND ADDRESS IN BLOCK LETTERS.

TRADE SERVICE AGENTS WANTED.

READ THE LATEST REPORTS BY THE LEADING RADIO EXPERTS OF THE DAY:-

I refer to the receiver marketed by the Northampton Plating Co. as a kit set at a price that is more than reasonable. I had a pleasant surprise when I first operated it. I found there were 12 or 13 stations easily brought in at loud-speaker strength on the medium waves, in addition to 5GB. The set has remarkable qualities of selectivity and sensitivity, two characteristics rarely coupled in any one receiver. It must be set down as a definite advance.

("NOTTINGHAM JOURNAL," December 21, 1929.)

Those who are too far from a station to use a crystal and are deterred from wireless by the present high cost of valves, will find it best to make a set from the Northampton Co.'s blueprints for two or three valves, price 3d. each. If they cannot afford a Mullard, the same company supply excellent valves at 4s. 11d., which give admirable reception, though so cheap. A thoroughly good two-valve set ought not to cost more than £2 10s., including everything, and a three-valve about 11s. more.

("REYNOLDS'S NEWS," January 12, 1930.)

READ THESE TESTIMONIALS.

I have had your Super 3 since Sept., 1929, and have had wonderful results, about 50 stations at full loud-speaker strength, and can get most of these any night of the week, chief among them being: Paris, Eiffel Tower, Budapest, Prague, Belgrade, Stockholm, Madrid, Toulouse, Stuttgart, Barcelona, Turin, Maravatra-Ostrava, Rome, Algiers, Langenberg, Oslo, Lahti, and Kansas. Wishing you every success.—W. T. Ensworth, Hants, 17/1/30.

I must write and tell you I am more than pleased with your three-valve set I have just made. It is the most wonderful bargain I have ever known in wireless, and it is all that you claim of it. I wish to recommend it to my friend, who is a keen wireless enthusiast.—W. P. T. Derby, 16/1/30.

I have now built up your Super Three Valve set, and, independent of price, I have never heard or seen a set to beat it. We are still getting fresh stations, and up to the present have logged 20 at full loud-speaker strength. As I am writing we are hearing an Aria from Rome. My last set cost me about £25. Your Super Three has cost me less than £5, including accumulators.—W. A. P., Norwich, 5/2/30

Referring to the 3-valve set recently supplied, I have pleasure in informing you how satisfied I am with it. I recently put an up expensive 4-valve, and had such bad results. I may say I have had many circuits in use up to 5 valves with very good results—that means quality of reception, volume, and distance. I purchased your Super 3 really for local use. As you will see, I am on top of the Brookmans Park Transmitter. The results I am getting are equal to my best with 4 and 5 valves. I can still hear my Continentals on the loud-speaker, and with perfect quality. Wishing you every success.—Yours faithfully, V. M., Chesnut, Herts.

I feel I must write and congratulate you on a wonderful circuit. I have now had your "Northampton 3" only two nights, but in those two nights it has fully justified itself. I have the poorest of poor indoor aerials, and I have in 10 minutes logged 10 stations on the Loud-speaker. I have had to insert a volume control because of the power of the local station (Bournemouth, 70 miles away) and 5GB. I have just received Oslo, Paris (2), Hamburg, Berlin, Budapest, and many others. Your "3" gives 10 per cent. better results than you specify. Wishing your sets the best of luck in the future.—Yours very satisfied, C. D. N.

I have examined the above testimonials and am satisfied that these are genuine communications.—Advertisement Manager, "News-Chronicle."


THE NORTHAMPTON PLATING CO. SUPER A.C. ELIMINATOR

SPECIAL OFFER



Seven days approval to test. This A.C. eliminator, value £4, will be sent to any address on payment of

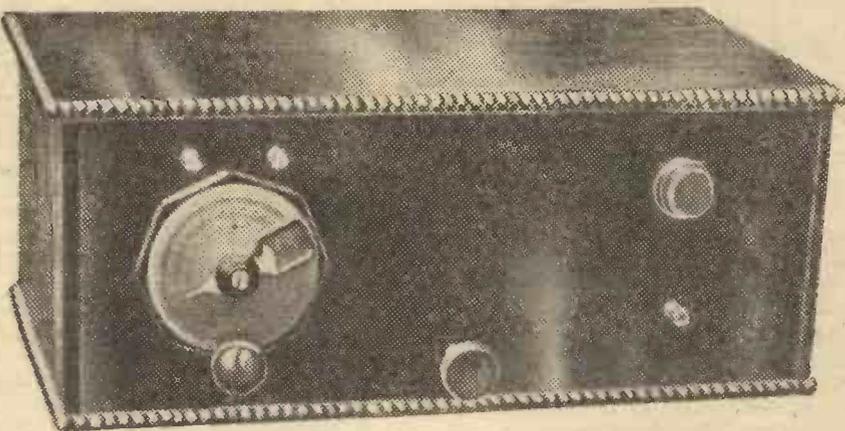59s. cash or C.O.D., with the guarantee that if it is not superior to any other eliminator on the market and not giving complete satisfaction the money will be instantly refunded if returned in good condition and undamaged. It is guaranteed to be most silent in operation, giving over 20 milliamperes, and suitable for all 2-, 3-, and 4-valve sets. Test it for yourself. Trade inquiries invited.



SPECIAL WIRELESS AND CYCLE BARGAINS

Usual Price.	Sale Price	Usual Price.	Sale Price.	Usual Price.	Sale Price.	Usual Price.	Sale Price.
10/- Latest Type Cabinet, 12 by 8	4/11	17/6 New Cossor Type Long-wave Coils, pair	9/6	12/6 Mullard Type Cabinet, 18 by 7	6/11	12/6 100-volt H.T. Battery	8/11
5/- Ebonite for same, 12 by 8	3/-	7/6 Volume Control	3/11	7/6 Aluminium Panel, 18 by 7	3/11	5/6 2-volt Accumulator	3/6
5/11 Transformer	3/6	7/6 H.F. Choke	3/11	17/6 Dual Coil for M.M.3	12/6	2/- Accumulator Carr.	11d.
4/6 .0005 Variable Condenser	2/11	2/6 Daventry 5GB Coil	1/3	Triotron Dull Emitter Valve	4/11	4/6 Neutralising Condenser	2/11
2/- .002 Condenser	1/3	10/6 6-volt Amplion Valve	3/11	5/- Cycle Tube	2/6	4/- Reaction Condenser	2/6
1/6 .003	10d.	12/6 Cone Unit	6/11	2/6 Cycle Tube	1/3	5/- Diff. Reaction	2/11
1/- Grid Leak, 2 meg.	10d.	12/6 Cone Speaker Cabinets	7/11	6d. Panel Transfer	3d.	2/- Loud-speaker Cord	11d.
1/- Anti-Mic. Valve Holder	9d.	2/- 12 in. Cone Speaker Frets	11d.	6/6 Double-reading Voltmeter	3/11	2/- 'Phone Cord	11d.
2/3 Rheostat	9d.	3/- 15 in. Cone Speaker Frets	1/11	Triotron Super Power Valve	6/6	6/- S.L.F. Condenser	3/11
2/- Indoor Aerial	9d.	7/6 Old Cossor Type Coils	3/11	15/- Titan Coil	9/11	21/- D.C. Eliminator, 15 milliamps	17/6
5/- Earth Tube	1/6	15/- Old Cossor Type Cabinets, 21 by 7	7/11	9/- 60-volt H.T. Battery	4/41	£4 A.C. 20 milliamps	59/-
10/- Guaranteed Phones	4/11	Ebonite for same	3/11			17/6 Electric Iron. Weight, 5 lb.	7/11
3/6 S.M. Dial	1/11					30/- Cone Speaker	9/11
						'Phones Repaired	2/6

Parts supplied for all sets at Reduced Prices. Send now to avoid disappointment. Cash with order or C.O.D. Special terms to those making sets. All goods guaranteed and exchanged if not satisfactory. Inquire for anything you want. Trade supplied. Send for our wonderful Bargain Price List, A.W.

Trade Service Agents Wanted.

Owing to the enormous number of inquiries and orders, write clearly Name and Address in Block letters to the firm that made Radio popular. Letters must be fully stamped.

NORTHAMPTON PLATING CO. (Radio & Cycle Manufacturers), NORTHAMPTON

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

RESISTANCE-CAPACITY coupling was one of the earliest forms of intervalve coupling used in valve amplifiers. It is still one of the most popular forms of coupling, although it has passed through many phases. The values of anode resistance have varied from a few ohms to several megohms, and the other constants in the circuit have varied accordingly. In fact, there are in use to-day resistance-coupled amplifiers having values as widely different as those just stated and probably all working with a certain degree of satisfaction.

This has created the impression that resistance-capacity coupling is not critical as regards the choice of values. Actually nothing is farther from the truth. This form of amplifier requires as careful design as any other form. Admittedly it is somewhat easier to vary the values of the components, for the average user cannot vary the inductance of the transformer at will, nor can he alter the characteristics to suit his requirements, whereas a change in the value of his resistance or coupling condenser will often make a very material difference

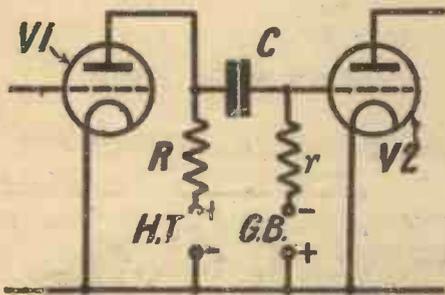


Fig. 1. Diagram of resistance-coupling system

to his quality. The purpose of this article is to suggest that in many cases the values used for this form of coupling are quite incorrect in the light of modern experience, and that from this point of view the system, as put into practice in the majority of cases, is out of date.

A QUESTION OF DESIGN

The design of a resistance-coupled amplifier can be divided into two distinct stages. In the first place, one may, by paying attention to the general details, produce an amplifier which is capable of giving good quality under normal conditions. The second stage results from an analysis of the working of such an amplifier under abnormal conditions, such as transient phenomena produced by cymbals or pizzicato strings and such-like effects. The benefits obtained here from the use of correctly-proportioned parts are only discernible on a good loud-speaker and to a good musical ear. I propose in the present article to discuss the first stage in the design and to review quite briefly the modern ideas on the subject. In a later and second article I propose to discuss those factors which affect the more critical listener, dealing with the phase shift or time lag which is experienced with this form of coupling.

There are three main components in a

IS RESISTANCE COUPLING OUT OF DATE?

By J. H. REYNER, B.Sc., A.M.I.E.E.

resistance-capacity coupled system, namely, the anode resistance, the grid leak, and the coupling condenser. The system is shown in skeleton form in Fig. 1, and its action is as follows. If varying voltage is applied to the grid of the first valve V_1 , similar but magnified voltages are produced across the anode resistance R due to the varying anode current of the valve. This voltage is applied across the grid and filament of the next valve V_2 , through a coupling condenser C , which serves to prevent the high-tension voltage from reaching the grid of the next valve. The grid-leak resistance r is necessary in order to see that the grid of the second valve is working with its correct bias point, the bottom end of the grid leak being connected to the grid-bias battery as shown.

THE ANODE RESISTANCE

The value of the anode resistance is determined by the valve with which it is to be used. If the resistance is small, most of the voltage developed is absorbed by the valve itself. As the external resistance is increased, so a larger proportion of the voltage is developed external to the valve, but beyond a certain point the increase is only relatively small. The amplification obtained from the valve in terms of the anode resistance is shown in Fig. 2.

On the other hand, if we start with a limited high-tension voltage, as is usually the case, then the larger we make the anode resistance, the less the voltage actually applied to the valve. Most of the voltage is wasted on the anode resistance, and only a small fraction is left for the valve. If we make the anode resistance three times that of the valve, we shall obtain one-quarter of the total voltage on the valve itself. Using a 120-volt battery, this means 30 volts only on the valve, which is quite small enough, and a lower value than this is not desirable.

In most cases the valve which is being

nature is only satisfactory where one is receiving relatively weak signals, and the modern tendency is to use an H.F. valve for a detector, even when R.C. coupling is being used.

Let us now consider the grid leak. Since the grid leak is virtually in parallel with the anode resistance, it must not be made too small or it will reduce the effective anode

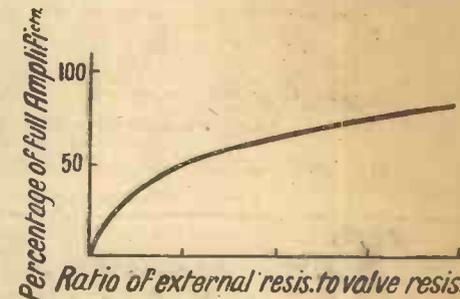


Fig. 2. Curve showing amplification obtained from a valve in terms of anode resistance

resistance and so cause a loss in signal strength. If the grid leak is made five or more times as great as the anode resistance, however, no trouble will be experienced on this account.

The grid leak must not be made too large, however, or there is a danger of what is known as "grid choking."

The value of the grid leak is actually wrapped up with that of the coupling condenser. It is essential that the coupling condenser shall act practically as a short circuit to all the speech currents, while still, of course, acting as a barrier to the high-tension steady voltage. The table given herewith shows the size of coupling condenser necessary to preserve the amplification at frequencies as low as 50 cycles. This value of coupling condenser will be seen to vary with the grid leak, becoming larger as the value of the grid leak is reduced.

At first sight it might seem economical, therefore, to use the largest value of grid leak permissible and use a smaller value of coupling condenser. I shall show in the concluding article, however, that this value of coupling condenser is the minimum which can be used, and that for the best results a distinctly larger value should be employed. This being the case, it pays to use a smaller value of grid leak.

Table showing relative values of coupling condenser and grid leak

Grid Leak (megohms)	Coupling Condenser (microfarads)
0.25	0.05
0.5	0.02
1.0	0.005
2.0	0.0035

This Six-Sixty Power Unit Gives Automatic Grid Bias

Say Six-Sixty and safeguard your valves from over-running. H.T. up to 200 volts, current up to 40 m/a. Fitted in a moment and takes no more space than existing batteries. Price £6:6:0. A winding for L.T. (5 amps at 4 volts A.C.) enables battery valves to be replaced at any time by

The highly successful Six-Sixty A.C. Valves

with their added power, range and selectivity. Ideal and standard replacement for A.C. mains sets, they can be fitted without trouble to almost any battery set by means of

The Six-Sixty A.C. All-Mains Conversion Equipment

which includes the Power Unit, specially selected Six-Sixty A.C. Valves and Six-Sixty 5/4 pin Valve-holder Adaptors. It modernises your set to true all-mains operation without any alterations to set-wiring. Complete equipment from £8:5:0.

Write for **FREE** Booklet giving full details of the whole Six-Sixty range.

**SAY
SIX-SIXTY**


(B.V.A. RADIO VALVES AND EQUIPMENT)

SIX-SIXTY RADIO CO., LTD., SIX-SIXTY HOUSE, 17/18 RATHBONE PLACE, OXFORD STREET, LONDON, W.1.


Telephone: Museum 6116/7.

To render music faithfully

IS THE AIM AND ACHIEVEMENT OF THE UNDY 8 POLE DYNAMIC SPEAKER

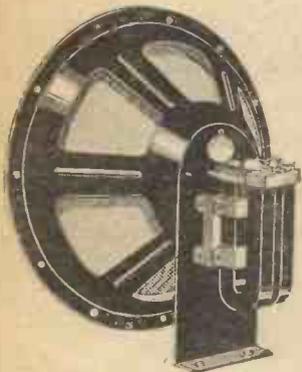


Complete 8-pole Unit with Chassis ready for building into Cabinet or Baffle-board - **50/-**

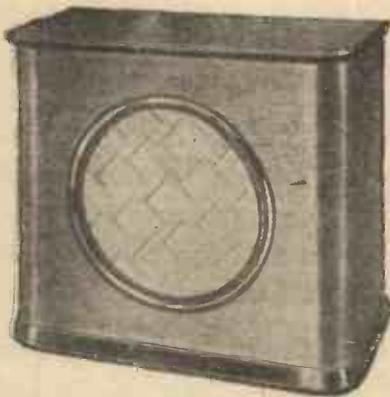

Undy 8-pole Dynamic Loud-speaker in attractive Mahogany Cabinet **70/-**



Undy 8-pole Dynamic Loud-speaker in highly polished Walnut Cabinet de-Luxe - **90/-**

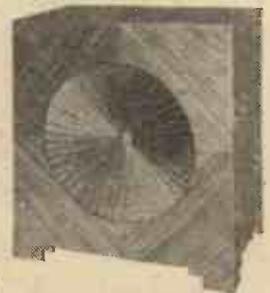

Undy 8-pole Dynamic Loud-speaker in polished Walnut Cabinet. The Loud-speaker for the most exacting requirements, at a reasonable price - **55/-**

CHOOSE FROM THESE FOUR TYPES

The Undy 8-pole Dynamic Loud-speaker is the turning point in Loud-speaker design. The best Loud-speaker for sensitivity, power and frequency range. You must hear it to-day!

"UNDY"

Obtainable from your usual dealer.

ASK FOR DEMONSTRATION

WE TEST FOR YOU

A weekly review of new components



and tests of apparatus.

Conducted by our Technical Editor, J. H. REYNER, B.Sc., A.M.I.E.E.


Astra Slow-motion Dial

SLOW-MOTION dials have been sufficiently long on the market for their faults to be fully discovered and remedied. In consequence the discriminating user of to-day demands a slow-motion dial that will provide a suitable reduction ratio, absolute smoothness in motion, and freedom from any form of backlash. In addition he may require to work three or four condensers in cascade, and the mechanism must, therefore, take such a load without a tendency to slip.

We have no fault whatsoever to find with the Astra geared vernier dial Type 1, which is marketed in this country by the Emkabe Radio Co., Ltd.

The operating knob of this component is fitted below the centre of the dial and drives a 13-1 ratio reduction tooth gearing. The teeth are well cut, and the driving shaft is

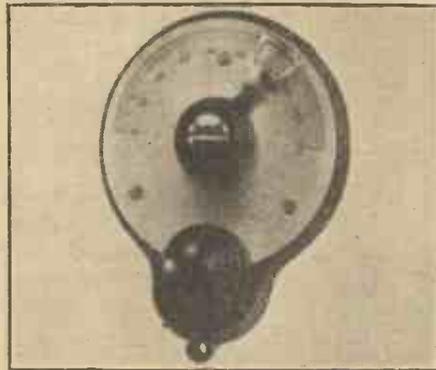constrained by a spring to bear on the larger driven wheel, with the object of avoiding backlash. By giving the knob a



Astra geared vernier dial

slight push upwards, the gear is brought out of engagement and the main spindle can be readily rotated from the central knob, which also carries a cursor moving over a scale in black lettering on a silvered metal front plate. As far as we can discover there should be nothing whatsoever to go wrong with this mechanism, since the device for putting the operating spindle in and out of gear is quite foolproof.

For mounting on a panel two holes only need be drilled, one for the main condenser spindle, and the other to take a metal support, which is also attached to the metal front plate, and may, therefore, be earthed. The condenser spindle fits into a split bush and is firmly fixed by screwing up an accessible knob on the front of the dial. A positive stop is provided in the minimum and maximum positions.

(Continued on page 848)

AS WITH TELSEN TRANSFORMERS SO ARE TELSEN COMPONENTS DESIGNED TO WITHSTAND


THE TEST OF TIME




TELSEN H.F. CHOKES. Designed to cover the whole wave-band range from 18 to 4,000 metres, extremely low self-capacity, shrouded in genuine Bakelite. Inductance 150,000 micro-henries. Resistance 400 ohms. Price 2/6 each.



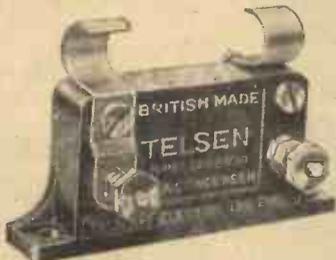TELSEN VALVE HOLDERS. Pro. Pat. No. 20286/30. An entirely new design in Valve Holders, embodying patent metal spring contacts, which are designed to provide the most efficient contact with the valve lens. Low-capacity, self-locating, supplied with patent soldering tags and hexagon terminal nuts. Fitted with nickel-silver shock-absorbing spring contacts. Price 1/- each.



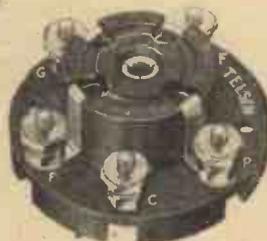TELSEN FIXED (MICA) CONDENSERS. Shrouded in genuine Bakelite, made in capacities up to .002 mf. Pro. Pat. No. 20287/30. .0003 supplied complete with Patent Grid Leak Clips to facilitate series or parallel connection. Can be mounted upright or flat. Tested on 500 volts. Price 1/- each.



TELSEN FIVE-PIN VALVE HOLDERS. Price 1/3 each.

All Telsen components embody many new and exclusive features which in construction are years ahead in radio component design. Thus — like Telsen transformers—Telsen components are built to withstand the test of time against all comers.

Start to build your new set now—start right—specify—

TELSEN COMPONENTS


Advt. of Telsen Electric Co., Ltd., Birmingham.

3 Essential Measurements

The H.T. applied to the Anode

The Grid bias applied to the Grid


The L.T. applied to the Filament

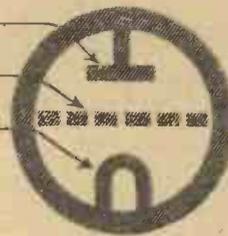

No receiver can work efficiently or satisfactorily unless the correct voltages are applied to the valves. If you want the best performance of which your set is capable, and expect length of good service from your valves, you must be CERTAIN that the various voltages are right, and this can only be done by measurement.

Don't guess—it's simpler and safer to measure.

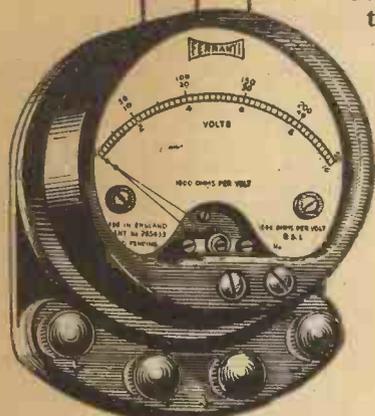Invest to-day in one of these high-grade instruments and take the first step towards better reproduction.



The FERRANTI 3-range Radio Meter, No. 16P, Portable Pattern, will test H.T. up to 150 volts
G.B. " " 30 " Price £2:10:0
L.T. " " 7½ "

FERRANTI RADIO METERS

FERRANTI LTD. Head Office & Works: HOLLINWOOD, LANCS.
LONDON: Bush House, Aldwych, W.C.2



TUNGSRAM SCREENED GRID VALVES

Tungram Screened Grid Valves — built to the Tungram tradition of quality — sold at the Tungram price of exceptionally low price. Tungram Screened Grid Valves complete the famous Tungram range. They are available now — your dealer stocks them.

For full particulars of the Tungram range write to department V.105.
TUNGSRAM ELECTRIC LAMP WORKS (GT. BRITAIN) LTD.,
Radio Dept., 72 Oxford Street, London, W.1.

Makers of the famous Electric Lamps.
Factories: Austria, Czechoslovakia, Hungary, Italy and Poland.
Branches: Belfast, Birmingham, Bristol, Cardiff, Glasgow, Leeds, Manchester, Newcastle, Nottingham & Southampton.

Prices: 2 v. and 4 v. Screened Grid Valves, 13/-; A.C. Screened Grid Valves, 16/-; L.F., 5/6; H.F., 5/6; R.C., 5/6; Power, 7/3; Super Power, 8/-; A.C. Indirectly Heated H.F. and L.F., 9/6 each; A.C. Directly Heated Power, 9/6; A.C. Directly Heated H.F. and L.F., 7/9; Rectifying Valves, 10/- each.
Tungram Photo Electric Cells: Nava E, £2:17:6.
Nava R, £3:3:0.





MAINS UNITS

McMichael, Rees-Mace, Selectors and other leading British Set Manufacturers recommend Regentone Combined Mains Units (A.C. and D.C.) for their own sets. Two years ago Regentone recommended the use of A.C. Valves rather than smoothed L.T. Units. To-day other manufacturers are following their lead.



MAINS COMPONENTS

Westinghouse specify them in every circuit of the "All-Metal Way 1931." Experts recommend them, and discerning constructors everywhere use them for their efficiency and reliability.



MAINS RECEIVER

The Regentone 4-valve A.C. All-Electric Receiver excels any other receiver in performance, smoothness of operation, reliability, and reserve of power—exactly as a six-cylinder car surpasses the performance of a four-cylinder. And the outward appearance is worthy of a receiver of such excellent performance.



ALL-ELECTRIC RADIO

If you are interested in Mains radio, whether Mains Units, Mains Components or Mains Receivers, the new Regentone Art Booklet, "The Simple Way to All-Electric Radio," contains much interesting information.

Write TO-DAY for your FREE COPY.

REGENT RADIO SUPPLY CO.,
REGENTONE HOUSE, 21, BARTLETT'S BUILDINGS, HOLBORN CIRCUS, LONDON, E.C.4.

Telephone: CENTRAL 8745 (5 lines).

Irish Free State Distributors:—Kelly & Shield Ltd., 47, Fleet Street, Dublin.

WE TEST FOR YOU

(Continued from page 846)

Owing to the smoothness of motion the dial is particularly pleasant to operate, and one may obtain a very fine graduation of tuning without a sign of backlash. The external appearance is quite attractive, whilst the diameter of the external moulding measures 3 in. The price of this component is 3s. 6d., and we recommend it for fine tuning.

Lewcos Constant-inductance Transformer

UNTIL quite recently the efficiency of a low-frequency transformer was often gauged from the inductance of the primary winding: whilst this inductance is of



Lewcos constant-inductance transformer

extreme importance, particularly when used in conjunction with high-impedance valves, it is now recognised that there are other factors requiring equal attention. Almost all iron-cored inductances vary in value when the current flowing through the winding is increased. If the variation is small throughout the working values of anode current, no perceptible distortion will result.

On the other hand if the inductance varies, as it often does, more than 50 per cent., due to the change in polarising current caused by speech modulation, the effect may be serious, since the amplification will be different for different strengths of signal, thereby detracting from the natural qualities of reproduction.

In the new Lewcos constant-inductance transformer, steps have been taken to overcome this source of distortion throughout a wide range of polarising currents. When tested in our laboratories the inductance without polarising current was found to be 35.7 henries. This had risen to 37 henries at 4 milliamps, and fallen again to 35 henries at 14.5 milliamps. Even with a current of 30 milliamps through the windings, the inductance did not fall below 30 henries.

We have had considerable experience of constant-inductance chokes and transformers and can vouch for their advantages when used under normal conditions.

The price is 20s. and it may certainly be recommended.

Postcard Radiō Literature

Gecophone Speakers

I LIKE the new Gecophone inductor dynamic speaker, which can be had either in chassis or complete cabinet forms. A little folder which I have received describes this, together with the "Stork" and "Junior Plaque" Gecophone speakers. **105**

A Portable for Indoors

The Amplion portable has two screen grid stages, and experts tell me that it has an excellent range. A folder which I have illustrates it well, and shows that it is in a neatly finished case, making it quite suitable for indoor use. **106**

Batteries Catalogued

Ever-Ready have sent me their latest catalogue of batteries and this seems to give the whole Ever-Ready range, from midget pocket lamp batteries to super capacity high-tension batteries, low-tension accumulators and car-starter batteries. **107**

For Home Builders

Home constructors will be interested in the new parts marketed by Edison Bell. There are some handy plugs, jacks, valve holders, R.C. couplers, transformers and resistances listed in a new catalogue. **108**

The New Melody-Maker

The new Cossor four-valve Melody Maker seems to be making a name for itself. It is so low priced. A new Cossor folder gives full details of this set and it will interest anyone who is on the lookout for a good kit receiver. **109**

A "Baby" Portable

The term "baby" seems to be justified by a new portable produced by V. Zeitlin and Sons, Ltd., for it weighs only 14 lb. and measures 9½ in. by 9 in. by 8 in. It is a three-valver and is fitted with a speaker. A two-valve headphone model is also available. **110**

A Useful Catalogue

A good general catalogue of handy accessories for set builders is that produced by Superlamp, Ltd. This gives details of all the new parts for the 1931 season. **111**

OBSERVED

GET THESE CATALOGUES FREE.

Here "Observer" reviews the latest booklets and folders issued by well-known manufacturers. If you want copies of any or all of them FREE OF CHARGE, just send a postcard giving the index numbers of the catalogues required (shown at the end of each paragraph) to "Postcard Radio Literature," AMATEUR WIRELESS, 58-61, Fetter Lane, E.C.4. "Observer" will see that you get all the literature you desire.

GERMANY RELAYS OUR DANCE MUSIC

ON two or three occasions recently the Berlin and Frankfurt broadcasting stations have given landline relays from Savoy Hill of dance bands engaged for the B.B.C. The other evening Germany took one and a quarter hours of dance music from Grosvenor House. It is interesting to remark that, since dance tunes seem to sweep from west to east, arriving in Germany several months after they are dead in this country, radio is in this instance not only killing space, but time as well. Judging by some of the direct broadcasts we occasionally pick up from German broadcasting stations, they are in dire need of good dance bands, such as those we import from America!

THE B.B.C. YEAR BOOK 1931

This annual, published on November 28, represents even a bigger attempt than has been made in previous years to chronicle the radio events and developments of the year and present them, with a wealth of photographs and illustrations, in the form of a year book. The period covered by the 1931 edition is from November 1, 1929, to October 31 of this year, and it is notable that in the short space of time allowed before going to press ample attention has been paid to the most topical radio happenings. The year book deals with each phase of the B.B.C.—programmes, policy, and engineering. It can be obtained, price 2s., from any book-stall or from the B.B.C. Bookshop at Savoy Hill.

Landline Balancing.—Apropos the article on B.B.C. landlines in our previous issue, there is a technical distinction that might have been made between "balancing" and "equalising." When a landline is balanced, the background noises due to cross currents and other causes are eliminated. But when the characteristic of the line is altered to enable it to handle the wide range of frequencies required for broadcasting, it is said to be equalised.—A. S. H.

Vert Wiring Clin.—It should be noted that the price of this handy wiring device is 2s. for a half-gross, sufficient for a three-valver, and not a gross as stated last week in the advertisement of W. Green and Sons (A), of Redclyffe, Horley, Surrey.

"Paper v. Electrolytic Condensers."—In connection with this article, which appeared on page 802 of last week's issue, it will be obvious that the sectional sketch shown illustrates the constructional features of an electrolytic condenser, and not a paper condenser, as stated.

It is estimated that 6,000,000 inhabitants living in German frontier provinces can only listen to foreign stations. In order to bring them in range of their own country the German Government is erecting three powerful broadcasting stations in Mueh-lacker, near Stuttgart; in Heilsberg, near Koenigsberg, and in the Rhineland.



READ THESE!

"I shall be pleased to introduce and recommend you to anyone of my acquaintance who is interested in wireless.
Although most of my friends possess wireless receiving sets, I shall try further to recommend you, and so hope thereby to make your promptitude, fair dealing, and trustworthiness known by my own dealings with you.
My own set has worked very well indeed, and has fully come up to my expectations."
J.E.B., Burnley.

"I want to take this opportunity of thanking you for the courtesy and particular attention you have given to my relatively small A/c, also the trouble you took in the early stages of my inquiries to make very clear all the points I raised. I may say that I have kept all the correspondence that has passed between us, and shall still keep it, as it is a testimonial in itself to your efforts to make a customer feel that he is a personal friend.
Here's wishing you a bumper season."
F.S., Sheffield.

EVERYTHING RADIO FOR CASH OR EASY TERMS WITH SERVICE AFTER SALES

PILOT RADIO KITS

... build one of these fine "A.W." Sets for Xmas

Success Guaranteed. Every specified component for your new set, down to the last screw, in an attractive carton, including The Famous Pilot Test Meter, without which no set is complete.

SHORT-WAVE TWO

(Described in this issue)
Kit 'A' Cash £4:13:10 (Or 12 monthly) 8/7
Kit 'B' Cash £5:12:10 (Or 12 monthly) 10/4
Kit 'C' Price £6:9:4 (payments of) 11/10

THE CHALLENGE THREE

(Described in "A.W." Nov. 8th, 1930)
Kit 'A' Cash £6:6:7 (Or 12 monthly) 11/7
Kit 'B' Cash £8:5:7 (payments of) 15/2
Kit 'C' Price £9:10:7 (payments of) 17/5

THE CHALLENGE FOUR

(Described in "A.W." Oct. 18th, 1930)
BATTERY MODEL
Kit 'A' Cash £7:19:10 (Or 12 monthly) 14/8
Kit 'B' Cash £11:1:10 (Or 12 monthly) 20/4
Kit 'C' Price £13:16:10 (payments of) 25/4
MAINS MODEL. For additional apparatus required add 28:3:5 to each of the cash prices above, or 15/2 to each of the monthly payments.

IMPORTANT NOTE

KIT "A" is less valves and cabinet. KIT "B" with valves less cabinet. KIT "C" with valves and cabinet. Any parts supplied separately.

SEND NOW FOR THE PILOT CHART

Contains detailed Price Lists of all the latest and best Kits, and over 30 valuable Hints and Tips for the Amateur Constructor.

IMMEDIATE DELIVERY

STRICT PRIVACY GUARANTEED to Easy Payment Orders

ALL ORDERS CARRIAGE PAID

PETO-SCOTT CO. LTD.

OUR NEW CATALOGUE describing ALL THE LEADING MAKERS' Receivers, Components, Radio Gramophones, Pick-ups, etc. A veritable guide to Radio. Get your copy to-day.
LONDON: 77 City Road, E.C.1 Phone: Clerkenwell 5416-7-8. 62 High Holborn, W.C.1 Phone: Chancery 8266. MANCHESTER: 33 Whitelaw Road, Chorlton-cum-Hardy. Phone: Chorlton-cum-Hardy 2028. NEWCASTLE, STAFFS: 7 Albany Road.

PLEASE SEND ME FREE YOUR (a) 1931 EASY WAY CATALOGUE; (b) LATEST P.L.O.T. RADIO CHART.

NAME _____

ADDRESS _____

A.W. 20/11/30

FIRST IN 1919—FOREMOST TO-DAY

Buy by post—it's quicker. Post this coupon NOW

MANUFACTURERS' KITS, ACCESSORIES, Etc., Etc.

- Send **10/-** COSSOR EMPIRE MELODY MAKER KIT, 1931 model, S.G., detector, and power. Cash Price £6 17 6
Only Balance in 11 monthly payments of 12 9.
- Send **23/6** 1931 OSRAM MUSIC MAGNET KIT, two S.G., detector, and power. Cash Price £11 15 0
Only Balance in 12 monthly payments of 18 6.
- Send **10/6** DYNAPLUS SCREENED THREE KIT, S.G., detector, and power. Cash Price £5 14 6
Only Balance in 11 monthly payments of 10 6.
All above Kit prices include valves and cabinet
- Send **7/4** EKCO 3F.20 H.T. ELIMINATOR, 20 m.a. Tappings for S.G., 60 volts, and 120/150 volts. For A.C. mains. Cash Price £3 19 6
Only Balance in 11 monthly payments of 7/4.
- Send **10/9** REGENTONE W.5 COMBINED H.T. ELIMINATOR AND TRICKLE CHARGER. One S.G., 1 variable and 1 fixed tapping for H.T. I.F. charging for 2, 4, and 6 volts. For A.C. mains. Cash Price £5 17 6
Only Balance in 11 monthly payments of 10 9.
- Send **8/6** EXIDE 120-VOLT W.H. TYPE ACCUMULATOR, in crates. Cash Price £4 13 0
Only Balance in 11 monthly payments of 8/6.
- Send **7/6** STANDARD WET H.T. BATTERIES, 144 volts, 20,000 m.a. Cash Price £4 2 0
Only Balance in 11 monthly payments of 7/6. Other voltages and capacities available. Detailed prices on application.
- Send **6/5** LAMPLUGH INDUCTOR SPEAKER, for perfect reproduction. Unit and chassis complete, ready mounted. Cash Price £3 10 0
Only Balance in 11 monthly payments of 6/5.
- Send **7/9** BLUE SPOT MODEL 51R CABINET SPEAKER. Cash Price £4 4 0
Only Balance in 11 monthly payments of 7 9
- Send **12/4** B.T.H. R.K. PERMANENT MAGNET SPEAKER. Unit only. Cash Price £6 15 0.
Only Balance in 11 monthly payments of 12 4.



READERS IDEAS & QUESTIONS

During a Thunderstorm

SIR,—I wonder whether if any of your readers have experienced a phenomenon which happened about two months ago? I was listening-in to the Manchester programme during a thunderstorm. There was a vivid flash of lightning and also a loud click in the loud-speaker, which is of the cone type. A red glow accompanied the loud click in the speaker, which seemed to come out for about a foot all round the speaker. I am using an indoor aerial. The speaker was not damaged in any way whatever.

W. M. (Manchester).

"The Exhibition Three"

SIR,—I have made up the "Exhibition Three" receiver and, whilst it works and gives reception, the tuning is flat and I seem to get a number of stations coming in at the same time. It seems that it is impossible to get selective tuning from the

receiver. I am using Atlas plug-in coils and have wired the receiver exactly as described. Is there any way in which the selectivity can be improved?

F. S. (Oldham).

If you have wired up the pins and sockets of your coil holders exactly as shown in our blueprint, then please note the following. Theappings on the Atlas coils are nearest the pin or plug end of the coil, which means that for proper selectivity the aerial coil holder should be wired so that its socket is connected to the earth terminal. If you will completely reverse the connections to all of your coil holders in the receiver, you will overcome your present trouble. In other words, the wire now going to the terminal which is connected to the plug of each coil holder should be taken to the terminal which joins the socket, and vice versa.

—ED.

The Limit in High Tension

SIR,—Last November you gave particulars of how to build the B.B.C. one-valve set, and in the instructions you mentioned that 120 volts H.T. could be used, but that the set would work satisfactorily on 60 volts.


A Lissen 60-volt battery has worked this set quite satisfactorily since last March, but for some time particular clarity of tone has been observed.

Testing the battery last week, I could only find 2½ volts. Testing this on three different voltmeters, I was still not satisfied that it was correct.

Having a second 2-volt accumulator at hand, I used it on the H.T. connections and found the set worked perfectly with full volume on phones. The valve is a Mullard PM1LF, which has been in constant use since December, 1928.

N. T. H. (Balham).

"A.W." Solves your Wireless Problems

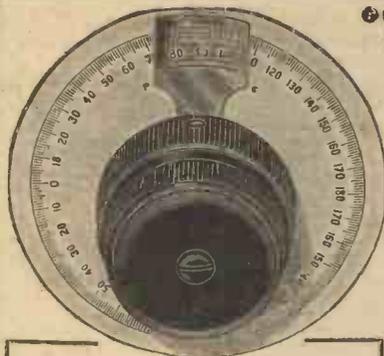

Our W.181 Dial has a fixed aluminium scale surveyed by a hair-line cursor. The ratio is 100-1, and the mechanism free of backlash, and noiseless. An outer bakelite rim completes an attractive article.

RETAIL PRICE 7/6

"Utility" MICRO-DIAL No. W.181


as used and recommended in the "Searcher Short-wave Two" described in this issue.

For ultra short-wave tuning this dial is without a rival—a point of view obviously shared by the designers of this new short-wave set. "Utility" Switches and Condensers are built up to a similar standard—you cannot get better value. Your local dealer is probably a "Utility" stockist. Write us direct for an illustrated 1930-31 List.

"Utility" Differential

Gives smooth reaction at all points of the scale. One-hole fixing and supplied with knob. Vernier mechanism can be fitted if desired. Prices:

Cat. No.	Cap.	Price
W.208	.0001	6/6
W.209	.00015	7/-
W.210	.0002	7/-
W.211	.0003	9/6
W.212	.0005	12/6

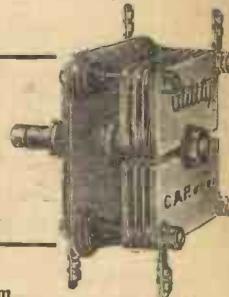

WILKINS & WRIGHT LTD., "Utility" Works, Holyhead Road, Birmingham.

"The Shielded Four-Electrode Valve"

Theory and Practice.
With Numerous Circuits.

By CAPT. H. J. ROUND, M.I.E.E.

Get a copy from any Bookseller or Bookstall, 2/6

A NEW CHUCK —that will definitely improve your loud-speaker

After considerable experimenting, we have at last designed an entirely new type of chuck for all cone loud-speakers. This is the TONAX, which by means of the screwing device behind the washer, grips the driving rod of the unit so as to eliminate all the trace of chatter.

We are confident that this chuck will improve the purity of your present cone speaker by 100 per cent.

It has a highly-polished nickel-plated finish, AND WILL FIT THE DRIVING ROD OF ALL MAKES OF UNIT. Supplied with specially lined washers.

Obtainable from most dealers, price 1/- each, or direct from the manufacturers, 1/2 post free. Get your TONAX chuck without delay and you will be surprised at the all-round improvement of your loud-speaker reproduction.



Trade inquiries invited

GARRATT STORES (Wholesale Dept.)

193 GARRATT LANE, WANDSWORTH, S.W.18

**HERE IS THE
RADIO GRAMOPHONE CABINET
YOU ARE LOOKING FOR**

INSTALL A
"LANGMORE"

and have your Gramophone,
Wireless Set, Loud-speaker
and Batteries all in one cabinet.

These cabinets are very strongly constructed of selected Oak and Plywood. Size overall, 3 ft. 2 in. high by 21 in. wide by 15 in. deep.

THE TOP SECTION. Size 4½ in. high by 18 in. wide by 14 in. deep, gives ample accommodation for gramophone and pick-up.

THE CENTRE SECTION. Size 10 in. high by 18 in. wide by 14 in. deep, is for the Wireless Set, to take a panel either 18 in. by 7 in. or 18 in. by 8 in.

THE BOTTOM SECTION. Size 14 in. high by 18 in. wide by 13½ in. deep, gives accommodation for Loud-speaker and Batteries.

The whole of the back is enclosed by double doors so that all parts are easily accessible. ALL are fitted with hinged top, heavy platform to take a 12" turntable for the Gramophone and a Substantial baseboard for the Wireless Set.

BEAUTIFULLY FINISHED
:: JACOBAN OAK ::

Trade Inquiries Invited.


THE MISCELLANEOUS TRADING CO., LTD.

13 & 17 NEW OXFORD STREET LONDON, W.C.1
Phone: Holborn 4891



Price 49/6 each

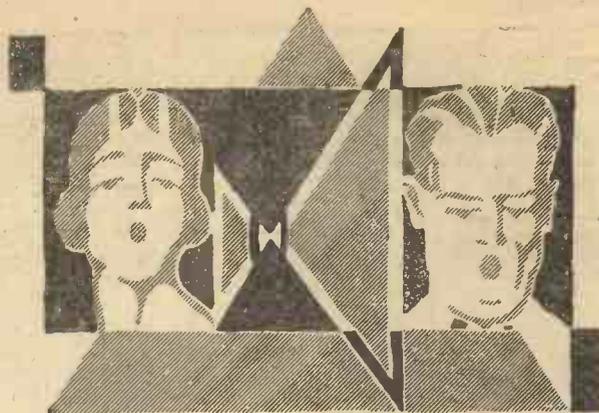PACKED FREE AND SENT CAR-
RIAGE PAID TO ANY ADDRESS
IN GREAT BRITAIN.



WATES

"DOUBLE CONE"
PRINCIPLE OF SOUND
REPRODUCTION PROVIDES
AN
INDEPENDENT MEDIUM
FOR
HIGH AND LOW NOTES
with astonishing realism
of speech and music

THE Wates Universal Chassis to which you can fit your present unit in fifteen minutes, employs two cones of special quality paper, scroll cut to obviate a direct line through the sound waves, and treated to ensure constant crispness.

The large cone responds to the lower frequencies and the small one to the upper registers, with a purity and fidelity that immediately transforms your speaker into a superb instrument, with a range of tonal quality that will amaze you.

Buy the Wates Chassis now, and for a few shillings enjoy fifty per cent better results. Supplied complete with screws, extension piece and fully detailed instructions for fitting to all popular units.

READ THE EXPERT'S REPORT ON
PAGE 714 IN "A.W." NOV. 8.


This report is your assurance of the high performance that is claimed for this fine chassis.

From all Radio Dealers or if any difficulty write direct for particulars to:—

The Standard Battery Co.
(Dept. A.W.) 104-108 SHAFTESBURY AVENUE,
LONDON, W.C.2.

PRICES: £ s. d.

Wates Chassis, 12"	..	11	6
14"	..	12	6
20"	..	17	6
Wates 14" Star Speakers complete, Oak	..	3	10 0
Mahogany	..	3	15 0
Universal bracket (only) for fitting various units to speakers	..	2	0
Wates 20", complete Oak	..	4	10 0
Mahogany	..	4	15 0
Silk-lined fret for 12" Chassis	..	4	0
For 14" Chassis	..	5	0

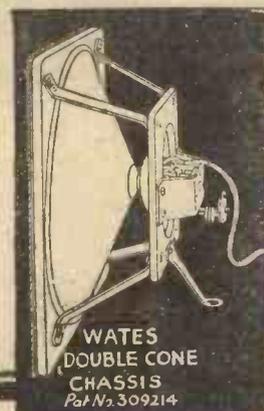

Why worry about old fashioned plug-in coils when the new British General Aerial Tuning Unit covers the full tuning range of 200 to 2,000 metres by means of a single dial. Easy to fix, simple to tune and guaranteed effective.

From all dealers of repute or direct from the manufacturers.
PRICE 14/6

BRITISH GENERAL
MANUFACTURING CO., LTD.,
Brockley Works,
LONDON, S.E.4.

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

BROADCAST TELEPHONY

Broadcasting stations classified by country and in order of wavelengths. For the purpose of better comparison, the power indicated is aerial energy.

Metres	Kilo-cycles	Station and Call Sign	Power (Kw.)	Metres	Kilo-cycles	Station and Call Sign	Power (Kw.)	Metres	Kilo-cycles	Station and Call Sign	Power (Kw.)
GREAT BRITAIN											
25.53	11,751	Chelmsford (G5SW)	15.0	313	958.5	Natan-Vitus	0.7	363.4	825.3	Algiers (PTT)	13.0
200	1,500	Leeds	0.10	316	950	Marseilles (PTT)	1.5	410	721	Radio Maroc (Rabat)	10.0
242	1,238	Belfast	1.2	328.2	914	Grenoble (PTT)	1.2	1,350	222.2	Tunis Kasbah	0.7
261.3	1,148	London Nat.	08.0	329.5	910.3	Poste Parisien	1.2	364	824	Bergen	1.0
288.5	1,040	Newcastle	1.2	345.2	869	Strasbourg (PTT)	12.0	365	821	Frederiksstad	0.7
288.5	1,040	Swansea	0.10	369.3	812.2	Radio LL (Paris)	0.5	453.2	662	Porsgrund	1.2
288.5	1,040	Stoke-on-Trent	0.10	385	779	Radio Toulouse	9.0	453.2	662	Nidaros	1.5
288.5	1,040	Sheffield	0.10	447	671	Paris (PTT)	2.0	1,060	283	Oslo	75.0
288.5	1,040	Plymouth	0.10	466	644	Lyons (PTT)	2.3	NORWAY			
288.5	1,040	Liverpool	0.10	1,446	207	Eiffel Tower	15.0	364	824	Bergen	1.0
288.5	1,040	Hull	0.10	1,725	174	Radio Paris	17.0	365	821	Frederiksstad	0.7
288.5	1,040	Edinburgh	0.4	GERMANY				453.2	662	Porsgrund	1.2
288.5	1,040	Dundee	0.10	31.38	9,560	Zeeseen	15.0	453.2	662	Nidaros	1.5
288.5	1,040	Bournemouth	1.2	218	1,373	Flensburg	0.6	1,060	283	Oslo	75.0
288.5	1,040	Bradford	0.10	227	1,319	Cologne	1.7	214.2	1,400	Warsaw (2)	1.9
301	995	Aberdeen	1.2	227	1,319	Münster	0.6	231	1,283	Lodz	2.2
309.9	968	Cardiff	1.2	227	1,319	Aachen	0.31	244	1,229	Cracow	1.5
356.3	842	London Reg.	45.0	232.2	1,292	Kiel	0.3	312.8	959	Wino	0.5
376.4	797	Manchester	1.2	239	1,256	Nürnberg	2.3	388.1	887.1	Poznan	1.9
398.0	752	Glasgow	1.2	246.4	1,217.2	Cassel	0.3	381	788	Lvov	2.2
470	626	Midland Reg.	38.0	253.4	1,184	Leipzig	2.3	400.8	732	Katowice	16.0
1,554	193	Daventry (Nat.)	35.0	259.3	1,157	Gleiwitz	5.6	1,411	212.5	Warsaw	14.0
AUSTRIA											
240	1,220	Linz	0.6	270	1,112	Kaiserslautern	0.25	POLAND			
240	1,220	Salzburg	0.6	276	1,085	Königsberg	1.7	214.2	1,400	Warsaw (2)	1.9
283.0	1,058	Innsbruck	0.6	283.6	1,058	Magdeburg	0.6	231	1,283	Lodz	2.2
352	851	Graz	9.5	283.6	1,058	Berlin (E)	0.6	244	1,229	Cracow	1.5
453	666	Klagenfurt	0.6	316.6	947.6	Bremen	0.3	312.8	959	Wino	0.5
517	581	Vienna	20.0	318.8	941	Dresden	0.3	388.1	887.1	Poznan	1.9
BELGIUM											
206	1,160	Antwerp	0.4	325	923	Breslau	1.7	381	788	Lvov	2.2
212	1,115	Binche	0.2	360	833	Stuttgart	75.0	400.8	732	Katowice	16.0
216	1,391	Chatelineau	0.25	372	806	Hamburg	1.7	1,411	212.5	Warsaw	14.0
243	1,235	Courtrai	0.1	390	770	Frankfurt	1.7	PORTUGAL			
244.7	1,226	Ghent	0.25	418	716	Berlin	1.7	240	1,247	Oporto	0.25
251.4	1,194	Schaerbeek	0.5	452.1	662	Danzig	0.25	ROMANIA			
338.2	887	Velthem (Louvain)	15.0	473	635	Langenberg	17.0	391	761	Bucharest	16.0
CZECHO-SLOVAKIA											
500	590	Brussels (No. 1)	1.2	533	563	Munich	1.7	720	416.6	Moscow (PTT)	20.0
203	1,139	Moravska-Ostrava	11.0	560	536	Augsburg	0.3	800	375	Kiev	20.0
279	1,076	Bratislava	14.0	566	530	Hanover	0.35	824	364	Sverdlovsk	25.0
294	1,030	Kosice	2.5	570	527	Freiburg	0.3	937.5	320	Kharkov (RV20)	25.0
342	878	Brunn (Brno)	3.0	1,635	183.5	Zeeseen	35.0	1,000	300	Lejningrad	20.0
487	617	Prague (Praba)	5.5	1,635	183.5	Norddeich	10.0	1,073	279.6	Kostov	4.9
DENMARK											
281	1,067	Copenhagen	1.0	HOLLAND				1,103	272	Moscow Popoff	40.0
1,153	260	Kalundborg	10.0	31.28	9,599	Eindhoven (PCJ)	30.0	1,200	250	Kharkov (RV4)	25.0
ESTONIA											
401	748	Reval (Tallinn)	0.7	290	1,004	Hilversum	8.5	1,304	230	Moscow (Trades' Unions)	100.0
FINLAND											
221	1,355	Helsinki	15.0	290	1,004	Radio Idzarda (The Hague)	0.6	1,380	217.5	Balkou	10.0
291	1,031	Vitpuri	15.0	1,071	280	Scheveningen-Haven	5.0	1,481	202.5	Moscow (Kom)	20.0
1,796	167	Lahti	54.0	1,875	160	Huizen	8.5	SPAIN			
FRANCE											
172.5	1,739	St. Quentin	0.3	ICELAND				251	1,193	Barcelona	1.0
200	1,500	Radio Roubaix	0.2	210	1,430	Budapest (Csepel)	1.0	206.7	1,125	Barcelona	10.0
210	1,430	Radio Touraine	0.2	550	545	Budapest	23.0	340	860	Barcelona (EAJ1)	8.0
222.9	1,316	Fécamp	1.0	IRISH FREE STATE				308	815	Seville (EAJ5)	1.5
235.1	1,275	Nimes	1.0	413	725	Dublin (2RN)	1.5	413.8	725	Radio Espana	1.0
244.9	1,224	Béziers	0.6	80		Rome (3RO)	9.0	424	707	Madrid (EAJ7)	2.0
249.5	1,202	Juan-les-Pins	0.5	296	1,023	Turin (Tocino)	8.5	490	652	San Sebastian	0.5
256	1,171	Toulouse (PTT)	1.0	312	916.2	Genoa	1.5	SWEDEN			
265	1,136	Lille (PTT)	15.0	332	905	Naples (Napoli)	1.7	230.6	1,301	Malmö	0.75
272	1,103	Rennes	1.2	441	680	Rome (Roma)	75.0	257	1,166	Hörby	15.0
280	1,049	Montpellier	2.0	453	662	Bolzano (IBZ)	0.2	800.2	999.3	Falun	0.65
287.2	1,044.6	Radio Lyons	0.5	501	599	Milan (Milano)	8.5	322	932	Göteborg	15.0
296.4	1,012.1	Limoges (PTT)	0.08	ITALY				436	689	Stockholm	75.0
300	1,000	Strasbourg	1.0	80		Rome (3RO)	9.0	542	534	Sundsvall	15.0
304	988	Bordeaux (PTT)	35.0	312	916.2	Genoa	1.5	770	389	Ostersund	0.75
308	973	Neuilly (Paris)	0.3	332	905	Naples (Napoli)	1.7	1,229.5	244	Boden	0.75
LITHUANIA											
1,935	155	Kaunas	7.0	441	680	Rome (Roma)	75.0	1,348	222.5	Motala	40.0
NORTH AFRICA											
363.4	825.3	Algiers (PTT)	13.0	453	662	Bolzano (IBZ)	0.2	SWITZERLAND			
410	721	Radio Maroc (Rabat)	10.0	501	599	Milan (Milano)	8.5	318.8	943	Basle	0.65
NORWAY											
364	824	Bergen	1.0	403	747	Berne	1.1	459	653	Zurich	0.75
365	821	Frederiksstad	0.7	478.7	454.6	Lausanne	0.6	760	395	Geneva	1.5
453.2	662	Porsgrund	1.2	TURKEY				1,200	250	Istanbul	5.0
453.2	662	Nidaros	1.5	1,595	188.7	Ankara	7.0	YUGOSLAVIA			
1,060	283	Oslo	75.0	306.3	978	Zagreb (Agram)	0.7	430.4	696.9	Belgrade	3.0
POLAND											
214.2	1,400	Warsaw (2)	1.9	574.7	522	Ljubljana	2.8	LITHUANIA			
231	1,283	Lodz	2.2	1,935	155	Kaunas	7.0	NEW OPERA PLANS AND THE B.B.C.			

JUNIT MAINS UNIT



Everything in the Junit has been designed for your convenience. It is very compact, being only 9" x 5" x 3 1/2". It operates on all mains from 200-250 volts. It is constructed to give perfect screening. It will operate all modern sets. The unit is so designed that your existing battery leads will easily reach the corresponding terminals on the unit. You need not buy additional leads.

MASTER OF THE MAINS

UNIT TYPE 150/4 A.C.
Giving 150 volts at 25 milliamperes load, and incorporating 4 volt centre tapped winding for supplying filament current for indirectly heated valves. Size 9 ins. x 5 ins. x 3 1/2 ins.

Tappings: One variable 0-150
" fixed 150
" " S.G.
Price £5 0 0

UNIT TYPE 120
Giving 120 volts at 20 milliamperes load. Size 9 ins. x 5 ins. x 3 1/2 ins.

Tappings: One variable 0-120
" fixed 120
" " S.G.
Price £4 7 6

UNIT TYPE 120/T.C.
Giving 120 volts output at 20 milliamperes load, and also containing trickle charger for 2, 4 or 6 volt accumulators. Size 9 ins. x 5 ins. x 3 1/2 ins.

Tappings: One variable 0-120
" fixed 120
" " S.G.
Price £5 17 6

SERVANT OF THE SET

JUNIT

Advertisement of the Junit Manufacturing Co., Ltd.,
2 Ravenscourt Square, W.6

NEW OPERA PLANS AND THE B.B.C.

LISTENERS who are anxious to have more broadcast operas will be pleased to hear of an arrangement made between the Covent Garden Opera Syndicate, Ltd., and the B.B.C. for carrying out a scheme of grand opera production over a number of years.

The undertaking will be administered by a company to be known as the Covent Garden Opera Syndicate (1930), Ltd., under the chairmanship of Mr. F. A. Szarvasy, the originator of the proposal.

More than two hundred performances will be given yearly, allocated between the

grand season of ten weeks at Covent Garden, autumn and winter seasons there of six weeks each, and two-week seasons in at least six other centres throughout the country.

Except for the grand season, popular prices will be charged at all performances and the artistes employed will be almost exclusively British.

An income of £30,000 has been guaranteed from various sources, and all the funds and earnings of the new company will be devoted to furthering the scheme.

Arrangements are in the course of being completed for the participation of Sir Thomas Beecham and the Imperial League of Opera. At least sixty performances per annum will be broadcast.

"SHORT-WAVE TWO"

You will want this H. & B. Kit after reading about this splendid set described in this issue.

Ebonite Panel, 14 in. by 7 in. (Trelleborg)	4 0
Short-wave Condenser, .00015 microfarad (Cyldon)	11 6
Reaction Condenser, .0002 microfarad (Dubiller)	5 6
Two Slow-motion Dials (Ormond)	5 0
400-ohm Potentiometer, panel mounting (Lissen)	2 0
On-off Filament Switch (Pioneer)	1 3
Two Valve Holders, anti-microphonic (Telsen)	2 0
Fixed Condenser, 2 microfarad (Lissen)	3 6
Fixed Condenser, 1 microfarad (Lissen)	2 6
High-frequency Choke (Telsen)	2 6
Two Fixed Condensers, .0001 microfarad (Telsen)	2 0
Grid Leak, 3 megohm (Dubiller)	1 8
Grid Leak Holder (Lissen)	6
Short-wave Inductance Unit (Eddystone, type CS3)	1 0 0
Low-frequency Transformer (Telsen "Ace")	8 6
15,000-ohm Spaghetti Resistance (Bulgin, Burne-Jones)	1 6
Two Terminal Blocks (H. & B.)	8
Four Terminals, marked: A, E, L.S., L.S+. (Elding-Lee)	1 6
Four Wander Plugs, marked: H.T., H.T., G.B., G.B. (Belling-Lee)	1 0
Pair of Panel Brackets (H. & B.)	1 3

CASH PRICE £3 18 10

Price of Kit includes Panel already drilled, Baseboard, all Wire and Screws needed.

Two Valves, Mullard, Cosmor, or Marconi, 19/- extra. Any Component Supplied Separately.

NOTE.—If you buy this KIT, we build set FREE if desired.

SCREENS AND COILS

For popular "A.W." and "W.M." Sets.

SCREENS	COILS
Regional Band-pass Four 2/9	Music Monitor .. 7/6
Five-point Three .. 2/9	Music Leader .. 10 6
The Arrow Two .. 1/9	Arrow Two by-pass coil 2/6
Continental Portable .. 1/9	IMPORTANT NOTICE. We supply KITS for all the above sets. Prices on application.
Horizon Four .. 2/6	
New Brookmans Three 1/9	

SCREENS, FOIL, AND COILS	"CHALLENGE THREE"	"CHALLENGE FOUR"
2 COILS, carefully matched, 2 1/2, pair post free.	3 COILS, carefully matched, 3 1/8 the set, post free.	
SCREENS. Set with foil, earthing terminals, and screws, 2/6, post free.	SCREENS. Set, complete with foil base and screws, 3/9, post free.	

Carriage paid on all cash orders. H. & B. C.O.D. charges paid on orders over £1.

H. & B. RADIO, 34, 36, 38 Beak Street, Regent Street, London, W.1. Gerrard 2834

TANNOY PRODUCTS

"ALL-ELECTRIC" RADIO-GRAMS

BY being 'not mass produced' but individually built, these instruments represent the embodiment of the best that modern technique and skill can produce. They require no winding and no batteries of any sort. Simply 'Switch On' either for Radio or Gramophone.


All Electric H.T., L.T. and Grid Bias, matched transformer-coupled moving coil loud-speaker, slow speed induction motor, illuminated dials. Cabinets in Oak, Mahogany and figured Walnut. Let us demonstrate one to you—for no words can fully justify our product—demonstrations arranged all over England.

PRICES from 45 Gns.

Tannoy Products, Dalton St., W. Norwood, S.E.27



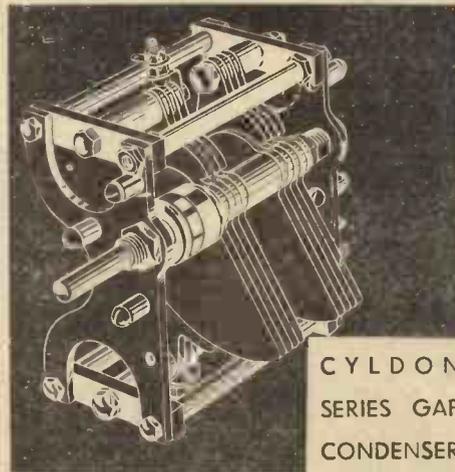180 S.W. STATIONS IN RANGE WITH CYLDON SERIES GAP



CYLDON SERIES GAP CONDENSER

Madagascar, Buenos Aires, Mexico, Indo-China, Canada, Siam, Schenectady N.Y., Argentina, Suva, Fiji Islands, Sydney (Australia), Cairo (Egypt), Chicago, Moscow (Russia), New Zealand, Khabarovsk (Siberia), Washington D.C. and 160 other short wave stations between 12 and 142 metres are definitely available to all short wave enthusiasts building or substituting their present condenser with the New CYLDON Series Gap Condenser.

Specified for the Searcher Short Wave 2 described in this issue.

Illustrated and described Type S.G. 15.

.00015 mfd. 16/6 From all Radio Dealers, or direct from makers.

TUNING for S. W. stations is like fishing—it needs skill, patience and a good outfit including the New CYLDON Series Gap Condenser.

1. Absolute silence in operation—no current passes through bearings: 2. No backlash—special construction of the bearings: 3. Exceptionally low minimum—the sections are series-spaced: 4. No pigtails—no inductance at high frequencies: 5. Frame work can be earthed—eliminating all hand-capacity. Definitely the greatest advance in Radio Technics since the Log-Mid-Line Condenser was introduced by CYLDON. You'll boast about a set built with CYLDON.

cyldon

FIVE YEARS GUARANTEE

SYDNEY S. BIRD & SONS LTD. CYLDON WORKS, SARNESFIELD ROAD, ENFIELD, MIDDLESEX, Tele: Enfield 2071/2

WIRELESS MAGAZINE

The Big British Wireless Monthly

1/-

LOTUS POWER RECTIFYING UNIT



FOR A.C. MAINS

The Lotus Power Rectifying Unit consists of a Transformer, Rectifying Valve, Condenser, and Smoothing Choke. It is suitable for the conversion of D.C. H.T. Eliminators to A.C., and the energising of moving coil speakers. The Unit is enclosed in a metal box, 6 1/2" x 5 1/2" x 6 1/2". Price complete £5, or 12 monthly payments of 9/-. From all Radio Dealers.

Write for illustrated Catalogue to GARNETT, WHITELEY & CO., LTD., LIVERPOOL.

Don't Forget to Say That You Saw it in "A.W."




ENDURANCE

Stonehenge represents to us today an enduring factor of a bygone age. Strength is symbolised by these monoliths. They derive their strength from their size. Heayberd Power Transformers and Chokes derive their strength from the fine workmanship and the best materials that are an integral part of their construction.

For silent power of enduring quality USE




COMBINED CHOKE and TRANSFORMER

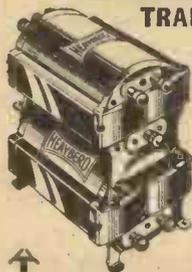

The new component which is actually two in one. For all mains. State voltage and periodicity when ordering. Prices for combined model from 2/6.

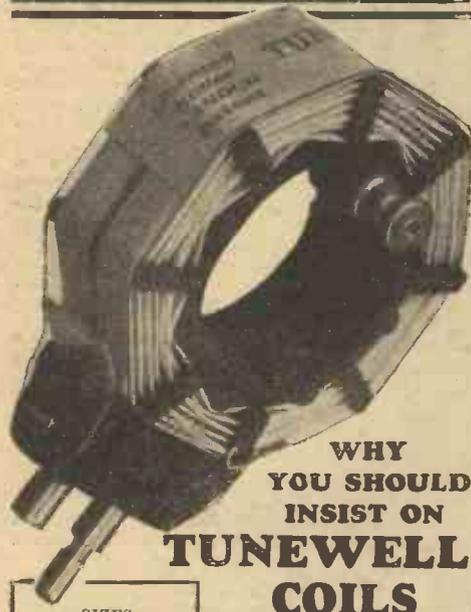F. C. HEAYBERD & CO
10 Finsbury Street, E.C.
*Phone: Metropolitan 7516.



WHY YOU SHOULD INSIST ON TUNEWELL COILS

SIZES AND PRICES Standard.	
25, 35, 50, 75 each	1/6
30, 40, 60, 100 each	1/8
125, 150 each	2/3
275 for 5XX each	2/6
200, 225 each	2/9
250 each	3/3
300 each	3/9
400 each	4/3
Centre tapped 9d. each extra.	
X type 1/- extra.	

- 1.—Longer tuning range for each coil.
 - 2.—Accurately made, suitable for ganging.
 - 3.—Solid construction; no cross wires.
 - 4.—Accessibility of terminal.
 - 5.—Price of whole range only a few pence more than "junk" coils.
- New dual range coil for Reinartz circuits. X-tapped on both high and low waves. Super-selective. 10/6
- Tunewell range of speakers, including plaque types from 28/6 to 42/-
- "Challenge" coils for straight or S.G. circuits. 10/6 each.
- TURNER & CO.,**
54 Station Road, London, N.11.



A SERIES of old musical comedies will provide the material for a programme which is to be broadcast nationally on December 9. The title of the programme is "Theatrescope," and it will be presented by John Watt.

The symposium by distinguished medical men who have broadcast on the special aspects of medicine with which they are principally concerned will be brought to a close on December 1 by Sir Humphry Rolleston, who will summarise the problem as a whole. Sir Humphry is one of the King's physicians.

"Seasonal" music and poetry are very popular, and on December 7 Manchester and Leeds listeners will hear a concert called "Winter Landscape," performed by the Northern Wireless Orchestra.

On December 11 the Hallé Society are giving a performance of Gustav Mahler's "Song of the Earth" for broadcast from the Manchester and Leeds transmitters.

When Mr. L. du Garde Peach and Mr. E. W. Lustgarten join issue on December 10, on the important question of whether it is better to live in the North Country or in a Northern town, listeners in Manchester and Leeds may be sure of enjoying a very amusing and witty forty minutes.

"Contrasts," which is to be broadcast on December 3 (Regional) and December 6 (National) is the work of Derek McCulloch.

The third talk in the series "Talks to Amateur Dramatic Societies" is entitled "How to Dress a Play" and will be broadcast from Cardiff by Miss Mariam Radford on December 8.

Scissors for Luck, by Dorothy Howard Rowlands, will be given from Cardiff by the Bristol Drama Club on December 9 during a programme which is introduced by the National Orchestra of Wales.

Mr. C. B. Cochran will take the chair at a studio discussion on December 8 between Mr. Hugh Walpole and Mr. Osbert Sitwell.
(Continued on page 856)

When Submitting Queries

Please write concisely, giving essential particulars. A Fee of One Shilling (postal order), a stamped addressed envelope, and the coupon on the last page must accompany all letters. The following points should be noted.

The designing of apparatus or receivers cannot be undertaken.

Modifications of a straightforward nature can be made to blueprints, but we reserve to ourselves the right to determine the extent of an alteration to come within the scope of a query.

Queries cannot be answered personally or by telephone.

BROWNIE



DOMINION BATTERY S.G.3

THE most sensitive and selective of all 3-valve combinations—screen grid, detector, and pentode—that's what you get in the wonderful Brownie DOMINION Battery S.G.3! Not only is it the finest receiver of its kind—it's the finest value too, for its cost in a handsome, richly polished solid walnut cabinet, including valves and royalty, is only £10 : 15 : 0 or 19/- down!

YOUR DEALER WILL DEMONSTRATE

Your dealer will be delighted to demonstrate the Brownie DOMINION Battery S.G.3. In any case send now for free illustrated catalogue of the complete Brownie range of Battery and Mains operated receivers. Prices from 50/-

DOMINION (BATTERY) S.G.3

Price, including valves & royalty £10 : 15 or 19/- down

BROWNIE WIRELESS COMPANY (G.B.) LTD.,
Dept. U., NELSON ST. WORKS, LONDON, N.W.1

SCRAP THAT DUD

That cheap pocket 30 ohms-per-volt meter; that several-in-one affair that ruined your H.T. battery with its 30 m.a. load per volt-reading. You want a

MULTI-RANGE DIX-ONEMETER

The extensive sale and increased use has enabled a reduced price to be offered below the already exceptionally low price.

DIX-ONEMETERS are now 50/- only, a remarkably small price for a meter worth £10 in comparison with others.

Latest Model. To 1st Grade Brit. Eng. Standard. Mirror Double Scale. Moulded Base. The finest Precision Multi-measuring instrument is the DIX-ONEMETER, the acknowledged Radio standard beloved by Expert and Amateur.

Imitations of its Bakelite case and mirror scale are inferior. They lack the 50 Multiplier Ranges, the Precision, the Duplex Scales, Knife-edge Needle, Accurate Bearings, and High Figure of Merit. Remember that the DIX-ONEMETER is nearly electro-static in its tiny load and can be used at 2,500 ohms per volt. On 100 volts the high value of 250,000 ohms can be used. Micro-Amps., Milli-Amps., and Amps to 20A. Milli-Volts and Volts to 2,000V. Resistances from 50 ohms to 50 million ohms. All these are measured with ease on the versatile and finely-made DIX-ONEMETER.

DIX-ONEMETER 50/- ONLY
Range Multipliers 6/6 each
Electrical and Radio Test Booklet Free.
ELECTRADIX RADIOS,
218, Upper Thames Street, E.C.4
Telephone: City 0191.

You **MUST** have the
"WIRELESS MAGAZINE"
Every Month Price 1/-



5-POINT SOLID!

Many modern valves, both 4-pin and 5-pin, have solid pins, and these frequent y make poor contact in holders designed to take split pins. The solution is the Benjamin "5-pin" whose special grip contacts in one piece with their tinned solder lugs give excellent connection to 4- or 5-pin solid or split. It is sprung, too!


Write for Catalogue No. 1142
The BENJAMIN ELECTRIC LTD.
Tariff Road, Tottenham, N.17
Tottenham 1500

19

BENJAMIN

PERFECT UNIT ALIGNMENT - AUTOMATIC

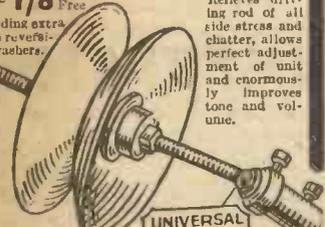Price 1/8 Post Free including extra large reversible washers.



Relieves driving rod of all side stress and chatter, allows perfect adjustment of unit and enormously improves tone and volume.

Pat. App. for. **UNIVERSAL BALL JOINT**

wonderful results on "A.W." LINEN DIAPHRAGM LOUD-SPEAKER

COMPLETE EQUIPMENT TO MAKE THIS FINE "A.W." SPEAKER

Specially prepared linen for 2" Speaker 5/- Golden tautening dope does not deteriorate. 1/- per tin. Weedon self-centring rod 1/6. 2 Reversible washers "extra large" 6d. 2 B.A. rods complete with nuts and washers per set 1/6. Straining wire 4d. per ft.

WEEDON'S GOLDEN TAUTENING DOPE Improves the tone 50% with age and maintains its tautness indefinitely. Sold 1/- in airtight tins. Price per tin

BEST IRISH LINEN specially selected for use with G.T. Dope. STRAINING WIRE, 4d. per ft. 18/- per sq. yd. 2 B.A. RODS complete with nuts and washers, 1/6

TRADE ENQUIRIES INVITED

WEEDON & CO. 89 Lonsdale Avenue, East Ham, London, E.6

DX THE STANDARD PLUG-IN COIL

Sold everywhere from 1/-

DX COILS Ltd, London, E.8

LET "A.W." SOLVE YOUR WIRELESS PROBLEMS

FULL-SIZE BLUEPRINTS

When ordering, please send Postal Order, NOT STAMPS

CRYSTAL SETS (6d. each)

B.B.C. Brookman's Park Set AW206
Regional Crystal Set WM176

ONE-VALVE SETS (1s. each)

Monodyne AW258
Hartley Single-valver WM198

TWO-VALVE SETS (1s. each)

Talisman Two (D, Trans) AW194
No-battery A.C. Mains Two (D, Trans) AW238
No-battery Gramo-radio 2 (D, Trans) AW239
1930 Talisman 2 (D, Trans) AW242
Easy Tune Short-wave 2 (D, Trans) AW245
Searcher Two (D, Trans) AW249
Arrow Two (D, Trans) AW250
Forty-five-shilling Two (D, 8 Trans) AW259
Searcher Short wave 2 (D, Trans) WM188
Brookman's Two (D, Trans) WM182
New Crusader (D, Trans) WM187
Radio-Record Two (SG, D) WM201
Gleaner Two (D, Trans) WM208
Music Monitor (D, Trans) WM213
Merlin Two (A.C. Set) WM220
Five-Point Two (D, Trans) WM220

THREE-VALVE SETS (1s. each)

Wide World Short-wave Three (HF, D, Trans) AW207
1930 Ether Searcher (SG, D, Trans) AW211
Best-by-Ballot Three (SG, D, Trans) Price 4d. free with copy of "A.W." AW217
Everybody's All-electric Three (SG, D, Trans) -A.C. AW221
1930 Clarion Three (SG, D, Trans) AW223
Beginner's Regional Three (D, 2LF) AW243
Britain's Favourite Three 1930 (D, 2 Trans) AW244
Car Three (D, R.C. Trans) AW247
The "A.W." Exhibition 3 WM161
Brookman's Three (SG, D, Trans) WM164
Community Three (D, RC, Trans) WM170
Brookman's Push-Pull Three (SG, D, Trans) 1/6 WM178
All-nations Three (D, 2 Trans) WM179
Inceptordyne (SG, D, Pentode) WM184
Brookman's A.C. Three (SG, D, Trans) 1/6 WM190
Music Marshal (D, 2 Trans) WM196
Gramo-Radio D.C. Three (SG D Trans) WM199
Concert Three (D, 2 Trans) WM205
New Lodestone Three (HF, D, Trans) WM209
De-Luxe Three (D, RC, Trans) WM212
Five-Point Three (SG, D, Trans) WM217
Falcon Three (A.C. Set) WM218
New Brookman's Three (SG, D, Trans) WM218

FOUR-VALVE SETS (1s. 6d. each)

Music-Lover's Gramo-radio (Loud-speaker) 1s. AW202B
Horizon Four (SG, D, 2 Trans) AW237
Challenge Four (2SG, D, Trans) with copy of "A.W." AW251
Challenge Four (2SG, D, Trans, mains operated) with copy of "A.W." AW252
1930 Monodial (2SG, D, Trans) WM158
Electric Four (All A.C. -SG, D, RC, Trans) WM174
Brookman's Four (2SG, D, Trans) WM180
Transportable Four (SG, D, 2 RC) WM189
Super Q4 (SG, D, 2 Trans) WM193
Lodestone Four (HF, D, RC, Trans) WM194
Searcher's Four (SG, D, RC, Trans) WM200
Invitation Four (SG, D, RC, Trans) WM211
Regional Band-pass Four (SG, D, RC, Trans) WM216
Five-Point Four (SG, D, RC, Trans) WM221
Regional A.C. 4 (SG, D, RC, Trans) WM221

FIVE-VALVE SETS (1s. 6d. each)

James Quality Five (2SG, D, RC, Trans) AW227
All-wave Lodestone Five (HF, D, RC, Push-pull) WM146
1930 Five (2HF, D, RC, Trans) WM171
Dual-screen Five (2SG, D, RC, Trans) WM185
Radio-Record Five (SG, D, Trans-parallel) WM188
Overseas Five (3SG, D, Trans) WM191

AMPLIFIERS (1s. each)

"A.W." Gramophone Amplifier AW205
Two-valve Amplifier AW216
"Mag" Gramo Unit AW224
Simple Gramophone Amplifier AW257
Radio-Record Amplifier (DC Mains) WM183
Selecto Amplifier (HF, Unit) WM210

MISCELLANEOUS (1s. each)

Short-wave Adaptor (1 v.) AW183
Simplest H.T. Unit AW197
By-pass Unit (Wavetrap) with copy "A.W." AW218
"Twin" Brookman's By-pass (6d.) AW222
James H. T. and L.T. Charging Unit AW232
Simplest H.T. Eliminator for D.C. Mains AW234
Simplest H.T. Eliminator for A.C. Mains AW240
Choke Output Unit AW246
Simple Tester Unit (6d.) AW248
"A.W." Improved Linen-diaphragm Speaker AW254
Handy L.T. and G.B. Unit for A.C. Mains AW255
Ohmic-coupled DX Unit WM189
Brookman's "Wipe-outs" WM192
Short-wave adaptor for Overseas Five WM202
Staminator Unit for A.C. Mains WM204
Universal Push-pull Amplifier WM207
Outspan Short-wave Adaptor WM214
"W.M." Standard A.C. Unit WM215
"W.M." Standard D.C. Unit WM219 1/-
Falcon A.C. Unit WM219 1/-

PORTABLE SETS

Continental Portable (SG, D, Trans) AW241 1/-
Pedlar Portable Two (D, Trans) WM195 1/-
Pedlar Portable Three (D, 2 Trans) WM197 1/-
James Portable SG3 (SG, D, Trans) WM203 1/-
Foursome Portable (SG, D, 2 Trans) WM206 1/6

Copies of the "Wireless Magazine" and of "Amateur Wireless" containing descriptions of any of these sets can be obtained at 1s. 3d. and 4d. respectively, post free. Index letters "A.W." refer to "Amateur Wireless" sets and "W.M." to "Wireless Magazine."

AMATEUR WIRELESS 58-61 FETTER LANE LONDON, E.C.4.

"UNIVERSAL" SUPER 8/6

Post Free.

MICROPHONE

IN USE IN ALL PARTS OF THE WORLD (as far afield as Russia and China!) for any or all of the following purposes—

DETECTAPHONE, DEAF AID, PULPIT MICROPHONE, LOUD-SPEAKING TELEPHONE, ANNOUNCEMENTS THROUGH LOUD-SPEAKER (with or without Valve Amplifier), WIRELESS TRANSMISSION (by leading Amateurs on Short Waves), Electric SOUND DETECTION, FOG COMPASS for ships at sea, BABY ALARM or INVALID CALL from Bedroom through Distant Loud-speaker (with or WITHOUT Valve Amplifier, or through Loud-speaker of Wireless Set if desired), CRYSTAL AMPLIFIER, MECHANICAL EFFECTS by Sound, such as opening Garage Door by sounding hooter of Car, switching on lights by blowing a whistle, etc., EXPERIMENTS.

A NEW INSTRUMENT, BRITISH MADE THROUGHOUT, and a vast improvement over all other types; will take up whispered words from a distance of several yards, also strongly amplify and transmit speech and music over a distance through Loud-speaker or Headphones.

NO OTHER MICROPHONE OF EQUAL SENSITIVENESS KNOWN

Each Instrument finely black-enamelled and fitted with a 2-ft. silk connecting cord.

SPECIAL MICROPHONE TRANSFORMER for connecting Super-Microphone to Radio Headphones, Loud-speaker, Valve Amplifier, or Wireless Set. 6/-

SMALL 10 OHMS EARPIECE for use with Super-Microphone as a HIGHLY EFFICIENT DEAF AID, or Detectaphone, etc.; thin 3-ft. Silk connecting cord fitted. Ear-piece Fine Black enamelled. 6/-

Full Directions for use of Super-Microphone and Diagrams of connections free.

Illustrated Lists of MODERN PUBLIC ADDRESS and ANNOUNCERS' MICROPHONES free.

FREDK. ADOLPH, Actual Maker,
27 FITZROY STREET, LONDON, W.1.
Phone: Museum 8329.

EDDYSTONE SHORT-WAVE APPARATUS

PLUG-IN S.W. COILS

EDDYSTONE S.W. coils have all the desirable features necessary to ensure efficient S.W. results. Lowest H.F. losses and self capacity. Wound with 16 g. enamel copper wire almost entirely air spaced, they are yet unbelievably mechanically strong.


No. 3	8-25 metres	-	2/6
No. 4	12-40 "	-	2/9
No. 6	14-60 "	-	3/-
No. 9	25-90 "	-	3/3
No. 12	40-120 "	-	3/6
No. 15	60-150 "	-	4/-



SHORT WAVE H.F. CHOKE

This special EDDYSTONE S.W. choke is designed for use in any position in a S.W. receiver for wavelengths between 10-80 metres. Wound on paxolin former with stand for vertical or horizontal mounting.

Price 2/6

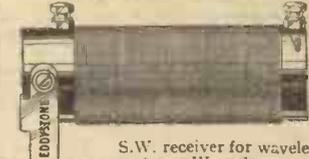

LOW LOSS VALVE HOLDER

A valve holder of low loss construction with one piece air spaced sockets. Bakelite insulating ring. Can be mounted direct on metal baseboard.

Price 1/6

Send for S.W. lists No. 30.

STRATTON & CO., LTD. London Service Depot: C. WEBB, LTD., BIRMINGHAM. 164 Charing Cross Rd., W.C.2.

THREE CONNECTIONS IN ONE

THE 'EEXE' TREBLE DUTY TERMINAL



40 DIFFERENT INDICATING TOPS
6 COLOURS

WRITE FOR LIST J100.

J.J. EASTICK & SONS 110 BUNMILL ROW LONDON, E.C.1

COMPONENTS

.0005 S.L.F., 3/-; S.M. Dials, 2/-; Ormond, 2/6. 1- and 2-mfd. Condensers, 2/- each. 18 by 7 Aluminium Panels, 2 4. Screens, 1/6. 16 by 7 Ebonite Panels, 3/6.

Ask for our Panel List. Prices right.

Dual-range Coils, 6/-; Set 4 S.W. D.X. Coils, 7/6. Diff. Condensers, 2/6, 3/6, 4/-; Reaction, 2/6. Cossor Coils, 7/-, 9/- set. All-wave Tuners, 7/6. Cone Units, 4/6. Exact Tuners, 14/-; Valve Holders, 9d., 1/-; Fretted Fronts, 18 in. square, 3/-; Cones, 8-in., 1/6. Transformers, 5/6. Coloured Wire, 10 ft. 5d. B/B Coil Mounts, 7d. 9-volt Grid Bias, 1/-.

QUOTATIONS BY RETURN. WRITE FOR LISTS.

(Kits, all makes, in stock).

F. SANDERS

79 High Street, Ilfracombe



YOU CAN BUILD A £40 GRAMOPHONE WITH OUR SCALE DRAWINGS FOR 40/-

Book of instructions 3d. Catalogue of Motors, Tonearms, Soundboxes, latest internal amplifiers Gramophones and Cabinets Free. Cash or Terms.

W. BURT, 185 High St., Deptford.

'Build Your Own Batteries'—'The Cells that Satisfy'

We supply complete Kits for making Super Capacity, Grid Bias, Block Type, Pocket Lamp, Wet Type and Bell, Batteries. You can build a 60 volt Wet Battery for 15/-. We supply a Standard size 120 Dry Battery for 12/-. All Batteries guaranteed.

Send 3d. for The Leyton Booklet, "Build Your Own Batteries," to—The Leyton Battery Co., 305 Church Rd., Leyton, E. 10

BUILD YOUR OWN HIGH-TENSION ELIMINATOR FOR 37/-

all components required, (including valve) supplied for 37/-. Post Free. Output 16 milliamperes, 120 volts.

Stamp for Diagram and Lists.

FEL-ECTRIC RADIO, 56 Garden St., Sheffield.

MAKE OR BUY A GRAMOPHONE AT

a quarter shop price. Or buy Cabinets for Wireless. British double spring motor, 12 in. direct turntable, swan arm, metal sound-box, amplifier, needle cups, for £1 18 6 p.p., and build your own Cabinet. Portable Gramophones from 15/6, postage 1/6. Motors from 7 6. Lists free. 64 pp. 1931 Catalogue No. 220 with Reduced Prices, Drawing and How to Make Gramos 3d. Established 26 years.

Regent Fittings Co., A.W., 120 Old St., London, E.C.1

For YOUR SET or RADIO-GRAM

Radio Furniture de luxe! Gives style to the home. Nothing cheap or shoddy. Advantages also of PIANO-TONE baffle enables BETTER REPRODUCTION (3,000 clients and Leading Experts.) DIRECT from makers, APPROVAL 7 days FREE. 75/- to £15, Cash or EASY PAYMENTS. Photograph FREE. PICKETTS, Radio Furniture Works (A.M.) Albion Road, Beckenham, Kent.

"RADIOGRAMS"

(Continued from page 854)

They are going to try to find the answer to the question, "What's Wrong with the Theatre?" and their remarks will be heard by listeners to the National programme.

"The Foursome's" vaudeville programme on the National on December 1, to be repeated regionally on December 5, will open with the "Two Pairs" (Claude Hulbert and Enid Trevor, with Paul England and Pat Paterson), followed by Harold Waldon in stories and songs, Halina Bruczowna, Gillic Potter (comedian), and Elizabeth Pollock.

Speeches following the luncheon given by the English Speaking Union in honour of American Thanksgiving Day will be relayed from the Park Lane Hotel to London Regional on November 27. Listeners will hear Lord Burnham and Sir John and Lady Simon.

A concert by the Afan Glee Society will be relayed to Cardiff from Port Talbot on December 11. The vocalists will be May Huxley and Dennis Noble.

Cardiff listeners heard the City of Bristol Police Band during Bristol Radio Week, and this band returns to the studio on December 13. Their performance will be followed by a Christmas concert by the University of Bristol Madrigal Singers.

The fifth talk in the series "Wales To-day and To-morrow" will be given from Cardiff by Professor J. Saunders Lewis on "The National Standpoint" on December 6.

"Amateur Wireless and Radiovision."

Price Threepence. Published on Thursdays and bearing the date of Saturday immediately following. Post free to any part of the world: 3 months, 4s. 6d.; 6 months, 8s. 9d.; 12 months, 17s. 6d. Postal Orders, Post Office Orders, or Cheques should be made payable to "Bernard Jones Publications, Ltd."

General Correspondence is to be brief and written on one side of the paper only. All sketches and drawings to be on separate sheets. Contributions are always welcome, will be promptly considered, and if used will be paid for. Queries should be addressed to the Editor, and the conditions printed at the head of "Our Information Bureau" should be closely observed. Communications should be addressed, according to their nature, to The Editor, The Advertisement Manager, or The Publisher, "Amateur Wireless," 58-61 Fetter Lane, London, E.C.4.

BANKRUPT BARGAINS.—List free. Transformers. Sutra, 3/-; Telsen Ace, 6/6. Radiogram, 9/6. Selector, 4/3. Condensers .0005 S.L.F. 2/6. Polar .0001, 2/-; Wave-master Differential, 2/9. Neutralising, 1 8, etc. Dual coils, 5/-; Bullphone ditto, 8/6. 6 pin coils, 2/3. Bases, 1/-; 2 pin coils, from 1/-; Speaker units, from 6/6. Kits, from 12/6. Three valve kits, 35/-; two valve, 24/-; Portables, new 5 valve guaranteed, £6 10/-; Three valve A.C. mains sets complete valves, £3. Eliminators. Bullphone D.C. 22/6. A.C. with Westinghouse rectifier 20 m/a £2. If you are building a set get my price, you will be surprised. Everything wireless and all goods new and of good quality. No Rubbish. Carriage extra or C.O.D.—Butlin, 143b Preston Road, Brighton.

SALE. Pair Blowave coils, two Ormond .0005 condensers, two Brownie dials, one Polar reaction condenser, all new, 35/-; Hooper, 48 Clive Street, Cardiff.

WE WILL ACCEPT YOUR SURPLUS APPARATUS (making you a high allowance) in part payment for any new apparatus: your inquiry will be dealt with promptly.—Bostock & Stonnill, 1 Westbourne Terrace, S.E.23.

HOME CINEMATOGRAPHS, latest models, electric lighting complete. Good optical effects, from 8/6 each. Illustrated list free.—Mechob Supply Co., (D. 16)-62 Oxford Street, London.

PREPAID ADVERTISEMENTS

Advertisements under this head are charged THREEPENCE PER WORD, minimum charge THREE SHILLINGS. DEPOSIT SYSTEM

As the Publishers cannot accept responsibility for the bona fides of advertisers in this publication, they have introduced a system of deposit which it is recommended should be adopted by readers when dealing with persons with whom they are unacquainted. It is here explained.

Intending purchasers should forward to the Publishers the amount of the purchase money of the article advertised. This will be acknowledged to both the Depositor and the Vendor, whose names and addresses must necessarily be given. The deposit is retained until advice is received of the completion of the purchase, or of the article having been returned to and accepted by the Vendor. In addition to the amount of the Deposit, a Fee of 6d. for sums of £1 and under, and 1s. for amounts in excess of £1, to cover postage, etc., must be remitted at the same time. In cases of persons not resident within the United Kingdom double fees are charged.

The amount of the Deposit and Fee must be remitted by Postal Order or Registered Letter (Cheques cannot be accepted), addressed to

"AMATEUR WIRELESS" ADVERTISEMENT DEPARTMENT 58/61 FETTER LANE, LONDON, E.C.4

DECORATE YOUR LOUD-SPEAKER YOURSELF.

Transfers giving painted effects on Fabric, Wood, Metal, etc. Sample and catalogue 1/-. A.W., Axon Ltd., Jersey, England.

ALEXANDER BLACK, Wireless Consultant, will call and cure your set. (London and Home Counties). Radio Association appointed representative. Components and McMichael Portables on hire.—55 Ebury Street, S.W.1. Sloane 1655.

ENGINEERS.—IMPORTANT NOTICE.—Results now to hand show that 93 per cent. of our candidates pass their Exams. at the first attempt, a remarkable record, unapproached by any other organisation and showing why we alone guarantee "NO PASS—NO FEE." If 93 out of every 100 ordinary men can succeed, why should you remain in the ranks? Now is the time to "get busy" and investigate. Our handbook, "ENGINEERING OPPORTUNITIES," explains the most simple and successful home-study methods of passing B.Sc., A.M.I.Mech.E., A.M.I.C.E., A.M.L.E.E., A.M.I.A.E., G.P.O., C. & G., Matric., etc., Exams. This book outlines Courses in all branches of Civil, Mech., Elec., Motor and Wireless Engineering, shows the unique advantages of our Appointments Dept. and includes a brilliant foreword by Prof. A. M. LOW, in which he shows clearly the chances you are missing. Send for FREE HANDBOOK now (state branch, post or Exam).—BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, 109 Shakespeare House, 29-31 Oxford Street, London.

WIRELESS BARGAINS.—New 5-valve Portable Sets, Radio-Grams, etc., for disposal by Liquidator of well-known Wireless Company. Sets ready for immediate use and may be bought singly.—P. G. Lambirth, Chartered Accountant, 4 Broad Street Place, E.C.2. London Wall 7120.

WET BATTERY REPLACEMENTS.—New Process Sacs, approximately 20,000 m.a., 2/6 per dozen. Particulars free.—Scottish Batteries (A.W.), Branside, Uphall Station.

PAY AS YOU LISTEN.—Receivers. Kits. everything you want, cash on delivery or credit. My terms are lowest.—R. Hillier, 10 Brymver Road, S.E.5.

"VERT" WIRING CLIP.—No soldering. No bending wires round terminals. Takes any number of wires to a terminal, any gauge. Tested and approved "Amateur Wireless." 4 gross (sufficient for 3 Valve set) 2/-. Trade Inquiries invited.—W. Green & Son (A) Redclyffe, Horley, Surrey.

TRICKLE CHARGERS, A.C. mains, for 2- and 4-volt accumulators, no upkeep; 18/6 carriage paid.—A. Benoit, 4 Manor Gardens, Gunnersbury Avenue, London, W.3.

HANDSOME SPEAKERS, 18 x 18 x 7, Polished Oak balanced armature, floating cone, fret, 23/6.—Parke 79c Turnpike Lane, N.8.

BANKRUPT STOCK BARGAINS, new and genuine, all satisfaction or cash refunded, any C.O.D. or A.W. deposit system. Telsen Ace transformers 3-1, 5/6. Watmel H.F. chokes, 1/6. Cossor transformers, 10/6. Mullard Permacore, 10/6. Ferranti AF3C, 16/6. Lotus reaction condenser .00034, 3/6. Wearite 4-pole rotary switches, 2/9. Graham Farish resistances, 250,000, 500,000 and 5,000 ohms, 1/3 each. Precision valve holders, large, 7d. each. Ediswan 4-meg. leaks, 8d. each. Ebonite leak holders, 3d. Ediswan 2-volt valves all new, H.F., L.F., 5/6 each; RCC, 4/6; Power, 6/6. Phillips 506 H.T. rectifier valves, 12/6. Osram U8, 12/6. L55 and Mullard DFA7, 16/6. all new. Note callers any time. Bus stop outside door, alight Fitzalan Street.—G. A. Ryall, 182 Kennington Road, London, S.E.11.

AGENTS WANTED to sell Wireless Goods, all makes in sets, components and accessories. Cash or easy terms. Liberal commission.—New Auto Supply Co., 241 Park Road, Aston, Birmingham.

RADIO SATISFACTION.—Osram, Mullard Kits. Cossor, Varley, McMichael Sets. Speakers. Kits assembled, no extra. Portables and Transportables. Delivery free. London area same day C.O.D. Send card for quotation. Batteries, Valves, Pick-ups, etc., at right prices.—Dudley, 37 Hartley Street, London, E.2.


FOR RESULTS.—Bronze-mesh Micro Earth Mat, also Brandes' Phones, Keystone Neutralising Condenser, Lissen Choke, Connecticut Switch, Sundries. Brand New. 18/6 lot, or offer.—Jeal, Holland, Oxted.

Amateur Wireless **COUPON**
Available until Saturday
DECEMBER 6, 1930

*Dubiliers
make a
mica condenser
for every job!*

TYPE 620

For use in radio circuits where comparatively small capacity is required. Arranged for vertical mounting.
PRICES 1/8 to 3/-

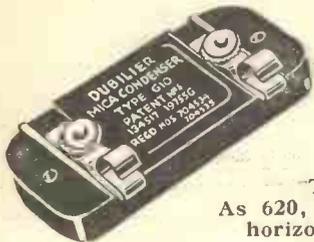

TYPE 610
As 620, but arranged for horizontal mounting.
PRICES 1/8 to 3/-



TYPE B775
Primarily designed for resistance coupling, but suitable for use in other circuits where a comparatively large capacity, capable of withstanding several hundreds of volts, is required.
PRICES 3/- to 18/-

Use Dubilier Condensers and be certain of satisfaction.

DUBILIER CONDENSERS

DUBILIER CONDENSER CO. (1925) Ltd.,
DUÇON WORKS, VICTORIA ROAD, N. ACTON, W.3.

**VOTED THE FINEST
ALL-MAINS UNITS
AT OLYMPIA**

BY winning the first place in the "Wireless World" Competition, the already famous "ATLAS" ALL - MAINS Units are voted the finest value obtainable at any price. Two variable tappings, unrivalled power, small size, and the Westinghouse Metal Rectifier, are among the outstanding features that lift model A.C. 188 far above the level of all competitors.

Ask your dealer for Folder 55, or write direct to the makers.


H. CLARKE & CO. (M/CR), LTD.
Old Trafford :: Manchester

MODERNISE YOUR SET WITH

CLARKE'S
"ATLAS"
MODEL A.C. 188



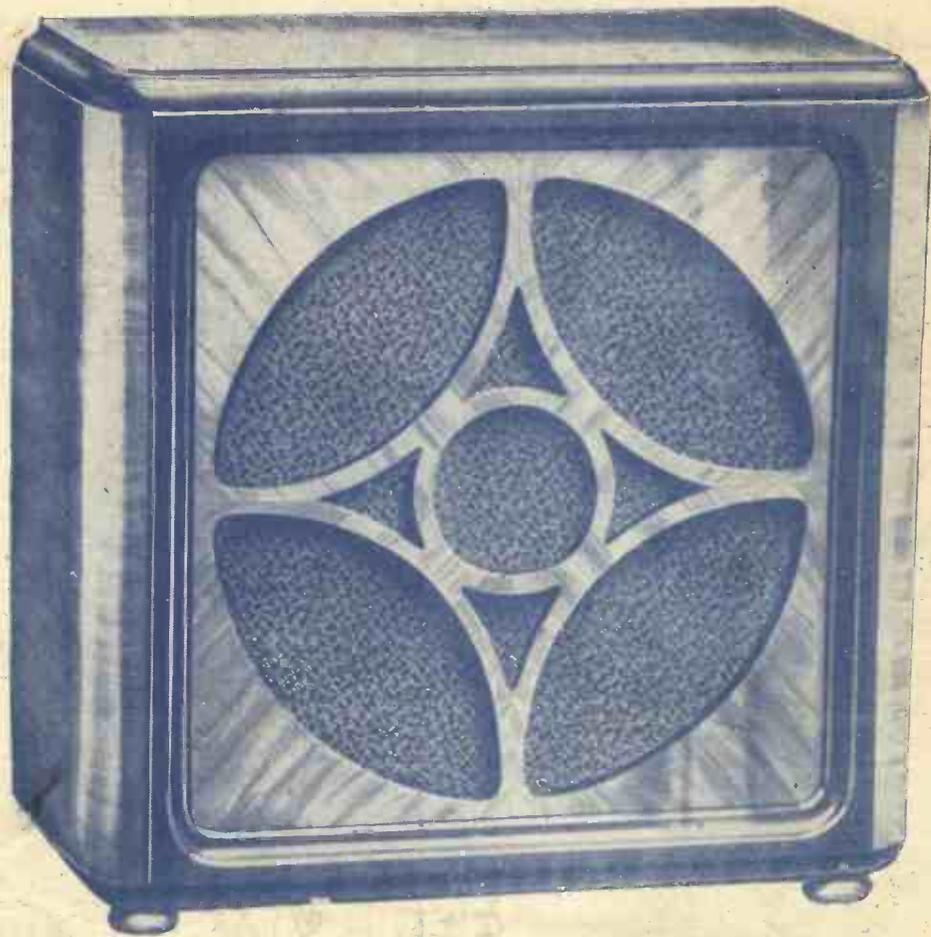Don't Forget to Say That You Saw it in "A.W."



BLUE SPOT 29R



Blue Spot Speakers are in a class all by themselves—Blue Spot Speakers are the best in the world. 29R is the best of the Blue Spot Speakers . . . Put two and two together, what follows? Yes, quite right, 29R is the best in the world.

£6-6-0

This price does not apply to the Irish Free State.

• THE BRITISH BLUE SPOT COMPANY LTD. •

BLUE SPOT HOUSE, 94/96 ROSOMAN STREET, ROSEBERY AVENUE, LONDON, E.C.1

Phone: CLERKENWELL 3570.

Grams: "BLUOSPOT; SMITH, LONDON."

Distributors for Northern England, Scotland and North Wales: H. C. RAWSON (Sheffield and London), LTD., 100 London Road, Sheffield; 22 St. Mary's Parsonage, Manchester; 183 George Street, Glasgow.