

PRACTICAL ELECTRONICS

MAY 1968

PRICE 2/6

ELECTRONIC PERCUSSION EFFECTS



Also

IN THIS ISSUE.....

**INTRUDER ALARM
FOR SMALL CRAFT**

TRANSISTOR CURVE TRACER


ADCOLA

PRODUCTS LIMITED
(Regd Trade Mark)

SOLDERING EQUIPMENT

for the

DISCRIMINATING
ENTHUSIAST

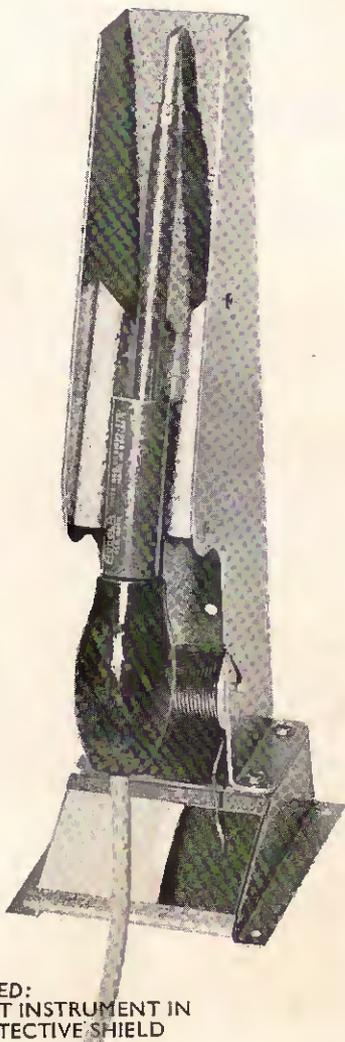

ILLUSTRATED:
L64 $\frac{3}{16}$ " BIT INSTRUMENT IN
L700 PROTECTIVE SHIELD

APPLY DIRECT TO:
SALES & SERVICE DEPT.
ADCOLA PRODUCTS LTD.
ADCOLA HOUSE
GAUDEN ROAD
LONDON, S.W.4
TELEPHONE 01-622 0291

THIS IS WHAT NORMAN EISENBERG WROTE ABOUT BOOKS BY G. A. BRIGGS IN HIGH FIDELITY MAGAZINE

U.S.A. JANUARY 1968

Is there any reason why audio books can't be written in high style? G. A. Briggs has been doing it ever since High Fidelity first emerged from the exclusive domain of engineers and began to be cultivated by the cultivated. Consider his temerity in opening a chapter on distortion in his classic *Sound Reproduction* with a quotation from Milton: "... dire was the noise of conflict". Or recall his wit in replying to a letter from a man who asked why "the body missing" from the sound when he put a back on his home-made speaker enclosure, and why the speaker sounded better when he took the back off again. Briggs wrote "... when you leave off the back ... you obtain ... reflection from the wall ... use the system which sounds best, even if contrary to every textbook. In any case, as the body has disappeared, there would not be much point in screwing down the lid of the coffin."

Nobody else writes them with quite that flair.



The BRIGGS books listed below are still obtainable.

AERIAL HANDBOOK (second edition)

176 pages, 144 illustrations
Price (semi-stiff cover) 15/- (16/- post free)
(cloth bound) 22/6 (24/- post free)



CABINET HANDBOOK

112 pages, 90 illustrations
Price 7/6 (8/6 post free)



AUDIO BIOGRAPHIES

344 pages, 64 contributions from pioneers
and leaders in Audio. Cloth bound
Price 25/- (26/6 post free)



MUSICAL INSTRUMENTS AND AUDIO

240 pages, 212 illustrations. Cloth bound
Price 32/6 (34/- post free)



LOUDSPEAKERS

Fifth edition—336 pages, 230 illustrations,
Cloth bound
Price 25/- (26/6 post free)



A TO Z IN AUDIO

224 pages, 160 illustrations. Cloth bound
Price 15/6 (17/- post free)



MORE ABOUT LOUDSPEAKERS

136 pages, 112 illustrations
Price 8/6 (9/6 post free)



PIANOS, PIANISTS AND SONICS

190 pages, 102 illustrations. Cloth bound
Price 18/6 (20/- post free)



AUDIO AND ACOUSTICS

168 pages, 140 illustrations
Price 12/6 (13/6 post free)



ABOUT YOUR HEARING

132 pages, 112 illustrations
Price (semi-stiff cover) 15/6 (16/6 post free)
Cloth bound 22/6 (24/- post free)



Sold by Radio Dealers and Book Shops or in case of difficulty direct
from the Publishers

RANK WHARFEDALE LTD.
IDLE, BRADFORD, YORKS. Tel.: Bradford 612552

Build Your Own Heathkit Electronics

A kit for every interest — Home Workshop — Hi-Fi — Radio — Test — Amateur

Latest STEREO TAPE RECORDER, STR-1



Fully portable—own speakers
Kit £45. 18. 0

FOR THIS SPECIFICATION

$\frac{1}{2}$ track stereo or mono record and playback at $7\frac{1}{2}$, $3\frac{3}{4}$ and $1\frac{1}{2}$ ips. Sound-on-sound and sound-with-sound capabilities. Stereo record, stereo playback, mono record and playback

on either channel. 18 transistor circuit for cool, instant and dependable operation. Moving coil record level indicator. Digital counter with thumb-wheel zero reset. Stereo microphone and auxiliary inputs and controls, speaker/headphone and external amplifier outputs... front panel mounted for easy access. Push-button controls for operational modes. Built-in stereo power amplifier giving 4W rms per channel. Two high efficiency $8" \times 5"$ speakers. Operates on 230V a.c. supply.

Versatile recording facilities. So easy to build—so easy to use.

Latest STEREO AMPLIFIER, TSA-12

12 x 12 watts output
Kit £30. 10. 0 less cabinet



Cabinet £2. 5. 0 extra

FOR THIS SPECIFICATION

17 transistors, 6 diode circuit. ± 1 dB, 16 to 50,000c/s at 12W per channel into 8 ohms. Output suitable for 8 or 15 ohm loudspeakers. 3 stereo inputs for Gram, Radio and Aux. Modern low silhouette styling. Attractive aluminium, golden anodised front panel. Handsome assembled and finished walnut veneered cabinet available. Matches Heathkit models TFM-1 and AFM-2 transistor tuners.

Full range power... over extremely wide frequency range. Special transformerless output circuitry. Adequately heat-sinked power transistors for cool operation—long life, 6 position source switch.

High-performance CAR RADIO, CR-1



Superb long and medium wave entertainment wherever you drive. Complete your motoring pleasure with this compact outstanding unit.

8 Latest semiconductors (6 transistors, 2 diodes). For 12V positive or 12V negative earth systems. Powerful output (4W). Preassembled and aligned tuning unit. Push-button tone and wave change controls. Positive manual tuning. Easy circuit board assembly. Instant operation, no warm-up time. Tastefully styled to harmonise with any car colour scheme. High quality output stage will operate two loudspeakers if desired. Can be built for a total price.

Kit (less speaker) £12. 17. 0 incl. P.T.
 $6" \times 4"$ Loudspeaker £1. 4. 5 extra.

Latest Portable Stereo Record Player, SRP-1

Automatic playing of 16, 33, 45 and 78 rpm records. All transistor—cool instant operation. Dual LP/78 stylus. Plays mono or stereo records. Suitcase portability. Detachable speaker enclosure for best stereo effect. Two $8\text{in} \times 5\text{in}$ special loudspeakers. For 220-250V a.c. mains operation. Overall cabinet size $15\frac{1}{2} \times 3\frac{1}{2} \times 10\frac{1}{2}\text{in}$.



Compact, economical stereo and mono record playing for the whole family—plays anything from the Beatles to Bartok. All solid-state circuitry gives room filling volume.

Kit £27.15.0 incl. P.T.



SSU-1

A wide range of SPEAKER SYSTEMS

HI-FI SPEAKER SYSTEM. Model SSU-1. Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical horizontal models with legs, Kit £12. 12. 0 without legs, Kit £11. 17. 6 incl. P.T.

The BERKELEY SLIM-LINE SPEAKER SYSTEM, fully finished walnut veneered cabinet for faster construction. Special $12"$ bass unit and $4"$ mid/high frequency unit. Range 30-17,000c/s. Size $26" \times 17"$ only $7\frac{3}{4}"$ deep. Modern attractive styling. Excellent value.

Kit £19. 10. 0.

Berkeley

Transistor Portables

UXR-1, now available in Modern coloured cases or leather.

6 transistor, 1 diode circuit. $7 \times 4\text{in}$. speaker. LW and MW coverage. Case: brown leather, or colours navy blue, coral pink, lime green. Please state 2nd choice.

Kit £11. 19. 0. Colour

Kit £12. 18. 0. Leather

UXR-2, choice of black or brown real leather cases.

7 transistor, 3 diode circuit. Battery saving circuitry. LW and MW coverage. Pushbutton wave change. Slide ruf tuning.

Kit £14. 18. 0. leather



UXR-1



UXR-2
HEATHKIT

SEE HEATHKIT MODELS AT:
GLOUCESTER
Factory and Showroom, Bristol Road.

LONDON
233 Tottenham Court Road, W.1.

BIRMINGHAM
17-18 St. Martin's House, Bull Ring.

Demonstrations by arrangement.

Deferred terms available over £10 (U.K. only).

Prices quoted are Mail Order prices.

Send for
Latest
FREE
Catalogue

36 pages,
many
models
in Colour

Please address all enquiries to

DAYSTROM LTD., Dept. P.E.5, GLOUCESTER

Please send me FREE CATALOGUE

Full details of model(s).....

NAME

ADDRESS

GOODMANS HIGH FIDELITY MANUAL



A Guide to full listening enjoyment

The Manual is much more than a catalogue of Goodman's High Fidelity Loudspeakers—it contains informative articles, including advice on stereo, special beginners page, and full cabinet drawings. You'll find it interesting as well as informative.

The Perfect Combination MAXAMP 30

TRANSISTORISED STEREPHONIC HIGH FIDELITY AMPLIFIER 15 + 15 watts • Silicon solid state • Integrated pre-amplifier
Negligible distortion • £49.10.0.

STEREOMAX MATCHING AM/FM STEREPHONIC FM TUNER

Transistorised • Outstanding specification • Stereo de-coder (optional)
£60.0.0. + £11.18.3. P.T. inc. Surcharge.

Both MAXAMP 30 and STEREOMAX have polished wood cases (10½" x 5½" x 7½" deep) in Teak or Walnut to order.

Full specifications of the Maxamp 30 and Stereomax are given in the High Fidelity Manual—send the coupon for your FREE copy—or pay an early visit to your Goodman's dealer.

FREE

Please send Hi-Fi Manual together with name and address of my nearest Goodman's dealer.

Name

Address

P.E. 5

GOODMANS LOUDSPEAKERS LTD

AXIOM WORKS • WEMBLEY • MIDDLESEX. Tel: 01-902 1200

The '309' AUDIO TRANSDUCER

A new concept in sound reproduction



The '309' Audio Transducer represents a breakthrough in sound reproduction without the use of hard to place loudspeakers. It has been designed to reproduce sound by utilising the vibrant qualities of wooden, plastic, glass, metal and similar surfaces. It has an exceptionally good frequency response and provides excellent quality music and speech. A versatile unit, fully waterproof and suitable for many indoor and outdoor uses. Impedance 8-15 ohms. Power Handling 10 watts.

9 GNS. P. & P. 4/6


Complete with simple instructions

Available from most dealers or direct from the Sole U.K. Distributors

ELECTRO-APPARATUS (LONDON) LTD.
BENTFIELD END, STANSTED, ESSEX Tel: Stansted 3437

MARTIN IS HIGH-FIDELITY

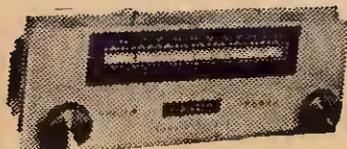PREFERRED FOR RELIABILITY, QUALITY, ADD-ON-ABILITY AND ECONOMY



F.M. TUNER



STEREO CONTROL ASSEMBLY

ONLY FROM MARTIN

MARTIN AUDIOKITS are available for Mono, and can be doubled up for stereo, or as complete stereo units. 3 ohm and 15 ohm systems are available. There is a special pre-amp for low output pick-ups and escutcheon panels to suit the arrangement you choose. The tuner is styled to match.

Start by sending for leaflets at once

MARTIN ELECTRONICS LTD.

UNITS INCLUDE:

- 5-stage input selector
- Pre-amp/tone controls
- 10 watt amp. (3 ohms)
- 10 watt amp. (15 ohms)
- Mains power supply
- F.M. Tuner

Trade enquiries invited

154/5 HIGH STREET, BRENTFORD
MIDDLESEX. 15Leworth 1161/2

so that your installation is always up to date. Most important of all is the power and quality which MARTIN Audiokits give you. Their sturdy construction assures compactness without sacrifice to quality or efficiency. They offer excellent value, are very easily installed and will give years of unflinching service. That is why people prefer MARTIN — it's simple to instal, good to listen to, and looks completely professional.

AMPLIFIER SYSTEMS • TUNERS • RECORDERS

MARTIN ELECTRONICS

154 High Street, Brentford, Middlesex
Please send Recordakit/F.M. Tuner/Audiokit
Hi-Fi Leaflets. (Strike out items not wanted)

Name

Address

P.E. 5/68

BUILD YOURSELF A QUALITY TRANSISTOR RADIO—FULL AFTER SALES SERVICE!

THE MAGNIFICENT ROAMER 7 MK IV

SEVEN WAVEBAND PORTABLE AND CAR RADIO WITH A SUPER SPECIFICATION

- 7 FULLY TUNABLE WAVE BANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band.
- Extra Medium waveband provides easier tuning of Radio Luxembourg, etc.
- Built in ferrite rod aerial for Medium and Long Waves.
- 5 Section 22 in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening.
- Socket for Car Aerial.
- Powerful push-pull output.
- 7 transistors and two diodes including Philco Micro-Alloy R.F. Transistors.
- Famous make 7×4 in. P.M. speaker.
- Air spaced ganged tuning condenser.
- Separate on/off switch, volume control, wave change switches and tuning control.
- Attractive case with hand and shoulder straps. Size 9×7×4 in. approx.
- First grade components.
- Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build with guaranteed results.

Total building costs
£5.19.6 P. & P. 6/6



Parts price list and easy build plans 3/- (FREE with parts).



TRANSONA FIVE

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE

Attractive case with rod speaker grille. Size 6½ × 4½ × 1½ in. Fully tunable. 7 stages—5 transistors and 2 diodes—ferrite rod aerial, tuning condenser, volume control, fine tone super dynamic 3in. speaker, all first grade components. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs
42/6 P. & P. 3/6




POCKET FIVE

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE

Attractive black and gold case. Size 5½ × 1½ × 3¼ in. Fully tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components, 7 stages—5 transistors and 2 diodes—super-sensitive ferrite rod aerial, fine tone 3in. moving coil speaker, etc. Easy build plans and parts price list. 1/6 (FREE with parts).

Total building costs
39/6 P. & P. 3/6

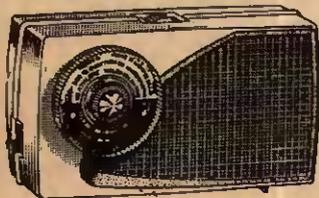

NEW MELODY MAKER SIX

3 WAVEBAND PORTABLE

8 stages—6 transistors and 2 diodes

Covers Medium and Long Waves and EXTRA M.W. BAND FOR EASIER TUNING OF LUXEMBOURG, etc. Top quality 3in. Loudspeaker for quality output. Two RF stages for extra boost. High "Q" 6in. Ferrite Rod Aerial. Approx. 350 milliwatts push-pull output. Handsome pocket size case with gilt fittings. Size 6½ × 3½ × 1½ in.

This amazing receiver may be built for only **69/6** P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with parts).



ROAMER SIX

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings, size 7½ × 5½ × 1½ in. World wide reception. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. All top grade components, 8 stages—6 transistors and 2 diodes including Philco Micro-Alloy R.F. Transistors, etc. (carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts).

Total building costs
79/6 P. & P. 3/6



SUPER SEVEN

THREE WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case size 7½ × 5½ × 1½ in. with gilt fittings. The ideal radio for home, car or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 3 R.F. stages, push-pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Price list 2/- (FREE with parts).

Total building costs
69/6 P. & P. 3/6

RADIO EXCHANGE Ltd

61a HIGH STREET, BEDFORD

Telephone: Bedford 52367

Callers side entrance Barratt's Shoe Shop. Open 9-5 p.m. Saturday 9-12.30 p.m.

A-Z

(MINUS X)

ALPHABETICALLY...

we can list the names

GEOGRAPHICALLY...

we can list the countries

All over the world students know that CREI HOME STUDY COURSES are supplying the answer to their need for advanced Technical Education in the field of Electronic Engineering Technology.

CREI PROGRAMMES ARE AVAILABLE IN:

- Electronic Engineering Technology
- Industrial Electronics for Automation
- Computer Systems Technology
- Nuclear Engineering
- Mathematics for Electronic Engineers
- Television Engineering
- Radar & Servo Engineering
- City & Guilds of London Institute: Subject 49 and Advanced Studies Subject No. 300

Write for free brochures to:

G.R.E.I. (London) (Dept. P.E.8)
WALPOLE HOUSE, 173/176 SLOANE ST., LONDON S.W.1
Telephone: Belgravia 8662

INTERNATIONAL DIVISION OF CAPITOL RADIO ENGINEERING INSTITUTE WASHINGTON D.C.

Please send me (for my information and entirely without obligation) full details of the educational programmes offered by your institute.....

Send details of the City & Guilds Programme.....

Name.....

Address.....

Electronics Experience.....

G.R.E.I. (LONDON) (DEPT. P.E.8), WALPOLE HOUSE, 173-176 SLOANE STREET, S.W.1

LIND-AIR COMPONENT BARGAINS

TRANSISTORS VALVES DIODES


WE HAVE A COMPLETE RANGE OF NEW AND OLD TYPES OF VALVES, TRANSISTORS AND DIODES. FULL LISTS AVAILABLE ON APPLICATION.

TRANSISTOR	VALVE	DIODE
OC3 6/-	V60201P 8/-	EZ80 6/6
OC16 20/-	V6030 10/-	EZ81 6/6
OC23 15/-	BFY60 8/6	FC034 6/6
OC28 12/6	BFY81 7/-	PCL85 11/6
OC22 10/-	BFY52 6/-	PCL82 10/6
OC24 17/6	BY212 10/-	PCL86 11/6
OC25 9/6	BY213 10/-	KT66 27/6
OC29 15/-	BCY33 7/6	KT68 27/6
OC35 12/6	BCY34 8/6	DY86 6/6
OC36 12/6	BCY39 12/6	EBCC3 9/6
OC41 5/-	BCY38 9/6	DK96 9/6
OC42 5/-	BCY12 7/6	DAF96 7/6
OC44 5/-	AC107 14/6	DL86 8/6
OC45 2/6	AC127 9/-	DF96 8/-
OC66 19/6	ACY17 8/6	FY81 7/6
OC70 4/-	ACY10 6/6	PL81 9/6
OC71 4/-	ACY20 5/6	PY33 10/6
OC72 5/-	ACY22 4/6	PL36 15/6
OC73 6/6	AF102 13/-	
OC76 6/-	AF114 7/-	
OC76 5/-	AF115 6/6	OAS 4/6
OC77 7/-	AF116 7/-	OA3 3/6
OC78 5/-	AF117 5/-	OA71 3/6
OC78D 5/-	AF118 17/6	OA31 2/6
OC83 6/-	AF124 10/-	OA95 9/6
OC81D 5/-	AF125 10/-	OA200 3/3
OC82 6/-	AF126 10/-	OA202 4/3
OC123 11/6	AF127 9/6	OA203 4/6
OC139 3/-	AF139 10/-	OA120 7/6
OC140 10/-	AF185 17/6	OA32 4/6
OC170 6/-	AF211 17/-	OA19 3/-
OC171 7/-	AF212 12/6	OA47 3/-
OC209 7/6	ASX26 6/6	OA70 2/-
OC201 12/6	MAT100 7/6	OA79 2/6
OC202 13/6	MAT101 8/6	IN31 2/-
OC203 10/6	MAT100 7/6	IN33 7/-
OC204 15/-	MAT131 8/6	IN254 4/-
OC205 15/-		IN256 6/6
OC206 19/6		IN537 6/6
OC271 12/6		IN647 5/-
ST721 15/-	EL84 9/6	IN2373 5/6
SY23 10/-	EF66 9/6	IN2374 15/-
ST140 4/-	EY86 9/6	IN2370 25/-
ST141 6/-	EY86 9/6	IN58 3/6
V62R 6/-	DY87 9/6	INU99 3/6
V64R 6/6	EOC83 8/6	GEX44 2/6
V68R 7/-	EOC81 5/6	GEX54 2/-
V106A 6/-	EAC360	
V1820P 10/-	UL84 8/6	PGT Power Mounting Kits 7/3
V1580P 10/-	UF41 10/6	
V13020P 8/-	UY41 8/6	


P.F. and insurance 2/-

MOTOR BARGAINS

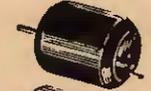Ideal for model makers, record decks, etc.




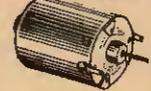6.3 d.c. Motor. 10,900 r.p.m. at 230mA. 1 1/2 in x 1 in dia. Shaft 1/8 in long x 3/64 in dia. 9/6. P. & P. 2/6.




9V d.c. Gram deck replacement motor. 2 in x 1 1/2 in dia. Shaft 1/8 in long x 3/32 in. 17/6. P. & P. 2/-.

1/8 H.P. MAINS MOTOR

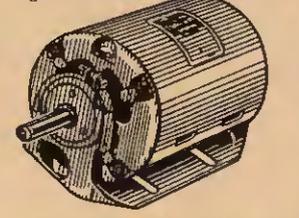

Made by Crompton Parkinson. Single phase 1/8 h.p. Motor. 230/250V; 50 cycles, 1-3A, 1,425 r.p.m. Continuous rating. Spindle 1 1/2 in x 1/2 in dia. Overall size less spindle approx. 8 x 6 in. Perfect condition. A bargain for the workbench. ONLY 79/6. Carriage 20/- (1/8 h.p. Motor also available 99/6, Carriage 20/-).


SELECTOR DRIVE

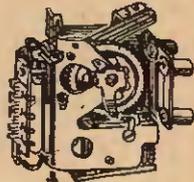

Numerous applications. Electro magnet and brass tooth wheel. A switch wiper and contacts are coupled to this

and arranged to be on for 10 pulses and off for 15. An Auxiliary contact is normally on but off 1 in every 25. Complete with suppressor, resistors, plus series contact for continuous operation. Ideal window displays, switching lamps, models, etc. 12V or 24V d.c. Brand new and boxed 12/6. P. & P. 2/6.

SYNCHRONOUS CLOCK MOTORS

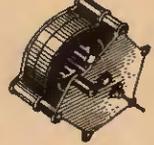


Geared for 40 revolutions per hour. 230V 50 cycle. With mounting flanges. Size approx. 1 1/2 in. deep x 2 1/2 in. ONLY 22/6. P. & P. 2/6.

DELAY ACTION TIME SWITCH



Made by Smiths. A.C. operation 200/250V. Double pole, will give time delays from 0-10 minutes. Size 2 1/2 in. dia. x 2 1/2 in. long inc. 1/2 in. x 3/16 in. dia. spindle. BARGAIN PRICE 17/6. P. & P. 2/6.

UNREPEATABLE BARGAINS!

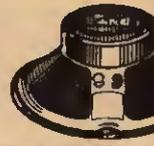

FANE 122/17 12in 25 WATT HEAVY DUTY HI - FI LOUD SPEAKERS. With high efficiency Anti-strope

Ferrite magnet. 17,000 gauss. Imp. 3-5 ohms. Brand new and guaranteed. List Price 212. LIND AIR PRICE 23.19.6. P. & P. 7/6.

E.M.I. COMBINATION LOUD SPEAKERS

13 1/2 x 8 in. Elliptical with 3 1/2 in dia. Tweeter. Imp. 8 ohms. Power handling 10 watts. Brand new and guaranteed. List price 23.5.0. LIND AIR PRICE 99/6. P. & P. 7/6. (Also available without tweeter 59/6 P. & P. 7/6).



Fane 302 3in TWEETERS. Imp. 3-5 ohms. 17,000 gauss. 12 watt. Brand New and guaranteed. List Price 23.15.0. LIND-AIR PRICE 88/6. P. & P. 3/6.

SEE LIND-AIR OPPOSITE

LIND-AIR (OPTRONICS) LTD.

London's
Leading
Component
shops

ALL POST
ORDERS TO
Dept. P.E. 568
25 Tottenham
Court Road
London, W.1

25 & 53 TOTTENHAM COURT ROAD, LONDON, W.1. Tel. 01-580 4534/7679
Open 9-8 p.m. Monday to Saturday inclusive. Open Thursday until 7 p.m.


3 1/2 WATT AMPLIFIER

An ideal basis for building your own portable record player. Just add speaker and turntable, and you will have an above-average model for a mere fraction of the cost. 2-3 watt printed circuit with control panel on flying lead. ON/OFF, TONE CONTROL AND VOLUME, colourful eschechon. Brimar valves: E280, ECL82 and composite installation booklet. Price **£4.5.0** P. & P. 3/6.



MAGNAVOX-COLLARO 3 1/2 TAPE DECKS

The very latest 3-speed model—11, 3 1/2, 7 1/2 i.p.s. available with either 2 track or 4 track head. Features include: Pause control; digital counter; fast forward and rewind; new 4-pole, fully screened induction motor; interlocking keys. Size of top plate 13 1/2 x 11 x 5 1/2 in deep below unit plate. For 200/250V a.c. mains, 50 c/s operation. New, unused and fully guaranteed. 2 track model **£10.10.0** 4 track model **£13.19.6** Carriage and Packing 12/6 extra.

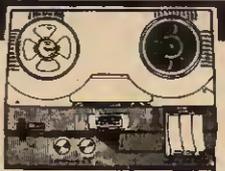

GARRARD DECKS

3000 with Sonotone 9TAHC Stereo Cartridge ..	£8.19.6
3000 with Sonotone 9TAHC Diamond Stereo Cartridge ..	£9.19.6
AT50 MKII less cartridge ..	£12.19.6
AT50 MKII with Decca Deram Stereo Cartridge ..	£17.14.0
SP. 25 MKII less cartridge ..	£10.19.6
SP. 25 MKII with Decca Deram Stereo Cartridge ..	£15.14.0
AP.75 less cartridge ..	£22.11.6
LAB.30 MKII less cartridge ..	£24.19.6
Mono Cartridge 17/6 extra.	
Stereo Cartridge 22/6 extra.	




TEAK FINISH PLINTHS with perspex cover 6 1/2 gns. (for LAB30 8 1/2 gns.). P. & P. 12/6 Agents for Thorens, Dual, Goldring, etc.

TRANSISTOR F.M. TUNER

SAVE **£2.2.0**

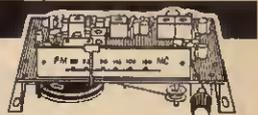6 Transistor FM tuner. Frequency range 88-108Mc/s. Size 6 x 4 x 2 1/2 in. Ready built for use with most amplifiers, 9V battery operation. Complete with instructions. LIST PRICE 9 gns. LIND AIR PRICE **7 gns.** P. & P. 4/-.



Multiplex adaptor for Stereo Radio Reception **£5.19.6** extra.

MARTIN TAPE AMPLIFIERS

FOR USE WITH ABOVE DECKS


2 track model **£14.10.6**; 4 track model **£15.19.6**. Carriage and Packing 12/6.

MULTIMETERS



MODEL TTC.1001. 20,000 O.P.V. with overload protection; d.c. volts, 4, 25, 125, 500, 2,500V; a.c. volts, 10, 50, 250, 100V; d.c. mA 250mA to 50A. With prods and carrying case **ONLY 85/-** P. & P. 3/6.

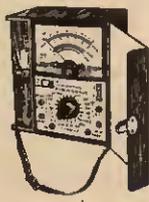MODEL TTC.1020. 50,000 O.P.V.; d.c. volts 0-3, 12, 60, 120, 300, 600, 1,200V; a.c. volts, 6, 30, 120, 600, 1,200V; d.c. mA 0-0.3-300. With prods and carrying case **ONLY £11.19.6** P. & P. 5/-.



9 in 1 ELECTRONIC KIT



Build nine different projects from one basic kit—simple instructions, no technical knowledge required for you to build a Police Siren, Metronome, Morse Code amplifier, Electronic Massager, W/T Transmitter, Radio, Telephone, One-transistor Radio Two-transistor Radio, Electronic Music Kit. Completely safe-operated on 9V PP3 battery. Hours of fun for boys and dads of all ages. Complete with all parts and simple step by step instructions. **ONLY 69/6** P. & P. 5/-.

AERIALS TV UHF VHF STEREO

Ventana Table Top V Aerial BBC/ITV, 26/6.
Crema Room Aerial Band I/II/III. Cream or Black, 25/6.
Yeomaster Table Top VHF/UHF Tunable Aerial. Chrome or Grey, 76/6.
YAGI all Channel Table Top Aerial BBC/ITV/VHF, 65/-.
HLS2 Loft Aerial HILO V + 5 for vertical Band III/II. With mounting arm and bracket, 55/-.
New Major 10 element BBC2 Aerial for loft or outdoor fixing. With roller bracket for up to 2in dia. mast, 45/9.
EL Hunter 13 element BBC2 Aerial as above, 57/-.
EL Explorer 18 element BBC2 Aerial as above, 69/-.
Loft Six. 6 element BBC2 Aerial for loft or outdoor fixing. With arm and bracket, 37/6.
J-Beam 4 element outdoor Band II VHF/EM Stereo Aerial. With mast, 67/-.
Please add 4/- postage.

STEREO HEADPHONES

STEREO HEADPHONES

Enjoy Stereo Sound as you have never heard it before. MODEL TTC. G111 as illustrated—soft padded ear-phones. Adjustable headband. Impedance 8 ohms per phone. Frequency range 25-15,000c/s. With 5ft lead. Price 69/6. P. & P. 4/6. Other similar types available. AKAI AS28S, 8 ohms, **£6.5.0**; CORAL E102, 16 ohms, **£5.19.6**; EAGLE SE1, 16 ohms, **79/6**. T.T.C. StereoSCOPE, 8 ohms, 49/6. P. & P. 4/6 each.



BARGAIN OFFER! FANTAVOX CASSETTE TAPE PLAYER



Specially designed to replay the well known and popular Musicassettes—pre-recorded tape cassette offering a wide choice of all types of music from pop to classical. Up to 40 minutes of quality reproduction through built-in speaker. Simple on/off and volume controls. Fully transistorised operating on six penlight batteries. Modern compact styling with earpiece socket and wrist strap. Size 6 1/2 x 4 1/2 x 2in.

LIND AIR PRICE, **£9.19.6**. Carr. Pkg. and Ins. 6/-.

COMPLETE HI-FI STEREO SYSTEM

ALL TRANSISTOR 6 WATTS PER CHANNEL STEREO HI-FI SYSTEM OFFERING A PERFORMANCE EQUAL TO IF NOT BETTER THAN SIMILAR SYSTEMS COSTING UP TO DOUBLE THE PRICE. Modern styling plus advanced circuitry using latest silicon transistors throughout.



The famous GARRARD 3000 Record Changer fitted lightweight tubular arm with SONOTONE 9TAHC STEREO/MONO DIAMOND CARTRIDGE will play all sizes of records. (4 speeds 78, 45, 33 1/3, 16 2/3 r.p.m.). Will play up to 9 records automatically, also provision for manual play. Amplifiers and controls are mounted below record player and incorporate Bass, Treble, Volume and Balance controls and On/Off, Gram/Radio, Mono/Stereo slide switches. TWO IDENTICAL LOUDSPEAKER SYSTEMS each incorporating full frequency reproduction and high frequency units with crossover network provide full separate reproduction and are complete with 10ft leads and plugs for connection to amplifier. Will fit easily on to bookshelves, room dividers or existing furniture. BRIEF SPEC. Player/Amplifier unit, Teak finish, size 16 1/2 x 14 x 8 1/2 in 200/250V a.c. operation. Inputs for Radio Tuner/Tape Recorder also outputs for Tape Recorder. Loudspeaker Systems. Teak finish, size (each) 13 x 7 x 8in. Supplied complete with instruction booklet, ready to plug in and play. SEND YOUR ORDER NOW OR CALL AND HEAR THIS MARVELLOUS HI-FI STEREO SYSTEM (Teak finish). Only 59 gns. plus 20/- Carriage and Insurance. (Rosewood 3 gns. extra.) (Clear Perspex Cover 3 gns. extra.)

LINEAR AMPLIFIERS



Latest a.c. Mains Models offering highest quality at modest cost. L768. All Transistor 12 watts Stereo. Inputs for Tuner, Gram, Mike, Separate Bass, Treble, Balance and Volume Controls **£15.15.0**. Carr. 7/6. Teak case **£3.10.0** extra. PTA 15 (as illus.). All Transistor, 15 watts Mono. Inputs for Tuner, Gram, Mike, Guitar, Bass, Treble and two volume controls, **£15.15.0**. Carr. 7/6. Teak case **£3.10.0** extra. L745. 2 Valve 6 watts Mono. Inputs for Tuner, Gram, Bass, Treble and volume controls, **£5.19.6**. Carr. 7/6. Metal cover 15/- extra. Full details sent on request.

SEE OPPOSITE

Litesold

20 WATT SOLDERING INSTRUMENT



● CONTROLLED TEMPERATURE

Design holds max. temp. of 380°C. within close limits.

● EASY BIT REPLACEMENT

Simple, fast replacement of low-cost copper bits. Non-wearing PERMATIP bits cut servicing costs.

● BEAUTIFULLY COMPACT

Length 7½". Weight 1½ oz.
Max. handle dia. 0.715"

● UNEQUALLED PERFORMANCE

Ideal for fast production soldering on the majority of modern electronic equipment.

● ALL VOLTAGES


The LITESOLD range includes six other models (10, 18, 25, 30, 35 and 55 watts), and many accessories. Please ask for colour catalogue L/37.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL
Tel. 01-688 8589 & 4559



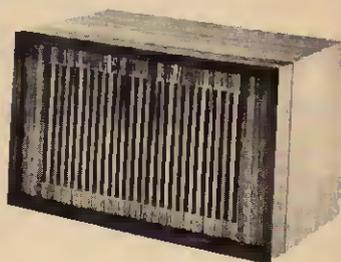FANTASTIC BARGAINS SONOTONE SOLENT 2 SPEAKER HI-FI SYSTEMS



● LIST £18 EACH

SPECIAL OFFER

11 gns. EACH POST 9/-


- Impedance 8 ohm. Power input up to 12 watts.
- Suitable for valve or transistor amplifiers.
- Frequency response 40c/s to 20 k/cs.
- Scandinavian style cabinet.
- Small attractive size 14 × 9 × 8½.
- On permanent demonstration.
- Reviewed by Hi-Fi News, The Gramophone, etc.

Send large s.a.e. for FREE Leaflets and Test Reports available from our Showrooms.

J. J. FRANCIS LTD.
123 ALEXANDRA ROAD
LONDON, N.8 BOW 1662

LEE ELECTRONICS
400 EDGWARE ROAD
PADDINGTON 5521

BUILD YOUR CIRCUITS ON VEROBOARD

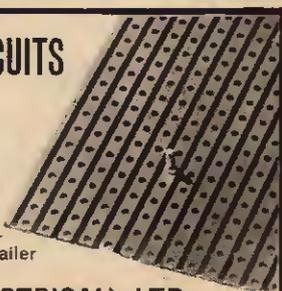

—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:

VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

All items previously advertised available, also see items advertised in Practical Wireless. Huge Hi-Fi and Components stocks at all branches.

TECHNICAL TRADING

- ★ LONDON (MUS 2639)
10 Tottenham Court Road
- ★ PORTSMOUTH
(Tel. 22034)
350-352 Fratton Road
- ★ SOUTHAMPTON
(Tel. 25851)
72 East Street
- ★ BRIGHTON (Tel. 23975)
6 Queen's Road


all mail order Brighton

FANTASTICALLY POPULAR ★ TAPE ★

We offer you fully ionized polyester/nylon and P.V.C. tapes of identical quality hi-8, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports **TRY ONE AND PROVE IT YOURSELF.**

Standard Play		Long Play	
3in. 150ft.	2/4	3in. 225ft.	2/8
4in. 300ft.	4/8	4in. 450ft.	5/8
5in. 600ft.	7/8	5in. 900ft.	10/8
5½in. 900ft.	10/8	5½in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	12/-
4in. 600ft.	5/-	5in. 1,800ft.	22/-
5in. 1,200ft.	11/-	5½in. 2,400ft.	34/-
5½in. 1,800ft.	19/8	7in. 3,600ft.	44/-
7in. 2,400ft.	27/-	Quadruple Play	
		3in. 600ft.	8/8

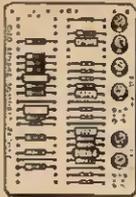Postages 1/- each.
Post Free less 2% on three reels.
Quantity and Trade enquiries invited.
NOTE. Large tape stocks at all branches.



PRINTED CIRCUITS

Five assorted circuit boards with transistors, diodes, resistors, condensers, etc. Guaranteed minimum 20 transistors. Ideal for experimenters. 5 boards for 10/- P. & P. 2/-.



F.M. WIRELESS MICROPHONES

94-104Mc/s. Transistorised. Operates from 9V battery. Complete with additional secret tie-clip microphone. List £12.10.0 ONLY 25/15/0. P. & P. 2/6. These cannot be operated in U.K.

MODEL TE.50 20,000 O.P.V. MULTIMETER

0/10/50/100/500/1,000V a.c. 0/5/25/50/250/500/1,000V d.c. 0-50µA 0/50/500µA. 0/5/50/500/5mA. 24/17/6. P. & P. 3/-.



NEW MODEL 500 30,000 o.p.v. With overload protection, mirror scale 0-5/12/5/10/25/100/250/500/1,000V a.c. 0/2.5/10/25/100/250/500/1,000V a.c. 0/50µA/5/50/500µA 12A d.c. 0/30kΩ/3MΩ/30MΩ. 25/17/6. Post Paid.

MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec: A: 0-7-6-9867; B: 5-200. Ico: 0-50 microamps. 0-5mA. Resistance for diode 200Ω-1MΩ. Supplied complete with instructions, battery and leads. 25.19.6. P. & P. 2/6.



VARIABLE VOLTAGE TRANSFORMERS

Brand New—fully Shrouded. Input 230V 50/60c/s. Output 0-280V

1A	£5.10.0
2.6A	26.15.0
5A	49.15.0
8A	54.10.0
10A	58.10.0
12A	62.10.0
20A	87.0.0

Post extra.



SILICON RECTIFIERS

200V P.I.V. 200mA	2/0
200V P.I.V. 5A	5/8
1,000V P.I.V. 5A	7/8
400V P.I.V. 5A	5/8
400V P.I.V. 6A	7/8
800V P.I.V. 600mA	0/8
800V P.I.V. 600mA	5/8
800V P.I.V. 5A (S.C.R.)	7/8
400V P.I.V. 900mA	3/8
70V P.I.V. 1A	3/8
150V P.I.V. 160mA	1/8
150V P.I.V. 25A	19/8
700V P.I.V. 100A	49/8
400V P.I.V. 5A (S.C.R.)	7/8
100V P.I.V. 6A (S.C.R.)	13/6
200V P.I.V. 6A (S.C.R.)	15/6
400V P.I.V. 6A (S.C.R.)	17/6

Discounts for quantities. Post extra.

★ TRANSISTORISED FM TUNER ★



feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. NOW 25/7/6. P. & P. 2/6. STEREO MULTIPLEX ADAPTORS 5 gns.



AVOMETERS

Supplied in excellent condition fully tested and checked. Complete with probes, leads and instructions. Model 47A 59.19.6 Model 8 8 11/6. Model 9 220. P. & P. 7/6 each.

TE22 SINE SQUARE WAVE AUDIO GENERATORS



8mc/s. 200c/s to 200 kc/s on 4 bands. 20c/s to 300c/s. Output impedance 5,000 ohms, 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads, 115. Carr. 7/6.

TE-20RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120kc/s—260 Mc/s on 8 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. 112/10/0. P. & P. 7/6. S.A.E. for details.

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER




2pf — 2,000 mid 2 ohms 200 megohms. Also checks impedance turns ratio, insulation. 200/250V a.c. Brand New 115. Carr. 7/6.

ARF-100 COMBINED AF-RF SIGNAL GENERATOR



AF. SINE WAVE 20-200,000 c/s. Square wave 20-30,000 c/s. 0/P HIGH IMP. 21V P/P 500Ω 3-8V P/P. TF. 100kc/s-300 Mc/s. Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V a.c. 227/10/0. Carr. 7/6.

TE-65 VALVE VOLTMETER

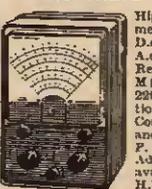

High quality instrument with 28 ranges. D.c. volts 1-1,500V a.c. volts 1-5,500V Resistance up to 1,000 MΩ. 220/240V a.c. operation. Complete with probe and instructions. 115. P. & P. 6/-. Additional Probes available: R.F. 35/- H.V. 42/6.



CATALOGUE

- ★ ELECTRONIC COMPONENTS
- ★ TEST EQUIPMENT
- ★ COMMUNICATIONS EQUIPMENT
- ★ HI-FI EQUIPMENT

We are proud to introduce our first comprehensive catalogue of Electronic Components and Equipment. Over 150 pages fully illustrated, listing thousands of items, many at bargain prices. Free discount coupons with every catalogue. Everyone in electronics should have a copy.


CLEAR PLASTIC PANEL METERS



First grade quality Moving Coil panel meters available ex-stock. S.A.E. for illustrated leaflet. Discount for quantity. Available as follows: Type MR 38P, 1 21/821a square fronts.

100-0-100µA 32/6	200mA	25/-	100V d.c.	25/-		
500-0-500µA 25/-	300mA	25/-	150V d.c.	25/-		
1-0-1mA	25/-	300mA	25/-	300V d.c.	25/-
1mA	25/-	750mA	25/-	900V d.c.	25/-
2mA	25/-	1A d.c.	25/-	750V d.c.	25/-
5mA	25/-	2A d.c.	25/-	15V a.c.	25/-
10mA	25/-	5A d.c.	25/-	50V a.c.	25/-
20mA	25/-	3V d.c.	25/-	150V a.c.	25/-
50µA	37/6	10V d.c.	25/-	300V a.c.	25/-
100µA	35/-	24V d.c.	25/-	300V a.c.	25/-
200µA	32/6	50V d.c.	25/-	'S' Meter	1mA
500-0-50µA	27/6	50V d.c.	25/-			
600-0-60µA	25/-						

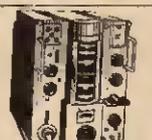POST EXTRA. Larger sizes available—send for listers. 29/6



ADMIRALTY B.40 RECEIVERS


Just released by the Ministry. High quality 10 valve receiver, manufactured by Murphy. Coverage in 5 bands 550kc/s-30Mc/s. I.F. 500kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O., calibrator, I.F. output, etc. Built-in speaker, output for phones. Operation 150/230V a.c. Size 19 1/2in x 13 1/2in x 1 1/2in. Weight 1 1/4 lb. Offered in good working condition, 222.10.0. Carr. 30/-. With circuit diagrams. Also available B.41 L.F. version of above, 10kc/s-700kc/s. 117.16.0. carr. 30/-.

UNR-30. 4-BAND COMMUNICATION RECEIVER

Covering 550 Kc/s—30 Mc/s. Incorporates variable BFO for CW/SSB reception. Built-in speaker and phone jack. Metal cabinet. Operation 220/240 v. A.C. Supplied brand new, guaranteed with instructions. £12.10.0 Carr. 7/6



NEW LAFAYETTE MODEL HA-700 AM/CW/SSB AMATEUR COMMUNICATION RECEIVER
8 Valves, 5 bands incorporating 2 MECHANICAL FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400 kc/s 500-1,500kc/s, 1.5-4.0Mc/s, 4-9-14Mc/s 10-5-30Mc/s. Circuits incorporates R.F. stage, aerial trimmer, noise limiter, B.F.O. product detector, electrical bandspread, 8 meter, slide rule dial. Output for phones, low to 25Ω or speaker 4 or 8Ω. Operation 220/240V a.c. Size 7 1/2in x 15in x 10in. Supplied brand new and guaranteed with handbook 26 GNS. Operation 10/-. S.A.E. for leaflet.

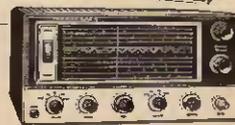

R.C.A. AR88 SPEAKERS
8in, 3 ohm speakers in metal case. Black crackle finish to match our 89 Receivers. Available Brand New and Stocked with leads. 59/6. Carr. 7/6.

LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER



19 transistors, 8 diodes, 1HF music power, 50W at 8Ω. Response 30-20,000 ± 2dB at 1W. Distortion 1% or less. Inputs 3MV and 250MV. Output 3-16Ω. Separate L and R volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 1/2in x 3 1/2 x 7 1/2in. Operation 115/230V a.c. 225. Carr. 7/6.

SINCLAIR EQUIPMENT



2.12 12 watt amplifier, 59/6. P24 Power Supply Unit, 59/6. Stereo 25 Preamp, 29.19.6. Q14 Speakers, 24.19.6. Micromatic Radio Kit, 49/6. Built, 59/6. Micro FM Radio Kit, 25.19.6.

SPECIAL OFFER

3 Z12 Amps, P24 Power Supply, Stereo 25 Pre-amplifier, 222.

ALL POST PAID

G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2



POCKET MULTI-METER

Size 3 7/8" x 2 1/4" x 1 1/2". Meter size 2 1/4" x 1 1/2". Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000. D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test prods, battery and full instructions, 42/6. P. & P. 3/6. FREE GIFT for limited period only. 30 watt Elctric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

3 to 4 WATT AMPLIFIER

3-4 watt Amplifier built and tested. Chassis size 7 x 3 1/4 x 1 in. Separate bass, treble and volume control. Double wound mains transformer, metal rectifier and output transformer for 3 ohms speaker. Valves ECC81 and 6V6. £2.5.0 plus 5/6 P. & P.

BSR TAPE DECKS

200/250 v. A.C. mains. Type TD2 Tape speed 3 1/2" twin track. Type TD10 2-track, 3 speed, plus rev. counter. Type TD10 4-track, 3 speed, plus rev. counter.

Due to 33 1/3% Purchase tax which is now applicable on these items, prices will be announced as soon as available.

Special offer ELEGANT SEVEN mk III

SPECIAL OFFER. Power supply kit to purchasers of 'Elegant Seven' parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains 200/250 volts. Output 9v. 100 mA. 9/6 extra.

Buy yourself an easy to build 7 transistor radio and save at least £10.0.0. Now you can build this superb 7 transistor superhet radio for under £4.10.0. No one else can offer such a fantastic radio with so many de luxe star features.




ONLY £4.9.6

- ★ De luxe wooden cabinet size 12 1/2" x 8 1/2" x 3 1/2". Plus 7/6 Post & Packing
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 1 1/2" x 2".
- ★ High 'Q' ferrite rod aerial.
- ★ I.F. neutralisation on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350mW.
- ★ Ready etched and drilled printed circuit board back printed for foolproof construction.
- ★ Fully comprehensive instructions and point to point wiring diagrams.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave, 168-535 metres and 1250-2000 metres.
- ★ All components: ferrite rod and tuning assembly mount on printed board.
- ★ 5" P.M. Speaker.
- ★ Parts list and circuit diagram 2/6, free with parts.

X101 10 WATTS (RMS) SOLID-STATE HI-FI AMP. WITH INTEGRAL PRE-AMP

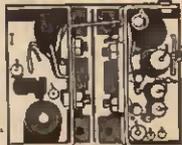Its great versatility ranges from a simple intercom, to a modern HI-FI STEREO AMPLIFIER (two are required for Stereo). The X101 is a brilliant new addition to our highly successful range of products. Its professional performance and advanced solid-state circuitry techniques ensures reliability, combined with high fidelity reproduction, at an unbeatable price of 49/6 + 2/6 P. & P.



SPECIFICATIONS: R.M.S. Power Output: 13W (music power), 10W (SINE WAVE). Sensitivity: for rated output 1mV into 3kΩ load. Frequency Response: minus 3dB points are 20Hz and 40kHz. Total Distortion: at 1kHz for rated output 1.5%; for 5W output 0.35%. Output Impedance: 3 ohms (3-15 ohms may be used). Supply Voltage: 24V d.c. at 800mA (6-24V may be used); output at 14V d.c. supply with 3 ohms speaker 7W. Size: 2 1/2" x 3 1/2" x 1 1/2". The fully comprehensive instruction manual does not only show the basics, such as circuit diagram and connections, but also gives practical easy-to-understand detailed information about the X101. Standard equalisation networks are given for most types of conventional inputs. They include: Tape head, Mag. P.U., Xial. P.U., Tuner, Mic, etc.

CONTROL ASSEMBLY. (including resistors and capacitors): 1. Volume, price 5/-; 2. Treble, price 5/-; 3. Comprehensive bass and treble, price 10/-.

POWER SUPPLIES FOR THE X101: P101/M (for Mono) 35/- P. & P. 2/6. P101/S (for Stereo) 42/6 P. & P. 2/6.

PR101/M: A High Quality, Monoral Pre-amp and Control Unit, particularly suitable for use with the X101 if a ready-built, comprehensive, multi-input system is desired.

CONTROLS: Selector Switch, Tape Speed Equalisation Switch (3 1/2 and 7 1/2 I.P.S.), Volume, Treble, Bass, three position scratch filter and three position rumble filter.


SPECIFICATION: Sensitivities for 200mV output at 1kHz. Tape Head: 3mV (at 3 1/2 I.P.S.), Mag. P.U.: 2mV. Cer. P.U.: 80mV. Radio: 100mV. Aux.: 100mV. Tape/Rec. Output: 100mV. Equalisation for each input is correct to within ±2dB (RIIA) from 20Hz to 20kHz. Tone Control Range: Bass: = -13dB at 60Hz; Treble: = -14dB at 15kHz. Total Distortion: (for 200mV output) < 0.02%. Signal Noise: > -60dB. Supply Voltage: 24V, d.c. 59/6 plus 2/6 P. & P. A STEREO VERSION (PR101/S) WILL BE ANNOUNCED SHORTLY.

THE CLASSIC: High Quality Solid-State Amplifier (Mono). **SPECIFICATION:** Switched inputs for: Tape head, Mag. P.U., Cer. P.U., Radio and Aux. Mains Input 220-250V, a.c., 50Hz. The Classic is the combination of the above described items (X101, P101/M and PR101/M) on one common chassis. Its performance and space age styling makes it the ideal choice for the value-conscious Hi-Fi enthusiast.

Available within 4 weeks. **8 gns.** P. & P. FREE.

STAR SR 150 COMMUNICATION RECEIVER

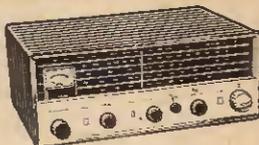Frequency range: 535 kc/s-30 Mc/s. four wavebands, four valve plus metal rectifier superhet circuit. Incorporates B.F.O. bands spread tuning, "S" meter, external telescopic aerial—ferrite aerial, built-in 4" speaker, easy-to-read dial. For 240v. A.C. operation. Complete, brand new, with full instruction manual. £17.17.0. P. & P. 10/-.




NEW! DORSET

600 milli-watt solid state 7 transistor plus diode and thermistor

Transistor Portable Radio plus Baby Alarm Facilities

Special offer—Power Supply Kit to purchasers of Dorset Portable Radios parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains, 200/250v., output 9v., 100mA. 9/6 extra.

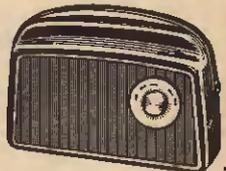Completely modernised high quality portable radio featuring complementary N.P.N. and P.N.P. output stage.



The comprehensive easy-to-follow drawings supplied make this the easiest-ever transistor radio set of parts, with the following features:

- Simple connections to only 6 tags on the R.F./I.F. module, 3 I.F. stages, osc. coil and 3 transistors which with their associated components are completely wired.
 - Only 4 connections on the A.F. module to complete the 4 transistor 600 milli-watt solid state amplifier.
 - Pre-aligned R.F./I.F. module built and tested.
 - A.F. module built and tested.
 - Fully tunable over M.W. and L.W. bands. M.W. 540-1640 Kc/s (557-183 metres). L.W. 150-275 Kc/s (2000-1100 metres).
 - Intermediate Frequency 470 Kc/s.
 - Sensitivity: M.W. at 1 Mc/s 10 microvolts plus or minus 3db. L.W. at 200 Kc/s 40 microvolts plus or minus 4db.
 - High Q internal ferrite rod aerial on both wavebands.
 - Class "B" modulated output stage with thermistor controlled heat stabilization. Class "B" output stage ensures long battery life. Current drain is proportional to the output level. Total current drain of the receiver under no signal conditions is 10-12mA. At reasonable listening level 20-30mA.
 - Extension sockets for car aerial input, tape recorder output (independent of vol. control) and Ext. Speaker.
 - All components (except speaker) mount on the printed circuit board. Easy to follow instructions. Size of cabinet 12" long, 8" high and 3" deep.
 - Finger tip controls.
- Circuit and parts list 2/6, free with parts.
PRICE: £5.5.0 plus 7/6 P. & P.

FIRST QUALITY P.V.C. TAPE

5 1/2" Std. 850ft. ..	9/-	5" L.P. 850ft. ..	10/6
7" Std. 1200ft. ..	11/6	3" T.P. 600ft. ..	10/6
3" L.P. 240ft. ..	4/-	5" T.P. 1800ft. ..	25/6
5 1/2" L.P. 1200ft. ..	11/6	5 1/2" T.P. 2400ft. ..	32/6
7" L.P. 1800ft. ..	18/6	7" T.P. 3600ft. ..	42/6
5 1/2" D.P. 1800ft. ..	18/6	4" T.P. 900ft. ..	15/-

P. & P. on each 1/6, 4 or more post free

600mW SOLID STATE 4-TRANSISTOR AMPLIFIER

Speaker output impedance 12 ohms. Frequency response 3db points 90 c/s and 12 Kc/s. Price 19/6 plus 1/- P. & P. 7" x 4" speaker to suit. 13/6 plus 2/- P. & P.

2 1/2 WATT ALL TRANSISTOR AMPLIFIER
AC mains 240v. Size 7" x 4 1/2" x 1 1/2". Frequency response 100 c/s-10 Kc/s. Semiconductor, two OC 75's, two AC 128's and two stabilisers AA129. Tone and volume controls on flying leads. £2.10.0. P. & P. 3/6. Suitable 8" x 5" 10,000 line high flux speaker 18/6. P. & P. 2/-.

8-WATT 4-VALVE PUSH-PULL AMPLIFIER & Metal RECTIFIER

Size 9" x 6" x 1 1/2". A.C. Mains, 200-250 v, 4 valves. For use with Std. or L.P. records, musical instruments. All makes of pick-ups and mikes. Output 8 watts at 5 per cent of total distortion. Separate bass and treble lift control. Two inputs, with controls for gram and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested. £4.4.0. P. & P. 11/- 8" x 5" Speaker to suit. Price 14/6 plus 1/6 P. & P. Crystal Mike to suit 12/6 plus 1/6 P. & P.

RADIO AND T.V. COMPONENTS. (ACTON) LTD.


21D HIGH STREET, ACTON, LONDON, W.3
Shop hours 9 a.m. to 6 p.m. Early closing Wednesday
Goods not despatched outside U.K.
All enquiries stamped addressed envelope. Terms C.W.O.
Also at 32 EDGWARE ROAD, LONDON, W.2.
PERSONAL SHOPPERS ONLY. Early closing Thursday.
All orders by post must be sent to our Acton address.

Now available Mullard 1968 Data Book

136 pages of data, including for the first time, colour-coded sections for quick reference—covering comparables and equivalents and all current Mullard semiconductors, valves, tubes and components for Radio, TV, Audio and HiFi applications.

PRICE 3/6 from your local TV retailer OR direct from Mullard—cash with order, plus 9d for p-and p.

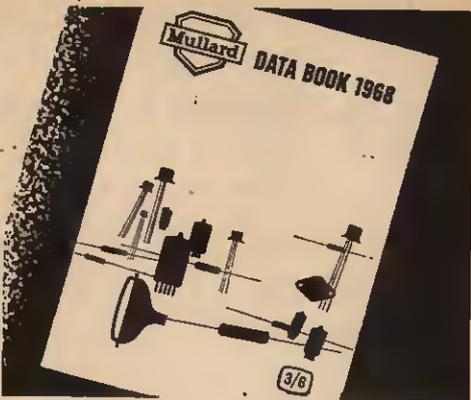Mullard Mullard Limited, Distributor Sales Division, Mullard House, Torrington Place, London, W.C.1.



TRANSISTOR STEREO 8 + 8




A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push-pull output per channel. (16 W mono). Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, C.R.K.I. board, attractive front panel, knobs, wire, solder, nuts, bolts—any extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of.

Brief Specification: Freq. response ± 2 db 20-20,000 c/s. Bass boost approx. to +12 db. Treble cut approx. to -18 db. Negative feedback 18 db over main amp. Power requirements 25 V at 0.6 amp.

STEREO AMPLIFIER

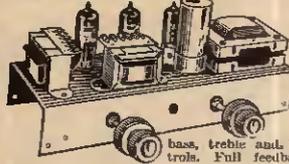Incorporating 2 ECL96s and 1 E280, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY £5.9.6
P. & P. 3/-
De-luxe version with ECL28 valves, sep. bass, treble and balance controls. Full feedback. 8 g/s. P. & P. 8/-.


3-VALVE AUDIO AMPLIFIER MODEL HA34



Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4.5.0**. P. & P. 6/-

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL54s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 2-16 ohm speaker and 3 independent volume controls, and separate bass and treble controls are provided giving good HiFi and cut. Valve line-up 2 EL54s, ECC83, E280, and E280 rectifier. Simple instruction booklet 2/6. (Free with parts.) All parts sold separately. **ONLY £7.9.6**. P. & P. 8/6. Also available ready built and tested complete with stat. input sockets, **£9.5.0**. P. & P. 8/6.

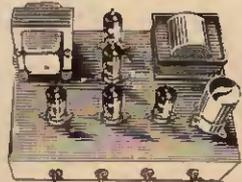

PRICES

Amplifier Kit	£9.10.0	P. & P. 4/6
Built and Tested	£12.10.0	P. & P. 4/6
Power Pack Kit	£2.10.0	P. & P. 4/-
Built and Tested	£3.0.0	P. & P. 4/-
Cabinet (as illus.)	£2.10.0	P. & P. 5/6

(Special offer—£14.10.0. Post Free if all above kits ordered at same time or can be supplied built and tested for **£18.0.0** Post Free).
Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.)

LATEST COLLARO MAGNAVOX 363 STEREO TAPE DECK. Three speeds, 4 track, takes up to 7in. spools. **£12.10.0**. Plus 7/6 Carr. & ins. (Tapes extra). B.S.R. TD.2. 4 track Stereo Tape Deck. 8g/s. Carr. 7/6. **QUALITY PORTABLE TAPE RECORDER CASE.** Brand new. Beautifully made. Only 49/6. P. & P. 8/6. Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser 35/- P. & P. 3/-.

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's original packing.		
LATEST B.S.R. MODELS		
TU12 Single Player with mono Cart.	£3.8.6	
GU7 Single Player with mono Cart.	£4.15.3	
UA25 Changer with mono Cart.	£6.7.6	

All plus Carriage and Packing 8/6.
See below for suitable stereo cartridge:
LATEST GARRARD MODELS
All types available 1000, SP25, 5000, AT60, etc.
Send S.A.E. for latest Bargain Prices!

BRAND NEW CARTRIDGE BARGAINS! LATEST B.S.R. X3M MONO COMPATIBLE CARTRIDGE
With turnover sapphire stylus suitable for playing 78, EP, LP and Stereo records with mono equipment. **ONLY 22/6**. P. & P. 1/6.
SONOTONE STARC Compatible Stereo Cartridge with diamond stylus 50/- and with sapphire stylus 40/- P. & P. 1/6 each.

QUALITY RECORD PLAYER AMPLIFIER
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer—matched for 3 ohm speaker. Size 7 1/2 in. w. x 4 in. d. x 6 1/2 in. h. Ready built and tested. **PRICE 75/-**. P. & P. 6/-
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. **PRICE 87/6**. P. & P. 7/6.

DE LUXE QUALITY PORTABLE R/P CABINET
Uncut motor board size 14 1/2 in. x 12 in. clearance 2 1/2 in. below 6 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD Antochanger or Single Player Unit (except AT60 and SP25). Size 18 in. x 10 in. x 8 in. **PRICE £33.0.0**. P. & P. 9/6.

VYNAIR AND REKINE SPEAKER AND CABINET FABRICS app. 54in. wide. Usually 35/- yd., our price 18/6 per yd. length. P. & P. 2/6. (min. 1yd.). S.A.E. for samples.

BRAND NEW 3 OHM LOUSPEAKERS
8in. 14/-; 6 1/2 in. 18/6; 5in. 27/-; 7in. x 4in. 18/6; 10in. 6/-; 8 1/2 in. 27/6.

E.M.I. 5in. x 5in. with high flux magnet 21/-.
E.M.I. 13 1/2 in. x 8in. with high flux ceramic magnet, 42/-. (15 ohm, 45/-). P. & P. 5in. 2/-, 6 1/2 in. & 8in. 2/6, 10in. & 12in. 3/6 per speaker.

BRAND NEW 12in. 15w. Hi-D Speakers, 3 or 15 ohm. Current production well known British make. Offered below list price at 89/6. P. & P. 5/-.
Cultar model's 25w. **£5.5.0**; 35w. **£8.8.0**.

E.M.I. 8in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3, 8 or 15 ohms. 15/- P. & P. 2/6.
12in. "BA" TWIN CONE LOUSPEAKER. 10 watts peak output. 3 or 15 ohm. 35/- P. & P. 3/6.

35 OHM SPEAKERS
3 1/2 in. 18/6; 7 x 4 in. 21/- P. & P. 2/- per speaker.


HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI
● Peak output in excess of 1 1/2 watts.
● All standard British components.
● Built on printed circuit panel size 6. x 3in.
● Generous size Driver and Output Transformers.
● Output transformer tapped for 3 ohm and 15 ohm speakers.
● Transistors (GET 114 or 81 Mullard OC81D and matched pair of OC81 o/p). ● 9 volt operation. ● Everything applied, wire, battery clips, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-**. P. & P. 3/-.
Also ready built and tested, 52/6. P. & P. 3/-.



FM/AM TUNER HEAD

Beautifully designed and precision engineered by Dornier and Wadsworth Ltd. Supplied ready fitted with twin 5000s tuning condenser for AM connection. Features FM section covers 86-102 Mc/s. I.F. output 10.7 Mc/s. Complete with ECC83 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-.
ORDER QUICKLY!
MATCHED PAIR AM/FM I.F.'s. Comprising 1st I.F. and 2nd I.F. discriminator. (465 Kc/s/10.7 Mc/s). Size 10 in. x 1 1/2 in. x 2 1/2 in. H. Will match above tuner head. 11/- P. & P. 2/-.

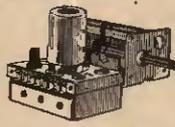

GOBLER P.M. TUNER HEAD. 88-100 Mc/s 10.7 Mc/s. I.F. 15/-.
Plus 8/6 P. & P. (ECC83 valves, 8/6 extr.)
B.T.C. SILICON VALVETONE HALF-WAVE RECTIFIERS. Type RA5. 508 AF. 5 amps. 950 P.I.V. 1 1/2 in. long x 1/2 in. dia. approx. List 50/-. **OUR PRICE 8/6**. P. & P. Free.

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400 pf x 146 pf. Fitted with trimmers and 5:1 integral auto motion. Suitable for nominal 470 kc/s. I.F. Size approx. 2 1/2 x 1 1/2 in. **ONLY 8/6**. P. & P. 2/6.

FW ONLY! BLENK MINATURE BELAYS. D.P.O. Gold plated contacts. Size approx. 1 1/2 x 1 1/2 x 1 1/2 in. 6v. at 30 mA. **ONLY 15/-**. P. & P. 1/6.

NEON A.C. MAINS INDICATOR. For panel mounting, cut out size 1 1/2 x 1 1/2 in. deep inc. terminal. White case with lens giving brighter light. For mains 200/250v. 2/6 each. P. & P. 6d. (6 or more post free).

VIBRATORS. Large selection of 2, 4, 6, 12, 24 and 32 Volt. Non-sync. 8/6; Sync. 10/- P. & P. 1/6 per vibrator. S.A.E. with all enquiries.

MAINS TRANSFORMER.

For transistor power supplies. Pri. 200/240v. Sec. 0-0-9 at 500 mA. 11/6. P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6.

MAINS TRANSFORMER.

For transistor power supplies. Tapped pri 200-250v. Sec. 40-0-40 at 1 amp (with electrostatic screen) and 82v. at 5 amp for diode lamps etc. Drop thro' mounting. Stack size 1 1/2 in. x 3 1/2 in. x 3 1/2 in. 27/6. P. & P. 2/6.

MATCHED PAIR OF 8 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS.

Stack size 1 1/2 x 1 1/2 x 2 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/- P. & P.

FARNKO 7-10 watt OUTPUT TRANSFORMERS to match pair of ECL 82's in push-pull, sec. tapped 2-7.5. 7-5 and 15 ohm. Stack size 2 1/2 x 1 1/2 x 2 1/2 approx. **ONLY 12/-**. P. & P. 3/-.
7-10 watt OUTPUT TRANSFORMERS to match pair of ECL 86's in push-pull to 3 ohm output. **ONLY 11/-**. P. & P. 2/6.

10-12 watt OUTPUT TRANSFORMERS. Size 2 1/2 in. x 2 in. 10-amp fitting. For two EL84's in push-pull. State 3 or 15 ohm impedance. 12/6. P. & P. 2/6.

ACOS HIGH IMPEDANCE CRYSTAL STICK MIKES. Listed at 42/-. Our price. 21/- P. & P. 1/6.
ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity. 15/6. P. & P. 1/6.

SPECIAL OFFER! MOVING COIL-MIKE. Fitted on/off switch for remote control. High quality. High or Low impedance. (State imp. req'd.) **BARGAIN PRICE 30/-**. P. & P. 2/6.

HARVERSON SURPLUS CO. LTD.
170 HIGH ST., MERTON, S.W.19 01-540 3985
Open all day Saturday Early closing Wed., 1 p.m.
A few minutes from South Wimbledon Tube Station. (Please write clearly)
OVERSEAS P. & P. CHARGED EXTRA. S.A.E. with all enquiries

OUTSTANDING HIGH FIDELITY DESIGNS FROM SINCLAIR

The
world's
smallest
radio



SINCLAIR MICROMATIC

The ultimate in personal listening, the Micromatic is as easy to have with you as your wrist-watch. It has enormous power and range, and the magnetic earpiece now supplied assures marvellous quality. Hear how Radio 1 and other stations simply pour in. Build it yourself or buy your Micromatic ready built. This is the set you will never be without once you hear it for yourself.

- 1½" × 1½" × 1"
- Tunes over medium waveband
- Slow motion tuning control
- Aluminium front panel and dial
- Magnetic earpiece


Complete kit including magnetic earpiece and instructions

49/6

Ready built with magnetic earpiece

59/6

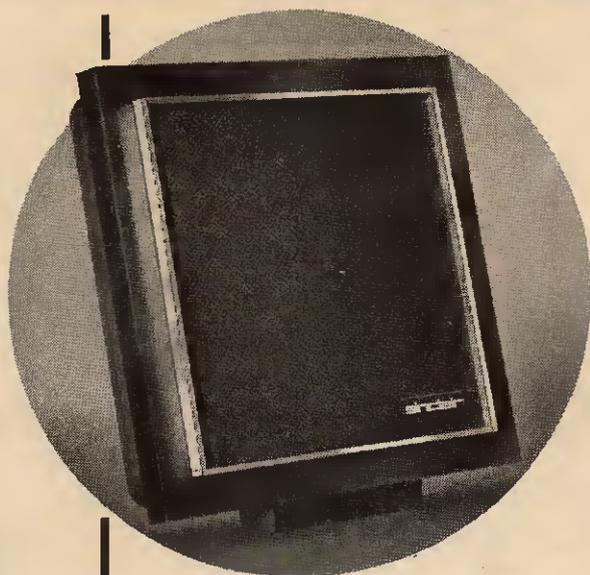Mallory Mercury Cell RM.675 (2 needed) each 2/9



SINCLAIR Q.14 LOUDSPEAKER

BRILLIANTLY EFFICIENT ... especially in stereo

When Sinclair Radionics decided to design and manufacture a new loudspeaker, it was required from the start that its performance should be worthy of today's best high fidelity standards and be so reasonably priced that the greatest numbers could afford it. By using ultra-low resonant materials to form its acoustically contoured housing, outstandingly brilliant performance resulted. Furthermore, the unusual form of the Q.14 meant it could be used as a free-standing shelf speaker, as a wall-corner sound radiator or flush mounted singly or in multiple units on a flat surface such as a wall. The correctness of the design of the Q.14 has amply proven itself since within a few months of its introduction, it is already amongst the four most demanded loudspeakers irrespective of price. Independent laboratory tests have already shown that the Q.14 has amazingly good performance characteristics. As a judge of good sound yourself, your ear will confirm this instantly. At its price, there is nothing to stop you changing to Sinclair at once.


- Size 9½in × 9½in × 4½in deep plus detachable base
- 15 ohms impedance
- Up to 14 watts loading
- Smooth response between 60 and 16,000 Hz
- British manufacture

The Q.14 is finished in matt black with solid aluminium bar embellishment on the front. Supplied in strong fitted carton and sent post free under money back guarantee if you are not satisfied.

IDEAL WITH Z.12 HI-FI SYSTEMS

sinclair

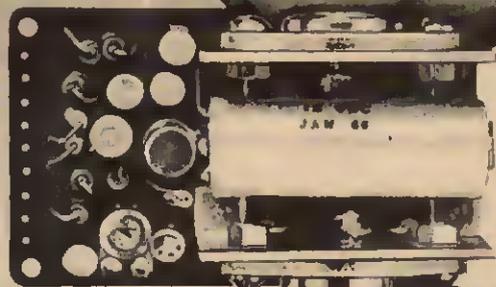SINCLAIR RADIONICS LTD., 22 Newmarket Road,
Cambridge Phone OCA-3 52996



SINCLAIR Z.12

COMBINED 12 WATT HI-FI AMP AND PRE-AMP

UNCHALLENGED LEADER IN ITS FIELD

No constructor's transistor amplifier has ever achieved such success as the Sinclair Z.12. It favours the user in so many ways—with fantastic power-to-size ratio, with far greater adaptability, with freedom to operate it from batteries or mains power supply unit (the new PZ.4 is ideal for this) with the opportunity to obtain superb stereo reproduction for very little outlay. Countless thousands of Z.12s are in use throughout the world—in hi-fi installations, electronic guitars and organs, P.A. installations, intercom systems, etc. This true 12 watt amplifier is supplied ready built, tested and guaranteed together with the Z.12 manual which details control circuits enabling you to match the Z.12 to your precise requirements. For complete listening satisfaction, use your Z.12 system with Q.14 loudspeakers. It assures superb quality with substantial saving in outlay.

- 3" x 1½" x 1¼"
- Class B Ultralinear output
- 15-50,000Hz ± 1dB
- Suitable for 3, 5, 8 or 15Ω speakers. Two 3-ohm speakers may be used in parallel.
- Input—2mV into 2kΩ
- Output—12 watt, R.M.S. continuous sine wave (24W peak)

"I made this (Z.12) stereo record player for my work as hospital chaplain and it has been a great success."


K.S.B. Basingstoke

"The Z.12 and Q.14 live up to your high standard. I could spend pages praising these products."

I.A.W. Hereford.

*Ready built,
tested and
guaranteed.*

89/6

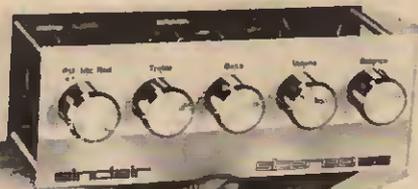

SINCLAIR STEREO PZ.4

For use with two Z.12's or any good hi-fi stereo system. Frequency response 25Hz to 30kHz ± 1dB connected to two Z.12's. Sensitivity Mic. 2mV into 50kΩ; P.U.—3mV into 50kΩ; Radio—20mV into 4.7kΩ. Equalisation correct to within ± 1dB on RIA curve from 50 to 20,000Hz. With brushed and polished aluminium front panel with solid aluminium knobs to match. Size 6½in X 2½in X 2½in plus knobs.

**BUILT
TESTED
AND
GUARAN-
TEED
£9.19.6**

SINCLAIR PZ. 4 STABILISED POWER SUPPLY UNIT



A heavy duty a.c. mains power supply unit delivering 18V d.c. at 1.5A. Designed specially for Z.12 assemblies. Ready built and tested.

99/6

WE PAY POSTAGE ON EVERYTHING YOU ORDER

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send POST FREE

**YOUR SINCLAIR
GUARANTEE**

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question. **FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS.**

NAME

ADDRESS

For which I enclose cash/cheque/money order

PE.5

Lasky's Radio

DON'T MISS THIS!

Lasky's Birthday Draw

The following 85 numbers have been drawn for prizes in our 35th Birthday Draw. Please refer to Page 12 of our Catalogue for details of entry if your number (on the front page of your Catalogue) is amongst those listed here:

000013	001415	002813	012902	024444	038888	047117
000092	001810	005414	012777	024518	029875	035900
000828	001582	002479	013028	024950	029900	030900
000899	001711	003060	013750	028515	029999	037017
000927	001777	003186	015000	027000	030188	038111
000929	001800	005000	016001	027009	030744	038212
000974	001900	005015	016020	028010	030844	039414
001054	001911	005101	020009	028455	030999	039865
001274	001922	005615	021414	028490	031010	043472
001288	001991	006768	021444	029080	032013	048782
001292	002101	008900	021500	029181	033417	047111
001333	002220	011717	023466	029444	034111	037388

The first 10 correct entries to be opened will receive 25 Lasky's Gift Vouchers, the next 25 will receive £1 vouchers and the next 50 will receive 10/6 vouchers.

Note: Members of Lasky's Radio staff and relatives are expressly excluded from entry in this competition.

HAVE YOU GOT YOUR LASKY'S CATALOGUE FREE Second Great Reprint Issue Now Ready. Just send your name, address and 1/- for post only.

SPECIAL INTEREST ITEMS!

DESIGNED ESPECIALLY TO REPLAY PHILIPS CASSETTE SYSTEM

THE FANTAVOX TAPE CASSETTE PLAYER

This machine is the first of its type and is designed specifically to replay pre-recorded tape cassettes made for the PHILIPS and other cassette systems. The cassette is simply slipped into the machine and is immediately ready to play. Each cassette gives over 40 minutes play (twice as long as ordinary cassettes)—simply turn cassette over. Constant tape speed 1 1/2 i.p.s. Only two controls off play and vol. Fully transistorised, powerful w/v, built in speaker, socket for personal earpiece. Operates on 6 pen-light batteries. Very attractively styled shockproof plastic cabinet size 8 1/2 x 4 1/2 x 9 1/2 in with wrist strap. Complete with cassette titles available: jazz, pop, shows and classics. This machine allows you to play the music of your choice anywhere—anytime.

LASKY'S PRICE £7.9.6 Post 5/-



CROWN MODEL TRF-6 AM/FM 9 TRANSISTOR RADIO

Unbelievably small for an AM/FM receiver—the Crown is only 4 1/2 in x 2 1/2 in x 1 1/2 in. Super sensitive 9 transistor superhet circuit with directionless stabilised reception. AM cover; MW 336-1,600kc/s. FM cover; 88-108Mc/s. Superb tone reproduction. 2 1/2 in. FM speaker. Precision tuning. 6 section (14 1/2 in) telescopic aerial—clips into side when not in use. Output 280mW max. Beautifully styled and finished cabinet in black plastic with silver metal trim. Operates on one 9V battery. Complete with leather purse, ear-piece and battery. List Price 18/ Gns.

SCOOP Price £7.19.6 Post 2/6



MODEL C-1000 MILI TESTER

A really tiny meter with "big" meter performance. Brief Specification: Movement sensitivity 400µA. D.C. volts ranges: 0-10, 50, 250, 1,000 volts, + 3% f.s.d. at 1K Ω P.V. A.C. volts ranges: 0-10, 50, 250, 1,000 volts + 4% f.s.d. at 1K Ω P.V. D.C. current: 0-1,100mA. Resistance range: 0-150k Ω. Size 2 1/2 in x 3 1/2 in x 1 1/2 in.

Lasky's Price 39/6 Post 2/6



Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271
Open all day Saturday, early closing 1 p.m. Thursday

33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605
Open all day 9 a.m.—6 p.m. Monday to Saturday


152/3 FLEET STREET, LONDON, E.C.4 Tel.: FLEet St. 2833
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

MOTORING PLEASURE

"EASI-TUNE" AM/FM MAJOR

V.H.F. CAR RADIO

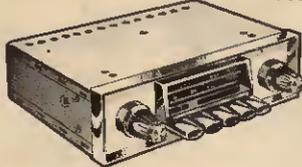


A completely new British made AM/FM car radio that brings the Hi-Fi quality of FM transmissions to your car (ALL the new local stations) PLUS medium waveband cover 180-570m and long waveband cover 1,160-2,000m (FM cover: 88-108Mc/s with automatic A.F.C.). Features Ave RAB1-

TUNE push buttons for wave change and instant selection of three of your favourite medium wave stations, plus full manual tuning. Nine transistor and four diode circuit gives immediate reception, powerful 3W output and superior performance at high speed. Other features include illuminated dial, red "on" indicator, tone control. Strong metal case size 7 x 2 x 3 1/2 in (fits all standard cut-outs). Very handsome appearance, silver/black/chrome finish. For 12V positive or negative earth operation. Complete with 7 x 4 in speaker, baffle board, universal mounting kit and instruction manual.

LASKY'S PRICE 23 Gns. Post FREE

NEW ANOTHER "EASI-TUNE" CAR ENTERTAINER

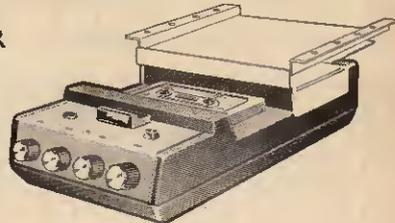THE STEREO-TONE STEREO TAPE CASSETTE CAR PLAYER



Another British first—right on time, right up-to-date the latest in travelling pleasure. Plays ALL the new great range of PHILIPS Musicassettes with over 250 titles now available—giving YOU the choice of music for your journey (each cassette gives up to 48min continuous play). The Stereo-Tone is compact, easy to fit and styled to enhance any car. Incorporates the well proven Philips tape play mechanism and a specially developed 12 transistor amplifier giving 2 1/2 W output per channel with sharp stereo separation. Controls include on/off with indicator, single control for start/stop, fast forward and rewind, sep. volume, bass, treble and stereo balance controls. Tape loading and change are super easy—the Stereo-Tone slides out from its vibration free mounting for inserting or turning cassette over then pushes back for obstruction free operation. The Stereo-Tone cabinet is made from high quality scratch proof CYCLOLAC plastic in dark grey with satin silver control panel with black knobs. Size only 9 1/2 x 5 1/2 x 3 1/2 in. Tape speed 1 1/2 i.p.s. with transistor motor regulator. Operates on all 12V positive or negative earth systems. Complete with two loudspeakers, baffle boards, leads, etc., simple (four screw fixing) mounting assembly AND one Free Musiccassette of your choice.

LASKY'S PRICE £29.0.0 Post FREE

TWO BAND TRANSISTOR CAR RADIO BARGAIN! MODEL CR-62

A new high quality imported all transistor superhet car radio that really breaks the quality/price barrier. A unique feature of this set are the four M/W band station pre-selection buttons which you yourself set to your own four favourite stations—this is in addition to full M/W band cover over 535-1,605kc/s and full L/W band cover over 150-300Kc/s (IF frequency 455kc/s). Externally adjustable aerial trimmers ensure maximum output. Six transistor (including one diode type) and one diode circuit provides powerful 2W output. The set is adjustable for use on either positive or negative ground 12V systems (external line fuse fitted). Standard mounting size 6 1/2 x 5 1/2 x 2 1/2 in—front panel 1 1/2 in larger all round—finished in anodised aluminium with black push buttons. Complete with mounting brackets, lead and plug and two "keys".

LASKY'S PRICE £9.19.6 Post 5/-

6 x 4in elliptical 8 Ω dynamic speaker 17/6 extra—Post FREE.

SPECIAL OFFER—LOCKING CAR AERIAL Model S3003 five section 402 extension heavy chrome telescopic wing mounting type with unique locking device to protect the antenna when closed. Complete with mounting bracket, lead and plug and two "keys".

LASKY'S SPECIAL PRICE 39/6 Post Free with the Royal CR-62. Post Sep. 2/6.

High Fidelity Audio Centers

42 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573
Open all day Thursday, early closing 1 p.m. Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789
Open all day Saturday, early closing 1 p.m. Thursday

VOL. 4 No. 5
May 1968

PRACTICAL ELECTRONICS

LABOUR OF LOVE

THE trouble with certain amateurs" we heard a well known professional recently complain, "is that they make things far too good". This was a mild protest at the fastidious concern for detail and elaboration indulged in by some spare time constructors.

In expressing this opinion, this critic certainly revealed his awareness of amateurs, and indirectly paid tribute to the high standard of craftsmanship often found amongst the non-professionals. This is certainly gratifying. In all walks of life too much distinction is maintained between the amateur and the professional. In general parlance the term professional, when applied to person or product, suggests superiority. Quite commonly it is assumed that the amateur represents merely the second best.

The activities and achievements of individuals in fields outside their normal vocation are often belittled without just cause. Resentment of outsiders poaching upon their exclusive preserves, plus a feeling of insecurity or even of inferiority (unadmitted, of course) may be contributory factors for the patronising manner adopted by some professionals towards their amateur brethren.

So far as our own particular field of interest is concerned, we have occasionally encountered such attitudes from individuals professionally engaged in the electronics industry. Happily such cases are the rare exception. Many of our most esteemed friends and associates are in the industry. Professionals they may be, but also real amateurs at heart. For what does the word really mean but a lover, or devotee. Genuine interest and high proficiency in a subject (whatever it may be) should not be automatically nor exclusively equated with professionalism. Let's face it, there are good and bad workers on both sides of the fence!

Now to answer the above quoted criticism levelled at some amateurs. A project undertaken for enjoyment in one's own time is bound to reflect this in countless little ways. The finalised piece of home-made equipment will carry some marks of the builder's own personality, and not an inspector's rubber stamp applied at the end of a production line. The amateur has no time sheet to fill in, and if the fancy leads him to a little extravagance—it is his own pocket he dips into. Fussy concern for detail is no cause for condemnation, but rather for envy. Many a professional must, on occasion, wished he could have spent more time or used more material on a given project. But in the commercial world things are necessarily rather different. Ay, there's the rub!

F. E. Bennett—Editor

THIS MONTH

CONSTRUCTIONAL PROJECTS

BOAT INTRUDER ALARM	326
TRANSISTOR CURVE TRACER	333
ELECTRONIC CYMBALS	342
P.E. ANALOGUE COMPUTER	360
FLUORESCENT CAMPING LIGHT	375

SPECIAL SERIES

NUCLEONICS FOR THE EXPERIMENTER—7	352
TRANSISTOR AMPLIFIER DESIGN—4	347

GENERAL FEATURES

DENTOPHONICS	372
--------------	-----

BEGINNERS

SEMICONDUCTOR BASICS—6	356
MULTIVIBRATOR	358

NEWS AND COMMENT

EDITORIAL	325
AUDIO FAIR PREVIEW	330
BOOK REVIEWS	346
BETTER SOUND	351
READOUT	376

*Our June issue will be published on
Friday, May 17*

All correspondence intended for the Editor should be addressed to: The Editor, PRACTICAL ELECTRONICS, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Advertisement Offices: PRACTICAL ELECTRONICS, George Newnes Ltd., 15/17 Long Acre, London, W.C.2. Phone: 01-836 4363. Telegrams: Newnes London. Subscription Rates including postage for one year, to any part of the world, 36s. © George Newnes Ltd., 1968. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is specially reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

INTRUDER ALARM

FOR SMALL
CRAFT

THIS article describes the construction of a simple low cost alarm that will prove effective as a deterrent to vandals or marauders visiting your yacht or motor-boat.

Although primarily designed to prevent unlawful entrance through boat doors and hatches, it may also be employed as a burglar alarm for cars or as a domestic sentinel. Current consumption on standby is exceedingly low, in the order of microamps and the choice of a silicon transistor in the first stage insures against fortuitous switching of the relay through thermal influences.

CIRCUIT DESCRIPTION

The circuit diagram for the alarm system is given in Fig. 1. In essence the circuit consists of an *npn* emitter follower TR1, the load of which is a 500 ohm 600 type relay RLA, followed by an astable pulse generator (TR2, TR3) switching an alarm at a selected frequency.

In the standby condition the transistor TR1 is held off by the loop of closed microswitches which are fitted to hatches and doors. It was found in practice that the relay would not trip even for a loop resistance of 50 kilohms, so it can be seen that high contact resistance, effected by alternative choice of contact plate switching through poor connection, should not reduce the efficiency of this alarm.

ACTIVATION OF ALARM

If the loop line is broken through forced entrance, the small quiescent current through R1 is diverted to the base of TR1 which switches on, so energising relay RLA. The normally open contacts RLA1 close. This has the initial effect of providing a latching potential to the relay by way of R2 thus ensuring that any attempt to cut off the alarm by closing doors or hatches and so completing the loop is frustrated since the relay armature is held in effect by its own contacts.

Any attempts by the marauder to rip out the loop wires are equally ineffectual with this latching action.

ASTABLE MULTIVIBRATOR

The closed relay contact RLA1 also completes the circuit for the complementary astable multivibrator circuit composed of TR2 and TR3. Most readers are

probably familiar with the conventional multivibrator, easily recognised by its crossed pair of feedback capacitors. The circuit employed in this boat alarm produces a similar output pulse, but it is very different in its operation.

In the standby condition the electrolytic capacitors C1 and C2 are discharged, but with the closing of RLA1, C1 charges through the point contact diode D1 and RLB coil with a time constant appropriate to this series train. Simultaneously C2 charges by way of RLB coil, VR1, and R3—with a relatively larger time constant.

Since the charging of C2 is exponential from zero, a negative potential will appear at the base of the *npn* silicon transistor TR2, proportional to the values of R3 and the frequency control potentiometer VR1. This negative bias holds off TR2 and consequently TR3, since no collector current is being passed to the base of this transistor. With the charging of C2 the negative-hold-off bias is removed and TR2 is switched into conduction with consequent bottoming of TR3.

This means that most of the supply volts now appears across RLB so closing the normally open contacts of RLB1. At this point the diode D1 is reverse biased and does not allow the rapid discharge of C1 through TR3. This capacitor now acts as a temporary supply to maintain the complementary pair in conduction. With the discharge of C1 and C2 by way of the base-emitter junction of TR2, D1, and VR1, the circuit reverts to its original state, with relay contacts opening prior to the next cycle of charging events.

MARK-SPACE RATIO

Whilst the consumption of the operating unit is a nominal 20mA, the current taken by the alarm audio transducer will be very much greater. A degree of power conservation can be achieved by adjusting VR1 for the smallest mark-to-space ratio.

This setting will of course, be a compromise between an urgent alarm repetition rate, if this is required, and the available capacity of the batteries employed.

If a bank of high power zinc-carbon dry cells, such as Ever Ready HP1's are used with a car horn, the mark-space potentiometer setting should be at its lowest—although it must be stated that these cells would be more suited to a large underdome bell as an alarm.


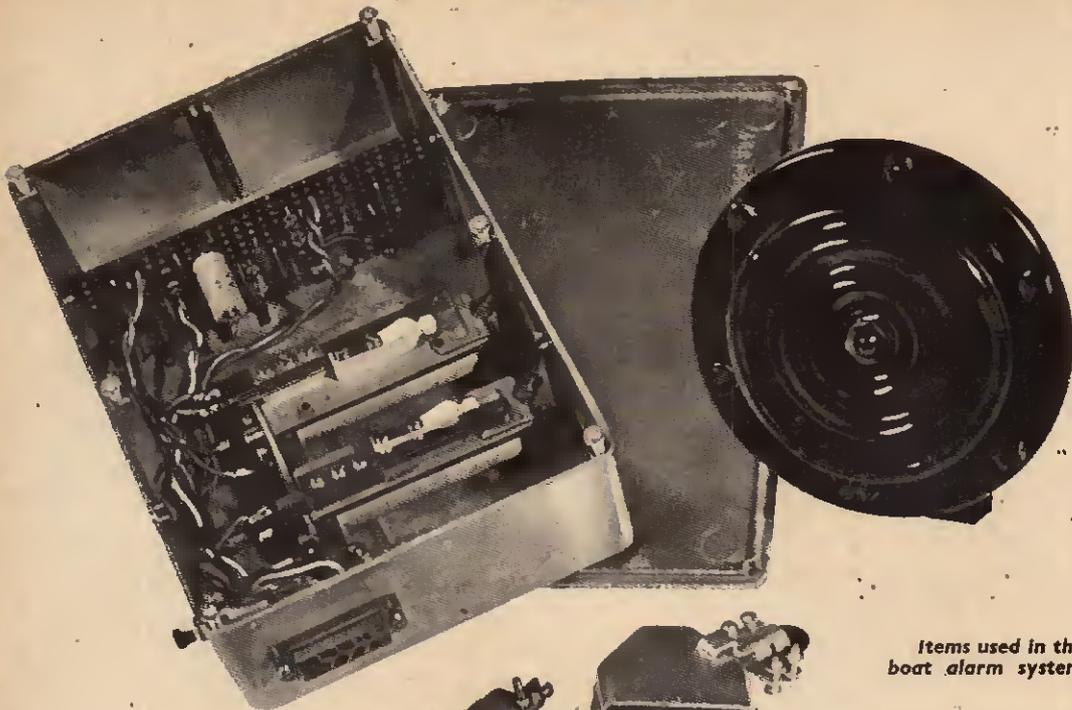


Fig. 3. Installation wiring of the boat alarm system

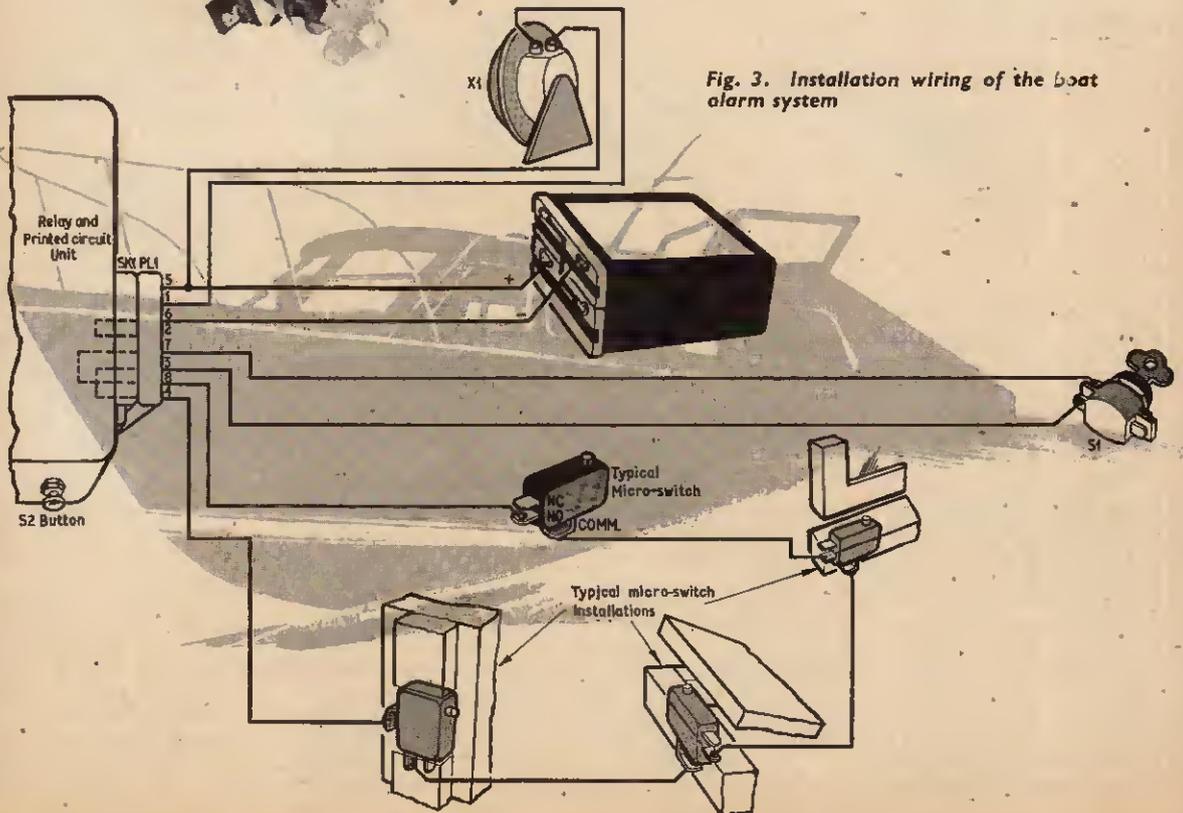

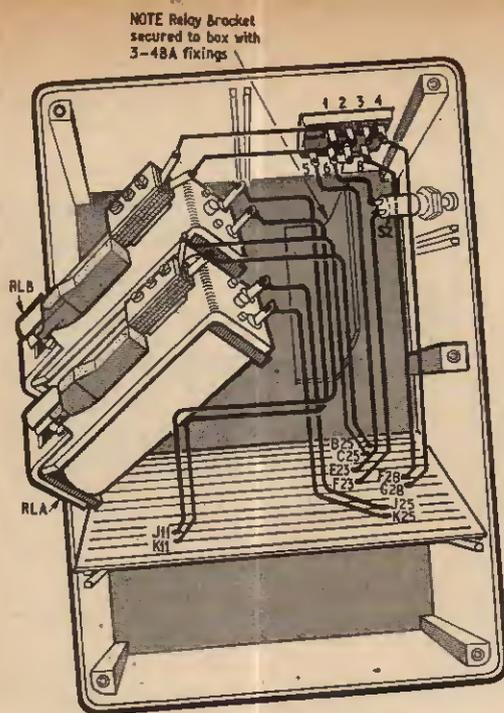


Fig. 4. Interior view of the main unit. Relays and circuit board have been moved from their normal positions to clarify the wiring details

Obviously secondary type batteries, i.e. lead acid or nickel cadmium will provide a much larger capacity, and may be preferred. Of the latter kind, the DEAC 5M6 is suitable (two will be required).

VETO SWITCH

The key operated rotary snap switch S1 is in shunt with the alarm loop and is intended to be installed outside the cabin or other protected enclosure. When S1 is closed the alarm is inoperative and hatches and doors can be opened with impunity.

When the cabin is vacated and the door locked prior to departing from the vessel, the keyswitch is turned and the key pocketed, leaving the system set up. It follows of course, that the siting of this switch should be such as to make it as inconspicuous as possible.

RESET SWITCH

If an intruder does set off the alarm the deactivation procedure on return would be to close the veto switch S1 with the key, and then press the push-to-break switch S2 which will de-energise relay RL1, so breaking the alarm contacts RLA1. Releasing this switch immediately sets the system to standby again.

CONSTRUCTIONAL DETAILS

A suitable housing for the electronic assembly is an S.T.C. diecast box slotted to take the Veroboard sub-assembly (see diagrams and photograph).

Since this box is made of an aluminium alloy it is essential to paint this with a waterproof metal primer (as used on boats) to prevent corrosion. This should be done after the unit is sealed so that the paint applied forms a barrier to corrosive influences. Technical data sheets on the choice of primers and paints applicable may be obtained by writing for relevant data sheets to British Paints Ltd., Little Ship Division, Northumberland House, 303-306 High Holborn, London, W.C.1.

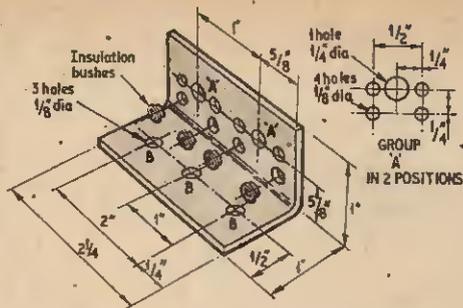


Fig. 5. Relay mounting bracket

In the relay sub-assembly, drilling of all holes in the mounting bracket should be done using the template shown as a guide. Since the circuit consists entirely of switching elements there is nothing particularly critical in the construction.

The unit should be given a functional check prior to boxing and particular care should be taken in making the breaks in the copper strip of the Veroboard at the extremes of the board, as one is sometimes inclined to do this extremely fast with a spot fact cutter and leave pieces of swarf to short adjacent strips.

LOOP CIRCUIT SWITCHES

It is recommended that linear action microswitches be used in the loop circuit as "break-in" detectors. Either the button or lever type microswitches may be used as both types can be suitably recessed for doors and hatches.

Perhaps a more economic system would be the employment of stainless steel shims arranged to operate as contact plates. Wiring to these plates would be by way of eyelet tags, the assembly being both electrically and mechanically joined by brads driven through eyelet tags and shims to the wood backing. As this was not tried in the prototype system it can only be a suggested possible alternative.

Connection to all microswitch detectors should be by miniature p.v.c. 7/40 wire. Although not as inconspicuous as thin enamelled wire, there is less likelihood of abrasion producing false alarms through short circuits if the loop wires are spliced in the run.

Since any attempt to cut wires will trigger the alarm, concealment of these wires by channelling is not really important. Any burglar who is *au fait* with alarm systems would be deterred if he was made aware of some protective guard against his intended pillaging; after all, many motorists display stickers on their windows to the effect that X's proprietary alarm system is installed—which is a daunting first line deterrent.

ACOUSTIC TRANSDUCER

The audible alarm device suggested is a v.h.f. car horn. However, since the contacts of relay RLB are heavy duty, other types of alarm may be fitted, such as a strident bell—this applies particularly if the system is adopted for home or business protection.

For the larger vessel with its own power supplies, existing hooters, marine horns, or loud hailers can be connected in the external switch circuit.

If the system is used for car protection, horn and headlights can be arranged in series with the RLB contacts. This will necessitate the use of an extra pair of contacts at the multi-pole connector PL1, SK1 for load sharing, as these contacts are only rated at 5 amps. ★



Baker "Major" loudspeaker

AUDIO FAIR PREVIEW



Garrard SL95 auto transcription turntable

By M. A. Colwell

NOW THAT stereophonic broadcasts are in full swing in the U.K. (albeit of insufficient quantity and in a limited number of areas) the manufacturers are jumping on what is now an established bandwagon. The trend to what is termed the "tuner amplifier" is spreading to include stereo.

The problem re-emerges: What is the best unit to buy? This is one question constantly being asked, and it is almost impossible to answer in a few words, because of the many and varied aspects which anyone would look into—not least of these being the capital cost.

Probably the best approach is to take advantage of free entrance facilities offered to that popular event, the Audio Festival and Fair (April 18 to 21). This year the Hotel Russell, Russell Square, London, W.C.1, will open its back doors once again to the hoards of enthusiasts who diligently sort their way through the hotel rooms looking (or should I say listening) for the ultimate in sound reproduction.

Among a plethora of equipment, no doubt, the regular visitor will find his pet subjects and the newcomer will be baffled by what may appear to him to be the old game of hunt the thimble. How best can we help him? First of all, decide before you go whether your visit will be confined to certain types of equipment or a general survey of the whole scene. Stamina could be sucked dry if you attempt to take in every single item and demonstration, so that by the time you reach the fourth floor you will be glad to go down again.

If you are set on a particular branch of the audio scene, get a catalogue—it will save quite a bit of shoe

leather. Browse through and make jottings of special interests. See the equipment on the ground floor booths; then after further jottings find your way to the demonstration rooms of your choice. The catalogue will help here again to locate these although, with a little common sense and observation of the direction arrows at strategic points, you should have no difficulty.


Now for the gear! The following is a preview of some of the equipment to be seen. It is interesting to note, during the current national prestige boosting campaign, that imported products are generally more expensive than the "home grown" varieties.

TUNER AMPLIFIERS


The "tuner amplifier" mentioned earlier is a term applied in recent years to equipment combining radio tuning and amplification. The addition of a loudspeaker (or in the case of stereo, two loudspeakers) is usually left to the choice of the user, since there is a wide variety of types at different prices according to one's requirements.

Typical examples are shown by the Sansui range. The one illustrated here is the Model 2000 stereo tuner amplifier which overcomes input matching problems by using a field effect transistor at the front end of the amplifier. Inputs are provided for tape head, pick-up, or tuner (internal) for mono or stereo listening.

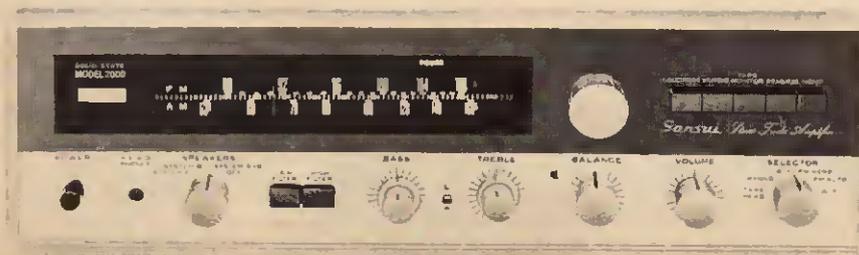Later this year the Sansui Model 3000A will be available and offers a higher power output than the current Model 3000. This is also in stereo. The importers are Technical Ceramics Limited.



Sansui Model 2000 stereo tuner amplifier

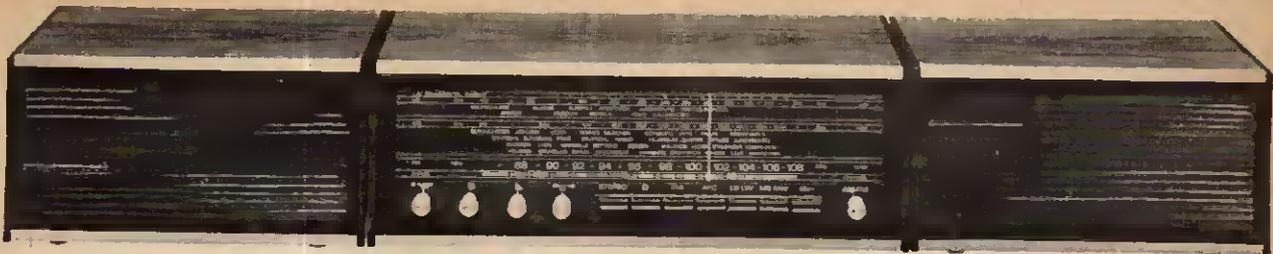

Arena stereo tuner amplifier type T1500F with two HT21 speaker units

Arena of Denmark will be introducing their new stereo tuner amplifier type T1500F through Highgate Acoustics. Modular construction has been used and it offers an output power of 6 watts per channel for input sensitivities of $10\mu\text{V}$ for a.m. and $1\mu\text{V}$ for f.m. The picture shows the unit with two matching speakers type HT21.

In addition to their current range of tuner amplifiers, the Trio Corporation of Japan are presenting a new solid state amplifier, the TK150E stereo, through their agents B. H. Morris & Co. (Radio) Ltd., a subsidiary of Lasky's Radio. The price compares modestly with the Supreme I—a 64W per channel stereo amplifier, employing separate bass, mid- and high-range amplifiers, expected to retail at £280.

Armstrong will be showing their Series 400 and Series 27 equipment which includes amplifiers, tuners, and stereo decoders.

When selecting f.m. tuners, look for a.f.c. This overcomes many drifting and fading problems often caused by intervening obstructions between transmitter and receiver, or varying atmospheric conditions.

Provisional information obtained from Rogers Developments (Electronics) Ltd., reveals a new f.m. tuner using an f.e.t. front end enabling it to handle large signals without cross modulation, while at the same time being suitable for areas of low signal strength. A.F.C. is incorporated in this model. A multiplex stereo decoder is available as an optional extra. This "Ravensbourne 2" tuner has been designed to match the "Ravensbourne" stereo amplifier.

SPEAKER UNITS

Many people have different ideas on what is the best speaker. It is largely a matter of personal choice since almost all manufacturers claim the best from their units. Look for a specification with a high flux density magnet and strong rigid frame if going for a moving coil type. Of course, it must have an impedance to match the amplifier. Excellent results are obtained with the established Quad electrostatic unit.

Well known names such as Wharfedale, Whiteley, Celestion, Goodmans, and so on, will no doubt attract

the usual audiences for comparative listening. Of course, they all use different records, pick-ups, and amplifiers, which may give slightly differing results. So it is difficult to make direct comparisons, especially when the rooms are packed with steaming bodies under the floodlights. Perhaps you may be athletic enough to dash from one room to another before the memory of what was heard first has faded.

In between the aural bliss of Satchmo and the "1812", take a look at the Titan Minor loudspeaker by Audio & Design. This uses a titanium cone on beryllium copper suspension. It is claimed to reproduce bass more efficiently than conventional types for its size. It is available housed in a cabinet $17\frac{1}{2}\text{in} \times 11\text{in} \times 8\frac{1}{2}\text{in}$. Power handling capacity is 15 watts from 40Hz to 22kHz, $\pm 4\text{dB}$.

DISC EQUIPMENT


Ancillary equipment can be added at various stages as funds permit, but it is always worth making notes at the Fair for future reference.

Pick-ups have seen some design changes in recent years and it will be interesting to see what is new. Tracking weight is frequently a subject of much confusion. Let it not be assumed automatically that the lighter the stylus pressure, the better the performance. Similarly with record wear, much depends on the design of the pick-up arm and, even more, on the true running of both turntable and disc.

Where these factors are near perfect, then one can entertain the $\frac{3}{4}$ ounce pressure, otherwise there is the risk of groove jumping on less accurate turntables and discs. Pick-up arms should be very free moving both horizontally and vertically.

Of unusual design, the Shure M75E-95G "Guard-a-Matic" Hi-Track cartridge, is designed specifically for the new Garrard SL95 transcription turntable (see later). The performance is equivalent to that of the M75E but with a retractile safety suspension system, claimed to provide scratch-proof, bounce-proof operation where floor vibration is a problem. Shure also

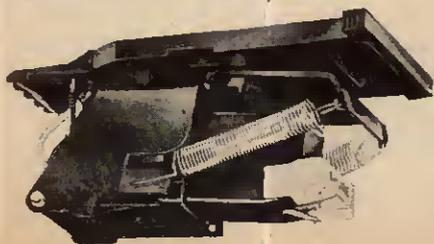Shure M75E-95G "Guard-a-Matic" cartridge with suspension system



Rogers "Ravensbourne 2" f.m. tuner



announce new models in the "economy" range of cartridges. The M31E and M32E have elliptical tipped styli for tracking at 1-2gm and 2½-5gm respectively.

Audio & Design are introducing a stereo "induced field" cartridge with an output of 0.9mV per cm/sec. It uses an elliptical tipped stylus and is intended for feeding into high impedance inputs.

Cosmocord have developed another version of the stereo compatible cartridge announced last year. The Acos GP91SC incorporates a mono crystal for mono or stereo records. The stylus is suspended on a flexible plastics arm so that it will track stereo grooves, while reproducing a mono signal. It is available in three versions with outputs of 200, 350, or 640mV at 1.2cm/sec.

The Goldring Model GL75 transcription unit, with "free field" stereo magnetic cartridge, maintains the tradition of their using variable speed motor units. The new pick-up arm has a sliding counter balance to calibrate stylus pressure, and can be raised or lowered hydraulically on to the disc by operating a simple lever.

Garrard equipment at a more modest price include the AP75 single record player, Models SL95 and SL75 auto transcription turntables and the Model 3500 auto turntable, with a low mass pick-up arm, and cue and pause control.

The Model SL95 features "gimbal-type" pick-up arm pivots; the arm has afromosa wood set into aluminium for low frequency resonance damping. The record platform can be pushed down out of the way for single play operation.

Following some suggestions made to B.S.R. they have now superseded the UA70 with a new Model UA75, which uses a heavy cast alloy machined turntable.

TAPE RECORDERS

Probably the most interesting news in the tape recording field is from Ferrograph. After 18 years of pounding on their "Tape Deck" (which was originally registered as a trade mark), with very little alteration to the basic design, they have decided to up-date the appearance and construction to the sleek squarish model basic to the new Series 7.

The electronics are similarly up-dated to all solid state silicon devices, including f.e.t. input stages. The machine can be used horizontally or vertically with easy

access to the electronic units. A time switch is incorporated for preset starting without the need for it to be previously powered. Several other features are to be found, based on principles in its forerunners. Pre-record facilities for multi-play echo will be found on stereo models, which are supplied with either half- or quarter-track heads.

For another example of a professional studio tape recorder, look out for the BTR4 by E.M.I. Its complementary portable recorder the L4, with film sync facilities is popular for field work among professionals and amateurs.

The latest Brenell deck, Mark 5 Series 3, will be on show; features of this model include a self-compensating braking system, and space for accommodating up to four heads for mono or stereo.

ACCESSORIES

Microphones for mono or stereo will be in abundance, including the MD409, and MD415 by Sennheiser (through Audio Engineering), specially designed for "pop" group vocalists. Both have anti-feedback properties and the bass response is tailored for close microphone technique.

The same Company is also demonstrating a new pair of stereo headphones, HD414, for those audiophiles who want personal listening while the wife watches the television.

The well known range of Shure microphones is to be supplemented by the Unidyne IV series, Models 548 (mono) and 548s (stereo). These are designed for professional applications and are fitted with Cannon type connectors.

Finally, a word of advice. Don't arrive at the doors without a ticket or you may not get in. Tickets can be obtained free of charge through your local hi fi dealer or from the organisers of the Audio Festival and Fair, 42 Manchester Street, London, W.1. (include a stamped addressed envelope). ★


Ferrograph Series 7 stereo recorder

Goldring GL75 transcription unit with lever operated pick-up arm



TRANSISTOR CURVE TRACER

By G.K. FAIRFIELD

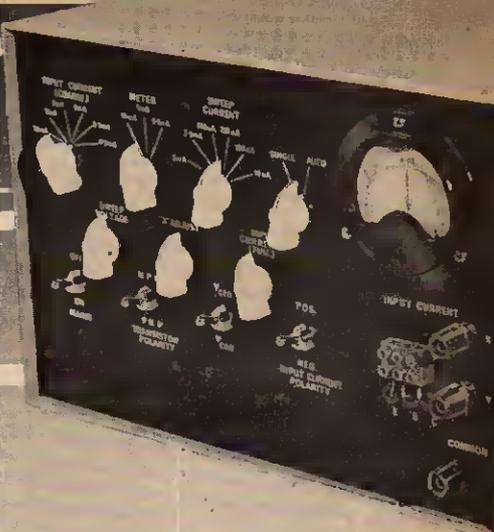

THE most useful test for a transistor is to plot its complete range of input/output characteristics. Not only will this show up the transistor limitations but a great deal of useful information can be derived from a study of the curves.

These characteristics can be produced by making measurements point-by-point using meters to indicate the value of currents flowing. However, this "static" method is subject to a number of serious limitations, the most important of which is the overheating and possible destruction of the transistor when measurements are attempted at the higher current end of its characteristics.

A much better method is to allow the transistor to reach its high current values for only a very short period of time. This is called the "dynamic" method and to use it a cathode-ray oscilloscope must be used to display the transistor characteristics.

This article describes a unit which may be connected to almost any conventional oscilloscope in order to display the transistor characteristics. Single curves can be shown and arrangements are included to permit "families" of ten or more curves to be displayed.

METHOD OF TESTING

The basic technique is shown in Fig. 1. Half sine waves of voltage are applied to the collector of the transistor from a mains transformer via a load resistance R_L and rectifier D1. A constant bias current is fed to the transistor input through switch S1, either to the base or the emitter depending upon whether common-base or common-emitter curves are required.

A voltage proportional to the collector current (I_C) is developed across the load resistance R_L and applied to the Y-plates of the oscilloscope. The collector voltage V_C is applied to the X-plates.

Thus as the voltage V_C varies from zero to the peak of the half sine wave, so the current I_C changes due to the non-linear characteristics of the transistor. The I_C/V_C transistor characteristic is plotted on the c.r.o. screen.

Since the transistor is put through this cycle of applied collector voltage change at a rate of 50 times per second (actually 100 times if the reverse change of V_C is also used as in Fig. 1) then a clear trace of this characteristic is maintained on the face of the tube. This curve is, of course, applicable to the particular bias current chosen which depends on V_{BE} and the value of bias resistor R_b . To plot a series of such curves it is only necessary to change the value of R_b in steps, allowing one complete curve to be traced for each fixed value of R_b .

With the simple arrangement of Fig. 1 it is possible to plot I_C/V_C curves for common-emitter or common-base configurations by suitable settings of S1. Both *pnp* and *npn* transistors can be tested by choosing the correct polarity of half-sine wave obtained by the appropriate setting of a reversing switch S2, connected to the rectifier D1.

In order to convert this circuit into a practical arrangement it is necessary to add a means of changing the

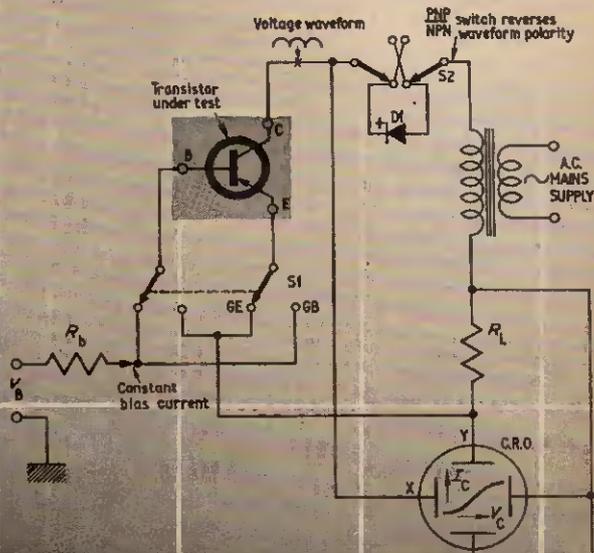


Fig. 1. Basic idea of the display system

value of R_b between each curve traced in order that multiple curves can be displayed. It will also be necessary to include a cathode follower (or emitter follower) between the X output of the circuit and the oscilloscope in order to avoid loading the high impedance collector circuit. This is particularly important when common base curves are to be displayed. Several different collector voltage and current ranges will be required to accommodate all the transistors that are likely to be tested.

PLOTTING FAMILIES OF CURVES

A convenient number of curves to produce a useful "family" is about ten. These curves will be traced one by one and in order to see them all together on the oscilloscope screen it will be necessary to repeat them fairly regularly (or alternatively a cathode-ray tube could be used having a very long persistence phosphor screen). What is required is a rapid single-pole ten-way switch stepping on automatically and continuously to repeat its sequence of ten positions. A Post Office type uniselector switch meets this specification admirably. For those not familiar with this device a brief description will not be out of place. Refer to Fig. 2.

The uniselector switch is operated by applying a pulse through the coil which pulls down an armature carrying a claw to engage on the ratchet wheel. This wheel is attached to the wiper arms of the switch; the fixed contacts are arranged in a semi-circle around the switch arm. Thus each applied pulse rotates the switch arm by one position and engages with the next fixed contact.

Many versions of the uniselector are available and can generally be adapted for our purpose. A number of parallel banks of switch contacts are usually found and three will be required for the Curve Tracer. A standard type of driving coil is one requiring 50 volts to initiate a switch operation. Other types may be found and the driving voltage can be changed or coil rewound to accommodate a different design. The one used in the prototype had a 75 ohm coil.

FINAL CIRCUIT

The complete circuit is shown in Fig. 3. A stabilised power supply is included which uses two 150V reference tubes V1 and V2. This supplies the constant voltage source for the base current determining network, and also voltage supplies for the cathode follower V3 driving the X-plates of the oscilloscope.

A five-pole, two-way switch S8 enables either a single curve to be traced or a family of characteristics displayed. (S is for a single sweep display; A is for auto-repetition.) It is convenient to commence our description of the curve tracer by considering switch S8 to be in the "single" position.

The appropriate polarity of base current is selected by switch S5 (generally negative for *pnp* and positive for *nnp* transistors, although a reverse characteristic may be required sometimes).

The reference voltage is applied to a potentiometer network S6 which allows a selection of input currents covering the range 10mA, 5mA, 2mA, 1mA, 500 μ A, and 200 μ A, depending on the switch position. Fine control of input current for a single trace is provided by potentiometer VR2, which can be calibrated 0-1, 0-2, and 0-5 if desired, to correspond with the choice of range available.

A meter is also included in the circuit to measure the exact value of current supplied to the base. This has current shunt resistors, wound to give full-scale deflection of 10, 1, and 0.1mA. The current passing

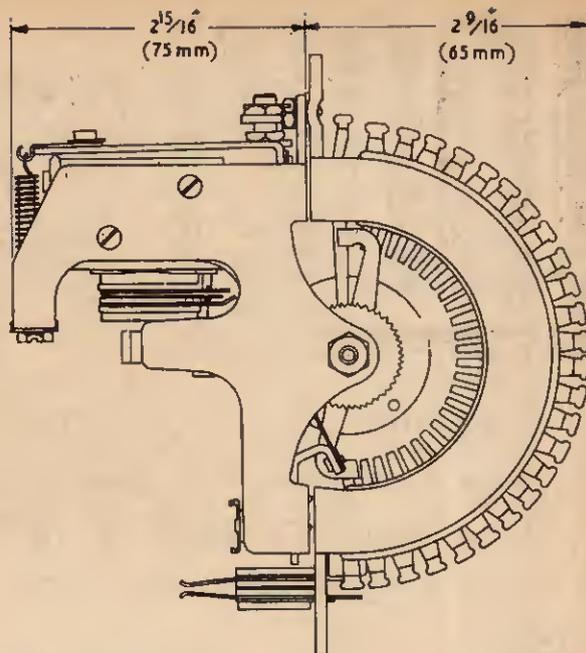


Fig. 2. Side view of uniselector; the armature is at top left above the coil

through the meter is direct current; a full-wave bridge rectifier has been included in the circuit. This is to avoid changing connections to the meter when the polarity of the input voltage is reversed by S8. If desired this bridge can be omitted and its place taken by a reversing switch similar to that shown for S2.

The configuration of the transistor undergoing test is selected by means of S4. This permits the current set by VR2 to be applied to the base or emitter depending upon whether it is desired to display the grounded emitter or grounded base characteristic.

The collector voltage is a rectified sine wave supplied via D3 from the 50V secondary of a mains transformer. The maximum amplitude of this sweep voltage is controlled by the setting of potentiometer VR1. The polarity of the sweep voltage is selected by S2 to suit either *pnp* or *nnp* transistors.

The sweep voltage is also applied via the cathode follower V3 to the X-plate of the oscilloscope tube. A preset adjustment VR3 is provided in V3 cathode circuit to give zero adjustment.

The current axis voltage, representing the change in collector voltage as the transistor collector potential is swept through its range of values, is taken from across a resistor, selected by S3, and fed to the Y-axis terminal of the oscilloscope tube.

Six current ranges are provided for maximum currents of approximately 5mA, 2.5mA, 500 μ A, 250 μ A, 100 μ A, and 10 μ A, depending on the position of S3. Resistor R7 is included to complete the circuit and prevent a surge in current which would otherwise occur each time S3 was moved to a new position.

When switch S8 is moved to the "auto" position, the uniselector is brought into action. Instead of the value of the input current being set by the position of VR2, a set of resistors, R26 to R34, are sequentially brought into circuit as the uniselector is stepped round to each of its contact positions in turn.

A separate curve is displayed during the time that the uniselector is stationary and a particular resistance

LOOK!

PRACTICAL!

VISUAL!


EXCITING!



a new 4-way method of mastering
ELECTRONICS
 by doing — and — seeing . . .


1 ▶ **OWN and HANDLE a**

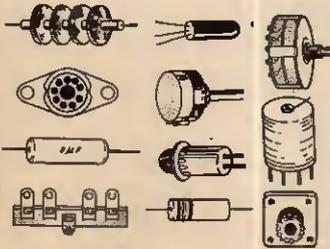complete range of present-day **ELECTRONIC PARTS and COMPONENTS**




2 ▶ **BUILD and USE**

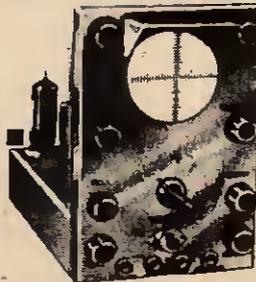a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ **READ and DRAW and**

UNDERSTAND CIRCUIT DIAGRAMS

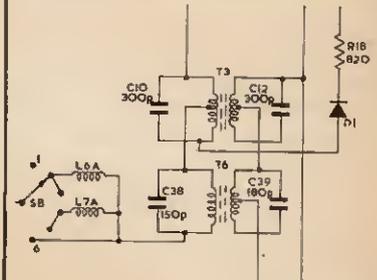

4 ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
 for
 BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE PE 5

VARIABLE VOLTAGE TRANSFORMERS



450
AMPS



PORTABLE TYPE
£9. 5. 0.

INPUT 230/240v. A.C. 50/60
OUTPUT VARIABLE 0-260v.
BRAND NEW
Keenest prices in the country.
All Types (and Spares) from
½ to 50 amp. from stock.

SHROUDED TYPE
1 amp, £5. 10. 0. 2.5 amps,
£6. 15. 0. 4 amps, £9. 0. 0.
5 amps, £9. 15. 0. 8 amps,
£14. 10. 0. 10 amps, £18. 10. 0.
12 amps, £21. 0. 0. 15 amps,
£25. 0. 0. 20 amps, £37. 0. 0.
37.5 amps, £72. 0. 0. 50 amps,
£92. 0. 0.

OPEN TYPE (Panel Mounting)
1 amp, £3. 10. 0. 1 amp, £5. 10. 0.
2½ amps, £6. 12. 6.

PORTABLE TYPE
1.5 amp. portable fitted metal case,
voltage, lamp, switch, etc. £9.5.0.
Similar to above 2.5 amp. £11.7.6.

100 WATT POWER RHEOSTATS (NEW)

AVAILABLE IN THE FOLLOWING VALUES

1 ohm, 10 a.; 5 ohm, 4.7 a.; 10 ohm, 3 a.;
15 ohm, 2 a.; 50 ohm, 1.4 a.; 100 ohm, 1 a.;
250 ohm, .7 a.; 500 ohm, .45 a.; 1,000 ohm,
280 mA; 1,500 ohm, 230 mA; 2,500 ohm, .2 a. Diameter
¾ in. Shaft length ¾ in., dia. ¼ in. All at 27/6 each.
P. & P. 1/6.

50 WATT. 1/5/10/25/50/100/250/500/1,000/1,500/2,500
ohm, 21/-. P. & P. 1/6.
25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500
ohm, 14/6. P. & P. 1/6.

VENNER ELECTRIC TIME SWITCH

200-250 v. A.C. 20 amp. contacts twice on,
twice off, at any manually pre-set time.
Spring reserve (in case of power cut) fully
tested £3/19/6. P. & P. 4/6. Or complete
in weatherproof metal case (illustrated)
£3/19/6, plus 4/6 P. & P. Can be supplied
with solar dial, on at dusk off at dawn.
Prices as above.

AIR BLOWER

Highly efficient blower unit fitted with
totally enclosed 200/250 v. A.C. 50 cycles,
¾ h.p. motor producing 2,800 r.p.m.
Outlet 2½" x 1½", used, but in first class con-
dition and tested. Price £3/15/-. P. & P. 7/6.

230/250V. A.C. SOLENOID

Heavy duty type, approx. 3 lbs. pull. Price:
17/6 plus 2/6 P. & P.

12/24V. D.C. SOLENOID

Approx. 8 oz. push. Price 8/6 plus 1/6 P. & P.

PRECISION INTERVAL TIMER

From 0-30 seconds (repetitive). Jewelled
balanced movement. Lever re-set.
Operates 230V. A.C. 5 amp. c/o Micro-
switch. New. Price 17/6 plus 2/6 P. & P.

CONDENSER 4,000 mfd 25v. 10/6 plus 1/6 P. & P.

CONSTANT VOLTAGE TRANSFORMER

Input 185-250 v. A.C. Output 230 v. A.C.
Capacity 250 watt. Attractive metal case.
Fitted red signal lamp. Rubber feet.
Weight 17 lb. Price £11/10/0. P. & P. 15/-.
P. & P. 1/6.

PHOTO MULTIPLIER. Type CV337. This super-
sensitive type 931A. Complete with special P.T.F.E. base
and divider network. 57/6 incl. P. & P.

RADIO ALTIMETER

This precision instrument, built
to highest Ministry specification, is based on a 24 v. D.C.
LOW INERTIA Integrating Motor. The Motor, fitted
with gold brushes and drawing only 800 microamp at
24 v. D.C., drives two precision pots with platinum
wipers through close tolerance gear-trains, including
miniature slipping clutch, combined with two sub-
miniature pots for calibrating the electrical bridge
circuit. The 3 in. calibrated dial, with a number
aperture indicating one rev. per revolution of pointer
with maximum of 5 revs. gives an effective scale length
of approx. 30 in. Offered at fraction of Manufacturer's
price, 32/6. P. & P. 6/-.

LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cad-
mium Sulphide Photocell, Relay,
Transistor and Circuit, etc., 6-12
volt D.C. op. price 25/- plus 2/6
P. & P. ORP 12 including circuit,
10/6 each, plus 1/- P. & P.

A.C. MAINS MODEL Incorporates
Mains Transformer, Rectifier and special
relay with 3, 5 amp. mains c/o contacts.
Price inc. circuit 47/6 plus 2/6 P. & P.

LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered
light source with focusible-
lens assembly and ventilated
lamp housing, to take MBC bulb. Separate
photo cell mounting assembly for ORP. 12
or similar cell. Both units are single hole
fixing. Price per pair £2.15.0. P. & P. 3/6.

**RESETTABLE HIGH SPEED
COUNTER.** 4 figure, 1,000 ohm coil,
36 48 v. D.C. operation. £3/10/-. P. & P.
1/6. 3 figure, 24 v. D.C. £1/12/6.
P. & P. 1/6.

DRY READ SWITCHES. New
special offer of Dry Read Switches half
amp. Contact. Size 1¼ x ¾. 4 for 10/-
Post Paid.

MINIATURE UNISELECTOR SWITCH

3 banks of 11 positions plus
homing bank. 40 ohm coil.
24-36 v. D.C. operation.
Tested, 22/6, plus 2/6 P. & P.

COMPACT HEAVY DUTY 6v. D.C. RELAY
2 change over, 30 ohm coil. 7/6 each.
P. & P. 1/6. 3 for 20/-. Post paid.

NICKEL CADMIUM BATTERY

Sintered Cadmium Type 1-2 v. 7AH.
Size: height 3½ in., width 2½ x 1½ in.
Weight: approx. 13 oz. Ex-R.A.F.
Tested. 12/6. P. & P. 2/6.

SANWA MULTI RANGE METERS

New Model U50D Multi tester,
20,000 OPV, mirror scaled with overload
protection. Ranges - d.c. volts: 100mV,
0-5 v. 5 v., 250 v., 1,000 v.; a.c. volts:
2-5 v., 10 v., 50 v., 250 v., 1,000 v.; D.C.
current: 5 µA, 0.5 MA, 5 MA, 50MA,
250 MA. Complete with battery and test
probe. £7/5/0 post paid. Three other
models available from stock. Descriptive
leaflet on request.

THYRISTOR 400 piv, 5 amp., 14/6
THYRISTOR 400 piv, 8 amp., 28/6

220/240 v. A.C. FAN UNIT

2,300 r.p.m. 6" blade size.
Smooth powerful motor.
All metal construction.
Continuously rated.
Individually tested.
Offered at fraction of
maker's price. £2.15.0.
P. & P. 7/6

SANGAMO WESTON

Dual range voltmeter. 0-5
and 0-100 v. D.C. FSD 1 m/a.
In carrying case with test
prods and leads, 32/6, P. &
P. 3/6.

A.C. CONTACTOR

2 make - 2 break (or, 2
c/o.). 15 amp. contacts.
230/240V. A.C. operation.
Brand new. Price 22/6 plus
1/6 P. & P.

20 Amp LEVER MICRO SWITCH

Brand new lever operated
Micro Switch, 20 amp. A.C.
c/o contacts. Price 4/6 each
plus 1/6 P. & P. 5 for £1
Post Paid.

COLOUR TELEVISION

With particular reference to the
PAL SYSTEM

There are 157 diagrams and photographs and
83 illustrations in colour.

by G. N. Patchett

40/- Postage 1/-

**MODERN TAPE RECORDING AND
HI-FI**, by K. Peters. 30/- Postage 1/-.

PAL COLOUR T.V., by Mullard. 12/6.
Postage 1/-.

**PRACTICAL WIRELESS SERVICE
MANUAL**, Pub. Newnes. 25/- Postage
1/-.

ELECTRONIC COUNTING,
by Mullard. 27/6. Postage 1/-.

**BASIC THEORY & APPLICATION
OF TRANSISTORS**, U.S. Dept. of Army.
12/- Postage 1/-.

RADIO VALVE DATA, 8th ed. compiled
by "WV". 9/6. Postage 1/-.

**TRANSISTOR SUBSTITUTION
HANDBOOK**, Pub. F. Sams. 15/- Post-
age 1/-.



THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
British and American Technical Books
19-21 PRAED STREET
LONDON, W.2

Phone: PADdington 4185

NEW
FROM

OLSON

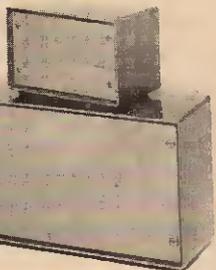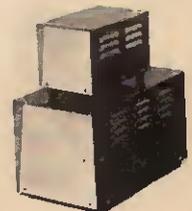

INSTRUMENT CASES AND CHASSIS

27 sizes and styles

OLSON ELECTRONICS Ltd.
Factory No. 8 5-7 LONG STREET
LONDON, E.2. Telephone 01-739 2343

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
57 BRIDGMAN ROAD, LONDON, W.4 Phone 995 1560
SHOWROOM NOW OPEN CLOSED SATURDAY

Personal callers only
9 LITTLE NEWPORT ST.
LONDON, W.C.2. Tel. GER 0576

CIRCUIT DIAGRAM

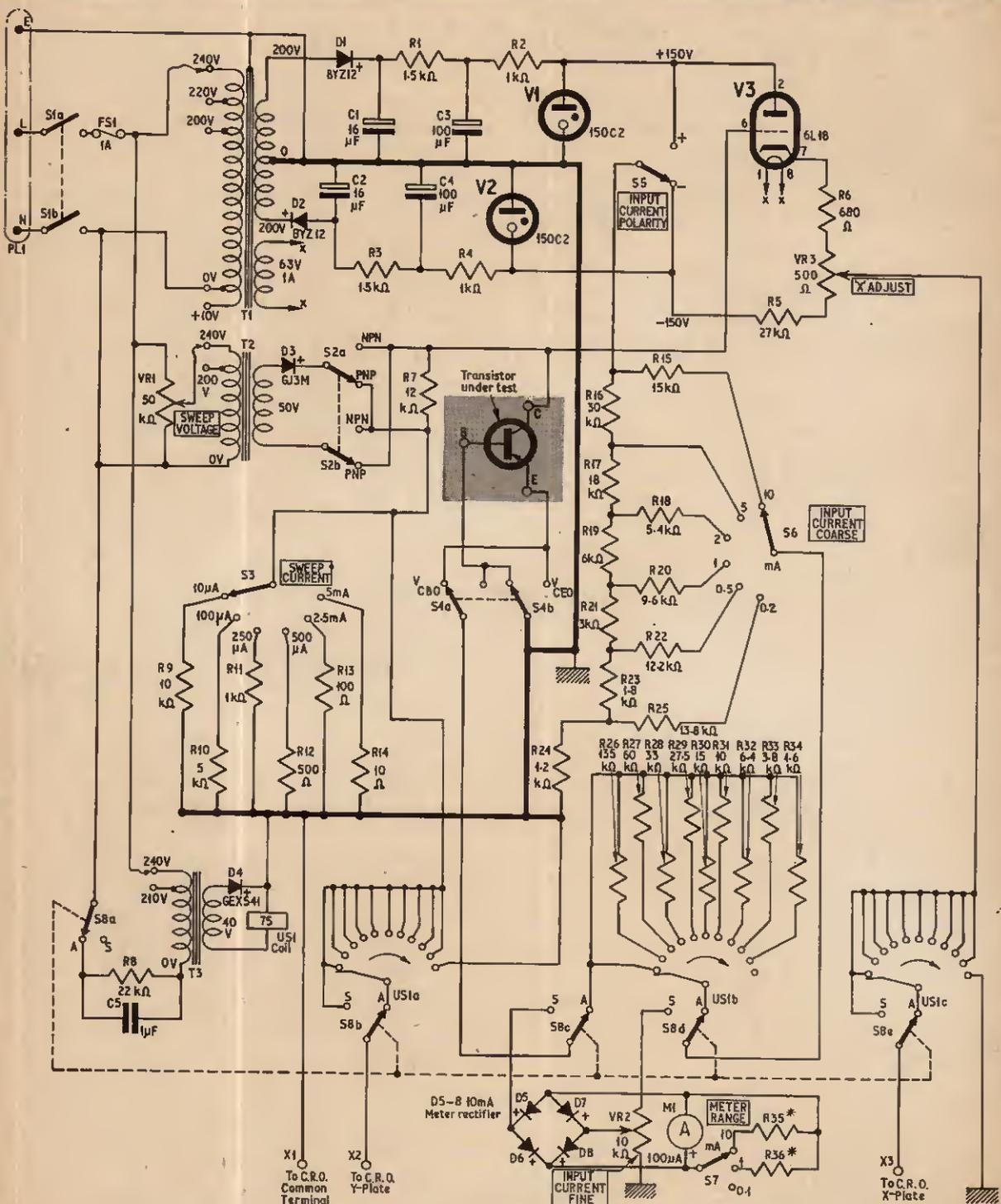


Fig. 3. The complete circuit of the curve tracer for connection to a d.c. oscilloscope



is in the circuit. The uniselector is automatically stepped on to the next position and a second curve is displayed. The process then repeats and the whole cycle repeats every 200ms. This is sufficiently rapid to give the illusion of a stationary set of curves being displayed on the screen simultaneously.

The uniselector is energised from the 40V secondary winding of a mains transformer T3 via rectifier D4.

COMPONENTS . . .

Resistors

R1	1.5k Ω	R13	100 Ω	*R25	13.8k Ω
R2	1k Ω	R14	10 Ω	*R26	135k Ω
R3	1.5k Ω	R15	15k Ω	*R27	60k Ω
R4	1k Ω	*R16	30k Ω	R28	33k Ω
R5	27k Ω	R17	18k Ω	R29	27k Ω
R6	680 Ω	*R18	5.4k Ω	R30	15k Ω
R7	12k Ω 5%	*R19	6k Ω	R31	10k Ω
R8	22k Ω 1W	*R20	9.6k Ω	*R32	6.4k Ω
R9	10k Ω	*R21	3k Ω	*R33	3.8k Ω
*R10	5k Ω	*R22	12.2k Ω	*R34	1.6k Ω
R11	1k Ω	R23	1.8k Ω	R35, 36	(see text)
*R12	500 Ω	R24	1.2k Ω		

All 10%, $\frac{1}{2}$ watt except R7, R8, R35 and R36
Resistors marked with an asterisk are not standard preferred values and should be selected from nearest preferred values, or made up from combination of two resistors to give each required value. See Table 1

Potentiometers

VR1	50k Ω linear carbon
VR2	10k Ω linear wirewound
VR3	500 Ω linear wirewound

Capacitors

C1	16 μ F elect. 450V	C3	100 μ F elect. 450V
C2	16 μ F elect. 450V	C4	100 μ F elect. 450V

Transformers

- T1 Mains transformer (Parmeko type P2752)
Pri.: +10, 0, 200, 220, 240V;
Sec. 1: 200-0-200V 75mA; Sec. 2: 6.3V 1A;
Sec. 3: 6.3V 2A; Sec. 4: 6.3V 1A
(Sec. 3 and sec. 4 are not used in this circuit)
- T2 Mains transformer (Douglas type MT 102AT)
Pri.: 0, 210, 240V
Sec.: 0, 19, 25, 33, 40, 50V 0.5A (Sec. 0-50V used for T2)
- T3 Same as T2 but Sec. 0-40V used

Valves

V1	Gas filled stabiliser type 150C2	V3	6L18 triode
V2	Same as V1		

The primary of this transformer is connected to the mains supply via one of the arms of the switch S8a. A time-constant (C5, R8) is included in the primary circuit in order to phase the application of an operating pulse to the uniselector to correspond to the half cycle when the collector sweep is inoperative.

COMPONENTS

It is appropriate to mention some of the components used in the instrument. The majority of them are easily obtained, but it may be necessary to select values of some resistors by measurement of a batch of the nearest preferred nominal types. Others will need to be made up by combinations of suitable values, these being indicated in the components list and in Table 1.

Resistors R35 and R36 are made from resistance wire (eureka or nichrome) to give the required values to indicate 10mA and 1mA f.s.d. on the meter. The thinner the wire used, the shorter its length need be. It can be wound on any insulating former to hand. If the wire obtained is not insulated make sure that adjacent turns do not touch; it is probably a good idea to deposit molten wax on the finished article to keep the wire firmly in place.

As an example, 38 s.w.g. eureka wire has a resistance of 23.8 ohms per yard or 1.5 inches measures one ohm.

Diodes

D1	BYZ12 or SJ403
D2	BYZ12 or SJ403
D3	GJ3M
D4	GEX541
D5-8	Meter bridge rectifier 10mA

Meter

M1	0-100 μ A moving coil
----	---------------------------

Fuse

FS1	1A chassis or panel mounting fuseholder
-----	---

Switches

- S1 Double-pole, on/off, toggle
S2 Double-pole, changeover, toggle
S3 2-pole, 6-way wafer (only 1 pole is used)
S4 Double-pole, changeover, toggle
S5 Single-pole, changeover, toggle
S6 2-pole, 6-way wafer (only 1 pole is used)
S7 Single-pole, 12-way wafer (only 3 ways are used) or 4-pole, 3-way (only 1 pole is used)
S8 6-pole, 2-way (only 5 poles are used)

Uniselector switch

US1	3 or 4 banks, each 25 ways, coil resistance 75 Ω
-----	---

Terminals

X1, X2, X3	Screw terminals (3 off)
------------	-------------------------

Plug and socket

PL1	Mains plug, chassis mounting, type P73
-----	--

Miscellaneous

- Chassis 10in \times 7in \times 2in or made from aluminium sheet 14in \times 11in 18 s.w.g.
Plywood or aluminium sheet for case 12in \times 8in \times 8in internal dimensions
Clamps and insulation for C3 and C4 (2 off)
Valveholders, B7G (2 off); B8A (1 off)
Tags boards, double, 18-way, 12-way, and 7-way
Tag strip, single, 5-way
Brackets for 18-way tag board
Pillars, 2 $\frac{1}{2}$ in long, for 12-way tag board
Grommets; 3-way terminal block
Seven knobs, nuts and bolts, wire

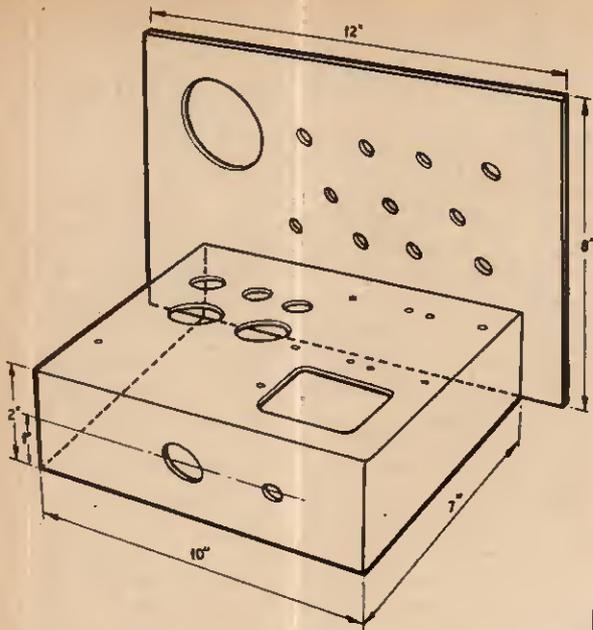


Table I: NON-STANDARD RESISTOR COMBINATIONS

Resistor	Required value	Combination
R10	5k Ω	10k Ω + 10k Ω in parallel
R12	500 Ω	1k Ω + 1k Ω in parallel
R16	30k Ω	15k Ω + 15k Ω in series
R18	5.4k Ω	2.7k Ω + 2.7k Ω in series
R19	6k Ω	12k Ω + 12k Ω in parallel
R20	9.6k Ω	6.8k Ω + 2.7k Ω in series
R21	3k Ω	1.5k Ω + 1.5k Ω in series
R22	12.2k Ω	12k Ω nominal selected by measurement
R25	13.8k Ω	56k Ω + 18k Ω in parallel
R26	135k Ω	560k Ω + 180k Ω in parallel
R27	60k Ω	120k Ω + 120k Ω in parallel
R32	6.4k Ω	33k Ω + 8.2k Ω in parallel
R33	3.8k Ω	8.2k Ω + 6.8k Ω in parallel
R34	1.6k Ω	5.6k Ω + 2.2k Ω in parallel

Fig. 4. Front panel and chassis assembled. Hole sizes and positions will depend on the components actually obtained, but the wiring diagrams in Figs. 5, 6, and 7 appear half scale and give a reasonable guide to positions

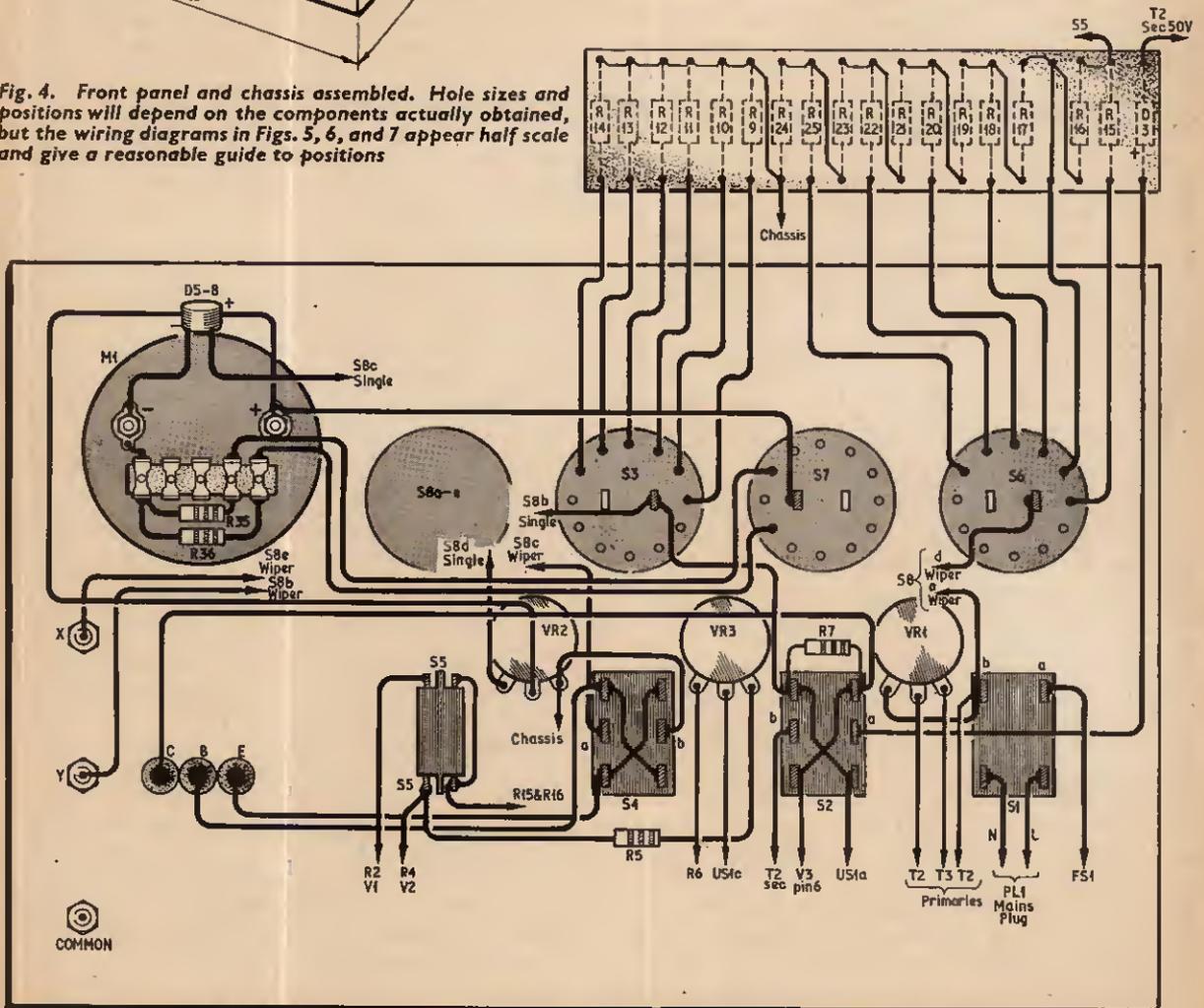


Fig. 5. Wiring the components on the front panel. The component group board is tilted up to show connections, but is in fact fitted to brackets on the front panel. This drawing appears approximately half scale

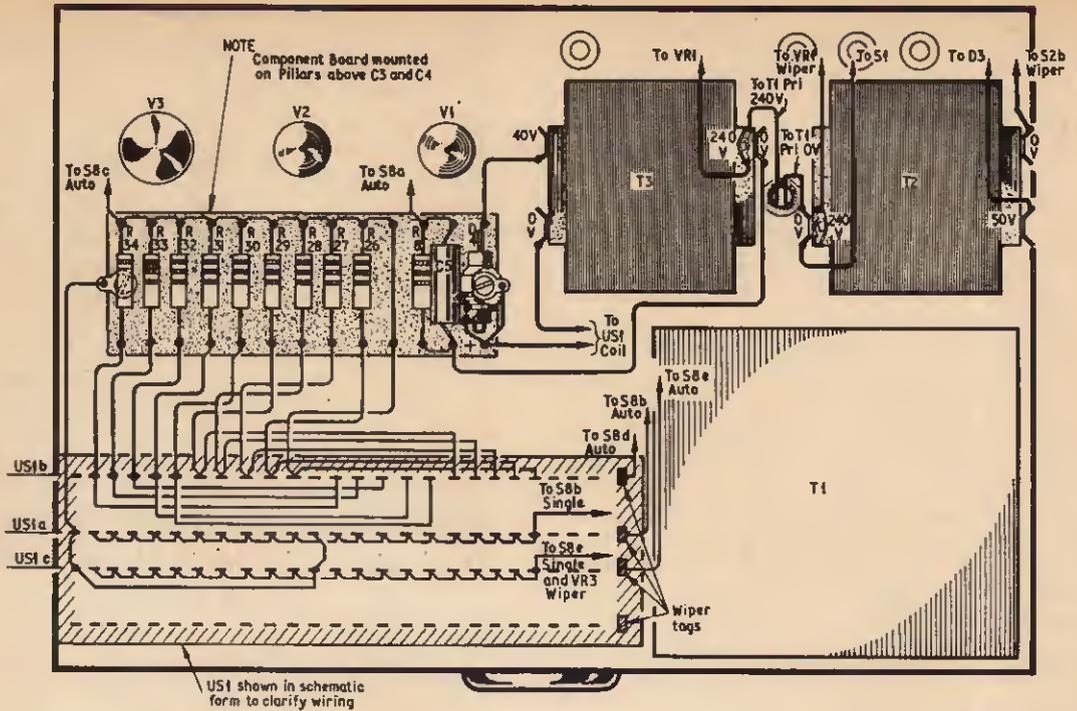


Fig. 6. Top side wiring of the chassis. Each dash on the uniselector represents an outlet tag; the wiper is at the right hand end and coil connections underneath (not visible here). The uniselector is mounted on pillars above the chassis. C3 and C4 are underneath the group board. This drawing appears half scale

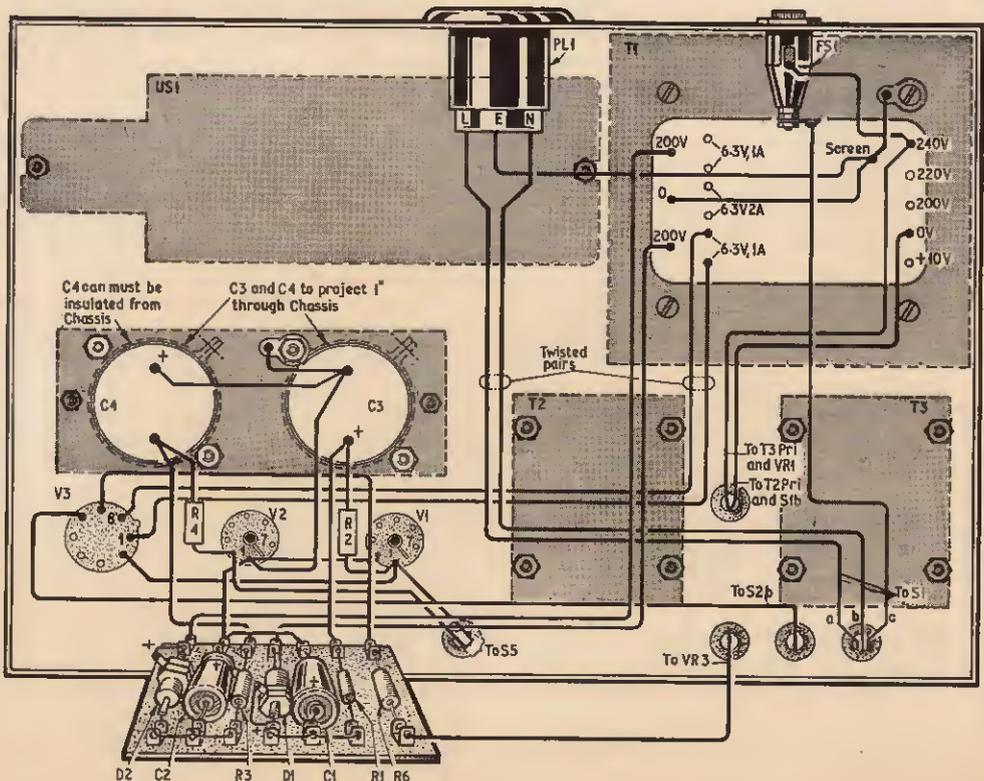


Fig. 7. Underside wiring of the chassis. The group board is tilted to show the component wiring clearly

Do not allow the wire to become stretched or the resistance will increase per unit length. The values of resistance needed for R35 and R36 will depend on the d.c. resistance of the meter coil. These can be calculated from the formula:

$$R_S = \frac{R_M \times I_M}{I_S - I_M}$$

where R_S is the shunt resistance required,
 R_M is the meter resistance,
 I_S is the current scale required,
 I_M is the nominal current rating of the meter (in this case $100\mu\text{A}$).

When making the calculation, resistances are in ohms and currents in amperes, so allowance must be made for the multiple and sub-multiple signs.

Capacitors C1 and C2 are tubular types and usually insulated. In any case the can of C2 must not be connected to chassis. C3 and C4 are the kind that have to be mounted vertically on the chassis, but here again the can of C4 must not be connected to chassis. It can be wrapped with plastics insulating tape.

The transformers have been selected as being readily available types. T1 has three 6.3V windings but only one is used for V3 heater. If desired, one of the other 6.3V windings can be used to supply a panel bulb, although this is not shown.

The diodes originally used were AEI types SJ403 but it may be easier to obtain the Mullard BYZ12, which has a substantially higher current rating.

The wafer switches are pre-assembled types that can be bought for a reasonable sum, but S8 may have to be a slightly more expensive "Yaxley" or "Maka-switch" type.

The uniselector switch is obtainable at many surplus stores. At least three banks are required and a 75Ω coil. Check the action of this component before buying to make sure that the wipers ride smoothly through the arc of contacts. This can be done by pressing the armature several times. No parts should be damaged otherwise operation may be intermittent. The uniselector has 25 ways; two series of 11 contacts on each bank are paralleled.

FRONT PANEL

Front panel mounting position is given in Fig. 4 with the wiring below it (Fig. 5). The wiring to S8 has been abbreviated in the interests of clarity, but it should not be difficult to ascertain the appropriate tags if wiring to them is followed in alphabetical sequence, from a pre-determined starting pole, in counter-clockwise fashion.


The "common" terminal on the front panel must make either direct connection to the panel (if metallic), or wired to a chassis connection.

Resistors for connection to S3 and S6 are mounted on an 18-way group tag board, which is fitted to the top of the front panel by right-angle brackets. If the resistors are uppermost, minor alterations to their values can be achieved *in situ* while the instrument is operating.

CHASSIS CONSTRUCTION

Drilling details of the chassis are not given because some adjustment may be necessary according to the components acquired. However, the top and underside wiring diagrams of the prototype (Figs. 6 and 7) are drawn to scale to give reasonable indication of the positions of the components.

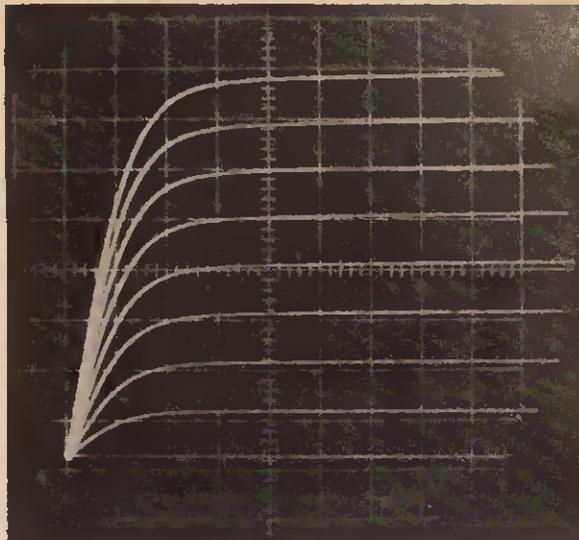Transformer T1 is mounted so that the turret tags project through the chassis for connection underneath.



Photograph of a family of I_C/V_C curves displayed on an oscilloscope

If there are "screen" tags on the transformers these must be connected to chassis.

The main power supply components are mounted on a group tag board under the chassis, while C3 and C4 are fitted (as mentioned previously) to clamps on the chassis. It may prove to be helpful to make the holes for these large enough so that they can project through to about one inch below the chassis top.

A 12-way group board is mounted on pillars above these two capacitors to take the resistors for US1b. Here again, easy access is achieved for alteration of component values.

Finally, before going on to the operation, a word of warning: if it is necessary to make alterations while the instrument is switched on, be careful where you put your fingers and soldering iron. Components on the front panel, as well as T2 and T3 carry exposed live mains.

OPERATION

The curve tracer must be used in conjunction with a directly coupled (d.c.) oscilloscope. The time base must be capable of being switched out of circuit and a d.c. amplifier substituted in its place. Not all oscilloscopes have this facility and it may be necessary to add an amplifier to the design of the unit. It need only have a modest gain of about a hundred times and quite a small bandwidth and could derive its power from the supply incorporated within the unit.

The type of display obtained is shown in the photograph. The illuminated graticule shown in the photograph was made from $\frac{1}{2}$ in perspex placed immediately in front of the oscilloscope screen. Edge lighting through one edge of the perspex by means of a low power bulb will light up the scribed scale lines. This graticule was found useful in calibrating the curves displayed on the screen.

The photograph shows the I_C/V_C characteristic of a low gain *npn* transistor having increasing values of reverse base bias. The ninth and tenth bias values bring the transistor into its cut-off region and consequently only a single straight line is traced for both steps.

★

ELECTRONIC CYMBALS

By A.J. BASSETT

PERCUSSION EFFECTS

THERE ARE two kinds of electronic music effects circuit : one can be considered as self-contained and self-generating; the other is dependent on a sound source from a musical instrument.

Sounds made by real cymbals or drums can be modified electronically to produce unusual effects. This is where the *Drummer's Whoosh Unit* comes in; this will be based on a modified version of the purely *Electronic Cymbals* described in the present article.

THE electronic cymbals unit uses the white noise generator (described in January) and a power supply (described in December) with a new filter circuit. The circuits of the white noise generator and power supply are reprinted in Fig. 1 so that the whole extent of the circuit involved is realised from the outset.

The power supply is not shown in the photographs as it was external to unit, but there is plenty of room to incorporate it in the box if required. Alternatively, the performer may prefer to use dry batteries, so making the unit entirely self-contained and portable.


If required to be housed in the same box as the *Drummer's Whoosh* amplifier, this can still be done, but we would recommend the constructor to exercise some patience until next month's article appears. The same box can house one white noise generator and filter for both purposes, with modifications to suit the *Drummer's Whoosh*.

With all these circuits it is necessary to add a power amplifier and, since there is a wide variety of commercial types available, the user should select one that will suit the environment in which he is performing. Tone controls are a desirable facility as will be seen later.

SWITCHED FILTER

One white noise generator will provide sufficient output to operate a set of cymbal effects circuits of different pitches and qualities, giving a set of transistorised "cymbals" of relatively small size, and at reasonable cost. The cymbals effect circuit is enclosed in the dotted line box in Fig. 1a.

The 100 kilohm potentiometer VR1 controls the level of the white noise signal fed to the filter circuit. The white noise is filtered and deliberately "coloured" by transformer T1 and capacitor C5, then passes by way of C6 to the base of TR1. This transistor is normally biased into non-conduction by a negative supply applied through R10. A 1.5V or 3V battery will usually suffice here, and serves to prevent a hissing noise between strokes.

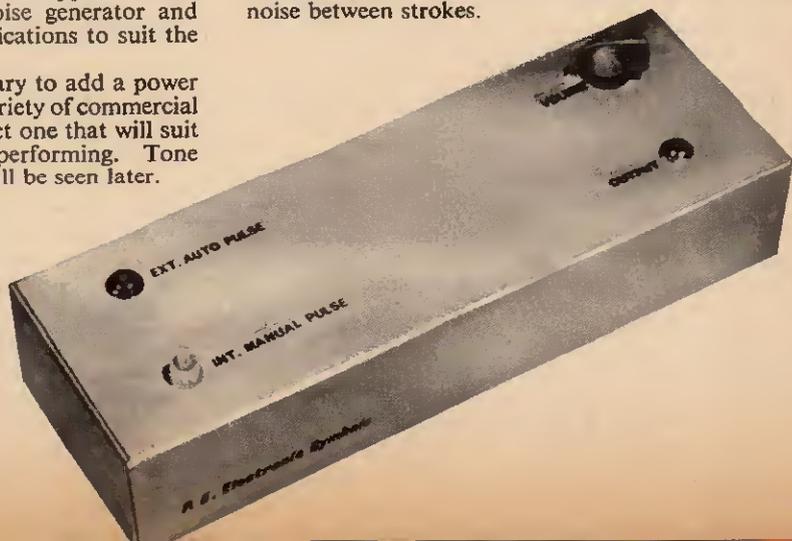

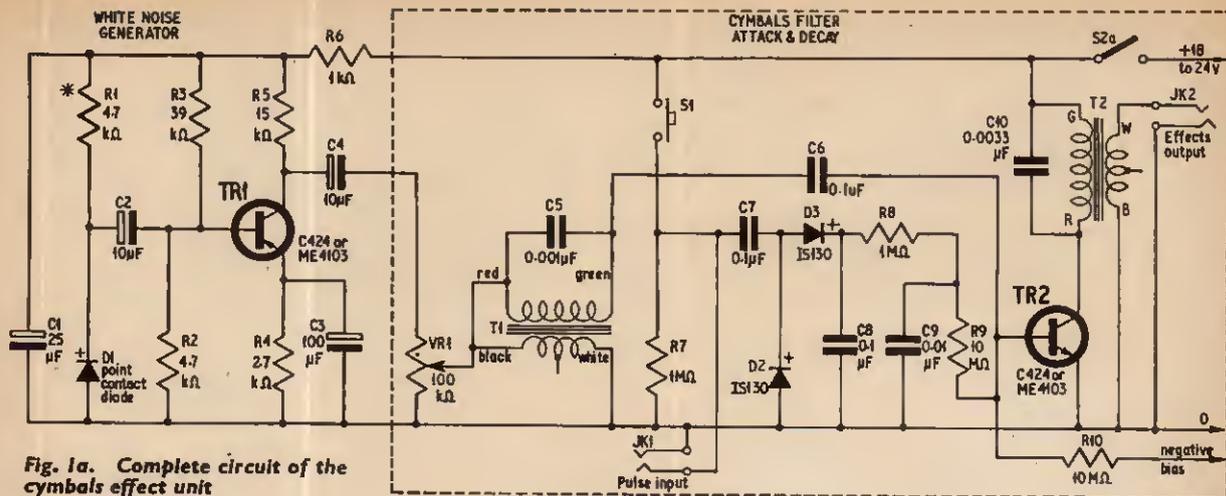


Fig. 1a. Complete circuit of the cymbals effect unit

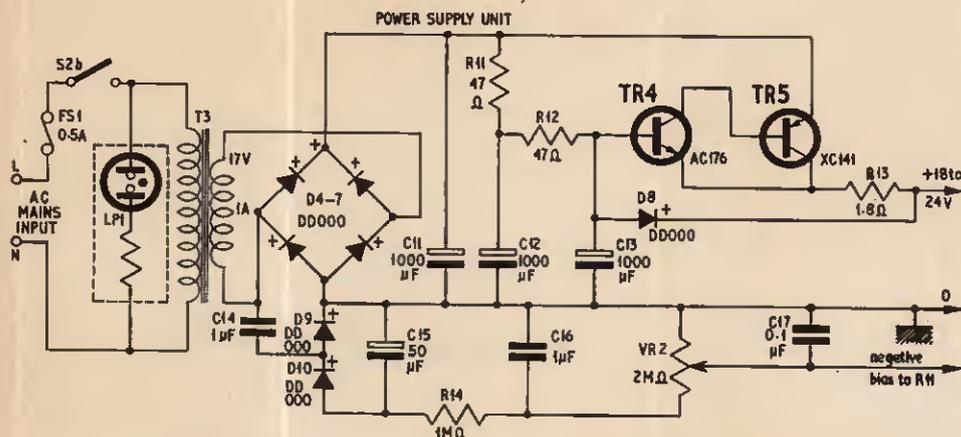


Fig. 1b. Modified power unit to supply negative bias

In order to simulate a cymbal stroke, a positive pulse must be applied to the circuit via C7, and must be of sufficient magnitude to overcome the negative bias with ease, and cause TR1 to conduct. To obtain a realistic result, this calls for a pulse of at least 6 volts, and indeed any voltage up to about 50 volts may be used.

A simple way to test the circuit would be to connect a 1 megohm resistor from C7 to the negative supply (common) line, and a Morse key or a push button switch from this input to the 18V to 24V positive supply line. A quick jab on the push button will charge up C8 via diode pump D2 and D3. C8 will then discharge by way of R8, R9, and TR1.

R8 and C9 act as a filter to reduce "thump" effects. As long as C8 holds sufficient charge, the potential maintained at the base of TR2 will cause TR2 to conduct, and to amplify the signal fed to its base via C6. As C8 discharges, the output from TR1 will die away. This output is fed through a further filter-circuit (T2 and C10) to the effects output jack JK2.

It is worth mentioning that a 1½V or a 3V battery connected between chassis and the negative bias line in this circuit will suffer negligible drain, and can be wired in permanently without any need for an on/off switch. A new leakproof battery would be likely to last for a number of years (well beyond normal shelf life), until corrosion sets in.

Better results may be obtained from the circuit by using an adjustable negative bias. The power supply circuit in Fig. 1b incorporates a negative bias supply suitable for the purpose. Bias adjustment may be used to control the decay time of the cymbal stroke.

ASSEMBLY AND TESTING

Prepare the printed circuit board according to the design shown (Fig. 2) and assemble parts on it as shown in Fig. 3. Fig. 2 shows the hole-spacing to suit a TO5 transistor encapsulation, and this spacing will suit type C424. If type ME4103 is used, the hole spacing may be made closer to suit the TO18 leadout arrangement of this transistor.

When assembly of the components on the cymbal-effects circuit-board is complete, wire it up to a white noise generator, d.c. power supply of 18V to 24V and an audio amplifier or mixer unit. Temporarily connect the positive supply line to the junction of D2 and D3. Switch on and adjust VR1 and the controls on the amplifier so that the sound of the white noise generator comes from the loudspeaker as a loud hiss.

Disconnect the positive line from D2 and D3. The sound should die away fairly rapidly. With some transistors, the sound will fade to a very low level without the need for a negative bias supply; others may need the application of a negative base bias via R10.


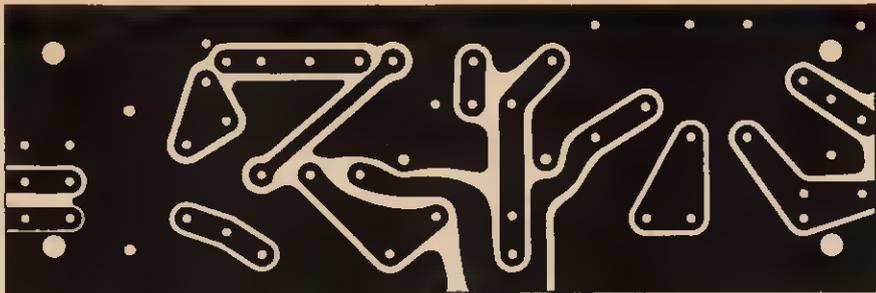


Fig. 2. Printed circuit pattern for cymbals filter (full size)

Fig. 3. Layout of components on the printed circuit board

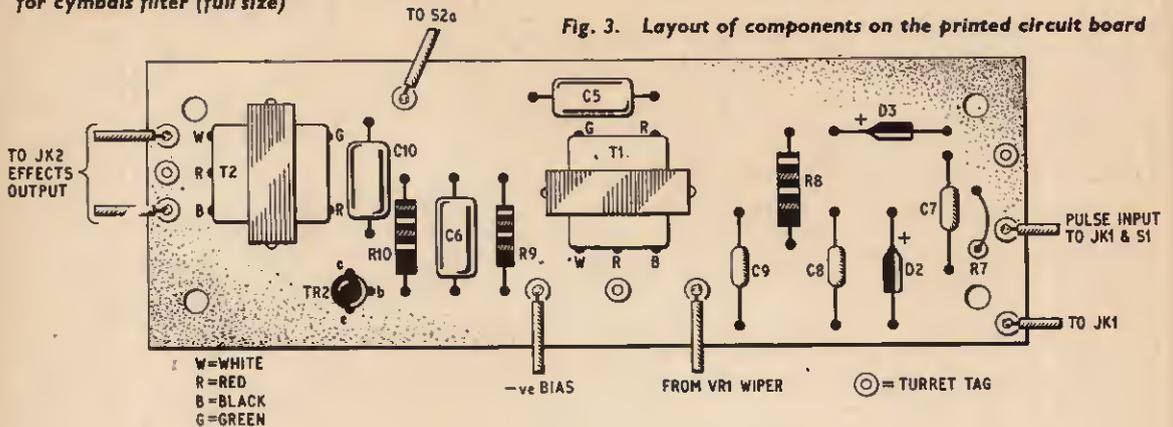

COMPONENTS

Resistors

R7 1M Ω R9 10M Ω
 R8 1M Ω R10 10M Ω
 All 10%, $\frac{1}{2}$ watt carbon

Potentiometer

VR1 100k Ω log. carbon

Capacitors

C5 0.001 μ F
 C6 0.1 μ F
 C7 0.1 μ F
 C8 0.1 μ F
 C9 0.01 μ F
 C10 0.0033 μ F

} All low voltage polyester or paper

CYMBALS FILTER

Transformers

T1, 2 Transistor transformers type LT44 (2 off)

Transistor and Diodes

TR2 ME4103 or
 C424 (S.G.S. Fairchild)
 D2 and D3 1S130 (2 off)

Jacks (with Plugs)


JK1, JK2 Standard $\frac{1}{4}$ in jack sockets (2 off)

Switches

S1 Single pole push on, release off push button
 S2 Double pole on/off toggle switch (S2a in low voltage line; S2b mains input to power unit if used)

Miscellaneous

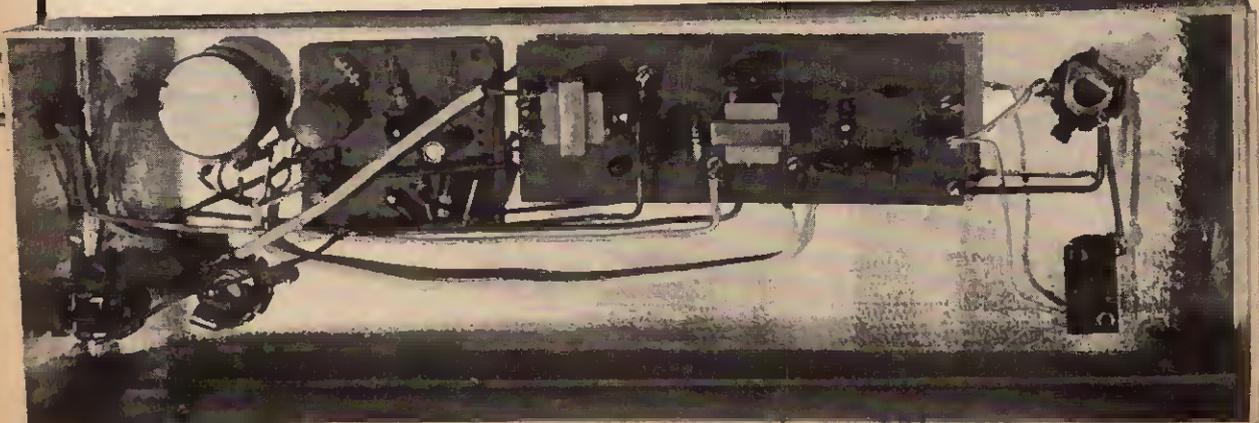Printed circuit board
 Single core screened cable
 Chassis 12in \times 4in \times 2 $\frac{1}{2}$ in
 Knob
 Component layout shown in Figs. 2 and 3



COMPONENTS . . .

POWER SUPPLY UNIT

Resistors

R11 47 Ω R13 1.8 Ω
R12 47 Ω R14 1M Ω 10% $\frac{1}{2}$ W
All 5% 3W, wirewound except R14

Potentiometer

VR2 2M Ω linear carbon

Capacitors

C11 1,000 μ F elect. 25V
C12 1,000 μ F elect. 25V
C13 1,000 μ F elect. 25V
C14 1 μ F polyester 160V
C15 50 μ F elect. 25V
C16 1 μ F polyester 160V
C17 0.1 μ F polyester 160V

Transformer

T3 Mains transformer, charger type. Pri. 240V mains; sec. 0-17V 1A

Transistors

TR3 XCI41 TR4 AC176

Diodes

D4 to D10 DD000 (Lucas) (7 off) or 1S130

Switch

S2b (see under *Cymbals Filter*)

Miscellaneous

FS1 Fuse 0.5A with holder
LPI Neon panel indicator with resistor
Printed circuit board 6in \times 2 $\frac{1}{2}$ in
Heat sink for XCI41
Knob

Component layout given in December 1967 issue

WHITE NOISE GENERATOR

Resistors

R1 4.7k Ω R4 2.7k Ω
R2 4.7k Ω R5 15k Ω
R3 39k Ω R6 1k Ω
All 10%, $\frac{1}{2}$ watt carbon

Capacitors

C1 25 μ F elect. 25V
C2 10 μ F elect. 25V
C3 100 μ F elect. 12V
C4 10 μ F elect. 25V

Transistor and Diode

TR1 C424 (S.G.S. Fairchild) or ME4013
D1 Point contact diode, any noisy type, such as sold for crystal receivers

Miscellaneous

Printed circuit board 2in \times 2in (Bonanza Board)
Connecting pins and wire
Component layout given in January 1967 issue

Components for cymbals filter given on previous page



in order to achieve a quiet background in between strokes, and a 1 $\frac{1}{2}$ V battery is usually quite sufficient.

If the positive line is quickly touched on to the junction of D2 and D3 a few times in succession, a sound similar to a cymbal stroke may be heard, but may not be very realistic at this stage, as adjustment of VR1 and the tone controls of your amplifier will have a considerable effect on the output qualities.

VR1 must not be set too high, or the effect will result in a continuous roaring or crackling sound. This is because the white noise is fed to the base of TR1 at a high level to overcome the negative bias. Turn down VR1 to a level somewhat below that at which the roar occurs. If, now, the cymbal strokes tend to have a somewhat crackly ending, VR1 must be set to an even lower level to give a smooth finish to each stroke.

VARIATIONS

The circuit is not by any means restricted to the component values given. By changing the values of C5 and C10 the cymbals pitch may be altered; the use of different transformers will give yet further ranges of effects. A choke or other inductor could be used in place of T2, and the output taken from the collector of TR1 by way of an 0.1 μ F capacitor.

Changing the values of C7, C9, and R9 will affect the "attack" and "decay" characteristics of the circuit,

although the combined value of R8 and R9 should not be reduced to a point which would result in excessive collector-dissipation in TR1 (rated about 200mW in free air).

METHODS OF OPERATION

For manual operation, the simplest method is to connect a 1 megohm resistor (R7) from C7 to the negative (common) supply wire, and apply pulses to this input from the 18V to 24V positive supply point by use of a Morse key or a push button switch. The final circuit shown in Fig. 1 performs the same function.

The circuit may also be operated electronically by connecting C7 directly to an electronic switching circuit (via JK1) such as a slow running multivibrator (for automatic "repeat" effects); a ring counter (for rhythm effects) or an electronic keying circuit. In all these circuits the pulse may be supplied from the collector of the switching transistor concerned. If using the multivibrator described in the article on a *Simple Rhythmic Control Unit* (February issue) JK1 would be connected to the collector of either TR1 or TR2 in that circuit.

The "Cymbals" circuit may be used very successfully with an electronic rhythm machine or a rhythm generator. An adaptation of the circuit may be used for beat group sound effects; this will be described next month in the *Drummer's Whoosh Unit*.



BOOK REVIEWS

BEGINNER'S GUIDE TO ELECTRICITY

By Clement Brown
Published by George Newnes Limited
185 pages, 7½ in. × 5 in. Price 15s

ANYONE starting a career or hobby in *electronics* might be put off by the title of this book when looking for an elementary guide. In order to understand and appreciate the technicalities of even the most simple of electronic circuits, one should have, or be able to grasp, the fundamentals of basic electricity. It comes at a time when more and more schools and training colleges are giving courses in the subject, and is therefore suitable for almost any beginner from 14 to 40 years of age.

It is written in an intelligently straightforward style that will complement course lectures and lab. experiments. Of necessity it is not by any means exhaustive but will certainly cover in adequate terms the theory to be found in advanced level G.C.E. and O.N.C. courses. Electronics is not strictly introduced until Chapter 7, and even then in only basic form.

Technical terms tend to baffle many beginners, but here they will find explanations easily understood, and related to everyday electrical appliances and electronic circuits. Valve and transistor theory is included. The relationship between theory and domestic and industrial applications provides a suitable balance to a book that could otherwise have been rather dry reading.

The final chapter gives some guidance for those wishing to make a career in this fascinating activity.

M.A.C.

ABC'S OF TRANSISTORS

By George B. Mann
112 pages. Price 20s

F.E.T. CIRCUITS

By Rufus P. Turner
160 pages. Price 25s

ABC'S OF VACUUM TUBES

By Donald A. Smith
128 pages. Price 20s

BRIDGES AND OTHER NULL DEVICES

By Rufus P. Turner
143 pages. Price 26s
Published by W. Foulsham & Co. Ltd.
All 8½ in × 5½ in

ANOTHER four titles in the impressive catalogue of Foulsham Sams educational primers in an expanding technology. All four of the books present their subjects with a minimum of mathematics apart from the last title which sets out the necessary bridge equations happily, without qualification. Treatment of the subject matter is succinct and well illustrated and all

four volumes are recommended as beginning texts for those anxious to be taught the rudiments of electronics.

ABC's of Transistors deals simply with the basic physical and electronic features of these devices and analyses their action in oscillators and amplifiers. Practical servicing and testing procedure of these circuits are also discussed.

F.E.T. Circuits is an excellent book for those readers who like their electronics practical. From a brief introductory chapter on structure and performance you are launched into the whole gamut of circuit applications of this versatile high impedance device: transmitters, receivers, test gear, control circuit, each one in effect a potted constructional project as all component and performance details are given.

ABC's of Vacuum Tubes. Dealing in the main with the construction and action, both dynamic and passive, of valves from the diode to the multigrid family. Biasing and classes of operation are covered and the final two chapters deal with miscellaneous and special purpose valves. Altogether a painless introduction to valve technology.

Bridges and Other Null Devices. Measurement is fundamental to all sciences. In electronics the bridge type circuit predominates in this application and this book sets out to explore its various forms for specific measurement purposes. From basic bridge circuit theory the reader is introduced to most of the equipment found in a test gear laboratory. Although the illustrations are of American equipment, the principles and measurement capabilities are universal.

G.G.

COLD CATHODE TUBES

By J. B. Dance, M.Sc.
Published by Iliffe Books Ltd.
125 pages, 8½ in × 5½ in. Price 35s

IN A world largely dominated by the semiconductor, glass enveloped devices are becoming increasingly rare. But one group of tubes seems to have gained a new lease of life due, indeed, to the general expansion of electronic techniques brought about by solid state devices. For visual displays of data, or indication of the operational condition of circuitry, there is no real substitute for the cold cathode tube. This can be a simple neon lamp (which may double as a voltage regular), or a rather more complex numerical or character indicator tube. The orange-red glow of neon is the outward manifestation of electronic sophistry, as we well know.

But the cold cathode tube family includes the well known G.M. tube for nuclear radiation detection, stepping tubes for counting circuits, and other important specialised types, besides.

The electronics enthusiast who is "genned up" on solid state may be lacking in knowledge about cold cathode tubes. He can now find the basic facts of gas discharges and straightforward descriptions of those tubes he is most likely to encounter in modern electronic apparatus in this book. Some experiments with neon diodes and trigger tubes are described and there are many practical circuits which show typical applications of the various devices. A good practical introduction to the subject, with a minimum of maths.

D.D.R.

Transistor Amplifier DESIGN

4 NEGATIVE FEEDBACK

By A. Foord

NEGATIVE feedback occurs when a proportion of the output voltage of an amplifier is fed back to the input in such a way as to reduce the overall gain, so that the gain with feedback is less than the gain without feedback. Feedback can be used to:

- (1) Give a predictable mid-band gain, the greater the amount of feedback the less sensitive the amplifier is to changes of transistor characteristics.
- (2) Increase bandwidth or to give a shaped frequency response curve which depends almost solely on the passive components forming the feedback network, and does not depend on an accurate knowledge of transistor parameters (which may vary between one specimen and the next of the same type).
- (3) Increase or decrease input or output impedances; by using different feedback arrangements it is possible to obtain input or output impedances higher (or lower) than those normally associated with transistor stages. In particular it is possible to arrange for a high input impedance and a low output impedance, so that amplifier stages can be cascaded without interaction.
- (4) Reduce the distortion which normally occurs in the final stages of an amplifier, where current and voltage swings are highest.

BASIC PRINCIPLE

Any study of negative feedback begins with a functional block diagram, Fig. 4.1.

The circuit has two signal paths: the forward path, which is usually an amplifier and contains all the active devices, is marked with its voltage gain A ; the feedback path B which has a gain less than unity. The bar above the symbol A indicates that there is a phase reversal in the amplifier, while B represents the fraction of the output voltage fed back to the input.

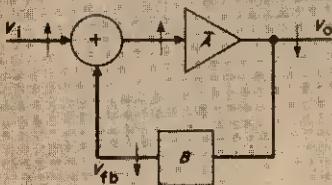


Fig. 4.1. Functional diagram of an amplifier with negative feedback path

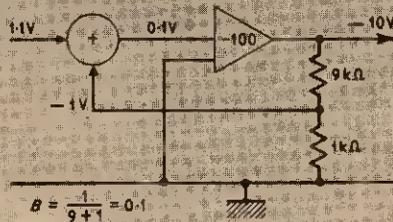


Fig. 4.2. A simple example of negative feedback

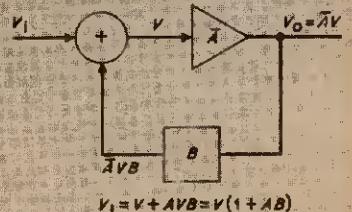


Fig. 4.3. Voltage relationships between the amplifier and the feedback circuit

The phase reversal to obtain negative feedback occurs in the amplifier; the arrows in the block diagram reassure us that the feedback is in fact negative. In a simple case this is obvious, but for more complicated arrangements a check will ensure that we do not accidentally use positive rather than negative feedback.

Take a simple example, Fig. 4.2. Without feedback we require an input of 0.1V to the amplifier for an output of -10V. If negative feedback is added making B equal to 0.1 times, 0.1V is still required at the input of the amplifier itself to obtain an output of -10V.

The input to the addition point needs to be 1.1V, so that when the -1.0V is added to the input we are left with 0.1V to give an output of 10V. The overall gain with feedback is now

$$G' = \frac{-10}{1.1} = -9.1 \text{ times}$$

The negative feedback has reduced the gain from its open loop value of 100 times to a closed loop gain of 9.1 times, therefore the closed loop gain is approximately $1/B$ times ($1/B = 10$).

A more detailed examination will show that the gain with feedback is approximately $1/B$ provided the closed loop gain is much less than the open loop gain, Fig. 4.3.

Starting at the input to the amplifier (call this V) then the output of the amplifier is AV , the voltage fed back is AVB , and the input is $V + AVB$. Then the overall gain with feedback is given by

$$G' = \frac{V_0}{V_1} = \frac{AV}{V + AVB} = \frac{\bar{A}}{1 + AB} = \frac{-1}{\bar{A} + B}$$

If B is much greater than $1/A$ (i.e. A is much greater than $1/B$) then $G = 1/B$.

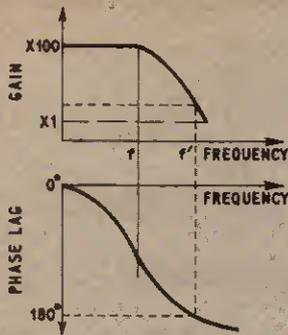


Fig. 4.4. Gain and phase characteristics which would cause instability

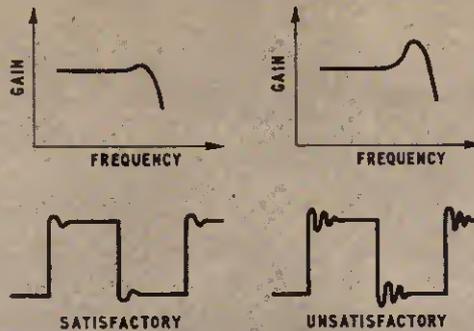


Fig. 4.5. Instability shown by "ringing" cycles

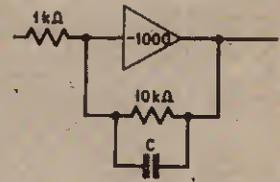


Fig. 4.6. The practical example of a high gain amplifier with feedback resistor and "anti-ringing" capacitor C

Therefore, the ideal gain with feedback (G') is equal to $1/B$, if the gain without feedback (A) is much greater than $1/B$.

To confirm this, compare the results using the accurate formula and the approximate formula; drop the minus phase sign since we are interested in magnitudes rather than the phase reversal we know occurs in the amplifier.

$$\text{Actual closed loop gain } G' = \frac{A}{1 + AB}$$

$$\text{Ideal closed loop gain } G = \frac{1}{B}$$

Calculation will show that, if the required gain with feedback is one tenth of the gain without feedback, then we do not need to use the accurate formula, since errors in assuming G equal to $1/B$ are small enough to be discounted.

STABILITY

Having assumed that the design of the amplifier is such that the feedback will always tend to reduce the gain, but unfortunately this will not always be so, any practical amplifier will contain reactive elements which will introduce a phase shift in the signal as it passes through the amplifier (quite apart from the 180 degree mid-band phase shift required to obtain mid-band negative feedback). The gain and phase characteristics of the amplifier might appear as Fig. 4.4.

Above a certain frequency f , gain falls and an extra phase lag is introduced. If we applied 100 per cent negative feedback to an amplifier with this characteristic, to give an overall gain of unity, the amplifier would oscillate.

While there is still greater than unity voltage gain around the loop, there is an extra 180 degrees of phase shift to cause the feedback (which was negative below f) to become positive at f' . The system would therefore oscillate at the frequency f' .

Designing for stability is complicated when a considerable amount of feedback is applied. Instability in a feedback amplifier is shown by a peak in the frequency response curve and ringing on a square wave signal (see Fig. 4.5).

Feedback over one or two stages is normally safe, although later on, when considering the use of 100 per cent feedback to raise input impedance, a non-mathe-

matical approach will be applied to the stability problem. For most purposes, it is in order to see that the frequency response curve does not have a peak of more than a couple of decibels in it, and that the square wave response is satisfactory, i.e. free from ringing effects.

The photographs show results obtained with a high gain amplifier, this had a gain of 1,000 times (60dB) without feedback, and a gain of 10 times (20dB) with feedback (see Fig. 4.6).

Photo A shows the leading edge of the 1kHz square wave input; photo B shows the ringing on the output waveform without the capacitor C, and this was considered unsatisfactory. The capacitor was adjusted in value to obtain the acceptable response of photo C. Since for clarity the photographs only show the leading edge of the square wave, the time scale was extended to show the leading edge more clearly. The capacitor was increased to reduce the bandwidth to 20kHz which increased the rise time to that shown in photo D.

Feedback around one stage only is called local feedback, and since only the common emitter stage provides a phase reversal of its output signal with respect to its input, it follows that local feedback can only be applied around the common emitter stage.

There are two basic ways of applying feedback to the common emitter stage; one arrangement is considered next, and the other is dealt with later, in the section on virtual earth amplifiers.

SERIES LOCAL FEEDBACK

Referring to Fig. 4.7, the resistor R_E in series with the emitter accounts for the applied feedback, this resistor enables a feedback voltage V_f proportional to load current, to be fed back in series with the input voltage V_i . The base-emitter voltage of the transistor is reduced by the feedback so that V_{BE} is less than V_i .

If R_E is small and of the same order of value as the internal emitter impedance r_E (say 100 ohms or so), then the amount of feedback is small. Distortion is slightly reduced and bandwidth is increased very slightly, at the expense of a small decrease in gain. If R_E is large then the gain is given by

$$G = \frac{V_o}{V_i} = \frac{R_L}{R_E}$$

The input impedance is given by

$$Z_i = h_{ie} R_E$$

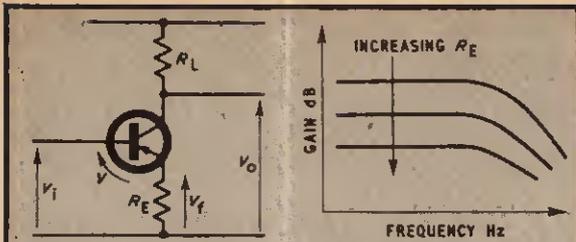


Fig. 4.7. Series local feedback by the unby-passed emitter resistor

Fig. 4.8. The effect of R_E on gain and frequency response

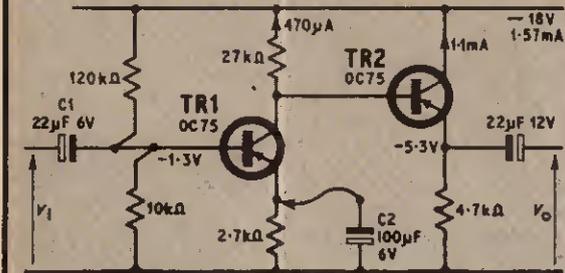
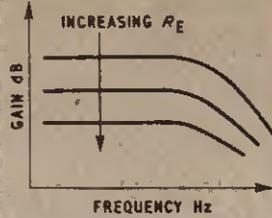


Fig. 4.9. Emitter follower output to prevent undue loading on the amplifier stage

In practice for a single stage amplifier biased in the normal way with a divider chain on the base, this increase in input impedance is masked to some extent by the shunting effect of the chain. The effect of R_E on gain and frequency response is as shown in Fig. 4.8.

To avoid loading R_L and to maintain a high gain without feedback, the output can be taken via an emitter follower, a practical circuit is shown in Fig. 4.9.

Since the transistor is used in common emitter we must work out approximately the bandwidth we would expect. For TR1 the collector current is of the order of 0.5mA. Suppose the transistor current gain is typically 50 at 0.5mA. The 3dB down point in common emitter is given by

$$f = \frac{f_T}{h_{fe}} = \frac{1,000}{50}$$

$$f = 20\text{kHz.}$$

One would expect the response to roll off somewhere at this frequency, the exact point depending on h_{fe} and f_T for the particular specimen of transistor. Since TR2 acts as an emitter follower the overall frequency response is limited by TR1 since an emitter follower has a frequency response far better than that of a common emitter stage.



Photo A. Leading edge of the 1kHz square wave

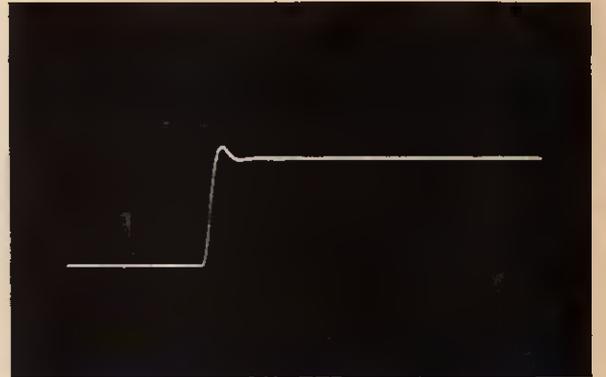


Photo C. Ringing is brought down to an acceptable level by selection of a parallel capacitor across the feedback resistor



Photo B. Ringing caused by non-selective feedback

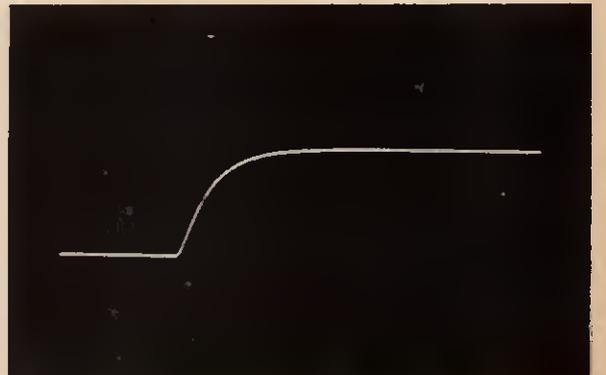


Photo D. Larger value of capacitance increases the rise time

The results without feedback (C2 connected) and with feedback are:

Gain without feedback = 310 times = 50dB
 Bandwidth = 30kHz
 Input impedance = 1k Ω
 Output impedance = 300 Ω
 Maximum output = 1.5V r.m.s. no load
 = 500mV r.m.s. into 1k Ω

The frequency response was measured under no load conditions at 100mV r.m.s. Up to 50kHz or so, the amplifier will provide 500mV r.m.s. into 1 kilohm, but above this frequency the emitter follower current gain starts to drop and the waveform distorts, so that 500mV would only be obtained without distortion into a load greater than 1 kilohm.

The gain without feedback appears high until we remember that the collector load is 27 kilohms rather than the 1 kilohm or so we would expect for another common emitter stage and a high gain transistor is being used.

Gain with feedback = $\frac{27}{2.7} = 10$ times = 20dB
 Bandwidth = 68kHz
 Input impedance = 7k Ω
 Output impedance = 300 Ω
 Maximum output = 500mV r.m.s. into 1k Ω
 (up to 50kHz)

The actual measured gain was 19.5dB, which is probably an error in measurement or tolerances on the collector and emitter resistors. Since the open loop gain is 30 times the closed loop gain, one might expect the gain of 20dB to be independent of variations in characteristics between one OC75 and the next, although the bandwidth might alter slightly.

Although the gain has been reduced by a factor of 30 times, bandwidth has only increased twice. Series local feedback is often used inside another overall feedback loop, where a predictable stage gain is required rather than an unpredictable (though higher) gain.

With an input impedance of 7 kilohms and an output impedance of 300 ohms, these amplifiers can be cascaded

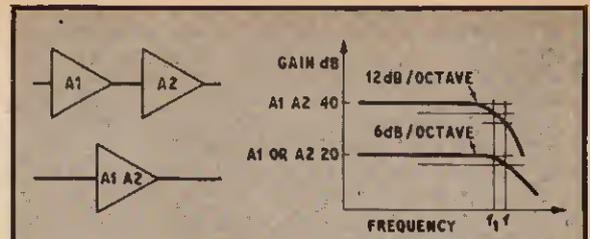


Fig. 4.10. Combining two identical amplifiers

Fig. 4.11. The response of each amplifier is added to give overall response

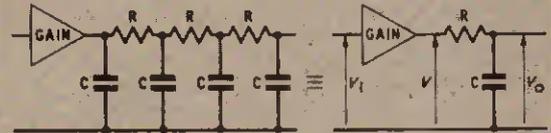


Fig. 4.12. Equivalent circuit of a transistor looks like that of a transmission line at high frequencies

Fig. 4.13. A single CR conversion of Fig. 4.12

without interaction. Bandwidth is also extended at the low frequency end, but since this is within our control (coupling and decoupling capacitors) the main benefit of this type of negative feedback is the predictability of mid-band gain rather than the small extension of bandwidth.

TRANSFER FUNCTIONS

The amplifier can be represented as a block, so that two amplifiers in series could be represented by adding the two separate gains in decibels (see Fig. 4.10).

$$A_1 = 10 \text{ times} = 20\text{dB} \quad A_1 A_2 = 100 \text{ times} \\ A_2 = 10 \text{ times} = 20\text{dB} \quad = 40\text{dB}$$

Working on the frequency response curve and adding decibels this would result in the response shown in Fig. 4.15.

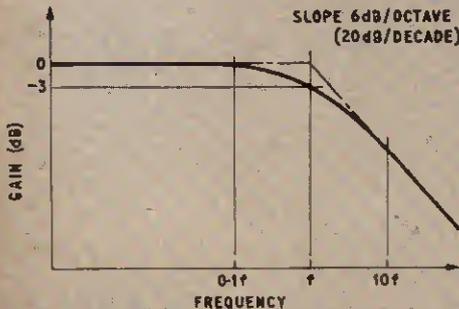


Fig. 4.14. Approximating the frequency response, then deriving the accurate response (solid line)

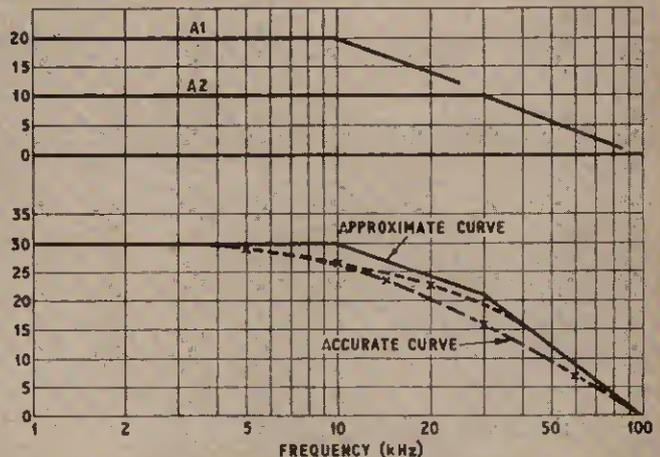


Fig. 4.15. Summing the response of two amplifiers in cascade

Where each amplifier was 3dB down (at f), the response is now 6dB down (for two identical amplifiers), and the new 3dB down point is lower down at f_1 , as one would expect. The slope of the curve for a single amplifier is approximately 6dB per octave, and for two amplifiers in series this will be 12dB per octave.

In the equivalent circuit of a transistor (Fig. 4.12) it appears as a transmission line for high frequencies, but as a first approximation it can be considered as a single CR network, Fig. 4.13.

Taking the CR network or single time constant on its own, at low frequencies C has a high impedance and $V_o = V_i$. At a frequency when C has a reactive impedance equal to R, V_o is 3dB down with respect to V_i , and continues to fall at 6dB per octave (20dB per decade) with increasing frequency, as in Fig. 4.14.

The solid line curve is the accurate frequency response, while the dotted line is the straight line approximation. The point f where the impedance of the capacitor is equal to the resistor is called the "turnover" or break point. The maximum error between the accurate and straight line approximation is 3dB which occurs at the break point. In practice the approximate curve is drawn; f is 3dB down, $0.5f$ and $2f$ are 1dB below the approximate curve; the accurate curve is drawn from this information.

For two amplifiers in cascade the procedure just outlined is shown in Fig. 4.15. The bandwidth of the two amplifiers in series is almost identical, but the ultimate slope is now 12dB per octave rather than the 6dB per octave for a single common emitter stage.

RELATION OF RISE TIME AND BANDWIDTH

A square wave can be considered as the sum of a number of harmonically related sine waves; these include a fundamental sine wave at the basic repetition frequency and frequencies of three, five, seven times, and so on (odd harmonics of the basic frequency).

If a square wave of 1kHz is fed into an amplifier with a sharp cut off at 1.5kHz all the harmonics are filtered out, leaving only the 1kHz fundamental, Fig. 4.16.

If the response of the amplifier is extended to 20kHz the output would consist of the fundamental and harmonics up to 19kHz. Harmonics at 21kHz,

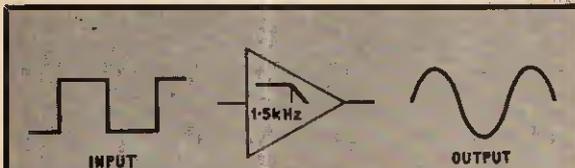


Fig. 4.16. A square wave signal can be filtered to give the fundamental frequency only

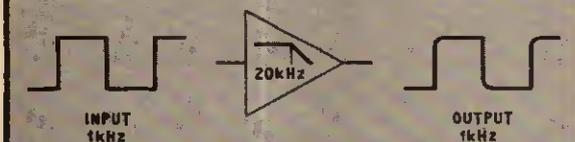


Fig. 4.17. Increase in the rise time of the square wave by loss of harmonics

23kHz upwards would be attenuated according to the roll-off of the amplifier response curve. The square wave would hardly be degraded at all, since the amplitudes of these harmonics (relative to the fundamental) are small. The loss in harmonics increases the rise time of the square wave, Fig. 4.17.

To determine the bandwidth of an amplifier we would feed in a square wave with a rise time better than we would expect the amplifier to handle, and measure the degradation on the output.

Suppose our square wave had a rise time of $5\mu s$ and after passing through the amplifier this was degraded to $25\mu s$, then our amplifier has a rise time of $\sqrt{(25^2 - 5^2)}$ or $24.5\mu s$ and its bandwidth is given by:

$$f = \frac{0.35}{\text{rise time}} = \frac{0.35}{24.5} \times 10^6 = 14.3\text{kHz}$$

This method is only an approximate means of determining bandwidth, it would tell us if our amplifier had a bandwidth of 20kHz or 10kHz, but we could not rely on discriminating between bandwidths of 20kHz and 17kHz.

However the edges of the square wave do represent the type of signals present in a transient, which simple sinewave testing cannot do, so that we can see immediately any instability or excessive overshoot or ringing in the amplifier. The disadvantages are that we do need a square wave of good rise time, and an oscilloscope capable of showing it.

Next month: Negative feedback applied to practical circuits.

BETTER SOUND

THE BBC announces that four programmes in a new series "Better Sound" will be broadcast on Fridays at 7.00-7.30 p.m. in Study Session, Radio 3 from May 3 to 24. Listeners will be invited to send questions of general interest, or requests for more information on particular topics covered in the series and these will be dealt with in two extra programmes which will follow the repeat of the series later in the year.

The series will be repeated on Radio 4 on Saturday mornings at 11.00-11.30 a.m. from August 17 to September 14. There will be no programme on August 31 (Bank Holiday weekend), but there will be two additional programmes on Saturdays, September 21 and 28.

Each programme will focus attention on one area of this wide field. A number of topics (e.g. microphones, loudspeakers, stereo) will therefore be treated in more than one programme. Advice on particular makes cannot be given and the construction and repair of equipment will not be dealt with.

Programme 1: Transmission and reception of radio, including stereophonic broadcasting. Explanation of AM and FM, etc.

Programme 2: The nature of sound, and room acoustics, with demonstrations of the effect of different placings of microphones and loudspeakers.

Programme 3: The reproduction of music in mono and stereo; hi fi equipment.

Programme 4: Tape-recording for the amateur.

The diagrams in the Study Notes (BBC Publications, 2/6 plus 5d postage) will be helpful in following the broadcasts and the explanations in the text of the basic principles of the transmission, recording and reproduction of sound in mono and stereo will be useful for reference, particularly for the less knowledgeable listener.

nucleonics

for the EXPERIMENTER

By M. L. Michaelis M.A.

7 — RADIOACTIVITY MEASUREMENT; STRACE RADIATION METER.

PREVIOUS articles in this series have discussed nuclear radiation, atomic structure, and the practical applications of nucleonic measurements; measuring methods and various kinds of detectors have been considered in a general way. A distinction has been made between activity measurements and energy measurements, and electronic methods for sorting electrical pulses from a spectroscopic, i.e. energy-distinguishing, nuclear radiation detector explained.

Now the point is reached where we have sequences of pulses, ready for activity determination, i.e. for counting the numbers arriving per unit time, corresponding to the numbers of radioactive atoms disintegrating per unit time. This counting process is the function of the actual *radiation meter* unit in any nucleonic equipment. This month, we will discuss the basic requirements and electronic circuit techniques which are involved. It is quite immaterial whether the pulses originate from a non-spectroscopic detector like a G.M. counter, or from a spectroscopic detector such as a scintillation detector with kick-sorter amplifier.

In the former case, the mean pulse frequencies may correspond to the gross activity of a mixture of different


kinds of radioactive atoms, whereas in the latter case, the activity of a particular species of radioactive atoms can be observed selectively, to the exclusion of others which may be present at the same time in the radioactive sample. However, the principles of making activity measurements, and the structure of the radiation meter used for the purpose, are the same in both cases.

ACTIVITY AND DETECTION EFFICIENCY

The activity of a radioactive sample is the number of atoms disintegrating in it in unit time, irrespective of the type of disintegration or the energy of the emitted nuclear radiation. We have already seen (in Part 3) that the unit of activity is the *curie* (Ci), corresponding to 2.2×10^{10} disintegrating atoms per minute. This is the activity of 1 gram of pure radium, by definition. Convenient practical units for amateur measurements are the *pico-curie* (pCi), corresponding to 2.2 disintegrating atoms per minute in the given sample, and the *nano-curie* (nCi), corresponding to 2,200 disintegrating atoms per minute in the given sample.

It is customary to take one minute as the time unit for radiation meters, so that their essential function is to determine the pulse counts per minute. The abbreviation c.p.m. is conventionally used for "counts per minute."

STRACE
RADIATION
METER

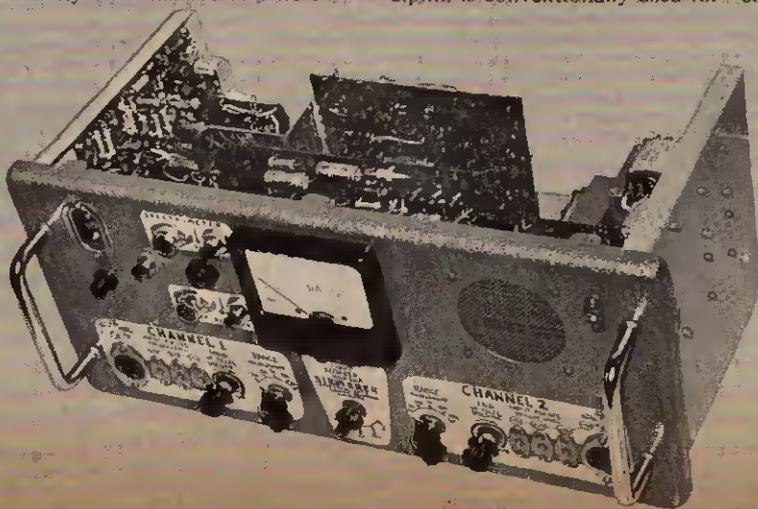

It is not possible to calibrate a radiation meter directly in pCi or nCi, but only in c.p.m. This is because the ratio of c.p.m. to pCi depends on the numerical detection efficiency of the radiation detector employed. The ratio is 2:2 only if every disintegrating atom in the radioactive sample produces an electrical response pulse in the detector. This is rarely the case in practice; a greater or smaller proportion of the radiations will miss the detector, so that the ratio c.p.m./pCi is practically always considerably less than 2:2. Of course, it is the aim of any detector and sample arrangement to achieve as high a numerical detection efficiency as possible. This is also referred to as the *geometry factor*.

TWO EXAMPLES

Two examples will make this point clear.

In the first case, consider a radioactive sample lying on a large flat radiation detector, i.e. G.M. counter. The nuclear radiations may be emitted in any direction by chance. Thus, on the average one half of them will fly upwards or obliquely upwards, and miss the detector. The other half will travel downwards or obliquely downwards, and enter the detector to produce a pulse. The ratio c.p.m./pCi would be 1:1 in this case.

In the second case, consider the sodium iodide crystal of our scintillation detector (see Part 5), with the radioactive sample placed at the bottom of the axial sample well. Nuclear radiation emitted in almost any direction will then strike the crystal, so that we would expect very nearly the ideal value of 2:2 for the ratio c.p.m./pCi.

In practice, we actually find values considerably smaller than 1:1 and 2:2 for the respective cases, because two further factors reduce the detection efficiency. Firstly, some quanta of radiation may be absorbed within the sample, or other insensitive material, before reaching the sensitive detector region. Secondly, some quanta may pass straight through the detector without getting absorbed to produce a pulse. Thus the ratio c.p.m./pCi is only about 0.1 for a liquid sample in the Mullard MX124/01 G.M. counter tube specified for our equipment (see Part 4). The scintillation detector possesses a considerably greater detection efficiency, under some conditions approaching closely to the ideal value of 2:2 for the ratio c.p.m./pCi.

RADIOACTIVE DECAY


Since the activity of a given radioactive sample is a statement of the number of atoms disintegrating per unit time in that sample, this activity must necessarily diminish with the progress of time, because the number of atoms left over is continuously decreasing. For any given species of radioactive atoms, the activity is strictly proportional to the number of atoms of that species which are present in the sample, i.e. the rate of decay is directly proportional to the amount present.

This is the basic characteristic of any exponential process (the rate of fall of the voltage across a capacitor discharging through a resistor is always proportional to the actual voltage left across the capacitor at the instant considered, or the rate of growth of a sum of money on compound interest is at all times proportional to the accumulated capital). Thus the activity of a simple radioactive sample decreases exponentially with time. This is a very important principle, known as the *radioactive decay law*.

Different species of radioactive atoms decay at different rates, which are specifically characteristic of the respective species, just as different capacitor/resistor combinations discharge at different rates according to the produce of capacitance and resistance (time constant) of the circuit.

DECAY HALF-LIFE

For radioactive samples, we specify a *decay half-life*. This is the time taken for one half of a large initial number of atoms to disintegrate. If we wait a further equal period of time, one half of the remainder will have disintegrated, i.e. the number of atoms still left over is halved during each successive half-life period. The process theoretically never goes to completion. The smaller the number left over becomes, the greater the random departures from

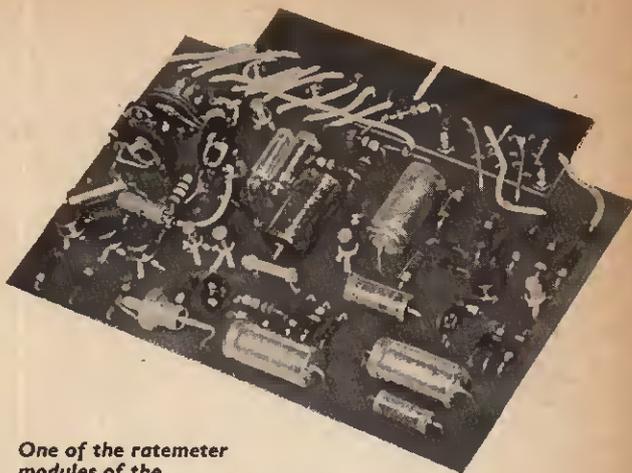

One of the ratemeter modules of the STRACE Radiation Meter

smooth exponential decay. Ultimately, when only one atom is left over, it is inherently impossible to predict how long it will continue to remain intact.

A similar indeterminacy prevails already at the outset, when we had a very large number of atoms. If we were to single out any particular atom for close observation, there is no way of predicting, in which successive half-life period it will meet its fate. This is subject to pure chance. Thus whilst we can be pretty sure that almost exactly one half of a large number of atoms will disintegrate in a half-life period, we are unable to determine in advance which particular atoms will belong to the decaying half.

STATISTICAL FLUCTUATIONS

The inherent unpredictability of the lifetime of any single radioactive atom introduces random fluctuations in the predictable mean behaviour of a large number of similar atoms. If the smooth exponential decay law would ideally demand that n atoms should disintegrate in a given sample within a certain time of observation, then the *actual* number of atoms observed to decay within that time will in all probability differ from n . It may be smaller or larger. If we repeat the experiment numerous times under identical conditions, the average of all observations will approach ever more closely to n . Regarding the discrepancies of individual results, we will find that these average to $\pm \sqrt{n}$. This is called the *mean uncertainty* of the count n .

As far as practical measurements are concerned, this means that if we want our activity reading to be reliable to within 1 part in n , we must count at least n^2 pulses before we stop the counter and divide by the total time taken. Otherwise random fluctuations will exceed our tolerance limit and the readings are meaningless to the envisaged accuracy.

It is common practice to specify four accuracy classes, namely 1, 5, 10, and 20 per cent. These correspond to desired reliabilities of 1 part in 100, 20, 10 and 5, so that we must respectively count at least 10,000, 400, 100 or 25 pulses.

Note carefully that it is solely the *total pulse count* which determines the statistical accuracy, quite irrespective of the time taken for clocking-up this count. The radiation meter must simply be left running until the required number of pulses have arrived, and if this takes a very long time in the case of low activities, the circuits must be designed with adequate long-term stability.

RADIATION METER TIMING

The relationships explained in the previous section dominate the design of practical radiation meters. In the case of digital counting, there are few basic problems as far as long-term stability is concerned. Professional equipment often adopts count timing here. In other

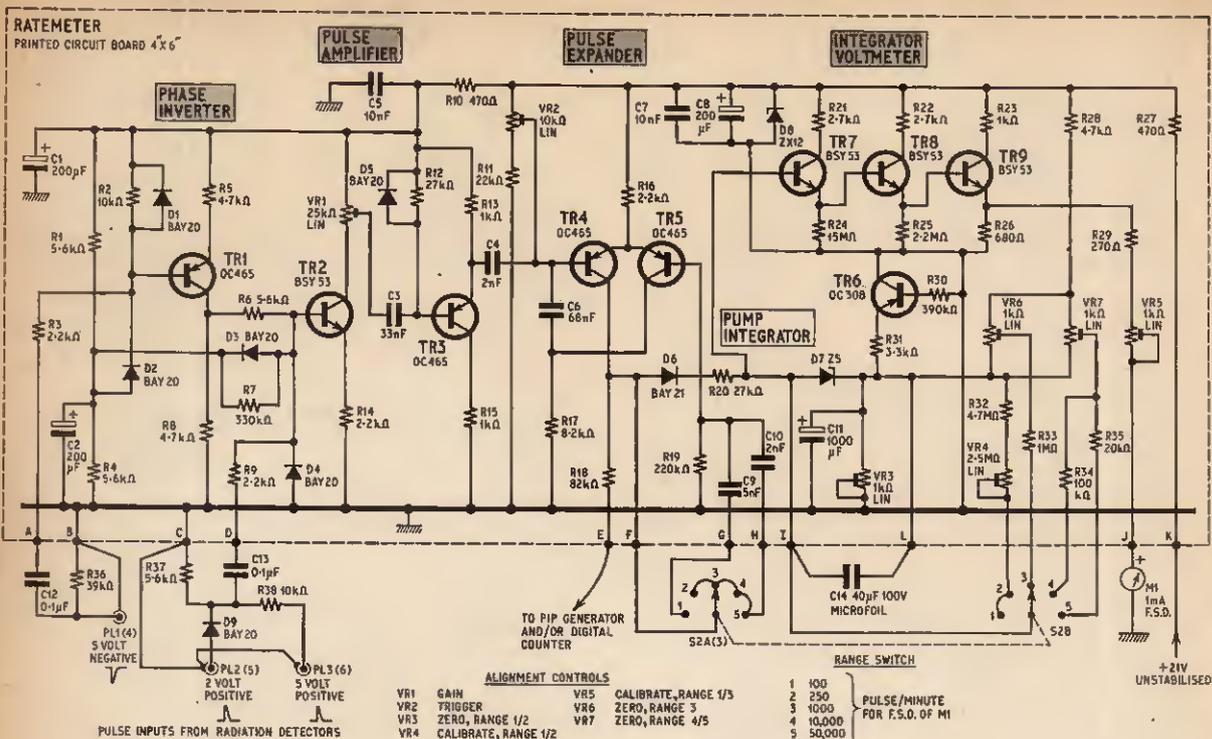


Fig. 7.1. STRACE RADIATION METER: Circuit diagram of the ratemeter module

words, the time taken to achieve a predetermined count is measured. Suppose we desire a statistical accuracy of 1 per cent. The clock will then be zeroed and the counter set to 10,000. The clock is then set running forwards and the counter backwards. When the counter reaches zero, it stops the clock automatically.

In the case of analogue counting, more special considerations are required. We remember that analogue counting establishes the activity reading as the voltage developed across a capacitor. Each pulse pumps a definite small electric charge into the capacitor, whilst the capacitor at the same time discharges through a precision resistor. The resulting voltage across the capacitor is directly proportional to the rate of arrival of the pulses. This voltage will fluctuate in a random manner, due to the random fluctuations of the pulse rate. The meter reading thus fluctuates over a certain range of the scale, instead of being steady.

RATEMETER TIME-CONSTANT

Consider the lowest range of the ratemeter in our STRACE equipment, which is 100 c.p.m. for full-scale deflection. The design figure is the 5 per cent statistical accuracy class, which calls for 400 pulses in the "counting time". These take four minutes to arrive at 100 c.p.m., so that the product of the integrating capacitor value (μF) and its discharge resistor (megohms) should be 240 seconds.

If the value of the capacitor is kept constant, but the value of the discharge resistor halved, then a given pulse rate will produce only half as great a meter deflection. The full-scale deflection c.p.m. value is thus doubled. But the statistical accuracy is unchanged, because although the time constant has been halved, the rate of arrival of the pulses for full-scale deflection has been doubled, so that the same number of pulses arrive within the time-constant period.

In general, this leads to a simple rule. The various desired c.p.m. ranges are obtained by switching corresponding different discharge resistors across the same integrating capacitor, whereby the same statistical accuracy

is then obtained on all ranges. This is most fortunate, since only one capacitor is thus required. The capacitor must be of immaculate quality, above all, it must have very low leakage and excellent long-term capacitance stability, so that it is rather expensive. Precision resistors are much cheaper, and only these are required in quantity according to the desired number of ranges.

STRACE RATEMETER MODULE

Fig. 7.1 shows the complete circuit of the ratemeter module for the STRACE radiation meter unit.*

The components within the broken-line rectangle are accommodated on a 4in \times 6in printed circuit board. Layout is in no way critical.

Almost any silicon *npn* transistors are suitable for TR2, 7, 8, 9, and almost any silicon *pnp* types for TR1, 3, 4, 5, provided collector voltage ratings are at least 12V working in all cases. TR6 may be any small germanium *pnp* audio power transistor, e.g. OC72 is also suitable. The small diodes may be any *silicon* type with small self-capacitance and at least 100V p.i.v. rating. D7 is a 5V miniature Zener diode, D8 is a 500mW dissipation (at least) 12V power Zener diode. Resistors should be ± 10 per cent, except those connected to S2B, which must be ± 5 per cent, or better still ± 1 per cent. The specified prototype semiconductor are all S.T.C./Intermetal types, but in no way imperative.

TR1 is a polarity inverter for those radiation detector types feeding negative pulses to PL1. D1 suppresses positive pulses or components while D2 prevents overload of TR1 on excessive negative pulse amplitudes at PL1. TR2 is the main pulse amplifier stage. It is fed at the base with the positive output pulses from TR1 collector, as well as with the inputs of positive-pulse radiation detectors connected to PL2 and/or PL3. D9 is included here to prevent short-out of PL3 input by the low-impedance output stage of a detector connected to PL2, thus it is not necessary to disconnect the cables of switched off detectors.

* (Ref to Fig. 2.1 for block diagram of STRACE Radiation Meter Unit.)

THRESHOLD LEVELS

VR1 is the collector load of the main pulse amplifier. It is preset to give the response threshold levels marked against PL1 to PL3. D4 suppresses negative pulses or components at TR2 base, and D3 prevents overload of TR2 if excessive positive pulse amplitudes are applied to PL2 or PL3. The diodes D1 to D4 associated with TR1 and TR2 thus make the circuit very tolerant of large differences in input pulse amplitudes. The performance is still perfect even if the pulses fed to PL1, PL2 or PL3 are ten times larger than the specified threshold values. Gain controls are thus not necessary on the front panel.

PULSE EXPANDER

TR3 is a driver emitter follower, to feed the pulse expander from the necessary low source impedance. The pulse expander TR4/TR5 is a transistorised equivalent of the valve-operated pulse expanders already introduced last month in the gamma ray spectrometer kick-sorter amplifier.

TR4 normally rests cut-off, and TR5 conducting. When a trigger pulse arrives via C4, the roles of the two transistors change over for a time determined by C9 or C10 in conjunction with R19. Thereafter, the transistors revert to the resting state of their own accord. The duration of conduction of TR4 in response to each trigger pulse from TR3 is independent of the form or duration of that trigger pulse, being determined solely by C9, C10 and R19.

PUMP INTEGRATOR

During each conduction pulse of TR4, a definite quantity of positive charge is pumped via D6 and R20 into the integrating capacitor C14. S2B switches the appropriate discharge resistor across C14, to establish the different c.p.m. ranges as discussed previously. The other wafer, S2A, of the range switch selects C9 or C10 for determining the pump pulse duration. On the lowest range (f.s.d. = 100 c.p.m.), C9 is in circuit and gives a long pump pulse, whereas the short pump pulse with C10 is used for all other ranges.

The value of the integrating capacitor C14 is 40 μ F, and the net value of the discharge resistance (R32, VR4 and the input impedance of the read-off voltmeter TR7, 8, 9) is 4 megohms for both range 1 and range 2. Due to the different pump pulse duration, range 1 is 100 c.p.m. and range 2 is 250 c.p.m. for full-scale deflection, so that the statistical accuracy is in fact somewhat poorer than 5 per cent on range 1 but somewhat better than 5 per cent on range 2 and all other ranges. This is a compromise made to avoid unduly high values for C14, or unmanageably high circuit resistances.

READ-OFF VOLTMETER

The read-off voltmeter for the integrator capacitor C14 comprises the remainder of the circuit on the right of Fig. 7.1. The design figure is for a 1mA f.s.d. meter and/or chart recorder connected to the output.


TR7, 8, 9 are cascaded current amplifiers to reduce the current drain on the integrator capacitor C14 for the voltage read-off process. VR3 sets a d.c. bias voltage in series with C14 on ranges 1 and 2, to overcome the silicon threshold of TR7, 8, 9. TR6 is in parallel with VR3 and possesses a compensating temperature coefficient to cancel thermal drift of the threshold level of TR7, 8, 9. TR6 must be positioned close to TR7, 8, 9 to sense the same temperature as the latter components.

VR6 and VR7 fulfil the same function as VR3 for the other ranges. VR5 sets the meter sensitivity for all ranges. D8 stabilises the supply voltage for all stages. D7 limits the maximum voltage developed across C14, to prevent damage to the meter M1 or TR7, 8, 9 if the range switch is set to a range too low in relation to the input pulse rate.

Next month: The remaining circuitry for the STRACE radiation meter; this includes the pip generator, audio amplifier, and power unit.

next month!

Build this Radio-Controlled MODEL BOAT

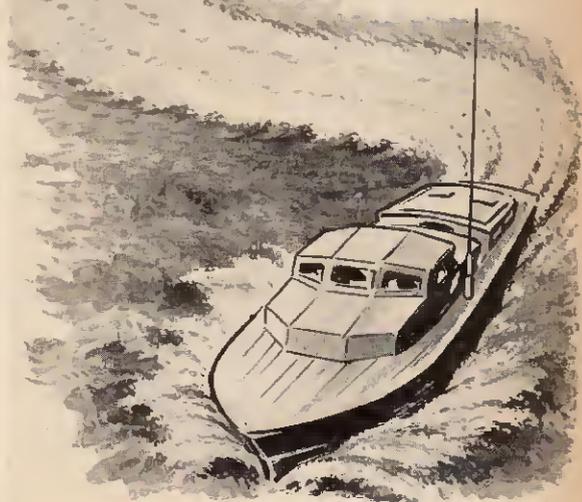

A pleasure to construct and a joy to run, this 34in kit-built diesel-powered high speed craft carries a multi-channel control system which will make it the king-pin of any water on which it is sailed. Incorporates proportional rudder and progressive throttle control for good manoeuvrability, with simultaneous or one-at-a-time operation of these systems. Full how-to-build instructions, with details of transmitter and receiver (including control gear). Begins in next month's issue. Don't miss it!

Other Constructional Projects include:

**DRUMMER'S WHOOSH UNIT
CAMERA TRIGGER**

PRACTICAL ELECTRONICS

JUNE ISSUE ON SALE FRIDAY MAY 17

Order your copy now!

SEMICONDUCTOR

BASICS

By G. J. KING

6—OTHER SEMICONDUCTORS

This series has so far dealt with the more commonly used members of the semiconductor family, and in this concluding article the aim is to consider briefly some of the more recent developments using semiconductor materials.

TUNNEL DIODE

The tunnel diode action differs considerably from the conventional diode. The main difference concerns the reverse current characteristic which reveals that the diode is highly conductive for all values of reverse voltage (see Fig. 6.1); the forward current changes with increasing forward voltage.

Initially, the forward current increases with forward voltage in the normal way up to current I_p due to forward voltage V_p . As the voltage is further increased the current starts to fall, and subsequently falls into a deep valley before it starts rising again to follow the normal diode forward characteristic. This is called a negative resistance characteristic because it is opposite to ordinary resistive current flow.

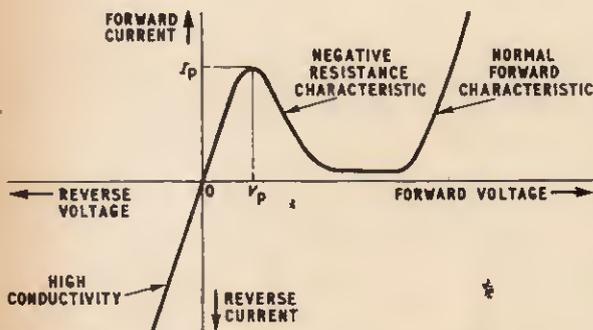


Fig. 6.1. Characteristics of tunnel diode. Note the negative resistance zone and that high conductivity occurs in the reverse direction

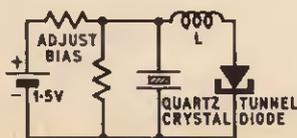


Fig. 6.2. Simple crystal-controlled oscillator using tunnel diode

The depletion layer (potential barrier or "space charge" region) is much narrower than in conventional junction diodes due to a very high concentration of p - and n -type impurities in the basic crystal. Hence, electrical charges are encouraged to traverse the junction by an action called tunnelling.

In most applications the tunnel diode is biased so that the operating point is established in the negative resistance region, and it is suitable for use as an amplifier, detector, oscillator, high-speed switch and rectifier. This latter aspect may seem strange in view of the high reverse conductivity.

Conventional rectifiers are arranged for substantial current flow in the forward direction, but extremely small in the reverse direction. Tunnel rectifiers, on the other hand, are arranged for substantial reverse current flow at very low voltages and much smaller forward current due to the negative resistance effect. This means that tunnel diodes can provide efficient rectification at much smaller signal voltages than conventional rectifiers, but note the reversed polarity requirements (for which reason they are sometimes called "back diodes").

Their amplifying attributes are particularly valuable at microwave frequencies (above 300MHz) due to low noise operation and low current demands.

Stabilisation assumes great importance when the device is arranged as an amplifier, for it has a great tendency to oscillate more freely than to amplify without oscillating. This results from the wideband negative resistance characteristic which, when the amplifier is really well designed, can yield gain over a bandwidth in excess of an octave without variable tuning.

There is no trouble at all in getting a tunnel diode to oscillate, even with only a fraction of a volt bias. A basic oscillator circuit using a quartz crystal as control is given in Fig. 6.2. This yields a high range of harmonics because as the diode oscillates it swings continuously from the low voltage state, through the unstable negative resistance region to the high voltage state.

INTEGRATED SCREEN TRANSISTORS

Early transistors were troubled with a high output/input feedback capacitance which called for neutralising techniques in high gain amplifying applications to prevent the amplifier from changing into an oscillator.

In ordinary transistors the unwanted feedback capacitance stems from the comparatively large bonding areas required for the emitter and base leadouts. The

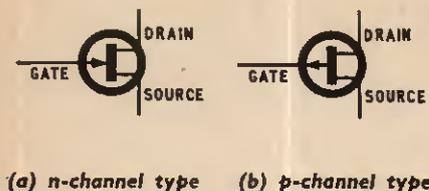


Fig. 6.3. F.E.T. symbols

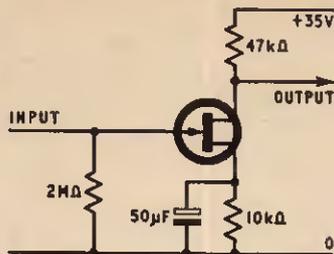


Fig. 6.4. F.E.T. audio amplifier circuit



Fig. 6.5. Make-up of silicon controlled rectifier (see text)

effect of this causes a portion of the output signal to get back to the input of the transistor in phase with the real input signal, thereby creating conditions for positive feedback. Even though oscillation may not actually occur the effect can distort the response characteristics of the amplifier.

The "integrated screen" is a section of diffused semiconductor beneath the base bonding area. Feedback capacitance is considerably reduced making them suitable for intermediate-frequency amplifiers in particular. Their use ensures that the response characteristics retain a close tolerance even when the equipment is mass produced.

FIELD EFFECT TRANSISTORS

The field effect transistor differs from the type of transistor that we have looked at so far, in that it is a voltage amplifier (as is the thermionic valve) rather than a current amplifier. It has a very high input impedance (millions rather than thousands of ohms) stemming from reverse biasing of the input junction required for normal operation. It will be recalled that the ordinary transistor is biased on the emitter/base junction for forward conduction, and it is this which endows it with the relatively low input impedance.

Basically, the f.e.t. consists of a slice of high resistance semiconductor sandwiched between two wafers of low resistance semiconductor having either *p*- or *n*-type characteristics. One end of the high resistance slice is called the source and the other end the drain. The two wafers are connected together to form what is called the gate.

The f.e.t. also differs from the ordinary transistor in that its action is governed only by one type of current carrier—either the electron or the hole—and for this reason it is sometimes termed "unipolar". Its symbol, too, is different, as shown in Fig. 6.3, where (a) is an *n*-channel type and (b) a *p*-channel type, the carriers being electrons and holes respectively.

Sectional view through a typical Texas f.e.t.



Fig. 6.4 shows basic f.e.t. amplifier stage, using an *n*-channel device. While the drain polarity is positive on the *n*-channel type, it is negative on a *p*-channel device, and the latter often incorporates a resistive potential divider across the supply, with the junction connected to the gate.

THYRISTOR

The thyristor (or silicon controlled rectifier) is a junction diode with four semiconductor layers in *npnp* formation, as shown in Fig. 6.5. The end *p*-type is called the "anode" and the end *n*-type the "cathode". The sandwiched *p*-type is the "gate" or triggering electrode.

Owing to the four-layer make-up, current will not flow from cathode to anode (or vice versa) under ordinary conditions. However, when a pulse is applied to the gate, current is allowed to flow in the forward direction from anode to cathode.

When the polarity of the applied source is reversed the thyristor, like an ordinary diode, only passes a small leakage current. Unlike an ordinary diode, it will not pass forward current again when the polarity changes back, that is, not until it is once more gated or triggered.

The gating pulse controls the instant during a forward input pulse at which diode conduction starts. Once triggered, conduction is maintained as long as the supply polarity is correct and until the forward current falls below a small holding value. In this way, the thyristor is considered as the semiconductor version of the thyatron trigger valve.

STRAIN GAUGE PRINCIPLE

Finally, a word or two about the semiconductor strain gauge principle. While the inherent resistivity of a piece of semiconductor like silicon depends on the various factors that we have already discussed, like the addition of impurities, heat and light, it also depends on mechanical strain. That is, by twisting, bending, or straining a small chip of semiconductor the crystal lattice is "distorted" and a change in resistivity occurs. This is the basic strain gauge principle, currently employed in various commercial and domestic devices.

A very interesting and fairly recent application of the principle is adopted in the strain gauge pick-up cartridge. The well-known crystal cartridge employs the strain gauge principle, but more recently has been replaced by the ceramic type. Very recent strain gauge pick-ups use a very small chip of silicon, less than 0.01in long and less than 0.00001in in cross section.



Multivibrator

AN ELECTRONIC SWITCH

LAST month's beginners project explored the light dependent resistor (l.d.r.) and its use as a "light-operated switch". This month's project demonstrates another "electronic" switch, namely the multivibrator.

The multivibrator is basically a two transistor circuit in which one transistor is switched on and the other off, i.e. the circuit has two distinct "states", and may be regarded as an electronic two-pole on/off switch, sometimes referred to as a "Flip-Flop".

To demonstrate the action of the multivibrator, two lamps have been inserted in the circuit and these flash on and off as first one transistor is switched on and then the other.

CIRCUIT

The circuit diagram (Fig. 1) has numbered circles, which represent the terminal strip connections; these are also indicated on the wiring diagram in Fig. 2.

The two transistors TR1 and TR2 employed in this circuit are inexpensive *npn* types 2N2926 readily available from most components shops, and advertised elsewhere in the magazine.

The collector of TR1 is capacitively coupled to the base of TR2 by C1, and the collector of TR2 is coupled to the base of TR1 by C2. These capacitors are electrolytic types and the polarities must be adhered to, see Figs. 1 and 2.

The cross-coupling of the multivibrator circuit produces what, in effect, is an oscillator, due to the feedback action of the capacitors. Oscillation is started by the unbalance in each half of the circuit due to component tolerances. The output waveform at the collector of each transistor is almost square.

THE OPERATION

When power is first applied to the circuit from the battery the unbalance between each half of the circuit

pushes one transistor towards current cut-off and the other towards full conduction.

Let us assume at the start that TR1 and LP1 is switched on and TR2 is off; the voltage at TR1 collector charges C1 because the collector end of C1 is less negative than the base of TR2. At the same time, the base of TR2 becomes negative bringing it into conduction from its off state and switches LP2 on.

The capacitor C1 discharges through VR1 and C2 starts charging, making the base of TR1 go negative.

The result is alternative conduction through TR1 and TR2.

The flow of current in the base of the transistors causes a larger flow of current in the collectors and it is this larger current which drives the lamps.

The timing of the switch-over is determined by the values of the capacitors, the amount of charge on them, and the value of resistors R1, R2, and VR1, through which the charge leaks away.

SWITCHING TIME ADJUSTMENT

By adjusting the setting of the potentiometer VR1, the value of the resistance affecting the discharge of each capacitor can be altered to change the switching time, so that one bulb will be on for a different period of time compared with the other. In fact, as one bulb comes on for a longer time, the other does so for a shorter time. This is called altering the mark-to-space ratio of the generated waveform.

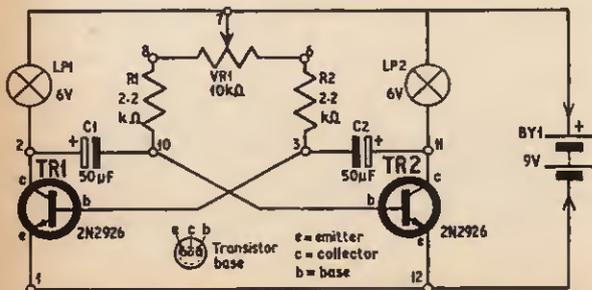


Fig. 1. Circuit diagram of the multivibrator. The numbered circles represent the terminal strip connections

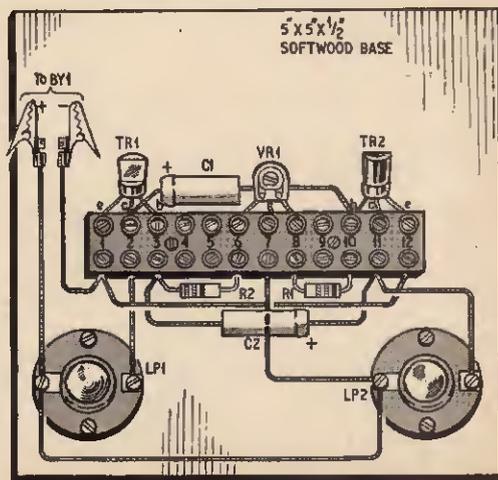


Fig. 2. Constructional and wiring details. Note the transistor and capacitor connections

Low consumption 6V lamps are used with a current rating of 0.06A (60mA), but lamps rated at 0.1A (100mA) will work just as well. Higher ratings should not be used unless the transistors are changed for higher current types.

USING PNP TRANSISTORS

If the reader wishes to use *pnp* transistors the capacitor polarities must be changed round, i.e. the positive ends are connected to the bases of the transistors. Also, the battery connections will have to be reversed, i.e. negative terminal connected to the lamps.

CONSTRUCTION

Commence the construction by cutting a softwood baseboard $5\text{in} \times 5\text{in} \times \frac{1}{2}\text{in}$. The next stage is to wire the 12-way terminal strip before mounting this in position on the baseboard. A plastics sleeved link wire should be inserted between terminals 1 and 12. The two resistors R1 and R2 should be positioned between terminals 3 and 6; 8 and 10.

The outer leads of the subminiature potentiometer VRI should be carefully bent so that they can be inserted in terminals 6, 7, and 8, see Fig. 2. The electrolytic capacitors C1 and C2 are positioned in terminals 2 and 10, 3 and 11. It is important that C1 and C2 are wired to the correct terminals; reference should be made to Fig. 2.

Finally, before mounting the terminal strip on the baseboard, the transistors should be mounted on the strip, see Fig. 2. Particular care should be taken to ensure that the transistor leads are wired to the correct terminals, as they can be damaged if wired incorrectly.

FINAL ASSEMBLY

The terminal strip and m.e.s. bulb holders can now be screwed to the baseboard, see wiring diagram for relative positions. The terminal strip should be checked against the wiring diagram and screwed to the baseboard with two $\frac{3}{4}\text{in}$ No. 4 countersunk woodscrews. The m.e.s. bulb holders are screwed to the baseboard with four $\frac{3}{4}\text{in}$ No. 4 countersunk wood screws.

COMPONENTS . . .

Resistors

R1 2.2k Ω R2 2.2k Ω
10%, $\frac{1}{4}$ watt carbon

Potentiometer

VRI 10k Ω linear subminiature preset

Capacitors

C1, 2 50 μF electrolytic, 12V (2 off)

Transistors

TR1, 2 2N2926 (2 off)

Lamps

LPI, 2 6V 0.06A (60mA) (2 off)

Miscellaneous

BY1 9V type PP9 battery
One 12-way plastics terminal block
Two m.e.s. bulb holders, batten mounting
Wooden baseboard $5\text{in} \times 5\text{in} \times \frac{1}{2}\text{in}$
Two miniature crocodile clips or battery connectors
Six $\frac{3}{4}\text{in}$ No. 4 countersunk wood screws
Plastic covered, single core copper wire



Total cost £1 approx.

A lead from terminal 11 is taken to LP2 bulb holder. Two leads are taken from the other connecting screw and wired to terminal 8 and LPI bulb holder, see Fig. 2. The other connecting screw of LPI should be wired to terminal 2.


Finally, the battery leads should be wired in circuit. The negative lead is taken from terminal 1 and clipped on the battery negative connector by a miniature crocodile clip. The battery positive lead is taken from terminal connecting both lamps together.

The crocodile clip acts as a simple switch if removed when not used. All the wiring should be given a final check before making the final battery connection. The multivibrator lamps will start flashing or switching on and off as soon as the supply is connected.

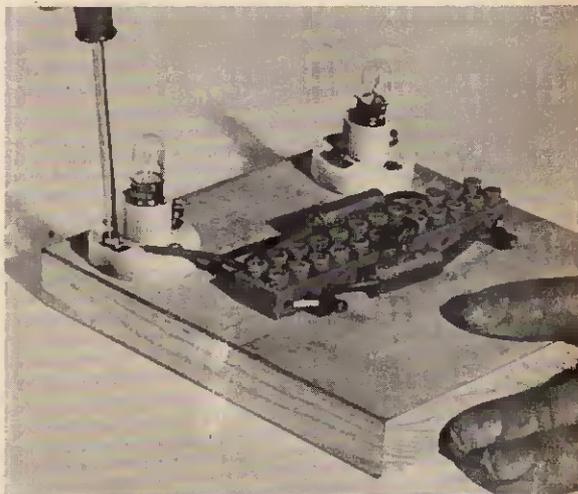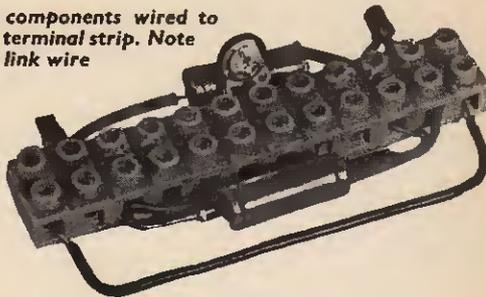All components wired to the terminal strip. Note the link wire



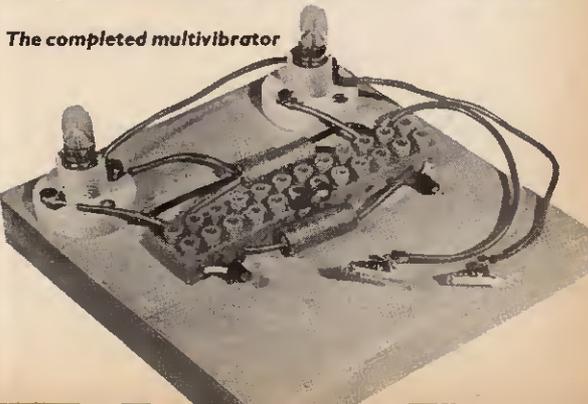Fixing a connecting lead to one of the m.e.s. bulb holders



The completed multivibrator

THE detailed explanation concerning the operation of UNIT "A" is continued in this month's article, with further practical examples.

We resume by considering the use of the operational amplifier as an integrator.

An operational amplifier will be handling time as well as voltage when acting as an integrator, so some means must be found of inserting intervals of time onto the computer. One method is to employ external oscillators to provide known functions of time in terms of frequency. An input to an integrator might consist of a steady d.c. voltage which is switched on for a time t (step function or square wave), or alternatively, a sinusoidal voltage of frequency f and period $1/f$.

If a graph is drawn of the resulting integrator output function, and this is the form that answers to problems involving change or motion will usually take, the X axis of the graph will be calibrated in intervals of time, with voltage on the Y axis. It follows that an oscilloscope, which also uses time on the X axis and voltage on the Y axis, can provide a convenient form of output display, especially when an integrator is operating at high speed.

The operational amplifier is converted to an integrator when a capacitor C_f is inserted, in place of a resistor, in the feedback path; see Fig. 5.1. When an input voltage $-E_{in}$ is applied to the integrator by means of a simple switch S for a time t , the output E_o will take the form of an increasing ramp voltage proportional to t with slope

$$-E_{in} \frac{1}{R_{in}C_f}$$

Note that the operational amplifier will continue to invert an input voltage even when used as an integrator.

THE INTEGRATOR IN EQUATION SOLVING

The electronic analogue computer does provide a powerful technique for obtaining rapid solutions to problems involving calculus, which cannot be equalled either by numerical methods or by a digital computer.

If differentiation and integration are regarded as straightforward mathematical operations, it will be found that the terms of, say, a second order differential equation can be manipulated on the computer in much the same way as the terms of a "steady state" algebraic equation.

For example, when an equation term y is differentiated against time its derivative dy/dt is obtained, and a second differentiation yields the second derivative d^2y/dt^2 . The reverse process is where integration of the second derivative d^2y/dt^2 produces the first derivative dy/dt , and another integration gives y as the result.


Fig. 5.2 shows how a simple integrator can handle equation terms. Combined operations are made possible by cascading integrators, while using coefficient potentiometers and computing component ratios for summation, multiplication, and division (Fig. 4.1).

The process of differentiation, although feasible if care is taken, is generally avoided on analogue computers because it gives rise to unstable operational amplifier configurations, but this imposes only a slight limitation since integration can be employed—in the majority of cases—in place of differentiation.

INTEGRATOR ACCURACY

The transfer accuracy of an operational amplifier, when it is used as an integrator, will be theoretically limited by its finite value of open-loop gain. However,

ANALOGUE COMPUTER

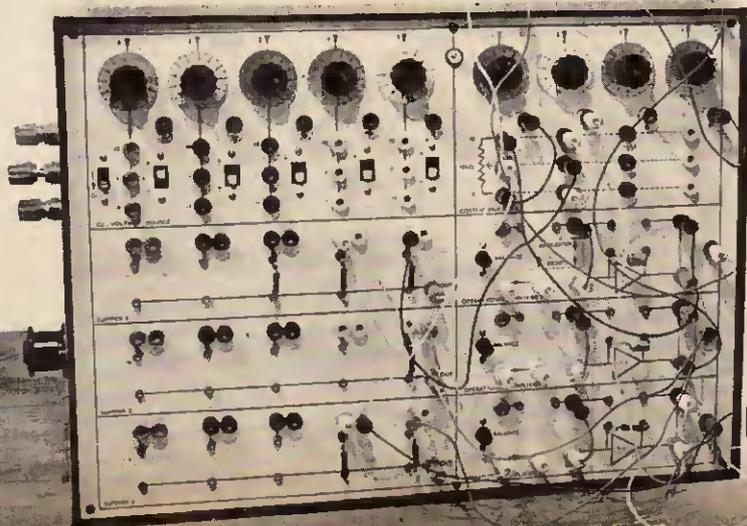

PEAC

By
D. BOLLEN

EXCEL

in

ELECTRONICS

Through this ICS 3-way Training Method:

1

MASTER THE THEORETICAL SIDE
From basic principles to advanced applications, you'll learn the theory of electronic engineering, quickly and easily through ICS. That's because each course is set out in easy-to-understand terms.

2

MASTER THE PRACTICAL SIDE
ICS show you how to develop your practical abilities in electronic engineering—*alongside* your theoretical studies. It's the only sure way to success. All training manuals are packed with easy-to-follow illustrations.

3

MASTER THE MATHEMATICAL SIDE
To many this aspect is a bitter problem. Even more so because no electronic engineer is complete without a sound working knowledge of maths. But new ICS teaching makes mathematics easier to learn.

Wide range of courses available include:
Radio/TV Engineering and Servicing, Closed Circuit TV, Electronics, Electronic Maintenance, Servomechanisms, Computer Engineering, Numerical Control Electronics, etc.

EXPERT COACHING FOR:
INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS
CITY AND GUILDS TELECOMMUNICATION TECHNICIANS
CITY AND GUILDS ELECTRONIC SERVICING
R.T.E.B. RADIO/TV SERVICING CERTIFICATE
RADIO AMATEURS' EXAMINATION
P.M.G. CERTIFICATES IN RADIOTELEGRAPHY

Build your own radio, transistor portable, and professional-type test instruments with an ICS Practical Radio and Electronics Course. Everything simply explained and easy to handle. All components and tools supplied. For details post coupon below.

Member of the Association of British Correspondence Colleges

FOR FREE HANDBOOK POST THIS COUPON TODAY
I.C.S., Dept. 131, INTERTEXT HOUSE,
PARKGATE ROAD, LONDON, S.W.11

NAME _____

ADDRESS _____

OCCUPATION _____ AGE _____ 5/68

INTERNATIONAL CORRESPONDENCE SCHOOLS

ORGAN BUILDERS! N.P.N. Sil. Planar Transistors. All Tested, 1/6 each or £5.0.0 per 100.

TRANSISTOR BARGAIN SALE! NEW STOCK AT UNBEATABLE PRICES!

OC4, OC4S, OC81D now only 1/8 each! £8.0.0 per 100
 OC71, OC73 equivalent 1/- each! £8.0.0 per 100
 ASY23 Switching Transistors 2/6 each! £10.0.0 per 100
 2N723 N.P.N. Silicon Planar, 300mW, 200Mc/s. High speed switching .. 2/6 each!
 2N723 N.P.N. Silicon Planar, Epitaxial, 300mW, 300Mc/s .. 2/6 each!
 2N744 N.P.N. Silicon Planar, Epitaxial, 300mW, 300Mc/s .. 2/6 each!
 AZ212 P.N.P. Germanium Alloy Diff. low noise V.H.F. amplifier .. 2/6 each!
 Complete sets of transistors for radio:
 2G344A/2G345A/2G371A/2G378A/2G378A + diode .. 10/- only!
 GET120, 2 wats. Heat sink included .. 3/6 each!
 Transistor Driver Transformers .. 2/6 each!
 Transistor Output Transformers (suitable for our kits above) .. 2/6 each!
 OC28 Equivalent .. 5/- each!
 BZY13, 6 amp rectifiers .. 3/6 each!
 Light sensitivity transistors similar to OC71 .. 2/- each!
 UNMARKED, UNTESTED TRANSISTORS TO CLEAR .. 7/6 for 50!
 Silicon diodes. Make excellent detectors. Also suitable for keying electronic organs, 1/- each; 20 for 10/-

BY100 type rectifiers. SPECIAL REDUCED PRICE! ONLY 2/6 each; 24/- doz.; £7.10.0 per 100; £50.0.0 per 1,000.

ELECTROLYTIC CONDENSERS! FANTASTIC SELECTION!

50µF 450 volts .. 1/3	20 + 4	275 volts .. 10d
64µF 275 volts .. 1/3	32 + 32	275 volts .. 1/6
80µF 15 volts .. 1/3	8 + 16	450 volts .. 2/3
500µF 25 volts .. 10d	50 50	275 volts .. 2/-
	40 + 40 + 20	275 volts .. 1/8
16/16/16, 350V .. 2/2	100/100, 50V .. 3/2	12,000µF, 30V .. 16/-
50/50/50, 350V .. 2/7	150/300, 300V .. 4/-	30,000µF, 30V .. 25/-
1,000µF, 70V .. 3/2	250/250, 325V .. 4/-	1,000µF, 15V .. 1/6
100/250, 275V .. 3/2	2,000/2,000, 25V .. 4/6	1,000µF, 18V .. 1/8
100/200/200/50, 275V 4/-	250µF, 50V .. 10d	500µF, 15V .. 10d
3,000µF, 35V .. 3/2		
0.25µF .. 3 volt 3µF .. 3 volt 64µF .. 2.5 volt		
1µF .. 50 volt 3µF .. 6 volt 64µF .. 9 volt		
1µF .. 350 volt 3µF .. 50 volt 100µF .. 3 volt		
1.2µF .. 16 volt 8µF .. 275 volt 100µF .. 6 volt		
2µF .. 3 volt 10µF .. 25 volt 100µF .. 9 volt		
2µF .. 9 volt 15µF .. 150 volt 150µF .. 12 volt		
2µF .. 70 volt 20µF .. 3 volt 200µF .. 3 volt		
2µF .. 150 volt 20µF .. 6 volt 200µF .. 4 volt		
2µF .. 350 volt 20µF .. 9 volt 200µF .. 16 volt		
2.5µF .. 16 volt 20µF .. 15 volt 250µF .. 2.5 volt		
2.5µF .. 25 volt 25µF .. 8 volt 250µF .. 9 volt		
3µF .. 35 volt 25µF .. 12 volt 250µF .. 2.5 volt		
3µF .. 25 volt 25µF .. 15 volt 250µF .. 9 volt		
3.2µF .. 6.4 volt 25µF .. 25 volt 350µF .. 10 volt		
4µF .. 4 volt 30µF .. 6 volt 400µF .. 2.5 volt		
4µF .. 12 volt 30µF .. 10 volt 400µF .. 15 volt		
4µF .. 75 volt 30µF .. 3 volt 500µF .. 4 volt		
4µF .. 100 volt 40µF .. 3 volt 500µF .. 6 volt		
6µF .. 6 volt 40µF .. 6.4 volt 640µF .. 2.5 volt		
6µF .. 25 volt 50µF .. 9 volt 750µF .. 12 volt		
6µF .. 3 volt 50µF .. 12 volt 750µF .. 12 volt		

All at 1/- each, 9/- per dozen. Mixed Packets of 20 (our selection) 10/-.

PAPER CONDENSERS

0.001µF .. 500 volt 0.02µF .. 600 a.c.	0.25µF .. 350 volt
0.001µF .. 1000 volt 0.02µF .. 350 volt	0.5µF .. 350 volt
0.002µF .. 500 volt 0.1µF .. 350 volt	0.5µF .. 500 volt
0.005µF .. 700 volt	

All at 15/- per 100, 3/- per dozen. Mixed Bags of 100 (our selection) 16/-.

MULLARD POLYESTER CAPACITORS. ALL HALF PRICE

0.0022µF 400 volts .. 4d	0.15µF 150 volts .. 7d
0.0018µF 400 volts .. 4d	0.22µF 100 volts .. 7d
0.0015µF 400 volts .. 4d	0.27µF 160 volts .. 8d
0.001µF 400 volts .. 4d	0.055µF 125 volts .. 7d
0.01µF 100 volts .. 4d	1µF 125 volts .. 1/6

58P Tubular pulse ceramic .. 6d each

VERY SPECIAL VALUE! Silver Mica, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values, 10/- per 100.

RESISTORS. Give-away offer! Mixed types and values, 1 to 1/2 watt. 5/6 per 100 at 5/- per 1,000. Individual values, 8d each. Also 1 to 3 watt close tolerance. Mixed values, 7/6 per 100; 55/- per 1,000.

WIRE-WOUND RESISTORS. 1 watt, 3 watt, 6 watt, 6d each, 7 watt and 10 watt 9d each.

CONNECTING WIRE. THIN, P.V.C. INSULATED. 10yd, 1/-; 100yd, 7/6; 500yd, 25/- (post 4/6); 1,000yd, 40/- (post 6/-).

VALVES. BRAND-NEW AND BOXED. ROCK-BOTTOM PRICES!

DY87 .. 6/9	BY86 .. 6/9	PC186 .. 8/5
EAB080 .. 7/-	EY87 .. 6/9	PF200 .. 11/8
EC082 .. 7/4	FAB080 .. 7/1	PL86 .. 10/1
EC083 .. 7/4	PC7 .. 10/6	PL81 .. 5/5
ECL80 .. 7/1	PCC84 .. 7/4	PL83 .. 8/5
ECL86 .. 8/5	PCC89 .. 10/6	PL84 .. 6/8
EF80 .. 7/1	PCF80 .. 8/5	PL600 .. 12/5
EF85 .. 7/1	PCF86 .. 10/1	PY32 .. 9/-
EF183 .. 9/5	PCL82 .. 8/6	PY81 .. 6/9
EF184 .. 8/5	PCL84 .. 8/5	PY82 .. 4/9
EY81 .. 6/9	PCL85 .. 8/5	PY900 .. 6/9

A further 10% discount will be given on lots of 50 of any one type.

RECORD PLAYER CARTRIDGES
 Sonotone Mono, 10/-; Acos GF67/29 Mono, 15/-; Acos GP91/36C Stereo compatible, 20/-; Acos GP94/1 Stereo, 25/- . All with needles.

Signal Injector Kit—10/- . Signal Tracer Kit—10/-.

VEROBOARD. All sizes in stock.

2 1/2in x 1in 0.15 matrix .. 1/1	17in x 3 1/2in 0.15 matrix .. 14/8
2 1/2in x 3 1/2in 0.15 matrix .. 3/3	
2 1/2in x 5 1/2in 0.15 matrix .. 8/11	5in x 2 1/2in 0.1 matrix .. 3/11
3in x 3 1/2in 0.15 matrix .. 3/11	3 1/2in x 2 1/2in 0.1 matrix .. 3/9
3in x 5in 0.15 matrix .. 5/6	5in x 3 1/2in 0.1 matrix .. 5/2
17in x 2 1/2in 0.15 matrix .. 11/-	3 1/2in x 3 1/2in 0.1 matrix .. 8/11

SPECIAL OFFER!
 Cutter and 5 Boards 2 1/2in x 1in, 9/8. Cutter only, 7/8. Pin Insert Tool, 9/6. Terminal Pin, Pack of 20, 3/6.

BARGAIN OFFER!
 For only Multimeters, 1,000Ω per volt, 45/-; 20,000Ω per volt, 80/-.

Orders by post 6/-.

G. F. MILWARD, 17 PEEL CLOSE, DRAYTON BASSET, Staffs.
 Please include suitable amount to cover postage. Stamped addressed envelope must be included with any enquiries.
 For customers in the Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8. (All POST orders to Drayton.)
MINIMUM ORDER 10/-


PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4" x 2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet Printed Circuits for Amateurs. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for

40 TRANSISTORISED PROJECTS

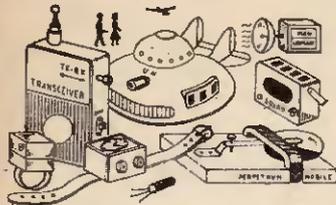A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



EXPERIMENTER'S
PRINTED CIRCUIT KIT
8/6

Postage & Pack. 1/6 (UK)

Commonwealth:

SURFACE MAIL 2/-


AIR MAIL 8/-

Australia, New Zealand,
South Africa, Canada

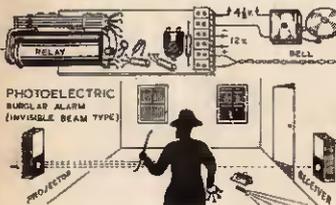(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRIFLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62" x .92" x .25". (11) Wristwatch Radio 1.15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) I-vale Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Cadmium Sulphide Photocell, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
39/6

Postage & Pack. 2/6 (UK)

Commonwealth:

SURFACE MAIL 3/6

AIR MAIL £1.0.0

Australia, New Zealand,
S. Africa, Canada & U.S.A.
Also Essential Data Circuits
and Plans for Building

12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-Light Alarm. (4) Relay-Less Alarm. (5) Warbling-Tone Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector Modulator. (9) Mains Power Supply. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood for building: 1, Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

JUNIOR PHOTOELECTRIC KIT

Versatile invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc. for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and pack. 1/6 (UK).

SUBMINIATURE SOLAR BATTERY. 10/6. Post and pack. 1/-. Output in Bright Sunlight: 2 v./250 microamps. Build that Sun Powered Wristwatch Radio for your Holiday and amaze your friends. Plans supplied free with each battery.

YORK ELECTRICS, 333 York Road, London, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

SILICON RADIATION DETECTOR

The NUTRONICS semiconductor radiation detector ND7 is a compact, low cost, versatile radiation detector with a window area of 7mm² and Alpha energy resolution of 50-100 Kev. FWHM, which has been expressly designed for use in educational establishments and by amateur experimenters.



The NUTRONICS semiconductor radiation detector ND7 detects Alphas, Beta, Gamma Radiation, Fission Fragments, X-rays and Protons.

Send for technical data sheet.

SOLID STATE NUTRONICS LTD.

5A Voltaire Road, London, S.W.4

Tel.

01-874 8608

R.S.T. VALVE MAIL ORDER CO.

144 WELLFIELD ROAD, STREATHAM, S.W.16
Special 24 Hour Mail Order Service

A61	7/6	EL90	6/-	QQV03/10	Z803C	15/-	11E5	42/-	9003	9/-
AZ31	9/6	EL96	9/6	Q02	0A2	6/3	12AC0	10/-	BY100	5/6
CIG	12/-	EL860	20/-	QQV3/20	0B2	6/-	12A26	11/-	TRANSISTORS	
CY30	16/3	EL90	20/6	Q03	0C3	5/6	12A26	9/6	4/3	4/3
DAF91	4/-	EL821	6/-	QQV04/15	OZ4	4/6	12A7	4/6	18131	4/3
DAF96	6/9	EL822	16/-	1001	1B3C7	5/6	12A7	3/9	2162	4/3
DOCC90	7/-	ELL80	20/-	QQV06/30	LR5	5/6	12A7	4/6	20210	12/6
DP91	3/-	EM34	20/-	25.5.0	2D21	5/-	12A7	6/3	20381	5/-
DP96	6/9	EM36	7/6	QQV5/10	2E26	20/-	12A7	4/6	20410	6/6
DEH01	80/-	EM81	70/-	Q07	3H44Y	8/9	12B36	5/0	20401	5/6
DH77	4/6	EM84	7/6	Q870/20	5/0	3A5	12E1	17/0	20402	6/6
DK91	5/6	EX32	35/-	Q875/20	5/0	3C46	12K7G7	6/-	20414	6/6
DK02	8/-	EY51	7/6	Q878/60	20/-	4X150A	12K8GT	8/-	20415	6/6
DK96	7/6	EY81	7/6	Q883/3	7/3	5H44Y	12Q7GT	4/6	20416	6/6
DL65	15/-	EY83	8/6	Q892/10	4/6	6T44	12R24T	18/9	20417	6/6
DL92	4/6	EY84	7/6	Q896/10	5/6	6V46	12R24T	19/6	20418	9/6
DL94	5/6	EY86	7/6	Q896/10	5/6	6V46	12R24T	19/6	20419	9/6
DL96	7/6	EZ40	8/-	Q8100/15	15/-	12Z4	12R24T	19/6	20420	9/6
DL910	12/6	EZ41	10/-	Q8100/16	8/-	12Z4	12R24T	19/6	20421	9/6
DL916	30/-	EZ60	5/6	Q8150/30	5/6	6J6012	13R24T	19/6	20422	9/6
DL913	30/-	EZ61	3/6	Q8150/36	6/6	6AK5	13R24T	19/6	20423	9/6
DM70	5/-	GT10	37/6	Q01	6AK6	5/0	13R24T	19/6	20424	9/6
DY86	6/-	GZ30	10/-	Q130/33	30/-	6AL5	13R24T	19/6	20425	9/6
DY87	6/-	GZ32	9/6	Q130/30	20/-	6AM6	13R24T	19/6	20426	9/6
EB8CC	12/-	GZ34	11/-	Q130/80	20/-	6AN8	13R24T	19/6	20427	9/6
EB18D	17/6	GZ37	12/6	Q130/80	20/-	6AQ4	13R24T	19/6	20428	9/6
EB38C	22/6	H33	12/6	Q130/80	20/-	6A4	13R24T	19/6	20429	9/6
EABC90	7/-	HL11D10	13/6	QV03-12	10/-	6A80	13R24T	19/6	20430	9/6
EAF42	10/-	KT61	12/6	QV04-7	12/6	6A87	13R24T	19/6	20431	9/6
EB91	3/-	KT66	16/-	QV05-25	17/-	6AT6	13R24T	19/6	20432	9/6
EB93	7/-	KT67	15/-	QV06-30	20/-	6A16	13R24T	19/6	20433	9/6
EB90	4/6	KT61(7C3)	15/-	R10	15/-	6B4G	13R24T	19/6	20434	9/6
EBF80	7/-	KT81(GEC)	18/-	R17	8/-	6BA4	13R24T	19/6	20435	9/6
EBF83	8/6	KT83	18/-	R18	7/6	6BE6	13R24T	19/6	20436	9/6
EBF89	8/6	KT88	27/6	R19	7/6	6BH6	13R24T	19/6	20437	9/6
EBI21	11/-	KTW61	10/-	R43/500	80/-	6J6	13R24T	19/6	20438	9/6
EBI31	27/6	KTW62	10/-	S300	35/-	6BN9	13R24T	19/6	20439	9/6
EBI32	27/6	MLA	12/6	SP41	3/6	6BQ7A	13R24T	19/6	20440	9/6
EC040	9/6	N37	17/6	SP61	3/6	6BR7	13R24T	19/6	20441	9/6
EC081	3/9	N78	15/-	STV280/40	4/6	6BR8	13R24T	19/6	20442	9/6
EC082	4/9	PC86	11/6	STV260/80	9/6	6BW4	13R24T	19/6	20443	9/6
EC083	6/3	PC88	11/6	PC97	8/9	6C2150	12/6	0C46	2/6	
EC085	5/6	PC92	9/6	PC97	8/9	6C2150A	12/6	0C46	2/6	
EC088	7/-	PC97	8/9	PC97	8/9	6C2150A	12/6	0C46	2/6	
EC090	6/6	PC98	9/6	PC97	8/9	6C2150A	12/6	0C46	2/6	
EC092	7/-	PC98	11/6	PC97	8/9	6C2150A	12/6	0C46	2/6	
EC093	11/-	PCC189	11/6	Q25	13/6	6CL6	8/6	180182	9/6	
EC142	11/-	PCF80	7/-	Q26	13/6	6CW4	12/-	190183	8/6	
EC183	8/6	PCF80	9/-	U101	13/6	6D4	13/6	801	8/6	
EC184	9/6	PCF81	10/-	U301	16/6	6DK4	9/-	803	35/6	
EC186	7/-	PCF802	10/-	U404	13/6	6E28	13/6	807	37/6	
EC192	7/-	PCF806	13/6	U24	22/6	6E24	13/6	811	37/6	
EC198	10/3	PCL82	7/6	UACB80	6/-	6E26	12/6	813	75/6	
EC199	10/3	PCL83	9/3	UAF49	10/3	6E28	11/6	860A	13/6	
EF9	20/-	PCL84	7/6	UBC41	8/6	6F40	2/6	872A	57/6	
EF37A	7/-	PCL86	9/-	UBC81	8/3	6G3	2/6	5651	7/6	
EF39	6/-	PEN14	20/-	UCB60	6/6	6G7	4/6	566A	8/6	
EF41	10/-	PEN16	20/-	UCB69	7/3	6K7A	2/6	5672	8/6	
EF49	6/6	PEN15DD	10/-	UCB75	7/6	6K86	10/6	5687	10/6	
EF86	6/6	PL200	13/6	UCB121	9/6	6L6C	7/6	5691	25/6	
EF89	5/-	PL36	10/6	UCB42	10/6	6Q7G	5/6	5749	10/6	
EF91	3/6	PL61	8/6	UCB41	6/6	6R7	5/6	5763	10/6	
EF92	2/6	PL82	7/3	UCB43	10/6	6R7GT	4/6	5803	10/6	
EF93	10/6	PL84	9/6	UCB41	10/6	6SN7GT	4/6	6057	10/6	
EF183	6/6	PL90	15/6	UCB81	8/3	6V6	4/6	6058	10/6	
EF184	6/6	PX4	14/6	UCB81	8/3	6V6	4/6	6059	10/6	
EF186	21/6	PY32	10/6	UCB81	8/3	6V6	4/6	6060	10/6	
EF60	10/6	PY32	10/6	UCB81	8/3	6V6	4/6	6061	10/6	
EF63	10/6	PY33	9/6	UCB81	8/3	6V6	4/6	6062	10/6	
EL34	10/6	YF81	9/6	VP45	26/6	7B7	7/6	6063	10/6	
EL41	10/6	YF82	6/6	VR105/30	5/6	7C5	10/6	6064	10/6	
EL42	10/6	YF83	6/6	VR150/30	5/6	7C5	10/6	6065	10/6	
EL51	7/6	YF80	10/6	YF81	6/6	7H7	20/6	6080	25/6	
EL54	7/6	Z30	10/6	Z319	25/6	7Y4	8/6	6086	5/6	
EL56	7/6	QQV02/10	45/6	Z769	35/6	10P13	10/3	6146	25/6	

All valves brand new and boxed. Postage 6d. valve.
OPEN DAILY TO CALLERS 9 a.m.—5.45 p.m. No early closing
C.W.O. Tel. 01-769 0199 & 1649 No C.O.D.

SEND S.A.E. FOR LIST OF 2,000 TYPES

TABLE 5.1

C_f	R_{in}	t
$1\mu F$	$100k\Omega$	2.8sec
	$10k\Omega$	800ms
$0.1\mu F$	$100k\Omega$	280ms
	$10k\Omega$	80ms
$0.01\mu F$	$100k\Omega$	28ms

Maximum value of t for an error of 1%

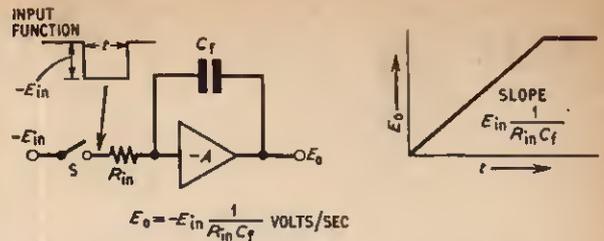


Fig. 5.1. The operational amplifier as an integrator

the situation is much more complicated than with, for example, a summing amplifier (Fig. 3.8) since the amplifier error can no longer be defined in terms of the simple relationship between closed-loop and open-loop gains.

As a guiding principle, integrating amplifiers may have very large values of closed-loop gain provided that the time t of an input function remains small. Closed-loop integrator gains of 1,000 or more are not uncommon in transistor computers, since low voltages and low impedances discourage the use of computing resistors of more than 100 kilohm, and capacitors of more than $1\mu F$ are too bulky. Table 5.1 is calculated for UNIT "A" amplifiers, and sets out the maximum allowable interval t for selected values of C_f and R_{in} , where the amplifier transfer error must not exceed one per cent.

Errors due to unwanted drift voltages also become significant when t is long and C_f is small. The greatest care must be exercised when zero-setting integrators to eliminate offset voltages, for good accuracy at long time intervals. Also, the computer should not be subjected to fluctuations of ambient temperature when computations cover several hours of integrator use.

COMPUTING CAPACITORS

The computing capacitors used for PEAC will normally lie within the range $0.01-1\mu F$, and the three values most commonly employed are $0.01\mu F$, $0.1\mu F$, and $1\mu F$. Polystyrene is the preferred capacitor dielectric, for high insulation resistance, but polyester makes an acceptable second best. Mica, paper, and ceramic capacitors should be avoided.

Small value polystyrene capacitors of ± 1 per cent and ± 2 per cent tolerance are easily obtained, but $0.1\mu F$ and $1\mu F$ precision components are rare and expensive. To get around this difficulty, the bridge circuit of Fig. 5.3 was devised to allow computing capacitors to be made up from specially selected low cost ± 20 per cent capacitors.

The circuit of Fig. 5.3 can be constructed in breadboard form on Veroboard or s.r.b.p., with miniature sockets to take C_x and R_1 . If an audio signal generator is not available to supply the bridge with about 10V r.m.s. at 1kHz, a signal could be obtained from a transistor multivibrator powered by the 25V computer power supply. Headphones serve to detect the null point when the bridge is in balance, and should have an impedance of about 2 kilohms.

The method of making up a computing capacitor of, say, $1\mu F$ is as follows. A capacitor panel of plain or perforated s.r.b.p. is fitted with small turret tags as in Fig. 5.4. A ± 20 per cent capacitor of about $0.68\mu F$ is wired into position on the capacitor panel before it is plugged into the bridge C_x sockets, and a 1 kilohm

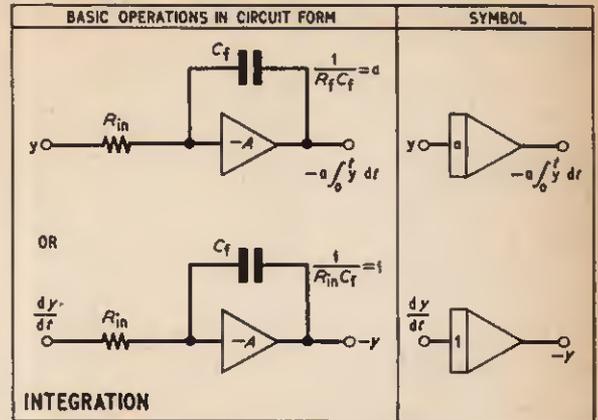


Fig. 5.2. The handling of equation terms by a simple integrator

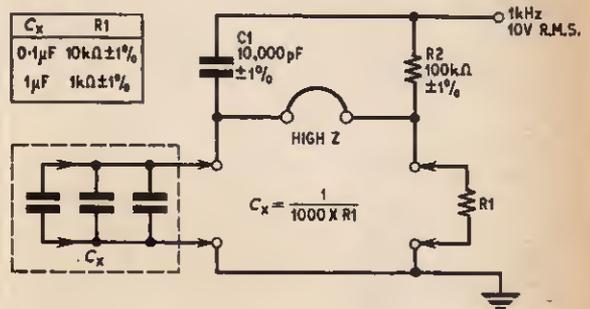


Fig. 5.3. Bridge circuit used for making up computing capacitors

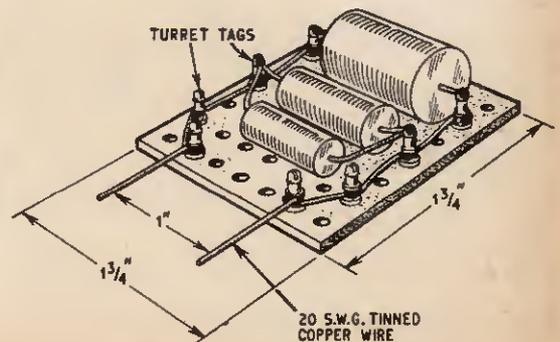


Fig. 5.4. Computing capacitor plug-in panel

resistor is inserted for R1. Assorted polystyrene or good quality polyester capacitors of lower value are then temporarily connected across the capacitor panel to increase C_x by small increments, while listening on the headphones for a drop in the level of the 1kHz tone as C_x approaches $1\mu\text{F}$.

A typical computing capacitor might finally consist of a parallel combination of the following values, $0.68\mu\text{F}$, $0.22\mu\text{F}$, $0.02\mu\text{F}$, and $0.005\mu\text{F}$.

If the required value of C_x is exceeded, the note in the headphones will increase in volume when the null point is passed. Allow capacitors to cool off after soldering, and before making a measurement, as heat can cause a temporary or permanent change in capacitance. With the Fig. 5.3 bridge circuit it is possible to detect increments of less than $0.01\mu\text{F}$ in a nominal $1\mu\text{F}$ capacitor.

DIFFERENTIAL ANALYSIS WITH UNIT "A"

A second order linear differential equation with constant coefficients has become firmly established as the "classic" introduction to differential analysis on the analogue computer.

The equation describes an oscillatory system with variable damping which can be used to simulate indirectly many physical systems, such as the spring pendulum, a tuned LC circuit, or a servomechanism. Also, the equation is easy to set up on the computer, and does not necessarily demand the use of integrator mode switching.

In general form the equation is,

$$a \frac{d^2y}{dt^2} + b \frac{dy}{dt} + cy = f(t) \quad (\text{Eq. 5.1})$$

where a , b , and c are the constant coefficients, y is unknown, and $f(t)$ represents some function of time. Equation 5.1 can be rewritten to suit a particular system by substituting appropriate terms.

Spring pendulum

$$m \frac{d^2y}{dt^2} + \mu \frac{dy}{dt} + ky = f(t) \quad (\text{Eq. 5.2})$$

where m is the mass of a weight suspended on a spring of constant k , which is damped by friction μ . The weight is displaced by an amount y when subjected to a force dependent on $f(t)$.

Tuned LC circuit

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = f(t) \quad (\text{Eq. 5.3})$$

where L is an inductance tuned by a capacitance C , and damped by a series resistance R . Q is the charge in coulombs on C at any instant of time. The current flowing in the tuned circuit is given by dQ/dt , and $f(t)$ represents an input function.

Servomechanism

$$\frac{d^2\theta_o}{dt^2} + 2\zeta\omega \frac{d\theta_o}{dt} + \omega^2\theta_o = \omega^2\theta_i \quad (\text{Eq. 5.4})$$

where θ_o is the angular displacement of the output shaft, ζ the damping factor, ω the angular velocity, and θ_i the angular displacement of the input shaft.

The obvious similarity between the above equations is emphasised when, in Fig. 5.5, it is seen that they all have virtually the same problem layout on the computer.

Furthermore, as the computer will allow operation at almost any fraction or multiple of real time, a spring pendulum and a tuned LC circuit can be simulated simultaneously, and interesting electro-mechanical parallels can be seen to exist between the properties of inductance and mass, resistance and friction, and capacitance and elasticity.

The only real difference between the analogous behaviour of a weight on a spring, a servo shaft, and a tuned LC circuit is that the LC combination will normally resonate at a much higher frequency.

PROBLEM EXAMPLE 3. TUNED CIRCUIT ANALYSIS

UNIT "A" will simulate any series tuned circuit by solving Equation 5.2, and will give answers in the form of a.c. meter readings or oscillograms. Tuned circuits resonating in the MHz region are catered for by slowing down the problem to some convenient decadal fraction of real time, so that a simulated circuit on the computer which is, for example, resonating at 300Hz, will serve as a model for a real circuit resonating at 30MHz, with suitable rescaling of L , C , and r .

To initially determine the relative values of L , C , R , voltage V , and current I , without too much paperwork, it is helpful to start with a representative tuned circuit which allows computer operation in real time, at frequencies convenient for display by an a.c. voltmeter or an oscilloscope. 50Hz is a good frequency to employ as a datum because it can be readily obtained from the mains supply; and rounded values of $L = 1\text{H}$ and $C = 10\mu\text{F}$ will also offer resonance at 50Hz.

Taking the circuit of Fig. 5.6a as a starting point, from the knowledge that a series tuned circuit will exhibit an impedance equal to R at resonance, the r.m.s. current flow at 50Hz will be E_i/R , or 20mA when $E_i = 2\text{V}$ r.m.s. and $R = 100$ ohms.

It is necessary to rearrange the basic equation, Equation 5.2, for the computer by dividing through by L , and solving for the second derivative.

$$\frac{d^2Q}{dt^2} = -\frac{R}{L} \frac{dQ}{dt} - \frac{1}{LC} Q + \frac{f(t)}{L} \quad (\text{Eq. 5.5})$$

Substituting known values from Fig. 5.6a,

$$\frac{d^2Q}{dt^2} = \frac{100R}{1\text{H}} \frac{dQ}{dt} - \frac{1}{1\text{H} \times 10^{-6}\text{C}} Q + \frac{f(t)}{1\text{H}} \quad (\text{Eq. 5.6})$$

$f(t)$ in the present case represents a sine wave input of 2V r.m.s. In other circumstances the input function could be a square wave of amplitude E_{in} and period $2t$.

Equation 5.6 is solved on the computer by successive integration. Looking at the symbolised diagram of Fig. 5.6b, it can be seen that there are two closed-loops, one linking the output of OA1 via CP1 to OA1/Input 1, and the other passing through OA1, OA2, and OA3, via CP2, and thence back to OA1/Input 3. The coefficient of CP1 will be multiplied by the gain factor associated with OA1/Input 1. CP2 coefficient is multiplied by the product of gains OA1/Input 3, OA2, and OA3, i.e. $1,000 \times 100 \times 1 = 100,000$.

d^2Q/dt^2 , obtained from the sum of the voltages present at the inputs of OA1, is initially assumed to be present. After one integration OA1 provides an output dQ/dt , and from this all the terms on the right hand side of Equation 5.6 are assembled. So, dQ/dt is multiplied by $R/L = 100$, using CP1 set for a coefficient of 0.1, and is taken back to OA1/Input 1 where it is then added to $f(t)/L = 2\text{V}$ r.m.s.

Nearly 1,700 Circuits and Diagrams plus full repair data for 800 POPULAR MODELS

Great New
Edition

1968 RIGHT BACK TO 1965 Radio & TV Servicing

Big time-saving repair library to
step up your earnings

Now off the Printing Presses—a great new edition of RADIO & TV SERVICING, to save your time, to boost your earning-power. Packed with CIRCUITS, REPAIR DATA and vital information, it covers all the popular 1965-1968 TVs, Radios, Grams, Record Players and Tape Recorders—including latest data on COLOUR TV. Thousands of sets of previous editions sold. Now you can examine this big NEW edition free for a week. 3 handsome volumes—over 1,500 pages written by a team of research engineers—there's no other publication like it. Speeds up repair work for year after year. Hurry—send no money—simply post this coupon below... There can be no reprint once stocks are sold and there's absolutely no obligation to buy under this free trial offer.

**FULL DATA & CIRCUITS
FOR REPAIR OF**

• TELEVISIONS including

COLOUR TV

- RADIOS, RADIOGRAMS
- CAR RADIOS
- RECORD PLAYERS
- TAPE RECORDERS

SERVICING DATA FOR ALL THESE MAKES

Aiwa, Alba, Baird (including colour TV), Beogram, Beolit, Bush, Carousel, Cossor, Dansette, Decca, Defiant, Dynaport, Dynatron, Eddystone, Ekco, Elizabethan, Ever Ready, Ferguson, Ferranti, Fidelity, G.E.C. (including colour TV), Grundig, H.M.V., Kolster-Brandes, Hitachi, Invicta, McMichael, Marconiphone, Masteradio, Motorola, Murphy, National, Newmatic, Pam, Perdio, Peto-Scott, Philips (including colour TV), Portadyne, Pye, Radiomobile, R.G.D., Regentone, Roberts' Radio, Sanyo, Sharp, Smith's Radiomobile, Sobell (including colour TV), S.T.C., Sony, Standard, Stella, Stereosound, Teletron, Thorn, Trans Arena, Ultra, Van Der Molen, World Radio.

PLUS LATEST DEVELOPMENTS IN RADIO AND TELEVISION

Including—Integrated Tuners, Stereo Multiplex Broadcasting—The Zenith-G.E. System. Receiver, Decoder and adjustments, Aerial, etc. Colour TV Receivers, Colour TV Test Card F, Servicing Transistor Equipment, Chemical Aids to Servicing, Batteries and Rechargeable Cells, Sound-on-Sync., Double Line Sync., Silicon Transistors, etc.

OVER 1,500 PAGES, PACKED WITH CIRCUITS, COMPONENT LAYOUT DIAGRAMS, PRINTED PANEL DIAGRAMS, TABLES AND WAVEFORM GRAPHS.

Handsomely bound in rich maroon and gold.

SENT TO YOUR HOME
POST-PAID ON 7 DAYS

FREE TRIAL

Absolutely no obligation to buy

To: Buckingham Press Ltd., 18/19 Warren Street, London, W.1
Please send Radio and TV Servicing, 3 volumes, without obligation to buy if you accept my application. I will return the books in 8 days or post:

Tick (✓) Full cash price of £12, or here 15/- dep. and 16 monthly payments of 15/-
If you are under 21 your father must fill up coupon.

Full Name.....
(Block letters)

Address.....

County.....



Occupation.....

Signature.....


Credit price £12.15s. For Eire & N.I. send £12 with coupon. Elsewhere overseas add 10/- P. & P.

Please tick (✓) here
The address on left is
My/your property
Rented
unfurnished
Furnished/accam
Company address
*If none of the above
please answer here*


RV3/3626

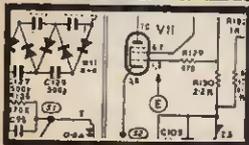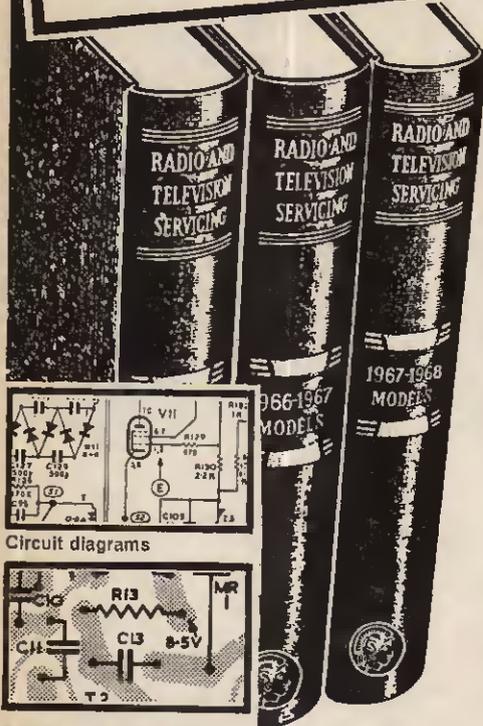


Circuit diagrams

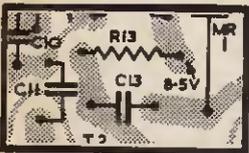


Printed panel diagrams

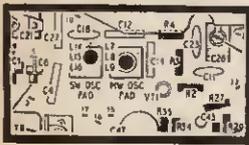

Component layout diagrams

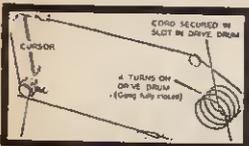

Drive-cord diagrams

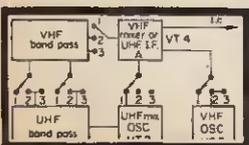

Block diagrams

Your guide to good motoring on holiday and at home



PREPARING FOR HOLIDAYS ON WHEELS

Planning and budgeting for home and continental holidays—caravanning, camping, motor caravanning—maps and routes to the sea and sun—comfort for drivers and passengers—safety devices—what to take in spares—tools, first aid-kits, etc.

HOLIDAYS EN ROUTE

How to use maps—recipes for alfresco meals—tips on continental driving—motoring in hot weather—motor sport.

CAR ANALYSIS AND MAINTENANCE

Engine—Ignition—Carburation—Cooling—Transmission—Tyres—Brakes—Suspension.

BIG DEMAND! MAKE SURE OF YOUR COPY 3/6

124 pages



TRANSISTORIZED POWER SUPPLY TYPE R32



Output Voltage:
0 to +15V
0 to -15V
Continuously variable

Current:
Up to 1A except at the max. voltage when automatic overload protection limits current to 0.6A

Regulation:
Full load to no load better than 0.1%

Ripple:
Max. volts/foot condition ripple 3mV p/p

Better than 1mV p/p, at most setting of voltage.
Output Voltage Variation:
Better than 2% for 10% mains variation

Dimensions:
5in x 5in x 8in deep
Voltage and current indicated on separate meters

PRICE: £17.5.0. P. & P. 12/6 (U.K. only)

TRANSISTORIZED A.F. SIGNAL GENERATOR TYPE R21



Frequency:
15Hz to 20kHz in three ranges

Constant Amplitude over the whole frequency range

Frequency Reading:
Direct off the scale

Frequency Accuracy:
3% over the band typical 3%

Output Voltage:
0 to 1V R.M.S. continuously variable

Harmonics:
Better than 1%

Battery Life:
Over 500 hours

Dimensions: 6in x 4in x 3in
PRICE: £10.15.0 (including battery, P. & P. 7/6 (U.K. only))

Comprehensive range of 1, 1/2, 1 watt carbon film resistors; sealed miniature carbon potentiometers; silicon rectifiers.

Please send for the technical literature for the above components enclosing 1/- in postage stamps to:

O. & R. ELECTRONICS LTD.
13 STEPHENSON HOUSE, FLEET RD.
LONDON, N.W.3

Mail Order only, Cash or P.O. with order
Minimum order for components 10/-

WENTWORTH RADIO

104 SALISBURY ROAD, HIGH BARNET

BAR 3057

ACY18	4/6	BC109	5/-	NKT217	7/9	NKT612	4/11	OC45	1/8	OC170	2/8
ACY19	4/6	BCY31	10/9	NKT261	3/6	NKT675	4/8	OC79	5/-	OC171	6/8
ACY20	4/8	BFY59	7/-	NKT271	3/6	NKT676	4/2	OC71	1/8	OC172	4/6
ACY21	5/-	BSY36A	8/-	NKT273	3/6	NKT713	4/3	OC72	1/10	2N4871	3/3
ACY22	3/8									2N404	6/-
ACY23	5/9									2N698	4/6
ACY32	5/9									2N706A	4/6
ACY40	3/10									2N1302	3/9
AD140	8/8									2N1304	4/6
AF114	4/3									2N1305	4/6
AF115	4/3									2N1307	7/-
AF116	2/3	MAT100	7/9	NKT274	3/6	NKT773	4/-	OC74	3/9	2N1368	9/-
AF117	2/8	MAT101	8/6	NKT304	11/-	OC35	8/6	OC75	3/9	2N501	9/6
AF118	4/6	NKT1	4/11	NKT493	15/-	OC36	8/6	OC77	3/6	2N512	4/6
BC108	4/9	NKT214	3/6	NKT451	12/-	OC44	1/11	OC81	1/9	2N746A	3/6
								OC8D	2/3	2N8010	6/7

LOWEST PRICES EVER

CASH WITH ORDER

P. & P. 9d.



TRANSISTOR BOOSTER
39/6

JUST PLACE NEAR RADIO —

- The Dewtron Wave Trap for portables
- ★ Boosts Radio 1, Luxembourg, Pops etc.
 - ★ Eliminates 'fading'
 - ★ Extends battery life.
 - ★ Replaces car aerial for portable sets.
 - ★ 7-day refund trial. £2 post free.

D.E.W. LTD., P.E., RINGWOOD ROAD, FERNDOWN, DORSET.



ADD NEW DIMENSIONS TO YOUR LISTENING —

- The revolutionary N.D. Effects Amplifier adds fabulous "Big Hall Stereo" effect to any transistor radio, tape or player. Adjustable echo, vibrato and tone. Requires only speaker and PP3 battery 8 gas. + 4/- P. & P. Tubular speaker 25/- extra.

Moving in the other direction on the symbolised diagram of Fig. 5.6b, dQ/dt is integrated by OA2 to obtain $+Q$. Inverting amplifier OA3 changes the sign of Q before passing it on for multiplication by $1/LC = 100,000$ (CP2 coefficient of 1). $-(1/LC)Q$ is then added, at OA1/Input 3, to

$$-\frac{R}{L} \frac{dQ}{dt} + \frac{f(t)}{L}$$

and the sum of all OA1 input voltages yields the required d^2Q/dt^2 . Because there are two closed-loops in the computer set-up the equation will be self-enforcing.

Routine. Switch on UNIT "A" power supply and allow a warm-up time of at least 15 minutes. Ensure that the three operational amplifiers are disconnected from their summer networks, and have no feedback components. Apply 10V d.c. voltmeter leads to OA1/SK13 and an earth socket, and zero-set OA1 for

an output voltage of less than $\pm 1V$ from the back of the UNIT "A" box, by means of VR1 (Fig. 3.7). Repeat for OA2 and OA3.

Set up the problem according to the patching circuit of Fig. 5.6b, but omit the feedback capacitors and the patching link between OA3/SK13 and CP2/SK1. Set CPI dial to approximately "1". Connect the voltmeter to miniature socket OA1/SK6 (Fig. 2.9) and zero-set OA1 again, but this time using the front panel control VR15.

Next, zero-set OA2 using VR16, and OA3 using VR17. Insert $0.1\mu F$ computing capacitors into OA1/SK11 and SK12, and OA2/SK11 and SK12, and make good the link between OA3 output and CP2. Set CP2 for a dial reading of "10". Apply the voltmeter to OA2/SK7 and zero-set the complete assembly of amplifiers by adjustment of VR15(OA1) only.

The problem layout will now be ready for dynamic checks and should not need to be re-zeroed for several hours if UNIT "A" is being operated in stable ambient temperature conditions.


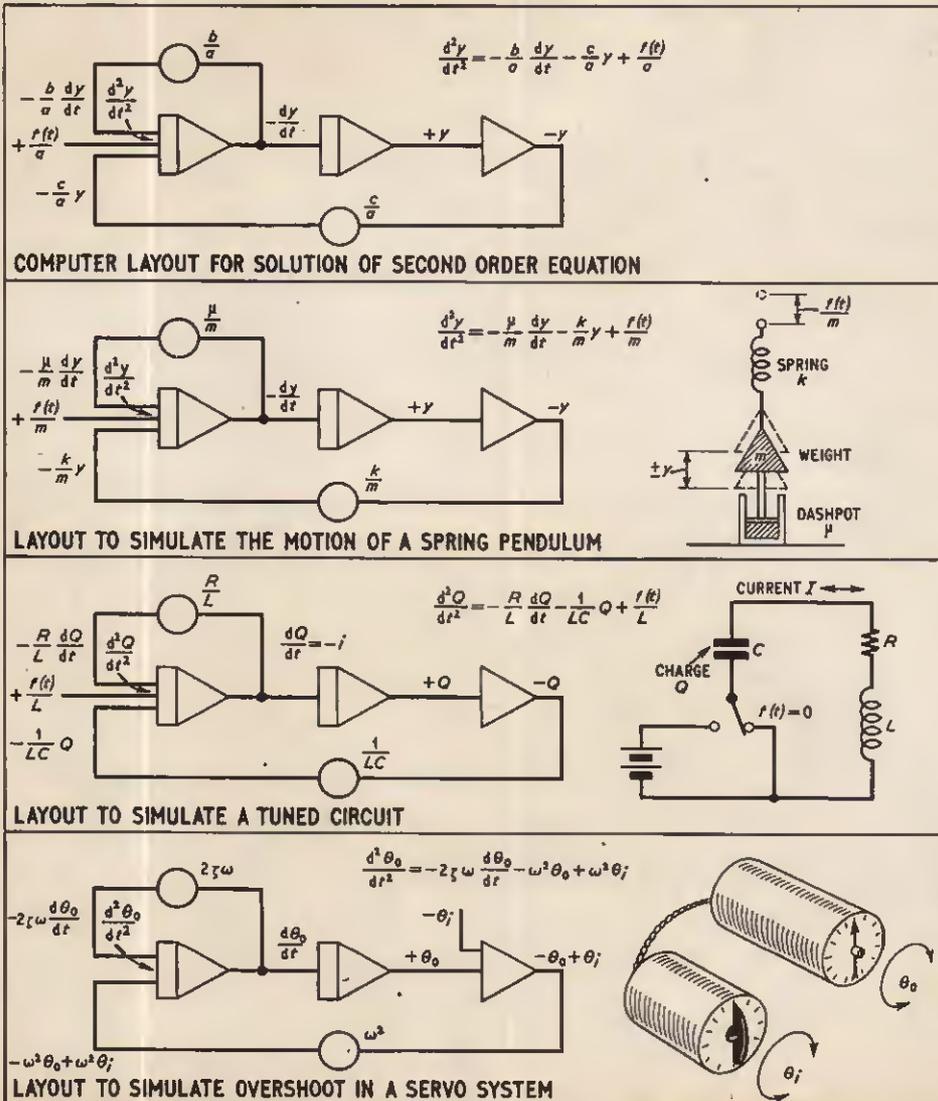


Fig. 5.5. A second order differential equation applied to physical systems

TABLE 5.2

SHOWING HOW COMPUTER OPERATING FREQUENCIES ARE RELATED TO CP2 SETTING AND AMPLIFIER CLOSED-LOOP GAINS

Resonant Frequency f	Typical Values L	C	CP2 Coefficient	$\frac{1}{LC}$	OA1 Input 3	OA2	OA3
0.05Hz to 0.5Hz	1,000H	10,000 μ F	0.1	0.1	10	10	0.1
	100H	1,000 μ F	1.0	10	10	10	0.1
5Hz to 50Hz	10H	100 μ F	0.01	10 ³	1,000	100	1.0
	1H	10 μ F	1.0	10 ⁵	1,000	100	1.0
500Hz	100mH	1 μ F	1.0	10 ⁷	1,000	1,000	10
1kHz	100mH	0.2 μ F	1.0	5 \times 10 ⁷	1,000	1,000	50

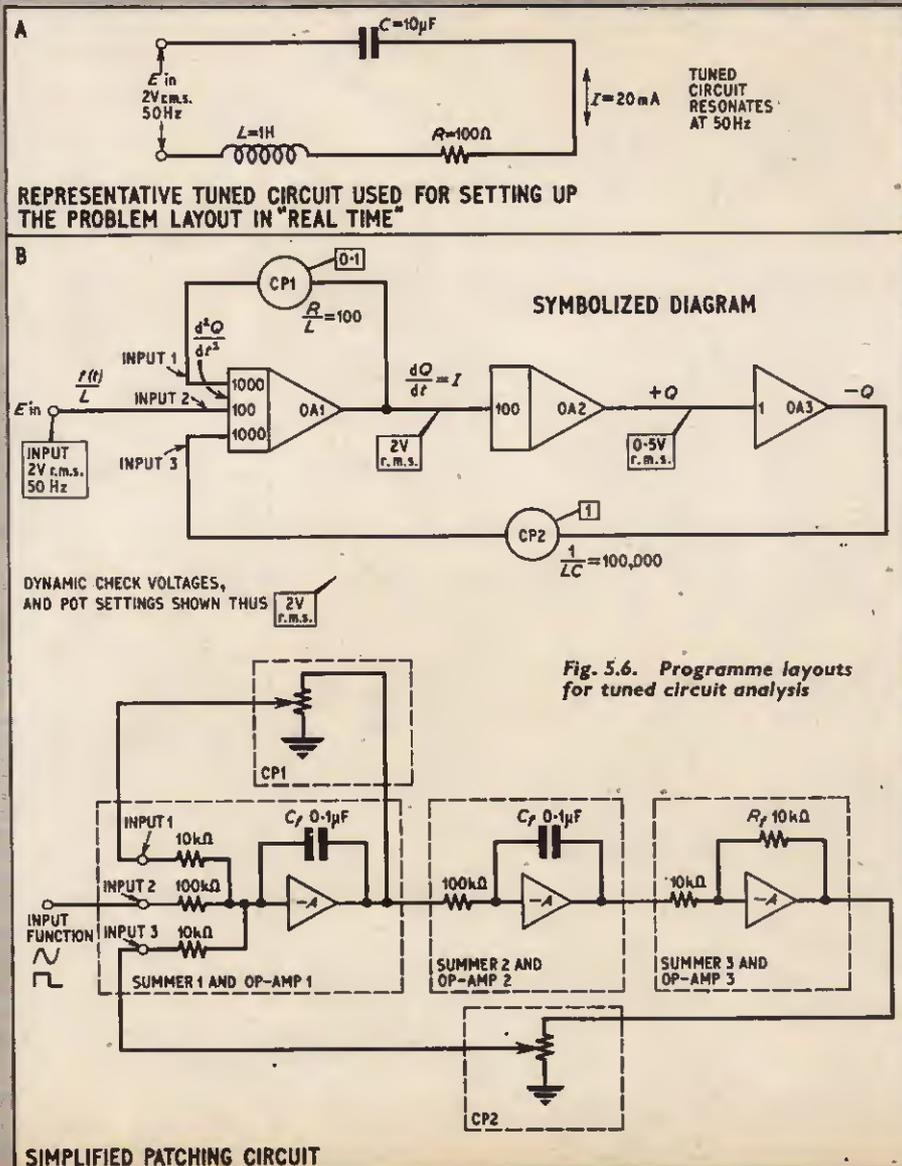

MINIATURE WAFER SWITCHES

4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/8 each, 36/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

SPECIAL BARGAINS

50 ohm 50 watt Wire Wound Pot-meters, 8/6 each. 1 Meg Miniature, Pot-meter Morganite standard, 1/2 spindle 1/- each; 9/- dozen.
1 Meg Miniature, Pot-meter Morganite preset screwdriver control, 6d each; 8/- per dozen.
Pro-Set 100K by Welwyn with intricate bakelite knob, 1/- each; 9/- per dozen.
100K Pot-Meter, Miniature type with double pole switch and standard 1/2 spindle, by Morganite, 2/- each; 18/- per dozen.
Blankets, 1/2. Enclosed, normally closed circuit, will open should blanket overheat, 4/6 each.
Thermal Relay, Can be used to delay the supply of HT while heaters warm up, or will enable 15A loads to be controlled by miniature switches or relays. Regular list price over £2, price 7/6 each.
Siemens High Speed Relay, Twin 1,000 ohm coils. Platinum points changeover contacts—Ex equipment 8/6 each.
Toggle Switch Bargain, 10A 250V normal one hole fitting 2/8 each; or 30/- per doz.
Electric Lock, 24V coil, but rewirable to other voltages, 4/6 each.
Compression Trimmers, Twin 100pF, 1/- each; 9/- per dozen.
Precision Wheatstone Bridge, Opportunity to buy cheaply. 100K wire wound pot. 15W rating, only 5/-.
Sheet Paraffin, Ideal for transistor projects. 12 panels each 6in x 8in, 5/-.
8in FM Loudspeaker, 3 ohm, 12/6; 80 ohm, 13/6.
Transistor Ferrite Slab Aerial with medium and long wave coils, 12/6.
Slide Switch, Sub miniature double pole change-over, 2/- each; 18/- per dozen.
Vacuum Cleaner Flex, Non-kinkable ribbed rubber, most pliable but very tough. 24/36 Cores. Normally, 1/8 per yard, offered at 23 per 100 yard coil, post and insurance 8/6.
Sub-Miniature Silicon Diodes, General purpose type with gold-plated leads, 1/- each or 7/6 per dozen.
Massage Tapes, 225ft Tape on 3in spools, normally 4/8 each, we offer 4 tapes for 12/6.
White Circular Flex, Ideal for lighting drops, twin made by BICC. Usually 8d yd, 100 yd coil for 30/-, plus 6/- postage.
Edgewise Control, Morganite, as fitted many transistor radios, 2K or 5K with switch, 2/6 each or 24/- per dozen.
15V Inverter, Full transistorised for operating a 20-watt fluorescent tube, size 8in long x 1 1/2 x 1 1/2. £3.19.0. Post and insurance 3/-.
Silicon Rectifier, Equiv. BY100 750mA 400V, 10/- each.
Miniature Pick-up for 7in records made by Comco-code, crystal cartridge with sapphire stylus only 8/8 or 36/- dozen.
Telescope Aerial for radio or transmitter, chrome plated, 6 section extends from 7 1/2in to 47in, 7/6 each, 64 per dozen.
Midget Meters for mains indicators, etc., 1/3 each or 12/- dozen.
Midget Relay twin 250 ohm coils, size approx. 1 1/2in x 1 1/2in x 1 1/2in. 4 pairs changeover contacts 7/6 each.
P.O. Type Relay, Twin 200 ohm coils, size approx. 3in x 2 1/2in x 1 1/2in. 4 pairs changeover contacts, 3/8 each.
Printed Circuit Board, Edge Connector, solder terminations, 32 contacts, standard spacing for wireboard, etc. 6in long but easily cut. 7/6 each, 80/- doz.
1,000W Fire Spiral, replacement for most fires. 1/3 each, 12/- doz.

FPS Eliminator. Play your pocket radio from the mains! Save 2s. Complete compact kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and inductors. Only 8/6 plus 1/- post.

PHOTO-ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit, laminated boards and chemicals, Latching relay, infra-red sensitive Photocell and Hood, 2 Transistors, cond., Terminal Block, Plastic case. Essential data, circuits and P.C.C. chassis plans of 10 photo-electric device including auto. car parking light, modulated light alarm, simple invisible ray switch—counter—stray light alarm—wobbling tone electronic alarm—projector lamp stabiliser, etc., etc. Only 39/6, plus 2/- post and insurance.

Be first this year SEED AND PLANT RAISING

Soil heating wire and transformer. Suitable for standard size garden frame. —18/6, plus 3/8 post and ins.

CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by fingertip control. Kit includes all parts, case, everything and full instructions 13/6, plus 2/8 post and insurance. Or available made up 22/6, plus 2/8 post and insurance.




SUPERTONE G.C.V.

Saves you work—It's partly built


Like its predecessors this latest Companion has full 10 performance—such as only a good wooden cabinet and bifur speaker can give, and due to its being partly built you will have it going in an evening. Note these features:

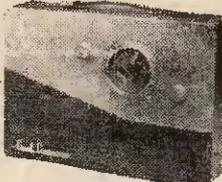- 7 Transistors, superhet circuit.
- Two-tone Cabinet, size 11 x 8 x 3in.
- All circuit requirements—Push-pull output—A.V.C. and feed back, etc.
- Printed circuit board all wired only connections, e.g., to Volume control W.C. Switch and Tuning Condenser.
- Pre-aligned 12 stages complete with full instructions. Price only 24.9.6 plus 6/8 post and insurance.




RADIO STETHOSCOPE

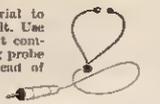Easiest way to track and—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, T.V., amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal carpiece 29/6—twin steelet instead of carpiece 2/8 extra post and ins. 2/9.




THIS MONTH'S SNIP MICRO-SONIC

7 transistor Key chain Radio in very pretty case, size 2 1/2in x 2 1/2in x 1 1/2in—complete with soft leather zippered bag. Specification: Circuit—7 transistor superheterodyne; Frequency range—630 to 1,600Kc/s; Sensitivity—5mV/m; Intermediate frequency—456Kc/s, or 455Kc/s; Power output—40mW; Antenna—ferrite rod; Loudspeaker—Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleaned away they should work perfectly—offered without guarantee except that they are new, 19/6 plus 2/8 post and insurance, less batteries.

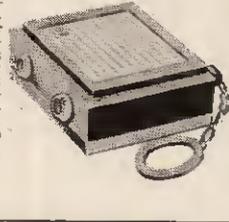

BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2 1/2in deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4 1/2 volts. Supplied complete with 2 spools ready to install. Record, Replay head is the sensitive M4 type intended for use with transistor, amplifier. Price 24/15/-. Post and insurance 4/8.

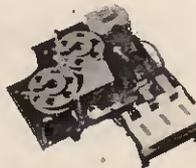

RECORD PLAYER SNIP

The "Princess" 4 speed automatic record changer and player engineered with the utmost precision for beauty, long life and trouble free service. Will take up to ten records which may be mixed—7in, 10in or 12in. Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess—a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only 25.19.6, complete with cartridge and ready to play. Post and insurance 7/6 extra.



CASSETTE LOADED DICTATING MACHINE

Battery operated and with all accessories. Really fantastic offer, a British made £31 outfit for only 28/19/6, brilliantly designed for speed and efficiency—cassette takes normal spools, drops in and out for easy loading—of normal functions—accessories include stethoscopic ear-piece—crystal microphone has on/off switch—telephone pick-up—tape reference pad—DON'T MISS THIS UNREPEATABLE OFFER SEND TO-DAY. 28/19/6, plus 7/8 post and insurance. Footswitch 18/6 extra. Spare Cassettes at 7/6 each, three for 21.



SENSITIVE HAND MICROPHONE

Dynamic type. Low impedance, moving ion, fitted in unusually neat plastic head with anti-microphonic coupling to handle. Extra small size but very sensitive. 15/- each.
B7G Valve Holder with bottom screen-p.t.f.e. insulation finest for HF and VHF, 1/- each; 10/- doz.
Fractional H.P. Motor, 240V 50c/—open construction ideal for ventilation fan—blower heater, etc.

Clock Motor, 230V 50c/s synchronous—self starting, 6/6.

Pentode Output Transformer—standard size, 40-1, ex equipment but O.K., 4/8 each; 48/- doz., post paid.

Neon Mains Tester, 1/8 each; 12/- doz.

MAINS TRANSFORMER, Upright mounting with primary tapped 200, 220, 240V H.T. Secondary is 250-0-250V at 100mA and it has two L.T. secondaries of 8-3V 1A—unused (removed from equipment), 15/- plus 3/8 post and insurance.

FLUORESCENT CONTROL KITS


Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-internal, mostly resin filled. Kit A.—15-20W, 19/6. Kit B.—30-60W, 17/6. Kit C.—80W, 17/6. Kit D.—125W, 22/-, Kit E.—65W, 19/6. Kit MF1 is for 6in., 9in., and 12in. miniature tubes 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/8 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/8 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12V for up to 500mA (class B working). Takes the place of any of the following batteries: P1, P3, P4, P5, P6, P7, P8, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 18/6, plus 3/8 postage.

MAINS MOTOR

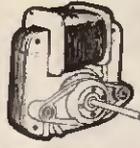Precision made—as used in record decks and tape recorders—ideal also for extractor fan blower heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post and ins. free.



RELAY SWITCHES. These enable micro switches, delicate thermostats or other low current devices to control up to 30A. Ideal to switch thermal storage heaters—motors, etc., made by the famous A.E.I. group these are listed at 225 each— you can buy if you hurry at a very keen price of 39/6 each and we will include diagrams and data. Mounted on panel size approx. 6 x 7 x 2 1/2in deep.

THERMOSTATS

Type "A" 16A for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob. Quickly adjustable from 30—300F, 9/6 plus 1/- post. Suitable box for wall mounting 5/- P. & P. 1/-.
Type "B" 16A. This is a 17in long rod type made by the famous Sunvic Co. Spindle adjusts this from 100—350F. Locking screw alters the setting, so this could be adjustable over 30° to 1,000F. Suitable



for controlling furnace, oven kiln, immersion heater or to make flame-start or fire alarm, 8/6 plus 2/8 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses, one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (18 yds, 10/-) is wound round the pipes. 7/8. P. & P. 1/2.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperatures. 7/6 plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, tanks or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50°F to 150°F. Price 18/- plus 2/- post and insurance.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/8. Semiconductor add 1/- post. Over £1 post free. S.A.E. with enquiries please.

ELECTRONICS (CROYDON) LIMITED

(Dept. P.E.) 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)

also at 266 LONDON ROAD, CROYDON, SURREY S.A.E. with enquiries please

**TWO-YEAR GUARANTEE
EX-RENTAL TELEVISIONS**

FREE ILLUSTRATED
LIST OF TELEVISIONS
17"-19"-21"-23"



WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

£19

STEREOGRAM CABINET

An elegant Stereogram Cabinet
in modern Veneered Mahogany
and cloth covered Front Panel
BLACK LEATHERETTE SIDE PANELS
Dimensions: 52" x 17 1/2" x 12"
Speaker positions for Twin
10" x 5" Speakers



OTHER MODELS—SEND FOR LIST

17in.—£11.10.0

3 Star Guarantee
★ Tube ★ Valves
★ Components Carr. 30/-

**TRANSISTOR CHASSIS
59/6**

6 Transistors, LW/MW, Tele-
scopic Aerial, Brand New,
Famous British Manufacturer,
(LESS SPEAKERS) P. & P. 4/6.
**SINGLE PLAYER
CABINETS 19/6.** P. & P. 7/6.
TRANSISTOR CASES 19/6.
Cloth covered, many colours.
Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 3/6.
Similar cases in plastic 7/6.

**RADIOGRAM CABINETS
ONLY £5.19.6**



An attractive discreetly
designed space saving
cabinet in natural grained
polyestered sapele. Press-
drop flap for autochanger
and record storage com-
partment. 10" x 5" speaker
position. Complete with
legs. Dim. 29 1/2" H x 14 1/2" D
x 29" W. Carr. Ins. 25/-.

DUKE & CO. (LONDON) LTD.
621/3 Romford Road, Manor Park, E.12
Phone 01-478 6001-2-3 Stamp for Free List.

**TWO SCOOPS FROM "KING'S"
CONTINUOUS LOOP**

(NEVER ENDING - NO REWINDING)

**TAPE CASSETTE
BULK PURCHASE
RIDICULOUS PRICE**

IDEAL BACKGROUND MUSIC - LANGUAGE
COURSES, ETC. 200ft. HIGH QUALITY AMPEX
TAPE. WILL FIT ALL TAPE RECORDERS.
CANNOT BE REPEATED

NEARLY ALL GONE
HURRY! NOW ONLY **18/-** EACH
P&P 6d.

FULL CIRCUIT - INSTRUCTIONS - PARTS
LIST TO BUILD YOUR OWN
TELEPHONE ANSWERING/RECORD
MACHINE - QUICK - AUTOMATIC
TAKES 100's OF CALLS: **25/-**
CHEAP TO BUILD. SEND NOW

7" AMPEX TAPE SPOOLS, ONLY 2/6
P. & P. 6d.

KING'S TELE-SERVICE CO.
105/107 DAWES ROAD, FULHAM, S.W.6
FULHAM 1668-2998

YOURS FREE FOR 7 DAYS

A PROGRAMMED COURSE OF INSTRUCTION
**BASIC ELECTRICITY (5 vols.)
ELECTRONICS (6 vols.)**



You'll find it easy to learn with this out-
standingly successful NEW PICTORIAL
METHOD—the essential facts are explained
in the simplest language, one at a time, and
each is illustrated by an accurate, cartoon-
type drawing. The books are based on
the latest research into simplified learning

techniques. This has proved that the
PICTORIAL APPROACH to learning is
the quickest and soundest way of gaining
mastery over these subjects. Each Volume
has a unique PROGRAMMED supplement
for you to test and check your knowledge.

The series will be of
exceptional value in
training mechanics and
technicians in Electricity,
Radio and Electronics.

WHAT READERS SAY

- "After reading section on Filter Circuits once, I under-
stood more about them than in a whole year from the
obscurities of other manuals." L. G., West Wickham.
- "I must say they are the best books on the subject as they
explain in simple language what other books make hard
going of." C. B., Hartlepool.
- "They have a wonderful system of imparting the subject
to the beginner." H. C. L., Leicester.
- "What a contrast to the many text books I have attempted
to struggle through." J. G., Rugby.

A TECH-PRESS PUBLICATION.

To The SELRAY BOOK CO., 60 Hayes Hill, Hayes, Bromley, Kent.

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets
on 7 DAYS FREE TRIAL, I will either return set, carriage paid in good condition
within 7 days or send BASIC ELECTRICITY including Programmed Supplement Cash
Price 95/-. BASIC ELECTRONICS including Programmed Supplement Cash Price
122/-. All prices include P. & P.

Deferred Terms readily available. This offer applies to UNITED KINGDOM ONLY.
Overseas customers Cash with order.

Tick Set required (Only one set allowed on free trial.)
BASIC ELECTRICITY Programmed Supplement BASIC ELECTRONICS Programmed Supplement

Signature..... (If under 21 signature required of parent)

NAME.....
BLOCK LETTERS
FULL POSTAL ADDRESS.....

POST NOW FOR THIS OFFER!

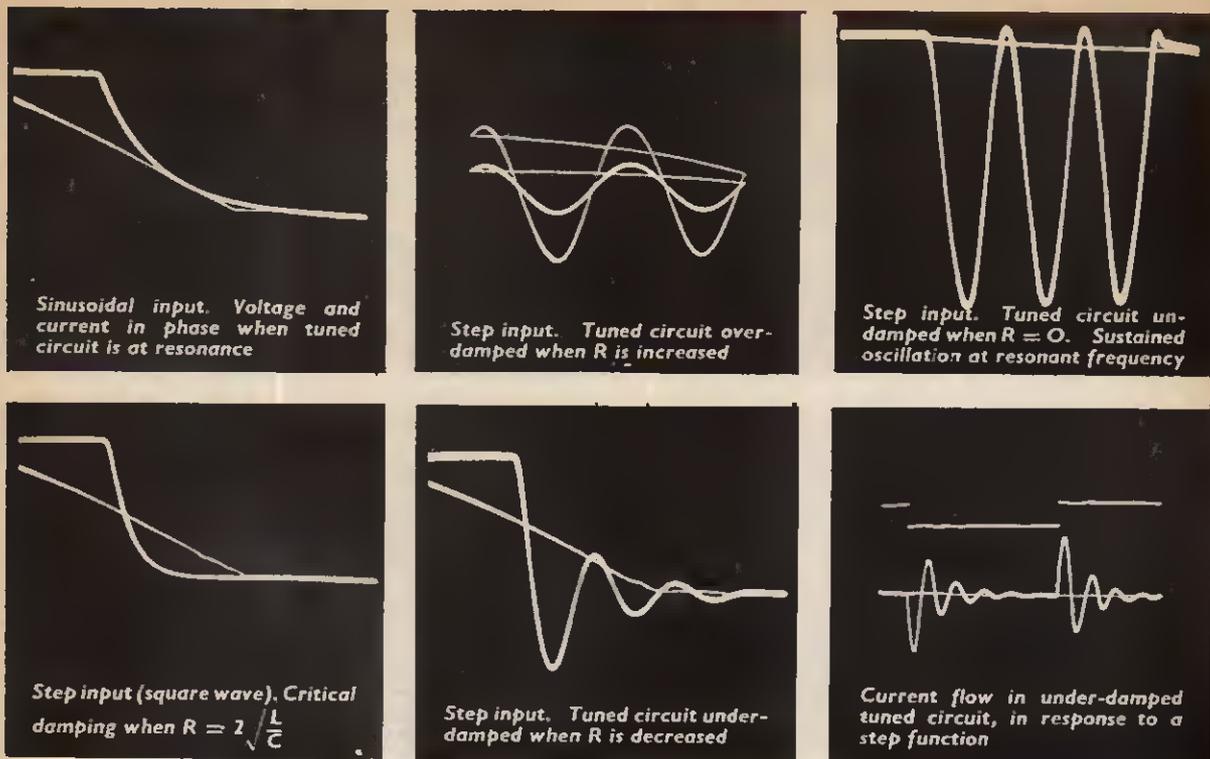


Fig. 5.7. Response of a simulated tuned circuit

Apply a 2V r.m.s. 50Hz signal to OA1/Input 2, and monitor by means of a reliable 10V a.c. meter of not less than 1 kilohm/volt sensitivity. The input function should preferably come from a low impedance source to avoid serious loading errors when the voltmeter is removed. Next, connect the a.c. voltmeter to the output of OA1 and adjust CP1 so that OA1 input and output voltages are exactly equal. CP1 could alternatively be set by the reference voltage and d.c. voltmeter method mentioned earlier, for a coefficient of 0.1. If the CP2 setting is altered it will be discovered that the simulated circuit goes off resonance, and can be tuned by CP2 between approximately 5Hz and 50Hz.

UNIT "A" will now be ready for analysis of the Fig. 5.6a tuned circuit, and will also cover a useful range of other values for L , C , and R in real time.

When handling sinusoidal or step functions, an amplifier will still have a maximum output voltage swing of $\pm 10V$, but this will be the peak voltage value. To check for overloading with an a.c. meter, ensure that amplifier output voltages do not exceed 7.07V r.m.s. for a sine wave function, and 5V mean for an equal mark-space square wave.

RESCALING PROBLEM EXAMPLE 3.

To rescale the problem for larger or smaller values of L and C , beyond the coverage of CP2, and by abandoning real time operation, note that a tenfold increase in tuned circuit frequency corresponds to a hundredfold increase in $1/LC$. For most applications, where the series resistance R will lie between zero and just beyond critical damping ($R > 2\sqrt{L/C}$), the scaling of R/L can stay as it is for all reasonable values of L and C , but should anyway only be changed by adjustment of the gain factor at OA1/Input 1. Similarly, the $f(t)/L$ gain of 100 at OA1/Input 2 can remain fixed.

It is not necessary to use inconveniently large or small input functions when rescaling for new voltages and currents. 2V r.m.s. could equally well represent an input function of, say, 0.2V r.m.s., and from Ohm's Law the current I will automatically become 2mA, instead of the former 20mA, even though it is still represented by 2 computer volts.

If it is desired to extend the computer operating time, by adjustment of integrator and inverting amplifier closed-loop gains, refer to Table 5.2, while remembering that integrator closed-loop gains are calculated on the basis of $1/R_{in}C_I$ where R is in ohms and C is in farads.

For reasons of reduced accuracy, it is not advisable to use computer operating frequencies above 1kHz or below 0.05Hz in connection with Problem Example 3. It should be mentioned that although frequencies in the region of 0.05Hz are too low for display on an a.c. coupled oscilloscope, the behaviour of a system can be demonstrated in slow motion by the oscillating movement of a d.c. voltmeter pointer (centre-zero).

Some typical oscillograms are given in Fig. 5.7 to show the response of a simulated tuned circuit. If the computer oscilloscope is provided with a good graticule, and has a linear response, amplitude and time measurements which are accurate to within approximately 5 per cent may be obtained straight from the trace.

The behaviour of a real tuned circuit can be evaluated by comparison with a simulated circuit. A tracing is made of the real circuit oscilloscope display, and is then superimposed on the readout given by the simulated circuit. The computer is adjusted so that time scales are related by a known factor, and tracing and readout display are identical, then quantitative measurements are taken from the computer voltages and dial settings. **Next month: The construction and operation of UNIT "B"**

DENTOPHONICS

BY F.R. BERTRAND, B.D.S.

THE term Dentophonics has been applied to the technique of broadcasting speech from the mouth by the use of electronics.

Dentophonics works on the same principle as a throat microphone, where a transducer picks up the sonic energy transmitted through the tissues as a person speaks. This is quite distinct to normal microphone techniques which rely upon air pressure waves.

Dentophonics (DP) is easily demonstrated by the following experiment. Plug a sonic probe into the input socket of an audio amplifier. Press the sonic probe against a subject's tooth as that subject is speaking, and the voice of the subject will be clearly heard through the loudspeaker.

TISSUE TRANSMISSION

A sonic probe with a broad surface will pick up sound from various parts of the head, including the forehead, temple, cheekbone, and the cheeks themselves. To obtain good speech reproduction from the cheeks, the sonic probe has only to be gently pressed against a cheek. This shows quite clearly that sound is transmitted through both hard and soft tissues of the body, and it would therefore be better to drop the term "bone conduction" and use the term "tissue transmission".

The extent of the tissue transmission of sound is shown by the following experiment.

A sonic probe was held firmly in a subject's extended right hand. This sonic probe was connected to the output of an audio amplifier, and a signal generator was connected to the input socket of the same amplifier. The same subject held another sonic probe in his extended left hand and this second sonic probe was connected to the input of another amplifier, a loudspeaker being connected to the amplifier output. The subject holding the probes was in one room, and the loudspeaker was in another room. When a signal of 1,000Hz was transmitted through the sonic probe in the subject's right hand, this signal was picked up by the sonic probe in the subject's left hand, and was clearly heard by an observer in the room with the loudspeaker.

BUILT-IN ELECTRONICS

Whilst speech may be picked up by a transducer from various sites of the head, the mouth offers the most interesting possibilities, in that there would appear to be no reason why miniaturised electronic equipment should not be built-in, at this present time. Already in various experiments to obtain information on the occlusion of the teeth, up to six radio transmitters have been "built into" the mouth.

Any miniaturised electronic equipment designed for placing in the mouth could be incorporated into bridges or dentures. The miniaturised equipment could be designed to be removable, and capable of being switched on or off.

A dentophonic appliance will have the advantages over a throat microphone, of being less bulky, and also of giving better and clearer speech reproduction. A DP probe will pick up speech from an artificial tooth provided the artificial tooth is firmly fitted.

The great advantage of dentophonics is the elimination of background noise. Transducers used for DP are designed to pick up the transmission of sound in solids, and should not pick up airborne sound. This means that the speech of a subject in a high level of background noise could be heard quite clearly without any interference by the background noise.

Another advantage of DP is that there will be no need for the so called "microphone technique" that the public speaker or performer has to learn.

One objection to DP is that the noise of the teeth occluding will be picked up; but this objection would only be valid where a subject has nervous clenching habits, as normally the teeth mainly occlude during mastication, the position of rest being with the teeth slightly apart.

POSSIBLE APPLICATIONS

The applications of DP will be many and varied, but this technique could certainly be used by the following persons: outside television and radio commentators, motor racing drivers, aviators and astronauts, public speakers, theatrical performers, and deep sea divers.

Where background noise is such that a subject's hearing may be damaged, the ears could be protected by muffling, and communication established by using the DP technique.

DP could be used for teaching deaf children to speak. The DP probe would pick up the sound of the deaf child's own voice, and even if the child had no hearing whatsoever, the child would be able to compare the movement his or her voice produced with the movement that the teacher's voice produced.

THROUGH SOLID MASS

Another interesting experiment can be described.

Two audio amplifiers were used, one had a microphone and a probe connected to it; the other had a DP probe and a loudspeaker connected to it. A subject spoke into the microphone, and as he was speaking the probe was pressed against the wooden casing of the first amplifier, and the second probe was pressed against the other end of the wooden casing of the same amplifier. The subject's voice was clearly heard over the loudspeaker. Thus, audio sound had been transmitted through a solid and picked up at the other end.

Perhaps this technique could be applied as a means of communicating with people who become entrapped in certain tragedies such as occur in mines or at sea.

Finally, it is apparent that dentophonics in conjunction with the audiodental technique opens up a new, relatively untried, but highly promising field of communications.

For Future Reference

- An index for volume three (January 1967 to December 1967) is now available price 1s 6d inclusive of postage.
- Easi-binders are available price 14s 6d inclusive of postage. State whether "Vol. 1", "Vol. 2", "Vol. 3" or "Vol. 4" is required.

Orders for Binders and Indexes should be addressed to the Binding Department.

Orders for copies of the Index only should be addressed to the Post Sales Department, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.



FLUORESCENT CAMPING LIGHT

By R. B. HAYLE

MODIFICATION FOR PRE-HEATING THE LAMP ELECTRODES

WE HAVE been advised by a well known lamp manufacturer that the 6W 9in lamp employed in the Fluorescent Camping Light (March 1968) is designed to be used only in circuits which arrange to pre-heat the lamp electrodes either before, or simultaneously with, the application of a pulse or steady state voltage across the lamp in order to start it.

It is explained that the practice of cold starting, as in our published design, can result in very heavy lamp end blackening, and a very short lamp life.

We are therefore publishing an alternative circuit by R. B. Hayle which incorporates a pre-heat facility.

In the modified circuit Fig. 1 the "low" output switch position is omitted, and a three-pole switch is used in place of the two-pole switch specified in the original circuit. This enables the electrodes to be energised via R4, which should be selected so that, with a 12V supply battery, the pre-heating current is not less than 160mA.

Under these conditions, switch S1 should be held in position 2 (pre-heat) for at least one second before going over to position 3. Capacitor C2 is permanently connected to C1, R1, R2, and T1. The switch is now used entirely for preheating and running. The amount of rewiring involved is not great, and readers will be able to convert their Camping Lights with little difficulty.

A modified wiring diagram of S1 is shown here in Fig. 2. Similarly modified versions of the main unit wiring are shown in Fig. 3.

The pot-core assembly LA5 can be obtained from retail outlets of Mullard components including Henry's Radio Ltd. whose address is on the back cover.

The author does not advise the circuit to be converted for a 6 volt battery supply. The saturation voltage across the transistor becomes a significant factor and leads to reduced efficiency. A 6V version would have lead to undesirable circuit complications.

Fig. 3. Top and underside views of the electronics including the modified wiring details

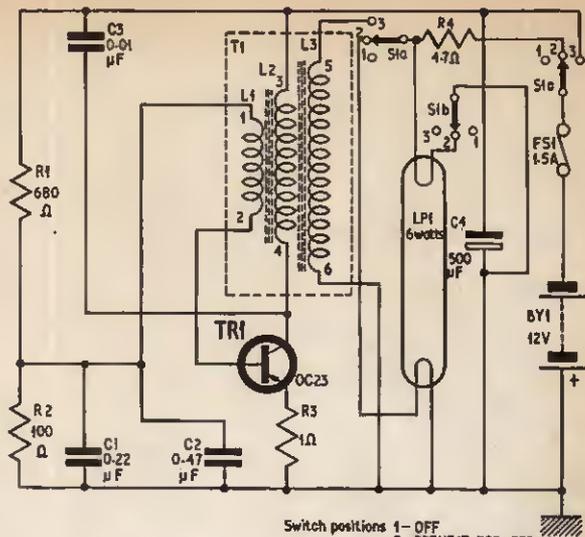


Fig. 1. Modified circuit diagram. An extra resistor R4 is needed


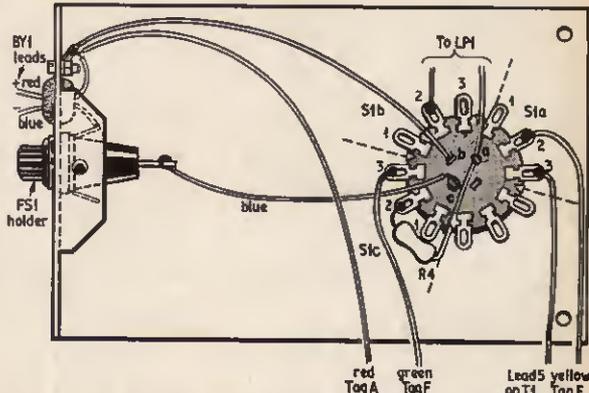


Fig. 2. New wiring details of S1. Resistor R4 is 4.7Ω 3W wirewound

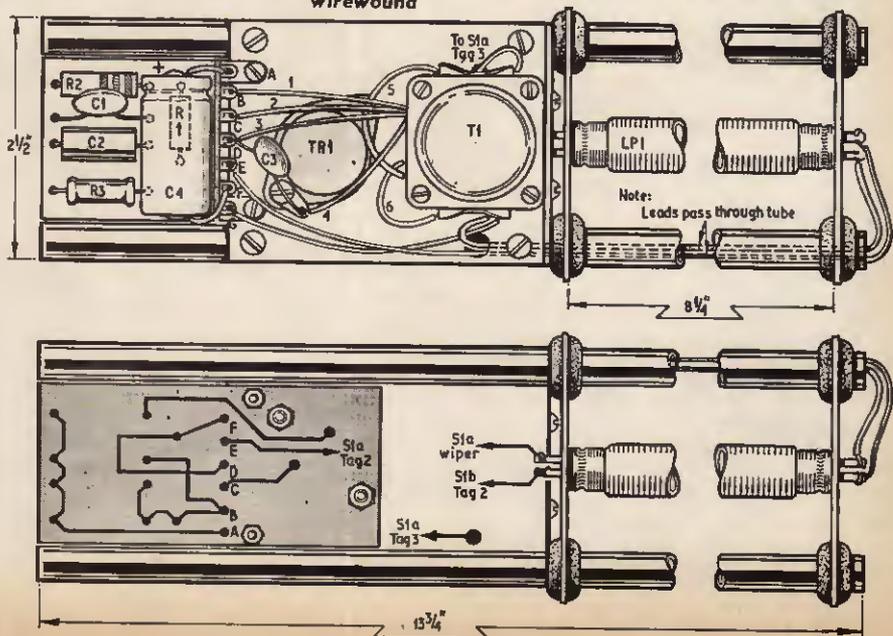

Readout —

A SELECTION FROM OUR POSTBAG

Traffic delay

Sir—I am interested in the mechanical delay system employed in car reverberation units that I have seen and heard on recent visits to the U.S.

Radiomobile have done some research but have since dropped the idea as they feel there is insufficient interest over here (or so they say).

One problem appears to be the harder springing of U.K. vehicles than that found on U.S. cars, however, I hear there is even one delay system now that allows the car to be driven off the curb without vibration to the unit.

I am told that the spring (or whatever) assembly should be mounted along the car axis and not across it.

I am not deterred by hard springing and am keen to build one and use it in conjunction with my car radio, and do not see the electronics posing too much of a problem.

I am advised that a 2 watt output from the echo amplifier would be sufficient against the 8 watt output of my radio. Control of echo is normally done from a potentiometer mounted under the dashboard.

A speaker mounted on the back shelf (if possible) alongside the main speaker makes the sound appear to be 100ft behind you. A marvellous sensation for relaxing in heavy traffic.

In conclusion, I should appreciate any information you or any readers could give me as to the best drive, pick-up units (to avoid microphony) and the best suspension to avoid rattle.

M. C. Bell,
Henley-on-Thames.

Any suggestions?

Cranky?

Sir—Whilst this magazine publishes many interesting and useful projects it sometimes contains circuits which are complicated when compared with the function they are intended to perform. I feel that there is a real danger of using electronics simply for the sake of using them. This could easily detract from the useful purpose of the magazine and the good standing of electronic experimenters. Any person using a complicated circuit to perform a simple function must be regarded as a "crank". For *Impact Counter* (March 1968) with a transducer, Schmitt trigger, twenty

resistors, eleven capacitors, seven transistors, five diodes, etcetera, why not connect the electro-mechanical counter to a pair of contacts and a battery? The contacts may wear but the saving on the other components would more than pay for them. As for the steam presence alarm, same issue, dare I suggest a whistling kettle?

F. Crimmins,
Folkestone, Kent.

IMPACT COUNTER. To answer this criticism, it is necessary to explain the particular problem this device was designed to cope with.

The original purpose of the impact counter was to count small neon lamps, which weigh $\frac{1}{16}$ oz. The contacts must not close more than once per neon, and must always close whether the neon wire leads are upwards or downwards. It is not possible to use anything but a very open funnel as the neons tend to bridge. The closure time must be long enough for the counter to operate properly, therefore the monostable pulse is adjusted so that it allows the neon to bounce inside the pulse length.

For industrial use reliability and ease of replacement are important. This circuit divides readily into four parts which can be tested independently.

STEAM PRESENCE ALARM. You can certainly suggest a whistling kettle, but it would be no use to a deaf person, or if you are out in the garden. The simple sensor can be used with an electronic relay to operate an audible alarm, or even to switch off the stove if you wish.

May we suggest these are two good examples of electronics being used practically?

What's in the box?

Sir—I was very interested by C. F. Weir's article in the February issue of P.E. on *Cine and Tape Sync*. His suggestion at the end for an all-electronic version prompted some thinking on my part because I possess a similar cine system to that of Mr Weir, but in 8mm.

It occurred to me that a 16 frame/sec projection has each frame flashed three times on the screen to avoid flicker, this being done by a rotating disc with three sectors in the optical projection system. Thus the screen picture flashes 48 times per second.

If the projection rate is increased to $16\frac{2}{3}$ frames/sec, then the picture


flashes become 50 per sec. This could be synchronised with a 50Hz signal from the second track of a tape recorder, if the flashes are detected by a light sensitive resistor. At this point I am stumped, because the next step is to convert any error in the two frequencies into a signal which will fire an s.c.r. in the power leads to the projector. The problem is set in the following diagram.

Could any readers possibly suggest a circuit for the black box?

The tape recorder need not be a full stereo type, but it should be four track with leads to the head winding which is not actually playing the sound track. This is the case with many Philips/Coscor/Stella machines which are mono with a stereo outlet socket. If the model is transistorised, then the same socket could provide power for the "black box", since a few milliamps at about -20V are available. Two-track machines could have a third head mounted to scan the lower track, which should be pre-recorded, when the upper track is recorded with 50Hz from a step-down mains transformer.

It is important to note that the s.c.r. will only control an a.c./d.c. type motor, and the control should never feed a transformer which is used to power a low voltage projector bulb.

D. Watts,
Lincoln.

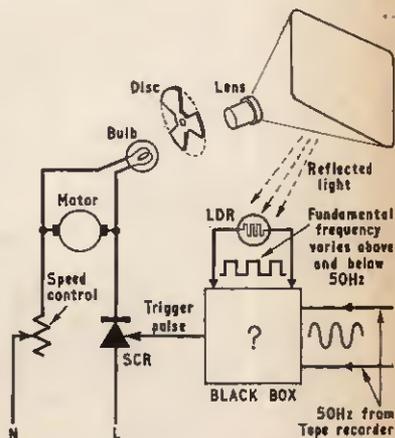

Series of talks

Sir—Your Sussex readers may be interested in the following announcement, which will shortly be locally advertised:

"A series of six talks and demonstrations on High Fidelity, Stereo and Sound production will be given weekly at the Portland Further Education Centre, 11 Portland Road, Hove, on Wednesdays, commencing 24th April, 1968. Evenings from 7.0-9.0 p.m.

Further details may be obtained from the Principal for Further Education at 62 St Leonards Gardens, Hove, Sussex."

BI-PRE-PAK LIMITED

TRANSISTORS PRICE

AC107	6/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	2/6	OC200	5/-
AC128	3/-	OC201	8/-
ACY17	5/-	2G301	2/6
AF114	4/-	2G303	2/6
AF115	3/-	2N711	10/-
AF116	3/-	2N1302-3	4/-
AF117	4/-	2N1304-5	5/-
AF118	3/6	2N1306-7	6/6
AF119	3/6	2N1308-9	8/-
AF178	10/-	2S303	2/6
BCZ11	5/-	Power Transistors	
BFY50	5/6	OC20	10/-
BSY25	7/6	OC23	10/-
BSY26	3/-	OC25	8/-
BSY27	3/-	OC26	5/-
BSY28	3/-	OC28	7/6
BSY29	3/-	OC35	5/-
BSY55A	3/-	OC36	7/6
OC41	2/6	GP826	40/-
OC44	1/11	2N2287	20/-
OC45	1/9	Diodes	
OC71	2/6	AA142	2/-
OC72	2/6	OA1Q	2/6
OC73	5/-	OA70	1/9
OC81	2/6	OA79	1/9
OC81D	2/6	OA81	1/9
OC83	4/-	OA182	2/-
OC139	2/6	IN914	1/6
OC140	3/6		

EXCITING NEW PAKS FOR AMATEURS, PROFESSIONALS, FACTORIES, ORGAN BUILDERS, AND THOSE PEOPLE THAT JUST USE LARGE QUANTITIES OF TRANSISTORS.

XA PAK

Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1000

XB PAK

Silicon TO-18 CAN type transistors NPN/PNP mixed lots, with equivalents to OC200-1, 2N706a, BSY27/29.

PRICE £5.50 PER 500
PRICE £10 PER 1000

XC PAK

Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £5 PER 1000

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMICONDUCTORS. FREE PACKS SUSPENDED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PACK.

P/P 2/6 PER PACK (U.K.)

PRE-PAKS

No.		Price
A1	6 Silicon rectifiers 8Y100 type	- 20/-
A3	20 Mixed marked and tested trans.	- 20/-
A13	25 New trans. & diodes marked & tested	20/-
A15	2 Power Comp. Pair. AD161/2	- 20/-
A17	3 Sil. stud recs. 6 amp. 400 PIV. BYZ12	- 20/-
A18	2 Sil. stud recs. 10 amp. 800 PIV.	- 20/-

B1	50 Unmarked untested, trans., new Mixed Types	- 10/-
B2	4 Solar cells, inc. Book of Instructions	10/-
B3	4 OA5 gold bonded, diodes Mullard	- 10/-
B5	7 Matched set, OC44,45/81D/81 + diode	- 10/-
B6	15 Red spot AF. trans. or white spot RF	10/-
B8	2 Power trans. OC26/35 type	- 10/-
B9	1 Light sensitive cell, ORP12 type	- 9/-
B10	10 50V trans. germ. PNP latest type	- 10/-
B44	1 Tunnel diode, AEY11, 1050 Mc/s	- 10/-
B21	2 Sil. recs. 10 amp., 50-100 PIV	- 10/-
B45	1 Power trans. ADY22/TK400A VCB64 IC 8 Amps. PNP	- 10/-
B49	2 Power trans. GET 9 VCB64 IC 8 amp. germ. PNP	- 10/-
B66	150—Germanium diodes, untested	10/-

C2	1 Unijunction, 2N2160 or 2N2646	- 15/-
C4	2 RF power trans., OC22 and BUY11	- 15/-
C15	4 Silicon PNP trans. in the 2S300 Series	15/-
C31	4 Sil. recs. 800 PIV 2 amp. top hat	- 15/-
C32	2 Power trans. TK400A/NKT404 VCB64 IC 8 amp. 70 amp. 400 PIV SCR special offer	15/- 70/-

INTEGRATED CIRCUITS (TEXAS)

SN7430 8 INPUT POSITIVE NAND GATE **19/6**

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for any car. State 4 or 6 cylinder. **20/- each**

FREE CATALOGUE AND LISTS for:—

TANTALUM CAPACITORS, TRANSISTORS, RECTIFIERS & CIRCUIT DIAGRAMS, SUBSTITUTION CHART

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

THERE IS ONLY ONE **BI-PRE-PAK LTD** BEWARE OF IMITATIONS

FREE!
PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

TRANSISTORS ONLY 1/- EACH

SILICON • PLANAR • N.P.N. • P.N.P

All these types available

2N929	2N706	2S131	2S103	2N696	2N1613	2S733	BFY10
2S501	2N706A	2S512	2S104	2N697	2N1711	2N726	2S731
2N2411	2N3011	2S102	2N2220	2N1507	2N1893	2N2906	2S732

All tested and guaranteed transistors—unmarked. Manufacturers over runs for the new PRE-PAK range.

FIRST EVER LOGIC KITS

Learn for yourself how computers work, even make one for yourself. Full instructions for a thoughts and crosses machine, binary counters, timers, etc. L.1. 5gns. L.2. 10gns. No need to purchase both kits, you can start with L.2. which incorporates L.1. Details free.

NEW UNMARKED UNTESTED PAKS

25	BSY95A NPN Silicon	TRANSISTORS	10/-
10	1000 PIV 1 amp. Min. Silicon	DIODES	10/-
25	BSY26-27 NPN Silicon	TRANSISTORS	10/-
10	10 Watt Silicon All Voltages	ZENERS	10/-
25	BFY50-1-2 NPN Silicon	TRANSISTORS	10/-
10	4 amp. Stud. Silicon	RECTIFIERS	10/-
25	BC107-8-9 NPN Silicon	TRANSISTORS	10/-
40	1N914-8 Sub. Min. Silicon	DIODES	10/-
50	Min. Germ. High Quality	DIODES	10/-
25	2N706 A NPN Silicon	TRANSISTORS	10/-

PRE-PAK, N.605 POWER TRANSISTOR EQUIVALENT TO NKT301-4 **5/- each**
TANTALUM CAPACITORS **4/- each**

FREE! A WRITTEN GUARANTEE WITH ALL OUR SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

Practical Electronics Classified Advertisements

The pre-paid rate for classified advertisements is 1/3 per word (minimum order 15/-), box number 1/6 extra. Semi-displayed setting £4.2.6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL ELECTRONICS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL ELECTRONICS, George Newnes Ltd., 15/17 Long Acre, London, WC2, for insertion in the next available issue.

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, 5000 models. List 1/6. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6. SHE 8441.

SERVICE SHEETS. RADIO, TELEVISION, TAPE RECORDERS, 1925-1963, by return post, from 1/- with free fault-finding guide. Catalogue 6,000 models, 2/6. Please send stamped addressed envelope with all orders/enquiries. HAMILTON RADIO, 54e London Road, Bexhill, Sussex.

WANTED

VALVES WANTED, brand new popular types boxed. DURHAM SUPPLIES (E), 175 Durham Road, Bradford 8, Yorkshire.

SITUATIONS VACANT

RADIO TECHNICIANS

A number of suitably qualified candidates are required for unestablished posts, leading to permanent and pensionable employment (in Cheltenham and other parts of the U.K. including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" Level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications. A knowledge of electro-mechanical equipment will also be an advantage.

Pay according to age, e.g. at 19—£828, at 25—£1,076.

Prospects of promotion to grades in salary range £1,159—£1,941. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply. Application forms available from:

Recruitment Officer (RT/54)
Government Communications Headquarters
Oakley
Priors Road
CHELTENHAM, Glos.

SITUATIONS VACANT (continued)

RADIO & TELEVISION SERVICING RADAR THEORY & MAINTENANCE

Vacancies regularly exist in industry for men with good knowledge of Radio TV and Radar. Our one-year day courses provide effective training. Shorter day courses available for men with experience. Write for details to:—

The Secretary, London Electronics College, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373 8721



A.M.I.E.R.E., A.M.S.E. (Elec.), City & Guilds, G.C.E., etc., on "Satisfaction or Refund of Fee" terms. Wide range of Home Study Courses in Electronics, Computers, Radio, T.V., etc. 132-page Guide—FREE. Please state subject of interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 124K), Aldermaston Court, Aldermaston, Berks.

YOUNG MAN, age about 17, required for interesting work concerned with machine tool automation. Suitable applicant must be interested in, and have some practical knowledge of electronics. AKERMAN & JEAVONS (Birmingham) LTD., Green St., Birmingham 12.

TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS.
- C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-meter and valve volt meter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES.

**INTERNATIONAL
CORRESPONDENCE
SCHOOLS**

**A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!**

International Correspondence Schools
(Dept. 152), Intertext House, Parkgate Road,
London, S.W.11.

NAME

Block Capitals Please

ADDRESS

5.68

20 PENYVERN ROAD, EARLS COURT, LONDON, S.W.5. Tel. 01-373 8721

This Private School provides full and part day training in the following professional subjects

RADIO & TELEVISION SERVICING RADAR THEORY & MAINTENANCE RADIO TELEGRAPHY



TAPE RECORDERS, TAPES, ETC.

TAPES TO DISC—using finest professional equipment—45 r.p.m. 18/-. S.A.E. leaflet. DERBY, High Bank, Hawk Street, Carnforth, Lancs.

20% CASH DISCOUNT on most famous makes of Tape Recorders, Hi-Fi equipment, Cameras, etc. Join England's largest Mail Order Club now and enjoy the advantages of bulk buying. Send 5/- for membership card, catalogues, price lists and ask for quotation on any item. C.B.A. (Dept. A18), 370 St. Albans Road, Watford, Herts.

FOR SALE

BRASS, STEEL, LIGHT ALLOY, STAINLESS STEEL TUBE. Bar Material, Tools, Mechanical, Electrical, plus Assorted Lots. Send S.A.E. for latest Cat. of 1,000 items. K. R. WHISTON, Dept. BPE, New Mills, Stockport.

ENTHUSIAST CLEARS OUT. All gear, components and manufacturers' information. Sell lot for 250. Phone 01-445 8276.

EXPERIMENTERS! Masterbox kits will provide a smart and efficient enclosure for your electronic whatever-it-is. Screwdriver assembly, modular construction. Details from COCKROBIN CONTROLS, 36 Villiers Avenue, Surbiton, Surrey.

100 PAGE Illustrated Catalogue No. 17 Government and manufacturers' electronic surplus, also new section of latest semi-conductors and miniature components. Credit voucher for 2/6 included. Price 3/- post free. ARTHUR SALLIS LTD., 93 North Road, Brighton.

★ HAMMERITE ★

HAMMER PATTERN ENAMEL

AIR DRYING • JUST BRUSH ON

TRIAL TIN

(covers 5 sq. ft.)

3/9

+ 9d. post.

2½ oz. tins 3/9, ½ pint (18/-) 1 pint 16/-. (Carr.: orders up to 5/-, 9d.; up to 10/-, 1/9; over 10/-, 3/-) Colours: blue, silver, black, bronze. No primer needed. Panel transfers, fireproof spray thinners. LIST FREE.

**INDUSTRIALISTS
SAVE TIME AND \$\$\$s
(2 pints will do a Man)**

AMAZING RESULTS - JUST TRY IT!

FINNIGAN SPECIALITY PAINTS (PE)
Mickley Square, Stocksfield, Northumberland
Tel.: Stocksfield 2280

MORSE MADE !! EASY

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed. For details and course C.O.D. ring S.T.D. 01-680 2800 or send 8d. stamp for explanatory booklet to:
G3CRS/B, 45 GREEN LANE, PURLEY, SURREY

EDUCATIONAL

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation. I.E.R.E.; City & Guilds; R.T.E.B., etc. Also practical courses with equipment. No books to buy. Write for FREE Prospectus to ICS (Dept. 577), Intertext House, London, SW11.

FREE TO AMBITIOUS ENGINEERS! 132 page Guide to B.Sc. (Eng.), A.M.I.E.R.E., A.M.S.E., A.M.L.M.I., City & Guilds, A.I.O.B., A.R.I.C.S., G.C.E., etc., on "Satisfaction or Refund" terms. Thousands of passes—over 600 Home Study Courses in all branches of Engineering, Building, Radio, Electronics, etc. Write: B.I.E.T. (Dept. 125K), Aldermaston, Court, Aldermaston, Berks.

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. A.M.I.E.R.E., R.T.E.B., City & Guilds, Radio, T.V., Telecoms., etc. For FREE 100-page book, write Dept. 856K, CHAMBERS COLLEGE, 148 Holborn, London, E.C.1.

EXTENSION SPEAKERS in mahogany, hand veneered and polished complete with 7 x 4 speaker. Retail price 48/- carr. paid. Trade enquiries invited. P. F. & A. R. HELME, Dept. PE, Butcher Pasture, Summerbridge, Harrogate, Yorks.

BRIMHAM

—A NAME WORTH HEARING!

FULL DETAILS OF:

BRIMHAM SPEAKER SYSTEMS

LOUDSPEAKER CABINETS FOR D.I.Y.

FROM

P. F. & A. R. HELME

(Dept. P.E.)

**BUTCHER PASTURE, SUMMERBRIDGE
HARROGATE, YORKS.**

CITY AND COUNTY OF BRISTOL BRISTOL TECHNICAL COLLEGE

Principal: E. Poole, B.Sc.(Eng.), C.Eng., M.I.Mech.E., M.I.Prod.E.

CAREERS IN RADIO AND RADAR

Marine Radio Officers

2-year full-time course for young men aged 16, upwards, leading to First and Second Class P.M.G. Certificates and B.O.T. Radar Maintenance Certificate.

Conversion Course (Second Class to First Class).

R.T. Courses (for Full or Restricted Licence).

Marine Electronic Maintenance Engineers Course (for qualified Marine Radio Officers).

Licensed Aircraft Radio Engineers

2-year full-time course for A.R.M.E. Licences, categories A and B, and six months courses for Radar Rating in association with the above.

Training given on the latest types of Marine and Aircraft Equipment in newly equipped Laboratories at

THE SCHOOL OF MARINE RADIO AND RADAR

Senior Lecturer-in-Charge: F. E. Barltrop

For details, write to:—

**The Registrar, BRISTOL TECHNICAL COLLEGE
ASHLEY DOWN, BRISTOL 7**


ELECTRICAL

COMMUNICATION RECEIVER

TYPE
T.R.G.D.X./20.C.

Brand new fully transistorised and fully portable Communications Receiver. Specifications: 4, complete ranges 550 Kcs to 36 Mc/s, covering all amateur bands, shipping and trawler bands, and broadcast band. A highly efficient double tuned superhet, comprising R/F aerial tuning section, A.V.C. and built in B.F.O. for C.W. or SSB reception. Ideal for fixed or mobile reception. With speaker and headphone output. Hammer finished robust steel case of pleasing modern design. Size approx. 8 x 7 in. British manufacture. Due to huge purchase we can offer these excellent receivers at less than half their normal price. Complete with handbook £10/10, carriage and insurance 17/6. Headphones if required 15/- extra, i.p. 2/4. FREE. First orders received up to fourteen days after publication date of this advertisement will receive free a wonderful battery eliminator enabling you to run this receiver and most transistor radios direct from the mains.

HEAT LIGHT SPEED CONTROL Unit

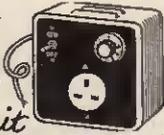

LATEST ELECTRONIC BREAKTHROUGH. CUT YOUR ELECTRICITY BILLS BY HALF. FINGER-TIP CONTROL OF ALL ELECTRICAL APPLIANCES UP TO 3,000 WATTS. HEAT. Vary the heat of your ELECTRIC IRONS, and have electricity. Ideal for ELECTRIC BLANKETS, household IRONS, shower your ELECTRIC KETTLE. Excellent for SUN-RAY LAMPS. LIGHT. Control the brightness of all household LAMPS, from a glimmer to full brightness. Ideal for SPOT LAMPS, ARC LAMPS, etc. Useful for FLOODLIGHTS, SPEED. Controls the speed of ANY ELECTRIC DRILL, for any application. Super for LATHES, GRINDERS, FOOD MIXERS, VACUUM CLEANERS, WASHING MACHINES, SPIN DRIERS, HEDGE CUTTERS. WILL CONTROL ALL UNIVERSAL MOTORS UP TO 2 H.P. These units must not be confused with ordinary resistances and rheostats that waste power. Contained in a strong metal case, in black or grey, size now 6 1/2 x 6 1/2 inches. SIMPLE TO USE. No specialised knowledge required. A unique electronic achievement, contains 7 transistors and thyristors and many other miniature electronic components. COMPLETELY SAFE AND APPROVED. Brand new and ready to use improved de-luxe model. Price £8/10, carriage and insurance 10/-. C.O.D. if required. Discount given to Schools, Universities and Research Establishments. Free demonstration at our premises. Dept. P.E.11

GLOBE SCIENTIFIC LTD

24 CAWOODS YARD, MILL STREET
LEEDS 9 TEL. LEEDS 25593
Callers welcome

MISCELLANEOUS

CALL OR SEND for list from the most interesting shop in Lancashire. Electrical Mechanical and Electronic Goods. ROGERS, 31 Nelson Street, Southport.

"PRACTICAL ELECTRONICS" Rhythmic Effects Unit. Impact Counter. Fluorescent Camping Light. Glissando Vibe. Spring Line Reverb Unit. I.C. Tape Recorder. Combotron. Analogue Computer. Photographic Exposure Meter. Water Level Alarm. Fuzz Box. Yodeler Door Monitor. Harmonic Distortion Meter. I.C. Gram Amplifier. Thyristor Power Controller. Transistor Millivoltmeter. Screenwriter Delay Unit. Investigator Oscilloscope. C.R.O. Trace Doubler. Light Operated Stopwatch. Proximity Detector. Photoflash Slave Unit. Integrated Stereo Amplifier, and all constitutional projects going back to Issue 1. Send s.a.e. for your choice of itemised price lists. AJAX ELECTRONICS, 18a Rumbold Road, Fulham, London, S.W.8.

MISCELLANEOUS

(continued)

3 GANG 500pF TUNING CAPACITORS

New and boxed 7/6 post paid

BIG BARGAIN PARCEL

Capacitors, resistors some high stab. rectifiers, potentiometers, diodes, transistors, connecting wire, etc., only 10/- post paid.

S.A.E. for lists of other bargains

SALOP ELECTRONICS

9a Greyfriars Road, Coleham, Shrewsbury, Salop

BOOKS AND PUBLICATIONS

SURPLUS HANDBOOKS

19 set Circuit and Notes 5/6 P.P. 6d
1155 set Circuit and Notes 5/6 P.P. 6d
H.R.O. Technical Instructions ... 4/6 P.P. 6d
38 set Technical Instructions ... 4/6 P.P. 6d
46 set Working Instructions ... 4/6 P.P. 6d
48 set Technical Instructions ... 6/- P.P. 6d
BC. 221 Circuit and Notes 4/6 P.P. 6d
Wavemeter Class D Tech. Instr. 4/6 P.P. 6d
18 set Circuit and Notes 4/6 P.P. 6d
BC.1000 (31 set) Circuit & Notes 4/6 P.P. 6d
CR.100/B.28 Circuit and Notes 9/6 P.P. 9d
R.107 Circuit and Notes 6/- P.P. 6d
A.R.88D. Instruction Manual. ... 16/- P.P. 1/6
62 set Circuit and Notes 5/6 P.P. 6d
52 set Sender & Receiver Circuits 7/6. post free
Circuit Diagrams 4/- each post free.
R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26.
A.1134, T.1154, CR.300, BC.342. BC.312.
BC.348,J.E.M.P. BC.624. 22 set.
Resistor colour code indicator, 2/- P.P. 6d.
S.A.E. with all enquiries please.
Postage rates apply to U.K. only.
Mail order only to:

Instructional Handbook Supplies
Dept. P.E., Talbot House, 28 Talbot Gardens
Leeds 8

RECEIVERS AND COMPONENTS

BARGAIN PARCELS of new surplus Electronic Components, 2/6, 5/-, 10/-, post free. DOLPHIN ELECTRONICS, 5 Pooles Way, Briar Close, Burntwood, nr. Lichfield.

COMPUTER PANELS

Eight assorted printed circuit panels with transistors, diodes, resistors, capacitors, etc. Guaranteed minimum 30 transistors. Ideal for Experimenters. 8 boards 10/- POST FREE.

Trade and Bulk enquiries welcome.

1500+2000 MFD Electrolytics 25 volt DC wks. 3/- each. 9d. P. & P.

KEYTRONICS, 52 Earis Court Road, London, W.8. Mail order only

RECORDING TAPES

7" D/P 2,400' 18/9
7" L/P 1,800' 12/-
7" STD 1,200' 7/-
5 1/2" D/P 1,800' 14/6
5 1/2" L/P 1,200' 8/9
5 1/2" STD 900' 6/3
5" D/P 1,200' 10/6
5" L/P 900' 7/-
5" STD 600' 5/-
3" D/P 300' 3/9
3" L/P 225' 2/9
3" STD 150' 2/-

Spools: 8 1/2", 5/6; 7", 2/3; 5 1/2", 2/-; 5", 2/-; 3", 9d.

Post and Packing up to 3 reels 2/9 otherwise 4/6.

OC22 8/- OC84 4/6 AFZ12 5/6
OC23 8/- OC170 4/- BCY33 5/6
OC24 8/- OC171 4/- BCY34 5/6
OC25 6/6 OC202 6/6 BCY38 5/6
OC26 6/6 OAB1 1/- BCY39 5/6
OC28 6/6 OA182 2/- BCY70 6/6
OC35 6/6 OA200 2/- BCY71 10/6
OC36 6/6 OA202 2/- BCY72 6/6
OC44 3/- AC107 6/- BFY18 5/6
OC45 2/6 AC126 4/- BFY19 5/6
OC46 3/- AC127 4/- BFY50 5/6
OC70 3/- ACY17 4/- BFY51 5/6
OC71 2/6 ACY18 4/- BFY52 5/6
OC72 2/6 ACY19 4/- BSY20 5/6
OC74 4/- ACY20 5/6 BSY21 5/6
OC75 2/6 ACY21 5/6 BSY27 4/6
OC78 3/- ACY22 4/- BSY28 4/6
OC78D 3/- AD140 8/- BSY29 4/6
OC81 3/- AD149 8/- BSY38 4/6
OC81D 3/- AF114 4/- BSY39 4/6
OC82D 3/- AF116 4/- BSY35A 4/6
OC82 3/- AF117 4/- BY100 4/6

Send S.A.E. for complete list. P. & P. 1/-
A. MARSHALL & SON (London) LTD.
28 Cricklewood Broadway, N.W.2
Tel. 01-452 0161/2. Dept. P.E.19

RECEIVERS AND COMPONENTS

(continued)

REPANGO Transistor Coils and Transformer, for the Constructor. Send stamp for lists RADIO EXPERIMENTAL PRODUCTS LTD., 33 Much Park Street, Coventry.

MICROMINIATURE MICROPHONES

Sensitive dynamic type. Will pick-up rustle of newspaper from 30 feet. Size 9 mm. x 9 mm. x 3.5 mm. Impedance 1 KΩ.

ONLY 18/6
Post free—C.W.O.

SHOWN MICRO DATA SYSTEMS
SIZE 30 BAKER ST., LONDON, W.1

DUXFORD ELECTRONICS (PE)

DUXFORD, CAMBS.

C.W.O. P. & P. 1/-. Minimum order value 5/-. (Trade inquiries invited)

CAPACITORS (Tubular, Axial Leads):
Electrolytic (Mullard) - 10% to +50%:
4V 8μF, 32μF, 125μF, 250μF, 400μF.
6.4V 8μF, 25μF, 50μF, 100μF, 200μF, 320μF.
10V 4μF, 16μF, 32μF, 64μF, 125μF, 200μF.
16V 2.5μF, 10μF, 20μF, 40μF, 80μF, 125μF.
25V 1.6μF, 4μF, 12.5μF, 25μF, 50μF, 80μF.
40V 1μF, 4μF, 8μF, 16μF, 32μF, 50μF.
60V 0.6μF, 2.5μF, 5μF, 10μF, 20μF, 32μF.
All values 1/3 each.
Polyester (Mullard) ±10%:
160V: 0.01μF, 0.015μF, 0.022μF, 6d, 0.033μF, 0.047μF, 7d, 0.068μF, 0.1μF, 8d, 0.15μF, 10d, 0.22μF, 11d, 0.33μF, 1/2, 0.47μF, 1/3, 0.68μF, 2, 1μF, 2/6.

0.001μF, 0.0015μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 0.0068μF, 0.01μF, 6d, 0.015μF, 0.022μF, 7d, 0.033μF, 8d, 0.047μF, 0.068μF, 9d, 0.1μF, 10d, 0.15μF, 1/1, 0.22μF, 1/5, 0.33μF, 2/1, 0.47μF, 2/6.

Polyethylene: ±5%. 160V: 5pF, 10pF, 15pF, 22pF, 33pF, 47pF, 56pF, 68pF, 100pF, 150pF, 220pF, 330pF, 470pF, 680pF, 820pF, 5d, 1, 1,000pF, 1,500pF, 2,200pF, 6d, 3,300pF, 4,700pF, 5,600pF, 7d, 10,000pF, 8d, 15,000pF, 22,000pF, 9d.

POTENTIOMETERS (Carbon): Long life, low noise. ±W at 70°C. ±20% ±1M, ±30% ±1M. Body dia. 1in. Spindle, 1in x 1in. 2in. each. Linear: 100, 250, 500 ohms, etc., per decade to 10M. Logarithmic: 5k, 10k, 25k, etc., per decade to 5M.

SEKELTON PRE-SET POTENTIOMETERS (Carbon): Linear: 100, 250, 500 ohms, etc., per decade to 5M.

Miniature: 0.3W at 70°C. ±20% ±1M, ±30% ±1M. Horizontal (0.7in x 0.4in P.C.M.) or Vertical (0.4in x 0.2in P.C.M.) mounting, 1/- each. 100V, ±0.1W at 70°C. ±20% ±1M, ±30% ±1M. Horizontal (0.4in x 0.2in P.C.M.) or Vertical (0.2in x 0.1in P.C.M.) mounting, 10d. each.

RESISTORS (Carbon film): High stability, very low noise. ±W at 70°C. Body 1/2in x 1/2in. Values in each decade: 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91 from 10V to 10M. 1/2W, 1/4W, 1/8W, 1/16W, 1/32W, 1/64W, 1/128W, 2.7M, 3.3M, 3.9M, 4.7M, 5.6M, 6.8M, 8.2M, 10M, ±10%, 2d. each.

SEMI-CONDUCTORS (All new): OAS, OAB1, 1/6, OC44, OC45, 1/9, OC71, OC72, OC73, OC81, OC8D, OC82D, OC70, OC71, 2/3, OC140, AF115, AF116, AF117, 3/-.

SILICON RECTIFIERS: 0.5A at 70°C. 400 P.I.V., 3/-, 800 P.I.V., 3/3, 1,250 P.I.V., 3/9, 1,500 P.I.V., 4/-.

SEND S.A.E. FOR JANUARY 1968 CATALOGUE

BYZ10 9/6 NKT674 6/-
BYZ11 8/- NKT677 6/-
BYZ12 6/6 NKT713 5/6
BYZ13 5/6 NKT734 5/6
GET102 4/- NKT736 5/6
GET103 4/- NKT773 6/6
NKT241 6/6 NKT781 6/-
NKT242 6/6 2N696 5/-
NKT244 5/6 2N697 5/-
NKT245 5/6 2N706 4/6
NKT261 4/6 2N706A 4/6
NKT262 4/6 2N708 5/-
NKT264 4/6 2N2220 5/-
NKT271 4/6 2N2221 5/-
NKT603 6/6 2N2222 3/-
NKT613 6/6

VEROBOARDS: 3 1/2" x 2 1/2", 3/6; 3 1/2" x 3 1/2", 4/3; cutter, 9/-.

DEE GEE: 30 watt Soldering Irons, 16/- each.

SPEAKERS: 3 ohm, 5", 14/6; 8" 25/6; 12", 39/6; 7" x 4", 16/6; 3", 9/6.

RESISTORS: 1/2 watt, 8d; 1 watt, 6d. ELECTROLYTICS: 15v 1 MFD up to 100 MFD, 1/6 each.

MULLARD

AC107	14/6	BFY50	6/-	OC82	4/6
AC127	6/-	BFY51	5/-	OC82D	4/3
AC128	4/-	BFY52	6/-	OC83	3/6
AC176	6/-	BSX79	3/-	OC84	4/-
AD140	12/8	BTY79-400R	24/6	OC123	7/-
AD149	11/-	BTY87-150R	23/-	OC139	12/-
AD161	7/6	BTY91-150R	35/-	OC140	12/-
AD162	7/6	BSX36-100	3/-	OC169	6/-
ACY17	5/-	BTY87-500R	47/-	OC170	4/-
ACY20	3/6	BYZ10	11/-	OC171	6/-
ACY21	4/-	BYZ12	7/6	OC200	6/-
ACY22	2/6	BYZ13	5/-	OC201	9/-
AFZ11	10/-	BZY93 C24	12/-	OC202	13/-
AFZ12	11/9	BY100	5/-	OC203	8/-
AF102	18/-	BYX20-200	8/-	OC204	11/-
AF114	4/9	GET102	5/4	OC205	10/6
AF115	4/9	GET103	4/4	OC271	19/6
AF116	4/9	GET111	10/-	ORP12	9/-
AF117	4/9	GET573	10/-	ORP60	8/-
AF118	9/-	OC19	5/-	ORP63	9/-
AF186	12/-	OC20	33/-	ORP93	18/-
AF239	12/-	OC22	13/-	ORP90	19/6
AS526	5/-	OC23	25/-	OAS	3/-
AS528	5/-	OC24	19/-	OA10	7/-
AS529	8/6	OC25	7/-	OA47	1/6
ASZ21	4/-	OC26	12/-	OA78K	1/6
BA115	2/6	OC28	12/-	OA73	1/6
BC107	4/3	OC29	15/-	OA79K	1/6
BC108	4/3	OC35	9/6	OA81K	1/6
BC109	4/3	OC36	13/-	OA85K	1/6
BCY10	20/-	OC41	3/6	OA90K	1/6
BCY12	22/-	OC42	4/-	OA91K	1/6
BCY30	7/6	OC43	3/-	OA95K	1/6
BCY31	9/-	OC44	3/-	OA200	2/-
BCY32	8/-	OC45	3/-	OA202	2/-
BCY33	6/-	OC71	3/-	OA210	7/6
BCY34	8/-	OC72	4/6	SX631	7/-
BCY38	19/-	OC73	3/-	SX636	10/-
BCY39	10/-	OC75	5/-	SX638	12/-
BCY40	16/-	OC76	3/-	SZ20C	13/-
BCY71	15/-	OC81	3/-	615V	95/-
BCZ11	10/-	OC81D	3/-	SVCI	19/9



J.E.D.E.C.

2N385A	11/-
2N388A	15/-
2N696	9/-
2N706	6/-
2N706A	4/6
2N711	7/6
2N1132	10/-
2N1302	5/-
2N1303	5/-
2N1304	6/-
2N1305	6/-
2N1306	8/-
2N1307	8/-
2N1308	10/6
2N1309	10/9
2N2147	17/-
2N2160	14/9
2N2644	10/-
2N3436	6/9



INTEGRATED CIRCUITS

Epoxy TOS 9
lead μ L 900 Buffer
@ 11/-
 μ L 914 Dual Gate
@ 11/-
 μ L 923 J-K Flip
Flop @ 14/-
4-page reprint on
IC usage circuits
data, etc. 2/6

FLANAR BARGAIN
2N1925 Yellow
4 for 10/-
NEW G.E.

Over 2,000 transistor and diode types ex stock.

Resistors: $\frac{1}{2}$ Watt 5% Miniature type, low noise—high stability. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades to 820K. 1-25 pieces, 4d; 25-99, 3d; 100 pieces or over, 2d each. 10% tolerance, $\frac{1}{2}$ Watt, 1 Meg. to 8-2 Meg., same price.
Preset potentiometers, Standard or Subminiature types, 20% tolerance. Lin. vertical or horizontal. 100, 250, 500 ohm, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1 Meg, 2.5 Meg, 5 Meg. All at 1/6 each. Discounts for quantities over 12 of 1 value.



BARGAINS IN SEMICONDUCTORS ALL TYPES



LST COMPONENTS

7 COPTFOLD ROAD
BRENTWOOD ESSEX
BRENTWOOD 7904
24 HOUR POSTAL SERVICE

"X" LINE MODULES

Send for details of our range of ready-built solid-state circuits, amplifiers, sirens, light flashers, etc.

FAIRCHILD AF 11 20W SOLID STATE AMPLIFIER KIT £8.8.0 Complete

Includes Printed circuit board, Semiconductors, Resistors, Capacitors, Heat sink and short circuit protection components. S.A.E. for details.

1968 CATALOGUE
34 pages +
NOW AVAILABLE
send 1/6 stamps

POST & PACKING 9d
per order
EXPORT ENQUIRIES WELCOME

TRANSISTOR MANUALS
G.E. New Edition 29/6
R.C.A. Latest Edition 27/6
+ 2/6 Post & Packing
RETAIL AND WHOLESALE SUPPLIED

GUARANTEE: All the above-listed semi-conductor devices are Brand New, First Grade, and guaranteed. We will replace at no charge any device found to be faulty. Further: all devices carry the Manufacturer's name or Trade Mark, type number and batch number. We do not offer for sale devices often described as "new and tested" or bearing re-marked type numbers, these often have a short and unreliable life. **LST COMPONENTS**

REDUCED PRICES

2N10738 PNP 120v 60W 1.5MHz (TO-41 can)
10/-, 2N2290 Electrically as 2N10738 (TO-3 can)
10/-, Ex-equipment, tested, either type 5/- each,
5 for 20/-. Rechargeable batt., DEAC 12.2v 450
mA/hr 17/6, P. & P. 2/6. P/cct board Edge Connectors,
0.2 matrix, 12 way 2/6, 17 way 3/-, 22
way 7/6, 30 way 4/-, 32 way 5/-, 2W pots, 1/-
spindle, 5k, 2k, 1k, 500, 100 ohms. 1/-, Presets,
min. pots 1W 270k, 100k, 330, 270 ohms, 9d.
Terms C.W.O., Min. order 5/-, P. & P. 1/-,
S.A.E. for list. Mail order only.
T. L. WILLIAMS
2 CHESTNUT CLOSE, ADDESTONE, SURREY

STUDENT ELECTRONIC SERVICES

194 Regent Road, Salford 5
We stock a wide range of Resistors $\frac{1}{2}$ and $\frac{1}{4}$ watt.
Buy individually OR try the S.E.S. Pre-Pack.
Stocks now include Potentiometers—Log. and Lin.
Enclose 6d. for complete price list

FANTASTIC OFFER !!!

Computer printed circuit boards.
Comprising transistors, diodes, resistors, etc. Ideal for constructing amplifiers, receivers, etc., etc.
Price: 5 boards for only 10/- P. & P. 2/-.
TELE-RADIO (1943) LTD.
189 Edgware Road, London, W.2

SUPER QUALITY NEW RESISTORS

Carbon film, low noise, high stabs:

Power	Range	Series	Per doz.	Per 100
1W	5% 5-10 to 330k Ω	E24	1/10	14/6
1W	10% 10 to 4.7k Ω	E12	+1d per resistor	
1W	10% 4.7k to 10M Ω	E12	1/9	13/6
1W	5% 4.7k to 10M Ω	E24	2/2	17/-
1W	10% 10k to 10M Ω	E12	3/3	25/10

1/6 per 100 less in 100's of one ohmic value.
Please state your choice of values.
Quality Carbon Skeleton Pre-sets: 100 Ω , 250 Ω , 500 Ω , 1k Ω , 2k Ω , 2.5k Ω , 5k Ω , 10k Ω , 20k Ω , 25k Ω , 50k Ω , 100k Ω , 250k Ω , 500k Ω , 1M Ω , 2M Ω , 2.5M Ω , 5M Ω , 10M Ω . Available in horizontal or vertical mounting, 1/- each.
Low Cost Volume Controls: 100 Ω , to 10M Ω , lin., 2/3 each; 5k Ω to 5M Ω , log., 2/3 each.
Log. Stereo: 100k Ω , 250k Ω , 500k Ω , 1M Ω , 2M Ω , L.S., 9/-, D.P. sw. 12/6.
Carbonics: 100, 220, 470, 1,000, 2,200, 4,700pF, 500V, 5d; 0.005, 0.01, 0.02, 0.05uF, 50V, 5d.
Electrolytics: 5, 10, 25, 50uF, 10V, 5/10uF, 25V, 9d; 100, 200uF, 10V, 25, 50uF, 25V, 1/-.
Sub-min. C426 range: all values in stock.

PICK OF THE NEW SEMICONDUCTORS

Silicon, many types including:
BC107, 45V, β 125-200, 4/-
BC108, 20V, β 125-900, 3/11.
BC109, 20V, β 240-900, 4/-
BC109 and BC169 are low noise types, BC167, BC168 and BC169 are plastic
Best Value For
Power: 2N3055, 115V, 100V, 16/6; 2N3054, 1/-.
Field Effect: MPF105, gm 2 to 6mA/V, 10/-; 2N3119, 14/6.
VHF and Fast Switching: BSX20 ft. 600MHz, 4/6.
High Gain: 2N3390, 8400-1,250, 6/-.
Low Noise: 2N3707, 5/-; 2N3391A, 5/6; 2N4058 (PNP), 5/6.
Sub-Miniature: BC122, 30V, 50mA, 80mW, 250MHz, 8/6.
Low Cost: 2N3926, 18V, 120MHz, 2/6 (our colour selection).
Also: 2N3702, 2N3703, 2N3704, 2N3705, 4/- each; BC109C, 4/3; BFY50, 5/3.

Germanium, many types including:
RP, VHF: NKT603F, 6/-; NKT613F, 5/9; NKT677F, 4/5.
Low Noise: 2G308, 6/9; 2G309, 7/9; NKT275, 3/8.

PEAK SOUND PRODUCTS
CIR-KIT No. 3 Pack, 12/6. Adhesive copper 5ft x 4in or 4in, 2/-; 100ft x 4in or 4in, 30/-.
Perforated board 0.1in matrix 5in x 3 1/2in, 4/-; 2 1/2in x 3 1/2in, 2/6; 2in x 3 1/2in, 2/6. Also SA-B, Stereo Amps at attractive prices.
TRANSISTORISED STEREO AMPLIFIER AND PRE-AMP SAB-8



Complete kit of this very popular amplifier, 16 watts total output, £10.10.0
Power supply kit, £3
Cabinet, £3

15% DISCOUNT on whole order and post free when purchasing on SAB-8!
The most successful amplifier of its kind yet. A real money saver.
Old-Timers: 2N1302, 2N1303, 3/6; 2N1304, 2N1305, 4/-; 2N1306, 2N1307, 6/-; 2N1308, 2N1309, 7/11.
High Power: NKT403, 14/10; 2N2147, 16/9; matching, 1/- pr.
Complementary Output: AD161 (NPN), 9/-; AD162 (PNP), 9/-.

Silicon Diodes:
Low cost: 1S940, 30V, 75mA, 1/3; OA202, 150V, 160mA, 2/-; BY238, 850V, 500mA, 3/11; 1N5054, 800V, 1A, 4/9.
Zener Diodes: 400mW, 5%, 2.7V to 33V (E24 values), 5/3.
Germanium Diodes: OA47, 1/9; OA70, 1/9; OA81, 1/6; OA90, 1/3; OA91, 1/3; OA95, 1/3.

ALL GOODS BRAND NEW • NO SURPLUS • FAST DELIVERY
Discounts: 10% over £3; 15% over £10.
Post and Packing: 1/-; free on orders over £1.
Catalogue: Send 1/- stamps—includes data on all types in stock and many equivalents.

ELECTROVALUE 6 MANSFIELD PLACE, ASCOT, BERKSHIRE

ADROIT ELECTRONICS

Lord Alexander House
Waterhouse Street
Hemel Hempstead, Herts

OC28	5/-	2N2646	12/6	NKT211	4/9	NKT227	8/3
OC35	7/6	2N2926	3/-	NKT212	4/4	NKT228	5/1
OC36	8/6	2N3053	10/-	NKT213	4/6	NKT601	4/9
OC44	1/9	2N3055	19/-	NKT214	3/6	NKT612	4/8
OC45	1/9	2N1482	5/-	NKT215	3/6	NKT613	4/9
OC70	2/3	2N1720	4/6	NKT216	8/3	NKT674	5/-
OC71	2/-	NKT124	8/6	NKT217	7/9	NKT675	4/4
OC72	2/-	NKT125	5/-	NKT218	4/1	NKT676	4/1
OC81	2/3	NKT126	5/-	NKT219	4/1	NKT677	4/1
OC140	4/6	NKT127	8/6	NKT221	4/8	TK20C	1/6
OC170	2/3	NKT128	5/9	NKT222	4/-	TK40C	1/6
OC171	12/6	NKT129	5/-	NKT223	4/1	OAS	1/-
2N696	4/6	NKT141	5/9	NKT224	3/6	OAB1	1/-
2N697	5/-	NKT142	5/-	NKT225	3/6	OAZ00	2/6
2N706	4/3	NKT143	4/9	NKT226	8/9	OAZ10	6/6

BRAND NEW GUARANTEED

R & R RADIO

51 Burnley Road, Rawtenstall
Rossendale, Lancs

Tel: Rossendale 3152

VALVES BOXED, TESTED & GUARANTEED

EBF80	3/-	PCC84	3/-	PY82	3/-
EBF89	3/6	PCF80	3/-	U191	4/6
ECC82	3/-	PCF82	3/6	U301	4/6
ECL80	3/-	PCL82	4/-	6F23	5/-
EF80	1/6	PCL83	4/-	10P14	3/-
EF85	3/4	PCL84	5/-	20P5	3/-
EF183	3/6	PL36	5/-	30F5	2/6
EF184	3/6	PL61	4/-	30L15	3/-
EY86	4/-	PL83	4/-	30P12	4/6
EL41	5/-	PY33	5/-	30C15	5/-
EZ40	4/6	PY81	3/6	30PL13	5/6
EBC41	4/6	PY800	3/6	30PL14	5/6

Send 9d. stamps for complete lists Transistors, Rectifiers, Integrated Circuits, Etc.

Cash with order please. Postage 9d. Airmail extra

POST, ONE VALVE 9d. TWO TO SIX 6d. OVER SIX POST PAID.

BI-PAK SEMICONDUCTORS

(DEPT. E)

8 Radnor House
93/97 Regent St
London W1

KING OF THE PAKS "SUPER-PAKS"
UNEQUALLED VALUE AND QUALITY
BRAND NEW UNTESTED SEMICONDUCTORS
SATISFACTION GUARANTEED IN EVERY PAK

ALL AT
10/-
PER PAK

★ QUALITY-TESTED VALUE PAKS ★ BARGAINS ★

UNIUNION
UT46 Eqvt. 2N2646, 2N3053, 2N3055, 2N3056, 2N3057, 2N4245, 2N4

RECEIVERS AND COMPONENTS

(continued)

Transistor ferrite rod aerials, MW and LW 5m long, 5/- no data.
 Small 7 transistor radios ideal for spares, or repair, in makers boxes with 4 nickel cadmium batteries, battery charger, leather case, stored coiled and no guarantee, bargain @ 22/6 + 2/- P. & P.
 Double gang potentiometers, 200k+200k log., 500k+500k lin, 3/- each.
 Parilla rods, 8 x 31in, 6d each.
 Disc ceramic, 1,000pF (P.C. type) short leads, 3d each; 2/3 doz. (500 VV).
 Transistor capacitors, 0.1mF 50VW, 4d each; 3/- doz. 2mF 6VW, 4d; 4mF 64VW, 50mF 6VW, 100mF 6VW, 10mF 12VW, 6d each; 100mF 9VW, 160mF 12VW, 330mF 9VW, 6d each; 400mF 16VW, 500mF 9VW 1/-.
 Set of 3 transistor double tuned I.F. transformers (470kc/s), 10/- with circuit.
 Mixed bag of silver mica capacitors, 100 for 8/-.
 Mixed bag of silver mica and tubular ceramics, 100 for 8/- (our selection).
 Transistors, GT46B (OC45) 1/6 each.
 Zener diodes, OA2947 2/6, OA2224 3/6, 187051A, 187075A 3/6.
 P.C. board, single sided, 1/2 in. thick, approx. 5in. x 2in, 4d; 4in. x 4in, 6d.
 Polystyrene capacitors, 1,000 pF 5%, 5,000pF 2 1/2%, 3d each; 2/6 doz. (50VW).
 Silver mica capacitors, 25, 30, 47, 50, 75, 82, 137, 220, 330, 375, 500, 1,000pF, wire ended, 350VW, 80, 230, 300, 370, 500, 680, 1,100, 1,500 pF, P.C. type, 200VW.
 Minimum order 5/-.
 POSTAL SERVICE ONLY. Postage: under £1, 1/8; £1 to £2, 2/8. Over £3 post free. S.A.E. for lists.

A. J. H. ELECTRONICS (GBAQN)
 59 WAVERLEY ROAD, THE KENT
 RUGBY, WARWICKSHIRE

STUDENT ELECTRONIC SERVICES

194 Regent Road, Salford 5

Constructional aids — including Assembly Stand (each individually made by craftsmen).

LEKTROKIT—the biggest money and time saver since the safety pin!

Everything to construct a professional job, from a variety of boards, pins to chassis plates and rubber feet.

Special introductory kit in 2 sizes.

Write now for complete price list AND sample resistors, enclosing 6d.

TRANSISTOR CAPACITORS (ELECTROLYTIC)

500mfd 4V	64mfd 40V	16mfd 25V
320mfd 10V	50mfd 10V	10mfd 25V
250mfd 4V	30mfd 10V	6.4mfd 64V
200mfd 16V	25mfd 25V	4mfd 64V
100mfd 16V	20mfd 12V	1mfd 25V

1/- each, 9/- per doz. Min. order 10/-
TRANSISTOR PANELS—OC45 or equiv., 20 for 20/-, 30—25/-, 50—35/-, 70—45/-, 40—30/-, 60—40/-, 50—30/- Postage 2/- per panel
 Brand new STC sil. EPT planar transistors 300 Mc/s 350 mW, all at 2/- each. 2N743, 2N753, 2N916, 85Y26, 85Y28, 85Y65, 85Y18, 85Y95A, 85Y29

TRANSISTORS OC45, TK22C @ 1/- each. OC76, OC139, 2G202, OC81, OC44 @ 2/- each. OC120, OC53, 2N1308, OC72, NKT216 @ 4/- each. OC23, NKT452, NKT453 @ 6/- each. 10 watt heat sink drilled for power trans. 5/-, 1,000mfd 30V 4/-, 3,000mfd 10V 2/-. T.V. capacitors 100 + 200 + 400mfd 275V 7/6, 100 + 200mfd 300V 5/6.

W.W. POTS 5, 10, 25, 50, 100, 250, 500 ohms, 1k, 2k, 2.5k, 5k, 10k, 25k, 50k, 100k, no preset 2/- each, Min. order 5/-. Postage 1/-
ZENER DIODES—2.4, 2.7, 3.6, 4.75, 5.25, 5.75, 6.2, 6.8, 7.5, 9.1, 13, 15, 16, 18, 20, 27, 30, 33 volts, 3/6 each, mostly 1 watt

POLYSTYRENE CAPACITORS 350V: 180, 270, 330, 390, 470, 560, 680, 820pf. 1,800, 2,200, 2,700, 3,300, 5,600, 6,800, 8,200
 125V: 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 4,700, 5,600, 6,800, 8,200. 0.012, 0.015, 80pf ceramic 200pf S.M. any selection 2/- doz. 4-40pf trimmers 4/- doz.

BRAND NEW BOXED CHASSIS, containing 2—OC35, 2—OC29 12 VVW resistors 30/- Postage 1/6

STEREO POTS. Less switch, single spindle, 1 meg + 1 meg log and 1 meg log + 1 meg rev/ log, 7/6 each.

NEW CROSS RADIO
 6 OLDHAM ROAD, MANCHESTER 4

RECEIVERS AND COMPONENTS

(continued)

RESISTORS

1/2 watt carbon film 5%
 All preferred values in stock from 10 ohms to 10 megohms 2d. each.
 Send S.A.E. for free sample

CAPACITORS

Mullard Miniature Metallised Polyester P.C. Mounting, all 250V D.C. working. 0.01mf, 0.022mf, 0.047mf, 0.1mf, 0.22mf, all at 6d. each
 Hunts tubular 0.1mf 200V working at 3d. each

Send 6d. stamp for extensive list of low priced Electronic Components, Instruments and Equipment

Please include 1/- postage and packing on all orders under £1

Dept. P.E.11
BRENSAL ELECTRONICS LIMITED
 CHARLES STREET, BRISTOL 1

PHOTO ELECTRIC CONTROL SYSTEM

Comprises a light source unit with optional Infra Red filter and lens system to force the light. Also a photo-electric relay control unit. Both housed in metal cases for bench or wall mounting, sensitivity control, mains on-off switch. Works from 230/240V a.c. Mains. Can be used as a simple on-off switch by breaking the beam of light (invisible if Infra Red filter is used) and as such it will operate as a burglar alarm, or will open doors, etc. Also in conjunction with a counter or other equipment it will perform many functions in the factory or warehouse. **£9.19.6**

F.M. WIRELESS MICROPHONE
 84-104Mc/s. Transistorised. Operates from 9V battery. Complete with additional secret tie clip microphone. List £12/10/- ONLY **£6.15.0**
 These cannot be operated in U.K.

TRANSISTORISED FM TUNER
 6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for **£6.17.6**
 use. Fantastic value for money

FM MULTIPLEX STEREO ADAPTOR
 Printed circuit bicuit, 4 trans., 6 diodes 9V with full instructions **£5.19.6**

BER TAPE HEADS
 BEAD, 39/6 pair
 8 TRACK

BER TAPE HEADS
 WALL, 39/6 pair
 4 TRACK

REFLEX CONE TYPE WATERPROOF SPKR.
 5 watt, 8 ohm, 300-16,000c/s PA **£4.5.0**
 & Music Relay

SUPER SILICON RECT. T.V., etc., 1,200 PIV 800mA, 6/-; or complete with instr. resistor, condenser, 7/8; 400 PIV HW 6A, 8/-; 200 PIV HW 6A, 8/-.

Stamped envelope for full selection and bargain offers in Multimeters, Radios, Baby Alarms, Intercoms, Walkie-Talkies, Rectifiers and Eagle Lists. UNDER £1—P. & P. 6d. OVER £1 post free. C.O.D. 3/6.

DURHAM SUPPLIES
 175F, Durham Road, Bradford, 8, Yorkshire

PLEASE MENTION
PRACTICAL ELECTRONICS
 When Replying to
 Advertisements

The RADIO AMATEURS HANDBOOK 45/-

1968 Ed. by A.R.R.L. Postage 4/6

COLOUR TV PAL SYSTEM, by Patchett. 40/- P. & P. 1/-.

F.E.T. CIRCUITS, by Turner. 25/- P. & P. 1/-.

BRIDGES AND OTHER NULL DEVICES, by Turner. 24/- P. & P. 1/-.

ABC'S OF TRANSISTORS, by Mann. 20/- P. & P. 1/-.

RAPID SERVICING OF TRANSISTOR EQUIPMENT, by King. 30/- P. & P. 1/-.

HI-FI YEAR BOOK, 1968 EDITION. 15/- P. & P. 1/-.

101 WAYS TO USE YOUR OSCILLOSCOPE, by Middleton. 21/- P. & P. 1/-.

COMPUTER CIRCUIT PROJECTS YOU CAN BUILD, by Boschen. 24/- P. & P. 1/-.

TRANSISTOR SUBSTITUTION HANDBOOK, new 7th edition. 15/- P. & P. 1/-.

SILICON CONTROLLED RECTIFIERS, by Lysel. 21/- P. & P. 1/-.

Where possible 24-hour service guaranteed

UNIVERSAL BOOK CO.
 12 LITTLE NEWPORT ST., LONDON, W.C.2
 (Leicester Square Tube Station)

"PLUS-3" MAINS CONVERTER

Provides three separate switched output voltages 6v, 7iv. and 9v. D.C. Suitable for all types of transistor equipment, radios, amplifiers, record players, etc. Attractive case with indicator light, mains lead, output socket, plug and lead. Size 4 1/2" x 3 1/2" x 2 1/2". (Extra lead with din plug for cassette recorders 7/6)



ONLY
57/6
 P. & P. 2/6

Mains unit for FI-Cord 202A £4.15.6. P. & P. 5/-.

R.G.S. PRODUCTS (RADIO) LTD.
 (Dept. P.E.), 31 Olivier Road, London, E.17

REPEAT OFFER OF CIRCUITS

- NOVIGTS AND CROSSES MACHINE
- BINARY ADDER AND SUBTRACTOR
- FOOTBALL POOL COMPUTER
- MULTIPLYING/DIVIDING ANALOGUE COMPUTER
- SIMULTANEOUS AND QUADRATIC EQUATION SOLVERS

All these circuits for 4/6 post 6d. Diagrams (9 pp.) text (26 pp.) parts and price lists. All purely electrical designs. We are the leaders in this field and can put a date on the publication of each circuit to show that we were the first. Our machines have appeared at exhibitions in this country and abroad, before learned societies and the TV cameras and have even made money for charity.
 Again showing that we lead, we have under development a new circuit, which will Add and Subtract Binary numbers both in parallel and serially as in a full scale computer. The formation of the Sum and Carry is shown step by step. This will prove an invaluable aid to teaching binary arithmetic and computer method. Full details available shortly.
PLANET INSTRUMENT CO., 25(E) DOMINION AV., LEEDS 7

ERSIN



5 CORE SOLDER

for quick,
easy, reliable
soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy also reduces wear of copper soldering iron bits.



**SIZE 5
HANDY SOLDER
DISPENSER**

Contains 10 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy. 2/6 each.



**SIZE 15
SOLDER
DISPENSER**

Contains 21 ft. coil of 60/40 Alloy, 22 s.w.g. Ideal for small components, transistors, diodes, etc. 3/- each.



SIZE 12

Ideal for home constructors. Contains 90 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each.



**BIB MODEL 8
WIRE STRIPPER
AND CUTTER**

Strips insulation cleanly and quickly, fitted with unique 8 gauge wire selector. Plastic handles. 9/6 each.

From Electrical and Hardware shops. If unobtainable, write to:
Multicore Solders Ltd., Hemel Hempstead, Herts.

**SHORT WAVE ONE VALVE
RECEIVER KIT** 39/6 + 2/6 P.P.

PEAC ANALOGUE COMPUTER KIT IN STOCK

UNIT 'A' COMPLETE £26.0.0 + 15/- P.P.

Punched aluminium panels and case for above \$4.17.6 + 5/- P.P.

CLUBMAN Mk. I KIT COMPLETE \$6.17.6 + 5/- P.P.

Without metal work \$4.12.6 + 2/6 P.P.

CLUBMAN Mk. II KIT COMPLETE £10.17.6 + 5/- P.P.

Without metal work £8.12.6 + 4/6 P.P.

EXPLORER KIT COMPLETE £4. 2.6 + 2/6 P.P.

STABILIZED POWER SUPPLY KIT 0-20V. 500ma
COMPLETE \$4.17.6 + 5/- P.P.

**COMBINED AUDIO OSCILLATOR AND FREQUENCY
METER £17 + 10/- P.P.**

PORTABLE TEST UNIT KIT

FLUORESCENT CAMPING LIGHT IN STOCK

**S.A.E. FOR TRANSISTORS, SEMICONDUCTORS, FULL LIST
700 TYPES**

3 SILICON RECTIFIERS, BY100 TYPE 10/-

10 MIXED MARKED TESTED TRANSISTORS 10/-

40 UNMARKED UNTESTED TRANSISTORS NEW 10/-

1 LIGHT SENSITIVE CELL ORP12 8/6

25 MIXED UNMARKED TESTED TRANSISTORS 10/-

2 TRANSISTOR COMP. PAIR AD161/162 16/-

P.P. 1/-

**OUR COMPONENTS CATALOGUE 5/- Post Paid with 10/- worth of
discount vouchers.**

OLRUS ELECTRONICS LTD.

748 HIGH ROAD, LEYTONSTONE

(NEXT TO GREEN MAN)

LONDON, E.11. Tel. 01-989 2751

CALLERS WELCOME—CLOSED ALL DAY FRIDAY

HIGH SPEED MAGNETIC COUNTERS (4 x 1 x 1 in). 4 digit. 12/24/48V. (state which) 6/6 each. P. & P. 1/-
COPPER LAMINATE BOARD (8 1/2 x 5 1/2 x 1/4 in). 2/8 each. 5 for 10/-
RE-SETTABLE HIGH SPEED COUNTER (3 x 1 x 1 in). 3 digit. 12/24/48V. (state which) 98/8 each.

BULK COMPONENT OFFERS

- 100 Capacitors 50pF to 5µF.
- 250 Carbon Resistors 1/4 & 1W. (Transistor types).
- 250 Carbon Resistors 1/4 & 1W.
- 100 Ceramic Capacitors 2-1000pF.
- 20 Vitreous W/W Resistors (5%).
- 12 Precision Resistors (1% several standard values included).
- 25 Close Tolerance Caps. (2%).
- 12 Silicon Diodes 500 p.i.v. 750 m.a.
- 4 Silicon Rects. 400 p.i.v. 3 amp.
- 8 Silicon Rects. 100 p.i.v. 3 amp.
- 50 Silicon Trans. (2N700/708, BSY28/29, BCY41/42 types.) Unmarked, Untested.
- 50 Silicon Diodes 200 m.a. 100 p.i.v. Sub. Min.
- 50 Silicon Diodes 200 m.a. 100 p.i.v. Sub. Min.

ANY ITEM 10/-, ANY 5 ITEMS £2.

S.C.R.s. (Thyristors) CRS1/30 5/8; CRS1/40 7/8; CRS3/10 7/8; CRS3/30 8/6;
CR89/40 10/-; CRS3/50 12/8 each.
3000 TYPE RELAYS (ex. new equip.) 10 for 25/- (our choice) p.p. 5/-.

PATRICK & KINNIE, 81 Park Lane, Romford, Essex
ROMford 44473



**PEAK-
SOUND
8 + 8W.**

TRANSISTOR STEREO AMPLIFIER IN KIT FORM

Build this for \$9.10.0 (4/8 post). Power Pack Kit \$2.10.0 (4/- post). Cabinet (see illustration) 50/- post paid or £14.10.0 the three items post paid. Parts List Booklet and full details 1/6 (free with kit). A.E.I. Circuit of 14 Transistors; 8W per Channel into 8 to 16 ohm Speaker. 50mV input. Ceramic, Crystal Cartridge, Radio Tuner or Output from Tape Recorder may be used. 20 to 20,000 Hz ± 3dB. Neg. Feed Back 15dB, 12m. x 8in. high x 8in. Cabinet. Gtr-Kit Board Construction, Bass, Treble and Vol. Control, for A.C. mains of 200-250V. Base Cut and Lift; Treble Cut and Lift. Fully built \$3 extra. Delivery by return of post.

GLADSTONE RADIO

**66 ELMS ROAD
ALDRSHOT, HANTS.**

(2 mins. from Station and Buses.)

Aldershot 22240

CLOSED WEDNESDAY AFTERNOON

CATALOGUE 6d.

BAKER MAJOR £8



The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 40 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker magnet assembly Alcomax II having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, or Module version as illustrated with tweeter, crossover and baffle. £10.19.6.

48 page Enclosure
Manual 5/9 Post Paid.

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665

YUKAN SELF-SPRAY SO PROFESSIONAL THE
YUKAN AEROSOL WAY—
Get these air drying **GREY HAMMER**
NOW! OR **(CRACKLE)** finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality, durable easy Instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 at our counter or 15/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.
SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 16/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Other Yukan Air Drying Aerosols. 16 ozs. or 12 1/2 oz. cans. paid include:
Zinc Chromate Clear Lacquer
Metallics: Grey, Blue, Bronze and Gold.

Please enclose cheque or crossed P.O. for total amount to:

YUKAN, DEPT. PE/E 307a, EDGWARE ROAD, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons.



VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

ELECTRONIC ENG.

Advanced Electronic Eng.—
Gen. Electronic Eng.—
Applied Electronics—
Practical Electronics—
Radar Tech.—
Frequency Modulation—
Transistors.

ELECTRICAL ENG.

Advanced Electrical Eng.—
General Electrical Eng.—
Installations—
Draughtsmanship—
Illuminating Eng.—
Refrigeration—
Elem. Elec. Science—
Elec. Supply—
Mining Elec. Eng.

CIVIL ENG.

Advanced Civil Eng.—
General Civil Eng.—
Municipal Eng.—
Structural Eng.—
Sanitary Eng.—
Road Eng.—
Hydraulics—
Mining—
Water Supply—
Petrol Tech.

RADIO & T.V. ENG.

Advanced Radio—
General Radio—
Radio & TV Servicing—
TV Engineering—
Telecommunications—
Sound Recording—
Automation—
Practical Radio—
Radio Amateurs' Examination.

MECHANICAL ENG.

Advanced Mechanical Eng.—
Gen. Mech. Eng.—
Maintenance Eng.—
Diesel Eng.—
Press Tool Design—
Sheet Metal Work—
Welding—
Eng. Pattern Making—
Inspection—
Draughtsmanship—
Metallurgy—
Production Eng.

AUTOMOBILE ENG.

Advanced Automobile Eng.—
General Auto. Eng.—
Auto. Maintenance—
Repair—
Auto. Diesel Maintenance—
Auto. Electrical Equipment—
Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? A.M.I.E.R.E., B.Sc.(Eng.), A.M.S.E., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Ex., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Electronics, Radio, T.V., Etc., A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Electronics Electronics Engineering Practical Radio Radio & Television Servicing Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES"—send for your copy now—FREE and without obligation.



POST COUPON NOW!

TO B.I.E.T., 316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

3d. stamp if posted in an unsealed envelope.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE


THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Published about the 15th of the month by GEORGE NEWNES LIMITED, Tower House, Southampton Street, London, W.C.2, at the recommended maximum price shown on the cover. Printed in England by THE CHAPEL RIVER PRESS, Andover, Hants. Sole Agents—Australia and New Zealand: GORDON & GOTCH (A/sia) Ltd.; South Africa and Rhodesia: CENTRAL NEWS AGENCY LTD.; East Africa: STATIONERY & OFFICE SUPPLIES LTD. Subscription rate including postage for one year: To any part of the World £1 16s. 0d.

NEW! SOLID STATE HIGH FIDELITY EQUIPMENT BRITISH MADE

POWER AMPLIFIERS—PRE-AMPLIFIERS—POWER SUPPLIES

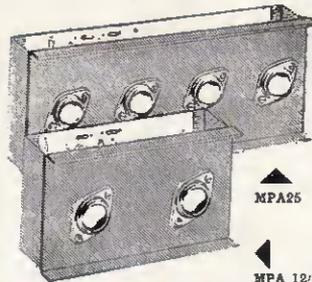We proudly present this new range of Audio Equipment developed from Dinadale Mk. II—each unit or system will compare favourably with other professional equipment selling at much higher prices. Brief details are below:—



System	Comprising	Price
A	5 watt mono for 8/5 ohm speakers	£10.3.0
1	19 watt mono for 8 to 5 ohm speakers	£13.17.6
2	12 watt mono for 12 to 16 ohm speakers	£14.12.6
4	24 watt mono two channel for 12 to 16 ohm speakers	£20.15.0
8	20 watt mono/stereo for 12 to 16 ohm speakers	£24.0.0
9	24 watt mono/stereo for 8 to 5 ohm speakers	£26.15.0
14	40 watt mono/stereo for 7 1/2 to 16 ohm speakers	£29.10.0

COMPLETE FULLY ILLUSTRATED BROCHURE FREE ON REQUEST 11 and 21

MPA 12/15

MANY OTHER SYSTEMS AVAILABLE Send for full details

THE FINEST VALUE IN HIGH FIDELITY — CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS



VHF FM TUNER
87/105 Mc/s Transistor Superhet. General tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3 1/2 x 2 1/2 in. Complete with dial plate. 5 Mullard Transistors, Plus 4 Diodes. Ask for Brochure 3
TOTAL COST TO BUILD £6.19.6 P.P. 2/6



Build the PRACTICAL ELECTRONICS FLUORESCENT CAMPING LIGHT AS DESCRIBED IN MARCH, 1968 Edition Total Cost including Construction Data Less Metalwork **59/6** POST and Tube **2/6**
All items available separately
ASK FOR PARTS LIST No. 43



FM STEREO DECODER Brochure 4
7 Mullard Transistors. Printed Circuit Design with Stereo Indicator. For use with any valve or transistor FM. Uses pot cores to Mullard design and ger. and silicon transistors. As used by B.B.C. and G.P.O. Complete Kit Price **£5.19.6 P.P. 2/6**

TRANSISTOR CAR RADIO
Send for Brochure 15



British Made 0-Transistor MW/LW. 12 volt 3 watt output. Push-button wave-change. Supplied built, boxed, ready to use with Speaker and Baffle. Car fixing kit and manufacturer's current guarantee. Special Bargain Offer. Positive or Negative Earth. 5 Push-button de-luxe version. **£9.19.6** P.P. 4/6
£11.19.6 + or — Earth


BUILD A QUALITY TAPE RECORDER with MARTIN RECORDAKITS
363 DECKS



★ TWO-TRACK. Deck £10.10.0. Amplifier. £14.10.6. Cabinet and speaker 7ms. Complete kits with microphone 7in. 1,200ft. tape, spare spool.
Today's Value **£45. 29 gns.** P.P. 18/6

★ FOUR-TRACK. Deck £13.10.0. Amplifier £15.19.8. Cabinet and speaker 7 ms. Complete kits with microphone 7in. 1,200ft. tape, spare spool.
Today's Value **£50. 32 gns.** P.P. 18/6

Ask for Brochure 6

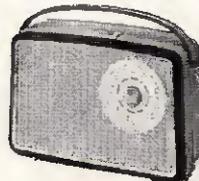

7-TRANSISTOR MW/LW SUPERHET PORTABLE NEW!
New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 Transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local, and continental stations. Size 10 x 7 x 3 1/2 in.
TOTAL COST TO BUILD £6.19.6 P.P. 4/6
Send for Brochure 1



MW/LW QUALITY TRANSISTOR RADIO TUNER
Fully tunable superhet with excellent sensitivity and selectivity. Output up to 1 volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder.
TOTAL COST TO BUILD £3.19.6 P.P. 2/6

Ask for Brochure 5



NEW MODELS NOMBREX TRANSISTORISED Test Equipment

BUILD THE PRACTICAL WIRELESS I.C. F.M. TUNER
AS PER DECEMBER, 1967 ISSUE
TOTAL COST 99/6 POST 2/6
Including R.C.A. CA3104 Circuit and Layout Diagrams. Parts List No. 40A
BUILD THE PRACTICAL WIRELESS SWITCHED F.M. TUNER
AS PER AUGUST, 1967 ISSUE
TOTAL COST 77/6 POST 2/6 Parts List No. 39
With Circuit and Layout Diagrams.
PRACTICAL ELECTRONICS GLISSANDOVIBE
85/- POST 2/6
AS PER FEBRUARY, 1968 EDITION Parts List No. 42

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1968 LIST OF 1000 types available from stock. Send for your FREE COPY TODAY. (List No. 36)
★ S.G.B.'s from 5/-
★ FIELD EFFECT TRANSISTORS from 9/6
★ POWER TRANSISTORS from 5/-
★ DIODES AND RECTIFIERS from 2/-
24 page Illustrated Brochure as above including Valves and Quartz Crystals. 1/- post paid.

GARRARD DECKS

all the LATEST MODELS

COMPLETE RANGE IN STOCK
FROM **£5.19.6**
Send for illustrated Brochure 18 & 17

MAYFAIR PORTABLE



ELECTRONIC ORGAN Ask for brochure 9
Also READY BUILT AND TESTED 128 gns. Deferred terms available.
DEPOSIT £36.8.0 and 12 monthly payments of £9. Total £144.8.0.
KIT OF PARTS Defered terms:— DEPOSIT £23.19.0 12 monthly payments of £7. TOTAL COST £113.19.0.
ORGAN COMPONENTS
We carry a comprehensive stock of organ components for TRANSISTOR AND VALVE FREE PHASE designs. Brochure 10

TOTAL COST TO BUILD 99 GNS.

- ★ Build this instrument stage by stage in your own home.
- ★ A truly portable instrument for all enthusiasts.
- ★ Fully TRANSISTORISED POLYPHONIC. British design.
- ★ Call in for a DEMONSTRATION and see for yourself.

EXPORT PRICES ON APPLICATION

MODEL	PRICE	leaflet No.
22	Power Supply	£14.0.0 22
30	Audio Generator	£19.10.0 24
31	R.F. Generator	£12.10.0 25
32	C.R. Bridge	£10.10.0 26
33	Inductance bridge	£20.0.0 29
27	Signal Generator	£10.10.0 14
66	Inductance bridge	£18.0.0 14

Send for descriptive illustrated Brochure. All units POST PAID including Battery.

CATALOGUE

- ★ 25 pages of transistors and semiconductor devices, valves and crystals.
- ★ 150 pages of components and equipment.
- ★ 50 pages of microphones, decks and Hi-fi equipment.

The most comprehensive—Concise—Clear components Catalogue in Gt. Britain. Complete with 10/- worth Discount Vouchers Free with every copy.

Send today 8/6 Post paid

LATEST EDITION
240 pages, 6,000 items
1,000 illustrations



HENRY'S RADIO LTD.



303 EDGWARE ROAD LONDON, W.2
PHONE: 01-723 1068/9
Open Mon. to Sat. 9 a.m.-6 p.m. Thurs. 9 a.m.-1 p.m.

WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION.

Full details on advertised products FREE on request