

PRACTICAL

SEPTEMBER 1985 · £1.00


ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING

New Series...
**Experimenting
with Robots**

**Alarm Systems
D.I.Y. Buyer's Guide**

Car Boot Alarm

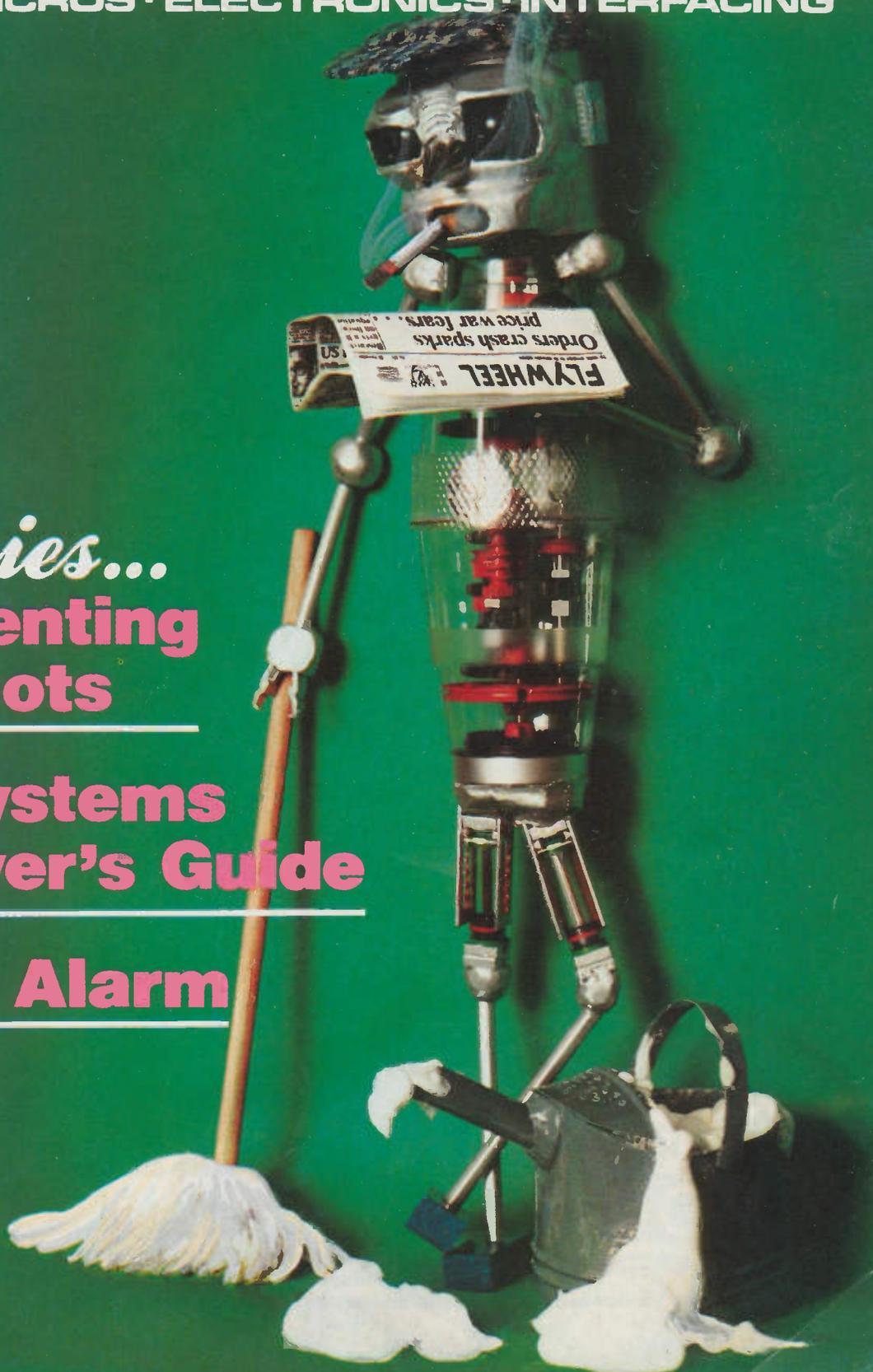



Industrial Soldering Equipment-for the discerning amateur

SEND FOR NEW CONCISE LEAFLETS




101 ELECTRONIC CONTROLLED SOLDERING STATION

for precision soldering
with accuracy suitable
for use on MOS, FET etc
240V input - 24V on tool.
Temperature range
120-420°C
Many extra features

'K' SERIES SOLDERING TOOLS FOR ALL APPLICATIONS

K1000 micro soldering
K2000 general electronic
soldering
K3000 heavy duty soldering

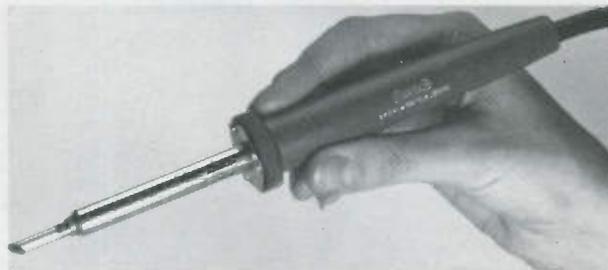
● Small selection of
**AD-IRON® LONG LIFE
SOLDERING TIPS**
suitable for all Adcola
soldering irons.



ADCOLA ACCESSORIES include: SIDE CUTTERS



SNIP NOSE PLIERS

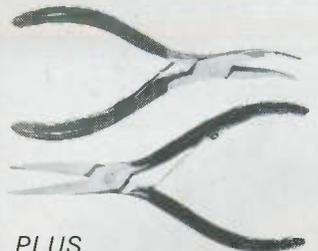

PLUS

- Desoldering Braid
- Desoldering Guns
- Tip cleaners
- Soldering aids
- Lamps, Lenses etc

ADCOLA
Regd Trade Mark
ELECTRONIC PRODUCTION EQUIPMENT

For a no obligation demonstration, please contact:
ADCOLA PRODUCTS LIMITED Gauden Road London SW4 6LH
Telephone Sales (01) 622 0291 Telex 21851 Adcola G

CONSTRUCTIONAL PROJECTS


EXPERIMENTING WITH ROBOTS by Mike Abbott Part One: Simple interface, plus a Latin-American dance?	10
CAR BOOT ALARM by D. Stone Protect the contents of your car boot with this simple circuit	22
RS232 TO CENTRONICS CONVERTER by Tom Gaskell BA (Hons) CEng MIEE Serial to parallel interface suitable for many peripherals	46
DIGITAL DELAY & SOUND SAMPLER WITH COMPUTER INTERFACE by John M. H. Becker Part Four: Final part—interwiring diagram and software	50

GENERAL FEATURES


ROBOTICS REVIEW by Nigel Clark A regular look at robotics and cybernetics	19
PLOTTER REVIEW by D. Whitfield MA MSc CEng MIEE A "natural" pantographic drawing aid for the BBC-B Micro	20
ALARM SYSTEMS—DIY BUYER'S GUIDE by Brian Butler An in-depth look at current trends and equipment/kits	25
SPACEWATCH by Dr Patrick Moore OBE	34
BBC MICRO FORUM by D. Whitfield MA MSc CEng MIEE Thermometer software	36
SERPENT REVIEW by Dick Becker & Roger Gay A close look at construction and control of SCARA's	39
SEMICONDUCTOR CIRCUITS by Tom Gaskell BA(Hons) CEng MIEE Baud Rate Generator (4702B)	44

NEWS & COMMENT

EDITORIAL	7	LEADING EDGE	16	READOUT	52
NEWS & MARKET PLACE	8	INDUSTRY NOTEBOOK	18	P.C.B. SERVICE	53
		BAZAAR	35		

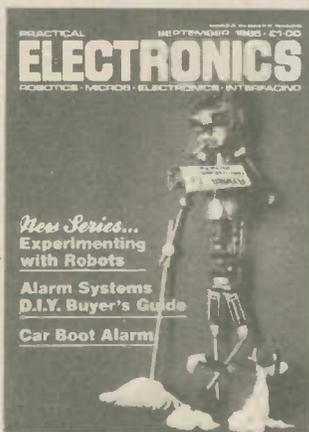

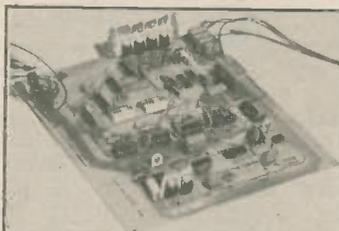This month's front cover picture shows a 21st Century working class robot checking the racing results. His gears and hydraulics were supplied courtesy of Fischer Technik.



ALARM SYSTEMS



D.I.Y. BUYER'S GUIDE

See Page 25

OUR OCTOBER ISSUE WILL BE ON SALE FRIDAY, SEPTEMBER 6th, 1985 (see page 4)

© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

250, HIGH ST., WATFORD, HERTS WD1 2AN, ENGLAND
 Tel. Watford (0923) 40588. Telex: 8956095 WAELE
 ORDERS NORMALLY DESPATCHED BY RETURN OF POST

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. SEND CASH, P.O.'s OR CHEQUE WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (ACCESS ORDERS BY TELEPHONE 0923-50234). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD £1 TO ALL CASH ORDERS. OVERSEAS POSTAGE AT COST. PRICES SUBJECT TO CHANGE.

VAT Export orders no VAT. U.K. customers please add 15% VAT to total cost incl. p&p. We stock thousands more items. It pays to visit us. Nearest underground/British Rail Station: Watford High Street. Open Monday to Saturday, 9.00am to 6.00pm. Ample FREE Car parking.

POLYESTER RADIAL LEAD CAPACITORS: 250V; 10n, 20n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 8p; 150n, 220n 10p; 330n, 470n 15p; 680n 19p; 1µ 23p; 1µ5 40p; 2µ 46p.

ELECTROLYTIC CAPACITORS (Values in µF): 500V: 10µ 52p; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3 8p; 4.7 9p; 10 10p; 15 12p; 22 13p; 33 15p; 47 12p; 68 16p; 100 19p; 220 26p; 1000 70p; 2200 99p; 50V: 68 20p; 100 17p; 220 24p; 40V: 6.8 15p; 22 3p; 33 2p; 100 42p; 1000 48p; 2200 90p; 25V: 4.7, 10, 22, 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470 31p; 680 34p; 1000 34p; 2200 50p; 3300 76p; 4700 92p; 16V: 2.5, 4.0 8p; 47, 68, 100 9p; 125 12p; 220 13p; 330 16p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 4700 79p.

TAG-END TYPE: 64V: 4700 245p; 3300 145p; 2200 120p; 50V: 3300 155p; 2200 95p; 40V: 4700 160p; 2200 70p; 3300 85p; 4000, 4700 95p; 10,000 250p; 15,000 270p; 16V: 2200 200p; 25V: 4700 95p; 10,000 320p; 15,000 345p.

TANTALUM BEAD CAPACITORS: 35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 16V: 2.2, 3.3, 16p; 4.7, 6.8, 10 18p; 15 36p; 22 36p; 33, 47 10p; 95p; 220 100p; 1000 140p; 10k, 15k 26p; 33, 47 50p; 100 75p.

SILVER MICA (pf)
 2, 3, 3.4, 6.8, 8, 10, 12, 18, 22, 27, 33, 39, 45, 56, 68, 75, 82, 85, 120, 150, 180, 190, 220, 250, 270, 330, 360, 390, 470, 600, 800 & 2200p
 1000, 1200, 1800 30p each
 3300, 4700 60p each

SIEMENS multilayer miniature capacitors:
 250V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 8n2, 10n, 15n, 22n 7p; 18n, 27n, 33n, 47n 8p; 33n, 56n, 68n 9p
 100V: 100n, 120n, 10p; 150n 11p; 220n 13p; 330n 18p; 470n 23p; 680n 30p; 1Mf 34p; 2Mf 50p.

CERAMIC CAPACITORS: 50V Range 1nF to 6800pF 49p; 10nF, 15n, 33n, 47n 5p; 100nF/30V 7p.

POLYSTYRENE CAPS: 10pF to 1nF 8p; 1n5 to 12nF 10p

RESISTORS S.I.L. Package: 7 Commedon, 100Ω, 470Ω, 680Ω, 1K, 2K2, 4K7, 10K, 47K, 100K 24p; 8 Commedon: (9 pins) 150Ω, 180Ω, 270Ω, 330Ω, 330Ω, 1K, 2K, 4K7, 6K8, 10K, 22K, 47K, 100K 26p.

LINEAR IC's

555 CMOS	80	LM337	210	TAA661	190	74S00	100	74S00	100
702	75	LM379	495	TAA670	275	74S01	100	74S01	100
709C 8 pin	35	LM380	120	TAD100	155	74S02	100	74S02	100
710	50	LM381N	175	TBA120S	70	74S03	100	74S03	100
747C 4 pin	10	LM382	190	TBA450	275	74S04	100	74S04	100
748C 8 pin	10	LM383	225	TBA550Q	330	74S05	100	74S05	100
753 8 pin	185	LM386	200	TBA641	290	74S06	100	74S06	100
810	160	LM389	160	TBA641S	390	74S07	100	74S07	100
9400C	375	LM393	85	TBA920Q	200	74S08	100	74S08	100
ADC0808	110	LM394CH	380	TBA990	350	74S09	100	74S09	100
AY-1-1320	225	LM558	170	TC4270	350	74S10	100	74S10	100
AY-1-5050	95	LM725CEN	300	TC4280A	220	74S11	100	74S11	100
AY-1-5720	210	LM733	65	TC4284-250	220	74S12	100	74S12	100
AY-3-8910	390	LM1871	300	TC9A50	100	74S13	100	74S13	100
AY-3-8912	450	LM1889	400	TC9A50	100	74S14	100	74S14	100
AY-5-1317A	630	LM2907	395	TCDA1008	180	74S15	100	74S15	100
CA3011	130	LM3900	70	TCDA1010	220	74S16	100	74S16	100
CA3012	170	LM3902	155	TCDA1022	400	74S17	100	74S17	100
CA3014	275	LM3911	185	TCDA1024	110	74S18	100	74S18	100
CA3018	86	LM3914	300	TCDA1034	350	74S19	100	74S19	100
CA3019	90	LM3915	345	TCDA1054	400	74S20	100	74S20	100
CA3020	210	LM3916	300	TCDA1490	350	74S21	100	74S21	100
CA3023	210	LM3960	150	TCDA2002	325	74S22	100	74S22	100
CA3029A	170	LM3962	270	TCDA2003	325	74S23	100	74S23	100
CA3035	255	LM5151L3	230	TCDA2006	320	74S24	100	74S24	100
CA3036	275	LM5151L3	230	TCDA2020	320	74S25	100	74S25	100
CA3043	275	LM5151L6	475	TCDA2030	100	74S26	100	74S26	100
CA3045	365	MB3712	200	TDB079T	420	74S27	100	74S27	100
CA3046	70	MB3756	440	TD161CF	400	74S28	100	74S28	100
CA3059	60	MC1204	225	TD161CF	400	74S29	100	74S29	100
CA3075	215	MC1301	90	TD1624-15	675	74S30	100	74S30	100
CA3080E	70	MC1310P	150	TD1701CF	400	74S31	100	74S31	100
CA3081	190	MC1445	250	TD1702CF	400	74S32	100	74S32	100
CA3085	160	MC1458	35	TD1704CN	110	74S33	100	74S33	100
CA3086	90	MC1469	300	TD181CF	550	74S34	100	74S34	100
CA3090A	375	MC1498	385	TD282C CPU	35	74S35	100	74S35	100
CA3123	165	MC1495	300	TD502A	55	74S36	100	74S36	100
CA3130	90	MC1496L	70	TD502A	55	74S37	100	74S37	100
CA3140	45	MC1596	225	TD502A	55	74S38	100	74S38	100
CA3160	90	MC3302	75	TD502A	55	74S39	100	74S39	100
CA3161E	180	MC3401	50	TD502A	55	74S40	100	74S40	100
CA3162	110	MC3403	65	TL507	110	74S41	100	74S41	100
CA3189	270	MC3404	85	TL509	110	74S42	100	74S42	100
CA3240	110	MC3405	150	UA2240	120	74S43	100	74S43	100
HA1366	175	MC3423P	80	UA7854D	225	74S44	100	74S44	100
HA1388	235	MC4016	100	UA7854D	225	74S45	100	74S45	100
ICL7106	675	MF1	100	UA7854D	225	74S46	100	74S46	100
ICL7107	975	MF68040	75	UA7854D	225	74S47	100	74S47	100
ICL7161	95	ML294	275	UA7854D	225	74S48	100	74S48	100
ICL7660	255	NE515	275	UA7854D	225	74S49	100	74S49	100
ICL8038CC	300	NE529	225	UA7854D	225	74S50	100	74S50	100
ICL8211	225	NE531	120	UPC956	90	74S51	100	74S51	100
ICM7217A	110	NE532	120	UPC956	90	74S52	100	74S52	100
ICM7220	110	NE533	120	UPC956	90	74S53	100	74S53	100
ICM7240	300	NE534	190	UPC1025H	375	74S54	100	74S54	100
ICM7555	300	NE555	200	UPC1156H	295	74S55	100	74S55	100
ICM7556	140	NE556	170	UPC1181	60	74S56	100	74S56	100
LA3350	250	NE560	350	UPC1182	425	74S57	100	74S57	100
LA4031P	340	NE561	440	UPC1366	195	74S58	100	74S58	100
LA4032	295	NE562	440	XR2202	375	74S59	100	74S59	100
LA4400	350	NE566	140	XR2207	400	74S60	100	74S60	100
LA4422	320	NE567	150	XR2211	575	74S61	100	74S61	100
LC7120	300	NE570	400	XR2216	675	74S62	100	74S62	100
LC7130	320	NE571	400	XR2266	360	74S63	100	74S63	100
LC7137	350	NE572	400	ZN414	680	74S64	100	74S64	100
LF347	120	NE583	150	ZN425E-8	345	74S65	100	74S65	100
LF351	60	OM335	650	ZN425E-8	345	74S66	100	74S66	100
LF353	90	RC1436D	55	ZN425E-8	345	74S67	100	74S67	100
LF355	90	RC4558	55	ZN425E-8	345	74S68	100	74S68	100
LF356	90	SAB3209	425	ZN425E-8	345	74S69	100	74S69	100
LF357	100	SAB3271	485	ZN425E-8	345	74S70	100	74S70	100
LF358	495	SAB4209	295	ZN459	245	74S71	100	74S71	100
LM10	325	SG3402	295	ZN0104E	605	74S72	100	74S72	100
LM301A	30	SL490	300	ZN0104E	605	74S73	100	74S73	100
LM307	45	SL924	100	ZN2A34E	925	74S74	100	74S74	100
LM308	75	SL6270	150			74S75	100	74S75	100
LM311	100	SN7603	350			74S76	100	74S76	100
LM318	150	SN76488	525			74S77	100	74S77	100
LM319	180	SN76489	400			74S78	100	74S78	100
LM324	45	SP0256AL	425			74S79	100	74S79	100
LM3342	110	TA7120	120			74S80	100	74S80	100
LM3352	130	TA7130	125			74S81	100	74S81	100
LM337	150	TA7134	150			74S82	100	74S82	100
LM339	40	TA7205	90			74S83	100	74S83	100
LM348	60	TA7220	120			74S84	100	74S84	100
LM349	125	TA7310	120			74S85	100	74S85	100
LM358	50	TA9A00	395			74S86	100	74S86	100

TRANSISTORS

AC127/8	35	BC308B	16	BFR981	105	TIP30C	37	2N914/5	32	2N5458/9	30
AC141/2	35	BC327B	15	BFX28/84	35	TIP31A	38	2N918	40	2N5485	36
AC176	35	BC167	15	BFX84	35	TIP31C	45	2N930	20	2N5777	45
AC187/8	35	BC441	34	BFY50/51	30	TIP32A	43	2N1131/2	40	2N6027	32
AC188	35	BC461	34	BFY50/51	30	TIP32C	45	2N1303/4/5	20		

SPEAKERS 8Ω, 0-3W, 2", 2-25", 2.5", 3" 0-3W, 2.5", 40Ω, 64Ω or 80Ω	OPTO LEDS price includes Clips TIL209 Red 3mm 10 TIL211 Green 3mm 14 TIL212 Yellow 14 TIL220 2" Red 12 0-2" Yel, Grn, Amber Rectangular LEDs with two part clip, R, G & Y 45 LEDS 18 Triangular LEDs R&G 18 0-2" Flashing LED Red 56 0-2" Bi colour LEDs 12 Red/Green 100 Green/Yellow 80 0-2" Tri colour LEDs 50 Red/Green/Yellow 85 0-2" Red High Bright 59 High Bright Green or 3" Green C.A. 100 LD271 Infra Red (emit) 46 TIL32 Infra Red (emit) 118 SFH205 (detector) 52 TIL78 (detector) 55 TIL38 50 TIL81 82; TIL100 90	0-5" LCD DISPLAYS 3 1/2 digit 495 4 digit 530 6 digit 625	VOLTAGE REGULATORS 1A T0220 Plastic Casing 5V +ve 7805 45p 7905 55p 12V 7812 45p 7912 55p 15V 7815 45p 7915 55p 18V 7818 45p 7918 55p 24V 7824 45p 7918 55p 100mA T092 Plastic Casing 5V 78L05 30p 79L05 50p 6V 78L06 30p 8V 78L08 30p 12V 78L12 30p 79L12 50p 15V 78L15 30p 79L15 50p	DIL SOCKETS Low profile wrap 8p 25p 14 pin 10p 35p 16 pin 10p 42p 18 pin 16p 52p 20 pin 20p 60p 22 pin 22p 65p 24 pin 25p 70p 28 pin 28p 80p 40 pin 30p 99p	
DIODES AA119 8 AA129 10 AA330 8 BA100 10 BY100 15 BY126 12 BY127 10 CRO33 198 OA30 10 OA47 10 OA70 9 OA79 10 OA81 10 OA85 10 OA90 8 OA91 8 OA95 8 OA200 8 OA202 8 IN914 4 IN916 5 IN4001/2 5 IN4003 6 IN4004/5 6 IN4006/7 7 IN4148 4 IN5401 12 IN5404 14 IN5406 15 IN5408 19 IS44 9 IS921 9 6A100V 40 6A400V 50 6A800V 65	BRIDGE RECTIFIERS (plastic case) 1A/50V 18 1A/100V 20 1A/200V 25 1A/400V 30 1A/600V 36 2A/50V 20 2A/200V 40 2A/400V 42 2A/600V 50 6A/100V 83 6A/400V 95 6A/600V 125 10A/200V 215 10A/400V 238 25A/200V 240 25A/400V 290 BY164 56	OPTO SWITCH Reflective TIL11 225 Slotted similar to RS 186	ICL7660 *248 LM317K 250 78H05 5V/5A 550 LM317 375 78H12 12V/5A 640 LM323K 500 78HG+5 to LM337T 175 +24V 5A 695 LM723 30 Yellow -2.25V to TBA6258 75 LM309 785 RC4194 375 LM309K 120 RC4195 165 TL497 185 78S40 225	DIL PLUGS (Headers) Pins Solder IDC 14 40p 95p 16 45p 100p 24 85p 135p 28 150p 200p 40 200p 225p	
ZENERS Range: 2V7 to 3V9 400mW 6 8p each 8 Range: 3V3 to 33V 1.3W 12 15p each 14 15408 19 1544 9 BA101 30 BB105B 40 BB106 40	VARICAPS BA101 30 BB105B 40 BB106 40	ALUM. BOXES 4x2 1/2x2 100 4x2 3/4x2 120 4x4x2 1/2 103 5x4x2 1/2 105 5x2 3/4x1 1/2 90 5x2 3/4x2 1/2 130 5x4x1 1/2 99 5x4x2 1/2 120 6x4x2 120 6x4x3 150 7x5x3 180 8x6x3 210 10x4 1/4x3 240 10x7x3 275 12x5x3 260 12x8x3 295	SLIDE 250V 1A DPDT 14 1A DPDT ON/OFF 15 1/2A DP ON/OFF 40	TOGGLE 2A 250V 14 SPST 35 14 DPDT 48 4 pole on off 54	DIL SOCKETS Pins Solder IDC 14 40p 95p 16 45p 100p 24 85p 135p 28 150p 200p 40 200p 225p
TRIACS 3A/100V 48 3A/400V 56 3A/800V 65 8A/100V 60 8A/400V 69 8A/800V 115 8A/300V 60 12A/100V 78 12A/400V 82 12A/800V 135 16A/100V 103 16A/400V 105 16A/800V 220 18A/100V 188 18A/400V 180 BT116 180 C106D 38 TIC44 24 TIC45 29 TIC47 35 T28054 38 2N4444 130	FERRIC CHLORIDE Crystals 1lb 275 195p + 50p p&p	ROTARY: (Adjustable Stop Type) 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 48p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p
DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way

DIODES AA119 8 AA129 10 AA330 8 BA100 10 BY100 15 BY126 12 BY127 10 CRO33 198 OA30 10 OA47 10 OA70 9 OA79 10 OA81 10 OA85 10 OA90 8 OA91 8 OA95 8 OA200 8 OA202 8 IN914 4 IN916 5 IN4001/2 5 IN4003 6 IN4004/5 6 IN4006/7 7 IN4148 4 IN5401 12 IN5404 14 IN5406 15 IN5408 19 IS44 9 IS921 9 6A100V 40 6A400V 50 6A800V 65	BRIDGE RECTIFIERS (plastic case) 1A/50V 18 1A/100V 20 1A/200V 25 1A/400V 30 1A/600V 36 2A/50V 20 2A/200V 40 2A/400V 42 2A/600V 50 6A/100V 83 6A/400V 95 6A/600V 125 10A/200V 215 10A/400V 238 25A/200V 240 25A/400V 290 BY164 56	OPTO SWITCH Reflective TIL11 225 Slotted similar to RS 186	ALUM. BOXES 4x2 1/2x2 100 4x2 3/4x2 120 4x4x2 1/2 103 5x4x2 1/2 105 5x2 3/4x1 1/2 90 5x2 3/4x2 1/2 130 5x4x1 1/2 99 5x4x2 1/2 120 6x4x2 120 6x4x3 150 7x5x3 180 8x6x3 210 10x4 1/4x3 240 10x7x3 275 12x5x3 260 12x8x3 295	SLIDE 250V 1A DPDT 14 1A DPDT ON/OFF 15 1/2A DP ON/OFF 40	TOGGLE 2A 250V 14 SPST 35 14 DPDT 48 4 pole on off 54	DIL PLUGS (Headers) Pins Solder IDC 14 40p 95p 16 45p 100p 24 85p 135p 28 150p 200p 40 200p 225p	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p
TRIACS 3A/100V 48 3A/400V 56 3A/800V 65 8A/100V 60 8A/400V 69 8A/800V 115 12A/100V 78 12A/400V 82 12A/800V 135 16A/100V 103 16A/400V 105 16A/800V 220 18A/100V 188 18A/400V 180 BT116 180 C106D 38 TIC44 24 TIC45 29 TIC47 35 T28054 38 2N4444 130	FERRIC CHLORIDE Crystals 1lb 275 195p + 50p p&p	ROTARY: (Adjustable Stop Type) 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 48p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p
DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p

DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p
DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p
DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p

DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p
DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p
DIAC ST2 25	VEROBORD 2 1/2x3 1/4 Clad Plain VQ Board 180p 2 1/2x5 1/4 DIP Board 395p 3 3/4x3 1/4 Vero strip 95p 3 3/4x5 1/2 95p 3 3/4x17 1/2 420p 275p 4 3/4x18 590p Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p	ASTEC UHF MODULATORS 6MHz Standard 375p 8MHz Wideband 550p	MINIATURE Non Locking Push to make 15p Push break 25p	PUSH BUTTON Spring loaded Latching or Momentary 6A SPDT cover 150 DPDT cover 200	SUB-MIN TOGGLE 2 amp SP changeover 64 SPST on off 58 SPDT off 150 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 88 DPDT on/off on 185 15p DPDT Biased 145 Push break 25p 4-pole 2 way 220	'D' CONNECTORS: Pins 9 15 25 37 way way way way	RIBBON CABLE (price per foot) Ways Grey Colour 10 15p 25p 16 20p 30p 20 25p 40p 26 40p 65p 34 50p 80p 40 60p 90p 64 90p 125p

SPECTRUM 32K UPGRADE

Upgrade your 16K Spectrum to full 48K with our RAM Upgrade Kit. Very simple to fit. Fitting instructions supplied. **ONLY £22**

2 rows	PCB Male with latch Strt.	Female Header Angle Pins	Female Card-Edge Connector
10 way	90p	85p	120p
16 way	130p	100p	195p
20 way	145p	166p	240p
26 way	175p	200p	320p
34 way	200p	236p	340p
40 way	220p	250p	350p
50 way	235p	270p	470p

SPECIAL OFFER

2764 - 250ns	1+	10+
27128 - 250ns	299	675
6116LP - 150ns	695	275
6264LP - 150ns	250	235
	725	699

TRANSFORMERS	3-0-3V, 6-0-6V, 9-0-9V, 12-0-12V, 15-0-15V or 100MA 130p
PCB mounting, miniature, Split bobbin	
3VA 2x6V /0.25A, 2x9V /0.15A, 2x12V /0.12A, 2x15V /0.2A, 2x25p	
6VA 2x6V /0.25A, 2x9V /0.3A, 2x12V /0.25A, 2x15V /0.2A 200p	
Standard split Bobbin type	
8VA 2x6V /0.5A, 2x9V /0.4A, 2x12V /0.3A, 2x15V /0.25A 250p	
12VA, 2x4.5V /1A, 2x9V /0.6A, 2x12V /0.45A, 2x15V /0.4A, 2x20p	
16VA 2x6V /1A, 2x9V /0.6A, 2x12V /0.4A, 2x15V /0.45A 350p	
20VA 2x6V /1A, 2x9V /1A, 2x12V /1A, 2x15V /1A 450p	
50VA 2x6V /4A, 2x9V /2A, 2x12V /2A, 2x15V /1.5A, 2x30V /1A, 2x30V /1A, 2x30V /1A, 2x30V /1A 500p	
50VA multi-tap: +30V, +12V, +5V, -5V, -12V or 1A 650p	
100VA: 2x12V /4A, 2x15V /3A, 2x20V /2A, 2x25V /2A, 2x30V /1.5A, 2x30V /1.5A 550p (75p p&p)	
(P&p charge to be added over & above our normal postal charge)	

TURNED PIN Low Profile Professional	
DIL SOCKET	
8 pin	25p
14 pin	40p
16 pin	42p
18 pin	47p
20 pin	60p
22 pin	70p
24 pin	80p
28 pin	90p
40 pin	120p

JUMPER LEADS	
10C FEMALE RECEPTACLE Jumper Leads 36"	
1 end	180p
2 ends	280p
	300p
	340p
	400p
	525p

COMPUTER CORNER

- **EPSON RX80 Printer** **£209**
- **EPSON RX80 F/T Printer** **£219**
- **EPSON FX80 Printer** **£315**
- **EPSON FX100 Printer** **£429**
- **KAGA/TAXAN KP810 Printer** **£239**
- **KAGA/TAXAN KP910 Printer** **£339**
- **BROTHER HR15 Daisywheel Printer** **£325**
- **Centronics PRINTER CABLE** for all the above printers to interface with the BBC Micro **£7**
- **KAGA KX1201G Hi-RES, Green Monitor**. **£90**
- **ZENITH 12" Hi-RES, Green Monitor** 40/80 column select switch, value for money. **£66**
- **MICROVITEC 14"** colour monitor. RGB input. Lead incl. **£175**
- **MICROVITEC 1451 Hi-res 14" Monitor incl. Lead** **£237**
- **KAGA VII 12" Hi-RES, RGB Colour Monitor** **£255**
- **KAGA VIII 12" ULTRA Hi-RES, RGB Colour Monitor** **£310**
- **TEX EPROM ERASER**. Erases up to 32 ICs in 15-30 min. **£30**
- **Spare UV lamp bulbs** **£8**
- **8 1/2" or 9 1/2" Fan fold paper** (1000 sheets) **£7 (150p)**

MANY MORE PRINTERS, MONITORS, INTERFACES, AVAILABLE. CALL IN AT OUR SHOP FOR DEMONSTRATION OR WRITE IN FOR OUR DESCRIPTIVE LEAFLET.

BT CONNECTOR

LJU 1/4A Mini Line Master	435p
LJU 1/8A Mini Line Slave	29

all in your

OCTOBER

issue!

New Series

INTRODUCTION TO MICROPROCESSOR SYSTEMS

This major new series not only answers the question, "What is a microprocessor and how does it work?", it shows how a complete *practical* microcomputer system is put together, often making use of relatively cheap and readily-available components



BBC BYTEBOX

There is a massive amount of utility software available for the BBC which is only available as firmware (ROM or PROM). This well designed project is able to support up to 16 'side-ways' ROMs for the BBC micro as well as providing a host of other useful features.

MODULATED SYNDRUM

A complete electronic drum in a box. Just connect up to an amplifier—or even a headset, if the neighbours object—and get the full range of disco drum effects



PRACTICAL

ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING

OCTOBER ISSUE ON SALE FRIDAY, SEPTEMBER 6



MARCO TRADING



RESISTOR KITS

1/4W Pack 10 each value E12 10R-1M
Total: 610 resistors **ONLY 4.80**

1/4W Pack 5 each value E12 10R-1M
Total: 305 resistors **ONLY 2.75**

1/2W Pack 10 each value E12 2R2-2M2
Total: 730 resistors **ONLY 5.25**

1/2W Pack 5 each value E12 2R2-2M2
Total: 365 resistors **ONLY 3.50**

50v Ceramic Kit 5 each value
125 Per Kit **£3.50**

SOLDERING AIDS

Antex 15W iron **5.00**
Antex 18W iron **5.00**
Antex 25W iron **5.20**
Antex Elements **2.00**
Antex Bits **0.95**
Antex Stands **1.90**
Desolder Tool **4.50**
Spare nozzle **0.65**
25W Kit-iron with 13A plug & stand **ONLY 7.20**

NI-CAD CHARGER

Universal charger to charge PP3, AA, C, D **PRICE 6.00**

SPEAKERS

4" Round 1.6W 4 Ohm **£1.50 pair**
4" Round 1.6W 4 Ohm Plus Mounting Bracket **£1.00 each**
2 1/4" Round 0.4W 8 Ohm 85p each

NI-CADS

PP3 **£4.45**, 4/16.00
AA **£0.95**, 10/8.00
HPI **£2.30**, 4/8.50
C **£1.95**, 4/8.75

SERVICE AIDS

ALL SERVICE PRODUCTS
Switch Cleaner **0.95**
Circuit Freezer **1.14**
Foam Cleaner **0.95**
Aero Klene **0.90**
Silicone Grease (Tube) **1.64**

VOLTAGE REGULATORS

78L05/12/15 **0.30**
7505/12/15 **0.55**
7905/12/15 **0.55**
LM317K **3.50**

DC MOTOR

6-12V **75p**
5 for **£3.00**

PLUGS SOCKETS

Metal Co-ax Plug **0.18**
Plastic Co-ax Plug **0.14**
Metal Line Socket **0.50**
Single Junc **0.30**
Socket **0.15**
Plastic Phono **0.15**
F.M. Plugs **0.20**
PL259 Plugs **0.20**
Reducer **0.15**
Low loss splitter 1 in. 2 out **1.00**
40 pin **0.34** 3.10/10

IC SOCKETS

Dip to Dip **0.35**
8 pin **0.08** 0.70/10
3 x 2 1/2 x 2" **0.65**
4 x 3 x 1 1/2" **0.63**
6 x 4 x 2 1/2" **1.15**
8 1/2 x 5 x 3 1/4" **2.15**

Colour Black, all boxes with lids and screws.

HEADPHONES

Super lightweight miniature silver bands, sponge earcups (stereo) **£2.50** and mono

PERSONAL STEREO CASSETTE

Fantastic price **£9.99** plus 50p extra postage. Murphy + Omega make. Complete with headphones and carrying strap.

WALKMAN TYPE SPEAKERS

Powered Stereo Speakers complete with carrying strap. Built-in Pre-amp. Needs to be heard to be believed. Uses 2 x D size batteries - not supplied. **£8.50** each (plus additional postage £1 set)

CLOCK RADIO - VHF/LW/MW

Mains, digital display alarm clock/radio. Alarm control/Wake to music. Sleep control - 10 min. Snooze. Hour/Minute Time Setting. Brightness Control. **£8.50** each (plus additional postage 75p per set).

PLASTIC BOXES

3 x 2 x 1" **0.35**
3 x 2 1/2 x 2" **0.65**
4 x 3 x 1 1/2" **0.63**
6 x 4 x 2 1/2" **1.15**
8 1/2 x 5 x 3 1/4" **2.15**

Colour Black, all boxes with lids and screws.

LED's

RED: 3mm + 5mm 10p each, 100 for **£6.00**. YELLOW: 3mm + 5mm 13p each, 100 for **£10.00**. GREEN: 3mm + 5mm 13p each, 100 for **£10.00**. Prices include counting clips

SPECIAL OFFER

The complete set of three strip-fix plastic signs, containing over two thousand words. Transmitters, frequencies, dials, letters and symbols etc. Three for **£3.75**.

Fuseholders

20mm Panel Mounting **0.28**
20mm Chassis Mounting **0.06**
1 1/4in Panel Mounting **0.35**
1 1/4in Chassis Mounting **0.342**
Carline 1 1/4in Mounting **0.10**

FUSES

OB 20mm 100mA to 63A: 6p each, 100 for **£3.50**. Slow Blow 20mm 100mA to 800mA, 20p, 100 for **£15.00**. 20mA to 800mA, 12p, 100 for **£7.50**. 1A to 63A: 10p, 100 for **£5.00**.

TELECOM EQUIP

BT Plug & 3M lead **1.25**
BT MASTER SOCKET **2.85**
BT Sec. Sckt. **1.95**
BT 4-core cable 1M **0.15** 100M **12.00**

ROTARY POTS

0.25W Carbon Log & Lin 1K-2M2 each **0.32**
10 3.00
Any 100 28.00

SCREENED CURLY LEADS

Black - 3 core (2 metres extended) each **£8.00/10** 75p

TRANSISTORS

AC128 **0.30** BF338 **0.38**
AC176 **0.28** BFX26 **0.28**
AF239 **0.68** BFX84 **0.24**
BC107 **0.10** BFX85 **0.26**
BC108 **0.10** BFX87 **0.26**
BC109 **0.10** BFX90 **0.21**
A.B.C. **0.12** BFY52 **0.21**
BC147 **0.09** BFY90 **0.20**
BC162 **0.09** BSX20 **0.34**
BC184 **0.09** BU208 **1.55**
BC184 **0.09** BU407 **1.65**
BC184L **0.09** MJ2955 **0.90**
BC212 **0.09** OC45 **0.58**
BC212L **0.09** OC71 **0.50**
BCY70 **0.15** OC72 **0.52**
BD131/2 **0.34** TIP31A **0.44**
BD133 **0.56** TIP32A **0.42**
BD135 **0.32** TIP33C **0.88**
BD136 **0.36** TIP34A **0.72**
BF115 **0.32** TIP2955 **0.60**
BF184 **0.32** TIP3055 **0.60**
BF185 **0.32** TIS43 **0.88**
BF194 **0.08** TIS88 **0.40**
BF195 **0.10** 2N3055 **0.45**
BF196 **0.10** 2SC1096 **0.68**
BF197 **0.10** 2SC1173Y **0.82**
BF200 **0.20** 2SC1306 **0.92**
BF224 **0.20** 2SC1307 **0.40**
BF244 **0.26** 2SC1657 **0.76**
BF244A **0.28** 2SC2028 **0.73**
BF244B **0.30** 2SC2029 **2.10**
BF259 **0.32** 2SC2078 **1.05**
BF262 **0.30** 2SC2166 **1.20**
BF263 **0.30** 3SK88 **0.65**
BF337 **0.38** 40673 **0.80**

DIODES

IN916 **0.04** AA119 **0.12**
IN4001 **0.05** AA129 **0.18**
IN4004 **0.06** AAY30 **0.16**
IN4005 **0.06** BA100 **0.24**
IN4007 **0.07** BY126 **0.12**
IN4148 **0.05** BY127 **0.10**
IN4149 **0.06** BY133 **0.16**
IN5400 **0.12** BY184 **0.40**

74LS

LS00 **28p**
LS01 **28p**
LS02 **28p**
LS03 **28p**
LS04 **32p**
LS05 **28p**
LS06 **28p**
LS07 **28p**
LS08 **28p**
LS09 **28p**
LS10 **28p**
LS11 **28p**
LS12 **25p**
LS13 **33p**
LS14 **58p**
LS15 **25p**
LS20 **28p**
LS21 **28p**
LS22 **28p**
LS30 **30p**
LS32 **28p**
LS37 **23p**
LS74 **38p**
LS122 **70p**
LS138 **45p**
LS139 **68p**
LS151 **75p**
LS155 **50p**
LS157 **45p**
LS158 **58p**
LS160 **60p**
LS161 **70p**
LS162 **72p**
LS163 **80p**
LS166 **1.95**
LS170 **1.75**
LS244 **1.00**
LS245 **2.00**
LS257 **73p**
LS393 **1.15**

MARCO TRADING (DEPT PE9)

The Maltings
High Street
Wem, Shropshire SY4 5EN
Tel: 0939 32763 Telex: 35565

OR... components are brand new and to full specification. Please add 50p postage/packing (unless otherwise specified to all orders then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges, etc. most welcome. (Do not forget to send for our 1985 catalogue - only 65p per copy. All orders despatched by return of mail. NEW RETAIL 1,000 sq. ft. shop now open. Mon-Fri 9.00-5.00, Sat 9.00-12.00



NEW 1985 CATALOGUE

WILL BE AVAILABLE AUGUST/SEPTEMBER. Range of components greatly increased - over 125 pages fully illustrated. Price **£1.00** per copy. (Free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelopes.

ESR

13a Station Road
Cullercoats - North Shields
Tyne & Wear - NE30 4PQ
Telephone 091 2514363

TRANSISTORS - RESISTORS - CAPACITORS - DIODES - LED'S - SCR'S - ICS - VOLTAGE REGULATORS - DISPLAYS - AUDIO & EDGE CONNECTORS - VERO/PCB'S - INSTRUMENT CASES & BOXES - POWER AMPLIFIERS & MODULES - MICROPHONES & STANDS.

WRITE OR PHONE FOR FREE PRICE LIST.

DEN FER ELECTRONIC PRODUCTS LTD

137 MYDDLETON ROAD, LONDON N22 **01-881 8302**

8" SPEAKERS, 70W **£8.00** MINI HEAD PHONES **£2.30**
6" SPEAKERS, 50W **£5.00** SOLDER, 1 metre **25p**
TWEETERS **£1.50** FERRIC CHLORIDE **£2.25**

SPEAKER GRILL MATTIAS **£2.50**

LOUDSPEAKER KITS, CROSSOVERS, CABINETS.

ELECTRONIC COMPONENTS - IC's, TRANSISTORS
MANY MORE PARTS.

Phone or write for your free Mail Order Catalogue.
Add 80p p&p + 15% VAT
CALLERS WELCOME

SUPERB EFFECTS



MONO-STEREO ECHO-REVERB (P.E. Sept. '84) 200ms echo (extendable), lengthy reverb, multitacking. Kit as published. Set 218BK **£55.66**
ENHANCED PHASER (P.E. Oct '84) Enhanced phasing with modulated filter shifting. Kit as published. Set 226BK **£39.13**
RING MODULATOR (P.E. NOV. '84) Fabulous effects generation. With multiwaveform VCO, noise gate & ALC. Kit as published. Set 231BK **£39.99**
MONO-STEREO CHORUS-FLANGER (P.E. Jan. '84) Superb dual mode music enhancement. Kit as published. Set 235BK **£55.66**
CYBERVOX (E.E. Apr. '85) Amazing robot type voice unit, with ring modulator and reverb. Kits as published. Set 228BK **£37.40**
STEREO NOISE GATE & VCA (P.E. May '85) Automatic noise reduction circuit for mono or stereo. Kit as published. Set 227BK **£26.61**
SIGNAL GENERATOR & F-V (P.E. Jan. '85) Audio test equipment. Multiwaveform VCO, & frequency to voltage converter, & sweep generator. Kit as published. Set 233 **£46.96**
BLOW BOX: Voice operated VCF & VCA for fascinating effects **SET 214 BK £29.33**
COMPANDER: Mono of stereo compression-expansion, switchable **SET 238 BK £22.99**
ENVELOPE SHAPER: Note triggered ADSR with VCA **SET 174 BK £25.20**
FREQUENCY DOUBLER: Guitar octave raiser & tone changer **SET 98 BK £15.30**
FUZZ: Smooth distortion, retains attack & decay character **SET 209F BK £19.58**
GUITAR SUSTAIN: Extends note decay time, with noise gate **SET 222 BK £25.31**
GUITAR TO SYNTH INTERFACE: With voltage & trigger outputs **SET 173 BK £41.41**
HAND CLAPPER: Auto & manual variable clap effects **SET 197 BK £26.69**
MOCK STEREO: Splits mono signal into stereo simulation **SET 213 BK £24.37**
MUSIC MODULO: 8 variable tremolo & wah guitar effects **SET 196 BK £23.56**
RHYTHM GENERATOR: Computer driven, BBC, Apple, 64 & similar **SET 185 BK £34.64**
STORM EFFECTS: Auto & manual wind, rain & surf effects **SET 154 BK £23.60**
TOM-TOM SYNTH: Sound triggered, multivariable drum effects **SET 190 BK £19.37**
TREMULO: Mono variable depth & rate modulation **SET 136 BK £15.62**
VOCODAVOX: Modular vocoder, 7 chans extendable **SET 152 BK £79.95**
VOADALE: Simple robot type voice modulator **SET 155 BK £18.31**
WAH-WAH: Auto, manual & note triggered, switchable **SET 140 BK £24.36**

Add 15% VAT. Add P&P £1.50 each kit. (Overseas Rates in Catalogue). Despatch usually 10-14 days

Project texts & circuits can be bought separately at 50p each plus large S.A.E. Boxes are steel & aluminium with black finish. All kits include PCBs, parts, instructions, boxes wire, solder. See other advert for more audio effects kits. For catalogue of over 70 kits send 9x4 S.A.E. (For overseas catalogue send £1 or 5 IRC's). Mail Order. Payment to Phonosonics, CWO, CHQ, PO, Access, Visa. Insurance cover 50p per £50 (obligatory on credit card orders. Details correct at press. E&OE.

BECKER-PHONOSONICS,
MAIL ORDER DEPT PE58, 8 FINUCANE DRIVE,
ORPINGTON, KENT, BR5 4ED. TEL: 0689 37821.

Tandy® Top Value In Test Equipment



Select the Function and It
Selects the Range
Automatically

£22⁹⁵



£69⁹⁵



- Folds Into Compact Case With Wrist Strap

- Automatic Power Off When Case Is Shut
- Automatic Polarity

[A] 25-Range Folding Multimeter. Features include fuse and surge-absorber protection, banana-type probe jacks and 4" 3-colour mirrored meter with automatic shunt protection (when folded shut). DC Volts: 0 to 1200. AC Volts: 0 to 1200. DC Current: 0-60µA, 3-30-300 mA. Resistance: 0-2-20-200K-2 megohms (centre scale 24). dB; -20 to +63 dB. Requires "AA" battery. 22-211 **£22.95**

[B] Folding LCD Multimeter With Autoranging. Features extra large 1 1/16" non-glare display with adjustable viewing angle, a "beep" indicator for quick continuity testing, and zero-ohms. adjust for super-accurate low resistance measurements. DC volts to 1000. AC volts to 500. Up to 10 amps AC and DC. Resistance to 2 megohms. Open: 10 7/8 x 4 5/8 x 1 1/2". Requires two "AA" batteries. 22-193 .. **£69.95**

Transistor Checker and Digital Logic Probe

[A] £9⁹⁵

£14⁹⁵ [B]

[A] Dynamic Transistor Checker. Makes Go/No-Go tests on small-signal and power types and allow you to match similar transistors. Indicates relative current gain, "opens" and "shorts". Requires "AA" battery. 22-025 **£9.95**

[B] Digital Logic Probe. The fast way to "peek inside" TTL, LS and CMOS digital circuits. Colour-coded LEDs indicate high, low or pulsed logic states (up to 10 MHz). Minimum detachable pulse width: 50 ns. 36" leads with clips obtain power from circuit under test. Low current drain. 22-302 **£14.95**



Overload and Polarity Protected

Reference Books



[A]



[B]



[C]

[A] Semiconductor Reference Guide. 1985 edition! Exclusive cross-reference and substitution section lists over 80,000 types. 276-4008 **£4.49**

[B] Getting Started In Electronics. The perfect introduction to the exciting world of electronics. Learn to build your own circuits. 128 pages. 276-5003 **£2.49**

[C] Timer IC Mini-Notebook. An excellent reference and hobby book. Large schematic diagrams. 32 pages. 276-5010 **99p**



Take A Look At Tandy, Today!

Visit your local store or dealer and see these and many more bargains. We service what we sell - over 2,900 exclusive lines!

See Yellow Pages For Address Of Store Nearest You

OVER 9,000 STORES & DEALERSHIPS WORLDWIDE



Known As Radio Shack In The U.S.A.
Prices may vary at Dealers
Offers subject to availability

MOVEMENT?

IN THE July leader we commented on *Twenty Years of Stagnation* in UK schools and invited anyone interested or involved in this area to let us know their views. Some enlightening letters concerning this subject appear elsewhere in the issue and we hope they will generate further thought and response.

A number of highly enthusiastic people and organisations in the UK are actively trying to push back the boundaries and help to introduce students to technology. However, two things worry us most:

1. There appears to be little lead from government and educational authorities.
2. Not one student (or ex-student) has written to us with any views or comments.


Maybe these two points are linked? It is possible that many students are never introduced to modern electronics in schools, that they never do more than a conventional (conservative—outdated—call it what you will!) general science course and are therefore not fired with enough interest to worry about the quality and variety of their education. Are we beginning to train children to accept the mundane or the dole queue? Come on you students (past and present), let us hear what you think of the system. Let us know what instruction is/was available to you, what you would like to see going on in schools and how you feel it would be of benefit to you.

LET DOWN

Going back to the first point—it is very sad that facilities are so lacking in schools. Mr. Henderson's letter from Priestly College, Warrington, illustrates how the staff feel society is letting them down.

The points about the "low esteem" of the teaching profession held by society and lack of specialist staff show that perhaps we all need to change our attitude towards education. While in no way wishing to get involved in politics, it is all too easy to blame the teachers when a continuing lack of investment in training, staffing and facilities, at Government level, is not allowing education in the UK to keep up with progress and the new demands of industry. Education which has, for many years, had a worldwide reputation for excellence. Perhaps the state schools should follow the lead given by the Independent Schools Microelectronics Centre? Copies of the leaders and of the letters we have received have been forwarded to the Department of Education in the hope of a reply.

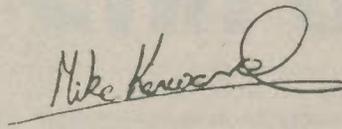We wish to be constructive and with this in mind would particularly like to hear of your ideas and the clubs, courses, specialist schools etc. that are working in this area.



Editor Mike Kenward

Secretary Pauline Mitchell

Editorial Tel: Poole (0202) 671191

Advertisement Manager
David Tilleard 01-261 6676

Secretary
Christine Pocknell 01-261 6676

Ad. Make-up/Copy
Brian Lamb 01-261 6601

Classified Ads
Mandy Morton 01-261 5846

Queries and letters concerning advertisements to:
Practical Electronics Advertisements,
King's Reach Tower,
Stamford Street, London SE1 9LS
Telex: 915748 MAGDIV-G

Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to **one published project only. We are unable to answer letters relating to articles more than five years old.**


Components are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Old Projects

We advise readers to check that all parts are still available before commencing any project in a back-dated issue, as we cannot guarantee the indefinite availability of components used. **We are unable to answer letters relating to articles more than five years old.**

Technical and editorial queries and letters to:
Practical Electronics Editorial,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG

BACK NUMBERS and BINDERS . . .

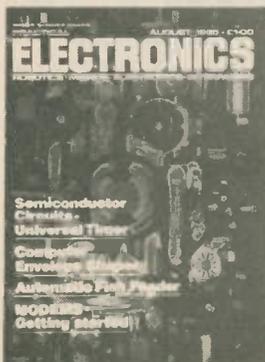

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. When ordering please state title, month and/or issue required.

Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including postage, packing and VAT.



SUBSCRIPTIONS

Copies of Practical Electronics are available by post, inland for £13, overseas for £15 per 12 issues, from: Practical Electronics, Subscription Department, IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment for subscriptions can also be made using a credit card.

Phone:
Editorial Poole (0202) 671191

We regret that lengthy technical enquiries cannot be answered over the telephone.

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

NEWS &

UK ABANDONS DBS


Only two years ago, great excitement abounded when plans to bring Direct Broadcasting by Satellite (DBS) to Britain were being finalised. Our hopes (or fears) of being treated to world-wide televisual entertainment have now been dashed. A Government selected body has decided that the potential demand is too small and the financial risk too great.

The unanimous pronouncement from 21 communications and broadcasting organisations, will have far-reaching effects on the proposed plans of many companies. Government franchised British Telecom, United Satellites, GEC-Marconi and British Aerospace will not now be building DBS satellites for Britain.

The High Street retailers and the manufacturers that supply them will also feel the pinch. Logically, the market for DBS dishes and associated conversion equipment would have been as vast as that of the television watching public; TV sales will also suffer. It is rumoured that a new 'novelty' will have to fill the gap if predicted sales figures are to be realised.

The future of Multiplexed Analogue Component signals (C-MAC) development must also be in jeopardy. The system is based on a single f.m. transmission channel with no sound carriers, colour carriers or subcarriers. It was designed to provide improved sound and picture quality from satellite broadcasts. (See, Getting to grips with MAC) *Practical Electronics*, Sept 83.

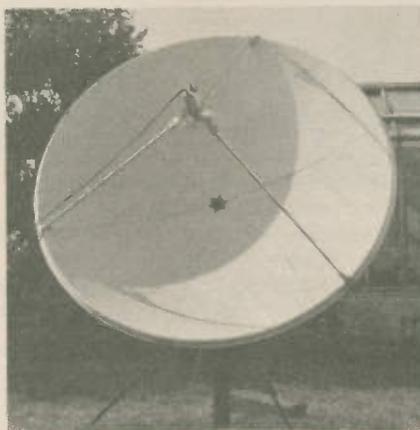The Government, having spent time and money attempting to initiate DBS, will not be amused. However, looking for an alternative use for the £500 million scheduled for the project may help to ease the pain. So might the news that a last-hour reprieve is in the offing.




Side-on semicon


A new range of 'side view' l.e.d.s from Telefunken Electronic, the TLP Series, has been designed to simplify the way in which p.c.b.-mounted l.e.d.s are positioned to provide visual indication. They will be particularly useful in confined spaces where 'top view' l.e.d.s are difficult to view without bending the leads.

The TLP 56 Series utilises a dense translucent lens material to ensure that the light is even and consistent without loss of intensity. Red, orange, yellow and green types are available, with luminous intensity ranging from typically 0.5 m.c.d. (red types) to 1.5 m.c.d. (green, orange and yellow types).

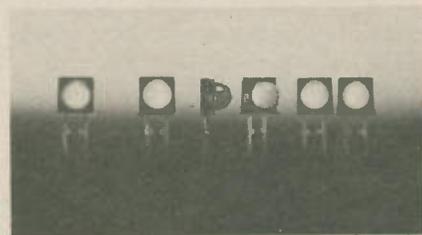Viewing angle (half intensity) is 50 degrees for red types and 80 degrees for others. Power-dissipation is 100mW maximum for all types with reverse voltages down to 6V d.c. (max 20V d.c.). The lens on each type is a dome of 3.5mm diameter, and base 4.8mm square. Overall length of the component (including leads) is 18mm. Further details from AEG-Telefunken (UK) (0753 872120).



KEYBOARD KITS

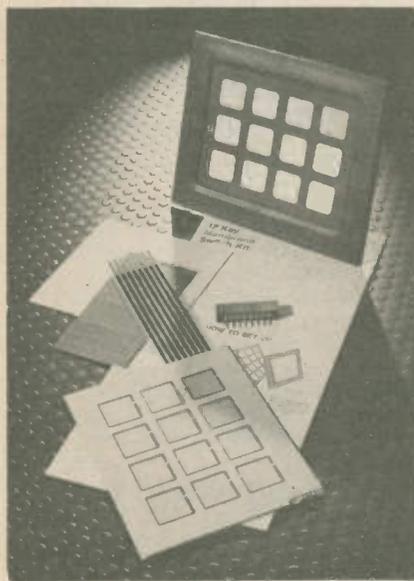

Swissinco has introduced a prototype keyboard kit which contains all the parts necessary to build a customised membrane switch/keyboard panel.

Available in 4, 12, 16, 40, 80 and 102-key versions, the new kit includes the basic switch unit, overlay, colour pad, edge panel and connector. Optional transfer lettering is available to add numbers, letters or functions words depending on the user's application.

A choice of key colour and lettering styles is available, and a complete keyboard assembly can be made up in a matter of minutes. The switch technology used in the membrane keyboard combines low cost with high reliability, and the switches have been reliability-tested to over three million operations.

Prices respectively (inc. VAT and p. & p.) are £7.57, £10.07, £11.45, £19.55, £40.99 and £34.68. From Swissinco U.K. Ltd., Unit 2, 225 Hook Rise South, Surbiton, Surrey KT6 7LD (01-397 7041).

NEW MICROS FOR OLD

Until 31st August Mitsubishi Electric (UK) Ltd. will be offering a £50 trade-in on any computer or video games machine against the sale of a new Mitsubishi MSX home computer.

This offer will run additionally to the free starter software pack—consisting of six top tape games "worth over £45"—and a comprehensive 300 page operating instruction manual and basic language handbook.

The Mitsubishi 32k memory ML-F48 and 64k ML-F80 MSX home computers retail in the High Street at around £219 and £275 respectively and are available from most Mitsubishi Electric dealers.

MARKET PLACE

WIDE ANGLE REVERSE LCD

Epson has introduced a new wide angle, high contrast, easily readable liquid crystal display known as "Black Shutter".

The display, based on guest-host design principles, is unusual in that it consists of a normally black opaque l.c.d. panel which, when activated, turns transparent to light. By placing a light source behind, the l.c.d. gives a clear, positive display that can be easily read from a wide angle.

The secret of the display is a black dye with very high light absorption qualities that eliminates the need for two polarisers. Normal twisted nematic l.c.d.s often cannot be read from an oblique angle, from a distance.



Black Shutter, which has up to 25 to 1 contrast, is available in two versions. The first is a high specification l.c.d. designed to meet with the requirements of the automotive industry and is suitable for application in temperatures between -30°C and $+80^{\circ}\text{C}$. The second system is suitable for use in consumer goods such as cookers, washing machines, clocks and office automation equipment, and has an application range between -10°C and $+60^{\circ}\text{C}$.

The system is easy to read under all conditions when backlit, and has low power requirements, common with l.c.d.s.

Patent it!

Patents, designs and trade marks are not just for the likes of ICI or their fellow multinationals, they are designed to protect us all.

Admittedly though, for those of us who have ventured into this world of forms and counter forms, it can seem a rather daunting place, and it is all too easy to just leave it to the professionals. It is the intention of the Patent Office to show us that this should not be the case.

To prove the point the Patent Office has made a video which explains how to register a design, patent or trade mark, and to demonstrate the benefits that can be derived thereafter. The video also illustrates how the Science Reference Library can act as an invaluable source of material with its databank of some two million British patents and 23 million foreign patents.

As part of a programme to inform inventors and companies about who they can protect their intellectual property the office can also provide speakers for seminars or lectures to expand on the information given in the film.

The video costs between £35 and £40 depending upon the format, or it can be hired for five days at a cost of £9.78 (inc. p&p). From, CFL Vision, Chalfont Grove, Gerrards Cross, Bucks. SL9 8TN (02407 4433).

A wide range of booklets is always available from, The Patent Office, State House, High Holborn, London, WC1R 4TT.

POINTS ARISING ...

DISK DRIVE PSU

April '85

The p.c.b. layout of Fig. 2 on page 20 shows R1 and R3 transposed.

SELF STUDY INTRO PACK

An 'Introducing Microelectronics' package produced for the educational market by Educational Electronics Limited is now available to a broader market. It is offered complete with all the components, circuit board and 136 page course booklet, needed to conduct a wide variety of investigations.

The course booklet, written by a leading authority on microelectronics assumes no previous knowledge of the subject. It provides a self-study guide to basic digital electronics and computer building blocks.

The basic circuit board is cleverly designed to incorporate a range of features that enables the user to make rapid progress. It contains four i.c. sockets, i.e.d.s., a pulser button and a pulse 'clock'. Bit patterns can be set up using the integral bit set switches and the edge connector port can be utilised for further experiments using a microcomputer.

The INTRO package is available at £59.50 inc. VAT and p&p from Educational Electronics Limited, 28 Lake Street, Leighton Buzzard, Beds, LU7 8RX (0525 373666).



Countdown ...

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Brian Butler.

Video Software Sept. 1-3, Olympia G3
 Personal Computer World Show Sept. 18-22, Olympia 2 M
 Electron & BBC User Sept. 27-29, UMIST, Manchester L
 Amstrad User Exhibition Oct 5/6th, Novotel F2
 Computer Graphics Oct. 16-18, Wembley Conf. Centr. O
 Cellular Communications Int. Nov. 5-7, Wembley Conf. Centre. O
 Electronic Publishing Nov. 5-7, Wembley Conf. Centr. O

Compec Nov. 12-15, Olympia K2
 Electron & BBC User Nov 14-17, New Horticultural Hall, London L


Computers In The City Nov. 19-21, Barbican Cntr. O
 Scottish Home Computer/Electronics Show Nov. 22-24, Anderston Centre, Glasgow W2

Leeds Electronics Show Sept. 24-26, University E

A1 Inst. Electronics ☎ 0706 43661
 E Evan Steadman ☎ 0799 26699
 F2 Computer Marketplace (Exhibitions) Ltd. ☎ 01-930 1612
 G3 Link House Video ☎ 01-686 2599
 K2 Reed Exhibitions, Surrey Ho., 1 Throwley Way, Sutton, Surrey.
 L Database ☎ 061-429 8157
 M Montbuild ☎ 01-486 1951
 O Online ☎ 01-868 4466
 T1 Cahners ☎ 0483 38085
 W2 Trade Exhibitions Scotland ☎ 041-248 2895

Experimenting With ROBOTS

Mike Abbott

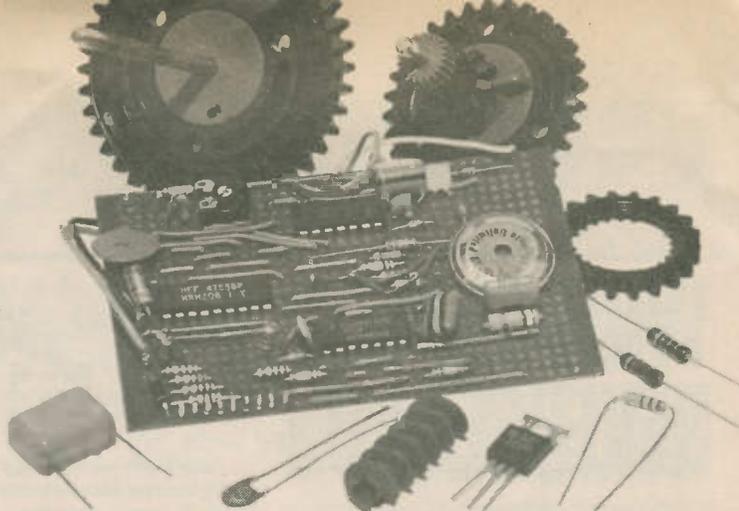

SO FAR, to the hobbyist and student, getting into robotics is a matter of purchasing a kit of parts, assembling those parts, and thereafter learning to "drive" the robot through the host microcomputer. The experience is much the same, whether the machine be a straightforward arm or a mobile unit with one or two sensors.

But what of the robots themselves? What of the engineering that goes into them, and of their peculiar and challenging marriage between electronics and mechanics? Potentially, there is a whole universe of intrigue to be explored in this world of gearwheels, motors, potentiometers and power transistors. At a glance, there would appear to be sufficient mechanical media available, in the shapes of *Fischer Technik*, *Meccano*, and even *Leggo (Technical)* to a limited degree, to open up that universe, along with the aid of improvised and home made bits and pieces. Interest is not confined to robot arms, nor even to the accepted formula mobiles. In fact, any servomechanism designed to do any job, controlled by "intelligent" electronics tends to be fascinating yet as far as this hobby is concerned it seems to be an underexploited area of creativity.

Experimenting With Robots is based on the aforementioned premise, but if the column is premature it will not continue for long, because although we have provided the "kick off" material it is hoped that the column will eventually become a kind of "Ingenuity Unlimited for robotics". Ideas, serious or silly, electronic or mechanical, tested or theoretical, large or small will be considered for publication. And, of course, payment at current rates will apply. If you think you have invented something which will interest other readers, then let us know.

GENERAL PURPOSE INTERFACE

With the exception of one feature, the interface described is both simple and conventional, allowing up to four servo-positional channels and one gripper control channel. Position-related voltages are generated by potentiometers mounted on the robot's axes, and these are compared to voltages generated by DACs to generate the error signals which drive the motors towards their null points. The DACs have onboard latches which are memory mapped into the host computer by a memory addressing circuit that can be set to any location by way of d.i.l. switches. The host computer requires no user I/O port. Numbers relating to angular positions (1-255) can be POKEd to the selected addresses in quick succession and the linear circuitry left to drive all the axes simultaneously. Although the interface does not provide a feedback path from the robot to the computer, the robot is nevertheless operating under closed loop conditions, and therefore likely to go where you expect it to, every time.

The value of the potentiometers mounted on the robot is not critical, the optimum being around 5K. The *Powertran Cybernetics "Micrograsp"*, which has 1k potentiometers, worked well with the

interface (with a few wiring alterations).

All, or part of the interface may be built on stripboard (as was the prototype), or on the p.c.b. illustrated. The interface should work with most microprocessors because it is driven from the data bus, and the address bus of its host, as opposed to requiring an I/O port. A second prototype was constructed on the p.c.b. and hitched up to a ZX81. It worked perfectly with this simple and inexpensive micro.

Since there is no point in cramming components together when there is no need, the p.c.b. is somewhat "rural" in appearance, which makes messing about with it all the easier. Particularly so with the fifth channel, which is not only unconventional, but which has a p.c.b. area that may be populated in different ways for different purposes. The technical possibilities of this channel are analysed further on.

CIRCUIT DESCRIPTION


The circuit diagram of the address decoding section is shown in Fig. 1, along with the servomotor driver circuits (4 channels). Address line A3 is not included in the base address decoding carried out by IC1-3. This is the case because that extra single bit of decoding would have required the use of another 74LS85, 75% of which would have been redundant, and because the consequences of ignoring A3 is simply that the group of eight decoded channels in the memory map become addressable again immediately above the first. See Table 1.

Address lines A0, A1 and A2 are decoded by IC4, along with an overflow line from the bulk decoding section, to generate 8 channel enable lines. The eight memory mapped channels start at the base address decoded by the bulk decoding section formed by IC1-3. These are 4-bit comparator i.c.s which generate a flag to show when the binary value of each input arm is the same. The 74LS85's are cascaded so as to compare a total of 12 bits (A4-A15), the overflow of which will only enable the 3-to-8 converter IC4 when the data bus agrees with the setting of the address select switch-bank (S1-S12).

The four servomotor driver channels are identical. Each one uses a Ferranti ZN428E8 DAC (Fig. 2) to latch a number in the range 0 to 255 from the data bus and convert it into proportional voltage. The DAC i.c. also provides a stable reference voltage, and looking at Channel A in Fig. 1 it can be seen that this is taken to the top end of the feedback poten-



Fig. 1. Circuit diagram of address decoding and the four servo channels

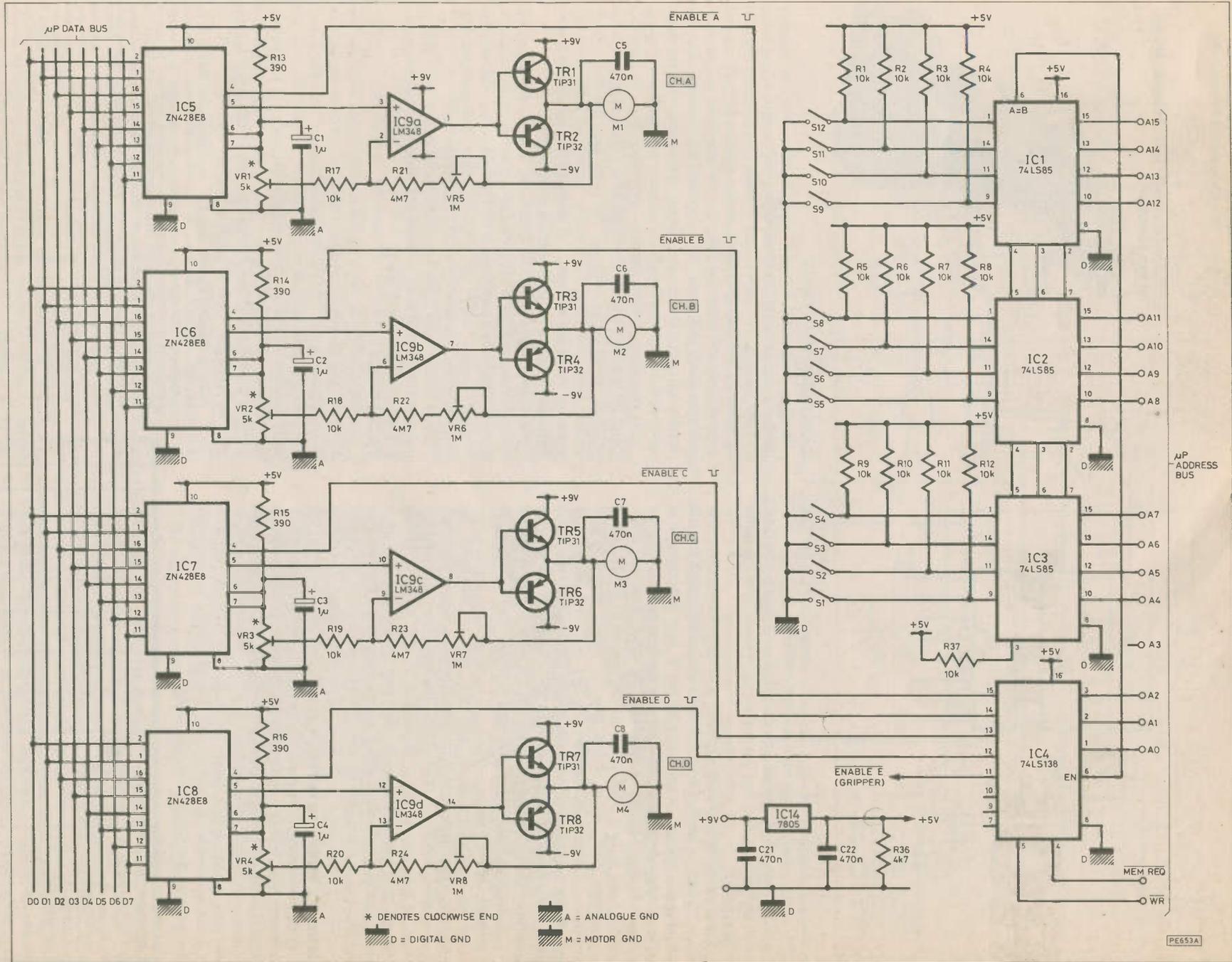

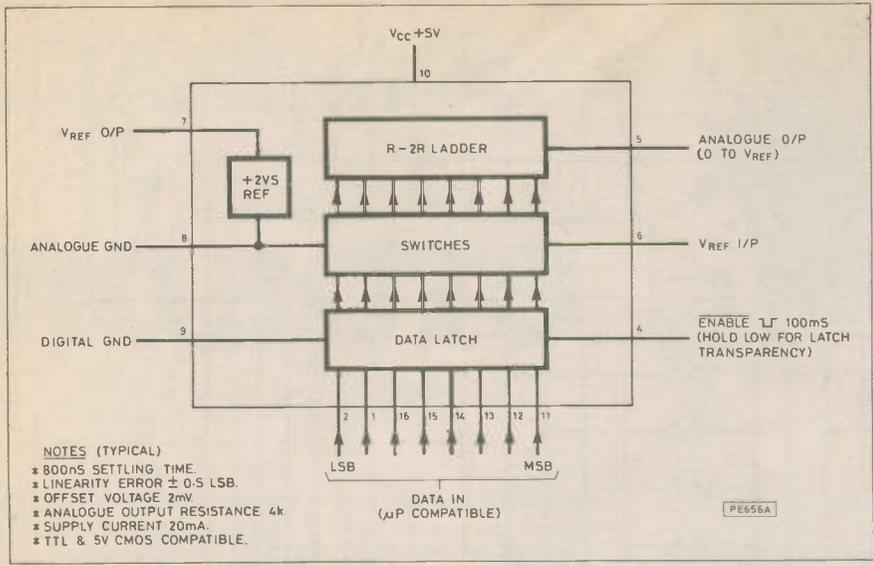


Fig. 2. The Ferranti ZN428E8 DAC incorporates μ P compatible data latch

The Powertran Cybernetics Micro-grasp robot arm



tiometer mounted on the robot. This connection (from IC5 pin 7 to VR1) ensures that the maximum position-related voltage from VR1 is exactly the same as the maximum voltage generated by the DAC itself, thereby ensuring that the entire loop is working to the same scaling factor.

The principle of operation is simple. A position instruction in the range 0-255 is latched into IC5 from the micro's data bus. A proportional voltage is produced at pin 5 and, assuming it is different from the voltage generated by position sensor VR1, the difference (error signal) is amplified by IC9a. This op. amp. operates in a very high gain mode, working almost as a comparator, since most of the time its output is driven into saturation. Current amplification by TR1 and TR2 allows this amplified error signal to drive the motor belonging to the same axis, which is wired in opposition to VR1, so that it will run in a direction which eventually cancels out the error signal. A closed loop control system is thus achieved in which the mechanism of the robot itself is a part.

Motors of anything up to 12V d.c. will run well with the interface, and their maximum permitted power rating is governed by the driver transistors (TR1-TR8). The transistors specified are rated at 3A, with a power dissipation of 3W at 25°C. Larger motors, or a heavy duty cycle, may well dictate the need for a larger heatsink. A curious effect results from taking the negative feedback loop around the op. amp from the emitters of the power transistors instead of directly from the amplifier output. The circuit was designed this way in order to avoid a *dead band* between the threshold voltages of the power transistors in which the op. amp's output would "wallow" around *outside* the control of the feedback loop. Taking the negative feedback path directly from the motor improves positional repeatability, but it has the side effect of never allowing the op. amp's output to settle at exactly 0V, which is without consequence, and means that sensitivity automatically increases as the null point is approached.

GAIN CONSIDERATIONS

Looking at Channel A again, it can be seen that the negative feedback path around IC9a incorporates two resistors, one fixed, and one variable. The series value of these two resistors will best be found by trial and error because the amount of gain required depends upon the reduction gearing in the axis under control. High reduction gearing between the motor and the potentiometer will require high gain in the op. amp. circuit, and hence a high feedback resistance. Low gain will result in inaccurate positioning of the axis.

Low reduction gearing between the motor and the potentiometer will require lower gain in the op. amp. circuit. High gain in this situation would cause hunting. That is to say, the motor overshoots back and forth, and never comes to rest. Generally speaking, the higher the reduction gearing in the servomechanism, the easier it will be to get positional accuracy.

Although the preset VR5, in Channel A, allows trimming to the optimum performance, it can be linked out. In this case it would be advisable to place solder pins in R21's position so that resistors may be "tacked" on to get the best effect. The professionals' euphemism for this method is SOT (Select On Test).

Some of the most basic laws of robotics design will begin to manifest themselves even at this early stage of experimentation, and in a most entertaining way.

TACACOOGA

The *TACACOOGA* is not a Latin-American dance step, but the acronym I found myself with when I added together all the features of this gripper circuit: *Torque Adjustable Closure, Automatic Cut-off On Opening Gripper Actuator* circuit. Don't run away! The p.c.b. will accommodate a number of conventional circuits as an alternative, and these are outlined further on. The *TACACOOGA* incorporates some of the ideas that tend to be speculated about but seldom tried, so I thought it best to begin at this, the mirky end.

Table 1. Setting up the address decoding switches will be easier using the above table. Switches S1 to S12 allow the interface to be memory mapped to any location in the host computer's memory, setting up the base address (channel A). The base address (in decimal) is found by adding up the binary weightings at which a logic 1 (switch open) occurs. Channel B will then be at the base address +1, channel C at base address +2, etc. The robot is controlled by the POKE instruction using these decimal addresses. Note that for reasons of economy of hardware address line A3 is not decoded, but this does not generally matter. Hence, in example 2, POKE 65520,5 would have the same effect as POKE 65528,5 since the decoder cannot sense the difference. The lower address bits decode the individual channels, and in example 2 the gripper channel appears at 65524.

Address Line	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4
Binary Weighting	32,768	16,384	8192	4096	2048	1024	512	256	128	64	32	16
Switch (0=closed)	S12	S11	S10	S9	S8	S7	S6	S5	S4	S3	S2	S1
Example 1	0	0	0	0	0	0	0	0	0	0	0	0
Example 2	1	1	1	1	1	1	1	1	1	1	1	1
Example 3	1	1	1	1	0	0	0	1	1	0	0	0

Memory location (Base address in decimal)

00000
65520
61824

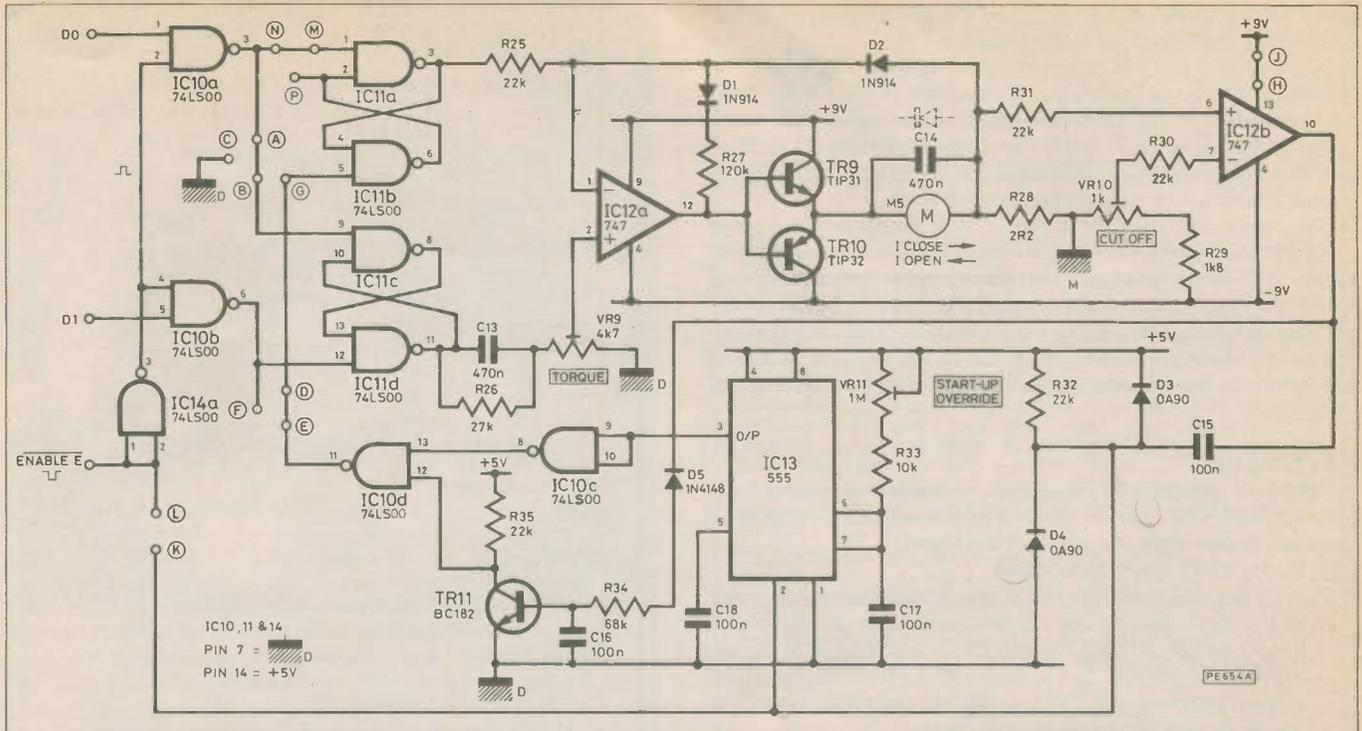


Fig. 3. Circuit diagram of the TACACOOGA

TAC...

The circuit diagram is shown in Fig. 3, and it can be seen that data from lines D_0 and D_1 are latched into two bistables formed of IC11, at the command of the Enable \bar{E} line from the address decoding section illustrated in Fig. 1.

To close the gripper a logic 1 must be present on D_1 and a logic 0 on D_0 (denary 2 on the data bus), when Select is pulsed high. IC10 pin 6 will then pulse low, thus setting bistable IC11c and d. The steady logic 1 so created on IC11d's output (pin 11) generates a positive voltage at the non-inverting input of op. amp. IC12. However, VR9, in conjunction with R26, reduces this +5V logic signal to the op. amp., making it adjustable between 0V and 0.75V. The op. amp.'s inverting input remains low.

When the output of IC12a rises towards positive it reverse biases D1 and cuts off the negative feedback path through R27. The output voltage rises rapidly because of open loop gain until TR9 begins conducting, at which point current is produced in the motor, and a positive voltage generated across R28. This voltage forward biases D2, thus activating the unity gain negative feedback path. Because an op. amp. configured with negative feedback always tries to bring its input voltages to the same potential, it is clear that its output will stop rising when the voltage across R28 is the same as the voltage on the wiper of VR9. Therefore, by adjusting VR9 we can adjust the voltage across R28. This resistor is a mere 2.2 Ω and is in the same current path as the motor, so that the motor current can be controlled by the voltage set across R28. The net effect is that VR9 controls the motor torque whilst the gripper is closed, or holding an object. With the component values specified the motor current may be varied from zero to just under 350mA.

... ACOOGA

The gripper opens when a logic 1 is present on D_0 and a logic 0 on D_1 and Enable \bar{E} is pulsed. IC11a output is set high, bistable IC11c and d is reset, and a positive voltage appears at the op. amp.'s inverting input. Because the output of op. amp. IC12a is driven negative, forward biasing D1, we have negative feedback

through R27, and an input resistor in the shape of R25. This is a conventional inverting amplifier with a gain of around 8, and its output swings negative to bias TR10 into conduction. The motor is therefore driven the opposite way, and its current produces a negative voltage across R28.

The comparator formed of IC12b is designed to ignore the "running" current of the motor, but to detect its "stall" current. The idea is that the motor runs in the "gripper open" direction until it strikes the end-stop, at which point the detected stall current is used to generate a signal to switch off the motor. This eliminates the need for limit switches mounted on the gripper. I have heard this possibility discussed many times, but the principle comes easier than the practise, I discovered.

The inverting input of IC12's second op. amp. is set to a negative voltage by way of VR10, and the amplifier compares this negative voltage with the negative voltage across R28. When the gripper motor is stalled its armature generates no back e.m.f. and so the motor conducts current heavily, and this in turn causes a greater negative voltage across R28. So, as soon as the voltage across R28 becomes more negative than the setting of VR10 the output of the op. amp. switches sharply negative to around -8V. The switch is rapid because the op. amp. is configured as a comparator, i.e. is in open loop gain configuration.

After two inversions (TR11 and IC10d) this signal resets bistable IC11a and b, thereby deactivating the motor.

As was stated earlier, the principle of operation runs aground on the fact that the motor is stationary at the outset, of course, and therefore the system immediately sends out a self-cancelling signal, for however briefly it may be, at start-up the motor conducts stall current.

The answer is a short time delay to override the start-up period of the motor, hence the 555 monostable circuit. By triggering the monostable from the same stall current signal, and gating the monostable's output back in at IC10d the stall current response is delayed long enough to overlook the motor start-up period. It might have been simpler to delay the stall current detect line with a C-R integrator, but the variability (VR11) of the monostable circuit

gives a more universal capability, and this is necessary when the system is intended for no specific robot.

The inversion at TR11 is nevertheless delayed a little by C16, and this is intentional to ensure that the stall detect signal on start-up does not reach IC10d before the override signal from IC13, which goes through more switching functions. Diodes D3 and D4, and R32 simply clip the trigger signal generated by IC12b to levels acceptable to a 555 timer working on a 5V rail.

The capacitor across the motor, C14 is essential to suppress electrical noise which would otherwise cause havoc with the logic. Finally, C13 provides a small start-up voltage boost to the motor when the gripper is instructed to close, and may only be necessary with some motors when set to a low torque by VR9. I found some model engineering motors quite difficult to use with this feature of the circuit, an old cassette deck motor being by far the most co-operative.

SETTING UP

Confusion will reign if you are not methodical in setting up a TACACOOGA. The best approach is as follows (all pot directions are seen looking from the centre of the board):

- 1) Rotate VR11 fully anticlockwise.
- 2) With the power off, set VR10 fully anticlockwise, and break LK1. Power up, and use the host computer to instruct the gripper to open. Using either a DVM, scope or logic probe, monitor the voltage on the collector of TR11. Rotate VR10 slowly clockwise until TR11's collector goes high. Leave the preset adjusted to 'just past' this point.
- 3) Starting with VR11 fully clockwise, rotate it anticlockwise, opening the gripper after each increment (operated from micro), until the gripper *consistently* swings fully open.
- 4) VR9 should be adjusted clockwise until the gripper closure torque suits your requirement. From the point of view of power dissipation, torque should be kept to the allowable minimum if long periods of closure are anticipated.

THE TRADE-OFF

The system concept is a trade-off in which the electronics is necessarily more complex in order to keep the mechanics simple. In the case of the torque control, or grip strength, the gripper jaw mechanism *must be kept* simple. If the motor has any kind of mechanical advantage, such as through a worm gear, the tactile nature of the system will probably be lost.

INSTRUCTION	BINARY				NOTES
	D ₂	D ₁	D ₀	DENARY	
OPEN	x	0	1	1	WILL AUTO-STOP
CLOSE	x	1	0	2	CONTROLLED TORQUE
NO CHANGE	x	0	0	0	
ILLEGAL	x	1	1	3	

SLACK JAW

Using the TACACOOGA driven gripper, at some angles it might drop shut again after obeying an instruction to open, due to gravity acting on the driven jaw. This is because the motor, and therefore the jaw, goes slack after striking the end-stop. In some applications this could be a nuisance, but one cure is to mount a small permanent magnet on the end-stop to capture the jaw once opened. If the driven jaw is not made of a ferrous material, then a small steel nut and bolt through it will give the magnet something to act on. The magnet needs to be strong enough to carry the weight of the jaw in the vertical position, but weak enough to allow the motor to pull the jaw away from it when energised in the "close" direction. An alternative is to use a very small pair of facing Velcro pads.

NEXT MONTH: Other gripper circuit configurations, the simplest gripper in the world (for the TACACOOGA), p.c.b. construction and software.

COMPONENTS...

STANDARD (FULLY POPULATED) INTERFACE

Resistors

R1-12	8 x 10k s.i.l. package (2 off)
R13-16	390 (4 off)
R17-20, R33, R37	10k (6 off)
R21-24	4M7* (4 off)
R25, R30, R31, R32, R35	22k (5 off)
R26	27k
R27	120k
R28	2.2/4W
R29	1k8
R34	68k
R36	4k7

*See text. All resistors 1/4W 5% unless otherwise stated

Potentiometers

VR1-4	5k linear nominal. Mounted on robot (4 off)
VR5-8	1M preset (4 off)
VR9	4k7 preset
VR10	1k preset
VR11	1M preset

Capacitors

C1-4	1μ elect. or tant. (4 off)
C5-8, C13, C14, C21, C22	470n (8 off)
C9-12, C15-22	100n disc cer. (12 off)

Transistors & Diodes


TR1, TR3, TR5, TR7, TR9	TIP31 (5 off)
TR2, TR4, TR6, TR8, TR10	TIP32 (5 off)
TR11	BC182 or equiv.
D1, D2, D5	1N914 or 1N4148 (3 off)
D3, D4	OA90 (2 off)

Integrated Circuits

IC1-3	74LS85 (3 off)
IC4	74LS138
IC5-8	ZN428E8 (4 off)
IC9	LM348
IC10, IC11	74LS00 (2 off)
IC12	747
IC13	555 timer
IC14	7805 regulator

Miscellaneous

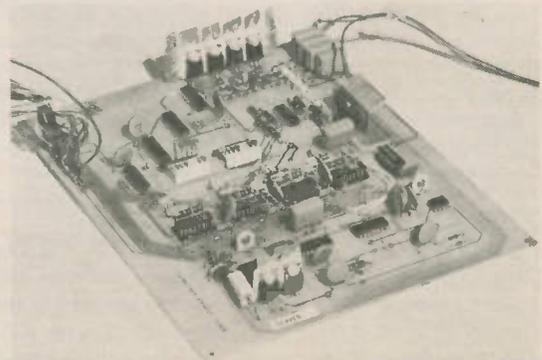S1-12 8 x dual-in-line switch (2 off)
 P.c.b. (copies available from PE Poole office on request) or Veroboard, eyelets or solder pins (through-board connection), 22 s.w.g. tinned copper wire, instrument wire, aluminium sheet, mica washers and heatsink paste, motors and robot parts (*who knows what?*)



Introducing...



Serpent

System from
£1515

Serpent SCARA assembly robot

Available as kit or ready built, 5 axes, 2kg capacity,
12 bit control system, Serpent I reach 400mm,
Serpent II reach 650mm.

BEING FEATURED IN PRACTICAL ELECTRONICS September issue



Please phone for brochure: 0264 50093.
West Portway Industrial Estate, Andover SP10 3PE.
A private and independent company giving prompt,
personal service.

THE START OF SOMETHING NEW

If you are leaving College and planning a career in modern communications or if your present job lacks interest and challenge... why not join us in GCHQ? We are recruiting

RADIO OFFICERS

who after initial training will become members of an organisation that is in the forefront of communications technology. Government Communications Headquarters can offer you a satisfying and rewarding career in the wide field of communications. Training involves a 32 week course (38 weeks if you come straight from Nautical College) which will fit you for appointment to RADIO OFFICER.

Not only will you find the work as an R O extremely interesting but there are also good prospects for promotion, opportunities for overseas travel and a good salary. Add to this the security of working for an important Government Department and you could really have the start of something new.

The basic requirement for the job is two years' radio operating experience or hold a PMG, MPT or MRGC or be about to obtain a MRGC.

Registered disabled people are welcome to apply.

Salaries start at £4,762 at age 19 to £5,755 at age 25 and over during training and then £6,399 at 19 to £8,510 at 25 and over as a Radio Officer. Increments then follow annually to £11,741 inclusive of shift and weekend working allowances.

For full details and application form 'phone 0242 32912/3 or write to:



Recruitment Office, Government Communications Headquarters,
Oakley, Priors Road, Cheltenham,
Gloucestershire, GL52 5AJ.

CMOS	4095	58p	74LS76	28p	74LS266	28p	PL55	140p	VOLTAGE REGULATORS	HA-1197	150p
4000	16p	4099	58p	74LS78	34p	74LS273	72p	PL500	110p	HA-1306W	170p
4001	16p	4501	30p	74LS83	46p	74LS279	46p	PL504	95p	HA-1319	250p
4002	16p	4502	30p	74LS85	50p	74LS280	140p	PL508	170p	HA-1339	170p
4006	30p	4503	32p	74LS86	30p	74LS290	30p	PL519	450p	HA-1342	170p
4007	18p	4504	60p	74LS90	39p	74LS365	42p	PY81	70p	HA-1368WR	160p
4008	44p	4505	260p	74LS91	73p	74LS366	44p	PY88	48p	HA-1368	160p
4009	30p	4506	80p	74LS92	46p	74LS367	44p	PY300A	160p	LA-1377	220p
4010	30p	4507	33p	74LS93	40p	74LS368	41p		7905	HA-1389	140p
4011	16p	4508	85p	74LS95	52p	74LS373	68p		7912	HA-1392	230p
4012	16p	4511	42p	74LS96	63p	74LS374	68p	7400	7915	HA-1397	250p
4013	20p	4512	46p	74LS107	35p	74LS375	58p	7401	16p	HA-1398	240p
4014	40p	4513	90p	74LS109	38p	74LS399	80p	7402	18p	LA-1201	85p
4015	40p	4514	90p	74LS112	38p	74LS670	80p	7403	22p	LA-1352	120p
4016	27p	4515	89p	74LS113	32p			7404	40p	LA-1365	140p
4017	39p	4516	51p	74LS114	38p			7405	10p	LA-3301	120p
4018	39p	4517	130p	74LS122	44p	DAF96	60p	7406	40p	LA-3350	200p
4019	33p	4518	85p	74LS124	40p	DF96	50p	7407	20p	LA-3361	115p
4020	50p	4519	38p	74LS124	85p	DL32	47p	7408	25p	LA-4030	120p
4021	43p	4520	44p	74LS125	36p	DY87	50p	7409	20p	LA-4031	140p
4022	43p	4521	90p	74LS126	42p	DY802	45p	7410	35p	LA-4032	140p
4023	15p	4522	50p	74LS132	44p	EBC80	50p	7411	32p	LA-4050	130p
4024	30p	4526	48p	74LS133	34p	EB91	44p	7420	22p	LA-4051	160p
4025	16p	4527	48p	74LS138	38p	EBF90	45p	7421	25p	LA-4100	120p
4026	80p	4528	44p	74LS138	38p	EBF99	50p	7425	15p	LA-4101	100p
4027	30p	4529	70p	74LS139	40p	ECC82	40p	7430	25p	LA-4102SK	140p
4028	38p	4532	56p	74LS145	85p	ECC83	43p	7437	28p	LA-4112	250p
4029	53p	4532	56p	74LS147	120p	ECC84	40p	7442	45p	LA-4125	210p
4030	26p	4551	85p	74LS148	110p	ECC85	40p	7447	60p	LA-4140	70p
4031	100p	4553	190p	74LS151	38p	ECH81	49p	7450	22p	LA-4201	120p
4032	54p	4556	29p	74LS153	42p	ECH82	45p	7451	10p	LA-4220	120p
4033	60p	4556	41p	74LS153	42p	ECH83	45p	7452	10p	LA-4430	130p
4034	95p	4557	190p	74LS154	100p	ECL80	57p	7454	25p	LA-4480	170p
4035	50p	4583	50p	74LS155	51p	ECL82	59p	7470	30p	LA-4461	180p
4036	220p	4585	46p	74LS156	49p	ECL84	57p	7473	30p	LA-5112	120p
4037	80p	4585	46p	74LS157	35p	ECL85	57p	7474	40p	LA-4420	120p
4038	50p	74LS SERIES		74LS158	47p	ECL86	49p	7475	25p	LA-4480	170p
4039	220p			74LS160	52p	EF80	31p	7481	90p	LA-4461	180p
4040	42p	74LS200	17p	74LS161	56p	EF85	34p	7482	10p	LA-4420	120p
4041	38p	74LS201	17p	74LS162	50p	EF89	43p	7485	30p	LA-4430	130p
4042	43p	74LS202	17p	74LS163	50p	EF183	45p	7486	28p	LA-4480	170p
4043	40p	74LS203	17p	74LS164	44p	EF184	53p	7489	80p	LA-4461	180p
4044	40p	74LS204	17p	74LS165	65p	EL34	190p	7490	35p	LA-3324	35p
4045	72p	74LS205	17p	74LS166	65p	EL35	190p	7492	45p	LA-3339	40p
4046	49p	74LS208	17p	74LS168	98p	EL84	50p	7493	35p	LA-3448	60p
4047	49p	74LS209	17p	74LS169	70p	EL95	50p	7495	48p	LA-3827	100p
4048	32p	74LS210	17p	74LS170	85p	EL500	80p	7497	80p	LA-3831	150p
4049	29p	74LS211	17p	74LS171	85p	EL504	80p	7498	30p	LA-3832	150p
4050	26p	74LS212	17p	74LS175	48p	EY86	31p	74111	52p	LA-3837	100p
4051	42p	74LS213	26p	74LS190	59p	EY87	31p	74116	85p	LA-3837 DIL	30p
4052	40p	74LS214	30p	74LS191	55p	EY88	32p	74119	85p	LA-3837	100p
4053	40p	74LS215	30p	74LS192	50p	EZ85	30p	74122	40p	LA-4741 DIL	18p
4054	58p	74LS220	17p	74LS193	57p	EZ80	50p	74123	20p	LA-4741 MET	45p
4055	58p	74LS221	17p	74LS194	57p	EZ81	50p	74125	40p	LA-4741	58p
4056	58p	74LS222	17p	74LS195	55p	EZ84	180p	74126	45p	LA-4748	35p
4057	16p	74LS226	17p	74LS196	52p	PCF801	110p	74127	40p	LA-4748	35p
4058	16p	74LS227	17p	74LS197	52p	PC85	42p	74141	55p	LA-3900	30p
4059	30p	74LS228	17p	74LS200	61p	PCF80	58p	74145	70p	LA-5153L	180p
4060	16p	74LS229	17p	74LS240	62p	PCF200	135p	74153	45p		
4061	16p	74LS230	17p	74LS241	60p	PCF801	110p	74155	45p		
4062	16p	74LS231	17p	74LS242	70p	PCF802	57p	74157	45p		
4063	16p	74LS232	17p	74LS243	64p	PCF806	115p	74160	50p		
4064	16p	74LS233	17p	74LS244	64p	PCF200	100p	74164	50p		
4065	16p	74LS234	17p	74LS245	64p	PC81	54p	74167	35p		
4066	16p	74LS235	17p	74LS247	50p	PCL82	63p	74173	50p		
4067	50p	74LS242	39p	74LS248	50p	PCL84	50p	74174	70p		
4068	50p	74LS247	39p	74LS249	92p	PCL85	55p	74175	65p		
4069	16p	74LS248	39p	74LS250	80p	PCL86	55p	74176	45p		
4070	16p	74LS251	39p	74LS251	50p	PCL805	55p	74180	50p		
4071	16p	74LS252	39p	74LS252	48p	PL32	45p	74186	45p		
4072	16p	74LS253	39p	74LS253	48p	PL36	32p	74197	45p		
4073	16p	74LS254	39p	74LS254	48p	PL38	32p	74199	45p		
4074	16p	74LS255	39p	74LS255	48p	PL42	32p	74200	45p		
4075	16p	74LS256	39p	74LS256	48p	PL44	32p	74201	45p		
4076	16p	74LS257	39p	74LS257	48p	PL48	32p	74202	45p		
4077	16p	74LS258	39p	74LS258	48p	PL52	32p	74203	45p		
4078	16p	74LS259	39p	74LS259	48p	PL54	32p	74204	45p		
4079	16p	74LS260	39p	74LS260	48p	PL58	32p	74205	45p		
4080	16p	74LS261	39p	74LS261	48p	PL62	32p	74206	45p		
4081	16p	74LS262	39p	74LS262	48p	PL66	32p	74207	45p		
4082	16p	74LS263	39p	74LS263	48p	PL70	32p	74208	45p		
4083	16p	74LS264	39p	74LS264	48p	PL74	32p	74209	45p		
4084	16p	74LS265	39p	74LS265	48p	PL78	32p	74210	45p		
4085	16p	74LS266	39p	74LS266	48p	PL82	32p	74211	45p		
4086	16p	74LS267	39p	74LS267	48p	PL86	32p	74212	45p		
4087	16p	74LS268	39p	74LS268	48p	PL90	32p	74213	45p		
4088	16p	74LS269	39p	74LS269	48p	PL94	32p	74214	45p		
4089	16p	74LS270	39p	74LS270	48p	PL98	32p	74215	45p		
4090	16p	74LS271	39p	74LS271	48p	PL102	32p	74216	45p		
4091	16p	74LS272	39p	74LS272	48p	PL106	32p	74217	45p		
4092	16p										

THE LEADING EDGE

SATELLITE BROADCASTING

Much has been happening, and equally important *not* happening, in cable and satellite television. First, the background, which now seems to have been conveniently forgotten in Government quarters.

In May 1981 the Home Office published a report on DBS, Direct Broadcasting by Satellite into homes. That report was prompted by the often-quoted WARC plan drawn up at the World Administrative Radio Conference held in Geneva in 1977.

This plan gave Britain, like most other countries, five channels, in the 12GHz band, for DBS. It also gave Britain an orbital slot, at 31° West, for a satellite. So far so good. But the report also gave some warnings, now apparently long forgotten, about the practical difficulties of running a DBS service.

The 31° West slot means that the UK satellite will be hanging in geostationary orbit over the Equator off the coast of Brazil. Dish aerials on roofs or in gardens will have to sight on that invisible spot in the sky. The Home Office warned that aerial alignment would have to be kept to within about 0.5 degrees and offered the reminder that in comparison the alignment of u.h.f. television aerials is far, far less critical.

The Home Office engineers went on to explain that GHz signals will not travel through ordinary roof tiles. This means that loft-type mounting is impractical, unless the roof is re-tiled with special electromagnetically transparent material.

The Home Office engineers also offered a guide to how easy it would be for a householder to find a suitable site for a dish aerial, with a view of the satellite unobscured by buildings, hills or even leafy trees. All will block the microwave signals.

At about 3pm on or about 13 October, the sun in the sky appears to an observer in the UK to be in the same position in the sky as that which a satellite in the orbital position assigned to the UK will occupy. The same test holds good at around 2pm on 2 March. You will be surprised, if you look for the sun at those times, to find how low in the sky it is hanging.

Assuming the sky is clear and the sun shining, only those parts of your house or garden in direct sunlight will be suitable spots for an aerial. If only part of the roof is in sunlight, it's tough luck if an aerial will look ugly, or be hard to secure, in that sunlight area. That's the only place you can put it.

SERVICE COSTS

In March 1982 the Home Secretary, then William Whitelaw, gave the BBC two channels for DBS. One was to be subscription

service and the other financed basically by licence fee revenue.

At first the BBC was overjoyed. But soon the cold hard reality sank in. The Home Office told the BBC that it had to rent a satellite from a consortium, called United Satellites Ltd., of British Aerospace, British Telecom and GEC Marconi.

The BBC winced when it heard the cost; a rental of £12.2 million per channel per year over seven years. That meant nearly £25 million a year on transponder rental for two channels before even a single penny was paid for programming. The BBC got cold feet and eventually opted out.

The Home Office then threw the offer open to the commercial TV companies, but insisted that private industry be involved as well. They knew the BBC and ITV management would fight like cat and dog and achieve nothing unless held in check by a third party influence. The two-channel service was expanded to three-channels so that the three parties would have fair shares of the programming.

Since July last year the future of DBS has been in the hands of the so-called Group of 21. The BBC has a 50 per cent share, the 15 ITV companies 30 per cent and the remaining 20 per cent is split between Consolidated Satellite Broadcasting Ltd., Granada TV Rental, Pearson the publishers, Thorn-EMI and Virgin.

The first thing the Group of 21 did was check the price of satellites. They found it had risen from £24.4 million for 2 channels, to £80 million a year for 3 channels.

Members of the Unisat Consortium made it clear, informally, to the press, that they were worried about the high prices being quoted, but had their hands tied by the Home Office. United Satellites, the holding company representing British Aerospace, British Telecom and GEC Marconi, has to be the official mouthpiece. All press enquiries have to be referred to Unisat.

I tried enquiring. Daniel Gruneberg, the man in charge at Unisat, made his position clear. The cost figures quoted in the press he said were "nonsense"; not just the currently quoted £80 million per year for three channels, but the original £24.4 million per year for 2 channels. That's odd, because it was the BBC who originally quoted the £24.4 million!

As the BBC were being asked to pay it, they should surely have been in a position to know. Gruneberg told me that in the past he had given briefings to journalists, but they had just "gone away and printed rubbish". So now he does not give briefings.

I then put the point to British Aerospace, British Telecom and GEC Marconi separately. If the Unisat mouthpiece thinks that

briefing journalists verbally produces "printed rubbish", then the consortium should produce a written briefing sheet on the crucial matter of satellite costs. That was a month ago, and so far I've heard nothing.

Meanwhile, behind the scenes, the Group of 21 is lobbying the Home Office to throw the contract for a DBS satellite open to tender. If that happens, one of two things will happen. Either a foreign satellite maker will win the contract, at around half the price being quoted by Unisat, or Unisat will drop its price to around half.

SIGHT AND SOUND

In what looks like a desperate attempt to stimulate some fresh confidence in the idea of a British satellite broadcasting direct into British homes, the members of the Unisat consortium have recently been trying to plant the idea in receptive minds that it is much easier to receive signals than the original Home Office report suggested. The deliberately leaked word now is that 12GHz signals *could* be received on a set top aerial, through a window, or by a loft aerial, through roof tiles.

It's true that receiver front end technology (mainly f.e.t.s) has improved greatly since the 1977 WARC conference. The 240W transmitters planned for Unisat will now be able to serve smaller dishes on the ground. But the laws of physics haven't changed. Either 12GHz signals will go through conventional roof tiles or they will not. A test, with a land-based transmitter, a receiver and a few roof tiles in between is all that is necessary.

The talk of a set top aerial is just plain daft. Of course, an aerial on top of a set will pick up signals through glass (provided it is unleaded), but only if there is direct line of sight between the aerial and the satellite and if no-one has dusted the aerial and moved its position by more than a degree or so. How many people have their TV sets in a room next to a window that is in direct line of sight with the sun at 3pm on October 13?

One further spanner has now been thrown in the works. The British Government decided, in November 1982, that any British satellite service must use the MAC transmission system developed by the IBA, instead of the Extended Pal system proposed by the BBC.

To cut a long, and well-worn story short, MAC (Multiplexed Analogue Components) separates the colour and black and white picture signals in *time*, rather than *frequency* as in existing colour TV systems. The sound is in digital code, slotted into the gaps in the video waveform.

British and other European broadcasters plan to use PCM digital sound. But the snag with PCM sound is that it falls apart on a go/no-go basis when the signal strength drops, for instance in poor weather/or if the aerial is misaligned (or behind roof tiles?). The picture, being analogue, gets progressively more snowy but the sound just switches off.

British Aerospace recently mounted an impressive demonstration which showed how modern receiver technology can squeeze acceptable pictures from a DBS signal, even in poor conditions, and as far away from Britain as the South of France. But, significantly, the demonstrations did not involve sound.

DELTA LINK

In America, Dolby Labs, best known for their analogue tape noise reduction system, have proposed an alternative approach to PCM. This is an update on the old idea of Delta Modulation, where only the signal changes are coded. The snag with Delta Modulation is that sampling has been much faster than for PCM, up to several hundred thousand times a second. Dolby used the old idea of Adaptive Modulation, where the coding steps are made of variable size and the transmitter sends a control signal which tells the receiver what size each step should be.

Normally, this would introduce unwanted background noise into the sound, and any error signal interfering with the control channel will knock out the system. Dolby solved the problem by using three bit streams instead of one. One runs slowly

and controls the step size by second; another runs slowly and controls the amount of pre-emphasis to keep the wanted signal above background noise; the third signal runs fast and carries the audio signals.

A memory circuit in the transmitter introduces a delay in the audio signal which gives the slow-moving control signals a chance to cope with the rapid changes of sound. The obvious advantage is that the extra expense, in the memory delay, is in the single transmitter, not the millions of receivers.

The remarkable thing about Dolby Delta Mod (and I have heard it demonstrated) is that when the signal is contaminated with errors, the sound degrades like an analogue sound signal. In fact it is very much like listening to a gramophone with a fluffy stylus.

The advantage of Delta Mod obviously appealed to Australian broadcasters. They chose MAC, but B-MAC with Dolby Delta Mod instead of C-MAC with PCM. When I reported this in print, the IBA jumped like a scalded cat, to defend C-MAC and downplay the Australian decision. Significantly, the Australians responded.

According to the Department of Communications in Australia, and I quote: "There is a definite advantage with the Delta Link system when operating at low receiver power, due to the very graceful degradation of subjective performance, compared to the rapid onset of irritating click noise with the C-MAC PCM sound". In other words the Australian broadcasters heard what I heard when Dolby Labs in Sarf

Francisco demonstrated Delta Modulation to me with deliberately degraded signal strength.

Perhaps instead of writing angry letters defending C-MAC PCM, the IBA could join with United Satellites to mount a demonstration of satellite transmission with PCM sound. They could then deliberately degrade the signal with aerial misalignment, and simulate bad weather and leafy trees in the signal path. We could then hear and see for ourselves how the system holds up in practice. It may well be significant that when GEC Marconi recently ran a test of its proposed satellite transponder, the press were not invited.

UPDATE

The Group of 21 have decided not to proceed with its planned British Satellite Service (see News & Market Place page 8). This follows pronouncements from a Government select body that "the potential demand is likely to be too small and the financial risk too great". Also, in their view, the Government constraints being imposed on them are too restrictive.

However, most European countries are still planning a satellite service using low power equipment. Now the big question is will the British DBS group be allowed to use cheap, low powered technology from abroad?


More on this subject in a later issue.

Next month we'll look at what is happening, and also equally to the point, *not* happening, in Cable TV in Britain.

BARRY FOX

SEPTEMBER FEATURES...

NEW SERIES TRANSDUCERS

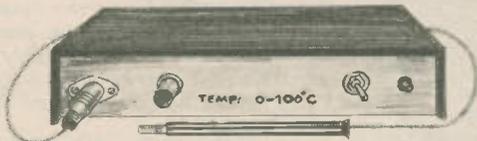


This series will begin with relatively simple projects, such as temperature measuring devices, and progress to such topics as strain gauges, pressure gauges and flux density indicators. The units may either be used as stand-alone devices, or in conjunction with a home computer.

EVERYDAY ELECTRONICS and computer PROJECTS

SEPTEMBER 1985 ISSUE ON SALE FRIDAY, AUGUST 16

PERSONAL STEREO P.S.U

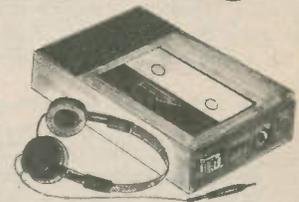Build this little project for infinite listening pleasure without running down the batteries—or running up the cost!




CARAVAN ALARM

A system designed to protect the caravan itself, but also articles left both inside and outside. As it is based on a "loop-alarm" it could also be used for other security applications.

FRIDGE ALARM

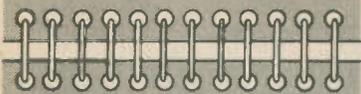Ever found the fridge door held open by a misplaced bottle or simply forgotten by young children as they pour their own drinks? Then you need our alarm to prevent the food being spoilt. It's simple and cheap and will warn you if the door is left open for more than a minute.



INDUSTRY NOTEBOOK

By Nexus



Bust . . .

First the bad news. The great *personal* computer boom has gone bust. Perhaps I played a small part in this by suggesting last Christmas that intending buyers would profit by delaying purchase.

There was nothing clever in this advice. The price war had already gained momentum during 1984 and fears had already been expressed that the peak trading month was unlikely to peak this time round. So prices tumbled to the benefit of the bargain hunter.

Huge unsold stocks during the first quarter of this year inevitably created ripples back down the line to manufacturing sub-contractors and component suppliers, short-fall in cash flow, plummeting share values, prospects of re-grouping, lay-offs, imminent bankruptcy.

One recalls earlier consumer crazes. The yo-yo, the hula-hoop and, more recently, the skateboard, that puzzle cube the name of which is already forgotten, and the BMX bike which still appeals and may enjoy permanency. I hesitate to include the PC as a passing novelty but the craze, if that is the name for a particular human phenomenon, is over.

Computer literacy is now much greater than that of the early 1980s and buyers will be much more discriminating. The big problem for those serving the low-price end of the market is how long they can survive once the Asian manufacturers start flooding the world in the manner we have already seen in pocket calculators. Again, incidentally, benefiting the buyer.

It is a pity that Sir Clive Sinclair, highly profiled as a superman in electronics, is now a victim of a fickle public. Hardly ruined but now dented in reputation. But he is still to be praised for creating a completely new business sector in electronics and for stimulating public interest in computers.

His present set-back is nothing new to him. His progression of ups and downs is closely linked with his obsession for tiny products. His first was the "smaller than a matchbox" Micromatic radio, which was profitable; his pocket calculators, success-

ful at first before intense competition set in. Then there was his early micro-TV, a comparative failure; his Black Watch, a disaster; his present flat screen pocket TV, which may yet prosper; and finally, his revolution in personal transport, the C5, gravely disappointing following an overheated publicity build-up.

But Sir Clive remains full of ideas for the future and, on the surface at least, is not discouraged by past failures and present doldrums. And those of us who were home-constructing in the 1960s and 1970s still remember with affection (sometimes exasperation!) his hi-fi modules and kits which were very often our first experience of solid state technology and particularly of early integrated circuits.

The personal computer business is now in a chaotic state. I often think there must be better ways of organising our affairs. Central planning, Soviet style? They would still be talking about it. Chaotic as free enterprise may appear, it does in practice deliver the goods faster and cheaper than planned economies and provides great opportunities for innovators to exercise their skills and investors to take calculated risks on profit and loss.

. . . and Boom

While consumer electronics has its periodic horrors the capital goods sector is doing quite nicely. 1984 was a record year with output up 19 percent at £3.2 billion, exports up 9 percent at just over a £1 billion. But imports were up 18 percent at £777 million carrying the warning that competition is still the name of the game.

The Paris Air Show, as much to do with electronics as aircraft, once again demonstrated that avionics is still the forcing ground for innovation in the electronics industry as a whole. The first miniature computers, shoe-box size, were being fitted in aircraft all of 20 years before Sir Clive brought his first model into the home.

GEC Avionics is the largest firm in Europe in this specialised market. With 12,000 people on the payroll its products sell at the rate of over £1 million per day with nearly £500,000 a day coming from overseas customers. The company also claims to have the widest range in avionics of any company in the world.

Even so, GEC Avionics still needs partners in many projects. One such is the link-up with Lockheed on world sales of a budget-priced Airborne Early Warning system based on Lockheed's C-130 Hercules aircraft, of which hundreds are in use throughout the world, fitted with GEC Avionics APY 920 Mission Avionics derived from the system developed for the British AEW Nimrod. Potential export sales, say GEC, could well exceed the whole cost of the British AEW programme.

Another GEC company, Marconi Radar Systems, has teamed up with Raytheon in tendering for the US Federal Aviation Agency Radar Replacement (FARR) programme. This involves the supply of up to 50 3-D solid-state unattended L-band radar systems for installation in the USA on a budget of some 500 million US dollars.

Early this year Racal Radar Defence Systems and Selenia in Italy teamed up on avionics equipment for fitting in a variety of aircraft. And, again at Paris, Smiths Industries Aerospace and Defence Systems announced a cooperative agreement with VDO of Germany and Thomson CSF of France on avionics for the new European combat aircraft. This agreement allows for later participation of Italian and Spanish avionics companies.

Smith Industries is one of the world's leading avionics companies with 60 percent of output exported. Pointer-on-dial cockpit instruments are no longer the mainstay of the business and may disappear entirely by the end of the century, displaced by the all-electronic display on the face of a cathode ray tube.

An example is the flight deck of the British Aerospace Advanced Turbo Prop (ATP), the first orders for which were announced at the Paris Show. Instead of the usual multiplicity of dedicated instruments most have been replaced by Smiths with four CRTs which can be switched to various roles as required by push-button. The push-buttons or keyboard may themselves be relegated to standby emergency use if and when Direct Voice Input is perfected. With DVI the flight crew will just tell the system what instrumentation is to be displayed and hey-presto it appears.

The advantages of the CRT displays don't end at the flight deck. Unseen and largely unthought of by the passenger is the costly business of ground maintenance. With dozens of different pointer instruments in each aircraft, spares holdings are expensive as, indeed, are the skilled mechanics to repair them.

With the new system a single CRT module as spare is all that is required and the airport electronics trouble-shooter can cope with that as easily as with the other systems he normally looks after. To him, it is just another black box. In fact expensive instrument mechanics at airports are all set to go the same way as those whose sensitive fingers once tweaked the relays in electro-mechanical telephone exchanges—retraining or early retirement.

In Brief

Electronics has done well in this year's defence estimates. Although the total equipment budget for the armed forces has been increased by only 3.8 percent the electronics spend is up by nearly 10 percent. Five years ago electronics accounted for 28 percent of the total spend. Now it is 36.5 percent.

The USA is still Britain's top export market helped along by vigorous marketing. A recent breakthrough is BICC's 10 million dollar contract for the supply of optical fibre cable for the US trunk network. The fibre will come from the BICC/Corning factory at Deeside and the completed cable from BICC's plant at Blackley, Manchester.

Another breakthrough is the Cable & Wireless partnership with Tel-Optik of the USA for the first private fibre-optic link between the UK and USA.

Robotics Review *Nigel Clark*

ONCE again we start with SCARAs as they are quickly becoming an option for people wishing to buy a small robot. Only a few months ago there were none on the market and now there are five.

Two months ago we had details of the Serpent, last month it was IVAX and the more powerful RTX. It is now the turn of **Reekie Technology** and **Feedback Instruments**.

John Reekie, who last year left **Colne Robotics**, the company he had created, to set up **Reekie Technology**, has chosen a SCARA to be one of the three products which are to be the first launched by the new company.

Cepek 1 has five axes plus an optional gripper, with the height being manually adjusted and other axes operating under computer control. It can lift 2kg and has repeatability of ± 0.25 mm. The drive is either all electric, steppers, or electric/pneumatic.

Vertical movement is limited to 250mm, with the shoulder and elbow being able to move through 200 degrees and 180 degrees. The gripper can rotate through a full 360 degrees and has 50mm of vertical movement. That gives it a working envelope with an arc of 200 degrees at a radius of between 100mm and 350mm.

The software for Cepek was developed by **TA Education**, of Sheffield. Reekie says that the arm will work with any micro but software has as yet only been developed for the BBC B, IBM PC, Apple IIe and Olivetti M24. Two programs are available, SCARA basic which comes with the Cepek package and SCARA Advanced which will cost an extra £130.

BASIC allows all the usual controls, such as keyboard instructions, edit, save and load plus three point variable ramping to allow various rates of acceleration and deceleration, continuous status display and a split screen display for all facilities and options. Additional features of the Advanced include point-to-point teaching, variation of speed of each axis and the creation of sub-routines. Costing about £3,000 the Cepek is aimed at the usual light industrial and education markets.

... vision, speech and voice recognition ...

Reekie's other products include the Reekie Universal Robot featured in *Practical Electronics* in recent months and selling in kit form at £249. Education and hobbyists are seen as potential customers.

The company has plans for extending RUR's capabilities with a number of additions, which will include vision, speech and voice recognition.

A conventional arm has also been developed. Looking remarkably like the Armdroid of Reekie's previous company it has

five axes and a gripper and uses stepper motors. However at £250 it is about half the cost of the Armdroid and is toothed belt driven, rather than cord.

Meanwhile back to the SCARAs, Feedback, the company which took over **Powertran**, has announced its own version with the snappy title of PW801. At a price of about £4,500 for the robot plus £1,500 for the workcell, it is again aimed at the education market.

It has four axes, the shoulder and elbow being powered by d.c. motors, controlled by shaft encoders, and the gripper rotation and vertical movement powered by stepper motors. The working envelope has an arc of 240 degrees with a radius of between 190mm and 380mm.

Software is available for the BBC B, Apple IIe and Apricot.

The machine has been designed to work in an educational workcell known as Pedro, which is said to stand for *pedagogic robotic workcell*. The software however has been designed to cover specific curricula and the package includes a tutorial text and a manual of hardware and software exercises. The whole package will cost in the region of £6,000 putting it in the colleges of further education area.

... possible to change grippers ...

Colne Robotics is developing a larger, more sophisticated version of its Armdroid 1. Already christened Armdroid II, it should cost about £3,000. Like its smaller brother, it is a jointed arm powered by stepper motors with additional control from optical encoders.

Unlike the earlier version however it has six axes plus a gripper, the extra axis being on the wrist giving it pitch, yaw and

rotation and is chain and toothed belt-driven. Its lifting capability is 500 gms and has an accuracy of 2mm. It will be possible to change grippers.

With an onboard processor it is intended to provide a comprehensive control language allowing it to operate in joint-offset or cartesian programming modes and a networking facility. Launch is expected towards the end of this year.

Responding to the need for more software Colne has launched its version of Forth for the Armdroid 1. Known, unexpectedly, as Colneforth, it is said to be highly interactive, emphasising the communication needed between user and robot.


Using the language each joint can be given commands allowing each axis to achieve specific positions and with FORTH's structured approach, complex sequences can be built up in a form which is simple to edit, extend and save. At a cost of £75, Colneforth is available for the BBC B and Commodore 64.

... a mobile base ...

At the less-expensive level, Alfred (published in *Everyday Electronics*—Nov. 84 to Jan. 85) from **Robot City Technology** of Milton Keynes is getting some extra facilities later this year. When introduced the makers said that Alfred had been designed in modular form so that it could be added to.

The first of these additions is expected in the autumn when a mobile base becomes available. Following that will be an onboard processor. At present it can be controlled from the BBC B or any micro with an 8 bit I/O port.

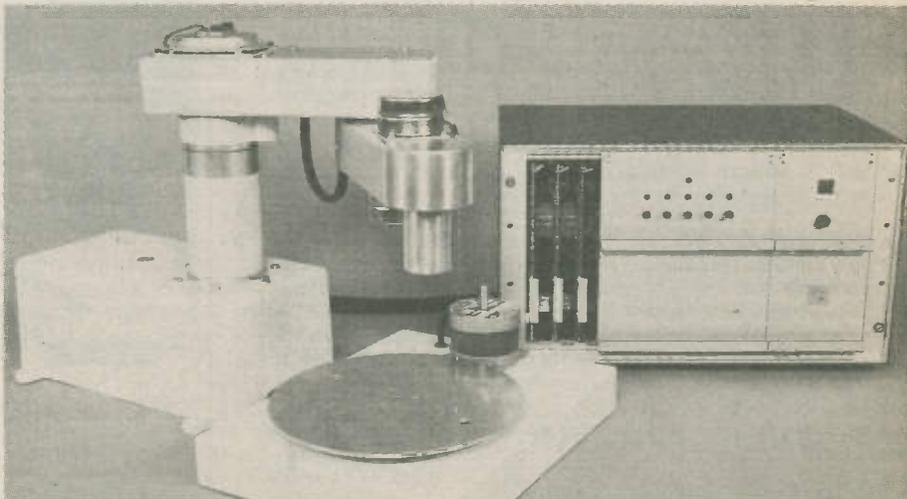Feedback Instruments' PW801 SCARA robot and Pedro workcell



PLOTTER

REVIEW...

D. WHITFIELD MA MSc CEng MIEE

DRAWING PICTURES should be a 'natural' application for the high resolution graphics facilities found on many of today's small computers. However, a standard computer keyboard is not exactly the most natural drawing instrument yet developed. Indeed, if the picture has to be built using a series of BASIC PRINT statements, the 'artist' either needs to be some form of software enthusiast, or (more likely) he loses interest very rapidly.

What is needed, therefore, is a more natural way of interacting with the computer to produce an image on the screen. After all, the computer is meant to be a tool that we use, rather than the other way round. It should adapt itself to the ways of the artist, rather than vice versa. This review looks at the Image Plotter, a product from Reekie Technology which allows you to produce pictures on the screen, but without having to use the keyboard as a 'pen'. First, however, a little background.

LIGHTPEN OR TABLET?

There are actually quite a number of different ways in which the natural hand-and-eye coordination inherent in freehand drawing can be supported by the computer. The best known of these is probably the lightpen, where the artist literally draws on the screen using a special pen linked to the computer. Using the CRT controller within the computer, linked to a light sensor in the pen, the artist's drawing movements are followed on the screen. This sounds easy, but it relies on being able to access the CRT controller in the computer, which is not always possible. Also, performance can vary significantly between different monitors, and even between different colours on the same monitor.

An alternative to the lightpen is the graphics tablet. With this the computer senses the position of the artist's pen on a drawing surface (the tablet), and then produces a corresponding display on the screen. In some situations this can be particularly convenient because it allows parts of existing drawings to be traced. Also, there are many different ways of sensing the position of the pen, depending on the accuracy required and the interface facilities on the computer. The Image Plotter is an example of this graphics tablet approach to computer drawing for the BBC Micro model B.

IMAGE PLOTTER


The Image Plotter system arrives complete with software (on tape or disc), a drawing arm, a calibrated overlay sheet, and a set of instructions. The overlay sheet forms the basis for the actual 'tablet', and measures approximately 420 x 630 mm. It is provided with self-adhesive strips to attach it to a smooth work surface or to a convenient backing board. On the overlay there is a squared grid approximately 320 x 250 mm, a number of calibration marks, and an area for attaching the drawing arm control unit.

The drawing arm is a pantograph arrangement which is attached to a small control unit at one end, and to the drawing stylus at the other end. On the control unit there are switches for mode control (toggle) and point plotting (pushbutton). The lead to the computer's analogue port also emerges from the control unit. After the overlay sheet has been fixed to a working surface or board, the control unit is attached to the sheet using a number of self-adhesive pads. One end of the pantograph arm is therefore fixed, and the computer uses potentiometers mounted on two of the pivots of the pantograph to follow the stylus position. The reach of the arm is approximately 600 mm and this allows it to cover the squared drawing area with ease. Overall this is a simple but very effective arrangement, and is best set up permanently on a piece of chipboard or similar material.

SOFTWARE

The hardware is only half the story when it comes to actually drawing pictures. The Image Plotter software provided with the system is really what makes it all so useful. The software is provided in three parts and a form which can be listed, and thus can be modified or extended for particular applications. The first part gives a load screen, and sets up various character definitions and machine code routines, before CHAINing in the second part to calibrate the plotter.

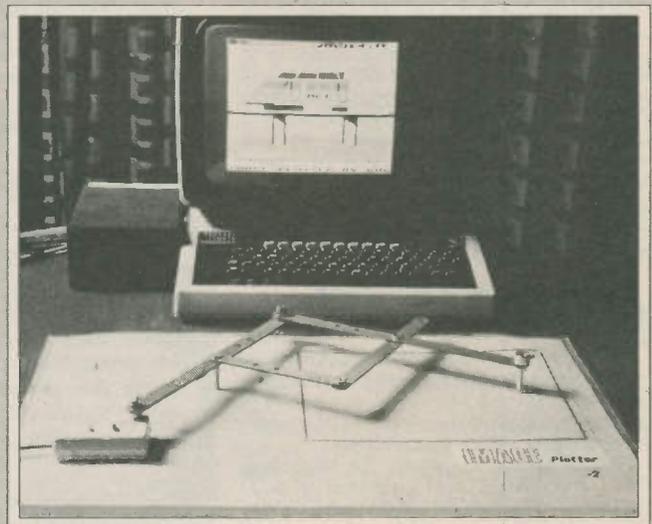Calibration is a question of relating the potentiometer settings on the pantograph to the position of the drawing



"A more natural way of interacting with the computer to produce an image on the screen"

stylus. The problem is that the components used in individual plotters and BBC Micro's all vary, even if only slightly. In addition, the ADC performance varies as the computer warms up. However, this can all be corrected in software by measuring the voltages from the arm's potentiometers when the stylus is in a known position. The eight calibration marks on the overlay sheet are used for this purpose. The software offers the choice of using the preset calibration values, a previously saved set of values, or of recalibrating the plotter. The latter involves moving the stylus to each calibration mark in turn, as indicated on the screen, and pressing the plot button at each point. This process is quick and easy, and when complete you have the opportunity of saving the new values for next time. When satisfied with the calibration, the final part of the software is CHAINED.

From now on all interaction with the system (except when entering text for labels on drawings) is via the drawing arm. The initial screen is essentially blank, with a row of sixteen boxes across the top, and a cross-hair cursor to indicate the current stylus position. The blank section is the drawing area, and the boxes at the top represent a menu. Selecting an option from the menu is a simple matter of moving the cursor into a box and pressing the plot button. It is a shame that the box positions are not marked on the overlay, but nevertheless the procedure is still very convenient. There are actually more options available than can be shown on one menu, and consequently switching between the menus is an option offered on each menu. Rather confusingly, the four menus are called 'modes' in the manual, but they are not related in any way to the micro's screen modes, and I rather prefer to think of them as simple 'menus'.


DRAWINGS

It is worth saying at the outset that it takes less than half an hour to become proficient with the Image Plotter, which gives some idea of its ease of use. At the start you are presented with a blank drawing sheet, which has a cursor and menu boxes as its only features, so how do you go about drawing on it?

The first thing to try is the way in which the cursor follows the drawing arm. With the mode switch in the 'move' position, the cursor moves with the arm. When you are happy with the way that the cursor behaves, the next thing to try is selecting an option from the menus. There are two main types of menu options: palette functions (which determine colour), and brush functions (which set the style or shape of the graphics). Selecting a menu option is simply a matter of moving the cursor to the appropriate box and pressing the plot button. The boxes are identified by numbers 1 to 16 (left to right) in the manual.

On menu 1, as on all four menus, box 14 moves the user on to the next menu, and box 15 displays the current menu number. Box 16 always shows the currently selected brush and the colour that the graphics will be drawn (initially black). Changing the drawing colour is easy, and uses boxes 1 to 8 on menu 1; move the cursor into the box of the chosen colour, and press the plot button. The single dot brush set up at the start allows you to draw like a pen on paper. To draw dots, simply move the cursor to the desired position and press the plot button. For drawing lines, change the mode switch from 'move' to 'plot', and now the line will follow the cursor. Switching back to 'move' is the equivalent to taking the pen off the paper.

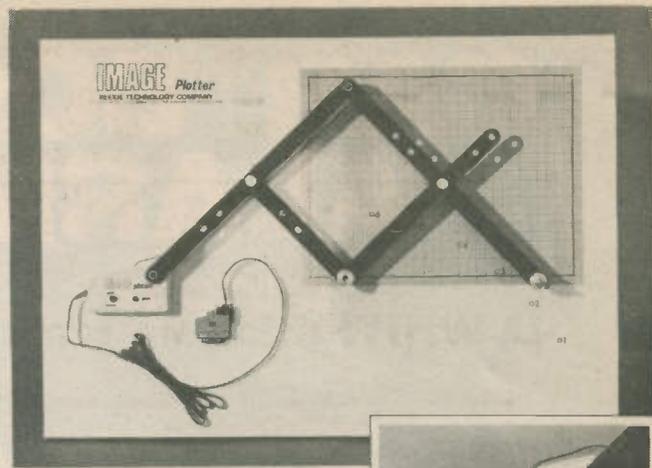Box 9 of menu 1 allows flashing colours to be selected instead of steady colours. The start-up freehand brush is box 10, and box 11 gives a straight line brush. This uses a 'rubber banding' technique which is really very effective, and is nice



A piece of chipboard makes an ideal backing board (Top). Control unit close-up (Right)



to use. The plot button is pressed when the cursor is at one end of the line. From now on, a line is drawn from this point to wherever the cursor is currently positioned. When you are happy with the line position, simply press the plot button to fix the line in place. The cursor is now free for drawing another line, or for selecting another menu option. Box 12 allows text to be typed in and then moved around the screen at will; the same text may be printed as often as required, and in any colour. The final option in menu 1 is to clear the whole drawing sheet; very wisely this has a double check facility!

The second menu provides a number of other shapes, which make great use of the rubber banding technique just described. The dotted line option works as for solid lines. Solid triangles, outline triangles, and dotted triangles are drawn by plotting three points. Rectangles are produced by plotting the two opposite corners, while circles are defined by their diameters. Two 'air brushes' are provided to add shading and subtlety, while box 13 allows an enclosed area to be filled with a colour.

The third menu allows you to change the palette make up, and change the plotting logic. This is designed to mirror the options of the PLOT command in BBC BASIC. The fourth menu allows the flash rates of the flashing colours to be varied, and pictures to be loaded or saved on the filing system. Once saved, a suitable screen dump can be used to output the image to a printer.


CONCLUSION

The Image Plotter is certainly easy to use, and can be recommended for all types of user. After about half an hour, you can safely put the manual away and concentrate on drawing. The performance is good, with no obvious feeling of having to wait for the computer while drawing. To see the results at their best really requires a colour monitor, such as the capabilities of the system. If you want a system which is simple but effective, and allows you to get the very best out of the BBC Micro's graphics facilities, then you should give careful consideration to the Image Plotter.

The Image Plotter is available in two forms, either as a kit at £37.95 or ready built from £44.45 (prices include VAT and p&p). From: Reekie Technology Company, Beaufort Road, Twickenham, TW1 2PQ (01-892 2877). (State tape or disc for software).

CAR BOOT ALARM

D. STONE

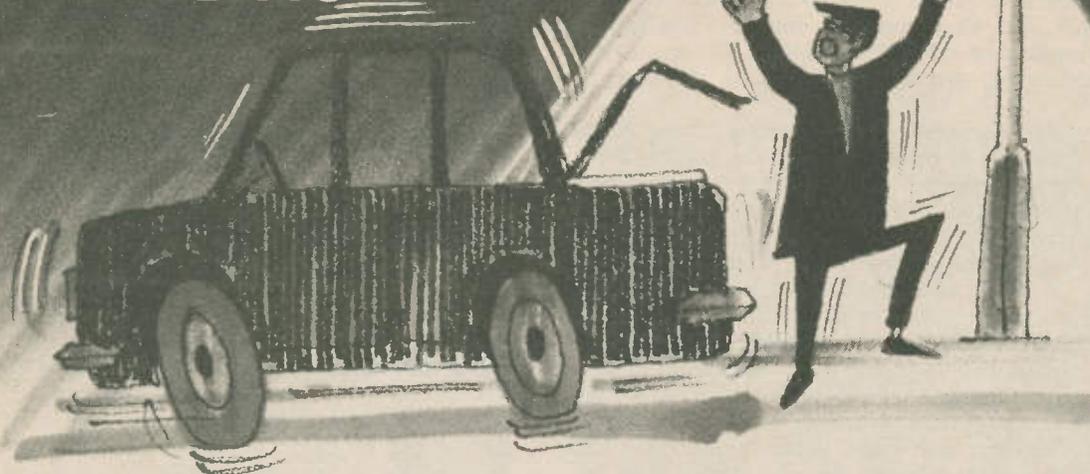

WHEN ASKED to design an alarm to operate in case of attempted theft from a car-boot, the first idea that occurred was to make use of the inbuilt courtesy light wiring. However, since the model of car—like many others—did not have a boot-light fitted as standard, some more thought was needed.

After a little experimentation with different triggering methods, it was decided to use a light-activated device. This operates on the elementary principle that when the boot is opened light is allowed in, and that when the boot is shut, it is dark. The circuit also had to be sensitive enough to trigger at night by street-light illumination.

CIRCUIT DESCRIPTION

The inverting input of IC1—a standard 741 operational amplifier—is held at half the supply voltage by the potential divider formed by R2 and R3; see Fig. 1. IC1 is wired as a comparator with its non-inverting input connected to the photo-Darlington pair TR1 and TR2, and resistor R1.

When light falls on TR1, the transistor passes a small current. This is amplified by TR2 and converted to a voltage drop by R1. As the voltage rises above the threshold voltage, governed by the potential divider, the output of the comparator changes state, and goes high. This output is scaled suitably by R4 and R5. This voltage level is now in turn converted to a base current by R6 to drive output transistor TR3. This transistor then drives either the horn, via relay RLA, or the indication l.e.d. D2.

In the "On" position, the relay will latch, as RLA1 shorts TR3; and even if the boot is immediately closed again, cutting off light from TR1, the horn will continue to sound until either S1 or S2 is switched. In the "Standby" position, the l.e.d. will simply indicate whether the boot is open or closed.

CONSTRUCTION

The circuit can be built using the p.c.b. layout, as shown in Fig. 2, or alternatively, by making use of matrix stripboard. As usual, the circuit should be built following the convention of resistors and capacitors first, followed by the semiconductors.

The majority of the prototype circuit was mounted in the car boot, with the relay being situated near the horn under the bonnet. The l.e.d. indicator, D2, was mounted on the dashboard—see the layout suggested in Fig. 3.

This layout, as it stands, is suitable for use with all vehicles which have a *negative earth* supply. If this is so, the boxed part of the circuit may be grounded by taking a flying lead from the "OV" point on the p.c.b., and bolting this lead to bare metal on the vehicle bodywork.

If the car has positive earth wiring, the circuit can still be used, but obviously great care is necessary to ensure that the whole of the circuitry is electrically isolated from the chassis. The simplest approach would be to mount the p.c.b. in a plastic box, and to run separate leads from the battery to provide the +12V and 0V supplies. If this is done, it is essential that some other warning

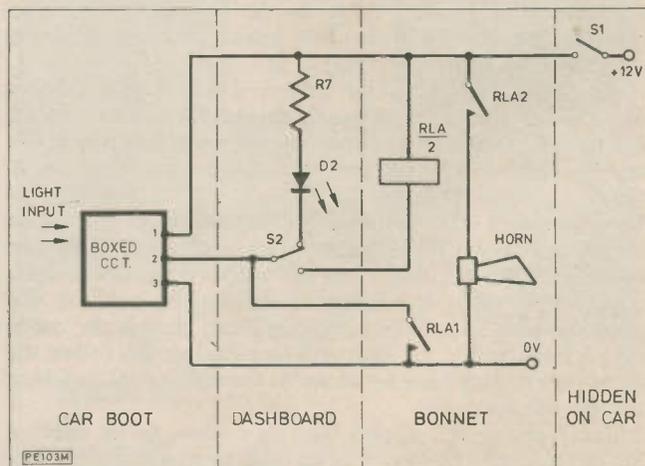


Fig. 3. Suggested layout for the system, showing the physical location for the elements of the circuit

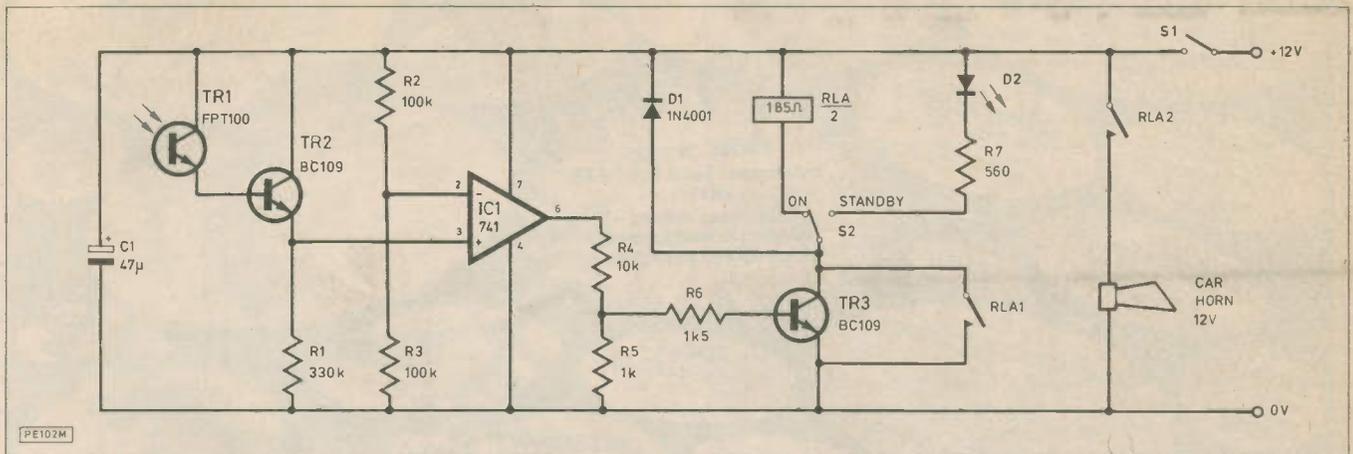


Fig. 1. Complete circuit diagram for the Car Boot Alarm

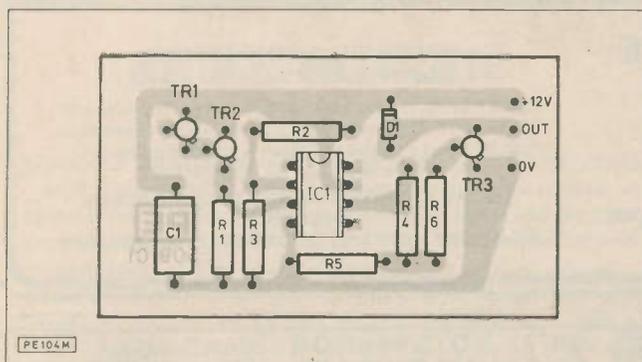


Fig. 2. Component layout on the printed circuit board, for the boxed part of the unit. The p.c.b. is available from the PE PCB Service, as shown in the components list

COMPONENTS . . .

Resistors

R1	330k
R2, R3	100k (2 off)
R4	10k
R5	1k
R6	1k5
R7	560

All ¼ Watt ±5%

Capacitor

C1	47µ electrolytic
----	------------------

Semiconductors

D1	1N4001
D2	green l.e.d.
TR1	FPT100 phototransistor
TR2, TR3	BC109 (2 off)
IC1	741 op-amp

Miscellaneous

RLA	Double-pole relay, coil resistance 185 ohms
S1	Single-pole switch
S2	Single-pole changeover switch
Suitable case for boxed part of the circuit; l.e.d. clip; interconnecting wiring; printed circuit board, available from the PE PCB Service, order code 509-01.	

device than the car horn be used—car accessory shops sell suitable units—and that all wiring and component mounting is electrically isolated from the car chassis.

To activate the alarm, S2 is switched to "Standby", and S1 is switched on. The l.e.d. should not be lit: if it is, then there is some light falling on the sensor. When the l.e.d. is out, S2 can be switched to "On", and the alarm is armed.

It is possible to wire the circuit without S1, and have the alarm switched between "Standby" and "On". The sensitivity of the detector is governed by R1: increasing the value of R1 will make the alarm more sensitive.

Initial setting-up will require "tweaking" the value of R1, and the constructor may find it useful at first to wire a 470k potentiometer into the position that R1 will ultimately go.

TESTING

Ensuring that the circuit works properly is obviously best done under real conditions. However, the repeated sounding of the car horn, as the project is tested, is likely to annoy the neighbours, and possibly invite a visit from the police.

The most sensible approach is to substitute a suitable buzzer, or a 12V lamp for the car horn (refer again to Fig. 1), and make adjustments in the workshop. Daylight falling on the phototransistor TR1 should activate the buzzer, and the value of R1 (assuming a potentiometer is used) should be altered until the buzzer always sounds in "normal" conditions of daylight. This (minimum) value of R1 should be measured, using an ohmmeter across the potentiometer removed from the circuit.

This process should now be repeated under subdued artificial lighting, and the new (maximum) value for R1 noted.

From these two readings, it ought to be possible to choose a standard-value resistor which will effectively be a compromise: 330k is suggested, as this worked well in the prototype. The chosen value resistor should be soldered in position, and the finished circuit will then be ready for installation.

IN USE

Once the system is in position, final testing can take place. With S1 closed and S2 in the "Standby" position, the alarm circuit should be checked for proper operation under day- and night-time conditions.

If the alarm is inconsistent, then either R1 or TR1 are likely to be the culprits—assuming that there are no wiring or component errors. However, when the system is in place and working correctly, the alarm should give satisfactory results over a long period. ★

SIREN KIT
Produces a loud swept frequency tone from a 9-15V supply. Enable input for easy connection to alarm circuits. Includes 5in horn speaker **£7.90**
Mini siren (with small speaker & box) **£4.30**

PASSIVE IR DETECTOR
Detects intruders body heat at up to 10m. 12Vdc supply. Output N/c contacts 950 135 **£45.00**

BOXES
Plastic, diecast aluminium

MULTIMETERS
Analogue from **£6.50**
Digital from **£26.55**

DIGITAL LOCK KIT
operates from 5 to 18Vdc supply and gives 5040 combinations. 10 way keyboard supplied. 750mA output. Ideal for disabling car ignition or for door lock when used with 701 150 lock mechanism **£11.50**
701 150 **£14.95**

BELL BOX
Brightly coloured and a deterrent by itself 950 130 **£10.00**

XENON BEACON
12V 170mA Orange weatherproof 950 133 **£10.50**

FREE 28 page catalogue. Send 9x6 SAE NOW!
Telephone orders — Access & Barclaycard RING 01-567 8910 (24hrs)

HIGH SECURITY IR TRANSMITTER/RECEIVER
Operating from 9-15Vdc, both units have 8 switches and will operate only if these have been set to the same code. Receiver provides latched or momentary output. Ideal for car locks garage door openers, burglar alarm switches etc XK119 **£21.75**

CMOS
4001 **16p**
4017 **39p**

LEDS
from **9p**

PRESSURE MATS
23x7ins **£1.70**
29x16ins **£2.60**

TRIACS

ALARM CONTROL UNIT
4 input circuits, 2 instant 2 delayed. Adjustable entry exist and alarm times. Built & tested. Full instructions supplied. Size 180x130x30mm 12 dc supply 950 160 **£26.00**

TOOLS
Side cutters **£2.10**
See Cat. for full range

WINDOW TAPE
50m **£2.50**
Terminators **36p/pr**

CONTACTS
for doors & windows Magnet & Reed Flush 950 140 **£1.05**
Surface 950 142 **75p**

BT Phone connectors starter pack **£9.50**

VERO

PANTEC KITS

BATTERIES
NiCADs eg AA 90p & Chargers

VELLEMAN KITS



ELECTRONICS
13 BOSTON RD
LONDON W7 3SJ
Tel. Orders: 01-567 8910
Enquiries: 01-579 9794
Shop Hours: Mon-Fri. 9am-5pm
Sat. 10am-4pm.

ORDERING INFORMATION:
ALL PRICES EXCLUDE VAT
FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.
LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
GOODS BY RETURN SUBJECT TO AVAILABILITY

CLEF ELECTRONIC MUSIC
THE CLEF CMS

The FULLY programmable digital synthesiser that you can AFFORD
THE NEW CLEF COMPUTER MUSIC SYSTEM is so user programmable that you need a BBC Micro to run it! 32 harmonically programmable oscillators. 32 programmable envelopes. 5 octave touch sensitive keyboard, up to 4 OSC/ENVS per note. Real time sequencing. Massive potential for future software. Complete system (without BBC Micro) **£495** built. Phone or write for details. Modular systems also available.

MASTER RHYTHM PROGRAMMABLE DRUMS

As Published in P.E.

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust. **COMPLETE KIT £79**
STRING ENSEMBLE ROTOR-CHORUS £198.50
ROTOR-CHORUS £98.00
MICROSYNTH P.C.B. & ELECT KITS £86.90
PERCUSSION SYNTH P.C.B. & ELECT KITS £97.90

88/72 NOTE PIANOS SPECIALISTS SINCE 1972
Using Patented electronic technique to give advanced simulation on Piano Key Inertia.
COMPONENT KITS including Keyboard
88 NOTE **£266**
72 NOTE **£234**
The above may also be purchased in four parts.
SQUARE FRONT KEYBOARDS
88 NOTE **£60**
49 NOTE **£29**
73 NOTE **£50**
30 NOTE **£19**
KEYSWITCH ITEMS ALSO AVAILABLE

BAND-BOX PROGRAMMABLE BACKING TRIO

As Published in P.E.

THREE PIECE BACKING BAND
Generates the sounds of three instrumentalists to back Soloists
DRUMS + BASS + KEYBOARDS
Over 3,000 chord changes (60 scores) on 132 different chords - 16 chord sounds. Master Rhythm also required.
FULL KIT £265 BUILT £370

CLEF PRODUCTS (ELECTRONICS) LIMITED
(Dept PE) 67 THORNWAY, BRAMHALL, STOCKPORT, CHESHIRE SK7 2AH
All Demonstrations by Appointment only

CRICKLEWOOD ELECTRONICS LTD
It's no secret!

that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LTD.
40 Cricklewood Broadway NW2 3ET.
01-450 0995 & 01-452 0161
ALL MAJOR CREDIT CARDS ACCEPTED
Telex 914877 Phone or write today

FREE! catalogue

NOW! SUMMER CATALOGUE

SPEED CONTROL KIT FOR MINI-DRILLS

Includes completely assembled control unit in smart box with room for transformer. The only connections to make are 2 wires to a suitable transformer. The control unit will handle 2A continuous, 3A intermittent. **£4.50**
Transformer for above, 15V, 1A continuous, (1.5A intermittent) for smaller type drill. **£2.90**. Brand new stock. The complete controller is advertised by major manufacturer for over £20!

HIGH TORQUE MOTOR FOR MINI DRILLS 12V to 18V, 40W, 1000 rpm per volt 5 pole rotor. Carbon brushes. 50x28mm dia. **£2.90**. (Fits any 35mm plastic film container!)

CHUCK & SET OF COLLETS to 2.5mm for above motor to make an inexpensive drill for PCB work **£2.00**

HSS DRILL BITS WITH SHANKS. 1.0mm - 5 bits for **£1.50**. 0.8mm, or 0.6mm - 5 bits for **£2.50** or 2 of each size (6 bits) for **£2.50**. (Not recommended for glass fibre PCB.)

COPPER CLAD s/s paxolin, 4 pieces (total 100 sq ins) **£1.00**

FERRIC CHLORIDE to make 500ml **£1.10**
CHARTPACK etch resist transfers, 1 sheet each (total 4) light & heavy lines, curves & dil pads **£1.50**
ETCH RESIST PENS (High quality pk of 2, fine & broad tips) **£1.50** or 3 pks **£4.00**.
NI-CAD RECHARGEABLE CELLS - AA - HP7 pack of 4 **£1.50** or 4 packs for **£5.00**. Ex equipment, tested & guaranteed 500mA Hr. Bargain! NI-CAD CHARGER & 4 AA cells + holder **£5.00**
ELECTRET MIC. INSERTS 9mm dia x 6mm with integral amp. Requires normal 1.5V **£1.10** each, or 6 for **£5.00**.
PRECISION THERMISTORS 5 types, any mix for **£2.00**. Approx resistance at 20 degrees C. 5M0, 1M0, 300K, 100K & 1K0.
Please add 80p P&P per order
Many other items for callers or send S.A.E. for stock list.
Goods normally sent by return

CRYDON DISCOUNT ELECTRONICS
40 Lower Addiscombe Road.
Croydon CR0 6AA

DIY ALARM SYSTEMS BUYER'S GUIDE

BRIAN BUTLER

PERHAPS this is the time of year when we are most concerned with home security. As the holiday season gets into top gear so does the nation's expanding band of house-breakers, and lazing in the seaside sun is a total waste of time if you are preoccupied with the vulnerability of your distant home.

As we are so often being reminded these days, burglary is on the increase and the chances of your home being illegally entered is therefore greater, it is estimated that a home is burgled in the UK every 60 seconds.

Of the £180 million worth of burglariously seized goods in 1983, only £7 million worth was ever recovered; on the other hand in 75 per cent of break-ins the value of the haul does not exceed £500.

How then can we best protect our property from unauthorised entry? Perhaps the installation of an intruder alarm would put the mind at rest.

PROTECTION REQUIREMENTS

The degree of protection required is probably the first and most fundamental consideration. For instance CCTV (Closed Circuit Television) is hardly necessary if all you want to protect is your prize petunias—a make/break contact in the conservatory door-frame is more suitable here. In the sections that follow, the main points to be considered when fitting an alarm system will be explained. It should then be a simple matter of fitting the most suitable system for your own requirements. At this point it may prove prudent to contact your local CPO (Crime Prevention Officer) who will point out to you where security improvements can be made in your home. The advice is free and the survey is free. The recommendations may well amount to nothing more than window locks, better door locks and security bolts etc. For the purpose of this guide however we will assume that an alarm system is required. Incidentally, each Police force has its own 'Intruder Alarms Policy' giving their guide lines and requirements for the installation and maintenance of systems.

Essentially a complete alarm system will consist of three main elements—a detection device or devices, a control unit and some method by which the alarm is raised; this will usually take the form of an exterior bell box/flashing light or both. Automatic telephone dialling systems can also be incorporated, which will auto-dial the police using a tape-loop technique.

DETECTION APPARATUS

In this section the majority of currently available detection devices are listed. The basic function of the item will be explained with its main characteristics. If it is intended, after due consideration, that the system is to be assembled with parts from different sources, then it must be borne in mind that the characteristics of the detection devices must match the capability of the control unit. The main thing to look out for here is that normally open and normally closed hardware are properly matched.

Make-break contacts


These are used to protect windows and doors and are in the main magnetic devices more commonly referred to as reed switches. They consist of two parts—a pair of contacts and a magnet. They are fitted on opposite sides of the door or window frame to be protected, so that the magnet will hold the contacts in a normally closed state. If the window or door is then opened the circuit is broken and the alarm raised. A hidden reed switch is more effective than a surface mounting type—if a thief can see it he can feasibly beat it. The suitability of such methods should be considered if metal frames are to be protected. Microswitches could be employed as an option in these areas.

Anti-tamper switches

As the name suggests these are simply microswitches strategically placed within the housings of the separate elements of the system; for instance in the exterior bell box or main control box etc. Any attempt to open by force such a protected enclosure will operate the spring-loaded switch. Further anti-tamper protection is often simply incorporated in connector blocks where the fixing screw in the housing holds two contacts in a normally closed condition, if the screw is removed the alarm is raised.

Pressure pads

These may be used in areas where it is expected that an intruder is most likely to tread. This is often in a busy area at the foot of the stairs for instance (see photo) or in a hallway or landing. Unfortunately, when placed in such areas these mats are also subjected to great wear by the householder and may therefore wear out rather quickly and be prone to false alarms, they also tend to 'creep'. Strategic placement of this 'sensor' is a thoughtful business. Its construction however is much simpler, a wafer technique is employed where an insulating layer separates the two normally open contact layers which make contact when pressure is applied to the surface.

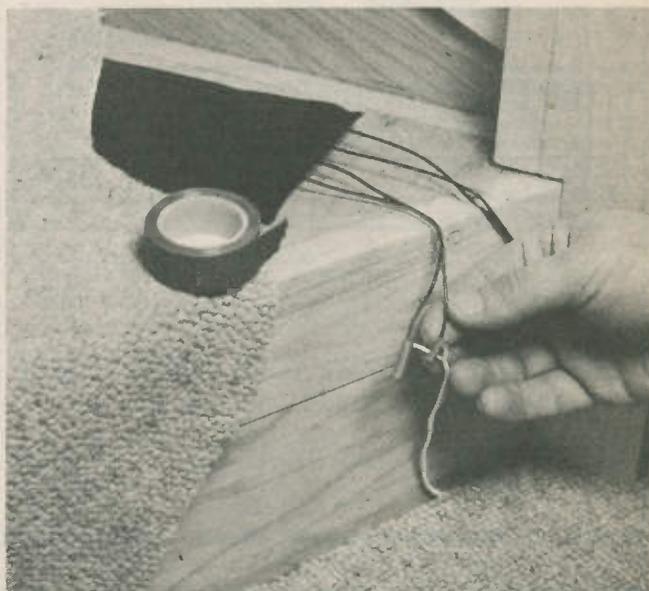

Crofton

THE VIDEO SPECIALISTS

If you need a monochrome or colour monitor, digitiser, T.V. camera, or door entry system **Crofton** must be your first choice – here are a few reasons why!



THE CROFTON PM101

This 9 inch metal cased, monochrome monitor is incredible value at **ONLY £82.80**

THE NOVEX 1414


This superb metal cased 14 inch RGB/COMPOSITE COMPUTER COLOUR MONITOR is unbelievable value at **ONLY £185.15**



CCTV CAMERAS

Though not new these cameras have been completely refurbished to a high standard in our own workshops and come complete with a standard lens, ready to work

ONLY £69.00

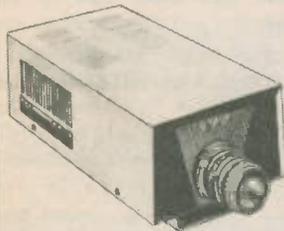

THE CROFTON SPECIAL CCTV OFFER

The Crofton special CCTV package and the door entry system described in this "Buyers Guide" are available at the following prices

SPECIAL CCTV PACKAGE	£193.00
DOOR ENTRY SYSTEM	£103.45

NOTE: We can also offer a multiscan system enabling the outputs from 4 cameras to be displayed simultaneously or individually on a single screen.

ELECTRONIC KEY FOB – Quickly locate mislaid keys. Fob emits a shrill tone in response to your whistle! **ONLY £10.53. ALL THE ABOVE INCLUDE VAT, CARRIAGE & INSURANCE AND AT THESE PRICES OUR STOCKS CANNOT LAST LONG. Delivery within 28 days.**

DON'T DELAY – PHONE YOUR ORDER TODAY!
MOST MAJOR CREDIT CARDS ACCEPTED

Be sure to request our free catalogue describing our range of T.V. cameras, fixed and zoom lenses, sequential switchers, special and general monitors (colour and b/w including the PHILIPS 7502, PHILIPS 7522 and PHILIPS 2007 plus the full Ikegami range), video digitisers, light pens, eeprom erasers etc.

CROFTON ELECTRONICS ☎ **01-891 1923**

35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX TW1 4AD

AFFORDABLE MCS

64K DIGITAL SAMPLER & DELAY LINE FOR SUPERB MUSICAL EFFECTS



Published in Practical Electronics

Full 64K memory. Up to 67KHz sampling rate. Audio bandwidth over 15KHz. Features special wow-less circuit controlling musical delay range from 4mS to 8 seconds. Maximum special effects delay 65 seconds. Companding ADC & DAC converters with equivalent of 15 bit sampling. Infinite loop sample storage. Controlling sweep modulator. Internal and external digital and voltage control. Effects generation for chorus, double tracking, reverse tracking, echo, flanging, phasing, reverb, vibrato, looped repeat and pitch variation, microprocessor control. BBC, Apple, Commodore and similar micros, or stand-alone. Mains powered.

19 INCH RACK MOUNTING UNIT KIT 234-R £295 PLUS VAT & £3.50 P&P

Published text available separately at £1.50 incl. post

MINI MCS

MICRO CONTROLLED SAMPLER FOR ECHO, REVERB AND OTHER DDL MUSIC EFFECTS



Published in Practical Electronics

Abridged version of the above sampler excluding on-board memory and timing. For direct control from a micro such as BBC, Apple, Commodore and similar. Includes companding ADC & DAC, computer interface, mix, feedback, filter, gain, level, PSU.

KIT 246-BK £95 PLUS VAT & £1.50 P&P

Both above units also enable a computer to be used as an audio oscilloscope and frequency counter.

Computer program listings for audio sampling and control available. See other advert for more audio effects kits. For catalogue of over 70 kits. Send 9x4 S.A.E. (for overseas catalogue send £1 or 5 IRC's).

Mail order. Payment to Phonosonics, CWD, CHQ, PD, Access, Visa. Insurance cover 50p per £50 (obligatory on credit card orders. Details correct at press. E&DE. Despatch usually 10-14 days.

BECKER-PHONOSONICS,
MAIL ORDER DEPT PE58, 8 FINUCANE DRIVE,
ORPINGTON, KENT, BR5 4ED. TEL: 0689 37821.

'RUR' HOBBY ROBOT

SPECIALLY SUITED FOR SCHOOLS

DESIGNER APPROVED KITS
AVAILABLE FROM



A complete kit of approved parts for the construction of the **RUR HOBBY ROBOT** as featured in PE is available as follows:

BASIC KIT £249
plus 15% VAT

ADD-ON ARM & ELEVATED TRAY £280
plus 15% VAT


CARRIAGE EXTRA Please write for a quotation

OFFICIAL ORDERS accepted from approved industrial or educational establishments, otherwise terms strictly **CASH WITH ORDER**

REEKIE ROBOTS

Beaufort Works, Beaufort Road, Richmond Road,
East Twickenham, Middlesex, TW1 2PQ.

Please allow 28 days for delivery

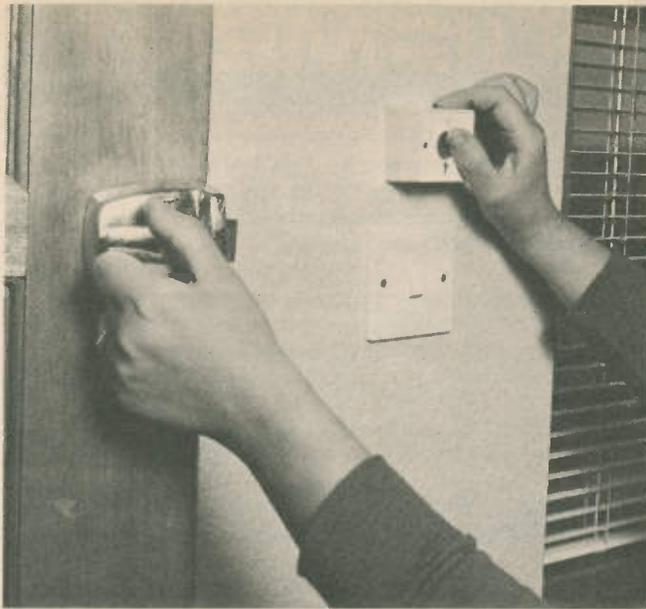

Panic buttons

A simple normally open or normally closed switch on a 24hr circuit. This circuit should be armed even when the rest of the system is off.

The fixture is usually fitted near the main entrance door (see photo) and/or, in many cases, in the master bedroom. It is quite simply depressed if the protectee is under imminent threat; the alarm will sound and the switch can only be reset with the use of a key.

Seismic detection

This device consists of a pair of contacts in a small enclosure, the contacts are kept in a normally closed state by a ball bearing which permanently rests across them. It would normally be fixed to a window pane so that when the glass is broken the ball bearing will move and the contact will be broken, sounding the alarm. Only a momentary break in the circuit need be detected as the control circuitry will latch into the alarm mode. These devices can be the cause of false alarms, if for instance a large shop window receives a 'Saturday night bump' this may be enough to trigger the device.

Window foil

A self-adhesive conductive, metallic strip which is simply stuck across the glass to be 'monitored', it forms as such, a closed circuit which is broken when the glass is broken.

Infra-red beam

There are several methods by which an intruder may be detected as he moves across a room. Perhaps the most straightforward of these is the infra-red beam which is transmitted across say a doorway or window to a photosensitive receiver unit. Because the beam is invisible to the human eye it is easy for an intruder to unwittingly step through it. When this happens the receiver senses the break in transmission and the alarm is raised. Careful consideration should be given to the placement of the transmitter and receiver. An experienced thief may spot them and just by-pass the beam.

VOLUMETRIC PROTECTION

Several methods have been devised to detect the presence of an intruder in a given area either indoors or outdoors. They can be used as part of a system or as 'stand alone' sentinels with on-board high-output sirens. These can be mains operated with or without battery back-up. Their effective ranges may vary considerably. Most of these units have a walk-test facility which uses an l.e.d. to display the sensitivity of the unit before the system is armed.

Passive infra-red

This method employs a heat sensor which peaks when human body heat is detected. A multi-faceted mirror directs the radiated heat information toward a focal point detector, each facet receiving information from a segment of the protected area. It is the movement of an intruder between these segments that gives the necessary modulation of radiated body heat required to trigger the alarm. These detectors are most sensitive to bodies which move across their field of 'vision'. According to my local CPO passive infra-red detectors are the least likely (of the volumetric detectors) to produce false alarms.

Ultrasonic

High frequency sound waves (in the 20-50kHz region) are transmitted and received by this device which will produce a balloon shaped area of protection emanating from the unit. If an object moves within this field a frequency shift occurs (due to the Doppler effect) to the waves which are reflected from the moving object. When this occurs the unit effectively receives two different frequencies which are combined to produce a beat note which is then amplified and used to operate the alarm. Most effective with objects moving in front of or towards the unit.

Radar/microwave

The radar system has essentially the same operating principles as ultrasonic but uses radio transmissions in the 10GHz region rather than sound waves. This enables the system to 'see' more as the radio waves penetrate more deeply into the environment, enabling for instance the detection of a moving object behind a piece of furniture or non-metallic structure.

Closed Circuit Television (CCTV)

CCTV equipment has now come down in price sufficiently to be of interest to the DIY home market. Several basic set-ups are available which include a camera with mounting bracket, a connecting lead and a monitor. Obvious applications would be hidden doorways and entrances etc.

CONTROL

The detection devices are connected to the control system by hidden wiring in most cases. The control box should be situated in a part of the property that is well protected once the system has been armed.

So that the user will not trigger the system an entry/exit delay is usually incorporated in the control box which allows a reasonable time for entry to and exit from the property before the system 'arms' itself; this is usually adjustable and between 30 seconds and three minutes.

The flexibility of the control mainly depends on the price of the system and many options are available. In some cases for instance the control will allow for the protected area to be split into more than one zone so that at night, for example, when the house is occupied and everyone is upstairs—then just the ground floor can be armed. This allows householders to move about upstairs at will during the night. Alternatively the whole house can then be armed when the house is empty. If personal attack buttons are incorporated in the system, it is generally arranged for these to be on a separate circuit which is armed 24 hours a day. If the house is occupied during the day then all but the panic buttons can be disarmed.

Most control panels allow for a test procedure to be carried out ensuring that the system is in good order. Controls are generally mains supplied with or without battery back-up.

RAISING THE ALARM

Once the system has been triggered various options are available as to how to raise the alarm. The most obvious and by far the most common is of course a simple audible warning device, usually the

SECURITY EQUIPMENT

- COMPLETE SYSTEMS
- SEPARATE COMPONENTS
- PROFESSIONAL QUALITY
- WHOLESALE PRICES
- TECHNICAL BACKUP
- COMPREHENSIVE CATALOGUE
- SUPER SERVICE
- FULLY GUARANTEED

SEND SAE OR 'PHONE FOR YOUR CATALOGUE NOW

C-TEC SECURITY

Dept. PER, Stephen's Way, Goose Green

Wigan WN3 6PH. (0942) 42444

Intruder Alarms and Accessories

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

contains
Control Unit
Enclosure & 2 mechanical fixings
Key Switch & 2 keys
LED's
5 1/2" Horn Speaker
4 high quality surface mounting Magnetic Switches

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straightforward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late order today.

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 - its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.

SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063 only £37.00 + V.A.T.



Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft
- Built in entrance and exit delay
- Built in timed alarm
- Key operated switch Off, Test and Operate
- Provision for an extension speaker
- Fully self contained
- Uses US 5063, PSL 1865 Key Switch 3901
- 3" Speaker 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built in LED indicator and test position the unit is easy set up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90db's of sound or even 110db's with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063.

RISCOMP LIMITED

Dept PE32,
51 Poppy Road,
Princes Risborough,
Bucks, HP17 9DB,
Princes Risborough (084 44) 6326

ALARM CONTROL UNIT CA 1250



Price £19.95+V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti tamper and panic facility
- Strobe/led output voltage
- 2 operating modes full alarm anti tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

HARDWARE KIT HW 1250

only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars (4x2 punched front panel), the unit is given a professional appearance by an adhesive silk screened label. Size 200 x 180 x 70mm

SIREN & POWER SUPPLY MODULE PSL 1865

only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110db's at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

NEW



TIMER SWITCH & POWER SUPPLY MODULE DP 3570 Price £13.95 + V.A.T.

The DP 3570 consists of an adjustable timer switch and stabilised 12V power supply for use in a wide range of applications including security lighting control and automatic switching. The timer section of the module provides switching of loads up to 3A for pre-set times, the duration of which may be set by the user to between 10 secs and 5 mins. The timed period may be triggered by the opening of a loop or the closing of external contacts, with the timed period commencing instantaneously or delayed to provide a form of entrance delay. The power supply section of the module provides a 12V output of up to 250mA which is sufficient for most applications. The module operates from either 240V a.c. supply or a 12V battery for which trickle charge facilities are included. Connections to the module are by means of screw terminal connectors with no soldering needed.

For mounting the unit an attractive moulded enclosure is available.

ME 357 only £2.85 + V.A.T.

INFRA-RED SYSTEM IR 1470 only £25.61+V.A.T.

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications.

Size 80 x 50 x 35mm

DIGITAL ULTRASONIC DETECTOR US 5063

only £13.95 + V.A.T.

This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

- 3 levels of discrimination against false alarms
- Crystal control for greater stability
- Adjustable range up to 25ft
- Built in delays
- 12V operation

ULTRASONIC MODULE ENCLOSURE

only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. for US 5063 order SC 5063, for US 4012 order SC 4012

RISCOMP THE SECURITY SPECIALISTS!

Add 15% V.A.T. to all prices
Add 70p post and packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday

Saturday 9.00 to 1.00 p.m.
S.A.E. with all enquiries.
Order by telephone of post using your credit card

Please allow 7 days for delivery

FULL RANGE OF ACCESSORIES STOCKED SEND SAE FOR DETAILS

exterior wall mounted siren or bell box. A bright flashing light is another option and sometimes the two are used together.

If tamper switches and back-up batteries are fitted to these bell boxes then they can be self actuating—if the wire to them is cut or the housing forced then the bell will sound. Internal warning bells are another option, they are usually fitted as well as an external bell. Basically an audible and/or visual alarm is intended to alert the neighbours and also to 'frighten off' the intruder.

Empty or 'dummy' boxes are sometimes fitted instead of or as well as the real thing, these can arguably deter as many prospective thieves as a real system.

If, for instance, an audible or visual alarm is not suitable—in a remote or quiet area, then a remote signalling system may be employed. In this case an automatic outgoing call device is used with a recorded message. Any number can be automatically dialled (usually 999) when an intruder is detected. Often an audible warning will be incorporated here which is set to sound after a specified delay. So that an intruder will not know he has been 'rumbled' until PC Plod is waiting outside. In some cases 'dedicated' outgoing telephone lines are used. Alternatively the existing line can be employed. Modules exist that will sound the alarm if the line is cut or blocked, the siren will sound instantly overriding the delay timer.

USEFUL ALTERNATIVES

Less elaborate techniques may be employed to deter the potential intruder and one or more of the following suggestions may be incorporated instead of, or as well as, those previously mentioned.

The use of plug-in time switches is gaining popularity for simply switching on and off (at pre-set times) such things as radios, TV's and bedside lamps etc. These timers have varying capabilities and full switching cycles range from 24 hours to 7 days. Your local electrical wholesaler should give you further information.

Another popular item is the photo-sensitive wall switch which can directly replace an existing wall switch. A photo-sensitive detector within the unit will switch on the room light when a low light threshold is detected—at dusk. Some units will switch off the lights after a preset period, whereas others will do so at dawn. Several types are available with varying capabilities—once again your local electrical wholesaler will help here. Plug-in timers and photo-sensitive replacement switches generally retail for under £20.


It is now well established that high on a burglar's list of 'don't likes' is a well lit property. The use of outside lights with proximity switches should therefore be considered; these can easily be incorporated into a system.

YOUR OWN HOME GUARD

The 'Neighbourhood Watch' scheme is gaining popularity and seems to give positive benefits. The principle is very simple—a group of householders get together to look after each others interests, peeling the proverbial eye. They basically adopt a more old-fashioned inter-protective community spirit and to a certain extent police their own environment. Your Crime Prevention Officer will help in establishing such groups with advice and film shows etc. In areas where the Neighbourhood Watch scheme has already been adopted a marked decrease in the incidence of vandalism, burglary and theft has been noted.

FALSE ALARMS

It is almost certain that anyone who has an alarm system will have had a false alarm and some systems are more vulnerable to this annoyance than others. More often than not it is operator error that causes the problems. A door or window which is not properly closed. Entering a protected area having forgotten to switch off the system. Pets, draughts blowing curtains etc. can trigger volumetric detectors, oversensitivity is a further problem; all these factors contribute to false alarms. Perhaps, as with all things, simplicity is the key.

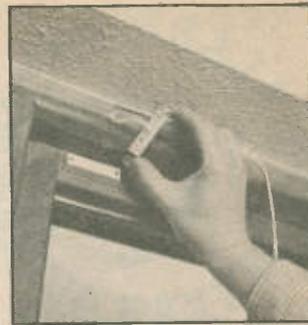

Typical applications of door and window contacts

In the vast majority of cases when the police are (automatically or otherwise) called to attend a potential intrusion it is attributed to a false alarm. Besides the obvious disadvantages of a system that persistently makes 'mistakes' we must consider the social effects.

The neighbours and/or keyholders, for instance, may decide that enough is enough, and so for that matter might the police. The local Environment Health officer may also employ the Control of Pollution Act 1974 in order to minimise a persistently noisy disturbance to the public. It is usual for systems, however, to switch off and reset automatically after a set time.

The names and addresses of keyholders should be given to the local Crime Prevention Officer. Regular maintenance of your system should also reduce the risk of problems. If secondary or back-up batteries are part of your system they should be checked regularly as is the case with professionally maintained systems.

GOVERNING BODIES

As with all installations, a degree of consumer protection with regard to standards of workmanship etc. is all important. Two main bodies look after our interests here. The National Supervisory Council for Intruder Alarms (NSCIA) who were founded in 1977 are an organisation who list installers that have been 'vetted' according to a demanding list of requirements.

On the other hand the British Security Industry Association (BSIA) cover the security industry more widely and include manufacturers in their listings as well as installers. Both the NSCIA and the BSIA are concerned with maintaining good standards throughout the professional security market. They liaise with the police, the Home Office and insurance companies etc., and both use the British Standards 4737 as their standard technical reference.

The BS 4737 is playing an increasingly important role in the industry, it covers just about every aspect of an alarm system, from maintenance and records to in-depth specifications on detection devices, warning devices and control circuit requirements. The BS 4737 can be consulted at most central libraries.

Although the DIY market is not strictly catered for by the above-mentioned organisations, the fact that they exist has influenced the manufacturing standards of much of the security market and therefore the incidence of goods manufactured to BS 4737 has been greatly increased.

ACKNOWLEDGEMENTS

Thanks to Jeff Brown, Crime Prevention Officer, Dorset Police H.Q., Winfrith.

Thanks to Alan Matley, Security Consultant, Secure Alarms, (Poole).

ADDRESSES

NSCIA, St. Ives House, St. Ives Road, Maidenhead, Berks., SL6 1RD; (0628 37512).

BSIA, 68 James' Street, London, SW1A 1PH; (01-493 6634).


British Standards Institute, Linford Wood, Milton Keynes, MK14 6LE; (0908 320066).

ALARM SYSTEMS D.I.Y. BUYER'S GUIDE

C-TEC K641/Kit comprises: 3 Pressure pads (one small); 6 pairs flush fitting magnetic contacts; 1 Panic button; 1 Bell; 1 Bell box (steel) (red, white or yellow); 1 Anti-tamper Microswitch; 1 Auto cut-off/reset control panel; 1 Rechargeable battery; 50 Metres 4-core cable; 100 Clips; Instructions. **Price:** £87-70. **Features:** Single zone; conforms to BS4737 and is expandable; Mains operation. **NB:** This company supplies a wide range of security equipment and kits (catalogue available). **Supplier:** C-TEC (Discount) Security, Stephens Way, Wigan, Lancs., WN3 6PH. (0942 42444).



ASP-515/Kit comprises: 5 Pressure pads (one small); 10 Pairs flush fitting magnetic contacts; 1 Panic button; 1 Bell; 1 Bell box (steel); 1 Bell reset module; 1 Siren; 1 Anti-tamper microswitch; 1 Auto-cut-off/reset control panel; 1 Rechargeable battery; 100 Metres 4-core cable; 100 Clips; Fixings; Instructions. **Price:** £136-86. **Features:** 3 Zones (1 main, 2 switchable), conforms to BS4737; mains operation. **NB:** This company supplies a wide range of security equipment and kits (catalogue available). **Supplier:** Advanced Security Products, Ealing Road, Aintree, Liverpool, L9 0HV. (051-523 8440).

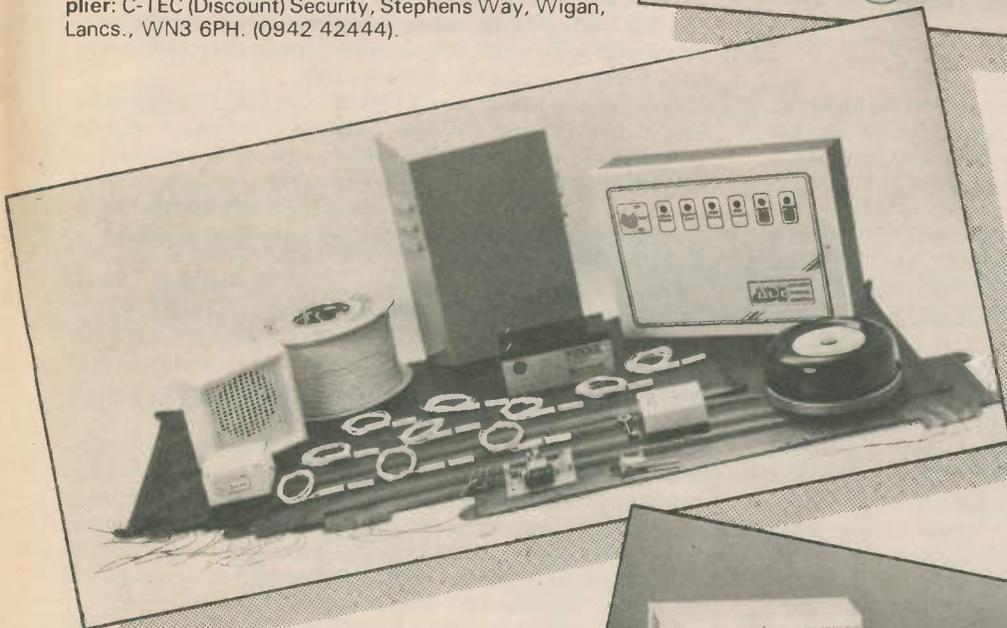

SECURE ALARMS DIY-1/Kit comprises: 6 Pairs magnetic contacts (5 flush fitting, 1 surface mounting); 1 Panic button; 1 Siren; 1 Bell box (polycarbonate); 1 Self-actuating module (bell box); 1 Anti-tamper microswitch; 1 Passive infra-red motion detector; 1 Auto cut-off/reset control panel; 1 Rechargeable battery; 100 Metres 4-core cable; 200 Clips; 1 Mains unswitched spur; Instructions. **Price:** £235-00. **Features:** 2 Zones (switchable), conforms to BS4737 and is expandable; mains operation. **NB:** This system can be tailored to customer specification upon request. **Supplier:** Secure Alarms, 96 Bourne-mouth Road, Parkstone, Poole, Dorset, BH14 9HY. (0202 737025).




The information in this guide gives a simple insight into, and a price/content comparison of, currently available DIY security equipment and kits. Further information can be gleaned from the addresses given.



COLOROLL HOUSEWATCH 2000/Kit comprises: 1 Pressure pad, 6 Pairs magnetic contacts (5 flush fitting, 1 surface mounting); 1 Panic button; 1 External box plus siren; 1 Auto cut-off/reset control panel; 50 Metres 2-core cable; 15 Metres 4-core cable; Plug-in mains adaptor; Fixings; Instructions. **Price:** £150.00 **Features:** 2 Zones (switchable), expandable (infra-red module £55 extra); mains operation. **Supplier:** Munford & White Ltd., Hither Green, Clevedon, Avon, BS21 6XU. (0272 870078).


MS-200/Kit comprises: 1 Pressure pad; 4 Pairs magnetic contacts (surface mounting); 3 Tamper-proof junction boxes; 1 Control unit with sounder; 1 Key switch; 25 Metres 2-core cable; Clips; Fixings; Instructions. **Price:** Around £64.00. **NB:** This kit is designed to give simple protection for up to five door/window points. Add-on kits available; battery operation. **Supplier:** Information contact, Moss Security Ltd., Unit 2, 46 Kneesworth Street, Royston, Herts SG8 5AG. (0763 45477).

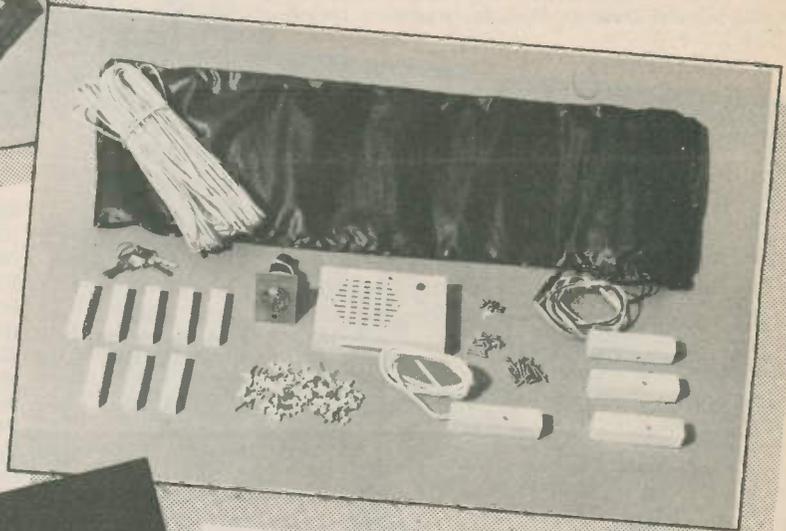

PIRSC/Kit comprises: 1 Key switch unit; 1 Infra-red/control unit; 1 Rechargeable battery; 1 Remote siren. **Price:** £148.35. **Features:** Both the key switch and the remote siren can be situated up to 500 metres distant from the main unit. The system is expandable. **NB:** A range of optional extras is available; mains operation. **Supplier:** Photain Controls Ltd., Unit 18, Ford Aerodrome, Arundel, West Sussex, BN18 0BE. (0903 721531).



TK ELECTRONICS: The items featured in this photograph represent a typical selection from the TK catalogue. Although this company do not stock complete kits, a wide range of elements are available enabling the assembly of systems suitable for most requirements. **Prices:** Typical prices for pictured item—Pressure mat £2.99; 6 Magnetic contacts (flush fitting) £7.24; Infra-red sensor £51.75; Siren £7.76; Xenon beacon £12.07; BS4737 2 zone control panel £57.21. **NB:** Catalogue available. **Supplier:** TK Electronics, 11 Boston Road, London, W7 35J. (01-579 9794).

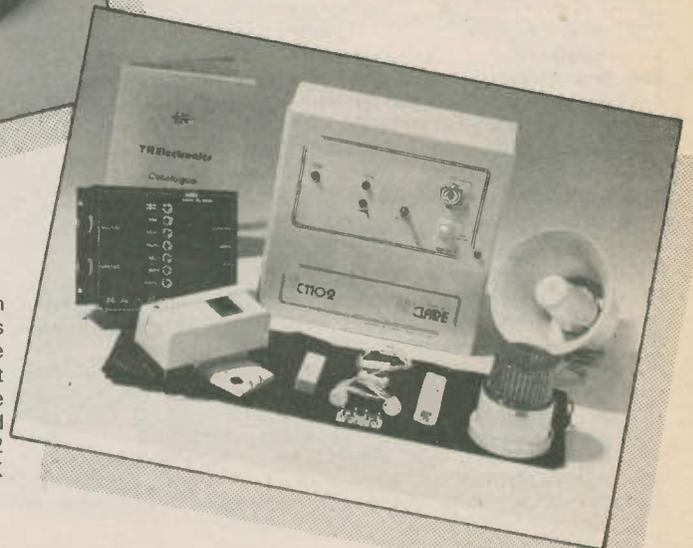


ALARM SYSTEMS D.I.Y. BUYER'S GUIDE

THIEFCHECK (HOOVER)/Kit comprises: 2 Pressure pads; 6 Pairs magnetic contacts (flush fitting); 1 Panic button; 1 External siren (in steel box); 1 Auto cut-off/reset control panel; 4-Core cable; Clips; Fixings; Instructions. **Price:** £166.89. **Features:** Passive infra-red accessories available; battery operation. **NB:** Batteries and 2-core cable not included. **Supplier:** Hoover PLC (Home Security Division), Perivale, Greenford, Middlesex. (01-997 3311).



CCTV KIT-1/Kit comprises: PM 101 nine-inch monitor; 1 (reconditioned) Ikegami one-inch vidicon camera; 1 20 Metre connecting lead; 1 Mounting bracket. **Price:** £193.20. **NB:** A multi-function door entry module is available as an accessory for this system. Basically as a timer/power supply it will allow interaction between camera and bell push or porch light etc., and facilitate a wide range of other functions such as two-way speech control etc. Can be tailored to customer requirements (mains operation). **Price:** £103.45. **NB:** Other CCTV equipment and catalogue available. **Supplier:** Crofton Electronics, 35 Grosvenor Road, Twickenham, Middlesex, TW1 4AD. (01-891 1923).

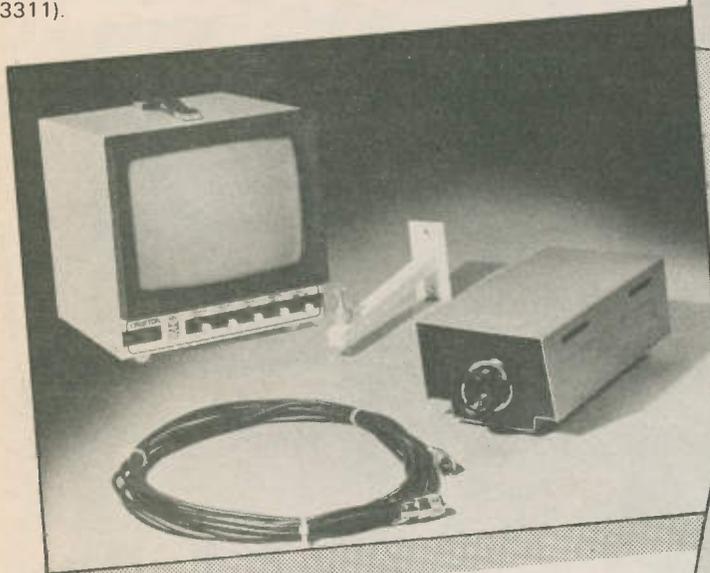

C-TEC K665/Kit comprises: 6 Pressure mats (4 large, 2 small); 10 Pairs magnetic contacts (flush fitting); 2 Panic buttons; 1 Bell; 1 Steel bell box (white, red or yellow); 1 Self-activation module; 1 Auto cut-off/reset control panel; 1 Rechargeable battery; 100 Metres 4-core cable; 100 Clips; Instructions. **Price:** £133.70. **Features:** 2 Zone system. **NB:** This company supplies a wide range of security equipment and kits (catalogue available); mains operation. **Supplier:** C-TEC (Discount) Security, Stephens Way, Wigan, Lancs, WN3 6PH. (0942 42444).




DRA-100/Kit comprises: 4 Transmitter units; 1 Siren; 1 Control unit; Complete instructions. **Price:** £159.85. **Features:** This is a Doppler shift radar alarm that will detect an intruder moving within the radius of operation of a transmitter, (from zero to around six metres). **NB:** This system requires complete assembly from component level. Its construction should only be considered by those with a fair knowledge of p.c.b. and electro-mechanical assembly. Mains operation. **Supplier:** Powertran Cybernetics Ltd., Portway Industrial Estate, Andover, Hants., SP10 3NN. (0264 64455).




PI-FLY: (left) This item is a small portable battery alarm, it is controlled with a key switch and detects movement. Once in position (in a filing cabinet drawer, or a briefcase for instance) it will trigger when moved, emitting a 98dB signal. Can be used on doors and windows.

PI-SPIDER (right) A similar battery operated device to the 'Fly' that will protect up to five items of value with its four tamper-proof 'tentacles' (the mains unit being the fifth sensor). Each 'tentacle' is 1.5 metres in length and is simply attached to a group of valuables such as TV's, videos, computers etc. **Prices:** Fly £24.95. Spider £34.95 **Supplier:** Product Innovation Ltd., 7 Berners Mews, London W1P 3DG. (01-580 7636).

PROPERTY PROTECTOR/Kit comprises: 2 Large Pressure pads; 6 Pairs magnetic contacts (surface mounting, with cable); 2 Tamper-proof junction boxes; 1 Passive infra-red motion detector; 1 Bell box (steel) with bell, auto cut-off/reset unit and rechargeable battery; 1 Control panel with rechargeable battery; Clips; Instructions. **Price:** £287.50. **Features:** 2 Zone (switchable) control. Expandable system, conforms to BS4737; mains operation. **Supplier:** Webalarm Products Ltd., 3 Bonsey's Lane, Chobham, Surrey. (099 057781).

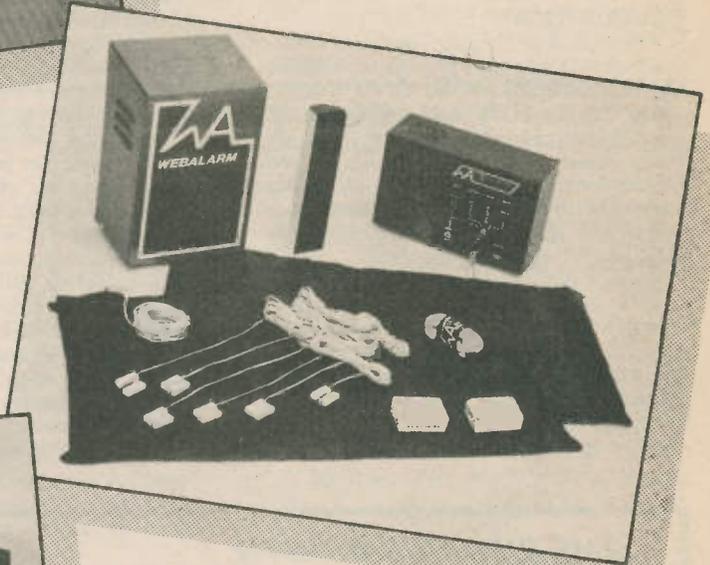


CK-5063/Kit comprises: 1 Siren; 2 Ready-assembled p.c.b.s; 1 Key switch; Fixings; Casing. **Price:** £37.95. **Features:** Stand-alone unit generates a 110dB alarm signal when triggered; Entry/Exit delay incorporated, also three levels of discrimination. **NB:** Some soldering/assembly reqd., mains operation (catalogue available). **Supplier:** Riscomp Ltd., 51 Poppy Road, Princes Risborough, Bucks. (08444 6326).

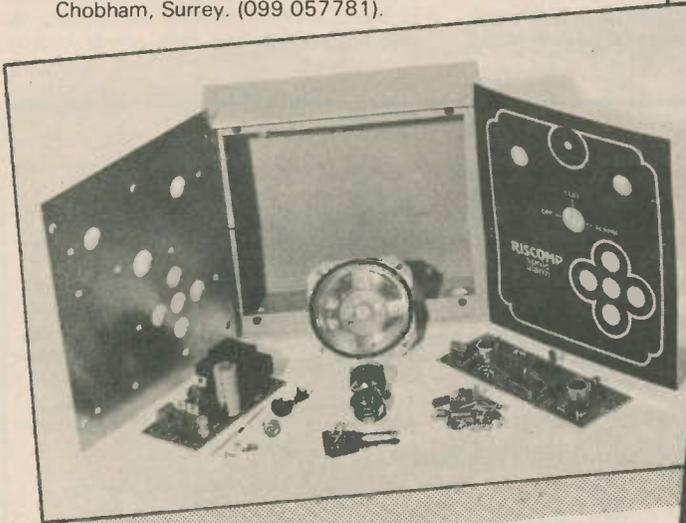

ALARM GUARD/Kit comprises: 1 Pressure pad; 5 Pairs magnetic contacts (surface mounting); 1 Panic button; 1 Bell; 1 Bell box (steel); 1 Auto cut-off/reset control panel; 4-Core cable; 2-Core cable; Clips; Fixings; Instructions. **Price:** £119.25 (Battery £7.48). **Features:** Expandable. **NB:** Battery operation. **Supplier:** Banham Patent Locks Ltd., 233-235 Kensington High Street, London, W8 6SF. (01-937 4311).



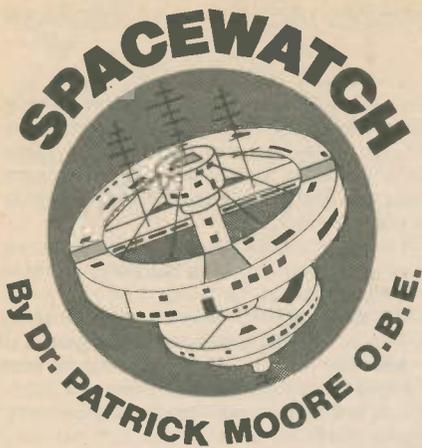

OBSERVATIONS

As reported last month, the Observatory of Los Muchachos, on the Canary Islands, has been officially opened by the King of Spain. It is now in full operation, though the great William Herschel reflector is not yet ready. A major telescope is being planned by the four Nordic countries, Denmark, Sweden, Norway and Finland, and other nations are also involved in the observatory, which is truly international.

Meanwhile, a new radio telescope has been sent to the high-altitude Mauna Kea Observatory, in Hawaii, at an altitude of almost 14,000 feet. It was commissioned by the Rutherford-Appleton Laboratory, and has a 15-metre "dish" designed to operate at millimetre and sub-millimetre wavelengths. It will probably be the most accu-

rate instrument of its kind ever built, and is a joint Anglo-Dutch project. Most radio telescopes stand in the open, but the high winds on top of Mauna Kea make it necessary to house the new instrument in an observatory which will automatically rotate with the movements of the telescope.

There are interesting new results concerning that somewhat mysterious region, the centre of the Galaxy. Astronomers in California have announced the detection of gas-streamers moving at a rate of at least 700,000 km/hour around the central region, and this may well indicate the presence of a Black Hole with at least 4,000,000 times the mass of the Sun. As yet it is impossible to be sure, but the evidence is growing that a central Black Hole really does exist there.

RECURRENT NOVAE

Considerable interest has been aroused this year by a new outburst of the recurrent nova RS Ophiuchi. During January it brightened so much that it was on the fringe of naked-eye visibility, though it soon faded back to its usual obscurity.

Normal novae are believed to be binary systems, made up of a red dwarf star together with a very dense White Dwarf. The White Dwarf pulls material away from the red star, and an accretion disk is built up around it. When sufficient material has accumulated, thermonuclear reactions are triggered off, and the resulting flare-up can be very spectacular.

The last really bright nova was a V.1500 Cygni, of 1975, which reached magnitude 1.8 at its maximum, though it faded very rapidly. (I was an independent discoverer of

this nova. It could hardly be missed, and was seen by many observers within a few hours of its outburst; I think I was 87th in order of priority!).

Recurrent novae differ inasmuch as they flare up more than once. This is not to say that a "classical" nova is limited to one outburst, but the interval between one maximum and the next must be very long indeed.

Of the recurrent novae, the best known is the so-called Blaze Star, T-Coroniae in the Northern Crown, which is normally of about the tenth magnitude, but which burst forth in 1866 and again in 1946, reaching naked-eye visibility on each occasion; in 1866, indeed, it brightened up to the second magnitude. Other examples are WZ Sagittae (outbursts in 1913, 1946 and 1979) and the southern T-Pyxis (1890, 1902, 1920, 1945 and 1965).

RS Ophiuchi, in the Serpent-bearer, has a normal magnitude of below 12. Previous outbursts occurred in 1901, 1933, 1958 and 1967, so that this year's event was the fifth to be observed. The maximum magnitude was 5.8, and the star would have been an easy binocular object; had it flared up at a more convenient time of the year.

It is now generally believed that the red component of a recurrent nova is not a dwarf, as with a classical nova, but a giant. Obviously this provides a greater supply of material, and the accretion disc round the White Dwarf companion is denser and more massive.

In January this year RS Ophiuchi ejected so much gas that its mass was as great as that of the Earth, and the ejection velocity

THE SKY THIS MONTH

With the longer nights, we are approaching the start of the new "observing season". The Moon is new on 16 August, so that it will not seriously interfere with the maximum of the Perseid meteor shower on the 12th; the Moon is next full on 30 August, by which time the shower will be over. The Perseids can always be relied upon to give a good display, and this year should be no exception.

Halley's Comet is still too faint to be seen except with large telescopes, but there is another comet on view: Giacobini-Zinner, which is being widely used as a "Halley rehearsal". Its position on 1 August is R.A. 1h 12m, declination N.59°57', which puts it in the constellation of Cassiopeia; and as the magnitude is above 9 it should be an easy telescopic object.

It was first seen in 1900, and has been observed at most returns since then. Its period is 6.5 years, and at times it has been associated with spectacular meteor showers—notably in 1933, when for a while the Z.H.R. or zenithal hourly rate of the "Giacobinids" exceeded 1000. No such display is expected this year, owing to the fact that the orbit has been perturbed by Jupiter, but the comet itself is well worth finding, particularly as an American spaceprobe is expected to by-pass it.

Jupiter reaches opposition on 4 August. Unfortunately it is rather low, in Capricornus, but it is visible for much of the night, and mutual phenomena of the four Galilean satellites have begun, to the great interest of planetary observers. Saturn, with its ring system wide open, is visible in the South-west during the evenings, and Venus is brilliant in the eastern sky before sunrise; it passes

only 7 degrees south of Pollux, one of the Twins, on 23 August—a good opportunity for a photograph!

Mars is too near the Sun to be seen, but Mercury becomes well placed in the morning sky late in the month, reaching its maximum western elongation (18 degrees) on 28 August. At its brightest Mercury attains a magnitude of -0.5, which is brighter than any fixed star apart from Sirius and Canopus, but it is never particularly easy to find, because it can never be seen against a really dark background.

SUMMER TRIANGLE

The evening stellar sky is still dominated by the so-called "Summer Triangle" of Vega, Deneb and Altair, with the Great Bear low in the north and the 'W' of Cassiopeia not far from the zenith. The Square of Pegasus has come into view, and it is interesting to survey its four stars with binoculars; three of them are white, while the fourth (Scheat, or Beta Pegasi, in the upper right-hand corner of the Square) is obviously orange. Beta Pegasi is a variable star, with a small range of from about magnitude 2.4 to 2.8 and a rough period of approximately 35 days.

Below the Square, skirting the southern horizon, is Fomalhaut in Piscis Australis, the Southern Fish—one of the stars found by IRAS in 1983 to have an infra-red excess, indicating the presence of cool material which may possibly be planet-forming or even a fully-fledged planetary system. Fomalhaut is only 22 light-years away, and is 13 times as luminous as the Sun.

was at least 3000 kilometres per second, with a temperature rising to millions of degrees. The outburst was also recorded at radio, ultra-violet and X-ray wavelengths; observations in infra-red were made with UKIRT, the United Kingdom Infra-Red Telescope on Mauna Kea.

UNPREDICTABLE

Recurrent novae are unusual stars, and may possibly provide a link between classical novae and the "dwarf novae" or SS Cygni stars, which show mild outbursts frequently (in the case of SS Cygni itself, about every 50 days). Clearly it is important to study their outbursts as closely as possible, and in this field amateur astronomers can play a valuable rôle. There are many regular observers, and it is always likely that an amateur will be the first to detect an outburst, in which case professional observatories can be alerted at once.

One can never tell just when a recurrent

nova will decide to "perform". With T-Coronae, the two observed outbursts were separated by eighty years; logically we cannot expect another before the end of the century—but one never knows.

It is also worth while keeping a watch upon old classical novae, some of which are of tremendous interest. For instance, there is HR Delphini, which flared up in 1967 and reached magnitude 3.6. It remained visible with the naked eye for months, and when I last observed it, a few nights ago, it was still above the 12th magnitude—whereas the more spectacular Cygnus nova of 1975 has now become so faint that it is hard to detect with any telescope.

Supernovae, of course, come into an entirely different category. Many have been observed in external galaxies, but the last supernova to be seen in our own system dates back to 1604, before the invention of the telescope. By the law of averages we are long overdue for another, but when it will

happen is something which nobody can foresee!

CAROLINE HERSCHEL

On a personal note, I greatly regret to have to report the death of Caroline Herschel, great-great-granddaughter of Sir William Herschel, who discovered the planet Uranus in 1781. Caroline—the namesake of William Herschel's famous sister, who acted as his assistant—was not herself an astronomer, but she took a great interest in science, and was actively involved in the setting-up of the Herschel Museum at 19 New King Street, Bath, from the garden of which William Herschel discovered Uranus.

Her delightful personality made her popular everywhere, and she will be sadly missed. It is tragic that she should not have lived long enough to watch the *Voyager 2* pass of her ancestor's planet, due in January next year.

FREE! READERS' ADVERTISEMENT SERVICE

PE BAZAAR

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid "date corner"**. Ads. will not appear (or be returned) if these rules are broken.

CLEARANCE! Memories, 2102's, £1.00; 2114's, £1.60; UAA170, £1.00; diode sockets, 16 pin, 5p, all brand-new. C. B. Shaw, 1 Guilford Cottages, East Langdon, Dover, Kent CT15 5JD. Tel: 0304 852097.

T199/4A expansion box, C/W interface, also 32k ram. Both new. Never used. £80 for both. Mr. C. Shaw, 123 Ironside Road, Hemsworth, Sheffield. Tel: 657898 after 6 p.m.

COMPONENTS Moving, must sell. Lots of junk, £2.00 a box plus 50p. postage and packing. J. H. Winpenny, Penpont Villa, Redruth Highway, Redruth, Cornwall.

VOX 1120 amp solid state pre-amp valve output (KT88's) 120W, inbuilt reverb. Rare vintage model. £180. R. Metcalf, 39 Bates Street, Crookes, Sheffield. Tel: 0742 683608.

MAGAZINES. PE 1979/85, one missing. PW 1968/85 and Radio Constructor 1967/79, both complete. Offers invited. A. L. Terry, 41 Abbey Road, Narborough, Leicester LE9 5DB. Tel: 0533 862428.

PRACTICAL WIRELESS and Practical Television 1947/50. Wireless World from 1930. Offers. Mr. Limburn, 74 Ellesfield Drive, Ferndown, Dorset.

MAGAZINES—PE 1969-78; PW 1960-65; most in Easi-binders. Offers for all or part. C. T. Watts, 27 Fairview Court, Manor Road, Ashford, Middx. TW15 2SH. Tel: 07842 51485.

PENSIONER wants tuner and i.f. panel for Decca TV model MS2400 or MS20000. All letters/calls answered. Mr. G. Martin, 39 Green Lane, Middleton, Manchester M24 2NF. Tel: 061-653 8275.

TAYLOR type 33a Oscilloscope, 5 MHz, £30; also AE1 CT52 Oscilloscope, 1 MHz, in metal transit case. £20. J. C. Priest, 53 Gaskell Crescent, Thornton-Cleveleys, Blackpool FY5 2TB. Tel: 0253 854486.

SHUGART SA801 8in. floppy disc drives. As new. Pair £190, including manuals + 20 blank new discs. Mr. P. Lacey, 32 Mill Close, Denmead, Portsmouth, Hants. Tel: 0705 266856.

WANTED: Word Wizard on tape. Eprom or disc from 'Premier'. J. Ockier, Mgr. Christiaensstraat 16, 8880 Tielt, Belgium.

PANASONIC TECHNICS set of service manuals, £1.50; small items (radios), £3.00. Colour televisions, videos, organs. SAE. E. S. Zych, 9 Edinburgh Drive, St. Ives, Cambs. PE17 6DA.

WANTED: Hardware manual or technical information in any form for TI-99/4A. Larry Lumsden, 46 Parnell Road, Harolds Cross, Dublin 12, Ireland.

TELEQUIPMENT D52 Oscilloscope, dual trace. Manual/leads. £50 ono. AVO multimeter model 40, £25 ono. Carlisle. Tel: 0228 20867.

TEKTRONIX 7603 four-trace Oscilloscope, recently calibrated. Cost £4,000 new. No reasonable offer refused. Barry Francis. Tel: 01-804 5081.

WANTED: IMFO scope Safgan DT420. Any reasonable price paid. Mike Smith, 1 Dan-Y-Lan, Aberkenfig, Bridgend, Mid. Glamorgan CF32 9AB.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules, I enclose a **cut-out valid** date corner.

Signature Date


Please read the RULES then write your advertisement here—one word to each box. Add your name, address and/or phone no. **COUPON VALID FOR POSTING BEFORE 6 SEPTEMBER, 1985** (One month later for overseas readers.)

SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WEST-OVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BE15 1JG.

BLOCK CAPITALS PLEASE

Name & Address:			

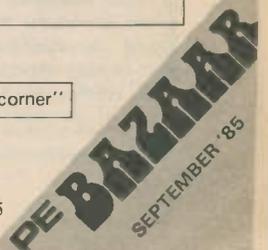For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid "date corner"**



BBC Micro Forum...

David Whitfield MA MSc CEng MIEE

THIS month I start with some software for the digital thermometer circuit described last month. As we shall see when investigating this, there is a little more to producing a usable project than the theory put forward might at first suggest. However, we have seen that putting micros to work in the real world frequently presents a few "wrinkles" to overcome. This is arguably one of the challenges which makes these problems all the more interesting!

THERMOMETER SOFTWARE

A simple program to provide a continuous display of temperature is given in listing 1. This assumes that the circuit is as shown last month (particularly that the value of series resistance is $1k\Omega$), and it provides a continuous display in Celsius and Fahrenheit. The preset resistor should be adjusted to give a correct reading when the sensor is used to measure a known temperature (see last month). The program includes a delay between readings to ensure a readable display. Even so, one of the first things which you may notice about the display is the sometimes quite significant fluctuation between readings. This is not quite so surprising, however, when you consider that each $^{\circ}C$ is separated by less than three ADC levels (each corresponding to approximately $0.44mV$). This means that any noise or other fluctuation on either the voltage from the sensor, or on the Vref used by the ADC, will show up as a significant temperature variation. What then can we do to improve this situation?

The voltage across the $1k\Omega$ series resistance is $1mV/^{\circ}C$, and this means that at room temperature the voltage being measured is around $300mV$. At the maximum temperature specified for the sensor ($150^{\circ}C$), the voltage will still only be around $450mV$. This compares with a maximum ADC input (i.e. the value of Vref) of approximately $1.8V$.

One possible way of improving the performance of the display, therefore, is to improve the noise immunity; that is to say, by increasing the voltage which the sensor produces for a given temperature. This is a simple process, and only involves increasing the series resistance, with a corresponding software change. The maximum value of series resistance is approximately $3.9k\Omega$, wired in series with the existing preset. Using this maximum means that each degree is now separated by approximately 9 ADC levels, with a corresponding improvement in immunity to sensor signal noise.

```
10 REM DIGITAL THERMOMETER
20 REM -----
30 :
40 X=@X: R=1000: Delay=30
50 ON ERROR GOTO 190
60 MODE 7: @X=@20105
70 VDU 23.1.0:0:0:0:
80 :
90 REPEAT: TIME=0
100 REPEAT UNTIL TIME>=Delay
110 T=ADVAL(1)*1800/(65.52*R)
120 T=T-273.2: PRINTTAB(8,12):
130 PRINT CHR$141;T;" 8C":
140 PRINTSPC(10);T*1.8+32;" 8F"
150 PRINTTAB(8)CHR$141;T;" C":
160 PRINTSPC(10);T*1.8+32;" F"
170 UNTIL FALSE :
180 :
190 VDU 23.1.1:0:0:0:
200 @X=X: PRINTTAB(0,23)
```

Listing 1. Simple thermometer display

The software change involves simply changing the value of "R" in line 40 of listing 1. It is worth noting in passing, that changing the value of R in the software is an alternative to adjusting the preset when calibrating the thermometer. We will come back to this later.

FURTHER IMPROVEMENTS

Even with the improvements above, the performance of the thermometer still leaves a little to be desired. It is soon apparent that, even when just calibrated, the temperature readings still seem to drift as time passes. One of the main reasons for this behaviour is the fact that the Vref used by the ADC drifts as the micro warms up. On my own machine, the value fell from $1.82V$ at switch on, to $1.77V$ after 30 minutes, finally settling down to $1.69V$ after 8 hours. This is equivalent to an error varying from $+1.1\%$ to -6.1% when compared with the nominal $1.8V$. This may not seem to represent much of an error for a temperature of $25^{\circ}C$, and indeed it is comparable with the accuracy of a typical room thermostat. However, the temperature sensor actually measures the absolute temperature, and this means that at $25^{\circ}C$ (approximately $298^{\circ}K$), the error in Vref is equivalent to a range of $-3.3^{\circ}C$ and $+18.2^{\circ}C$. This is quite a sizeable error!

One way of compensating for this reference drift is to adjust the value which the software assumes for Vref; the default value is set to $1800mV$ in line 110. However, this is not very practical in many situations, particularly since the thermometer may be used at different times after switch-on, hence when the value of Vref will be

different. An alternative, and more practical solution, is to use the improved thermometer circuit shown in Fig. 1. This includes a bandgap voltage reference source (Vcal) which is measured on the second ADC channel. If the bandgap reference is measured by the ADC, the value read will correspond to a known voltage, and hence this reading can be used to calibrate the ADC levels. By including a measurement of the bandgap source every time the temperature sensor is measured, the Vref drift can be compensated. The bandgap source shown in Fig. 1 has a nominal voltage of $1.22V$, has a typical temperature coefficient of only $30ppm/^{\circ}C$, and is available for around $\pounds 1$ from sources such as RS (282-283).

```
10 REM Digital Thermometer v2.0
20 REM -----
30 REM
40 REM This parameterised digital
50 REM thermometer display program
60 REM allows various circuit and
70 REM s/w configurations to be used
80 :
90 FX=4 : REM ADC bits ignored
100 TX=75 : REM Display interval
110 RX=2200 : REM Series resistor
120 Vcal=1220: REM Bandgap voltage
130 Vref=1800: REM ADC nominal ref
140 TempX=1 : REM Sensor channel
150 CalX=2 : REM Ref volts channel
160 :
170 MODE 7: ON ERROR GOTO 400
180 FX=2*FX: VDU 23.1.0:0:0:0:
190 PRINTTAB(2,22)"(Z/X to dec/inc)"
200 PRINTTAB(22,22)"(N/M to dec/inc)"
201 PRINTTAB(15,6)"Bandgap Ref:"
202 PRINTTAB(17,12)"ADC Ref:"
210 :
220 REPEAT: @X=@020105
230 Cs=INKEYS(TX)
240 IF Cs="T" RX=RX+5
250 IF Cs="R" RX=RX-5
260 IF Cs="X" Vref=Vref+5
270 IF Cs="Z" Vref=Vref-5
280 IF Cs="M" Vcal=Vcal+5
290 IF Cs="N" Vcal=Vcal-5
300 X=1000*(ADVAL(TempX)/DIV FX)*FX/RX
310 Xref=X*Vref/65520-273.2
320 Xcal=X*Vcal/(ADVAL(CalX)/
DIV FX)*FX-273.2
330 PRINTTAB(8,8)CHR$141;Xcal;" 8C":
SPC(10);Xcal*1.8+32;" 8F ""TAB(8)
CHR$141;Xcal;" C":SPC(10);
Xcal*1.8+32;" F "
340 PRINTTAB(8,14)CHR$141;Xref;" 8C":
SPC(10);Xref*1.8+32;" 8F ""TAB(8)
CHR$141;Xref;" C":SPC(10);
Xref*1.8+32;" F "
350 @X=@000006
360 PRINTTAB(3,20)"Vref = ";Vref;"mV":
SPC(7);"Vcal = ";Vcal;"mV":
370 PRINTTAB(5,2)"R = ";RX;
" ohms (R/T to dec/inc)"
380 UNTIL FALSE
390 :
400 VDU 23.1.1:0:0:0:
```

Listing 2. Calibrated thermometer display

TECHNICIAN ENGINEERS

COMMUNICATIONS AND ELECTRONICS

A Planned Career in Technology in the Cotswolds

Salaries up to £11,445

- **VACANCIES** at both **TECHNICIAN ENGINEER** and **ENGINEERING TECHNICIAN** level.
- **CHALLENGING WORK** in the development and support of highly sophisticated communications and computer systems.
- **OPPORTUNITIES** for gaining experience in a wide variety of technical roles.
- **EXTENSIVE ENGINEERING FACILITIES**
- **CAREER PLANNING** aided by regular assessments of performance.
- **ADVANCEMENT** opportunities on the basis of proven ability.
- **OVERSEAS** service (voluntary).
- **FLEXIBLE** working hours with up to six weeks leave.
- **RELOCATION EXPENSES** in most cases.

Applicants for the higher grade of **TECHNICIAN ENGINEER** should normally possess a BTEC Higher National Certificate/Diploma in electronics or other relevant subject; or a City and Guilds Full Technological Certificate, or an equivalent qualification. An aggregate of at least 8 years relevant training and

experience is required. Registration as a Technician Engineer (T.Eng) would be an advantage. **Salary Scale: £9,113 – £11,445**
Applicants with BTEC ONC or equivalent and at least 4 years relevant training and experience are eligible for posts at the **ENGINEERING TECHNICIAN** level for which a structured training programme is provided. **Salary Scale: £6,599 – £9,135**

INTERESTED? Then for either post send for full details and application form to the address below, quoting Ref: T/6523/85



THE RECRUITMENT OFFICE, GCHQ, ROOM A/1108
OAKLEY, PRIORS ROAD, CHELTENHAM, GLOS GL52 5AJ
OR TELEPHONE (0242) 32912/3

BOOKS FOR THE BBC MICROCOMPUTER

FROM MACMILLAN

Operating the BBC Microcomputer: A Concise Guide
Graham Leah

Paper £1.95 0 333 37155 0



Interfacing the BBC Microcomputer
B. R. Bannister and Michael Whitehead

Paper £7.50 0 333 37157 7

File Handling on the BBC Microcomputer
Brian J. Townsend

Paper £6.95 0 333 36808 8



George's Computer Bookshop, 87 Park Street, Bristol BS1 5PJ

A Science Teacher's Companion to the BBC Microcomputer Philip Hawthorne

Paper £9.50 0 333 38285 4

Advanced Graphics with the BBC Model B Microcomputer

Macmillan Microcomputer Books
Ian O. Angell and Brian J. Jones
Paper £9.95 0 333 35052 9

Good BASIC Programming with the BBC Microcomputer

Macmillan Microcomputer Books
Margaret A. White
Paper £5.50 0 333 36704 9

Using Sound and Speech on the BBC Microcomputer

Macmillan Microcomputer Books
M. A. Phillips
Paper £6.95 0 333 37155 0

Assembly Language Programming for the BBC Microcomputer 2nd ed

Macmillan Microcomputer Books
Ian Birnbaum
Paper £8.95 0 333 37096 1



Beginner's Guide to Interfacing the BBC Microcomputer M. A. Phillips

Paper £6.95 0 333 38652 3
(forthcoming September)

ORDER FORM

Please send me the following books:

QTY

Operating the BBC Microcomputer £1.95

Interfacing the BBC Microcomputer £7.50

File Handling on the BBC £6.95

Science Teacher's Companion £9.50

Advanced Graphics with the BBC £9.95

Good BASIC Programming £5.50

Using Sound and Speech £6.95

Assembly Language Programming £8.95

A Beginner's Guide to Interfacing £6.95

NAME

ADDRESS

I enclose my cheque for £

Please charge my Access Barclaycard credit card.

Account number

Please post your order to George's Computer Bookshop, 87 Park Street, Bristol BS1 5PJ.

Signature
(please add 10% for post and packing)

Expiry date

Please allow 28 days for delivery



Serpent Robot Review

DICK BECKER
ROGER GAY

SCARAs are a relatively new class of small industrial robot filling the gap between simple pneumatic pick-and-place robots and servo controlled robots modelled upon the human arm like the *Unimation Puma*. SCARAs originated in Japan and having rapidly become established in manufacturing in that country are now spreading throughout Europe and North America; being used for handling and assembling small components.

Prices of SCARAs are generally in the range £15K-£25K. Load capacities rarely exceed 10kg and the actual load may be just a screw or integrated circuit weighing a few grams. Some manufacturers offer alternatives to a gripper such as devices for hole tapping, spot welding and soldering, presumably for soldering to top side of p.c.b.s where flow soldering is not to be recommended.

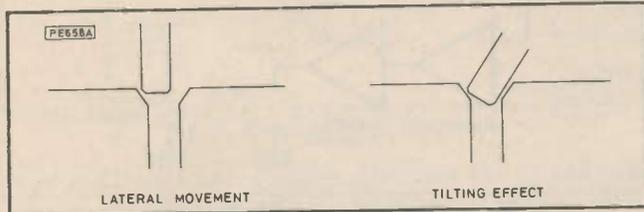


Fig. 1. Illustration of selective compliance

COMPLIANCE

SCARA is an acronym for Selectively Compliant Articulated Robot Arm. This feature comes from the fact that any servo controlled arm will automatically have springiness or compliance in the plane of the operation of that arm. A small displacement of the arm will cause a small correcting force to be applied by the servo system whilst a larger displacement will cause a larger correcting force, hence the springiness. A SCARA has joints moving in only the XY (horizontal) plane. Assuming good engineering the arm will be stiff (non-compliant) in the vertical direction. The arm is thus selectively compliant!


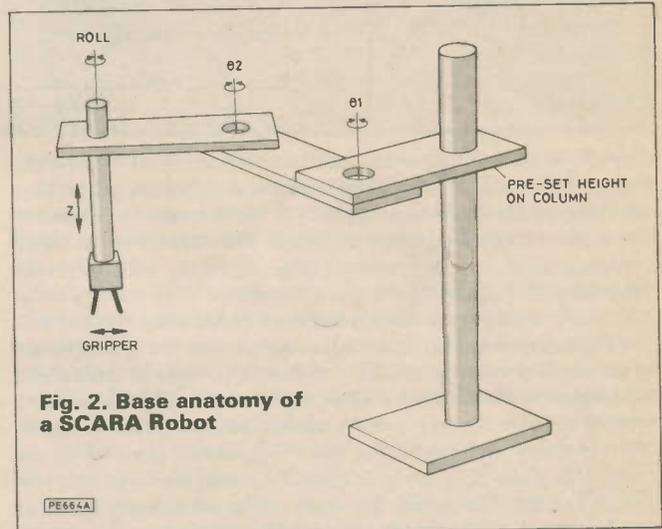


Fig. 2. Base anatomy of a SCARA Robot

The significance of selective compliance becomes apparent during assembly operations (Fig. 1). If there is a small error of position then the compliance in the XY plane will allow the part to be inserted into a hole, with a chamfered edge, when vertical pressure is applied. Had there been lack of stiffness (i.e. compliance) vertically then the part could tilt and jam.

SCARA ANATOMY

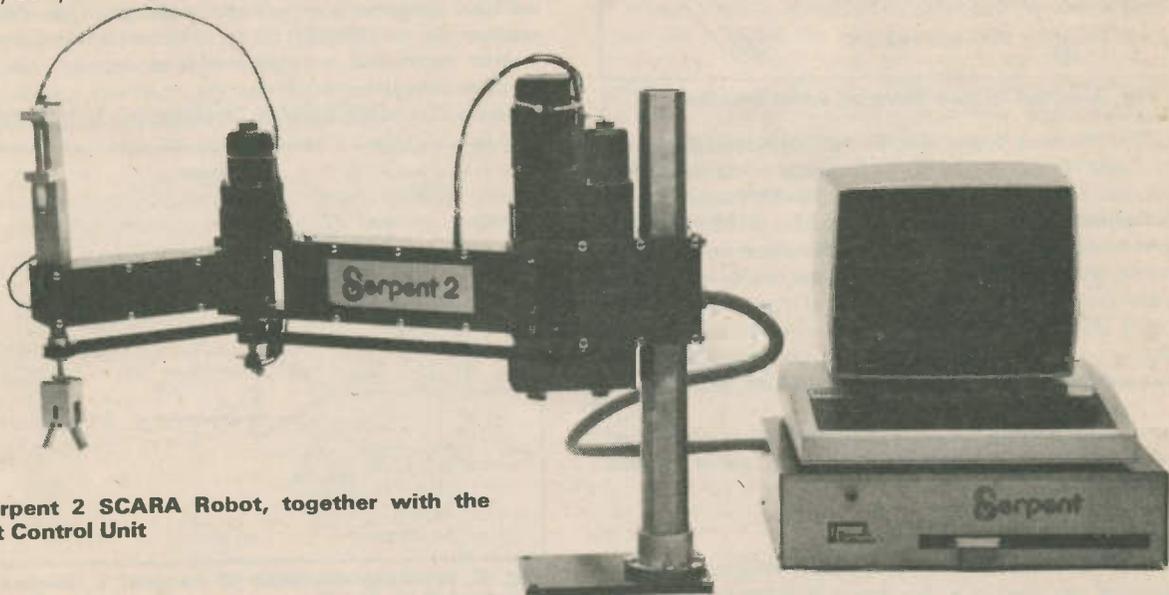The anatomy of the SCARA is shown in Fig. 2. SCARAs operate predominantly on the XY plane, there being 2 servo controlled horizontal joints. THETA 1 is the shoulder and THETA 2 the elbow. A third rotary axis is ROLL which is the wrist. Typically this is belt driven from a motor at the fixed end of the arm. This at first sight seems a strange way of driving it as there would usually be little



The Serpent 2 SCARA Robot, together with the Serpent Control Unit

SPECIFICATIONS

SERPENT I

Main arm length	250mm
Fore arm length	150mm
Theta 1 axis (shoulder movement)	200°
Theta 2 axis (elbow movement)	250°
Roll axis (wrist rotation)	450°
Z axis (up-down)	75mm
Control system	12 bit
Resolution	1:4096 (3.7 minutes of arc)
Repeatability	1.0mm
Maximum tip velocity	550mm/sec
Capacity	2.0kg

SERPENT II

Main arm length	400mm
Fore arm length	250mm
Theta 1 axis (shoulder movement)	200°
Theta 2 axis (elbow movement)	250°
Roll axis (wrist rotation)	450°
Z axis (up-down)	75mm
Control system	12 bit
Resolution	1:4096 (3.7 minutes of arc)
Repeatability	1.5mm
Maximum tip velocity	850mm/sec
Capacity	2.0kg

difficulty in placing the motor close to the joint itself. Having the motor on a fixed point keeps down the mass at the gripper end but the main reason for the arrangement is that it keeps the wrist and hence the workpiece at a constant angle with respect to the bench irrespective of arm movements (Fig. 3). It is, therefore, not necessary to constantly compute a suitable drive for the wrist motor in order to avoid turning the work piece when moving it.

Vertical movement of SCARAs is very simple. The overall height of the arm is pre-set by adjusting its position on a fixed column and the gripper is moved only a small amount in the Z direction by a vertical actuator. Sometimes the vertical actuator is servo driven, e.g. by motor and ball screw, but more usually pneumatics are used. This gives high speed operation working between two pre-set end stops. The gripper generally has pneumatically powered jaws but vacuum pick-up devices are also popular.

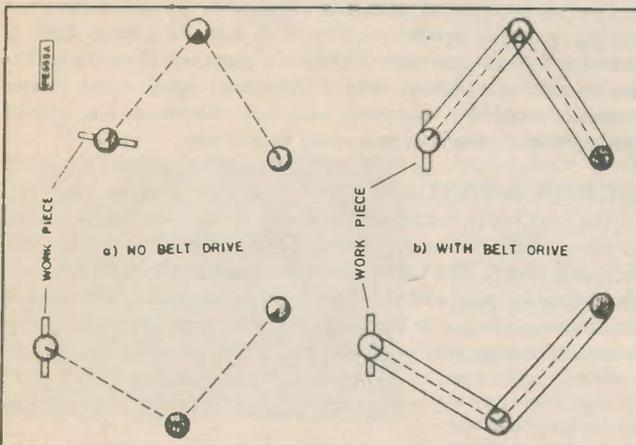


Fig. 3. Effect of belt drive on wrist rotation

The SERPENTs were designed to be fully representative of the SCARAs found most frequently in industry. There are two articulating joints of the arm using d.c. servo motors under closed-loop servo control. There is wrist rotation by d.c. servo motor also under closed loop servo control. A very fast vertical axis operates pneumatically and there is a pneumatic gripper readily replaceable by a vacuum pick-up pad. Compressed air, at a pressure of 5 to 8 bars, enters the control box via a plug-in connector from a compressor or regulated CO₂ cylinder. A combined electrical/pneumatic connector takes the signals and air to and from the robot.

The servo control system is extremely flexible being based on hardware but with software control of the servo system characteristics.

SERVO CONTROL

The simplest form of servo control of a d.c. motor consists of a power amplifier preceded by a comparator (Fig. 4) which gives an

output voltage dependent on the difference between a voltage representing the desired position and a voltage representing the actual position. If a potentiometer is fitted to the axis being moved then this provides the position indicating voltage. Assuming the amplifier is linear then the drive voltage to the motor will depend linearly upon the error voltage, i.e. the difference between desired

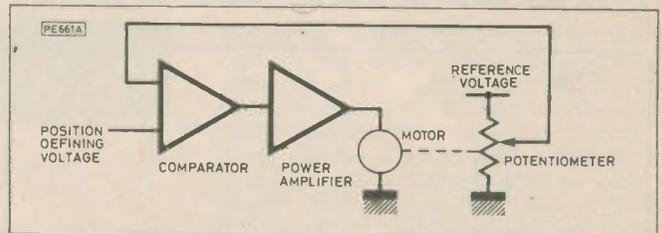


Fig. 4. Basic servo control system

position and actual position. As the desired position is reached the drive to the motor reduces thereby slowing it down and finally stopping it when the error is zero which occurs when the desired position is finally reached.

Such a simple control system, however, ignores the effects of inertia and the drive capability of motors at low voltage. Inertia would result in overshooting the target unless the gain of the amplifier is very low resulting in low operating speed of the arm. Furthermore, as the gain is reduced, the motor drive voltage for a given error voltage is also reduced.

Because of friction, a motor requires a certain amount of voltage on it before any rotation occurs, consequently when there is sufficient gain the arm will stop moving before the target is reached. On the MENTOR robot, described earlier this year, there is little inertia and a simple non-linear network on the servo amplifier giving it extra gain near the target was adequate for the 8-bit resolution of that system. However, the SERPENTs are much

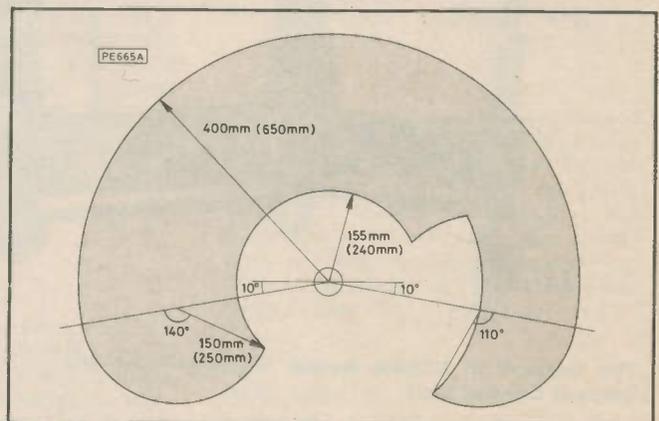


Fig. 5. Working envelope of Serpent 1 (Serpent 2 figures in brackets)

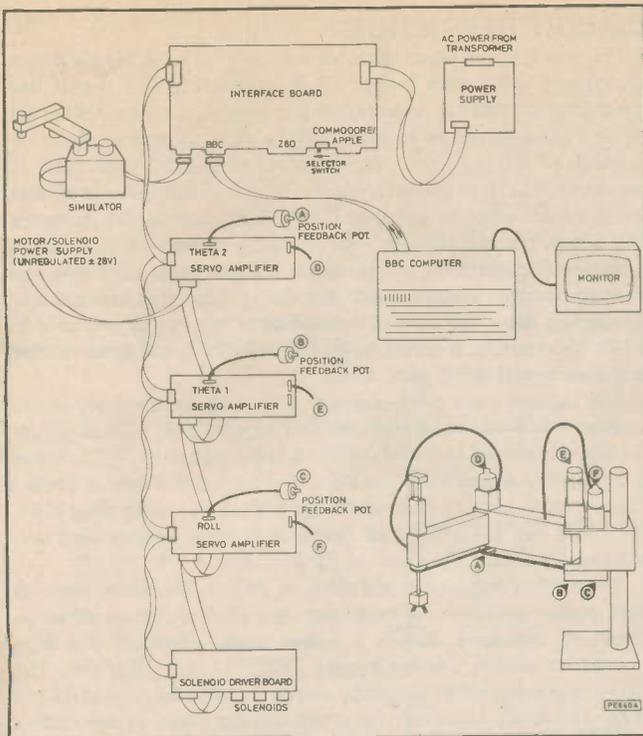


Fig. 6. Serpent control system

larger and faster covering a large workspace (Fig. 5) with high accuracy making 12-bit resolution necessary. A more complex control system was therefore required.

One approach to the problem of control would be to send the position data to a micro-based system, compute a suitable drive voltage and send it to the motor via an ADC (analogue to digital converter) or PWM (pulse width modulation) pulse generator. The drawback of this is that if a computer is used then it must be constantly working on the servoing and if halted the arm would go out of control. A second microprocessor, devoted to servo control could, however, be used under supervision of the computer but then intelligibility and accessibility of the software would be lost. This would seriously detract from the system's value for education and training purposes.

An alternative approach is to use hardware which provides analogue servoing which will continue without computer intervention and have programmability of the hardware characteristics which are hence modifiable under computer control.

THE SERPENT CONTROL SYSTEM

The SERPENTS are controlled by three servo amplifiers (Fig. 6), a solenoid driver (for the pneumatics) and an interface board connected to a small computer, e.g. BBC, Commodore 64, Apple, etc. Most of the software is written in BASIC. Machine code sub-

outines are called from BASIC only where high speed of execution is essential.

The interface board is a well proven design being the same as used for the NEPTUNE hydraulic robots and was described in the *PE October 1984* issue. Data from the computer is passed to the interface board which is essentially a multiplexed DAC (digital to analogue converter) and multiplexed ADC and provides six outputs and 16 inputs of 12-bit resolution analogue voltages.

The position of each rotary axis of the arm is sensed by a high quality (conductive polymer) potentiometer and after adjusting offset and gain in the buffer (Fig. 7) there is a 0 to +10V signal which passes via an ADC to the computer for it to know the current position of the arm. Desired position comes from the computer via a DAC as a voltage also in the range 0 to +10V. The comparator gives an error voltage in the range -10V to +10V. As ADCs do not like bipolar signals the buffer converts the error voltage to a range of 0 to +10V. The error voltage next passes through a VCA (voltage controlled amplifier) controlled by another DAC output which enables the gain of the system to be software selectable. Finally a power amplifier drives the motor with a voltage in the range of -24V to +24V.

With this software adjustable system there are different levels of control which can be exercised. At the simplest level the computer sends out 4 bytes to the interface board (memory mapped). Two bytes define the desired position of the axis whilst the other 2 bytes define the gain that the amplifier is to have whilst reaching its target. In software, progressively greater control can be achieved by increasing the complexity of the algorithms used for modifying the gain.

The gain required depends upon the error signal (directly accessible) and the velocity and acceleration (derived from successive reading of the current position). Velocity, acceleration and deceleration are all controllable from the computer though full commitment of the computer is not required in that if it is interrupted then the hardware will continue taking the arm to the desired position.

In the main control program "CHARMER" a multi-tasking technique is used to keep a machine code servo routine operating in the background whilst the main program continues in BASIC. This has been achieved through the use of interrupts. Most 6502 machines are fitted with or can be fitted with a 6522 VIA (Versatile Interface Adaptor). The BBC computer includes a VIA as standard. This chip has two 16-bit timers, one of which can be used to generate an interrupt request (IRQ) whenever it counts down to zero.

Where there is no VIA an external counter, e.g. a 555, can be used. On receiving the interrupt and after completing its current instruction, the 6502 loads its program pointer with the interrupt service routine vector giving control to this routine. By altering the vector to the start of one's own routine, multi-tasking is easily implemented. The interrupt service vector is at location &FFFE and &FFFF, which is normally ROM, but on some computers, e.g. the BBC, the resident interrupt service routine indirections through a location in RAM. On the BBC the locations are &206 and &207.

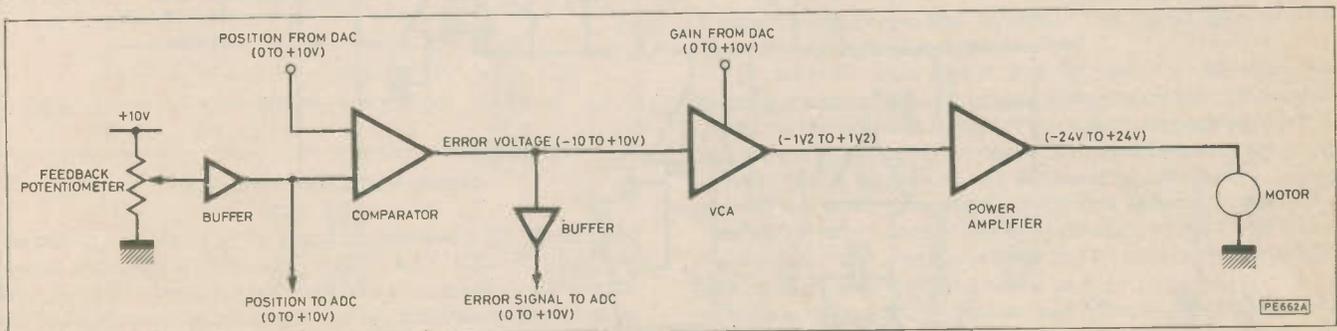


Fig. 7. Basic servo amplifier of the Serpent

CIRCUIT OPERATION

The circuit of the servo amplifier is shown in Fig. 8. IC1a is a high impedance unity gain buffer to avoid loading and hence delinearising the position sensing potentiometer. As it is impractical to fit a potentiometer to give exactly zero voltage at the zero position of the axis the voltage is nulled out by VR1. Gain is provided by IC1b to give a range of 10V. IC2b is an inverter so that the feedback voltage going to the ADC is positive. D1 prevents any possibility of a reverse voltage during setting-up. IC2a is the comparator comparing the feedback voltage from IC2b with the desired-position voltage from the DAC. IC5a is a level shifter converting the -10V to +10V range error voltage to one of 0 to +10V for the ADC. It works by adding in +10V to the error voltage and then applying 0.5 gain.

The voltage controlled amplifier which alters the gain of the system is IC3. IC3b is a transconductance amplifier whose gain is linearly dependent upon the current flowing into pin 16. IC3a takes a 0 to +10V signal from the DAC and converts it into a current ranging from zero to approximately 500µA for controlling IC3b. VR2 nulls out any offsets so that zero in gives exactly zero out. VR3 sets the maximum gain of the system.

The motors require several amps at 24V to fully drive them. A high power amplifier not dissimilar to a 60W audio amplifier is, therefore, necessary. IC4 is a power driver providing the drive current for power transistor pairs TR1/TR3 and TR2/TR4. The gain of the stage when driven by a large signal is the ratio of R22 to R17, i.e. X40, however, for small signals there is insufficient voltage to cause conduction in the diode network and the gain is increased, in that region, by the ratio of R41 to R40, i.e. there is over 20 times extra gain for very small error signals. The effect of this is to provide the motor with sufficient voltage to move even when the error is less than 1 bit. After that the voltage only increases gradually with increasing error.

VR4 is used to null out the input offset voltage so that zero error gives zero output to the motor. IC4 includes transistors to protect

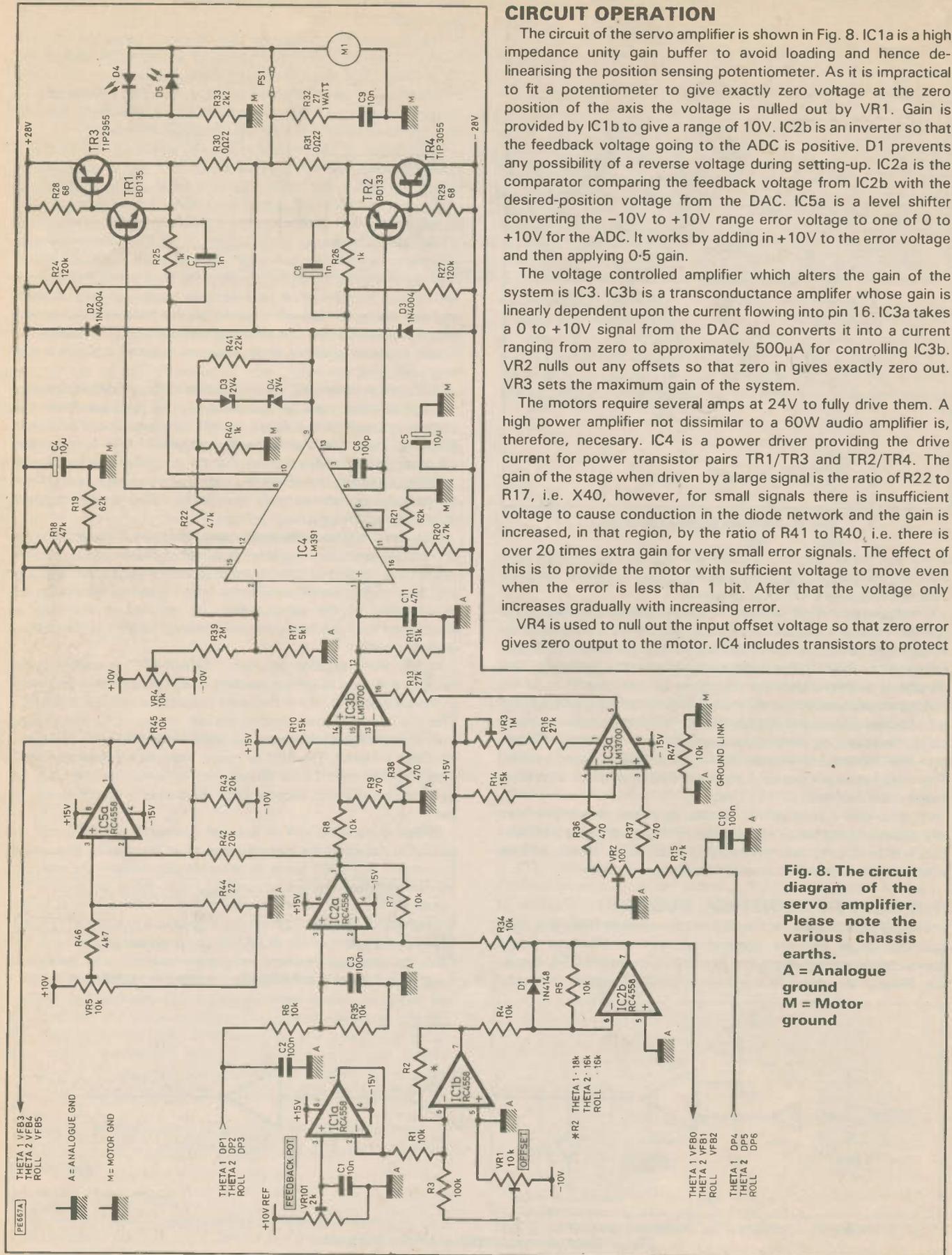


Fig. 8. The circuit diagram of the servo amplifier. Please note the various chassis earths. A = Analogue ground M = Motor ground

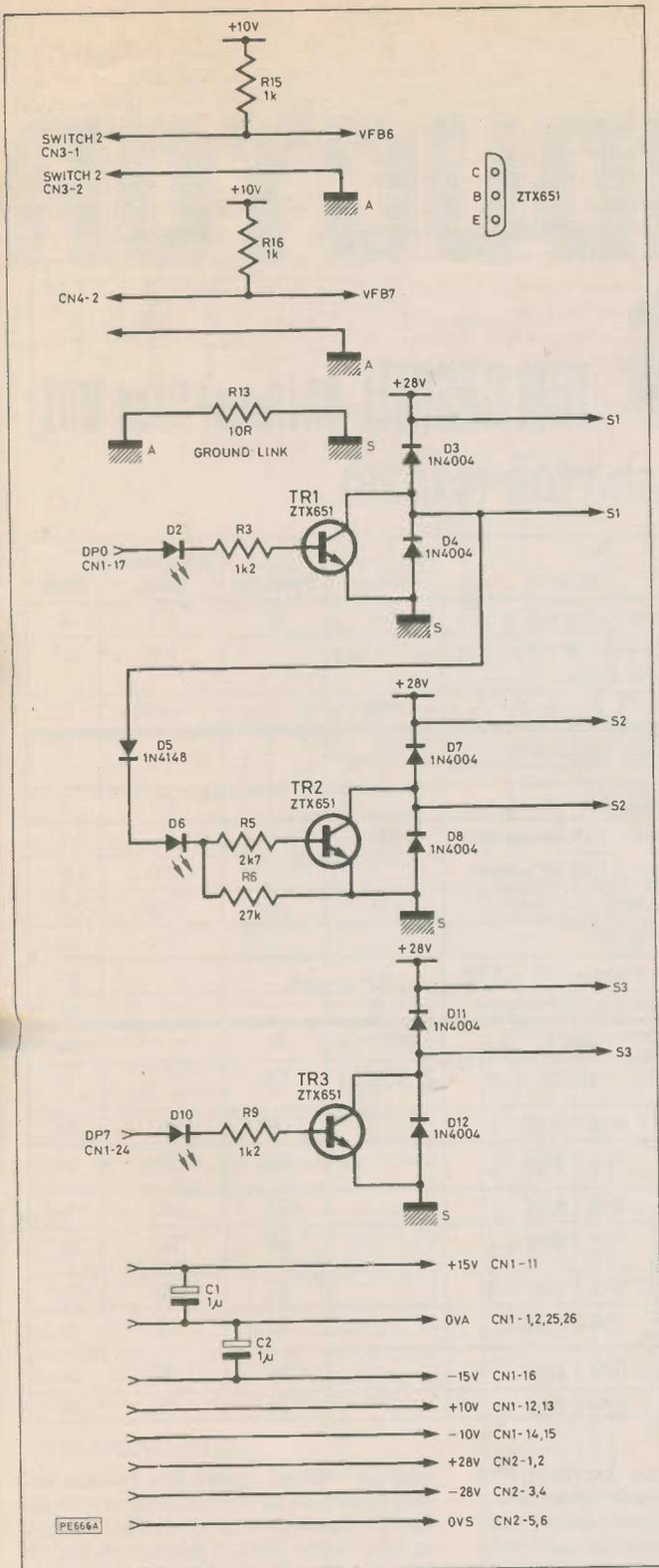


Fig. 9. Solenoid driver circuit

the power transistors in the event of overload if the motors are stalled. Resistors R18 to R21, R24 to R27, R30, R31 set the voltages and currents at which the protection operates. D2 and D3 are flywheel diodes protecting the power transistors from reverse voltages which can occur when an amplifier drives an inductive load. C6 to C8 and network R32/C9 are for providing high

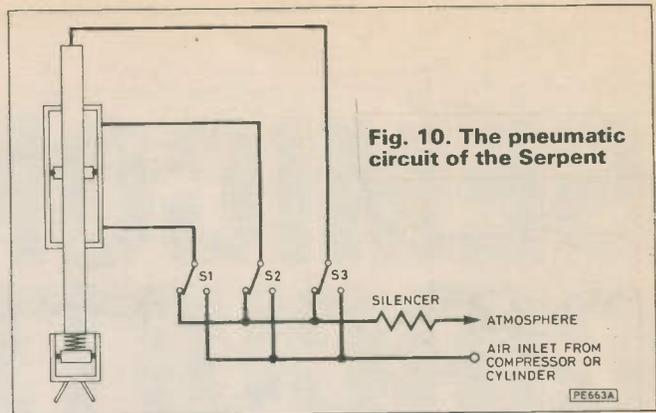


Fig. 10. The pneumatic circuit of the Serpent

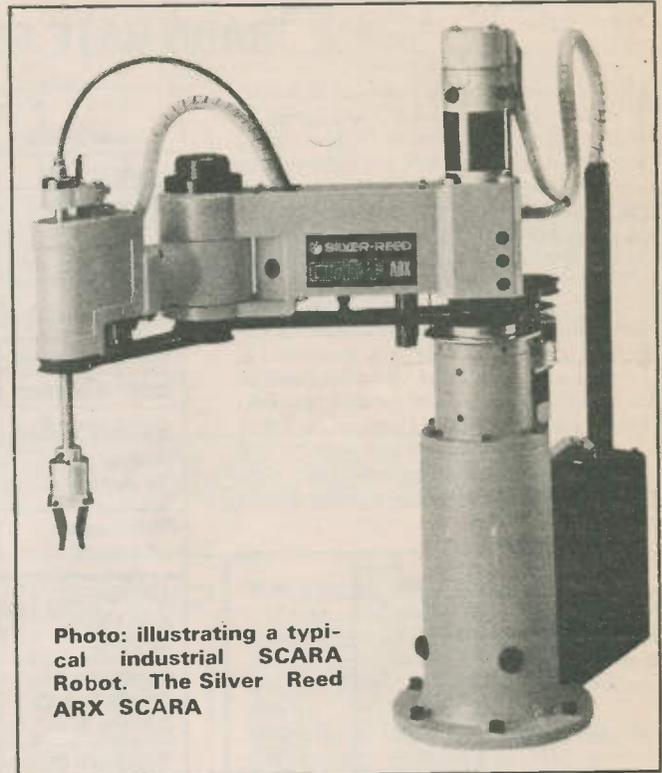


Photo: illustrating a typical industrial SCARA Robot. The Silver Reed ARX SCARA

Constructor's note

The SERPENTs are available as self-assembly kits or ready built from: Cybernetic Applications, West Portway Industrial Estate, Andover, Hants SP10 3PE. A range of FMS (Flexible Manufacturing System) workcell components will also be available.

frequency stability to the amplifier. The l.e.d.s give a visual indication of the output of the amplifier.

The solenoid driver circuit (Fig. 9) used for controlling the pneumatic circuit (Fig. 10) consists of little more than 3 transistors switching the solenoid current. The control voltages are the 0 to 5V outputs off one of the latches on the interface board. When DP₀ is high TR1 is turned on and saturates at only about 100mV thereby not getting hot despite 300mA of collector current. TR1 thus switches on valve S1 applying pressure to the lower end of the Z axis cylinder. The low voltage on TR1 collector holds off TR2 switching S2 into the state where air from the upper end of the cylinder is released to the atmosphere. Miniature needle valves on the cylinder adjust the ascent and descent rates of the axis to give it smooth travel.

SEMICONDUCTOR CIRCUITS

TOM GASKELL BA (Hons) CEng MIEE

BAUD RATE GENERATOR (4702B)

WITH the dramatic increase in recent years of cheap, readily available LSI circuits, there has been a corresponding increase in smaller scale i.c.s to service them and provide various interconnection and buffering facilities. These smaller i.c.s are often known as 'glue' chips, and typically comprise of data latches, tri-state buffers, memory control functions, etc. One of the most commonly used LSI devices is the UART—a Universal Asynchronous Receiver/Transmitter. This is a versatile i.c. which is used to convert serial data into 8-bit parallel data words, or parallel data into serial data stream. UARTs are often found in modems, RS232 inputs and outputs, and microcomputer cassette recorder interfaces; in fact, wherever serial and parallel data is required to interact.

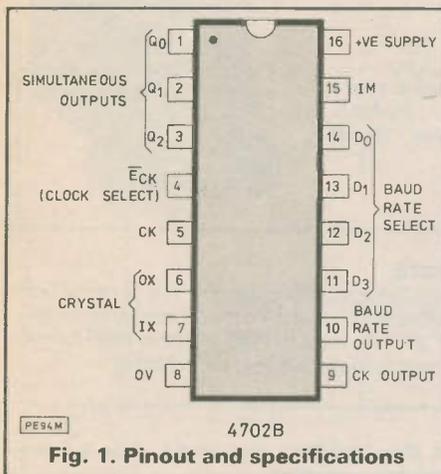


Fig. 1. Pinout and specifications

The UART, however, is not a fully self-contained device. Amongst other things, it requires one or two clocks—square wave oscillator inputs which control and define the speed of transmission or reception of data. The usual arrangement is that the serial data will be received or transmitted at a rate of one-sixteenth of the clock rate. Hence, if the clock was a 16kHz waveform, the serial data rate would be 1000 baud, where a baud is defined as one bit per second. This month's featured i.c. is a baud rate generator—a specially designed 'glue'

Characteristic	Notes	Minimum Value	Typically	Maximum Value	Units
Supply voltage	All spec's measured at 5.0V	4.5	5	5.5	V
Quiescent current	$E_{ck} = +5V$, $CK = 0V$ (Other I/P's at either)			1.0	mA
Temperature range		-40		+85	°C
Input high threshold	For logic 1 (all inputs)	3.5			V
Input low threshold	For logic 0 (all inputs)			1.5	V
Output high voltage	Current $< 1\mu A$ (all outputs)	4.5			V
Output low voltage	Current $< 1\mu A$ (all outputs)			0.5	V
Input current (all inputs)	Input at 0V	-15	-30	-100	μA
	Input at +5V			1.0	μA
Output current (all outputs)	Current source O/P = 4.5V	-0.3			mA
	Current sink, O/P = 0.4V	1.6			mA
Minimum clock pulse width (at pin 5)	Logic 1	120	60		ns
	Logic 0	120	60		ns
Propagation delay CK (pin 5) to CK O/P (Pin 9)	0 to 1 edge		130	260	ns
	1 to 0 edge		110	220	ns
Propagation delay CK O/P (pin 9) to $Q_0, Q_1, \text{ or } Q_2$	0 to 1 edge		53	367	ns
	1 to 0 edge		45	367	ns
Propagation delay CK (pin 5) to baud O/P (pin 10)	0 to 1 edge		37	85	ns
	1 to 0 edge		32	75	ns
Output transition time (all outputs)	0 to 1 edge		80	160	ns
	1 to 0 edge		35	75	ns

chip which provides an excellent and flexible way of feeding clock signals into a UART to produce industry standard baud rates, but which can also be used as a general purpose clock source and divider system.

BLOCK OPERATION

The 4702B is a 16 pin CMOS device, with pinout and specifications shown in Fig. 1. The block diagram is shown in Fig. 2. The clock source can be either external, via pin 5, or internally generated by a crystal oscillator. The crystal oscillator requires

only an external crystal, one resistor, and two capacitors to operate. Selection of the clock source is done at pin 4; if pin 4 is held at logic 0, the clock is taken from the CK input (pin 5), whereas if pin 4 is held at logic 1, or left open circuit (due to the internal pull-up resistor), the clock will be taken from the crystal oscillator. The clock signal which is selected is suitably buffered, and is made available at pin 9. The clock signal divided by 2, 4, and 8 is made available at pins 1, 2, and 3 respectively.

There then follow a number of divider circuits which provide a variety of clock

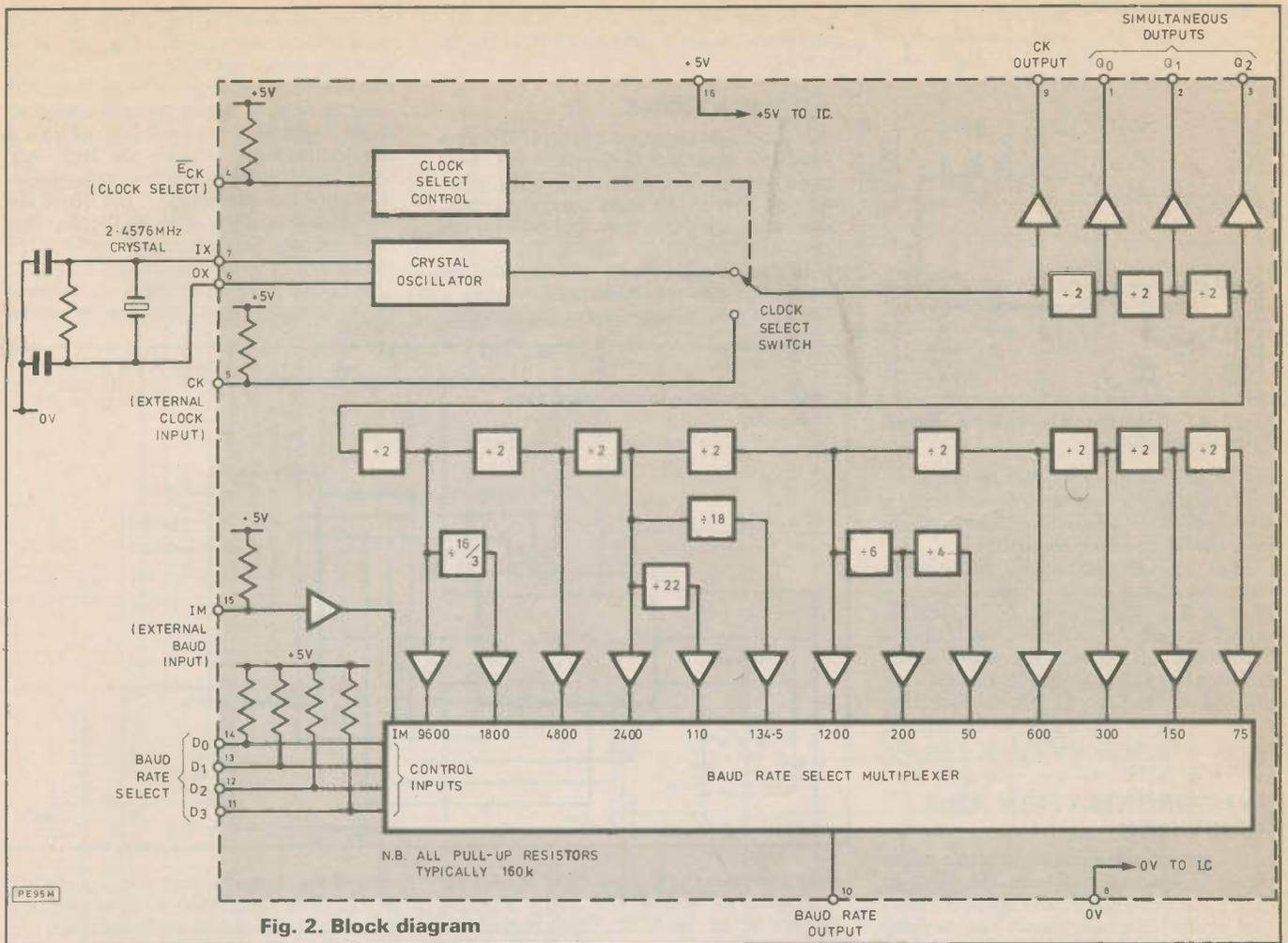


Fig. 2. Block diagram

frequencies to the baud rate select multiplexer or output switch. These clock frequencies, when used with a UART, will produce baud rates which are commonly used in electronic systems, from 50 baud which is used in old electromechanical devices, up to 9600 baud for modems and RS232 data links. The actual frequency which is fed to pin 10 can be selected by using the baud rate select inputs D_0 to D_3 . Fig. 3 shows the baud rate select codes, with their corresponding baud rate output and the actual output frequencies, which are 16 times the baud rate itself. Note that there are two different codes corresponding to 2400 baud: either of these may be used.

THE DIVIDERS

There are slight complications involving the implementation of the divider chain which give rise to inaccuracies, or even potential difficulties in some circumstances, with some of the outputs. The 134.5 baud output has a frequency error of -0.87% , and the 110 baud output has an error of -0.83% . The division by $16/3$ to produce the 1800 baud signal is done by dividing by 5 twice, then by 6 once, then by 5 twice, then by 6 once, etc. The average frequency of all this is exactly correct, but the output waveform is not a square wave (all other outputs are square waves, i.e.

D_3	D_2	D_1	D_0	BAUD RATE OUTPUT	ACTUAL OUTPUT FREQUENCY
0	0	0	0	1m/16	1m
0	0	0	1	1m/16	1m
0	0	1	0	50	800
0	0	1	1	75	1200
0	1	0	0	134.5*	2152*
0	1	0	1	200	3200
0	1	1	0	600	9600
0	1	1	1	2400	38400
1	0	0	0	9600	153600
1	0	0	1	4800	76800
1	0	1	0	1800	28800
1	0	1	1	1200	19200
1	1	0	0	2400	38400
1	1	0	1	300	4800
1	1	1	0	150	2400
1	1	1	1	110*	1760*

* = These values are approximate: The actual outputs are 2133Hz & 1745Hz respectively

Fig. 3. Output baud rate selection

50/50 mark/space ratio) and there is a small amount of frequency modulation present. When the divide-by-16 effect of the UART is taken into account, the resulting distortion in frequency is less than 1%, but care should be taken if the 1800 baud output is

to be used for other purposes. Similarly, the 134.5 and 110 baud errors would be easily tolerated in most UART based systems, but if used in other types of circuitry these frequency discrepancies should be borne in mind.

The baud select codes 0000 and 0001 both cause the I_m input (pin 15) to be routed directly to the baud rate output, with no division taking place. This can be used to select either external clocks to the output, or even to select the individual clock output, or half clock, quarter clock, or eighth clock, by connecting pin 15 to pin 9, pin 1, pin 2 or pin 3 respectively. Specifically, the standard rate of 19200 baud will be obtained if Q_2 (pin 3) is connected to I_m , then I_m is selected by the baud select codes.

USING THE I.C.

All the logic inputs to the 4072B have internal pull-up resistors to the +5V supply rail, which makes it very easy to use external switches to select various rates and facilities. The switches merely have to pull inputs down to 0V; when switched off, the internal resistors pull the inputs up to logic 1. The resistors can vary in value between 50k and 333k, but are typically around 160k. The use of actual logic signals at inputs rather than switches, is perfectly acceptable of course. The inputs are really

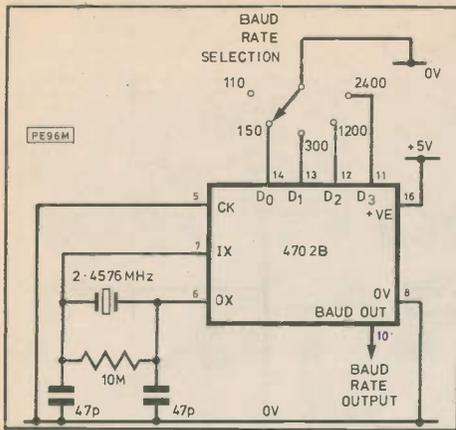


Fig. 4. Simple switched Baud Rate Generator

only CMOS compatible due to the minimum voltage required for a logic 1 being a fairly high 3.5V. The outputs, however, are both CMOS and TTL compatible.

The external components required to make the crystal oscillator operate can be seen in Fig. 4. Although a 2.4576MHz crystal is required to obtain the standard baud rates, it is perfectly acceptable to use different frequency devices if other uses are planned for the i.c. If this is done, the capacitor values might have to be changed to arrange for the correct loading of the new crystal, however.

SYNCHRONISATION AND RESETTING

The output of the baud rate select multiplexer is synchronised with the clock to cancel out the considerable internal delays that would otherwise occur due to time delays in the various stages of division. The baud rate output signal, however, can take several hundred nanoseconds to change after the baud rate select inputs have changed. The i.c. also has an internal reset facility. This senses the first high level at the CK input (pin 5) after \bar{E}_{ck} is taken low, and resets all the internal dividers. If \bar{E}_{ck} is taken high (logic 1) or left open circuit, thus selecting the crystal oscillator to be the clock, then CK must be kept low (held at

0V, or logic 0), since a high level at the CK pin would apply a continuous reset inside the i.c.

APPLICATIONS

A simple arrangement of the 4702B as a baud rate generator is shown in Fig. 4. A baud rate selection switch allows the selection of five of the most commonly used baud rates, all of which are derived from the 2.4576MHz crystal.

In Fig. 5, eight baud rate outputs are made available simultaneously by using a 74LS259 addressable latch. The simulta-

neous outputs shown in Fig. 5 with the baud rate selection codes given in Fig. 3, it can be seen that the output baud rates seem to 'lag one behind' what might be expected; 9600 baud is coming out of the pin where we might expect 4800 baud to come out. This is due to the delay between the baud rate select inputs being changed, and the respective baud rate appearing at pin 10 of the 4702B, as described earlier. By the time that the baud rate output changes, the 74LS259 has moved on to the next channel.

By using different crystals, or external clocks, many different frequencies can be

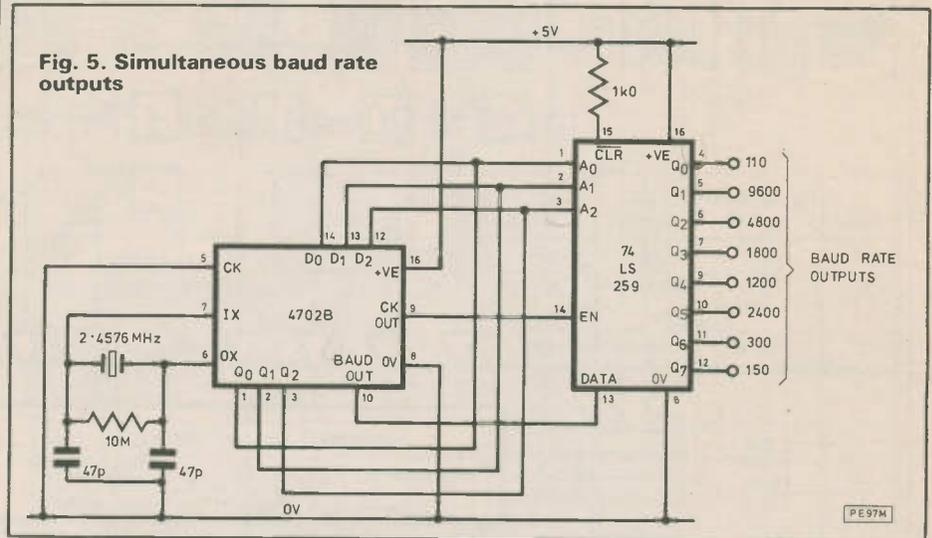


Fig. 5. Simultaneous baud rate outputs

neous outputs Q_0 , Q_1 , and Q_2 of the 4702B are used to address the eight separate latches in the 74LS259. These outputs go through two complete sequences of eight states of every period of the highest output frequency (ie. the frequency corresponding to 9600 baud). Using the outputs to control the baud select inputs D_0 , D_1 , and D_2 causes the 4702B baud rate output to represent eight different baud rates in sequence, changing in rapid succession. This multiplexed output is converted back to eight separate baud rate outputs in a de-multiplexing action by the 74LS259. Comparing

catered for. Although the i.c. is intended to be a baud rate generator, it can be used as a general purpose crystal oscillator/divider in many control and timing applications. In practice, the majority of applications are likely to use the i.c. as the clock for a UART in a data transmission type of circuit, so that is the basis of this month's applications project.

AVAILABILITY

The 4702B is available from Maplin Electronic Supplies Ltd.

AN RS232 TO CENTRONICS CONVERTER

MOST printers communicate with microcomputers using either the RS232 or the Centronics communications standards. The two are completely dissimilar; RS232 is a serial data arrangement, whereas Centronics uses parallel data transmission, each having their own advantages. Unfortunately, many printers only offer Centronics inputs, or cost considerably more if fitted with an optional RS232 interface. Similarly, some computers only have RS232 outputs available. This project enables printers with Centronics interfaces to be driven from RS232 serial data links, with a wide range of baud rates and data formats being catered for.

Fig. 6 shows the circuit diagram, with the control table shown in Fig. 7. IC1 is connected as a straightforward baud rate generator, with baud rate selection by S1 to S4. IC2 is a standard 6402 UART used as a receive device only, i.e. serial in, parallel out. Serial data comes in from pin 3 of the RS232 connector. Transistor TR3 along with its associated components form a buffer for the incoming data, converting it from its potential range of up to $\pm 12V$, to the 0 to +5V logic signal fed into the receive input of IC2, pin 20. TR2 drives the i.e.d. D18 to show when data is being received.

The serial data is converted to parallel within IC2 and fed out to the Centronics

output via pins 5 to 12. When one parallel word's worth of data has been converted by IC2, the DR output (pin 19) goes to logic 1. Assuming that the busy line from the printer is low (i.e. the printer is ready for new data) then the monostable of IC3 is triggered, and produces 5 μ s wide negative going pulse at IC3 pin 12. This pulse is used to reset the DR output (via the DRR pin), and is also fed to the printer as a STROBE line, to latch the parallel data into the printer. If the printer happens to be busy (i.e. it's still printing the last piece of information sent) it sets pin 11 of the Centronics connector to a high level. This prevents any triggering of IC3 and turns

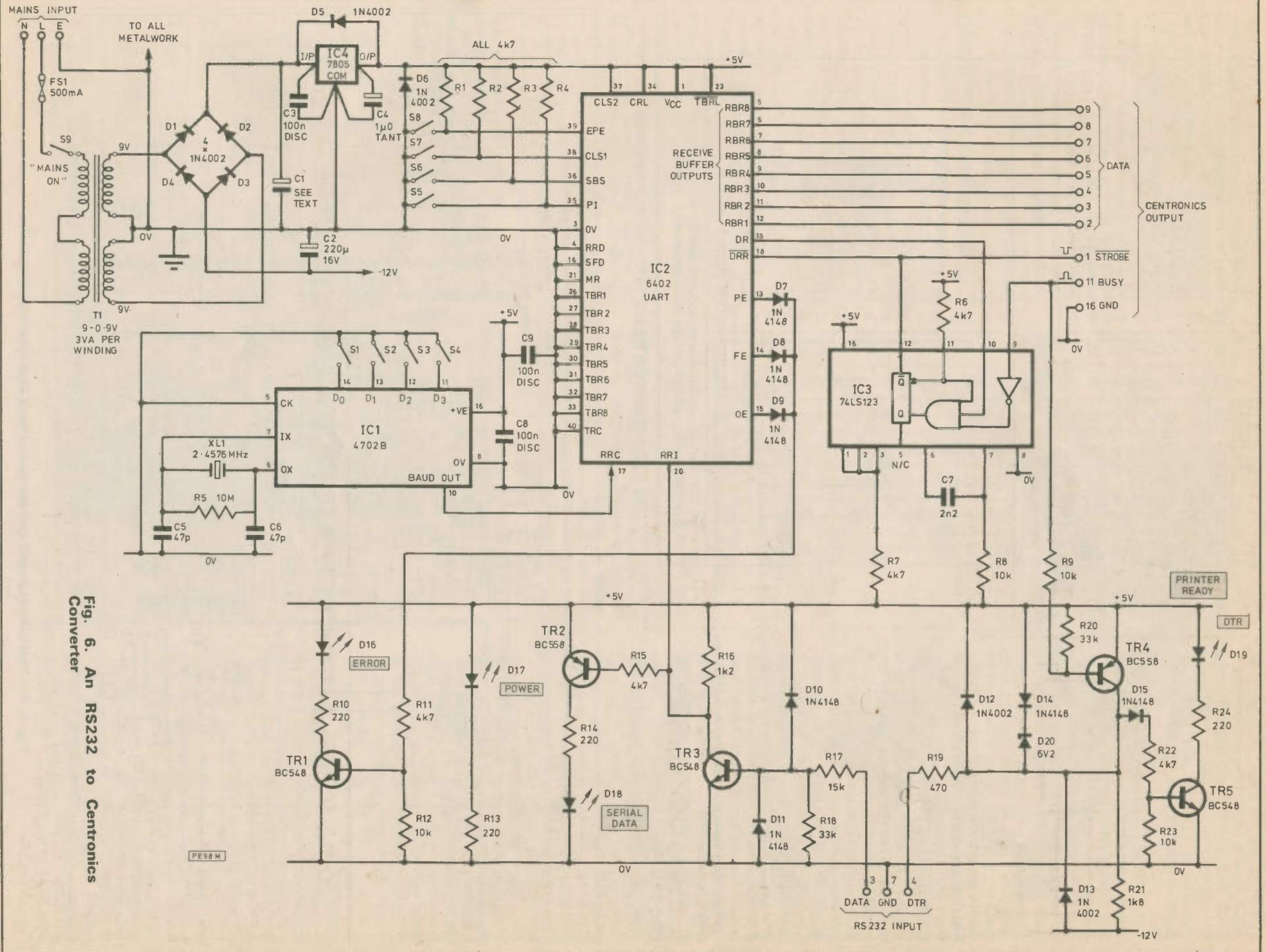


Fig. 6. An RS232 to Centronics Converter

TR4 off, causing the RS232 DTR line to be pulled down to -6.8V. (The negative excursion is limited by D14 and D20.) This tells the computer to wait before sending any more data. D19 is turned on as soon as the printer is ready for data, and off when it is busy.

D7, D8 and D9 form a simple 'OR' gate which causes D16 to be turned on if there was a parity error, framing error, or even over-run error in the received data. Hence, any illumination of D16 shows that the problems exist in the decoding of incoming serial data. S5, S6, S7 and S8 set up the various options for parity, stop bits, and character length as shown in Fig. 7. A regulated +5V, and an unregulated -12V supply, are provided by T1, D1 to D4, IC4 and their associated components.


CONSTRUCTION

The p.c.b. layout for the circuit is shown in Fig. 8. All components are kept very low profile to allow the board to be mounted close to the upper surface of a suitable box, with holes cut out to allow the d.i.l. switch (S1 to S8) and the l.e.d.s to poke through. The l.e.d.s are held firmly off the board with cut lengths of 'Rawplug' or similar, and the d.i.l. switch is held off the board by placing it in a standard (not low profile) 16 pin d.i.l. socket. Naturally, the transformer, fuse-holder, and mains switch (S9) are mounted inside the case itself. C1 should be at least 470µF 16V, and preferably higher in value—2200µF would be ideal. Due to the likely size, this capacitor may also be mounted off the board, and should be held

SWITCHES								FUNCTION
S1	S2	S3	S4	S5	S6	S7	S8	
x	x	x	x	x	x	x	0	ODD PARITY
x	x	x	x	x	x	x	1	EVEN PARITY
x	x	x	x	x	x	0	x	IF SELECTED WITH SWITCH S5
x	x	x	x	x	x	1	x	7-BIT CHARACTER LENGTH
x	x	x	x	x	0	x	x	8-BIT CHARACTER LENGTH
x	x	x	x	x	1	x	x	1 STOP BIT
x	x	x	x	x	1	x	x	2 STOP BITS
x	x	x	x	0	x	x	x	PARITY ENABLED
x	x	x	x	1	x	x	x	PARITY INHIBITED
BAUD RATE SELECTION				FUNCTION SELECTION				BAUD RATE
0	0	0	0	x	x	x	x	
1	0	0	0	x	x	x	x	1m/16
0	1	0	0	x	x	x	x	50
1	1	0	0	x	x	x	x	75
0	0	1	0	x	x	x	x	134.5
1	0	1	0	x	x	x	x	200
0	1	1	0	x	x	x	x	600
1	1	1	0	x	x	x	x	2400
0	0	0	1	x	x	x	x	9600
1	0	0	1	x	x	x	x	4800
0	1	0	1	x	x	x	x	1800
1	1	0	1	x	x	x	x	1200
0	0	1	1	x	x	x	x	2400
1	0	1	1	x	x	x	x	300
0	1	1	1	x	x	x	x	150
1	1	1	1	x	x	x	x	110

x = "Don't care" condition—can be either 0 or 1
 0 = Switch turned on (or a low voltage level)
 1 = Switch turned off (or a high voltage level)

Fig. 7. Control of the RS232 to Centronics Converter

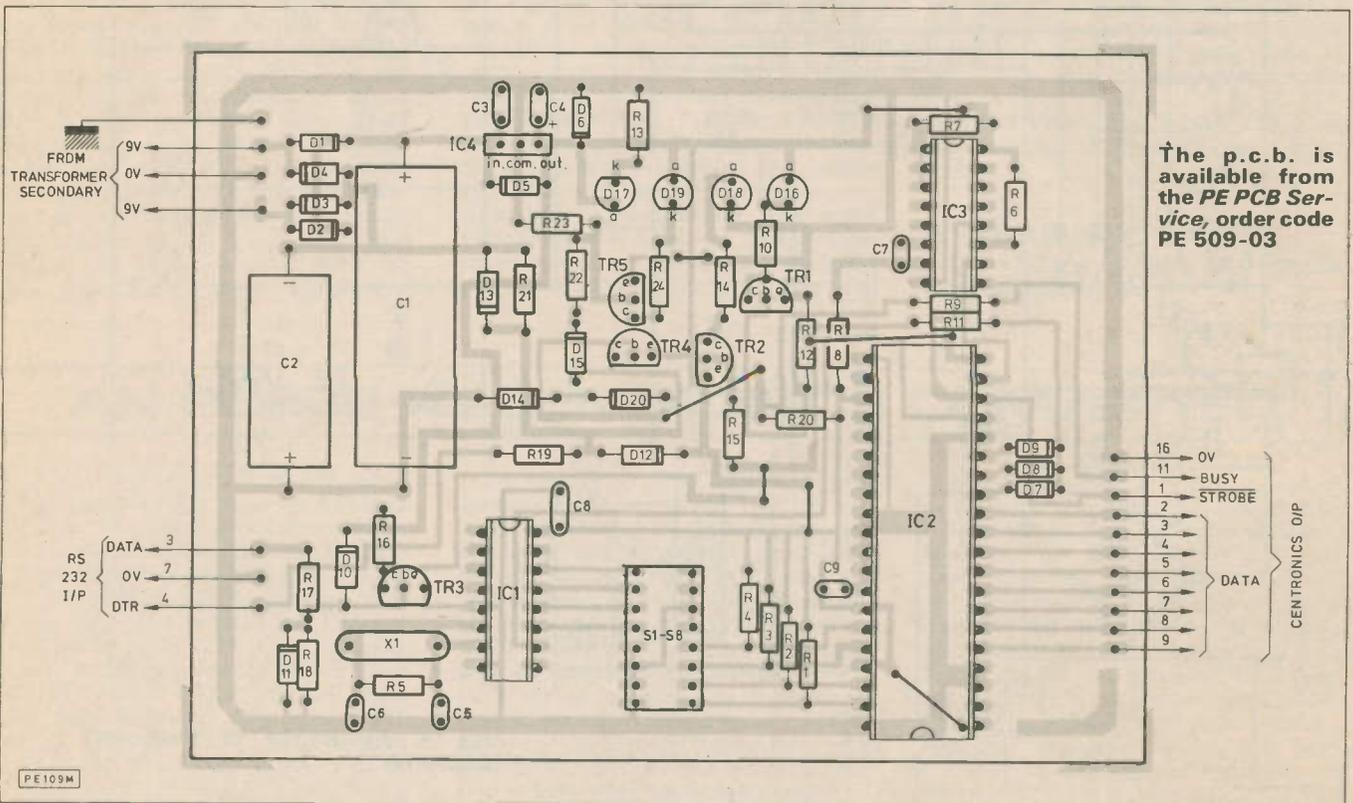

The p.c.b. is available from the PE PCB Service, order code PE 509-03

Fig. 8. Printed circuit board component layout and interwiring details


inside the case with suitable clips. Mains earth should be taken to the case (if metal) and all exposed metalwork, as well as to 0V. Take GREAT CARE with the mains wiring, and shroud all mains connections carefully.

The Centronics output can be wired up on a flying lead to a 'Centronics type' 36-way plug. The lead should be as short as practical; preferably less than 1 metre, and certainly it must be less than 1.5 metres in length, and should ideally be screened multicore or a ribbon cable. The RS232 connector is normally taken to be a 25-way 'D-type' connector with socket contacts. This can either be on a flying lead, or more conveniently as a chassis mounted socket fixed to the case.

USING THE CONVERTER

Switches S1 to S8 should be set according to the format of the computer's RS232 output. If this is not known, try 300, 600, 1200 or 2400 baud to start off with, and most probably 8-bit character length, one stop bit, and even parity, or possibly parity inhibited. The 'error' i.e.d. will flash if incorrect settings are being used, although sometimes the printer will apparently still function normally. Completely spurious characters being printed, or no printing action at all, is usually symptomatic of incorrect baud rate settings. Note that selecting parity to be inhibited can cause errors to be detached, since the UART will assume that the serial data contains no parity bits—if the incoming data *does* contain parity bits, errors will occur.

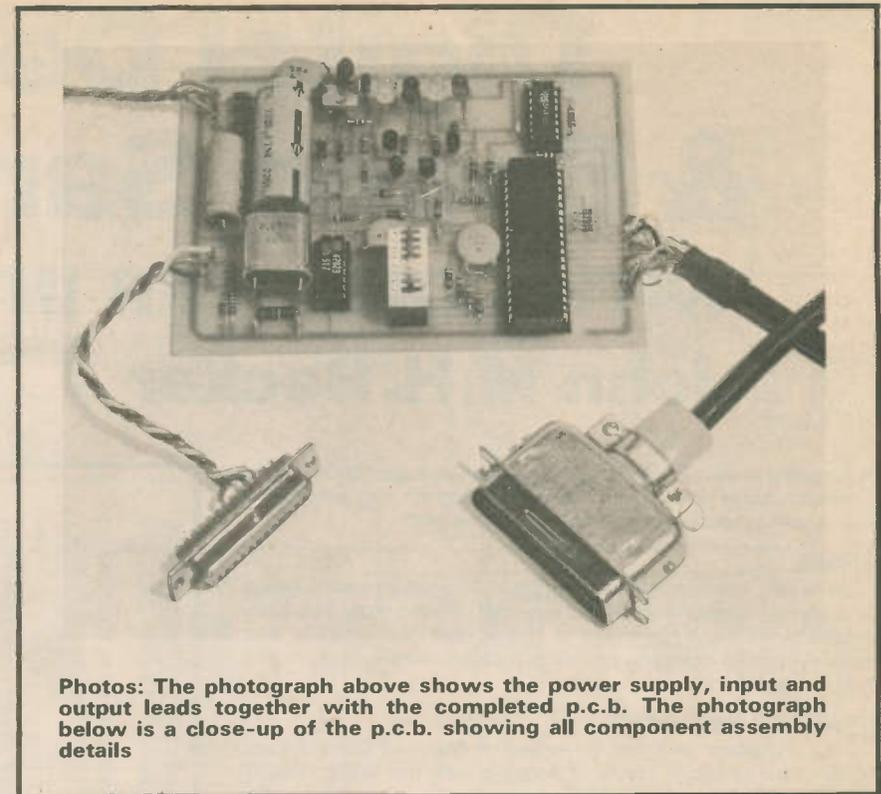Finally, note that the RS232 standard is notorious for having a vast number of alternatives with regard to pin numbering, data format, and handshaking lines. Specifically, the DTR line is often applied to different pins, so try moving DTR to pin 20 of the connector for a start; if that doesn't



Photos: The photograph above shows the power supply, input and output leads together with the completed p.c.b. The photograph below is a close-up of the p.c.b. showing all component assembly details


help, then it will be necessary to look more carefully at the RS232 requirements of the computer, especially if it requires more handshake lines to be held at a fixed voltage level, as sometimes happens. Despite this cautionary note, the RS232 to Centronics converter will prove ideal for use with almost all normal RS232 and Centronics systems.

SEMICONDUCTOR CIRCUITS

This article brings to an end the current series of Semiconductor Circuits. In the past two years we have looked at a wide range of different integrated circuits, from electronic locks, doorbells, and power supplies through to VCAs, timers, and thermometers. Throughout the series I have tried to steer slightly away from the beaten track of very well known i.c.s., whose characteristics and performance are thoroughly documented. Hopefully, this has had two significant effects; the first being to stimulate new ideas, showing different ways of going about circuit design and different techniques, and the second being to introduce the reader to specific integrated circuits which can implement functions either previously unknown, or perhaps which were considered too complex to be practical.

Throughout the series I have tried to give plenty of practical hints and suggestions about using the i.c.s. I do hope that you have found the articles to be of interest, and that some of the applications projects have been of practical use, either in their own right as self-contained circuits, or as illustrations of applications for the i.c.s. featured each month.

We hope to be able to produce some 'Semiconductor Circuits Specials' on an occasional basis in months to come, covering larger families of i.c. devices. For the moment, though, thanks to my friends and colleagues for their help and suggestions during the preparation of the series, and the best of luck to you if you decide to try some of the industry's more interesting or unusual i.c.s. for yourself! ★

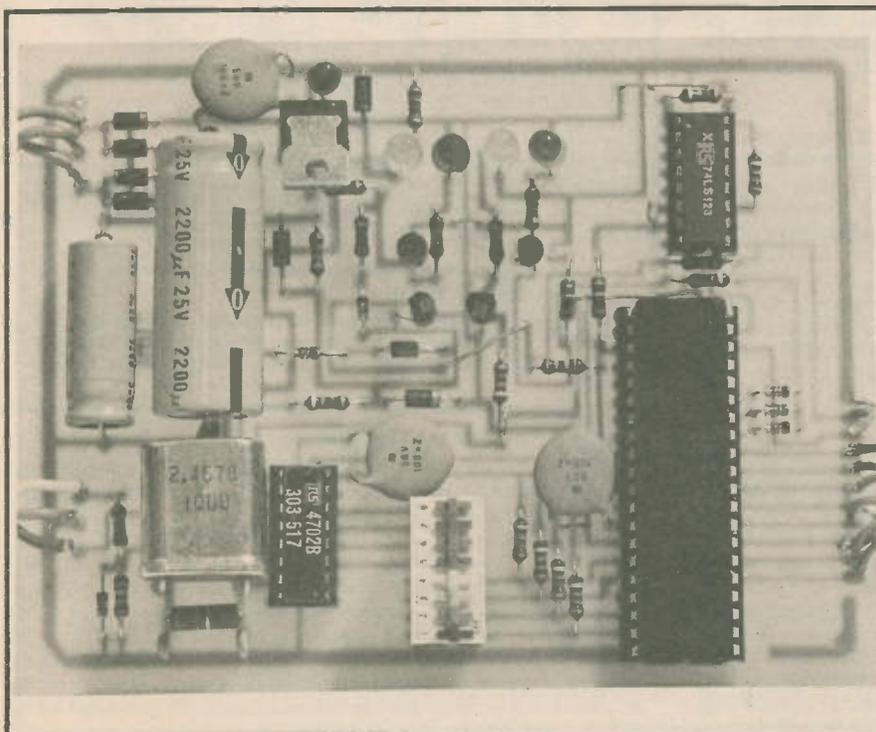

Digital Delay & Sound Sampler WITH COMPUTER INTERFACE

John M.H. Becker Part 4

In this, the final part of this project, we will complete all the constructional details with the wiring diagram and also take a look at using the unit as a computer only version.

WIRING

The wiring diagram is shown in Fig. 17 together with a list of p.c.b. points which have to be connected. Wiring should be fairly straight forward but remember to check each joint carefully. It is probably best to tick each connection on the wiring diagram and chart as each connection is made.

COMPUTER PROGRAMS

If the computer program is written in Machine Code a data transfer rate of about 15kHz is possible with the 3032. This is more than adequate for the computer to act as the memory for musical echo effects without the use of the unit's own memory. Programs written in Basic are unfortunately far too slow to use for normal musical purposes, though some special effects programs might be written successfully in Basic. I am not an expert on Machine Code programming, but Listing 1 shows an example of one code that enables the 3032 to be used as an echo unit. The 3032 uses a 6502 microprocessor, as do many makes of computer, including, I believe, the various Commodores, Apples, Atari, Acorn and BBC, so this code can probably be readily converted for these machines amongst others. For series 2, 3 and 4 Commodore PETs it is likely that the code can be used unchanged. For other machines, some location addresses as indicated will need to be changed. Your manual should give the equivalents.

BASIC PROGRAM

In the program in Listing 2, lines 100 to 260 are the sub routine that accesses the machine code program. Lines 270 to 360 are the decimal equivalents of the code's Hex numbers. These allow it to be self-entered, by line 130, into memory from location 1808. Then the Basic sub routine calls up the machine code routine which runs until an interrupt from the unit causes the code to drop back to Basic for the next instruction about the delay factor to be used. I have allowed for factors of 1 to 119 to be programmed, using 30464 memory locations (119 x 256). Other memory sizes may need a different maximum delay factor. Lines 790 to 870 are the Basic equivalent of the machine code so that you know the principle, but is far too slow for musical use.

KEYBOARD SCAN

If you are writing your own code, you will probably need to disable the computer's keyboard scanning routine by the use of SEI at the start. On the 3032 the keyboard is scanned 60 times a second, and this rate is clearly heard on an audio processed signal, as the data transfer is interrupted during the scan. For this reason on my own program I call up SEI to disable the scan and rely on the S1 switch on the unit to signal an interrupt so that the code drops back to Basic whereupon another delay factor can be entered. With your machine or experience in machine code programming you may find a different way. Switching S8 back to internal memory will have the same effect upon the computer as pressing the interrupt switch S1.

Program Listing 1

```
#0710 78 SEI ; DISABLE INTERRUPT
#0711 A2 00 LDX #00 ; & RESET LSB COUNTER
#0713 A9 01 LDA #01 ; SET LATCH TO CAI
#0715 8D 4B E8 STA #E84B ; TOGGLE CB2 DOWN
#0718 A9 CD LDA #CD ;
#071A 8D 4C E8 STA #E84C ;
#071D A9 ED LDA #ED ; TOGGLE CB2 UP & DOWN
#071F 8D 4C E8 STA #E84C ;
#0722 A9 CD LDA #CD ;
#0724 8D 4C E8 STA #E84C ;
#0727 A0 00 LDY #00 ; SET PA0-7 AS INPUTS
#0729 8C 43 E8 STY #E843 ;
#072C AD 4D E8 LDA #E84D ;
#072F 29 02 AND #02 ; LOOK FOR CAI SET AND
#0731 D0 08 BNE #073B ; IF SUCCESSFUL THEN
#0733 C8 INY ; BRANCH AHEAD
#0734 C0 00 CPY #00 ; OTHERWISE IF FAILED
#0736 F0 02 BEQ #073A ; AFTER 256 ATTEMPTS
#0738 D0 F2 BNE #072C ; THEN JUMP BACK
#073A 60 RTS ; TO BASIC
#073B E8 INX ;
#073C E0 00 CPX #00 ; INCREMENT LSB COUNTER
#073E D0 1E BNE #075E ; AND IF LESS THAN 256 STEPS
#0740 EE 63 07 INC #0763 ; THEN JUMP AHEAD
#0743 AC 63 07 LDY #0763 ; OTHERWISE INCREMENT MSB
#0746 C0 81 CPY #81 ; IF MAIN ADDRESS AND CHECK
#0748 90 05 BCC #074F ; THAT IS HAS NOT PASSED
#074A A0 06 LTY #08 ; MAXIMUM. IF IT HAS THEN
#074C 8C 63 07 STY #0763 ; THEN RESET TO MINIMUM
#074F EE 6B 07 INC #076B ; ADDRESS
#0752 AC 6B 07 LDY #076B ; ALSO INCREMENT DISPLACEMENT
#0755 C0 81 CPY #81 ; ADDRESS AND CHECK THAT IT
#0757 90 05 BCC #075E ; NOT PASSED MAXIMUM.
#0759 A0 08 LDY #08 ; IF IT HAS THEN RESET
#075B 8C 6B 07 STY #076B ; TO MINIMUM
#075E AD 41 E8 LDA #E841 ; GET SIGNAL DATA AND
#0761 9D 00 08 STA #0800'X ; STORE IT AT CORRECT ADDRESS
#0764 A0 FF LDY #FF ; SET PA0-7 AS OUTPUTS
#0766 8C 43 E8 STY #E843 ;
#0769 8D 00 08 LDA #0800'X ; GET DATA FROM DISPLACEMENT
#076C 8D 4F E8 STA #E84F ; ADDRESS AND SEND TO OUTPUT
#076F 4C 1D 07 JMP #071D ; THEN LOOP BACK AGAIN
```

LOCATIONS -
#E841 (DECIMAL 59457) DATA REGISTER
#E843 (DECIMAL 59459) DATA DIRECTION REGISTER
#E84B (DECIMAL 59467) SHIFT REGISTER & LATCH
#E84C (DECIMAL 59468) CB2 PLUS CAI POLARITY
#E84D (DECIMAL 59469) CAI INTERRUPT
#E84F (DECIMAL 59471) USER POST DATA LINES
#0800 (DECIMAL 2048) DATA STORE LOC (UPDATED BY PROGRAM)
AS WRITTEN PROG STARTS AT #0710 (DECIMAL 1808) FOR EACH 256 LOCATIONS
FURTHER ON INCREMENT THE #07 BY #01. THUS TO START AT DECIMAL 2320 (512
PLACES LATER) ALL #07'S BECOME #09. THE #08 MUST ALSO BE INCREMENTED BY
BY THE SAME AMOUNT/ IN THIS CASE TO #0A. ADJUSTING THE #81 RAISES OR
LOWERS THE MAXIMUM MEMORY LOCATION BEFORE RESET TO THE START ADDRESS, SO TO
RESET AT 32768 INSTEAD OF 33024 AS HERE/ #81 BECOMES #80.


Constructors' Note

A full kit of parts or separate p.c.b.s and Commodore 64 and PET computer programs are available from: **Becker Phonosonics**, 8 Finucane Drive, Orpington, Kent BR5 4ED.

COMPUTER ONLY VERSION

The unit has been designed so that the timing, addressing and internal memory circuits can all be omitted and the remaining circuits used directly with a computer. For this short version all components on p.c.b. Figs. 12, 14 and 15 are omitted, and also IC33, IC34, C34, R60, S4 to S8, VR14, 15, 18, 19, 20. IC24a is not used and its pins 11 to 15 should be taken direct to the 0V line. In the place where IC33 would have been connect pin holes 1 and 2, 10 and 11. Link p.c.b. points 14 to 52, and 40 to 54. Take 63 also to 39 (as well as to 15) so that the computer toggling output is used to generate the negative voltage needed. Insert C31 on the p.c.b. in Fig. 13, which then activates a frequency generator within IC5.

Fig. 17. Wiring diagram of the Digital Delay And Sound Sampler

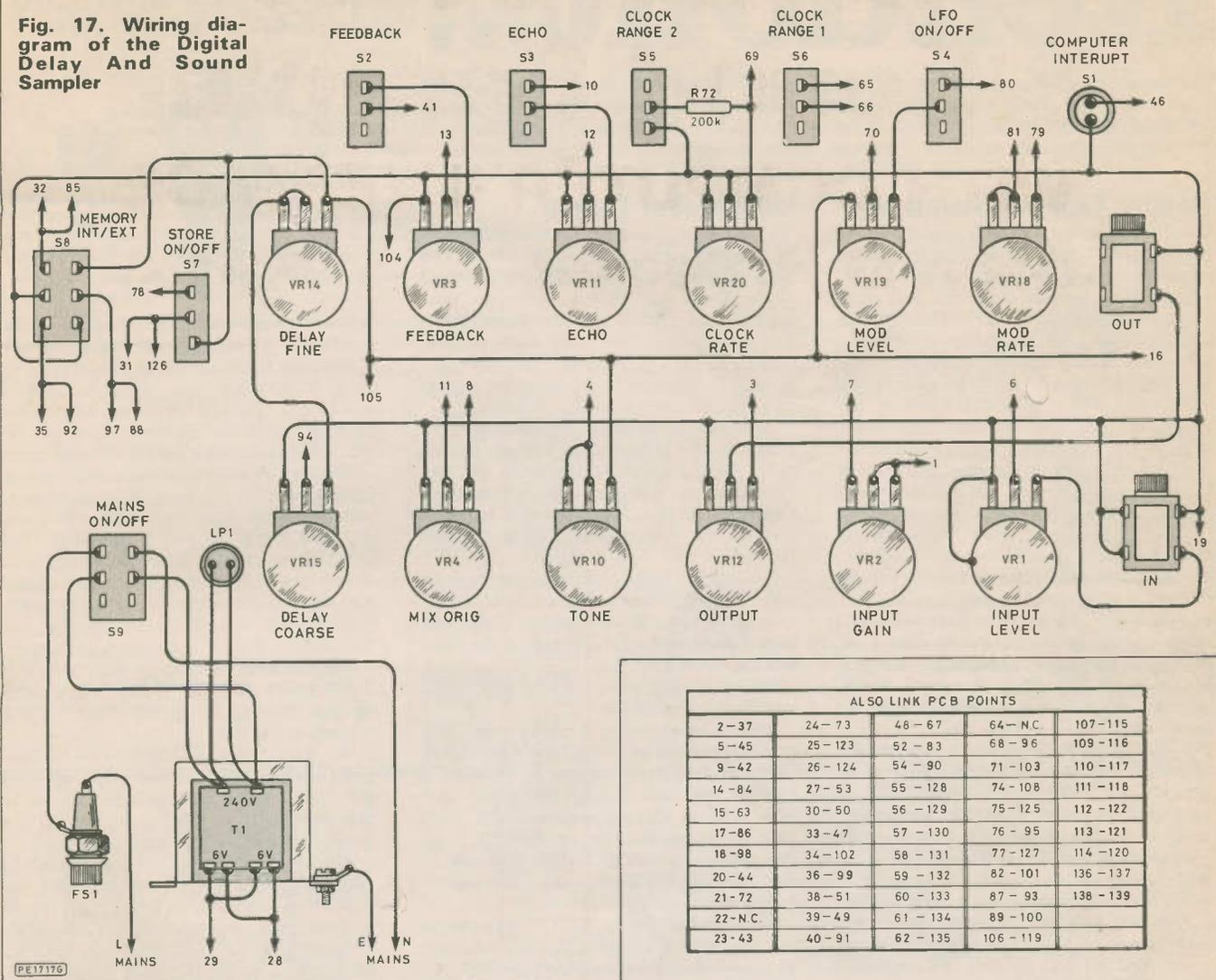

Program Listing 2

```

:00 PRINT "DELAY CONTROL BASIC SUB ROUTINE PLUS
110 PRINT "XXXXXXXXXXXX"
120 D=1808
130 FORA=0T099:READC:POKER+A,D,C:NEXTA
140 C=8:POKE52,1:POKE53,C
150 B=119
160 PRINT "DELAY FACTOR 1-":B
170 INPUT A
180 IFA<0THENA=A-B*(A)
190 IFA=0THENA=1
200 IFA<0THENA=A-B:GOTO200
210 A=B+1+C-A
220 IFA<0THENA=A-B*(A+1):GOTO220
230 POKE(D+83),C
240 POKE(D+91),A
250 SYS(D)
260 GOTO160
270 DATA120,162,0,169,1,141,75,232,169,205
280 DATA141,76,232,169,237,141,76,232,169,205
290 DATA141,76,232,160,0,140,67,232,173,77
300 DATA232,41,02,208,0,200,192,0,248,2
310 DATA208,242,96,232,224,0,208,30,238,99
320 DATA7,172,99,7,192,123,144,5,168,8
330 DATA140,99,7,208,107,7,172,187,7,192
340 DATA129,144,5,168,8,140,107,7,173,65
350 DATA232,157,0,8,160,255,140,67,232,189
360 DATA0,8,141,79,232,76,29,7,0,0
370
380
390 EXPLANATION OF ABOVE
400 ALL LINES FROM LINE 370 ON MUST BE OMITTED WHEN TYPING IN PROGRAM
410 "C" IS THE COMMODORE WAY OF SAYING "CLEAR THE SCREEN"
420 "XXXXXXXXXXXX" IS THE COMMODORE WAY OF MOVING THE CURSOR DOWN 10 PLACES
430 D=1808: START ADDRESS FOR MACHINE CODE AS GIVEN
440 FORA=0T099:READC:POKER+A,D,C:NEXTA
450 PUTS MACHINE CODE PROG DIRECTLY INTO MEMORY FROM LOCATION 1808 ONWARDS
460 C=8:POKE52,1:POKE53,C
470 THIS LOWERS THE TOP OF MEMORY AND RESERVES IT FOR SIGNAL DATA USE
480 LOCATIONS 52 & 53 ARE COMMODORE 2000, 3000, AND 4000 SERIES LOCATIONS
490 INDICATING LSB AND MSB OF TOP OF MEMORY
500 CALCULATES AS (8 X 256) + 1 = 2049: THUS THE MEMORY ABOVE 2048 IS
510 RESERVED, FURTHER EXAMPLE - POKE 52,10: POKE 53,15
520 MEANS (15 X 256) + 10 = 3850, I.E. MEMORY RESERVED ABOVE 3849
530 B=119:SETS MAXIMUM DELAY FACTOR
540 PRINT "DELAY FACTOR 1-":B
550 INPUT A
560 DELAY FACTOR OF ONE IS MINIMUM DELAY OF 1 X 256 MEMORY BYTES
570 DELAY FACTOR OF 119 IS MAXIMUM DELAY OF 119 X 256 MEMORY
580 BYTES = 30464 MEMORY BYTES - I.E. MEMORY LOCATIONS FROM 2048 TO 32512
590 (2048 + 30464) CAN BE USED FOR DATA STORAGE, FOR THE 3032 CONFUTER
600 THIS PUTS LAST 256 BITS OF DATA ONTO THE SCREEN (FOR INTEREST ONLY)
610 IFA<0THENA=A-B*(A) IF -VE NUMBER IS USED, CONVERT TO A +VE ONE
620 IFA=0THENA=1: PROHIBITS THE USE OF A ZERO FACTOR
630 IFA<0THENA=A-B:GOTO200: RESTRICTS RANGE
640 A=B+1+C-A: MAKES LOW NUMBERS HIGH AND HIGH NUMBERS LOW
650 IFA<0THENA=A-B*(A+1):GOTO220: RESTRICTS NUMBER TO WITHIN RANGE
660 POKE(D+83),C: RESETS MACHINE CODE COUNTER TO MINIMUM MEMORY LOCATION
670 POKE(D+91),A: RESETS DISPLACEMENT COUNTER TO MINIMUM
680 SYS(D): JUMPS INTO MACHINE CODE ROUTINE
690 GOTO160: AFTER DROPPING OUT OF MACHINE CODE GO FOR NEXT INSTRUCTION
700 IF YOU ARE LOCATING MACHINE PROG HIGHER IN MEMORY, SOME DATA NUMBERS
710 NEED CHANGING, FOR EXAMPLE IF YOU ARE LOCATING AT 2320 THEN IN
720 LINES 320 TO 360 NUMBERS "7" BECOME "9" AND "8" BECOMES "10"
730 TO LOWER MAXIMUM MEMORY LOCATION BY 256 PLACES TO 32768 THEN IN LINES 320
740 AND 340 "129" BECOMES "128".
750
760
770 BASIC EQUIVALENT OF MACHINE CODE
780
790 F=10:REM DELAY FACTOR
800 M=2048:D=M+F:POKE59467,1:POKE59468,205
810 POKE59468,237:POKE59468,205:POKE59459,0:Y=0
820 IFEPEEK(59469)=0THENB=0
830 Y=Y+1:IFE<255THENB=20
840 END: (RETURN TO BASIC SUB ROUTINE FOR NEXT DELAY FACTOR)
850 K=PEEK(59457):POKEK,K+M+1:IFM<33024THENM=2048
860 POKE59459,255:POKE59471,PEEK(D):D=D+1:IFD>33024THENM=2048
870 GOTO810
    
```

Readout...

The letters published below have been received in response to an Editorial in the July issue, they show a gratifying movement in some areas but tend to underline the need for Government initiative in technical education. We will be following up this subject (see this month's Editorial)—more views are welcome.

Twenty Years of Stagnation

Sir—I write in response to your editorial July 1985 and your favourable comments regarding AEB 'O' level electronics.

You may be aware that AEB also offer *Electronic Systems* at 'A' level. This syllabus attracts about 1,000 candidates each year.

It would be easy to believe that *Electronic Systems*, taken as a *Third 'A'* level alongside Maths and Physics, would produce the motivation required to steer sixth form students towards degree courses in Electrical Engineering. However, the Institution of Electrical Engineers do not appear to encourage such a subject combination.

I quote from their booklet *Have you got what it takes to be an Electrical Engineer*—"Minimum qualifications for entry to an electrical engineering degree course are normally GCE 'A' levels in Mathematics and Physics, and to have a wide choice of course, it is advisable to take a third subject. This may be a second science or maths subject or an arts subject such as economics".

This view is also echoed in a pamphlet published recently by the Standing Conference on University Entrance—I quote—"You might think Electronics 'A' level has specific relevance as a preparation for university courses in the same field... Most admissions tutors will be prepared to accept Electronics as a third 'A' level but it is a common view that a traditional arts subject such as English or a foreign language is preferable on general educational grounds".

I think that the reasoning behind these statements goes something like this—

1) Vocational and Practical subjects such as Electronics, Technology etc. do undoubtedly provide career motivation towards engineering,

but

2) They do not select sixth form students with high standards of literacy and scholarly culture—only an Arts 'A' level is capable of providing these assets,

therefore

3) It is better to have a shortfall of engineers rather than accept students who have been tainted by subjects which required them to increase competence by the *practice* of skills and the *use* of knowledge.

Perhaps the education system in our country is a glorious example of the tail wagging the dog to the detriment of everyone.

David L. Thompson,
Welbeck College,
Notts.

Independent Course

Sir—We have been regular subscribers to *Practical Electronics* for many years at The King's School, and have tried a wide range of the ideas and projects given in your excellent magazine. I was very interested in your comment under *Twenty Years of Stagnation* in your Editorial recently and thought I would mention what is happening in a number of Independent Schools.

Recognizing the need for development in this field the Independent Schools pooled their resources in the formation of The Independent Schools' Microelectronics Centre or ISMEC. The Centre is based in Oxford at Westminster College, North Hinksey.

For the last three years, Charles Sweeten was its Director and he had a couple of staff to help. Among the variety of activities and papers produced by the Centre is the Electronics course, coming in three sections, called *Electronics 11-13*, *Electronics 13-16* and *Electronics 16-19*.

The thinking behind the course is a coordinated and integrated approach, based on the *real* situation in schools. By using a systems approach and by fitting the work into existing Physics courses, and since nearly everyone does Physics up to 'O' level, this means that the old problem of how to find the time within the curriculum can be solved relatively easily.

We have been using "11-13" for a couple of years, have trialled the "13-16" and will be one of the trial schools for the "16-19" as soon as the work has been completed. Clearly there have been teething problems, but we have found the courses to be interesting, educationally valuable and fun to do.

I hope this gives you some encouragement in the light of your worried remarks.

J. M. Roslington
(Physics Department),
The King's School,
Worcester.

Unanimous Support

Sir—May I congratulate you on your editorial on the state of electronics education in Britain in the July issue of *Practical Electronics*.

As a manager of a 60 place ITeC with a strong electronics bias, my staff and I are acutely concerned with the issue and unanimously support your protest at the general neglect of technology in our education system.

However, some glimmer of hope may be emerging—albeit at the moment on a somewhat localised scale.



Among a growing range of socially useful hardware and software coming out of this Centre our most successful product to date is an Electronics Pack, commissioned by our local Education Authority, which aims to start "hands-on" electronics training for 9 to 10-year olds in primary schools.

We have monitored initial use of the Pack in local primary schools and can attest to its success and its popularity with both teachers (non-technical) and pupils alike. The first 500 Packs are now out in force in classrooms in our 125 local primary schools and samples are being requested from isolated schools in Merseyside, Cheshire and Lancashire. We feel it deserves wider use.

We are now proceeding with a further 1,000 packs and would like to see them spread throughout more than 12,000 schools in the UK.

We have two local teachers on secondment working with us to develop Stage II of the pack, which will include devices to interface with a BBC computer in the conduct of more advanced experiments.

This is only one of several initiatives taken by Wirral Metropolitan Borough Education Authority to introduce a strong technological element into its education programme which I feel might well be worth an article. Charles Harrison, Wirral's Science Inspector of Schools has offered to host a fact finding tour of local schools and colleges.

Please keep up the pressure!

Vic Taylor,
Bromborough In-Tech Centre,
Wirral, Merseyside.

Doing Our Best

Sir—We are trying to do our best! (Ref. UK Losing Ground—*Editorial*, July '85).

When we opened in 1979 as a Sixth Form College in Warrington we introduced AEB 'A' level Electronics Systems. Having a "New Town" with Science Parks we were perhaps more conscious of the wind of change than other areas of the country.

Since we have taken on board AEB 'O' level Electronics (as soon as it was introduced) and 'O' and 'A' level Computer Science. From our viewpoint the constraints we feel are:

Accommodation. We have one physics laboratory and two classrooms converted to an "Electronics Lab" and "Com-

PRACTICAL ELECTRONICS PRINTED CIRCUIT BOARD SERVICE

Printed circuit boards for certain PE constructional projects are now available from the PE PCB Service, see list. They are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: **PE PCB Service, Practical Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG.** Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title, order code and the quantity. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

NOTE: Please allow 28 days for delivery. We can only supply boards listed here.

PROJECT TITLE	Order Code	Cost
Spectrum Autosave	MAR '84 403-01	£2.90
Sustain Unit	405-02	£2.90
Audio Signal Generator	MAY '84 405-03	£4.28
"	405-04	£2.90
Cross Hatch Generator	JUNE '84 406-01	£3.52
Simple Logic Analyser I	407-01	£7.73
EPROM Duplicator	JULY '84 407-02	£3.74
Alarm System	407-03	£3.19
Oscilloscope Calibrator	407-04	£4.23
Comm. 64 RS232C Interface	408-01	£3.02
Field Measurement	AUG '84 408-02	£3.19
"	408-03	£2.90
Simple Logic Analyser II	408-05	£2.93

Parallel to Serial Converter		409-01	£2.92
Through the Mains Controller	SEPT '84	409-02	£2.90
"		409-03	£2.90
Logic Probe	OCT '84	410-01	£2.90
Computer DFM Adaptor	NOV '84	411-01	£2.90
Ni-Cad Charger	DEC '84	412-01	£2.90
Outrider Car Computer (Set of 2)	JAN '85	501-01/2	£9.10
Modular Audio Power System			
Pt-1: Power Amp Board	FEB '85	502-01	£4.19
Spectrum DAC/ADC Board		502-02	£3.69
Modular Audio Power System			
Pt-2: Pre-Amp/Line Driver		503-01	£5.00
Main Board		503-02	£5.12
Heart Beat Monitor	MARCH '85		
Main Circuit Board		503-03	£8.90
Detector		503-04	£6.62
Low Cost Speech Synthesiser		503-05	£3.42
Power Control Interface		504-01	£3.36
Disc Drive PSU		504-02	£6.54
Modular Audio Power System	APRIL '85		
Pt-3: Test Signal Source		504-09	£4.20
Power Supply		504-10	£4.17
Amstrad Synthesiser Interface		505-01	£4.23
Rugby Clock Pt-2		504-03	£24.22
"	MAY '85	504-04	£9.06
"		504-05	£5.12
"		504-06	£9.54
"		504-07	£5.40
"		504-08	£10.24
CBM64 MUSIC KEYBOARD			
Keyboard	JUNE '85	506-02	£4.55
Main PCB		506-03	£3.50
MTX 8 Channel A to D	JULY '85	507-01	£3.92
Voltmeter Memory Adaptor		506-01	£3.28
Envelope Shaper	AUGUST '85	508-01	£3.73
Car Boot Alarm	SEPT '85	509-01	£2.90
RS232 To Centronics Converter		509-03	£4.95

puter Lab" respectively. These labs are in use for teaching purposes every minute of every day, and even then we have to teach physics 11 hours each week out of the laboratory.

Staffing. Staffing policy is number, rather than curriculum based. For example, our school is allocated a certain number of staff and has to cover curriculum needs from this.

Thus numbers in physics and electronics and maths classes are large in order to support minority subjects. With the practical work involved in electronics we therefore have to limit numbers taking the subject (even if we had the accommodation to cope).

Perhaps the most worrying aspect of all is the fact that none of our electronics or physics students over the past years has ever considered the possibility of a career in teaching. They are all too aware of the low esteem in which the teaching profession is currently held by society.

We are fortunate in that we are due to have a New Technology Design Centre built at the college. However, in the current economic climate we are not counting on anything until we see the first brick laid.

How do we staff it? We have to find the staff from our normal allocation!

We do try but need support from society.

D. Henderson, B.Sc.
Priestly College, Warrington.

PRESTEL UNITS

These are brand new and we understand tested, came with manufacturer's guarantee now void as the manufacturer no longer trades. These originally sold for over £150. We offer them complete, except for 7 plug in i.c.'s and price is only £14.95 (less than the value of the modem included).



25A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. Independent 60 minute memory jogger. A beautiful unit at £2.50.



TOP OF THE POPS LIGHTING

if you use our disco switch These have 12 x 10 amp changeover switches each rated at 10 amps so a whole street could easily be lit with one. Switches adjustable and could be set to give a running light, random flashes, etc etc. 230 volts main operation. Brand new, made by Honeywell. Offered at approximately one third of cost. **ONLY £6.90**

EXTRACTOR FANS - MAINS OPERATED

Woods extractor.
5" - £5.75, post £1.25. 6" - £6.95, post £1.25.
5" Plannair extractor £6.50, post £1.25.
4" x 4" Muffin 115v. £4.50, 230v. £5.75, post 75p.
All the above ex-computer, those below are unused.
4" x 4" £8.50, post 75p.
9" American made £11.50, post £2.00.
Tangential Blower 10 x 3 air outlet, dual speed £4.50, post £1.50.



BURGLAR ALARM PARTS

Pressure Pads unnoticeable under carpets. Make contact when trodden on, 2" x 4" £1.75, 12" x 10" £1.25.
Control Box for use with pressure pads door/window. Switches - maintains alarm once triggered - fitted with removable key master switch - test for working switch, relays etc. £11.50.
Alarm Bell 12" gong heavy cast construction - mains operation £23 + £4 carriage.
Squawker Alarm 6-12v DC or 12-24v AC as used in mugger alarms also suitable car or m/c 75p each, 100 £58, 1000 £375.
Quiet Alarm will tell just you that alarm has been triggered. 9v DC, selectable three levels of sound £1.15.
Wiring Staples plastic headed hardened pin right size for fig 8 flex-box of 500 £2.95.

ROCKER SWITCHES Standard size fit 11.5 x 28 mm cut out. Single pole on/off - 15p each, 1000 for £75. Single pole changeover 20p each, 1000 for £100. Single pole changeover with centre off - 25p each, 1000 for £1.25. Single pole on/off with neon 36p, 1000 for £180.

MINIATURE WAFER SWITCHES

2 pole, 2 way - 4 pole, 2 way - 3 pole, 3 way - 4 pole, 3 way - 2 pole, 4 way - 3 pole, 4 way - 2 pole, 5 way - 1 pole, 12 way. All at 25p each or 10 for £2.00.



12volt MOTOR BY SMITHS

Made for use in cars, etc. these are very powerful and easily reversible. Size 3/2" long by 3" dia. They have a good length of 1/4" spindle. Price £3.45. Ditto, but double ended £4.25.



MINI MONO AMP on p.c.b., size 4" x 2" (app.)

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



J. BULL (Electrical) Ltd.

(Dept. PE) 34-36 AMERICA LANE, ESTABLISHED
HAYWARDS HEATH, SUSSEX RH16 3DU 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add £1 service charge. Monthly account orders accepted from school and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote.



SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Dept., Practical Electronics, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5846.)

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

COMPONENTS FOR ROBOTICS, motors, micro switches, relays. S.A.E. details: I.J.C., 14 Lechlade Gardens, Fareham, Hants PO15 6HF.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. **FORRESTERS (NATIONAL RADIO SUPPLIES)**, Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

BARGAIN BUMPER BOX OF BITS

Contains: working calculator, working watch module, Various ICs, transistors, display tubes, PCBs, diodes batteries, gears, switches, etc., etc. All useful items. Would cost much, much more if bought separately. **ONLY £15** (inc VAT and P&P). Send cheque/PO to:

Barbara Page, Spares Dept., Decimo Ltd, 4-18 Chobham St., Luton LU1 3BS

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 Mfd's. — 5p.
22 & 47—6p. 100—7p. (50V—8p) 220—8p. (50V—10p), 470—11p. (40V—16p), 1000/15V—15p. 1000/25V—25p. 1000/40V—35p. 4700V/25V—70p.

Subminiature bead Tantulum electrolytics.
0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 6.3V — 14p.
2.2/35V, 4.7/25V—15p. 10/25V, 15/16V—20p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V—32p.
15/25V, 22/25V, 47/10V—35p. 47/16V—80p.

Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.
10% 390 pf. to 4700 pf.—4p.

Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.

Polystyrene E12 Series 63V. Horizontal Mtng.
10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.

Miniature Polyester 250V Vert. Mtng. E6 Series.
0.1 to 0.68—4p. 1—5p. 15, 22—6p. 33, 47—10p.
.68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

Mylar (Polyester) Film 100V. Vertical Mounting.
0.01, 0.022, 0.047—3p. 0.1, 0.22—4p. .04, .05, 0.1—5p.

High Stability Miniature Film Resistors 5%.
1/4W E24 Series 0.51R—10M0. — 1p.
1/2W E12 Series 1R0 to 10M0. — 11/2p.
1W E12 Series 10R to 10M0. — 5p.

1/4W metal film E12 Series 10R-1M0. 5% — 2p. 1% E24 — 3p.
1N4148—2p. 1N4002—4p. 1N4006—6p. 1N4007—7p.

BC107/8/9—12p. BC147/8/9, BC157/8/9, BF195 & 7—10p.
8 Pin i.c.'s. 741 Op. amp.—20p. 555 Timer—24p.

Dil. Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.
LED's. red, green, yellow, 3 & 5mm.—10p. 8mm.—35p.

Grommets for 3mm.—2p. Grommets for 5mm.—2p.
20mm. Q.B. Fuses .15, .25, .5, 1, 2, 3 & 5A—5p.

20mm. Anti Surge 100mA to 50A—8p.
20mm. Fuseholders P.C. or Chassis Mtng.—8p.

Battery Snaps (pairs) PP3—6p. PP9—12p.
400mW Zener diodes E24 series 2V7 to 33V—8p.

Prices VAT inclusive Post 20p. (Free over £5.00).

THE C.R. SUPPLY CO.
127, Chesterfield Rd., Sheffield S8 0RN.

RECEIVERS AND COMPONENTS

TRANSCEIVERS, RECEIVERS. Large selection. Send SAE with enquiries to: **KRAMER COMMUNICATIONS**, 86 Fendale, Waterlooville, Portsmouth, Hants.

TURN YOUR SURPLUS capacitors, transistors, etc into cash. Contact **COLES HARDING & CO.**, 103 South Brink, Wisbech, Cambs. Tel. 0945 584188. Immediate settlement.

7 SEGMENT LED DISPLAYS. 4 inch C.A.N. Six displays on P.C.B. £1.00 per board. p&p 25p. **BLUE ELECTRONICS**, 13 Sketty Avenue, Sketty, Swansea SA2 0TE. Tel. (0792) 476584.

COMPUTING

BBC MICRO BAR CODE READER with software to read Acom user codes and product codes—Only £15 (inc. VAT and P&P). **RED GIANT SOFTWARE LTD.**, 3a Oakcroft Close, Pinner, Middx HA5 3YY.

Z80 PROCESSOR CARDS, RAM CARDS. Old stock ideal for educational or hobbyist applications. Also large range of new cards. For details contact **ASD ENGINEERING**, Erith, Kent DA8 1QL. Tel. (03224) 49235.

SERVICE SHEETS

BELLS TELEVISION SERVICES for service sheets of Radio, TV, etc £1.50 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to **B.T.S.**, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

SOLE SUPPLIERS TV/VIDEO repair manuals/circuits. 1000's s/manuals supplied by return. S/sheets £2.50 except civ/ m.centres/stereos £3.50. LSAE with every order/query please brings free price list/magazine inc. s/sheet or phone 0698 884585/883334 outwith business hours. **TIS(PE)**, 76 Church Street, Larkhall, Lanarkshire.

FOR SALE

PROMS - EPROMS - PALS

EPROMS from £3.25 (2716/2732/2764 etc)
PROMS from £1.50 (TBP/82S/63 series etc)
PALS from £4.25 (12H6/16C1/16L8 etc)

Full Programming Service available
SAE for full price list (incl. RAMs etc)

Any i.c. supplied - if it exists we will find it
PLS, 16 Wordsworth Drive, Cheam, Surrey SM3 8HF.
Phone 01-644 8095 (usually manned 0800-2000 hrs)
Private and professional enquiries welcome.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)

NAME

ADDRESS

.....

.....

PRACTICAL ELECTRONICS

Classified Advertisement Dept., Room 2612, King's Reach Tower, Stamford Street, London SE1 9LS Telephone 01-261 5846

Rate:
36p per word, minimum 12 words. Box No. 60p extra.

HOME SECURITY

WHO CAN PUT A PRICE ON A PEACE OF MIND

PROFESSIONAL EQUIPMENT AT LOW! LOW! PRICES.
HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES
 ADVANCED SECURITY PRODUCTS LTD
 2 Ealing Road, Aintree,
 Liverpool L9 0HU, Merseyside.
Tel: 051-525 3440

FIVE CATALOGUE PHONE OR S.A.E.

CENTURION ALARMS

Manufacturers of Professional Alarm Equipment, for DIY & the TRADE. Send now for our New 16-page Brochure, Full of Information & the Lowest prices.



CENTURION Dept PE
 93 Wakefield Road,
 Huddersfield.
 HD5 9AB
 W. Yorks.

Tel: (0484) 21000
 or 35527 24 hr.

Centurion is a Registered Trademark of Centurion Alarms

MISCELLANEOUS

TINPLATE YOUR PCB'S for easy soldering. Hot solution dip for ten minutes. Half gallon kit £6, post paid. HERBERT, 93 Carisbrooke Road, Newport, I.O.W.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC. Faced steel. Vast range, competitive prices start at a low £1.50. Punching facilities at very competitive prices. BAZELLI, (Dept. 23), St. Walfreds, Foundry Lane, Halton, Lancaster LA2 6LT.

THE SCIENTIFIC WIRE COMPANY
 811 Forest Road, London E17. Telephone 01-531 1568

ENAMELLED COPPER WIRE				
SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	9.09	5.20	2.93	1.97
TINNED COPPER WIRE				
14 to 30	3.97	2.41	1.39	0.94
Fluxcore Solder	5.90	3.25	1.82	0.94

Prices include P&P VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

MISCELLANEOUS - CONTD.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showroom, opposite Odsal Stadium.

CLEARING LABORATORY, scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders etc. Tel. 0403-76236.

HEATHKIT U.K. SPARES AND SERVICE CENTRE. Cedar Electronics, Unit 12 Station Drive, Bredon Tewkesbury, Gloucestershire. Tel. (0684) 73127.

3 STATE TTL LOGIC PROBE
 Ready to use in durable moulded plastic case complete with lead and crock clips to connect to 5v supply on board under test.
 Three colour L.E.D. display shows high, low or intermediate logic levels up to 1 MHz. Suitable for fault finding in most digital applications.

Special Offer Price £14.50 + 50p p&p
 Cheque/P.O. to:
LYON ELECTRONICS
 23 Langloft Road, Stroud, Gloucestershire GL5 1LS
 Tel: 04536 79053

To advertise on these pages
Phone Mandi 01-261 5846

COURSES

FULL-TIME TRAINING COURSES

2 YEAR B-TEC National Diploma (OND) ELECTRONICS & COMMUNICATIONS ENGINEERING
(Television & Computing)

15 MONTHS B-TEC National Certificate (ONC) ELECTRONIC EQUIPMENT SERVICING
(Television & Video)

15 MONTHS B-TEC National Certificate (ONC) COMPUTING TECHNOLOGY

9 MONTHS B-TEC Higher National Certificate (HNC) COMPUTING TECHNOLOGY & ROBOTICS

HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK
 SHORT COURSES WITH PREVIOUS KNOWLEDGE
 NO EXTRA CHARGES FOR OVERSEAS STUDENTS

Prospectus from:
LONDON ELECTRONICS COLLEGE
 Dept: AA, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721.

★ BAKER ★
 GROUP P.A. DISCO AMPLIFIERS post £2

150 watt Output, 4 input Mixer pre-amp. Illustrated £99
 150 watt Output, Slave 500 mv. Input 3 Speaker Outputs £80
 150 + 150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs £125
 150 watt P.A. Vocal, 8 inputs, High/Low Mixer Echo Socket £129
 100 watt Valve Model, 4 inputs, 5 Outputs, Chassis only £99
 60 watt Mobile 240v AC and 12v DC, 4-8-16 ohm + 100v line £89
 Reverb Unit for Microphone or Musical Instruments £35 PP £1.
 Electronic Echo Machine for micretc £85 PP £1. Deluxe £95.

BAKER LOUDSPEAKERS

Type	Model	Size	Watts	Ohms	Price
P.A./Disco/Group	DG50/10	10in	50	8/16	£20.00
Midrange	Mid 100/10	10in	100	8	£25.00
Hi-Fi	Major	12in	30	4/8/16	£18.00
Hi-Fi	Superb	12in	30	8/16	£28.00
P.A./Disco/Group	DG45	12in	45	4/8/16	£18.00
Hi-Fi	Wooler	12in	30	8	£25.00
Hi-Fi	Auditorium	15in	60	8/16	£39.00
P.A./Disco/Group	DG75	12in	75	4/8/16	£22.00
P.A./Disco/Group	DG100	12in	100	8/16	£28.00
P.A./Disco/Group	DG100/15	15in	100	8/16	£39.00

300W Mid-N-Top system complete £125.00 carr. £12

DISCO CONSOLE Twin Decks, mixer pre amp £145, Carr £10.
 Ditto Powered 120 watt £199; or Complete Disco £300.
 120 watt £300; 150 watt £360; 300 watt £410. Carr £30.

DELUXE STEREO DISCO MIXER/EQUALISER plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. £129 PP £2
 Headphone Monitor, Mike Talkover Switch
 As above but 3 Deck inputs, 4 Line/Aux inputs, 2 Mic. inputs, 2 Headphone Monitors, Stereo Graphic + LED Display £145.

P.A. CABINETS (empty) Single 12 £24; Double 12 £40, carr £10.
 WITH SPEAKERS 75W £56; 90W £75; 150W £84; 200W £92.
 HORNBOXES 200 Watt £32, 300 Watt £38. Post £4.

OUTDOOR HORNS 8 ohms. 25 watt £22. 30 watt £25. 40 watt £33.
 20W plus 100 watt line £38. Post £2.
 MOTOROLA PIEZO ELECTRONIC HORN TWEETER 3 1/2in. square £6
 100 watts. No crossover required. 4-8-16 ohm, 7 3/8 x 3 1/8in. £10

CROSSOVERS, TWO-WAY 3000 c/s 40 watt £4.50, 60 watt £5, 100 watt £5.
 3 way 950 cps/3000 cps. 60 watt £6.50, 80 watt £7, 100 watt £10.
 LOUDSPEAKER BARGAINS Please enquire, many others in stock.
 4 ohm, 5in, 7x4in. £2.50, 6/2in, 8x3in. £3, 8in. £3.50, 6/2in, 25W £7.50,
 8 ohm, 2 1/2in, 3in. £2; 5x3in, 6x4in, 7x4in, 5in. £2.50; 6/2in, 8 x 3in. £3;
 £4.50; 10in, £5; 12in, £6; 8in, £5W £6.50, 8in, 12in, 15in, 17in, £25.
 15 ohm, 2 1/2in, 3/2in, 5x3in, 6x4in. £2.50, 6/2in, 10W £5, 8in, £4, 10in, £7.
 25 ohm, 3in, £2; 5x3in, 6x4in, 7x4in. £2.50, 120 ohm, 3/4in dia. £1.

Make	Model	Size	Watts	Ohms	Price	Post
AUDAX	WOOFER	5/2in	25	8	£10.50	£1
GOODMANS	HIFAX	7 1/2 x 4 1/4in	100	8	£34	£2
GOODMANS	HB WOOFER	8in.	60	8	£13.50	£1
WHARFEDALE	WOOFER	8in.	30	8	£9.50	£2
CELESTION	DISCO/Group	10in.	50	8/16	£21	£2
SEAS	WOOFER	10in.	50	8	£19.50	£2
WEM	WOOFER	10in.	300	8	£36.00	£2
GOODMANS	HPS/Group	12in.	120	8/15	£34.00	£2
GOODMANS	HPO/Disco	12in.	120	8/15	£34.00	£2
H+H	DISCO/Group	15in.	100	4/8/16	£49	£4
GOODMANS	HP/BASS	15in.	250	8	£74	£4
GOODMANS	HPO/BASS	18in.	230	8	£97	£4
PEZZERIS	TWEETER	3/4in.	60	8	£7.50	£1
AUDAX	TWEETER	2 1/2in.	30	8	£4	£1

METAL GRILLES 8in. £3.00, 10in. £3.50, 12in. £4.50, 15in. £5.50, 18in. £7.50. Loudspeaker Covering Vynair etc. Samples. S.A.E.

DISCO SOUND / LIGHT CONTROLLER
 Ready Built Deluxe 4 Channel 4,000 watt sound chaser + speed + programme controls £69. Mk.2 16 programmes, £89, PP £2
 DISCO "PARTY LIFE", Sound Flashing, Light Show, 4 lamps, self contained unit 240V AC. No other connections needed £34.95, PP £2.

MAINS TRANSFORMERS

250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A.	Price Post
350-0-350V 250mA, 6.3V 6A CT £12.00, Shrouded	£7.00 £2
220V 25mA, 6V 1 Amp £3.00, 220V 45mA, 6V 2 Amp	£4.00 £1
250V 60mA, 6.3V 2A.	£5.00 £1

Low voltage tapped outputs available
 1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6.00 £2
 ditto 2 amp £10.50 3 amp £12.50 5 amp £16.00 £2
 31-25-0-25-33 volt 6 amp

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid.
 9V, 3A; 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1 1/2A; 30V, 5A + 17-0-17V, 2A; 35V, 2A; 20-40-60V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 50V, 2A.

£8.50 post 50p MINI-MULTI TESTER
 Pocket size instrument. DC volts 15, 150, 500, 1000. AC volts 15, 150, 500, 1000. DC 0.1ma, 0-150ma. Resistance 0 to 100K. De-Luxe Range Doubler Meter, 50,000 o.p.v. 7 x 5 x 2in. Resistance 20 meg in 5 ranges. Current 50µA to 10A. 0-25V to 100V DC. 10V ranges. £25.00 post £1 to 1000V AC.

PANEL METERS 50µA, 100µA, 500µA, 1mA, 5mA, 100mA, 500mA, 1 amp, 2 amp, 5 amp, 25 volt, VU 2 1/4 x 2 x 1 1/4in. £5.50 post 50p

PROJECT CASES. Black Vinyl Covered Steel Top, All Base
 4 x 2 1/2 x 2 1/4in. £2.50; 6 x 4 x 1 1/2in. £3.50; 8 x 5 x 2in. £4.00;
 11 x 6 x 3in. £5.50; 11 3/4 x 6 x 5in. £9.00; 15 x 8 x 4in. £12.00.

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75;
 6 x 4in. 5sp; 12 x 8in. £1.30; 10 x 7in. 9sp; 8 x 6in. 9sp; 14 x 3in.
 72p; 12 x 5in. 9sp; 16 x 10in. £2.10; 16 x 6in. £1.30.
 ALUMINIUM BOXES. 4 x 4 x 2 1/4in. £1.60; 7 x 5 x 2 1/2in. £2.90;
 3 x 2 x 1in. £1; 4 x 2 1/2 x 2in. £1.20; 4 x 4 x 1 1/2in. £1.50;
 6 x 4 x 2in. £1.90; 6 x 4 x 3in. £2.20; 8 x 6 x 3 in. £3.00;
 10 x 7 x 3in. £3.60; 12 x 6 x 3in. £3.60; 12 x 8 x 3in. £4.30;
 10 x 4 1/2 x 3in. £2.90; 4 x 5 1/4 x 2 1/2in. £1.50; 4 x 2 3/4 x 1 1/2in. £1.20.

HIGH VOLTAGE ELECTROLYTICS

16/450V	50p	220/400V	£2	20+20/350V	75p
20/500V	75p	8+8/500V	£1	32+32/350V	50p
32/350V	45p	8+16/450V	75p	32+32+32/450V	£1.50
32/500V	95p	16+16/350V	75p	16+32+32/500V	£2

SINGLE PLAY RECORD Oecks. Post £2.

Make	Drive	Model	Cartridge	Price
BSR	Belt	12 Volt	Ceramic	£22
BSR	Rim	P207	Ceramic	£22
AUTOCHANGER	BSR	Ceramic	£22	£22
AUTOCHANGER	GARRARD	Ceramic	£24	£24

DECCA TEAK VENEERED PLINTH space for small amplifier
 Board cut for BSR or Garrard 18 3/4in. x 14 1/4in. x 4in. £5. Post £1

★ ★ ★ "STOP PRESS" ★ ★ ★
 H & H 1000 Watt stereo/mono. Professional Power
 Amplifiers S500D Reconditioned, guaranteed. £275, carriage £5.

RADIO COMPONENT SPECIALISTS
 Dept 3, 337, WHITEHORSE ROAD, CROYDON
 SURREY, U.K. Tel: 01-694 1665
 ACCESS Post 55p Minimum Callers Welcome. VISA Same day despatch. Closed Wed. Lists 34p.

Marshall's

A. MARSHALL (LONDON) LTD

A. Marshall (London) Ltd.
Electronic Component Distributors
85 WEST REGENT STREET
GLASGOW G2 2QD
TELEPHONE: 041 332 4133


SPECIAL OFFER TO READERS OF PRACTICAL ELECTRONICS
SEND US ONLY 1/2 THE MARKED PRICE; ALL ITEMS EX STOCK

TRANSISTORS	2N3711	0.15	AF106	0.15	BC239C	0.15	BF183	0.30	ZTX530	0.27	SN7450	0.20	DIODES	CV7227	0.55	Z/DIODES	36V	0.10	
2N398	0.35	2N3771	1.70	AF280	0.50	BC250	0.15	BF195	0.27	ZTX531	0.27	SN7451	0.20	AA116	0.12	400mW	39V	0.10	
2N697	0.23	2N3772	1.90	BC115	0.19	BC251	0.15	BF199	0.18			SN7453	0.20	AA118	0.15	2V4	0.10	43V	0.10
2N698	0.80	2N3794	0.15	BC116	0.19	BC251B	0.15	BF225J	0.24	IC's		SN7454	0.20	AA119	0.15	2V7	0.10	47V	0.10
2N706A	0.22	2N3854A	0.20	BC118	0.19	BC253	0.15	BF255	0.20	CA3034	1.20	SN7460	0.20	AA129	0.12	3V	0.10	1 Watt	
2N708	0.25	2N3856A	0.25	BC132	0.23	BC256	0.15	BF271	0.20	CD4000	0.18	SN7470	0.30	AA144	0.12	3V3	0.10	3V3	0.15
2N718	0.27	2N3905	0.15	BC136	0.23	BC256A	0.15	BF451	0.30	CD4012	0.20	SN7472	0.28	AA147	0.10	3V9	0.10	4V7	0.15
2N753	0.25	2N3962	0.25	BC149B	0.15	BC250	0.15	BFX13	0.42	CD4017	0.50	SN7483	0.60	BA102	0.12	4V3	0.10	5V6	0.15
2N914	0.20	2N4059	0.15	BC149C	0.15	BC262A	0.23	BFX86	0.40	CD4025	0.20	SN7484	1.20	BA130	0.12	4V7	0.10	5V6	0.15
2N929	0.20	2N4060	0.15	BC154	0.27	BC262B	0.23	BSY28	0.30	CD4069	0.20	SN7491	0.63	BA142	0.12	4V3	0.10	7V3	0.15
2N1131	0.30	2N4062	0.18	BC158	0.15	BC266	0.15	BSY54	0.25	CD4071	0.20	SN7492	0.30	BA144	0.10	7V5	0.10	8V2	0.15
2N1507	0.15	2N4286	0.15	BC159	0.15	BC266A	0.15	BSY65	0.35	CD4072	0.20	SN7493	0.30	BA154	0.12	10V	0.10	10V	0.15
2N1637	0.18	2N4288	0.15	BC159B	0.15	BC266B	0.15	ME0413	0.15	CD4073	0.20	SN7496	0.34	BA155	0.12	10V	0.10	11V	0.15
2N1638	0.25	2N4898	1.40	BC167	0.15	BC308	0.15	ME4101	0.15	CD4075	0.20	SN74107	0.28	BA157	0.15	10V	0.10	13V	0.15
2N1991	0.35	2N5033	0.40	BC167B	0.15	BC308A	0.15	ME4104	0.15	CD4082	0.32	SN74141	0.58	BA182	0.14	10V	0.10	16V	0.15
2N2193	0.50	2N5129	0.15	BC168B	0.15	BC308B	0.15	MJ430	1.75	LF137414	0.40	SN74155	0.50	BA201	0.10	13V	0.10	18V	0.15
2N2193A	0.55	2N5222	0.15	BC168C	0.15	BC309	0.15	MJ481	1.20	LM349N	0.90	SN74162	0.96	BA202	0.15	16V	0.10	22V	0.15
2N2217	0.25	2N5223	0.15	BC169B	0.15	BC347	0.15	MJ490	1.20	LM716	0.95	SN74180	0.85	BA243	0.10	18V	0.10	30V	0.15
2N2368	0.24	2N5246	0.32	BC170B	0.15	BC350	0.15	MPP103	0.36	LM923	0.44	SN74184	1.34	BA316	0.10	20V	0.10	33V	0.15
2N2714	0.15	2N5247	0.26	BC171B	0.15	BC414	0.15	MPS3638	0.15	LM7824C	1.00	SN74190	0.85	BA317	0.10	22V	0.10	39V	0.15
2N2923	0.51	2N5448	0.15	BC172A	0.15	BC416A	0.15	MP5A	0.24	SA5560	1.98	SN74198	1.40	BA318	0.18	24V	0.10	43V	0.15
2N3133	0.25	2N6109	0.38	BC173	0.15	BC559	0.15	TIS45	0.55	SA5590	2.04	SN74LS27	0.75	BAV19	0.10	27V	0.10	51V	0.15
2N3392	0.15	40312	0.84	BC173B	0.15	BC559B	0.15	TIS46	0.67	SL701C	2.00	SN74LS151	0.35	BAV20	0.12	30V	0.10	62V	0.15
2N3393	0.15	40316	0.75	BC174B	0.15	BCY58	0.18	TIS49	0.65	SN7410	0.20	SN74LS365	0.35	BAW49	0.11	33V	0.10	82V	0.15
2N3402	0.15	40363	1.20	BC178B	0.20	BCY72	0.20	TIS52	0.72	SN7412	0.18	SN74LS368	0.42	BAV36	0.16				
2N3415	0.15	40389	0.73	BC183A	0.15	BCY78	0.15	TIS58	0.77	SN7420	0.20	SN76115	1.65	BAV44	0.12				
2N3566	0.15	40512	0.50	BC183C	0.15	BD116	0.75	TIS64	0.50	SN7423	0.25	SN76116	1.75	BAV93	0.10				
2N3638	0.15	AC132	0.21	BC213B	0.15	BD138	0.35	TIS93	0.32	SN7440	0.20	SN76226	0.75	BY134	0.30				
2N3642	0.15	AC152	0.53	BC213L	0.15	BD540A	0.40	ZTX107	0.15	SN7441	0.65	SN76666	0.70	BY188	0.20				
2N3662	0.15	AC188	0.30	BC214	0.15	BDY17	1.80	ZTX109	0.17	SN7446	0.45	SO42P	1.18	CV5020	0.30				
2N3706	0.15	ACY22	0.65	BC214B	0.15	BF160	0.24	ZTX303	0.24	SN7447	0.45	TCA160C	2.25	CV7047	0.11				
2N3708	0.15	ACY30	0.86	BC238B	0.15	BF177	0.25	ZTX330	0.24	SN7448	0.45	TMS4116	1.00	CV7071	0.11				

TRADE ENQUIRIES WELCOME

ADD 60p FOR POST & PACKING + 15% VAT

WHERE TO FIND US

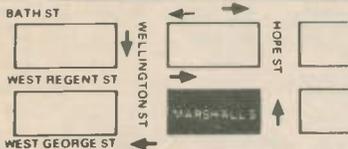

CALL IN AND SEE US

9-5.30 MON TO FRI
9-5.00 SAT
EXPRESS MAIL ORDERS
ACCESS/BARCLAYCARDS
WELCOME
SAME DAY SERVICE



MAIL ORDER

WE REGRET WE CANNOT ANSWER MAIL ORDER/ STOCK ENQUIRIES WITHOUT AN S.A.E. SAME DAY SERVICE TRADE AND EXPORT ENQUIRIES WELCOME

TELEPHONE

MAIL ORDER
041-332-4133
SHOP AND STOCK ENQUIRIES
041-332-4133
TRADE
041-332-4135

TRAIN FOR A BETTER JOB IN ELECTRONICS

Everyday more people are needed to design, install, operate and service electronic systems.

It's big business and the career opportunities are both limitless and richly rewarding.

Prepare yourself for a future in Electronics with an ICS Home-Study Course quickly, easily and in your own time.

Proven teaching methods

ICS is the world's largest correspondence school with over 90 years experience.

So far nearly 9 million people have taken advantage of our tried and tested teaching methods.

Find out how we can help you. Send today for your FREE information pack. No obligation.



Please send me full details of the Electronics Course.

NAME: _____

ADDRESS _____

P. Code _____

International Correspondence Schools,
Dept. EDS95, 312/314 High Street, Sutton,
Surrey SM1 1PR. OR PHONE

01-643 9568/9 or
041-221 2926 (24 hrs.)

INDEX TO ADVERTISERS

Adcola Products	I.F.C.
ADE	55
B.N.R.E.S.	I.B.C.
Bull J.	53
Centurion Alarms	55
Clef Products	24
Cricklewood Electronics	24
Crofton Electronics	26
Croydon Discount Electronics	24
C.R. Supply Co.	54
C-Tec Security	28
Cybernetic Application	15
Decimo	54
Den Fer Electronics	5
Electrovalue	I.B.C.
ESR	5
G.C.H.Q.	15 & 37
Grandata Ltd.	15
Greenwood Electronics	I.B.C.
ICS Intertex	56
London Electronic College	55
Lyon Electronics	55
Macmillan Education	37
Maplin Supplies	O.B.C.
Marco Trading	5
Marshalls	56
Phononics Ltd.	5 & 26
Program Logic Services	54
R.C.S.	55
Reekie Robots	26
Riscomp Ltd.	28
Scientific Wire Co.	55
Tandy	6
T.K. Electronics	24
Watford	2 & 3

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, PRACTICAL ELECTRONICS will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of PRACTICAL ELECTRONICS summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.


We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc. received as a result of answering such advertisements. Classified advertisements are excluded.

New from **ORYX-PORTASOL** Portable Gas Soldering Iron

ORYX – market leaders in soldering irons and accessories introduce the revolutionary PORTASOL. This new approach to catalytic soldering iron technology is truly

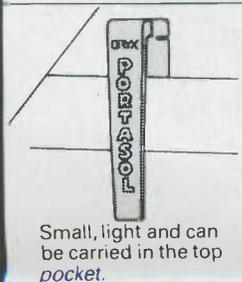
pocket portable (173 mm) and independent of any external energy source. PORTASOL is powered by ordinary cigarette fuel and one filling lasts for 60 minutes continuous use.




Small, light and can be carried in the top pocket.



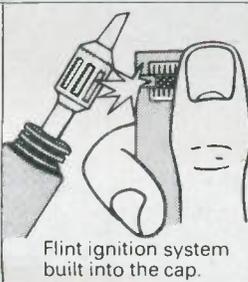
Powered by ordinary cigarette lighter fuel.



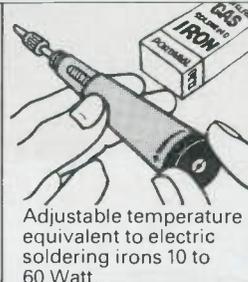Flint ignition system built into the cap.



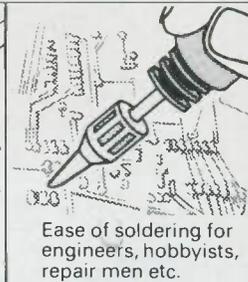Adjustable temperature equivalent to electric soldering irons 10 to 60 Watt.



Ease of soldering for engineers, hobbyists, repair men etc.

- ★ Portasol makes an ideal and handy present.
- ★ Immediately available for use anytime anywhere.
- ★ Portasol meets all safety standards.
- ★ No problem with statics.
- ★ Adjustable temperature for sensitive components.

ONLY
£17.25
INCLUDING VAT, P&P

Greenwood Electronics, Portman Rd, Reading Berks RG3 1NE

ORDER WITH THIS COUPON TODAY

To: Greenwood Electronics, Portman Rd, Reading Berks RG3 1NE.
Please send(qty.) PORTASOL at £17.25. I enclose cheque/P.O./cash for £..... or debit my Barclaycard no Access no. Expiry date

NAME

ADDRESS

Please send technical leaflet. Tick Allow 14 days for delivery.

PE1

You can depend on

ELECTROVALUE

to supply the fine range of test & measurement gear by

thandar

Made in U.K.

FREE 44 PAGE PRICED AND ILLUSTRATED CATALOGUE ON REQUEST

● Over 6000 items stocked

- counters
- multimeters
- scopes
- signal generators etc.

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475
North Branch, 680 Burnage Lane, Manchester M19 1NA
Telephone 061 432 4945
Please mention this publication when replying

BRITAINS FOREMOST QUALITY COMPONENT SUPPLIERS

Master Electronics - Microprocessors - Now! The Practical Way!

- Electronics – Microprocessors – Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio – T.V. – hi-fi and all types of electronic/computer/industrial equipment.



New Job? New Career? New Hobby?
SEND THIS COUPON NOW.

FREE! COLOUR BROCHURE OR TELEPHONE US 062 67 6114
Please send your brochure without any obligation to OR TELEX 22758 (24 HR SERVICE)



NAME I am interested in
ADDRESS ELECTRONICS
 MICROPROCESSORS
 RADIO AMATEUR LICENCE
 CITY & GUILDS EXAMS
Other Subjects

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ14 0HS

More This Month at Maplin

- Colour-coded IDC cables
- 16-way (XR80B) ONLY 32p per metre.
 - 20-way (XR81C) ONLY 40p per metre.
 - 26-way (XR82D) ONLY 54p per metre.
 - 34-way (XR83E) ONLY 70p per metre.
 - 40-way (XR84F) ONLY 82p per metre.
 - 50-way (XR85G) ONLY 99p per metre.
- 4-way flat flexible telephone lead (XR86T) ONLY 18p per metre.
- Stepper motor 48 steps/rev, 12V 0.13A per phase, 4-phase unipolar, 57g, working torque 8mNm max. ONLY £9.95 (FT73Q).
- Driver chip for motor: SAA1027 ONLY £3.75 (QY76H).
- ★SAVE★ 1 Kit containing everything you need: motor, SAA1027, data sheet and passives ONLY £13.35 (LK76H).

Sounds Terrific



Professional Quality
High Power Loudspeakers
featuring:

- ★ Virtually indestructible high-temperature voice-coil reinforced with glass-fibre.
 - ★ 100% heat overload tolerance.
 - ★ Advanced technology magnet system.
 - ★ Rigid cast alloy chassis.
 - ★ Linen or Plastiflex elastomer surrounds.
 - ★ 5-year guarantee (in addition to statutory rights).
- Prices from £18.95.

Send S.A.E. for our free leaflet XH62S.


Top Ten Kits



THIS/MONTH	DESCRIPTION	CODE	PRICE	BOOK
1. (1)	Live-Wire Detector	LK63T	£2.95	14 XA14Q
2. (2)	75W Mosfet Amp.	LW51F	£15.95	Best E&MM
3. (3)	Cor Burglar Alarm	LW78K	£7.49	4 XA04E
4. (4)	Porylite	LW93B	£10.95	Best E&MM
5. (5)	U/sonic Intruder Dctr	LW83E	£10.95	4 XA04E
6. (6)	8W Amplifier	LW36P	£4.95	Catalogue
7. (10)	Logic Probe	LK13P	£10.95	8 XA08J
8. (8)	Syntom Drum Synth.	LW86T	£12.95	Best E&MM
9. (9)	Computodrum	LK52G	£9.95	12 XA12N
10. (7)	Light Pen	LK51F	£10.95	12 XA12N

Over 100 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.

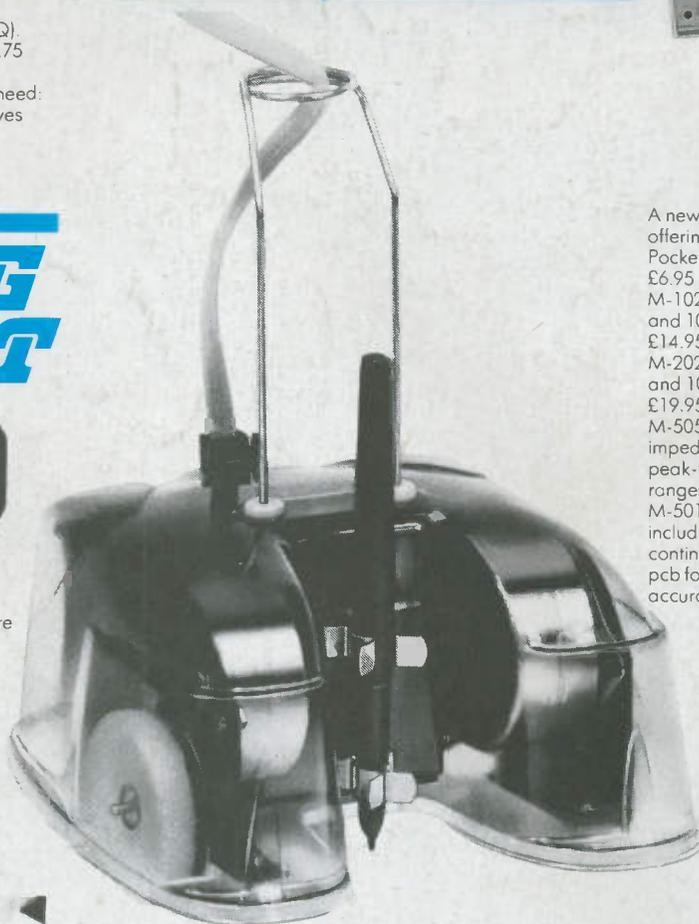Is it a turtle? Is it a robot? Is it a buggy? Yes! it's Zero 2.



- May be used by any computer with RS232 facility.
- Stepper Motor controlled.
- Half millimetre/half degree resolution.
- Uses ordinary felt-tip pens.
- Built-in 2-tone horn, line-follower, LED indicators.

The Zero 2 Robot is the first truly micro robotic system available and remarkably it costs less than £80. Complete kit (only mechanical construction required) £79.95 (LK66W). Full details of power supply and simple interfacing for BBC, Commodore 64 and Spectrum, in Maplin Magazine 15 price 75p (XA15R).

MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD

Mail-order: P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 552911

SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356-7292.
- LONDON 159-161 King Street, Hammersmith, W6. Telephone: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevois Valley Road. Tel: 0703-225831
- SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Telephone: 0702-554000. *Shops closed all day Monday.*

More Choice In Multimeters



A new range of very high quality multimeters offering truly amazing quality at the price.

Pocket Multimeter, 16 ranges, 2,000Ω/V DC/AC £6.95 (YJ06G)

M-102BZ with continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95 (YJ07H)

M-2020S with transistor, diode and LED tester and 10A DC range, 27 ranges, 20,000Ω/V DC £19.95 (YJ08J)

M-5050E Electronic Multimeter with very high impedance FET input, 53 ranges, including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95 (YJ09K)

M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated pcb for long-term reliability and consistent high accuracy (0.25% + 1 digit DCV) £42.50 (YJ10L)



The Maplin Service

All in-stock goods despatched same day for all orders received before 2.00 pm.

All our prices include VAT and carriage (first class up to 750g).

A 50p handling charge must be added if your total order is less than £5.00 on mail-order (except catalogue).



☎ Phone before 2.00 p.m. for same day despatch.

1985 CATALOGUE

Pick up a copy now at a branch of W.H. Smith* or in one of our shops. Price £1.35, or by post £1.75 from our Rayleigh address (quote CA02C).

*Some branches are now out of stock.

All offers subject to availability. Prices firm until 9th November 1985.

