

Australia \$1.75 New Zealand \$1.95 Malaysia \$4.95

PRACTICAL

OCTOBER 1985 · £1.00

# ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING

*New Series...*

## **Introduction to Microprocessor Systems**

---

## **BBC Bytebox Modulated Syndrum**

---


**SPACEWATCH with Dr. Patrick Moore · ROBOTICS REVIEW**





# Industrial Soldering Equipment-for the discerning amateur

SEND FOR NEW CONCISE LEAFLETS

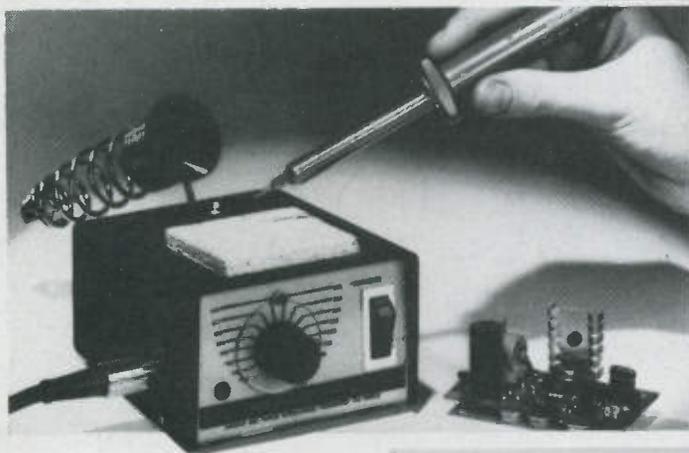


## 101 ELECTRONIC CONTROLLED SOLDERING STATION

for precision soldering  
with accuracy suitable  
for use on MOS, FET etc  
240V input - 24V on tool.  
Temperature range  
120-420°C  
*Many extra features*

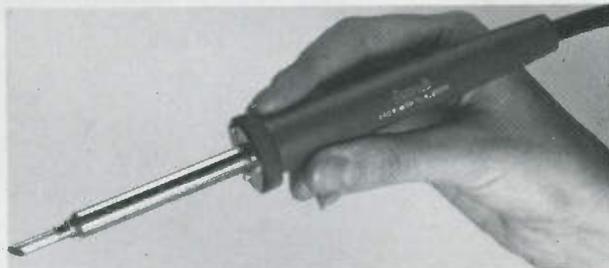
## 'K' SERIES SOLDERING TOOLS FOR ALL APPLICATIONS

K1000 micro soldering  
K2000 general electronic  
soldering  
K3000 heavy duty soldering


● Small selection of  
**AD-IRON® LONG LIFE  
SOLDERING TIPS**  
suitable for all Adcola  
soldering irons.


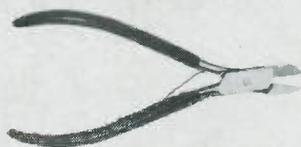
## ADCOLA ACCESSORIES include: SIDE CUTTERS



## SNIPE NOSE PLIERS

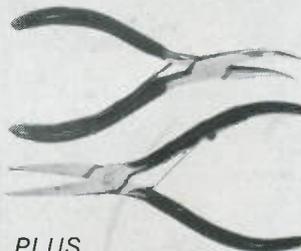

## PLUS

- Desoldering Braid
- Desoldering Guns
- Tip cleaners
- Soldering aids
- Lamps, Lenses etc

**SEE US AT  
INTERNDPCON  
STAND 1701  
BLUE HORN**

# ADCOLA

Regd Trade Mark

**ELECTRONIC PRODUCTION EQUIPMENT**

*For a no obligation demonstration, please contact:*

**ADCOLA PRODUCTS LIMITED** Gauden Road London SW4 6LH  
Telephone Sales (01) 622 0291 Telex 21851 Adcola G

Upgrade your 16K Spectrum to full  
with our RAM Upgrade Kit. Very  
easy to fit. Fitting instructions  
included. **ONLY £18**



## CONSTRUCTIONAL PROJECTS

<b>BYTEBOX</b> by Ray Stuart Part One: System concept and design—facilitates 16 "sideway" ROMs for the Beeb	10
<b>TOUCH CONTROL PSU</b> by R. A. Penfold Novel power supply with a very practical application	28
<b>MODULATED SYNDRUM</b> by R. A. Penfold Be a big hit with this music project	32
<b>EXPERIMENTING WITH ROBOTS</b> by Mike Abbott Part Two: Constructing the five channel interface	46

## GENERAL FEATURES


<b>INTRODUCTION TO MICROPROCESSOR SYSTEMS</b> Part One: Basic terms and concepts	20
<b>ROBOTICS REVIEW</b> by Nigel Clark A regular look at robotics and cybernetics	26
<b>SPACEWATCH</b> by Dr Patrick Moore	38
<b>INGENUITY UNLIMITED</b> Readers' circuit ideas	40
<b>IVAX REVIEW</b> by Phil Dane Details of an advanced SCARA design which has four axes of movement	42
<b>BBC MICRO FORUM</b> by D. Whitfield MA MSc CEng MIEE Secrets of the analogue port	50

## NEWS & COMMENT

<b>EDITORIAL</b>	7	<b>INDUSTRY NOTEBOOK</b>	16	<b>NEXT MONTH</b>	27
<b>NEWS &amp; MARKET</b>	8	<b>READOUT</b>	18	<b>BOOK REVIEWS</b>	36
<b>PLACE</b>	8	<b>BAZAAR</b>	19	<b>P.C.B. SERVICE</b>	52



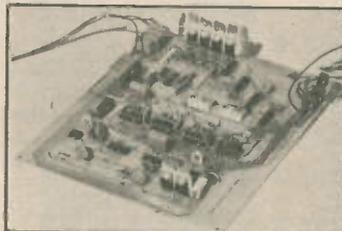This month's front cover picture shows the National Semiconductor 32 bit microprocessor smashing a "memory barrier" formed by a floppy disc. Courtesy of National Semiconductor.



**OUR NOVEMBER ISSUE WILL BE ON SALE FRIDAY, OCTOBER 4th, 1985 (see page 27)**

© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.





## 64K DDL & MCS

DIGITAL DELAY LINE & MICROCOMPUTER  
CONTROLLED SAMPLER FOR SUPERB MUSICAL EFFECTS



Published in Practical Electronics

Full 64K memory. Up to 67KHz sampling rate. Audio bandwidth over 15KHz. Features special wow-less circuit controlling musical delay range from 4mS to 8 seconds. Maximum special effects delay 65 seconds. Companding ADC & DAC converters with equivalent of 15 bit sampling. Infinite loop sample storage. Controlling sweep modulator. Internal and external digital and voltage control. Effects generation for chorus, double tracking, reverse tracking, echo, flanging, phasing, reverb, vibrato, looped repeat and pitch variation, microprocessor control. BBC, Apple, Commodore and similar micros, or stand-alone. Mains powered. SET 234-BK £275.00

## MINI MCS

MICRO CONTROLLED SAMPLER FOR ECHO,  
REVERB AND OTHER DDL MUSIC EFFECTS



Abridged version of the above sampler excluding on-board memory and timing. For direct control from a micro such as BBC, Apple, Commodore and similar. Includes companding ADC & DAC, computer interface, mix, feedback, filter, gain, level, PSU. SET 246-BK £95.00

DDL & MCS published texts can be bought separately at £1.50 plus large SAE. Other texts available separately at 50p plus large SAE. Boxes are steel & aluminium with black finish. All kits include PCBs, parts, instructions, boxes, wire, solder.

For catalogue of over 70 kits. Send 9x4 S.A.E. (for overseas catalogue send £1 or 5 IRC's). Mail order. Payment to Phononics, CW0, CH0, PO, Access, Visa. Insurance cover 50p per £50 (obligatory on credit card orders. Details correct at press. E&OE. Despatch usually 10-14 days.

BECKER-PHONONICS, DEPT PE50, 8 FINUCANE DRIVE, ORPINGTON, KENT, BR5 4ED.  
TEL: ORPINGTON 37821 (STD 0689, LONDON 66).

## MORE P.E. AUDIO EFFECTS



- MONO-STEREO ECHO-REVERB (P.E. Sept. '84) 200ms echo (extendable), lengthy reverb, multitacking. Kit as published. Set 218BK £57.66
- ENHANCED PHASER (P.E. Oct '84) Enhanced phasing with modulated filter shifting. Kit as published. Set 226BK £42.36
- RING MODULATOR (P.E. NOV. '84) Fabulous effects generation. With multiwaveform VCO, noise gate & ALC. Kit as published. Set 231BK £45.58
- MONO-STEREO CHORUS-FLANGER (P.E. Jan. '84) Superb dual mode music enhancement. Kit as published. Set 235BK £59.99
- CYBERVOX (E.E. Apr. '85) Amazing robot type voice unit, with ring modulator and reverb. Kits as published. Set 228BK £44.76
- STEREO NOISE GATE & VCA (P.E. May '85) Automatic noise reduction circuit for mono or stereo. Kit as published. Set 227BK £26.61
- SIGNAL GENERATOR & F-V (P.E. Jan. '85) Audio test equipment. Multiwaveform VCO, & freq. to voltage converter, & sweep gen. Kit as pub. Set 233 £46.96

## OTHER SUPER SOUND KITS

- BLOW BOX: Voice operated VCF & VCA for fascinating effects SET 214 BK £29.33
- COMPANDER: Mono of stereo compression-expansion, switchable SET 238 BK £22.99
- ENVELOPE SHAPER: Note triggered ADSR with VCA SET 174 BK £25.20
- FREQUENCY DOUBLER: Guitar octave raiser & tone changer SET 98 BK £15.30
- RUIZ: Smooth distortion, retains attack & decay character SET 209F BK £19.58
- GUITAR SUSTAIN: Extends note decay time, with noise gate SET 222 BK £25.31
- GUITAR TO SYNTH INTERFACE: With voltage & trigger outputs SET 173 BK £41.41
- HAND CLAPPER: Auto & manual variable clap effects SET 197 BK £26.69
- MOCK STEREO: Splits mono signal into stereo simulation SET 213 BK £24.37
- MUSIC MODULO: 8 variable tremolo & wah guitar effects SET 196 BK £23.56
- RHYTHM GENERATOR: Computer driven, BBC, Apple, 64 & similar SET 185 BK £34.64
- STORM EFFECTS: Auto & manual wind, rain & surf effects SET 154 BK £23.60
- TOM-TOM SYNTH: Sound triggered, multivariable drum effects SET 190 BK £19.37
- TREMULO: Mono variable depth & rate modulation SET 136 BK £15.62
- VOCODAVOX: Modular vocoder, 7 chans extendable SET 152 BK £79.95
- VODALEK: Simple robot type voice modulator SET 155 BK £18.31
- WAH-WAH: Auto, manual & note triggered, switchable SET 140 BK £24.36

Add 15% VAT. Add P&P £1.50 each kit. (Overseas Rates in Catalogue).

**SIREN KIT**  
Produces a loud swept frequency tone from a 9-15V supply. Enable input for easy connection to alarm circuits. Includes 5in horn speaker £7.90  
Mini siren (with small speaker & box) £4.30

**PASSIVE IR DETECTOR**  
Detects intruders body heat at up to 10m. 12Vdc supply. Output N/c contacts 950 135 £45.00

**BOXES**  
Plastic, diecast aluminium

**DIGITAL LOCK KIT**  
operates from 5 to 18Vdc supply and gives 5040 combinations 10 way keyboard supplied. 750mA output Ideal for disabling car ignition or for door lock when used with 701.150 lock mechanism £11.50  
701.150 £14.95

**MULTIMETERS**  
Analogue from £6.50  
Digital from £26.55

**HIGH SECURITY IR TRANSMITTER/RECEIVER**  
Operating from 9-15Vdc, both units have 8 switches and will operate only if these have been set to the same code Receiver provides latched or momentary output Ideal for car locks, garage door openers, burglar alarm switches etc XK119 £21.75

**CMOS**  
4001 16p  
4017 39p

**BELL BOX**  
Brightly coloured and a deterrent by itself 950 130 £10.00

**XENON BEACON**  
12V 170mA Orange weatherproof 950 133 £10.50

**PRESSURE MATS**  
23 x 7ins £1.70  
29 x 16ins £2.60

**TRIACS**

**FREE 28 page catalogue. Send 9x6 SAE NOW!**  
Telephone orders - Access & Barclaycard RING 01-567 8910 (24hrs)

**BT Phone connectors starter pack** £9.50

**ALARM CONTROL UNIT**  
4 input circuits, 2 instant 2 delayed. Adjustable entry exist and alarm times. Built & tested. Full instructions supplied. Size 180 x 130 x 30mm 12 dc supply 950 160 £26.00

**TOOLS**  
Side cutters £2.10  
See Cat. for full range.

**WINDOW TAPE**  
50m £2.50  
Terminators 36p/pr

**LEDs**  
from 9p

**VERO**

**PANTEC KITS**

**BATTERIES**  
NiCADs eg AA 90p & Chargers

**VELLEMAN KITS**

**CONTACTS**  
for doors & windows Magnet & Reed Flush 950 140 £1.05  
Surface 950 142 75p

## ELECTRONICS

13 BOSTON RD  
LONDON W7 3SJ

Tel. Orders: 01-567 8910  
Enquiries: 01-579 9794

Shop Hours: Mon-Fri. 9am-5pm  
Sat. 10am-4pm.

## ORDERING INFORMATION: ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.

LOCAL AUTHORITY AND EXPORT ORDERS  
WELCOME  
GOODS BY RETURN SUBJECT TO AVAILABILITY



## UNIVERSAL NI-CAD CHARGER

with battery test facility and LED indicators. For PP3, AA, C & D cells. **£5.99**

**NI-CAD RECHARGEABLE CELLS AA/HP7** 500 mA Hr. Pack of 4 £1.50 or 4 pks for only £5. (Ex-equip, tested & guaranteed)

**PANEL VOLTMETER** 3 x 3ins Dual range. 50V + 10V, 1mA Isd D.C. mfrd. by ERNEST TURNER - Tropicalised. Gives the professional look to any equipment £4.50 ea. 2 for £8 or 5 for £15

**ELECTRET CONDENSER MICROPHONE** mod. EM109 a small mic. for cassette recorders etc. High output. Excellent quality. Fitted with a 3.5mm jack plug, incl. Bat. £4.50 ea or 2 for £8

**ELECTRET MIC. INSERTS** 9mm dia x 6mm with integral amp. Requires normal 1.5V £1.10 ea or 6 for £5

**PRECISION THERMISTORS** low current, v. fast response, nominal resistance at 20 degs C. 5MΩ, 1MΩ, 300K, 100K & 1K any mix for £2 or 10 £3.50

### BLEEPERS & BUZZERS

**MINI-BLEETONE** 2-tone, 5-30V DC, 5-15mA £2.50 ea 3 for £6 or 10 for £18 (advertised elsewhere for £5.05 ea)

**MINI-PANEL MNTG.** with 100mm wire leads (22 x 15 x 15mm) 400Hz, 70dB at 30cm. 20mA Type MB6 6V. Type MB9 9V. Type MB12 12V £1.60 ea 3 for £4

**MINI-PCB MNTG.** 3 types as above but PCB mounting - same price.

**HIGH POWER PANEL MNTG.** 100mm leads (25mm dia x 17mm) 50mA 400Hz 8dB at 30cm. Type LB6 6V. Type LB9 9V. Type LB12 12V £1.70 ea or 3 for £4.50

GOODS SENT BY RETURN POST - PLEASE ADD 80p P&P TO TOTAL ORDER  
Shop open daily 10 am-5.30 pm (closed Wednesdays)

CROYDON DISCOUNT ELECTRONICS

40 Lower Addiscombe Road, Croydon CR0 6AA. Tel. 01-688 2950

### D.C. RELAYS

**B1A** 14-PIN DIL. 1-pole n/o 1A contact. Coil 5V-12V, 1200R. 75p ea. 5 for £3 or 10 for £5 PCB mntg. Read 5V Coil

**E1M0** 1-pole n/o 2A. 175R 90p ea or 5 for £2.50; **E1M1** 1-pole n/c 2A. 140R 90p ea or 5 for £2.50; **E2M** 2-pole 1 n/o. 1 n/c. 2A 100R. £1.10 ea or 5 £4.25

**G2L** 1-pole c/o 10A contact. Coil 4V-8V 70R 26 x 10mm footprint, 25mm tall £1.90 ea or 3 £4.70 **G2V** 2-pole c/o 1A contacts. Coil 4V-8V 60R PCB Mntg. £2 ea

**KH11** 4-pole c/o 3A contacts. Coil 12V, 150R. Solder tags £2 ea or 3 for £5.50 **K52** 2-pole c/o 6A. Coil 9V-18V, 180R. PCB mntg. £2 ea or 3 for £5.50

**K13** as above but 12-20V, 430R - same price **K3W** 3-pole c/o 6A contacts. Coil 6V, 38R, PCB mntg. £2.50 ea

**K6W** 2-pole c/o 6A contacts. Coil 6V, 30R. Solder tags £2 ea

**SPECIALS** - ex-equip. good. 2-pole c/o contacts. 1-2A Continental plug-in. 12V coil, 700R. 70p ea. 5 for £3 or 10 for £5

### D.C. MOTORS

**HIGH TORQUE** 40W Reversible, 1000rpm 3V-18V. 2A max working. dia 28 x 50mm + shaft (15 x 2.3mm dia). Torque at 2A = 0.54 lbs.inch approx. £2.90

**CHUCK** with 3 collets fits above motor to use as drill. Takes up to 2.5mm drills £2

**HSS DRILL BITS WITH SHANKS.** 1mm - 5 bits £1.50. 0.8mm or 0.6mm - 5 bits £2.50 (not rec. for glass fibre PCB)

**TINY** virtually inertia-less motor i.e. no iron in rotor. 1.5-3V 15mm dia x 30mm + shaft 6 x 1.6mm. With governor - can be bypassed £1.50

**NOMINAL 12V** motor works down to 1V ex-unused equip. VCR transport mech. 33mm dia. 30mm o/a + shaft 12 x 2mm a bargain at 75p ea or 3 for £1.75

**MINI TDY** motors 1-3V 19 x 18 x 9mm 50p ea or 5 for £2

# Crofton

## THE VIDEO SPECIALISTS

If you need a monochrome or colour monitor, digitiser, T.V. camera, or door entry system Crofton must be your first choice - here are a few reasons why!




### THE CROFTON PM101

This 9 inch metal cased, monochrome monitor is incredible value at **ONLY £82.80**
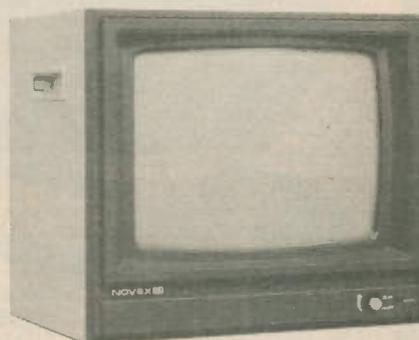
### THE NOVEX 1414

This superb metal cased 14 inch RGB/COMPOSITE COMPUTER COLOUR MONITOR is unbelievable value at **ONLY £185.15**



### CCTV CAMERAS



Though not new these cameras have been completely refurbished to a high standard in our own workshops and come complete with a standard lens, ready to work

**ONLY £78.20**

Short mains lead version requiring case respray available from £66.70  
Weatherproof housings, motorised pan & tilts etc. available at extra cost.

### THE CROFTON SPECIAL CCTV OFFER

The Crofton special CCTV package and the door entry system described by P.E. in the September 1985 issue are available at the following prices  
**SPECIAL CCTV PACKAGE £193.00**  
**DOOR ENTRY SYSTEM £103.45**  
NOTE: We can also offer a multiscan system enabling the outputs from 4 cameras to be displayed simultaneously or individually on a single screen.

**ELECTRONIC KEY FOB** - Quickly locate mislaid keys. Fob emits a shrill tone in response to your whistle! **ONLY £10.53.**

ALL THE ABOVE INCLUDE VAT, CARRIAGE & INSURANCE AND AT THESE PRICES OUR STOCKS CANNOT LAST LONG.

**DON'T DELAY - PHONE YOUR ORDER TODAY!**  
**MOST MAJOR CREDIT CARDS ACCEPTED**

Delivery within 28 days.


Be sure to request our free catalogue describing our range of T.V. cameras, fixed and zoom lenses, sequential switchers, special and general monitors (colour and b/w including the PHILIPS 7502, PHILIPS 7522 and PHILIPS 2007 plus the full IKEGAMI range), video digitisers, light pens, eprom erasers etc.

**CROFTON ELECTRONICS** ☎ 01-891 1923

35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX TW14 4AD
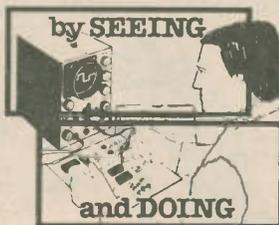
## Master Electronics - Microprocessors - Now! The Practical Way!

- **Electronics - Microprocessors** - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- **Recognise and handle all current electronic components and 'chips'.**
- **Carry out full programme of experimental work on electronic computer circuits including modern digital technology.**
- **Build an oscilloscope and master circuit diagram.**
- **Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.**



### New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

#### FREE! COLOUR BROCHURE

Please send your brochure without any obligation to

OR TELEPHONE US 062 67 6114  
OR TELEX 22758 (24 HR SERVICE)



NAME \_\_\_\_\_ I am interested in

ADDRESS \_\_\_\_\_  ELECTRONICS

\_\_\_\_\_  MICROPROCESSORS

\_\_\_\_\_  RADIO AMATEUR LICENCE

\_\_\_\_\_  CITY & GUILDS EXAMS

Other Subjects \_\_\_\_\_

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ14 0HS

# Tandy® Top Value In Test Equipment

Select the Function and It  
Selects the Range  
Automatically



A  
**£22<sup>95</sup>**



B  
**£69<sup>95</sup>**

- Folds Into Compact Case With Wrist Strap

- Automatic Power Off When Case Is Shut
- Automatic Polarity

**A 25-Range Folding Multimeter.** Features include fuse and surge-absorber protection, banana-type probe jacks and 4" 3-colour mirrored meter with automatic shunt protection (when folded shut). DC Volts: 0 to 1200. AC Volts: 0 to 1200. DC Current: 0-60 $\mu$ A, 3-30-300 mA. Resistance: 0-2-20-200K-2 megohms (centre scale 24). dB; -20 to +63 dB. Requires "AA" battery. 22-211 ..... **£22.95**

**B Folding LCD Multimeter With Autoranging.** Features extra large 1 1/16" non-glare display with adjustable viewing angle, a "beep" indicator for quick continuity testing, and zero-ohms adjust for super-accurate low resistance measurements. DC volts to 1000. AC volts to 500. Up to 10 amps AC and DC. Resistance to 2 megohms. Open: 10 7/8 x 4 5/8 x 1 1/2". Requires two "AA" batteries. 22-193 .. **£69.95**

## Transistor Checker and Digital Logic Probe

A **£9<sup>95</sup>**

B **£14<sup>95</sup>**


**A Dynamic Transistor Checker.** Makes Go/No-Go tests on small-signal and power types and allow you to match similar transistors. Indicates relative current gain, "opens" and "shorts". Requires "AA" battery. 22-025 ..... **£9.95**

**B Digital Logic Probe.** The fast way to "peek inside" TTL, LS and CMOS digital circuits. Colour-coded LEDs indicate high, low or pulsed logic states (up to 10 MHz). Minimum detachable pulse width: 50 ns. 36" leads with clips obtain power from circuit under test. Low current drain. 22-302 ..... **£14.95**



Overload  
and  
Polarity  
Protected

## Reference Books

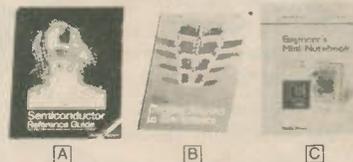

**A Semiconductor Reference Guide.** 1985 edition! Exclusive cross-reference and substitution section lists over 80,000 types. 276-4008 ..... **£4.49**

**B Getting Started In Electronics.** The perfect introduction to the exciting world of electronics. Learn to build your own circuits. 128 pages. 276-5003 ..... **£2.49**

**C Timer IC Mini-Notebook.** An excellent reference and hobby book. Large schematic diagrams. 32 pages. 276-5010 ..... **99p**



## Take A Look At Tandy, Today!

Visit your local store or dealer and see these and many more bargains. We service what we sell - over 2,900 exclusive lines!

See Yellow Pages For Address Of Store Nearest You

OVER 9,000 STORES & DEALERSHIPS WORLDWIDE



Known As Radio Shack In The U.S.A.  
Prices may vary at Dealers.  
Offers subject to availability

## 21 YEARS

**N**EXT month PE has been around for 21 years. I do not intend to go on too much about it now as we will be carrying a special feature (and an extra eight pages) next month. In the feature we will look at the history of PE, some of the "landmark" projects along the way, the personalities, the moves, some advertisers etc. In addition to the special anniversary issue we will increase the size of the magazine—by adding about 20mm on the height. This is the second time in the history of PE that the page size has been increased—if you do not know when it happened before, find out next month!

Twenty one years is a long time in electronics, however, it may surprise some younger readers just what hobbyists were building all those years ago. Although I was in no way connected with PE when it was launched, there are still people on the staff who were; people who have made it a success and who, with your help, ensured the magazine prospered and continued. In fact when PE was launched, I was just starting an apprenticeship with the Ministry of Aviation and never dreamed I would eventually edit the exciting new magazine we apprentices read so avidly.


Interestingly, our history is based on three sets of seven year periods with major changes at the end of each seven years—and strangely it does seem to be happening again now!

## PRICES

Perhaps it is unfortunate that we have to keep up with all aspects of progress; I am thinking of inflation and the way it affects the cost of the magazine. With this in mind I must tell you that from next month PE will cost £1.10. For some time our cover price has been lower than our competitors and we have maintained this situation for as long as possible, but economics now force us to go up 10p. For your information the first issue cost 2/6 (12½p for those who do not remember £.s.d.); that's about 750 per cent inflation in 21 years. However, a single transistor was then around 5/- (25p) which would be equivalent to over £2 now, instead of the 15p or so we actually have to pay.

For those who may consider the 10p price rise is to pay for extra paper the new size issue will require, let me assure you that due to the complexities of Web Offset printing the size increase has not added to our printing or paper costs.

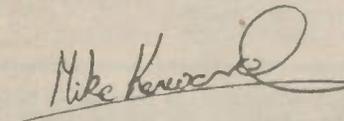We do try our best to contain the cover price and keep up the quality and content of each issue. You may have noticed that our type size is much smaller than some publications which means more words per page and, therefore, more information in each issue.



**Editor** Mike Kenward

**Secretary** Pauline Mitchell

**Editorial Tel:** Poole (0202) 671191

**Advertisement Manager**  
David Tilleard 01-261 6676

**Secretary**  
Christine Pocknell 01-261 6676

**Ad. Make-up/Copy**  
Brian Lamb 01-261 6601

**Classified Ads**  
Mandy Morton 01-261 5846

*Queries and letters concerning advertisements to:*  
Practical Electronics Advertisements,  
King's Reach Tower,  
Stamford Street, London SE1 9LS  
Telex: 915748 MAGDIV-G

## Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to **one published project only. We are unable to answer letters relating to articles more than five years old.**

Components are usually available from advertisers; where we anticipate difficulties a source will be suggested.

## Old Projects

We advise readers to check that all parts are still available before commencing any project in a back-dated issue, as we cannot guarantee the indefinite availability of components used. **We are unable to answer letters relating to articles more than five years old.**

*Technical and editorial queries and letters to:*  
Practical Electronics Editorial,  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG

## BACK NUMBERS and BINDERS . . .



Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. When ordering please state title, month and/or issue required.

Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including postage, packing and VAT.



## SUBSCRIPTIONS

Copies of Practical Electronics are available by post, inland for £13, overseas for £15 per 12 issues, from: Practical Electronics, Subscription Department, IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment for subscriptions can also be made using a credit card.

**Phone:**  
**Editorial Poole (0202) 671191**

**We regret that lengthy technical enquiries cannot be answered over the telephone.**

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

## ROOM FOR EXPANSION

According to British Telecom sources, if the whole of the telephone network could be 'monitored' at any one time during the average day, 25 per cent of numbers being dialled would be unanswered. If BT could persuade more people to employ answering machines then, of course, those calls could be answered. The potential increase in turnover further broadening the smiles of shareholders.

Since the majority of big businesses now have well established intercommunications set-ups, it is the smaller businesses and the man in the street that are presently being courted by BT marketeers. The machines displayed in a recent exhibition were aimed at this market.

Items of particular interest were multi-function desk phones with many switching capabilities that will undoubtedly in the long run make the standard switchboard (and it's operator) redundant. Also in the pipeline are 'desk phones of the future' which might well incorporate a 'mini' data printer, it is expected, by then, that the telephone system will be essentially digital as will the desk sets—making present-day modems obsolete.



The data-transmission field has just been boosted with the launch of BT's communications service enabling the transmission of text, photo's, data and speech. This new service Integrated Digital Access (IDA) will, according to Mr Kane (BT Director of Marketing), "Transform communications in the UK and have a major impact on the business community".

The system at present is only linked from London to several key areas in the south. As the Advanced Integrated Services Digital Network (ISDN) is progressively expanded, the facility will become available to us all. It is planned that by 1987 around 190 centres in the UK will be able to use IDA.

A similar innovation is already in use, using the analogue system (via A/D converters). IMTRAN (Image Transfer) consists of a portable receiver/transmitter unit which plugs into a standard telephone socket. It can be connected directly to a body-scanner, or to a TV camera focused on X-ray pictures or medical records etc. High resolution images are received on a TV monitor screen, enabling doctors to analyse the pictures at far off locations soon after they have been taken.

## Three from Croydon

Where would you find the specifications of over 20,000 British, European and Japanese transistors? In *Towers' International Transistor Selector* (sorry, no acronym!) of course.

This compendium gives a comprehensive tabulation of basic transistor specifications and offers information on characteristics; case details; terminal identifications; applications use; manufacturers and equivalents. The devices covered are a selection of the more common current and widely used obsolete types.

Since its introduction in 1974, the book has been updated three times, the most recent (update 3) is presently retailing for a daunting £12.95.

Those of us, however, who appreciate that its predecessor (update 2, 1980) would be a very handy tool, can buy this equally extensive reference source for just £6.75, inc. VAT and p. & p., from Croydon Discount at the address below.



Also available from the same supplier is the 'Monacor' DMT-700, a handy-sized (67 x 112 x 25mm) 3½ digit l.c.d. digital multimeter—ideal for the hobbyist/service engineer.

Ranges as follows: 0-1kV d.c. (4 ranges); 0-500V a.c. (2 ranges); 0-200mA d.c. (3 ranges); 0-2kΩ (4 ranges); Diode test; Overload protection; Auto-polarity.

This manageable, well priced multimeter is being offered to PE readers at the special price of £29.95 inc. VAT.

For readers interested in robotics (see: *Experimenting with Robots*, page 46) it should be noted that d.c. motors, micro-switches, relays and other 'robotalia' can be sourced at this address. Croydon Discount Electronics, 38 Lower Addiscombe Road, Croydon, Surrey CR0 6AA (01-688 2950).

## SOUND INVESTMENT

A 'sound-meter' kit is now available from Cambridge Kits, with £4 off for PE readers.

This self-contained, hand-held unit, designed to BS 5969 with "A" weighted frequency response to compare both low and high frequency annoyance, measures all types of sound and checks whether legal limits in factories and residential areas etc. are being met. It is ideal for comparing appliances, lawn mowers, paper shredders etc. or measuring the effect of sound proofing or double glazing.

There is a built-in calibrator and the measurement range is from 40dB (public library) to 120dB (overhead jet take-off). It features peak sound level response, even with

pulsating or irregular sounds. There is a linear dB sound scale and knob to set the measurement level, which makes an l.e.d. flash when exceeded, or the operator can watch the l.e.d. and turn the knob to measure the sound level—there is no flickering meter needle to guess at. The meter runs from an internal PP3 type battery or external 9V supply.

The kit is available at an introductory price of £23.20 including VAT and UK postage if ordered from Cambridge Kits, 45 (JF) Old School Lane, Milton, Cambridge, before the end of October 1985. Allow 28 days for delivery. From 1 November 1985 the regular price will be £27.20.

# MARKET PLACE


## CLEAN MAINS

Most home computing enthusiasts will perhaps by now be aware of the frustrating problem of an unstable mains supply creating havoc with a micro.

Mainsborne 'spiky' transients and r.f. interference can crash a program or hopelessly corrupt computer data, necessitating many hours of further work. Several surge-filtering devices are presently available, and the peace of mind that comes with one could be well worth the purchase price.

New from Tony Firshman Services is the competitively priced 'Computer Cleaner'. Housed in a typical double-adaptor casing the basic unit incorporates capacitive filtering (1-30MHz), an inductive element for r.f., up to around 130MHz; and a mains transient suppressor.

The unit is capable of protecting more than one computer, but has only one outlet. A double-adaptor could be plugged into the unit for this purpose. A four-way trailing socket version is also available for those with a need to supply larger amounts of laundered power. The basic 'Computer Cleaner' plug costs £14 and the four-way socket £24, prices inc. VAT and p&p. (Allow 28 days for delivery). From Tony Firshman Services, 43 Rhyl Street, London, NW5 3HB. (01-267 3887).

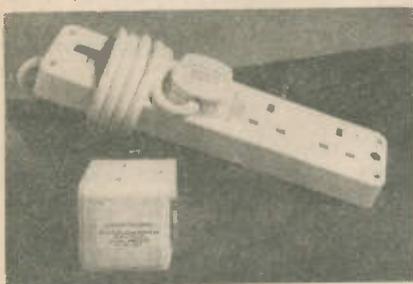

## POINTS ARISING...

MODEMS Part 3  
August '85

The telephone number given for access to the Prestel 'Enterprise' computer (page 24) cannot be used from outside the London area. If in London 618 1111 is correct; unfortunately it cannot be prefixed with '01-' as printed. People outside the London area should ring the Prestel Information Office on 01-822 1122 for the number relevant to their area.

CYLINDER THERMOSTAT  
May '85

The tendency of the cylinder thermostat relay to 'chatter' is the result of mains spikes (generated when the relay contacts open and close) being picked up by the sensitive parts of the circuit.

The easiest cure is to put a time delay in the circuit so that short interference pulses do not get through to operate the relay. In most cases a 100µF/10V electrolytic capacitor connected across R11 will provide a complete cure. This value can be increased to 1000µF or more in severe cases. The negative terminal of the capacitor is connected to the end of R11 nearest to the centre of the board.

It is also possible that interference may enter the circuit via the sensor lead in situations where the environment is particularly prone to electrical noise. To prevent this a 10K resistor should be inserted between the inverting input of IC2 and the sensor terminal block TB2.2 This can be inserted by breaking the pcb track where it passes between TR1 and VR2 and soldering the resistor across the break. It may

also be advantageous to increase the value of C2 to 100nF.

The amount of electrical interference generated when switching inductive components such as pump motors and boiler solenoids is surprising. With hindsight it is clear that the modifications should have been designed in. Perhaps this experience will be of help to those designing similar circuits in the future.

## Briefly...

Availability of a BBC-B interface for the 'Memocon Crawler Robot' has been announced by Red Giant, it will retail at £6.95. In the near future a further BBC-B interface will be launched for the Fischerteknic Robot Kit, this will cost around £25 with a 20 per cent reduction for schools. Details from, Red Giant Software Ltd., 3a Oakcroft Close, Pinner, Middlesex.

• • • • •

The new Greenwell catalogue has just been published. It contains a wide range of components, books, meters, connectors and all the usual requirements of the electronics hobbyist. A special listing within the catalogue (list No. 21), offers exceptional prices on a wide range of 'returned' goods. The catalogue's one pound purchase price can be redeemed with discount vouchers. From, Greenwell Electronic Components, 443 Millbrook Road, Southampton SO1 0HX (0703 772501).

• • • • •

DID YOU KNOW that Prestel charge 6p per minute for computer time between 8 a.m. and 6 p.m., Monday to Friday and between 8 a.m. and 1 p.m., Saturday. However, at all other times the service is FREE.

## Countdown . . .

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Brian Butler.

Personal Computer World Show Sept. 18-22. Olympia 2 M  
Electron & BBC User Sept. 27-29. UMIST, Manchester L  
Amstrad User Exhibition Oct 5/6th. Novotel F2  
Computer Graphics Oct. 16-18. Wembley Conf. Centre. O  
Cellular Communications Int. Nov. 5-7. Wembley Conf. Centre. O  
Electronic Publishing Nov. 5-7. Wembley Conf. Centre. O

Compec Nov. 12-15. Olympia K2  
Electron & BBC User Nov 14-17. New Horticultural Hall, London L  
Computers In The City Nov. 19-21. Barbican Cntr. O  
Scottish Home Computer/Electronics Show Nov. 22-24. Anderston Centre, Glasgow W2  
Leeds Electronics Show Sept. 24-26. University E

A1 Inst. Electronics ☎ 0706 43661  
E Evan Steadman ☎ 0799 26699  
F2 Computer Marketplace (Exhibitions) Ltd. ☎ 01-930 1612  
K2 Reed Exhibitions, Surrey Ho., 1 Throwley Way, Sutton, Surrey.  
L Database ☎ 061-429 8157  
M Montbuild ☎ 01-486 1951  
O Online ☎ 01-868 4466  
T1 Cahners ☎ 0483 38085  
W2 Trade Exhibitions Scotland ☎ 041-248 2895

# Bytebox

PART 1...RAY STUART



SINCE its introduction the BBC microcomputer has been widely accepted in education, industry and the home with over 400,000 units having been sold to date. This has given birth to a large quantity of software such as alternative languages to BBC BASIC, e.g. PASCAL, FORTH and LISP, and a wide range of utilities such as word processors, data bases, and machine code monitors. Much of the above mentioned software is only available in Read Only Memory (ROM) or Erasable Programmable Read Only Memory (EPROM). These are devices, programmed with the code for that particular utility, which retain their data when power is removed.

The BBC microcomputer is designed to support up to 16 of these ROMs, called "SIDEWAY (or PAGED) ROMs", numbered 0 to 15, but has only room for 4 such devices on its printed circuit board. BASIC and Disc Filing System (DFS) being the two commonly fitted ROMs. In order to allow the full complement of 16 ROMs to be available to the user, an additional printed circuit board has to be fitted to the BBC microcomputer.

This article describes BYTEBOX, a system that fulfils this and other requirements.

## DESIGN PHILOSOPHY

The experiences and views of several users in education and industry as well as those of home users were considered when the design of BYTEBOX was undertaken. The system was therefore designed to allow simple installation with no soldering being necessary.

A second view expressed was that of overheating. Some people had found that the inside of their BBC microcomputer became too hot when an internal ROM board was fitted, particularly if it was also powering a disc drive and/or other peripheral devices. This they said caused "funny things" to happen after the computer had been switched on for some time. Some had cured this by running the BBC microcomputer with its cover removed. However, they found this impractical as they then tended to drop screwdrivers, coffee and the like into the exposed circuitry, sometimes with disastrous results. With this in mind the design allows the system to be housed in an external box of similar finish to the BBC microcomputer.

Most users said that they would, at some time, if not immediately, require some Random Access Memory (RAM) in their system. Some people required 16K of RAM, whilst others only wanted 2K or 4K as they found it hard to justify the £70 or so required for two 6264s. Others said that they wanted battery backed RAM with write protect facilities. In order to provide all these requirements it was decided to provide 16K of optional RAM as standard, but also to provide additional plug-in units for greater versatility. Whatever RAM was to be used it was considered essential that this would be automatically selected whenever the SIDEWAY memory area was written to. In addition the fitting of RAM onto the main board should not require links to be altered and still allow 15 ROM/EPROMs to be supported.

## EPROMS

It is well known that the BBC's printed circuit board is designed for ROMs rather than EPROMs, with the result that some EPROMs from certain manufacturers will not function correctly. This is caused by incorrect, as far as EPROMs are concerned, termination of one of the ROM's pins. This was to be rectified in the design so that any make of EPROM could be used.

The inclusion of a Zero Insertion Force (ZIF) socket was thought to be a very useful addition, especially by users who evaluate or frequently change ROMs, who are developing their own or have more than 16 utility ROMs. This socket, which was to be accessible from outside the unit, was therefore included in the design specification.

The 27128 type EPROMs are expensive and sometimes difficult to find. However, 2764s are easier to find and the cost of two such devices is less than that for one 27128. An option was therefore included to allow two 2764s to replace one 27128.

In order to fulfil the first requirement, i.e. easy to install, it was necessary to find a suitable way of extracting all the required data, address and control signals as well as power via a single socket. As with all computers and microprocessor based systems it is the Central Processing Unit (CPU) that generates these signals. In the BBC microcomputer a 6502 microprocessor is used (see Fig. 1). There is only one socket in the BBC microcomputer from which all this information is available, namely, the 6502 socket.

The decision was therefore made to design a system in which the 6502 microprocessor is removed from the BBC microcomputer and located in the external system. This system is then connected to the BBC microcomputer via a 40-way ribbon cable which is plugged into the socket left vacant by the 6502.

The additional circuitry necessary for the full complement of 16 ROM/EPROM/RAMs to be supported would impose unacceptable loading on the 6502 microprocessor's outputs. Therefore one of the design objectives was to buffer all address, data, and control lines used by the system. All of these objectives have been achieved in the BYTEBOX system described in this article.

## SIDEWAY (or PAGED) ROM

Before BYTEBOX can be discussed in detail it is necessary to understand the concept of sideways or paged ROMs as they are sometimes called. The reason that they are called sideways ROMs is due entirely to their physical location within the BBC, in that they are located on the side of the printed circuit board, hence "SIDEWAY".

The BBC microcomputer is an 8-bit (one Byte = 8 bits) machine with 16 address lines that enable it to directly access  $2^{16}$  (65,536) bytes of memory. This is normally called 64K bytes as 1024 is referred to as 1K. However, it can be seen that as each ROM can contain 16K bytes (if 27128 type devices are used) and, as there can be 16 such ROMs in the system the total memory contained by

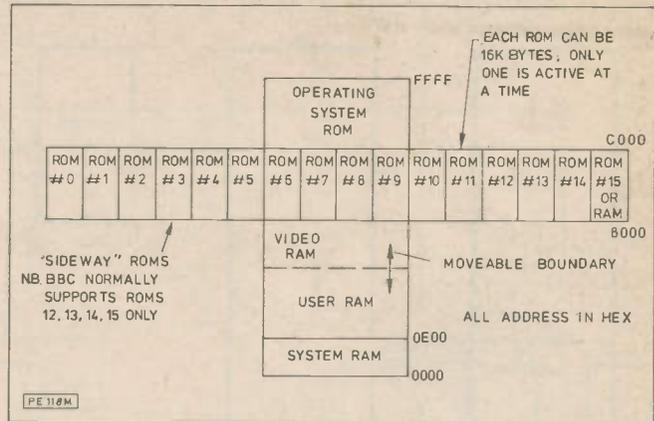
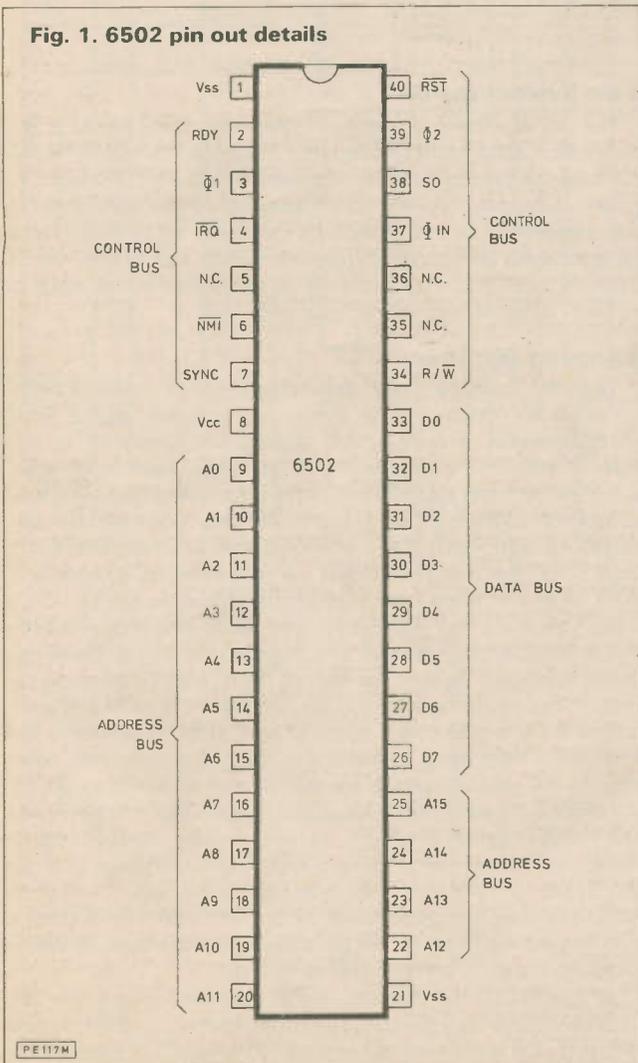


Fig. 2. The BBC Micro memory map

the ROMs alone is 256K bytes. This is far in excess of the address range of 64K. In addition, the BBC microcomputer has a further 16K of Operating System (O.S.) ROM and 32K of System RAM, thereby making a grand total of 304K of memory. How can this be so when it can only access 64K bytes?

The memory map of the BBC microcomputer is shown in Fig. 2. It can be seen that all 16 SIDEWAY ROMs in fact occupy the same memory area between &8000 and &BFFF. (Addresses are in Hex notation, a convention that will be used throughout the article and denoted by &). This is acceptable as only one ROM can be selected at any one time, thereby occupying the 16K bytes available. This can be likened to a book containing 16 pages, only one of which can be read at a time, hence the term PAGED ROMs.

In practice the BBC microcomputer may appear to use more than one ROM at a time, but what is in fact happening is that the Operating System is constantly switching between ROMs. For example, if one is running a program in BASIC (one ROM), it is possible to call a ★ command contained within another ROM; say ★CIRCLE in a graphics generator ROM. In this case the Operating System will find the graphics ROM, execute the ★CIRCLE command, and then return to the BASIC ROM. Whichever ROM is selected is called the "current ROM". The method by which the current ROM number is decided is complex and outside the scope of this article, but is well detailed in books such as "The Advanced User's Guide".

ROMs and EPROMs have a pin designated "chip select" (CS) which, when taken to logic 1 disables the device. This in effect removes that device from the system and it no longer plays an active role. However, if this pin is now connected to logic 0 the device is enabled and can now take an active role in the system. The trick therefore of having 16 ROMs in the system is to only enable one at a time.

In the BBC microcomputer this is achieved by arranging for a hardware 4-bit latch, located at address &FE30, to contain the number of the currently selected ROM. Only the upper two bits are decoded thereby limiting the number of useable ROMs in the BBC microcomputer to four. BYTEBOX, however, uses all four bits of its latch which are subsequently decoded to provide 16 chip select lines. The circuit is designed such that only one of these 16 lines can be at logic '0' at any one time, thereby preventing a number of ROMs trying to access the system at the same time.

## BYTEBOX

BYTEBOX was designed as an external system, housed in its own case and taking its power from the host BBC microcomputer. The block diagram, Fig. 3, outlines the system design, with Fig. 4 showing the circuit in detail.

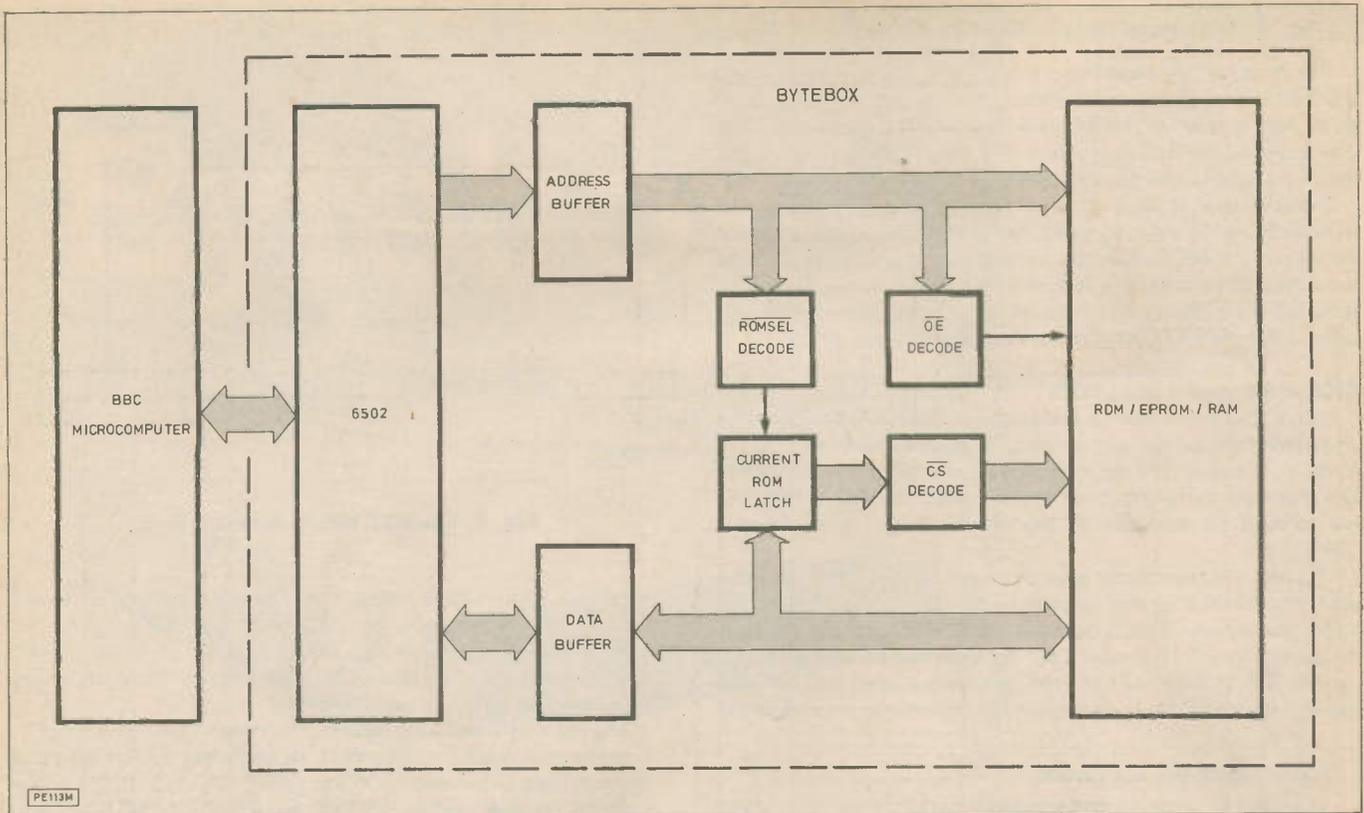


Fig. 3. Schematic diagram of the Bytebox system

## BUFFERS

The main printed circuit board forms the heart of the system and contains all the buffers and decoders required to support the 16 ROM/EPROMs.

As mentioned above, the design philosophy requires that the 6502 microprocessor, normally located inside the BBC microcomputer, is moved onto this board. The BBC microcomputer is connected to the Romboard, via a 40-way ribbon cable that is plugged into SK1. The 6502 (IC1) is connected in parallel with this, thereby allowing all the signal lines to pass to the BBC microcomputer as normal. However, the signals required by the Romboard are also fed to a number of buffers to prevent the additional circuitry loading the original system.

It can be seen in Fig. 1 that the 6502 microprocessor has an output called R/W on pin 34. This signal is used to inform the remaining circuit of the data flow direction. This signal is buffered by two inverters, IC5a and IC5b, which are part of a 74LS04. The 6502 microprocessor also produces a clock signal  $\phi$ 1 on pin 3, the inverted form of which is required later. IC5c is used to provide this whilst also acting as a buffer.

The sixteen address lines, A0 to A15, are fed to IC2 and IC3, two 74LS244 non-inverting tri-state buffers. In this design there is no need for these devices to be tri-stated therefore their mode select inputs, pins 1 and 19, are connected to logic '0'. Address information only travels in one direction, out from the 6502 microprocessor, so no flow direction information needs to be supplied to these buffers.

This is not the case, however, with the data bus (D0 to D7). The microprocessor not only needs to write data to the remainder of the circuit, but must also be capable of reading data from the memory devices. Therefore the type of buffer required, has to be bi-directional, with the direction of data flow being selected by the 6502 microprocessor. IC9, a 74LS245, is employed to provide this facility. The R/W line from IC5a is fed to the data bus buffer's direction control input, pin 1, to allow it to transmit data in the correct direction.


The circuit requires two sets of address decoders, one to enable the current ROM latch and the other to enable the ROM/EPROM/RAMs. First consider the decoding for the current ROM latch. As mentioned above the BBC microcomputer stores the number of the current ROM at address &FE30. However, the latch can in fact be addressed by any value between &FE30 and &FE3F, i.e. 16 memory locations. Normal convention is to denote this range by &FD3X, where X can be any hex value.


## ADDRESS DECODING

The BBC microcomputer generates a signal called ROMSEL covering this range, but as this is not available on the 6502 microprocessor socket it also has to be generated on the ROMBOARD. This is achieved by using two interconnected chips, IC4 a 74LS30 and IC6 a 74LS138. The decode circuit and the bit code for &FE3X are shown in Fig. 5. The only time that the output for the 74LS30 NAND gate can be logic '0' is when all its inputs are logic 1. For this reason its inputs are connected to A5 and A9 to A15, all of which are logic 1 when the address is &FE3X. IC6, a 74LS138, is a 3 line to 8 line decoder which also has two active low and one active high chip select inputs. Only when these chip select inputs are valid will the data on the A, B and C inputs be decoded. The output from the 74LS30, is inverted by IC5f and fed to one of the low chip select inputs of the 74LS138, the other low chip select input being connected to A8, and the high chip select input to A4. All these inputs are valid when the address is &FE3X. A7 and A6 are both logic 0 for &FE3X which when combined with the R/W signal and the other decode circuit inputs mentioned above, will produce a logic 0 on the Y0 output of the 74LS138, i.e. A, B and C will all be logic 0. But why use the R/W line? This is used to ensure that the current ROM latch is enabled only when it is written to. We have therefore reproduced the same ROMSEL signal as the BBC microcomputer.

In addition to the ROMSEL signal described above, the BBC microcomputer also generates an output enable signal OE. As with ROMSEL, OE is not available at the 6502 socket and therefore has

**Fig. 4. Complete circuit diagram of the Bytebox system**

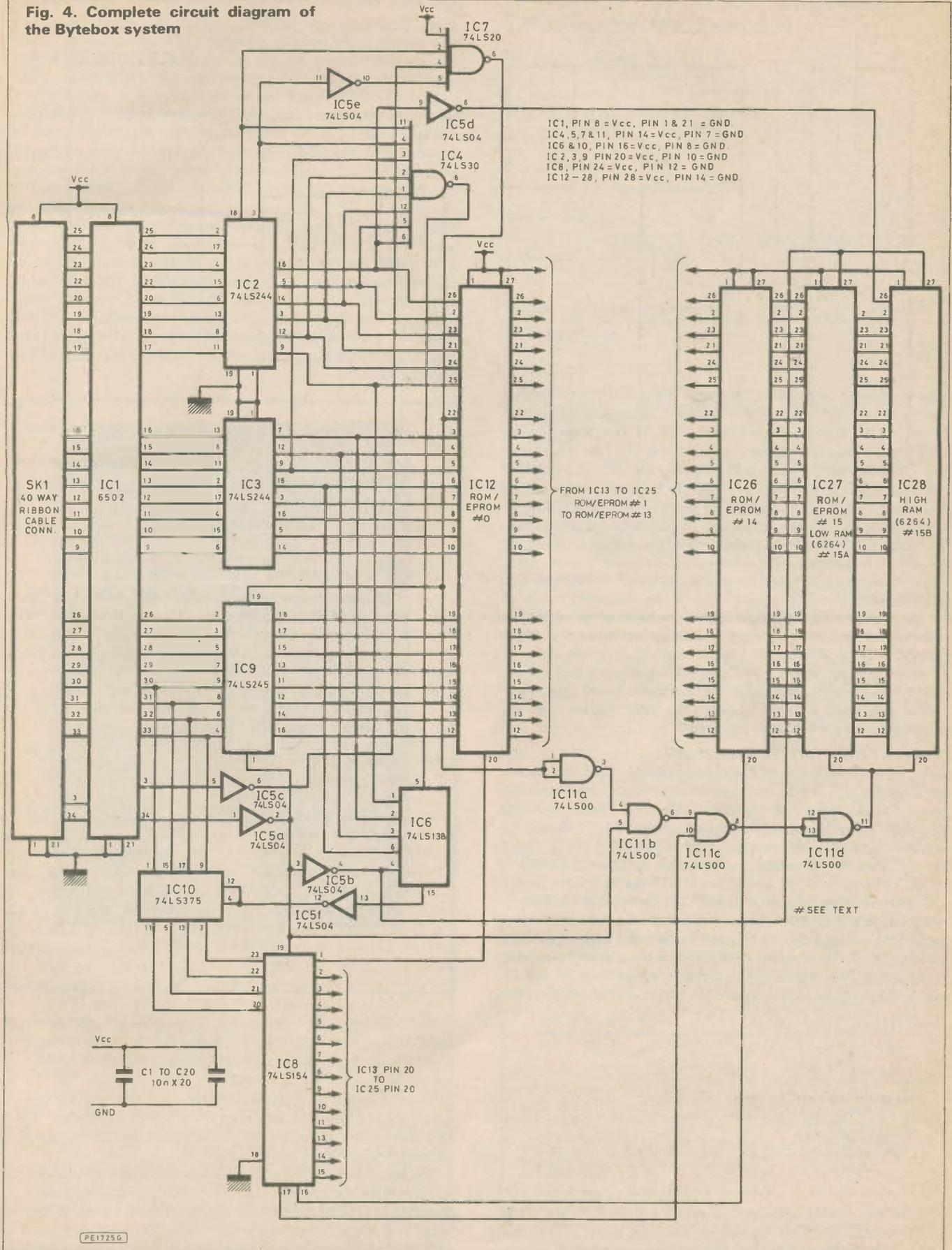

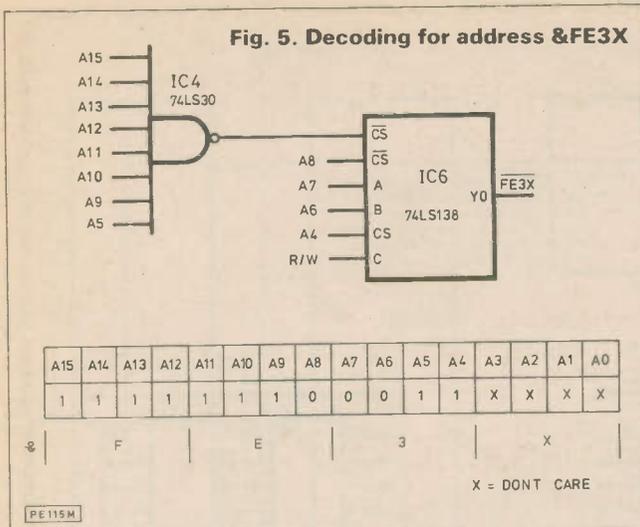

to be generated onboard. Fig. 6 shows the circuit and bit pattern relating to this ROM/EPROM/RAM enable OE output. This has to be valid for the address range &8000 to &BFFF as indicated by the BBC microcomputer's memory map (see Fig. 2). This is achieved by a 74LS20, a four-input NAND gate. Like the 74LS30, this chip has to have all its inputs at logic 1 to produce a logic 0 at its output. Fig. 6 also shows the bit pattern for the address range &8000 to &BFFF. It can be seen that only A15 and A14 remain constant over the range, therefore only these two address lines need to be considered by the decoding circuitry.


In the section on buffering it was stated that the 6502 generates a clock signal  $\phi 1$ . This is also used by the decoding circuit to ensure that the ROM/EPROM/RAMs are accessed when the address and data lines are valid. In order to provide the 74LS20 with logic 1's on all its inputs it is necessary to invert the A14 line by means of IC5e, part of a 74LS04. The fourth input to IC7 is unused and is therefore tied to logic 1 to ensure correct operation.

We now have the two decoded address signals that are essential to the remainder of the circuit.

### CURRENT ROM LATCH/DECODER

As stated above the BBC microcomputer writes the current ROM number into a 4-bit latch at address &FE3X, the data being present on the lower four data lines, D0 to D3. These four data lines are therefore fed to IC10, a 4-bit latch type 74LS375, and the ROMSEL signal described above is fed to its enable inputs, pins 4 and 12. Thus data is written into the latch whenever ROMSEL is active, i.e. whenever the address is &FE3X during a write cycle.


The outputs from the latch contain the current ROM number in hex form. However, 16 separate chip select lines are necessary as each of the memory devices requires its own chip select line. IC8, a 4-line to 16-line decoder type 74LS154, is therefore incorporated in the circuit. This device has two enable inputs, pins 18 and 19, which have to be at logic 0 before the device will decode the input

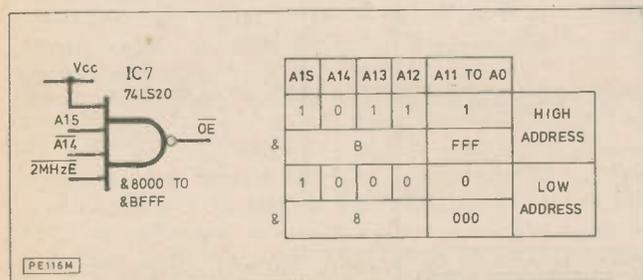

**Fig. 6. Bit pattern for the enable output (OE)**

data. One of these inputs, pin 18, is connected directly to logic 0 whilst the other is connected to the R/W line. When the system tries to write to the sideways memory, this signal is at logic 1. This disables IC8 thereby turning all the ROM/EPROMs off, which prevents data bus conflicts which would otherwise produce faults.

However, if RAM is fitted in the system it is necessary to generate a chip select signal for ROM/EPROM/RAM position 15 during a write cycle, for it is here that RAM will be located. In addition, this chip select line must be automatically generated irrespective of the value stored in IC10, the current ROM latch. It is therefore evident that some additional circuitry is necessary. To this end IC11, a quad two-input NAND gate type 74LS00, is incorporated. The output enable OE signal is inverted by IC11a and gated with R/W line by IC11b to produce a signal, on pin 6, only when a SIDEWAY write cycle occurs. IC11c acts as an OR gate to combine the position 15 read select (from IC6 pin 17) and the write select (from IC11b pin 6) signals. Thus an active high chip select signal for memory read or write cycles is available for memory device 15. The memory devices require the chip select signal to be active low, the active high signal from IC11c pin 8 is therefore inverted by IC11d.

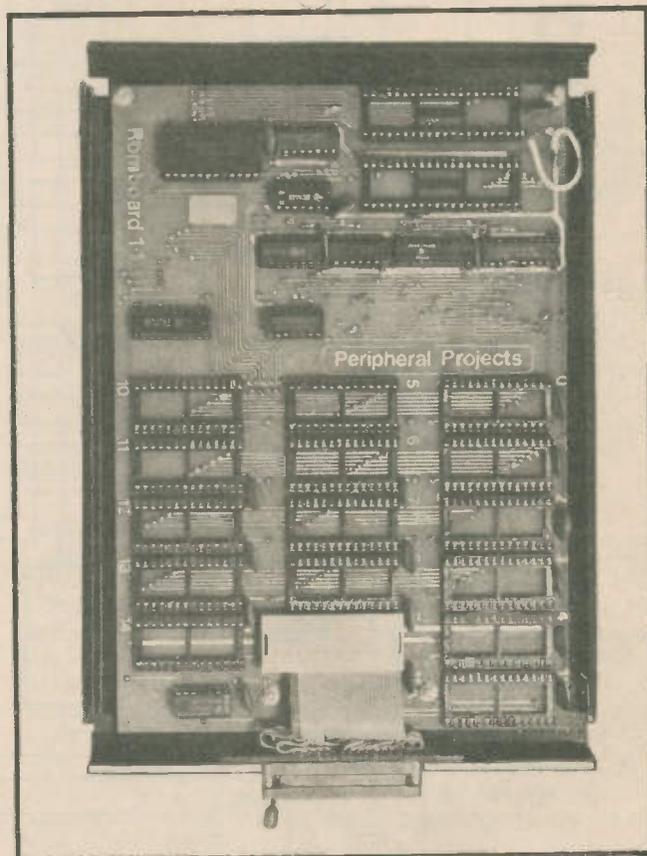

The three memory devices that can be used with the main printed circuit board are; the 27128 type (16K Byte ROM/EPROM), the 2764 type (8K Byte ROM/EPROM) and the 6264 (8K Bytes RAM).

It can be seen that they are extremely similar, this is by design rather than accident, as they conform to a JEDEC standard. They only differ in 3 of their 28 pins, i.e. pins 1, 26 and 27. Pin 1 is not used by RAM or ROM but is by EPROM.

The BBC microcomputer's printed circuit board is designed to support ROM, consequently pin 1 is not connected. However, it is specified in EPROM data sheets that pin 1 must be connected to logic 1, if not spurious faults can occur. Some manufacturer's EPROMs are more prone to giving errors, when used in the BBC

## COMPONENTS . . .

### MAIN BOARD

#### Semiconductors

IC1	6502*
IC2	74LS244
IC3	74LS244
IC4	74LS30
IC5	74LS04
IC6	74LS138
IC7	74LS20
IC8	74LS154
IC9	74LS245
IC10	74LS375
IC11	74LS00
IC12-IC26	ROM/EPROM* (as required)
IC27	ROM/EPROM or 6264*
IC28	6264*

#### Capacitors

C1-C20	100n disc ceramic (20 off)
--------	----------------------------

#### Miscellaneous

Printed circuit board; through link pins; i.c. sockets\*; 40-way IDC d.i.l. connectors (2 off); 40-way ribbon cable; case\*; insulated pillars.

\* See text

### 6116 RAM BOARD

#### Semiconductors

IC101-IC108	6116 (8 off)
IC109	74LS138

#### Capacitors

C101-C105	100n disc ceramic (5 off)
-----------	---------------------------

#### Miscellaneous

Printed circuit board; i.c. sockets; 14-way plugs (2 off).

### BATTERY BACKED RAM BOARD

#### Semiconductors

TR1,TR2	BC109 (2 off)
D201	OA47
IC201-IC202	6264 (2 off)
IC203	74LS00

#### Capacitors

C201	10 $\mu$ tant.
C202	100n disc ceramic

#### Resistors

R201	1k5
R202,R203,	10k (3 off)
R207	
R204,R206	1k (2 off)
R205	4k7

#### Miscellaneous

P.c.b. mounted 3-6V battery; SW1 single pole p.c.b. mounted switch\*; printed circuit board; 14-pin plugs (4 off); i.c. sockets.

\*See text

### 2764 EPROM BOARD

#### Semiconductors

IC301-IC302	2764* (as required)
IC303	74LS00

#### Capacitors

C301-C302	100n disc ceramic (2 off)
-----------	---------------------------

#### Miscellaneous

Printed circuit board; i.c. sockets; 14-way plugs (2 off).

\*See text

### ZERO INSERTION FORCE (ZIF) SOCKET ASSEMBLY

28-pin Textool ZIF socket  
28-way ribbon cable  
28-way IDC d.i.l. connector\*  
Printed circuit board

\* See text

#### Constructor's Note

All components, including EPROMS, printed circuit boards, case, or complete kits as well as ready built units are available from: **PERIPHERAL PROJECTS**, 25 Braycourt Ave, Walton-on-Thames, Surrey KT12 2AZ. Please send SAE for details.

microcomputer, than others due to the technology used to produce them. To prevent errors occurring in BYTEBOX pin 1 is connected to logic 1. Pin 26 on all EPROM and ROM is required to be at logic 1 for all modes other than programming EPROMs. As this system does not have provision for programming, pin 26 on all ROM/EPROM chips is tied to logic 1.

For RAM chips pin 26 is reserved for the  $\overline{R/W}$  input. It can be seen that this pin is at logic 1 when a read is required, this is the same requirement as for the ROM/EPROMs. The result of this is that for position 15 (IC27) this pin is connected to the  $\overline{R/W}$  line making it suitable for all three types of memory. Note: positions 0 to 14 (IC12 to IC26) will only support ROM/EPROM. IC28 is reserved for RAM only.

The 6264 device is an 8K Byte RAM chip, therefore to provide 16K bytes of RAM two are required (IC27 and IC28). As previously described, a chip select signal is available for either a read or write to these chips. A second chip select signal is therefore required to identify which of the two 6264s is to be enabled. Examination of the 6264 pinout reveals a second chip select input, pin 26, which in this case is active high. The A13 signal can be used to split the 16K memory block into two 8K halves. When A13 is logic 0 the lower half is addressed, and when it is logic 1 the upper half is addressed. All that is required therefore, is to feed A13 to pin 26 on one of the two 6264s, and  $\overline{A13}$  to pin 26 of the other.  $\overline{A13}$  is available from the output of the inverter IC5d. By using the above method 16K bytes of RAM can be inserted into position 15 without having to make any alterations to the board whilst still leaving space for 15 ROM/EPROMs.

**NEXT MONTH: P.c.b. designs, constructional details and installation. Also battery backed-up RAM and alternative memory boards.**



# INDUSTRY NOTEBOOK

By Nexus



## Jitters

Measured by investor confidence it was a long hot summer. The electronics industry lost its sparkle and this time round you couldn't say it was just a result of the old stock exchange maxim "sell in May and go away".

The collapse earlier in the year of Sinclair and Acorn started the rot. After all, these two enterprises had seen off a number of smaller competitors, had been profitable and looked sound enough until the PC market turned sour. Unhappily the investing public tends to equate highly publicised outfits in the consumer and entertainment sectors with the electronics industry as a whole. Rather like condemning the performance of a department store just because the toy fair had suffered a bad season.

Booms and busts are nothing new in the consumer market. The boom in video recorders in 1982 and 1983 had turned into a near slump by 1984 when deliveries to the trade fell by half. There is such a thing as saturation in any market and, when prices are falling, consumers hang back in the expectation of lower prices later on, or the novelty merely wears off.

The problems of the consumer sector of the industry were not confined to the comparative tiddlers. The giants with heavy consumer market business were also suffering. Philips in the UK had a record turnover, topping £1 billion for the first time, yet trading results showed heavy losses in 1984.

Then came warnings from chairmen of reduced profit expectations, not least from GEC and Racal. So electronic shares were marked down all round.

There were other factors which possibly contributed to a spasm of selling. Continued high interest rates, increasing wage costs, rising value of the pound, continued squabbling in the EEC, downturn in the US economy and uncertainty in oil pricing.

The mood of dejection persisted even when companies turned in good results. Cable & Wireless profits rose 29 percent from £190 million to £245 million but the share price was clipped by 20p. Ferranti profits were up 19 percent at £46 million and their shares dropped. Investment sentiment was decidedly nervous and made more so by gloomy news from Thorn EMI and STC.

It is exactly a year since I recorded on this page the purchase for £95 million by Thorn EMI of the Government holding in Inmos. My comment was that the Government was pleased to pass on a responsibility no longer welcome and to recover the taxpayers' investment. Last July Inmos announced redundancies both in the UK and USA. Also a year ago I was writing of STC's expansion plans which included the creation in STC of 3,000 new jobs. Alas, a year is a long time in the electronics industry.

## Work Patterns

Scotland's Silicon Glen is a perfect example of a shifting pattern of employment in the industry. The workforce over a period of six years from 1978 to 1984 declined from 36,800 to 36,650 while output doubled and redoubled. As a proportion of the whole the unskilled operators employed fell in this period by 18 percent while scientists and technologists increased by 94 percent and technicians by 26 percent. Even the number of craftsmen declined by 9 percent.

Although electronics may be regarded as a special case this is not entirely so. According to John Cassels, director general of the National Economic Development Office, the pattern is generally the same throughout industry. In short, the unqualified will have little hope of employment.

The trend is confirmed by the scramble by progressive companies for new graduate intake with employment prospects firmer than for many years. One report claimed that 20 percent of vacancies for graduates were unfilled with the highest proportion in industry.

Another shift, this time at workbench level, is the no-strike, single-union workforce pioneered by the EETPU now under the able leadership of Eric Hammond. Universally hated by left-wing militants, he expects to double the number of no-strike deals by the end of the year.

His present membership is 365,000 but if a projected merger with the engineering workers and with the white-collar ASTMS can be agreed, then the new grouping would be 1.7 million strong. This could provide a powerful influence on the whole of the labour movement in its attitude to wealth creation and consequent security and prosperity for workers.

Even if no merger took place the electricians' example would remain that there are more sensible ways of conducting negotiations than walking out on the job which, in effect, is merely soiling one's own nest.

## Pressing On

Despite difficulties in some sectors the electronics industry remains in good shape with plenty of major contracts being signed. The size of some of the orders brings the state of the industry into proper perspective.

Ten years ago the annual turnover of the Racal Electronics Group was just short of £80 million. In one three-month period up to mid-summer this year, Racal-Tacticom received orders for tactical radio equipment to the value of £81 million, and this for a single product line.

Marconi Radar in a £38 million deal is supplying an extension and update to the Sultanate of Oman's integrated air defence system. This is an enhancement of air defence capability with which Marconi was involved in 1976 and 1979.

Then there is a nice contract worth 150 million dollars to a consortium headed by British Aerospace. This is for a new generation of *Inmarsat* communications satellites. Almost without our noticing it ship-to-shore communications by satellite has had a healthy growth rate with 43 member states now participating. The first of the second generation *Inmarsats* will be ready for launch in 1988, as yet, it has not been decided whether the *Space Shuttle* or *Ariane* will be the launch vehicle.

Of course not all recent contracts are in the multi-million pound or dollar bracket but there are plenty of £1 million and upwards.

Electronics research is also healthy despite the chronic shortage of engineers. GEC has just drawn together into a single research company the three great but separate strands of the Marconi Research Centre at Great Baddow, the Hirst Research Centre at Wembley and the Engineering Research Centre at two locations in the Midlands. All the research effort will now be coordinated more efficiently in the new company, GEC Research Ltd.

The total complement of GEC Research is currently 2,500 people of whom 1,300 are scientists and engineers with first or higher degrees. Over 10 percent of the professionally qualified staff are women. Income of the company is some £60 million per annum, roughly one tenth of the total R & D spend within GEC.

There is good news for those who grouse about the Japanese who use the UK only as production units within the EEC. Matsushita, better known by the brand name Panasonic, is to set up R & D labs in the UK headed by an as yet unnamed British scientist.

# CLEF ELECTRONIC MUSIC

## THE CLEF CMS



The FULLY programmable digital synthesiser that you can AFFORD  
**THE NEW CLEF COMPUTER MUSIC SYSTEM** is so user programmable that you need a BBC Micro to run it! 32 harmonically programmable oscillators. 32 programmable envelopes. 5 octave touch sensitive keyboard, up to 4 OSC/ENVS per note. Real time sequencing. Massive potential for future software. Complete system (without BBC Micro) £495 built. Phone or write for details. Modular systems also available.

## MASTER RHYTHM PROGRAMMABLE DRUMS



As Published in P.E

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.  
**COMPLETE KIT £79**  
**STRING ENSEMBLE ROTOR-CHORUS MICROSYNTH P.C.B. & ELECT KITS**  
 £198.50  
 £98.00  
**PERCUSSION SYNTH P.C.B. & ELECT KITS**  
 £86.90  
 £97.90

## 88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation on Piano Key Inertia.

### COMPONENT KITS

Including Keyboard  
 88 NOTE £266  
 72 NOTE £234  
 The above may also be purchased in four parts.  
**SQUARE FRONT KEYBOARDS**  
 88 NOTE £60  
 49 NOTE £29  
 73 NOTE £50  
 30 NOTE £19  
**KEYSWITCH ITEMS ALSO AVAILABLE**



## BAND-BOX PROGRAMMABLE BACKING TRIO



As Published in P.E.  
**THREE PIECE BACKING BAND** Generates the sounds of three instrumentalists to back Soloists  
**DRUMS + BASS + KEYBOARDS** Over 3,000 chord changes (60 scores) on 132 different chords - 16 chord sounds. Master Rhythm also required.  
**FULL KIT £265 BUILT £370**

**CLEF PRODUCTS (ELECTRONICS) LIMITED**  
 (Dept PE) 67 THORNWAY, BRAMHALL, STOCKPORT, CHESHIRE SK7 2AH  
 All Demonstrations by Appointment only  
 TEL 061-485 4889

## Introducing...



WITH 'PERSPEX' SEE-THROUGH CYLINDERS!

COMPLETE SYSTEM UNDER £1000! including software!



**NAIAD MICRO ELECTROHYDRAULIC ROBOT**  
 BEING FEATURED IN WIRELESS WORLD November Issue



Please phone for brochure: 0264 50093  
 West Portway Industrial Estate, Andover SP10 3PE.  
 A private and independent company giving prompt, personal service.

## ROBOTS for EDUCATION TRAINING and INDUSTRY




**MENTOR System** from £495



Hydraulic using water!

**NEPTUNE System** from £2195

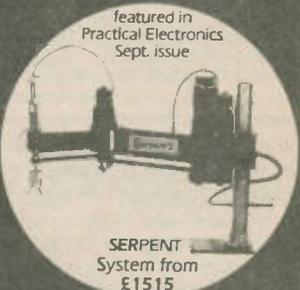

featured in Practical Electronics Sept. issue

**SERPENT System** from £1515

**MENTOR DC** servo desktop robot; 8 bit control system; 300gm capacity; 420 reach.

**NEPTUNE I/II** 6/7 axes 8/12 bit control system 2.5kg capacity. 1120mm reach.

**SERPENT I/II** 5 axes 12 bit control system 2 kg capacity 400/650mm reach.

Robots programmed from keyboard or handheld simulator (model robot).

Robots may also be taught by 'lead by the nose' method.

Extensive software is supplied free with each robot.

Leads available for connection to BBC, ZX Spectrum, Apple IIe, Commodore 64 and VIC 20.

Most other micros are also easily usable with these robots.

Robots available as kits or ready built.

FMS (Flexible Manufacturing System) work cell additions also available.



Please phone for brochure: 0264 50093.  
 West Portway Industrial Estate, Andover SP10 3PE.  
 A private and independent company giving prompt, personal service.



## 'RUR' HOBBY ROBOT

### REEKIE INDUSTRIAL & ROBOTIC CONTROL CPU CARD


The electronic Hardware for the Reekie Universal Robot (R.U.R.), as articulated in the June and August 1985 issues of "Practical Electronics" is also very suitable for many other Industrial Applications. It is therefore offered for sale as a stand alone system providing the following:

Z8 CPU with internal 2K RAM and Tiny Basic/Debug program.

4 K of RAM/ROM on board expandable to 126K if required, through the Edge Conn. 20 lines of I/O is available for such functions as; Motor operation, Sonar, LEDs, Sound, Speech Synthesis, Voice Recognition, Burglar Alarm, Smoke and Fire detection and for add-on Logic Board for the Reekie all Belt Robot Arm. RS232/432.

The on board options for RAM/ROM expansions means use of Custom Built EPROM Firmware for which Assemblers are available to assist users of the Z8 system to 'Blow' their own EPROMs.

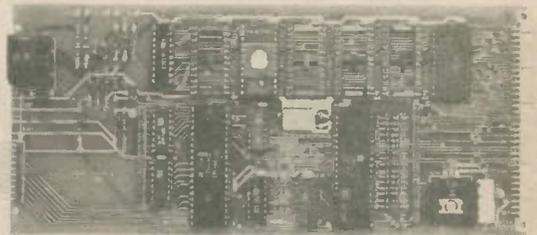**£130.74 + VAT**  
 Carr £8.00 extra. Built & tested as illustrated



**TERMS:** ACCESS CARDS & OFFICIAL ORDERS from approved industrial or educational establishments accepted, otherwise terms strictly CASH WITH ORDER. Please allow 28 days for delivery

## REEKIE ROBOTS

Beaufort Works, Beaufort Road, Richmond Road, East Twickenham, Middlesex TW1 2PQ.



# Readout...

## Confused

Sir—May I make a couple of suggestions for articles in your magazine Practical Electronics. The ideas spring from an excellent series of articles by Tom Gaskell, namely *Digital Design Techniques* which started in August 1981. Paragraph three in the introduction to the series says it all.

From a more theoretical understanding of digital electronics I am now able to design with confidence using the series as a "bible". Without this series I would neither have had the time, money and in some cases knowledge to sift through manufacturers' data sheets to extract the relevant information.

Suggestion one—I am rather confused by all the new logic families, so how about an up-date article giving relevant practical information set out in the same easily understood way of Tom's earlier article?

Suggestion two—As my designs get more sophisticated and use more i.c.s (my latest design for a burglar alarm so far contains 15 chips), the question of can I use a microprocessor instead raises its head. The answer must be yes, but where do I start? What are the practical hardware considerations to be taken into account, which is the best microprocessor to concentrate on, what about software—is it practical to use it to create large time delays, how about connecting a small key pad etc. etc?

I do not possess a microcomputer nor do I really want to, or learn a language. I understand '1's and '0's, i.e. machine code. Perhaps the first practical project for the series would be a "programmer" for entering the '1's and '0's in the ROMS.

I have a theoretical understanding of microprocessors but lack the practical knowledge (refer again to paragraph three in Tom's series).

I hope you will be able to use my suggestion.

Brian McWhinnie,  
Glasgow.

*Points taken—see Introduction to Microprocessor Systems (page 20). How about that for service?*

## Twenty Years of Stagnation

Sir—I welcome your editorial (July issue) on what appears to be the lack of development of "electronics" as a subject available within the curriculum of our secondary schools.

I speak as a mathematics/physics/electronics teacher with 25 years' teaching experience in Scotland and England and also on the continent and in Africa. Perhaps I am most concerned with what is happening, or rather not happening, here in Scotland, although I should say that I have an enlightened headmaster, himself a physicist, who was prepared to stick his neck out and introduce the A.E.B. 'O' level Electro-

electronics course in this school. Scotland, however, has a national policy, recently stated by the Scottish Education Department, NOT to introduce electronics as a separate subject, although Scotland is reputedly host to some 40 per cent of the European electronics industry.

It is very difficult to pin-point the reasons for this apparent apathy, or in some instances, outright opposition. I see some of them as follows:

- (i) Electronics and microelectronics are somehow seen as synonymous with computing and microcomputing.
- (ii) The government, in its wisdom, has seen fit to deluge schools, including primary, with computers. We now have perhaps more computers per capita in schools than any other country in the world—however, it is a known fact that the vast majority of these are underused or misused with the result that the average pupil's concept of the computer and its applications extends to being able to load a program from a tape or disc and spend countless hours playing 'Space Invaders' and similar mindless games, whilst the government and the majority of teachers think they are being exposed to "electronics"—99 per cent will never see a transistor or a silicon chip!
- (iii) These computers were largely introduced to mathematics departments where teachers rapidly became fluent in the new vocabulary without in most cases (not all, of course) having the faintest idea of how a computer works or the practical applications to which it can be put. "Interfacing" to them means 'plugging in another bit of hardware' and producing another bit of "magic". Teachers with applied science or engineering backgrounds were probably the last to be equipped with a computer—some are still waiting!!
- (iv) Teacher training in this field (electronics) is grossly inadequate, probably because the trainers themselves don't have the skills. Regional education authorities no longer provide suitable in-service training or indeed refuse to allow teachers to attend such courses, even during their holidays, except at their own expense.  
I myself was refused the funding to attend an excellent national course on interfacing, I was instead expected to become fully proficient, along with less experienced colleagues, in the art of interfacing by attending a 3-day "crash" course organised by my employees. When I tried to inquire into this policy, I was told that

if I became better qualified I might leave and another regional authority would benefit!

- (v) There is a very pronounced "no man's land" between the frontiers of pure physics and pure engineering in schools, and it takes a bold man to attempt to cross onto his neighbour's ground. Indeed, in many schools, teachers from either department are barely on speaking terms.  
Again, I am fortunate in this respect. A few schools have successfully implemented courses in Technology where the fields of physics and engineering overlap.
- (vi) Change in education in Britain is incredibly slow. Ten years is not uncommon—I was piloting a 16+ combined physics course in England in 1974—where are we now? We have thousands of working parties, consultative committees, pilot schemes etc. whereas with a little goodwill, common sense and adequate finance, even major changes could be introduced in a matter of months.  
The teachers on the whole are willing. It is their masters, the bureaucrats, who no longer ever see a pupil or indeed who may never have seen one, who are responsible for the chaos in education today.  
Opinions of practising teachers are sought, in the guise of "consultation", but it seems to me that these professional opinions are then all too often ignored. The end result is that unwanted changes are then introduced, resulting in a disgruntled, disillusioned and demoralised teaching profession.

## A Clear Distinction

To conclude, I think it is high time that some or all of the following steps be taken to avoid the present chaos in education and to ensure that today's youngsters leave school prepared for the new technology without which this country will continue its headlong decline:

- (1) A clear distinction must be made between "microelectronics" and "microcomputing".
- (2) The government must ensure that adequate provision is made in the



school curriculum for microelectronics either as a separate subject or as part of physics or technology courses. In particular, more care must be taken to ensure that course choices are realistic so that pupils are not for example forced to make the choice between electronics and several other traditionally girls' subjects such as domestic science or secretarial studies.

- (3) Resources must be made available, particularly when the expertise is to hand. It is pointless putting vast numbers of microcomputers in schools where there is no expertise and even less motivation.
- (4) Teachers must be given the opportunity to re-train by attending in-service courses run by experienced, and preferably practising, teachers.
- (5) Teacher-training courses in colleges must be up-dated so that at least some of the new entrants to teaching have some awareness of electronics. Far

too many of the older generation of pure physics teachers are either 'afraid' of electronics or downright opposed to becoming involved.

- (6) Finally, teachers' pay must be improved in order to attract suitable entrants. My 24 year old son, a graduate electronics engineer, has a far higher income than mine!

Andre H. G. Saunders, B.Sc.,  
Kelso High School,  
Roxburghshire.

### Don't Bank on IT

Sir—As a member of a band of home computer constructors, which has a good newsletter, lots of software, including two BASICS and FORTH. I took the trouble to write to five top chip manufacturers asking for details and data sheets on various i.c.s, for instance, interfacing, real time clock, DAC's, etc.

The idea was to build up a "Data Bank" so members could get the information that

they need to use that special chip. It may have even appeared as a newsletter article describing its function and use.

However, things went wrong as only one manufacturer bothered to reply; this was Ferranti, who supplied a good deal of useful information. In fact, I wrote again and they sent details of the ZN447-9 ADC's and the ZN1035E programmable timer (0.01 sec. to 3months) MPU bus compatible, to name but two!!—*Well done, Ferranti!*

To those who, like Motorola, Nat Semi, G.I., etc., who found it all too much trouble, I say shame on you; we the public are the ones who buy your products, you should keep us informed—it can only help your sales!

Lastly, to anyone out there in the manufacturing or retail business; like to send us data sheets or details? They would be most welcome!

Mel Saunders,  
7 Brumcliff Road,  
Thurmby Lodge,  
Leicester LE5 2LH.

## FREE! READERS' ADVERTISEMENT SERVICE

# PE BAZAAR

**RULES** Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid "date corner"**. Ads. will not appear (or be returned) if these rules are broken.

**HP185A** high frequency dual trace scope with 187B plug in, 10 mv/cm, delayed trigger, 500 MHz calibrator, £150 ono. Mr. J. H. Rudge, 20 Blackthorne Close, Solihull, West Midlands. Tel: 021 705 8459.

**HI-RES** board (C.U.A.) for UK101, £20. Also printer R5232C 300 baud and power supply. Offers please. C. J. Hellen, Vine Cottage, Main Road, Alresford, Colchester, Essex. Tel: Wivenhoe (020622) 5671.

**PE85 FEB.** Modular Audio Power System boards, components i.c.s mounted. Offers plus postage. Mr. L. T. Hill, 14 Rothesay Terrace, Bedlington, Northumberland.

**OSCILLOSCOPE** Tequipment D61 twin beam, x10 probe. Little used, £120 ono. D. Callender, 17 Badger Way, Banbury, Oxon. (0295) 53475.

**TEKTRONIX** oscilloscope dual trace, 10 MHz, good condition, £85. Marconi LCR bridge, £85. Nova 3 mini-computer. Reasonable offer. T. Haley. Tel: 01-868 4221.

**MICROPROCESSOR** (plus) microcomputer, input/output board, printer. All for £250. Includes manuals, student workbook. Mr. D. H. Slater, rear of 25 New Market Street, Colne, Lancs. BB8 9BJ.

**INTERAK** computer Z80A, 64K ram, RS232 interface, ASCII keyboard, card frame, psu, monitor eprom, manuals, £230. Mr. B. Seeds, 47 Conygar Road, Tetbury, Glos. GL8 8JF. Tel: 0666 53084.

**PE DEC 68**—Dec 84. PW May 69—Nov 82. WW Jan 75—Dec 84. R&EW first—Jan 84. ETI Jan 80—Dec 84. Offers. Bill Harvey, 23 Orleans Avenue, Glasgow G14 9LA. Tel: 041-954 9948.

**WANTED:** Information on Crypton motorscope major, model BDX17, and on Brimar tube D21/106H. B. D. O'Gorman, 15 Stafford Road, Caldicot, Gwent.

**WANTED:** 'Television' magazines, 1977 to 1983. Tel: 01-451 3093.

**WANTED:** Philips 1700 LVC or VC video

tapes. Phone Dingwall (0349) 61376. D. Parsonage, 2 Mount Park, Riccall, York.

**WANTED:** Repair or set-up manual for President Adams SSB/AM transceiver. Buy or borrow Mr. W. Weeks, 104 Oldfield Rd., Hampton, Middx. Tel: 01-979 2680.

**WANTED:** Teletext chip set or system for external connection to television. Tel: Mil-lom 2998 after 6 p.m.

**TEKTRONIX 581A** scope, plug in type 82, manuals £5 both. Tel: Fareham 239919 evenings.

**15-CORE CABLE**—16 to 18 meter lengths. Suitable telephone audio etc. Not screened. Offers plus p&p. L. T. Hill, 14 Rothesay Terrace, Bedlington, Northumberland.

**UK101** cased, 24K, basic 5, codekit, toolkit, Cegmon, J1 board, ROM-board, 8120 ZX81 £10. ASC11 keyboards £3 each. A. Pearson, Gilmoor, Wythes Lane, Fishtoft, Boston, Lincs. Tel: 0205 65309.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature..... Date.....

**Please read the RULES** then write your advertisement here—  
one word to each box. Add your name, address and/or phone no.  
**COUPON VALID FOR POSTING BEFORE 4 OCTOBER, 1985** (One month later for overseas readers.)

**SEND TO:** PE BAZAAR, PRACTICAL ELECTRONICS, WEST-OVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BE15 1JG.

BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid "date corner"**

# Introduction to MICRO SYSTEMS

MICHAEL TOOLEY BA    DAVID WHITFIELD MA MSc CEng MIEE    PART 1

THE MICROPROCESSOR began its life labelled by many as a solution in search of a problem. Since the early seventies, however, microprocessor systems have developed at a quite breathtaking pace. Indeed, hardly a day now passes without an announcement of some new way in which the microprocessor will revolutionise an aspect of our everyday lives. One consequence of this change is that there is now quite widespread awareness of the fact that microprocessors can do many things better, faster and/or cheaper than ever before. However, for most people a considerable mystery still surrounds the question: "What is a microprocessor and how does it work?"

*Introduction to Micro Systems* is a new PE series aimed at providing readers with a basic understanding of the concepts involved in using microprocessors. Examples of applications will be used wherever possible to make the series as relevant and meaningful as possible. The examples used will, as far as possible, be taken from the type of control applications encountered in everyday life.

At this point, we should explain that the term "micro" will be used in the series to mean microprocessor, not to be confused with a small/home computer based on a microprocessor (which we will think of as a microcomputer).

To cover the subject of micros in full detail would probably involve using all of the available pages in PE from now until some time in the next century. This is clearly not very realistic for an introductory series. Fortunately it is not necessary in order to give a basic appreciation of the fundamental concepts. Then, once the basics have been grasped, it should be possible to make use of the mind-boggling variety of books available on individual micros and micro techniques to answer detailed or specialist queries. This series is thus by way of an introduction to the subject of micros, and we will start by looking at a few of the basic concepts.

## BASIC CONCEPTS

There are a number of basic ideas and techniques which inevitably come up sooner or later in any discussion of micros. Two which are fundamental to this series are digital logic and binary number systems. Regular readers will know that the former topic has been dealt with at some length in two previous PE series: *Introduction to Digital Electronics* and *Sequential Logic Techniques*.

For the benefit of new readers of PE, however, we will also be giving suggestions for suitable background reading as the series progresses. Before we start, however, it seems appropriate to briefly review some of these basic terms and concepts from the viewpoint of their use in this series.

Micros and micro systems are designed around electronic circuit blocks which operate on signals which can be in one of two stable states. These binary states are usually represented by two different voltage levels, and the circuits which manipulate them are referred to as logic gates.

In this series we shall be using positive logic notation, where the level closest to 0 volts is referred to as a logic 0, and the level furthest from 0 volts (usually close to the +5 volt supply level) is referred to as a logic 1. These logic levels are often referred to as

simply 0 and 1, respectively. A typical range of voltage levels for these logic levels is shown in Fig. 1.

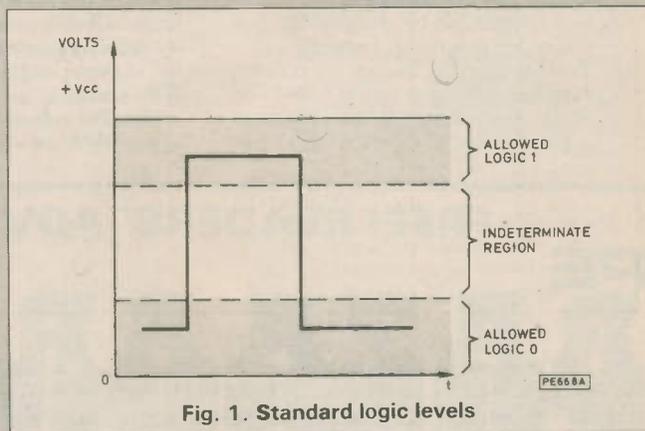


Fig. 1. Standard logic levels

Micro applications are frequently involved in counting or representing more than just two possible values or options, e.g. the temperature of a room may take a value from 0 to 30°C. It is clearly undesirable to have a different logic signal to represent each of the possible temperature values; in the example this would need 31 such signals.

Instead, the normal way of using the binary states of digital logic to represent a larger range of values involves the binary system of numbers. This provides a method of effectively coding a number of signals to represent a much larger number of combinations, and relies on the principle of binary numbers.

In the decimal number system, each digit can take one of ten different values (from 0 to 9). Each digit represents units of 1, 10, 100, 1000, etc, i.e. increasing in powers of 10. Thus, for example, the decimal number  $325 = (3 \times 100) + (2 \times 10) + (5 \times 1)$ . In the binary number system, however, each digit can only take the values of 0 and 1. Each binary digit is known as a *bit* (a contraction of *binary digit*), and the increasing bits in a binary number have values which go up in powers of 2. The decimal equivalent of the digits in a binary number are therefore, 1, 2, 4, 8, 16, 32, 64, etc. Thus, for example, the binary number 10101 has the decimal equivalent of:  $(1 \times 16) + (1 \times 4) + (1 \times 1) = 21$ .

Using the binary system, therefore, a small number of logic signals can be used to represent a large number of different values, and in our temperature example, 5 bits (one signal for each) are enough to represent the temperature range. In fact, 5 bits would be enough to allow us to represent a temperature range of 0 to 31°C.

## THE HEX SYSTEM

One problem with the binary system is that numbers can be cumbersome to write down, particularly for large values. Even worse, they are almost impossible to remember when they have a large number of bits; for example, 16 bits would be required for a decimal number of up to 65535. The *hexadecimal* system (i.e.

numbers in base 16), is therefore frequently used as a convenient and useful shorthand instead of binary.

A *hex digit* represents exactly four bits, and increasing hex digits count in units of 1, 16, 256, etc. To allow each digit to be expressed in only one character, the hex system uses the numeric characters 0 to 9 and A to F to represent the decimal values 0 to 15. The correspondence between decimal, binary and hex digits is shown in Table 1.

**Table 1: Digit values**

Decimal	Hexadecimal	Binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
10	A	1010
11	B	1011
12	C	1100
13	D	1101
14	E	1110
15	F	1111

As an example of the advantage of hex, the decimal number 61680 has a binary equivalent of 1111000011110000, whereas in hex the equivalent is F0F0. Binary numbers in micros usually have a number of bits which is a multiple of four, typically 8, 16, 32 or even 64; eight bits is usually known as a *byte*.

## LOGIC GATES

As has been mentioned, a logic gate is an electronic circuit whose input(s) and output(s) are all logic levels. The way in which the input and output signals are related depends on the logic function of the gate—a typical logic function (an AND gate) is shown in Fig. 2.

These gates are usually found in convenient groups in single *integrated circuits*, often referred to as “chips”. The number of logic functions which can be put inside a single chip has risen steadily as technology has advanced, and the micro represents one of the most complex examples of this trend. Modern micros have the equivalent of many thousands of individual gates inside a single chip.

Digital systems are concerned with the processing of logic signals, and one of the most important elements in a digital system is the memory cell. Each cell is usually in the form of a “flip-flop”, which is able to remember (or “store”) the value of a single logic level (i.e. 1 or 0), even after the original signal has disappeared. There are many different types of flip-flop, depending chiefly on the way in which the storage action is to be triggered. However, the same basic storage principle applies to them all. The internal circuit for a typical MOS technology memory cell is shown in Fig. 3.


Groups of 8, 16, or 32 memory cells are often found inside micros. They are usually arranged so that all the cells in the group are loaded or cleared in the same operation. These memory cell groups are usually referred to as registers. When used in a register, all of the memory cells are usually loaded and cleared at the same time. Hence registers are used a great deal within a micro for storing binary numbers.

## A CHOICE OF MICROS


Now that we have covered the basics for the series, it is time to start looking at some actual micro systems. As we have said, this is a series aimed at practical aspects of micros, and as such it is

important that the examples are based as far as possible on real micros. The problem otherwise is that it can be difficult to translate the theory into practice. However, this raises the inevitable question: “Which Micro?” to use in the series.

The difficulty with this question is that there is no single answer which will satisfy the needs and preferences of everyone. Inevitably, different micros are often used in similar applications. At the other extreme, in many cases we may need to add to an existing system, where the choice of micro has already been made. Instead of settling on a single micro for the whole series, therefore, we will instead be using a number as the series progresses.

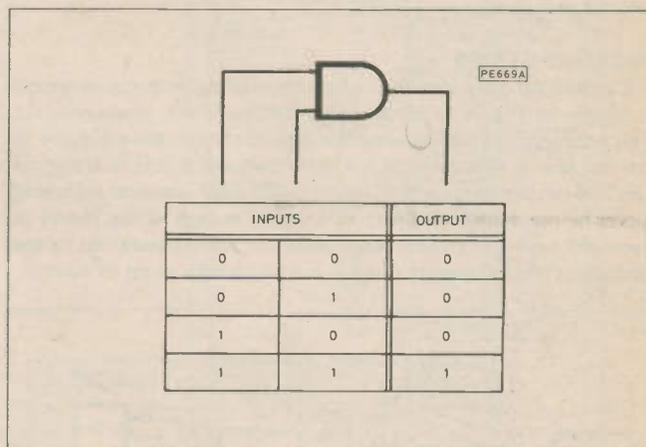

**Fig. 2. The AND gate symbol and its truth table**

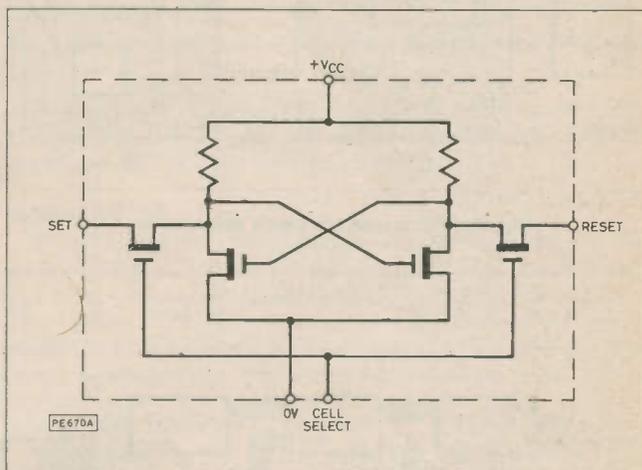

**Fig. 3. A CMOS memory cell**

We are starting with the Motorola 6800 micro, which although no longer quite in the “state-of-the-art” category, still has many points in its favour. Its clean and simple architecture is readily understood, and the micro is widely available with its range of support chips at low cost, e.g. the basic micro is now available for around £2 from a number of advertisers in *PE*. Once the principles have been grasped by studying the 6800, it is then a much easier step to move on to the later generations of micros. The other micros we shall be looking at will include the Z80, 6809 and 6502, all of which are used in popular home computers.

It is fashionable in certain circles to consider that 16-bit processors like the 68000 are *the* micros of today, and that nothing else is worthy of consideration. However, at around £30 for just the basic chip, these devices are still beyond the reach of the hobbyist;

even worse, they have often been the subject of early promises from imaginative manufacturers, who haven't even got samples available yet!

For around £10, on the other hand, it is possible to buy the chips off-the-shelf to build a complete 6800-based micro system. It is also true that many of the "simpler" micros are still better suited to the type of control applications found in everyday life than some of their more prestigious and sophisticated successors. It's not so much that the 16-bit machines wouldn't work in these applications, it's more a matter of their being a sledgehammer to crack a nut. After all, you would not consider using a Formula 1 racing engine to power a lawnmower. As the saying of the sage has it, a good designer is someone who can do for £10 what any fool can do for £100; a good point to bear in mind when reading of the attractions of the new wonder chips.

## MICRO SYSTEMS

The internal organisation of a basic general purpose micro system is shown in Fig. 4 as a simplified circuit block schematic. An alternative way of representing this type of system, shown in Fig. 5, can be used to illustrate the typical information flow in a control application; the micro effectively forms the information switching centre of the system. We will be looking at each of the blocks in these schematics in greater detail as the series progresses, but for the moment a brief summary of each will be enough to get us started.

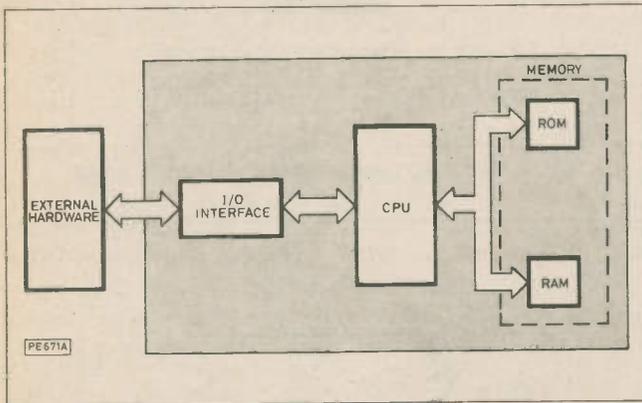


Fig. 4. Micro system block schematic

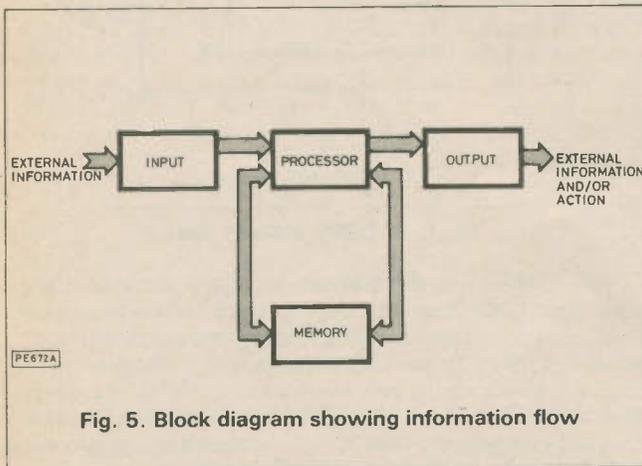


Fig. 5. Block diagram showing information flow

A micro-based system almost inevitably now consists of a number of interconnected integrated circuits. Fig. 4 shows these as including a central processing unit (CPU), memory for storing instructions and data, and some input/output (I/O) capability. These basic units are connected together by a series of buses which

carry binary number values and control signals. The actual width of each bus (i.e. the number of bits used to represent a value) depends on the chip family (group of related chips) used to build the system, but typical values are 8, 16, 24 or 32 bits. The control signals are used to coordinate and control the correct operation of the system, and usually include various timing signals.

The CPU is the heart of the system. Its role is to execute arithmetic and logical functions in accordance with the program of instructions stored in the memory. In passing, it is worth noting the use of the short form spelling "program" as the accepted practice in the micro field.

The memory is an array of one-bit memory cells, which are usually arranged in groups of eight bits (bytes). In some micro systems these groups can be 16 bits (words) or even 32 bits (double-words), but internally they usually remain organised as bytes. This organisation means that each byte can store values ranging from 00000000 (decimal 0, hex 00) up to 11111111 (decimal 255, hex FF). Each byte is accessed by means of its location (its address) in the array, although only one byte can be addressed at a time. This memory organisation is illustrated diagrammatically in Fig. 6.

Memory comes in two main types: read/write and read-only. The first type is known as random access memory (RAM), and is used to store, temporarily, data which is subject to change during the running of the program. In some systems, where more than one program may be loaded from an external store (e.g. programs loaded from a floppy disc into a microcomputer), the program is also stored in RAM. However, this is not common in control applications.

The second type of memory is read-only memory (ROM), which

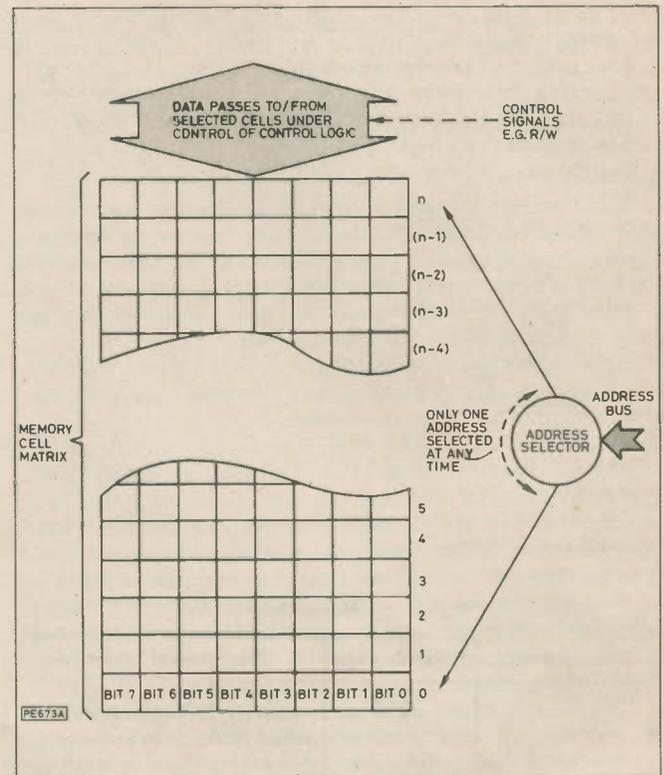


Fig. 6. Schematic diagram showing the organisation of semiconductor memory as a matrix of cells. Each address identifies a byte of data

is used to store fixed data and programs. The contents of the ROM must be "blown" during the development or manufacture of the system, and they cannot easily be changed thereafter. This permanent storage system means that the program is saved even when the power is switched off, and is immediately available at switch-on.

It must be stressed at this early stage that there is nothing physically stored in the memory which distinguishes program bytes from data bytes. It is only a matter of how the system is organised that determines how a byte is used, and it is not at all uncommon for the two to get confused during debugging; the results can be bewildering.

The system is here shown interfacing to external hardware, usually known as peripheral hardware. This hardware can take many forms, from the keyboard and display on the now-familiar home computer, to all sorts of control valves and switches, as might be found in a central heating system. The important point is that in a system of this type, the I/O forms the link between the micro and the real world. Without it, the micro would be confined to talking to itself. As you might guess, therefore, the range and ease of use of the I/O has a significant effect on the usefulness of any micro system.

Now that we have identified the major building blocks of a micro system, we can go on to look at each of them in a slightly more detailed way. Whenever we look at a new system, it is always a good idea to start by trying to identify the basic blocks just described. This then gives us a good start in the process of working out the system's basic structure. Once this structure has been established, it is then much easier to fill in the detail, already knowing how the major parts fit together.

### A BASIC MICRO SYSTEM

A more detailed version of the type of system outlined in Fig. 4 is shown in Fig. 7. This system is based on the Motorola 6800 family, and represents a basic system of the type that might be found in, say, a home security system. As we go on to look inside the individual system elements in detail, it is useful to compare this schematic with the earlier one. This will provide a useful background against which to consider the workings of the individual components; the problem otherwise is that you can end up looking at the details of all of the parts of the system before you get any idea of how it works at all.

The sequence we are going to follow is typical of the order in which one might analyse a newly encountered system in order to work out how it is organised.

### THE CHIP SET

The first step in analysing any micro system is a simple one, and it is to identify the micro family being used. This is usually found by looking at the larger chips' part numbers. Ignoring an alphabetic prefix (which is the manufacturer's identity code), the first two digits, and the number of digits in the part code usually give the best idea of the micro family, e.g. 68xx chips are from the 6800 family, 99xx are from the 9900 series. Once this is known, the appropriate manufacturer's data sheets can be consulted for further details. Table 2 gives examples of CPUs and typical peripheral chips from popular micro families.

Table 2: Micro Chip Sets

Manufacturer	CPU Device	Peripheral Devices
Motorola	6800	6821 (PIA), 6850 (ACIA)
Zilog	Z80	Z80-P10, Z80-SIO, Z80-CTC
MOS Tech	6502	(6522 (VIA), 6551 (ACIA)
Intel	8080	8253 (PIT), 8251 (USART)
Motorola	6809	Same as 6800
Intel	8085	Same as 8080
TI	9900	9901 (PPIO), 9902 (ACC)

As mentioned, the system in Fig. 7 is built around chips from the 6800 micro family. The CPU is the 6800 itself, and in the following discussion this should be viewed as the heart of the system. The memory shown is in two parts, one part is RAM (the 6810) and the other is ROM (the 6830). The I/O interfaces are provided by the

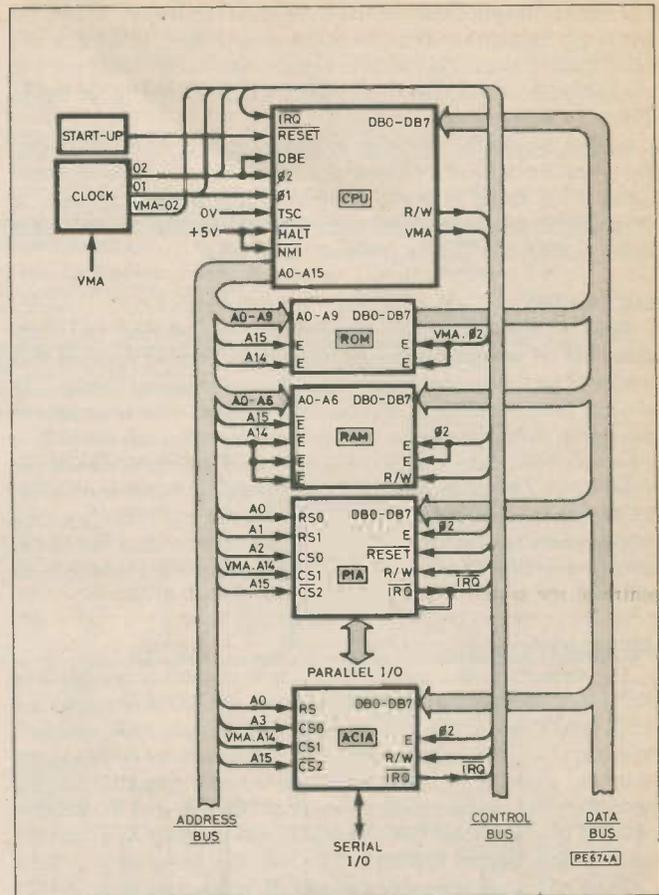


Fig. 7. System configuration for a system based on the 6800 CPU

6821 Peripheral Interface Adapter and the 6850 Asynchronous Communication Interface Adapter. The remaining elements of the system are the clock and the start-up circuits.

### ADDRESSING

The CPU addresses the system devices (ROM, RAM, PIA and ACIA) via the address bus. The bus used by the 6800 is 16 bits wide, and is thus capable of addressing 65536 unique memory locations (hex: 0000 to FFFF). The individual lines are labelled from the least significant (A0) up to the most significant (A15) to indicate their binary significance, i.e.  $2^0$  to  $2^{15}$ , respectively. Thus, for an address of F000, address lines A0-A11 are all set to logic 0, while lines A12-A15 are all at logic 1.

The address bus is a unidirectional bus which carries a 16-bit address value generated by the CPU to the remainder of the system. The devices on the bus are arranged so that only one responds to a particular address. To simplify the problem of a device recognising when it is being addressed by the CPU, individual devices are usually allocated blocks of consecutive addresses.

During the design or analysis of a micro system it is usual to draw out the allocation of addresses on what is usually called an address map. These maps show the whole addressing range of the micro, with address 0000 at the bottom and FFFF at the top for a micro with a 16-bit address bus. Blocks of addresses are then marked in to show how they are used, making it easy to identify any gaps or overlaps. Fig. 8, for example, is the address map for the system in Fig. 7. Although a very simple idea, an address map is an extremely useful tool in micro system design.

In smaller systems, the allocation of addresses to system units is usually arranged so that it is easy to detect which device is being addressed. For example, if addresses from 8000 (hex) upwards are

allocated to the program memory, the most significant address bit (A15) can be used to select the ROM area, without looking at any other address lines. This helps to explain why not all of the parts of the system are connected to the whole width of the address bus in Fig. 7.

Indeed, by careful allocation of addresses, it is possible to avoid the need for special (address decoding) logic circuits in small systems. In larger systems, however, address decoding logic is invariably required because there are not enough address lines spare to allow this simple approach to be used.

### DATA BUS

Once the CPU has addressed one of the system devices via the address bus, it needs a means of transferring data to or from that device. This is provided by means of the bidirectional *data bus*. In general, it is the width of this data bus which is used to categorise micros. In 6800 systems the data bus is 8 bits wide, and the 6800 is therefore referred to as an 8-bit micro; other examples include the 8080, 8085, Z80, 6809, and the 6502. The Z8000, 8086, and 68000, on the other hand, are examples of 16-bit micros. There is even a micro which has only a 1-bit data bus. The 8-bit data bus in the 6800 system thus allows one byte to be transferred at a time to/from the CPU.

### MEMORY

The memory in this simple system is composed of one block of ROM and one block of RAM. Looking at the ROM first, this is a 6830 device, which has a capacity of 8192 memory cells, arranged as an array of 1024 bytes. In addition to the memory elements, the chip also includes a number of enable inputs to simplify address decoding. The configuration shown is arranged so that the ROM is mapped into addresses C000 to C3FF; address lines A14 and A15 are used to select the ROM.

The RAM block is provided by a 6810, which is an array of 1024 memory cells arranged as 128 bytes. The on-chip decoding is a little different from that in the ROM, but the result is the same. The RAM is mapped into addresses 0000 to 007F.

### INPUT/OUTPUT DEVICES

The I/O devices in the system are connected directly to both the address bus and the data bus, and operate under program control. Each of them is controlled by a series of internal registers which appear as memory locations as far as the CPU is concerned.

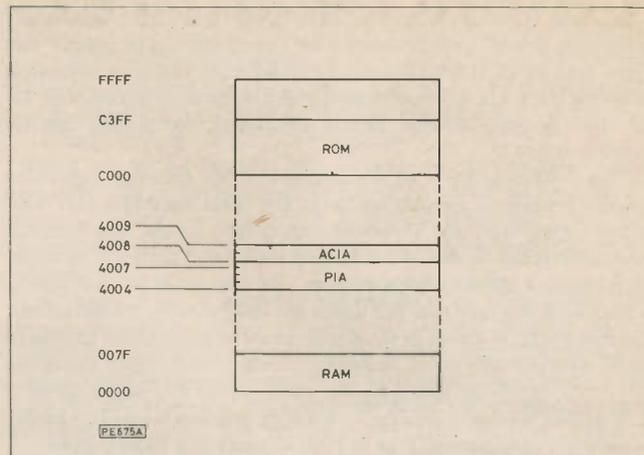


Fig. 8. Address map for 64k memory space

The various registers allow data to be transferred and control to be exercised over the interface. The six registers in the 6821 share addresses 4004-4007, while the four registers of the 6850 share addresses 4008-4009.

The 6821 Peripheral Interface Adapter (PIA) provides the system with a parallel connection to the outside world. The 6821 is a programmable device which gives the user the ability to set it up from a program to suit the particular application. This allows the 16 I/O lines to be used in whatever manner is appropriate to the application, e.g. one can be used for turning on a lamp (i.e. an output), while another may be used for detecting the tripping of a switch (i.e. an input). In addition, there are four control lines provided to allow the micro and the outside world to be synchronised.

The 6850 Asynchronous Communications Interface Adapter (ACIA) is the serial I/O equivalent of the 6821. This allows data to be converted from parallel form (as held in the memory and transferred on the data bus) into serial form as required in such applications as modems.

### CONTROL SIGNALS

The final set of signals which pass around the system are for timing and control purposes. For example, because the data bus is bidirectional, an address in the RAM area could either mean that there is data on the bus to be written to that location, or that the data already in the location should be put onto the data bus. One of the signals (R/W), therefore, indicates whether the current address and data values refer to a read or a write operation.


Other signals on the control bus (which is not a bus in the true sense of the word) include signals to provide timing, reset the system, etc. It is also worth noting that in some cases, control signals may originate from outside the system shown in Fig. 7—for example, interrupt requests and I/O "handshake" signals. However, we will be looking much more closely at these control signals when we study the 6800 CPU in detail next month.

**NEXT MONTH:** Having established some of the basic principles of micro systems, we move on to look in detail at the workings of the 6800.



A home computer (above) is an example of a microprocessor system. The machine shown is based on a standard 8-bit micro

# ILP FROM JAYTEE

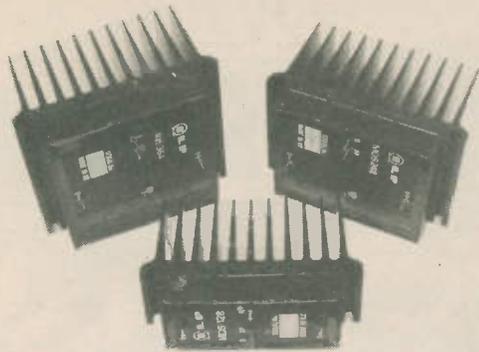

## THE SPECIAL DISTRIBUTOR FOR SPECIAL AMPLIFIERS

ILP have long been recognised as manufacturers of top quality amplifiers.

All ILP products are built to extremely high specification for the ultimate in hi-fi performance. They're unique in being completely encapsulated with integral heatsinks, and can bolt straight onto the chassis. They're also extremely robust, ensuring high levels of reliability as well as performance.

ILP Amplifiers are now available through Jaytee. The UK Distributor with the availability and service to match the quality of the amplifiers.

FOR FREE DATA PACK PLEASE WRITE TO OUR SALES DEPT.



### PREAMPLIFIER MODULES

All modules are supplied with in line connectors but require potentiometers, switches, etc. If used with our power amps they are powered from the appropriate Power Supply.

Type	Application	Functions	Price
HY6	Mono Pre-Amp	Full Hi Fi facilities.	£8.45
HY66	Stereo Pre-Amp	Full Hi Fi facilities.	£11.95
HY73	Guitar Pre-Amp	Two Guitars plus Microphone.	£12.45
HY78	Stereo Pre-Amp	As HY66 less tone controls.	£10.95
NEW! HY83 Guitar and Special Effects Pre-Amp as HY 73 Plus Overdrive and Reverb			£18.95

MOUNTING BOARDS: For base of construction we recommend the B6 for HY6 £0.95. B66 for HY66-78 £1.45.

### MOSFET MODULES

Ideal for Disco's, public address and applications with complex loads (line transformers etc.). Integral Heatsink slew rate 20V/μs distortion less than 0.01%

Type	Output Power Watts (rms)	Load Impedance Ω	Price
MOS128	60	4-8	£34.45
MOS248	120	4-8	£39.45
MOS364	180	4	£64.45

### BIPOLAR MODULES

Ideal for Hi Fi, Full load protection integral Heatsink, slew rate 15V/μs

Type	Output Power Watts (rms)	Load Impedance Ω	Price
HY30	15	4-8	£10.45
HY60	30	4-8	£10.45
HY6060	30+30	4-8	£21.95
HY124	60	4	£17.45
HY128	60	8	£17.45
HY244	120	4	£22.45
HY248	120	8	£22.45
HY364	180	4	£33.45
HY368	180	8	£34.95

Distortion less than 0.01%

### POWER SUPPLY UNIT

Type	For Use With	Price
PSU30	PRE-AMP	£6.45
PSU212	1 or 2 HY30	£16.45
PSU412	1 or 2 HY60, 1 HY6080, 1 HY124	£18.45
PSU422	1 HY128	£20.45
PSU432	1 MOS128	£21.45
PSU512	2 HY128, 1 HY244	£22.45
PSU522	2 HY124	£22.45
PSU532	2 MOS128	£22.95
PSU542	1 HY248	£22.95
PSU552	1 MOS248	£24.95
PSU572	2 HY244	£26.45
PSU722	2 HY248	£27.45
PSU732	1 HY364	£27.45
PSU742	1 HY368	£29.45
PSU752	2 MOS248, 1 MOS368	£29.45

All the above are for 240v operation.



Jaytee Electronic Services, 143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL Telephone: (0227) 375254

# TECHNICIAN ENGINEERS

## COMMUNICATIONS AND ELECTRONICS

A Planned Career in Technology in the Cotswolds  
Salaries up to £11,445

- **VACANCIES** at both **TECHNICIAN ENGINEER** and **ENGINEERING TECHNICIAN** level.
- **CHALLENGING WORK** in the development and support of highly sophisticated communications and computer systems.
- **OPPORTUNITIES** for gaining experience in a wide variety of technical roles.
- **EXTENSIVE ENGINEERING FACILITIES**

- **CAREER PLANNING** aided by regular assessments of performance.
- **ADVANCEMENT** opportunities on the basis of proven ability.
- **OVERSEAS** service (voluntary).
- **FLEXIBLE** working hours with up to six weeks leave.
- **RELOCATION EXPENSES** in most cases.

Applicants for the higher grade of **TECHNICIAN ENGINEER** should normally possess a BTEC Higher National Certificate/Diploma in electronics or other relevant subject; or a City and Guilds Full Technological Certificate, or an equivalent qualification. An aggregate of at least 8 years relevant training and

experience is required. Registration as a Technician Engineer (T.Eng) would be an advantage. **Salary Scale: £9,113 – £11,445** Applicants with BTEC ONC or equivalent and at least 4 years relevant training and experience are eligible for posts at the **ENGINEERING TECHNICIAN** level for which a structured training programme is provided. **Salary Scale: £6,599 – £9,135**

**INTERESTED?** Then for either post send for full details and application form to the address below, quoting Ref: T/6523/85



THE RECRUITMENT OFFICE, GCHQ, ROOM A/1108  
OAKLEY, PRIORS ROAD, CHELTENHAM, GLOS GL52 5AJ  
OR TELEPHONE (0242) 32912/3

# Robotics Review *Nigel Clark*

A MIDDLESBROUGH GP won the first Robotat contest held as part of the European Personal Robotics Conference in London in July. Although the device of Dr John Marr failed in the aim of playing a game of robot table tennis it had potential according to the organiser, John Billingsley, and won Dr Marr a trip to San Francisco in September to take part in the U.S. finals of the competition.

.. resembled an anglepoise lamp which used a chip vision system ..

Known as Zillian, Dr Marr's device resembled an anglepoise lamp which used a chip vision system similar to the Snap system. The bat managed to make contact with the ball and made a hitting movement but was not able to control the direction the ball took after that. The bat also required some assistance in locating the ball by use of a joystick.

To help with his expenses in getting to the States, Dr Marr received £500, donated by Joe Bosworth, the founder of **RB Robot**.

In second place came John Knight and David Lowery of Fareham, Sussex, with Kung Fu, which combined a vision system of which Baird would have been proud and the combined power of a Dragon and Acorn Atom. Movement was provided by a spring, the bat being halted by a magnetic clutch.

Knight and Lowery represented Britain in the European finals in Brussels in August with the help of £100 from the Institute of Mechanical Engineers.

There were two other entries which lacked the precision of the others but contained the same amount of enthusiasm for the idea.

This was the first public showing of the devices, development of which began soon after the contest was announced by Billingsley at the beginning of last year. An earlier workshop was held to assess progress and swap ideas.

The competition has attracted a lot of interest from throughout the world but to date working devices are thin on the ground. Billingsley said that **ATT** in the States had been working on the idea but with the help of a Puma and Vax which he thought was overdoing it a little.

.. Robot was already ahead of the Micromouse ..

He added that the signs for the future were encouraging. Robotat was already ahead of the Micromouse contest, which he also organises, at the same stage.

His major problem is now finding a venue for future contests. Anyone organising an

exhibition in May or June next year, who would like to offer space for the Robotat and Micromouse contests should contact Billingsley at Portsmouth Polytechnic.

Four new robots arms were unveiled at the Education, Training and Development Exhibition held at the NEC in the summer.

The most unusual was the HS3 Tracer Robotic System from **LJ Electronics**. It is based on the concept of an XY plotter but instead of a pen it has a small gripper which moves up and down to pick and place.

At a cost of about £600 it comes with a p.c.b. assembler kit and, in case you should want to use it as a plotter, a pen carrier and three coloured pens are also supplied. It is described as a robotic table rather than an arm.

The drives for the X and Y axes are stepper motors while d.c. motors power the up and down movement and the gripper. The company says the table was developed to be used with a vision system. It was felt that a system suitable for a normal arm was unnecessarily complicated. Restrict the area of operation and the vision system, which will be supplied in the future, can be simpler.

Max-1 marks the entry of **Flight Electronics** into the robot market. At a price of £399 plus VAT it resembles a larger version of the Ogre with a similar robust construction.

Max-1 has three axes, waist, shoulder and elbow, plus a gripper all powered by d.c. motors with optical feedback. The drive transmission to the three axes is by metal worm gears with the gripper using a lead-screw.

With the arm fully extended Max-1 is said to be able to lift 4lbs. It is to go on sale in the autumn when more details will be available.

Another machine with an autumn launch is the latest in the ever increasing range from **Cybernetic Applications**. In keep-

ing with the names of its other products, this one is called Naiad, a water nymph, as it is hydraulically powered, using water.

.. cylinders are made of see-through acrylic ..


It has five axes plus a gripper with the axes powered by different kinds of hydraulic piston. The gripper is pneumatically-powered. All the cylinders are made of see-through acrylic so that students can see how they work.

Control is possible using all the normal micros, including C64, Apple, IBM PC and BBC B. It is also intended to have a model controller as do the rest of the company's arms. A price has yet to be fixed but it will be less than £1,000.

Finally, anyone with £8,250 plus VAT might be interested in the latest arm from **TecEquipment**, the MA3000. It does not have the sophistication of its smaller companion, the MA2000, but is larger and more rugged and is intended for colleges which would normally be looking at the Puma to do a similar job. It has a reach of 750mm, can lift 2kg with an accuracy of 3mm. Powered by d.c. motors, with potentiometers, it has nine speeds, five axes plus a pneumatic gripper and is controlled by a BBC B.


If you have an old ZX-81 gathering dust in a cupboard and you are wondering what to do with it there is a kit supplied by **Maplin Electronic Supplies** for £50 which will allow you to turn it into a simple line follower. The kit contains the electronics on three p.c.b.s, two d.c. motors and an infra-red sensor for line following.

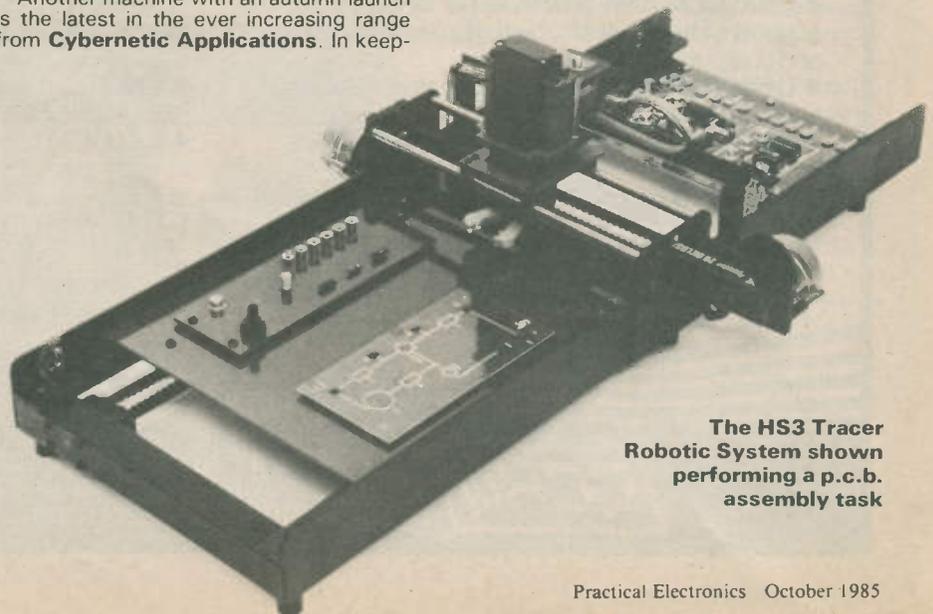Known as Trundle it was developed as a school project and was featured on 4 *Computer Buffs* on Channel Four.



The HS3 Tracer Robotic System shown performing a p.c.b. assembly task

all in your  
**NOVEMBER** issue!

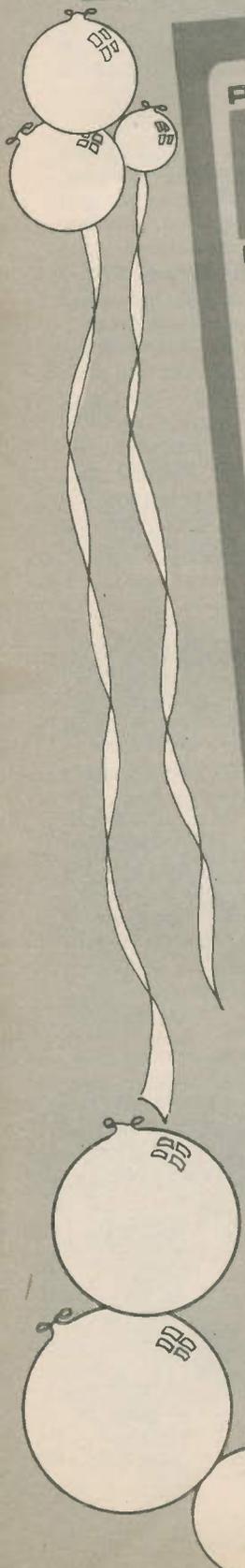

NOVEMBER 1985 £1.10

**PRACTICAL**  
**ELECTRONICS**  
ROBOTICS • MICROS • ELECTRONICS • INTERFACING

**WE'RE**  
**2**  
**TODAY!**

**8**  
**EXTRA**  
**PAGES**

- \* REVIEW... **21 YEARS of ELECTRONICS**
- \* **DISCO LIGHTS CONTROL**
- \* **commodore USER PORT EXPANDER**

Thanks to our READERS!

NOVEMBER ISSUE ON SALE, OCTOBER 4

**NEW**  
**SIZE**


# TOUCH controlled PSU

R.A.PENFOLD

THE idea for this power supply came about as a result of the author occasionally connecting a new circuit to the bench power supply, switching on, and then discovering that the output voltage was too high. It had been left at the 25V or thereabouts required for the previous session, whereas the new circuit required 5V or 9V. It is surprising just how many semiconductors can be in-

Using a very simple system this power supply provides zero volts at switch-on. The output voltage is controlled in a novel way, with a set of touch contacts being used to increase the output voltage and a second set being used to decrease it. A built-in meter indicates the output voltage so that the desired potential can easily be set. This may seem to be a rather gimmicky way of doing things, but it does in fact provide good results with low output noise and good regulation, and is a perfectly practical approach.

The supply has a maximum output current of 1A, and current limiting protects the unit against output short circuits and other overloads. The output voltage range is from 0V to 20V, but the full 1A output can only be supplied at output potentials of around 17V or less. This voltage range and current rating is adequate when developing and testing the majority of circuits, including such things as 5V logic circuits, 9V battery powered projects, and 12V car projects. Measured at an output potential of 10V, the regulation is better than 1% and the output noise is under one millivolt peak to peak at all output currents.

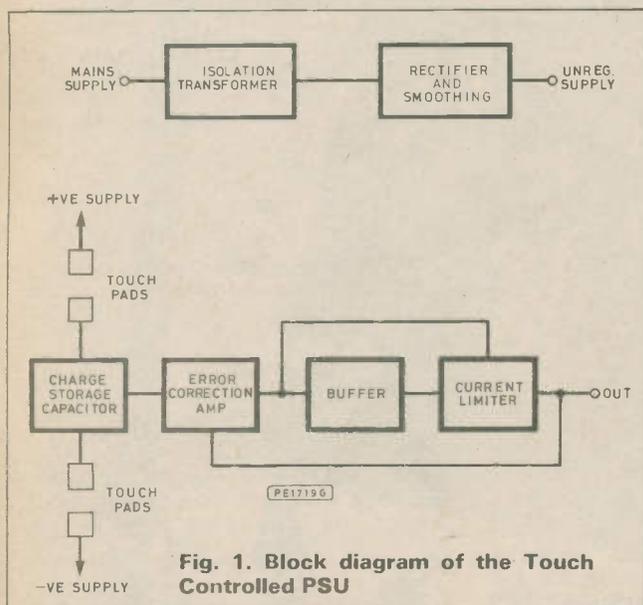


## SYSTEM OPERATION

The first requirement is to derive an unregulated d.c. supply from the mains supply. A regulator circuit fed from this supply is then used to reduce the output potential to the required figure and to provide accurate stabilisation. The unregulated voltage under full load must be a few volts more than the required maximum output voltage. The extra voltage is needed to compensate for losses through the regulator even at maximum output voltage. Also, there is likely to be a substantial amount of ripple on the unregulated supply, and the voltage at the bottom of the ripple waveform must be sufficient to maintain the maximum output voltage after the voltage drop through the regulator has been taken into account.

A transformer is used to step-down the mains voltage to a more suitable level, and the transformer also provides isolation from the dangerous mains supply. A rectifier provides full wave rectification of the transformer's a.c. output to produce a pulsating d.c. supply. This is reasonably smoothed by a high value capacitor. However,

stantly destroyed by this occurrence. What is needed to combat this problem is a supply that always starts at zero volts when it is switched on, with the user then having to set the required output potential before using the unit. With this system it is obviously impossible to damage components at switch-on due to an excessive output voltage.

**"Touch-Up" and "touch-down" control**

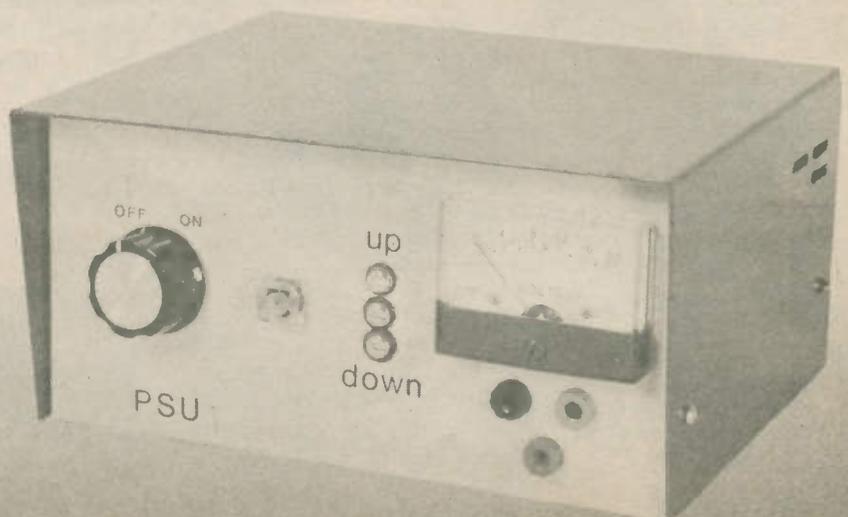


# TEST GEAR PROJECT

at high load currents the ripple content will still be at least a few hundred millivolts peak to peak, and the electronic smoothing provided by the regulator circuit is essential if a low noise level on the output is to be achieved.

In order to obtain a well regulated output voltage a highly stable reference voltage is needed. The basic action of the circuit is to stabilise the output at the same potential as the reference source,

transistor is switched on and pulls the output of the error amplifier lower in potential. This prevents any significant rise in the output current, and even with a short circuit on the output little more than one amp flows since the transistor is then switched on so hard that it pulls the output voltage down to practically zero. Note that the current limiter circuit is included within the negative feedback loop so that the feedback compensates for any small voltage variations

**Fig. 2. Complete circuit diagram of the Touch Controlled PSU**

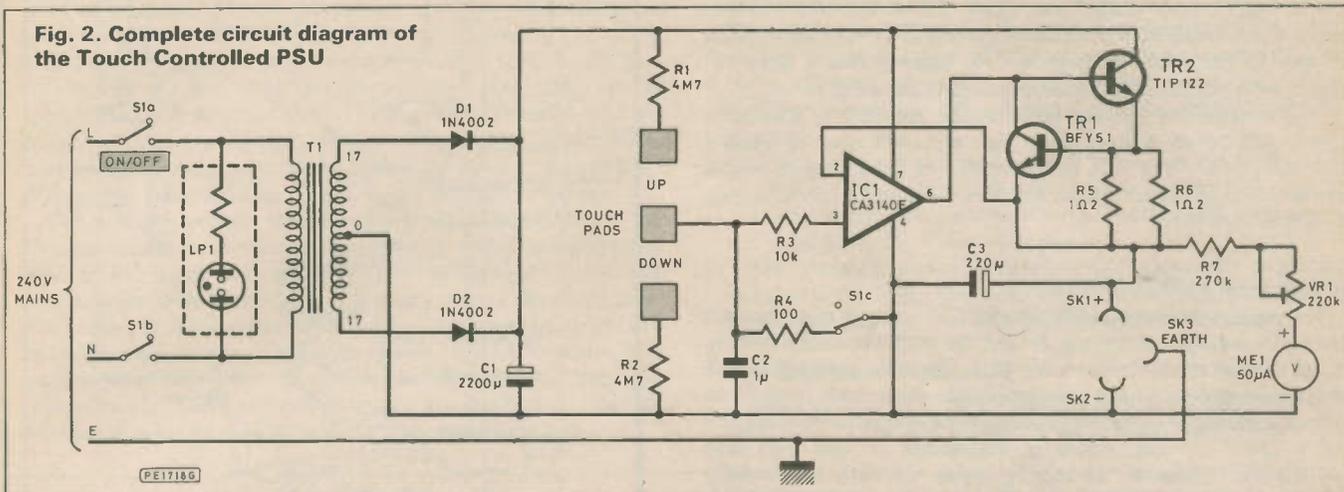

and we therefore require a reference voltage that is adjustable over a range of about 5V to 20V. In a conventional power supply unit this voltage is provided by a potentiometer fed from a simple Zener stabiliser circuit. In this case we are using a charge on a capacitor as the reference source. Operating one set of touch pads feeds a current into the capacitor from the positive supply rail and increases the charge voltage (and therefore the output voltage as well). Touching another set of contacts gradually discharges the capacitor into the negative supply rail, causing the charge potential and output voltage to fall.

## SWITCH-ON

At switch-on the charge on the capacitor is zero, and the initial output from the power supply is consequently zero volts as well. Although the circuit may seem to lack a voltage regulator, the voltage across the capacitor is in fact very stable, and is totally unaffected by noise on the unregulated supply, or any voltage variations on this supply caused by loading or fluctuations in the mains voltage. In the long term the charge on the capacitor will leak away, mainly due to slight imperfections in the capacitor itself, but provided a good quality component is used the charge voltage will not change significantly for an hour or more. This supply could not be recommended for applications that require a highly stable supply to be maintained for many hours at a time, but few amateur users will require this feature.

The reference voltage is fed to one input of an error correction amplifier. The output of this amplifier drives a buffer stage which enables high output currents to be accommodated. The other input of the error amplifier is fed from the output. The purpose of the amplifier is to compare the output voltage with the reference voltage, and make any correction necessary to balance the two signals. This is really just a simple negative feedback system.

It is important for any bench power supply to have protection against damage due to the inevitable short circuits and general overloads on the output. The most common form of overload protection, and the one incorporated in this design, is current limiting. The current limiting circuit at the output monitors the output current, and has no effect if the current is less than one amp. If the output current significantly exceeds this figure a

caused by this circuit during normal operation. Of course, when the current limiter comes into action it overrides the feedback action by "crowbaring" the output of the error correction amplifier.

## CIRCUIT OPERATION

The full circuit diagram of the Touch Controlled Power Supply is shown in Fig. 2.

T1 is the mains transformer and the mains supply connects to its primary winding via an on/off switch, S1. The output of T1 is rectified by D1 and D2 which make up a conventional push-pull type fullwave rectifier circuit. C1 is the smoothing capacitor.

C2 is the charge storage capacitor. In order to set the output voltage accurately it is necessary to have quite slow charge/discharge rates, but on the other hand the rates must not be so slow that it takes a long time to make large changes in the output voltage. R1 and R2 are used to limit the charge and discharge rates respectively to a suitable compromise, and it takes typically about seven seconds to take the output voltage from zero to 20V. The precise time taken depends on exact component values, and also on the skin resistance between the touch contacts (usually about 1 megohm or so). S1c is used to discharge C2 when the unit is switched off, thus ensuring that no residual charge remains when the unit is switched on again. R4 provides current limiting to protect S1c against sparking at the contacts and eventual failure.

## SPECIFICATION

Input.....	Mains 240V a.c.
Output voltage.....	0 to 20V regulated
Output current.....	1A max.
Regulation.....	1% at 10V
Noise.....	1mV pk-to-pk
Control.....	Touch plates
Indication.....	Neon, meter

IC1 is the error correction amplifier and this is just an operational amplifier used in the non-inverting mode. Protection resistor R3 couples the voltage on C2 to the non-inverting input of IC1. The output of the power supply connects direct to the inverting input of IC1 giving 100% negative feedback and the required overall unity voltage gain. IC1 is a type which has an output stage capable of providing output voltages almost right down to the negative supply potential. This is important as it enables IC1 to function properly without having to provide it with dual supply rails. IC1 also has a PMOS input stage, and again, this is important in this application. The PMOS input stage gives IC1 an input impedance of around 1.5 million megohms. This ensures that it does not significantly discharge C2 even over a long period of time.

TR2 is an emitter follower buffer stage. The TIP122 is in fact a power Darlington device which has a current gain of several thousand times. It is thus easily capable of producing an output current of up to one amp from the drive current of a few milliamps available from IC1.

### OVERLOAD PROTECTION

The parallel resistance of R5 and R6 (0.6 ohms) is in series with the positive output of the supply, and the output current therefore flows through these components. This generates a voltage across them, and this voltage is proportional to the output current. At output currents of up to 1A the voltage developed across R5 and R6 is 0.6V or less, which is inadequate to bias TR1 into conduction. However, at slightly higher currents this voltage becomes large enough to bias TR1 into conduction. TR1 then diverts some of the output current from IC1 to earth through the load, pulling its output voltage lower in the process. However hard TR1 conducts it is not possible for it to reduce the output voltage of IC1 to zero, and on the face of it a short circuit across the output could still cause a massive current to flow. In practice this cannot happen as there is a voltage drop of about 1V or so through TR2, and this enables TR1 to pull the output potential down to a level that prevents more than about 1.2A from flowing even with a short circuit on the output.

C3 provides final smoothing of the output and also aids good stability. R7, VR1, and ME1 form a simple voltmeter circuit which is used to monitor the output potential of the unit. VR1 is adjusted to give the meter a full scale value of 20V. A separate earth socket (SK3) is provided so that either output of the unit can be earthed, but neither output need be earthed. In practice it is advisable to earth one or other of the outputs unless a floating supply is essential. Apart from the improved safety this also helps to minimise breakthrough of radio frequency signals from the mains supply to the output.

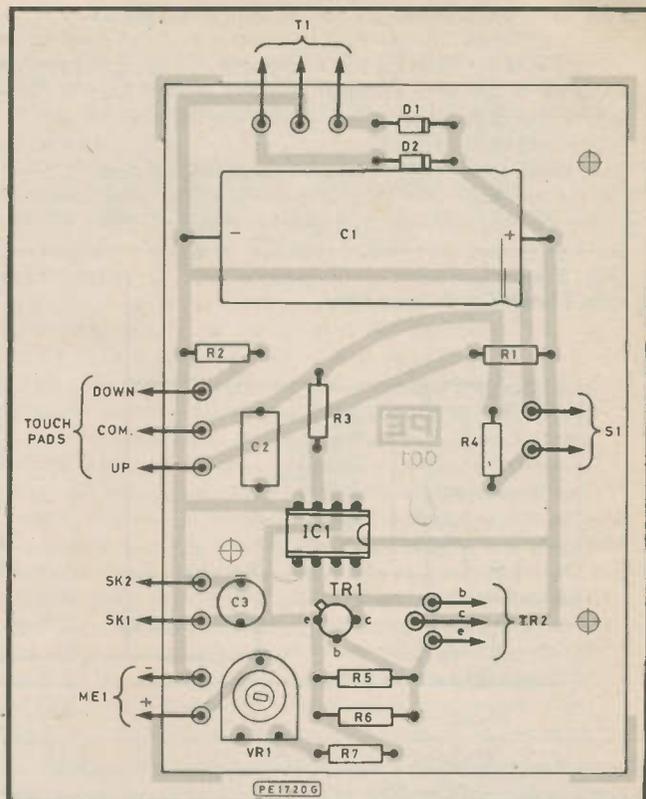


Fig. 3. Component layout and p.c.b. design

### CONSTRUCTION

Start construction by fitting the components to the p.c.b. following the component layout of Fig. 3. C2 must be a carbonate capacitor or some other high quality plastic foil type, and should not be an electrolytic or even a tantalum bead capacitor. Only a good quality plastic foil type will have a sufficiently low leakage level to give good results in this circuit. It must also be a miniature printed circuit mounting type if it is to fit onto the board without difficulty.

As IC1 has a MOS input stage it requires the usual MOS antistatic handling precautions. It should be fitted in an 8-pin d.i.l. integrated circuit holder, but it should be left in the protective packaging and should not be plugged into circuit until the unit is in all other respects finished. Fit pins to the board at the points where off-board connections will eventually be made.

## COMPONENTS . . .

### Resistors

R1, R2	4M7 (2 off)
R3	10k
R4	100
R5, R6	1Ω ½ W 5% (2 off)
R7	270k
VR1	220k sub-min horizontal preset
All ½ W carbon 5% unless noted	

### Capacitors

C1	2200μ 35V axial elect.
C2	1μ carbonate
C3	220μ 25V radial elect.


### Semiconductors

D1, D2	1N4002 (2 off)
TR1	TIP122 <i>npn</i> power Darlington

TR2	BFY51 silicon <i>npn</i>
IC1	CA3140E MOS op. amp

### Miscellaneous

ME1	50μA panel meter
SK1, 3	4mm sockets (3 off)
T1	Mains primary, 17-0-17V 2A secondary
LP1	Panel neon with integral series resistor
S1	4-way 3-pole with adjustable end stop
Metal instrument case about; 200 x 150 x 100mm; Printed circuit board PE PCB Service-100; Control knob; Touch contacts; Mains lead and plug; 8-pin	

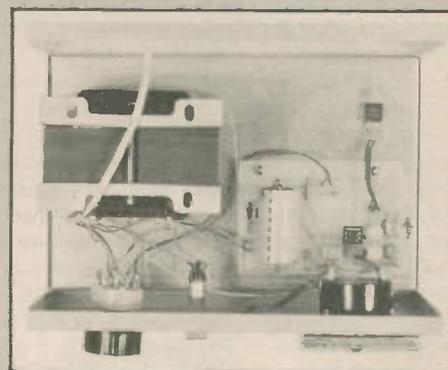

d.i.l. i.c. holder; Plastic power transistor insulating kit; Soldertag, grommets, wire, pins, etc.

A metal instrument case having approximate outside dimensions of 200 by 150 by 100 millimetres is about ideal for this project. It is not essential to use the specified type, but the case must be of all metal construction, and it must have sufficient internal height to accommodate the mains transformer.

The front panel and internal layouts of the prototype can be seen from the photographs and it is advisable to keep to these general arrangements. The mains transformer is mounted on the chassis or base panel, and a solder tag is fitted on one of the mounting bolts to provide a chassis connection point for the mains earth lead. The mains transformer fitted to the prototype is a type having twin 17V, 2A windings which are connected in series to act as a 17V-0-17V winding. The unit should work well using similar transformers, such as an 18V-0-18V type rated at about 1.6A, or a twin 20V component rated at 1A or more and suitably connected. Do not use a transformer having a rating of more than 20V as this could produce an excessive unloaded voltage.

TR2 and the printed circuit board are also mounted on the chassis or base panel. The printed circuit is mounted using three 6BA or M3 bolts, and spacers must be included to hold the connections on the underside of the board clear of the metal case. The chassis or case acts as a heatsink for TR2. As its heat-tab connects internally to the collector terminal it must be insulated from the chassis or base panel using the appropriate (plastic T066) type of insulating kit. Use a continuity tester or a multimeter set to a high resistance range to ensure that TR2 is properly insulated.

contacts from the case, and this can be achieved by mounting small grommets on the front panel and then mounting the contacts in these. An alternative would be to mount the contacts on a piece of plastic sheet, and then glue this in place on the front panel. Cutouts for the contacts would, of course, have to be made in the front panel. Whatever method is adopted, mount the contacts as close together as possible, otherwise they will be inefficient and difficult to use.

A hole for the mains lead is made in the rear panel of the case and this should be fitted with a grommet to protect the cable. S1 is a 4-way 3-pole rotary switch having an adjustable end stop, and the latter is set for 2-way operation.


The unit is completed by adding all the hard-wiring, and this is all detailed in Fig. 4. As the mains supply is involved, take great care when wiring up the unit, and thoroughly check for errors.

#### ADJUSTMENT AND USE

Start with VR1 at about half maximum resistance and then switch on. If the unit is functioning properly there should be no



Fig. 4. Wiring diagram of the Touch Controlled PSU

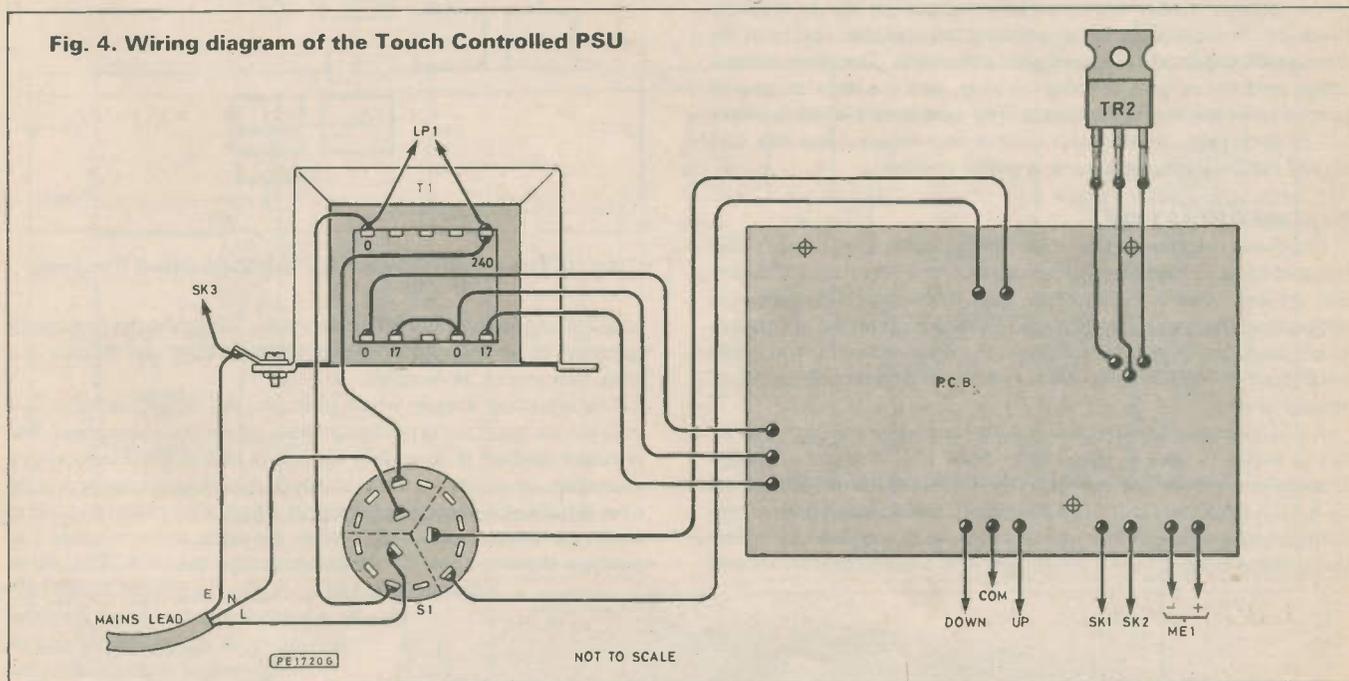

Mounting ME1 might prove a little difficult as most panel meters require a main mounting hole some 38 millimetres in diameter. Probably the easiest way of making this is to use a fretsaw, but if one of these is not available a simple alternative is to drill a ring of small, closely spaced, holes just within the border of the required cutout. A needle file can then be used to join up the holes, after which a large half-round file is used to tidy up and enlarge the cutout as necessary. The meter itself can be used as a sort of template when marking the positions of the four small mounting holes.

Either proper touch pads can be obtained, or M4 panelhead screws can be pressed into service. In either case soldertags must be fitted under the mounting nuts to enable connections to be made to the contacts. It is obviously essential to insulate the

significant deflection of the meter at this stage. By operating the "up" touch contacts it should be possible to build up the output voltage and obtain a strong deflection on ME1. By operating the "down" contacts it should be possible to take the output voltage back down to about zero again.

In order to calibrate the output voltmeter, a multimeter set to a suitable d.c. voltage range should be connected across the output of the unit and the output voltage is then set as accurately as possible at 20V. VR1 is then adjusted to give precisely full scale deflection on ME1. Ideally the scale plate of ME1 should be carefully removed so that the 0 to 50 scale can be replaced with a more convenient 0 to 20 one, using rub-on transfers. Meter movements are very delicate and great care must be taken if a new scale is fitted to ME1. ★

# Modulated Syndrum

R.A. Penfold

THE CLASSIC and much-used syndrum sound is a falling pitch effect, usually over a high- to middle-frequency range. Most syndrums are actually capable of producing a range of sounds, but the basic effect is the same with only the frequency range and duration being variable. This syndrum design takes things a step further and in addition to the standard syndrum effect a modulated falling pitch sound can be generated. In other words, instead of a straightforward fall in pitch the tone can be made to vary up and down, with an overall fall in pitch.

This enables some interesting sounds to be generated, and the unit is certainly much more versatile in this respect than an ordinary syndrum. Three modulation waveforms are available, and both the modulation depth and frequency are adjustable. The pitch, sweep range, and decay time are also variable, giving a large degree of control over the sound produced. The output amplitude is about 3V peak-to-peak from a low source impedance, and the unit should readily drive any power amplifier or mixer.

## SYSTEM OPERATION

The block diagram of Fig. 1 shows the general make-up of the unit and helps to explain the manner in which it functions. With any unit of this type it is of more than academic importance to understand the way it functions, as there are a number of controls to set up properly in order to obtain the desired sound, and it can be difficult to master this unless you have a reasonable idea of what's what.

A VCO (Voltage Controlled Oscillator) produces the basic signal, but in order to give a reasonable drum sound some envelope shaping is required. The output of the VCO is therefore processed by a VCA (Voltage Controlled Amplifier), which is fed with a high control voltage almost immediately the unit is triggered, and then this voltage decays over a period which is adjustable from around


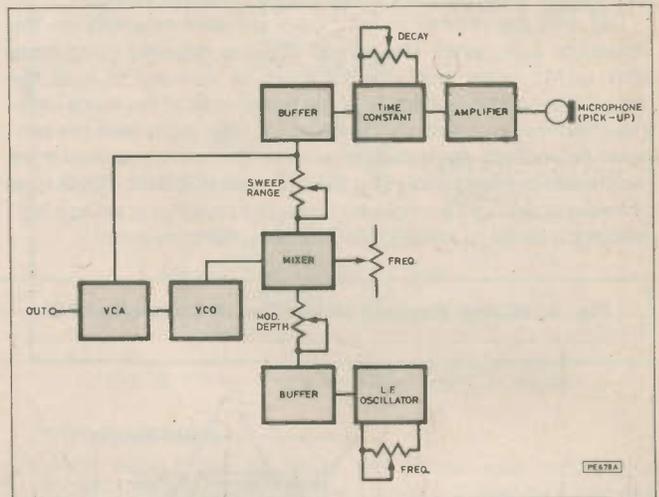


Fig. 1. The block diagram for the Modulated Syndrum

only 200ms or so to about four seconds. This gives the fast attack common to all drum sounds, plus either a short, dull sound, or a long, rich sound, as required.

The envelope shaper which provides the control voltage is a very simple type, but is perfectly adequate for this application. The principal method of triggering the unit is to strike the case with a drumstick, or to simply tap it by hand. A pick-up mounted on the case produces a short burst of signal which is amplified and fed to a time constant circuit. This rectifies the signal and smooths it to produce the d.c. control voltage needed by the VCA. The attack time is fixed and quite short while the decay time can be adjusted over the range specified previously. A buffer stage matches the high output impedance of the time constant circuit to the low input impedance at the control input of the VCA.

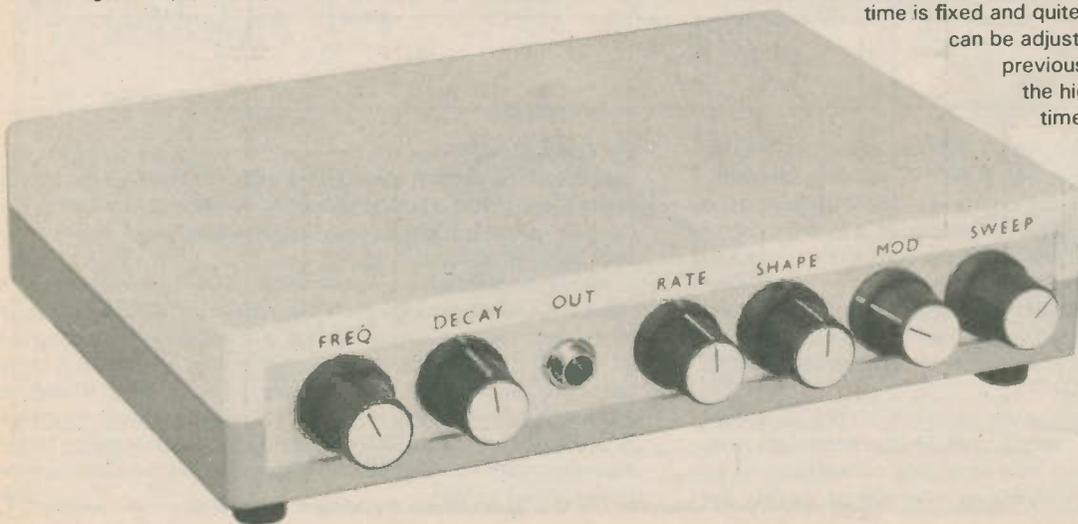

A falling control voltage is needed for the VCO in order to produce the falling pitch effect, and the obvious source for this voltage is the envelope generator. It is necessary to have control of the basic pitch of the VCO plus the sweep range so that the desired effects can be generated, and the output of the envelope shaper is therefore fed to the control input of the VCO by way of a level control and a mixer. The output level potentiometer acts as the sweep range control. Another input of the mixer is fed with an adjustable bias voltage, and it is this that sets the basic pitch of the VCO.

The modulation is applied merely by coupling the output of a low frequency oscillator into a third input of the mixer. A buffer amplifier is needed to match the high output impedance of the oscillator to the relatively low input impedance of the mixer, and a level control is included to enable the modulation depth to be adjusted.

Although the unit was designed primarily for manual triggering, a trigger input is included so that the unit can be controlled by a computer or other digital control circuit.

## CIRCUIT OPERATION

The full circuit diagram of the unit is shown in Fig. 2. The VCO is built around the two transconductance operational amplifiers of IC1, and the configuration is similar to a conventional dual

operational amplifier triangular/squarewave oscillator. IC1a acts as the Miller integrator and IC1b is the Schmitt Trigger.

The advantage of using a transconductance operational amplifier as the integrator is that it enables the operating frequency to be voltage-controlled by way of the amplifier bias input. In fact it is the bias current that determines the operating frequency, but the inclusion of R4 in series with this input gives a current flow that is roughly proportional to the applied voltage, and the oscillator is effectively a voltage controlled type.

Each transconductance amplifier of the LM13600N has a Darlington pair emitter-follower output stage, and discrete output buffers are consequently unnecessary: resistors R5 and R7 provide the output loads. The output from IC1a is a triangular wave and IC1b provides a squarewave output. In this application the triangular waveform with its much lower harmonic content seems to give by far the better sounds, and it is therefore this output signal that it utilized. A wide frequency range is available, and the full audio range can in fact be covered by the VCO.

The VCA is based on another transconductance amplifier, IC2. Only one section of IC2 is used, and the second amplifier and output buffer are just ignored. IC2 operates in the standard VCA configuration, but to avoid the need for dual supply rails, R1, R2 and C2 are used to provide a centre tap on the supply. This is also used to bias the VCO circuit. Although C2 may seem to have an un-


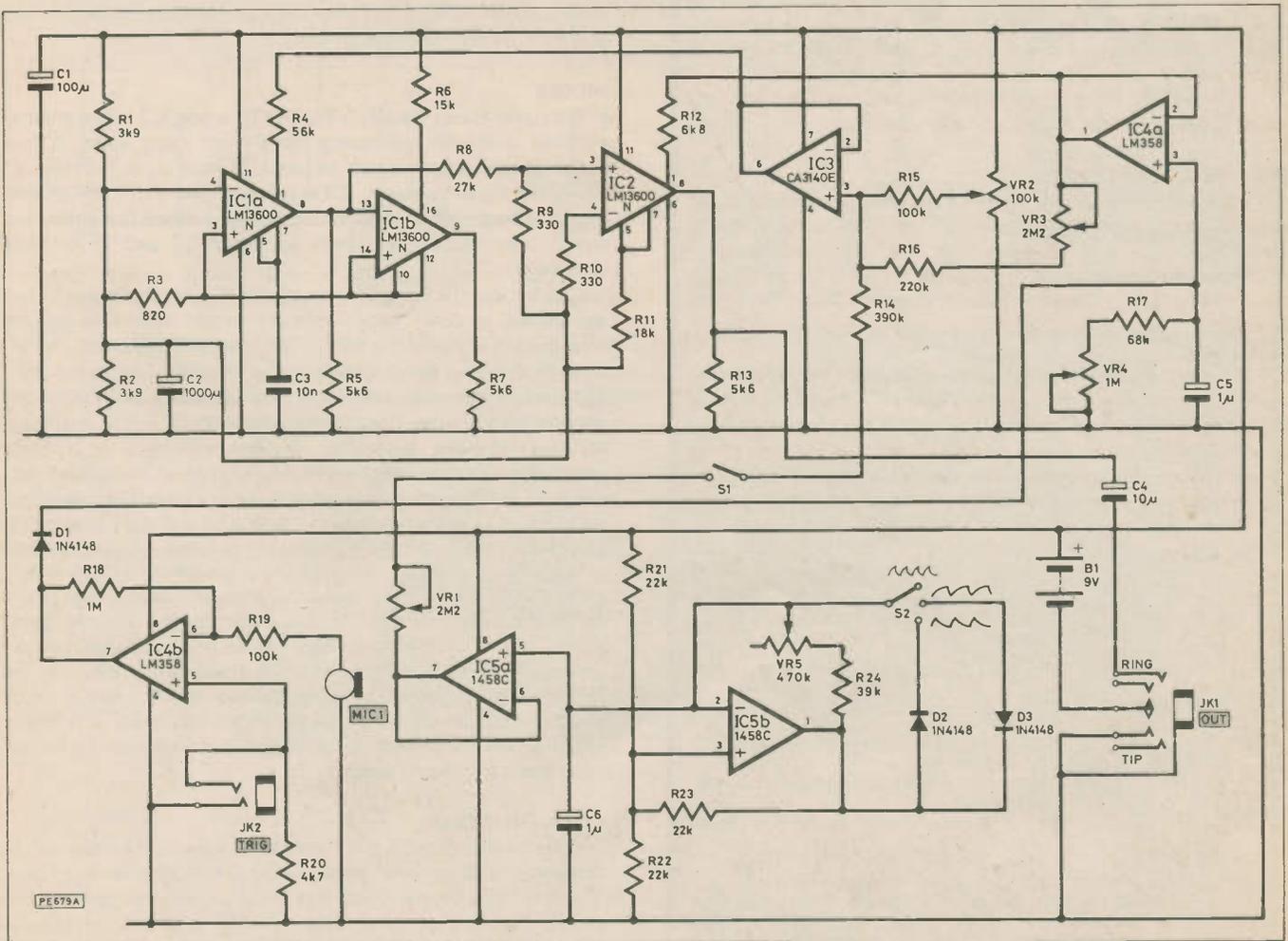


Fig. 2. The complete circuit diagram for the Modulated Syntrum

usually high value, this is in fact essential in order to prevent a significant breakthrough from the VCO to the output of the VCA when the latter is cut off. Again, the VCA is really current- rather than voltage-controlled, but series resistor R12 provides the conversion from current to voltage operation.

MIC1 is the pick-up which can be either a ceramic resonator or a crystal microphone insert. IC4b is an inverting amplifier with a voltage gain of 20dB which also ensures that MIC1 feeds into a reasonably high input impedance of 100k. The non-inverting input of IC4b is biased to the negative supply rail so that the output signal is half-wave rectified. This gives a series of positive output pulses which are fed to the time constant circuit.

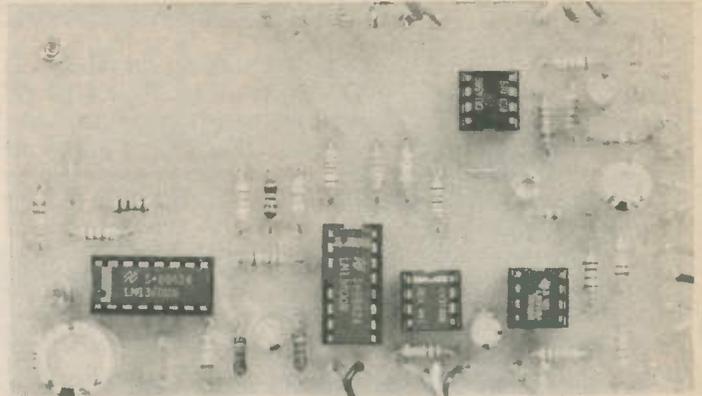If a trigger pulse is fed to JK1 then IC4b acts as a non-inverting amplifier and supplies a single, but longer, pulse to the time constant circuit. Its effect is much the same though. A pulse duration of anything from about 5ms to 50ms is suitable. Note that the LM358N device used for IC4 is a type which is capable of producing output voltages right down to the negative supply



The completed circuit board. Note the two link wires and the use of i.c. sockets

## COMPONENTS . . .

### Resistors

R1,R2	3k9 (2 off)
R3	820
R4	56k
R5,R7,R13	5k6 (3 off)
R8	27k
R9, R10	330 (2 off)
R11	18k
R12	6k8
R14	390k
R15,R19	100k (2 off)
R16	220k
R17	68k
R18	1M
R20	4k7
R21,R22,R23	22k (3 off)
R24	39k
All	¼ watt 5% carbon

### Potentiometers

VR1	2M2 linear with switch (S1)
VR2	100k linear
VR3	2M2 linear
VR4	1M linear
VR5	470k linear

### Capacitors

C1	100µ 10V radial elect.
C2	1000µ 10V radial elect.
C3	10n carbonate
C4	10µ 25V radial elect.
C5,C6	1µ 63V radial elect. (2 off)

### Semiconductors

D1,D2,D3	1N4148 (3 off)
IC1,IC2	LM13600N or LM13700N (2 off)
IC3	CA3140E
IC4	LM358N
IC5	1458C

### Miscellaneous

B1	9 volt PP3
JK1	standard jack with d.p.d.t. contacts
JK2	3.5mm jack socket
MIC1	Ceramic resonator or crystal mic. insert
S1	Part of VR1
S2	3-way 4-pole rotary (only one pole used)
S3	Part of JK1
Verocase about 205 x 140 x 40mm; printed circuit board, available from the PE PCB Service, order code PE-005; six small control knobs; battery connector; 16-pin d.i.l. i.c. holders (2 off); 8-pin d.i.l. i.c. holders (3 off); wire, fixings, solder. etc.	

potential, and that the circuit relies on this property for correct operation. Alternatives such as the 1458C are *not* suitable for the IC4 position.

C5 is the smoothing capacitor, and this rapidly charges from the low source impedance of IC4b when the unit is triggered. However, D1 prevents C5 from discharging through the output stage of IC4b, and the only discharge path is through the relatively high resistance of R17 and VR4. This gives the required fast attack and slow decay times, with the decay period being variable by means of VR4. IC4a is the buffer stage which ensures that the VCO and VCA do not significantly load C5.

### MIXER


The mixer circuit is really a passive type and IC3 is just a buffer amplifier. Although a summing mode mixer might seem to be a better choice it would not be suitable here as it provides an unwanted signal inversion. IC3 is another type which can provide output voltages right down to the negative supply potential, and again most alternatives (such as the 741C and LF351) are unsuitable.

IC5b acts as the low frequency oscillator, and this is a standard operational amplifier astable circuit. In this case it is not the squarewave signal at the output of IC5b that is required, but the roughly triangular signal across timing capacitor C6. This is not a high quality triangular waveform as C6 charges and discharges exponentially, rather than linearly, through R24 and frequency control VR5. The somewhat rounded waveform is perfectly satisfactory for the present application though. The signal across C6 is at a high impedance, but IC5a provides the necessary buffering. VR1 is the modulation depth control and S1 enables the modulation to be switched out altogether when it is not required.


The normal waveform across C6 can be changed by switching either D2 or D3 into the charge/discharge path. Switching D2 into circuit bypasses VR5 and R24 during the charge half-cycle, giving a very short charge time. This results in a sawtooth output waveform of the type having a fast attack and a ramp on the trailing edge. When D3 is switched into circuit it has a similar effect, but it is the discharge half-cycle that is affected. This gives a sawtooth waveform, but of the type having a ramp on the leading edge and a fast decay time.

### CONSTRUCTION


With the exception of the controls, sockets, and battery, all the components fit onto the printed circuit board, as shown in Fig. 3. The only MOS device is IC3 and the usual antistatic precautions should therefore be taken when dealing with this component. Some component retailers now supply the LM13700N instead of the LM13600N, and either type is suitable for IC1 and IC2 in this circuit.

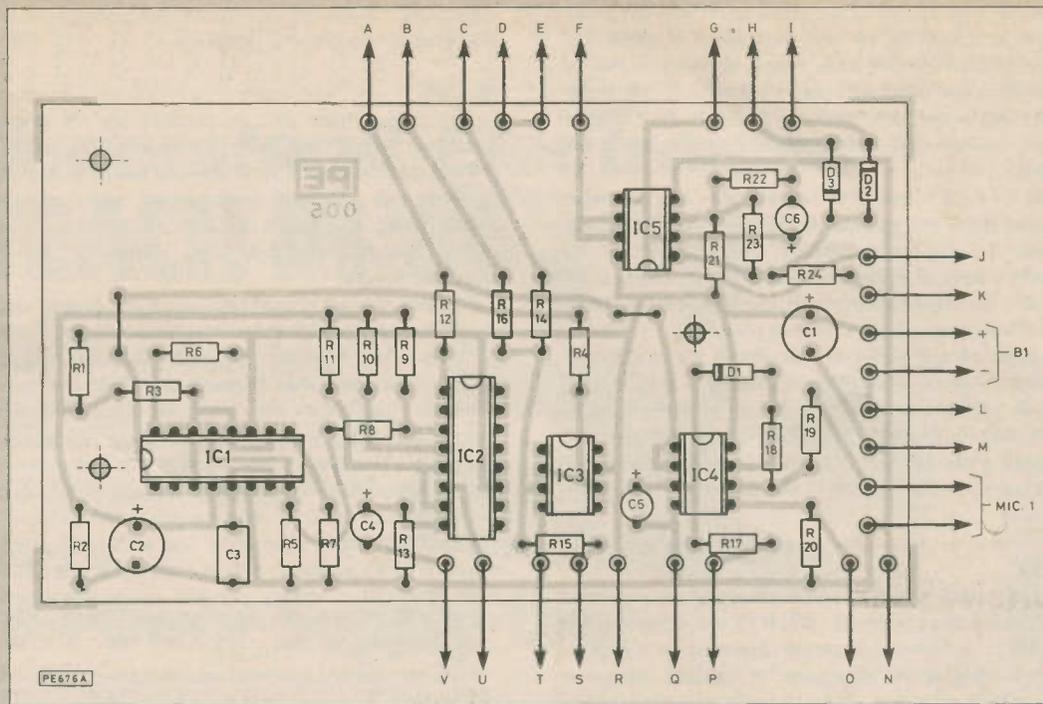

**Fig. 3. Component layout on the printed circuit board. This board is available from the PE PCB Service, order code PE-005**

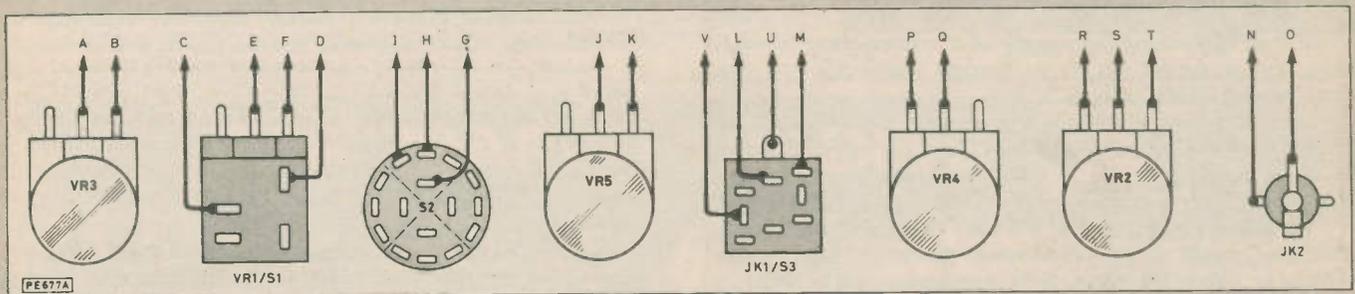

**Fig. 4. Positioning of the controls. The lettered leads from the controls should be terminated at the identical locations on the p.c.b. Note that JK2 is fixed to the rear panel**

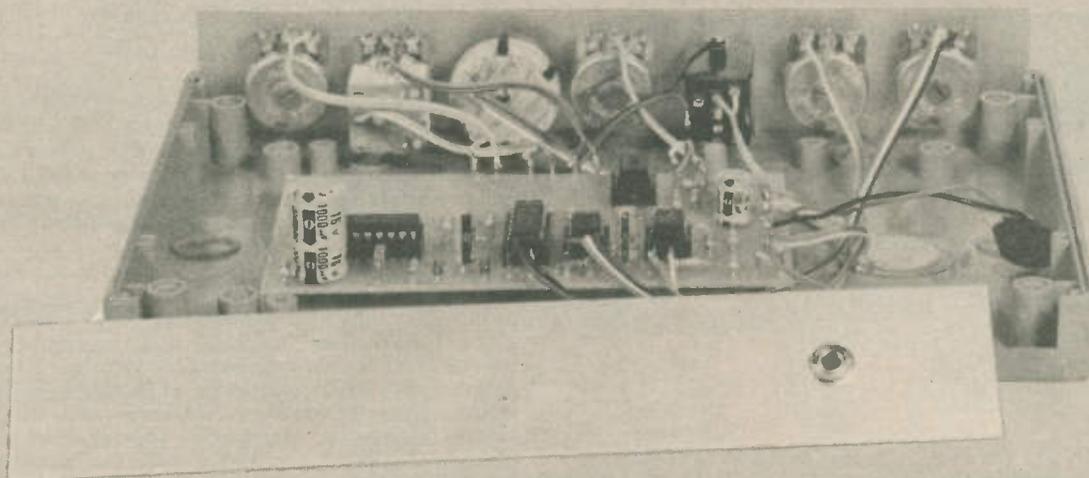

**The completed Modulated Syndrum with top panel removed showing interwiring and location of the p.c.b. The MIC insert is glued to the base of the case, right of the circuit board**

Do not overlook the two link wires, one near to R1 and the other just below IC5. It is advisable to use the types of capacitor specified in the components list, as other types, although perfectly suitable from the electrical point of view, might not fit onto the board properly. At this stage, only pins are fitted to the board at the points where connections to off-board components will eventually be made.

The case needs to be a reasonably tough type, and a plastic Verocase with metal front and rear panels is used as the housing for the prototype. This measures about 205 x 140 x 40 millimetres, and will readily accommodate all the components. All the controls plus JK1 are mounted on the front panel—JK2 is fitted on the rear panel. S1 is ganged with VR1, but obviously a separate switch could be used here if preferred. Similarly, S3 is a set of make contacts on JK1, which has d.p.d.t. contacts (a socket with s.p.s.t. contacts is unlikely to be obtainable), and the unit is automatically switched on and off as the plug is inserted into JK1 and removed. Again, a separate switch could be used here, but it might then be difficult to find space for all the controls on the front panel.

### CIRCUIT BOARD

The printed circuit board is mounted on the base panel of the case using M3 or 6BA fixings, with R5, R7, R13 etc. towards the front of the unit. MIC1, whether a ceramic resonator or a crystal microphone insert, is glued to the base panel of the case using any good quality household adhesive. Most inserts and resonators either have solder tags or flying leads, but one type of resonator does not. With this type leads must be carefully soldered direct to the inner (silver coloured) and the outer (copper coloured) contacts, and the component must obviously be mounted with this side facing upwards. Do not leave the soldering iron in place any longer than is absolutely necessary when making these connections, and be careful not to accidentally short-circuit the two contacts with excess solder.

To complete the unit the hard-wiring is added. This is illustrated in Fig. 4 in conjunction with Fig. 3 (e.g. point "A" in Fig. 3 is connected to point "A" in Fig. 4). Provided the leads to MIC1 are kept quite short it is not necessary to use screened cable here.

If the unit is to be triggered manually using a drumstick it is advisable to use some self-adhesive plastic or foam rubber material to protect the case over the area where it will be struck. It does not matter where on the case the unit is struck since the

vibrations will always be transmitted through the case to MIC1 so that proper triggering is obtained.

### IN USE


The output from JK1 is coupled to the amplifier, mixer, or whatever via an ordinary screened jack lead. As explained previously, the unit is automatically switched on when the plug is inserted into JK1, and switched off again when it is removed. When initially testing the unit it might be more convenient to plug a pair of headphones into JK1, preferably a medium or high impedance type.

Tapping the unit should produce some sort of output, and a little experimentation with the controls should soon reveal whether or not everything is working properly, and should give an idea of the range of sounds that is available. The unit should be touch-sensitive, with the sweep range and volume being to some extent dependent on how hard the unit is struck. Some picks-ups are more sensitive than others, and if the unit seems to be grossly oversensitive making R18 lower in value should cure the problem. A higher value for R18 will give increased sensitivity.

The trigger input is ideal for use with MOS and CMOS outputs which provide a logic 0 output voltage of virtually zero volts. TTL outputs could in theory provide a logic 0 potential that would prevent the VCA from fully cutting off, although this problem does not seem to occur in practice.

Note that when using the sawtooth modulation waveforms the modulation frequency will be about double that obtained when using the triangular waveform. Also, the two sawtooth waveforms will sound little different when the modulation frequency is fairly high, but the difference should be quite apparent at low frequencies.

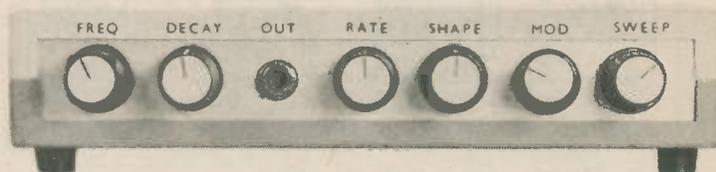A wide range of frequency, sweep range, and modulation is available, and it is well worthwhile spending some time familiarising yourself with the effects that can be obtained, and noting the control settings that give the best effects (there should be plenty of these). ★




# BOOK REVIEWS

### A PRACTICAL INTRODUCTION TO THE NEW LOGIC SYMBOLS

**Author** Ian Kampel  
**Price** £11.50 hardcover  
**Size** 223 x 142mm. 150 pages  
**Publisher** Butterworths  
**ISBN** 0 408 01461 X

Few engineers will welcome a title that threatens to impose yet another new standard upon them. However, the new logic symbols explained in Ian Kampel's work are already in use in some areas—notably VLSI design—and it seems likely that all the major technological countries will change to this new symbolism in the

near future. The standard for symbols on which the book is based is the International Electrotechnical Commission Publication 617; the relevant British Standard is BS3939 Section 21. As the author comments in his introduction, this new language exists, and "It is also a language which has a real incentive for people to learn it: *in due course their career may depend upon it!*"

The essence of the new logic symbols is the embodiment of a "systems", or top-down approach. A single symbol can be used to represent what previously would have been given as a complex circuit diagram; but that symbol itself may be further broken down into the equivalent of block-diagram form, or even into individual gates or i.c.s.

An instructional book on such a subject is obviously welcome, and *A Practical Introduction to the New Logic Symbols* clearly defines the terms used before going on to give examples. The approach reflects the "language" itself, progressing from simple definitions to increasingly complex symbols. In this way, each chapter builds on its predecessor, so that the book has to be read sequentially, rather than as a reference work. This requirement reflects the way the new symbols themselves work: it is not a question of a simple "new-for-old" swap, but the adoption of a new method of thinking—a new grammar. Every engineer, and engineering student, needs at least to be aware of this new standard, and this book meets that need more than adequately.

D.A.B.

# OCTOBER FEATURES...

## Understand Electronics TEACH IN '86

A new series in nine parts, designed to give a comprehensive background to modern electronics. The emphasis is on the *practical* rather than the theoretical. Many interesting exercises will be dealt with, giving the participant an excellent grounding in all aspects of our field, with the minimum of soldering. This course—with optional software—will be of interest to the complete newcomer as well as to those with some previous experience. A useful related project will also be featured every month (below).



**NEW  
SIZE**

### PROJECT 1

## Safe Power Supply Unit

This is a +9V/-9V d.c. unit designed for use with the *Teach-In '86* series (see above). It is the first of nine related projects, each relevant to that month's *Teach-In* notes. This unit is not essential for *Teach-In* participants (batteries can be used) but it will nevertheless always be a useful tool in its own right.

## Soldering Buyer's Guide

Soldering is a vastly underrated business in the world of the electronics enthusiast, and its true importance cannot be too highly stressed. It is in reality a simple task 'when you know how' and the combination of a good soldering iron and capable hands will minimise dry-joint problems and ensure a much higher rate of 'first time working projects'. This guide shows you how—it also features a wide range of currently available irons and equipment.

## EVERYDAY ELECTRONICS and computer PROJECTS

OCTOBER 1985 ISSUE ON SALE FRIDAY, SEPTEMBER 20

ORDER YOUR COPY NOW



## MARCO TRADING



### NI-CAD CHARGER

Universal charger to charge PP3, AA, C, D  
PRICE £6.00.

### NI-CADS

PP3	£4.45,	4/16.00
AA	£0.95,	10/8.00
HP11	£2.30,	4/8.50
C	£1.95,	4/8.75

### SOLDERING AIDS

Antex 15W iron	5.00
Antex 18W iron	5.00
Antex 25W iron	5.20
Antex Elements	2.00
Antex Bits	0.95
Antex stands	1.90
Desolder Tool	4.50
Spare nozzle	0.65
25W Kit-iron with 13A plug & stand	ONLY 7.20

### CLOCK RADIO - VHF/LW/MW

Mains, digital display alarm clock/radio. Alarm control/Wake to music. Sleep control - 10 min. Snooze. Hour/Minute Time Setting. Brightness Control. £3.50 each (plus additional postage 75p per set).

### SPECIAL OFFER

The complete set of three strip-fix plastic signs, containing over two thousand words. Transmitters, frequencies, dials, letters and symbols etc. Three for £3.75.

### SPEAKERS

4" Round 1.5W 4 Ohm	£1.50 pair
4" Round 1.5W 4 Ohm Plus Mounting Bracket	£1.00 each
2 1/4" Round 0.4W 8 Ohm	85p each

### HEADPHONES

Mono	£2.50
Super normal lightweight	
Miniature silver bands, sponge earcups	
Stereo	£2.50

### 74LS

LS00	28p
LS01	28p
LS02	28p
LS03	28p
LS03	32p
LS08	28p
LS09	28p
LS10	28p
LS11	28p
LS12	25p
LS13	33p
LS14	58p
LS15	25p
LS20	28p
LS2	28p
LS22	28p
LS30	30p
LS32	28p
LS37	23p
LS74	38p
LS122	70p
LS138	45p
LS139	68p
LS151	75p
LS155	50p
LS157	45p
LS158	58p
LS160	60p
LS161	70p
LS162	72p
LS163	80p
LS166	1.95
LS170	1.75
LS244	1.00
LS245	2.00
LS257	73p
LS393	1.15

### MINIATURE DC MOTORS

High quality reversible. Ideal for model maker and electronic home brew enthusiast. (Order code 3-5-086).  
6-12 volt working voltage. Dia = 25mm x 38mm. Pulley dia 10mm. Price 75p each, 10 for £6.00, 100 for £48.00.  
(Order code 35-522).  
Fujiya DC motor. Working volts 9V. Body dia = 35mm x 42mm. Pulley dia 8mm to 3mm. Price 85p, 10 for £8.50, 100 for £53.00.

### TRANSISTORS

AC128	0.30	BF338	0.38
AC176	0.28	BFX26	0.28
AF239	0.68	BFX84	0.24
BC107	0.10	BFX85	0.26
BC108	0.10	BFX87	0.26
BC109	0.10	BFY50	0.21
A.B.C.	0.12	BFY52	0.21
BC147	0.09	BFY90	0.90
BC182	0.09	BSX20	0.34
BC182L	0.09	BU208	1.55
BC184	0.09	BU407	1.65
BC184L	0.09	MJ2955	0.90
BC212	0.09	OC45	0.58
BC212L	0.09	OC71	0.50
BCY70	0.15	OC72	0.52
BD131/2	0.34	TIP31A	0.44
BD133	0.56	TIP32A	0.42
BD135	0.32	TIP33C	0.86
BD136	0.36	TIP34A	0.72
BF115	0.32	TIP2955	0.60
BF184	0.32	TIP3055	0.60
BF185	0.32	TIS43	0.88
BF194	0.08	TIS58	0.40
BF195	0.10	2N3055	0.45
BF196	0.10	2SC1096	0.68
BF197	0.10	2SC1173Y	0.82
BF200	0.20	2SC1306	0.92
BF224	0.20	2SC1307	0.40
BF244	0.26	2SC1957	0.76
BF244A	0.28	2SC2028	0.73
BF244B	0.30	2SC2029	2.10
BF259	0.32	2SC2078	1.05
BF262	0.30	2SC2166	1.20
BF263	0.30	3SK88	0.65
BF337	0.30	40673	0.80

(Order code SPDC).

Fujiya motor. Complete with speed control board using UPC1447H. Working voltage 12V-0.9V. Body dia = 32mm x 38mm. Shaft dia 2mm. Price £2.50 each. 10 for £22.00, 100 for £175.

### MICS

Sanyo Dynamic Microphone. 1" meter cable. Plug on-off. Switch stand. Price £1.50.

### SWITCHES

Sub-Miniature Toggle SPST	60p	SPDT	63p	DPDT	66p
Miniature Toggle SPST	68p	SPST	65p	DPDT	72p
DPDT Centre off	85p				
Standard Toggle SPST On/Off Plate					48p
DPDT On/Off Plate					58p
Push-To-Make					20p
Push-To-Break					25p
Rotary Switch					
1 pole 12 way, 2 pole 6 way, 3 pole 4 way, 4 pole 3 way					50p

### DIODES

IN916	0.04	AA119	0.12
IN4001	0.05	AA129	0.18
IN4004	0.06	AA130	0.16
IN4005	0.06	BA100	0.24
IN4007	0.07	BY126	0.12
IN4148	0.05	BY127	0.10
IN4149	0.06	BY133	0.16
IN5400	0.12	BY184	0.40

### LED.s

3mm			
Red	10p	10/85p	
Green	13p	10/100p	
Yellow	13p	10/100p	
5mm			
Red	10p	10/85p	
Green	13p	10/100p	
Yellow	13p	10/100p	

### SERVICE AIDS

ALL SERVISOL PRODUCTS	
Switch Cleaner	0.58
Circuit Freezer	1.14
Foam Cleanser	0.58
Agro Klene	0.30
Silicone Grease (Tube)	1.84

### PLUGS SOCKETS

Metal Co-ax Plug	0.18
Plastic Co-ax Plug	0.14
Metal Line Socket	0.58
Single Junc	
Socket	0.30
Plastic Phone	0.15
F.M. Plugs	0.20
PL259 Plugs	0.30
Reducer	0.15
Low loss splitter 1 in. 2 out	1.00

### PLASTIC BOXES

3 x 2 x 1"	0.35
3 x 2 1/2 x 2"	0.65
4 x 3 x 1 1/2"	0.83
6 x 4 x 2 1/2"	1.15
8 1/2 x 5 x 3 1/4"	2.15

Colour Black, all boxes with lids and screws.

### RESISTOR KITS

1/4W Pack 10 each value E12 10R-1M	4.80
Total: 610 resistors	ONLY 4.80
1/4W Pack 5 each value E12 10R-1M	2.75
Total: 305 resistors	ONLY 2.75
1/2W Pack 10 each value E12 2R2-2M2	5.25
Total: 730 resistors	ONLY 5.25
1/2W Pack 5 each value E12 2R2-2M2	3.50
Total: 365 resistors	ONLY 3.50
50V Ceramic Kit 5 each value 125 Per Kit	£3.50
Zener Pack 50FF 400MV	£3.50

### PRE-SETS

Vert + Horiz 100R to 1M 10p, 100 for £6.50  
2 Watt

### CERAMIC CAPACITORS

All 50V. 1p to 10 nf 4p each, 100 for £2.75

### COPPER WIRE

Tinned + Enamelled Copper Wire. 2oz reels: 14 to 30 swg £1.00 per reel.

### ZENER DIODE

400 mW 3v to 75v: 8p each, 100 for £6.00. 1 watt 3v3 to 200v: 15p each, 100 for £12.50

### VOLTAGE REGULATORS

78L05/12/15	0.30
7525/12/15	0.55
7905/12/15	0.65
LM317K	3.50
IC SOCKETS	1.84

### FUSES

QB 20mm 100mA to 6.3A: 6p each, 100 for £3.50. Slow Blow 20mm 100mA to 200mA: 20p, 100 for £15.00. 20mA to 800mA: 12p, 100 for £7.50. 1A to 6.3A: 10p, 100 for £5.00.
---

### TELECOM EQUIP

8 pin 0.08 0.70/10	
14 pin 0.11 0.85/10	
22 pin 0.21 1.95/10	
28 pin 0.30 2.75/10	
40 pin 0.34 3.10/10	
BT Plug & 3M lead	1.25
BT MASTER SOCKET	2.85
BT Sec Kit	1.95
BT 4-core cable 1M 0.15	
100M 12.00	

### B.T. TELEPHONES

Viscount £32.00; Statesman £29.50; Slimtel £22.50; Viscount 12 £39.50. All telephones listed carry British Telecom 12 month guarantee.

**MARCO TRADING (DEPT PE10)**  
The Maltings  
High Street  
Wem, Shropshire SY4 5EN  
Tel: 0939 32763 Telex: 35565

ORDERING: All components are brand new and to full specification. Please add 50p postage/packing (unless otherwise specified) to all orders then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges, etc, most welcome. (Do not forget to send for our 1985 catalogue - only 65p per copy. All orders despatched by return of mail.  
NEW RETAIL 1,000 sq. ft. shop now open Mon-Fri 9.00-5.00, Sat 9.00-12.00



**NEW 1985 CATALOGUE**  
WILL BE AVAILABLE SEPTEMBER/OCTOBER  
Range of components greatly increased - over 125 pages fully illustrated. Price £1.00 per copy. (Free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelopes.



### SPACE STATION KOUROU

The European Space Agency's probe to Halley's Comet, *Giotto*, was launched successfully from Kourou, in French Guiana, on 2 July, and is now on its way to a rendezvous with the comet on 13 March next year. Kourou, now a major rocket base, has been developed strikingly during the past few years, and has become a major commercial competitor to Cape Canaveral; since it may be said that the Ariane rocket is now just as reliable as the Space Shuttle.

A new section at Kourou is almost ready,

and launchings are regular and—usually—smooth. From the coast close to the rocket base it is possible to see some of the islands in the group which includes the notorious penal colony of Devil's Island, closed as recently as 1945. Some of the ex-convicts settled in the area after their release, and it is said that one of them now runs a profitable restaurant in the town!

Elsewhere in South America, at the Cerro Tololo Observatory in Chile, a group of astronomers using the 158-inch reflector there believe that they have been able to give an accurate age-estimate for the globular cluster 47 Tucanæ, a huge, symmetrical star-system containing many tens of thousands of suns. Globular clusters lie in the galactic halo, and most of them are a long way away. Only three are clearly visible to the naked eye—Omega Centauri and 47 Tucanæ in the far south of the sky (never rising above the British horizon) and Messier 13 in the northern constellation of Hercules.

Through a telescope 47 Tucanæ is a superb sight. It is in fact more impressive than the larger and brighter Omega Centauri—because Omega Centauri fills the field of view, whereas 47 Tucanæ does not, and its form can be clearly seen. The Cerro Tololo astronomers have studied the most

massive stars in the cluster, and have estimated their ages as being about 16,000 million years.

This is said to be more accurate than any previous values. It also raises some important problems, because the age of the universe itself—that is to say, the time which has elapsed since the so-called "big bang", when the universe in its present form came into existence—has been given variously as between 15,000 and 20,000 million years, with a decided preference for the lower value. If 47 Tucanæ really is 16,000 million years old, then our preferred estimates must be revised upward.

### GARNET STAR

A few bright naked-eye stars are strongly red. Betelgeux in Orion is one, Antares in the Scorpion another; Aldebaran and Arcturus are orange, and so on. Optical aid shows that many fainter stars are extremely red. But of all the naked-eye stars perhaps the most strongly coloured is Mu Cephei, in the far north. Sir William Herschel, discoverer of the planet Uranus, nicknamed it "the Garnet Star", and likened it to a glowing ember.

Cepheus is not a distinctive constellation; it adjoins Cassiopeia, with its celebrated W-formation, and is so near the celestial pole

## The Sky This Month

Bright planets are fairly well represented this month. Venus is brilliant in the eastern sky before dawn, and on 21 September it passes close to Regulus in Leo—a good opportunity for amateur photographers!

Jupiter is an evening object and, with a magnitude of  $-2.3$ , is far brighter than any other star or planet apart from Venus; but it is well south of the celestial equator, and by the end of the month it sets around midnight. Saturn is also an evening object in the south-west after sunset. The rings are wide open, so that the planet is a beautiful sight in even a modest telescope.

Mercury and Mars are close together in the early part of September; again in the morning sky, but they will not be particularly easy to make out. Mars incidentally, is three magnitudes fainter than Mercury.

The minimum separation between the two is 46 seconds of arc. It is surprisingly seldom that one planet occults another; the last occasion was on 3 January 1818, when Venus passed in front of Jupiter, and the next will not be until 22 November 2065, when the same thing will happen.

Halley's Comet is still faint, and perhaps the main interest this month will centre upon Comet Giacobini-Zinner, which will be by-passed by the American probe ICE (International Cometary Explorer). Giacobini-Zinner, with its period of 6.6 years, can sometimes reach the fringe of naked-eye visibility.

It will not do so this year, but as the magnitude will reach 8 or so it will be a reasonably conspicuous telescopic object. Positions for September will be as follows:

Sept.	R.A.	Dec.
2	5h 12min	+36°27'
12	5 55	22 32
22	6 27	8 58

At the end of the month the comet will cross the celestial equator, and by December the declination will be  $-38^\circ$ , so that British observers will lose sight of it; the magnitude will have faded to about 11. Photographers would be well advised to practise upon Giacobini-Zinner in preparation for Halley.

During September evenings the "Summer Triangle" of Vega, Deneb and Altair is still very much in evidence, with Ursa Major at its lowest in the north and the W of Cassiopeia not far from the zenith.

Pegasus, the Flying Horse, dominates the southern aspect, with its four main stars making up the famous "Square". It is difficult to understand why Alpheratz, one of the four, has been transferred to the neighbouring constellation of Andromeda.

Andromeda is, of course, celebrated because of the presence of Messier 31, the nearest of the large spiral systems at a distance of 2.2 million light-years. It too can be used as a convenient "photographic rehearsal" for Halley's Comet.

Low in the south, look for Fomalhaut in Piscis Australis (the Southern Fish) which is of the first magnitude and is one of our nearer stellar neighbours; it was also found by IRAS to be associated with an infra-red excess indicating cool, possibly planet-forming material. In the east the Pleiades have come into view, soon to be followed by the orange-red Aldebaran, the so-called "Eye of the Bull". By the early hours of the morning Orion has come back into view, led by the red supergiant Betelgeux and the glittering white Rigel, at least 60,000 times more luminous than our Sun.

that it never sets over the British Isles. Mu Cephei lies not far from a triangle of fairly dim stars of which one is Delta Cephei, the prototype short-period variable.

Mu is itself variable; the magnitude range is from about 3.6 to 5.5, so that the star is always visible with the naked eye, but it is far from conspicuous, and when it is near minimum the colour is hard to discern without binoculars or a telescope. Yet when any optical aid is used, Mu Cephei lives up to Herschel's nickname.

How far away is it, and how luminous is it? Clearly it is a red supergiant—a star which has used up its main store of hydrogen “fuel” and is approaching senility; but its distance has never been well determined. One estimate gave around 1500 light-years, in which case the star would have something like 50,000 times the luminosity of the Sun—as against a mere 15,000 Sun-power for Betelgeux.

### STELLAR HEAVYWEIGHT

New studies of it have now been carried out at the high-altitude Pic du Midi Observatory, in the French Pyrenees. Using the 2-metre reflector there, N. Mauron has examined Mu Cephei in the light of sodium, and has announced that the star is sur-

rounded by a vast envelope with an apparent diameter of as much as one minute of arc.

He also finds that Mu Cephei is much further away, and much more luminous, than has been previously believed. The power is now given as about 100,000 times that of the Sun, outclassing even such cosmic searchlights as Deneb and Canopus.

According to Mauron, the circumstellar “cloud” is shining because sodium atoms are scattering light in the outer part of a violent stellar “wind”. We have become used to talking about the solar wind—a stream of atomic particles being sent out by the Sun constantly in all directions and which, incidentally, has a marked effect upon some types of comet-tails, driving them outward; but we have heard less of the much stronger “winds” produced by very massive stars. And if the new data are correct, Mu Cephei is very massive indeed, and is the equal of 20 Suns. This is not a record, but it puts Mu Cephei very much into the class of stellar heavyweights.

Moreover, the star itself is huge. The diameter has been estimated as over 800,000,000 miles, which is comparable with the size of Jupiter's orbit round the Sun. Again this may not be a record but it dwarfs Betelgeux, whose diameter is no

more than 250,000,000 miles at most!

### DECEPTIVE APPEARANCES

In astronomy, as in so many other subjects, appearances can be very deceptive. Looking at Betelgeux and at Mu Cephei, it seems that Betelgeux is much the more impressive of the two; it is in fact one of the brightest stars in the sky. But in reality things are very different. If Mu Cephei were as close to us as Betelgeux, it would cast perceptible shadows, and if it were as near as Alpha Centauri at a mere 4.3 light years, it would appear almost as a second sun.

If you have a pair of binoculars, I suggest that you go out on the next clear night and locate Mu Cephei. You cannot fail to recognize it; its hue is so striking that there is no fear of mistake. It may seem like a tiny, glowing point, but we have to realize that it is one of the most remarkable stars we know.

What will happen to it eventually? It is squandering its reserves of energy; it will not last for nearly as long as the Sun before disaster overtakes it. It may collapse into a neutron star, or even produce a black hole. But this will not happen for tens of thousands of years at least, so that there is plenty of time for us to look at and admire the “Garnet Star”.


## MOSFET POWER AMPLIFIERS

**PAT 500**

(Mono Unit)

**PAT 500 illustrated 500w into 4 ohms, 280w into 8 ohms**

**£45.00 kit, £49.60 built**

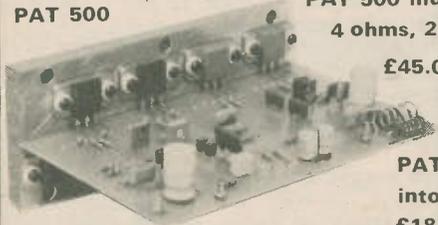

A range of 3 Mosfet Power amplifiers which incorporate the latest developments in Mosfet technology, using new techniques developed by CSL Sound Systems in the professional and Audiophile market these amplifiers outperform the standard Mosfet amplifiers in specification and musicality giving a smooth response throughout the audio range with dynamic low frequency performance often lacking in Mosfet amplifiers. All of the P.A.T. series use 160v Mosfets to give incredible headroom with exemplary distortion and noise levels.

**PAT120 120w into 8 ohms**  
**£18.50 kit, £21.00 built**

**PAT 200 200w into 8 ohms**  
**£28.00 kit, £30.50 built**

### AMP - 01 - M

STATE OF THE ART PRE-AMP,  
NOW AVAILABLE, AS DESCRIBED  
IN HI-FI NEWS MAGAZINE, S.A.E.  
FOR DETAILS.

P.S.U Capacitors 15000 uf 100vw computer grade £6.95  
10000uf 80vw industrial grade £4.80  
400v 35amp bridge rectifiers £2.95  
240v A.C. fan, 120mm, 90cfm £14.00  
24v D.C. fan, 120mm, 90cfm £22.00  
D.C. fan controller increases fan speed as temperature rises £8.50

Fan guards for above fans, block plastic £1.45  
Toroid 240v primary, 55-0-55sec, 160VA £11.50  
Toroid 240v primary, 55-0-55sec, 300VA £16.50  
Toroid 240v primary, 55-0-55sec, 625VA £26.50

### Accessories



Prices do not include V.A.T

allow 70p per order for P & P. C.W.O

allow 14 days delivery.

### AP100 Pre-amplifier

(Mono Unit)





**AP100 £9.80 kit, £11.45 built**

### Protection circuit

Protect your costly speakers from D.C. damage due to incorrect inputs or P.S.U. failures, this unit contains a heavy duty relay to disconnect the speakers if a D.C. condition appears at the amplifiers output.

**£7.50 kit, £8.30 built**

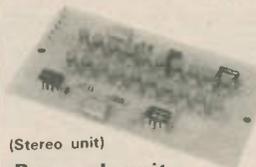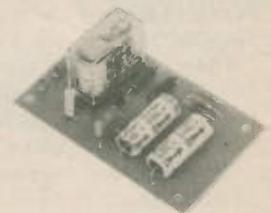

(Stereo unit)

**Bargraph unit**

A Stereo 2 x 10 LED unit, displays the output voltage of the PAT units in db's, green amber and one red LED give warning of clipping levels, each channel is adjustable to various loads and output powers. Note, this unit is fitted with flat top LEDs to allow a flush panel mounting.

**£12.95 kit, £15.10 built**

## C.S.L Sound Systems

Unit 27, Tything Road West

Arden Forest Ind. est.


Alcester, Warwickshire B49 6EP

Tel: (0789) 764710



# THREE ACES FROM ALCON!


## SUPER 20 A♣

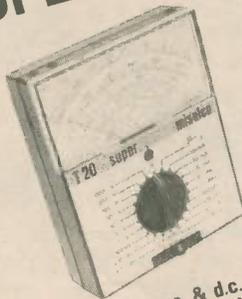

**20kΩ/V a.c. & d.c.**  
**39 RANGES - INDESTRUCTIBLE**  
 automatically protected on all ranges but 10A  
 Accuracy: d.c. ranges and Ω 2% a.c. 3% (of f.s.d.)  
 39 ranges: d.c. V 100mV, 1.0V, 3.0V, 10V, 30V, 100V, 300V,  
 1000V;  
 d.c. I 50μA, 100μA, 300μA, 1.0mA, 3mA, 10mA, 30mA,  
 100mA, 1A, 10A  
 a.c. V 10, 30V, 100V, 300V, 1000V; a.c. I 3mA, 10mA, 30mA,  
 100mA, 1.0A, 10A  
 Ω 0-5.0kΩ, 0-50kΩ, 0-500kΩ, 5MΩ, 50MΩ.  
 dB from -10 to +61 in 5 ranges.  
 Dimensions: 105 x 130 x 40mm.

**ONLY £33.50**

## MINI 20 A♥

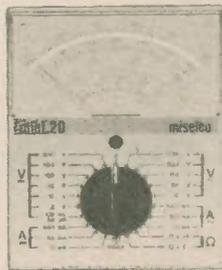

**20kΩ/V d.c. & 4kΩ/V a.c.**  
**28 RANGES WITH PROTECTIVE FUSE**  
 Accuracy: 2% d.c. and resistance, 3% a.c.  
 28 ranges: d.c. V 100mV, 3V, 10V, 30V, 100V, 300V,  
 600V. d.c. I 50μA, 600μA, 6mA, 60mA, 600mA,  
 a.c. V 15V, 50V, 150V, 500V, 1500V; a.c. I 30mA,  
 300mA, 3.0A. Ohms 0-2kΩ, 0-2MΩ.  
 dB from -10 to +62 in 6 ranges.  
 Dimensions: 105 x 130 x 40mm.

**ONLY £21.60**

## SUPER 50 A♠



**50kΩ/V a.c. & d.c.**  
**39 RANGES**  
 Accuracy: d.c. ranges and Ω 2% a.c. 3% (of f.s.d.)  
 39 ranges: d.c. V 150mV, 1.0V, 3.0V, 10V, 30V, 100V,  
 300V, 1000V. d.c. I 20μA, 100μA, 300μA, 1.0mA,  
 3mA, 10mA, 30mA, 100mA, 1A, 3A. a.c. V 10, 30V,  
 100V, 300V, 1000V; a.c. I 3mA, 10mA, 30mA,  
 100mA, 1.0A, 3.0A.  
 Ω 0-5.0kΩ, 0-50kΩ, 0-500kΩ, 5MΩ, 50MΩ.  
 dB from -10 to +61 in 5 ranges.  
 Dimensions: 105 x 130 x 40mm.

**ONLY £36.30**

### 3 HIGH QUALITY TEST INSTRUMENTS AT SUPERDEAL PRICES

EACH INSTRUMENT HAS A CLEAR MIRRORED SCALE AND COMES COMPLETE WITH A ROBUST CARRYING CASE, LEADS & INSTRUCTIONS.  
 PRICES Our prices include VAT and postage and goods are normally despatched by return.  
 Please write or telephone for details of these and the many other instruments in the Alcon range, including multimeters, components measuring, automotive and electronic instruments.

**ALCON** Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

You can depend on

## ELECTROVALUE

to supply the fine range of test & measurement gear by

**thandar**

Made in U.K.

**FREE 44 PAGE PRICED AND ILLUSTRATED CATALOGUE ON REQUEST**

● Over 6000 items stocked


- counters
- multimeters
- scopes
- signal generators etc.

**ELECTROVALUE LTD** 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475  
 North Branch, 680 Burnage Lane, Manchester M19 1NA  
 Telephone 061 432 4945  
 Please mention this publication when replying

BRITAINS FOREMOST QUALITY COMPONENT SUPPLIERS

## SAXON MOSFET AMPLIFIERS

**UNBEATABLE PRICES!!!**

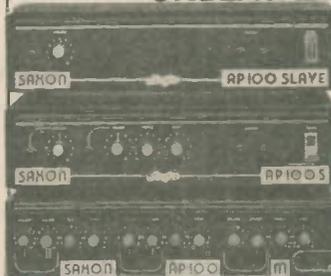

### SLAVE MODEL

AP 100 100W RMS ..... £69  
 AP 200 200W RMS ..... £89

### 2 INPUT GENERAL PURPOSE MODEL

AP 100S ..... £79  
 AP 200S ..... £99

### P.A. MODEL

- ★ 6 INPUTS
- ★ 3 CHANNELS
- ★ ECHO IN/OUT


★ TREBLE/BASS EACH CHANNEL ★ INDIVIDUAL VOLUMES  
 ★ MASTER PRESENCE  
 Write or phone for a **FREE BROCHURE** on these incredible amplifiers  
**P.E. HYPERCHASER** £84.95


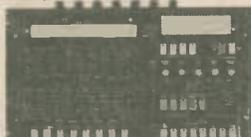
### 4 CHANNEL PSEUDO INTELLIGENT LIGHT UNIT

- ★ 16 Programmes
- ★ Manual Flash Buttons
- ★ Manual/Auto Programme
- ★ Strobe Outputs
- ★ Individual Dimming
- ★ Sound To Light

Not just a light unit but a sophisticated & comprehensive effects unit. A full kit of parts including P.C.B., Facia, Case, etc. Reprint of article on request.



### P.E. STAR DESK

£209

- 8 + 4 CHANNEL LIGHT MIXING DESK
- ★ 8 Channel Twin Preset Mixer
- ★ Strobe Outputs
- ★ 4 Independent Channels
- ★ 4/8 Channel Sequences
- ★ 8 Programmes
- ★ Manual Flash Buttons
- ★ 1KW Output/Channel (can be boosted to 2KW/Ch)
- ★ Timed Crossfade
- ★ Soft/Hard Sequence

A truly magnificent unit ideal for clubs, groups, drama, etc. A full kit of parts inc. PCB, Facia, Case, etc. Reprint of article on request.



### BENSHAM RECORDING LTD

327 Whitehorse Road, Croydon, Surrey CR0 2HS  
 (01) 684 8007  
 9am-5pm, Mon-Sat



All prices include VAT and Post & Packing. Please allow 14 days for delivery

# IVAX Review

Phil Dane (Powertran Cybernetics)

In the past the design of robots has followed the basic form of the human arm but recently there has been a distinct trend for assembly machines to be of a more rational concept. It has become obvious, through experience, that it is both difficult and impractical for machines to successfully emulate the discrete and complex movements of humans.

## SCARA

An increasingly common rationalisation of robot design is that of the SCARA (Selective Compliance Assembly Robot Arm). This type of robot arm (Fig. 1) consists of a horizontal jointed arm with a gripper which has both vertical and rotational movement. The arm is set to a predetermined height which means that the only change in potential energy occurs when the gripper is being raised or lowered. This is not so with a conventional anthropomorphic arm.

Noting this trend towards the use of SCARAs in industry, Powertran have developed a bench top machine which may be used in education or training and incorporates all the features of its industrial counterpart.


## IVAX

The new SCARA from Powertran has been named IVAX and is said to be more sophisticated than some other designs as it employs four servo controlled axes rather than three. The extra axis provides controlled vertical movement using a rack and pinion drive. This allows the arm to be tolerant to small variations in the height of the workstation otherwise each station would require discrete height adjustments.

IVAX has been designed with a total concept in mind, to enable complete emulation of many industrial applications, with work stations which may be expanded or re-configured as and when required. Also its open frame design means that many of the moving parts including the optical encoders may be viewed whilst the machine is in operation, a facility very useful to students and trainees.
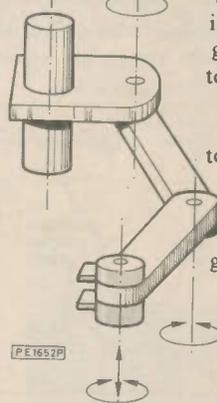
## MECHANICS

The three rotational axes of the IVAX are illustrated in Fig. 2. They all use the same type of d.c. motor with integral gearbox, optical disc read by two slotted opto switches (giving phase/quad) and precision 30 to 1 secondary gearbox. Axes 0 and 1 also make use of constant torque springs which eliminate the effect of backlash in the secondary gearbox.



Axis 3 in addition drives through a 1 to 1 toothed belt which is shown in Fig. 2d. The gripper (see photo) has parallel jaws and is self centring. It has 'vee' grooves in both the horizontal and vertical planes to ensure positive gripping action. The gripper is actuated through a pneumatic circuit controlled by a three-way valve, and for those establishments without a separate compressed air facility the IVAX has its own tiny compressor which is 'whisper' quiet.

## SPECIFICATION

### Description

D.c. servo powered SCARA robot arm with independent input/output. Microprocessor controlled. Command entry from hand-held teach pendant or external computer via parallel interface.

### Configuration

Arm with two rotational axes of motion in horizontal plane. Gripper with vertical and rotational position and on/off control.

### Drive

D.c. servo motors driven from Pulse Width Modulated amplifiers. Pneumatic gripper.

### Feedback

Open frame optical encoders providing continuous positional feedback on all four numerically controlled axes.

### Control

Resident Z80A microprocessor or additionally external computer via parallel interface.

### Resolution

1:3240 on all rotational axes (5 minutes of arc). Better than 0.2 millimetres on vertical axis.

### Operating Envelope

Partial toroid; external radius 280mm, internal radius 108mm, depth 40mm.

### Speeds

Rotational speeds to 60 deg/sec in steps of 0.25 deg/sec.

### Movement


Rotational axes	270 deg
Vertical linear axis	40mm
Gripper opening	15mm

### Work Cell Interface

16 Inputs: Switch to ground or 5 volt digital.  
16 Outputs: Open-collector sinking 30 milliamps.
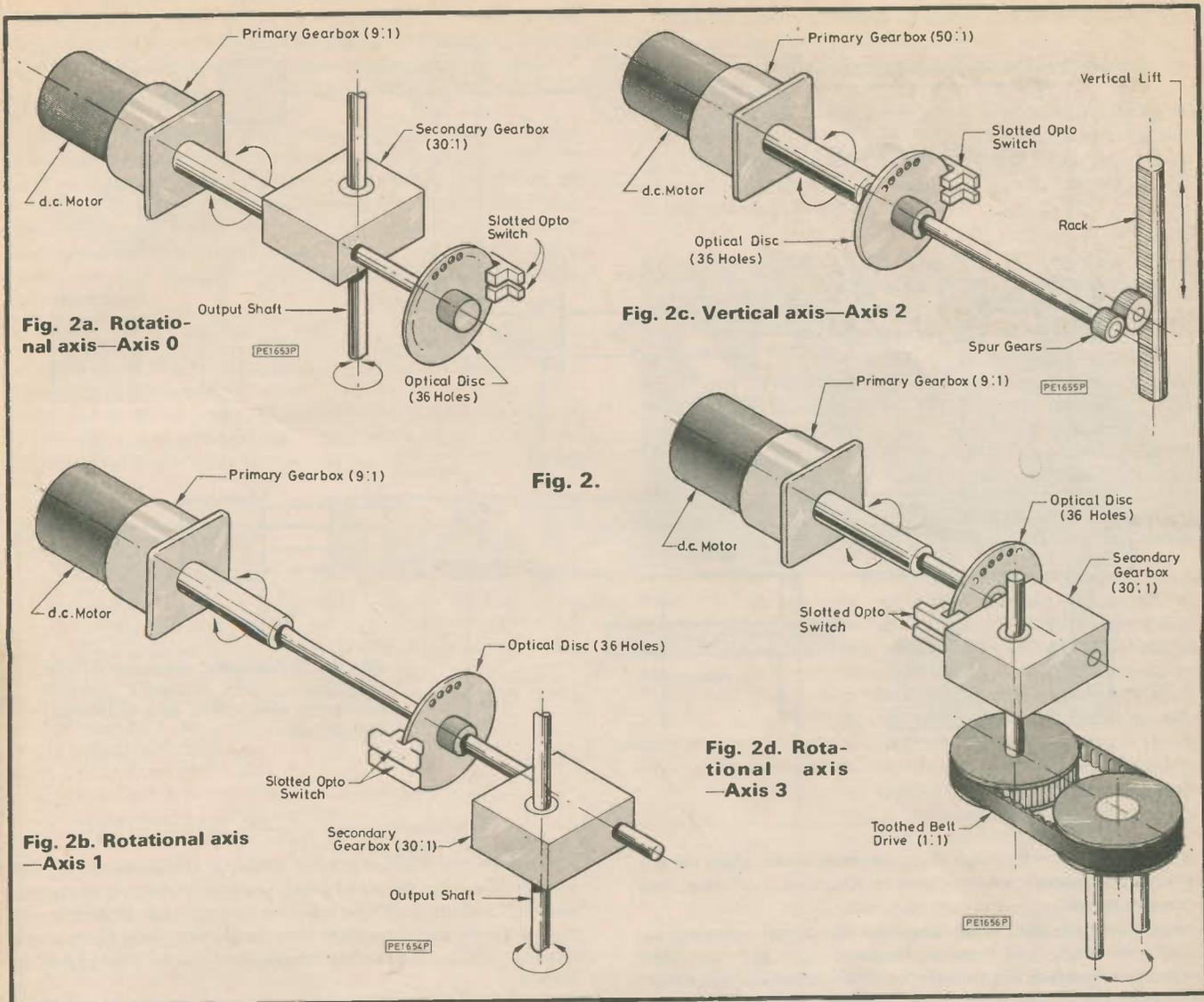
### Other Features


Optional EEPROM non-volatile storage provided for 3 programmable sequences of 32 steps.  
Optional large capacity RAM for storage of 15 programmable sequences.


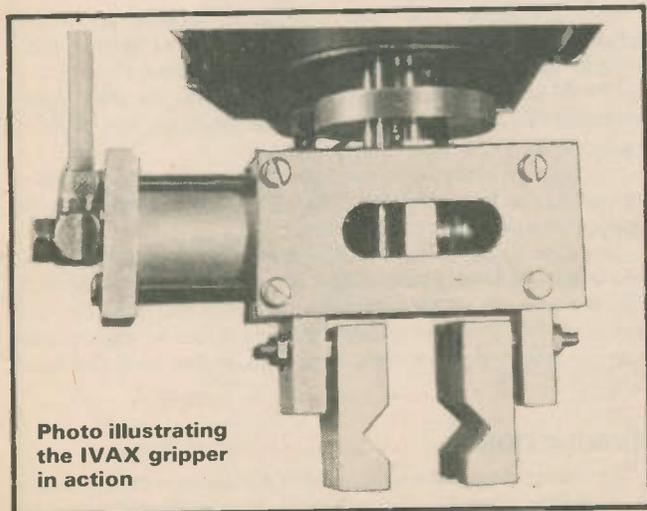
## ELECTRONICS

The electronic control system makes use of complex circuitry which is illustrated in the schematic diagram of Fig. 3.

The heart of the IVAX controller is the Z80A microprocessor running at 4MHz. The controller monitors the inputs, controls the




axes of IVAX (speed and acceleration), has sequence control, monitors for errors in the closed loop system, updates the EEPROM (if fitted), communicates with the host computer and receives information from the teach pendant. The controller also executes commands from the host computer and teach pendant. On board RAM can either be 2K or 8K bytes, enabling a storage of 3 to 15 sequences respectively (a sequence is 32 steps). An optional non-volatile storage (2K) can be fitted in the form of EEPROM. This option enables up to 3 sequences to be stored so that the system can be switched off, or during mains failure the program stored in EEPROM will not be corrupted.

For educational courses in maintenance, testing and fault finding on microelectronics systems, test points have been provided so that all areas of interest can be monitored. An added facility of the system is that the IVAX firmware includes setting up tests which demonstrate the correct functioning of all circuit elements.

An EEPROM is an electrically erasable and programmable read only memory for use where permanent storage is required but also offering the ease of changing the data stored if required.

An expansion port is fitted which allows the electronics to control a further four axes and numerous other input/output devices. Half of the Z80A input/output address map, together with all necessary signals, is available for further control. Numerical control of each of the robot's four axes is achieved through independent closed loop systems to give reliability, accuracy and repeatability. Optical

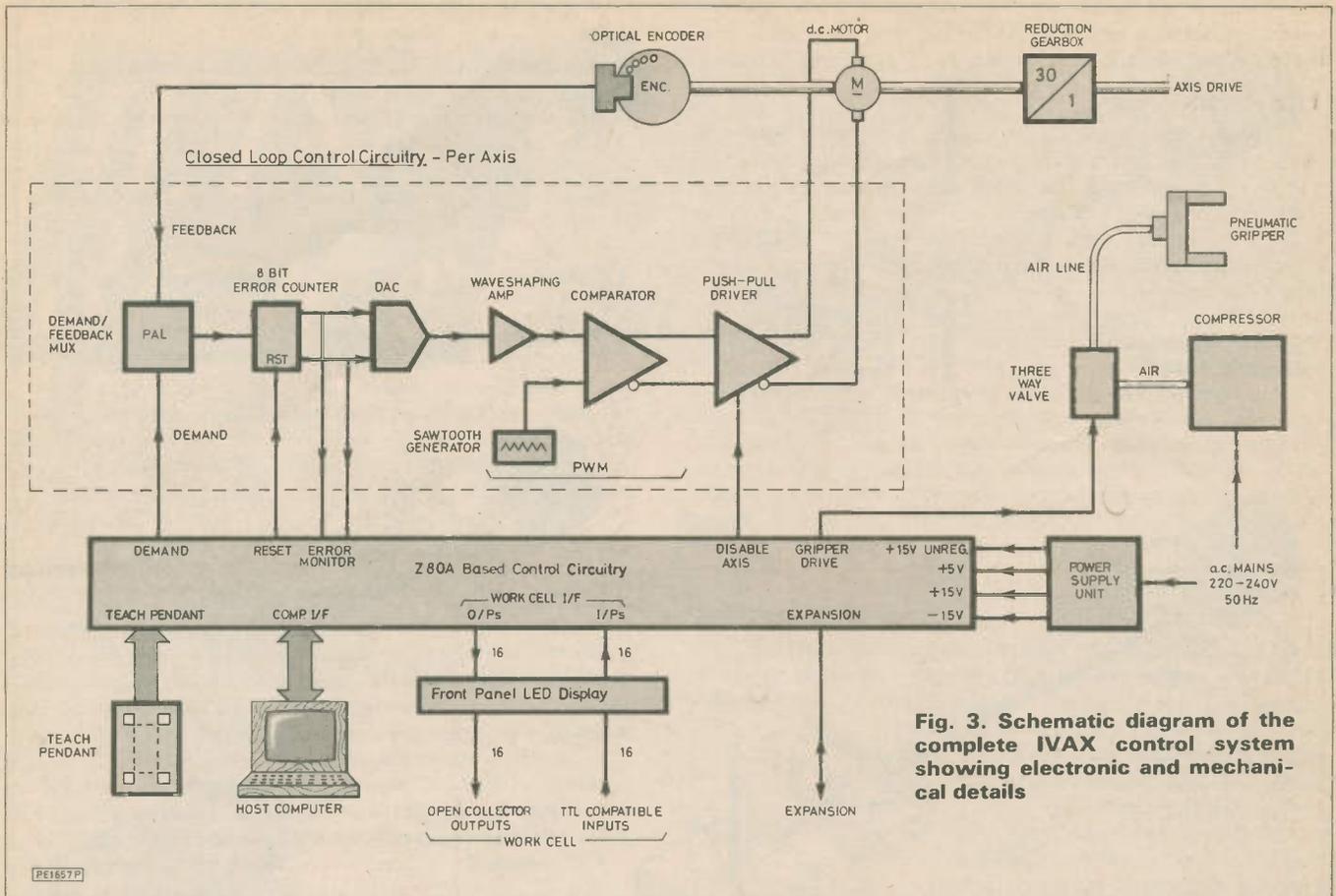

**Fig. 3. Schematic diagram of the complete IVAX control system showing electronic and mechanical details**

encoders are used with pulse width modulated amplifiers for d.c. servo drives to give a resolution on the major axes of better than 5 minutes of arc.

A watchdog circuit is incorporated into the system to protect the robot from abuse. The firmware monitors the robot's operation every 5ms. If stalled, for example, by a person holding the robot's arm, the firmware will halt the robot, reducing the axis error to zero and thus protecting the robot from damage; however, the robot's position is still maintained. The inputs and outputs are continuously displayed on the control unit by light emitting diodes (i.e.d.s). The outputs can be individually or simultaneously programmed through single host computer commands.

### HOST COMPUTER (BBC 'B' OR APPLE IIE)

Although the IVAX can be controlled by using the teach pendant, its full potential can only be realised using a host computer, which will allow the digital inputs to be monitored and the outputs to be controlled. The host computer also enables programs to be written for the IVAX in which decisions can be made on the basis of the digital input status. As IVAX is capable of off-line programming and conditional sequence control, it is possible to write programs on the host computer which can be down-loaded to IVAX to allow the host to be used elsewhere.

### PROGRAMMING

The supplied software consists of procedures and functions so that the IVAX can be controlled entirely using BASIC commands from a host computer such as the BBC. The co-ordinates for the commands are simple cartesian x,y,z co-ordinates with an angle (in degrees) for the gripper orientation. With the x,y and z dimensions being in millimetres the writing of off-line programs becomes a simple matter.

Consider the following brief example (Program 1): In this program the robot moves to a start position, picks up a workpiece, moves to a position where a tolerance testing gauge is fitted, inserts the workpiece into this gauge, tests for the workpiece being within tolerance (input 2 low) and switches output 3 on for 'GO' and off for 'NOGO'.

As can be seen the procedure name implies the function the robot is performing thus making programs very simple to follow. Many other simple to use procedures exist. Impressive examples of which include being able to program speed and acceleration of an axis with just a single command for each. Speed can be set to any number in the range 1 to 255 with 255 being the maximum speed of 60 degrees/second for the rotational axes.

User procedures also exist and are invaluable for writing programs, for example being able to record the present robot position and gripper state with just a single command.

The BASIC software gives complete access to the Z80A based controller and allows user programs to be simulated, run, or down-loaded to the IVAX quickly and easily.

Any location of the IVAX controller memory can be read from or written to the host computer, thus providing a window on the operation of the Z80A based system.

Complete listing of the IVAX firmware is made available and provision has been made within the firmware for students to enhance and extend the operation of the IVAX. This not only makes the IVAX robotic system a learning device for engineers but also for system programmers using high or low level (machine) languages.

### SIMULATION

As with its industrial counterparts IVAX comes complete with its own graphic simulation for the BBC so the principles of simulation

and off-line programming can be demonstrated. When condition sequencing has been written into the program the simulator stops at that point and enquires as to the state of the appropriate input.

### THE WORKCELL

A typical workcell (see photo) consists of two input conveyors (with component feed rate control), measuring gauges, reject bins and an output conveyor. The robot picks components from the conveyors and presents them to the measuring devices, one checks for oversize, one for undersize, which give either a go/nogo signal to the inputs of IVAX. Reject components are placed in the appropriate bin and passed components are placed on the output conveyor.

The robot may also be programmed to:


1. Alternate between servicing each input conveyor if there is a component present on each (components are detected by a reflective opto switch).

2. Concentrate on one conveyor if there is a queue of components and may also stop the conveyor. (See flowchart Fig. 4.)

Alternatively the robot is available with a CNC Mill and feed conveyor.

With the ability to analyse 16 inputs and set 16 outputs, IVAX can cope with an immense number of events and can take a tremendous variation of actions, provided all have been anticipated by the programmer.

With the system being so flexible in both hardware and software it makes an ideal tool for project work. The increasing use of robots in industry implies a need for the training of a substantial number of personnel of all levels, but especially technicians and engineers in the technology of robots.

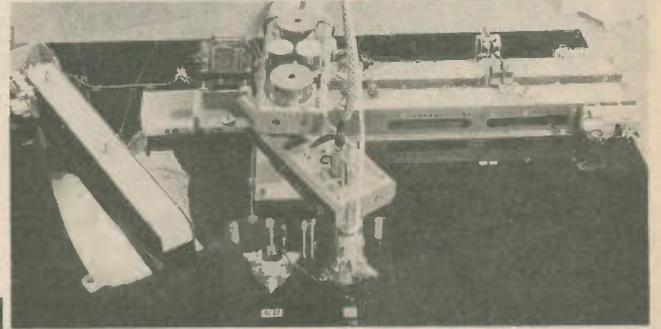


Program 1

```

10 PROCINIT          REM: INITIALISE FIRMWARE VARIABLES
20 RMODE=ROBOT       REM: ROBOT MOVEMENT ONLY
30 SMODE=STPINS      REM: ROBOT MOVEMENT/INSERT INTO MEMORY
40 PROCDROP (-90,-230,0,-180) REM: START WITH GRIPPER OPEN
50 PROCPICK (-90,-230,25,-180) REM: WORKPIECE POSITION THEN CLOSE GRIPPER
60 PROCPICK (-90,-230,0,-180) REM: RAISE GRIPPER
70 PROCPICK (0,280,0,0)    REM: TEST POSITION
80 PROCDROP (0,280,30,0)  REM: LOWER WORKPIECE INTO GAUGE
90 PROCWAIT (1)        REM: PAUSE
100 PROCIFLO (2,20)     REM: IF 'GO' JUMP TO LABEL 20
110 PROCOUT (3,FALSE)  REM: TEST 'NOGO' OUTPUT 3 OFF
120 PROCGOTO (5)       REM: JUMP TO LABEL 5
130 PROCLABEL (20)    REM: LABEL 20
140 PROCOUT (3,TRUE)   REM: TEST 'GO' OUTPUT 3 ON
150 PROCLABEL (5)     REM: LABEL 5
    
```

Fig. 4. Program flowchart

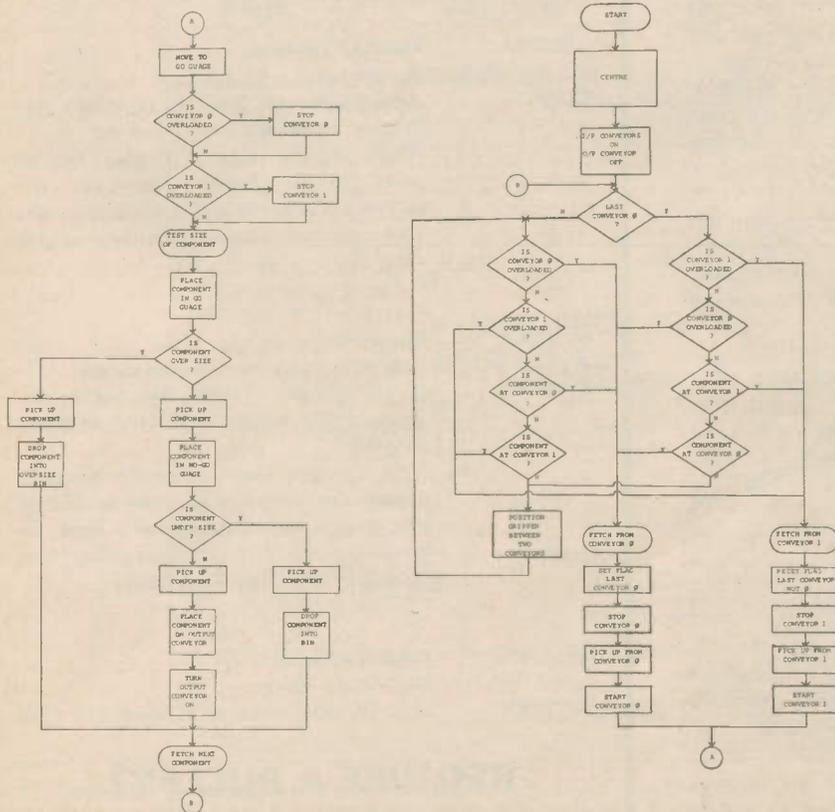

Robot technology encompasses not just the mechanical engineer but also the electronic engineer. They must come together to work as a team to develop the automation of production. This calls on universities, colleges and training establishments to provide courses with hands-on experience to enable technicians to retrain in the new robot technology and Flexible Manufacturing Systems. This is the reason why Powertran Cybernetics Education Division has developed the SCARA IVAX robotic workcell.

Up until now the robots available for education and training have only been able to pick and place, with many of them no more than toys. The IVAX SCARA is different. It has been designed to simulate an industrial robot having conditional sequence control. The Powertran IVAX SCARA robot has taken the state of the art technology used on industrial FMS and scaled it down to perform actual production line techniques involving: measurement, palletising, decision making, assembly work and milling.

### BUYERS NOTE:

The basic system comprises: a power supply unit, control unit, IVAX SCARA robot, teach pendant, software, manual and coursework.

If purchased in kit form a comprehensive construction booklet is provided.

This product can be obtained from:

**Powertran Cybernetics Limited**

(Education Division),

Portway Industrial Estate,

Andover,


Hampshire,

SP10 3PE.

☎ (0264) 64455.

# Experimenting With ROBOTS

Mike Abbott Part 2

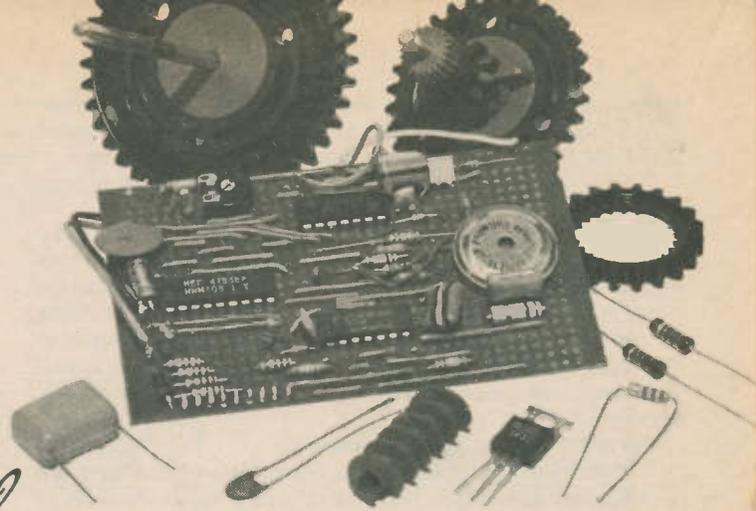

LAST month we looked at a robot interface with four conventional servo channels, plus an unconventional channel dubbed the *TACACOOGA*. This month we look at the construction of that interface. It is designed, where possible, to use the kind of cheaper components most likely to be found in the constructor's "junk" box. We also illustrate the ultra-simple gripper (Fig. 5).

## MECHANICAL ADVANTAGE


Should you wish to use a more sophisticated gripper mechanism, in which the motor is geared down to drive the jaw, then the *TACACOOGA* may be used *in reverse*, but a single-pole changeover type limit switch is required.

Only two changes are necessary. One is to swap the gripper motor wires so that the automatic cut-off (stall current detect) operates when the gripper is *closing* instead of opening. The other change is to remove the link between A and B in LK2 and wire a microswitch so that it detects when the jaw is fully open, switching point B to point C (0V).

With this arrangement the Torque control preset might as well be set to maximum motor speed. The stall current cut-out feature will activate when the gripper bites onto the object it is to grasp. Note that even with VR10 set to maximum sensitivity your gripper might only pick up an egg safely if it is hard boiled. Part of the entertainment of experimental robotics is in the matching of electronics and mechanics to application.

In this slightly more conventional arrangement, I suppose the circuit name should be truncated to ACOOC (Automatic Cut-Off On Closure). This configuration does assume a high reduction gearing between motor and jaw, so that when the motor is de-energised

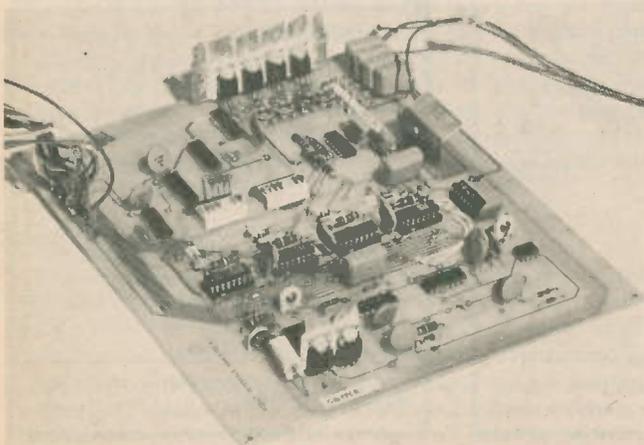the jaw cannot roll back from the object in its grip. A worm drive is a typical arrangement for this purpose.



## NEED A GEARWHEEL?

Listed below are some useful addresses for those who wish to procure modular mechanical and electrical components suitable for *Experimenting With Robots*. The common denominator with all these type building media is cost. Components are not particularly cheap, but they do offer the advantage of being re-usable, so that when the initial outlay is divided by the number of variants constructed each individual machine works out to be quite inexpensive. In addition to this, these modular systems are highly educational in a subject area of great importance to future industry.

MEDIUM: **Fischer Technik**  
AVAILABILITY: Toy stores  
SUPPLIER: Artur Fischer UK Ltd., 25 Newtown Rd., Marlow, Buckinghamshire SL7 1JY  
(The complete range of Fischer Technik parts is surprisingly extensive, and includes many electronic modules). The little engineer appears courtesy of this company

MEDIUM: **Meccano**  
AVAILABILITY: Specialist model engineering shops  
SUPPLIER: M. W. Models, 4 Greys Rd., Henley-on-Thames, Oxfordshire RG9 1RY. ☎ 0491 572436.  
(This company seems to be the Meccano *Mecca*, providing a mail order service to UK and overseas customers from an amazing stock. Write to "Everything Meccano", or telephone for details.)

MEDIUM: **Lego Technic**  
AVAILABILITY: High Street shops  
SUPPLIER: Lego UK Ltd., Wrexham, Clwyd LL13 7TQ

## REQUIRE A PULLEY?

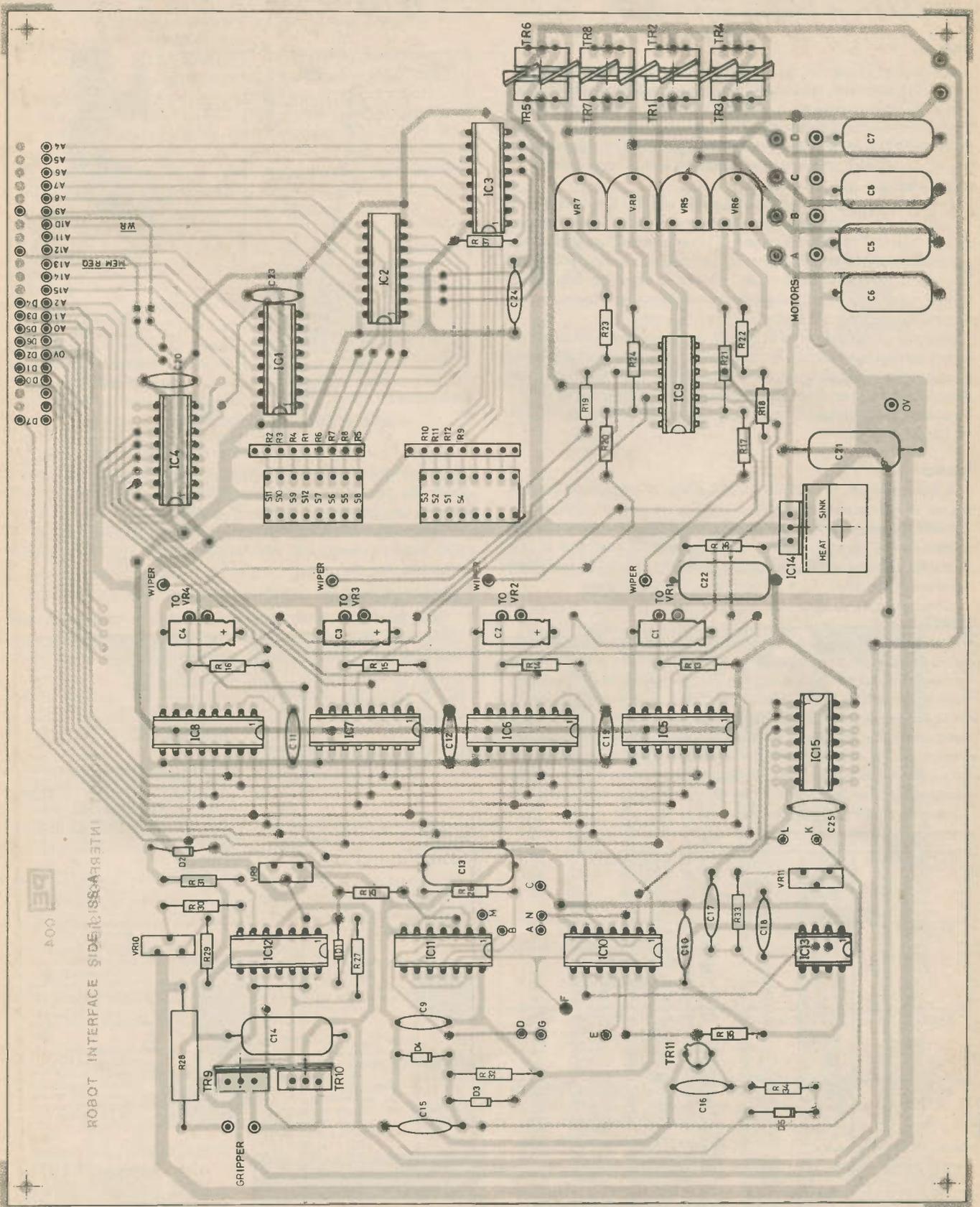


Fig. 4. Component layout on the double-sided p.c.b. Note that the black "dots" represent through-board links. Use eyelets, or tinned copper wire to make these connections first. Last month's Components List requires correcting. The 100n capacitors are as follows: C9-12, C15-20, C23-25 (13 off). This board is available through the *PE PCB Service*, order code 004

## PAG

The gripper circuit may be used in yet another configuration, and this is called *Pulse Activated Gripper*. In this mode of operation the gripper motor is driven for a preset time period generated by IC13 triggered from the Enable E line. The time period is the same for each motor direction. The options link table should be referred to if the p.c.b. is used. Table 2 also indicates which components to omit or link out.

The PAG may work to your satisfaction with C17 at 100nF, but should a longer motor duration be required for a particular gripper design then C17 may be increased in value to suit. The pulse width generated by IC13 should be set to just long enough in duration to fully open, or fully close the jaw. No undue strain on the motor should result from the energisation period lasting a fraction of a second longer than the motor's limits of travel.

With the circuit operating in this mode, the preset VR9 ought to be set to maximum torque, although altering its setting might allow you to null a slight difference in motor travel time between each direction of the jaw. Alternatively, the torque limiting facility might be utilised to advantage in the "close" direction, to control the grip on fragile objects.

## SPAG

A Symmetrical PAG (SPAG) can be built if the torque control aspect of the circuit is of no use, and still more components saved. Table 2 shows how VR9 can be lost, and if the link references are related to the circuit diagram in Fig. 3, it will be seen that IC12a operates as a straightforward linear amplifier, and IC12b becomes redundant.

## EPUD

Although the experimenter may discover other ways to configure the gripper circuit, the *Electromagnetic Pick-Up Driver* is the last variation to be discussed here. By removing the components indicated in Table 1, the circuit becomes a simple solenoid driver for a robot capable of picking up ferrous objects. The Torque control facility remains intact, and allows greater freedom of choice of the solenoid rating. Since the solenoid might be an unspecified "junk box" item, stripped from a relay, or even home spun, VR9 can be adjusted until the pick-up has adequate "attraction" without overheating.

MODE	FUNCTION	P.C.B.	LINKS
TACACOOGA	Torque Adjustable Closure, Automatic Cut-Off On Opening Gripper Actuator	Fully populated	A - B D - E J - H M - N
ACOOOC	Automatic Cut-Off On Closure	Wire limit switch with <i>n.o.</i> contacts between link positions B and C. Board fully populated Change R27 to 68k	D - E J - H M - N
PAG	Pulse Actuated Gripper	Omit R29, R30, R31, R32, R34, D3, D4, D5, TR11, VR10, C15, C16	B - G D - E L - K M - N
SPAG	Symmetrical Pulse Actuated Gripper	Omit as PAG, plus VR9, C13 and D2. Short out R28. Short out D1. Change R27 to 56k. Link VR9 (top) to VR9 wiper position	B - G D - E L - K M - N
EPUD	Electromagnetic Pick-Up Driver	Omit R29-34, VR10, VR11, C13-18, D3, D4, TR10, TR11, IC13. Replace C14 with 1N4001 diode. Link out R27	A - B B - G M - P

Table 2. TACACOOGA options. All unmentioned links should be left open

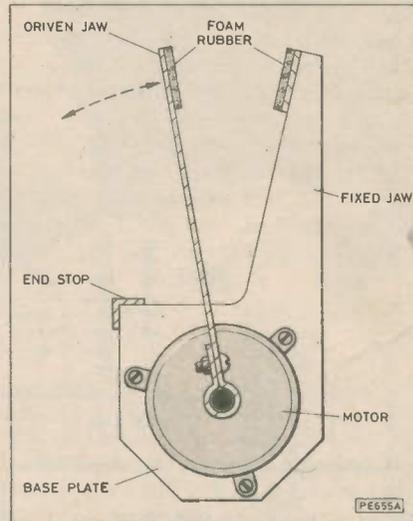



Fig. 5. The simplest gripper possible? A pair of 'electric pliers' for use with the TACACOOGA. An old cassette recorder motor will probably prove adequate

It is worth noting at this point that driving an op. amp. from TTL outputs in the way that IC11 drives IC12a will work reliably only if both the op. amp's inputs are driven from the same piece of silicon, i.e. the same TTL chip. It appears at a glance that in the EPUD configuration R25 might just as well be connected directly to OV, but if it were, the driver circuit would probably become unstable.

## CONSTRUCTION

Only one or two notes are necessary in connection with assembling the p.c.b. (Fig. 4). The first step is to decide how many channels are required initially, and therefore how much of the

Fig. 6. Heatsink dimensions

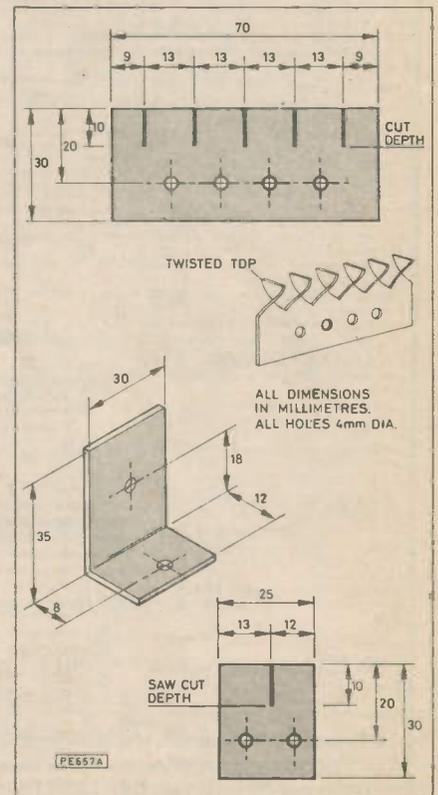

p.c.b. is to be populated. The next step is to decide which mode the gripper circuit should be used in; whether it is to be used as the full TACACOGA, as a derivative thereof, or as a straightforward motor (or electromagnet) switch.

When ready to proceed with construction, first insert the through-board links. Although the p.c.b. is double-sided, through-plating has been omitted to control its cost to the constructor. Eyelets or pieces of 22 s.w.g. tinned copper wire should be used for these links where they occur underneath i.c.s and other components, but elsewhere the use of solder pins will create an abundance of "easy clip-on" test points. The through-board links should be made *before* any components are inserted, of course, particularly those located beneath IC5-8 and IC13.

If the p.c.b. is drilled to 0.8mm for the i.c.s, you may find it necessary to open out the holes to 1mm for the passive components, or greater in the case of power components.

Sockets should at least be used for IC5-8, if not all d.i.l. components, including the addressing switches.

The three heatsinks are cut out of sheet alloy, and their dimensions are shown in Fig. 6. The two shared heatsinks require the use of mica washers and 4BA nylon nuts and screws to secure the transistors. Heatsink compound should be applied, and the transistors mounted loosely on the heatsink before inserting them in the p.c.b. If they are tightened to the heatsink whilst in situ, and then soldered, the transistors' leads will not be left under permanent stress.

The remaining components may be soldered in any order, and the i.c.s inserted in their sockets afterwards. During any subsequent experimentation with the board it must be borne in mind that there are three distinct OV systems on the p.c.b. which meet at a common "star" point. These are: *Analogue Ground*, *Digital Ground*, and a high current line for the motors, called *Motor Ground*. Cross wiring these during any exercise will most likely lead to

unwanted voltage drops along p.c.b. tracks which in turn upset the digital logic, or the accuracy of the analogue circuits. This point is particularly important to remember if you intend building all, or part, of this interface on stripboard.

## SOFTWARE

A program to demonstrate the complete interface, and written in BASIC for the standard ZX81, is shown in Listing 1. The program assumes that all the address decode switches are off (logic 1's), so that the interface is located at base address 65520.



```

10 LET L=65520
20 PRINT "WHICH CHANNEL: 0,1,2,3,4 ?"
30 INPUT C
40 CLS
50 LET M=L+C
60 PRINT "CHANNEL ";C
70 IF C = 4 THEN GOTO 200
100 PRINT "POSITION: ↑ - 255 ?"
110 GOTO 230
200 PRINT "SELECT "
210 PRINT "'1) OPEN GRIPPER"
220 PRINT "'2) CLOSE GRIPPER"
230 INPUT P
240 POKE M,P
250 PRINT " "
260 GOTO 20

210 PRINT "'1) CLOSE GRIPPER"
220 PRINT "'2) OPEN GRIPPER"

```

Listing 1  
Demonstration  
Program

} Alternative lines for  
} ACIOC

**NEXT MONTH:** Give your robot shifty eyes!

### PRESTEL UNITS

These are brand new and we understand tested, came with manufacturer's guarantee now void as the manufacturer no longer trades. They are originally sold for over £150. We offer them complete, except for 7 plug in i.c.s and price is only £14.95 (less than the value of the modem included).

### YOUR TELEPHONE

Can be frustration free with the ABS one push dialling unit. You program its index with up to 220 of your important numbers. From then on all you do is flip the index to the person you want, press the call button and the number will be dialled automatically (numbers not worth programming can still be fast push button dialled). Should the number be engaged whether it is in your index or not it will be memorised and at a touch of the button you can try again. Another big feature - the built in speaker and microphone allow you to have your hands free for other jobs whilst awaiting your call. The ABS unit is B.T. approved and simply plugs into a B.T. socket and a mains point. We have 50 only of these, so send or phone your order **TODAY** the price **£37.50** but you will save this in a few weeks even if you value your time at only 10p a minute.

**25A ELECTRICAL PROGRAMMER**  
Learn in your sleep: Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch, independent 60 minute memory jogger. A beautiful unit at **£2.50**.

**TOP OF THE POPS LIGHTING**  
if you use our disco switch  
These have 12 x 10 amp changeover switches each rated at 10 amps so a whole street could easily be lit with one. Switches adjustable and could be set to give a running light, random flashes, etc to 230 volts main operation. Brand new, made by Honeywell. Offered at approximately one third of cost. **ONLY £6.90**

**EXTRACTOR FANS - MAINS OPERATED**  
Woods extractor.  
5" - £5.75, post £1.25. 6" - £6.95, post £1.25.  
5" Plannax extractor £6.50, post £1.25.  
4" x 4" Muffin 115v. £4.50, 230v. £5.75, post 75p.  
All the above ex-competitor, those below are unused.  
4" x 4" £8.50, post 75p.  
9" American made  
£11.50, post £2.10.  
Tangential Blower 10 x 3  
air outlet, dual speed  
£4.60, post £1.50.

### BURGLAR ALARM PARTS

Pressure Pads unobtrusive under carpets. Make contact when trodden on. 2" x 18" £1.75, 12" x 10" £1.25. Control box for use with pressure pads door/window. Switches - maintains alarm once triggered - fitted with removable key master switch - test for working switch, relays etc. £11.50.

Alarm Bell 12" gong heavy cast construction - mains operation £23 + £4 carriage.  
6" Gong Bell, heavy construction, suitable in or out. 12 volt operated. £7.50.

Squawker Alarm 6-12v DC or 12-24v AC as used in mugger alarms also suitable car or m/c 75p each, 100 £58, 1000 £375. Quiet Alarm will tell just you that alarm has been triggered. 3v DC, selectable three levels of sound £1.15.  
Wiring Staples plastic headed hardened pin right size for fig 8 flex-box of 500 £2.95.

**ROCKER SWITCHES** Standard size fit 11.5 x 28 mm cut out. Single pole on/off - 15p each, 1000 for £75. Single pole changeover 20p each, 1000 for £100. Single pole changeover with centre off - 25p each, 1000 for £125. Single pole on/off with neon 36p, 1000 for £180.

**MINIATURE WAFER SWITCHES**  
2 pole, 2 way - 4 pole, 2 way - 3 pole, 3 way - 4 pole, 3 way - 2 pole, 4 way - 3 pole, 4 way - 2 pole, 6 way - 1 pole, 12 way. All at 25p each or 10 for £2.00.

**12voh MOTOR BY SMITHS**  
Made for use in cars, etc. these are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle. Price £3.45. Ditto, but double ended £4.25.

**MINI MOND AMP** on p.c.b., size 4" x 2" (app.)  
Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, very perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.

**J. BULL (Electrical) Ltd.**  
(Dept. PE) 34-36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

**MAIL ORDER TERMS:** Cash, P.O. or cheque with order. Orders under £12 add £1 service charge. Monthly account orders accepted from school and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote.

CMOS	4095	589	74LS76	28p	PL95	140p	VOLTAGE REGULATORS	HA-1197	150p
4000	15p	4099	586	74LS78	34p	74LS273	75p	PL500	110p
4001	16p	4501	30p	74LS83	45p	74LS279	45p	PL504	95p
4002	16p	4502	30p	74LS85	52p	74LS280	140p	PL508	170p
4006	30p	4503	40p	74LS86	30p	74LS280	30p	PL519	450p
4012	19p	4504	60p	74LS90	39p	74LS285	42p	PY88	70p
4008	44p	4505	260p	74LS91	75p	74LS366	44p	PY500A	160p
4009	30p	4506	60p	74LS92	46p	74LS367	43p		7805
4010	32p	4507	33p	74LS93	40p	74LS368	41p		7812
4011	16p	4508	85p	74LS95	52p	74LS373	68p		7815
4012	16p	4510	42p	74LS96	63p	74LS374	68p	7400	22p
4013	20p	4511	42p	74LS107	35p	74LS375	58p	7401	15p
4014	40p	4512	45p	74LS109	36p	74LS389	80p	7402	18p
4015	40p	4513	90p	74LS112	38p	74LS670	80p	7403	22p
4016	27p	4514	30p	74LS113	32p			7404	40p
4017	39p	4515	85p	74LS114	36p			7405	10p
4018	40p	4517	51p	74LS122	44p	DAF96	60p	7407	40p
4019	33p	4517	51p	74LS122	44p	DAF96	60p	7408	40p
4020	50p	4518	40p	74LS123	50p	DF96	50p	7409	25p
4021	45p	4519	30p	74LS124	85p	DL92	47p	7409	20p
4022	43p	4520	44p	74LS125	36p	DI97	50p	7413	35p
4023	19p	4521	90p	74LS126	42p	DI92	45p	7414	45p
4024	30p	4522	50p	74LS132	44p	EABC80	50p	7417	32p
4025	16p	4526	48p	74LS133	34p	EB91	44p	7420	22p
4026	68p	4528	44p	74LS136	35p	ED90	45p	7421	25p
4027	30p	4528	44p	74LS138	36p	EB93	50p	7425	15p
4028	38p	4529	76p	74LS139	40p	EC82	43p	7430	25p
4029	53p	4531	55p	74LS145	83p	EC83	43p	7437	26p
4030	28p	4532	170p	74LS147	120p	EC84	40p	7442	45p
4031	100p	4533	190p	74LS148	109p	EC87	40p	7447	22p
4032	54p	4535	29p	74LS151	38p	EC81	49p	7450	22p
4033	60p	4536	41p	74LS153	42p	EH84	52p	7451	10p
4034	59p	4537	180p	74LS154	100p	EL82	57p	7454	25p
4035	50p	4583	55p	74LS155	51p	EL86	59p	7470	30p
4036	220p	4584	36p	74LS156	49p	EL84	57p	7473	30p
4037	80p	4585	49p	74LS157	35p	EL85	57p	7474	40p
4038	58p	4586	17p	74LS158	47p	EL86	49p	7475	25p
4039	220p	4587	60p	74LS160	32p	EF80	31p	7481	90p
4040	42p	74LS00	17p	74LS161	56p	EF85	34p	7482	70p
4041	38p	74LS01	17p	74LS162	50p	EF89	43p	7485	40p
4042	43p	74LS02	17p	74LS163	50p	EF83	45p	7486	20p
4043	40p	74LS03	17p	74LS164	44p	EF84	53p	7489	80p
4044	40p	74LS04	17p	74LS165	65p	EL34	190p	7490	35p
4045	72p	74LS05	17p	74LS166	80p	EL36	50p	7492	45p
4046	49p	74LS06	17p	74LS168	98p	EL84	50p	7493	35p
4047	49p	74LS09	17p	74LS169	70p	EL95	50p	7495	40p
4048	32p	74LS10	17p	74LS170	55p	EL500	80p	7497	80p
4049	26p	74LS11	17p	74LS174	40p	EL504	100p	74107	30p
4050	26p	74LS12	17p	74LS175	46p	EL506	57p	74111	57p
4051	42p	74LS13	17p	74LS180	59p	EV87	31p	74116	50p
4052	40p	74LS14	30p	74LS191	55p	EV88	32p	74119	85p
4053	40p	74LS15	17p	74LS192	50p	EZ35	45p	74122	40p
4054	58p	74LS26	17p	74LS193	57p	EZ80	50p	74123	20p
4055	58p	74LS21	17p	74LS194	37p	EZ81	55p	74125	40p
4056	58p	74LS22	17p	74LS195	56p	EZ34	180p	74126	45p
4060	53p	74LS24	38p	74LS196	67p	PC87	100p	74132	42p
4063	57p	74LS26	17p	74LS197	52p	PC82	33p	74131	25p
4066	30p	74LS27	76p	74LS221	81p	PCF80	56p	74145	70p
4067	160p	74LS28	17p	74LS240	62p	PCF200	135p	74153	45p
4068	16p	74LS30	17p	74LS241	60p	PCF801	110p	74155	45p
4069	16p	74LS32	17p	74LS242	70p	PCF802	57p	74157	45p
4071	16p	74LS33	17p	74LS243	64p	PCF806	115p	74160	50p
4072	16p	74LS37	17p	74LS244	64p	PCH200	109p	74164	50p
4073	16p	74LS38	17p	74LS245	78p	PCL81	54p	74167	35p
4076	16p	74LS40	17p	74LS246	50p	PCL82	63p	74173	50p
4077	16p	74LS47	50p	74LS249	82p	PCL84	50p	74174	70p
4078	16p	74LS48	50p	74LS251	60p	PCL85	55p	74175	65p
4081	16p	74LS51	17p	74LS252	58p	PCL805	55p	74176	50p
4082	16p	74LS54	17p	74LS256	85p	PFL200	85p	74182	45p
4085	42p	74LS55	17p	74LS257	48p	PL36	80p	74192	40p
4086	34p	74LS73	28p	74LS258	45p	PL82	45p	74196	40p
4089	26p	74LS74	26p	74LS259	62p	PL82	32p	74197	55p
4093	26p	74LS75	28p	74LS260	42p	PL84	50p	74393	70p

**GRANDATA LTD.**  
9 & 12 THE BROADWAY, PRESTON ROAD  
WEMBLEY, MIDDLESEX ENGLAND  
Telephone: 01-904 2093 & 904 1115/6  
Telex: 932885 Summit

# BBC Micro Forum...

David Whitfield MA MSc CEng MIEE

THIS month *BBC Micro Forum* moves on to look at some of the less obvious elements of the analogue port. First under the microscope are the two pushbutton inputs nominally provided for joysticks.

## JOYSTICK FIRE BUTTONS

One of the most popular uses for the analogue port (in the early days of owning a computer, at least) is for connecting the games joysticks. Most of us just plug them in without a second thought, and then get on with alien blasting, or whatever, until the early hours of the morning. It may be of interest, however, to look at just how the joysticks are usually connected up to the analogue port. As shown in Fig. 1, each joystick is, in fact, a pair of potentiometers wired between  $V_{ref}$  and ground. The fire buttons act by shorting the pushbutton inputs to ground. The figure shows the connection from the wiring side of the plug. With the four-channel ADC (described last month), there is clearly no problem catering for two independent joysticks.

The 'fire' or pushbutton inputs are internally connected to PB4 and PB5 on the system VIA. The levels on these inputs are normally at logic 1, but change to logic 0 when the corresponding button is pressed. The easiest way to read the state of the bushbuttons, however, is to use the Basic ADVAL function. Using the following statement:

$X = \text{ADVAl}(0) \text{ AND } 3$

will give the following values for X, depending on the button states as follows:

- X=0 no buttons pressed
- X=1 left button pressed
- X=2 right button pressed
- X=3 both buttons pressed

The left button is labelled button 0, and the right one button 1 on the connector drawing.

Clearly the fire buttons can be replaced by almost any other switch, or by any circuit which switches between two states. This can be a useful addition to the user port in applications which require more lines than those available.

## LOW COST JOYSTICKS

Adding joysticks to the BBC Micro can be relatively expensive since analogue potentiometer types are required. Mr. A. Moran of Reading has suggested a simple way of interfacing the lower cost switch type of joystick via the user port. Usually, it is necessary to build some form of interface between the analogue port and this type of joystick, but his approach does away with

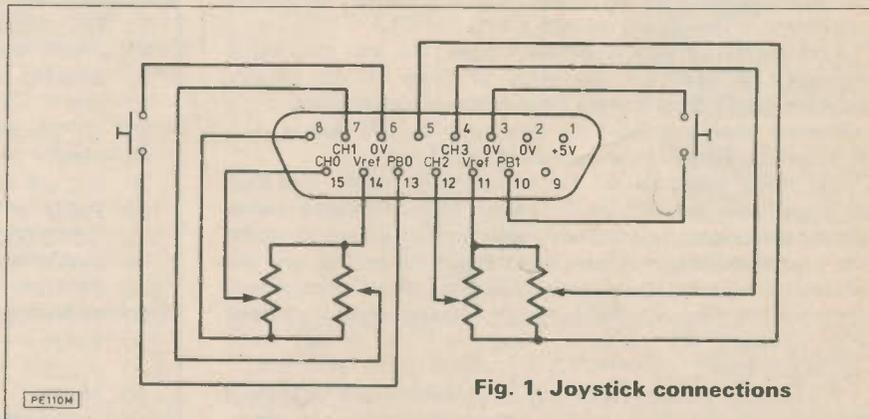


Fig. 1. Joystick connections

that problem, and allows a lower cost solution to be produced. Indeed, if you don't already own one, you could even try building your own switch joystick using two 2-way centre-off switches, some rubber bands, and a pushbutton switch; any offers for a design?

The interface to the user port is shown in Fig. 2, where the connections are those for a Philips G700 joystick. The connections for other popular models such as the Atari, Competition Pro, Quickshot, etc., are all similar. If in doubt, a simple battery and bulb arrangement will allow the exact connection details to be determined. The pull-up resistors are to ensure good noise immunity. With the joystick connected in this way, the switches will return a logic 0 when closed. Listing 1 provides an interesting demonstration of the joystick at work. The relationship between the user port bit values, and the joystick movements, are given in Table 1. The program allows an asterisk to be moved around the screen, and produces a satisfying 'zap' when the fire button is pressed. The program also allows

diagonal movement by testing each direction independently.

In passing, readers may already have noticed in last month's column that long lines in program listings have been broken for printing. This has been done manually (hence all of the mistakes are mine!), in an attempt to break each line at an identifiable point. This is to try to avoid the problems which can occur when an automatic line breaker is used, and I do try to break lines at obvious points like commas or where extra spaces will do little or no damage.

User Port	Joystick Movement	Value Read
Bit 0	LEFT	1
Bit 1	RIGHT	2
Bit 2	UP	4
Bit 3	DOWN	8
Bit 4	FIRE	16

Table 1. Switch values

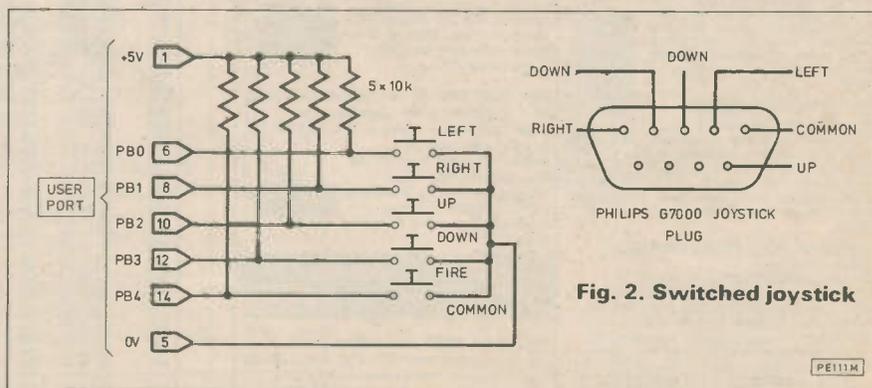


Fig. 2. Switched joystick





### SUPER HY-LIGHT STROBE KIT

Designed for Disco, theatrical uses, etc.

Approx. 16 joules. Adjustable speed. Price £45 + £2 p&p (Total inc. VAT £54.05). Case and reflector price £15 + £2 p&p (total inc. VAT £19.55). Footcapp SAE for further details including Hy-Light and Industrial Strobe Kits.

### ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt CALLERS ONLY

2ft 20 watt £7.40 + £1.25 p&p (£9.99 inc. VAT)

18in. 15 watt £5.00 + 75p p&p (£6.61 inc. VAT)

13in. 10 watt £4.00 + 75p p&p (£5.46 inc. VAT)

12in. 8 watt £3.60 + 50p p&p (£4.71 inc. VAT)

9in. 6 watt £3.00 + 50p p&p (£4.02 inc. VAT)

6in. 4 watt £3.00 + 50p p&p (£4.02 inc. VAT)

220V AC Ballast Kit for either 6in, 9in or 12in tubes £5.50 p&p 55p (£6.96 inc. VAT).

For 13in. & 18in. Tubes £6 p&p 75p (£7.76 inc. VAT).

For 12V DC op. 12in. & 13in. tubes only £5.50 p&p 75p (£7.18 inc. VAT).

175 WATT SELF-BALLASTED BLACK LIGHT MERCURY BULBS.

Available for either B.C. or E.S. fitting, price £10.80 + p&p £1.25 (total inc. VAT £13.85).

400W UV LAMP & BALLAST complete — £48.80 + p&p £3.50 (£60.15 incl. VAT).

400W UV LAMP only, £20.00 + p&p £2.50 (£25.88 incl. VAT).

ROBOT ENTHUSIASTS

1. ESCAP precision Swiss-made ironless rotor, 6V DC geared motor with 70:1 gearbox, 6V DC — 16 r.p.m. 3V — 8 r.p.m. amazing power; no load current; only 10ms. approx. Size: 4 x 2 1/2 cm. Ex-equipment, tested and guaranteed. ONLY £4.50 + 50p p&p (total inc. VAT £5.75).

MICRO SWITCHES

Type 1. Heavy duty 10A c/o contacts. Type 2. V3 c/o contacts. Type 3. Sub-miniature c/o contacts. All button type. Price £6.90 inc. VAT for 10, any type. Post paid. N.M.S.

VORTEX BLOWER & SUCTION UNIT

Powerful multi-stage dynamically balanced totally enclosed rotors, 1 1/2in. inlet and outlet, 110V AC. £22.00. Switchable transformer for 240V AC £8.00 p&p £3.00 — total £37.95 inc. VAT.

VBL4 CENTRIFUGAL BLOWER

240V AC powerful 1/50 h.p. .23A motor. £18.00 + £2.00 p&p (Total inc. VAT £23.00). N.M.S.

CENTRIFUGAL BLOWER

Smith Type FFB 1706. 240V A.C. Aperture 45-40mm £6.50 p&p £1 (inc. VAT £8.62).

12/24V DC CENTRIFUGAL BLOWER

0.4A producing 30 cu.ft. £7.50 + £1.00 p&p — total inc. VAT £9.78. N.M.S.

METER 30mm dia. 0-300V A.C. M/C rect. £5.00 p&p £1 inc. VAT £6.90.

COOLING or EXTRACTOR FAN

Quiet smooth running. Size 4 3/4 x 4 3/4 x 1 1/2. Supplied for 240V a.c. operation. Price £4.75 + £1 p&p (Total inc. VAT £6.62) N.M.S.

HEAVY DUTY SOLENOID

Mf. by Magnetic Devices 230V AC. Intermittent operation. Approx. 20lb pull at 1.25in. Ex-equip. Tested £10.00 + £1.50 p&p — total inc. VAT £13.23.

### VARIABLE VOLTAGE TRANSFORMERS

INPUT 230, 240V a.c. 50/60 OUTPUT 0-260V.

200W, 1A Max. £18.50

0.5KVA 2 1/2A Max. £21.00

1KVA 5A Max. £29.00

2KVA 10A Max. £41.00

3KVA 15A Max. £56.00

5KVA 25A Max. £99.00

10KVA 50A Max. £181.00

15KVA 75A Max. £275.00

### 3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual input 200-240V or 380-415V. Star connected

3KVA 5amp per phase max. £113.40

6KVA 10amp per phase max. £170.10

10KVA 16amp per phase max. £345.45

Comprehensive range of TRANSFORMERS L.T. ISOLATION & AUTO (110-240V). Either cased with American socket and mains lead or open frame type available for immediate delivery. Leaflet on request.

### 12V D.C. BILGE PUMPS

400 G.P.H. 15ft. head, 3amp, £8.00 + £1.00 p&p (£9.35 inc. VAT).

700 G.P.H. 10ft. head, 3.5amp, £11.50 + £1.50 p&p (£14.95 inc. VAT).

1750 G.P.H. 15ft. head, 9amp, £15.00 + £1.75 p&p (£19.26 inc. VAT).

SINGLE DIAPHRAGM COMPRESSOR NMS

Max. 20 PSI. One CFM approx. 240 volts A.C. £18 + £2 p&p (£23 inc. VAT).

### EPROM ERASURE KIT

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case to include 12, 8 watt 2537 Angst. Tube. Ballast unit, pair of bi-pin leads, Neon indicator, safety microswitch, on/off switch and circuit.

LESS CASE: Price £13.60 + 75p p&p (Total inc. VAT £16.50).

Warning: Tube used in this circuit is highly dangerous to the eyes. Unit must be fitted in suitable case.

### SOLID STATE E.H.T. UNIT

Input 230V A.C. Approx. 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec, to continuous. Designed for boiler ignition.

Dozens of uses: In the field of physics and electronics, e.g. supplying neon or argon tubes etc. £6.50 + 90p p&p (Total inc. VAT £8.50) N.M.S.

### A.C. CAPACITOR

16 UF 900V A.C. 50/60 Hz. Ideal power factor correction etc. 9 1/4 x 6 x 4 3/4 ins. Wt. 7 1/2 Kg. Price £12.00 + £3.00 p&p (Total inc. VAT £17.25). N.M.S.

### FROM STOCK AT PRICES THAT DEFY COMPETITION

DC GEARED MOTORS

AC CAPACITORS

STROBE KITS

FLASH TUBES

CONTACTORS

SYNCHRONOUS MOTORS

RELAYS

RED SWITCHES

SOLENOIDS A.C. or D.C.

PROGRAMME TIMERS

WIDE RANGE OF XENON TUBES

WRITE/PHONE IN YOUR ENQUIRIES

### Superior Quality Precision Made SUPER POWER RHEOSTATS



New ceramic construction, heavy duty brush assembly, continuously rated.

25 WATT £10/25/50/100/150/250/300/500/1KΩ

1.5kΩ £4.25 + 30p p&p (£5.23 inc. VAT).

50 WATT 250Ω £6.50 + 50p p&p (£8.05 inc. VAT).

100 WATT 1/5/10/25/50/100/250/500/1KΩ/1.5kΩ/2.5kΩ/3.5kΩ

£10.25 + 75p p&p (£12.65 inc. VAT).

Black Silver Skirted Knob calibrated in Nos 1-9, 1 1/2in. dia. brass bush. Ideal for above Rheostats 30p ea. + VAT.

### INSULATED TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work constant speed clutch. Size L 8in., W 4in., H 6in. weight 6lb.

500V. 300 megohms. £49 p&p £2 (£58.65 incl. VAT).

1000V 1000MΩ £55 + p&p £2 (£65.95 incl. VAT) SAE for leaflet.

### LT. TRANSFORMERS

\*Special Offer: 0-6.3V-0-6.3V at 10 Amp (12V 0-10 Amp or 6V at 20 Amp) Price £9.00 p&p £2.00 — inclusive of VAT £12.65 N.M.S.

### GEARED MOTORS

5 rpm 240V AC Mf. by Carter. £5.05 £1 p&p (£8.11 inc. VAT). N.M.S.

20 rpm 115V AC Synchronous, torque approx. 80lb/in. £20.00 + £4 p&p (Total inc. VAT £27.80). N.M.S.

TRANSFORMER 240V operation, £9.15 + £2.00 p&p (Total inc. VAT £12.82).

28 rpm Torque 20lb.in. reversible 1/80th h.p. 110V AC. Price: £3.50 + p&p £1.80 (Total inc. VAT £12.99).

Suitable TRANSFORMER for 230-240V AC operation. Price: £5.20 + p&p £1.40 (Total inc. VAT £7.98). N.M.S.

38.3 rpm GEARED MOTOR. Torque 35lb.in. reversible 115V AC inc. start capacity. Price: £11.55 + £2.00 p&p (Total inc. VAT £15.58). N.M.S.

Suitable TRANSFORMER for 230V AC operation. Price: £5.20 + 50p p&p (£5.96 inc. VAT).

57 rpm 240V 1/22 h.p. continuously rated REVERSIBLE 50lb.in. manuf. by Wynstruments. New. Ideal for garage doors, curtains etc. ONLY £12.00 + £2.00 p&p (incl. VAT £16.10), inclusive capacitor.

71 rpm Torque 10lb.in. reversible 1/70th h.p. 110V AC motor. Price: £9.50 + £1.80 p&p (Total inc. VAT £12.99).

Suitable TRANSFORMER for 230-240V AC operation. Price: £5.20 + p&p £1.40 (Total inc. VAT £7.98). N.M.S.

24V DC 200 rpm 10lb/in. Mf. by either Parvalux or Cater. Ex-equip. tested. £8.00 + £1.50 p&p (Total inc. VAT £10.90).

230/240V AC SYNCHRONOUS, 2 rpm, 6 rpm, 6 rev per day. Any type: £4.80 + 50p p&p (Total inc. VAT £5.10).

### CHECK METER

200-240V A.C. 50amp, fully reconditioned. £7.50 + £1.75 p&p (Total inc. VAT £10.64).

### SANGAMO WESTON TIME SWITCH

Type S251 200/250 A.C. 2 on/2 off every 24 hours, 20 amps contacts with override switch. Dimeter 4"x3". Price £9.50 + £1.50 p&p (£12.65 inc. VAT & p&p). Also available with solar dia R&T. Other types available from stock.

N.M.S. New Manufacturers' Surplus R&T Reconditioned and tested Goods normally despatched within 7 days.

Ample parking space

Showroom open

Monday-Friday



## SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB. Tel: 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only. Open Saturdays

9 Little Newport Street

London WC2H 7JJ

Tel: 01-437 0576

NEW LOOK

# IT'S BIGGER-IT'S BETTER

## TEST-GEAR SPECIAL

How to construct a FET-DIP OSCILLATOR covering frequencies from 1.8 to 150MHz, a SIMPLE CAPACITANCE METER for values up to 1uF and more besides.

## GET READY FOR 50MHZ

Make your own 50MHz transverter — a high performance, proven design for use with your 28MHz transceiver. The circuit can be adapted for 70MHz (4 metres) or 144MHz (2 metres). Full details for all three bands.

## PLUS LOTS MORE IN

Practical **Wireless** The Radio Magazine

At £1 — Britain's least expensive radio hobby magazine.

NEW STYLE Practical **Wireless** The Radio Magazine

Get Ready For **50MHZ**

Build This Transverter

● TEST GEAR SPECIAL ● FET-DIP OSCILLATOR, SIMPLE CAPACITANCE METER & MORE

OCTOBER ISSUE OUT NOW



# SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Dept., Practical Electronics, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5846.)

## NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

TURN YOUR SURPLUS capacitors, transistors, etc into cash. Contact COLES HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 584188. Immediate settlement.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. FORRESTERS (NATIONAL RADIO SUPPLIES), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## BARGAIN BUMPER BOX OF BITS

Contains: working calculator, working watch module, Various ICs, transistors, display tubes, PCBs, diodes batteries, gears, switches, etc., etc. All useful items. Would cost much, much more if bought separately. **ONLY £15** (inc VAT and P&P). Send cheque/PO to:

Cyril Young, Service Dept., Decimo Ltd, 4-18 Chobham St., Luton LU1 3BS

## EDUCATION/TUITION

### IMPROVE YOUR PROSPECTS

With skills that are in demand. Learn the easy way with a Modern Home Study Course in:

## ELECTRONICS

Train for a success in the fastest ever growing Industrial Sector. Course includes topics such as: Simplified Circuit Theory, Resonance, Transistor Amplifiers, Filters and Non-Linear Wave Shaping, Digital Circuits, Micro-Computers etc. (Use our course to help prepare for BTEC or C&G examinations.)

Write or telephone today for Free Prospectus - No Obligation

### IDEAL SCHOOLS, Ref: PE1

60 St Enoch Square, Glasgow G1, UK or Tel: 041-248 5200.

## FOR SALE

### PROMS - EPROMS - PALS

EPROMS from £3.25 (2716/2732/2764 etc)  
PROMS from £1.50 (TBP/82S/63 series etc)  
PALS from £4.25 (12H6/16C1/16L8 etc)  
Full Programming Service available  
SAE for full price list (incl. RAMs etc)  
Any i.c. supplied - if it exists we will find it  
PLS, 16 Wordsworth Drive, Cheam, Surrey SM3 8HF.  
Phone 01-644 8095 (usually manned 0800-2000 hrs)  
Private and professional enquiries welcome.

## SERVICE SHEETS

BELLS TELEVISION SERVICES for service sheets of Radio, TV, etc £1.50 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

## RECEIVERS AND COMPONENTS

### SWITCHED MODE POWER SUPPLIES

70 watt power supply with better than 0.25% regulation. Designed and manufactured by well known British Company.  
Input 180v to 275v a.c. 40 Hz to 70 Hz.  
Outputs + 5v @ 9 Amps (13 Amps Peak)  
+12v @ 3 Amps  
-12v @ 0.5 Amps

### Special Price Silicon Express

£50.00  
inc VAT and P&P  
Access accepted

Silicon Express Limited Silicon House  
Fowke Street Rothley Leicestershire  
LE7 7PJ, UK  
Tel: 0533 374917 Telex 342835

### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.  
22 & 47—6p. 100—7p. (50V—8p). 220—8p. (50V—10p).  
470—11p. (40V—10p). 1000/15V—15p. 1000/25V—25p.  
1000/40V—35p. 4700V/25V—70p.

**Subminiature bead Tantalum electrolytics.**  
0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 53V — 14p.  
2-2/35V, 4-7/25V—15p. 10/25V, 15/16V—20p.  
22/16V, 33/10V, 47/6V, 68/3V & 100/3V—32p.  
15/25V, 22/25V, 47/10V—35p. 47/16V—80p.

**Subminiature Ceramic Caps. E12 Series 100V.**  
2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.  
10% 390 pf. to 4700 pf.—4p.

**Vertical Mounting Ceramic Plate Caps. 50V.**  
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.

**Polystyrene E12 Series 63V. Horizontal Mtg.**  
10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.

**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
0.1 to 008—4p. 0.1—5p. 0.15, 0.22—6p. 0.33, 0.47—10p.  
0.68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

**Mylar (Polyester) Film 100V. Vertical Mounting.**  
0.01, 0.022, 0.047—3p. 0.1, 0.22—4p. 0.4, 0.5, 0.1—5p.

**High Stability Miniature Film Resistors 5%.**  
1/4W E24 Series 0.51R—10M0. — 1p.  
1/2W E12 Series 1R0 to 10M0. — 11/2p.  
1W E12 Series 10R to 10M0. — 5p.  
1/4W metal film E12 Series 10R 1M0. 5% — 2p. 1% E24 — 3p.  
1N4148—2p. 1N4002—4p. 1N4006—8p. 1N4007—7p.  
BC107/8/9—12p. BC147/8/9, BC157/8/9, BF195 & 7—10p.  
8 Pin i.c.'s 741 Op. amp.—20p. 555 Timer—24p.  
Dil. Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.  
LED's, red, green, yellow, 3 & 5mm.—10p. 8mm.—35p.  
Grommets for 3mm.—2p. Grommets for 5mm.—2p.  
20mm. O.B. Fuses .15, .25, .5, 1, 2, 3 & 5A—5p.  
20mm. Anti Surge 100mA to 5.0A—8p.  
20mm. Fuseholders P.C. or Chassis Mtg.—8p.  
Battery Snaps (pairs) PP3—6p. PP9—12p.  
400mW Zener diodes E24 series 2V7 to 33V—8p.  
Prices VAT inclusive Post 20p. (Free over £5.00).

### THE C.R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for .....

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME .....

ADDRESS .....

.....

.....

## Practical Electronics

Classified Advertisement Dept., Room 2612,  
King's Reach Tower, Stamford Street,  
London SE1 9LS Telephone 01-261 5846

Rate:  
36p per word, minimum 12 words. Box No. 60p extra.

**COURSES**

**FULL-TIME TRAINING COURSES**

**2 YEAR**

**B-TEC National Diploma (OND) ELECTRONICS & COMMUNICATIONS ENGINEERING**  
(Television & Computing)

**15 MONTHS**

**B-TEC National Certificate (ONC) ELECTRONIC EQUIPMENT SERVICING**  
(Television & Video)

**15 MONTHS**

**B-TEC National Certificate (ONC) COMPUTING TECHNOLOGY**

**9 MONTHS**

**B-TEC Higher National Certificate (HNC) COMPUTING TECHNOLOGY**

**& ROBOTICS**

HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK

SHORT COURSES WITH PREVIOUS KNOWLEDGE

NO EXTRA CHARGES FOR OVERSEAS STUDENTS

Prospectus from:

**LONDON ELECTRONICS COLLEGE**

Dept: AA, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721.

**MISCELLANEOUS**

**RECHARGING NICAD CELLS**

Using D.C.? Charging too cool? Charging too long? **YOU'RE DOING IT WRONG!**

Keep your Nicad cells from early failure with this revolutionary new charging system (as published in July 85 "Wireless World")

Send s.a.e. for kit details to:  
J. Biles Engineering, 120 Castle Lane, Solihull, West Midlands B92 8RN.

**HEATHKIT. U.K. SPARES AND SERVICE CENTRE.** Cedar Electronics. Unit 12, Station Drive, Bredon, Tewkesbury, Gloucestershire. Tel. (0684) 73127.

**CLEARING LABORATORY,** scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders etc. Tel. 0403-76236.

**BURGLAR ALARM EQUIPMENT.** Ring Bradford (0274) 308920 for our catalogue or call at our large showroom, opposite Odsal Stadium.

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from PVC. Faced steel. Vast range, competitive prices start at a low £1.50. Punching facilities at very competitive prices. **BAZELLI,** (Dept. 23), St. Wilfreds, Foundry Lane, Halton, Lancaster LA2 6LT.

**SURPLUS COMPONENT PACKS.** Over 100 unused components in each includes resistors, capacitors, inductors. £2.00 & 50p P and P. Send cheque/P.O. to: R. King, The Old Police House, Bury Road, Woolpit, Suffolk.

**INSTRUMENT CASES** in structural foam manufactured cheaply in small lots. Write to Minnow Plastics, 6 Avonmouth Street, London SE1 6NX, or phone 01-407 0910.

**MISCELLANEOUS - CONTD.**

**THE SCIENTIFIC WIRE COMPANY**  
811 Forest Road, London E17. Telephone 01-531 1568

ENAMELLED COPPER WIRE				
SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	9.09	5.20	2.93	1.97
TINNED COPPER WIRE				
14 to 30	3.97	2.41	1.39	0.94
Fluxcore Solder	5.90	3.25	1.82	0.94

Prices include P&P VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

**SOFTWARE**

**CMOS SINGLE-CHIP PROCESSORS.** User configurable macro assembler for 6301/6303 devices. Fast execution on BBC, Apple or Pet. £16 each. Versions also available for 6805, 65C02 & 6809 devices. SAE full details: M. J. TYLER, 2 Parkview, Cashes Green, Stroud, Glos. 04536 77257.

**HOME SECURITY**

**WHO CAN PUT A PRICE ON A PEACE OF MIND?**

PROFESSIONAL EQUIPMENT AT LOW! LOW! PRICES.

**HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES**

2 Ealing Road, Aintree, Liverpool L9 0HU, Merseyside.

**Tel: 051-525 3440**

FREE CATALOGUE PHONE OR S.A.E.

**CENTURION ALARMS**

**Manufacturers of Professional Alarm Equipment for DIY & the TRADE.** Send now for our New 16-page Brochure, Full of Information & the Lowest prices.



Tel: (0484) **21000** or 35527 40 hr.

**CENTURION Dept PE**  
93 Wakefield Road, Huddersfield. HD5 9AB W. Yorks.

© CENTURION is a Registered Trademark of Centurion Alarms

**TRANSFORMERS & POWERS SUPPLIES**

**TRANSFORMERS AND POWER SUPPLIES** at very low prices. Manufacturers surplus and end of production runs. All English made. Send S.A.E. for list. Titan Transformers, Central Hall, Duncombe Street, Grimsby DN32 7EG.

**★ BAKER ★**

**GROUP P.A. DISCO AMPLIFIERS** post £2

150 watt Output, 4 input Mixer pre-amp. Illustrated	£99
150 watt Output, Slave 500 mv. Input 3 Speaker Outputs	£80
150+150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs	£125
150 watt P.A. Vocal, 8 inputs. High/Low Mixer Echo Socket	£129
100 watt Valve Model, 4 inputs, 5 Outputs. Chassis only	£99
60 watt Mobile 240V AC and 12V DC. 4-8-16 ohm + 10" line	£89
Reverb Unit for Microphone or Musical Inst. £35 PP. £1.	
Electronic Echo Machine for mic/etc £85 PP. £1. Deluxe £95.	

**BAKER LOUDSPEAKERS**

Type	Model	Size	Watts	Ohms	Price
P.A./Disco/Group	DG50/10	10in	50	8/16	£20.00
Midrange	Mid 100/10	10in	100	8	£25.00
Hi-Fi	Major	12in	30	4/8/16	£18.00
Hi-Fi	Superb	12in	30	8/16	£28.00
P.A./Disco/Group	DG45	12in	45	4/8/16	£18.00
Hi-Fi	Woofer	12in	80	8	£25.00
Hi-Fi	Auditorium	15in	60	8/16	£39.00
P.A./Disco/Group	DG75	12in	75	4/8/16	£22.00
P.A./Disco/Group	DG100	12in	100	8/16	£28.00
P.A./Disco/Group	DG100/15	15in	100	8/16	£39.00
300Watt Mid-N-Top system complete					£125.00 each carr. £12

**DISCO CONSOLE** Twin Decks, mixer pre amp £145. Carr £10. Ditto Powered 120 watt £199; or Complete Disco 120 watt £300. 150 watt £360; 300 watt £410. Carr £30.

**DELUXE STEREO DISCO MIXER/EQUALISER** plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. Headphone Monitor, Mike Talkover Switch **£129** PP £2. As above but 3 Deck inputs, 4 Line/Aux inputs, 2 Mic. inputs, 2 Headphone Monitors, Stereo Graphic + LED Display £145.

**P.A. CABINETS** (empty) Single 12 £34; Double 12 £40. carr £10. **WITH SPEAKERS** 75W £56; 90W £75; 150W £84; 200W £92. **HORNBOXES** 200 Watt £32, 300 Watt £38. Post £4. **FULL RANGE SYSTEMS** 200W £100; 400W £150. carr £10.

**OUTDOOR HORNS** 8 ohms, 25 watt £22, 30 watt £25, 40 watt £33. 200W plus 100 watt line £38

**MOTOROLA PIEZO ELECTRONIC HORN TWEETER**, 3 1/2in square 66 100 watts. No crossover required. 4-8-16 ohm, 7/8x3 1/8in. £10

**CROSSOVERS TWO-WAY** 3000 cps 60 watt £5.50, 80 watt £7, 100 watt £10. **LOUDSPEAKER BARGAINS** Please enquire, many others in stock.

4 ohm, 5in, 7x4in £2.50; 6 1/2in, 8x5in £3.8in, £3.50; 6 1/2in, 25W £7.50. 8 ohm, 25in 3in £2; 5x3in, 6x4in, 7x4in, 5in, £2.50; 6 1/2in, 8 x 5in £3; 8in, £4.50; 10in, £5; 12in, £5.8in, 25W £5.50; 8in, Twin Cone 60W £12.50. 15 ohm, 2 1/4in, 3 1/2in, 5x3in, 6x4in, £2.50; 6 1/2in 10W £5; 8in, £4; 10in, £7. 25 ohm, 3in, £2; 5x3in, 6x4in, 7x4in, £2.50; 120 ohm, 3 1/4in dia, £1.

Make	Model	Size	Watts	Ohms	Price	Post
AUDAX	WOOFER	5 1/2in.	25	8	£19.50	£1
GOODMANS	HIPAX	7 1/2x4in	100	8	£30	£2
GOODMANS	HB WOOFER	8in	60	8	£13.50	£1
WHARFEDALE	WOOFER	8in.	30	8	£3.50	£2
CELESTION	OISCO/Group	10in.	50	8/16	£21	£2
SEAS	WOOFER	10in.	50	8	£19.50	£2
WEM	WOOFER	10in	300	8	£36.00	£2
GOODMANS	HPB/Group	12in	120	8/15	£34.00	£2
GOODMANS	HPD/Disco	12in	120	8/15	£34.00	£2
H+H	DISCO/Group	15in.	100	4/8/16	£69	£4
GOODMANS	HP/BASS	15in.	250	8	£74	£4
GOODMANS	HPO/BASS	18in.	230	8	£87	£4
PERLESS	TWEETER	3 1/4in.	60		£7.50	£1
AUDAX	TWEETER	2 1/2in.	30	8	£4	£1

**METAL GRILLES** 8in, £3.00, 10in, £3.50, 12in, £4.50, 15in, £5.50, 18in, £7.50. Loudspeaker Covering Vymair etc. Samples. S.A.E.

**DISCO SOUND / LIGHT CONTROLLER**

Ready Built Deluxe 4 Channel 4,000 watt sound chaser + speed + programme controls. £69. Mk.2 16 programmes. £99. PP £2. **DISCO "PARTY LIGHTS"**, Sound Flashing, Light Show, 4 lamps, self contained unit 240V A.C. No other connections needed £34.95. PP £2.

**MAINS TRANSFORMERS**

	Price	Post
250-0 250V 80mA, 6.3V, 3.5A, 6.3V 1A.	£7.00	£2
350-0 350V 250mA, 6.3V 6A CT £12.00 Shrouded	£14.00	£2
220V 25mA, 6V 1 Amp £3.00 220V 45mA, 6V 2 Amp	£4.00	£1
250V 60mA, 6.3V 2A.	£5.00	£1

Low voltage tapped outputs available  
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £5.00 £2  
ditto 2 amp £10.50 3 amp £12.50 5 amp £18.00 £2  
31-26-0-26-31 volt 6 amp £14.00 £2

**LOW VOLTAGE MAINS TRANSFORMERS** £5.50 each post paid  
9V, 3A; 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1 1/2A; 30V, 5A+ 17-0-17V, 2A; 35V, 2A; 20-0-60V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 50V, 2A.

**£8.50 post 50p MINI-MULTI TESTER**  
Pocket size instrument. DC volts 15, 150, 500, 1000. AC volts 15, 150, 500, 1000. DC 0.1ma, 0.150ma. Resistance 0 to 100k. De-Luxe Range Double Meter, 50,000 o.p.v. 7 x 5 x 2in. Resistance 20 meg. In 5 ranges. Current 50µA to 10A. 0.25V to 1000V DC. 10V to 1000V AC. £25.00 post £1

**PANEL METERS** 50µA, 100µA, 500µA, 1mA, 5mA, 100mA, 500mA, 1amp, 2amp, 5amp, 25 volt, VU 2 1/4x2 1/4in. £5.50 post 50p

**PROJECT CASES.** Black Vinyl Covered Steel Top, Ali Base  
4 x 2 1/2 x 2 1/4in. £2.50; 6 x 4 x 1 1/2in. £3.50; 8 x 5 x 2in. £4.00; 11 x 6 x 3in. £5.50; 11 1/4 x 6 x 5in. £9.00; 15 x 8 x 4in. £12.00.

**ALUMINIUM PANELS** 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75; 6 x 4in. 5sp; 12 x 8in. £1.30; 10 x 7in. 9sp; 8 x 6in. 9sp; 14 x 3in. 7sp; 12 x 5in. 9sp; 16 x 10in. £2.10; 16 x 6in. £1.30.

**ALUMINIUM BOXES.** 4 x 4 x 2 1/4in. £1.60; 7 x 5 x 2 1/2in. £2.90; 3 x 2 x 1in. £1; 4 x 2 1/2 x 2in. £1.20; 4 x 4 x 1 1/2in. £1.50; 6 x 4 x 2in. £1.90; 6 x 4 x 3in. £2.20; 8 x 6 x 3 in. £3.00; 10 x 7 x 3in. £3.60; 12 x 5 x 3in. £3.60; 12 x 8 x 3in. £4.30; 10x4 1/2x3in. £2.90; 4x5 1/4x2 1/2in. £1.50; 4x2 3/4x1 1/2in. £1.20.

**HIGH VOLTAGE ELECTROLYTICS**  
16450V 75p 20+20/350V 75p  
20/500V 75p 8+9/500V £1 32+32/500V 50p  
32/350V 45p 8+16/450V 75p 32+32+32/450V £1.50  
32/500V 95p 16+16/350V 75p 16+32+32/500V £2

**SINGLE PLAY RECORD DECKS.** Post £2

Make	Drive	Model	Cartridge	Price
BSR	Belt	12 Volt	Ceramic	£22
BSR	Rim	P207	Ceramic	£22
AUTOCHANGER	BSR	Ceramic	£22	
AUTOCHANGER	GARRARD	Ceramic	£24	

**DECCA TEAK VENEERED PLINTH** space for small amplifier Board cut for BSR or Garrard 18 3/4in. x 14 1/4in. x 4in. £5. Post £1

\*\*\* "STOP PRESS" \*\*\*  
H & H 1000 Watt stereo/mono. Professional Power Amplifiers 5500D Reconditioned, guaranteed. £275, carriage £5.

**RADIO COMPONENT SPECIALISTS**

Dept 3, 337, WHITEHORSE ROAD, CROYDON SURREY, U.K. Tel: 01-684 1665

Post 65p Minimum. Callers Welcome. **ACCESS** **VISA**

Same day despatch. Closed Wed. Lists 34p.

Post 65p Minimum. Callers Welcome. **ACCESS** **VISA**

Same day despatch. Closed Wed. Lists 34p.

# ESR

13a Station Road  
Cullercoats - North Shields  
Tyne & Wear - NE30 4PQ  
Telephone 091 2514363

TRANSISTORS - RESISTORS - CAPACITORS -  
DIODES - LED'S - SCR'S - ICS - VOLTAGE  
REGULATORS - DISPLAYS - AUDIO & EDGE  
CONNECTORS - VERO/PCB'S - INSTRUMENT  
CASES & BOXES - POWER AMPLIFIERS &  
MODULES - MICROPHONES & STANDS.

WRITE OR PHONE FOR FREE PRICE LIST.

## CRICKLEWOOD ELECTRONICS LTD

It's no secret!



NOW! SUMMER CATALOGUE

that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

**CRICKLEWOOD ELECTRONICS LTD.**  
40 Cricklewood Broadway NW2 3ET.

01-450 0995 & 01-452 0161

ALL MAJOR CREDIT CARDS ACCEPTED  
Telex 914977 Phone or write today

# It's easy to complain about an advertisement. Once you know how.

One of the ways we keep a check on the advertising that appears in the press, on posters and in the cinema is by responding to consumers' complaints.

Any complaint sent to us is considered carefully and, if there's a case to answer, a full investigation is made.

If you think you've got good reason to complain about an advertisement, send off for a copy of our free leaflet.

It will tell you all you need to know to help us process your complaint as quickly as possible.

The Advertising Standards Authority. ✓  
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 1 Brook House,  
Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

## TRAIN FOR A BETTER JOB IN ELECTRONICS

Everyday more people are needed to design, install, operate and service electronic systems.

It's big business and the career opportunities are both limitless and richly rewarding.

Prepare yourself for a future in Electronics with an ICS Home-Study Course quickly, easily and in your own time.

### Proven teaching methods

ICS is the world's largest correspondence school with over 90 years experience.

So far nearly 9 million people have taken advantage of our tried and tested teaching methods.

Find out how we can help you. Send today for your FREE information pack. No obligation.

**ICS** Please send me full details of the Electronics Course.

NAME: \_\_\_\_\_  
ADDRESS \_\_\_\_\_

P. Code \_\_\_\_\_


International Correspondence Schools,  
Dept. EDSA5, 312/314 High Street, Sutton,  
Surrey SM1 1PR. OR PHONE



01-643 9568/9 or  
041-221 2926 (24 hrs.)

## INDEX TO ADVERTISERS

Adcola Products.....	Cover 2
A.D.E.....	55
Alcon Instruments.....	41
Bensham Recording Ltd.....	41
B.N.R.E.S.....	5
Bull J.....	49
Centurion Alarms.....	55
Clef Products.....	17
Cricklewood Electronics.....	56
Crofton Electronics.....	5
Croydon Discount Electronics.....	5
C.R. Supply Co.....	54
CSL Sound.....	39
Cybernetic Applications.....	17
Decimo.....	54
Electrovalue.....	41
ESR.....	56
Flight Electronics.....	Cover 3
G.C.H.Q.....	25
Grandata.....	49
ICS Intertext.....	56
Ideal Schools.....	54
J. Biles Engineering.....	55
JAYTEE Electronics.....	25
London Electronics College.....	55
Maplin Supplies.....	Cover 4
Marco Trading.....	37
Phonosonics.....	4
Programme Logic Services.....	54
Radio Component Specialists.....	55
Reekie Robots.....	17
Scientific Wire Co.....	55
Service Trading.....	53
Silicon Express.....	54
Tandy.....	6
T.K. Electronics.....	4
Watford Electronics.....	2, 3

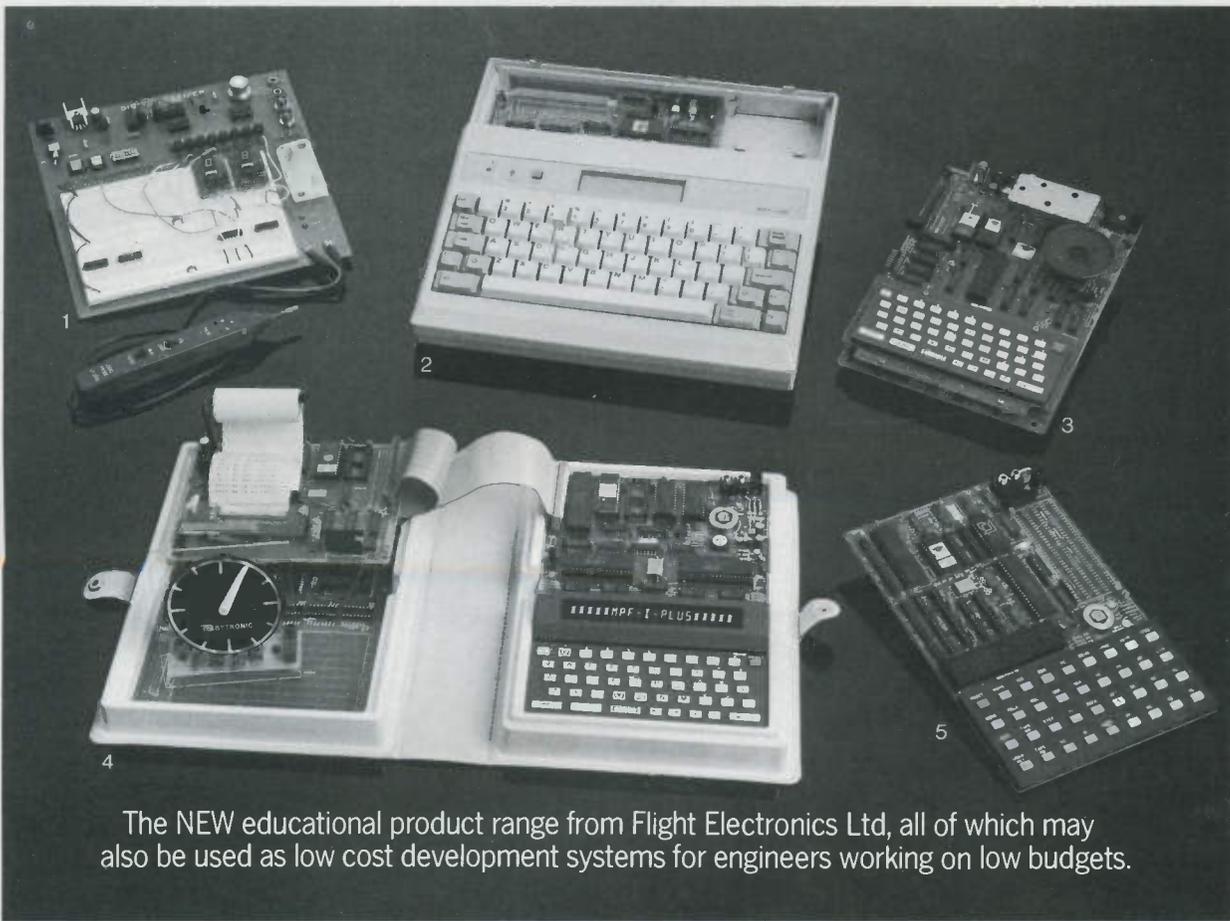

The NEW educational product range from Flight Electronics Ltd, all of which may also be used as low cost development systems for engineers working on low budgets.

#### 1 DT-01 Digital Trainer

For breadboarding, digital circuits, flip-flops and monostable multivibrators, counters, encoders, decoders, multiplexers, demultiplexers and sequencers, registers, LED and 7 SEGMENTS LED displays, memory devices, etc.

#### SPECIFICATION

AC ADAPTOR JACK: I/P DC +12V, 800mA.  
 POWER SW: AC ADAPTOR.  
 BATTERY: 1.5V x 4  
 PULSE SW: Two bounce-free pushbuttons.  
 LOGIC SW: Eight logic level switches in DIP type.  
 DC O/P: DC +5V, 750mA for user.  
 B-023 BREADBOARD: Solderless breadboard with 1580 interconnected tie points.  
 CLIP TERMINAL: Logic probe clip terminal.  
 BATTERY HOLDER: 1.5V x 4.  
 LED DISPLAY: Eight LED buffered logic level indicators.  
 BNC JACKS.  
 SELECT SW: Clock range selection.  
 LOW: 10 - 40 HZ.  
 HIGH: 1K - 20K HZ.  
 BANANA JACKS.  
 CLOCK ADJ: Fine adj. of clock frequency.  
 Includes Logic Probe.

#### 2 MPF-1/88

#### SPECIFICATION

MICROPROCESSOR: 16 bit CPU, Intel 8088, 4.77 MHz version with an 8-bit data bus.  
 RAM MEMORY: 4K standard RAM on two 2K byte RAM chips. Expandable to 24K by using three 8K byte RAM chips.  
 ROM MEMORY: 16K standard ROM on two 8K byte ROM chips. Expandable to 48K by using three 16K byte ROM chips.  
 ROM memory contains program code for the monitor, line assembler, and disassembler.  
 DISPLAY SCREEN: 20 character x 2 line LCD display shows any 2 lines of a 20 character x 24 line logical screen.  
 KEYBOARD: 59-key, full-size QWERTY keyboard.  
 PRINTER INTERFACE: Centronics standard parallel interface with 16-pin connector.  
 CASSETTE INTERFACE: Can be used with any monaural cassette recorder.  
 RECORDING SPEED: 1000-2000 bits/second.  
 BUS CONNECTOR: 62-pin IBM

#### 3 MPF-1/65

#### SPECIFICATION

ADVANCED INTERACTIVE MONITOR: The heart of the MPF-1/65 software resides in 16K bytes of ROM.  
 DISASSEMBLER: The built-in disassembler allows the user to list 6502 microprocessor instructions on both printer and video display.  
 SCREEN EDITOR.  
 TEXT EDITOR.  
 TWO PASS ASSEMBLER.  
 PRINTER DRIVER.  
 DEBUGGING FEATURES.  
 INPUTS AND OUTPUTS  
 AUDIO SPEAKER.  
 AUDIO CASSETTE INTERFACE: 1000-Baud  
 PARALLEL PRINTER INTERFACE: Centronics/EPSON  
 VIDEO MONITOR INTERFACE.  
 COLOUR TV INTERFACE.  
 SYSTEM EXPANSION CONNECTOR: 50 pin connector to provide Interface with RS-232c or ROM cartridges.  
 KEYBOARD: Standard calculator 49 key keyboard with 153 ASCII codes.  
 PROFESSIONAL DOCUMENTATION: User's Manual and Monitor Source Code Listing Manual are standard.

#### 4 MPF-1P

#### SPECIFICATION

Z80 CPU high performance microprocessor with 158 instructions.  
 4K RAM, Battery Back-up circuits provided for the user to keep the contents of the RAMs.  
 8K ROM, sophisticated monitor expandable to 16K.  
 8K of sophisticated monitor, including text editor, two pass assembler, line assembler, break point, system initialization, keyboard scan, display scan, tape write and tape read, register and memory modification, insert, delete, move relation, fill and step execution.  
 20 digits, 14-segment green phosphorescent display.  
 49-key alphanumeric keyboard including editing and functional keys.  
 Audio cassette interface: 165 baud average rate for data transfer between memory and cassette  
 Extension connectors: all CPU buses usable for expansion.  
 2.25" diameter speaker.  
 9V, 1.0A adaptor provided.  
 Three complete self-learning textbooks with experiments and applications.

#### 5 MPF-1B

#### SPECIFICATION

CPU: Z80 CPU high performance microprocessor with 158 instructions.  
 RAM: 2K bytes expandable to 4K bytes.  
 ROM: 2K bytes of sophisticated monitor expandable to 8K bytes.  
 INPUT/OUTPUT: 24 system I/O lines.  
 MONITOR: 2K bytes of sophisticated monitor. Monitor includes system initialization, keyboard scan, display scan, tape write and tape read.  
 DISPLAY: 6-digit, 0.5" red LED display.  
 AUDIO CASSETTE INTERFACE: 165-Baud  
 EXPANSION FACILITY:  
 Z80-P10 16 uncommitted lines.  
 Z80-CTC 4 uncommitted timer channels.  
 USER AREA: Provides a 3.5" x 1.36" wire wrapping area for user's expansion.  
 POWER REQUIREMENT: 9V, 1.0A adaptor is provided.  
 KEYBOARD: 36 keys including 19 function keys, 16 hex digit keys, and 1 user-defined key.

**Multitech**

## FLIGHT ELECTRONICS LTD

Flight House, Quayside Road, Bitterne Manor, Southampton, Hampshire SO2 4AD.  
 Telephone (0703) 34003/227721. Telex 477793 KEMPSA G.

## More This Month at Maplin

Colour-coded IDC cables

- 16-way (XR80B) ONLY 32p per metre.
- 20-way (XR81C) ONLY 40p per metre.
- 26-way (XR82D) ONLY 54p per metre.
- 34-way (XR83E) ONLY 70p per metre.
- 40-way (XR84F) ONLY 82p per metre.
- 50-way (XR85G) ONLY 99p per metre.
- 4-way flat flexible telephone lead (XR86T) ONLY 18p per metre.

Stepper motor 48 steps/rev, 12V 0.13A per phase, 4-phase unipolar, 57g, working torque 8mNm max. ONLY £9.95 (FT73Q).

Driver chip for motor: SAA1027 ONLY £3.75 (QY76H).

★SAVE★ 1 Kit containing everything you need: motor, SAA1027, data sheet and passives ONLY £13.35 (LK76H).

## Sounds Terrific



Professional Quality High Power Loudspeakers featuring:

- ★ Virtually indestructible high-temperature voice-coil reinforced with glass-fibre.
- ★ 100% heat overload tolerance.
- ★ Advanced technology magnet system.
- ★ Rigid cast alloy chassis.
- ★ Linen or Plastiflex elastomer surrounds.
- ★ 5-year guarantee (in addition to statutory rights).

Prices from £18.95. Send S.A.E. for our free leaflet XH62S.


## Top Ten Kits



THIS/LAST MONTH	DESCRIPTION	CODE	PRICE	BOOK
1. (1)	Live-Wire Detector	LK63T	£2.95	14 XA14Q
2. (2)	75W Mosfet Amp.	LW51F	£15.95	Best E&MM
3. (3)	Cor Burglar Alarm	LW78K	£7.49	4 XA04E
4. (7)	Logic Probe	LK13P	£10.95	8 XA08J
5. (5)	U/Sonic Intruder Dcttr	LW83E	£10.95	4 XA04E
6. (4)	Portyrite	LW93B	£10.95	Best of E & MM
7. (6)	8W Amplifier	LW36P	£4.95	Corologue
8. (-)	Noise Gate	LK43W	£9.95	Best E&MM
9. (9)	Computodrum	LK52G	£9.95	12 XA12N
10. (-)	DXer's Audio Processor	LK05F	£9.85	7 XA07H

Over 100 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.
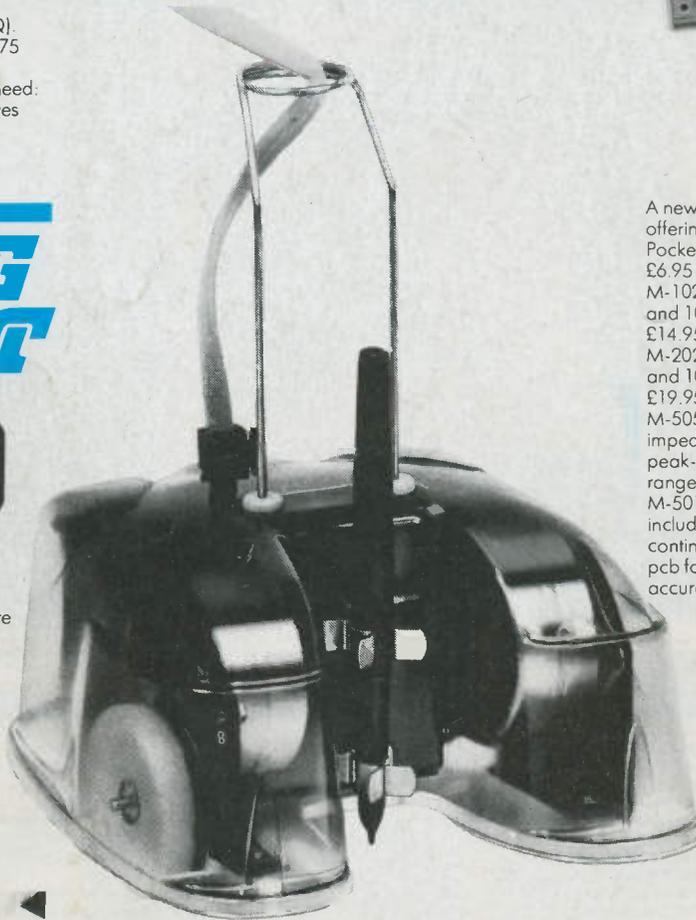
# Is it a turtle? Is it a robot? Is it a buggy? Yes! it's Zero 2.



- May be used by any computer with RS232 facility.
- Stepper Motor controlled.
- Half millimetre/half degree resolution.
- Uses ordinary felt-tip pens.
- Built-in 2-tone horn, line-follower. LED indicators.

The Zero 2 Robot is the first truly micro robotic system available and remarkably it costs less than £80. Complete kit (only mechanical construction required) £79.95 (LK66W). Full details of power supply and simple interfacing for BBC, Commodore 64 and Spectrum, in Maplin Magazine 15 price 75p (XA15R).

# MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD

Mail-order: P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Telephone: Southend (0702) 552911

SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356-7292.
- LONDON 159-161 King Street, Hammersmith, W6. Telephone: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevois Valley Road. Tel: 0703-225831
- SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Telephone: 0702-554000. Shops closed all day Monday.

## More Choice In Multimeters



A new range of very high quality multimeters offering truly amazing quality at the price. Pocket Multimeter, 16 ranges, 2,000Ω/V DC/AC £6.95 (YJ06G)

M-102BZ with continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95 (YJ07H)

M-2020S with transistor, diode and LED tester and 10A DC range, 27 ranges, 20,000Ω/V DC £19.95 (YJ08J)

M-5050E Electronic Multimeter with very high impedance FET input, 53 ranges, including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95 (YJ09K)

M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated pcb for long-term reliability and consistent high accuracy (0.25% +1 digit DCV) £42.50 (YJ10L)



## Top Ten Books

1. (1)	Loudspeaker Enclosure Design and Construction	WM82D	£3.25
2. (4)	Mostering Electronics	WM60Q	£4.70
3. (3)	Remote Control Projects	XW39N	£2.75
4. (9)	How to Build Your Own Solid State Oscilloscope	XW07H	£2.10
5. (5)	International Transistor Equivalents guide	WG30H	£3.25
6. (8)	How to Design and Make Your Own PCBs	WK63T	£2.05
7. (2)	Power Supply Projects	XW52G	£2.10
8. (-)	Rodio Control for Beginners	XW66W	£1.95
9. (-)	How to Use Op-amps	WA29G	£2.45
10. (7)	Electronic Synthesiser Projects	XW68Y	£1.95

## The Maplin Service

All in-stock goods despatched same day for all orders received before 2.00 pm.

All our prices include VAT and carriage (first class up to 750g).

A 50p handling charge must be added if your total order is less than £5.00 on mail-order (except catalogue).



☎ Phone before 2.00 p.m. for same day despatch.

All offers subject to availability.

Prices firm until 9th November 1985.