

PRACTICAL

JUNE 1989 • £1.25

ELECTRONICS

SCIENCE & TECHNOLOGY

BOATING REVOLUTION!

Ruling the micro waves

**8 EXTRA PAGES
IN OUR NEW LOOK
ISSUE!**

METRONOME DELUXE

**Build the beats
for precision**

SOLAR HEATING CONTROLLER


**Let the
sun get
you into
hot water**

SATELLITE SIGHTING

Dishing in the signals

**PLUS
ANOTHER
EASI-BUILD
PROJECT!**

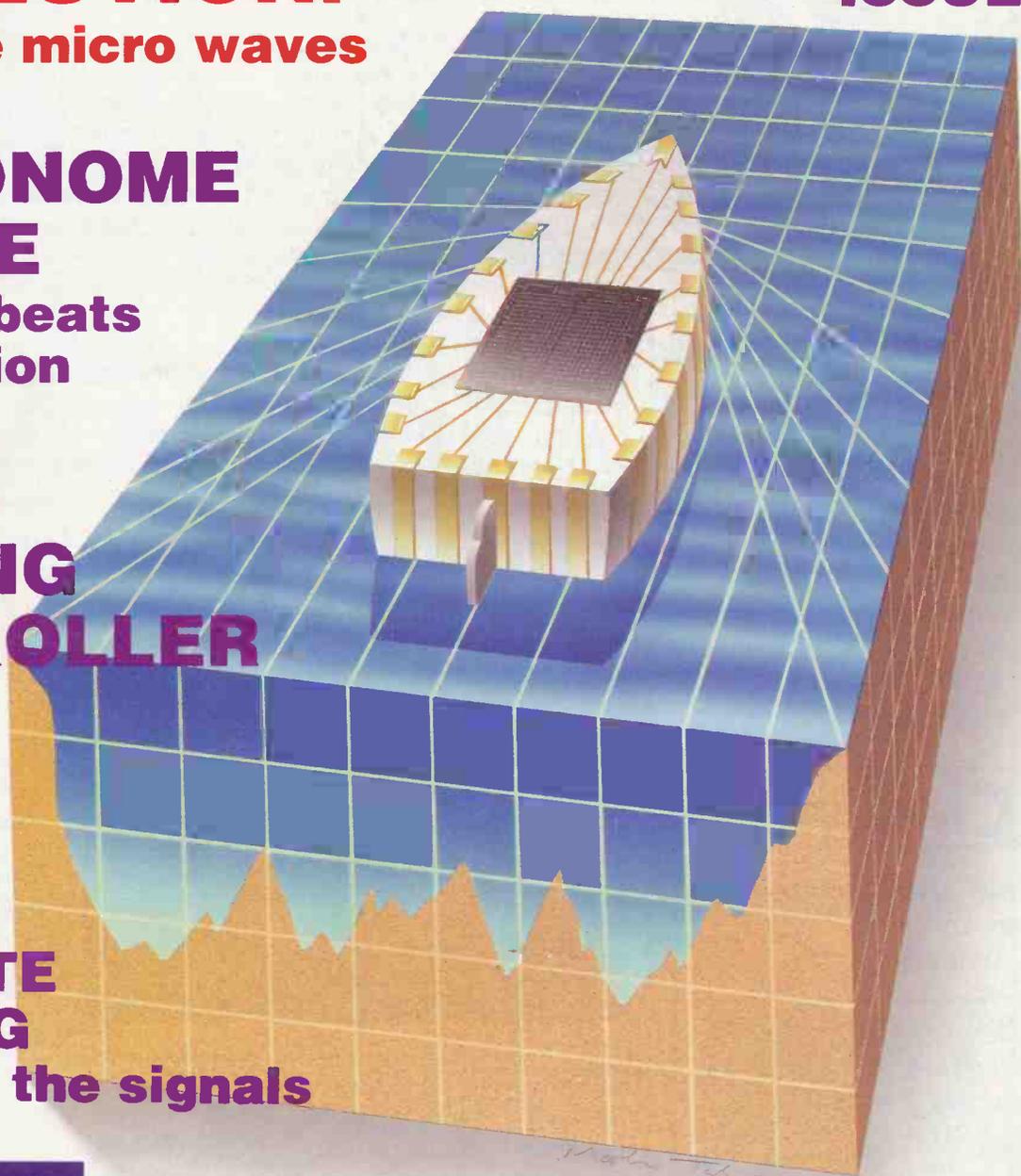**TRUE RMS METER
Rooting out meanness
in metering**



Cirkit NEWS

YOUR CHANCE TO WIN...



Once again, you'll need all your wits about you to identify the six items we've picked from the catalogue, and a Lodestar audio signal generator worth more than £180.00 is waiting for the sender of the first all-correct entry drawn in this season's competition.

Second and third prizes are top-of-the range multimeters from Cirkit's outstanding new range, offering frequency and capacitance measurement and transistor test, and valued at £55.00 each.

Fourth and fifth prize-winners will receive recently published books to the value of £30.00.

Cirkit

Cirkit Distribution Ltd

Park Lane
Broxbourne
Herts
EN10 7NQ
Telephone (0992) 444111
Fax (0992) 669021


Also at

53 Burrfields Road
Portsmouth
Hants
PO3 5EB
Telephone (0705) 669021
Fax (0705) 695485


NEW CATALOGUE OUT 25th MAY

Over 3,000 product lines feature in the Summer 1989 edition of the Cirkit Constructors' Catalogue, available from most larger newsagents or direct from the company priced at £1.50. The latest books, an RF frequency meter, two new PSU designs and a 3.5MHz converter are among the innovative new kits this issue, while our construction project - a 2 Watt stereo amplifier - is bound to prove an absorbing activity for dedicated constructors. In the test equipment section there's a whole new range of multimeters, a bench DVM and a triple output PSU.

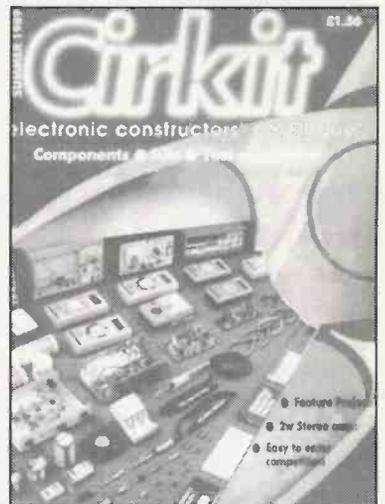For eagle-eyed readers who enjoy a challenge of a different sort, there is the opportunity of winning an audio signal generator worth more than £180.00 in the latest fiendish competition. All prices now include VAT for quicker, easier ordering; and Cirkit's same-day despatch of all orders, combined with value-for-money discount vouchers, makes the line-up even more attractive.




D-MM GOOD VALUE!

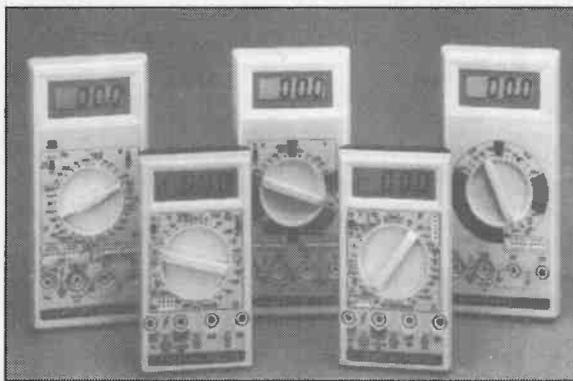

Cirkit's six new digital multimeters are packed with sophisticated extra facilities: capacitance measurement, frequency measurement up to 20MHz, temperature reading, transistor test and logic test in addition to the usual volts, current (DC and AC) and resistance measurement - and all unbeatable value with prices ranging from **£20.00** to **£55.00!**

FEATURE PROJECT: 2W STEREO AMP

Our construction project this issue is for a straightforward but very effective 2 Watt stereo amplifier. Based on the LM1877, it is the perfect amplifier for a 'Walkman' cassette deck and equally suitable for AM/FM radios or mixer desks. Featuring 2W per channel and 75dB channel separation, it operates from a 10-26 volt supply, making it ideal for in-car applications. The catalogue includes full details of this economical kit.

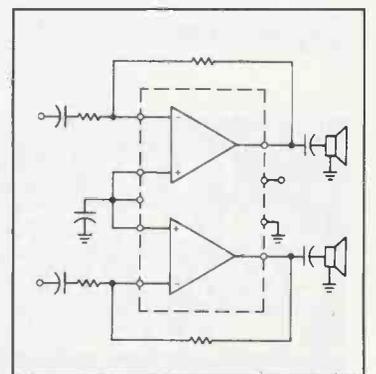

PRACTICAL ELECTRONICS

VOL 25 NO 6

JUNE 1989

CONTENTS

COMPETITION

- ASTRA TV AERIALS - THE WINNERS**.....36
Who's won flat aerials for Astra tv, and how geared up you all are!

CONSTRUCTIONAL PROJECTS

- DELUXE METRONOME by Robert Penfold**12
Musicians not content with common time can now keep their tempos well tempered with a tempus perfectum constructum!
- SOLAR HEATING CONTROLLER by Andrew Williams**...27
Hot under the collar about your heating bills? Let the sun contribute to the family coffers and you'll really end up in hot water!
- DIGITAL ELECTRONICS by Owen Bishop**.....32
Logically progressing from the principles behind data chips, Owen puts them on the bus and examines their roles in computer systems.
- TRUE RMS METER by Rod Cooper** 49
The problems of power measurement for unusual waveforms are thoroughly examined and a constructional solution presented.
- EASI-BUILD CIRCUIT by John Becker**57
Another in the new series of useful simple projects that you can build in your idle moments. It's a Wheeby-Jeeby siren circuit this month!

SPECIAL FEATURES

- BOATING REVOLUTION by John Becker**19
Even the humblest messer-about-in-boats can join the revolution afloat now that micro electronics begin to rule the waves.
- SATELLITES - Signal Reception by Tom Ivall**..... 40
Maximising satellite tv signal power and the vital requirements for satisfactory aerial alignment.

REGULAR FEATURES

- EDITORIAL** by John Becker - Micro greenery9
- LEADING EDGE** by Barry Fox - Stereo confusion8
- SPACEWATCH** by Dr Patrick Moore - Pulsars and lunar outbursts. 46
- INDUSTRY NOTEBOOK** by Tom Ivall - Mips for the minority 65
- READERS' LETTERS** - and a few answers 31
- TRACK CENTRE** - the pcb track layout page 54
- MARKETPLACE** - what's new, where and when4

PRODUCT FEATURES

- BOOKMARK** - your Ed looks at some new books38
- ARMCHAIR BOOKSHOP** - a haven for practical bookworms 66
- PCB SERVICE** - professional PCBs for PE Projects68
- BAZAAR** - Readers' FREE advertising service69
- ADVERTISERS' INDEX** - locating favourite stockists.....70

PE TAKES TECHNOLOGY FURTHER - BE PART OF IT!




Page 19 ▲

▼ Page 12



Page 5 ▼

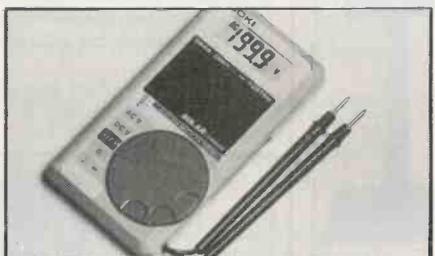

NEXT MONTH

Codes are the tools of trade for spy catchers, city slickers and hi-tech hackers - we reveal the cryptic low down on Encryption. That sinking feeling when timing slides to tape will sync without trace when you've built our Projector-Recorder Synchroniser. And you needn't get your fingers burnt if you use our Electronic Thumb heat monitor. That's just for starters, there's even more great interest lined up for the July 1989 issue.

- ★ PLUS ANOTHER GREAT COMPETITION TO ENTER!
- ★ DON'T MISS OUR JULY 1989 ISSUE
- ★ ON SALE FROM FRIDAY JUNE 2ND
- ★ AND STILL AT ONLY £1.25
- ★ YOU CAN'T BEAT OUR VALUE
- ★ OR OUR NEW GOOD LOOKS!

MONITORING REVOLUTION

Ferguson has launched a revolutionary new range of monitor-style sets, where design and advanced technology are the watchwords.

There are four new "K-Series" sets in 51 cm and 59 cm presentations: the 51K7, with Fastext (fast access teletext); and the 51K5 and 59K5, additionally featuring on board NICAM digital stereo decoders.

The new Super Planar Black Matrix Tubes with anti-reflective screen – (featured on 59 cm models) – provide significant improvements in picture quality. Stereo twin speakers give superior sound, and on the 51K5 and 59K5 models, the on board NICAM digital stereo decoders will provide the benefit of digital stereo sound when broadcasting commences in 1989.

Super Planar picture tubes are simply the flattest TV tubes available, offering a perceptibly wider viewing angle and larger screen area to FST models.

All models include tv/video remote control handsets that access on screen graphics, the display giving instant information on volume, colour, brightness, contrast and channel status. Another feature of On Screen Graphics is "Child Lock". Other standard features



include: 40 programme frequency synthesis tuning; led displays; a headphone socket; and a Peritel socket.

The 51K7 and 59K7 will retail at around £429.99 and £499.99 respectively. The NICAM digital

stereo models, the 51K5 and 59K5, will retail at around £529.99 and £599.99 respectively.

CONTACT: Anne Waterman, Ferguson Limited, Great Cambridge Road, Enfield, Middx. EN1 1UL. Tel: 01-363 5353.

Micro Thermometer

Temperature trend indication on the Keithley 820 thermometer automatically registers increasing, decreasing or stable temperature readings. Never again need there be a doubt about when to take a reading.


Features like microprocessor control, 0.1 accuracy and 0.1 degree (°F and °C) resolution throughout its full measurement range, coupled with high repeatability, render precision measurements for any application. Dual point measurements via the two thermocouple inputs permit easy two point comparison. With six data logging registers, the 820 stores the maximum and minimum temperature readings for both inputs, and simultaneously retains maximum and minimum differential readings.

The 820 is protected with a drop proof, splash proof, dust free case that features a built-in tilt stand/hanger for bench use or hands free, plus an AC adapter socket.

CONTACT: Keithley Instruments, 1/3 Boulton Road, Reading, RG2 0NH. Tel: 0734 861287



CATALOGUE

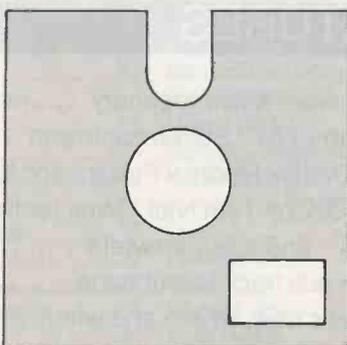

DATABASE


We have recently received the following literature:

Wotan are a company who specialise in electronic lamps. Their products include a range of miniature fluorescent lamps that will be of interest to anyone who wishes to contribute to the green welfare of society by consuming less power. Although the lamps are not yet too readily available in retail shops, I acquired information from Wotan when they were exhibiting at the Ideal Home Exhibition in March. If you are interested in obtaining information on the availability of these lamps contact **Wotan Lamps Ltd**, Wotan House, 1 Gresham Way, Durnsford Road, London SW19 8HU. Tel: 01-947 1261.

Greenweld's new Spring supplement is now available and will be of great interest to all electronics constructors. It's got 32 well filled pages covering many great lines, including a whole new range of exciting products, such as sophisticated calculators, disco and music gear, Metex meters, leads and high power speakers. There's an enticing list of surplus lines at bargain prices as well - Greenweld are famous for such offers! Not only that, but there's a great competition to enter with a top of the range Metex multimeter as first prize. Another fantastic offer is that with every order over £10 a free set of headphones and speakers are yours for the asking. Don't miss out on these great offers - send a large sae for a copy of this supplement to **Greenweld Electronics Ltd**, 443c Millbrook Road, Southampton, SO1 0HX. Tel: 0703 772501.

Maplin have a catalogue that will be of interest to professional electronics buyers. Their latest electronic component buyer's encyclopaedia is a forty page colourful source of essential products at reasonable prices which fall even further the more you buy of each product. This latest edition has over 800 new products including a wide range of transistors, digital and analogue ics, diodes, crystals, and a superb range of top quality Antex soldering irons. There is also a good range of aerosol and service aids from Electrolube. It is good to know that these aerosols are free of CFCs and will not affect the ozone layer. If you are a professional electronics buyer you owe it to yourself to immediately ask for a copy of this catalogue from **Maplin Professional Supplies**, PO Box 777, Rayleigh, Essex, SS6 8LU. Tel: 0702 552961.

It's always a pleasure to receive the latest news letter from BAE, the British Amateur Electronics Club. Their latest edition has just come in (I assume it's the latest even though it's dated "Fourth Quarter 1988") and as usual has plenty of good advice and tips, this time mainly relating to microprocessors. If you don't already belong, you really ought to join this nationwide club, I am sure that you will benefit from the experience of sharing electronics with others of similar interests. For further information write to the Chairman, B.A.E.C., C.Bogod, 26 Forrest Road, Penarth, South Glamorgan. And do please enclose an sae to cover the postage of his reply.

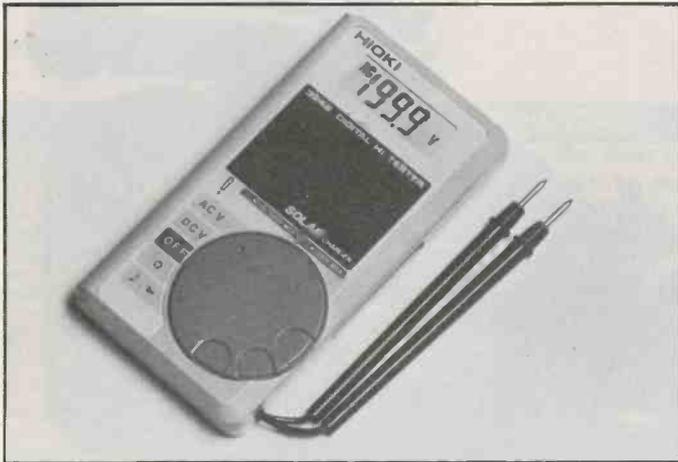

Solar Powered DMM


Universal Instruments have announced the availability of a pocket-size digital multimeter with an internal power cell that is automatically recharged by solar powered to give continuous use without the need for regular battery replacement.

The Hioki model 3242 is an easy to operate autoranging instrument with a single rotary switch and a 3 1/2 digit liquid crystal display showing units and symbols of measurement and polarity. DC voltage is measure from 0.1mV to 500V in 5 ranges with a basic accuracy of better than 1%, whilst ac voltage is from 1mV to 500V and input impedances are greater than 10M ohms. Resistance is from 0.1 to

20M ohms in six ranges plus audible and visual continuity and all are protected to 250V.

This compact hand held instrument measures just 120 x 65 x 18mm, which includes a fully enclosed test lead storage compartment, and weighs approximately 100 gms. Fully guaranteed for 12 months the latest Hioki innovation is supplied ready for use with a transparent vinyl storage case that allows the battery to be recharged even when the unit is not in use.

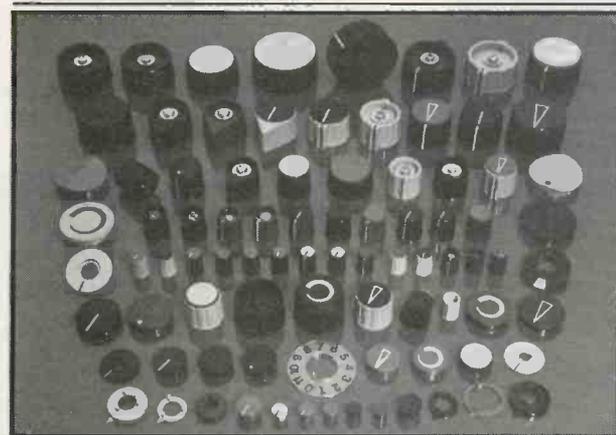CONTACT: Universal Instrument Services Ltd. Unit 62. GEC Site, Cambridge Road, Whetstone, Leicester, LE8 3LH. Tel: 0533 750123.



KNOBS FOR MORE JOBS

Comprising a variety of diameters ranging from 8mm to 45mm, in four basic colours, Bulgin's expanded Multi range has a choice of collet (four colours) or push-fit (two colours) versions, making it one of the most versatile selections of control knobs available on the market.

Among the many advantages offered are pre-loaded collets which obviate the need to loosen screws before fitting - the control knobs are simply pushed on and the screw tightened. They are supplied with slotted head fixing screws as standard. Wing- and arrow-shaped formats



If you are organising any event to do with electronics, big or small, drop us a line - we shall be glad to include it here.

Please note: Some events listed here may be trade or restricted category only. Also, we cannot guarantee information accuracy, so check details with the organisers before setting out.

May 8-10. Eurobus 89 - German Conference. Munich Sheraton Hotel, Munich. 01-940 4625.

May 9-12. Automan. Robotics and automation exhibition. NEC, Birmingham. 01-891 5051.

May 31-Jun 2. Computer Training Show. Olympia 2, London. 01-486 1951.

Jun. 5-9. Lasers, Optoelectronics, Microwaves. 9th International Trade Fair and Congress. Munich Fair Centre. 01-948 5166.

Jun. 6-8. Computer North. G-Mex, Manchester. 061 832 4242.

Jun. 13-15. Software Tools 89. Wembley Conference Centre. 01-868 4466.

Jun. 14-15. Instrumentation Scotland. The Forum, Livingstone. 0822 614671.

Jul. 10-13. EWEC '89. European wind energy conference and exhibition. Scottish Conference and Exhibition Centre, Glasgow. No reference tel. known.

Jul. 24-26. Vacuum Microelectronics - 2nd International Conference. Bath. Contact Dr R.A. Lee. GEC Hirst Research Centre, Wembley, Middx. HA9 7PP. 01-908 9000.

Aug. 25-Sep 3. International Audio and Video Fair. Berlin. 01-408 0111.

Sep. 4-6. Eurobus 89 - UK Conference. Novotel Hotel, London. 01-940 4625.

Sep. 12-15. EPOS 89. The World's largest exhibition of retail information systems. Alexandra Palace, London. RMDP. 0273 722687.

Oct. 16-20. Systems, Computers and Communications. 11th International Trade Fair and Congress. Munich Trade Fair Centre. 01-948 5166.

Oct. 24-26. Sensors and Systems - International Transducer Exhibition and Conference. Wembley Conference Centre. 0822 614671.

are available in addition to traditional round models and a low profile version with its height reduced by approximately 20 per cent is available, making it particularly suitable for all instrument construction.

The range may be further individualised with a comprehensive selection of caps in various shapes and colours and a variety of markings. These can be snapped into position and are supplied in three basic models

- flat, prismatic or curved - in blue, yellow, green, metallic (flat only), light grey, dark grey, black and red. The flat caps may be marked with an indicator line, arrow, curved arrow or an aluminium disc; prismatic caps with a distinctive point; and curved caps with an indicator line; or left unmarked as required.

Contact: A.F. Bulgin and Co PLC, Bypass Road, Barking, Essex IG11 0AZ. Tel: 01-594 5588.

CAM-ZOOM DEBUT



Announced as the world's first VHS-C camcorder with a built in 12x variable speed power zoom fl.6 lens, Sharp's high-performance VL-C750H has made its UK debut.

The newcomer shares a range of features with Sharp's previous camcorder introductions, the well-received 8x power zoom VL-C650H - including a one-touch full auto system with full information lcd display, a 1/1000th sec high speed electronic shutter, a 0.5-inch solid state ccd image sensor and high quality picture system, fade control,

self timer and palm fit grip design.

The 12x variable speed power zoom is the big feature of the new camcorder, offering the possibility of a "swoop" close-up from 1x to 12x in just six seconds or a more controlled zoom in 25 seconds. It has a macro capability, too.

The lcd display offers easy at-a-glance information covering not only the "full auto on" symbol but also warnings of low battery charge, excess dew or a cassette with no tab or no tape time remaining.

Recording mode (sp/lp), lap time/tape counter, tape speed, focus mode, white balance and shutter speed mode symbols are displayed as well.

Editing functions catered for include flying erase head, audio-video fade in/fade out and audio dubbing, the latter permitting creative background sound effects and/or voice over.

Other key features are the camcorder's VHS index search system - which enables the user to set index points on the tape for rapid

location of specific sequences for playback or editing - and the ability to tilt the electronic viewfinder for low angle shooting.

Incorporating a directional electret condenser microphone, the VL-C750H measures 131mm wide, 157mm high, 301mm deep and weighs 1.5 kg (without battery).

For further information contact: Sharp Electronics (UK) Ltd., Sharp House, Thorp Road, Newton Heath, Manchester M10 9BE. Tel: 061-205 2333.

DUETTO FOR UNO

A new concept in speaker design is an event. To produce a stereo sound-stage from a single cabinet has been a goal for speaker designers for many years.

After 15 years painstaking research and testing Walter Schupbach has achieved that goal, resulting in the Stereolith "Duetto" system.

The Duetto drive units are arranged on either side of a prism shaped cabinet, and can be placed in front of the listener, either at floor level or suspended from the ceiling. The resulting sound stage places the musical instruments both in the horizontal and vertical planes, over the full width of the listening room, without the need for being in a "sweet spot" for maximum effect.

Not only is the system suitable for hifi listening it will also enhance the stereo capabilities of pre-recorded software with television sets, video recorders and video disc players, as well as facilitate the use of surround sound, and can be used in any location where a pair of conventional speakers is aesthetically unacceptable.

The Duetto is available in either black or white, with a choice of either matt or piano lacquer finish, at prices from around £400.

For more information please contact: F.W.O. Bauch Ltd., 49 Theobald Street, Boreham Wood, Hertfordshire WD6 4RZ. Tel: 01-953 0091.



DIAL-A-CHIP

Electronic designers can now, at the touch of a button, not only select the components they need, but order them direct from stockists, in a new development of Dialcom's Password electronics database service.

This expansion of the service allows buyers to access information on stock levels and prices for components in the UK, and then use Telecom Gold, British Telecom's electronic mail service, to order them from the distributor.

The development follows the decision of Macro Marketing, one of

the UK's largest semiconductor trade distributors, to provide Password with data on its entire stock of more than 30,000 components. Information on price and availability is up-dated daily from Macro's Tandem computers to Password's cluster of Pyramid super-mini machines in London.

New features of the service include the ability to search by manufacturer or part number, view up to six price breaks for quantity discount and list alternate parts that meet the specification criteria if stocks are low or out.

NATTY IDEAS WANTED

At West Bank and British Petroleum are launching a joint award scheme to help people put their innovative technological (and, of course, electronic!) ideas into practice.

The aim of the awards is to help with the cost of development in order to turn an idea into a commercially viable proposition. The judges will make bi-monthly awards up to a maximum of £2,000 per successful entry.

For details and application forms phone NatWest on 01-374 3643.

Mr. Bill Noseworthy, Dialcom's Head of Design and Engineering Services, is delighted with the new development. He commented: "It provides the basis for a sophisticated 'trading floor' that brings suppliers and buyers into electronic communication with one another. I am confident that other distributors will follow Macro's lead, and use Password as the mechanism for trading with their customers in the future."

Companies interested in accessing the Password range of services can call Dialcom free on 0800 200700, or Macro Marketing on 06286 4383.



Klippping Coax

The exact stripping of various coaxial cable types using standard tools is a time-consuming procedure involving the adaption of the tool to suit different requirements.

Following intensive research, Klippon has introduced the CST Insulation Stripping Tool for cables measuring 2.5 to 8.00mm diameter. It allows 2 or 3 stage insulation and braid stripping in a single cycle – reducing the stripping and setting times considerably. It also enables

the user to record the individual setting once it has been established.

Important features include an exchangeable screw holder which acts as a 'memory' various sized cassettes with standard cutter spacings and colour coding for easy identification. Weighing just 65g, the CST measure just 100mm x 42mm x 25mm.

CONTACT: John Bauckham, Klippon Electronics Ltd., Power Station Road, Sheerness, Kent, ME12 3AB. Tel: 0795 580999

Digitape

Solex have introduced a couple of feature-packed ultrasonic tapeless measure, the UR2000 and UR3000.

These two compact units incorporate a host of features which seem set to make the humble tape measure completely redundant! A three mode display function enables readings to be obtained in either metric (to the nearest cm), imperial/metric (feet to two decimal places) or imperial (feet and inches) all clearly displayed on the large lcd. A memory recall facility will store the last reading entered even after the unit is switched off.

The UR3000 has a few extra

surprises in store – just enter the length, width, and height of a room using the unit's independent auto memories and, at the touch of a button, the cubic capacity or floor area of the room will be displayed. Both models have a range from 60cm to a full 10 metres with accuracy better than 1% of the reading.

Available on 14 days approval, the units are priced at just £29 + vat for the UR2000 and £49 + vat for the UR3000.

CONTACT: Steve Fenson, Sales and Marketing, Solex International, 95 Main Street, Broughton Astley, Leics, LE9 6RE. Tel: 0455 283486.

CHIP COUNT!

Highlighting some new semiconductor products.

INDEPENDENT AUDIO AMPS

Two new audio amplifier chips have been released that require no extra external components, apart from decoupling capacitors. The Philips TDA7052 and TDA7053 can deliver 1W mono or 2 x 1W stereo class-B audio output. These new chips feature a wide operating range, from 3V to 15V, and are the first low power consumer ics to incorporate bridge-tied load (BTL) configuration. Their typical quiescent currents are only 4mA and 9mA respectively, and neither chip requires a heat sink. With a fixed closed-loop voltage gain of 40dB, the TDA7052 connects to a mono speaker, while the TDA7053 is in fact two TDA7052s on a single crystal with compatible pinning, thus the same pcb design can be used for both stereo and mono amplifiers.

FASTEST 24-PIN PLD

Philips new programmable logic array PLUS173D features a worst case propagation delay of 12ns, and so exceeds the performance level of 24-pin PAL devices. The new device is made with two programmable arrays (AND and OR), thus providing a more flexible solution for complex combinatorial applications than PAL devices, which support programming only in the AND array. As a result, the PLUS173D can support an OR function of up to 32 inputs wide, compared to 7-input wide decoding functions on earlier devices. Another feature is its programmable output polarity, allowing each of its ten bi-directional in-out lines to be programmed active high or low.

SMALLEST 1M DRAM

With a chip area of only 40.5sq.mm, the Hitachi HM511000A and HM514256A are the world's smallest die for DRAMs. The smaller size of these die means that, compared with the currently available devices, some 55% more die can be obtained from a 6-inch wafer. This should result in increased production volumes of 1M DRAMs during 1989. Let's hope that increased yield on ranges like this will enable manufacturers to get back to producing more SRAMS – the international shortage still seems acute (have you tried to buy any lately?)

HIGH-PERFORMING MFLOPS

TI has disclosed a processor capable of 3million floating point operations per second (Mflops) in both single and double precision. With its exceptional performance, the SN74ACT8847 will allow supermini manufacturers to provide supercomputer performance in desktop systems, says Wally Rhines, executive vice president of TI's Semiconductor Group. The '8847 is the highest performance single chip floating point processor in the industry. When its multiplier and ALU operate in parallel, the chip can attain speeds of over 50Mflops. Such performance levels are critical to designs of future high-end systems such as minicomputers and 32-bit personal computers.

Manufacturer's details for further information

Hitachi Europe Ltd., 21 Upton Road, Watford, Herts, WD1 7TB, Tel: 0923 246488. Philips Components Ltd, Mullard House, Torrington Place, London WC1E 7HD, Tel: 01-580 6633. Texas Instruments Ltd., Manton Lane, Bedford, MK41 7PA, Tel: 0234 270111.



There is currently a great deal of confusion over stereo sound for video and tv.

The first VHS video recorder machines used a low fi linear track, and were mono.


Then the use of Dolby B improved sound quality a little.

Then some machines split the linear track into two halves to give stereo. This was an unsatisfactory system, because the half tracks are very narrow. So signal level is low, which aggravates this, and any tape weave causes one channel to disappear intermittently.

Then came hifi stereo, with the sound recorded as an fm signal by two extra heads on the rotating video head drum. This is called depth multiplex stereo because the sound and picture signals are interleaved in frequency and recorded at different depths in the tape coating.

To preserve compatibility, all hifi recorders also have linear sound heads; and all hifi tape recordings have both hifi and linear sound tracks. But to save on cost and complexity the linear sound heads on most

LEADING

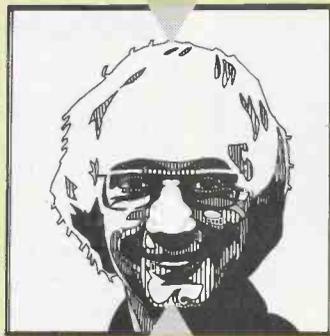

EDGE

Now Nicam chips are being incorporated into the latest stereo tv sets. The extra cost of providing Nicam is around £100 or £150, but it will come down as stereo becomes a familiar option.

No-one who has heard music programmes, films or sports broadcasts in Nicam can be in any doubt that the system works beautifully and adds considerably to the programme's impact.

In short, it would be crazy for anyone buying a new stereo tv or stereo vcr not to choose one which is either Nicam-ready, or can be easily retrofitted with Nicam chips.

DISHTRAUT

I have just heard something from a firm making satellite dishes that neatly sums up the appalling ignorance which currently abounds in the trade.

A dealer was taking orders for satellite systems ahead of the Astra launch, warning customers that if they did not pay a deposit

STEREO CONFUSION

(if not all) hifi machines are now mono, without Dolby. There is no need to provide stereo linear capability because virtually all the major duplicators now record stereo tapes in hifi.

Of course the duplicators also record a linear track, for compatibility with non-hifi machines. Some may record the linear track in stereo, for good measure, even though most non-hifi machines will play the linear track in mono only.

The trend to stereo has meant that many stereo tv sets have been sold over the last five years, with two sets of speakers and two amplifiers.

These sets are intended to reproduce the stereo sound available from pre-recorded video cassettes and video discs. With some clever connections, they can also reproduce simulcasts, where a radio station simultaneously broadcasts the stereo sound for a tv programme.

But these sets are *not* able to receive broadcast stereo in the new Nicam, all-digital system.

The Nicam broadcast stereo system was developed by the BBC, and there have been test transmissions on BBC1 and BBC2 from the Crystal Palace transmitters for the last two years. But, owing to cutbacks, the BBC has relinquished its lead and ITV will start the first Nicam service, from London and Yorkshire, this autumn. The BBC accountants (notably Director General Michael Checkland) will then have to face commercial reality and follow ITV.

Although Nicam receiver chips have become available over the last year (from Toshiba first, then Texas Instruments and Mullard/Philips) they have so far been used only in VHS video recorders – mainly from JVC.

BY BARRY FOX
Winner of the
UK Technology Press Award

While satellite TV hogs the headlines, another television revolution has happened quietly – Nicam stereo is here to stay.

in advance they would not get a dish "before June".


Sensibly, the sales staff were asking customers where they intended to put their dish and advising them on whether they would be able to get a line of sight on the Astra satellite.

But, until the mistake was discovered, one salesman had for weeks been telling customers that as long as they had a North-facing wall they would be able to receive Astra.

Exactly the opposite is true.

PE

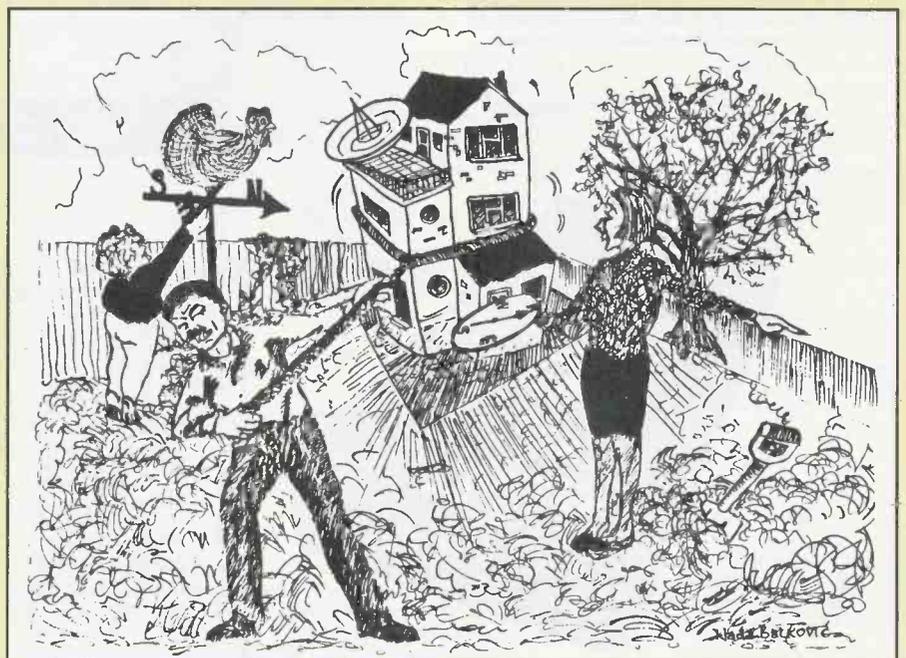Which leads us to speculate on what problems may arise from this mistake . . .



As yet there do not appear to be many ways in which PE can appropriately comment on ecological matters. Most aspects of electronics seem to be for the general good of society, though as 'green' issues become more thoroughly discussed, I expect that some areas of electronic production may come under scrutiny regarding environmental safety.

Take solder, for example. We are nationally becoming more conscious of the effect of lead upon the environment. Quite rightly we are in the process of encouraging the use of lead-free petrol, and I for one use it whenever possible. What about solder, though? It's an alloy consisting mainly of lead and tin. Although more usually the lead content is between 40% and 60%, it can be over 90% in some types. I get through about 2.5kg a year. Some of it probably ends up in the atmosphere simply from the fumes produced when soldering. Eventually, in years to come, the rest of this solder will end up discarded on a refuse tip. Surely this is a further source of lead pollution? And if I'm polluting the environment, what about manufacturers of electronic equipment? Think of the solder quantities they must use, all of which will sometime end up discarded. But what choice is there? Or am I misinterpreting the polluting effect of lead?

PRACTICAL ELECTRONICS



EDITORIAL

How about ferric chloride as used for etching the copper from pcbs? Where does that end up when discarded? I'll bet you don't take yours down to an approved disposal site. You'll no doubt tip it down the drain, in common with many other people. Have you ever given thought to what that could ultimately do to the water supply? Remember that we are currently being informed that our water is not as pure as it should be. And even when etchant is disposed of "safely", as industrial pcb manufacturers will ensure, is it really safe? Perhaps it may be necessary to look for an environmentally safe pcb etchant.

I was pleased to report recently that one manufacturer, Philips, has started to make batteries whose electrolyte is relatively harmless when discarded. Other manufacturers will undoubtedly follow suit, hopefully with a totally harmless product. Wotan is another company concerned for the environment. They are conscious of how much power is wasted in lighting applications and have produced electronically controlled lamps which consume less power for a given light output. The lamps can be plugged into any normal light socket and are not much bigger than a standard light bulb. You will find a further reference to them in the catalogues section on page four.

On the consumer electronics front, we shall all increasingly become more aware of power consumption factors. One of the themes repeatedly referred to at the Home Automation conference, on which I reported in April and May, was that of microprocessor control of heating. It is also likely that manufacturers will soon be stating on their products how much power they consume. Hopefully, consumers will then buy equipment that maximises power efficiency as much as it does functionality.

I am maintaining a watchful look out for other electronically related environmental matters, and shall keep you informed.

THE EDITOR

Editor:

John Becker

Sub-Editor:

Helen Armstrong

Technical Illustrator:

Derek Gooding

Advertisement Sales:

Sarah Holtham

Business Manager:

Mary-Ann Hubers

Circulation:

David Hewett

Publisher:

Angelo Zgorelec

Editorial and Advertising Address:

Practical Electronics,
Intra House, 193 Uxbridge Road,
London W12 9RA
Tel: 01-743 8888
Telecom Gold: 87: SQQ567
Fax: 01-743 3062

Advertisements

All correspondence relating to advertise-



ments, including classified ads, should be addressed to: **The advertisement department, Practical Electronics, at the above address and telephone number.**

Readers' Enquiries

All editorial correspondence should be addressed to the editor and any letters requiring a reply should be accompanied by a stamped addressed envelope, or equivalent payment.

We regret that lengthy technical enquiries cannot be answered over the phone.

Subscription Address:

Practical Electronics, Subscription Dept.,
P.O. Box 500, Leicester LE99 0AA.

Annual Subscription Rates:

U.K. £15.00 Overseas £18.00

Cover Illustration

Mark Taylor

© Intra Press 1989. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. All material is accepted for publication on the express understanding that the contributor has the authority to permit us to do so. **ISSN 0032-6372**

Published on 1st Friday of each month by Intrapress, 193 Uxbridge Road, London W12 9RA. Typesetting, artwork and film by Gilfillan Ltd. Mitcham, Surrey and printed in England by McCorquodale Magazines Ltd. Andover, Hants. Distributed by Seymour Press 01-679 1899. PRACTICAL ELECTRONICS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

MAGENTA ELECTRONICS Ltd

PROJECT KITS

Magenta supply Full Kits: Including PCB's (or Stripboard), Hardware, Components, and Cases (unless stated). Please state Kit Reference Number, Kit Title and Price, when ordering. REPRINTS: If you do not have the issue of P.E. which includes the project, you will need to order the instruction reprint as an extra: 80p each. Reprints are also available separately - Send £1 in stamps. Magazine dates refer to Everyday Electronics.

REF NO.	KIT-TITLE	PRICE	REF NO.	KIT-TITLE	PRICE
812	ULTRASONIC PET SCARER May 89	£13.80	581	VIDEO GUARD Feb 87	£8.39
811	MIDI PEDAL Mar 89	£39.98	584	SPECTRUM SPEECH SYNTH. (no case) Feb 87	£20.92
810	MIDI MERGE Mar 89	£11.59	578	SPECTRUM I/O PORT less case Feb 87	£3.44
809	CALL ALERT Mar 89	£13.51	569	CAR ALARM Dec 86	£12.47
807	MINI PSU Feb 89	£22.71	563	200MHz DIG. FREQUENCY METER Nov 86	£62.98
806	CONTINUITY TESTER Feb 89	£10.28	561	LIGHT RIDER LAPEL BADGE Oct 86	£10.20
505	4 CHANNEL LIGHT DIMMER Feb 89	£37.99	560	LIGHT RIDER DISCO VERSION	£19.62
803	REACTION TIMER Dec. 88	£29.98	559	LIGHT RIDER 16 LED VERSION	£13.64
802	PHASOR (Light Controller) Dec 88	£25.61	556	INFRA-RED BEAM ALARM Sept 86	£28.35
801	DOWNBEAT METRONOME Dec. 88	£17.57	544	TILT ALARM July 86	£7.82
800	SPECTRUM EPROM PROGRAMMER Dec 88	£26.97	542	PERSONAL RADIO June 86	£11.53
796	SEASHELL SYNTHESIZER Nov 88	£24.99	528	PA AMPLIFIER May 86	£26.95
795	I.R. OBJECT COUNTER Nov 88	£29.63	523	STEREO REVERB Apr 86	£26.44
790	EPROM ERASER Oct 88	£24.95	513	BBC MIDI INTERFACE Mar 86	£27.94
786	UNIVERSAL NICAD CHARGER July 88	£6.99	512	MAINS TESTER & FUSE FINDER Mar 86	£8.82
780	CABLE & PIPE LOCATOR April 88	£15.35	497	MUSICAL DOOR BELL Jan 86	£18.72
775	ENVELOPE SHAPER Mar 88	£14.99	493	DIGITAL CAPACITANCE METER Dec 85	£41.55
769	VARIABLE 25V-2A BENCH POWER SUPPLY Feb 88	£49.73	481	SOLDERING IRON CONTROLLER Oct 85	£5.47
763	CAR LAMP CHECKING SYST. Feb 88	£7.10	464	STEPPER MOTOR INTERFACE FOR THE BBC	
739	AUDIO SIGNAL GENERATOR Dec 87	£13.64		COMPUTER less case Aug 85	£11.68
740	ACCENTED BEAT METRONOME Nov 87	£20.95		1035STEPPER MOTOR EXTRA	£14.50
744	VIDEO CONTROLLER Oct 87	£16.26		OPTIONAL POWER SUPPLY PARTS	£5.14
745	TRANSTEST Oct 87	£29.14	461	CONTINUITY TESTER July 85	£6.20
734	AUTOMATIC PORCH LIGHT Oct 87	£9.70	455	ELECTRONIC DOORBELL June 85	£7.56
736	STATIC MONITOR Oct 87	£17.17	453	GRAPHIC EQUALISER June 85	£26.94
723	ELECTRONIC MULTIMETER Sept. 87	£8.66	444	INSULATION TESTER Apr 85	£19.58
728	PERSONAL STEREO AMP Sept 87	£46.96	430	SPECTRUM AMPLIFIER Jan 85	£6.91
730	BURST-FIRE MAINS CONTROLLER Sept 87	£14.31	392	BBC MICRO AUDIO STORAGE SCOPE	
724	SUPER SOUND ADAPTOR Aug 87	£13.57		INTERFACE Nov 84	£36.25
718	3 BAND 1.6-300MHz RADIO Aug 87	£38.39	387	MAINS CABLE DETECTOR Oct 84	£5.53
719	BUCCANEER I.B. METAL DETECTOR inc. coils and case, less handle and hardware July 87	£26.53	386	DRILL SPEED CONTROLLER Oct 84	£8.68
720	DIGITAL COUNTER/FREQ METER (10MHz) inc. case July 87	£26.45	362	VARICAP AM RADIO May 84	£13.15
722	FERMOSTAT July 87	£26.45	337	BIOLOGICAL AMPLIFIER Jan 84	£24.14
711	VISUAL GUITAR Tuner Jun 87	£67.07	263	BUZZ OFF Mar 83	£5.68
715	MINI DISCO LIGHT Jun 87	£12.14	242	2-WAY INTERCOM no case July 82	£5.69
707	EQUALIZER (IONISER) May 87	£22.99	240	EGG TIMER June 82	£6.86
700	ACTIVE I/R BURGLAR ALARM Mar 87	£12.59	205	SUSTAIN UNIT Oct 81	£17.63
		£35.65	108	IN SITU TRANSISTOR TESTER Jun 78	£9.42
			106	WEIRD SOUND EFFECTS GEN Mar 78	£7.82
			101	ELECTRONIC DICE Mar 77	£6.26

TOP KITS

MOSFET VARIABLE BENCH 25V 2.5A POWER SUPPLY




A superb design giving 0-25V and 0-2.5A. Twin panel meters indicate Voltage and Current. Voltage is variable from zero to 25V. Current-Limit control allows Constant Current charging of NICAD batteries, and protects circuits from overload. A Toroidal transformer MOSFET power output device, and Quad op-amp IC design give excellent performance.

OUR KIT REF. 769 £49.73

COMPONENTS, KITS, BOOKS, TOOLS, MOTORS, GEARS, PULLEYS, OPTICAL FIBRES, ROBOTICS, AND MUCH MUCH MORE-IN OUR CATALOGUE £1.00

MOTOR-GEARBOX ASSEMBLIES

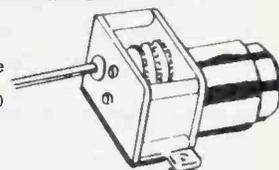Miniature gearboxes complete with quality electric motor. Variable ratios by fitting 1 to 6 gears. 1.5-4.5v, 3-2200 rpm. Long 3mm shaft. Ideal for robots and buggies.



SMALL (MGS) £3.49 LARGE (MGL) £3.98

ADVENTURES WITH ELECTRONICS

BOOK £4.75 PACK £20.98
An easy to follow book suitable for all ages. No soldering, uses an S DEC breadboard. Lots of clear diagrams and instructions to build 16 projects. Component pack includes S DEC and all components for the projects.

LEGO Technic Sets
TEACHERS WE ARE STOCKISTS OF THE WHOLE RANGE. CONTACT US FOR BROCHURES. VERY COMPETITIVE PRICES AND QUICK DELIVERIES

STEPPING MOTORS 12 VOLT

48 STEPS 1035 £14.50
200 STEPS M0200 £16.80

OPTICAL FIBRES TRIAL PACK OF 10 METRES. Nine assorted types & data.

£1.99

'EQUALISER' IONISER



KIT REF 707 £15.53

A mains powered Ioniser that produces a breeze of negative ions in the air. A compact, safe, simple unit that uses a negligible amount of electricity.

ULTRASONIC PET SCARER



Produces high power ultrasound pulses. L.E.D. flashes to indicate power output and level. Battery powered (9V-12V or via *Mains Adaptor).

KIT REF 812 £13.80
*Mains Adaptor £1.98

DIGITAL FREQUENCY 200 MHz METER

KIT REF 563

£62.98

An 8 digit meter reading from A.F. up to 200 MHz in two ranges. Large 0.5" Red LED display. Ideal for AF and RF measurements. Amateur and C.B. frequencies.



VISUAL GUITAR TUNER



Crystal controlled, with a super rotating LED display. Indicates high, low, and exact degree of mistuning. Use with pick-up or mic. Also has audible output.

KIT REF E711 £21.99

3 BAND SHORTWAVE RADIO



OUR KIT REF 718 £26.53

Covers 1.6-30 MHz in 3 bands using modern miniature coils. Audio output is via a built-in loudspeaker. Advanced design gives excellent stability, sensitivity and selectivity. Simple to build.

0283 65435



MAGENTA ELECTRONICS LTD
 PE 13 HUNTER STREET,
 BURTON-ON-TRENT,
 STAFFS. DE14 2ST.
 0283 65435, Mon-Fri 9-5 Sat 9-2
 Access/Barclaycard (Visa) by
 phone or post.
 24 hr Answerphone for credit
 card orders.
 Our prices include VAT

ADD £1 P&P TO ALL ORDERS.
 PRICES INCLUDE VAT.
 SAE ALL ENQUIRIES.
 OFFICIAL ORDERS WELCOME
 OVERSEAS: Payment must be
 sterling.
 IRISH REPUBLIC and BFPO. UK
 PRICES.

FROM MAGENTA

A SELECTION OF OUR BEST PROJECT KITS

As usual these kits come complete with printed circuit boards, cases, all components, nuts, screws, wire etc. All have been tested by our engineers (many of them are our own designs) to ensure that you get excellent results.

INSULATION TESTER

An electronic High Voltage tester for mains appliances and wiring. An inverter circuit produces 500 volts from a PP3 battery and applies it to the circuit under test. Reads insulation up to 100 Megohms. Completely safe in use.



OUR KIT REF 444 £19.58

DIGITAL CAPACITANCE METER

Simple and accurate (1%) measurements of capacitors from a few pF up to 1,000 uF. Clear 5 digit LED display indicates exact value. Three ranges — pF, nF, and uF. Just connect the capacitor, press the button and read the value.




£41.55
 OUR KIT
 REF 493

MAGENTA

LOWCOST

68000

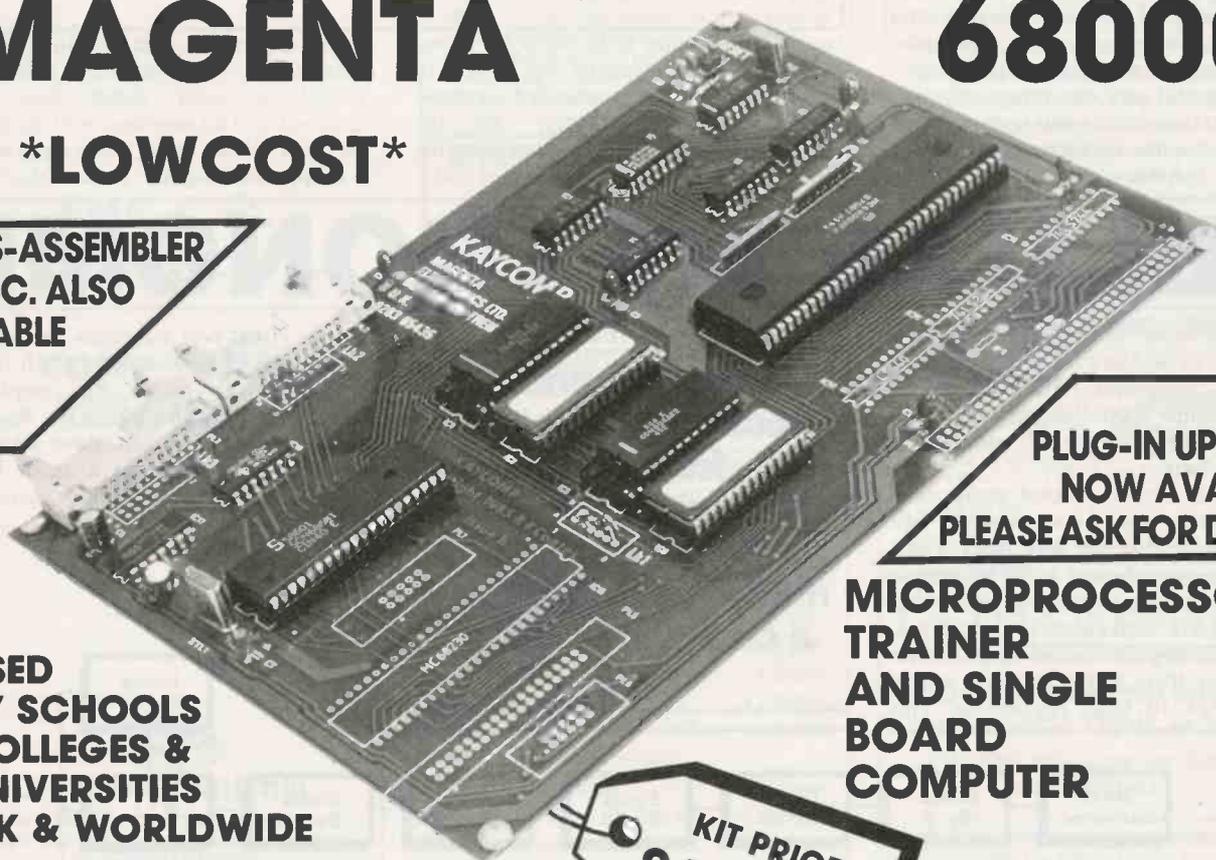**CROSS-ASSEMBLER
 FOR BBC. ALSO
 AVAILABLE
 £60.00
 (DISK)**



**68020
 PLUG-IN UPGRADE
 NOW AVAILABLE
 PLEASE ASK FOR DETAILS**

**USED
 BY SCHOOLS
 COLLEGES &
 UNIVERSITIES
 U.K & WORLDWIDE**

**MICROPROCESSOR
 TRAINER
 AND SINGLE
 BOARD
 COMPUTER**

***PERFECT FOR ROBOTICS
 APPLICATIONS REQUIRING
 POWER AND SPEED***

**KIT PRICE
 £110 INC VAT**

OTHER OPTIONS, DATA PACKS,
 AND LITERATURE AVAILABLE
 — SEND FOR DETAILS.

- Full 8MHz 68000 Processor with 16 bit data bus.
- Top-class monitor program included on two Eproms.
- Communicates via RS232 interface to terminal, BBC computer, P.C. computer etc.
- Use as a Trainer, or as a stand-alone computer system.
- Fast, powerful processing — Ideal for real time control systems.

- Dual U.A.R.T. allows simultaneous connection of printer and terminal.
- Add-on options include: G64 Bus, 68230 P.I.T. 8k and 32K Ram upgrades, and line by line assembler.
- Available from stock now — with support literature and full technical back up.

STANDARD SYSTEM IN KIT FORM (Ref 600)	£110.00	68230 P.I.T. ADD ON OPTION (Ref 603)	£ 11.97
STANDARD SYSTEM BUILT & TESTED	£190.00	G64 BUS ADD-ON (Ref 604)	£ 5.49
LINE BY LINE ASSEMBLER PROGRAM (IN EPROM)	£ 27.00	8K x 16 RAM UPGRADE (Ref 605)	£ 19.25
POWER SUPPLY (Ref 609)	£ 13.99	32K 16 RAM UPGRADE Ref 606	Phone

Those readers who can remember back to electronics construction in the late '60s and early '70s will no doubt recall the very simple metronome designs of that era. These early metronome circuits were mainly based on unijunction transistors operating as relaxation oscillators, or a little later on the 555 astable was the more popular choice. These circuits were designed for simplicity, and often used only about half a dozen or so components! This metronome circuit is quite definitely a totally different concept, and it was designed to overcome the weaknesses of simple metronome projects. I believe it succeeds in doing so, but it inevitably costs substantially more to construct than a very basic design.

A common complaint about simple electronic metronomes is that they do not permit the beat rate to be set very accurately, and have poor repeat setting accuracy. This is due to the use of simple C - R oscillators that cover a fairly wide frequency range. Even using a large control knob and scale this inevitably gives quite cramped scaling, and compromises results. A lot of careful and very time consuming calibration is needed in order to obtain what is often still quite mediocre accuracy. The method of frequency generation utilised in



permits the beat rate to be easily set at any desired figure, or something very close to it. The use of a crystal controlled timebase ensures excellent accuracy, and the frequency synthesiser technique removes the need for any calibration of the finished unit.

An accented beat facility can be switched in, with anything from every second to every eighth beat being emphasised. This emphasis is in the form of the usual "click" sound being replaced with a deeper and slightly louder "thud" type

DELUXE METRONOME

BY ROBERT PENFOLD

Turning a phase locked loop into a frequency synthesiser gives you the ultimate in modern electronics - a choice of click or thud!

this unit is based on frequency synthesis techniques, as used in a lot of modern radio frequency equipment. The frequencies involved in this application are very much lower, but the principle of operation is exactly the same.

The beat rate is selected using three switches rather than a potentiometer. Two of the switches are ten way types which enable a beat rate from 1 to 99 per minute to be selected, with a resolution of one beat per minute. The third switch is a range type, and by selecting the second range a beat rate span of 10 to 990 is obtained, with a resolution of 10 beats per minute. This

sound. Visual beat indicators are provided in the form of separate leds which flash in sympathy with normal and emphasised beats. Although the circuit is based on sixteen integrated circuits, these are all low power cmos types, and a small 9 volt battery is adequate as the power source.

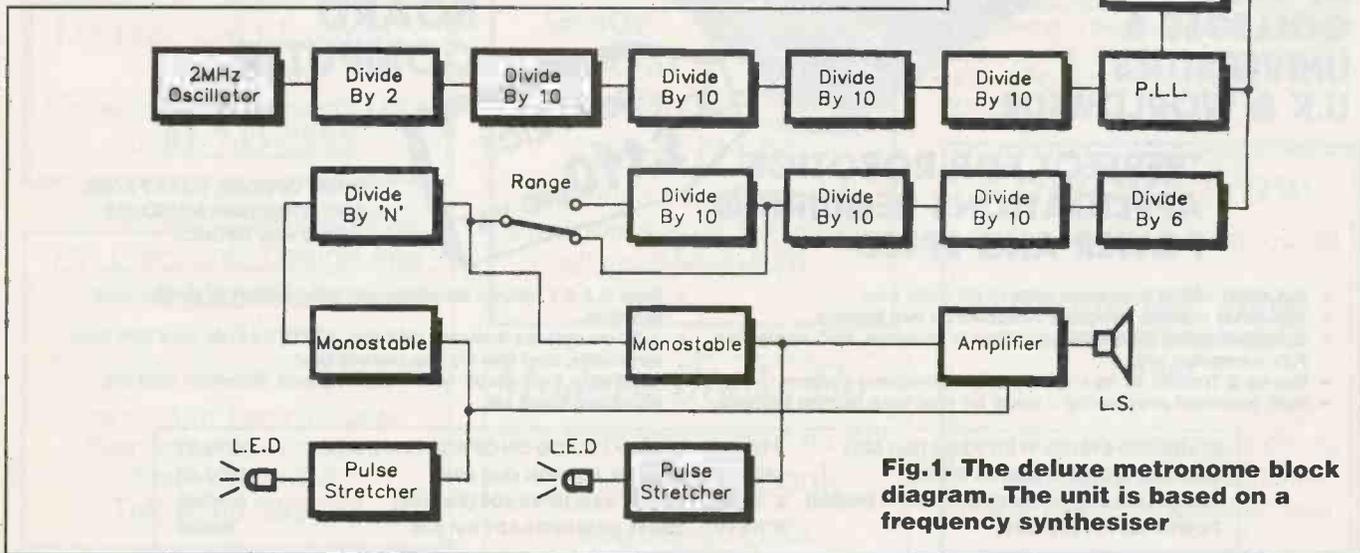


Fig.1. The deluxe metronome block diagram. The unit is based on a frequency synthesiser

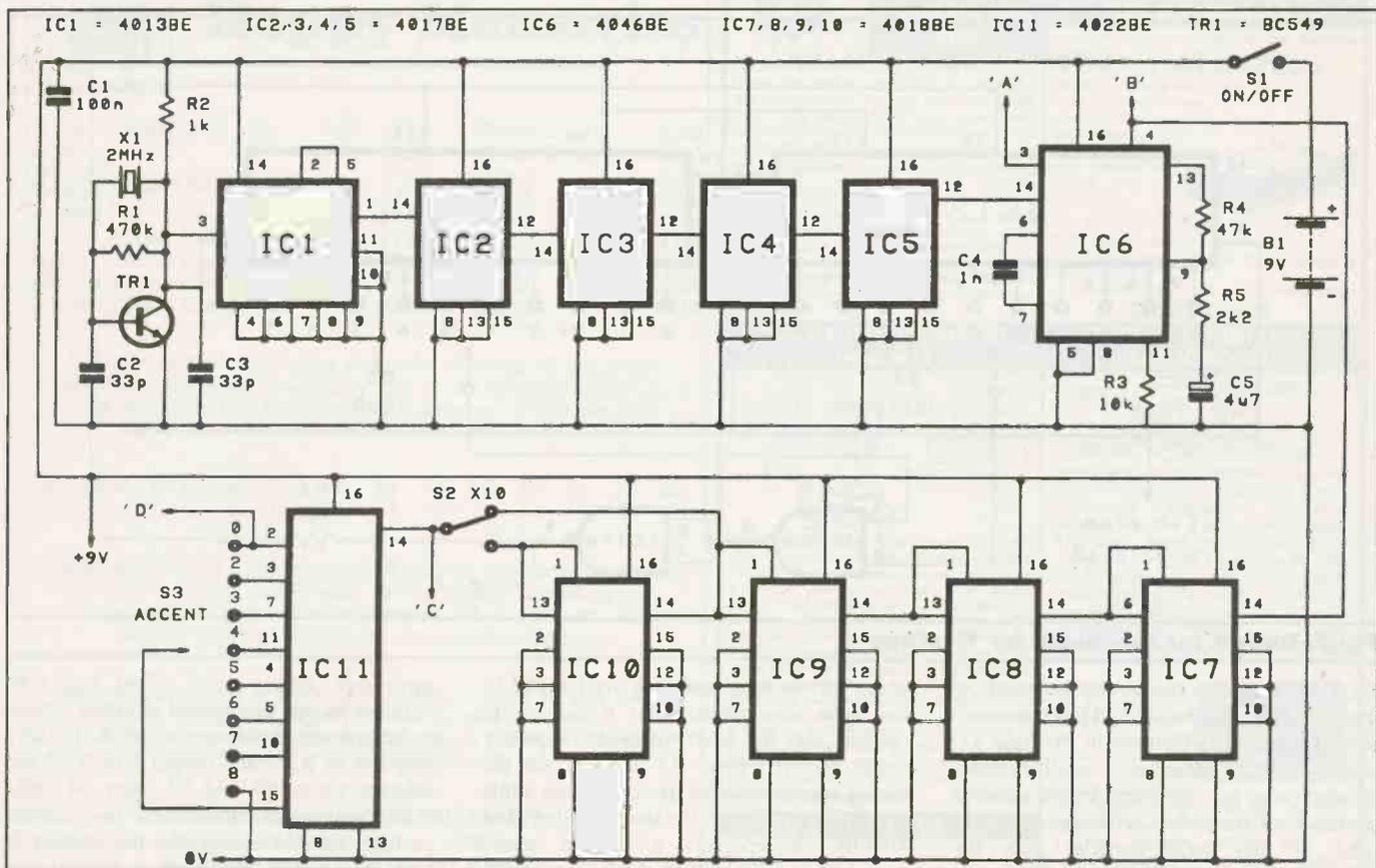


Fig.2. The main circuit diagram

FREQUENCY SYNTHESIS

The block diagram of Fig.1 shows the general make up of the unit, and should help to clarify the overall method of operation. The phase locked loop (pll) stage is at the heart of the unit, and is the main stage of the frequency synthesiser section. Although it is shown here as a single stage, the pll actually consists of a vco, a phase comparator, and a lowpass filter. The basic action of a phase locked loop is to maintain its vco at the same frequency as and in-phase with an input signal. In this case the input signal is a 100Hz squarewave derived from a 2MHz crystal oscillator and a series of frequency divider stages.

In order to make a phase locked loop function as a frequency synthesiser it is merely necessary to add a divide by 'N' circuit between its vco output and the input of its phase comparator. As a couple of simple examples, consider the action of the circuit with divisions of 2 and 5. With a 100Hz input, in order to obtain a matching 100Hz signal from the vco and divider the vco must function at 200Hz. After division by two this gives the correct 100Hz input signal to the phase comparator. Similarly, in order to give a 100Hz input to the phase comparator with a division by 5, the vco must operate at 500Hz. In fact the vco frequency will always be equal to the

100Hz input frequency multiplied by the division rate through the divide by 'N' stage. It is the signal from the vco that constitutes the output of the frequency synthesiser. In theory any output frequency that is a multiple of 100Hz can be obtained, although in practice the lock-on range of the phase locked loop will place a rigid constraint on the maximum available output frequency. Some phase locked loops have quite narrow lock-on ranges, but this application usually requires a type that has a very wide lock range.

In this case the divide by 'N' circuit provides divisions of 1 to 99 inclusive, and the cmos phase locked loop used in the design is well able to handle this wide frequency range. Of course, this gives a basic 100Hz to 9.9kHz frequency range, which is well above the required frequency span of about 0.5Hz to 6Hz. However, some frequency division is all that is needed in order to give an appropriate output frequency range. A divide by six stage followed by a series of three divide by ten circuits give an overall division rate of 6000. This provides an output frequency that is in multiples of 0.0166Hz. At a first glance this may seem an odd figure to use, and it is perhaps more conveniently thought of as 1 cycle per minute. This gives the unit its basic 1 to 99 beats per minute range, and by switching out the final divide by ten stage the beat range can be altered to 10 to 990 beats per minute.

The output from the frequency synthesiser is a squarewave signal, but what

we require in order to provide the standard metronome "click" sound is a very brief pulse of around 0.5 milliseconds in duration. This is obtained by triggering a monostable from the squarewave signal, and the resultant pulses are used to drive the loudspeaker by way of a simple amplifier stage. Accented beats are obtained by feeding the squarewave output signal to a divide by 'N' stage. This can be switched out if no accentuation is required, or set for a division rate of 2 to 8 when the accentuation is required. This divider drives a second monostable which has a longer output pulse of around 5 milliseconds in duration. The output of this monostable is mixed with the output of the first monostable, and it has the effect of lengthening the output pulses on accented beats so as to give the required deeper "thud" sound.

Visual indication of the normal and accented beats are provided by driving leds from the two monostables. Simply driving the leds direct from the monostables does not give very good results as the output pulses are too brief. The leds visibly flash, but their apparent brightness is quite low. Two pulse stretcher circuits are used to give longer and more noticeable flashes from the leds.

THE CIRCUIT

The main circuit diagram appears in Fig.2, but the divide by 'N' and output stages are shown separately in Fig.3 and

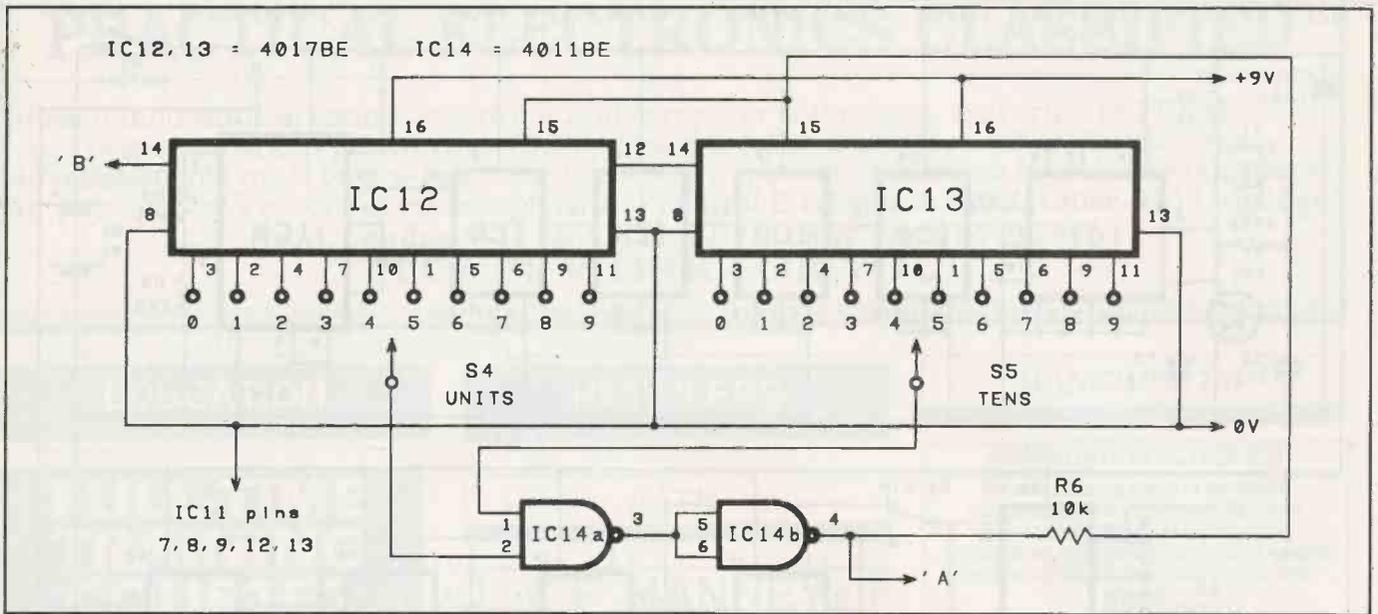


Fig.3. Circuit for the divide by 'N' stage

Fig.4 respectively. The circuit is based on that of the "Synthesised AF Generator" project which was featured in PE June 87, albeit with extensive modifications. Readers who are interested in the detailed operation of frequency synthesisers should refer to this earlier article, plus the companion feature ("Frequency Synthesisers") in the same issue.

TR1 acts as the basis of the 2MHz crystal oscillator, and this uses a standard configuration. There is no need to include a trimmer to permit fine adjustment of the output frequency as any error here will be totally insignificant. IC1 is a dual 'D' type flip/flop, but in this circuit only one section is utilised, and it operates as a simple divide by two stage. This is followed by a series of four 4017BE one of ten decoders. In this case these devices operate as simple divide by ten circuits using the "carry" outputs and ignoring the other ten outputs of each device.

IC6 is a cmos 4046BE "micropower"


phase locked loop, and it is well suited to this type of application as it can easily operate over the relatively wide frequency range involved here. R3 and C4 are the timing components for its vco section while R4, R5, and C5 form the lowpass filter. The 4046BE incorporates a second phase comparator and a zenor diode for supply stabilisation purposes, but in this circuit neither of these extras are used.

The divide by 'N' circuit is based on IC12 and IC13, which are both 4017BE one of ten decoders. They are connected in series so that the basic action of the circuit is to provide a division by one hundred. However, the division rate is always less than this due to the inclusion of IC14 which resets both devices prematurely. It has one input driven from IC12 and the other driven from IC13, and the resetting of the dividers occurs when the two outputs that drive IC14 are both high. The action of a one of ten decoder is for its outputs (numbered from "0" to "9") to go high in sequence on

successive input pulses. Two ten way switches enable any output of either device to be connected through to IC14. If (say) output 4 of IC13 and output 7 of IC12 are selected using S5 and S4, then 74 input cycles will occur before these two outputs go high simultaneously and the counter is reset. The circuit can therefore provide any division rate from 1 to 99 merely by dialing up the required division rate on S4 (the units) and S5 (the tens). Note that "00" is not a valid setting for these switches, and will probably produce quite a high output frequency.

The output from the vco feeds a divide by six stage which is a 4018BE with the appropriate method of connection. S2 is the range switch, and it selects the output from either IC9 or IC10. IC11 is the divide by 'N' circuit that provides the accentuated beats. This is a 4022BE one of eight decoder, and it is used in what is essentially the same way as the 4017BEs in the main divide by 'N' circuit. No gating is needed in this case

Fig.4. Circuit for the output section of the unit

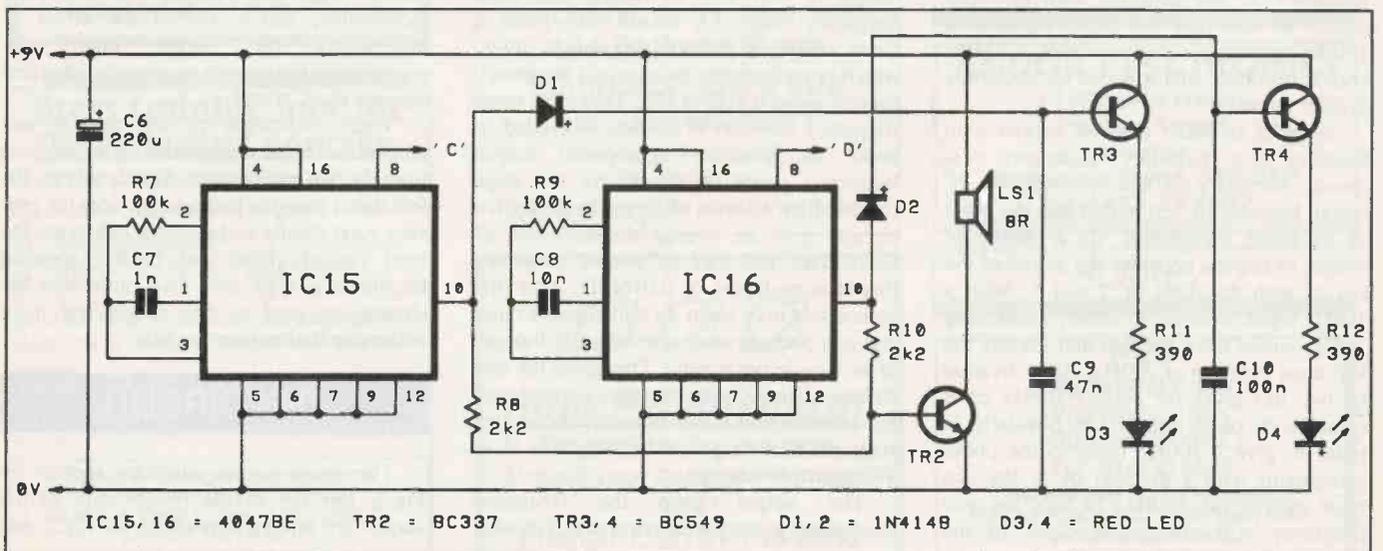

as only a single device is involved, and it can directly reset itself. With output "0" (pin 2) connected through to the reset input IC11 is held permanently in the reset stage, and this disables the accented beat function. It is from this output that the divided output signal is taken.

Both the monostables are based on 4047BE cmos monostable/astables integrated circuits (IC15 and IC16) which are connected here to operate in the positive edge triggered monostable mode. C7 and R7 give an output pulse duration of approximately 0.45 milliseconds from IC15, while the values of R9 and C8 given an output pulse duration of about ten times this figure from IC16. The monostables drive the loudspeaker via a simple common emitter amplifier (TR2) which really operates as a switch rather than a linear amplifier. This is acceptable since the output signal is just simple pulses.

The led indicators are D3 and D4, and they are driven from the monostables via emitter follower buffer amplifiers. The diodes and capacitors at the inputs of these stages provide the pulse stretching, but the pulses to the leds still need to be quite short. Otherwise at high beat rates the leds would be permanently switched on, or would seem

to blink off rather than flash on. The led which indicates the emphasised beats (D4) is flashed on for approximately twice as long as the other led. This factor, plus the use of a separate led for the emphasised beats, helps to make the emphasised beats stand out very clearly even when the volume of the music is so loud as to largely mask the sound of the unit.

As the circuit is based on low power cmos integrated circuits, and the loudspeaker is only fed intermittently with very brief pulses, the current consumption of the unit is very modest at only about 5 milliamps (a little more than this at high beat rates). A small (PP3 size) 9 volt battery is therefore perfectly satisfactory as the power source even if the unit is likely to receive a great deal of use.

they should not be plugged into place until the project is finished in all other respects. The crystal is mounted direct on the board, and it must be a miniature wire-ended type (HC-49/U or similar) if it is to fit into place easily. Crystals can easily be damaged by excess heat when they are being soldered in place, so try to complete these soldered joints reasonably rapidly. The capacitors must be miniature types if they are to fit easily into the available space. In the case of the polyester types they should have 7.5 millimetre pin spacing. There are a fair number of link wires to fit onto the board, and the trimmings from resistor leadout wires should suffice for these. At this stage only fit single-sided printed circuit pins at the points where connections to the controls, leds, and loudspeaker will eventually be added.

I used a case for the prototype that is considerably larger than is really necessary. You may have to opt for a case of similar dimensions in order to obtain one with suitably generous front panel dimensions, or with a little ingenuity a much smaller case could probably be used. For example, by using one of the large sides of a case as the front panel it would be much easier to accommodate the front panel mounted

CONSTRUCTION

Details of the printed circuit board are provided in Fig.5. The first point to note is that all sixteen integrated circuits are cmos types, and that they consequently require the standard anti-static handling precautions to be observed. I would strongly urge the use of sockets for all these components, and

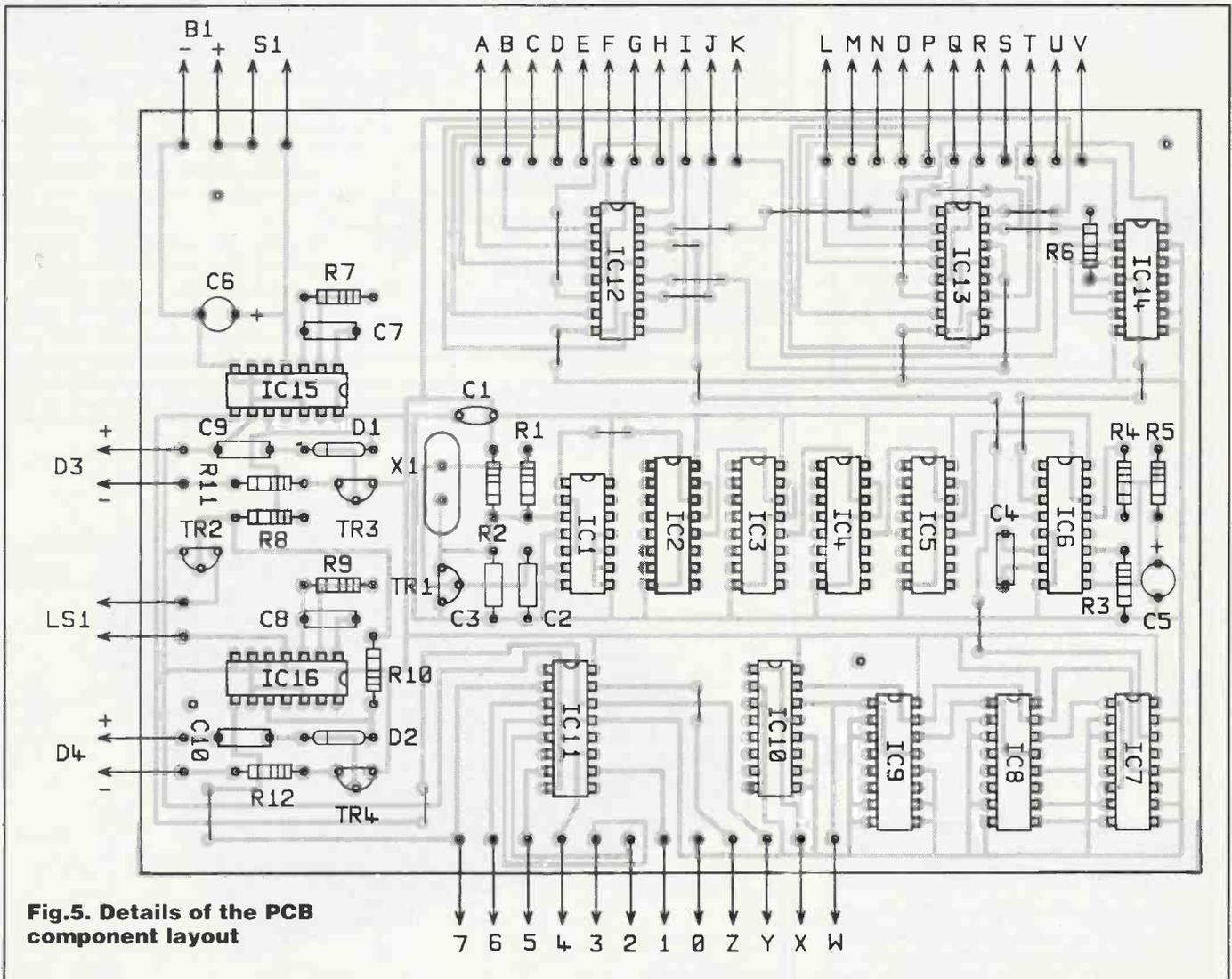


Fig.5. Details of the PCB component layout

components, or the loudspeaker could be fitted on the top panel of the case in order to reduce the amount of front panel space that is required. I would not recommend the use of a very small loudspeaker in order to save space. Small loudspeakers give relatively low volume, especially when fed with a simple pulse signal of the type involved in this application. I would recommend the use of a loudspeaker of at least 75 millimetres in diameter.

The exact front panel layout used is not critical, but S4 and S5 should be mounted side-by-side with S5 to the left of S4, so

COMPONENTS

Resistors

R1	470k
R2	1k
R3, R6	10k (2 off)
R4	47k
R5, R8, R10	2k2 (3 off)
R7, R9	100k (2 off)
R11, R12	390 (2 off)

All resistors 1/4W 5% carbon film

Capacitors

C1	100n ceramic
C2, C3	33p polystyrene (2 off)
C4, C7	1n polyester (2 off)
C5	4u7 63V radial elect
C6	220u 10V radial elect
C8	10n polyester
C9	47n polyester
C10	100n polyester

Semiconductors

IC1	4013BE
IC2, IC3, IC4, IC5, IC12, IC13	4017BE (6 off)
IC6	4046BE
IC7, IC8, IC9, IC10	4018BE (4 off)
IC11	4022BE
IC14	4011BE
IC15, IC16	4047BE (2 off)
D1, D2	1N4148 (2 off)
D3, D4	Red panel leds (2 off)
TR1, TR3, TR4	BC549 (3 off)
TR3	BC337

Miscellaneous

X1	4MHz miniature wire-ended
S1	spst miniature toggle
S2	spdt miniature toggle
S3, S4, S5	12 way 1 pole rotary with end stop, break before make (3 off)
LS1	8R impedance, 75mm dia. or more
B1	9 volt (PP3 size)

Case about 240 x 220 x 100mm (see text), printed circuit board, control knob (3 off), 14 pin dil ic holder (4 off), 16 pin dil ic holder (12 off), battery connector, pins, ribbon cable, stand-offs, etc.

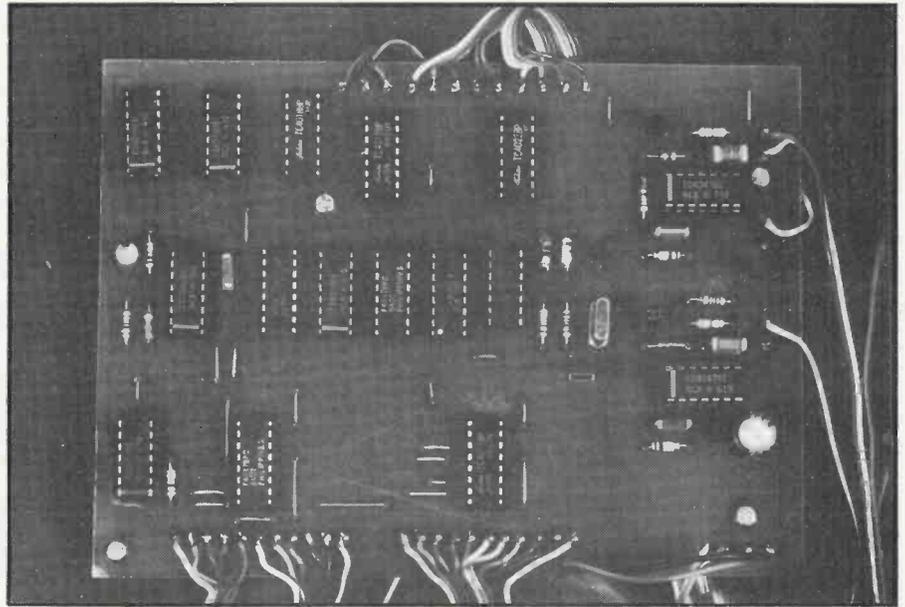


Photo of the completed PCB


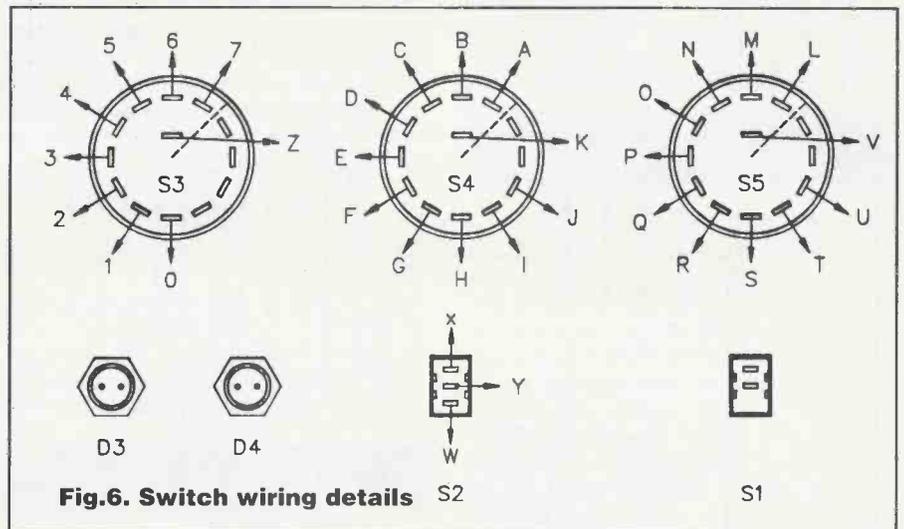


Fig.6. Switch wiring details

Photo of the completed wiring layout within the case

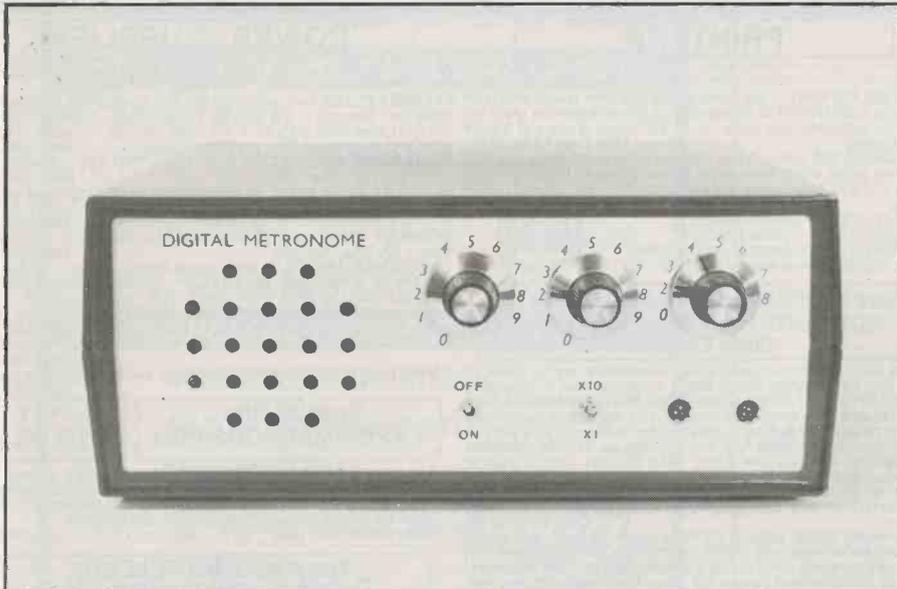



that it is easy to dial up the required number of beats per minute. The three rotary switches are all 12-way single pole types having adjustable end-stops (set to 8-way operation for S3, and 10-way operation for S4 and S5). With most of these switches the end-stop can be omitted if desired, so that the quick route from position 9 to position 0 (or whatever) can be taken. If you do this, connect the unused tags of each switch to one of the tags that is used, so that inputs of the counter chips can not be left floating. These switches must all be of the break before make variety. Otherwise two outputs will be short circuited together each time one of these switches is moved from one setting to the next!

A grille is needed for the loudspeaker, and the quickest way of producing this is to drill a matrix of holes about 5 millimetres in diameter. It is not as easy as you might think to make a really good job of this. It is best to start by drilling small holes (about 2 millimetres in diameter) as accurately as possible, and then enlarge these to the required size. If you use a loudspeaker of about 100 millimetres or more in diameter it may have provision for screw fixing, but smaller types usually have no built-in mounting bracket of any type. Often the

only practical method of mounting them is to use a good quality adhesive such as an epoxy type. Try to avoid smearing any adhesive onto the diaphragm as this could seriously impair the efficiency of the loudspeaker. The printed circuit board is mounted on the base panel of the case using stand-offs or 6BA bolts plus short spacers.

To complete the unit the point-to-point wiring must be added. This wiring is shown in Fig.6, which must be used in conjunction with Fig.5 (eg point 'A' in Fig.5 connects to point 'A' in Fig.6). This wiring can be added using ordinary multi-strand hook-up wire tied into neat cable-forms, but ribbon cable offers a much quicker and easier solution. The cathode (+) terminals of the leds are usually indicated by shorter leadout wires.

IN USE

Even if you do not normally bother to mark panel legends on your projects, it is advisable to at least mark S4 and S5 with "0" to "9" scales so that it is easy to set them up for the required beat rate. Even fairly rough-and-ready scales will make the unit very much easier to use. The use of a crystal controlled frequency synthesiser

means that this is the only form of calibration that is required. Before switching on the unit set S2, S4, and S5 for a sensible beat rate of around 50 to 100 beats per minute. When the unit is switched on it should produce the metronome "clicks" at a suitable rate - switch off at once and recheck all the wiring if there is any sign of a malfunction. To test that the unit is functioning accurately, set the controls for 60 beats per minute, and check against a clock or watch with seconds indication that the correct one "click" per second is being produced. With the accentuation switched on the accented beats should stand out quite clearly from the normal ones. However, the accented beats can be emphasised still further if desired by making C8 higher in value. Do not use a value many times larger than the specified value though, as this could produce a double "click" instead of the "thud" sound, and this would give confusing results.

PE

ED LINES

OPTICAL ILLUSION

Rumours that home automation might be aided by the use of a single fibreoptic cable coupled into the national grid seem to have been quashed. There have been suggestions that such a cable might carry many diverse data channels, ranging from tv programmes to telecommunications. In view of the current high-level attention being given to methods by which society can best be linked through microprocessed technology, speculation on how to make further use of the national grid is understandable.

However, according to a DTI report, the government has said that it is not prepared to underwrite the technology of national grid comms, nor to allow BT to do so either. I wonder if anyone has considered putting fibreoptic links through gas pipelines? (Have you ever stopped to marvel that, if it weren't for the kinks in the pipe, you could look right down your gas cooker to the bottom of a North Sea gas well?)

SOFTMACHINE
DISTRIBUTION LTD

386 MOTHER BOARDS

16/20MHz 386 M/B
16/20MHz 286 M/B
VGA CARD

Ex-stock Cash & Carry, from Computer Casing Specialist
Trade Hours: 10-6pm (Sat 10-1pm)

SOFTMACHINE DISTRIBUTION LTD.
Unit F, 18 Harbet Rd, Lea Valley, Hastingwood Trading Estate,
North Circular Rd, Edmonton, London N18 3LR
Fax: 01-807 2748 Tel: 01-803 6068

DEMS ONLY

Hobbyline

Now available free to hobbyists, - Latest stock listing
INCLUDING

Receiving Valves, Rectifiers and Diodes,
Thyristors and I.C.'s Plus a selection of discreet
semi conductors for your listing
Either phone (0375) 360062

OR

Send a large S.A.E. to: Compstock (Hobby)
Electronics, Compstock House, London Road,
Stanford Le Hope, Essex, SS17 0JU

COMPSTOCK

THE 'ALADDINS' CAVE OF ELECTRONIC & COMPUTER EQUIPMENT

COLOUR MONITORS

16" Decca, 80 series budget range, colour monitors, features include: PIL tube, attractive teak style case, guaranteed 80 column resolution, only seen on monitors costing 3 times our price, ready to connect to a host of computer or video outputs. Manufacturers fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee. 1000's sold to date.
DECCA 80 RGB - TTL + SYNC input for BBC type interface etc.
DECCA 80 COMP 75 11 composite video input with integral audio amp & speaker ideal for use with video recorder or TELEBOX ST or any other audio visual use.
Only £99.00 (E)

HIGH DEFINITION COLOUR

BRAND NEW CENTRONIC 14" monitors in attractive style moulded case featuring hi res Mitsubishi 042 dot pitch tube with 669 x 507 pixels, 28Mhz bandwidth. Full 90 day guarantee.
 Order as 1004-N2 for TTL + sync RGB for BBC etc **£159.00 (E)**
 1003-N1 for IBM PC etc fully CGA equiv **£189.00 (E)**
 1005-N2 RGB interface for QL 85 columns. **£169.00 (E)**

20" & 22" AV Specials

Superbly made, UK manufacture, PIL tube, all solid state colour monitors, complete with composite video and sound inputs, attractive teak style case, ideal for a host of applications including Schools, Shops, Disco's, Clubs etc. Supplied in EXCELLENT little used condition with 90 day guarantee.
20" Monitor £165.00 (F) **22" Monitor £185.00 (F)**

MONOCHROME

MOTOROLA M1000-100 5" CRT black & white compact chassis monitor measuring only 11.6h, 12w, 22d, ideal for CCTV or computer applications. Accepts standard Composite video or individual H & V syncs. Operates from 12v DC at approx 0.8a. Some units may have minor screen marks, but still in very usable condition. Fully tested with 30 day guarantee & full data. **Only £29.00 (C)**
 Fully cased as above, with attractive moulded, desk standing swivel and tilt case Dim. cm 12h, 14.5w, 26d. **£39.00 (C)**
 JVC type 751-7 5" ultra compact black & white chassis monitor for 12v 0.7a DC operation Dim cm 11h, 14w, 18d. Simple DII circuit data included to convert data and separate sync input to composite video input. Ideal portable equipment etc. Supplied with full data.
Brand New £65.00 (B)
 KGM 324 9" Green Screen, Little used fully cased, mains powered high res monitors with standard composite video input. Fully tested and in excellent condition. **£49.00 (E)**
20" Black & White monitors by AZTEK, COTRON & NATIONAL
 All solid state, fully cased monitors, ideal for all types of AV or CCTV applications. Units have standard composite video inputs with integral audio amp and speaker. Sold in good, used condition-fully tested with 90 day guarantee. **Only £85.00 (F)**

FLOPPY DRIVE SCOOP

Drives from Only £39.95

A MASSIVE purchase of standard 5.25" disk drives enables us to offer you prime product at all time super low prices. All units unless stated are removed from often BRAND NEW equipment, fully tested and shipped to you with a full 120 day guarantee. All units offered operate from +5 and +12 volts DC, are of standard size and accept the common standard 34 way interface connector.
TANDON TM100-2A IBM compatible 40 track FH double sided **Only £39.95 (B)**
TANDON TM101-4 FH 80 track double sided **Only £49.95 (B)**
JAPANESE Half Height double sided drives by Canon, Teac, Toshiba etc. Specify 40 or 80 track. **Only £75.00 (B)**
TEAC FD55-F 40-80 track double sided Half Height **Brand New £115.00 (B)**

DISK DRIVE ACCESSORIES

34 Way interface cable and connector single **£5.50**, Dual **£8.50 (A)**
 5.25" DC power cable **£1.75**. Fully cased PSU for 2 x 5.25" Drives **£19.50 (A)**
 Chassis PSU for 2 x 8" drives **£39.95 (B)**

8" DISK DRIVES

SUGART 800/801 single sided refurbished **£175.00 (E)**
 SUGART 851 double sided refurbished **£260.00 (E)**
 MITSUBISHI M2894-63 Double sided switchable Hard or Soft sector **BRAND NEW £275.00 (E)**
SPECIAL OFFER Dual 8" drives with 2MB capacity in smart case with integral PSU **ONLY £499.00 (F)**

COMPUTER SYSTEMS

TATUNG PC2000. Big brother of the famous EINSTEIN, the TPC2000 professional 3 piece system comprises: Quality high res GREEN 12" monitor, Sculptured 92 key keyboard and plinth unit containing the Z80A CPU and all control electronics PLUS 2 Integral TEAC 5.25" 80 track double sided disk drives. Many other features include Dual 8" IBM format disk drive support. Serial and parallel outputs, full expansion port, 64k ram and ready to run software. Supplied complete with CPM, WORDSTAR, BASIC and accounts package.
BRAND NEW
 Full 90 day guarantee. **Only £299(E)**
 Original price OVER £1400

EQUINOX (IMS) S100 system capable of running either TURBO or standard CPM. Unit features heavy duty box containing a powerful PSU, 12 slot S100 backplane, & dual 8" double sided disk drives. Two individual Z80 cpu boards with 192k of RAM allow the use of multi user software with upto 4 RS232 serial interfaces. Many other features include battery backed real time clock, all IC's socketed etc. Units in good condition and tested prior despatch, no documentation at present, hence price of only **£245.00 (F)**
 S100 PCB's IMS A466 64k dynamic RAM. **£55.00 (B)** IMS A930 FDC controller **£85.00 (B)**. IMS A862 CPU & i/o **£65.00 (B)**

SAE for full list of other S100 boards and accessories.

PRINTERS

Bulk purchase brings you incredible savings on a range of printers to suit all applications. Many other "one off bargains" can be seen at our South London Shop

HAZELTINE ESPRINT Small desktop 100 cps print speed with both RS232 and CENTRONICS interfaces. Full pin addressable graphics and 6 user selectable type fonts. Up to 9.5" single sheet and tractor paper handling **Brand New Only £199.00 (E)**
CENTRONICS 150 series. A real workhorse for continuous use with tractor feed paper, either in the office, home or factory, desk standing 150 cps 4 type fonts and choice of interfaces. Supplied BRAND NEW Order as:
 150-SN up to 9.5" paper handling **£185.00 (E)**
 150-SW up to 14.5" paper handling **£225.00 (E)**
 150-GR up to 14.5" paper plus full graphics **£245.00 (E)**
 When ordering please specify RS232 or CENTRONICS interface.

Ultra Fast 240 cps NEWBURY DATA NDR 8840 High Speed Printers Only £449 !!

A special purchase from a now defunct Government Dept enables us to offer you this amazing British Made, quality printer at clearance prices. **SAVING YOU OVER £1500 !!** The NDR8840 features high speed 240 cps print speed with integral, fully adjustable paper tractor, giving exceptional fast paper handling for multi part forms etc. The unit features 10 selectable type fonts giving up to 226 printable characters on a single line. Many other features include Internal electronic vertical and horizontal tabs, Self test, 9 needle head. Up to 15.5" paper, 15 million character ribbon cartridge life and standard RS232 serial interface. Sold in SUPERB tested condition with 90 day guarantee. **Only £449.00 (F)**
EPSON model 512 40 column 3.5" wide paper roll feed, high speed matrix (3 lines per second) printer mechanism for incorporation in point of sale terminals, ticket printers, data loggers etc. Unit features bi directional printhead and integral roll paper feed mech with tear bar. Requires DC volts and simple parallel external drive logic. Complete with data RFE and tested. **Only £49.95 (C)**
EPSON model 542 Same spec as above model, but designed to be used as a slip or flatbed printer. Ideal as label, card or ticket printer. Supplied fully cased in attractive, small, desk top metal housing. Complete with data RFE and tested. **Only £55.00 (D)**
PHILIPS P2000 Heavy duty 25 cps bi directional daisy wheel printer. Fully DIABLO, QUME, WORDSTAR compatible. Many features include full width platen - up to 15" paper, host of available daisy wheels, single sheet paper handling, superb quality print. Supplied complete with user manual & 90 day guarantee plus FREE dust cover & daisy wheel. **BRAND NEW Only £225.00 (E)**

Most of the items in this Advert, plus a whole range of other electronic components and goodies can be seen or purchased at our

** South London Shop **

Located at 215 Whitehouse Lane, London SE25. The shop is on the main 68 bus route and only a few miles from the main A23 and South Circular roads. Open Monday to Saturday from 9 to 5.30, parking is unlimited and browsers are most welcome. Shop callers also save the cost of carriage.

MODEMS

Modems to suit all applications and budgets. Please contact our technical sales staff if you require more information or assistance.

SPECIAL PURCHASE V22 1200 baud MODEMS ONLY £149 !!

MASTER SYSTEMS type 2/12 microprocessor controlled V22 full duplex 1200 baud. This fully BT approved modem employs all the latest features for error free data comms at the staggering speed of 120 characters per second, saving you 75% of your BT phone bills and data connect time !! Add these facts to our give away price and you have a superb buy !! Ultra slim unit measures only 45 mm high with many integral features such as Auto answer, Full LED status indication, RS232 interface, Remote error diagnostics, SYNC or ASYNC use, SPEECH or DATA switching, integral mains PSU, 2 wire connection to BT line etc. Supplied fully tested, EXCELLENT slightly used condition with data and full 120 day guarantee.

LIMITED QUANTITY **Only £149 (D)**

CONCORD V22 1200 baud as new **£330.00 (E)**
 CONCORD V22 1200-2400 BIS **£399.00 (E)**
 RIXON Ex BT Modem 27 V22 1200 **£225.00 (E)**
 DATEL 4800 / RACAL MPS 4800 EX BT modem for 4800 baud sync use. **£295.00 (E)**
 DATEL 2412 2780/3780 4 wire modem unit EX BT fully tested. **£199.00 (E)**
 MODEM 20-1 75-1200 BAUD for use with PRESTEL etc EX BT fully tested. **£49.00 (E)**
 TRANSDATA 307A 300 baud acoustic coupler with RS232 I/O **Brand New £49.00 (E)**
 RS232 DATA CABLES 16 ft long 25w D plug to 25 way D socket. Brand New **Only £9.95 (A)**
 As above but 2 metres long **£4.99 (A)**
 BT plug & cable for new type socket **£2.95 (A)**

RECHARGEABLE BATTERIES

Maintenance free, sealed long life LEAD ACID
 A300 12v 3 Ah **£13.95 (A)**
 A300 6v 3 Ah **£9.95 (A)**
 A300 6-0-6 v 1.8 Ah RFE **£5.99 (A)**

NICKEL CADMIUM

Quality 12 v 4 Ah cell pack. Originally made for the TECHNICOLOUR video company, this unit contains 10 high quality GE nicad, D type cells, configured in a smart robust moulded case with DC output connector. Dim cm 19.5x 4.5 x 12.5. Ideal portable equipment etc. **BRAND NEW £24.95 (B)**
 12v 17 Ah Ultra rugged, all weather, virtually indestructible refillable NICAD stack by ALCAD. Unit features 10 x individual type XL1.5 cells in wooden crate. Supplied to the MOD and made to deliver exceptionally high output currents & withstand long periods of storage in discharged state. Dim cm 61 x 14 x 22 Cost over £250 Supplied unused & tested complete with instructions **£95.00 (E)**

EX EQUIPMENT NICAD cells by GE Removed from equipment and believed in good, but used condition. "F" size 7Ah 6 for £8 (B) Also "D" size 4Ah 4 for £5 (B)

BRAND NEW 85 Mb Disk Drives ONLY £399

End of line purchase enables this brand new unit to be offered at an all time super low price. The NEC D2246 8" 80 Mb disk drive features full CPU control and industry standard SMD interface, Ultra high speed data transfer and access times leave the good old S1506 interface standing. Supplied BRAND NEW with full manual. **Only £399.00 (E)**
 Dual drive, plug in 135 Mb sub system for IBM AT unit in case with PSU etc. **£1499.00 (F)**
 Interface cards for upto 4 drives on IBM AT etc available **Brand new at £395.00**

POWER SUPPLIES

All power supplies operate from 220-240 v AC Many other types from 3v to 10kV in stock. Contact sales office for more details.
PLESSEY PL12-2 Fully enclosed 12v DC 2 amp PSU. Regulated and protected. Dim cm 13.5 x 11 x 11 **New £16.95 (B)**
AC-DC Linear PSU outputs of +5v 5.5a, -5v 0.6a, +24v 5a. Fully regulated and short proof. Dim cm 28 x 12.5 x 7 **New £49.50 (C)**
POWER ONE PHC 24v DC 2 amps Linear PSU fully regulated **New £19.95 (B)**

BOSHERT 13088 switch mode supply ideal disk drives or complete system. +5v 6a, +12.2.5a, -12.0.5a, -5v 0.5a. Dim cm 5.6 x 21 x 10.8 **New £29.95 (B)**

BOSHERT 13090 same as above spec but outputs of +5v 6a, +24v 1.5a, +12v 0.5a, -12v 0.5a **New £39.95 (B)**

GREENDALE 19A01E 60 Watt switch mode outputs +5v 6a, +12v 1a, -12v 1a, +15v 1a. Dim 11 x 20 x 5.5 RFE Tested **£24.95 (B)**
CONVER AC130-3001 High grade VDE spec compact 130 watt switch mode PSU. Outputs give +5v 15a, -5v 1a, + & -12v 6a. Dim 6.5 x 27 x 12.5 Current list price £190. Our price **New £59.95 (C)**
FARNELL G6/40A Compact 5v 40 amp switch mode fully enclosed **New £140.00 (C)**

FARNELL G24 5S Compact 24v 5 amp switch mode fully enclosed **New £95.00 (C)**

Special Offer EXPERIMENTORS PSU

ONLY **£16.95 (C)**

Made to the highest spec for BT this unit gives several fully protected DC outputs most suited to the Electronics Hobbyist. +5v 2a, + & -12v 1a, +24v 1a and +5v fully floating at 50ma. Ideal for school labs etc. Quantity discount available. Fully tested with data RFE = Removed From Equipment

The AMAZING TELEBOX Converts your monitor into a QUALITY COLOUR TELEVISION

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and video monitor turning same into a fabulous colour TV. Don't worry if your monitor doesn't have sound, the TELEBOX even has an integral audio amp for driving a speaker plus an auxiliary output for Headphones or Hi Fi system etc. Many other features: LED Status indicator, Smart moulded case, Mains powered, Built in BS safety specs. Many other uses for TV sound or video etc. Supplied BRAND NEW with full 1 year guarantee. Carriage code (B)



TV SOUND & VIDEO TUNER ONLY **£29.95**

TELEBOX ST for monitors with composite video Input **£29.95**
 TELEBOX ST as ST - but fitted with integral speaker **£34.95**
 TELEBOX RGB for use with analogue RGB monitors **£59.95**

Colour when used with colour CRT. RGB version NOT suitable for IBM-CLONE type colour monitors. DATA sheet on request. PAL, overseas versions CALL.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of IBM and NEW cooling fans.

AC FANS Specify 240 or 110 v
 3" Fan dim 80 x 80 x 38 **£8.50 (B)**
 3.5" ETRI slimline 92 x 92 x 25 **£9.95 (B)**
 4" Fan Dim 120 x 120 x 38 **£9.95 (B)**
 As above - TESTED RFE **Only £4.95 (C)**
 10" round x 3.5" Rotron 10v **£10.95 (B)**
 DC FANS
 Papst Miniature DC fans 62x62x25 mm
 Order 812 6-12v or 814 24v **£15.95 (A)**
 4" 12v DC 12w 120 x 120 x 38 **£12.50 (B)**
 4" 24v DC 8w 120 x 120 x 25 **£14.50 (B)**
 BUHLER 12v DC 62 mm **£12.95 (A)**

1000's of other fans and blowers in stock CALL or SAE for more details

SPECIAL INTEREST

Please call for availability or further info.
RACAL-REDAC real time, colour drafting PCB layout system **£3950**
DEC VAX11/750 inc 2 Mb Ram DZ, and full doc etc. **£275**
BRAND NEW £8500
HP7580A 8 pen digital A1 drum plotter with IEEE interface **As New £4750**
CHEETAH Telex machine **£995**
 1.5 kw 115v 60 Hz power source **£950**
 500 watt INVERTER 24v DC to 240v AC sine wave 50 Hz output **£275**
SOLDER SYSTEMS tin lead roller tinning machine for PCB manufacture **£350**
CALLAN DATA SYSTEMS multi user INTEL based UNIX system complete with software and 40 Mb Winchester disk drive **£2750**
WAYNE KERR RA200 Audio, real time frequency response analyzer **£3000**
TEKTRONIX 1411R PAL TV test signal standard **£600**
TEKTRONIX R140 NTSC TV test signal standard **£875**
HP 3271A Correlator system **£350**
PLESSEY portable Microwave speech / data link 12v DC, 70 mile range. The pair **£275.00**
 19" Rack cabinets 100's in stock from £15.00

DISPLAY ELECTRONICS

All prices for UK Mainland. UK Customers must ADD 15% VAT to total order value. Minimum order, cash £5, Credit Card £10. Official account orders from Government Depts, Universities, Schools & Local Authorities welcome - minimum account order value £25. Carriage charges (A) £1.50, (B) £3.50, (C) £6.50, (D) £8.50, (E) £10.00, (F) £15, (G) Call. All goods are supplied subject to our standard conditions of sale. All guarantees given on a return to base basis. We reserve the right to change prices & specifications without prior notice. Bulk trade & export enquiries most welcome.

MAIL ORDER & OFFICES
 Open Mon-Fri 9.30-5.30
 32 Biggin Way,
 Upper Norwood,
 London SE19 3XF

LONDON SHOP
 1000's of Bargains for callers
 Open Mon-Sat 9.30-5.30
 215 Whitehouse Lane,
 South Norwood, London SE25

DISTEL © The ORIGINAL
 FREE of charge dial up data base
 1000's of items + info ON LINE NOW!!!
 300 baud 01 679 1888, 1200/75 01 679
 6183, 1200 FDX 01 679 8769

ALL ENQUIRIES
01 679 4414
 FAX 01 679 1927
 TELEX 894502





Of all the active leisure pursuits, sailing and cruising probably represent the largest single market to benefit from the dramatic advances in electronic technology. In the last five years microprocessors and miniaturised components have led to a booming proliferation of sophisticated control and monitoring products relating to practically every conceivable aspect of leisure marine. The rapid expansion in the ranges available vividly demonstrates how high-technology is being increasingly applied to satisfy a vast consumer market. This market spent around £570,000,000 during 1987!

With nearly 250,000 visitors to the Boat Show at Earls Court in January, there can be no doubt that many PE readers are amongst those who love messing about in boats. If you are one of that crew, I am sure you will find this review to be of great interest through finding out more about equipment (and some of its scientific background) that can add to your boating pleasure, and to your safety at sea. If you are a devout landlubber, have your eyes opened by reading on and seeing how technology, once having found a foothold, takes giant steps forward. You all could undergo a sea-change.

The report has been compiled from



The Earls Court Marina

benefit to any seafarer, whether on a small craft, or piloting the largest oil tanker. Some are equally usable by motorists and even hikers. With the digital conversion comes the additional benefit of being able to interconnect the sensor to more sophisticated

Judging by data quoted by some manufacturers, the likely variations in the strength of the earth's magnetic field (which varies around the globe) is around 5 to 40 micro Teslas.

Numerous options are available for sensing the pointer position, including pulse counting

BOATING REVOLUTION

information obtained at the Boat Show, from subsequent discussions with manufacturers, and from data offered by other related organisations. It is not a catalogue of all products on the market, but rather, is a look at the different facilities being catered for by an emerging technology, both simple and complex. Though individual products are quoted, it is not implied that they are the only versions available; many manufacturers have similar products and I have no bias towards any particular company.

If anyone would like a list of relevant manufacturers and suppliers who were at the Boat Show please send a small stamped addressed envelope to me at the Editorial address.

Since compasses show us which way to go, let's head off in that direction first ...

MAGNETIC SENSORS

In its conventional form the rotating compass card, dancing around in its containing bowl, is only capable of providing a real-time analogue readout of the magnetic bearing. A variety of electronic methods have become available which allow the bearing to be displayed in a digital format and to be further processed. The techniques are of

BY JOHN BECKER

A LIFE ON THE OCEAN WAVE-GUIDE


Modern craft do not so much make use of the sea as exploit a hi-tech highway. (With apologies to Joseph Conrad - *The Mirror of the Sea*, 1906.)

equipment, such as computers, automatic navigators and chart plotters.

Technology has provided us with several ways by which the compass bearing can be sensed and digitised. It can be assessed indirectly by monitoring the position of a compass pointer, or directly by sensing the direction and strength of a magnetic field.

or proximity detection by means of optical, magnetic or mechanical detectors. For directly sensing magnetic fields, I am aware of three techniques: using fluxgates, Hall effect devices or magneto-resistive products. Only the first two appear to be in common use.

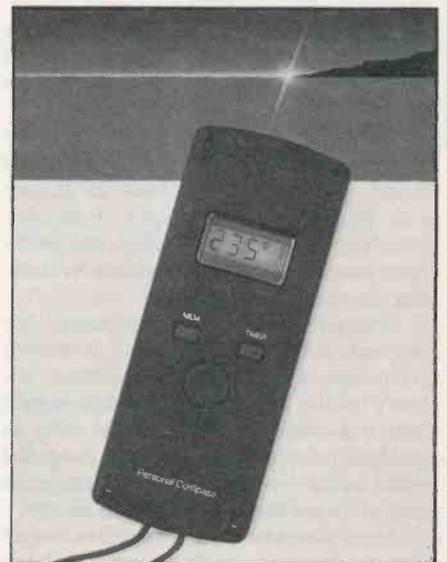Fluxgate techniques involve the complex frequency relationship between the fields



Autohelm personal compass



NASA Marine Stingray compass set

induced in one or more coils; Hall effect devices produce an output current or voltage proportional to the strength and direction of a magnetic field; magneto-resistive products change their resistance in response to magnetic field variations.

Some commercial digital compasses make use of Hall effect devices, though the vast majority use the fluxgate technique, employing microprocessors to establish the correct bearing and its digital reading.

PRACTICAL COMPASSES

It is practical, and cost effective, for even the smallest craft to use a digital compass of some type. These range from simple all-in-one units containing the sensor, decoding circuitry and display, to those comprising a remote sensor well away from interference, a display in a position convenient to the helmsman or pilot, and a range of interfaces to other navigation equipment. It seems that no manufacturer bothers to produce a digital compass that does nothing else - they take advantage of miniaturisation and microprocessor control to incorporate other features, such as deviation from desired heading, variable damping, correction inputs and even additional analogue readouts.

The nearest exception to the last statement is Autohelm, who have a small handheld digital compass using the latest in fluxgate and microprocessor techniques. Even this, though, also has memory storage and timing functions. This instrument is ideal for land-based use as well as marine.

Otherwise, the simple units are represented by those such as lcd steering compasses. Displaying, for example, the boat's heading as a digital readout in degrees from 0 to 360°, the steering angle using an analogue pointer, the course made good, and with tactical self-checking for errors of magnetic disturbance or low battery voltage.

Most compass units allow selection of variable damping to electronically stabilise readings to suit sea conditions, fast in response

to calm weather, progressively slower for rougher weather. Across the spectrum of different compasses, typical accuracies seem to be within about 1°. Widespread use is made of keyboard data entry pads for entire ranges of functions, companies vying with each other to stress how waterproof they are even in atrocious sea conditions.

Incidentally, in my report on *Electronica 88* in *PE Feb 89*, I had meant to comment (but forgot!) on how many items of electronic apparatus are now designed for resistance to harsh environments. There were examples of multimeters and even computer keyboards shown immersed in water as well as covered by sand.

Typical of the more advanced electronic compasses is one of Rigel's. It uses a microprocessor controlled fluxgate sensor taking many thousands of readings per second, averaging them and displaying the


bearing on an lcd in both digital and analogue format. It shows how far off course a craft may be on an analogue display, and an audible intermittent tone increasingly sounds if the vessel deviates from the selected course. It shows the direction and rate of turns, has selectable damping factors, automatic deviation correction and even automatic compensation for angles of dip up to 80° north or south. Just by turning the boat through one full circle it establishes the coefficients for calculating bearings, and then automatically locks the display onto the desired heading. It interfaces to satellite navigators, autopilots and on-board computers.


One of the more surprising compasses available is one for the blind! Apparently, there are many visually handicapped yacht sailors and Autohelm have produced a unit that provides a spoken output of the compass heading, updating it every few seconds. The target course can be set in 1° or 10° steps, and once on course a push button locks the heading into memory. Then a high/low pulse tone indicates off-course errors both in direction and magnitude. When sailing to windward a double push button is used to initiate a tack routine, automatically talking the skipper onto course for the new tack. Autohelm say that with this speaking compass the blind only need sighted help in order to keep a secure lookout.

CRAFT SPEED

Speed measurement is usually done by counting pulses generated by Hall effect sensors. In principle, this simply involves the use of a magnet attached to a rotating shaft inducing pulses across a fixed sensor. It is also possible to use shaft rotation for turning a motor, so producing an ac or dc voltage, either

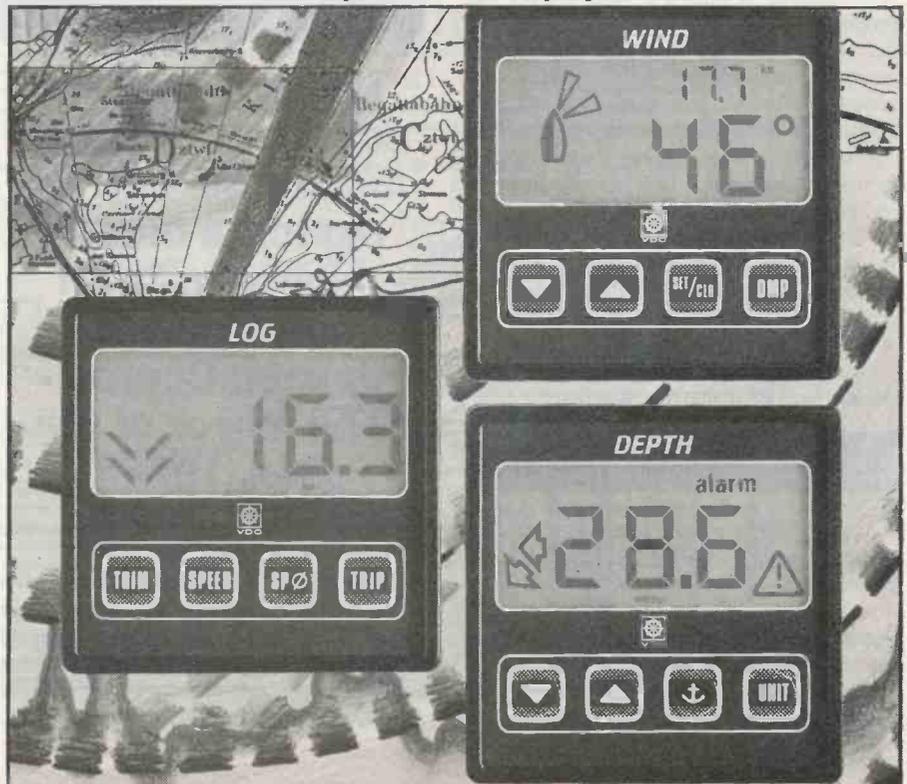A selection of VDU's compact sensor displays



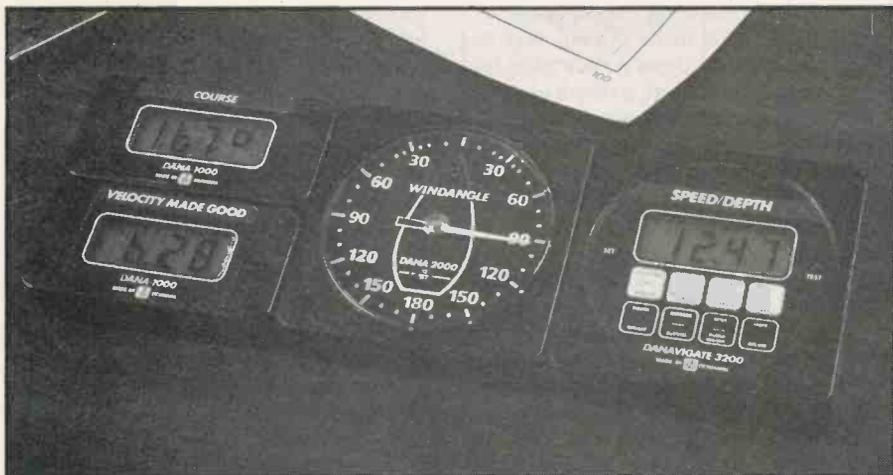

Typical repeaters in the Dana range

of which can be readily measured. Speeds of up to 30 knots are allowed for by most instruments, though some are intended for powerboats and typically can monitor up to 50 or 60 knots. Some units record and display the peak speeds reached - always a good talking point!

Two basic types of transducer appear to be in common use, the tunnel propeller and the paddle wheel. Both types are prone to non-linear reaction to the force of water driving them, largely due to the turbulence created along the hull. Electronics can be used to partly compensate for the effects and some models have calibration adjustments built in to fine tune readings to suit the craft. Different rates of sampling are selectable by many instruments, typically variable from one second to six seconds, so allowing for different sea and speed conditions. Electronics cannot yet solve the problem of rotor fouling by seaweed, but it can monitor the condition and some units have a "rotation stopped" sensor coupled to the display readout.

At the simple level, Autonnic have a speed monitor specially for wind surfers. It uses a

tunnel propeller sensor, needs no cut-outs in the board, basically using a special tape bonding technique to hold it in place. It runs from a PP3 battery which can power it for up to 300 hours - typically representing a year's active use. Other speed monitors are specifically designed for training and regatta use. Some of these can also monitor a craft's trim and have facilities for plugging in a wind speed sensor.

DISTANCE LOGS

Most speed instruments combine distance readouts as well - it's relatively easy to convert the revolution data to represent both speed and distance. Distance logging commonly allows monitors to measure up to around 1000 nautical miles (nm), though 300 nm and 10,000 nm models are available. Most speed and log monitors provide a variety of memory mode and function options, usually keypad operated with suitable water resistance. So that data is not lost during battery changing, many models use a non-

volatile memory (nvram), with data retention periods quoted from around three months up to five or more years.

Several levels of memory storage and timing are common. For example, permanent memory stores for recording the total distance travelled; resettable trip distance memory; timers that count up in hours, minutes and seconds; timers counting down from a preset time for race starting purposes; and timers serving as stop watches for lap timing.

Many logs are designed for interfacing with satellite navigation equipment, typically producing 100 pulses per nm.

WIND SPEED

A wide variety of wind speed and direction monitors is obtainable for use in different situations. The impellers are normally designed for masthead mounting, frequently using Hall effect sensors. Data is usually transmitted by wires, though fiberoptic links are becoming common. Dana mention a rate of 1.65 pulses per knot, but otherwise data rates seem to be generally unquoted. The impellers and their monitors typically cater for speed ranges variably expressed in units of up to 40 m/sec, 80 knots, or 0-15 on the Beaufort scale. They are commonly designed for accuracies of up to ± 1 knot within temperature ranges of -10° to $+70^{\circ}$ C.

Liquid crystal displays are used for both analogue and digital representation, some of them making use of colour. Models show information relating to such diverse functions as apparent wind speed (relative to the craft's speed), true speed, apparent wind angle, and the tack in degrees highlighted in red and green for port and starboard. Other functions include representations of the velocity made good, speed up-wind or down-wind, and trim control.

Some models allow maximum permissible wind speed and off-course limitations to be set, with audible and visual alarm outputs, and visual recall of maximum wind speeds experienced. Many wind monitors can be interfaced to other instruments for measurement of factors that build up a complete picture of a yacht's performance. At the simplest end of these options, Autonnic have a low cost handheld wind speed sensor accessory for plugging into meters such as their water speed unit.

Nearly as simple is a handheld wind speed monitor from Monro. It gives an instant digital readout in knots, and is probably of equal interest to those on land as well as at sea.

REPEATERS AND MULTIFUNCTIONS

Secondary display units for use in conjunction with main sensors are available from many companies. These can be positioned in any required convenient position on other parts of craft. Many of the single

Seafarer Microlog - provides 18 microprocessor controlled navigation functions





Lowrance LCD fish finder and recorder

Far more common now are recording sounders with microprocessor controlled memory storage, plus video or lcd displays. One of Lowrance's models uses a widescreen supertwist liquid crystal display graph having 128 vertical pixels. They say it is suitable even for high boat speeds and is as easy to operate as a bank's automated cash machine: the user does little more than answer on-screen questions to tune the unit to personal needs.

Koden claim to have invented the first colour video sounder and have a variety of models. One of them has 17 display modes, plus 12 split-screen modes. Such techniques require intensive use of computerisation and sophisticated software algorithms.

Multiple sonar sounders are available for simultaneous sideways and downwards scanning. These facilitate locating fish and underwater features such as ledges and rocks. They are ideal for navigating through narrow channels right up to the berth, even in zero visibility. Kelvin Hughes have a unit that uses three transducers, one looking downwards, and two for side scan operation each variable between +4° and -90° by remote control. The power output is an incredible 3300W rms reaching down to 4500 feet. Their display screen shows images in 16-colour detail.

FISH FINDERS

Many companies stress the importance they place on their units being able to detect fish from their echo shapes. In this way fish can be seen suspended in weed or holding close to the bottom and, apparently, expert fishermen are capable of telling the type of fish displayed. Some models can detect fish only three inches long and within three inches

of the bottom. One depth recorder is specifically called a Fish Finder. It has a high resolution supertwist nematic lcd screen and a display-freeze function allowing the image to be studied at leisure.

Hummingbird say that they pioneered fish identification about two years ago. Their TCR model uses a thin film transistor screen having over 115,000 pixels and showing the fish in red! They go a couple of stages further still - they show bigger fish in red with a black dot behind them and have an alarm that sounds when they are detected. Many depth sounders have water temperature sensors as well since fish are often to be found in warmer waters. Kelvin Hughes' colour sounder MS705 resolves water temperature to within 0.2° between 0-50°C.

LOCH NESS

And talking of fish finders - Lowrance seem proud that their depth recorders were used to search for the Loch Ness Monster! In November 1987 a team of scientists led an expedition, Operation Deepscan, to sweep Loch Ness with sonar instruments. Twenty four boats equipped with Lowrance X16s (interestingly, these are paper chart recorders) were positioned across the one mile loch width and made two passes at slow speed over the entire 23 mile length. In many places the loch is over 200 metres deep and several sonar contacts were made with moving objects at depths below 46 metres, including one significant contact at 185 metres. But despite this concerted effort follow-up boats were unable to locate the same objects, and the results remain inconclusive. I don't think I'd feel safe to dive there, though!

MANUFACTURING INFO

Lowrance are particularly informative about their manufacturing techniques. They say they use streamlined robotic assembly procedures and make use of surface mounting devices (smds). The latter is interesting to know since I have previously commented that smds seem to be slow in finding manufacturing acceptance. Their products are all designed to withstand total submersion in water, and the displays are filled with nitrogen to prevent fogging. In their labs test samples are pounded, frozen, sprayed with both fresh and salt water, and heated to 150°C. Each product is thoroughly bench tested for eight hours, and samples from each week's production are further run for 500 hours - the

Furuno colour video sonar



equivalent of more than sixty 8-hour fishing days. Some of these units are then continuously tested for 5000 hours. No wonder they can safely offer a full three year warranty.

The same company advise that the key to higher definition and wider viewing angle on a liquid crystal graph display is the vertical count of high contrast blue pixels. These screens are designed not to black-out in high temperatures (I've had cheap in-car lcd clocks that do this on hot sunny days - a rare but aggravating phenomenon).

Their comments on transducer frequencies are valuable, especially to anyone thinking of making a depth sounder. 50kHz is satisfactory for deep water or where ground discrimination is important, but it suffers from poor definition. Frequencies of around 200kHz are best for use in depths under 150-200 feet and give better target separation and definition. 455kHz is even better! Wide angle sensors are best for broad bottom coverage, narrow angles are required for high definition. Transducers having various transmission angles and operating at all these frequencies are found amongst sounders right across the range.

DIVE COMPUTERS

No mention of depth would be complete without mentioning the decompression computers now coming in for scuba divers. As you probably know, in order to avoid decompression sickness (the bends), a diver can only stay under water for a given length of time, irrespective of the air available. The total duration is determined by the maximum depth, the time spent at that and intermediate depths, the temperature of the water, the lapsed time since an earlier dive, and the diver's physical make up (ignoring the diver's alcohol content - we like our beer!)

Previously, we would make estimations from printed charts or circular plastic "calculators", and try to remember the figures during the dive, not always with the greatest accuracy. Now electronics has come to our assistance and several companies sell decompression computers which are worn on the arm and show a variety of parameters.

One such model is the Edge, the electronic dive guide from Orca Industries, and probably the top of the range. The Edge does not merely read a set of tables, but continuously calculates and displays data for twelve different body groups. The display shows the remaining no-decompression time or remaining decompression time, the safe ascent depth, the dive time, maximum depth, water temperature, surface interval time, and scrolling repetitive dive table. Such aids to safety would have been unthinkable without microchip technology. Incidentally, underwater video cameras are also now available for scuba divers.

BAROMETERS

Much to my surprise, it seems that there are no electronic barometers readily available to the leisure cruising market. If you want one you can always build the barometer project we published in the Sep-Oct 88 issues - another first for PE, it seems!

ELECTRONIC MISCELLANY

Mains inverters which convert 12V and 24V dc boat supplies to mains voltages for powering domestic equipment, such as tv, video, hifi etc, are well catered for. Abbey Transformers enable you to monitor your electricity consumption with their Portometer - its ideal for caravans as well as boats. The Autolite, from Rochford Marine, is a light activated automatic switch specifically designed for marine applications, such as turning on anchor lights at dusk.


Ventilation is another subject that can be put under electronic control. Swiftech have a solar powered ventilator, additionally backed up by a nicad rechargeable battery.

SEXTANT COMPUTER

This computer does not do away with the need for a sextant, but it does take the chore out of the calculations. The software includes a full sun almanac to the year 2000, has six programs and holds data on up to ten stars of your choice. The star calculator program gives the azimuth and the intercept, and enables the unit to be used day or night. Basically, all you do is take two sights with a short interval between them, enter the dates, times and altitudes into the computer and it tells you where you are to within three miles, anywhere on earth. To the computer, the maths are a doddle - all it does is resolve the spherical trigonometric equations provided by the crossing of two Great Circles, and Neptune's your uncle! (but thank Autonnac for this goody).

PC NAVIGATION SIMULATION

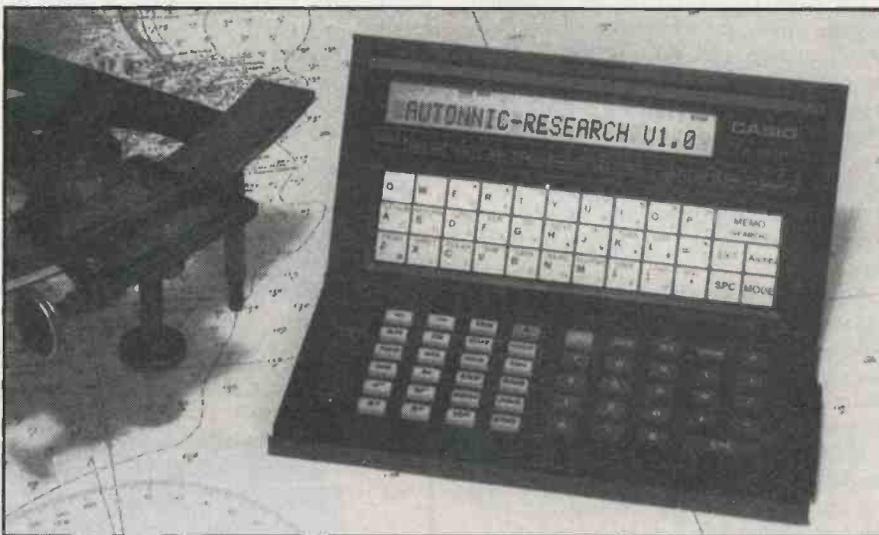Not surprisingly, software is available for yachtsmen who wish to practise navigation all the year round without getting their feet wet.



Autonnac sextant computer

Home cooking at sea is becoming serviced by all mod-cons. Powamate have introduced what they claim is the world's first microwave cooker designed to run from 12V or 24V dc supplies.

Consideration to safe and fast battery charging has been given by TWC Systems. Their regulator is intended for use in series between a generator and the battery, and efficiently controls the full charging of batteries.

Solar panels for marine use are available from Ampair and PAG Solar Technology. Some of the feature points are that they are flexible, waterproof, robust, and non-slip. They come in a variety of shapes and sizes.

Ampair also go in for wind driven generators. They can be mounted to the mast, on deck, or even in your back garden at home.

Pilot Courseware have a software training package suitable for any IBM compatible PC, including the Amstrad 1512 and 1640, which enables you to become the armchair skipper of a 36 foot yacht with auxiliary engine. You sail round the challenging waters of the Channel Isles in realistic conditions with 3D seascape views from the yacht. Your tools are a hand bearing compass, a full range of cockpit instruments including Decca receiver and an electronic chart. Weather, tide, land, buoys, lighthouses and boat performance are all accurately modelled, and there are print, save and jump forward options. The program comes on disk and is equally usable with ega, vga and cga screens. **PE**


Next month we look at computerised navigation and plotting, radar, and global communications.

Are we about to create a race of Supermen?

Brainwave

β BETA – Concentration, problem solving, active thought.
α ALPHA – Relaxation, pleasure, tranquility, positive feelings.
θ THETA – Imagination, creativity, hypnotic imagery.

monitor

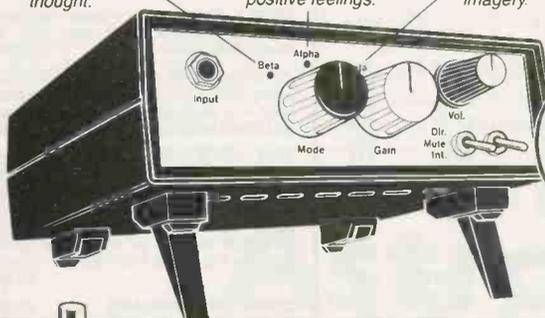

BRAINWAVE MONITOR PARTS SET ONLY
£39.80
 + VAT

The ETI Brainwave Monitor must be the most astonishing project ever to appear in the pages of an electronics magazine. It will allow you to hear your brainwaves and judge the relative levels of various types. It will also help you to control your mind more effectively, to be at peak performance in all situations.

Doesn't my mind work perfectly well when left to its own devices?

If you've ever been confused, unsure of yourself, shy, unable to pass exams or to impress people at interviews, you know perfectly well that it doesn't. Your mind (and everybody else's) is full of bad habits, inappropriate responses, feelings of inadequacy, all pulling you down. Why should you put up with it?

Mind training sounds like hard work!

It can be. If you want to do it the hard way, go and study under a Zen master for fifty years or so. You'll get there in the end! With the brainwave monitor it takes no effort at all. Just the opposite in fact – trying is the one thing you mustn't do!

How do I start?

At first you use the monitor's internal indicator to exercise your mind. In direct mode you improve the time percentage, in integrate you concentrate on the amplitude. After that, the choice of direction is yours. With the Alpha Plan you can reach the core of your personality to root out the weakness and replace it with inner strength. Otherwise you can just enjoy the feelings of pleasure and clear headedness that alpha training brings, or the creativity and imagery of the theta state.

A friend told me I can use brain power to control lights and things. I can't believe it!

As a matter of fact, you can do more than that! The interface sockets on the monitor allow you to turn lights on and off, control toys and electrical gadgets, play computer games, all with your mind! Are we about to create a race of Supermen? Only time will tell.

The Brainwave Monitor is featured in the September, October and November 1987 issues of ETI. The approved parts set contains: two PCBs, all components including three PMI precision amplifiers, shielded box for screening the bio-amplifier, attractive instrument case with tilting feet, controls, switches, knobs, plugs and sockets, leads and materials for electrodes, full instructions for assembly and use.

Parts are available separately. We also have a range of accessories, professional electrodes, books, etc. Please send a stamped, self-addressed envelope if you just want the lists. Otherwise, an SAE + £2 will bring you lists, construction details and further information.



SILVER SOLUTION

This powerful silver plating compound must be the greatest revolution in electronics since the IC! Just wipe on with a cloth to plate PCB tracks, connectors, wire, component leads, etc. with a layer of pure silver!

Essential for:

- * RF circuits
- * Top flight Hi-Fi
- * Bio-electronic circuits and electrodes

LARGE BOTTLE (150ml) SILVER SOLUTION £14.20 + VAT!
 N.B. The solution will take to brass, copper, etc. but not to steel or pre-plated components.



THE ALPHA PLAN

Can you really train your brain to think more effectively?
 Can you really achieve peak performance in things you're 'no good at'?
 Can you really overcome fear, shyness, uncertainty?
 And can you do it all without really trying?

Dr. David Lewis's famous Alpha Plan has all the answers. It was recently investigated by a QED television documentary (Alpha – How to Succeed Without Really Trying). And the conclusion? It works!

Dr. Lewis's book 'The Alpha Plan' is yours for only **£2.50** (no VAT).
Your future is waiting.

Complete Parts Sets for ETI Projects

MAINS CONDITIONER

FEATURED IN ETI, SEPTEMBER 1986

It is astonishing how many people buy or build top-flight hi-fi equipment, and then connect it to a noisy, spiky mains supply. Rather like buying a Ferrari and trying to run it on paraffin, you might think. Expecting crystal clear sound, the poor music enthusiast ends up with a muddy, confused mush, and feels that he has somehow been cheated. 'Is this hi-fi?' My music centre sounded just as good!


The domestic mains supply is riddled with RF interference, noise, transient spikes, and goodness knows what else. Computers crash, radios pop and crackle, tape recordings are spoiled and hi-fi sounds 'not quite right'. Why put up with it when the solution is so simple? The ETI mains conditioner is the lowest cost upgrade you will ever buy, and probably the most effective!

Our approved parts set consists of PCB, all components, toroid, enamelled wire, fixing ties, fast response VDR, and full instructions.

ETI MAINS CONDITIONER PARTS SET

ONLY £5.40! + VAT

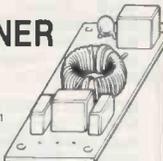*Note: the toroid and VDR supplied are superior to the types specified in the article.



KNIGHT RAIDER

FEATURED IN ETI, JULY 1987

The ultimate in lighting effects for your Lamborghini, Maserati, BMW (or any other car, for that matter). Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves lazily from left to right leaving a comet's tail behind it. Flip the switch again and the point of light becomes a star, bouncing backwards and forwards along the row. Press again and try one of the other six patterns. An LED display on the control box let's you see what the main lights are doing.

The Knight Raider can be fitted to any car. It makes an excellent log light) or with low powered bulbs it can turn any chic's pedal car or bicycle into a spectacular 'TV age' toy!

The control box parts set consists of case, switches, LEDs, PCB components, hardware and instructions. The sequence board includes PCB, ICs, power FETs, components, hardware and instructions.

KNIGHT RAIDER CONTROL BOX ONLY

£7.90 + VAT!

KNIGHT RAIDER SEQUENCE BOARD ONLY

£15.90 + VAT!

MATCHBOX AMPLIFIER

FEATURED IN ETI, APRIL 1986

No ordinary amplifiers, these. When our first customer's took an interest, it was for the diminutive size (both modules will fit in a matchbox!), the total disregard for power supplies and speaker impedances, and the impressive power output from these little amplifiers. When they re-ordered, it was for the sound quality.

Two amplifier modules were described, both based on the powerful L165V IC. The single IC version will deliver over 20 Watts with a suitable speaker and power supply. The bridge version can provide up to 50W! Although the specified supply voltage and speaker impedance must be used to achieve maximum power, both modules are quite happy to work from any voltage between 12V and 32V, and will accommodate any type of speaker. The bridge version is ideal for giving a boost to car hi-fi systems, driving two 4 Ohm speakers in parallel on each channel for best effect.


Both designer-approved parts sets consist of a roller-tinned printed circuit board and all components. The L165V ICs are also available individually, with a free mini data sheet giving specifications and suggested circuits.

SINGLE IC MATCHBOX AMPLIFIER SET

(20W into 4 Ohms) £6.50 + VAT

BRIDGE AMPLIFIER SET

(50W into 8 Ohms) £8.90 + VAT

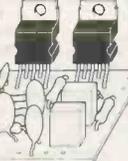

POWERFUL AIR IONISER

FEATURED IN ETI, JULY 1986

Ions have been described as 'vitamins of the air' by the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than dead air.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products, was reliable, good to build, and fun! Apart from the serious applications, some of the suggested experiments were outrageous! We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller-tinned printed circuit board, 56 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs about a third of the price of the individual components. What more can we say?

We can supply a matched set of parts, fully approved by the designer, to build this unique project.

The set includes a roller-tinned printed circuit board, 56 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs about a third of the price of the individual components. What more can we say?

Instructions are included

DIRECT ION PARTS SET £12.60 + VAT



PROJECT BOX

PROJECT CASE WITH PP3 BATTERY COMPARTMENT

ONLY £2.60! + VAT



LM2917 EXPERIMENTER SET

Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the 'Next Great Little IC' feature (ETI, December 1986).

LM2917 Experimenter Set £5.80 + VAT

RUGGED PLASTIC CASE

Suitable for mains conditioner and mains controller.

ONLY £1.80 + VAT



SPECIAL OFFER

Our best selling ioniser kit is now available with an elegant white case

WHITE IONISER PARTS SET ONLY £12.80! + VAT

Prices shown are exclusive of VAT, so please add 15% to the order total. UK postage is 80p on any order. Carriage and insurance for overseas orders £4.50. Please allow up to 14 days for delivery.

Specialist SEMICONDUCTORS LIMITED

FOUNDERS HOUSE
 REDBROOK
 MONMOUTH
 GWENT

NEW THIS MONTH

SWITCH BARGAINS

50,000 miniature switches by C&K. Top quality sub-min and mintoggle, rocker, slide, lever & push switches from 5p each!! Over 100 types in Bargain List 46, together with 15,000 thumbwheel switches from 20p & 5,000 DIL switches from 5p. Ask for your FREE copy now!!

Z808 Mega Solar Cell - This 300x300mm unit incorporates glass screen and backing panel, so is very robust. Wires are attached. Output is 12V 200mA min on a sunny summer day. Can be series or parallel wired for greater output. £24 ea (difficult to pack singly) or box of 7 for £99.

LCD DISPLAYS

Z4115 8 digit 12.7mm high, with holder. 14 seg allowing alpha-numeric display. List £15+ £4.50
Z4148 6 digit as above £3.00
Z1637 3.5 digit direct drive, sim to RS588-572. 12.7mm digits. £2; 10/£17.50; 100/£100

TEST GEAR

AG2603 AUDIO GENERATOR/COUNTER. Combination unit with 6 digit display Generator has a freq range from 10Hz-1MHz sine or sq wave. The counter operates from 10Hz-150MHz from internal or external source. Excellent value at £175

SG4162 RF GENERATOR/COUNTER. Similar to above, but generator has a range from 100kHz-150MHz £179

SE6100 SIGNAL TRACER £55

FC5250 FREQUENCY COUNTER, 10Hz-150MHz £65

CM3300 CAPACITANCE METER 0.1pF-99.9mF £65

Full details of all above on request.

SEMICONDUCTORS

Hundreds in Cat - look at these sample prices:
LM317K £1.00; 68008L £3; 27C256-25 £5; 68A00 £1.20; LM223K £3; DL1416 £7; RBG1000 £1.20; DL3416 £8; 555 20p; 741 20p; 74LS240 25p

HALF PRICE KITS!!

Range of 'OK' Kits at half price!! 5 diff. top quality kits containing all parts, inc. PCB, plastic case and comprehensive instructions!

- EK1 Quick Reaction £2.90
- EK2 Electronic Organ £3.34
- EK3 Digital Roulette £4.29
- EK4 Electronic Dice £3.98
- EK5 Morse Code Oscillator £1.99

CURRAH MICROSPEECH

We've bought up remaining stocks of this popular add-on to re-sell at a fraction of the original cost!

Z4140 New complete set for ZX Spectrum unboxed. (They were bulk packer) £7.95

Z4142 Speech 64 for the C64. No software needed! New and working, but no case. With full instructions. £6.00

Z4138 Microslot 'T' connector allowing peripherals to be connected to the Spectrum. New & boxed £2.00

Also a quantity of 'returns' available - see Bargain List 43 for details



Z811 Cumana touch pad for the BBC B computer. Enables you to draw on the screen using the stylus with the touch sensitive pad. Supplied with 2 stylis, power/connecting leads and demo tape with 4 progs. Originally sold at £79.95. Our price: £19.95

1989 CATALOGUE

- ★ 100 BIG pages of components and equipment
- ★ Low, low prices
- ★ Fast "by return" service
- ★ 28 pages of Surplus Bargains
- ★ Only £1 - send for yours now!

32 page **SPRING SUPPLEMENT** featuring Calculators, Disco Gear, Speaker Cabs, Metex Meters, + lots of surplus! **FREE** with Cat, or send large SAE.

WIN a top of the range Metex Meter! Enter our Competition - full details in the Spring Supplement!
FREE Headphones + Speakers - Full details in the Spring Supplement.

SPEECH SYNTHESIZER KIT

Z315 All parts inc. PCB to make a speech synth for the BBC micro £4.99

Z316 De-luxe version - also includes V215 case, 1m 20W cable plus connector £7.99

MICRO PANELS

Z620 68000 Panel. PCB 190 x 45 believed to be from ICL's 'One per Desk' computer containing MC68008P8 (8MHz) 16/8 bit microprocessor, + 4 ROM's all in skts; TMP5220CNL, 74HCT245, 138, LS08, 38 etc. £5.00

VIDEOTAPES - Top quality VHS E180 tapes by Videolab at unbelievable prices! £2.50ea; 10/£20; 40/£64.

13A TEST PLUG - 2 neons illuminate to show any faults on line Only 99p

SOLDER BARGAIN

Shipping error to our supplier means you benefit! 500gm reel of 16SWG resin cored solder at a low, low price. **ONLY £3.95; 10 reels £33.00; 50 reels £150.00**

EPSON SERIAL INTERFACES

Model 8143 £15
Model 8143 with 2k buffer £25
Just arrived - full details on next list

COMPONENT PACKS

K560 Semiconductors - Over the years we have purchased many transistors, diodes, ICs etc. which for one reason or another have accumulated in one of our stock rooms. Rather than spend weeks sorting and listing them, we have decided to make them into packs. All components are full spec marked devices. Some may be coded. We believe this to be one of the best value packs ever offered, as many high value components are included. Packs are made up by weight; this means contents are very approximate - if there are several bulky power devices, there will be considerably fewer parts than those packs containing all small signal items.
Pack of approx 100 £5.50
Pack of approx 250 £12.00
Pack of approx 1000 £40.00

K539 Led Pack - not only round but many shaped leds in this pack in red, yellow, green, orange and clear. Fantastic mix.
100 £5.95 250 £13.50

K547 Zener Diodes - Glass and plastic. 250mW to 5W ranging from 3V to 180V. All readily identifiable. **100 for £4.50**

K546 Polystyrene/mica/ceramic caps. - Lots of useful small value caps up to about .01µF in voltages up to 8kV. Good variety.
100 £2.75

K528 Electrolytic Pack - All ready cropped for PCB mounting, this pack offers excellent value for money. Good range of values and voltages from 0.47µF to 1000µF, 6V to 100V
100 £3.95 250 £8.95 1000 £32

K518 200 Disc Ceramic Caps - Big variety of values and voltages from a few pF to 2.2µF; 3V to 3kV **£1.00**

K530 100 Assorted Polyester Caps - All new modern components, radial and axial leads. All values from 0.01 to 1µF at voltages from 63 to 1000V!
Super value at £3.95

DIL SOCKETS

Must clear excess stocks - 1/4 million low profile top quality IC sockets to dispose of!

Pins	10	100	1000
8	40p	£3.00	£20
14	68p	£5.10	£34
16	72p	£5.40	£36
18	76p	£5.70	£38
20	80p	£6.00	£40
22	84p	£6.30	£42
24	88p	£6.60	£44
28	92p	£6.90	£46
40	96p	£7.20	£48

'D' CONNECTORS

	15W	25W	37W
R/A plugs	40p	50p	60p
R/A skts	50p	60p	70p
W/W plugs	40p	50p	60p
W/W skts	50p	60p	70p
S/P plugs	40p	50p	60p
S/P skts	50p	60p	70p

All top quality gold plated

Z345 OPTICAL SHAFT ENCODER. Similar to RS631-632, but 80% cheaper! **£8.50**

K520 Switch Pack - 20 different assorted switches - rocker, slide, push, rotary, toggle, micro etc.
Amazing value at only £2.00

K569 Reed Switch Pack. A selection of about 15 types of reed switch from submin 12mm long to 5A rated 50mm long, mostly form A (make), few form C (Change-over).
Pack of 30 £2.75

K540 Resistor Pack - mostly 1/8, 1/4 and 1/2W, also some 1 and 2W in carbon, film, oxide etc. All have full length leads. Tolerances from 5 to 20%. Excellent range of values. **500 £2.50 2500 £11.00**

K503 100 Wirewound Resistors - From 1W to 12W, with a good range of values. **£2.00**

JOYSTICKS

Z004 Skeleton Joystick, switch type. Good quality, made by AB. Brass spindle has 44mm long black plastic handle attached. Body has 4 mounting holes. These really are a fantastic bargain! **Only £1.00**

Z8831 Dragon Joystick. Made by Dragon Data. Hand-held with fire button. 2m lead with 5 pin DIN plug. Uses 2 x 100k pots. **£3.00**

Z615 BBC Joystick. Internal resistors give the required voltage levels. 2 fire buttons. Rubber suction feet. 120 x 110 x 155 **£3.00**

POWER SUPPLIES

Z975 Cased PSU 92x57x45mm with built-in 13A mains plug. Output 14V ac @ 600mA. **£3.00**

Siliconix mains PSU 62x46x35mm with built-in cont. 2 pin plug. Output 4.5V DC 100mA to 3.5mm plug **ONLY £1.00**

Z4113 BBC Computer PSU (early models). Steel case 158 x 72 x 55mm, 2m long mains lead, rocker switch, fused. Outputs: +5V at 2.5A; -5V at 100mA **£3.95**

Z4170 Plug in power supply. Built in 13A plug. Output 6V DC 300mA on 2m long lead terminated in a 3mm power plug. British Made to BS415 **£1.50**

KEYBOARDS



Z8852 Keyboard: Superb brand new keyboard 392x181 with LCD displaying 1 line of 10 characters & a further line with various symbols. 100 keys, inc separate numeric keypad. Chips on board are 2x74HC05, 80C48. **£15.00**



Z8848 Alphanumeric plus separate numeric keyboard. 104 keys plus 11 chips. 442x175mm. **£12.00**

Z4116 24 way (8 x 3) membrane keypad. Large (200 x 90mm) area - they were used in a teaching aid. Overlay template and pinout supplied. **£3.00**

Z810 KEYBOARD Really smart alpha numeric standard qwerty keyboard with separate numeric keypad, from ICL's 'One Per Desk'. Nicely laid out keys with good tactile feel. Not encoded - matrix output from PCB taken to 20 way ribbon cable. Made by Alps. Size 333x106mm. **£8.95**

COMPUTER KEYBOARD £4.00
Yes, only £4 for this Cherry keyboard - 67 full travel keys inc. function keys. Size 340x130mm. Pale/dark brown **£4.00**

Z8863 KEYBOARD - High quality by Micros witch. 69 keys, 6 LED's, 15 various LS chips + socketed D8048 by Intel. Output via 7 way plug. Size 317x170mm **£12.00**



GREEN SCREEN HI-RES 12in MONITOR CHASSIS

Brand new and complete except for case, the super high definition (1000 lines at centre) makes this monitor ideal for computer applications. Operates from 12V d.c. at 1.1A. Supplied complete with circuit diagram and 2 pots for brilliance/contrast, plus connecting instructions. Standard input from IBM machines, slight mod (details included) for other computers **Only £24.95+£3 carr.**

MONITOR INTERFACE KIT

Enables our hi-res monitor (above) and most others to be used with virtually any computer, PCB **£3.00**
Complete set of on-board components plus regulator and heatsink **£9.95**
Suitable transformer for interface and above monitor **£5.31**

Z8837 DUAL SHEET FEEDER.

Brand new breakdown unit. Contains 3 x 12V stepper motors (48 step) plus driver pannel with 4 x TIP115, 4 x TIP110, LM3302, 2 x 7407; 2 solenoids, buzzer, microswitches, control panel, 2 optocouplers plus lots of gears and mechanical bits. **£24.95+£3 carr.**

Z8862 10 game video unit - 2 hand held controllers with joysticks, beautifully made. Requires 7.5V DC input (suitable PSU £2.95). Composite video and sound outputs (modulator + wiring details for direct connection to TV £6) **£9.95**

Z8858 Hitachi Video Battery Charger BC60U for DP60 batts used in GP7 camera. Extremely high quality unit. **£17.00**

NOTICE TO RETAILERS

Greenweld Electronics Ltd. have been appointed Official Wholesalers of Verobloc, Veroboard, Easwire and Accessories by Vero. We will be only too happy to supply all your Veroboard requirements at Trade Price. Ring, write or fax us for full information and prices.

SOLDER SPECIAL!!
* 15W 240V ac soldering iron
* High power desolder pump
* Large tube solder
ALL FOR £7.95



All prices include VAT; just add £1.00 P&P; Min. credit card £5. No CWO min. Official orders from schools welcome - min. invoice charge £10.00. Our shop has enormous stocks of components and is open 9-5.30 Mon-Sat. Come and see us!
HOW TO CONTACT US
By post using the address below; by phone (0703) 772501 or 783740 (ansaphone out of business hours); by FAX (0703) 787555; by EMail Telecom Gold 72:MAG36026; by Telex 265871 MONREF G quoting 72:MAG36026.

443C MILLBROOK ROAD, SOUTHAMPTON, SO1 0HX.



For a basic solar heating system, such as that in Fig. 1, a heat transfer fluid (usually water) is pumped through the solar collector where the fluid gains heat. It then passes through a heat exchanger coil where most of the heat gained is transferred to the stored water. A temperature sensor is attached close to the solar collector output and another on the storage cylinder, and the electrical output from each of these sensors is fed to a differential temperature controller. The controller switches the pump motor on when sensor 2 output is greater than that of sensor 1 (ie, when the fluid in the collector is hotter than the stored water). Heat is thus transferred to the stored water through the heat exchanger. The controller switches the pump off when sensor 2 output is less than that of sensor 1, so preventing heat being transferred back to the solar collector and lost, during the night or when the weather is dull, for example.

Fig. 2 shows this operation in more detail.

You will notice that the controller

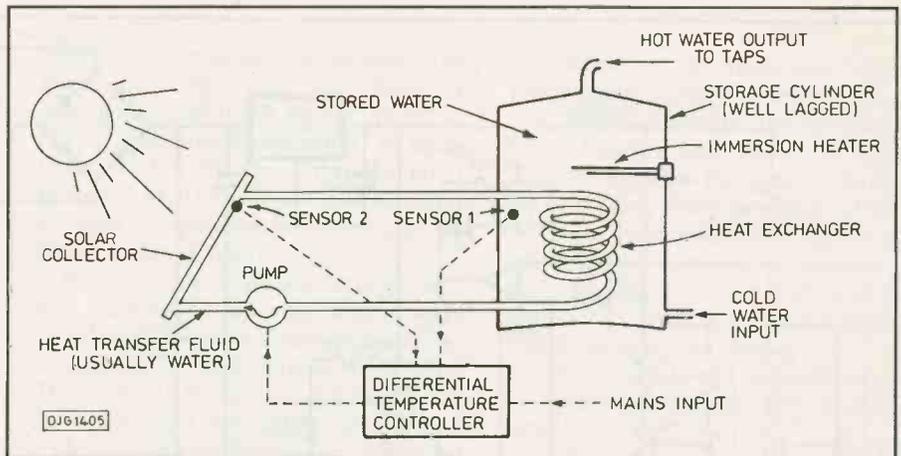


Fig.1. Basic solar heating system

fluid and the stored water increases. It will be seen that there is necessarily a minimum temperature difference to ensure that the rate at which heat energy is flowing through the heat exchanger is greater than the rate at which electrical energy is being used by the pump motor.

In the past differential temperature controllers often used thermistors for temperature sensors. One problem with this technique was ensuring that both sensors had almost identical characteristics, so that the controller would switch on and off at the required temperature difference irrespective

SOLAR HEATING CONTROLLER

switches the pump on when the temperature of the collector is (for example) 4°C higher than the stored water and off when the collector is only 2°C higher. This lag or hysteresis is essential to prevent the pump switching on and off almost continuously under conditions where the solar light intensity is only sufficient to raise the collector temperature slightly above the stored water temperature. When the pump operates, the relatively cool heat transfer fluid entering the collector cools it and so reduces its temperature, but the 2°C lag enables most of the hot fluid stored in the collector to be pumped through the heat exchanger before the pump switches off.

The rate at which heat is transferred to the stored water becomes greater as the temperature difference between the transfer

BY ANDREW WILLIAMS

HOT WATER FROM THE SUN

High accuracy silicon temperature sensors make the most of the UK's weak sunlight.

of the actual stored water temperature. To overcome the variations in sensor characteristics the controller was often set to switch on with a relatively large temperature difference (eg 8°C at a stored water temperature of 30°C). This ensures that at all other temperatures the rate at which energy was being transferred to the stored water was always greater than the rate at which energy was being used by the pump motor.


HEAT LOSSES

The heat losses from the collector by radiation, convection and conduction all increase as the collector temperature increases. This results in heat input to the transfer fluid as the temperature rises. Consequently it is advantageous to keep the temperature of the collector as low as possible. This requirement conflicts with the method of setting up the controller in the previous paragraph.

In recent years semiconductor sensors have become available (eg LM 335) which, after an initial adjustment, have almost identical characteristics enabling the switching to be carried out at the minimum temperature difference.

It is often impossible to mount the collector very close to the storage cylinder because of the necessity of siting the

Fig.2. Typical solar heating pump on-off pattern

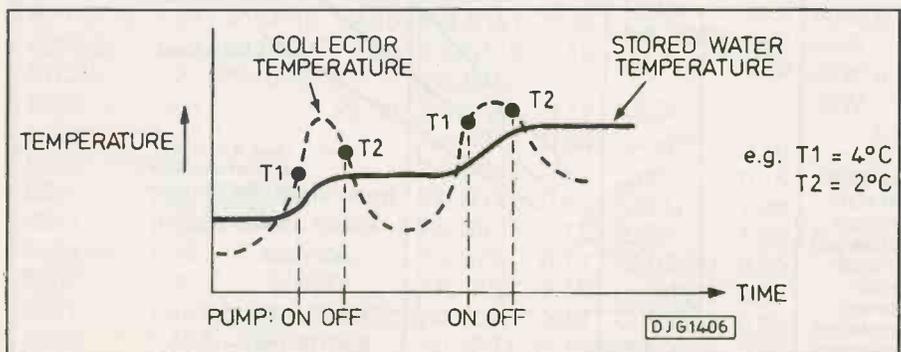

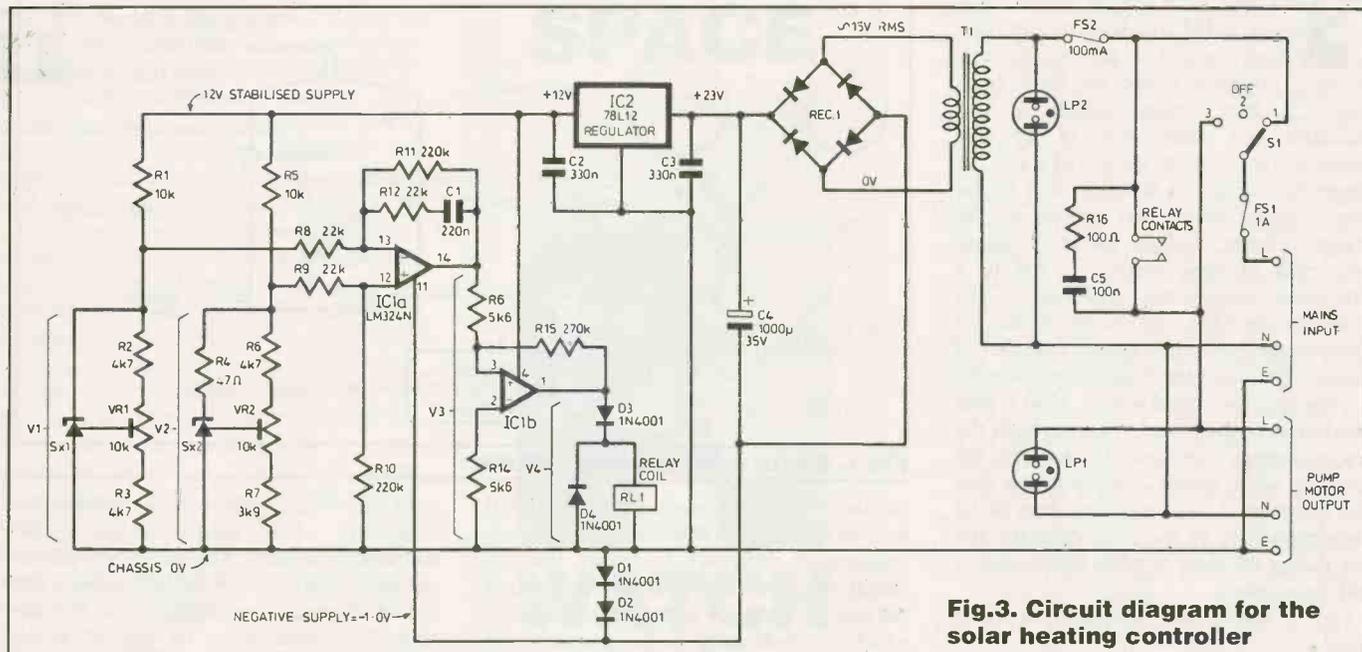


Fig.3. Circuit diagram for the solar heating controller

collector in a position where it will be in full sun for most of the day. This means that there will be some heat loss from the pipe joining the collector and the heat exchanger. Thus the temperature of the heat transfer fluid will be less when it arrives at the heat exchanger than when it left the collector. This temperature reduction will be very small when the temperature of the heat transfer fluid is low, but will increase as the temperature of the heat transfer fluid rises.

To offset this problem, the controller should switch the pump on with an increasing temperature difference between collector and stored water. This ensures that the minimum temperature difference across the heat exchanger remains relatively constant irrespective of the stored water temperature. The new semiconductor sensors mentioned above are ideal for providing this type of characteristic.

OPERATIONAL CONTROL

The sensors S1 and S2 in Fig. 3 behave like Zener diodes, where the voltage across the sensor is directly proportional to the temperature in degrees Kelvin. Adjustment of VR1 and VR2 enables the voltage across the sensor to be set to a precise value, eg if the voltage across Sx1 is set to 2.730V at 273K (ie 0°C) then the change in voltage across the sensor is 10mV for each degree Kelvin (or °C) of change.

IC1A is configured as a differential amplifier, ie, it amplifies the difference in the voltages across Sx1 (V1) and S2 plus R4 (V2). The dc and low frequency gain of this stage is 10, being determined by $R11/R8 = R10/R9 = 10$.

Thus $V3 = 10(V2 - V1)$

SETTING UP

Fasten Sx1 and Sx2 in close contact with a small metal sheet (the size of the sheet is not especially critical). Position a thermometer so that its bulb is in contact with the metal sheet and surround the sheet and lower part of the thermometer with some thermal insulation, such as expanded polystyrene, fibre-glass, cotton-wool etc. The sensors should be left with the control unit switched on for about a quarter of an hour to reach thermal equilibrium. The temperature is then noted, and V1 set by adjusting VR1 so that:

$V1 = (2.730 + (\text{temperature in } ^\circ\text{C}) \times (0.01))\text{V}$ eg, if the temperature is 18°C then $V1 = (2.730 + (18) \times (0.01))\text{V} = 2.91\text{V}$
A setting within $\pm 0.05\text{V}$ is sufficient.

Set V3 to -0.5V by adjusting VR2 to ensure that the pump will turn on when sensor Sx2 is 5°C hotter than sensor Sx1.

It is also possible to set to alternative switching temperatures:

eg -0.40V - 4.0°C, -0.60V = 6.0°C etc.

Note that in each case V3 is set to a *negative voltage* when Sx1 and Sx2 are at the *same temperature*.

FURTHER FACTORS


Pin 11 of IC1 is taken to a point below earth (chassis) potential via two diodes D1 and D2, to ensure that V3 and V4 are capable of going slightly negative.

IC1B is a regenerative comparator, thus when $V3 < 0$ (negative) then V4 is slightly negative, at about -0.35V, and when $V3 > 0$ (positive) then V4 is close to the positive 12V rail at about 11V. When Sx1 is at the same temperature as Sx2, then V3 and V4 are both negative, making D3 reverse biased so that no current flows through the relay coil. This ensures that the relay contacts are open and the pump is switched off.

When the collector sensor Sx2 becomes close to 5°C hotter than the cylinder sensor Sx1 then V3 becomes close to 0V, the positive feedback via R15 causes V4 to rise quickly to about 11V. D3 is now forward biased so that the relay coil is energised, hence the relay contacts close and the pump is switched on.

Diode D4 suppresses any back-emf through the relay coil when the current is switched off.

Fig.4. Graphical illustration of R4 function

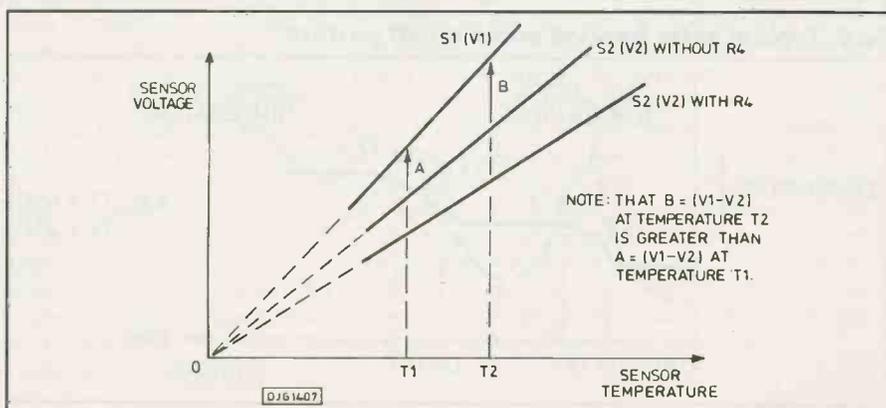

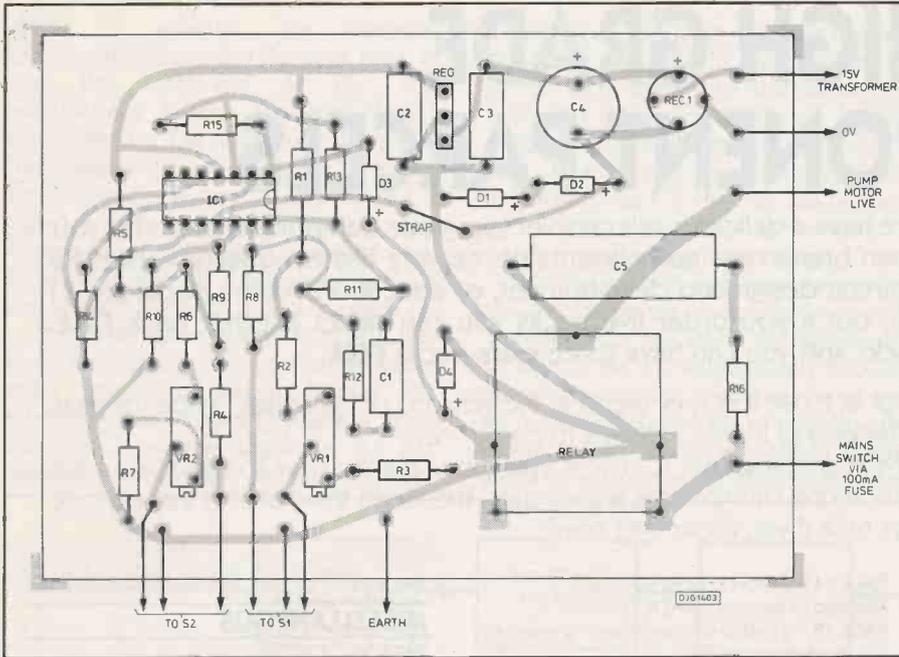


Fig. 5. Printed circuit board layout

COMPONENTS

RESISTORS

R1,R5	10k
R2,R3,R6	4k7
R4	47k
R7	3k9
R8,R9,R12	22k
R10,R11	220k
R13,R14	5k6
R15	270k
R16	100k

All resistors 1/4W 5% or better

CAPACITORS

C1	220n
C2,C3	330n
C4	100n 35V elect.
C5	100n 250Vac working

SEMICONDUCTORS

D1-D4	1N4001
IC1	LM324
IC2	78L12
Rec 1	W005 bridge rectifier

SENSORS

SX1	LM335H
SX2	LM335Z

POTENTIOMETERS

VR1,VR2	10k 15-turn preset
---------	--------------------

MISCELLANEOUS

T1	mains transformer, 15V secondary, 100mA min.
RL1	Relay, 12V spco, 1640 Ω coil.
S1	1p 12w mains switch.
LP1,LP2	mains neon
F1	1A fuse
F2	100mA fuse

Printed circuit board, box, wire, to suit.

in series with Sx2, results in V2 becoming greater than the voltage across Sx2 alone. Thus, the voltage across Sx2 needs to be smaller during the initial line-up procedure, making Sx2 less sensitive to temperature changes, as shown in Fig. 4.

Consequently, R4 increases the differential as the temperature rises, and to an extent greater than the sensors alone would give.

Although in Fig. 3 the difference in temperature between switching on and off has been set at approximately 2°C, the differential can be varied by altering the value of R15, eg 200k = 3°C hysteresis; 620k = 1°C hysteresis.

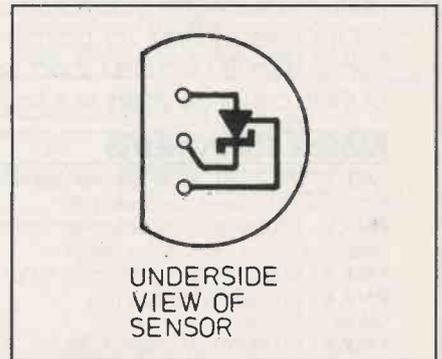


Fig. 6. The sensor connections

WHEREFORE R4

With both sensors at the same temperature V3 is set to -0.5V, making V2 0.05V smaller than V1.

Sensor Sx2 must become hotter than sensor Sx1 (by 5°C) to make V1 equal to V2; the condition required to operate the pump. Theoretically, both sensors would give zero output at 0° Kelvin, thus Sx1 is slightly more sensitive to temperature changed than Sx2 because of the initial setting difference. This effect is best shown graphically as in Fig. 4.

Note that B = V1-V2 at temperature T2 if greater than A = V1-V2 at temperature T1.


The potential drop cause by including R4

FINAL COMMENTS

Although IC1 is a quad op-amp and only two of its amplifiers are used, it was chosen because it is capable of sensing input voltages right down to the negative rail, it has a low power consumption and is readily available at a reasonable cost. **PE**

Parts of this circuit are at mains potential and normal insulation and safety practices should be observed.

Fig. 7. Panel connection details

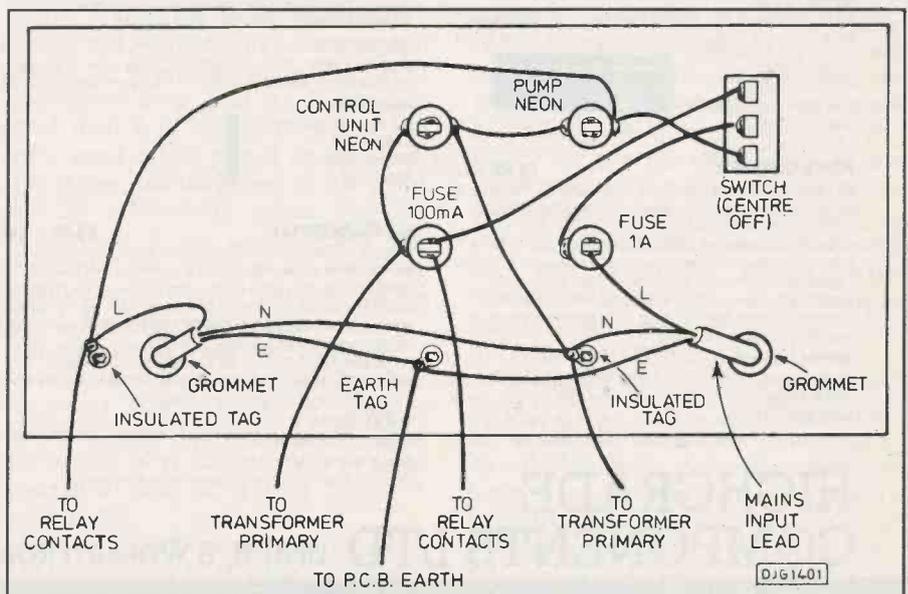

HIGH GRADE COMPONENT PARCELS

COMPONENT PACKS

This month we have a delicious selection of top grade component packs for you. They all contain brand new components of the very highest quality – ideal for experiment, circuit design and development, or education. All the packs are £1 (+ VAT) each, but if you order five packs you can select another pack **FREE**. Order ten packs and you can have three extra packs **FREE**.

FOR THE EXPERTS – Just look at those ICs! They are all at the very top of their class, made for peak performance without compromise. The kind of ICs it's a delight to design with.

Of course, there's no point in buying an expensive IC unless you know exactly how to use it, so each comes with its own data sheet, specifications, design ideas and circuits. The nicest thing of all is that any one of them could be yours in a few days time if you order right now!

PASSIVE COMPONENTS

PACK 1 – 200 RESISTORS. Mostly 1/4W carbon film. Lots of E12 values with some E96.
PACK 2 – 100 CAPACITORS. Ceramics, metallised film, all types. A fine selection!
PACK 3 – 30 ELECTROLYTICS. Values to 500µF.
PACK 4 – 15 LARGE ELECTROLYTICS. Values to 5,000µF.
PACK 5 – 10 TANTALUM CAPACITORS. Values to 47µF.
PACK 6 – 20 HIGH VALUE POLYESTER CAPS. Values to 2µ2.
PACK 7 – 15 DIL RESISTOR NETWORKS.
PACK 8 – 20 CARBON AND CERMET TRACK PRESETS.

OPTO ELECTRONICS & DISPLAYS

PACK 11 – 10 5mm LEDs: 4 red, 2 yellow, 2 orange, 2 green.
PACK 12 – 10 3mm LEDs: 4 red, 2 yellow, 2 orange, 2 green.
PACK 13 – 2 CQY89A high power infra-red emitters.

PACK 14 – 2 HIGH POWER SENSORS. Matched to emitters in PACK 13.
PACK 15 – 2 FND10 0.1" miniature 7-segment CC LED displays.
PACK 17 – 20 NEON BULBS (use 100k series resistor for mains).
PACK 18 – 2 INFRA-RED COMPONENTS. Emitter and phototransistor.
PACK 19 – 3 FLASHING LEDS. A built-in IC makes the LED flash.
PACK 21 – 1 SLOTTED INFRA-RED OPTO SWITCH.
PACK 23 – 10 RECTANGULAR GREEN LEDS. For bar graph, etc.

SEMICONDUCTORS

PACK 26 – 3 TAG136D MAINS TRIACS (400V, 4A).
PACK 27 – 30 IN4000 SERIES RECTIFIERS.
PACK 28 – 30 MIXED SEMICONDUCTORS. Transistors, diodes, SCRs, ICs, FETs, etc.
PACK 29 – 20 ASSORTED ICs. CMOS, TTL, linear, memory, all sorts.
PACK 30 – 20 TRANSISTORS. High grade general purpose NPN.

PACK 31 – 1 CF 585 CALCULATOR IC. With data.

MISCELLANEOUS

PACK 36 – 4 12V BUZZERS.
PACK 37 – 3 PANEL NEON LAMPS.
PACK 39 – 5 'BEEHIVE' TRIM CAPS.
PACK 40 – 3 VDRs. Mains transient suppressors – just wire between L and N of plug.
PACK 42 – 12 PP3 BATTERY CONNECTORS.
PACK 43 – 100 MYSTERY PACK. At least 100 top grade components.
PACK 44 – 1 MINI BIO-FEEDBACK KIT. With PCB, components and instructions.
PACK 45 – 1 MINI DREAM MACHINE KIT. With PCB, components and instructions.

EXTRA PACKS

PACK 50 – 12 BC212 TRANSISTORS. General purpose PNP.
PACK 51 – 12 BC213 TRANSISTORS. General purpose PNP.
PACK 52 – 2 PIEZO BUZZERS. Use as microphone, speaker or buzzer.

HI-FI PRE-AMPLIFIER IC

£2.80! + VAT

The HA12017 is a top grade Hi-Fi pre-amplifier, turning in a THD of less than 0.002% over the entire audio bandwidth! The low noise, wide dynamic range and excellent power supply ripple rejection make this IC the first choice for an audio pre-amplifier of formidable specifications.

Each IC is supplied with its own data sheet giving performance figures and graphs, the circuit for a top flight pre-amplifier and a PCB foil pattern and component layout.

SPECIFICATIONS

THD = 0.002% typ. ($f = 20\text{Hz}$ to 20kHz , $V_{out} = 10\text{V RMS}$, RIAA)
 Input noise $V_n = 0.185\mu\text{V typ.}$ (IHF-A network, $R_g = 43\Omega$, RIAA)

Supply rejection:

SVR+ = 56dB typ.
 ($f = 100\text{Hz}$, $R_g = 43\Omega$)
 SVR- = 45dB typ.
 ($f = 100\text{Hz}$, $R_g = 43\Omega$)

POWER AMPLIFIER IC

£3.90! + VAT

As easy to use as an ordinary op-amp, the L1165V's massive $\pm 3\text{A}$ current handling make it the ideal choice for a minimum component Hi-Fi amplifier.

This IC's data sheet includes circuits for a basic amplifier, a motor controller and a power oscillator. A separate sheet gives circuits and construction details for two high quality audio amplifiers, one giving 20W and the other 50W output. All information comes free with the IC. PCBs for the amplifiers are available separately, if required.

SPECIFICATIONS

Output current: $\pm 3\text{A}$ Frequency range: DC to 200kHz
 Supply voltage: 12V to 35V Input noise: $2\mu\text{V}$ (10Hz to 10kHz)

ACCESSORIES 20W Hi-Fi amplifier PCB £1.20 + VAT
 50W Hi-Fi amplifier PCB £1.60 + VAT

UHF AMPLIFIER

£12.20! + VAT

The OM335 is a high gain wideband amplifier (10MHz to 1.4GHz) for VHF and UHF signals. It can be used as a masthead amplifier for better TV reception, a booster for indoor aeriels, a distribution amplifier, and so on. The only external component needed is a decoupling capacitor for the power supply!

Each amplifier is supplied with a data sheet giving specifications, design hints and performance figures. A separate leaflet, also supplied with the IC, gives a complete design for a TV aerial booster, with layout and construction details. A PCB for the amplifier is available separately, if required.

SPECIFICATIONS

Frequency range: 10MHz to 1.4GHz Noise figure: 5.5dB typ.
 Mid-band gain: 26dB at $V_s = 24\text{V}$ Supply voltage: 9V to 26V

ACCESSORIES

PCB for TV aerial booster
 £1.80 + VAT
 Screening piece
 80p + VAT

BAR GRAPH DISPLAY

£3.60! + VAT

For visual impact, there's nothing to beat a bar graph display – you can see at a glance exactly what's going on. The LM3915 needs only ten LEDs and a few resistors to make a moving dot or expanding bar display. The logarithmic response means that the graph will automatically be scaled in dBs and will cover a wide dynamic range – ideal for audio work.

The data we supply with the IC gives circuits for a peak detector, VU meter, vibration meter, light meter, audio power meter, and a dozen more project ideas!

SPECIFICATIONS

Range: 30dB in 3dB steps
 Supply voltage: 3V to 25V
 Outputs: direct LED drive (no series resistors needed).

A/D CONVERTER

£4.80! + VAT

Built-in clock generator, easy interface to microprocessors, outputs suitable for MOS and TTL, differential inputs – the ADC0804's got the lot! As a stand alone converter, it needs only one external resistor and one small cap. What could be easier?

The converter comes with its own data sheet, giving full specifications, design hints and over 25 circuit ideas! Stocks limited on this one I'm afraid, and at this price they'll be gone in no time, so reserve yours now.

SPECIFICATIONS

Resolution: 8 bits Access time: 135ns
 Supply voltage: 5V Outputs: MOS and TTL

COMMUNICATION THROUGH THE MAINS

£6.20! + VAT

Messages through the mains is the function of the LM1893. Although intended for reliable, long distance data communication, it can just as easily become a powerful mains intercom – the instructions tell you how. Each IC contains a transmitter which sends an FSK modulated signal along the mains wiring of your house or office. The IC also has a receiver to pick up and decode the signals, so two ICs will give you full two-way communication without any wires or cables!

The instruction leaflet gives detailed design procedures, circuits, and everything you need to know to build a speech or digital communications system.

SPECIFICATIONS

Transmission rate: up to 4.8kBaud
 Carrier frequency: selectable 50kHz to 300kHz
 Power boost: optional x10 power boost with single transistor.

UK Orders: Please add 80p postage & packing and 15% VAT to the total (including postage).

Europe and Eire: Please add £2.50 carriage and insurance. No VAT.

Outside Europe: Please add £4.50 carriage and insurance. No VAT.

HIGH GRADE COMPONENTS LTD

UNIT 8, 8 Woburn Road, Eastville, Bristol BS5 6TT.

ACORNS TO OAKS

Dear John,

Your editorial in Jan 89 reminded me that I too have been reading PE since the first issue back in 1964, and continue to enjoy it as much as I did then. During that time I spent several years working abroad, but I always managed to make sure PE followed me. In fact, I can probably thank PE, together with my earlier avid reading of PW and PTV for their contribution towards a successful career with IBM.

One of the first PE projects which I undertook was the scope featured in PE 1965. It gave me excellent service for many years, and was eventually given to a neighbour's son, who was just setting out in electronics.

Sometime after I had built this project I acquired a huge array of test equipment, built into a large unit. I noticed that one of the two in-built scopes had a marked similarity with the original one I had built. Digging out the March 65 issue, close examination of the cover photograph led me to believe that it was the author's original scope. Perhaps if the author, Mr Cairns, reads this he might care to confirm if this is the case. I still have this scope, now retired.

My interest then turned to an electronic ignition system, modifying some circuits from PE; it worked well, with a 1/4 inch spark gap! Soon my attention became focussed on the then emerging ttl chips. I was asked to build some automatic timing equipment for a local motor club, but such was the distrust then for digital electronics, I had to build a unit which operated a normal stopwatch via a solenoid!

If you have any comments, criticisms or suggestions, write and let us know. We are interested in what you think and say, especially regarding our new style and your views on our role for the 1990s.

The situation had changed by 1972 when I put together my own design for a digital stop clock with 3-foot 7-segment displays for the model flying club in Salzburg. The knowledge needed to design the timer circuits naturally came from PE. It worked well but within a month after finishing it the first integrated clock chip appeared - all that work now available in one piece of plastic encapsulated silicon.

The pocket calculator appeared on the scene, and I built several Sinclair kits. I also built the PE Feb 74 battery charger/inverter which many a time proved useful in keeping the gas central heating running during power cuts.

Along came microcomputers, and I purchased one of the first Radio Shack TRS80 machines, expanding it myself and building an interface to drive a typewriter. This machine taught me a lot about microcomputers.

Current projects at home are few and far between; the occasional special circuit for radio control, and I plan to add a-d capability to my IBM PC. I have often thought about building some satellite tv receiving equipment, but that will probably not now come about as commercial equipment becomes more readily available and cheaper.

I still read PE every month. It helps me to keep abreast of new developments as well as providing interesting articles on wider ranging subjects. Keep up the good work, and best wishes for the next 25 years. I wonder what you will be featuring in 2014 ...

Peter Short, Kings Worthy, Hants.

These are just extracts from a much longer, and extremely interesting letter. Peter Short has obviously been as enthralled by electronics across the years as I have. His comment on "all that work now available in one piece of ... silicon" reminds of my very early attempts to build what I then described as a computer. It was nothing more than a long series of divide-by-two circuits feeding into a neon counting display. But each divider was formed of many transistors, diodes and resistors, and was on its own wiring board, measuring at least 4 x 6 inches! I also recall building a valve driven divider once upon a time.

I'll be most interested to hear of other reader's reminiscences about electronics over the last 25 years, especially if they relate to PE in some way.

Ed.

FIRST COURSE

Sirs,

I would like to begin a course on electronics but the books in my library seem dated. What books would you recommend for a beginner, and where should I buy my "bits and pieces"?

L. Bird, Rugby.

I am often asked questions along these lines, this is why we recently updated the PE Armchair Bookshop and put books into rough categories. You will find a wealth of interest in all the beginners books (and the others) but I suggest you buy more than one to give yourself a wider variety of subject matter and the benefit of several authors' viewpoints.

We have many good advertisers who sell components and other "bits and pieces". It would not be fair for me to recommend any one in particular - study their adverts and ask for their catalogues.

Ed.

TRUMPET BLOWING

Dear John,

Just a short note to say thanks very much for the recent excellent mention of Revox Systems.

M. Cooper, F.W.O.Bauch Ltd.,

Dear John,

We were delighted to read your article 'Servicing an Era!' (PE Nov 88, P5) and would like to express our admiration and thanks for your ability to compose such an interesting and well-written tribute

G. Cohen, Service Trading Co.

Many thanks - it makes editing PE even more worthwhile when I know that advertisers and readers are happy.

Ed

KILOSCOPY

Dear Ed,

Many thanks for your recent article on building an oscilloscope. It's been well worth waiting for.

I have a double gun tube that requires a potential voltage of 1.5kV. Can you recommend a suitable power supply?

C.P. Williamson, Chessington.

The Battery to Mains and HT Converters articles in PE Jul-Aug 88 show ways of increasing voltages from one level to another. One method of ac voltage multiplication described is very simple when only low currents are required and does not need many components - just a few diodes and capacitors that will withstand the increased potential.

For your application you will also need to compare the data sheets for your tube and the one for which the project was designed to

determine the changes you may need to make to voltages for the other control plates - a matter on which we cannot advise you as the subject is lengthy.

Ed.

BANANARAMA TELE

Dear Ed,

Further to the question of paw-paws being used as tv aerials (PE Dec 88 and Feb 89) *Electronic Engineering* of Jan 84 published a report confirming their reception ability. Other vegetation was also named, such as date, coconut and banana palms, and even ferns, as having antennic properties. Several reference sources were quoted, going as far back as 1961.

G.J.Lane, Chesham, Bucks.

Could this be an answer to the satellite tv reception dish problem of only being allowed one dish without planning permission? Now Astra is

up and BSB is coming, it might speed up the reforestation following the Great Storm of 87. Just imagine Kent and Sussex full of steerable banana plants connected by coconut-fibre optics. And would more of us watch date-time television? Mind you, I think the Germans have been on to this for a long time - their word for television is "fernsehen" ...

Ed.

MORE COMPACT CD

Dear Ed,

Last year PE published a series on CD technology. Your author quoted a playing time of about 60 minutes, but I understand that 73 minutes is a more correct figure.

M.L. Peake, Bilston, W.Mids.

Technology moves on, 75 minutes can now be fitted in, and they're still working on more playing time.

Ed.

SUPERCHARGED

Dear Ed,

Your 'Beware Batteries' comment in PE Feb 89 reminded me of two Exide T20 1.5V batteries I have sitting on my desk.

Recently, I moved house and came across a box of my old childhood toys in the loft. Picking up a racing car powered by two batteries, I pressed the button and was surprised to see the wheels turn at full speed. Taking out the batteries, they were found to be in perfect condition, no leakage and still holding 1.5V. I estimate them to be about 26 years old, at least the same age as PE!

Ian Doble, St Agnes, Cornwall.

We're still supercharged too!

Ed.

The various integrated circuits that go to make up a computer system, from memory chips to microprocessors, have been described in Parts 7 & 8. This month we see how they are put together to make a computer system, and how the system is made to operate as a whole.

A computer is a device, usually electronic, that is designed to process data automatically. *Processing* consists of storing data in memory, performing mathematical operations on it, performing logical operation on it, and taking decisions based on the data. The *data* includes numerical values, text, graphics, and information of various kinds, such as the fact that an airline passenger Mr X has made a request to be served vegetarian meals during the flight. Since the computer processes the data automatically, the data also includes a *program*, telling the computer what processing it must do and how to do it.

Electronic computer systems are of two kinds, analogue and digital. Analogue computers simulate (or are an analogue of) a physical system. The aim is to discover how the physical system behaves without actually having to operate it 'for real'. For example, an analogue computer could simulate the behaviour of a river system with dams and reservoirs. The flow of

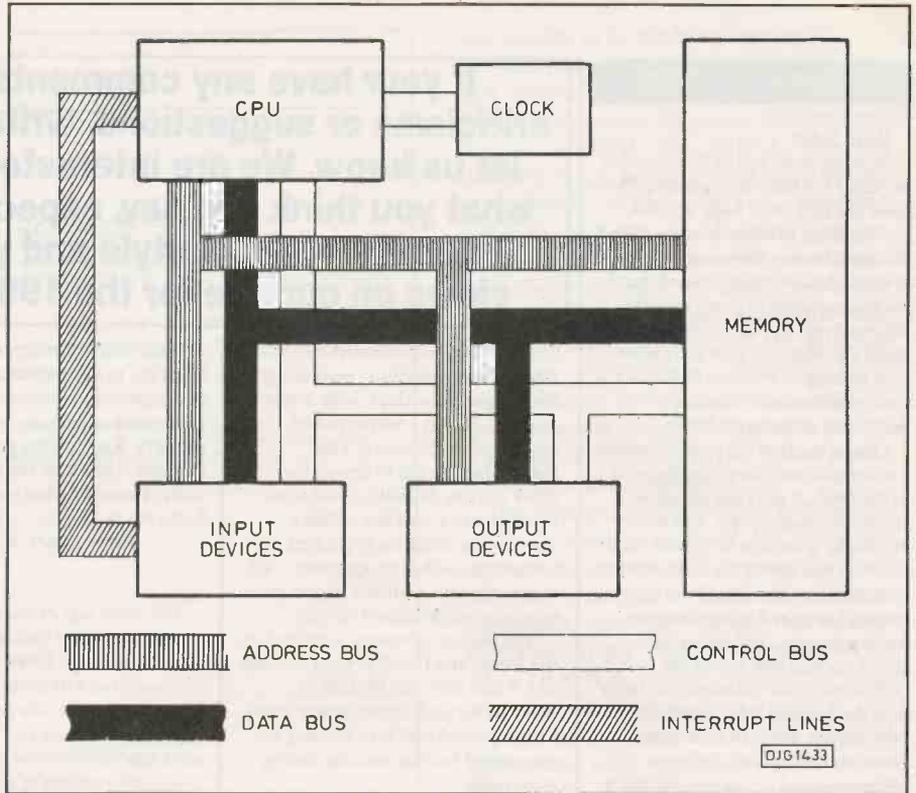


Fig.1. Block diagram of a computer system

DIGITAL ELECTRONICS

BY OWEN BISHOP

PART 9 – COMPUTER SYSTEMS

electric charge in the computer is an analogue of the flow of water in the river system. The computer is used to predict the rates of flow, the losses due to evaporation, the amount of water available for domestic use or for irrigation, the risks of flooding etc – *before* the dams have actually been built at great expense. Analogue computers are also useful in designing mechanical structures such as bridges and airframes.

In this series our main interest lies in things digital and so we shall study the digital electronic computer in some detail. In a digital computer, data is stored and handled in binary form. It may be represented as high or low voltage levels, or by flip-flops that are in either the 'set' or 'reset' states.

Digital computers are of two main types. Some of them (the kind we usually call to mind when the word 'computer' is mentioned) are able to perform a wide variety of tasks. This group includes everything from the pocket calculator to the main-frame computer. With the exception of the more elementary pocket calculators, they can be programmed for all kinds of applications including mathematics, word processing, acting as video-text terminals, and as games machines. Specialised word processors fall into this group since, though

So, we've already examined the chips that go into a computer. Now we look at how they relate to a complete system.

they are primarily designed for processing text, they are usually able to perform a number of other functions too.

The other main group of computers consists of those that we are less aware of because they don't have the typical 'keyboard plus video monitor' appearance. Indeed these computers are usually hidden away inside a device that looks nothing like a computer. We are referring to the computers used to operate such devices as washing machines, video recorders, cash registers, robot arms, and electronic toasters. The group also includes the computer systems used in aircraft and increasingly in road vehicles. These systems are all *dedicated* computers. They

are programmed to perform only one task or a few closely related tasks.

COMPUTER ARCHITECTURE

Fig.1 shows the main sections of a computer system. This diagram applies to all computers from pocket calculators, video games machines, and the control circuits of an electronic kitchen scales to the mightiest of mainframes. Most of the actual work of the system is done by the *central processing unit* (cpu). It is here that data is processed – acted on mathematically or logically – and decisions are taken. In many computers the cpu consists of a single integrated circuit a *microprocessor*. As explained in Part 7 (PE, Apr 1989), this is driven by an astable circuit, acting as a clock. The frequency of the clock is high, perhaps 2MHz or more, so that the operations of the microprocessor are performed exceedingly quickly and in rapid succession. This high speed is what gives the computer its power. As we shall see later, it does not do anything very complicated but, what it does do, it does *fast*. The cpu of mini-computers and main-

frame computers usually has more than one microprocessor and perhaps a special-purpose 'number cruncher' ic to help with the more involved parts of the calculations. This gives these machines the power to process more data and process it faster than micro-computers.

Memory often takes up the majority of the space on the computer board. Exceptions to this are some of the dedicated computer systems. These may require only a small memory. The memory may even be included on the same chip as the microprocessor. In some of the older micros the computer boards are covered in crowded ranks of memory chips, but with the development of chips capable of storing 256 kilobytes or more, memory is becoming less of a consumer of board space.

In the so-called 8-bit micros, such as the BBC Microcomputer, the Commodore 64, the Amstrad CPC series and the cheerful Speccy, memory is organised in *bytes*, each consisting of eight *bits*. Physically, each byte is represented on the memory chip by a set of eight flip-flops (or other devices such as capacitors). Each byte is identified by its *address*. When the byte is addressed, 8 bits of stored data can be read from it or (provided that the chip is a ram chip) written into it. In the micros mentioned above, as well as many others, an address has 16 bits. Addresses range from 0000 0000 0000 (0 decimal) to 1111 1111 1111 1111 (65535 decimal). The maximum amount of addressable memory is thus 65536 bytes or 64 *kilobytes*, usually referred to as 64K. For convenience, addresses are usually written in hexadecimal. We shall indicate such numbers by prefixing them with '&'. In hex, the addresses in a 64K machine run from &0000 to &FFFF.

Some parts of memory are rom (read only memory). This is used for *permanent* storage of:

* **Operating system programs** – tell the computer how to perform its routine tasks. This includes what to do when first switched on, such as testing memory, clearing the monitor screen, displaying the name of the computer on the screen and the word 'Ready', then waiting for input from the keyboard.

* **Resident programming language(s)** – most home micros have a Basic interpreter program, which tells the computer how to understand instructions coded in the Basic language. Some do not have a language in rom. It has to be loaded into ram before programming begins.

* **Data needed by the computer** – for example, the patterns to be used for displaying alphanumeric characters on the screen.

* **Special-purpose programs** – examples include word-processing, spreadsheet and data-base programs. It is convenient to have such programs instantly available in rom rather than to have to wait while they are

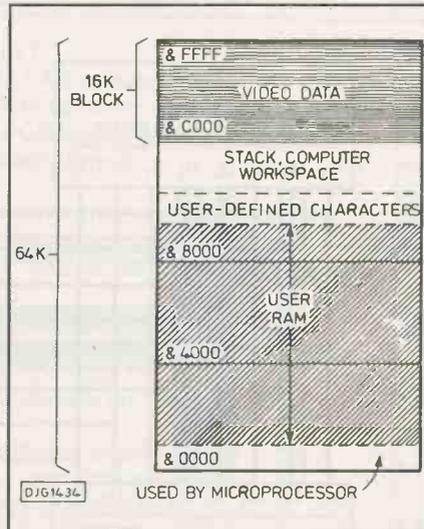


Fig.2. Memory map of RAM in Amstrad CPC series computers

loaded from tape or disk. With some machines this rom is in the form of a plug-in cartridge. Cartridges are available for programming languages, utility programs and games programs.

Other parts of memory are ram (random access memory). This is used for *temporary* storage of:


* **Programs** – loaded from tape or disk

* **Data needed by the programs**, such as lists of names, addresses, contents of spreadsheets, patterns of user-defined characters.

* **Data used or produced by the computer** – how long the computer has been switched on, what display mode it is in, what colours it is displaying, what was the last key pressed, the current position of the cursor, and many other such items essential to the operation of the computer. The part of memory holding this data is known as the *workspace*.

* **Stack** – here the computer stores data produced at one stage of an operation until it is required at some later stage in the operation.

Fig.3. Memory map of Amstrad CPC series computers when ROMs are switched in

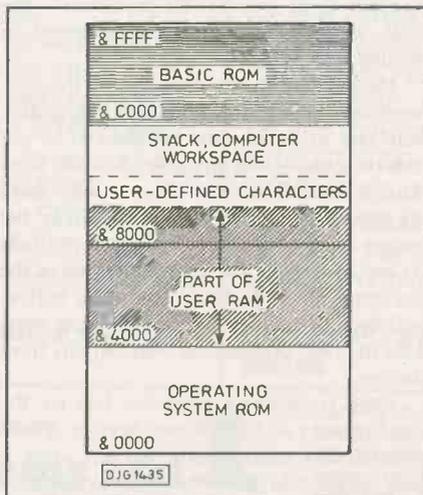

* **Video data** – this is often a *bit map* of the screen. Each picture element (*pixel*, the smallest individual dot produced on the screen) is represented by one or more bits of video memory.

As an example of memory allocation, Fig.2 shows the *memory map* of computers in the Amstrad CPC series. All the addresses from &0000 to &FFFF are occupied by ram. A large portion of this ram is occupied by video data. In some other computers there may be an entirely separate video ram, so allowing more main ram space for the storage of other data. Certain areas are reserved for essential purposes such as the stack, workspace and the storage of user-defined characters. There is a small area at the lowest addresses reserved for use by the microprocessor. The remaining ram, referred to as the *user* ram, is available for storing programs, data etc.

Since *all* the possible memory addresses &0000 to &FFFF are occupied by ram, where is the rom? The Amstrad's rom consists of two blocks of 16K each. One block, the Operating System rom is given addresses &0000 to &3FFF. These addresses are the same as those of the lower 16K of ram. When any data is *stored* in memory it goes to ram. When data is *read* from memory, either the rom *or* the lowest 16K of ram (but not both) can be read from at any one time. When the microprocessor is supposed to be using the Operating System (perhaps to scan the keyboard for input) the rom is switched in (Fig.3). At that instant it is not possible for it to obtain data from the corresponding block of ram. However when the keyboard has been scanned, rom is switched out automatically and ram is switched in. The microprocessor returns to running a program stored in ram.

Similarly the other block of rom (holding the Basic interpreter program) has the addresses &C000 to &FFFF, coinciding with the top block of ram. Rom is switched in when the microprocessor has to interpret a Basic statement, ram is switched in when the video display has to be updated.

The switching in of different blocks of memory is a way of making more than 64K available without needing addresses of more than 16-bits. The same principle can be applied to allow other 'sideways roms', such as word-processors, to be called up as required. In the same way we may have a second block of 64K of ram that can be switched in to provide extra storage. The Amstrad CPC128, the Spectrum 128K machines and the C-128 are examples of machines that provide double memory capacity in this way.

INPUT DEVICES

These include keyboards, tape readers (eg a cassette recorder), disc drives, optical compact disc readers, bar code readers, joysticks, mice, and digital pads. With dedicated computers the input devices may

include various push-buttons (as on a washing machine) switches and levers (as on a robot control panel), and sensors (eg temperature and water-level in a washing machine; a light sensor to detect how brown the toast has been cooked in an automatic toaster; thermal sensors in a heat-seeking missile).

All of these devices give a digital reading that can be transferred to the microprocessor. If the devices detect analogue data (such as the position of a joystick, or the amount of browning of the toast), an analogue-to-digital converter is an essential part of the device. Some computers (eg the BBC Micro) have on-board a-to-d converters for handling analogue input data.

The input devices of a computer are each allocated one or more addresses within the range of memory addresses. These devices appear to the microprocessor as locations in memory from which data is read in the usual way.

OUTPUT DEVICES

Output devices include video monitor screens, loudspeakers, tape recorders (these act both as input and output devices, as do disk drives), printers, plotters, robot arms, motors, led displays, and lcd displays. These too have addresses in memory to which the microprocessor sends data when the output device is to be activated.

INTERRUPTS

Fig.4 shows interrupt lines which run to the cpu from an input device. A signal (usually a logical low) on one of these lines causes the microprocessor to complete whatever operation it is engaged in and then to jump to a special part of its operating system program known as an *interrupt servicing routine*. The interrupt signal comes from an external device, such as a telephone modem or another computer. It may be that the external device has data that it wants to send to the computer. In this case the interrupt servicing routine would cause the microprocessor to accept data from the external device and perhaps store it in memory. Then, depending on what data was received, the computer might continue with what it was doing before, or take new action based on the newly-received data. These interrupts are usually handled so rapidly that the user of the computer is unaware that there has been any break in the machine's action.

BUSES

The operation of a computer depends on the transfer of data between the cpu, the memory and the input and output devices. The system adopted for this is known as the

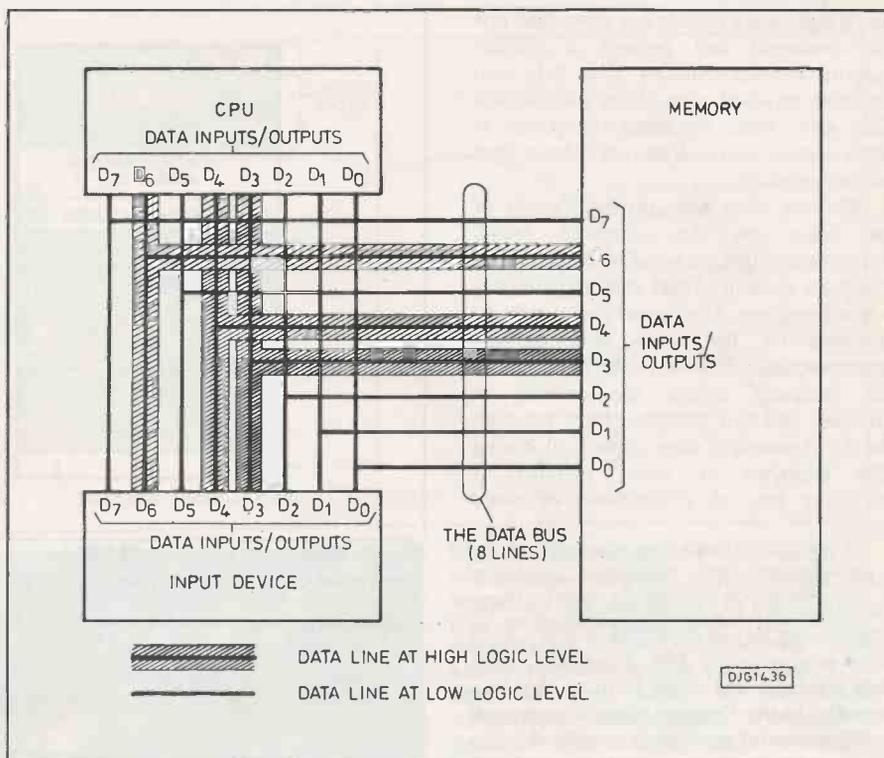


Fig.4. The data bus connections (output devices and other buses omitted for clarity)

bus system. Taking the *data bus* as an example, this normally consists of a set of 8 lines. These may be wires or printed circuit board tracks. All relevant parts of the computer are permanently connected to the data bus (Fig.4). The data is represented by voltage levels (logical high or logical low) present on the 8 lines. Each line corresponds to one bit of data and the bus as a whole carries an 8-bit byte. In Fig.4 the bus is carrying the data 01011010. What this means to the computer depends on what is happening in the computer at that time. Voltage levels 01011000 might mean:

- * a numeric value, equivalent to 88 decimal
- * a code value representing the text letter 'X'
- * an instruction code to the microprocessor (&58 in hex), telling it to transfer the contents of Register B to Register E (if it is a Z80 processor – the code would mean something different to another type of processor).

Data is put on the data bus by the cpu, memory and the input devices. Naturally, only one of these must be allowed to put data on to the bus at any given instant. They mustn't all talk at once! This is why there are sets of 8 *three-state buffers* joining the output circuits of these devices to the bus. At any instant the buffers of only one of the devices will be enabled. The other buffers will be in their high-impedance third state. This in effect disconnects their outputs from the bus.

Data is received from the bus by the cpu, memory and the output devices. These receive data continuously but act upon it only when told to do so. For example, a

memory chip stores the data that is on the bus only when its chip-select input is low and the write-enable line is low.

Mention of the write-enable line (which we examined in Part 7 brings us to the *control bus*. This is a set of lines including the write-enable (WE) line that command different parts of the computer circuit to become active or to behave in some particular way. A memory chip stores data when WE is low, and puts data on the data bus when WE is high, for example.

Finally, the *address bus*, consisting (usually) of 16 lines enables the cpu to indicate which of the memory locations, or the registers in input and output devices, it wishes to communicate with. For example, when the cpu puts the address of an output device on the address bus, the data that the cpu simultaneously puts on the data bus is received by that device.

USING THE BUSES

Two of the ways the buses are used are illustrated in Figs.5 and 6. The numbers in each figure indicate the order in which the operations are performed, up to the point at which data has been transferred. Thus the sequence for inputting data (Fig.5) is:

1. The input device receives data (eg a joystick is moved to a given position).
2. The cpu places the address of the input device (eg the joystick interface) on the address bus. This address remains there while...
3. The cpu places a signal on the control bus to tell it to...
4. Place data (eg representing the

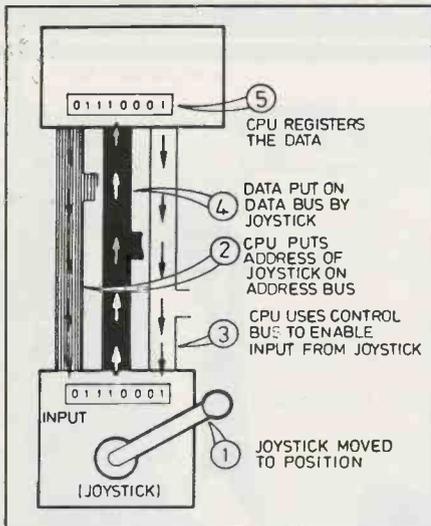


Fig.5. Data flow then CPU reads position of joystick



joystick position) on the data bus. This data remains there while...

5. The cpu reads the data into one of its registers. Data has now been transferred from the input device to the cpu. Three further stages follow, that are not shown in the diagram:

6. The cpu places a signal on the control bus to make the input device inactive.

7. The data from the input device is therefore removed from the data bus.

**Fig.6. (below). Data flow when CPU stores data in RAM
Fig.7. (right). The main features of a programmable input-output device. This one can send data to or receive data from two independent external devices (e.g. keyboard and printer).**

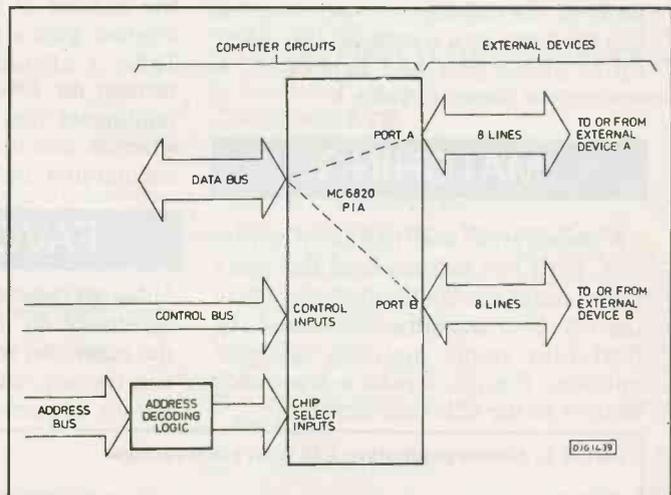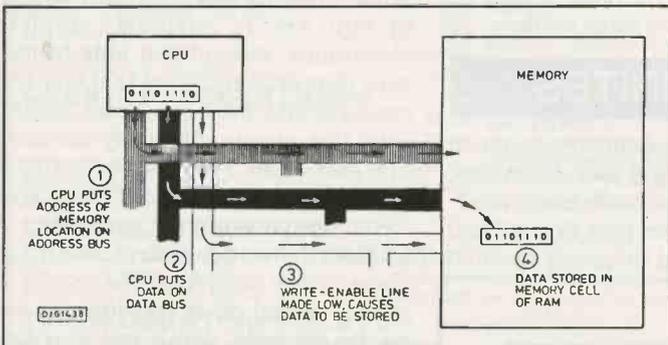

8. The cpu removes the address of the input device from the address bus.

This completes the operation. Although this sounds a very complicated sequence of events, its duration, from start to finish, is only a few microseconds. The other kinds of data transfer follow similar sequences.

INPUT-OUTPUT

One special type of input-output device is known as a *programmable input-output chip* or *pio* (Fig.7). It is sometimes called a *pia*, short for *peripheral interface adapter*. It is intended for connecting a wide range of input or output devices to the computer. These may include printers, joysticks, the keyboard, and many others. Even the simplest of micros may have two or three pios, perhaps one for the printer, one for the keyboard and one for the user to connect to any chosen device such as a modem, or Midi synthesiser.

A pio can be programmed for use either as an input or output device or for both purposes at the same time. Most pios have 8 independent input-output lines, each of which can be inputs or outputs. The pio has chip select inputs which are used to select the chip when a given address is put on the address bus by the cpu. The chip can be written to or read from, just as a memory

chip. When it is being written to, data written in its registers appears on the output lines. It is sent to any peripheral device, such as a printer, connected to the pio. Conversely, when the pio is being read from data being sent to it from an external device (such as a joystick or mouse) is transferred to the data bus and registered by the cpu.

TEST YOURSELF

(Answers next month)

1. What does a computer do?
2. Which part of the computer does the data processing?
3. What do we call the part of the computer where data is stored?
4. Name the three kinds of bus in a computer
5. What is an interrupt service routine?
6. Name four kinds of input device and four kinds of output device.

NEXT MONTH we shall continue by looking at the way the CPU is instructed, via a software program. There will also be another module to build - a sound operated sensor

PE

Keep up to date with the latest ideas and innovations in electronics and technology!

SUBSCRIBE TO **Practical Electronics**

Yes! Please send me the next 12 issues of Practical Electronics!

I enclose cheque payable to Intra Press
 £15.00 (UK) - £18.00 (Overseas) or debit
 my Access/Visa card No:
 Expiry date.....
 Signature.....

Name.....
 Address.....

 Postcode.....

Send your subscription order with remittance to: **Practical Electronics, Subscription Dept., P.O. Box 500, Leicester LE99 0AA**

REACH FOR THE SKY!

BUT IT'S BEAM-DOWN TIME NOT SHOOT-DOWN TIME FOR THE TRIUMPHANT THREE IN PE'S AERIAL CONTEST

ASTRA SATELLITE TV FLAT
AERIALS HAVE BEEN WON IN
THE HOT DRAW BY:

R.W.J.Marsh of Tunbridge Wells
D.F.J.Reeves of Swindon
N.Kemp of Boston

CONGRATULATIONS AND
HAPPY VIEWING!

12 month's PE subscription goes to the
runners-up.



In the PE Feb 89 competition we offered three of Sir Clive Sinclair's new flat aerials for receiving Sky satellite tv programmes. We asked you to say in which order you rated thirteen test-gear items. Those whose rating of the first six matched the majority view were entered into the draw. As a survey we also asked which items you had access to. A summary is shown in Table 1.

MATCHING

It's no surprise that multimeters rate first, but I had half-expected that more of you might put continuity tester top of the list. Your majority selection of the first four items matches my own opinion, though I rate a frequency counter as the fifth most important.

PRIMEORDIAL

To establish the primary order we awarded 13 points to the favourite, 12 to the second, etc. Multiplying points by the number in agreement and adding together gave a total number of marks. Table 1 also shows the percentage ratings for positions. So, 67% rated multimeter first, 21% rated it second, whereas less than 1% rated frequency counter first, but 14% rated it 6th.

FAVOURITES

Although there was distinctive common agreement on the first four favourites, the other two were insufficiently clear-cut. Consequently, for item five, we said anyone who selected frequency counter,

signal generator or signal tracer would be put in the draw. Likewise, for item six, anyone saying frequency counter or semiconductor tester would be entered.

REVEALING

The percentages of you who have access to (or own) equipment is most revealing. 67% of entrants having the use of a scope confirms how interested so many of you are in seriously applying electronics. 48% of you able to make your own pcbs reaffirms that you enjoy constructing projects. From Table 2, with 10% of you apparently not having any gear at all, I am reassured that we have a fair proportion of newcomers to electronics amongst our readership. It's too lengthy to detail here, but I have done further analysis of the results and drawn several other conclusions, such as, for example, which test gear items you might be interested in constructing.

TABLE 1. Access percentage and final place ratings.

ACCESS	PLACE	RATING	PLACES 1-13 PERCENT PRIORITY FAVOURED .												
			1	2	3	4	5	6	7	8	9	10	11	12	13
42%	7	Capacitance checker	0	1	4	8	10	12	16	9	9	9	7	8	4
59%	10	Continuity checker	4	4	4	4	4	5	6	7	12	7	9	11	20
20%	13	Eprom programmer	0	0	0	0	3	5	5	6	7	13	14	17	25
11%	12	Frequency analyser	0	1	2	3	5	3	7	11	14	13	13	17	7
40%	8	Frequency counter	0	2	3	5	11	14	10	8	13	10	9	6	4
18%	11	Logic analyser	0	1	2	1	6	6	8	12	11	13	14	12	10
88%	1	Multimeter	67	21	3	1	2	1	1	1	1	0	0	0	1
67%	2	Oscilloscope	16	35	20	8	6	5	4	4	0	0	0	0	1
48%	9	PCB making gear	0	3	4	5	10	9	7	7	7	11	8	10	16
82%	3	Power supply	10	27	27	13	7	6	2	3	1	1	2	1	1
41%	6	Semiconductor test	0	1	5	9	10	14	10	11	11	10	9	6	2
56%	4	Signal generator	0	3	24	30	14	11	7	3	2	2	3	0	0
31%	5	Signal tracer	1	1	3	13	11	9	13	14	7	8	7	7	4

Note that decimal places have been ignored.

TABLE 2 - Who has access to how many items.

ITEM QUANTITY	0	1	2	3	4	5	6	7	8	9	10	11	12	13
APPROX PERCENT OF ENTRANTS	10	4	5	7	8	9	13	10	10	11	7	3	2	4

**ENTER OUR
NEW
EXCITING
COMPETITION
NEXT
MONTH!**

ELMASET INSTRUMENT CASE

300 x 133 x 217mm deep £10 ea (£2.20)

REGULATORS

LM317T PLASTIC TO220 variable £1
LM317 METAL £2.20
7812 METAL 12V 1A £1
7805/12/15/24V plastic 35p 100+20p 1000+ 15p
7905/12/15/24 plastic 35p 100+20p 1000+ 15p
CA3085 T099 variable reg 2/£1
LM338 5A VARIABLE £5

COMPUTER ICs

IM6402 UART £3
8086 processor equipment £2
USED 41256-15 £3.80
USED 41256-15 £4.20
4164-15 ex equipment £1
9 x 41256-15 SIMM MODULE NEW £36
8 x 4164-15 SIP MODULE NEW £8
41256-10 SURFACE MOUNT EX NEW BOARDS £4
HD146818 CLOCK IC £2
2864 EEPROM £6
27128A 250nS EPROM NEW £3.20
FLOPPY DISC CONTROLLER CHIPS 1771 £10 ea
FLOPPY DISC CONTROLLER CHIPS 1772 £16 ea
68008 PROCESSOR EX-EQPT £5
ALL USED EPROMS ERASED AND BLANK CHECKED CAN BE PROGRAMMED IF DESIRED.
2764-30 USED £2
2716-45 USED £2 100/£1
2732-45 USED £2 100/£1
2764-30 USED £2 100/£1.60
27128-25/30 USED £2.50
27C256-30 USED £3
1702 EPROM EX EQPT £5
2114 EX EQPT 60p 4116 EX EQPT 70p
6264-15 8k static ram £6
4416 RAM £3.50
USED 4416-15 RAM £2
ZN427E-8 £3.50
ZN428E-8 £3.50

CRYSTAL OSCILLATOR

1.8342 MHz £1 each

CRYSTALS

2.77 MHz/4.9152 MHz/49.504MHz £1 each

TRANSISTORS

BC107, BCY70 PREFORMED LEADS
full spec £1 £4/100 £30/1000
BC557, BC548B 30/£1 £3.50/100

SIL RESISTOR NETWORKS

8 PIN 10k 22k 5/£1
8 PIN 22k 5/£1
10 PIN 68R 180R 22k 5/£1

POWER TRANSISTORS

OC35 (Marked CV7084) £1
POWER FET IRF9531 8A 60V 2/£1
2SC1520 sim BF259 3/£1 100/£22
TIP141/2 £1 ea TIP112/125/42B 2/£1
TIP35B TIP35C £1.50
SE9301 100V 10A DARL. SIM TIP121 2/£1
2N3055 EX EQPT TESTED 4/£1
PLASTIC 3055 OR 2955 equiv 50p 100/£35
2N3773 NPN 25A 160V £1.80 10/£16

QUARTZ HALOGEN LAMPS

A1/216 24V 150 WATTS £2.25
H1 12V 50W (CAR SPOT) £1.50

ZIF SOCKETS 2/£1.50

TEXTTOOL single in line 32 way. Can be ganged (coupling supplied) for use with any dual in line devices.

LARGE ELECTROLYTIC CAPACITORS COMPUTER GRADE

3300uF 350V SIC SAFCO FELSIC 037 £6 (£1.50)
2200uF 160V SIC SAFCO FELSIC C038 £4 (£1.20)

TURNS COUNTING DIALS FOR MULTITURN POTENTIOMETERS

all for 0.25" shaft
10 turn dial 21 mm dia. fits 3mm spindle £2
10 turn digital dial (3 digits) for 3mm or 6mm shaft £3.50
10 turn clock face dial for 6mm spindle £4

MISCELLANEOUS

SLOPING FRONT PLASTIC CASE 225 x 215 x £4.90 (£1)
76 mm WITH ALI FRONT PANEL 200 x 130mm
HUMIDITY SWITCH ADJUSTABLE £2
WIRE ENDED FUSES 0.25A 30/£1
NEW ULTRASONIC TRANSDUCERS 40kHz £2/pair
12 CORE CABLE 7/0.2mm OVERALL SCREEN. £1/3 metres
POWERFUL SMALL CYLINDRICAL MAGNETS 3/£1
OP AMP LM10CLN £2.90
BNC 50 OHM SCREENED CHASSIS SOCKET 3/£1

BNC TO CROC CLIPS LEAD 1 metre £1

MOULDED INDUCTOR 470µH

size of a 1 watt film resistor 5/£1

TO-220 HEAT SINK sim RS 403-162 10/£2.50

SMALL MICROWAVE DIODES AEI DC1028A 2/£1

D.I.L. SWITCHES 10 WAY £1 8 WAY 80p 4/5/6 WAY 50p

180 volt 1 watt ZENERS also 12v & 75v 20/£1

PLASTIC EQUIPMENT CASE 9 x 6 x 1.25 in. WITH FRONT AND REAR PANELS CONTAINING PCB WITH EPROM 2764-30

AND ICS 7417 LS30 LS32 LS74 LS367 LM311 7805 REG, 9 WAY

D PLUG, PUSH BUTTON SWITCH, DIN SOCKET £1.90

VN101M 60V 1/2A 50hm TO-92 mosfet 4/£1 100/£20

MIN GLASS NEONS 10/£1

RELAY 5v 2 pole changeover looks like RS 355-741 marked STC

47WB05T £1 ea

MINIATURE CO-AX FREE PLUG RS 456-071 2/£1

MINIATURE CO-AX FREE SKT. RS 456-273 2/£1.50

DIL REED RELAY 2 POLE n/o CONTACTS £1

PCB WITH 2N2646 UNIJUNCTION with 12v 4 POLE RELAY £1

400m 0.5w thick film resistors (yes four hundred megohms) 4/£1

MINIATURE CO-AX FREE PLUG RS 456-071 2/£1

MINIATURE CO-AX FREE SKT. RS 456-273 2/£1.50

STRAIN GAUGES 40 ohm Foil type polyester backed balco grid alloy £1.50 ea 10+ £1

ELECTRET MICROPHONE INSERT £0.90

Linear Hall effect IC Micro Switch no 613 SS4 sim RS 304-267 £2.50 100+ £1.50

HALL EFFECT IC UGS3040 + MAGNET £1

OSCILLOSCOPE PROBE SWITCHED X1 X10 £10

CHEAP PHONO PLUGS 100/£2 1000/£18

1 pole 12 way rotary switch 4/£1

AUDIO ICS LM380 LM386 £1 ea

555 TIMER 5/£1 741 OP AMP 5/£1

ZN414 AM RADIO CHIP 80p

COAX PLUGS nice ones 4/£1

COAX BACK TO BACK JOINERS 3/£1

4 x 4 MEMBRANE KEYBOARD £1.50

15.000uF 40V £2.50 (£1.25)

INDUCTOR 20µH 1.5A £1

NEW BT PLUG + LEAD £1.50

1.25" PANEL FUSEHOLDERS 3/£1

CHROMED STEEL HINGES 14.5 x 1" OPEN £1 each

12v 1.2w small wire ended lamps fit AUDI VW TR7 SAAB VOLVO 10/£1

12V MES LAMPS 10/£1

STEREO CASSETTE HEAD 10/£1

MONO CASS. HEAD £1 ERASE HEAD 50p

THERMAL CUT OUTS 50 77 85 120°C £1 ea

THERMAL FUSE 121°C 240V 15A 5/£1

TRANSISTOR MOUNTING PADS TO-5/TO-18 £3/1000

TO-3 TRANSISTOR COVERS 10/£1

STICK ON CABINET FEET 30/£1

PCB PINS FIT 0.1" VERO 200/£1

TO-220 micas + bushes 10/50p 100/£2

TO-3 micas + bushes 15/£1

PTFE min screened cable 10m/£1

Large heat shrink sleeving pack £2

CERAMIC FILTERS 6M/9M/10.7M 50p 100/£20

MAINS LEAD WITH MOULDED 13A PLUG AND IEC SOCKET £1.50

IEC chassis plug rfi filter 10A £3

Potentiometers short spindles values 2k5 10k 25k 1m 5/£1

2M5 in 5/£1

500k lin 500k log 4/£1

40kHz ULTRASONIC TRANSDUCERS EX-EQPT NO DATA £1/pr

PLESSEY INVERTER TRANSFORMER 50 CYCLES £6 (£3)

ZENERS

5.6V 1W3 SEMIKRON 50K AVAILABLE @£25/1000
SUPPRESSOR OF606 120V BI DIRECTIONAL ZENER
IN 3 AMP W/E PACKAGE 5/£1

DIODES AND RECTIFIERS

1N4148 100/£1.50
1N4004/SD4 1A 300V 100/£3
1N5401 3A 100V 10/£1
BA158 1A 400V fast recovery 100/£3
BA159 1A 1000V fast recovery 100/£3
120V 35A STUD 65p
BY127 1200V 1.2A 10/£1
BY254 800V 3A 8/£1
BY255 1300V 3A 4/£1
6A 100V SIMILAR MR751 4/£1
1A 800V BRIDGE RECTIFIER 4/£1
4A 100V BRIDGE 3/£1
6A 100V BRIDGE 2/£1
8A 200V BRIDGE 2/£1.35
10A 200V BRIDGE £1.50
25A 200V BRIDGE £2
25A 400V BRIDGE £2.50

SCRs

PULSE TRANSFORMERS 1:1+1 £1.25
2P4M EQUIV C106D 3/£1
MCR72-6 10A 600V SCR £1
35A 600V STUD SCR £2

TICV106D 800mA 400V SCR 3/£1 100/£15

MEU21 PROG. UNIJUNCTION 3/£1

TRIACS

BT137-600 8A TO-220 2/£1
BT138-600 12A TO-220 70p
NEC TRIAC AC08F 8A 600V TO220 5/£2 100/£30
TXAL225 8A 400V 5mA GATE 2/£1 100/£35
TRAL2230D 30A 400V ISOLATED STUD £4 each

DIACS 4/£1

CONNECTORS

D25 IDC SOCKET FUJITSU £2
34 way card edge IDC CONNECTOR (disk drive type) £1.25
CENTRONICS 36 WAY IDC PLUG £2.50
CENTRONICS 36 WAY IDC SKT £4.00
BBC TO CENTRONICS PRINTER LEAD 1.5M £3.50
CENTRONICS 36 WAY PLUG SOLDER TYPE £4
USED CENTRONICS 36W PLUG+SKT £3

USED D CONNECTORS price per pair

D9 60p, D15 £1.50, D25 £2, D37 £2, D50 £3.50 covers 50p ea.

WIRE WOUND RESISTORS

W21 or sim 2.5W 10 of one value £1
R10 OR15 OR22 2R0 2R7 4R7 5R0 5R6 8R2 10R 12R 15R 18R
20R 22R 27R 33R 47R 56R 62R 91R 120R 180R 390R 430R
470R 680R 820R 910R 1K15 1K2 1K5 1K8 2K4 2K7 3K3 3K0 5K0
R05 (50 milli-ohm) 1% 3w 4 FOR £1
W22 or sim 6W 7 OF ONE VALUE £1
R47 R62 1R0 1R5 1R8 3R3 6R8 9R1 12R 20R 24R 27R 33R 51R
56R 62R 68R 100R 120R 180R 220R 390R 560R 620R 910R
1K0 1K2 1K5 1K8 2K2 2K7 3K3 3K9 4K7 8K2 10K 15K 16K 20K
W23 or sim 9W 6 of one value £1
R22 R47 1R0 1R1 1R5 56R 62R 100R 120R 180R 220R 300R
390R 680R 1K0 1K5 5K1 10K
W24 or sim 12W 4 OF ONE VALUE £1
R50 2R0 9R1 18R 27R 56R 68R 75R 82R 100R 150R 180R
200R 220R 270R 400R 620R 1K0 6K8 8K2 10K 15K

PHOTO DEVICES

SLOTTED OPTO-SWITCH OPCOA OPB815 £1.30
2N5777 50p
TIL81 PHOTO TRANSISTOR £1
TIL38 INFRA RED LED 5/£1
4N25, OP1252 OPTO ISOLATOR 50p
PHOTO DIODE 50p
MEL12 (PHOTO DARLINGTON BASE n/c) 50p
RPY58A LDR 50p ORP12 LDR 70p
LEDs RED 3 or 5mm 12/£1
LEDs GREEN OR YELLOW 10/£1 100/£6.50
LEDs ASSORTED RD/GN/YW + INFRA/RED 200/£5
FLASHING RED OR GREEN LED 5mm 50p 100/£35

STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K, G16 1M, RES @ 20°C DIRECTLY HEATED TYPE £1 ea
FS22BW NTC BEAD INSIDE END OF 1" GLASS PROBE
RES @ 20°C 200R £1 ea

CERMET MULTI TURN PRESETS 3/4"

10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K
50K 100K 200K 500K 2M2 50p each

IC SOCKETS

6 pin 15/£1 8 pin 12/£1 14/16 pin 10/£1 18/20 pin 7/£1,
22/24/28 pin 4/£1 40 pin 30p

SOLID STATE RELAYS

40A 250V AC SOLID STATE RELAYS £18

POLYESTER/POLYCARB CAPS

100n 63v 5mm 20/£1 100/£3 1000/£25
1n/3n/5n/6n/2/10n 1% 63v 10mm 100/£6
10n/15n/22n/33n/47n/68n 10mm rad 100/£3.50
100n 250v radial 10mm 100/£3
100n 600v sprague axial 10/£1 100/£6 (£1)
2u2 160v rad 22mm 100/£10
10n/33n/47n 250v ac x rated 15mm 10/£1
470n 250v ac x rated rad 4/£1
1U 600V MIXED DIELECTRIC 50p ea.

RF BITS

12 volt CO-AXIAL relays sim. RS 349-686 £6
Ex-equipment, with BNC tails
10/£1 TRIMMER CAPS ALL 4/50p
8/£1 SMALL 5p 2 pin mounting 5mm centres
6/£1 SMALL MULLARD 2 to 22pF 4/50p
4/£1 SMALL MULLARD 5 to 50pF 4/50p
grey larger type 2 to 25pF
3/£1 TRANSISTORS 2N4427 60p
2/£1 FEED THRU CERAMIC CAPS 1000pF 10/£1

MINIATURE RELAYS

Suitable for RF
5 volt coil 1 pole changeover £1
5 volt coil 2 pole changeover £1
12 volt coil 1 pole changeover £1

MONOLITHIC CERAMIC CAPACITORS

10n 50v 2.5mm 100/£4.50
£2 100n 50v 2.5mm or 5mm 100/£6

KEYTRONICS

TEL. 0279-505543

FAX. 0279-757656

P O BOX 634

BISHOPS STORTFORD

HERTFORDSHIRE CM23 2RX


MAIL ORDER ONLY

MIN CASH ORDER £3.00 OFFICIAL ORDERS WELCOME
UNIVERSITIES COLLEGES SCHOOLS GOVT DEPARTMENTS
MIN. ACCOUNT ORDER £10.00

P & P AS SHOWN IN BRACKETS (HEAVY ITEMS)
65p OTHERWISE (LIGHT ITEMS)

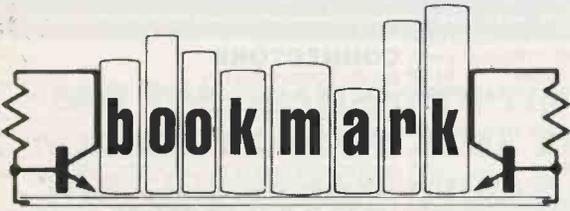ADD 15% VAT TO TOTAL
ELECTRONIC COMPONENTS
BOUGHT FOR CASH





Your Ed looks at some of the new books recently received.

Remote Control Handbook. Owen Bishop. Babani BP240 £3.95. ISBN 0-85934-185-2. Owen Bishop will be a familiar name to PE readers, especially as at the moment he is the author of the very successful Digital Electronics series we are running. He is the author of many books and this latest one is the successor to his Remote Control Projects published in 1980. This new book contains improved and updated versions of some of the previous circuits. Additionally, there are a number of completely new circuits included. Many of these are concerned with aspects of remote control that have increased in importance during the last few years. In particular, there are circuits for interfacing computers to remote control systems, as well as for using fibre optics and domestic mains wiring as transmission links. There are new circuits for stepper motors, plus v-f and f-v conversions. The systems have been designed in modular form enabling many to be linked together to form more complex networks. I definitely recommend this book to the adventurous constructor.

Teach Yourself Electronics. Malcolm Plant. Teach Yourself Books (Hodder and Stoughton). £4.50. ISBN 0-340-42230-0. Anyone familiar with the Teach Yourself series will know their reputation for quality and reliable information. This addition to the series is intended as a first introduction which explains simply and clearly how electronic devices and circuits work, and how they are used in computer, communications and control systems. It describes the functions of devices such as resistors, capacitors, and semiconductors, explains the theory of logic gates and Boolean algebra. Finally, some of the specialist applications of electronics in instrumentation, control and telecommunications are described. It does not give a blow-by-blow account of everything you might want to know, but it will give you a basic understanding and background knowledge of today's electronics. A glossary is included.

Experiments With Eproms. Dave Prochnow. Tab Books. £13.20. ISBN 0-8306-2962-9. This book looks at the basic principles behind eprom technology and then describes 15 constructional projects for use in stand-alone and computer-based modes. They include a simple project that determines the logic present on digital ic pins, two eprom programmers, an eprom eraser, speech and music synthesiser. Although this book was written primarily for US readers and as such has areas that are less relevant to UK readers, much of the information should be universally of interest to experienced constructors.

Troubleshooting and Repairing TVRO Systems. Stan Prentiss. Tab Books. £13.10. ISBN 0-8306-2992-0. Stan Prentiss is a former NASA satellite engineer and is a member of the Satellite Operators and Users Technical Committee (SOUTC). In this guide he emphasises the uses and operations of the latest troubleshooting equipment, including spectrum analysers, oscilloscopes and digital multimeters. Specific diagnostic procedures for using this equipment are discussed and detailed operation of current receivers described. In addition to information on antennas, feeds, multi-cabling, block-down converters and scramblers, he gives much attention to Ku band and its advantages and disadvantages. This is very much a book for the specialist reader who should examine it first to assess its relevance to applications outside the USA.

20 Innovative Electronics Projects for Your Home. Joseph O'Connell. Tab Books. £10.80. ISBN 0-8306-2947-5. I am far from happy that some of the projects in this book should be offered to UK readers. Several of the projects shown are related to mains control and telephone circuits. In Britain we have different mains voltage requirements and more restrictive telephone regulations than in the US. Additionally, some of the components specified neither relate to, nor are likely to be available in Britain. I have repeatedly

commented in these pages about Tab Books failure to make their published information relevant to UK readers. Copies of my comments are sent to their agents but I have had no indication that Tab Books have recognised that British readers will frequently find it difficult, if not impossible, to make use of varying amounts of information in their books. Though knowledgeable readers may well find academic interest from US-specific information, and may be able to modify circuits to meet different needs, sadly, those who are less experienced may at least run into constructional difficulties, and at worst be in danger from non-compatible mains power requirements. The solid state electric blanket control is one circuit that especially bothers me in this respect. In the case of a telephone accessory circuit shown, I believe that UK readers would be contravening Telecom regulations by using it. On the more positive side, there are a number of circuits in this particular book which will be of more wide-spread appeal, but the book should be examined before purchase.

An Introduction to Loudspeakers and Enclosure Design. Vivian Capel. Babani BP256. £2.92. ISBN 0-85934-201-8. Vivian Capel is another contributor to PE whose writings I find of interest - you may remember he did a series on compact discs from July-Sept 88. Having built my own high powered speaker enclosures some years ago I know some of the pitfalls that the inexperienced can encounter. This book should help constructors to avoid any major problems. It explores many types of enclosure and drive units looking at their good points and snags. The whys and wherefores are examined so that readers can make informed choices of design, or even design their own enclosures. Crossover units are explained, and a step by step description of a *Kapellmeister* enclosure is given. This stereo image design involves novel features which overcome many of the disadvantages of more conventional types.

Enhanced Sound - 22 Projects for the Audiophile. Richard Kaufman. Tab Books. £7.75. ISBN 0-8306-9317-3. A professionally produced book which lives up to its title and claim that you can "get better sound from your audio equipment without spending a lot of money". Eleven chapters cover basic components, semiconductors, tools and techniques, projects without psus, psus, preamps and amps, opamps, active filters, crossovers, fm antennae, and speaker design. The latter chapter, and that on filters, include programs written in Basic to assist in calculations. The book is liberally illustrated with circuit diagrams, keeps maths to a minimum, and the project components appear to be UK, though a list of US suppliers is quoted. A useful book.

Satellite Television Installation Guide. John Breeds. Swift TV Publications. £11.95. ISBN 0-948251 43 3. The recent launch of the Astra satellite and the imminence of BSB will create many more jobs for satellite tv receiver installers. Although satisfactorily installing a suitable antenna may be beyond the capabilities of many divers, those who have the tools and patience necessary will reap benefits from the clearly illustrated information given in this 47 page booklet. It consists of fourteen sections, and the contents range from how to wire up the indoor unit via the video recorder, installing fixed and multi-satellite dish mounts, through to a handy site-survey planner. Swift says that this is an ideal study manual for trainees on CAI courses accredited by the City and Guilds of London Institute. I feel obliged to stress to would-be diyers that I have recently heard it said on several occasions that the alignment accuracy of receiving dishes is absolutely critical to obtaining the best reception. It is also vital that the dishes should be robustly mounted so that their weight presents no problems even in the highest winds. Dish installation is not a job for the casual bodger! Stop Press: We've just heard that the second edition has been released with even more information.

Publisher's addresses:

Bernard Babani (Publishing) Ltd, The Grampians, Shepherds Bush Road, London, W6 7NF.

Swift Satellite TV Services, 17 Pittsfield, Cricklade, Swindon, Wilts, SN6 6AN. 0793 750620.

Tab Books are imported from the USA by John Wiley and Sons Ltd, Baffins Lane, Chichester, W. Sussex, PO10 1UD. 0243 779777.

Teach Yourself Books, PO Box 702, Dunton Green, Sevenoaks, Kent, TN13 2YD. 0732 450111.


MAKING ELECTRONICS C.A.D. AFFORDABLE

PCB CAD, FOR THE PC/XT/AT – EASY-PC AND TINY-PC

- Are you still using tapes and a light box?
- Have you been putting off buying PCB CAD software?
- Have you access to an IBM PC/XT/AT or clone inc Amstrad 1640 & 1512
- Would you like to be able to produce PCB layouts up to 17" square?
- With up to 8 track layers and 2 silk screen layers?
- Plus drill template and solder resist?
- With up to eight different track widths anywhere in the range .002 to .531"
- With up to 16 different pad sizes from the same range?
- With pad shapes including round, oval, square, with or without hole and edge connector fingers?
- With up to 1500 IC's per board, from up to 100 different outlines?
- With auto repeat on tracks or other features – ideal for memory planes?
- That can be used for surface mount components?
- With the ability to locate components and pads on grid or to .002" resolution?
- With an optional auto via facility for multilayer boards?
- With the ability to create and save your own symbols?
- That can be used with either cursor keys or mouse?
- That is as good at circuit diagrams as it is a PCB's?
- That outputs to Dot Matrix Printer, or, with extra drivers can drive a pen plotter or photoplotter.
- Where you can learn how to use it in around an hour?


TINY-PC £95.00 + VAT EASY-PC £275.00 + VAT

**BRITISH
DESIGN
AWARD
1989**

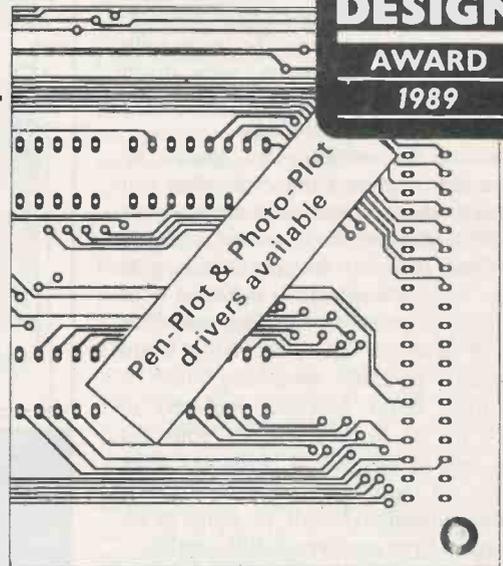

SMITH CHART PROGRAM – Z-MATCH

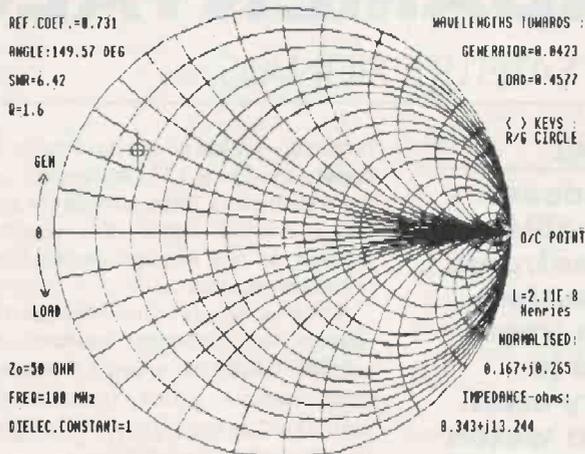For IBM, PC/XT/AT and clones inc. Amstrad 1512 and 1640 and BBC B, B+ and Master.




Z-MATCH – Takes the drudgery out of R.F. matching problems. Includes many more features than the standard Smith Chart.

Provides solutions to problems such as TRANSMISSION LINE MATCHING for AERIALS and RF AMPLIFIERS with TRANSMISSION LINE TRANSFORMER and STUB MATCHING methods using COAXIAL LINES MICROSTRIP, STRIPLINE and WAVEGUIDES. The program takes account of TRANSMISSION LINE LOSS, DIELECTRIC CONSTANT, VELOCITY FACTOR and FREQUENCY. Z-MATCH is supplied with a COMPREHENSIVE USER MANUAL which contains a range of WORKED EXAMPLES

£130 for PC/XT/AT etc £65.00 for BBC B, B+ and Master

CIRCUIT ANALYSIS BY COMPUTER – ANALYSER II

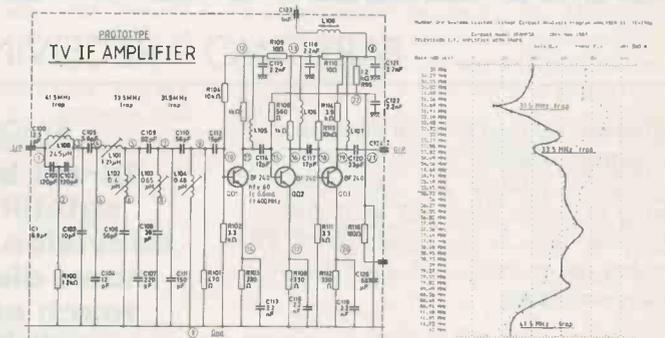For IBM, PC/XT/AT and clones inc. Amstrad 1512, 1640, R.M. NIMBUS, and BBC B, B+, and Master.



"ANALYSER II" – Analyses complex circuits for GAIN, PHASE, INPUT IMPEDANCE, OUTPUT IMPEDANCE and GROUP DELAY over a very wide frequency range.

Ideal for the analysis of ACTIVE and PASSIVE FILTER CIRCUITS, AUDIO AMPLIFIERS, LOUDSPEAKER CROSS-OVER NETWORKS, WIDE-BAND AMPLIFIERS, TUNED R.F. AMPLIFIERS, AERIAL MATCHING NETWORKS, TV I.F. and CHROMA FILTER CIRCUITS, LINEAR INTEGRATED CIRCUITS etc. STABILITY CRITERIA AND OSCILLATOR CIRCUITS can be evaluated by "breaking the loop". Can save days breadboarding and thousands of pounds worth of equipment.

£195 for PC/XT/AT etc. £130 for BBC B, B+ and Master

All prices Ex-VAT
WRITE OR PHONE FOR FULL DETAILS:- REF PE

Number One Systems Ltd



Harding Way, St Ives, Huntingdon Cambs, PE17 4WR
Tel: St Ives (0480) 61778

We provide full after-sales support with free telephone 'hotline help' service.

Software updates are free within 6 months of purchase date.

First, you find satellite, as Winnie-the-Pooh might have said. This is by no means as simple as pointing a television aerial in the general direction of your nearest tv station. To begin with the satellite transmitter is very much farther away – 36,000km or more in the case of geostationary satellites.

Because the satellites are spaced by only a few degrees from each other and the microwave transmissions are not very powerful, it's necessary to use a highly directional receiving antenna collecting as much electromagnetic radiation as possible – a parabolic dish antenna. This type of antenna has a receiving beam (radiation pattern) something like a searchlight beam. In effect you have to search for the wanted satellite with this beam, and it only has to be two or three degrees off the correct angle to miss the satellite altogether. Result: no signal at all, or a signal from another satellite nearby.

As I said in Part 1, this article is about receiving signals from satellites in the geostationary orbit (see Fig. 2 in Part 1). These geostationary satellites, about 150

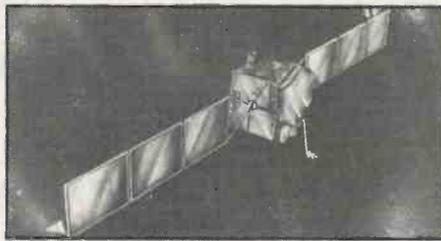
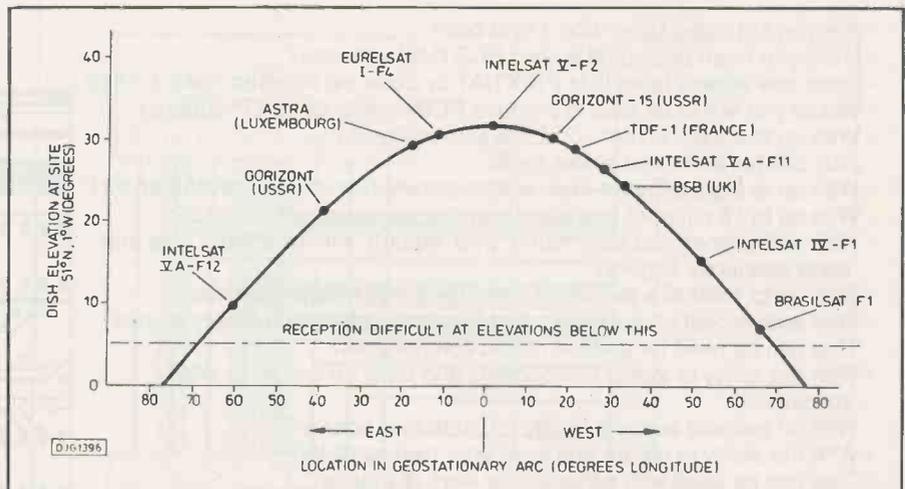


Fig. 2. Graph of dish angles of elevation needed for receiving signals from different orbit locations in the geostationary orbit (de-grees longitude). This assumes the same receiving site as in Fig. 1. A few of the forty or so GEO satellites accessible from this part of the world are shown on the graph.

SATELLITE FUNDAMENTALS

PART TWO – RECEIVING SATELLITE SIGNALS

altogether, are used for a variety of tasks – telecommunications, broadcasting, navigation, military and meteorological being the main ones. But we'll confine ourselves here to the signals which PE readers can probably best make use of – television signals.

SIGNAL GROUPS

This means two main groups: low-power tv signals coming from communications satellites, and higher-power signals from direct broadcasting satellites (dbs). In both cases the microwave signals

BY TOM IVALL

Direct broadcast satellite, cable television, electronic news distribution, reach earth from satellites in geostationary orbit. Before we can watch the tv, the tv (through satellite aerials) must watch them.

received – which have wavelengths in the region of 25 to 27 millimeters – are converted into a form suitable for feeding into the aerial socket of a standard tv receiver, so that they can be displayed as normal tv pictures.

So the tv signals of interest come from a number of different satellites. Each satellite carries a group of microwave relay stations called transponders. A transponder is basically a receiver feeding its output into a transmitter.

In the low-power communications satellites, some of the transponders are used for telecommunications (voice, data, etc) and some for television signals distribution. Of the last-mentioned group,


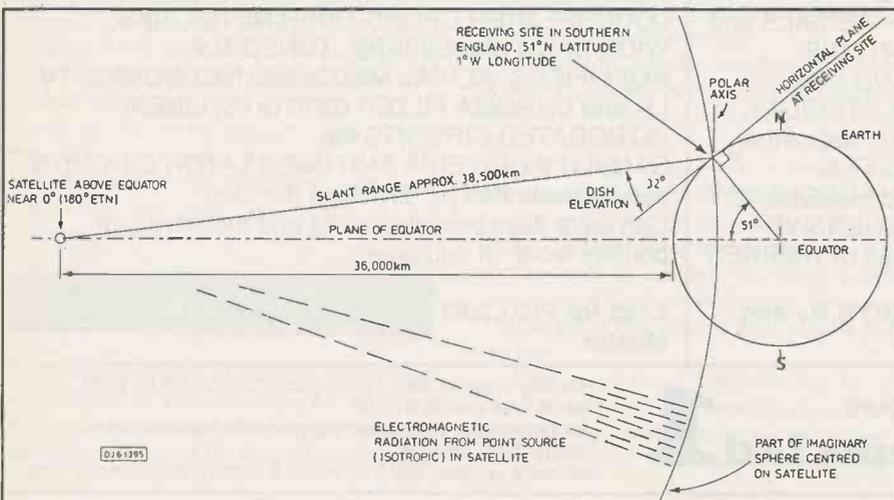


Fig. 1 Receiving conditions at a site in southern England for a geostationary satellite at an orbital position approximately above the Greenwich meridian (zero degrees longitude). Here the receiver dish antenna has to point due south, at an elevation of about 32°. Receiving other satellites on either side to the east and west would require different angles of dish azimuth and elevation. Also shown is part of an imaginary sphere in space centered on the satellite. This comes into the explanation about the rf power available at the receiving site.

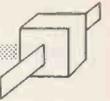

some of the tv signals are internal to broadcasting organisations (news feeds, programme exchanges, etc) while the remainder supply programmes to cable television companies and various community systems and can also be received by private individuals using their own television receive-only (tvro) equipment.

In the high-power direct broadcasting satellites all the transponders are dedicated to broadcasting to the general public – mainly tv programmes but some radio and teletext as well. They use high power for this very reason, to make reception as easy and inexpensive as possible. Among them we must include the recently launched Astra satellite. Although this transmits at medium power, and on frequencies in a communications band, it is specifically designed for dbs. The comsats use low

polarisation, modulation of the carrier wave, and encoding of the information conveyed. This article will concentrate on the two most fundamental characteristics for reception, orbital position and rf power.

SATELLITES AVAILABLE

Before you can decide which signals and programmes you want to receive you must check on what GEO satellites are actually 'visible', in the electromagnetic-wave sense, from where you live. Microwaves behave much the same as light waves. This means there has to be a direct line-of-sight, or unobstructed straight-line path for the waves, between each satellite and your receiving antenna.

If you happen to live somewhere on the

For a satellite due south of this position (eg the Intelsat V-F2) the line-of-sight from the receiving antenna is at an angle of about 32° up from the ground (elevation), as shown by the 'slant range' line in Fig. 1.

Looking east or west of this point, there will be other satellites 'visible' to the antenna, but at lower angles of elevation. The farther one looks east or west the lower is the angle of elevation, until at the extreme points of about 75° east or west no more of the geostationary orbit, and the satellites in it, will be visible.

The cut-off at these extreme points occurs simply because the surface of the Earth gets in the way and blocks the direct line-of-sight. Fig. 2 illustrates this by a graph which shows required angles of elevation for a dish antenna, located at 51°N and 1°W, for different points on the

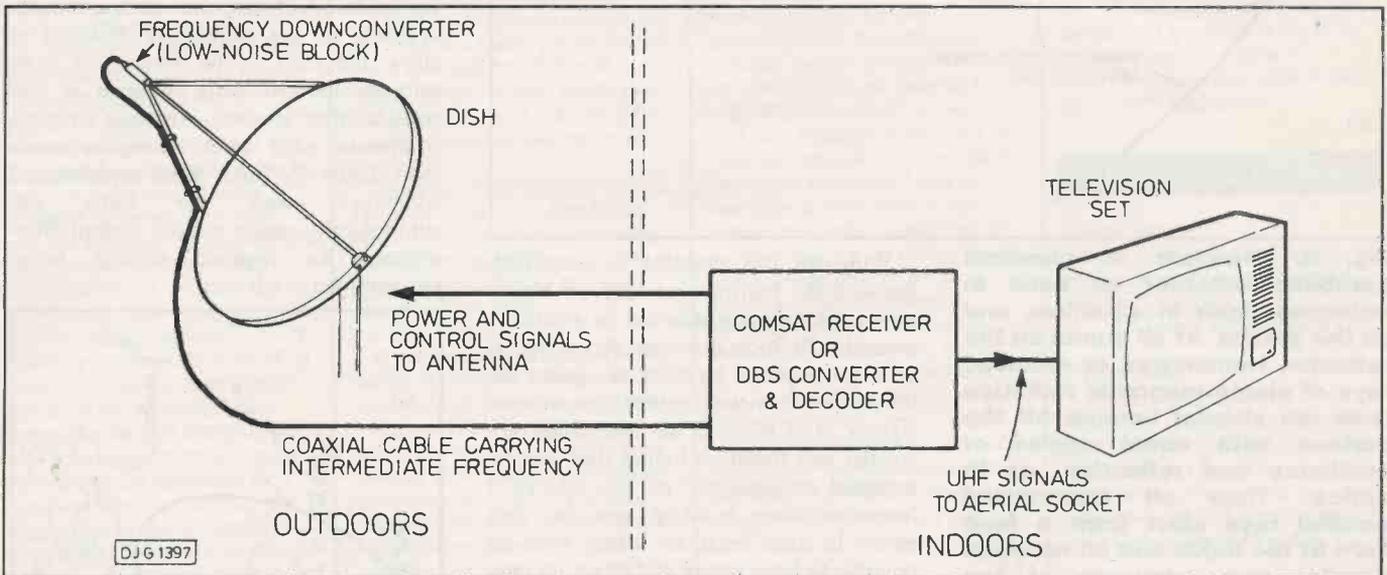


Fig. 3. Outline of equipment needed for receiving tv signals from GEO satellites, both dbs and communications spacecraft. In practice there are many variables, including dish area and pointing angles, signal frequency, wave polarisation and tv signal encoding, which determine what actual equipment is required for different satellites, and their transponders.

power because they were never intended for broadcasting in the true sense, only for broadcasting signal distribution.

But in both groups each transponder (or sometimes half of the capacity of a transponder) normally handles one television programme channel. So this is equivalent to a tv channel coming from a local terrestrial broadcasting station.

Signals from satellites have the following characteristics: position in space, radio frequency (rf) power, frequency and wavelength, wave

equator, some of the GEO satellites will be more or less above you and the others will be spread along an east-west arc in the sky down to the horizon. A large number of the satellites will be 'visible' because you are at the nearest position on Earth to the geostationary orbit (see Fig. 1) and there is no ground in the way to block your antenna's 'view'.

However, the majority of PE readers probably live in the northern hemisphere and a big group of these will be in the UK. *We have many readers who live in the Southern Hemisphere. Ed.* If you are in the UK, your situation will be more like that of the receiving site shown in Fig. 1. This, by way of example, is at a latitude of 51° North and longitude of 1° West, which happens to be near Petersfield in Hampshire.

From here you have to look towards the south to get a direct line-of-sight to part of the geostationary orbit. Obviously the equatorial plane of this orbit lies South of everywhere in the northern hemisphere.

geostationary orbit. It also shows some of the satellites accessible between the two cut-off points.

The graph line, corresponding to part of the GEO, is cut off at the points where the antenna elevation is zero – that is, looking straight along the ground, horizontally. In practice, though, the antenna beam must have a minimum elevation of about 5° because below this level – shown by the broken line – the receiver picks up too much man-made electrical interference and natural electrical noise (from heat radiation) from the ground.

You can find what satellites are available from published charts corresponding to Fig. 2 for your geographical position, in conjunction with information in satellite tv programme magazines, which usually give the orbital positions of the satellites. The accompanying table is just a short list as a guide.

However, the actual availability of signals from these satellites depends

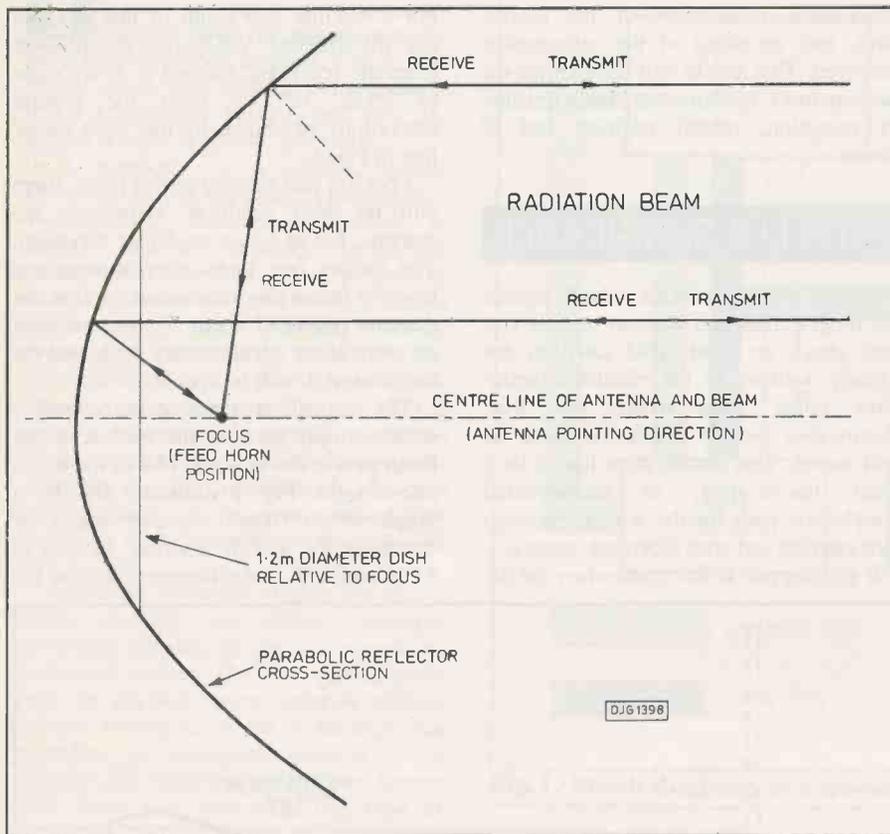


Fig. 4. Principle of classical parabolic reflector as used in antennas, both in satellites and on the ground. At all points on the reflector, transmitted or received rays of electromagnetic radiation (two are shown) bounce off the surface with equal angles of incidence and reflection, as in optics. Thus all transmitted parallel rays start from a feed horn at the focus and all received parallel rays converge at the focus. The part of the parabola occupied by a 1.2-metre diameter dish is shown. Other reflectors are designed to work from offset feed horns, to avoid the efficiency loss caused by equipment parts like struts being within the beam and blocking the incoming and out-going radiation. In practice the beam is not perfectly parallel but diverges slightly.

finally on where you can find a suitable place to set up your dish antenna. You must have a site from which there is a clear, unobstructed view of the southern sky at about 25° up from the horizontal, with as much angular deviation to left and right as possible. This may conveniently turn out to be in your back garden. But if it happens to be in your front garden you'll probably have to consult your family and neighbours to see if they'll agree to having a dish antenna on public view there. Failing these sites, it may be necessary to mount the dish on the site of your house.

With dbs this problem is simplified. Because the transmissions are on higher power the dish antennas can be smaller – generally 30-90cm diameter, depending on your geographical location, as against the 90-180cm diameter needed for comsat signals. And because the dbs dishes are smaller and therefore lighter they can be mounted conveniently on the side of a house or other building near the roof eaves. In some locations it may even be possible to have indoor dishes set up near windows. (Remember, though, that microwaves are impeded by glass. Ed.)

The equipment you will need for either comsat transmissions or dbs is shown in very general form in Fig. 3.

POINTING THE DISH

To point a receiving antenna accurately, the centre-line of the dish – which is a parabolic reflector as shown in Fig. 4 – must be made to point along the microwave beam coming from the satellite, up to the spacecraft itself. This means that the dish must be capable of being swung in two planes: in azimuth (horizontally, round the points of the compass); and in elevation (vertically, from the horizontal upwards).

Both of these angular distances are measured in degrees – azimuth from a north or south reference point, and elevation from the ground upwards. Some commercial dishes have mechanisms, called az/el mounts, which allow these

movements to be made independently.

First you must decide which satellites and channels you wish to receive. With dbs you can't use the same antenna dish for Astra, BSB and TDF-1, even at different times, because these satellites are at different orbital positions, requiring different azimuth and elevation settings. Furthermore, Astra operates on comsat frequencies (around 11 GHz, see table) while the other two work in the dbs band (around 12 GHz). This, and the fact that the two bands use different wave polarisations, means that the same rf downconverter unit on the antenna (called a low-noise block or LNB) is not usable for all three dbs satellites.


But because Astra operates in a comsat band, it can be received by the same antenna equipment and receiver as used for the low-power comsats – tvro equipment. And here the antenna mounts available on the market are designed to allow the dish to be swung, in both azimuth and elevation, to point at one satellite after another. With the simplest equipment each az/el setting is made individually by hand. More sophisticated equipment does the same job automatically under remote control from indoors, the required settings being programmed in advance.



Fig. 5. Coverage of a satellite transponder beam or 'footprint', is shown by contour lines like this. Here the line encloses an area of signal strength corresponding to a beam eirp of 50 dbW (100 kW). Other such contour lines outside this one would show how the eirp tails off at the outer edges of the coverage.

Although the dish must be positioned in both azimuth and elevation there is one type of antenna mount, now widely used, which simplifies the process by reducing it to a single mechanical displacement. Robert Calaz, managing director of Race Communications Ltd, South Ascot, Berks, kindly showed me how this works.

As the mechanism swings the dish

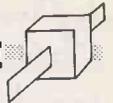

round in azimuth, the elevation continuously changes at the same time, so that the centre-line of the dish automatically follows the geostationary arc in the sky. The input drive is a single linear movement, provided by a dc motor-driven linear actuator. This mechanism is called a polar mount, because the axis about which the dish swings in azimuth is fixed parallel to the Earth's spin axis – a line between the north and south poles.

The polar mount is similar in principle to the equatorial mounting of an optical or radio telescope, which enables the telescope to automatically follow a given star in its movement across the sky. But because geostationary satellites are very

almanac you can easily calculate the time of day, on any particular day, at which the sun is exactly due south. Alternatively, the Intelsat V-F2 shown in Fig. 2 is only slightly off the Greenwich meridian, at 1°W. From a site somewhere near the meridian in the UK the dish can be lined up on this by trial-and-error, using a signal-strength meter in the receiver.

With the polar mount, once the peak of the antenna swing is accurately aligned with the arc at due south, the mechanism, if correctly set, will automatically track the geostationary orbit. Fine corrections can be made to this tracking by adjusting the mount so that maximum strength signals are obtained, on the signal-strength meter,

directions (isotropically) it would evenly 'illuminate' the interior surface of an imaginary sphere. At some receiving site in southern England this sphere would have a radius of about 38,500km, as shown in Fig. 1, and therefore an internal surface area ($4\pi r^2$) of well over 10,000 million million, or 10^{16} , square meters. So a dish antenna with an area of about 1 square metre would receive the 45W divided by the sphere area (assuming no losses), which comes to about one five-hundredth of a picowatt – a completely inadequate power for practical purposes.

However, the spacecraft transmitter antenna actually has a parabolic reflector (Fig. 4) to concentrate the 45W into a

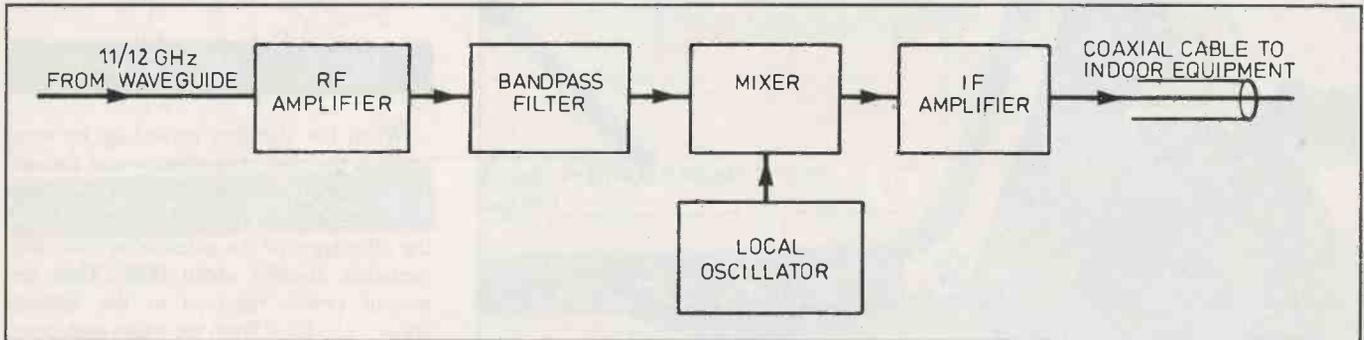


Fig. 6. Schematic of frequency downconverter or low-noise block mounted near the focus of a parabolic dish antenna (Fig. 4). This receives microwave signals via waveguide from a feed horn at the focus and converts them to a lower frequency for feeding along a coaxial cable to the receiver or converter unit indoors.

much nearer than the stars the difference in latitude between the two axes – antenna and Earth – is more significant than with telescopes. So a device for making an angular a correction for this, called declination offset, has to be built into the polar mount mechanism. In the UK, declination offset works out to an angle of 6-7°, depending on the latitude of the receiving site.

In practice the first step is to find a possible antenna site by simple observation and guesswork. Next, this position must be checked with a compass and inclinometer to make sure that it provides an unobstructed view of the geostationary arc (eg, as in Fig. 2) – or at least a useful part of it. A simple inclinometer can be made from card, plastic or wood with the aid of a protractor.

In setting up an antenna on a polar mount the most critical operation is to get the highest point of its azimuth-elevation swing to coincide exactly with the peak of the geostationary arc at due south. A compass is not accurate enough to find this point in the sky, but by using an

from a satellite somewhere to the east (say Eutelsat I-F4) and one somewhere to the west (say Intelsat VA-F11).

Some handbooks and some antenna suppliers provide helpful charts or tables for antenna pointing. (*We've one in our book service. Ed.*) These will show, for a particular satellite, the antenna angles of azimuth and elevation needed at different geographical locations in latitude and longitude.

SIGNAL POWER

After finding the orbital position of a satellite and being able to point your dish antenna at it accurately, the next most fundamental thing is to get an adequate signal from it to operate a receiver and give a good quality picture on the tv set. This means that the power of the signal must be substantially greater than the noise power in the space-to-Earth link (downlink) so that when both are amplified in the receiver you don't see the noise as speckles on the tv screen.

In practice we must take whatever rf power is transmitted by the satellite. Then we collect enough of it, by using a sufficiently large diameter dish antenna, to give a ratio of rf carrier power to noise power (c:n ratio) of at least 2:1, or 3 decibels (dB).

Suppose a satellite transmitter generates an rf signal power of 45 watts – a medium value. If this were radiated uniformly in all

narrow beam. This concentration is measured as the gain of the antenna, and a typical gain value of just over 2,200 times (or 33dB) would multiply the 45W by this amount to give an effective power in the beam of 100kW.

This effective power, which is real enough where received, is called the equivalent (sometimes 'effective') isotropically radiated power, or eirp for short. It is equivalent to the much higher rf power that would have to be radiated from an isotropic source to produce the same power as at the centre of the concentrated beam.

If you look at the coverage areas of 'footprints' of satellite transponder beams on maps you'll see contours of the kind shown in Fig. 5. The contour encloses an area within which the satellite transmitter is beaming down a certain eirp. The greater the eirp the stronger will be the signal received. But in practice the power contour is not labelled straightforwardly in watts or kilowatts but in decibels relative to 1 watt, or dB(1W). This is always abbreviated to dBW. So in the example shown 50dBW means 50 decibels relative to 1W, or 100,000 times 1W, or 100kW.

This apparent complication is actually a simplification for communications engineers, who find it more convenient to do calculations on rf powers, gains and losses (even bandwidth and noise power) by adding and subtracting the logarithmic decibels than multiplying and dividing. So the practice and terminology is used by everyone concerned.



Example of a frequency downconverter mounted on struts near the focus of a parabolic dish antenna. The cable at the bottom-right carries an intermediate frequency (if) signal to the indoor receiver and also brings in a supply of power to the converter electronic circuits. This maker calls the unit a low-noise converter (LNC) but others use the term low-noise block (LNB) for the same thing.

But what does this mean for you, in terms of signal strength coming into your dish antenna?

Well, what you receive is influenced by various losses in the space-to-Earth downlink, and there are also measured in decibels. The most fundamental one is the free space loss. It's what would occur in the theoretical condition of both the transmitting antenna and your receiving antenna being isotropic.

Here the power from the transmitter antenna would radiate uniformly in all directions, and at the receiving antenna could be considered as evenly illuminating the interior of an imaginary sphere, as discussed above. The amount of power falling on a given area of the sphere is important to know because the area of your dish (part of the imaginary sphere) determines how much power is collected for your receiver.

This value is the power density, measured in dBW per square metre, and is usually called the power flux density (pfd). The free space loss is due partly to the fact that the pfd is inversely proportional to the distance between the two antennas, r ; this component is called the spreading loss and is actually $10 \log_{10} 4\pi r^2$.

Overall, the free space loss in dB is given by the formula: $20 \log_{10} 4\pi r/\text{wavelength}$. For example, with a distance of 38,500km between satellite and receiving dish and a carrier frequency

of 12GHz, making the wavelength 25mm, the free space loss comes to 205.1dB.

In practice this free space loss is partly counteracted by the concentration into beams given by the transmitting and receiving antenna reflectors, so that the radiated power is not in fact isotropic.

Another unavoidable form of attenuation is due to the signal having to pass through the Earth's atmosphere. Losses in the various gases are negligible, but those due to water in the form of clouds, rain, mist, sleet and snow are more severe. Moderate rain causes a loss of about 1-2dB at 12GHz, heavy rain anything up to 10dB and torrential rainstorms anything up to 20dB.

POWER RECEIVED

When the signal is picked up by your antenna the dish concentrates and focuses the energy to provide a gain, as explained above. The gain figure takes account of the efficiency of the antenna in collecting radiation, usually about 60%. Thus the overall power received at the antenna focus, calculated from the gains and losses mentioned above is:

= eirp - free space loss - atmospheric loss + receiver dish gain dBW

As an example, assuming the satellite produces an eirp of 52 dBW, the atmospheric attenuation is 1 dB and the dish has a gain of 44 dB, the power received is:

= 52 - 205 - 1 + 44 dBW


= - 110 dBW

which works out to a power of 10 picowatts.

If the power flux density at the receiving point is known from, say, the satellite operator, you can work out how much power is being collected by your dish antenna. For example, under the international dbm plan the pfd is supposed to be - 103 dBW/m² in the centre of the beam. A dish of 1 square metre area would collect 50 pW and with a typical efficiency of about 60% it would give about 30 pW at the focus.

With such low power signals coming in, it's most important that the noise power generated by your receiving equipment is kept even lower. Otherwise you will get a lot of annoying speckles on the tv picture. This means that the first electronic circuits which amplify and frequency-convert the received microwave signal must use very low-noise transistors. Hence the descriptions 'low-noise block (LNB)' for these circuits - which in manufacturers' literature is partly a description and partly a claim!

Fig. 6 is a schematic of the standard LNB, which is mounted on the dish antenna itself close to the focus so that a

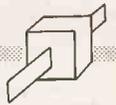

length of waveguide called a feed horn just encloses the focus point. It consists of a low-noise transistor rf amplifier, a bandpass filter, a local oscillator, a mixer and an intermediate frequency (if) amplifier. The if output frequency for comsat transmissions is in the range 0.95-1.7 GHz, and the if signal is fed along a coaxial cable to the receiver indoors.

Typical noise figures being claimed for these LNBs are in the region of 1.6dB. Noise figure measures the amount of noise introduced by the electronic system itself. It is defined as the ratio of the input to output signal-to-noise power ratios (or

noise factor) expressed in decibels. The lower dB value, the less noise is introduced, and 0 dB would mean no circuit noise introduced at all. A noise figure of 1.6 dB shows that the noise factor is 1.45. This would be given by, say, an input s:n power ratio of 6:1 and an output s:n power ratio of 4:1.

Finally, if you do decide to set up your own satellite tv receiving station don't forget that you need a licence to operate it, in addition to your ordinary tv licence. This costs £10 and is valid indefinitely. To get it you must first obtain and fill in a TVRO Licence application form issued by

the Department of Trade and Industry, Radiocommunications Division, Room 513, Waterloo Bridge House, Waterloo Road, London, SE1 8UA (tel: 01-215 2221 or 2306). You then send the form and the £10 licence fee to an address given on the form. Incidentally, this doesn't clear you from any planning permission you might also have to obtain from your local authority to install a dish (or dishes) on your house or in your garden.

The next article will deal with more of the fundamental characteristics of satellite signals.

PE

Table: Some geostationary satellites transmitting television signals

Satellite name	Owner nationality	Type of Service	Orbital position	Band	Downlink frequency allocation
Astra	Luxembourg	dbt	19.2°E	Ku	10.7-11.7 GHz
Eutelsat I-F4	international	comsat	13°E	Ku	10.7-11.7 GHz
Gorizont-15	USSR	comsat	14°W	C	3.4-4.2 GHz
TDF-1	France	dbt	19°W	Ku	11.7-12.5 GHz
Intelsat VA-F11	international	comsat	27.5°W	Ku	10.7-11.7 GHz
BSB*	UK	dbt	31°W	Ku	11.7-12.5 GHz

* Due for launch in late 1989. See next article for more complete information on frequency bands

Component Solutions Ltd.

0782 641884


CPU		MEMORIES		LOGIC		MISCL.		CRYSTALS		SPECIAL OFFERS	
Z80A	1.50	2716	1.50	74LS00	0.14	1488	0.40	1.8432MHZ		74HC00/02/08/32	0.12
8085	1.50	2732A	3.50	74LS02	0.14	1489	0.40	0.90		74HC10/74/123/139	0.12
80C85	3.20	2764	1.50	74LS04	0.14	7805	0.20	4 Meg	0.50	4013/4017/4040/4066/4081/	
6502	3.00	27C64	2.75	74LS08	0.14	7905	0.20	6 Meg	0.50	40097/40098	0.12
8031	2.20	27128	3.50	74LS10	0.14	LM320T	0.15	8 Meg	0.50	8mhz crystals HC18/U	0.25
80C31	3.20	27C128	3.50	74LS14	0.15	LM339	0.15	10 Meg	0.50	SCN 2681AC128	0.50
63A03	5.00	27256	3.50	74LS20	0.16	LM380N	0.15	12 Meg		POTS 3296W50 Ohm	0.20
64180-8	12.00	27C256	3.50	74LS30	0.16	79L05	0.20			2716 - 1.50, 2764 - 150	1.50
Z80ACTC	1.50	27C512	7.00	74LS32	0.16	BC183	0.08	SOCKETS		5% DISCOUNT	
Z80API0	1.50	6116LP-15	3.00	74LS74	0.16	BC184	0.08	8W	0.08 0.12	on orders above £25.00	
Z80AS10	1.50	6264LP-126.00		74LS86	0.16	6N136	0.40	14W	0.14 0.18	Full price list available,	
8155	1.80	62256LP-12		74LS138	0.18	6N138	0.40	16W	0.22	many more special offers	
8243	1.40		12.50	74LS139	0.18	6N139	0.40	20W	0.18 0.24	please phone or write for	
8251	1.20	4164-15	2.40	74LS151	0.24	TL084	0.25	24W	0.30	details.	
8253-5	1.20	41256-15	7.00	74LS153	0.18	AM2966PC	1.25	28W	0.28 0.45	COMPONENT SOLUTIONS LTD	
81C55	1.20	511000-10		74LS164	0.50	ICL7107	0.50	40W	0.55	112 BURREINGTON DRIVE	
8212	1.45		26.00	74LS240	0.18					NEW PARK, TRENTHAM,	
82C55	1.80			74LS244	0.24	LEDS		S&F TP		STAFFORDSHIRE, ST4 8SP.	
6522	2.40			74LS245	0.24	3mm	0.10	Also available		PLEASE ADD 0.75P P&P THEN 15%	
6551	3.20	All items from		74LS373	0.15	5mm	0.15	IDC< D, 41612		VAT TO TOTAL	
6845	2.85	stock quick		74LS01	0.12	ILQ74	1.80	connectors.		ALL TRANSACTIONS CHEQUE	
6809	1.60	service,		74LS73	0.12	ILQ2	1.50	Capacitors, wire,		WITH ORDER	
6802	1.90	quality		74LS157	0.15	ULN2001	0.60	ribbon cable,			
6821	1.40	products only,		74LS07	0.15	ULN2002	0.60	diodes,			
6850	1.40	low prices		74LS377	0.15	ULN2003	0.60	transistors			
						ULN2004	0.60	resistors solder,			
								computer leads			

The Soviet probe Phobos 2 is now in orbit round Mars, and is sending back data. Meanwhile, Voyager 2 is on its way to Neptune, and is still functioning well, so that during the actual encounter, in August, we may hope for results as good as those already obtained from Jupiter, Saturn and Uranus.

Two supernovæ have been 'in the news' recently. Much has been heard of the Supernova 1987A, which flared up in the Large Cloud of Magellan in February 1987 and became visible with the naked eye – the first supernova to do so since Kepler's Star of 1604. Astronomers have been wondering whether it would produce a pulsar, made up of neutrons and spinning around very rapidly; pulsar material is amazingly dense – an eggcup full of it would weigh thousands of millions of tons – and the rotation rates are very high. The most famous pulsar is that in the Crab Nebula, known to be the remnant of the supernova of 1054.

So far as 1987A was concerned, it was assumed that after the explosion, the dense cloud of debris around the site of the outburst would hide the centre. It was even suggested that the end product might be a black hole. However, in February 1989 a group of American astronomers at Cerro Tololo, in Chile, announced the discovery of a pulsar rotating almost 2000 times per

SPACE

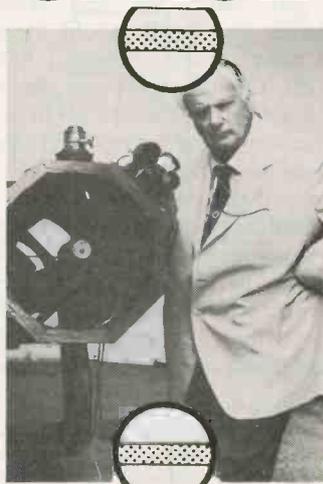

WATCH

BY DR PATRICK MOORE CBE

**In a violent Universe
even the Moon may
not be passive**

second. This announcement caused great interest, but it was not confirmed by other groups, so that either there has been some error in interpretation or else the pulsar is being intermittently obscured by material swirling around it.

The other old supernova is S Andromedæ, seen in 1885 in the Andromeda Galaxy (M.31). It reached the sixth magnitude, but its true nature was not appreciated, because at that time the so-called "spiral nebulae" were generally regarded as minor features of our Galaxy rather than independent systems. The outburst soon faded away, but is now known to have been a Type I Supernova – that is to say, an outburst involving the complete destruction of the white dwarf component of a binary system rather than the collapse of a single massive star, as with the recent supernova in the Large Cloud of Magellan. The remnant of S Andromedæ has now been identified by astronomers at Kitt Peak, in Arizona, using the 4-metre reflector there. The expanding cloud spreading out from the old supernova is now about one light-year across, with an expansion speed of some 4,000 kilometres per second. It is a great pity that S Andromedæ did not flare up a century later, when we would have been able to take full advantage of it!

THE SKY THIS MONTH

Of the five bright planets, four are in the evening sky this month, but none is really well placed – apart from Mercury, which reaches its greatest eastern elongation (21 degrees) on May 1, and should be visible in the evening twilight for the first ten days of the month. Venus is emerging after sunset, and is becoming more and more evident, but the phase is still well over 95 per cent, so that no telescope will show definite features on the disc. Mars remains on view after dark, but the apparent diameter has now fallen to only between 4 and 5 seconds of arc and the magnitude to +1.7; the phase is 95 per cent. Jupiter will be lost in the evening twilight by the end of the month.

Saturn, Uranus and Neptune are fairly close together, in Sagittarius, and now rise around midnight, so that even though they are low down from British latitudes this is a good time to identify the two outer giants. They are easy enough to find. Uranus has an apparent diameter of 3.9 seconds, of arc and a magnitude of 5.6; any small telescope should be enough to distinguish it from a star, and it is decidedly green. Owners of adequate telescopes should look for the two senior satellites, Titania and Oberon. Neptune, with an apparent diameter of no more than 2.5 seconds of arc, is within binocular range (magnitude 7.9) and is bluish rather than green, but in small telescopes it does look like a star, and one has to identify it by its slow movement from night to night.

The Moon is new on May 5, and full on the 20th. The date of new moon coincides with the maximum of the meteor shower known as the Eta Aquarids, which will therefore be seen to advantage. These meteors represent the debris of Halley's Comet, and around May 5 there should be plenty of them. Of course, Halley's Comet itself has now been lost to view except with the world's largest telescopes; it will not next return to perihelion (its

closest point to the Sun) until the year 2061.

The main spring constellation, Leo (the Lion) is still very conspicuous, now slightly west of south during the late evening; it is followed round by Virgo (the Virgin), one of the largest constellations in the sky, with its bright star Spica and its rather obvious Y-outline of moderately bright stars. It is here that we find the Virgo cluster of galaxies, over 50,000,000 light-years away. Not many of these galaxies are visible with small telescopes, but the cluster contains many hundreds of members, some of which are much larger than our Milky Way galaxy. High on the south lies Arcturus in Bootes (the Herdsman), which is orange in colour, and is actually the brightest star in the northern hemisphere of the sky; it is surpassed only by Sirius, Canopus and Alpa Centauri, all of which lie south of the celestial equator. In the east, the "Summer Triangle" (Vega in Lyra, Deneb in Cygnus, and Altair in Aquila) is becoming prominent, and will dominate the evening sky throughout the summer.

Low in the south lies the immense, sprawling constellation of Hydra, the Watersnake. Below Spica in Virgo you will see a third-magnitude star, Gamma Hydra, and close to this is a famous variable, R Hydra, which reaches its maximum brightness on May 13, and should then be easily visible with the naked eye (magnitude 4.1/2). R Hydra is a red star, which was a period of variation of less than 400 days – it seems to have been nearer 500 days a century ago, so that it has changed its habits! It is thought to be about 350 light-years away, and to be as luminous as 250 Suns, so that it is not nearly so powerful as a red giant such as Betelgeux in Orion. This month is a good time to look for it; binoculars bring its colour out very well. Incidentally, the conspicuous little quadrilateral of stars making up Corvus, the Crow, lies closely to its west, and makes a good 'pointer' to it.

THE PROCLUS OUTBURST ON THE MOON

For many years it was tacitly assumed that the Moon must be totally inert, and that nothing has happened there for at least a thousand million years. Practical lunar observers were not so sure, and occasionally reported short-lived, localised outbursts due probably to gaseous emissions from below the crust. My own name for them - TLP, or Transient Lunar Phenomena - proposed in the 1950s has

now been generally accepted.

TLP are not easy to see, and very difficult to record photographically. The only really good spectrogram of a TLP was obtained by the Russian astronomer N. Kozyrev as long ago as 1958, when he recorded an outburst in the large walled plain Alphonsus. However, new photographic confirmation has now been obtained by the Greek astronomer G. Kolovis, of the University of Thessaloniki, who has photographed a bright outbreak near the crater Proclus. It seems that the event covered an area about 22 x 18 kilometres wide, with a total energy of around 1017 erg. Very careful analyses have

shown that it cannot have been due to a photographic effect of anything of the sort, and mundane phenomena such as aircraft in our own atmosphere have also been ruled out.

Proclus, near the border of the lunar Mare Crisium, is one of the brightest craters on the Moon, and has been the site of previously report TLP. The Kolovos photograph provides confirmation that the amateur observers have been right, and that the Moon is not so inert as used to be thought. Further confirmation may be forthcoming before long. In spite of the Apollo landings, the Moon can still provide us with plenty of surprises!

PE

Do not miss a single issue of Astronomy Now

Britain's leading astronomical magazine

Edited by well known astronomer and
regular contributor to *Practical Electronics*
Dr. Patrick Moore CBE

Place a regular order with your newsagent or for £15-00
(overseas £18-00) take out an annual subscription from Intra Press,
Intra House, 193 Uxbridge Road, London W12 9RA



HART ELECTRONICS

HART ELECTRONICS are specialist producers of kits for designs by JOHN LINSLEY-HOOD. All kits are APPROVED by the designer.

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS



Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit £33.70
VU Meters to suit £2.30 each
Reprints of original Articles 75p no VAT
860X Stereo Mic Amplifier £8.70

LINSLEY HOOD 300 SERIES AMPLIFIER KITS

Superb integrated amplifier kits derived from John Linsley-Hood's articles in Hi-Fi News. Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35 35 Watt. Discount price for Complete Kit £98.79
K300-45 45 Watt. Discount price for Complete Kit £102.36
RLH485 Reprints of Original Articles from Hi-Fi News £1.05 no VAT

LINSLEY-HOOD SUPER HIGH QUALITY AM/FM TUNER SYSTEM.



Our very latest kit for the discerning enthusiast of quality sound and an exotic feast for lovers of designs by John Linsley-Hood. A combination of his ultra high quality FM tuner and stereo decoder described in "ELECTRONICS TODAY INTERNATIONAL" and the Synchrodyne AM receiver described in "Wireless World". The complete unit is cased to match our 300 Series amplifiers. Novel circuit features in the FM section to include ready built pre-aligned front-end phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together make a tuner which sounds better than the best of the high-priced exotica but, thanks to HART engineering, remains easy to build. The Synchrodyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HiFi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of it's sound it is incredible value for money. To cater for all needs four versions are available with variations up to the top of the range full AM/FM model, with any unit being upgradeable at any time. Send for our fully illustrated details.

Complete stereo record, replay and bias system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life.
K900W Stereo Kit with Wound Coils and Twin Meter Drive £65.67
RJ51 Reprints of Original Articles £1.30 no VAT

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £7.66
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £14.86
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £14.60
HX100 Stereo Permalloy R/P Head. Special Offer £2.49
MA481 2/2 Language Lab R/P head £13.35
SM166 2/2 Erase Head. Standard mounting, AC type £8.85
SM150 2/2 Erase Head. DC Type £3.60
HQ751E 4/4 Erase Head for Portastudio etc. £46.80
Full specifications of these and other special purpose heads in our lists.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback £4.54
Curved Pole Type for inaccessible heads £4.85

Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and Insurance as follows:

INLAND
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50

OVERSEAS
Please send sufficient to cover
Surface or Air Post as
required.

Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE
(0691) 652894

ALL PRICES EXCLUDE VAT
UNLESS STATED






UK Distributor for the complete ILP Audio Range



- Bipolar Modules
15 watts to 180 watts
- Mosfet Modules
60 watts to 180 watts
- Power Supplies
- Pre-amplifier Modules
- 100 volt line Transformers
- Power Slave Amplifiers

UK Distributor for Toroidal Transformers

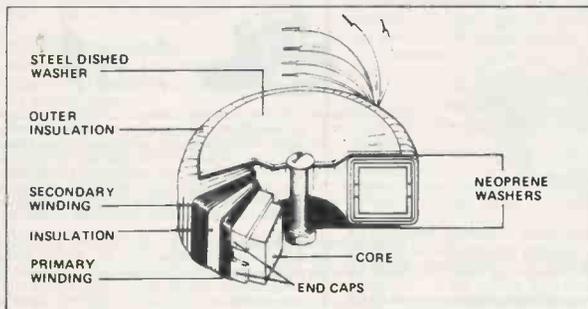

- Standard range available from stock 15VA to 625VA
- Design and manufacture up to 3KVA with fast prototype service

Write or phone for prices and data.

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254 Fax: 0227 365104

SURVEILLANCE PROFESSIONAL QUALITY KITS

A range of high quality kits as supplied to leading UK security companies, all in-house designed and produced, not to be confused with cheap imports. All kits come fully documented with concise assembly and setting-up details, fibreglass PCB and all components. All transmitters are fully tuneable and can be monitored on a normal VHF radio or tuned higher for greater security. All units available ready built if required.

MTX Micro Miniature audio transmitter. 17mm x 17mm. 9V operation. 1000m range	£10.95
VT500 Hi-power audio transmitter. 250mW output. 20mm x 40mm. 9-12V operation. 2-300m range	£12.95
VOX75 Voice activated transmitter. Variable sensitivity. 30mm x 40mm. 9V operation. 1000m range	£15.95
CTX900 Sub-carrier scrambled audio transmitter. Cannot be monitored without decoder fitted to radio. 30mm x 40mm. 9V operation. 1000m range	£18.95
DSX900 Sub-carrier decoder unit for monitoring CTX900. Connects to radio earphone socket. Provides output for headphones. 35mm x 50mm. 9-12V operation	£17.95
HVX400 Mains powered audio transmitter. Connects directly to 240V AC supply. 30mm x 35mm. 500m range	£15.95
XT89 Crystal controlled audio transmitter. High performance. 100mW output. Supplied with xtal for 108MHz. Others available to 116MHz. 85mm x 28mm. 9V operation. 2-300m range	£29.95
TKX900 Tracker/Beeper transmitter. Transmits continuous stream of audio pulses. Variable tone and rate. Powerful 200mW output. 63mm x 25mm. 9V operation. 2-300m range	£18.95
ATR2 Micro size telephone recording interface. Connects between telephone line (anywhere) and cassette recorder. Tape switches automatically with use of phone. All conversations recorded. Powered from line. 10mm x 35mm	£10.95
TLX700 Micro Miniature telephone transmitter. Connects to line (anywhere) switches on and off with phone use. All conversations transmitted. 20mm x 20mm. Powered from line. 1000m range	£10.95
XML900 RF bug detector. Variable sensitivity. Triggers LED and beeper when in presence of RF field. Detects MTX 15-20 feet. 55mm x 55mm. 9V operation	£21.95
XL700 Professional bug detector/locator. Variable sensitivity. Twin mode ten segment LED readout of signal strength with variable rate beeper. Second mode AUDIO CONFIRM distinguishes between localised bug transmission and normal legitimate signal such as pagers, cellular etc. 70mm x 100mm. 9V operation	£49.95

UK customers please send cheques, PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft or Eurocheque and add £5.00 per order for shipment. Credit card orders accepted on 0827 714476. Full catalogue available on receipt of 23p stamp. Trade enquiries welcome.

THE WORKSHOPS
95 MAIN ROAD, BAXTERLEY
Nr Atherstone, WARKS CV9 2LE

08927 714476

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60 OUTPUT 0-260V	
200W 0.1 amp max £24.00 p&p	£3.00 (£31.05 inc VAT)
0.5KVA 2.5 amp max £26.50	£3.75 (£34.75 inc VAT)
1KVA 5 amp max £34.00	£4.25 (£43.99 inc VAT)
2KVA 10 amp max £49.00	£5.50 (£62.68 inc VAT)
3KVA 15 amp max £65.00	£6.25 (£81.94 inc VAT)
5KVA 25 amp max £115.00	
Carriage on request	

VOLTAGE CHANGING TRANSFORMER

125W Watt auto. Tapped 090V, 100, 110, 115, 120, twice to obtain voltages between 90 + 240V. Fitted in heavy duty louvered metal case. Fused input. £39.50 incl. p&p and vat.

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO (110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

UNTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £10.44 (£12.90 inc VAT) Caller only	(£9.99 inc VAT)
2ft 20 watt £7.44 + £1.25 p&p	(£7.19 inc VAT)
13in 10 watt £5.50 + 75p p&p	(£6.04 inc VAT)
12in 8 watt £4.50 + 75p p&p	(£6.04 inc VAT)
9in 6 watt £3.60 + 50p p&p	(£4.72 inc VAT)
6in 4 watt £3.60 + 50p p&p	(£4.72 inc VAT)

230V AC BALLAST KIT for either 6in, 9in or 12in tubes £5.50 + 55p p&p (£6.96 inc VAT)
For 13in tubes £6.00 + 75p p&p (£7.75 inc VAT)

400 WATT UV LAMP

Only £28.00 + £2.50 p&p (£35.08 inc VAT)

175 WATT SELF BALLASTED BLACK LIGHT MERCURY BULBS

Available with BC or ES fitting £18.65 inc.

12 VOLT BILGE PUMPS

Buy direct from the importers

500 GPH 15ft head 3 amp £16.00 inc.

1750 GPH 15ft head 9 amp £19.25 + £2.00 p&p (£25.00 inc VAT)

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angstrom Tube Ballast unit pair of bi-pin leads neon indicator on/off switch safety microswitch and circuit £14.00 + £2.00 p&p (£16.40 inc VAT)

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical users etc. Approx 16 joules. Adjustable speed £48.00 + £2.00 p&p (£57.50 inc VAT)

Case and reflector £22.00 + £2.00 p&p (£27.60 inc VAT) SAE for further details including Hy-Light and Industrial Strobe Kits.

700 WATT UV LAMP

Only £28.00 + £2.50 p&p (£35.08 inc VAT)

175 WATT SELF BALLASTED BLACK LIGHT MERCURY BULBS

Available with BC or ES fitting £18.65 inc.

12 VOLT BILGE PUMPS

Buy direct from the importers

500 GPH 15ft head 3 amp £16.00 inc.

1750 GPH 15ft head 9 amp £19.25 + £2.00 p&p (£25.00 inc VAT)

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angstrom Tube Ballast unit pair of bi-pin leads neon indicator on/off switch safety microswitch and circuit £14.00 + £2.00 p&p (£16.40 inc VAT)

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical users etc. Approx 16 joules. Adjustable speed £48.00 + £2.00 p&p (£57.50 inc VAT)

Case and reflector £22.00 + £2.00 p&p (£27.60 inc VAT) SAE for further details including Hy-Light and Industrial Strobe Kits.

700 WATT UV LAMP

Only £28.00 + £2.50 p&p (£35.08 inc VAT)

175 WATT SELF BALLASTED BLACK LIGHT MERCURY BULBS

Available with BC or ES fitting £18.65 inc.

WIDE RANGE OF XENON FLASHTUBES

Write/Phone your enquiries

SOLID STATE RELAY

Single make will switch up to 250 V AC 10 amp operating voltage 3-32 V DC silent contactless opto-isolated. Fraction of maker's price £3.00 + 50 p+p. Total inc VAT £4.03.

SPECIAL OFFER AC CAPACITORS

1.5 MFD 440V £2.00	5 MFD 440V £4.00
2 MFD 440V £2.50	5.4 MFD 280V £2.00
4.1 MFD 440V £3.50	5 MFD 660V £3.00
	12 MFD 400 £4.00

p+p 50p per unit plus VAT to be added to total.

TORIN CENTRIFUGAL BLOWER

230V ac 2,800 RPM 0.9amp 130mm diameter impeller outlet 63 x 37mm overall size 195 x 160 x 150mm long. Price £17.50 + £2.50 p&p (£23 inc VAT)

SHADED POLE GEAR MOTORS

In the following sizes:
9 RPM 12 RPM 80 RPM 160 RPM 110V AC or 240V AC with capacitors (supplied) Price inc. VAT + p&p £12.65

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation price inclusive p&p + VAT £23.00.

12 V DC COOLER EXTRACTOR FAN

New brushless motor 92mm sq. Total inc p&p + VAT £11.50.

SOLID STATE ENT UNIT

Input 230/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics. eg supplying neon or argon tubes etc. Price less case £8.50 + £1.00 p&p (£10.93 inc VAT) NMS

COOLING FANS-BRAND NEW!

200/400V AC American Boxer 'Pewee' 7-bladed high efficiency cooling unit 80mm sq x 40mm deep 40cm approx £10.35 inc.

EX-EQUIPMENT FANS

120mm sq x 33mm deep in either 115V or 230V AC Tested and guaranteed Price £7.76 inc.

Large selection of various speed geared motors from stock. Phone or write for details.

From stock at prices that defy competition

C/F Blowers Program Timers
Microswitches Synch Motors
write/phone your enquiries

NMS - NEW MANUF SURPLUS
R&T - RECONDITIONED AND TESTED

Ample
Parking Space
Showroom open
Monday/Friday

SERVICE TRADING CO
57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
01-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10



Using just a couple of 1N4148 diodes, a cheap op-amp and a 1mA meter, a true rms reading ammeter and voltmeter can be built for use with difficult waveforms.

- * More accurate than the ac scales provided on multimeters.
- * Can be used at higher frequencies than most other instruments.
- * Works regardless of how distorted the waveform is.
- * Gives better performance than true rms ic converters in respect of crest-factor.
- * Gives isolation from signal source.

It is no longer just the traditional applications in power electronics, such as servomotors and power supplies, that have solid-state controls. Many everyday devices like incandescent and fluorescent lamps, electric drills, all types of heating elements from soldering irons to storage heaters and domestic appliances such as food processors now have electronic controls. Often they handle large amounts of power – several kilowatts.

The application of electronic control is extending further and further, and it is often no longer adequate to use the ac scales

A THERMAL CONVERSION AMMETER AND VOLTMETER FOR POWER ELECTRONICS

True RMS measurement is more useful than peak or average metering for non-sinewaves – but many meters don't give a true reading.

of waveform shape, and which has good frequency response (into the MHz range). These designs of dmm are better, but they still have technical snags, explained later.

the movement introduces an inductance in the circuit being measured. This can pose severe difficulties.

To illustrate the diversity of waveforms that have crept into everyday use, a few commonly-encountered examples are shown in Fig. 1.

In order to measure the true rms value of waveforms like these shown, the best method is to convert the signal to heat and then measure the heat in the form of temperature rise. To understand how this works, it is necessary to have a good grasp of what the words root-mean-square actually mean when applied to both ac and dc systems. If you already have a good grounding, you can skip this next section.

RMS DEFINED

Consider the simple circuit shown in Fig. 2. Suppose the switch is turned on and off every second to give a waveform across resistor R as shown in Fig. 3.

What is the *effective* voltage across R? At first glance, you may think that since 10V

TRUE RMS METER

provided on a multimeter for measurement. On both moving-coil and digital multimeters, the ac scales optimistically labelled "RMS" are more often than not false scales based on an averaging technique that is only true at 50 Hz and for pure sine waves. Try using these instruments on a 440 Hz switched-mode power supply and you soon discover your mistake. An explanation of how these scales are calibrated is included later.

However, some dmm (digital multimeter) instruments use a sophisticated ic which performs a rapid calculation of the rms value of an incoming waveform almost regardless

BY ROD COOPER

Also, the ics used are expensive.

Another instrument used for rms measurement is the moving-iron meter, and the movements on some are far removed from the cheap and badly made meters usually associated with the name moving-iron, and are precision engineered. The final photo shows the Sangame-Weston moving-iron movement which has excellent design and engineering. Nevertheless, it still gives problems when the waveform is complex when the frequency rises beyond a few hundred Hz. Also, the coil which energises

appears across R for only half a cycle, the effective voltage would be 5V. In other words, the effect on R would be the same as connecting a 5V battery straight to it without the switching.


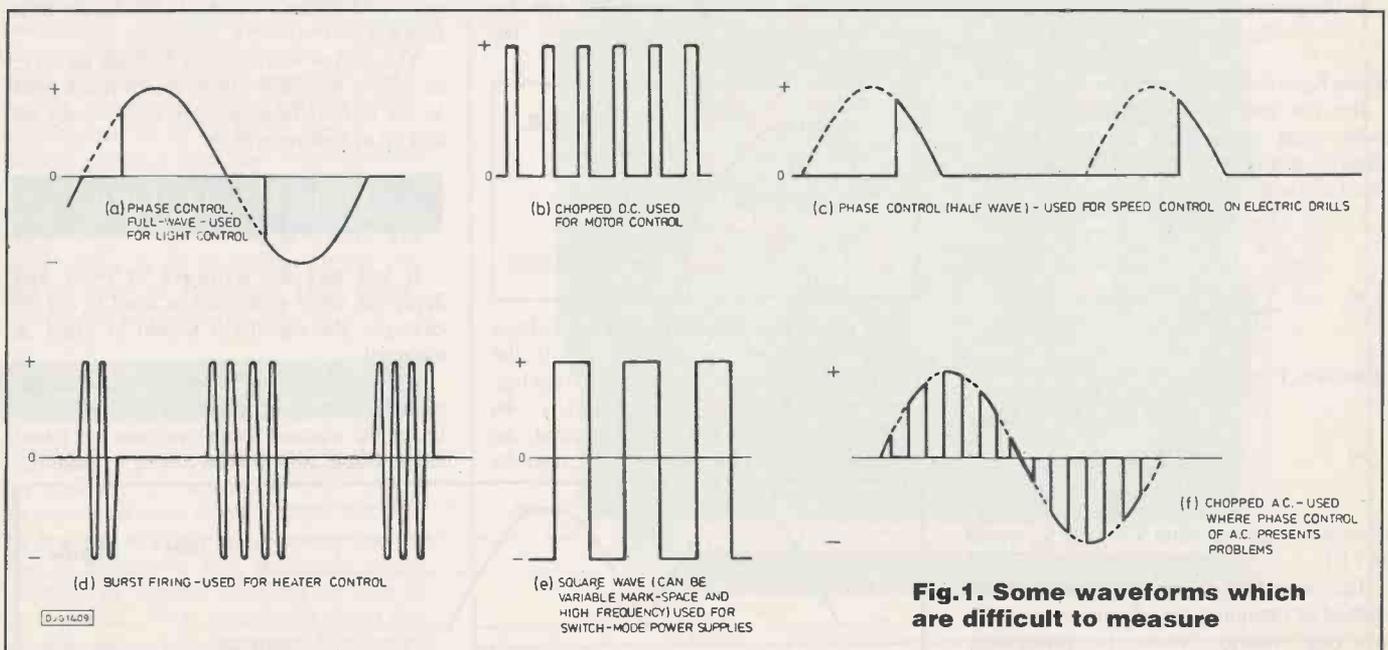
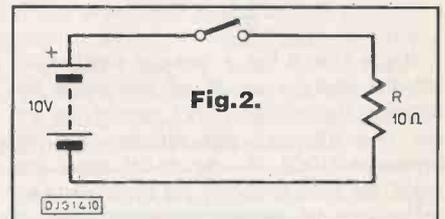


Fig. 1. Some waveforms which are difficult to measure

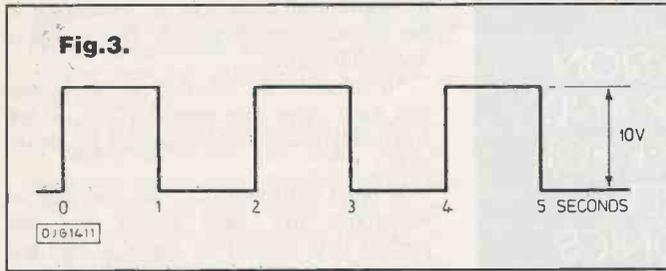

But, if you connected a wattmeter to the 10V switched circuit you would find a power level of 5 watts, and if you then measured the 5V unswitched circuit, you would find a power level of only 2.5 watts. Clearly the effective voltage of the 10V switched circuit is not 5V but something in between 5V and 10V.

Before going further, note that this is a dc circuit and that rms values are not confined solely to ac systems – far from it. Also note that when the effective voltage is mentioned, this refers to a voltage equivalent to that steady dc voltage which would produce the same effect; in our example this means heat in the resistor.

$$\text{Now, } P = \frac{V^2}{R}$$

where P is the power level, V the voltage and R the resistance.

$$\text{and } E = P.T$$

where E is energy, P is power again, and T is time.

Combine these two equations:

$$E = \frac{V^2 T}{R}$$

If you look at Fig. 3, you can easily work out the energy content of one pulse by squaring the voltage (10V) multiplying by the time (1 sec) and dividing by the resistance (10Ω). As the on/off times are equal, the average energy per cycle could be obtained by dividing by 2.

$$\text{In the general case, } E_{av} = \frac{V^2 T}{2R}$$

where E_{av} is the mean energy level.

But the mean, or effective, energy per cycle must be related to the mean or effective power level, P_e , which in turn must be related to the effective voltage V_e .

$$\text{i.e. } E_{av} = P_e T = \frac{V_e^2 T}{R}$$

$$\text{so } \frac{V^2 T}{2R} = \frac{V_e^2 T}{R}$$

$$\text{cancelling T and R; } V_e^2 = \frac{V^2}{2}$$

$$\text{so } V_e = \frac{V}{\sqrt{2}}$$

If we substitute the value $V = 10V$, V_e would be 7.07.

This round-about but easily understood method of obtaining the effective voltage by involving energy levels is particularly

relevant when considering the thermal-conversion technique because the heat energy produced in resistor R represents the mean electrical energy level.

It should be clear from this example that the same result could be arrived at graphically. First, square the voltage pulse, as in Fig. 4.


Then, find the area under the squared pulse, divide this by the time for one cycle to get a mean, then take the square root to get the effective voltage.

This could be done even if the waveform was not regular by counting the squares under the graph, whereas the mathematical method would fall down. This method lucidly describes in fact what rms means – the root of the mean of the squared value.



Although there are instances where the effective or rms voltage can be arrived at graphically or by calculation, these methods are useless when it comes to waveforms shown in Fig. 1. Imagine trying to calculate or solve by counting squares any of these! Hence an instrument which reads true rms with any waveform, regardless of shape, is very useful.

MEASURING AC VALUES

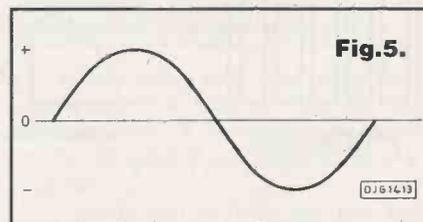Consider one cycle of a sine wave with peak voltage V_{pk} , as in Fig. 5. As the area under the positive curve is equal to the area under the negative curve, the sum of the two is zero; it follows that the average value of a sine wave is zero, ie not much use for practical purposes. We could rectify the waveform, as in Fig. 6.



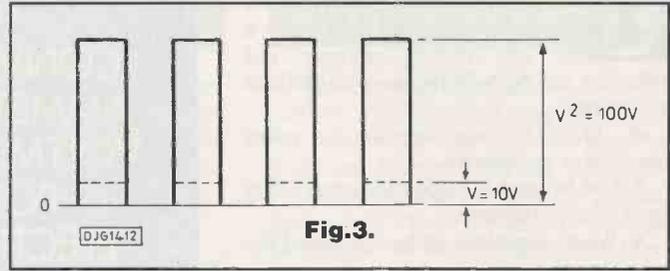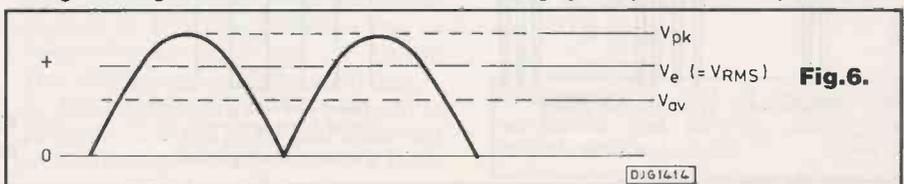We could now obtain an average voltage graphically or by calculation. Or, if the rectified voltage was applied to a moving-coil meter, which is intrinsically an averaging device, we could obtain an average reading. The scale could then be



calibrated in average volts, but this would not be much use for subsequent calculations, and would not be very popular. Alternatively, the meter scale could be given a false calibration in RMS values. This would only be correct for the particular sine-wave in question. In the UK the most frequent measurement is of course 50 Hz on a reasonably respectable sine wave – the mains supply. So instrument manufacturers, of both digital and moving coil meters, make use of this so-called average-sensing rms calibrated display for this very reason. However, depart from the 50 Hz sine-wave criteria and you are in trouble; the average shown no longer has any relationship to the rms value.

It is here that thermal conversion and special calculating ics come into their own, but there are two differences between the two techniques. Thermal conversion meters can give electrical isolation between signal and meter. This is very useful if you are measuring 3-phase mains supply between phases or if you are measuring a supply which is floating, and which cannot be grounded.

Also, thermal conversion meters have good crest factor handling properties, whereas ic converters are limited to a factor of 6 or 7 at present.

Crest factor is defined as the ratio of peak value to rms value, any dc component being disregarded, and is best visualised by reference to a practical example, as shown in Fig. 7.



Here, the voltage peaks are 350V but the rms value is small – around 10V. So the crest factor is 350 : 10 = 35.

This sort of waveform is difficult for an ic to follow, but such spikes are so much grist to the mill to thermal converters – they all end up as heat regardless.

RMS FOR SINES

If you take the signwave of Fig. 5 and apply the same technique as used in our dc example, the waveform shown in Fig. 6 is obtained.

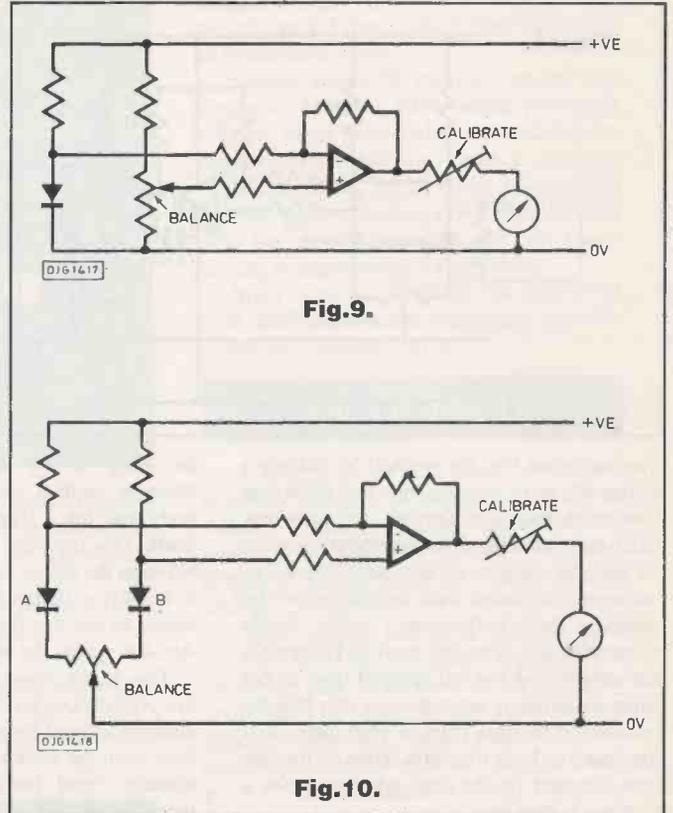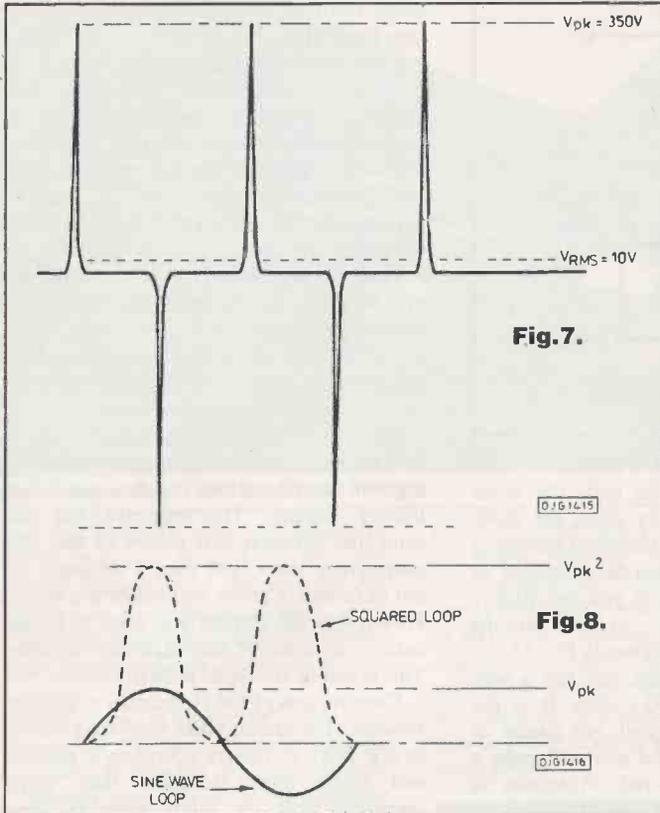Note that squaring the negative part of this cycle results in a positive value. The area under the squared loops can now be found either graphically as before or by calculation.



The mean can be found, the square root taken to get the rms value' but whichever method you use the result will be that $V_{rms} = 0.707 V_{pk}$. The mathematical proof of this well-known result can be found in most textbooks on trigonometry. This formula can only be used on sine-waves and not on other ac waveforms.

When a device such as a motor is said to be rated at 5 amps, this refers to the rms current, not to the average or peak current, and makes no assumption as to the waveform shape. As we have seen from Fig. 1, if the motor was fed from an electronic control a truly complex waveform could be applied to it, but the primary limit would still be the rms rating. This should be borne in mind when using electronic controls. There would of course be other limits, such as the insulation breakdown limit and frequency limit, and these must be remembered as well.

Although voltage has been used in these examples, the same results are true for current measurement, eg $I_{rms} = 0.707 I_{pk}$.

THERMAL-CONVERSION METER

When forward-biased, a silicon diode shows a voltage drop of about 2mV for every 1°C increase in temperature, and if connected to a suitable voltage amplifier it makes a good thermometer. A typical circuit is shown in Fig. 9.

This circuit only measures one temperature quantity and would be fine for measuring ambient temperature, or the temperature of a particular object. For measuring temperature differences independent of ambient

temperature, it is necessary to add a second diode to cancel out changes in ambient temperature, as in Fig. 10.

Diode A can now be attached to the object whose temperature above ambient is required, and diode B can be left to sample ambient temperature. This is the basic circuit for the meters to be described. In the ammeter version, a few turns of relatively thick Nichrome wire are wound round diode A to form a low-resistance heating element, and the current to be measured is passed through it. Any temperature rise is registered by the meter, which can directly calibrated in amps.

The voltmeter version has a large number of turns of thin Nichrome wire wound round diode A to form a high-resistance heating element, and this is the only difference between the two meters, except of course the meter is calibrated directly in volts. Nichrome is the preferred material for the heater element because it has a higher resistivity compared to Constantan or Manganin, and this means fewer turns of wire for a given resistance and thus lower thermal mass, which it is important to keep low.

THERMAL CONSIDERATIONS


As it stands, the instrument would be very insensitive and inaccurate. This is because the heat generated by the input heating coil would be free to dissipate to the surroundings by radiating heat and by convection via the air. Very little heat would

be available to raise the temperature of the diode body by conduction. Also, what little heat was conveyed to the diode would be influenced by the vagaries of random convection and random radiation. For these reasons, the sensor assembly is encased in insulation to stop these heat losses, to reduce their random nature, and to provide a carefully-controlled exit for the heat.

Heat has to have some exit from the insulated sensor, otherwise the sensor would be unable to reach a stable state - temperature would continue to increase. Also, when the input was removed, it would take an inordinate length of time to cool down. The insulation defines the heat exit path, in this design down the diode leads and heater coil leads by conduction.

To make the conduction a consistently reproducible quantity, the leads are terminated in copper heat sinks. The sensitivity of the sensor is determined by how long the conduction path is made. If the leads are long, sensitivity will be increased, and if the leads are short it will decrease. However, increasing the sensitivity also increases the time-constant of the sensor, the time needed to reach a stable temperature. This must be adjusted so that the meter can be read within a reasonable time - say 30 seconds.

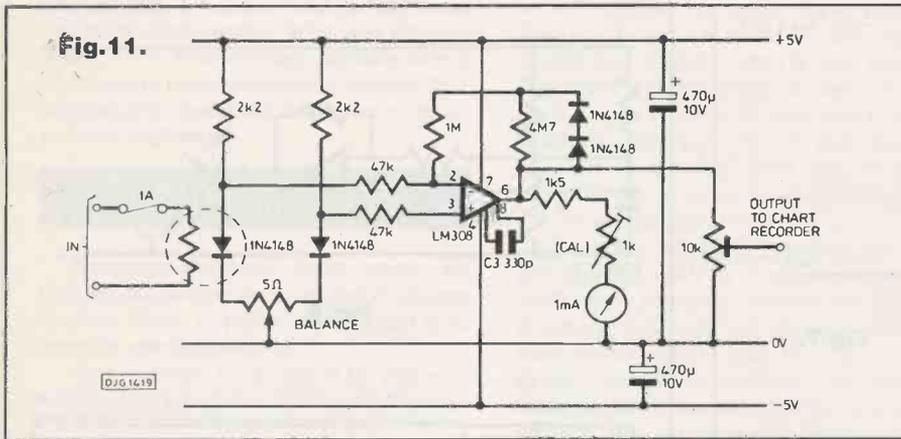Although this is a complex subject, insulating the sensor is easy. Two pieces of polystyrene sandwich the sensor on each side. Polystyrene is ideal for this purpose, in fact this project would be almost impossible to make if it were not for the excellent insulating and mechanical properties of polystyrene. The only small problem is that polystyrene is fairly transparent to radiation.



made from the copper blocks with solder tags fixed to the blocks with a central screw which also acted as the clamping fastener.

Although using copper blocks gave good performance, drilling and soldering was a time consuming process. Later on, I discovered that copper washers clamped onto the diode and heater leads gave just as good a performance but was a much quicker method of doing the same job, and this is the recommended system. Fig. 14 shows the set-up. Whereas the compensating diode was inserted into a drilled hole in the copper block, it must be attached to copper washer systems either with a clip or with an adhesive like Araldite and covered with insulation.

The polystyrene used was a 5mm sheet, as sold for wall insulation, but a piece of ceiling tile will do just as well if it is sawn into thinner sections. The reflective foil was cemented between two pieces of this thin polystyrene sheet, and then a rectangle cut out to fit neatly above and below the sensor. Polystyrene tile cement was used to fix the various sections of this sandwich together. This is readily available from diy stores.


Construction of the electronics is straightforward. The circuit takes very little current (a few mA), so battery operation is possible and much more desirable than mains operation from the safety point of view,

You can prove that for yourself by holding a ceiling tile up to a strong light and observing how much light gets through, and also how much heat radiation. The polystyrene used to encase the sensor is not very thick, so radiation is reflected back into the sensor by coating the polystyrene with bright aluminium foil. The foil used in kitchens is not suitable, but the foil stripped from an old paper capacitor is since it is so thin that the increase in thermal mass is negligible. It is important to keep the mass down so that the time constant (ie the time taken to make a reading) is kept low.

After a period of operation, heat transferred along the diode leads and heater coil leads will warm up the heat-sinks. This could result in drift, so to compensate for this the second diode, diode B, is attached to the heat sinks. When the instrument is cold, diode B, registers the ambient temperature. When the heat sinks slowly warm up, the sensor, which is now insulated from the outside world by the polystyrene, sees the ambient temperature as that of the heat sinks. Diode B now corrects for this apparent increase in ambient temperature.

the body of the diode. Araldite is then liberally applied over the coil, the diode body and for a short way along the diode leads. This provides the electrical insulation between the heater coil and the electronics, so it is vital – particularly if you specifically intend to use this feature – to make sure the Araldite covers the area shown in Fig. 13.

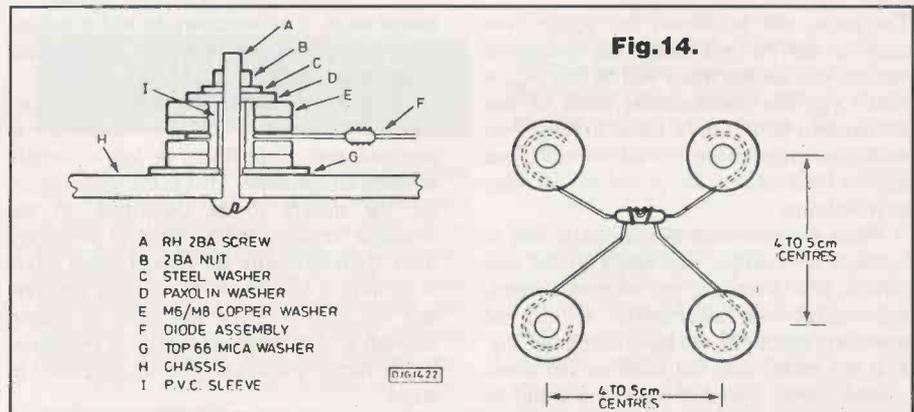This is the basic sensor, and has a very low resistance, around 0.1 ohm. It is not easily damaged by overload, but sooner or later even the most careful user will make a mistake and burn it out. Protection is therefore needed, and a 1 amp 20mm quick-



AMMETER CONSTRUCTION

The full circuit is shown in Fig. 11.

A short piece of bare 30 swg Nichrome wire is wound round a former of slightly less diameter than the body of the 1N4148 diode to be used. A wooden cocktail stick will do. There are only four turns, and these are wound as shown in Fig. 12 in order to render the coil essentially non-inductive. The coil is then slipped off the former and pushed onto

blow fuse will give good defence. Unfortunately this fuse adds 0.1 ohm to the resistance at the input, but this is better than having to remake the sensor. There is no practical alternative to a fuse.

The Nichrome wire is clipped short, leaving about 0.5 cm for attachment of leads. 26 swg copper wire is soldered onto the two Nichrome stubs to make the electrical and thermal conduction leads.


The heat sinks are best made of copper, which has the best thermal conductivity of the commonly available materials, twice as good as aluminium and three times better than brass. I used four square cubes of 1.5 cm side and soldered both the diode leads and heater coil leads into fine holes drilled in the sides. The lengths of the leads from the diode and the heater coil were also about 1.5 cm. Since the meter was enclosed in an aluminium case, the copper heat sinks were clamped to the case base via mica washers and silicone grease in order to increase the thermal capacity. Electrical connections were



especially if you intend to float the meter above ground potential. Also, if you intend the latter it is wiser to use a plastic case instead of a metal one. The heat sinks can still be attached to a metal chassis inside the case to give similar thermal performance.

The reason I used a mains supply was that I intended to run a chart recorder for very long periods, using the ammeter as a signal processing unit, so it had to remain switched on for days on end. If you want use the mains, a suitable circuit is shown in Fig. 15.


As I used a metal case, I made certain of the insulation between input and the case using a 500V insulation tester ("Megger").

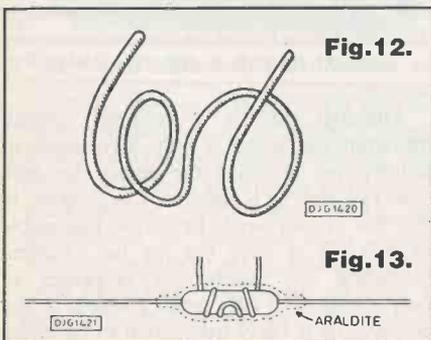You will notice that the feedback path in Fig. 11 is different from that in Figs. 9 and 10, both these circuits being linear-response. The temperature rise in the sensor follows a square-law response, since the power level is defined by I^2R , where I is the current being measured and the R the resistance of the heating coil. Such square-law responses are inconvenient when it comes to practical



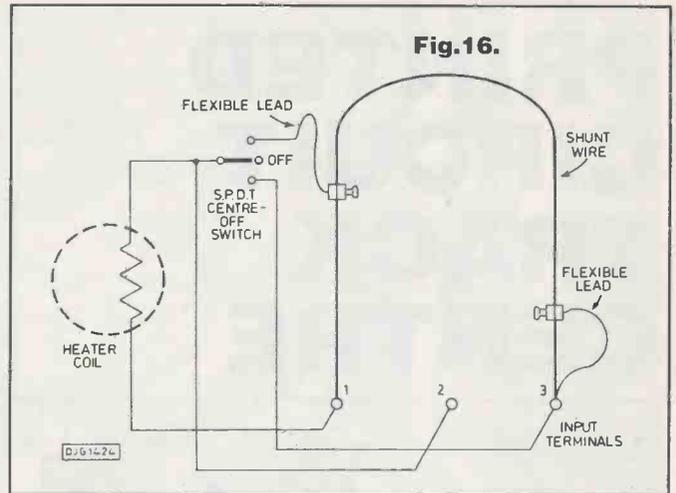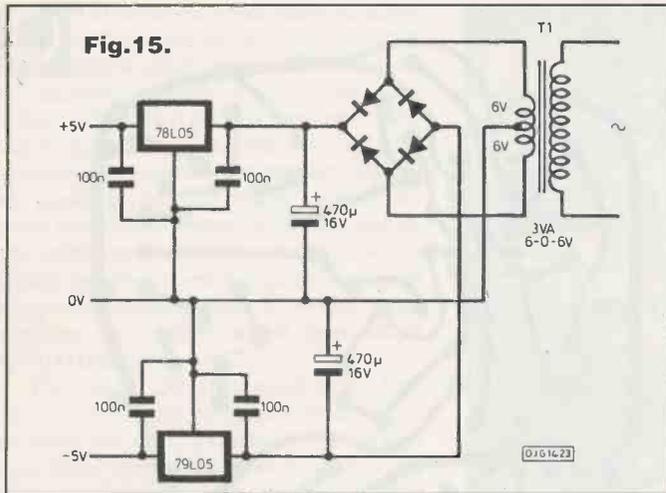

measurement, so the output from Fig. 11 has been modified to overcome this difficulty, by making the op-amp respond in a complementary manner. The two diodes and two resistors in the feedback path achieve a fair degree of linearisation by decreasing the gain of the opamp as the output voltage increases. Note that complete linearisation would need a complex circuit, and that this circuit is the simplest consistent with good results.

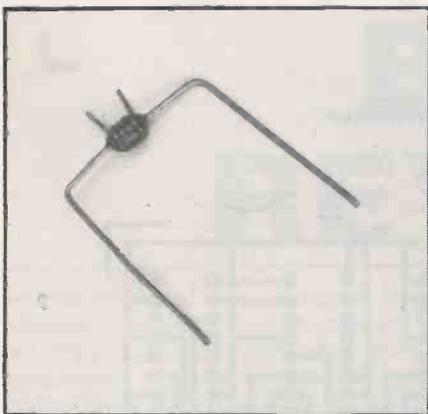

Diode and heater coil assembly after applying araldite

CALIBRATION

Because the scale is not completely linear, as already explained, the existing figures on the 1mA meter must be removed. This is quite easy if you set about it the right way. First, remove the glass/plastic cover and the meter scale. These are usually held by screws, but sometimes clips are used and these may have to be bent back to release these parts. Next, scrape off the figures, but not the scale itself, with either a razor blade or art knife. It is not necessary to scrape off every bit of the numerals, so do not overdo the scraping. Small bits and pieces are readily removed using a hard rubber type eraser. When this is done, the scale plate is returned to the meter, but not the cover. The figures are replaced with Letraset during calibration.

Calibration is achieved by comparison with the dc scales of an accurate ammeter. I



used the dc current scale on a Solartron 7045 dmm for example and this was more than adequate. A variable voltage psu capable of giving at least 1 amp, and a 3.3 ohm 10 watt resistor are needed. The two ammeters and resistor are connected in series and the psu set to show 1A on the accurate meter. The meter under test is then adjusted to fsd with R_{cal} . Make sure the zero is set before you do this.

The fractions of 1A are then set up the same way, and the positions on the scale marked with Letraset. Needless to say, do not touch the zero control while this is done. It is tempting to do this because of the thermal time-constant, but is not necessary.

EXTENDING THE RANGE

A simple shunt circuit is shown in Fig. 16 and this has the advantage of using readily-available components. The switch only has to handle 1 amp and is a spdt type with centre-off position (Electrovalue S 7103 for

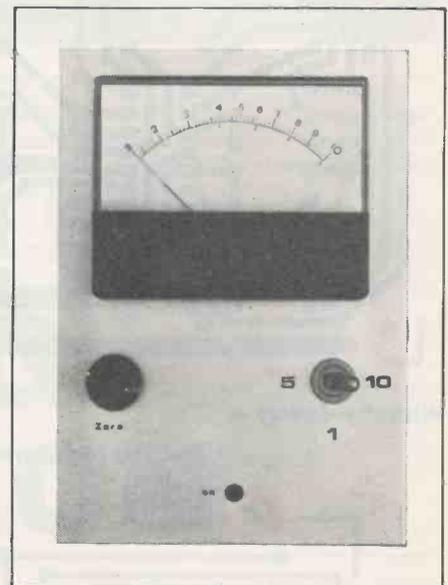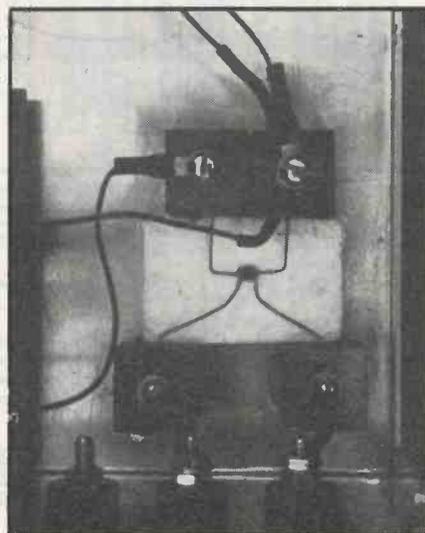Heat sinks, diode sensor and connections, and lower polystyrene layer just prior to adding upper layer. Note that shunt and input fuse have been removed for clarity



The completed instrument. Note the recalibrated scale on the meter


The Sangamo-Weston moving iron meter referred to earlier



example). In the centre-off position the meter reads 1A with input via terminals 1 and 2, that is with the shunt out of circuit. In the two other positions the meter reads 2A or 10A, with the input via terminals 1 and 3. The sliding contact for calibrating the shunt is the metal screw connector taken from a terminal block, and is the sort that has a central tongue contact, rather than a screw acting directly onto the wire.

The wire used for the shunt was a 12 cm length of 20swg Nichrome, but a similar length of 24 swg Constantan could be used instead. The correct length has to be found by experiment, starting with a length longer than is required. Calibration is the same as before, using a psu and dc ammeter.

PRINTED CIRCUIT TRACK CENTRE

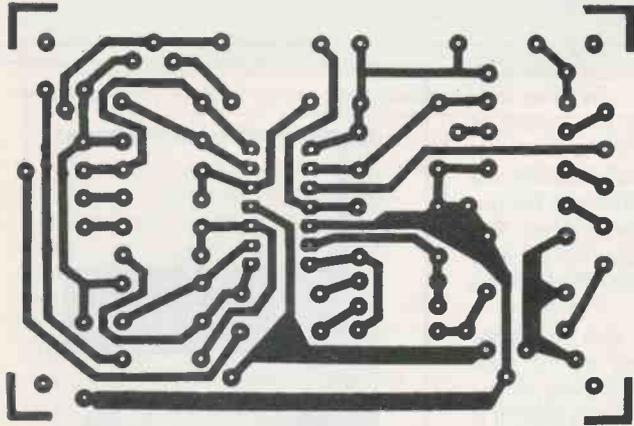


Wheeby-Jeeby ▲

▼ Deluxe Metronome



▲ Solar Heating Controller

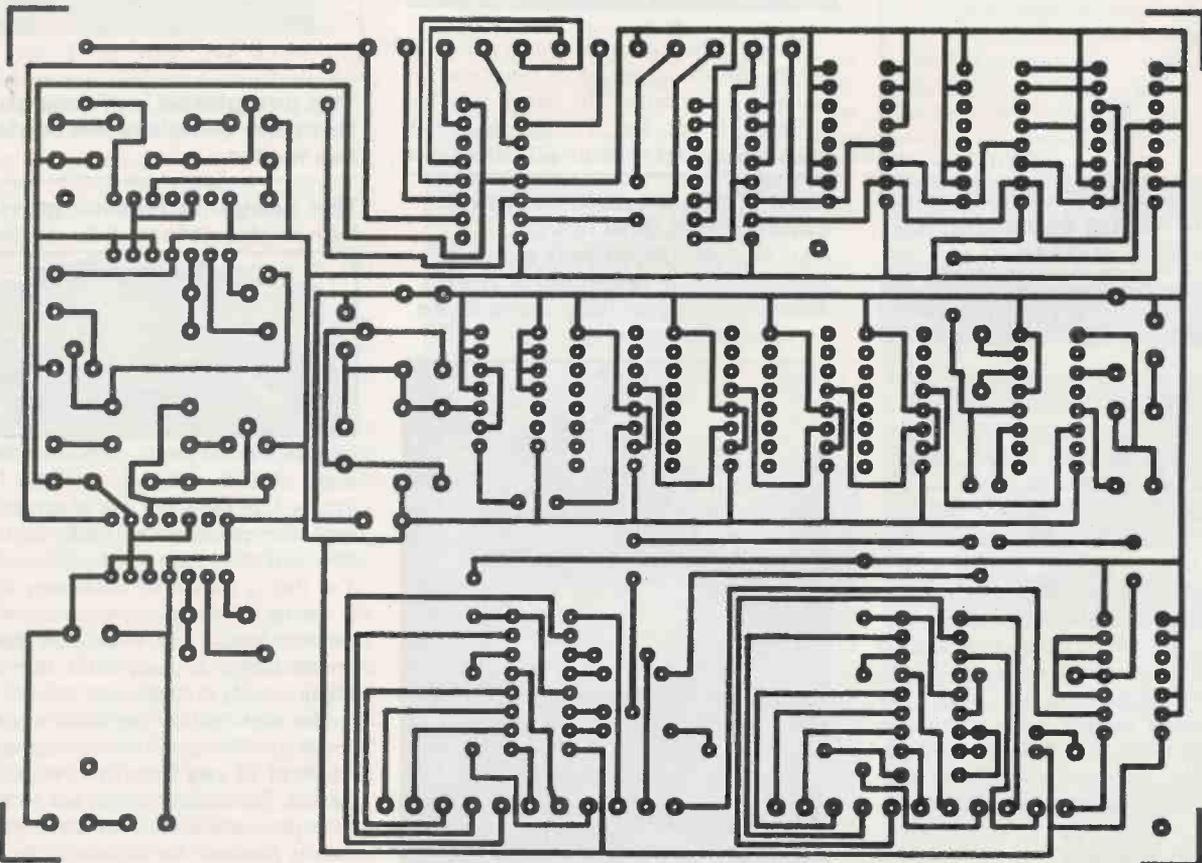

NATIONAL COMPONENT CLUB

SPECIAL OFFERS * SPECIAL OFFERS

SCANNER KIT(T)

A complete, six channel LED chaser kit for less than a fiver! The kit comes complete with all components, including PCB and instructions simple enough for even a complete novice. Works from 6-15vdc.

Only £4

MAINS POWER SUPPLY FOR ABOVE £1

* SPECIAL OFFER PACKS *

100 ASSORTED CAPACITORS £1

30 ASSORTED TRANSISTORS £1

25 ELECTROLYTIC CAPACITORS £1

12 LED's (5mm red or green) £1

5 555 TIMER IC's £1

5 741 OP-AMPS £1

FREE MYSTERY PACK WITH ALL ORDERS OVER £6

Please add £1 P&P, but do not add VAT.
P.O. or cheque to: NATIONAL COMPONENT CLUB, DEPT PE,
BAILEY HILL, CASTLE CARY,
SOMERSET BA7 7AD

We now accept Access - phone (0963) 51171

*** FREE CLUB MEMBERSHIP ***

Just phone above number or write for details

Interak 1 BUILD YOUR OWN COMPUTER



INTERAK can be commenced with the minimum of outlay. Bare boards from £10.95; beg borrow or steal the components, or buy from us - all parts available separately. No special or custom chips (ie PALs, ULAs, ASICs etc) used - no secrets.

Go as fast or as slowly as your funds and enthusiasm permit.

Made for those who must know what goes inside. Full circuit diagrams and descriptions are provided. And honestly, can you really use a computer effectively if you don't know what's inside and nobody will tell you?

Solid engineering construction - something to be proud of. 19" 3U rack mounting, plug in circuit boards and modular construction keeps obsolescence at bay.

Flourishing Independent Users Group, and newsletter. Hundreds of programs on disk at little or no cost from the Users Group.

Program in machine code (Assembler), Basic, "C", Forth, etc Database, Word Processing, Scientific applications.

Cassette tape operation or disk (up to 4 drives, 1 Megabyte 3.5" available from us, but you can add 3", 5.25", 8" if you want). Disk operating system CP/M Plus.

64K RAM. Z80 based at present with potential for expansion to a 16 Megabytes address space and Zilog's latest Z80280 in the future.

Needs no specialised knowledge to construct, and we will happily get you out of a jam if you get into one.

Availability of personal and individual after sales service, impossible to obtain from large companies, who are only after your money.

Security of supply - from Greenbank Electronics, established in 1970.

Greenbank

For more details write or phone us:

Greenbank Electronics, Dept (E6P), 460 New Chester Road,
Rock Ferry, Birkenhead, Merseyside. L42 2AE. Tel: 051-645 3391



CAN YOU ANSWER YES TO ANY OF THESE QUESTIONS: -

- 1) DO YOU PROGRAM YOUR HOME COMPUTER?
- 2) HAVE YOU INTERFACED YOUR HOME COMPUTER WITH A PERIPHERAL?
- 3) ARE YOU INTERESTED IN AMATEUR RADIO?
- 4) ARE YOU FAMILIAR WITH DIGITAL ELECTRONICS?
- 5) ARE YOU DOING A COURSE INVOLVING ELECTRONICS?

If you can answer YES to one or more of these questions, you should consider entering the Computer Servicing Industry.

Micro System Maintenance Ltd is an established national computer service company and prides itself on successfully training individuals to become service engineers. The company has an established Training School in Weston-Super-Mare for the provision of training in both technology and the repair of personal computers and peripherals.

The selected candidates will be provided with a company car linked to an attractive benefits package.

If you wish to know more please feel free to contact MSM at the following address.


MICRO SYSTEM MAINTENANCE LIMITED
15 WESTMEAD INDUSTRIAL ESTATE
WESTLEA
SWINDON SN5 7YS
TEL: (0793) 616888



★ LEARN BY BUILDING ★ ENJOY BY USING ★

PROJECT KITS

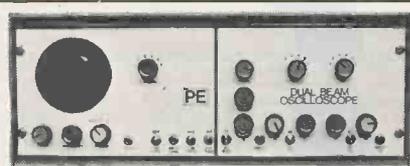★ BE CREATIVE ★ RAISE YOUR SKILLS ★ GET KITTED! ★



DUAL BEAM OSCILLOSCOPE

2Y-amps, 6 ranges, variable level, DC to over 1MHz. 4 modes - Y1, Y2, Y1 & Y2, Y1 & Y2 to X. Time base variable from 0.05Hz to 20KHz. Variable sync level, polarity and source. Separate bright-line, brilliance and focus controls. Independent trace deflection controls. Details in catalogue.

BURGLAR ALARM CONTROLLERS

MULTIZONE CONTROL

SET280 £23.90
Two entry-zones, anti-tamper loop, personal attack, entry-exit timing, timed duration, automatic resetting, latching LED monitors.

SINGLE ZONE CONTROL

SET279 £10.50
With timed duration control and latching LED monitor. Both units can be used with any standard detection devices, such as contact or magnetic switches, pressure pads, tremblers, ultrasonics, infrared etc., and will activate standard bells, strobes or sirens.

COMPUTER KITS

The software listings published with the computer kit projects are for use with C64, PET and BBC computers.

CHIP TESTER SET258F £41.50

Computer controlled logic and chip analyser.

EPROM PROGRAMMER SET277 £26.20

Computer controlled unit for 4K Eproms.

MICRO-CHAT SET276 £69.50

Computer controlled speech synthesiser.

MICRO-SCOPE SET247 £49.50

Turns a computer into an oscilloscope.

MICRO-TUNER SET257 £57.40

Computer controlled, tuning aid and freq counter.

MORSE DECODER SET269 £26.70

Computer controlled morse code-decoder.

MORE KITS IN CATALOGUE
SEND MEDIUM S.A.E. FOR CATALOGUE AND
WITH ALL ENQUIRIES
(OVERSEAS SEND £1.00 TO COVER POSTAGE)

VARIOUS

VOICE SCRAMBLER SET287 £49.50

32 switchable channels to keep your communications confidential.

STORMS! £35.50 each unit

Raw nature under panel control! Wind & Rain SET250W.

Thunder & Lightning SET250T.

DISCO-LIGHTS SET245F £69.50

3 chan sound to light, chasers, auto level.

EVENT COUNTER SET278 £36.60

4-digit display counting for any logic source.

ASTRONOMY



SIDEREAL CLOCK SET295 £49.50

Dual purpose star-time and solar-time digital clock with alarm.

ENVIRONMENT

WEATHER CENTRE

Keep the Met Office in check and monitor the wind speed and direction, rain, temperature, soil moisture and sunny days.

Six detector circuits - KIT 275.1 £18.50

Automatic metered control monitor circuit - KIT 275.2 £41.50

Optional computer control circuit - KIT 275.3 £15.50

ELECTRONIC BAROMETER

SET285 £41.20

Computer controlled unit for monitoring atmospheric pressure.

GEIGER COUNTER SET264 £65.50

A nuclear radiation detector for environmental and geological monitoring. With built in speaker, meter and digital output. This project was demonstrated on BBC TV.

ORDERING

Add 15% VAT. Add P&P - Sets over £50 add £3.00. Others add £2.00. Overseas P&P in catalogue. Text photocopies - Oscilloscope £3.00, Geiger £3.00, Weather £2.00, others £1.00, plus 50p post or large SAE. Insurance 50p per £50. MAIL ORDER, CWO, CHQ, PO, ACCESS VISA. Telephone orders: Mon-Fri, 9am - 6pm. 0689 37821. (Usually answering machine).

WHEEBY-JEEBY SEE CATALOGUE!

PHONOSONICS, DEPT PE95, 8 FINUCANE DRIVE, ORPINGTON, KENT, BR5 4ED.

MAIL ORDER

OUT NOW!

CRICKLEWOOD ELECTRONICS


1989 100 PAGE COMPONENT CATALOGUE PRICE £1

SEND OFF FOR YOUR COPY TODAY...

- WE STOCK AN UNRIVALLED RANGE
- ALL OUR COMPONENTS ARE FIRST CLASS BRANDED ITEMS
- WE OFFER A SAME DAY SERVICE ON ALL STOCK ITEMS
- NO MINIMUM ORDER—IF YOU NEED ONE COMPONENT WE CAN SUPPLY ONE COMPONENT
- WE HAVE ADOPTED A NEW LOWER PRICING POLICY + QUANTITY DISCOUNTS
- FREE VOUCHERS WITH YOUR CATALOGUE—ORDER ONE NOW!...

JUST FILL IN THE COUPON OPPOSITE AND POST IT WITH YOUR £1 PAYMENT TO THE ADDRESS BELOW. YOU WILL RECEIVE NOT ONLY OUR SUPERB 100 PAGE CATALOGUE, BUT ALSO FREE VOUCHERS WHICH YOU CAN USE ON YOUR NEXT COMPONENTS ORDER.

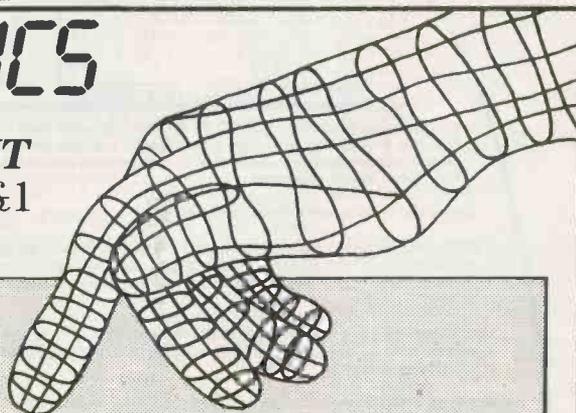CRICKLEWOOD ELECTRONICS LTD 40 CRICKLEWOOD BROADWAY LONDON NW2 3ET TEL: 01-450 0995/452 0161 FAX: 01-208 1441 TELEX: 914977



FREE VOUCHERS!

SEND OFF FOR YOUR CATALOGUE AND VOUCHERS TODAY.

I WOULD LIKE TO RECEIVE..... COPY(COPIES) OF THE 1989 CRICKLEWOOD ELECTRONICS COMPONENT CATALOGUE. I ENCLOSE £..... PLEASE ENCLOSE MY FREE VOUCHERS.

Tape your £1 coin here, or send a cheque or postal order for £1.00 for every catalogue you require.

NAME.....

ADDRESS.....





Each time a new school electronics course is about to start, I receive a flood of letters from pupils who want a simple circuit to build for their project. As a quick guesstimate I reckon that at least half of those students are looking for circuits that make noises or cause lights to flash.

For anyone who is an early starter in the great fun game of electronics, any circuit that falls into these two categories has obvious attractions since, barring acute failure to do things right, it is immediately obvious that the circuit is working. For most circuits of this type, you don't need any special test gear to set them up. You just twiddle any of the preset or panel controls until you can see or hear that things are happening.

So, as this month's theme I'm offering you noise maker - in the form of a siren generator. Well, to be strictly honest, it doesn't on its own directly produce noises, but if you plug it into a separate amplifier module, it most certainly will! Practically any amplifier will do, whether it's the home hifi unit, or one of those low cost modules available from many of PE's advertisers. It

BLOCK BUSTING

Have a look at Fig.1. It's not as complicated as it might appear to the inexperienced eye. There are four main sections to it, each based upon one opamp. The circuit around IC1a is a sine and squarewave generator, IC1b and IC1d are each squarewave generators, and IC1c is the mixer stage.

I'm not going to overload you with technicalities on the precise theory of how things work, but briefly point out a few essential facts that should help you to modify things if you want to.

SINE TIME

With S1 closed, the circuit around IC1a is in the sinewave mode, or rather, it produces a waveform that can be loosely termed as a sinewave. It actually requires a somewhat more complex circuit to produce a true sinewave, though for our purposes here, the shape is good enough to deserve the term.

The rate of oscillation is determined by the values of C1 and C2, and the twin resistances of VR1a and VR1b, plus the series resistances of R2 and R5. The frequency will also be affected by the action of R3 and R4, and the two back to back diodes D1 and D2. It's really only the capacitors and VR1 that need concern you.

Turning VR1 for maximum resistance across its twin tracks will produce the lowest frequency signal. Minimum resistance will, as expected, produce the highest frequency. VR1 does not need to be a log pot, it could equally well be a linear one - indeed for interest, you might care to try both log and lin and discover how these types affect the rate at which the frequency responds to pot rotation position. You could also use a pot value of less than 1M - this would reduce the overall frequency range.

Should you want to completely change the range of oscillation controlled by VR1, C1 and C2 may be changed for different values. They should, though, have roughly identical values to each other. Increasing their values will produce a lower frequency range, and vice versa. With S1 open, C1 is taken out of circuit and the oscillator

WHEEBY JEEBY SIRENS

will need a speaker of course! Alternatively, the unit can be plugged directly into headphones, or into a simple piezo electric audible warning device. You could even plug it into a cassette recorder and tape the sounds.

As well as having the pleasure of building the circuit, you will also discover two ways in which a circuit can be made to oscillate, and how a simple mixer can be made. With only minor modifications, any of these circuit blocks can be extracted and used for other purposes.

BY JOHN BECKER

**Let the sirens
lure you to
plug in your
soldering iron
again!**


produces a roughly square-shaped waveform.


FIELDING FETS

Ignoring VR2 and the two transistors for the moment, the circuits around IC1b and IC1d form virtually identical oscillators. The only difference is that the capacitor values are dissimilar. In each case it is the capacitor value that sets the basic frequency range; C9 is smaller than C4 so the oscillator around IC1d has a slightly higher frequency range than that of IC1b. As with the oscillator around IC1a, the frequency can be varied by altering the value of the resistance of a potentiometer, in this case, VR3 and VR4 respectively. The pot values are not critical, and may be increased or decreased to suit your own choice. They may also be either log or lin.

TWIN FREQS

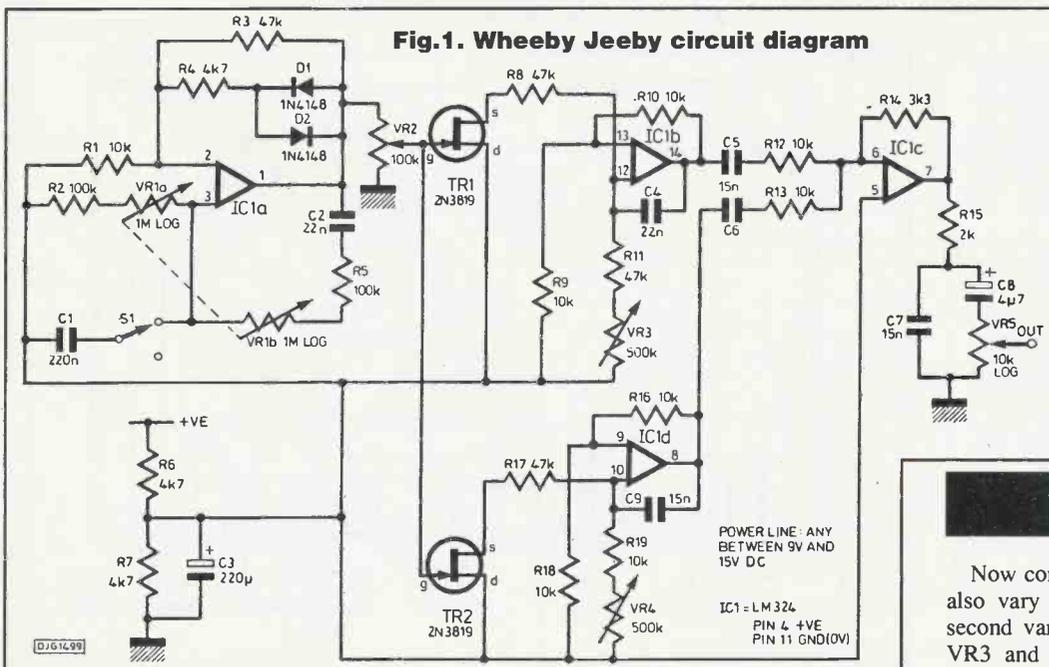Now comes a slightly clever bit! We can also vary the frequencies by means of a second variable resistance in parallel with VR3 and VR4. In this instance we take



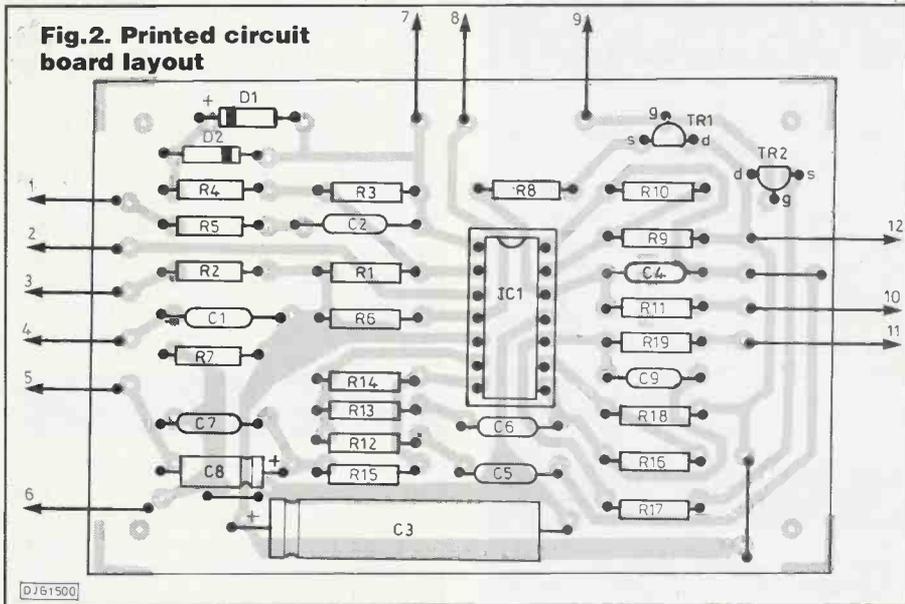

signal is then taken via VR5, the volume control, to any amplifier as mentioned above. The purpose of R15 and C7 is to slightly smooth the corners off the square waveform to make it a little less harsh to the ear. They may be omitted if preferred, and VR5 taken directly to the output of IC1c.

What you will hear is two sirens running at different frequencies which are independently variable from the panel, in terms of rate, tone and depth.

If you think of using the mixer on its own for other purposes, there are couple of things you should note. First, in the application here I have restricted the bass end of the frequency response by use of a smallish value for C5 and C6. For a better bass response their values should be increased; 100n will allow more bass through, and 1µF will allow even more. If electrolytic capacitors are used, their positive ends should face R12 and R13 respectively. Secondly, the signal amplitude across IC1c is determined by the ratio of R12 to R14. Here it is set for a reduction to about one third. Making R14 33k would give an increase of about times three.

advantage of one of the characteristics of a field effect transistor (fet), that it can be used as a variable resistance. That resistance will vary depending on the voltage present at its gate input. By changing the voltage TR1, for example, will

behave in a similar fashion to VR3 being varied, in other words TR1 can control the oscillation frequency. By connecting the fet gate to the first oscillator, the fet's effective resistance will change in sympathy with the oscillator's frequency output. Consequently, the frequency produced by IC1b will also vary in sympathy with the control frequency.

To give even more flexibility, VR2 has been included between the control oscillator and the fets to allow panel variation of the depth of modulation control. The net result is that the oscillators around IC1b and IC1d will produce a frequency that sweeps up and down within the range set by VR2, VR3 (or VR4) and at a rate set by VR1.

BOARD LODGING

I've been exceptionally kind to you this month - I've shown a pcb instead of a stripboard layout, and a suggestion on how you might wire up the circuit in a box. If you prefer to build the circuit on stripboard you should find the pcb layout very easy to follow and reinterpret to suit the different construction method. If you have the stripboard and pcb layout side by side horizontally, the component positions can be practically identical, cutting the strip tracks as necessary.

I hope to have another interesting simple project for you next month.

PE

COMPONENTS

RESISTORS

R1, R9, R10, R12,	
R13, R16, R18	10k (7 off)
R2, R5	100k (2 off)
R3, R8, R11,	
R17, R19	47k (5 off)
R4, R6, R7	4k7 (3 off)
R14	3k3
R15	2k2
All resistors 0.25W 5% carbon film	

CAPACITORS

C1, C2	220n polyester (2 off)
C3	220µF 25V electrolytic
C4	22n polyester
C5-C9	15n polyester (4 off)
C8	4.7µF 16V electrolytic

SEMICONDUCTORS

D1, D2	1N4148 (2 off)
TR1, TR2	2N3819 (2 off)
IC1	324

POTENTIOMETERS

VR1	1M log dual rotary
VR2	100k lin rotary
VR3, VR4	500k lin rotary (2 off)
VR5	10k log rotary


MISCELLANEOUS

PP3 battery and clip, pcb supports (4 off), 14-pin ic socket, mono jack socket, spst switches (2 off - S1 and for battery on-off), knobs (5 off), Phonosonics pcb number 151A, box and wire to suit.

MUTUAL MIXING

The outputs from IC1b and IC1d are mixed together at IC1c. The composite

Fig. 3. Suggested box layout

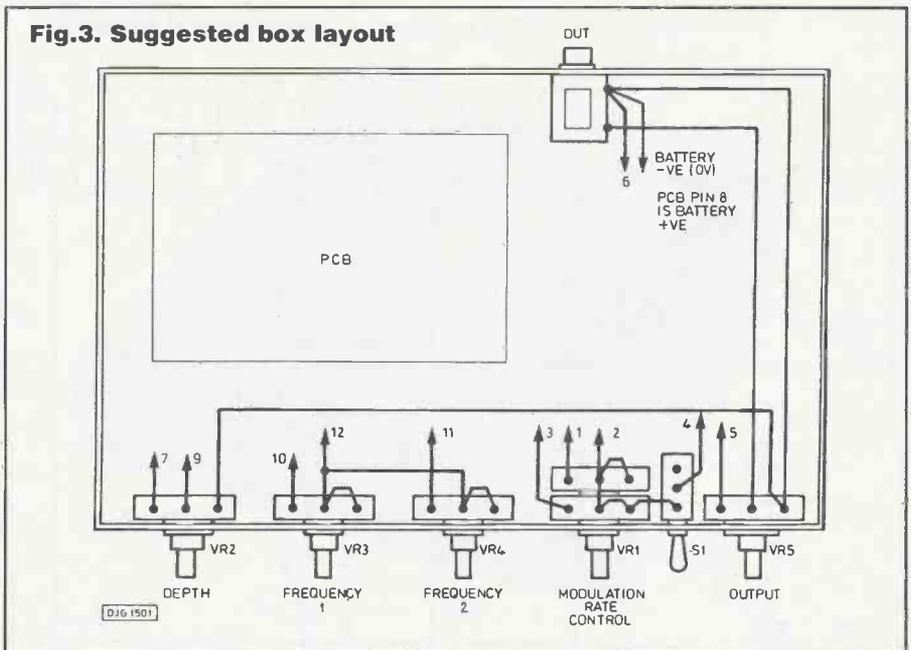



Happy Memories

4116	150ns Only pulls	1.00	2716	450ns 5 volt	3.20
4164			2532	450ns Only pulls	3.50
41256	100/120/150ns	Call	2732	450ns	3.90
41464			2764	250ns	2.85
41000			27128	250ns	4.90
6116	150ns Low power	3.50	27256	250ns	3.95
6264	150ns Low power	6.95	27C256	250ns	4.25
62256	120ns Low power	13.65	27512	250ns	7.95
2114	200ns Low power	1.75	27C512	250ns	8.95

Second-hand (Pulled) chips available for many of the above devices, 'phone for availability and price. Quantity prices on request. Data free on memories purchased. Other devices stocked, full list available.

Low profile IC sockets: Pins	8	14	16	18	20	24	28	40
Pence	5	9	10	11	12	15	17	24

We always have a large quantity of surplus computer equipment for sale; printers, disk-drives, add-on boards, monitors etc: Please ask for our surplus equipment list or call with your requirements as stocks are constantly changing.

Please add 50p post & packing to orders under £15 and VAT to total. Access orders by 'phone or mail welcome. Non-Military Government & Educational orders welcome for minimum invoice value of £15 net.

Happy Memories (PE), FREEPOST,
Kington, Herefordshire. HR5 3BR.
Tel: (054 422) 618 Sales, 628 Fax


(No stamp needed unless first-class required)

Need an extra pair of hands?

It's often the case that conventional methods just won't do. Fortunately there is now an alternative with the

MULTI-PURPOSE JIG

It will hold a circuit board steady for assembly and wiring—
It can hold things while glue sets—
It can hold models for painting and repair—
All its interchangeable heads rotate through 360 degrees so you can position your workpiece to best advantage—no need to take it out to turn it over either—just rotate it to where you want it.
Precision spring loaded head for holding pressures of up to 5.5lbs.

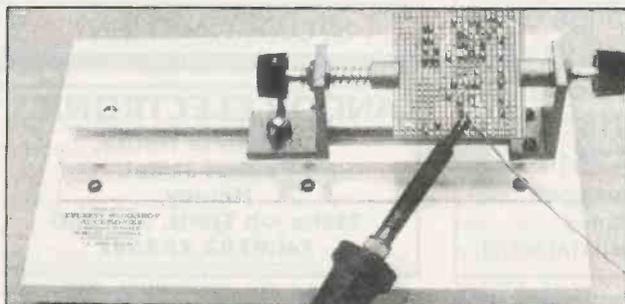

Each jig is hand built for a lifetime of use.

Supplied with circuit board assembly head, 12.5mm rubber faced heads and static discharge lead. Other heads and accessories available.

Standard jig takes items up to 310 x 145mm **£19.50**
Mini jig takes items up to 148 x 85mm **£16.50**

inc. VAT and carriage

EVERETT WORKSHOP ACCESSORIES
5 Railway Terrace, Henllan, Llandyssul,
Dyfed SA44 5TH Tel: 0559 371226



THREE SIMPLE CONSTRUCTION KITS

Especially aimed for the beginner. Have fun with your project even after you have built it and also learn a little from building it. These kits include high quality solder resist printed circuit boards, all electronic components (including speaker where used) and full construction instructions with circuit description.

- SK1 DOOR CHIME - plays a tune when activated by a pushbutton £3.90
 - SK2 WHISTLE SWITCH - switches a relay on and off in response to whistle command £3.90
 - SK3 SOUND GENERATOR - produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun £3.90
- SPECIAL OFFERS FOR SCHOOL AND TRAINING CENTRES** - Contact Sales Office for discounts and samples.

SOLID STATE RELAY BARGAIN

- ZERO VOLTAGE SWITCHING:- No radio interference problems.
- 2.5KV INPUT to OUTPUT ISOLATION:- No risk of damage to your computer or driver circuits
- 4 KV TERMINALS TO HEAT-SINK ISOLATION:- Simply bolt onto a heatsink.
- 3V to 32V INPUT VOLTAGE:- easily interfaced to TTL or CMOS LOGIC.



- 24V to 240V rms LOAD VOLTAGE:- allowing mains loads to be switched.
- BUILT IN SNUBBER NETWORK:- Enabling switching of inductive loads.
- 10A MAXIMUM CURRENT:- 4A with no heatsink fitted at 40°C.

CD240/10 **£2.25**

ELECTRONIC GUARD DOG KIT




One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the bite! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would-be intruder think you have a guard dog and try his luck elsewhere. The kit is supplied complete with high quality PCB, mains transformer, all components and instructions. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect. Don't delay, fit one before you go on holiday and let our dog help you guard your home.

XK125 Complete kit of parts £24.00

POWER STROBE KIT

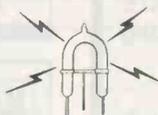Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz, this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator.



Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality pcb, components, connectors, 5Ws strobe tube and full assembly instructions. Supply: 240V ac. Size: 75x50x45.

XK124 Stroboscope Kit £13.75

VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits.

- Supply: 240V AC or 15-24V DC at 10mA.
- Size (excluding transformer) 9 x 4 x 2 cms.
- The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available MK9 (4-way) and MK10 (16-way), depending on the number of outputs to be used.
- MK12 IR Receiver (incl. transformer) **£16.30**
- MK18 Transmitter **£7.50**
- MK9 4-Way Keyboard **£2.20**
- MK10 16-Way Keyboard **£6.55**
- 601 133 Box for Transmitter **£2.60**

SUPER-SENSITIVE FM MICROBU



Highly sensitive FM transmitter measuring only 45 x 25 x 15mm, including the built-in microphone. Frequency 88-100MHz enabling reception on a standard domestic FM radio. Range approximately 300m depending on terrain. Powered by 9V PP3 (7mA). Its small size and highly sensitive electret microphone makes it ideal for surveillance, baby alarm, etc.

INTRODUCTORY PRICE £5.50

MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at present times over a 7-day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box 18 time settings.

- CT6000K **£47.20**
- XK114 Relay kit for CT6000 includes PCB connectors and one relay. Will accept up to 4 relays 3A/240V c/o contacts **£4.30**
- 701 115 Additional relays **£1.80**

DISCO LIGHTING KITS

- DL1000K This value-for-money 4-way chaser features by-directional sequence and dimming. 1kW per channel **£19.25**
- DL21000K - A lower cost uni-directional version of the above. Zero switching to reduce interference **£10.80**
- DLA/1 Optional opto input allowing audio 'beat/light response 77p
- DL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. **£15.60**

The DL8000K is a 3-way sequencer kit with built in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES 80 different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300W output per channel. And the best thing about it is the price: **ONLY £31.50.**

GIANT SOLAR CELLS

NOW IN STOCK these giant size solar panels 12 x 12in will deliver 12 volts 200mA in bright sunlight and 11.5 volts 60mA on a typical British summer day (dull and overcast). HUNDREDS OF USES in the car or caravan, e.g. Charging NiCads, powering low voltage circuits where mains or battery supplies are inconvenient or coupled to a lead acid battery and a simple inverter you could build yourself a self contained mains supply for low power appliances. Stock No. 303 145. **£14.50 (plus £1.75 for p&g on total order)**

TK
13 BOSTON RD.
LONDON W7 3SJ
Tel: 01 567 8910

ORDERING INFORMATION:
ALL PRICES EXCLUDE VAT

FREE P&P on orders over £50 (UK only), otherwise add £1 + VAT. Overseas P&P: Europe £3.50. Elsewhere £10. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002. LOCAL AUTHORITY AND EXPORT ORDERS WELCOME. GOODS BY RETURN SUBJECT TO AVAILABILITY

SEND 9" x 6" SAE & 50p FOR CATALOGUE OR CALL AT SHOP Mon-Fri 9-5 pm Saturday 10-4 pm



PRACTICAL ELECTRONICS CLASSIFIED

Reach thousands of serious electronic and computer enthusiasts. Advertise in PE Classified pages: Rates 20p per word or £8.50 per single column cm (plus VAT). All classified advertisements must be pre-paid. Send your copy with the remittance (payable to Intra Press or payment by Visa or Access accepted) to: Practical Electronics, Intra House, 193 Uxbridge Road, London W12 9RA. Tel: 01-743 8888. Fax: 01-743-3062

LET PE WORK FOR YOU!

EDUCATION

FULL-TIME TRAINING COURSES

**2 YEAR
BTEC NATIONAL DIPLOMA**
Electronics and
Communications
Engineering

(TV, Computers, Programming, IT)

**1 YEAR
BTEC NATIONAL CERTIFICATE**
1. Electronic Equipment Servicing
(TV, Video, CCTV)
2. Computing Technology
(Microprocessors, DataComms, Interfacing)
3. Information Technology
(Telecomms, Satellite TV, Networks)
4. Software Engineering
(Assembler, BASIC, Pascal, CAD/CAM)

★ Those eligible can apply for E.T. grant support ★

★ An equal opportunities programme ★

COURSES COMMENCE
Monday 18th Sept. 1989

LONDON ELECTRONICS COLLEGE

Dep: AA, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721

Start training now for the following courses.

- Telecomms Tech C&G 271
- Radio Amateur Licence C&G
- Microprocessor
- Introduction to Television

Send for our brochure - without obligation or telephone us on 06267 79398 (Ref: PE5/89)
Name.....

.....

Radio & Telecommunications
Correspondence School,
12 Moor View Drive, Teignmouth,
Devon TQ14 9UN

RETAILERS

BATH

L.F. HANNEY

77 Lower Bristol Road, Bath,
Avon.
Tel: 0225-24811

Your electronics component specialist for
AVON, WILTS. & SOMERSET
Open every day, except on Thursday

BURTON -ON-TRENT

MAGENTA ELECTRONICS Ltd

Shop now open - callers
welcome!

135 Hunter Street,
Burton-on Trent,
Staffs. DE14 2ST

EDINBURGH

OMNI ELECTRONICS

stock a wide range of
electronic components at
174 Dalkeith Road
Edinburgh EH16 5DX
Tel: 031 667 2611

Open Mon-Fri 9am-6pm
Sat. 9am-5am
Send 2x19 stamps for NEW CATALOGUE!



Help PE Readers!

Put projects into practice.
Project your component image
here!

Phone PE on 01-743-8888

MANCHESTER

DEANSGATE ELECTRONICS

We stock a large range of electronic components, test equipment, telephone accessories, computer accessories, microphones, speakers, disc lighting, mixers, meters, stylus, so call in and have a look around.

263 Deansgate, Manchester
Telephone: 061-834 1185

SOUTHAMPTON



**BIG STOCK
- KEEN PRICES!**

See our display advertisement in this magazine!

SOUTHSEA

ELECTRONIC COMPONENTS

EVERYTHING FOR YOUR NEXT PROJECT
THE BIGGEST DISPLAY IN THE SOUTH
IS AT

FRASER ELECTRONICS

42 ELM GROVE ★ SOUTHSEA ★ HANTS
Telephone: 0705-815584

Barclaycard

Access

STOKE-ON-TRENT

ANDOR ELECTRONICS

11 Victoria House,
Paxton Street,
Hanley,
Stoke-on Trent, ST1 3SD
Tel: 0782 283642

SURREY

PLS

16 Central Road
Worcester Park
Surrey KT4 8HZ
Tel: 01-330 6540
Programmable device specialists.
(PAL's PROM's, PLD's etc). Many other
components in stock

Resistors 1/4 W 5% carbon (E12) 1p metal film 1% (E24) 3p
 Resistor Pack 85 different E12 values + zero ohm link total contents
 1000 resistors £8.95
 LEDs red/green 3/5mm 6p each. Yellow 11p
 Cable ties 75mm 1p each £5.95/1,000 £49.50 per 10,000
 Stepping motor 4 phase 12v 7.5 step 50 ohms £8.95
 SAA1027 stepping motor driver chip £3.95
 Miniature FM transmitter Kit 100-108 Mhz high quality sound Ideal for
 cordless microphones or guitars etc £7.94

Special offers
 Computer Grade Capacitors with screw terminals
 5800uf 60v £4.00 4700uf 63v £1.50
 3800uf 20v £1.95 8700uf 10v £1.50
 7 segment Common anode led display 12mm £0.45
 LM2931ATS.0 Low drop out 5V regulator T0220 package £0.65
 BS250 P channel MOSFET £0.45
 BC559 transistor T092 PNP £3.95 per 100
 74LS05 hex inverter £10.00 per 100
 AM27S02DC memory £1.50
 Stereo LW/MW/FM Tuner pre-amp assembly complete with
 volume/tone controls and tuning scale
 Brand new in makers carton £5.95, faulty £1.95
 Circuit diagram description and setting up procedure for tuner
 assembly described above £0.50
 Motor start capacitors 1.5uf 440vac £1.95
 40 of 370vac £5.95 4uf 250vac + 100uf £0.55
 LNE mains suppressor 2x5mf + 100uf £0.55
 5 digit 6V electromagnetic counter £1.95
 oval 8 ohm speakers 136x70mm £0.60
 Hour counter (used) 7 digit mains 250V 50Hz £0.95
 LCD display 16 digit 7x5 dots dot matrix £2.50
 Query keyboard 58 key uncased good quality switches £5.00
 CMOS TTL 74HC 74F Linear transistors kits capacitors
 resistors tools etc always in stock
 Please add 75p P&P per order VAT included
JPG Electronics 276 Chatsworth Road, Chesterfield S40 2BH
 Access orders (0246) 211202. Callers welcome

**THE C.R.
 SUPPLY**

copy with
Gilfillan


Cooke International

GOOD USED TEST EQUIPMENT ALWAYS AVAILABLE & WANTED
 SCOPES ANALYSERS SIG GENS BRIDGES POWER METERS
 DC - MICROWAVE EQUIPMENT

Aimec 304 HF Oscillator 60kHz-100MHz 104v output (1) £200
 Dana Model 4500 5 1/2 digit Auto OMM (2) £65
 Dana Model 8110, Auto Time & Frequency 8 digit counter, 0-20MHz £250
 Fluke 871A Differential voltmeter (1) £170
 HP 214A Pulse Generator High power 100vohm/50 Ohms (1) £185
 HP 431B RF Power meter with lead and mount (6) £260
 HP 606A HF Signal generator 50kHz - 66 MHz 3v output (1) £95
 HP 6080 VHF Signal generator 10 - 420 MHz with Mod. (1) £150
 HP1740A 100MHz General purpose oscilloscope with delay (1) £750
 HP3300A Function generator 0.01-100kHz all modes (1) £150
 HP 3406A Broad band RF sampling voltmeter (1) £265
 Marconi TF 1313A Universal LOR Bridge (1) £250
 Philips PM3370 OC-60MHz dual trace scope with delay (1) £175
 Tektronix 611 storage display (1) £200
 Tektronix 465 DC-100 Mhz dual trace with delay (3) £750

WIDE RANGE OF ITEMS AVAILABLE - SEND FOR LISTS - COMPETITIVE
 PRICES & BARGAINS TO CALLERS! BULK & TRADE TERMS
 HOURS OF BUSINESS: MON-FRI 9.30 - 5.00
 UNIT 4 FORDINGBRIDGE SITE, MAIN ROAD, BARNHAM,
 BOGNOR REGIS, WEST SUSSEX PO22 0EB
 Tel: 0243 545111 Fax: 0243 542457
 ★ WHILE STOCKS LAST ★

**Phone
 Sarah Holtham**

with your
 classified ad!

01-743 8888

We now accept payment by
 Access and Visa

**You can also use PE
 Fax Line:
 01-743-3062**

A & G ELECTRONICS LTD

If you are buying Electronics Components
 elsewhere you are almost certainly paying
 too much! Write to us for a free 1989
 catalogue and start saving money. Please
 send two 19p stamps towards postage.
P.O. Box 443 London E14 6JU Tel: 01-519-6149

**UNUSED AND SURPLUS TO
 REQUIREMENTS**

10 Relays Misc. voltages and types £10.00 inc. VAT
 30 Potentiometers & Trimmers misc. £6.00 inc. VAT
 10 3/4 Rectangular cermet trimmers PC mount - mixed std
 value £3.00 inc. VAT
 10 Mixed miniature pushbutton switches £2.50 inc. VAT
 20 Mixed 1/2 watt W/W Resistors with variable TAP £4.00 inc. VAT
 10 Miniature Panel Neoms £2.00 inc. Vat
 Postage and packing £1.30 per pack.
**BLORE-BARTON LTD Raedham
 House, Burnham Bucks SL1 8AG**

CAMBRIDGE COMPUTER SCIENCE LTD

5 1/4 inch Disk Drives, 80 Track DSDD £34.00 each
 3" Disk Drives, 40Tk, SSDD £28.00 each
 5.25" Disks, DSDD, 48tpi boxed in 10s £3.00/box £27.00(10s)
 Dual Disk Drive Power Supply £20.00 each
 Lead to connect one drive to psu £2.00 each
 Single Data lead (BBC Micro to Disk Drives) £2.00 each
 Dual Data lead (BBC Micro to 2 Disk Drives) £4.00 each
 Dual leads (BBC Micro to 2 Disk Drives) £2.00 each
 20 pin dil low profile IC sockets £0.50 (ten) - £5.00 (100)
 QWERTY keyboard with Cursor keys,
 function keys & numeric pad £6.00 each
 Hitachi 640 * 200 dot matrix LCD display £40.00 each
 Toroidal transformer, mains in, 12V @4A,
 12V @0.4A, 12-0-12 @0.1A, 12-0-12 @0.2A
 & 9-09 @0.2A £4.00 each - £6.00 for 2 - £8.00 for 3
 All items new and boxed. Add 15% VAT to all prices. Prices
 include postage. Add 50p to orders below £5.00.
Dept PE, 374 Milton Road, Cambridge, CB4 1SU
Tel: 0223 327602

TURN YOUR SURPLUS

ICS transistors etc into cash, immediate
 settlement. WE welcome the opportunity to
 quote for complete factory clearance.
 Contact:
COLES-HARDING & CO.,
 103 South Brink, Wisbech, Cambs.
 ESTABLISHED 15 YEARS
 Tel: 0945 584188 - Fax: 0945 588844

☆☆☆ RESISTOR PACKS ☆☆☆

1/4W 5% CARBON FILM
 E12 RANGE 10R to 10M
 1p each + 25p P&P

10 OF EACH VALUE
 Total 730 resistors
 £6.95

RMOS P.O. Box 3
 USK GWENT NP5 2YF

**SURPLUS/REDUNDANT ELECTRONICS
 COMPONENTS WANTED**

ICs - Tuners - Transistors - Valves - Diodes etc - any
 quantity considered - immediate payment.
ADM ELECTRONICS SUPPLIES
 Tel 0827 873311 Fax: 0827 874835

★★★★ KITS ★★★★★

- Miniature VHF/FM transmitter £3.75 ●
 - Telephone transmitter (no batteries needed) £6.99 ●
 - Automatic telephone monitor to start/stop your cassette when
 telephone is used, recording all conversations £8.99 ●
 - Voice operated switch £9.99 ●
 - AF/RF signal injector tracer £5.99 ●
 - Bleeper VHF/FM transmitter £9.99 ●
 - High power telephone transmitter £7.99 ●
 - Tricolour car battery monitor £4.25 ● Rogerbleep £4.99 ●
 - Receiver preamp, 15db gain £7.99 ●
 - Drill speed controller, complete with cable,
 socket, box etc. £9.99 ●
- SAE LIST, P&P Free , Eire and overseas £2
 Access orders accepted by telephone.
 Cheque / P.O. to:
**A.C. Electronics, 99 Greenheath,
 Hednesford, Staffs.**

★ Series X Mixer Kits

- ★ up to 1,000 inputs
- ★ 60+ 100 mm faders, pots,
 panels and audio switches
- ★ 6 auxiliaries
- ★ versions for recording PA,
 radio, disco
- ★ circuit diagrams
- ★ From £9.92



Send 19p for catalogue to: **K. Tek, P.O. Box 172a,
 Surbiton, Surrey KT6 6HN. Tel: 01-399-3990**

J. N. BULL ELECTRICAL

Please note our correct telephone
 numbers: **0273 734648 or 203500**
 For other details see our display
 advertisement!

Special offer while stocks last - 6264
 LP 15 Static Ram £5.95 all inclusive.
 Spiretroniks, 2 Woodclose,
 Chesterfield, Derbyshire S42 6SD
 Tel: 0246 2788280

FOR SALE

Thurlby LA 160A Logic Analyser &
 3 Pods never used £350.00 & VAT.
 Ready for collection.
 Phone : 021-434 3434 Ext.: 225
 (contact Andrew Harvey)
PRODUCTS FOR OFFICES Ltd.

CLASSIFIEDS

SERVICES

PCB Design Program for Amstrad CPC664/6128 and Amstrad PCW 8256/8512

Design and manufacture your own PCB's using this powerful yet easy to use utility. Double or single sided boards - 8 pads styles - 5 track widths - plus many other features for only £29.99 incl. Details from: CADsoft Systems, 18 Ley Crescent, Astley Manchester M29 7BD

MAKE YOUR OWN PCB'S

Just about everything from polishing blocks to plated through hole equipment. Very keen prices - discount on quantity.

S.A.E. for complete price list or telephone:

Ward Electronics,
27 North Street, Redruth, Cornwall TR15 1HU
Tel: 0209 211050

Printed Circuit Board Design, Using Computer Aided Design Photoplotting, Phototype PCB's *Special reduction for new clients!*

Call Neville Sanderson on: 0532-870253
N.C.A. DESIGNS

WORKSHOP SERVICE MANUALS

Video Recorders - £12.50

Most Colour TV, Audio, Test, Vintage, Amateur etc. £6.00

Please state Make/Model/Type with order.

FREE Catalogue Unique Repair and Data Guides with all orders or LSAE for your copy.

MAURITON ELECTRONICS LTD (PE),
8 Cherry Tree Road, Chinor, Oxfordshire OX9 4QY
Tel: (0844) 51694

LOW COST ELECTRONIC DESIGN SERVICE

No project too big or too small. Other services available. For full details send S.A.E. to: Spiretroniks, 2 Woodclose, Chesterfield, Derbyshire, S42 6SD
Tel: 0246 278280

Let Practical Electronics work for you!
Phone our Advertisement Dept. on: **01-743-8888**

For Electronic Design and PCB Manufacture call

PROTO DESIGN

Unit 8, Ilford Trading Estate
Paycocke Road Basildon
Essex SS14 4DR
Tel: 0268 289923

IS YOUR
CLASSIFIED AD
A TIGHT SQUEEZE?

**STRETCH
OUT**

in display pages of PE!
Phone Sarah Holtham
on
01-743-8888 for details!

TECHNICAL INFO SERVICES (PE)
76 Church St, Larkhall, Lanarkshire ML9 1HE
Phone 0688 884585 Mon-Fri, 9-5
any other time 0598 883334 FOR FAST QUOTES
WORLD'S LARGEST COLLECTION SERVICE MANUALS Most unobtainable elsewhere. Prices range from only £4.50 + large s.a.e. any quotation, no obligation to buy.
WORLD'S SOLE Suppliers of TV & Video Repair manuals, etc. from TV TECHNICAL, Thorn etc. Every published service sheet in stock, supplied full size, not bits & pieces. CTV's or any combination £3.50 plus Lsae, any other single item £2.50 plus Lsae. Complete Circuit Sets for most Videorecorders only #7 set (no serv shts made). LSAE for QUOTATIONS plus GIANT CATALOGUE NEWSLETTERS BARGAINS FREE S/Sht as available.
Comprehensive TV Repair Manual £9.50. Complete Radio Service and Repair Course £9.50. Complete Repair & Service Manuals Mono TV £12.50; CTV £17.00, Video £19.50. Complete Repair Data with circuit - Mono TV £9.50, CTV £12.50; Video £10.50.
£3.00 plus LSAE BRINGS THE ONLY COMPREHENSIVE SERVICE SHEETS & MANUALS, CATALOGUES plus FREE CHASSIS GUIDE and £4.00 OF VOUCHERS

BOOKS

Electronics: Build and Learn - by R. A. Penfold. Price £5.95. Available from all good bookshops or PE Book Service.

"Satellite Television - Installation Guide" by John Breeds.

Price - £11.95

Available from Practical Electronics Book Service or all good bookshops.



Modern Books Co.

19-21 Praed Street, London W2 1NP
for all your book requirements

SURVEILLANCE

NEW VHF MICROTRANSMITTER KIT, tuneable 80-115 Mhz, 500 metre range, sensitive electret microphone, high quality PCB. **SPECIAL OFFER** complete kit **ONLY £5 POST FREE**. Access orders telephone 021 411 1821. Cheques/ P.O.'s to: Quantek Electronics Ltd, (Dept P.E.), 45a Station Road, Northfield, Birmingham, B31 3TE
Surveillance devices, lasers, Tesla coils, scramblers, ultrasonic and many more, over 150 designs. Send SAE to: Placentre, Old Wharf, Dynock Road, Ledbury HR8 2HS

MISCELLANEOUS

Laboratory stock clearance equipment, computers, ECG transducers, Geigers, anemometers, spare motors etc. SAE list. Laboratories, Maplehurst, RH13 6LL Tel: 0403 819236

Make money in 1989! Use Practical Electronics classified pages for your small ads. For details phone Sarah Holtham on 01-743-8888.

Surveillance construction guides /plans:- 16 blueprints for Bugging, Tracking, Telephone Transmitters £3.00. Find hidden Bugs using Bug Locator/detector device £3.50. Bugdefeater unit jams walkie-talkie, Bug Transmissions £3.50. Special Offer - Order all three for £9.00. Cheque/P.O. - Mr. C. Boosey, 24 Summerfield Road, Torquay, TQ2 7DL.

Mains 'KEYNECTOR' quick and handy connector for electrical appliances. No need for plugs, just place wires under spring loaded keys. Completely safe, keys locked when fuse housing closed. Neon glows when unit is live. £8.40 plus £1.50 p&p, cash/cheque/ P.O. Trade prices on request. FORMAX, Golden Hill Fort, Freshwater, Isle of Wight, PO40 9TF. Tel: 0983 752535

Small Press monthly - the guide to what is happening in the Small Press world. May issue out now. 50p (plus 20p p&p or A5 SAE): SPG, BM BOZO, London WC1N 3XX (Full address).

Program Now

The Advanced Programmers' Journal

The one tool every programmer should have!

From all good newsagents or directly from Intra Press - price £1.50
From the publishers of Practical Electronics



No. 2 LIST BAKERS DOZEN PACKS

All packs are £1 each, if you order 12 then you are entitled to another free. Please state which one you want. Note the figure on the extreme left of the pack ref number and the next figure is the quantity of items in the pack, finally a short description.

- BD4 5 Surface mounting 5am switches. Intended for mains but equally suitable for battery circuits.
- BD5 3 White flush switches. Will replace any standard size switch.
- BD8 2 30 volt 80 watt brass cased elements. Ideal for frost protection, pet warmers.
- BD14 4 Photo transistor Mullard reference OCP70.
- BD16 4 Reel to reel tape heads. 2 record, 2 erase.
- BD17 1pr Ultrasonic transducers. 1 to transmit the other to receive.
- BD20 4 Different mains micro switches, each average 1,000,000 operations.
- BD23 1set Loud speaker cross-overs up to 40 watt for woofer, mid-range and tweeter.
- BD26 2 Counters, belt driven as in tape decks.
- BD36 2 Air spaced tuning condensers. 1/4 in spindle with trimmers.
- BD37 2 Ditto, but solid di-electric.
- BD41 6 Standard size rocker switches. 13 amp at 230 volts.
- BD46 1 Time-on switch. Stays on up to 6 hours, depending on control setting.
- BD48 2 Reed relays. 4-8 volt coil operated.
- BD51 1 12 volt relay. Miniature enclosed with 2 change-over contacts. 700ohm coil.
- BD57 5 Miniature switches for battery circuits, dolls houses, etc.
- BD60 4 Ferrite rods. 4 in long, 1/4 in diameter. Suitable for aerials, inverter transformers, etc.
- BD64 10 Assorted control knobs, 1/4 in spindles, push-on and grub screw type.
- BD65 4 Different thermostatic switches. Control mains or battery devices.
- BD69 2 25 watt 8 ohm variable resistors (pots).
- BD71 4 Wire wound pots with built-in knob. One each 180hm, 35ohm, 50ohm and 100ohm.
- BD78 5 5amp stud rectifiers, 50 volt.
- BD82 4prs Porcelain fuse carriers and fuse holders (make your own fuse board).
- BD84 10 .1mfd 250 volt mains suppressor condenser (cut out the clicks).
- BD85 1 Mains shaded-pole motor with 1/4 in shaft.
- BD86 2 5 in aluminium fan blades. Will fit 1/4 in shaft.
- BD93 4 11 pin bases for relays, etc.
- BD94 5 B7G valve bases.
- BD95 4 B9A valve bases with metal skirt.
- BD98 1 Motor driven stud switch. Ex-fruit machines.
- BD101 1 Delayed-on switch. Can be set at any time up to 2 hours. 115 volt so supplied with dropper.
- BD104 1 Cased mains unit. 4.5 volt regulated output.
- BD106 2 12 volt alarms. Round, approximately 2 in diameter. Sounds like car horn.
- BD109 10 Assorted 1/4 in spindle volume controls.
- BD110 10 Slider type volume controls.
- BD114 1 2 watt amplifier made by Mullard, their reference 1172.
- BD115 1 Wall mounting thermostat, 24 volt.
- BD126 4 Batters holders, MES, will take torch bulbs, etc.

VERY POWERFUL 12 VOLT MOTORS - 1/4 HORSEPOWER Made to drive the Sinclair C5 electric car but equally adaptable to power a go-cart, a mower, a rail car, model railway, etc. B rand new. Price £15.00 plus £2.00 postage. Our ref 15P8.

WHITE CEILING SWITCH 5 am 2 way surface routing with cord and tasle. Mady by the famous Crabtree Company. Price £1 each. Our ref BD528.

13A SWITCH SOCKETS Top quality made by Crabtree, fitted in metal box with cutouts so ideal for garage, workshop, cellar, etc. Price £2 each. Our ref 2B37.

MAINS TRANSFORMER Upright mounting. Normal mains input, gives 25V at 3.5A so should be ideal for big amplifier, etc. Price only £4. Our ref 4P24, please add £1 postage.

POWERFUL IONISER

Generates approx 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, workroom, etc. Makes you feel better and work harder - a complete mains operated kit, case included. £12.50 plus £2 postage. Our ref 12P5/1.



ORGAN MASTER Is there a three octave musical keyboard. It is beautifully made, has full size (piano size) keys, has gold plated contacts and is complete with ribbon cable and edge connector. Can be used with many computers. We can supply informationa sheet. Brand new, only £15 plus £3 postage. Our ref 15P15.

ULTRA SONIC INTRUDER ALARM Small, nicely cased, will detect movement in a room up to 10m x 10m. Ingenious construction makes it independent of the mains: cannot be switched off, even with its on/off switch, until you know the secret; has delayed action enabling you to switch it on and leave the room; it has an inbuilt piezo sounnder which is very penetrating and high pitched and would frighten away most intruders. Has internal switching and could be coupled to an outdoor alarm if required. It is the basis of a very efficient burglar alarm, or has other uses. For instance: you could disconnect the internal sounnder and using the internal switches you would know when somebody arrives without that person being aware that you know. Similarly, the unit could be used to operate other equipment ultrasonically. It is brand new, guaranteed OK, complete but less battery (PP3 alkaline type). Price is £20 plus £3 insured delivery. Our ref 20P11.

110 DECIBEL HORN For use with the ultra sonic intruder detector. Ideal for external positioning to attract the attention of neighbours should you have an intruder. This unit has its own mounting bracket and comes complete with good length of lead. Price £7. Our ref 7P9. Incidentally, this could also be used as a loud speaker.

3 1/2 FLOPPY DISC DRIVE - DOUBLE SIDED, DOUBLE DENSITY, 80 TRACK Shugart compatible, has 34 way IDC connect and will interface with almost any computer. Made by the famous Japanese NEC Company. Price £59.50 plus £3 insured post.



ATARI 65XE COMPUTER

At 64k this is most powerful and suitable for home and business. Brand new, complete with PSU, TV lead, owner's manual and six games. Can be yours for only £45 plus £3 insured delivery.

65XE COMPENDIUM Contains: 65XE Computer, its data recorder XC12 and its joystick, with ten games for £62.50 plus £4 insured delivery.

TIME AND TEMPERATURE LCD MODULE This is a 12 hour clock, a Celsius thermometer, a Fahrenheit thermometer, a too hot alarm and finally a too cold alarm. Nice size, approx 50mm x 20mm, with 12.7mm digits which clearly display the time or temperature. Requires only a 1.5v battery and a few switches. Comes complete with circuit diagram and explanation. Price £6. Our ref 6P12.

CAMERAS Three cameras, all by famous makers. Kodak, etc. One disc, one 35mm and one instamatic. All in first class condition believed to be in perfect working order but sold as untested. You can have the three for £10 including VAT, which must be a bargain - if only for the lenses, flash gear, etc. Our ref 10P58.

1/8th HORSEPOWER 12 VOLT MOTOR. Made by Smiths, the body length of this is approximately 3in, the diameter 3in and the spindle 6/16th diameter. It has a centre flange for fixing or can be fixed from the ends by means of 2 nuts. A very powerful little motor which revs at 3,000 rpm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years, price £8. Our ref 6P1, discount for quantities of 10 or more.

PHILIPS LASER

This is helium-neon and has a power rating of 1.6mW. Completely safe as long as you do not look directly into the beam when eye damage could result. Brand new, full spec. £30 plus £3 insured delivery. Mains operated power supply for this tube gives 1kv striking and 1.25kv at 5mA running. Complete kit with case £15. Battery operated P.S.U. now available at £16.

HAND-HELD VIDEO LAMP. Main operated and will enable you to take professional standard videos. Made by the famous Ferguson Company, this uses a 1000w halogen lamp in a fan cooled, hand-held and hand switched metal housing. Comes complete with option of barn-door assembly and camera bar. Obviously intended to retail at over £60, we offer these as £30 each plus £3 insured delivery. Our ref 30P3.

HIGH RESOLUTION MONITOR. In black and white, used Philips tube M24/305V. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. 5 and new. £16 plus £5 post. Our ref 16P1.

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape 1 1/2 x 4 x 1 1/2 in. The electronically run fuse not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc. or for a caravan. £8 each. Our ref 8P28.

ACORN COMPUTER DATA RECORDER (ref ALF03) this is a mono data recorder with switchable motor control intended for use with the Acorn Electron or BBC computers but also functions with almost any other computer and can be used for normal record and play back of music and speech. Can be battery operated but is supplied with a mains adaptor. Brand new in manufacturer's wrapping. Price £10. Our ref 10P44.



MUSIC FROM YOUR SPECTRUM 128 We offer the Organ Master three octave keyboard, complete with leads and the interface which plugs into your 128. You can then compose, play, record, store, etc. your own music. Price £19 plus £3 special packing and postage. Order ref. 19P1.

FDD BARGAIN

3 1/2 in made by Chiton of Japan. Single aided, 80 track, Shugart compatible interface, interchangeable with most other 3 1/2 in 5 1/4 in drives. Completely cased with 4 pin power lead and 34 pin computer lead £40. Our ref 40P1.

OUR ALADDIN'S CAVE. You may be a new reader and now know that we have a shop at 12 Boundary Road, Hove, where you can go and have a browse around at our assortment of 'goodies'. Unfortunately, because of staff shortages, we cannot be open on Saturdays yet, so the hours are 9.30am to 5pm, Monday to Friday. We of course still serve callers at 250 but request that you bring a completed order form as 250 is really the mail order depot.

J & N BULL ELECTRICAL

Dept PE, 250 PORTLAND ROAD, HOVE

BRIGHTON, SUSSEX BN3 5QT

MAIL ORDER TERMS: Cash, PO or cheque with order. Orders under £20 add £1.50 service charge. Monthly account orders accepted from schools and public companies. Access and B/card orders accepted minimum £5. Phone (0273) 734648 or 203500.

POPULAR ITEMS

Some of the many items described in our current list which you will receive if you request it



EHT TRANSFORMER 4kv 2mA Ex-unused equipment. £5. Our ref 5P139.

FOIL CAPACITORS Axial ended. 33uf 100v. 4 for £1. Our ref DB672. Many other sizes in stock, send for May newsletter.

4 CORE TINSEL COPPER LEAD As fitted to telephones, terminating with flat BT plug. 2 for £1. Our ref BD639.

EHT TRANSFORMER 8kv 3mA. £10. Our ref 10P56.

DOUBLE MICRODRIVES We are pleased to advise you that the Double Microdrives which we were offering at about this time last year as being for the 'QL', 'OPD' and several other computers are again available, same price as before namely £5. Our ref 5P113.

SOFTWARE FOR REMAKING Just arrived. Large quantity of mainly games. All re on normal tape spools in cassette holders and should be suitable for wiping out and re-making into games or programmes of your own design. We offer 5 different for £2 or 100 assorted for £20. Important note: We cannot say which titles you will get nor accept orders for specified titles or 'so many, all different', etc., so only order if you can take them as they come. Order ref 5 for £2 is 2P24, 100 assorted is 20P10.

VERY USEFUL MAGNETS Flat, about 1in long, 1/2in wide and 1/4in thick. These are polarised on their faces which makes them ideal to operate reed switches in doors and windows or to hold papers or labels, etc., to metal cabinets, or even to keep cupboard doors firmly closed. Very powerful: 6 for £1. Our ref BD274(a).

ACORN COMPUTER DATA RECORDER REF ALF03 Made for the Electron or BBC computers but suitable for most others. Complete with mains adaptor, leads and handbook. £10.00. Ref 10P44.

FREE POWER! Can be yours if you use our solar cells - sturdily made modules with new system bubble magnifiers to concentrate the light and so eliminate the need for actual sunshine - they work just as well in bright light. Voltage input is .45- you join in series to get desired voltage - and in parallel for more amps. **Module C** gives 400mA, Price £2. Our ref 2P199 **Module D** gives 700mA, Price £3. Our ref. 3P42.

SOLAR POWERED NI-CAD CHARGER 4 Ni-Cad batteries AA (HP7) charged in eight hours or two in only 4 hours. It is a complete, boxed ready to use unit. Price £6. Our ref. 6P3.

METAL PROJECT BOX Ideal size for battery charger, power supply etc.; sprayed grey, size 8in x 4 1/4in high, ends are louvred for ventilation other sides are flat and undrilled. Order Ref. 2P191. Price £1.

4-CORE FLEX CABLE. Cores separately insulated and grey PVC covered overall. Each copper core size 7/0.2mm. Ideal for long telephone runs or similar applications even AFIR Very sensitive. A magnet! **STEREO HEA100** metres coil £8. Order ref. 8P19.

6-CORE FLEX CABLE. Description same as the 4-core above. Price 15 metres for £2. Our ref. 2P197 or 100 metres £9. Order ref. 9P1.

13A PLUGS Good British make complete with fuse, parcel of 5 for £2. Order ref. 2P185.

13A ADAPTERS Takes 2 13A plus, packet of 3 for £2. Order ref. 2P187.

28V -0-20V Mains transformers 2 1/2 amp (100 watt) loading, tapped primary. 200-245 upright mountings £4. Order ref. 4P24.

BURGLAR ALARM BELL - 8" gong OK for outside use if protected from rain. 12V battery operated. Price £8. Ref. 8P2.

VERY RELIABLE CAPACITOR 4.7µ 400v nonelectrolytic so not polarised, offered in all can, size 1 3/4x1 1/2in high. A top grade capacitor made for high class instrument work. Ideal for PCB mounting. 2 for £1. Our ref BD667.

CAPACITOR BARGAIN - axial ended, 4700µF at 25V. Jap made, normally 50p each, you get 4 for £1. Our ref. 613.

SINGLE SCREENED FLEX 7.02 copper conductors, pvs insulated then with copper screen, finally outer insulation. In fact quite normal screened flex. 10m to £1. Our ref DB668.

M.E.S. BULB HOLDERS Circular base batten type fitting. 4 for £1. Our ref DB127s.

SPRING LOADED TEST PRODS - Heavy duty, made by the famous Bulgin company, very good quality. Price 4 for £1. Ref. BD597.

3-CORE FLEX BARGAIN No. 1 - Core size 1.25mm so suitable for long extension leads carrying up to 13 amps, or short leads up to 10 amps. 15mm for £2. Ref. 2P190.

3-CORE FLEX BARGAIN No. 2 - Core size 1.25mm so suitable for long extension leads carrying up to 13 amps, or short leads up to 25A. 10m for £2. Ref. 2P190.

ALPHA-NUMERIC KEYBOARD - This keyboard has 73 keys giving trouble free life and no contact bounce. The keys are arranged in two number pad, board size is approx. 13" x 4" - brand new but offered at only a fraction of its cost, namely £3 plus £1 post. Ref. 3P27.

WIRE BARGAIN - 500 metres 0.7mm solid copper tinned and p.v.c. covered. Only £3 plus £1 post. Ref. 3P31 - that's well under 1p per metre, and this wire is ideal for push on connections.

1/8th HORSEPOWER 12 VOLT MOTOR Made by Smiths, the body length of this is approximately 3in, the diameter 3in and the spindle 5/16th of an inch diameter. It has a centre flange for fixing or can be fixed from the end by means of 2 nuts. A very powerful little motor which revs at 3,000 rpm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years. Price £8. Our ref 6P1, discount for quantities of 10 or more.

3 VOLT MOTOR Very low current so should be very suitable for working with solar cells. £1 each. Our ref BD681.

MINI SPEAKERS to use instead of headphones with your personal stereo - simply plug in to earphone socket. Excellent sound quality, only £4 per pair. Our ref 4P34.

SEALED LEAD ACID BATTERIES Japanese made re-chargeable and maintenance-free. Leak-proof construction, so could be used in any position. Long life expectancy - usually four to five years. 12V 2.6Ah £10 each. Our ref 10P59 v 1Ah, £5 each. Our ref 5P135.

INNER EAR STEREO HEADPHONES Ideal for lady listeners as they will not mess up your hair! Come complete in a neat carrying case. Price £3. Our ref 3P56.

STEREO HEADPHONE AMPLIFIER Very sensitive. A magnetic cartridge or tape head will drive it. Has volume control and socket for stereo headphones. 3v battery operated. £1 each. Our ref BD680.

FET CAPACITOR MICROPHONE EAGLE CI.200 Output equivalent to a high class dynamic microphone while retaining the characteristics of a capacitor microphone. Price £1. Our ref BD646.

SUM-MIN TOGGLE SWITCH Body size 8mm x 4mm x 7mm SBDT with chrome dolly fixing nuts. 4 for £1. Our ref BD649.

SUB-MIN PUSH SWITCH DPDT. Single hole fixing by hexagonal nut. 3 for £1. Our ref BD650.

USE PC COMPILERS FOR AN SBC


For really fast development of stand alone systems, use a Lancer or Hunter target board with Hexatron's PromDOS. This emulates DOS and BIOS calls, gives you silicon discs and even allows you to run non-ROMable compiled code in a ROM environment. Too good to be true? - Call us now for a free demonstration.

THE SDS LANCER

An 8088/V20 target board with two serial ports, four parallel ports, six counter-timers, four 32 pin memory sockets, battery backup, RTC, watchdog timer, optional 8087, optional mains psu & case.

THE SDS HUNTER

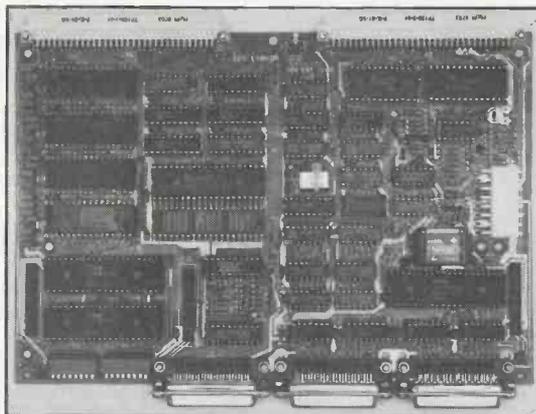An 80188 target board with 256k bytes EPROM, 256k bytes battery backed RAM, 256k bytes D-RAM, two serial ports, three counter-timers, RTC, watchdog timer, optional mains power supply and case.




Sherwood Data Systems Ltd

Unit 6, York Way, Cressex Estate, High Wycombe. Tel. 0494-464264

Join up with LITESOLD

Professional Soldering Equipment

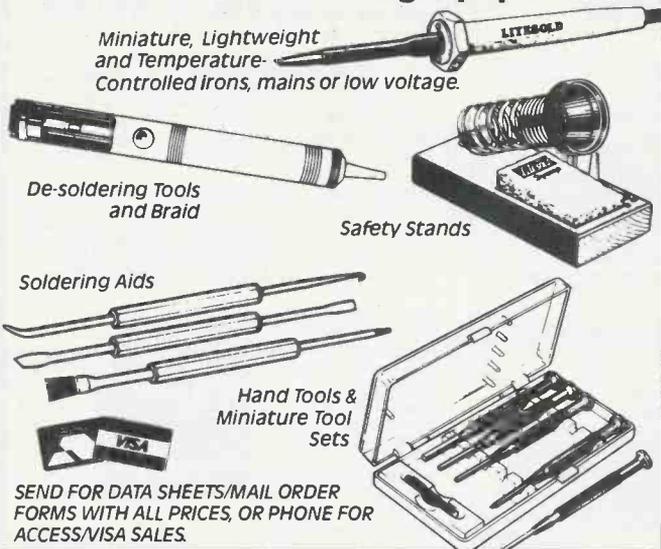Miniature, Lightweight and Temperature-Controlled irons, mains or low voltage.



De-soldering Tools and Braid

Safety Stands

Soldering Aids

Hand Tools & Miniature Tool Sets

SEND FOR DATA SHEETS/MAIL ORDER FORMS WITH ALL PRICES, OR PHONE FOR ACCESS/VISA SALES.

JOIN UP WITH THE PROFESSIONALS
LIGHT SOLDERING DEVELOPMENTS LTD
 97-99 Gloucester Road, Croydon CR0 2DN
 01-689 0574

PCB DESIGNER


FOR THE 48K ZX SPECTRUM

Now you can produce high quality printed circuit boards/circuit diagrams/component layouts on your 48K ZX Spectrum. If you don't own one it's worth getting one just for this suite of programs! Comprehensive manual included with getting started tutorial.

FULL SUITE FOR ONLY £30.00 INC.


PCB LAYOUT:

Produce quality printed circuits directly from your EPSON RX/FX or compatible dot matrix printer using a dense 1:1 printout on positive photoresist coated board. Or super quality using x2 printout and photoreduction. Many features such as 15 track widths; 15 pad sizes; 16 transistor/ic/corners; 20 connectors; large multiscreen WYSIWYG display gives a clear uncluttered view of pads, tracks and drill holes: 0.1in. grid on/off; Block move; copy; mirror; rotate; erase; area fill (ideal for earth plane); preview; undo; dimensionally accurate printer routine with quick print; 1:1 or 2:1 dumps. Custom pad design and library. Available separately for £20.00

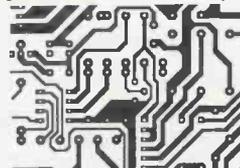

COMPONENT LAYOUT

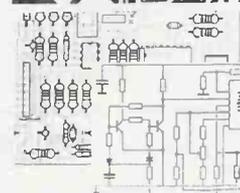Draw component layouts directly or from existing pcb layouts using a unique track reducing facility. The following components are provided: resistors, capacitors, ics, diodes, transistors, line drawing, printout and block commands as above.



CIRCUIT DIAGRAMS

Features similar to the above programs with a library of electronic symbols including resistors, capacitors, diodes, transistors, fets, op amp, switches, inductors, logic gates.

Version now available for EE Centronics Interface—see Jan issue State version required from: Disciple/+D; Discovery; +3; Microdrive & Tape. Important! Tape and Microdrive users please state Centronics interface in use or send £1 for details.

KEMSOFT THE WOODLANDS, KEMPSEY, WORCESTER WR5 3NB. Tel. 0905 821088 after 6 p.m., or see us on A.I.X-386 BULLETIN BOARD 0905 52536/754127 on any computer with modem.

A new socio-economic indicator which seems to have emerged from the electronics field is 'mips per capita'. Readers familiar with computer jargon will know that mips is an abbreviation for million instructions per second. In this case it measures each person's 'consumption' of digital processing power, through computers or other electronic systems using digital information processing. So it's rather like that measurement unit 'energy consumption per capita' one finds in tables of socio-economic statistics put out by international bodies like the World Bank.

Although mips is well established as an engineering measure of processing speed, the idea of bringing it into a social context as a commodity which can be used by the individual, or 'consumed', is something new. The concept, I believe, is due to Professor I. Runge of the Fraunhofer Institute for

INDUSTRY



NOTEBOOK

enlightenment. Looking over one's shoulder to see what the Joneses have got is considered quite natural. Life can be perfected. Living in a permanent state of debt to achieve this is positively virtuous.

For those who are misguided enough to question this doctrine there is a thoroughly sensible answer. There always is. Everything will come right in the end because of the process the economists call 'trickle down'. The idea is that if a minority of countries – or persons – is allowed and encouraged to become extremely rich it will act as a motor for economic growth. Its wealth will not remain entirely with itself but, through activities like consumption or investment, will percolate down to others who are less well off. As a result of this process, the theory goes, the present stark inequalities between people will eventually be smoothed out by improvements in capital investment and productivity in the poorer countries.

MIPS FOR THE MINORITY

BY TOM IVALL

TRICKLE CHARGING
DOESN'T FILL THE
COFFERS

**Are we grabbing
more and more
trivia while the
other half gets less
and less of what it
needs?**

Microstructure Technology in Munich, West Germany. He has recognised, quite rightly, that digital signal processing is now introducing technical criteria once exclusive to computer technology into a much wider field.

He has a chart, for example, which shows the increasing demand for information processing in terms of mips that will result from such developing electronic systems as digital television, the videophone, high-definition tv, pattern recognition in automobiles and man-machine interfaces for computers. By the turn of the century, he reckons, each human being in the industrialised countries will be producing on average a demand for 100,000 mips.

But the operative phrase here is, of course, "in the industrialised countries." These number about twenty in all. One can hardly imagine the kind of applications listed above as having any relevance to the lives of the majority of the world's population, spread mainly among the hundred or so developing and third world countries. The situation parallels that of energy consumption mentioned above. In the USA, for example, on average each citizen consumes 70 times as much energy (in joules) per day as a person living in the forty or so poorest countries of the world, and 12 times as much per day as someone living in the fifty slightly richer countries. Yet the USA represents only 4-5% of the world's total population.

Our plentiful supplies of mips and joules – and all the sophisticated equipment they make possible – are very nice for us in the industrialised countries. There seems nothing wrong in using and enjoying what has been provided for us. All the same, what I find an almost indecent spectacle is our incessant demand for more and more, against the drab background of poverty and deprivation lived by the majority of mankind.

Technology advances can be seen in an academic or professional sense, like scientific discoveries, as pure additions to the common stock of human knowledge. But the real motivation behind them, of course, is commercial competition and its built-in necessity to sell newer and newer products and services. So we find ourselves locked in a feverish cycle of innovation and obsolescence that gets shorter and shorter. Meanwhile the waste and pollution pile up.

Today, when there are no longer any technical reasons for failing to supply all the world's inhabitants with adequate food, clothing and shelter and health and education services, it seems to me deplorable that in Western Europe, America and Japan we have huge productive resources locked up in catering for the buying power of an already affluent minority. Part of the system is to keep persuading this minority that they really do have 'needs' which, in their benighted state of ignorance, they had never realised before. The discovery of these needs is presented as a form of

It's obvious that 'trickle down' does work in particular cases. For example, an entrepreneur with a desire to become rich sets up a new business in some town. If he is successful – and he will have a strong motivation to be so – his activity will provide work and income for employees, perhaps additional sales for suppliers to his firm, and extra business for local shop serving the employees. But in the world at large it doesn't function at all well. In the developing countries there is still widespread undernourishment, poverty, ill-health and crippling indebtedness to the richer nations.

Apart from the way it works, 'trickle down' has two pernicious effects on human beings. First, it creates enormous disparities in income and wealth between individuals. This can lead to envy and strife. Secondly it sets up the acquisition of wealth and power, or a life given over to getting and spending, as a desirable model for all to copy. When people are excessively preoccupied with the means to life, in place of life itself, they become dehumanised into production machines. Pursuit of the means actually destroys the end.

To return to mips, I've studied the technology of hdtv with great interest, and written about it in this journal, but I have to confess that I could manage without this particular enhancement in my own life. And I suspect that many other people would be happy to give up future gratifications of this kind in goods and services if they felt that the productive resources needed to provide such facilities could be diverted to more urgent and humane purposes.

When filing this report, Tom warned me that it was "A bit subversive in places." True, but as much as I am devoted to technology, I am also conscious that humanitarian considerations on a broader scale must not be overlooked. Ed.

PE

PRACTICAL ELECTRONICS BOOK SERVICE

Here is your Editor's choice of books he thinks will be of interest to electronics and computer enthusiasts

BEGINNERS AND EARLY STARTERS

NEW Mini-Matrix Board Projects.

R.A.Penfold. 112 pages. £2.50.

Order Code BP99

Shows a selection of 20 useful and interesting circuits that can be built on a mini-matrix board of 24 holes by 10 copper strips in size - an ideal book for early experimenters.

NEW From Atoms to Amperes.

F.A.Wilson. 160 pages. £2.95.

Order Code BP254.

For the absolute beginner, clearly explaining the fundamentals behind the whole subject of electricity and electronics.

NEW Electronic Projects for Beginners.

F.G.Rayer. 128 pages. £1.95.

Order Code BP48

Specially for the newcomer to electronics who is looking for a book containing a wide range of easily made projects. Some circuits need no soldering and many others show actual component and wiring layouts.

Electronics Build and Learn

R.A.Penfold. 128 Pages. £5.95.

Order Code PC 101

Combining theory and practice, the book describes a circuit demonstrator unit that is used in subsequent chapters to introduce common electronic components and circuit concepts, complete with practical experiments.

Practical Electronic Building Blocks

R.A.Penfold. There are two books -

Book 1 : 128 pages. £1.95.

Order Code BP117

Book 2 : 112 pages. £1.95.

Order Code BP118

Book 1 is about oscillators and gives circuits for a wide range, including sine, triangle, square, sawtooth and pulse waveforms and numerous others from voltage controlled to customised ic types.

Book 2 looks at amplifiers, ranging from low level discrete and opamp types to ic power amps. A selection of mixers, filters and regulators is included.

30 Solderless Breadboard Projects

R.A.Penfold. Two books each of 160

pages. Book 1 : £2.25. Order Code

BP107. Book 2 : £2.25. Order Code

BP113.


Each project is designed for building on a Verobloc breadboard and is accompanied by a description, circuit and layout diagrams and relevant constructional notes. Many of the components are common to several projects. Book 1 covers linear devices, and Book 2 covers cmos logic chips.

Beginners Guide to Building

Electronic Projects R.A.Penfold. 112

pages. £1.95. Order Code BP 227

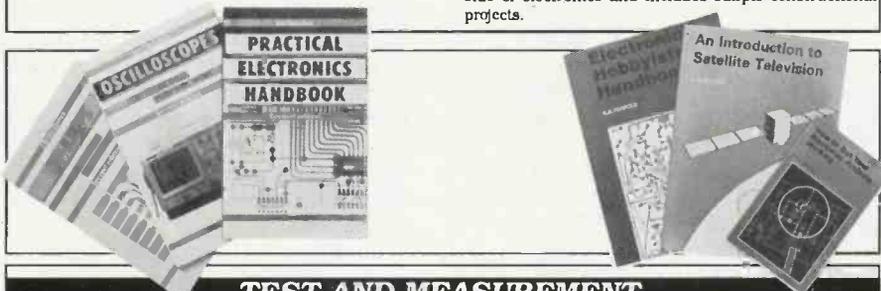Shows the complete beginner how to tackle the practical side of electronics and includes simple constructional projects.



TEST AND MEASUREMENT

How to Get Your Electronic Projects Working.

R.A.Penfold. 96 pages. £2.50.

Order Code BP110.

Essential reading for anyone who wants first-time success in project assembly. Covers tracing mechanical faults as well as testing for failures of active and passive components of most types.

Modern Electronic Test Equipment

K.Brindley. £6.95.

Order Code NT4

Detailed information and discussions on analog and digital meters, oscilloscopes, signal sources, frequency, time and event counters, spectrum and logic analysers, displays and other test equipment.

Getting the Most from Your Multimeter

R.A.Penfold. 112 pages. £2.95.

Order Code BP239

There's more to what you can do with a meter than meets the casual eye. The book covers the basics of what you can do with analogue and digital meters and discusses component and circuit testing.

Oscilloscopes

I.Hickman. £6.95.

Order Code NT3

Subtitled 'How to Use Them, How They Work' the book is illustrated with diagrams and photographs and is essential reading for any one who wants to know about scopes, from first principles to practical applications.

SATELLITE TV

NEW Satellite TV Installation Guide - 2nd edition John Breeds. £11.95. Order Code STV1

Full of vital information for any competent diyer who wishes to install a satellite tv antenna and obtain optimum reception quality.

An Introduction to Satellite Television

F.A.Wilson. 112 pages. £5.95.

Order Code BP195

Informative answers to many of the questions about this communications revolution. The information is presented on two levels, one aimed at the complete beginner, the other at professional engineers and serious amateur enthusiasts.

AUDIO AND MUSIC

Introducing Digital Audio

I.Sinclair. 112 pages. £5.95.

Order Code PC102

A non-mathematical introduction to the new digital technology, discussing the principles and methods involved in devices such as cd, dat and sampling.

Electronic Music Projects

R.A.Penfold. 112 pages. £2.50.

Order Code BP74

24 practical constructional projects covering fuzz, wah, sustain, reverb, phasing, tremolo etc. The text is split into four sections covering guitar, general, sound generation and accessory projects.

More Advanced Electronic Music Projects

R.A.Penfold. 96 pages. £2.95.

Order Code BP174

Complementing BP74 by covering more advanced and complex projects including flanging, chorus, ring modulation, plus a selection of drum, cymbal and gong circuits.

NEW Computer Music Projects

R.A.Penfold. 112 pages. £2.95.

Order Code BP173

Shows how home computers can produce electronic music and covers sequencing, analogue and Midi interfacing, digital delay lines and sound generators.

Practical Midi Handbook

R.A.Penfold. 160 pages. £5.95.

Order Code PC103

A practical how-to-do-it book for musicians and enthusiasts who want to exploit the capabilities of Midi. Covers keyboards, drums, sequencers, effects, mixers, guitars, and computer music software.

Midi Projects

R.A.Penfold. 112 pages. £2.95.

Order Code BP182

Practical details of interfacing many popular home computers with Midi systems, and also covering Midi interfacing to analogue and percussion synths.

NEW Electronic Synthesiser Construction.

R.A.Penfold. 112 pages. £2.95.

Order Code BP185.

Even relative beginners should find the monophonic synthesiser described here within their capabilities if the book is thoroughly read. Individual aspects of the synth are dealt with separately and pcb designs are shown for the main modules.

DIGITAL AND COMPUTING

NEW A Concise Introduction to MS-DOS.

N. Kantaris. 64 pages. £2.95.
Order Code BP232

A ready-reference guide for those who need a quick insight into the essential command functions of this operating system, but who don't have the time to learn it fully.

An Introduction to Computer Peripherals

R.A. and J.W. Penfold. 80 pages.
£2.50. Order Code BP170

Covers such items as monitors, printers, disc drives, cassettes, modems, etc, explaining what they are and how to use them with your computer and with each other.

Microprocessing Systems and Circuits

F.A. Wilson. 256 pages. £2.95.
Order Code BP77

A comprehensive guide to the elements of microprocessing systems, covering the fundamental principles behind this important subject.

Introduction to 6800/6802 Microprocessor Systems

R.J. Simpson and T.J. Terrell. 238 pages. £10.95. Order Code NT9

The book covers systems hardware, programming concepts and practical experimental work that will assist in understanding the 6800/6802 microprocessor, with additional information on the 6802D5E evaluation system.

NEW An Introduction to 68000 Assembly Language.

R.A. and J.W. Penfold. 112 pages.
£2.95. Order Code BP184

Covers the fundamentals of writing programs that will vastly increase the speed of 68000 based machines such as the Commodore Amiga, Atari ST range, Apple Macintosh, etc.

Getting the Most from Your Printer

J.W. Penfold. 96 pages. £2.95.

Order Code BP181

How to use the features found on most dot-matrix printers from programs and popular wordprocessors, showing examples of what must be typed to achieve a given effect.

Micro Interfacing Circuits

R.A. Penfold. Two books, each of 112 pages.

Book 1 : £2.25. Order Code BP130.

Book 2 : £2.25. Order Code BP131

Both books include practical circuits and useful background information though pcb layouts are not included. Book 1 mainly covers computer input-output techniques. Book 2 deals primarily with practical application circuits.

NEW An Introduction to 6502 Machine Code.

R.A. and R.W. Penfold. 112 pages.
£2.50. Order Code BP147

Covers the main principles of machine code programming on 6502-based machines such as the Vic-20, Oracle/Atmos, Electron, BBC and Commodore 64. It assumes no previous knowledge of microprocessors or machine code and gives illustrative programming examples.

NEW A Z-80 Workshop Manual.


E.A. Parr. 192 pages. £3.50.
Order Code BP112

A book for those who already know Basic but wish to explore machine code and assembly language programming on Z80 based computers.

Practical Digital Electronics Handbook

M. Tooley. 208 pages. £6.95.
Order Code PC 104

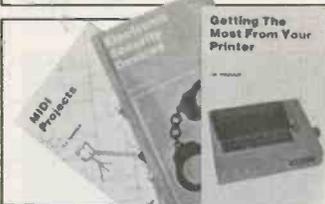Nine constructional projects introduce digital circuits, logic gates, timers, microprocessors, memory and interface circuits - an essential book for anyone interested in digital devices.



GENERAL CONSTRUCTIONAL

NEW Electronic Science Projects.

Owen Bishop. 144 pages. £2.95.
Order Code BP104

A bumper bundle of experimental projects ranging in complexity and including a colour temperature meter, electronic clock, a solid state (led display) scope, an infra-red laser, a fascinating circuit for measuring the earth's electrical field strength, and many more.

Electronic Security Devices

R.A. Penfold. 112 pages. £2.50. BP56

Full of ideas for keeping your valuables safe. The circuits include designs for light, infra-red, ultrasonic, gas, smoke, flood, door and baby sensors.

NEW More Advanced Electronic Security Projects. R.A. Penfold. 112 pages. £2.95. Order Code BP190

Follows on from where BP56 leaves off and describes a number of more up-to-date and sophisticated projects, such as pyro-sensors, infra-red and doppler-shift detection, fibre-optic loops, and many others.

NEW Electronic Projects for Cars and Boats.

R.A. Penfold. 96 pages. £1.95.
Order Code BP94

15 fairly simple projects that can be used with a car and/or boat. Stripboard constructional details are included, as are explanations of the circuit theory.

Power Supply Projects

R.A. Penfold. 96 pages. £2.50.
Order Code BP76

A selection of power supply designs, including simple unregulated, fixed voltage regulated and variable voltage stabilised, ni-cad charger, voltage step-up, and inverter.

More Advanced Power Supply Projects

R.A. Penfold. 96 pages. £2.95.
Order Code BP192

Covers more advanced topics than BP76 and includes precision supplies, switch mode and computer controlled supplies, plus a selection of miscellaneous circuits.

NEW Popular Electronic Circuits.

R.A. Penfold. 160 pages. £2.95.
Order Code BP80

Containing a wide range of circuit designs for experienced constructors who are capable of producing working projects direct from a circuit diagram without specific constructional details.

DATA AND INFORMATION BOOKS

Digital IC Equivalents and Pin Connections

A. Michaels. 320 pages. £5.95.
Order Code BP140

Linear IC Equivalents and Pin Connections

A. Michaels. 256 pages. £5.95.
Order Code BP141

Between them these two books show equivalents and pin connections of a popular user-orientated selection of European, American and Japanese ICs. They also include details of functions, manufacturer and country of origin. The Digital ICs book also quotes details of packaging and families.

Opamps

B. Dance. £6.50.
Order Code NT2

Subtitled 'Their Principles and Applications' this interesting book is written in a simple non-mathematical style and provides a source of practical circuits that use both commonplace and more sophisticated opamps.

Electronic Hobbyists Handbook

R.A. Penfold. 96 pages. £4.95. Order Code BP233

Provides a source of useful information that the amateur enthusiast is likely to need for day-to-day pursuance of hobby electronics.

Practical Electronics Handbook

I. Sinclair. £7.95.
Order Code NT1

A useful and carefully selected collection of standard circuits, rules-of-thumb and design data for enthusiasts, students and engineers involved in radio, computing and general electronics

Newnes Electronics Pocket Book

I.E. Parr. £6.95.
Order Code NT10

Presents all aspects of modern electronics in a readable and largely non-mathematical style, and is a good source of valuable information for enthusiasts and professional engineers alike.

NEW Key Techniques for Circuit Design

G.C. Loveday. £6.95.
Order Code BM 101

Tackles the problems of designing circuits from scratch, introducing the concept of target specifications, the design sequence, device selection, rules of thumb, and useful equivalent circuits.

HOW TO ORDER

State your order code and your name and address clearly. Enclose a cheque, PO or international money order (add 50p postage per book - £1.00 for overseas surface mail), and send to:

PE Book Service
Intra House
193 Uxbridge Road
London W12 9RA

Books are normally delivered within 10 days but please allow 28 days for delivery.

READY-MADE P.C. BOARDS

Simplify your project assembly – use a ready-made printed circuit board. All are fully drilled and roller tinned. Just slot in the components as shown in the project texts, and solder them. PCBs are the professional route to project perfection.

MAIL ORDERING

Select the boards you want, and send your order to
**PE PCB SERVICE, PRACTICAL ELECTRONICS,
193 UXBRIDGE ROAD, LONDON W12 9RA.**

Prices include VAT and postage and packing. Add £2 per board for overseas airmail. Cheques should be crossed and made payable to **Intra Press**.

Quote the project name and PCB Code Number, and print your name and address in **Block Capitals**. Do not send any other correspondence with your order.

TELEPHONE ORDERS (OPEN 24 HOURS)

Use your Access card and phone your order to

0268 289923

clearly stating your name and address, card number, and order details.


All orders receive priority attention, but allow 28 days for delivery in case a PCB is temporarily out of stock.

WE CAN ONLY SUPPLY THE PCBs LISTED HERE

**CHECK LATEST ISSUE FOR
PRICES BEFORE ORDERING**

PHOTOCOPIES OF THE TEXTS MAY BE BOUGHT FROM THE EDITORIAL OFFICE AT £1.00 EACH PART (£1.50 OVERSEAS), P&P INCLUSIVE.

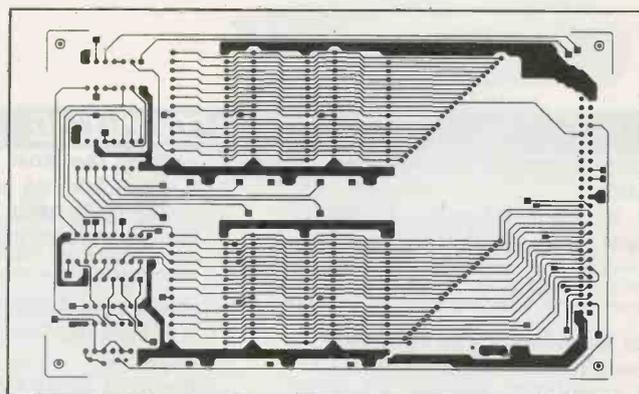COMPONENTS ARE AVAILABLE FROM ADVERTISERS.



OCT 86			
DRUM SYNTHESISER	121	£7.67	
MAINS DELAY TIMER – selectable 15 to 120 mins. Set of 2 PCBs.	122	£7.92	
MAINS DIMMER – touch control up to 400W.	123	£3.90	
NOV 86			
REMOTE JOYSTICK – infrared computer controller. Set of 2 PCBs.	124	£10.86	
BABY ALARM – through-the-mains transceiver.	125	£10.71	
DEC 86			
VIDEO ENHANCER – manually adjustable video improvement.	126	£8.76	
JAN 87			
VIDEO FADER – simple inexpensive video mixer	127	£4.50	
VOICE SCRAMBLER – confidential trans.	128	£8.06	
MAR 87			
4 CHANNEL ENHANCER	135	£4.60	
LIGHT PEN – uses fibre optics for accuracy	136	£4.10	
ULTRASONIC TAPE MEASURE	138	£9.50	
APR 87			
VIGILANTE CAR ALARM – keeps cars alert	139	£5.90	
MAY 87			
BRIGHT FUZZ – Foot operated overdrive	145	£3.90	
JUN 87			
AUDIO SIGNAL GENERATOR	146	£10.20	
JUL 87			
WORD GENERATOR – 16-bit binary words	147	£13.42	
SCOPE STORE oscilloscope add-on data storage	148	£11.94	
SEP 87			
SPEECH PROCESSOR – clarifies speech	150	£5.86	
GCSE TIMER UNIT – versatile variable delay	151	£5.18	
FUNGEN – triple waveform signal generator	152/153	£9.69	
LIGHT CONTROLLER – delayed switching	154	£4.64	

OCT 87			
GUITAR TO SYNTH – music interface	157A/B	£9.95	
NOV 87			
DUAL POWER SUPPLY – GCSE	158	£6.20	
MIDI EXPANDER – Music Interface	159	£5.04	
DEC 87			
RS 232C TO MIDI	160	£6.43	
TEACHER RADIO – GCSE	161	£5.58	
JAN 88			
LEGO BUGGY DRIVER	163	£6.42	
FEB 88			
TEACHER TALKBACK – GCSE	164	£6.36	
DC MOTOR SERVO	165	£7.53	
MAR 88			
APPLIANCE TIMER	166A/B	£9.38	
TEACHER LIGHTSHOW – GCSE	167A/B	£9.09	
LOGIC ANALYSER – Double-sided	168	£20.65	
APR 88			
LIGHT METAL EFFECTS	169	£7.10	
TEACHER COUNTER	170	£4.95	
	171	£4.92	
MAY 88			
RF SPEECH PROCESSOR	172	£6.26	
JUN 88			
AMSTRAD ROM EXPANSION	173	£10.80	
MAINS MODEM	174	£4.27	
JULY 88			
VOCALS ELIMINATOR	175	£4.31	
AUGUST 88			
SPEAKING CLOCK	176	£16.75	
SEPT 88			
BBC MULTIPLEXER	177	£4.50	
OCT 88			
METAL DETECTOR	178	£6.50	
DEC 88			
PLD PROGRAMMER	179	£9.90	
	180	£4.90	
PANNING MIXER	181	£7.80	
JAN 89			
RUDOLPH'S NOSE	182	£6.25	
ANGEL'S HALO	183A/B	£9.40	
CANDLE FLICKER	184	£6.25	
PULSATING STAR	185A/B	£13.00	
RANDOM PUDDING	186	£6.25	
MAR 89			
CAMERA SHUTTER TIMER	187	£9.95	
APR 89			
PC MULTIPOINT	188A/B	£20.55	
MAY 89			
KIRLIAN CAMERA	189A/C	£10.50	
JUN 89			
SOLAR HEATING CONTROLLER	190	£7.20	
DELUXE METRONOME	191	£10.95	

Free Reader Adverts

*Searching for that elusive component?
Surplus equipment to sell?
Read the rules and fill in the form below to have your free ad published in PE BAZAAR.*

Casio MT-70 electronic keyboard. Twenty voices, rhythms, light pen, etc., memory. Perfect condition, offers around £100. Tel: Ambleside (05394) 32329.

Thermometer/Lightmeter (-50 to +650°C). British made and unused. With G/purpose type T thermocouple probe. £38.00 Tel: Blandford: 56727.

For Sale: components; spare calc., computer (Tandy) RAMs, filter diode, caps, resist. £25.00. Tel: 01-450 9820.

Wanted: Cossor 339 circuit diagram with all resistor values or owners of above please contact me. J.C. Van der Walt, PO Box 313, Swartruggens 2835, South Africa.

For sale: point-contact and other early types of transistor. Write for lists and prices. Andrew Wylie, 2E Welbeck Mansions, Inglewood Road, London NW6 1QX

Wanted: Tantek PCB and front mask for Tantek expander and address of Tantek. Dragan Trajkov, Bote Bocevski, 11, 91000 Skopje, Yugoslavia.

Transistor curve tracer Tektronik type 575 power supplies SMPS +5V ± 12. Offers. Tel: 0889 26446.

NEC 8100 Arrowriter matrix printer £40. IBM PC compatible with clock etc. £220. Swap 256K Drams? Tel: 0423 872045 (evenings).

Practical Electronics May 1979 to Dec. 1988. Most issues. Offers plus p&p. Allan Dunnett, 11 Silverknowes View, Edinburgh EH4 5PY. Tel: 031 336 4904 (evenings).

Commodore business package, Tractor printer 8023P, Twin disk 82501p (with fault), monitor & keyboard 8096K. Offers? Tel: 0272 843151, P.S. Aston, Clevedon Road, North Weston, Portishead, Bristol BS20 8PL.

Oscilloscope Hameg 103 single trace with switchable X1/X10 ground probe. Extremely accurate. As new £150 ono. P. Herman, tel: 01 542 6093.

Bio-feedback - looking for any experimentors who have equipment or circuit diagrams or interest in this subject. Chris Blythe, 29 St. Marks Road, Windsor, Berks SL4 3BD. Tel: (0753) 841417.

Philips 14 inch colour TV, KT3, spares only, £5 complete, buyer collects. Roy Fletcher, 29 Hirst Close, Long Lawford, Rugby, Warks.

Wanted: Newbrain computer manual. Will pay good price. D. Humphreys, 23 Borth Avenue, Offerton, Stockport, SK2 6AJ. Tel: 061-483 0265.

Elektor mags. No. 1 to no. 68. Dec 1974 to Dec 1980 complete. Clean copies. Offers. Buyer to pay delivery costs. D. Clay, 6 Wyke Beck Avenue, Leeds LS9 0JQ.

External 5 1/4 inch floppy disk drive case with power supply. New. £10 plus p&p. Steve Kirkby, 131 Park Road, Chandlers Ford, Hants. Tel: 0703 895827 (8.30 to 4.30).

Wanted: working labgear teletext adaptor for television. Any offers? Phone Michael on 01-764 5742. Michael Banbrook, 87 Glenister Park Road, London SW16 5DS

Wanted: back numbers of Practical Electronics. Jan, July, Sept 1981. JB Hanson, 47 Langdale Road, Woodley, Stockport SK6 1BH.

Wanted: 'Basic' transceiver (C.B., walkie-talkie) and any books, accessories. Send details: A. Khan, 73 Park Road, Bolton, BL1 4RQ.

Four 16K dynamic RAM ICs in original packaging. Full info. Cost £3.49 each, sell 4 - £6.00. A. Khan, 73 Park Road, Bolton, BL1 4RQ.

Breaking BBC-B for spares. Z80 second processor £95. Complete speech system £10. OWHY peripherals also wanted. Tim Hargreaves, 23 Clandon Avenue, Tunstall, Stoke-on-Trent ST6 5UX. Tel: 0782 838554.

Eproms 2716, 2732, 2764 used £1 each. 5 1/4 DSDD disk drive £32. Te: 0383 731193.

For sale: Hitachi oscilloscope V203F 20MHz £200 Tel: (0297) 21537.

Cable, top quality telephone/signal cable, six and twelve solid cores, white, 20-30p metre quick sale. Roger Yarwood, 14 Betony Vale, Royston, Herts SG8 9TF.

Wanted: I.R. detector photo-voltaic type near I.R. invisible wave length band of the spectrum. L. Pott, PO Box 251, Chester, Cheshire.

Wanted: books or information on constructing linear motors AC and DC plus control circuits for same. G. Easterbrook, 44 Guinness Lane, Exwick, Exeter, Devon.

Electronics mags back issues, PE, ETI, PW etc. £1.00 each or £5.00 for 10 copies. Tel: (0734) 700657.

55ft aerial mast in 10 tubular sections. Hinged base and fittings. Heavy duty. £200. Tel: Reading 701163.

Computer CBM64. Load IT cassette deck speech synth. Joystick loads of games. Tel: 01-560 6116.

Wanted: magazines, Practical Electronics or similar. Will collect reasonable distance from Norwich. Tel: 0603 623874.

PE BAZAAR

Name & Address			

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules.
Signature.....Date.....

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be posted within one month of cover date. (One month later for overseas readers).
Send this form (or a photocopy of it) to:
PE Bazaar, Practical Electronics, 193 Uxbridge Road, London W12 9RA.

TRANSFORMERS

12/24V or 12-0-12V	2 x 12V Secs	2 x 25V Tapped Secs to give
24V	12V	5,7,8,10,13,17, 20,25,33,40, 50V
0.15	0.05	or 20-0-20V or 25-0-25V
0.25	0.5	50V
0.5	1	25V
1	2	£
2	4	P&P
3	6	0.5
4	8	1
6	12	2
8	16	3
10	20	4
15	30	5
20	40	6
30	60	8
41	83	10

MAINS ISOLATORS

Pri 120V x 2 or 220/240V or 415/440V Sec 440V or 240V or 110V Centre Tapped	20VA	60	100	200	250	500	1000	1500	2000	3000	6000
£8.33	2.50	13.60	15.87	22.49	27.20	41.91	76.01	98.04	117.96	165.41	353.43
	p	p	&	p						O.A	O.A

AUTOS

105,115,220,230,240V For step-up or down	80VA	150	250	350	500	1000	1500	2000	3000	4000	5000	7500	10kVA	50/25V or 25-0-25V
£6.91	1.92	10.03	12.25	14.05	19.05	34.03	40.40	60.41	102.72	133.35	155.28	239.70	283.23	O/A
		p	&	p						O/A	O/A	O/A	O/A	O/A

EX STOCK

60/30V or 30-0-30V	2 x 30V Tapped Secs	60V	30V	£	P&P
0.5	1	0.5	1	6.72	2.09
1	2	1	2	10.25	2.20
2	4	2	4	13.17	2.53
3	6	3	6	19.05	2.64
4	8	4	8	21.72	2.75
5	10	5	10	27.46	3.19
6	12	6	12	31.32	3.41
8	16	8	16	44.04	4.12
10	20	10	20	51.28	4.40
12	24	12	24	59.09	4.89

30/15V or 15-0-15V

2 x 15V Tapped Secs Volts available: 3,4,5,6,8,9,10,15, 18,20,27,30V or 15-0-15V	30V	15V	£	P&P	
0.5	1	0.5	1	4.55	1.81
1	2	1	2	6.19	1.98
2	4	2	4	10.01	2.20
3	6	3	6	11.60	2.42
4	8	4	8	13.84	2.53
5	10	5	10	17.72	2.64
6	12	6	12	19.41	2.91
8	16	8	16	25.74	3.02
10	20	10	20	29.94	3.24
12	24	12	24	33.42	3.35
15	30	15	30	37.43	4.01
20	40	20	40	51.10	6.54

CASED AUTOS 240-115V

240V Cable Input, 3-pin 115V USA Socket Outlet	20VA	£9.85	2.03
80	13.38	p	2.14
150	17.34	&	2.58
250	21.13	p	3.57
500	34.66		3.57
1000	48.65		5.00
2000	86.70		6.13
3000	124.46		O/A

110V to 240V Cased Autos
Now available
12V LIGHTING
TRANSFORMERS
Full range

Send SAE for lists. Please add 15% to all items after P&P

BARRIE ELECTRONICS LTD
TELEPHONE: 01-555 0228 (3 lines)

electronize MICRO-PRESSURE CAR ALARM KIT



CHECK THESE FEATURES

- ★ Micro-Pressure intruder detection.
- ★ Operates on all doors and tailgate.
- ★ No door switches needed.
- ★ Automatically armed 1 minute after leaving vehicle.
- ★ 10 second entry delay with audible warning.
- ★ Sounds horn intermittently for 1 minute.
- ★ Easy fitting - only 3 wires to connect - no holes to drill.
- ★ Compact design can be hidden below dashboard.
- ★ Low power drawn from horn circuit - no supply connections.
- ★ All solid state Power MOSFET output - no relays.

This new design employs a unique pressure sensing system to activate the alarm. As any vehicle door is opened, air is drawn out, causing a minute drop in air pressure. A sensor detects this sudden pressure change and sets off the alarm.

Fitting is extremely simple. Only two wires connect to the horn circuit, switching the horn and also powering the alarm. The low power circuit draws less than 2mA. A single control wire connects to the ignition circuit or hidden switch to arm the system whenever the vehicle is left.

As with all Electronize kits everything is included, high quality components and clear, easy to follow instructions, and all for the lowest possible price.

MICRO-PRESSURE ALARM KIT	£11.95	Please add £1.00 postage & packing
ASSEMBLED READY TO FIT	£17.95	

Also Available
TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION
Extended CDI System

DIY PARTS KIT	£17.95	Please add £1.00 postage & packing
ASSEMBLED READY TO FIT	£23.90	

ELECTRONIZE DESIGN
2 Hillside Road, Four Oaks, Sutton Coldfield, B74 4DQ

INDEX TO ADVERTISERS

A & G Electronics	61	J.P.G. Electronics	61
A.C. Electronics	61	Kemsoft	64
A.D.M. Electronics Supplies	61	Keytronics	37
Andor Electronics	60	K-Tek	61
Astronomy Now	47	Labcentre Electronics	70
Barrie Electronics	70	Litesold	64
B.K. Electronics	IBC	London Electronics College	60
Blore-Barton Ltd	61	Magenta Electronics	10,11,60
Bull J.	61,63	Maplin Electronics	OBC
Cadsoft Systems	62	Mauritron Electronics	62
Cambridge Computer Science Ltd	61	Micro Systems	55
Circuit Distribution	IFC	Modern Book Co.	62
Classified Ads	60-62	National Component Club	54
Coles Harding	61	N.C.A. Designs	62
Component Solutions	45	Number One Systems	39
Compstock	17	Omni	60
Cooke International	61	Phonsonics	56
Cricklewood Electronics	56	PLS	60
C.R. Supply Co.	61	Program Now	62
Deansgate	60	Proto Design	62
Display Electronics	18	Radio & Telecommunications Correspondence School	60
Electronize Design	70	RMOS	61
Everett Workshop	59	Service Trading Co	48
Fraser Electronics	60	Sherwood Data	64
Greenbank Electronics	54	Soft Machine	17
Greenwell Electronics	26,60	Specialist Semiconductors	25
Hanney, L.F.	60	Spiretroniks	61
Happy Memories	59	Suma Designs	48
Hart Electronics	47	Technical Info Services	62
High Grade Components	30	T.K. Electronics	59
Jaytee Electronics	48	Ward Electronics	62

PLEASE MENTION PRACTICAL ELECTRONICS WHEN REPLYING TO ADVERTS

Labcenter Electronics

PC-B

The original budget priced PCB design aid for PC compatibles. Can you afford NOT to join the CAD revolution?

PC-B PRO

A PCB layout editor with all the power and versatility you could possibly want, but which you can learn to use within an hour. Features include: exceptional ease of use; ultra fast graphics; box copy/move/rotate/delete; pick and copy/move/delete; user extendable package library; user configurable object sizes; connectivity highlight; etc, etc.

PC-B AR

An auto-routing tool to use in conjunction with PC-B PRO. Features maze search algorithm with 25 or 50 thou grid.

ORDERING

PC-B	£69-95
PC-B PRO	£229-95
PC-B PRO/AR	£399-95
DEMO DISK	£5

All prices are inclusive. Please state EGA/VGA or PC1512 when ordering. We accept ACCESS.

14 Marriner's Drive, Bradford, BD9 4JT
Telephone: 0274 542868

OMP POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

OMP POWER AMPLIFIER MODULES Supplied ready built and tested.

OMP POWER AMPLIFIER MODULES Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. PRICE £33.99 + £3.00 P&P.



NEW SERIES II MOS-FET MODULES
OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor, >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB. Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB. Size 300 x 155 x 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB. Size 330 x 175 x 100mm. PRICE £79.99 + £4.50 P&P.

NOTE— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS, STANDARD— INPUT SENS. 500mV BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE)— INPUT SENS. 775mV, BAND WIDTH 50KHz, ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE:— INSTRUMENTS, P.A., DISCO, ETC.

- ALL MCKENZIE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. RES, FREQ. 80Hz. FREQ. RESP. TO 14KHz. SENS. 99dB. PRICE £28.59 + £2.00 P&P.
 - 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID. RES, FREQ. 70Hz. FREQ. RESP. TO 6KHz. SENS. 100dB. PRICE £34.70 + £2.50 P&P.
 - 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 103dB. PRICE £47.48 + £2.50 P&P.
 - 12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 98dB. PRICE £36.66 + £3.50 P&P.
 - 12" 100 WATT C12100TC TWIN CONE HIGH POWER WIDE RESPONSE, P.A., VOICE, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 14KHz. SENS. 100dB. PRICE £37.63 + £3.50 P&P.
 - 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 100dB. PRICE £64.17 + £3.50 P&P.
 - 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES, FREQ. 45Hz. FREQ. RESP. TO 5KHz. SENS. 100dB. PRICE £85.79 + £3.50 P&P.
 - 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 98dB. PRICE £53.70 + £4.00 P&P.
 - 15" 200 WATT C15200BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. PRICE £73.26 + £4.00 P&P.
 - 15" 250 WATT C15250BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. PRICE £80.53 + £4.50 P&P.
 - 15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 102dB. PRICE £94.12 + £4.50 P&P.
 - 18" 400 WATT C18400BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 27Hz. FREQ. RESP. TO 3KHz. SENS. 99dB. PRICE £167.85 + £5.00 P&P.

EARBENDERS:— HI-FI, STUDIO, IN-CAR, ETC.

- ALL EARBENDER UNITS 8 OHMS EXCEPT EB8-50 AND EB10-50 DUAL 4 AND 8 OHM. BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND**
- 8" 50 WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 97dB. PRICE £8.90 + £2.00 P&P.
 - 10" 50 WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 99dB. PRICE £12.00 + £2.50 P&P.
 - 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. RES, FREQ. 35Hz. FREQ. RESP. TO 3KHz. SENS. 96dB. PRICE £27.50 + £3.50 P&P.
 - 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO. RES, FREQ. 28Hz. FREQ. RESP. TO 3KHz. SENS. 92dB. PRICE £21.00 + £3.00 P&P.
 - 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES, FREQ. 26Hz. FREQ. RESP. TO 3KHz. SENS. 93dB. PRICE £32.00 + £3.50 P&P.
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 5 1/4" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 63Hz. FREQ. RESP. TO 20KHz. SENS. 92dB. PRICE £9.99 + £1.50 P&P.
 - 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 38Hz. FREQ. RESP. TO 20KHz. SENS. 94dB. PRICE £10.99 + £1.50 P&P.
 - 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 40Hz. FREQ. RESP. TO 18KHz. SENS. 89dB. PRICE £12.99 + £1.50 P&P.
 - 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 35Hz. FREQ. RESP. TO 12KHz. SENS. 86dB. PRICE £16.49 + £2.00 P&P.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W FM TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.49 + £1.00 P&P

FM MICRO TRANSMITTER (BUIG) 100-108MHz VARICAP TUNED COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATT, PRICE £8.62 + £1.00 P&P



3 watt FM Transmitter



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. VISA ACCESS ACCEPTED BY POST, PHONE OR FAX.



* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

OMP VARISPEED TURNTABLE CHASSIS.



★ MANUAL ARM ★ STEEL CHASSIS ★ ELECTRONIC SPEED CONTROL 33 & 45 ★ VARI PITCH CONTROL ★ HIGH TORQUE SERVO DRIVEN DC MOTOR ★ TRANSIT SCREWS ★ 12" DIE CAST PLATTER ★ NEON STROBE ★ CALIBRATED BAL WEIGHT ★ REMOVABLE HEAD SHELL ★ 1/8" CARTRIDGE FIXINGS ★ CUE LEVER ★ POWER 220/240V 50/60Hz ★ 390x305mm ★ SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE.

PRICE £59.99 + £3.50 P&P.

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500
PRICE £16.99 + 50p P&P

GOLDRING G850
PRICE £6.99 + 50p P&P

OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS:— MXF200 (100w + 100w)
MXF400 (200w + 200w) MXF600 (300w + 300w)

All power ratings R.M.S. into 4 ohms.

FEATURES: ★ Independent power supplies with two Toroidal Transformers ★ Twin L.E.D. Vu meters ★ Rotary indexed level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 Fan Cooled with D.C. Loudspeaker and Thermal Protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:— MXF 200 W19" x H3 1/2" (2U) x D11"
MXF 400 W19" x H5 1/4" (3U) x D12"
MXF 600 W19" x H5 1/4" (3U) x D13"

MXF200 £171.35
MXF400 £228.85
MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS, FINISHED IN HARDWEARING BLACK VYNIDE WITH PROTECTIVE CORNERS, GRILLE AND CARRYING HANDLE, INCORPORATES 12" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE: 45Hz-20KHz BOTH MODELS 8 OHM, SIZE H18" x W15" x D12"

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.99 PER PAIR
OMP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL.— £12.00 PER PAIR

OMP SLIDE DIMMER 1K WATT & 2.5K WATT

CONTROLS LOADS UP TO 1KW & 2.5KW. SUITABLE FOR RESISTIVE AND INDUCTIVE LOADS BLACK ANODISED CASE, READILY FLUSH MOUNTED THROUGH PANEL/CABINET CUT-OUTS. ADVANCED FEATURES INCLUDE:—

- ★ FULL 65mm SLIDE TRAVEL
- ★ NEON MONITOR INDICATOR
- ★ FLASH OVERRIDE BUTTON
- ★ HIGH & LOW LEVEL PRESETS
- ★ FULLY SUPPRESSED TO BS 800


SIZES:— 1KW H128xW40xD55mm
2.5KW H128xW76xD79mm

PRICES:— 1K WATT £15.99
2.5K WATT £24.99 + 60p P&P

PIEZO ELECTRIC TWEETERS—MOTOROLA

PIEZO ELECTRIC TWEETERS — MOTOROLA

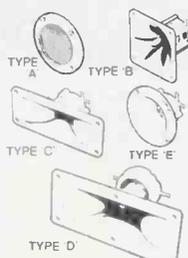Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.90 each + 50p P&P.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.00 each + 50p P&P.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each + 50p P&P.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £9.99 each + 50p P&P.


TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £5.99 each + 50p P&P.

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £3.99 + 50p P&P.

STEREO DISCO MIXER


STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following:—
3 Turntables (Mag). 3 Mics. 4 Line including CD plus Mic with talk over switch Headphone Monitor. Pan Pot L. & R. Master Output controls. Output 775mV. Size 360x280x90mm. Supply 220-240V.

Price £134.99 — £4.00 P&P

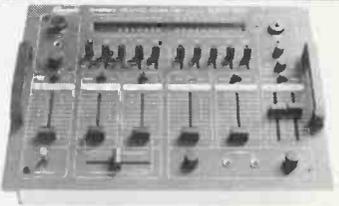

B. K. ELECTRONICS Dept PE
UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR
TEL: 0702-527572 FAX: 0702-420243


Superb Triple-Trace 20MHz Oscilloscope

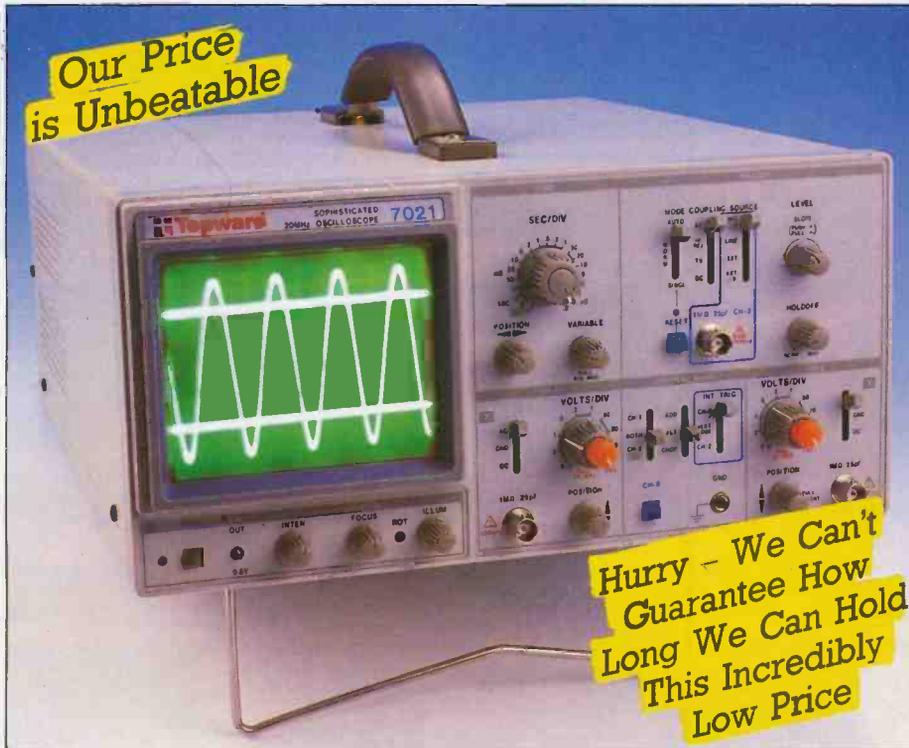

Precision laboratory oscilloscope. 3 Channels - 3 Trace. Sensitive vertical amplifier 1mV/div allows very low level signals to be easily observed. 150mm rectangular CRT has internal graticule to eliminate parallax error. X-Y mode allows Lissajous patterns to be produced and phase shift measured. TV sync separator allows measurement of video signals. 20ns/div sweep rate makes fast signals observable. Algebraic operation allows sum or difference of Channel 1 and 2 to be displayed. Stable triggering of both channels even with different frequencies is easy to achieve. 50mV/div output from Ch 1 available to drive external instrument e.g. frequency counter. A hold-off function permits triggering of complex signals and aperiodic pulse waveforms.

ONLY
£ 287⁴⁹
 XJ61R

40MHz Triple-Trace Oscilloscope

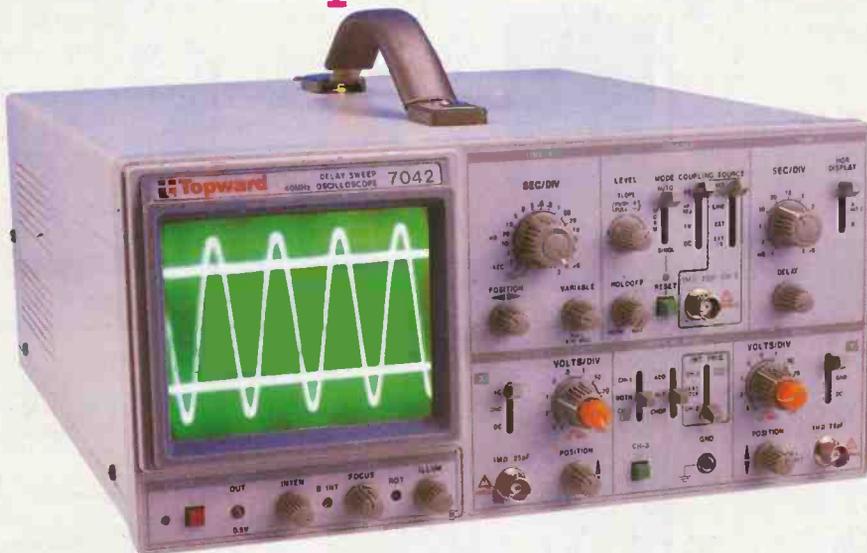

As above, but with 40MHz bandwidth and super bright 12kV tube even at the highest frequencies. This instrument also has a delayed sweep time base to provide magnified waveforms and accurate time interval measurement. Truly superb precision instrument.

ONLY
£ 499⁹⁵
 XJ60Q

✂

Order Coupon Send to P.O. Box 3, Rayleigh, SS6 8LR

Qty.	Description	Code	Price

Add carriage 50p

Name Total

Address

..... Post Code

I authorise you to debit my Credit Card account for the cost of goods despatched.

Card No.

Access, Amex, Visa delete as required

Ordering by Credit Card please sign

Expiry date of Credit Card

PE

Maplin ELECTRONICS

P.O. Box 3, RAYLEIGH, ESSEX SS6 8LR.



PHONE BEFORE 0702 554161
5PM FOR SAME DAY DESPATCH

ALL PRICES INCLUDE VAT.

All items subject to availability. Subject to availability both items will be on sale in our shops in Birmingham, Bristol, Leeds, London, Manchester, Nottingham, Southampton and Southend-on-Sea.

Alan 29 June 1980