
# <text>

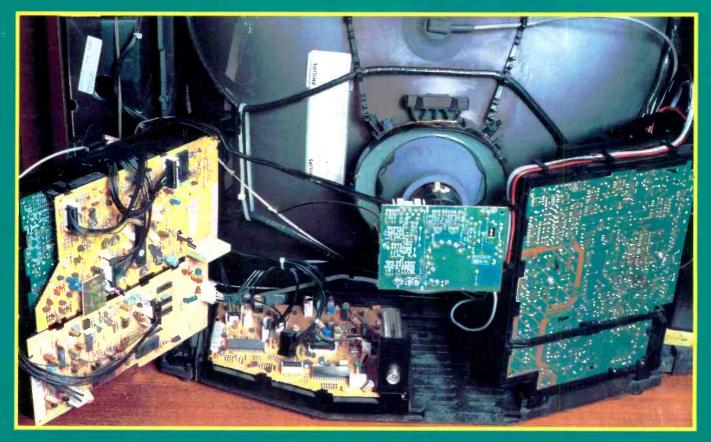

The B&O L/LX2500/2800 Chassis CD Laser Assemblies • DX-TV Test Report • The Trinitron Tube TV Fault Finding • VCR Clinic Characteristics of Op Amps




# For the Best Deal in Spares...


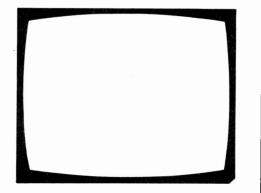
#### ELECTRONIC COMPONENTS AUTUMN '88

Over 400 Pages

Open an Account NOW. See Coupon Opposite ...



# TELEVISION

April 1989

#### Vol. 39, No. 6 Issue 462

On sale March 15th

#### COPYRIGHT

© IPC Magazines Limited, 1989. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

#### CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

#### **INDEXES**

Indexes to Vols. 36 and 37 are available at 80p each from the Editorial Office (address above).

#### SUBSCRIPTIONS

An annual subscription costs £18 in the UK, £21 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

#### **BACK NUMBERS**

Subject to availability, copies of issues published during the last 12 months are available at £1.80 each from Television, Vouchcheck Services, Unit A6, Poplar Business Park, Prestons Road, London E14 9LR. Please make cheques/postal orders payable to IPC Magazines Ltd.

#### **QUERIES**

We regret that we cannot answer technica queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in Television, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. Correspondents should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

#### this month

n	405	Leader			
e o o er al	406	The Sony Trinitron Tube         Nick Be           How the unique Sony Trinitron tube works, with an account of some of the improvements that have been introduced in recent years and detailed guidance on setting up.         Nick Be			
nt	408	Servicing Compact Disc Players, Part 2 This time a look at the various types of laser optica units in use, with an account of what the various ite each assembly do.	<i>Joe Cieszynski</i> I ems in		
e , , t,	413	Long-distance Television Reports on DX conditions and reception and news f abroad. Some excellent tropospheric openings prov fine start to the year.			
e	414	Next Month in Television			
C r,	416	TV Fault Finding Reports from Roger Burchett, Alfred Damp, Bob McClenning, Ian Bowden, Nick Beer, J. Olijnyk and J. L. Howard.	John		
nt s	418	Teletopics News, comment and developments.			
e d t	420	<b>Camcorder Servicing, Part 3</b> How a colour camera tube provides a composite luminance plus R/B carrier output and the way in which these signals are processed. Particular attention is paid to the various controls found in a colour tube camera and the effects they have on the display.			
s.	424	The B and O L/LX2500/2800 Chassis These sophisticated sets employ microcomputer corr via three bus lines and have an unusual chopper po supply circuit. Once these features of the receiver ar understood fault finding should not present many problems. How to tackle a set stuck in standby and summary of faults found to date.	ver		
Э	428	Letters			
, r 1	430	Strange Things Some unusual faults have cropped up recently.	Les Lawry-Johns		
6	431	The Philips VR6470 and Related Models A guide to the usual fault conditions found in these popular VCRs.	Barry Loughran		
l / t	434	Test Report: The Crotech 3133 Scope A thorough bench test of this 25MHz dual-trace oscilloscope shows that it's well suited to TV/VCR servicing.	Eugene Trundle		
6 r 1 6	436	VCR Clinic Fault reports from Philip Blundell, Eng. Tech., Alan Shaw, Paul Hardy, Eugene Trundle, Nick Beer, Ian Bowden and B. Ross.			
t r	438	A Look at Operational Amplifiers, Part 1 How these versatile devices work and the characteristics that determine circuit design.	Keith Cummins		
)	440	Service Bureau			
r D	441	Test Case 316			
•		OUR NEXT ISSUE DATED MAY WILL BE PUBLISHED ON APRIL 19			



pp. 403 411 412 (444 673 405 (como

<b>P. V.</b> 104 ABBEY ST Tel: 0254 36521/3 Telex: 635562 Gr Partners S. & B. 24hr. answering	REET, 32611/3 iffin G Cuckne	ACCRIN 390936 (For P.V. ell	GTON, LANCS BB5 1EE. ) New 0254	TRADE COUNTER OPEN MON-SAT 9am-5pm Fax No. \$ 395361		£7.50 + VAT up to 25K (except tubes). We do not despatch on Saturdays.	for any reason we are or as quickly as possible. fair and efficient service us a ring – we'll give yo need is not listed – we w change without notice. supply an equivalent. We need expiry dates t	S ARE ZERO V.A.T In the day we receive your order. If it of stock we will try to inform you We try our best to give a speedy, . V.A.T. invoice on request. Give us vervice. Please ask if what you all try to help. Prices are subject to in some cases we may have to for credit card orders.
VIDEO S SPECIAL P			WE ARE SOMETIMES A ONLY EX. RENTAL, WO PLEASE RING FOR PRIC 5+ MIX VIE	RKING VIDEO REC CE AND AVAILABII	LITY.	AMSTRAD SPAI VIDEO RECOROER VCR4600/52 1750 Pinch Roller (also 4500) 1226 Clutch (also 4500) 1227 Gear Holder (also 4500)	00 3.75 4.25 10.53	Please send large SAE (30p stamp) for our complete catalogue ORDERS WELCOME FROM
REPLACEMENT VID	EO HEA			PLEAS		1231 RF Clutch 7593 Belt Kit 1981 Cass. Lamp (also 4500) VIDED RECORDER VCR 7000	5.19	SCHOOLS, COLLEGE, GOVERNMENT ESTABL. SATELLITE TV
**         4500'5200'9000           PSF1 (VIP1000)         **           **         7000 SHSSR           **         765           **         751 3HSSV           **         3HSSV		RD111         3HSSV.           RD120         3HSSV.           RD121         3HSSV.           RD220         3HSSV.           RD225         3HSSV.           R2200         3HSSV.           R3300         3HSSV.           R3320         3HSSV.           R3320         3HSSV.           R3320         3HSSV.           R3350         3HSSV.           R3360         3HSSV.           R3660         3HSSV.	18.00 NV233 18.00 NV253 18.00 NV253 18.00 NV277 18.00 NV326 18.00 NV327 18.00 NV333 18.00 NV333 18.00 NV345 18.00	3HSSU2N           3HSSU2N           3HSSU2N           3HSSU2N           3HSSU2N           3HSSN	36.97 36.97 36.97 38.00 18.00 35.99 18.00 18.00 43.40 43.40 25.99 25.99 18.00	MD150143         Dew Sensor           MD150148         Loading Motor           MD150247         Keel Brack Unit           MD150287         Video Lamp           Video Lamp         Video Lamp           759         Pinch Roller           1059         Ider           7500         Bert Kit           1950         Cass. Lamp           VICEO RECORDER VCR 9000         1758           1758         Pinch Roller           1225         RF Clutch (also 4500)           1226         Clutch (also 4500)           1227         Gear Holder	3.75 1.80 1.45 0.45	ARE YOU READY? Please ring for prices or Sakura Remote Controlled Satellite Dish £215 We also have Signal Strength Meter
VS9300 3HSSV	18.00 H 18.00 H 18.00 H 18.00 H H	R4100         3HSSV.           R7200         3HSSV.           R7600         3HSSV.           R7610         3HSSV.           R7650         3HSSV.           R7650         3HSSV.	18.00 NV470 18.00 NV480 18.00 NV600 18.00 NV777 18.00 NV777	0 3HSSU2N 0 3HSSU2N 0 3HSS3N 0 3HSS4NB 7 3HSS3N	36.97 36.97 35.99 41.95 35.99	1227         Gear Holder           1981         Cass. Led (also 4500)           7592         Beit Kit (also 4500)           MD150821         Drive Belt           MD150820         Main Belt           Video Head (PSFI)         Video Head (PSF)	3.25 1.25	£45 Compass £6
W00         3H5SV           W01         3H5SV           W06         3H5SV           W16         3H5SV           W22         3H5SV           W23         3H5SV           W24         3H5SV           W23         3H5SV           W24         3H5SV           W23         3H5SV           W24         3H5SV           W30         3H5SV           W30         3H5SV           W31         3H5SV           W35         3H5SV	18.00 18.00 18.00 N 18.00 P 18.00 P 18.00 P 18.00 N 18.00 N 18.00 N	IR7700 3HSSV. IEC V760 PS3BS. V764 PS3BS. I830 PS3BS. I831 3HSSV. I832 3HSSV. I833 3HSSV.	18.00 NV861 NV200 NV300 NV300 NV750 19.00 NV752 19.00 NV757 18.00 NV781 18.00 NV817 18.00 NV817 18.00 NV817 18.00 NV821	00         3HSSN           50         3HSSN	18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00	NAT. PANASONIC VID VXP0243 PlayIdlerNV8600/8610 VXP0401 IdlerUnitNV33/3/366 VXP0344 IdlerUnitNV300 VXP031 IdlerUnitNV3000 VVP031 IdlerUnitNV3000 VVF031 IdlerUnitNV3000 VVF031/30/830/850	0 SPARES 1.10 1.08 1.22	RG59BU Cable (for short to medium runs 100 metres) £19.95 TR100 Cable 100 metres (for longer runs)
3V36         3HSSVA	18.00 P 24.00 P 24.00 24.00 S 47.00 S 47.00 S 18.00 S 18.00 S	V2300 PS3BS. V2400 PS3BS. ILF1 PS4B2S ILC5 PS3BS. ILC5 PS3BS.	19.00 19.00 19.00 <b>SHAF</b> 10 29.95 381 19.00 383 19.00 384	20 3HSSN 20 3HSSN	26.95 26.95	VXP0521 Idler Arm Unit NV370/430 830 850 VXP0325 Loading Gear NV333:2000/3000/7800 VXP0520 Load Gear Unit VDG0016 Action Gear NV333:2000/3000 VDG0017 Interim Gear NV333:2000/3000	4.08	£29.95 Screw on F connectors 35p (suitable for both type: of cable) F connectors crimp
HITACHI 7/T5500 3HSSHA 7/T0000 3HSSHA 7/T8040 3HSSHA 7/T8100 3HSSHA 7/T8100 3HSSHA 7/T8500 3HSSHA	25.50 S 25.50 S 25.50 S 25.50 S 25.50 S 25.50 S 25.50 S	ILC7 PS3BS ILC8 PS5B3S ILC9 PS5B3S ILC20 PS4B2S ILC24 PS4B2S ILC30 PS4B2S ILC30 PS4B2S ILC33 PS4B2S	19.00 385 39.95 386 39.95 387 29.95 387 29.95 481 29.95 481 29.95 482 29.95 482 29.95 2000 29.95 2000	3HSSSP 3HSSSP 3HSSSP 3HSSSP 3HSSSP 3HSSSP	26.95 26.95 26.95 26.95 26.95 26.95 26.95 26.95 26.95	Direct Rep. Video Bulb VXP0433 Play Idler Unit NV333/336 HITAGHING COSE VCR GEC 4000H/HITACHI 8000 Belt Counter (122) V654241	ARES	on (RG59) 24p F connectors crimp on (TR100)
TØ700         3HSSHA           T9000E         3HSSHA           T95003         3HSSHA           T95005         3HSSHA           T95005         3HSSHA           T9700         3HSSHA           T9900         3HSSHA           T19900         3HSSHA           T4000         3HSSH           T4200         3HSSH           T5000         3HSSH	25.50 S 25.50 S 25.50 S 25.50 S 25.50 S 25.50 S 25.50 S	LC40 PS482S LT50 PS583S LF60 PS583S LK95 PS583S L200 PS583S L200 PS583S L2000 PS38S2 L8000 PS38S2 L8000 PS38S2	29.95 3300 39.95 9100 39.95 9300 39.95 9300 39.95 9500 25.00 9600 25.00 9700 25.00	3HSSSP 3HSSSP 3HSSSP 3HSSSP 3HSSSP 3HSSSP 3HSSSP	26.95 26.95 26.95 26.95 26.95 26.95 26.95 26.95	Belt Take-up (239) V6354401 Idler FF/RWD V6413663 Lamp Tape Sensor V5762281 Play Idler Assy V6414221 Pressure Pinch Roller V6383762 Pulley FF/RWD V6383531 Relay V5641204	0.40 2.68 0.87 5.04 6.96 0.70 3.42	18p Crimping tools £19.95 Top grade crimping tools
775500 3HSSH 7711E 3HSSHB JRION /H1 3HSSN /H2 3HSSN	18.00 P 18.00 5	CANYO/FISHER VHP615 3HSSSF VHP910 3HSSSF 000 PS3BSF		REPLACEMENT HEAD AND GUARANTE JINE HEAOS 8900UB SLC9 3300/9700 a 9600 (upper assy)		VCR GEC V4100/HITACHI VT11 Bel 312 V5355601 Bel 313 V5355591 Bel 317 V5357531 Bel 318 V535581 Capstan Motor V5577355/6 Clutch Assembly	E 0.47 0.40 0.63 0.54 29.94 8.47	£29.95 See 'Aerial Equipment for Wall Brackets, Masts, etc.
USTIDA (31 PS3BT	30.00 P 30.00 D 18.00 D 18.00 6 25.00 6 30.00 2	PHILIPS           JV462         3HSSU1           4460         3HSSU1           5520         3HSSU1           5558         6462/3/	35.00         GENI           35.01         Sorryi           29.95         Sorryi           Sharp         Toshit           Hrack         Hrack           N         25.99           Sharp         Sharp           N         25.99           N         25.99           Folio         School           6560         6660           45.00         Amstr	i VT336 GEC 4004 9300/9435/9500 \$ V2000 \$ 1700 ad 7000	35.62 53.00 64.00 71.00 40.00	SERVICE MANUALS GEC-V4004 Hitachi-VT33E GEC-V4005H Hitachi-VT63	9.69 6.43	NEW PRODUCTS Nat. Pan. Service Manuals
BELT         KITS           Akai         VS9300/9500/9500         980           JVC         HR3300/3320/333         TCE 6989;5V00/SV16'           KVZ         Nat. Pan. NV70008/7         VY0008/7           VK3         Sony SLC5/7         VK4           Sony SL25/7         Sony SL2000UB         Sony SL3000UB           VK4         Sony SL3000UB         NK6           NK7         Sany 9300P         NK7	0 0/3360 SV22 00B	no. of bel	VHS (general purpose) Thom.JVC Sharn 381/383/3869/1004900.9 Sharp 0006/GEZZ VC300/387/48 6/496/581/5/8581 Sanyo Reel Drive Pulley 143-0-66 Hitach1F/F Idler 68869/71 (UT116 Philips VHS Idler 4822 522/203 30 Fisher/Siemens 143-0-4904 0090 Fisher/Siemens 143-0-4904 0090 Sisher/Siemens 143-0-4904 0090 Sisher/Siemens 143-0-4904 0090 Sisher/Siemens 143-0-4904 0090 Sisher/Siemens 143-0-4904 0090 Sisher/Siemens 143-0-4904 0090	LUTCH ASSY jetc. jetc. 500-0005/GEZZ 11/2/3 2 T0202/TD 1282 	4.95 2.20 2.20 3.50 3.50 4.50 1.85	Beit (259) V6355291 Beit (289) V6355482 Beit Take-up (213) V6354231 Capstan Motor V5577324 Uiter FF Rewind V68614711 Lamp Tape Sensor V5767131 Pay Ider Assy V6861482 Pulley FF/Rewind V6345173 Remote Control Handset V7084733	0.63 0.63 0.40 30.00 2.43 0.65 5.02 0.40 13.40	
VK8         Nat. / Pan.         NV2000B.           VK9         Nat. Pan.         NV86008/86           VK10         Toshiba V8600.         VK10           VK11         Sharp VC7300.         VK13           Sanyo VTC5000.         VK13         Sanyo VTC5000.           VK13         Sanyo VTC5000.         VK14           VK14         Sanyo VTC5000.         VK15           VK15         JVC HR7650/3V31.         VK16           VK16         Hitachi 5000         VK17	10/V011	6 1.7 7 1.5 6 1.4 5 1.5 2 1.5 5 1.8 3 2.0 6 1.7				(Gen. Hitachi Idler)		New Ferguson           Service Manuals           3V35         £2           3V38 Supp.         £1.5           3V39 Supp.         £1.5
KY18         Sharp 9300           KY19         Hitachi V18000 08300/8           K/20         Hitachi V111/33           K/21         Hitachi 9500           K/22         Sony SLC6           K/23         Sanyo 5500           K/24         Nat. Pan. NV300/NV33           K/25         Toshiba V7540           J/C/HR 7700/3V23         J/C/HR 7700/3V23	33.	5 1.4 5 1.4 3 1.0 6 1.5 3 1.1 6 1.5 5 1.9 2 0.9 4 1.7 3 1.1 5 1.4 5 1.2 5 1.2 1.2 1.2 1.2 1.2 1.2 1.2 1.2	JUC TC25/200001 06 16           JUC T22/24           JUC T22/24           JUC 3660/1100 /700           JAka VS9700           Sharp VC5000 6500           Sony T. C. General           5		-	GEC-2069 Y2370551 VIDEO LAMPS Nat. Pan. VHS Bulb (also Sharp) General Purpose VHS Bulb 3V23 with Plug Amstrad 4500 4600 5200 9000 Hitachi 9300 9500		3V48         £9.9           3V53         £9.9           3V54/5         £10.2           3V58         £10.9           3V59         £13.5           3V64/5         £13.0           FV10D         £7.9           FV11R         £3.9
K28         Amstrad         7000           KX38         Amstrad         4500,9000           KX39         Amstrad         4500,9200           VK29         Natsrad         4500,9200           VK29         Natsrad         4500,9200           VK29         Nat. Pan         NU777           VK30         Sony T9	0	3 1.4 32 5.1 4 1.0 6 2.2 4 1.2 0	5 VHS Drum Motor 9 VHS Capstan Motor 9 Sanyo 5000 Reel Motor 9 Sharp Reel Motor		25.50 25.50 12.95 19.50	IOLER TYRES 0.DIA I.DIA Sony 23.7 17.4 Sony 24.2 18	<i>WIDTH</i> 4.9 0.50 5.1 0.50 4.9 0.50	VIOE0 TAPES           SKC         E120 (VHS)         2.3           E180 (VHS)         2.4         2.4           E240 (VHS)         2.4         3.4
VK32         Sanyo 1100-1300-130           VK33         Ferguson 3V35-36           VK34         Ferguson 3V42-3-4-5-           VK35         Fisher FVHP710-716-7           VK36         Panasonic NV370-430           VK37         Hitachi 9300	8	0. 0. 1. 1. 0.	5 VIDEO CARE 9 Video Cleaning Tape VHS 0 Universal Copying Kit 0 Head Cleaner 9 Beta Eccentricity Gauge 5 Chamois Cleaning Sticks		8.23 7.50 0.96 57.92 0.25	Suny         23.7         17.4           Somy         24.2         18           Hitachi         31.8         25           Nat. Pan.         37.0         29           Nat. Pan.         31.2         25           Akai         26.0         20           JVC         39.3         32.8           JVC         33.0         23.9	3.9         0.52           3.1         0.56           3.9         0.50           3.9         0.56           4.0         0.56	E240 (VHS)         3.4           Scotch         E60 (VHS)         3.0           E120 (VHS)         2.8           E180 (VHS)         3.5           L750 (BETA)         3.6

<b>REMOTE HAND SETS</b>	AERIAL EQUIPMENT GENERAL LASHING KITS/ACCESSORIES	LABGEAR	INTEGRATED CIRCUITS
	6" Pressed Bracket	CM7261 P.U. 12.3 6 CM7262 P.U. 13.5 CM7265 UHE/WE 16.5	0 40028
TV/Video - TVR-1-MD1511910	6" Bracket with Kit (lashing kit)	CM7065 UHF/VH WB	8   HAL16L8CN
CTV 1409 – MD1409221 15. VCR 5200 – MD151175 17.	U   9" Bracket with Kit 2 DA	2   UM7253 Benind Set (Mains)	1 MAD0040 0.40
VCR 7000 – MD150583	0 Double Brackets with Kit 5.2	CM7243 Second Set Amp	3 MC1377 1.55
DECCA	0 13, 5" Cradle Bracket	CM7243         Second Set Amp         14.7           CM7033         Three Set Amp         18.5           CM7063         Dist, Amp         18.5           CM7063         Dist, Amp         49.9           CM9700         27MHz CB Suppressor         49.9           CM6011         Outdoor Spitter         8.6           CM9003:00 Flush Sing         Outlet         2.3           CM90017 Insuh Sing         Outlet         2.3           CM9010 Flush Sing         Outlet         2.3           CM9030 Flush Sing         Outlet         2.3           CM9010 Flush Sing         Outlet         2.3           CM9010 Flush Sing         Outlet         2.3           CM9010 Flush Sing         Outlet         3.8           CM9010 Flush Sing         Outlet         3.1           CM9010 Flush Sing         Combiner         3.2	MC1376         1.35           MC1376         1.15           MC1488P         0.75           MC1489AP         0.77
80/100 Non-Txt US8511 19.5	0 Standard Repair Pack	CM9700 27 MHz CB Suppressor	0.77 MC68008 17.97
101 Series Non-Txt US 8513	a j Corrier Plates	CM9003/00 Flush Sing. Outlet	ZX81 Rom
FIDELITY	Lashing Wire	CM9010 Flush Twin Outlet 2.4	5 Spec 48K Rom. 5.00 7 ULA2C210E ZX81 3.95 Spec 128K + 2 Rom 5 51
CTV 20R/22R/140R	Rawibolts	CM9033 6 Way Pass Spit	Spec 128K + 2 Rom
4 Button IR8876	1   Coax Plugs 0.18	CM0000 Flugh TV/FM Emulator 2.0	CU02990D1/C1 Dom 2 00
F14R 12 Button FD09156	1 Coax Plug Female		7 TC74HC04 0.86 TMS1000 8.95
Txt 32 Button IR8983	0 Attenuators	CM7057 Televerta Down UHF/VHF	TMS1000 8.95 TMM23128P-1951 10.66 ULA6C001E (Spec) 6.50
G.E.C. 4001/Hitachi 9300	Tape Sm 0.32 Lg	CM7274 4 Way Dist, Amp. 26 1	I ULA2G007 (M/D) 3.24
GC56520831/C1404H-C1658H-IR8314	WALL BRACKETS	CM7082 UHF/VHF Dist. Amp	ULA1H035E (Ram Pk)
GCA 512220/C1653 22.0 GCA 512230/C2086H-C2087H	12°18K	CM7080/10 UHF MHA	Z80A CPU 1.70 Z80A/CPU 4.50
GCA 514620/C2089H-C2090H IR8823	9" Welded		20RA043 11.25
C2290H, C2889 GCA 510710/C2067H-IR8456	18" T&K	Universal No. 1 Clamp	SN7438N
GCA 510870/C2069-C2269H-IR8877	24" T&K	SB11 Splitter	74LS32 0.90
GRUNDIG RTP05/VRCIR138 – TP8-120-120E	1" × 1"	C0811 Outlet	74LS157 0.78 74LS132 0.63
TTP06/IR107N - TP160-160E 13.5	2" × 2"	PU1300 MHA 9.00 Diplexers	74LS260 0.83 Ram 2114 2.31
RTP07/R380N - TP200-300-390 13.5 RTP20/VRC112 - TP16-21-21VHR 13.5	J Bolts	Matched Transformer 2.83	251641-02 POA 2732 3.30
RTP400/401 IR401 – TP400VT-500VT 13.5 VRC 204 U.S. – TP12 13.5	2" U Bolts	XS04 4 Way DA	2764 3.75 27128 4.95
IR 8613 TXT TP400TT 13.5	UHF TV AERIALS 10 Element State Group A, B, CD, WB	Super Set Top Aerial	27256 5.90 Ram 4118 2.92 Ram 4116-4 1.10 Ram 4116-2 1.10
GRANADA	18 Element 4,12	Traveller Aerial	Ram 4116-4
Universal IR8450	DIY Aerial Pack 10 Ele, 3ft Mast, Coax Fittings	XG8 High Gain Aerial	Ram 4116-2 1.10 8249 3.00
CVC 32 RG15-US8573	VHF/FM AERIALS	Power Sensor Aerial with Amp	8247
CVC 45 - RG5-US8262	3 Element	Loop Aérials 1.00 Coax Cable S540 100m 33.70	BBC UID ULA
RG 306 – With Fine Tune IR8650	Omni Directional (Round)	TELESCOPIC AERIALS	41256-15 8.95 6502 Commodore 3,50
J.V.C.	MASTS 3 ft Crank L or S Shape	Toshiba Closed Length 206mm 1.55	6522 4.00
TP 843/Txt IR170	6ft 1"	NEC 252mm 1.88	6510 Commodore 7.07
G11 Txt IR8435/IR170/843	10 ft 1.5"	JVC 195mm 1.67	6561 Commodore 7.74
G11 Txt US 31 Button 691-17181	14.41	Sanyo 150mm 1.74 Sanyo 65mm 1.62	6569 Commodore
G11 Non Txt US 8263	Plastic Single	Sony 235mm 2.18 Sony 160mm 1.55	8360 Commodore 19 61
G11 2 Function US 8518	Metal Single 8 45	Hitachi 237mm 1.55 Hitachi 300mm 1.67	8701 Commodore 5.46 906114 Pla. Comm. 4.51 901225 Cha. Rom. Comm. 3.37
KT3/K30 Txt Ir8420	Metal Double 0.88	Aiwa 00mm 1.32	901226 Bas. Rom. Comm. 8.71
(Replaces RC5 Series)	OUTLET BOXES Surface Single	Sharp AANTR00017CEZZ 245mm 2.17	901227 Ker. Rom. Comm. 6.63 ZTX182/BC182
SONY	Surface Twin 1,10		777213 0.15
SLC5 – RM 75T	Flush Single	Ribbon with FM plug	ZTX214
SLC7 – RMT 200	Flush Twin	noboli witi otax piug	ZTX551 0.39 ZTX551 0.39 ZTX650/1 0.27
THORN/FERGUSON TV REMOTES	LEADS	ELECTRICAL PLUGS SOCKETS	ZTX750
The following TV remotes are exact replacements for Thom sets and cover a wide range of chassis inc, TX9/10 90/100, Please state	LWITTY W/F U.D.	Safe Block Mains	1524/2
model number of set or original hand set number.	10M Fiv 1.90	C3W 3 Pin 10A Flex Connector 1.50 TS1 13A Single Trailing Socket 1.40 TS2 13A Twin Trailing Socket 2.65	Markey and Bak da data
Order	I FIG 8 Mains Leads 0.62	4 Way 13A mains connector	We have not listed our full range IC's. These are a few of our new
Type Type T651 M739 All One	Computer to TV         10           S Pin Din to 5 Pin Din         0.98           TA81 Car Battery Thom 1691         4.47           T 451 Car Battery Thom 1615         35	13Amp Plugs         0.48           Surge Protector Plug         12.50           320A Single Gang 13A Socket         1.30           3208 Single Switched 13A Socket         1.95	types. Please ask for catalogue for full list of ICs and Semis.
T652 M738 Price SAME DAY DESPATCH T653 M737 FAST FAID FEDICIENT	TA51 Car Battery Thom 1615	320A Single Gang 13A Socket	
T716 M737 13.00 CEDIACE	Car Battery Philips 3.95 Scart Leads 2M (Open End) 2.50 Scart Plugs 1.95	320C Two Gang 13A Socket 2.53 320D Two Gang Switched 13A Socket 3.02	AN5620
T718 US8517	I SCATL SOCKETS	3200 Two Gang Switched 13A Socket         2.53           3200 Two Gang Switched 13A Socket         3.92           1thermational Travel Plug.         3.50           3202 One Gang/One Way Switches         0.60	STK5326
T719 M737 Addis T720 M739 We cannot advertise our	Scart to Scart Lead	320G TWO Gand/ TWO WAY SWITCHES	STR5401
T721 M737 complete range of products.	Test Lead Kit	3 Way Mains Adaptor	TAD100
T724 M739 something which is not listed,	CABLES Antiference Coax 100m S540 33.70	COMPUTER ACCESSORIES	TBA673D 2.50 TBA2800 1.60
T725 M750 ie: Stationery, Styli, Axial/ T731 M738 Radial Electrolytics, Mixed		DISKS	AN6520N         2.88           LA7800         3.75           STK5481         6.50           STR5420         5.80           TAJ100         2.82           TAJ100         2.82           TBA6730         2.50           TBA6730         5.50           TDA1670         3.60           TDA1870         6.46
1732 M739 Dialectric Caps., Polyester 1733 M738 Caps., Carbon Resistors,	4 Core Security Cable (100m) 5.55	Goldstar 5.25" Floppy Disks 2DD DS/QD (Box 10)	TDA2005
T734 M734 Wirewound Resistors.	/ 5H Coax Lable (100m) Low Loss         13.60           / 7SR Coax Cable (250m) Low Loss         32.75           4 Core Security Cable (100m)         5.55           6 Core Security Cable (100m)         7.94           8 Core Security Cable (100m)         7.94           9 Core Telephone Cable (100m)         9.99           4 Core Telephone Cable (100m)         13.28           3402 3 Core Round 13amp (50m)         28.21           1362 3 Core Round 6amp (100m)         15.475           2242 2 Core Round 6amp (100m)         15.475           4 Core File Lobe (100m)         70.82	Goldstar 31/2" Diskettes HF 2DD DS/DD (Box 10)	I DA2005
1736 M739 Filament Lamps, Thermistors, 1737 M737 LEDs, IC Sockets, Floppy	6 Core Telephone Cable (100m)	Unbranded 3 <sup>1</sup> /2" Diskettes DS/DD (Box 10)	TUA3651
1738 M738 Discs, Computer Cassettes, 1739 M739 Thom New Life Tubes	3402 3 Core Round 13amp (50m)	DS/DD (Box 10)	TDA3653AQ
T740 M740 (collection only), New Mono	2242 2 Core Round 6amp (100m) 15.47 4 Core Flat Cable (100m) 20.82	STORAGE BOXES 3 <sup>1</sup> /2" Library Case (10)	UPC577 2.46
T742 M742 Tubes, Crystals, Cables (post T748 M748 charges extra), Aenal	Twin Core Cable Screened (100m)	Lockable Box Holds	UPC577 2.46 UPC1378 2.50 UPC5743 3.75 UPD8048 0.93
T750 M750 Equipment, Electrical Plugs/ T769 M739 Sockets, Components for	1 Same Commission Street Street Area Street	(40 × 3/2") (20 × 3")	UPD8048 0.93
T770 M739 Sinclair, Amstrad Security	Microphone (100m) E 26	COMPUTER CASSETTES	
T772 M742 Products, Satellite Dishes and T773 M740 Accessories.	F041 2mm Loudspeaker Cable (100m) 5.53 CCPU2 Twin Pick Up 100m 9.95	C15	DON'T FORGET WE HAVE A FULL RANGE OF SECURITY PRODUCTS INCLUDING
T775 M739 T778 M738	Colour Coded (100m)	Special Prices on 20 or more	PRODUCTS INCLUDING
	3183Y 3 Core 15amp upt 3kw Flexible 1.5 sq mm	AUDIO CASSETTES Altai C90 0.25	NEW CASTLE CONTROL PANELS.
THORN VIDEO REMOTES	3183Y 3 Core 10amp upto 2kw	IDK D60 0.70	ASK FOR CATALOGUE
3V231.R. 8817	6491X Earth Green/Yellow 6mm 39.60	TDK D90 0.90	
3V351.R. 8946	6242Y Grev Lighting	AUDIO SPARES CASSETTE HEADS	DV
P.R.C. 6000	Twin/Earth 1mm	Mono/Record/Playback 4 22	<b>T</b> .V. TUBES
Programmable remote control unit will operate most infra-red equipment	CABLE TIES	Notification     4.32       Stereo Playback     4.79       Stereo/Record/Playback     4.99       Stereo/Record/Playback     6.90	TEL: 0254
REMOTE REPAIR KITS	Up to 25mm Diam. (100)	Stereo/Record/Playback/Dolby	36521 24 hour
Includes Foil/Buttons/Inst.	TV WALL BRACKETS	MOTODE	32611 answer
KT3/K30 Without Txt	P5245 Teletwist (12"-20")	6v MD6515 (Clockwise)	390936 phone
RC 5352 Range	P6041         11tite         Twister         14,08           P5218         Swivel and Titt         Bracket         24,67	9v (Anti Clockwise)	TELEX: 635562
REMOTE CONTROL TESTER	Heavy or hulting items such as askis will be seek to use 1.11	MU LUNS         4.95           6V MD6515 (Clockwise)         4.95           9v MD6516 (Clockwise)         4.95           9v (Anti Clockwise)         4.95           12v (M12517 (Clockwise)         4.95           12v         (Anti Clockwise)         4.95	GRIFFIN G (for P.V.)
a new device which tests infra red equipment	Heavy or bulkier items such as cable will be sent by overnight carrier at £7.50 + VAT	EXPORT ORDERS WELCOME	FAX No. 0254 395361

**TELEVISION APRIL 1989** 

ŕ

i -----

\_

section of the local division of the local d

-

¢

y.



#### **TV SERVICE SPARES**

#### SATELLITE T.V.

ON DEMONSTRATION AT 172 WEST END LANE NOW! - ENQUIRIES WELCOME

**PHILIPS SPARES G8 PANELS** (Tested) Power £12.50, Scan £15.00, Signals £15.00 p.p. £2.50. **KT3, K30 PANELS**, tested, exchange: Sound, power, bridge rect, frame, RGB £7.50 each. Decoder (Non-text) £10.00 p.p. £1.50. **G11 PANELS** (tested), frame, IF, decoder £12.50 each. p.p. £2.00. Scan £15.90 p.p. £2.80. FOwer tested exchange £18.00 p.p. £2.80. **G11 PANELS** EX-RENTAL (untested) Scan, Frame, Decoder £2.50 p.p. £2.00. **G11 IF PANELS** (Lested), less Tuner £1.60 p.p. £1.30. **G11 IF PANELS** (new) less Tuner £1.60 p.p. £1.30. **G11 IF PANELS** (new) less Tuner £1.60 p.p. £1.30. **G11 IF PANELS** (new) less Tuner £1.60 p.p. £1.30. **G11 GPOS** Touch Tune Channel Selector (replaces old type) incl. Instructions £20.00 p.p. £1.80 G11 6POS Touch Tune Channel Selector (replaces old type) incl. Instructions £20.00 p.p. £1.80 G9 POWER SUPPLY UNIT £5.00 p.p. £2.30. G8 6 Position Channel Selector (sloping buttons) £2.50 p.p. £1.00. HANDSETS (new replacements) p.p. £1.50. G11 ULTRASONIC non-text £19.50, infra-red text £19.50. Others available. KT3 non-text (RC4001), KT3, K30 Text £19.50. HAMDSETS EX-RENTAL, TEXT UNTESTED. KT, TEXT/VIDEO TYPE £3.50 ref f1 00 p(p. £1.00. MANUALS p.p. 80p, G11, K35, 2A **£3.50.** KT3 **£4.50,** CTX-E, CTX-S, CF1 **£1.50** KM(K40 SYSTEM 4 **£3.50** THORN/FERGUSON SPARES 8000, 8500, 8800, 9800 PANELS tested, exchange. Power £8.80, Frame, Decoder £10.00 p.p. £2.30. 9000 Series IF/Decoder tested £10.00 p.p. £2.30. TX9 Panels complete & tested £28.00 exchange (shop only) TX9 Panels ex-factory for small spares includes IC's & semiconductors, etc. £3.00 TX9 Panels ex-factory for small spares includes IC's & semiconductors, etc. 23.00 p.p. £2.00. TX9 panels salvaged ex-factory for spares incl. electronic & mains transformer. **58**,50 p.p. £3.00. TX9/TX10 Facia, control panel incl. infra-red receiver **58**,50 p.p. £2.00 TX10 Focus control **28**,50 p.p. £1.00. TX9/TX10 Saw filter IF panel £5.00 p.p. 80p. TX9/TX10 Remote & tuning control panel 1515 (incl. SAA5012) £7.50 p.p. £1.80. REMOTE CONTROL HANDSETS — TX9, TX10 inred-red text £19.50 p.p. £1.20. ITT SPARES: CVC30 series convergence & purity panels £2.50 p.p. £1.50. CVC30 series panels surplus (untested) £2.50 each, CMP31, CMF31, CMA30, CM532 p.p. 80p, CMD33 p.p. £1.80. CVC20/30 series chassis for small spares (shop only) £2.50. BUSH SPARES: 720/T22 panels, tested, exchange, power scan drive £18.00. Scan £25.00 p.p. £2.50. T20/T22 touch tune panels + controls £3.50 p.p. £1.50. GEC SPARES: 20AX MKII line time base £18.00 p.p. £2.00. Power (PC778) tested exchange £18.00 p.p. £2.00. SONY SPARES: ON/OFF SWITCH 21mm or 26mm, spaced holes, universal Sony on/off **£4.20** each p.p. 80p. HANDSETS (New Replacement) RM-604, 606, 613, 615, 630, 632, 635 **£19.50** p.p. £1.00. TELETEXT DECODER PANELS (tested) — Muhard VM6101 Type £25.00, Philips KT3, K30 £20.00 p.p. (2.30. MULLARD VM6230 teletext decoder (similar to VM6101) plus additional Prestel unit, VM6330 & Line Coupler £20.00 p.p.£3:00. VARICAP TUNERS: Grundig 8630 series £5.00 p.p. £1.00. U321, U322/ NSF204, ELC1043 (equiv), SC4, VHF NSF203 £7.80 p.p. £1.80. UHF/VHF UV411 £10.80 p.p. £1.00. LOPTS New and guar. P/P £1.50, Bobbins 80p. 
 R. B. M. T20, T22
 £9,80

 R. B. M. T20, T22 Bobbin
 £5,60

 DECCA Bradford (state Mod No)
 £8,80

 FIDELITY ZX2000, 3000 (Not 22") £15,50
 GEC 2110 series

 GEC 2110 series
 £10,60

 TTT CVC 51 to 9, CVC 20
 £9,80

 TTT CVC 51 to 9, CVC 20
 £9,80

 TTT CVC 45
 £9,80

 PHILIPS G8
 £8,80

 PHILIPS G9
 £7,80

 PHILIPS G5
 £27,00

 PHILIPS CTX-E
 £22,50

 PHILIPS CTX-S
 £22,50
 TRIPLERS: THORN 9000 £8.80. **TRIPLERS:** THORN 9000 £8.80. UNIVERSAL (best quality) £7.80. CONTINENTAL TVK & BG RANGE (quote exact no.) replacements £13.80 DECCA/TATUNG £7.80 p. p. £1.50. THORN 1500 30R5 stick £1.50 p.p. &0p. Others available. 6.3V CRT Boost Transformers for Colour & Mono £5.90 p.p. £1.40. 455 CRYSTALS for Remote Control Handsets. 4 for £1.00 p.p. 50p. VHF to UHF Converters £26.50 p.p. £2.50. CALLERS WELCOME AT SHOP PREMISES THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15% b) VISA Telephone 01-794 8751, 794 7346 MANOR SUPPLIES 172 WEST END LANE, LONDON, NW6 1SD

PLEASE ADD VAT 15% TO ALL PRICES INCL P+P

 $\sim$ 

.

and the second s

-

### WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. G.G.L.COMPONENTS PO BOX 72, UNIT 7, SOUTH JOHN STREET, CARL

.

-----

**BUY WITH** 

	TS WITH US								
CAPACITORS	INTEGRATED	TYPE	PRICE (E) 1	TYPE	FAX (0228) 5'	IDIZ/ INE O/P TR	ANS	TRANSISTOR	s type pric
1UF at 250V	CIRCUITS		4.95	TDA2530 TDA2532		CA 100	8.30	TYPE	PRICE BU807
10UF at 250V				TDA2540	1.70 PERG	USON 1690/1		BC107	BU907
2011F -+ 25/61 An AN	1303	STR4090		(DA2541 TDA2560		USON 1790/1		BC147 BC148	
22  Fat2501/ 655 AN	1303			TDA2576A		USON TX9		BC148 BC307	
17UF at 250V	I318B.39	STR5010	I3A <b>6.50</b> <u>T</u>	TOA2577	2.95	USON TX90 (14		BC327	
00UF at 250V	7145M 2.95			DA2578A		USON TX90 (20		BC328	
на	1339A		T	TDA2581		USON TX100 9		BC337	
	1366W 1.85			[DA2582	105	USON TX1001		BC338	12 CCOC/A
STATE DELOC FIA	1366WR1.85			(DA2591/3	1.95 FIDEL	LITY ZX2000		BC360 BC546	
V101 40 FIA	1374			ι UA2394 ΓDΔ2595		Mod.)		BC547	
Y133	1392	TA71936	4.50 T	TDA2600		LITY ZX300		BC548	10 T9064V
Y1/9 HA	1397	TA7205/	P	TDA2611A		ITY ZX 22"/26" .	11.30	BC557	
1223 HA	13001 4.50	TA7222F	' <b>1.85</b> ‡	DA2653A				BC558	10 TIP31C
Υ227	13008 12.95	TA7227.		DA20000		RI CT4/5		BC639	25 TIP32C
	12011.25	TA7270.		TDA3330		VC20		BC640 BD131	
	1230	TRA1005.	<b>3.3</b> 0 T	TDA3540		VC25/30/32 Impact 80		BD132	50 TIP112H
ν40U/	44402.75	TBA120		DA3541		PS G8		BD222	
15408 <b>20</b> LA4	4445	TBA800	° <b>85</b> T	TDA3561A		PS G11		BD225	JU 100007A
LA4	4460	TBA8103	S1.25 ⊺	TDA3562A		PS KT3		BD237	4U 2SC1034
	4461	TBA820.		DA3565		PS K13 PS K30		BD238	
2X61C (1.3 Watt) 3V3, 4V7, LA7	7800	1BA820		TDA3571 B/Q. TDA3650				BD278A BD437	
	7801	TRACE	2X <b>2.25</b>	DA3651		PS CTX 14"/16" PS CTX 20"		BD437 BD438	40 2SC3156
(1, 10V, 11V, 12V, 13V, 15V, MC V 20V 24V 27V 30V 33V, MC	13002	TRA144	G <b>235</b> †	DA3651AQ			0.00	BD677	65 2SD725
V, 20V, 24V, 27V, 30V, 33V, MC V, 47V, 56V, 62V, 75V, SAV 0V, 110V, 120V, 130V, Pkts SAV	A1250	TDA440	C	[DA3652	2,95 HDM	T20/22A		BD701	95 2SD870
0V, 110V, 120V, 130V, Pkts SA/	A12514.95	TDA1020		DA3653AU	4.55 SHAR	P C1410		BD707	95 2SD1398
5 per value	A30273.95	TDA1035	T <b>2.40</b> †	DA4500		OFF SWIT	CHES	BD807	7805
SA/	A5000A	TDA1037	<b>1.95</b> Ť	DA4503	4.65	a 80/100		BF337 BF338	
	A5010	TDA1044		DA4600/2 DA4600/2D		son TX9/10 (Ri		BF422	
ntinental 20AX Focus 8.95 CAA	A50124.95 A50305.95	TDA1151	<b>1.25</b> T S <b>1.80</b> <u>T</u>	DA4600/2D DA7270		son 1X9/10 (Hi son TX90 (Rem	1 75	BF423	
ntinental 30AX Focus 8.95 SAA	A5050		P 265	DA8180		son 1X90 (Rem y AVS Series	4 50	BF458	
CCA 80	F1039P 2.75	TDA1190	Z	DA8190	2.80	y AVS Series y CTV140		RF460	95 THREEDO
CLA 100 7.35 SL4	70/1DP	TDA1470		DA9503 JPC1031H		γCTV140 γCTV14R		BF470	
CCA 120/130	80	TDA1506		JPC1181H		γCTV14R γCTV14S		BF757 BF871	/U ELC 1043/06
CVC45	90 <b>2.90</b> 430 <b>1.95</b>			JPC1182H		y c i v i 45 lig CUC731		BR103	
ILIPS G8 550	430			IPC1185H	250 01010	ni CPT2650		BR303	1.95 U322
ILIPS KT3	432		A	PC12650		s G8	4.95	BT151/800	1.15 U341
M T20/22A	76660N65		A	JPC1378H				BU126	1.50 U343(coax skt)
URN 9000	471C6.95	TDA1870		IPC1382	4.35	s G11 s G11 (Rem)		BU205	
016	(077 <b>6.95</b>	TDA1908		JPC1394C		s GTT (Rem) s KT3		BU208A	U411
	(2129 11.95			0040PU				BU208D BU326A	1.30 LIE5-831E
	(433	TDA2002				s KT/CTX (Rem)		BU407	
	(435 <b>5.95</b>	TDA2003				11 (Rem) 720/22A 3K3 Vo		BU407D	
	(437 6.95		9.55					BU426A	
, 1.25A, 1.6A, 2A, 2.5A, STK	(439 7.50	TDA2020		6 Pin Dil-Dil		(V1612 (Rem)		BU500 BU508A	- FIDELITY ZX(220/385)
	(459 8.55	TDA2030		8 Pin Dil-Dil	18 50NV K	(V2022 (Rem)	4.76	BU508A BU508D	.1.95 PHILIPS C11/470/2501
mm Q/B: (Pkts of 10) STK	(461	TDA2170		4 Pin Dil-Dil		g 160/161		BU526A	
0MA, 630MA, 800MA, 1A, STK , 2.5A, 3.15A	(463	TDA2270		8 Pin Dil-Dil		g 165 Universal		BU536 BU705	
us Unit TX 10	HM6251 HM9032 VIDEO SPARE V4000/VT8000	5.95	Kit (Genuine) Cassette Lamp Pinch Roller Play Idler (Genuine)		VTC5000/5300 Loading Roller Pinch Roller Reel Idler (Genuine)	8.50	Channel Ba Pinch Rolle	mp	Sharp VC8300 Sharp VC9300
h Button TX9 16.95	Capstan Motor	31 05	Reel Idler (Genuine)		Reel Motor (Genuine)		rewind Idle	er3.50	Universal
h Button TX10	FF/Rew Idler		Video Head		Video Head		VC9300/381		
Choke TX9	FF/Rew Pulley		NV7000/7200		FVHP615		Capstan Mo	otor	
er14.95	Pinch Roller		Complete Maintenance		Gear Idler Assembly		<b>Cassette La</b>	mp1.95	VIDEO HEADS
2/100	Play Idler	4.50	Kit (Genuine)		Pinch Roller		Pinch Roller	3.95	Alba 4000
0/P Trans TX90 14" 19.75	Video Head		Cassette Lamp		Reel Idler	E 0E		Senuine)	
0/P Trans TX90 20" 19.75							Reel Idler (C	(Genuine) 47 co	
	V4001/VT9300/9500				Video Head		Reel Motor	(Genuine)	Amstrad VCR4600
	Capstan Motor		Pinch Roller Play Clutch (Genuine)		Video Head		Reel Motor Unlock Ass	(Genuine)	Amstrad VCR4600 Amstrad VCR7000
0/P Trans TX100 110° 20.95	Capstan Motor FF/Rew Idler		Pinch Roller		Video Head	24.95	Reel Motor Unlock Ass Video Head	(Genuine)17.50 embly	Amstrad VCR4600 Amstrad VCR7000 Amstrad VCR9000 Ferguson 3V00/22/29/39
0/P Trans TX100 110° 20.95 1s Trans. (TX90) 17.95	Capstan Motor FF/Rew Idler FF/Rew Pulley		Pinch Roller Play Clutch (Genuine)		Video Head SERVICE MAN (All Genuine	24.95 IUALS	Reel Motor Unlock Assivideo Head	(Genuine)	Amstrad VCR4600 Amstrad VCR7000. Amstrad VCR9000 Ferguson 3V00/22/29/39 Ferguson 3V32
0/P Trans TX100 110° 20.95 Is Trans. (TX90) 17.95 Iff Switch (Remote) 1.75	Capstan Motor FF/Rew Idler FF/Rew Pulley Pinch Roller		Pinch Roller Play Clutch (Genuine) Reel Idler (Genuine)		Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete	24.95 IUALS	Reel Motor Unlock Assivited Video Head VC481 Capstan Mo	(Genuine)	Amstrad VCR4600 Amstrad VCR7000 Amstrad VCR9000 Ferguson 3V00/22/29/39 Ferguson 3V32 Ferguson 3V42/44/45/55
0/P Trans TX100 110° 20.95 is Trans. (TX90)	Capstan Motor FF/Rew Idler FF/Rew Pulley Pinch Roller Play Idler		Pinch Roller Play Clutch (Genuine) Reel Idler (Genuine) Video Head		Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX10 Complete	24.95 IUALS a) a27.95 te38.95	Reel Motor Unlock Assivited Video Head VC481 Capstan Mc Pinch Roller	(Genuine)	Amstrad VCR4600. Amstrad VCR7000. Amstrad VCR7000. Ferguson 3V00/22/2/33. Ferguson 3V32 Ferguson 3V42/44/45/55. Fisher FVH520/615/20.
0/P Trans TX100 110°20.95 Is Trans. (TX90)	Capstan Motor FF/Rew Idler FF/Rew Pulley Pinch Roller Play Idler Video Head		Pinch Roller Play Clutch (Genuine) Reel Idler (Genuine) Video Head		Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX10 Complet Ferguson TX85	24.95 IUALS a) a27.95 te38.95 9.95	Reel Motor Unlock Assivited Head Video Head VC481 Capstan Mc Pinch Rotter Reel Idler (G	(Genuine)	Amstrad VCR4600. Amstrad VCR9000. Amstrad VCR9000. Ferguson 3V00/22/29/39. Ferguson 3V32. Ferguson 3V42/44/45/55. Fisher FVH520/615/720. Hitachi 8000/3300/9500.
0/P Trans TX100 110°20.95 Is Trans. (TX90)	Capstan Motor FF/Rew Idler Pinch Roller Play Idler Video Head V4100/VT11E/VT33E	31.95 	Pinch Roller		Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX10 Complete Ferguson TX85	24.95 IUALS e) e	Reel Motor Unlock Assi Video Head VC481 Capstan Mc Pinch Rotler Reel Idler (G Reel Motor	(Genuine)	Amstrad VCR4600. Amstrad VCR7000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/85/5. Fisher FVH520/615/720. Hitachi W01/330. Hitachi VT11/33E. Panasonic NV230.
0/P Trans TX100 110°20.95 s Trans. (TX30)	Capstan Motor FF/Rew Idler FF/Rew Pulley Pinch Roller Piay Idler Video Head Video Head Va100/VT11E/VT33E Capstan Motor (VT11E)		Pinch Roller Play Clutch (Genuine) Reel Idler (Genuine) Video Head REMOTE CONT Ferguson TX9 U/S Basic Ferguson TX9/10 N/Text.		Video Head	24.95 IUALS a	Reel Motor Unlock Assi Video Head VC481 Capstan Mc Pinch Rotler Reel Idler (G Reel Motor	(Genuine) 17.50 embly 35 23.95 xtor 22.95 r 3.95 senuine) 3.95 (Genuine) 18.50	Amstrad VCR4600. Amstrad VCR7000. Amstrad VCR9000. Ferguson 3V00/22/29/39. Ferguson 3V42/44/45/55. Fisher FVH520/515/720. Hitachi 8000/3300/9500. Hitachi VT11/33E. Panasonic NV230. Panasonic NV333.
0/P Trans TX100 110°20.95 is Trans. (TX90)	Capstan Motor FF/Rew Idler FF/Rew Pulley Pinch Roller Play Idler Video Head V4100/VT11E/VT33E Capstan Motor (VT11E) Capstan Motor (VT33E)		Pinch Roller		Video Head	24.95 IUALS a) a	Reel Motor Unlock Assiv Video Head VC481 Capstan Mo Pinch Roller Reel Idler (G Reel Motor Video Head	(Genuine) 17.50 embly	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/85/55. Fisher FVH520615/720. Hitachi 8000'3300'9500. Hitachi V11/33E. Panasonic NV333. Panasonic NV333.
0/P Trans TX100 110°	Capstan Motor Fr/Rew Idler Pr/Rew Villey Pinch Roller Play Idler Video Head V4100/VT11E/VT33E Capstan Motor (VT33E) Clutch Assy.	31.95 	Pinch Roller Play Clutch (Genuine) Reel (Jer (Genuine) Video Head <b>REMOTE CONT</b> Ferguson TX9 U/S Basic Ferguson TX9/10 M/Text. Ferguson TX9/10 Text. Ferguson TX100 Text.	3.95 4.95 1.25 17.95 <b>TROLS</b> 14.50 t12.95 12.95 t12.95 t12.95	Video Head	24.95 IUALS e) e	Reel Motor Unlock Assivideo Head VC481 Capstan Mc Pinch Rotler Reel Idler (G Reel Idler (G SOI	(Genuine) 17.50 embly 23.95 xtor 22.95 isenuine) 3.95 (Genuine) 18.50 23.95 WY SPARES	Amstrad VCR4600.           Amstrad VCR7000.           Amstrad VCR7000.           Ferguson 3V00/22/9/39.           Ferguson 3V10/22/9/39.           Ferguson 3V2.           Ferguson 3V42/44/45/55.           Fisher FVH520/615/720.           Hitachi W000/3300/9500.           Hitachi VT11/33E.           Panasonic NV230.           Panasonic NV333.           Panasonic NV330.
0/P Trans TX100 110" 20.95 Its Trans. (TX90)	Capstan Motor Fr/Rew Idler Fr/Rew Pulley Pinch Roller Play Idler Video Head Video Head Vatou/VT11E/VT33E Capstan Motor (VT11E) Clutch Assy. Fr/Rew Idler (Genuine)	31.95 	Pinch Roller	3.95 4.95 1.25 17.95 <b>TROLS</b> 5	Video Head	24.95 IUALS a) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Assis Video Head VC481 Capstan Mc Pinch Rotter Reel Idler (C Reel Motor Video Head SOI Capstan Mc	(Genuine)	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR7000. Ferguson 3V00/22/9/39. Ferguson 3V42/44/45/55. Fisher FVH520/615/720. Hitachi R000/3300/9500. Hitachi V11/33E. Panasonic NV230. Panasonic NV330. Panasonic NV330. Panasonic NV330.
0/P Trans TX100 110°20.95 is Trans. (TX30)	Capstan Motor Hr/Rew Idler	31.95 	Pinch Roller	3.35 4.55 1.25 17.55 <b>TROLS</b> 12.95 12.95 12.95 12.95 12.95 14.55 14.55	Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX10 Complet Ferguson TX100	24.95 IUALS a) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Assiv Video Head VC481 Capstan Mo Pinch Roller (C Reel Idler (C Reel Motor Video Head SOI Capstan Mo Pinch Roller	(Genuine) 17.50 embly 23.95 stor 22.95 ienuine) 395 (Genuine) 395 (Genuine) 18.50 23.95 NY SPARES stor C7 27.95 C5/6/7 3.95	Amstrad VCR4600.           Amstrad VCR7000.           Amstrad VCR7000.           Ferguson 3V00/22/9/39.           Ferguson 3V10/22/9/39.           Ferguson 3V2.           Ferguson 3V42/44/45/55.           Fisher FVH520/615/720.           Hitachi W000/3300/9500.           Hitachi VT11/33E.           Panasonic NV230.           Panasonic NV333.           Panasonic NV330.
0/P Trans TX100 110" 20.95 is Trans. (TX90)	Capstan Motor Fr/Rew Idler Fr/Rew Villey Pinch Roller Play Idler Video Head V400/VT11E/VT33E Capstan Motor (VT13E) Capstan Motor (VT33E) Clutch Assy Fr/Rew Idler (Genuine) Pinch Roller Video Head	31.95 	Pinch Roller Play Clutch (Genuine) Reel (Jer (Genuine) Video Head <b>REMOTE CONT</b> Ferguson TX9 U/S Basic Ferguson TX9/10 M/Text. Ferguson TX9/10 Text. Ferguson TX100 Text. Ferguson 3V30 Video Ferguson 3V33 Video Ferguson 3V35 Video	3.95 4.55 1.25 17.95 TROLS 514.50 12.95 12.95 12.95 12.95 15.95 16.95 16.95	Video Head	24.95 IUALS a) 27.95 te	Reel Motor Unlock Assiv Video Head VC481 Capstan McC Pinch Roller Reel Idler (G Reel Motor Video Head SOI Capstan McC Pinch Roller Pinch Roller	(Genuine) 17.50 embly 35 xtor 22.95 r 35 Senuine) 395 (Genuine) 18.50 23.95 NY SPARES tor C7 27.95 C5/6/7 3.95 C9 5.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/45/55. Fisher FVH5200615/720. Hitachi 8000/3300/9500. Hitachi VT11/33E. Panasonic NV/330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV730. Panasonic NV730. Pan
0/P Trans TX100 110"	Capstan Motor	31.95 	Pinch Roller	3.35 4.55 1.25 17.95 TROLS 12.95 12.95 12.95 14.55 15.95 14.95 16.95 16.95 12.95	Video Head	24.95 IUALS a) a	Reel Motor Unlock Assi Video Head VC481 Capstan Mo Pinch Roller Reel Motor Video Head SOI Capstan Mo Pinch Roller Pinch Roller Rewind Kit C	(Genuine)	Amstrad VCR4600.           Amstrad VCR4000.           Amstrad VCR7000.           Amstrad VCR9000.           Ferguson 3V00/22/29/39.           Ferguson 3V10/22/29/39.           Ferguson 3V2.           Ferguson 3V42/44/45/55.           Fisher FVH520/615/720.           Hitach i W00/300/9500.           Hitach i VT11/33E.           Panasonic NV230.           Panasonic NV333.           Panasonic NV330.           Panasonic NV330.           Panasonic NV330.           Panasonic NV730.           Panasonic NV730.           Panasonic NV777.           Panasonic NV679.
0/P Trans TX100 110"	Capstan Motor	31.95 	Pinch Roller Play Clutch (Genuine) Reel Idler (Genuine) Video Head <b>REMOTE CONT</b> Ferguson TX9/10 N/Text. Ferguson TX9/10 Text. Ferguson TX9/10 Text. Ferguson X23 Video Ferguson 3/33 Video Ferguson 3/35 Video Fidelity CTV14R/S Forundia TP200	3.35 4.55 1.25 1.25 1.25 1.25 1.450 t12.95 1.255 t12.95 1.455 1.6,35 16,35 16,35 12,95 12,95	Video Head	24.95 IUALS a) a) a) a) a) b) a) a) b) b) a) b) b) b) b) b) b) b) b) b) b	Reel Motor Unlock Ass: Video Head Vcket Capstan Mc Pinch Roller Reel Motor Video Head Video Head SOU Capstan Mo Pinch Roller Pinch Roller Rewind Kit (	(Genuine) 17.50 embly 35 xtor 22.95 r 35 Senuine) 395 (Genuine) 18.50 23.95 NY SPARES tor C7 27.95 C5/6/7 3.95 C9 5.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR7000. Ferguson 3V00/22/97/39. Ferguson 3V32. Ferguson 3V32. Ferguson 3V42/44/45/55. Fisher FVH200/510/720. Hitachi 8000/3300/9500. Hitachi VT11/33E. Panasonic NV230. Panasonic NV230. Panasonic NV330. Panasonic NV330. Panasonic NV730. Panasonic NV730. Panasonic NV730. Panasonic NV777. Panasonic NV779. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV61011/15.
0/P Trans TX100 110" 20.95 Is Trans. (TX90)	Capstan Motor	31.95 	Pinch Roller Play Clutch (Genuine) Reel (Jer (Genuine) Video Head <b>REMOTE CONT</b> Ferguson TX9 10 M/Text. Ferguson TX9/10 Text. Ferguson TX9/10 Text. Ferguson TX100 Text. Ferguson 3V33 Video Ferguson 3V35 Video Fierguson 17400 Text. Fierguson 3V35 Video Fierguson 3V35 Video Fierguson 3V35 Video Fierguson 17400 Text. Fierguson 3V35 Video Fierguson 1740 Text. Fierguson 1	355 455 125 17.55 7ROLS 17.95 12.95 12.95 12.95 14.95 16.95 16.95 12.95 12.95 12.95	Video Head	24.95 IUALS a) a) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Ass: Video Head Vcket Capstan Mc Pinch Roller Reel Motor Video Head Video Head SOU Capstan Mo Pinch Roller Pinch Roller Rewind Kit (	(Genuine) 17.50 embly 23.95 stor 22.95 ienuine) 3.95 ienuine) 3.95 (Genuine) 18.50 23.95 <b>NY SPARES</b> tor C7 27.95 C5/6/7 3.95 C9 5.95 5/7 4.65 5/6 3.45	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/855. Fisher FVH520/615/720. Hitachi W010/300/9500. Hitachi W11/312. Panasonic NV330. Panasonic NV330. Panasonic NV366. Panasonic NV360. Panasonic NV370. Panasonic NV77000. Panasonic NV62017. Panasonic NV62017. Panasonic NV62027. Panasonic NV62027.
0/P Trans TX100 110"	Capstan Motor	31.95 	Pinch Roller	335 435 125 175 <b>IROLS</b> 1450 1295 1295 455 1295 1595 1695 1695 1695 1695 1695 1695 16	Video Head	24.95 IUALS a) a	Reel Motor Unlock Ass. Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOI Capstan Mc Pinch Roller Pinch Roller Rewind Kit ( Video Head	(Genuine) 17.50 embly 35 xtor 22.95 r 3.55 Senuine) 3.55 (Genuine) 18.50 XY SPARES xtor C7 27.95 C5/6/7 3.95 C9 5.55 C5/6/7 4.65 C5/6/7 15.50	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR7000. Ferguson 3V00/22/97/39. Ferguson 3V32. Ferguson 3V32. Ferguson 3V42/44/45/55. Fisher FVH200/510/720. Hitachi 8000/3300/9500. Hitachi VT11/33E. Panasonic NV230. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV730. Panasonic NV730. Panasonic NV730. Panasonic NV777. Panasonic NV779. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV700. Panasonic NV61011/15.
0/P Trans TX100 110"	Capstan Motor	31.95 	Pinch Roller Play Clutch (Genuine) Play Clutch (Genuine) Video Head <b>REMOTE CONT</b> Ferguson TX9 U/S Basic Ferguson TX9/10 Ptxt Ferguson TX9/10 Ptxt Ferguson TX100 Text Ferguson 3/31 Video Ferguson 3/35 Video Ferguson 3/35 Video Ferguson 3/35 Video Ferguson 3/35 Video Ferguson 3/35 Video Fidelity CTV14R/S. Grundig TP200 Grundig TP400TT ITT R530/305 Text ITT R5301 Fext	335 425 125 1795 TROLS - 1450 - 1295 d 1295 d 1295 d 1295 d 1295 1695 1695 1695 1695 1295 1595 1595 1595 1595 1595 1595	Video Head	24.95 IUALS a) a) a) b) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Ass: Video Head Capstan Mc Pinch Roller Reel Mator Video Head SOI Capstan Mo Pinch Roller Rewind Kit C Video Head	(Genuine) 17.50 embly 23.55 botor 22.95 isenuine) 395 (Genuine) 395 (Genuine) 18.50 botor C7 27.95 C5/67 3.95 C5/67 3.95 C5/67 4.65 C5/67 19.50 C5/67 19.50 C5/67 19.50 C5/67 19.50	Amstrad VCR4600.           Amstrad VCR4000.           Amstrad VCR7000.           Amstrad VCR9000.           Ferguson 3V00/22/9/39.           Ferguson 3V10/22/9/39.           Ferguson 3V2.           Ferguson 3V42/44/45/55.           Fisher FVH520/615/720.           Hitach 1000/300/9500.           Hitach 1000/300/9500.           Hitach 1000/300/9500.           Panasonic NV233           Panasonic NV330.           Panasonic NV330.           Panasonic NV330.           Panasonic NV330.           Panasonic NV730.           Panasonic NV777.           Panasonic NV679.           Panasonic NV679.           Panasonic NV619.           Panasonic NV62021/75.           Philips VCR6460/6560.           Sanyo VHR11001300.
0/P Trans TX100 110" 20.95 is Trans. (TX90)	Capstan Motor	31.95 	Pinch Roller	335 425 125 1795 7ROLS 14.50 12.95 12.95 15.95 15.95 16.95 12.95 1	Video Head	24.95 IUALS a) a) a) b) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Assa Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOU Capstan Mo Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/27 Akai VS1/27	(Genuine) 17.50 embly 35 embly 23.95 botor 22.95 ienuine) 395 (Genuine) 18.50 botor C7 27.95 C5/67 3.95 C5/67 3.95 C5/67 4.65 C5/67 19.50 C5/67 19.50 C5/67 19.50 C5/67 19.50	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/85/55. Fisher FVH5200615/720. Hitachi 8000/9300/9500. Hitachi V11/33E. Panasonic NV730. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV730. Panasonic NV500. Panasonic NV500. Panas
0/P Trans TX100 110"	Capstan Motor FF/Rew Viller, Pinch Roller Play Idler Video Head V400VT11EVT33E Capstan Motor (VT11E). Capstan Motor (VT33E). Clutch Assy FF/Rew Idler (Genuine). Pinch Roller Video Head V400VT152 Capstan Motor End Sensors (Pair). Pinch Roller Video Head. Video Head. V400VT53E Capstan Motor End Sensors (Pair). Pinch Roller Video Head. Video Head.	31.95 	Pinch Roller	335 435 125 1795 7ROLS 1450 1295 4295 4295 1595 1695 1695 1695 1295 1295 1295 1295 1295 1295 1295 12	Video Head	24.95 IUALS a) 2.77.95 te	Reel Motor Unlock Ass. Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOI Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/27 Amstrad VC	(Genuine)         17.50           sembly         35           semuly         35           senuine)         355           senuine)         355           senuine)         355           Senuine)         355           Senuine)         355           Senuine)         18.50           SC 5/6/7         355           5/5/7         4.65           5/5         3.45           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           5/5         3.65           6/5         3.65           5/5         3.55           5/5         3.55           5/5         3.65           5/5         3.65           5/5         3.56           5/5         3.65 <t< td=""><td>Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/855. Fisher FVH520/615/720. Hitachi W11/318. Panasonic NV300. Panasonic NV500. Panasonic NV6100. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500.</td></t<>	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/855. Fisher FVH520/615/720. Hitachi W11/318. Panasonic NV300. Panasonic NV500. Panasonic NV6100. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500.
0/P Trans TX100 110" 20.95 is Trans. (TX90)	Capstan Motor	31.95 	Pinch Roller	335 425 125 1795 TROLS 	Video Head	24.95 IUALS a) a	Reel Motor Unlock Ass. Video Head Capstan Mc Pinch Roller Reel Idler (B Reel Idler (B Reel Motor Video Head SOI Capstan Mc Pinch Roller Pinch Roller Rewind Kit ( Video Head VIdeo Head VIDE Akai VS1/27 Amstrad VC	(Genuine) 17.50 embly 35 stor 22.95 fr 35 Senuine) 3.95 (Genuine) 18.50 (Genuine) 18.50 (Genui	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR7000. Ferguson 3V00/22/97/39. Ferguson 3V32. Ferguson 3V32. Ferguson 3V42/44/45/55. Fisher FVH200f15/720. Hitachi 8000/3300/9500. Hitachi VT11/33E. Panasonic NV230. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV730. Panasonic NV730. Panasonic NV730. Panasonic NV730. Panasonic NV730. Panasonic NV70. Panasonic NV610111/15. Panasonic NV610111/15. Panasonic NV610111/15. Sanyo VHR1000. Sanyo VHR1500. Sanyo VHR1500
0/P Trans TX100 110" 20.95 is Trans. (TX90)	Capstan Motor FF/Rew Viller, Pinch Roller Play Idler Video Head V400VT11EVT33E Capstan Motor (VT11E). Capstan Motor (VT33E). Clutch Assy FF/Rew Idler (Genuine). Pinch Roller Video Head V400VT152 Capstan Motor End Sensors (Pair). Pinch Roller Video Head. Video Head. V400VT53E Capstan Motor End Sensors (Pair). Pinch Roller Video Head. Video Head.	31.95 1.95 3.95 22.95 23.95 25.9	Pinch Roller	335 425 125 7780LS 7780LS 7780LS 7780LS 71295 71295 71295 71595 71205 71295 71205 71205 71205 71200 71200 71000 71000 71000 71	Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX10 Complete Ferguson TX80	24.95 IUALS b) 2	Reel Motor Unlock Assa Video Head Capstan Mc Pinch Roller Reel Idder (C Reel Motor Video Head SOO Capstan Mc Pinch Roller Pinch Roller Pinch Roller Rewind Kit ( Video Head VIDE Atai VS1/2/C Amstrad VC Amstrad VC	(Genuine) 17.50 embly 23.55 botor 22.95 isenuine) 355 (Genuine) 18.50 18.50 NY SPARES http:/// 27.95 C5/67/ 3.95 C5/57 4.65 C5/67/ 19.50 C5/67/ 20.50 C5/67/ 20.5	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/855. Fisher FVH520/615/720. Hitachi W11/318. Panasonic NV300. Panasonic NV500. Panasonic NV6100. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500.
0/P Trans TX100 110" 20.95 its Trans. (TX90)	Capstan Motor	31.95 1.95 3.95 3.95 22.95 7.95 23.95 7.95 23.95 1.95 1.95 1.95 1.95 1.95 22.95 1.95 1.95 22.95 1.95 22.95 1.95 22.95 1.95 23.95 25.	Pinch Roller		Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX90 Complete Ferguson TX90. Ferguson TX90. Ferguson TX90. Fidelity AVS1600. Fidelity AVS1600. Fidelity CIV14R. Fidelity CIV14R. Fidelity CIV20R. Philips CF1. Philips CF1. Philips CT2. Philips K13. Philips K35. Philips K35. Philips X35. Philips X35.	24.95 IUALS a) a	Reel Motor Unlock Assi Video Head Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit ( Video Head VIDE Atai VSI/2 Amstrad VC Amstrad VC Ferguson 33 Ferguson 33	(Genuine) 17.50 embly 35 embly 22.95 r 32.95 isenuine) 3.95 (Genuine) 18.50 22.95 NY SPARES NY SPARES NY SPARES tor C7 27.95 C5/6/7 3.95 C5/6/7 3.95 C5/6/7 19.50 C5/6/7 19.50	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR7000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/85/55. Fisher FVH5200615/720. Hitachi 8000/9300/9500. Hitachi V11/318. Panasonic NV730. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV730. Panasonic NV730. Panas
0/P Trans TX100 110" 20.95 Its Trans. (TX90)	Capstan Motor	31.95 1.95 3.95 23.95 23.95 29.95 250 3.95 22.95 15.95 49.95 DEO	Pinch Roller	335 425 125 1795 7ROLS 14.50 12.95 4.12.95 4.12.95 4.12.95 4.12.95 15.95 16.95 12.95 16.95 12.95 12.95 14.50 0.15.95 14.50 0.15.95 15.95 14.50 0.15.95 15.95 14.50 15.95 14.50 15.55 14.50 15.55 15.55 14.50 14.50 15.55 12.55	Video Head	24.95 IUALS a) 2.7.95 te38.95 	Reel Motor Unlock Assa Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOO Capstan Mo Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/2/C Amstrad VC Ferguson 3/ Ferguson 3/ Ferguson 3/	(Genuine)         17.50           sembly         35           sembly         23.95           xotor         22.95           sienuine)         3.95           (Genuine)         18.50           xotor C7         27.95           C5/67         3.95           xotor C7         27.95           C5/67         3.95           25/7         4.65           25/6         3.45           C5/67         19.50           C5/67         19.50           C0 BELT KITS         3/5           3/500         1.95           R7000         1.50           (23.3         1.75           23/30         1.80           3/53/3         1.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR9000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V32. Fisher FVH520/615/720. Hitachi 8000/300/9500. Hitachi VT11/33E. Panasonic NV300. Panasonic NV5000. Panasonic NV6202/750. Philips VCR46206560. Sanyo VHR1100/1300. Sanyo VHR1500. Sanyo VHR1500. Sentra 8000. Sharp VCS30/381/481. Sharp VCS30/381/4
0/P Trans TX100 110" 20.95 Its Trans. (TX90) 77.95 Its Trans. (TX90) 77.95 It Switch (Remote) 1.75 It Button TX90 12.95 It Butt	Capstan Motor	31.95 1.95 3.95 22.95 23.95 25.9	Pinch Roller	335 425 125 1795	Video Head	24.95 IUALS a) a) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Asss Video Head Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit ( Video Head Video Head VIDE Akai VSI/27 Amstrad VC Ferguson 33 Ferguson 34	(Genuine)         17.50           sembly         35           semular         23.95           xtor         22.95           senuine)         3.95           senuine)         3.95           senuine)         3.95           Senuine)         3.95           Senuine)         18.50           XY SPARES         23.95           tor C7         27.95           C5/6/7         3.95           C5/6/7         3.95           C5/6/7         1.95           C0 BELT KITS         355           C3/30         1.95           723/30         1.95           723/30         1.95           723/30         1.95           723/30         1.95           723/30         1.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR7000. Ferguson 3V00/22/28/39. Ferguson 3V00/22/28/39. Ferguson 3V42/44/45/55. Fisher FVH52/0615/720. Hitachi 8000/9300/9500. Hitachi 8000/9300/9500. Hitachi V11/318. Panasonic NV/330. Panasonic NV/330. Panasonic NV/330. Panasonic NV/330. Panasonic NV/330. Panasonic NV/330. Panasonic NV/30. Panasonic NV/30. Sany VHR1150. Sany VHR1500. Sany VHR1500. Sany VS1/850. Sany VS1/850. Sany VS1/850. Sany VS1/850. Sany VS1/850. Sany VS1/850. Sany VS1/850. Sany VS1/850. Sany VS1/850. Sany VS20. Sany VS1/850. Sany VS20. Sany VS31/850. Sany VS31/850. Sany VS31/850. Sany VS31/850. Sany VS32. Sany VS31/850. Sany VS32. Sany VS31/850. Sany VS32. Sany VS31/850. Sany VS32. Sany VS31/850. Sany VS32. Sany Sany Sany Sany Sany Sany Sany Sany
0/P Trans TX100 110" 20.95 ts Trans. (TX90) 17.95 ts Trans. (TX90) 12.95 pt = 1.75 B Utton TX90 12.95 pt = 1.75 FERGUSON VIDEO SPARES VIDEO SPARES	Capstan Motor	31.95 1.95 	Pinch Roller	335 425 125 1795 TROLS - 14.50 12.95 12.95 12.95 12.95 12.95 12.95 14.95 16.95 16.95 15.95 12.95 12.95 15.95	Video Head	24.95 IUALS a) a) a) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Assa Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOU Capstan Mc Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/2/2 Amstrad VC Ferguson 3% Ferguson 3% Ferguson 3%	(Genuine)         17.50           sembly         35           sembly         23.95           stor         23.95           senuine)         3.95           (Genuine)         3.95           (Genuine)         3.95           NY SPARES         23.95           NY SPARES         5.95           C5/67         3.95           C5/67         3.95           C5/67         1.95           R4500         1.95           R4500         1.95           R7000         1.50           72/30         1.90           73/53         1.95           29/30         1.90           29/30         1.95           20/615         1.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR4000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/5/55. Fisher FVH520/615/720. Hitachi 8000/3300/500. Hitachi V11/1/3E. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV579. Panasonic NV579. Philips VCR462/6560. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHS1/500. Sanyo VHR1500. Sanyo VHR1500. Sany
0/P Trans TX100 110" 20.95 hs Trans. (TX90)	Capstan Motor	31.95 1.95 3.95 23.95 23.95 23.95 23.95 23.95 23.95 23.95 23.95 23.95 23.95 23.95 23.95 25.95 1.95 49.95 DEO	Pinch Roller	335 425 125 1795 7ROLS 7ROLS 7295 7295 71450 71295 712	Video Head	24.95 IUALS a) a	Reel Motor Unlock Assi Video Head Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit C Wideo Head Video Head Video Head Amstrad VC Amstrad VC Ferguson 33 Ferguson 33	(Genuine)         17.50           sembly         23.55           otor         22.95           r         3.35           sienuine)         3.95           isenuine)         3.95           isenuine)         3.95           NY SPARES           http://www.space           tor C7         27.95           C5/6/7         3.95           5/5/7         4.65           C5/6/7         1.95           C9         5.95           C9         5.95           C9         5.95           C9         5.95           C9         1.95           C9         5.95           C9         1.95           C9         5.95           C9         1.95           C9         5.93           C9         2.23           C9         2.23           C10/16/22         2.250           C23/30         1.95           V3203         1.95           V3320         1.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR7000. Ferguson 3V00/22/28/39. Ferguson 3V00/22/28/39. Ferguson 3V42/44/45/55. Fisher FVH52/0615/720. Hitachi 8000/9300/9500. Hitachi 8000/9300/9500. Hitachi V11/318. Panasonic NV/330. Panasonic NV/330. Panasonic NV/330. Panasonic NV/330. Panasonic NV/330. Panasonic NV/30. Panasonic NV/30. Sany VHR1150. Sany VHR1500. Sany VHR1500. Sany VHR1500. Sharp VC300/381/481. Sharp VC56/2. Solvava 1000. Sony C56/7. Sany 20/30.
0/P Trans TX100 110° 20.95 hs Trans. (TX90) 17.95 hs Trans. (TX90) 1.75 B trans. (TX90) 1.25 er	Capstan Motor	31.95 	Pinch Roller	335 435 125 1795 7ROLS 14.50 12.95 4.12.95 4.12.95 4.12.95 15.95 16.95 16.95 15.95 15.95 15.95 15.95 15.95 15.95 15.95 15.95 15.95 12.95 15.95	Video Head	24.95 IUALS b) 2	Reel Motor Unlock Ass Video Head Capstan Mc Pinch Roller Reel Idder (C Reel Motor Video Head SOO Capstan Mo Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit (C Amstrad VC Amstrad VC Am	(Genuine) 17.50 embly 35 embly 23.95 botor 22.95 isenuine) 355 (Genuine) 18.50 may space 18.50 tor C7 27.95 C5/67 3.95 C5 55 C5/7 4.65 C5/67 19.50 C5/67 19.50 C5/	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR4000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/5/55. Fisher FVH520/615/720. Hitachi 8000/3300/500. Hitachi V11/1/3E. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV579. Panasonic NV579. Philips VCR462/6560. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHS1500. Sanyo VHR1500. Sanyo
0/P Trans TX100 110" 20.95 hs Trans. (TX90) 17.95 hs Trans. (TX90) 12.95 pt 2014 17.95 FERGUSON 12.95 pt 2014 17.95 NIDEO SPARES VIE22 ht 2015 17.95 h Motor 24.95 h Motor 27.95 o Head 77.95 Jan Motor 27.95 h Motor 27.95 h Motor 27.95 h Motor 27.95 h Motor 24.95 h Motor 24.95 h Motor 27.95 h Motor 27.95 h Motor 24.95 h Motor 24.95 h Motor 24.95 h Motor 25.95 h Motor 25.95 hs Trans. 21.95 hdler. 226 hdler. 226	Capstan Motor	31.95 	Pinch Roller	335 425 125 1795 TROLS 	Video Head	24.95 IUALS a) a) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Asss Video Head Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit C Kawi VSI/2 Amstrad VC Amstrad VC Amstrad VC Ferguson 33 Fisher RVHS Ferguson 33 Fisher RVHS Panasonic N Panasonic N Panasonic N	(Genuine)         17.50           gembly         23.95           stor         22.95           signification         3.95           senuine)         3.95           senuine)         3.95           senuine)         3.95           senuine)         3.95           Senuine)         18.50           XY SPARES         23.95           tor C7         27.95           C5/6/7         3.95           C5/6/7         3.95           C5/6/7         1.95           C6         3.45           C5/6/7         1.95           C6         3.65           C5/6/7         1.95           C6         3.65           C5/6/7         1.95           C7         1.95           C9         5.25           C9         1.95           C9         1.95 <td>Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR4000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/5/55. Fisher FVH520/615/720. Hitachi 8000/3300/500. Hitachi V11/1/3E. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV579. Panasonic NV579. Philips VCR462/6560. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHS1500. Sanyo VHR1500. Sanyo VHR1500. Sanyo</td>	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR4000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/5/55. Fisher FVH520/615/720. Hitachi 8000/3300/500. Hitachi V11/1/3E. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV579. Panasonic NV579. Philips VCR462/6560. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHS1500. Sanyo VHR1500. Sanyo
VIDEO SPARES           VIDEO SPARES           VIDE2           Stan Motor         24.95           h Roller         3.95           h Roller         5.65           - Up Clutch (Small)         5.65           - Up Clutch (Small)         5.65           - Up Clutch (Large)         5.95           o Head         17.95           X90         30           stan Motor         37.95           Ing Motor         8.70           h Roller         4.00           Lamp         80           Idler         2.45           - Up Clutch         2.45           - Up Clut	Capstan Motor	31.95 1.95 3.95 23.95 23.95 23.95 25.9 3.95 22.95 15.95 1.95 4.95 0EO 13.75 1.95	Pinch Roller	335 425 125 1795 7ROLS 14.50 12.95 15.95 15.95 12.95 12.95 12.95 12.95 12.95 12.95 12.95 12.95 12.95 12.95 12.95 15.95 15.95 12.95 14.50 12.95 1	Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX90 Complete Ferguson TX90 Ferguson TX90 Fidelity AVS1600 Fidelity AVS1600 Fidelity CTV14R Fidelity CTV20R Fidelity CTV20R Fidelity CTV20R Fidelity CTV20R Philips CTX-E Philips CTX-S Philips CTX-S Philips K13 Philips K35 Philips K3 Philips X3 Philips X3 Philips X4440 Philips X445 Ferguson 3V46/45 Ferguson 3V46/45 Ferguson 3V46/45 Ferguson 3V46/55 Ferguson 3V45 Ferguson 3V45 Ferguson 3V45 Ferguson 3V59 Ferguson 3V59 Ferguson 3V59 Ferguson 3V59 Ferguson 3V55	24.95 IUALS a) 2.7.95 te38.95 	Reel Motor Unlock Ass Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOO Capstan Mo Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/22 Amstrad VC Ferguson 33 Ferguson 34 Ferguson 33 Ferguson 34 Ferguson 34 Fer	(Genuine)         17.50           embly         35           senuine)         323.95           botor         22.95           senuine)         3.95           ienuine)         3.95           (Genuine)         18.50           otor C7         27.95           C5/67         3.95           C5/67         3.95           C5/67         3.95           C5/67         19.50           C5/67         19.50           C5/67         19.50           C000/16/22         2.50           V330         1.95           V4330         1.95           V1330         1.95           V1330         1.95           V1300         1.95           V1730         1.95           V1770         1.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR4000. Ferguson 3V00/22/28/39. Ferguson 3V32. Ferguson 3V42/44/5/55. Fisher FVH520/615/720. Hitachi 8000/3300/500. Hitachi V11/1/3E. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV300. Panasonic NV579. Panasonic NV579. Philips VCR462/6560. Sanyo VHR11001. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHR1500. Sanyo VHS1500. Sanyo VHR1500. Sanyo
0/P Trans TX100 110° 20.95 hs Trans. (TX90) 17.95 et al. (TX90) 1.75 B trans. (TX90) 1.75 B trans. (TX90) 1.25 et al. (TX90) 1.	Capstan Motor	31.95 1.95 3.95 23.95 29.95 29.95 25.0 3.95 22.95 15.95 15.95 49.95 DEO 13.75 3.95 3.95 3.95 1.95 3.95 1.95 3.95 1.25 1.25	Pinch Roller		Video Head	24.95 IUALS b) 227.95 te38.95 9.95 1.95 	Reel Motor Unlock Ass. Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOU Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/27 Amstrad VC Amstrad VC Amstrad VC Amstrad VC Amstrad VC Panasonic h Panasonic h Panasonic h Panasonic h Panasonic h	(Genuine)         17.50           gembly         35           senuine)         23.95           vitor         22.95           senuine)         3.95           senuine)         18.50           vitor         23.95           NY SPARES         23.95           NY SPARES         23.95           C5/6/7         3.95           C5         5.95           C5/6/7         3.95           C5         5.95           C5/6/7         1.95           C6         3.45           C5/6/7         1.95           C6         3.45           C5/6/7         1.95           C7         2.95           C3/3         1.95           C3/3         1.95           V330         1.95           V330         1.95           V/730         1.95           V/730         1.95           V/730         1.95           V/730         1.95           V/7000/2010         1.95	Amstrad VCR4600 Amstrad VCR4000 Amstrad VCR4000 Ferguson 3V00/22/28/39 Ferguson 3V00/22/28/39 Ferguson 3V2 Hitachi 8000/3300/9500 Hitachi 8000/3300/9500 Hitachi VT11/33E Panasonic NV230 Panasonic NV330 Panasonic NV330 Panasonic NV330 Panasonic NV300 Panasonic NV430 Panasonic NV430 Panasonic NV430 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/11/15 Panasonic NV610/2520 Philips VCR462/6560 Sanyo VHR1100/1300 Santy 07C5000/5500 Sentra 8000 Sentra 8000 Sony C560/ Sonyo C567/ Sonyo C20/30 Sonyo C567/ Sonyo C20/30 Sonyo C20/30 Son
0/P Trans TX100 110" 20.95 hs Trans. (TX90) 17.95 est Trans. (TX90) 12.95 er. 14.35 FERGUSON 12.95 er. 14.35 FERGUSON 12.95 h Button TX90 24.95 h Motor 24.9	Capstan Motor	31.95 1.95 3.95 22.95 23.95 23.95 25.9 3.95 25.9 3.95 15.95 4.95 15	Pinch Roller		Video Head	24.95 IUALS a) a) c) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Ass Video Head Capstan Mc Pinch Roller Reel Idder (C Reel Motor Video Head Capstan Mc Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/27 Amstrad VC Ferguson 30 Ferguson 30 Fergu	(Genuine)         17.50           sembly         35           sembly         23.95           stor         23.95           senuine)         3.95           Genuine)         3.95           (Genuine)         3.95           MY SPARES         23.95           NY SPARES         18.50           stor C7         27.95           C5/67         3.95           C5/67         3.95           C5/67         1.95           Af500         1.95           R4500         1.95           R7000         1.50           000/16/22         2.50           V/330         1.95           V/330         1.95           V/370         1.95           V/370         1.95           V/777         1.95           V/700/200         1.95           V/700/200         1.95           V/200/2010         1.95	Amstrad VCR4600. Amstrad VCR4000. Amstrad VCR4000. Ferguson 3V00/22/23/39. Ferguson 3V32. Ferguson 3V42/44/5/55. Fisher FVH520/615/720. Hitachi 8000/3300/9500. Hitachi VT11/38. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV330. Panasonic NV370. Panasonic NV570. Panasonic NV570. Panaso
0/P Trans TX100 110° 20.95 hs Trans. (TX90) 17.95 hs Trans. (TX90) 12.95 pt 2000 12.95 pt 2000 12.95 pt 2000 12.95 pt 2000 12.95 h Bulton TX90 24.95 h Roller 24.95 h Roller 24.95 h Roller 24.95 h Roller 3.95 h Roller 3.95 h Roller 3.95 h Roller 3.95 h Roller 3.95 h Roller 4.50 h Roller 5.55 h Roller 1.00 h Roller 2.25 h S Trans 7.15 h Roller 2.05 h S Trans 7.15 h Roller 2.05 h Roller 2.55 h S Trans 7.15 h Roller 2.55 h S Trans 7.15 h Roller 2.05 h Roller 2.55 h S Trans 7.15 h Roller 2.05 h Roller	Capstan Motor	31.95 .1.95 .2.95	Pinch Roller		Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX90 Complete Ferguson TX90 Ferguson TX90 Ferguson TX90 Fidelity AVS2000 Fidelity AVS2000 Fidelity CTV14R Fidelity CTV20R Fidelity	24.95 IUALS a) 2.7.95 te .38.95 .9.95 .14.95 .5.05 .5.05 .5.00	Reel Motor Unlock Ass Video Head Capstan Mc Pinch Roller Reel Idder (C Reel Motor Video Head SOO Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit (C Revind Kit (C Video Head VIDE Atai VS1/2/C Amstrad VC Amstrad VC Amstrad VC Amstrad VC Panasonic h Panasonic N Panasonic N	(Genuine)         17.50           sembly         35           sembly         23.95           stor         23.95           senuine)         3.85           senuine)         18.50           senuine)         18.50           variable         23.95           NY SPARES         23.95           variable         1.95           Var	Amstrad VCR4600 Amstrad VCR4000 Amstrad VCR4000 Ferguson 3V00/22/97/39 Ferguson 3V10/22/97/39 Ferguson 3V12/44/45/55 Fisher FVH5200615/720 Hitachi W010/3300/9500 Hitachi W110/133E Panasonic NV/330 Panasonic NV/330 Panasonic NV/330 Panasonic NV/330 Panasonic NV/330 Panasonic NV/330 Panasonic NV/300 Panasonic NV/30 Panasonic NV/30 Panasoni
0/P Trans TX100 110° 20.95 hs Trans. (TX90) 17.95 et al. (TX90) 1.75 B trans. (TX90) 1.75 B trans. (TX90) 1.25 et al. (TX90) 1.	Capstan Motor	31.95 .1.95 .2.95	Pinch Roller	335 425 125 1795 TROLS 14.50 12.95 15.95	Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX90 Complete Ferguson TX90 Ferguson TX90 Fidelity AVS1600 Fidelity CTV14R Fidelity CTV20R Fidelity	24.95 IUALS b) 2.7.95 te38.95 .9.95 .1.95 .5.95	Reel Motor Unlock Ass Video Head Capstan Mc Pinch Roller Reel Motor Video Head SOO Capstan Mo Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit C Rewind Kit C Video Head VIDE Akai (S1/2/ Amstrad VC Amstrad V	(Genuine) 17.50 embly 35 embly 23.95 bit 22.95 f 3.25 isnuine) 3.95 (Genuine) 18.50 tor C7 27.95 C5/7 23.95 C5/7 3.95 C5/7 3.95 C5/7 4.65 C5/6/7 19.50 C5/6/7 19.	Amstrad VCR4600 Amstrad VCR4000 Amstrad VCR4000 Ferguson 3V00/22/28/39 Ferguson 3V00/22/28/39 Ferguson 3V42/44/45/55 Fisher FVH5200615/720 Hitachi 8000/3300/9500 Hitachi V11/33E Panasonic NV/330 Panasonic NV/30 Panasonic NV/30
0/P Trans TX100 110" 20.95 hs Trans. (TX90) 17.95 est Trans. (TX90) 12.95 er. 14.35 FERGUSON 12.95 er. 14.35 FERGUSON 21.25 er. 14.35 FERGUSON 21.25 hs Trans. 24.95 h Motor 25.95 o Head 77.95 Holler 2.95 tan Motor 27.95 here 1.95 here 1.95	Capstan Motor	31.95 .1.95 .2.95	Pinch Roller	335 425 125 1795 TROLS 1450 1295 1295 1295 1295 1495 1595 1595 1295 1295 1295 1295 1295 1295 1595 1595 1295 1295 1595 1295 1295 1295 1595 1295 1295 1295 1595 1295 1295 1595 1295 1595 1295 1295 1595 1295 1295 1595 1295 1595 1295 1595 1295 1595 1295 1595 1595 1295 1595 1295 1595 1595 1595 1595 1595 1595 1595 1595 1595 1595 1595 1295 1595 1595 1595 1595 1595 1295 1595 1595 1595 1595 1295 15	Video Head SERVICE MAN (All Genuine Ferguson TX9 Complete Ferguson TX90 Complete Ferguson TX90 Ferguson TX90 Ferguson TX90 Fidelity AVS2000 Fidelity AVS2000 Fidelity CTV14R Fidelity CTV20R Fidelity	24.95 IUALS a) a) b) c) c) c) c) c) c) c) c) c) c	Reel Motor Unlock Ass. Video Head Capstan Mc Pinch Roller Pinch Roller Sol Capstan Mc Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Pinch Roller Rewind Kit ( Video Head VIDE Akai VS1/27 Amstrad VC Amstrad VC Amstrad VC Panasonic h Panasonic N Panasonic N	(Genuine)         17.50           embly         23.95           stor         22.95           r         3.35           senuine)         3.95           sienuine)         3.95           sienuine)         3.95           Sienuine)         23.95           NY SPARES         23.95           stor C7         27.95           C5/6/7         3.95           C5/6/7         3.95           C5/6/7         19.50           C5/6/7         19.50           C8         1.95           7000         1.95           723.30         1.95           195.20/515         1.95           20/615         1.95           1933         1.95           1933         1.95           1930         1.95           1931         1.95           1932         1.95           1933         1.95           1930         1.95           1931         1.95           1935         1.95           1935         1.95           1935         1.95           1930         1.95           1930	Amstrad VCR4600 Amstrad VCR4000 Amstrad VCR4000 Ferguson 3V02229/39 Ferguson 3V322 Ferguson 3V322 Ferguson 3V322 Ferguson 3V324/44/45/55 Fisher FVH200615/720 Hitachi 8000/300/9500 Hitachi VT11/32 Panasonic NV230 Panasonic NV230 Panasonic NV306 Panasonic NV306 Panasonic NV300 Panasonic NV300 Panasonic NV300 Panasonic NV777 Panasonic NV700 Panasonic NV707 Panasonic NV700 Panasonic












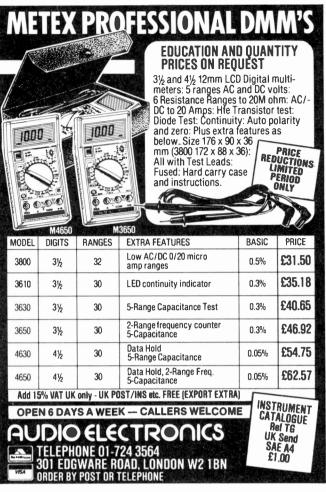

#### TV LINE OUTPUT TRANSFORMERS PRICES INCLUDE VAT & CARRIAGE

VIDEO HEADS, TR/	ANSIST	ORS, IC's, ALSO STOCKED.
SAIRD: 8290, 8752, 8773, 8180	12.00	TT: VC200 to VC402 9.20
ANK BUSH MURPHY A774 with stick rectifier A816, T16, T18, Z712, Z715 20, T22, T26, Z179, A823	9.78 10.35 11.50	CVC1, CVC2 (F0RGESTONE)         11.50           CVC5, CVC7, CVC8, CVC9, CVC9         10.35           CVC25, CVC30, CVC32, CVC45         9.20           CVC800, 1100, 1150, CVC40         P.O.A.           CVC1200, 1204, 1210, 1215, 2600         P.O.A.
718 Basic unit JECCA: 1210, 1211, 1511 700, 2001, 2020, 2401, 2404 251730, 1733, 1830, 1835 10, 70, 80, 90, 100	13.50 11.50 9.20 9.20 9.20	PYE:         169, 173, 569, 368         9.20           CT200,         CT200/1,         CT213         10.35           725-731,         735, 737, 741         9.78           PHILIPS:         170, 210, 300         9.20           320 series         9.78
20, 130, 140, 160 <b>ERGUSON, THORN:</b> 1590, 1591 690, 1691. built in rect. 600, 1615, 1700, 1790 900, 900, 900, 900, 900, 900, 900, 900,	P.O.A. 9.20 9.78 P.O.A.	TX, T8, TX2, TX3 mono         P.0.A           G8 and G9 Series         9.20           KT2, T8, TX3, series         9.20           CTX, K13, Series         9.20           CTX, G11, K30, K4, K40, split diode         P.0.A           K12, CF1, 2A, 2B, 3A, NC3         P.0.A
000, 3500, 8000, 8500, 8800 1000, 9200, 9300 series 1500, 9600, 9650 series 1X9, TX10,TX90, TX100, TXP5 <b>I/OVIESTAR</b> 3781, 3787, 8180 X10 focus unit	P.O.A. 12.00 12.00 P.O.A. 12.00 10.87	REDIFUSION Mk1 to 5         P.O.A.           DORIC Mk3, Mk1         11.50           SONY KV 1400, 1612, 2000         P.O.A.           GRUNDIG: most models in stock         NORDMENDE: 8290, 2206, 2306           NORDMENDE: 8290, 2206, 2306         P.O.A.
RT0 10203 0111 RDELITY: FTV12 mono X2000 ZX3000 14", 16", 20" X3000 22"	10.35 16.43 27.28	SANYO: 5101, 5103, 7118, 7130 P.O.A. SHARP: C1851H, C2051H, 1405 P.O.A. HINARI: CT4, CT5 P.O.A. TANDBURG: 190, CTV2, CTV3 P.O.A. TELEFUNKEN: most models in stock
<b>3.E.C.</b> 2047 to 3135 mono 201H, 1501H, 2114, 3133, 3135 DUAL & SINGLE hybrid col.	9.20 9.20 10.00	HITACHI: 1471, CPB260, 2501 P.O.A. SAISHO MATSUI SENTRA P.O.A.
SINGLE STD solid state SINGLE STD split diode	12.00 P.O.A.	Delivery by return of post. Tidman Mail Order Ltd.,
NDESIT: 24EGB, 12LGB, 12SGB	10.35	236 Sandycombe Road,
WINDINGS IYNE: main winding RBM: T20, T22, T26, Z179 WALTHAM: W125 eht winding KORTING: hybrid winding THORN: 8000, 8500, 8800 eht	6.80 6.33 2.37 6.90 6.70	Richmond, Surrey TW9 2EQ. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm & 1.30-4.30 pm Sat 10 am to 12 noon.

	-		
			ULAR BAKERS DOZEN PACKS
			l available) cks are £1 each, if you order 12 then you are
		entitle	d to another free. Please state which one you
			Note the figure on the extrme left if the pack mber and the next figures is the quantity of
		items	in the pack, finally a short description.
	BD2	5	13A spurs provide a fused outlet to a ring main
	UUL	5	where device such as a clock must not be switched
	BD7	4	off in flex switches with neon on/off lights, saves
	BD9	2	leaving things switched on 6v. 1A mains transformers upright mounting with
	BD11	1	fixed clamps
			61/2" speaker cabinet ideal for extensions, takes your speaker. Ref BD137
	BD13	12	30 watt reed switches, it's surprising what you can make with these - burglar alarms, secret swit-
	BD22	2 2	ches, relay etc. etc. 25 watt loud speaker two unit cross-overs
-	<ul> <li>BD29</li> <li>BD30</li> </ul>		B.O.A.C. stereo unit is wonderful value nicad constant current chargers adapt to charge
			almost any nicad battery
	BD32	2	humidity switches, as the air becomes damper the membrane stretches and oeprates a microswitch
X	<ul> <li>BD34</li> <li>BD42</li> </ul>		2 meter length of connecting wire all colour coded 13A rocker switch three tag so on/off, or change
	BD45	1	over with centre off 24hr time switch, ex-Electricity Board, automati-
	0040	'	cally adjust for lengthening and shortening day.
	BD49	10	Original cost £40 each. neon valves, with series resistors, these make
	BD56	- 1	good night lights mini uniselector, one use is for an electric jigsaw
			puzzel, we give circuit diagram for this. One pulse
	BD59	2	into motor, moves switch through one pole flat solenoids - you could make your multi-tester
	BD67	1	read AC amps with this suck or blow operated pressure switch, or it can
			be operated by any low pressure variations such as water level in water tanks
	BD91	2	mains operated motors with gearbox. Final speed 16rpm. 2 watt rated
-	-BD103/	1	6 750MA power supply, nicely cased with input
	BD120	2	and output leads stripper boards each contains a 400v 2A bridge
			rectifier and 14 other diodes and rectifiers as well as dozens of condensers etc
	BD122 BD128	10m 10	twin screened flex with white pvc cover very fine drills for p.c.b. boards etc. Normal cost
			about 80p each
	BD132	2	plastic boxes approx, 3" cube with square hole through top so ideal for interrupted beam switch
	BD134	10	motors for model aeroplanes, spin to start so needs no switch
	*BD139	6	microphone inserts - magnetic 490 ohm also act as speakers
	BD148	/ 4	reed relay kits you get 16 reed switches and 4 coil sets with notes on making c/o relays and other
	80140		gadgets
	BD149	6	safety cover for 13A msockets - prevent those inquisitive little fingers getting nasty shocks
	BD180	6	neon indicators in panel mounting holders with
	BD193	6	5 amp 3 pin flush mounting sockets makes a low cost disco panel - need cable clips
	BD196	1	in flex simmerstat - keeps your soldering iron etc always at the ready
	BD199	1	mains solenoid very powerful has 1" pull or could
	BD201	8	push if modified keyboard switches – made for computers but have
	BD210	4	many other applications transistors type 2N3055 probably the most useful
	BD211	1	power transistor electric clock mains operated put this in a box and
	BD221	5	you need never be late 12v alarms make a noise about as loud as a car
1	-		hom. Slightly soild but OK
	BD242	2	$6'' \times 4''$ speakers 4 ohm made from Radiomobile so very good quality
7	BD252	-)	panostat, controls output of boiling ring from simmer to boil
-	80259	50	leads with push on $\frac{1}{4}$ " tags – a must for hook ups – mains connections etc
	BD263	2	oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted
	BD268	1	into pattress
			mini 1 watt amp for record player. Will also change speed of record player motor
	BD283	/ 3	mild steel boxes approximately $3^{\prime\prime} \times 3^{\prime\prime} \times 1^{\prime\prime}$ deep – standard electrical
-	BD293 BD305	50	mixed silicon diodes tubular dynamic mic with optional table rest
2	80667	2	4.7uf, non-polarised block capacitors, pcb mounting
	BD400	4	Books. Useful for beginners. Describes amplifiers,
	BD653	2	test equipment and kit sets Miniature driver transformers. Ref LT44. 20k to
	BD553a	2	1k, centre tapped 3.5 volt operated relays, each with two pairs CO
	Most of	her packs	contacts still available and you can choose any as your free
	one.	F	,,,,,,,,,,

#### POWERFUL IONISER

Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, shop workroom etc. Makes you feel better and work harder – a complete mains operated kit, case included £12.50 + £2 P&P. Our ref 12P5.1.



25A ELECTRICAL PROGRAMMER Learn in your sleep. Have radio playing and kettle boiling as you wake – switch on lights to ward off intruders – have a warm house to ward on initiders – have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/ off switch. A beautiful unit at £2.50.

ULTRA SONIC INTRUDER ALARM. Small, nicely cased, will detect movement in a room up to 10m × 10m. Ingenious construction makes it independent of the mains; cannot be switched off, even with its ULTIA SUMIC INTRUDUE ALARM. SMall, nicely cased, will detect movement in a room up to 10m. X 10m. Ingenious construction makes it independent of the mains; cannot be switched off, even with its ovioff switch, until you know the socret, thas delayed action enabling you to switch it on and leave the room; it has an inbuilt piezo sounder which is very penetrating and high pitched and would inghine away most intruders. Has internal switching and could be coupled to an outdoor alarm if required. It is the basis of a very efficient burglar alarm, or has other uses. For instance: you could disconnect the internal sounder and using the internal switches you would know when somebody arrives without that person being aware that you know. Similary, the unit could be used to operate other equipment ultra-soncally. It is brand new, guaranteed OK, complete bul less battery (PP3 alkaline type). Price is E20 plus £3 insured delivery. Our ref 20P11.

110 DECIBEL HORN. For use with the ultra sonic intruder detector. Ideal for external positioning to attract the attention of neighbours should you have an intruder. This unit has its own mounting bracket and comes complete with good length of lead. Price C2. Our ref 7P9. Incidentally, this could also be used as a loud speaker.



ATARI 65XE COMPUTER At 64K this is most powerful and suitable for home and business. Brand new, complete with PSU, TV lead, owner's manual and skx games. Can be yours for only £45 plus £3 Insured deilvery.

DATA RECORDERS. ACORN for Acorn Electron, etc., reference number ALF03, with TV lead, manual and PSU. Brand new, Price £10 plus £1.50 post. Order ref 10P44. ATARI XC12 for all their home computers. With leads and handbook. Brand new, Price £15 plus £2 post. Order ref 15P20.

JOYSTICK FOR ATARI OR COMMODORE for all all Atari and Commodore 64 and Vic20. New Price 55. Order ref 5P126

EXTRA SPECIAL OFFER. The ATARI Compendium contains computer 66XE, data recorder XC12, joystick and ten games for 257.50 plus £4 insured delivery.

WALKMAN TYPE PERSONAL STEREO CASSETTE PLAVERS. These are not second-hand but are slightly reject and may need some attention. All are complete with stereo headphones and are famous makes: Sanyo, Panasonic, Sony, etc. Stereo cassette type, no radio, 55 each. Our ref 5P132.

SPECIAL OFFER is ten of the cassette only version, our ref 5P132, for £40. This offer is our ref 40P3.

PANEL METERS. Beautifully made moving coil instruments In heavy duty casings, much superior to those coming from the Far East. Meter face size is 72mm x 86mm, fixing hole size is 70mm. Price is ES each. The following models are in stock: 0.5amp. Our ref SP133/40. 0-45volt DC. Our ref SP133/40V. 0-55volt DC. Our ref SP133/40V. 0-56volt DC. Our ref SP133/200V. 0-100 DC. Our ref SP133/200V.



ORGAN MASTER is a three Chickin MASTER is a time octave musical keyboard. It is beautifully made, has gold plated contacts and is complete with ribbon cable and edge connector. Brand new, only £12 plus £3 postage. Order ref 12P5.

MUSIC FROM YOUR SPECTRUM 128. We offer the Organ Master three octave keyboard, complete with leads and the interface which plugs into your 128. You can then compose, play, record, stor give, your own music. Price £19 plus £3 spectal packing and postag Order ref 1921. Order ref 19P1-

CAMERAS. Three cameras, all by famous makers, Kodak, etc. One disc and two different instant cameras. All in first class condition, believed to be in perfect working order but sold as unlested. You can have the three for £10 including VAT, which must be a bargain – if goty for the leases, flash gear, etc. Our rel 10P58.

HAND-HELD VIDEO LAMP: Mains operated and will enable you to take professional standard videos. Made by the famous Ferguson Company, this uses a 1000 hadogen tamp in a fan cooled, hand-heid and hand-switched metal housing. Comes complete with optional bam-door assembly and camere bar. Obviously immedied to retail at over £60, we offer these at £30 each plus £3 insured delivery. Our ref 30P3.

1/8th HORSEPOWER 12 VOLT MOTOR. Made by Smiths, the body length of this is approximately 3in, the diameter 3in and the spindle 5/16th of an inch diameter. It has a centre fange for fining or can be fixed from the end by means of 2 nuts. A very powerful itide motor which revs at 3,000 pm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years. Price £6. Our ref 6P1, discount for quantities of 10 or more.

PHILIPS LASER This is helium-neon and has a power rating of 1.6mW. Completely safe so long as you do not look directly into the beam when eye damage could result. Brand new, full spec, 530 pitus £31 naured delivery, Vains operated power supply for this tube gives 8ky striking and 1.25ky at 5mA running. Complete kit with case £15. No extra for post if ordered with tube. Battery PSU also available £15.

HIGH RESOLUTION MONITOR. 9in black and white, Uses Philips tube M24/306W. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new, E16 plus £5 post. Our reference 16P1.

12 VOLT BRUSHLESS FAN, Japanese made. The popular square shape (4½n x 4½n x 1¾n). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref 8P26. FDD BARGAIN

a

31/zin made by Chinon of Japan. Single sided, 80 track, Shugart compatible interface, interchangeable with most other 31/zin and 51/ain drives. Completely cased with 4 pin power lead and 34 pin computer lead. £40. Our ref 40P1.

OUR ALADDIN'S CAVE. You may be a new reader and not know that we have a shop at 12 Boundary Road. Hove, where you can go and have a browse around at our assortment of 'goodies'. Unfortunately, because of staff shortages, we cannot be open on Saturdary syst, so the hours are 9 30am to 500pm, Monday to Friday. We of course still serve callers at 250 but request that you bring a completed order form as 250 is really the mail order depot.

Generous discounts for quantities



companies. Access & B ca (0273) 734648 or 203500.

#### **BARGAINS STILL AVAILABLE**

#### DOUBLE MICRODRIVES. We are pleased to

advise you that the Double Microdrives which we were offering at about this time last year as being suitable for the 'OL', 'DPD' and several other computers are again available, same price as before namely £5. Our ref 5P113,

NDISE FILTERS – MAINS INPUT PLUG TYPE. Japanese made, this is a chassis mounting block with a built in noise filter to cut out surges and voltage peaks which could interfere with and possibly even damage your equipment. These are easy to mount and have a flange with how foung noise. They take the standard 3 (lat pin plug, 2amp model. Price 3: each. Our ref 3P50.

LEAD LAMP.-Molonsts' Special. Normal hand-grip type holder, with glass cover to protect the lamp and further protection in the form of a wire guard with a hook for hanging. Deals loft light for or car repairs, etc. Takes 60w lamp. Has good length flex. Price \$4 Dwt.ref 4P31.

PHONE LEADS. 3 metres long, correctly colour coded, one and has flat plug which fits standard BT socket, other end has tag connectors. 2 for £1. Our ret BD639.

SUB-MIN TOGGLE SWITCH, Body size 8mm  $\times$  4mm  $\times$  7mm SBDT with chrome dolly fixing nuts. 4 for £1 00. Order ref BD649:

VERY POWERFUL MAGNETS. Although only less than 1 in long and not much thicker than a pencil these are very difficult to pull apart. Could be used to operate embedded reed switches; etc. Price 50p each, 2 for £1.00. Our ref BD642.

**CLEAR LACQUER.** Quick drying for the protection of transfers, markings, maps, etc. Also protects wood and metal. Exceptionally clear. Large can for  $\mathfrak{L}1$  00. Order ref B0660.

PAPST AXIAL FAN. MANUFACTURERS REF NO TYP4580N. This is mains operated 15watt tating and in a metal frame with metal blades so 0K in high temperatures. Body size approximately 434in square  $\times$  13% in thick. £6 00 each, pius £1.00 postage. Our re 6F6.

SOFTWARE FOR REMAKING, Just arrived, Large quantity of maily games. All are SUP INVERTING REMAINS, JUSI allives, Large quantity of inlang galaxies, and and on normal lage spool in cassette holders and should be suitable for wiping out and re-making into games or programmes of your own design. We offer 5 different for 22 or 100 assorted for £20. Important note. We cannot say which titles you will get nor accept orders for specified titles or 'so many, all different', etc., so only order you can take them as they come. Order ref 5 for £5 is 2P224, 100 assorted is approximate. you car 20P10.

VERY USEFUL MAGNETS. Flat, about 1 In long, <sup>1</sup>/2 in wide and <sup>1</sup>/4 In thick. These are polarised on their faces which makes them ideal to operate reed switches in doors and windows or to hold papers or labels, etc. to metal cabinets, or even to keep cupboard doors firmly closed. Very powerful. 6 for £1. Our ret BD274(a).

3 CORE FLEX BARGAIN No. 1 – Core size 5mm so ideal for long extension lead carrying up to 5 amps or short leads up to 10 amps. 15mm for £2. Drder Ref 2P189.

3 CORE FLEX BARGAIN No. 2 – Core size 1.25mm so suitable for long extension leads carrying up to 13 amps – or short leads up to 25Å, 10m for  $\Omega$ . Order Ref. 2P190.

ALPHA-NUMERIC KEYBOARD - this keyboard has 73 keys with contactless capacitance switches giving long trouble free life and no confact bounce. The keys are arranged in two groups, the main area field is a OWERTY array and on the right is a 15 key number pade, board size is approx. 13" x 4" — band new but offered at only a fraction of its cost namely £3, plus £1 post. Ref. 3P27.

TELEPHONES – We have just received a consignment of desk telephones, rotary dial type, in good working order and in a new condition. We offer these at £5 each plus £2 special packing and postage. This model would have the connecting lead with four tags to groing into the old type junction box. Dur et §F137.4 Or to £5 you can have the same telephone but with the new flat BT type plug fitted. Our ref 6P10.

WIRE BARGAIN – 500 metres 0.7mm solid copper tinned and p.v.c. covered. Only  $\mathfrak{L}3 + \mathfrak{L}1$  post. Ref. 3P31 – that's well under 1p per metre, and this wire is ideal for 63 push on connections

 $\label{eq:capacitor bargain - axial ended - 4700uf @ 25v Jap made. Normally 50p each, but you will get 4 for £1. Ref. 613.$ 

SPRING LOADED TEST PROOS - heavy duty made by the famous Bulgin company. Very good quality. Price tour for E1. Ref. BD597

SOLAR POWERED NI-CAD CHARGER 4 NI-CAD batteries AA (HP7) charged in eight hours or two in only 4 hours. It is complete, boxed ready to use unit. Price 66. Our Ref. 6P3.

FREE POWERI Can be yours if you use our solar cells – sturdily made modules with new system bubble magnifiers to concentrate the light and so eliminate the need for actual sunshine – they work just as well in bright light. Voltage input is .45 – you join in series to get desired voltage – and in parallel for more armos. Module A gives 100mA. Price £1. Our Ref. BD631. Module C gives 400mA. Price £2. Our ref 2P199. Module D gives 200mA. Price £37-Our Bef. 342

SWITCH AC LDADS WITH YOUR COMPUTER. This is easy and reliable if you use our solid state relay. The has no moving parts, has high input resistance and acts as a noise barrier and provides 44W isolaton between logic terminals. The turn-on voltage is not critical, anything between 3 and 300, intergat\_exertance is about 1K onm. AC loads up to 10A can be waithed. Prevents 12 each. Ref. 2P183.

**METAL PROJECT BOX.** Ideal size for battery charger. power supply etc; sprayed grey, size  $8^{\circ} \times 4^{1}$ / $4^{\circ} \times 4^{\circ}$  high ends are lowvered for ventilation other sides are flat and undrilled. Order Ref. 2P191. Proc. 42

BIG SMODTHING CAPACITOR. Spraque powertytic 39,000uF at 50V. £3. Our Ref.

4-CDRE FLEX CABLE. Cores separately insulated and grey PVC covered overall. Each copper core sized 7/0.2mm. Ideal for long telephone runs or similar applications even at mains voltage. 20 metres £2. Our Ref. 2P196 or 100 metres coll £8. Order Ref. 8P19.

13A PLUGS. Good British make complete with fuse, parcel of 5 for £2. Order Ref

13A ADAPTERS - Takes 2 13A plugs, packet of 3 for 12 Order Rel, 2P187.

POWERFUL 12V MOTOR was intended for Sinclair Electric Car, rating approx.  $v_3$  HP. Price £15 plus £2 post.

RE-CHARGEABLE NICADS 'D' SIZE these are tagged for easy joining together but tags can easily be removed, virtually unused, tested and gntd. \$2.00 each. Ref 2P141, 6 for \$10. Ref 10P47.

6T HANDSET with curty lead terminating at 8T plug. Colour cream. Price £5.00. Our reference 5P123.

SINGLE SCREENED FLEX 7.02 copper conductors, pvc insulated then w screen, finally outer insulation. In fact quite normal screened flex, 10m ref BD668. Ditto, but solid conductor. 10m for £1. Our ref BD668A. then with copper 10m for £1. Our

WHITE CELLING SWITCH 5 amp 2 way surface mounting with cord and tassle. Made by the famous Crabtree Company. Price £1 each. Our ref BD528.

NEW, LARGER, MORE VARIED CATALOGUE NOW READY (includes Credit Tickets PRIORITY CATALOGUE ORDER (3), Special Offer sheets, Order Form & Pre-Paid envelope) only £1.00 or free on Name. Address application with any order over £15. Prices in new catalogue and advertisement may vary as material for advertisement I enclose £1.00 cheque/P.O./cash for catalogue is prepared 6/8 weeks before issue of Television. NEW REDUCED PRICES FOR TELEVISION SPARES VALVES ANOTHER SPECIAL OFFER UNIVERSAL P.C.B. ASSEMBLY JIG 0 ACCOMMODATE P.C.B. SIZE UP TO MAXIMUM: 265 × 238m SPECIAL OFFER APRIL 12241 (37501) 3227 (17706) 1227 Type DAF96 DF96 DK96 DM71 DY86/87 DY802 CV850 CV4015 E180F EABC80 
 (f)
 1.45

 1.45
 1.45
 1.45

 1.45</td TV ANTENNA AMPLIFIER JVC Cont. HR-D111EG HR-D120E HR-D120EG HR-D121E HR-D121EG HR-D225E HR-D125EG REPLACEMENT 18.00 18.00 18.00 18.00 18.00 18.00 18.00 VIDEO . (G.E.C.) 1-WAY KU700 T100 
 TUO
 I-YWA1
 IC/YWA1

 1 in 1 out attenna amplifier for colour and black and white TV. White plastic case with on-off switch, LED indicator and Im lead. Band width
 300MHz 890MHz

 Band width
 300MHz 890MHz
 750

 Minoedance
 750
 751
 ACA VP7100 VP77EG VP788EG VS1EG VS2EG VS10EG VS9500EG VS9500EG VS9500EG VS9900EG 1-----18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 11 HR-D125E N.E.C. N-830EG N-831EG N-832 N-833EG PVC-2300 PVC-2400 (NORMAL PRICE OVER £50.00) OUR PRICE £15.00 18.00 18.00 18.00 18.00 18.00 19.00 mpedance. Power EAF42 EB91 EBC41 ECC81 ECC82 ECC83 ECC84 ECC85 ECC88 ECC88 ECC185 12V Twin - 10 . ims Fluorescent Lamp 12 Double Tubes Attractive white fitting, ribbed perspex diffuser. On/off switch. Sit cable. Transistorised circuitry. Keyhole fixing, 12V D.C. 8W Tubes, Dimensions: 368 x 67 x 43 mm. Ideal for Caravens, Boats, Vans etc. 14 10+ 50+ 14 £4.99 £4.50 PVC-2400 NA THONAL PANASON NV2000 NV3200 NV332 NV332 NV330 NV460 NV7200 NV460 NV7200 NV460 NV7200 NV8600 NV8610 VEH0121 VEH0218 PRICE: £7.99 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 25.99 24.70 24.70 46.75 18.00 18.00 18.00 18.00 18.00 20.10 "CLOSED-CIRCUIT" TELEVISION SYSTEM PRICE £150.00 Domrising: 1 × CAMERA 1× MONITOR 1 × CAMERA mrising: ECC18 ECF80 ECF82 ECF83 ECF83 ECF83 ECF83 25.99 S 12NOLT RECHARGEABLE UNIT ECH84 ECL85 ECL96 EF90 EF91 EF95 EF183 EF184 10 × D × Size Ni-Cads (4 Ah) in a black plastic case, Fuse h 12 volt output when charged equipment. Fully guaranteed. 245 × 75 × 75 mm. CONFLET HITACHI VT3000 VT11EG VT14 VT33 VT34 VT4000 VT4200 VT4200 VT5000 VT5000 VT9000 VT9000 VT9500 VT9700 SANYO VTC3000 Illustrations not to scale. For guidance supplied may vary from those illustrated. only - actual Items 19.55 26.75 28.25 28.00 28.75 26.75 26.75 26.75 26.50 25.50 25.50 25.50 25.50 23.10 £7.99 each + P&P £1.85 + VAL VC200 VC300 VC300 VC3300 VC3300 VC3300 VC3300 VC9300 VC9700 26.95 26.95 26.95 26.95 26.95 26.95 26.95 £7.25 for 10 + P&P 14.50 + WAT OUARTZ-HALOGEN SPOTLIGHT RUANT 2-TRALOUED STOLLISTI ison beid or hanging. Heat resistant poly-carbonate nousing, highly polshed reflector. Protocive lens voer, doubles as base stand. Writh Driffl switch not 12t curly cable terminating in clear lighter plug troduces 250,000 candle power – 5 times the netenshy of average car headlamps gwer: 1240.c. 43, 55W.OMS: 180 × 88 × 110mm. CHARGING UNIT FOR THE ABOVE TEV UNIT EH90 EL34 EL36 EL81 EL84 EL85 EL85 EL95 EL509 EL509 EM80 EM80 EM80 EV51 EV96/87 EV98 EV98 EV98 EV900A Annafactured by Sait, these chargers are suitable for the above battern packs advertised in the May assue of "WHAT WIDED" — Page 61. The chargers are tas as we have modeled them to a suitable to the chargers are tas obtained after 10-12 hours lovernight charging. Supplied complete with main and charging each fitted with a spin plot (Bp mp) and version available upon request). Abhough as equipment, these chargers are half version date. VC9700 **SONY** SL-C44E SL-C6E SL-C6ES SL-F1 SL-F30PS SL-F30PS SL-20E SL-C24E SL-C24E SL-C30E7 VC9700 is In lead £5.99 28.00 19.00 19.00 19.00 28.00 28.00 25.00 28.00 28.00 28.00 28.00 and charging lead fitted with a 4-pin plug (5-pin plug version available upon request) Athough its: equipment, these chargies are high tested and guaranteed Dimensions 355 × 280 × 150 mm. 4-PIN £10.00 6-PIN £10.00 + £1.85 P&P + VAT V19/00 JVC HR2200E HR250E HR3300E HR3300E HR3600EG HR7600EG HR7600HS HR7600HS HR7600HS HR7600HS HR7600HS HR700HS HR700HS HR700HS HR7010E HR0110EG HR0110EG 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 18.00 NI-CAD BATTERY CHARGER 1+ £4.50 each 10+ £4.25 each 100+ £3.75 each Univer PRICE HELPING HANDS 
 NI-CAO BATTERIES

 AAA
 £1.25
 £1.20 ea/10

 AA
 .50 .55 ea/10
 .56 ea/10

 C
 £2.10
 £1.30 ea/10

 D
 £2.20 ea/10
 £2.20 ea/10

 D
 £2.20 ea/10
 £3.90 ea/10
 WITH **OSCILLOSCOPES** MAGNIFIER TOSI V31 V33 5470 V55G V57G V960 28.00 28.00 25.50 18.00 18.00 30.00 COSSOR CDU150. Dual Trace. 35MHz. Delay Sweep. Dual State. Portable 8 × 10 Display with Manual. Price £165.00 each £3.99 BOOKS OATA VOLUME 1 - Trans data & drawings Carriage £10.00 each Plus V.A.T. DATA VOLUME 2 - as above C-Z DATA VOLUME 3 - 2N-2N8735 Set of 4 DATA VOLUME 4 - 2SA & on DIODES VOLUME 4 - 2SA & on DIODES VOLUME 2 Path VOLUME 2 £3.99 £10.75 £10.20 £13.50 £13.50 £10.65 £220.60 £13.55 £19.50 £13.00 £13.00 £14.65 £13.00 £13.00 £13.00 HR-D1106 18-50 PINCH RÖLLERS AKAL 7100/77EG/1EG/2EG/10EG/2EG/300/9500/9700/9800 245 Other types of Oscilloscopes arriving all the time-telephone for info' on latest stock. LOGIC PROBE n use - good quality - logic probe. Displays the logic state of each gate of D dos, etc. devices Logic state displayed in light and sound. Pulse impriment capability allows pulse detection down to Smarc. plane complete with comprehensive instruction manual. SIGNAL GENERATORS Marconi TF2002AS 72MHz, A.M. & F.M. **£120.00** Marconi TF2002B 88MHz, A.M. & F.M. **£120.00** CARRIAGE £10.00 + VAT Both Volumes I.C. CMOS I.C. TTL I.C. LIN VOLUME 1 I.C. LIN VOLUME 2 abon: ing voltage: 4-16Vdc hokis: HI - 70% Vcc; LO - 30% Vcc Impedance: 1 Mohm 2 nput impedance: 1 Mohm Max. input frequency: 20MHz Drder Code - TEST/LOGIC PRICE - £7.99 RESISTORS CARBON FILM 5% 215 AAL, FAR, IYA GU SAANYO, YIC3000F SHARP, VC200700/300/387/60000/300/9500/9700 SONY, SL C44/5/67/F1/F30/3000/20/24/24/30 TUSHBA, 5470/55/57 Both volumes THYRISTORS A to Z TRANSISTORS A to Z TRANSISTORS A to Z TRANSISTORS 2N-3N Both volumes 1/4W 1R0 to 10M (E12 Range) 1/2W 2R2 to 10M (E24 Range) 1W 10R to 2M2 (E12 Range) 2W 10R to 2M2 (E6 Range) 2p each. 15p/10. 75p/100 2p each. 15p/10. 75p/100 5p each. 40p/10. 3.00/100 8p each. 60p/10. 5.00/100 T.V. AERIAL ACCESSORIES Co-Ax Cable 75 Ohm 100 Metre Reel £11.00 Co-Ax Metal Plug Co-Ax Line Socket Co-Ax Line Connector VIDEO BELT KITS AKAI HITACHI VT5000 LAMP 0.45 1+ 200 2012 Both volumes Failt range of BABANI Books on TV/RADIO/ AERIALS Etc. e.g. INTROUCTION TO SATELUTE T.V. 112 pages – Suits Beginners and Profession alka. Send for further information and list. 10+ 18p 22p RESISTOR KITS - each walue individually packed 2.15 1.05 Very pact to each value E12 – 2R1 to 1M 300 pieces Very pact to each value E12 – 2R1 to 1M 400 pieces Very pack to each value E12 – 2R2 to 2M2 365 pieces Very pack to each value E12 – 2R2 to 2M2 365 pieces Very pack to each value E12 – 2R2 to 2M2 355 pieces Very pack to each value E12 – 2R2 to 1M 353 pieces Very pack to each value E12 – 0R1 to 1M3 53 pieces Very pack to each value E12 – 0R1 to 1M3 53 pieces VT5000E 3V00/3Y22 3V29 3V35 3330 3360 7700 7650 6.5 4.50 2.96 6.50 7.75 4.70 9.50 13.75 21.75 JVC/FERG JVC/FERG JVC/THOR JVC itiway Splitters 2.20 1.30 1.45 2.40 2.34 0.56 0.68 15p 59p 5125 £1.25 £1.40 £1.75 ine 1ace Mounting sket Splitter/Combiner sket Splitter/Combiner Switched MAINS SWITCHES PB3008 Oecca/GEC SONY {Universal} PB5030 Rank Remote PB3003 Philips G8 Plastic NV300 NV777 NV2000 NV3000 NV7000 NV7200 1.62 1.16 1.44 1.50 1.30 NAT. PAN ADDITIONAL KITS ADDITIONAL KITS DISC CERAMIC 50V ZENER DIODES 568 ELECTROLYTICS R. FUSES CABLOW 20mm PRE-SET POTS-H PRE-SET POTS-V 125 pieces 55 pieces 100 pieces 80 pieces 80 pieces 120 pieces 120 pieces £3.50 £3.50 £7.25 £3.75 £7.50 £8.75 £6.75 way ideal for small hotels etc. Single Rush Mounting Outlet Double Fush Mounting Outlet Double Fush Mounting Outlet Co-Az Laads – 2 metras – PU/PL Co-Az Laads – 2 metras – PU/Socket TW/Mede Anghlfer 7233 Improves signal 3 times Beend Set Amplifier 723 Improves signal to 2 sets 50% PB3003 Philips G8 Plastic PHILIPS KT3 (Remote) PB3020 PHILIPS KT3 Non Text 5031 PHILIPS G11 Remote 205/1 ITT CVC5 SANYO 0.45 VTC5000 VBS9000 VTC9300 PB3005 PHILIPS G11 Thorin TX90 00E2 158-001 2.48 1.62 3.05 2.10 1.72 1.10 V1C9300 SHARP 5 SHARP 11 VC6300 VC7300 VC9300 SHARP SERVICE AIDS £16.95 Aero Duster Super 40 Rapid Fire Extinguishes Silicone Grease Tube Silicone Grease Spray Heat Sink Compound Solda-Mo. Solda-Mo. Standeti gauge 1.2mm Industrial reel 1.2mm SetWille AIDS Golddene Degrassing Solvent Supa Freaze-ti Foam Cleanser VideoTape Head Cleaner Pastic-Seal Aero-Klene Anti-Static Spray ellist Excel Polish TRIPLERS 1.55 1.94 3.45 1.82 TRIPLER Universal PHILIPS KT3 30AX 196/17 + Pos Focus £15 75 1.78 1.18 1.45 1.26 1.14 1.40 1.16 1.28 1.24 485 675 875 SONY 1.64 2.58 1.90 SL-C5/7 SL-C8000 CB Interference Suppressor 9709 Minimises CB interference on TV 15.55 1,48 TV/FM Diple TOSHIBA IDLERS SHARP SHARP HITACHI HITACHI HITACHI FISHER PISHER SANYO V7540 REMOTE CONTROLS parates UHF TV signals from FM radio signals £4.95 0.80 15.00 15.00 14.75 15.00 15.00 1.6 155 159 PHILIPS KT3/30 Teletext PHILIPS KT3/30 Non Text THORN T718 TX9/10 3W LC THORN T720/24/32/36/39 THORN T731/T738 NIDL 0005 GEZZ NIDL 0006 GEZZ SOLDERING SECTION aldering Station complete with 30W 4 00W from (state which) 253 W iron skycomplete with stand, m lead & plug attached 537 from Kit 259 15 from Kit 255 W iron kä/complete with steel plug attached 7 180% as above 19 9000 19 9000 19 9000 19 9000 19 9000 19 9000 19 9000 10 6886971 IDLER 143-0-4204-00400 GEAR IOLER 143-0-4204-00900 RELL DRIVE PULLEY VTC 5150 662T-01201 TAKE UP IDLER PU51402/A 6 x. 3 with stand, 1 0.20 7.99 8.30 Antex 15W vron Antex 18W vron Antex 26W vron Antex elements Antex brits Antex brits Soldersucker Spare nozzles for Soldersucker 28 5.40 5.80 5.80 3.20 1.15 2.20 2.99 0.80 BT APPROVED EQUIPMENT Master Socket (Hush) 12.30 Sacondary Socket (Hush) 15.10 Sacondary Socket (Hush) 15.10 Sacondary Socket (Hush) 15.10 B.T. Cable (per metre) 15 B.T. Cable (per metre) 15 Per 100 metres 15 Line Jack Cord with Plug 15.25 Winng Diagram 0-4.63 1.32 7.55 1.55 £2.90 FERG/JVC THORN/JVC PANASONIC PANASONIC MOTORS 36a 25p £17.35 £28.04 VXP 0344 Reel Motor SANYO VTC 5150 4-529V-10800 ныя токо: ЗАЧТ U VI С 5150 4-529V-10800 8.00 Reel Motor SHARP VC9300/9800 RMATV 1008 GEZZ 19.25 Capstan Motor - FERGUNG 3/35 PU55371V/M 28.25 Audio Motor Recorder 12V CW 34mm 3.15 Audio Motor 9V CW 34mm 3.15 ORVX PORTASOL GAS SOLDERING IRON ICE £16.00 each. SPARE TIPS - 1, 2.4, 3.2, 4.8mm £4.00 each FULL RANGE OF TRANSISTORS ES.90 I.C's, CMO's I.C's, CMO's See our cu Electrolytic Capacitors Disc Caramic Capacitors Thick Film Capacito SOLDER: 60% TIN 40% ALLOY 22g. Non-corrosive Multi-core Solder. S00gm Reel £4.33 each. 10 Reels 18g 23.75 DESOLDERING PUMP Polyester Capac Polyestyrene Cap FM TRANSMITTER European made Metal Oxide Capacitor Very High Quality 'MINI-BUG' -- Ideal for Beby Alarm etc.!! ONLY E2.98 each 18g. Non-corrosive Multi-core Solder. 500gm Reel £4.99 each. 10 Reels 18g £3.75 SAFEBLOC Normally £8.99 SPARE TIP 0.60 FOR DUICKLY AND SAFELY TESTING EQUIPMENT ON MAINS VOLTAGE. SIMPLY CONNECT WRE TO CUPS AN CLOSE LID. 81.75 À Very good range is obtainable - we have obtained over V2 mile, but it does depend on conditions Simply remove cover - insert battery - and you're ready 20mm FUSES MAINS PLUGS 13A FUSED UIICK 8L0W - 80mA, 100, 125, 160, 200, 250, 315, 400, 500, 630, 800, 1A, 1.25, 1.5, 1.6, 2, 2.5, 3.15, 4, 5, 6.3, 45p/10 IME DELAY - 50mA, 60, 800, 100, 125, 160, 200, 250, 315, 400, 500, 630, 00, 1A, 1.25, 1.6, 2, 2.5, 3.15, 4, 5, 6.3, 10 90p/10 Simply remove core to go Reception can be obtained on any EM. Radio Frequency: 105-109 MHz F.M. Power: PP3 9V Battery (not included). Dimensions: 425" × 225" × 0.75". Drder Code – \$0,734 3 PIN 1 @ 46p each 10 @ 42p each 100 @ 35p eac 1 DONIESTIC MAINS FUSES £1.00/10 3A. 5A. 13A Price: £8.50 1 4 QUICK FUSES 14 1 254 24 124 50p/10 ORDERING: All components are brand new and to full specification. Please add £1.00 postage/packing (unless otherwise specified) to all orders EAST CORNWALL COMPONENTS and then add 15% VAT to the total. Minimum order £5.00. Either send **119 HIGH STREET** cheque/cash postal order or send/telephone your Access or Visa


PO

WEM SHROPSHIRE SY4 5TT TEL: 0939 32689 TELEX: 35565

RARCIAVCARD

VISA

add £1.00 postage/packing tuniess otherwise specified) to all orders and then add 15% VAT to the total. Minimum order £5.00. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges etc most welcome. (Do not forget to send for our catalogue – only £1.00 per copy). Delivery by return on ex-stock items. All prices subject to change without notice. RETAIL shop open Mon-Sat 9.00 5.00. Sat 9 12.00

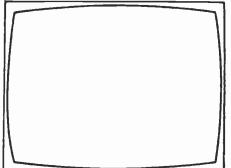

#### **EDITOR**

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 393.

#### ADVERTISEMENT MANAGER

David W.B. Tilleard 01-261 6671

#### SECRETARY

Janet Reeve 01-261 6671

#### CLASSIFIED ADVERTISEMENTS

Pat Bunce 01-261 5942

#### ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey 01-261 6035

#### SUBSCRIPTION ENQUIRIES

0444 440 421

#### **CORRECTIONS**

See note on page 419.

#### **COVER PHOTO**

This month's cover photograph shows the panel layout in the B and O L/LX2500/2800 chassis. See article on page 424.

**TELEVISION APRIL 1989** 

# TELEVISION

#### The Spares Business

The TV/VCR Spares Guide that comes with this issue is the fourth we've produced. When we compiled the first one in 1986 we thought that most of the spadework had been done. Just a matter, we felt, of a bit of checking and a few revisions next time. How wrong we were! We continue to be surprised at the extent of the changes in this section of the industry year by year. Each year we have had to reset the Guide completely – there just hasn't been enough of the old one left unaltered to make it worthwhile to preserve anything. It makes us wonder for how long the Guide continues to be useful once published? Maybe we should update it at six monthly intervals? Many of the important changes are included in the Teletopics column as they occur of course, and provided a listing of this sort doesn't get too out of date – yearly publication ensures that – it at any rate serves as a starting point: directory enquiries or someone at the other end will tell you about any changes that have taken place, though it's all very time consuming.

consuming. There have been deeper influences at work behind the mere changes of address, telephone number and franchises. For a start the role of the specialist component distributor has increased considerably in recent years. As far as manufacturers are concerned, spares have become an increasing headache. For a forward looking management concerned with the chassis after next and the way in which the market is evolving, the idea of having to devote time to the problems of yesterday's sets, many ten or twenty years old, is not looked upon favourably. Of far greater concern than management time however is the money locked up in stocks, the cost of storage and the expense of handling orders for lots of small items and lots of small (relatively) payments. Simpler by far to sell TVs and videos by the lorryload. There is too the hassle factor. Why isn't this item available and so on? Really the supply of spares is probably not logically a part of running a modern mass production operation – which is not to say that many firms don't continue to make a very good job of it.

many firms don't continue to make a very good job of it. The pressure on costs and profits in a highly competitive industry is probably the main factor that has led to so many major manufacturers deciding to contract out their spares operations. In-guarantee commitments to appointed dealers have to be serviced of course – and those dealers get a better service when the manufacturer isn't struggling under a mountain of orders for bits and pieces for items of every sort produced over an ever extending time span. For many, perhaps most, in the servicing industry today the first call for spares will be to a distributor rather than to a manufacturer's service department. It helps in many ways. Orders for a wide variety of items for different brands can be obtained from a single source, and the distributor knows perfectly well which bits are common to a number of manufacturers' models and can stock, supply and advise accordingly. Such firms are well placed to judge the needs of the servicing industry and to cater for a wide range of different equipment. So CHG, CPC, HRS, SEME, Willow Vale and one or two others are playing an increasing role in the spares supply industry – and in the supply of accessories, service

So CHG, CPC, HRS, SEME, Willow Vale and one or two others are playing an increasing role in the spares supply industry – and in the supply of accessories, service equipment and other items. It's a logical development, since separating the provision of spares from the manufacture and marketing of products for the mass consumer electronics market is a natural step. We have long wondered why a similar split hasn't occurred at the retail end, with the public buying from one type of outlet and getting its repairs done at another. This was common in the States at one time, though we don't know the exact position today. The disadvantage is that the service shop can miss out on a potential sale when an item obviously at the end of its life is brought in. But a nice little line in reconditioned sets can take care of that.

When the specialist distributors first started to take a larger share of the spares trade we wondered how they could make a go of something the manufacturers found so unprofitable? There seem to be several answers to this. First by buying in quantity at good prices, secondly in making use of modern order handling techniques, i.e. computerisation, and thirdly in aiming to provide a first rate, same day service to a large number of known customers with accounts.

All this leaves the dabbler and the individual customer increasingly out in the cold. Most distributors will not accept individual orders and few manufacturers will supply anything other than say a few cosmetic items to keep individual customers happy. You won't find that many shops are willing to go to the trouble of obtaining the odd spare part, especially for a make or item that's the least bit obscure. Maybe there's an opening for a small orders service of some sort?

A further major factor that has led to many manufacturers reducing their after sales service to the public is consumer legislation and the threat of litigation. Modern consumer electronics products are inherently safe, especially if manufactured to BEAB approved standards. This safety can however easily be nullified by the inexperienced operator. What then if an accident occurs? Could a manufacturer who has supplied parts in good faith be held partly responsible when a bodged repair results in an accident? This possibility has concentrated the minds of more than a few manufacturers and has led to a clamp down on the supply of parts by many of them, though it must be said that many others continue to take a very relaxed attitude – if you know exactly what you want and its part number and supply payment with order you will get your spare part. It's difficult to decide on the balance of public benefit in this respect.

It's difficult to decide on the balance of public benefit in this respect. The spares industry is a complex one that has been changing rapidly in recent times. Bona fide repairers have benefitted from this, but there are still possibly some unsatisfied areas of demand.


# The Sony Trinitron Tube


The Trinitron colour tube, designed by and used exclusively by Sony in all its colour receivers, was the first to have an in-line gun arrangement. It has a single gun assembly with three cathodes mounted in line horizontally, a striped-phosphor screen, an aperture grill with vertical slots instead of the traditional type of shadowmask, and a faceplate with cylindrical rather than parabolic curvature. The Trinitron tube produces a very good display - some people, including the author, would say the best. There are sound technical reasons for making this claim, for example the design of the large electron lens which provides excellent resolution. An advantage of the cylindrical in comparison with the traditional parabolic faceplate is the fact that most of the external light that falls on it is reflected away from instead of towards the viewer, thus improving the contrast and reducing eye strain. The Black Trinitron introduced a couple of years ago gives a further improvement in this respect (the faceplate has been darkened to a black colour).

Since the first Trinitron tubes appeared in the UK in the late sixties there has not been a great deal of change in the design, though a number of improvements have been introduced. More recently we have had the Black Trinitron mentioned above and the Pan-focus gun which gives uniform focusing over the entire screen area, eliminating any need for dynamic focusing.

#### The Trinitron Gun

Fig. 1 shows the basic Trinitron gun arrangement. Note that the beams cross over during their passage through the electron lens system. We have used the traditional UK A1, 2, 3 etc. system of electrode identification though Sony prefers G1, G2 (A1) etc. which is really more logical. Conventional tubes generally employ what is

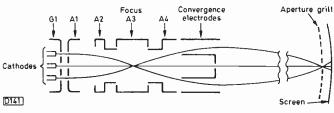

 

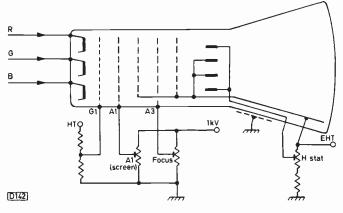


Fig. 2: Inputs to the various electrodes.

#### Nick Beer

referred to as bipotential focusing, i.e. the first anode (A1, G2) is at about 800V while the focus electrode is at around 20 per cent of the final anode voltage (e.h.t.). With the Trinitron the A1 (G2) voltage is about 200-800V, the focus electrode (A3, G4) is at around 350-800V while A2 and A4 are internally connected to the e.h.t. voltage. The convergence electrodes act as an electron prism, deflecting the beams after their cross-over in the electron lens to ensure convergence at the aperture grill. This is where the horizontal static convergence voltage is applied. Most of you will have seen the large H stat controls in Sony TV sets. By adjusting this control well away from its correct setting you can see the effects of incorrect RGB beam convergence.

In the earliest Trinitron tubes the convergence voltage was applied via a connection on the tube's neck – you may recall the rubber boots on the neck of the tube in the KV1300! Subsequently connection was made by means of a two connection e.h.t. cap. In the latest tubes an external connection is not required at this end. Instead the arrangement is as follows. A high resistance (IBR) is incorporated in the neck of the tube, between the final anode and the convergence electrode. The potentiometer to control the horizontal static convergence voltage is connected to the earthy end of the IBR, enabling the connection to be made through a pin at the tube's base.

To improve corner focusing a "double astigmatic" lens is now used. What this means is that the holes in the G1 plate, which provides prefocusing, are now oval instead of circular. To improve the focus from the centre to the edge with large-screen tubes the Pan-focus system has been introduced. This involves a change in the position and angles of the cathodes and makes it unnecessary to apply a parabolic dynamic focus waveform to the focus electrode.

Tube flashovers can destroy costly devices in the associated circuitry, though they don't usually damage the tube itself. They tend to occur during only the first 100 hours or so of tube use. A flashover consists of a discharge from one of the high-voltage electrodes to one at a lower potential. To protect the external circuits the latest tubes employ Peak Current Elements (PCEs), which are basically high-impedance resistors, within the tube. There are two of these, one from A4 to A2 and the other in series with A3. In the event of a flashover a very high voltage will be developed across these PCEs, as a result of which the charge cannot reach the c.r.t. connections and external circuitry.

As with other types of tube the degaussing shield is now incorporated within the tube. It's made of low-carbon steel which has low permeability and a thickness of only 0.15mm. This reduces the size and weight of the receiver and also greatly simplifies tube replacement.

#### Setting up a Trinitron

Many readers will probably be more interested in the alignment of Trinitron tubes. In common with the conventional shadowmask tube in its modern form, i.e. with FS screen etc., the corner convergence and focusing are not

406

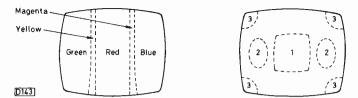


Fig. 3 (left): Display produced with the yoke pushed forward for purity adjustment. Complementary colours will be present between the primary colour areas. Adjust the purity rings to centralise the red area.

Fig. 4 (right): Areas affected by the methods of adjusting the purity. (1) Affected by the rings, (2) affected by yoke positioning, (3) corrected by using disc magnets.

perfect. This is probably a side effect of the struggle to produce lower cost receivers, with more extras piled in for the same price. With the Trinitron tube however quite a lot of twiddling is possible to try to make the picture as good as possible. We've had our fair share of faulty (usually not worn out) Trinitron tubes in recent months. Reliability doesn't seem to be as good as with earlier versions. Some seem to set up quickly and accurately while others can take hours to get right. The following notes are based on Sony's recommendations plus our practical experience.

The usual reason for alignment is tube replacement. The deflection yoke will have been removed from the old glass, as will the three rubber bungs that stabilize the yoke.

While you are about this it's a good idea to dust out and clean the cabinet after removing the old glass. The chassis should also be cleaned – this is much easier when it's out of the set. Also clean the e.h.t. cap and lead thoroughly. Standard precautions when handling c.r.t.s should be observed: wear goggles at all times; discharge the tube before removal; do not lift the tube by the neck etc.

Transfer the degaussing coils, Aquadag braid etc. to the new tube, ensuring correct routing and securing of these items. Then fit the yoke, after first ensuring that the strip of adhesive fabric under the yoke's securing clamp has been fitted to the new tube – the new c.r.t. usually comes without this.

Once the receiver has been restored to operation, display a red raster from a pattern generator and degauss the tube. To be sure about this you may prefer to place the receiver looking west so that there is minimal interference from the Earth's magnetic field. Another point worth making here for the uninitiated is to make sure that no extraneous sources of magnetism are present near the set. Sources can include a loudspeaker, a screwdriver or an isolation transformer under the bench. Another factor that can cause problems is a metal-framed bench that has become magnetised – this is quite often the case. The effect produced by these sources of magnetism is a purity error that cannot be shifted.

#### Purity Adjustment

The next factor to deal with is beam landing. With the red raster still displayed, square up the display as far as you can then push the yoke as far forward as possible to produce the display shown in Fig. 3 - red in the middle with green and blue on either side. This effect is present because the deflection angle is incorrect. The red section of the display should be at the centre of the screen. If it isn't, use the purity magnets to move it to the correct position. Move the two purity rings together in a scissor

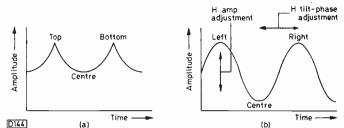


Fig. 5: Waveforms present at the dynamic convergence coils, (a) for vertical axis correction (field rate parabola), (b) for horizontal axis correction (line rate sinewave).

action. Once the red area has been centred, move the yoke backwards until a full red raster is obtained. In practice small purity errors will still be present. Position the yoke for optimum purity then correct these small purity errors by using disc magnets that stick on the back of the c.r.t. – these magnets are available from Sony under part number 1-452-032-00. They are self-adhesive. Also available are disc magnets that can be rotated with a screwdriver to give fine adjustment – part number 1-452-094-00. Fig. 4 shows the effects produced by these three methods of purity correction. Secure the yoke in position with the three rubber wedges.

#### **Convergence Adjustment**

Finally we come to convergence. Display a crosshatch pattern from a pattern generator to show the convergence errors present. The aim of convergence is to superimpose the red, green and blue rasters correctly. Thus errors show up as red, blue and green edges to the crosshatch pattern. As with purity adjustment there are three stages.

First comes static convergence. Horizontal static convergence is carried out by adjusting the voltage applied to the convergence electrodes in the c.r.t. This affects the outer blue and red beams, not the centre green beam. Adjust the H stat control so that the vertical crosshatch lines are correctly converged at the centre of the screen – red and blue on green to give white lines with no colour separation. Two ring magnets are provided on the tube neck for vertical static convergence. Adjust the rings simultaneously for optimum convergence of the horizontal crosshatch lines at the centre of the raster.

You may find that in addition to the ring magnets there is an extra magnet, or maybe two extra magnets, at the base end of the neck. These are known as BMC magnets. The usual one is mounted horizontally to give a wider range of H stat adjustment. Move it in or out. In older sets a second BMC magnet may be mounted vertically to assist with V stat adjustment. You may find it necessary to add a BMC magnet when a new c.r.t. has been fitted. If you do, recheck the purity as a BMC magnet can have quite an effect on this. Part numbers for BMC magnets are quoted in the Sony service manuals.

Dynamic convergence corrects errors at the edges of the screen. With modern flat, square screens corner convergence is particularly difficult. Dynamic convergence correction coils are mounted on the yoke, behind the deflection coils. By altering the amplitude and phase of the waveforms fed to these coils (see Fig. 5) the beam deflection angles in these difficult areas can be altered. Vertical and horizontal correction waveforms are fed to the coils.

For vertical correction at the top and bottom of the screen an inverse parabola is used. Its amplitude is

adjusted by means of the Y bow control. When this control is incorrectly set there will be separation of the red and blue horizontal lines to one side at the top and bottom of the screen.

Horizontal axis correction affects the vertical lines at the left and right of the screen. The drive waveform is this time sinusoidal, produced by an LC circuit from a line frequency pulse. The H tilt control balances the effect of the correction between the right- and left-hand sides of the screen by phase shifting the sinewave. The H amp control adjusts the amount of correction at both sides by altering the amplitude of the sinewave. The effects are fairly obvious. Misadjustment of the H amp control shows up as separation of the RGB lines vertically, at each side. If the effect is different at each side of the screen the H tilt control is incorrectly adjusted.

Corner errors, which can be stubborn and particularly annoying with teletext, can be corrected to some degree by using Permalloy stick-on magnets (part number X-4308-815-0). These are self-adhesive magnets on long strips of plastic. They are slid under the scan coils and stuck to the back of the tube. If after fine movement of these magnets you still have minute errors you will have to resign yourself to the fact that that's it. Don't waste hours trying with no evident improvement. Some tubes give perfect results, others don't – that's modern tubes.

# Servicing Compact Disc Players

#### Part 2: Laser Assemblies

The optical assembly in a CD player incorporates a gallium arsenide laser diode, a laser power control circuit, a complex lens assembly and the photodetectors that provide output voltages corresponding to the recorded digital information and any focus and tracking errors. From the servicing point of view it's probably only necessary to be aware of the safety precautions required when handling the laser, to know how to set the laser power (this is not adjustable in later machines) and to know how to diagnose a faulty laser. A more thorough understanding of the optical assembly does however help you to understand the functions of the focus and tracking servos, helps you to interpret the waveforms in these waveforms are incorrect.

As CD players have evolved, several types of laser assembly have been developed and come into use. They can be divided into two basic categories however: threebeam and single-beam arrangements. There is not a lot of difference between them, but the single-beam type uses a unique method of obtaining a tracking error signal.

#### Three-beam Optical Units

Fig. 1 shows the basic elements contained in a threebeam optical unit. The various components are as follows.

The laser diode can be considered as a LED that operates in the infra-red region, at a wavelength of around 790nm. Unlike a LED however a laser diode is very sensitive to temperature and current changes. If the current increases fractionally as a result of a change of temperature the light output will rise very sharply. Because of the laser action this increased light output will produce a further current increase leading to additional light output and so on. The cycle of events can be likened to thermal runaway in a transistor. Because of this the laser's light output must be carefully controlled. An automatic photo output control (APC) circuit is used for this purpose. An example is shown in Fig. 2. Its operation is as follows.

The light output is monitored by a photosensitive device mounted next to the laser diode. This device's output voltage is then used to control a simple current regulator. In the Mitsubishi circuit shown VR991 sets the laser's power output at approximately  $400\mu$ W, measured using a laser power meter. The output depends on the manufac-

#### Joe Cieszynski

turer and varies over a range of  $250-400\mu$ W. Regulation is carried out by Q993 which is in series with the laser. The feedback from the monitoring device is applied to the base of Q991 which, via Q992, controls the current flowing through Q993. Once set the circuit will continuously correct variations caused by temperature changes and, in the long term, will compensate for the reduced output as the laser diode ages.

Intermittent jumping, failure to play certain discs or failure to play any disc can be caused by the laser's output having fallen to such an extent that the APC circuit can no longer provide compensation. Readjustment of the laser's output is sometimes all that's required, but with a well used machine it's unlikely that this cure will be long lived. A word of warning here. When resetting the power output take care to ensure that it's not turned up too high – this would greatly reduce the laser's life (rather like operating a colour tube for a long period of time with the first anode voltages set too high – the tube ages more rapidly). In fact in some machines it's possible to blow the laser instantly if the control is turned too far. We'll discuss the various ways of carrying out this adjustment later on.

In all later machines the APC circuit is capable of compensating for diode ageing right up to the point where the diode has virtually failed. This does away with the need for power output adjustment.

The next item is the diffraction grating. This consists of a plate with a number of slits. As the single beam from the diode passes through these slits it's split (by diffraction) into three, the power in each side beam being about 25 per cent of that in the main beam.

The polarising prism is used to separate the emitted and reflected beams. As shown in Fig. 1, the polarising plate allows the emitted beam to pass straight through the prism. By the time the beam has travelled through the prism and the quarter-wave plate, been reflected off the disc and then travelled back through the quarter-wave plate it will have been subjected to a 90° phase shift. When it reaches the polarising plate once more it will be reflected (bent) towards the pickup detectors.

By the time the laser's beam reaches the collimator lens it's elliptical in shape and is diverging. The collimator lens is used to correct the divergence, adjust the beam diameter and shape it into a circle. The principle of the collimator lens is shown in Fig. 3.

The quarter-wave plate is a crystal which has been cut


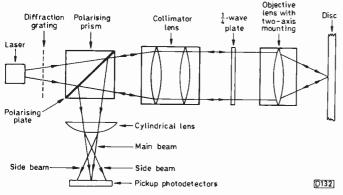


Fig. 1: Arrangement of the various items that comprise the T-type three-beam laser optical unit.

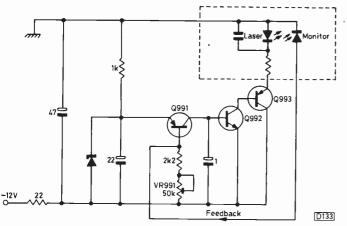

*Fig. 2: Laser current stabilising circuit used in an early Mitsubishi CD player.* 

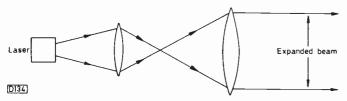


Fig. 3: Principle of the collimator lens.

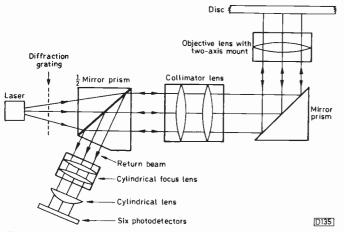


Fig. 4: Arrangement of the flat optical pickup (FOP).

so that light passing through it will be subjected to a 45° phase shift. Because the reflected beam in a CD player laser assembly passes through the quarter-wave plate twice it's subjected to a total phase shift of 90°.

The objective lens focuses the beam so that the spot diameter at the disc's reflective surface (not the outer surface of the disc) is  $1.7\mu m$ . The diameter is set by

moving the lens towards the disc until the pickup detectors give a reading corresponding to a  $1.7\mu$ m circle. This lens is also used to focus the reflected beam.

Like the objective lens the cylindrical lens is an ordinary ground lens. It's used to focus the reflected beam on to the pickup detector diodes.

The T-type laser optical assembly shown in Fig. 1 was the first type to be used. With this type the laser beam is split into three, a main beam which is picked up by the four main photodetectors to give data and focus error outputs and two side beams which fall on two further photodetectors at either side to produce the tracking error signal.

The main problem with the T-type assembly is its comparatively large size. To reduce the deck size, and make possible the introduction of personal CD systems, a smaller laser assembly was required. For this reason Sony developed the single-beam assembly. It still left player manufacturers with some design problems which we'll go into later. A better solution was found in what is called the flat optical pickup (FOP). This is illustrated in Fig. 4: you will see that the polarising prism and quarterwavelength plate have been replaced by a half mirror prism.

When light meets a half mirror prism fifty per cent of it passes straight through and the other fifty per cent is reflected. In the arrangement shown in Fig. 4 fifty per cent of the light emitted by the laser is reflected back and lost, the other fifty per cent passing through to the disc. Although the light reaching the photodetectors is only 25 per cent of the original beam it's still sufficient for accurate detection.

The advantage of this assembly lies not only in its small size. In the event of a disc having a minute mirror impurity the phase of the reflected light may alter slightly. With the T-type assembly this means that the phase of the light in the return beam is not at 90° to that of the emitted beam, resulting in incorrect reflection at the polarising prism and thus a dropout. With the FOP assembly the phase of the light is irrelevant. This type of assembly is thus not affected by such mirror impurities.

#### Single-beam Optical Units

We'll now take a more detailed look at the single-beam assembly, which was introduced a few years ago by Sony and Philips in an attempt to reduce the size of CD players. We've seen that the two additional beams in a three-beam assembly are used to produce a tracking error signal. The single-beam assembly has only four photodetectors which have to produce the data signal, the focus error signal and the tracking error signal. Although the Philips and Sony assemblies differ in the way in which they achieve this multiple use of a single reflected beam, in both cases the three signals must be separated from each other and this



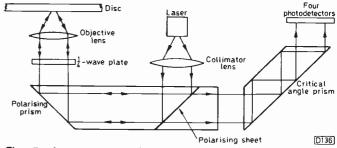


Fig. 5: Arrangement of the single-beam laser assembly used in some Sony CD players.

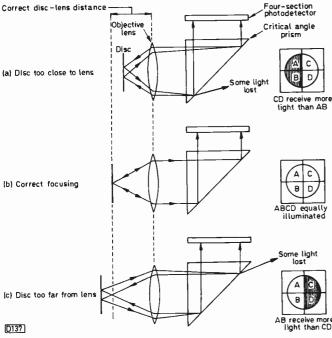

D137

Fig. 6: Use of a critical-angle prism to obtain a focus error signal with a single-beam assembly.

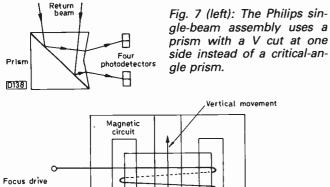

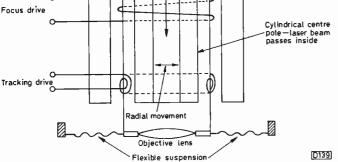


Fig. 8: Basic arrangement of the two-axis mounting for the objective lens, giving focus and fine tracking adjustment.

requires more complex circuitry in the laser preamplifier. This, coupled with the fact that the single-beam assembly still uses a polarising prism and is thus susceptible to mirror impurity effects, caused other manufacturers to opt instead for the three-beam FOP assembly. This trend has continued ever since. Whether or not an improved singlebeam device will come to replace three-beam arrangements remains to be seen.

Fig. 5 shows the arrangement of the Sony single-beam assembly. If you compare this with the arrangement shown in Fig. 1 you will see that they are in many respects the same. The main differences consist of the omission of the diffraction grating, the changed position of the collimator lens and the inclusion of the critical angle prism.

The critical angle prism does far more than bend the

beam through 90° and focus it on to the photodetectors. A brief description of its effect is called for. The prism is cut at a critical angle, 42°. Only when light enters at this angle will maximum output be obtained at the other end. Light entering at any angle other than 42° will not achieve a 90° turn, so the output will be reduced. In the Sony assembly - see Fig. 6 – the reflected beam strikes the prism at the critical angle only when it's a parallel beam, and this occurs only when the disc focus is correct. When the objective lens is too close to or too far from the disc the return beam will be either convergent or divergent. In either case part of the beam will be lost at the prism so that the light falling on two of the four pickup photodetectors will be reduced. From this the focus servo can determine the position of the object lens with respect to the disc. Fig. 6 illustrates the principle.

The Philips single-beam assembly differs from the Sony version in not using a critical-angle prism. Instead the prism is cut to a V shape at the side where the light emerges – see Fig. 7. As a result the beam is split in two. The four photodetectors are mounted in two pairs and are arranged so that the three signals (data, focus error and tracking error) can be separated. We will discuss this in greater detail when we come to servo systems.

#### The Two-axis Lens Mounting

To achieve correct focusing and tracking the objective lens is mounted on a two-axis arrangement with rubber supports, as a result of which it's free to move both vertically (for focusing) and radially (for tracking). Two sets of coils are wound on a former at the centre of which the lens is mounted. There are four permanent magnets in close proximity to these coils. The coil/lens assembly is suspended between the magnets, on rubber suspension mounts. See Fig. 8.

When a focus error is detected the servo alters the current in the focus drive coils, moving the lens towards or away from the disc until correct focus has been reestablished. When the machine is in the stop mode, i.e. there's no current in the coils, the lens will be centrally positioned. When a disc is inserted the focus servo initially pulls the lens fully inwards (away from the disc) then moves the lens progressively outwards until correct focus is achieved.

The tracking servo keeps the beam on the correct track section – as shown in Fig. 3 last month, the track pitch is only  $1.6\mu m$ . Those familiar with CD players will be aware that in most cases the laser assembly is carried across the disc on a motor-driven sled. This arrangement is sufficient for coarse tracking, but the motor and gear assembly cannot possibly work to a precision of  $1.6\mu m$ . In addition the disc may be slightly eccentric on its axis, making the track "wobble" as the disc rotates. The tracking servo therefore controls not only the sled motor but also the current in the tracking coils. The current flowing in these coils produces radial movement of the lens assembly. Radial lens movement of typically  $\pm 70\mu$ m is achieved by the coils: once this movement is at its extreme the sled motor operates briefly, restoring the lens to its central position. This joint action of the sled motor and the radial drive can be likened to the operation of a linear tracking tone arm on a conventional audio disc player.

Having taken a detailed look at the different types of laser assemblies in use, next month we'll deal with more practical matters - laser handling, adjustment and fault diagnosis.



7 5825

411

<b>SPECIAI</b>		R TH	IS MO	NTH				
UNIVERSAL TRIPLER. NEW TYPE	C	£4.00 4-6 Volts Relays GI1 6 touch unit w	with cable form & sockets	25p £13.00				
AMSTRAD Line O.P. Transistors with Diode	85p or 20 fe	24n Thom Panel with S	THORN PANELS	£15.00 to £40.00 £2.00				
VIDEO LAMPS, Long Lead. HITACHL& GEC FRAME, Thick Film. FIDELITY SPLIT DIODE	AF \$20 ECCOUSEE \$10 ECCOUSE	E£10	(357 564/03 508/161 515/353 515/173 515/357 TX9 ~ TX10 - TX100	£3.50				
NEW G11 LINE OP PANEL	IEW G11 FRAME PANEL WITH TDA 2600	TALL STREAM ST	THORN MAIN CHASS 1. TX100, TX925 E15.00 TX10 Ano TEXT DECODER TX10 \$8.0	de Cap and Lead £1.00				
PHILIPS YEARS AHEAD THE CREDIT CARD CALCULATOR Solar Powered NEW PHILIPS SBC 1833 Solar & Battery Powered Ca	alculator	ES.75 TEXT DECODER PANELS VM6103/	VM6101/2 TRX	00.013 00.013				
THORN PANEL TX9 REC & REMOTE PANELS with TX 10 DEC & DEMOTE PANELS with	th Mains Trans vith Mains Trans	£5.00 £5.00 £5.00	PHILIPS VIDEO TAP					
TX 10 TUBE BASE ON PANEL		£2.00 Philips Travelling a	dphones SBC3160's alarm clock calculator per calculator SBC1888	£12.00 £7.50 £26.00				
THORN PANEL No. 515-353, 548.02, 564.01, 509/102 THORN TX STEREO SOUND O.P. PANEL (I.C. TA THORN VIDEO AERIAL AMP 01 M4-597-001	2, 515/173, 508/161	£5.00	ALTO RANGE Resistance Pocket 3000 Philips					
KT3-K30-K4-K40 CTX ETC Mains Switch	75p each	CVC 40 Cabinets NEW IN - ITT BONES		£15.00 Post £5.00				
G8 LOPTS PHILIPS	£6.00 £3.00	LINE TRANSFORMER Philips WANDER PHONES Key Pad a	and Hand Set. No Case.	£12.00 £1.00				
PHILIPS DESK TYPE Dual Power Calculator SBC1704 K40 FOCUS POT	£7.00 £1.00	TV AERIAL AMPS VIDEO HEAD 3HSS made in t	I way £9; 2 way £11; 3 way £15; 4 way £40; 1	i way £50; 4 way 6dB each £30				
4.7μ KT3 W/W FOCUS POT HDK TPA6006	10 for £1.00 £2.00	SCIENTIFIC CALCULATOR S THORN 8500 LOPT	SBC1704 Philips. In case	£7.00 £2.00				
KT3 Triplers	AB3013/HO448328) £5.00 £2.00	NEW GEC 2110 LOPT		£2.00 50p				
RECEIVER K3 Tex Front Panels with 1.C.s (SAA.92/P/SA G8 100K Pots on Panel & Lead for 6 Push Button Unit K40 Mains Switch remote K35 Mains Switch remote K35 Mains Switch remote	£1.00 75p £1.50	DX-TUNER VHF-UHF SEND TUNER GEC 20AX POWER SUPPLY		50p 75p £10.00				
K35 Mains Switch remote K35 Aerial Socket and Plug in Lead to Tuner KT3-K30 Slider Pots 4.7ku LARGE Foacs Pots. Fits Pye, GEC, 1TT, Decca	20p each 75p	THORN 9000 4.7m 400V		40p				
8 PUSH BUTTON UNIT for CTX Chassis	£1.50 ¢ £4.00 £5.00	12 VOLT BATERY PACK Nic G8 TUNER V/C/AP on Panel	ad A.A.	£5.00 £1.50				
EX DECCA 80-100 Prame THORN 8000-8500-8800 Decoder	£5,00 £6,00 50 for £1.00	G8 SPEAKER 9,000 SPEAKER		75p £1.00				
GLASS BEADS Diodes 2007 24 G11 Tip Switch G11 HF Panel	£20.00 £8.00	THORN 9000 Sound OP Panel ONE LC K35 Decoder		£30p £7.90				
GIT IF Panel GIT Decoder Panel JVC HEADS 31:55 GIT Condenser 470/250V ITT	£8.00 £20 £2.00	K30 IF/K35 IF THORN Lopt 8500-8800		£2.00 £4.00				
G9 Power Panel	£3.50 £1.25 £2.00	TX9 THORN Tuner Panel with THORN CHASSIS 1600-1700 S		£3.00 £10.00				
Go Plabador Unit Ga Push Button Unit Ga Con Panel New Back Type KT4-KT-K30 Handert Replacement HT520 METER 20,000 First Diode Protector Logic Test Fa	£4.00 £12.00 £15.90	THORN 1600 Rec- & Anode Cap KT3-K30 Slider Pots 4.7k		50p £1.00 for 10				
HT520 METER 20,000 Fuse Diode Protector Logic Lest Pa HT420 9000 SERIES Decoder 01 929 014 080 Thorn	£12.00 £5.00	THE DO THIN TOTA	6p each 20 for £1.00					
LATEST VIDEO For Latest Philips, GEC, Pye and Hitachi. Front panel with	a memory chip and push button and pots and £6.00 NEW	100K POT & 20K v/cap type w KT3 K30 Speaker		5p				
LED's. 20AX GEC LOPT Panel with Split Diode RANK T20 Fouces Pot		K30 Push Button Switch 6 Wa K35 Sound O/P Panel Plug in a	and KT3 sound o/p	£1.00 £3.00				
20AX GEC LOPT I'anel with Split Diode RANN, T20 Fouces Pot RANN, T4 Fouces Pot 16° LOPT Split Diode 2433481 Ex Panel Split Diode 2433782 Split Diode 2433782 Split Diode 2433782	£1,00 £6.00 £5 £6	K35 12 way Push Button Unit K35 L.O.P.T. Split Diode		£1.50 £6.00				
Split Diode 2433752 T703A LOPT Transformer Rank with Focus Pois and Diod HITACHI Mains Switch	le £2.00 50p	G8 6 Button Unit, New Type		£6.00 £2.00 £1.00				
HITACHI AF Socket I CONDENSER Axail Leads 450 A/C 1200 D/C	30a 15p	6 off LED DISPLAYS, Mixed HAND SET TESTER, Infra R ABRIAL SPLITTER with filte	led	£3.00				
GREEN FLAT, NEC, LED's	£1.00		Microphone	£2.00 M				
GREEN FLAT, NEC, LED'S           15V015V I Amp Print Type           12+12V 2.8VA Print Tx1'           8+8V I Amp Print	£1 75p 75p	BUGU DEPERON Major Switch	with Screw Holes Fixing	4 for £1 £3.50				
8+8V   Amp Print ET396 UHF V/CAP Luner, small FIDELITY Panels with I.C. FIDELITY LOPT Split Diode AT2076/80	£7.50 £1.00	PYE 731 New Power Supply	x Reads	£4.00 6p each. 20 for £1.00				
A1 2076/80	£3.00 £5.00		1	£5.00 £4.00				
TT CVC20 to 45 PANELS Send for list MULLARD TEL-TEX DECODER Type VM6103	£7.00			£3.00 25p				
WE HAVE OVER 1,000 6 DIODE TRIPLER AT £1 EACH THORN main T/V chassis complete TX9-TX10-TX90-TX92		SPLIT DIODE FBS1245AR		£5.00 15 for £1.00				
TX10 8 way button unit TX900 with PRR-SR7 PHILLPS VHS Tape 180	£8.00 £6.00 £2.25	GEC TEXT PANEL PC895A7	7	£10 £13 to £46 HEADS				
2431851 2433952 2432211 2432984	CTK Lopt 36212	TRANSFORME	ERS AT2036/00 AT2076/55 AT2048/11 AT2076/71T AT2055 AT2080/15	SHARP MSHIFCF09				
2432301 K4 L.O.P.T. 2432491 K40 2432871 2434274 SPLIT-DIODE	33651 36072 36362 L.O.P.T.		A T2075/35         A T2076/35           £1.00         A T2076/38         OT2041           £1.00         A T2076/51         FB165KA Orio	" <b>£1U</b>				
2432981 2432984 2433212	36383 36482 36761 DIU	UE 3111-268-30050	£1.00         CVC 820         2076/51           £1.00         CVC 800         2432461	EACH				
2433481 2433581 2433751	36831 36832 36833	3122-138-96044	<b>E2.00</b> <b>E1.00</b> <b>REGULATED POWER SUPPLY.</b> Size 6"x5"x2'/2". 0-3v - 0-4.5v - 0-6v <b>E1.00</b> Jamo, Preset 3v-to-12 volts. 1	VIDEO MOTOR for VT568 type VC62DD8 £8.00 MD TUBER IE for VT564 Microbi				
2433452 TX100 THORN ITT Tuner IF CMR800/3 £20 L.O.P.T.	36921/79 £5 EACH	3122-138-98094	£1.00         1amp. Pre-set 3v-to-12 volts, 1 amp.         1 £5.00 Post £2.00.           £20. SEND FOR LIST OF VIDEO SPARES,					
ITT TUNER CAN CMR 800/3 £20.00 I.C. Holders	SEND FOR DATA 20 AMP COST OVER \$	400. 30 VOLT TO 15 VOLTS	FARNELL POWER SUPPLY 19" RACK MO	UNT POST £8, IN CASE £20				
Decca 100 Lopi Panel and Frame £5.00         DIL - DIL           PIN DATA         40 Pin × 4         £1.00								
Min with co-ax socket UHF v/cap         42 Pin × 5         £1.00           tuner 40dB gain £1.50 or 10 for         28 Pin × 5         80p           £10         16 Pin × 10         70p	S	ENDZ	COMPONENTS					
Can be adapted for video         24 Pin × 5         75p           TTT PANEL         14 Pin × 10         70p			EBURYNESS, ESSEX SS3	8AF.				
CMC 301 CMC 113 CMC 302 18 Pin × 10 80p CMC 115 CMC 303 CMC 96/4			Y SERVICE					
	.00 All items subject to availability. No Accounts: No Credit Cards. Postal Order/Cheque with order.							
<u>£5.00</u> CMR 800 Jó Pin × 10 £1.00				10     £1.00       4     £1.00   Add 15% VAT, then £1 Postage. Add Postage for Overseas.				
£5.00         DIL – QIL           CMR 800         16 Pin × 10         £1.00           Powers Suppl. Switch Mode         18 Pin × 10         £1.00           22 Pin × 10         £1.00         22 Pin × 10           Switch Mode         24 Pin × 10         £1.00		15% VAT, then £1 Posta	ge. Add Postage for Overseas.					
£5.00         DIL – QIL           CMR 800         16 Pin × 10         £1.00           Power Supply Switch Mode         18 Pin × 10         £1.00	Add	15% VAT, then £1 Posta Callers: T						

-

# Long-distance Television

**Roger Bunney** 

1989 certainly got off to an encouraging start, with January providing four weeks of good reception conditions. Tropospheric propagation was present almost throughout the period, thanks to a stationary high-pressure system that loitered over Western Europe. The frequent tropospheric openings provided excellent signals, ducting, reception of numerous u.h.f. Danish TV2 transmitters, even Austrian Band III/u.h.f. signals in the Midlands. There were also F2 and SpE signals – a fine start to the year.

The first F2 reception was on the 5th, when a distant Russian ch. R1 signal was present at around 0830 for an hour. The 13th produced Arabic text and programming on ch. E2, at 0805-0903. The 15th was perhaps the most interesting day for F2 reception however: a ch. E2 signal that almost certainly came from Malaysia was received by both Tim Anderson (St. Leonards) and Garry Smith (Derby) between 0850-0920. Tim thinks it was a programme about knitting, with a multiburst test pattern as a floater. Garry logged Arabic captions and a programme about aircraft. He noted a clock at 1715, which strongly suggests Malaysia since this country is at +8 hours with respect to GMT. On the same afternoon Chris Howells (Lichfield) noted weak ch. A2 (525-line) signals for about two hours. At 0830 a Russian ch. R1 signal was seen. A further Russian signal was received at 1230, which is unusual since this is rather late - it's likely to have been a minimum hop distance signal, possibly from the Moscow region. The maximum sunspot count (273) occurred on the 13th.

With such a high level of sunspot activity it was not unexpected that auroral openings occurred. The dates here were the 11th, 13th, 15th, 16th and 17th, with a major event on the 20th and 22nd and the promise of a repeat performance on the 27th day of the solar cycle, during February.

SpE produced several minor openings and reception of isolated signals from time to time. The log is as follows.

5/1/89 YLE (Finland) ch. E3; NRK (Norway) ch. E2. 7/1/89 TVE (Spain) E2.



- 9/1/89 SVT (Sweden) E2; NRK E2; DR (Denmark) E3; RUV (Iceland) E4.
- 10/1/89 TVE E2, 3; ORF (Austria) E2a; ARD (W. Germany) E2; TSS (USSR) R1.
- 11/1/89 RAI (Italy) IA.
- 13/1/89 TVE E2.
- 14/1/89 TVE E2.
- 20/1/89 TVE E3.

21/1/89 YLE E3, 4; TVE E2, 3; TSS R1.

22/1/89 NRK E3.

27/1/89 TVE E2, 3.

29/1/89 TVE E2; SVT-1 E2 via auroral reflection.

The spectacular tropospheric conditions are still present as I write this at the beginning of February. Here in my valley location at Romsey, Hants RTL (Luxembourg) ch. E7 has been a fairly strong signal for much of the month. Following excellent signals during the first week the first major spell of activity was between the 15th-25th. Propagation was both conventional and via ducting. Highlights were ORF chs. E7, 8 and 24 (under Sandy Heath!), numerous W/E German signals, Denmark including the new TV2 stations, plus NRK and SVT in Band III and at u.h.f. There was classic ducting on the evening of the 18th with very strong W. German Band III signals here at Romsey along with signals from nearer co-channel transmitters. On the 20th Cyril Willis received TVP (Poland) chs. R7 and 8.

The excellent conditions continued up to the 25th. The mass of logs received detailing reception at particular locations make it very difficult to give an overall picture. Sufficient to say that on the 24th Simon Hamer in North Wales received Luxembourg ch. E7, Belgium chs. E3, 8, 10, 11, 28, 43, 44, 46, 49, 55, 62 and 63, Holland chs. E4, 5, 6, 7, 27, 29, 30, 31, 32, 34, 35, 39, 42, 45, 47, 50, 53 and 54, all the French Band III channels plus L22, 25, 28, 34, 35, 37, 40, 48, 52, 56 and 63, East Germany ch. E12, AFN (Holland) ch. A80, all the W. German Band III channels plus chs. E21, 27, 30, 34, 35, 37, 40, 48, 53 and 57, Denmark chs. E5, 8, 10 and 30, and NRK ch. E5. Tim Anderson's log at St. Leonards on the south coast tells much the same story but with more W. German signals (most channels in fact), more Danish signals plus Swiss Band III/u.h.f. signals and Austria ch. E8. On the 25th Mark Baldwin logged NRK Gausta ch. E8 at 3kW!

Reception opened up again on the 30/31st and on into February, with much the same story. Several DXers have reported reception of the Luxembourg ch. E36 transmitter. This is the Dusseldorf/ Burscheid outlet at only 20kW. It has been causing problems for VCR owners in that



Reception of a Saudi Arabian identification card by lan Waller in Lincoln, via the 4GHz Arabsat satellite at 26°E.

**IRISH T.V. DEALERS** 

VIDEOS UHF-VHF Ferguson, Sharp, ITT, Panasonic, Nord, etc fully serviced. Top Loaders, from £150 each. Front Loaders from £175 each.

TV's UHF-VHF Most makes in stock 8,16, and multi Channel remotes. Fully serviced from £75 each, untested off the pile £30 each.

#### EXPORT SPECIALISTS

"Sets modified for African transmission" T.V. TRADE SALES

E.D.I. HOUSE, KYLEMORE PARK WEST, DUBLIN 10. TEL. 0001 264139 or 263517



#### BUILD THIS SIGNAL TRACER

Although designed – by David Botto – primarily for fault location in the audio sections of TV sets and VCRs this signal tracer can also be used in other parts of the circuit. It's simple, using a couple of operational amplifier chips (one 741 plus one LM386) and a handful of external components, and can be easily built up on matrix board. The tracer speeds fault diagnosis by enabling you to move through the circuit quickly to see where the signal gets lost or becomes distorted – you can literally ride round the circuit! There's a built-in speaker for signal indication or an external speaker or oscilloscope can be connected. Two signal probes provide for r.f. or a.f. signals.

#### GRUNDIG'S SATELLITE TV RECEIVER

For the coming of Astra Steve Beeching obtained a Grundig offset dish and STR20 tuner, one of the most widely available TVRO combinations, to see how they performed. He compared them with an earlier tuner and some larger dishes and found that they gave just as good results – except when the chicken got in the way...

#### OPERATIONAL AMPLIFIERS

In Part 2 of his article on the subject Keith Cummins describes the basic practical uses for operational amplifiers, goes through a typical circuit design problem and also mentions some faultfinding pitfalls.

#### SOLID-STATE IMAGE SENSORS

то.....

The next item to be covered in Camcorder Servicing is the solid-state CCD image sensor used in the latest generation of cameras and camcorders. How it works and the symptoms that arise under fault conditions.

#### • TEST REPORT: LASER POWER METER

Now that CD players regularly appear in the workshop a means of measuring the output from laser optical units is required. Nick Beer reports on the Leader LPM8000.

PLUS ALL THE REGULAR FEATURES

#### ORDER YOUR COPY ON THE FORM BELOW:

(Name of Newsagent)

Please reserve/deliver the May issue of TELEVISION (£1·50), on sale April 19th, and continue every month until further notice.

NAME	
ADDRESS	
	•••••

area. We also have a report of the new NDR "Nordtext" being seen.

A letter from Ryn Muntjewerff reports similar reception conditions in Holland, but with signals from transmitters farther to the east – Czechoslovakia, Austria, Poland, "many" E. German stations, a Russian ch. R45 relay and signals from Grunten in the deep south of Germany on chs. 43/46. Ryn also reports seeing a new Czechoslovakian test pattern based on the PM5544 but with the identification "1 SR-P". On the 3rd Dutch DXers received Satander, Spain, chs. 40 and 56, a very good catch. On that day Tim Anderson logged the Basque ETB-1 ch. 35 and ETB-2 ch. 38 outlets.

Anthony Mann (Perth, Western Australia) comments on the excellent F2 conditions in his part of the world during late December. On the 23rd the Australian amateur VK3OT had two-way contact at 50MHz with OH2BA in Finland. On the same day Anthony received various ch. E2/R1/C1 Malaysian and Chinese stations via SpE/F2. On the previous day he received 50MHz amateur signals via double-hop SpE from New Caledonia, a distance of over 3,000 miles. Incidentally the Australian ch. 0 TV transmitter DDQ-0 now has a negative 80kHz offset, vision being 46·172MHz and sound 51·67MHz – ABMN-0 remains at 46·24/51·74MHz. Useful should you hear them on a scanner if F2 is that good!

R. Bengal in Bangalore, India, reports that he's been receiving many F2/TE and SpE signals, particularly from the Gulf area, using a 13-element ch. E5 aerial. We've suggested a wideband Band I aerial to improve his reception.

My thanks to the following for sending in comments and reception reports: Tim Anderson (St. Leonards), Garry Smith (Derby), Peter Schubert (Rainham), Cyril Willis (King's Lynn), Roger Fussell (Torpoint), Iain Menzies (Aberdeen), Simon Hamer (Powys), David Oliver (Birmingham), Mark Baldwin (Northants) and Ryn Muntjewerff (Holland).

Perhaps the main event of the period was the coming on air of Astra at 19·2°E. Over the space of a few days an increasing number of channels became available, doubling the choice of signals for suitably equipped viewers. Interesting that from the start of TV transmissions after the end of World War Two it took over thirty years for four channels to become available in most parts of the UK. Within perhaps two years from planning to transmissions via the Astra satellite we now have over eight channels and by the year's end there should be nearly twelve. I recall the lines "never mind the quality, look at the width"...

#### News Items

**Finland:** Relays transmitting the Swedish SVT-1 service are now operational in Helsinki. Further relays covering the greater part of the south/south west of the country will be opened during the next two years.

**Spain:** Regional broadcaster RTV Madrid is due to start test transmissions in April, with programmes from May 2nd. Another regional broadcaster due to come on air is Canal Sur, in Andalusia, based in Seville.

**Italy:** The mystery ch. E2 transmissions of the US originated CNN have been identified as coming from Telemarket. The UK Super Channel was also transmitted at times. These two offerings were transmitted during periods when Telemarket was not producing its own material.

Uganda: TV coverage is to be extended to nearly seventy

per cent of the country via transmitters that are being commissioned by NEC at Lira, Mbarara, Masaka and Mbale. The equipment had been delivered some years previously but due to the turbulent political situation had never been brought into operation.

**Nigeria:** The broadcasting authority NTA has requested funds to update its radio/TV broadcasting equipment, much of which is now over twenty years old.

**Poland:** The Italian RAI-1 service is now being transmitted from Krakow on ch. R50, covering a radius of 70km. **Norway:** NRK Rogaland (Stavanger) regional broadcasts are now being transmitted by Bjerkreim on ch. E6 and Bokn on ch. E8.

**Shetlands:** It's rumoured that the Shetlands Islands Broadcasting Company is transmitting Sky Television. Reception is apparently from a dish atop the studio building at Lerwick. Can anyone confirm this and provide further details?

#### Satellite TV Book

A second edition has been published of John Breeds' "Satellite Television - Installation Guide". I'd thoroughly recommend it for engineers, aerial installers and satellite enthusiasts. It's well produced with high-quality paper and clear text and layout and covers the essentials of signal propagation, satellite position (elevation/azimuth) with maps for various craft, dishes, mounts, electronic equipment, how to erect and align aerials, how to fit LNBs/ polarotors, cabling, footprints, plugs - even how to calculate wall bolts/plugs for a mounting bracket. It clears up many of the questions a newcomer always asks. I wish the book had been available when I started with my first 90cm patio mount - even this humble system is dealt with. If you're in the trade or, like me, a satellite receiving enthusiast, this is the book you need! It's available at £11.95, including post and packing, from Swift Television Publications, 17 Pittsfield, Cricklade, Swindon, Wilts SN6 6AN.

#### **Test Card Video**


If you're into test cards, the new British Amateur Telvision Club video "The Development of the TV Test Card" will be essential viewing. In this one-hour video George Hersee, designer of BBC test cards, talks on the development of and different types of test cards that have been used, going back as far as Test Card A. He's interviewed by Andy Emmerson. The video is recorded on a three-hour VHS tape and costs £5 from Andy at 71 Falcutt Way, Northampton NN2 8PH – postage paid in the UK, add accordingly for overseas despatch. I've viewed the tape and can recommend it as being extremely interesting. Incidentally does anyone have a photograph or illustration of the old BBC Test Card B?

#### Amateur TV Activities – 1989 Contests

The British Amateur Television Club has supplied the following list of contest periods for 1989. These are periods when ATV operation will be very active, giving the TV-DXer the opportunity to receive signals with greater predictability than the usual random occurrences. If possible, listen to the ATV calling frequency – 144.75MHz.

The Spring Vision contest was from March 11th at 1800 GMT to March 12th at 1200. Sorry we didn't get that in before.

#### **TELEVISION APRIL 1989**

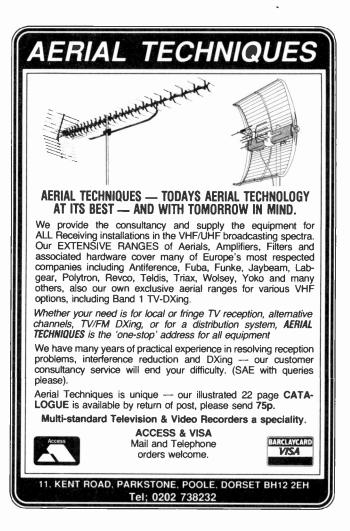

The Summer Fun contest is from June 10th at 1800 GMT to June 11th at 1200.

The IARU (international) ATV contest is from September 9th at 1800 GMT to September 10th at 1200.

The Autumn Vision contest is on November 12th from 0001 to 2359 GMT.

The Winter ATV contest (joint European) is from December 9th at 1800 GMT to December 10th at 1200.

#### Soviet TV

Bernd Trutenau of the Benelux DX Club has supplied details of the Estonian TV network and the channel allocations. The following list includes only those transmitters likely to be seen in the UK via SpE.

Region	Channel	Region	Channel
Tallinn Tartu Kohtla-Jarve Parnu Haapsalu	R4 K1 R1 K2, R5 L R4 E R3 K1	Kallaste Narva	R3 E R5 K1 R5 E R3 E R4 K1, R2 L
Rakvere Kunda Jogeva	R3 E R1 K1 R5 K1	Poltsamaa Sillamae	R1 K1 R3 K1

E = Eesti TV, L = Leningrad TV, K1 = CT-1 (Russian first programme), K2 = CT-2 (Russian second programme, networked).

Test transmissions using the UK teletext standard are at present being carried by Eesti TV on weekdays from 1450-1500.

# TV Fault Finding

#### **Rediffusion Mk 3 Chassis**

The very large number of these sets in my area are beginning to suffer from tuning problems. This particularly affects the six-button Rodé-Stucky selector unit. It can be stripped and cleaned, clearing the problem, provided care is taken.

To remove the unit from the set take out two selftapping screws in the front panel. Next remove the buttons by inserting a small screwdriver in the holes on the underside of the surrounding moulding and prising them off. The cover over the switches and lamp is removed by prising off with a screwdriver in the four slots. You will find that the circuit board is attached to the plastic carriage by four screws, two of which are not immediately obvious as they are covered by plastic plugs. Remove these and the board is free. The selector unit can be unsoldered after which the tracks, on a subpanel riveted at one end of the main panel, are exposed. Cleaning is then a simple job, with no fear of damaging the plastic. Reassembly is also simple. **R.B.** 

#### Jackson Mk 2 Chassis

The models I've seen fitted with this chassis have come in the guise of the Triumph 8209. The soldering is not of the best and it pays to resolder the heavy wound components (chopper and line output transformers) and to check carefully with an eyeglass for dry-joints. The main one to date has been on R29 (27k $\Omega$ ) which is mounted under the board. It tends to be held to the print at one end, with a "blob" of solder at the other end. Depending on how well this "blob" makes contact with the print the fault shows up as a curious slowness for the line to lock, intermittent line slip with colour drop out, or unlocked lines if you so much as breathe on the set. If the set is left too long like this the BU508D line output transistor TR15 will go shortcircuit and soon after R125 (4.7Ω, 2W safety resistor) will go open-circuit. So if you come across a case of a dead BU508D in one of these sets, soak test it very carefully after checking the above points.

Intermittent colour on its own is generally due to a dryjoint on one leg of the crystal.

Spares for these sets are available (trade only) from Jackson Products Ltd. For the address and telephone number see under Harwood in the TV/VCR Spares Guide.

#### Thorn 9600 Chassis

After a very few occurrences of "flickering" – presumably due to h.t. variations, seeing what happened next – the mains fuse F1 blew violently. W533 was found to be shortcircuit. This device is a BY299-1000 which is no longer available. The MR818 is a suitable replacement. Safety resistor R518 (1 $\Omega$ ) also went open-circuit. **R.B.** 

#### **Rank T22 Chassis**

This one had received amateur attention and was nonoperative. Once the 200V supply had been restored a check was made on 4R16 (910 $\Omega$ ) in the 12V regulator circuit. It was found to be still within tolerance, but 4D5 (BZY88C5V6), 4D6 (BZY88C6V2) and 4D7 (1N4148) were short-circuit, with scorch marks on the panel, and 4R58 (56 $\Omega$ , safety) was open-circuit. When these were replaced the set started up but there was no raster. The TDA2532 RGB matrixing chip IC6 on the signals panel proved to be faulty. **R.B.** 

#### **GEC C2110 Series**

For intermittent no colour, sometimes coming and going if you tap the board, clean the pins of the TBA560 chroma/ luminance processing chip and its holder. A clue is that the luminance varies as well. **R.B.** 

#### **Philips CTX-S Chassis**

In recent months we've had a number of these sets in with faulty chroma delay lines (type DL701). Symptoms range from intermittent loss of colour to permanent no colour or alternatively severe Hanover blinds. The latter fault can be tracked down to the delay line by tapping its case.

As in the later KT3 chassis it pays to clean the pins of the chrominance chip. These can also be responsible for the no colour symptom when dirty. **R.B.** 

#### Philips 2A Chassis

This is becoming a stock fault with these sets. The reported fault is a dead set and you will normally find that the BU508 line output transistor is short-circuit. If so examine C2609 carefully for bulges and arcing around its legs – this will destroy the BU508. At the same time check whether R3601 ( $5.6\Omega$  safety resistor) is open-circuit. It supplies the EW modulator. If it is you will usually find that C2616 has gone open-circuit. A.D.

#### Salora 16J20

The problem with this set was no picture, sound o.k. An article on the TDA3562 colour decoder chip, in the October 1987 issue, was the key to discovering the cause of the fault. A scope check on the sandcastle pulse input at pin 7 of this chip showed that the field component of the pulse was incorrect. Moving back through the circuit brought us to transistor TB400 (BC237B) which proved to be defective. Replacing this brought everything back perfectly. When scoping the field component of the sandcastle pulse it helps to remove the other components by isolating pin 7 of the TDA2594 chip – clearing the decks so to speak. **B.McC.** 

#### Ferguson TX85 Chassis

This set was dead. The mains input fuse had blown, the TIPL791A chopper transistor had gone short-circuit collector to emitter and the TEA2018A chopper control/ driver chip had an internal short from its 11V supply input (pin 6) to its non-isolated chassis connection (pin 2). The fuse, transistor and chip were replaced and the set was switched on. It appeared to be working normally, apart from a scream from the power supply. So the set was quickly switched off.

A meter was connected to the h.t. output (97.5V) from the chopper power supply to check that the regulation was correct and the set was switched on. The h.t. was correct, but after about fifteen seconds the fuse blew. We found that the transistor and the chip had once more failed. A thorough check was then made on the components in the power supply. This revealed that R101 ( $1.2k\Omega$ , 5W) in the snubber network across the chopper transistor had gone open-circuit. When all these items had been replaced the set was o.k. **I.B.** 

#### Ferguson TX90 Chassis

The customer had complained of intermittent lack of height which was of course due to dry-joints on the field output transistors, but when setting up the contrast etc. I noticed that there was a dark band down the left-hand side of the picture and severe ringing on low-contrast scenes. I decided to bridge the electrolytics in the video circuits and while looking for C132 saw a capacitor with electrolyte leaking from its top - C132 (10 $\mu$ F, 50V) in fact. It had a small hole in the underside, visible only after it was lifted upright. C132 decouples pin 4 (brightness control) of the  $\mu$ PC1365C colour decoder chip IC103. N.B.

#### **Decca/Tatung 130 Chassis**

This set had been in several times for intermittently going into the standby mode. Several things had been tried – the tripler, the BU426A chopper transistor, the TDA4600 chopper control chip, etc. As the fault was of such an intermittent nature I decided to change the line output transformer, suspecting an internal arc. This put matters right. N.B.

#### **Decca 80 Chassis**

We've had a spate of these recently with no sound and field collapse due to the relevant supply being absent. Rectifier diode D400 on the line output panel tends to go short-circuit. **N.B.** 

#### Panasonic TX-C21 (U4 Chassis)

The customer complained that when he turned the sound up the picture went green! Now these sets have a fair audio output, but somehow this seemed unlikely. I was able to instigate the fault however by tapping around – particularly on the text panel. There were several suspect joints in the RGB interface section but the actual cause of the trouble was a peach of a joint at one end of jumper lead JF which connects pin 23 of the TROM chip IC5013 to R5063, running from top to bottom of the panel. N.B.

#### Salora 1G5

No picture with the c.r.t.'s cathode voltages high and the e.h.t. low was traced to a faulty IPSALO transformer (FM214). It had not broken down in the usual way, i.e. wires broken away from the transformer's pins, so a replacement was required. N.B.

#### Salora 24L67

The complaint with this set was of intermittent picture disturbance. A field engineer didn't see the fault and couldn't provoke it, so thinking that the aerial could be at fault he left the customer with a set-top aerial as a check. The next day another field engineer discovered that the fault was very sensitive to tapping in the middle of the single-board chassis. On the bench this proved to be so but no dry-joints or breaks could be found. Very precise tapping narrowed the source of the fault to the area left of the tuner, where even slight application of heat and freezer would instigate it. After a lot more prodding the cause of the trouble was found to be a break within R179 (100k $\Omega$ ). No visible damage could be seen – maybe a poor connection to one end cap? N.B.

#### Tatung 130 Chassis with System 30 RC

This set was stuck on standby. Overriding the momentarymake contact on the mains switch produced the expected screaming from the line output stage, so the tripler's input lead was disconnected. When switched on again the set remained in standby but overriding the momentary-make contact this time got the set going, without a raster of course. After fitting a new tripler the set worked but only with the momentary-make contact overriden. So attention was turned to the microcomputer control system, which had probably been dealt a deathly blow by the offending tripler. Latch-on of the MAB8021 chip didn't operate but a new MAB8021 didn't improve matters. Replacing the 74LS293N flip-flop chip IR08 did however restore normal operation. The other clue was that the channel LEDs were corrupt. N.B.

#### Triumph CTV8210

This colour portable suffered from field collapse and the customer said he'd seen smoke coming from it. Both R930 (100 $\Omega$ ) and L905 (4.7mH) were open-circuit. The cause of the burn up was not far away. C914 (100 $\mu$ F) had a leak that measured about 2k $\Omega$ . J.O.

#### **Philips KT3 Chassis**

Not a fault but a point to bear in mind if a twiddler has been at work. With this chassis you get a white line that looks like field collapse if the height control has been turned right down. J.O.

#### Rediffusion 365138 (Mk 5 Chassis)

This colour portable was dead. As I'd no manual and didn't recognise the chassis I was on the point of giving up before I started. I noticed some high-value resistors in the power supply however, so I thought I'd check them. Bingo! R718 (120k $\Omega$ ) was open-circuit. But this was not the end of the story. I switched on and the set was still dead. Cries of "oh dear!" – well I think that's what I said . . . Further investigation led me to R628 (1k $\Omega$ ) which was open-circuit. Don't ask me what blew first. J.O.

#### Salora 22J21

There was no raster though the sound was o.k. A check at the c.r.t. base showed that there was no first anode (G2) voltage. The  $2.2k\Omega$  feed resistor had burnt out. As cold checks didn't show any leakage I examined the base panel and found evidence of tracking between the 1kV input and the BCL connection – surprisingly this lead didn't connect to any component on the c.r.t. base panel. After replacing the  $2.2k\Omega$  resistor and disconnecting the BCL lead the first anode voltage and hence the brightness were restored. Rather than risk a future call-back the damaged c.r.t. base panel was replaced. J.L.H.

# **Teletopics**

#### SATELLITE TV

BSB's intention to apply for the franchise for the two other official UK satellite TV channels in the 12GHz band could result in some technical changes. There is a trade off between the number of channels and the output power. BSB's first satellite has five transponders but two were intended to act as a back-up: using all five would mean reduced signal strength, at any rate until BSB's second satellite is put into orbit in mid-1990. Reduced transmission power would affect the design of BSB's "squarial", which might have to be larger – 30cm instead of 25cm – and of wider bandwidth. BSB proposes to use adaptive pre-emphasis to improve the signal-to-noise ratio.

Sky Television's descrambler is to be activated by a smart card. A new card with a modified chip will probably be sent to subscribers every three months, when a change is made to the encryption control coding. In this way lapsed subscribers can be cut off. The cards are to be manufactured in the UK by a joint venture being set up by Sky's parent company News International. Production is to start in the autumn and the aim is to manufacture two million cards during the first year. The operation will employ around 400 people.

The separate £10 licence to operate a satellite TVRO installation has been abolished. Some 7,000 licences were issued, the cost barely covering the paper work involved. Abolishing the satellite TV licence does not affect the legal requirement to have a normal TV receiving licence.

The "to be announced" channel in our Astra list on page 357 last month is being used by MTV, the pop music channel.

Philips has joined the group of companies under contract to produce set-top units for the BSB services. The other companies under contract are Ferguson, Nokia and Tatung – BSB has said it will appoint up to five manufacturers who will have access to BSB's encryption/access control technology. Philips intends to establish production capacity to turn out 50,000 units a month and is strongly backing the use of MAC for satellite TV transmissions.

Ferguson has announced a range of equipment for reception of the Astra and BSB transmissions. Model SAP1 at £300 is for Astra, with a 32-channel tuner and 60cm dish. Model SAP2 at £330 has the same electronics with an 80cm dish. These models can be upgraded to provide unscrambling. Due in September is the SBP1 for BSB, with a 10-channel tuner, Eurocypher decoding and a Squarial. Two further models, the SAP3 (60cm dish) at £400 and the SAP4 (80cm dish) at £430, are due in December. These are for Astra reception and will incorporate Palcrypt decoding. So completely separate systems will be required for Astra and BSB.

#### SATELLITE TV INSTALLATION KIT

Connexions (UK) plc, Unit 3, South Mimms Distribution Centre, Huggins Lane, Welham Green, Herts AL9 7LE (0707 272 091) has introduced a professional satellite TV installation kit. It comes in a durable polypropylene case at an inclusive trade price of £129.95 plus VAT. The kit comprises a CX9102F aerial setting meter, CX9201 inclinometer, CX9202 compass, CX9200 crimp tool, CX9057 multimeter, CX9018 in-line amplifier, CX9056 insertion tool, CX9002 two-way splitter, CX9053 F-type coupler, CX9054 F-to-N adaptor, CX9055 N-to-F adaptor, 100 CX9051 F-type connectors and ten CX9052 protective weather "boots". The CX9056 insertion tool provides quick and easy application of F-type connectors to RG6 coaxial cable and is exclusive to Connexions. All items are available separately and can be obtained from Connexions distributors.

#### SUPER VIDEO

Sony has released details of the first equipment to use the Hi-Band Video 8 system. Basic details of this system, which brings Video 8 picture quality to a par with S-VHS, were given in the May 1988 Teletopics column. There are two models, the CCD-V900 camcorder at the equivalent of about £1,070 and the EVS-900 VCR at some £1,090. These are being released in Japan this April and no European launch dates have so far been announced. Sony is also releasing the first metal evaporated tape cassettes. There are three, the 60-minute version costing £9. Also being launched are five high-grade MP tapes, with the 60minute version priced at £6. These new tapes can also be used with standard Video 8 equipment.

Meanwhile two more S-VHS camcorders have been announced in the UK. The JVC GR-S77E is a compact S-VHS-C model with 420,000 pixel CCD image sensor, 10lux sensitivity, an eight-head system for SP/LP, two-speed  $\times 8$  zoom, a variable speed (1/50th, 1/250th, 1/500th and 1/ 1,000th sec) fast shutter, three-page digital superimpose and date/time recorder. The weight is 1.2kg and the suggested price £1,300. The full-sized Hitachi S-VHS camcorder Model VM-S7200 is being released in May. Features include  $\times 8$  zoom, four-speed fast shutter, VISS index system, self timer and edit search. The weight is 2.7kg and the suggested price £1,500.

#### BATC RALLY/CONVENTION

This year's British Amateur Television Club convention/ rally is being held on April 30th at a new location, the Founder's Suite at the Coventry Crest Hotel. This is conveniently located on the A46, 500 yards south of junction two on the M6. There will be demonstrations covering all aspects of amateur and satellite TV equipment and a wide range of trading stalls. The hotel's training centre will be used in the afternoon for technical lectures. There is ample parking and the rally opens at 10 a.m. Admission is free to BATC members on production of a ticket from CQ-TV, 50p to non-members. Trade enquiries to G8CJS or G8OZP who are QTHR.

#### **BROADCASTING NEWS**

The Home Office has appointed the accountancy/ consultancy group Price Waterhouse to study ways of privatising the BBC and IBA radio and television transmitter network. Price Waterhouse has been given just ten weeks to prepare a report. Privatisation of the transmission system was suggested in the recent government white paper on the future of radio and TV broadcasting in the UK.

In Japan NHK has now started daily trial HD-TV transmissions – a full service is to begin next year when two new satellites have been launched. The first transmissions were made during the Seoul Olympics, when NHK installed over two hundred HD-TV sets in public locations. These sets were hand built by several manufacturers

and are reputed to have cost around £42,000 each. Sets on sale will not come cheap, in particular due to the large amount of digital storage required. The MUSE technique, which is used to provide bandwidth compression with NHK's HD-TV system, requires field stores and interpolation for motion detection correction.

The BBC has been taking out patents on an improved version of PAL. The idea is to monitor reception at the transmitter, assess impairments and produce a digitally coded correction signal which is transmitted in teletext form. Sets able to take advantage of the system would include circuitry to decode the error signal and provide correction. Other sets would simply ignore the extra signal.

#### **PUBLICATIONS**

The 1989 RETRA Year Book and Directory has now been published. Copies can be obtained from the Association's headquarters at £20 each – for the address see "RETRA on the move" elsewhere on this page. Contents of this impressive 256-page book include a points-to-remember section on useful legal and business information, a glossary of satellite TV terms, a section listing brand names and their manufacturers, an international TV systems/mains voltages list and addresses of leading manufacturers.

A new expanded and revised second edition of John Breeds' book "Satellite Television Installation Guide" has now been published. It's available at £11.95 inclusive of post (in the UK) and packing from Swift Television Publications, 17 Pittsfield, Cricklade, Swindon, Wilts SN6 6AN. It's certainly a very useful and practical work.

#### WILLOW VALE'S COPS

Willow Vale has introduced a computer ordering parts system (COPS) for the radio and television servicing trade. Dealers holding an account with Willow Vale can obtain a password which will give them on-line access via a PC with telephone modem to Willow Vale's mainframe computer for information on availability, prices, etc. for over 50,000 stock items. Advantages include access and ordering without manufacturers' part numbers, access and ordering with part numbers, actual on-line stock availability, part number information, prices and discounts, technical pages and hints, back order display/amendment/ deletion, etc. COPS differs from other Viewdata type systems in being user-friendly and not requiring mandatory use of part numbers – all you need is the model number for which a list of parts is displayed in alphabetical order. Dealers not already so equipped can obtain from Willow Vale a terminal complete with modem for £350 plus VAT.

#### EXPANSION AT SONY BRIDGEND

Sony is to invest £36 million to increase production of colour TV receivers and Trinitron colour tubes at its Bridgend plant in South Wales. Bridgend is Sony's main European centre for colour TV receiver and tube production. Tubes and components made there are also used at plants in West Germany and Spain. It's anticipated that the expansion will create three hundred new jobs, many for people highly qualified in state-of-the-art automated manufacturing and surface coating technology. The initial announcement of Sony's intentions was made last Autumn and the new extension is due to be completed in

**TELEVISION APRIL 1989** 



May 1990. Sony already employs a workforce of 1,500 at Bridgend.

Matsushita (Panasonic) has announced that it itends to increase production in Europe over the next three years. It's likely that new manufacturing facilities will be located in South Wales where the company already has a major plant.

#### RETRA ON THE MOVE

After ten years at its Newington Causeway headquarters RETRA has moved to Bedford. The purpose of the move is to reduce overheads and improve the services offered to RETRA's 1,500 members. Council meetings will continue to be held in London. The new address is RETRA House, St. John's Terrace, 1 Ampthill Street, Bedford MK42 9EY, telephone number 0234 269 110. RETRA's new headquarters is a 3,000 sq. ft building near the town centre, close to the A1 and M1.

#### CORRECTIONS

Several errors in recent issues have come to our attention. First the computer program for satellite dish alignment, see page 354 last month. The colons in line 90 should have been the string escape character – this is available below and to the right of the break key. The program will not run properly with colons in line 90. There are also a few spacing errors which affect the displays obtained.

On page 351 last month (VCR Clinic) Panasonic NV-100/NV-10B should have been NV100/NV-V10B. Under the Ferguson FV11 on the same page the symptom intermittent failure to eject should have read tapes ejected when inserted. Nick Beer comments that dry-joints have started to appear on the take-up photosensor with this machine, making it go to stop. There was also an error in the article on S-VHS, page 334. VHS recordings *can* be made on S-VHS tape but not the other way round. When a non-S-VHS cassette is inserted the machine goes into the VHS mode irrespective of the selection made by the user.

In a letter on page 750 of the August 1988 issue the part number of the flywheel holder used in the GEC V4004/ Hitachi VT33 was given incorrectly. The GEC part number is V7376323. The recommendation is to use this in the later GEC V4005/Hitachi VT63/64 to cure noisy operation.

A note on errors in the article on j notation (February 1989) is being prepared.

# **Camcorder Servicing**

Part 3

So that it can display a full range of colours the screen of a colour TV tube is backed by phosphor stripes in the primary colours red, green and blue. In a similar though different way the faceplate of a colour camera tube is covered with colour stripes so that it can distinguish between colours. Although the tube's target covers most of the faceplate the area actually used consists of a  $7.2 \times 5.6$ mm rectangle – see Fig. 1. Within this area the purity of the target material and its sensitivity are kept within fine limits. The image from the lens is focused on this rectangle and to suppress signals outside this area the rest of the faceplate is covered with a black mask. The backfocus adjustment ensures that the distance between the lens and the tube's faceplate is correct. It's done with the lens set at infinity and the iris fully open.

#### The Colour Stripe Filter

For colour recognition the image area is covered with a precise fine-stripe filter. The main output from the tube consists of a wideband luminance signal (Y), or rather green. Stripes are used to obtain a red and blue carrier signal. By adding red, green and blue you get white. As the light transmission of red and blue filters is fairly low the filter instead uses the complementary colours yellow and cyan, thus obtaining improved low-light sensitivity. Cyan is -R and yellow -B of course. Feed the signals through inverting amplifiers and you get red and blue. It really is that simple!

The stripes are laid down diagonally as shown in Fig. 2, at an angle of 25° 40′ to the vertical plane. Their width is 13.95 $\mu$ m, there's a gap of 13.95 $\mu$ m between the stripes and the pitch is 30.89 $\mu$ m. The cyan stripes slope from left to right, giving a scanning sequence cyan, gap, cyan, gap etc. The yellow stripes slope from right to left, giving yellow, gap, yellow, gap etc. The colour pixels are the diamond crossovers, identified in Fig. 2 as lines n - 1, n, n + 1, n + 2 etc.

The filter stripes act not only as a colour filter. Their physical dimensions and spacing are arranged so that a signal with specific parameters is generated. As the electron beam scans the area behind the stripes it generates a complex signal determined by the stripe structure. Since the number of stripes along each line is fixed, a carrier signal is generated – think of a child running along some railings with a stick, generating a tone. With the VHS-C system the carrier generated in this way is 4·3MHz. Note that this is not the 4·43MHz PAL subcarrier: it's the camera's R/B carrier signal. Note also that the scanning width is critical: if you alter the tube's scanning width the 'carrier frequency will alter.

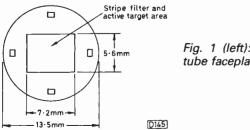


Fig. 1 (left): The camera tube faceplate.

#### Steve Beeching, T.Eng.

Green is present over the whole filter area since white is R + B + G, cyan is B + G and yellow is R + G. The output from a Saticon tube thus consists of two superimposed signals, wideband luminance which you can call green if you prefer and a 4.3MHz carrier which contains the red and blue colour information. The carrier is amplitude modulated by the red and blue signal components which have a phase difference of 180°.

A little thought given to Fig. 2 will show how this phase difference occurs. Assuming that the line scan is from left to right, progressing down the target in the sequence n - 1

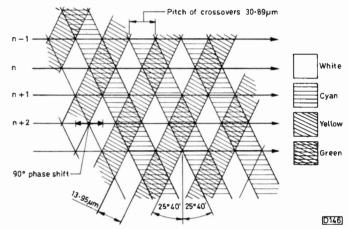


Fig. 2: The colour stripe filter arrangement.

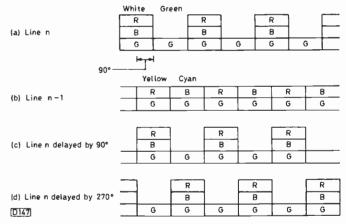


Fig. 3: Separating the R and B components of the R/B carrier signal obtained from the tube.

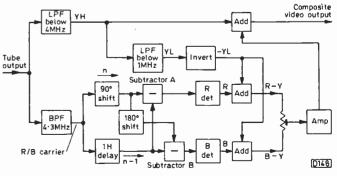


Fig. 4: Block diagram of the R/B signal separation system.

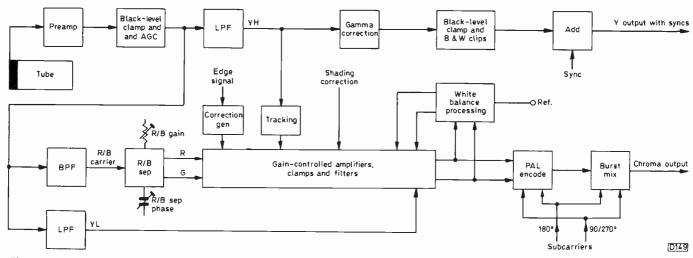


Fig. 5: Block diagram of a typical colour video camera using a pick-up tube.

1, n, n + 1, you can see that with the cyan stripes from left to right the cyan signal gets later and later on successive line scans. With the yellow stripes from right to left however the yellow signal occurs earlier and earlier on successive line scans. Now for the clever bit. The accurate  $30.89\mu$ m stripe pitch means that the cyan signal is retarded by 90° per line while the yellow signal advances by 90° per line. A 180° phase difference is thus maintained between the two components of the colour signal on a line by line basis, enabling them to be separated in a similar manner to what happens in the decoder of a colour TV receiver.

#### Separating the R and B Signals

The outputs obtained from the arrangement shown in Fig. 2 are illustrated in Fig. 3. Use of a one-line delay line enables us to mix the signal from line n with that from line n - 1. Line n consists of white, green, white etc. As white is equivalent to R + B + G this is RGB, G, RGB, G etc. as shown in Fig. 3(a). The previous line n - 1 consists of yellow, cyan, yellow, cyan, which is R + G, B + G, R + G, B + G etc. as shown in Fig. 3(b). Note the 90° phase shift between lines n and n - 1.

The way in which the red and blue components of the signal are separated is shown in Fig. 4. The tube's output is fed through a low-pass filter to separate the luminance component and a 4.3MHz bandpass filter to separate the colour carrier. Line n's signal passes through a 90° phase shift network to compensate for the phase shift between lines, then to subtractor A and via a further 180° phase shift network to subtractor B. The signal from line n - 1 is present at the output from the 1H (one line) delay line and is fed to both subtractors. Thus n's signal has been delayed by 90° at subtractor A and 270° at subtractor B. These conditions are shown at (c) and (d) in Fig. 3. Subtracting n - 1, i.e. (b) in Fig. 3, from (c) and (d) gives

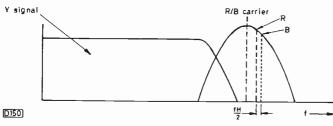


Fig. 6: Frequency spectrum of the tube's output.


B, B, B, B and R, R, R, R respectively. After detection we get baseband R and B signals which, when added to -Y, provide the conventional R - Y and B - Y colourdifference signals. These are added to Y to give a standard composite luminance-chrominance signal. In practice things are a bit more complicated. The colour signal is clamped, tidied up and vertical edge correction is added.

#### Camera Block Diagram

Before looking at the rest of the processing we'll consider the overall camera arrangements. Fig. 5 shows a block diagram. The tube's output is first amplified by a high-gain, high-impedance preamplifier whose output is shown in Fig. 6. A.G.C. and black-level clamping are then applied after which the signal paths split, the full bandwidth luminance signal passing to the gamma correction circuit while a bandpass filter separates the R/B carrier and another low-pass filter (cut off above 1MHz) separates a Y signal component that's used to produce the colour-difference signals. The R/B signal is subject to the processing described above, a variable resistor (R/B separation gain) and capacitor (R/B separation phase) being used to ensure accurate separation of the R and B signals. Vertical edge correction is applied at this point to remove any discolouration in black and white horizontal edges in the vertical scan. After separation the R and B signals pass along parallel paths via voltage-controlled amplifiers. where correction waveforms are added for grey-scale tracking and colour shading. Two amplifiers are driven by the white balance circuits. These can give fixed white balance, set white balance or auto white balance. After clamping and filtering - Y is added. The following sections provide PAL encoding and addition of the burst signal.
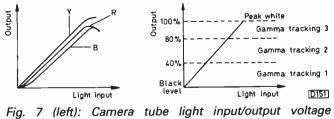
#### Gamma Correction

As the tube's output is not a linear voltage change for a linear light input change compensation is required. This is called gamma correction. The problem is made more complicated by the fact that the levels of Y signal and R/B carrier obtained from the tube do not remain constant with respect to each other throughout the range of input light. At low light levels the R/B carrier amplitude is lower in proportion to the Y signal level. This cannot be allowed in a high-sensitivity colour camera as there would



characteristic.

Fig. 8 (right): Triple-level tracking correction.

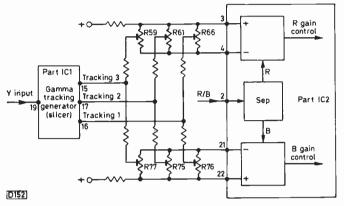


Fig. 9: Basic triple-level tracking circuit.

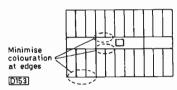


Fig. 10: Vertical edge correction adjustment.

be a tendency towards dark green pictures at low light levels when the R/B output falls off. It can be seen from Fig. 7 that the tube's sensitivity to blue is lowest, the red sensitivity falling between this and the higher Y sensitivity.

At mid-range light levels the sensitivity differences remain constant and can be equalised by gain adjustment so that the signals track together. At the extremes of low and high light however the red and blue signal levels fall off first. To prevent different tints at different light levels a triple-level tracking correction system is used. Fig. 8 shows the effect of this. Tracking (1) works at output levels up to 40 per cent, tacking (2) at between 40 and 80 per cent and tracking (3) at above 80 per cent. Tracking is

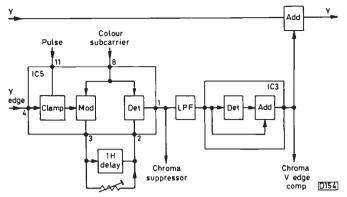


Fig. 11: Block diagram of the edge compensation system.

corrected by adjusting the gains of the red and blue control amplifiers against a Y reference signal.

A similar system is used in most camcorders, based on two chips – see Fig. 9. IC1 is referred to as the gamma tracking generator. It provides three outputs which are derived from the luminance input.

The output at pin 16 is clipped at 40 per cent. Thus luminance signals up to 40 per cent are supplied to tracking controls R66 and R76 to provide white balancing up to this level.

Pin 17 produces an output when the luminance level is between 40 and 80 per cent, white balancing then being via R61 and R75.

Pin 15 produces an output at high light levels, to R59 and R77.

It's not easy to adjust these controls without the correct lighting (3,200°K) and a grey-scale chart. The controls are interactive at the crossover levels of 40 and 80 per cent, and considerable interadjustment is required to get the whole grey-scale tracking correct. Usually a compromise is found. Peak white levels can be adjusted only if control over the automatic iris is possible or a small white area within a black background is illuminated to fool the iris control and open up the iris to provide peak white conditions.

#### Edge Correction

Better quality broadcast cameras have an aperture correction circuit to crispen the pictures by correcting transition edges in both the horizontal and vertical directions. VHS camcorders have a vertical edge enhancement circuit which works by mixing signals from direct and delayed TV lines – it's often referred to as contour

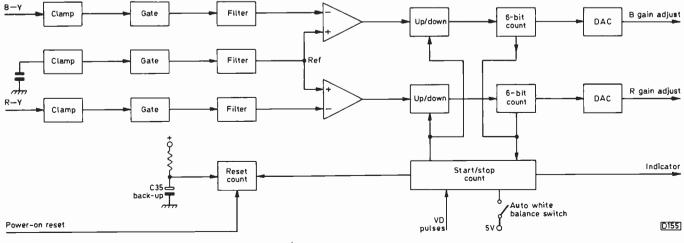


Fig. 12: The white balance system.

correction. This is tied up with the vertical edge correction previously mentioned in the colour separation circuit. If a picture has a dark grey area at the top of the screen and a white area below it the first white horizontal line would, without correction, be discoloured. This is because of the fact that the R/B separator circuit operates over two lines of signal, and since the line above is dark no previous colour exists!

Fig. 10 shows vertical edge correction adjustment. A grey-scale is used. When titled at an angle of about 20° any edge colouration can be seen and removed or minimised.

The edge compensation system is shown in Fig. 11 – its output is used for vertical edge enhancement and is also used for discolouration correction at horizontal edges. A Y edge input signal enters IC5 at pin 4. After clamping, the signal is amplitude modulated, using the colour subcarrier. The reason for modulation is to get the signal through the one-line delay line, after which it's detected (demodulated). A subtraction process occurs in the detector circuit as a result of which the output at pin 1 consists of only signals that occur on one line and not the next, i.e. a difference component. If the two lines concerned are as previously described, i.e. a change from dark to white, a single line output will be produced. This has to be seen at field rate and shows up as a single spike pulse. The output goes to the colour suppressor to kill colouration of very dark or black areas following a transition from white to black during the field scan. It also goes via a low-pass filter to a second detector in IC3 where low-level spikes and noise are removed leaving only clean, healthy spikes. These are added to the luminance signal to beef up the vertical resolution and are also applied to the vertical edge correction system in the R/B channels.

#### White Balance

The purpose of the white balance circuit is to reduce the colour-difference signals to zero when the camera is pointed at a white surface – despite the colouring effect of the lighting. Once this is achieved, in theory all other colours will be correct.

While the circuit may look complicated – see Fig. 12 – the operation is fairly simple. It's based on the two six-bit binary counters whose outputs are DA converted to obtain variable d.c. levels which are used to adjust the gain in the red and blue channels. The R-Y and B-Yinuts are clamped and gated and fed to two operational amplifiers whose other input is a reference level – you can think of this as a fixed green reference level. The circuit relates the red and blue signal levels to green so that R =B = G, which is white. When the auto white balance switch is closed the counters are enabled. Count up or down is determined by either a high or low output from the comparator amplifier in each channel, the latter output in turn being dependent on the difference signal being lower or higher than the reference level. As six-bit counters are used a total count of 64 is available. At power-on reset the count is 32, giving equal possibilities up or down. Counting is controlled by the VD pulses which occur once per field. When a balance is obtained, by a change of state at either comparator, each counter stops and produces the appropriate d.c. output. C35 can hold the count during power off for a few hours. If the counters reach either 111111 or 000000 without any change a warning is produced - the indicator gives a flashing signal: it produces a permanent signal to indicate

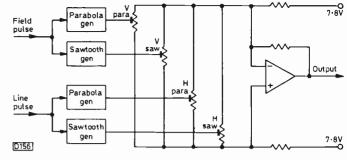


Fig. 13: Method of producing the dynamic focusing and the shading correction waveforms.

the balanced condition.

If the white balance is in the fixed condition the d.c. levels are set to a 1.8V reference. Camera adjustments are made in this condition.

#### Setting up and Fault Symptoms

So much then for an overall view of the camera section as used in JVC and Ferguson camcorders – Panasonic ones are similar. Adjustments should not be attempted without at least a good oscilloscope, e.g. one of the Grundig ones previously reviewed, and preferably a vectorscope. What about fault symptoms and areas to look at?

Any problem that reduces or eliminates the R/B carrier will turn the picture green – not necessarily all over. The scanning linearity over the target area must be uniform: any defocusing or nonlinearity will turn the picture green, i.e. areas of the picture will shift towards green.

Green in the corners or any part of the perimeter of the picture will be due to incorrect dynamic focus correction and/or poor focusing as the tube ages.

Red or blue shading can be corrected by means of the static shading (four) and red/blue dynamic shading (four each) controls.

The dynamic shading controls are set using a white card with an oscilloscope connected to the R-Y and B-Y test points. Adjust for flat lines at line and field rate.

The same test points can be used for horizontal linearity and dynamic focusing (four controls) adjustment but an R/B carrier test point (after the bandpass filter) is much better. This will give you a typical carrier waveform with a ghostline across the centre. Use a white card. Scanning and dynamic focus adjustments should aim for a flattopped symmetrical rectangle, nice and straight with no falling off at the start and end and with the ghostline in the middle. This takes practice. The first time anyone sets up a camera it can take days rather than hours – with the option of cocking it up completely and sending the camera along to me with a blank cheque!

Parabolic and sawtooth waveforms at line and field rate are used for dynamic focusing, for R/B dynamic shading correction and for static shading. Fig. 13 shows the basic circuit arrangement.

Static shading adjustment is carried out with the lens cap on, monitoring the YH (full bandwidth luminance) signal, to get flat lines at line and field rate.

Static focus is adjusted on a white card while monitoring the R/B carrier.

When carrying out dynamic focus adjustment be careful that the correct setting isn't masked by incorrect shading adjustment.

The control arrangements differ somewhat with dif-

ferent cameras/camcorders. For precise setting up instructions for a particular model refer to the relevant manual.

Before making any of these adjustments the correction waveforms must be reduced to zero (flat) irrespective of the picture. It all takes a long time to do and may not produce better results if the tube's emission is low. Beware – an aged tube will have inconsistent sensitivity over the target area, producing shading and a poor grey scale. You cannot get rid of this by using the adjustments, particularly if the tube has a poor lag characteristic or a tendency to green at low light levels.

Failure of the R-Y signal will produce a picture that's mostly green and yellow, with no reds at all. Failure of the B-Y signal will product a picture that's all reds and

purples with no green. It's also possible to get just chroma, i.e. a dark picture with only red and blue highlights. This indicates a failure in the luminance signal (YH) path.

If the vertical scanning is incorrect the Y signal circuits can clamp on video, reducing the Y signal and turning the picture magenta. This can often be verified by aiming the camera below a window or other bright light source and then tilting it upwards. If the picture turns magenta when the bright light hits the top of the picture, adjust the vertical centring and/or height until the picture is linear without the effect being present.

In the next part we'll deal with the CCD (solid-state) image sensor.


## The B & O L/LX2500/2800 Chassis


#### Nick Beer

The Beovision L2500, L2800, LX2500 and LX2800 chassis are used in models with type numbers in a series 37XX, e.g. 3701, 3702, 3712, 3720, 3741, 3752, 3760 and many others. As the chassis numbers suggest, there are 25 and 28in. models. LX sets come complete with teletext while the L sets can have a teletext panel fitted if required. The cabinets are teak, rosewood or "White Line". Fig. 1 shows the panel layout.

The sets are typically B and O, with high-quality finish, an excellent picture and superb sound, also flexibility of use/presentation. For example, a set can be used as the central item in the B and O Link System, in which compatible hi-fi, TV or video equipment can be controlled and operated via a remote control unit and a Beolink terminal or Master Control Panel. So you could say watch TV or video then select a track on your compact disc player and listen to its output via the stereo speakers of an LX type set. There's an LX-sat satellite TV decoder which, installed in the main receiver, can provide the display on a remote set in another room while the main set continues to provide terrestrial TV reception or VCR playback. We shall have more to say about the Link System in a later article.

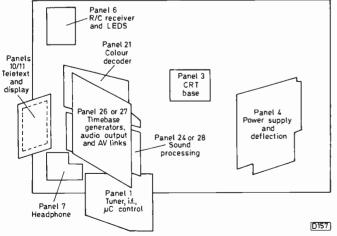As you might expect, with provision for so many features and B and O's reputation for fitting twenty per cent more components than are basically necessary, the circuit is rather daunting. Once you understand the workings of the set however you should have little difficulty in



 

tackling faults. The few troubles we've experienced to date have been fairly simple ones.

The most common fault so far has been failure of the mains switch. It's one of only two controls on the set, the other being a channel-step button. The mains switch brings the set into operation in the standby mode. Full operation is obtained when channel selection (or step) is used. What often happens is that the mains switch fails to latch. Fitting a replacement can be tricky. In view of this when we instal a set we usually advise against frequent use of the mains switch, suggesting instead operation via the remote control unit.

#### The Microcomputer Control System

To understand these sets it's important to know a bit about the microcomputer control and data bus system, which is outlined in Fig. 2. Operation of the set is controlled by three microcomputer chips which act via three bus lines. These buses are of the I2C type, i.e. each has two lines, one for serial data and the other for the clock signal. Arbitration is used to sequence/organise communication between the various devices in the control circuitry, to ensure that the correct overriding etc. takes place.

Two of the microcomputer control chips, 1IC6 (type MAB8461) and 1IC5 (MAB8441), are on panel 1 along with the tuner and i.f. circuitry. The set's main control line is Bus 1 which is controlled by 1IC6. Its serial data output is at pin 2 and its clock output at pin 3. This bus provides the control link to the tuning interface and memory, to 1IC5 which controls Bus 2 and to 24IC10 (on panel 24) which controls Bus 3. Bus 1 also controls the brightness, contrast and colour, via the SAB3037 DA converter/ decoder chip 21IC3 on panel 21. 1IC6 receives data from the remote control receiver at pin 12, which also receives Link System information from the Aux 1 socket. Remote control information from the VCR is fed into and out of the set via pin 8 of the scart socket, entering 1IC6 at pin 27. The AV remote control information from the Aux 3 socket enters at pin 26.

Power failure detection is also carried out by 1IC6, sensing being at pin 1. Fig. 3 shows the arrangement. The two transistors 1TR22 and 1TR15 provide a high input at pin 1 in the event of a fault being sensed on one of the lines they monitor. 1TR15 senses a number of supplies in

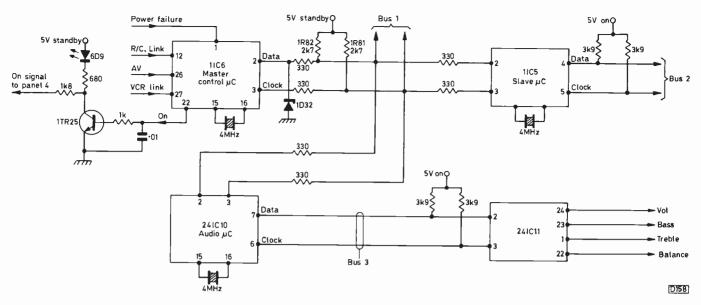


Fig. 2: Outline of the microcomputer control system.

the set, also the beam current, via a diode gate arrangement. 1TR22 monitors the supplies derived from the 17V line. When pin 1 of 1IC6 goes high the set goes into the standby mode.

The slave microcomputer 1IC5 controls the display panel (11) in L models and the teletext panel (10) in LX models, via Bus 2. Its serial data and clock pins for this bus are 4 and 5 respectively.

The third microcomputer chip 24IC10 (MAB8410) on panel 24 controls the SAB3037 chip 24IC11 via Bus 3. 24IC10 receives Bus 1 information on pins 2 (data) and 3 (clock), its outputs to Bus 3 being at pins 6 and 7. The SAB3037 acts in the same way as 21IC3 but this time provides d.c. outputs to control the volume, bass, treble and stereo balance.

For the serial data and clock signals to be transmitted along the relevant lines a d.c. level is required. The Bus 1 lines are pulled up to the 5V standby potential via 1R82 (data) and 1R81 (clock). In addition the data line is protected by the 5.6V zener diode 1D32. These items are suspect if there's no pull-up voltage and thus no data transmission along Bus 1. 11C5's Bus 2 lines are pulled up to the 5V on rail as this chip does not need to be active in the standby mode. The Bus 3 lines are likewise pulled up to 5V on.

#### **Circuit Features**

We will now take a brief look at some of the main circuitry used in these sets, starting with the chopper power supply – see Fig. 4.

When going from standby to on the voltage at pin 22 of 11C6 (see Fig. 2) goes low. Thus transistor 1TR25 switches off and pin 3 of the operational amplifier chip 4IC1 (Fig. 4) is positively biased from the 5V standby supply. The other input, pin 2, of this section of 4IC1 is held at 2.5V by a zener diode stabilised feed. The output voltage at pin 1 of this chip therefore rises to 15V. As a result, 4C23 charges via 4D26 and 4R32, producing a positive-going ramp which is fed via 4R31 to the emitter of 4TR4. This transistor with 4TR5 form a regenerative switch. When 4TR4's emitter becomes positive with respect to its base it switches on, in turn switching 4TR5 on. 4C23 is then discharged via 4R34 and 4D23. The low voltage at the collector of 4TR5 when it switches on is fed back to

the base of 4TR4 via 4C21 and 4R23. Thus 4TR4/5 are held on. As 4C21 discharges via 4R30 4TR4/5 unlatch. The sawtooth voltage thus developed drives 4TR6, the chopper driver transistor, which in turn drives the BU508 chopper transistor 4TR1 via 4T3. Note that 4T1/2/3 provide mains isolation. For timing and regulation, a negative-going pulse derived from winding 17-18 of the chopper transformer 4T1 is fed to the base of 4TR5 to control its switch-off time. The pulse obtained from 4T1 is an exact replica of 4TR1's collector waveform. It's clipped by 4R36, 4D28 and 4TR16 to produce a squarewave which is then differentiated by 4C22 and 4R27 to obtain the negative-going pulse that switches 4TR5 off. With 4TR4/5 off, 4C23 can once more begin to charge. The circuit is thus self-oscillating.

In the TV mode, regulation is based on monitoring the 150V h.t. supply produced by 4D6/4C10. A tap on the potential divider 4R8/37/90/38 feeds pin 6 of 4IC1. The other input pin of this section of 4IC1 is held at 5 1V by the action of zener diode 4D24. The error output at pin 7 of 4IC1 sets the bias at the base of 4TR4 and in consequence the point at which this transistor switches on. This regulation loop is kept stable by the action of 4C19 and 4R28.

In the audio only mode the 150V rail is not loaded and cannot be used as the basis for regulation. In this mode the 17V supply is used as the basis for regulation, via 4D47 and 4D48.

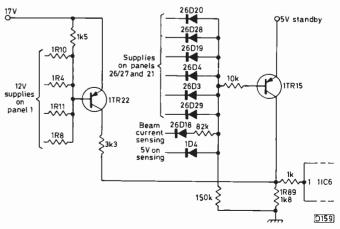


Fig. 3: The power failure detection circuit.

During start-up 4C23 charges via 4D26 from the 17V standby supply. When running 4C23 charges via 4D25 from winding 17-18 of 4T1. Since the voltage here depends on the mains input, the charging of 4C23 will vary as the mains supply varies, thus providing stabilisation against changes in the mains input.

The regulation provided by this circuit is certainly impressive. The set will run on 60V (and that's with a 28in. c.r.t.!) and will start up with a 150V input.

The line output stage is conventional, using a BU508 (4TR11) line output transistor, a diode-split line output transformer, and a diode modulator for EW correction. The line output transformer provides the e.h.t., first anode, focus and c.r.t. heater voltages and also the +12V and -12V supplies used by the TDA2170 field output chip. The line drive signal is generated by a TDA1940 chip on panel 26/27 and is fed via 26/27TR3 to panel 4 where four transistors (4TR8/9/10/15) are used in the driver stage (no driver transformer). The purpose of 26/27TR3 is to act as a switch to remove the line drive in the audio only mode – this prevents e.h.t. generation.

The field sync pulse output from the TDA1940 chip on panel 26/27 is passed to the colour decoder panel 21 and then back to 26/27TR21. This transistor's output is used to control the field oscillator, which consists of an LF353 dual operational amplifier chip (26/27IC6). Half of another dual operational amplifier chip, 26/27IC7 (LF358), acts as the field preamplifier which drives the TDA2170 on panel 4. The other half of 26/27IC7 provides EW drive. The TDA2170 drives the field scan coils directly – this is made possible by the energy efficient c.r.t. deflection system.

The field oscillator runs at 47Hz to allow for graphics injection (e.g. tuning information) with no signal and thus no sync. The sync provides the extra three for 50Hz.

Two TDA2040 chips on panel 26/27 provide 15W of audio output per channel at  $8\Omega$ . Each channel has a 4in. woofer and 2in. tweeter, with external speaker options.

#### **Table 1: Tuning Display Frequencies**

Channel	On-screen display-MHz	Channel	On-screen display-MHz
21	471	46	671
22	479	47	679
23	487	48	687
24	495	49	695
25	503	50	703
26	511	51	711
27	519	52	719
28	527	53	727
29	535	54	735
30	543	55	743
31	551	56	751
32	559	57	759
33	567	58	767
34	575	59	775
35	583	60	783
36	591	61	791
37	599	62	799
38	607	63	807
39	615	64	815
40	623	65	823
41	631	66	831
42	639	67	839
43	647	68	847
44	655	69	855
45	663		

The output from the audio detector is mono of course. It's split and fed via switching i.c.s 28IC1/2 then through 28IC7 to the dual volume/tone control circuits in 28IC8.

Teletext subtitles can be recorded on these sets and also printed by a suitable printer (LX versions of course). As mentioned earlier, the L models are teletext adaptable. This calls for removal of the display board – but hang on to this for diagnosis (it can prove a Bus 2 fault or teletext decoder fault). Note also that because of the power fail circuit these sets will not operate unless one or other of these boards is fitted. The on-screen display with text sets is provided by the text panel.

Tuning is not by the well-known channel numbers (21-68) but by frequency. Table 1 shows the equivalents.

Despite the fact that the retail price of the LX2800 was over  $\pounds1,000$  these sets sold well in our area. They have since been replaced by the LX2502/2802 series (38XX type numbers) which have only two buses and built-in Link processing.

#### Stuck in Standby

Our experience has been that faults are usually supply related or in the Bus 1 system. In either case the set will go into standby, as previously described. If you have a set that's stuck in standby and you don't know where to start, proceed as follows.

(1) Try to start the set in the audio only mode. If the set comes on you can rule out faults in the secondary supplies as these will all be up and running. It's likely that there's a Bus 1 fault. The best policy is to switch off, short out the test link connected to pin 11 of 11C6 and try the set in the TV mode again. This overrides bus error detection. The set will now more than likely start. If so check for data and clock signals on the appropriate lines. If absent check for d.c. pull-up. As previously mentioned absence of pullup can be caused by open-circuit pull-up resistors or the protection zener diode being short-circuit. Another possibility is excessive loading due to a faulty i.c. The bus lines should give a resistance reading to chassis of  $3.5k\Omega$ . A quick check is to remove the  $330\Omega$  series resistors (see Fig. 2) to see if this resistance returns. Also look for tuning. If there's none, suspect a fult in the tuning interface or memory.

(2) If the set won't start in the audio only mode look for loading on the power supply, i.e. 4T1's secondaries, for example a short-circuit line output transistor. Such secondary loading is indicated by a noise in the chopper transformer. If there's no noise, suspect a mains input or control circuit fault. 4R3 could be open-circuit or 4TR1 may have failed. For repeated failure of 4TR1 check whether 4C15  $(1\mu F)$  is open-circuit.

(3) Check for power failure detection at pin 1 of 11C6. A high here indicates an overload on one of the l.t. supplies.

Once you've understood the basic operation of the chopper power supply and the bus control arrangements you should have no difficulty in repairing faults in these sets. Develop the correct technique for these areas and the rest is much the same as with anyone else's sets!

#### Fault Report

Here's a list of some of the faults we've had. (1) A completely dead set (no standby light) is usually due to a burnt up mains switch. If the subpanel is damaged, as it usually is, the complete assembly (part number 8003605) should be replaced – this is done through the

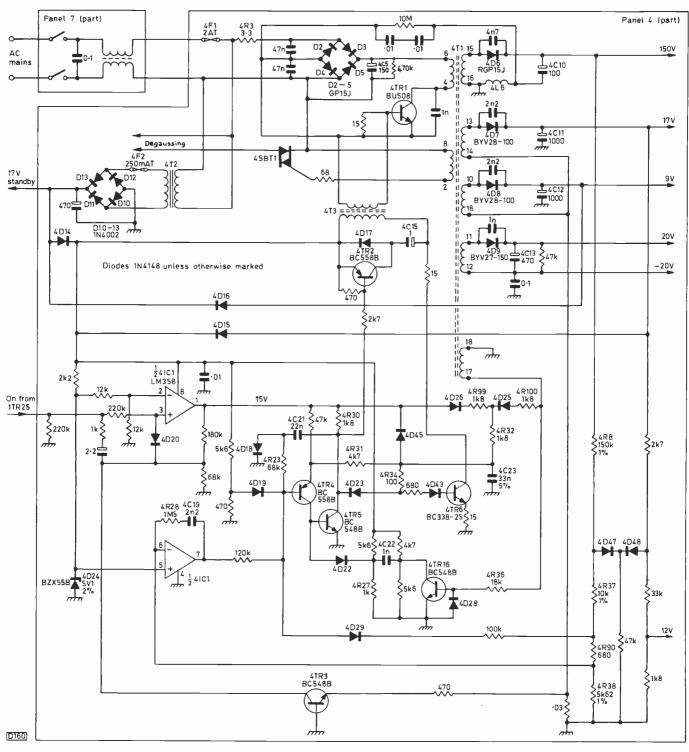


Fig. 4: The chopper power supply circuit. In earlier versions 4R32 was  $3.9k\Omega$  with 4R99 and 4R100 omitted. There have been other minor modifications to the circuit.

flap in the bottom of the cabinet.

(2) The most common cause of a set being stuck in standby, again usually preceded by smoke, is an opencircuit surge limiter resistor (4R3,  $3 \cdot 3\Omega$ ). A type with improved construction is now supplied.

(3) Reduced width and height has on a number of occasions been traced to the line flyback tuning capacitor 4C32 (1.5nF) being open-circuit.

(4) Stuck on standby, not a Bus 1 fault. The line output transistor 4TR11 short-circuit.

(5) A few lines of field foldover on the picture. Check the  $0.1\Omega$  resistors 4R74 and 4R75 in series with the supplies to the TDA2170 field output chip.

(6) No control of a VCR via the Aux 2 socket when used

in conjunction with a Beomaster 5500 and Master Control Panel 5500. Data reaching 1IC6 (MAB8461) but no output to the scart socket. Programming of options (datalink) correct but 1IC6 faulty.

(7) No picture when brought on from standby via the MCP 5500 with the above system. 21IC3 (SAB3037) faulty.

(8) No line or field sync after a few seconds. IC5 (TDA1940) on panel 26/27 faulty.

(9) Teletext not running, top line only displayed. Horizontal phase control 26/27R65 slightly off.

As a final note, when removing the back cover it's not necessary to remove the screws completely – this saves losing them.

# Letters

### **REBUILT 30AX TUBES**

Having read the article on servicing the Ferguson TX10 chassis (January) I feel I must comment on the final section under the heading "the tube". The author says that retubing a TX10 is a good proposition but goes on to say that sadly very few rebuilt tubes perform to the original standard. I've been in charge of our small rebuilding business for thirty years and can assure you that our 30AX tubes perform to the original standards - many of our customers tell us this. We are an associate of CHS Ltd., Barmby Road, Pocklington, Yorkshire ('phone 0759 303 068) who distribute our tubes to the servicing trade. J.R. Leigh, Retube Ltd.,

North Somercotes, Louth, Lincs.

### EHT ARCING

In reply to G.R. Darby, my article on e.h.t. arcing (January) was written in "strong terms" following a spate of faults that came into our workshop following misguided attempts to deal with problem. A large Japanese manufacturer does indeed smear silicone grease under the anode cap – but the points here for those who pour it over a dirty cap are *smear* and *under*. To keep matters brief I didn't originally mention the problems caused by gas heaters. The point to note is that the whole treatment hinges on the area being thoroughly cleaned.

Nick Beer,

Bideford, Devon.

I feel I really must comment on Les Lawry-Johns' article in the February issue. There have been many letters in the magazine over the past few months on the subject of cowboys and amateurs attacking equipment and getting the trade a bad name. An article on servicing to BEAB standards appeared recently and in the January issue there was an article on dealing with e.h.t. arcing. In view of all this how can someone of Les's standing report fixing two e.h.t. discharge problems by bodging with tape? I'm pleased that the customers were happy when they left the shop. Perhaps they won't be when their sets burst into flames as a result of smouldering PVC tape. We should all be working to stamp out such bad practices.

G.R. Darby, Proprietor Monitech, Earls Barton, Northampton.

I'd like to support the views expressed by G.R. Darby (Letters, March) on the subject of e.h.t arcing. So much in servicing is a matter of common sense. Manufacturers and service organisations alike, no matter what their size, are aware that the products they handle go into people's homes. Thus safety is the first consideration and price, though important, is secondary.

As Mr. Darby says, e.h.t. arcing is common with TV sets installed in homes where the occupants smoke heavily, run a bottled-gas heater, dry cloths in front of the fire and so on. No service engineer in his right mind would patch up a final anode connector which has failed under these conditions, but when a new cap has been installed it would be sensible to add some sealant to attempt to delay the date of the next replacement. Not good for business may be, but life's a gamble anyway! Many workshops

salvage undamaged e.h.t. caps from defective triplers and diode-split line output transformers, saving expensive repairs whilst keeping the job wholesome. Common sense and good judgement are again necessary here.

TV manufacturers generally don't seal final anode connectors because it involves additional expense and another operation on the production line, for something that's of benefit to only a small minority of the end users.

All of us in this industry have a duty towards the general public in making sure that the repaired equipment we return to their homes is as safe as it was when new, if not safer.

K. Rutherford, Nottingham.

### AMSTRAD AND RANK PARTS

Since I last wrote (Letters March) I've been told by CPC that they can now order R814 (27 $\Omega$ , 20W) for the Amstrad CTV2200/2210 under the revised part number 1422031.

With reference to D.R. Isham's interesting letter, if any reader would rather buy the selector cams/nuts for the four-button mechanical tuner used in many Rank sets I have a stock and can supply 16 for an s.a.e. plus £1 (coin or P.O.).

Dave Mackrill, 32 Southwater Road, St. Leonards-on-Sea. East Sussex TN37 6JS.

### **ORACLE PUZZLE SOLVED**

In reply to C. Russell's letter (February), the information on the Oracle lines mentioned is ITV's own data broadcast system used by a chain of chemist shops, the city, betting shops, some libraries, etc., etc. To receive the pages you require a special decoder and to be enabled by ITV - unless enabled for a fee the decoder will not reveal any more than a standard TV set with teletext does. But you would be amazed by what can be done with a second-hand computer, a few chips and a few hundred hours.

A.J. Goloshof,

Tewkesbury, Glos.

In reply to C. Russell, I managed to get this on page 799 (ITV):

P799 AIR CALL TELETEXT STOP						
VALID AT 19-JAN-89 — 3:25 PM						
ATTACHED TO SYSTEM — SYSC-SYS16						
НР ТХ —	9	LP TX —	0			
SC Q5 —	0	CA Q5 —	0			
FRO — 572612 FR1 — 0						
TURN TO PAGE 700						

Although I've tried page 700 nothing happens, but if you turn to page 188 more details are available. I suspect that pages 701-3, 713-5 and 719 are part of this system for which a decoder would be required. Incidentally "P799" is very difficult to stop because it scrolls down the screen in a fraction of a second every sixty seconds.

D.R. Hindley,

Bradford, West Yorkshire.

I think I can shed some light on the latest Oracle puzzle (letters, February). With the aid of the wildcard facility on the time-page entry to my computer's teletext card I was soon able to determine that the time code to hold page 799 is 1312. Despite the reveal button exposing more information, the key words on this page are "air call teletext". This name is mentioned (as Televox is) on page 270, regional advertising. I was then led to page 188 and from there to the telephone. In reply to my call I was told that the company is providing an ASCII data transmission service that can be an economical alternative to a modem link.

The data is encrypted and appears as garbage on pages 715 etc. on the TV screen. For subscribers with a blackbox adaptor however the data can be decoded and fed to an RS232 port. Companies that use this service include High Street stores, travel agents, etc. The information on page 799 is for the benefit of the providers of the system, some of the details of which may I suspect have changed slightly since the page was composed. I could find no sign of activity on page 700.

Tim Bolt.


Cambridge.


### CURE FOR FIELD JUDDER

I was recently given an old Betamax machine that was otherwise going to the tip – I wanted it in order to see a Donohue tape on cryonic suspension recorded by a friend who has a Betamax VCR. In view of the resale value of working Betamax machines professional repair is no longer economic. So it was not unreasonable to try something unconventional.

Unfortunately the machine, a Toshiba V5470B, suffered from drum wear and tape alignment problems. This meant that although a picture could be obtained it was not up to the usual standard. Although the dots and lines on the screen could be cleared the f.m. envelope was still poor, causing an infuriating field judder.

Despite not having a service manual I was able to find the playback video level control and a test point where the head switching squarewave was present. Examination of the video at this control showed that the sync pulses are positive going. I therefore made up a circuit (Fig. 1) that provides a pulse slightly in advance of each field sync pulse. The positive edge of the head switching squarewave is inverted by Tr1 and then passed through a differentiator to Tr2. A second differentiator feeds the input to Tr3. An output pulse is thus obtained from both edges of the squarewave. If the manual had been available a better take-off point from an electrical point of view could probably have been found, but the test point is in a very convenient position. The output, a series of narrow pulses at field frequency, is fed via a  $1k\Omega$  resistor to the video level control where it's mixed in with the video signal. As the pulses are derived from the head rotation servo they are effectively a "flywheel field sync" and are therefore immune to all but the most serious interference. Since they come slightly in advance of the real field sync pulses it doesn't matter what mess interferes with these.

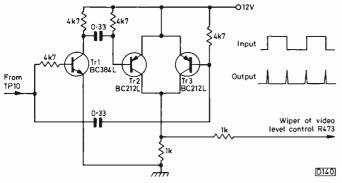

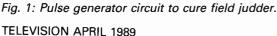

The circuit was built on a small piece of tagstrip and held in place by stiff wires to TP10, which is at the top side of the machine on the panel next to the top left-hand corner of the tuner setting panel. The earth connection was taken to a chassis point near this while the 12V supply required was taken via a wire connected to the large electrolytic at the top right-hand corner of the mechanical section. The machine was then turned over to make the connection to the playback level control. With the machine upside down and the bottom cover removed this control is at the bottom left-hand corner of the big panel. The 1k $\Omega$  resistor was soldered to the wiper of this control, the connecting lead being taken through the machine back to the new circuit.

It would seem to me that this is a good way of generating the field sync signal in all VCRs. It will improve reliability and the playback of poor tapes. The cost of the circuitry at the manufacturing stage would be negligible.

John de Rivaz, B.Sc. (Eng.), Porthtowan, Cornwall.

### **HELP WANTED**

Can anyone supply a service manual/circuit diagram for the Sona 12in. monochrome portable Model S1286? The set was made in Rumania and distributed by Reay Electrical Distributors Ltd. who are unable to help. *K. Pocock, 500 Ripponden Road*,

Oldham, Lancs OL4 2LL.

Does anyone know of a source of the CA3023 i.c.? It's a 16MHz wideband amplifier. Grandata had listed it but no longer has stock. Another problem is the scarcity of 8501 chips for Commodore 16s and Plus 4s. A container load from the States wouldn't dent the requirement for these i.c.s!

A. Gall, 2 Commerce Street, Arbroath, Angus DD11 1NB.

Can anyone suggest a source of the TBA641A12 i.c. which no longer seems to be in stock anywhere? *F. Dawson, 32 Perry Street, Darwen, Lancs BB3 3DG.* 

Is there an ex-Rediffusion engineer or anyone out there who can help me make an old lady happy? The problem is teletext interference with a Mk. 13A monochrome receiver. I've tried several things but can't get rid of the lines. I'll gladly accept a reverse charge call on 0773 810 522 (daytime) or 0602 384 176 (evenings). *C. Newman, 58 Portland Road,* 

Selston, Notts.

Can anyone supply a line output transformer for the Plustron Model CTV14? Several firms have been tried without success.

Len Sutton, Kildare Bungalow, Baghill Lane, Pontefract, West Yorkshire WF8 2HE. Telephone 0977 797 063.

### **TDA1004A AVAILABLE**

Your correspondents who asked about the TDA1004A i.c. (February) might like to know that it's available from Greenweld Electronics Ltd., 443 Millbrook Road, Southampton SO1 0HX ('phone 0703 772 501). *David Hills*,

Newport, Gwent.

# Strange Things

### Les Lawry-Johns

Some odd things have been happening to sets around here. Take the two Ferguson TX9s that came in recently.

### A Couple of TX9s

The first was brought in by a chap from just over the road. He said the colours were wrong - blue faces etc. I told him to call back later and started on it. The faces were certainly blue, as was the colour of the snooker table. I checked everything thoroughly, first the resistors etc. on the tube base panel then back to the output transistors on the main panel. There was nothing amiss so, feeling a bit of a fool, I removed the RGB drive leads from the tube's base panel. Red at the bottom, blue in the middle and green at the top. I put the red lead at the top and the green one at the bottom. The faces then looked all right but the fields were blue. So I changed over the green and blue leads, which produced green fields and a green snooker table. We now had the blue lead at the bottom, the green lead in the middle and the red one at the top. I didn't like doing this and it worried me. The set was left working all day and when the chap came back I told him what I'd done. He looked at the picture and said it was perfect. I asked him whether anyone had worked on the set and he said no.

So what had gone wrong to make it necessary to swap over the drive leads? The manual says that the green lead should be at the bottom, the red one in the middle and the blue one at the top. Surely the cathodes can't change their colours in this way? The leads looked to be undisturbed, correctly wrapped round – now they are soldered on. The set continues to work well. Strange.

The second TX9 came in with intermittent field collapse. I fitted a new TDA1170S field timebase chip and the set worked for several hours. Then suddenly the field collapsed again and when I pulled the chassis out the field scan was restored. I tapped around and it collapsed again. Next I found that there was no voltage at D94, the rectifier that provides the 24V supply for the field timebase. After a lot of mucking about I discovered that the field collapse came and went when pin 12 of the line output transformer was tapped – it connects the earthy side of the winding that feeds D94 to chassis. I cursed myself for not thinking of this earlier and remade the joint. No amount of tapping had any effect after that. Another easy job made difficult by my bungling.

### **Fidelity Problems**

Fidelity CTV14Rs (ZX2000 chassis) never used to give me any trouble. One came in the other week and seemed to work fine after I'd fitted a new line output transformer. Shortly afterwards it came back. This time I found that the BU208 line output transistor was shorting intermittently. On the last time it had done so it had blown the BUW84 chopper transistor. So I replaced both transistors and the set worked fine. Until next morning, that is. When I switched it on there was a loud bang. This time the BUW84 had shorted, blowing the mains fuse. I checked everything and fitted a new line output transformer, a new BU208 (just in case), two new bridge rectifier diodes, another BUW84 and a mains fuse. The set then worked normally but next morning there was another loud bang at switch on and I was back at square one. Why should a set that works perfectly when repaired go bang next morning? To cut a long story short, apart from two line output transformers, three BU208s, several BUW84s and of course fuses I must have fitted at least a dozen mains rectifier diodes before the set would work reliably.

When the owner came back I told him what had been happening to the set, and to me. He took it away and gave me back an aerial amplifier he'd purchased a week before, refusing to take any money for it. There are some nice people about - I'd begun to think that they were getting to be a bit thin on the ground.

Incidentally I'd like to thank those nice TV boys in Plymouth who repaired my daughter's Fidelity set – the one I'd given her some time ago. I hope it didn't give them as much trouble as the set just mentioned. I also wish they'd come and fix this CTV14 (ZX3000 chassis) that came in with a blank white screen. The lady who brought it in said there wasn't much wrong with it and I'd be able to do it in no time.

I thanked her and started on it. The screen was bright with white lines across it. So I turned down the first anode knob on the line output transformer and changed the TDA3562A colour decoder chip. With the new chip installed a picture appeared. I'd turned the brightness down, and when the controls were readjusted there was a good monochrome picture. But when the colour control was turned up the picture remained in black and white. She said the set required only minor treatment so I gave it up and returned it. I feel ashamed of myself, but there it is – I'm getting old and don't want to do things for nothing.

### The Pye G11

A Pye G11 came in recently with no sound or vision. I did my usual checks before switching on – the mains and h.t. fuses all seemed to be intact. So I switched on and heard the e.h.t. rustle up. But there was no l.t. supply at the lower left side i.f. panel. When the line output panel was swung out I found that the lower, 1A l.t. fuse was open-circuit. After switching off I checked from the fuseholder to chassis. There was a dead short which disappeared when the long socket was unplugged. So I turned my attention to the lower left side i.f./tuner panel, having refitted the socket on the line output panel.

As the short was still present I suspected the 12V regulator. When I removed the power input socket however the short disappeared. I started to frown at this and went back to the line output panel. Removing the socket here once more cleared the short. So what was I up against? A short in the wiring? I checked for this but there were no shorts.

It appeared that the short was present only when the socket was connected. I then did what I should have done in the first place. I again removed the socket, then checked from the fuseholder to the panel's true earth (not the frame). This time the short showed. A look at the circuit suggested that the LT1 supply's reservoir capacitor C1350 was the culprit, and when this was removed all was well. A new  $150\mu V$ , 50V electrolytic restored the sound and vision and after a final check it was time to write out the bill. Another example of making life difficult for myself . . .

### Philips VR6470 and Related Models

### **Barry Loughran**

The machines covered by these notes include the Tatung VRH8495TK, the Philips VR6470 and VR6670 and the Pye DV468, DV562 and DV761. They all use Philips mechanisms and electronics and there are probably other clones. We've serviced a hundred or so of them, and as a result have been able to note a few common faults. These are listed below.

**13V line missing:** Replace transistor 7001 (BD436) and IC7051 (LM393). Always replace them both before switching on.

Loud crackling noise while loading: This is usually caused by a broken tooth on the rack slider. Replacement is the only cure.

Noisy playback, rewind, fast forward or no rewind or fast forward picture search: This has always been found to be due to coupling 214. Repairing this will restore normal operation.

Tape jams in deck: Can be tape stop broken in cassette deck, spring 215 bent or cam 217, 206 broken.

**Poor Picture:** Usually caused by poor video heads. The type of head used often seems to last for only about one

year. On a few occasions the cause of the trouble has been the spring coming off back-tension lever 204.


Switches off when fully loaded: Check whether the capstan motor is trying to go in reverse. If so replace IC7251 (L293B).

**Tape loads then unloads:** If this is not caused by a badly positioned cassette deck try replacing the tape-end sensors.

Tape loads only half way when play is pressed: The threading motor can have a tight spot.

This has covered most of the main problems we've had with these machines. On one or two occasions however we've had a very weird problem. The complaint has been that at times the machine won't accept a tape. On each occasion when the machine has been put on the bench the fault has been present and no initial measures would cure it. The tape was then loaded half way using a battery connected to the threading motor. After connecting the mains the machine unloaded and after this the machine accepted a tape on all occasions. We could instigate the fault only by unloading the tape, switching off at the mains then reconnecting the machine. The cause of the problem was eventually traced to the fact that when IC7551 was being reset it held the threading motor on for six seconds longer than it should have done. Replacing IC7551 puts matters right.

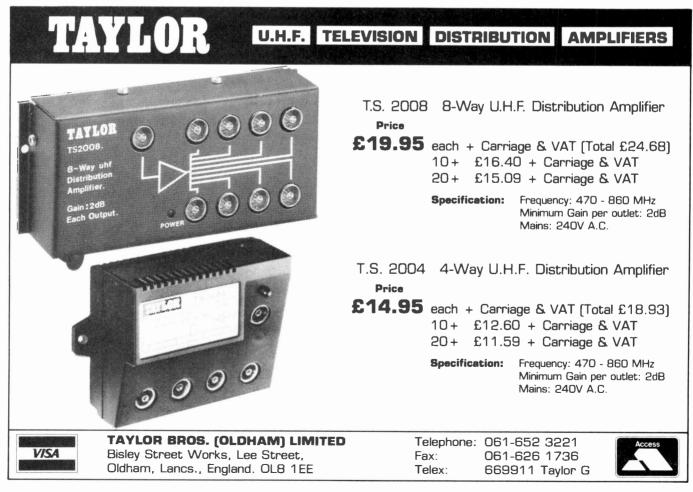As a final point, when replacing the top plate make sure that the pressure roller assembly is located properly. Otherwise the teeth on the rack slider can be broken at the first attempt to load a tape.



**TELEVISION APRIL 1989** 

ź

2 2551129 166 1/6/169 0007 BOLTA 000 BOLTA 000 100 BOLTA 000

NV100 NV200 NV366	Orion H1 H2	V400 V400 V500E V500H	V302 V350 V380	V250 V300E V300H V300K	V100E V1001 V100H V100K V101 V102 V102 V150 V150	<b>NEC</b> PVC470E PVC2400 <b>NordMende</b> Spectravideo VIS Spectra W
m m m m	mm -		п ппО <sup>(5)</sup>	л л О О	тсс оогт © € € 0	
20VR20 20VR22 20VR22 20VR23 22VR20	VR2323 VR2323 VR2324 VR2334 VR6520	VR2022 VR2023 VR2024 VR2025 VR2225	N1500 N1700 VR2020 VR2021	NV8600 NV8610 Philips	NV2000 NV2010 NV3000 NV7000 NV7200 NV7800 NV7800 NV8400	NV370 NV688 NV730 NV777B NV788 NV788 NV7850
ד <u>ב</u> ת ד	· لد ۲ ۲ U	ב ה ה ה ת	(1) (1) (1) (3)	ლი ი	៣ ç ល៣ ា ៣ ៣ ៣ ៣ ៣	ᇭ ᇬ ᄀᅟᇚᇭᇭᇭᇭᇭᇭ
<b>Sanyo</b> VC8700 VC9700 VPR5800	Salora SV8300 Sansui SV7020	VR7720 <b>Saisho</b> VR705	VR6024 VR6028 VR6068 VR6069	VR6010 VR6012 VR6020 VR6022	<b>Rank</b> 6910 <b>Saba</b> VR2000 VR6000 VR6000 VR6004	23VR24 23VR33 6520 <b>RCA</b> TC3451X
mOO	C B	וד 🛄	ד וד וד וד	ד וד וד וד ו	ם ורודאו	m 777
VC3300 VC6300 VC7300 VC7700	VC390 VC482 VC486 VC496 VC2300	VC220 VC381 VC385 VC387	FM204.7 FM304 Sharp	Siemens CVC500 FN204.6	VTC5600 VTC6500 VTC9300P VTC9300PN VTC M10 Schneider SVC20	VTC3000 VTC3000P VTC5000 VTC5150 VTC5300 VTC5500
	<b>"</b> იიიი	مەمە	ד וד	ם תיו	G moomi	Immmm>m
V8600 V8650 V8700 V9600	<b>Toshiba</b> V31B V33B V55B V55B V57B	<b>Teleton</b> VG200B VG220B VG240B	<b>Telefunken</b> All F except: VR520	<b>Tatung</b> VRH8300 VRH8500	SL3000 SL8000 SLC5 SLC5 SLC7 SLC7 SLC7 SLC7	VC7750 VC8300 VC9300 VC9700 <b>Sony</b>
۵۵۵۵	റെപ്രമ	ត ត ត	C	<i>د</i> 0	m m m m m m m m	00000

# **TELEVISION VIDEO INFO CARD - 2**

### **INTERCONNECTING LEADS**

To link two VCRs for signal exchange, find the intersection of their group columns and rows in the matrix then refer to the list for source and part number of the link required.

								(~~=	1 6/		100	- U D. U V-			P V U V	- 0		-
							981/0	51-50	:Е Ча	ł	*006-	19 Pi 211	7	2	211-68	33 b!	511-684	181
							7	CL93	SAF	4	951A	AV 69		g	29-112	35 b!	989-112 !c	121
					= 44		0	1-1	LZ !a	1 9 9 L	899-	18 b! 511	7	68	IAAV.	eЧ	<b>VRA137</b>	ł
					= 6 9		7870	51-50	2E 44	-	699-	112 ig 711	7	2	29-112	31 B!	029-112 !c	191
		Э	loen	ni9 =	= !d		*0	06-l	LZ !c	24 E	¥134	ЯУ 6Ч		22	ILAAV	eЧ	641AAV 69	-
							2	89-L	LZ !c	23 L	990-	16 Pi 211	7	G	69-IIZ	30 b!	169-117 !c	19L
			(ι	(3u			*0	06-l	LZ !c	25 E	1-20482	25 AG		0\$	VBA14	eЧ	EELAAV 6	-
		<b>۲8</b> ۲	0Z-13	ZE 4	d		3	89-L	LZ !c	119	*006-	12 LZ !d St	7	3	29-112	29 P!	599-LLZ !c	171
											IBIA	AV 69		88	гаяν	eЧ	241AAV 69	ł
											£69-	117 Pi 211	7	l	29-112	28 b!	LL9-117 !c	13 E
			1 m (m		otqet		•				<del>1/</del> 69-	13 b! 511	7	1484	1351-50	48	APLAAV 6	ł
		,	۸q (p								841A	AV 69		*0	06-IIZ	27 Pi	511-68t	121
			,		-g pi			•••	,		069-	t5 b! 511	7	£t	лΑЯΛ	еЧ	341AAV 69	ł
				/ou	ION4			-			9⊅1∀	AV 69		2	89-112	26 Pi	289-112 le	111
							6 10				889-	tI b! 511	7	3	89-112	26 Pi	*006-LLZ !c	101
К	99					be	əl-γq				*006-	t0 b! 511	7	98	гаяν	еЧ	629-117 la	6
ſ	179	23						•	dns		8132	AV 69		8	511-66	54 b!	089-112 la	8
Н	22	۱S	09				alers				t <del>/</del> 99-	36 B! 211	2	19	ILAAV.	еЧ	<b>JELAAV 6</b>	ł
Ð	67	48	L4	97			STS		etur		-993	38 b! 511	2	3	511-69	53 b!	LL9-117 !d	17
Н	9Þ	44	43	45	11			tsol	∕l :9:	toN	151A	AV 69		32	IAAV.	еЧ	021AAV 69	ł
Э	40	36	38	22	36	32					۱99-	37 Pi 211	2	7	511-66	22 b!	Z69-112 !d	9
D	34	33	35	31	30	56	58				741A	AV 69		lt	'NBA1	eЧ	511-662	9
С	<b>Z</b> Z	97	52	54	53	52	2٦	50			689-	36 Pi 211	2	9	29-112	51 b!	- 711-674 -	17
В	6٤	3٤	۲L	9٤	S۱	14	13	٦S	11		051A	AV 69		33	I A A V	еЧ	629-112 le	31
A	0١	6	8	L	9	S	4	3	2	L	099-	39 b! 511	2	2	211-68	20 b!	189-112 le	5
	К	ſ	н	Ð	Н	Э	D	С	В	A	*006-	34 Pi 211	2	*0	511-90	19 Pi	849-117 la	11

### **VCR-TV LINKS**

(ug·L)

50 Pi 211-685

Pa VRA144

Γ₄ιΑЯV 69

	24 b! 211-216	Ph 321-20485	ETIAAV 69	DIN	-8 NIC	I-9 ТЯ,	∀CS	ΛL
30 +	23 b! 211-20e	+006-112 iq ∂1	9 Pi 211-515	30	6Z	82	К	
29 Pi 211-900*	22 Pi 211-900†	071AAV 69	681AAV 69	ĹŹ	97	SS	ñ	
(m£)	ITIAAV 69	16 Pi 211-511	8 Pi 211-505	54	53	52	Ĥ	
Ph 321-20487	21 Pi 211-512	081AAV 69	Ph 321-20484	LZ	07	6L	וי. פ	
(ug·Ļ)	181AAV 69	14 b! 211-201	×006-112 ¦d 7	81	21	91	Ĕ	
Ph 321-20486	20 b! 211-202	13 b! 211-900*	6 Pi 211-517	٩L	14	εı	Э	VCB {
38 b! 211-900∗	19 211-900÷	STIAAV 69	5 Pi 211-507	15	LL	ΟL	ā	
27 Pi 211-515	Pa VRA174	15 b! 511-213	*006-LLZ !d Þ	6	8	Ĺ	ō	
Pa VRA183	18 b! 211-218	281AAV 69	3 b! 511-214	9	g	4	8	
26 Pi 211-505	₽81AAV 69	11 b! 511-203	2 b! 211-504	3	2	L	A	}
26 Pi 211-900*	17 Pi 211-508	10 Pi 211-900∗	*009-112 ig 1					

Notes: TV/VCR manufacturers can supply link-leads to couple any two of their own products. Special leads can be made up by Lektropacs, 17 Turnham Green Terrace, London W4 (01-994 2784); quote length required and equipment model numbers or socket types.

\* The Pinnacle SCART-Universal lead consists of a SCART plug and lead with terminal adaptors for groups A K inclusive.

+ Available from Tape Recorder Spares Ltd., 206 Ilderton Road, London SE15 (01-639 7844).

Etron. Brand name used by Nikkai Imports Ltd.

Expert. Spares from Tatung, GEC or Luxor depending on chassis.
Ferguson Ltd., Service Division, PO Box 121, Lea Valley Trading Estate, Angel Road, Edmonton, London N18 3BP. 01-807 3060. Move due to Box 1594 Crown Road, Enfield, Middx EN1 1DV. 01-804 7979. Trade only. See also CPC, HRS, Chas Hyde, Wizard.
Fidelity. Spares available from SEME, CPC, McLelland, Wizard and Willow Vale.
Finlux. Lohja UK, Ltd., Valley Farm Way, Stourton, Leeds LS10 1SE. 0532 714 521. Trade only.

Fisher Sales (UK) Ltd., PO Box 294, Watford, Herts WD2 8JF. 0923 222 244. Fujitsu General. See Teleton Electro (UK) Co. Ltd.

Galaxy monochrome portables. See Iskra Ltd.

**GEC.** Spares available from Hotpoint Ltd., Celta Road, Peterborough PE2 9JB. 073 368 989 See also CPC, Chas Hyde, McLelland, SEME, Wizard.

General. See Teleton Electro (UK) Co. Ltd.

GoldStar UK Sales Ltd., Goldstar House, 264 Bath Road, Slough SL1 4DT. 0753 691 888 Spares for Model GHV1232I available from Cathay Electronics.

Goodmans Loudspeakers, Tees Building, Unit 2-3, Mitchel Way, Portsmouth PO3 5PR. 0705 673 734

**Grundig** International Ltd., Mill Road, Rugby, Warwickshire CV21 1PR. 0788 565 128. Account holders only supplied. See also Willow Vale. Spares for VCR4000 and SVR4004 ranges available only from Willow Vale.

HMV. Sets use Ferguson or Fidelity chassis.

Harwood. Spares available (trade only) from Jackson Products Ltd., 18th Floor, Station House, Harrow Road, Stonebridge Park, Wembley, Middx HA9 6DE. 01-900 0433.

Hinari Consumer Products Ltd., Unit 6-10, Badenheath Place, Westfield, Cumbernauld, Glasgow G68 9HX. 0236 722 505. Account holders only supplied. See also CPC, Chas Hyde, SEME.

Hitachi Sales (UK) Ltd., Hitachi House, Station Road, Hayes, Middx UB3 4DR. 01-848 8787, Account holders can use 01-569 1843 (known part no.) or 01-569 1975 (part no. not known). See also Chas Hyde, McLelland, Wizard.

HRS Electronics plc., 11 Garretts Green Lane, Garretts Green, Birmingham B33 0UE. 021 789 7575. Wide range of spares including Ferguson, Philips, Rank etc. Trade only.

 Huanyu. Spares available from Audio Visual Technical Support Ltd., 67A Shelson Avenue, Feltham, Middx TW13 4QS. 01-890 3004 or 3010.
 Chas Hyde & Son Ltd., Prospect House, Barmby Road, Pocklington, York YO4 2DP. 0759 303 068. Official spares distributors for Ferguson, Philips, Pye and Sharp. Spares stocked for Amstrad, GEC, Hinari, Hitachi, Matsui, Saisho, Samsung, Sanyo, Sony, Toshiba etc. Trade only.

Indesit. Spares no longer available from manufacturers/agents.

Ingersoll. Spares available from Plusmaster. Iskra Ltd., Redlands, Coulsdon, Surrey CR3 2HT. 01-668 7141. ITC(bv), P.J.E. Marketing Ltd., Sporhams Farm House, Sporhams Lane, Danbury, Chelms-ford, Essex CM3 4AJ. 0245 414 292.

**ITT and ITT Nokia**. Spares available from Hoopwell Ltd., Unit B9, Larkfield Trading Estate, Larkfield, Maidstone, Kent ME20 6SW, 0622 882 285. See also Wizard.

JVC (UK) Ltd., JVC House, Eldonwall Trading Estate, Priestley Way, Staples Corner, London NW2 7BA. 01-450 3282. Trade only. Konica, Plane Tree Crescent, Feltham, Middx TW13 7HD. 01-751 6121.

Körting. Spares available from Telefaults, St. Michael's Road, Pitts Hill, Turnstall, Stoke-on-Trent ST6 6LS. 0782 813 757.

Lincoln. Spares for Model 35C available from Nikkai Imports Ltd.
Lloytron Electronics Ltd., Service Dept., Kingsonic House, Derby Street, Cheetham, Manchester MM8 8HB. 0618 328 320.
Loewe Opta UK Ltd., Sherwood House, 33-35 Wellfield Road, Hatfield, Herts AL10 0BS. 0707

Logik. Brand name used by Dixons. See Mastercare Components, CPC

Marconiphone. See Ferguson Ltd. \_uxor. Spares available from NCS.

Marantz Audio UK Ltd., Unit 15-16, Saxon Way Industrial Estate, Moor Lane, Harmonds-worth, Middx UB7 0LW. 01-897 6633.

Mastercare Components Division, Maylands Court, Maylands Avenue, Hemel Hempstead, Herts HP2 7DE. 0442 232 000.

Matsui. Brand name used by Currys. Spares available from Mastercare Components, CPC Chas Hyde.

McLelland-Datatext Ltd., Unit 3A, Bankfield Industrial Estate, Kitson Road, Leeds LS10 1NT. 0532 455 169. Wide range of spares including Fidelity, GEC, Hitachi, Philips, Sanyo, Sharp and Sony. I rade only.

Metz. Spares available from Visionair Rentals, 5 Crown Point Parade, Crown Dale, London SE19 3NG. 01-670 2555. Trade only.

Mitsubishi Electric (UK) Ltd., Traveller's Lane, Hatfield, Herts AL10 8XB. 0707 276 100. Morphy Richards Technical Services Ltd., 6 Albany Parade, Brentford, Middx. 01-560 5331. Murphy. More recent sets fitted with Fidelity chassis. Many sets fitted with Rediffusion chassis. Model CTV3500 refer to Cathay Electronics. Older sets fitted with Rank chassis (see HRS Electronics plc.).

National, National Panasonic. See Panasonic.

NCS, Bridgemead Close, Westmead Industrial Estate, Westmead, Swindon, Wilts SN5 7YG 0793 511 636. Trade only.

NEC Home Electronics Division, NEC House, 1 Victoria Road, Acton, London W3 6UL. 01-993 8111. Trade only. See also SEME.

Neptune. Spares available from Ampmace Ltd., Falkland Close, Coventry CV4 8HQ. 0203 NEI, Network. Spares available from HRS Electronics plc. 471 241. Trade only.

Nikkai Imports Ltd., Regents Park House, 45 Byron Street, Leeds LS2 7QJ. 0532 441 640. NordMende. Spares available from Ferguson Ltd. Agents in Ireland: Reynolds Electronics Lta.

Olympus Optical Co. (UK) Ltd., 2-8 Honduras Street, London EC1Y 0TX. 01-253 2772. Trade only.

Orion. Spares for some models available from Hinari Consumer Products Ltd. or Hinari stockists.

Osaki. Brand name used by Rumbelows. Spares for Models P50G, P60G, T22P, VCR31,

VCR32, VCR33 available from Cathay Electronics. Panasonic (UK) Ltd., 300-318 Bath Road, Slough, Berks SL1 6JB. 075 382 1111. Move to Southern Industrial Estate, Bracknell due in early May. Orders can be sent via depots as follows: Bristol 0454 201 263, Hinckley 0455 632 777, Livingston 0506 419 719, Normanton 0924 895 681

Plusmaster (Electronics) Ltd., No. 26 The Craft Centre, West Wilts Trading Estate, Westbury, Philips Service, 604 Purley Way, Croydon CR9 4DR. 01-686 5414. Account holders only supplied. See also CPC, HRS, Chas Hyde, McLelland, SEME, Willow Vale, Wizard.
 Pioneer High Fidelity (GB) Ltd., 1-6 Field Way, Greenford, Middx UB6 8UN. 01-575 7199.

Plustron. Spares available from Ross Microwave Ovens, 17-23 Waterloo Road, Burslem, Wilts. 0373 826 739.

Stoke-on-Trent ST6 2EH. 0782 838 462.

Prinz. Brand name used by Dixons. See Mastercare Components.

Proline. Brand name used by Comet Radiovision.

Pye. See Philips Service.

Radionette. See Tandberg.

Rediffusion Business Electronics Ltd., TV Spares Dept., Unit 9, Mole Business Park, Randalls Road, Leatherhead, Surrey KT22 7BA. 0372 386 732.

Reynolds Electronics Ltd., Unit 20, Chestnut Road, Western Industrial Estate, Naaf Road, Dublin 12. 01-500 144.

Rigonda. Technical and Optical Equipment (London) Ltd., Zenith House, 69 Lawrence Road, Tottenham, London N15 4TG. 01-800 8088.

Rumbelows. See telephone directory for local service centre. Saba. Spares only available from Saba Gmbh, 7210 Rottweil, Konigsberger Str. 12, W Roberts Dynatron Co. Ltd., Molesey Avenue, West Molesey, Surrey KT8 ORL. 01-979 7474

Germany.

Salora. Spares available from NCS. Saisho. Brand name used by Dixons. See Mastercare Components, CPC, Chas Hyde.

Samsung Electronics (UK) Ltd., Industrial Unit A, Stafford Park 12, Telford, Shropshire TF3 3BJ. 0952 292 262. See also Chas Hyde. Agents in Ireland: Reynolds Electronics Ltd. Sanyo Marubeni (UK) Ltd., PO Box 294, Watford, Herts WD2 8JF. 0923 222 244. See also

Chas Hyde, McLelland

Schneider (UK) Ltd., Schneider House, 5 Harrowden Road, Brackmills, Northampton NN4 0BE. 0604 769 255. Seleco (UK) Ltd., Orchard House, Amersham Road, Chesham, Bucks HP5 1NE. 0494 774 366.	
<b>SEME</b> Ltd., Units 2E and 2F, Saxby Road Industrial Estate, Melton Mowbray, Leics LE13 1BS. 066 465 392. Wide range of spares including Ferguson, GEC, Hinari, Philips, Pye, Sharp. Full range stocked for Fidelity and NFC. Trade only excent for Fidelity and NFC cabinet	
parts. Sentra Consumer Products Lockslev Road Brichouse W Yorks HD6 10F 0484 714 355	TV/VCR SPARES GUIDE 1989
Sharp. Spares available from Willow Vale Electronics Ltd., 11 Arkwright Road, Reading, Berks. 0734 876 444. See also Chas Hyde, McLelland, SEME.	The following list gives spares department addresses and telephone numbers or, where these are the same, service department or head office addresses and telephone numbers.
Siemens. Spares for Model numbers beginning FF available from Mastercare Components (see above). Spares for Model numbers beginning FC available from John Langman Ltd., 5 Bryants Close, Frenchav, Bristol BS16 1PA – 0272 567 184. Spares available in the	Also included are details of major spares distributors.
Republic of Ireland from Siemens Ltd., Domestic Appliances Division, Dublin Industrial	Aiwa UK Ltd., Unit 5, Heathrow Summit Centre, Skyport Drive, West Drayton, Middx UB7
Estate, Finglas, Dublin 11 – telephone no. 302 855.	0LY. 01-897 7000.
Sinclair. Spares available from CPC Ltd.	Akai (UK) Ltd., Haslemere Heathrow Estate, 12 Silver Jubilee Way, Parkway, Hounslow,
Skantic. See Salora.	Middx TW4 6NF. 01-897 6388.
Solavox. Brand name used by Comet Radiovision Services Ltd.	Alba Radio Ltd., Unit 1A, Rippleside Commercial Estate, Ripple Road, Barking, Essex. 01-594
Sonatel. Brand name used by Morphy Richards Consumer Electronics Ltd.	5533. Early large-screen CTVs use Philips or Thorn Chassis. Trade only.
Sony (UK) Ltd., Spares Division, PO Box 58, Newbury, Berks RG13 4LX. 0635 60000. Account	Ambassador. Brand name used by Sentra Consumer Products.
holders only supplied. Spares obtainable from SES at Oldbury 021 544 8818, Dulwich 01-	Amstrad. Spares available from CPC Ltd. and Chas Hyde & Son Ltd. Reynolds Electronics
693 9622, Glasgow 041 554 2751, Leeds 0532 527 387, Staines 078 466 111. See also CPC,	Ltd. handle computers in Ireland.
Chas Hyde, McLelland. Steepletone Products Ltd., Park End Works, Croughton, Nr. Brackley, Northants NN13 5RD. 0869 810 081	Aro. Spares available from HRS Electronics plc. ASA. Spares can be ordered from Finlux. Agents in Ireland: Bagenalstown TV Centre,
Sunkyong Europe Ltd., Sunkyong House, Springfield Road, Hayes, Middx UB4 0TY. 01-561	Nuarket square, bagenalstown, co. carlow. 01-503 21501. Hade Only.
1200. Trade only.	Autovox. See Comer Radiovision Services Ltd.
Tandberg. R.D.E. Tandberg, Holly Tree House, The Green, Full Sutton, York YO4 1HW. 075	Benkson. B. Benkert Ltd., Benkson House, 26 Thames Road, Barking, Essex 1G1,1 0JA. 01-594
972 795.	7532. Trade only.
Tashiko. Brand name used by Granada. Spares available from UK Rental & Retail Ltd., Unit 37. Roman Way Industrial Estate. Preston. Lancs PR2 5BD. 0772 651 551. Trade only.	Beovision/Beocord. Bang and Olufsen UK Ltd., Eastbrook Road, Gloucester GL4 7DE. 0452 307 377. Trade only.
Tatung (UK) Ltd., Service Division, Stafford Park 10, Telford, Shropshire TF3 3AB. 0952 613 111. Trade only.	Binatone International Ltd., Binatone House, 1 Beresford Avenue, Wembley, Middx HA0 1YX. 01-903 5211. Trade only.
<b>Telefunken</b> . Paul Spring Electronics, 6 Oasthouse Way, St. Mary Cray, Orpington, Kent BR5	Blaupunkt. Robert Bosch Ltd., PO Box 98, Broadwater Park, North Orbital Road, Denham,
3PT.068 931 341. Trade only. Spares for 712/712A and earlier chassis no longer available.	Uxbridge, Middx UB9 5HJ. 0895 838 383. Trade only.
Teleton Electro (UK) Co. Ltd., 154 Great North Road, Birchwood Industrial Estate, Hatfield,	Bush Radio plc., Wharf Road, Enfield, Middx EN3 4TE. 01-805 2065. Trade only. Spares for
Herts AL9 5JN. 070 727 2841.	Rank produced CTVs (up to T24/T26 chassis) available from HRS Electronics plc.
Tensai. UK agents John Walker Ltd., 55 North Street, Thame, Oxfordshire UX9 3BN. 0844	<b>Canon</b> (UK) Ltd., Unit 4, Brent Trading Centre, North Circular Road, London NW10. 01-459
213 277.	1266.
<b>Texet.</b> The Hiro Co., Ltd., Elizabeth House, Elizabeth Street, Manchester M8 8JJ. 0618 347 432.	Cathay Electronics, 7 Blacklands Way, Abingdon Business Park, Abingdon, Oxfordshire OX14 1SU. 0235 325 555.
Thomson. TV and VCR spares available from K.M. Services Ltd., 19 Market Place, Brackley,	Cihan. Spares available from HRS Electronics plc.
Northants NN13 5AB. 0280 701 650. Trade only. For camera and microwave spares see	Classic monochrome portables. See Iskra Ltd.
Trusmaster (Electronics) Ltd.	Commodore. Spares for Commodore computers available from HRS Electronics plc.
Toshiba Technical Centre, Units 6/7, Admiralty Way, Southern Trading Centre, Camberley,	Comet Radiovision Services Ltd., Service Dept., Marshgate Industrial Estate, Marshgate,
Blackwater, Surrey GU15 3DT. 0276 694 000. Trade only. See also Chas Hyde.	Doncaster DN5, 8AF, 0302, 340, 486
Trical. Brand name used by Hinari Consumer Products Ltd.	Contec. CTVs sold by Dixons. Spares available from Mastercare Components.
Triumph. Brand name used by Currys. See Mastercare Components, CPC.	CPC Ltd., 186-200 North Road, Preston, Lancs PR1 1YP. 0772 555 034. Official spares
Vega. Technical and Optical Equipment (London) Ltd., Zenith House, 69 Lawrence Road, Tottenham, London N15 4TG. 01-800 8088.	stockists for Amstrad, Ferguson, Fidelity, GEC, Hinari, Logik, Matsui, Philips, Pye, Saisho, Sinclair, Sony and Triumph. Crown Spares available from HRS Flectronics of
Willow Vale Electronics Ltd., 11 Arkwright Road, Reading, Berks RG2 0LU. 0734 876 444. Official spares stockists for Ferguson, Fidelity, GEC, Grundig, Philips, Pye, Sharp. Other spares available.	Decca. See Tatung (UK) Ltd. and Wizard Distributors. Spares for chassis up to and including the 110/115 series available from D & S Electonic Services, Building 15, Unit 4, Stanmore
Winthronics. Spares available from Lloytron Electronics Ltd.	Deric. Rediffusion brand name. See Rediffusion Business Electronics Ltd.
Wizard Distributors, Empress Street Works, Empress Street, Manchester M16 9EN. 0618 725	Deric. Rediffusion brand name. See Rediffusion Business Electronics Ltd.
438 or 0618 480 060 Spares stocked include Decca Ferruison Eidelity. GFC Hinari	Dwektron colour sets. See Iskra Ltd.
Hitachi, ITT, Philips, Pye, Rank, Sony, Trade only.	Dynatron. Pre-1981 sets see Philips Service. Post-1981 sets see Roberts Radio Ltd.
York, Spares available from Plusmaster (Electronics) Ltd.	Ekco. See Philips Service.
Zanussi. Spares available from Seleco (UK) Ltd. See above.	Elftone Electronics Ltd., 4 Beresford Avenue, Wembley, Middx HA0 1YZ. 01-902 6222.

# ★ NEW LOWEST PRICES ★

AKAI Machine Nos.: VP77 VP88 VP7100 VP7200 VS1 VS2 VS3 VS5 VS10 VS9300 VS9500 VS9700 VS-P1 VS-P5	VHS P	NV3000 NV7000 NV7200	103 0115 2 NV332 N NV7500	IV333 NV340 NV390 NV2000 NV7800 NV7850 NV8170		HEADS Head Part No. BETA A BETA B		Price 1 + £16.95 £16.95
AMSTRAD Machine Nos.: VCR4500 VCR5200 Machine Nos.: VCR7000 VCR4500 VCR5200	VHS T VHS R	NV8200 NV8400 NV8600 NV Head Part Nos.: VEH0171 V Machine No.: NV370 NV370	EH0218	3620	VHS B VHS M	BETA D BETA E BETA T		£29.26 £34.49 £21.00
	VHS T	Head Part Nos.: VEH0171 Machine No.: NV330 NV777			VHS N	BETA W BETA X		£19.95 £31.92
FERGUSON/JVC Machine Nos.: 3292 8903 3V00 3V01 3V06 3V16 3V22 3V23 3V24 3V29 3V30 3V31 3V35 3V36 3V38 3V39 3V49	VHS A	Head Part Nos.: VEH0286 Machine No.: NV430 Head Part Nos.: VEH0174 Machine No.; NV366			VHS W VHS X	VHS VIDE VHS A VHS B VHS C	0	£14.95 £14.95 £19.95
FISHER Machine Nos.: FVH D520 D530 D620 D720 P420 P510 P520 P530 P615 P620 P622 P710 P720 P721 P722	VHS U	SHARP Head Part Nos.: DDRMU 00 Machine No.: VC581/2/3 651	1 681/2/3/	5 659 699	VHS S	VHS D VHS E VHS F VHS H		£81.76 £74.15
GEC Head Part Nos.: 5458161 5458165 Machine Nos.: 4000H 4001H 4002H Head Part Nos.: 5458282 5458413 5458415 5458992	VHS I	Head Part Nos.: DDRMU 00 Machine No.: 2C9 VC110 VC386 VC387 VC388 VC477 VC9100 VC9300 VC9400 VC	VC200 V VC481 V	C220 VC300 VC381 VC384 C482 VC930 VC970 VC3300	VHS C	VHS I VHS K VHS L VHS M		121.25 121.25 121.25 121.25 131.37 16.95
Machine Nos.: 4001H 4004H	VHS K	Head Part Nos.: DDRMU 00 Machine No.: VC7300 VC770	00 VC7750	)	VHS D	VHS N VHS P		£26.95 £14.95
HITACHI Machine Nos.: VT3000	VHS A	Head Part Nos.: DDRMU 00 Machine No.: VC6300			VHS E	VHS R VHS S VHS T		£21.00 £19.50
Head Part Nos.: 5458104 Machine Nos.: VT4000 VT4200 VT5000 VT5500	VHS H	Head Part Nos.: DDRMU 00 Machine No.: VC8300			VHS L	VHS U VHS V		£19.95 £21.95 £29.00
Head Part Nos.: 5458161 5458165 Machine Nos.: VT6500 VT7000 VT8000 VT8040 VT8100 VT8500		Head Part Nos.: DDRMU 00 Machine No.: VC2300	U1 HE14		VHS F	VHS W VHS X		£21.95 £33.59
VT8700 VT9000 VT9300 VT9500 VT9700 VT9900 Head Part Nos.: 5458282 5458413 5458415 5458992 Machine Nos.: VT11 V14 VT33 VT34 VT330 VT340 VT5030 VTP10 VTP:	VHS 1 30 VHS K	SANYO Head Part Nos.: 1430242 TC Machine No.: VTC5000 VTC Head Part Nos.: 1430242 TC	5150 VTC5	0242 T22300 5300 VTC <b>54</b> 00	BETA D	VHS Z ORIGINAL 01X0 003 2 01X0 027 0		£16.50 £31.35 £46.02
Π		Machine No.: VTC5350 VTC Head Part Nos.: 1430762 TC	5500		BETA D	01X0 033 8 01X0 040 0	25	£47.05 £48.32
Machine Nos.: VR3605 VR3033 VR3905 VR3913 VR3914 VR3935 VR3943 VR3963 VR3993 VR3975 VR3985 VR3986 VR3833	VHS A	Machine No.: VTC9300 VTC9 Head Part Nos.: 143072 T02	9455 VTC9	3500	BETA X	01X0 056 0 01X0 057 0	102	£61.55 £31.36
JVC (see also Ferguson)		Machine No.: VTC9300PS V SONY			BETA X	01X0 082 0 01X0 083 0		£46.02 £66.03
Machine Nos.: HP4000 fR2200 HR3000 HR3320 HR3330 HR3350 HR3360 HR3660 HR3750 HR3860 HR4100 HR7200 HR7600 HR7610 HRD110 HRD111 HRD120 HRD121 HRD140 HRD150		Head Part Nos.: A6762 044/ Machine No.: SL3000, 8000			BETA A	PHILIPS 310 274 44 691 200 54		POA £49.68
HRD220 HRD225	VHS A	Head Part Nos.: A6762 012/ Machine No.: SL5W, 5000 5	A, 038A, 0	055A, 129A	BETA B	691 200 98 691 201 12	i i	£62.02 £61.66
MITSUBISH! Machine No.: HS200	VHS A	Head Part Nos.: A6762 072/ Machine No.: SLC20, C30, (	A, 122A, 1	136A, 139A, 213A		691 201 66 691 201 78	i i i i i i i i i i i i i i i i i i i	£61.93 £49.96
HS7008	VH700	SLF1, F30, HF72, HF100, T2	20, <b>T</b> 30		BETA W	691 202 87		£55.37
FERGUSON/JVC           VID1         01X0-003-381         Tension band T3292/PU545           VID2         01X0-018-024         Take up idler T3292/PU477           VID3         01X0-018-025         Rewind idler assembly T3V1           VID4         01X0-018-029         Take up idler T32V0/PU442           VID5         01X0-018-729         Take up idler T3V00/PU492           VID6         01X0-040-006         Loading belt T3V29/30/PU44           VID6         01X0-040-007         Take up idler 3V29/30/PU44           VID7         01X0-040-007         Take up idler 3V29/30/PU44           VID8         01X0-040-017         Reel motor assembly 3V29/           VID8         01X0-045-009         Capston motor 3V35/36/38/3           VID10         01X0-065-016         Cass. housing Assy. 3V35/3	52 16/PU49282 80 3941-2 1 T3V23/PU 1967B 30/PU <b>5138</b> 1 39/PU55371	49042 V	2.55 5.00 6.20 6.95 0.26 4.50 2.90 27.95 27.00 27.00	AKAI           VP 77         DBK135           VP 66         DBK135           VS 1         DBK135           VS 1         DBK135           VS 2         EG           DBK135         DBK131           VS 3         EG           DBK135         DBK131           VS 3         EG           DBK135         DBK136           VS 3000         DBK103           VS 39700         DBK103           VS 39700         DBK103           VS 39700         DBK103	CD.86 CD.86 CD.86 C1.65 C1.76 C1.76 C1.76 C1.76 C1.76 C1.76 C1.76 C1.76 C1.65 C1.65 C1.65 C1.65 C1.65 C1.65 C1.65	BEL HR 2200 HR 3300 HR 3360 HR 3660 HR 3660 HR 4100 HR 7600 HR 7600 HR 7700	<b>TS</b> JVC DBK137 DBK107 DBK126 DBK103 DBK103 DBK103 DBK133 DBK139 DBK138 DBK132 DBK132 DBK138	10.68 11.65 11.65 11.65 11.65 11.65 10.86 10.86 10.86 11.76
GEC/HITACHI				FERGUSON		NATIO	NAL PANAS	DNIC \$1.76
VID11         V5577355         GEC 4100/Hitachi VT11E c;           VID12         V6413663         GEC 4000/Hitachi VT33 t/r           VID13         V6861471         GEC 4001/2/Hitachi 93/9500           VID14         V8861482         GEC 4001/2/Hitachi 93/9500           VID15         V6866971         GEC 4001/2/Hitachi 93/9500           VID16         V2423461         ET541 Tuner Unit	ewind arm ) f/f rewind ) play idler a	am	24.30 2.86 1.95 4.75 1.80 6.00	3292 DBk103 3 V 01/16 DBk103 3 V 22 DBk103 3 V 22 DBk103 3 V 24 DBk187 3 V 31/32 V107806 3 V 33/36 DBk150 3 V 33/36 DBk150 3 V 42/43/44 V107540 3 V 45/48 54 V107540	11.65 11.65 11.65 10.83 10.83 10.88 10.88 10.88 10.88 10.70 10.70	NV 330 NV 332/333 NV 336 NV 450 NV 777 NV 2000 NV 3000 NV 7000 NV 7200	DBK110 VID7521 VID7521 DBK133 DBK131 DBK109 DBK113 DBK111 DBK140	11.76 11.52 11.52 11.30 11.08 11.76 11.08 11.08 11.08
NATIONAL PANASONIC	No.		0.05	3 v 55/57 VID7540 FISHER	£0.70	NV 8600	DBK112	£1.76
VID17         VXP0329         Fast forward idler NV2000           VID18         VXP0344         Idler NV7000/7200           VID19         VX20078         Tension Band NV7000           VID20         VXP0521         Idler NV370           VID21         VXP0521         ReeI Idler NV777		PLEASE NOTE	0.85 0.85 3.50 2.65 3.40	VBS 7000         DBK146           VBS 7600         DBK105           VBS 7600         DBK105           VBS 7000         DBK105           VBS 9000         DBK10           FVHP 420         VID7532	12.56 12.34 12.34 11.76 11.62	VC 381/383 VC 385/386 VC 2300 VC 6000/6300 VC 6500/7300	SHARP DBK116 DBK116 VID7545 DBK117 DBK117	단.52 단.52 단.03 단.76 단.76
VID22 VXP0432 Pinch Roller NV333 VID23 VXP0401 Idler wheel NV333		HANDLING	3.30 1.25	GEC V 4000 H DBK129 V 4001 H DBK129	£0.68 £0.68	VC 7700/7750 VC 8300 VC 9300/9500 VC 9700	DBK118 DBK119 DBK120 DBK121	£1.76 £1.76 £1.52 £3.18
SANYO/FISHER	£	1.25 + VAT		V 4002 H DBK129 V 4100 H DBK128	£0.68 £1.24	40.9700	SONY	
VID24         4529/10800         Reel motor VTC5000/5150           VID25         1430662101201         Reel drive pulley           VID26         PR2758         Pinch roller VTC5000/5150           VID27         1430490400900         Gear idler Fisher FVH-P615           VID28         1430420400300         Heart idler Fisher FVH-P615			9.50 6.50 3.85 6.50 2.95	HITACHI VT 11-VT 86 DBK128 VT 3000 DBK128 VT 5000 DBK125 VT 6500 DBK142 VT 7000 DBK142 VT 8000 DBK144 VT 8000 DBK144 VT 8000 DBK144	£1.24 £1.65 £1.46 £0.77 £0.68 £0.68 £0.68 £0.68	SL 8000 SL 8080 SL 8500 SL 8600 SLC 5 SLC 6 SLC 7 SLC 9 SLC 9 SLJ 7	DBK115 DBK115 DBK115 DBK115 DBK100 VID7519 OBK100 DBK130	22.66 22.66 22.66 21.55 21.55 21.36 21.55 21.76
SHARP VID29 RMOTP1029 Capston motor 73/9300			33.55	VT 9300 DBK129 VT 9500 DBK129 SANYO	£0.50 £0.50	SLJ 7 SLT 7 ME SLT 7 MER	DBK100 DBK100 DBK100	£1.55 £1.55 £1.55
VID30         RMOTV1008         Reel motor VC9700           VID31         NIDL0006         Idler VC387H etc           VID32         NIDL0005         Reel idler VC3900 etc           VID33         NIDL0004         Idler wheel VC2300			18.85 1.75 1.85 2.15	VTC 5000,5150 VID7807 VTC 6000 VID7807 VTC 5300 DBK10 VTC 5400 DBK10 VTC 5500 DBK10	£1.19 £1.19 £0.70 £0.70 £1.76	V 55/57 V 66/67	TOSHIBA VID7543 VID7540	£0.91
VIDEO LAMPS/BULBS				I V1C 9350 DBK145	£0.78 £2.66 £2.66	V 7540 V 8600 V 9600 V 5250	DBK123 DBK124 VID7810 DBK148 DBK148	£0.91 £1.76 £1.76 £0.91 £7.66
VID34 LA9295 Universal lamp without sock VID35 LA9210S Universal lamp with socket			0.45 0.50	VTC M10/11/20 VID7809 VTC M21/30/31 VID7809 VTC M50 VID7809	£0.61 £0.61 £0.61	V 5250 V 5280 V 5475	DBK148 DBK122	£0.91 £2.66 £2.66 £1.76
VID36 NAT/PAN. P.C. MTG. leadless lamp VID37 SHARP 9300 Etc. lamp plus plastic shrou	d		0.50 2.53	Full list available wit	h order	TEL	EX 33849	<del>9</del> 0
NEW IN STOCK, A LARGE RANGE OF SLIN Just Supply Make, Model & Part N For an Immediate Quote. Average	lo. IF Pl	DSSIBLE		or SAE please 9" Telephone 0902 - (24hr. answering ma for Access & Barclaycar	× 4" 712083 <sup>chine</sup>	Stock For quantitie asi Orders from Nationals etc. All o	queries by post of s of 100+ per line tor special quote. Govt. Institutions, , accepted with offi joods should be del within 4 working day	only – Please Schools, icial order, ivered

REGISTERED OFFICES THE COACH HOUSE, UXTON LANE; TELFORD \* MAIL ORDER CALLERS STRICTLY BY APPOINTMENT

# Test Report: The Crotech 3133 Scope

An oscilloscope is an essential tool for servicing TV, video and similar consumer electronic equipment. Modern general-purpose scopes offer many advantages over the vintage types still in use in many workshops — higher sensitivity, greater bandwidth, improved triggering facilities and better display tubes, all at very reasonable prices. The Crotech model reviewed here is representative of modern design.

### **Basic Features**

Crotech has a range of oscilloscopes. I picked the 3133 as being best suited, in terms of price and specification, for use by the "brown goods GP" on the bench and in the field. It's manufactured in India and is a dual trace type with a bandwidth of 25MHz and a maximum sensitivity of 2mV/division. It offers Y add, invert and subtract modes as well as X-Y operation and a facility for Z (brightness) modulation.

The rectangular display tube runs at 2kV and has  $8 \times 10$  screen divisions of 1cm. The timebase range is from 200msec/div to 500nsec/div, extendable with  $\times 5$  expansion and vernier control to about 40nsec/div. Comprehensive triggering facilities are provided, including a TV sync separator, a low-pass filter and hold-off control.

Extra features include a *dual* component tester and auxiliary d.c. outputs of 5V at 1A and  $\pm 12V$  at 200mA. These can be used to power the equipment under test or other bench test equipment such as a DMM or a function or signal generator,

Further details are given in the accompanying specification — see Table 1.

### **On Test**

The scope was put to work on the bench and used for fault diagnosis, testing and setting up TV sets, VCRs and audio equipment over a long period. It proved to be easy to drive and is straightforward in operation. The control panel layout is logical, with all the controls for each section grouped together. The only slight disadvantage is the positioning of the Y1 input socket half way up the lefthand side of the fascia where its plug and lead tend to obscure the controls — I'd rather have had it at the bottom of the control panel or even on the side of the instrument. All the controls have a positive and solid feel.

Starting with the Y amplifiers, I found that these were free of drift and that the bandwidth was in excess of the specification. The lowest gain setting offers 10V/div, so that a maximum 800V peak-to-peak signal can be displayed via a 10:1 probe. This is not enough to be able to examine the waveform at the collector of a line output transistor, but then most 10:1 probes are rated at only 600V or 800V peak input anyway.

My first action was to set up the probes using the convenient front panel calibrated output. I found that no single probe-trimmer setting would give "square corners" at all settings of the Y1 gain switch. Slight variations in the factory setting of the attenuator trimmers probably accounts for this — the Y2 channel was much better in this respect. The absence of a vernier gain control is no real

disadvantage with a 1-2-5 switch sequence, and certainly avoids mistakes due to misadjustment.

The Y invert and add facilities permit rejection of common-mode signals in the Y1 and Y2 channels or, if required, a full-bandwidth "piggy-back" display at 1mV/ div sensitivity by connecting both probes to the test point and adding the waveforms. A more serious use for the Y-add mode is when investigating glitches and gate operation in logic circuits.

The range of timebase sweep speeds is well matched to the instrument's Y amplifier and display sections. A continuously variable control bridges the eighteen preset steps and a  $\times 5$  horizontal magnification switch is provided. Where the required "segment" display can be achieved by careful triggering this is preferable to horizontal expansion since it involves no brightness penalty.

The triggering facilities are comprehensive: inputs from the mains, Y1 or Y2 channels or a BNC socket on the front panel can be used, with a.c. or d.c. coupling, processing via a low-pass filter or a TV sync separator from which either the field or line rate can be selected, a negative or positive flank at variable level can be used, and there's an auto-trigger facility which ensures that you don't lose the trace with no signal input. These arrangements work well provided you take the trouble to study the instruction manual and get to know just what you are doing with the trigger controls --- so many operators poke and twiddle at random until some sort of jittery stationary display comes up on the screen! Personally I prefer external triggering. It's easily done with this scope via a third probe or clip-lead connected to the BNC front-panel mounted external trigger socket - for most TV work merely hanging the probe near the line output transformer suffices

The X-Y facility has a 1MHz horizontal amplifier bandwidth with access via the Y2 channel. It would be useful for servicing CD players, though the opportunity to try this out didn't arise during our test period. A form of X-Y display is used in the component tester feature.

The component tester works at 50Hz, applying a voltage of 8-6V r.m.s. to the device being tested and measuring the resulting current (maximum 28mA). Voltage is indicated on the screen as horizontal deflection and current as vertical deflection, so that each type of component gives a unique signature — diagonals for resistors, circles and ellipses for capacitors, knees and crank-handles for semiconductor devices and so on. Fine for quick checks, but its usefulness depends on the operator getting into the habit.

An incentive to use this mode of testing is the provision of two identical component testers, one for each trace. This permits comparison — overlay if required — of the characteristics of two devices for test, selection or matching purposes. Using this feature in two identical items of equipment or channels could provide a quick and easy way of tracking down faults, perhaps in situations where inductors are involved or where applying the operating power leads to damage. . .

The heart of an oscilloscope is its c.r.t., which virtually dictates the design of all the other sections and also determines the price and usefulness of the instrument. In

**Operating modes:** Channel 1; dual trace alternate or chopped (at 100kHz); Ch. 1 + Ch. 2; Ch. 1 - Ch. 2; X-Y operation.

Y amplifiers: A.C. or d.c. coupled. Bandwidth d.c. to 25MHz (-3dB point). 2mV to 10mV/division in 12 steps, 1-2-5 sequence. Rise time <14nsec. Accuracy  $\pm$ 3%. Input impedance 1M $\Omega$ /25pF.

**Timebase**:  $0.5 \mu$ sec/division to 0.2sec/division in 18 steps. Vernier control and  $\times 5$  magnifier. Accuracy  $\pm 5\%$ .

**Trigger:** Auto/normal; internal/mains/external; TV line or field; a.c./d.c./low-pass filter; positive- or negative-going slope; 5:1 hold-off. Sensitivity 1 div in most modes.

**X** amplifier:Input via Y2; bandwidth d.c. to 1MHz (-3dB point); other details as for Y amplifier (see above).

Probe test: 200mV peak-peak squarewave at 1kHz.

**Auxiliary outputs:** +5V (negative ground) at 1A maximum; 12-0-12V (floating) at 200mA.

**Component tester**: Dual capability. 50Hz, 8·6V r.m.s. maximum. Maximum current 28mA.


**Display:** 130mm flat-face mono-accelerator c.r.t., 2kV e.h.t., P31 phosphor, ruled 8  $\times$  10cm divisions.

**Power:** 115/220/230/240V a.c. at 48-62Hz. Consumption 40VA without auxiliary outputs loaded.

**General:** Weight 8-5kg, size 165 high  $\times$  330 wide  $\times$  395 deep mm. Instruction manual, component tester/power supply leads and two input leads with BNC plugs supplied with scope. Optional extras: switched probes  $\times 1/\times 10$ ; light hood; front panel transit cover with probe pouch; top cover, probe pocket.

this price range you get a mono-accelerator tube working at 2kV e.h.t. Its display is adequate for most TV, audio and VCR work, but the limited brightness available can make it difficult to see short duty-cycle events like a magnified portion of a video head sweep, a field sync pulse train or a horizontal segment of a picture such as the multiburst or colour-bar features of a test pattern. Loss of brightness in these and similar situations can be minimised by (a) using a light hood, (b) operating in the single-beam mode, and (c) avoiding X-expansion by careful use of the trigger and hold-off controls. For better performance in this respect you have to buy a more expensive scope with a higher e.h.t.

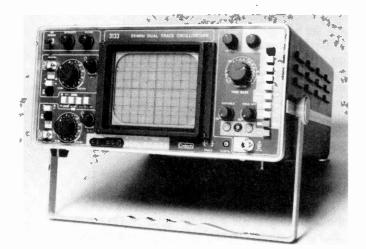The tube fitted in the review model didn't defocus at any setting of the brightness control, which is a better



The Crotech 3133 25MHz dual-trace oscilloscope. TELEVISION APRIL 1989

performance than with many scopes we've tried out. The brightness reserve is not very high though, and I found that the brightness control was fully advanced throughout my tests of the instrument.

The graticule is not integral with the tube's faceplate. You thus get a degree of parallax error when taking readings. Maintaining a large waveform display keeps this to a minimum. The 0/10/90/100 per cent markers on the graticule are useful in experimental, testing and design work for measuring time-constants and rise times.

The 5V/1A and 12-0-12V/200mA supplies are available at miniature sockets at the bottom of the front panel. Handy connecting leads, terminated with colour-coded mini-croc-clips, are supplied. I found that both voltage sources were accurate and well stabilised, and capable of withstanding a sustained dead short cruelly put on to test the machine's defences. These auxiliary supplies are a useful and convenient source of power. Well worth having.

The 3133 is a big oscilloscope, well made and attractive in appearance. There's very little plastic in its construction, which is unusual these days. Inside the aluminium case I found the circuit beautifully laid out on four main glassfibre PCBs, with two smaller sub-boards. The e.h.t. generator sector is in a separate screened compartment. The switches and potentiometers appear to be sturdy and of good quality — this fact along with the beefy, coolrunning mains transformer and the generally sturdy construction of the instrument suggest that if bought now it will carry on well into the twenty first century. The component reference numbers (and in some cases the values) are clearly marked on the PCBs — more than can be said for many TV sets and audio equipment.

### User's Manual

The user's manual provides full circuit diagrams and descriptions, board layouts, parts lists and alignment instructions. Most of the parts used are readily available so that service and repair, should it ever be required, should present little difficulty. Also supplied with the instrument is a little book entitled "Getting the best from your scope". This supplements the operating instructions in the user's manual. Very good.

### Conclusion

In conclusion this is a good oscilloscope, well made and with a performance which I would describe as being competitive rather than spectacular. It's main competition comes from the almost identically priced Hameg HM203-6. Buying the Crotech model gives you an extra 5MHz of bandwidth in each channel, the dual component test facility and the auxiliary d.c. outputs. You lose the vernier Y controls and the internal c.r.t. graticule. Certainly I feel that the Crotech 3133 is good value for money, and I would confidently recommend it to anyone looking for a good general-purpose oscilloscope. For use in the field I feel that the front panel transit cover (an optional accessory) is essential to protect the knobs and tube bezel. For viewing short duty-cycle traces the light hood, also an optional accessory, is really a necessity.

### Availability and Price

The scope is available from Crotech Instruments Ltd., 2 Stephenson Road, St. Ives, Huntingdon, Cambs PE17 4WJ (0480 301 818) at £319 plus VAT.

# VCR Clinic

### Philips VR6468

At switch on the cassette carriage moved in and out as usual but the clock display was out and none of the keyboard controls worked. The +13a supply was missing at the keyboard panel as R3509 ( $15\Omega$ ) on panel P607 was open-circuit. **P.B.** 

### Grundig VS400

The customer complained that when a cassette was ejected a loop of tape was sometimes left hanging out of it. The only way in which I could make the fault occur was to press stop with the machine in rewind search. The tape then wasn't drawn back into the cassette. Slight readjustment of the mecha state switch was required. **P.B.** 

### Ferguson 3V31

The trouble with this machine was field bounce in the still frame mode, the vertical pulse control on the front panel having no effect. A dry-joint was eventually found at C75 on the servo board. **P.B.** 

### Philips VR6462

If play is selected without a cassette inserted these machines usually provide the test pattern. This one produced the test pattern even with a cassette in! The test signal is enabled by the TPI signal on Bus C: it was high all the time because transistor 7508 was open-circuit. **P.B.** 

### Grundig VS220

For intermittent faults such as the display goes haywire or the mechanism does odd things check the ripple on the +12Vd supply. If it's excessive either C437 or C436 has probably dried up. **P.B.** 

### Ferguson 3V65

Playback of a test tape was good but there was a smeary E-E picture. Replacing the luminance module IC101 put this right.

### **Orion VHL3**

There was no sound muting in the search mode. The DTC124F digital transistor Q1025 was faulty. A.S.

### Hinari VXL5

This machine would operate for about twenty seconds in play or record then shut down. The take-up reel sensor was faulty. Here's a tip: switch to counter, press play and observe the erratic and irregular number changes. **A.S.** 

### **Amstrad TVR3**

Here's an interesting one we've had with several of these new combi-units (TV plus VCR). The remote control handset operates the VCR functions but not the TV ones. The fault lies within the VCR section, associated with the remote control receiver. Ribbon cable CL8 to the front of the tuned circuit can should have six leads but a five-wire

### Reports from Philip Blundell, Eng. Tech., Alan Shaw, Paul Hardy, Eugene Trundle, Ian Bowden, Nick Beer and B. Ross

cable is fitted, leaving a vacant hole at either end of the ribbon. Fitting a short length of wire cures the problem. So much for quality control . . . **A.S.** 

### Hitachi VT17

The heads had worn out and were replaced. After doing this I was left with a problem: the top half of the picture was fine but the lower half was noisy and there was a definite division between the two. The cause of the fault was traced to the relay on the video drum PCB. It shorts out the trick mode heads during normal playback but was not doing its job properly. A replacement provided an effective cure. **P.H.** 

### Philips VR6542

The problem with this machine was that recordings had intermittent colour. It was to some extent signal-dependent – a weaker signal was more prone to cause the symptom. Changing IC501 on the Y/C panel made no difference and we eventually found that the 627kHz signal was off frequency by about 70kHz. Resetting this produced reliable operation.

We've had several of these machines that don't seem to like E240 cassettes – the tape commits suicide on the mechanism though there doesn't seem to be any mechanical fault. Does anyone have any ideas about this? **P.H.** 

### JVC HRD320

The problem with this brand new machine, straight out of the box, was that three of its buttons were inoperative – set–, set+ and Ch. set. On investigation we found that D11 on the timer/display board had been fitted back-to-front. It's part of the key-scan matrix. The diode was undamaged and fitting it the correct way round restored normal operation of all the buttons. The same symptoms would arise with other makes and models fitted with this type of timer/display board. E.T.

### Sony CCD-V30

The viewfinder tube in this camcorder displayed a picture locked to a multiple of the line rate. This occurred with both camera and playback pictures. Operation through a TV set via the r.f. modulator showed that all was well within the basic camcorder circuitry, so we concentrated on the electronic viewfinder. The line hold control RV952 was responsible for the problem, due to poor contact at the riveted end of its carbon track – flexing and twisting this little preset could restore a normal picture display. It's strange to recall that the symptom and the root cause of the fault were common with the TV sets of the sixties! E.T.

### JVC HRD110/120/Ferguson 3V35 etc

A common problem with this range of machines is that the retaining studs on cam gear 1 (PQ30028) of the cassette loading mechanism break. This allows the associated slide gears to escape, producing symptoms such as no front loading, no eject, loading system jammed etc. The only long-term cure is to replace gear 1, but a temporary cure (while awaiting spares?) can be achieved by refitting the stud using a small self-tapping screw through the back of gear 1. The sort that RS Components used to call an "8BA binder" will work. This assumes of course that you can find the broken stump of the plastic stud!

### Panasonic NV370

The user's description of the fault with this machine was "no functions". At switch-on an eerie "heartbeat" noise came from within and continued until the machine switched itself off a few moments later: it was caused by the capstan motor shunting back and forth. Meanwhile eject wouldn't work.

This effect is usually due to a missing 5V rail, Q501 on the head drum assembly being open-circuit. The 5V line was intact this time, but the 12V line was missing. We quickly traced the cause of this to an open-circuit safety resistor (R1101) in the unregulated 12V supply. It appeared to have failed for its own internal reasons. E.T.

### Panasonic NV-G45

This machine was faulty when taken from the box. The playback picture would come and go, due to drum speed variations that could also be heard. When we turned the machine on its side to remove the bottom cover the fault cleared. While looking for a loose plug/socket connection we removed the drum cylinder and found a crack almost half way across the double-sided stator panel, between the socket and where the panel enters the drum unit. **I.B.** 

### Panasonic NV-M5

This camcorder was stuck in the camera mode. Normally when the clear cover over the VTR controls is slid up to uncover them a small microswitch (SW6313) operates. It closes for camera, opens for the VTR mode, but something was wrong with the switching. When closed (camera mode) SW6313 connects the base of QR6009, a UN2113 pnp transistor with internal bias resistors, to chassis. As a result positive key-scan pulses pass to the control chip IC6001. SW6313 should be open and QR6009 off in the VTR mode. Even with QR6009's base disconnected however the pulses were getting through as the transistor had an emitter-to-collector leak. I.B.

### Panasonic NV788

The complaint was of a poor picture. On test however the picture was all right except in the still mode, when almost half the picture was lost in noise. Having seen this problem with other machines I checked the playback tension, suspecting that this was low (10g-cm instead of 30g-cm). The cassette carriage assembly was removed, a cassette was put in it and another one was held in the machine. A check on the back tension then proved that it was correct. I tried again with the cassette carriage refitted and spotted the cause of the problem – the back-tension post arm, which runs against the tape, moved too far to the left and rested against part of the carriage assembly. With the assembly removed the arm moved far enough to give the correct tension. The cure was to move the fixed end of the brake band to pull the arm further to the right when running then adjust the tension spring for correct back tension. This problem could very easily arise if the

brake band is replaced and the position of the back tension arm, when playing a tape, isn't checked before refitting the carriage. I.B.

### Panasonic NV-G40

We've had several of these machines with faulty video heads when new, but the complaint with this one was very grainy r.f. loop-through. A check on the unswitched 12V supply to the r.f. amplifier showed that this was low at about 5.2V. Further checks indicated that the rail was not being loaded excessively so attention was directed to the power supply, which is usually very reliable. Regulator transistor Q1004 (2SD1330) was soon found to be opencircuit. **N.B.** 

### Sony SL-F1

The complaint with this portable machine was that it wouldn't play. We found that the pinch press lever had become disengaged from the pinch solenoid lever. When a new press lever had been fitted - the original one had a worn plastic arm - the machine played for about twothree seconds then cut out. We then found that the takeup torque was low. Since fast forward operation was perfect it seemed that the cause of the fault was servo rather than motor trouble. While checking the waveforms in the reel servo I found the rather unlikely cause of the fault - a speck of solder was bridging two contacts on adjacent print lands. At first sight it looked like a single length of track, but the short effectively joined pin 1 of IC201 (supply FG) to pin 29 of IC601 (syscon-2). Fortunately no lasting damage had been done. The short must have been present from new and it's remarkable that it had only now showed up. Our customer accepted the estimate but refused a second one for the drum surfaces causing the usual rewind trouble - apparently he rewinds his tapes in another machine! N.B.

### Grundig 2 $\times$ 4 Super

The customer brought this machine along in a great hurry as he wanted to record a programme. He said it wouldn't load a cassette. The cause was quickly found – the cassette-in switch CL wasn't making. As a temporary measure to enable the customer to make his recording we shorted the switch out by linking pins L1-6 and 7 on the switch board. This restored normal operations including unloading. To load it was necessary to insert a cassette then press "tape", after which the machine would load. Note that if the CL-closed signal is not present no functions are available (play, wind, etc.) even with a loaded tape. **B.R.** 

### Philips VR2021

This machine would thread up and then unthread about two seconds later. The head and reels turned during this period, as they should, but the head speed was slow. A check on the voltages around the servo and motor drive amplifier circuits showed that they were incorrect, the cause being lack of signals from the head pulse optocoupler circuit on board P61. This was in turn due to the LED on the winding spool optocoupler unit P60 being open-circuit. The LEDs for P64 (tape tension optocoupler), P60 and P61 are connected in series via a limiting resistor from the 12V line. So there were no pulses to the head servo circuit. **B.R.** 

# A Look at Operational Amplifiers

### Part 1

The operational amplifier has been with us for many years but until recently had generally not figured significantly in the TV/video field. The audio and servo sections of VCRs and CD players lend themselves to the use of operational amplifiers however so perhaps it's time we gave them a closer look.

The first use of operational amplifiers was in analogue computers – a long time ago! They were used to perform arithmetical *operations*, for example the addition and subtraction of voltages representing numerical values. While this original need for the operational amplifier has largely disappeared, the basic concept nevertheless provides an extremely useful building block for circuit design in a multitude of applications.

### **Basic Op Amp Features**

Fig. 1 shows the circuit symbol for an operational amplifier. In its simplest form it consists of an amplifier with two inputs and one output. The inputs are referred to as inverting and non-inverting: the inverting one is identified by the minus symbol and the non-inverting one by the plus symbol – these are not power supply connections! A positive voltage applied to the non-inverting input causes the output to move positively while a positive voltage applied to the inverting input moves the output in the negative-going direction. In addition to its inputs and outputs the operational amplifier needs a power supply. Very often this consists of both positive and negative voltages, balanced about earth (0V).

The d.c. gain of a typical operational amplifier chip is generally enormous. A voltage gain of half a million is common today, and it's this fact that enables us to use the amplifier to carry out neat and clever functions, with just a few peripheral components. Because the gain is so large it's generally expressed in dBs. This is known as the "open-loop gain". Normally the loop is closed, using passive components, and we shall soon see that the performance of such a circuit is defined almost entirely by the passive components. Consequently the design can be made totally predictable and repeatable. Ideal, for example, for use in mass-produced servo systems.

Let's get down to business then and take a further look at the operational amplifier shown in Fig. 1. Say it's openloop gain is 500,000, i.e. 114dB. Thus a change of  $+2\mu V$ at the non-inverting input, relative to the inverting input, will produce a +1V change at the output. Conversely a change of  $+2\mu V$  at the inverting input, relative to the non-inverting input, will produce a -1V change at the output. Having made this basic point, we must consider two further points.

First, if both inputs move by the same amount in the same direction the changes subtract from one another. Thus the output doesn't change. Putting this another way we can state that the output changes only when there's a difference change between the two input voltages. This ability of the operational amplifier to ignore changes in the same direction is called common-mode rejection. It's important and we'll return to it later.

Secondly if the inputs move in opposite directions the output moves by an amount that's proportional to the sum

of the changes of the input voltages, i.e. the total potential difference between the two input terminals. We'll elaborate on this later.

### Basic Circuits

We'll next consider some basic operational amplifier uses.

The inverting amplifier is shown in Fig. 2. In addition to the operational amplifier there are two resistors, R1 and R2. Remember that the typical operational amplifier requires a difference of only  $2\mu V$  between the two inputs to produce a 1V change at the output. This is the key to what happens. Let's take a simple, practical example. Say R1 is 1k $\Omega$  and R2 is 5k $\Omega$ . Positive and negative 10V supplies are connected to the chip.

Say we connect +1V to the input. The immediate effect of this is that the inverting input tries to move away from 0V (the non-inverting input) via the potential divider R1-R2. The output moves negatively, applying sufficient negative-going voltage to R2 to move the inverting input back towards 0V (within a few microvolts!).

The situation is thus as follows. The inverting and noninverting inputs are very close together in terms of voltage, so close in fact that since the non-inverting input is at 0V the inverting input is at virtually 0V – we call it a virtual earth. This means that R1 has 1V at one end and 0V at the other. As its value is  $1k\Omega$ , the current flowing through it is 1mA. No current is flowing into the operational amplifier's inverting input, so the current flowing through R1 also flows through R2. Since R2 is  $5k\Omega$ , with 1mA flowing through it the voltage developed across R2 is 5V. The sense of current flow means that the operational amplifier's output stands at -5V. It can't do anything else!

What do we know from this? Simply that the gain of the circuit with the closed-loop feedback as specified is -R2/R1. We put +1V in and -5V comes out. The gain is -5 (-5,000/1,000 = -5). This gain is defined entirely by the values of R1 and R2: the more precise their values, the more precisely the gain of the circuit is defined.

Since the input resistor R1 "sees" a virtual earth, the circuit's input impedance is simply R1. The output imped-

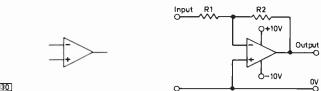




Fig. 1 (left): The operational amplifier circuit symbol. Fig. 2 (right): The basic inverting amplifier circuit.

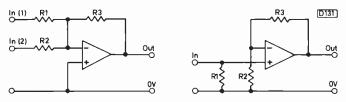


Fig. 3 (left): The summing and inverting amplifier. Fig. 4 (right): The non-inverting amplifier circuit.

ance is low: a few ohms is typical, but the amplifier won't have the capability of high-current drive (more on this later).

The second circuit, Fig. 3, is a summing and inverting amplifier. There are two input resistors R1 and R2 and this time the feedback resistor is R3. The junction of the three resistors is the virtual earth point, and the arithmetical sum of the currents here is zero. Seen from input one the gain is -R3/R1 while from input two it's -R3/R2. Note that since each input resistor is connected to virtual earth, the input resistors are "unaware" of each other and there's no cross-coupling between the inputs.

If we call the current through R1 I1, that through R2 I2 and that through R3 I3, then I1 + I2 = I3. That is,

(V1in/R1) + (V2in/R2) = (-Vout/R3).

If we make R1, R2 and R3 equal, then V1in + V2in = -Vout, i.e. the output is the sum of the input voltages with the sign reversed.

By manipulating the values of the resistors we get different input to gain ratios and overall amplification as required. Use of a ladder of input resistors provides the basis of a digital-to-analogue converter.

Having dealt with the basic inverting operational amplifier configuration I hope you'll feel more at home with the principles involved. We can summarise the action of a feedback-controlled operational amplifier by stating two important rules:

Rule 1: The output of a feedback-controlled operational amplifier always moves to try to reduce the voltage between its two inputs to zero.

Rule 2: For most practical purposes we can say that the inputs draw no current.

Fig. 4 shows the basic non-inverting operational amplifier circuit. The input is applied to the non-inverting input, which has a high impedance – determined by the value of R1. The gain is determined by the 'amount of feedback, and is inversely proportional to the feedback attenuator network R3, R2. The amount of potting down is R2/(R2 + R3). Thus the gain is (R2 + R3)/R2.

In the special case where R3 is zero and R2 is not fitted we have a voltage-follower with a gain of one. It's like an up-market emitter-follower: it can drive well in both directions and has no offset of 0.6V between the input and output – a very useful configuration which we'll come across again later.

### **Quoted Characteristics**

From what we've said so far you'll see that the basic design of operational-amplifier circuits can be carried out by means of very simple calculations. There are pitfalls to watch out for however. Having covered the fundamentals we can move on to consider the operational-amplifier characteristics that have to be taken into account when the device is used in more demanding applications. We shall also see why, although operational amplifiers are great for use in servo, audio and power supply applications, you won't find them used much in video circuits. We must next define some of the basic characteristics.

(1) Open-loop gain. This has already been mentioned: it's the d.c. gain with no feedback applied.

(2) Input offset voltage. However hard the manufacturer pursues this ideal, the input circuits within an operational-amplifier chip are never identical. The input offset voltage

is the difference in input voltages (at the inverting and non-inverting inputs) required to bring the output to zero. Some operational amplifiers have the facility to trim the input offset voltage to zero externally, using a potentiometer connected to pins set aside for this purpose. With a good operational amplifier the input offset voltage can be of the order of microvolts: for the old 741 type it can be up to 6mV.

(3) Gain-bandwidth product. Operational amplifier data sheets quote a gain-bandwidth product figure. Up to now I've quoted the open-loop d.c. gain. The gain falls as the frequency rises however. The gain-bandwidth product refers to the closed- as well as the open-loop gain. In other words it applies whatever gain we intend. It works like this. If we use an operational amplifier whose gain-bandwidth product is 1MHz and design the circuit for a gain of 100, the gain will fall off significantly as the frequency approaches 10kHz. That is, gain (100) × bandwidth (10kHz) = the gain-bandwidth product (100 × 10,000 = 1MHz).

If you are restricted to the use of this particular operational amplifier with its 1MHz gain-bandwidth product and need to maintain the gain right up to 10kHz you can use two amplifiers in cascade, each providing a gain of ten. This will give you a useful bandwidth up to 100kHz while still maintaining the overall gain of 100.

(4) Slew rate. This is the rate at which an operational amplifier's output can change. It's usually quoted in volts/ microsecond. What it means is that as the frequency rises so the maximum attainable peak-to-peak output voltage drops off. From the point where the slew rate limiting starts to "bite", the maximum amplitude falls as the reciprocal of frequency.

(5) Phase margin. This is a more difficult characteristic, but it's as well to be aware of it. A typical operational amplifier circuit's open-loop gain rolls off in the same manner as the response provided by a simple *RC* filter, i.e. it follows a 6dB/octave curve. This means that every time the frequency is doubled the gain is halved. It results in a 90° lagging phase shift to begin with, increasing up to  $160^{\circ}$  as the frequency approaches the gain-bandwidth figure (that is, the gain is approaching one). The phase margin is the difference between this phase shift and  $180^{\circ}$ , where the feedback becomes positive. Generally speaking this does not cause problems at low frequencies, but it can be a real pain at higher (e.g. video) frequencies, when the operational amplifier can "hoot", i.e. produce parasitic oscillations.

I recall designing a 2MHz active low-pass filter using operational amplifiers. It produced the desired 18dB/ octave roll-off, but also produced a low-amplitude hoot at 20MHz. All attempts to manipulate the operational amplifier circuit to get rid of the hoot mucked up the frequency response. In desparation I finally used a pisection passive filter to give an 18dB/octave roll-off above 5MHz. This wiped out the hoot as far as the outside world was concerned, but of course I knew what was still going on inside the unit! Not one of my proudest moments – I don't talk about it much any more, despite the fact that the unit has continued to provide sterling service for many years.

So much then for the basic characteristics of operational amplifiers. Next month we'll look at some more classic operational-amplifier circuits.

# Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £2 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

### SHARP C2002

This set is reluctant to start up from standby. It's more willing to start in the evening when the room temperature is higher. Once running the set will continue to operate unless switched off by remote control then on again.

We suggest you check the following components for being high-resistance or open-circuit and replace as necessary: R616 1.5M $\Omega$ , R717 390k $\Omega$ , R709 and R710 both 68k $\Omega$  and C715 10 $\mu$ F, 100V. Before you do this check thoroughly for dry-joints around IC701, T701 and T602.

### FIDELITY CTV1404R

There are two problems with this set. First, when one channel has been tuned to a particular station all the other channels are tuned to the same station, and the channel isn't stored. The M491B and TDA4500 chips have been replaced but the fault remains. When the channel is changed via the handset the same picture is displayed though the channel indicator will run through numbers 1-8. Secondly there's cramping at the bottom of the picture. All capacitors in the vicinity of the TDA3651 field output chip have been replaced.

For the first problem we suggest that you check, preferably by substitution, the 500kHz resonator connected to pins 7 and 8 of the control chip IC201. Also make sure that the 5V supply (pin 9) is present, correct and free from ripple and hash. The TDA3651 chip could well be responsible for the second problem, but before condemning it check the 25V supply at pin 9. It's important that this line is well decoupled.

### HITACHI CPT2228

The remote control system suffers from reduced range and intermittent reception. A check with another receiver has proved that the handset is in order and the  $\mu$ PC1373H IR preamplifier chip has been changed.

First check that the infra-red receiving window/filter is clean and hasn't become obscured with age – try operation "naked" to prove this. If necessary check C1802 and C1804, then the SFH205 photodiode – the latter by substitution. If the remote-control a.g.c. is operating correctly there should be little change in the pulse amplitude at SC1803 with the handset at a distance of up to 15 feet or so.

### PANASONIC NV2000

Forward and reverse rewind are all right but when the play switch is pressed the cassette begins to load then after a few seconds the machine stops loading. The belts have been changed but the problem persists. It's almost certain that the mechacon section is not receiving an afterload signal from the deck. This may be because loading is not being completed for some mechanical reason (though the belts you have changed are the most common cause of this) or because the mode selector switch S6551 is faulty or incorrectly positioned. Close examination should reveal which of these is causing the trouble. Instructions for mode selector switch adjustment are given in the full manual.

### FERGUSON TX10 CHASSIS

There's a very faint vertical white line with a kink in the lower half – the kink tends to move up and down – seven inches from the left-hand side of the screen. It can hardly be seen except on darker scenes, but annoys the customer. I've tried moving the cables etc.

Ensure that the triple RGB lead to the c.r.t. base panel is correctly folded and dressed and not dangling near the timebase or chopper sections. If this is o.k., suspect that one of the semiconductor devices, a diode or transistor, in the chopper circuit is faulty and radiating. Check this by substitution, starting with the chopper transistor TR701 then D703.

### SHARP VC378

Failure of the Digitron display led us to check the power supply which appears to be in order apart from the fact that the a.c. output, which is specified as 7.5V, reads only 2.2V when measured with an Avo meter. A scope check shows a good trace with about 6.2V p-p at a frequency of around 200kHz. Are these readings normal and how would 7.5V a.c. have been measured? The negative component fed to the Digitron circuit is 16.5V d.c., which appears to be about right with the main negative line at 22V.

The 7.5V figure is probably the r.m.s. a.c. voltage across terminals ER9 and ER10: it feeds the display tube's heater. Since the -22V supply is about correct, the oscillator is clearly running all right. Check that the display segments are being pulsed by the display driver chip. If so the fluorescent panel itself is suspect – it may have lost its vacuum.

### SONY KV2022UB

This set is working well apart from the fact that there are four teletext lines across the top of the screen and also four faint white lines across the centre of the screen. None of these lines are present at switch on. They appear after about five minutes then remain.

The problem is probably due to ageing electrolytic capacitors. Check, preferably by substitution, those associated with the field output stage - C563, C566, C587 etc. Also if necessary check D575.

### SANYO VTC9300

This machine will not run. When switched on, only the eject and stop switch levers will go the full length of travel. When moved to the right with a small screwdriver the bar inside the machine to the front of the video heads will allow the rewind, fast forward and play buttons to be depressed to maximum. The electronics appear to be in order.

First ensure that the stabilised 12V line is exactly correct. If not, replace the regulator transistor Q702 with a TIP41 type and adjust VR701 for 12V at C709. If the machine appears to work normally when the latching bar is overridden it's likely that the afterload switch (the large microswitch on the upper deck surface) has failed or that the end-sensor oscillator has stopped – check with a scope, then for power to the CX141 chip on the syscon panel. A further possibility is that the machine thinks it has dew (low at collector of Q807). Check if necessary that the solenoid switching transistors Q801/2 are not leaky.



# 316

Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

TV and video servicing can be a complex business these days. Various levels of skill and expertise are required, depending on the nature of the fault and the age and design of the equipment. At busy times – which is most of the time recently! – the simpler jobs are passed on to those who are less experienced and whose normal job is not full-time bench servicing, but who can achieve much under the guidance of a senior engineer.

An early Ferguson TX9 colour receiver (PC1001 main panel) looked a likely candidate for this treatment. The fault was described as "set dead", and we assumed that the internal mains fuse had blown. So John took off the back cover and checked FS1. It was intact, and so was the fuse in the mains plug. The set was next plugged into a safety-isolated socket and switched on. There was a slight buzz from the degaussing system followed by silence and no picture. John settled down with his meter and the set's circuit diagram.

He found that the output from the mains bridge rectifier W62-W65 measured above 200V – there's no reservoir capacitor here as the bridge supplies a regulating thyristor. This voltage was also present at the thyristor's anode. Switching to the meter's d.c. range John found, rather to his surprise, that some 130V was present at the cathode of the thyristor and that over 120V was present at R197, on the other side of the reservoir inductor. In short, the power supply was working correctly.

Further meter checks quickly established that the 115V h.t. potential was present at the collectors of the line driver transistor VT67 and the line output transistor VT68. There was no voltage at their bases however, so John concluded that the basic problem was lack of line drive. Sure enough a borrowed oscilloscope showed a complete absence of line drive pulses at the base of VT68, at the line driver transformer T2 and at the base of VT67. This led him back through the coupling capacitor C173 to pin 3 of the TDA9503 sync/line generator chip IC54. He found zero voltage at this pin and very soon found that there was a total absence of voltage at all the other pins as well.

The circuit diagram for the PC1001 version of the TX9 chassis is very helpful in using brightly coloured lines and symbols to indicate the source and routing of the various

supply lines. From this John saw that the operating power for the TDA9503 chip is provided by the 12V regulator IC56. This receives an input of 15V from rectifier diode W95, which is fed from a winding on the line output transformer. Of the various possibilities here, W95 and IC56 were picked out for the initial checks. An ohmmeter test proved that the diode was in order and the regulator was checked by substituting a known good one from the stores.

A commendable effort, but fruitless since the set still didn't work. The h.t. was present, but there were no 15V and 12V supplies. As a further step John checked the continuity of the winding that feeds W95, and also checked its reservoir capacitor C193. He then consulted the others in the workshop. Having poured out his troubles, explaining matters with the aid of the circuit diagram, he was given a short description of the operation of the circuit in the line timebase area. As a result he soon found the cause of the trouble. What had he overlooked? See next month for the solution.

### ANSWER TO TEST CASE 315 – page 360 last month –

Before the problem was finally solved, three engineers had given their attention to the faulty Toshiba V66 VCR described last month! The sort of picture jitter it produced is symptomatic of very short-term changes in the head scanning velocity, but the fact that it was more severe towards the bottom of picture suggested that the tape's movement became progressively rougher towards the exit side of the drum at the right.

This was the clue that led Sage to examine the exit guide. It consists of a nylon sleeve which spins freely on a highly machined shaft. When Sage went in with his little screwdriver he "stuck" this rotating sleeve, completely altering the jitter effect on the picture. When he removed the guide he found that the nylon sleeve didn't run smoothly on its shaft. As an experiment, one tiny drop of oil was introduced into the guide. After cleaning the outer surface of the sleeve the guide was then replaced in the machine. When a scrap tape was run the picture was seen to have rigid, straight verticals.

While this proved the point, there was the possibility of tape polution if the treated guide was left in the machine. A new guide assembly was ordered and fitted before the machine went home to Crowfield.



Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £18, overseas (surface mail) £21 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

# SIMPLY THE WHOLESALE SUPPLIER OF THE EX-RENTAL T.V.'S & VIDEO RECORDERS IN THE UNITED KINGDOM


# RING OUR LOCAL MANAGER FOR DETAILS

### **AVONMOUTH** FARNBOROUGH WAREHOUSE WAREHOUSE MAJOR **KARLA HEATH CLIFF PARSONS** REGIONAL B B 0252 540814 0272 235093 7/8 KINGSGROVE INDUSTRIAL EST. WAREHOUSES **5 PORTVIEW ROAD INVINCIBLE ROAD** AVONMOUTH FARNBOROUGH YOUR SERVICE HANTS, GU14 70S **BRISTOL BS11 7LQ** LINWOOD SUNDERLAND AINTREE WAREHOUSE WAREHOUSE WAREHOUSE **BRIAN CADE** IAN McCLELLAND IAN DORAN B 雷 雷 091 523 5554 051 530 1285 0505 29284 1a LYON ROAD 9A/B UNIT 2. RACECOURSE IND. EST. LINWOOD INDUSTRIAL ESTATE 94 CARRMERE ROAD **ORMSKIRK ROAD** LINWOOD LEECHMERE INDUSTRIAL EST. AINTREE **RENFREWSHIRE PA3 3BQ** SUNDERLAND SR2 9TE LIVERPOOL L9 5AL



AA117 AA119 AA12 AA119 AA12 AA119 AA12 AA119 AA12 AA119 AA120 AA119 BA118 BA14
9 9 9 9 9 9 9 9 9 9 9 9 9 9
BD1777 BD1799 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD1791 BD2252 BD1791 BD2252 BD2233 BD2233 BD2233 BD2233 BD2233 BD2233 BD2235 BD2235 BD2235 BD2235 BD2235 BD2235 BD2235 BD2235 BD2235 BD22434 BD2245 BD22434 BD2245 BD2249 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2312 BD2345
BF4479           BF4479           BF4493           BF4493           BF4493           BF4943           BF493           BF4943           BF493           BF493           BF493           BF595           BF595           BF595           BF595           BF595           BF7615           BF7863           BF7863           BF7863           BF7863           BF7864           BF7863           BF7870           BF7863           BF7870           BF7870           BF7870           BF7871           BF7872           BF7873           BF7873           BF7873           BF7873           BF7873           BF7873           BF7874           BF7875           BF7874           BF7874           BF7875           BF7874           BF7974           BF7974           BF7974           BF7974           BF7974           BF7974
30p #8p #2 #2 #2 #2 #2 #2 #2 #2 #2 #2 #2 #2 #2
M.25011 M.23051 M.23053 M.30000 M.23053 M.3000 M.250512 M.25015 M.2501
2N.1132 2N.1613 2N.1613 2N.1613 2N.2015 2N.52215 2N.5
30p 332p 322p 322p 36p 6 6p 77p 4 4p 4 4p 9 90p 10p 11p 112p 13p 13p 70p 10p 11p 112p 13p 70p
Jan Sao           Jan Sao <td< td=""></td<>
A NGE 20 ANGE 20 AN
AN-316 AN-316 AN-3181 AN-3300 AN-322 AN-320 AN-322 AN-3502 AN-35712 AN-3572 AN-5730 AN-5732 AN-5730 AN-5732 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5730 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-5320 AN-7116 AN-7716 AN
4500 + 4000 + 20
HA-1125 HA-1125 HA-1125 HA-1137 HA-1367 HA-138
✓ 135; 380, p 110, p 110, p 110, p 110, p 110, p 110, p 100, p 380, p 380, p 380, p 380, p 380, p 180, p 380,
LA 7027 LA 7027 LA 7032 LA 7032 LA 7032 LA 7032 LA 7046 LA 7046 LA 7047 LA 7048 LA 7051 LA 7051 LA 7051 LA 7051 LA 7221 LA 7221 LA 7221 LA 7220 LA 7250 LA 7506 LA 7506 LA 7506 LA 7506 LA 7506 LA 7508 LA
20500 p 20800 p 28800
STK-4181 STK-4311 STK-4332 STK-4352 STK-4352 STK-4352 STK-4352 STK-4352 STK-4733 STK-4803 STK-4813 STK-4833 STK-4843 STK-4853 STK-4893
1100p 1300p 1400p 1300p 1400p 1577b 15
STK. 6962 STK. 7216 STK. 7216 STK. 7216 STK. 7216 STK. 7216 STK. 7309 STK. 7309 STK. 7404 STK. 7404 STK. 7405 STK. 7406 STK. 7405 STK. 7406 STK. 7406 STK. 7406 STK. 7406 STK. 7406 STK. 7406 STK. 7406 STR. 7407 STR. 7
2900 + 29
UPC-1018 UPC-1021 UPC-1023 UPC-1025 UPC-1026 UPC-1026 UPC-1026 UPC-1026 UPC-1026 UPC-1026 UPC-1107 UPC-1182 UPC-1182 UPC-1182 UPC-1182 UPC-1182 UPC-1182 UPC-1185 UPC-127 UPC-127 UPC-127 UPC-127 UPC-127 UPC-137 UP
200 p 200 p 20

deal

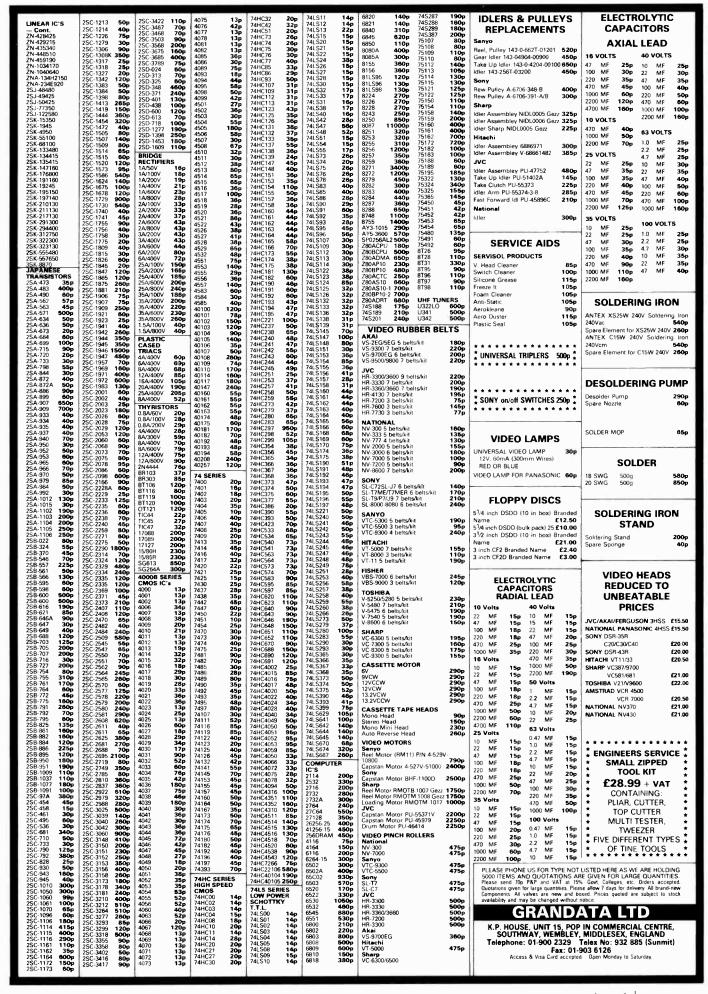

+ P&P & VAT 445



# CRACK OPEN AN EASTER BARGAIN WE SHELL OUT

A FAIR DEAL

GARY WINTERTON OFFERS A FULL RANGE OF EX-RENTAL TV & VIDEOS NO ORDER TOO LARGE OR TOO SMALL YOU COLLECT OR WE WILL DELIVER

> T.E.S.D. LTD. UNIT 6, 68 BAYTON ROAD EXHALL, COVENTRY CV7

Ring Gary on 0203 368437 TRADE ONLY

FAST VIDEO SPARES	FAST
ALL STOCK ITEMS ARE DESPATCHED BY RETURN OF POST	

### VIDEO HEADS

VIDEO	TEAUS
REPLACEMENTS	GENUINE HEADS
All our replacement heads are brand new precision Japanese heads not refurbished.	Panasonic NV2000, NV2010
Panasonic	NV7000, NV7200
3HSS(N) £19.90	NV333. NV370
Fits model numbers: NV2000, NV2010, NV7000, NV7200,	NV366
NV2000, NV2010, NV7000, NV7200, NV72000, NV7200, NV700, NV7200, NV7200, NV7200, NV7200, NV7200, NV7200, NV7200, NV7200	NV688, NV777, NV788
NV333, NV8600, NV8610. 3HSS-UI(N)	NV730
Fits model numbers: NV370 & Philips VR6460.	All others available P.O.A.
3HSS(4N) £46.50	Ferguson
Fits model number: NV366	3V00, 3V16, 3V22 3V29, 3V30
VR6460. £46.50 SHSS(4N) £46.50 Fits model number: NV366 SHSS(4NB) £54.60 Fits model number: NV730	31/32
Ferruson	3V32 3V35, 3V36, 3V38, 3V39
Ferguson £19.90 3H5S(v). £19.90 Fits model numbers: 3V00, 3V16, 3V22, 3V29, 3V30, 3V31, 3V35, 3V36, 3V38, 3V39, HB 2300, HB 2300, HB 2326,	Sharp
Fits model numbers: 3V00, 3V16, 3V22,	VC7300, VC7700, VC7750
HB2200 HB3300 HB3330 HB3360	VC8300
HR2200 HR3300, HR3330, HR3360, HR7200, HR7300, HRD120, HRD130	VC9300, VC9500, VC9700
3HSS4VB £54.60 Fits model numbers: 3V32.	VC381, VC383, VC386
Oh	VC482
3HSS(SP) £29.90	All others available P.O.A.
Fits model numbers: VC9100 VC9300	Sanyo
VC9500, VC9700, VC381, VC8381, VC383, VC388, VC482.	VTC5000, VTC5150 VTC5300, VTC5400
	VTC9300
PS3B(T) £31.90	Sony
Fits model numbers: V9600, V31B, V33B.	SLC5, SLC6, SLC7
Hitachi 3HSS(H)£26.50	SL8000, SL8080
3HSS(H) £26.50 Fits model numbers: VT8000, VT9300 etc.	SLC20, SLC30
Come	SLC9
PS3B(S) £24.90	Toshiba
Eite model numbers: SLC5 SLC6 SLC7	V9600
SL3000 also various NEC models. P84B(2S)	V8600
Fits model numbers: SLC20, SLC30, SLC40,	V55, V56
SLF1. PS5B(3S)	Hitachi
Fits model numbers: SLC9, SLT50, SLC8,	VT5000, VT5500
SLF60.	VT6500 VT8000 VT8300
Amstrad/Saisho	VT8500, VT8700
Amstrad/Saisho 3HSS(R)	VT9300, VT9500, VT9700
	VT11E, VT14E VT17E, VT19E
HSS(FI) £34.50 Fits model numbers: VCR4500, VCR5200,	VT33E
VCH9000 etc.	
Fisher/Fidelity 3HSS(SF) £29.90	Philips VR6460
3HSS(SF) £29.90 Fits model numbers: FVHP615, FVHP710,	VR6462
V1000.	Please call if your model is not list

THIS MONTH'S

**SPECIAL** 

**VIDEO HEADS** 

3HSS(V)

FITS FERGUSON & JVC

3V00 - 3V16 - 3V22

3V29 - 3V30 - 3V31

3V35 - 3V36 - 3V38

3V39 - HB3300

TE UNIT 3, PLESSEY

GENUINE HEADS	
Panasonic	
NV2000, NV2010	£44.00 £44.00
NV333. NV370	£44.00
	£64.50
NV366 NV688, NV777, NV788	£64.50
NV730	£67.50
All others available P.O.A.	
Ferguson	
3V00, 3V16, 3V22	£59.90
3V29, 3V30	£59.90
3V32 3V35, 3V36, 3V38, 3V39	£66.90
	£59.90
Sharp	
VC7300, VC7700, VC7750	£69.90 £69.90
VC8300. VC9300, VC9500, VC9700	£69.90 £62.00
VC381, VC383, VC386	£62.00
VC482	
VC482 All others available P.O.A.	202.00
Sanvo	
VTC5000, VTC5150	£39.90
VTC5300, VTC5400	£39.90
VTC9300	£39.90
Sony	
SLC5, SLC6, SLC7	£49.50
SL8000, SL8080	£49.50
SLC20, SLC30	£54.50
SLC9.	£54.50
Toshiba	
V9600	£59.90
V8600	£69.90
V31, V33	£59.90 £59.90
V55, V56	109.90
Hitachi VT5000, VT5500	C 40 C 0
V15000, V15500	£49.50 £49.50
VT6500, VT8000, VT8300 VT8500, VT8700	£49.50 £49.50
VT9300, VT9500, VT9700	£49.50
VT11F VT14F	£45.50
VT17E, VT19E	£54.60
VT33E	£49.50
Philips	
VR6460	£44.00
VR6462	£44.50
Please call if your model is not listed	ί.

GENUINE	BELT	KITS	REPLACEMENTS
Panasonic		Panase	
NV2000, NV2010	£6.50	NV2000	NV2010
NV7000, NV7200			NV7200
NV333, NV366			VV366
NV370, NV830, NV850	62.80	NV8600	NV8610
NV688		Fergus	
NV777. NV788	64 70	3100 31	/16,3V22
NV8600, NV8610			
NV730		3/29.3	/30
NV230, NV430, NV870	£2.80	3V35.3	/30 /36, 3V38, 3V39
NV870, NV810		Sanyo	
Ferauson		VTC500	0, VTC5150
3V00, 3V16, 3V22	£6.50	VTC530	0. VTC5400
3V23			0
3V29, 3V30	£4.90	Sonv	
3V35, 3V36, 3V38, 3V39	£2.90	SLC5 S	LC7
Sanvo		SI C6	
VTC5000, VTC5150	£1.99	SI 8000	SL8080
VTC5300, VTC5400	£4.50	Sharp	020000
VTC9300		VC7300	VC7700 VC7780
Sonv		VC8300	, VC7700, VC7780
SLC5, SLC7	£6.50	VC9100	, VC9300, VC9500
SLC6	\$7.50	VC381	VC383, VC386
SL8000, SL8080	£6.50	Hitach	i
Sham		VT5000	VT5500
VC7300 VC7700 VC7750	£6.50	VT8000	VT8300, VT8500
VC8300	£6.50	VT9300	VT9500, VT9700
VC7300, VC7700, VC7750 VC8300 VC9100, VC9300, VC9500	£6.50	VT11E	VT14E, VT17E, VT19
VC381, VC383, VC386	£6.50		
Hitachi		Akai	
VT5000. VT5500	£6.50	VS9700	
VT8000, VT8300, VT8500		VS2.VS	3, VS4, VS5
VT9300, VT9500, VT9700		VS9300	, VS9500, VS9800
VT11E, VT14E, VT17E, VT19	£6.50	Many of	hers available
VT33E		,	SENSOR LAMPS
Akai			sonic
VS9700	£6.50		son/JVC
VS2, VS3, VS4, VS5	£4.90		C9300 etc.
VS9300, VS9500, VS9700	£6.50	Sharp V	C7300 etc
Many others available		Ametroo	7000 etc
,		All Hitoo	hi
		Annuac	hi SENSOR L.E.D.'s
			sonic
CREDIT CARD ORDERS BY		All Fera	Json/JVC
TELEPHONE		All Hitac	hi
RECEIVED BY			END SENSORS
HECEIVED DT			END SENSORS

4 PM. ARE DESPATCHED

AME DAY

WE CARRY HUNDREDS OF VIDEO SPARES

INC. PLAY IDLERS, CLUTCHES, MOTORS, SERVICE MANUALS, TENSION BANDS,

BELTS AUDIO/CONTROL HEADS, ALIGNMENT TOOLS AND TAPES ETC.

\*\*SPECIAL ORDER FACILITIES\*\*

\*\*FOR NON-STOCK ITEMS\*\*

£4.95

£4.95 £4.95 £4.95

£4.95

£4.95

£5 Q5

£5.95 £5.95

£4.95 £4.95 £4.95 £4.95 £4.95 £4.95

PINCH ROLLERS 

Ferguson/JVC 3V00, 3V16, 3V22, 3V23 3V24 HR3300, HR3360, HR3660, HR2200 3V29, 3V30, HR7200, HR7300

3V35, 3V36, 3V38, 3V39 HRD120..... Sanyo VTC9100, VTC9300 VTC5000, VTC5150, VTC5300, VTC5400

Sony SLC5, SLC7..... SLC6.... SL8000, SL8080....

Sharp VC7300, VC7700, VC7750



£3.50 £3.00 £3.00 £3.95

£3.50 £2.90

JVJJ - 1110000	VC8300	
HR2200 – HR3360 🛛 🗖	VC9100, VC9300, VC9500 VC381, VC383, VC386	
· · · · · · · · · · · · · · · · · · ·	VC651 etc.	
HR7200 – HR7300 🛛 🗖	Hitachi	
	VT5000, VT5500	
HRD120 – HRD130	VT8000, VT8300, VT8500	
	VT9300, VT9500, VT9700	
£16.00 + VAT	VT11E, VT14E, VT17E, VT19 VT33E	
	Akai	
ADD 70p POST & PACKING	VS9700 VS2, VS3, VS4, VS5	£6.95
	VS2, VS3, VS4, VS5 VS9300, VS9500, VS9700	£0.95
	Amstrad	- 1.00
	VCR4500, 4600 Pinch Roller mod kit	£9.95
EI EVIDEA CEI	DINCEC	
ELEVIDEO SEI	HVILED	
DI FOOTY DISCINECO DADY TECHNOLOGY DOIVE BEE	TON NOTTINCUAM NCO 2ND	
PLESSEY BUSINESS PARK, TECHNOLOGY DRIVE, BEE	SIUM, NUTTINUMAM NUS ZNU	
TEL: 0602-226070 FAX LINE: 06		
24HR ANSWERING SERVICE FOR ORDERS PLACED	AFTER 5.30 p.m.	
Please add 70p post & packing and then add 15%	6 VAT to total	

OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, COLLEGES, ETC. EXPORT ENQUIRIES WELCOME. ALL ENQUIRIES SHOULD BE ACCOMPANIED BY STAMPED ADDRESSED ENVELOPE

### AMRICK VISIONS WHOLESALE ER YOU CAN he working set who WE SPECIALISE IN SUPPLYING TRADE CUSTOMERS WITH TOP QUALITY WORKING EX-RENTAL TV's & VIDEO's. WE OFFER GOOD PRODUCT, FRIENDLY SERVICE & KEEN PRICES TV'S VIDEOS Т PHILIPS G11 TEXT......£50 Н PHILIPS KT3/30 ..... £35 F Н

PHILIPS KT3/30 TEXT	£70
THORN TX9/10	£35
THORN TX9/10 TEXT	£70
THORN STEREO TEXT	£90
BUSH T20/22/26	£20

THORN 3V29/30	£70
HITACHI 8500/9300	£70
HITACHI VT11	£80
HITACHI VT33	£100
SHARP 9300/381	£90
AMSTRAD 7000	£70


We also stock Hitachi, Sony, Panasonic, Sanyo, Toshiba, etc.


PRICES All prices subject to VAT but INCLUDE HANDSETS where appropriate **SPECIAL DISCOUNTS & DELIVERY ON LARGE QUANTITIES AMRICK VISIONS WHOLESALE & 0533 55** 

**113 NARBOROUGH ROAD, LEICESTER** 

**APPROX 5 MINS** FROM JUNC 21 M.1. OPEN MON-SAT 9AM-6PM

AN103 AN1270 AN203	£1.95 AN6610 £2.20 AN6676 £2.20 AN6677	£1.95 BA1320 £7.50 BA1330 £6.30 BA1350	<b>£1.25</b> HA11749 <b>£1.75</b> HA11750 <b>£1.80</b> HA11753	£4.75 LA4440 £5.00 LA4445 £8.50 LA4460	22.75 STK082 22.75 STK084 21.80 STK430	27.75 STR6020 27.60 TA7063P 25.50 TA7066P	26.75 TDA3540 21.50 TDA3541 21.50 TDA3560	£3.80 £3.60 £4.50		
AN210 AN211A AN217B	E1.75 AN6780 E2.30 AN6811 E2.20 AN6873 E2.20 AN6873	<b>£2.30</b> BA5102A £1.60 BA5204 £4.50 BA5402A <b>£3.50</b> BA5406	2.75 HA11758 2.75 HA11768 2.75 HA11768		£1.80 STK431 £2.50 STK433 £2.80 STK435	25.95 TA7073AP 25.25 TA7074P 25.50 TA7122AP	22.75 TDA3561A 21.95 TDA3562A 20.90 TDA35621	£4.95 £6.00 £2.70		
AN228W AN236	12.90 AN6884 12.50 AN7105	£2.75   BA5408 £2.50   BA6104	12.75 HA11816 12.80 HA11828	£6.50 LA4508 £9.50 LA4520	£4.25 STK436 £2.85 STK437 £2.50 STK439	25.25 TA7136P 26.50 TA7140P 25.95 TA7145P	£1.75 TDA3652 £2.50 TDA4420	£3.30 £3.75	LONDON W2 1LG	045
AN240P AN241P AN259	£1.50 AN7106K £1.50 AN7110 £2.75 AN7111	£2.95 BA6124 £1.50 BA6208 £1.50 BA6209	12.80 HA12001 12.95 HA12002 13.75 HA12035	£6.50 LA4570 £2.95 LA5112 £9.50 LA5527	23.75 STK441 21.85 STK443 21.95 STK457	27.95 TA7193P 27.95 TA7205AP 26.50 TA7207P	£4.00 TDA4500 £1.00 TDA4600/2 £1.75 TDA4600/2D	£3.95 £2.95 £2.95	VIDEO HEADS	
AN260P AN262 AN264	22.20 AN7112E 21.60 AN7114E 23.75 AN7115E	62.95 BA6304 62.50 BX342 61.60 HA1124A	62.20 HA12038 65.00 HA12402 62.75 HA12413	£6.75 LA6324 £2.95 LA6358S £2.75 LA6458D	£2.50 STK459 £1.20 STK461 £1.20 STK463	£6.75 TA7208P £7.50 TA7217AP £8.40 TA7220P	<b>£1.75</b> TDA7270 <b>£1.60</b> UPC575C <b>£2.50</b> UPC1001H	£2.20 £1.00 £2.20	JVC/FERGUSON 3HSS PANASONIC 4HSS	£16.00 £16.00
AN271A AN274 AN277	22.50 AN7116 AN7120 AN7130	£1.50 HA1124DS £1.50 HA1125 £1.30 HA1137W	23.50 HA13001 21.75 HA13007 21.75 HA13402	£2.95 LA7016 £4.95 LA7031 £4.95 LA7032	22.75 STK465 22.75 STK501 4.50 STK0025	C8.50         TA7222AP           C6.25         TA7223P           C4.95         TA7225P           C4.75         TA7227P	£1.30         UPC1018C           £2.30         UPC1025H           £3.20         UPC1031H           £2.20         UPC1031H	£1.95 £2.30 £1.95	HITACHI VT11/14/33 HITACHI VT5000 HITACHI VT8000/9000	£21.00 £22.00 £21.00
AN295 AN301	23.50 AN7140 23.50 AN7143	22.75 HA1144 22.20 HA1151 22.95 HA1156W	£4.25 HA13432 £2.50 LA1111 £1.20 LA1130	£4.50 LA7215 £0.95 LA7224 £2.75 LA7505	£2.75 STK0029 £2.95 STK0039 £2.95 STK0040	£4.75   TA7229P £6.25   TA7230P	£3.25 UPC1032H £1.95 UPC1158H	£0.60 £0.95	HITACHI VT7/17/19 SHARP Most modeis not 6300/7300	£38.00 £22.00
AN302 AN303 AN305	23.30 AN7145M 22.75 AN7146M 23.50 AN7149N	22.50 HA1167 22.80 HA1196 22.95 HA1197	£3.75 LA1140 £1.75 LA1222 £3.70 LA1230	22.20 LA7507 21.00 LA7520 21.50 LA7521	£2.95 STK0049 £3.25 STK0059 £4.50 STK006011	£6.50 TA7232P £7.00 TA7233P £9.50 TA7240AP	22.95 UPC1181H 22.95 UPC1182H 22.95 UPC1182H	£2.50	SANYO VTC5000 AMSTRAD/SAISHO SONY DSR36	£36.00 £22.00 £20.00
AN313U AN315 AN316	22.95 AN7154 22.30 AN7156N 23.75 AN7158N	£1.90 HA1199 £2.50 HA1319 £3.25 HA1366W	<b>£1.85</b> LA1231 <b>£2.50</b> LA1240 <b>£1.80</b> LA1260	£2.00 LA7751 £1.95 LA7755 £2.95 LA7800	£4.75 STK0080 £3.20 STK1060 £1.95 STK2025	27.75 TA7241AP 27.95 TA7269P 27.50 TA7270P	22.95 UPC1188H 25.50 UPC1225H 22.75 UPC1230H	\$2.75 \$2.75 \$2.50	TOSHIBA 9600	\$23.00
AN318 AN337 AN340P	£4.95 AN7160 £5.25 AN7161 £5.25 AN7166	23.75 HA1366WR 23.75 HA1367 23.95 HA1368	£1.85 LA1353 £3.25 LA1365 £1.90 LA1368	22.50 LA7801 21.50 LA7806 22.50 LA7808	22.95 STK2028 2.75 STK2029 22.95 STK2038	<b>£7.50</b> ΤΑ7271Ρ <b>£5.75</b> ΤΑ7272Ρ <b>£9.50</b> ΤΑ7273Ρ	12.75 12.95 1900 12.95 1900 1263C 1263C 1277H	12.50 12.75 12.75	VIDEO SPARES JVC Idier PU47752	£4.95
AN360 AN362L	£1.30 AN7178 £1.50 AN7213	22.75 HA1368R 22.95 HA1370 21.95 HA1372	£1.95 LA1385 £3.70 LA1387 £3.50 LA1460	<b>£1.95</b> LA7820 <b>£3.60</b> LA7910 <b>£2.50</b> LA7920	22/75 STK2125 22.20 STK2129 21.75 STK2230	£6.75         TA7274P           £6.75         TA7280P           £6.50         TA7281P	C3.50 UPC1363C C2.95 UPC1364C	£2.75 £4.75	JVC Pinch Roller HITACHI Idler VT11-14-17 HITACHI Idler Piay VT8000	£2.95 £1.75 £2.75
AN363N AN366P AN374P	23.50 AN7218 21.70 AN7222N 22.20 AN7223	£1.75 HA1374 £3.50 HA1377 £3.95 HA1384	22.50 LA1464 22.20 LA2100 23.95 LA2101	<b>£3.20</b> LB1405 <b>£2.95</b> LB1409 <b>£3.30</b> LC4066B	22.20 STK2240 22.95 STK2250 22.95 STK3041	£9.50 TA7282AP £9.50 TA7283AP £6.50 TA7288P	22.95 UPC1365C 22.95 UPC1384C 22.95 UPC1387C	£3.50 £3,50 £2.50	HITACHI VT8000 İdler F/F/Rew. HITACHI VT9000 Play Idler	£1.85 £2.95
AN377 AN610P AN612 AN5010	£2.00 AN7224 £1.80 AN7256 £1.80 AN7273 £4.75 AN7310	£3.50 HA1388 £3.50 HA1389 £3.95 HA1389 £1.20 HA1389R	<b>123.50</b> LA3160 <b>122.20</b> LA3201 <b>122.20</b> LA3210 <b>122.50</b> LA3220	£1.50   LC7130 £0.95   LC7131 £0.75   LC7132 £2.95   LC7136	23.50 STK3042 23.75 STK3044 24.00 STK3062III 23.75 STK4026	26.50 TA7299P 25.95 TA7317P 26.75 TA7328P 25.75 TA7343AP	22.95 UPC1391H 22.75 UPC1394C 22.20 UPC2002 22.95 UPC2002	£1.50 £1.95 £0.80	HITACHI Pinch Roller 8000/9000 SHARP Piay Idler JVC Drum Motor SANYO Capstan Motor SANYO Reel Drive Pulley SANYO Pinch Roller 5000/5300 SANYO Pinch Roller 5000/5300	£2.95 £1.95 £22,50
AN5010 AN5151N AN5265 AN5410	£4.75 AN7310 £6.50 AN7311 £3.20 AN7410 £5.50 AN7415	£1.20 HA1392 £1.20 HA1394 £3.00 HA1396 £2.95 HA1397	£2.95 LA3300 £3.75 LA3301	22.95 LC7136 21.65 LC7137 21.30 LC7800 22.75 M5134P	23.75 STK4020 24.50 STK4060 23.95 STK413111 23.25 STK414111	<b>26.75</b> TA7343AP <b>26.75</b> TA7358P <b>26.75</b> TA7607AP <b>27.50</b> TA7608CP	12.95 UPC4558C 12.95 BC639 13.95 BC640	£0.90 £0.22 £0.22	SANYO Capstan Motor SANYO Reel Motor	£29.50 £8.00
AN5410 AN5411 AN5430 AN5510	23.50 AN7415 23.50 AN7420 22.95 BA301 22.75 BA311	<b>£2.95</b> HA1397 <b>£3.25</b> HA1398 <b>£0.80</b> HA1457W <b>£0.95</b> HA11215W	22.75 LA3310 E2.75 LA3350 E2.75 LA3351 E2.75 LA3361 E4.35 LA3370	£1.30 M5155P £1.20 M51102L £2.80 M51104L	<b>£3.25</b> STK41411 <b>£1.85</b> STK415111 <b>£3.95</b> STK4332 <b>£3.95</b> STK4352	27.50 TA7609P 25.75 TA7613AP 26.50 TA7628P	2.70 BFR90 22.75 BFR91 22.95 BFY90	£0.70 £1.20 £0.50	SANYO Reel Drive Pulley SANYO Pinch Roller 5000/5300 SANYO Pinch Roller 9300	£5.00 £5.95 £4.95
AN5512 AN5612 AN5620X	<b>£2.75</b> BA313 <b>£3.75</b> BA314 <b>£3.50</b> BA318	£0.80 HA11219 £2.20 HA11221 £1.50 HA11223W	£3.25   LA4030P £2.75   LA4031P £3.80   LA4032P	22.00 M51513 21.95 M51514 21.90 M51515BL	£1.80 STK4392 £1.95 STK4803 £2.50 STK4833	27.50 TA7640AP 28.50 TA7658P 29.50 TC9106BP	£1.75 BR303 £1.75 BR303 £1.75 BRY56 £4.95 BT106	£1.50 £0.20 £1.00	SONY Capstan Motor 1100	£28.75
AN5722 AN5730	£1.80 BA328 £1.60 BA333 £1.85 BA335	<b>£1.50</b> HA11225 <b>£1.50</b> HA11225 <b>£1.50</b> HA11226 <b>£3.60</b> HA11235	23.30 LA4002 21.95 LA4100 24.50 LA4101 22.30 LA4102	<b>£1.20</b> M5151568L <b>£1.00</b> M51517L <b>£1.40</b> M51518L	22.80 STK4843 22.80 STK5211 22.20 STK5315	28.95   TD62105P 26.75   TDA1010A 26.75   TDA1011A	23.50 BU208A 22.25 BU208D 22.50 BU326A	£1.20 £1.80 £1.95	ENQUIRIES OTHER ITEMS	£5.50
AN5732 AN5750 AN5753	£1.85 BA340 £3.75 BA343 £1.95 BA402	£2.50 HA11251 £2.75 HA11401 £0.95 HA11423	£2.75 LA4110 £2.80 LA4112 £4.75 LA4120	£1.75 M51521L £1.75 M83705 £2.95 M83712	£1.90 STK5324 £1.80 STK5325 £1.50 STK5421	25.75 TDA1074A 26.75 TDA1151 26.50 TDA1170N	£2.75 BU500 £1.20 BU508A £1.50 2N3055	£1.80 £1.80 £0.50	CASSETTE MOTORS	
AN6250 AN6326N AN6327	£2.30 BA403 £3.70 BA511A £4.75 BA514	£1.95 HA11440 £1.85 HA11701 £1.90 HA11703	£3.95 LA4125 £3.50 LA4126 £4.50 LA4137	22.20 MB3713 22.60 MB3714 21.95 MB3722	£1.60 STK5451 £2.95 STK5471 £3.50 STK5476	26.75 TDA1170S 26.50 TDA1510 26.75 TDA1515	£1.50 2N3773 £4.50 2SA733 £4.50 2SA1104	£1.50 £0.40 £2.50	6-9-12-13.2 Volts C.W. 12-13.2 Volts C.C.W.	ជ3.45 ជ3.45
AN6328 AN6330 AN6340	£4.20 BA516 £2.95 BA521 £7.85 BA524	£1.90   HA11704 £1.80   HA11705 £2.75   HA11706	25.20 LA4140 26.95 LA4145 24.75 LA4160	£0.90 MB3730 £1.70 MB3731 £2.40 MB3756	22.50 STK5720 23.50 STK5730 22.60 STK7216	<b>£6.80</b> TDA1515A <b>£4.25</b> TDA1908A <b>£6.50</b> TDA2002	£4.50 2SA1106 £1.75 2SB536 £0.80 2SB546A	£2.75 £0.95 £1.50	Mono £1.50 Auto Rev.	£2.75
AN6341N AN6342N AN6344	£4.00 BA526 £2.50 BA527 £4.75 BA532	<b>£3.50</b> HA11710 <b>£1.75</b> HA11711 <b>£1.60</b> HA11713	£3.75 LA4170 £9.50 LA4178 £6.50 LA4182	23.50 MB3759 22.50 MB8719 22.20 STK011	22.30 STK7308 23.85 STK7404 23.95 STK8250	25.95 TDA2003 26.95 TDA2004 28.95 TDA2005	£0.90 2SC461 £2.20 2SC1364 £2.75 2SC1942	10.35 10.50 12.95	Stereo £2.50 Enquines invited for any Japanese I.Cs. As we have	imported
AN6350 AN6356N AN6357N	<b>£7.50</b> BA536 <b>£3.85</b> BA546 £4.95 BA547	£2.50 HA11714 £2.20 HA11716 £2.50 HA11717	25.95 LA4183 24.75 LA4192 25.75 LA4201	£2.95 STK014 £1.95 STK015 £1.60 STK016	27.25 STK825011 25.20 STR380 26.25 STR440	£10.75 TDA2006 £5.80 TDA2020 £5.80 TDA2030	£1.50   2SC1969 £1.50   2SC2166 £1.50   2SC2580	£1.75 £1.00 £2.75	for over 10 years. ITEMS DESPATCHED WITHIN 48 HOURS Please add 60p post and packing and then add 15% V	AT to total
AN6360 AN6362 AN6363	24.50 BA612 25.50 BA631A 28.50 BA656	£1.80 HA11718 £5.75 HA11724 £4.50 HA11727	£4.75 LA4220 £9.25 LA4230 £9.50 LA4420	£1.50         STK025           £2.25         STK043           £1.75         STK077	£7.50 STR441 £10.50 STR451 £6.50 STR2012	25.80 TDA2170 25.80 TDA2581 26.75 TDA2611A	2.50 2SC2581 22.50 2SC3156 21.35 2SD401A	ជ2.95 ជ3.50 ជា.50	Callers by appointment: opening times 10am-5pm, Mon-Fri, 9-12 Sat	
AN6371 AN6387	£4.25 BA843 £5.95 BA1310F	£4.50 HA11745 £1.75 HA11747	<b>£9.00</b> LA4422 <b>£9.50</b> LA4430	21.75 STK078 21.50 STK080	26.75 STR4090 27.50 STR4211	26.75 TDA2653A 26.75 TDA3505	23.80 2SD1398 25.20 2SD1453	£2.50 £1.85	VISA/ACCESS ACCEPTED MIN. TELEPHONE ORDE	R £5.00

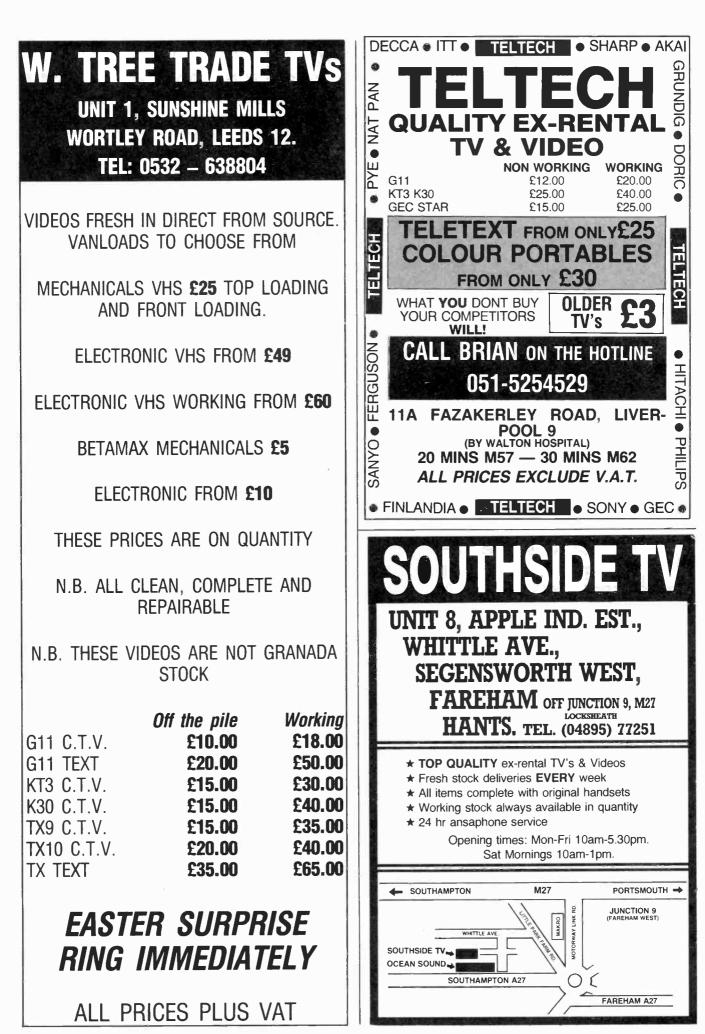

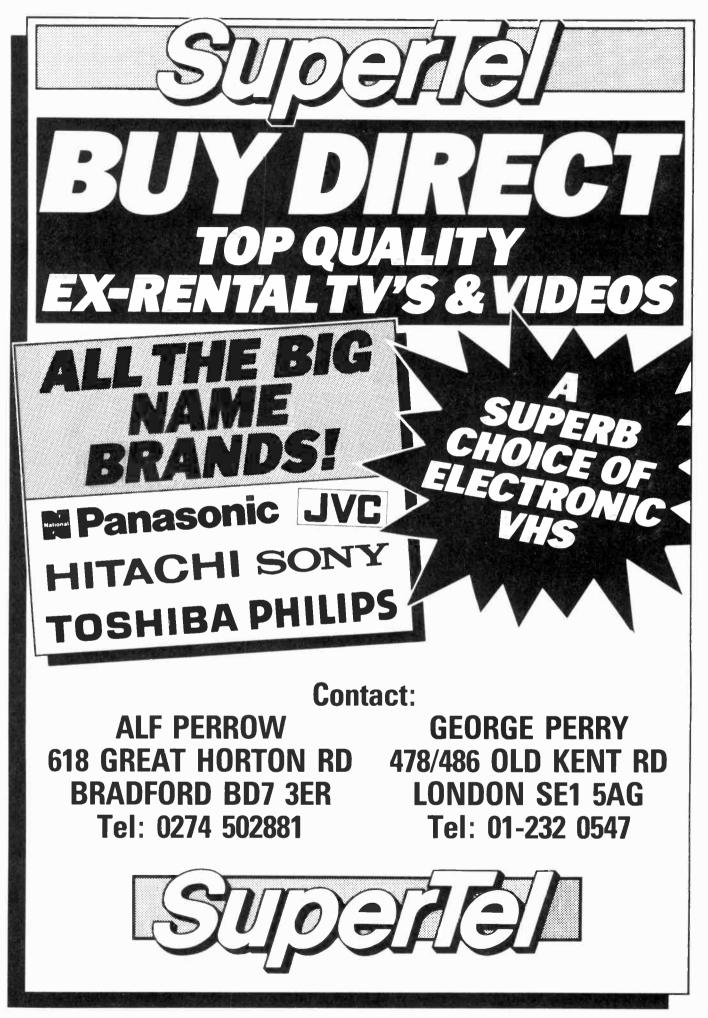



FOR GUARANTEED CTV & VIDEO'S TRADE SERVICE AVAILABLE ON ALL MAKES EXPORT ENQUIRIES WELCOME COURTEOUS SERVICE

# A Link with Europe

**Ring Norman - Gloria - Paul on new number** 

021 779 5465 021 779 5466 021 779 4701

\* TRADE ONLY SATELLITE ENQUIRIES



We are one of the South's leading Trade suppliers of top quality ex-rental TV and Videos. A good range held in Philips, JVC, Sony, Toshiba, Hitachi and National Panasonic colour TVs including portables, teletext and remote control models.

**CUSTOMER READY STOCK** 



**ELECTRONICS SERVICES** 

TILE CROSS ROAD

MARSTON GREEN BIRMINGHAM B33 0NW

Telephone: 021 779 5734

TILE CROSS TRADING ESTATE

Satellite

**UNIT 18** 

NOW IN STOCK EX-GRANADA MODELS FINLANDIA/REDIFFUSION Mk 3, 4 & 4A BASIC, REMOTE & TELETEXT VERSIONS

ACT SIMON HE

ක (0273) **5716**72

Fax:

We specialise in supplying working stock that has been professionally refurbished to a high standard. Our engineers pay special attention to the cosmetics as well as the electronics, so come to us for competitively priced stock that is *genuinely* ready for your showroom and your customers.

**RING OUR HOT LINES NOW!** 

**ZONEPORT** UNIT N2, LONDON ROAD TRADING ESTATE, SITTINGBOURNE, KENT CONTACT BRIAN MOLLETT

**☎** (0795) 28166



SPECIAL OFFER REDIFFUSION TRANSLATOR NO. 847038 23.99 plus £3 P&P inc. VAT





### VHS VIDEOS **FERGUSON**

3V00, 3V22, 3V23, 3V16, 3V29, 3V30, 3V31, 3V32, 3V35

HITACHI

5000, 8000

### NATIONAL PANASONIC

NV8600, 8610, 2000, 7000, 370, 333, 2010

SHARP 620, 630, 640, 2300 H T/P Untested from £70

# BETAMAX VIDEOS

SANYO VTC 9300, 5300

SONY C5, C6, C7 Untested from £25 HITACHI VHS TUNER/TIMER £10. HITACHI VHS BATTERY CHARGER £10, ROBERTS VHF RADIOS £5 VHS/Beta tapes used from 40p each

Sorry must collect as we do not send through the post.

# **PLUS**

17" 18" 20" 22" 26" Hybrid/ Solid State from £8. Also available **CTVs Remote Control & Teletext** All prices subject to 15% VAT

**Discount for Quantities** Complete loads delivered from pick up point

**JOHN CARTER** (Electrical) LTD FURNACE ROAD, **GALLOWS INN, ILKESTON** 

Phone: 0602 303124

**TELEVISIONS – VIDEOS – TELEVISIONS** 



A NEW NAME IN

**TRADE SURPLUS TVs** 

Large selection mainly THORN — GRANADA STOCK

### Discount ten or over

ALL SIZES AVAILABLE Thousands in stock. Good quality. Fresh stock every week.

Portables, Teletext, VHS Videos, STD 20", 22", 26"

Complete loads at discount prices

All stock collected from source by our transport and handled with care.



IEW-TEL TELEVISIONS SWAN STREET, EVENWOOD, 832832 Nr. BISHOP AUCKLAND, CO. DURHAM.



# for the independent dealer

on new or reconditioned **TV Receivers**, Video Cassette Recorders and Satellite **Reception Equipment.** 

For details and guotations contact



BROUGHFAME ITD Colonnade House, High Street, Worthing, Sussex, BN11 1NZ Tel. (0903) 820968

11%	et M	idland	ts T.V.	& Vio	len
			olesale	n viv	
N	IUW (	JPEN	in wai	LSALL	
OVER 3000 Huge stocks workin			AT UNBEATABLE	PRICES - HURR	
HOUL STOCKS WORKIN	CTV's		EUTS OF STEURA	VIDEO's	
	Working	Non-Working		Working	Non-Working
PHILIPS G11	£18 £30	£10 £20	FERGUSON 3		£50
KT3/K30 BUSH T20	£30 £18	£20 £10	JVC 7200 PANASONIC	£75 £75	£60 £60
TX9	£35	£25	SHARP	£80	£65
G11 TEXT	£50	£30	MECHANICAL	£45	£35
TX TEXT	£60	£45	3V31/3V35	£90	£70
STEREO TEXT	£90	£75	HITACHI VT11	£80	£65
TEST Y	DUR OWN S	SETS		INUTES FROM JUN	
NEW INFRA RE	D HAND SETS F	ROM £10	SHOWROOM	WAREHOUSE IN I	and the second second second second
	O HEADS FROM	A THE PROPERTY AND A STREET, AND	LARGE QUANTITY	OFF LITTLE LO	Contraction of the second s
		ALL DOMAIN DATA ASS	OF READY TO SELL	CALDMORE, W	ALSALL
BLUCKS UF	10 SETS FRO	141 £40	VIDEO'S & TV'S	TEL. 0922 72	4542
<b>★ DELIVERY</b>	CAN BE ARRA	NGED \star	Call in - you will be delighted		
ALL PRICES SUE	JECT TO V.A.T. AND Q	UANTITY	Open l	Monday-Saturday 9am - 7pn	n Sunday 10am – 2 pm
	SERVISCARE	THE ULTIMATE IN P COVERS WITH EXTR. * FREE PERS * USED AND Standard Extra La Portable VCR (Sta Jumbo (: Giant Ju Company Logo W charge (or free with	e can reproduce your exact bulk orders). Ask for de ECON( ghtweight but durable, th r money and, as with all Standard TV Extra Large TV Portable TV VCR (Standard & S	WHITE GOODS HEAVILY PA TER AND HANDY DOCUMEN BOLD BRILLIANT V TIONALS! 17.5 18.5 15.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 134.0 16.0 16.0 16.0 16.0 16.0 16.0 16.0 16	ADDED PROTECTIVE TATION POCKET VHITE PRINT! Oplus VAT Oplus VAT
	TELECARE	TO ORDE	WHY ARE OUR MUF ecause engineers L and simple to R: State printing required THE MUFFS vell House', 3 Fenham Ha	FS SO POPULAR AN IKE using them! – n use, they really do (name only) with order and COMPAN Il Drive, Newcastle-upon	ID EFFECTIVE? on cumbersome o the job! d cheque to:
		* Places allow 00 de		(091) 272 4646	a part by where it is a
		* Please allow 28 day	rs ior aelivery	* A receipted invoice will be	e sent by return of post.



### . \_ \_

# **BOLTON COMMUNICATIONS PROJECT** SATELLITE TELEVISION COURSES

To be held at	THE LAST DROP HOTEL, BOLTON.
Four Day	SATELLITE TELEVISION INSTALLATION COURSE 20th, 21st, 22nd & 23rd March, 1989 – £300.
One Day	<b>INTRODUCTION TO SATELLITE TELEVISION</b> 20th March, 1989 – £90.
Three Day	SATELLITE RECEIVER SERVICING COURSE 21st, 22nd & 23rd March, 1989 – £280.
Accommodation a	vailable at £65 per night.
TO BE HELD AT	BOLTON METROPOLITAN COLLEGE.
One Day	<b>CITY AND GUILDS COURSE ON FIXED DISH SATELLITE</b> <b>INSTALLATION</b> (offered on behalf of the Confederation of Aerial Industries). Course dates: 10th April, 8th May, 5th June and 3rd July, 1989.
	For further information please contact:

Terry Tudor (Project Manager),

Bolton Metropolitan College, Manchester Road, Bolton BL2 1ER. Tel: (0204) 31411 Ext. 3371/3395

# **ALL YOUR CCTV REQUIREMENTS**

CCTV CAMERAS		SEQUENTIAL VIDEO SWITCHERS		CAMERA 'C' MOUNT LENSES	
10 Lux CCD 180 Line	£230.00	2 Camera Auto Switcher	£55.33	1/2" 12mm F1.4 No Iris	£21.49
CCD2 Camera 0.3 Lux	£356.25	4 Camera Auto Switcher	£72.50	1/2" 12mm F1.4 Focus & Iris	£52.97
CCD Camera Auto Iris Adaptor	£20.53	6 Camera Auto Switcher	£81.25	1/2" 6mm F1.4 Focus & Iris	£60.78
CCD Camera Power Supply	£25.66	8 Camera Auto Switcher	00.683		,
2 Lux 240V AC Vidicon Camera	£119.44	12 Camera Auto Switcher	£115.00	2/3" LENSES	
Dummy Camera	£25.66	4 Camera Auto/SW, Looping/Bridging	£93.75	12.5-100mm F2 8:1 Manual Zoom	£259.89
		8 Camera Auto/SW. Looping/Bridging	£131.25		
CAMERA HOUSINGS		4 Camera Auto/SW. Digital/Bridging	£150.00	12.5-75mm F1.6 6:1 Manual Zoom	£153.94
Outdoor Housings 240V AC	£115.99	8 Camera Auto/SW. Digital/Bridging	£156.25	18-108mm F2.5 6:1 Manual Zoom	£309.87
Outdoor Housings 24V AC	£133.31			11-110mm F1.8 10:1 Manual Zoom	£534.78
340mm Indoor Painted Housing	£32.50	ALARMED AND SPECIALS		4.0mm F1.4 Focus & Iris	£126.25
340mm Indoor Stainless Housing	£48.75	Alarmed 8 Way 8 Zone	£437.50	4.8mm F1.8 Focus & Iris	£91.25
370mm Indoor Painted Housing	£28.75	Quad 4 Way Compressor Alarmed	£698.75	6.0mm F1.8 Focus & Iris	00.003
370mm Indoor Stainless Housing	£49.37			6.5mm F1.4 Fixed Prism	£149.94
1000 LINE METAL CASED MONITORS		VIDEO TIME AND DATE GENERATOR		8.0mm F1.4 No Iris	£37.49
9" Black/White Monitor	£87.49	Time and Date Generator	£146.25	8.0mm F1.3 Focus & Iris	£49.47
12" Black/White Monitor	£99.99	Time/Date/Message/Stop Watch	£134.25	16.0mm No Iris	£19,19
12 Diddiv withte worldow	133.83			16.0mm F1.6 Focus & Iris	£41.49
PAN & TILTS		BRACKETS			
240V Outdoor Unit with Cont/Box	£406.25	Short Camera Bracket	£8.61	AUTO IRIS & PINHOLE LENSES	
As above but 24V AC	£437.50	Long Camera Bracket	£8.61	8.5mm F1.3 Auto Iris	£137.50
24V Indoor Unit with Cont/Box	£218.75	90 Degree Camera Bracket	£8.61	16.0mm Auto Iris	£136.25
As above but 24V AC	£218.75	Camera Scanner Mount	£8.61	9.0mm F3.5 Pinhole with Iris	£130.25 £207.50
		Camera Scanner U-Hinge Mount	£15.33		
INDOOR PANNING UNITS		Pan & Tilt Comer Bracket	£56.25	As above but Right Angle	£267.50
Fixed Sweep Scanner	£24.07	Pan & Tilt Flat Corner Adaptor	£10.00	9.0mm F3.5 Auto Iris Pinhole	£374.99
240V Indoor Panning Unit	£66.87			As above but Right Angle	£449.99
As above but 24V AC	£66.87	VIDEO AMPLIFIERS		11.0mm Short Pinhole with Iris	£132.50
1 Camera 240V Panning Cont/Box	£36.25	240V Camera Amplifier	£36.12	W/A Auto Iris Attachment	£65.00
As above but 24V AC	£36.25	240V Camera Distribution Amplifier	£57.81	Special 2× Range Extender	£50.00
5 Camera 240V Panning Cont/Box	£90.00	24V Camera Amplifier	£36.12	Special Extension Tube Kit	£27.50
As above but 24V AC	£90.00	24V Camera Amplifier PCB	£23.62	Camera Lens Sizing Viewer	£131.25

### IF IT'S CCTV - WE CAN SUPPLY IT



THIS IS JUST A SMALL SELECTION OF OUR STOCK ITEMS



# ATTENTION


All dealers in the south west

Do you want good clean stock at the right prices?

Non-working ty's From	£5
-----------------------	----

Working tv's	From £20
Working text	From £75
Working electronic VHS	From £75

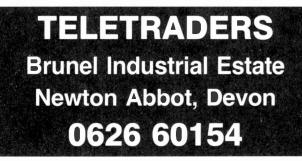Guarantee's available on all Working stock





		IDLER ASSEMBLIES Sham VC9300/9500 etc. VC9300/9500 etc. VC9300/9500 etc. VC9300/9500 etc. VC9300/9500 etc. V19300/9500 V19800/8500 etc. V19900/8500 etc. V1990/8500 etc. V19900/8500 etc. V19900/8500 etc. V19900/	IDLER ASS           From 02.80         Sharp           00.55         VC9300/9500           VC481/581 etc         VC9300/9500           0.270         ND10066EZ2)           0.10         Hitachi           VT11/33/14/17         V19300/9500           0.12         V19300/9500           0.12         V19300/9500           0.12         V19300/9500           0.12         V18000/8500           0.75         V18000/8500           0.75         Take up Clutch           0.75         Take up Clutch           0.75         Take up Clutch           0.75         3/29/30 Take           0.50         3/29/30 Take           0.75         3/29/30 Take	ITS           Jobo         Solo           ROLLERS         Bit           els         Solo           JUODES         Solo           JW Most values in stock         TRANSISTORS           C0.10         BF259           C0.10         BF458           CD.07         BH269           CD.07         BU108           CD.07         BU108           CD.07         BU108           CD.07         BU208           CD.07         BU208           CD.07         BU208           CD.07         BU208           CD.07         BU208           CD.07         BU208	Sony and £13.50         BELT Mary M Sanyo V           \$\$ Sanyo V         PINCH Mary M           \$\$ Sanyo V         PINCH           \$\$ Sanyo V         PINCH           \$\$ Sanyo V	REMOTE CONTROLS Ferguson, Grundig, ITT, Phillips, Hitachi various models TV & Video CAR RADIO/AUDIO MOTORS 6V, 9V, 12V and 13.2V c anticlockwise. LINE OUTPUT TRANSFORM	ADS
NESK-Production         CAR RADIO-AUDITO MOTORS         PNICH ROLLERS         CV C3003001041/1351 efc. (NULL           Nesk-Production System         Car RADIO-AUDITO MOTORS         PNICH ROLLERS         CV C3003001041/1351 efc. (NULL           Nesk-Production System         Nesk-Production System         PNICH ROLLERS         CV C3003001041/1351 efc. (NULL           Nesk-Production System         Nesk-Production System         PNICH ROLLERS         CV C3003001041/1351 efc. (NULL           Nesk-Production System         Nesk-Production System         Nesk-Production System         PNICH ROLLERS         CV C3003001041/1351 efc. (NULL           Nesk-Production System         Nesk-Production System         Nesk-Production System         PNICH ROLLERS         CV C30030000041/1351 efc. (NULL           Nesk-Production System         Nesk-Production System         PNICH ROLLERS         CV C300300000000000000000000000000000000	E1 L005GEZZ E4 E1 E1 E2 E1 E2 E2 E2 E2 E2 E2 E2	VC9300/9500 etc	VC481/581 elc VC930/9500 NDL006GZZ) 20.10 Hitachi VT11/33/14/17 VT300/9500 C0.22 VT300/9500 C0.22 VT300/9500 C0.72 VT8000/8500 C0.70 VT8000/8500 C0.75 Ferguson C0.75 Ferguson C0.75 Take up Cutch C0.75 3/29/30 Take C0.50 3/29/30 Take	ROLLERS ets	Kwise         and         Many M           53.50         ZENEF         BZX85-           S         65.00         BC107B           C2.50         BC108B         BC147A           BC147A         BC147A	CAR RADIO/AUDIO MOTORS 6V, 9V, 12V and 13.2V c anticlockwise.	/Ferguson most models
Parameterization         Parameterization<	23. 14. 14. 14. 14. 14. 15. 14. 15. 15. 15. 15. 15. 15. 15. 15	71 11/33/14/17/19/63 etc /79300/9500 etc. Play Idler. /78300/9500 F/F Idler. /78000/8300/8500/8700 F/F Rew Idler. /78000/8500 etc. Ff/Rew Pulley Figuson Farguson Farguson Clutch (mechanical models) X29/30 Take up Idler. X29/30 Take up Idler. X29/30 Take Idler.	VT11/33/14/17 C0.22 VT9300/9500 C0.22 VT9300/9500 C0.22 VT8000/8500 C0.75 VT8000/8500 C0.70 VT8000/8500 C0.75 Take up Clutch C0.75 Take up Clutch C0.75 3/29/30 Take t C0.50 3/29/30 Take t	3W Most values in stock TRANSISTORS 	S BZX85 - 5 C8.50 BC107B 5 C8.50 BC107B BC107B BC107B BC147A BC172C	LINE OUTPUT TRANSFORM	
318553-1-privation:NV730       122.3       0 <td< td=""><td>24. 21. 22. 22. 22. 22. 22. 22.</td><td>Ferguson Take up Clutch (mechanical models) 3V29/30 Take up Idler 3V29/30 Take up Clutch 3V29/30 Take up Clutch 3V29/30 Take Idler</td><td>20.70 V18000/8500 6 20.70 20.75 Ferguson 20.75 Take up Clutch 20.75 3V29/30 Take u 20.50 3V29/30 Take u 20.50 3V29/30 Take u</td><td></td><td></td><td>ITT CVC 25/30/32 Rank Bush T20A</td><td>220.00 Panasonic NV230/470/480/G9/G10/ 234.20</td></td<>	24. 21. 22. 22. 22. 22. 22. 22.	Ferguson Take up Clutch (mechanical models) 3V29/30 Take up Idler 3V29/30 Take up Clutch 3V29/30 Take up Clutch 3V29/30 Take Idler	20.70 V18000/8500 6 20.70 20.75 Ferguson 20.75 Take up Clutch 20.75 3V29/30 Take u 20.50 3V29/30 Take u 20.50 3V29/30 Take u			ITT CVC 25/30/32 Rank Bush T20A	220.00 Panasonic NV230/470/480/G9/G10/ 234.20
Anstand Thrump Inde:         Anstand Sissing - VCR4000, 7000, 9000 also Saich, Ofro Thrump Inde:         With Basic modeling and Sissing - VCR4000, 7000, 9000 also Saich, Ofro Thrump Inde:         State Sissing - VCR4000, 7000, 9000 also Saich, Ofro Thrump Inde:         State Sissing - VCR4000, 7000, 9000 also Saich, Ofro Thrump Inde:         State Sissing - VCR4000, 7000, 9000 also Saich, Ofro Thrump Inde:         State Sissing - VCR4000, 7000, 9000 also Saich, Ofro Thrump Inde:         State Sissing - VCR4000, 7000, 9000 also Saich, Ofro Sissing - VCR4000, 7000 also Saich, Ofro Sissing - VCR4000, 7000, 9000 also Saich, Ofro Sissing - VCR4000, 7000	12. 12.	V35 Reel Idler V35/36/38/39 Take un Clutch		£0.07 BU326A £0.07 BU407		Universal Video Copying Kit Universal Video Copying Kit (scart) Video Cassette Lamp suitable for Fer	nasonic NV777/330         £32.20           anasonic NV730         £46.00           anasonic NV366         £45.00           8000/9500 etc.         £22.00
3HSSY-VHR110011101300       639.50       Ihom X1070cus bht       83.55       B02438       0.2.30       TP31       63.33       Phasaenic         SHSSY-VHR110011101300       639.50       Ihom X1070cus bht       83.55       B02438       0.2.30       TP31       63.33       Phasaenic       NV6000810 TP31       0.0.30       NV6000810 TP31       NV600821       NV6000810 TP31       NV600821       NV6008	UIIIL £3.	antin	20.95 3V35 Reel Idler 20.75 3V35/36/38/39 20.75 Sanyo 20.75 Sanyo 20.75 VTC5000/5150 20.75 VTC5000/5150	£0.07 BU508A £0.07 BU508D £0.07 BU806 £0.07 BU806 £0.07 BU807 £0.22 BU7111	20.50 BC548 9500 20.50 BC548 20.50 BC549 20.50 BC559B 20.60 BC559B	With plastic moulding Cassette Lamp suitable for Amstrad 70 Cassette Lamp suitable for Hitachi 93 Universal Cassette Lamps 40ma or 60r CRT Anode Caps	84600, 7000, 9000 also Saisho, Orion, 524.10
Ferguson/VVC (Mechanical models)       E21.45       Thom 1690, 3000, 3500, 8000, 8500, 9000, TS       E1.80       TD 102600, 15.05       Ester       Fisher         Reit Mixtors       Starty VC/300/TS/01800, 124.53       E1.80       TD 20500, 15.05       Ester       Fisher         Shary VC/300/S00 etc.       E1.80       TD 20500, 15.05       Ester       Fisher       Fisher         Parasonic W/3300/S00 etc.       E1.80       TD 20500, 15.05       Ester       Fisher       Fisher         Parasonic W/3300/S00 etc.       E1.80       TD 20500, 15.05       Ester       Fisher       Fisher         Parasonic W/3300/S00 etc.       E1.80       TD 20500, 15.05       Ester       Fisher       Fisher       Fisher         Parasonic W/3300/S00 etc.       E1.80       TD 20500, 15.05       Ester       Fisher       Fisher       Fisher         Parasonic W/3300/S00 etc.       E1.80       TD 20500, 15.05       Ester       Fisher			C0 20 m	£0.22 BUX84 £0.30 TIP29 £0.30 TIP31 £0.30 TIP32 £0.30 TIP32 £0.30 TIP32	<b>£4.50</b> BD238 <b>£8.50</b> BD2438 <b>£6.95</b> BD2438 <b>£4.60</b> BD243C. <b>£4.60</b> BD244 <b>£4.60</b> BD244	Video Tape Splicing Kit Hitachi TV Frame Module HM6251	IR1500 £52.00
Ferguson/2000       Herzel and etc.       E21.45       Thom 1690, 3000, 3500, 8000, 8500, 9000, TS       E18.80       E1.00       TD A2500, E1.0       Fisher         Reit Motors       Starp VC7300/7007/500,3000       E24.85       TO A3500, E20.0       Fisher       Fisher         Sharp VC300/500 etc.       E1.80       TD A2500, E1.0       E1.80       TD A2500, E1.0       Fisher         Sharp VC300/500 etc.       E1.80       TD A3500, E22.0       Fisher       Fisher       Fisher         Sharp VC300/500 etc.       E1.80       TD A11902, E1.90       TD A3550, E22.0       Fisher       Fisher         Sharp VC300/700/7300, V29.400, PHR200/7300, E22.70       Sony AIAD PANASONIC SPARES       TD A11902, E1.90       TD A3550, E23.0       Fisher         AVAILABLE, PLEASE QUOTE       TD A11902, E1.90       TD A3500, E23.0       Fisher       Fisher         Sony SLC7/26 (BH F11000)       E22.20       Sony AIAD PANASONIC SPARES       TD A11902, E1.90       TD A3500, E30.0       Fisher         Sony SLC7/26 (BH F11000)       E22.20       Sony AIAD PANASONIC SPARES       TD A11902, E1.90       TD A14903, E3.0       Fisher         Sony SLC7/26 (BH F11000)       E22.00       Fisher       TD A14903, E1.80       TD A14903, E1.80       Fisher         Sony C7/26 (BH F11000)       E22.00 <t< td=""><td>23. 20. 700/7200/78 (VXP033 20.</td><td>V333/366 Idler Arm (VXL0997) IV8400/8600/8610/8620 (VXP0245) IV333/366 etc. (VXP0401) NV7 VXP0344) NV2000/3000 VXP0329)</td><td>120.40 VV333/366 Idle thick base) VV8400/8600/4 10.85 VV8400/8600/4 VV2P0344) VV2P0344) VV2P0329)</td><td></td><td>BF197 BF197 BF198 BF198 BF198</td><td>TV ON/OFF SWITCHES ITT, Phillips, Decca, Thom, Fidelity, etc. State model and part number fo Sony Universal with two brackets</td><td>TORS</td></t<>	23. 20. 700/7200/78 (VXP033 20.	V333/366 Idler Arm (VXL0997) IV8400/8600/8610/8620 (VXP0245) IV333/366 etc. (VXP0401) NV7 VXP0344) NV2000/3000 VXP0329)	120.40 VV333/366 Idle thick base) VV8400/8600/4 10.85 VV8400/8600/4 VV2P0344) VV2P0344) VV2P0329)		BF197 BF197 BF198 BF198 BF198	TV ON/OFF SWITCHES ITT, Phillips, Decca, Thom, Fidelity, etc. State model and part number fo Sony Universal with two brackets	TORS
Capatan Motors       ************************************	£4. £4. £3. £2.	isher VHP615 Idler Assembly VHP615 Gear Idler Assembly VHP905/910 Gear Idler Assembly VHP520/530 Idler		£1.00 TDA2653A £1.00 TDA2600 £0.85 TDA2611A £0.45 TDA3560 £1.00 TDA3561 £1.50 TDA3562A £1.20 TDA3562	£0.90 TBA500 TBA800 ★ ★ ★ ★ TBA820N TBA920S	* ORDER FACILITY FOR O	0/5150/5300/5400
Please add 75p per order for p&p and then add 15% VAT.     183 Acre Lane, Northampton NN2 8DX. Telephone: (0604) 847800      Oscillos and the second se	£4.	REWIND KIT Sony C5:7 Rewind Kit			TE TDA1412 TDA1940 TDA2521	* AVAHABLE. PLEASE Q * MANUFACTURERS PAR	rs (mechanical models)
CENTREVISION SLOPER ROAD, LECKWITH, CARDIFF. Exit 33 off M4 SOUTH WALES' LARGEST AND BEST WHOLESALER WITH 20 YEARS' EXPERIENCE	TARGAYA VISA		VAT.	nd then add 15%		Please add 75p pe	
CENTREVISION SLOPER ROAD, LECKWITH, CARDIFF. Exit 33 off M4 SOUTH WALES' LARGEST AND BEST WHOLESALER WITH 20 YEARS' EXPERIENCE		+/800	0004) 847800	. relephone: (		are Lane, Mortham	105 AU
BEST WHOLESALER WITH 20 YEARS' EXPERIENCE	OR RF Bands 1/3 (P&P £7) 1 L MC101 8 Patt omplete with Ba (82514 1 Test Patterns ( ONLY £40 £80 (P&1 be CM6038-DB C	Over 20 Test Patterns SADELTA Mazzi LOLDUR BAR GENERAT Video B Functions Sound Carrier Unused SADELTA CULUR BAR GENERATIOR PAI Pocket Sze: Richargeable Batteries Co Charger Adgotto Unused (PARTION PAI BECCANORI ING Colour Bar Generator Not Address Colour Bar Generator KG1 & CARGERAFIFICIOSTRENCTI MITTERS LABGERAF CROSSNATCH CENTRATION TIME LABGERAF CROSSNATCH CENTRATION TIME CARGERAFIFICIOSTRENCTI MITTERS	O         Over 20 Test           Sweep Dual TB 5475         SADELTA MI weep 5500         SADELTA MI Video 8 Fun SADELTA CI ep 5500           Pccket Size (startery Unused Councy of Charger Ada Sattery Unused Councy of Charger Ada (startery Of Charger Ad	RONIX 2215 Dual Trace 60MHz Delay 5 RONIX 456 Dual Trace 100MHz Delay 5 RONIX 456 Dual Trace 150MHz Delay S S3 1065 Three Trace 60MHz Delay Swe FIV 10105F Dual Trace 150MHz Mams/1 DUPMENT 0755 Dual Trace 150Hz Mams/1 DUISSAD Dual Trace 150Hz Mams/1 S0 1530A Dual Trace 151Hz Mams/1 G 203 A Dual Trace 150Hz G 203 A Dual Trace 150Hz		, CARDIFF. Exit 33 (	r Road, Leckwith
AV/0.8 Complete with Batteries & Leads	0NLY £45(P&I S	Unused (P&P £7) ADVANCE SG62B AM 150KHz-220MHz MULTIMETERS	C180         Unused (P&F           £10         ADVANCE SC           State Portable AC or         £130           £150         Solid State	ble 8 × 10cm Display nal front cover containing 2 probes etc IBS SM111 Dual Trace 18MHz Solid : nal DC operation 8 × 10cm Display EX 40108 Dual Trace 10MHz	- CO Po Op SE ext	SALER WITH	BEST WHOLE
AV0 BM V2 Complete with Batteries & leads MARCON IT 2006 AM FM 10MHz - 15MHz 50G Gen 1275 MARCON IT 2015 AM FM 10MHz - 15MHz 5	AVO 8) Complete d & Black with 2 ( £5 (P&1 £15 (P&1	AV0 8 MkV Complete with Batteries & leads AV0 TEST SET No 1 (Military version of A batteries & leads TEST LEADS suitable for AVOMETERS Rec Clips & 2 Prods Black Ever-Ready case for AVOs Unused	g Gen . £500 AV0 8 MkV C Sig Gen . £375 g Gen with Synchron- E550 E425 Kave Stresses Kave Stresses Black Ever-f Cann	20NI TF2008 AM FM 10MHz – 510MHz 20NI TF2015 AM/FM 10 – 520MHz Sig 2171 . 20NI TF2015 without Synchroniser 20NI TF2016 AM/FM 10MHz – 120MHz	S!		
PRONE: UZZZ 344/54       MARCONISANDERS IS SOURCE 60568 850 - 2150Mtr. 200 H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.       C7       VO TRANSISTOR ANALYSIS MA2 C1446 5 Deet with batteries and operating instruction H P 594 SWET DSCILLATION 7 - 12 464r.         EXAMPLE       VIDE VIDE VIDE SWET DSCILLATION 7 - 12 464r.       C7       VIDE VIDE VIDE SWET DSCILLATION 7 - 12 464r.         EXAMPLE       VIDE VIDE VIDE SWET DSCILLATION 7 - 12 464r.       C7       VIDE VIDE VIDE SWET DSCILLATION 7 - 12 464r.         EXAMPLE       VIDE VIDE VIDE SWET DSCILLATION 7 - 12 464r.       C7       VIDE VIDE VIDE SWET DSCILLATIO	ONLY 125 6 Suitcase style ( ions ONLY 125 6 Hz 20MW - 10W ONLY 125 (P&I	E7) AVD TRANSISTOR ANALYSIS Mk2 CT446 plete with batteries and operating instructiv (P&P E7) MARCONI AF POWER TF893A 20Hz – 35KP manual MARCONI RF POWER METER TF1152A 1	2400 (P&P 27) 2450 MARCONI AI 2275 manual 2100 MARCONI R	220 Signal Generator 7 – 12 4012 220 Signal Generator 7 – 11 GHz 214A Signal Generator 800 – 2100 MHz DGRAPH RTS2 Recorder Test Set "KE Wow & Flutter Meter ME108	HI FEI W(		
100/V 3200/ 100/V 3200/V 3200/ 100/V 3200/V 3200/ 100/V 3200/V 3200/ 100/V 3200/V 3200/V 3200/V 3200/ 100/V 3200/V 3200/	NT 60MHz Delay Sw e 20MHz Compo	NEW EQUIPMEN HAMEG DSCILLDSCOPE 604 Dual Trace 6 Component Tester + two probes HAMEG DSCILLDSCOPE 203 6 Dual Trace Tester with two probes	E100 E125 37A 400Hz or 1KHz E150 HAMEG DSC From E150 E95 E95 Tester with V	/-300V LTG200DM 1Hz-1MHz Sine-Square 20NI Automatic Distortion Meter TF23; ures down to 0.01% 20NI TF2700 UNIVERSAL LCR Bridg	- 10 LE MA Me MA		
New and rebuilt for most makes of T.V.	1						
including: Hitachi, Panasonic, Philips, Thorn, 240v In-24V Out 100VA £4P8P 54 Meteor 1000 - 600 MHz	5) Iterval etc e functions) &P £4) Meteor 1	BLACK STAR COUNTER TIMERS (P&P 55 APOLLO 10 - 100MHz Radio Period Time in APOLLO 100 - 100MHz (As above with more BLACK STAR FREQUENCY COUNTERS (P) 100MHz Methor 600 - 500MHz Methor 1000 - 10Hz	RMERS E15 EACH PAP E5 E5 EACH PAP E5 E5 EACH PAP E5 E5 EACH PAP E4 E4 P&P E4 Metror 100MHz Metror 100	In – 240V Out 500VA In – 240V Out 100VA In – 24V 200VA	24	sonic, Philips, Thorn,	cluding: Hitachi, Pana
including: Hitachi, Panasonic, Philips, Thorn, Toshiba, Sharp, Sony Mullard 20AX, 30AX etc. Thorn New Life now in stock Two year guarantee with a four year option. Cash or credit allowed for certain types of In-line glass.	) Iterval etc Eunctions) &P C4) Meteor 1 OCENERATOR ) //deo tand held 28 ra with batteries & is	BLACK STAR COUNTER TIMERS (P&P E5 APOLL 010 - 100MHz Radio Period Timeria ADOLL 010 - 100MHz Radio Period Timeria BODUNI AR IRCUENCY COUNTERS PJ Methor 600 - 60MHz Methor 600 - 16Hz BLACK STAR JUPTOR <u>500 Etamotion</u> - Square Trangua - HHZ - 500KHz (P&P P4 DAM-HZ COUNTER BRA ENERATOR Pail TV HUNG CHANG DMM 7303 - 3 <sup>1</sup> /2 digit - Including 1010 Radio ENERATOR Pail TV (P&P P4) Asabove DMM 60100 25%	RMERS ETS BACH PAP 25 ST BACH PAP 25 ST BACH PAP 25 ETS BACH PAP 25 ST BACH PAP 24 ETAP 87 ETAP 87 ETAP 87 ETAP 87 St PAP 14 Metror 600- Start Tig Start	In - 240V Dot 500VA In - 240V Out 100VA In - 24V Out - 24V Out	24 24 24	sonic, Philips, Thorn, ullard 20AX, 30AX etc now in stock h a four year option. rtain types of In-line glass	ncluding: Hitachi, Pana shiba, Sharp, Sony M Thorn New Life Two year guarantee wi sh or credit allowed for ce
including: Hitachi, Panasonic, Philips, Thorn, Toshiba, Sharp, Sony Mullard 20AX, 30AX etc. Thorn New Life now in stock Two year guarantee with a four year option. Cash or credit allowed for certain types of In-line glass. Price list available on request. EXPRESS TAV. SUPPLIES The Mill. Mill Lane	5) terval etc functions) &P C4) Meteor 1 SENERATOP //deo tand held 28 ra with batteries & e ST TOP_PAP (3) POSSIBLE: theck availab	BLACK STAR COUNTER TIMERS (PAP ES APOLLO 10-100MHz Radio Period Timer a APOLLO 10-100MHz Radio Period Timer a BODLO 100-100MHz Radio Period Timer a BODLO 100 PAPER AND A STAR Methor 600 - 100MHz Radio Paper A Methor 600 - 100MHz Radio Paper A BLACK STAR JUPTOR Son EllaCTION BLACK STAR JUPTOR Son EllaCTION BLACK STAR JUPTOR Son EllaCTION Solities Transpace Antre Son EllaCTION BLACK STAR JUPTOR SON ELLACTION CANADA SON ELLACTION AS ADONE DATA SON AS ADONE DATA SON AS ADONE AS ADONE DATA SON AS ADONE DATA SON AS ADONE AS ADONE DATA SON AS ADONE DATA SON AS ADONE AS ADONE DATA SON AS ADONE DATA SON AS ADONE AS ADONE DATA SON AS ADONE DATA SON AS ADONE DATA SON AS ADONE AS ADONE DATA SON AS ADONE DATA SON AS ADONE DATA SON AS ADONE AS ADONE DATA SON AS ADONE DATA SON AS ADONE AS ADONE AS ADONE DATA SON AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE DATA SON AS ADONE AS ADONE AS ADONE AS ADONE DATA SON AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADONE AS ADO	RMERS CISEACH PAPTS SISEACH PAPTS Meteor 500 Meteor 500 Meteor 500 Carlying case Carlying case Siseach PAPTS Meteor 500 Meteor 500 Carlying case Siseach PAPTS Meteor 500 Meteor 500 Carlying case Siseach PAPTS Meteor 500 Meteor 500 Carlying case Siseach PAPTS Meteor 500 Meteor 500 Carlying case Siseach PAPTS Meteor 500 Meteor 500 Carlying case Siseach PAPTS Meteor 500 Carlying case Siseach PAPTS Meteor 500 Carlying case Siseach PAPTS Meteor 500 Meteor 500	In - 240V Out 500VA In - 240V Out 100VA In - 24V 200VA In - 24V 200VA SPECIAL OFFI HAMEG MODULAR S 101 Man Frame with HM8032 sine With HM8030 2 Function Generator 0 He. and HM8011 2 Digital Multimeter ONLY £400 D EQUIPMENT - WITH 33. Is a VERY SMALL SAMPLI	S U	sonic, Philips, Thorn, ullard 20AX, 30AX etc now in stock tha four year option. rtain types of In-line glass le on request.	ncluding: Hitachi, Panas shiba, Sharp, Sony M Thorn New Life Two year guarantee wi sh or credit allowed for ce Price list availab PRESS T.V
including: Hitachi, Panasonic, Philips, Thorn, Toshiba, Sharp, Sony Mullard 20AX, 30AX etc. Thorn New Life now in stock Two year guarantee with a four year option. Cash or credit allowed for certain types of In-line glass. Price list available on request. EXPRESS TRV SUPPLIES	i) i) i) i) i) i) i) i) i) i)	BLACK STAR COUNTER TIMERS (P&P ES APOLLD 10 - 100MHz Radio Period Time in APOLLD 10 - 100MHz Radio Period Time in BLACK STAR HEOLINCY COUNTERS PI Henrice Counter (Part 2) Henrice Counter (Part 2) Henrice Counter (Part 2) HUNG CHANG DMM 7030 3 <sup>1</sup> 2 digit + micialing 10 Ann & 2010 1% Complete (Saftymg Caser Herbits) DSCILLOSCOPES PROBES Switched +1 INTEE MANUALS SUPPLIED IF AE or Telephone for Lists. Please C COF READING BEAKS RES REG DEFRESSIONS (PART 2) COMPRESSION	RMERS CIS BACH PAPTS DIS BACH PAPTS DIS BACH PAPTS CIS PACH PAPTS CIS PACH PAPTS CIS PACH PAPTS CIS PACH PAPTS CIS PACH CIS PAC	In - 240V Out 500VA In - 240V Out 100VA In - 24V 200VA In - 24V 200VA SPECIAL OFFFI HAMEG MODULAR S 101 Man Frame with HM8023 Sine With (HM8030 2 Function Generator 0 He. and HM8011 2 Digital Multimeter ONLY £400 ED EOUIPMENT - WITH 33 IN a VERY SMALL SAMPL IN a VERY SMALL SAMPL IN a VERY SMALL SAMPL STI 110 WYKEHAM Telephone:	S U	sonic, Philips, Thorn, ullard 20AX, 30AX etc now in stock tha four year option. rtain types of In-line glass te on request. <b>SUPPLUE</b> Bristol 0454-3162	ncluding: Hitachi, Pana: shiba, Sharp, Sony M Thorn New Life Two year guarantee wi sh or credit allowed for ce Price list availab PRESS T.V , Mill Lane, Staffs. 7600

1

----


----









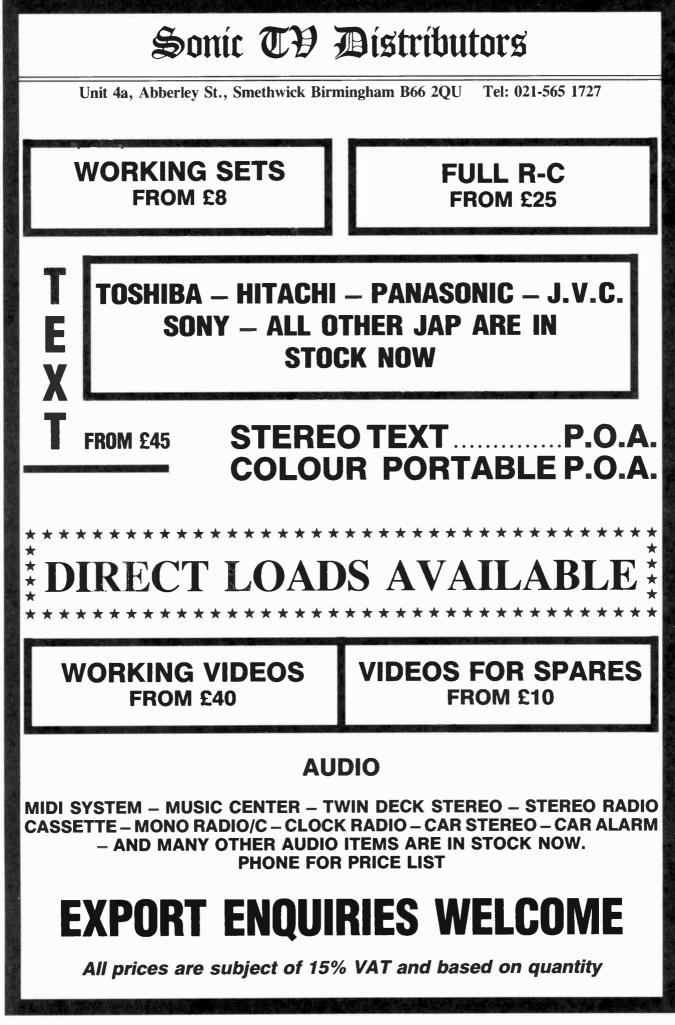

# **NORTH WEST ELECTRONICS** HUGE STOCKS NOW IN FOR '89

#### GOOD SELECTION OF THORN TV'S & VIDEOS FROM STANDARD **TO STEREO TEXT AT KEEN PRICES!**

### WORKING TV's

Bush T20/22, T24/6	£25
PyeG11	£25
Pye KT3	£35
Pye K30	£40
Ferguson TX 9/10	£40
Grundig	£20
Hitachi 226 etc.	£55

## WORKING VIDEO's **TRY BEFORE YOU BUY!**

Sharp Electronic 7300	£65
Ferguson 3V29	£75
Sharps 8300	£75
National Panasonic	£75
Ferguson 3V30	<b>£80</b>
Sharp 9300	£85

# BRADFORD

SPRING MILL STREET. MANCHESTER ROAD. **BRADFORD 5 5 MINS FROM MOTORWAY** 



308186

**QUANTITY OF BRAND NEW** TOWER SYSTEMS. MIDI SYSTEMS, PERSONAL RADIOS ETC

**IN STOCK NOW** K35/K30 TEXT **TX10 & HITACHI TEXT** 



WO	RKIN	G EX-	EQUI	PMEN	T PA	NELS
	IF	Con-	De-	Line	Power	Frame
		verger	coder	scan		
T20/2	2 X	5	14	18	17	14
T26	Х	5	16	20	17	Х
718	7.50	5	14	20	3	14.00
Philip	s					
G11	14.50		12	20	20	11.50
All	prices	inclu	de Pos	stage	& Pac	king.
			/ + h			

**TRADE SHOWROOM** LARGE QUANTITY OF READY TO SELL VIDEO's & TV's CALL IN, YOU WILL BE DELIGHTED!

LATER VIDEO'S NOW IN STOCK 3V35/44/65, Hitachi VT33 Philips 6660/64, UR 60,

AND MANY MORE

100's PX **HOOVER JUNIOR** VACS All models in stock

VISA

WELCOME

ACCEPTED WITH

BANKERS CARD

#### **UNTESTED TV's**

Bush T20/22	£10
Pye G11	£15
Pye KT3	
Pye K30	
Ferguson TX9/10	
Grundig	£10
Hitachi 226 etc.	£35
Thorn 9000	£10
Plus many more GEC I	тт


#### many more; GEC, III, etc from £5

### **UNTESTED VIDEO's**

Sharp 7300	£35
Ferguson 3V29	£50
Sharp 8300	£50
National Panasonic	£45
Ferguson 3V30	£55
Sharp 9300	£55
Betamax all makes from	£10
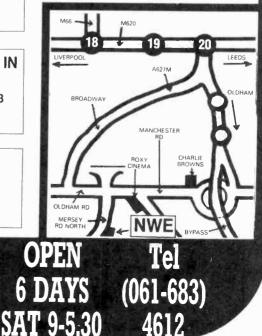
# MANCHEST

UNIT 3 MERSEY ROAD NORTH INDUSTRIAL ESTATE. FAILSWORTH











#### Ku BAND SATELLITE TV THEORY, INSTALLATION AND REPAIR

This 383 page manual by Baylin & Gale of USA covers dish theory, uplinks, footprints, site survey, installation and adjustment, descrambling, cable TV, even includes a computer program for finding your satelite. Second Edition £23.



n £23. Priceds Europe £6.00 extra per item. Pay by cheque, ACCESS MASTERCARD, or COD J. VINCENT TECHNICAL BOOKS, 24 RIVER GARDENS, PURLEY, READING RG8 88X. TEL: 0734 414468 (Answerphone)

SITUATIONS VACANT

# = Field Service Engineers Come And Join In Our Success

Part of a highly successful and fast growing organisation, Granada Group plc, we at Granada Microcare install and service an extensive range of micro-computer based office and commercial equipment, mainly in the business market. Due to our expansion, we are now looking for talented Field Service Engineers to come and share in our success.

Based at our site in North West London, but also working from home whenever this is practical, you will be responsible for the repair of a variety of micro-based products in the computer and telecommunications fields.

With a B/Tech National Certificate or an equivalent qualification, you should be able to demonstrate a sound overall knowledge of digital electronics. Additionally, you will need some field experience on related products, coupled with good interpersonal skills.

In return for your abilities, we can offer you a highly competitive salary of c£ 12,000 depending on your experience, full training is provided together with an attractive selection of large company benefits including a car, staff discounts, pension scheme and free life assurance. What's more, our impressive development means your future career prospects could be outstanding.

To apply, please send a full CV to: Vic Eltringham, Personnel Controller -Commercial Operations, UK Rental & Retail Ltd, PO Box 31, Ampthill Road, Bedford MK42 9QQ. Or telephone for an application form on (0234) 226624 (24 hour answerphone), quoting reference number VSE7.



#### **TV SERVICE ENGINEERS**

Due to our involvement in satellite TV, we urgently require experienced bench and field TV engineers. Bench engineers will work in fully equipped workshops in Mitcham and field engineers service areas in Greater London and home counties. Top salaries are offered and a 'better-than-average' estate car provided for field engineers. Existing holiday arrangements will be honoured.

Triadcolour



TV SERVICE LTD

SKILLED TECHNICIAN WANTED. Good pay rates apply. JOMILL ENTERPRISES, 173 Dalston Lane, E8, Tel. 01-533 2229.





## INDEX TO ADVERTISERS

ADi Adr Apr Apr Apr Apr Apr Apr Apr Apr	M Electronic Supplies	419 402 399 468 459
Bi- Bi- Bi- Bi- Bi- Bi- Bi- Bi- Bi- Bi-	Tech	411 456 398 469 457 454 463 403
Ce Ch Co Cr Cr Cr	Impion Wholesale Ltd	401 468 446 457 467
Do	ata-Go splay Electronics Ltd onberg Electronics	400
El El El	ast Cornwall Components	468 459
Fc F.	intdown Channel 5 ord, Frank T. Services	458
GGGG	eneral Factors	. 397 . 470 . 445 . 471
ır	latton TV Trade Disposals lockløy Discount Televisions I.T.V. Ltd. Lussain Central TV Ltd.	. 401
	.T.V.C	. 400
	ondon Electronics College Manor Supplies Marstall Ltd. Mauriton Electronics Mulfis Company, The	. 396 . 460 . 469 . 466 . 455
	YGK	
	Dmega Electronics.           Pagworth, E.           PC TV Services.           Phoenix TV Wholesale.           Poost a Part Electronics.           Powell, T.           Promerc.           Pro-Vision.           P. V. Subes.           394	. 456 . 462 . 446 . 456 . 449 . 462 . 462 . 443
	Radio and TV Components Acton Ltd Radio Components Specialist Relay Omagh Ltd Reliable Wholesale TV Reposessed TV Centres Riscomp Ltd	411 462 460 401 462 443
	Satellite Televisions	450
	Tatra L Id. Taylor Bros (Oldham) Ltd. Technical Advisory Systems Technical Information Services Teleprice Ltd. Teleview Televices Televi	469 461 469 469 442 458 448 462
	TV Hade outes	45.
	Vincent, J. Technical Books	470
	Williams, Dave. Willow Vale Electronics. Witsgrove Ltd. Wing Electronics. Wing Electronics. Wing Clectronics. With a construction of the construct	46

VIDEO MACI				NTS
We Sp	ecialize i	in all typ	es at	
UNBEAT	ABL	E PI	RICES	5!!!
VIDEO HEADS			RLDWIDE	
3HSS-N         16.00         34           3HSS-A         21.00         31           3HSS-B         20.00         31           3HSS-H         20.00         31           3HSS-H         20.00         31           3HSS-H         20.00         31           3HSS-(A)         20.00         31           3HSS-(A)         20.00         31           3HSS-PB         25.50         31           3HSS-PB         20.00         31           3HSS4-NA         40.00         31           3HSS4N-C         44.00         34	HSS-R HSS-Y HSS-SF HSSU-2N HSS6-NA HSS6-NA HSS4V-A HSS3-SY	30.00 27.00 20.00 21.50 30.00 21.75 30.00 60.00 44.00	PS3BS-1 PS3BS-2 PS3BT PS4B-2S PS5B-3S PSF-1 VT5000 VT3300 VT3300 VT33E/ 3HSS4V-B 3HSS4V-B 3HSS4V-B	16.25 21.00 30.50 35.50 20.00 30.00 30.00 20.00 44.00
BELT KITS			R OUR FUL	L LISTS
SONY C7         1.33         SI           SONY C9         1.38         SI           SONY SL         1.50         TC           FERG.3V22         1.30         TC           FERG.3V23         0.37         HI           FERG.3V29         0.90         HI           FERG.3V31         0.71         AN	HARP 7300 HARP 8300 HARP 9300 DSH. 7540 DSH. 9600 T. VT11 T. 5000 MST. 7000	1.38 1.38 1.38 1.08 0.66 0.83 1.50 0.60	SANYO 5000 SANYO 5300 SANYO 5300 SANYO 9300 N.PAN 300 N.PAN 777 N.PAN 7000 N.PAN 8600	0.50 0.80 1.00 1.50 1.25 1.16 0.85 1.28
AND MANY MORE SINGL	E BELTS CAPS	STAN BELTS L MOTOR		L MAKES
ALL OUR COMPO	NENTS ARE			
VIDEO DISPLAY CORF Griftronic Emission Limited Unit 2, Avenue Farm Ind. I Stratford-upon-Avon Warks. CV37 0HU. please add 75p pe	Est.		· ·	<ul> <li>295883</li> <li>298510</li> <li>31470</li> <li>415243</li> </ul>
MAIL ORDER ADVERTISING British Code of Advertising Practice Advertisements in this publication are re conform to the British Code of Advertising R respect of mail order advertisements where	Practice. In honey is		ILL-TIN RAININ OURSE	
paid in advance, the code requires advertis orders within 28 days, unless a longer deliv is stated. Where goods are returned ur within seven days, the purchaser's money refunded. Please retain proof of postage/de this may be needed.	rery period ndamaged / must be		2 YEAR NATIONAL DII Electronics and	
Mail Order Protection Scheme If you order goods as a private individual Order advertisements in this magazine ar post in advance of delivery, Television wil you for compensation if the Advertiser shoul bankrupt or go into liquidation provided:	nd pay by	(TV, Com	nunication Engine puters, Program <u>1 YEAR</u> TIONAL CER	nming, IT)
(1) You have not received the goods or money returned; and	had your		onic Equipment	
(2) You write to the Publisher of summarising the situation not earlier tha from the official on sale date of the public not later than three months from that dat retain proof of payment).	n 28 days	2. Co (Microproces	V, Video, CCT mputing Techno ssor, DataComms,	logy Interfacing)
Please do not wait until the last moment to When you write, we will tell you how to n	nake your		ormation Techno ms, Satellite TV, N	
claim and what evidence of payment is required. We guarantee to meet claims from readers accordance with the above procedure as	s made in		oftware Enginee r, BASIC, Pascal,	
possible after the Advertiser has become bankruptcy proceedings or gone into liquidati limit of £4,050 per annum for any one Adv affected and up to £12,150 per annum in res advertisers.*	subject to in up to a pretiser so in up to a pretiser so in the second s	COL Mon	JRSES COMMEN day 24th April 1	ICE 989
This guarantee covers only advance payme direct response to an advertisement in this			vailable with E.T. (	

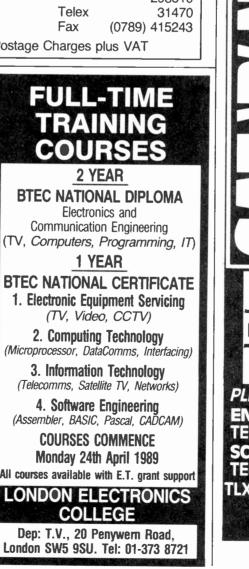direct response to an advertisement in this magazine (not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. All display advertisements are covered but only boxed trader classified advertisements are included. Advertisements as loose inserts are not covered.



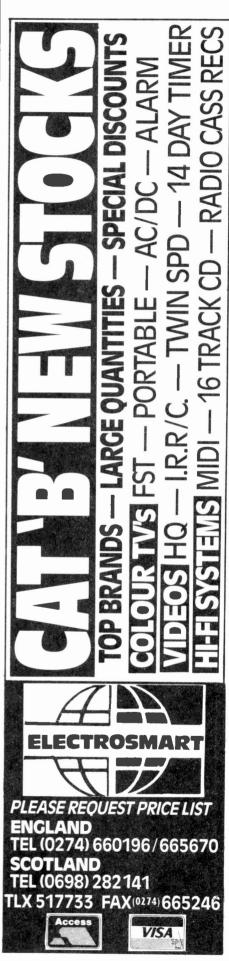

	CV 8617	io İ		Varta Batteries 2.4V	NI.CD 5 Hour	s Battery	Regulated Power Supply
Hill Intercom £10 Philips small stereo	Y 716 Y 729	10p 10p 30p	T 9004 40p T 9005 40p T 9051V £1.00	100M/A 50p TV Battery 50p	Charger with batt	ery test £6	3-12 volts 1 amp in box with switch and mains lead \$4
headphones £2.50 Rank UHF 4 push	Y 730 Y 827: 6A/1KV Y 860	10p 20p	ZTX 107 10p ZTX 108c 10p	1.2V NC. 2.4V NC. each 4 amp-1.2V Nickel	Hill Deluxe Uni Oad Charger	versal Ni-	Philips' Video Cleaning Cassette SBC461 £6
GRC power supply	Y 933 Y 969	30p 5p 50p	ZTX 109k 5p ZTX 213 5p	Cadmium Battery D Cell £1.00	Niekel Cadmiun Charger AA-C-D	n Battery -PP9 <b>£4.50</b>	Philips' Headphones Compact Disc Stereo Type £10
PC743B £10 Rank front panel	Y 997 Min 12 volt Relays	30р 75р 40р	ZTX 341 10p ZTX 342 10p	3.25V Battery 50p 12V Video Battery Tacks	12 Volt Aerial Ch	anger over	ITT Display Tube 58705 500
Z950 £5 GEC IF tuner panel	R 1038 R 1039 R 2009	40 o I	ZTX 384 10p ZTX 451 10p	4Amp U2 Cells 210 24V 4Amp (100VA)	Relays 144 Mc/s 45		8 Seg Disphay FND500 20p
PC786B £12.50	R 2010b R 2029	80p £1 50p	ZTX 550 10p MJ 2253 60p	Trans £4.00 Mains 240V (100VA) to	6 Push Button Un 2100 Series Repla Touch Button Un	cement for	Pocket Personal D.M.M. Volts range AC, DC 200M/V to 400V. Res. 2000Km 220
Rank IF 742   £3     TX10 8 Button Unit	R 2210 R 2257 R 2265	60р 60р 50р	MJE 3040 60p MJE 2209 10p	240V out fully shrouded £5.00	8 SEG LED Dis		Export PYE731
6 Button Unit	R 2305 R 2306	50p   30p	SP 8385 50p SAB 3205 £1.00	ITT CVC45 8 way resistor unit for v/cap £3	driver 1.C. LM	1017 50p	6 Push Button unit with (UHF- VHF) band switch £4
Rediffusion Mark 3 £5 Rediffusion Mark 4 & 7	R 2322/2323 R 2323 R 2396	pair 80p 15p	SAB 4209 £1.00 300M + 700 320V £1.80	CVC40 8 button unit with mains lead & slider pots	PHILIP: MIN. HEAD P		ITT Micro Phone M5 50p with switch
Push Button unit £10	R 2396 R 2461 R 2030	50p 80p 50p	200 + 100 + 100 + 30 300 V 50p 150 + 200 + 250M 300 V 50p	with sockets £10.00 Rook on An Introduction	£1.50 Elostronic B		1 <sup>1</sup> /2 Volt Sub Min Relays 25p Philips Solar Scientific SBC1730 Calculator £12
Tuner IF Cans ITT CMR200 £10	R 2443=BD124 R 2540	30p	Computer Transformer 20v/2.25A; 20v/1.5A;	to Satellite TV £5.95 No VAT	6 volt, 12-vo	lt 40p	15v-0-15v 1 Amp
ITT SEL HF Modul 2	R 2737 R 2738=T1P41 R 2775=T1P41c	40p 30p 40p	17/.5A; 19/.5A; 28/.05A £3	Book TV DX Handbook by R. Bunny £5.95 No VAT	15 . 015V, 1A Print Type Trans	£1	Transformers £1 RGP30K 10p
UK IF Tuner £8	R 3129=T1P47 R 4050	£1.00	OLD TYPE TEX. I.C. TX004F £3.50	Electronics Hobbyists Handbook £4.95 No VAT	12v DC Relay 1 print type 10		RGP30K         10p           RGP30G         8p           RGP10B         5p           RGP15         10p           RGP15G         6p
4 types of front panels Fidelity 2000/3000 types £5	S 2008b 2SD898B 2SC1042	80p £1 £1	TX005GN £3.00 TX904 £3.00	Hills £4.50	Changeover	£1	116024WG3 100
CVC20, CVC32 1.F.	2SC1942 Hitachi sets etc. STR454	£1 £2	X908 £4.00 MM2102AN £2.00	Multi Core 60-40 Soldar 500G 20 SWG		£4.50 £5.00	GP10 5p GP15Q 5p
CVC40 Cans £5 CMR800/3 NEW £20	STR6020 S 2000AF line o.p.	£2 £1	Voltage Regulators +5V/UA78PO5SC 30p	15 Watt Stereo Amp Sanyo	Module with Data	50p	THORN RGP80G 30p DUBLE 7 SEG Displays 15p LN5 26RA or 10 for £1
CMR800/3 £20 CMR803/2 £20	2SC940 BU 105/04 BU 108	£1 80p £1	-8V/79M08c 30p +6V/78M06c 30p	25 Watt Solder Iron	Various Tools and	£4.00	
CMR803/2 £20 20AX Line lin coil 50p	BU 124 BU 126	50p 80p 65p	+10v/78LA10 20p LM 317T 30p	Self adjusting cutter stripper 10 mixed tube bars	rannoas rous alla		£5.00 £4.00
GEC switch mode	BU 180a BU 204	65p 60p 75p £1	LM 337 30p LM 342/18 30p	5000 Diodes-Resistors T/V V/Aerial 300 $\Omega$ or 75 $\Omega$			£3 pack £1.50
trans 20AX ITT mains CVC9 to CVC33 print type 60p	BU 205 BU 206 BU 207	£1	LM 340T 5.0 50p +12V/LM 340T12 50p	* D/P push mains switch Mains lead & two pin socket	for radio cassette		20p each 35p
ITT 2,800 mains	BU 208 BU 208A	80p 75p	+18V/MC78M18 +24V/78M24 20p 30p	T/V loop aerial Radio Telescopic Aerial			75p £1.00
remote switch 50p NEW	BU 208D BU 222 BU 326	90p £1 £1	MC 7724cp MC 7824 40p	Philips Neon Lamps for TV Freeze Philips	sets		5p £1.20 £1.20
2110 GEC Sound O/P	BU 407 BU 426A	60p 45p	TIS 90 10p TIS 92 20p	Foam Cleaner Philips Contact Cleaner Philips	a Classer and Ant	Corona	£1.20 £1.20 All at £1.40
Panel £1 2110 GEC L.O.P.T.	BU 426V BU 500	60p £1.10	TIS 93 20p	Cans of Anti Static, Degreas Lorlin Full Remote Relay S Mains timer. 13 amp — up	witch fit most 1/V s	sets, mains 4	tag, 2 tag 12 volt £1.00
Panel £6 2110 GEC Power	BU 500D BU 508A BU 508V	£1 90p £1	U 19885 U 3832 7 15p	Screen locking agent, large of Red E.H.T. LAED and An	can ode Can	use, plugs in	£1.50 £1.00
Panel £5	BU 705 BU 807	£1 £1	U 3845 / 15p MR 508 / 10p	Weller solder iron 25 watt Hitachi Silver Oxide Battery		SR44 1.5V	£4.00 60p
Line o/p frame panels GEC 20AX £10.00	BU 824 BUT 11	50p 50p	MR 501 10p MR 502 10p	100 Coax Plugs			£12.00 £4.00
ITT CVC40 Push Button Unit & Mains	BÚT13 600V-28A BUW 11	£1 50p	BCW 71R 30p BYF 1202 10p	De-solder pump + 2 nozzels Flat Red LED and Green 500gm 60/40 solder reel			5p £6
Switch £12 Tuner & IF Panel.	BUW 84 BYW 20-08-9 BYW 95	60p £1 10p	BYF 1204 10p BYF 3126 40p	Solder 1 kilo reel Dual v/u meter -20 – +10db K30 thermistor 232266298009	)		£5.50 £1
Complete 6 button and preset IF with s/wave	BUX39 25A-150V BUX84	£1 50p	BYF 3214 40p BYX 10 10p	De-solder Pump			75p £2.50 £16.00
filter and tuner. Mullard M342 5"×6 <sup>1</sup> /2" £6.00	BUX85 BUY49	50p 20p	BYX 36/600 35 p BYX 38/300 25 p	Portasol Flameless Gas Sold Green & Red, LED pack m Hill Meter Leads, S/Rubber	ixed		100 for £1.00 £4.00
POTS	TIC 106a TIC 116m TIC 116n/Y 1003	30p 30p 30p	BYX49/600R 75p BYX 55/350 10p		HILLS		
BA 301 £1	TIC 126N TIC 225S	30p 30p	BYX 55/600 (Bead) 10p BYX 71/350 20p	Miniature Linesman Pliers Miniature Side Cutters	£2.20 £2.20	) Miniatur Miniature En	
HD 3884 2A23 £3 TA 4184 £1	TIC 226E TIC 226m TIC 236m TAG 226/600	30p 30p 30p	BYX 71/600 50p BYX 72/300 20p	KT3 PANELS Sound Output RGB Output	Chroma	100 Fuses 100 W/W R	£2.00 £1.50
TA 2125 £1 TA 4190 £1	TICV 106D	30p	BYX 36/600 50p BYV 95B 10p	Panel, I.F. Panel and Line	OSC £7.00 each	BF 199	20 for £1 m 100k pots. Rank £2
TA 4138 <b>£1</b> TA 4196 <b>£1</b> TA 4174 <b>£1</b>	(T092 case 2A/400V) TIP 29	10p 25p	BVY 95C 12p BYV 96D 10p	PYE 6 Key Switch & Panel		BF 470	20 for £2
TA 4139 £1 TA 4198 £1	T1P 30 T1P 30A T1P 30B	25p 25p 25n	BYZ 106 10p BPW 41 15p	G11 Front Panel	£10	some with le Philips, Pye	IF Aerial Isolating Sockets, ong leads. Fit ITT, GEC, £1.00
TA 4167 £1 TA 4199 £1	T1P 30C T1P 31	25p 25p	BYW 56 2A/1000v G/1 8p BYW 29/50 15p	SONY 1400KV Chroma Par SONY 1400KV Touch butto	nel £6 on unit £3.50	r mups, rye	Mixed Packs
BA 546 £1 BA 328 £1 TA 4176 £1	TIP 32 TIP 33B TIP 33C	25p 25p 25p 25p 25p 25p 25p 25p 70p	BYW 95C 10p BZU 15/24 54p	GEC Decoder Panel PC772 PC446		Replacemen	wer Trans RCA 16182 NPN t for BD124 and Mounting
TA 4145 £1 TA 4191 £1	TIP 34A TIP 34B	50p	BZY 93c75 BZV 15/18 50p 30p	12 Volt Mains Trans 500M/			£1.00 Sunt Bulbs & Neons £1.50 £1.50
TA 4188 <b>£1</b>	TIP 34C TIP 35B	60p 70p 50p	BZV 15/30 BZW 70c6v2 10p	Double 1.5 Digital Display.		10A 25 LED red 201/C Holds	البول yellow/green £1.50 ۲۶ £1.20
TA 4183 £1 TA 4197 £1	TIP 35C TIP 35D TIP 36	70p 80p 50p 70p	BZX 79.3v 10p	High brightness	20p	201/C Holde 20 Large LI 20 Small LE	rs         £1.20           ED Red         £1.00           ED Red         £1.00
TA 4183 £1 TA 4195 £1	TIP 36C TIP 41	150	Bush thyristor RCA 76122 £1 Transformer 240v/20v-500Ma75p Chassis type Transformer	Quantity Reduction		10×20 Turn	100K Pots £1.00
TA         4175         £1           TA         4177         £1           TA         4192         £1	TIP 41B TIP 41D	40p 70p	Chassis type Transformer 240v/12 Volts 500m/a 75p CVC 20 tube base £2	BY204/4 BY206 KT3 touch button black	25 for £1.00 25 for £1.00 6 for £1		ransistor B.F. and B.C. and
TA 4146 £1 TA 7265 £3	TIP 42 TIP 42/BRC 6109 TIP 48	10p 10p 40p	Tube Base Rank & G11 \$1.20	G11 touch button red K30 full remote Dawer Ass	6 for £1	PET	SI.50 111107 210.00
	T1P 49 T1P 57	40p 30p 30p	Infra red led LD57CA 15p	I.C. K30 VHF. UHF Dawer As	÷.00	12 Volt 4 A Type D Cel	mp Video Battery Pack 10 of ts £8.50
The Service Engineers Guide to Teletex £2	TIP 110 TIP 100 TIP 102	20p 30p 30p	15K-20 turn pots 20p Thorn 3500 2A cut out 50p	BY298 3 amp/fast/R BU126	10 for £6.00	40 glass ree	d switch
4 Types Fedility front papels with i.c. & pats	TIP 115 TIP 117	30p 30p 50p 50p 35p 40p	BBH/SAFETY	BU205 BU105	10 for £8.00	40 Pots	Pin, 10 Tube Bases.
panels with i.c. & pats £2 each	TIP 125 TIP 126 TIP 127	35p 40p	MAINS ISOLATING TRANSFORMER	BF458 BF224	10 for £1.00 20 for £1.40	mixed	£2.00 s, Condensers, Resistors on
BB 103 10p BB 105A×12 £1 BB 105B×12 £1	TIP 130	40p 30p 6p	250V-250V/A £10	50 Ceramic Condensers	40 for £1.00 £1.50	Bandolier 20mm Fuse	£1.00 Holders
BB 105G×12 £1	TIP 131 TIP 136 TIP 140	ор 30р 50р	BRIDGES KBL 005 30p	Mixed Mounting Kit for Po Transistors 300 Condensers	50p £1.50	Chassis Mo EHT Diode	unt 20 for £1
BB 121a 10p 47 10p each 1A/1600V 10p	TIP 142 TIP 640	30p 50p 80p 50p 35p mp 75p	KBL 02 30p KBP 04 30p	300 Condensers 300 Resistors 150 Electrolytics	£1.50 £2.00	300 Mixed	
	TIP 2955 TIP L761A-1000V/4A	35p mp 75p	W02 15p W004 15p	15 Dulbe Philipe	40p	100 500M/A Mixed V/Ca	Fuse £1 ap Pots ITT-GEC-Hitachi-
DG3P EQV-BY228 10		30p	W005 20p	I GECTION THE THEFT		Philips etc.	20 for £1
DG3P EQV-BY228 10 for £1	T 6032 T 6036 T 6040	40p 40n	W005 20p 800V Bridges 2 <sup>1</sup> / <sub>2</sub> Amp 30p			ITT Mains	Switch with Remont
DG3P EQV-BY228 10		40p 40p 40p 40p 40p		SENDZ C	MPONENTS	ITT Mains CMC113	

05407		G8 LOPT Panel		00 Multi-Caps	ר
SENUZ	COMPONENTS EE BACK PAGE	Rank T20 Z136 Panel	56	00         220 MFD Sprague 385V         50p           .00         350V 300M + 300M         £1.00           .00         100V 400M         60p	
TO ORDER SE	E BACK PAGE	NEW GEC 20AX Power Supply Switch M Field + Jungle panel for GEC 3133/3135 GEC 2110 line panel with transformer GEC 2110 tuner unit + 1F Panel	£1 £7.	.50 350V-400M 60p .00 Thorn 3500	
Matsushita PY34220 Tuner £7 C Cam Decoder with TDA3591 £5	K35 Decoder £8.00 K35 Sound OP £4.00	Pye/Chelsea Line op panel Pye 205 T/unit	£12. £12. £3.	.00 KT3/200/25/25/385v £1.00	
Toshiba VHF/UHF EG522F £6 Mitsumi MEC1-F51 £5	Thick Film Daughter K13 3122-127-43891 £3	Pye 713 IF panel and tuner Pye 713 Chroma	25% £10.	00 200+200+75+25M 325V £1.00 300+300+150+100+50M4ED	
	LC. £5 K35 IF £5.00	Pye/Chelsea Timebase panel with LOPTI Pye 731 Frame Panel		.00 G11 CAP 470/250 £2.50 .00 47/220/350 60p	
Thorn Spares New 9000 Decoder £8.50		Pye 731 Convergence Panel Pye 731 Chroma Pye 731 IF panel + tuner		an 2500/2500/63v 50p	
9000 Frame panel         £8           (4000 Cyclops panel         £1.50           8800 convergence panel         £6		GEC portable chassis + LOPTI 2114 New	ALL £10. £4. £6.	.00 300/100/10/16/275v £1.50 100/200/325v 40p	
500 convergence panel £6 4000 Power supply £3	Fidelity Tube Base with transitor & focus	Mono RANK Chassis 127A NEW NEW G9 Frame Panel	PANELS £10. £4.	00 200/200/75/25M 375V £1.00 00 Thorn TX9 Caps 500+500M 175V £1.00	
1600 Mains lead, switch 1605 IvNPN T066 80v/6A 10n	pot £1.50	NEW G11 IF Panel           G8 Tuner Unit + Panel         £4.00	£10. 420M 400V £1.	000 1500/2000/30v 50p 00 150/150/100/320s 62.00	
9000 Sound output panel         £1           3500 Focus unit         £1.50           3500 Mains Trans         £4	Bush Tube Base on panel £1.00	G8 IF & Chroma £6.00 G8 Khroma £3.00	470M 380V £1. 220/400V £1.	00 100/350 + 300/200/100/16/275v £2.00 225+25/380 GFC 70p	
3500 cut outs 10 for £4 3500 1F panel £2	IX10 Tube Base on Panel £3.00	G11 IF Detector £3.00	-	0p 500/500/25v 50p 150/150/100/30ck 75p	
3500 Frame panel £3 3500 Line panel £3	Line Transformers Line O.P. Trans. Mono T.X. 12"-14"	G11 Selector gain module £3 Complete CVC 825 Chassis £15			1
3500 A1 Diode 20p Export 3500 IF panel £2	Philips 27482 £10	AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670 £3.00	1+1 MFD Mains Filter ITT 3 Pin 1 1/(00 × 10 3	ITT 8 and 6 Push Burton         £1.00           5p         Pyc 725 LOPTs         £6.00           Pyc 731 LOPTs         £6.00           Thom 8500-88800 LOPTs         £5.00	
IC board with set of SN74LS £1 4000 Tube base £4 3500 A1 pots 50p	4822 £10 10273 £10	Z714 RANK IF Panels 6MHz 1 1 C. SL437F £3.00	22/100 1 4.7M/100	0p 5p CMC 301 front panel £5.00	1
Beam limiter panel £1.50 3500 Power panel with Y969 £1	Thorn 1690 LOP1         £7,50           2 J/Pots 3,500 1 off each type         £3,00           G8 Trans Philips         £7,00	Z909B RANK IF Panels           Export 5.5MHz 2 1.C.'s           TBA1205B TCA2705Q           £2.50	4700/100 7	5p CMC 302 Panel with TC mains switch	1
3 Way regulated adaptor 240V 6V/ 7.5/9V/300mA £3.50	G11 Split Diodé £12.00 CVC820 Split Diode [17] £10.00	K35 IF £6.00 Z743 RANK IF Panel	300 300/300∨ 8	0p CMD 800 Decoder £8,00	
Rank/Toshiba preh unit 0354 £9.50 4 Push button unit preh £1.00	Thorn B/W AD5308F + Stik + Lead £1.50 GEC 2040 £3.00	Export 5.5MHz 3 LC.'s TBA750+SC9504P+	1/250 Pulse 2,2 250v 1	5p G11 £1.50 0p 11 C Receiver Panel	
6 Push button VHF/UHF for v/cap. GEC-Decca type £7.00 7 Push button for CVC5 ITE £8.00	GEC 2110 £7.00 Mullard AT 2036 £1.50	SC9503P £1.50 Pye G11 Front panel with transducer,	7N5 1500V 1 3n3/250 A.C. 4	5p 3 LC. Power Supply G11 Full Remote 0p Receiver Panel ===±3.00	
KT3 12 Push button unit £2.00 KT3 (Export) 12 P.B.u £2	Pye 169 Line Trans £3.00 Pye mono £3.00	pots, tuner pots, 6 pb switch+lead <b>£5,00</b> Pve 6 button switch portable <b>£1,00</b> GEC V/cap VHF/UHF tuner and IF+	.39/250V I	Op         PFILLIPS SBC 469 Storest Microphone           5p         £23,00           5p         Meterst Lills 520           E17-00	A
5 Push button Unit Thorn £1.00 5 Push button GRC £6.00	Rank mono T704A         £3.50           Split Diode Trans         £7.00           GEC 20 AX Rank Z522         £3.00	GEC V/cap VHF/UHF tuner and IF+ sound O/P PC 706B3 (Export) £12.00 GEC Line O/P PC 659B3 £6.00	22/250 1 47/250 1	5p Meters Hills 420 £10.00 21 fills HD5000 Digital Meter 1000V DC	$\triangleright$
Push button PYE 731 £6.00 Hearing aid unit £3 Rank Z718 4 P/B/Unit MECH £4	Rank L.O.P.T. 2970 £3.00 CVC32 £6.00	2110 GEC Power Panel £8.00 CVC 20 Front panel with sliders +	100/250 G11 470/250	75 11T100 Multimeter £6.75	
Rank Z718 4 P/B/Unit MECH £4 7 Button Unit GEC with Lamps £7 997 Push Button Unit £6.00	CVC30 ITT         £7.00           CVC32 Line Tran         £7.00           CVC800 Line Trans         £6.00	mains input panel £4 CVC 40 PUSH BUTTON ASSY with	700/250	EI 11500 Multimeter £9.00 EI 117700 £15.00	
2916B panel £5.00 F513AP panel £5.00	CVC800 Line Trans         £6.00           CVC825 Split Diode         £10.00           CVC 45         £5.00	sliders: complete with lamp assy + pots 8 button units £9,00	800/250 4	00 [11D1000 Digital £20.00 0p [11D3000 Digital £25.00 0p [11D5000 Digital £25.00	$\checkmark$
Maine Drannar	GEC Portable G10T2041 £3.00 GEC Portable G10T2046 £3.00	CVC9 slider pots panel 50p Universal Focus. Fits Pye, Thorn and	4/350	5p EED5500 £29.00 EED5000 Dividual £32.00	
Mains Droppers           Pye 731 3+56+27R         50p           Thorn 50/17/1K5         £1.00	EHT Split Diode Leads ITT         £1.00           3500 L.O.P. I. & HT Trans         each £2.00           LOPT Rank Z763         £5.00	Decea Units. T147 Rank tube base on panel £1.00	4.7M/350v	HD9500 Digital with capacity Temp     HD9500 Digital with capacity Temp     J Trans Volts Obms and Amps ranges     60	$\vee$
20/20/20/48/117 £1.00	K35 Split Diode 3122/13835930 £10.00	Z718 Focus Unit £1,50 T20 Focus Unit £1.00		Infra Red	
70/10/6 for Thorn 4000         50p           8/320/70/39         £1.10           Thorn 50-40R-1K5         50p	Universal Tripler with small focus pot. Green type £7.00	Large Type 75p Decca Small 75p KT3 Focus Unit 75p	22/375	0p Works at 24 feet – Sound repeater. 5p Works off 9 volt battery £8.00 5p Fits in top peeke	
Ae Socket & Lead GEC, ITT, Philips, Pye 25p XX3/4 Thorn £1	· · · · · · · · · · · · · · · · · · ·	K30 Focus Pot 75p K30 Tube base on panel £1.00	330/385 CVC 820HT 60		
Thorn 1600-1700 £1.50 Rank Toshiba Tube Bases 30p	Black Triplers £6.00 S.T.C Universal Tripler £6.00	TX10 Focus Units         £8.50           CVC 32 Focus Unit         75p	KT3 E/W .39/400 15 .56K/400v 20	Philips K4-K35, RC5350-RC5300, P RC5370, RC5375, repaired same day	ĺ
	11 TJT £2.50 11 TGA £2.00	Fedility Focus Unit 14R-14S 30p 3500 Thorn Focus Unit £1.00	.22/400 10	P   RC4001 Full Remote K13 K30 Teletext	
20.000 Per Volt HT420 Hills Meter 10 Amp AC/DC	IT1 CVC 5-8-9         £3.50           Rank T25LE Tripler         £2.00	ITT Small for use with Split Z718 Bush Focus £2.00	33/400 400/400 400/400	Dp NEW Type RC4001 9 CH not 12 £6.00	
1,000 and ohmes range £10 4 ohmes ranges 0-1000 volt AC/DC	Rank 11TCP A823         £3.50           TU 25 30K Rank         £3.00           11 TEZ Rank         £3.00	Diode         50p           Remo TV12SP         50p           1600 Thorn EHT Rec and Lead         50p	394K/400V 20 220/450 40	Di GEC Full Remote Infra-red, 1983 models £15.00	
AEG KT2000/641-005	G9 Philips £4,00 GEC 2110 £4,00	TV14 50p TV20 £1.00	.47/500 22 0.1/600 15 0.1/1200V wire end 20	50 775571404	
Hand Sets	3500 Thorn         £3.00           8500 Thorn         £4.00           9000 Thorn         £7.00	1V45 50p Thorn 14/1500 rec stick 5p	0.1/450 A/C wire end 20 .22/1000 20	Dp         HAND SETS           Dp         24 Buiton CT938 Fulnemote         £5,00           p         32 Buiton CT983 Videotext         £6,00	
Fidelity All Types £15 to £35	9500 Thorn £4.00 9600 Thorn £4.00	TX10.8 Button Unit £10.00	1.047/600 1.15	THORN         E7.00           VCR Front Display Panel         £7.00	
KT3-K30	2040 GEC £3.50 GEC TVM25 Tripler £2.00	TX10/TX100 16 Button £10.00	0.01/1000	DP Large type ITT TV and V C R Handset #15.00	l l
DF-425 DF-550 E.W. 10p	Universal Impler         £5.00           G8 Tripler         £5.00           CVC20-32         £5.00	G11 drawer ASS 2 pots Mains switch and lead £2.00	.47/1000v 65 .47/250V A.C. 10 .001K/1250 10	GFC Ultrasonic 8CH Full Remote £10.00	ł
DF-513 correction 10p DF-557 50p	Decea 80 100 £4,50 Grundig TVK 52 £2,50	K.30, Drawer Ass with pots cable	0.0047/1500 0.005/1500 10	in Local Oluasonje Orič Puli Kemole	Į
DIODES	11TBO Pye 731 £3.00 11THY £4.00	forme £1.00 TX10 Drawer with 8 way pols as £2.50	10 10 11 11 11 11 10 10 10 10 10 10 10 1	P   New Replacement for G11 Ultrasona 1	
Y 126 10p Y 127 10p	D22 for Pye 18" colour portable £4.00 ' LP 1193/63 £4.90 BG 100/41 £3.25	TXto Ex. port with band switch	2n2/1500 15 01/1600 15	p Thorn 4000 insert with 7 buttons £5.00 p Decca RC 11 £14.00	
Y 133 10p Y 134 10p	ERO Tripler print type with foacs PO7 BG2087	PHILIPS BATTERIES	G11.8200/2KV 15 0.1/2KV 20 3n9/2KV 15	Dynatron-Full remote CTV 62, 63, 64	
Y 176 25p Y 179 40p Y 184 25p	T/text ultrasonic rec'r panel £14,60 12-14V. 20 for £5.00 200/for £26.00 GEC 8 touch unit assy complete with all	(Small Types) HAND SETS	0.0015/2KV 10 6n2/2KV 15	P Elitachi infra red handset £18.00	
Y 187 10p Y 190 40p	LC's + pots GII E W. Transformer / 50p	$\begin{array}{c c} SR41 \\ SR43 \\ SR44 \\ SR44 \\ \hline \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\$	2n2/2KV 15 470pt 4KV 10	p 1826 £12.00	
Y 196 30p Y 198 10p	G11 Transient Suppressors 2457 20p G11 Scan Cods	SR54 LR43 C P 25p 25p	7500pf/2KV 3000PF/3000V 4n7/2KV 15		
Y 204/4 8p Y 206 – BY 407 Eqv. 8p Y 208/800 8p	G11 100K tuner pots / 12 for £1 KT3 IF panel / 16 00	LR44 LR54 (5415 25p	$\frac{60.2/2KV}{701/1500V}$ 10	P (I C SAA1250) £14.00 Philips infra red full remote 9 channel for	
Y 210/400 5p Y 210/800 10p	KT3 line OSC transformer £1 KT3/K30 infra-red receiver head £1	CR2032 25p 10 500PF 2KV 20p	8n2/1500V 10 9n1/2000V 10	p 60 CP2605 £6.00 Philips infra red full remote 12 channel tor 60 CP2605 £12.00	
Y 223 605	K30 drawer unit with IC's (home) £10	22/1000 20p 1AA7750 £1.00	0.0082/2000 1/ 15	P K F3/K30 T/Text £15.00	
Y 224/600: 4.8A/600v bridge 50p Y 226 15p Y 227 15p Y 228 1500v 20p	K30 drawer unit with IC's (export) £10	HA411485         £1.00           UPC1373         50p           M50143         £1.00	1800/4KV // 5 4.7nf/5KV // 10	p K13 Power supply £4.00 p GEC intra-red 2236-2026 £4.00	
tat BY229 black 15p Y 299 Red 20p	KT3 receiver panel £8 KT3 huc driver transformer 50m	M491BBI £1.00 M58657P 25p	170/8KV // 10 180/8KV // 10		
Y 229/400 30p Y 299/60p Tag 30p	Pye, K30, GEC, etc. Pre-mains stand-by witch	M50441/550 3p M58658P £1.00	1000/10KV 10	p No RC5150-RC5176-RC5171-RC5177.	
Y 237 5p Y 254 10p	Decca 80/100 IF panel E5 NPN PNP 80V 6 Amp TO66 O.P. Trans. Bair 25p	Delay Line TDK Small Gray 10p TDK Blue Type 50p	4//100         80           Tube Increated 167         £1.0           Rank Scorn Decoder Panel UHF & VHF 2015A         £13.0           UUF 2015A         £13.0           UUF 2015A         £12.0	p         \$60         \$37.56         \$37.66         \$37.16         \$37.177.00         \$p\$         \$special Price         \$£13.00         \$p\$         \$special Price         \$£13.00         \$special Price         \$£14.00         \$special Price         \$£14.00         \$special Price         \$£15.00         \$special Price         \$\$\$15.00         \$special Price         \$	
Y 255	5 button touch tuner BBC1/2JTV12 video with ic SAS 560T/570T	TDK Blue Type 50p	VHF 2015A £13.0 19 of .91 CAP G11 £2.0	0 CVC 15 3 and 7 Day	
Y 406 8p Y 527 20p	Control panel 5 sliders + mains lead £1.50 G11 8 touch button unit replaces old-6 P.B.U. £21	CVC 20-25-30 Mains Switches	Philips K4 CAP 150M/385V 50	p         TX9 with Text         £12.50           TX9 & TX10 button print         £2.00	
Y 407a 10p Y 448 10p	Tube base + base unit for 820 Euro chassis £4.00	RANK & ITT Mains Remote On-Off Switch	oder Panel £3 5 (720R) £1.5	0 I/V & Video Processor 1200 Type £10.00	
Y 527 10p Y 602 10p	GEC Line O/P Trans. & Rec Stick for Portable £3.00	RANK & ITT Remote Switch 2800 ohm G11 Mains Switch	£1.5 50	0 PHILIPS P UNIVERSAL HAND SET £12.00 RC5 K F3 - K45	
YV 26C 10p 247 10p P20G 5p	CVC 20/25/30/35/40 decoder panel £10 CVC 20/25/30/35/40 decoder panel	4 amp Mains Switch GEC Mains Switch 4 amp	25 .30	p We have all parts for Philips Handsets	
RP80G (TX10) 30p K 3102 50n	(untested)         £5           CVC 40/45 IF panel         £5           40K Transducer         50p	KT3 Mainswitch G8 Mains Switch G11 Preh Red LED P/Button for C.H. Cha	€1.0 75 20	p RC5300 £12.00	
VV 28/200 205	PHILIPS NE511N £1.20 LM337M Reg. 30n	RANK TOSHIBA Transductors TPC-2011 Maint Switch ITT Long Turo, Brint	50	D TEXTAT VPF	
BPC35-02 Bridge £1.50 ridge Rec. D35B10 40p	20 GEC Black Spark Gaps £1.00 KT3 Front Panel Control Assy. £2.50	Mains Switch Philip Long Type TAG Mains Switch Philip Long Type TAG 2000 Chassis Fidelity Mains Switch (4 TAG) 2000 Chassis Fidelity Mains Switch (4 TAG)	- 75 75 75	D THORN HAND SETS	
ternational Rectifier EHT Diodes G77	BTW 30/50 50p 0/HV34 6KV 3 for 8p	2000 Chassis Fidelity Mains Switch (4 TAG) 250V/4A White Lorlin Mains Switch KT3-K30-K35 Full Remote Mains Switch (6	60	p 9000 - 9600 TX9 - TX10 - TX100 p Text and Non-Text £10.00	
A/600V Stud Diodes 20p	BTW 92/800R £3 25A473 PNP C/P 10p	Teletext Adaptor Kit TY-500 Panasonic Philips Battery Tester All Types and charger	£1:	2 RC5171 £12.00	
	r		5	K35-K4 HAND SET	

-

Tuner Units           There 14/48 gam           23.10         23.50           Min, UHF Tuner 40/48 gam         23.50           23.10         23.50           24.10         Family with Data Tuner MFC1           25.10         Family with Data Amosfel         23.50           25.01         Family with Data Amosfel         23.50           25.01         Family with Data Amosfel         23.50           25.02         Fusion NUE Zyr737101m         E5           72.06         Family with Data Amosfel         25.50           72.06         Family with Data Amosfel         25.50           72.07         Family with Data Mosfel         25.50           72.06         Family with Data Amosfel         25.50           72.07         Family with Mosta Tuner         55.60           72.07         Family with Mosta Tuner         54.00           ELC 20103         NEW 54.00         ELC 20103         NEW 54.00           ELC 20103         NEW 55.00         25.00         25.00           CHT 2010 HI- Very Small         55.00         25.00         23.10           CHT 2010 HI- Very Small         55.00         25.00         23.10           CHT 2011 HIF         55	Shoeburyness, ESS SAME DAY SE SAME DAY SE SAME DAY SE SAME DAY SE SAME DAY SE SAME DAY SE Southend Tel analysis of the state of the sta	gnton, SEX SS3 8AF ReVICE Technical Information by ts : No Credit Cards e with order £1 Postage overseas 2 London Rd., 2. Fax 0702 338805 orders accepted on official	Dorn         M.1.238/B         64.00           M.1.238/B         62.00           M.1.926/B         62.00           M.18441/P         62.00           MAB84410/P         62.00           MAB84410/P         62.00           MAB84410/P         62.00           MAB84410/P         62.00           MAB84410/P         62.00           MAB8422P-Qui5         62.00           MAB84410P         62.00           MAB84410P         62.00           MAB84410P         62.00           MAB84410P         62.00           MAT811         62.00           MM55011         61.00           MM55011         61.00           MS84018-84         65.00           MS84018-84         65.00           MM52910N-4         75.0           MM53010N         61.0           NH1200B1C         20.0           NA1100	SN76220 SN77622N SN77632N SN77634A SN77634 SN77630 SN77630 SN77630 SN77630 SN77630 SN776630 SN776630 SN776630 SN776630 SN776630 SN776630 SN776630 SN776630 SN776630 SN776730 SN776730 SN776730 SN776730 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN776770 SN77670 SN776770 SN77650 SN77660 SN77660 SN77650 SN77650 SN77650 SN77650 SN77650 SN77650 SN77660 SN77660 SN77660 SN77660 SN77660 SN77660 SN77660 SN77660 SN77660 SN77660 SN77660 SN77660 SN77670 SN77660 SN77660 SN77670 SN7760 SN7760 SN7760 SN7760 SN7760 SN7760 SN7760 SN7760 SN7760 SN7760 SN7760 SN770 SN7760 SN7760 SN7760 SN770 SN7760 SN7760 SN7760 SN770 SN7760 SN7770 SN770 SN770 SN770 SN7700 SN770 SN	12.00         TDA25(6)         75p           11.00         TDA2575A         £1.00           61.00         TDA2575A         £2.00           61.00         TDA2577A         £2.00           61.00         TDA2578A         £2.00           61.00         TDA2584         £2.00           61.00         TDA2581         £2.00           61.00         TDA2581         £2.00           61.01         TDA2581         £3.00           61.01         TDA2581         £3.00           61.01         TDA2581         £3.00           61.01         TDA2811         £5.75           60p         TDA2681         £1.00           75p         TDA2681         £1.00           61.00         TDA2811AO         £1.00           61.00         TDA2840         £2.00           61.00         TDA2840         £1.00           61.00         TDA3852         £3.00           61.00         TDA3848
BFX84         25p         -10,257           BFY50         15p         25D716           BFY52         20p         25D789           BFY50         25p         25D789           BFY90         25p         25D789           BFY40         25p         25D826           BFW41         25p         25D878           BRX43         15p         25D870           BRX43         15p         25D830           BRX483         15p         25D830           BRX56         30p         25D1432           BS856         10p         25D1432	£1.00         B: 4-40         .300           B: 24.85         100           300         B: 24.85         100           8: 0         B: 24.60         25.9           9: 0         B: 24.60         100           9: 0         B: 24.60         100           9: 0         B: 25.46         100           10: 0         B: 55.46         100           10: 0         B: 55.87         100           10: 0         B: 55.87         100           10: 0         B: 55.87         100           10: 0         B: 65.53         100           10: 0         B: 65.57         100           10: 0         B: 65.58         100           10: 0         B: 75.7         100           10: 0         B: 75.7         100           10: 0         B: 75.8         100           10: 0	ItA 11440         Sop           ItA 11440         Sop           ItA 11440         £1,00           ItE F4001         10p           ItE F40051         10p           ItE F40538         30p           ItE F40538         50p           ItE F40538         50p           LA102         £1,00           LA7831         £2,00           LM1111N         £1,50           LM1025=SAA         £2,00           M1024=SAA         £2,00           M1024=SAA         £2,00           M1024=SAA         £2,00           M1024=SAA         £2,00           M1024=SAA         £2,00           M1024=SAA         £2,00	SASS80         75p           SASS80         75p           SASS80         75p           SASS80         75p           SASS80         75p           SASS80         75p           SASS80         75p           SASS80         75p           SASS80         75p           SASS80         2200           SI-37F         £4.000           SI-37F         £4.000           SI-37F         £4.000           SI-37B         £3.000           SI-971B         £3.000           SI-4747         £1.00           TAA731         £1.00           TAA711         £1.50           TAA711         £1.50           TAA721         £1.00           TAA611B         £1.00           TAA7117P         S0p           TA7117P         S0p           TA7240AP         £3.00           TA7240AP         £3.00           TA7250P         £1.00           TA7260AP         £3.00           TA7750P         £1.00           TA7750P         £1.00           TA7750P         £1.00           TA750P         £1.00	SN770566 SN770715N SN770715N SN777071N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN77771N SN777N SN7771N SN777N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N SN77N S	2055         MJE2405         £1.00           756         MJE2801         30p           61.00         MJE2805         50p           20.00         MJE13015         50p           20.00         MJE13015         50p           30p         Sanikron Diode         30p           70p         Power FET         70p           70p         UN88A1*         50p           21.00         A1222         25p         BF181         20p