JULY 1990 TEAL EIR235 (in: VAT) £1-60 THE SERVICE OF THE SERVICE O



De Luxe Component Tester Project The Ferguson FV30's Chopper PSU Philips' BSB Receiver • DX-TV CD Player PS and Control Systems TV Fault Finding • VCR Clinic Test Report • CD Player Casebook



A COMPLETELY NEW DIMENSION IN SOUND QUALITY!

DECODER

★ Fully tested and aligned ★ Ready to install into almost any modern colour TV set

The Maplin NICAM 728 Decoder converts the additional digital code present[†] in the TV signal to a high quality stereo soundtrack with a quality similar to that of Compact Disc.

This fully working system is based upon the Toshiba NICAM chip set, and comes ready assembled.

[†]Currently being transmitted from Crystal Palace, Emley Moor, *Wenvoe, **Winter Hill, **Mendip and ***Black Hill.

Upgrades almost any modern colour TV setno need to purchase a new TV set or VCR!

* From April, **From May, ***From June according to IBA schedule

- Features
- ★ Single + 12V power requirement
- ★ Automatic audio switching (Mono-Stereo-Bilingual)
- * British Design
- ★ Reverts to FM audio if NICAM is not present
- High Quality Optimum Performance without any additional IC's

FNON

★ NIĆAM mode indicators



British

The World's most advanced high quality stereo system for landbased television!

TELEVISION ENGINEERS This price available to trade only, ring 0702 554171 and quote AM00A special 250 off dea

PLUS VAT EACH

554171 and quote AM00A special 250 off deal reference: Television. Trade: 1 off - £113, 10 off - £75, 50 off - £69.50, *250 off - £60 plus VAT each. Normal Retail Price £129.95 (lnc. VAT) each (Order Code AM00A)


Initial availability limited – book your orders now!



All items subject to availability, all items will be on sale in our shops in Birmingham, Bristol, Leeds, Hammersmith, Edgware, Manchester, Nottingham, Newcastle-upon-Tyne, Reading, Southampton and Southend-on-Sea.

Issues 34, 35 & 36 of the Maplin Magazine contain full details of the NICAM decoder and the NICAM TV tuner projects. Order codes: XA34M price £1.00, XA35Q price £1.20, XA36P price £1.20.

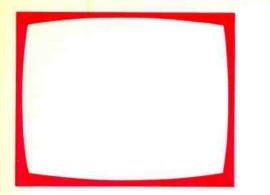★ Build-it-yourself NICAM decoder in kit form; order as LP02C £99.95



TELEVISION

July 1990

Vol. 40, No. 9 Issue 477

On sale June 20th

COPYRIGHT

© IPC Magazines Limited, 1990. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

INDEXES AND BINDERS

Indexes to Vols. 36 and 37 are available at 80p each from the Editorial Office (address above).

Binders that hold twelve issues of *Television* are available for £4.50 from Television Binders, 78 Whalley Road, Wilpshire, Blackburn BB1 9LF. Make cheques out to "Television Binders".

SUBSCRIPTIONS

Annual subscription £20 UK, £24 overseas by surface mail (air mail rate on application). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BACK NUMBERS

Subject to availability, copies of issues published during the last 12 months are available at £1.80 each from Television, John Denton Services, Unit 13, Thornham Grove, Stratford, London E15 1DN. Please make cheques/postal orders payable to IPC Magazines Ltd.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. Correspondents should enclose a stamped addressed envelope.

this month

677 Leader 678 TV Fault Finding

- Reports from Philip Blundell, AMIEIE, Eugene Trundle, lan Bowden, Chris Avis, Mick Dutton, T.J. Welford, Hugh MacMullen, Stephen Leatherbarrow and Nick Beer.
- 681 The Philips BSB Satellite TV Receiver The STU902 satellite TV receiver was found to be easy to install and capable of providing excellent sound and vision, particularly with RGB connection to the main receiver.
- 682 Teletopics

News, comment and developments.

684 Next Month in Television

685 Ferguson's R and D Activities Ferguson's R and D laboratories at Enfield have now been integrated with Thomson's world-wide network

been integrated with Thomson's world-wide network of laboratories in eight countries.

Joe Cieszynski

Ian Martin

- 686 Servicing CD Players, Part 17 Joe This concluding instalment in the series looks at CD player power supplies and the CPU from the point of view of servicing. With recommendations on tests to make when the CPU chip is suspect.
- 689 De Luxe Component Tester, Part 1 David Botto This easy to build and simple to use tester enables a wide range of components to be checked in conjunction with an oscilloscope to provide the display. Using it to check all the components on a PCB can save much time. It can be used as a signature tester and for continuity tests, and is useful for identifying unmarked components.

696 The Ferguson FV30's Chopper PSU The design of the FV30 represents a shift to a more European approach, in particlar with its chopper power supply. The latter may present a problem to those not familiar with this technique. How the circuit works and how to deal with a dead VCR.

Les Lawry-Johns

Roger Bunney

Nick Beer

J LeJeune

700 CD Player Casebook

The House Husband

- Reports from Mike Leach and Keith H.C. Parker.
- 701 Long Distance Television DX conditions and reception and news from abroad.
- 706 Test Report: Electronic Visuals' Vectorscopes Serious camera/camcorder servicing calls for the use of a vectorscope to set up the circuits. The units available from Electronic Visuals provide excellent performance at an affordable price.
- 707 Test Case 331

708 VCR Clinic

Reports from Philip Blundell, AMIEIE, Eugene Trundle, lan Bowden, Alfred Damp, Stephen Leatherbarrow and Nick Beer.

710 Letters

699

OUR NEXT ISSUE DATED AUGUST WILL BE PUBLISHED ON JULY 18

	فالمحالة الأراد التركي
LinkEAR IC'S Cent ZSA 979 2SA 989 BSp 2SC 1111 25C 2228A 415 60p 2SC 2228 25C 3179 2SC 2228 160p 2SC 2228 25D 160 2SC 2228 25D 160 2SD 180 210p 2SD 1609 25D 1941 500p 2SD 1944 VIDEO HEA TEA.1002 550p 2SA 300 25C 1115 280p 2SC 1116 25D 2228 25p 2SC 2228 25p 2SC 2228 25p 2SC 2228 25p 2SC 2228 25p 2SC 2228	£9.50 £9.40
ULN-2804 170p 25A-1084 100p 25C-1278 110p 25C-226 120p 25C-238 120p 25D-844 200p 25D-1843 100p 25K-197 140p ULN-2804 170p 25A-1085 75p 25C-1278 110p 25C-229 120p 25C-238 120p 25D-844 200p 25D-1843 300p 25K-323 130p ULN-2804 170p 25A-1081 100p 25C-1279 30p 25C-229 120p 25C-329 120p 25D-845 250p 25D-1884 300p 25K-323 130p UPC-16C 160p 25A-1034 190p 25C-1306 30p 25C-229 60p 25C-330 170p 25D-950 250p 25D-1844 300p 25K-323 130p UPC-16C 220p 25A-1034 190p 25C-1306 30p 25C-229 60p 25C-330 170p 25D-950 250p 25D-1844 300p 25K-323 130p UPC-16C 160p 25A-1034 190p 25C-1306 30p 25C-229 60p 25C-330 170p 25D-950 250p 25D-1910 280p 35K-88 70p VS-109/201/202/301/303	£24.00
UPC-555 60p 25A-1104 200P 25C-131 240P 25C-331 40p 25C-331 240P 25C-333 140P 25C-331 240P 25C-333 140P 25C-331 25C-333 140P 25C-331 240P 25C-333 140P 25C-333 140P 25C-331 140P 25C-331 140P 25C-331 140P 25C-331 140P 25C-331 140P 25C-333 140P 25C-331 140P 25C-331 140P 25C-331 140P 25C-331 140P 25C-331 140P 25C-331	£21.00 0 £18.00
UPC-580 300p 25C-138 35p 25C-233 200p 25C-333 80p 25D-879 60p W06 14/800V 23p FERGUSON UPC-589 395p 25C-138 35p 25C-233 240p 25C-333 80p 25D-879 60p W06 14/800V 23p FERGUSON UPC-595 190p 25A-1142 150p 25C-334 150p 25C-340 50p 25D-882 80p BR81D 2A/100V 33p 3V32/JVC HR7655 UPC-595 190p 25A-1152 150p 25C-138 150p 25C-341 150p 25C-341 150p 25C-341 35p 25C-244 35p 25C-341 35p 3V42/44/45/46/47 3V32/JVC HR7655 3V32/JVL HR7655 3V42/44/45/46/47 3V42/44/45/46/47 3V42/34/45/46/47 3V42/34/45/46/47 3V43/34/45/46/47 3V43/34/35/3 3V42/34/45/46/47 3V43/34/35/3 3V42/34/45/46/47 3V43/34/35/3 3V43/34/35/3 3V43/34/35/3 3V43/34/35/3 3V43/34/35/3 3V43/34/35/3 3V43/34/35/3 <t< td=""><td>£34.50 £21.00 £46.50 £36.50</td></t<>	£34.50 £21.00 £46.50 £36.50
UPC-1025 230p 25A.1206 100p 25C.1403 500p 25C.2432 100p 25C.346 150p 25D.800 400p BR34 3A/200V 43p UPC-1025 95p 25A.1208 700p 25C.3437 2100p 25C.3407 150p 25D.800 400p BR34 3A/400V 43p UPC-1028 90p 25A.1208 100p 25C.3437 2100p 25C.3457 200p 25D.817 30pp BR34 3A/400V 43p UPC-1022 90p 25C.1410 150p 25C.3437 210p 25C.3459 250.017 30pp BR34 3A/400V 43p UPC-1032 60p 25C.1419 150p 25C.2407 110p 25C.3466 30p 25D.923 336p BR62 6A/200V 80p UPC-1032 60p 25C.1448 100p 25C.2417 100p 25C.2417 100p 25C.3466 30pp 25D.933 36ph BR251 35A/100V 155p 722.910	710/715/720/721/ £19.00 £29.00 £29.00 £30.00
UPC-1186 Stop 25C-147 125p 25C-2483 120p 25C-373 30p BR354 35A/400V 225p UPC-1187 150p 25C-1373 100p 25C-1475 100p 25C-373 100p 88356 35A/600V 230p UPC-1188 400p 25C-1495 80p 25C-3500 80p 25C-3507 80p 25C-3507 80p 25C-3507 80p 25C-3507 80p 25C-3507 80p 25C-3507 80p 25C-1012 120p 87164 15A/800V 40p VT11/1/4/3/8 1/63 UPC-1200 325p 25A-1318 30p 25C-1517 65p 25C-3567 55p 25C-3676 55p 25C-3676 55p 25C-3676 55p 25C-3677 55p 25C-3677	
UPC (123) 230 bit (120 bit	£38.00 £31.50 £14.00 £19.00 , 8500, 8700, 9300, £16.50
UPC:1368H 425p 5SA.1482 5000 2SC.1481 3000 2SC.2870 600 2SC.389 725 2SD.1111 600 11C253D 20A400V 190p UPC:1378 210p 2SC.1481 300p 2SC.1482 100p 2SC.2778 780 2SD.789 720p 2SD.1111 60p 11C253D 2A4400V 205p NA TIONAL UPC:1378 210p 2SC.1482 100p 2SC.2578 220p 2SD.1138 80p 2SC.1482 100p 2SC.2578 200p 2SD.3138 80p 2SC.1481 80p 2SC.2578 240p 2SC.3811 80p 2SD.1159 90p NV 430/NV 460 NV 430/NV 460 NV 330 NV 366 4 HEAD NV 330 NV 366 4 HEAD NV 366 4 HEAD NV 366 4 HEAD NV 330 NV 360 NV 360 NV 360 NV 360 NV 380 NV 330 NV 380 NV 330 NV 380 NV 380 NV 380 NV 380 NV 380 NV 380	£22.30 £21.00 £28.50 £41.00 £43.50 £50.00 £41.50 £28.00 £41.00 £28.00
ZN-423 100p ZB-784 200p ZB-784 200p <th< td=""><td>£42.00 £28.00 £41.25</td></th<>	£42.00 £28.00 £41.25
ZN-133 1906 25B 72 45p 25C.127 1906 25D.127 1906 71C.45 22p VTC 5000, VTC 5400, VTC 6000, ZN-1034 640p 25B-77 160p 25C.1857 85p 25C.2719 800p 25D.127 1906 71C.45 27p 32p VTC 5000, VTC 5400, VTC 5400, VTC 6000, ZN-1034 640p 25B-775 160p 25C.1877 120p 25D.288 90p 25D.128 300p TIC45 32p VTC 6500 VTC 6500, VTC 5100, VTC 5400, VTC 5400, VTC 5400, VTC 5400, VTC 5100, VTC 510,	£28.00
25A-636 300p 25C-382 120p 25C-1914 40p 25D-545 60p 25D-1379 100p * U341 500p * SHARP 25A-636 50p 25C-454 45p 25C-2814 400p 25D-549 120p 25D-1380 100p * U341 500p * SHARP 25A-636 50p 25C-454 45p 25C-2813 400p 25D-551 400p 25D-1380 100p * * U341 500p * SHARP 25A-636 50p 25C-454 45p 25C-2813 400p 25D-555 500p 25D-1380 100p *	
25A 647 20p 25C 451 30p 25C 427 120p 25D 57 30p 25D 132 150p 25A 648 60p 25C 495 60p 25C 495 60p 25C 495 60p 25C 495 70p 25D 57 53p 25D 132 150p VIDEO LAMPS VC 381, VC 383, VC 387, VC 387	£18.75 100,
25A.747A 600p 25C.633 120p 25C.1981 150p 25C.2929 280p 25D.638 60p 25D.1407 160p 16000 16000 16000 <	SLE1 SLETUP
Z5A.771 130p Z5C.733 Z5p Z5C.2003 Z5p Z5C.2001 Z00p Z5D.661 G0p Z5D.1427 Z80p Z5U Z40p SLF1E Z40p SLF1E Z40p SLF1E Z40p SLF1E Z5D.783 Z5p Z5C.2021 400 p Z5C.783 Z5p Z5C.2004 G0 p Z5C.783 Z30p Z5D.666 70p Z5D.1428 450p SV Z40p SLF1E DSR.4381 FOR SLC 2014 G0 p Z5C.783 Z40p SLF1E DSR.4381 FOR SLC 27 AANGE SL Z40p SLF1E DSR.4381 FOR SLC 27 Z40p SLF1E DSR.4381 FOR SLC 27 Z40p SLF1E DSR.4381 FOR SLC 27 Z40p SL 5100 Z5C.2021 E00 p Z5C.793 Z40p Z5C.793 Z40p Z5C.793 Z40p Z5C.793 Z40p Z5C.793 Z40p SL 5100, SL 3000) Z40p SL 5	£18.00
25A.887 50p 25C.428 25p 25C.2027 450p 25D.476 250p 13.2V CCW 290p TOSHIBA 25A.886 90p 25C.4287 25p 25C.2028 75p 25C.3087 900p 25D.4761 15p 25D.1433 160p 152V CCW 290p TOSHIBA 25A.886 90p 25C.4389 20p 25C.2028 75p 25C.3067 150p 25D.1433 140p 440p *	£17.80
25A.913 200p 25C.941 25p 25C.2056 450p 25C.3077 120p 25D.125 350p 25D.1456 60p * CASSETTE TAPE HEADS * <td>LTD</td>	LTD
25A 950 25A 950 25C 100 25A 950 25C 100 25A 950 25C 100 25A 950 25C 100 25A 950 25C 100 25C 100 25A 950 25C 100 25C 100	EQF

						-		-				-	-	
VCR	FERGUSON	VIDEO MOTORS	40008 S	740		74HC 74HC	253 30	6p 74	LS114	35p	8256 1	200p	75188 75189	55p 55p
PINCHROLLERS		AMSTRAD	4000 4001	13p 740 13p 740	02 18p	74HC 74HC 74HC	258 54	0p 74	LS123 LS124 LS125	85p	8259	220p 280p 400p	75195 75451 75454	185p 40p 65p
AKAI VS9300, VS9500, VS9700,	3292, 3V00, 3V01 150p 3V16, 3V22, 3V23 65p	VCR-7000 REEL MOTOR 1700p FERGUSON & JVC	4002 4006	13p 740 34p 740	04 35 p	74HC 74HC	273 43 279 3	2p 74	LS126	30p 30p	8272 1	200p	75492 8T26	55p 95p
VS9800 280p VS1, VS2, VS3, VS4, VS5, VS6,	3V23 65p 3V29/30 120p 3V31/32 85p	CAPSTAN MOTOR 2100p	4007 4008 4009	13p 740 38p 740 20p 740	06 36p	74HC 74HC 74HC	280 6 283 6	1p 74	LS133 LS136 LS138	30p	8282		8728	110p
VS9, VS10 360p	3V35/36 80p 3V38-39 80p	PU-45979 CAPSTAN MOTOR 1950p	4009 4010 4011		08 25p	74HC 74HC	299 10 354 3	5p 74	4LS139	28p 65p	8284	440p 360p	OPTO	
AMSTRAD	3V42/43 65p 3V44/45 65p	PU-55371V DRUM MOTOR 1950p	4012	13p 74 19p 74	13 30p	74HC 74HC 74HC	365 3	4-p 74	4LS147 4LS148 4LS151	75p	8288	650p 100p	COUPLER	15
VCR4500, VCR4600, VCR4600 Mk2, VCR4700 280p	3V45/54 65p 3V55 65p	PU-46414 REEL MOTOR PU-51381V 2650 p	4014 4016	32p 74	16 40p 17 32p	74HC 74HC	367 3 368 3	6p 74	4LS153 4LS154	31p	8755 1 AY3-1015	400p 290p	_	-
VCR5200 360p VCR7000 360p		NATIONAL	4017 4018	29p 74	120 22p 121 25p 125 15p	74HC 74HC 74HC	374 4	8o 74	4LS155 4LS156 4LS157	36p 36p 22p	SP0256AL2 Z80ACPU	150p	4N25 4N26	50p 50p
FERGUSON	FISHER	REEL MOTOR 1350p MYN-135V5L	4019	14.	130 25p	74HC 74HC 74HC	377 5 386 2	2p 74 0p 74	4LS158 4LS160 4LS161	27p 38p 38p	Z80ADMA		4N27 4N28	50p 50p
3V00, 3V16, 3V22, 3V23 280p 3V29-30, 3V31-32 280p	V85-7000 245p	FOR NV333, NV366	4021 4022	36p 74	138 32p 142 38p	74HC 74HC	393 4 423 6	7p 74 5p 74	4LS162 4LS163	38p 36p	Z808P10	220p 340p	4N29 4N30	50p 90p
3V35-36, 3V38-39, 3V42-43, 3V44-45, 3V48, 280p	VBS-9000 120p	SANYO REEL MOTOR 630p	4023 4024	250 74	147 60p 150 22p 151 10p	74HC 74HC 74HC	533 6 534 6	5p 74	4LS164 4LS165 4LS166	36p 50p 55p	Z808CTC	200p 320p	4N31 4N32	90p 100p
3V53, 3V54-55, 3V56-57, 3V58-59, 3V64-65, FV10-11, FV12-14	нітасні	4-529V-10800	4025 4026	13p 74 60p 74	454 25p 470 30p	74HC	541 7 563 6	0p 74	4LS168 4LS169	60p 55p	280AS10 280AS10-1 280BP10-2		4N33 4N36 4N37	100p 58p 58p
HITACHI	HIACH	SHARP REEL MOTOR 1350p	4027 4028	29p 74	473 25 p 474 35 p	74HC 74HC 74HC	573 6	8p 74	4LS170 4LS174 4LS175	68p 30p 32p	Z80ADART		4N38	58p
VT11, VT33 280p VT61-62, VT63-64, VT65,	VT-11, VT-33 100p VT-5000 120p	RMTOV 1008 GEZZ	4029 4030 4031	17p 74	475 25p 481 90p	74HC	583 9 595 8	Op 7.	4LS190 4LS191	47p 43p		200p 65p		Sec. 2.
VT86-88, 280p VT110-122, VT120-128, VT130-135,	VT-5500 130p VT-8000 60p	SONY CAPSTAN MOTOR 700p	4032	52p 74	482 60p 485 28p 486 28p	74HC 74HC 74HC	620 11	Op 7. Op 7.	4LS192 4LS193 4LS194	41p 41p 41p	75110	75p 100p	LED DIS	LAYS
VT138-150, VT168,-220 VT5000, VT8000, VT9300,	VT-8500 60p VT-9300 50p	A-6751131A FOR SLC6 CAPSTAN MOTOR 2500p	4034 4035	76p 74 42p 74	489 75p 490 35p	74HC	643 9	10p 7.	4L\$195 4L\$196 4L\$197	44p 45p		110p 95p	MAN.72	115p
VT9500 280p	VT-9500 50p VT-9700 60p	BHF 1100D FOR SLC7	4036 4037	75p 74	492 45p 493 35p	74H0 74H0 74H0	648 12	0p 7	4LS221 4LS240	42p 45p 45p	75154	100p 700p	MAN.74 MAN.464	115p 180p
JVC HR3300, HR3330, HR3360,		VIDEO LAMPS	4038 4039 4040	180p 74	495 48p 497 80p 4107 30p	74H0 74H0 74H0	670 7	5p 7	4LS241 4LS242 4LS243	42p 43p 50p	75182 75183	95p 95p	MAN.891 DL. <mark>74</mark> 7	0 230p 160p
HR3560, HR4100, HR7700 280p HR7200, HR7330, HR7660,	JVC	12V60mA (300mm WIRES) PANASONIC VIDEO LAMPS 60p	4041 4042	36p 74 30p 74	4111 52p 4116 85p	74H0 74H0	C690 11	0-p 7 0-p 7	4LS244 4LS245	40p				
HR7610, HR7650, HR7655 280p HRD110, HRD111, HRD120,	HR-3300, HR-3330, 150p	IDLERS & PULLEYS	4043 4044	36p 74 36p 74	4119 85p 4122 40p	74H(24015 8	5p 7	4LS247 4LS248 4LS249	40p 40p 70p				
HRD121, HRD140, HRD150 280p HRD160, HRD225, HRD455,	HR-3360, HR-3660, HR-4100 180p	REPLACEMENTS	4045 4046 4047	42p 74	4123 20p 4125 40p 4126 45p	74H0	C4017 4	18-p 7	4LS251 4LS253	24p 36p	SOL	DERI	NG IR	ON
HRD565, HRD725	HR-7200 70p HR-7600 80p		4048 4049	27p 74 18p 74	4132 42p 4141 55p	74H0	C4024 3	14p 7	4LS256 4LS257 4LS258	52p 32p 35p	ANTEX XS			ing Iron
MITSUBISHI HS200, HS300, HS301, HS302,	HR-7610 95p HR-7650 75p	6886971 190p	4050 4051	20p 74 38p 74	4145 70p 4153 45p	74H0 74H0	24040 3	14-р 7 18-р 7	4LS259	50p 30p 22p	240Vac Spare Elem			
HS303, HS304, HS310, 280p	HR-7655 90p HR-7700 77p	V-6861482 320p	4052 4053 4054	35p 74	4155 45p 4157 45p	74H0	C4051 8	35p 7 35p 7	4LS266 4LS273 4LS279	44p 33p	ANTEX C			540p
HS320, HS700 NATIONAL	HRD-110, HRD-111, 100p HRD-120, HRD-225		4055	52p 74	4160 50p 4164 50p 4167 35p	74H0 74H0	C4053 8 C4059 8	35p 7 35p 7	4LS280 4LS283 4LS290	88p 51p 26p	Spare Elen	nent for	C15W 240	260p
NV100, NV180, NV300, NV333,	HRD-250, HRD-455, 100p HRD-565, HRD-566, HRD-725,	PU-47752 450p	4060 4063	40p 74 52p 74	4173 50p 4174 60p	74H0	C4066 3	33p 7	4L\$293 4L\$365	26p			_	-
NV340, NV366, NV600, 280p NV777, NV788	HRD-755	PU-51402A 145p TAKE CLUTCH	4066 4067 4068	120p 74	4175 65p 4176 45p 4180 50p	74H	C4078 3	32p 7	74LS366 74LS367 74LS368	31p 28p 30p				
NV230, NV370, NV430, NV460, NV730, NV810, NV830, 280 p	MITSHUBISHI	PU-55373 225p IDLER ARM	4069	13p 74	4180 50p 4182 45p 4192 40p	74H	C4316 10 C4351 1	00p 7	4LS373 4LS374	45p 45p			RING P	
NV850, NV870, NV890, NV2000, NV2010, NV3000, NV7000,		PU-55373-3-8 285p FAST FORWARD IDLER	4071 4072	13p 7/ 13p 7/	4196 40p 4197 45p	74H	C4510 12	20p 7	74LS375 74LS390 74LS393	46p 42p 37p			NG IR	
NV7200, NV7800, NV8600, NV8610, NV8620, NVG14	HS-200 200p	PU-45896C 210p	4073 4075 4076	13p	4393 70p	741	C4515 12	200 7	74LS399 74LS629 74LS641	68p 95p 88p	240Vac		XS25W 240	540p
NVG7, NVG10, NVG12, NVG18 360p	NATIONAL	IDLER 200p	4077 4078	13p H 13p C	NGH SPEED	74H	C4518 C4520	55p 7	74LS642 74LS644	105p 105p	240Vcm		OV Solder	540p
NVG21, NVG25, NVH65 360p PHILIPS		SANYO	4081 4082	13p 74	4HC00 14p 4HC02 14p 4HC03 14p	74H	C4543	75p	74LS645 74LS670 74LS674	105p 62p 310p	Spare Eler	ment for	C15W 240	V 260p
VR6460 280p	NV-300 160p NV-333 135p NV-777 100p	REEL PULLEY 143-0-662T-01201 520p	4085 4086 4089	30p 7	74HC03 14p 74HC04 15p 74HC08 18p	74H 74H	C22106 54 C40104 1 C40105 2	80p 90p	74LS687	250p			_	70
SANYO VHR1100, VHR1300, VHR1500,	NV-777 100p NV-2000 150p NV-3000 160p	IDLER	4093 4094	18p 7- 44p 7-	74HC10 20p 74HC11 14p		S SERIES	- 18 M	C'S 2114	200p				
VHR2300 360p VTC5000, VTC5150, VTC5500,	NV-7000 95p NV-7200 90p	NIDL0005 GEEZ 195p	4095 4098 4099	50p 7	74HC14 26p 74HC20 19p 74HC21 20p	SCI T.T.	IOTTRY	- 1 C	2532 2716 2732	330p 200p 280p	DESO Desolder		RING P	290p
VTC9300, VTCM10, VTCM20 280p	NV-8600 160p	NIDL0006 GEEZ 195p	4501 4502	27p 7	74HC27 20p 74HC30 20p	74L 74L 74L	S01	12n 3	2732A 2764 27C64	300p 240p 550p	Spare No.			60p
SHARP VC381, VC386, VC2300, VC3300,	PHILIPS	REW, PULLEY	4503 4504	55p 7	74HC32 20p 74HC42 30p 74HC51 20p	74L	S03 S04	12p 12p	27128 26256-25	350p 400p	_	_	_	
VC7300, VC7700, VC8300 360p VC9100, VC9300, VC9500, VC9700		A-6706-348-B 400p REW. PULLEY	4500	58p 7	74HC51 20p 74HC73 24p 74HC74 24p	74L 74L	S08	12p 3	41256-12 256DRAM 4116	250p 250p 75p				
VC387, VC481, VC482, VC483, VC486, VC496, VC581 360p	VR-6460 170p		4508 4510	67p 7 32p 7	74HC75 28p 74HC76 28p	74L 74L 74L	S10 S11	12p 12p	4164 6116 6264	150p 180p 270p	SOLDER /	MOP		65p
VC582, VC583, VC585 VC651, VC681, VC685, VC750,	SANYO	SERVICE AIDS	4511 4512	38p 7	74HC77 35p 74HC85 33p 74HC86 29p	74L 74L	S13 S14	20p 24p	6502 6502A	300p 400p		-	_	
VC780, VC781, VC785, VC787 360p		PRODUCTS	4513 4514 4515	65p 7	74HC86 29p 74HC93 50p 74HC107 28p	74L	S15 S20	14p 14p	65C02 6503 6520	930p 570p 170p				
VC793, VCT72	VTC-5000 75p VTC-5300 100p		4516 4517	36p 7 100p 7	74HC109 28p 74HC112 28p	74L 74L	S22 S24	14p 35p	6522 6530	330p 1050p		SOL	DER	1
SONY SLC5, SLC6, SLC7 360p	VTC-5500 95p	FREEZE IT 125p	4519	28p 7	74HC113 28p 74HC123 35p	74L	S27	14p	6532 6545 6551	460p 880p 530p	18 SWG 20 SWG	500g 500g		500p 650p
SLC9, SLC20, SLC24, SLC30, SLC33, SLC44, SLHF100 360p		FOAM CLEANER 120p ANTI-STATIC 120p	4521	86p 7	74HC125 32p 74HC126 33p 74HC131 36p	74L	S30 S32	14p 15p	6800 6802	210p 220p				
SLC33, SLC44, SLHP100 3000 SLF1, SLF11, SLF25, SLF30, SLF60, SLF100	SHARP	AEROKLEANE 100p AERO DUSTER 125p PLASTIC SEAL 115p	4526 4527	38p 7 41p 7	74HC132 33p 74HC133 33p	74L 74L	S31 S38	15p 15p	6803 6808 6809	800p 500p 600p	-			
*****	VC-381/383/386 125p		4528 4529 4532	65p 7	74HC137 62p 74HC138 33p 74HC139 22p	74L	S40 S42	15p 25p 52p	6810 6818 6820	150p 380p 140p	SOL		ING IR	ON
* 75 OHM COX CABLE WITH * * SOCKETS FOR TV TO VIDEO *	VC-6300 150p VC-7300/7700/7750 150p VC-8300 150p	than one Servisol	4532 4551 4553	75p 7 140p 7	74HC147 42p 74HC148 38p	74L 74L	S48 S51	48p 13p	6821 6840 6845	140p 310p 620p			AND	
* BLACK COLOUR 2 METRES * * LONG, ONLY £1 EACH + VAT * * * * * * * * * * * * * * *		be £2.00	4555 4556	29p 7 36p 7	74HC151 32p 74HC153 32p 74HC153 90p	74L 74L 74L	.S55 .S73	15p 24p	6850 8080A	110p 400p	Soldering Spare Sp			200p 40p
VCR BELT KITS		* * * * * * * * *	4557 4583 4584	60p 7 30p 7	74HC155 48 74HC157 34	741	.S74 .S75 .S76	24p	8085A 8086 8088	300p 500p 500p				
AKAI	SONY	★ UNIVERSAL ★ ★ TRIPLERS ★	4585 40100	40p 120p	74HC158 34 74HC160 44	74L	\$78 \$83 \$85	24p 37p	8155 8156 81LS95	360p 360p 120p				
VP-7100 160p VS-1 150p	SL-C5, SL-C6 140	* 450p *	40101	150p	74HC161 44 74HC162 44 74HC163 44	741	.S86 .S90	25p 26p	81LS96 81LS97	130p 130p	1. FL		Y DISC	
VS-2EG 100p VS-4 120p	SC-C7 140 SC-C9 165	******	40103	80p 140p	74HC164 44	74	.591 .592 .593	55p 32p 26p	81LS98 8224 8226	130p 240p 240p	Name		10 in box)	£7.50
VS-4 120p VS-5EG 100p VS-9300 160p	SL-8000-8080 200	+ + + + + + + + + + + + + + + + + + +	40106	35p 50p	74HC166 60p 74HC173 52p	741	_S95 _S96	41p 52p	8228 8243	270p 250p 850p	51/4 inch 31/2 inch		oulk p <mark>ack) 2</mark> (10 in box)	8randed
VS-9300 160p VS-9500 155p VS-9700 160p	TOSHIRA	* SONY ON/OFF *	40108 40109 40110	74p	74HC174 38 74HC175 38 74HC181 180	741	S107 S109 S112	28p 28p 28p	8251	1000p 270p	Name 3 inch CF			£13.00 £2.40
VS-9800 155p		* SWITCHES *	40114 40117	180p 180p	74HC182 601 74HC190 461	, 74	LS113	28p	8253	230p	3 inch CF	_	ve are HO	
AMSTRAD TVR-1-2-3 210p	V-55/57 85	+++++++++	40147 40160	55p	74HC191 55 74HC192 53 74HC193 41		5000 ITE! Please ser	VIS ANI	D QUOTAT P&P and V	AT at 15	ARE GIVEN F 5%. Govt. Col	OR LAR leges, etc	GE QUANT c. Orders ad	cepted
VCR-4600 & Mk 2 210p	V-5475 160		40161 40162 40163	55 p	74HC193 41 74HC194 46 74HC195 46		Quotations Component	given for ts. All va	r large quan alves are ne	titles. Ple ew and t	ase allow 7 da boxed. Prices	avs for de	livery. All bra	ind-new
VCR-4700 210p VCR-5200 210p VCR-7000 80p	V-8600 150		40174 40175	48p 60p	74HC221 80 74HC237 50		evenedility		RAN	_	ATA		ſD	
	PAGES FOR MORE		40181 40182	170p 70p	74HC238 55 74HC240 48 74HC241 47			HOUS	e, Unit	15, PO	P IN CON	MERC	IAL CEN	
			40193	48p	74HC241 47 74HC242 55 74HC243 60		SC	DUTH	081-900	MBLE 2329	Y, MIDDL Telex N	ESEX, 0: 932	ENGLAN	D
🔶 GRAND	ATA BARGAINS	★K30, K35, K40, KT3, KT4 ★ ★ ★ ★ ★ ★ ★ ★	40208	240p	74HC244 44 74HC245 48	p .		Acces	Fi s & Visa Ca	ax: 08 rd accept	1-903 612 ted. Open M	26 Ionday to	Saturday.	
			olu			1						_		

link-up to profits *
FILMNET DECODER
 WITH BUILT IN INTERFACE SWITCHES TO & FROM FILMNET — SKY — NORMAL TV CHANNELS. NO PLUGGING OR UNPLUGGING. COMPLETELY AUTO FIT AND FORGET COMPLETE WITH LEADS POWER ON LED INDICATOR 12 MONTHS GUARANTEE DIRECT FROM MANUFACTURER MEANS EXTRA PROFITS OPERATES FROM EXTERNAL 12v 300ma DC POWER SUPPLY
PLUS VAT CALL OR PHONE: *QUALITY DISCOUNTS 24 HOUR ANSWERING SERVICE.
Link-Up Communications Limited
20 ELMORE GREEN ROAD, BLOXWICH, WALSALL, WEST MIDLANDS WS3 2HW. (0922) 402786
MAKE YOUR INTERESTS PAY! Train at home for one of these Career Opportunities Over the past 100 years more than 9 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home- study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we

	Electronics		TV, Video & Hi-Fi Servicing				
	Basic Electronic Engineering (City & Guilds)		Refrigeration & Air Conditioning				
	Electrical Engineering		Car Mechanics				
	Elec. Contracting/ Installation		Computer Programming				
	GCSE/GCE/SCE over 40 examination subjects to choose from						
I	Name:						
	Address:						
	P. Code						
	International Correspondence Schools, Dept. EGS70, 312/314 High Street, Sutton, Surrey SM1 1PR. Tel: 081-643 9568 or 041-221 2926 (both 24 hours).						

J

VIDEO HEADS DIRECT FROM THE IMPORTERS

5000 41.09 551 17.95 7300 41.09 3300 41.09 3300 41.09 3300 17.95 AVOX 23.21 IY 5/6/7 5/6/7 14.50 8/9 31.37 20 16.57 FUNG 9/8500 9/8500 9.25 SHIBA /31/32 /31/32 17.86 /50/51 17.86 /57/9 9.50 /64 18.80 /73/74 18.80 /73/74 18.80 /20.866 18.80 /20.866 19.04 /20/880A 19.04 /20/880A 19.04 /20/880A 19.04 /20/850Histerie 19.04
7300 41.09 3300 41.09 3300 17.95 SERIES 17.95 AVOX 23.21 Y 5/6/7 14.50 8/9 31.37 20 20 16.57 FUNG 0/8500 9.25 SHIBA /31/32 17.86 //57 /5/57 9.50 //64 /5/8/6 18.80 //73/74 /78/81 18.80 //28/86 0/26/860A 19.04 20/880A 0/28/80A 19.04 20/850
3300 17.95 SERIES 17.95 AVOX 23.21 IY 5/6/7 14.50 8.9 17.95 14.50 17.95 14.50 17.95 14.50 17.95 14.50 17.95 14.50 17.06 17.66 17.07 16.57 1700G 9.25 1718B 17.86 173 /73 17.86 173 /74 18.80 173 /74 18.80 178 20.55 185 18.80 173 /74 18.80 173 /74 18.80 18.9 20.55 185 /86 18.80 18.00 17.86 18.00 19.04 18.00 19.04 19.04 20.80 19.04 20.80
SERIES 17.95 AVOX 23.21 JY 5/6/7 14.50 8/9 31.37 20 16.57 FUNG //8500 9.25 5/HBA //31/32 17.86 //50/51 17.86 //50/51 17.86 //50/51 17.86 //73/74 18.80 .20.55 .20.55 //8/81 18.80 .20.55 .20.55 //8/81 18.80 .20.55 .20.480A 19.04 20/880A 19.04 20.820A 19.04 20/880A 19.04 20.820A 19.04
AVOX 2.23.21 V 5/6/7 14.50 8/9 31.37 20.16.57 FUNG 0/8500 9.25 SHIBA /31/32 17.86 /50/51 17.86 /50/51 17.86 /57 9.50 /64.18.80 0/73/74 18.80 0.73/74 18.80 0.20.55 /85/86 18.80 0.20.55 /85/86 18.80 0.20.80A 19.04 20/880A 19.04 50 21.03
23.21 IV 5/6/7 14.50 8/9 31.37 20 16.57 FUNG 0/8500 9.25 SHIBA /31/32 17.86 //50/51 17.86 17.86 //57 9.50 9.50 //64 18.80 7/3/74 /73/74 18.80 17.86 //78/81 18.80 20.55 //8/86 18.80 00/96 0/20/860A 19.04 20/880A 20/880A 19.04 20/860A
IV 5/6/7 14.50 8/9 31.37 20 16.57 FUNG 0/8500 9.25 SHIBA /31/32 17.86 //50/51 17.86 /50/51 //64 18.80 /73/74 /73/74 18.80 /73/74 //78/81 18.80 0/20.55 //8/81 18.80 0/20.55 //8/81 18.80 0/20.55 //8/81 18.80 0/20.46 //28/80 19.04 20/880A /20/880A 19.04 20.103
5/6/7 14.50 8/9 31.37 20.16.57 FUNG 5/8500 9.25 SHIBA /31/32 17.86 /50/51 17.86 /50/51 17.86 /57 9.50 /64.18.80 /73/74 18.80 1/3/74 18.80 0.20.55 /85/86 18.80 00/96 17.86 000/810A 19.04 20/880A 19.04 50 21.03
5/6/7 14.50 8/9 31.37 20 16.57 FUNG 5/8500 9.25 SHIBA /31/32 17.86 /50/51 17.86 /50/51 17.86 /57 9.50 /64 18.80 /73/74 18.80 20.55 /85/86 18.80 00/96 17.86 000/810A 19.04 20/880A 19.04 20/880A 19.04
8/9 31.37 20 16.57 FUNG 9.25 SHIBA 7.86 //31/32 17.86 //50/51 17.86 //57 9.50 //64 18.80 //73/74 18.80 //73/74 18.80 //73/74 18.80 //73/74 18.80 0/2055 18.80 //28/8 18.80 0/2055 18.80 0/2056 18.80 0/2080A 19.04 20/880A 19.04 20/880A 19.04
20
y/8500 9.25 SHIBA /31/32 17.86 /50/51 17.86 /57 y/64 18.80 /73/74 18.80 /73/74 18.80 .20.55 /85/86 18.80 /78/81 18.80 .20.55 /85/86 18.80 0/0/96 17.86 19.04 20/880A 19.04 208/80A 19.04 20.32 19.04 19.04
y/8500 9.25 SHIBA /31/32 17.86 /50/51 17.86 /57 y/64 18.80 /73/74 18.80 /73/74 18.80 .20.55 /85/86 18.80 /78/81 18.80 .20.55 /85/86 18.80 0/0/96 17.86 19.04 20/880A 19.04 208/80A 19.04 20.32 19.04 19.04
SHIBA /31/32 17.86 //57 9.50 //64 18.80 /73/74 18.80 /73/74 18.80 /78/81 18.80 /95/86 18.80 00/96 17.86 00/96 17.86 000/810A 19.04 20/880A 19.04 50 21.03
/31/32 17.86 //50/51 17.86 //57 9.50 //64 18.80 /73/74 18.80 /78/81 18.80 /78/81 18.80 00/96 18.80 00/96 17.86 00A/810A 19.04 20/880A 19.04 50 21.03
y50/51 17.86 y/57 9.50 y/64 18.80 /73/74 18.80 /78/81 18.80 y/26 18.80 y/26 18.80 y/28/81 18.80 y/28/86 18.80 y/26/86 18.80 y/26/86 17.86 y/26/86 19.04 20/880A 19.04 50 21.03
%57 9.50 %64 18.80 /73/74 18.80 /78/81 18.80
//64 18.80 //73/74 18.80 //78/81 18.80 //78/86 18.80 //78/86 18.80 00/96 17.86 000/810A 19.04 20/880A 19.04 50 21.03
/73/74
\/78/81 18.80 20.55 20.55 \/85/86 18.80 00/96 17.86 00A/810A 19.04 20/880A 19.04 50 21.03
//85/86 18.80 /00/96 17.86 /00A/810A 19.04 20/880A 19.04 50 21.03
00/96 17.86 00A/810A 19.04 20/880A 19.04 50 21.03
00A/810A 19.04 20/880A 19.04 50 21.03
20/880A 19.04 50 21.03
50
CIDICII
00/301
02/310
03/304
18/710
.C.
ERIES
SERIES
ON
ERIES 19.04
IASONIC
00/200 12.43
80 33.98
30/260
50/280
66
70
30
50/460
30 42.03
88
30/770 25.79
77 21.84
80
10/830
50/950 P.O.A
70/890 51.18
70 51.18
18
80
80
80
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37 130 20.05
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37 130 20.05 11/15 21.37
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37 130 20.05
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37 130 20.05 11/15 21.37 14/15 21.37 20/21 33.98 25/28 33.98
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37 130 20.05 11/15 21.37 14/15 21.37 20/21 33.98 25/28 33.98 30/31 20.05
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37 130 20.05 11/15 21.37 14/15 21.37 20/21 33.98 30/31 20.05
80 47.51 7/9 21.57 10/11 21.37 12/120 21.37 130 20.05 11/15 21.37 14/15 21.37 20/21 33.98 25/28 33.98 30/31 20.05
3

Please add VAT and p&p 90p

OMEGA ELECTRONICS CROWN HOUSE, NORTH CIRCULAR RD, LONDON NW10 7PN. MARCLAYCARD VISA TEL: 081-965 5748 FAX:081-965 7813

BUY WITH **G.G.L.COMPONENTS** WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. PO BOX 72, UNIT 7, SOUTH JOHN STREET, CARLISLE, CUMBRIA CA2 5AL BARCLAYCARD **REPUTATION COUNTS WITH US** PHONE (0228) 39693/20358 FAX (0228) 515127 PRICE (£) TYPE PRICE (£) LINE O/P TRANS TRANSISTORS PRICE (£) TYPE CAPACITORS INTEGRATED TYPE BU508AF TDA2577. TDA2578A TDA2578A TDA2581. TDA2581. TDA2581. TDA2594. TDA2594. TDA2594. TDA2595. TDA2600. TDA2605A TDA2655A TDA2655A TDA2655A TDA3330. PRICE TYPE R4090 DECCA 100 8.30 1UF at 250\ CIRCUITS BU508\ 2.95 STR40090... STR50103A STR50103A 7 95 BC107 BC147 15 FERGUSON 1690/1 4 7UF at 250\ 25 PRICE (E) 9.95 BU807 1.30 TYPE 6.50 10UF at 250V 22UF at 250V 33UF at 250V 75 FERGUSON 1790/1 7 95 808264 2.25 AN303 AN305 3.75 3.50 3.95 4.95 2.95 40 BC148 10 FERGUSON TX9. 23.50 STR441 BC303 12 BU908 FERGUSON TX90 (14") AN318 6.95 19.75 STR451 6.95 4.95 **BUT11A** BC32 47UF at 250\ ...65 1.25 AN5620 4.95 FERGUSON TX90 (20") 19.50 100UF at 250V (All Single Ended PCB Type) 2.50 STR454 **BUT12** 2.95 AN7145M HA1339A BC328 FERGUSON TX100 90 STR5412 6.95 20.95 BUX84. R2540... .80 2.35 2.95 5.95 3.50 3.50 3.50 1.95 .70 HA1339A HA1366W BC337 11 STR58041 STR58041 STR6020(KIT). TA7193P 6.95 1 50 -1F 5-5V-Cap FERGUSON TX100 110 20.95 BC338 12 5.75 4.50 1.40 1.85 2 50 FIDELITY ZX2000 14"/20" BC360 35 HA1366WR 5.95 SG264A. T6071V(KIT) DIODES BC54 10 .12.50 HA1376 2.45 TA7205AP (Inc. Mod.). BC547 BC548 BC557 TYPE PRICE 10 T9053V T9054V T9064V T1P29E HA1377 2.95 3.95 FIDELITY ZX3000 14" TA7222P 10 10 10 2.95 BY127 HA1392 2.95 TDA3540 TDA3541 11.50 TA7227 2.95 202 BY133 20 HA139 3.9 TA7270 FIDELITY ZX 22"/26" 22.95 TIP29E TIP31C TIP32C TIP41C TIP42C HA13001 HA13008 BY179 65 4 50 TDA3560 TDA3561A BC558 TBA120AS TBA120U TBA800P TBA810S 45 1.00 12.95 4.95 HINARI CT4/5. 19.95 BY22 1.25 BC639 25 BY222 2 TDA35624 ITT CVC20 8.50 BC640 25 LA1201 45 BY229/800. BY299 BYX55/600 1N4007.... 95 25 TDA3565 TDA3571 B/Q **BD131** 50 ITT CVC25/30/32 LA1230 LA1365 45 3.95 4.75 1.95 3.80 BD132 BD222 BD225 50 ITT Compact 80 PHILIPS 68 2.45 21 95 TIP112H .30 .07 **TBA820** DA3650 s۵ 2.95 2.95 3.20 LA4440 2.75 15/80H. 15/85B .9.95 **TBA820**M 1.25 DA3651 ι Δ4445 2.45 TBA920S 1.95 DA3651A0 PHILIPS G11 18.95 1N5408.. 2 LA AASI 2 45 TBA920S ... TBA950/2X TBA1440G TDA440.... TDA1020... TDA1025T. TDA1025T. BD237 40 40 70 2SC867A 2SC1034 7.75 4.95 3.95 4.65 2.85 3.30 6.95 2.80 2.95 3.95 3.95 2.60 2.25 TDA3652 (Genuine PHILIPS KT3 2.45 1.95 2.90 12.95 R2M LA4461 LA7800 TDA3652 TDA36534 TDA36544 TDA4500 TDA4503 TDA4600/ TDA4600/ TDA4600/ TDA8180 BD238 3.95 5.95 2.95 2.90 3.50 4.95 6.50 2.35 2.95 50 50 70 70 2.95 SKE5E3/10 1.50 PHILIPS K30 19.95 BD2784 2SC1114 2SC1413A 2.95 2.95 2.75 2.40 1.95 ٩Ō BD437 40 ZENER DIODES PHILIPS CTX 14"/16 17.95 LA7801 BD438 BD677 40 2SC1942 2SC3156 BZX61C (1.3 Watt) 3V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 15V, 4V7 M293B1 6.95 3.95 PHILIPS CTX 201 17.95 BD450 BD677 BD701 BD701 65 MC13002 **RBM T20/22A** TDA1037 2SD725 2D 95 95 95 28 MC14497F 450 2.95 1.25 2SD870 TDA1044 SHARP C1410 23.95 20V, 24V, 27V, 30V. 33V 18V SAA1250 3.85 TDA8180 TDA8190 TDA9503 TDA9513 TDA1151 2SD139 36V, 47V, 56V, 62V, 75V 100V, 110V, 120V, 130V. Pkt 4 94 BD807 TDA1170S TDA1180P TDA1190Z 2SD1453 1.80 3.95 BF337 SAA5000/ 2.65 7805 7812 **ON/OFF SWITCHES** 1.00 BF338 .30 .35 2.85 3.25 4.35 3.80 of 5 per value... SAA5010 4.95 4.95 TF 41014 RF422 UPC1031H UPC1031H UPC1181H UPC1182H .1.00 SAA5012 Decca 80/100 7815 7824 BF423 BF458 BF460 BF470 E.H.T. TRAYS TDA1470 25 Ferguson TX9/10 (Rem) . 1.75 SAA5030 5.95 1.70 Continental 20AX Focus 8.95 Continental 30AX Focus 8.95 DECCA 80 720 TDA1506 SAA5050 6.95 1.70 Ferguson TX90 (Rem) 1.75 TDA1510 SAF1039I SL470/1D 2.75 UPC1185F TUNERS TDA1512 3.50 Fidelity AVS Series 1.50 50 70 UPC1230H UPC1365C 4.35 ELC 1043/05 ELC 1043/06 ET548 TDA1515 4.50 Fidelity CTV140. 1.50 2.85 2.90 1.95 1.95 5.95 5.95 5.95 6.95 7.50 DECCA 100 7.35 BF757 TDA1670A TDA1670A TDA1770A TDA1908A TDA1950A SL480 4.20 3.70 1.95 3.95 1.50 1.55 995 1420 950 995 795 1495 1695 995 1195 1195 DECCA 120/130..... ITT CVC20/25/30/32 3.70 4.35 2.95 1.75 7.95 **UPC1378H** Fidelity CTV14R 2.95 BF871 .80 SL490 SL143 UPC1382 6.95 Fidelity CTV14S 2.95 BB103 75 U321 PHILIPS G8 550 PHILIPS KT3 0.55 7.50 7.90 BR303 BT151/800 1 95 U322 U341 U343(coax skt) U343(phono). U344C U411 (Phono). **UP** SI SI 1431 Grundig CUC731 3.50 1 15 **Z80ACPU** 1432 A47 Philips G8 1.35 TDA2002 * PHILIPS SPECIALS BU126 7.95 TDA2003 Philips G11 1.35 **RBM T20/22A** MEMORY BU205 TDA2004 2.90 Philips G11 (Rem) 1.75 **THORN 9000** 8.00 BU208/ 1.45 1.95 1.45 RETENTION UNIVERSAL 5.70 Philips KT3. 1.50 BU2080 U411 (Coax) TD A202 3.20 BATTERIES Philips KT/CTX (Rem) 1.75 BU3264 (43) FUSES TDA2030 TDA2170 1.80 Small(3.95 BU407 1.25 FUSES 20mm A/S: (Pits of 10) 250MA, 315MA, 400MA, 500MA, 630MA, 400MA, 1A, 125A, 16A, 2A, 25A, 315A, 4A, 5A, 63A,8A......120 20mm O/B: (Pits of 10) 500MA, 630MA, 10A, 1A, 2A, 2.5A, 3.15A......60 K459 8.55 9.95 2.9 Large (2.4v) Philips P1 Cass. Deck Philips P6 Cass. Deck Pve G11 (Rem). 1.75 TDA2170 TDA2270 TDA2525 TDA2530 TDA2532 TDA2540 TDA2540 TDA2541 BU4070 1.50 1.35 TV ELECTROLYTICS (46 24.50 RBM T20/22A 3K3 Vol 3.95 BU426A 9.95 11.95 6.95 4.95 8.95 K46 Sony KV1612 (Rem). FIDELITY ZX(220/38 PHILIPS G8(600/300 3.95 BU500 1.95 1.75 1.95 2.50 2.75 3.95 3.95 3.95 **K46**5 Sony KV2022 (Rem) I C SOCKETS 3.95 BU508A **K533** PHILIPS G11(470/250 BU5080 2.20 18 Pin D 18 Tatung 160/161. 1.75 BU526/ RBM T20 A(220/A00) Tatung 165. 1.75 TDA2540. TDA2560. TDA25764 1.35 1.95 28 Pin Dil-Dil 40 Pin Dil-Dil .30 .40 THORN 1690 (4700/25) THDRN 9000(400/400) BU536 BU705 STK5482 STK7308 1.00 Thorn Universal All Video Heads SANYO/FISHER SHARP VIDEO SPARES NV2000/2010 **GEC/HITACHI SPARES** FERGUSON TV SPARES where possible are Konig and carry full Complete Maintenance **VIDEO SPARES** VC8300 TX9/10 Focus Unit TX10 HM6232 .5.95 21.50 HM625 VTC5000/5300 4.70 Kit (Genuine) Cassette Lamp ...70 7.95 Cassette Lamp Loading Roller Pinch Roller ... manufacturers 5,95 .70 1.25 Channel Bank HM9032 Line 0/P Trans TXS .23.50 warranty Pinch Roller Play Idler (Genuine) 3 95 8.50 Pinch Roller 3.95 Line O/P Trans TX10 29.95 **VIDEO SPARES** 1.25 1.25 5.70 **Rewind Idle** 3.50 .1.95 Reel Idler (Genuine) On/Off Switch (Remote) **VIDEO HEADS** V4000/VT8000 Reel Idler (Genuine) Reel Motor (Genuine). 7.95 VC9300/381 24.95 22.95 23.50 Alba 4000 Push Button TX9 Capstan Motor 31.95 Video Head Video Head 17.95 35.00 apstan Motor assette Lamp 29.95 Amstrad VCR4500 Push Button TX10 16.95 2.6 1.95 3.95 3.95 FF/Rew Idler FVHP615. Tuner 14 95 Amstrad VCR4600 NV7000/7200 FE/Rew Pulley .85 Gear Idler Assembly. 5.95 Amstrad VCB7000 24.95 nch Roller 3.95 Complete Maintenance Kit (Genuine) TX90/100 Reel Idler (Genuine) ... Reel Motor (Genuine) Pinch Roller 4.50 Amstrad VCR9000 22.95 17.50 Amstrad VCR9000 Ferguson 3V00/22/29/39. Ferguson 3V32. Ferguson 3V42/44/45/55. Ferguson 3V43. Fisher FVH520/615/720. 4 50 Play Idler Line O/P Trans TX90 14 19.75 5 95 17.50 23.95 14 95 Reel Idle 70 Line O/P Trans TX90 20 Line O/P Trans TX100 90 22.95 Cassette Lamp 19.75 Video Head 24.95 Video Head 47 50 Video Head 47.50 24.95 49.95 24.95 19.95 19.95 3.95 19.95 Pinch Roller V4001/VT9300/9500 VC481 Play Clutch (Genuine) 4.95 20.95 Capstan Motor FF/Rew Idler.... Line O/P Trans TX100 110 31.95 Capstan Motor 22.95 Reel Idler (Genuine) 1 25 SERVICE MANUALS Mains Trans. (TX90) On/Off Switch (Remote) 17.95 1.95 Reel Idler (Genuine) ... Reel Motor (Genuine) 3.95 17.95 Video Head 18.50 Hitachi 8000/9300/9500 1.75 FF/Rew Pulley (All Genuine) Video Head 23 95 Hitachi VT11/33F Push Button TX90 12.95 Pinch Roller .3.95 Ferguson TX9 Complete 27.95 Mitsuhishi HS302 29.95 REMOTE CONTROLS 14.35 Tuner 3.95 Play Idler Ferguson TX10 Complete Ferguson TX85 38.95 SONY SPARES Mitsuhishi 303/310 29.95 Video Head 22.9 Ferguson T725 Ferguson TX9 U/S Basic 14 95 Panasonic NV330.... Panasonic NV333... Panasonic NV366... Panasonic NV370/380 9.95 29 95 Pinch Roller C5/6/7 Rewind Kit C5/7..... Rewind Kit C6..... FERGUSON 3.95 23.35 14.95 34.95 19.50 V4100/VT11E/VT33E Ferguson TX90 Ferguson TX9/10 N/Text **VIDEO SPARES** 12.95 Capstan Motor (VT11E 26,95 Ferguson TX100 18.95 Ferguson TX9/10 Text 12.95 3V00/16/22 Capstan Motor (VT33E) Clutch Assy 29.95 Ferguson 1790/1 Fidelity AVS1600 1 95 Video Head C5/6/7 19.50 Ferguson TX Stereo Text 12.95 Capstan Motor 24.95 7.95 Panasonic NV430 24.95 Drum Motor Pinch Roller 24.95 Ferguson TX100 Text 15.95 Panasonic NV688 44.95 FF/Rew Idler (Genuine) VIDEO BELT KITS Ferguson 3V23 Video Fidelity AVS2000 5.95 3.95 14.95 Panasonic NV730 34.95 Pinch Roller 3.95 Fidelity CTV14R 5.95 Akai VS1/2/3/5..... Amstrad VCR4500 Ferguson 3V31 Video Ferguson 3V35 Video 16.94 Panasonic NV777 29.95 Take-Un Clutch (Small) . 5.65 Video Head 22.95 Fidelity CTV20F 5 95 1.95 Panasonic NV/7/ Panasonic NV788 Panasonic NV2000/7000 Panasonic NVG7/9 Panasonic NVG10/11/15 44.95 16.95 Take-Up Clutch (Large) 5.95 Amstrad VCR7000 1.50 V4005/VT63E Fidelity CTV20T Amstrad VCH /000 Ferguson 3V00/16/22 Ferguson 3V23 Ferguson 3V29/30 Ferguson 3V35/39 Fisher FVH520/615 Ferguson 3V43 Fidelity CTV14R/S 14.95 Video Head 15.95 2.50 Capstan Motor End Sensors (Pair). 15.95 Philins CF1 6.95 24.95 29.95 44.95 39.95 19.50 37.50 27.95 12.95 1 75 Philips CTX-E 2.50 3V29/30 Grundig TP200 12 95 1.80 1.95 1.95 1.95 1.95 Philips CTX-S Capstan Motor Loading Motor 37.95 Pinch Roller 4.95 Panasonic NVG18.... Panasonic NVG20/21/25. Philips VCR6460/6520... Philips VCR6460/6520... Samsung VX510/616 Sanyo VHR1100/1300... Sanyo VHR1100... Sanyo VHR1500.... Sanyo VTC5000/5500.... Sentra 8000... Panasonic NVG18 12.95 Grundig TP400TT 4.50 8 70 Video Head 49.95 Philips KT3 Grundig TP630/650 ITT FS9/FS10 Text ITT RG301/305 Text ITT RG306 Text 12.95 3.50 Philips K35 .4.5 Pinch Roller 15.95 Hitachi 8000 PANASONIC VIDEO Philips KT4/40 5 95 Pilot Lamp ...80 Hitachi 9300 SPARES 2.85 Philips 2A Hitachi VT11 1.95 Reel Idie 14.50 29.95 42.95 NV333/366 2.45 Philips 2B 6.95 Panasonic NV333 Panasonic NV370 1.95 Take-Up Clutch Philips G11 U/S Full Rem Philips G11 I/R Full Rem. 15 95 Complete Maintenance Kit (Genuine) 1.95 42.95 35.00 24.95 23.95 27.50 24.95 Take-Up Idler. 12.95 VIDEO RECORDERS 13.75 anasonic NV730 1.95 Video Head 15.95 Sentra 8000 Sharp VC9300/381/48 Sharp VC581/583/682 12.95 Ferguson 3V44/45 Panasonic NV/30 Panasonic NV2000/2010 Panasonic NV7000/7200 Sanyo VTC5000 Philips G11 I/R Text. 11.95 1 95 Cassette LED Philips KT3/30 N/Text 1.95 12.95 Ferguson 3V46/47/52 11.95 3V35/36 Pinch Boller 3.95 Philips KT3/30 Text Philips RC5 (Genuine) 12 95 Ferguson 3V54/55 11.95 Capstan Motor Play Idler (Genuine) 4 95 Solavox 1000. 12.5 Cassette Housing 25.95 Ferguson 3V59 11.95 Sanyo VTC5300 1.95 19.50 Reel Idler (Genuine) Sony C5/6/7 Sony C20/30 Philips AV5600 Video... Redifusion Mk.4 Text... Redifusion Mk.4A Text Ferguson 3V65 Mains Trans. 21.95 15.95 11.95 Sharp VC7300 2.50 Reel Motor (Genuine) 14.95 22.95 Ferguson FV11 Sharp VC8300 Sharp VC8300 Sharp VC9300 Sony C5/7 13.95 9.95 2.45 Reel Idler Video Head 17 95 Toshiba V9600/V31B 74 95 18.50 2.45 9.95 2.45 Take-Up Clutch Ferguson FV12 NV370/38 2.50 ORDERING 15.75 Philips VR6460 Philips VR6462 Take-Up Idler 1.40 Sony RM604/605/606 .6.50 Complete Maintenance 1.95 Sony RM613/615 Sony C6 15.75 6 50 Please add 75p for p/p U.K. Add 15% VAT to this total. 15.95 Video Head Kit (Genuine) 12,95 Sony RM630/632/635 15 75 Philips VR6467 3.95 VIDEO PILOT LAMPS Pinch Rolle 3V44/45 e Manuals £1.00 p/p each. Export Orders p/p 15.95 Tatung RTP40/43/45. Philips VR6520 6.50 Ferguson 3V23 (Plug) Ferguson 3V29 (Plug) Panasonic NV2000/7200 80 37.95 Reel Idler (Genuine) Capstan Motor Philips VR6542 6 50 Cassette Housing 28.95 Video Head 21.95 charged at cost ery by return on stock Minimum Order £5.00 6 50 **REPAIR KITS** Philips VR6560 8.95 NV730/770 Loading Motor 6.50 8.95 Deliv items

Philips KT3/30 N/Text

Philips KT3/30 Text

12.95

6.50

6.50

Phillips VR6660

Philips VB6760

Complete Maintenance

Kit (Genuine)

.1.95

26.95

TELEVISION JULY 1990

.95 .50

Sharp VC9300


Universal


Take-Up Clutch


Video Head





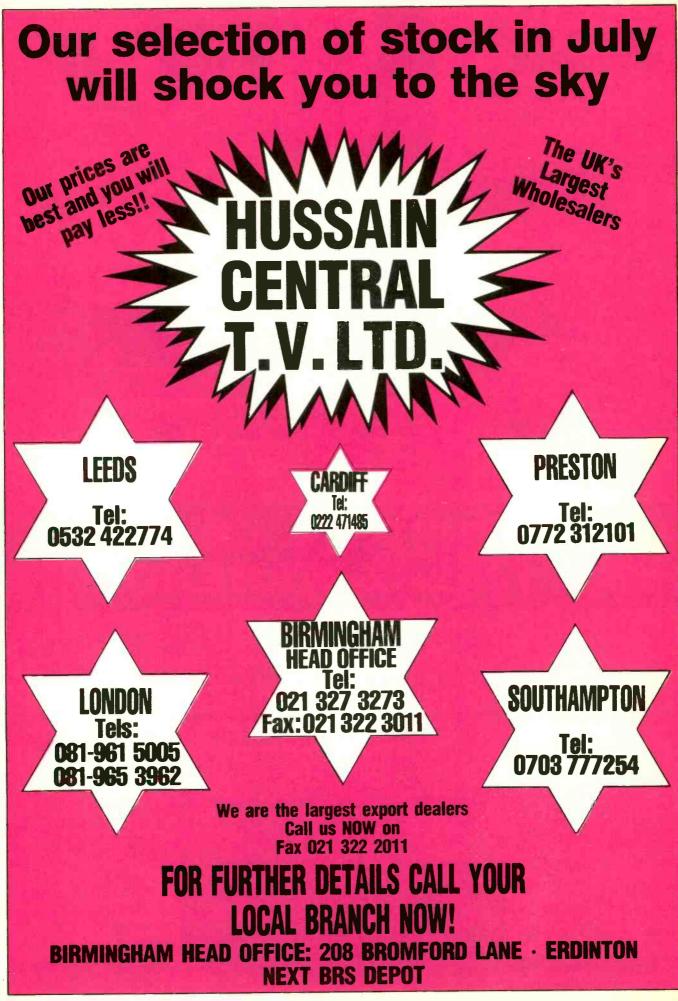

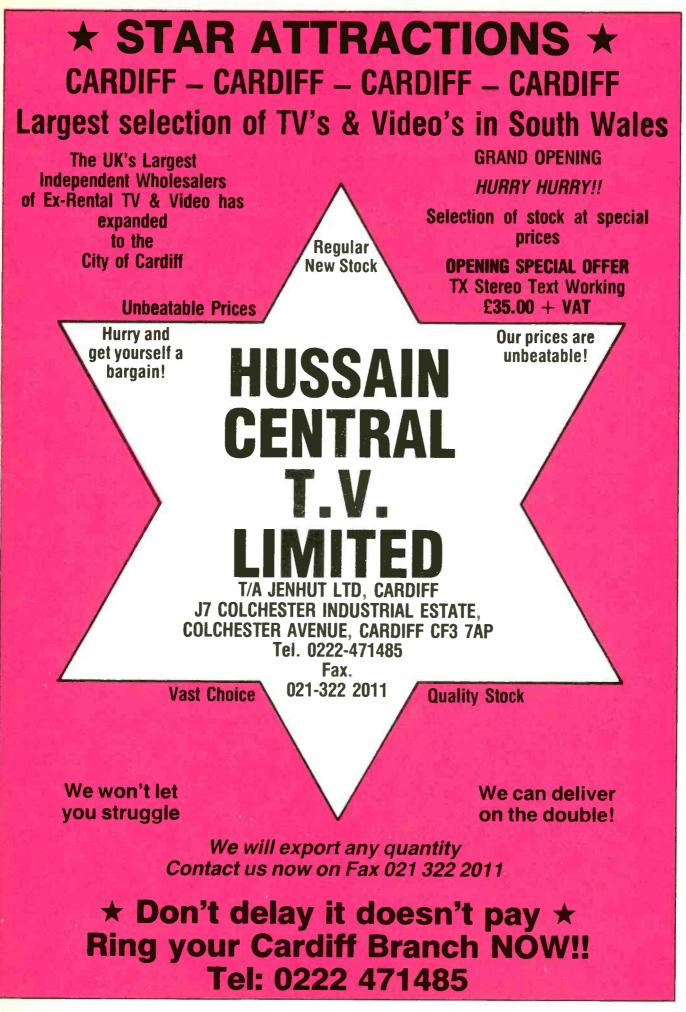

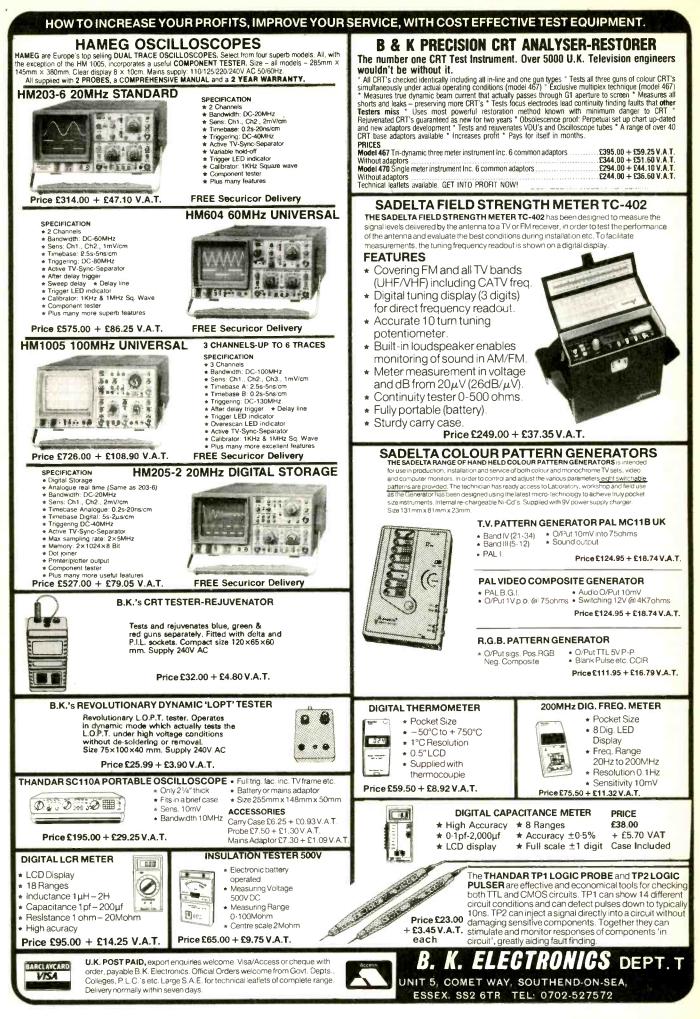

ONE POUND PACKS

All packs are £1 each. Note the figure on the extreme left is the pack ref number and the next figure is the quantity of items in the pack, finally a short description

- 13A spurs provide a fused outlet to a ring main where devices such as a clock must not be here devic vitched off BD9 2 6V 1A mains transformers upright mounting with fixing clamps. 6½ in speaker cabinet ideal for extensions, takes our speaker. Ref BD137. BD11 1 30 watt reed switches, it's surprising what you can make with these – burglar aiarms, secret swit-ches, relay, etc., etc. 25watt loudspeaker two unit crossovers. **BD13** 12
- BD22 BD30 22 Nicad constant current chargers adapt to charge
- almost any nicad battery. Humidity switches, as the air becomes damper the BD32 2
- membrane stretches and operates a micros **BD42** 13A rocker switch three tags so on/off, or change 5
- ver with centre off. 24hr time switch, ex-Electricity Board, automati-cally adjust for lengthening and shortening day, priginal cost £40 each. BD45 1
- BD49 5
- **BD56** 1
- Diginal cost £40 each. Neon valves, with series resistor, these make good night lights. Mini selector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through one poie. Suck or biow operated pressure switch, or it can be operated to perule a concentration such as the concentration of the concentration BD67 be operated by any low pressure variation such as
- water level in water tanks BD103A 1
- 6V 750m Apower supply, nicely cased with mains input and 6V output leads. Stripper boards, each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well BD120 2
- as dozens of condensers, etc. Very fine drills for pcb boards etc. Normal cost BD128 10
- about 80p each. Plastic boxes approx 3in cube with square hole BD132 2
- through top so ideal for interrupted beam switch. Motors for model aeroplanes, spin to start so Moto **BD134** 10
- no switch needs no switch. Microphones inserts – magnetic 400 ohm also act BD139 6
- as speakers. Reed relay kits, you get 16 reed switches and 4 BD148 4
- coil sets with notes on making c/o relays and other gadgets BD149 6
- gaugets. Safety cover for 13A sockets prevent those inquisitive little fingers getting nasty shocks. Neon indicators in panel mounting holders with **BD180** 6
- lens. 5 amp 3 pin flush mounting sockets make a low cost disco panel. BD193 6
- BD199 1
- cost disco panel. Mains solenoid, very powerful, has 1in pull or could push if modified. Keyboard switches made for computers but have many other applications. Electric clock, mains operated, put this in a box and you need never be late. 12V alarms, make a noise about as loud as a car hoom. Sliohtly solied but Ok **BD201** 8
- BD211 1
- BD221 5
- hom. Slightly soiled but OK. Panostat, controls output of boiling ring from RD252 1
- 8D259 50
- Panostal, controls output of boiling ring from simmer up boil. Leads with push-on ¼in tags a must for hook-ups mains connections etc. Oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if titted into attempt BD263 2
- fitted into nattress BD268 1
- Mini 1 wat amp for record player. Will also change speed of record player motor. Tubular dynamic mic with optional table rest Miniature driver transformers. Ref. LT44. 20k to BD305 BD653 12
- 1k centre tapped. 3.5V relays ear **BD548** 2 relays each with 2 pairs changeover
- contacts. 4.7 µf non-polarised block capacitors, pcb BD667 2

There are over 1,000 items in our Catalogue. If you want a complete copy please request this when ordering.

12-220V INVERTER KIT. This kit will convert 12V OC to 220V AC. It will supply up to 130 Watts with a large transformer. As supplied it will about 15 Watts. Heatsink required. Price is £12.00. Ref. 12P17. ill handle

PERSONAL STEREOS. Again customer returns but complete and with stereo headphones a bargain at only \$3.00 each. Our ref. 3P83.

MAINS OPERATED MICROWAVE CONTROL PANEL with touch switches. This unit has a 4 digit display with a built in clock & 2 relay outputs – one for power & 1 for pulsed power level. Could be used for all writches. This unit has a 4 digit display with a built in clock & 2 outputs – one for power & 1 for pulsed power level. Could be used it sorts of timer control applications. Only £6.00. Our ref. 6P18.

EQUIPMENT WALL MOUNT. It is a multi-adjustable metal bracket that could be used for mounting flood light, loud speaker, TV camera, even a fan and on almost any sort of wall or ceiling even between wall and ceiling. Our price only £3. Our ref 3PT2. Or 2 for £5. Our ref SPT52.

STABILIZED POWER SUPPLY KIT 2-25V 2A. A kit for a bench or lab power supply containing PCB, transformer, heatsink and all other components. Short circuit protected. Case required. Priced at £20.00. Ref. 20P25

GEIGER COUNTER KIT. Complete with tube, PCB and all components. 9V operation. Only £39.00. Ref. 39P1.

COPPER CLAD PANEL for making PCB. Size approx 12in long \times 8½in wide. Double-sided on fibreglass middle which is quite thick (about 1/16in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price E1 each. Our ref BDBB3.

POWERFUL IONISER

Generates approx. 10 times more IDNS than the ETI and similar circuits. Will refresh your home, office, shop workroom etc. Makes you feel better and work harder - a complete mains operated kit, case included £12.50. Our ref 12P5/1. REAL POWER AMPLIFIER for your car, it has 150 watts outpu-Frequency response 20hz to 20Khz and signal to noise ratio, better tha 60 db. Has built in short circuit protection and adjustable input level to su your existing car sterce, so needs no pre-am. Works into speakers. Re 30P7 described below. A real bargain at only £58.00. Order ref: 57P1

REAL POWER CAR SPEAKERS. Stereo pair output 100w each. 4-Ohm impedence and consisting of 61/2" wooler, 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair 530.00. Order ref: 30P7.

STEREO CAR SPEAKERS. Not quite so powerful – 70w per channel 3" woofer, 2" mid range and 1" diameter. Again, in a super purpose built shelf mounting unit. Price per pair: £28.00. Order ref. 28P1.

VIDEO TAPES. These are three hour tapes of superior quality, under licence from the famous JVC Company. Offered at only £3 Our ref: 3P63. Or 5 for £11. Our ref: 11P3. Or for the really big user

F20. Our ret 20P20 ELECTRONIC SPACESHIP



Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with really detailed instructions. Ideal present for budding young electrician. A youngster should be able to assemble but you may have to help with the soldering of the compo-nents on the pcb. Complete kit £10. Our ref 10P81.

12" HIGH RESOLUTION MONITOR, Amber screen, beauti-fully cased for free standing, needs only a 12v 1.5 amp supply rechnical data is on its way but we understand these are TTL input. Brand new in maker's cartons. Price: £22.00. Order ref: £2P2.

MICROWAVE TURNTABLE MOTOR. Complete wi sensing electronics that would have varied the cooking lime, window displays etc. Only £5.00. Ref: 5P165.

MAINS FANS. Snail type construction approx 5"×4" mounted on a metal plate for easy fixing. New. £5.00 each. Ref: 5P166.

COMPUTER KEYBOARDS. Brand new uncased. Only £3.00 each.

PANEL METERS. 270 deg movement. New. £3.00 each. Ref: 3P87.

SURFACE MOUNT KIT. Makes a super high gain snooping amplifier on a PCB less than an inch square! £7.00. Ref: 7P15.

CB CONVERTERS. Converts a car radio into an AM CB receiver.

EHT TRANSFORMER. Television type line output transformer, good for high voltage experiments. £2.00 each. Ref: 2P277.

COMPOSITE VIDEO KITS. These convert composite vid separate H. sync, V. sync and video. Price £8.00. Our ref: 8P39

BUSH RADIO MIDI SPEAKERS. Stereo pair. BASS reflex system using a full range 4in driver of 4ohms impedance. Mounted in very nicely made black fronted walnut finish cabinels. Cabinet size approx 8 ¹/₂m wide, 14in high and 31/2in deep. Fitted with a good length of speaker flex and terminating with a normal audio plug. Price £5 the pair plus £1 post. Our ref 50.4.1 5P141

31/zin FLOPPY DRIVES. We still have two models in stock: Single sided, 80 track, by Chinon. This is n the manufacturers metal case with leads and ICD connectors. Price £40, reference 40P1. Also a double sided, 80 track, by NEC. This is uncased. Price £60.00, reference 60P2. Both are brand new.

ASTEC PSU. Mains operated switch mode, so very compact. Outputs: $\pm 12v_25A$, $\pm 5v_5A$, $\pm 5v_5A$, $\pm 12v_5A$, $5v_5A$

VERY POWERFUL 12 VOLT MOTOR. ¹/ard Horsepower Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20. Our ret 20P22.

SINCLAIR C5 WHEELS INCLUDING INNER TUBES AND TYRES 13" AND 16" DIAMETER SPOKED POLY CARBONATE WHEELS ONLY E6 EACH. 13" Ref 6P10, 16" Ref 6P11

PHILIPS LASER

Prilip Control for the second £15, ditto for 12v battery. Also £15. Our r ef 15p2

ORGAN MASTER. Is a three octave musical keyboard. It is beautifully made. has full size (piano size) keys, has gold plated contacts and is complete with nbbon cable and edge connector. Can be used with many computers, request information sheet. Brand new, only £15 plus £3 poslage. Our ref 15P15.

FULL RANGE OF COMPONENTS at very keen prices are available from our associate company SCS COMPONENTS. You may already have their catalogue, if not request one and we will send it FOC with your goods.

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape (41/2m × 41/2m × 13/4m). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan £8 each. Our ref 8P26.

MINI MONO AMP. on p.c.b. size 4" × 2" (app.) Filted volume control. The amplifier has three transistors and we estim-ate the output to be 2W rms. More technical data will be included with the amp. Brand new. perfect condition, offered at the very low price of £1.15 each of 13 for £12.00



Dept. T.V., 250 PORTLAND ROAD, HOVE.

BRIGHTON, SUSSEX BN3 50T. MAIL ORDER TEHNS: Cash, P.O. or cheque with order. Please add E2 50 Service Charge. Monthly account orders accept from schools and public companies. Access & Bicard orders are accepted – minimum E5. Phone (0273) 734648 or 033500. Fax 0273 23077.

POPULAR ITEMS - MANY NEW THIS MONTH

JOYSTICKS for BBC, Atari, Oragon, Commodore, etc. All 55 each. State which required

TELEPHONE TYPE KEY PAO. Really first class rear mounting unit. White lettering on black buttons. Has conductive rubbers contacts with soft citck operation. Circuit arranged in telephone type array. Requires 70mm by 55mm cut out and is connected by 10-pln IDC socket. Price: \$2.00 each. Order ref: 2P251.

SUB-MIN PUSH SWITCHES. Not much bigger than a plastic transistor but double pole. PCB mounting. Three for $\mathfrak{L}1$. Dur ret BD688.

AA CELLS. Probably the most popular of the rechargeable NICAD types. 4 for £4.00. Our ref. 4P44.

MINI RADIO MODULE. Dnly about 2 in square with ferrite aerial and solid dia tuner with its own knob. It is a superhet and it operates from PP3 battery and would drive a crystal headphone direct but be better with our mini mono amp. Price £1. Our ret BD716

BULGIN MAINS PLUG AND SOCKET. The old faithful 3 pin with screw terminals. The socket mounts through a 1/2n hole and the mains is broughlin by the insulated ping. Used to be quite expensive but you can have 2 pairs for £1 or 4 of either plug or socket for £1 you could make yourself a neat and compact bench panel with these. Dur ret B0715, B0715S or B0715P.

MICROPHONE. If you want a low cost microphone then just arrived we have a very small hand-held dynamic mic with on/off switch in the handle, its lead terminates with one 3.5 plug and the other a 2.5 plug for remote control. Price only £1. Our ref B0711.

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES 140% 100w pair made by the famous Hitachi Company. Reference 25K413. Only £4 the

Available in H pack, Ref: 2SJ99 and 2SK343, Ref. 4P51.

TIME AND TEMPERATURE LCO MODULE. A 12 hour clock a Celsus and Fahrenheit thermometer a too hot alarm and a top cold alarm. Approx 50×20 mm with 12, 7mm digits. Requires 1AA battery and a lew switches. Comes with full data and dagram. Price 56:00. Our ref: 9P.

REMOTE TEMPERATURE PROBE FOR ABOVE. £3.00. Our ref: 3P60.

600 WATT AIR OR LIQUIO MAINS HEATER. Small coil heater made for heating air or liquids. Will not corrode, lasts for years. Coil size 3in x 2in mounted on a metal plate for easy fixing. 4in dia, Price £3.00, Ref; 3P78 or 4 for £10,00, Dur ref; 10P76

EX-EQUIPMENT SWITCHED MODE POWER SUPPLIES. Various makes and specs but generally + -5, + -12v ideal bench supply. Only £8.00, Our ref. 8P36.

ACORN OATA RECORDER. Made for the Electron or BBC computer but suitable for others, Includes mains adaptor, leads and book. \$12.00. Ret; 12P15.

PFTE COATEO SILVER PLATEO CABLE. 19 strands of .45mm copper will carry up to 30A and is usually indextructure. Available in red or black. Regular price is over £120 per reel. Our price only £20 00 for 100m reel. Ref. 20P21 or 1 of each for £35.00. Ref 35P2. Makes absolutely superb speaker cable!

NEW PIR SENSORS. Infra red movement sensors will switch up to 1000w mains, UK made. 12 month manufacturers warranty, 15-20m range with a 0-10min timer, adjustable wall bracket. Only £25.00. Ref. 25P.

10 MEMORY PUSHBUTTON TELEPHONES. These are customer r sold as seen. They are complete and may need slight attention. Price £6 00. Ref. 6P16 or 2 for £10.00. Ref. 10P77. BT approved.

NON-MEMORY PUSHBUTTON TELEPHONES. Same condition as above with radial £3.00. Dur ref: 3P79 BT approved.

SPECTRUM PRINTER INTERFACE. Add a centronics interface to your Spectrum complete with printer cable for only £4.00. Our ref. 4P52.

SPECTRUM SOUND BOX. Add sound to your Spectrum with this device. Just plug in. Complete with speaker, volume control and nicely boxed. A snip at only £4 00. Dur ref. 4P52.

BBC JOYSTICK INTERFACE. Converts a BBC joystick port to an Atari type port. Price £2.00 Our ref: 2P261

TELEPHONE EXTENSION LEAO, 5mm phone extension lead with plug on one end, socket on the other. White, Price £3.00, Our ref: 3P70 or 10 leads for only £19.001 Ref: 19P2.

LCO OISPLAY, 4¹/2" digits supplied with connection data £3.00. Ref: 3P77 or 5 for £10. Ref: 10P78. CROSS OVER NETWORK. 8 Ohm 3 way for tweeter midrange and wooter nicely cases with connections marked. Only £2.00. Dur ret: 2P255 or 10 for £15.00. Ref

REVERSING LIGHT ALARM. Fits to car reversing light and sounds when reversing. Only £2.00. Our ref. 2P248.

BASE STATION MICROPHONE. Top quality uni-directional electret condenser mic 600r impedence sensitivity 16-18khz – 68db built in chirne complete with mic stand bracket: £15.00. Ref. 15P28.

 $\mbox{MICROPHONE STANO}.$ Very heavy chromed mic stand, magnetic base 4" hlgh. £3.00 if ordered with above mic. Our ref. 3P80.

SOLAR POWERED NICAO CHARGER, 4 Nicad AA battery charger. Charges 4 batteres in 8 hours. Price £6.00. Our ref: 6P3.

HIGH RESOLUTION MONITOR. 9in black and white, uses Philips tube M24/ 306W. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new, £20.00. Our ref: 20P26

SHARP PLOTTER PRINTER. New 4 colour printer originally intended for Sharp computers but may be adaptable for other machines. Complete with pens, paper etc. Price £16.00. Our ref: 16P3.

CENTRONICS ADAPTER KIT for above plotter printer converts it to Centronics compatible. Price is £4.00. Ref: 4P57.

CAR IONIZER UNIT. Improve the air in your car, clears smoke and helps prevent fatigue. Case reg. Price £12.00. Our ref; 12P8.

NEW FM BUG KIT. New design with PCB embedded coll 9v operation. Priced at £5.00. Our ref: 5P158.

NEW PANEL METERS 50UA. Movement with different scales that are brought into view with a lever. Price only £3.00: Ref: 3P81.

STROBE LIGHTS. Fit a standard edison screw light fitting 240V 40/min, flash rate available in yellow, blue, green and red. Complete with socket. Price £10 each. Ref. 10P80 (state colour required).

ELECTRONIC SPEED CONTROL KIT. Suitable for controlling our powerful 12v motors. Price £17.00. Ref: 17P3 (heatsink required).


EXTENSION CABLE WITH A OIFFERENCE. It is flat on one side making it easy to fix and look tidy. 4 core, suitable for alarms, phones etc. Our price only 25.00 for 50m reel. Ref: 5P153.


METAL PROJECT BOX. Ideal for battery charger, power supply etc. Sprayed grey size 8" × 4" × 4¹/2". Louvred for ventilation. Price £3.00. Ref. 3P75.

675

MAINS 15 WATT SOLOERING IRON. Price £3.00. Our ref: 3P65.

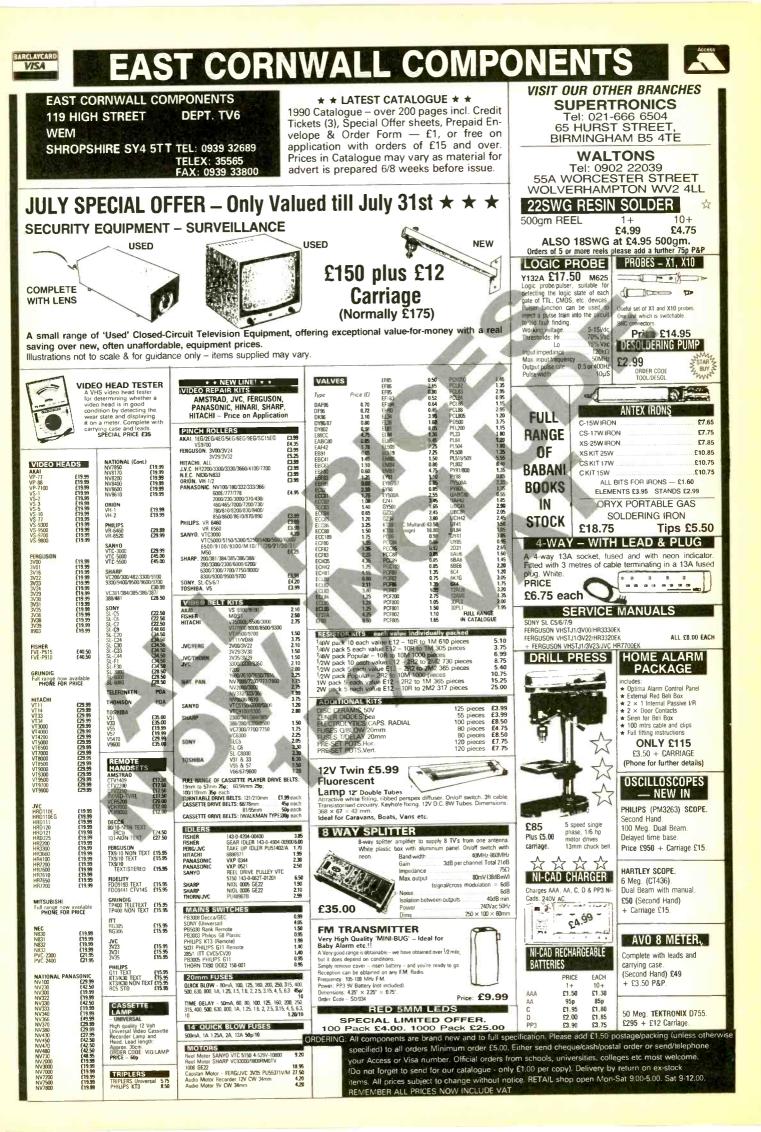SOLDERING IRON STAND. Price £3.00. Our ref: 3P66.



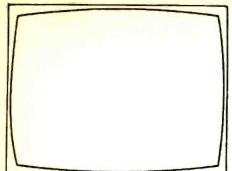

EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 665.

ADVERTISEMENT MANAGER

Kevin Attridge 071-261 6671

SECRETARY

Janet Reeve 071-261 6671

CLASSIFIED ADVERTISEMENTS

Pat Bunce 071-261 5942

ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey 071-261 6035

PUBLISHER

Philippa Gardner 071-261 6408

SUBSCRIPTION ENQUIRIES

044 440 421

COVER PHOTO

This month's cover photograph shows David Botto's De Luxe Component Tester being used witha Scopex oscilloscope (see article on pages 689-694). It was taken at Rawling's Radio's workshop in Bournemouth.

Last month's cover photograph showed the Ferguson TX100 chassis, not the TX10 as stated on page 597.

TELEVISION JULY 1990

Satellite Success

Although it is still early days and the broadcasters are still making substantial losses it's beginning to look as though satellite TV is going to be a success story, at least in the UK. Another two-three years and both Sky and BSB could be breaking even, if not showing a profit. The significant factor is that the public is clearly taking to satellite TV. You see more and more dishes around. There are now well over 800,000 Sky Television installations in the UK. Possibly a significant help has been the trouble-free nature of satellite TV reception. The equipment has turned out to be reliable, apart from a few sillies. There has been nothing to frighten the public, like the expense of tube replacement in the early days of TV and damage to expensive tapes in the early days of the VCR. And the pictures are good. Early suggestions that PAL was not suited to satellite transmission have proved to be false. MAC is significantly better of course, especially with RGB interconnection, but the public has never been all that bothered about the quality of its TV pictures. The important points have always been acceptable programming and low cost. As far as equipment is concerned, satellite TV has turned out to be a bargain.

TELEMISION

That Sky's programming has so far proved to be acceptable to the public is proved by its success in getting people to subscribe to its scrambled services. By early June Sky had something like 540,000 subscribers, a good proportion of the total number of Sky installations. Apart from films, sport has as expected turned out to be a major draw. During England's cricket tour of the West Indies Sky broadcast 175 hours of live cricket. According to Sky, 125,000 Sky TV installations were carried out during the period.

According to Sky, 125,000 Sky TV installations were carried out during the period. Despite the delays over the start of its services BSB seems to have got off to a good start. The company is well funded – the total investment now stands at some £1.35bn – and is expecting to break even in year three or four of its present fifteen year franchise, when it should have around three million subscribers. Public acceptance of satellite TV and take-up of the equipment has turned out to be

Public acceptance of satellite TV and take-up of the equipment has turned out to be greater than in the case of either colour or the VCR in their early days. That alone should indicate success. For most people the cost of subscription to scrambled services is marginal, much the same as renting two-three video cassettes a week, which is common enough practice. It's certainly less than most people spend on other forms of entertainment. One wonders whether this will have an adverse effect on the burgeoning video chains, which have been a substantial growth industry over the last couple of years. One might have thought that the traditional moan about the cost of the TV licence would suggest reluctance to pay for TV. But it's a matter of psychology: a weekly or monthly sum looks less than an annual one.

Once the advertising revenue starts to build up, satellite TV should be made. But will there be enough room for both Sky and BSB, and what effect will they have on the ITV services – and on the still infant cable industry? Provided costs are kept down there should be room for both Sky and BSB. People seem to like the thought of lots and lots of channels, and as a precedent ITV and the BBC have coexisted successfully for about 35 years now. Once the number of satellite installations/hook-ups has increased satellite TV will have the advantage over ITV of a much larger potential audience. That's something which could concern the ITV companies, but the public is unlikely to desert its traditional viewing habits overnight. It will be up to the terrestrial broadcasters to get their programming right. What is beginning to look doubtful is the likelihood of the Ch. 5 service getting off the ground. Cable has the advantage of providing all the channels from a single source, but loses out on MAC. At one time the government, rather naively, seemed to look upon cable as being the vehicle for a great leap forward into an information-based society – or some such notion. The public showed little interest. It does seem to be the simplest way of getting the most channels, but then again the public is used to sticking up an aerial and plugging in and seems to have accepted the dish in the same way. There's growing alarm amongst environmentalists as the number of dishes increases, and many local councils have put their feet down. The Squarial is almost insignificant outdoors however while environmentally friendly dishes have now become available.

Satellite TV has not to date taken off in the same way in the main Continental European countries. It seems that continuing debate over transmission standards and unwillingness to invest in suitable programming are responsible for this. The greater reliance on cable networks could also be a factor. Perhaps they simply need Rupert Murdoch to give them a shove! Be that as it may, SES, the Luxembourg-based company that owns the Astra satellites, has turned out to be a success. It was a considerable gamble to put up a private satellite using what are officially non-broadcasting frequencies. SES is now in profit however and has paid its first dividend.

Further ahead, satellite TV is seen as the way to further technological advances – enhanced TV, high-definition TV and so on. This could be a major factor from the point of view of the electronics industry, but one wonders whether the public will take to such offerings. In the UK, certainly, what the public seems to want is simply lots of channels and acceptable programmes at little cost. Cheap and cheerful you could say. It will need a mammoth sales effort to get HD-TV across. But doubtless someone will come up with a way of doing it at little extra expense, and as usual we'll be left moaning about the lack of profit for the trade!

TV Fault Finding

Philips G110 Chassis

This set would intermittently come on with the picture shifted over and a black vertical bar in the centre of the screen. I finally found that there was a leak from pin 12 of the TDA2579 timebase generator chip to chassis due to a solder bridge under chip capacitor C2460. **P.B.**

Philips 25GR57/63/25B

This set had no sound. I don't know whether the Nicam section was working as our transmitter doesn't have stereo sound yet, but the fault was on the Nicam panel. The mono a.f. signal was present at the input to IC7100 but there was no output. Fitting a new TDA8415 put matters right. **P.B.**

Finlux 1000 Series

We've found the cause of a blown 1.25A fuse to be a dry-joint at one end of LU3. Check this, especially in cases where a replacement fuse appears to cure the fault. If you don't you'll be back sooner or later. **E.T.**

Panasonic Z3T Chassis

This set frequently failed to start up. When the fault was present there was no drive to the power supply control octocoupler D811. In addition the set didn't respond to remote commands as it should have done since there's a separate standby supply for the remote control receiver and the microcomputer control chip. This is a 5V supply that's derived from a small transformer and regulator circuit. A check on the output from this circuit, at TPE2, showed that the voltage was $4 \cdot 4V$ which was not too far down. After checking the regulator circuit we found that the $5 \cdot 1V$ zener diode D1124 was leaky, with only $4 \cdot 4V$ at its top end. This small voltage drop was enough to cause the fault. **I.B.**

Philips KT3 Chassis Edition II

The initial fault caused us no problems – the usual tripping tripler. A replacement produced sound and e.h.t. but no picture. When the setting of the first anode control was advanced we found that there was a blank raster with flyback lines. In went the usual TDA3560 colour decoder chip, and out went my last flicker of self-confidence – there was still no picture. Several voltages around the TDA3560 were very low, the blanking/reference input pin 8 being at virtually zero volts. This led me to the TDA2571Q chip IC367 on the sync panel. It wasn't producing the burst key output at pin 13. Fitting a replacement completed the job. C.A.

Bush 2044

This Amstrad clone had poor sound with erratic flashes on the picture. It's the chassis with the little intercarrier sound panel and a tweak of the quadrature coil restored normal sound. The flashes were caused by the tuner, but an impatient owner meant that we'd no time for an MCES repair. Hang on though, the tuner looks familiar. Yes, it's the one used in the old Ferguson/Baird VCRs (8930 etc.)! A quick exhumation in our scrap graveyard

Reports from Philip Blundell, AMIEIE, Eugene Trundle, Ian Bowden, Chris Avis, Mick Dutton, Nick Beer, Hugh MacMullen, T.J. Welford and Stephen Leatherbarrow

produced an identical tuner and another happy customer. C.A.

Hitachi CPT2050

This multi-standard Salora set had erratic height variations with simultaneous changes from pink to green faces. Pin 12 of the TDA2653 field chip provides a 50/60Hz control voltage for system switching. At 50Hz field frequency the voltage should be 0.2V. It was fluctuating wildly, which confused the decoder. Fitting a new chip cured the height problem and restored pink cheeks. C.A.

Mitsubishi CT2101TX

This set had suffered from line output transformer failure about six months previously. The failure had been spectacular, with a room full of black smoke that came from a pin hole in the transformer's plastic encapsulation. A new transformer restored perfect operation until a few days ago when the customer phoned to say that the picture had gone small all round but was super sharp.

When we collected the set we found that the output from the power supply was 145V instead of 115V. We'd no time to make any further tests since the chopper transistor failed and blew the fuse. A complete rebuild was necessary, changing all the semiconductor devices and checking the capacitors and resistors. We then powered the set via a variac. The output from the power supply reached 115V long before the input was raised to 200V. The set-volts control worked, but its range was limited. Substitution checks were the next step, starting with capacitors. When we came to C918 and C915 (both $33\mu F$) which are in parallel we found that C915 had never been fitted. Replacing C918 provided a cure: a capacitance check showed that it was only 10μ F, hence the insufficient control. If we'd taken more notice of the board rather than the circuit we would probably have found the fault more quickly. Wouldn't it be helpful to have accurate information and M.D. an update service?

GEC C1407H

This colour portable was dead except for a whining noise that came from the power supply. We suspected the regulator chip but the cause of the problem turned out to be the 3V zener diode 2D910. It was shortcircuit. M.D.

Luxor SX9 Chassis

The customer's complaint was that the remote control sometimes didn't work. We put the set on soak test for a long time and confirmed that the remote control system stopped working on several occasions. Another handset was tried, and we found that by switching the set off and on normal operation was restored. One time while the set was on soak test we noticed the width jump in and out. A check around the switch-mode transformer revealed that there were several dry-joints, particularly at pin 1. Repairing these cleared both the width and the remote control problem.

Incidentally if you get one of these sets that switches on and goes straight to standby, check the diodes on the secondary side of the switch-mode transformer. If these are o.k. the problem is almost always due to shorted turns in the line output transformer. M.D.

Saisho CM260TT

This teletext set is fitted with the Fidelity ZX5000 digital chassis. The chopper transistor TR1 was found to be short-circuit between all its legs and the 1.6AT mains fuse was open-circuit. Replacing the BU145A still left us with the dead set symptom however – time to look a little deeper.

The operation of the auxillary 5V supply was found to be all right, but the TIL111 optocoupler IC13 was providing a negative voltage at the input to the chopper control chip IC1 (type UC3844 fitted). Fitting a new optocoupler cured the dead set fault but bearing in mind the nature of the chopper transistor's failure we also replaced IC1.

Ferguson TX90 Chassis (20in)

The problem with this set was occasional partial field collapse. After some very inconclusive cold checks I took some voltage readings. The upper transistor TR104 in the field output stage is biased by a chain of four resistors. The third resistor in this chain, R187 (6.2k Ω), was found to be going open-circuit. When removed its body had a tell-tale ring around it. S.L.

Schneider STT6010

If you find the on/off switch faulty in one of these sets don't panic. The "universal" PC mounting Sony switches fit perfectly. This set is similar to some Telefunken models of late, with a plug-in teletext module at the rear of the set. S.L.

Ferguson TX100 Chassis

The fault with this 110° set was lack of width. Both the width and the EW presets worked and the h.t. was correct at 119V, but the picture could not be made to fill the screen. The 110° version of this chassis has a separate EW/width correction panel fitted: it plugs into the main board. We eventually found that the cause of the trouble was that the width coil had been fitted – it should be present only in the 90° version. Linking it out brought full width. Watch out for that one! S.L.

Grundig CUC70KT

When this set was powered it would make a strained attempt to start then trip. The longest time it stayed on for was one and a half minutes – long enough for us to discover that the h.t. was low and that the line output transistor was hot. We soon found that D471 in the diode modulator circuit had gone short-circuit. Replacing it with a BY299 produced a good picture but there were EW problems. R571 was open-circuit. S.L.

Ferguson TX90 Chassis (20in)

There was excessive height with poor linearity and the height control had minimal effect. The cause of the

TELEVISION JULY 1990

trouble was that D137, a 68V zener diode, was faulty. It didn't measure short- or open-circuit however, nor did it have any reverse leakage. But a replacement cured all the symptoms. S.L.

Fidelity CTV140R

This remote-control set refused to budge from channel one, which is selected at switch on. Voltage checks suggested that the ML923 selector chip was faulty, so a new one was obtained and fitted. There was now a change in the voltages obtained around this i.c., but the basic problem remained the same. C221 $(0.01\mu F)$ was eventually found to be leaky.

On soak test the set developed another fault. The signals would disappear intermittently or, more often, drift a little. Replacing the SL471 chip and the tuner put this right.

Philips K35 Chassis

The symptoms were a blank raster with brilliant, defocused flyback lines. A scope check showed that drive signals were reaching the RGB amplifiers on panel U10. The 155V and 13V supplies were present here but there were no clamp pulses at pins 3, 11 and 18. These 140V pulses come from the line output transformer via R455 (560 Ω) which was dry-jointed. **T.J.W.**

Philips K30 Chassis

We've had two of these sets in recently. The problem with the first one was that the sound remained all right but after about half an hour there were just lines on the screen, with no luminance or chrominance information. We eventually discovered that R8380 (47 Ω) was opencircuit. This resistor feeds 13V to pin 12 of the TDA2571AQ sync/line generator chip. It wasn't burnt in any way.

The second set would periodically switch off then come back on again. The usual faults were not apparent, but after a long time and some very careful listening we found that the bead at the end of the e.h.t. lead in the line output transformer socket was a dry-joint. Resoldering this put matters right. **H.MacM.**

Decca DT9476

Spurious channel changing with this set was caused by occasional flashovers in the focus gap at the c.r.t. base. H.MacM.

Ferguson TX10 Chassis

The display would fade out after a couple of hours or so. After prolonged examination we discovered that the c.r.t. heaters went out. The cause was that the two wrapround connections for the c.r.t.'s heater supply were dirty. Soldering them cured the trouble. I've always hated these wrap-round connections. **H.MacM.**

Panasonic U3/U4 Chassis

A common fault with these sets is that they come on in standby permanently or intermittently when you use the mains switch on the set. We've found that the cause has always been carbonised contacts on relay RY1001 (TSE1827). The cover is easy to remove for cleaning but replacement relays are very reasonably priced. **N.B.**

P. V.	TUBES		1/390936 1. Telex 635562 Griffin G rvice (For P.V.)
SECURITY ALA Ultrange of security products for your own requirem but extensive range: PACKAGE A E105.00 (Typical 3 bed house) 1 Wo zone keyswitched patel 9 Polyprop. bell box/back platesticker 9 Battery/Tamper switch 9 External Sounder 1 Yow passive infra red detectors 1 Five pairs window/door contacts 9 Hotmal sounder 9 U00m 4 core cable and clips 1 Internal sounder 9 Buzger for extilentry timer Panic button	ARM SYSTEMS ents. We list two examples of complete packages from PACKAGE B £150.00 (Larger house or shop) * Commander 5 Zone Digital Panel with built in internal sounder * Light and Sound Unit – Sounder in 'Foam Resis- tant' zinc coated steel box with back and front tamper switch and strobe * Battery * Five Pairs Window/Door Contacts * Three Passive infar aed Detectors * 100m 6 Core Cable & Clips	EXTERNAL LIGHTS DETECTORS WE HAVE A FULL RANGE OF UNITS. SELF- CONTAINED COURTESY LIGHTS, FLU- ORESCENT LIGHTS INCL. DETECTOR 500W FLOODLIGHTS, PASSIVE INFRA RED DETECTORS. PHANTOM FLOOD £49.00 IS A COMBINED EXTERNAL PASSIVE IN- FRA RED DET. AND TUNGSTEN HALOGEN FLOODLIGHT. 15M RANGE WIRED TO MAINS WITH AUTOMATIC SWITCHING DEVICE. EXCELLENT VALUE!	DEGAUSSING COILS EXTERNAL STICK TYPE COIL FOR DEMAGNETISING E27.50 LOADFAST LADDER LOCK PREVENTS LADDERS SLIPPING OFF ROOF RACK. STOPS THEFT E15.99 PER PAIR AVAILABLE ALSO - RANGE OF FIXING STRAP MADE TO ANY REQUIREMENTS We have parts others can't reach!!
IDLERS/TAKE UP CLUTCH ASSY. Dur stock of idlers is extensive. We are adding new types all the time. Send us your old one if you are not sure. We'll match it up. New Types are: [14201] GOLDSTAR 435038A £1.85 [14207] JVC FV10/11/12 PU58645 £2.10 [14085] HITACHI H16876043 £3.30 We have GENUINE parts for Philips, Ferguson, Nat. Pan., NEC, Sony, Hitachi, GEC, Fidelity. JUST ASK!!!	REPLACEMENT VIDEO HEADS As well as the better known types: FEGUSON 3HSSV £10.50 MATIONAL PANASONIC 3HSSN £10.50 We have 1000's of heads which cover most makes. NEW one are: AMSTRAD 6000/6110 (10028) £27.00 HIMARI VXL8/9/10/11 (10028) £27.00 VTV100/200 SAMSUM6 6900 (10302) £27.00 FUNAI (G) 8059-01-19 (100296) £27.00 HITACHI VTR1E/62/64 (10083) £29.00 VT130/138/250 (10081) £32.00	BELT KITS WE HAVE MANY GENUINE INDIVIDUAL BELTS FOR FERGUSON, SONY, HITACHI ETC. AS WELL AS A COMPLETE RANGE OF GOOD QUALITY REPLACE- MENT BELT KITS. COMPLETE VIDEO REPAIR KITS CONTAIN A TOTAL PACKAGE TO REPAIR VIDEOS. CONTAIN A TOTAL PACKAGE TO REPAIR VIDEOS. CONTAIN DLERS, BELTS, TENSION BANDS FOR E.G. 3V35 E19.95 MANY OTHERS TRANSPARENT TEST CASSETTE TO DIAGNOSE FAULTS IN ACTION E4.50	PINCH ROLLERS ALL REPLACEMENT TYPES E2.75 VIDEO TAPES WATCH OUR SPECIAL OFFERS FOR BEST PRICE ON SKC E180E240 VHS. BY POPULAR REQUES WE ARE ABLE TO SUPPLY VIDEO TAPE FOR BET AND PHILIPS 2000 VIDEO S. L750 (Beta) £3.35 VGC 240 £4.00 VGC 480 £5.00 VGC 480
COMPUTER SPARES Got a Commodore 64 or Sinclair Spectrum to repair? We have the bits! Membrane 48k Spectrum £2.50 Membrane 5000000000000000000000000000000000000	NEW VALVES Over 2000 types available for domestic radio, TV, amateur radio and industrial. Send S.A.E. for list. ELECTRONIC KITS For the enthusiast, DIY, or college and school projects. e.g. ROBOT VOICE £8.32 (C RADIO U STROBOSCOPE £17.25 £17.25	REMOTE CONTROLS 100'S OF HAND UNITS IN STOCK. SPECIAL TYPES TO ORDER. ASK!! New TYPES THIS MONTH HITACHI A518612 IR9143 IR9143 IR9144 PANASONIC 2031/3 IR9092 MATSU/SAISHO IR9121 ALL RC12 RC51 SAISH/OMAT/TRIUMPH AMSTRAD RC12	TRIPLERS FULL LIST IN CATALOGUE. SEND S.A.E. UNIVERSAL £4.75 PHILIPS KT3 £7.00 THORN 9000 £8.70 RANK 720 £7.12 LOPTX FIDELITY 14", 20" with Mod Kit £12. HIMARI (Genuine) £18. PHILIPS (Gen C90 (4822-140-10306) £27. 0603-083-001 £225. 0603-083-001 £225. 0603-088-001 £225. THORN/THOMPSON ICC5 £18.
WEAK SIGNAL? LABGEAR BOOSTERS Amplifier to Improve TV/Video Reception (Up to 3 times signal strength) (M7253 E17.00 Amplifier to operate 2 TVs/Video from one aerial (Doubles Signal) (M7243 E15.84 GOOD SIGNAL? Use a SET TDP AERIAL. ANTIFER- ENCE are super sensitive. ENCE are super	CRIMPING TOOL	AERIALS READY FOR FITTING COMPLETE KIT FOR LOFT OR GUTTER FIXING. COAX CONNECTED. INCLUDES 10ELE WIDEBAND AERIAL 3t CRANKED MAST LOFF BRACKET 15H COAX AND CLIPS E9.50 COAX PLUG ALSO EVERYTHING FOR RIGGERS!! F.M. AERIALS FM Stereo 108 range 88-108 MHz ALL ROUNDER OMNI Directional	WANT TD RUN A FEW TELLY'S/VIDEOS, YOU NE A DISTRIBUTION AMP. FROM OUR RANGE OF LABGEAR OR ANTIFERENCE CM7298 WIDE BAND ONE UHF + ONE FILTERED FM IN- PUT. EIGHT OUTPUTS AND FULL OUTPUTS WHICH MAY BE SPLIT TO SERVE DTHER OUT- LETS. MAINS. EST.27 £59.127 £49.12
Olympic Set Top - SEE SPECIAL OFFERS GENUINE SPECIFIC SPARES We can obtain original parts for the following makes to order: JVC E.G. FERGUSON SHARP IOLERS NAT. PAN. 0005GE27 (14275G) £3.30 FIDELITY 0006GE27 (14275G) £3.30 PHILIPS 3V54 Mains Trans £21.90 NEC 3V35 Cap. Motor HITACHI (15152G) £22.29 SONY FV10 Cap. Motor SHARP NECW! SURFACE MOUNTED DEVICES 0.25 Watt Resistor Kit £47.50 86 Valves from IR to 8M2 (10 of each) 0.2 Watt Potentiometer Kit £35.50	TRADE SALES OF TOP QUALITY USED TELEVISIONS AND VIDEOS 14", 16", 20", 22", 26" STANDARD/REMOTE/TELETEXT First Class Condition & Appearance TOP LOADING VIDEOS FRONT LOADING VIDEOS SOME REMOTE CONTROLS Complete with instruction book + leads. TV STANDS £5.00 LITTLE TWISTER TV BRACKET £14.08 ★ SPECIAL OFFERS ★ 180m 75R LOW LOSS COAX £12.95 13A PLUG TOPS (British) (10) £3.50 SKC ALDIO TAPE 6×90 (3pkt) £1.50 CASTLE PETITE ALARM PANEL £36.00 (5 Zone Digital) DIMMY ALARM BOX £3.00	"WORKSHOP MUSTS" Fine Tip 15w Antex Iron 240v £6.20 Stand Tip 25w Antex Iron 240v £6.50 Cordless Gas Iron Portable £15.99 Solder Sucker £5.40 Super Wick Desolder Braid 2mw × 30m Zmw × 30m £11.99 Solder 18 SWG £5.00 22 SWG £6.50 Servisol Switch Cleaner/LWB £1.42 Video Head Cleaner Servisol £1.18 Servisol Switch Cleaner/LWB £1.42 Video Head Cleaner Servisol £1.18 Servisol Sulicone Grease Tube £2.00 Servisol Silicone Compound Sealant £2.98 Test Meters H7700 Bench £15.95 Digital Bench £28.42 Digital Pocket £14.92 Sidecutters 4.5" £2.50 Micro Cutters £5.00 Heavy Duby Sping £5.50 <td>LISTED IN OUR CATALOGUE SEND LARGE S.A.E. PLEASE BATTERIES CABLE CAPACITORS CONNECTORS COMPUTER DISKS ELECTRICAL ACCES. FUSES INTEGRATED CIRCUIT LOPTX LEADS MANUALS PUSH BUTTON UNITS PHONE ACCES. POTENTIOMETERS RELAYS SEMICONDUCTORS STRIPBOARD STYLI SMOKE DETECTORS</td>	LISTED IN OUR CATALOGUE SEND LARGE S.A.E. PLEASE BATTERIES CABLE CAPACITORS CONNECTORS COMPUTER DISKS ELECTRICAL ACCES. FUSES INTEGRATED CIRCUIT LOPTX LEADS MANUALS PUSH BUTTON UNITS PHONE ACCES. POTENTIOMETERS RELAYS SEMICONDUCTORS STRIPBOARD STYLI SMOKE DETECTORS
Ceramic Capacitor Kit £29.95 24Dpcs 24 valves 10pF - 100nF Semiconductor Kit £7.45 10 of each BC807-40, BC817-40, BC846B, BC850C, BC856B, BC860B BC856B, BC860B Matrix Sector	METAL COAX PLUGS (100)	Goods are despatched on the day we receive your	TUBES Days a

Philips' BSB Satellite Receiver

Just over a year ago I wrote in these pages on my experiences in installing an Amstrad SRX200 Astra satellite TV receiver system. After many delays the BSB satellite is now on air and set-top receivers are beginning to become available from the four appointed receiver manufacturers. As a former "Sky Pioneer" and now a BSB "Launch Club Member" I awaited the arrival of yet another set-top box.

The Philips STU902 D-MAC receiver and aerial arrived four days after the official launch of the BSB services. I opened the aerial carton first as I was eager to find out which type had been supplied. It turned out to be the Matsushita flat-plate Squarial – compact dish aerials from Channel Master and Marconi are the other alternatives. Incidentally the Philips receiver is sold with the aerial unspecified, whereas with some brands either type can be ordered at cost.

Description

The STU902 appears to be quite large, with its VCR-sized front panel, but is less than ten inches deep and of light weight. Peeping through the ventilation slots I could see a double-sided PCB with surface-mounted components – and lots of empty space. I was glad to note that the receiver runs cool.

The only control on the front panel is the on/standby button. Accompanying it are two LEDS that indicate standby and stereo reception. All other functions are selected via the remote control handset. Ten channels can be selected, giving provision for the current five BSB channels and five future channels. Standby, TV/sat mode and a range of specific BSB functions are also catered for, and the handset can be used to control the volume and for programme selection with recent Philips TV sets.

The receiver's rear panel has three Belling-Lee type r.f. connectors, for aerial input, r.f. output and satellite TV aerial input. There's also a 21-pin scart socket for AV outputs, wired for both composite video and RGB, utilising both slow and fast blanking, plus stereo audio. Other connectors include jacks for future expansion of the internal data bus and access control module (the part that gives the receiver its identity and authorisation to receive programmes). With a view to the future, the STU902 has an option to provide video outputs with either the current 4:3 aspect ratio or the future 16:9 aspect ratio. This option is again selected via the on-screen menu system. There's no decoder loopthrough, as external descramblers will not be required. Unfortunately there are no separate audio outputs for connection to a hi-fi system.

The Squarial, though larger than the original specification because of BSB's power reductions to cater for the extra channels (there were originally to have been three), seems small. It's solid and a joy to handle in comparison with the Astra dishes. In fact it seemed a pity to put it outside! The tubular metal wall bracket supplied is very easy to attach to a wall, using four 10mm bolts that were not supplied. The Squarial and its alternatives use an F connector for their output and power supply feed. All the BSB channels employ

lan Martin

right-hand circular polarisation, so there's no need for a polariser cable as required with some linearly polarised systems. Although the BSB signals are at higher frequencies than those from Astra, the same type of signal cable can be used, e.g. RG59, as the i.f. output from the LNB is in the same range, around 1GHz.

Installation

And so to the ladder! BSB's Marco Polo satellite is at 31°W while Astra is at 19.2°E, i.e. the satellites are about 60° apart when viewed from the UK. Thus if you know the direction of Astra in your area, Marco Polo shouldn't be too difficult to find. In any case a map showing elevation angles and magnetic azimuth bearings is included in the aerial pack. As I don't have a signalstrength meter - though I do now have a compass - I set up the STU902 and a portable TV set near the proposed aerial fixing point and set the receiver to the set-up mode, using the back panel switch. This useful feature provides a split-screen display, one half showing the actual signal noise and the other an internally generated signal-strength bar graph and noise level indication. A picture was seen almost immediately, sliding sideways across the screen. It was a D2-MAC signal from the TDF-1 satellite. Moving the aerial further westward resulted in the noise disappearing and a welcome to BSB message appearing. The signal was so strong that maximum signal with zero noise could easily be achieved. To get the "centre" position I rocked the Squarial from side to side and up and down, selecting the mid-position. Even covering the aerial with my hands didn't reduce the signal level at the receiver.

After locking the Squarial in position I quickly ran cable round and through the wall, moved the receiver back indoors and connected it to my TV set via a scart lead. BSB's customer service centre was then called. A lady answered and asked me a few questions about the system. Shortly after I'd disclosed the receiver's identity number, which can be called up from the handset, it was authorised for reception and BSB's five channels came in, very loud and very clear.

Performance

Picture and sound quality are excellent via an r.f. link, superb by AV connection and simply stunning when connected to the receiver in RGB form. With a normal picture the extended video response can easily be seen in the RGB mode, the MAC originated picture having none of the PAL coloured "fluff" that snags the sharp edges. The stereo also seems to be better than with Astra transmissions, the digital audio having almost zero noise, though this does depend on the programme content and quality.

I found that in general the system performs very well, the picture and sound quality surpassing anything I've seen before. There are some niggles however. The lack of teletext is a major omission. It's a convenient way of finding out the day's programme schedule with terrestrial TV and Astra. We're promised teletext in the future with the BSB channels however. In the meantime a feature built into the Philips STU902 and other BSB receivers enables you to see details of the current programme, running time and classification rating, as well as those of the next programme. The classification system also works in conjunction with the parental lock, whereby a four-digit secret code can be entered via the handset to lock out certain groups of movies and other programmes.

When the receiver is switched on from standby it comes on in the RGB mode, using the composite video signal for synchronisation. At the same time the scart slow switch and fast blanking (pins 8 and 16 respectively) go high. This means that a TV set connected to the receiver via the scart connectors is forced into the external AV mode. If the TV set accepts external RGB but has no slow switch, the RGB will appear synchronised to the video signal from the set's tuner until the

Teletopics

LASER DISC ASSOCIATION FORMED

Philips has announced the formation of a European Laser Disc Association to promote the video disc system in Europe. Participating companies include Panasonic, Philips, Pioneer, Polygram, Sony, Telemedia Bertelsmann and Warner Home Video. The three main objectives are to create awareness of the Laser Disc System (formerly known as LaserVision or Compact Disc Video), to organise software availability and to maintain compatibility within the Laser Disc standard. According to Philips there are over 9,000 Laser Disc titles available in Japan and the sales of players are expected to reach the million mark this year. US sales are expected to reach 400,000 with over 4,000 titles available. Philips says that the European market is more difficult because of the diversity of languages and tastes.

TELETEXT LATEST

Channel 4 plans to start a teletext timer service next year. The system will work by inserting digital start codes in the Oracle teletext transmissions. To use the system consumers will have to buy a new type of VCR that will contain a teletext decoder and additional circuitry. To operate the timer, the user simply calls up the teletext TV listings page and selects programmes with a cursor: the timer details are stored and the VCR starts to record only when it senses the start code. In addition to its simplicity the system ensures that viewers don't miss programmes that start later than scheduled. The first of the new VCRs are expected to be on sale by the end of the year.

The latest top-of-the-range models from Sony incorporate Nicam decoders and a 200-page teletext memory. The memories are constantly updated, offering the viewer instant access to the 200 selected pages. The 29in. Model KVE2912 has a suggested price of £1,000 while the 25in. KVE2512 sells at around £800.

SATELLITE NEWS

The DTI's Radiocommunications Agency has applied for five additional channels, at present unallocated, to be made available for UK DBS use. Application has been made to the International Frequency Registration TV/sat button on the STU902's handset is pressed. The logic of going into the RGB mode at switch on is understandable from the point of view of offering the best picture quality. But a method of overriding it by presetting the receiver would be helpful, to accommodate customer preferences and TV set variations.

BSB's D-MAC transmission standard provides better quality pictures and sound than any other current source, including terrestrial and satellite TV. Thus if a choice is to be made between the two rival satellite broadcasters BSB and Sky on technology alone, BSB would be the one to go for. In the final analysis however success will go to whichever company offers the better programming. For the present, in my opinion the two systems complement each other. If you're after the BSB service the Philips STU902 can provide excellent reception of it.

Board. The frequencies would be at the same orbital position as the UK's present five allocated channels. It's not expected that any new services using the extra channels would start for several years - the application has been made to provide for possible future growth in satellite TV services in the second half of the decade. To avoid possible interference to other radiocommunications services extensive consultation with other European countries will be necessary.

Amstrad has introduced the first integrated receiver/ decoder, Model SRD400, for use with the Astra satellite. According to Sky Television the overwhelming majority of receiver installations during April were for its own subscription package - a total of 62,414 systems compared to some 14,000 sold by High Street outlets.

Marconi has developed a 60cm "squarish" satellite TV aerial with a 60° pick-up field, wide enough to cover the major satellites broadcasting to Europe including Astra and BSB's Marco Polo. Since no movement of the aerial is required the user would be able to record programmes from one satellite while viewing programmes from another. The aerial would cost around £400 but Marconi does not think production would be worthwhile until combined BSB/Sky receiver/decoders become available.

Now that there are a number of Filmnet decoders on the market many viewers have two or more decoders. Manually changing from one to another can be a chore. JDA Audio Visual (32 Branbridges Industrial Estate, East Peckham, Tonbridge, Kent TN12 5HF - telephone 0622 872 400) has thus introduced Proswitch, an automatic decoder switch which controls up to three decoders of automatic switching type at once. The unit is an electronic switching interface, not just a diode steering arrangement. The trade price is £15 plus leads.

HD-TV

The CCIR, meeting in Dussledorf, failed to agree on an international standard for high-definition TV. While agreement was reached on 27 characteristics, including such things as screen dimensions and colour shades, there was no agreement on the two main features - the number of lines and the field rate.

Philips and Thomson have signed an agreement to devote over £2bn to the development of a complete HD-TV system for Europe. The aim is to have the system in operation by 1995. The agreement includes the companies' work on the Eureka programme but goes far beyond this to include everything from



TV SERVICE SPARES

PHILIPS SPARES

PHILIPS SPAKES C8 CHANNEL SELECTOR £2.50 p.p. £1.50. KT3, K30 PANELS, tested, exchange, sound, power, bridge rect, frame, RGB £7.50 each. Decoder (Non-text) £10.00 p.p. £1.50. G11 6 POS touch tune channel selector (replaces old type) £18.00 p.p £1.80 G11 PANELS (tested), frame, IF, decoder £12.50 each, p.p. £2.00. Scan £15.00 p.p. £2.80. Power tested exchange £18.00 p.p. £2.80. G11 PANELS EX-RENTAL (untested) Scan, Frame, Decoder £2.50 p.p. £2.00. G11 BANEL Service for \$5 0 p. 6 130. GII IF PANELS EARELYTAL (unresteu) scan, France, Decouel 22:50 p.p. 22:00. GII IF PANEL (new) less Tuner £2:50 p.p. £1:30. MANUALS K35, 2A, 2B, CP90 £3:50. KT3 £4:50, CTX-E, CTX-S, CFI £1:50. KT4, K40, 3A £4:50 p.p. £2:50. BACK UP BATT. 2:4V £6:00, 1:2V £3:20 p.p. 80p. K30, KT4, CTX-EHT Lead £3:20 p.p. £4:00. **THORN/FERGUSON SPARES** 8000, 8500, 8800, 9800 Decoder £10.00 p.p. £2.30 9000 Series IF/Decoder tested £10.00 p.p. £2.80. **TX9** RFI Choke L64 £3.50 p.p. 80p. **TX9/TX10** Facia, control panel incl. infra-red receiver £5.00 p.p. £2.00 **TX90TX10** Facia, control panel incl. infra-red receiver £5.00 p.p. £2.00 **TX10** Focus control £8.50 p.p. £1.00. **TX91TX10** Saw filter IF panel £5.00 p.p. 80p. **TX91Utrasonic** remote control panel £7.50 p.p. £2.50. **TX910** Remote & tuning 1508A (incl. SAA5012) £2.50 p.p. £1.80. **TX910** Remote & tuning 1536 (incl. SAA5012, SL471) £3.50 p.p. £1.80. **TX910** Remote & tuning 1536 (incl. SAA5012, SL471) £3.50 p.p. £1.80. **TX910** Sereo Audio Board £3.50 p.p. £1.80. **TX10** Stereo Audio Board £3.50 p.p. £1.80. **TX10** Stereo Audio Board £3.50 p.p. £2.80. **TX90** Mains TX £18.60 p.p. £2.80. **TX90** 14" Chassis complete & boxed (untested) £20.00 p.p. £2.80. **TX90** 16" Dual Standard. New (untested) £25.00 p.p. £2.80.

IC SELECTION										
AN5900	£2.20	SAF1032	£4.50	TA7681AP	£5.80	TDA2577A	£4.80	TDA3566	£5.80	
CNX62	£4.80	SAF1039	£2.20	TA7698AP	£9.80	TDA2578	£3.80	TDA3571	£4.80	
LA4445	£3.00	SL470/471	£4.00	TBA120	£1.20	TDA2579	£3,80	TDA3576	£5.80	
LA7800	£1.80	SL486	£3.20	TBA750	£2.20	TDA2581	£2.20	TDA3650	£8.30	
LA7520	£7.20	SL490	£2.80	TBA920	£2.20	TDA2582	£2.80	TDA3651	£4,20	
LA7801	£3.50	SL1430	£1.80	TBA950	£2.20	TDA2593	£2.80	TDA3653A	£2.90	
M293B1	£5.80	SL1432	£1.20	TCA270	£1.80	TDA2593	£3.80	TDA3653B	£3.20	
M494	£9.80	SN762260N						TDA3654	£3.20	
MC13002P		SN76705	£9.80	TCA800	£6.80	TDA2595	£4.80	TDA4420	£2.20	
MDA2061	£3.80	STK5325	£6.80	TDA1035T	£2.40	TDA2600	£7.50	TDA4421	£3.21	
MDA2062	£3.80	STK5332	£6.80	TDA1037	£1.90	TDA2611A	£1.90	TDA4442	£6.80	
ML237	£3.80	STK5421	£5.80	TDA1044	£2.90	TDA2640	£3.20	TDA4500	£5.80	
ML238	£6.80	STK 5422	£7.50	TDA1082	£3.80	TDA2653A	£3.20	TDA4501	£6.80	
ML926	£4.80	STK5471	£6.50	TDA1170	£2.20	TDA2654	£5.70	TDA4502A	£13.50	
SAA1024	£5.80	STK 5481	£8.80	TDA1180	£2.20	TDA2655B	£8.60	TDA4503	£5.80	
SAA1025	£5.80	STK7308	£10.80	TDAH90Z	£2.20	TDA2670	£3.20	TDA4505	£6.80	
SAA1124	£3.50	STK7348	£10.80	TDA1470	£2.80	TDA2680	£3.80	TDA4600	£3.45	
SAA1250	£3.80	STR441	£7.80	TDA1670A	£3.20	TDA2690	£3.80	TDA4601	£2.80	
SAA1251	£6.80	STR450	£6.80	TDA1701	£3,80	TDA2780	£3,50	TDA4610	£6.80	
SAA3027	£5.80	STR451	£5.80	TDA1770	£3.20	TDA3190	£4.20	TDA5510	£5.80	
SAA5000	£2.80	STR454	£5.80	TDA1870	£6.80	TDA3301	£6.80	TDA8180	£6.80	
SAA5010	£5.80	STR4090A	£8.80	TDA 1908	£2.80			TDA8190	£3.80	
SAA5012	£5.80	STR4090S	£10.50	TDA (940)	£3.20	TDA3330	£3.50	TDA9403	£3.80	
SAA5020	£5.80	STR4211	£6.80	TDA1950	£3.50	TDA3500	£6.80	TDA9503	£3.80	
SAA5030	£5.80	STR 5412	£5,80	TDA2150	£3.20	TDA3510	£9,80	TDA9513	£4.80	
SAA5040	£6.80	STR50103	£8.80	TDA2270	£2.80	TDA3540	£2.50	TEA1009	£2.20	
SAA5050	£6.80	STR 54041	£6.80	TDA2510	£6.80	TDA3541	£3.50	TEA1014	£3.50	
SAA5230	£5.80	STR58041	£13.50	TDA2548	£5.80	TDA3561A	£5.80	TEA2018A	£2.20	
SAB3035	£6.80	STR6020	£5.80	TDA2576A	£3.80	TDA3562A	£5.80	THS1000N2L1	£3.80	
SAB3037	£15.80	TA7680AP	£5.80	TDA2577	£4.80	TDA3565	£3.80	UPC1378	£5.00	
IC p.p 50)p									

 $\begin{array}{l} \textbf{VARICAP TUNERS: } Grundig 8630 \ series \ \textbf{\pounds5.00} \ p.p. \ \textbf{\pounds1.00.} \ U321, \ U322/\\ U341/N, \ \textbf{ELC1043} \ (equiv), \ \textbf{SC4}, \ \textbf{VHF} \ \textbf{NSF203} \ \textbf{\pounds7.80} \ p.p. \ \textbf{\pounds1.80}. \ \textbf{UHF/VHF} \\ \textbf{UV411} \ \textbf{\pounds10.80}, \ \textbf{U343} \ \textbf{\pounds10.80} \ p.p. \ \textbf{\pounds1.00}. \end{array}$

LINE OUTPUT TRANSFORMERS

BUSH T20, T22	PHILIPS KT3 £9,80
DECCA 80, 100	PHILIPS K30, 35 £22, 50
FIDELITY ZX2000, CTV140 £15.50	PHILIPS CTX-E, S £22.50
FIDELITY ZX3000	PHILIPS KT4, 40 £22.50
FIDELITY ZX3000, 22" £22.80	PHILIPS 2A £23.80
HINARI CT4, CT5£24.80	PHILIPS CF1 £32.80
HITACHI CPT1456	PYE 731, 741
ITT Compact 80, 100 £17,89	SONY KV1882 £34.50
ITT CVC5-9, CVC20 £9.80	SONY KV2092, 2096 £34,50
TT CVC25, 30, 32	SONY KV2704 £60.00
FTT CVC45	THORN 1590, 91, 1612, 13, 1712£4.80
TT CVC800, 801, 803	THORN 3787 (NORDMENDE) £9.80
ITT CVC1100£18.50	THORN 3000/3500 Scan, EHT £4.00
FTT CVC1150, 1175. £22,80	THORN 9000, 9600 £9,80
FIT CVC1200, 1201£18.50	THORN TX9
ftt CVC1204£11.50	THORN TX10 (Chopper) £16.50
ITT Digi 3 £19.80	THORN TX85
PHILIPS 320	THORN TX90 14", 20" £19.80
PHILIPS G8	THORN TX100, 110° Green Spot £19.80
PHILIPS G9 £12.80	THORN TX100 90° FST Yellow Spot £21.80

LOPT's p.p. £1.50

 TRIPLERS: THORN 9000 £8.80 p.p. £1.50.

 UNIVERSAL (best quality) £7.80 p.p. £1.50.

 CONTINENTAL TVK & BG RANGE (quote exact no.) replacements £13.80

 DECCA/TATUNG £7.80 p.p. £1.50.


 6/3V CRT Boost Transformers for Colour & Mono £5.90 p.p. £1.40.

 455 CRYSTALS for Remote Control Handsets. 4 for £1.00 p.p. 50p.

 VHE to LHE Converters £29.85 p.p. £2.50.

VHF to UHF Converters £29.85 p.p. £2.50.



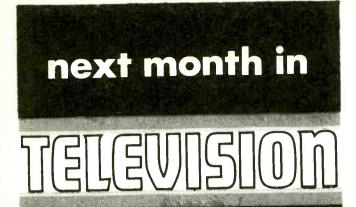

SERVICING THE PANASONIC U4 CHASSIS

The U4 chassis was a successor to the U3 with updating in the remote control, microcomputer tuning and teletext areas - there were no nonremote control versions. Screen sizes are 16-26in. and Model numbers include the TC1631, TC1641, TX2034. TX1642, TC2033, TC2043, TX2034, TC2233, TX2200, TX2230, TX2230/1, TC1632, TC2232, TX2244, TX2636, TX2646, TX2233, TX2234, TX3300 and TX-C21. While the power supply, timebase and signals circuits are reliable there were problems initially with the microcomputer control system. Nick Beer reports.

PAL/SECAM ADAPTATION OF THE TX9

Richard Edeson, G4FBA, discovered that a Mullard technical handbook gives details of the TDA3591 SECAM decoder which works in conjunction with the TDA3560 PAL decoder chip. It's available from Sendz Components on a PCB and the decision was taken to try it out in a Ferguson TX9 chassis. The System was found to work well. So here you are, PAL/SECAM operation of the TX9 with full circuit details.

TEST REPORT:

MUTER TUBE REGENERATOR

Since a duff tube often means that a set has come to the end of its economic life it's essential to be sure that it is in fact defective and that nothing can be done to restore it. The Muter BMR90 is a sophisticated tube tester/reactivator that uses the latest technology in this field. Eugene Trundle tried one out.

COMPONENT TESTER USES

Part 2 of David Botto's De Luxe Component Tester feature provides full details for carrying out tests on a wide variety of components including i.c.s. Also signature and in-circuit testing.

PLUS ALL THE REGULAR FEATURES – including a Test Case item on an ITV reception problem following a BSB satellite TV installation.

Π

Please TELEVISION (£1.60), on July sale

Milel	YOUR COPY UN	- <u>1</u> 8 - 9		
то	•••••••••••••••••••••••••••••••••••••••		(Name of Ne	ewsagent)
Diago	reconvo/deliver	the	August	issue

18th, and continue every month until further notice.
NAME
ADDRESS

complete studios to flat-screen displays and i.c.s.

Thomson is due to start producing 36in. sets with 16:9 aspect ratio screens at its Anagni plant in Italy this autumn. Both Philips and Thomson have set up production lines for 33in. FS tubes in Europe.

TRADE NEWS

The Kingfisher bid for Dixons/Currys has been barred by the government following the Monopolies and Mergers Commission's report on the bid. Philips has taken a 25 per cent interest in Bang and Olufsen. The aim is to benefit from B and O's design and marketing expertise. Toshiba is to increase CTV production at its Plymouth plant from 500,000 to 600,000 sets a year.

The Sentra brand has returned to the market now that Sentra has been taken over by Roadstar UK Ltd. The new address is Roadstar UK Ltd., Roadstar House, Tavistock Industrial Estate, Ruscombe Lane, Berks RG10 9NJ - telephone 0734 321 032.

Poly Peck International plc has increased its holding in Sansui to 70 per cent. Poly Peck's Capetronic and Imperial subsidiaries are now part of Sansui. Capetronic is one of the world's largest original equipment manufacturers of consumer electronics products, with operations in the USA, Taiwan, Hong Kong, Malaysia and China. Imperial produces large-screen colour sets in Italy and distributes a wide range of consumer electronic products. It was founded in Germany in the 30s.

SERVICING NEWS

Sony has established a network of fifteen Video-8 repair centres to provide specialist camcorder servicing. Seven are SES companies (former Sony Service Departments) and a further eight have been chosen from Sony's 115 authorised service companies.

Willow Vale Electronics has published for the trade the second edition of its spare parts listing guide for all Grundig TV, audio and video equipment. In A4 size the perfect-bound catalogue is the most up-to-date Grundig components parts list available. It includes exploded diagrams and complete information on straight service exchange units. Thomson has appointed Willow Vale distributor for its range of consumer electronics spares. For further details contact Willow Vale Electronics, 11 Arkwright Road, Reading, Berks RG2 0LU - telephone 0734 876 444.

A.Z. Electrics has moved to 183 Acre Lane, Northampton NN2 8DX. Telephone 0604 847 800, fax 0604 844 382.

Charles Hyde and Son Ltd. has withdrawn, for policy reasons, from being an approved supplier of spares and components for Sharp UK Ltd. CHS is still able to obtain and supply the popular range of Sharp genuine spares usually required.

SEME's latest catalogue, with 230 pages, features a special video spares supplement for easy reference and also contains details of Fidelity spares. Since Fidelity ceased production some eighteen months ago warranty claims are no longer applicable, but SEME will continue to supply chargeable spares for as long as possible. SEME Ltd., Unit 2E, Saxby Road Industrial Estate, Melton Mowbray, Leics LE13 1BS - telephone 066 465 392.

Adcola has introduced an updated range of desoldering stations known as the 565 series. The units have proved to be virtually impossible to block due to the unique design of both the heating element and the

combined stored vacuum system. They are now static free, following use of a polycarbonate static passive material, type D-FR. For further details apply to Adcola Products Ltd., Adcola House, Gauden Road, London SW4 6LH - telephone 071 622 0291.

3-D TV SYSTEM

A 3-D TV system has been on display recently at laboratories in Covent Garden, London. It produces the depth effect without the need for the viewer to wear special glasses. The principle used is to digitise the programme material, identifying focus points in each field and processing these to produce what are called stereo cues. These activate a special screen in front of the TV set, with the result that the eyes receive slightly different images. For obvious reasons technical information on the system is at present limited.

NEW PANASONIC CAMCORDER

Panasonic has relased details of a new camcorder that incorporates some interesting technology. The following specifications apply to the NTSC version, but Panasonic says that a PAL version would be similar. Model NV-S1 is a VHS-C camcorder weighing just 750g without battery and tape. The new C1 tape loading mechanism is 29 per cent lighter than a conventional mechanism. A lighter head drum and four-layer PCB that incorporates the camera and VCR circuitry contribute to the compactness. Other design features include a new lightweight lens system and a $\frac{1}{3}$ in. CCD imager with 270,000 pixels and the performance of a $\frac{1}{2}$ in. unit.

The electronic image stabilising (EIS) system is claimed to reduce picture shake by up to 15 per cent. Each field is stored in a RAM and analysed during record signal processing to check whether movement between successive fields is due to hand shake or a fast moving object being tracked by the camera. When shake is detected the EIS system cuts off the picture edge and enlarges the stable centre portion to fill the display area.

An 8-bit digital AF system is claimed to offer improved focusing performance. The NV-S1 also offers "snap shot" recording (a five-second still picture) and a still/strobe feature that records a still image every 0.2 sec for picture effects. No UK price has been announced but launch is expected before next Christmas.

Ferguson's R and D Activities

Our May issue leader gave a decidedly misleading impression in suggesting that research and development at Ferguson's Enfield headquarters have come to an end. We have since been briefed on Ferguson's current R and D activities and take this opportunity to put the record straight.

There have been redundancies at Enfield, a total of 104 of whom 70 are leaving the company. The main reason for this is the ending of manufacturing activities at Enfield. Many of those who have left were engaged in technical back-up activities for the plant, work which is obviously no longer required. Some of those made redundant at Enfield have moved to a new applications laboratory which has been set up at Ferguson's Gosport plant, where all manufacturing activities are now centred. A further sixty engineers at Gosport are engaged in test gear, production engineering, etc.

Research and development will continue at Enfield, as part of an eight-laboratory network operated by Ferguson's parent company Thomson Consumer Electronics. These laboratories are responsible for a wide range of activities from basic research through to applications technology. Together the laboratories employ over 1,200 qualified engineers and technicians and the number is growing. Each laboratory has specific expertise, but all contribute to overall development and the system gives each market access to a wide range of research and applications development work.

Thomson's R and D laboratories are situated at Enfield, Los Angeles, Indianapolis, Strasbourg, Hanover, Villingen, Tokyo and Singapore. Enfield's activities are obviously focused on product development for the UK market but subjects of special expertise include Nicam, Fastext, PAL and D-MAC systems and equipment. The highly specialised laboratory at Los Angeles concentrates on the development of complex software and operating systems for audio and video equipment. Interactive menu control is an example of the work carried out here. Indianapolis acts as the R and D centre for the Americas, concentrating on basic research and TV development, digital signal processing and the development of new chassis and i.c.s. The laboratory works in close collaboration with the David Sarnoff Research Centre, in particular on an HD-TV standard for the American market. In Europe, work on HD-TV and future TV systems is being mainly carried out at Strasbourg, which is also concerned with improvements to existing TV standards and digital signal processing in both the transmission and recording fields. Hanover is involved in fundamental research, in particular digital signal processing in the context of the Eureka and Race projects. The Tokyo laboratory enables Thomson to keep in touch with the Japanese research scene. Singapore is the product development centre for the Far East. It's engaged in audio, video and TV products for both local and world markets, and in conjunction with other Thomson laboratories develops key components such as tuners and modulators.

Villingen is the control centre for Thomson research worldwide and is by far the largest of the eight laboratories. Its responsibilities include audio, video and TV product development, the development of key components for micromechanics (CD drives, video decks, optical and magnetic pickups), the development of microelectronic components such as i.c.s, also h.f./ s.h.f. components, SMD and hybrid technology and product-specific software. The laboratory is involved in fundamental work on new recording techniques including matrix scanning, and undertakes contract research for third parties.

As a major company in the international consumer electronics field – market leader in the USA and number two in Europe – Thomson is well aware of the need to invest in R and D and be at the forefront of product development. Enfield continues to play an important role in this work.

Servicing Compact Disc Players

Part 17: Power Supplies and CPUs

The power supply and central processor unit are the only two sections of a CD player we've not so far considered in this series of articles. Although there's nothing particularly novel about them, the series would be incomplete without some comments on these subjects.

Power Supplies

CD player power supply arrangements are straightforward and require little attention. It's important however to remember that the power supply circuitry is there! When fault finding it's all too easy to forget obvious things such as a missing supply rail. Such problems can cause havoc, especially when everything is under the control of a central microcomputer chip.

Perhaps the most important feature to bear in mind is the use of both positive and negative supply lines for motor direction control. When we covered the servos in parts 10-13 we saw that forward and reverse drive is required not only for the various motors (e.g. disc, sled and drawer) but also for the two-axis device. In most cases the direction of the current flowing through these motors and coils is controlled by a push-pull transistor arrangement. Fig. 1 shows two methods. The arrangement shown at (a) employs four transistors and a single supply line: current direction is controlled by switching on either Tr1 and Tr2 or Tr3 and Tr4. The second circuit shows two transistors connected across equal but opposite supply rails: because of the number of motors and coils that require two-way operation in a CD player this is the simplest approach and is used in most machines. In addition to this, some of the preset controls operate with the slider moving between a positive and a negative supply. An example was the focus offset circuit shown in Fig. 4, part 10 (December 1989).

When one considers the number of devices that require two-way drive it's easy to see why the loss of a single supply rail can give rise to any number of symptoms, from the sled racing to one end of its travel at switch on to the disc running backwards at great speed. Further problems may arise when a player has been left

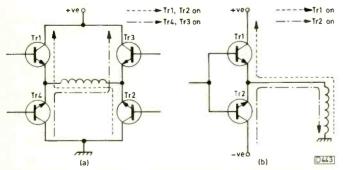


Fig. 1: Two methods of controlling the direction and amount of current flowing through a motor or actuator coil, (a) with four transistors and a single supply line, (b) with two transistors connected between positive and negative supply lines.

Joe Cieszynski

on for a long period, for example if it's part of a midi system and the customer continues to use the rest of the system for a number of weeks before sending it in for repair. In such cases be on the lookout for burnt out driver transistors, burnt out motors and possibly even an open-circuit coil in a two-axis device.

Such problems may not arise where adequate protection is provided by means of circuit protectors. But this brings us to another point. Although effective when a fault develops, these small devices can themselves be the cause of may complaints. When you encounter a player with a missing supply line a quick check on the circuit protection is always advisable.

Fig. 2 shows a typical CD player power supply. The +5V line will be used by i.c.s such as the CPU and decoder chips. Other i.c.s may make use of both the +5V and -5V lines to form an overall 10V supply. Motor driver circuits would use positive and negative lines as shown in Fig. 1(b). The regulators may consist of i.c. packages or discrete component circuitry.

The Central Processor Unit

One point we've emphasised during the course of this series is that a set of i.c.s is often found in the r.f., decoder and servo sections of players produced by different manufacturers. One chip that will always differ however is the central processor/ microcomputer, since this i.c. contains the program that customises the player to the manufacturer's specification. A CD player's CPU is very often a single VLSI chip that controls everything from the basic player operation to the front display. There will generally be some additional logic to control the servos, generally contained within the servo chip, and some of the more sophisticated players may have a separate display control chip. Despite its major role in the player, the CPU is generally a far less complex device than that found in VCRs and modern TV sets.

The CPU's inputs come from the customer keypad, the deck sensors and the decoder. One important piece of data is the Q subcode which, as we've seen, contains information such as track number, index, playing and running times and pre-emphasis control. The decoder also generates an error flag when the Q subcode is corrupt: this flag is sent to the processor which then carries out CRCC error correction. The Q subcode was discussed in part 7.

Another important central processor input is the focus o.k. (FOK) signal which is generated in the r.f. stage. We saw in part 10 how this signal is produced when correct focus is achieved, and that the CPU will not permit disc run up until it has received an FOK input. Thus the presence or absence of the FOK signal is a valuable clue when the player won't spin the disc at all.

Outputs from the CPU are sent to the drawer and deck driver circuits, the servo and decoder chips, and the front display. In addition the processor provides output signals to control the laser power supply, the deemphasis circuit and the audio mute system.

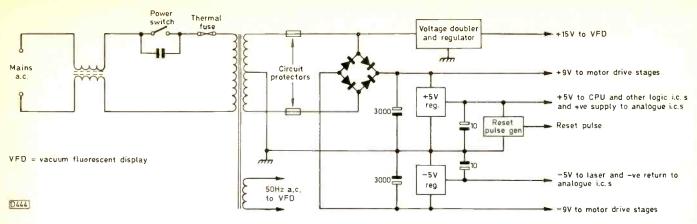


Fig. 2: A typical CD player power supply arrangement.

Fig. 3 shows in block diagram form the basic CPU arrangement.

When the player is dead or haywire it's all too easy to blame the CPU chip. Unfortunately such chips are often surface mounted and sensitive to static damage, as a result of which they are not easy to replace. It's important therefore that other possibilities are ruled out before the CPU is condemned. The following standard checks apply not only to a CD player's CPU but to any simple microcomputer chip.

(1) Check the supply rail(s). The microcomputer control chip will be powered from a 5V supply and this line should be one of the first checks to make when the player is dead, especially if the front display is out or is providing a very strange reading. In some cases there may be more than one supply to the CPU chip, so beware.

(2) The second thing to check is the clock oscillator. The CPU chip can't function unless this is working, and it's not uncommon for the oscillator to fail. The oscillator is normally within the CPU chip, but will operate in conjunction with an external ceramic resonator or quartz crystal. Most problems occur with ceramic resonators as they are prone to breaking loose inside their plastic encapsulation as a result of which they go open-circuit either permanently or intermittently.

It's best to check the oscillator using an oscilloscope. A signal in the 2-10MHz region should be seen, at an amplitude of about 5V peak-to-peak. The output may be sinusoidal but is more often than not some form of clipped sinewave. Don't fall into the trap of looking at a much lower-amplitude, "mushy" waveform and mistaking this for the real thing. When the oscillator is defective the usual culprit is the resonator or crystal, although it could be the part within the chip. Either way the recommendation is to change the resonator first - it has two legs rather than eighty!

(3) Check the reset pulse. This is generated at switch-on to clear the CPU of any rubbish that it may store in its memory during power-up. Many strange faults in audio, video and TV equipment can be caused by failure of a reset pulse generator, so it's wise to check this signal when the microcomputer chip is misbehaving. We'll return to the reset pulse generator circuit shortly.

(4) Check the earthing or, to be more precise, the lack of it. Don't forget to test for breaks in the PCB, the wiring, the plug connectors, etc. A common give-away is when you get a supply rail voltage reading at all the i.c. pins.

The above are the main tests that apply to any microcomputer circuit. If the fault persists it may prove useful, depending on the fault symptom(s), to check the following.

(5) The key scan signals, if used. These may be generated by the CPU chip or by an additional "function-control" chip and appear on the scope's screen as a constant data stream. If this is missing the most likely culprit is the chip from which it emanates.

(6) The input logic conditions. The signals here are not of the same type as the high frequency data signals. They come mainly from sensor switches in the player's mechanism and provide a simple high/low logic reading.

gåribål'di (gar-i-böl'di, -bal'di)

Defined as-n. Type of biscuit with currants: Name of famous Italian general

Tel: 0494 773918

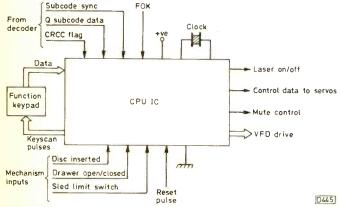


Fig. 3: The basic central processor system used in a CD player, showing the main input and output data lines and signals including the clock and reset pulse.



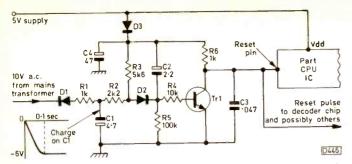


Fig. 4: Typical reset pulse generator circuit. This one is used in the Sanyo Model CP-08.

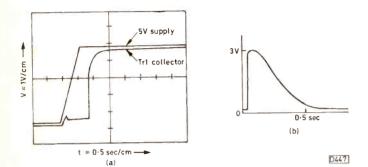


Fig. 5: Timing diagrams for the circuit shown in Fig. 4.

You can easily check them using a logic probe or a d.c. voltmeter. Where the condition is incorrect, be on the look out for such things as a defective switch, a worn or broken cam, worn belts, a sticking mechanism, an open-circuit lead or a defective buffer (transistor or gate) between a sensor and the relevant CPU input.

(7) The function keypad. We've already mentioned the key scan signals which are the outputs at several pins of either the CPU or a function control chip. The presence of these signals themselves is not an indication that the function selector keypad is operational. When a key is depressed there must be a signal that goes back to the CPU. It may be a key scan signal or an analogue signal that consists of a d.c. level – developed by a resistor ladder arrangement. Check that the appropriate input is present at the relevant pin of the CPU when a key is depressed. Possible faults are open-circuit keypads or hairline cracks in the front panel.

It's equally important that the CPU should not receive an input when no keys have been depressed. Shortcircuits or resistive leaks in the function keys are not uncommon. In addition buffers or diodes between the keys and the CPU can fail, making a CPU input look as though a key is permanently depressed.

(8) The output conditions. Before condemning a CPU chip, check that its output conditions are in fact wrong. Although this is uncommon, it's possible for the observed symptoms to give the impression that the CPU is faulty when the fault actually lies in circuitry beyond this point.

Reset Pulse Generator

There are many variations in the way in which a reset pulse is generated. The basic idea however is to use an RC circuit with a short time-constant to take the CPU's reset pin (and the reset pins of any other chips containing memory) briefly either high or low after switch-on. The reset signal is necessary to prevent corrupt data being

stored in an i.c.'s memory – this data is generated at random during the period when the supply rails are being established.

Fig. 4 shows an example of a reset pulse generator circuit. In this case when the mains supply is switched on capacitor C1 begins to charge to a negative potential via D1 and R1. At the same time the 5V rail starts to rise from 0V, this supply appearing at the CPU's Vdd pin. The positive supply also appears at the base of transistor Tr1, via R3, D2 and R4. Thus Tr1 conducts, taking the CPU chip's reset pin low. This condition continues until the point is reached where the negative charge developed by C1 reverse biases D2. Tr1 is then cut off and the reset pin rises to 5V. The timing of the circuit is such that the charge developed by C1 does not cut Tr1 off until the 5V supply has been fully established.

The trace shown in Fig.5(a), made using d.c. input coupling to the scope, shows the reset pin being held low until the 5V supply is firmly established. It was obtained using a digital storage scope set for a single sweep (the scope had a built-in printer). Such equipment is not generally available in a service workshop, but I've obtained the same trace using a standard dual-beam scope set for a single-shot trigger with the brightness turned up to make use of the phosphor's persistence.

The trace in Fig. 5(b) shows the waveform at the collector of Tr1 following switch-on, with the scope set to a.c. input coupling. This is often helpful as an initial check to see whether the reset circuit is doing anything at all.

If the reset generator fails, the player is likely to show all sorts of fault symptoms because the CPU and other chips such as the decoder will be operating with rubbish locked into their memories. This data will be lost every time the player is switched off, but new rubbish will be stored at the next power up. This can lead to the situation where the customer complains that the player is suffering from faults too numerous to mention, though the troubles are all due to a single component.

In Conclusion

So we come to the end of this series. I'm aware that in some sections there was rather a lot of theory, but wherever possible I've attempted to relieve this with practical comments and advice.

At the start of the series I commented on the value of having a good grasp of the theory on which CD players are based and concluded that such an understanding is helpful when you are faced with what appear to be difficult and obscure faults. The value of such an understanding extends beyond just CD players however. The principles of DA and AD conversion for example are used in a lot of other equipment today. I feel that the CD player provides a sound training for servicing much of the domestic electronic equipment that we will be encountering during the next few years, since it introduces the engineer to such new features as optical pick-up control and readout, digital servos, data handling systems, data storage and so on.

Acknowledgements

In conclusion some thanks are due. First to Ken Clements of Pioneer UK for his technical support in the early stages of preparing these articles, and more recently to George Cole for answering my queries on the unused subcode words.

De Luxe Component Tester

Part 1

More and more TV/video service engineers are finding that a component tester makes their life easier. The de luxe component/signature tester described in this article is easy to construct and simple to use. You'll find that it's often quicker to use the tester to check every component on a PCB rather than having to spend time tracing out the circuitry then testing likely suspects. Colleague Pete, who has been using my first component tester unit since details of it were published back in 1984, now wants to get his hands on this latest one which incorporates many extra features.

The de luxe tester will rapidly check bipolar transistors, diodes, zener diodes, thyristors, LEDs, VCR end sensors, capacitors, resistors, chokes, mains transformers, loudspeakers and many other components. It also operates as a signature tester, and is particularly helpful when you're trying to identify unmarked surfacemounted or other components.

The tester can be used with almost any oscilloscope. If you've an old one that's gathering dust because it doesn't meet modern requirements you can connect it to the tester permanently. Set the scope to its X/Y mode: the internal timebase isn't used because the tester supplies a horizontal scanning voltage. The waveform displayed on the scope's screen instantly and accurately reveals the condition of the component under test.

The usual way of checking transistors and diodes is with an ohmmeter. This is o.k. when the fault is a dead short or an open-circuit, but it's not a completely reliable test procedure. The component tester really scores here, by revealing the slightest defect or leakage in a transistor or diode. Another benefit, except when testing thyristors, is that only two test leads are required. This is a lot easier than having to do the juggling act that some transistor testers call for, as you try to hold three prods in contact with a transistor's leads.

The unit also serves as a useful continuity tester for general servicing work.

Principle of Operation

The tester operates as an extension of an oscilloscope's circuitry. To obtain the best results, it's essential to understand exactly how the tester works.

Fig. 1 shows at (a) to (f) the operation of the tester. In Fig. 1(a) an a.c. voltage is connected across the two resistors R-low and R-high via terminals A and B. Almost the full a.c. voltage is applied to the scope's X (horizontal) input, producing a horizontal line on the screen – see Fig. 2(a). If terminals Ch and T are shorted across, as shown in Fig. 1(b), the entire a.c. voltage is applied to the scope's Y (vertical) input, producing a vertical line on the screen – see Fig. 2(b).

If a diode or transistor junction is connected across T and Ch (chassis), as shown in Fig. 1(c), the diode will conduct when the a.c. waveform at Ch is positive-going – the diode is reverse biased when the waveform at Ch is negative-going. Fig. 2(c) shows the resultant waveform display on the scope. Reverse the diode and you'll see the waveform shown at Fig. 2(d). With a good diode (or transistor) junction the waveforms displayed will be

TELEVISION JULY 1990

David Botto

sharp and clear, with sharp right-angled corners.

A zener diode produces the waveform shown in Fig. 2(e). The diode's barrier potential produces one upright line, the other being produced by the reverse conduction zener characteristic.

Fig. 1(d) shows a thyristor connected with its anode to terminal T and its cathode to terminal Ch. With a good thyristor you'll see the waveform shown in Fig. 2(a). When a suitable d.c. voltage is applied to thyristor's gate the device will fire, producing a diode waveform of the type show in Fig. 2(d).

A resistor connected across T and Ch – see Fig. 1(e) – lowers the value of R-high. As a result less a.c. voltage is fed to the scope's X input while the a.c. voltage at the Y input increases. This produces an angled line, see Fig. 2(f), because an a.c. voltage is present at both the X and Y inputs of the oscilloscope. The angle of this line depends on the ohmic value of the test resistor. If the scope's sensitivity at its X and Y inputs is the same, the angle of the line will be 45° when the ohmic values of R-low and the parallel combination of R-high and R-test are equal.

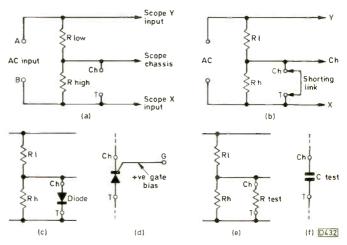


Fig. 1: Principle of the tester (a-b); (c) shows a diode test, (d) a thyristor test, (e) a resistor test and (f) a capacitor test.

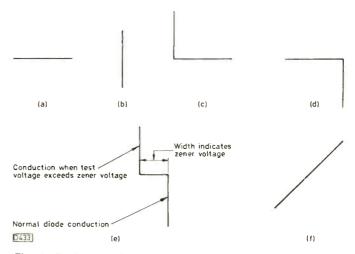


Fig. 2: Basic waveforms (a-d); zener diode waveform (e); resistor waveform (f).

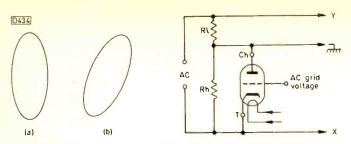


Fig. 3 (left): Waveform produced by a good capacitor (a) and a leaky capacitor (b).

Fig. 4 (right): Valve testing circuit.

A capacitor connected across T and Ch will charge first in one direction then the other. The result is an elliptical display on the screen as shown in Fig. 3(a). The size of the ellipse depends on the value of the test capacitor. Leakage in the capacitor shows up as a badly tilted ellipse – see Fig. 3(b) – since this is the same as connecting a resistor across R-high. Because of the low test voltage used, electrolytic capacitors can be checked.

The a.c. voltage applied to points A and B can range in frequency from 20Hz to 25kHz. The tester makes use of the 50Hz mains frequency because this is convenient and stable.

The tester's principle is not new – it dates back to the days when the valve was supreme in fact. When a diode valve is connected with its anode to Ch and its cathode to T it will conduct only when Ch is positive with respect to T. With a triode or multigrid valve the anode current will vary with changes in the a.c. or d.c. voltage at the control grid. If the a.c. grid voltage is of a different frequency to the mains the circuit operates as an effective dynamic valve tester. Anyone interested in servicing vintage equipment might find this feature useful. See Fig. 4.

Circuit Description

Fig. 5 shows the complete circuit of the de luxe component tester. The 240V a.c. mains supply is applied to points A and B, the miniature green neon N1 providing an indication that the instrument is powered. Fuses F1/2 and resistors R1/2 connect the mains input to the primary windings of the two miniature mains transformers M1 and M2. Resistors R1 and R2 limit the power applied to the component under test. With no load connected to the secondary windings of transformers M1 and M2 the a.c. voltage across their primary windings is 240V. When a load is connected across either secondary winding however the a.c. voltage across the primary windings drops. This limits the power applied to the component under test, protecting small diodes, transistors and i.c.s.

Two miniature transformers, from RS Components, were used to obtain the correct voltage drop and to save space and cost. It's best to use the transformers specified. The secondary windings are connected in series so that, off load, 20V, 40V and 80V a.c. test voltages are fed to switch SW4A. When a component is being tested these voltage levels fall considerably. SW4B is ganged with SW4A: when position 2 is selected the amber neon N2 lights, indicating that the correct a.c. input voltage has been selected for i.c. testing. By selecting position R on switch T4 the voltage applied to the i.c. under test is reduced still further. Switch SW4 is rated at 125V a.c., which is appropriate since it's connected to the centre tap on M1: the neon N2 still lights brightly at this reduced voltage.

User control VR1 sets the amplitude of the vertical trace. Initial adjustment is done with the "set" position of switch T4 selected. VR2 adjusts the horizontal drive output voltage applied to the scope's X (horizontal) input. It has a calibrated scale so that the user can measure the voltage of a zener diode under test. The zener voltage scale's range of 1·1-63V could be extended to cater for higher voltage zener diodes, but for general servicing a maximum of 63V is usually sufficient.

ICH1 is a 28-pin, zero-force insertion type i.c. socket. Switches SW1/2/3 together with toggle switches T1/2/3 select the i.c. pins so that waveform tests can be made between all adjacent pins. Each pin of socket ICH2 is directly wired to the same number pin of socket ICH1.

Small transistors or diodes can be inserted in sockets Q1 and Q2. Switch SW3B selects these sockets in turn: they are handy for making comparison checks between two devices.


T is the thyristor test socket. VR3 adjusts the gate bias voltage applied to the device from the 1.5V battery. This socket is intended for use with small thyristors: larger ones can be checked by using three test leads plugged into the instrument's T, G and Ch sockets.

Construction

The accompanying photographs show the finished unit and its interior layout. Everything possible has been done to ensure ease of construction and reliability in use. The case, obtained from RS Components, is a tough one designed to stand up to everyday use in the workshop. It's made of a type of plastic that's easy to drill. The useful built-in battery compartment holds four batteries, though the tester uses only one. The case size is such that all the components can be housed without being packed too closely. It doesn't take up much room on the bench.

The components list includes everything you'll need to build the tester. The parts have been carefully selected taking quality, price and ease of construction into account. By using them you'll need only to drill some round holes and make the cut-out section behind the PCB. To ensure trouble-free construction and operation it's best to stick to the recommended parts. The specified resistors are of higher wattage rating than is strictly necessary, but this will contribute to long-term stability and reliability. To avoid scratching the case it's best to have a rubber instrument mat on the bench while constructing the unit.

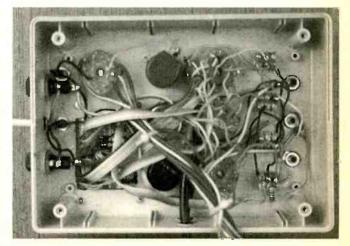Begin by drilling the round holes required in the top



Inside view of the top section of the tester.

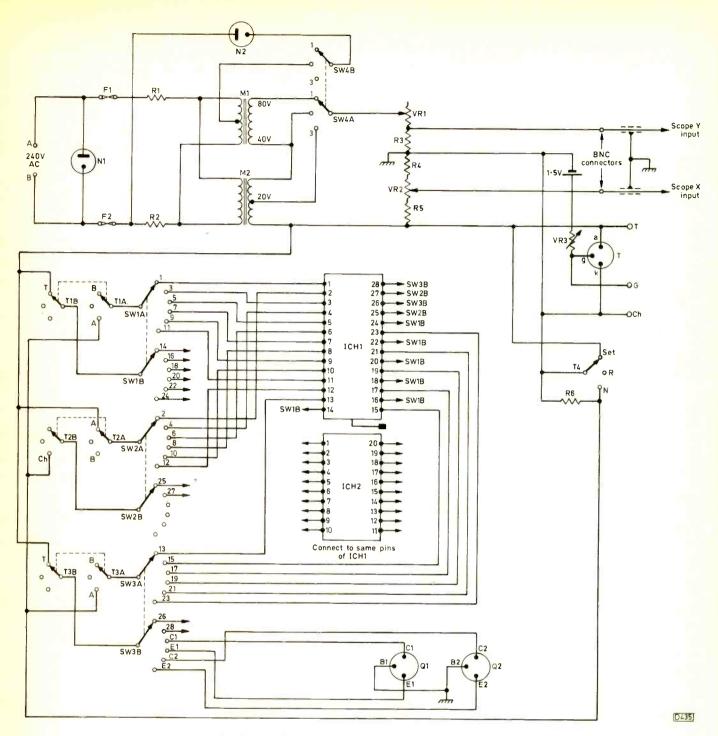


Fig. 5: Circuit diagram of the de luxe component tester.

panel. This is the larger section of the case: the lower section is the one with the battery compartments. Fig. 6 shows the top panel layout and measurements. The hole sizes suit the specified components. Next drill the holes at the top of the case for the two fuseholders and the mains lead grommet, see Fig. 8. Then drill the two holes (see Fig. 7) for the X and Y black coaxial cables that go to the scope: these holes are on the right-hand side of the case and are fitted with grommets.

You can now fit all the panel-mounted controls, lamps and sockets. Leave the fixing nuts for switches SW1/2/3 slightly loose. Fit the fuseholders and the grommets for the mains lead and the leads to the scope. Continue by drilling four small holes at each corner of the rectangular plastic section that has to be removed. Use the small PCB as a template. The rectangular hole is easy to cut out using a trimming knife with a suitable saw blade fitted.

TELEVISION JULY 1990

Be sure to wear a pair of safety goggles Kitemarked to BS2092 standard when you drill and cut the holes. Flying plastic chips can cause serious damage to your eyes.

The positions of the two miniature mains transformers and resistors R1/2 can be seen in the accompanying photograph. It's preferable to use nylon plastic nuts and bolts to secure the parts to the case. Four heavy-duty self-sticking cushion feet should be fitted to the bottom of the tester: these will keep it rock-steady on your bench.

Complete the instrument wiring as shown in the circuit diagram but leave the wiring to switches SW1/2/3 and the small panel-mounted PCB for the present.

Fig. 9 shows the socket layout on the small PCB, which is available from Tandy. It's not necessary to make you own panel: the two i.c. holders and three transistor sockets fit nicely on the Tandy one. Use either

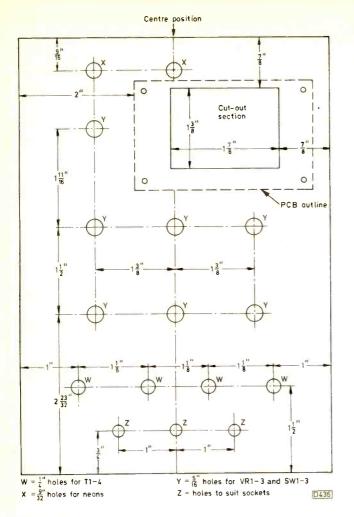


Fig. 6: Top panel layout.



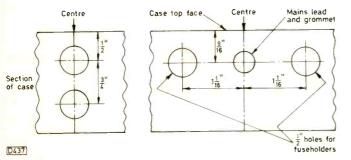


Fig. 7 (left): Side holes for the coaxial cable leads – sizes according to grommet and cable diameter.

Fig. 8 (right): Holes at top of case for the fuseholders and mains cable. Mains lead hole to suit cable/grommet.

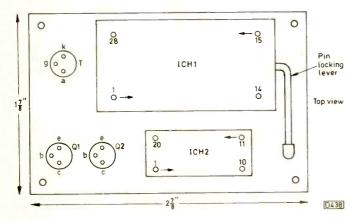

 

a small 17W iron or preferably a temperature-controlled iron fitted with a suitable bit to wire up the panel.

Wire pins 1-20 of holder ICH1 to pins 1-20 of holder ICH2, using light-gauge insulated wire. Take care when working on the PCB that solder blobs don't short sections of the copper print together.

Next solder strips of ribbon cable to the panel for connection to switches SW1/2/3. Cut and divide a sufficient quantity of ten-conductor bonded-ribbon cable into pieces of 14in. length – this length gives you a little extra tolerance during the wiring process. The specified cable is colour coded and the divisions and colours used in the original unit are shown in Table 1. Solder the cables to the i.c. socket pins, marking each bunch of coloured cables with the numbers of the i.c. pins to which they are connected. Bolt the PCB to the top of the case so that the cables feed into the instrument. You can

Table 1: Connections to SW1-3.

Suggested colour coding for ribbon cable divided into strips. Pin numbers are for holders ICH1 and ICH2.

Colour	ICH pin	Switch
Strip I Brown Red Orange Yellow Green Blue	1 2 3 4 5 6	SW1A SW2A SW1A SW2A SW1A SW2A
<i>Strip 2</i> Green Blue Mauve Grey White Black	7 8 9 10 11 12	SW1A SW2A SW1A SW2A SW1A SW2A
<i>Strip 3</i> Brown Red Orange Yellow	13 14 15 16	SW3A SW1B SW3A SW1B
<i>Strip 4</i> Green Blue Mauve Grey White Black	17 18 19 20 21 22	SW3A SW1B SW3A SW1B SW3A SW1B
<i>Strip 5</i> Brown Red Orange Yellow	23 24 25 26	SW3A SW1B SW2B SW3B
<i>Strip 6</i> Green Blue	27 28	SW2B SW3B
Strip 7 to transistor holders Yellow Orange Red Brown	Q1/2 Q1 collector Q1 emitter Q2 collector Q2 emitter	SW3B SW3B SW3B SW3B SW3B
	TELEVISION J	ULY 1990

Components List

Electrical items

M1, M2	6VA miniature mains transformers
	with 0-20V/0-20V secondary windings.
	RS Components stock no. 196-319
F1, F2	1AT 20mm fuses
NI1	240V as seen many light Tout

- 240V a.c. green neon light. Tandy N1 stock no. 272-708
- **N2** 240V a.c. high-brightness amber neon light. Tandy stock no. 272-707 VR1
- 1kΩ linear taper potentiometer
- VR2 1MΩ linear taper control. Preferred type Tandy 271-211
- VR3 3kΩ wirewound linear taper control R1, R2 4-7kΩ, 5W small wirewound
- **R3** 1·2kΩ, 1W
- **R4** 10kΩ, 1W **R5**
 - 470kΩ, 1 W
- **R6** 4·7kΩ, 1/2W

1.5V Ever Ready Silver Seal RS6 or equivalent battery

Switches

- SW1-4 Rotary two-pole six-way switches. Tandy stock no. 275-1386. SW4 could be a three-way type
- T1-4 Miniature d.p.d.t. toggle switches, onoff-on. Tandy stock no. 275-620

Case

- Plastic instrument case, style 3, RS Components stock no. 505-117. 190mm long, 138mm wide, 68mm high
- Four heavy-duty cushion feet, Tandy stock no. 642-342
- Small sheet of thin transparent plastic to cover panel scale
- Lettering plus Klarlack clear varnish. See text

now cut the cables to the correct lengths to reach switches SW1/2/3. Allow a little extra length in case you need to remove the PCB. Fig. 10 shows the switch contact arrangement used by the two-pole, six-way Tandy switches which are well made and reasonably priced. Finally wire the PCB leads to the switches. At this stage it's worth making ohmmeter checks to ensure that the ribbon cables from the switch connections of SW1/2/3 go to the correct i.c. pins and transistor holders. Check all wiring carefully.

Fit 4mm plugs at one end and mini or micro clips at the other end of the three test leads that plug into sockets Ch, T and G. The small clips are useful when holding small devices and when making in-circuit tests.

The last job, after completing the construction, is to fit the scales with the zener diode voltage indications and

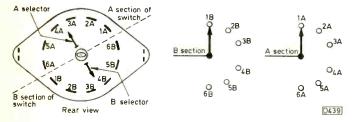


Fig. 10: Details of the Tandy switch suggested for use in positions SW1-4.

TELEVISION JULY 1990

Mechanical parts

- Length of terminal block for transformer leads 4BA nylon nuts and screws to secure transformers and tagstrip. RS Components stock no. 522-055.
- Two 2ft 6in lengths of good-quality black coaxial cable to connect to scope plus two BNC plugs

Mains cable, 3ft, white

- Moulded grommets to suit mains and scope leads
- Experimenter's i.c. Perfboard, Tandy stock no. 276-150. Four screws, nuts, washers and spacers to suit

One zero-insertion force 28-way i.c. socket. RS Components stock no. 402-248

- One 20-pin i.c. holder
- Three PCB transistor holders (Q1, Q2, T). RS Components stock no. 401-661
- Ten-conductor bonded ribbon cable. Tandy stock no. 278-7050
- Three 4mm insulated panel mounting sockets, two black one red
- Three miniclip test leads with 4mm plugs, Tandy stock no. 278-1160
- Nylon wire ties
- Six moulded knobs with 1/4in shaft fittings and white line indicator, 3/4in diameter. Tandy stock no. 274-415

One moulded knob with 1/4in shaft fitting and white line indicator, 1in diameter. Tandy stock no. 274-416

Circuit varnish


Panel scale - see text

Calibration zener diodes

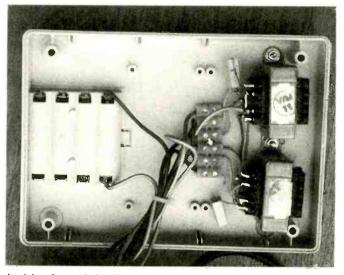1.1V, 2.7V, 3.3V, 4.4V, 5.1V, 5.6V, 7.5V, 9.1V, 12V, 30V, 47V, 56V, 61V

the SW1/2/3 switch position indications. Fig. 11 shows the scale full size. Copy it on to white paper and then photocopy it on to a thin white card. The fixing nuts of the panel controls will hold the card in position.

The lettering on the front of the tester is best done with dry-transfer lettering. Apply a coat of Pelikan Klarlack clear varnish over each letter, using a tiny



Inside view of the bottom section of the tester.

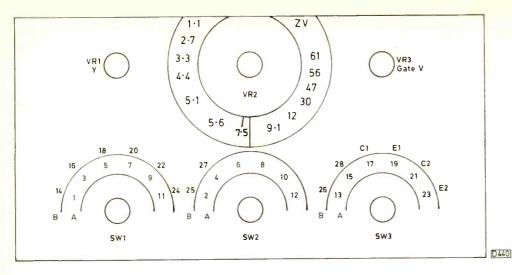


Fig. 11: Component tester scale, shown full size. Letters A and B indicate the toggle switch (T1-3) positions that select the marked scales of SW1-3.

brush, to prevent the letters being rubbed off. You can get the letters and varnish from a local art shop. Don't use cellulose varnish – this will remove the letters and the surface of the case.

Testing and Calibration

Check that the four toggle switches T1-4 are set to their centre positions. Connect the tester to the mains supply. The green neon should light. With SW4 in position 2 the amber neon should light.

Disconnect from the mains supply and turn VR1 and VR2 to their centre positions. Plug the screened leads, fitted with BNC connectors, to the scope's X and Y inputs. If these connectors won't fit your scope fit ones that will. Select external X drive – with some older scopes this may be labelled external horizontal drive. If in any doubt consult the instruction book. Set the scope's Y input to its least sensitive d.c. range. If the scope is an older model with just an a.c. input the tester will work but you may get a double image.

Reconnect to the mains supply and set the tester's volts knob (SW4) to position 2. Adjust the scope's X (horizontal) gain control until you obtain a centred horizontal line that slightly overscans the screen. Move

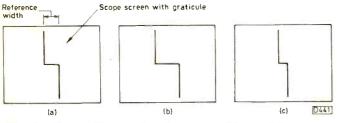


Fig. 12: Zener scale calibration: (a) 7.5V, (b) 12V and (c) 5.1V zener diodes.

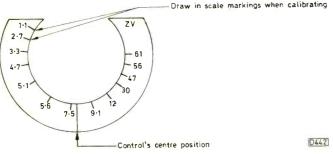


Fig. 13: How the ZV scale calibration is checked: for accuracy the lines connecting the figures to the scale edge should be drawn in on Fig. 11, using a range of zener diodes.

T4 to the set position. This should produce a vertical line. Turn VR1 to half-way and adjust the scope's Y (vertical) gain control until the line almost scans the screen. Centre the line then switch T4 to its N (normal) position.

Connect a diode across sockets T and Ch, anode to the Ch socket. If all is well you'll obtain a sharp, clear waveform of the type shown in Fig. 2(c).

To calibrate the ZV (zener voltage) scale, first make sure that the volt selection switch SW4 is still in position 2 and that the centre position of VR2 coincides with the centre scale line, then connect a 7.5V zener diode via the test leads between sockets Ch and T, with its anode to socket Ch. You should see the waveform shown in Fig. 2(e). Move the pointer line of VR2 to the 7.5V scale marking on the ZV scale. Adjust the scope's X gain (width) control until the horizontal section of the waveform covers just a small section of the screen - see Fig. 12(a). Replace the 7.5V zener diode with a 12V one. The horizontal section of the trace should widen as shown in Fig. 12(b). Turn VR2 to reduce the width until the horizontal section of the trace again covers exactly the same small section of the screen as in Fig. 12(a). The pointer line should now be opposite the 12V marking on the ZD scale. Connect a 5.1V zener diode across the test terminals and the horizontal section of the trace should narrow as in Fig. 12(c). Turn VR2 until the horizontal section of the trace is again as in Fig. 12(a). VR2's white line should read off $5 \cdot 1V$ on the scale.

Provided you've used the specified Tandy control the ZV scale should be fairly accurate as drawn. Just the 7.5V calibration line is shown in Fig. 11. Fig. 13 illustrates the calibration procedure just outlined. Although the scale shown in Fig. 11 has been found to be accurate with several different scopes, to allow for component tolerances it's best to calibrate the scale using a range of known good zener diodes, drawing in the rest of the calibration lines yourself.

In addition to checking zener diode voltages the ZV scale enables you to identify the voltage of a zener diode whose markings have rubbed off.


After the instrument has been tested and the zener scale has been correctly calibrated, cover the scale with a thin sheet of clear stiff plastic to keep it clean. The panel control nuts will hold the scale and plastic cover without the need for glue that could damage the case.

Finally, using a small brush, apply a thin coat of circuit varnish to all soldered joints.

Next month we'll describe a broad range of tests that can be made with the unit.



The Complete Range is available from

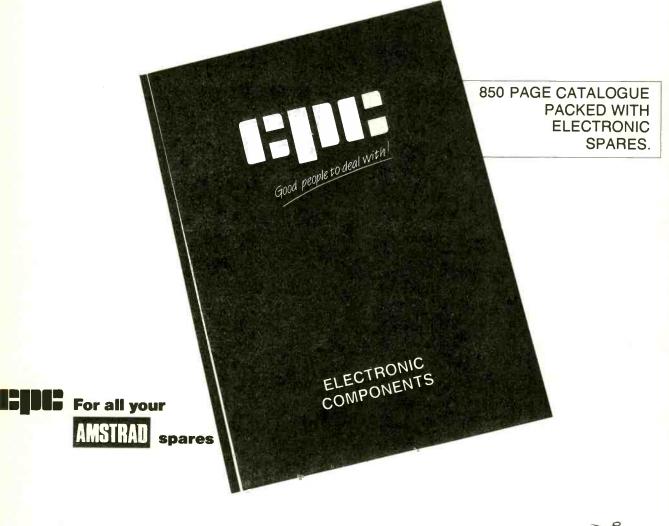

IT'S EASY To open a trade account

Simply let us have two trade references and one bank reference. Just complete the form alongside, cut out and Fax. or post FREEPOST to C.P.C. and you can enjoy the many benefits and cash savings you get when you trade with C.P.C.



ORDERS PLACED UP TO 5.30pm DESPATCHED THAT DAY

Phone: (0772) 555034. Fax: (0772) 201905

	Trade Reference 2
Bank Reference	
Name (Business or C	ompany)

The Ferguson FV30's Chopper PSU

The FV30 was the first of a new generation of Ferguson VCRs that show a trend away from Japanese design ideas towards a more European approach. Notable amongst these design trends is the use of a switch-mode power supply which is energised as long as the mains supply is connected to the machine. Although servicing the FV30 is not as simple as its predecesors, the power supply need not be a daunting prospect in a fault condition.

You'll find the power supply on the right-hand side of the machine. Take care over physical handling as the live mains and other high voltages are present on the PCB. Use of a mains isolating transformer is strongly recommended. With transistors that are directly connected you can get multiple failures under a fault condition. This is particularly so when the chopper transistor TP37 fails.

The power supply is capable of operating with a mains input over the range 110-240V a.c., either 50 or 60Hz. Consumption is 42VA maximum. There are three operating modes: (1) standby, (2) tuner (E-E) and (3) full operation. In the standby mode the power supply provides outputs for the microcomputer chip, the panel display, the r.f. mixer-booster and for tuning. In the tuner operation or E-E mode (tuner switch at "on") the

J. LeJeune

power supply energises all the signal processing and control unit circuitry: this enables the machine to be used as a receiver with an output on ch. 36 or a video output via the scart connector. With full operation all the circuits are energised.

As there's no master switch the power supply is constantly on (when the mains supply is connected), providing a standby voltage. The microcomputer chip controls the application of power to the various parts of the machine. Fig. 1. shows the basic power supply circuit.

Circuit Operation

Three voltages are established when the machine is connected to the mains supply. These are: (1) a 300V supply which is provided by the mains bridge rectifier DP01-4 in conjunction with the reservoir capacitor CP07. (2) A 2-2.5V supply which is produced in under two seconds by DP11, RP12 and CP14. (3) A 3.5Vsupply which is produced in under two seconds by DP11 with RP11 and CP38.

When the second of these supplies has reached 1.5V the start-up oscillator TP16/17 will run at about 20kHz, driving the chopper transistor TP37 via TP28 and the

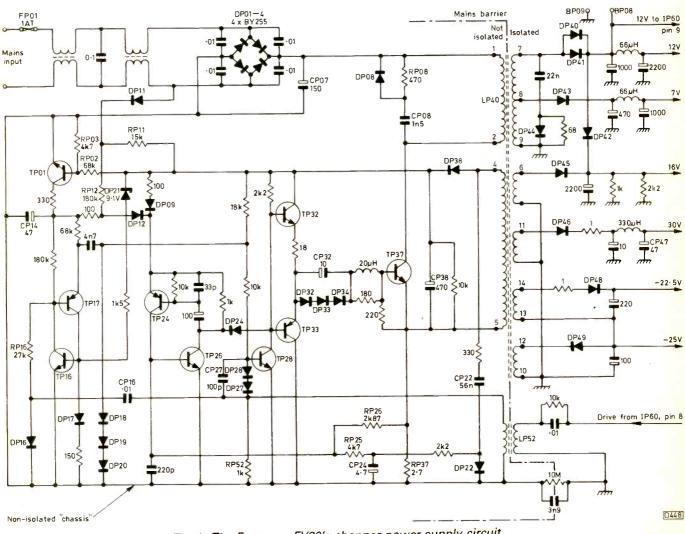


Fig. 1: The Ferguson FV30's chopper power supply circuit.

driver transistors TP32/3. At this time supply (3) powers these latter transistors (TP28/32/33). When the chopper transistor TP37 is switched on, the lower end of the chopper transformer's primary winding (pin 2 of LP40), which is supplied by the mains bridge rectifier, is grounded via RP37. As a result, a rising ramp current flows through the winding. When TP37 is switched off by the drive waveform the flux established by the ramp current collapses, energising the transformer's secondary windings.

Once the circuit has got going the drive for TP28/32/33/ 37 is provided by the regulator chip IP60 (see Fig. 2) via the isolating transformer LP52. DP40/41 supply 12V to pin 9 of this chip to power the emitter-follower output transistor within IP60. DP46 provides a 30V supply which is fed via RP59 to the 24V zener diode DP59. This is the main supply to the chip, which generates a reference voltage that appears at pin 12 and is then fed to pins 2 and 13. Within the chip the voltage at pin 2 is compared with that at pin 1, tapped from the set 12V control PP57. The error voltage thus produced is added to a sawtooth signal generated within the i.c. This is the classic pulse-width modulator arrangement. Over the whole feedback loop, the on time of the drive pulse applied to the chopper transistor is determined by the sample voltage at pin 1 of IP60.

The pulse-width modulated drive at pin 8 of IP60 is coupled to the base of TP28 via LP52 and DP27/28/ CP27. During the start-up period it also synchronises the start-up oscillator via CP16/DP16/RP16.

As the circuit starts up DP38 develops about 13V across CP38. This supply powers TP28/32/33 and also, via the potential divider RP02/3, switches on TP01. As a result the supply to the start-up oscillator is effectively removed and it stops, leaving the chopper transistor under the control of IP60 which, via the PWM feedback, compensates for variations in the mains supply voltage and the VCR's current consumption, keeping the various voltages derived from the chopper transformer's secondary windings constant.

Transistors TP24/26 provide drive limiting in the event of excessive current demand from any of the circuits within the machine. CP22 and DP22 develop about -6V across CP24. This voltage is linked to the base of TP26 via RP25. When the chopper transistor TP37 switches on a positive voltage is developed across RP37. This appears at the base of TP26 via RP26. As a result TP26's base is normally at around -2V. Should the current demand be excessive TP37 will remain on for a longer period during each cycle of the switch-mode power supply's operation and the voltage developed across RP37 will rise. Should the voltage at the junction of RP25/6 swing positively TP24/26 will switch on, interrupting the drive to TP37. TP24/26 form a monostable oscillator which will remain on long enough to allow the circuit to stabilise and resume normal operation.

As voltages (2) and (3) rise slowly due to the time-contants RP12/CP14 and RP11/CP38, the chopper transistor is switched on for only very short periods initially, then for progressively longer periods until IP60 takes over. This constitutes a soft-start system, to ensure that the power is brought up slowly.

We'll next take a closer look at the operation of IP60. The inputs to the voltage comparator stage are at pins 1 (feedback from PP57) and 2 (reference voltage from pin 12). The second comparator (input pins 13 and 14) is so biased that it does not affect the regulation. Pin 3 provides a feedback path to stabilise the comparator,

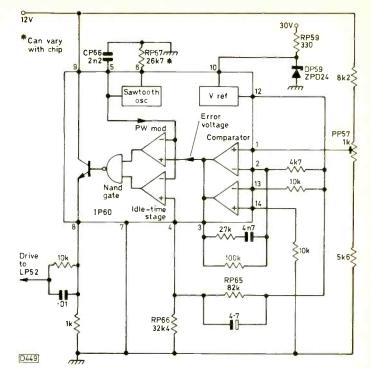


Fig. 2: The MC34060 regulator chip.

whose output at this point is applied to the non-inverting input of the following pulse-width modulator. The other (inverting) input to this stage (pin 5) comes from the internal sawtooth oscillator whose timing components CP66 and RP67 are connected to pins 5 and 6 respectively. The point during the sawtooth when the pulse-width modulator's output changes state depends on the error voltage. In this way a variable pulse-width drive waveform is produced to control the on/off times of the chopper transistor. The oscillator runs at approximately 20kHz.

The pulse-width modulator's output is one input to a NAND gate whose other input comes from the "idletime" stage. This stage receives the sawtooth waveform at its inverting input and the reference voltage from pin 12 at its non-inverting input (pin 4) via a potential divider (RP65/6). It produces at its output a constant pulse-width 20kHz signal. When both its inputs are positive the NAND gate provides a negative-going output. The maximum pulse-width output from the NAND gate is therefore determined by the output from the idle-time stage. This provides stable limiting of the maximum output pulse width provided by the chip.

The chopper transistor TP37 is driven by a complementary-symmetry driver stage (TP32/33). When T28 is turned off by the output from IP60 TP32 conducts and TP33 is cut off. CP32 charges until there is sufficient forward bias for diodes DP32/3/4 to turn on. This arrangement provides the correct drive conditions for TP37 which switches on. When TP28 is switched on again by the PWM drive TP32 is turned off and TP33 conducts, discharging CP32 via TP37's base current. As a result TP37 is rapidly switched off. The flow of current in LP40's primary winding is thus interrupted and the magnetic flux it created in the transformer's core collapses rapidly. This produces a high back-e.m.f. in the primary winding and the other windings coupled to the core. These secondary outputs are rectified to produce the various rails required by the VCR.

IP60 monitors the 12V supply and as a result of the tight coupling of the other windings to LP40's core all the

supplies derived from the transformer are stabilised.

The snubber network RP08, DP08, CP08 is included to protect TP37 from the fast-rising transient that would otherwise be present when it switches off.

Many of the supplies derived from the chopper transformer are fed to a switching circuit which consists of a simple transistor logic arrangement controlled by two switching signals – see Fig. 3.

In the standby mode the on/off monitor line is low because of the connection via RP93 to the -25V line. When the machine is set to the tuner (E-E) mode the on/off monitor line goes high, switching on TP77. As a result TP75 switches on and the 12V supply is applied to the signal circuits. TP73 also switches on, allowing 7V to be fed to the low-level servo stages and to the 5V regulator IP73. The latter supplies 5V to the signal circuits and to the collector of TP88. When play is pressed the servo on/off line ges high, switching on transistors TP71 and TP70. Thus 16V is passed to the servo system. In addition TP83 and TP88 are switched on to supply 12V and 5V to the servos. As a result of this arrangement power is applied to the servos in correct sequence.

Servicing

Switch-mode power supplies are about to become a way of life in the video sector. Though many engineers may hanker after the traditional mains transformer and static regulator designs, the switch-mode power supply operates at higher efficiency and does this at lower cost and less weight. Now to the servicing aspects.

The FV30's power supply, also the similar arrangements used in the FV31 and FV32, have a characteristic which, in human beings, would be described as volatile. Care is therefore required when servicing these power supplies as mistakes like forgetting to change the testmeter to volts from amps when checking a voltage, or

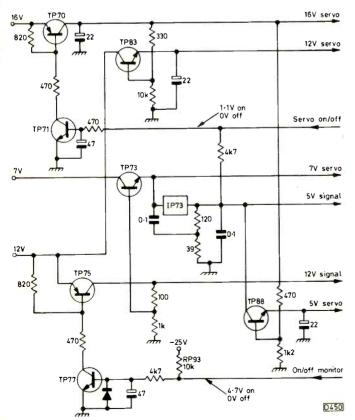


Fig. 3: The power switching circuitry.

a slight slip of a meter probe, will cause mayhem amongst the directly-connected transistors. Great caution is also necessary because of the high voltages present.

We should point out from the start that the circuit is sensitive to mains-borne transients. This can be the cause of repeated failure in the field. Make sure that the connections to the mains plug are sound and that the wall socket is satisfactory. If a domestic appliance is suspected of creating mains-borne voltage spikes, try fitting a suitably rated VDR to the offending item's mains input – or to the mains input in the VDR. These VDRs provide effective transient limiting.

The most common failure is a dead machine with fuse FP01 blown. In this event the chopper transistor TP37 is suspect number one. If you find that it's short-circuit RP37 will almost certainly have suffered as well. It should be investigated and if necessary replaced. If RP37 has been damaged it's certain that other items will have been affected because the 300V supply from the mains bridge rectifier will have passed via the shorted TP37 to the driver and preceding stages. It's therefore advisable to check TP24/26/28/32/33 plus diodes DP22/24/27/28/32/ 33/34. The start-up oscillator normally survives, but DP11, DP08 and DP38 could also have been damaged and may need replacement. It's often more economical to replace all the semiconductor devices en masse rather than risk another catastrophy when you switch on.

Say you've replaced all the dead silicon but you're reluctant to switch on before making certain that the same event won't instantly occur. Check the copper tracks around RP08 and the soldering to this resistor. These steps could save further mass destruction. Look for cracks in the print and bridge any you find with hook-up wire between the nearest solder pads.

A stage by stage check can now be made to ensure that all is well. First, if you've fitted a new TP37 take it out again! Remove TP01 and DP21. The start-up oscillator should now run continuously. Look for a sawtooth signal at the emitter of TP17 and check for 3V across CP14. There should also be about 12V across CP38. If there isn't, check that RP37 is o.k. The drive signal is applied to the base of TP28, but under these conditions it may be insufficient to turn TP28 on.

With no drive TP28 is on and TP32 is off. Check this part of the circuit by turning off TP28, using a shorting link between TP28's base and "chassis" – remember that it's live on this side of the chopper transformer. TP28 should switch off, TP32 on and TP33 off.

Checking the trip circuit under these conditions is not easy. A suggestion is to connect a 1.5V dry cell between the base of TP26 and "chassis", positive side to TP26's base, with a 470 Ω resistor in series with the cell to limit the base current. This should turn TP26 on and indicate whether the trip circuit is likely to work in the restored power unit.

The regulator chip IP60 can be checked with the aid of a 12V supply. You need to apply this to test point BP08 and the positive side of CP47 as IP60 requires supplies at pins 9 and 10 to get going (the latter supply is normally derived from the 30V line). Connect an oscillope to pin 8 of IP60. If the chip is working you should see a pulse output.

You will find that you can work on the power supply more easily if it's removed from the cabinet. Desolder the mains lead and use another one for testing if you've no desire to struggle with the one fitted to the cabinet. Bare live terminals will be all too readily accessible, so great care must be taken.

When you are sure that your checks confirm that the unit will run, replace TP01 and DP21, fit TP37 and switch on. If you have a variac you can be more prudent, using it to set the mains input at 110V before you try the unit. If the power supply works under these conditions, set the 12V rail correctly (monitor at test point BP08) by adjusting PP57 *slowly*. Then raise the mains input to 240V and check that the 12V setting is maintained. If you've been thorough the power supply should work normally and the machine can be returned to its owner. If you haven't – go back to square one and try again!

The House Husband

Les Lawry-Johns

Well here I am, still trying to get used to retirement: confined to the bungalow and wondering what to do after I've done some of the jobs a housewife does. I never realised how hard they work and the different things they have to do. H.B. goes out most mornings to earn a few bob and I'm left to my own devices. I suppose I'll get used to it but I don't know when. The shop hasn't sold yet and I don't suppose it will for a while. If things don't change I might even rent it out to someone. At least that would help me pay the bank a little of what I owe it. I still get a few jobs, some of which might interest you.

For example the Philips G11 set I had to pick up the other day. There was only a vertical white line in the centre of the screen. This told me that the line timebase was working but the line scan coils weren't being driven. On inspection I found that the scan coupling capacitor C3135 (0.91μ F) had bulged out. When it was removed and checked it proved to be open-circuit. I found a replacement of the same value and rating but of more rectangular shape and fitted it, ensuring that it didn't touch any nearby components. When the set was switched on again there was a full raster but no vision or sound. I had to tune in all the stations as the owner had probably tried retuning in an effort at clearing the white line. It was then soak tested for a while before being returned to the owner who was pleased that it had been done so quickly – and cheaply (I can't bring myself to charge the current rates).

The next set I had to visit was a Bush one fitted with the Rank T20 chassis. This had no visible picture. The e.h.t. was o.k. so I took the coward's way out and increased the first anode voltages. This produced a picture but I'd forgotten the brightness network, so I couldn't do the job properly. The customer seemed to be quite happy however so I left him with it. I know a resistor had gone high in value but I didn't have the circuit with me. I may go back and do the job properly one day: when he calls me again for something else.

Then there was the Philips K30 with a scrambled picture and poor sound. I'd repaired the set some time ago – removing the aerial socket and repairing it. I thought that the present trouble would be a repeat performance but when a screwdriver was placed in the socket a much better picture was resolved. So I checked the cable from the VCR and then connected the main aerial cable to the set directly. The picture was till scrambled and as the plug and cable were o.k. I had to refer the owner to an aerial rigger. I used to put up aerial cable to the set directly. The picture was still

The jobs are not all that many, which is why I'm not writing so much. It's mainly a question of doing things like peeling the potatoes, which I'm doing while H.B. is out teaching her daughter to drive. Nobody did that for me. I had to teach myself on an airfield in Egypt. The

second time I drove the lorry a Chief Petty Officer hailed me down and asked for a lift. As I was driving he commented "you blokes amaze me the way you can handle these vehicles". I didn't like to tell him I couldn't drive and wasn't licenced. A few nights later I was in charge of the night guard and had to post several men around the airfield. It was coming up for midnight so I popped over to the marine section and borrowed one of their lorries. While I was driving it around the hangers the port side wheels slipped into a hollow and the whole thing turned over. Luckily no one was hurt but we were unable to turn it back up. I waited till the next morning before reporting it and was subsequently charged and brought up before the C.O. As the officers from my squadron appeared on my behalf I got off lightly. A month's stoppage of leave I think, which didn't mean much being stuck out there. It's funny that I can remember such things that occurred fifty years ago but can't remember what happened yesterday.

But I can remember popping down to the shop when who should turn up but Beardy and Nonbeardy. This surprised me after the dust up we'd had on the previous occasion. They carted in a Philips K30 and said that it went off a few moments after it was switched on. When I switched it on I could hear the sparking. After removing the back cover I saw the arcing around the e.h.t. cap. I switched off and to my surprise the cap wasn't even clipped on. So I cleaned the area around the top of the tube and sprayed it with antistatic solution, then looked at the cap which was in a sorry state. I had to clip it off and look for another one, then peel the insulation back to prevent further discharge. Having done this it was just a matter of soldering the leads and pulling back the covering. When I clipped on the cap and switched the set on it came to life and stayed that way. After refitting the rear cover it was time to face the intrigued two.

"That's that" I said.

"Is that all it was?" said Beardy. "We don't have to pay for a little thing like that, do we?"

"Oh yes you do, and the next time you can try to do it yourself" I commented, wondering whether they would remember to discharge the e.h.t. cap to earth as I had done if they did try. After a struggle I manged to get £15 out of them before they left, vowing never to return to such a pricey establishment.

When I got back to the bungalow Stan from SEME called, not to take an order but to see if I was still alive and to see H.B. He left me the latest SEME catalogue which is full of interesting things. After he'd gone H.B. started on me.

"That cassette in the car is mucking about all over the place."

I'd fitted it only the week before and it was brand new. So that's another job I've got to do. I suppose I may get around to doing it one of these years . . .

CD Player Casebook

Sony Laser Problems

I've had a few problems recently with Sony laser assemblies. The type concerned is the KSS-150, which is used in various machines from different manufacturers. Various symptoms have been present. The first time I had trouble was with a Sony CDM20S that suffered from focus problems (jumping and skipping, etc.). Next there was a Denon DCD920 which spun the disc backwards at TOC readout. A Yamaha CDX630XE came in with the focus offset control at one end, while a Samsung CD ghetto blaster had no light emission at all. All these machines were fitted with variants of the KSS-150. Replacements cured the various faults. M.L.

Technics 5LP-420

Amongst the domestic machines available, Technics, Sony and Philips players are my favourites. When working correctly they knock spots off many other makes, especially the cheaper ones. This particular Technics player however produced all the signs of having a nasty fault: the laser assembly wouldn't return to the centre of the disc for TOC readout. I tried the plugs and sockets, to no avail, then took the main board out to check circuit protectors IC4 and IC5. As everything seemed to be all right I replaced the panel and ordered a service manual. Thought I'd just check again - and the machine worked! When I took the board out a second time I saw the cause of the problem. There were bad dry-joints around the regulators. A good old solder up and the machine worked very well. So there you are madam: your CD player is repaired but now weighs 3lb M.L. more than when you brought it in!

Pioneer Laser Problems

I've had problems getting the right laser unit for recent Pioneer models. Pioneer now supply revised versions of their lasers and until I discovered the code we were putting the wrong laser in certain machines. Most of these assemblies look exactly alike and all use the same method of fitting. They also have the same pin connections to the flexi PCB. The original part numbers were:

PWY1003, used in Model PDM-50 for example PWY1007, used in Model PDX-940 for example

The correct replacements are type PWY1010 for the PWY1003 and type PWY1009 for the PWY1007. The two different types of laser are not interchangeable. If you fit a PWY1010 in place of a PWY1009 or vice versa it will not work and you could end up with the same fault symptom you had before. It's easy to do, I've done it and believe me you can be chasing your tail for hours. So check the part number with the manual first, then when the new one arrives check it against the replacement part numbers above. M.L.

Pioneer Multiplay PDM-610

This machine wouldn't eject the CD magazine fully. Instead of ejecting it by a couple of inches there would be partial ejection with the magazine jammed inside the player. I watched the operation of the mechanism for some while before I realised what was going on. Basically, the machine didn't return the disc into the magazine fully when eject was pressed. Thus the machine couldn't carry out the full eject operation.

The mechanism is rather complicated and difficult to explain. What was happening was that the lever that returns the disc into the magazine moved too slowly. It's driven by two sliding plastic plates beneath the top half of the mechanism. These two drive plates are separated by two ball bearings, presumably to reduce friction, and the problem was that one of the ball bearings was missing.

Stripping the mechanism is easy. Putting it back together isn't! But I was pleased that when everything had been reassembled after replacing the ball bearing the machine played and ejected perfectly. M.L.

Yamaha CDX2

We've had many of these machines with the complaint that the drawer will not open, close, does so intermittently or produces an occasional smell of burning. In all cases we've found that transistors TR220/1/2/3 have failed. Yamaha recommended that in addition to these motor-control transistors the 7V regulator TR232 and the mechacon control chip IC401 (MSM6404A-42RS) should be replaced. It seems that the chip can on occasions produce open and close control signals at the same time. Following this advice has cured the problem on all the machines I've had until recently when a player that had previously suffered from the problem was returned. There was a bit of additional information however – the player hadn't been used for some time.

After much thought I recalled that an almost identical circuit is used in the Yamaha CD2. My records showed that we'd not had failures of this type with the CD2. The difference is that with the CD2 the mechacon chip is on the main PCB while in the CDX2 it's on a small subpanel (operation 2). The problem turned out to be due to dirty contacts on the three- and four-pin plugs associated with the drawer limit switch and the logic drive betwen IC401 and TR220/1/2/3. K.H.C.P.

Denon DCD1300/1500/1700

On examination you may find that when the complaint with one of these machines is skipping and jumping the motor drive to the laser sled is very erratic in direction and seems to move with large jumps. In almost every case we've found that the cause of the fault is not the sled motor or its control but a laser with very low output. So check this first before ordering a very expensive motor. If the laser is poor I suggest you give the customer a quote as the laser assembly is even more expensive at approximately £150. K.H.C.P.

Interference from CD Players

Since the introduction of low-power Band II Community radio stations I've started to receive f.m. tuners for checking with the complaint that the local stations are sometimes "noisy" or "slightly unstable". No fault has been found with the tuners but on house calls to several customers I've discovered that they sometimes switch from playing a CD to the tuner in their hi-fi separates system without stopping the disc, allowing it to play to the end. The "unstable" interference is caused by the harmonics of the player's PLL, as it tracks the data from

Long-distance Television

Roger Bunney

April was a relatively quiet month, though there are indications that sporadic E conditions are already building up: a minor SpE spell occurred during the month, which is always a good pointer for a reasonable season to follow. The log below is varied and includes a flurry of excitement. Reception is SpE unless otherwise indicated.

- 5/4/90 TVE (Spain) ch. E2.
- 6/4/90 During a minor F2 opening Simon Hamer logged Australia ch. 0 at 1215 GMT, also TSS (USSR) ch. R1 and an unidentified ch. E2 signal, probably from the Arabian Gulf.
- 7/4/90 ARD (West Germany) E2.
- 9/4/90 +PTT (Switzerland) E2; TVE E2; TVP (Poland) R2.
- 10/4/90 TSS Eeste R2.
- 11/4/90 RAI (Italy) IA, B; Telemarket E2, TVA IA and a third Italian E2 signal these are all "Private" stations.
- 12/4/90 RTP (Portugal) E3.
- 14/4/90 TVE E2; unidentified E2 programmes.
- 18/4/90 TVE E2; TSS R1, 2; YLE (Finland) E3; TDF (France) L3; RAI IC.
- 19/4/90 +PTT E2, 3.
- 20/4/90 TVE E2, 3.
- 21/4/90 TVA IA.
- 22/4/90 TVE E2.
- 23/4/90 TVE E2, 3, 4; RTP E2.
- 28/4/90 JRT (Yugoslavia) E3, 4; CST (Czechoslovakia) R2.
- 30/4/90 DR (Denmark) E3; +PTT E3; TVE E3.

A massive auroral event was seen on the evening of the 10th, giving signals throughout Band I and into Band III. RTE (Ireland) was seen on chs. B, D, F, G, H, I and J, all with distortion and the characteristic humming effects.

There was a minor tropospheric opening from the 23rd to the 26th, with signals mainly from West Germany, Denmark and the Benelux countries. High pressure at the end of the month, continuing into early May, produced an established lift and at the time of writing reports of reception from West/East Germany and Denmark are coming in from DXers in Scotland and down to the southern UK. The weather maps suggest that this could be a "big" one.

My thanks to the following for sending in reception reports: Tim Anderson (St. Leonards), Roger Fussell (Torpoint), Iain Menzies (Aberdeen), Peter Schubert (Rainham), Simon Hamer (Powys), David Glenday (Arbroath) and Bill Cotterill (Tipton).

The French La Sept service is to transmit to Czechoslovakia and Poland via the TDF satellite. The service will include a compilation of East European offerings,

TELEVISION JULY 1990

the disc, getting out of the player and into the tuner. If the player is on but stopped the interference is not apparent or at worst there's a slight hiss. The best cure is physical separation of the tuner/aerial lead and the CD player. I've found that Philips machines in particular give rise to this complaint. **K.H.C.P.**

CNN, MTV and sports from current satellite fare. Poland hopes to transmit the La Sept service for three hours daily on each TVP network.

Superchannel, currently at 13°E, is to move to a new higher-powered satellite in the Eutelsat-2 series due for launch later this year. There are to be six Eutelsat-2 series satellites in all, one held as an in-orbit spare. Eutelsat has also confirmed that it's seeking tenders for the Europsat DBS craft which it hopes to launch in the mid 90s.

News Items

Rumania: There is now regional programming at several locations, usually between the morning and afternoon network programmes and after the main network close-down at night. The networks now call themselves TRL – Televiziunea Romana Libera. TRL-2 is back on air. During 1300-1330 local time weekdays TRL-1 relays the satellite distributed French-language programme Canal France Internationale.

East Germany: The GDR TV network is now known as DFF (Deutscher Fernsefunk), as it was in the early 70s. Test cards show either DFF-1 or DFF-2. Regional programming is spreading, with "Nord Report" going out from the Rostok studios over the Schwerin, Marlow and Helpterberg transmitters at 1600 local time. The Dresden studios will provide the next regional opt out, from the Dresden, Lobau, Leipzig and Karl-M-Stadt transmitters. Following German reunification DFF-1 will transmit ARD-1 and DFF-2 ZDF-2, with private stations such as RTL+, Sat 1 etc. also being transmitted in the GDR area. Neighbouring countries have agreed in principle to permit DFF programming in their schedules. RTL+ is to start transmissions on ch. E44 at 100kW e.r.p. soon.

Czechoslovakia: CT-1 (Russian service relay) is now carrying a mix of satellite distributed programming including the French TV5 service.

Lithuania: Ch. R38 (600kW e.r.p.) now carries the Polish TVP-1 service, Leningrad TV having been dropped.

Iceland: All Stod-2 programmes (Reykjavik ch. E12) are now scrambled. There are plans for a second commercial service to start this autumn, using the logo SYN-TV – with scrambling.

Greece: More private stations are due to open – to date the government has received over a hundred applications from programmers seeking channels. Several private stations are at present on air illegally.

Poland: It looks as though advertising will be included with TVP-2. The country's first private station, TV Echo, is now transmitting from Wrocklaw on ch. R28 for four-five hours daily. Satellite programming is included. Lublin is to have its own station soon. TVP-3 Warsaw is now on ch. R44.

Spain: The Channel 9 regional station in Valencia is now in operation, transmitting from 1900-2400 weekdays and longer at the weekends. Approval has been given for the start of a fourth nationwide service.

Cyprus: Coverage is being increased in the Turkish



Times past. On the left the 1938/9 BBC tuning signal from Alexandra Palace. Arrows A and B had been added in the magazine (see text) to indicate particular points. The centre photo shows BBC announcer Elizabeth Cowell while that on the right shows Jasmine Bligh, another BBC duty announcer, both received in 1938 at the New York RCA research station via F2 layer propagation. Alexandra Palace operated on ch. 1 (vision carrier 45MHz).

controlled area. A new transmitter in the far eastern part of the island will broadcast to Israel, Syria and the Lebanon.

Africa: TVZ (Zanzibar) is seeking funds to upgrade its system. A microwave link is being set up between Libya and Egypt. A new station and studio are to be set up in Rwanda within five years.

New Zealand: Private stations are being set up, using the u.h.f. channels. It's thought that with careful planning twelve main and sixty relay transmitters could be accommodated.

Amateur radio: Over 120 permits have been issued in Italy allowing 50MHz operation with 6W input to the aerial. Limited 50MHz operation is now allowed in Egypt, and in West Germany amateurs can in most areas operate at up to 25W e.r.p. with horizontal polarisation.

From our Correspondents . . .

George Gaskin, our correspondent in Gibraltar, has installed a WB4 Band I wideband array atop the block of flats in which he lives. His first reception turned out to be not exactly exotic! Noting a weak ch. E3 TVE signal he assumed that good tropospheric conditions were providing him with reception from the Canaries. It later transpired that reception was from a communal distribution system over the border at a distance of 1km. Identification was established when computer-generated advertisements were inserted.

Wenlock Burton writes from Victoria, Australia reporting that a teletext service, Austext, is now carried on his local ch. 7. It includes promotions for "Data Broadcasting", a firm specialising in point-to-point links similar to page 777 on Oracle.

W. Drake in Lowestoft is currently using XG21W and Fernseh aerials for DXing and has experienced considerable success with tropospheric reception, including DFF ch. E34 and signals from Denmark and West Germany.

David Tilley has received several satellites as well as Astra using his 60cm Amstrad dish. He wants to swap his JVC C-210KM FST receiver, in new condition with PAL/SECAM/NTSC (3.58/4.43) and baseband inputs/ outputs, for a JVC FST set incorporating teletext. Write to him at 6 West Down, Ashthomas, Tiverton, Devon EX16 4NR or telephone 0884 820 765.

EBU Listings

Belgium: Two American Forces stations have been listed this month, clearing up a mystery. They are Everbert ch. 33 with 2kW e.r.p. and Florennes ch. 34 at

10W e.r.p., both with horizontal polarisation. Note that AFRTS Shape continues to use ch. 34 with 4.5kW e.r.p. vertical. These transmitters all use 525 lines.


Holland: Smilde ch. E6 and Markelo ch. E7 (NOS-1) now have two-carrier sound.

France: Many new La Cinq and M6 transmitters are listed. Those with over 1kW e.r.p. are as follows: Valenciennes ch. E34 M6, ch. E49 La5, 5kW horizontal; Chalon-Sur-Sadne ch. E41 M6, ch. E44 La5, 2kW vertical; Parthenay ch. E60 La5 30kW horizontal.

New DX-TV Array

Bearing in mind environmental considerations, there's long been a need for an efficient, compact v.h.f. array for DX use covering Bands I, II and III. I was asked to produce such a design by Aerial Techniques, and the result is shown in the accompanying photograph. At the rear of the array there's a three-element wideband system covering chs. E2-4 (48-70MHz) with a gain of typically 2-4·5dBd over the range 50-65MHz. For Band II a three-element proximity coupled system covers 75-100MHz (chs. R3-5 and IC) with a gain of around 2·5dBd: it's coupled to the Band I dipole by the closely spaced discrete Band II elements at each side of the main folded dipole. At the front there's an eight-element wideband system covering 175-230MHz (chs. E5-12) with a gain of 7-9dBd.

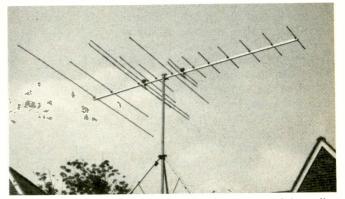A single one-inch sided square boom is used with half-inch diameter hard-drawn seamless elements throughout, giving a really strong system. Connections can be made to each dipole (low v.h.f. and high v.h.f.) using 75Ω feeders. Alternatively a phasing harness with single feeder or a diplexer can be used. For DX use separate feeders are best. The photograph shows the



The new TV-DXing/export wideband v.h.f. aerial available from Aerial Techniques.

TELEVISION JULY 1990

aerial prior to being erected on a conventional mast and less feeder(s). Aerial Techniques is distributing the aerial – see nearby advertisement or phone 0202 738 232 for further details.

DTI News

The Radiocommunications Division of the DTI is to operate as an "Executive Agency" in future. Its aims are laid down as providing an effective, quality service to radio users by managing the radio spectrum, allocating and assigning radio frequencies and ensuring interference-free use of the spectrum. This should mean obtaining licences more quickly for fixed, mobile and marine applications.

The Agency has listed frequencies allocated for "independent programme making" for contracted work to IBA franchise holders and the BBC and for radio/TV links. The frequency bands to be used impinge on the conventional TV broadcasting bands used for TV-DXing. For radiomicrophones, at 10mW or less, the frequencies are 191.9, 208.3, 216.1, 583.455, 584.435, 585.570 and 588.4MHz - the latter four frequencies will be subject to geographical limitations after mid-1992. The bands for talkback and sound links are: 48.4-48.5MHz (8 12.5kHz channels); 52.85-52.95MHz (8 12.5kHz channels); 199.6-199.8MHz (20kHz channels); 457.25-457.35MHz (8 12.5kHz channels); 460.5-460.75MHz* (20 12.5kHz channels); 462.75-462.85MHz (8 12.5kHz channels); 467-467.25MHz* (20 12.5kHz channels); 854.75-855.25MHz (20 25kHz channels); 860.25-860.75MHz (20 25kHz channels). Allocations asterisked are temporary.

Times Past

A reader has sent me several copies of vintage TV magazines, all pre-war, that make very interesting reading. *Television and Short Wave World*, dated April 1939, claimed to be the "first television journal in the world", though No. 1, Vol. 1 of *Television*, the "world's first television journal", appeared as the monthly official organ of the Television Society back in March 1928 (it continues to be published by the Royal Television Society). The content of this latter issue was mainly concerned with mechanical scanning, selenium cells and televisors. The 1939 magazine informed readers of progress with French TV from an experimental station at Montrouge, using 405 lines. Details of the studio and transmitter are given – the latter fed 6-8kW to the aerial, providing signals over a 20km radius.

TV activity was on the increase in 1939. NBC and RCA were conducting experimental services in Washington, USA. JOAK-TV intended to transmit a 25-frame signal from a 100m mast at the Kamatacho Laboratory, Tokyo. In London an OB relay point had been established at Swains Lane, Highgate, with onward connection to Alexander Palace via coaxial cable. The BBC was planning to build a transmitter in the Manchester area, and setmakers were operating at full capacity – one large company had a 30 per day quota and was 350 receivers behind schedule.

A 1939 article on receiver problems and transient distortion used the BBC tuning signal to illustrate various points. Of DX interest are two photographs of F2 reception taken in October 1938 at RCA's Riverhead, Long Island establishment. They show 405-line signals from Alexandra Palace!

TELEVISION JULY 1990



	EL	CTRONIC	COMPO	NENT DIS	TRIBUTORS
AN115	2050	TA7063 60g	STK0029	TIP33 500	
AN203	2000	TA7069 180p	STK0040	TIP41A 20p	VOLTAGE I.C. SOCKETS
AN340P		TA7140 120p	STK0050	TIP42C 230	REG 8 PIN 050
AN610P		TA7208	STK0080 675p	MJE340. 25p	7000
AN3310K		TA7214	STK043	MJE371	/012
AN5011		TA7230 160p	STK080	MJE521 350	7005 20 PIN 121
AN5071	120p	TA7233235p	STK082 700p	. 2N3055	7012 25 ZZ PIN 14
AN5256		TA7267	STK435	2N3773	7008 35a 24 PIN 150
AN5410		TA7317150p	STK459	2SA350 60p	ZENER DIODE 40 PIN 200
AN5512 AN5615		TA7325	STK563		
AN5015		TA7401	STK2028 600p		317 COLL 0C. LEU 3
AN5732	1550	TA7604	STK2230 570p STK2250 910p		LOWALLO Smm B C V 10
AN6340		TA7628	STK2250		241-004
AN6371	5000	TA7654	STK3042	2SA949 80p 2SA1060 145p	DIODES
AN6912	.2250	TA7668	STK1070 1185p	2SA1103	IN4001
AN7105	2000	TA7757	STK4121 780p	2SA1166	IN4002 04p IN5402 08p IN4003 03p IN4148 04p
AN7224	.2100	TA8111	STK4121-2780p	2SA1220 110p	BY133
AN7421	2500	TBA120S 650	STK4191-2. 1060p	2SA1250	
BA301		TBA231A 140p	STK4332	2SA1306 80p	IOLERS
BA328	85p	TBA540	STK4352	2SB176	HITACHI VT11 FF/REW IDLER 155p HITACHI VT9000 PLAY IDLER 295p
BA402	50p	TBA120U 50p	STK5325 640p	2\$B337145p	HITACHI VT9000 FE/REW IDLER 249p
BA682		TBA820M 50p	STK5331 400p	2SB435198p	JVC HR7650 REEL IDLER
BA1330	150p	TBA890	STK5332	2S8507	JVC HR7650 TAKE UP CLUTCH 2756
BA6219	315p	TBA1441 165p	STK5471	2SB524	JVC HR7650 TAKE UP IDLER 145p
BA6235 HA1137	. 1750	TCA650 285p	STK5482 500p	2SB548	AKAI VS4 TAKE UP IDLER 4250 AKAI VS4 FF/REW IDLER 4250
HA1137	1500	TCA660. 180p TCA830. 78p	STK6325 400p	2SB557 160p	AKAI VS4 FF/REW IDLER 425¢ PAN NV730 FF/REW/PLAY IOLER 3500
HA1377	1800	TCA830	STK7216 600p	2S8596	PAN NV370 PLAY IDLER 1850
HA11221	2000	TCA3089	STK7404 672p STK8250 700p	2SB646 70p 2SB701 122p	PAN NV2000 PLAY IDLER 90p
HA11244	1650	TDA311V	STK7217 6400	2SB701	PAN NV7000 CLUTCH
HA12002	2800	TDA1010	STK7308	2S8829	PAN NV333 FF/REW IOLER
HA13001	185p	TDA1012 105p	STR370 630p	2588886	HRD 110/120 CARRIAGE 2350p HRO 110/120 CAPSTON MOTOR 2050p
HA13403	550p	TOA1029 280p	STR441 460p	2SC380 20p	
KA2101	1650	TDA1047	STR451	2SC506	SPECIAL OFFERS
LA1207	.245p	TDA1170S 100p	STR455	2SC998	
LA1260	.300p	TDA1412 100p	STR456A	2SC1018 185p	VIDEO HEADS
LA1352	145p	TOA1908A 95p	STR1096 400p	2SC1172	
LA1365	.110p	TDA2002 110p	STR4090 625p	2SC1185 300p	JVC-FERGUSON-ITT 3HSS(v) 975p
	.110p	TDA2005 110p	STR6020 480p	2SC1293 45p	PANASONIC 4HSS(N) 1000p JVC-HRD140-150 2385p
	.110p .115p	TDA2700	STR40090590p	2SC1342 108p	PANASONIC NV730-770 2800p
	650	TDA2578A	STR50103A 580p	2SC1394	PANASONIC NV600 (3Head) 2200p
LA4185	.300p	TDA3560	STR58041	2SC1413 230p	PANASONIC NV366 (4Head Ong 3672)
	130p	TDA3562 225p	STK4843	2SC1569	PANASONIC WV450 (3Head) 2200p
LA4445	2150	TDA2600 465p	STK4311	2SC1678 112p	PANASONIC NV470-NVG10-G11 (3Head) 2200g
LA5523		TDA2530	STK7309 6500	2SC1682 1450	HITACHI VT5000-VT5500. 1900p
LA5527	140p	TDA3590 320a	AC141	2SC1730	HITACHI VT8000-VT9500 1700p
LM301	250	TDA3653	AC142 35p	2SC1942 1800	SONY C20-C30-C40
LM339	35p	TDA4100 325p	ACY20	2SC2238	8U208A (Min 10P/Cs) 600p
LM318	1150	TDA4503 652p	AU113	2SC3466	BU508A (Min 10P/Cs)
LM358	. 40p	TDA3652 485p	BC182A 07p	2SD357 38p	Please phone us for types not listed
LM747	. 55p	TDA46002D	BC108 08p	2SD387 75p	Please add 60p post & packing and then add 15% VAT TO THE TOTAL
LM1112	235p	TDA4600/2	BC307B 08p	2SD560	
		TDA3654 390p	BC337	2SD612 80p	All items subject to availability, and prices can change without notice.
LM3915	.240p .225p	TDA3590	BD135	2SD655	Govt, colleges, schools & institutes
LB1405	225p	UPC324C	BD124	2SD792	orders accepted. All components are
M5143P	2850	UPC571H. 190p UPC1001H 200p	BD238 32p BF240 12p	2SD819	brand new. Best quotations given on
M5186AP	.3250	UPC1161C140p	BF259 700	2SD836	large quantities
M5214	1150	UPC1178C 1050	8U126 68p	2SD849	Export-Mail Order enquiries welcome.
M5219L	1600	UPC1177	BU208	2SD898B	Access and Visa accepted.
M50120	700p	UPC1197C 1200	BU208A 700	2SD995L	the second se
M51381P	240p	UPC1212C 170p	BU208A (JAP) 900	2SD1135 1000	J.J. COMPUNENTS
M54544AL	635p	UPC1230H2150p	BU326A 75p	2S01153 40p	63, THE CHASE, EDGWARE,
M58485	.900p	UPC1366 175p	6U407	2SD1265 110p	MIDDY HAD EDN FUELAND
M33712	138p	UPC1397C 300p	BU500 105p	2SD1365	MIDDX. HA8 5DN, ENGLAND
M3722	300p	UPC4558C 50p	8U508A 80p	2SD1397 240p	Tel: 081-952 4641. Fax: 081-952 4641
M3731	280p	UPC1378H210p	BU508D	2SO1492 300p	CALLERS BY APPOINTMENT ONLY

EC	ON	IOM	IC D	EV	ÍCE	S F	PO B	OX	1	5, N	10	LVE	R	HAI	ИF	рто	N,	W	/2	4A	Z
15/80H 15/85B 17052 17053 17074 17089 17127	2.72 3.28 4.58 5.61 9.30 3.45	2SC1678 1 2SC1741 1 2SC1810 1 2SC1815 0 2SC1826 0 2SC1829 2	S8 AN2140 25 AN234 70 AN236 20 AN240P 67 AN241 25 AN245 50 AN253	2.40 5.09 3.33 0.99 1.71 5.04 1.80	BC207 BC212B BC213L BC214 BC225 BC237 BC238	0.19 8D 0.26 80 0.10 8D 0.10 8D 0.40 8D 0.10 8F 0.10 8F	X54B 0.31 X62A 2.09 X63A 1.96 Y20 1.21 Y81 1.16 115 0.29 117 0.66	BU126 BU137 BU205 BU206 BU207 BU208 BU208/02	1.10 6.53 1.15 1.27 1.65 1.12 2.35	HA1196 HA13001 HA1306 HA13402 HA13342 HA13365 HA1366WR	7.43 1.73 2.25 7.06 2.65 4.02 2.88	MC1330P MC1350P MC1351P MC1352P MC1357P MC1357P MC1358P MC14493P	1,98 0.45 1.25 1.40 2.15 1.48 5.50	SAS560T SAS570T SAS570S SAS580 SAS6600 SAS660 SAS660	5.42 5.42 1.95 2.85 1.33 1.33 1.33	STR1096 STR4090 STR440 STR451 STR453 STR454 STR454 STR6020	11.20 6.43 6.18 6.18 8.16 5.52 6.96	TBA970 TBA990 TCA270S TCA270SQ TCA290A TCA290A TCA420A TCA4400	3.60 1.98 2.15 1.05 2.39 2.16 2.25	TDA4440 TDA4442 TDA4500 TDA4600-2 TDA4610 TDA4620 TDA4620 TDA4620	1.95 4.15 4.75 1.75 3.40 7.75 14.20
17376 1N4001 1N4002 1N4003 1N4004 1N4005 1N4005	1.58 0.04 0.06 0.05 0.05 0.05 0.08	2SC1893 3 2SC1906 0 2SC1921 1 2SC1923 0 2SC1929 2 2SC1929 2 2SC1942 1 2SC1959 0	.02 AN260 98 AN272 37 AN295 30 AN301 25 AN302 98 AN305 20 AN315 95 AN316	3.85 7.92 7.63 2.45 3.09 8.88 2.46 4.95	BC238B BC239B BC251A BC294 BC300 BC301 BC302 BC303	0.08 8F 0.25 8F 0.31 8F 0.50 8F 0.38 8F 0.34 8F 0.53 8F 0.53 8F	121 0.25 123 0.13 127 0.13 137 0.29 153 0.58 154 0.26	BU208D BU209 BU226 BU326A BU326A BU406 BU406D	1.12 1.43 1.75 2.55 0.99 1.24 1.24 0.54	HA1367 HA13688 HA1368 HA1370 HA1374 AA117 HA1377 HA13898	2.75 1.95 2.65 3.71 1.80 9 1.95 2.05	MC14494P MC14497 MC14510BAL MC14511BCP MC14528BCP MC1712 MC5192 MC7724CP	2.15 7,10 3.75 1,10 2.15 3.88 19.50 3.49	SAS670 SAS6710 SBA750 SC84203 SC9504P SDA2006 SDA2006 SDA2112/2 SG264A	1.33 2.21 1.61 19.35 1.95 17,10 9.20 5.26	T6029V T6035V T6036 T6037 T6044V T6045 T6049	7.98 0.73 0.67 2.11 0.97 1.20 1.45	TCA530 TCA640 TCA650 TCA6608 TCA730 TCA750 TCA8000 TCA8305	2.24 2.25 3.05 2.60 2.75 2.25 5.95 2.38	TDA5700 TDA7270S TDA8190 TDA9403 TDA9503 TDA9513 TDB1033 TDB1081	2.75 2.25 4.30 3.70 2.92 3.15 2.68 7.24
1N4007 1N4148 1N4448 1N5401 1N5402 1N5403 1N5404 1N5408	0.03 0.05 0.11 0.13 0.18 0.10	2SC1953 1 2SC1962 1 2SC1969 1 2SC1983 0 2SC1985 1 2SC2009 0	.53 AN318 .53 AN318 .53 AN320 .83 AN321 .51 AN322 .55 AN337 .34 AN340P .33 AN355	7.16 5.47 2.25 6.78 5.37 1.53 1.65	BC307A BC308A BC309 BC317A BC327 BC328 BC337	0.06 8F 0.11 8F 0.17 8F 0.13 8F 0.09 8F 0.11 8F 0.09 8F	158 0.18 159 0.18 160 0.31 167 0.38 173 0.34 177 0.55 178 0.400	BU412 BU426A BU500 BU508A BU536 BU608 BU705	5.29 1.67 1.53 1.50 1.55 1.85 2.50	HA1389 HA1392 HA1394 HA1397 HA1398 HA1406 HA1452	2.39 2.22 2.65 2.75 2.75 2.07 0.85	MCR106/5/6 MCR220/7 ME0431 ME6002 ME6102 ME8001 ME8001 ME0411	123 125 075 026 028 034 0,75	SG613 SG629 SG6533 SI1125H SI1630HD SKE2F1/04 SKE2G3/04	10.70 8.27 9.00 7.50 20.62 1.25 0.73	T6052V T6058 T6059 T9003V T9005V T9011V T9013V T9014V	0.87 3.06 4.22 1.25 2.38 1.40 4.95 2.42	TCA890 TCA900 TCA910 TCA940 TCA940E TD3F800R TD3F800H TD3F900H TDA1001B	5.44 2.04 1.65 0.82 2.93 4.78 5.50 2.31	TEA1002 TEA1009 TEA1014 TEA1020SP TIC106C TIC106M TIC44 TIC45	4,93 0,80 3,00 4,93 0,61 0,65 0,72 0,55
1N914 1S1555 1S44 1S921 2N2219A 2N3053 2N3054	0.18 0.10 0.10 0.37 0.35 0.99	2SC2063 0 2SC2078 3 2SC2073 1 2SC2085-0 1 2SC2091 1 2SC2141 2	AN362 19 AN370 39 AN5111 54 AN5120N .65 AN5132 .30 AN5250 .44 AN5610 .87 AN5612	150 3.95 3.43 4.50 4.42 4.40 7.43 2.20	BC338 BC368 BC440 BC441 BC454 BC454 BC460 BC461 BC462	0.12 BF 0.19 BF 0.69 BF 0.46 BF 0.36 BF 0.42 BF 0.47 BF 0.51 BF	180 0.36 181 0.32 182 0.34 183 0.39 184 0.43 185 0.39	BU807 BU826A BUW84 BUX84 BUX85 BY126	0,98 1.40 1.95 0.66 0.50 0.69 0.13 0.13	HD14538 HD38702-A2 HD38750A53 HD38750A-7 HD38800A50 HD44801A05 HISH1010 HISH1004	2.07 7.95 5.77 7.25 14.09 14.07 14.60 6.00	MJ2501 MJ3001 MJ481 MJE2955 MJE3055 MJE340 MJE520 ML231	3.30 1.43 1.53 3.30 1.25 0.49 0.49 0.99	SKE4F1/06 SKE4F2/08 SKE4F2/06 SKE4F2/10 SKE4F2/10 SKE4F3/10 SKS1/10 SL1310	0.38 1.07 0.80 1.36 0.96 1.36 2.15 3.14	T9016 T9019W T9034V T9035V T9051 T9054V T9057V	1.02 1.98 1.34 6.65 7.70 5.98 3.44	TDA 1003A TDA 1005A TDA 1005A TDA 1006A TDA 1010AF TDA 1011 TDA 1010 TDA 1011A	1.47 2.22 7.00 4.25 1.14 1.05 1.51	TIC47 TIP120 TIP110 TIP112 TIP112 TIP121 TIP121 TIP126	0.77 1.55 0.35 0.45 0.95 0.40 0.38
2N3055 2N3442 2N3702 2N3703 2N3705 2N3705 2N3706 2N3707 2N3711	1.16 0.14 0.18 0.15 0.14 0.16	2SC2216 0 2SC2233 1 2SC2236 1 2SC2278 1 2SC2278 1 2SC2314 0 2SC2335 + Kit 7	ANS612 ANS630 ANS630 ANS701N ANS630 ANS701N J4 AN6250 J87 AN6300 .00 AN6310 .26	4.20 3.95 1.68 1.75 4.40 4.54 5.62	8C463 8C478 8C479 8C532 8C546 8C547 8C548	0.30 BF 0.32 BF 0.41 BF 0.28 BF 0.08 BF 0.10 BF 0.10 BF	195 0.14 196 0.17 197 0.24 198 0.17 199 0.17 200 0.37 218 0.36	BY133 BY164 BY176 BY179 BY182 BY182 BY187 BY189	0.10 0.44 0.93 1.42 1.05 0.77 1.76	HISH1002 HM6231 HM6232 HM6251 HM7103 HM9032 HM9012	9.50 12.24 7.20 5.69 4.85 4.00 3.22	ML2328 ML2378 ML238 ML923 ML926 MM5314N MM5316N	3.01 1.95 5.65 3.10 3.58 8.99 3.50	SL1430T SL414 SL432A SL439 SL471 SL480 SL490	2.31 3.69 3.44 2.48 2.13 7.24 2.37	T9062V T9064 TA7027 TA7050 TA7051 TA7054 TA7060AP TA7061AP	0.49 4.20 1.74 1.74 2.55 0.71 1.27	TDA1028 TDA1034B TDA1035S TDA1035T TDA1037 TDA1037 TDA1037D TDA1044 TDA1044	2.45 2.42 2.95 1.70 1.79 2.05 2.10	TIP132 TIP137 TIP29 TIP2955 TIP29A TIP29B TIP29C TIP29D	0.99 0.96 0.84 0.86 0.46 0.63 0.40 0.75
2N3771 2N3772 2N3773 2N3819 2N3823 2N3904 2N3908	1.56 1.55 1.61 0.40 1.17 0.50 0.62	2SC2565 4 2SC2570 1 2SC2577 1 2SC2578 6 2SC2671 0 2SC268A 1 2SC288A 1	L10 AN6341 .85 AN6363 .34 AN6531 .75 AN6551 .91 AN6552 .85 AN6610 .50 AN7111	2.22 16.00 1.95 0.50 0.68 1.86 1.25	BC549 BC550 BC556 BC557 BC558 BC559 BC559 BC560C	0.10 BF 0.11 BF 0.08 BF 0.10 BF 0.10 BF 0.10 BF 0.14 BF	240 0.19	BY207 BY208 BY210-400 BY210-600 BY210-800 BY223	1.62 0.22 1.15 0.18 0.31 0.19 1.25 2.60	HM9015 HT4207 HT4208 KA2101 KC581C KC582C L200CV LA1201	324 1325 20.65 1.00 7.75 4.85 1.69 0.75	MM5318N MM5369N MM5387AA/N MM5841N MN1400VL MN1405 MN1435VX MP1192	3.11 2.01 6.20 6.93 13.65 7.92 8.81 5.07	SL901B SL918A SN16861AN0 SN16862AN SN16966N SN29717N SN29715N	8.32 9.07 0.82 2.98 10.25 7.19 3.66 6.04	TA7061AP TA7069 TA7070P TA7072P TA7074P TA7076P TA7089P TA7089P TA7092P	127 3.13 1.83 2.57 1.98 7.50 3.10 9.94	TDA1047 TDA1059B TDA1054M TDA1060 TDA1082 TDA1082 TDA1151 TDA1190 TDA11902	325 0.80 121 2.60 325 0.95 127 2.48	TIP3055 TIP30A TIP30C TIP31A TIP31B TIP31C TIP32A	0.75 0.66 0.41 0.40 0.34 0.38 0.30 0.35
2N4101 2N4240 2N4444 2N5293 2N5294 2N5296 2N5297 2N5298	2.68 1.66 0.50 0.50 0.50 0.50 0.50	2SC373 1 2SC383 1 2SC388 1 2SC388 1 2SC394V 0 2SC403C 0 2SC458 0	40 AN7115 .16 AN7145 .33 AN7145 .37 AN7145 .81 AN7151 .81 AN7156 .60 AN7158 .34 AN7218 .392 AN7223	2.52 2.80 9.90 2.37 3.37 2.10 0.80 4.55	BC635 BC636 BC637 BC639 BC640 BCX34 BD115 BD116	0.20 BF 0.24 BF 0.15 BF 0.24 BF 0.55 BF	256 0.15 257 0.34 258 0.33 259 0.34 262 0.57 263 0.57	BY226 BY227 BY228 BY229-1000 BY229-600 BY255	0.15 0.20 0.60 1.12 1.20 0.13 1.23	LA1210 LA1230 LA1320 LA1357N LA1363 LA1364 LA1365J	1.56 1.18 2.87 9.00 1.05 3.02 1.45	MP2794 MP2812 MP8512 MPC596 MPF256C MPS6570 MPSA42	4.00 5.07 1.57 2.13 0.60 0.48 0.15	SN29722 SN29723AN SN29764AN SN29767 SN29770BN SN29770BN SN29771BN	11.95 8.77 2.60 3.90 3.69 5.75 5.59	TA7093P TA7102P TA7108P TA7109 TA7122B/P TA7122P TA7124P TA7129P	3.99 5.88 1.61 3.71 0.87 2.34 1.90	TDA1200 TDA1235 TDA1236 TDA1270 TDA1327A TDA1327A TDA1412 TDA1420	1.51 3.88 4.30 3.74 6.93 1.08 1.52	TIP32B TIP32C TIP33 TIP33A TIP33C TIP34 TIP34	0.46 0.28 0.82 1.02 0.95 0.75 0.36
2N6109 2N6130 2N6133 2N6180 2N6292 2SA1006 2SA1011	0.85 1.25 0.73 1.60 1.50 1.65	2SC535 0 2SC536 0 2SC537 0 2SC605L 1 2SC605L 1 2SC620 1	35 AU107 L79 AU110 L06 AU113 L54 AY106 L16 BA524 .46 BA310 .54 BA1310	7.72 5.69 14.63 2.90 8.94 0.14 1.50	BD124 BD131 BD132 BD133 BD135 BD135 BD136 BD137 BD137	0.42 BF 0.42 BF 0.53 BF 0.36 BF 0.36 BF 0.41 BF	273 0.21 274 0.20 324 0.22 336 0.33 337 0.31 338 0.34 355 0.44 362 0.66	BY299 BY407 BY409 BY448 BY713 BYW56	0.20 0.60 0.90 1.49 1.40 1.12 0.29 0.23	LA1385 LA1387 LA3350 LA3361 LA3390 LA4032P LA4100 LA4100	1.53 4.75 1.43 1.60 5.52 2.35 1.25 1.30	MPSA56 MPSA92 MPSU05 MPSU10 MPSU56 MPSU60 MR818 MR854	0.00 0.15 0.86 1.70 0.65 1.33 0.33 0.50	SN29791 SN29798N SN2709 SN7400N SN7401N SN7401N SN7402N SN7404N SN7408N	1.67 5.56 0.44 0.61 0.36 0.65 0.52 0.27	TA7130P TA7136AP TA7137P TA7141AP TA7146P TA7148P TA7148P TA7149P TA7152P	1.27 1.89 0.98 3.87 4.85 1.67 3.26 3.16	TDA1440 TDA1470 TDA1470P TDA1506 TDA1506 TDA1510 TDA1512 TDA1515 TDA1559	3.45 2.90 4.25 5.74 4.60 2.57 2.55 3.15	TIP41B TIP41C TIP42A TIP42B TIP42C TIP47 TIS43 TIS90	0.31 0.51 0.29 0.79 0.50 0.65 1.43 0.21
2SA1015 2SA1012 2SA1020Y 2SA1020Y 2SA473 2SA766S 2SC1173Y 2SC1474	0.80 0.99 0.45 0.75 4.95 1.25	2SC681 2SC682 1 2SC682 1 2SC684 1 2SC693 0 2SC710 1 2SC711A 0	L67 BA1320 40 BA1322 38 BA1330 65 BA145 163 BA145 15 BA154 156 BA155 126 BA155 1278 BA156	1.38 3.95 2.75 0.19 0.25 0.40 0.12 0.05	00138 00139 00140 00144 00150 00157 00157 00160 00163	0.24 BF 0.35 BF 1.43 BF 0.75 BF 0.67 BF 1.60 BF	363 0.50 371 0.50	BYX71-600 BYX71-350 BYY56 BZY93C30 C106D C106M CA3046	0.85 0.88 1.48 1.86 0.37 0.76 1.55	LA4102 LA4112 LA4125 LA4138 LA4138 LA4140 LA4192 LA4220	0.75 1.35 2.25 4.98 0.70 1.50 1.25	MR914 MSM5816RS MSM5840H MVS460-02 NE542 NE555 NE556	1.20 17.35 12.26 0.34 2.75 0.36 0.65	SN7410N SN74121 SN7413N SN74141N SN74151AN SN74154N SN74154N SN74190	0.27 1.60 0.37 2.65 1.51 1.27 1.35	TA7161P TA7162P TA7172P TA7172P TA7193P TA7204P TA7206P	4.50 3.61 1.41 1.75 4.80 1.95 12.49	TDA1670 TDA1770 TDA1905 TDA1908 TDA1908 TDA1940 TDA1950 TDA2005	2.72 2.88 1.27 2.55 3.26 2.50 1.76	TL011CP TL494CN TLD72CP TMP4320 TMS1024NLL TMS1025N TMS3720ANS TMS3748NS	11.95 S 5.25
2SC1509 2SA1095 2SA1103 2SA329 2SA489 2SA490 2SA490 2SA493 2SA552	1.35 3.00 6.00 1.17 1.32 2.25	2SC734 1 2SC783 3 2SC790Y 1 2SC828 0 2SC867A 3 2SC876 0 2SC930 0	43 8A159 198 BA182 185 BA222 128 BA302 104 BA311 196 BA312 154 BA313 13 BA317	0.09 0.19 1.66 1.24 0.65 1.45 0.76 0.04	BD166 BD175 BD179 BO181 BO182 BD183 BD184 BD187	0.28 BF 0.30 BF 0.99 BF 0.99 BF 0.99 BF 0.99 BF 1.21 BF	450 0.25 451 0.25 457 0.41 458 0.45 459 0.26 460 1.60 469 0.33 469 0.33	CA3090AQ CA3094 CA3094 CA3131EM CD4001 CD4002 CD4002 CD4008	0.83 3.25 1.72 2.95 0.24 0.27 1.35 0.20	LA4420 LA4422 LA4430 LA4440 LA4445 LA4460 LA4461 LA4461	1.72 1.00 2.88 2.55 1.80 1.50 1.60 1.19	NP1106 0A202 0A47 0A91 0A95 0C28 0C29 DC36	11.51 0.11 0.16 0.14 0.09 2.52 2.15 7.53	SN7420N SN7430 SN7440N SN7472 -SN7474N SN7490AN SN74US26N SN76001N	0.34 0.49 0.27 1.54 0.44 0.75 1.45 1.65	TA7207P TA7208P TA7210P TA7214P TA7215P TA7215P TA7217AP TA7222 TA7226	1.48 2.15 1.45 3.63 2.58 1.45 1.95 3.57	TDA2006 TDA2004 TDA2002 TDA2003 TDA2030 TDA2030 TDA2140 TDA2150 TDA2151	1.35 0.99 0.90 1.00 1.05 4.77 4.48 2.47	TMS3755 TMS3894NL TMS5102NLL TUA2000 TY60108 ULN2204 UPA53C	9.66 19.25 6.25 8.96 2.97 8.50 4.94
23A302 2SA564 2SA614 2SA628 2SA639S 2SA659 2SA673 2SA684	0.62 4.88 0.37 1.75 0.49 1.50	2SC940 4 2SD1128 2 2SD1138 0 2SD1273 1 2SD1453 1 2SD152K 2	1.68 BA318 2.90 BA328 2.94 BA333 2.94 BA333 2.94 BA335 2.33 BA5102A 2.64 BA511 2.87 BA514	0.09 2.22 1.37 6.27 2.15 1.95 1.00	80189 80190 80201 80202 80203 80204 80204	0.43 BF 0.55 BF 0.49 BF 0.60 BF 0.46 BF 0.41 BF 1.73 BF	471 0.25 472 0.33 479 0.65 480 0.85 491 0.55 506 0.43 532 0.24	5 CD4012 8 CD4013 1 CD4016 8 CD4017 0 CD4020 8 CD4021 4 CD4023	0.24 0.33 0.25 0.30 0.75 0.39 0.28	LA7020 LA7025 LA7027 LA7040 LA7040 LA7042 LA7800 LA7801	13.86 11.97 10.92 9.20 3.90 1.30 3.21	0C44 0C45 0C72 0C75 0N236 0N782 0T121 0T5042	1.95 0.18 0.44 1.06 1.65 1.45	SN76013ND SN76023N SN76023ND SN76033N SN76110N SN76115AN SN76131 SN76227N	7.45 2.97 3.91 5.54 0.90 1.61 0.82 2.45	TA7229P TA7230P TA7233P TA7240AP TA7240AP TA7245P TA7310P TA7313AP TA73134	4.66 1.35 3.61 2.55 1.95 2.15 0.65 3.50	TDA2160 TDA2161 TDA2170 TDA2270 TDA2520 TDA2522 TDA2522 TDA2524 TDA2525	4.01 5.11 4.75 2.50 2.25 11.20 4.50 5.58	UPC1003 UPC1009C UPC1025H UPC1028H UPC1032H UPC1032H UPC1042C UPC1156H UPC1161C	5.95 6.32 2.90 0.82 8.95 3.94 4.98
2SA697 2SA699 2SA715 2SA748 2SA817 2SA835 2SA836 2SA836	0.95 1.95 0.18 2.50 0.89	2SD24 2SD257 2SD292 2SD313 2SD325D	0.47 BA521 0.60 8A524 2.29 8A526 1.38 8A527 1.09 8A532 2.92 BA536 2.126 BA6209 1.05 BA656	1.20 8.94 7.96 2.98 1.20 0.99 1.06 1.51	B0208 B0222 B0225 B0228 B0229 B0232 B0234 B0237	0.46 BF 0.63 BF 1.05 BF 0.49 BF 0.42 BF 0.36 BF	596 0.11 597 0.2 694 0.2 757 0.5 759 0.4 761 1.0 762 0.3 865 0.4	7 CD4028 2 CD4040B 8 CD4047 7 CD4047 5 CD4047 5 CD40452 4 CD4066	0.64 0.84 0.45 1.06 0.24 0.33 0.23 0.23	L81274 LC7800 LD3120 LD3150 LM1017N LM1877 LM2808 LM2877	1,90 9,20 1,13 2,75 1,81 2,95 5,94 7,45	PT6042 PT8504 R1038 R1039 R2008B R2009 R2010B R2010B R2029	325 5.13 2.19 2.19 1.33 1.58 2.98 1.33	SN 76226DN SN 76226DN SN 76228N SN 76242 SN 76243 SN 76396 SN 76533N SN 76532N	2.98 3.27 5.23 5.23 2.90 2.47 0.91	TA7323P TA7325P TA7339P TA7340P TA7607AP TA7609 TA7611AP	3,15 1,15 1,85 5,95 1,30 2,35 2,32	TDA2532 TDA2530 TDA2541 TDA2540 TDA25450 TDA25450 TDA2560 TDA2575A	2.50 2.20 1.00 0.99 5.94 2.50 0.50	UPC1182H UPC1186H UPC1181H UPC1185H UPC1185H UPC1188 UPC1212C UPC1225H	1.38 1.05 1.35 2.10 8.77 0.80 2.82
2SA872 2SA884 2SA937R 2SA940 2SA940 2 2SA950 2SA950 2SA951	0.59 2.15 0.97 2.23 2.14 0.72 1.75	2SD353 2SD389 2SD401 2SD414 2SD471 2SD560 2SD600 2SD6000 2SD6000000000000000000000000000000000000	A.50 BA7100 241 BA841A 1,40 BA843 1,90 BA854 2,13 BAV18 2,95 BAV19 2,96 BAV20	11.35 28.96 3.96 5.76 0.06 0.24 0.36	80238 80239 80240 80241 80242 80243A 80243C 80244 80244	0.45 BF 0.57 BF 0.39 BF 0.37 BF 0.62 BF 0.50 BF 0.42 BF	870 0.3 959 0.4 960 0.5 970 0.3 R39 0.4 R61 0.3 R62 0.5	2 CD4081 9 CD4093 9 CD4511 4 CD4528 2 CD4556 0 CR02AM 8	0.25 0.14 0.40 0.52 1.47 1.70 4.19	LM317CKC LM324N LM339N LM340K EM340K EM340N LM360N LM567CN	1.08 0.98 0.43 11.85 2.15 1.50 1.71 10.23	R2030 R2257 R2265 R2305 R2322 R2323 R2354A R2354B	1.33 2.35 1.49 1.18 0.67 0.76 0.64 2.01	SN76545 SN76546N SN76549 SN76570 SN76611 SN76620 SN76660N SN76666N	4.87 3.47 2.45 3.08 2.59 2.59 2.48 1.20	TA7616P TA7622AP TA7628P TA7629P TA7630P TA7640AP TA7672P TA7676P	5.25 8.94 1.40 7.50 0.95 2.40 2.75 2.81	TDA2578A TDA2576A + TDA2581 TDA2581 TDA2582 TDA2591 TDA2594 TDA2593 TDA2595	2.95 Kit 12.35 1.60 1.35 2.15 2.45 1.99 2.46	UPC1230 UPC1238 UPC1278H UPC1351C UPC1350C UPC1353 UPC1355C UPC1363	1.88 2.10 5.95 1.81 1.40 1.63 2.13 4.20
2SA966-Y 2SA999 2SB774 2SB185 2SB375 2SB400 2SB400 2SB405 2SB511	0.65 1.13 3.87	2SD613 1 2SD636 0 2SD639-R 1 2SD655 0 2SD657 2 2SD661A 0	1.65 BAV21 1.03 BAW62 1.04 BAX12 1.05 BAX12 1.07 BAX13 1.96 BAX16 2.80 BC107B 2.80 BC108B 2.11 BC109B	0.12 0.11 0.49 0.11 0.08 0.11 0.15 0.14	B0244C B0245C B0245C B0253 B0278A B0317 B0318 B0375 B0380	0.83 BF 0.85 BF 1.05 BF 0.70 BF 1.20 BF 2.72 BF 0.42 BF	R79 0.2 R81 0.2 R86 1.0 R89 1.6 R90A 0.6 X29 0.3 X84 0.3 X85 0.3	9 CX095D 8 CX104 3 CX108 7 CX109 4 CX130 7 CX134	4.19 3.14 8.77 12.48 7.20 8.76 4.50 11.49	LM6402/011 LM6402A093 LM748 LM8360 LM8361 LR3419 LR3471 LU1141	10.15 0.69 3.87 2.95 9.37 9.37 7.27	R2443 R2461 R2540 R2540X R2615 RCA2060 RGP01-15	1.36 1.50 1.65 3.30 0.67 2.00 0.70	SN 76708 SN 76709N SN 76707N SN 76705N SN 76730 SN 76810N SN 76832N	4.86 9.63 1.23 2.97 5.54 0.60 1.35	TA7726P TAA320A TAA350A TAA570 TAA621AX1 TAA661B TAA691	10.25 1.27 6.59 1.85 4.85 0.95 8.58	TDA2600 TDA2611AQ TDA26120 TDA2611A TDA2610 TDA2610 TDA2620 TDA2630	7.00 2.80 4.68 1.25 2.79 1.96 2.50	UPC1362 UPC1365C UPC1366 UPC1360C UPC1378H UPC141C UPC1458	1.80 2.50 1.65 2.30 1.95 4.95 2.90
2SB54 2SB546 2SB56 2SB618A 2SB631 2SB643 2SB669	1.39 0.56 2.80 2.22 2.00 0.50 3.67	2SD773 2SD811 2SD823 2SD837 2SD841 2SD856 2SD8570	0.60 BC113 7.63 BC119 1.96 BC126 1.48 BC132 1.75 BC135 0.89 BC137 1.84 BC138	0.14 0.36 0.20 0.14 0.14 0.18 0.34 0.33	BD410 BD433 BD434 BD435 BD435 BD435 BD436 BD437 BD438 BD441	0.49 BF 0.44 BF 0.45 BF 0.49 BF 0.49 BF 0.45 BF 0.52 BF 0.59 BF	TX86 0.3 FX87 0.5 FX88 0.3 FX89 0.4 FX50 0.3 FY51 0.3 FY52 0.2 FY79 0.4	CX157 CX158 CX177 CX187 CX187 CX755 CX885A	11.83 5.52 10.45 8.80 5.26 12.95 6.85 0.40	LU52012 LU52011 LU03112 M193 M21C M23C M293 M51102L	20.62 14.95 12.37 6.83 1.10 1.38 6.71 2.77	RGP10 RGP30M RT402 RT905A S1299 S2800D S2802 S2818 S3702S	0.23 0.28 1.58 3.20 5.34 1.50 2.90 4.05 5.21	SN94041 SN94042 SPS5384 ST1702L STA401 STA441C STA471C STK0029	5.54 4.35 1.98 0.99 2.49 2.70 8.70 9.55	TAA700 TAA930 TAA970 TAG626-600 TBA120AS TBA120SB TBA120SB TBA120T TBA120U	2.37 4.36 2.83 1.20 1.45 0.40 0.57 2.50	TDA2631 TDA2640 TDA2652 TDA2653 TDA2653 TDA2654 TDA2670 TDA2680 TDA2680 TDA2740	2.73 3.80 9.62 5.16 4.73 2.48 3.20 10.14	UPC151C UPC2002 UPC30C UPC324C UPC32C UPC32C UPC339C UPC41C UPC4556C	2.95 1.48 2.51 4.70 4.95 4.35 2.99 1.24
2SB681 2SB695 2SB774 2SB819 2SC1096 2SC1104 2SC1106 2SC1114 2SC1116	3.96 1.98 0.65 1.13 1.16 3.98 4.54 3.25 4.35	2SD894 2SD896 2SK105H 7805-T022 7808 7812-T022 7815	I.15 BC139 I.75 BC140 2.19 BC141 2.15 BC142 0.63 BC143 0.45 BC147 0.35 BC148B 0.64 BC148C	0.30 0.31 0.26 0.34 0.14 0.13 0.11	B0442 B0509 B0510 B0519 B0529 B0530 B0533 B0534 B0535	1.64 Bl 0.75 Bf 0.78 Bf 0.75 Bf 0.69 Bf 0.67 Bf 0.52 Bf	FY90 0.8 FY90 2.2 R100 0.2 R101 0.7 R103 0.8 R303 1.1 RC84 2.0 RX44 0.6 RX44 0.6	6 E5024 3 E5386 6 GD243 7 GF758 5 HA11215 8 HA11211. 0 HA11225	0.28 0.25 1.95 0.84 1.75 2.53 4.29	M5115P M51203L M51231P M5134 9341 M51353P M51381P M51393AP	5.24 3.15 0.95 4.13 5.25 5.98 4.50	S40W S6080B SA8063 SAA1006 SAA1020 SAA1025 SAA1025 SAA1024 SAA1075	13.10 9.98 5.17 1.85 4.76 4.40 2.50 4.25	STK0050 STK016 STK022 STK031 STK040 STK054 STK058 STK058	7,85 11,23 8,95 12,95 13,34 9,35 27,50	TBA120A TBA1440 TBA1441 TBA395 TBA395 TBA396 TBA400 TBA440C TBA4800	1.05 1.94 1.95 1.10 1.20 2.39 2.34 1.30	TDA2780AQ TDA2795 TDA2791 TDA2910 TDA3300B TDA3300 TDA3506 TDA3501	9.12 2.78 1.81 13.25 7.24 3.16 4.40 5.50	UPC474 UPC554C UPC575C2 UPC580C UPC587C2 UPC592H UPC595 UPC595 UPC596	5.11 1.85 1.55 6.60 1.34 2.15 2.95 1.98
2SC1124 2SC1129 2SC1131 2SC1158 2SC1162 2SC1172 2SC1172 2SC1195 2SC1213	1.26 1.65 0.64 3.33 0.55 2.22 6.09 0.89	7905 AD140 AD143 AD145 AD161 AD162 AF114	D.80 BC149B 1.06 BC153 1.93 BC154 1.60 BC159 0.65 BC160 0.65 BC161 2.47 BC168 0.90 BC169C	0.13 0.14 0.14 0.16 0.40 0.28 0.36 0.16	B0536 B0537 B0538 B0544B B0677 B0679 B0680 B0681	0.50 81 0.50 83 0.67 83 0.75 83 0.33 83 0.43 83 0.43 83 0.66 83 1.48 83	RY39 0.6 SS38 0.7 STB0140G 4.9 STC0246 5.9 STC0233 6.1 STC0143 3.0 STD1043 2.1 SV57B 3.9	5 HA11235 0 HA11124 3 HA1125 9 HA1137W 2 HA1137W 2 HA1138 7 HA11414 5 HA1156 1 HA1156	3.46 1.95 5.25 4.29 1.38 3.75 4.20 1.16 5.79	M51394P M5142P M5144P M51513L M51515BL M51517L M5192 M5194AP	14.50 6.85 4.27 2.55 2.75 2.90 3.13 5.74	SAA1121 SAA1124 SAA1130 SAA1174 SAA1250 SAA1251 SAA1351 SAA3027P SAA5000	7.44 2.60 6.69 7.77 3.95 3.20 8.11 2.71 3.25	STK077 STK1039 STK2110 STK2145 STK2240 STK2250 STK3042 STK3044 STK4019	928 5.75 7.33 16.95 16.65 18.95 6.08 5.75 9.29	TBA510 TBA520 TBA530 TBA540 TBA560C TBA5700 TBA5700	1.37 1.29 1.30 1.72 1.40 1.60 1.71	TDA3501 TDA3500 TDA3510 TDA3520 TDA3540 TDA3540 TDA3560 TDA35710 TDA3576	5.50 7.58 5.95 9.71 2.20 2.22 5.83 3.63 7.48	UPD1514C UPD2819C UPD553-164 UPD8049C-1 X0022CE X0029CE X0031CE X0035TA X0040TA	4.76 4.98 19.52 111.50 5.75 7.09 6.32 6.18 4.50
2SC1226 2SC1293 2SC1306 2SC1317 2SC1364 2SC1383 2SC1383 2SC1398 2SC1398	0.41	AF118 AF127 AF139 AF178 AF179 AF180 AF181	1.20 BC170 1.20 BC170 1.00 BC171 0.40 BC172B 1.45 BC173 0.55 BC174B 0.55 BC177 0.53 BC178 0.53 BC179	0.16 0.11 0.27 0.17 0.27 0.35 0.26 0.26	BD696 BD699 BD700 BD707 BD709 BD710 BD809 BD810 BD810 BD879	1.85 8: 3.70 8: 0.60 8: 0.80 8: 0.50 6: 0.45 8: 0.57 8: 0.57 8:	SW68 0.6 SX19 0.3 SX20 0.1 SY52 0.5 SY79 0.5 T108 1.4 T119 1.7 T120 2.1	4 HA1167 9 HA11706 0 HA11705 1 HA11703 5 HA11701 6 HA11710 7 HA11713 8 HA11713	6.60 6.60 3.61 8.00 3.45 3.57 3.45 2.90 9.40 9.99 7.76	M5231L M53274P M54532P M54544L M58478P M58485P MA06 MA8001	1.58 1.33 1.45 2.97 6.75 14.05 1.07 0.82	SAA5010 SAA5012 SAA5020 SAA5020 SAA5050 SAB1009B SAB3011 SAB3013	3.50 5.50 5.78 6.33 4.90 5.98 7.34 4.69	STK433 STK4332 STK435 STK4352 STK436 STK437 STK4372 STK460	6.18 4.75 7.12 1.95 5.95 6.91 13.13 9.36	TBA673 TBA700 TBA720 TBA730 TBA7500 TBA7500 TBA760 TBA800 TBA810S	2,60 1,85 4,32 3,55 2,50 1,71 1,08 1,61	TDA3590 TDA3591 TDA3650 TDA3652 TDA3651AC TDA3651AC TDA3651A TDA3651A	6.79 6.45 5.90 5.74 3.95 2.45 2.50 4.50	X0042CE X0043CE X0056CE X0057GE X0057GE X0074GE X0077GE X0079CE	4.50 4.35 6.25 6.00 5.77 15.29 14.60 4.95 4.95
2SC1446 2SC1447 2SC1475 2SC1505 2SC1505 2SC1514 2SC15730 2SC1583 2SC1583	1.25 2.07 0.60 1.00 1.37 1.91 0.34 3.99	AF239 AF279 AN115 AN155 AN206 AN208 AN210	0.53 BC182 0.88 BC182LB 0.98 BC183LB 1.99 BC183LB 1.89 BC184 2.58 BC184 8.55 BC186 2.28 BC187 3.25 BC214	0.09 0.14 0.09 0.70 0.13 0.25 0.28 0.35	BD895 BD901 BD902 BDW83C BDW84C BDX32 BDX53A BDX53A	2.18 B 0.55 B 0.56 B 0.99 B 1.65 B 4.93 B 3.35 B	T123 1,9 T151-800R 0.9 T76018 2.4 U106 2.4 U108 1.5 U109 2.2 U101 5.6 U125 2.4	8 HA11715 5 HA11714 2 HA11716 8 HA11725 0 HA11725MF 5 HA11755P 8 HA11781 8 HA1180	13.10 18.26 16.00 6.23 21.15 5.15	MC1310P MC1327P	1.16 1.99 1.85 1.69 1.75 2.99 1.95 1.33	SAB3021 SAB3024 SAB3209 SAB3210 SAF1032P SAF1039 SAS5010 SAS560S	3.95 6.36 5.82 3.21 2.99 1.95 8.39 1.91	STK466 STK4833 STK501 STK502 STK5314 STK5730 STK7216 STK772	10.10 9.52 6.32 7.25 9.48 3.20 14.90 3.71	TBA810T TBA820 TBA820M TBA830 TBA920 TBA940 TBA940 TBA950	1.75 0.66 0.82 3.50 1.65 1.87 1.55	TDA4050B TDA4280 TDA4290 TDA4400 TDA4420 TDA4422 TDA4422 TDA44275 TDA4421 TDA4421 S AT COST	3.40 7.20 1.95 4.90 2.30 8.32 9.00 2.27	X0092CE X0096CE X0109CE X0113CE X0113CE X0195CE X0204CE X0261CE ZPY120	620 11.25 9.48 9.60 8.74 8.98 3.25

USE YOUR	ACCESS O	RË	ARCLA	YCA	RD	ଞ T	EL (902	7120	83
	PLUS + PL	E/			FR MIXE	OM E		1 C	DINTS	ACH
AKAI Machine Nos.: VP77 VP88 VP7100 VS10 VS9300 VS9500 VS9700 VS-P1	VP7200 VS1 VS2 VS3 VS5	VHS A	NATIONAL PANASO Head Part Nos.: VEH0099 Machine Nos.: NV300 NV NV3000 NV7000 NV720	NIC 0103 0115 0 322 NV332 NV 00 NV7500	0121 0131 /333 NV340 N NV7800 NV7	V390 NV2000		HEADS Head Part No. BETA A		Pnce 1 + £17.50
AMSTRAD Machine Nos.: VCR4500 VCR5200 VC Machine Nos.: VCR7000		VHS T VHS R	NV8200 NV8400 NV8600 Head Part Nos.: VEH017 Machine No.: NV370 NV3 Head Part Nos.: VEH017	NV8610 NV86 VEH0218 3708	620		VHS B VHS M	BETA B BETA D BETA E BETA T		£16.95 £23.75 £34.49 £21.00
VCR4600 FERGUSON/JVC Machine Nos.: 3292 8903 3V00 3V01		VH4600	Machine No.: NV330 NV3 Head Part Nos.: VEH028 Machine No.: NV430 Head Part Nos.: VEH0174	777 6			VHS N VHS W	BETA W BETA X VHS VID VHS A	EO	£19.95 £31.92 £11.95
3V29 3V30 3V31 3V35 3V36 3V38 3V FISHER Machine Nos.: FVH — D520 D530 D	39 3V49	VHS A	Machine No.: NV366 SHARP Head Part Nos.: DDRMU	0002 HE17/2	1/27		VHS X	VHS B VHS C VHS D VHS E		£11.95 £18.75 £81.76 £75.43
P530 P615 P620 P622 P710 P720 P7 GEC Head Part Nos.: 5458161 5458165		VHS U	Machine No.: VC581/2/3 Head Part Nos.: DDRMU Machine No.: 2C9 VC1 VC386 VC387 VC388 VC4 VC9100 VC9200 VC9400	0001 HE00 0 10 VC200 VC 477 VC481 VC	002 HE02 04 (220 VC300 V 2482 VC930 V	05 06 /C381 VC384 C970 VC3300	VHS S VHS C	VHS F VHS H VHS I VHS K		£47.81 £21.28 £21.28 £21.25
Machine Nos.: 3436161 5436165 Machine Nos.: 4000H 4001H 4002H Head Part Nos.: 5458282 5458413 54 Machine Nos.: 4001H 4004H	158415 5458992	VHS I VHS K	VC9100 VC9300 VC9400 Head Part Nos.: DDRMU Machine No.: VC7300 VC Head Part Nos.: DDRMU Machine No.: VC6300	0001 HE09 7700 VC7750	00 009700		VHS D VHS E	VHS L VHS M VHS N VHS R		£81.87 £14.75 £26.95 £21.00
HITACHI Machine Nos.: VT3000 Head Part Nos.: 5458104		VHS A	Head Part Nos.: DDRMU Machine No.: VC8300 Head Part Nos.: DDRMU Machine No.: VC2300				VHS L VHS F	VHS S VHS T VHS U VHS V		£19.81 £18.98 £21.95 £29.00 £24.24
Machine Nos.: VT4000 VT4200 VT500 Head Part Nos.: 5458161 5458165 Machine Nos.: VT6500 VT7000 VT80 VT8700 VT9000 VT9300 VT9500 VT97	000 VT8040 VT8100 VT8500	VHS H VHS I	SANYO Head Part Nos.: 1430242 Machine No.: VTC5000 V	TC5150 VTC5	242 T22300 300 VTC5400		BETA D		FERGUSON	£35.00 £14.25
Head Part Nos.: 5458282 5458413 54 Machine Nos.: VT11 V14 VT33 VT34	453415 5458992	VHS K	Head Part Nos.: 1430242 Machine No.: VTC5350 V Head Part Nos.: 1430762 Machine No.: VTC9300 V	TC5500 T02000 TC9455 VTC9	<mark>5</mark> 00		BETA D BETA X	01X0 003 01X0 027 01X0 033 01X0 040	085 825 002	£31.35 £46.02 £47.05 £48.32
ITT Machine Nos.: VR3605 VR3033 VR39 VR3943 VR3963 VR3993 VR3975 VR3		VHS A	Head Part Nos.: 143072 Machine No.: VTC9300PS SONY	6 VTC9350	46 1476		BETA X	01X0 056 01X0 057 01X0 082 01X0 083	002	£61.55 £31.36 £46.02 £66.03
JVC (see also Ferguson) Machine Nos.: HP4000 HR3300 HR33 HR3750 HR3860 HR4100 HR7200 HR	20 HR3330 HR3350 HR3360 17600	VHS A	Head Part Nos.: A6762 0 Machine No.: SL3000, 80 Head Part Nos.: A6762 0 Machine No.: SL5W, 500 Head Part Nos.: A6762 0	000, 8080, SL 12A, 038A, 0 0 5100 SLC5,	T 6Me, 7, 7E. 55A, 129A C6, C7		BETA A BETA B	PHILIPS 310 274 4 691 200 5 691 200 9	4	POA £49.68 £62.02
MITSUBISHI Machine No.: HS200 HS700 HS303 HS304		VHS A VH700	Machine No.: SLC20, C3 SLF1, F30, HF72, T20, T Please see next col. for	0, C33, C40, 1 30	C44	5	BETA W	691 201 1 691 201 6 691 201 7 691 202 8	6 8	£61.66 £61.93 £49.96 £55.37
FERGUSON/JVC VID1 01X0-003-381 VID2 01X0-018-024	Tension band T3292/PU545904 Take up idler T3292/PU47752			2.55 6.73			VE	BEL		
VID3 01X0-018-025 VID4 01X0-018-729 VID5 01X0-040-006 VID6 01X0-033-454 VID7 01X0-040-007 VID8 01X0-040-017 VID9 01X0-065-009 VID10 01X0-065-016	Rewind idler assembly T3V16/ Take up idler T3V00/PU49280 Loading belt T3V29/30/PU4894 Roller Assy. (cass. Housing) T3 Take up idler 3V29/30/PU4896 Reel motor assembly 3V29/30// Capston motor 3V35/36/39/F Cass. housing Assy. 3V35/36/3	41-2 3V23/PU49 7B PU51381V PU55371V	1	6.20 7.96 0.26 4.50 2.45 27.95 20.92 22.55	VP 77 VP 68 VP 7100 VS 1 VS 2 EG VS 3 VS 5 EG VS 10 VS 9300 VS 9500 VS 9500	DBK135 DBK135 DBK103 DBK101 DBK101 DBK101 DBK104 DBK103 DBK103 DBK103	印 86 1 42 1 76 1 50 1 50	HR 2200 HR 3300 HR 3330 HR 3360 HR 3600 HR 3660 HR 4100 HR 7200 HR 7650 HR 7650	DBK137 DBK107 DBK126 DBK103 DBK107 DBK103 DBK127 DBK139 DBK132	20.68 25.25 21.65 21.42 25.25 21.42 22.50 21.42 20.86 20.86 20.85
GEC/HITACHI VID11 V5577355	GEC 4100/Hitachi VT11E capsi	iton motor		26.78	VS 9800 3292	DBK102 DBK103 FERGUSON DBK103 DBK103	£1.96 £1.42	HR 7700 NATIC NV 300 NV 330	DBK108 INAL PANASO DBK110 DBK110 DBK110	
VID12 V6413663 VID13 V6861471 VID14 V6861482 VID15 V6886971 VID16 V2423461	GEC 4000/Hitachi VT33 t/f rew GEC 4001/2/Hitachi 93/9500 t/l GEC 4001/2/Hitachi 93/9500 pl GEC 4004/Hitachi VT33 t/f rew ET541 Tuner Unit	f rewind ar lay idler as		2.10 2.07 4.20 1.80 13.50	3 V 01/16 3 V 22 3 V 23 3 V 24 3 V 31/32 3 V 35/36 3 V 38/39 3 V 42/43/44 3 V 45/48/54	DBK103 DBK103 DBK108 DBK137 VID7806 DBK150 DBK150 VID7540 VID7540 VID7540	1.42 1.42 10.85 1.40 1.40 1.25 1.25 1.25 1.95 1.95	NV 332/333 NV 336 NV 450 NV 777 NV 2000 NV 3000 NV 7000 NV 7200	VID7521 VID7521 DBK133 DBK131 DBK131 DBK131 DBK113 DBK111 DBK140	62.10 62.10 61.50 61.57 61.57 61.95 61.15
NATIONAL PANASONIC VID17 VXP0329 VID18 VXP0344 VID19 VXZ0078	Fast forward idler NV2000 Idler NV7000/7200 Tension Band NV7000	PI	EASE NOTE	0.85 0.85 2.85	3 V 55/57 VBS 7000 VBS 7600 VBS 7000	VID7540 FISHER DBK146 DBK105 DBK105	£1.95 £2.66 £1.15 £1.15	NV 8600 VC 381/383 VC 385/386	DBK112 SHARP DBK116 DBK116	£1.76 £2.15 £2.15
VID20 VXP0521 VID21 VXP0463 VID22 VXP0432 VID23 VXP0401	Idler NV370 Reel Idler NV777 Pinch Roller NV333 Idler wheel NV333	ALL	VIDEO SPARES HANDLING	1.65 4.30 3.50 0.85	VBS 9000 FVHP 420 V 4000 H V 4001 H	DBK10 VID7532 GEC DBK129 DBK129	£1.76 £1.99 £1.10 £1.10	VC 2300 VC 6000/6300 VC 6500 VC 7300 VC 8300 VC 9300/9500	VI07545 DBK117 DBK117 DBK118 DBK120 DBK121	22.15 22.15 20.99 21.40 21.40 21.50 22.10 21.20 22.65
SANYO/FISHER VID24 4529V10800 VID25 1430662T01201 VID26 PR2758 VID27 14304904009900 VID28 143044040300	Reel motor VTC5000/5150 Reel drive pulley VTC 5000 Pinch roller VTC5000/5150 Gear idler Fisher FVH-P615 Heart idler Fisher FVH-P615	£1	.25 + VAT	9.50 5.49 2.95 4.50 2.95	V 4002 H V 4100 H VT 11-VT 88 VT 3000 VT 5000 VT 5000 VT 6500 VT 7000 VT 8000	08K129 DBK128 HITACHI DBK128 0BK103 0BK125 DBK142 DBK142 DBK143 DBK129	1.10 1.95 1.95 1.42 1.46 20.77 20.68 1.10	VC 9700 SL 8000 SL 8080 SL 8500 SL 8500 SLC 5 SLC 5 SLC 6	SONY DBK115 DBK115 DBK115 DBK115 DBK100 VID7519	22.00 22.00 22.00 22.00 21.05 21.65
SHARP VID29 RMOTP1029 VID30 RMOTV1008	Capston motor 73/9300 Reel motor VC9700			29.95 16.14	VT 8500 VT 9300 VT 9500 VTC 5000.515	DBK144 DBK129 DBK129 SANYO VID7807 VID7807	£0.68 £1.10 £1.10 £1.19	SLC 5 SLC 6 SLC 7 SLC 9 SLJ 7 SLT 7 ME SLT 7 MER	DBK100 DBK130 DBK100 DBK100 DBK100	£1.95 £2.00 £1.95 £1.95 £1.95
VID31 NIDL0006 VID32 NIDL0005 VID33 NIDL0004	Idler VC387H etc Reel idler VC9300 etc Idler wheel VC2300			1.60 1.80 3.50	VTC 5000 VTC 5300 VTC 5400 VTC 5500 VTC 6500 VTC 9300	VID7807 DBK105 DBK105 DBK106 VID7533 DBK104 DBK145	E1.19 E1.15 E1.95 E1.00 E3.12 E1.70	V 55/57 V 66/67 V 7540 V 8600	TOSHIBA VID7543 VID7540 DBK123 DBK124	£1.95 £1.95 £1.79 £1.79
VIDEO LAMPS/BULBS VID34 LA9295 VID35 LA9210S VID36 NAT/PAN. VID37 SHARP 9300	Universal lamp without socket 2 Universal lamp with socket 310 P.C. MTG. leadless lamp Etc. lamp plus plastic shroud.			0.35 0.50 0.20 1.27	VTC 9350 VTC M10/11/20 VTC M21/30/3 VTC M50	0 VID7809 1 VID7809 VID7809	20.61 20.61 20.61	V 9600 V 5250 V 5280 V 5475	VID7810 DBK148 DBK148 DBK122 Prices subject to	£1.95 £2.66 £2.66 £1.50
	, proprietate and star				I Full list	available with	n order	1	ation without notic	* 0

REGISTERED OFFICE: THE COACH HOUSE, MUXTON LANE, TELFORO * MAIL ORDER - CALLERS STRICTLY BY APPOINTMENT

Test Report: Electronic Visuals Vectorscopes

The number of cameras and camcorders in use is steadily increasing. This has implications for the service department. Many smaller dealers have adopted the policy of returning all such units to the manufacturer when repair is necessary unless the fault is particularly straightforward. The result is complaints from manufacturers that they are getting far too much equipment back with faults that are in no way special. One complaint is that they don't like being used as dealers' service departments. A knock-on consequence is that when a dealer has a real problem and desperately needs assistance he's likely to encounter considerable delays.

The suggestion for this test gear review came from a Panasonic engineer. Panasonic has always been amongst the best when it comes to dealer support. The company has very good terms for the test gear it feels dealers should have. With the increase in camera/camcorder work, Panasonic considers that more dealers should invest in a vectorscope, particularly where an appreciable number of cameras with tube type pickup devices are handled.

That same Panasonic engineer seems to have got the wrong idea about my article on camera workshop accessories back in January 1989. My comment about the alignment charts in Panasonic service manuals was not intended to be derogatory. The purpose of that article was simply to suggest ways in which the smaller workshop could make a start with camera/camcorder servicing without having to invest large sums of money, the aim being to provide a better back-up service by carrying out the simpler repairs required. If the amount and complexity of work increases, the situation must naturally be reviewed. In this case more money should be invested so that the job can be done as well as possible. There are various things on which the money can be spent, the largest single investment being a vectorscope - hence this review. But you should certainly consider getting the manufacturers' approved alignment charts, particularly the colour chart for use in conjunction with a vectorscope.

The EV4061

The Electronic Visuals Model EV4061 reviewed here is a combined vectorscope and waveform monitor. Electronic Visuals also has available a similar unit without the waveform monitor, Model EV4021. The prices are around £1,700 and £1,000 respectively, but for overseas customers these prices are subject to alteration to take exchange rate variations into account. The EV4021 is understood to be the lowest priced vectorscope available in Europe.

The unit came well packed in a sturdy box. Also included were a detachable mains lead (of the same type as used in the old Sony SLC7 VCR), an instruction/ service manual and a plug for the remote socket. This appeared to be of the B9A valve base pattern. My first impression was of the unit's small size, measuring $132 \times 216 \times 432.5$ mm. When I put it on the bench it was dwarfed by the trusty Gould oscilloscope.

The front panel is uncluttered, with the controls bordering the 10×8 cm display. Beneath the display


there are the familiar scope controls for trace intensity, focus and backlight brightness. The latter has a fantastic range, allowing excellent viewing in any conditions. Switching between the vectorscope and waveform monitor displays is by means of a very sound switch at the bottom left-hand corner. A "six vector" presentation is given in the PAL vectorscope mode. In the waveform mode there's a choice between displays at field rate, twice field rate, line rate and twice line rate, with optional magnification in the two times ranges.

The inputs are arranged at the back of the unit, using BNC sockets. Each of the three inputs A, B and reference has a pair of sockets, allowing loopthrough. There's also a buffered monitor output socket. With the unit unpowered there's no output here – if you require an output for a monitor when the unit is switched off you use the loopthrough provided by the two sockets for each input.

Some adjustments require the vectorscope to be terminated at 75Ω , so a plug made up with suitable resistors will be useful. Input switching is carried out by means of the switch at the top left. This also has a 1V, 60kHz calibration setting.

The horizontal and vertical position potentiometers are on opposite sides of the front panel. The two remaining major controls are for vector gain and phase control. Vector gain increases the vector by up to five times. A calibrate position is included. The phase control provides a continuous 360° rotation. Finally at the bottom right corner of the control panel there are a small toggle switch and push-switches for d.c. restoration and external reference.

The instructions provided summarise these controls, the rest of the manual containing circuits and service information. This is understandable since to explain the possible uses of the unit would be a very lengthy business. The manufacturer has therefore decided to leave things to the individual. As most service manuals for video equipment explain exactly what's needed for a particular adjustment this should cause no problems.

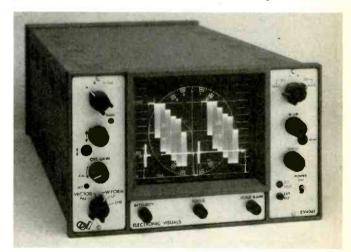

The Electronic Visuals' EV4061 combined vectorscope and waveform monitor which was received for review. The EV4021 vectorscope only is housed in the same case and is of similar appearance – it would be more suitable for the average workshop contemplating camera and camcorder servicing.

In the past the unit has been used mainly in TV studio and field applications. It's only now beginning to appear in service workshops – Panasonic's amongst them. I found the unit magnificent to use. The display is superb, easy to see and to use. To be able to flick over and see the signal at field or line rate is very helpful. The unit's compact size makes it easy to add to an already busy bench area. Camera adjustments are very much quicker and more accurate than with an oscilloscope – if indeed you can do it with just the latter.

I would not expect the average workshop to invest in the EV4061 version since the price differential is quite





Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Philbert had the usual motley selection of deliveries and service calls to make this Friday morning. The symptom in one case was given as "jumbled teletext". Mr. Hayes, the customer concerned, wanted to go on holiday. Twe w;ekz in Ten\$rife or ton deys in Maj½rwa? He had a good guess at G&tw½c\$ airport but wanted to be sure.

Philbert knew that he lived in an area that was not of the best for TV reception, and by luck he had in the van a teletext receiver for delivery after repair. Into Mr. Hayes' living room it went to provide a check. On this set the pages were displayed clearly, with virtually no incorrect symbols or misspellings. Not the aerial then, so Philbert turned his attention to the teletext decoder in the ailing TV receiver. It was a middle-aged model using the Mullard/Philips SAA series four-chip teletext decoder set of i.c.s. First he checked the 5V and 12V supplies. The voltages were correct and the ripple levels were low.

Next he carefully examined the text display on each channel in turn. Some of the four were better than the others. Channel Four was the worst, though the TV picture on this channel was acceptable. Each channel was then tuned for best results, at the front control panel, but this didn't improve the text situation at all. Indeed things were so bad with the Ch. 4 text display that even the clock and header row sometimes flickered over to nonsensical figures and symbols. Our man finally had a judicious twiddle of the clock tuning coil at pin 21 of the SAA5030 VIP chip while watching the clock display in the header row of the Ch. 4 index page. If the slug was moved far from its original setting in either direction the display went from bad to worse. He restored the setting to the original position and went off to consult the workshop worthies on the matter.

Back at the base the story was recounted in detail to a sympathetic colleague. The upshot of this was that Philbert returned to Mr. Hayes later that afternoon armed with an anti-static outfit and some electronic bits and pieces. Following his instructions, he first decoupled the decoder's supply lines with capacitors large and small. Then he checked the earthing of the teletext large and you would seldom need the waveform monitor facility. The EV4021 represents excellent value for money: at around $\pounds 1,000$ it should end further argument – the price is little more than that of a new high-specification scope.

Availability

For further details contact Electronic Visuals Ltd. at Goldsworth Road, Woking, Surrey GU21 1RU (telephone 4083 771 663). My thanks to Brian Elliott of Electronic Visuals for his help.

decoder panel. There was no change to the symptoms with the extra decoupling capacitors temporarily hooked in, and the earthing leads and joints proved to be o.k. Next then for Philbert's hour of glory, with the impressed Mr. Hayes as an onlooker. Philbert spread out his anti-static mat, earthed his wrist and his little soldering iron with a flourish, and produced a foil-wrapped SAA5030 chip fresh from the stores.

Fifteen minutes later the new chip had been fitted. The teletext panel was replaced in the set and Ch. 4 text was selected via the remote control keypad. How their faces fell! The text display was as mixed up and confused as before, with sprinklings of \pounds symbols, odd blocks of graphics and misspellings. Philbert, crestfallen, twiddled the bit-clock coil again. There was no improvement. He wished he was in Ten\$rife or Maj¹/₂rwa.

Bright and early next day Dave appeared on the scene – it was Philbert's day off – with a replacement decoder panel that had proved to be o.k. in the workshop. Into the set it went, but the symptoms remained as before with very little improvement. Dave was convinced that there was something wrong with the signal from the aerial. So he tried a complete replacement TV set. Good teletext! Where lay the problem then? See next month for the answer.

ANSWER TO TEST CASE 330 – page 617 last month –

Picture foldover, and in fact linearity problems generally, are much rarer now than they were in the old days. The Ferguson TX10 set featured in last month's puzzle had foldover at the top of the picture, indicative of a slow or constricted field flyback. The lads in the workshop were on the right trail in checking out the flyback generator circuit associated with pins 6 and 8 of the TDA3652 field output chip, and the low-amplitude pulse at pin 6 should have led to further investigation in this area.

The normal action of this circuit is that C776 (100μ F) charges to the supply line potential (26V) via D771 and R774 during the scan period. At the end of the scan the flyback generator within the chip whips pin 8 up to 26V, thus raising the positive plate of C776 to 48V and reverse biasing D771. In this way the supply to the deflection yoke is boosted, ensuring a fast reversal of the current flowing in the field scan coils. This wasn't happening, because R774 had increased in value form its normal 620 Ω to about 1.7k Ω . Maybe a little more thought about the low-amplitude pulse at pin 6 would have got our fault-finders there a bit more quickly. Maybe that was what Sage was muttering as he settled down at his own bench, while RT dismantled the Christmas tree of components under the TX10's main PCB.

VCR Clinic

Philips DMP Series Decks

When taking the top plate from the mechanism be careful as you remove the erase plug: if you don't release the clips first you can easily break off part of the erase head mounting. This happens to be where the 180° roller adjusting screw operates, the result being that the tape path goes way off adjustment. Usually the engineer glues the erase head back on but leaves the L-shaped lug off, thinking that it has no effect – it comes into use only when threaded up. . . To do the job properly a new scanner ring is required. **P.B.**

Pye DV464/Philips VR6462

"Goes beserk" said the fault note, which wasn't far wrong. At switch on the deck would initialise then the clock would go off, the deck would go into wind and wouldn't stop. All this was accompanied by clouds of smoke from the i.f. module. The smoke was coming from R3426 as C2422 was short-circuit. It's part of the tuning voltage generator... **P.B.**

Philips VR6468

On occasions the cassette would eject when play or rewind was selected. If the service mode was selected the error was -2 (capstan not rotating). This time it wasn't loss of the tacho signal: the capstan motor had a dud spot. **P.B.**

Blaupunkt RTV310

The problem was tuning drift, with a hum bar superimposed on the snow. C1103 (47μ F, 100V) on the power supply PCB was open-circuit. **P.B.**

Philips VR6362

The clock display would either go off or only one digit would appear – it was an intermittent fault. When it occurred the machine didn't answer the keyboard. Crystal 1001 on the clock module was dry-jointed. **P.B.**

JVC HRD320

The problem was very intermittent loss of the playback picture. Days would pass without the fault showing. Sometimes it would tease us for a few minutes at first switch-on from cold. We tried replacing the luminance chip IC101 but this didn't cure the problem. The symptom finally stayed for long enough to enable us to do some scope tests. These proved that low-pass filter LPF102 was the culprit. These filters have many internal joints, which probably explains why they are so often the cause of exasperating intermittent signal problems. **E.T.**

Samsung VI910

The reported fault was of cutting out intermittently on playback. No cause could at first be found: the most likely suspect, the reel drive idler, appeared to be fine. After the machine had worked correctly for several days it came to a stop - when we noticed it the tape had unlaced and the machine was in the off mode. We restarted it and it ran for only a few seconds before

Reports from Philip Blundell, AMIEIE, Eugene Trundle, Ian Bowden, Alfred Damp, Stephen Leatherbarrow and Nick Beer

stopping again. This time we noticed that the power LED went out momentarily just as the machine cut out. We restarted it again, with a meter handy. This time when the fault occurred the machine just stopped dead with the tape still fully laced. We quickly found that the 13V supply, from which all the other supplies are derived, was missing. The cause was the 3132V regulator chip IC1. It could be turned on again by applying just a few drops of freezer to its case. I.B.

Panasonic NV-G21

When we switched the machine on a squealing noise came from it. After removing the top cover we noticed that the capstan rotor was vibrating. A check at the torque control input pin of the BA6430S motor driver chip IC2001 revealed some bursts of 1.8V spikes that sat on a d.c. level of 1.5V. The timing of these bursts seemed to coincide with changes in pitch in the noise coming from the motor. After checking with another machine however we found that these bursts are quite normal. We also discovered that the noise would fade away when the machine had been on for a few moments. A quick spray of freezer on the motor driver chip brought the fault back again, proving that the i.c. itself was the cause of the problem. **I.B.**

Panasonic NV-L25

This seemed to be a very strange fault at first. The customer said that the two words "write" and "release" would intermittently appear in the display and that when this happened nothing could be done with the machine. Unusually for an intermittent fault it showed up straight away for us, and we found that by lifting the front right corner of the machine slightly it cleared. As soon as the top cover screws had been removed however the fault wouldn't occur, no matter how the machine was flexed. With the top cover removed the cause of the fault was spotted straight away. A flat 14-way connecting cable goes from P7401 on the main PCB to P7501 on the display PCB. It hadn't been bent down far enough and the insulation had been cut through at connection five (serial data line) by the front of the metal top cover. This connection was thus earthed when the cover screws were LB. fitted.

Panasonic NV-G21

This machine showed very little sign of life. There was no display and no LED indications. In fact all that worked was the r.f. amplifier. The cause was quickly traced to the power supply – there was no 6V and hence no switched 5V output from the STK5338 multi-voltage regulator chip IC1001. It was the second machine we'd had in a single week with the same fault. I.B.

Mitsubishi HS-B30

The owner complained that the counter didn't work correctly. In fact the digital readout didn't change at all. At the same time a noise bar moved through the picture, indicating absence of the CTL pulses. Replacement of the audio/control head cured both faults. This is rather intriguing: why complain about something as trivial as the counter when the playback picture quality is so poor?

As a footnote I received another VCR with the same complaint/symptoms later the same day. This one was a brand new Akai, but this time all that was necessary was to clean the control head. A.D.

Ferguson 3V57

This machine would intermittently stop due to either reduced amplitude or missing take-up reel pulses. The usual causes of this problem with these machines are dry-joints or a defective reel optocoupler. This time however I found that the switched 12V supply to the reel sensor board was low and varying. When the supply and the reel pulse waveform were monitored you could see that the latter disappeared when the supply dropped to 9.5V. The cause of the problem was on the power supply board: D3 was leaky with a reading of approximately 600Ω .

Ferguson FV13H

The job card said "dirty heads". When the machine was tested there was no picture but sound could be heard. So I switched off and set about cleaning the heads. When the test tape was tried again the symptoms were the same. I stopped the tape, ejected it and was about to attempt to clean the heads a second time when I noticed that the drum, which was slowing and about to stop, was actually running backwards! Not really believing my eyes I tried the test tape again and sure enough the drum was rotating backwards. So attention was turned to the servo board. After finding an incorrect voltage I replaced the VC2023B2 servo chip. This restored normal drum rotation. **A.D.**

Tashiko VVE922

Failure to record colour was the complaint with this particular Japanese nightmare. The more I looked for the cause of the fault the more intermittent it became. I tried creeping up on it but this didn't help. How do they know? Anyway, after a long foray into the machine with a hairdryer in one hand and freezer in the other VR303 (627kHz set potentiometer) proved to be the cause. Don't twiddle – the setting is critical. S.L.

Amstrad VCR4500/9000

On several occasions we've had no tuning or poor band coverage due to the 43V zener diode D517 on the power supply module. It's type GZA43Y but I always make do with a 33V and 9.1V zener diode together as 43V zeners don't exactly grow on spares cabinets. S.L.

Panasonic NV370/Philips VR6520

There was severe hum on both picture and sound in the E-E mode. It also showed very clearly with the test signal displayed. C1102 (2,200 μ F, 25V) on the power supply panel was bulging out its innards for all to see and was virtually open-circuit. S.L.

Amstrad VCR7000

Due to no take up, poor fast wind etc. we had to replace the reel idler in this machine. No surprise here of course,

TELEVISION JULY 1990

but we were surprised to find that the symptoms were still present after the replacement. The drive circuitry is very simple and the fault was quickly traced to Q15 (2SD1348) which was short-circuit base-to-collector. For those who may not know this, the idler is the same as the one used in the Sharp VC9300/VC381 range of VCRs. S.L.

Panasonic NV333

A case of no tuning voltage was traced to R7019 on the panel mounted vertically at the rear of the deck. Its value is 10Ω and there appeared to be no contributory cause to its failure. S.L.

B and O VHS80

Chewing tapes it said. Easy I thought – the idler is faulty for sure. More fool me! I found that the capstan motor didn't move in fast forward and rewind, nor did it move to give take-up in play or record. But it did thread. There was also a loud scratching noise during threading. A check on the circuit revealed that I'd had this problem before, but the resistor was o.k. this time. So time for some proper fault-finding.

There was no output from the capstan drive switching chip IC1151 though it was being switched correctly. This was because there was no motor supply input. There should be a regulated 4.2V input which is obtained from the 16V rail via Q1158. This transistor's collector voltage was high as it had no base bias because R1153, a tiny 1k Ω resistor, was open-circuit. Replacing this resistor restored motor drive. In the fast modes the reel drive was sluggish. A new idler upped the torque, but the deck didn't lace completely and because of this there was no take-up in the play and record modes. The cause was much simpler this time: the loading belts were very worn – as were the pinch roller and the other belts.

The mechanism is very similar to that in the Hitachi VT11. N.B.

Sony CCD-F340E

The card listed two faults, a loud screeching sound when rewinding and poor life from the battery – there was no indication as to whether it was the sole battery that had been used. I decided to deal with the noise first as I'd a fair idea of the likely cause, a faulty supply reel table. This had to be ordered and was fitted a couple of days later. I then looked into the battery problem.

The battery sent with the machine wasn't of Sony manufacture. It was a high-capacity (1,400mAh) Maxell one. As it was flat we charged it then tried it out. On continuous play it lasted for just a quarter of an hour. The camcorder was drawing the correct 6.5W in the camera record mode, and when flat the battery voltage had dropped to just over 5V.

We've found that the most common cause of loss of battery capacity is incorrect use/charging. The problem arises when people charge the battery, use it for a short time without "flattening" it, then charge it again. This is commonplace in the shop of course, where camcorders are constantly being demonstrated and the batteries left on charge. We've had some success with continually flattening and recharging batteries for a period to reactivate them. Customer education is the best cure. The fault seems to affect mainly batteries used with Sony camcorders and their clones – not just Sony batteries either. N.B.

Letters

MEDIUM-WAVE INTERFERENCE

I can sympathise with Ivor Nathan (Letters, March) over his problem with interference. Fortunately there's a well established solution, at least for medium-wave reception. The subject was very well covered in "The Loop Aerial Revived", *Wireless World* July 1979. The main point is that a long-wire aerial is unsuitable for a.m. reception in an urban environment because it's very sensitive to local electrical interference. Due to the short distance between the interference source and the aerial capacitive coupling is significant. Since most of the radiation is produced by high r.f. voltages (sparks, TV video output, TV line pulses) this capacitive coupling results in a high interference level. Electromagnetic interference radiation is relatively small.

What's required is a magnetic pickup device. One can be made for next to nothing. Make a frame about $1m \times 1m \times 50mm$. This is easy to do with two lengths of $50 \times 20mm$ timber joined in an X formation. Wind seven turns of fairly heavy wire round the frame, keeping a few mm between the turns. Connect the ends to a 500pF tuning capacitor. Place a radio with a ferrite-rod aerial inside the loop, with the coils on the rod in the same orientation as the loop. Tune the loop and the signal strength will rise dramatically. An alternative method of coupling is to wind a one-turn loop on the frame and connect it via twin cable to the receiver's external aerial socket.

Not only does this produce lots of signals with hardly any interference, it's also directional. Thus interference can often be nulled out by turning the loop. In addition, being tuned it helps to suppress image reception. Here in Nottingham I've received local stations as far away as Bradford and Southend using this loop aerial. David Robinson,

Radcliffe-on-Trent, Nottingham.

INTERLACED SCANNING

I was interested to read David T. Looser's letter in the May 1990 issue and feel prompted to make the following comments. Interlacing provides 25 complete pictures per second at an overall flicker rate of 50Hz. The technique is to transmit 50 half pictures by scanning odd lines during the first fiftieth of a second and even lines during the second fiftieth. The price paid for doing this is an adjacent line-to-line flicker at 25Hz. If interlacing is not used and the other system parameters remain substantially unchanged only half the screen area is scanned, in other words half the elements that make up the picture have gone. This of course affects the camera as well half the photosensitive area wouldn't be scanned either. So, even if David Looser prefers to watch such a picture, half the information has disappeared. I don't understand how his claim that "the vertical resolution is virtually the same" can be compatible with his later statement that "the line structure is quite noticeable". I recall the importance of interlacing with the 405-line system. Failure produced a 202-line picture which even the uninitiated thought was pretty awful! The idea for interlaced scanning came from the EMI team that developed the 405-line system fifty years ago. I think it

unlikely that any great revelation is going to contradict their theory.

The argument that since VDUs don't employ interlacing TV sets needn't either is specious since we're not comparing like with like. At normal TV viewing distances the angle subtended to the eye by the screen is typically ten degrees in the vertical plane and the 25Hz line-to-line flicker is not very obvious. VDU users sit much closer to the screen and the ten-degree angle just mentioned can be thirty degrees. As a result the line structure is far more obvious. With interlacing there's a further problem that's far more relevant to VDUs than TV sets. If you get close to an interlaced picture and run your eye up and down the screen the raster breaks into a pattern of half the number of lines, moving up or down. When you stop the eye movement the number of lines appears to double, back to normal, and the 25Hz flicker can be seen.

So there are good reasons for not using interlacing with VDU displays. First, any 25Hz flicker is more obvious, because the operator is close to the screen. Secondly when reading down the screen, or having the display scroll through, the eye's tracking movement causes the break-up effect described above. Enduring this for a day can cause headache and eye fatigue. The definition of small 312-line VDUs is quite adequate for the characters used in word processing etc.

Truly high-definition computer displays employ both sequential scanning and a large number of lines – typically 1,250 – so that even with a magnifying eyepiece it's impossible to see the line structure. All you see are the phosphor dots of the delta-gun tube which, incidentally, is perfectly converged. This level of performance is essential for the computer-aided design of modern densely-packed PCBs for example. Such definition calls for a video bandwidth in excess of 25Hz, which brings us back full-circle to the use of interlacing as a means of reducing the bandwidth requirement with a TV transmission.

Keith Cummins, Holbury, Hants.

THE FISHER FVHP615

With reference to the problems Dave Mackrill mentions at the end of his article on the fishy Fisher FVHP615, we service hundreds of these machines and can say that the final problem of tight supply and take-up reels is normally caused by the reel assemblies beginning to fall apart. All that's required is a push down on the centres of the reels and the problem is solved. Fred will most likely be calling back with tight reels!

C. Green, Budget Video Warehouses Ltd., Dartford, Kent.

PIONEER LASER UNITS

In the CD Player Casebook column for May Mike Leach quotes the price of the laser pick-up for the Pioneer PDZ-72T as £27 plus VAT. I wish we could sell them for that! As it is, our target retail price is £43.87 plus VAT, though trade customers will of course pay less. Mike's point about laser pick-up prices is well understood by ourselves and probably by most manufacturers. At our trade price Pioneer actually make a loss on each one we sell, but frankly we want to make a profit selling CD units, not laser pick-ups!

Of more concern to us is the fact that many if not most

laser pick-ups are changed "on spec". All too often it's a question of "problem with a CD player – change the laser pick-up"!

Our training officer Ken Clements has been running two-day courses on CD for a few years now, all over the country. We think, and many engineers write to tell us, that it's an excellent course, with a very high practical content. Any of your trade readers who repair Pioneer CD players are welcome to contact us to find out when they can join one of them.

Roger J. Wood, National Service Manager, Pioneer High Fidelity (GB) Ltd., Service Division, Field Way, Greenford. Middx UB6 8UZ.

QUALITY OF 625-LINE TRANSMISSIONS

I'm writing to support Ray Truner's views (Letters, May) on the present quality of 625-line transmissions. I remember being astounded at the quality provided by early colour TV programmes transmitted during the BBC's sixtieth anniversary celebrations a year or so ago. particularly the edition of "Going for a Song". By adjusting my TV set just to underscan the tube face I can see that much broadcasting equipment is out of alignment, whether on BBC where the start of the active line is delayed or Channel Four where the active line finishes too early – with ITV this varies from company to company. I can also see the lining up of shots from mixer desks. Further, why does London Weekend Television use so much clipping and correction that the pictures produce a "cardboard cutout" effect? Is there no such thing as true black level? I'm beginning to think that it's all a plot to show how good HD-TV is. Would any TV company care to comment?

S.J. Cowie, Shrewsbury, Shropshire.

SOUND QUALITY ETC

I read with interest John C. Priest's letter on cabinet design and TV sound quality in the April issue. Like John Priest I think that the sound quality of TV sets has got progressively worse over the years, due in part to the flimsy cabinets used and the tiny speakers often fitted in large-screen TV sets these days, but I feel that the type of audio amplifier also plays a large part in the sound quality obtained.

Nowadays the vast majority of sets tend to use amplifier chips, reducing labour costs. To my ears these chips often sound harsh and are fatiguing to listen to for any length of time. They tend to suffer from crossover distortion at low volume levels, and many are inherently unstable, the TBA820 for example – if you don't believe me, try disconnecting the Zobel network (usually 1 Ω plus 0.22 μ F) connected across the output and hear it scream!

Many older designs used a transformer-coupled class A audio amplifier which provided a more pleasant sound despite greater distortion (on paper anyway!). Most of the distortion produced by this type of circuit is in fact second harmonic distortion, to which the human ear is very insensitive. Transformer-coupled amplifiers do tend to sound a bit on the warm side, but I don't find this colouration unpleasant – though my Decca 30 does sound as if it has a cold at times!

Many of the discrete push-pull designs used in TV sets over the years are capable of providing good sound, notably the class A designs once used by Philips. Class B designs can also sound good, though the rather underbiased effort in the Philips TX portable chassis sounds awful, with crossover distortion clearly in evidence.

In TV Fault Finding, February, Stephen Leatherbarrow comments on the unreliability of many STK type thick-film modules. This may be because too much heatsink compound has been used during assembly. My Onkyo tuner-amplifier uses an STK463 in its output stage and gives excellent sound but the STK463 blew after the first few months. On removing it I found a thick dollop of heatsink compound on the underside. This had prevented good contact between the module and its heatsink, the result being an excessive local temperature rise and early failure. The replacement was installed with a small amount of compound carefully smeared over the whole surface. It has given trouble-free service now for seven years.

Incidentally my Sony KV2000 suffered from decoder trouble recently. The colour was weak, with considerable noise on saturated primary colours. Voltage checks in the decoder showed that Q302 was conducting excessively. This was caused by the a.c.c. preset VR303 being dirty. A squirt of switch cleaner cured the fault. Dirty potentiometers seem to mar this set's otherwise excellent reliability now that it's getting on a bit. S. Pearson,

Chipping Norton, Oxon.

CHARLES HYDE

Your TV/VCR Spares Guide 1990 failed to list the full range of spares we can provide. In addition to being the sole non-account spares distributor for Sanyo UK we are one of the three approved distributors for Ferguson and one of the five approved suppliers of spares and components for Philips Consumer Electronics in the UK. We also carry a range of spares for Decca, Fidelity, Hinari, Hitachi, ITT, Sentra, Seleco, Sharp, Sony and Toshiba.

We at CHS, as we are often called, have been operating since October 1959 and are the oldest, by at least six years, of the established national independent spares and components distributors. We have no diversification into finished goods, industrial electronics or office equipment goods and spares, concentrating our efforts on supplying the home entertainment service trade with the spares and components dealers need very quickly to get consumers' equipment back into working order as soon as possible.

We have an automatic computer ordering system called CHESS (Charles Hyde Express System for Spare parts ordering) which enables customers to gain direct access into our main frame computer and enquire about the availability and price of all products in our catalogues and place orders for immediate processing.

Freddie Whipp, Sales Manager, Charles Hyde and Son Ltd., Prospect House, Barmby Road, Pocklington, York YO4 2DP.

WELL DONE SES

There have been many letters in recent times about the poor service given to the small Independent Retailer/ Service Department by manufacturers and their agents. Occasionally however one obtains exceptional service, so I'd like to commend Sony agents SES (Staines) Ltd. (Unit 1, Causeway Industrial Estate, Lovett Road, Staines TW18 3AN). During a recent visit the reception area simply oozed efficiency and all staff were quite exceptionally polite and helpful. Despite the fact that we are not Sony dealers we obtained immediate replacement of a failed on/off switch in a couple of KV2092 receivers free of charge while we waited – and a threemonth guarantee covering the complete sets! Well done. *Barrie Hay TV*,

Lancing, Sussex.

MANOR SUPPLIES TELETEXT ADAPTOR

I wonder whether anyone can provide details of the i.c. and transistor working voltages for the Manor Supplies Mk II Mullard teletext adaptor as this information is no longer held by Manor? Any expenses would of course be reimbursed.

E.G. Kempshall, 109 Portland Road, Hove, East Sussex BN3 5DP.

HOW GREEN IS SATELLITE TV?

I wonder whether satellite technology is as green as David Tilley suggests. The satellites themselves are green so long as they don't re-enter the atmosphere. But putting a satellite into orbit requires a huge expenditure of highly volatile energy in relation to the size of the payload, and as the launch vehicle punches its way through the atmosphere, including the ozone layer, its propellant gases hurtle back into the atmosphere. Three decades of satellites and space probes have greatly increased our knowledge, but can anyone place his hand on his heart and declare that rockets are environmentally friendly?

D.F. Bishop, Ripley, Derby.

CABINET DESIGN

May I echo John C. Priest's views (Letters, April) on the awful design of CTV cabinets in particular? It's clear that manufacturers are either so arrogant about the reliability of their products that they think they'll never need to be fixed, or they just don't give a damn for the poor beleagured service engineer. Many field engineers must at some time have had no choice but to balance a large, unwieldly PCB on one knee while squatting in a corner of a dingy room and work on it while it's live. Sometimes we have to handle metalwork that we know is at half mains potential due to the use of the ubiquious bridge rectifier.

Until quite recently TV sets had a servicing position that gave access to both sides of the main PCB without having to undo numerous cable clips. The service manuals blandly instruct you to ensure that all cables are fastened back in their original positions – which is impossible unless a Polaroid camera is part of your toolkit. We are also told always to use an isolating transformer when servicing. I'd like to ask those who write this sort of thing to carry one up to a top flat after having parked a couple of streets away.

Refitting the backs of some modern receivers is more difficult than repairing them. Numerous screws, PCB support slots moulded into the back, AV/audio/scart/ aerial socket bits and pieces etc. all cause hassles. One top name Japanese set flaps alarmingly when the back is off: the paper-thin plastic can't support the weight of the c.r.t. properly.

Dave Henniker, Edinburgh.

TRANSFERRING FILM TO VIDEOTAPE

A correction is required to my article on transferring film to videotape (May 1990). The audio/video output from the JVC GRA-30E camcorder is available at an 8-pin mini DIN plug. If connection is to be made to a JVC VCR with a 10-pin camera socket the JVC VC-V810U conversion cable will be required. While writing I would like to thank Ernie Kendall (Letters, page 525) for his interesting and helpful comments on the interference problems I described in an earlier letter. *Ivor Nathan*,

Southgate, London N14.

SATELLITE RECEPTION ON OLD SETS

There has been mention in the daily press of Sky TV reception on old TV sets. I have for some time owned a Pye Model 99 (T14 chassis) monochrome portable which has a v.h.f./u.h.f. tuner of Italian manufacture. It had a small power supply fault and after putting this right I tuned through the v.h.f. band. Skysport came through with a little snow on the screen but quite a stable picture. The aerial used is outside my premises and has only five elements, of Z design, with two vertical bars as reflectors.

I'm puzzled as to how on earth microwave signals can be picked up by this 1972-vintage receiver and demodulated. Perhaps other readers would care to comment? D.H. Davies,

Ebbw Vale, Gwent.

RGB DRIVE TO THE TX10

Now that the BSB satellite with its D-MAC transmissions is in operation I'm wondering whether the analogue RGB output from a BSB receiver could be fed to the RGB data inputs in a Ferguson TX10 chassis? These inputs go to pins 13, 15 and 17 of the TDA3560 colour decoder chip. The appropriate write voltage would be required at pin 9, and sync would have to be fed to the timebases. Or can these inputs handle digital data only? *Brian Webb*,

Havant, Hants.

J. LeJeune comments: The data inputs at plug 18 on the signals processing board in the TX10 chassis can be used for analogue inputs. They should be a.c. coupled into the

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., St Ives plc. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £20, overseas (surface mail) £24 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

colour decoder chip, which has black-level restoration in it. The brightness can be controlled but not the contrast as this is carried out before demodulation of the chroma signal. Contrast control at RGB level is very difficult – one has to maintain accurate tracking in order to preserve the grey scale. The inputs can be switched by feeding 1.5V to pin 5 of plug 18, which goes to pin 9 of the TDA3560. Sync can be fed to the pin marked "video" adjacent to C748 on the main chassis or to pin 2 of plug 19 on the signals board.

The very last version of the TX10, the 22B5 professional series, was equipped with a scart socket for analogue/ TTL signals. Unfortunately parts are no longer available for this model. The contrast problem remains.

FOR DISPOSAL

I have for disposal two new 19in. twin-panel c.r.t.s of the type used in the Pye 11U and KB 801. An excellent A66-120X must also go. These are free for collection but a phone call first would be appreciated. D. Goulbourne, 130 Dunedin Road, Great Barr, Birmingham B44 9DG. Telephone 021 325 0833.

A good home is wanted for a Dynatron Model TV51 with 24in. screen, full wired remote control and multiband radio. They don't make them like this any more. It's in immaculate condition in a highly-polished cabinet with double doors. Very clean chassis. No cocktail cabinet makers please.

S.J. lemon, 34 Guildford Road, Frimley Green, Camberley, Surrey GU16 6NP. Telephone 0252 836 519.

HELP WANTED

Can anyone supply an i.f. panel for the Thorn 2000 chassis? The set has been in working order for 21 years but the panel met with an accident recently. Also does anyone know of a cure for teletext lines at the top of the screen with this chassis? All costs will be met in full. J. M. Williams, Ardro, Pendyffryn,

Valley, Anglesey, N. Wales. Telephone 0407 740 710.

80.

E

NTENSIT

VISUALS

ELECTRONIC VISUALS

Can anyone supply a seven push-button selector (assembly 959P00501) for the Mitsubishi Model CT180B, new or secondhand? All expenses paid. J. Aldrich, 38 Parsonage Lane, Burwell, Cambs CB5 0EN.

Can anyone lend or sell me a circuit diagram for the Sharp multi-standard Model CP1491SP? Leon Electronics, 11 Woodland Close, Three Bridges, Crawley, West Sussex. Telephone 0293 20 536.

I urgently require two E421 dual n-fet input amplifier transistors for my Scopex 4D-10A oscilloscope. All expenses paid. Ben Hosseinally, 3 Villa Chambly, Curepipe Road, Mauritius.

Does anyone know where we can obtain the moving-coil meter used in the Ferrograph RTS-1 test set? *R. Sherwin, Bristol Sony Centre,* 8-10 Bond Street, Bristol BS1 3LU. Telephone 0272 290 448.

68

R

Tel, 0483 771663 Tx 859139


THE FIRST – and still the lowest cost – TV SIGNAL MONITOR

: (0] N

Goldsworth Road, Woking, Surrey, England GU21 1RU

EV4061 COMBINED VECTORSCOPE & WAVEFORM MONITOR

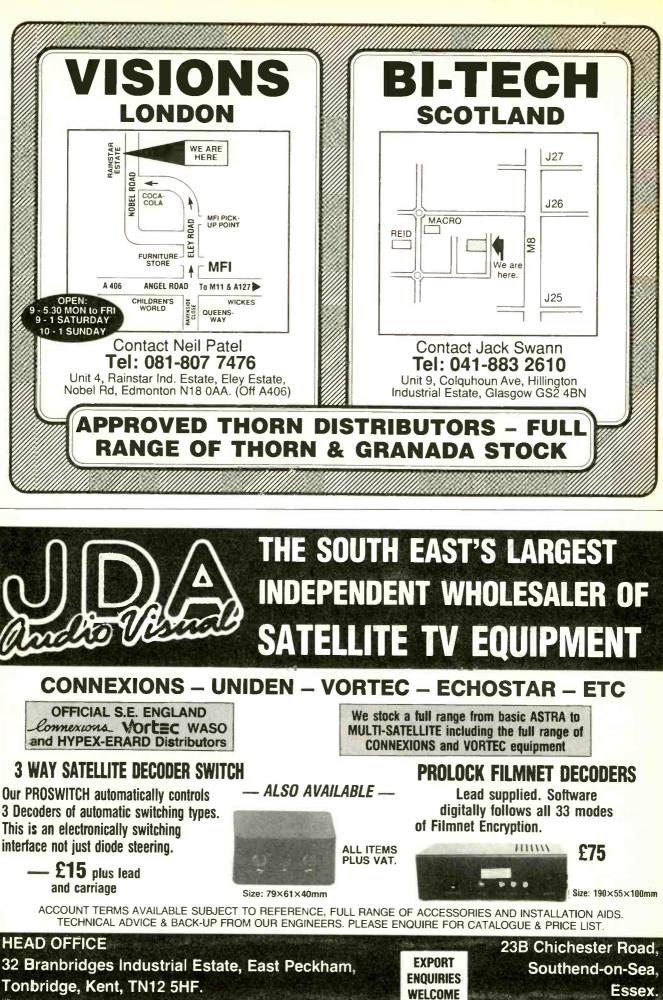- Broadcast standard measurements
- Ideal for edit suites
- □ Simple operation
- Amplitude and Phase checks at the turn of a switch



Telephone (0622) 872400 Fax (0622) 872635

Telephone 0702 468222

	RENTAL T.V.'s & CORDERS
	PRICE
FARNBOROUGH WAREHOUSECLIFF PARSONS 0252 5408147/8 KINGSGROVE INDUSTRIAL EST. INVINCIBLE ROAD 	AVONMOUTH WAREHOUSE KARLA REALE 0272 235093 5 PORTVIEW ROAD AVONMOUTH BRISTOL BS11 7LQ
SUNDERLAND WAREHOUSE BRIAN CADE 091 523 5554 94/B 94 CARRMERE ROAD LEECHMERE INDUSTRIAL EST. SUNDERLAND SR2 9TE	LINWOOD WAREHOUSE IAN DORAN 0505 29284 1a LYON ROAD LINWOOD INDUSTRIAL ESTATE LINWOOD RENFREWSHIRE PA3 3BQ
AINTREE WAREHOUSE IAN McCLELLAND 051 530 1285 UNIT 2, RACECOURSE IND. EST. ORMSKIRK ROAD AINTREE LIVERPOOL L9 5AL	NOTTINGHAM WAREHOUSE JOHN JEYS 0602 491385 REAR ENTRANCE, UNIT 7 ORCHARD BUSINESS PARK SANDIACRE NOTTINGHAM NG10 5BP

MAIDSTONE, KENT For details ring Janet Snook on 0252 540814



TELEVISION JULY 1990



ALL PRIC EXC. VAT Orders un £15 Add	CES I. nder 85p P&P 5	ጠሀ	ELEC	TRO	NICS	- 20			Access
	55 SLATEF	ORD ROAD, EL	INBURGH EH11 1P	3. Tel: 031 337	6950/031 346 7497	7. Fax: 031	337 2446.	Telex: 7216	65

THIS IS JUST A SMALL SELECTION OF THE WIDE RANGE OF PRODUCTS IN THE VIDEO AND SEMI-CONDUCTOR FIELD WHICH WE CAN NOW SUPPLY.

SMJ ELECTRONICS, inc. IBC, is the sole Scottish distributor for Ross consumer electronics and Kewmode products, and have a wide range of portable audio, televisions, headphones, leads, camcorder batteries and accessories available.

Importer and Wholesaler of Electronic Components

Distributor of Audio and Video Products

QUALITY QUALITY QUALITY	HIGHSURG	GE OF T	HE HEART HE SOUTH F OFF A24 HORSHAM
★ WORKING P.I.L. TYPE	E GOODS GUARANTEED AND ALL GOODS READY FOR S TVs FROM £15 ★ ELECTRO ★ TELETEXT TVs INC. HANDS LOW PRICES FOR MAR	SHOWROOM. DNIC TYPE VIDEO RECORDE SETS FROM £65.	RS FROM £65
BUY A KT3 AND K300 WHILE ST TOP LOADERS SHARP 8300 SHARP 9300 SHARP 9300 SHARP 8381/381H SHARP 482/581 HITACHI VT11	£75 PANAS From £90 etc	ND GET ONE FREE HS GUARANTEE ON DELAY RING TODA 3 Nat. Pan LL SONIC, HITACHI, GEC, ITT	CRT. £70 £15 From £20 £35 , PHILIPS, PYE £P.O.A.
	EN ON ALL STOCK Teleph URGE TATION ROAD INDUS NEAR HORSHAM, WE		5 WERPHONE





1//050		UNDER 1	VALUE £3.50 + VAT	BELT	KITS	
	HEADS		GENUINE	DELI		REPLACEMENTS
REPLACEMENTS	GENUINE HEADS		Panasonic		Panase	
All our replacement heads are brand new	Panasonic		NV2000, NV2010	£6.50	NV2000	NV2010
precision Japanese heads not refurbished.	NV2000, NV2010	£48.30	NV7000, NV7200			NV7200
Panasonic	NV7000, NV7200	£48.30	NV333, NV366			VV366
3HSS(N) £12.50	NV333, NV370	£48.30	NV370, NV830, NV850			NV8610
Fits model numbers:	NV366		NV688		Fergus	ion
V2000, NV2010, NV7000, NV7200,	NV688, NV777, NV788	£67.28	NV777, NV788	£4.70	3V00,3\	/16, 3V22
V333, NV8600, NV8610.	NV730		NV8600, NV8610	£6.50	3V23	
HSS-UI(N) £12.66 Fits model numbers: NV370 & Philips	All others available P.O.A.	204.50	NV730	£1.90	3V29.3	/30
VR6460.			NV230, NV430, NV870	£3.20	3135.3	/36, 3V38, 3V39
E26.25	Ferguson		NV870, NV810		Sanvo	
its model number: NV366	3V00, 3V16, 3V22		Ferauson		VTC500	0, VTC5150
3HSS(4NB) £26.25	3V29, 3V30		3V00, 3V16, 3V22	C6 50	VTC530	0. VTC5400
Fits model number: NV730	3V32	£66.95	3V23		VTC030	0
Ferguson	3V35, 3V36, 3V38, 3V39	£31.95	3V29, 3V30		Sonv	0
EIQUSUII EIQUSUII	Sharp		3729, 3730	24.90		LC7
HS5(V)	VC7300 (equiv only)	C45 24	3V35, 3V36, 3V38, 3V39	£3.90		
3/29 3/30 3/31 3/35 3/36 3/38 3/39	VC8300	C70.25	Sanyo			01.0000
HR2200 HR3300, HR3330, HR3360, HR7200, HR7300, HRD120, HRD130.	VC9300, VC9500, VC9700	270.23	VTC5000, VTC5150			SL8080
R7200, HR7300, HRD120, HRD130.			VTC5300, VTC5400		Sharp	
E29.75	VC381, VC383, VC386		VTC9300	£6.50		VC7700, VC7780
Fits model numbers: 3V32.	VC482	£65.50	Sony			
Sharp	All others available P.O.A.		SLC5, SLC7	£6.50	VC9100	VC9300, VC9500
3HSS(SP)	Sanyo		SLC6	£7.50	VC381.1	VC383, VC386
Fits model numbers: VC9100 VC9300	VTC5000, VTC5150 (equiv only)	£26.46	SL8000, SL8080	£6.50	Hitach	
/C9500, VC9700, VC381, VC8381, VC383,	VTC5300, VTC5400 (equiv only)	\$26.46	Sharp	20.00		VT5500
/C388, VC482.	VTC9300 (equiv only)	625.02	VC7300, VC7700, VC7750	C6 50		VT8300, VT8500
Toshiba		200.02	VC8300.		VT0200	VT9500, VT9700
Toshiba PS3B(T)	Sony		VC9100, VC9300, VC9500		VT11E	VT14E, VT17E, VT19
its model numbers: V9600, V31B, V33B.	SLC5, SLC6, SLC7	£49.50				VI14E, VI17E, VI13
	SL8000, SL8080	£49.50	VC381, VC383, VC386	£6.50		
Hitachi	SLC20, SLC30	£54.50	Hitachi		Akai	
E24.92 Fits model numbers: VT8000, VT9300 etc.	SLC9	£54.50	VT5000, VT5500	£6.50	VS9700	
	Toshiba		VT8000, VT8300, VT8500		VS2, VS	3, VS4, VS5
Sony	V9600	00 000	VT9300, VT9500, VT9700	£3.30		VS9500, VS9800
S3B(S) £17.82 its model numbers: SLC5, SLC6, SLC7,			VT11E, VT14E, VT17E, VT19	£6.50	Many of	hers available
its model numbers: SLC5, SLC6, SLC7,	V8600 (While Stocks Last)		VT33E	£6.50		SENSOR LAMPS
L3000 also various NEC models.	V31, V33	159.90	Akai			sonic
284B(2S) £18.33 its model numbers: SLC20, SLC30, SLC40,	V55, V56	231.95	VS9700	\$6.50	AllPana	son/JVC
SEF1.	Hitachi		VS2, VS3, VS4, VS5	64 90		
\$55B(3S) £44.25	VT5000, VT5500	£49.50	VS9300, VS9500, VS9700	56 50	Sharp V	C9300 etc
its model numbers: SLC9, SLT50, SLC8,	VT6500, VT8000, VT8300	£49.50	AMSTRAD		Sharp V	C7300 etc
SLF60.	VT8500, VT8700		VCR4500, 4600 mod kit	C4 05		7000
Amstrad/Saisho	VT9300, VT9500, VT9700			14.93	All Hitacl	ni
BHSS(R)	VT11E, VT14E		Many others available			SENSOR L.E.D.'s
Fits model numbers: VCR7000 and all mod-	VT17E, VT19E		CREDIT CARD		All Pana	sonic
als using Orion chassis.	VT33E		ORDERS BY	Access	All Ferau	Ison/JVC
3HSS(FI)		1,49.30	TELEPHONE		All Hitacl	ni
Fits model numbers: VCR4500, VCR5200,	Philips					
/CR9000 etc.	VR6460		RECEIVED BY			END SENSORS
Fisher/Fidelity	VR6462		4 PM. ARE	RELAVEARD		
Fisher/Fidelity BHSS(SF) £18.75 Fits model numbers: FVHP615, FVHP710,	VR6467	£37.47	DESPATCHED	VISA	Amstrad	
its model numbers: EVHP615, EVHP710	Please call if your model is not liste		SAME DAY			REEL MOTORS
/1000.					Chorn)//	C9300, VC381 etc.
LARGE RANGE OF REMO	TE CONTROL'S					
					Amstrad	/Saisho etc.
FOR TV AND V	IDEO r-				Panasor	nic NV333, NV366
				1	SanvoV	TC5000 5300 5400



WE CARKY HUNDREDS OF VIDEO SPARES
INC. PLAY IDLERS, CLUTCHES, MOTORS,
SERVICE MANUALS, TENSION BANDS,
BELTS AUDIO/CONTROL HEADS,
ALIGNMENT TOOLS AND TAPES ETC.
SPECIAL ORDER FACILITIES
EOR NON-STOCK ITEMS

PINCH I

Panasonic	
NV2000, NV2010, NV7000, NV7200	£4.95
NV333, NV366, NV370, NV430	£4.95
NV730	£7.95
Ferguson/JVC	
3V00, 3V16, 3V22, 3V23 3V24	£4.95
HR3300, HR3360, HR3660, HR2200	£4.95
3V29, 3V30, HR7200, HR7300	£4.95
3V35, 3V36, 3V38, 3V39 HRD120	£4.95
Sanyo	
VTC9100, VTC9300	£4.95
VTC5000, VTC5150, VTC5300,	
VTC5400	£4.95
Sony	
SLC5, SLC7	£5.95
SLC6	£5.95
SL8000, SL8080	£5.95
Sharp	
VC7300, VC7700, VC7750	£4.95
VC8300	£4.95 £4.95
VC381, VC383, VC386	£4.95 £4.95
VC651 etc.	£4.95
Hitachi	14.33
VT5000, VT5500	£5.95
VT8000, VT8300, VT8500	£4.95
VT9300, VT9500, VT9700	£4.95
VT11E, VT14E, VT17E, VT19	£4.95
VT33E	£5.95
Akai	
VS9700	£6.95
VS2 VS3 VS4 VS5	£6.95
V\$9300, V\$9500, V\$9700	£4.95
Amstrad	
VCR4500, 4600 MOD KIT	£4.95

CREDIT CAR ORDERS BY TELEPHONE RECEIVED B' 4 PM. ARE DESPATCHE SAME DAY	Y	ACCESS MARCEAVEARD VISA	All Fergu All Hitach Hitachi V Amstrad
INDREDS OF VI			Sharp VC Amstrad/ Panason Sanyo V Panason
NUALS, TENSIO JDIO/CONTROL TOOLS AND TA	DN BANI Heads, Apes et	DS,	Fergusor Sharp VC Sharp VC Hitachi V
L ORDER FACIL Non-stock ite			Sharp VC Sharp VC
ROLLERS		LARGE RANGE	Fergusor Fergusor Fergusor
700 0 , NV7200 0, NV430		OF IC's & SEMI- CONDUCTORS AVAILABLE	Hitachi V Hitachi V Hitachi V Hitachi V
23 3V24 3660, HR2200 HR7300 39 HRD120	£4.95 £4.95	FOR TV, AUDIO & VIDEO	Sony C5, Akai VS1 Many, m IDL
VTC5300,	£4.95	Panasonic NV2000, NV2 NV7000, NV7	

	£6.50	Many others available	
		SENSOR LAMPS	
		All Panasonic	£1.80
	£6.50	All Panasonic. All Ferguson/JVC	£0.65
		Sharp VC9300 etc	£2.90
	10.50	Sharp VC9300 etc. Sharp VC7300 etc. Amstrad 7000	£1.80
	£4.95	Amstrad 7000	£2.30 £1.80
		All Hitachi SENSOR L.E.D.'s	\$1.80
		All Panasonic	£2.90
Acc	#55	All Ferguson/JVC	£2.90
		All Hitachi	£5.75
		END SENSORS	
TARG	WCARD	Hitachi VT64E £1.2	0 each
	SA	Amstrad	£5.96
-		REEL MOTORS	
		Sharp VC9300, VC381 etc Amstrad/Saisho etc	£18.20
		Amstrad/Saisho etc.	18.20
		Panasonic NV333, NV366	C0 00
ES		Sanyo VTC5000, 5300, 5400 Panasonic NV7000, 7200	£19.80
S.		DRUM MOTORS	
o ,		Ferguson/JVC 3V00, 3V22, etc.	\$24 75
		Sharp VC7300, VC7700	£26.40
- 1		Sharp VC7300, VC7700 Sharp VC8300	£26.40
		Hitachi VT5000	£25.80
- 1		CAPSTAN MOTORS	
			£39.90
		Sharp VC8300. Sharp VC7300, VC7700 Ferguson/JVC 3V00, 3V16, 3V22 Ferguson/JVC 3V29, 3V30 Ferguson/JVC 3V35, 3V36, etc. Hitachi VT5000	£29.30
-		Ferguson/JVC 3V00, 3V16, 3V22	£24.75
LADCE	DANCE	Ferguson/JVC 3V29, 3V30	234.00
DANGE	IC's	Hitachi VT5000	C25 80
& S	RANGE IC's Emi	Hitachi VT8000, 8500, etc.	£34.50
CONDU	ICTORS	Hitachi VT9300, 9500, etc.	£34.50
	ABLE	Hitachi VT8000, 8500, etc. Hitachi VT9300, 9500, etc. Hitachi VT11, VT14, VT17	£28.80
FOR		SORV C5 C/	£42.90 £29.90
	DEO	Many, many more!	129.90
		IDLER WHEELS	
Pana	sonic	IDEEN WILLES	
Pana NV20			£2.90
Pana NV20 NV70	a sonic 00, NV20 00, NV72		£2.90 £2.90
Pana NV20 NV70 NV33	asonic 00, NV20 00, NV72 3, NV366		£2.90 £2.90 £2.90
NV20 NV70 NV33 NV37	00, NV20 00, NV72 3, NV366 0, NV230	10	£2.90 £2.90 £2.90 £4.50
NV20 NV70 NV33 NV37 NV77	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788	10	24.00
NV20 NV70 NV33 NV37 NV77 NV73	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0	10	£4.50
NV20 NV70 NV33 NV37 NV77 NV73	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0	10	£4.50
NV20 NV70 NV33 NV37 NV77 NV73	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0	10	£4.50
NV20 NV70 NV33 NV37 NV77 NV73	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0	10	£4.50
NV20 NV70 NV33 NV37 NV73 Ferg 3V00 3V00 3V29 3V35	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0 	10(Genuine)	£4.50 £4.50 £5.95 £6.95 £3.90 £3.90
NV20 NV70 NV33 NV37 NV73 Ferg 3V00 3V00 3V29 3V35	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0 	10(Genuine)	£4.50 £4.50 £5.95 £6.95 £3.90 £3.90
NV20 NV70 NV33 NV37 NV77 NV73 Ferg 3V00 3V00 3V29 3V35 Sanj VTC9	00, NV20 00, NV72: 3, NV360 0, NV230 7, NV788 0 	10(Genuine)	£4.50 £4.50 £5.95 £6.95 £3.90 £3.90 £1.90
NV20 NV70 NV33 NV37 NV77 NV73 Ferg 3V00 3V00 3V29 3V35 Sanj VTC9 VTC5 VTCN	00, NV20 00, NV72: 3, NV366 0, NV230 7, NV788 0 , 3V16, 3V , 3V16, 3V , 3V30, HF , 3V30, HF , 3V30, SV , 000, VTC3 0000 Reel 0 410 Reel 0	10(Genuine)	£4.50 £4.50 £5.95 £6.95 £3.90 £3.90 £1.90
NV20 NV70 NV33 NV77 NV77 NV77 SV00 3V00 3V29 3V35 Sanj VTC9 VTC9 VTC5 Sonj	00, NV20 00, NV72; 3, NV366 0, NV230 7, NV788 0. JUSON/JU , 3V16, 3V , 3V16, 3V , 3V36, 3V JO 100, VTC 000 Reel 0 410 Reel d	10	£4.50 £4.50 £5.95 £6.95 £3.90 £3.90 £1.90 £6.50 £9.90
NV20 NV70 NV33 NV77 NV77 NV77 SV00 3V00 3V29 3V35 Sanj VTC9 VTC9 VTC5 Sonj	00, NV20 00, NV72; 3, NV366 0, NV230 7, NV788 0. JUSON/JU , 3V16, 3V , 3V16, 3V , 3V36, 3V JO 100, VTC 000 Reel 0 410 Reel d	10	£4.50 £4.50 £5.95 £6.95 £3.90 £3.90 £1.90 £6.50 £9.90
NV20 NV70 NV33 NV37 NV77 NV73 Ferg 3V00 3V00 3V29 3V35 Sanj VTC9 VTC5 VTCN Sonj SLC5 SLC6	00, NV20 00, NV72: 3, NV366 0, NV230 7, NV788 0 3, NV768 0 3, NV788 0 3, NV768 0, NV788 0, NV729 0, NV788 0, NV768 0, NV	10(Genuine)	£4.50 £4.50 £5.95 £6.95 £3.90 £3.90 £1.90 £6.50 £9.90
NV20 NV70 NV33 NV37 NV77 NV73 Ferg 3V00 3V29 3V35 Sanj VTC9 VTC5 VTCN SLC5 SLC6 Shat	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0 300, NV788 0 300, HF 3, 300, H	10	£4.50 £4.50 £5.95 £3.90 £3.90 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95
NV20 NV70 NV33 NV37 NV77 NV73 Ferg 3V00 3V29 3V35 Sanj VTC9 VTC5 VTCN SLC5 SLC6 Shat	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0 300, NV788 0 300, HF 3, 300, H	10	£4.50 £4.50 £5.95 £3.90 £3.90 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95
NV20 NV70 NV73 NV77 NV73 Ferg 3V00 3V00 3V29 3V35 Sany VTC9 VTC5 VTCN SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0 USON/JU 3V16, 3V 3V16, 3V 3V30, HF 3V30, HF 3V30, HF 3V30, HF 3V30, HF 3V36, 3V 000 Red I 410 Red d 9 00, VC930 1, VC930, 1, VC930 2, VC483 2, VC483 2, VC483 2, VC483 1, VC930, 1, VC930 1, VC930	10	14.50 £4.50 £5.95 £6.95 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95 £3.90 £3.90 £3.90
NV20 NV70 NV73 NV77 NV73 Ferg 3V00 3V00 3V29 3V35 Sany VTC9 VTC5 VTCN SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5	00, NV20 00, NV72 3, NV366 0, NV230 7, NV788 0 USON/JU 3V16, 3V 3V16, 3V 3V30, HF 3V30, HF 3V30, HF 3V30, HF 3V30, HF 3V36, 3V 000 Red I 410 Red d 9 00, VC930 1, VC930, 1, VC930 2, VC483 2, VC483 2, VC483 2, VC483 1, VC930, 1, VC930 1, VC930	10	14.50 £4.50 £5.95 £6.95 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95 £3.90 £3.90 £3.90
NV20 NV70 NV37 NV77 NV77 SV00 3V00 3V00 3V29 3V35 Sanj VTC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SL	00, NV20 00, NV72 3, NV360 0, NV230 7, NV788 0 <i>uson/JV</i> <i>uson/JV</i> <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 4V <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 3V <i>avt6</i> , 3V <i>av</i>	10	14.50 £4.50 £5.95 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95 £3.90 £2.98 £3.90 £3.90 £3.90 £3.90 £3.90 £3.90 £4.95 £5.96 £5
NV20 NV70 NV37 NV77 NV77 SV00 3V00 3V00 3V29 3V35 Sanj VTC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SL	00, NV20 00, NV72 3, NV360 0, NV230 7, NV788 0 <i>uson/JV</i> <i>uson/JV</i> <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 4V <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 3V <i>avt6</i> , 3V <i>av</i>	10	14.50 £4.50 £5.95 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95 £3.90 £2.98 £3.90 £3.90 £3.90 £3.90 £3.90 £3.90 £4.95 £5.96 £5
NV20 NV70 NV37 NV77 NV77 SV00 3V00 3V00 3V29 3V35 Sanj VTC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SL	00, NV20 00, NV72 3, NV360 0, NV230 7, NV788 0 <i>uson/JV</i> <i>uson/JV</i> <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 4V <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 3V <i>avt6</i> , 3V <i>av</i>	10	14.50 £4.50 £5.95 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95 £3.90 £2.98 £3.90 £3.90 £3.90 £3.90 £3.90 £3.90 £4.95 £5.96 £5
NV20 NV70 NV37 NV77 NV77 SV00 3V00 3V00 3V29 3V35 Sanj VTC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SL	00, NV20 00, NV72 3, NV360 0, NV230 7, NV788 0 <i>uson/JV</i> <i>uson/JV</i> <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 4V <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 3V <i>avt6</i> , 3V <i>av</i>	10	14.50 £4.50 £5.95 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95 £3.90 £2.98 £3.90 £3.90 £3.90 £3.90 £3.90 £3.90 £4.95 £5.96 £5
NV200 NV700 NV333 NV37 Ferg 3V000 3V29 3V35 Sany VTCS SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SLC5 SL	00, NV20 00, NV72 3, NV360 0, NV230 7, NV788 0 <i>uson/JV</i> <i>uson/JV</i> <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 4V <i>avt6</i> , 3V <i>avt6</i> , 3V <i>avt7</i> , 3V <i>avt6</i> , 3V <i>av</i>	10	14.50 £4.50 £5.95 £3.90 £1.90 £6.50 £9.90 £4.95 £4.95 £4.95 £3.90 £2.98 £3.90 £3.90 £3.90 £3.90 £3.90 £3.90 £4.95 £5.96 £5
NV200 NV700 NV333 NV377 NV777 NV773 Ferg 3V000 3V295 Sany VTCc5 Song VTCS5 VTCS5 SLC55 SLC	00, NV20 00, NV723 0, NV736 0, NV730 7, NV788 0 3V16, 3V 3V16, 3V 3V16, 3V 3V16, 3V 3V16, 3V 3V16, 3V 3V16, 3V 3V16, 3V 3V16, 3V 3V16, 3V 00, VC53 00, VC530 1, VC383, 2 etc. (Eq. 2, VC483, 2 etc. (Eq. 2, VC483, VC483, 2 etc. (Eq. 2, VC483, V	10	14.50 5.95 5.95 5.95 5.99
NV200 NV700 NV33 NV377 NV777 NV773 SV000 3V200 3V205 Sany VTCS Sony VTCS SUC5 SLC55	00, NV20 00, NV723 0, NV366 0, NV230 7, NV788 0 0 0 0, NV230 7, NV788 0 0, NV230 7, NV783 0 100, VTC 0 0, VTC3 0 0, VTC30 0 0, VTC30 0 1, VC33 0 1, VC33 0 1, VC33 0 0, NV230 0 0, VTC30 0 0, VTC30 0, VTC30 0 0, VTC300 0 0, VTC300 0, VTC300 0, VTC300 0, VTC300 0, VTC3000 0, VTC3000 0, VTC3000 0, VTC30000 0, VTC3000000000000000000000000000000000000	10	14.50 25.95 25.95 23.90 21.90 26.50 29.90 24.95 24.95 23.90 23
NV200 NV700 NV33 NV377 NV777 NV773 SV000 3V200 3V205 Sany VTCS Sony VTCS SUC5 SLC55	00, NV20 00, NV723 0, NV366 0, NV230 7, NV788 0 0 0 0, NV230 7, NV788 0 0, NV230 7, NV783 0 100, VTC 0 0, VTC3 0 0, VTC30 0 0, VTC30 0 1, VC33 0 1, VC33 0 1, VC33 0 0, NV230 0 0, VTC30 0 0, VTC30 0, VTC30 0 0, VTC300 0 0, VTC300 0, VTC300 0, VTC300 0, VTC300 0, VTC3000 0, VTC3000 0, VTC3000 0, VTC30000 0, VTC3000000000000000000000000000000000000	10	14.50 25.95 25.95 23.90 21.90 26.50 29.90 24.95 24.95 23.90 23
NV200 NV700 NV33 NV377 NV777 NV773 SV000 3V200 3V205 Sany VTCS Sony VTCS SUC5 SLC55	00, NV20 00, NV723 0, NV366 0, NV230 7, NV788 0 0 0 0, NV230 7, NV788 0 0, NV230 7, NV783 0 100, VTC 0 0, VTC30 0 1000 Reel 0 7 9 00, VC30 1, VC30 1, VC30 1, VC33 1,	10	14.50 25.95 25.95 23.90 21.90 26.50 29.90 24.95 24.95 23.90 23
NV200 NV700 NV33 NV377 NV777 NV773 SV000 3V200 3V205 Sany VTCS Sony VTCS SUC5 SLC55	00, NV20 00, NV723 0, NV366 0, NV230 7, NV788 0 0 0 0, NV230 7, NV788 0 0, NV230 7, NV783 0 100, VTC 0 0, VTC30 0 1000 Reel 0 7 9 00, VC30 1, VC30 1, VC30 1, VC33 1,	10	14.50 25.95 25.95 23.90 21.90 26.50 29.90 24.95 24.95 23.90 23
NV200 NV700 NV33 NV377 NV777 NV773 <i>Ferg</i> 3V000 3V295 <i>San</i> VTCS <i>Son</i> VTCS <i>Son</i> VTCS <i>Sufo</i> <i>Slc55</i> <i>Slc65</i> <i>Sha</i> VC38 VC48 VC48 VC48 VC48 VC48 VC48 VC48 VC4	00, NV20 00, NV723 0, NV366 0, NV230 7, NV788 0 0 0 0, NV230 7, NV788 0 0, NV230 7, NV783 0 100, VTC 0 0, VTC30 0 1000 Reel 0 7 9 00, VC30 1, VC30 1, VC30 1, VC33 1,	10	14.50 25.95 25.95 23.90 21.90 26.50 29.90 24.95 24.95 23.90 23

£3.50 £3.00 £3.00 £3.95

£3.50 £2.90 £3.50 £2.90

£1.00 £2.50 £4.25

23.60 24.95 24.25 £3.50

£3.90 £3.90 £3.90 £3.90

£4.50 £1.50 £1.50 £3.90 £3.90

£3.90 £3.95 £3.50



UNIT 21,

Ferguson 3V23

Ferguson 3V31

Sharp 9500H

Sanyo VHR330

Samsung VT5107

Sanyo VHR2300

Tashico 140 971

Front Panels Ferg. 3V22

Front Panels Pan 2000/2010

C12 DATA TAPES

0.90

1.00 2.00

1 00

0.55

0.90

0.90

1.80

0.50

0.90

Philips CTX-5.

Sony C5/C6/

AN 3313

AN 3320K AN 6884

AN 6884 AN 7112E HA 1124 HA 1319 HA 1397 HA 12017 KM 4164B

LA 7016 LA 7530N

I M 324

LM 380N

Hitachi 8300

Sanyo Fisher VTE5000 VHSAS1

DISCOUNT TRADE WAREHOUSE

Ex-rental Thorn and Granada T.V.'s. Sold as it arrives — untouched — direct from the depots.

 $\star \star \star \star \star \star$ LARGE SELECTION OF VIDEOS Buy them as you please!! — No order too Working — Untested — or Non-working Large or Small $\star \star \star \star \star \star$ **Ring Bill Parry Now** on:- 0733 320193 B'Grade F.S.T.'s and other modern T.V.'s or call in at working — at Discount Prices $\star \star \star \star \star \star$ **BENEDICT SO...** Non-working TX9/10 Text and K30 Basics – WERRINGTON, Limited Supply Available at LOW LOW Prices! PETERBOROUGH. WE HAVE THE WIDEST CHOICE Of Used Oscilloscopes In the Country **"SUMMER SALE** VIDEO SERVICE MANUALS SELECTED SPARES Nat. Pan. Compendum 2000/2010/333/370 Sony Compendum C5/C6/C7/C9 NIX 475 Duai Trace 200MHZ Delay Sweep NIX 465 Duai Trace 100MHZ Delay Sweep OS1100 Oual Trace 30MHZ TV Trig R COU150 Dual Trace 35MHZ Oelay Sweep 19.00 Hitachi 5000 Series Video Heads 8.00 19.00 Ace Assemblies Sony C9, C5 10.00 Ferguson Compendum 3V00/3V22/3V23. Nat. Pan. 2000 .19.00 EISO TELEQUIPMENT CT71 Curve Tracer MARCONI TF2503 RF Millivoltmeter 50KHZ-1.5GHZ Ace Assemblies Sony C9, C7 15.00 Delay 2650 Delay 2425 250 2750 2400 2300 2275 2275 2130 2160 2150 2160 Electronic Construction
 10.00 Sweep PHILIPS OSCILLOSCOPE PM3217 Oual Trace SOMHz Modulator/Splitter Sony C6 10.00 10.00 HILTRS USCILLUSCUPE HMX217 Juai Trace SMM12 SMM12 SSG DOSIGNEGROE DUI Trace 20MH2 GOULD 1471 Digital Storage Dual Trace 20MH2 HP 17440 Dugital Storage Dual Trace 20MH2 Delay Sweep GOULD 05 SSG04 Dual Trace 30MH2 Delay Sweep GOULD 05 SSG04 Dual Trace 30MH2 Delay Sweep GOULD 05 SG04 Dual Trace 30MH2 TV Trag PHILTPS PM3733 Dual Beam 10MH2 TV Trag COULD 05 SG04 Dual Trace 15MH2 TV Trag THIS IS JUST A SAMPLE – MAAY OTHERS AVAILABLE FHT Probes for use with Ave 8 etc 5.00 5.00 MARCUNI AF FOWER Meter TF1152/1 OC-500MHZ 0.5-25W 50 MARCONI RF Power Meter TF1152/1 OC-500MHZ 0.5-25W 50 C25 Sanyo 5000 Channel Select PCB 10.00 10.00 Sanyo VTC9300 Modulators 6.00 10.00 ohm FARNELL Pulse Generator System 1HZ-10MHZ Si ngle/ Hitachi VT63 Servo PCB. 10.00 Die JSUI AVW23 AC Voltmeter Dual Chan 10HZ-500KHZ, 300uV 275 10.00 10.00 Hitachi VT63 Loading Gear 6.00 100V SOLARTRON 7045 Multimeter 4.5 digit LEO 30 ranges. A Manual (P&P 27) AV0 8 Multimeters with Batteries & Leads AV0 C1446 Transistor Analyser Mk2 Batteries & oceration instructions. 10.00 Hitachi 5500 Loading Motor Hitachi 5500 Reel Motor 3 50 al (P&P £7) Multimeters with Batteries & Leads Lif46 Transistor Analyser Mk2. Suitcase style. With tes & operation instructions 10.00 4.00 TEKTRONIX 2215. Dual Trace 60MHz Sweep Delay. With manual, Probes, Front Cover, Pouch only 0500 Hitachi 5500 Capstan Motor 10.00 **TELEVISION MANUALS** MARCONI TF2015 AM/FM 10.520MHz. Sig Gen TF2171 MARCONI TF2015 Hitachi VTH-VT14 Loading Motor Nat Pan NV333 Guide Roller 4.00 **COLOUR BAR GENERATION-KG1** 2.50 with £450 £250 2.00 8 PATTERNS (RP £4) Only £25 3.00 71. CONI TF2015 without Synchroniser TF2171. CONI TF2016 AMIFM 10KHz-120MHz Sig Gen Nat Pan NV333 Loading Gear 3.00 £400 £175 QUALITY POWER SUPPLY UNITS TF2173 540 MARCONI IF2016 without Synchroniser TF2173 5175 MARCONI MOD Meters TF2300, TF2300B, TF2303 from 5100 FFROGRAPH RTS2 Recorder Fest Set 500 from 5200 LEADER LINV186A Two Channel Milliwottmeter SH2-S00KH Nat Pan NV333 Supply Roller 1.50 120 2am + 9v 1 amp ideal for bench servicing. . 6.00 2 50 Nat Pan NV333 Take-up Boller Nat Pan 2000 Inerta Roller 2.50 LEADER LMV186A Two Channel Millwottmeter 5Hz-500KHz 1mV-300V E100 MARCONI TF2337A Automatic Ojstortion Meter 400Hz VIDEO PLASTIC PANELS Nat Pan 2000 Supply Reel Table 2 50 5.00 £100 trom £125 EEVEL Decade Use 1906A 0.7471227072. Low Usual Com 23 FRANELL RMG RF Millivoltmeter S0KHZ-1.5GHZ; ImV-300V E6D LOGIC PROBE type 33000A TTLCmos (PAP E3) MANY MORE ITEMS AT RIDULOUS PRICES — List available. 1KHz MARCONI TF2700 Universal LCR Bridge Battery Sonv C7 Capstan Motor . 10.00 5.00 R 1.5-E1,600 E1,250 E500 E500 Loudspeakers 50 × 90mm 8Ω 2 Watt 2.00 TEKTRONIX 491 SPECTRUM ANALYSER 5.00
 EAGUE TA
 ST CLIDING
 Ankl Stc T
 Figure T

 SYSTRID ODANER 1702 So Genome
 TODAL 504 C
 TS 200


 POLARAD Sig Gen type 11078 0.8 4 65Hz
 S00
 TS 200

 POLARAD Sig Gen type 11078 0.8 4 65Hz
 S00
 TS 200

 POLARAD Sig Gen 12084 8.95-116H with Freq Doubler 15015-216H
 TS 200
 TS 200

 POLARAD Sig Gen 12084 8.95-116H with Freq Doubler 15015-216H
 TS 200
 TS 200

 FOLARAD 1207A Sig Gen 3 7-8.46HZ with Freq Doubler 2750
 TS 200
 TS 200
 SHOP NOW OPEN AT 6 OAKLAND AVENUE, **NEW EQUIPMENT** MEG OSCILLOSCOPE HM1005 Triple Trace 100N HASLINGTON, Near CREWE. HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz, Uelay Timebase HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Savaan Sweep HAMEG OSCILLOSCOPE HM203 6 Oual Trace 20MHz C SINCLAIR ZX PRINTER ROLLS Box 5 £5.00 E375 Digital E200 -1MHz HAMEG OSCILLOSCOPE HM203 6 Dual Trace 20MHz Compo-nent Tester HAMEG OSCILLOSCOPE HM205 3 Dual Trace 20MHz. 0114 Stotate THANDAR TA2080 Logic Analyser 20MHz. 8 CHANNEL THURLBY PL3200MD 0.30V 2A Twice Quad Mode .each £0.25 Injunctor Fr.3200MD 0.307 ZA twice Utad Mode Order Meters FEDDRACK FSG806 Sweep Function Generator 0.01Hz MHD FEDDRACK FSG806 Sweep Function Generator 0.01Hz MHD RACAL 9905 Seres Universal Country FSG80Hz (Crystal Oven) ______ MARCOM ATTENUATORS TF2162 DC 1MHz 600 ohm 0.11LB (F&PET) _______ ISB All other models available. All oscilloscopes supplied with 2 probes SEMICONDUCTORS SEMICC LM 383T. LM 8363. M54648L M54898AP M58657P MC 1309 MC 1458CP MM 4864V MM 1204P 0.90 0.90 2.00 SN 2973AN APOLLO 10-100MHz Counter Timer Ratio/Period/Time 0.40 SN 2973AN. SN 29771AN SN 29861N. SN 74L5741. STK 461. TA 7122P. TA 7193P. TA 7203. TA 7203. 3.00 etc. APOLLO 100-100MHz (As above with more functions) METEOR 100 FRE QUENCY COUNTER 100MHz METEOR 1000 FREQUENCY COUNTER 104 METEOR 1000 FREQUENCY COUNTER 104 JUPITOR 500 FUNCTION GENERATOR 0.1Hz 500KHz Sin 2000 FUNCTION FUNCTION GENERATOR 0.1Hz 500KHz Sin 2000 FUNCTION F 0.30 0.20 6.00 0.90 3.00 1.40 2.00 8 00 4.00 3.00 1.50 £110 £709 Tri ORION COLOUR BAR GENERATOR Pal/TV/Video All other Black Star Equipment available from £30 (P&P£7) \$ BENCH PSUs — Please Enqui 1.40 0.90 0.90 10.00 TELEPHONES YESI REAL DIAL TYPE IFLEFHORES table don't slide around the desk. Type no 746 supplied with standard B T plug (used) (usarity Discussion) Dirty Steach (P&PE) TA 7288P HUNG CHANG DMM 7030 3-digit, Hand held 28 ranges 10Amp AC/DC 0.1% Acc (p&p C4) As above DMM 6010 0 25% Acc E39.50 MN 1204P S-40W TA 7302P TBA 4800 1.95 Carrying Cases for above OSCILLOSCOPE PROBES Switchable × 1: × 10 (P&P £3). SAA 1124 SAA 1276 2.00 TBA 510 1 20 2.00 TBA 673 0.90 Used Equipment – With 30 days guarantee. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage. GOOD NEWS. ALL PRICES NOW INCLUDE VAT AND CARRIAGE. POSTAGE U.K. ONLY STEWART of READING 110 WYKEHAM ROAD, READING, BERKS R66 1PL Telephone: (0734) 68041 Fax: (0734) 351696 Callers Welcome 9am-5.30pm Mon-Fri (until 8pm Thurs) BELL RADIO SYSTEMS 322 HUNGERFORD ROAD, CREWE, CHESHIRE CW1 1HG. BARGEAVCARD Telephone 0270 582849

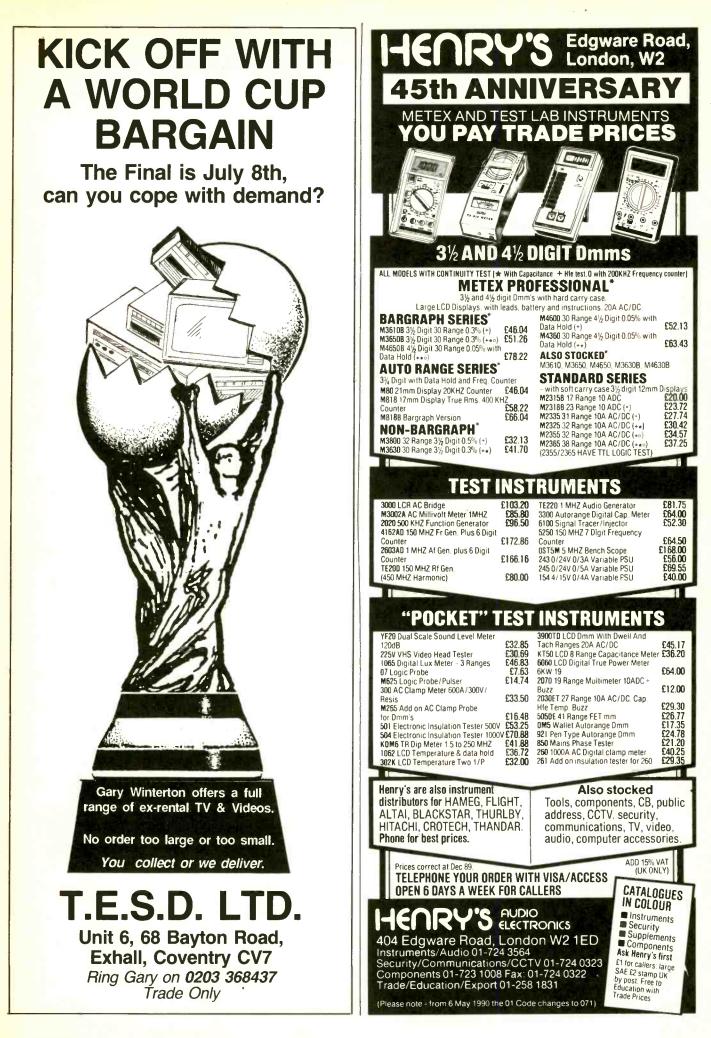

SEMPLE SERVICE D THORN TELEPRICE DISTRIBUTOR SIMPLY THE BEST **BEST QUALITY BEST PRICES IN EX-RENTAL TV & VIDEO EQUIPMENT**

RING TONY ON 0553 766766 FOR YOUR BEST DEAL YET!

SEMPLE SERVICE 59 HALL RD **CLENCHWARTON** KINGS LYNN NORFOLK



IEW-TE CO DURHAM A NEW NAME IN

TELEVISIONS – VIDEOS – TELEVISIONS

TRADE SURPLUS TVs

Large selection mainly THORN — GRANADA STOCK

Discount ten or over

ALL SIZES AVAILABLE Thousands in stock. Good quality. Fresh stock every week.

Portables, Teletext, VHS Videos, STD 20", 22", 26"

Complete loads at discount prices

All stock collected from source by our transport and handled with care.



VHF/UHF CTV from £30 VHF/UHF F/L VHS Videos from £150

All Serviced to a High Standard

FOR EXPORT CALL

T.V. TRADE SALES

E.D.I. House, Kylemore Park West **DUBLIN 10** Telephone: 6264139/6263517

THRIFTY SPARES (WALES) C/O CENTREVISION, SLOPER ROAD, LECKWITH, CARDIFF C	F1 8AB
INCREASE YOUR PROFITS WITH USED SPA	
MANY MAKES OF USED VIDEO AND TV PANELS - GUARANTEED V	VORKING
HUNDREDS NOT LISTED – PHONE OUR HOTLINE 0222 344218	
VIDEO THORN, HITACHI, TOSHIBA, ITT, SHARP, AMSTRAD, PANASON	IC ETC.
USED WORKING VIDEO SPARES	
MIXED BOOSTER	£15.00 £12.50
SERVO PANEL £15.00 DRUM ASS LOADING MOTOR ASS £10.00 CAPSTAN MOTOR BOTTOM BOARD £20.00 POWER PANEL	£15.00 £15.00
MODULATOR	
ALL ABOVE PRICES VAT INC. MANY MAKES OF TV USED SPARES ALSO IN STOCK	
TV TUBES A1 TESTED OPENING HOLIBS 9am-10m - 20m-50m	£20.00

OPENING HOURS 9am-1pm – 2pm-5pm POSTAGE & PACKING £2.00 ORDERS OVER £50 P&P FREE DON'T DELAY PHONE 0222 344218 TODAY

IDEO DISPLAY CORPORATION

NEW VIDEO HEADS - NEW REPLACEMENT HANDSETS - NEW MONITOR CRT TUBES BELTS - IDLERS - FLAPS & TRIMS - VINYLS - PAINTS - SERVICE MANUALS MOTORS - PINCH ROLLERS - CO-AX & SCARTS - TOOLS - TRIPLERS etc etc

> UNBEATABLE 2:10=5 $\Delta \mathbf{I}$

SPECIAL 'PICK & MIX' QUANTITY DISCOUNTS

HANDSETS

THORN/FERGUSON

TX 9/10/90/100 (State Type)	£10.75
3V31/2/5/43/45	£13.00
3V23	
Professional Series	
8000-9000	£10.50

PHILIPS/PYE £11.75 NEC/HITACHI A512230/A514620 type £15.00

SPECIAL

OFFFR

SONY

ÎTT

NEW HITACHI

VT5000 HEAD

KV1612UB/1614E/2204E/KV2704UB/ £13.00 2760E/5020 2760E/5020 13.00 FORALL require KV2210/2220/2730/2740 £15.00 FORALL Upgradable

each

CONTROL Replaces up to 15 Remotes. Does not require original

REMOTE

£17.85

£12 75

UNIVERSAL

Other 'Head to Head' Universals available

Trimline Srs. Non Text £11.50 Trimline Srs. Text £11.50

CALL FOR BEST PRICE

VT3000-3HSS-V

VT5000/5500-3HSS-H VT5000/5500-3HSS-H£21.45 VT6500/7000-3HSSHHA £17.85

VT8000/8300-3HSSHA £17.85

VT8000/8700-3HSSHA £17.85 VT9300/9500-3HSSHA £17.85

VT9700-3HSSHA£17.85

AND MANY MANY MORE T YPES . . . ASK FOR LISTS 3V54/55/57-3HSS-VA £24.68 ITT SHARP HITACHI **VIDEO HEADS** 3V32-8942-3HSS4VB£37.95 VR3605/95-3HSVL£12.75 VC105 etc 3HSSSP£20.25 VT11/14/33/-3HSSHB £17.85 3V43/53/57-3HSS6VA £48.55 VT61/63/-3HSSHB VR3833/3906-3HSSV £12.75 AKAI VC205 etc 3HSSSPB £20.25 3V48-3HSS4VC £40.50

and other models

all models 3HSS-V

AMSTRAD

4500/	5200/9000/PSF1	£18.90
TVR2/	4600/4700/PSF2.	£21.45
VCR7	000 3HSS-R	£21.45

FERGUSON

3V00/1/6/22-3HSS-V	£12.00
3V29/30 etc 3HSS-V	£12.00
3V16/23/24/-3HS-VL	£12.00
3V31/35/6/83HSS-VL.	£12.00
3V39/49/etc 3HSS-VL	£12.00
3V42/44/45 3HSS-VA	£24.68
3V46/47/52-3HSS-VA .	£24.68

0/1/6/22-3HSS-V£12.00 9/30 etc 3HSS-V£12.00 6/23/24/-3HS-VL£12.00 1/35/6/83HSS-VL£12.00 9/49/etc 3HSS-VL£12.00 2/44/45 3HSS-VA £24.68 6/47/52-3HSS-VA £24.68	JVC HR2200/3660-3HSSVL 7600/10/50/700 etc £12.75 HRD140-160-3HSSVA£23.00 HRD725/755-3HSS6VA£48.55	PANASONIC NV2000 types 3HSS-N£12.75 NV250 etc 3HSSU2N 4 Head types NV366 etc 3HSS4NA S41.00	SANYO VHR1100 etc 3HSSSYB £22.00 VHR1300 etc 3HSSSY£27.00 VTC5000 etc PS3BSF £24.30 VTC9300 etc PS4BSF £31.30	SONY SL5000 etc PS3BS1 £'15.55 SL8000 etc PS3BS2 £15.55 SLC20 etc PS4B2S £20.00 SLF60 etc PS5B3S £33.75
PLEA BELT KI AMST. 7000 3 Bell FERG. 3V22 Bells FERG. 3V22 Bells FERG. 3V23 4 Bell FERG. 3V31 4 Bells FERG. 3V35 4 Bell HIT. VT111 6 Bells	TS HIT. 5000 7 Bell Is £0.65 £1.15 N.PAN 300 6 Be S £0.40 S £0.70 S £0.70 S £0.70 S £0.62	s £1.20 SANYO 5300 5 F s £0.46 SANYO 5500 3 F ils £1.10 SANYO 9300 5 F ils £1.70 SANYO 9300 5 F ils £0.78 SHARP 7300 7 F elis £0.87 SHARP 8300 5 F	Bells £1.40 SONY SLC7 6 Bells Bells £1.68 SONY SLC9 6 Bells Bells £1.32 SONY SL8000 6 Bells £1.32 SONY SL8000 6 Bells £1.32 SONY SL8000 6 Bells £1.32 SONY SL8000 6	E1.18 E1.50 E1.50 Bells E0.75
	Video Display dedicated to NEW CATHODE (INCL. COLOUR PS2 OUR MAIN DEPO	CATHODE RAY T Corporation is the world's I the cathode ray tube replac RAY TUBES FOR ALL POP TYPES) ALL PHOSPHOR CARRIES AN INVENTORY finimum Order – 5 Pieces/Mix	cement market. ULAR MONITORS GRADES AVAILABLE, OF 250,000 TUBES	NT!

ALL PRICES EXCLUSIVE OF V.A.T. (UNLESS OTHERWISE STATED) MINIMUM ORDER £5.00 PLEASE ADD £1.00 P&P FOR SINGLE ITEMS (+V.A.T.) OR £1.50 FOR MULTIPLE ORDERS

UNIT 2, AVENUE F **BIRMINGHAM ROAD** INDUSTRIAL EST 'RA FOR D ON-AVON WΔ (S OHU 31470 GRIFEM G PHONE: (0789) 295883/29851 FAX: (N789)

Did you know that the faults and remedies for video, CD and TV in the

ASWO VIDEOTEXT INFORMATION SYSTEM

are from hundreds of technicians all over Europe



For more information write, phone or fax: ASWO (UK) LTD Heston House, 7/9 Emery Road, Brislington, Bristol BS4 6PF

Tel: 0272 · 724475 – Fax: 0272 · 723374 TECHNICIANS AND ASWO VIDEOTEXT INFORMATION SERVICE · THE UNION OF THE FUTURE!

TRADE SALE OF EX-RENTAL CTV'S & VCR'S CHEAPEST POSSIBLE PRICES ANY AMOUNTS SMALL OR LARGE

GRADE 'A' STOCK

THORN CTV's

COLOUR PORTABLES, ALL MAKES, £50. FERGUSON TX9 AND TX10 TEXT, £58 incl. Hand Set. FERGUSON STEREO TEXT SUPER SOUND ALL MODELS, £70 incl. Hand Set. Prices FERGUSON TX9 & TX10 NON-TEXT, £29. ALSO SOME NON-THORN SETS FROM £20. All Sets Serviced and Working **VIDEOS ELECTRONIC** FERGUSON/DER 8929/8930/8940 8941/44 & 3V31/39 NEW SELECTION OF NON THORN SOUT ALSO 3V32/8942 PLUS 3V42 ONWARDS & LONDON 8945 ONWARDS. OUTLE

CROYDON TV'S

26A Portland Road South Norwood SE25 PHONE or CALL Tel: 081-655 0894 FOR DIRECTIONS AND STOCK PRICES



For Friendly Service! Try us, you will like us

REMOTE HANDSETS, VIDEO HEADS PLUS MANY

SPARES FOR CTV'S, VIDEOS IN STOCK NOW.

94 SOHO HILL, HOCKLEY, BIRMINGHAM B19 1AE

STEREO TEXT

FSTs etc

TELEVISION JULY 1990

3V47

Slimline etc

AN3792	E2.95 AN7169	£2.95 HA11706	£3.75 LA4145	£1.70 PLL02A	£5.00 STK5211	£6.75 TA7609P	£2.70 BC516	£0.20	TPOWELL	Andread
AN3821K	£5.95 AN7171K	£3.50 HA11710	£3,75 LA4160	£2.20 SAA1124	£2.50 STK5314	£6.75 TA7611AP	£2.20 BC517	£0.20	T. POWELL	
AN3822K	£6.95 AN7172K	£2.95 HA11711	£6.50 LA4170	£1.75 SAA5000	£1.95 STK5315	£6.75 TA7628P	£1.95 BC639	£0.22 £0.22		and all
AN5010	£2.95 AN7173K	£3.50 HA11713	£3.50 LA4178	£2.20 SAa5030	23.50 STK5324 STK5325	25.75 TA7640AP 26.75 TC010688	L1.94 DD2420	£0.22 £0.50	AC DADDINGTON ODEE	
AN5011	£2.95 AN7178	£2.50 HA11714	£3.50 LA4180	£1.95 SAA5042 £1.95 STA201A	L0.00 CTVE222	01 co 10000r	L4.33 PD3/4C	£0.50	16 PADDINGTON GREE London w2 1LG Tel: 071-723 9246	N
AN5030	£5.25 AN7420	£1.95 HA11715	LJ. DU 1 A 4192	CO 20 STASUIA	13.93 CTK5227	CT 25 TUATUTUA	1.40 BERGO	£0.70	LONDON W2 11 C	
AN5033	£5.25 AN7470	£2.20 HA11716	£4.75 A4190	C1 75 STA4UTA	EJ.50 STK5338	CA SO IUAIUII	1.40 BER91	£1.20		
AN5071	£1.20 BA1335	£2.50 HA11717	£4.75 LA4192	\$1.75 SIA4416	2.75 STK5421	£6.50 IUA1015	£1.50 BFY90	£0.50	Tol: 071 722 02/6	
AN5135K	£3.95 BA1355	£2.20 HA11718	£4.75 LA4201	£1.60 STK0029	£4.75 STK5422	£6.50 TDA1170N	£1.50 BRY56	£0.20	TEI. U/ 1-723 3240	1.1
AN5150	£5.50 BA5102A	£2.50 HA11724	£8.00 LA4220	£1.50 STK0039	£4.75 STK5451	£5.30 TDA1170S	£1.50 BU208A	£1.00	HIDEO HEADO	
AN5151N	£6.50 BA5115	£2.50 HA11727	£8.50 LA4260	£2.30 STK0040	£6.25 STK5471	£5.50 TDA1506	£4.35 BU208D	£1.00	VIDEO HEADS	
AN5256	£2.20 BA5204	£2.20 HA11736	£6.50 LA4261	£2.30 STK0049	£6.50 STK5481	£5.95 TDA1510	£3.60 BU326A	£1.20	JVC/FERGUSON 3HSS	£10.5
AN5265	£1.75 BA5402A	£2.50 HA11744	£5.95 LA4270	£2.75 STK025	£8.50 STK5482	£5.95 TDA1510S1	£3.95 BU406	£0.95	PANASONIC 4HSS	£10.5
AN5410	£3.95 BA5406	£1.50 HA11745	£7.50 LA4280	£2.95 STK077	£6.95 STK5720 £6.95 STK5725	£4.25 TDA1515A	£2.50 BU407	£0.70 £0.95	PANASONIC NV366	£30.0
AN5435	52.20 BA5408	52.20 HA11745N	T £7.50 LA4420 £7.50 LA4422	£1.50 STK078 £1.50 STK433	£6.95 STK5725 £5.25 STK5730	CA OF UMIDEE	1.90 DU4264	£0.93 £0.80	PANASONIC NV366 Original	£41.0
AN5436	52.20 BA6104 BA6109	\$2.20 HA11747A \$1.60 HA11747A		£1.50 STK435	£5.50 STK6732	CH1 75 10A1/10A	24.90 BLIA26E	£0.70	PANASONIC NV730/770 Original	£41.0
AN5510	E2.75 BA6122	52.20 HA11749	£4.25 LA4440	52.50 STK437	£7.50 STK7308	C5 05 TUA2002	£0.801 BU500	£1.50	PANASONIC NV230/450/470	\$27.5
AN5512	£2.95 BA6124	£2.50 HA11750	£5.00 LA4445	£2.20 STK443	£8,95 STK7309	66 50 TUA2003	£0.95 BU508A	£1.00	DANASONIC NV270/280	£20.0
AN5515	52.20 BA6208	£1.95 HA12002	£1.95 LA4446	£2.20 STK457	£7.50 STK7348	£4.95 TDA2004	£1.95 BU508D	£1.00	DAMASONIC NV370/300	£23.0
AN5521	£2.20 BA6209	£1.95 HA12003	£2.20 LA4460	£1.80 STK459	£7.75 STK7404	£6.95 TDA2005	£1.95 2N3055	£0.50	PANASUNIC NVSSU/11	
AN5612	£3.75 BA6218	£1.95 HA12045	£3.25 LA4461	£1.80 STK461	£8.50 STK8050	£9.50 TDA2006	£1.50 2N3773	£1.50	PANASUNIU NV/88	£44.5
AN5613	£2.50 BA6219	£2.20 HA12046	£3.75 LA4465	£2.30 STK463	£9.50 STK8250	£8.95 TDA2020	£1.50 2SA1106	\$2.75		£18.5
AN5620X	£3.50 BA6229	E2.20 HA13001	£1.90 LA4466	£2.30 STK465	£9.95 STK8260	£12.50 TDA2030	£1.50 2SA1186	£3.95	HITACHI VT5000	£15.0
AN5622	£3.20 BA6238A	£1.95 HA13007	£4.50 LA4500	£2.50 STK10504	£7.25 STR370	£5.20 TDA2510	£3.95 2SA1264	£1.95	HITACHI VT8000/9000	£18.5
AN5700	£1.75 BA6239A	£2.20 HA13008	£4.95 LA4505	£2.80 STK1060	£7.95 STR371	£5.20 TDA2600	£6.00 2SA1489 £1.30 2SA1516	£2.95 £2.50	HITACHI VT7/17/19	£36.0
AN5701	£1.20 BA6302A	£1.80 HA13118	£2.75 LA4507	£2.50 STK1070	£9.75 STR380 £7.50 STR381	25.20 TDA2611A 25.20 TDA2653A	£1.30 2SA1516 £3.50 2SB528	£2.50	SHARP Most models not 6300/7300	£20.0
AN5722	£1.60 BA6304	£1.75 HA13403V	£5.50 LA4508	£2.50 STK2025 £1.75 STK2028	£7.50 STR381 £7.50 STR440	25.20 TDA2653A 25.20 TDA3500	£5.50 2SB631	C0.00	AMSTRAD/SAISHO/HINARI	£21.0
AN5730 AN5732	£1.85 BA6305 £1.85 BA6328	£1.95 KA2101 £2.20 KA2206	£1.95 LA4510 £1.75 LA4520	£1.50 STK2029	£6.50 STR441	£5.20 TDA3501	£4.50 2SB775	£1.80		£17.5
AN5750	£1.85 BA6328 £3,75 BA6411	52.20 KA2212	£1.20 LA4570	£2.75 STK2038	£9.50 STR450	£5.20 TDA3505	£4.20 2SB863	\$2.95	SONY DSR35	£19.0
AN5753	£1.95 BA7005	£2.20 KA2261	£1.20 LA6358D	£1.20 STK2048ii	£9.75 STR451	£5.20 TDA3510	£4.50 2SC1403A	£4,50	SUNT USR33	
AN5900	£1.40 BA7023L	£2.50 KA2284	£1.20 LA7031	£2.60 STK2125	£6.75 STR453	£5,20 TDA3560	£3.90 2SC1413A	£2.60	TOSHIBA 9600	£21.0
AN6130N	52.50 BA7751AL	£1.95 LA1130	£2.50 LA7032	£2.95 STK2129	£6.95 STR454	£5.20 TDA3561A	£3.95 2SC1815	£0.10		
AN6136	£1.95 EXB341	£4.50 LA1135	£2.50 LA7042	£2.80 STK2139	£8.00 STR455	£5.20 TDA3562A	£4.50 2SC1913	£1.20		
AN6247	£1.75 HA1196	£1.75 LA1140	£2.20 LA7520	£3,25 STK2155	£9.50 STR457	£5.20 TDA3651	£2.70 2SC1969	£1.75	I WE Wer PLAT 52	14 4
AN6250	£1.50 HA1197	£1.80 LA1150	£1.75 LA7530	£2.75 STK2230	£6.50 STR1096	£4.95 TDA3651AQ	£3.95 2SC2166	£1.00	INO Direch Dellas	\$2.9
AN6310	£5.50 HA1199	£1.50 LA1170	£1.75 LA7800	£1.50 STK2240	£9.50 STR2005	£5.95 TDA3652	£3.50 2SC2235	£0.40	HITACHI Idlar VI11 14 17	£1.7
AN6326N	£3.50 HA1338	E2.95 LA1185	£1.60 LA7801	£1.50 STK2250	£9.50 STR2012	£6.20 TDA4500	C3.95 2SC2335	£1.20		\$2.7
AN6327	£3.50 HA1339A	£3.50 LA1230	£1.50 LA7806	£2.50 STK3041	£6.50 STR2013	£5.20 TDA4501	£4.50 2SC2570	£0.50 £2.75	HITACHI Idler Play VI8000	22.1
AN6328	£3.50 HA1366W	£1.80 LA1231N	£2.00 LA7808	2.75 STK3042 2.75 STK3044	£6.50 STR3115 £5.75 STR3125	25.95 TDA4503 26.20 TDA4505	£4.50 2SC2580 £3.95 2SC2581	\$2.95	HITAGHT VT8000 Idler P/F/Rew.	£1.8
AN6330 AN6332	£2.95 HA1366WR £4.75 HA1367	£1.85 LA1320 £3.50 LA1363	£1.60 LA7820 £1.20 LA7830	£2.20 STK3062	25.75 STR3125 26.75 STR4090	£6.20 TDA4510	C3.95 2SC2581 C3.95 2SC2681 C2.75 2SC3153 C2.50 2SC3156	\$2.80	HITACHI VI 9000 Play Idler	\$2.9
AN6340	£3.75 HA1372	£3.50 LA1365	£1.50 LA7831	£2.50 STK3082ii	£6.95 STR4211	£4.50 TDA4600	E2.75 2SC3153	£3.20	HITACHI Pinch Roller 8000/9000	£2.9
AN6341N	£2.80 HA1377	£2.20 LA1385	£1,95 LB1403	£2.20 STK3102iii	£5.75 STR5015	£6.20 TDA4600-2	£2.50 2SC3156	£3.70	SHARP Play Idler. ORIGINAL	£3.5
AN6342N	£2.50 HA1388	£2.95 LA1460	£2.50 LB1405	£2.20 STK3152Hi	£9.50 STR5412	£5.20 TDA4600-2D	£2.50 2SC3281 £4.95 2SC3300	£2.95	JVC Drum Motor	£22.5
AN6344	£4.75 HA1392	£2.20 LA2000	£1.75 LB1416	£1.50 STK4017	£5.75 STR6020	£5.20 TDA7250	£4.95 2SC3300	\$2.95	SANYO Capstan Motor	£29.5
AN6346N	£3,75 HA1394	£2.50 LA2100	£2.20 LB1640	£2.20 STK4025	£6.50 STR50020	£6.20 UPC575C	£1.00 2SC3409	£2.75	SANYO Reel Motor	£8.0
AN6356N	£3.85 HA1396	£3.75 LA2200	£1.50 LB1649	£2.50 STK4121ii	£6.95 STR50103A	£5.50 UPC1025H	E2.30 2SC3466	£2.95	SANYO Reel Drive Pulley	£5.0
AN6357N	£4.50 HA1397	£2.50 LA2400	£1.50 LC7137	£4.50 STK4122H	£5.95 STR54041	£6.20 UPC1156H	£3.50 2SD358	£0.60		VETOR
AN6359N	£5.50 HA1398	£2.50 LA3101	£1.75 LC7363	£3.75 STK4131ii	£6.75 STR58041 £6.75 TA7193P	£6.20 UPC1185H £4.00 UPC1188H	£2.50 2SD371 £2.75 2SD424	£2.50 £3.95		SISTORS
AN6360	52.60 HA11122W	£2.95 LA3160	£0.95 LC7800	£3.75 STK41321 £3.75 STK41414	£6.75 TA7193P £7.50 TA7205AP	£1.00 UPC1191V	£1.20 2SD476	£1.00		
AN6362	£4.50 HA11211 £3.25 HA11215A	£2.30 LA3161 £2.20 LA3201	£1.20 LC7815 £0.95 LM1303N	£3.75 STK4141ii £1.50 STK4141v	£7.95 TA7217AP	£1.60 UPC1197C	£2.75 2SD424 £1.20 2SD476 £1.60 2SD525	£0.90		
AN6371 AN6387	25.50 HA11215A	£2.20 LA3201 £1.75 LA3210	£0.95 LM1303N	£2.75 STK4141V	£7.30 TA7222AP	£1.30 UPC1230H	£2.50 2SD600	£0.70	6-9-12-13.2 Volts C.W.	\$2.9
AN6562	£1.50 HA11219	1.75 LA3220	£1.50 LM3915N	£2.75 STK4151	£7.50 TA7229P	£3.25 UPC1237H	C2.20 2SD768	£1.20	12-13.2 Volts C.C.W.	12.9
AN6610	£1.80 HA11223W	£2.50 LA3300	£1.65 M5218L	£1.95 STK4152	£7.85 TA7230P	£1.50 UPC1241H	£1.95 2SD811	\$2.95	TE TOLE TONS D. D. TT.	<u>.</u>
AN6671K	£4.95 HA11225	£1.95 LA3301	£1.30 M5218P	£0.95 STK4161ii	£7.95 TA7232P	£1.95 UPC1263C	£2.30 2SD845	\$2.95	CASSETTE HEADS	
AN6676	£5.50 HA11226	£4.50 LA3310	£2.20 M51102L	£2.95 STK4162n	£7.95 TA7233P	£2.50 UPC1277H	C2.50 2SD898B	£2.95	Mono C1 20 Auto Rev	£2.7
AN6677	£4,95 HA11227	£2.20 LA3350	£1.30 M51104L	£3.20 STK4171i	£8.95 TA7240AP	£2.95 UPC1278H	£2.50 2SD1207	£0.60	Ch	L.L. /
AN6876	£1.50 HA11235	£1.95 LA3361	£1.20 M51358P	£1.75 STK4172ii	£8.95 TA7241AP	£2.95 UPC1288V	£2.75 2SD1275	£1.00		
AN7062	£2.75 HA11244	£2.95 LA3370	£2.50 M51393A		£8.95 TA7243P	£2.95 UPC1318AV	£2.75 2SD1276	£1.20		imported
AN7106K	£2.50 HA11251	E2.50 LA3376	£2.20 M51397A	P £5.50 STK4191ii	£9.50 TA7250BP	£2.95 UPC1335V	£2.75 2SD1397	£2.00		e imponito
AN7143	£2.50 HA11401	£2.80 LA3600	£1.50 M51521L	£1.90 STK4192ii	£9.50 TA7251BP	£2.95 UPC1363C	£2.75 2SD1398	£1.50		
AN7147	£2.50 HA11423	£2.20 LA4030	£2.50 M51522L	£1.50 STK4332	£4.50 TA7270P	22.50 UPC1364C	£4.20 2SD1406	£1.50		
AN7148	£2.30 HA11440	£2.95 LA4031P	£1.95 M54543L	£1.75 STK4352	£5.90 TA7271P	E2.50 UPC1365C	E2.95 2SD1407	£1.95		VAT to tota
AN7149N	E2.50 HA11580	25.25 LA4032P	£1.90 M54544L	52.75 STK4793TV	£9.50 TA7280P	E2.95 UPC1373H E2.75 UPC1387C	£1.20 2SD1426 £1.95 2SD1427	£2.95 £3.30		
AN7156N	£2.50 HA11701	£3.50 LA4100 £4.50 LA4101	£1.20 MB3712 £1.00 MB3730	£1.50 STK4803 52.20 STK4833	£8.50 TA7281P £9.50 TA7299P	52.95 UPC1391H	£1.50 2SD1427	13.30		ats
A4171C1								14.20		
AN7161 AN7166	£3.50 HA11703 £3.70 HA11704	£5.20 LA4101	£1.40 MB3731	£2.75 STK4843	£8.95 TA7317P	£1.50 UPC1403CA	£5.50 2SD1453	£1.85		

DALBANI (UK) LTD.

JAPANESE COMPONENTS SPECIALISTS ELECTRONIC COMP. DISTRIBUTORS (Imp. Exp.) EX-STOCK DELIVERY 6,000 DIFFERENT PARTS

TF	RANSISTOF	RS	I	NTEGRATE	D CIRCUIT	rs
2 <mark>SA</mark>	BD	MJ	AN	M	STK	UPC
2SB	BDX	MJE	BA	MB	STR	UPD
2SC	BF	IN	СХ	MC	ТА	CMOS
2SD	BT	2N	HA	MN	TBA	
2SJ	BU	TIP	KA	NE	TC	
2SK	BUT		LA	SAA	ТСА	
3SK	BUW		LB	SAB	TD	
AD	BUX		LC	SI	TDA	
BC	BUY		LM	STA	TTL	


STOCKISTS OF IC'S & TRANSISTORS, AUDIO AND VIDEO HEADS, MOTORS, IDLERS, PULLEYS, ROLLERS, BELTS AND TYRES FOR RADIO CASSETTE, VIDEO AND TV'S. (ORIGINAL AND COPY REPLACEMENT PARTS AVAILABLE)


 DALBANI (UK) LTD

 587A KINGSTON ROAD, RAYNES PARK, LONDON SW20 8SA, ENGLAND

 Tel: 081-543 1971 ● Fax: 081 542 2082 ● TIX 914040

NEW TRADE WAREHOUSE IN SCOTLAND

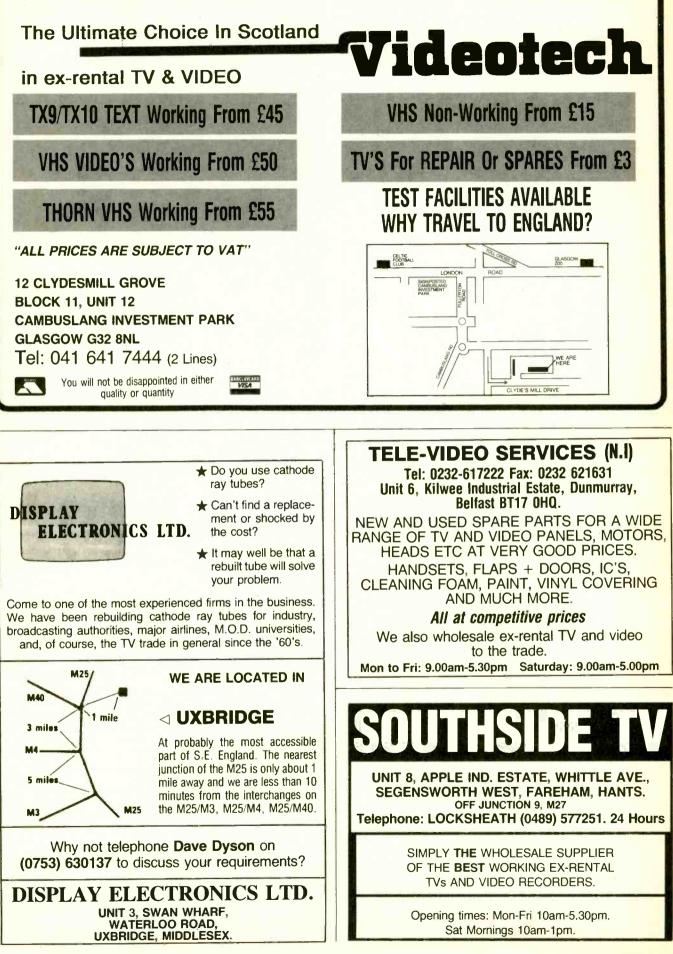

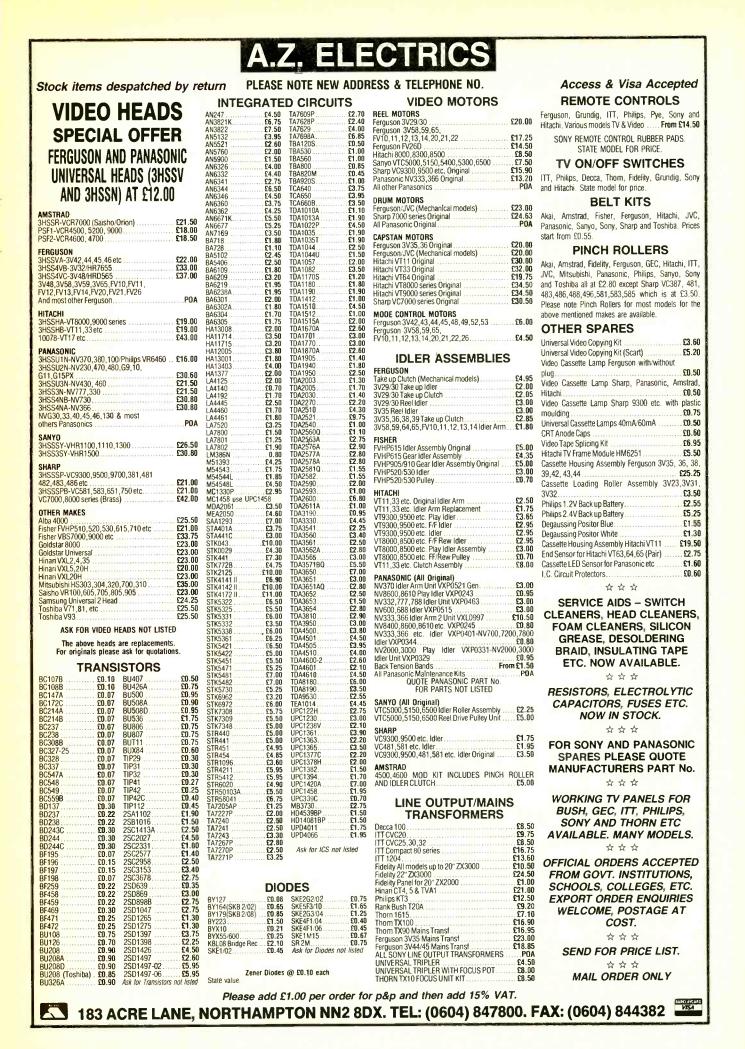

L.R.C. SPARES New 1990 Catalogue out now!


PHONE NOW FOR YOUR FREE COPY

TEL 071-323 2107 FAX 071-323 2191

JULY SPECIAL OFFER IR738 & IR740 REPLACEMENT REMOTE HANDSETS FOR MOST FERGUSON CTV'S £11.50 + VAT

We carry thousands of original & replacement parts to fit

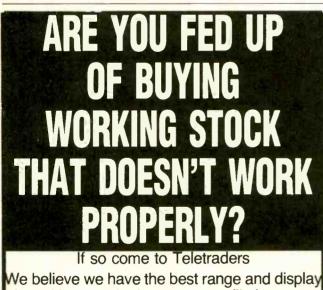JVC, Panasonic, Sony, Ferguson, Akai etc. 3/5, WHITFIELD STREET, LONDON W1P 5RA



We believe we have the best range and display of working stock that you are likely to see anywhere.

Why not come along and see for yourself You won't be disappointed

 \star Guarantee's available on all sets \star

TELETRADERS Brunel Industrial Estate Newton Abbot, Devon Tel. 0626 60154

TV LINE OUTPUT TRANSFORMERS PHONE 01-948 3702

ALBA . AMSTRAD . BUSH . DECCA . DORIC . ETRON . FERGUSON . FIDELITY . GEC . GRUNDIG . GRANADA . HITACHI . HINARI . INDESIT . ITT . KIMARI . NIKKAI . MATSUI . MURPHY . OSAKI . NORDMENDE . REDIFFUSION . PYE . PHILIPS . SANYO . SAISHO . SHARP . SONY .. SOLOVOX . SUSUMU . TANDBURG . TELEFUNKEN . THORN . TRIUMPH.

We also supply: TRANSISTORS . EHT TRAYS . VIDEO HEADS FROM £14.25 . BELT KITS . PINCH ROLLERS . IDLERS . FUSES . IC's . etc.

Callers welcome at our self service shop.

We also manufacture TOROIDAL TRANSFORMERS

TIDMAN MAIL ORDER LTD . 236 SANDYCOMBE ROAD . RICHMOND . SURREY . TW9 2EQ. Mon-Fri 9 am to 12.30 pm & Approx. 1 mile from Kew Bridge. Sat 10 am to 12 noon

COMPUTER SOFTWARE

DO YOU RENT TELEVISIONS? DO YOU STILL USE A CARD SYSTEM? DO YOU FIND IT DIFFICULT TO KNOW YOUR ARREARS TOTAL AT ANY GIVEN TIME? If you do then we recommend our computer TV and Video Rental package. This package includes * automatic updating of each customer's record * alphabetical print-out of each customer's record * alphabetical print-out of each customer's arrears and payments missed * total arrears immediately available * easy to use and operate. New Higher Purchase programme now available as well. These programmes operate on all IBM compatibles running under MS-DOS. Free demonstration discs available. WILLIAM J THOMPSON Donaghanie Post Office

Beragh Co. Tyrone

Telephone Beragh 58214 (0662 7)

PARTS PROBLEM?

For Sharp Sansui



Phone David Allen 0734-876444

Grundig



Phone Stan Perkins 0734-876444

Philips/Pye Whirlpool



Phone Frank Pratt 0734-876444

Ferguson GEC **Fidelity**



Phone Philip Pratt 0734-876444

Amstrad, Akai, Fisher, Mitsubushi, Moulinex, Goldstar, JVC, Nat Panasonic, Pioneer, Matsul, Saisho, Samsung, Salora, Sanyo, Sony, Toshiba, Yamaha and many others.

NO PROBLEM



Phone Mike Curtis 0602-870789

You will not be disappointed, they know what they are talking about



Nillow Vale

ectronics



FOR SALE FIND FAULTS FAST Much quicker than a 'scope, our compact SIGNAL TRACER enables you to follow the signal path and hear the signals. Wonderful for finding breaks, distortion, oscillations, crackles etc in Audio and IF's. Completely isolated, PP9 powered. AF and RF probes supplied. Model P37: £44.50 + £3 p&p + VAT = £4.62. Just Released.

 $\begin{array}{c} \textbf{COMPACT AUDIO OSCILLATOR} \\ \text{5Hz to 20kHz in one sweep, ideal for response testing. Sine/$ Triangle 0 – 2V from 500hms + Square/Pulse 5V 500hm. PP9powered. Model P38 £64.95 + £3 p&p + VAT = £78.14.Output Cables: BNC to Crocs £3.50 ea inc VAT. $PP9 Batts: £2.90 extra inc p&p & VAT. \\ \end{array}$

20 Folly Lane, St Albans, Herts AL3 5JT 9×4 SAE or Tel. 0727 44785 for more details AS NEW BMR 90 CRT Regenerator analyzer, plus 8 sockets some specialised, £350. Ask for Patrick on 071-253 2232.

SERVICING BOOKS RADIO AND TELEVISION Volume 1 to 1980/81 models (26 books) Newnes to McDonald, £200 ono. (0703) 223684.

BUSH T20-22-26 Panel Repairs/Exchange service. Ring Letchworth 672820.

METERS

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.



ESTABLISHED 14 YEARS TV & Video Repair Business For Sale. To include large house, landscape garden, workshop with drive-in access. All equipment. £120,000 freehold. Tel. Northampton 0604 847100.

box number £2.00 extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2331, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 071-261 5942).



NOW OPEN IN CORNWALL

DECENT, CLEAN WORKING & NON WORKING THORN TV's & VCR'S AT COMPETITIVE TRADE PRICES LARGE WAREHOUSE PREMISES

COWELL TV & VIDEO WHOLESALE MEVAGISSEY ST. AUSTELL (0726) 842582 (0726) 69384

BOOKS AND PUBLICATIONS

IO COLOUR	DEAD SET	TRIPPING
FA	157 F	IX
TV	& VIDEO FAULT FILES	
Fast Fix fault ca either television and camera faul TV Fault Fiding, 1981-1989 incl sands of faults manufacturers example is a PI p744/Aug '88. with a speedy this magazine boxed, quick to could pay for its	k issues of Television the rd filing systems list the faults or Videorecon the faults or Videorecon the faults or Videorecon VCR Clinic and Servic usive. Each card file which are collated and name and then chassis hilips K30 with a blank The Fast Fix card files means of locating fau saving you time and o use and easily upd elf with just one succes East. Fix Video C3	the symptoms of der, camcorder <i>Magazine</i> under <i>ce Bureau</i> from contains thou- d indexed under s or model. An raster, look on will provide you ths published in money. Ready atable. Fast Fix ssful repair. Fast
sen	d cheque/P.O. payable	2
	A. G. Humphreys, 13 Mansfield Avenue,	NO
St John's P	ark, Hawarden, Dees	ide, Clwyd. 🔀
	details telephone 02	3
* WILL	NOT ACCEPT A CASS	
SAT	ELLITE SYSTE	MS
	EURO-SAT	-
	EURO-SAI	
	LIERS TO H.M.F RERS OF G.R.P. DIS	
	LIERS TO H.M.F RERS OF G.R.P. DIS 258 80cm DIA 278 2.0M DIA 288 2.3M/PETA	248.50 £180

OCHRE MILL TECHNICAL SERVICES. Are now on 0666 (Malmesbury) 823228. Grundig TV spares, all models to 1983. Fast, friendly, helpful, sensible prices. Gt Lype Farm, Charlton, Nr Malmesbury, Wilts SN16 9DR

	instructions is	The kit, whi especially	obtained every time ich comes with full useful on ex-rental
12	work for thos	e sets with	excellent cabinets
had at your	and good but	scratched t	ubes which may be could pay for itself
with your fin	tioh!	ces. The Ki	could puty for hour
SPECIAL PR	ICE \$35.00 + \$2 5	50 P&P Ele	ctric drill required
OFECHALTIN		ERVIC	
100			
8 ORCHARD	d Abbotts, Herts SG	0 871474	* MAIL URDEN * * CALLERS STRICTLY
Stanstea	d Abbotts, Herts SG	12 <u>8AH</u>	BY APPOINTMENT *
LINE OUTPUT	TRANSFORMERS	TRIPLERS O	Continued
ASA	from 8.39	Nordmende	
Autovox	from 9.45	Philips	from 5.25
B&0	from 8.39 to 9.45	Saba	from 5.25 to 8.39
Blaupunkt	from 10,49 to 18.90	Siemens	from 5.25 to 8.39
Decca	from 8.39 to 13.65	Telefunken	from 5.25 to 8.39
Grundig	from 6.30 to 12.60	TRIPLERS -	Grundig Chassis
	from 8.39 to 13.65	CUC 2201	each 9.95
FTT Körting Loewe Oota	from 7.35 to 9.45	CUC 3400	each 9,95
Loewe Opta	from 9.45 to 13.65	CUC 3410	each 9,95
Luxor	trom 9.45	CUC 2600	each 9.95
Nordmende	from 8.39 to 18.90	CUC 2800	each 9.95
Philips	from 6.30 to 16.80	CUC 2400	each 9,95
Saba	from 10.49 to 14.69	CUC 2410	each 9.95
Salora	from 8.39	CUC 2200	each 9.95
Siemens	from 9.45 to 18.90	CUC 3300	each 9.95
Telefunken	from 9.45 to 11.55	CUC 2210	each 9.95
TRIPLERS			DDE TRANSFORMER
ASA	from 7.35	for Grundig	
Autovox	from 5.25	CUC 95	each 7.95
Decca	from 5.25 to 6.30	CUC 120	each 7.95
Grundig	from 5.25 to 6.30 from 5.25 to 9.95 from 5.25 to 8.39 from 5.25 to 8.39 from 5.25 to 9.49	CUC 220	each 7.95
III Î	from 5.25 to 8.39	NO ACCOUR	ITS/NO CREDIT CARDS
Körting	from 5.25 to 8.39	POSTAL C	ROER/CHEQUE WITH
Loewe Opta	from 5.25 to 9.49	OROER/	ADO 2.50 FOR P&P
LOPTX for Siem	ens FF 3057 Colour TV	Original Part N	o. 52-46300 3009, 24.95
	PLEASE ASK FOR OU		
DON	IBERG ELE	CTRON	IICS LTD
CCUOOL M	ASTERS HOUSE, RA	MAFAST CO	DONEGAL FIRE
	ANTERN RUUSE RA		

1 to 24 volts up 1 1/2 amps D.C	BLE VOLTAN	to 20 volts up t ad. Twin panel	to 1 amp. 1 te I meters for	o 16 volts up 1
Fully variable. Operates from 240V A.C. Compact Unit size 9×51/2×3	ins.	an x	1	£42 VA + Post C
RAC	IO COMP	ONENT S	PECIAL	STS
ACCESS	337 WHITEHO SURREY, U. E. Delivery 7 day	K. Tel: 081	684 1665	VISA

TV TRADE CENTRE NEW MILTON HANTS "THE BEST WAREHOUSE IN THE SOUTH"

Large selection of good clean ex-rental TV's and videos the trade. Guaranteed working or untested/faulty. PHONE (0425) 638885 for details/prices. Unit 2, Millfield, Queensway, Stem Lane Ind Estate, New Milton, Hants.

MERSEYSIDE + NORTHWEST DEALERS PRICES FOR GOOD CLEAN WORKING STOCK – SERVICED, READY TO RETAIL
Mk III£15.00
Mk IIIA£17.00
G11£17.00
Mk IV£36.00
Mk IV TEXT
G11 TEXT
K30 TEXT
PANTEXT
MECHANICAL VIDEOS VHS

IN 5's - £10 each TO CLEAR Ideal for Spares or Repair

SLOT METERS £2 each

Please ring with your requirements **DISCOUNT TV SERVICES 29 CHURCH STREET RUNCORN, CHESHIRE** Tel: 0928 577203




TELEVISION JULY 1990

EURC

TEL: 061-962 0524

do not supply system

ST., SALE,

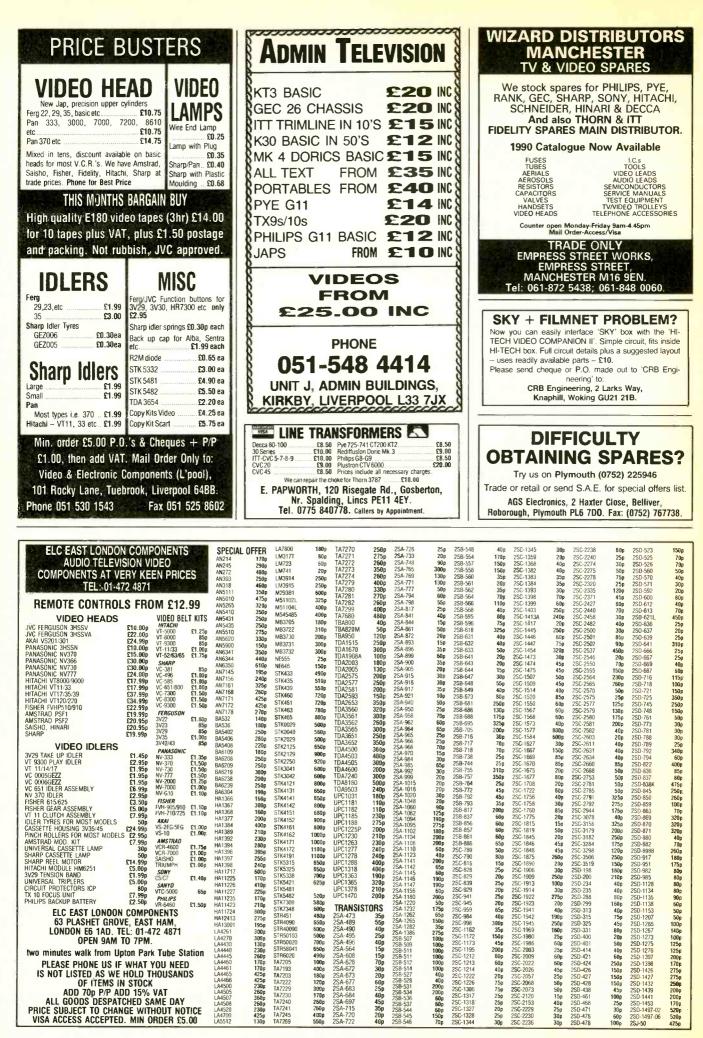

7<mark>3</mark>2

TELEVISION JULY 1990

MM		B	ESCO I	LIMIT	ED	
J 0274	71		T/			
FAX: 029						
Zian ANY	A NO	RTH	WEST	ELEC	TRON	ICS
ANN E	NTIRE	RANG	E OF EX-	RENTA	L TVs &	VIDEOS
			DAY, WORK			
V	Vorkin <mark>g</mark> VH	IS vide <mark>o fr</mark> on	itachi, Ferguson £35.00. Late	models alwa	ys available.	elc.
	FERGU	SON, PYE,	PRICES ON HITACHI, PHIL	IPS, BUSH,	ITT, etc.	
FERGUSON			AINS FROM £ £55.00. PHILIF			VAILABLE.
			R TV AND V			
	,	Working	Ex-Equipme	ent Panels	5	
IF T20//22X	Co 5	onverger	Decoder 14	Line scan 18	Power 17	Frame 14
T26 X 718 7.50	5 5		16 14	20 20	17 3	X 14.00
Philips G11 14.		ices include	12 e Postage & Pa	20 acking But	20 + VAT	11.50
	★ IF TH		REQUIRE IS NOT L		ASK *	
SPRINGMILL STRE	FORD			UNIT 3	MANCHE MERSEY RD.	NORTH IND EST.,
MANCHESTER ROA RING: TONY OR TE			rices are plus VAT based on quantity	FAILS	NORTH DAVID (061) 68	
OPEN 6 DAYS 9am					6 DAYS 9am-5	
VISA WELCOME				CH	EQUES ACCEPTE	WITH BANK CARD
	INTRI					ADARIV
INDEPEN	IDENI TESTED		VISION	8. VID	EO CON	VIPANY UNTESTED
all sizes	from £30	from £20	VISION VHS	all sizes	from £30	from £20
all sizes TOSHIBA all sizes	from £30 TESTED from £30	from £20 UNTESTED from £20	VISION VHS VIDEO TESTED FROM	all sizes GRUNDIG all sizes	from £30 TESTED from £30	from £20 UNTESTED from £20
all sizes TOSHIBA all sizes VARIOUS (from £30 TESTED	from £20 UNTESTED from £20 SIONS		all sizes GRUNDIG all sizes VARIO	from £30 TESTED	from £20 UNTESTED from £20 VISIONS
all sizes TOSHIBA all sizes VARIOUS (unte: TELETE)	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION	from £20 UNTESTED from £20 SIONS R/C		all sizes GRUNDIG all sizes VARIO TEL	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI	from £20 UNTESTED from £20 VISIONS 0 V R/C
all sizes TOSHIBA all sizes VARIOUS (untes TELETE) untes	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00	from £20 UNTESTED from £20 SIONS R/C		all sizes GRUNDIG all sizes VARIO TEL	from £30 TESTED from £30 US COLOUR TELE tested from £10.0	from £20 UNTESTED from £20 VISIONS 0 N R/C 0
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION sted from £30.00 LOADS AVAILAE	from £20 UNTESTED from £20 SIONS R/C BLE	FROM	all sizes GRUNDIG all sizes VARIO TEL	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 ESS & VISA ACCE	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION sted from £30.00 LOADS AVAILAE	from £20 UNTESTED from £20 SIONS R/C BLE		all sizes GRUNDIG all sizes VARIO TEL	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 ESS & VISA ACCE	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION sted from £30.00 LOADS AVAILAE	from £20 UNTESTED from £20 SIONS R/C BLE	FROM ESSESSE	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EESS & VISA ACCE	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION sted from £30.00 LOADS AVAILAE RE ALL GENU	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHE	FROM E E & TWO'S INCLU	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EESS & VISA ACCE G YOUR TRADE	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED
all sizes TOSHIBA all sizes VARIOUS (untes TELETE) untes DIRECT THESE A	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION sted from £30.00 LOADS AVAILAE RE ALL GENUI	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHE	FROM EE & TWO'S INCLU	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EESS & VISA ACCE G YOUR TRADE	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT THESE AI	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION sted from £30.00 LOADS AVAILAE RE ALL GENUI WE ARE RE-FI	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHEL ALL EN(FROM ESSINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN I EXPORT DNS & VII LCOME	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EESS & VISA ACCE G YOUR TRADE	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED CARD
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT THESE AI	from £30 TESTED from £30 COLOUR TELEVI sted from £5.00 XT TELEVISION sted from £30.00 LOADS AVAILAE RE ALL GENU WE ARE RE-FE	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHEI ALL ENC	FROM ESSINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM SINCLUM	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN IEXPORT INS & VII ICOME AN CABINETS A	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EESS & VISA ACCE G YOUR TRADE	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED CARD
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT THESE AI TELEX: 378414 BLB ALL OUR TELEVISIO NU (10,00	from £30 TESTED from £30 COLOUR TELEVI sted from £30.00 LOADS AVAILAE RE ALL GENU WE ARE RE-FL IRD G NS AND VIDEO OTTINGHA	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHEI ALL EN(DS ARE IN GOOD	FROM E & TWO'S INCLU S LARGEST D TELEVISIO QUIRIES WE D ORDER WITH CLE NEW Black &	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN IEXPORT INS & VII ICOME AN CABINETS A (6,000	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EERS OF DEOS ERS OF DEOS	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED CARD CARD
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT THESE AI TELEX: 378414 BLB ALL OUR TELEVISIO (10,00 Unit 3-3	from £30 TESTED from £30 COLOUR TELEVI sted from £30.00 LOADS AVAILAE RE ALL GENU WE ARE RE ALL GENU WE ARE RE-FI IRD G NS AND VIDEO OTTINGHA 0 sq. feet Ware a Meadow Tra Meadow Lane	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHEI ALL EN(DS ARE IN GOOD M ehouse) ding Est.	FROM E & TWO'S INCLU S LARGEST D TELEVISION D ORDER WITH CLE NEW Black & White Portable	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN IEXPORT DNS & VII ICOME AN CABINETS A (6,000 2 min fro	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EERS & VISA ACCE G YOUR TRADE ERS OF DEOS	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED CARD CARD CARD CARD CARD CARD CARD CAR
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT THESE AI TELEX: 378414 BLB ALL OUR TELEVISIO (10,00 Unit 3-3 Near Nott	from £30 TESTED from £30 COLOUR TELEVI sted from £30.00 TOADS AVAILAE RE ALL GENU WE ARE RE ALL GENU WE ARE RE-FE IRD G NS AND VIDEO OTTINGHA 0 sq. feet Ward 3 Meadow Tra Meadow Lane IS County Footh re Yard, Notting	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHEI ALL EN(DS ARE IN GOOD M ehouse) ding Est.	FROM E & TWO'S INCLUE S LARGEST D TELEVISION OUIRIES WE D ORDER WITH CLE NEW Black & White Portable TV'S Battery & mains for	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN IEXPORT INS & VII ICOME AN CABINETS A (6,000 2 min fro Meadou	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EESS & VISA ACCE G YOUR TRADE G YOUR TRADE ERS OF DEOS	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED CARD CARD CARD CARD CARD CARD CARD CAR
all sizes TOSHIBA all sizes VARIOUS (unter TELETE) untes DIRECT THESE AN TELEX: 378414 BLB ALL OUR TELEVISIO (10,00 Unit 3-3 Near Nott In National Tyr	from £30 TESTED from £30 COLOUR TELEVI sted from £30.00 LOADS AVAILAE RE ALL GENU WE ARE RE ALL GENU WE ARE RE-FE IRD G NS AND VIDEO OTTINGHA 0 sq. feet Ward 3 Meadow Tra Meadow Lane is County Footb	from £20 UNTESTED from £20 SIONS R/C BLE INE PRICES ON EUROPE URBISHEL ALL ENI OS ARE IN GOOD M ehouse) ding Est. ball Ground gham NG2 3HQ	FROM E & TWO'S INCLUE S LARGEST D TELEVISION OUIRIES WE D ORDER WITH CLE NEW Black & White Portable TV's Battery &	all sizes GRUNDIG all sizes VARIO TEL ACC DED JUST BRIN IEXPORT INS & VII ICOME AN CABINETS A (6,000 2 min fro Meador 27 Amo	from £30 TESTED from £30 US COLOUR TELE tested from £10.0 ETEXT TELEVISIOI Tested from £50.0 EERS & VISA ACCE G YOUR TRADE ERS OF DEOS	from £20 UNTESTED from £20 VISIONS 0 N R/C 0 PTED CARD CARD CARD CARD CARD CARD CARD CAR

N. IRELAND T	NOT THE OWNER WATER	WHOLESALE	COMME	VIDEO RCIALS CASTER	OPENED
 ★ TVs FROM ONLY £15 ★ VCR FROM ONLY £40 ★ WE HAVE A HUGE SELECTION OF 		COLOUR TV's from £8	LARGE STOCK OF ORIGINAL SECONDHAND REMOTES FROM £2		NEW STOCK ARRIVING EVERY WEEK
H I I I I I I I I I I I I I I I I I I I	IGH QUALITY B GRADE PRODUCTS SAVE £££s	FERG K30 from £30	WORKING TEXT from £55	DISCOUNT For Quantity	WORKING VIDEOS from £65
	MAKES INCLUDE TOSHIBA, HITACHI, SANYO etc	working g11's £18	WE STOCK GRANADA & THORN	BPW from £2	working TV's from £15
UNIT 13A GORTRUSH IND. EST. DERRY ROAD,	TRONIC	PORTABLES from £55	DELIVERY Service	THORN FRONT LOADER from £80	TV/VIDEO LEADS 10 for £2
OMAGH, CO. TYRONE.	TELEPHONE (0662) 247911	UNIT 43 APLEY RD — 0302 344553 DONCASTER SOUTH YORKSHIRE (Entrance Elmfield Road)			

MULTIVISION TELEVISION WHOLESALERS

WORKING TELEVISIONS

Decca (Various models) £15 from £12 Finlandia CTVs £20 Ferguson TX10 GEC Starline (some remote) £15 **ITT** Trimline £25 Nat Pan remote £30 Philips/Pve £15 Philips KT3 + K30 £28 **Rediffusion Mk3** £12

Desitifications MILO secolds 00	5
Rediffusion Mk3 cable £5	
Toshiba from £15	5
Nat Pan T/Text £60)
Philips KT3 + K30 T/Text £60)
Philips G11 T/Text £45	5
Rediffusion Mk4 T/Text £60)
B/W TVs £5	5


NON WORKING

PhilipsVR6462 (for spares)£18PhilipsVR6467 (for spares)£18HitachiVariousModels£18(for spares)£18

Delta CTV's (off the pile) B/W TV's (off the pile) £5


£2

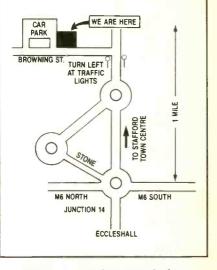Genuine untested stock always available All prices subject to V.A.T.



UNIT 6, BROWNING ST. STAFFORD ST16 3AT. TELEPHONE: 0785 58222.

TELEVISION JULY 1990

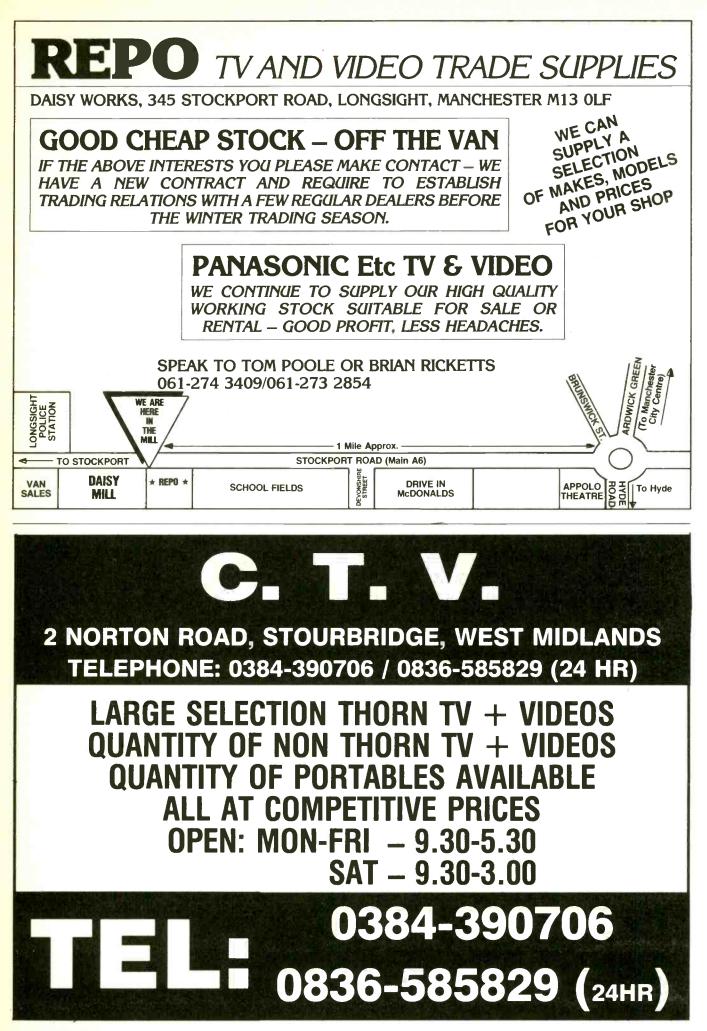





TELEVISIONS

Philips	£15.00
GII Teletext	£30.00
KT3/30 Basic	£25.00
KT3/30 Text	£45.00
GEC Starline	£15.00
GEC Hitachi Basis	£20.00
GEC Hitachi R/C	£25.00
TX9-10	£25.00
TX10-9 Teletext	£45.00
Jap Basic from	£25.00
Jap R/C from	£25.00
Jap Text from	£50.00
Rediffusion Mk II Basic	£25.00
Rediffusion Text	£50.00
Tatung F.S.T. Basic	£65.00
Tatung F.S.T. Text	
Finlandia Inline	£12.00
Trimline from	£20.00

VIDEO

Hitachi VT8300/EQ	£48.0 <mark>0</mark>
3V29-30	£55.00
Sharp VT9300/EQ	£75.00
NV333/366	£65.00
NV230/	£95.00
Philips Various types from	£75.00

MINIMUM QUANTITY OF FIVE

MIDI SYSTEM	£35
80w STEREO	£55
50w STEREO	£30
5″ B/W TV	£35

VIDEOS FOR **SPARES**

BIRMINGHAM UNIT 4A ABBERLEY STREET LONGBRIDE ROAD SMETHWICK PRESTON BIRMINGHAM PR2 5BB B66 2QU TEL: 0772 655011 TEL: 021 565 1727 FAX: 021 555 5367 TELEX NO. 0902 333 199

PRESTON UNIT 34 ROMAN WAY PANASONIC

JVC

EX-GRANADA

EXPORT ENQUIRIES WELCOME ALL PRICES ARE SUBJECT TO 15% VAT & BASED ON QUANTITY

TVs - COLOUR - TVs

Fully working TVs, all with EXCELLENT CABINETS. Fully soak tested for immediate sale and all on working display.

Always a good mix of K-73 – K-30 Mark 3 and 4 Grundig and many others. Basic to text. Changes daily.

Off the pile stock available from around £5 upwards. Direct loads available to suit you – Phone us.

MAIL ORDER USED VCR SPARES

3-V29-30-35 etc. Panasonic 2000, 2010, 7000, 7200, 777, 370 and others. Akai, Hitachi, Sharp, Pye, Philips, Samsung changing daily. Phone for details and prices. S.A.E. by post.

GENERAL FACTORS – Open 10am-5pm Mon-Fri Union St., off Sepulchre Gate West, Doncaster South Yorks DN1 3AE Tel 0302-349583 Fax 0302-349510 2¹/₂ miles from A1M for M18 – M1



DIRECT FROM THE FACTORY WHERE THE BEST COSTS LESS

FINEST QUALITY LOWEST PRICES SPECIAL DISCOUNTS FOR

BULK BUYERS

2 YEAR GUARANTEE, 4 YEAR OPTIONAL

ALL MAKES INC. SONY

NATIONWIDE DELIVERY

SHERWOOD TUBES LTD 60A PEVERIL STREET, NOTTINGHAM NG7 4AH. Tel. 0602 786896

THIS MONTH'S SPECIAL OFFERS FROM HRS

	Save	Price	Order Code	
Original Ferguson/ JVC Head	£4.00	£11.95	PU3132J	
7 Seg Led Display Red	£1.25	0.25	LDD05	
5 Volt 1 amp Regulator	0.40	0.25	T7805	
TV Thyristor (BT106)	£1.00	£1.50	VT106	
BFY 50 Transistor	0.11	0.18	BFY50	
Octal Tri State Bus	0.24	0.65	74LS245	
 3 State 4×2 inp Mulpxr	0.50	0.47	74LS257	
Dual VCO	0.40	£1.99	74LS629K	

OFFER VALID UNTIL 31st JULY 1990

Telephone your order NOW.


All offers apply to account customers only.

If you would like to hear more about the 35,000 HRS stocklines, 24 hour delivery and account facilities **© 021-789 7575**

HRS ELECTRONICS PIC Garretts Green Lane, Birmingham B33 OUE.

Tel. 021-789 7575 Fax: 021-789 8040

SERVICE SHEETS

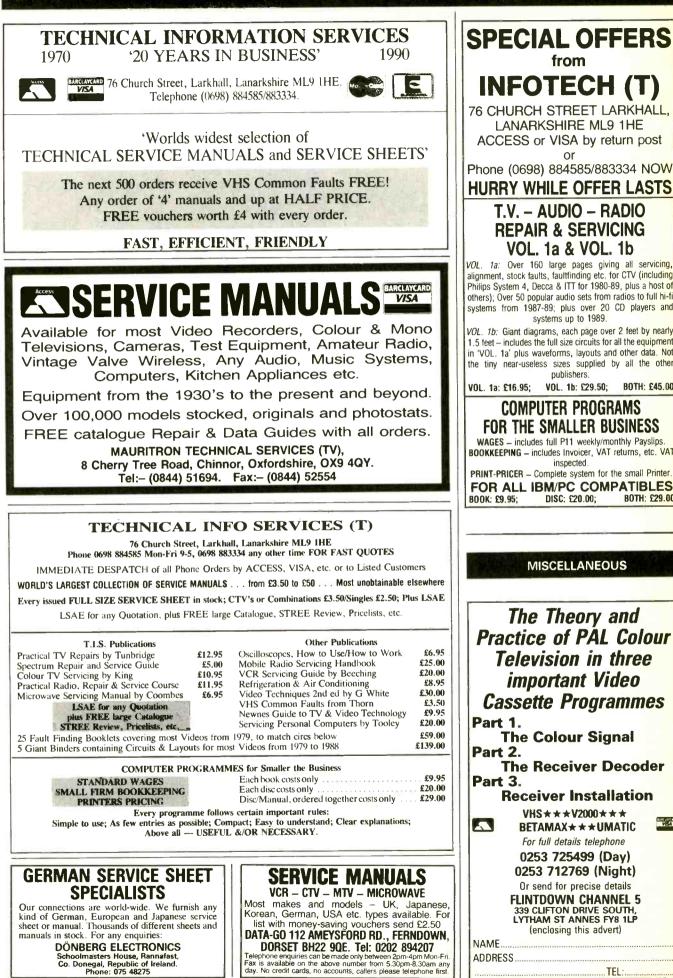

LANARKSHIRE ML9 1HE ACCESS or VISA by return post or Phone (0698) 884585/883334 NOW HURRY WHILE OFFER LASTS T.V. - AUDIO - RADIO **REPAIR & SERVICING** VOL. 1a & VOL. 1b VOL. 1a: Over 160 large pages giving all servicing, alignment, stock faults, faultfinding etc. for CTV (including Philips System 4, Decca & ITT for 1980-89, plus a host of others); Over 50 popular audio sets from radios to full hi-fi systems from 1987-89; plus over 20 CD players and systems up to 1989. VOL. 1b: Giant diagrams, each page over 2 feet by nearly 1.5 feet - includes the full size circuits for all the equipment in 'VOL. 1a' plus waveforms, layouts and other data. Not the tiny near-useless sizes supplied by all the other publishers. VOL. 1a: £16.95; VOL. 1b: £29.50; BOTH: £45.00 COMPUTER PROGRAMS FOR THE SMALLER BUSINESS WAGES - includes full P11 weekly/monthly Payslips. BOOKKEEPING - includes Invoicer, VAT returns, etc. VAT inspected. PRINT-PRICER - Complete system for the small Printer. FOR ALL IBM/PC COMPATIBLES BOOK: £9.95; DISC: £20.00: BOTH: £29.00 MISCELLANEOUS The Theory and Practice of PAL Colour Television in three

important Video **Cassette Programmes** Part 1. The Colour Signal Part 2. The Receiver Decoder Part 3. **Receiver Installation** VHS***V2000*** VISA BETAMAX * * * UMATIC For full details telephone 0253 725499 (Day) 0253 712769 (Night) Or send for precise details **FLINTDOWN CHANNEL 5** 339 CLIFTON DRIVE SOUTH, LYTHAM ST ANNES FY8 1LP (enclosing this advert) NAME. ADDRESS.

TEL:..





TECHNICALLY SPEAKING WE'RE ON TOP OF THE WORLD

Thatcham, Berkshire Salary range c.£15k-£19k

(+Car for some positions)

Sony's success is due not only to our extensive product range, but also to our commitment to both quality and people. To help continue this success, we're keen to hear from Service Technical Support and Product Support professionals at several levels. With City and Guilds 224, HNC or equivalent, you could join the team whose ability and enthusiasm have helped establish a worldwide reputation for product excellence.

SERVICE TECHNICAL SUPPORT Service Engineering Manager

Already accomplished in a Technical Support role you will take responsibility for the management of your department. Your section will research and resolve product, trade and customer related problems, and investigate service technical requirements. You will be involved in liaising with factories and dealers and maintaining a hands-on approach.

Technical Support Engineer

Using a practical approach, your responsibility is the investigation and resolution of technically related product, trade and customer problems. You will maintain close liaison with factories, and make planned visits to dealers and service companies to provide information, assist technicians and monitor the market place. Evaluating new products you will influence future product serviceability, and research technicians' repair requirements.

Trade Technical Adviser

Providing technical expertise, the majority of your service contact will be by telephone. After training you will be fully conversant with Sony circuitry, providing information to technicians on fault finding, diagnostic procedures and circuit operation. By collating information from your calls you will provide feedback to our Service Engineering and Product Quality Departments. You will also spend periods repairing product to maintain hand-on knowledge.

PRODUCT SUPPORT Product Quality Engineers

Your key responsibility is the investigation of design and production problems on new products and resolving these with our factories. You will initiate action on quality issues, monitoring the market by close liaison with our dealers and evaluating products for quality and customer acceptability.

Whichever position you are best suited to, you should demonstrate good communication skills, finding it easy to interface at all levels. In return, we offer salaries ranging from c.£15k-£19k and a car for some positions. You will also enjoy the kind of benefits one would associate with a name like Sony. These include BUPA, 25 days' holiday, discount on our products and, where appropriate, relocation assistance.

For an application form, please telephone Maggie Swann on 0784 467234. Alternatively, please write to her at Sony (UK) Limited, Sony House, South Street, Staines, Middlesex TW18 4PF.



A UNIQUE OPPORTUNITY TO EXPAND YOUR SKILLS

You're a qualified repair technician with some experience of TV or video, maybe working in the Service industry. You're looking for a way to use and develop your skills.

AGB Television is the answer.

We're one of the world's leading research organisations, and have just been awarded the world's largest ever contract to install our specialist electronic devices to TV's and VCR's throughout the country.

TECHNICAL SERVICE ENGINEERS

Initially, we need 40 engineers to work until March 1991. After that, the cream of the group will be offered permanent positions.

It's well paid, non-rental, non-routine work, and the rewards include a company car.

If you've got the qualifications and the enthusiasm, and a clean driving licence, switch on to AGB Television.

For details, contact Sarah de Buriatte, on 081 997 8484, or send a curriculum vitae to



The Research Centre, West Gate, London W5 3HH.

AGB TELEVISION RECRUITMENT







VISA

Comet

Further information literature - cheques payable to: TECHNICAL ADVISORY SYSTEMS, 33 FOXCOTE, ASTLEY VILLAGE, CHORLEY, LANCASHIRE PR7 1XE. Telephone: (02572) 75667

HEWIT STREET

CREWE

Fire

Garage

Manor Supplies 683 Applin Electronics Cover II Apultron (TV) 738 Multivision 734 Multivision 734 Multivision 734 Multivision 734 Multivision 734 Multivision 733 Multivision 733 Multivision 733 Jorth West Electronics 733 Jmega Electronics 669 *apworth, E 732 CV V Services 730 *beonk TV Wholesale 716 *owell, T 725 *Y Tubes 680 tadio Component Specialist 730 telay Omagh Ltd 728 rend2 Components 744, Cover III, Cover IV Multivison 737 Molt Electronics 738 echnical Information Services 738 eleprice Ltd 720 uppervision 717 echnical Information Services 738 eleprice Ltd 728 </th <th></th> <th>_</th>		_
ADDVERTISEERS Admin Television 732 Admin Television 732 AGB Television 741 AGS Electronics 720 ASS Dectronics 720 ASS Dectronics 720 ASS Dectronics 720 BAS Electronics 727 Bell Adio Systems 720 BAS Electronics 741 Bowli Ltd 741 Centropio Wholesale Ltd 742 Chromavac Ltd 771 Critt 730 Crew TV & Video Wholesale 730 Crew TV & Video Wholesale 732 Crew TV & Video Wholesale 733 Crew TV & Video Wholesale 734 Crew TV & Video Wholesale <th></th> <th></th>		
Admin Television 732 Aenal Techniques 733 AGS Electronics 732 AD Discount IV Warehouse 720 As Di Becontino 734 AS Di Electronics 729 As Mattion Systems 720 Bar Bettonics 644 Bull, Ja N Electrocal 674 Central IV 742 Central IV 742 Centrevision 743 Construct 742 Centrevision 743 Construct 742 Centrevision 742 Construct 742 Construct 742 Construct 743 Construct 744 Construct 744 Construct 745 Construct 744 Construct 743 Construct 744 Construct 745 Construct 741 Dispate Electronics 740 Construct 744 <t< td=""><td></td><td></td></t<>		
Aenal Echniques 703 AGS Electronics 732 Alb Discount TV Warehouse 732 At Discount TV Warehouse 732 Aswo (UK) Ltd. 724 Aswo (UK) Ltd. 724 Bell Fadio Systems 720 Bowl Ld. 726 Bowl Ld. 727 Bowl Ld. 727 Bowl Ld. 727 Bowl Ld. 727 Bowl Ld. 737 Compare Ld. 741 Conteonume Electronics 730 Concourse Ld. 726 Consour LV Seconces 730 Concourse Ld. 726 Databan (UK) Ltd. 725 Databan (UK) Ltd. 725 Databan (UK) Ltd. 726 Databan (UK) Ltd. 726 Databan (UK) Ltd. 732 Donberg Electronics 730, 738, 739 East Commal Components 732 Databan (UK) Ltd. 732 Databan (UK) Ltd. 732 Databan (UK) Ltd. 7	ADVERTISERS	
Aenal Echniques 703 AGS Electronics 732 Alb Discount TV Warehouse 732 At Discount TV Warehouse 732 Aswo (UK) Ltd. 724 Aswo (UK) Ltd. 724 Bell Fadio Systems 720 Bowl Ld. 726 Bowl Ld. 727 Bowl Ld. 727 Bowl Ld. 727 Bowl Ld. 727 Bowl Ld. 737 Compare Ld. 741 Conteonume Electronics 730 Concourse Ld. 726 Consour LV Seconces 730 Concourse Ld. 726 Databan (UK) Ltd. 725 Databan (UK) Ltd. 725 Databan (UK) Ltd. 726 Databan (UK) Ltd. 726 Databan (UK) Ltd. 732 Donberg Electronics 730, 738, 739 East Commal Components 732 Databan (UK) Ltd. 732 Databan (UK) Ltd. 732 Databan (UK) Ltd. 7	Admin Television	732
AGS Electronics 732 At Discount IV Warehouse 720 Aswo (UK) Ltd. 724 Az Electrics 727 Beil Fadio Systems 720 Beil Fadio Systems 720 Bit Cleatonics 720 Bit Cleatonics 720 Bit Cleatonics 720 Bit Cleatonics 720 Central IV 741 Central IV 742 Centrevision 743 Convent V4 Video Wholesale Ltd 717 Cital 716 Cital 717 Convent V4 Video Wholesale 730 Covent V4 Video Wholesale 730 Covent V5 v1 v2 724 Covent V4 Video Wholesale 730 Covent V5 v2 724 Covent V5 v2 724 Covent V5 v2 724 Covent V4 Video Wholesale V1 724 Covent V5 v2 724 Covent V4 V400 V5 738 Display Electronics Ltd 738 Display Electronics Ltd 738 Display Electronics Ltd 737 </td <td>Aenal Techniques</td> <td>703</td>	Aenal Techniques	703
Aswo (UK) Ltd. ??4 Az Electrics ??2 Bell Radio Systems ??00 B K. Electronics ??7 Bowl Ld. X. Electronics Gampion Wholesale Ltd. ??4 Central IV ??42 Centrol IV a Video Wholesale ??43 Corew Minolesale IV ??42 Corewall Components ??43 East Commonics ?73 East London Components ?73 East London Components ?73 Cores IV Supplies ?74 Ectrosant IV ?72 Scal Components ?73 Cores Visuals Ltd ?73 Ectrosant IV ?72 Cores Pro	AGS Electronics	732
Bell Hadio Systems 720 B K. Electronics 674 B M. B. K. Electronics 674 B M. B. K. Electronics 674 Campion Wholesale Ltd 743 Centrevision 743 Chromava Ltd 771 Citkit 776 Campion Wholesale Ltd 773 Core With Va Video Wholesale 730 Crew Wholesale TV 742 Corgodin TV Senvices 730 Display Electronics 730, 738 Display Electronics 730, 738, 739 Display Electronics 730, 738, 739 Commole Devices 744 Commole Devices 744, 705 East Comwall Components 736 Cast Components 736 Cast Components 730 Garchata Ltd 666,676,68 Gardid J 667,68 Gardy J, W. 730 Herror S. 730 Herror S. 730 Herror S. 730 General Zacors 731	Aswo (UK) Ltd.	724
B.K. Electronics 674 Bull, J.& N Electrical 741 Bull, J. & N Electrical 755 Campion Wholesale Ltd 743 Chrear IV 742 Chrear IV 743 Chrear IV 742 Chrear IV 742 Chrear IV 742 Chrear IV 743 Chrear IV 744 Carbon Wholesale IV 742 Coydon IV's 742 Coydon IV's 742 Cordon IV's 742 Dalbaci (W) Ltd 755 Dalbaci (W) Ltd 756 Dalbaci (W) Ltd 756 Danberg Electronics Ltd 726 Danberg Electronics 738 Danberg Electronics 743 Sconomic Devices 704 Coromic Devices 704 Coromic Devices 704 Coromonic Devices 713 Coromonic Devices 714 Devices 713 Coromonic Devices 714		
Bull, J. & R. Electrical. 675 Campion Wholesale Ltd. 743 Central IV 742 Contral IV 742 Convert IV State Wholesale 733 Convert IV State Wholesale 735 Data IV 742 Convert IV Services 731 Dispay Electronics Ltd 726 Donberg Electronics 730 Consel Devices 740 Consel Devices 741 Electronic Please 741 Electronic S 732 Consel Devices 741 Electronic S 731 Consel Devices 741 Electronics 737 Control State Ltd 757 Control State Ltd 757 Schandal Ltd 757	B.K. Electronics.	674
Central IV	Bowtil Ltd. Bull, J & N Electrical	675
Ventrevision (43) Chromavac Ltd (71) Cirkit (71) Cirkit (71) Cirkit (71) Cirkit (71) Colebourne Electronics (73) Crew Wholesale TV (742) Creydon TV's (742) Creydon TV's (742) Creydon TV's (742) Dalabari (UK) Ltd. (725) Data-Go (738) Dispay Electronics Ltd. (73) Dispay Electronics Ltd. (74) East Commic Devices (74) East Components (73) East Components (73) Ecrosmart (74) Ecrosmart (75)	Campion Wholesale Ltd. 7	743
Cirkit 716 Colebourne Electronics 730 Construction 724 Colebourne Electronics 730 CPC 695 Crewe Wholesale TV 742 Croydon TV's 742 Croydon TV's 742 Croydon TV's 742 Croydon TV's 742 Display Electronics Ltd 725 Display Electronics Ltd 726 Conomic Devices 704 Conomic Devices 731 Conomic Devices 733 Conomic Devices 741 Flictronic Visuals Ltd 666 Components 676 Gardatal Ld 666 Components 730 Gardatal Ld 666 Components 730 Conductor 733 Conductor 734 Macro Lopi	Centrevision	743
Convention Yalion Crew Wholesale TV Crew Wholesale TV Crew Wholesale TV Crew Yalion Crew Yalion Crew Yalion Crew Yalion Crew Yalion Data Go 738 Discourt IV Services 730 Discourt IV Services 730 District Components 742 East Comwall Components 732 East Common Components 741 Electronic Visuals Ltd 713 Electronic Visuals Ltd 714 Electronic Visuals Ltd 731 Evental Factors 731 Grandata Ltd 666 General Factors 731 Truphreys, A.G. 730 Ty C.C. 733 Ty C.C. 733 Ty C	Chromavac Ltd.	717
Convention Yalion Crew Wholesale TV Crew Wholesale TV Crew Wholesale TV Crew Yalion Crew Yalion Crew Yalion Crew Yalion Crew Yalion Data Go 738 Discourt IV Services 730 Discourt IV Services 730 District Components 742 East Comwall Components 732 East Common Components 741 Electronic Visuals Ltd 713 Electronic Visuals Ltd 714 Electronic Visuals Ltd 731 Evental Factors 731 Grandata Ltd 666 General Factors 731 Truphreys, A.G. 730 Ty C.C. 733 Ty C.C. 733 Ty C	Clearvision 7 Colehoume Electronics 7	724
Crewe Wholesale TV 742 Crydon TV's 724 C TV 735 Dalbani (UK) Ltd. 725 Dalbar GO 738 Discourt TV Services 731 Display Electronics Ltd. 726 Donberg Electronics Ltd. 732 East Comwall Components. 732 East Commic Devices 704, 738 Economic Devices 704, 735 Economic Devices 741 Electronic Visuals Ltd. 713 Electronic Televisions 736 Garbaldi 686 General Factors 731, 737 Golden Components 670 Grandata Ltd. 666, 667, 668 Fardy, J. W. 730 Topolety B. Scoult Televisions 724 HS Electronics 730 Colkey Discount Televisions 724 HS Electronics 730 Locomponents 730 JDA Audio Visual 714 JL Components 730 Indictch 738 <tr< td=""><td>Cowell I V & Video Wholesale</td><td>/30</td></tr<>	Cowell I V & Video Wholesale	/30
C. I. V	Crewe Wholesale TV	742
Data-Go 738 Display Electronics Ltd. 726 Donberg Electronics 730, 738, 739 East Comwall Components. 732 Economic Devices 744 Electronic Visuals Ltd. 713 Electronic Visuals Ltd. 766 Grandata Ltd. 666.667.668 tardy, J.W. 730 Tenny S. C. C. S. 734 Tilghsurge 736 Tenny S. C. C. C. T. 737 Tumphreys, A.G. 730 Tectronic S.C. C. T. 738 TV C. 733 Indech. 739 Pano Supplies 669 nolocch. 738 TV C. 733 Ink-Up Communications Ltd. 669 Applin Electronics 730 Apolin Ulrich. 733 <tr< td=""><td>C.T.V</td><td>735</td></tr<>	C.T.V	735
Discount IV Services	Dalbani (UK) Ltd	725
Dispat pelectronics 730, 738, 739 East Comwall Components. 732 Conomic Devices 744 Ectonomic Devices 744 Electronic Visuals Ltd 713 Electronic Visuals Ltd 687 Beneral Factors 731, 737 G L Components 670 Grandata Ltd 666, 667, 668 ardry, J W 730 Highsurge 714 Tighsurge 721 Tighsurge 731 Tockley Discount Televisions 724 Tockley Discount Televisions 724 Tockley Discount Televisions 734 Ty C 738 Ty C 734 Gelectronics 730 </td <td>Discount TV Services 7</td> <td>731</td>	Discount TV Services 7	731
East Comwall Components. 676 Cast London Components. 732 Conomic Devices 744 Electronic Visuals Ltd. 713 Electronic Visuals Ltd. 687 Garibaldi 687 General Pactors 731 Grandata Ltd. 666,667,668 Hardy, J.W. 730 Hardy, J.W. 730 Hockley Discount Televisions 724 HS Electronics 737 Humphreys, A.G. 730 Humphreys, A.G. 730 Humphreys, A.G. 732 Hockeh 738 T.V.C. 738 T.V.C. 733 DA Audio Visual 714 J.J. Components 730 Agein Electronics Cover I J.D.Audio Visual 714 J.J. Component Secoland 741	Display Electronics Ltd. 7 Donberg Electronics 730, 738, 7	726 739
Economic Devices 704,705 EC S. 741 Electronic Visuals Ltd 713 Electronic Visuals Ltd 713 Express TV Supplies 741 Flintdown Channel 5 738 Garbaldi 687 General Factors 731,737 S G. L. Components 670 Srandata Ltd 666,667,668 4ardy, J.W. 736 Garbala Ltd 666,667,668 4ardy, J.W. 721 Tightsurge 713 Tuphreys, A.G. 730 Tuscan Central TV 572,673 bex of Scotland 744 CS 669 Intolech 738 TV C. 733 JDA Audio Visual 714 LJ. Components 703 MGE Electronics 734 Apon Supplies 683 Applie Electonics 734 Maor Supplies 683 Applie Electronics 734 Maor Supplies 683	East Comwall Components.	676
E.C.S. 741 Electronic Visuals Ltd. 713 Electronic Visuals Ltd. 713 Electronic Visuals Ltd. 741 Filtidown Channel 5. 738 Garbaldi 687 General Pactors 731 General Pactors 731 General Pactors 731 Gold Components 666,667,668 'ardy, J.W. 730 eteny's 721 tighsurge 718 tockley Discount Televisions 724 HS Electronics 730 ussain Central IV 672, 673 bex of Scotland 741 CS 669 notolech 738 TV C 733 IDA Audio Visual 714 LJ Components 730 Juditio Visual 714 LJ Components 730 Juditio Visual 714 Juditio Components 730 Juditio Visual 714 Juditio Components 730	Fconomic Devices 704 7	705
Electromant 743 Express TV Supplies 741 Rintdown Channel 5 738 Garibaldi 687 General Factors 731,737 G G L. Components 670 Grandata Ltd 666,667,668 fandy, J.W. 730 ereny's 721 tighsurge 718 tockley Discount Televisions 722 tussain Central TV 572, 673 DA Audio Visual 714 LJ Components 730 mascantistics 733 DA Audio Visual 714 LJ Components 734 Kesh Electronics 734 Agelin Electronics 683 Applin Electronics 683 Applin Electronics 734 Mauritorn (TV) 734 Mauriton (TV) 734 Mauriton (TV) 734 Mauriton (Wholesal	E.C.S. 7	741
Flintdown Channel 5 738 Garibaldi 687 General Factors 731,737 G G L Components 670 Grandata Ltd 666,667,668 Hardy, J W. 730 General Ltd 666,667,668 Hardy, J W. 730 General Ltd 666,667,668 Hardy, J W. 730 Ussain Central TV 721 Ussain Central TV 726,773 Ussain Central TV 726,773 JDA Audio Visual 714 J. Components 730 MG Electronics 733 IDA Audio Visual 714 J. Components 733 MG Electronics 734 Kesh Electronics 736 Applin Electronics 728 Apanor Supplies 6689 Apult Ulinch 738 Alder, Ulinch 739 I.G. T. Electronics Ltd 741 Applin Electronics 728 Applin Electronics 733 Muttivision	Electrosmart	43
Garbaldi 687 General Factors 731 G L Components G L 666,667,668 fardy, J.W 730 renny's 721 lighsurge 718 fockley Discount Televisions 724 HS Electronics 730 umphreys, A.G 730 ussain Central TV 672, 673 bex of Scotland 741 CS 669 foloch 733 JL Components 714 JL Components 734 Kesh Electrics 730 Maor Supplies 668 Aanor Supplies 663 Aapin Electronics 734 desh Electrics 730 JL Components 714 JL Components 701 Adurtion (TV) 738 Adurtion (TV) 738 Adurtion (TV) 739 JL C.T Electronics Ltd 741 Orth West Electronics 732 Tothe Service		
General Pactors 731,737 G.G.L. Components 670 Grandata Ltd 666,667,668 fardy, J.W. 730 renny's 721 tighsurge 718 tockley Discount Televisions 724 HS Electronics 737 turnshreys, A.G. 730 tussain Central IV 672, 673 bex of Scotland 741 CS 669 notolech 738 J.J. Components 730 tussain Central IV 669 notolech 738 Auoritorics 734 fesh Electroics 734 desh Electroics 734 desh Electroics 734 desh Electronics 738 daulor Supplies 669 daulor Supplies 669 daulor Supplies 669 daulor Supplies 669 dauor Supplies 669 dauor Supplies 669 daporton (TM) 738	Garibaldi	687
tardy, J. W. 730 tenry's 721 tighsurge 718 tockley Discount Televisions 724 HSE Electronics 730 tumphreys, A. G. 730 tumphreys, A. G. 730 bex of Scotland 671 CS 669 ntolech 738 T. V. C. 733 DJA Audio Visual 714 LJ. Components 703 MGE Electronics 734 Kesh Electrics 730 Jink-Up Communications Ltd. 669 Aanor Supplies 683 Adaplin Electronics Cover II Aduitry Ulrich 738 Valutivision 734 Aduler, Ulrich 739 J. G. T. Electronics Ltd. 741 Valutivision 732 Types Electronics 730 Indenxity Whotesale 730 Types Electronics 730 Intry Ulrich 732 CT V Services 730 Indepa Electronics 732 CT V Services <td>General Factors 731 7</td> <td>37</td>	General Factors 731 7	37
Highsurge 718 Hockley Discount Televisions 724 HRS Electronics 737 Humphreys, A.G. 730 Hussain Central TV 572, 673 bex of Scotland 741 CS 669 Inolech 733 IDA Audio Visual 714 J.J. Components 703 MG Electronics 734 Kesh Electrics 730 J. M. Up Communications Ltd 669 R. C. Spares 728 Aaon Supplies 683 Aguint Electronics Cover II Aduentron (TV) 738 Autitivision 734 Martinon (TV) 738 Auter, Ulrich 739 Auter, Ulrich 739 Auter, Ulrich 731 Morth West Electronics 732 Y. Tubes 680 Aguint (TVV) 732 Yutivision 732 Yutivision 732 Yuter Stelectronics 732		
Highsurge 718 Hockley Discount Televisions 724 HRS Electronics 737 Humphreys, A.G. 730 Hussain Central TV 572, 673 bex of Scotland 741 CS 669 Inolech 733 IDA Audio Visual 714 J.J. Components 703 MG Electronics 734 Kesh Electrics 730 J. M. Up Communications Ltd 669 R. C. Spares 728 Aaon Supplies 683 Aguint Electronics Cover II Aduentron (TV) 738 Autitivision 734 Martinon (TV) 738 Auter, Ulrich 739 Auter, Ulrich 739 Auter, Ulrich 731 Morth West Electronics 732 Y. Tubes 680 Aguint (TVV) 732 Yutivision 732 Yutivision 732 Yuter Stelectronics 732	Hardy, J.W	30 21
bes of Scotland 741 CS 669 Infolech 733 IDA Audio Visual 714 J.J. Components 703 IDA Audio Visual 714 J.J. Components 703 MG Electronics 734 Kesh Electrics 730 ink-Up Communications Ltd 669 R. C. Spares 728 Aanor Supplies 683 Applin Electronics Cover II Auditron (TV) 738 Multivision 734 Multivision 733 Mauriton (TV) 738 Auter, Ulrich 733 Mage Electronics Ltd 741 forth West Electronics 733 mega Electronics 669 Paworth, E 732 CY V Services 730 Scowell, T 725 V Tubes 680 Cadio Component Specialist 730 Gordenoment Specialist 732 MJ Electronics 738	Highsurge 7 Hockley Discount Televisions 7	18
bes of Scotland 741 CS 669 Infolech 733 IDA Audio Visual 714 J.J. Components 703 IDA Audio Visual 714 J.J. Components 703 MG Electronics 734 Kesh Electrics 730 ink-Up Communications Ltd 669 R. C. Spares 728 Aanor Supplies 683 Applin Electronics Cover II Auditron (TV) 738 Multivision 734 Multivision 733 Mauriton (TV) 738 Auter, Ulrich 733 Mage Electronics Ltd 741 forth West Electronics 733 mega Electronics 669 Paworth, E 732 CY V Services 730 Scowell, T 725 V Tubes 680 Cadio Component Specialist 730 Gordenoment Specialist 732 MJ Electronics 738	HRS Electronics 7	37
CS 669 Intolech 738 Intolech 733 JL Components 733 IMG Electronics 734 Kesh Electrics 730 ink-Up Communications Ltd. 669 R. C. Spares 728 Aanor Supplies 683 Adapin Electronics Cover 11 Adauriton (TV) 738 Adultivision 734 Auter, Ulrich 739 J. G. T. Electronics Cover 11 Adultivision 734 Auter, Ulrich 739 J. G. T. Electronics 669 agworht, E. 732 CT V Services 730 Theenix TV Whotesale 716 Yorubes 680 tadio Component Specialist 730 telay Orngh, Ltd. 728 telay Orngh, Ltd. 728 telay Orngh, Ltd. 728 telay Orngh, Ltd. 732 telay Components 744. Cover IV. Intervoot Tubes Ltd. Tase Elevice	Hussain Central TV	73
Infolect 738 T.V.C. 733 DA Audio Visual 714 LJ. Components 703 MG Electronics 734 Gesh Electrics 730 Jink-Up Communications Ltd 669	Ibex of Scotland	41
IDA Audio Visual 714 LJ Components 703 MKG Electonics 734 Kesh Electrics 730 Jink-Up Communications Ltd 669	Infotech	38
J.J. Components 703 MG Electronics 734 Geht Electronics 734 Geht Electronics 734 Geht Electronics 730 ink-Up Communications Ltd 669 R.C. Spares 728 Aanor Supplies 683 Aapin Electronics Cover II Mauritron (TV) 738 Autitrysion 734 Muter, Ulrich 733 Inge 2 Electronics 669 Page a Electronics 669 Page a Electronics 669 Page a Electronics 733 Mega Electronics 736 Autitry Wholesale 716 Poenix TV Wholesale 716 Page Detronics 728 Pago TV 735 Statio Component Specialist 730 Poenix TV Wholesale 716 Pago TV 735 Page Detroice 722 My Electronics 738 Mute Ulutotions 736 Pago TV 73		
Kesh Electrics 730 Jink-Up Communications Ltd. 669 "R. C. Spares 728 Aanor Supplies 683 Aapin Electronics Cover II Adurting (TV) 738 Adultry (Unich. 739 Adultry (Unich. 739 J. G. T. Electronics Ltd. 741 Adulter, Ulrich. 733 Jorth West Electronics 669 Papworth, E. 732 Ch Y. Services 730 Propenkit V. Wholesale 716 Youngh Ltd. 744 Every Ory 735 etay Dragh Ltd. 728 etay Orugh Ltd. 726 etay Orugh Ltd. 726 etay Orugh Ltd. 726 etay Orugh Ltd.	J.J. Components	03
ink-Up Communications Ltd 669 R.C. Spares 728 Aanor Supplies 683 Aapin Electronics Cover II Mauritron (TV) 738 Adultivision 734 Auter, Ulrich 739 Judit Station 734 Auter, Ulrich 739 J.G. T. Electronics Ltd. 741 storth West Electronics 669 Payworth, E 732 CTV Services 730 Procenx TV Whotesale 716 Youge Statist 730 Adaio Component Specialist 730 Paymoth, E 722 Vary Ubes 680 dataio Component Specialist 730 Poemax TV Whotesale 716 Por V 735 Stemple Service 722 Por V 735 Stemple Service 722 Adaio Component Specialist 730 Forcer Vales-Service 722 Stemple Service 722 Porder Ltd		
R.C. Spares 728 Aanor Supplies 683 Aapin Electronics Cover II Valuer, Ulrich 738 Auter, Ulrich 738 Multivision 734 Auter, Ulrich 739 J.G. T. Electronics Ltd. 741 storth West Electronics 669 Page Alectronics 669 Paworth, E 732 CT V Services 730 Phoemix TV Whotesale 716 Yough Ltd 728 Gaito Component Specialist 730 Stemple Service 722 May Electronics 680 tadio Component Specialist 730 Foreword Tubes Ltd 727 May Electronics 728 ergo TV 735 Stemple Service 722 Autives Ltd 737 My Electronics 738 Group Intervice 738 ergo TV 735 ergo TV 735 ergo TV 736 <t< td=""><td></td><td></td></t<>		
Applin Electronics Cover II Applin Electronics Cover II Autirty of TV9 738 Multivision 734 Autirty Of TV9 738 Multivision 734 Multivision 734 Multivision 734 Multivision 733 Mage Electronics Ltd. 741 forth West Electronics 669 Payworth, E 732 CT V Services 730 Provinty TV Wholesale 716 Orwell, T 725 V. Tubes 680 Addio Component Specialist 730 Mapin Ltd 728 Reind Components 744, Cover III, Cover IV Multeronics 738 Multeronics 738 Multeronics 738 More V Mones Ltd 737 Multeronics 738 Mapin Ltd 728 More V Merson Components 744, Cover III, Cover IV Stervices Nulteronics 738 Gonic V Distribu	L.R.C. Spares	28
Adurtion (TV) 738 Adultr, Ulrich 734 Auter, Ulrich 739 J. G. T. Electronics Ltd. 741 Auter, Ulrich 739 J. G. T. Electronics Ltd. 741 Jorth West Electronics 733 Jmega Electronics 669 Paworth, E. 732 C TV Services 730 Hoenix TV Whotesale 716 Youngh Ltd. 725 Very Types 680 tadio Component Specialist 730 Herwood Tubes Ltd. 737 Berpie Service 722 Herwood Tubes Ltd. 737 Md Electronics 738 Group Jonetts 744, Cover IV, Cover IV, Prevood Tubes Ltd. Herwood Tubes Ltd. 737 Md Electronics 738 Gennical Movisony Systems 742 echnical Advisony Systems 742 echnical Information Services 738 elevideo Services 719 elevideo Services 719 elevideo Services <td>Manor Supplies</td> <td>83 r II</td>	Manor Supplies	83 r II
Auter, Ulrich. 739 J. G. T. Electronics Ltd. 741 Jorth West Electronics 733 Drega Electronics 669 Japworth, E. 732 CT V Services 730 Phoenix TV Whotesale 716 Yorkers 730 Idia Component Specialist 730 Idia Component Specialist 730 Idia Component Specialist 730 Idia Component Specialist 730 Idia Components 744, Cover IV Inervood Tubes Ltd. 737 Multer Components 744, Cover IV Inervood Tubes Ltd. 737 Multer Components 740 Oontr V Distributors 738 Ideprote Ltd. 717 echnical Advisory Systems 742 echnical Advisory Systems 742 elevideo Services 719 elevideo S	Mauritron (TV)	38
Jorth West Electronics 733 Dimega Electronics 669 apworth, E. 732 2°C TV Services 730 To Y Services 730 Virtubes 680 tadio Component Specialist 730 etay Omagh Ltd 728 etay Omagh Ltd 728 etay Components 744, Cover III, Cover IV etay Descrite 737 Must Electronics 718 oright Service 722 etay Components 744, Cover III, Cover IV herwood Tubes Ltd 737 with Electronics 718 oright Services 736 oright Systems 742 echnical Advisory Systems 742 echnical Information Services 738 eleprice Ltd 715 etarders 728 elevideo Services (MI) 726 echnical Information Services 739 elevideo Services (MI) 728 elevideo Services (MI) 728 elevideo Commercial	Muter, Ulrich	39
Image Electronics 669 agworth, E. 732 CT V Services 730 Orboenix TV Whotesale 716 Yowell, T. 725 V Tubes 680 tadio Component Specialist 730 telay Omagh Ltd 728 tepo TV 735 service 722 endiz Component Specialist 730 service 722 endiz Components 744, Cover IIV, Forward Ubes Ltd nervice Service 732 endiz Components 744, Cover IV hervood Tubes Ltd 737 Mc Electronics 718 foric TV Distributors 736 echnical Advisory Systems 742 echnical Advisory Systems 722 idena Mail Order Ltd 728 elevideo Services 719 elevideo Services	N.G.T. Electronics Ltd	41
CV SerVices 730 horenix TV Wholesale 716 Youngh LT 725 Variable 680 telay Omagh Ltd 728 tepo TV 735 semple Service 722 terpo TV 735 semple Service 722 tendy Components 744, Cover IU, Cover IV herwood Tubes Ltd 737 Sonic TV Distributors 736 foring TV Distributors 736 conic TV Distributors 736 trewart of Reading 726 trewart of Reading 727 trigge conclat Intormation Services 738	Omega Electronics 6	69
tadio Component Specialist 730 teay Ornagh Ltd. 728 teay Ornagh Ltd. 728 teay Ornagh Ltd. 735 teay Ornagh Ltd. 735 teap Ornagh Ltd. 735 term to Service 722 tend Components 744, Cover III, Cover IV tend Components 736 tend Components 737 M Electronics 718 toric TV Distributors 736 toric TV Distributors 736 tepervision 717 echnical Advisory Systems 742 echnical Advisory Systems 742 echnical Advisory Systems 728 elevideo Services 719 elevideo Services (NII) 726 elevideo Services (NII) 726 tere W, Trade Stales 722 iden Adl Order Ltd. 728 tere W, Trade Stales 722 ideo and Electronic 730 V Trade Centre 730 V Trade Centre 730 V Trade Stales <td>Papworth, E</td> <td>32</td>	Papworth, E	32
tadio Component Specialist 730 teay Ornagh Ltd. 728 teay Ornagh Ltd. 728 teay Ornagh Ltd. 735 teay Ornagh Ltd. 735 teap Ornagh Ltd. 735 term to Service 722 tend Components 744, Cover III, Cover IV tend Components 736 tend Components 737 M Electronics 718 toric TV Distributors 736 toric TV Distributors 736 tepervision 717 echnical Advisory Systems 742 echnical Advisory Systems 742 echnical Advisory Systems 728 elevideo Services 719 elevideo Services (NII) 726 elevideo Services (NII) 726 tere W, Trade Stales 722 iden Adl Order Ltd. 728 tere W, Trade Stales 722 ideo and Electronic 730 V Trade Centre 730 V Trade Centre 730 V Trade Stales <td>Phoenix TV Wholesale</td> <td>16</td>	Phoenix TV Wholesale	16
tadio Component Specialist 730 teay Ornagh Ltd. 728 teay Ornagh Ltd. 728 teay Ornagh Ltd. 735 teay Ornagh Ltd. 735 teap Ornagh Ltd. 735 term to Service 722 tend Components 744, Cover III, Cover IV tend Components 736 tend Components 737 M Electronics 718 toric TV Distributors 736 toric TV Distributors 736 tepervision 717 echnical Advisory Systems 742 echnical Advisory Systems 742 echnical Advisory Systems 728 elevideo Services 719 elevideo Services (NII) 726 elevideo Services (NII) 726 tere W, Trade Stales 722 iden Adl Order Ltd. 728 tere W, Trade Stales 722 ideo and Electronic 730 V Trade Centre 730 V Trade Centre 730 V Trade Stales <td>PV. Tubes</td> <td>25 80</td>	PV. Tubes	25 80
semple Service 722 sendz Components 744, Cover III, Cover II hervood Tubes Ltd. 737 Mu Electronics 718 sonic TV Distributors 736 cehnical Advisory Systems 742 echnical Advisory Systems 742	Radio Component Specialist	30
semple Service 722 sendz Components 744, Cover III, Cover II hervood Tubes Ltd. 737 Mu Electronics 718 sonic TV Distributors 736 cehnical Advisory Systems 742 echnical Advisory Systems 742	Repo TV	35
herwood Tubes Ltd. 737 WA Electronics 718 conic TV Distributors 736 conic TV Distributors 720 uppervision 717 echnical Advisory Systems 742 echnical Information Services 738 elerace Ltd 715 eleraders 728 elevideo Services 719 elevideo Services (NI) 726 rige Nail Order Ltd 728 rige August 722 idman Mail Order Ltd 728 ree, W., Trade L V. 671 V Virade Sales 722 ideo and Electronic 723 ideo topiay Corporation 723 ideo topiay Corporation 724 rew -Fel 722 isions London 714<	Semple Service	22
Jonic TV Distributors 736 Jony 740 Jouthside TV 726 Jewart of Reading 720 Jupervision 717 echnical Advisory Systems 742 echnical Information Services 738 eleprace Ltd 715 elerdraders 728 elevideo Services 719 elevideo Services (NI) 726 E S.D. Ltd 721 hrifty Spares (Wales) 722 idman Mail Order Ltd 728 etew. V. Trade States 729 ideo Display Corporation 729 ideo and Electronic 732 ideo endon 723 ideo topsay Corporation 721 Yeard State 722 ideo and Electronic 732 ideo topsay Corporation 723 ideo topsay Corporation 721 Yilade State Electronics Ltd 722 Villiams, Dave 732 Villow Vale Electronics Ltd 723 Villow Vale Electronics Ltd	Sherwood Tubes Ltd. 7	37
Journs de IV. 726 Jupervision 720 Jupervision 717 echnical Advisory Systems 742 echnical Advisory Systems 748 eleprice Ltd. 715 elevideo Services 718 elevideo Services 719 E S D. Ltd 721 hrifty Spares (Wales) 722 idman Mail Order Ltd 728 ree, W. Trade T V 671 V Trade Commercial 734 V Y Trade Centre 730 V Trade Sales 722 ideo and Electronic. 732 ideo elevideo 711 Vest Midlands TV & Video 671 Villiarws, Dave 732 Vizard Distributors 732	Sonic TV Distributors	36
itewart of Reading 720 uppervision 717 echnical Advisory Systems 742 echnical Information Services 738 eleprice Ltd 715 eletraders 728 elevideo Services 719 elevideo Services 719 elevideo Services 719 elevideo Services (NI) 726 ree, V. If crease (Wales) 722 idman Mail Order Ltd 728 ree, W., If rade T. V. 671 V Kideo Commercial 734 V Trade Centre 730 V Trade Sales 722 ideo and Electronic 723 ideo topshay Corporation 723 ideo topshay Corporation 724 Viet Midlands TV & Video 671 Villiow Vale Electronics Ltd. 729 Vizard Distributors 732	outhside (V	26
echnical Advisory Systems 742 echnical Information Services 738 eleprice L1d 715 eletraders 729 eletraders 729 eletraders 729 elevideo-Services 719 pier-Video-Services (NI) 726 F. S. D. Ltd. 721 hrith's Sparse (Wales) 722 idman Mail Order Ltd 728 ree, W., Trade T.V. 671 V Trade Centre 730 V Trade Centre 730 V Trade Sales 722 ideo and Electronic. 732 ideo end Electronic. 723 ideotech 726 isions London 714 Vest Midlands TV & Video 671 Villiarns, Dave 732 Villow Vale Electronics Ltd. 729 Vizard Distributors 732	tewart of Reading 74 Supervision 77	20 17
eleptical 715 eletraders 728 elevideo Services 719 elevideo Services 719 elevideo Services 721 hrifty Spares (Wales) 722 diman Mail Order Ltd 728 ree, W., Trade T, V. 671 V & Video Commercial 734 V Trade Sales 722 ideo and Electronic 732 ideo Lopiay Corporation 723 ideolech 726 isions London 714 vest Midlands TV & Video 671 Villow Vale Electronics 732 villooton 723 ideologiay Corporation 723 villooton 714 vest Midlands TV & Video 671 villow Vale Electronics Ltd. 729 villow Vale Electronics Ltd. 729	Fechnical Advisory Systems	42
eletraders 728 eletvideo Services 719 elevideo-Services (NI) 726 F. S. D. Ltd. 721 hrithy Spares (Wales) 722 idman Mail Order Ltd. 728 ree, W., Trade T.V. 671 V Trade Commercial 734 V Trade Centre 730 V Trade Sees 722 ideo and Electronic. 732 ideo end Electronic 723 ideotech 726 iew-Tel 722 isions London 714 Vest Midlands TV & Video 671 Villiams, Dave 732 Villow Vale Electronics. Ltd. 729 Varad Distributors 732	eleprice Ltd	15
ele Video-Services (NI) 726 E S D. Lid. 721 hrifty Spares (Wales) 722 idman Mail Order Ltd. 728 ree, W., Trade T V. 671 V Trade Commercial 734 V Trade Cantre. 730 V Trade Sales 722 ideo Display Corporation. 733 ideotech 725 ideotech 725 ideotech 726 Vest Midlands TV & Video 671 Villiawa, Dave 732 Vizad Distributors 732	elevideo Services 72	28
Idee w, Irade T, V. b7 Visca Wa Video Commercial 734 Virade Centre 730 732 Virade Sales 722 732 ideo and Electronic 732 733 virade Sales 722 732 ideo and Electronic 732 732 ideo tech 726 726 isions London 714 714 vest Midlands TV & Video 671 732 Viliow Vale Electronics Ltd. 729 732 Vizard Distributors 732 732	ele-Video-Services (NI) 72	26
Idee w, Irade T, V. b7 Visca Wa Video Commercial 734 Virade Centre 730 732 Virade Sales 722 732 ideo and Electronic 732 733 virade Sales 722 732 ideo and Electronic 732 732 ideo tech 726 726 isions London 714 714 vest Midlands TV & Video 671 732 Viliow Vale Electronics Ltd. 729 732 Vizard Distributors 732 732	hrifty Spares (Wales)	22
V rade centre 730 V rade centre 730 V rade centre 731 v rade sales 722 ideo and Electronic 732 ideo Lipsilay Corporation 723 ideolech 726 isions London 714 vest Midlands TV & Video 671 Villiams, Dave 732 Villow Vale Electronics Ltd. 729 Vizard Distributors 732	ree, W., Trade T.V. 67	71
ideo and Electronic 732 ideo Display Corporation 723 ideotech 726 isons London 721 isons London 714 Vest Midlands TV & Video 671 Villiams, Dave 732 Villiams, Dave 732 Vizard Distributors 732	V & Video Commercial	34 30
Ideo Lisplay Corporation 723 Ideolech 726 Isons London 714 Vest Midlands TV & Video 671 Villiams, Dave 732 Villow Vale Electronics Ltd. 729 Vizard Distributors 732	V Trade Sales 72	22
Ideotecn /2b Ideotecn /2b Isions London 714 Vest Midlands TV & Video 671 Villiams, Dave 732 Villow Vale Electronics Ltd 729 Vizard Distributors 732	(Ideo Lisplay Corporation	13
Vest Midlands TV & Video 671 Villiams, Dave 732 Villow Vale Electronics Ltd 729 Vizard Distributors 732	Ideotech	2b
Villams, Dave 732 Villow Vale Electronics Ltd. 729 Vizard Distributors 732	/isions London71	14
Vizaru Distributors	Vest Midlands TV & Video 67 Villiams, Dave 72	71
	Nilow Vale Electronics Ltd. 72	29
oneport 716		





TELEVISION JULY 1990

							-
SPECIAL OF	FEF	?]	THI	<u>S M</u>	0	NT	Н
UNIVERSAL TRIPLER. NEW TYPE VIDEO LEADS	£	64.00 .80m	PHILIPS HIGH GR		£2.50	THORN FRA	
AMSTRADLine O. P. Transistors with Diode 2SD/453	£	EI.00	PH. V200	ILIPS TAPES	£6	IC TDA.	52
BU206A		. 240	V200240		£6.50	REPLACEM	IENT
HTTACHL& GEC FRAME, Thick Film			VCC360		£7.50	TDA3654 £	2.00
K30 FRONT PANEL TEL-TEX TYPE NEW G11 LINE OP PANEL		ພ.00 k	THORN TX85 CHAS	SSIS			£15
PHILIPS VEARS AHEAD			Late TX100 Thorn H	land Set Pads Mixed	Fast-Text	and Non-Text	or 5 for £4
THE CREDIT CARD CALCULATOR Solar Powered		L8.00	TX100 Manuals			LI CACI	£1 ench
THORN PANEL TX9 REC & REMOTE PANELS with Mains Trans TX10 REC & REMOTE PANELS with Mains Trans	£	E5.00					NEW
TX100 FRONT PANEL TX10 TUBE BASE ON PANEL	£	E5.00	DC and AC and Re	AUTO RANGI sistance Pocket 300		£12.00	PHILIPS
TX9 IF	£	E2.00	GI1 8 Touch Button	n with Lamps, Non-	remote	£18.00	6 Touch Unit
THORN TX STEREO SOUND O.P. PANEL (I.C. TA7227P)	£	E1.00	Philips New Hand S Text Sets after G11		it all	£12.50	£12.50
THORN VIDEO AERIAL AMP 01 M4-597-001	CV	C 40 Cabin	ets	-	£10.00	TV AERIAL/VIDEO	
G8 LOPTS PHILIPS \$6.00 SBC3140	£5.00 NE	W IN = H	T BOXES			Combiner Switch and S	ockets 50p
GH LOPTS £3.00 Philips Stereo Head	Phone	_	FORMER Philips TX 12" ONES Key Pad and Hand		£12.00	Lead	Sub
PHILIPS DESK TYPE Dual Power Calculator SBC1704 17.00 Philips SBC3050 Stereo O Microphone Microphone	Condenser Electric		VERSAL BATTERY TES		65.00	THORN RECEIVER P	NE
K40 FOCUS POT £1.00 Μικτορποια 4.7μ KT3 W/W 10 for £1.00 Philips SBC3040 Mono U		IORN 8500	LOPT		£2:00	564/314	
FOCUS POT HDK TPA6006 £2.00 Condenser Microphone		W GEC 21	10 LOPT			564/323 M293B1	
KT3 Triplers K3 Tex Front Panels with I.C.s (SAA3027P/SAB3013/		UNER V	HF-UHF SEND FOR D	АТА	50p	M293B1 SAA5012 £6 HCF4556BE	
HO448328) £5.00 G8 100K Pots on Panel & Lead for 6 Push Button Unit £2.00			WER SUPPLY Mark 2		£10.00	MC14493P	
K35 Mains Switch remote 75p PANE K35 Aerial Socket and Plug in Lead to Tuner £1.50 PANE	L £5 TH	IORN 9000			-40p	TX100	
KT3-K30 Slider Pots 4.7ku 20p each WITH K	100	TUNER V	/CAP on Panel		£3.50		
LARGE Foacs Pots. Fits Pye, GEC, ITT, Decca 8 PUSH BUTTON UNIT for CTX Chassis 1.50		SPEAKER				THORN RECEIVER P. 564/314	ANELS
G8 Power Supply Panel £4.00 PHILIPS NEV		00 SPEAK			£1.00	544/301 544/321	
EX DEC CA 80-100 Frame 25.00 U/V HAND S THORN 8000-8590-8800 Decoder 26.00 U/V HAND S		NE LC K35	Sound OP Panel		£30p £7.00	544/341	
GLASS BEADS Diodes 200v/1.2A G11 Tip Switch £20.00	30 101 11.00	40 IF/K35 II			£5.00	SAA1060 MAB8440P	
G11 IF Panel £8.00 NEW	TH	IORN Lopt	8500-8800		£4.00	SAB3035	£6.0 <mark>0</mark>
		9 THORN	Tuner Panel with ICS Pot	s & mains trans.	£3.00		
G9 Power Panel G8 Transductor f1.25 G8 Transductor f1.25 G8 Push Bauton Unit			Rec- & Anode Cap		50p	BRIDGES RECTIFIER	
G8 Con/Panel New Back Type £4.00 IVIIACD - 210 FOR		F3-K30 Slide		£1.	6p each	BR-31 50V 2Amp	for £1.00
KT4-KT3-K30 Handset Replacement £12.00 HT520 METER 20,000 Fuse Diode Protector Logic Test Facility £15.90 HT420 £12.00		_	GEC 20k Pots and 100K a	and 69K Philips 20	for £1.00		
9000 SERIES Decoder 01 929 014 080 Thorn £5.00			20K v/cap type with band		5p	TX90 MOD 37141B	
LATEST VIDEO For Latest Philips, GEC. Pye and Hitachi. Front panel with memory chip and push button. LED's.	and pots and KI	13 K.30 Spe	aker		30p	The Sweep Tuning Syst	
LED's. 20AX GEC LOPT Panel with Split Diode \$4.00	R.J		ton Switch 6 Way		£1.00	TX9 139/001	£5.00
20AX GEC LOPT Panel with Split Diode \$4.00 RANK 120 Fouces Pot 75p RANK 718 Fouss Pot \$1.00 16' LOPT Split Diode 2433481 \$6.00 75 \$6.00			P Panel Plug in and KT3 ush Button Unit	sound o/p	£3.00 £1.50	THE THE THE T	C1.00
	NEL £5		Unit. New Type		£2.00	T6070V TX9 Transistor TX9 90D4-106-004	£1.00
Split Diode 2433523 Each Index Mit Focus Pots and Diode 22.00 8 T703A LOPT Transformer Rank with Focus Pots and Diode 22.00 8 HITACHI Mains Switch 50p	Dutton -		SPLAYS, Mixed		£1.00	TX9 90D4-099-001 Chopper Transformer	£1.00 £1.00
HITACHI Mains Switch 30p	±±A	AND SET T	ESTER, Infra Red		£3.00	TX9 06D4-025-001 cho TX9 90D4-093-001-01G	
1 CONDENSER Axail Leads 450 A/C 1200 D/C 15p		_	ITTER with filter		00.13		
MAINS TRANSFORMER 240v in/20v/8v £1.00 GREEN FLAT, NEC, LED's 3p each 100 for £2			IONAL Dynamic Microph	hone	£2.00	20MM IAmp A5 Fuse	
15V015V 1 Amp Print Type fl			TS with Band Switch ON Mains Switch with Scr	ew Holes Fixing	10p 4 for £1	£3.	00 per 190
8+8V 1 Amp Print 75p		VE 731 Line		controns riving	£3.50		
ET596 UHF VICAP Tuner, small f2.59 FIDELITY Panels with I.C. AT2076/80 f1.00 FIDELITY LOPT Split Diode AT2076/80 f1.00 DEUX DOC DUIN DOC AT2076/80	LATOR PY		Power Supply		£4.00	TX90 TX925 TX100 Mains Switch with Star	vietw
AT 2076/80 1111111 5 4			at 3 amps. Glass Beads	6p each, 20		and Lead	
ITT CVC20 to 45 PANELS Send for list MULLARD TEL-TEX DECODER Type VM6103		T3 Line Ou HORN 8500	tput Transformer		£5.00 £3.00	3 for £1 o	r 50p each
WE HAVE OVER 1,000 6 DIODE TRIPLER AT \$1 EACH	7.5		AYS 4 Bank Displays Z-	6042T	25p		
THORN main T/V chassis complete TX90-TX925 and TX90.20"			E FBS1245AR		£5.00	UNIVERSAL VIDEO	
TX900 with PRR-SR7 £6.00		_	ANEL PC895A7 IST OF VIDEO SPARES	£13 to £4	£10 6 HEADS	Mono 11 Piece Kit Stereo 14 Piece Kit	£8.00 £8.00
PHILIPS VHS Tape 180 £2.25 2432871 TX100 Green Spot CTK Lopi CTK Lopi				AT2036/00 A1	2076/55 2076/71T	SHARP MSHIFCF09	
2432301 TX100 Blue Spot £15 24353016 TX 100 Yellow Spot 2433952 L.00.P.T. 10.00 CDI IT DIADE 30072			ANSFORMERS	AT2055 A1	20/6/11 2080/15 O ST CT3325	TX9 LOPT	
2434393 TX90 White Spot SPLII-DIUDE 36362	L.O.P.T.	3[12-	338-30633 £1.00	AT2076/38 01	2041 165KA Orion		
T9048A Split Diode 110° £12.50 £10 EACH 36482 S	PLIT DIODE		268-30050 £1.00 138-98094 £1.00	CVC 820 207	6/51 12461 2433451		4-235 -01
K4 L.O.P.T. 36831 36832	PHILIPS		338-30634 £2.00 138-96044 £1.00	REGULATED POWER	SUPPLY,	VIDEO MOTOR for VT56	s type
K40 TX9 L.O.P.T. 36833 3692179	£10 EACH	3122-	138-53861 £1.00 138-98094 £1.75	Size 6"×5"×2 ¹ /2". 0-3v - lamp. Pre-sel 3v-to-12 v amp. £5.0		AMP TUNER IF for VT568	£8.00 3 Hitachi £9.00
		1					
CMR 800/3 £20.00 SENO FOR DATA 20 AM	P COST OVER £400.	30 VOLT	TO 15 VOLTS FARNE	LL POWER SUPPLY	19" RACK M	IOUNT POST 28, IN	CASE £20
and Frame \$5.00 DIL - DIL	12	2V/1 AMP	POWER SUPPLY WIT	H MAINS PLUG £4			
din with an av cocket ITHE vigan 42 Pin X 5 13.00	S HALOGEN LIGHT. N	NEW. NO	on/off switch, no sion modulator a	T V /RE 25-1000	J. BLACK IN	TRANSMITTER CP OF	00
Can be adapted for video 16 Pin × 10 70p	1 OFF - BOI	HDE & SC	HWARZ EKFZ T.V. M	ONITORING RECEIVE	R £1,200		
TTT PANEL 24 Pin x 5 14 Pin x 10 75p 10p CMC 301 CMC 13 CMC 302 RPin x 10 80p CMC 105 CMC 304 Geo 4964 T	VR3 Amstrad oshiba V-81F	Casse Casse	tte Mechanisr tte Mechanisr	ns. New £35 ns. New £35	with hea with hea	ads.	
<u>£5.00</u> CMR 800 DiL - QiL DiL - QiL SENDZ C	strad Televisi	ion Tu 63 BIS	ner UHF. Sma HOPSTEIGNT(II. Fits most / ON, SHOEBUR	mstrad	<u>s. £6.</u>	AF.
if or m > 10 if or m > 10 if or m > 10 28 Pin x 4 28 Pin x 4 100 SEL ITT AB Mains Switch AB Mains Switch IfB254Pi2 Front Panel u/v 30p	s sub ject to availab	S bility. No	AME DAY SER Accounts: No Credit en £1 Postage. Add	VICE t Cards. Postal Ord	ler/Cheque		
EI5.00 DECCA - GEC - ITT 6 miles button - £5.00 212	LONDON ROA	AD, SO	Callers: To sho UTHEN. Tel. 07	p at 02-332992. Fa	x 0702 3	338805	
100 BC-BF Transistor £1.00 N6315 £10 Open 9-12/2.:	30-6. GVMT + sc	chool ord	ers accepted on o	fficial headings. A	add 10% /	nandling charge.	

ų

SEND7		Voltage Regulators +5V/UA78PO5SC 3	CV 8017		
SENDZ o	OMPONENTS	-8V/79M08c +6V/78M06c	μ Υ 716 μ Υ 729 μ Υ 730	10p 30p	
TO ORDER	SEE BACK PAGE	LM 3171 LM 337	μρ (±7.50) δμρ (¥ 827:6Α/1ΚV μρ (¥ 860)	10р 20р 30р	MAB 8420P-C031 £3.00 MAB 8400B-6 £3.00 MAB 8400P-D070 £3.00
	€1 K35 Decoder €8.0 K35 Sound OP €4.0 Thick Film Daughter KT3 3122-127-4389	LM 3401 5.0 5	Гр Y 933 Гр Y 969 Гр X 969	5p 50p	MAB 8440P-D033 £3.00 MAB 8440P-D056 £3.00
11A 411485	9p E1 12 C.H. K30 Tex Rec Front Panel with LC. E2	3 +18V/MC78M18 +24V/78M24	p Min 12 volt Relays	30p 75p	MAB 8441P-F132 €2.00
M58657P M491BB1	£1 K35 1F £5.0	· · · · · · · · · · · · · · · · · · ·	P R 1038 P R 1039 R 2009	40p 40p	M58484P £2.00 Hand Sets — Fidelity £15.00 (a £35.00
M50441/550	El K4 Focus Por EL.00	118 92 2	P R 20106	80p £1	Philip New A/V Hand Set £10
Receiver TX100 Panel LC, No. SAB3035	Fidelity Tube Base with transitor & focus pot £1.50		P R 2210 R 2257	50p 60p 60p	ITT 8 and 6 Phish Button £1.00 Pyc 725 LOPTs £6.00 Pyc 731 LOPTs £6.00
	E6 Bush Tube Base on panel £1.00	U 3832	P R 2265	50p 50p	Thora 8500-8800 LOPTs £5.00 CMC 301 front page1 £5.00
New Model Philips Meter £25.6	TX10 Tube Base on Panel £3.00 F100 L.O.P.T. Green Spot	MR 508 MR 501 MR 502	P R 2322/2323	30p pair 80p	CMC 303 front panel €5.00 CMC 302 Panel with TC mains switch
	25 TX100 Thorn	BCW 71R 30 BYF 1202 10	P R 2396	15p 50p	CMD 800 Decoder £8.00
	Line Transformers 5 G8 Lopt £5.00		P R 2030 P 2132-PD121	80p 50p	C7 Hand Set £6.00
4 Types Fidelity from panels with i.e & pats £2 eac	6 Diode Tripler, Mullard 75p	BYX 36/600 35	P R 2540	30p £2 40p	3.1 C. Power Supply G11 Full Remote Receiver Panel £3,00
BB 103 BB 105A×12	P 27482 £10	BYX 49/600R 75 BYX 55/350 H	R 2738=T1P41	30p 40p	Meters Hills 520 £17,00 Meters Hills 420 £10,00 Hills HD5000 Digital Meter 1000V DC
BB 105B×12 BB 105G×12 BB 105G×12	1 10273 £10 1 Thorn 1090 LOPT £7,50	BYX 55/600 (Bead) 10 BYX 71/350 20 BYX 71/600 56	P R 4050	40p £1	756AC 10 Amp 20 MRG Rangers £28
BB 121a 10 47 10p cac		BYX 72/300 20 BYX 36/600 50	2SD898B	80p £1	ITT100 Multimeter £6.75 ITT300 Multimeter £7.75 ITT500 Multimeter £9.00
LA/1600V 10 DG3P EQV-BY228 10 for £	p CVC820 Split Diode IFT £10.00 1 Thorn B/W ∧D5308F + Stik +	BYV 95B 10 BYV 95C 12 BYV 96D 10	5	£I	117700 £15.00 11D1000 Digital €20.00 11D1200 Low Cost Digital €13.00
2 amp bridge rec. wire end 15 SKE4G2/02 15 Eqv. BYX71/600 500ns,	P GEC 2110 £7.00	BYZ 106 10 BPW 41 15 BYW 56 2A/1000v G11 8	 STR454 STR6020 	£2 Ki) £6	H122500 €18.00 H133000 Digital €25.00 H125500 Digital €29.00
Thorn Spares	Mullard AT 2036 £1.50 Pyc 169 Line Trans £3.00 Pyc mono £3.00	BYW 29/50 15 BYW 95C 10	2SC940 BLU05/01	£1 £1 800	11D0000 Digital £32.00 11D8000 Digital £35.00 11D9500 Digital with canacity Temp
New 9000 Decoder £8.5 9000 Frame panel £	0 Rank mono 1704A £3.50 8 Split Diode Trans £7.00	BZY 93c75 50 BZW 15/18 30	BU 108 BU 124	80p £1 50p	Trans Volts Ohms and Amps ranges (60) Infra Red
3 Way regulated adaptor 240V 6V/ 7.5/9V/300mA £3.5	Rank L.O.P.T. 2970 £3.00 0 CVC800 Line Trans £6.00	BZW 15/30 BZW 70c6v2 BZX 79.3v 10	BU 126 BU 180a	80p 65p	Hanset Tester Works at 24 feet – Sound repeater. Works off 9 volt battery £8.(8)
Rauk Toshiba preh unit 0354 £9.5 4 Push button unit preh £1.0 6 Push button VHF/UHF for		Bush Ibyristor RCA 76122	BU 205 BU 206	60p 75p £1	Fits in top pocket.
v/cap. GEC-Decea type £7.00 7 Push button for CVC5 FIT £8.40	GEC Portable GIOT2046 €3,00 EHT Split Diode Leads ITT €1,00	Transformer 240v/20v-500Ma 75 Chassis type Transformer	BU 207 BU 208	£1 80p	Repaired Handsets Philips K4-R35, RC5350-RC5360, RC5370, RC5375, repaired some day £60,00
KT3 12 Push button unit KT3 (Export) 12 P B.u 6 Push button Unit Thorn £1.00	2 LOPT Rank Z/63 £5.00	240v/12 Volts 500m/a 75 CVC 20 tube base £ Tube Base Rank & G11 £1.20	BU 208D	75p 90p £1	RC5370, RC5375, repaired some day EE0.00 RC4001 Full Remote KT3 K30 Teletext
6 Push button GRC £6.06 6 Push button PYE 731 £6.00	with small focus not. Green toxy 67 no.	Infra red led LD57CA 15	BU 326 BU 407	£1	Handsets exchanged £15.00
Hearing aid unit £3.00 Rank Z718 4 P/B/Unit MECH £4.00 7 Button Unit GEC with Lamps £7.00	KT3 Triplers £6.00	15K-20 turn pots 20 Thorn 3500 2A cut out 50	BU 500	45p £1.10	NEW Type RC4001.9 CH not 12 £6.00 GEC Full Remote Infrasred, 1983 models
697 Push Button Unit £6.00 Z916B panel £5 00	£2.50	BRIDGES KBL 005 30p	BU 500D BU 508A BU 508V	£1 90ρ €1	EI5.00 TOSIUBA HAND SETS
T513AP panel £5.00 Video Tuner		KBL 02 300 KBP 64 300 W02 15p	BU 705 BU 806A	£1	CT9485 £4,00 CT9476 £4,00 CT9433 £4,00
V.6100/05 T/V and Tel/Text unit and	TU 25.30K Rank £3.00 11 TEZ Rank £3.00	W004 15p W005 20p	BU 807 BU 824 BUT 11	Sob L	Rediffusion MK3 £5.00
hand set £50.00 Send for data.	GEC 2110 £4,00 3500 Thorn £3.00	S00V Bridges 252 Amp 30p G11 drawer ASS 3 pots Mains switch and	BUT13 600V 28A BUW II	50p £1 50p	TOSHIBA HAND SETS 24 Button (T1938 Fuliremote £5,00
TT14 GEC TEX-DECODER 13 IC Panel with cable form £9.50	\$500 Thorn £4.00 9000 Thorn £7.00	Lead £2.00	BUW 84 BYW 20-08-9	60p £1	32 Button C1983 Videotext £6.00 THORN
PHILIPS Decoder SAA IC 5020-5030	9000 Thom £4.00 2040 GFC £3.59	K30 Drawer Ass with pots cable forme £1.00	BYW 95 BUX39 25A-150V BUX84	£I	VCR Front Display Panel £7.00 Large type FTT TV and V.C.R
5040B-5050 K40 Text Panel 68.00	GEC TVM25 Tripler E2.00 Universal Tripler E5.00 G8 Tripler E5.00	TX10 Drawer with 8 way pots, ass. £2.50 TX10 Ex. port with hand switch (drawer)	BUX85 BUY49	50p	Handset £15.00 GEC Ultrasonic 8CI1 Full Remote £10.00
6F-425	CVC20-32 Decca 80 100 £4.50	and U.H.F. only £2.50	TIC 106a TIC 116m	30p	G11 Full Remote Ultrasonic £32.00 G11 Ultrasonic Teletext Handser £20.00
OF-550 E.W. 10p OF-513 correction 10p		Hills Meter for the car man, volts, samp, ohm with dwell and r.p.m. £35,00	11C 116n/Y 1003 T1C 126N T1C 225S	3000	S C.H. Ultrasonic GEC Full Remote C201411/C221911 £15,00 New Replacement for G11 Ultrasonic
OF-557 50p DIODES	D22 for Pyc 18" colour portable £4.00 LP 1193/63 £4.00 BG 100/41 £3.25	Hills 9 piece tool kit in case £5.00	TIC 226E TIC 226m	30p 30p	Full Remote £12.00 Thorn 4000 insert with 7 buttons £5.00 Decca RC 11 £14 00
Bridge KBF-08 40p BY 126 H0p	ERO Tripler print type with foaes PO7 BG2087 E5	Abbey Security Smoke Alarm Model 101 £4.00	TIC 236m TAG 226/600 TICV 106D	30p 1 30p 4	Decca RC 12 £14.00 GFU Infra-red full reletext £20.00 Dynatron-Full remote CTV 62, 63, 64
BY 133 10p BY 134 10p	Thext ultrasonic rec'r panel £14.00 12-14V. 20 for £5.00 200 for £25.00 GEC 8 touch unit assy complete with all	Self adjusting cutter stripper £5.00	(11092 case 2A/400V) TTP 29	10p 1	E19,00 E18,00 Philips full remote KT3, 16C928(20C934) 228/7324: K12 26C 797/18T-66K
BY 176 25p BY 179 40p BY 184 25p	LC.'s + pots £4.90 G11 E.W. Transformer 50p G11 E.W. coils £1.00	10 mixed tube bars £4.00	TIP 30 TIP 30A TIP 30B	25p	826 £12.00 311. Full remote top button assy. £12.00
BY 187 10p BY 190 40p	G11 Transient Suppressors 245V 20p G11 Scan Coils £5,00	5000 Diodes-Resistors £3 park	TIP 30C TIP 31	25p	H1. Full remote repair service (exchange mit) EC infra red full remote 8 channel LCSAA1250) €14.00
BY 196 30p BY 198 10p BY 204/4 80	G11 100K taner pots 12 for £1 K13 IF panel £6.00 K13 line OSC transformer £1	T/V V/Acrial 30802 or 7502 £1.50 * D/P push mains switch 20p each	TTP 32 TTP 33B TTP 33C	50p P	Philips infra red full remote 9 channel for 0 CP2605 £6.00
BY 206 - BY 407 Eqv. 8p BY 208/800 8p	K 1'3/K30 infla-red-receiver head £k K30 drawer unit with IC's	Mains lead & two pin socket for radio	TTP 34A TTP 34B	70p p 50p h 60p K	Philips intra red full remote 12 channel or 60 CP2605 £12.00
BY 210/400 5p BY 210/800 10p BY 223 60p	(home) £10 K30 drawer unit with IC's	cassette 35p	TIP 34C TIP 35B TIP 35C	70p	CT3/K30/17/Fest £12.50
BY 224/600: 4.8A/600v bridge 50p BY 226 15p	(export) £10 K13 AE Sockets 50p K13 receiver panel £8	I/V loop aerial 75p Radio Telescopic Aerial €1.00	TIP 35C TIP 35D TIP 36	oopte	113 Power supply £4,00 U-C infra-red 2236-2026 £4,00 U-C infra-red 2236-2026 £14,00 U-C wish paid handset button blobs 10p
BY 228 1500v 20p Flat BY 229 black 15p	KT3 line driver transformer 50p Pyc, K30, GEC, etc. Pre-mains stand-by switch £1	Philips Silicon Grease £1.50	- 3'1P-36C T'1P-4	70p P 15p N	ach ve & Philips handset KT3-K30 chassis. lo RC5150-RC5176-RC5171-RC5177
BY 299 Red 20p BY 229/400 30p	Decea 80/100 IF panel £5 NPN PNP 80V 6 Amp TO66 O.P.	Freeze Philips £1.15	TIP 41B 31P 41D TIP 42	70p R	CHOOL KT3 and Teletex £13.00 ECHOOL KT3 and Teletex £14.00 E CVC 32 buncher required £15.00
BY 299/60p Tag 30p BY 237 5p BY 254 10p	Trans. pair 25p 5 button touch tuner BBC1/2 ITV1/2 video with ic SAS 5601/57017 £7,00	Foam Cleaner Philips €1.15	TTP 42/BRC 6109 TTP 48	10p C	VC 32 Hand Set £15.00 VC 45 3 and 2 Pin
BY 255 30p BY 298 10p	Control panel 5 sliders + mains fead £1.50 G11 8 touch batton unit replaces old 6 P.B.U. £24	Contact Cleaner Philips £1.15	TIP 49 TIP 57 TIP 100	30p T 30p T	λ9 with Text £12.50 λ9 & TX10 button print £2.00
BY 406 8p BY 527 200	Tube base + base unit for 820 Euro chassis £4.00	100 Coax Plugs £12.00	11P 102 11P 102 11P 110	30p 20p T	X III Focus Pots £5.50 FIT /V & Video Processor, 1200 Type €10.001
BY 407a 10p BY 448 10p	GEC Line O/P Trans. & Rec Stick for Portable £3.00 CVC 20/25/30/35/40 decoder panel £10	De-solder pump + 2 aozzies Philips £4.00 Flat Red LED and Green 5p	TIP 115 TIP 117	50p 50p	PHILIPS UNIVERSAL HAND SET €12.00 RC5
BY 527 10p BY 602 10p	CVC 20/25/30/35/40 decoder panel (untested) <u>£5</u> CVC 40/45 IF panel <u>£5</u>	500gm 00/40 solder reel £6	TIP 125 TIP 126 TIP 127	400	KT3 ~ K45 We have all parts for Philips Handsets
BYV 26C 10p F 247 10p	40K Transducer 50p PHILDPS NE511N £1.20	Dual v/u meter $-20 - \pm 10$ db EI	TIP 130 TIP 131	30p R	C5353 £15.00 C5300 £12.00
GRP80G (TX10) 30p XK 3102 50o	LM337M Reg. 30p 20 GEC Black Spark Gaps £1.00 KT3 Front Panel Control	K30 thermistor 232206298000 75p	TTP 136 TTP 140 TTP 142	30p PI 50p	hilips RC5 £15.00
BYV 28/200 20p Bridge TX10 800/3 amps 30p	Assy. £2.50 BTW 30/50 50p	De-solder Pump £2.50	TIP 640 TIP 2955	80p 50p Pi 35p	Replace Hand Set for hilips KT3-K30, K4 etc £12.30
KBPC35-02 Bridge £1.50 Bridge Rec. D35B10 40p		Portasol Flameless Gas Soldering Iron£16.00	TIP L761A-1000V/4Amp T 6032	75p 30p T	THORN HAND SETS 9000 - 9600 - TX9 - TX10 - TX100 ext and Non-Text - €10,00
	BTW 92/800R 3	Green & Red, LED pack mixed100 for £1.00	T 6036 T 6040 T 6047	40p 40n	PHILIPS C5171 E12.00
	35 4 (33 050) (10)	Hill Meter Leads, S/Rubber and Probes £4.00	T 6049 T 6051	40p 40p 40p	K35-K4 HAND SET Repaired for £5.00
		· · · · ·			

TELEVISION JUNE 1990

Tuner Units TX90-TX100 Tuners with E socket £5.00	SENDZ COMPONENTS	ML 926 €1.00 1 MAB\$400B-C £2.00	ТВА625 50р ТВА051 £2.00 ТВА673 £1.00	TDA2575A £1.00 TDA2577A £2.00 TDA2578A £2.00
Thorn TX Tuner V/Cap eqv.to ELC1043 E4.50 Min. UHF Tuner 40dB gain 2"×1/2"×1/2" £1.50	63 Bishopsteignton,	MABS40 P-D070 €2.00 MABS40 P1001 €3.00 MABS420PC035 €2.00	113А750Q £1.50 1136А750) £1.50 1136А780 £1.50 ТВА810 50р ТВА810АР 60р	TDA2579A £2.00 TDA2581 £2.00 TDA2591 £1.00 TDA2593 £3.00
VHP-UHF with Data Tuner MECT-FST 63 F400 Family with Data Mosfet Thorn TX10 Export V/Cap UHF, VHF63	SAME DAY SERVICE All items subject to availability. Technical Information by telephone only. No Accounts : No Credit Cards	MAB8440P £2.00 MAR8400XX £3.00 M708LB1 £2.00	TBA8108 60p TBA820 60p TBA820M 25p	TDA2560 50p 1 DA2556 £1.50 TDA2600 £5.75
V/Cap Rank UHI Z776T/Unit 66 V/Cap Rank VHF Z773T/Unit 65 NEW G8 Tungt V/Cap 63.50 T20.6 Push Butten Unit 67	Postal Order/Cheque with order Add 15% VAT, then £1 Postage	MM5387 £1.00 MM561 £1.00 MM5840 £3.00	TBA920 £1.50 TBA920Q £1.50 TBA990Q £1.00	TDA2611A £1.00 TDA2611AQ £1.00 TDA3651A £1.00
ELC2000 on Panel £2.50 GEC 2110 V/Cap £5 FE618Q £20.00	Add Postage for overseas Callers: To shop at 212 London Rd., Southend. Tel. 0702 332992. Fax 0702 338805	K35 Philips Receiver IC MA1250 BJC £3.00	TMS1000NL £2.00 TMS1943 N2L (clockchip) £1.00 TMS9980 £4.00	TDA3652 £2.50 TDA2653 £4.00 TDA2650 £2.100 TDA2650 £2.100
ELC1042 NEW 66.00 ELC1043 (Ex Panel) 63.75 ELC2000 NEW 64.00	Open 9-1/2.30-6, GVMT + school orders accepted on oncian headings add 10% handling charge.	M \$40A 84 £5.00 M \$8400 1-84 £5.00 1 MM 5290N-4 75p	TMS9901 €1.00 TMS27083G45 45p TMS2716J1. €1.90	「口入2690」 £1.00 「口入2593 £1.00 「口入3647 £1.00
ELC2004 NEW 08.00 ELC2003 64.00 ELC2006 NEW 04.00 GRC Tumor V Con Hitschi Alter	Astec UM1623 VHF £2.00 BD646 50p Astec UM1286 £4.00 BD676A 30p BD877 20p BD826 50p	MM53108N £4 MN1250BJC £2 MR1366 20p	TMS3529 £1.00 TMS3720ANS £3.00 TMS4014 70p	TDA3048 £3.00 TDA3083 £2.00 TDA3190 £1.00
GEC Tuner V/Cap Hitachi Alter 1979 ETS48, ETS47, ETS41B EX.00 ETS46 66.00 ET546 UEIF Tuner	Modulators with Data BD933 30p UHF Modulator CCIR £3.00 BD934 30p	N641001 £1.00 NE555P 60p NE555 60p	TX-012 £1.00 TMS9902 £1.20 ULN2004P £1.50 ULN2216 75p	TDA300B £5.00 TDA301B £4.00 TDA3505 £3.00 TDA3505 £3.00
ET566P UDF Very Small £2.50 ET598P VHP/UHF Very Small £5.00 UHF, ET566P, small £6.00	UHF/VHF Tuner EGG13F £6.00 BDX75 20p FNV-57465G2 VHF/UHF £5.00 BDX64B 50p	NE640 50p HD38980C £3.00 Hd 20p	UPC566F1 EE.00 UPC585C EE.00 UPC1009C E2.00	TDA3560 £4.00 TDA3561A £3.00 TDA3562A £3.00
ASTEC UM1R3 €10.00 V314 (VHP) €5.00 V334 €4.00 U321 €6.00	BDU65 50p 9000 Thom Tuner on Panel \$7.00 B7761 30p B1769 30p B7788 30p	OPTG01 20p OPTG01 20p P1(2369 10p	UPC103111 £2.00 UPC1353C £1.00 UPC1363C £2.75	TDA3566 £3.50 TDA3564 £4.00 TDA3565 £3.00
U322 68.00 U341 UHF 66.00 U342 (UHF) 65.00	Change over switch co-ax type box BF819A 30p with fead 50p BF809 30p		UPC1364C £2.00 UPC1365C £2.00 UPC1365C £2.00 UPC1366C £1.00 UPC137811 £2.00	TDA3571A £2.75 TDA3581 £3.00 TDA3590 £3.00 TDA3591 £1.00
U343 Phono £5.00 U343C £6.00 U344C £10.00	BER71 30p Delay Lines BER52 7p DL700 €1.00 BER81 15p DESCO 10 BER81 15p		UPC1514C £3.00 UPC2002 35p UPD1943G £2.00	TDA3592A £3.00 TDA3650 £3.50 TDA3651 £3.00
U411 UHF £4.00 UVF10 £8.00 U.V. 411 Tuner £8.00 U.V. 412 £8.00	KT 3 Luminence 75p BF300 10p Luminance Delay Line (CVC 45) BF132 20p Go-Ax Joint Isp ItEW11 30p	SAA1074 £3.00 SAA1075 £3.00 SAA1124 £2.00	UPD804941C £2 SN29848 50p SN297708N £2.00	TDA3651AQ £3.50 TDA3652 £3.50 TDA3653AQ £2.00
U.V. 415 £7,00 U.V. 417 £5,00 U.V. 418 £10,00	Co-Ax Belling Lee Plug 12p BF-X85 100V, tamp 30p Co-Ax Splitter £1.00 BSD215 50p	SAA1130 £2.50 SAA1174 £3.00 SAA1176 £2.00	SN29771BN €2.00 SN29772BN €2.00 SN7402N €1 SN7472N £1	TDA 3653 €3.00 TDA 3654 €3.00 TDA 3654O €2.00 TDA 354O €2.00 TDA 3710 €3.50
U.V. 617 UHE VITE Tuner 1500 DKO \$5.00 U743 Tuner Fidelity/Amstrad 2000 V/Cap Tuner \$5.00	NE2NoH Small Neon Limps GEC ANo350 C2.00 & Philips 5p BRC-M-200 40p Mullard 5 Watt Amps, LP1162 BRC-M-300 50p	SAA1251 €4.00 SAA1272 €3.00 SAA1274 €3.00	SN74107 £1.00 SN74167 70p SN7472N 20p	TDA3800 €4.00 TDA3180 €2.00 TDA4260 50p
Small V/Cap Milsami UHF 64.00 VHF £ ÚHF ET598P Tuner £6.00	New 75p BKC 1084 £1.00 BRC 3064 £1.00 BT P822 £1.00 BT P822 £1.00 BT P822 £1.00	SAA1276 £3.00 SAA1292 £10.00 SAA1292 £3.00 SAA1293 £3.00 SAA1294 £4.00	SN75108AN £1.00 SN76001 £1.00 SN76013ND £2.00	TDA4501 €3.00 TDA4505N4 €3.00 TDA4505N4 €3.00 TDA450 €2.00
Portable & rotary Tuners Sanyo & Mitsun UHF £5.00 Moslit UHEVHF (new type) £8.00 UE721831 Fid-day V/Cap T/Unit £6	ii 12" 90% black and while £10 12" 90% black and while £10 BTT6018/ML237B £1.50 127/110" 31/510 Post £2.50 £5 BTT6218 £1.50 BTT8218/ML237B £1.50	SAA5000A £1.50 SAB3013 £2.00 SA63037 £2.00	SN76018 £1.00 SN76110N £1 SN76115AN 50p SN76131 50p	TDA46092D D8 £1.00 TDA46002 Flat £3.00 TDA4601 £2.00 TDA4501 £3.00
UL2-5-5H effective year product 23.00 HITACHI 20 Turn Pot 400 U321 on parel 66.00 Turner unit VHS Sylvania GTR Videon	S.W. Filters S.W. Filters BT18224 £1.00 BUP22A £1.00 FW2011 500 CA270AE 500	SAB3210 £2.00 SAB4209 £2.00 TBO0124 £1.00	SN76141N £1.00 SN76226 £1.00 SN76227N £1.00p	TDA9403 £3.00 TDA9503 £3.00 TDB2033 £1.00
MIS 900 C2.50 Toshiba VHF-UHF EG522F C5.00 Mullard Video Modulator, Application,	HVV2013 50p SW185 £1 CA20KW 50p SW453 50p SW153A 50p CA20KE 50p SW150 £1 SW154 50p CA20KE €1.00	SAA300SP €3.00 SAA3000A €2.00 SAA5000A €2.20 SAA5010 €2.20 SAA5012A €5.00	SN76228N £1.00 SN76270 £1.00 SN76532N £1.00	TDD1610S 50p TD6306P £2.00 TDA1060 £3.00
video tape recorders. TV cameras, video games, closed circuit T/V, C.C.L.R system, Data supplied £10,00 4 button Rank Z18 Tunei £4,00	ЦИУ2013 50p САЗнал. 50p RW303 50p F1035B 50p САЗнал. 50p SY2153 50p F1045A 50p САЗНАС 50p CA3195 50p F1045A 50p CA3193 40p	SAA5020 63.50 SAA5025D 63.00 SAA5030 64.50	SN76545N £3.00 SN76546 £3.00 SN76550 .00 SN76552 .00	
BF694 F0p 2SC3795 BF758 30p 2SC3973F BF758 30p 2SC3973F BF756 30p 2SC7350	30p BC368 10p CA3146 21.00 3 30p BC369 10p CA3146 21.00 15p BC384 10p CA3189 40p 15p BC384 10p CBF16848 50p	SAA5040A (3.00 SAA5042A (3.00 SAA5043 (4.00	SN76570 £1.00 SN76620 50p SN7660N 40p	ТЕА5114 £1.00 ТДАЗЛОВ £6.00 SN74LS 125AN ЗФр
BFT34 E5p 2SD180 T BFT34 10p 6Δ BFT84 8p 2SD200	15p BC413 10p CD4555BE 30p 62.00 BC414 10p DM7492 50p 0017492 40p	SAA5050 £4.50 SAA5051 £2.00 SAA5052 £2.00	SN70620AN 50p SN70606 £E.00 SN76705N £E.00	SN74LS 248 50p SIL4516 50p SN16861NG 50p
BFW11 20p 25D401 BFX29 30p 25D716 BFX84 25p 25D787	£1.00 BC 416 P10 11, λ1196 400 £1.00 BC 440 300 11, λ1370 £2, 00 30p BC 454 10p 11, λ1377 £3, 00 30p BC 455 10p 11, λ1377 £3, 00	SAA5241 P/A TEX IC \$5.00 SAF1032p \$2.50 SAF1039 \$2.00	SN76707N 75p SN76708AN 75p SN76720 £1.00 SN76709N £2.00	SN16964AN 50p SN29764AN £1.00 UA721 40p
BF Y52 20p 2SD820 BF Y52 25p 2SD868 BF Y90 25p 2SD870 BL Y49 25p 2SD870	€1.00 BC456 10p 11A11423 €1.00 75p BC460 25p 11A11440 50p £1.00 BC462 10p 11A11484 £3.00	SAS000 £1.00 SAS670 £1.00 SAS580 750	UA783P3C 40p BT100A/02 40p BT138-10A 70p	UA7300 40p MPS43A 25p MD13005 30p
BPW41 25p 2SD880 BRC116 25p 2SD1264 BRX43 15p 2SD1266	€1.00 BC478 100 HA17458 500 €1.00 BC527 100 HEF4001 100 HEF4001 82527 100 HEF4518B 250	SA\$3210 £2.06 S1.437F £4.00 S1.471 50p	BT146 30 TBA540Q €1.50 TCA270 €1.00 TCA270 €1.00	MH2340 28p MJE600 25p
BRX48X 10p 2SD1415 BRY56 30p 2SD1427 BS568 10p 2SD1427 SD1432	€1.00 BC536 10p 11E1-4053B 30p €1.00 BC547 10p 11E1-4056BP 20p €1.00 BC548 10p 11E1-4058B 20p	SL480 £1.00 SL901B £4.50 SL971B £3.00	TCA270S £1.00 TCA270SQ £1.00 TCA240 £1.00	MJE3055 £1.00 MIF2801 30p MIF2955 50p
BSY95a 10p 2SD1577 BTY80 20p 2SD1878 BSY95a 10p 17p 2SD1878	£1.00 BC557 10p K5731D 1001012 £1.00 105 LA3230 50p	\$1,918 £4.50 \$1,1430 £1,00 \$15,4793 £3,00 \$17,85041 £5,00	TCA80 £1.50 FCA80 £1.00 TCA940 £1.00	MUE13005 50p Sanikron Diode 30p Power FET
BSX20 17p BC107 FT3055 30p BC108 TCE82 30p BC109	10p 10C 357 10p 1.A 7830 €2.00 10p BC635 10p 1.A 7831 €2.00 5p BC636 10p 1.A 7831 €2.00	TA7122 €1.15 TAA320A 50p TAA470 £1.50	TCEPID0 £1.00 TCEI20CO £1.00 TCEI20CO £1.00 TCEI20CO £0.00 TCEI20CO £0.00 TCEI20CO £0.00	V NS8AF 50p Transistors A1222 25p BF181 20p
TCE520 30p BC115 2N930 5p BC114 2N2221 8p BC115	10p BCX32 25p LN8361 £3.00 10p BD116 25p PCF8571P £5.00 10p BD124 30p M913 £2.00	TAA570 720 TAA611B £1.00 TAA621 £2.00 TA7108P £1.00	1DA400 50 1DA1003A €1.0 1DA1010 €1.0	A1223 25p BF182 20p AC106 25p BF184 20p AC121 25p BF194 10p
2N2906 10p BC117 2N3055 40p BC119 2N3055 40p BC125	20p BD124 (menal) 30p M1024=SAA €2.00 20p BD134V 25p M1025=SAA €2.00 30p BD134V 25p M1025=SAA €2.00 30p BD134V 25p M1025=SAA €2.00	TA7117 50p TA7120P 50p	TDA1013 £1.0 TDA1012 £1.0 TDA1013A £1.0 TDA1013A £1.0 TDA1060A £1.5	AC124 25p 18F195 10p AC128 25p 18F196 10p AC137 25p 18F197 12p
2N3702 10p BC126 2N3701 10p BC139 2N3583 50p BC140	10p BD132/238 30p MC470p C75p 10p BD135 25p MC1312 30p BD136 300 MC1312	TA7240AP £3.00 TA7265 £3.00 TA7609P 50p	TDA 1035T £1.0 TDA 1035SB £1.0 TDA 1072 £	0 AC131 25p BF199 10p AC138 25p BF200 20p
2N3904 15p BC141 2N4355 E0p BC143 2N4342 £1.00 BC147	25p (BD138	TA7227P £1.00p TA7265AP £3.00 TA7680AP £3.00 TA7680AP £3.00	1DA1150 50 1DA1151 30 1DA1154 50 1DA1154 50 1DA11708 €1.0	AC153K 25p BF224 15p AC142K 25p BF238 20p AC169 25p BF234 16p
2N4444 £1.00 BC148 2N5278 20p BC153 2N5278 40p BC153 2N5983 30p BC154	HOP BD183 TOP MC14002 15p 10p BD202 30p MC14013 25p 10p BD202 30p NC14013 25p 10p BD204 30p NC14013 25p	118A120A 40p 118A120AS 50p 118A120SA 40p	TDA1180 €2.0 TDA1190 £1.0 1DA1200 75 TDA1270 £1.5	0 AC1/6 250 191244 400
2No(099 40p BC157a 2No(099 40p BC158 2No(109 40p BC158 2No(130 50p BC159	10p BD207 60p NIC 44504 50p 10p BD221 20p MC 14514 50p 10p BD222 30p MC 1748 80p 10p BD222 30p MT 1-043056 £1.00	1BA1208B 400 1BA1201 500 1BA12050 £1.00	TDA1327A 69 TDA1365 €3.0 TDA1512 €2.0	AC188 25p BF257 20p ACY21 25p BF258 25p ACY21 25p BF262 15p
2N6133 20p BC1N01 2N6348 20p BC171 2N6399 10p BC172	6 25p BD228 30p ML231 C2.50 5p BD226 20p ETT6016 C2.00 5p BD233 30p ML232 €1.00 5p BD233 30p ML232 €1.00	1BA120U 75p 1BA120Q 30p 1BA120C 40p	TDA 1540P £3.0 TDA 1670A £2.0 TDA 1908A £1.0 TDA 2002 £1.0	0 AD143 S40 BE263p 25p 0 AD149 540 BE264 15p 0 AD161/462 BE271 10p 0 pair 40p BE273 10p
2SA437 20p BC173 2SA673P 10p BC174 2SA844P H0p BC183	5p B12235 30p M1-23/15 41.00 5p B12238 30p M1-23/B 44.00 5p B1239 15p M1-230 €2.00	1BA1441 £2.00 TBA231 75p TBA395Q 50p	1DA2003 25 1DA2004 £2.0	p AF17A 25p B1774 10p AF139 25p BF324 25p 0 AF139 100 BF337 50p 0 AF181 100 BF337 50p 0 AF39 55p BF3355 30p
2SA992 H0p BC204 2SB474 30p BC207 2SB456 H0p BC212	Sp BD240 S0p Hypesters Sp BD243c 30p Philips Kits OT121 Sp BD244 S0p IRB6a	113 A 396 75p 50p 113 A 440P £1,00 90p 113 A 1440C £1,00	17DA2020 £1.0 17DA2030 £2.0 17DA2140 £3.5	Al ² 239 25p Bl ² 552 20p Al ² 367 25p Bl ² 362 20p Al ³ 67 25p Bl ² 363 15p Al ⁴ 02 €1.75 Bl ² 363 15p Al ⁴ 02 €1.75 Bl ² 361 15p Al ⁴ 02 €1.75 Bl ² 361 15p Al ⁴ 02 €1.75 Bl ² 361 15p Al ⁴ 02 €1.75 Bl ² 02 €1.75
2SB686 75p BC213 2SC515A £1.00 BC214 2SC772 20n BC237	5p BD252 20p B10b Plastic 5p BD253B 50p B7106 Metal £ 87106 Metal £ \$ \$ \$	20p TBAASKO £1.00 30p TBA520 £2.00 .20 TBA520 £2.00 .00 TBA530 £2.00		0 BU 1949 50 BE391 15p 0 BU 1949 50 BE394 10p 19 BE115 20p BE394 10p 0 BE121 20p BE419 30p 0 BE121 20p BE419 30p
2SC381 10p BC238 2SC458 50p BC239 2SC491 50p BC250	5p BD373b 20p BRC443 G11 Division	75p TBA560CO £1.00 TBA570 £1.50	1DA2600 63.0 1DA2640 62.0 1DA2522 65.0	BF 127 20p BF 423 15p B BF 137 20p BF 423 15p 0 BF 137 20p BF 448 30p 0 BF 157 20p BF 448 30p 0 BF 160 20p BF 471 30p 0 BF 160 20p BF 471 30p
2SC732 10p BC251	50 RD437 250 MC8726	250 4MHz 000 4.433-619	1DA2532 41.0 1DA2540 80 1DA2541 €1.0	0 gipton bis
2SC733 100 BC262 2SC940 £1.00 BC263 2SC1030 £1.00 BC263b 2SC1051 \$00 BC298 2SC1052 C/18 300 BC298 2SC1514 300 BC298 2SC1514 300 BC308	20p BD139 30p HC3M4 L 30p BD1349 50p HC3444 L 10p BD544D 40p 12084 L 30p BD544D 40p 12084 L 30p BD5630 50p 12084 L 30p BD5678 30p 12084 C	00 6MHz 00 8.867238 00 114394000 00 114394000	110/_040 12.1	0 Dr100 200 0 Thorn Transformers 0 DT2076/78 E10 90D3403 E10
25C 1514		50p Antistatic Isolators 2.00 Disc Type Black 10p	1 113 A 3565	
2SC1750 50p BC328	10p BD509 30p 10p BD510	CSA 3.97M 15	MA721PC £1.00 M50430-8505P £1.00	MN1250BJC £1.00
23C 1942 £1.00 BC337 2SC2027 £1.00 BC338 2SC2068 20p BC347 2SC2068 20p BC347	10p BD519 30p Gs Degatism 10p BD534 30p TTTP776312 10p BD535 30p TTTP776312	75p 6MEG CDA 25j 35p 6MHz SFE 12j 709 SFE 5.5MHz 20j 15p SFD40B 15j 229 CSB455A 15j	2 TD6359P £1.0 3 M58657P £1.0 9 PCD8572 £1.0) M50441-5505P €1.00) M491BB1 €2.00) H∆513385 €1.00
28C2229 15p BC350 28C2688 20p BC365	10p BD544D 30p pr7376 file isset pr734 20p BD552 30p Deguising thermision (fils most second provided on the	ts) 20p C3D4237A 151 50p 50p	P FID74EC86P £1.0	