

MAKING TV AERIALS

Practical Television '66

JANUARY 1960

AND TELEVISION TIMES

CONTENTS

ACORN TV BOOSTER
FRAME GRID VALVES
SAFETY WITH SERIES HEATERS
SERVICING TV RECEIVERS
YOUR PROBLEMS SOLVED
ETC. ETC. ETC.



This splendid AVO instrument has been developed to meet a definite demand for a sturdy pocket-size multi-range test meter at a modest price, suitable for use on modern electronic apparatus as well as for radio and television receivers, motor vehicles, and all kinds of domestic appliances and workshop equipment. Readings are obtainable quickly and easily on a very open scale, and range selection is by means of a robust, clearly marked rotary switch of the characteristic AvoMeter type. Measurements of A.C. and D.C. Voltage, D.C. Current and Resistance are made by means of only two connection sockets.

Designed and Manufactured by

AVO LTD AVOCET HOUSE • 92-96 VAUXHALL BRIDGE RD. • LONDON • S.W.1
A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES.

Just Right for your pocket !

THE

MULTIMINOR

19 Ranges

- D.C. Voltage :** 0-1,000V in 7 ranges
- A.C. Voltage :** 0-1,000V in 5 ranges
- D.C. Current :** 0-1A in 5 ranges
- Resistance :** 0-20,000 Ω, 0-2M Ω.
- Pocket Size : 5½ x 3½ x 1½ inches.
- Weight : 1 lb. approx.

List Price **£9 : 10s.**

Complete with Test Leads and Clips.
Leather Case if required 32/6.

Sensitivity :

10,000 ohms per volt on D.C. voltage ranges.
1,000 ohms per volt on A.C. voltage ranges.
Accuracy :
On D.C. 3% of full scale value.
On A.C. 4% of full scale value.
To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.

Telephone : VICTORIA 3404 (12 lines)

RST

MAIL ORDER DEPARTMENT
211 Streatham Road, Mitcham, Surrey
ALL VALUES LISTED ARE NEW STOCK
• Terms C.W.O. or C.O.D. Postage 3d. per valve.
MITCHAM G201.

6AZ1 10/6	EF92 5/-	PCF82	UY85 7/6	6K8G 7/6
6B5 8/6	EL42 10/-	VP4B 17/6	6K8GT 7/6	
6AF91 7/6	EL94 9/-	PCL82	W81M 5/9	6L1 12/6
6AF96 9/6	FL90 8/6	11/6	W142 9/-	6L6G 15/6
6F91 5/-	FM80 10/-	PCL83	W719 7/6	6L18 7/6
6H719 7/6	EM81 10/-	12/-	W727 7/6	6L19 12/6
6K91 9/-	ES81 10/6	PEN41	X78 21/-	6L19 21/-
6ABC90	ES84 10/6	7/-	X79 21/-	6N7G/GT 7/6
	6EY85 9/6	PEN4VA	Z21 12/6	
6AF42 10/-	6EY91 9/-	21/-	Z77 5/-	6SL7GT 7/6
6B91 5/-	6EZ35 7/-	PL96 15/-	Z152 7/6	6SN7GT 16/6
6BC41 9/6	6E40 7/6	PL61 14/9	Z719 7/6	
6BF80 9/6	6E241 7/6	PL82 8/-	3N4G 7/-	6V6G 5/6
6BF99 9/-	6E230 7/6	PL83 10/6	5V1G 9/6	6X5GT 5/6
6C91 9/6	6E281 7/6	PY81 9/-	5N4GT 5/6	7B7 10/6
6CC91 8/-	6C2 21/-	PY82 8/-	5Y3GT 8/6	7Y4 7/6
6CC91 8/-	6C4 17/6	PY83 8/6	5Z4G 10/-	8Y3 5/6
6CC93 9/6	6C13 17/6	RY83 8/6	R10 21/-	10LD11
6CC81 9/6	6C13C 21/-	R19 19/6	TDD4 17/6	12A8 10/-
6CC85 9/6	6G32 11/6	H30 5/6	TP22 17/6	12AT5 10/-
6CF90	6H3 5/6	H63 9/6	U142 8/-	12AT7 10/-
	6H3 9/6	HBC90 9/6	U147 7/-	12AX7 9/6
6CF82 12/6	HL2 6/6	HL2 6/6	U153 9/-	12BA6 9/6
6CH35 9/-	HL133D 10/-	UABC80 8/-	UA142 9/6	12B7 9/6
6CH42 10/-	KT3C 10/-	UA142 9/6	UB21 8/6	12BHT 15/-
6CH81 9/-	KT86 10/6	UCF90 8/6	UC42 8/6	12J7G 9/6
6CL90	LZ319 12/6	UCF90 8/6	UCH42 9/-	12K7GT 8/6
	MKT1(5) (or 7) 17/6	UCH81 9/-	6D2 5/-	12K8GT 12/6
6E37A 8/6	ML1 15/-	UCH81 9/-	6F1 15/6	12Q7 8/6
6E40 15/-	MSP4 17/6	UCL83 23/6	6F12 5/-	12Q7GT 8/6
6E41 9/3	MU14 9/-	6F43 4/6	6F13 17/6	35Z4GT 8/6
6E42 10/6	MX49 17/6	6J7GT 8/6	6F43 4/6	50L6GT 7/6
6E90(A) 4/6	N142 9/6	6K7 4/6	6K7 4/6	813 50/-
6E91 4/-	N153 11/6	6K7GT 4/-	6K7GT 4/-	
6E92 13/6	PCC94 9/6	6K7GT 4/-		
6E99 10/-	PCF80	UY41 7/6		
6F91 5/-				

SEND FOR LISTS.

Quotations given for any types not listed. Obsolete and old types a speciality.

TELEVISION TUBES REBUILT

BUY DIRECT FROM THE FACTORY!

12 MONTHS' GUARANTEE

12" - - - - £5. 0.0
14" - - - - £5.10.0
17" - - - - £6.10.0

Carriage and insurance 12/6 extra.

MARSHALLS for TELEVISION

131 St. Ann's Road, Tottenham,
London, N.15.

Telephone: STAmford Hill 3267


A REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at 7½" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone
- ★ Erase and fast rewind

£13.12s

Special moving-coil microphone and tape extra.

EASY TERMS

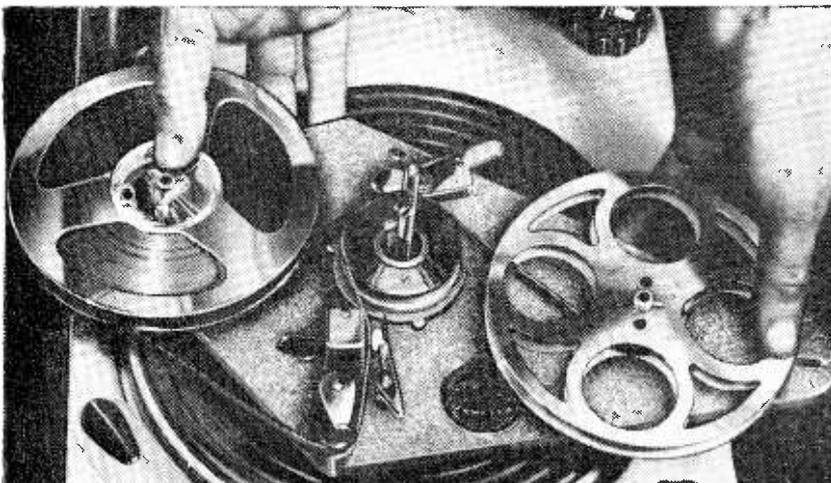

Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely new . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get a quality that has to be heard to be believed! Everyone is praising the Gramdeck.

"The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

"Ingenious—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER.
 "Ingenious and robust."—BRITISH SOUND RECORDING ASSOCIATION JOURNAL.

"Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."—BRITISH RADIO & TV RETAILERS REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."—AMATEUR CINE WORLD.

WORKS FROM ANY RECORD-PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy, today.



MADE BY THE FIRM THAT MAKES RADAR EQUIPMENT FOR VISCOUNTS & BRITANNIAS

FREE BOOK—POST NOW!

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.

(Write if you prefer not to cut page)

NAME

ADDRESS

Gramdeck (Dept. PT 804) 29 Wright's Lane
Kensington, London, W.8

Gramdeck

GRAMPHONE TAPE RECORDER
HIGH QUALITY TAPE-RECORDING FOR EVERY HOME

GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

ANY ORDER		INSURED		AGAINST		DAMAGE IN TRANSIT		FOR ONLY 8d. EXTRA.											
0B2	17/6	6C8	12/6	6X4	6/6	198G6G	9002	5/6	DL96	9/1	EL34	15/1	KTZ63	10/6	QSI150/15	UCL82	11/6		
0Z4	6/1	6C9	12/6	6X5GT	6/1	AC/PEN	AC/PEN	7/6	DM70	7/6	EL38	26/6	L63	6/1	10/6	UCL83	19/3		
1A3	3/1	6C10	10/6	6/30L2	6/1	19H1	10/1	5-pin	23/3	EA50	2/1	EL41	9/1	LN152	10/6	R12	9/1		
1A5	6/1	6C6DG	36/6	7A7	12/6	20D1	15/3	7-pin	15/1	EABC80	9/1	EL42	12/11	LN309	11/6	R18	14/1		
1A7	21/11	6CH6	12/6	7B6	21/3	20F2	26/6	AC/2PEN	7/6	EAC91	7/6	EL81	12/6	MH4C	7/1	R19	19/11		
1CS	12/6	6D3	19/11	7B7	8/6	20L1	26/6	23/3	23/3	EAF42	9/6	EL84	8/6	MHL4	7/6	SD6	12/1		
1D6	10/6	6D6	6/6	7C5	8/1	20P1	26/6	AC2PEN/	EB34	2/6	EL85	11/11	MHLD6	12/6	SP4(7)	15/1	UF86	17/11	
1H5GT	11/1	6E5	12/6	7C6	8/1	20P3	23/3	DD	26/6	EB41	8/6	EL91	5/1	ML4	12/6	SP41	3/6		
1L4	6/1	6F1	26/6	7D8	23/3	20P5	23/3	AC4PEN	EB91	5/6	EL95	10/6	MU14	9/1	SP42	12/6	UL41	9/1	
1LD5	5/1	6F6G	7/1	7H7	7/1	25A6G	11/1	26/6	EB3	23/3	EM34	10/1	MX40	15/1	SP61	3/6	UL44	26/6	
1LN5	5/1	6F6GTM	8/1	7R7	12/6	25L6GT	10/1	AC5PEN	EB33	7/1	EM71	23/3	N37	19/11	SU25	26/6	UL46	14/6	
1NSGT	11/1	6F8	12/6	7S7	10/6	25U4	16/7	23/3	EB41	8/6	EM80	9/6	N78	19/11	SU61	9/6	UL84	8/6	
1R5	7/6	6F11	17/3	7V7	8/6	25Y5	10/6	AC6PEN	EB81	8/1	EM81	9/6	N108	19/11	T41	23/3	UM4	17/3	
1S4	9/1	6F12	5/6	7Y4	8/1	25Y5G	10/1	AC/SG	EBF80	10/1	EM84	10/1	N308	20/7	TDD4	24/7	URIC	9/1	
1S5	7/6	6F13	11/6	7Z4	18/7	25Z4G	9/6	AC/TP	EBF83	13/11	EN31	30/1	N339	29/10	TH4B	15/1	UU6	19/11	
1T4	6/1	6F14	26/6	8D2	3/6	25Z5	10/6	AC/VP1	EBF89	9/6	EY51	9/6	P61	3/6	TH41	26/6	UU7	16/7	
1U5	10/1	6F15	15/3	8D3	5/6	25Z6G	10/1	AC/VP2	EBL21	23/3	EY83	16/1	PABC80	7/6	TH233	33/2	UU8	26/6	
2A7	10/6	6F16	9/6	9BW6	15/3	25Z6GT	4/1	ATP4	5/1	EBL31	23/3	EY84	14/1	13/11	TH2321	20/1	UU9	7/6	
2P	26/6	6F17	12/6	9D2	5/6	16/7	AZ1	18/7	EC52	5/6	EY86	10/1	PCC84	8/1	TF22	15/1	UYIN	18/7	
2X2	4/6	6F32	10/6	10C1	12/1	27S0	19/11	AZ31	10/1	EC54	6/1	EZ35	6/1	PCC85	9/6	TF25	19/6	UY21	16/6
3A4	7/1	6F33	7/6	10C2	26/6	28D7	7/1	AZ41	13/11	EC70	12/6	EZ40	7/6	PCC88	23/11	TF2620	33/2	UY41	7/6
3A5	10/6	6G6	6/6	10D2	12/1	30C1	8/1	B36	24/7	EC92	13/3	EZ41	7/6	PCC89	14/1	TY86F	13/3	UY85	7/1
3B7	12/6	6H6GTG	3/1	10F1	17/6	30F5	7/1	BL63	7/6	ECC32	10/6	EZ80	7/6	PCF80	8/1	U12/14	12/1	VMS4B	23/3
3D6	5/1	6H6GTM	3/6	10F9	10/6	30FL1	10/1	C1	12/6	ECC33	8/6	EZ81	7/6	PCF82	11/6	U16	12/1	VP(7)	12/6
3Q4	7/6	6J5G	5/1	10LD3	8/6	30L1	8/1	C1C	12/6	ECC34	24/7	FC2A	24/7	PCL82	12/6	U18/20	9/1	VP4(7)	15/1
3Q5GT	9/6	6J5GT	5/6	10LD11	8/1	30P12	8/1	CBL1	26/6	ECC35	8/6	FC4	15/1	PCL83	11/6	U22	8/1	VP2B	14/6
3S4	7/6	6J5GTM	6/1	15/11	30P16	8/1	CBL31	23/3	ECC40	23/3	FC13	26/6	PCL84	12/6	U24	29/10	VP4B	23/3	
3V4	7/6	6J6	5/6	10P13	15/6	30PL1	11/6	CCH35	23/3	ECC81	8/1	FC13C	26/6	PEN4DD	U25	13/6	VP13C	7/1	
3R4GY	17/6	6J7G	6/6	10P14	19/3	31	7/6	CK506	6/6	ECC82	7/6	FW4/500	9/1	PEN25	26/6	U26	10/1	VP23	6/6
3U4G	8/6	6J7GT	10/6	11D3	24/7	33A/158M	8/1	CL33	19/3	ECC83	8/1	FW4/800	9/1	PEN25	19/11	U31	10/1	VP41	6/6
3V4G	11/1	6K6GT	8/1	12A6	6/6	35/51	12/6	CV63	10/6	ECC84	9/6	FW4/800	9/1	PEN36C	10/1	U33	26/6	VR75/30	17/6
3X4E	12/6	6K7G	5/1	12AC6	15/3	35/51	12/6	CV271	10/6	ECC89	9/6	FW4/800	9/1	PEN40	10/6	U36	26/6	VR105/30	17/6
3Y3G	8/1	6K7GT	6/1	12AD6	17/3	35A5	21/3	CV428	30/1	ECC91	5/6	G230	10/6	PEN40DD	U37	26/6	VR105/30	17/6	
3Y3GT	7/6	6K8G	8/1	12AE6	13/11	35L6GT	9/6	CY1	18/7	ECF80	11/6	G232	12/6	PEN44	25/1	U43	9/6	VR150/30	9/1
3Y4	12/6	6K8GTG	12A7H	8/1	35W4	7/6	CY31	16/7	ECF82	10/6	G234	14/6	PEN44	26/6	U45	9/6	VR150/30	9/1	
3Z3	12/6	12A8H	12/6	35Z3	10/6	D1	3/1	ECH3	26/6	H30	5/1	PEN45	19/6	U50	8/1	9/1	9/1	VR150/30	9/1
3Z4G	10/6	6K25	19/11	12AT6	7/6	35Z4	6/6	D15	10/6	ECH21	23/3	H63	12/6	PEN45DD	U52	8/6	VT61A	5/1	
5Z4GT	12/6	6L1	23/3	12AT7	8/1	35Z5GT	9/1	D63	5/1	ECH35	9/6	HABC80	10/6	PEN45	26/6	U54	19/11	VT501	5/1
6A7	26/6	6L6G	9/6	12AU6	23/3	41MTL	8/1	D77	5/6	ECH42	10/6	13/6	PEN46	7/6	U76	6/6	W6M	26/6	
6A8	10/1	6L6M	12/6	12AU7	7/6	42	23/3	DAC32	11/1	ECH81	9/1	HL23	10/6	PEN383	23/3	U78	6/6	W6	6/6
6AB7	8/1	6L7GT	12/6	12AV6	12/7	43	12/6	DAF91	7/6	ECH83	11/1	HL23DD	10/6	PEN453DD	U107	16/7	W81M	6/1	
6AB8	10/6	6L18	13/1	12AX7	8/1	50C5	12/6	DAF96	9/1	ECL80	10/6	17/3	33/2	U191	16/7	W107	15/3	W8	6/1
6AC7	6/6	6L19	23/3	12BA6	8/1	50CD6G	10/1	DD41	13/11	ECL82	10/6	HL41	12/6	PEN/DD	U201	16/7	W229	18/7	
6AG5	6/6	6LD3	8/6	12BE6	10/1	36/6	DF33	11/1	ECL83	19/3	HL41DD	40/20	33/2	U251	14/1	X24M	24/7		
6AK5	8/1	6LD20	15/11	12BH7	21/3	50L6GT	9/6	DF66	15/1	EF9	23/3	19/3	PL33	19/3	U281	19/11	X31	26/6	
6AL5	5/6	6N7	8/1	12E1	30/1	53KUC	19/11	DF70	15/1	EF22	14/1	HL42DD	14/1	PL36	14/1	U282	22/7	X41	15/1
6AM6	5/6	6P1	19/3	12J5GT	4/6	72	4/6	DF91	6/1	EF36	6/1	19/3	PL38	26/6	U301	23/3	X42	15/1	
6AQ5	8/6	6P25	12/6	12J7GT	10/6	75	24/7	DF96	9/1	EF37A	8/1	HN309	24/7	PL81	12/6	U329	14/1	X61(C)	12/6
6AT6	8/6	6P28	26/6	12K5	17/11	77	8/1	DF97	9/1	EF39	5/6	HVR2	20/1	PL82	8/1	U339	16/7	X61M	26/6
6AU6	10/6	6Q7G	8/1	12K7GT	6/1	78	8/1	DFH30	15/6	EF40	15/1	HVR2A	6/1	PL83	9/1	U403	16/7	X63	10/1
6AV6	12/7	6Q7GT	11/1	12K8GT	14/1	80	9/1	DH63	8/1	EF41	9/6	KF35	8/6	PL84	12/8	U404	8/6	X65	12/6
6B7	10/6	6R7G	10/1	12Q7GT	6/6	83	15/1	DH63(Met)	EF42	11/6	KK32	21/11	PL820	18/7	U801	29/10	X66	12/6	
6B8G	4/6	6SA7GT	8/6	12SA7	8/6	83V	12/6	17/6	EF50(A)	7/1	KL35	8/6	PM2B	12/6	U4020	16/7	X76M	14/1	
6B8GT	5/1	6SC7	10/6	12SC7	8/6	85A2	15/1	DH76	6/6	EF50(E)	5/1	KLL32	24/7	PM12	6/6	UABC80	9/1	X78	21/3
6BA6	7/6	6SG7GT	8/1	12SG7	8/6	150B2	15/1	DH77	8/6	EF54	5/1	KT2	5/1	PM12M	6/6	UAF42	9/6	X79	21/3
6BE6	7/6	6SH7GT	8/1	12SH7	8/6	185B7	33/2	DH101	28/6	EF73	10/6	KT33C	10/1	PM24M	21/3	UB41	12/1	X101	33/2
6BG6	23/3	6S7GT	8/1	12S7	8/6	185BTA	33/2	DH107	13/11	EF80	7/1	KT36	29/10	PM4	10/6	UBC41	8/6	X109	33/2
6BH6	9/1	6SK7GT	8/1	12SK7	8/6	304	10/6	DK32	21/11	EF85	7/1	KT41	26/6	PX25	59/8	UBC81	11/4	XDC(1.5)	6/6
6B16	7/6	6L7GT	8/1	12SQ7	12/6	305	10/6	DK40	21/3	EF86	12/6	KT44	15/1	PY31	16/7	UBF80	9/1	XFG1	18/1
6BQ7A	15/1	6SN7GT	6/6	12SR7	8/6	402Pen/A	DK91	7/6	EF89	9/1	KT61	12/6	PY32	17/11	UBF89	9/6	XFY34	17/6	
6BR7	23/3	6SQ7GT	9/1	12Y4	10/6	23/3	DK92	10/6	EF91	5/6	KT63	7/1	PY80	7/6	UBL21	23/3	XH(1.5)	6/6	
6BW6	10/6	6SS7GT	8/1	14B6	19/3	807	7/6	DK96	9/1	EF92	5/6	KT66	15/1	PY81	9/1	UCC84	14/7	XSG(1.5)	6/6
6BW7	7/1	6U4GT	12/6	14H7	23/3	956	3/1	DL33	9/6	EF97	13/3	KT88	22/6	PY82	7/1	UCC85	9/1	X7	6/6
6BX6	7/1	6U5G	7/6	14S7	27/10	1821	16/7	DL66	15/1	EF98	13/3	KTW61	8/1	PY83	9/6	UCF80	16/7	Y63	7/6
6C4	7/1	6U7G	8/6	14ST	26/6	5763	12/6	DL68	15/1	EK32	8/6	KTW62	8/1	PZ30	19/11	UCH21	23/3	Z63	10/6
6C5G	6/6	6V6G	7/1	18	23/3	7193	5/1	DL92	7/6	EL32	5/6	KTW63	8/1	QP21	7/1	UCH42	9/6	Z66	20/1
6C6	6/6	6V6GTG	8/1	19AQ5	10/6	7475	7/6	DL94	7/6	EL33	12/6	KTW41	8/1	QP25	15/1	UCH81	9/6	Z77	5/6

FULL RANGE OF TRANSISTORS AND GERMANIUM DIODES IN STOCK. TECHNICAL DATA AND PRICES FREE ON RECEIPT OF SELF ADDRESSED ENVELOPE.

NEW METAL RECTIFIERS—FULLY GUARANTEED

Technical leaflet on Metal Rectifiers free on receipt of S.A.E.

DRM-1B	15/4	RM-1	7/1	WX3	3/6	14A100	27/1	14RA 1-2-8-2	17/6	16RE 2-1-8-1	8/6
DRM-2B	16/2	RM-2									

COMPLETELY RE-SCREENED C.R.T'S

Midland Tubes Ltd., offer a new service in the rebuilding of C.R. Tubes. Each tube is completely re-screened and aluminised, and fitted with a new Gun Unit. All types—Triodes to Electrostatics.

12 months' Guarantee and Free, immediate delivery.

Please write or 'phone.

MIDLAND TUBES LIMITED

37 George Street, Manchester, 1. Tel.: Central 4568.



R.S.C. (BRADFORD, LEEDS and MANCHESTER)

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/9 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 6 p.m. Wednesdays until 1 p.m. S.A.E. with enquiries, please. Trade supplied.

R.S.C. TRANSFORMERS Fully Guaranteed

Interwired and Impregnated
TOP SHROUDED DROP THROUGH
 261-0-260 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 17/9
 351-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
 250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 29/9

TULLY SHROUDED UPRIGHT
 Midret type 21-3-11 ... 17/9
 250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 25/9
 300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 27/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 27/9
 350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 35/9
 425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v 4 a C.T. 5 v 3 a ... 49/9

FILAMENT TRANSFORMERS
 All with 200-250 v 50 c/s Primaries : 6.3 v 1.5 a, 5/9 ; 6.3 v 2 a, 7/6 ; 0-4-8.5 v 2 a, 7/9 ; 12 v 1 a, 7/11 ; 6.3 v 3 a, 8/11 ; 6.3 v 6 a, 17/9.

CHARGER TRANSFORMERS
 200-250 v 0-9-15 v 11 a, 11/9 ; 0-9-15 v 3 a, 16/9
 0-9-15 v 5 a, 19/9 ; 0-9-15 v 6 a, 23/9.

OUTPUT TRANSFORMERS
 Standard Pentode 5,000 to 3 ohms ... 3/9
 Small Pentode 5,000 to 3 ohms ... 5/9
 Standard Pentode, 7,8,000 to 3 ohms ... 5/9
 Push-Pull EL84 to 3 or 15 ohms ... 18/9
 Push-Pull 10-12 watts 6V6 to 3 or 15 ohms ... 18/9
 Push-Pull 10-12 watts 6V6 to 5, 8 or 15 ohms ... 21/9

SMOOTHING CHOKES
 100 ma 10 h 250 ohms ... 8/9
 80 ma 10 h 350 ohms ... 5/6
 60 ma 10 h 400 ohms ... 4/11

SELENIUM METAL RECTIFIERS
 Special quotes for quantities of 50 to 5,000.
L.T. (H.W.) F.W. (Bridge)
 250 v 50 ma ... 3/11 6/12 v 1 a ... 3/11
 250 v 80 ma ... 5/11 6/12 v 2 a ... 6/11
 250 v 100 ma ... 6/11 6/12 v 3 a ... 9/9
 Contact Cooled 6/12 v 4 a ... 12/3
 250 v 80 ma ... 6/11 6/12 v 5 a ... 14/6
 250 v 75 ma 6/12 v 6 a ... 15/6
 250 v 75 ma 6/12 v 10 a ... 25/9
 F.W. (Bridge) 8/11 6/12 v 15 a ... 27/9

CO-AXIAL CABLE lin.
 75 ohms 14/36 ... 8d. yd.
 Twin-screened Feeder ... 11d. yd.

ACCUMULATORS, 2 v 16 A.H. New Ex-Govt., 5/6 ea.; 3 for 15/.

BATTERY SET CONVERTER KIT
 All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma, fully smoothed and fully smoothed L.T. of 2 v at 0.4 to 1 a. Price including circuit, 49/9. Or ready for use, 9/9 extra.

ALL DRY RECEIVER BATTERY ELIMINATOR KIT—All parts for the construction of a unit (metal-case 5 1/4-1 1/2 in.) to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or ready for use, 46/9.

D.C. SUPPLY KIT—Suitable for Electric Trains. Consists of mains trans. 200-250 v 50 c.p.s. A.C. 12 v 1 a Selenium F.W. Bridge Rectifier, 2 Fuseholders, 2 Fuses, Change Direction Switch, Variable Speed Regulator. Partially drilled Steel Case, and Circuit. 33/9

TELEVISION RECTIFIERS
 250 v 200 ma. Size 3 x 1 1/2 in. Brand New, 6/9.

54-56 MORLEY STREET, BRADFORD. ARCADE, BRIGGATE, LEEDS, 1. 5/7 COUNTY ST., (Market St.), MANCHESTER. 8/10 BROWN ST., 29-31 Moorfield Rd., Leeds, 12. Mail orders to Dept. N.,

EX-GOVT. MAINS TRANSFORMERS

All 200-250 v 50 c/s input. Removed from New ex-Govt. units. 22/9
 275-0-275 v 100 ma, 6.3 v 7 a, 5 v 3 a ... 11/9
 300-0-300 v 60 ma, 6.3 v 2 a ... 11/9
 265-0-265 v 150 ma, 6.3 v 11 a, 5 v 3 a, 5 v 3 a ... 29/11
 350-0-350 v 100 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
 450-0-450 v 250 ma, 6.3 v 3 a, 6.3 v 1 a, 5 v 6 a ... 49/9
 0-24-26-28 v 15 a, A.C. (marked with D.C. rating after rectification.) 69/6 carr. 15/-.

AUTO 0-110/120-220/240 v, 50 watts ... 8/11

EX-GOVT. SMOOTHING CHOKES—
 60 ma 5-10 h 250 ohms ... 2/11
 80 ma 10 h 150 ohms ... 6/9
 100 ma 5 h 100 ohms Tropicalised ... 3/11
 100 ma 8-10 h 100 ohms Parmeko ... 6/9
 120 ma 12 h 100 ohms ... 8/9
 150 ma 10 h 150 ohms ... 9/9
 200 ma 3-5 h 100 ohms Parmeko ... 7/9
 0-10-25 v 24 a, 79/6, carr. 15/-.

EX-GOVT. CASES. Well ventilated, black crackle finished, undrilled cover. Size 14 x 10 x 8 1/2 in. high. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage.

BATTERY CHARGERS

For 200/250 v 50 c/s A.C. mains. 12 months guarantee. Attractive, well ventilated hammer finished cases. 6 v or 12 v 4 amp. with meter and variable charge rate selector, as illustrated. 69/9
 Or Deposit 13/3 and 5 monthly payments of 13/3. 6 v or 12 v 1 amp type. Also suitable for electric train power supply. Only 27/9, post 2/9.



A NEW SERVICE BY SUFFOLK

Suffolk Tubes now offer the finest service available in rebuilt picture tubes.

EACH TUBE IS COMPLETELY RE-SCREENED AND ALUMINISED

Normal rebuilds still available at reduced costs.
All fitted with **NEW GUN UNITS**
and fully guaranteed for 12 MONTHS.
Free, immediate delivery in U.K.

SUFFOLK TUBES LTD

The largest independent
Tube Rebuilders in
London.



Suffolk Hall, 1-3 Upper Richmond Road, Putney, S.W.15. Tel.: VAN 5267, 4304.

Now . . . in your own home, **LEARN**

NO PREVIOUS TECHNICAL
EXPERIENCE NEEDED!

**PRACTICAL
EQUIPMENT**
(INCLUDING TOOLS)
GIVES YOU A REAL
LABORATORY
TRAINING

RADIO - TELEVISION - ELECTRONICS

"The trained electronics
engineer has a great
career ahead of him."

Valuable FREE Book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the trained man—high pay, a prosperous future—or if you prefer it—independence in your own business. If you are trained at home by E.M.I. Institutes you will be in the hands of *specialists* who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

We Definitely Guarantee
"NO PASS—NO FEE"
Full details of the Courses, Practical Equipment, convenient monthly payments, our Employment and Advisory Depts., and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. There is no obligation and the book will be sent to you quite free of charge.

FREE BOOK - POST NOW!

Please send me a free copy of your Guide to Careers in Electronics.

NAME

ADDRESS

Subject or Exam



Practical Radio
Radio & Television
Servicing
Practical Electronics
Electronics Engineering
Automation
Basic Practical and
Theoretic Courses for
beginners in Radio,
T.V., Electronics, Etc.
A.M. Brit. I.R.E.,
City & Guilds Radio
Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
"NO PASS—NO FEE"

E.M.I. INSTITUTES


SCHOOL OF ELECTRONICS

The Specialist Electronics Division of the British Institute of Engineering Technology.
(DEPT. SE/20), COLLEGE HOUSE, 29-31, WRIGHT'S LANE, KENSINGTON, LONDON, W.8.

Radio Stethoscope

This can be slipped into the pocket, rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator. The stethoscope is a complete fault-finder.

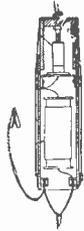All the necessary parts to make this tracer 9.6. post 1/-.



Tester & Reactivator

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will reactivate them, supplied complete with full instructions. Price £3. post 2/3 and ins.

T.V. Service Sheets

200 sheets covering most popular post-war televisions by leading makers—Cossor, Ekco, Ferguson, Pye, etc., £2. post free. PREVIOUS PURCHASERS OF THESE SHEETS PLEASE NOTE: WE CAN SUPPLY SHEETS Nos. 100-200. £1. or IF20-200. 10/-.

T.V. Masks

Latest type grey crystallate
14in. 10 - 17in. 12/-
Plus 1/- post.


A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50,000, with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions. price 19/6, plus 2/6 post and insurance.



Avo Prodclips

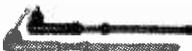The advantage of these testprods is that by pressing the trigger at the side they become crocodile clips and can be left in circuit. This is a great time saver when servicing. Price 15/- pair.



Components Would Cost More

Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 1amps and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230 250 A.C. mains. Special snip price of 55/-, plus 3/6 post and ins.



Assure your future


The ownership of a good instrument has been the turning point in many a famous career. You can own the latest Pullin Series 100 Test Set which is undoubtedly a most useful instrument by a firm long famous for fine instruments, entirely redesigned. It has a square movement with diacron plastic cover, this makes for a brighter, more readable scale, extra scale length and wider angle of vision. With the test set is included a pair of combined testprods and crocodile clips also a stand for inclining the meter at the best reading positions. Ranges A.C. Volts : 0-10, 0-25, 0-100, 0-250, 0-500, 0-1,000 ditto D.C. A.C. Current 0-100 mA. D.C. Current 0-25, 0-10, 0-100, 0-500 mA. Resistance : 0-1M and 0-10K. All at 10,000 ohms per volt. Price £12 7/6 or £14/- deposit and 26 fortnightly payments of 10/-, non callers add 5/- cart. and insurance.



FREE GIFT.—All purchasers of the above items this month will receive Range Extender scale and data which add capacity 2Pp—1mPd. in two ranges. Inductance 0-100 henrys, etc., etc.

Five Useful Articles

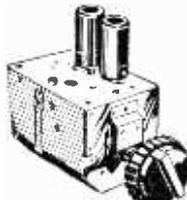
Our 1960 catalogue now ready gives constructional hints and circuits for five useful articles such as moisture operated switch etc. Send for this catalogue to-day. Price 2/6 refundable from purchases.



TURRET TUNER

Brand new stock, not surplus, with coils for Band I and III, complete with valves PCC84 and PCF80—I.F. Output 33'38 Mc.s with circuit diagram 79 6. Knobs 3 6 extra, post and ins. 2/6.

FOUR ITEMS FOR PRICE OF ONE

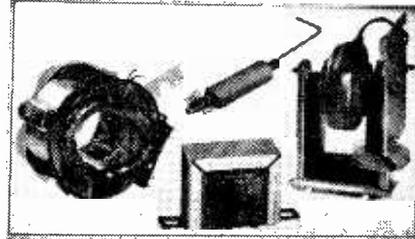

Set of modern T.V. parts, suitable for modernising old television or for a new one. For wide angle 14in. or 17in. tubes comprises: (1) Line output B.H.T. transformer. (2) 700 scanning coils on ferrite yokes. (3) Width control with ferrite core. (4) Frame output transformer. (5) Circuit diagram of a modern television. Offered at the price of the Line output transformer only, namely, 57/6, plus 2/6 post and insurance.

Band III Converters

Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including two EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as extra.) Price only 19 6. plus 2/6 post and insurance. Data free with parts or available separately, 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.



Building a Scope?



3in. oscilloscope tube. American-made type No. 3EP7, octal base 6.3 v. 6 amp. heater, electrostatic deflection, brand new and guaranteed with circuit diagram of alignment scope. 15/- each, plus 1/6 post & ins.

14in. T.V. Cabinet



14in. T.V. cabinet of the latest styling—beautifully veneered and polished—limited quantity, sale price

15/- each. Carriage and packing 3/6 extra. Masks 10/- extra.

Wondergram



This is a record player which operates from Lorch batteries. It is amazingly small and can, in fact, be carried in the pocket—it weighs only about 2lb. Despite its small size it will play all modern records, 7in., 10in. and 12in. at 33 r.p.m. or 45 r.p.m. Completely transistorised, it gives 100 milliwatt undistorted output. Price £15.15.0. H.P. terms available.

Miniature Microphone

American made. Dynamic type, real bargain at 2/6, plus 6d. post.



All items advertised can be obtained from the following Companies.

Electronics (Finsbury Park) Ltd.
29, Stroud Green Rd.,
Finsbury Park, N.4.
Phone: ARCHWAY 1049.
Half day Thursday.

Electronics (Manor Park) Ltd.
520, High St. North,
Manor Park, E.12.

Electronics (Ruislip) Ltd.
42-48, Windmill Hill,
Ruislip, Middx.
Phone: RUISLIP 5780.
Half day Wednesday.

Electronics (Croydon) Ltd.
268, London Road,
Croydon.
Phone: CRO 6558.
Half day Wednesday.



'CATHODRAY' VISCONOL CONDENSERS

for the most stringent conditions


The 'Visconol' Process — exclusive to T.C.C. — means greater dependability and a longer useful life than ever before. It is the answer by T.C.C. research engineers to the insistent demand for condensers which will stand up to higher and still higher voltages. A selection from the range is given below. Features include: low power factor; complete dielectric stability; resistant to voltage surges; ample rating at higher temperatures; proof against breakdown or flash-over. Full details on request.

Cap. in μ F.	Max. Wkg. at 60°C.	Dimens. (Overall)		T.C.C. Type No.	Price
		Length	Dia.		
.0005	25000	5 $\frac{1}{8}$	1 $\frac{1}{8}$	CP57H00	18/-
.001	6000	2 $\frac{1}{2}$	27 $\frac{32}{100}$	CP55Q0	6/-
.001	12500	3	1 $\frac{3}{16}$	CP56V0	10/-
0.001	20000	2 $\frac{1}{2}$	1 $\frac{1}{8}$	CP56G00	10/-
.002	18000	5 $\frac{1}{8}$	1 $\frac{1}{8}$	CP57X0	18/-
.01	6000	3	1 $\frac{3}{16}$	CP56Q0	10/-
.02	12500	6 $\frac{1}{8}$	2	CP58V0	20/-
.05	6000	5 $\frac{1}{8}$	1 $\frac{1}{8}$	CP57Q0	18/-
.1	7000	6 $\frac{1}{8}$	2	CP58Q0	20/-
.25	1000	3	1 $\frac{3}{16}$	CP56V	10/-



THE TELEGRAPH CONDENSER CO. LTD

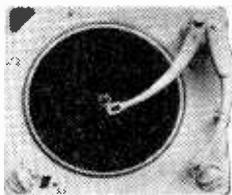RADIO DIVISION: NORTH ACTON LONDON W.3 Tel: ACORN 0061



COLLARO CONQUEST AUTOMATIC CHANGER

With manual play, also turn-over crystal pick-up, 4-speed. A.C. mains, 200/250 P. & P. 3/6 volt.


PRICE

£7.19.6

★ Space does not allow us to show everything we have in stock. We have every value in Resistors, Condensers, Electrolytic Condensers, Silver Mica Condensers and Ceramic Condensers.

PLEASE SEND US YOUR ENQUIRIES, AND WE SHALL BE PLEASED TO SEND YOU OUR LIST.

T.V. CHASSIS 21"

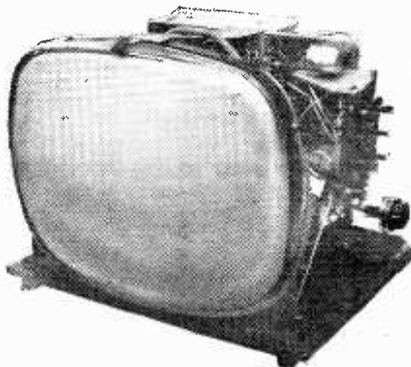

21in. Television Chassis. VHF Radio, volume loaded for all Channels. These sets are brand new.

Made by famous manufacturer. CALLERS ONLY.

Every set tested for you on both Channels before you buy.

UNDER HALF PRICE

39 GNS



GARRARD AUTOMATIC CHANGER RC120/D MARK 2

incorporating Auto and Manual play, dual styli 4-speed. SPECIAL PRICE

9 GNS

SPEAKERS


3 1/2in. Rola Celestion ... 19/11
5in. Goodmans ... 19/6
6 1/2in. Plessey ... 18/6
8in. Goodmans ... 22/-
7 x 4in. Goodmans ... 19/6
8 x 5in. Goodmans ... 21/-
10 x 6in. Rola Celestion ... 29/6
10 x 6in. Plessey ... 27/6
12in. Plessey (3-ohm) ... 32/6
12in. Plessey, 15-ohm, cloth suspension ... 55/-

WIRECOMP ELECTRONICS


378 HARROW ROAD, LONDON, W.9.

Tel.: CUNNINGHAM 9530

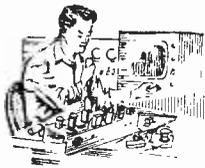Hours of business: 9 a.m.-6 p.m. Open all day Saturday.



Practical Television

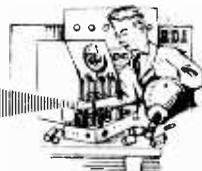

& TELEVISION TIMES

Vol. 10 No. 112

EVERY MONTH

JANUARY, 1960

INDEPENDENT TELEVISION

THE latest report of the Independent Television Authority (1958-59) was issued recently. It is now five years since the 1954 Television Act and five years before the Act is due to expire.

When the ITV was first established there were two schools of thought; one that ITV would provide a low standard of entertainment and one that the competition between BBC and ITV would give rise to a better overall standard of television. This latter supposition has proved to be correct.

During the initial five years of the Authority there have been several periods when its policy concerning advertisements has been adversely criticised. It has often been said in the Press that the advertisements inserted in the programmes are too long and too frequent. In this latest report, the Authority replies in detail to these criticisms. It states that before transmissions began in 1955 the Authority had fully considered how to give effect in precise terms to the general duty placed upon it by the Television Act of securing that:

"The amount of time given to advertising in the programmes shall not be so great as to detract from the value of the programmes as a medium of entertainment, instruction and information."

In the report for 1954-55, the Authority decided that the time given to "spot" advertising should not exceed six minutes an hour averaged over the day's broadcasting. Advertising magazines and features being excluded from this time limitation.

When the Authority was criticised for permitting what was described as an excessive quantity of advertising there was not in its view "any persuasive evidence that advertising was spoiling the programmes for viewers in general." The Authority says that "on the contrary, there was available week by week the simple, though certainly not decisive, test of the relative number of viewers able to choose between the two television services. Though a programme entirely free from advertising was always available at the turn of a switch, viewers as a whole in the 7,000,000 homes able to choose regularly tuned their sets to the programme with advertisements for 70 per cent. of the time." The Authority also states that ITV's share of the audience was rather higher than average during periods when there was most advertising. This attempt to prove that viewers did not think the amount of advertising excessive can only confuse; it could well be that the generally lighter programmes put out by ITV were preferred by most viewers in preference to those of the BBC in spite of the inclusion of advertisements. The widespread criticism of the advertising policy of ITV cannot have been founded upon a myth and the Authority should remember that it was constituted as a public guardian rather than a public relations officer for the programme companies.

Our next issue, dated February, will be published on January 22nd

Editorial and Advertisement Offices :
PRACTICAL TELEVISION
George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1960.

Phone : Temple Bar 4363.

Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for transmission
by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year.

Inland - - £12.0 per annum
Abroad - - £10.6 per annum
Canada - - 19s. per annum

CONTENTS :

	Page
Editorial	171
Frame Grid Valves... ..	172
Analysing and Servicing TV Receivers	175
EHT Supplies	179
Making Television Aerials... ..	182
Fold-over	186
Safety with Series Heaters... ..	190
An Acorn Valve TV Booster	192
Telenews	194
Pungent Pointers	196
Servicing TV Receivers	199
Underneath the Dipole	203
Letters to the Editor	207
Your Problems Solved	211

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Frame Grid Valves

THE LATEST ADDITION TO THE RANGE OF VALVES FOR DOMESTIC TELEVISION

ONE of the latest developments in the field of television has been the introduction of frame grid valves. Frame grids are not new, and their use is not limited to receiving valves. Fully fledged frame grids were used as far back as 1943, and recognisable ancestors can be found in the suppressor grids of some pre-war screened pentodes. Some present-day types use ring-like frames; and the Mullard QV02-6, a double tetrode transmitting valve, has two separate frame grids (one for each tetrode) mounted on opposite sides of the shared cathode. Some manufacturers have used either punched plates or one-piece boxes and have thus eliminated the need for welding.


A discussion of the relative merits of the various kinds of frame, as well as a great deal of background information, can be found in the *Bell System Technical Journal* for October, 1951.

The variety of devices which go under the name of valve is immense: variety not only of size and shape (for example, the subminiature pentode and the klystron), but also of structural detail. If one looks, for instance, at bases, there is a bewildering array which takes in "pee-wee" and "super-jumbo" and a multitude of arrangements of leads and lugs.

Grids

Grids, perhaps, are even more diverse, with little but their general function of "control" in common. There is not much physical similarity between the fanned-out structure of loops which was used in certain very early receiving valves, the straight rods of the octode, the beam plates of the power tetrode, the stiff hairpin of some small thyratrons, the perforated disc of larger types, the elegant structure of almost invisible wires in the first disc-seal valves (such as the wartime CV90), and the familiar cage—round, rectangular, lozenge-shaped—of conventional receiving types. Yet these structures are all known as grids.

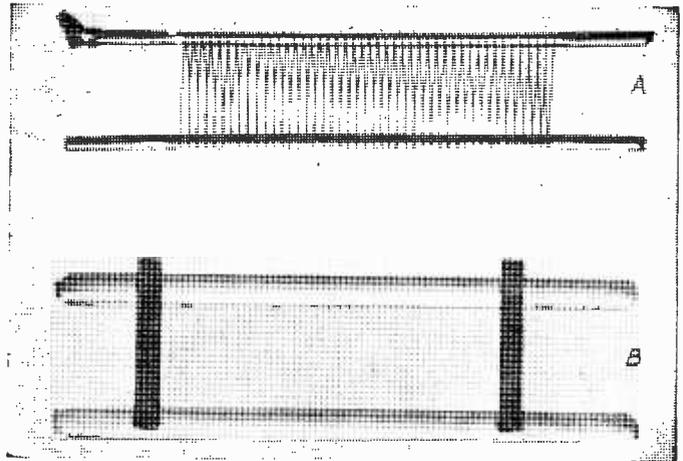In recent years the control grid of the receiving



At A is illustrated a conventional grid and at B a frame grid. Both are shown magnified.

valve has had to meet a number of new demands, and it has undergone—in certain valve types—a further change of shape. The new requirements, which occur mainly in "professional" equipment (computers, telephone carrier systems, radar, and so on), are: a much enhanced degree of uniformity between valves of a particular type, so that valves can be interchanged or replaced without upsetting the operation of a critically adjusted circuit; a high "figure of merit"; and mechanical rigidity.

Figure of Merit

This is a term which has had a number of different definitions. In R.F. circuits it is used as an indication of the bandwidth over which the required amplification of the stage can be obtained.

So far as valve characteristics are concerned the requirement is that the ratio of slope to interelectrode capacitance shall be as favourable as possible, so that each mA/V of slope shall be obtained at the lowest possible cost in capacitive loading. In practical valve design a favourable ratio is achieved by pushing up the slope to a high value, even though the means used to achieve a high slope may, in fact, also produce some increase in capacitance.

High Slope

The slope of a valve is determined very largely by the control grid. It is a measure of the efficiency with which the grid controls the flow of electrons. A relatively "inefficient" grid can be found in the television picture tube, in which the grid (a plate with a simple circular hole) requires something like -100 volts to reduce a current of two or three hundred micro-amps to zero. The slope of a C.R.T. may be of the order of $50\mu\text{A/V}$, which is sufficient for its purpose.

At the other extreme is the Mullard E180F, which is an R.F. pentode for use in wideband amplifiers in telephone carrier systems, radar

This article first appeared in Mullard "Outlook" and will be of especial interest to readers living in the fringe areas of television transmitters.

sets, and measuring equipment. A 40mA anode current is reduced to zero by only -3 volts, and the slope at working point is 16.5mA/V. The E88CC, a double triode for use in cascode circuits and as a multivibrator and cathode follower in computers, has a slope of 12.5mA/V. A similar slope is given by the PCC89, a new double triode cascode R.F. amplifier for television receivers.

Frame Grids

The three types just mentioned achieve their high slopes (and high figures of merit) by means of the frame grid. An efficient grid implies a small grid-to-cathode spacing, and a close mesh of very thin wires. Broadly speaking, the smaller the grid-to-cathode gap, the higher the figure of merit. Thus the problem becomes a question of structural design.

A typical frame grid for a receiving valve consists of two stout rods of molybdenum which are held rigidly apart by stiff cross-pieces. The dimensions of this frame are very closely controlled. For example, the main rods are drawn to size within limits of ± 0.005 mm. The grid wire is wound on the frame under tension (about 15 grams) and is anchored to the frame at each end. The tension of the wire is sufficient to maintain the accurate spacing of the windings. Gold-plating of the entire structure may be used as a precaution against grid emission.

Parallel Meshes

A frame grid thus consists of two exactly parallel flat meshes of taut wire. The grid is threaded over the cathode in the usual way. Since the distance between the two meshes can be accurately predetermined by a suitable choice of rod size, the clearances between the meshes and the two faces of the cathode are also accurately controlled. The flatness and rigidity of the meshes allow very small grid-to-cathode clearances to be used; and the thin wires (which in a normal grid structure would not be self-supporting) allow the grid to have the greatest electrical effect with the least physical obstacle. High slopes are possible without risk of grid-to-cathode short-circuits. Also the valve characteristics are better determined than would otherwise be possible.

The input capacitance of the valve may be higher with this technique; but the great increase in slope more than outweighs it, and an increased figure of merit is obtained.

Structural Accuracy

Accuracy in the grid structure implies, of course, accuracy in other components—notably the cathode and the spacing micas. Much use is made in frame-grid valve manufacture of optical techniques, such as assembly and inspection under the microscope, and projection of large images of components on to a carefully dimensioned blown-up drawing.

When frame grid valves are used in R.F. amplifiers, frequency changers, and I.F. stages, their greatly improved characteristics result in a substantial increase in gain in each of the successive stages; therefore much more efficient front

ends can be built. A television front end with frame grids throughout can have an overall sensitivity which is six or eight times better than with ordinary valves.

In the normal reception areas a far better performance is obtained for a given signal at the aerial. There is also a reduction in the risk of sound-on-vision. In fringe areas the improved performance can mean that specially modified receivers and elaborate aerials will often be unnecessary.

Introduction of PCC89

Within the last few years, frame grid valves have become firmly established in a wide range of "professional" and industrial applications—computers, and so forth—where efficient and high-grade performance is a *sine qua non*. Mullard are now introducing the frame grid into the domestic television valve range.

The first frame grid valve for television is the Mullard PCC89—a double triode for use in cascode R.F. stages. It has a slope of 12mA/V, which is just twice the slope of the PCC84. In a practical tuner a noise factor of 5dB at 200Mc/s can be achieved; this compares favourably with 6½dB for the PCC84. The valve underlines all the well-known virtues of the cascode R.F. amplifier. In particular, it ensures a high signal level at the grid of the mixer, so that the noise generated in the frequency changer stage is of little significance.

Future Progress

The PCC89 is already being widely used in the latest receivers. Development work on other types, and on the improved circuits in which they will be used, is well advanced. Mullard hope

COMPARATIVE TABLE

	A	B	C
R.F. cascode amplifier	PCC84	PCC89	PCC89
Frequency changer	PCF80	PCF80	PCF86
First i.f. (sound & vision)	EF85	EF183	EF183
Second i.f. (sound)	{ EF80 { EB91	{ EF183 { EB91	{ EF80 { EB91
Second i.f. (vision)	{ EF80 { OA70	{ EF183 { OA70	{ EF80 { OA70

to be able to announce shortly a triode-pentode frequency changer, and also a pentode I.F. amplifier, each showing advantages of the same order as those given by the PCC89.

The introduction of frame grid valves into television receivers is a significant and substantial advance. It is the latest step in the course of continuous development which has marked the valve manufacturer and receiver design from the very beginning.

Circuit Comparison

The advantages provided by the frame grid can be illustrated by a comparison of two receivers having the valve line-ups shown as "A" and "B" in the table above. Frame grid valves are indicated by heavy type.

With a typical good quality tuner operating in

Analysing and Servicing TV Receivers

No. 12—ELECTROSTATIC DEFLECTION AND RECEIVER POWER SUPPLIES

will then be possible to use a magnetic tube without disturbing the oscillator wiring.

Faults in Electrostatic Receivers

There are still many experimenters using electrostatic tubes such as the VCR97 and other ex-government types with the Miller transitron timebases and this section will be of particular interest.

Non-linearity and Foldover.


Check the sync output condenser and resistor feeding into the generator suppressor grid. Check the flyback condenser fitted across the screen grid and suppressor grid of the generator, and the resistor from the suppressor grid to chassis. The above faults apply to both line and frame.

No Hold or Multiple Pictures.

Check the H.T. and generator valve and the charging condenser across the anode and control grid. Check the anode and suppressor grid resistors and, if the trouble still persists, alter the control grid resistors. If this fault appears on both line and frame after the set has been working satisfactorily, attention should be paid to the sync separator stage. A common complaint on the frame is multiple pictures with the top rolled over or the bottom rolled up (short bodies, no legs, large heads, etc). The charging condenser should be checked for loss of capacity first, then the feedback condenser. Vertical cramping all over the picture could be due to hum in the timebase.

Raster Darker on One Side Than the Other.

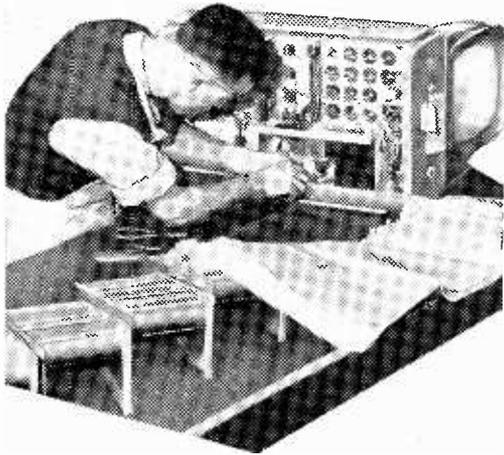If a push-pull output is used, such as 6SN7, etc., the two sections are not balanced. Check



IN the previous article the operation of a Miller Transitron timebase was described and a circuit given in Fig. 50. (See page 147 of the December, 1959, issue.)

For those readers who are contemplating changing over from an electrostatic to a magnetic tube, the negative going output from V1 is unsuitable for feeding into a line amplifier where scanning coils are employed. A positive-going output on scan is therefore required and it will be negative-going on flyback. Let us assume the output from V1 was fed into the grid of a line amplifier which employs scanning coils and flyback EHT. The output waveform at the amplifier anode would be positive-going on scan and negative-going on flyback. Because flyback EHT requires a positive-going pulse, this would be the wrong polarity and, apart from this, damage may take place to the line components. Therefore, at the amplifier input, the waveform must be positive-going on scan and negative-going on flyback and its output at the anode will be the reverse, namely, negative scan, positive flyback. However, there is no need to scrap the timebase. The positive-going output from the oscillator V1 can be achieved by transferring the width control and condenser C3 from the anode to the cathode circuit as in Fig. 52 and altering their values. This circuit will scan a 12in. tube. If a greater scan is required a phase reversing valve can be employed as given in Fig. 53. It

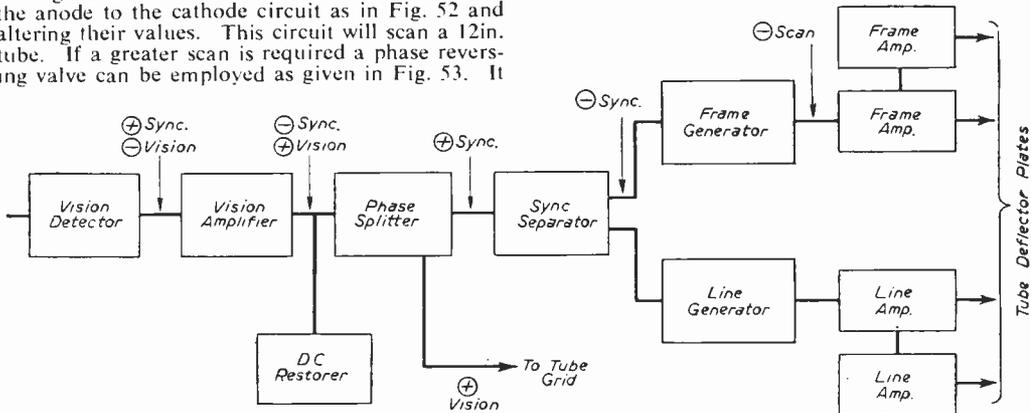


Fig. 51.—Block diagram of a receiver employing electrostatic deflection.

all the components in this stage. (Note that part of the raster may not be in focus.)

The Whole Raster Drifts Sideways.

The condensers feeding the tube deflector plates are leaky. These condensers must be perfect. Hum will also cause this fault; check the smoothing if the raster waves. Increasing the brilliance will sometimes remove the whole raster, leaving the screen blank.

Intermittent Interlace.

This may occur if the signal is strong or if the contrast is set at maximum. The fault is that the picture signal is breaking through to the frame generator. Check the sync integrating circuit feeding into the frame generator.

Prominent Flyback Lines.

Check the D.C. restorer diode and its components. Shadowing of the raster on the right can also be the cause of faulty D.C. restoration.

Hum and Waving Raster.

This fault is also common in home-built electrostatic receivers. Faulty or inadequate smoothing is the cause. This was more fully dealt with in the line and frame faults section.

Raster Collapsed to Line.

The frame timebase is at fault if the line is horizontal. If the line is vertical, the line timebase is not working. No particular component

No Raster, Only a Bright Spot.

Turn down the brilliance to save burning the tube face. Both the timebases are out of action. Check the H.T. and the L.T. supply.

Lack of width or Height.

Check the timebase valves for low emission,

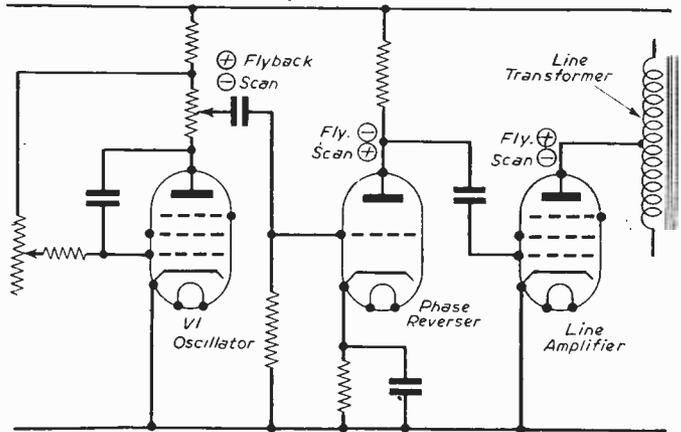


Fig. 53.—Incorporating a phase-reversing valve when changing from electrostatic deflection to magnetic deflection.

low H.T., excessive EHT, check the value of the charging condenser and the coupling condenser from the generator to the amplifier, examine the value of the anode resistors.

Picture is Left to Right.

Captions read as though viewed through a mirror. Reverse the connections to the two line deflecting plates on the tube.

Picture Upside Down.

Reverse the two wires feeding the frame deflecting plates on the tube.

The phase splitter is not likely to give any trouble and the rest of the electrostatic receiver can be serviced in the same way as a commercial magnetic model. A phase splitter with D.C. restorer suitable for an electrostatic working grid modulated tube was shown in Fig. 37 C.R.T. section.

The Power Supply

There is nothing unusual about a television H.T. and L.T. power supply. It is similar to a radio receiver A.C. or A.C./D.C. supply except that higher H.T. voltages were used in the older T.V. receivers and the current consumption was at least three times as much as a radio. To-day, with valves specially designed for A.C./D.C. work where the H.T. voltage is limited, the H.T. voltage has dropped to 200 or less and the H.T. current has risen even higher in some designs owing to the greater scanning power required on the line and frame for wide angle tubes. A typical power supply of about ten years ago is shown in Fig. 54. Many are still giving excellent service to-day owing to their reliability. C1 and C2 are optional, but they tune the smoothing choke L1 to a frequency of 100c/s. C3 is the


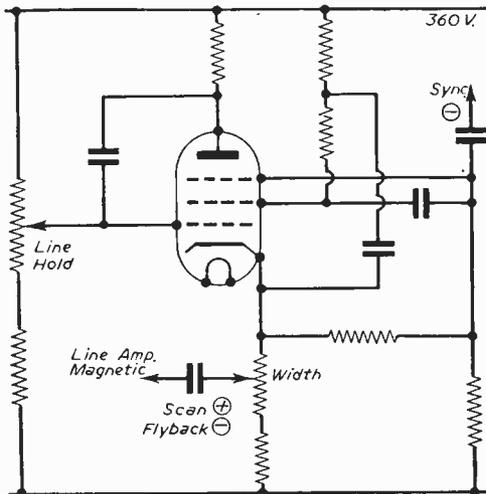


Fig. 52.—Miller transitron timebase.

can be pin-pointed here. Check the H.T. and valves first, the charging condenser and components generally. Keep the brilliance low.

Fig. 54.—A typical A.C. power supply.

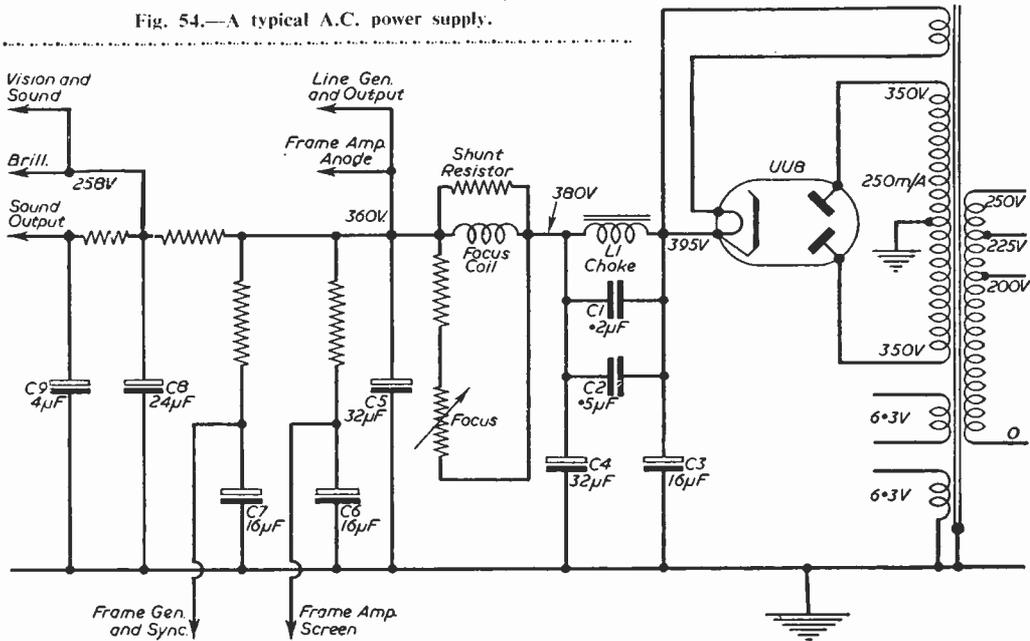

reservoir condenser and C4 and C5 are the smoothing capacitors. Notice the care taken to ensure adequate decoupling between stages to prevent any interaction or feedback along the H.T. line and to ensure a smoothed, ripple-free D.C. supply. The decoupling capacitors are C6, 7, 8, 9. The function of the focus coil has been discussed in a previous article. Transformer fed parallel heaters are shown in Fig. 55.

Auto-transformer

In Fig. 56 is the circuit of another type of A.C. supply; the transformer is auto-wound. The extension of the primary winding steps up the voltage to 350V and no H.T. secondary winding is therefore required, but the natural impedance provided by the secondary winding of Fig. 54 is missing. Therefore, to limit the peak cathode current to a safe value, surge limiting resistors must be fitted to the rectifier anodes, these are shown as R1 and R2. It will be noticed that the chassis is no longer isolated from the mains, a procedure which is now common practice. Figs. 57 and 58 show the present-day trend in H.T. and

L.T. power supplies. In Fig. 57, two rectifiers are used in parallel to give the required current output without being overloaded, although a metal rectifier can be used in this position if required (as shown dotted). In Fig. 58, a series heater

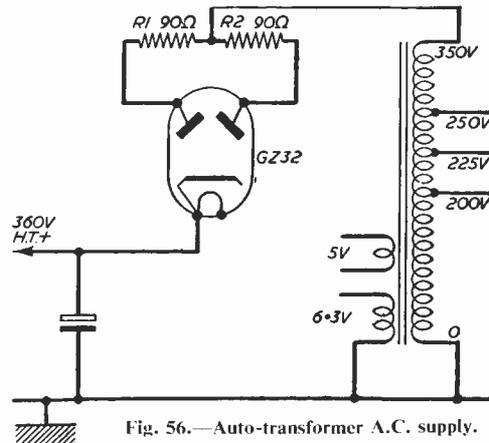


Fig. 56.—Auto-transformer A.C. supply.

arrangement with thermistor and mains voltage dropper is shown. The thermistor has a negative temperature coefficient of resistance and has the appearance of a 1W resistor. Its function is to limit surges; when it is cold its resistance has the high value of 4,800Ω, but, as the valves begin to draw current, the temperature of the thermistor rises and its resistance value falls until the valves are drawing 0.3A when the resistor value is 44Ω. This 44Ω must be allowed for when calculating the value of the mains dropper. The thermistor

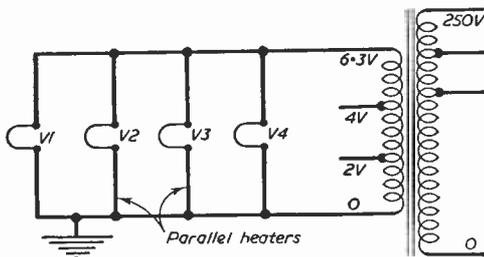


Fig. 55.—Parallel heater circuit.

nearly always has a shunt resistor across it, partly to cut down the time the valves take to warm up to their operating temperature and more important to prevent excessive current flow through the thermistor when first switching on. Valves with high heater to cathode insulation are always placed at the "hot" end of the chain and the valves with lower insulation such as detectors at the "earthy" end. The tube is placed at the

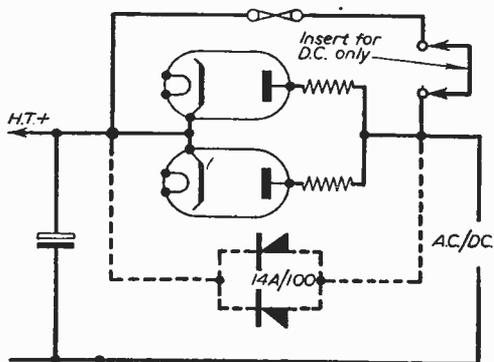


Fig. 57.—Using two rectifiers, which can be metal or valve types, in parallel.

earthy end of the chain in most receivers, but not in all. In the case of parallel heaters, never remove the video output valve with the set switched on, otherwise the tube cathode may receive voltage in excess of its rated maximum which is usually between 150V and 200V, but was only 50V to 100V in some of the earlier tubes.

It seems to be common practice to leave the set switched on while changing valves. In a series-connected heater circuit this is not a good practice; the set should be switched off before a valve is removed. In the case of an open-circuited heater, each valve should be removed in turn and its heater tested for continuity, or use a resistance meter along the heater chain with the valves in position until the break is found, with the set disconnected, of course.

When a break in the heater chain occurs as indicated in Fig. 59, although none of the valves are alight, a high voltage at nearly mains potential will be present at the heaters of the four valves on the right as no current is being consumed, and as some of their cathodes are at or near earth potential, the strain of 200V or more between heater and cathode is inviting further valve breakdowns.

The surge limiting resistors referred to in Fig.

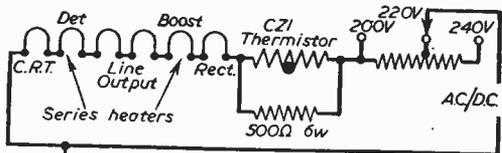


Fig. 58.—Series heater wiring including a thermistor.

56. are ordinary resistors and should not be confused with the surge limiting resistor of Fig. 58.

No Valves Alight in A.C./D.C. Heater Chain

After examining the fuses check the heaters for open circuit or high resistance and the thermistor for the same fault as it may be damaged. In some circuits, the thermistor may be shunted with a resistor which may have gone open circuit and the mains dropper should also be checked. If some of the valves light up very bright and others seem dead, check the adjacent valves in the chain for heater to cathode shorts and examine the heater by-pass condensers for shorts. If all the valves light up, but certain parts of the set refuse to work, see that both heaters of any twin valves are alight (valves such as the EB91, 6SN7, B36, and H.T. rectifiers, etc.).

Tracing H.T. Faults

When a receiver is known to be working correctly, before switching on take a resistance reading across the H.T. line at the rectifier and other H.T. points if you wish, the black or negative test prod to H.T.+ of course, and the red or positive prod to chassis. The reading may take a minute to settle down. Switch on and check the H.T. current consumption at the rectifier cathode and also the voltage at the same point and keep these readings for reference. When a fault occurs such as lack of height and lack of width, check the H.T. voltage and if it is found to be low, measure the current consumption and if it is higher than previously measured, switch off and measure the resistance as above. If it is lower than expected there is a leakage somewhere. More often than not a condenser is faulty and

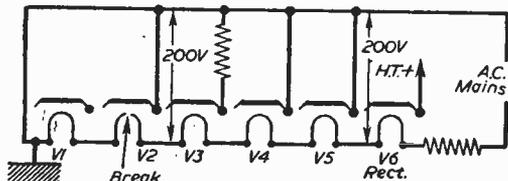


Fig. 59.—An open-circuit heater chain.

replacement will reduce the consumption, raise the voltage and probably save unnecessary valve buying. Here are a few examples.

Low H.T. volts, Low Current Consumption, Resistance Normal

The fault is low emission of the rectifier or dried up reservoir capacitor.

Low H.T., High Current, Resistance Normal

Check valve current consumption, especially the oscillators and line output valve. Line output valves not oscillating properly or receiving sufficient drive from the previous stage (if a separate generator is used) will consume excessive current thereby causing a voltage drop. Check also for soft valves.

(Continued on page 185)

EHT Supplies

No. 3.—INDEPENDENT SUPPLIES WITH PULSE OPERATION

(Continued from p. 120 of the December, 1959, issue)

By W. Cleland

LAST month's article dealt with obtaining EHT from the line output circuits of the TV receiver, but in some sets, EHT generation, although on the pulse principle, is made the work of a separate valve, and the damping arrangement used in the line output circuit is not duplicated in the EHT generator. As a result, instead of a series of pulses, there is a series of bursts of decreasing oscillations. If these are synchronised with line frequency, the repetition rate will be 10,125c/s, but it is possible to employ some other frequency.

Because, owing to the absence of a damping diode, the oscillations are not abbreviated to single fly-back pulses, the inverse voltage on the EHT rectifier is nearly twice as large for the same EHT voltage. On the other hand, the negative half-cycle can be used, with an additional rectifier, for voltage doubling, although it is of lower amplitude than the initial positive half-cycle of the burst of oscillation. The succeeding half-cycles cannot be used as they are of still lower amplitude, and will not make the rectifiers conduct, so their energy is lost.


Anode Coil

The anode coil used in this type of circuit may be described as a choke, that is, a coil with a high L/C ratio, but it will be necessary to connect the anode to a tapping on it, and to use a step-up ratio, in order to avoid exceeding the peak pulse rating of the valve.

As a separate pulse circuit does not have to supply a precisely defined current wave for scanning purposes, the grid input waveform can be varied. The requirements are that the valve should be switched on for a period to enable the current in the anode coil to rise to a high value, and then suddenly switched off, leaving the anode circuit free to produce its train of diminishing oscillations. If a saw-tooth input is used, the length of the conducting period will depend upon the value of grid bias and upon the amplitude of the saw-tooth, but the current in the choke will not be a complete saw-tooth wave as with a line-output circuit. Instead, it will consist of a saw-tooth pulse followed by a sinusoidal wave which will have subsided by the time the next saw-tooth pulse arrives.

Current Surge

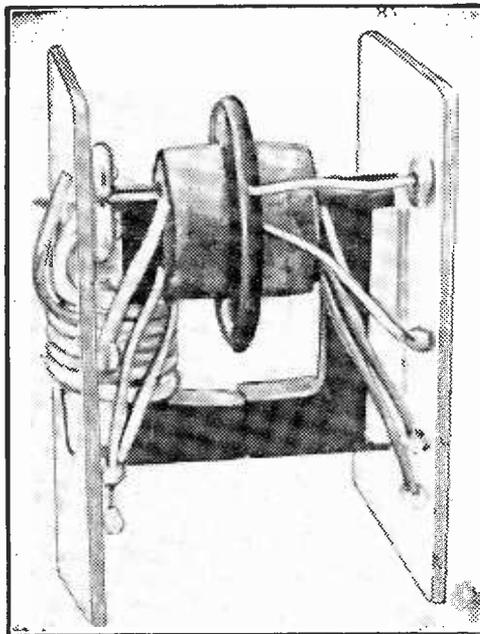On the termination of a saw-tooth pulse, the current of the inductance surges at an increasing rate into the stray capacitance until a peak voltage is reached at zero current, many times larger



A home-constructed line-output transformer.

than the initial voltage drop across the circuit when the energy was being supplied.

Each succeeding peak of the oscillation is smaller than the preceding one owing to circuit losses, but as only the first positive and first negative pulses can be used, the circuit does not require a high Q-value.

The value of EHT potential produced will depend upon the peak current reached in the anode circuit, and can be varied by applying bias to either the control grid or screen grid. Regulator circuits can thus be added without difficulty, deriving the control voltage either from the EHT output itself via a potential divider, or from a separate rectifier working at a lower voltage. The regulator circuit is made more effective by subtracting a fixed reference voltage, so enabling the control circuit to tap a higher proportion of the variations occurring in the EHT output.

Insulation

Air ceases to be a good insulator when the humidity is high, or when ionisation occurs in regions of steep potential gradient, e.g., in the neighbourhood of a pointed electrode. An EHT unit is more reliable when air as an insulator is supplemented by other materials, especially if dust accumulations and the ingress of moisture can be prevented.

When very high voltages are required (e.g., 25kV for a projection receiver), the coil, rectifiers and condensers are immersed in petroleum jelly, and special precautions are taken to exclude moisture. Damp conditions always involve risk when a line transformer is not adequately protected, and if persistent sparking occurs it may be necessary to apply a suitable insulating paste.

Breakdown

Dielectric breakdown is thermal in nature. The heat losses increase with voltage and with frequency, making low-loss material necessary, especially at radio frequency. Breakdown is more liable to occur after a television set has been switched on for some time and has become heated. A breakdown might only be a small puncture of the insulation, but sparking at this point will prevent the peak voltage from being reached. Occasionally more extensive damage can occur.

Care has to be taken not to apply excessive H.T. voltages to EHT units, as the margin of safety for a line output transformer or R.F. coil, and for EHT rectifiers, is not very large, and the production of an excessive EHT potential invites considerable risk of component failure. Conditions under which this mistake is likely are an experimental arrangement, with only part of the receiver on the supply. The lightly-loaded H.T. line will then be at a higher voltage than normal.

Screening

Because of the likelihood of producing radio interference, line output stages and EHT units should be in screened compartments. Adequate spacing has to be provided, and sufficient insulation to avoid the bluish haze called corona which makes it easy for brush discharges to occur. (This is accompanied by the smell of ozone.) It is not at all beneficial to breathe large amounts of ozone as it is poisonous. It is in fact, a powerful chemical agent, which can cause the breakdown of insulating materials.

Brush discharges and sparking cause radiation of noise and may affect the picture. The picture will also be very much impaired if a break should occur in the fine wire lead from the EHT

coil as the EHT voltage may still be produced, but with sparking occurring at this point.

Corona

The bluish haze of corona can be seen in the dark around high voltage conductors, even when these are too well insulated for arcing to occur. Ions in the air are accelerated to collide with molecules, so producing further ions. The effect increases with frequency.

EHT Measurements

Instruments for measuring EHT voltages, have to impose little or no additional load at the setting at which the reading is taken, as any appreciable current drawn would result in a low reading. An electrostatic voltmeter is the closest approach to the ideal, drawing no energy from a direct voltage supply except for leakage, and the small initial surge during the movement of the pointer. Meters of this type have a simple construction consisting of a moving vane swinging between fixed vanes, plus an air damping arrangement. Their application, however, is limited to potentials below 10kV, because of corona formation. Special electrostatic voltmeters, on the attracted disc principle, are used for higher voltages, but are unlikely to be used in servicing television receivers.

Standards have been laid down for measurement by spark gaps, but are intended principally for 50c/s alternating voltages (up to 900kV) much higher than the EHT direct voltages used in television sets, at which the lengths of the spark gaps are too small to give readings of high accuracy. A gap of about $\frac{1}{16}$ in is all that can be expected at 12kV, and to read this with accuracy calls for micrometer precision. Moreover, the

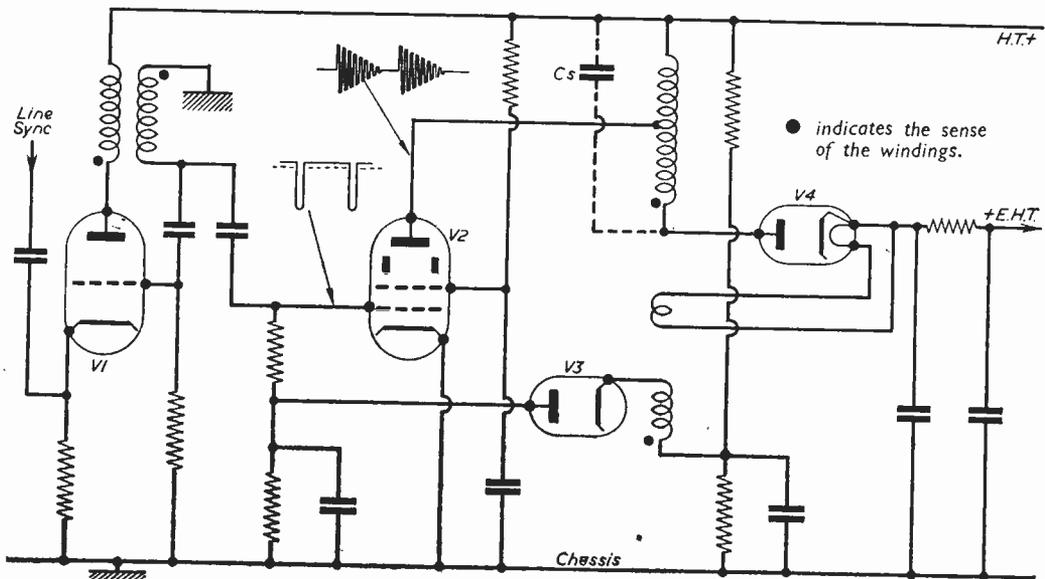


Fig. 9.—Pulse-type EHT supply. A series of negative pulses from the blocking oscillator, V1, releases burst of free oscillation in the anode circuit of V2. The regulation is improved by V3 which supplies a control bias to V2 from a separate winding.

electrodes must be perfectly clean. Grease or moisture on their surfaces will cause large errors. A resistance (of about 1 kilohm per kilovolt) should be used in series with a spark gap to limit the maximum current, although the use of a very high resistance would reduce the current of

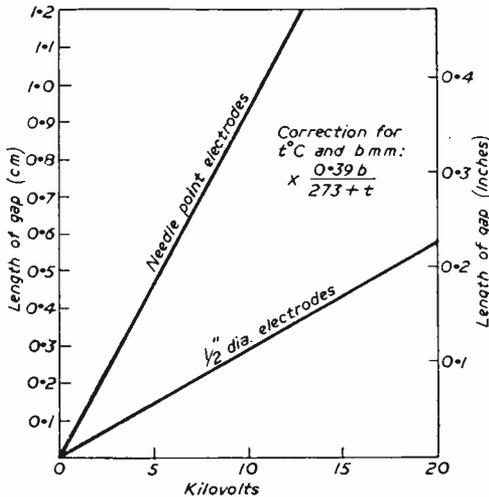


Fig. 10.—Spark gap lengths in air at 760 mm. Hg pressure and at 25 deg. C.

the spark too much and make it almost invisible. The resistance should be long enough to avoid flash-over.

Needle Points

The gap for a given voltage may be increased more than three times by replacing the sphere electrodes by needle points, but variation in the sharpness of the points gives rise to errors, in addition to the instability caused by the formation of corona owing to the concentration of the charge at the points. Sphere gaps are more reliable, although also affected to as much as 5 per cent. in setting by daily changes in air pressure and temperature. Accurate measurements can, however, be made by applying corrections for these.

Another instrument which draws very little current is a vacuum tube voltmeter fed from a potential divider. This requires a very high series resistance which is reliable at high voltages. A suitable resistance costs several pounds, and the cost is increased by the need for it to be housed in an insulated probe. The unusually high cost of such resistances is due to the difficulty in manufacturing them, since their long tracks of thin resistive coating must be uniform and trustworthy. The voltage drop along them has to be uniform, and the resistor has to be able to withstand surges.

Home-made Resistances

A home-made resistance of the pencilled-line type will burn out with a few surges, and it is difficult to know how much reliance can be placed upon improvised resistors such as a batten

of dry wood with two nails driven into it, or a length of ferrite rod of a certain grade.

Measurements at a few kilovolts with a current of, say, 1mA can, of course, be carried out by using a number of ordinary precision resistors in series with a milliammeter as the load on the supply. If a microammeter is used, it may be wise to protect it against surges by connecting a large capacitance across it.

There is also the possibility of measuring the actual pulse voltage at the anode of the EHT rectifier, which will be approximately equal to the rectified voltage. The most practical method would be the use of a capacitive potential divider with a very small series capacitance, feeding a high impedance indicator such as a vacuum tube voltmeter. A neon lamp could be used, the capacitance across the lamp being a variable one adjusted until its value is just high enough to extinguish the lamp.

Rectifier Anode Measurements

Owing to the high leakage inductance of the EHT winding in a line output transformer, the rectifier anode connection is very sensitive to any increased capacitive loading, and there is also the possibility of introducing feedback and radiation. It is doubtful whether accurate measurements could be made by this method except with a very small series capacitance.

A good picture of adequate brightness is usually accepted as indicating that the EHT voltage is correct, and with experience a spark drawn by a well-insulated screwdriver can provide a rough check in doubtful cases.

Books Received

THE TELEVISION ANNUAL, 1960. Edited by Kenneth Baily, 160 pp. 6in. × 9in. More than 170 half-tone illustrations. Published by Odhams Press Ltd., Long Acre, London, W.C.2. Price 10s. 6d.

This latest edition of the Television Annual follows the same popular style as its predecessors. Many popular television personalities have contributed articles and there are pen-portraits of many others. The book is lavishly illustrated, presented artistically and should prove popular with all television viewers.

TV REPAIR AND MAINTENANCE. By Robert Hertzberg. Published by Fawcett Books, Greenwich, Connecticut, U.S.A., and available from Frederick Muller Ltd., Ludgate House, 110, Fleet Street, London, E.C.4. 144 pp. 6½in. × 9½in. Price 5s.

This is an American publication and is written in the chatty style popular in the U.S.A. Naturally, it is written from the American point of view and thus not completely applicable to British television, particularly the sections on the television signal and line and frame scanning. The sections on V.H.F. TV will also be unfamiliar, but nevertheless much TV servicing practice is common to both sides of the Atlantic and the book, which illustrates almost every procedure mentioned, will be of use to many enthusiasts.

Making Television Aerials

PRACTICAL DETAILS OF YAGI ARRAYS

By R. E. F. Street

THE function of a receiving aerial for television is much the same as that of the aerial used for reception of sound broadcasts on the domestic radio receiver; namely, to collect a strong enough signal to operate the set satisfactorily. Of course, the situation is somewhat different on the medium and long waves commonly used for broadcasting; signals travel

the brightest parts, or areas of good reception being nearest the transmitter. Those parts in shadow, behind a hill, mountain, or other large object, are out of sight of the transmitter, and there, reception is either impossible or extremely difficult.

Signal Strength

Many different kinds of aerial are employed for television reception and which type is employed in a particular location depends largely upon the strength of the signal received there. In general, the stronger the signal, the simpler the aerial. However, it is not possible to prophesy which type of aerial will be the "best" one for a given location as so much depends on local conditions. This fact is often illustrated; sometimes an indoor aerial suffices in one house while across the road a five element array is required to secure an acceptable picture. Thus, the selection of the aerial is only possible by a combination of experience, trial and error. This

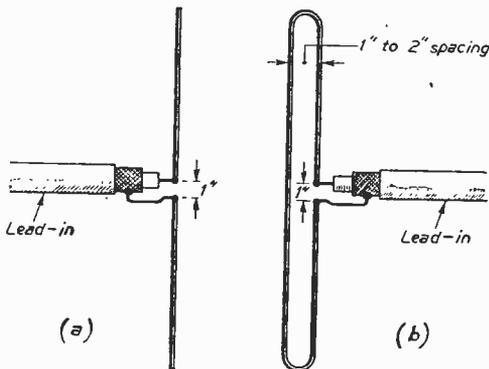


Fig. 1a (left).—The construction of a simple dipole.
Fig. 1b (right).—The construction of a folded dipole.

large distances and are still easily picked up by a simple aerial such as a short length of wire. However, on the short wavelengths, or high frequencies, used for television, the signals do not travel so far and consequently more efficient aerials are required for television than for ordinary broadcast reception. As the frequency employed is raised, the range of the transmitter tends towards what is known as the "optical" range. The meaning of this expression is clear if one imagines that the transmitter is replaced by a very powerful light: all the area illuminated receives signals,

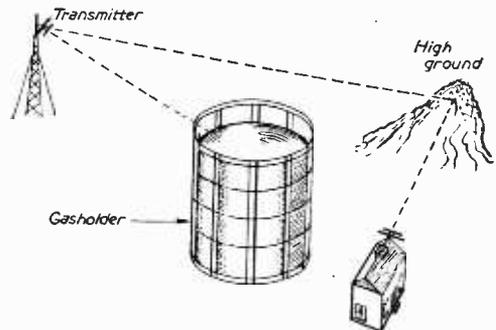


Fig. 3.—If there is an obstacle between the transmitter and the receiving aerial, a reflected signal can sometimes be utilised.

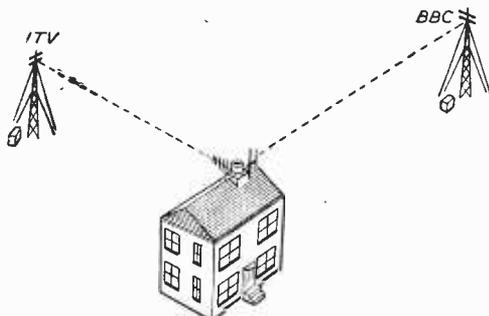


Fig. 2.—Yagi aerials are directional and must be pointed towards the transmitter.

fact is rarely appreciated and should therefore be noted carefully.

For first experiments, at least, therefore, the aerial design selected must be such that the aerial can be modified to give better results if necessary. A design which fulfils this requirement is the Yagi aerial, named after a Japanese engineer who carried out much of the early work on this type of aerial. Yagi aerials are often termed "arrays" and vary in complexity from the two element (BBC "H" aerial) to the 9 or 10 element (ITV "toast-rack") type.

Dipoles

When discussing Yagi aerials, it is necessary to know what is meant by a dipole. A simple dipole

is therefore illustrated (Fig. 1a) and consists of two lengths of metal rod or tube separated by a gap of about one inch. The connections to the downlead are made as shown. The cable illustrated is known as "coaxial" cable. This name is derived from the construction of the cable; the outer braiding forms a tube of conducting material around the inner wire which is therefore coaxial with the braiding. Most television receivers have a coaxial socket for the aerial lead and are intended for use with this type of cable. It is important to use cable having a characteristic impedance of around 80ohms, although the meaning of this term need not concern us here.

Aerials and receiver aerial inputs possess a characteristic impedance, too, also measured in ohms. It is necessary that the impedances of the aerial, cable and receiver are approximately equal for satisfactory operation. Now, the impedance of a simple dipole (Fig. 1a) is around 80ohms and therefore matches the coaxial feeder. The manufacturer of the set adjusts the input impedance to about 80ohms and thus the condition given above is satisfied the aerial matches the cable and the cable matches the set.

Folded Dipoles


However, as the aerial becomes more complicated and develops into a "toast-rack", the impedance of the aerial becomes lower and no longer matches that of the

TABLE Ia.—BBC TELEVISION TRANSMITTING STATIONS

Channel	Station	Frequencies (Mc/s)		Effective Radiated Vision Power (kW)	Polarisation
		Sound	Vision		
1	Crystal Palace	41.50	45.00	200	V
	Divis	—	—	12	H
2	Holme Moss	48.25	51.75	100	V
	Dover	—	—	0.25-1	V
	North Hessary Tor	—	—	1-15	V
	Truleigh Hill	—	—	0.2	V
3	Rosemarkie	—	—	1	H
	Kirk o' Shotts	53.25	56.75	100	V
	Rowridge	—	—	1-32	V
	Norwich	—	—	1-10	H
4	Blaen-plwyf	—	—	1	H
	Sutton Coldfield	58.25	61.75	100	V
	Sandale	—	—	16	H
	Folkestone	—	—	0.007	H
5	Les Platons	—	—	1	H
	Meldrum	—	—	4-17	H
	Wenvoe	63.25	66.75	100	V
	Pontop Pike	—	—	12	H
	Douglas, I.O.M.	—	—	0.25-2.8	V

TABLE Ib.—ITV TRANSMITTING STATIONS

Channel	Station	Frequencies (Mc/s)		Effective Radiated Vision Power (kW)	Polarisation
		Sound	Vision		
8	Burnhope	186.27	189.75675	100	H
	Lichfield	186.25	189.75	200	V
9	Black Mountain	191.230	194.74325	100	H
	Croydon	191.27	194.75675	120	V
10	Winter Hill	191.25	194.75	100	V
	Black Hill	196.2395	199.7305	475	V
	Emley Moor	196.2605	199.7372	200	V
	St. Hilary	196.2395	199.7305	200	V
11	Chillerton	201.25	204.75	100	V
	Down Mendlesham	201.23	204.74325	200	H

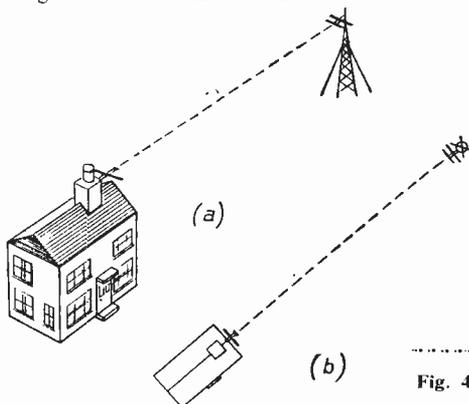

cable. The aerial impedance has to be increased and this is achieved by employing a "folded" dipole (Fig. 1b) which consists of a metal rod or tube bent so as to form a flat loop. A gap of about 1in. is left between the ends (to which the coaxial cable is connected as shown). The distance between the sides of the loop is about 1in. to 2in. as is also indicated in Fig. 1b. The impedance of a folded dipole is four times that of a dipole and thus if an array is made in which the impedance of the dipole is lowered to 20ohms, folding the dipole increases the impedance to 80ohms and thus matches the cable. It should now be apparent why "H" aerials use a simple dipole and

Fig. 4.—Unlike vertical dipoles, horizontal dipoles are directional and need to be positioned broadside on to the transmitter.

multi-element arrays a folded dipole; it is to ensure that the dipole impedance matches the cable impedance.

Aerial Dimensions

The length of the various elements employed in a Yagi aerial depends on the frequencies at which it is to be used; the higher the frequency, the shorter the elements become. ITV stations operate in Band III on frequencies considerably higher than those employed by the BBC which lie in Band I and thus ITV aerials are not so large as BBC aerials. This difference in size enables more complicated arrays to be used for ITV reception because the larger the aerial, the more difficult it is to support it; the weight of a multi-element BBC aerial is so great that only very rarely can even a three element type be erected and supported from a chimney stack while the mounting of even a ten or twelve element ITV aerial is comparatively easy. As was previously stated, the higher the frequencies employed, the shorter the range of the transmitter and the more complicated the aerial required. Thus, luckily, where the complicated arrays are required (on the higher frequencies) it is easier to construct them.

Polarisation

One more factor needs to be taken into account; the polarisation of the waves from the transmitter. This governs whether the receiving aerial needs to be placed with the plane of the elements vertical or horizontal. The quickest way of determining the correct mounting is to inspect the aerials on your neighbours' houses to see whether they are horizontal or vertical. Table I gives details of the BBC and ITV transmitters and the polarisation is indicated; V for vertical and H for horizontal.

Aerials are often said to be "directional." This means that, when mounted, they have to be moved or rotated until the signal received is as strong as possible. Generally, they are then pointing towards the station (see Fig. 2) but, sometimes, a signal is reflected from an obstacle and this reflected signal is stronger than the direct signal and then the aerial is pointed to receive the reflected signal (see Fig. 3). It should be noted that a simple, vertical, dipole is not directional and receives signals equally well from any direction. However, a horizontal dipole is directional and must be arranged for best reception, generally broadside on to the direction of the station (see Fig. 4). It must be stressed that arrays do not necessarily have to be pointed direct at the station; much depends on local conditions and the only method is to move the aerial to point in different directions until best results are obtained.

Type of Array

It is often stated that to secure good results in fringe areas or areas of weak signal strength, it is necessary to use the most complicated array that can be devised. This is rarely the best policy; as the array becomes more complicated, its length increases and approaches a wavelength. Reflection effects become more troublesome and

better results may be obtained with a simpler array. In difficult situations, moving the array a few feet, or raising it slightly, will often enable a good picture to be obtained.

It should now be clear that in areas known for their poor reception, and in other districts too, the best way of obtaining good results is trial and error. Although the difficulties may seem formidable in the light of what has been said above, in the majority of instances there is no difficulty in obtaining good results at the first attempt.

Construction

The materials used in the construction of the aerial depend on the location of the aerial; near the transmitter, the crudest materials—wire and wood—suffice, while where signal strength is low, and every precaution must be taken to prevent loss of strength, better quality materials must be employed. Copper-plated rod can often be purchased cheaply and the "real thing"—aluminium or duralumin rod or tube—may be

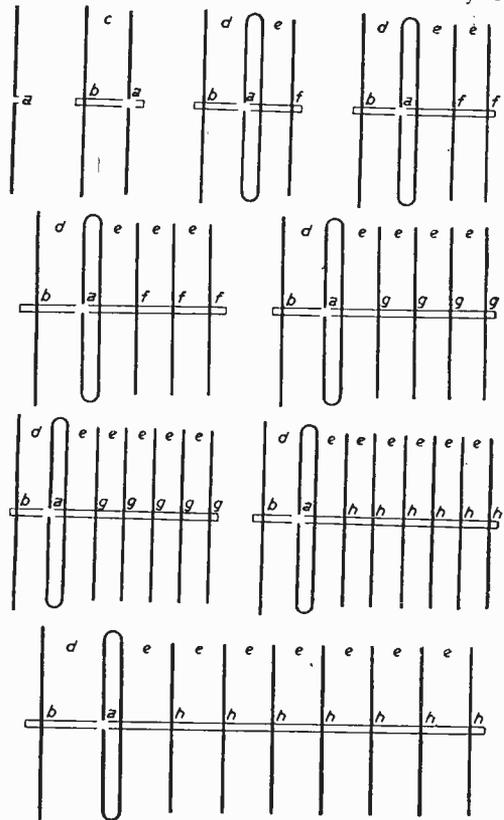


Fig. 5.—Various aerials ranging from a simple dipole to a 9-element Yagi. The letters "a" to "h" refer to the lengths of the elements or to their spacings, e.g., "a" is the length of the dipole, "b" the length of the reflector.

As it is not practicable to construct multi-element BBC aerials, dimensions "g" and "h" for channels 1 to 5 are not given in the table on the next page.

used for ambitious arrays. If the array is to be used outside, then, of course, construction is more difficult as the insulation needs to be good and the array must weather any storms, etc. On the whole, it is advisable for the majority of amateurs only to construct indoor aerials as, without extensive facilities, the construction of sound, outside aerials is extremely difficult, tedious and often disappointing.

In Fig. 5 are illustrated various types of Yagi aerial with their dimensions indicated by letters. Table II gives the dimensions required for reception of the various BBC and ITV stations. It

the transmitter. The elements progressively added in front of the dipole are called directors and increasing their number increases the signal picked up and makes the array more directional. Adding more reflectors, however, is found to make little improvement and thus only one is used, even in the nine-element array.

Insulation

The various elements do not need to be insulated from the supporting cross bar, provided they are mounted or bolted at their mid-points. The cross

TABLE II.—DIMENSIONS OF THE AERIALS ILLUSTRATED IN FIG. 5.

Channel	a		b		c		d		e		f		g		h	
	ft.	in.														
1	10	7	10	11	5	7	2	9½	7	7	9	9	*	*	*	*
2	9	2	9	8	4	10	2	5	6	7	8	5	*	*	*	*
3	8	4	8	9	4	5	2	2½	6	0	7	8	*	*	*	*
4	7	8	8	1	4	0	2	0	5	6	7	1	*	*	*	*
5	7	1	7	5	3	9½	1	10½	5	1	6	6	*	*	*	*
8	2	5½	2	7	1	3½	7¾	1	9½	2	3½	2	3	2	2	2
9	2	5	2	6½	1	3	7½	1	8½	2	2½	2	2	2	1½	1½
10	2	4	2	5½	1	3	7½	1	8	2	2	2	1½	2	1	1
11	2	3½	2	5	1	2½	7½	1	7½	2	1	2	0½	2	0	0

will be noted that no details are given of BBC aerials with more elements than three. As mentioned, such aerials would be very large and impossible to mount or accommodate.

Directors and Reactors

The illustrations in Fig. 5 proceed from a simple dipole, through the "H" aerial to complicated multi-element arrays. The element added to form the H aerial is called a reflector and, broadly speaking, it increases the signal from the aerial. In each case, the transmitter is assumed to be to the right of the array and the reflector is seen always to be the element furthest from

bar can be made of wood or metal depending on the weathering qualities required.

From the information given, it should be possible to construct an aerial suitable for most locations and the procedure is to choose the design from Fig. 5 and then to determine the dimensions from Table II. The dimensions have been calculated to give good results; it is very unlikely that they will be the same as those employed by commercial aerial manufacturers or those mentioned in other publications. This fact should be borne in mind if any comparisons of element lengths and spacings are made.

ANALYSING AND SERVICING TV RECEIVERS—(Continued from page 178)

Low H.T., High Current, Resistance Low

Leakages across H.T. supply, usually capacitors, or speaker transformer or transformers in the timebases have leakages from windings to core.

High H.T., Low Current, Resistance Normal

Could be high or open circuit anode and screen resistors or a transformer primary o/c.

The Fuses Blow on Replacement

It is futile to keep replacing fuses in a set that has an intermittent short circuit. This can be an expensive business. When this fault occurs, it is useful to know the correct circuit resistance. Check the resistance and if this is normal, the fault is probably arcing in the rectifier. If the rectifier is at fault, do not forget to check the anode surge resistors, if fitted. One of these going open circuit can cause one half of the rectifier to be overloaded. The same applies if two rectifiers are in parallel.

If lack of width is experienced, check the value of the surge resistors as they have been known to go "high" on load. If no short is apparent (resistance normal) with the set off, watch the valves carefully when warming up especially the line output or booster diode for arcing over. But if the resistance is very low or zero, it could be any coil, condenser, or transformer insulation breakdown causing a dead short to develop.

Pyramid Shaped Raster with Lines Wide Apart

Check the smoothing condenser for open circuit or loss of capacity.

Line and Frame Cramping

When this occurs in both timebases simultaneously the fault is nearly always low H.T. voltage or dried up smoothing capacitor.

When overhauling a receiver it is wise to check all resistors over the value of 100kΩ especially the ¼W type. These often increase in value; a 330k often rises to 1M and 1M rises to 2M. This increase is often the cause of that common fault of no line or frame lock.

FOLD-OVER

THE CAUSES AND CURE OF THIS FAULT WHICH IS OFTEN CONFUSED WITH INCORRECT LINE-LOCK

MANY of the letters we receive seeking our advice on faulty receivers refer to the faults of line and frame foldover. It is clear from this correspondence that the nature of these faults is not completely understood and this article was prepared to make matters clear.

Foldover is where the edge of the raster is folded back on itself like the fold of a curtain. In the line timebase it usually occurs at the left-hand edge and in the frame timebase at the top.

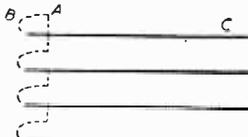


Fig. 1.—Section of raster showing foldover on line.

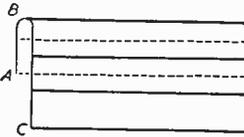


Fig. 2.—Foldover on the frame scan.

In order not to confuse the issue we will deal with the horizontal (line-scan) case first.

Appearance

The most obvious evidence of foldover is that there is a bright band of light on the left-hand edge of the raster. The bright band must not be confused with a bright line due to insufficient damping; in the latter case, the line exists at a point from the left-hand edge, while foldover exists from the very edge and inwards.

The width of the band varies with the degree of flyback delay and can stretch for an inch or more in bad cases to a mere strip in mild cases.

If the raster is observed closely, the edge will be seen to be folded back on itself like the fold of a curtain. Fig. 1 gives an enlarged view of a small section of the raster showing the fold.

The fault can be most easily recognised when a figure (or lettering) is entering from the left side of the picture. The figure will be seen to start from A, move to B (i.e., to the left) and then to the right towards C. In a picture not suffering from foldover, the figure would appear to start from B and move to C.

The movement from A to B is in reverse; for example, if the letter E was travelling across the screen from the right to the left (this is the usual direction of travel for wording), then it would appear as an E until it got to the left-hand edge and then would appear reversed as \exists as it travelled from B to A.

When foldover occurs in the frame circuit, the top of the raster is partially folded back, as in Fig. 2. In this case, supposing a letter Y was travelling from the bottom to the top of the

screen, then from C to B it would appear as Y, but from B to A it would appear upside down: λ .

Foldover must not be confused with cramping, though sometimes the two appear together. Cramping in the frame circuit, for example, would cause the Y to shrink suddenly as it got to the top, but would not cause it to start travelling back down the screen again upside down.

The fault must not be confused with false frame or line lock. There is a certain type of false line lock which makes part of the picture appear as a very much elongated wraith superimposed backwards on top of the main picture. Too fast a frame speed will give a somewhat similar condition, part of the picture being superimposed on the other part (example, the full figure of a man would appear as in two halves, the waist upwards being superimposed on the waist downwards so that his head appears between his legs!).

The cause of foldover is quite simple to understand. Let us consider a single line of picture: when the line is due to commence the bias on

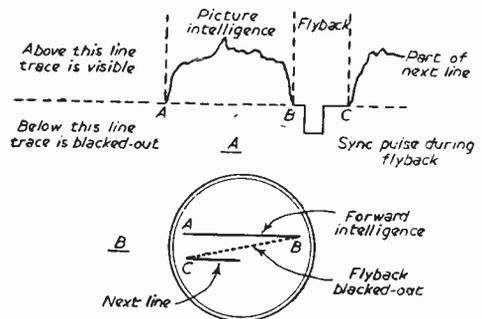


Fig. 3.—Waveform for one line.

the picture tube is reduced. The spot appears and moves from left to right, but we do not see it as a travelling spot but as a continuous line.

When the extreme right-hand edge has been reached the TV signal causes the bias on the tube to increase so much that the spot is blacked out. The line sync pulse is then applied and the line oscillator is triggered so that the blacked-out spot flies back to the left-hand side of the screen ready to start the next line. Fig. 3 shows the conditions existing for one line.

If the flyback time is longer than the duration of the blacked-out period, then the spot will not reach the left-hand edge before the intelligence of the next line is received.

(Continued on page 189)

BRAND NEW A.M.-F.M. (V.H.F.) CHASSIS AT £13.6.8. (P. & P. 10/-)



Why buy a F.M. Tuner at the same price ?
 Tapped input 220-225 v. and 226-225 v. A.C. ONLY.
 Chassis size 15" x 6 1/2" x 5 1/2" high. New manufacture.
 Dial 14 1/2" x 4" in gold and black.
 Pick-up. Extension Spaker. Ae. E., and Dipole sockets. Five " piano " push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested with all valves & O.P. Transformer. Tone Control Fitted.
 Covers 1,000-1,900 Mc. ; 200-500 M. ; 88-89 Mc/s.
 Valves E280 rect., ECH81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit chassis, 47/6.
 10" x 6" ELLIPTICAL SPEAKER. 20/-
TERMS :—(Chassis) £4.16.8 down—10% carr. and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.9.2 down and 7 Monthly Payments of 32/-.


We are specialists in I.T.A. Converters. Our converters give direct switching I.T.A. to B.B.C. metal rectifier. co-axial plug, can be fitted in 5-10 mins., and need no alteration to your set. ALL AREAS. ALL SETS. ALL CHANNELS. 12 months guarantee (3 months on valves).

"READY TO USE" I.T.A. CONVERTER


Separate gain controls. Valves PCF80 and PCC84. Switch positions I.T.A. (1)—I.T.A. (2)—B.B.C. Bakelite moulded cabinet 8 1/2" x 4" x 6". £5.5.0. P. & P. 3/-.



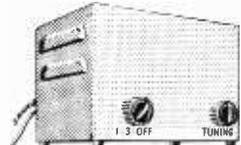For the last 200 I.T.A. Converters of this type (Brand New and Fully Guaranteed) we will accept the "Below Cost" figure of ONLY 60/- (3/- P. & P.) Reduced from £4.7.6.
 Two valves ECC81—grey hammer finish—Switch positions—OFF, I.T.A., B.B.C. Own Power supply. BUY IT NOW.




60/- (3/- P. & P.)

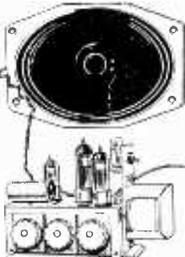

3-VALVE AMPLIFIER (INCL. RECT.). Capable of giving 6 watts. 8" x 5" Speaker wired-in. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size, 6 1/2" x 3" x 2 1/2".

Only 67/- (P. & P.)

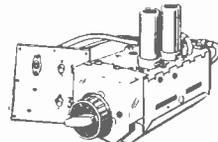THE BRAYHEAD TURRET TUNER. £7.7.0 post free. Complete with booklet and fitting instructions. State set and model no. when ordering. Converts your 5-channel B.B.C. only set to receive 13 channels.




I.T.A. AERIALS clipping to existing mast 1.2" dia. 3-element. 27' - 5-el. 35' - 9-el. 55' - Loft mounting. 3-el. 20' - 5 el. 27' 6" ; Combined single B.B.C. and 5-el. I.T.A.. 75' - with chimney lashings ; Co-axial cable semi-air-spaced, 8d. yd. or 20 yds.. 12/6. aerial and cable prices carr. paid.

NEW SWISS MADE ELECTRIC SHAVER for 200-250 v. A.C. or D.C. ONLY £5 (carr. pd.). Precision made by watchmakers. Rotary head, a perfect shave in 3 mins. This is the dual voltage model selling in Switzerland for 110 Fr. (£9).


50 SILVERED MICA AND CERAMIC CONDENSERS, 10/-, 50 RESISTORS, 5/-.

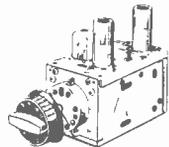A few 10 Mc/s **CYLINDR TURRET TUNERS** complete with contrast control panel and knobs. New and Boxed. Listed at £7.7.0. OUR PRICE £5. post paid. ONLY E10L, F10L and U10L are available.



BRAND NEW INCREMENTAL TURRET TUNER by famous manufacturer for 35 to 38 Mc/s with knobs. Valves PCC84 and PCF80, or valves UCC81 and UCF80. LAST FEW DOZ. REDUCED ONLY 40/-.

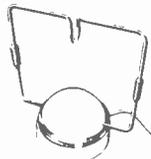
I.T.A. TABLE TOP AERIAL
 An I.T.A. cable top aerial with amazing performance. The Wolsey Hi-Q at 19/6 (2/6 post). Gives good reception up to 20 miles, and has cross-over unit in base with socket for B.B.C. aerial. Same model but very slightly tarnished for ONLY 12/6 (2/6 post).



PERSPEX UNSCRATCHED. (Post 2/- each or 6 post free.) 12" x 9 1/2" x 1" clear, 4/6; 14 1/2" x 11" x 1" clear, 5/-; 15" x 12" x 1" tinted, 6/-; 17" x 13 1/2" x 3/16" clear, 7/-; (Also 15" x 12" slightly scratched at 3/-.)

NEW PRE-SET WIREWOUND POTENTIOMETERS,—6 different values as used in modern sets. 10/- post paid.

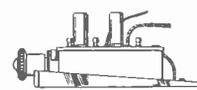NEW WAXED TUBULARS, 350 v. or above. 3 of each. .001 .002. .005. .01. .02. .05. .1. .5 mF. Total 24 for 5/6, post paid.



CHASSIS CONVERTER INTERNAL MOUNTING
 Specification as 5 gn. model above ; with leads for power supply, etc. Size 9" x 2" x 5" high. PRICE £2.17.6 (2/6 post). Power pack, fully wired with connection instructions, 25/- extra.

AUTOMATIC RECORD CHANGERS. COLLARO CONQUEST with manual play also. Turn over crystal pick-up, 4-speed, A.C. mains 209-253 v., see illus.



£7.10.0 (5/- P. & P.)

NEW CAN TYPE ELECTROLYTICS

40-40 mF. 300 v. (1 1/2" dia.)	2/6
40 mF. (300 v.)-40 mF. (150 v.)-8 mF. (150 v.)-(1 1/2" dia.)	2/9
100-200 mF. 275 v. (1 1/2" dia.)	5/6
100-200 mF. 350 v. (2" dia.)	7/6
100-200 mF. 25 v. (1 1/2" dia.)	1/3
1 mF. 500 v. (Tubular)	1/-
100-400 mF. 275 v. (2" dia.)	7/6
400 mF. 250 v. (1 1/2" dia.)	3/6

Post 6d. on one. Two or more Post Free.

Delivery by return. C.O.D. 2/- extra. Terms : Cash with order or one-third down and balance plus 7/6 (up to £7.10.0) in four equal monthly payments. Balance over £7.10.0 add 1/- in £1 and pay in not more than 6 monthly payments. See special terms for A.M.-F.M. chassis. All new goods unless stated. Send 6d. for 16-page catalogue.

GLADSTONE RADIO 58A HIGH STREET, CAMBERLEY, SURREY. TEL. 22791
 or callers to 3 Church Road, Bristol. 5. Tel. 51207 (Camberley class. S. 10)

Let I.C.S. train YOU!



COURSES ON:—

- RADIO and TELEVISION
- SERVICING · ELECTRONICS


EXAMINATION COURSES FOR:—

- C. & G. Radio Servicing Certificate (R.T.E.B.)
- British Institution of Radio Engrs., etc.
- Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.
- C. & G. Radio Amateurs' Exam. (Amateurs' Transmitting Licence)

LEARN - AS - YOU - BUILD

Practical Radio Course

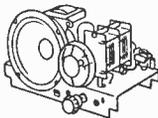- A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.
- Other Learn-as-you-Build radio courses are available




5-VALVE SUPERHET RECEIVER



RF/AF SIGNAL GENERATOR

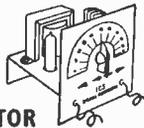MULTI-TESTER
(Sensitivity 1,000 ohms per volt)



Post this Coupon TODAY! for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

International Correspondence Schools
(Dept. 164B), Intertext House, Parkgate Road,
London, S.W.11.

Please send book on

Name and Address Age

Occupation I.60

INTERNATIONAL CORRESPONDENCE SCHOOLS

MAKE SOUND JOINTS SIMPLY BY USING Multicore

ERSIN MULTICORE

Contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON

5/-

HANDYMAN'S CARTON

Suitable for 200 average joints. 6d.



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SAVBIT TYPE 1 ALLOY

A specially formulated alloy to reduce the wear of soldering iron bits. Contains 5 cores of non-corrosive Ersin Flux and is ideal for all soldering purposes.



SIZE 1 CARTON 5/-

Available in three specifications.

HOME CONSTRUCTORS 2/6 PACK

In addition to the well-known Home Constructors Pack (containing 19ft. of 18 s.w.g. 60/40 alloy) a similar pack is now available containing 40ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits.



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruded flex 3/16 each



MULTICORE SOLDERS LTD.,
MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3686)

REGUNNED TV TUBES

Supplied from Stock and despatched by British Railways same day. COMPLETE NEW GUNS fitted in every tube and fully guaranteed for TWELVE MONTHS FROM DATE OF INSTALLATION.

	Mullard	Mazda
12 in.	£5.0.0	£5.0.0
14 in.	£5.0.0	£5.0.0
15 in.	—	£6.0.0
17 in.	£6.0.0	£6.0.0
21 in.	£8.0.0	£8.0.0

Carriage 5/- extra.

Other types available. Please contact:—

CLARKSONS (Tube Distributors)
120, Commercial Road, LEEDS 5
Phone: Leeds 56916

In Fig. 4 we have the conditions existing when the flyback time is prolonged and it will be seen that the flyback period extends into the next line. The practical result is shown in the tube face as in Fig. 4B.

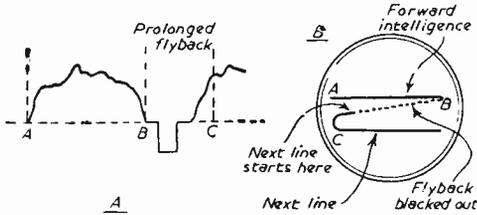


Fig. 4.—Waveform when flyback is late.

In the simple case the cure of the fault is obvious: reduce the flyback period by reducing the value of the condenser or resistance in the flyback circuit.

With electrostatic circuits this will usually effect a cure. With electromagnetic circuits, however, the fault is not so easy to remedy.

One common cause of the trouble in home-constructed circuits is the overdamping of the line coils. Fig. 5 shows a typical circuit, where C and R damp the oscillations which result from the return of the spot to the left of the picture. Too low a value of R or too high a value of C will overdamp the circuit and foldover will be experienced.

Critical Values

The value of C and R must be so chosen that neither overdamping nor underdamping is caused and for this reason R is usually separated into two parts—a fixed component and a variable component, the latter being labelled "Line Linearity."

Too little damping will cause the left-hand edge to be stretched and in the limit will show as a

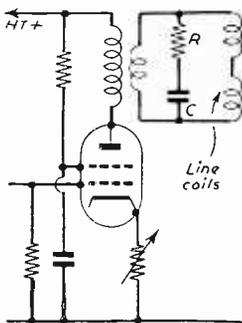


Fig. 5.—Line output stage with damping components.

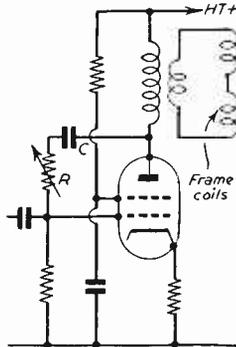


Fig. 6.—Frame output stage with feedback.

broad white band, set in a little from the edge of the picture.

Too high a bias on the output valve will also cause foldover. In this case the valve will not start its forward drive soon enough, due to over-biasing, and so picture intelligence will commence before the output valve becomes operative.

In this case the cure is to reduce the bias, but care must be taken in home-constructed circuits to check that this is the real cause and not to risk under-running the valve.

If the screening grid voltage is too low the results will be similar, but once again the position should be checked carefully. The screening grid of the output valve should not be run red-hot or the valve will be damaged.

Self-driven timebases can suffer from foldover, especially where the flyback pulse is used for production of EHT. It is essential to ensure that the valve is working on the correct portion of its curve to prevent foldover.

Where a circuit of this nature has been functioning satisfactorily previously then the development of foldover is usually due to a fall in emission of the valve, or a loss of voltage on the H.T. line.

Foldover at the Right

This fault is not so common as foldover at the left. When the fault occurs on the right it is usually accompanied by cramping.

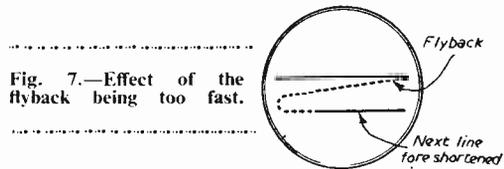


Fig. 7.—Effect of the flyback being too fast.

At the extreme right the output valve is delivering its maximum power. If the fault develops in what was previously a good picture, then the most likely cause is falling emission of the output valve.

In a newly-built circuit attention should be paid to the biasing of the output valve to ensure that the full drive is available.

The trouble can also originate in excess driver valve output, if one is used, or in the employment of incorrect values in the linearity circuit.

Where a recovery diode is used to supplement the H.T. it should be checked for loss of emission.

Foldover at the Top

Fig. 6 shows a typical frame output stage. Correction of linearity is usually effected by a feed-back circuit as shown by C and R.

When foldover occurs at the top, the valve is on the anode-cut-off portion of its curve and any variation due to low H.T. volts, incorrect bias, or loss of emission will cause the trouble.

The bias should be checked and if a new circuit has been built, then suspect overbiasing of the valve.

Too low a screen voltage will have a similar effect by shifting the operating point of the valve on its characteristic curve. Note also in this case that the screen voltage must not be made too high and it must never be run red-hot.

Foldover at the Bottom

Some correction here is usually gained by the linearity correction arrangements. The cause is similar to cramping at the top and the two faults often accompany one another.

Safety with Series Heaters

CIRCUITS FOR OPERATION ON A.C. OR D.C. MAINS MAY BE DANGEROUS UNLESS PRECAUTIONS ARE TAKEN

By J. Gray

BECAUSE of the large number of valves in a TV receiver, series operation of the heaters is often employed. The elimination of the mains transformer, and the isolation from mains currents which it provides when present, introduces a particular element of danger—that of the "live" chassis. Shocks from this cause are quite

With circuit "C" the chassis is safe to touch when the set is switched on, but becomes alive through the heater chain when the switch is opened.

At "D" the chassis is returned directly to the neutral main, and the switch is in the "L" side of the circuit. This method of connection affords maximum safety with a single-pole switch.

A double-pole switch is sometimes used, as at "E." When opened, this switch completely disconnects the receiver. But when the set is on, the chassis *can* be alive if the chassis side of the circuit changes to go to the "L" main instead of to neutral.

For these reasons, it is wise to use a non-reversible (polarised) plug, and in all cases the chassis can then be wired to the "N" main. Circuits such as those at "B" or "C" should also be modified, the switch being included in the "L" side of the circuit.

A single fuse is occasionally included, and if this has been included in the neutral side of the circuit in error, the receiver may be alive when the fuse blows, though it was safe with the fuse intact. A single fuse should thus always be in the same side of the circuit as the switch, that is, so as to disconnect the "L" main.

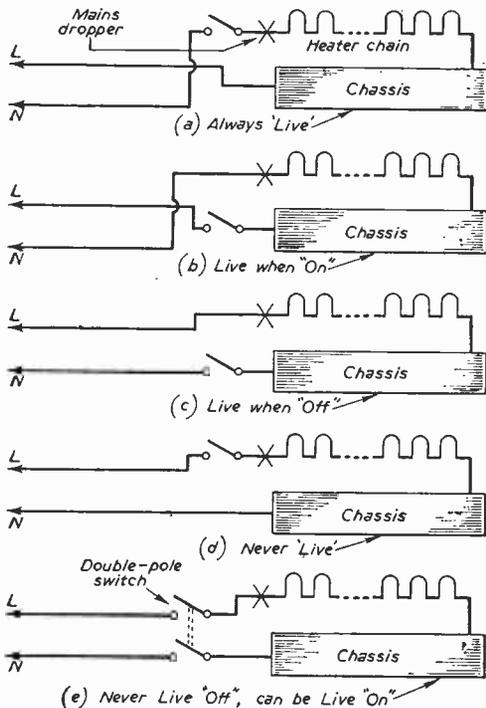


Fig. 1.—Results of various methods of connecting the mains.

likely when current is drawn from a reversible plug or adaptor, or if the on/off switch has been placed in the wrong side of the circuit.

Danger

Fig. 1 shows ways in which the switch, heater chain and chassis may be connected to the mains supply. At "A" the situation is at its worst, the chassis being wired directly to the "L" main, which is at mains voltage above earth. A mains shock can thus be expected if the chassis or any other metal parts fixed to it or connected with it are handled, even with the receiver switched off.

At "B" the switch is in the "L" circuit, as it should be, but is returned to chassis. With the switch open, the chassis is connected to the neutral main "N" via the heaters. But with the switch closed, the chassis is alive.

Other Precautions

It is not wise to assume that the correct mains connections will always be employed. A non-reversible plug may be removed and an adaptor or reversible 2-pin plug may be substituted. It will then be purely a matter of chance whether the receiver chassis is safe to handle or not. Or the power supply cord may be lengthened with twin flex by someone who ignores the correct method of connecting up the receiver. If so, the chassis may again be taken to the live main, as at "A" in Fig. 1.

For these reasons it should not be possible for the user to touch any metal item which is in

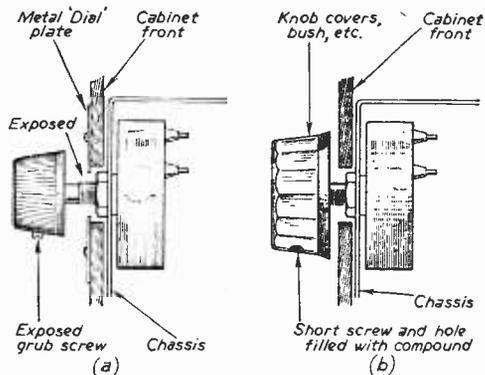


Fig. 2.—The danger of exposed metal parts.

contact with the chassis, or wired to it. It is not unusual for danger to arise at the control knobs, especially in home constructed sets. A metal indicator or dial plate may be used, as shown at "a" in Fig. 2, and may be in contact with the bush or holding nut of a component. If no plates are used, a small knob, or long spindle, may allow the fingers to touch the spindle, bush,

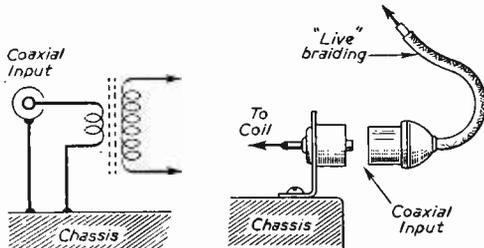


Fig. 3.—How the aerial connection may be "live".

or nut. Even if this is not possible, the grub screw may be insufficiently sunk, so that shocks are likely when operating the controls.

Precautions

These dangers can be eliminated by cutting down the spindle if necessary, and using a knob which fits near the panel, so that it is impossible to touch the bush, etc. A knob of this type is shown at "b" in Fig. 2. Spring-loaded knobs which grip a flat on the component spindle are best, but ordinary knobs are satisfactory if the grub screw is well sunk, and the hole filled with insulating compound. Metal indicator plates which

may be in contact with the component bush are not recommended in any circumstances.

A check should also be made that no other metal parts which may be reached from the outside can possibly be in contact with the chassis. Metal gauze used to cover a speaker opening may sometimes be in contact with the chassis, or with a speaker having its frame returned to the chassis. Brackets should not be fixed to the chassis to hold a back on the cabinet, or the bolt heads may be alive. It should, in fact, be impossible to touch any metal which may become alive when the receiver is correctly fitted to its cabinet, with the back in position.

Aerial Circuit

The danger of a live aerial connection is also sometimes overlooked, and the aerial may be returned directly to the chassis, as in Fig. 3. If a screened feeder with bare braiding is used, this error can be very dangerous. Both sides of the aerial socket or sockets should be insulated from the chassis, and isolating condensers of high quality and 500V or 750V rating should be wired from socket or sockets to the receiver coil circuit. Screened feeders should also have an outer insulated sheath, and wire with bare braiding should never be pressed into service for aerial connections of this kind.

It will thus be seen that there are two points to bear in mind if a receiver of this type is to be as safe as possible. First, it should be so connected that the chassis and other parts will not become alive at mains voltage from the "live" side of the supply. And, secondly, construction and fitting should be such as to safeguard the user from contact with metal parts which *may* be alive from changed mains connections.

BBC TV in Caithness and Orkney

AS a result of the good progress made, and the special steps taken with the installation of the temporary BBC stations at Netherbutton, in the Orkneys, and at Thurmster, near Wick, the Thurmster station was brought into service on December 15, and transmits on Channel 1 (vision 45Mc/s, sound 41.5Mc/s). The Orkney station was opened a week later, on December 22, and transmits on Channel 5 (vision 66.75Mc/s, sound 63.25Mc/s). Both transmissions use vertical polarisation, which means that receiving aerials will need to be mounted in the vertical position.

Tests

There are regular test transmissions from the new stations between 10 a.m. and 1 p.m. each weekday. These tests will be of assistance to the radio trade in installing receivers and aerials, but as they are primarily for engineering purposes they are subject to interruption and variation in power without notice.

Because of their lower power and temporary aerials the coverage of the temporary stations is not as great as that to be provided later by the permanent stations. The temporary stations will

serve the towns of Kirkwall and Wick and their immediate surroundings. In their permanent form the two stations are expected to serve almost the whole of the Orkney Islands and Caithness, with a total population coverage of some 43,000.

Links

The Thurmster station receives its programmes by radio from the BBC's television station at Meldrum and in turn transmits these programmes to the Orkney station. As Thurmster in its temporary reduced-power condition cannot be received direct in the Orkneys, it has been necessary to set up a relaying station. This is on the high ground at Brabstermire, a few miles north of Wick, where the signals from Thurmster are picked up and conveyed to the Orkneys by a microwave radio link. With this arrangement, which has enabled the Orkney station to be brought into operation much earlier than would otherwise have been possible, there may be short periods when adverse radio propagation conditions affect the quality of the transmissions, but it is expected that the pictures will be of a satisfactory standard for the greater part of the time.


An Acorn Valve TV Booster

THE cheap surplus acorn pentode is a very efficient amplifier at V.H.F. and a stage using this type of valve will be found to give a worthwhile increase in sensitivity. It is capable of allowing satisfactory picture reception in circumstances when no picture at all can be received without the extra stage.

If normal reception is obtained without the booster, it can still prove of occasional utility in providing satisfactory results with an indoor aerial, so that the receiver can be moved temporarily into another room, even if the usual outdoor aerial feeder cannot be changed so suit. The booster will, however, generally be most useful in fringe areas or localities where signal strength is poor.

Circuit

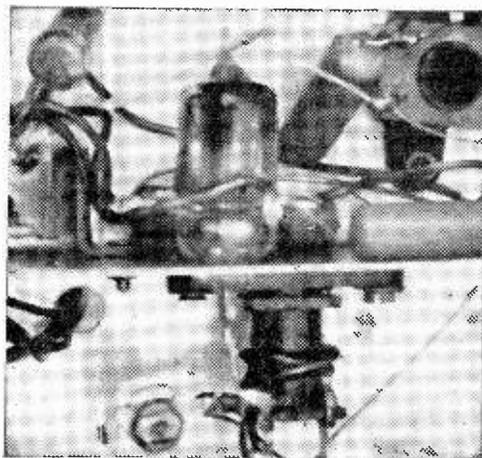The circuit is shown in Fig. 1, and is intended for operation with an A.C. receiver only, where the extra 0.15A can be drawn from a 6.3V heater circuit. The H.T. consumption is only about



This view shows clearly the method of mounting the valve to protrude through the sub-chassis.

8mA at 250V. If the H.T. line is of higher voltage than this, a resistor must be wired in series with the H.T. positive connection to the booster. For a 300V H.T. circuit, a 6.8k resistor is suitable. If necessary, the booster will operate successfully with its own power pack. One heater lead should then be wired to H.T. negative.

Valve connections are shown in Fig. 2. The long end of the valve carries the anode pin, and when the valve is viewed from this end other pin connections are as in Fig. 2. Viewing the valve

from the grid end will give wrong suppressor grid and screen grid connections.

Leads are soldered directly to the tips of the pins. The iron should be really hot, and should be removed *immediately* the joint has formed. Keeping the iron in contact with the pin may fracture the glass seal of the valve.

Coils

It will be found that the dimensions of these are in no way critical because turns can be added or removed, if necessary, to obtain resonance. Formers $\frac{3}{8}$ in., $\frac{1}{2}$ in. and $\frac{3}{4}$ in. in diameter, plain or

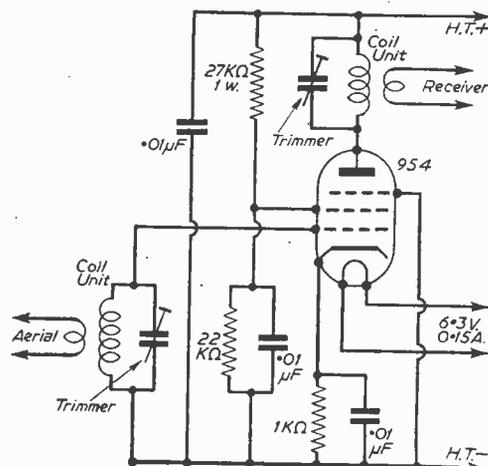


Fig. 1.—The circuit diagram. Power is obtained from the H.T. and L.T. supplies of the receiver.

ribbed, were found to be satisfactory. It was also found satisfactory to omit the trimmers, and tune the coils by means of their cores alone, or to use air-cored coils, with pre-set trimmers.

With tuning by cores alone, and using $\frac{3}{4}$ in. diameter formers, 11 turns will serve for Channel

COMPONENTS LIST

Resistors : 27k 1W
22k.
1k.
6.8k 1W (H.T. dropper, if needed).

Condensers :
3 0.01 μF 25 V.W
2 "beehive" trimmers (10 or 30 pF maximum).
954 acorn valve.

Aluminium for sub-chassis (4½in. x 3½in. approx.).
Aluminium chassis (4½in. x 3½in. x 1½in. approx.).
Tag strip, wire, solder, etc.

oster

A useful unit for obtaining better results in fringe areas or receiving distant stations. By F. G. Rayer.

1, 10 turns for Channel 2, 9 turns for Channel 3, and 8 turns for Channel 4 or Channel 5. The tuned winding is of 24s.w.g. or similar wire, with turns slightly spaced. A 2-turn coupling loop of insulated connecting wire or flex is placed on top of the tuned section, as in Fig. 2.

As the coils are tuned, picture brilliance will increase considerably. If this effect is not achieved, the number of turns on the coils should be modified. When tuning by cores alone, the exact value of stray circuit capacity has considerable effect on the frequency, but it should generally be easy to find the correct tuning point. If tuning is by pre-set condensers, these should be of the beehive type, with a low minimum capacity, and one turn should be removed from the coils. It is best to use sufficient turns so that resonance is obtained with the trimmers near minimum capacity.

Construction

The booster is completely wired up on a chassis about 4½ in. long, with two flanges each about 1½ in. wide. This can be made by taking a piece of aluminium 4½ in. × 3½ in. and bending it at

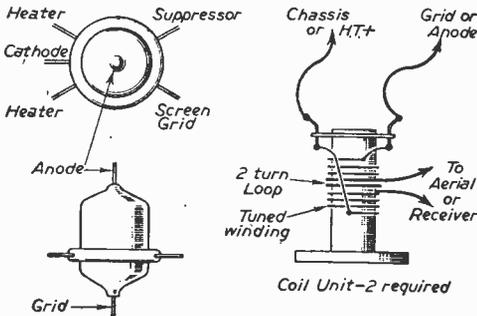



Fig. 2.—Coil and valve data. Note that the pin connections for the valve are only correct when it is viewed from the anode end.

right angles down the middle. When finished, the unit fits inside a box, case or outside chassis approximately 4½ in. × 3½ in. × 1½ in. deep.

Layout and wiring are shown in Fig. 3. The grid pin of the valve projects through a ¼ in. dia. hole, to reach the aerial coil. The valve is held by short, stiff leads going to the coils, etc. Wiring will be easier if heater leads and cathode and suppressor pins are connected before fitting the valve in place.

A small tag strip held by a bracket holds the 22k and 27k resistors secure, and forms connecting points for the H.T. leads.

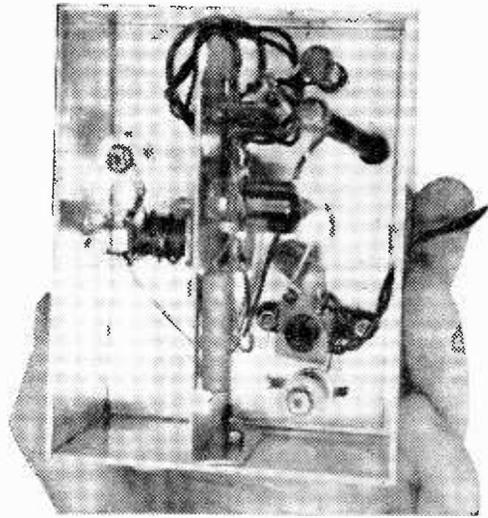All leads should be short and rigid. This is particularly important with trimmer, coil and valve connections. The point "M.C." consists of two tags tightly bolted to the chassis.



The completed booster.

Tuning

For tuning, an insulated tool is necessary. This may be a piece of ebonite rod or similar insulated material, filed to engage with the slot in the cores. Or, if trimmers are used, a piece of ebonite or similar material can be filed to engage with the hexagonal top of the trimmers.

When the unit is completed, it is placed in the outer chassis described. To hold it, the two bolts securing the anode coil are removed, and passed through outer chassis, booster chassis, and coil feet. A small flange or bracket on the vertical portion of the chassis may also be bolted to the side of the outer chassis.

Size

As can be seen from the illustration above, the finished unit is of small dimensions and, in many television receivers, it should be possible to accommodate it within the cabinet. Care should be taken, however, that the unit is not sited above the H.T. rectifier valve or similar source of heat otherwise tuning drift will occur.


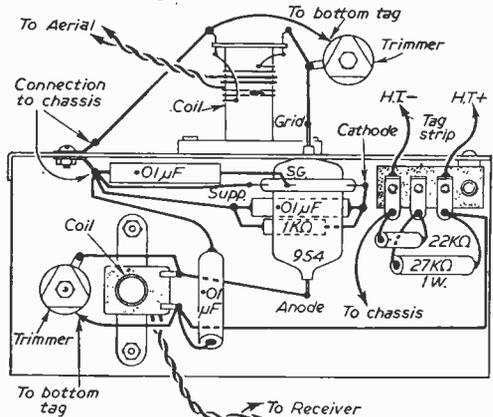


Fig. 3.—Chassis layout and wiring diagram.

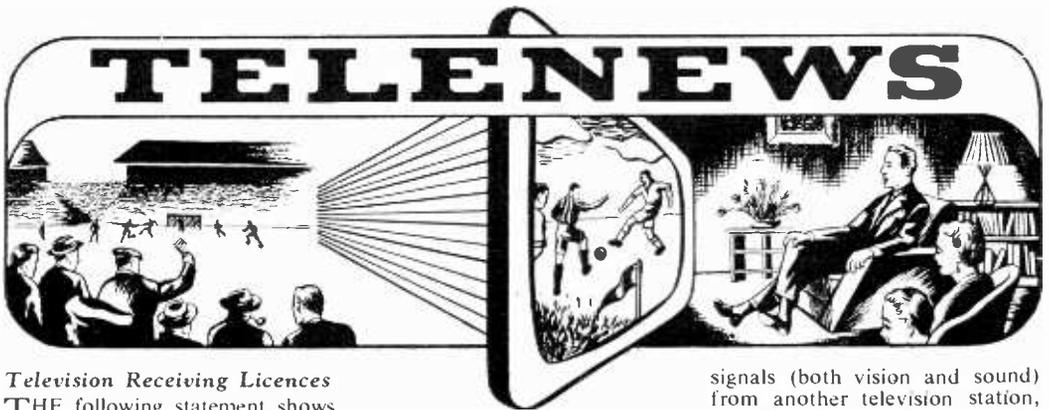

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of October, 1959, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,747,921
Home Counties	1,297,314
Midland	1,516,923
North Eastern	1,606,956
North Western	1,328,133
South Western	814,116
Wales and Border Counties	587,685
Total England and Wales	8,899,048
Scotland	822,425
Northern Ireland	122,892
Grand Total	9,844,365

First African TV Network

CAMERAMEN and technicians in white dinner jackets spun dials and pushed buttons as WNTV, Africa's first television network, went on the air in Western Nigeria on October 31.

The Western Nigerian Premier, Obafemi Awolowo, whose Action Group Government was the guiding force behind the creation of the TV network, described the new medium as one which can "help transform Nigeria into a more modern and prosperous nation."

All of Western Nigeria's top officials plus 500 prominent guests turned out for the resoundingly successful two-hour opening ceremonies, which included excerpts from WNTV's coming attractions, at Ibadan's Western Hall.

Sir James Robertson, Governor-General of Nigeria, said that although he had had serious doubts that the network could be ready so soon he now has high hopes that it will play a

useful part in the education of the younger Nigerian generation.

Translators

THE BBC has placed a contract to the approximate value of £115,000 with Marconi's Wireless Telegraph Co. Ltd., for the supply of television translators, low power television transmitters and amplifiers, and frequency - modulated sound translators and amplifiers.

These equipments will be used to extend the coverage of the BBC television and V.H.F. sound broadcasting services to areas where reception is at present non-existent or unsatisfactory.

A television translator is an equipment which picks up the

signals (both vision and sound) from another television station, amplifies them and re-transmits them on new frequencies.

The low-power transmitters are used where direct pick-up from an existing station is not possible. These accept the vision and sound signals at video and audio frequencies—usually over coaxial cable—and transmit them from a point within the area of indifferent reception.

The frequency - modulated translators will carry out a similar function to their TV counterparts, but for the BBC's V.H.F. sound service.

I.T.A.'s Dover Station

THE Authority regrets that it is not yet able to give a date for the start of programme transmissions from its new



Independent television came to Northern Ireland on October 31st, 1959, when I.T.A.'s transmitting station at Black Mountain, near Belfast, came into full programme service. The illustration shows the Master Control Room. (See "TV in Northern Ireland.")

station at Church Hougham, near Dover. An opening before the end of 1959 cannot now be expected. This is because special tests are likely to be required in order to establish that the signal from the main directional aerial system will not cause an unacceptable degree of interference in the service areas of certain existing television stations on the Continent. A further announcement about these tests will be made as soon as possible.

North-eastern ITV

SATISFACTORY reception of programmes screened from the I.T.A. Burnhope transmitter is noted in parts of the counties of Berwick and Roxburgh, says Television Audience Measurement Limited in a report on their latest boundary survey.

The survey, which was carried out in September and October, 1959, showed that Burnhope ITV transmissions were being received satisfactorily in areas both north and west of the I.T.A. 250 μ V/m contour line which was previously regarded as being the provisional boundary of the North East ITV area. In the south, however, it was established that Burnhope transmissions were not being received satisfactorily as far south as the I.T.A. contour line.

The revised TAM ITV area extends as far north as St. Abb's Head and includes a broad sweep of rising country to the north of the Tweed, beyond the Cheviots, from Gordon to Reston and including Duns and Kelso. Relay services bring in Eyemouth and Berwick while Jedburgh owes its inclusion to a communal aerial system.

TV in Northern Ireland

THE Independent Television Authority's new transmitting station at Black Mountain, near Belfast, which came into full programme service on October 31st, is estimated to have brought over a million more people within range of Independent Television.

All the main transmitting equipment and the greater proportion of the associated studio equipment for this station has been supplied and installed by

Marconi's and includes two 4kW vision transmitters and two sound transmitters together with combining units, programme input equipment, flying spot caption scanner, control desk and test equipment.

The duplication of transmitters

E.M.I. The mast is a three-sided structure, each side being 8ft. 6in. across and is built up of three solid round steel legs braced together with angle steel lattice work. The mast foundation is a solid concrete block 23ft. 6in. square on which a steel pedestal



A group of interested visitors examine an "S" band power distribution board engineered in high Q triplate strip transmission line and exhibited at the 1959 Farnborough Air Show. The double-sided board, designed by Cossor Radar and Electronics, Ltd., was printed and etched to extremely fine limits by Printed Circuits, Ltd., of Borehamwood. It houses 32 "S" band components consisting of branch arm and proximity couplers, cross-over network matched loads, and variable attenuators.

follows established practice; in this particular instance one vision and one sound transmitter will carry the programme service, with the remaining pair immediately available as standby, although if the requirement ever arose the vision transmitters could be operated in parallel (as also could the sound transmitters) to double their respective output powers.

I.T.A. Mast at Mendlesham

FOR the new I.T.A. service for East Anglia a stayed aerial mast 1,000ft. high and weighing 140 tons has been erected at Mendlesham, Suffolk. It is the highest man-made structure of any kind in this country. The design and erection of the mast were carried out by British Insulated Callender's Construction Co. Ltd. to the requirements of the I.T.A. and their main contractor, E.M.I. Electronics Ltd. The steelwork was fabricated and galvanised by Painter Bros. Ltd., of Hereford, and the transmitting aerial was supplied by


rests to carry the mast. The mast is supported by steel wire stays, the heaviest of which is made up of 259 wires, has a diameter of 2 $\frac{1}{2}$ in. and weighs nearly 5 tons. The mast was erected in ten weeks.

Appointment

THE Plessey Company Limited announce the appointment of Mr. R. E. Verguson, M.S.M.A., as Commercial Manager of a new grouping which includes the Sheet Metal Division and the Amar Tool and Gauge Company Limited with the Industrial Hydraulics Division, at Cheney Manor, Swindon.

Mr. Verguson, who is well known in the Swindon area, served as a navigator with the Royal Air Force during the war. He joined Plessey in 1946, and has held senior sales and commercial appointments in several of the Company's divisions. He has been Sales Manager of the Industrial Hydraulics Division since its inception.

PUNGENT POINTERS

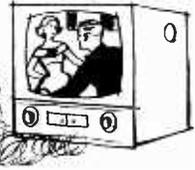

ANGER CAN OFTEN BE SENSED

By L. E. Higgs

THE engineer in radio and television to-day is quite literally finding his nose a very useful accessory in tracing short cuts to damaged, or about to be damaged, components in the complex assortment of equipment that finds itself on the benches of the repair trade.

The collection of "symptom smells" in the memory of any practical serviceman is greater than many of us realise, and their source can quickly be pinpointed.

Soldering Iron

Many materials are, in their normal state, inert from the point of view of odour, but most of them give forth some vapour when touched with the magic wand of the workshop; the soldering iron. The welter of smells produced by an apprentice (and others) with an iron one size too large when replacing a line output transformer in a cramped layout has to be experienced to be believed; acrid rubber, sweet sickly P.V.C., burnt bitumastic compound and the occasional waft of melted condenser wax all mark the progress through the job to anyone standing a few feet away.

The soldering iron, even when used properly, can claim many casualties when laid down; the coax aerial lead, the mains lead (a blown fuse or flash out often precedes the smell) and even the bench top, lino or rubber. Burnt cardboard tells us another service manual has suffered and we are all concerned about our clothes when the dreaded smell of scorched wool assails our nostrils. A deep iron stand or many of them scattered about the benches could help here but they need to be used with staff ingrained with the habit of keeping to them.

Transformers

Probably the mains transformer is our first memorable smell, unmistakable when the charred varnish of complete destruction is sensed, but the smell of overheated impregnation wax tells the man who can differentiate between them that all is not lost and an off-load run when cool, with rectifier out, shows the transformer still to be serviceable after the external circuit short is cleared.

The worst of them all is generally agreed to be the flashing selenium rectifier; an object of disgrace and disgust with a characteristic odour sometimes described as "putrid organic" although most of us have a more apt workshop name.

The printed circuit receiver has again brought to the fore the mixture of burnt phenolic resin sheet and running wax. Usually a safe bet is that a red hot screen resistor is burning its associated decoupling capacitor.

Another symptom that tells us how a circuit is behaving is the ozone from brushing EHT—out lights for this one. The steaming cloud from a cement-coated volts dropper on switching on for the first time after storage in a damp place (usually while awaiting parts) is also well known. In this category, red hot wire-wounds can be detected before being seen, and the smell from a heater current thermistor tells us that the current is on before the valves light.

Anyone who has seen the result of an over-excited electrolytic capacitor with the garlands of aluminium foil surrounding a gaping upright cylinder, cotton gauze and a splatter of white, steaming spots all over the cabinet interior cannot fail to forget the delicate aroma of aluminium borate that accompanies it; or the older smell from an overloaded one watt resistor of the solid, uninsulated carbon type as its cellulose paint bubbles off—sometimes with flames.

Hazards

Working on the carpet in the customer's home has brought a particularly new danger when the chassis is out of its slim line cabinet—the unnoticed volts dropper lying on dense layers of snow white hearth rug. Here again, the dangers of the soldering iron are apparent. A useful aid to the outside man is the safe, quickly heating transformer iron of which the safety outweighs the clumsiness.

Many smells are not necessarily a sign of fault, but are worth remembering. New receivers often give off traces of hot varnish and plastic when first switched on and one in particular can be relied upon to produce smoke or steam in a gently drifting cloud, and yet all be normal.

When high temperature valves are plugged in for the first time their labels are often detected as is the new paint on a replaced selenium rectifier. Resin-covered solder, switch cleaner and cabinet polishes, too, have a niche in the serviceman's memory.

Some of the less often occurring odours are from the older days and many can remember accumulator acid, soldering fluxes, pitch tops from H.T. and G.B. batteries and, the oldest of the plastics, the rubbery, full strength of ebonite when an odd piece was thrown on a fire.

Just as ears are part of a driver's senses on the road, so even more in working on radio and television, an intelligent, often instinctive, appreciation of smells by the engineer, in conjunction with ears, eyes, and mental following of circuit processes, help him to build up a quicker diagnosis, and lead to more efficient working.

The Biggest Money-Maker in the Business!

NEWNES
RADIO & TELEVISION SERVICING

SERVICING DATA FOR
300 Popular Models
(1958-1959)
IN ONE VOLUME



Covering many of the newer models now in use all over the country, this volume fills an urgent need for technical data. It contains all the circuits, components and chassis layout diagrams you need for

300 popular 1958-1959 Models. Examine it Free for 7 days—complete form on next page.

672 PAGES OF WANTED DATA

TELEVISION, RADIO, RECORD AND TAPE SERVICING DATA

Alba, Argosy, Berec, Beethoven, Bush, Champion, Collaro, Cossor, Cyldon, Decca, Defiant, E.A.R., Eddystone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B, McMichael, Marconiphone, Masteradio, Murphy, Pageant, Pam, Perdio, Peto

Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Spencer-West, Stella, Ultra, Vidor, Walter.

RECENT DEVELOPMENTS SECTION Includes: Picture Tube Repair, Car Radio Interference Suppression, Valve and Picture Tube Data.

HEATER RATINGS, BASE CONNECTIONS, EQUIVALENTS

SERVICING DATA PRE-1953 UP TO 1959
Over 2,300 Models
YOUR COMPLETE LIBRARY IN SEVEN VOLUMES



Includes the 300 models and data in the volume on left

Here you have Newnes Complete Servicing Library—early popular models to 1959—almost every set you may be called upon to service. This data is, as you know, absolutely invaluable. It is worth its weight in gold for years on end—increasing your income by quicker servicing. Study the complete set for 7 days—without obligation.

TELEVISION, RADIO, RECORD AND TAPE SERVICING DATA

Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, Bush, Champion, Collaro, Cossor, Cyldon, Decca, Defiant, E.A.R., Eddystone, Ekco, E.M.I., English Electric, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Spencer-West, Stella, Strad, Ultra, Vairadio, Vidor, Walter, Webcor, White-Ibbotson.

Also—Large Fold-out Charts—Television Trouble Tracing; Servicing VHF/FM and AM/FM receivers; Servicing Printed Circuit Equipment; Servicing Transistorised Equipment. Data on—Colour Codes, Valves and Picture Tubes, Medium and Long Wave Broadcasting Station Wavelengths, TV and VHF/FM Stations and Channels.

4,250 CIRCUITS AND DIAGRAMS • 4,150 PAGES

2 Years' Free Postal Advisory Service

EXAMINE EITHER—FREE FOR 7 DAYS
without obligation to buy

See overleaf for more details and REPLY-PAID FORM FOR POSTING

Newnes Radio & Television Servicing

PAYS FOR ITSELF OVER AND OVER AGAIN!

"More than repaid the cost in a short period," says E. J. S. (Wolvercote).

"One glance only was enough to convince me of its worth," writes J. F. B. (Leicester).

"Of immense help and in constant use."—T. A. (Uxbridge).

"A boon and a must."—J. S. (Manchester).

SEND FOR FREE EXAMINATION TO-DAY—SEE BELOW

HOW TO FOLD THIS PAGE FOR POSTING



1. Detach complete page and fold across at (A), turning this strip downwards out of sight.
2. Then fold at (B) and (C).
3. Tuck (C) into (B) so that Reply-paid portion with NEWNES address is shown.

(A) Fold along here

FINALLY POST QUICKLY!

DETACH PAGE HERE



(B) Fold along here

Postage will be paid by George Newnes Ltd.

No Postage Stamp necessary if posted in Gt. Britain or Northern Ireland.

BUSINESS REPLY FOLDER
Licence No. W.C. 1129

GEORGE NEWNES LIMITED,
15-17 LONG ACRE,
LONDON, W.C.99

(C) Fold along here

POST TO-DAY NO STAMP REQUIRED

Place tick against your choice below:

Radio and Television Servicing
(Pre-1953 to 1959 Models)
SEVEN VOLUMES
10/- Dep. 15 monthly payments of 15/- . Paying £11.15s. in all. Cash in 8 days £11.5s.

Radio and Television Servicing
(1958-1959 Models)
SINGLE VOLUME
12/6 Deposit. 4 monthly payments of 10/- . Paying 52/6 in all. Cash price in 8 days 50/-.

Send me the book or books I have selected, without obligation to purchase. I will either return the book or books in 8 days or send the deposit 8 days after delivery, then the monthly subscriptions as set out above, until the total subscription price of the book or books I have selected has been paid.

Mr., Mrs., Miss,

Address

.....

Occupation


Your Signature

(Or your Parent signs if you are under 21) **R58/RV89**

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

Servicing Television Receivers

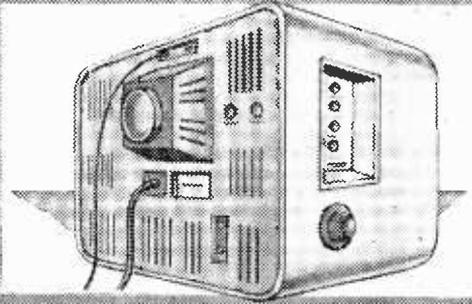

No. 51.—THE PHILCO A1497, A1800 AND A1810

By L. Lawry-Johns

(Continued from page 129 of the December 1959 issue)

THE details given last month should enable most faults in the power-pack circuits to be remedied easily. We shall now deal with faults in the line timebase and EHT circuits. When testing for the presence of EHT, a handy tool to use is a spark-plug tester which is sold in many stores and is a small screwdriver with a high voltage neon in the handle. When the blade is advanced to the R12 the neon will glow vividly. It is unnecessary actually to touch the anode or single-wire end with the blade. The presence of EHT at the anode causes the vivid glow and thus absence of glow denotes that the required voltage is not reaching the R12 and that something is wrong in an earlier stage.

Line Whistle

In actual fact the absence or partial absence of the normal line whistle would have already betrayed this but it is worth while mentioning.

Assuming that the spark or glow is produced at the R12 anode, move the screwdriver over to the right-hand side or double wire end. If the R12 is lighting up, a thin blue spark should be drawn from here but of much reduced violence and a neon of the type mentioned will intermittently glow. It will not glow steadily as at the anode as the voltage is now rectified. If the R12 is out and the spark is absent or much subdued, turn the brilliance down to zero and

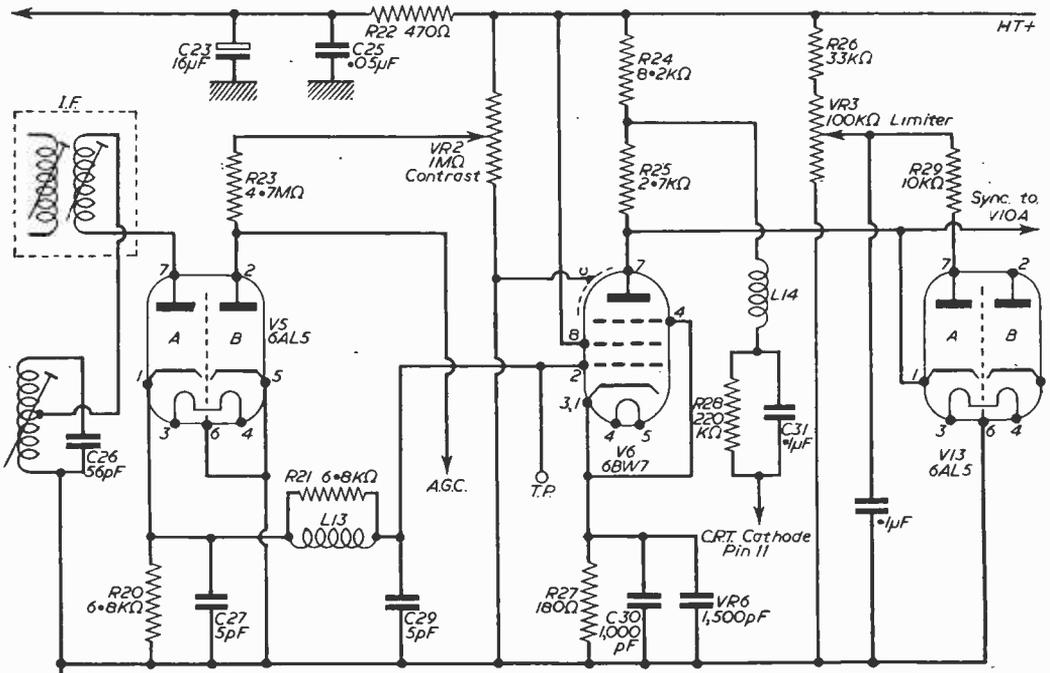


Fig. 1. 5. —Vision detector, AGC diode, video amplifier, vision limiter and H.T. feed (via R22) to early stages.

observe the effect on the R12. If it now glows, turn up the brilliance half-way or so and check the adjustment of the ion-trap magnet. If the magnet is clamped firm and has not been altered, however, check V11, V12 and V15, then VC5, etc.

C.R.T. Cathode Voltage

Also check C.R.T. cathode voltage (pin 11) 115V is approximately correct. If absent, check tube for heater-cathode short; also V13 and resistor R24.

Assuming, however, that the R12 is well and truly out it can be assumed that its heater is o.c. and a new valve should be soldered in position.

Dull Picture

Advance contrast and, or, brilliance. If the picture merely blurs and turns negative, it can be assumed that the tube emission is low and a new or rebuilt tube is required. If advancing the brilliance brings up a fairly bright raster, however, make a thorough check of the video amplifier stage (V6) including R20 and R24, V5, V6 and V13 and, of course, the setting of VR3. If the picture will not stand an increase of contrast or brilliance and merely defocuses and fades out, expanding as it goes, check the ion-trap magnet setting and then change the R12 (V14).

Bright Raster. No Picture. Sound O.K.

Assuming the sound is in order and that the brilliance VR8 produces a raster but no picture signal, check V4, V5 and V6. Then, if these are in order, check the feed resistor to pin 8 of V4. If this is charred, check the 0.003 μ F decoupling capacitor. If this has shorted, replace it; replace the 1.5k Ω feed resistor and see that R22 has not been damaged. The above assumes that the brightness is controllable. Sometimes the symptoms are that the brightness control does not alter the raster at all; it remains bright. Again, the control may work in reverse.

In all cases of this nature, the proper procedure is to find out what has disturbed the working conditions of the tube. As already stated the cathode voltage should approximate to 115V. This is at pin 11. The voltage at pin 2 is dependent upon the setting of the brilliance control and should swing from zero to 150V at maximum.

Video Load

The voltage at pin 11 is dependent upon the voltage drop across R24 (as this is the load resistor of the video amplifier). There are many possible causes of a low voltage at this point and the possibility of oscillation in the I.F. stage should not be overlooked. If this is suspected, short pin 2 of V6 to chassis, i.e., link "test point" to chassis. This should restore normal anode voltage if oscillation is the cause. If not, check V6, VC6 and C30 for shorts, ensuring that about 2V is dropped across R27 (pins 1, 3 or 9 to chassis) under no load conditions. Then check R25, R24, V13 (heater/cathode short in section A) and the tube itself.

Lack of Height

In all cases of lack of height and frame distortion, e.g., picture compressed at bottom, stretched at top, the ECL80, V11, should be checked, then V10. If these are not at fault, attention may be turned to C45, R41, C46 and C47. Only if these are passed without fault should C42 and 44 be suspected.

Frame Hold

If VR4 is at one end for optimum lock, check R40. If VR5 (*height*) exercises undue influence upon the hold, check C40. If the frame revolves either way (up or down) with no positive lock, check V13 and the components associated with section B, R37, etc. If both line and frame pulses are weak, check R31 (2.2M Ω).

Poor Gain

If there is a weak and ragged picture, more particularly on Band III, check tuner unit valves, especially PCC84, then V3 but ensure that the aerial system is in order. If all else is in order check tuner unit components, particularly the 47k connected to pin 2 of the PCC84.

Low and Distorted Sound

Check V7, V8 and V9. Then check 270k Ω resistor to pin 7 of the 6AT6 and the 3.3M to the limiter metal rectifier (WG5B). The 270k is coloured red, violet, yellow, the 3.3M is coloured orange, orange, green.



ANOTHER film show, sponsored by this journal and our companion journal *Practical Wireless*, is to be held at Caxton Hall, Westminster, on Friday, January 22nd, 1960, at 7.30 p.m., when the Editor will take the chair, admission will be by ticket only. The event, which has proved so popular in previous years, is being arranged in conjunction with Mullard Ltd.

Films

The films are entitled "Photo Emission," "From us to View" and "Mirror in the Sky." The latter film deals with events leading up to the experiments by Sir Edward Appleton to confirm the existence of the Heaviside layer, and continues with the discovery of the Appleton layer and the developments of the pulse techniques which became the basis of radar. The film concludes with one of the latest scientific achievements—the radio telescope.

Tickets

Applications for tickets should be made now. Please mark your envelopes "Caxton Hall" in the top left-hand corner and send a stamped, addressed envelope for the tickets. All applications will be dealt with in strict rotation.


Pay weekly at rates which you can easily afford—AND INTEREST FREE, TOO!

TRANSFORMERS

MAINS TRANSFORMER 5/9
Primary 200-250. Secondary 0-100-250 150 mA. Suitable for small amplifier with 1 series valves. 2 1/2 in. x 1 1/2 in. P. & P. 1/9.

OUTPUT TRANSFORMER & SMOOTHING CHOKE COMBINED 4/9
2 1/2 in. x 1 1/2 in. Suitable for EL84s in single or push/pull output. P. & P. 1/9.

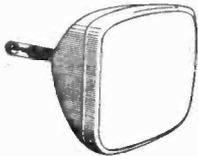MAINS TRANSFORMER 7/9
Primary 200-250. Secondary 300-0-300. 6 v. 3.3 amps. P. & P. 1/9.



RE-BUILT T/V TUBES

SEND ONLY **8/6** WITH ORDER. BALANCE AT THE RATE OF 8/6 A WEEK FOR 19 WEEKS. 12-month guarantee.

NO EXTRAS · NO INTEREST · NO DEPOSIT. Completely rebuilt gun assembly new cathode, heaters, etc., giving the high standard required for long picture life, quality and value. Carr. & Ins., 15/6. Engineer available to fit. Express service, same day as ordered. Write for details.

FULL ALLOWANCE ON YOUR OLD TUBE.
CASH PRICE **£8.10.0.**

17" T/V for only 11/1 a week

for 36 weeks (4 weeks payment in advance) or over a shorter period if so desired.

Beautiful latest finish cabinet in contemporary style covered and washable.


Polished legs, 18 in. optional extra for 25/-.

17 in. Rectangular Tube. Guaranteed fully for 12 months.


12 channels. "Turret Tuned"—ITV/BBC. Extra coils at only 7/6 a pair (with order).

Chassis. 14 B.V.A. Valves. Salvaged but reconditioned and guaranteed 3 months.

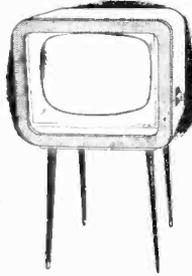Due to overwhelming orders, some delay may occur. Please enquire when ordering.



CASH PRICE
19 GNS.
Carr. & Ins., 30/-.

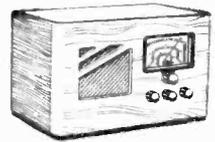

HOME RADIO

5/1 (Initial Payment)

BALANCE PAYABLE AT 3/11 OVER A PERIOD OF 19 WEEKS.

AC/DC. Universal mains 5 valve octal superhet 3 waveband receiver can be adapted to gram p.u. In attractive wooden cabinet 9 1/2 x 18 1/2 x 11 1/2 in. Ins. carr. 4/6.

Cash price **79/6.**

IF GOODS ARE BOUGHT ON TERMS, CARRIAGE & INSURANCE MUST BE SENT WITH INITIAL PAYMENT.

C.H.I.

4/7

Initial Payment




RECORD PLAYER CABINET

Balance at 3/5 per week over 19 weeks.

Size 14 1/2 x 16 1/2 x 8 1/2 in. Takes B.S.R. U.A.8 4-speed Auto-changer, 7 x 4 in. elliptical speaker. Most of the modern portable amplifiers. Attractive speaker grille and recessed control panel. Carr. & Ins., 4/6.

Cash price **69/6.**

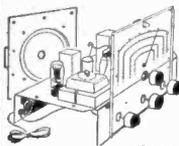


SUPER CHASSIS

5/1 initial payment & 19 weeks at 3/11.

5-valve superhet chassis, including 8 in. P.M. speaker and valves. Four control knobs (tone, volume, tuning w/change switch). Four w/bands with position for gram. p.u. and extension speaker. A.C. Ins. & carr. 5/6.

SOLO SOLDERING TOOL 12/6

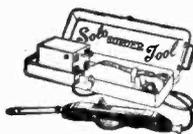110 v., 6 v. or 12 v. (special adaptor for 200/250 v. 10/- extra). Automatic solder feed, including a 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.



PORTABLE AMPLIFIER MK. D.3. 5/7 initial payment & 19 weekly payments of 4/5.

De luxe model. Printed circuit. Latest design. Dimensions 7 in. x 2 1/2 in. x 5 in. A.C. only. Mains isolated 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve, giving higher undistorted output. Volume, treble and bass control. Knobs 3/6 extra. P. & P. 3/6.

CASH PRICE **89/6.**

12 MONTHS' GUARANTEE.

Many other types and sizes of beautifully designed cabinets in stock at prices from 29/6 to 79/6.

U.A.8. B.S.R. MONARCH 4-SPEED AUTOCHANGER. 8/1 initial pymt & 19 wkly pymts of 6/11. (Cash price £6.19.6.)

U.A.12. LATEST B.S.R. MONARCH 4-SPEED MIXER. 9/7 initial pymt & 19 wkly pymts of 8/5. (Cash price £8.9.6.)

COLLARO CONQUEST 4-SPEED AUTOCHANGER. 8/1 initial pymt & 19 wkly pymts of 6/11. (Cash price £6.19.6.)

COLLARO CONQUEST STEREO AUTOCHANGER. 12/6 initial pymt & 19 wkly pymts of 11/6. (Cash price 11 guineas.) Carr. & ins., on the above 5/6.

B.S.R. FUL-FI CRYSTAL TURNOVER CARTRIDGES 19/6. Brand new. Including sapphire needles for L.P. or Standard. Can be fitted to all standard P.U. arms. P. & P. 9d.

★ Recommended for Stereophonic Sound ★

Bin. P.M. Speakers. 8/9. With 7 x 4 in. elliptical speakers, O.P. Trans. fitted, 10/- Post 2/6. 19/6. Post 2/9.

EXTENSION SPEAKERS 19/9

Polished oak cabinet of attractive appearance. Fitted with Bin. P.M. speaker W.B. or Goodmans of the highest quality.

Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. carr. 3/9.



(DEPT. E.1.) **DUKE & CO.**
621/3, Romford Road, Manor Park, E.12.
Tel.: 1LF. 6001/3. Send for our FREE catalogue.

NEW! TAYLORMETER Model 127A

20,000 o.p.v. POCKET SIZE!

Performance equal to a high priced instrument
OUTSTANDING FEATURES:

- ★ Sensitivity 20,000 o.p.v. D.C. 1,000 o.p.v. A.C.
- ★ 20 Ranges.
- ★ D.C. Current 50µA, to 1 Amp.
- ★ D.C. Volts 0.3 v. to 1,000 v. (25 kV by probe).
- ★ A.C. Volts 10 v. to 1,000 v.
- ★ 3 Resistance Ranges from 0-20 megohms (self-contained).
- ★ Meter 40µA 3½" arc. Accuracy D.C. 3%, A.C. 4%, Ohms 5%.
- ★ Dimensions 5½" x 3½" x 1½".
- ★ Weight 14oz.


Price: £10.00

Credit Sale Terms available
 9 monthly instalments of
 £1.4.4.

Complete with Instruction Manual
 and Interchangeable test
 prods and clips.
 High quality leather case, if required,
 £1.12.0.
 H.V. Probe for 25 kV £4.15.0.

Write for full details
 and catalogue.

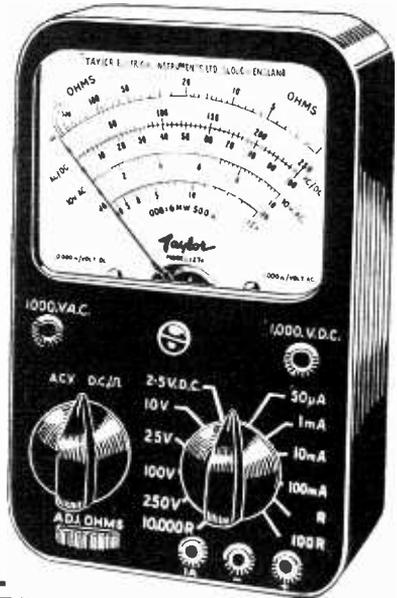**TAYLOR ELECTRICAL
 INSTRUMENTS LIMITED**
 MONTROSE AVENUE, SLOUGH, BUCKS.



Telephone: Slough 21381.
 Cables: Taylins, Slough.



*** TOP QUALITY AT
 UNAPPROACHABLE
 PRICES**

With 12 Months
 Full Guarantee

NEW GUN TV TUBES

*This means Completely New Gun Assembly with New Button and Base. Rescreened and Realuminised. Virtually A New Tube. All Mullard and Mazda Types.

12" — 14"	-	-	-	-	£6. 10. 0
15" — 17"	-	-	-	-	£7. 0. 0
21"	-	-	-	-	£9. 0. 0

Electro Statics 10/- extra.

Carriage and Ins., 10/- (Goods) Terms: C.W.O.
 20/- (Pass)

● 10/- refunded on receipt of old tube, clearly marked sender's name and address, cartoned and consigned.

SABRINA C.R.T. COMPANY
 "Buck & Bell Works", Banbury, Oxon.
 Phone 370

Now Vidio offer even better value with a new service.

C·R·T'S RE-SCREENED AND ALUMINISED


All type of tubes available, each fitted with new Gun Units and completely guaranteed for a year, and delivered anywhere in the United Kingdom — now. Standard C.R.T's still available at reduced prices.

For full details write direct to:

VIDIO REPLACEMENTS LIMITED

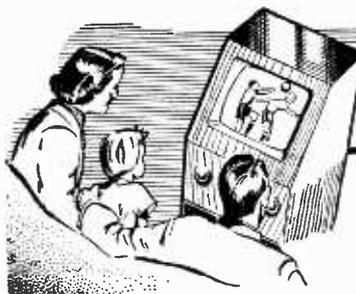R.T.R.A. Approved.
 Hales Street,
 Deptford High Street,
 London, S.E.8.
 or
 Tel.: TIDeway 4506.





UNDERNEATH THE DIPOLE

A MONTHLY COMMENTARY

By Iconos

SOME of the best and most popular items on BBC and I.T.A. programmes have been films made specially for television in film studios and on exterior location. *Wagon Train*, *Robin Hood*, and several series of Westerns and "whodunits" have scored high audience ratings, with TAM and Nielsen's over a long period, both here and in the U.S.A. These are all films made with traditional cinema techniques in scripting, direction, photography and editing. Next come the television films made with a technique more akin to live television, with multiple cine cameras photographing on film (35mm or 16mm) long, staged sequences for such items as *I Love Lucy*, *Burns and Allen* and various quiz shows. This type of production is almost the same as telerecording from live television cameras on to film or videotape, and its use is increasing as fast as suitable subjects and script material becomes available.

A Slump?


WHILE *Wagon Train*, *Sea Hunt* and other American and British cinema technique series continue to register popularity, very few new series of this type seem to be appearing. Making a film series involves quite a large investment, and it is usual to make a pilot episode for showing to the networks for securing contracts. During the last few months, over 200 such pilot films made in America were shown to executives of American networks by independent producing companies, but only about 10 per cent. made the grade, and were actually booked. The quality of the scripts, production, star values and technical gloss is becoming so important and the competi-

tion is so fierce, that this type of production has become highly speculative. Costs of production have risen very considerably and it is now essential for a series to be sold to networks in America as well as Britain, before the production of No. 2 and subsequent episodes up to the usual total of 39 is commenced. Film studio lighting and techniques are in the main outdated when it comes down to high-speed work, turning out a half-hour film in about 2½ days. In this short time, there is no leeway to allow for script revisions, changes of artists, breakdowns of equipment and all the other normal hazards of film production. Slow speed of production at Shepperton studios and overtime bans very nearly brought to a halt the elaborate and glossy *Third Man* series, which is being made partly in England and partly in Hollywood. Happily, management and union executives got together and pro-

duction was resumed on this ambitious series, a co-operative venture of the BBC, with the NTA organisation of America. A-TV have entered into a similar co-operative deal with Independent Telefilm Corporation of America, for making top-class television film in London and Hollywood. All of these factors, together with the failures of the smaller companies making these cinema-style television films, point to the fact that this type of production will be mainly carried out by the larger organisations, who are able more easily to recover the high production costs.

Transatlantic Telerecording

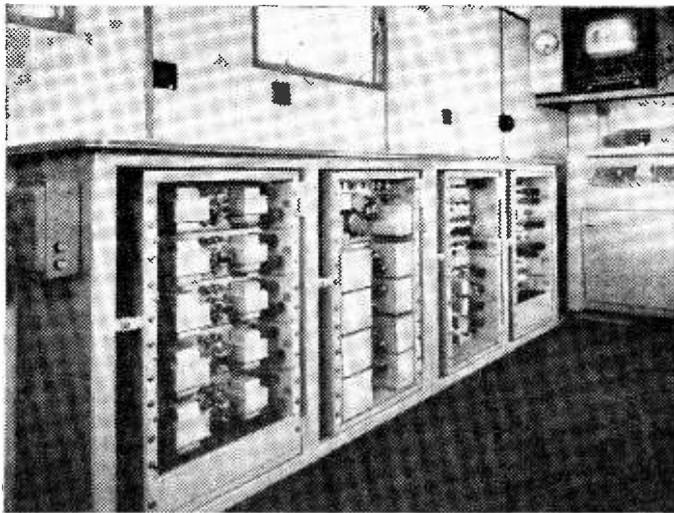GRANADA made great use of their video tape line standard converter during President Eisenhower's visit to Britain, as already reported in this journal. Two Ampex video tape machines were mounted on trucks and taken



The first mobile Ampex Videotape recording unit to be mounted in a specially designed vehicle is being put into operation by TWW. The view above shows the interior of the van; all equipment is mounted in four low-level racks topped by a working area and in the background is the record monitor and part of the Ampex console.

from Granada's Manchester H.Q. to London Airport for making magnetic transfer on the spot, in time to catch planes to America at almost the last minute! American viewers were thus able to see their President's progress on their home screens a few hours earlier than they would if the usual all-film method, with its processing and printing had been carried out.

The speediest way of all, so far as transatlantic operations are concerned, is the BBC method of using the transatlantic telephone cable system. At this end, a very slow-speed flying spot telecine scans the film every other frame, sequentially, at 200 lines. At the Canadian end, at Montreal, a similar flying spot equipment, converted into a telerecorder, records the impulses at the same rate and speed on film. It takes about fifty minutes to transmit 30 seconds of film material in this manner, and results are said to be good. The slow speed, reduced line standards and alternate film frame methods are necessary to contain the signal information within the 4.5kc/s bandwidth available on the transatlantic cable. Naturally, the quality is inferior to the video tape recording, but for red-hot news it is still considered worth while.

TV Studios

IT is interesting to note that both A-TV studios at Elstree and Teddington have had a very long connection with show business. One of the existing stages at the Elstree plant was constructed in about 1913 and was the first brick-built film studio to be erected in England, from which daylight was excluded and photography relied upon artificial lighting. This stage—about 70ft. X 30ft.—had its effective height raised by lowering the floor level by about 5ft., a tricky undertaking which was carried out in 1928. The original silent film stage at Teddington, also built in 1913, was all-glass, in which daylight was supplemented by enclosed arc lamps similar to those used at that time for shop-fronts and street lighting. Later on, this greenhouse type of stage was converted into a brick and breeze-block dark studio and it was in continuous use for many

years, with a fine large modern extra stage added. Later, the Teddington studio became an aeroplane factory. However, a few months ago ABC-TV took it over and, once more, it is back in show business.

"Busy" Titles

I HEARD the news that the BBC were proposing to use 21in. monitors with some mis-giving. While it is true that there are large numbers of viewers who possess 21in. television receivers, there are also very many who still have 14in. or even 12in. screens. These viewers already have some difficulty in reading the titles and credits on some of the BBC programmes, in which the lettering is small and the background picture "busy." It has seemed to me that the caption writers and directors at the BBC are inclined to become a little too arty-crafty with their titles, which might be acceptable on 21in. screens and yet are not at all satisfactory on the small screens. The I.T.A. programme contractors, who also used large monitor screens in those regional control rooms laid out in the American style, seem to have avoided falling into this trap. Generally, the style of type is solid and clear, easily readable, just as the commercials are. But a fault common to both I.T.A. and BBC titling is excessive speed on the roll-up or creeper titles at the end of subjects. Sometimes these creep up the screen at an alarming rate which

slows up and comes to a stop for an excessive time on the name of the producer! I put this down to the speed control or: the caption machine being manipulated as a means of contracting or stretching the programme time to the exact second. Personally, I dislike roll-up or creeper titles, which arc hard on the eyes and most inartistic. I prefer the end credit titles to be a series of cards held quite still and dissolved from one to another.

Anglia Opens

NEW regional stations in East Anglia and Ulster are now in operation. Anglia began with an ambitious play, *The Violent Years*, starring Lawrence Harvey and Hildegard Neff, which had been pre-recorded on videotape. This was a very well produced drama with varying exterior backgrounds, first-class interior sets, well handled cameras and expert cutting—in short, it had the professional polish one might expect of a crew that had worked together for months. It traced the career of a boy and man through his stormy life, starting in Austria during the first world war. Dramatic situations were excellently handled by the director, Peter Graham Scott—and there were plenty of them. This kind of opening to a regional station was much more effective, I thought, than the conventional hotch-potch usually served up on these occasions. Anglia avoided the obvious.

PRACTICAL WIRELESS

Chief Contents of January Issue

Now on Sale, 1/6

USING THE RF24
 PREVENTING I.F. BREAKTHROUGH
 A TRANSISTOR REFLEX RECEIVER
 A QUALITY V.H.F./F.M. RECEIVER
 A CRYSTAL RECEIVER AND AMPLIFIER
 A TRANSISTORISED MIXER UNIT
 CALCULATING RESISTOR VALUES
 BECOMING AN AMATEUR
 AN INEXPENSIVE T.R.F.
 BEGINNERS' TEST-METER
 ETC. ETC. ETC.

7-VALVE AM/FM RADIOGRAM CHASSIS

Surplus Bargain Offer


TRS

Valve Line up:
ECC85, ECH81,
EF89, EAB C80,
EL84, EM81, EZ80.



3 waveband and switched gram positions. Med. 200 m.-500 m. Long 1,000 m.-2,000 m., VHF/FM 88-95 Mc/s.
4 Controls. Vol., On-off, Tone, Tuning, Wavechange. P.U., Ae. and E., and speaker sockets. Magic eye tuning. Philips continental tuning insert with permeability tuning on FM, and combined AM/FM IF transformers, 460 Kcs and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry, including AVC and Neg. Feedback. 3 watt output. Sensitivity and reproduction of a very high standard. Chassis size 1 3/4 in. x 6 1/2 in. Height 7/8 in. Edge illuminated glass dial 1 1/2 in. x 3 1/2 in. Vertical pointer, Horizontal station names, gold on brown background. A.C. 200/250 v. operation.

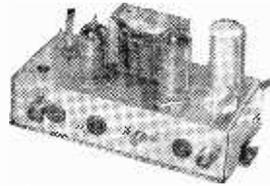£13.10.0 Carr. and Ins. 5/- . Complete with 4 knobs walnut or ivory to choice.



BAND 3 TV CONVERTER

All channels 7-13 (180-205 Mc/s).
Mk. 2 Model. Latest cascade circuit using ECC84 and EF89 valves. 18db gain over standard circuits. Built-in Power Supply 200-250 v. A.C. Size 8 1/2 in. x 3 in. x 4 in. Simple to fit—only external plug-in connections. Wired and aligned ready to use. Only 7/6 P. & P. 9/6.
B1-B3 changeover Sw. and BBC Aerial Socket fitted and wired, 8/- extra.
Band 3 Aerials. Single Dipole with 4 yds. cable, 1 1/2/9, 3 Element Beam, 25'., 5 Element, 32/6, etc. B1-B3 Crossover Units, 7/6.

RECORD PLAYER BARGAINS

NEW RELEASE by E.M.I.—4-speed Single Player Unit fitted with latest stereo and monaural Xtal cartridge and dual sapphire stylus. Auto stop and start. A fidelity unit and bargain buy at only **£6.10.0**.

BBR—UAS Model.—4-speed autochanger with crystal turnover cartridge, etc., wired for stereo, Bargain **£6.10.0**.

Garrard—Latest RC121/D/Mk 2—fitted with G.C. Xtal cartridge, plug-in monaural head. Auto manual selector, etc. The connoisseur's choice for audio perfection. Bargain 10 gns.
Plug-in stereo head GC8/10 **£2** extra.

All above are brand new, fully guaranteed models. Carr. and Ins. 4/6.

Comprehensive bargain range of Collaro, BSR and Garrard Units in stock. Send for comprehensive bargain lists.

RE-GUNNED TV TUBES

New Reduced Prices!

And now 12 months' Guarantee!

12in. £6 17in. £8.10.0
14in. £7 21in. £10.10.0
15in. £7.10.0 Carr. and Ins. 10/-
All tubes Rebuilt with new Heater Cathode and Gun Assembly—reconditioned virtually as new! Full 6 months' unconditional Guarantee. As used by our own Service Dept. Comprehensive stocks—quick delivery. 10/- part exchange allowance on your old tube.

RECORD PLAYER CABINETS

Contemporary Cabinet styled, rexine Price covered cabinet **£33.0.0**

in two-tone fawn and brown, Carr. and or mottled red. Ins. 3/6. with white polka dot. Size 18 1/2 x 13 1/2 x ht. 8 1/2 in., fitted with all accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, etc. Unent record player mounting board 14 x 13in. supplied.



2-valve AMPLIFIER Mk. 2

Latest developed circuit giving a higher fidelity response and greater output (2-3 watts) using twin stage valve ECL82 and neg. feedback Tone Control. Complete with knobs, etc., wired and tested ready to fit in above cabinet.

ONLY **£2.17.6** P. & P. 1/-.
6in. speaker and matching transformer, 22/- P. & P. 1/6.

SEMI-CONVERTERS. E.H.T. Type Fly-back Voltages. K3/25 2 kv., 5/-; K3/40 3.2 kv., 8/9; K3/45 3.6 kv., 7/3; K3/50 4 kv., 7/8; K3/100 8 kv., 13/6. MAINS TYPES.—RM1, 125 v. 60 mA., 4/6; RM2, 125 v. 100 mA., 5/6; EM3, 125 v. 120 mA., 7/6; RM4, 250 v. 250 mA., 16/-; RM4B type 270 mA., 17/6; RM5, 250 v. 300 mA., 21/-.

SPEAKER FRET.—Expanded Bronze anodised metal 5 x 8in., 2/3; 12 x 8in., 3/-; 12 x 12in., 4/6; 12 x 15in., 6/-; 24 x 12in., 9/-, etc.

Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

FULLY GUARANTEED VALVES NEW REDUCED PRICES

1R5, 1T4 7/6	DF96	9/-	HF80	9/6	6PCF82	10/6	
1R5	7/6	DK96	9/-	EF86	13/6	6PCL83	12/6
3A1, 3V4	9/-	DL26	9/-	EF91	8/6	PL81	12/6
6Z4	9/6	5E18	9/6	EL41	10/6	PL82	9/6
6K7	8/6	EBC80	9/6	EL84	8/6	PL83	11/6
6K8	8/6	EBC41	9/6	EM81	9/6	PY80	7/6
6X7	8/6	ECC83	9/6	EY51	10/-	PY81	9/6
6BN7	8/6	RCC84	10/6	EY86	10/-	PY82	7/6
8V6	7/6	ECP80	11/6	EZ80	7/6	PY83	10/6
6X4	7/6	ECP82	11/6	EZ81	7/6	U25	12/6
7CS	9/-	ECH81	10/6	MU14	9/6	U191	12/6
7Y4	8/6	ECL80	10/6	PCC84	10/6	UCH42	10/6
DAF96	9/-	ECL82	11/6	PCF80	10/6	UF41	10/-

Send for List.

SPECIAL PRICE PER SET

1R5, 1T4, 1R5, 3B4 or 3V4	£7/6
DK96, DPF96, DAF96, DL96	£8/6
6K8, 6K7, 6Q7, 6V8, 6Z4 or 6X3	£8/6

COAX 80 OHM CABLE.

Stand 3/4 in. diam. Low Loss Semi-Air Spaced Aeraxial.

SPECIAL REDUCED PRICES

20 yds. 12/6, p. & p. 1/6; 60 yds. 32/6, p. & p. 5/-; 40 yds. 22/6, p. & p. 2/6; All other lengths 8d. per yard.

Coax Plugs 1/-, Sockets 1/-, Couplers 1/3, Cable End Sockets 1/6, Outlet Boxes 4/6.

SPECIAL OFFER

Superior type Art leather covered Portable case. Well-known Manufacturer's surplus, in attractive tan colour with non-farsh gilt fittings.

Knockout price **15/6** Post & Pack. 2 6

ALTERNATIVE OFFER

Above case fitted with latest BBR 4-speed TU5 Record Player Unit. Full-FI Xtal pick-up. Ready mounted and wired. Complete with mains lead and detachable screened pick-up lead. An ideal portable record player unit for tape or amplifier use.

Bargain **5 gns.** Post & Pack. 4 6



VOLUME CONTROLS

10,000 ohms—2 Megohms. All long spindles. Morganite Midget type. 3/4 in. diameter. Guar. 1 year. Log or Lin. Ratios. Loss Sw. 3 x .1 D.P. sw. 4/8. Twin Gang control; 1 meg.; 1 meg.; 1 meg.; less Sw. 8/9 ea.

TYGAN FRET (Murphy pattern) 12 x 12in., 2/-; 12 x 15in., 3/-; 12 x 24in., 4/-, etc.

SPEAKERS P.M. 3 ohm 2 1/2 in. Elac. 16/6, 3 1/2 in. Goodmans, 18/6, 5 1/2 in. R. & A. 17/6, 6 in. Celestion 18/6, 7 x 4 in. Goodmans, 18/6, 8 in. Rolat, 20/-, 6 in. Special Cone G.Mans, 21/6, 10 in. R. & A. 25/-

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 1lb 7d., 1lb. 1/1, 2lb. 1/6, 5lb. 3/-, 10lb. 2/6. Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.

TRS

RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Buses: 130A, 133, 159, 166 and 190

LASKY'S RADIO

MAKER'S SURPLUS COMPONENT BARGAINS

WIDE ANGLE 38 mm.

Line E.H.T. Trans. Ferro-cube core, 9-16 kV.....	19 6
Scanning Coils, Low Imp. line and frame.....	19 6
Ferro-cube cored Scanning Coils and Line Output Trans., 10-15 kV, EHT winding Line Trans. with width and linearity controls, circuit dia., pair...	50 -
Frame Output Transformer	6 6
Frame or line block osc. Transformer	4 6
Focus Magnets Ferro-cube P.M. Focus Magnets Iron Cored	19 6
Duomag Focalsisers	22 6
300 m a Smoothing Chokes	10 6


STANDARD 35 mm.

Line Output Transformers 3.9 kV, E.H.T. and 6.3 v. winding, Ferro-cube.....	17 6
Scanning Coils, Low Imp. line and frame.....	7 6
Frame or line blocking oscillator Transformer...	4 6
Frame Output Transformer	7 6
Focus Magnets :	
Without Vernier	12 6
With Vernier	17 6
200 m a Smoothing Chokes	7 6

TV CHASSIS SNIP

BRAND NEW, BY WELL-KNOWN MAKERS

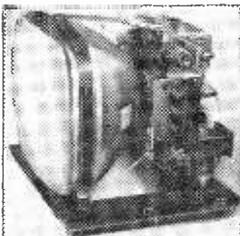For 200-250 v. A.C. mains. 90 deg. deflection, complete with brand new Mullard valves and C.R. Tube. 12-channel turret tuning covering all BBC and ITV channels. Limited number, factory soiled only. Full data and circuit diagram supplied. WORTH DOUBLE



LASKY'S PRICE
21in. 39 GNS.
17in. 29 GNS.

Also a few less valve and C.R. Tube at various prices for caletts.

12-channel TURRET TUNER

Complete with PCC81 and PCF80 valves, I.F. 33-38 Mc/s. Complete with coils for five Band I channels and channels 8, 9, 10. Band III. New and unused. **TO-DAY'S VALUE OVER £7. LASKY'S PRICE 49/6**


20,000 VALVES in stock including new and manufacturers' surplus, also imported Valves. Send for our new list and save money.

'THE' MAYFAIR' TV RECEIVER. Most components are obtainable from our Edgware Road branch.

OUR 100-PAGE COMPONENTS CATALOGUE is a real money-saver! Price 2 -, post 6d., together with our latest "Bargain Bulletin."

LASKY'S (HARROW ROAD) LTD.

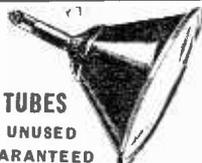Open All Day Saturday, Early Closing, Thurs. Mail Orders to Dept. P.T., Edgware Road, 42, TOTTEHAM COURT ROAD, W.1. 207, EDGWARE ROAD, LONDON, W.2. Telephone : MU 2606. PADDINGTON 3271 2.



C.R. TUBES NEW, UNUSED & GUARANTEED

16in. Metal Cone, famous make. Type T901.B. 6 volt, .3 amp. heater, ion trap, 12-14 kV. E.H.T., wide angle, standard 38 mm. neck. LIST £16.
LASKY'S PRICE £6.9.6.
 Carr. & Insur. 21 -.
 Mastec, Anti-Corona, Bases and Ion Traps available.

FERRANTI 9in. T93, 4 v. heater, triode, octal base, standard deflection. LIST £9.
LASKY'S PRICE 50 -

FERRANTI 12in. T12 H and T12 S1. LIST £12.

LASKY'S PRICE 84/-
 Carr. & Insur. 12 6.


REGUNNED C.R. TUBES
 11 in. £6.10.0 ... Carr. 12 6.
 17 in. £6.19.6 ... Carr. 21 -.
 21 in. £7.19.6 ... Carr. 21 -.

NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE... PRACTICAL... FASCINATING... 1st stage receiver

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation. **AT LAST**—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory. **YOU LEARN BY BUILDING** actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics! **INSTRUCTION MANUALS** and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated text-books are included with the Courses. **IN FACT** for the 'Do-it-Yourself' enthusiast, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation.

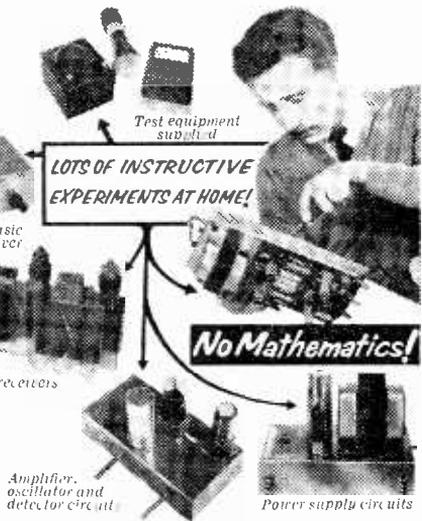

BUILD YOUR OWN • RADIO EQUIPMENT • TEST GEAR • HI-FI INSTALLATION—AND LEARN AS YOU DO IT

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

FREE-POST TODAY

To: RADIOSTRUCTOR, (Dept. G40), 44 Market Place, Reading, Berks.
 Please send brochure, without obligation, to:

Name _____
 Address _____

BLOCK CAPS. PLEASE

(821) We do not employ representatives 1-40

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

SPECIAL NOTE : Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

TELEVISION IN SHETLAND

SIR.—Television in Shetland is only in its infancy. Only a few people have sets as the only signals we can receive come from Medrum, about 180 miles away. Sometimes the pictures are as clear as received in Aberdeen but mostly the signals come and go in a most frustrating manner. It all depends on the weather conditions and the temperature. We hope that when the power of the Orkney station is increased we will get better reception.

One of the pioneers in Shetland is a Mr. Mustard who is a very keen experimenter. Sometimes he receives pictures from Belgium. He said that the effects of the Aurora Borealis could be seen in the pictures. I obtained a second-hand set and found that it was possible; not only can you see the effect but you can actually hear the Aurora Borealis.

I was interested in the article on "A Closed Circuit Colour TV System." I have an article written in 1893 on a closed circuit colour TV system entitled "Seeing by Wire."—A. HARCUS (Shetland).

BBC MONITORING

SIR.—I wonder if the BBC have any standard of monitoring the News Bulletins. Repeatedly I have found that in some cases, there are large white areas with all detail completely missing, in spite of adjustments to my brightness and contrast controls. As scenes change, so does the contrast and I have not found this on the London I.T.A. station, where the adjustment from scene to scene appears to be much more consistent. I appreciate that different scenes have different lighting levels, but is there no way in which the transmitter can be monitored so that the level can be adjusted to suit the majority of commercial sets? After all, most of us have commercial sets with round about 2Mc/s detail and it seems to me from much of the BBC transmission that the level is set for those with 3Mc/s sets.—G. R. CADMAN (Holloway).

AERIAL CHOICE

SIR.—It seems that you have previously mentioned the possibility of our houses eventually becoming overburdened with aerials. I.T.A., F.M. and BBC now present quite an array and I think it is time something was done to find

some arrangement which will cover all eventualities in this direction. I know that in theory the aerial must resonate to the frequency being received, but surely manufacturers do not make separate aerials for each station in the country. Do not they cut the aerial so that it resonates in the middle of the BBC band or in the middle of Band III? I appreciate that if this is done, there is a compromise in the bandwidth, of reception, but I have read that in the U.S.A. special wide-band aerials are now made to ensure extremely wide reception and they use 6Mc/s bandwidth. We do not see any "Bow tie" or similar aerials here, and I would have thought that now was the time to introduce something of this type to avoid the unsightly and perhaps dangerous erections appearing on our roof tops.—F. R. TIERNEY (Peterborough).

[The article in this issue on aerial design will no doubt have an especial appeal to you, and we should be glad to hear from any readers who have tried to make a single aerial to cover I.T.A., F.M. and BBC channels satisfactorily.—ED.]

A TV OSCILLOSCOPE

SIR.—I recently built a 'scope described in your issues, and in case any other readers are building this and run into difficulties I should like to point out a slip which was made in the circuit given on page 499 of the May issue. In this the two lower half-wave units shown next to the words "C.R.T. Heater Winding" are incorrectly drawn and should be reversed. Otherwise I have found this a most useful unit.—R. BEVINS (York).

A PECULIAR FAULT

SIR.—I recently had much correspondence with you concerning trouble in my set. You made several very helpful suggestions, but none of them proved effective in overcoming the trouble. Eventually I decided it was kill or cure, so I took the chassis right out and settled down one evening to a very complete examination. After nearly an hour I solved the mystery and pass on the information in case it may be of help to others who have an apparently insurmountable difficulty. The valveholders were of a type having a flat metal clip inserted in the bakelite moulding and in practice the metal legs of the valves should go down between the metal edges of the clip—the two parts of the clip being diametrically opposite each other on the valve leg. What had happened was that the leg had become slightly bent and as the valve legs went into the holder one of them (actually G2) pushed the two parts of the clip so that owing to its springiness the two parts jumped away from the short valve

leg. Raising it slightly enabled it to make contact, but pushing it right home removed contact. To avoid buying a new valveholder and going to all the trouble of rewiring, I just placed a thin piece of cardboard beneath the valve so that it could not be pushed right down.—D. R. WAITE (Edmonton).

625 LINE DEFINITION

SIR.—Since the announcement that there may be at some time a system available in this country on the 625 line system, I have been toying with the idea of making an experimental set, and owing to lack of a suitable transmission on which to base my experiments I wonder if any of your readers living on the S.E. coast may have access to French or other continental transmissions and have made any tests. The main thing I am interested in is how to switch the frame and line timebases to cover the increased detail. It seems not too difficult if a multivibrator is used, to switch the essential parts so that the frequency will cover either the present low definition or the new high one, and the turret tuner could easily be modified to cover the necessary channel. Presumably the bandwidth would be widened to 4 or even 6Mc/s and I think this could be accomplished by shunting the I.F. circuits and other coils, whilst the F.M. set which most of us now use could be employed for the sound channel. The big snag appears to be in

FRAME GRID VALVES

(Continued from page 174)

Sound Take-off

In fringe areas it is particularly necessary to have a high gain A.G.C. system on both vision and sound signals. Vision A.G.C. must be given priority, since variations of sound level are more tolerable than picture variations.

The vision A.G.C. is normally fed to the R.F. stage and to the first vision I.F. stage, thus giving a substantially constant vision I.F. voltage at the anode of this latter stage. The sound I.F. signal can be taken off from this point, and the sound A.G.C. will then have to handle only the fluctuations of sound-to-vision ratio. The alternative arrangement is to take off the sound I.F. before the first vision I.F. stage. If this is done, then the sound A.G.C. will need to have a control range even greater than that of the first vision I.F. valve.

For this reason it is preferable to use the earlier of these arrangements, in which the first I.F. stage is common to sound and vision.

Fringe Receiver I.F. Strip

The circuit diagram (on page 174) shows an I.F. strip for a fringe area receiver. It consists of a common I.F. stage for sound and vision, followed by separate second I.F. stages. All three stages use the frame grid EF183. The strip would be used with the frame grid PCC89 in the R.F. stage and the conventional PCF80 mixer. It is, in fact, a realisation of receiver "B." Receiver "C" would consist of a PCC89 R.F. stage, PCF86 frame grid mixer, EF183 first I.F., and the separ-

ate sound and vision I.F. stages modified to take the conventional EF80.

RECTIFIER REPLACEMENT

SIR.—In the November issue, I read that one of your readers is having trouble in replacing the U25 EHT rectifier in a Murphy V240. I overcame this difficulty two years ago. I took the complete unit out of the set and with a small blade of a penknife I carefully turned the metal lip back and then poured out the oil. Then I lifted the complete transformer out of the can. After replacing the valve in the usual way I refilled the can with the oil and put the transformer back, pressing the metal lip down with a screwdriver blade, taking care to see that the rubber top was strapped all the way round. After that with the aid of a soldering iron and some bitumen from an old battery, I made an excellent seal good enough to hold the oil without leaking. I put the unit back and I have had no trouble since.—B. W. RODGERS (Sheffield).

[In re-assembly the oil should be introduced into the transformer hot, with the bright metal bung in the rubber top removed. If this is then replaced after the can has been sealed, whilst it is still hot, an airtight seal may result. We hesitate to suggest that readers try this method without some knowledge of their facilities or skill.—Ed.]

ate sound and vision I.F. stages modified to take the conventional EF80.

The "B" version as shown has one or two special features. The screen-grid potential divider currents of V1 and V3 are fed into the cathode resistors of these two valves, giving an improved initial grid control rate (that is, change of gain with change of grid potential). The 1.5V grid bias of V3 is partly cathode bias and partly a voltage of about -0.4 produced in the grid circuit by the contact potential of the EB91. There is no 22Ω compensating resistor in the cathode lead of V3, since the 82pF capacitor on the grid effectively swamps any change of grid-to-cathode capacitance brought about by gain control. Neutralisation is provided by the ±10 per cent. capacitors which are shown.

Performance

The adequate gain provided by the "B" and "C" receivers has already been discussed. In both receivers the first I.F. stage handles large signals without causing cross-modulation. The sound I.F. stage has adequate A.G.C. to handle normal variations of sound-to-vision ratio; and simultaneous fading of sound and vision is eliminated by the vision A.G.C. Receiver "B" using the I.F. strip as shown and a PCF80 in the mixer stage is slightly better than the "C" version for signal-handling ability and sound A.G.C. Receiver "C," with PCF86 mixer and I.F. strip modified to take the EF80 in the separate sound and vision stages, provides rather more gain. The differences, however, are not very great in comparison with the superiority of both circuits over the conventional receiver "A."

guaranteed Tubes REGUNNED NEW

ALL GUARANTEED 12 MONTHS

CRM92, MW22-7, MW22-14	£2/15/-	—	—
MW22-14C, MW22-17, MW22-18	£3/5/-	£5/10/-	—
CRM121, CRM121A, CRM122	£3/15/-	£5/15/-	£7/19/-
MW31-14C, MW31-17, MW31-18	£4/10/-	£6/15/-	£8/19/-
121K, 141K, AW36-21, C14FM, CRM141, CRM142, MW31-16	£5/5/-	£6/15/-	—
MW31-74, ME36-24, MW36-44, C17FM, CRM171, CRM172, MW43-64, MW43-69, C14BM, C17BM, CRM151, CRM152A, CRM152B, CRM153, MW43-80, MW41-1, MW53-20, MW53-50	£6/15/-	£9/10/-	—

NEW 108K TV TUBES SPECIAL OFFER : £2/19/-

THAT SECOND SET? 13 CHANNEL T.V.'s COMPLETE, UNTESTED

12" — £3.19.

14" — £7.10.

CARRIAGE FREE BUT AT CUSTOMER'S RISK ALSO 12" 5 CHANNEL T.V.'s UNTESTED 55/- CARRIAGE

100 CONDENSERS 10/-

A must for your spares box. A well-balanced assortment of miniature silver mica and ceramic condensers. 3-10,000 PF. List value over £5.

GUARANTEED P.M. SPEAKERS. Standard 3 ohms, ex-equipment, tested top makes, performance guaranteed.

6in. 7/- 5in. 11/- 10in. 13/-

EXTERNAL I.T.V. CONVERTERS WITH INTERNAL POWER PACK. Well-known make at a very competitive price, completely enclosed. Finished in hammered gold. Very compact. Can be put inside practically all T.V.s. Gain and Trimming controls. Listed at £3/10/- £7.7.0. Our Price, Carr. 2/6. £3/10/-

FAMOUS MAKE KITS AMPLIFIER, £5.15.0. P/M £8.19.0.

PHILIPS OPTICAL PROJECTION UNITS Complete with MW6 C.R.T. untested £2.19.0

TUNING CONDENSERS .005 twin gang, 4/-

PICK-UP CARTRIDGES ACOS, 22/6. POWER POINT, 18/6. STEIG AND REUTER, 15/-, SONOTONE, 17/6

CO-AXIAL CABLE

Semi-Air-Spaced low loss. 1-19 yds. 7d. per yd., p. & p. 1/3. 20-39 yds., 6d. per yd., p. & p. 1/3

50 YARD DRUMS 22/6. P. & P. 2/- 100 YARD DRUMS 40/- P. & P. 3/-

INFRA RED HEATERS

1,200 w.: 2ft. 9in. long..... £3.5
2,000 w.: 2ft. 9in. long..... £3.15
AMAZING VALUE 5/- carr.

100 RESISTORS 7s. 6d. A WELL-BALANCED SELECTION—A MUST

H.T. RECTIFIERS

280LU779A (240 v. 80 mA.), 5/- RM1, 6/- RM2, 6/6. RM3, 9/- RM4 (ER4), 15/6. RM5 (ER5), 21/- 14A86, 17/- 14A97, 23/- 14A100, 25/- 18RA, 1-1-16-1, 7/6. 14RA 1-2-2-2, 18/- 18RD 2-2-2-1, 14/- 14RA 1-2-2-3, 22/- BURWELL T.V. AERIALS. Complete Illustrated Price List of 1 to 12 element Band I and II aerials at amazing competitive prices (3d. stamp).

TRANSISTORS AND DIODES RED SPOT. Transistors for I.F., L.F. and Output up to 800 kc/s, 4/8 ea. (4/8 each in dozens). WHITE SPOT. R.F. and I.F. 2.5 Mc/s. 7/- (6/6 each in dozens). KA103, 15/-; KA104, 17/6; XB104, 10/-; GET15, 25/-; 745/10P "GOLTOP" 15/- GERMANIUM DIODES. General purpose famous makes 9d., 8/- doz. DIODES. Equivalent to GEX44 3/8.

B.S.R. MONARCH UA8

4-speed mixer Autochanger £7.19.6

COLLARO "CONQUET"

Hi-Fi 4-speed, 10 record Autochanger. Brand new, untested. £6/19/6 Limited Quantity

STEREO: Famous make single player. Stereo equipped. Unrepeatable at this price. £6/19/- Carr. 3/-

4-SPEED RECORD PLAYERS

Latest Turntable, together with lightweight Star Galaxy dual supply crystal (turnover pick-up) head. Truly amazing value. at £3/10/- Carr. 3/-

TRADE ENQUIRIES INVITED ON ALL ITEMS. SPECIAL TERMS FOR QUANTITIES.

VALVES ALL GUARANTEED 3 MONTHS PL81 SOLED. AMAZING 7/- VALUE AT ONLY 7/- EY51 SHORT ENDS 6/- U25 SHORT ENDS 8/-

074	5/6	6BR7	10/6	6P28	9/6	12BA6	8/-
1A3	2/6	6BW6	7/6	6Q7G	7/6	12BE6	9/-
1A3GT	6/-	6BW7	7/6	6Q7	9/3	12C8	6/6
1A7GT	12/6	6BX6	5/6	6SA7	6/-	12J3GT	3/6
1C5GT	10/6	6C4	4/-	6SD7	9/-	12K7GT	6/6
1D3	2/6	6C5	5/6	6SG7	5/-	12K8GT	6/6
1HG7	10/6	6C6	4/3	6SH7	4/6	12L-	12/-
1L4	3/9	6C9	9/6	6SJ7	5/6	12Q7GT	6/-
1N5GT	9/9	6C10	8/9	6SK7	5/6	12R67	6/-
1R5	7/6	6CD6G	18/6	6SL7GT	6/-	12SK7GT	9/6
1R5	6/6	6CH6	9/6	6T	10/6	12S7GT	9/6
1T4	5/3	6D2	4/-	6SN7GT	4/9	14S7	13/6
2A7	8/6	6D3	6/6	6S87	6/6	19A25	7/6
2D21	4/6	6D6	4/6	6U4GT	10/6	19BGG6	16/-
3A5	9/6	6F1	6/6	6V6G	5/6	19-	18/-
3A5	6/6	6F6G	8/6	6V6GT	8/6	20D1	9/6
384	7/-	6F12	4/-	6X2	9/6	20P2	9/6
3V4	7/9	6F13	6/6	6X4	6/-	20L1	12/6
3R40	9/6	6F14	5/6	6X5G	5/-	20P1	11/6
5U4G	5/9	6F15	8/6	6X5GT	8/6	20P3	12/6
5Y4G	9/6	6F2	6/6	6T4	11/6	20T4	15/-
5Y4G	6/-	6F6M	2/-	7B6	8/-	25A8G	8/6
3Y3GT	7/-	6J5	4/6	6B7	7/6	25L6G	6/-
3Z4G	9/-	6J6G	2/-	7C5	7/6	25L6GT	9/-
2Z4GT	11/-	6J3GT	3/6	7C6	7/6	25Y3G	9/-
6A7	9/6	6J6	2/6	7H7	7/6	25Z4G	7/9
6A8G	8/6	6J7G	9/6	7K7	8/-	25Z6	9/6
6A8B	2/6	6J7GT	6/6	784	9/6	27S1	16/-
6A7	4/6	6K6GT	6/6	797	7/6	30C1	7/9
6A7	6/-	6K7G	2/3	10C1	9/-	30P11	9/6
6A7	4/6	6K7GT	3/3	10C2	12/6	30L1	7/9
6A8G	6/6	6K8	9/6	10F1	9/6	30P4	12/6
6A5L	4/-	6K8GT	9/6	10F9	12/6	35L6GT	9/6
6A6M	4/-	6K25	7/6	10P13	12/-	35W4	6/9
6A6Q5	6/9	6L1	13/6	10P14	12/-	35Z4GT	8/6
6A76	7/-	6L6G	7/6	12A7H	8/-	35Z6GT	8/6
6B9G	3/6	6L7	6/-	12A18	10/6	7/6	CL33
6BA6	6/6	6L18	9/6	12A7F	8/6	50C5	10/6
6BE6	6/6	6L19	11/6	12A7T	6/6	30L6GT	6/6
6BG6G	12/6	6LD20	8/6	12A7U	8/6	53K10	10/6
6B36	6/6	6P25	7/6	12A27	7/6	34K10	8/6

VALVES

PRICES REDUCED GUARANTEED 3 MONTHS. 24 HOUR SERVICE FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days. A.S.E. POST LIST OF 300 TYPES.

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozens). Post: 1 valve, 6d.; 2-11, 1/-

5/-	D152	6/6	EA50	9d.	ECC81	3/6	EN1
6/18	DA30	12/6	EABC80	7/9	ECC80	10/6	EN10
6/18	DA100	25/-	EAC81	5/3	ECC82	10/6	EN11
6/18	DA91	8/6	EBA4	1/6	ECH42	8/9	EN16
6/18	DAF95	8/3	EB41	7/-	ECL50	8/6	EN18
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN20
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN21
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN22
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN23
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN24
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN26
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN27
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN28
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN29
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN30
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN32
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN33
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN34
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN35
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN36
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN38
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN39
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN40
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN41
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN42
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN44
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN45
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN46
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN47
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN48
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN50
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN51
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN52
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN53
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN54
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN56
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN57
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN58
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN59
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN60
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN62
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN63
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN64
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN65
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN66
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN68
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN69
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN70
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN71
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN72
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN74
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN75
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN76
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN77
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN78
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN80
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN81
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN82
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN83
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN84
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN86
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN87
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN88
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN89
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN90
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN92
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN93
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN94
6/18	DF96	8/6	EB41	8/6	EP39	4/6	EN95
6/18	DF96	8/3	EB41	7/-	ECL50	8/6	EN96
6/18	DF33	9/-	EB91	4/-	ECL52	11/-	EN98
6/18	DF36	5/3	EB3	9/-	EP36	2/6	EN99
6/18	DF92	5/3	EB33	5/-	EP37	4/6	EN100

EP91	4/-	KT263	5/-	8U2150A	4/6	UF6	9/6
EP92	4/9	LB3	2/9	4/6	UP6	16/-	16/-
EP95	6/6	LM152	8/6	T41	7/6	UP89	8/6
EL32	4/-	JN309	11/6	U18	9/-	UL41	7/6
EL32	9/-	L2318	7/9	U22	6/6	UL44	12/6
EL55	12/6	MU14	1/6	U44	9/6	UL46	9/6
EL41	9/3	S37	11/-	U25	12/-	UL84	8/3
EL42	9/6	X78	15/-	U26	12/-	UM90	9/6
EL54	8/3	N108	11/-	U31	7/9	UM96	9/6
EL85	11/-	P41	4/6	U33	11/-	U107	9/6
EL91	4/9	P61	2/3	U35	8/6	U108	16/6
EL95	9/6	PC84	7/9	U50	6/-	U19	7/-
EM34	9/3	PC85	9/6	U52	6/3	U14	6/6
EM80	9/3	PC89	18/-	U78	6/-	U585	7/6
EM81	9/3	PCP80	7/9	U91	9/6	U1R150	30/-
EM84	10/6	PCP82	9/9	U91	9/6	1-	7/-
EM85	10/6						

D.C. OSCILLOSCOPE



A.C. MAINS 200-250 VOLTS

SIMPLIFIED SERVICING PROBLEMS WHEN USING THE 'TESTGEAR' SCOPE 3in. D.C. OSCILLOSCOPE

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain extremely stable differential Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking T.V. Line O/P Transformers, etc.; Provision for external I.P. and CRT Brightness Modulation. Size 10in. high, 6in. wide, 9in. deep. Wgt. 11 1/2 lbs. £15.15.0. plus P. & P. 7/6, or 30/- deposit, plus P. & P. 7/6 and 12 monthly payments of 28/6.

FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE.

WOLSEY 3-ELEMENT FOLDED DIPOLE

I.T.V. Aerial less mounting bracket for External use, complete with 12 yds. of coaxial cable, 15-; 4 element, 17/6; 5 element, 25/- P. & P. on above, 3/6.

E.H.T. Smoothing Condenser 500 p.f., 18 KV. D.C. 1/6. working.

LINE E.H.T. TRANSFORMER

By famous manufacturer. 14 Kv. Complete with built-in line and width controls. Winding for EY51 Rectifier. 19/6 P. & P. 2/6.


CHANNEL TUNERS

Will tune to all Band I and III stations. Brand new by famous manufacturer. Complete with PCC84 and PCF80 valves (in series).

4 P. 16-19 Mc.s or 33-38 Mc.s, also can be modified as an aerial Converter (instructions supplied). Complete with knobs 22/6, plus 3 P. & P.

HEATER TRANSFORMER to suit the above, 200/250 v., 6-, plus 1 P. & P.

SIGNAL GENERATOR

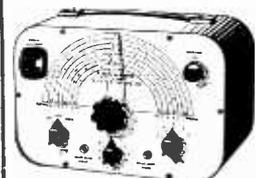

£6.19.6 or 25/- deposit and 6 monthly payments of 21/6 P. & P. 5/- extra. Coverage 100 Kcs-100 Mc.s on fundamentals and 100 Mc.s to 200 Mc.s on harmonics. Metal case 10in. x 6in. x 5in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal Modulation of 400 c.p.s. to a depth of 30%, modulated or unmodulated R.F. output continuously variable. 100 milli-volts.

C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

F.M. TUNER UNIT I.F. 10.7 Mc/s.


Permeability tuned, by famous German manufacturer. Coverage 88-100 Mc.s. Complete with ECC85, size 4in. x 2in. x 2in.

25/- P. & P. Circuit Diagram 1-, FREE with Unit.

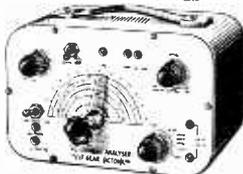10.7 Mc.s. I.F. and discriminator coil 2/6 per pair.

ALIGNMENT ANALYSER TYPE MC12

A.C. mains 200/250V. Provides: "Wobulator" (Swept Frequency) operation, for FM-TV alignment linear frequency sweep up to 12 Mc.s. From 400 kc s-40 Mc.s. Capacitance Measurement. Two ranges provided 0-60pF and 0-120pF. Special Facility enables true resonant frequency of any tuned cct. I.P. transformer, etc., to be rapidly determined. Cash price £8.19.6, plus 5/- P. & P. H.P. Terms, 25/- deposit plus 5/- P. & P. and six monthly payments of 21/6.



RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3. All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

TV TUBES

LEADING MAKES

£10 21 in. £14

Makers' years guarantee

or

Our Brand Nu-Gun Tubes

£7.10.0 or 8/6 for 20 weeks

Immediate delivery

13 months' guarantee

Carriage and Insurance Paid

Engineers required all areas

EXPRESS ELECTRONICS

281 Parliamentary Road, GLASGOW

BEL 4569

GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

METERS, 500-0-500 Microamp. 3in. dia. 37/6 ea. Dual Range 0-5 v. 0-100 v. FSD 1 m a, 20 - ea. : 50-0-50 Microamp., 2in., 30 -
I.T.A. AERIALS. New 3 element 22/6, 5 element 27/6.
CO-AX CABLE 6ft. yd. AIR SPACE (19) 3d. DIPLERS 12 -
GERMAN DIODES 1/-, 10 - doz. TRANSISTORS from 6/-,
VOLUME CONTROLS, Long Spindle Midget, 10 K-2 Meg. Less Switch. 3/-, D.P. switch 4/6.
CONDENSERS, Twin Gang .0005 Standard 5/6. Midget 6/6.
VENER SYN. METRS. 200 250 v. with gear train driving. 3 dials, 110-1,000 hrs. 25 - ea.
SEL. RECS. 12 v. 1 amp. 5/-, 2 amp. 11/6. 4 amp. 15/-, 500 v. 4 amp. containing 30.35 mm. discs. 10/- ea.
12 WAY P.V.C. CABLE. Screened & P.V.C. covered, 2/6 yd.
ELECTROLYTICS, Canned. 20-20 mfd. 450 v., 2/6 ea. 25 - doz.
VAR. SLIDERS, 10 ohm 30 w. for chargers, trains. 3 - ea.
FERRITE Rod Aerials. Med. & Long Wave. 10/- ea.
CONNECTING WIRE, P.V.C. 100ft. 2/6, various coils.
RELAYS, Large stocks, assorted sizes, from 2/6 ea.
MICROPHONES, Carbon 5/6. Inserts 2/6. Tannoy 7-. Throat 4/6. Button 2/-, Trans. 4/6. Acos Crv. 33 1/2, 28/6.
VENER SLIDER-ZINC ACCT. MULTIPLIERS. H105, New 15/-.


VALVES TESTED ON MULLARDS ELECTRONIC TESTER

1L4	5/-	6D2	6/-	6X4	7/-	EA50	1/6	EY51	5/-
17A5	6/6	6P1	7/6	6X5	7/-	EABC80		EY51	8/-
1U4	6/-	6F6	7/-	8D2	4/6			P61	4/6
3A4	6/-	6F13	7/6	9D2	5/-	EB41	7/6	PEN45	7/6
5Z4	9/-	6J5	6/-	10F1	7/6	EB91	5/6	PEN46	7/-
4D1	4/-	6J6	6/-	12A6	7/6	ECH42	8/-	SP41	4/-
6AG5	5/-	6J7	6/-	12A8	8/-	ECH80	9/-	SP61	4/-
6AL5	5/-	6K7	4/6	12AT7	6/-	EF36	5/-	VR150/30	
6AM5	5/-	6L6	6/6	12AU7	7/-	EF37	9/-	UL84	9/-
6AM6	6/-	6SA7	6/-	12AX7	7/-	EF39	5/6	UL48	9/-
6AQ5	6/-	6SC7	4/6	12BH7	10/-	EF50	3/6	VCR97	
6AU6	7/-	6S7	5/-	12SH7	5/-	EF50	5/-		15/-
6BA6	9/-	6SK7	5/-	12SQ7	6/6	EF80	8/-	VCR138A	
6BE6	5/6	6SL7	6/-	12SK7	5/-	EF91	6/-		25/-
6BH6	5/-	6SN7	7/-	15D2	6/-	EF92	7/-	VCR139A	
6BW6	6/6	6U5	6/6	50C5	10/-	EL32	5/-		25/-
6C4	5/-	6V6	6/6	807	8/-	EL91	5/6		25/-

SECONDHAND VALVES, YOUR CHOICE, £1.0.0 for EIGHT: ECL80, 6C4, 6AM6, 6AG6, 6J6, EF50, 6BE6, 3A4, EF30, SP61, P61, 6L5, FY30, FY32, 7Z7, 6AL5, 6Y3, EL33, EF42, 6D2, 20P1, 6F13, SP41, EY51, EB91, EF91, EF39, PCL83, EF36, PEN45, PEN46.

HUGGETT'S LIMITED

2-4 PAWSONS ROAD, WEST CROYDON

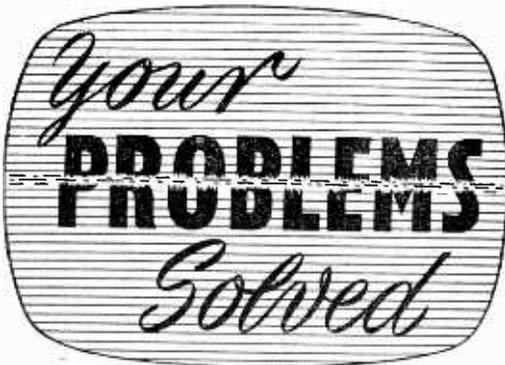

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 215 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

MURPHY V200A

A fault has appeared and I shall be very glad of your advice. Most of the valves have only recently been tested—V3, 9 and 10 are new. The fault, which is intermittent, causes the whole picture to appear out-of-focus. Similarly, "bands" of the picture about 1in. wide will appear out-of-focus, the part of the picture affected appearing to move aside approximately 1/16in. C32 and C39 have been replaced by new ones. C34 and 57, C61, C49 and 64 have been tested. C65 and 66 have been replaced—the power factor on test being poor, but the new replacement has not affected the slightest improvement in the picture.—R. D. Rapley (Hayes, Middx).

Your fault is a heater-cathode leakage on the C.R.T. This may be cleared by fitting a 2 volt low capacity C.R.T. transformer instead of the present heater supply. Remove the existing heater and other wiring before connecting the 2 volt secondary of the transformer to the C.R.T. base and use chassis and the top end of the mains fuse as useful points to obtain a switched mains supply. The transformer should mount on the two holes at the bottom of the rear hoop holding the chassis.

G.E.C. BT5145

A few seconds after the picture comes through it begins to break up from the top and is quickly blotted out by horizontal lines about 1/4in. apart, very similar to sound on vision but permanent. If I switch off then on again after a few seconds, the same thing happens. It seems a perfect picture for those few seconds. Also the focusing magnet has to be set at an acute angle to get the picture in centre. Is this likely to cause any trouble?—T. Sherliker (Kings Heath, Birmingham).

The break-up of the picture may well be caused by a drift in the line oscillator valve as it warms up. You would be advised to check this valve by substitution.

No harm will result from having the focus magnet set as described. The reason for this could be in the tube itself—this may have a gun assembly which is twisted—or a faulty magnet producing an incorrect field on the tube axis.

MARCONI VT3DA

Could you please let me know the following: Vision I.F. frequency, sound I.F. frequency, C.R.T. heater volts and current.—M. Nevill (Welling, Kent).

The I.F. is sound 10.5Mc/s, vision 14Mc/s. The tube is an Emitron 14KP4 (Mullard equivalent MW3624) which has a 6.3V, 0.3A heater.

FERGUSON 997T

For the past 10 days or so the whole picture shakes sideways, only a very small amount and very quickly. Apart from this the picture and sound are good. I have read all the servicing information on this set published in your journal and I have tried everything I can think of including valve substitution (renewal of EY51), checking screening can to chassis, etc. When the trouble first started I put it down to atmospherics. I will be grateful for any suggestions you can offer.—A. Leslie (Sutton, Surrey).

This fault is caused by trouble in the line fly-wheel circuits. In most cases the trouble is the result of a fault in V15, V16 or V17, these being the two EF80's situated either side of the line oscillator transformer in the near left-hand corner of the chassis when viewing from cabinet rear, and the EB91 directly behind the transformer. Check with valves known to be in good order.

Another cause is alteration in value of the 0.01 μ F capacitors (2) across the windings of the line oscillator transformer. They are contained in the screening can.

FERRANTI 14T3/D (Converted)

The above set was given to me with sound O.K. on both channels. The raster is working, but there is no picture. I have tried all appropriate valves by substitution, but now have no raster and the sound is completely dead although all valves light up except EY51. Your comments would be appreciated.—L. Ramsey (Streatham, S.W.16).

The original fault may be caused by breakdown of a decoupling capacitor and resistor in one of the vision I.F. stages. A close study of the components will reveal the burnt resistor. The capacitor should also be replaced.

The additional fault is caused by failure of the line oscillator. You may have instigated a short-circuit during your previous tests, or the line output transformer may have broken down.

COSSOR 930

I should be pleased if you would tell me how to connect the Philco turret tuner No. A1747 to the above set. The arrangement appears different from standard and I have no circuit diagram of the tuner. I enclose a copy of the instructions. I have already altered the leads on the turret tuner plug to correspond to the 6BX6 socket

of the Cossor.—A. C. Wildsmith (Nevilles Cross, Durham).

We suggest you proceed as follows: Short R7, remove C11 and take the H.T. end of R12 to chassis. Remove V1 and V2 and plug in the two plugs from the tuner. The V2 plug should be amended so that the wire which went to pin 1 goes to pin 7, the wire which went to pin 2 stays there. The wire which went to pin 3 goes to 5 and 1, the wire which went to pin 6 goes to 8, and the wires to pins 7 and 8 are taken to 5 and 1. The heater wires now go between 4 and 5, instead of between 9 and 4 and 5 joined. L4 will now take the place of T5 in the instructions.

PYE FV1

The EHT on this set suddenly ceased. I fitted a new EY51, but still no EHT. I then examined the line output transformer and found a short on the heater winding. I fitted a new transformer, improved type with anti-corona cup, but still no EHT. The EY51 heater does not light. I have changed the frame and line oscillator valves, the line H.T. volts are only 125 volts but should be 200. I have changed the rectifier and the main condenser, but the H.T. volts are still 125.—J. Macey (Barking, Essex).

Your low H.T. is associated with your present trouble, and the metal H.T. rectifier or 100 μ F section of the smoothing condenser are usually the culprits. Check these two items again and ensure that you have 230V A.C. on the mains side of the metal rectifier.

If overheating takes place you may have an H.T. short, and if this coincides with the disappearance of your EHT we advise you to suspect the deflector coils. These may be checked by disconnecting their line coil feeds. If they are faulty this action will restore EHT.

MARCONIPHONE VT53DA

The picture "jitters" so that there are two pictures, vertically. Frame linearity and vertical hold will remove fault, but adjustment is critical, and the vertical hold is at extreme setting so that the picture is liable to roll. Please can you advise me as to the trouble?—R. F. Angel (Potters Bar, Middx).

Sharply tap KT33C valve to see if this is causing the jitter, then check the small red and black rectifier (WX6) which is on the long tag strip under the chassis (interlace diode) and the associated 330pF filter capacitor.

ULTRA Y73

Can I use a Mazda C.R.M. 171in. tube in an Ultra Y73 combined TV and radio receiver? I note in the data booklet, the scanning angles are given as 51deg. for C.R.M. 151 and 69deg. for C.R.M. 171 tubes. I can overcome the tube mounting difficulties and also heater supply, but will the present line timebase have sufficient power to scan the C.R.M. 171 tube?—J. Roe (Brighton 6).

Although the C.R.M. 171 can be fitted you may find the line power insufficient to scan the tube horizontally. However, the resultant lack of width will not be severe. It is corner shadows which

may prove most troublesome. As far as the heater is concerned, the 2V supply will have to be removed and a 12.6V transformer installed. The required first anode supply for pin 10 may be derived from the junction of the width and linearity coils.

FERGUSON 989

I have a Ferguson 989 which I would like to convert to receive Channel 10 STV. I have a 13 channel tuner, but I do not know what stages to cut-out or what other connections to make. I have a circuit diagram for the set.—A. Cameron (Whiteinch, Glasgow).

The tuner unit must have an I.F. output of 16-19.5Mc/s, oscillator high, and must have series heaters (PCC84/PCF80). You must identify the various tags or leads such as the two heater tags (L.T.), the H.T. tag, the I.F. output and the cathode and grid tags (if any). You should remove the rear right side EF80 (V1) and the next EF80 (to its right) which is V2. Join pins 4 and 5 on V2 socket together. Connect the tuner heater leads to pins 4 and 5 of the V1 socket. Join the H.T. lead to pin 8 of the V1 socket. Join the I.F. output (inner) to pin 7 of the V2 base with the screening of the coaxial cable joined to pin 3. Join the cathode connection (if any) of the tuner to pin 3 of the V1 base and the grid connection (if any) direct to chassis (of the tuner). Connect the metal of the tuner to the receiver chassis with a length of braiding to ensure good contact.

AMBASSADOR CONSOLE

I have a 2V output and boost isolation transformer with which I wish to boost a 2V tube in an Ambassador (15in. round tube) console set, the tube being a Mazda C.R.M. 1523.—D. Walters (Alfreton, Derby).

As you do not quote the receiver model number we must assume this to be TV10C. When fitting the transformer, first remove the existing heater leads to pins 1 and 12 on either side of the keyway. These leads must be separately taped, not joined. The secondary leads from the transformer are soldered to pins 1 and 12 in their place, leaving the 100kilohm resistor in position. The primary leads are taken, one to chassis, one to the 230V mains tap or to the on/off switch. If desired both leads may be connected to the on/off switch.

ALBA T744

Quite recently my 17in. television set has been giving trouble. On switching the set on in the evening, the picture is very good and full size, but after a while it is reduced in size by a black section along the bottom and right-hand side. This section cannot be cleared by any of the controls. If a particularly light coloured picture is shown, a black semi-circle appears at the top of the screen, and gradually blots out the whole picture. A slight turn of the contrast control, to darken the picture, and the picture immediately appears although, of course, darker than at first.

(Continued on page 215)

LOUDSPEAKER UNITS
 All Brand New. Note the Special Prices.
 All Permanent Magnet 3 ohms Impedance.
 1 1/2 in. square Celestion ... 18/6
 2 in. square Celestion ... 18/4
 3 in. square Elac ... 19/6
 5 in. round Goodman, Celestion & Plessey 18/6
 6 in. round Celestion ... 17/6
 8 in. round Elac & Celestion ... 22/6
 8 in. round Plessey ... 32/6
 6 in. x 4 in. Plessey ... 19/6
 6 in. x 4 in. Plessey & Goodman ... 19/6
 6 in. x 5 in. Allen (Golden) ... 25/6
 8 in. x 6 in. Goodman & Celestion ... 25/6
 Special Offer: 8 in. Golden Eight, 15 ohms
 speech coil, 42/6.

TRANSFORMERS 3-WAY MOUNTING TYPE
 NT1 Primary 200/250 v., Secondaries 250-4-20 v. 80 mA., 0-6.3 v. 4 A., 0-4 v. 2 A., both tapped at 4 v., 21/9 each.
 NT2 Primary 200/250 v., Secondaries 350-0-30 v. 80 mA., 0-6.3 v. 4 A., 0-5 v. 2 A., both tapped at 4 v., 21/9 each.
 NT2 Primary 200/250 v., Secondary 30 v. 2 A., taps at 3 v., 4 v., 6 v., 8 v., 9 v., 10 v., 15 v., 20 v., 24 v., 21/9 each.
 Postage and packing please add 2/- per transformer.

RECORD PLAYER UNITS
 B.S.R. Monarch Model U48, 4-speed, 10-record capacity, Full-F1, turnover crystal cartridge. £8.4.6
 Collaro Conquest, fully mixing changer on 7 in., 10 in., and 12 in. records, fitted with Studio "0" crystal cartridge. £7.19.6
 Garrard RC120/D 11, 4-speed automatic unit, manual control to enable records to be played singly. £8.17.6.
 Collaro AC4/564, 4-speed single player with automatic stop, fitted Studio "0" crystal cartridge. £8.19.6.

Fico One-in-One Radiometer, for all practical testing. 32/6.
 Tavana Soldering Irons. 40 watt. 16/9 each.

ALPHA RADIO TERMS.—Cash with order or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 15/-; 20/- add 1/9; 40/- add 2/6; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

ALPHA RADIO SUPPLY CO.

VALVES GUARANTEED ALL TESTED BEFORE DESPATCH

CY31	16/7	KTW61	6/6	5Z4G	9/-
DAF96	9/9	OZ4	5/6	6A7	10/-
DF96	8/9	PCC84	9/-	6AL5	6/6
DK96	8/9	PCF80	9/6	6AM6	5/-
DL96	8/9	PL81	12/6	6F6G	7/6
EBC33	6/9	PL82	8/6	6F1	14/-
EBC41	9/6	PX25	12/6	6F13	14/-
ECC84	10/-	PY80	7/6	6F15	14/-
ECC85	9/6	PY81	8/6	6K7G	4/-
ECCF80	12/-	Pen4VA	15/-	6K8G	7/6
ECH42	9/6	Pen25	6/-	6L6G	8/-
ECH81	9/-	PenA4	15/-	6L18	11/6
ECL80	10/-	SP41	3/-	6Q7G	7/6
EF39	5/9	SP61	3/-	6SL7GT	9/-
EF40	14/6	U14	8/6	6SN7GT	7/6
EF41	9/9	U25	14/-	6U4GT	12/-
EF42	11/-	U191	11/6	6V6G	6/-
EF50	4/-	UCH42	10/6	6V6GT	7/9
EF96	13/-	UF41	9/-	6X5G	7/-
EL41	10/6	VU39	9/-	12AT7	7/6
EL42	10/6	(MU12)14/8/9	12AT7	12AU6	8/-
EL84	9/-	1C5GT	12/6	12AX7	8/-
EM80	10/-	1H5GT	9/-	59/6	8/-
EY51	10/-	1N5	10/6	12C9	9/-
EY86	10/-	1S5	6/6	25A8G	10/6
EZ50	7/6	1T4	6/-	25L6GT	10/6
EZ80	7/-	3S4	7/6	3Z4GT	8/-
GZ32	12/-	3V4	8/6	42	8/-
KT33C	8/6	5U4G	6/6	KT66	17/6
KT66	17/6	5Y3GT	8/-		

CATALOGUE
 Our 1960 catalogue is now available. Please send 1/- in stamps for your copy. Trade Catalogue also available. Please attach your Business Letter Heading.

ACOS MICROPHONES
 Acos Mic 39-1. Crystal Stick Microphone for use as a hand, desk or floor stand unit for high quality recording, broadcasting and public address work. List Price £3.5.0. OUR PRICE 39/6. With stand. 47/6. With Floor Stand Adaptor. 52/6. Postage 1/6. Mic-40, as supplied with most modern tape recorders. With folding rest and 8ft. lead. Listed at 35/- . OUR PRICE 25/- . 40 to 6,000 c.p.s.

TELEVISION TUBES
 Re-gunned. 12 months guarantee. All types available—typical examples MW 43.64 £6. CRM 141 £5.10.0. CRM 171 £6. Carriage & ins. 10/- extra.

RECTIFIERS FOR BATTERY CHARGERS
 12 v. 1 amp. ... 4/3 | 12 v. 3 amp. ... 10/-
 12 v. 2 amp. ... 7/- | 12 v. 4 amp. ... 12/-
 12 v. 5 amp. ... 14/6

TELEVISION BAND III CONVERTORS
 INVICTOR Mode. 245. Self-contained own power unit. Bands 6 to 10. Listed £9.19.6. **OUR PRICE £3.19.6.**
 INVICTOR 13 Channel Adaptor, for Models 118, 119, 120. Listed £7.19.6. **OUR PRICE £9.19.6.**
 WOLSEY TC185 Aerial Converter. Listed £9.19.6. **OUR PRICE £3.19.6.**

CARY UNIVERSAL TEST METERS
 Pocket size multi-range test meters of excellent quality, cover all the most useful ranges (A.C. volts, D.C. volts, resistance and current). Supplied complete with test prods, instruction book and batteries.
 Model A-10 (2,000 ohms per volt) £4.17.6
 Model B-20 (10,000 ohms per volt) £6.10.0
 Plus P. & F. 3/6 on each.
 Fully detailed and illustrated leaflet available.

103 LEEDS TERRACE, WINTOUN STREET, LEEDS, 7.

A television course for you to study at home

Entirely new! Practical!
Bang up to date!

THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains numerous clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all the relevant knowledge that you need to know!

This is what you've been looking for! You can now gain thorough knowledge of this vast subject in your spare time at home. The course includes: production of the signal,

scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost you very little, the book you need is included in the cost.

To THE BENNETT COLLEGE
 (DEPARTMENT A55) SHEFFIELD

Please send me details of the new
 Television Servicing Course

NAME _____

ADDRESS _____

AGE _____

TELEVISION SPARES

All Makes All Models By return of post

- LINE OUTPUT TRANSFORMERS FRAME OUTPUT TRANSFORMERS
- DEFLECTOR COILS
- LINE AND FRAME BLOCKING OSCILLATOR TRANSFORMERS
- ALL POTENTIOMETER AND SLIDER CONTROLS
- MAINS DROPPERS METAL RECTIFIERS
- GERMANIUM DIODES FOCUS MAGNETS
- ION TRAPS E.H.T. CONDENSERS

Our Range of Spares is probably the most extensive in the country and includes all Spares for Tape Recorders, Radio and Record Player Units.

Technical Advice Free. Service Manuals supplied on loan.

Terms: C.W.O. or C.O.D. All Components are supplied at list prices, plus 2/6 p.p.

Please enclose S.A.E. with all enquiries.

NEWBURY RADIO

272, ROMFORD ROAD, FOREST GATE, LONDON, E.7.

MARyland 3100

NOW!
UNBEATABLE PRICES
12 MONTHS GUARANTEE
ELECTROVAC
BRAND NEW GUN
CATHODE RAY TUBES

Under the ELECTROVAC process at our fully equipped factory of over 6,000 sq. ft., all tubes are opened, ALL expendable parts removed, a Brand New Electron Gun fitted and a vacuum produced to give a performance and life AS NEW. Progressive picture and vacuum tests over five days ensure the utmost reliability in service. Each tube carries an unconditional **Twelve Months' Guarantee**. The following are prices for the most widely used types, ex stock:

12"	Mullard, Mazda, Ferranti, Emitron Cathodeon, G.E.C., Cossor Types	£6.6.0
14"	" " " "	£6.6.0
17"	" " " "	£7.7.0
21"	Mullard, Mazda, Ferranti, Cossor and Emitron types	£9.9.0

Plus carriage, packing and insurance 10%, refundable in full on receipt of old tube in our carton supplied.
 Cash with order. Regret no C.O.D.

ELECTROVAC MANUFACTURING CO. LTD.
 (Dept. P.T.12) Chapel Works, Sunnyside Road, Chesham Bucks.

For Safety's Sake
 use
AVO Prodclips

Pat. No. 748811
 with Trigger-Action Spring-Loaded Clips

PRESS TRIGGER TO OPEN
 RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prodcs. they are invaluable for reaching and holding test points which are difficult of access.

Post Free
15/-
 per pair.

AVO LTD · AVOCET HOUSE,
 92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
 VICtoria 3404 (12 lines)
 A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES.

If the set is left completely alone, the picture only appears again if a darker scene is shown. As this darkening of the screen only occurs during certain programmes, I cannot think that there is much wrong with the set, and would very much appreciate your help in rectifying this fault.—J. T. Stonehouse (Bradford, Yorks).

We would advise you to change the PY82 H.T. rectifier, centre the picture by means of the shift lever on the focus assembly and set the ion trap magnet on the rear of the tube neck for maximum brilliance. If the picture still fades in bright scenes, change the EY86 EHT rectifier valve.

G. D.C. BT2747

Please can you give me details for replacing C.R.T. 7401A in the above model?—J. Ridgway (Newcastle, Staffs).

Remove the back cabinet internal screening lead and two screws holding cabinet chassis. The cabinet can now be removed. Do not forget the knobs. Detach EHT connector and base connector of tube with ion trap magnet if fitted. Release two clips securing strap round tube and, supporting tube with one hand on flare and other hand on coil assembly, draw tube slowly forward until clear. Do not tilt tube as the neck may break. To replace reverse the procedure.

McMICHAEL T.M.51

This set was out of use for a long time and on trying it, it operated normally for about 30 minutes and then the EHT failed. The EY51 was replaced without success and the line output valve was tested and found O.K. All H.T. voltages appear to be correct, D.C. resistances of line output transformer and associated components are correct. It was noticed that the line transformer was rather warm and insulation was melting. I removed EHT heater winding, which consisted of about 10 turns of varnished copper wire which appeared to be in order. I have rewound with polythene covered aerial wire and although there is a hefty spark at anode of EY51 there is still no life at heater end of this valve. Disconnected EHT smoothing condenser, removed tube anode clip but still no life. There appears to be a faint sound of oscillation which varies with line hold control. Width and line coils checked for continuity.—R. Davies (East Keswick, nr. Leeds).

Our only suggestion is that the line transformer is a fault and was from the start. The only cure is a replacement or a rewind. The one fitted by McMichael now is a modified and more efficient one.

BANNER BT117

Although there is a very good picture on both channels and the aerial is the same as when set was new five years ago, the scan lines appear to continually vibrate causing background flicker on the screen although picture is perfectly locked.—S. Edwards (Spool 5).

You should try the effect of adding to the existing H.T. smoothing. Try connecting a 200 μ F. 275V.W. capacitor across the H.T. line. The flicker may be caused by non-standard mains.

SPENCER WEST MODEL 174

The vision on both the BBC and I.T.A. is perfect, but the only sound is a tuneable hum. Is the fault in the turret tuner or in the other part of the set?—F. Mather (Leigh, Lancs).

The fact that a tuneable hum is received shows that the sound stages are in order and that the fault is in the turret. The PCF80 is likely to be at fault.

DECCA MODEL D17

What is the method of picture shift for the above model?—R. Angell (Codnor).

The picture shift controls on the Decca D17 provide a small amount of D.C. through the line or frame scanning coils. The effect of the current is to move the picture in accordance with the direction of the current flow. This is a development of the system used on the earlier Plessey Mk. 11 chassis (as in the Regentone Big 12, etc.).

INVICTA T112

My set is completely dead and I suspect short or open circuit in power transformer. I also find sparking in middle of central rectifier and I am wondering if this could indicate a further fault in the set. I should be obliged if you could tell me the type of transformer I require for a replacement.—R. Robertson (Falkirk, Stirlingshire).

There is no mains transformer in the T112. It is an A.C./D.C. receiver with series connected valves. If there is no sign of life at all, this is probably due to a flashover—the metal rectifier blowing the fuse(s). Check the fuse(s), see that the on/off switch is working and establish continuity of the mains dropper resistor, if the fuses are in order. Then check the heater chain (checking the valve heaters in turn).

COSSOR 944

The trouble is lack of brightness, very poor contrast, out of focus and distortion. When the room is in complete darkness and I turn the brightness very low there is nothing wrong with the picture quality at all. At all times the picture remains the same size.—H. Marks (Ponders End, Middx).

Your symptoms are those of a low emission on C.R. tube. Before discarding it, try readjusting the ion trap magnet, which may have slipped from the setting of maximum brightness.

QUERIES COUPON

This coupon is available until JANUARY 22nd, 1960, and must accompany all Queries sent in accord with the notice on page 211.

PRACTICAL TELEVISION, JANUARY, 1960.

SETS & COMPONENTS

H.M.V. 151N. English Electric 151n. Ultra. etc.. Televisions not working. originally £175 each. **£5/10/-**. TOMLINS, 127, Brockley Rise, Forest Hill S.E.23.

VALVES. new and used. from 1/6 each. All guaranteed. All types Radio. Television Components. Lists free. **HAMILTON RADIO.** 237, Sedlescombe Rd. N., Hastings.

FIX IT YOURSELF AERIALS! Pre-assembled ready for instant fitting. New season models. Loft 5EL. 30". Clip on 5EL. 30". 3EL. 42/6. Diapole + 5EL + Chimney Kit. 75/- **FRINGE AREA MODELS** for high gain. Band 1. 3EL array. 80". Band 3. Double 3 Array. 72/6. Double 8 Array. 100/- Fringe area super low loss Coaxial. 1/3 yd. Standard low loss. 71d. yd. T.V. Fault Finding Book. 5/8. All items carriage paid. C.W.O. S.A.E. for aerial list, etc.

HASE SUPPLIES, 34, PRINCE STREET BRISTOL (Dept. P.T.V.)

BARGAIN.—17in. Baird. **£14/10/-**; 2in Bush. **£9/10/-**; working order and both with I.T.A. **RADIO ELECTRIC.** 497, High Rd., Leytonstone. E.11. (Leytonstone 1546.)

REBUILT TV TUBES

FULLY GUARANTEED 12 MONTHS

ALL MAKES — 12" to 21"

BLANE & MARTIN ELECTRONICS
SANDOWN LANE
LIVERPOOL

Details on request. Tel. SEF. 3428

144 MIXED RESISTANCES, 10/-; 72 mixed Condensers. 5mmf.-0.1mf., silver mica, paper and mica. 18/-, all new, p. and p. **1/6 LEDSHAM TRADING CO.,** Ledsham, Cheshire.

T.V. TUBES. Genuine re-gunned tubes with 6 months' guarantee; 14in. rectangular and 17in., **£6** each, carriage extra. **T.V. ELECTRIC & CYCLE CO.,** 1 High St., Chalvey, Slough (Tel.: 21860).

T.V. TUBES, factory rebuilt (re-gunned). fully guaranteed. 14in. **£4**, 17in. **£5**, p. and p. **10/-**. 24. Bristol Rd., Brighton.

I.T.V. CONVERTERS. Stirlings. Pennine. Aerialite, etc.. 55/- each. Tubes. 12in. etc., from 40/- p.p. **O.D.B.,** 25, Ramshead Approach, Leeds. 14.

LONDON TELEVISION

OFFER THE FOLLOWING BARGAINS. RIGIDLY TESTED EQUIPMENT TELEVISION VALVES. Individually Boxed. 3/- to 7/6 each.

WIDE ANGLE SCANNING TELEVISION CHASSIS. Complete less valves. 30/- each. Most makes in stock.

TELEVISION COMPONENTS at Bargain prices. Please write for your individual requirements. Carriage extra.

The undermentioned Televisions for Personal Callers Only.

14in. TELEVISIONS. Working. **£40.00** to **£8.00**. **17in. TELEVISIONS.** **£9.00** to **£14.00**. Trade enquiries invited.

4, HENDERSON RD. EASTNEY, PORTSMOUTH.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

NEW TUBES

	2 Years' Guarantee	1 Year Guarantee
12 in. Type M.W.	£10.10.0	£7.10.0
14 in. Type M.W.	£10.10.0	£8. 0.0
17 in. Type M.W.	£12. 0.0	£9. 0.0
17 in. Type C.R.M.	£13.10.0	£10. 0.0

and Equivs. Carriage 5/-
10 in. Cossor, NEW—**£5.10.0**

LINE OUTPUT TRANSFORMERS

Direct Replacements for 500 sets. Compare these prices. (Add 2s. 6d. post):

Pye. LV30, 16T, CS17, etc.	50/-
1BT. V4, etc., LV21, Luxury 17, CW 17CS.	60/-
Cossor. 930, 931, 933, 934, etc.	60/-
Baird. T29, T163,	53/-
T164, T167, T172, 2014, 1712, etc., 1812, etc.	60/-

And Line Osc., Frame O/P and Osc., Scan Coils.

NEARLY ALL SETS COVERED.

State Make and Model. S.A.E. please.

OTHER BARGAINS—NEW!

4-speed AUTOCHANGER, BSR UA8, only **£6.15.0**.

VERDIK Quality-Ten Amplifier and Preamp., 10-watt Ultra linear. For the connoisseur. Listed 23 gns. Our Price **£14.19.6**.

Carriage, etc., on the above, 5/-.

Transistors. Equiv. Red Spot, TSI. Only 5/-.

WESTWAY RADIO

5, Westward Way, Harrow, Middlesex.

SAVE ON REPAIRS.—100,000 salvaged Radio and TV Spares. Valves. Tubes for practically any set made since 1936. Prices from: LOT. 17/6; POT. 7/6; osc. tr. 6/-; Sound. 2/6; Mains. 10/-; EHT Mains. 50/-; Def. Coils. 12/6; Speakers. 5/-. Tubes. Mullard. Mazda, etc.. 9-10in. 30/-; 12-14in. £2/19/6; 17in. £3/19/6. All picture tested, fitted free or sent subject to 14 days' money-back guarantee; Mullard 6 months' guarantee. Valves. 1,000 types from 1/6; EF91. EB91. 6J5. 2/6; EF80. UF42. 10F1. 6P1. 6SN7. 3/6. We can save you pounds! Send s.a.e. with enquiries or for complete list. "ST. JOHN'S RADIO." 156, St. John's Hill, S.W.11. (BAT 9838.)

CALLING 9in. Television owners. Brand new, factory fresh. 9in. Ferranti Tubes, originally **£14/10/-**, will replace Mazda, Brimar, G.E.C., etc. **£4/10/-** each, 6 months' guarantee. **TOMLINS,** 127, Brockley Rise, Forest Hill, S.E.23.

SALVAGED VALVES

All at 2/6 each

EF91	U31	10F1
DH77	VP4B	B36
Z77	ECC81	KT33C
EB91	6P13	EF50
	6P28	& Many Others

Minimum Order 8/- S.A.E. for List. All Valves Tested on Mullard High Speed Valve Tester. C.W.O. to—**ARION TELEVISION, 4 Maxted Rd., S.E.15**

TELEVISION TUBES

NEW TV TUBES. TWELVE Months' Guarantee

12" CRM 121	£ 8.10.0
12" MW 31-74	7. 0.0
14" MW 36-24	8. 0.0
14" AW 36-21	9. 0.0
14" MW 36-44	9. 0.0
17" MW 43-64	9. 0.0
17" MW 43-69	9. 0.0
17" AW 43-80	10. 0.0
21" MW 53-20	15. 0.0
21" MW 53-80	15. 0.0

FULLY Rebuilt TV Tubes TWELVE Months' Guarantee

MW and AW types fitted with NEW "guns" supplied by MULLARD, LTD.

12" MW 31-74 CRM 123	5. 0.0
14" MW 36-24 CRM 141	5.10.0
14" AW 36-21 CRM 142	5.15.0
17" MW 43-64 CRM 171	6.15.0
17" MW 43-69 CRM 172	6.15.0
17" MW 43-80 CRM 173	6.15.0
21" MW 53-20 CRM 211	8.15.0
21" MW 53-80 CRM 212	8.15.0
15" CRM 152 CRM 153	10.10.0

Carriage for each item 10/-

CATHODE RAY TUBE SERVICE

35, Broomwood Road, St. Paul's Cray
Orpington 21285
Battersea 6859

RECLAIMED VALVES, tested and perfect. Huge stocks. Any type, price 5/-, plus 6d. postage each; delivery by return. **LEWIS,** 57, Chalford Walk, Woodford Green, Essex.

AERIALS AT TRADE PRICES

For Example **DOUBLE FIVE ARRAY** COSTS ONLY **60/-**.

Band III Self-contained Pre-Amplifiers Only 60/- Band II Converters, 100/- Turret Tuners, 94/-. Complete Rebuilt T.V. Tubes from 45. Revacuumed ones, All Sizes. **£2.10.0**. All Tubes are Guaranteed. Super Low-loss Coaxial Cable, 1 1/2 yd. Standard, 6d. yd. Diplexers, 5/- each. S.A.E. FOR FULL LISTS.

G. A. STRANGE, Broadfield, North Wrexall, Nr. Chippenham, Wilts. Tel.: Marshfield 235.

INDICATORS, type 277, with lin. C.R.T. 4/VR91. 2/VR92. 37/6 (p.p. 3/6). Type 101, with VCR530 (6in. Blue. magnetic; octal base), and 2/EB91, 2/EF91. 2/R10, new cond., 30/- (post 3/6). Type 1, with VCRX263. 2/EF52. 5/6J6.1. 6V6. 1/EY51. 2/EB91. 3/EF91. R.F. EHT Generator and 28 kc/s. xtal. 45/- (rail 7/6). Type 97 with VCR517. 10 valves. 30/- (rail 7/6). List and enquiries, s.a.e. please. Terms, c.w.o. Postage extra. Immediate despatch. **W. A. BENSON,** 136, Rathbone Rd., Liverpool. 15.

T/V SPARES

LARGEST RANGE OF NEW AND USED SPARES

Line Outputs our Speciality. Used from 21. New from 45/-. Also breaking hundreds of T/Vs for Spares. All Coils. Transformers, Chassis, Valves, etc. No List. Send S.A.E. and State Requirements for Immediate Quote.

VALVE KITS. A complete Kit for YOUR set (one of each type) from 50/-. Quote Model Number for exact price.

TV BARGAINS. Reconditioned All-channel Models at New Low Prices. 14inch from 22 kns., 17inch from 29 kns. Fully guaranteed. Terms available.

T.C.S. LTD., 28, Brockley Cross, S.E.4. T1Deury6391.

FOR SALE

VALVES, Condensers, Record Changers and Players, Cabinets, Amplifiers, Speakers, etc., etc. Send for free list to: H. F. JAMES, 21, Claremont Rd., Twickenham, Middx.

100 BAYS of brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep, stove enamelled dark green; sent unassembled, 6-shelf bay, £3/15/-; sample delivered free; quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. (Tel: 69018.)

TELEVISIONS, 12in., 14in., 17in. and Projections. Require attention, from £3. In working order—12in. BBC from £7. 14in. BBC/TA with regunned CRT from £18. 17in. from £25.

Send for Lists. Carriage Paid.

CADMAN'S

Service Department, Bryan St., Hanley, Stoke-on-Trent.

VALVE CARTONS at kept prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a, Godwin St., Bradford, 1.

SERVICE SHEETS; also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20, Extension, Shepherds Bush Market, London, W.12 (Phone: SHE 3052.)

SATISFACTION ASSURED. — 12in. Televisions, £9/10/-; 14in., £16; 17in., £19/10/- Write for quotation, stating requirements. We guarantee satisfaction. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

NEW ELECTROLYTICS, 12 for 5/-; 50 Resistors, 5/-; 25 Condensers, 5/-; Meta Rectifiers, 250v. 60ma., 4/6; P.M. Loudspeakers (used), 7/6; Valves from 1/8; Complete Kits: Crystal Set 7/9, Pocket Transistor Radio 27/9, Valve Radio 36/-. All guaranteed; postage extra; lists free. HAMILTON RADIO (T), 237, Sedlescombe Rd. Nth., Hastings.

MAKING YOUR OWN TELESCOPES, Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc., then our booklets "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2, 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

C. EDWARDS

1070 HARROW ROAD, LONDON, N.W.10, LADBROKE I734

Offers
S/H T.V. in
First-class
Condition.
12in. £5. 0.0.
14in. £7.10.0.
17in. £15. 0.0.
(all 5 channel)
+ 15/- carriage.
Guaranteed
tubes, all sizes,
12" 30/-, 14" £3,
17" £4.



in stock: **PYE, FERGUSON, EKCO**
CASH ONLY. — 15/- Carriage.
Trade Enquiries Welcome.

1,000 TELEVISIONS, all makes, from £3 working, 10/- not. Callers only. 9 till 6, including Sats. 39, Whitehorse Lane, Stepney, London.

ASTOUNDING VALUE.—9in. Televisions, 45/-; 12in. Televisions, 70/-; 14in., £9/10/-; 15in., £5/10/-; 17in., £14. Complete but not guaranteed working; as received in part exchange. TOMLINS, 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available; carriage 7/6.

WANTED

ALL TYPES OF VALVES WANTED. PL81, ECL80, EY51, U25, PCF80, P230, U801, etc., etc. Best cash price by return. STAN WILLETT'S, 43, Spon Lane, West Bromwich, Staffs. (Tel.: WES 2392.)

NEW T.V. VALVES WANTED. Send valves, cash by return to: P. J. F. ANDREWS, 61-63, Rosemary Rd., London, S.E.15.

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S. 155, Swan Arcade, Bradford, 1.

SITUATIONS VACANT

TV TECHNICIAN—AUSTRALIA

Very progressive electrical store Gosford, near Sydney, N.S.W., requires experienced maintenance man, capable carrying out T.V. repair work and aerial installation. Must drive vehicle.

Good customer approach required. Family man is desirable.

Salary in region £A20 per week (£16 sterling), plus bonus scheme and overtime. Reply in writing (name and address in block letters) not later than January 5th, 1960, to W. D. Scott & Co. Ltd., 12, Thayer Street, London, W.1.

BRITISH RELAY WIRELESS LTD.

Due to rapid continuing expansion in the field of sound and television relay the services of competent ENGINEERS are required for varied and interesting work comprising:—

TEST, ALIGNMENT, CALIBRATION AND MAINTENANCE

of a wide range of equipment for

TELEVISION TRANSMISSION

and

DISTRIBUTION

Opportunities, are offered for employment on experimental work.

Applicants, who should be competent in the use of electronic measuring instruments, are invited to write, stating age, experience and qualifications, to:

B.R.W. LTD.

1-7, Croft St., Bermondsey, S.E.8.



A career on good pay in a skilled, expanding trade

RADAR OR WIRELESS MECHANIC

in the

Royal Air Force

Immediate vacancies; full training for suitable applicants in skilled radar and wireless maintenance, etc., full allowances and all found; month's leave a year; chance to travel, plus all the wider interests of Service life. Call or write for details to: Central Recruiting Office, (PTN 525a) Victory House, Kingsway, London, WC2

AERIALS

MAKE YOUR OWN AERIALS

SAVE £25+
TV aerial manufacturer offers "do-it-yourself" kits, 50 components include castings, pressings, mouldings, tubes, brackets, can be utilized to make 100 different models. TV, V.H.F., amateur. Brochure gives full illustrations, element dimensions and prices. Discounts for quantities.

THE RICHARD MAURICE EQUIPMENT CO.

Portsmouth Road, Cobham, Surrey. COBHAM 3239.

EDUCATIONAL

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation—I.C.S. Courses for the enthusiast and for those seeking examination qualification. Brit.I.R.E., City and Guilds, R.T.E.B., etc. Build your own equipment with Practical Radio Course. Write to-day for free book. INTERNATIONAL CORRESPONDENCE SCHOOLS. Intertext House, Parkgate Road (Dept. 516), London, S.W.11.

INCORPORATED Practical Radio Engineers home study courses of radio and T.V. engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text free. "The Practical Radio Engineer" journal, sample copy 2/-. 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet 1/-. all post free from the SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

(Continued overleaf)

EDUCATIONAL (continued)

★ LEARN ★

RADIO & T/V
SERVICING

for your OWN
BUSINESS/HOBBY

● by a new exciting no-maths system, using practical equipment, recently introduced to this country.

FREE Brochure from:—

RADIOSTRUCTOR

DEPT. G78, 46, MARKET PLACE,
READING, BERKS. 1/60

MISCELLANEOUS

LOUDSPEAKERS, Electric Clocks and Shavers repaired promptly. MODEL LOUDSPEAKER SERVICE, Supton on Cherwell, Oxford.

PHOTOELECTRIC PARKING LIGHT SWITCH will switch your lights on at dusk—off at dawn—automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Negligible consumption (.008amp.). Protect your car at night. Avoid accidents, fines. Save your battery. Kit of parts. 52/6; built and tested. 57/6; instructions only, 1/-. Pat. applied for. "ST. JOHN'S RADIO," 156, St. John's Hill, S.W.11. (BAT 9838.)

RADIO

AT LAST VHF-FM-AM for the family man. Astonishing De Luxe VHF FM Radio offer. Merging of world famous Co., enables us to offer £24 DE LUXE VHF-FM AM Radios for £15.10.0. Factory fresh. Maker's guarantee, extra thrilling quality. All features including Ferrite aerials. Our satisfaction guarantee or purchase price refunded. AC DC 200/250 v. Smaller radio with VHF FM AM. £13.10.0, originally £21. Carriage paid.

TOMLIN ELECTRICAL, 127, Brockley Rise, London, S.E.23.

SERVICE SHEETS

SERVICE SHEETS FOR SALE, all types, from 1/- each. Also Radio, Television Books. List free. 100 Television Service Sheets, covering 330 popular models, 18/6. HAMILTON RADIO, 237, Sedlescombe Rd., N. Hastings.

FAULTFINDER FILES (TV) showing common faults that each receiver is prone to and other useful servicing information. 2/- ea. List 9d. plus postage. S.P. DISTRIBUTORS, 11, Old Bond St., London, W.1.

SERVICE SHEETS. Radio, T.V., 5,000 models. Lists 1/-. S.A.E. enquiries. TELRAY, 11, Maudland Bk., Preston.

SERVICE SHEETS.—We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- ea. and for hire. Why tolerate delay in obtaining Service Sheets when we will despatch by return? List 1/-, s.a.e. with enquiries. S.P. DISTRIBUTORS, 11, Old Bond St., London, W.1.

SERVICE SHEETS for sale, T.V. 4/-; Radio, 3/-; also hire; immediate delivery: s.a.e. please. Callers welcomed. SULTAN RADIO, 6, Mt. Ephraim Rd., Tunbridge Wells, Kent. (Phone: 22710.)

SERVICE SHEETS, Radio and TV, 4/- ea.; also hire. List 1/-. GLOBE SUPPLIES, 33, Fairfield Close, Sidcup, Kent.

A SUPER SPECIAL T.V. TUBE OFFER

Why buy rebuilt or reconditioned tubes when we can supply you with a brand new 17" tube to replace the MW 43-64, 43-69, 171K, 172K, 17 ASP4, 17 AXP4, C17-1, C17-A, CR17-22, C17-FM, MW 43-80. Made by world-famous manufacturers complete with 12 months' maker's guarantee. Our Unbeatable Price £8.10.0. Also available brand new 14" to replace 36-24, 36-44, TR14-21, TR14-22, 14 KP4, 14-LP4, 14K, C36-24 or for AW 36-20, 36-21, 12" brand new 31 MW 31-74, all at £7 each. Also Cossor 65K 15" 4 volt filament equivalent to TA15 or 85K by fitting 6 volt filament transformer 10 gns. Cossor 108K 10" equivalent to EMI 315 £6.10.0. Ferranti 9" T9/5 4 volt filament 50/-. Post, packing & insurance 10/- extra.

NEW MAX ELECTRONICS

for London's Finest Bargains in electronic and radio equipment. Also Largest Selection of Tape Recorders in the U.K. Also in stock 500 shop soiled and L.P. reprocessed TV sets in all sizes. All Guaranteed.

220, Edgware Road, London, W.2.

TEL. PAD 5807.

FIRST-CLASS TELEVISION and RADIO COURSES . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.J.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE


Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING (Dept. 462), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg. Australia: P.O. Box 4570, Melbourne.

54 Gns.—'17'

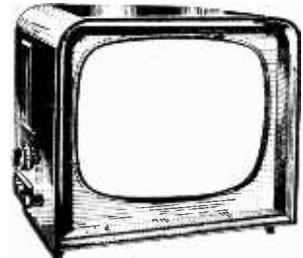

A full specification 17in. Television Receiver to Spencer-West standards now available at your Dealers. Remarkable performance and priced at 54 Gns. only, complete.

For Leaflet apply to:—

SPENCER-WEST LTD.
Quay Works, Great Yarmouth
Norfolk

Phone: Sales 4908/9

Grams: Spencer-West, Great Yarmouth

BRAND NEW GUARANTEED VALVES

CHECK THESE PRICES AND SEE HOW WE CATER FOR THE CITIZEN'S POCKET

DAF96	8/-	EF86	11/-	PY82	7/6
DF96	8/-	EL41	9/-	PY83	8/6
DK92	8/6	EL84	8/-	UAF42	9/-
DK96	8/6	EY51	10/-	UBF89	9/-
DL94	8/-	EY86	10/-	UCC85	8/6
DL96	8/-	PCC84	8/6	UCH42	9/-
EBC41	9/-	PCC85	11/-	UCH81	9/2
ECC81	5/9	PCF80	9/-	UF41	8/6
ECC82	8/9	PCF82	10/6	UF89	8/2
ECC83	6/-	PCL82	10/6	UL41	8/6
ECC84	8/11	PL36	13/10	U25	12/6
ECC85	8/11	PL81	11/10	1RS	6/9
ECF80	10/10	PL82	8/-	1S5	6/6
ECL80	9/6	PL83	8/11	1T4	5/-
EF80	6/6	PY81	7/6	3S4	7/6

Postage 6d. valve extra.

May we quote for obsolete and transmitting types. (S.A.E. please.)

CITIZEN'S VALVE SERVICE (REGD.)

Office Address—No Callers:

103, GANTSHILL CRESCENT,
ILFORD, ESSEX.

LINE OUTPUT TRANSFORMERS

Most types available. State Make and Model Number of Receiver when ordering.

S.A.E. please with all enquiries.

HOWORTH

5 POLLARD LANE, BRADFORD, 2, YORKS
Tel. 37030

A 3d. stamp will bring you a copy of our latest

RADIO & TELEVISION COMPONENT Catalogue

JAMES H. MARTIN & CO.
FINSHURWHITE, NEWBY BRIDGE, ULVERSTON, LANCs.

IS YOUR T.V. TUBE DIMMING? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE



PRICE **27/6**

Post, packing, & ins. 2/6.
C.W.O. C.O.D.

● NO SOLDERING ● NO WIRING ● JUST PLUG IN ● IT'S AUTOMATIC ● IT'S GUARANTEED!
We can offer these units for any make of set. IMPORTANT. State name, address, & make and model no. of set, & tube in block caps.

SINCLAIR ELECTRONICS,
Dept. P.T., 33, BERWICK ST., W.I. Callers Welcome—Trade Enquiries Invited.

RES. CAP. BRIDGE 37/-

p. & p. 2—
Check all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading

READY CALIBRATED
Stamp for details of this and other kits.

RADIO MAIL (Dept. VU)
Raleigh Mews, Raleigh Street, Nottingham

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

Rewinds to all makes.

H.W. FORREST (Transformers) Ltd.
Shirley, Solihull, Warwickshire
Tel.: Shirley 2483

NYLON · P.T.F.E

ROD, BAR, SHEET, TUBE, STRIP, WIRE

No Quantity too small
List on application

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1
SLOane 3463

Works:
36, ROSEBERY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester, Birmingham, Leeds.

B.B.C. - I.T.V. - F.M. AERIALS



B.B.C. (BAND 1). Telescopic loft, 18/6. External, S/D. 26/3.

I.T.V. (BAND 3). 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element 63/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H", 28/-. 3 Element loft, 52/6. S/D loft, 12/6. External S/D, 28/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 6d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. T.P.)
3B, Godstone Road, Kenley, Surrey

Television Tubes

TO BE SURE OF REAL SATISFACTION

FIT A TUBE WITH ALL THE LATEST DEVELOPMENTS

AS ADVERTISED ON TELEVISION

Specification:

- Correct Plug-in Replacements.
- Very Latest Small Particle Silver Activated Phosphor Screens, giving High Brilliance, Fine Definition and Maximum Contrast.
- Special Design of Electron Guns with Smaller Anode Apertures giving Finer Focus.
- Correct percentage Blue Phosphor giving Whiter High Lights.
- Improved Emissive Substance for Cathode Coating gives Better Emission and Longer Life.
- 12 Months Guarantee with Further 12 Months on Guarantee Replacements.

Correct Replacements available for Mullard (A.V. and M.W.), Mazda Cathodeon, Emitron, Cossor, G.E.C., English Electric types, Emiscope and Brimar Pyrex types, 10/- extra.

12in., 14in. sizes. £6.10.0.
15in., 16in., 17in. sizes. £6.19.6.
Post and Packing 10/6. Terms C.O.D. or C.W.O.

HAVE THE VERY BEST.

LAWSON TUBES

156, Pickersleigh Rd., Malvern, Worcestershire.

EDDY'S (Nottm.) LTD.

172 ALFRETON ROAD, NOTTINGHAM

Surplus New and Guaranteed Valves

1D5	9/6	6V6G	5/9	ECC84	9/-
1L4	3/9	6V6GT	6/6	ECC85	8/6
1S5	6/6	6X4	6/-	ECF80	10/6
1T4	4/9	6X5GT	6/6	ECL82	11/-
3S4	7/-	7C6	7/6	EF36	2/6
3V4	7/9	7H7	7/6	EF37	4/-
5U4G	5/9	7H7	7/6	EF42	8/6
5Z4G	9/-	7S7	9/6	EF50	9/9
6B8G	2/11	7Y4	7/6	EF80	6/6
6BA6	6/6	10F1	10/-	EF86	11/-
6B16	6/6	12A6	6/6	EF91	4/-
6C4	3/6	25A6G	8/-	EL84	8/3
6J6G	2/6	25Z4G	7/9	EY51	9/6
6J5GT	3/6	35W4	6/9	EY86	9/6
6J5M	4/3	807(B)	3/9	EZ80	6/9
6K7G	2/6	AZ1	12/6	PEN36C	6/6
6K8G	6/6	DAF96	8/3	PL33	9/-
6P28	9/6	DF96	8/3	PL83	8/9
6Q7G	7/6	DK96	8/6	PY31	8/6
6SA7M	6/-	DL96	8/3	PY80	7/-
6SG7M	5/-	EB41	7/-	PY82	7/6
6SK7GT	5/-	EB91	4/-	U31	7/9
6SN7GT	4/9	ECC81	6/-	U35	8/6

NIFE ACCUMULATORS.

Single Unit Size 3 x 2 1/2 x 3/4 amp. hrs., 1/11. P. 1/6.

ACOS CRYSTAL PICK-UPS.

Turnover head (2 sapphire styli), 29/11. Post 2/6.

HEADPHONE CORDS.

High Quality, 6ft. length, 1/11 Pair. Post 6d.

SPEAKER GOLD GRILL.

6in. x 4in., 1/- each. Post 6d.

VIBRATORS.

12 v. 4 pin., 4/11. Post 1/-.

DIMMER SWITCHES.

Ideal for train speed regulators, 1/11. Post 9d.

NEON MAINSTESTER/SCREW-DRIVERS,

3/11. Post 3d.

GERMANIUM DIODES,

1/- each, 9/6 Dozen. Post 5d.

RECTIFIERS.

RM1, 4/9. RM2, 6/6. RM3, 7/6. RM4, 4/9. RM5, 19/6. Contact cooled 200-60 mA., 7/6. Post 1/-.

INSULATION TAPE.

10 yds. 3/4 in. width, 9d. Post 4d.

JACK PLUGS.

Standard Type, 1/11. Post 6d.

CO-AXIAL CABLE.

Air spaced. Suitable for T.V. Fringe area V.H.F., etc. 71d. yard. Cut to any length.

CAR RADIO KITS.

7 transistors Long and Medium, 2 watts output. R.F. stage and automatic gain control. 6 or 12 volts. Complete kit with cabinet. 10 gns. Post 5/-.

LUXEMBOURG EXPANDING AERIALS.

Compact and easy to fit. No Technical Knowledge required. Greatly improves reception, 3/11. Post 6d.

CONDENSERS.

Tubular wire end (not ex-Govt.). 8 mfd., 450 v., 1/9; 8-8, 450 v., 2/6; 16 mfd., 450 v., 2/9; 16-16, 450 v., 3/9; 16-8 450 v., 4/-; 32 mfd., 450 v., 3/9; 32-32, 350 v., 4/-; P. 1/-.

MORSE TAPPERS.

Plated contacts adjustable gaps. Heavy Duty, 3/6. Post 9d.

MINIMOTORS.

For model makers. High Speed. 1 1/2 v. to 6 v., 8/6. Post 1/-.

THROAT MIKES,

1/-, Post 6d. Could be used for electrifying musical instruments.

DYNAMOTORS,

200 v. D.C. to 12 v. D.C. Ideal for train sets, etc., 19/11. Post 2/6.

TRANSISTORS SUB-MINIATURE CONDENSERS,

1.6 mfd., .5 mfd., 8 mfd., 10 mfd., 16 mfd., 25 mfd., 32 mfd., 2/3 each. Post 6d.

GRAM AMPLIFIERS.

High Sensitivity 3 watts output. Separate volume and tone controls. Printed circuit, 59/11. Post 4/-. Fully Guaranteed. Size 8 x 2 1/2. Max. height, 5in.

Any parcel insured against damage in transistor for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and Packing 6d. per valve extra. Over £3 free. C.O.D. or C.W.O. only. C.O.D. charge 3/- extra. S.A.E. with enquiries.

"PERTH" 1960 SHOW MODEL RECORD PLAYER CABINET

EXCEPTIONAL NEW YEAR OFFER Stereo Cabinet with Extension



99/6

Portable 1960 "Perth" show model. In two tone colours. Extension speaker cabinet secured in lid. (Arrow indicates position when fixed.) Size 18 x 11 x 18 1/2 in. high. This stereophonic player complete retails at 95 Gns. ; in the shops today. Carr. & Ins. 5/6, with order. Or 6/1 initial payment & balance of 4/11 for 19 weeks.

EXTENSION SPEAKER 19/6.

In oak cabinet, fitted with 8in. P.M. Speaker. Std. matching to any receiver 2-5 ohms. Switch and flex incl. P. & P. 3/6.



8in. P.M. SPEAKER 5/9.

Had a slight cone repair not affecting the quality. Tested and guaranteed. P. & P. 2/9.

PLESSEY T.V. CHASSIS 9/6.

A host of valuable spares for the T.V. Amateur incl. : Valve holders, I.F. Transformers, Frame O.P. Transformers, Line transformer, O.P. Transformer controls, condensers, Less valves. A good buy to occupy those long Winter evenings. Ins. Carr., 10/6. DRAWINGS FREE with order.


FOCUS MAGNETS. 9/9. Brand new 38 mm. Incorporating picture shift control. Post 1/3.

ELAC FOCUS MAGNET. 12/6. Brand new 35 3/8 mm. P. & P. 1/3.

Stamp for FREE Catalogue Dept. Tl.

PP COMPONENTS LTD.
219, ILFORD LANE, ILFORD, ESSEX ILF 0295

RECORD OR TAPE CARRYING CASE

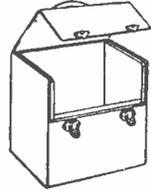

Beautifully covered in washable leatherette. Strong modern case and carry handle. Hinged lid. 2 1/2 x 2 1/2 in. plated clip fasteners. P. & P. 2/6. To hold 30 E.P. 7in. records. 21/9. To hold 40 E.P. 7in. records. 23/9. To hold 20-10in. or 12in. records. 22/6. To hold 50 10in. records. 24/6. These also hold 10 large tapes.

★ TRANSFORMERS ★ REVISED LIST

MAINS AUTO. 8/9. 0-205-225-245 v. at 300 mA. Isolated windings. 6.4 v., 6.3 v. and 2 v. P. & P. 3/9.
MAINS TRANS. 5/9. 200-250 v. at 150 mA. Sec. 0-200-250 v. Suitable small amplifiers. 2 1/2 x 1 1/2 in. P. & P. 1/9.
MAINS TRANS. 7/9. 300-0-300 v. Prim. 200 250 v. 6.3 v. at 3 amp. P. & P. 2/9.
MAINS TRANS. 6/9. 300-0-300 v. at 80 mA. Prim. 200-250 v. 6.3 v. at 3 a. 5 v. at 3 a. P. & P. 2/9.
O.P. TRANS. AND SMOOTHING CHOKES. 4/9. Suitable for EL84. Single or Push-Pull Output. P. & P. 1/9.
O.P. TRANS. 1/3. Std. size 2-6 ohms. P. & P. 1-2/6 for 21. Carr. 5/6.
FRAME O.P. TRANS. 1/9. 500 ohms prim. Sec. 18 ohms. P. & P. 1/6.
HEATER TRANS. 3/9. 2-1 ratio. Auto trans. 2-1 v. 3 watts. P. & P. 1/9.
HEATER TRANS. 12/9. 12 v. at 1 A. Prim. 0-200-250 v. P. & P. 1/9.
EY51 ISOLATION TRANS. 5/9. 7 Kv. 1-1 Ratio P. & P. 1/9.

Stamp for FREE Catalogue Dept. Tl.

BAKELITE CABINET
5/9 Brand new. Attractive design. Size 12in. x 7in. x 5 1/2 in. Colour brown. Ideal small receivers, etc. P. & P. 3/3.

TELEVISION SERVICING HANDBOOK

A practical guide to television receiver fault-tracing, alignment, adjustment and repair, for the service engineer, amateur and student, with chapters on aerials and Band III conversion.

By Gordon J. King.
30/- Postage 1/3.

TV FAULT FINDING, a Data Pub.
5/- Postage 6d.

AN INTRODUCTION TO THE CATHODE RAY OSCILLOSCOPE, by H. Carter, 12/6. Postage 8d.

TELEVISION EXPLAINED, by W. E. Miller, Revised by E. A. W. Spreadbury, 12/6. Postage 1/-.

RAPID RADIO REPAIR, by G. W. Turner, 23/- Postage 1/-.

MODEL RADIO-CONTROL, by E. L. Safford, 21/- Postage 1/-.

RADIO VALVE DATA, 6th Ed. Compiled by "W.W." 5/- Postage 9d.

NEW 1960 CATALOGUE, 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAD STREET, LONDON, W.2.

Phone : PADdington 4185.
Open 6 days 9-6 p.m

VALVES

SAME DAY SERVICE

NEW ! TESTED ! GUARANTEED !


SETS	IR5.	IS5.	IT1.	3S4.	3V4.	DAF91.	DF91.	DK91.	DK92.	DL92.	DL94.	any	4 for 25/-	5 for 27/-
1A7GT	12-	6L18	12 3	30C1	7 6	EBL21	20 6	EZ80	6 3	T1141	16 6			
LD5	9 6	6P25	9 -	30L1	7 9	EC92	11 -	EZ81	7 -	U25	11 6			
1H5GT	10 -	8Q7C	7 6	35L8GT	10 -	ECC81	7 6	FW 500	9 6	U26	12 6			
1N5GT	10 -	6Q7GT	9 6	35Z4GT	6 -	EC92	6 6	GZ32	9 -	U32	7 6			
1R5	6 9	6SL7GT	7 -	35Z5GT	8 6	EC93	7 -	KY32	7 -	U32	5 3			
1S4	9 -	6SN7GT	5 6	43	12 6	ECC84	8 9	KT41	14 6	U76	6 9			
1R5	6 3	6U4GT	11 -	50CD6C	26 9	ECC85	9 6	KT61	10 -	U78	6 9			
1T4	5 3	6V6GT	4 -	50L6GT	9 9	ECF80	11 6	KT63	6 6	UABC80	8 6			
1U5	6 6	6V6GT	7 6	AZ31	9 8	ECF82	10 -	KT71	12 6	UAF42	9 6			
3A5	10 6	6X4	6 9	E36	9 8	ECH21	20 6	MH1	6 -	UBC41	7 9			
3Q4	8 6	6X5GT	6 -	CL33	11 -	ECH35	6 9	MU11	7 9	UBF80	9 6			
3S4	6 9	7B7	8 -	DAC32	10 -	ECH42	9 6	MX40	12 6	UBF80	8 6			
3V4	7 6	7C5	8 -	DAF91	6 3	ECH81	8 6	N18	8 6	UBI21	20 6			
5U4G	5 3	7C6	8 -	DAF96	8 6	ECL80	8 6	PCC81	7 9	UCB84	12 9			
6V4G	10 3	7HT	8 -	DC990	10 6	ECL82	10 -	PCC89	14 -	UCB85	8 -			
5Y3GT	7 6	7S7	9 9	DF93	10 -	EP38	5 8	PCF80	7 6	UCF80	14 -			
5Z4G	9 6	7X4	8 -	DF91	5 3	EP41	9 8	PCF82	9 3	UCH21	20 6			
6AL5	3 9	10C1	14 6	DF96	8 6	EP42	11 6	PC182	9 3	UCH42	9 6			
6AM5	5 -	10C2	17 6	DH76	6 6	EPF80	6 6	PC183	11 -	UCH81	8 6			
6AM6	3 9	10F1	15 6	DH77	7 3	EPF85	6 9	PC184	7 9	UCI32	11 6			
6AQ5	7 -	10F4	10 6	DK32	12 -	EP86	11 -	PC1A4	11 -	UCI33	14 6			
6AT6	7 3	12AH8	10 6	DK40	14 -	EP89	8 -	PCN36C	9 6	UCF41	13 6			
6BA6	6 -	12AT7	7 6	DK91	6 9	EP91	3 9	PCN45	3 -	UF42	8 6			
6BE6	6 -	12AU7	6 6	DK92	8 6	EPF92	4 6	PCN46	5 6	UF89	7 6			
6BH6	6 9	12AX7	7 -	DK96	8 6	EL33	10 -	PL36	13 -	UL41	8 -			
6BJ6	6 -	12BA6	6 9	EA42	9 6	EL35	21 6	PL38	14 6	UL44	21 6			
6BR7	10 6	12K7GT	5 8	DL33	12 3	EL41	9 -	PL81	10 -	UL84	8 -			
6BW7	6 6	12K8GT	11 6	DL82	6 9	EL42	10 6	PL82	7 6	URIC	8 -			
6CD6G	26 9	12Q7GT	5 6	DL94	7 6	EL84	8 -	PL83	8 6	UYIN	12 6			
6F1	14 8	12Z3	7 6	DL96	8 6	EM34	8 6	PV32	11 -	UY21	14 -			
6F4G	6 6	14S7	16 9	EABC90	9 6	EM80	9 -	PY80	7 6	UY41	6 6			
6F13	12 6	19AQ5	7 6	EA42	9 6	EM81	9 -	PY81	6 9	UY65	6 9			
6F14	17 6	20F2	17 6	EB91	3 9	EM84	10 -	PY82	7 -	VP4B	9 6			
6K7G	3 9	20L1	17 6	EBC33	7 -	EY51	9 6	PY83	8 -	VP41	6 -			
8K7GT	6 -	25A6G	11 -	EBC41	8 6	EY86	8 3	PZ30	17 -	W76	6 6			
6K9C	6 9	25Z4C	9 -	EBF80	8 -	EBF80	6 9	SP61	3 6	W77	4 6			
6L1	16 9	25Z6GT	9 6	EBF89	8 9	EZ41	7 6	T41	15 6	Z77	3 9			

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

Post 6d. per valve extra.
Any Parcel Insured Against Damage in Transit 6d. extra.
Any C.O.D. Parcel 2/6 extra.

Build your own Aerials...

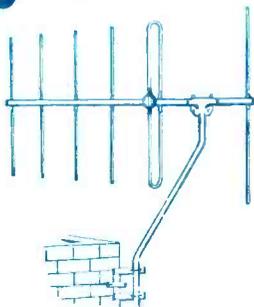

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.
 Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above to:—

Fringelevision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

AS ADVERTISED ON TELEVISION

Save £££

12 Months' Guarantee

FACTORY REBUILT ... TELEVISION TUBES

Immediate delivery

ALL TYPES FITTED WITH NEW GUN

TYPES

MW31-74	- 12 in.	£5 . 12 . 6	MW36-24/44	14 in.	£5 . 17 . 6
MW43-64/69	17 in.	£7 . 0 . 0	MW53-20/80	21 in.	£9 . 10 . 0
CRM141	- - 14 in.	£5 . 17 . 6	CRM171	- - 17 in.	£7 . 0 . 0

TERMS TO THE TRADE

Plus 10/- carriage and insurance.
Cash with order or C.O.D.

RE-VIEW (LONDON) LTD.

10 High Street

Colliers Wood, S.W.19

Telephone: Liberty 3272

