
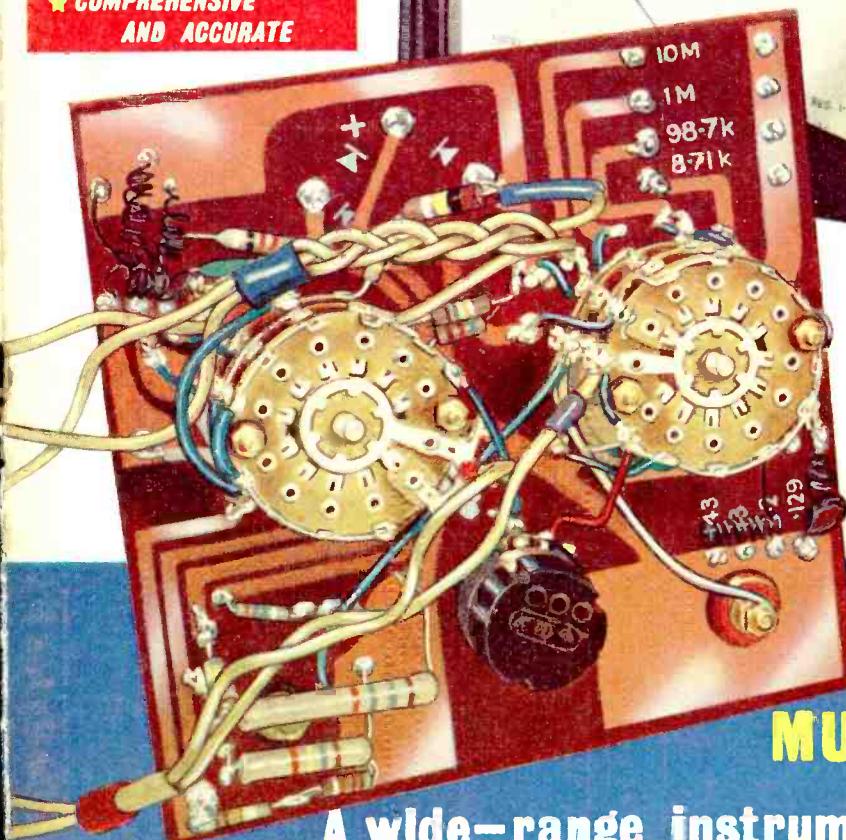


Practical

OCTOBER
1961

1'6


TELEVISION

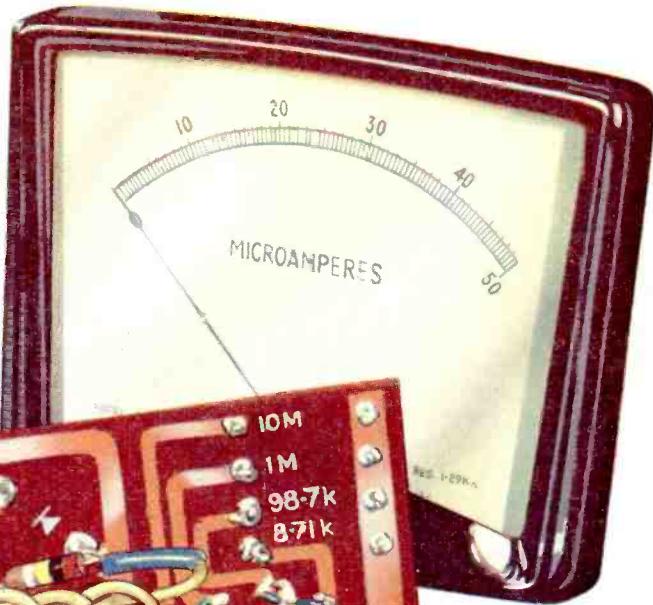

THE P.T.
MULTIMETER

A wide-range instrument
measuring Volts, Amps and Ohms

Build your own Aerials...

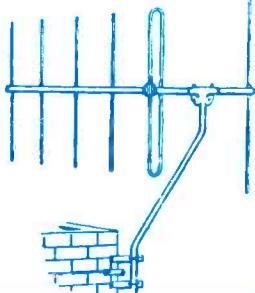

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.
Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:-

Fringevision Ltd.

MARLBOROUGH, WILTS. Phone: 657/8

SPECIAL FOR THE "HAMS" RADIO STATION

Illustrated

½ inch detachable bit
soldering instrument
List No. 70


Combined Protective Unit
with Wiper/Abrasion Pad
and Solder Reel
List No. 700

Apply SALES & SERVICE

ADCOLA
MAKERS OF

(Regd. Trade Mark)
GAUDEN ROAD
CLAPHAM HIGH ST.
LONDON, S.W.4

Telephones:
MACaulay 4272-3101

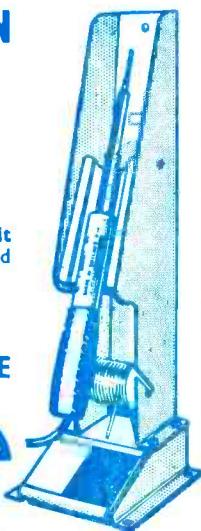

British & Foreign
Patents, Registered
Designs, etc.

Telegrams:
"SOLJOINT, LONDON"

THOUSANDS

OF SATISFIED PEOPLE

VIEW ON **E.M.S.**

REBUILT TELEVISION TUBES

- ★ A NEW GUN IN EVERY TUBE
- ★ BUY DIRECT FROM THE FACTORY
- ★ 18 MONTHS' GUARANTEE

12 inch £5.0.0 14 inch £5.10.0

17 inch £6.10.0

Immediate dispatch on receipt of Remittance
Carriage and insurance 12/6 extra
£1 Refunded on receipt of your
old Tube

For the benefit of South Coast customers we have an
agent in BRIGHTON. See our classified
advertisement for further details.

SPECIAL TERMS TO THE TRADE

MARSHALL'S for TELEVISION LTD.

131 St. Ann's Road, Tottenham, London, N.15
STAMFORD HILL 3267 & 5555


HARVERSON SURPLUS CO. LTD.

83 HIGH STREET, MERTON, LONDON, S.W.19

CHErrywood
3985/6

2 BAND SUPERHET CHASSIS with Speaker

ONLY £5.17.6
Plus 6/6 Post & Packing

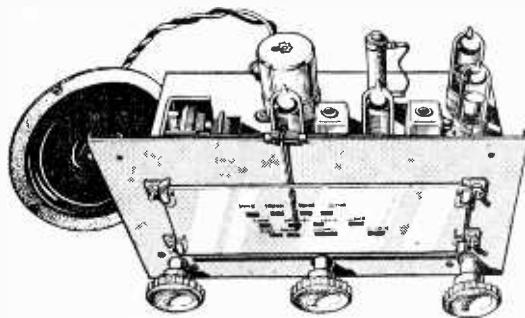

A quality 4 valve AC/DC superhet chassis made by a world famous manufacturer. Long and Medium wave coverage. Fitted with a cord and drum reduction tuning drive and attractive illuminated glass dial (size $6\frac{1}{2} \times 2\frac{1}{2}$ in.). Controls: Volume on/off, tuning and wave change. The receiver is self-powered, employing a mains dropper and a valve rectifier. Chassis dimensions $6\frac{1}{2} \times 9 \times 5\frac{1}{2}$ in. high. Supplied complete with a good quality 5-inch loudspeaker, valves (UCH42, UAF42, UL41, UY41), AC/DC mains input lead, ivory knobs, etc.

DON'T HESITATE, ORDER NOW! This unbeatable bargain is bound to sell out quickly at only £5.17.6, plus 6/6 post and packing.

THE HARVERSON 6 TRANSISTOR PLUS DIODE SUPERHET KIT

A first class 2 wave band transistor superhet in kit form. ★ Printed circuit panel (size $8\frac{1}{2} \times 2\frac{1}{2}$ ins.) ★ 3 Pre-aligned IF Transformers. ★ Output Transformer. ★ 5 inch 5Ω Speaker. ★ High gain Ferrite rod aerial. ★ First grade G.E.C. transistors. ★ Push/Pull output. All parts down to the minutes; item with simple instructions.

ONLY £6.19.6, plus 2/6 P. & P.

Cabinet to suit (if available) 15/- extra.

TRANSISTOR AMPLIFIER KIT

A complete kit of parts to build a compact 4-transistor amplifier, with volume control and printed cct. board. Two GT3 driver transistors, transformer coupled. 1 watt output from matched pair GT15. Supplied with output transformer and 2½in. 3 ohm speaker. Ideal for record player, etc. 59/6, plus 4/6 P. & P.

CONDENSER/RESISTOR PARCEL

50 mixed P.F. Condensers and 50 mixed Resistors. An assortment of useful values. All popular sizes—all new—a must for the serviceman and constructor. ONLY 10/-, P. & P. 1/-.

THE HARVERSON COMPLETE FM/VHF RECEIVER KIT

A complete VHF/FM Receiver in Kit Form.


Superb specifications. Everything supplied for Only £6.19.6, plus 4/6 P. & P. (See Practical Wireless October 1961 issue page 464 for full details).

20,000 VALVES IN STOCK. Lowest prices ever. See our list in October Practical Wireless, or send for your requirements.

4 STATION PRESET CHASSIS with Speaker

ONLY £4.17.6

Plus 6/6 P. & P.

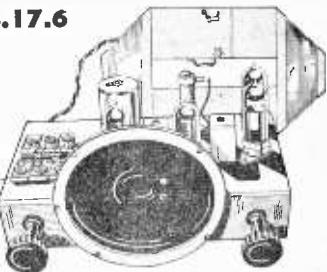


A compact, 4 station preset mains transportable receiver for operation from AC/DC mains. Two simple controls, volume on/off and 4 position station selector. The latter is set to Light Programme (Long Wave). Third Programme, Home Service and Light Programme (Medium Wave), but may of course be adjusted to alternative selections if required.

A frame aerial with throw-out extension is supplied, making this receiver ideal as a general purpose transportable set for the home. A fully smoothed power supply is provided from AC/DC mains input by a mains dropper and a valve rectifier. The good tonal qualities are assisted by the provision of a quality 5in. speaker, which is ready-mounted on the chassis (this is easily detachable if alternative positioning is required). Valve line up, UCH, UAF42, UL41, UV41. This chassis (size $9 \times 6\frac{1}{2} \times 5\frac{1}{2}$ in. high) is supplied complete with valves, knobs, mains lead, aerial, etc. It is beautifully made by a famous maker, and is first-class buy at the rock bottom price of only £4.17.6, plus 6/6 post and packing.

HARVERSON'S F.M. TUNER KIT

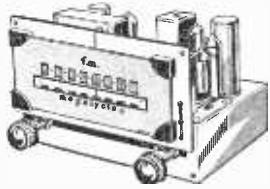At last a quality F.M. Tuner Kit at a price you can afford. Just look at these fine features, which are usually associated with equipment at twice the price.



★ F.M. Tuning Head by famous maker. ★ Guaranteed Non-drift. ★ Permeability Tuning. ★ Frequency coverage 88-100 Mc/s. ★ OA81 Balanced Diode Output. ★ Two I.F. Stages and Discriminator. ★ Attractive maroon and gold dial (7 x 3in. glass). ★ Self powered, using a good quality mains transformer and valve rectifier. ★ Valves used ECC85, two EF80's, and EZ80 (rectifier). ★ Fully drilled chassis. ★ Everything supplied down to the last nut and bolt. ★ Size of completed tuner $8 \times 6 \times 5\frac{1}{2}$ in. ★ All parts sold separately. £4.19.6, plus 8/6 P. & P. & Ins. Circuit diagram and illustrations, 1/6, post free.

OUTPUT STAGE AND SPEAKER FOR F.M. TUNER

All parts, including speaker, ECL82 valve, and simple instructions to make two-stage output unit for converting F.M. tuner into F.M. receiver. ONLY 59/6, plus 4/6 P. & P.

TELEVISION TUBE BARGAINS

COSSOR 108K 10-in. New & boxed, 15/-, plus 6/- P. & P.
75K 10-in. New & boxed, 15/-, plus 6/- P. & P.

Ion trap magnets to suit the above, 2/9, 3d. P. & P.
REBUILT TUBES. We can supply all types and sizes of good quality rebuilds at competitive prices.

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.I.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE. ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND
TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.

OA2	17/6	6F6G	7/-	12AC6	15/8	77	8/-	DL66	17/6	EF50(A)	7/-	HVR2	20/-	PX4	10/6	UBF80	9/-	Z66	17/6
OB2	17/6	6F12	4/6	12AD6	17/8	78	6/6	DL68	15/-	EF50(E)	5/-	HVR2A	6/-	PY31	17/-	UBF89	9/-	Z77	4/6
OZ4	5/-	6F13	11/6	12AE6	14/3	80	9/-	DL72	15/-	EF54	5/-	KF35	8/6	PY32	12/6	UBL21	23/10	Transistors	
IA5	6/-	6F23	10/6	12AH7	8/-	83	15/-	DL92	7/-	EF73	10/6	KL35	8/6	PY80	7/6	UCC84	14/11	and diodes	
IA7GT	12/-	6F24	12/6	12AH8	12/6	85A2	16/-	DL94	7/6	EF80	6/-	KL32	30/7	PY81	8/6	UCC85	9/-	CG1C	3/-
IC5	12/6	6F32	10/6	12AT6	7/6	90AG	67/6	DL96	8/6	EF85	6/-	KT2	5/-	PY82	7/-	UCF80	17/-	CG4E	3/-
ID6	10/6	6F33	7/6	12AT7	6/-	90AV	67/6	DM70	7/6	EF86	10/6	KT33C	10/7	PY83	8/6	UCH21	23/10	CG6E	3/-
IG6	17/6	6H6	3/-	12AU7	6/6	90CI	16/-	EF80F	30/-	EF89	9/-	KT36	30/7	PY88	13/7	UCH42	9/6	CG7E	7/6
IHS5T	10/6	6J5	5/-	12AX7	7/6	90CG	37/6	EF86	30/-	EF91	4/6	KT41	21/0	PZ30	20/5	UCH81	9/6	CG10E	3/-
IL4	3/6	6J6	5/6	12BA6	8/-	101	13/6	EA50	2/-	EF92	4/6	KT44	12/6	QP21	7/-	UCL82	11/6	CG12E	3/-
ILD5	5/-	6J7G	6/-	12BE6	9/-	150B2	18/6	EF76	9/6	EF97	13/7	KT61	12/6	OP25	14/6	UCL83	19/9	GD3, 4, 5,	
ILN5	5/-	6J7GT	10/6	12BH7	21/9	185BT	34/-	EABC80	9/-	EF98	13/7	KT63	7/-	Q5150/15	UF41	6, 8, 4/-			
INSGT	10/6	6K7G	5/-	12J5G7	4/6	304	10/6	EAC91	4/6	EF183	19/1	KT66	15/-		10/6	UF42	12/6	OA70	3/-
IR5	6/6	6K7GT	6/-	12J7GT	9/6	305	10/6	EAF42	9/-	EF184	12/6	KT88	24/-	R12	9/-	UF80	10/6	OA73	3/-
IS4	9/-	6K8GT	10/6	12KS5	18/4	807	7/6	EB34	2/6	EK32	8/6	KTW61	6/6	R18	14/-	UF85	9/-	OA79	3/-
IS5	6/-	6K8G	6/6	12K7GT	5/6	956	3/-	EB41	8/6	EL32	5/-	KTW62	7/6	R19	20/5	UF86	18/4	OA81	3/-
IT4	3/6	6K25	20/5	12K8GT	14/-	1821	17/-	EB91	4/-	EL33	12/6	KTW63	6/6	RGI/240A	UF89	9/-		OA86	4/-
IU5	6/-	6L1	23/10	12Q7GT	5/-	4033L	12/6	EBC3	23/10	EL34	5/-	KTZ41	8/-		54/-	UL41	9/-	OA91	3/6
2P	27/2	6L6G	8/-	12SA7	8/6	5763	12/6	EBC33	5/-	EL38	27/2	KTZ63	7/6	RK34	7/6	UL44	27/2	OA95	2/6
3AA	6/-	6L6M	9/6	12SC7	8/6	7193	5/-	EBC41	8/6	EL41	9/-	L63	6/-	SP4(7)	14/6	UL46	14/6	OA210	11/-
3AS	10/6	6L7GT	7/6	12SG7	7/-	7475	7/6	EBC81	8/-	EL42	10/6	MHL4	7/6	SP41	3/6	UL84	8/6	OA211	20/-
3B7	12/6	6L18	13/-	12SH7	8/6	9002	5/6	EBC80	9/-	EL81	17/-	MHL6D	12/6	SP42	12/6	UM4	17/8	OC16	48/-
3D6	5/-	6LD20	16/4	12S7I	8/6	AC/PEN	EF88	14/3	EL83	20/5	ML4	8/6	SP61	3/6	UM34	17/8	OC19	48/-	
3Q4	7/6	6N7	8/-	12SK7	6/-	5-pin	23/10	EBC89	9/6	EL84	7/6	MS4B	23/10	SU25	27/2	UM80	15/8	OC22	28/-
3Q5GT	9/6	6P28	27/2	12SQ7	11/6	7-pin	EBL21	23/10	EL86	17/8	N37	23/10	TDD4	12/6	UU6	20/5	OC26	25/-	
354	7/-	6Q7G	6/6	12SR7	8/6	AC2PEN	EF86	14/3	EL87	21/0	PABCO 14/3	U12/14	T41	9/-	UR1C	19/1	OC23	87/-	
3V4	7/6	6Q7GT	11/-	12Y4	10/6	DD	EBL31	23/10	EL91	5/-	N78	20/5	TH41	27/2	UU2	27/2	OC28	25/-	
5R4GY	17/6	6R7G	10/-	19AQ5	10/6	AC6PEN	7/6	EBC52	5/6	EL95	10/6	N108	23/10	TP22	15/-	UY1N	19/1	OC35	25/6
5U4G	6/6	6SA7GT	8/6	19HI	10/-	AC/TP	EC54	6/-	EL820	19/1	N308	21/1	TP25	15/-	UY21	17/-	OC44	11/-	
5V4G	10/-	6SC7	7/6	20D1	15/8	ATP4	5/-	EC70	12/6	EL821	27/2	N339	15/-	TP2620	34/-	UY41	7/6	OC45	10/-
5Y3	6/6	6SG7GT	8/-	20F2	27/2	AZ1	19/1	EBC81	27/6	EL822	25/-	P61	3/-	TY86F	13/7	UY85	7/-	OC65	22/6
5Z3	20/5	6SH7GT	8/-	20L1	27/2	AZ31	10/-	EBC92	13/7	EM34	9/6	PABC80 14/3	U12/14	T4/6	VMP4G	15/-	OC66	25/-	
5Z4G	9/-	6S17GT	8/-	20P1	27/2	AZ41	14/3	ECC32	5/6	EM71	23/10	PCC84	8/-	UI6	10/-	VMS4B	15/-	OC70	6/6
6A7	10/6	6S5K7G	6/-	20P2	23/10	B36	15/-	ECC33	8/6	EM80	23/10	PCC85	9/-	UI9	36/-	VP2	12/6	OC71	6/6
6A8	9/-	6S7LGT	6/6	20P4	27/2	B63	7/6	ECC34	25/2	EBC81	9/-	PCC88	18/-	U22	8/-	VP4	15/-	OC72	8/-
6AC7	4/-	6S7NG7	5/6	20P5	23/10	C1	12/6	ECC35	8/6	EBC84	10/6	PCC89	18/-	U24	30/7	VP28	14/6	OC73	16/-
6AG5	5/6	6S7Q7GT	9/-	25A6G	10/6	CIC	12/6	ECC40	23/10	EM85	17/8	PFC80	8/-	U25	18/4	VP4B	23/10	OC75	8/-
6AG7	7/6	6S7GT	8/-	25L6GT	10/-	CBL1	27/2	ECC81	6/-	EN31	53/-	PFC82	10/6	U26	10/-	VP13C	7/-	OC77	15/-
6AK5	8/-	6U4GT	12/6	25YSG	10/-	CBL3	23/10	ECC82	6/-	EN51	9/-	PFC84	17/-	U31	9/6	VP23	6/6	OC78	8/-
6AL5	4/-	6U5G	7/6	25Z4G	9/6	CCH35	23/10	ECC83	7/6	EN83	17/-	PFC86	15/-	U33	27/2	VP41	6/-	OC81	8/-
6AM6	4/6	6U7G	8/6	25Z5	9/6	CK506	6/6	ECC84	9/-	EN84	14/-	PCL82	10/-	U35	27/2	VR105	8/-	OC139	24/-
6AQ5	7/6	6V6G	7/-	25Z6G	10/-	CL33	19/9	ECC85	8/6	EN86	9/-	PCL83	10/6	U37	27/2	VR150	7/6	OC170	13/6
6AT6	7/-	6W6GTG	8/-	27SU	20/5	CV63	10/6	ECC88	18/-	EZ35	6/-	PCL84	12/6	U45	11/6	UT61A	5/-	OC171	14/6
6AU6	10/-	6X4	5/-	28D7	7/-	CY1	19/1	EFC80	10/6	EZ40	7/-	PCL85	17/-	U50	6/6	VT501	5/-	OC200	16/6
6BB8	5/-	6XSGT	6/-	30C1	8/-	CY31	11/-	EFC82	10/6	EZ41	7/-	PCL86	17/-	U52	6/6	WT6	5/6	OC203	24/-
6BA6	7/6	6J6	6/6	30F5	6/-	D15	10/6	EFC86	20/5	EZ80	7/-	PENA42/13	U54	20/5	W81M	6/-	OP71	29/6	
6BE6	6/-	7B7	8/6	30FL1	10/-	DAC32	10/6	EHC3	27/2	EZ81	7/-	PEN4DD	U76	6/-	W107	19/1	TJJ	40/-	
6BG6G	23/10	7C5	8/-	30L1	8/-	DAF91	6/-	EHC21	23/10	FC4	15/-	PEN25	4/6	U201	17/-	X41	15/-	T13	50/-
6BH6	8/-	7C6	8/-	30L15	11/6	DAF96	8/6	EHC35	6/6	FV4/500 8/6	8/-	PEN45	19/6	U251	14/-	X61(C)	12/6	TP1	40/-
6BJ6	6/-	7H7	8/-	30P4	12/-	DD41	14/3	EHC42	9/-	FV4/800 8/6	8/-	PEN45	19/6	U251	14/-	X61(C)	12/6	TP1	40/-
6BQ7A	15/-	7R7	12/6	30P12	7/6	DE25	7/6	EHC81	9/-	GU50	27/6	PEN46	7/6	U281	20/5	X63	9/-	TP2	
6BR7	12/6	757	9/6	30PL1	13/6	DF33	10/6	EHC83	14/3	GZ30	9/-	PEN383	17/6	U282	23/2	X65	12/6	T51	10/-
6BW6	8/6	7V7	8/6	30PL13	13/6	DF66	15/-	ECL80	9/-	GZ32	10/-	PEN393	17/6	U301	23/10	X66	12/6	T52	12/6
6BW7	6/-	7Y4	7/6	315AS5	21/9	DF91	3/6	ECL82	10/6	GZ33	20/5	PEN/DD	U329	14/-	X76M	14/-	T53	15/-	
6C4	5/-	8D2	3/6	315L6GT	9/6	DF96	8/6	ECL83	19/9	GZ34	14/-	4020	34/-	U339	17/-	X78	23/10	T54	24/-
6C5	6/6	9B8V6	15/8	315V4	7/6	DF97	9/-	ECL86	17/-	GZ37	20/5	PL33	19/9	U403	17/-	X79	23/10	V30/10P	28/6
6C6	6/6	9D2	4/-	35Z3	10/6	DH63	6/6	EF9	23/10	HABC80	PL36	12/-	U404	8/6	X109	17/8	X101	9/-	
6C9	13/6	10C1	13/-	35Z4GT	6/-	DH76	5/-	EF22	14/-	13/6	PL38	27/2	U801	30/7	XD1(L)	6/6	X102	10/-	
6C10	9/-	10C2	27/2	35Z5GT	9/-	DH77	7/6	EF36	4/-	HL2	7/6	PL81	10/6	U4020	19/1	XFG1	18/5	XAI03	15/-
6CD6G	37/5	10F1	27/2	43	10/-	DK32	12/-	EF37A	8/-	HL23	15/8	PL82	7/6	UABC80	9/-	XFY12	9/6	XAI04	18/-
6CH6	9/-	10LD11	16/4	150C5	10/-	DK91	6/6	EF39	5/6	HL23D	7/6	PL83	9/-	UAF42	9/6	XFY34	18/-	XBI02	6/-
6D6	6/6	10P13	15/-	50CD6G	RM-5	DK92	9/-	EF40	15/-	HL42DD	PL84	13/-	U841	12/-	XH1(I)	6/6	XBI03	6/6	
6E5	12/6	10P14	19/9	37/5	DK96	8/6	EF41	9/-	PL85	19/9	PL820	19/1	U841	8/6	XSG1(5)	6/6	XBI04	7/-	
6F1	27/2	12A6	5/-	50L6GT	9/6	DL33	9/6	EF42	10/6	HN309	25/2	PM84	17/8	U8C81	11/6	Y63	7/6	XCI01	6/6

ALL GOODS BRAND NEW AND SUBJECT TO FULL MAKERS' GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL SECONDHAND GOODS OR MANUFACTURERS' REJECTS.

Standard tubular condensers | MIDGET TUBULAR CERAMIC | LOW VOLTAGE BIAS | RESISTORS

-001/1000 v.....9d. -1/500 v.....9d. -25/500 v.....1/3

-02/500 v.....9d. -5/350 v.....1/3

ANY SIZE 9d. | CONDENSERS | CONDENSERS | Close tolerance types

1/2 watt 4d. 1/2 watt 5d. 1 watt 6d.

1/4, 1/2, and 1 watt all 1/- each.

METAL RECTIFIERS Full List with ratings free for S.A.E.

Less switch 3/- each. With D.P. switch 4/- each.

10K 25K 50K 100K LW7 21/- RM-2 7/6 RM-3 7/6 RM-4 14/- RM-5 19/6

12/- RM-6 7/6 RM-7 7/6 RM-8 14/- RM-9 19/6

14/- RM-10 7/6 RM-11 7/6 RM-12 14/- RM-13 19/6

16/- RM-14 7/6 RM-15 7/6 RM-16 14/- RM-17 19/6

18/- RM-18 7/6 RM-19 7/6 RM-20 14/- RM-21 19/6

20/- RM-22 7/6 RM-23 7/6 RM-24 14/- RM-25 19/6

22/- RM-26 7/6 RM-27 7/6 RM-28 14/- RM-29 19/6

24/- RM-30 7/6 RM-31 7/6 RM-32 14/- RM-33 19

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the RIGHT course:

RADIO & TELEVISION ENGINEERING
INDUSTRIAL TELEVISION
RADIO & TELEVISION SERVICING
RADIO SERVICE AND SALES
VHF/FM ENGINEERING : ELECTRONIC
COMPUTERS & PROGRAMMING


ics provides thorough coaching
for professional examinations:

Brit. I.R.E., City and Guilds Tele-
communication Technicians, C. & G.
Radio & TV Servicing (R.T.E.B.);
C. & G. Radio Amateurs.

LEARN AS YOU BUILD

Practical Radio Courses

Gain a sound up-to-professional-
standards knowledge of Radio
and Television as you build **YOUR
OWN** 4-valve T.R.F. and 5-valve
superhet radio receiver, Signal
Generator and High-quality Multi-
meter. At the end of the course
you have three pieces of permanent
and practical equipment and a fund
of personal knowledge and skill.
ICS Practical Radio courses open a
new world to the keen Radio
amateur.

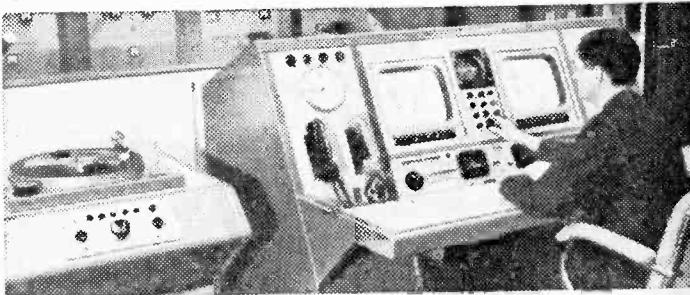

**THERE ARE ICS COURSES TO
MEET YOUR NEEDS AT EVERY
STAGE OF YOUR CAREER.
FILL IN AND POST THIS
COUPON TODAY.**

You will receive the FREE 60 page
ICS Prospectus listing examinations
and ICS technical courses in radio,
television and electronics PLUS
details of over 150 specialised
subjects.

Other ICS courses include:
MECHANICAL, MOTOR,
FIRE, ELECTRICAL &
CHEMICAL ENGINEERING.
FARMING, GARDENING.
ARCHITECTURE &
WOODWORKING.
SELLING & MANAGEMENT.
ART. PHOTOGRAPHY,
etc., etc.

**PLEASE STATE ON COUPON
SUBJECT YOU ARE
INTERESTED IN . . .**

INTERNATIONAL CORRESPONDENCE SCHOOLS

(DEPT. 172). INTERTEXT HOUSE, PARKGATE RD., LONDON, S.W.11

PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

.....

OCCUPATION..... AGE.....

10.61



TAPE RECORDER AMPLIFIER £7.19.6



Compact, well designed 5 valve amplifier. Output 3.5 watts. Input Microphone, Radio and gram. Size 9" x 3" x 4in. Ins. Carr. 4/6. 12 months' guarantee. Terms available.

EXTRAS—Dial plate incl. sockets and super-impose switch, 3/6. Knobs 2/6.

VALVES SALVAGE GUARANTEED

50/- Each.	30/- Doz.
B36, EBF80, ECC31, ECC34, ECC81, ECC82, ECC85, ECC91, ECH42, EFB80, EF92, EL32, EV51	
KT36, KTW61, L63, N14, N37, U22, U31, UC10, 6L18, 6S77, 6U4GT, 10D1, 10F1, 20D1,	
5/- Each.	60/- Doz.
EBC33, EBF80, ECF90, ECL80, EL33, EL35, EL41, EY55, GZ32, KTC3C, KV33, LA162, LA162, N309, N309, PC531, PCE51, PCF82, PL38, PL38, PY80, PY82, 6F6, 6K8, 7AN7, 9BW6, 20F5, 20L1.	
Postage: 1-7d. 8-16d. 12-26d	

STAMP FOR
LATEST
FREE LIST.

DUKE & CO. (LONDON) LTD. 621/3 Romford Road
Manor Park, E.12

SUB-MINIATURE COMPONENTS NOW THE

- Ferrite aerial with Long and Medium Wave Coils 4in. long for pocket superhet, complete with circuit showing component values etc. 7/6d.
- Ferrite aerial as above, but 5in. diameter, 5in. long for table model receiver or portable. 10/6d.
- Three I.F. Transformers with oscillator coil and circuit details to work with Item 1. 19/8d.
- Three I.F. Coils and oscillator to work with item 2. 23/8d.
- Smallest possible electrolytics. 1MFD, 2MFD, 4MFD, 5MFD, 6MFD, 8MFD, 10MFD, 20MFD, 30MFD, 50MFD, 100MFD, 200MFD all 1/8d. each.
- Smallest 1/2 watt resistors all 10% values 5d. each.
- Miniature condenser 1.1/0d., .5, .04, .02, .01 all 8d. values below this 7d.
- Miniature slide switch double pole change over 2/6d.
- Edgegewave volume controls 2K, 5K, 10K and 20K 2/6d. each.
- Small edgegewave controls with switch 2K, 5K, 10K and 20K 4/6d. each.
- Red Spot Transistors tested and suitable all A.F. applications 2/6d.
- White Spot Transistors tested and suitable as I.F. or mixer 3/6d.
- Set of six transistors for superhet Mullards in original packets, fully guaranteed, comprising OC44, OC45, OC45, OC81D and matched pair OC91. 22 the set.

SPECIAL SNIP—this month.

The Pocket "5" as described alongside, but fully made up and ready to work. £5.16.0, plus 2/6 post and insurance.

ILFord 6001/3

DE LUXE RECORDER CABINET 79/6



Beautifully styled, rexine covered cabinet in Red or Beige. Size 14" x 13" x 9in. Storage compartment in lid for Tapes and microphone. Easily adapted to Record Player Cabinet. Ins. Carr. 4/6.


SCOTCH BOY TAPES

5½ inch 19/9 7 inch, 25/-
Limited quantity. Post Free.

17 in. EX RENTAL SETS

£11.10.0

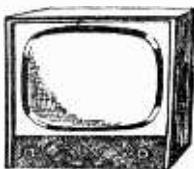Excellent Table models:
ITA/BBC. Famous manufacturer. 12 months guarantee. Terms available. Collection advised, or delivery rate by arrangement up to 50 miles, or despatched in 3 parcels for easy assembly 25/-.



TV TUBES

12 months' guarantee
H.P.
Terms available

21in. 99/6
17in. 90/-
15, 14, 12in. 70/-

Ins. Carr. 15/6.

£1 extra without old bowl, refundable if same received within 14 days.

35/- 14 in. TV TUBES
14KP4 and 36/24

Due to large purchase of Rental replacement stocks. Carr. 5/-.

TRANSISTORS

Per Set **47/6** Post Free

MULLARD
1-OC81D 6/9, 2-OC81 6/9,
1-OC44 9/9, 2-OC45 8/9,
Diode 1/9.

GEC | EDISWAN
114 6/9 | XC121 8/9
2-874 8/9 | XB113 8/9

9 a.m.—6 p.m.
Half day
Thursday

MARK IV

Read These Testimonials

D. A. Hilton, Leigh, Lancs.
I received my "Pocket 4" on Christmas Day, and made it up on Boxing Day and am very pleased with the results. It brings in local stations and many foreign stations including Luxembourg at good strength. I am 13 years old."

Mr. J. Bell, Wolverhampton.

"I am writing to express my satisfaction at the standard of your kit for your "Pocket 4" Transistor set and also to state that it has come up to my expectations in regard to performance."

Mr. R. Bell, Newcastle-on-Tyne.

"I have built your "Pocket 4" Transistor set, I am very pleased with it."

Mr. F. Jackson, Jarrow, Middx.

"I have built the "Pocket 4" and am more than pleased with the results."

Mr. G. Bamford, Runcorn.

"I find this set even better than you claim it to be and most certainly up to your usual standard of quality. I feel that nobody could fail to build it up and get results. Even the first-time-ever novice, as your circuit diagrams and instructions are so clear and precise."

Mr. A. J. Simmonds, Welling, Kent.

"I purchased from you a week ago the "Pocket 4" Transistor Kit, I put it together last night in 1½ hours, on switching on the set I was right on Radio Luxembourg. I must say thank you because not only has the set a very attractive appearance, it also behaves fantastically."

Mr. D. C. Smith, London.

"I am sending you a testimonial for the "Pocket 4" Transistor Kit. I have had it for about 10 weeks now and am very pleased with it. I have had no trouble at all in getting it to work and I am very happy with the results."

Mr. G. H. Williams, London.

"I am sending you a testimonial for the "Pocket 4" Transistor Kit. I have had it for about 10 weeks now and am very pleased with it. I have had no trouble at all in getting it to work and I am very happy with the results."

Mr. G. H. Williams, London.

"I am sending you a testimonial for the "Pocket 4" Transistor Kit. I have had it for about 10 weeks now and am very pleased with it. I have had no trouble at all in getting it to work and I am very happy with the results."

Mr. G. H. Williams, London.

"I am sending you a testimonial for the "Pocket 4" Transistor Kit. I have had it for about 10 weeks now and am very pleased with it. I have had no trouble at all in getting it to work and I am very happy with the results."

Mr. G. H. Williams, London.

"I am sending you a testimonial for the "Pocket 4" Transistor Kit. I have had it for about 10 weeks now and am very pleased with it. I have had no trouble at all in getting it to work and I am very happy with the results."

Mr. G. H. Williams, London.</

THE GREATEST MONEY-MAKER EVER OFFERED TO THE RADIO MAN!

ALL THE CIRCUITS, DIAGRAMS, REPAIR DATA
AND INFORMATION YOU NEED FOR NEARLY

2,700 Models COMPLETE IN 7 VOLUMES

TELEVISION · RADIO · RADIOPHONICS · CAR RADIOS
TAPE RECORDERS · RECORD REPRODUCERS

Newnes RADIO AND TELEVISION SERVICING provides at instant call, any time, day or night, all the circuits and data you need for almost all the popular TV and Radio sets in use. It is the only complete library of servicing data and worth its weight in gold!

1954-1961 Popular Models—Over 4,400 Pages

Servicing Data for all these makes—Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, Ford Motor Co., Garrard, G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Portogram, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Robert's, Radio, Sobell, Sound, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.

GIVES LATEST DEVELOPMENTS AND TIME-SAVING HINTS



Please send me Newnes
RADIO AND TELEVISION SERVICING
(in 7 Volumes) without
obligation to purchase. I
will return in 8 days or
send 16/- deposit 8 days
after delivery, then
twenty monthly sub-
scriptions of 16/-, paying
£16.16s. in all. Cash
price in 8 days is £16.

To: George Newnes, Ltd., 15-17 Long Acre, London, W.C.2

Name _____

Address _____

Occupation _____

Your Signature _____
(Or Parent's Signature
if you are under 21)

Tick (✓) where applicable	
House OWNER	
Householder	
Living with Parents	
Lodging Address	

RVIW



TEST IT ON
7 DAYS

FREE TRIAL

ABSOLUTELY NO
OBLIGATION TO BUY

Make sure of seeing this great
profit-maker in the quiet of
your own home.

ACT TO-DAY

MORE THAN 4,500 CIRCUITS AND
COMPONENT LAYOUT DIAGRAMS

FREE TELEVISION ENGINEERS' POCKET BOOK (Value 12/6)

This 272-page book is the perfect companion to your servicing set. Covers basic circuitry, fault-finding, interference, alignment, valves, etc.

**Every purchaser is entitled to 2 YEARS'
FREE POSTAL ADVISORY SERVICE**

REPLACEMENT TUBES

**REBUILT CATHODE RAY TUBES ARE NOW USED BY
OVER 80% OF RETAIL SERVICE DEPARTMENTS
AND RENTAL ORGANISATIONS**

FOR QUALITY, RELIABILITY AND SERVICE BUY FROM BRITAIN'S LEADING GROUP OF INDEPENDENT MANUFACTURERS OF REBUILT CATHODE RAY TUBES

SUFFOLK TUBES LIMITED
1/3 UPPER RICHMOND ROAD
PUTNEY, LONDON, S.W.15.
Tel: Vandyke 4304/5267

MIDLAND TUBES LIMITED
37 GEORGE STREET
MANCHESTER, 1.
Tel: Central 4568/4569

VIDIO REPLACEMENTS LIMITED
HALES STREET
DEPTFORD HIGH STREET S.E.8.
Tel: Tideway 4506/2177

ALL TYPES

Scotts Radio Ltd.
4 Church Street
Brighton
Tel: Brighton 26891

Weston Hart Ltd.
236/8 Fratton Road
Portsmouth
Tel: Portsmouth 24125

Lawsons Ltd.
36 Cornhill
Bury St. Edmunds, Suffolk
Tel: Bury St. Edmunds 3304

J. H. Sunderland
11 Clements Street
Rochdale, Lancs.
Tel: Rochdale 48484

Wizard Productions
16 Withy Grove
Manchester
Tel: Dea 2772

J. Charlesworth & Son
14 Hightown
Crewe, Cheshire
Tel: Crewe 2535

KEEN PRICES WRITE FOR BROCHURE

Taylors
162 Eastney Road
Milton, Portsmouth
Tel: Portsmouth 35000

Wanda Electrics
9 Manor Road
Gravesend
Tel: Gravesend 3766

Stowmarket Co-operative
Bury Street
Stowmarket, Suffolk
Tel: Stowmarket 51/52

Frank H. Hunt & Co.
Stepcote Hill
Exeter, Devon
Tel: Exeter 56687

H. Knowles
54/56 Chester Road
Manchester
Tel: BLA 9031

Radio Services Ltd.
30 Mona Street
Amlwch, Anglesey
Tel: Amlwch 594

PROMPT DELIVERY

Hi-Lite Ltd.
89 Southbourne Grove
Southbourne, Bournemouth
Tel: Bournemouth 44344

R. Watson
Leathern Bottel
Wavenden, Woburn Sands, Bucks
Tel: Woburn Sands 2027

R.E.S. Ltd.
17/19 Paynes Lane
Coventry
Tel: Coventry 28781

Gwalia Radio & T.V.
Llanstephan
Carmarthen
Tel: Llanstephan 284

J. Wildbore Ltd.
6-12 Peter Street
Oldham
Tel: Mai 4475

Tele-Car Ltd.
66 Osborne Street
Glasgow, C.1
Tel: Bell 1912/3

Practical Television

AND TELEVISION TIMES

VOL. 12, No. 133, OCTOBER, 1961

Editorial and Advertisement Offices:

PRACTICAL TELEVISION

George Newnes Ltd., Tower House
Southampton Street, W.C.2.

© George Newnes Ltd., 1961

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

SUBSCRIPTION RATES

Including postage for one year

Inland - - - £1.20 per annum
Abroad - - - £1.06 per annum
Canada - - - 19s. per annum

Contents

	Page
Editorial	7
Telenews	8
Servicing Television Receivers	10
Metal Rectifiers and Crystal Diodes	12
Uncommon CRT Faults	15
Variable Voltage Stabilised Power Supply ...	17
Tracing TV Faults ...	20
A Precision Wobbulator	25
Practical Television Multi- meter	28
PC97 Beam Triode	35
Underneath the Dipole	39
Letters to the Editor ...	43
ITA Station in South-East England	44
Your Problems Solved... ...	47

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television", George Newnes, Ltd., Tower House, Southampton Street, London, C.I.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the British Commonwealth and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Our Free Blueprint

In every copy of this issue, is a blueprint for a comprehensive multimeter—the latest PRACTICAL TELEVISION design. This blueprint is the culmination of several months' work on a design which did not employ special parts and would therefore be especially suitable for the amateur radio or television enthusiast. For range selection, two standard 3-pole, 12-way rotary switches are used and the combinations of settings obtainable with these two switches provide 21 ranges. Included in this number are four ranges for the measurement of alternating current—this provision is unusual and is seldom found even in commercial instruments intended for the use of the amateur constructor. Of course, the need to avoid the inclusion of specialised parts has meant that a current transformer could not be used for these ranges and these scales are not linear.

The rectifier used for the A.C. readings is a bridge type made up of four OA70 germanium diodes—a readily obtainable type. This was thought preferable to using a meter rectifier on two counts; firstly, as already mentioned, OA70's are readily available, and, secondly, their use enables the instrument to be employed (for comparison purposes) at R.F.

The series resistors and shunts are described in detail in the text of the article on the Multimeter and no special equipment is needed when adjusting these components to their correct values for the meter movement concerned. In fact, the meter movement is used as the standard in the procedure given.

Although a printed circuit is used as the basis of the construction of the meter, it would be possible to use a conventional method with tag-strips, but the advantage of the actual-size layout given on the blueprint would be lost. Complete information is given on making the printed circuit and no difficulty should be experienced.

This design has been produced to give the amateur the chance of acquiring a comprehensive instrument equal in sensitivity to many expensive designs on the market ($20,000\Omega/V$) and at considerably reduced cost. Next month, we shall give details of a suitable case for the completed instrument together with more information on the calibration, and we are confident that any amateur who makes the meter will be assured of good results.

INCREASED PRICE

At last the ever increasing costs of production have caught up with us, and it is now a necessity that the price of this magazine should be increased to 1s. 9d. The October issue of PRACTICAL TELEVISION then, is the last at the present price of 1s. 6d. and with the November issue the price will be increased by 3d.

This decision was not one easy to make, but was the inevitable result of a continued rise in cost of paper, printing and many other expenses.

Our next issue, dated November, 1961, will be published on October 20th.

Telenews

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of July, 1961, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London	1,948,296
Home Counties	1,594,721
Midland	1,723,126
North Eastern	1,846,948
North Western	1,500,582
South Western	978,023
Wales and Border Counties	692,502
Total England and Wales	10,282,198
Scotland	1,034,430
Northern Ireland	168,178
Grand Total	11,484,806

625-Line TV at the Radio Show

TWENTY-ONE of the television receiver manufacturers who exhibited at this year's Radio Show in London had on show TV sets working on the 625-line standard.

This was the first time that commercial exhibitors had shown 405/625-line TV sets in operation at the Radio Show and visitors saw them working alongside standard 405-line receivers.

Continuous daily transmissions of a 625-line monochrome demonstration picture were relayed from the Radio Show control room to the manufacturers' stands, where converters raised the frequency into the UHF band.

Colour Television on a Large Scale

A NEW large screen colour television projector has recently been developed at the Marconi Colour Television Laboratories.

The projector accepts either separate red, green and blue signals, or a composite coded signal, and projects a picture measuring 12ft by 9ft on to a screen 25ft away. Each colour channel has a separate video

amplifier with a bandwidth of 10Mc/s, and these amplifiers feed 5in. cathode ray tube projectors operating at 50kV EHT.

The three projectors are mounted side-by-side, and only the centre one is on the normal to the screen. An electronic correction waveform has therefore to be applied to each of the outer cathode ray tubes to avoid "keystone" distortions of the picture.

Microwave Link for Satellite Television Stations

THE British Broadcasting Corporation has awarded a contract to Pye Telecommunications Limited for the supply of four microwave links.

The links will operate in the 7000Mc/s band and each will consist of a transmitting terminal, with two transmitters, and a receiving terminal, with two receivers.

The equipment will be used to convey programmes to certain new low-power satellite television stations which are being set up to extend the coverage of the BBC's television service.

New TV Station for Wales

THE Postmaster-General has approved the ITA's plan for the erection of a station to serve the Flint-Denbigh area of Wales.

As announced in June, a group known as the Wales Television Association, has been selected as the programme company for the combined West and North Wales area which will be covered by three stations, one in Pembrokeshire, a second in the Lleyn Peninsula and this third one for Flint and Denbigh. The total population coverage of the three stations is estimated to be of the order of one million. The Authority has been assured of the



A general view of this year's Radio Show, at Earl's Court, London.

group's intention to broadcast, at good viewing times, programmes of specific interest to the Welsh audience, including regular Welsh-language programmes.

It is hoped that the Pembrokeshire and Lleyn stations will begin transmissions in less than a year's time, with the Flint-Denbigh station coming on the air some months later.

Transmitting Aerials for Five New Stations

THE British Broadcasting Corporation has placed contracts with EMI Electronics Ltd., for transmitting aerials and feeder systems at five new stations in Scotland, Wales, Cornwall, Lancashire and Oxfordshire, which the BBC is building to extend its television and sound services and to improve reception in the fringe areas.

At the station now under construction at Llandrindod Wells in Central Wales, turnstile arrays have been installed on an 80ft section at the top of a 250ft mast.


The stations under construction at Redruth, Cornwall and Beckley, near Oxford, will be equipped with television and VHF sound arrays on 500ft masts later this year. The Morecambe Bay station, to be built near Barrow, will be provided with a television aerial on a 250ft mast, while the Scottish station being built at Ashkirk, near Selkirk, will be equipped with television and VHF sound arrays on its 700ft mast.

All these arrays will be horizontally polarized with the exception of the television array at Ashkirk which will be vertically polarized.

Hospital Operating Theatre has Built-in TV System

THE Queen Elizabeth Hospital, Birmingham, was equipped with a new type of closed circuit television assembly during August. The installation was officially handed over to the Dean of the Faculty of Medicine at the University of Birmingham by Mr. B. R. Greenhead, Technical Controller of A.B.C. Television, which has presented two television camera channels to the University. Both Camera channels have been supplied by EMI Electronics Ltd.

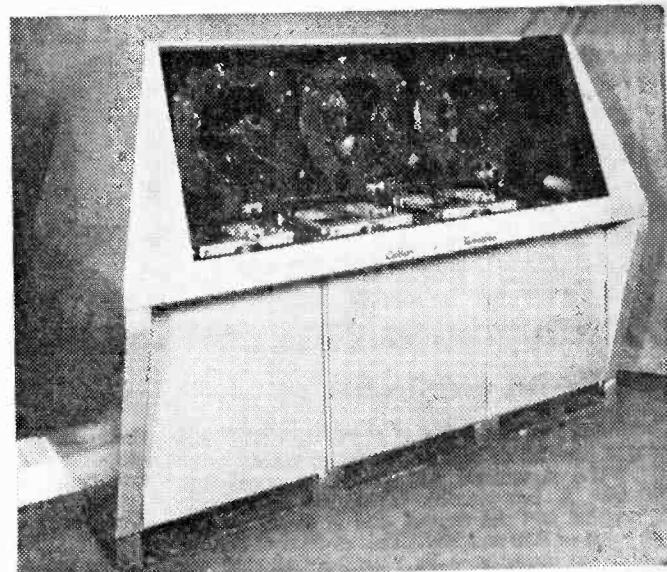One channel works on the 625-line standard and has been installed in theatre No. 3 of the Queen Elizabeth Hospital and will



This new colour television projector has been developed at the Marconi Colour Television Laboratories. Three separate red, green and blue projectors are used to produce the full colour picture.

be used for graduate and post graduate study of surgical operations.

A second portable channel—405-line standard—will be used for microscopy, behavioural research and many other study and research projects in the Medical school.

The EMI camera installed in the operating theatre will enable a large number of students in an adjoining lecture room to watch, on large screen television receivers, operations performed by the tutorial staff.

A two-way microphone talk-back system between the lecture room and the operating theatre will enable surgeons to explain operations step-by-step, and to give an immediate answer to questions raised by the medical students.

The camera, operated by remote control from the adjoining lecture room, is fitted with a motorised zoom lens which will allow for general long shots and detailed close-up study. The camera, in a sterilised housing, is built into the surgical lamp above the operating table. By means of a reflecting mirror the camera will always be centred exactly on the area of surgery, and requires no adjustment by the surgeon or his assistants.

Television Equipment Contract

A CONTRACT for the major equipment required by Grampian Television Limited in their new Studio Centre at Aberdeen has been awarded to Pye T.V.T. Ltd., of Cambridge.

Equipment being supplied by Pye includes three Staticon Television channels, three Broadcast Staticon cameras with their associated control and monitoring equipment and a comprehensive master control system designed specifically to meet Grampian's operational requirements.

Underwater TV for Russian Tugs

FOLLOWING an order for TV equipment placed by the Finnish shipbuilding firm Valmet Oy, Marconi underwater television cameras will be used for salvage operations by a fleet of seven Russian tugs.

Seven Marconi-Siebe, Gorman cameras and monitors are to be delivered to the Pansio Shipyard, Turku, for installation on board the diesel-driven salvage tugs now being built.

Diving equipment, and underwater cutting and electric arc welding devices, are carried by the tugs. The cameras will enable salvage experts to see work being carried out by divers.

Servicing Television Receivers

No. 72—THE INVICTA 338

By L. Lawry-Johns

(Continued from page 604 of the September issue)

THE method of biasing the frame output valve V11A is unusual and should be noted (see Fig. 3, last month). There are no cathode components and the control grid is biased by the high value of R56 and R57. This method of biasing enables the linearity to be varied by altering the H.T. at V12A (which would normally alter the overall height or vertical amplitude) whilst variation of the screen voltage of V11A, with feedback from T4, alters the height.

The bias of the sound output valves is also unusual since it is derived from the line output valve control grid, the normal (-32)V being divided by R44/R45 to provide some (-7)V to the lower end of the volume control. Decoupling being carried out by C41 (25 μ F).

Valve Functions

V1 is the usual cascode R.F. amplifier (PCC84) feeding V2 (PCF80) mixer-oscillator. The output of the tuner is taken to the main deck via coaxial cable where it is amplified by V3 (EF85) which is

the common vision and sound I.F. amplifier. The output of V3 is split to feed V4 (EF80) vision I.F. amplifier and V8 (EF80) sound I.F. amplifier. The output of V4 is demodulated by V5 (OA70 crystal diode) which is inside the final I.F. coil (T1) can — see Fig. 5 (last month).

The video signal is taken via L6 to V6 PCL84 pentode section where it is amplified before being passed on to the tube cathode and V6 triode which is used as the sync separator. The AGC is derived from the triode grid, the actual applied AGC voltage being controlled manually by a cancelling voltage from the contrast control. The sync pulses are passed by C56 to the line oscillator section of V12 (ECC82) and by R64 to the interlace circuit V11B (PCL82 triode) before the filtered frame pulses are presented to the frame oscillator section of V12 (see Fig. 3).

The line oscillator works in conjunction with the line output V13, i.e., there is no separate oscillator as such and this also applies to the frame timebase where V12 and V11 pentode form the frame oscillator.

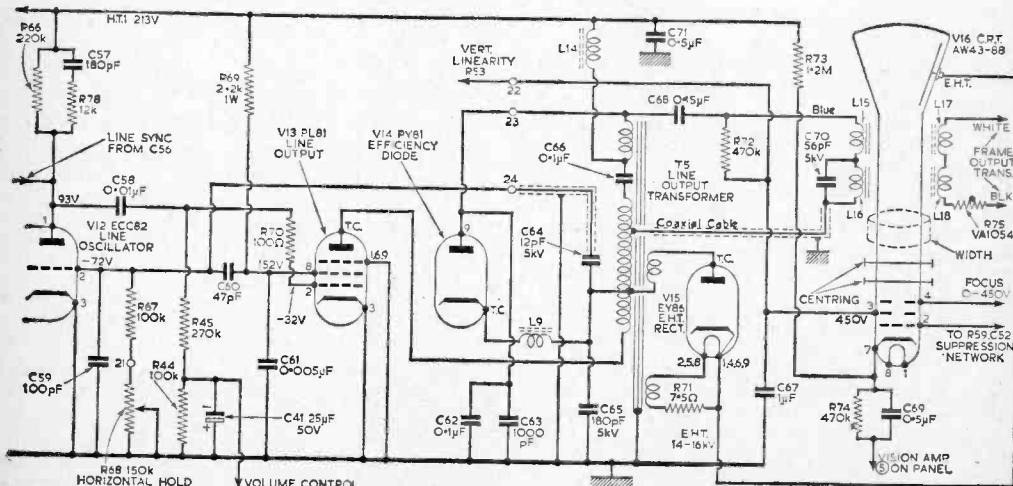


Fig. 6.—The line timebase circuit: note the connection of the volume control to the grid of the PL81, and the boost line feed to the frame linearity control.

The efficiency diode is V14 (PY81) and V15 (EY86) is the EHT rectifier. V8 is the sound I.F. amplifier, the output signals of which are passed to an OA79 crystal diode for detection. The detected A.F. signals are amplified by V10A and then R/C coupled to the volume control for amplification by V10B, the sound output (see Fig. 7).

Fault Symptoms

No signals. Raster on screen when brilliance is turned up, noise from loudspeaker but no vision or sound signals.

Suspect V1, V2 and V3 and check H.T.2 voltage (197). If valves and H.T. are in order, check R4 (5.6k) by the side of the tuner unit—the oscillator H.T. feed resistor. Also check the similar resistor inside the tuner (same circuit). There is another 5.6k in the mixer anode feed circuit, which should be checked.

No Results, Heaters Not Alight (See Fig. 4 last month)

Check the mains input and 1A fuse. Check mains at the large right-hand side mains dropper (black). The 70Ω section (R30) seems to have a habit of going o.c. If this section is found to be o.c., the dropper may be replaced or a 70Ω 10W resistor wired across the tags. When using a neon tester, a glow will be obtained on one tag but not at the other when a section is o.c. Note: at all times it should be ensured that the black lead is connected to the *neutral* side of the mains. If a neon tester lights when applied to the chassis the mains leads or plug must be reversed.

If the dropper records mains potential at all tags, it is necessary to check through the heater chain to ascertain which heater is o.c. The heater chain was shown in Fig. 4.

No Picture, Sound in Order

Advancing the brilliance does not produce a raster.

Remove the rear cover and check the line timebase and EHT. If the line timebase is working, the characteristic whistle should be heard varying with the hold control. If the whistle is absent, note the condition of the PL81. If this is red hot internally, V12 (ECC82) may well be at fault or the PL81 itself may be internally shorted. If a new valve restores the line timebase, but the width is reduced or the PL81 still overheats, check R69 2.2k and use a wire-wound resistor as a replacement.

If the PL81 does not overheat but the timebase appears to be dead, check the PY81, and capacitor C66. If the line timebase is working, check EHT at the anode of the tube. If it is absent, suspect the EY86 (V15). If EHT is present, check the voltage at pin 3 of the CRT. If it is low remove the lead from the tag and check the voltage at the lead. If it is now about 450, suspect a 1st anode-cathode short in the tube. Replace the lead on tag 3 and short pin 7 to pin 8 (chassis). This may clear the short. If not, short out R72 (470k) and again short 7 to 8. With R72 out of the circuit the short should be blown clear.

If the EHT and first anode voltages are in order and the cathode voltage is approximately 150 (this depends upon the signal input) check the voltage swing at pin 2 (grid) which should vary from


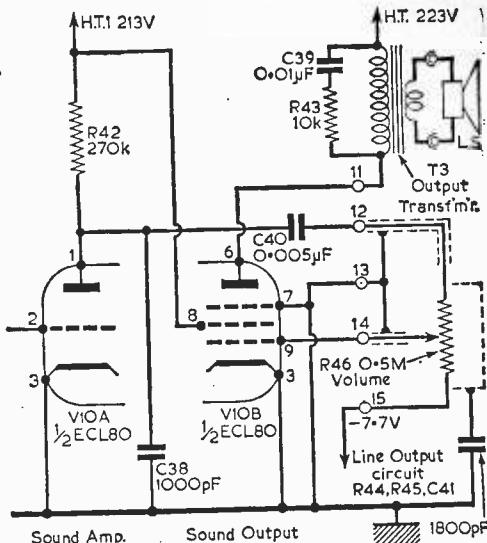


Fig. 7 (above).—The sound output circuit: note the grid bias of V10B.

Fig. 8 (below).—The connections and trimming points of the tuner unit.

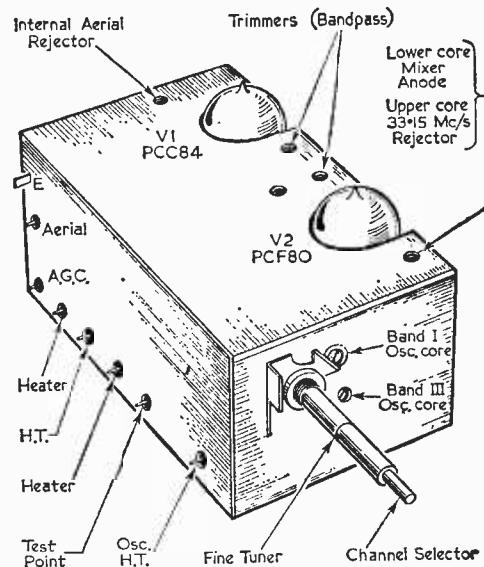

0.213V. If the voltage at pin 2 remains low check C24 (0.25μF) and C52 (0.05μF).

Lack of Width

Ensure that the width sleeve on the neck of the tube has not been pushed in too far under the scanning coils. To adjust this sleeve, it may be necessary to slacken the assembly. Do not rotate the sleeve.

(Continued on page 36)

metal rectifiers

CRYSSTAL diodes are a form of metal rectifier, and all metal rectifiers may be considered as semiconductors. That is to say, they conduct a current of electricity with very little resistance in the "forward" direction, while in the "reverse" direction considerably more resistance is offered to the flow of current. The forward and reverse actions, therefore, depend upon which way round the voltage is applied to the rectifier, for, like a battery and electrolytic capacitor, a metal rectifier is polarised.

Characteristics

In Fig. 1 is shown the metal rectifier symbol and its polarising. When the voltage is applied so that current flows in the forward direction, as shown at (a), two things will be observed: one, the current flow is in the same direction as the "arrow" in the symbol and, two, in order to produce a forward flow of current, the positive of the battery or supply source needs to be connected to the negative of the rectifier and the negative of the battery needs to be connected to the positive of the rectifier. If the polarities are matched, as shown in Fig. 1(b), then there is a low reverse current. These points are well worth remembering.

The symbol arrow thus indicates the direction of current in the *forward* direction. The positive terminal is usually colour-coded red and corresponds to the cathode of a rectifier valve, while the negative side corresponds to the anode of a valve rectifier. This means, then, that if the valve in the rectifier circuit of Fig. 2(a) is replaced by a metal rectifier, the rectifier would be connected as shown in Fig. 2(b).

These circuits show one of the outstanding advantages of a metal rectifier against a valve, and that is that no heater power is required. The total efficiency of a metal rectifier is therefore better than a valve rectifier, which is one of the reasons why metal rectifiers are being used more and more by circuit designers.

Rectifier Types

There are four basic materials from which metal rectifiers are made: selenium, copper oxide, ger-

manium and silicon. Copper oxide and selenium rectifiers have been used in the past mainly for power rectification and are formed by a number of elements clamped in series between metal plates or discs which are used for cooling. Germanium and silicon rectifiers, on the other hand, are formed by a single crystal, for which reason they are usually referred to as crystal diodes.

Selenium stacks are extensively used to provide H.T. supplies for domestic radio and television receivers, and of recent years, they have been


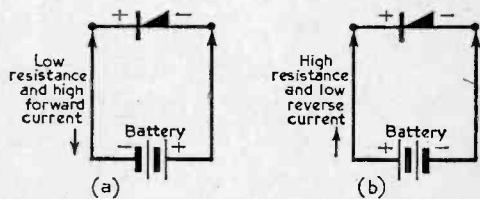


Fig. 1 (above).—When a supply source is connected to a metal rectifier as shown at (a), a high forward current will result in the direction of the arrow. When it is connected as in (b), there will be only a small reverse current.

Fig. 2 (below).—If the valve in the circuit of (a) were replaced by a metal rectifier, it would be connected as shown in (b).

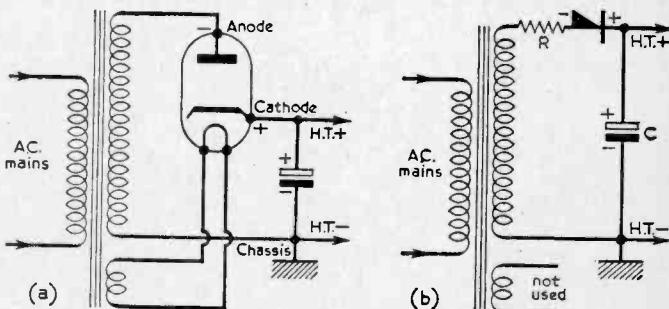

reduced in size by improvement in design and by utilising the chassis on which the circuit is built as a heat conductor, thereby dispensing with the air-cooling fins or plates. Such rectifiers are called "contact-cooled."

Silicon rectifiers are now being used as power rectifiers, and since the forward and reverse losses are below those of selenium and copper oxide units,

and crystal diodes

THE FUNCTIONS AND METHODS OF OPERATION
OF THESE TWO COMPONENTS

By W. Faine

they are more efficient and can be made very much smaller than the older type of rectifier. Indeed, a silicon rectifier designed for 250V r.m.s. and 300mA is no more than $\frac{1}{2}$ in. in diameter and a little over $\frac{1}{2}$ in. in length and weighs only one-tenth of an ounce. However, because of their higher efficiency they require special treatment in the circuit. (A very useful article on such rectifiers and their uses appeared on page 465 of the June 1960 issue.)

Germanium diodes or rectifiers are used mostly in signal circuits, and because of their low self-capacitance they make very good R.F. detectors and mixers. Crystal diodes generally are produced in three ways. There is the point contact type, which is the direct descendant of the "cat's whisker" crystal detector. This has an extremely low internal capacitance, a low forward current and a relatively low reverse voltage. Then, there is the junction diode which provides a higher forward current and is more of a power rectifier. Finally, there is the bonded diode, which in effect is a low-capacitance version of the junction diode.

Rectifier Characteristics

If a milliammeter were connected in series with the circuit of Fig. 1(a) and the applied voltage progressively increased from zero, a curve as shown by

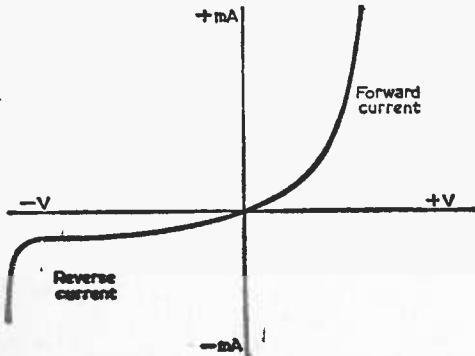


Fig. 3.—The general characteristic curve of a metal rectifier or crystal diode.

the forward current in Fig. 3 could be plotted. Similarly, if the same process were undertaken with the circuit of Fig. 1(b) a curve as shown by the reverse current in Fig. 3 could be plotted. The actual voltages required and the resulting currents would depend upon the type of rectifier under test.

If the forward current rating of the rectifier were exceeded, the rectifier would fuse, and in the case

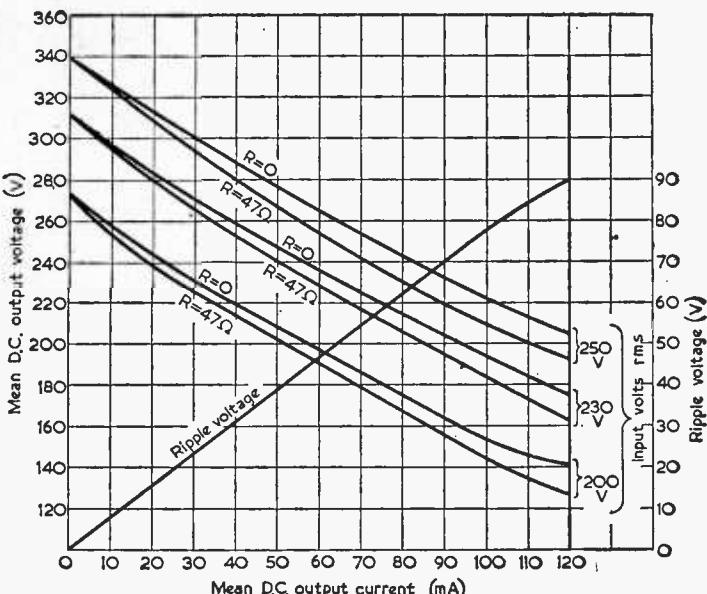


Fig. 4.—The output characteristics curves of a selenium rectifier.

of a selenium or copper oxide stack, severe overheating would first occur, probably accompanied by flashing between the elements and a very unpleasant smell.

Similar symptoms would result by overrunning the rectifier in the reverse current sense. From Fig. 3 it will be noticed that the reverse current increases gradually up to a certain point where there is a rapid increase in current. The voltage at which this rapid increase in current occurs is called the "reverse turnover voltage," and the resulting current will destroy the rectifier.

With power rectifiers, this turnover voltage is of the order of 400V, while with smaller diodes it is considerably less. When selenium or copper oxide rectifiers are connected in series, the turnover voltage (sometimes termed peak inverse voltage) is increased, and this is the reason why two or more rectifier stacks are connected in series in certain power units. It should be noted, however, that copper oxide rectifiers are not generally suitable for mains power supply units.

Applications of Power Rectifiers

When a metal rectifier is used as shown in Fig. 2(b) there are three factors to be considered: the rectifier shall be capable of supplying the required current; the maximum input voltage (r.m.s. A.C.) should not be in excess of the rectifier rating; the maximum peak inverse voltage should not be exceeded.

When the A.C. voltage at the negative terminal of the rectifier in Fig. 2(b) swings positive, a very heavy current flows from the power source through the rectifier to charge the reservoir capacitor C. This current is limited only by the resistance of the power supply and rectifier and can rise to a

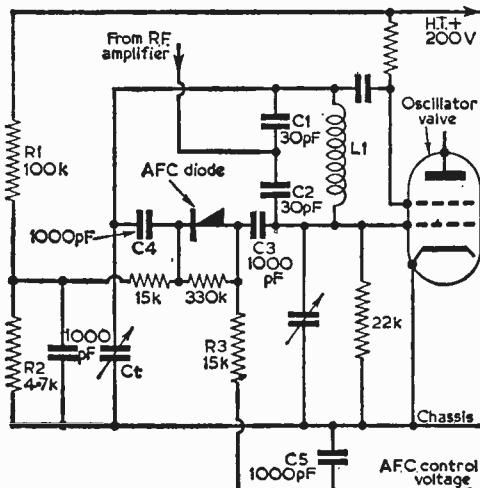


Fig. 5.—An AFC circuit.

value many hundreds of times the working current when a large value reservoir capacitor is used. With silicon rectifiers such a heavy initial current could cause immediate failure since the current is much larger with this type of rectifier owing to its lower forward resistance. To avoid this and to hold the current to a reasonable level a surge limiting resistor R must be included in the circuit, as shown.

A similar resistor is usually also recommended with selenium stacks to minimise ageing which could be aggravated by heavy peak currents. Generally speaking, however, a selenium stack can withstand an almost unlimited instantaneous peak current, though this is not the case with silicon units. Typical values of R are 25Ω for a silicon rectifier and 22Ω or 47Ω for a selenium stack, depending upon the number of elements.

Higher H.T.

Normally, owing to the greater efficiency of a silicon rectifier, when such a unit is used to replace a valve or selenium rectifier, the resulting H.T. voltage is somewhat in excess of that originally obtained. Thus, to avoid exceeding the ratings of associated components it may be found necessary to reduce the output voltage, either by using a surge limiting resistor of slightly larger value, or by increasing the value of the smoothing or H.T. feed resistor, or both.

When the A.C. voltage at the negative terminal of the rectifier in Fig. 2(b) swings negative, there occurs a reverse voltage across the rectifier equal to the positive voltage across C together with the peak voltage of the A.C. If the applied r.m.s. A.C. is, say, 200V, then the peak value will be 280V (peak voltage = $1.4 \times$ r.m.s. voltage). The voltage across the reservoir capacitor under this condition may be 230V, thereby giving a peak inverse voltage across the rectifier of 510V. This may be as high as 2.8 times the applied r.m.s. voltage in some circuits, having a low load.

In Fig. 4 is given the output characteristics of a well-known selenium rectifier stack (STC Type

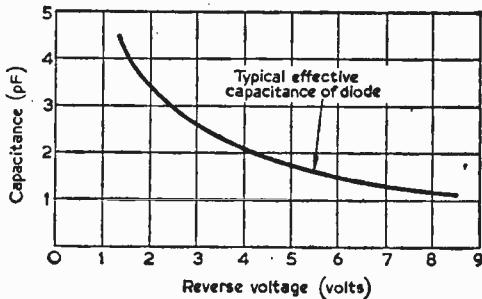


Fig. 6.—This graph shows how the capacitance of a germanium diode varies with a change in reverse voltage.

DSM2/3) with an $8\mu F$ reservoir capacitor. This shows the output voltage and input voltage over a wide range of load currents with, and without, a surge limiting resistor. The ripple voltage is also given and, as is common to all rectifier circuits, this increases with increase in load current. With a larger reservoir capacitor, a larger output voltage is obtained for a given input voltage and the ripple voltage is also smaller. However, by reducing the ripple voltage the time over which the diode conducts is also shortened, which means that the charge of the reservoir capacitor has to be restored during the small intervals at the peaks of the positive-going waves, and this requires current pulses many times in excess of the mean current load.

Diode as Variable Capacitor

The self-capacitance of silicon and germanium rectifiers is not constant but is dependent on the reverse voltage. For instance, as the reverse voltage increases, so the capacitance decreases.

This effect is exploited for automatic-frequency-correction of local oscillators in television and VHF-FM receivers. The diode is connected in such a way across the oscillator tuned circuit that it represents a part of the tuning capacitance. Thus, the frequency of the oscillator may be altered within a small amount by varying the diode bias voltage.

Oscillator Tuning

In Fig. 5 is shown such a circuit. The main capacitance across the oscillator coil L_1 is that made by C_1 and C_2 in series. Also in parallel with L_1 is the AFC diode. C_3 and C_4 simply give DC isolation and are of such large value that they have negligible effect on the diode capacitance. C_t is the oscillator tuning capacitor.

The diode is biased from a standing bias of about $(-4)V$ obtained from the potential divider, R_1 and R_2 , across the H.T. supply. The control voltage is obtained from a discriminator circuit, which gives either a positive or negative control voltage depending to which side of the tuning point the oscillator has drifted. Thus, if the oscillator tends to drift off frequency, the control bias automatically brings it on tune again.

This circuit is based on the S.T.C. Type GD14 germanium point-contact diode, and the diagram in Fig. 6 shows how its capacitance varies with reverse voltage.

(To be continued)

Uncommon CRT faults

SOME PECULIAR FAULTS WHICH MAY NOT, AT FIRST, BE ASSOCIATED WITH THE PICTURE TUBE

By D. P. Samuel

THERE are many tube faults which are very well known, such as obvious low emission, causing a dim picture which may go negative, or black on whites, when the brightness is turned up; shorting electrodes, causing just a blank raster or uncontrollable brightness; open-circuit heater—and other similar faults and their tell-tale effects.

On the other hand, there are tube faults resulting in symptoms which appear to be unrelated to the tube itself and, conversely, there are receiver faults whose symptoms sometimes mislead the experimenter into suspecting tube trouble.

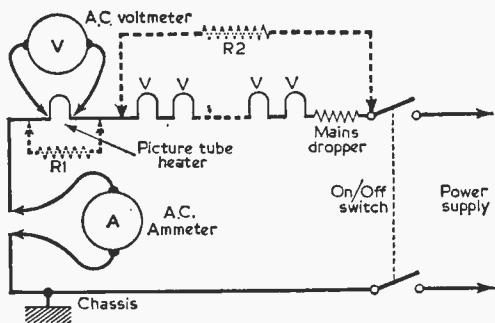


Fig. 1.—A typical heater chain circuit of a television receiver, showing ways of measuring voltage and current, and of fitting compensating resistors.

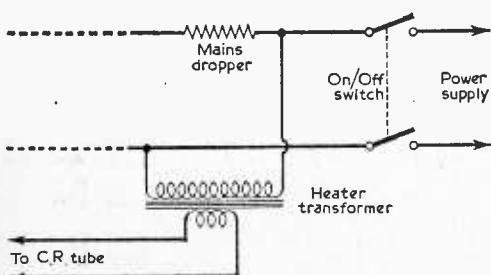


Fig. 2.—The correct method of wiring a heater transformer for the CRT. The resistor R1 of Fig. 1 should be included to balance the heater chain.

Shorting or Ageing Heater

Normal low emission symptoms are caused by the electron-emitting substance on the tube cathode deteriorating with age. This means that there are fewer electrons—and fewer electrons impinging on the screen results in a loss of brightness.

However, the quantity of electrons emitted also depends on the temperature of the cathode, and since it is the heater which raises the cathode to the temperature which produces most electrons, it can be understood that a low-emission system *may* be caused by a faulty heater and not by a worn cathode.

The heat produced by the heater depends on the power that it consumes and, in almost all modern sets, this power is extracted from the heater chain current (see Fig. 1). A heater is rather like a small electric fire the power loading of which is related to the resistance of the element and the voltage applied across it.

Let us take an ordinary picture tube heater rated at, say, 6·3V and 0·3A (typical figures). When such a heater is *hot* and has 6·3V across it, then its current will be 0·3A (or should be). The wattage loading of the heater is equal to the voltage multiplied by the current which, in this case, is 1·89W. This simply means that the tube manufacturer has discovered that the heat produced by a loading of 1·89W is sufficient to bring the cathode in the tube to the optimum emitting temperature. Theoretically, if the loading is greater, no more electrons will be emitted and if the loading is smaller fewer electrons will be emitted.

Now, the tube heater is placed in series with the heaters of all the other valves in the receiver which, like the tube heater, all require 0·3A. The resistive elements of the heater circuit are, in fact, adjusted in relation to the supply voltage so that exactly 0·3A will flow in each heater.

Loading

Assuming that the tube heater is in good order, exactly 6·3V will be developed across it and the heater will load at the optimum 1·89W. However, this will happen only if the resistance of the tube heater is correct and the same as it was when new. The optimum resistance for the heater can easily be found from Ohm's law by dividing the heater voltage by the current, e.g., $6.3/0.3$, which is equal to 21Ω . This is the "hot" resistance, of course, for when the heater is cold its resistance will be smaller—this is why thermistors are used in series-connected heater circuits. The resistance of a thermistor is high when cold and low when hot, and thus cancels out the opposite effect of the heaters.

It sometimes happens that the resistance of a heater becomes less as it ages. Let us suppose that it falls to 15Ω from its optimum 21Ω . Now, since the current in the heater chain is controlled (the very small decrease in resistance of the whole chain will

have no significant effect on the current), the current in the tube heater will remain at 0·3A, but the voltage across it will now be 0·3 multiplied by 15 (Ohm's Law), which works out to 4·5V. The heater loading will have changed from 1·89W to 1·35W (i.e., $4\cdot5 \times 0\cdot3$), which is a drop of 0·54W.

This means that even if the emitting properties of the cathode are in order, it will be unable to provide the full quota of electrons for a picture of normal brightness.

Heater Short

Exactly the same thing happens if a part of the heater short-circuits. The resistance of the heater will be less than optimum, the voltage across it will

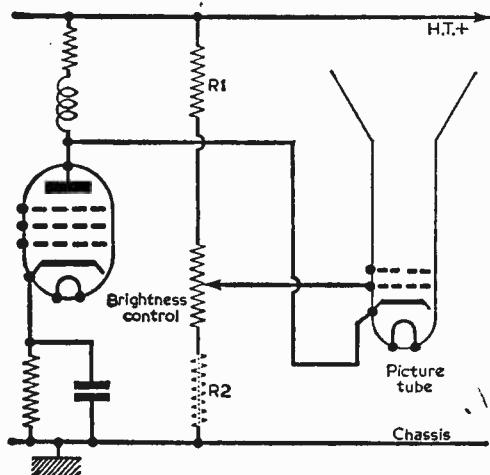


Fig. 3.—Occasionally, when using reconditioned tubes or if there is a change in the tube characteristics, the resistors R1 and R2 may require a different value to compensate.

fall, the current will remain essentially normal and the wattage loading will be reduced. It must be remembered that this happens only because the heater chain current is little affected by the change in the resistance of the tube heater. If the tube heater were fed from a transformer, then matters would be entirely different. The voltage across the lower resistance heater would hold at 6·3V and the current would rise. In the case formerly illustrated, the current would rise to 6·3/15, which is a little over 0·4A. The wattage loading would also rise to $6\cdot3 \times 0\cdot4$ which is a little over 2·5W—0·61W more than it should be.

A heater transformer provides a constant voltage supply, while a series-connected heater chain provides a constant current supply, which is the reason for the two effects described. The effect on the heater itself is that an aged or partially shorting heater in a constant voltage circuit will glow far brighter than normal and in a constant current circuit will be dimmer than normal. These points are well worthwhile observing during the course of diagnosing for tube trouble.

The use of a Constant Voltage Supply

Provided the emission of the cathode is fairly

reasonable a tube with an aged or partially shorting heater can usually be made to produce a picture of good brightness by removing it from the constant current supply and connecting it in a constant voltage circuit.

Before this procedure is adopted, however, one must be sure that the heater is, in fact, to blame. This can be proved with an A.C. multimeter. First, it should be ascertained that the heater chain current is 0·3A by connecting an A.C. ammeter in series with the tube heater, and then an A.C. voltmeter should be connected in parallel with the heater. Alternatively, the heater voltage of several valves in the chain could be measured — if the reading is correct (usually 6·3V), the heater current may be taken as correct. If the current is correct and the voltage across the heater of the tube is low, then the heater is responsible. If the current is low, the voltage across the heater will also be low even if the heater is in good condition. Such trouble would indicate that the mains dropper is set to an incorrect value.

A constant voltage for the tube heater can be obtained from a 6·3V heater transformer. The tube should be disconnected from the heater circuit and a resistor (R1 in Fig. 1) having a value equal to the heater resistance should be connected in place of the heater (in the example given it would be 21Ω rated at 3W or 5W). A heater transformer should be wired into the circuit as shown in Fig. 2. The primary of the transformer should suit the power voltage and should be connected across the receiver side of the on/off switch, so that the switch will also switch on and off the tube heater.

Overloading

As we have already seen, a constant voltage applied across a low resistance heater will increase the loading above normal. Most heaters can stand this, but it must be remembered that the heater is then being overloaded so that the improvement obtained may only be for a short while, as the heater may eventually become open circuited.

This same set-up can, of course, be used to enhance the emission of a tube with a worn cathode. In this event, however, the heater transformer secondary should deliver about 7 or 8V as the process is one of raising the temperature of the cathode in order for it to "boil off" more electrons. This may or may not be successful, depending on the condition of the cathode. It may also result in almost immediate heater failure. Nevertheless, if the tube is otherwise useless, there is nothing to lose.

A tube with a heater-to-cathode short, or intermittent short of this kind, can be subjected to similar treatment, but in this case the heater transformer must be of the low-capacitance variety to prevent the higher frequency video signal components from being lost in the low-impedance heater circuit and mains supply.

An alternative method of passing more current through a low resistance heater is to bypass all the heater chain, except the tube heater, by an additional resistor (R2 in Fig. 1). The value of this resistor should really be adjusted until the voltage across the tube heater rises from its low value to its normal value.

(Continued on page 22)

Variable Voltage Stabilised Power Supply

By R. Brown

MAKING A SIMPLE UNIT FOR WORKSHOP EXPERIMENTAL PURPOSES

(Continued from page 596 of the September issue)

W

E can now fix the minimum output voltage. This must be such that the valve, V2, has sufficient anode voltage. Under the conditions in which it is being worked, an anode voltage of as low as about 30V is sufficient, and this fixes V_{out} at about 200V.

The Circuit Diagram

The complete circuit diagram was given in Fig. 5. A number of additional components have to be added to the basic circuit, in order to ensure optimum conditions in a practical unit.

A capacitor C3 is connected across the neon V4. This has the value of $0.1\mu F$ and its purpose is to reduce the effects of random noise in the neon stabiliser, which otherwise would be present in the output voltage. With the basic circuit, the gain to the 100c/s ripple voltage is the same as the gain to ordinary mains variation and the load variations, and the ripple is considerably reduced by the stabiliser. The gain to the ripple can, however, be considerably increased by connecting a capacitor, C5 of $0.25\mu F$, across the potentiometer R1 (Fig. 1). This acts as a short circuit to the ripple voltage and prevents the reduction in gain introduced by R1 and R2 of the basic circuit operating at ripple frequencies.

The single potentiometer R1 of the basic circuit is replaced by two potentiometers R8 and R9, and a fixed resistance R7. This allows finer control of the voltage and the pre-set potentiometer R8 is used when setting up the


power supply to ensure that R9 controls the output voltage over the desired range of 200V/300V.

A large capacitor C6 of $0.5\mu F$ is connected across the output terminals. This serves to reduce any residual noise and ripple voltages. The value of the output voltage is indicated by a moving coil meter M1. This can be any of the small moving-coil milliammeters available on the surplus market. A one millamp movement was suggested in the components list, but this is not critical. The resistance R11 should have a value such that, with an output voltage of 300V the meter gives full scale deflection. With a 1mA meter, R11 should be 300k. This will ensure that 300V does give full scale deflection. The meter scale can now be calibrated to indicate 0-300V.

A further capacitor C4 was found to be necessary. This is a $20pF$ capacitor, connected between anode and grid of V3. It was found that in certain circumstances the unit became unstable. This is an effect common in negative feedback systems and was cured in this case by using C4 to reduce the high frequency gain of the system. It may well be found with some units that C4 is not in fact necessary and the unit is stable without it. However, it is a small cheap component and is well worth having. It is conceivable that instability could occur even with C4 in place, although this effect has not been met with in practice. If instability should occur then it can be cured by increasing the value of C4. It is most unlikely that instability will occur with C4 in place, and it is worth keeping the value of this component to a minimum, for the reduction in high frequency gain it causes increases the high frequency noise in the output from the unit.

The resistances R6 and R4 are grid stoppers included to prevent any tendency for parasitic oscillations to build up.

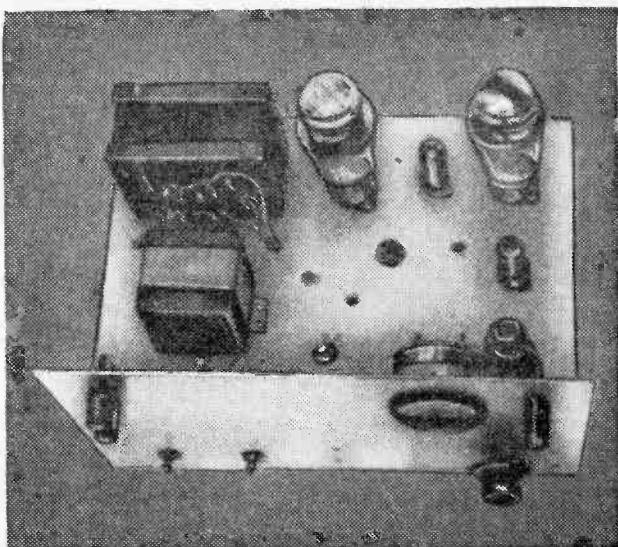The value of R2 could be chosen to give a convenient value of screen voltage for V2, but it



An above-chassis view of the unit.

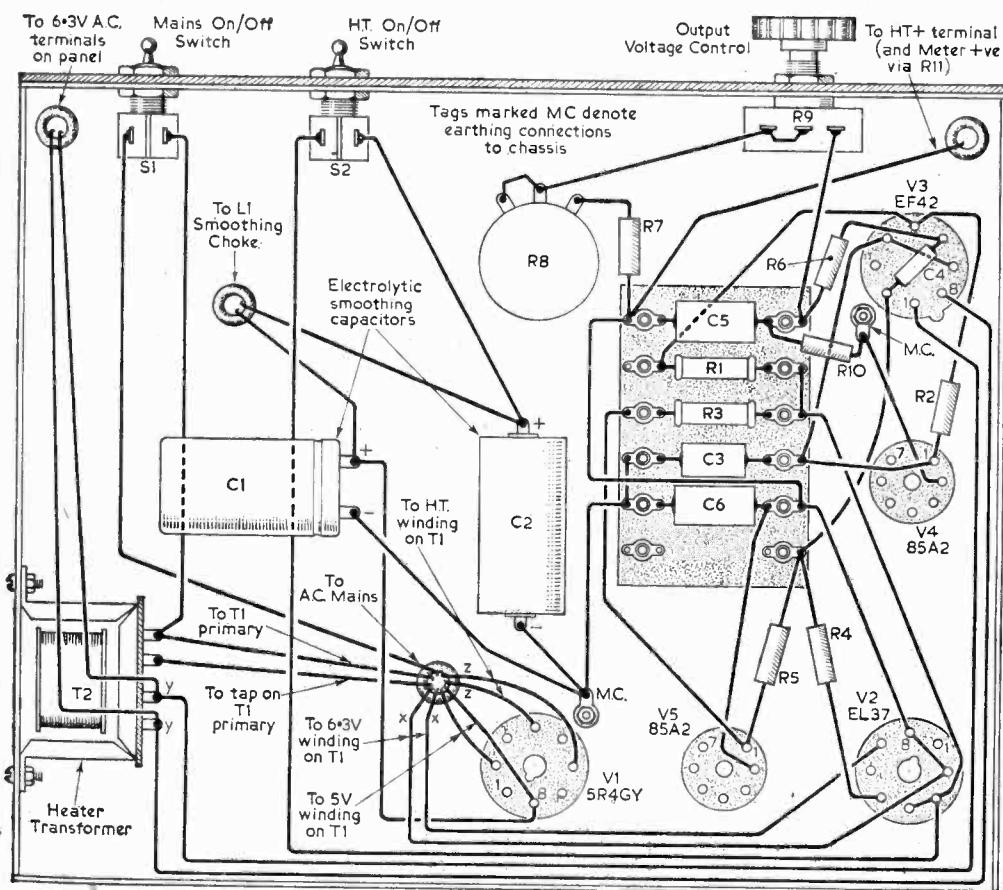


Fig. 6.—The underchassis layout of components and wiring diagram.

can, if carefully chosen, also assist in the stabilisation. In fact it will increase the stabilisation through screen feedback quite considerably, provided it has a value equal to $\mu_2 g_2 rV_4$; where $\mu_2 g_2$ is the amplification factor between g₁ and g₂ in V3 and rV₄ is the A.C. resistance of V4. In the case of the EF42, the value of $\mu_2 g_2$ is about 85 and the value of rV₄ for the 85A2 is 300Ω. A more realistic value for $\mu_2 g_2$ is 65, and this gives a value for R2 of 23.5k; 22k is a suitable value for this position.

The H.T. Supply

The H.T. supply unit is of quite conventional form, the valve used being a 5R4GY—quite a large valve for this application, but it does leave something in hand for any future increase in the output. Two transformers are shown, one providing 350–350V, 60mA for the H.T., 5V for the 5R4GY, and 6.3V for the EL37. The other transformer provides 6.3V for the EF42, and 6.3V output on the front panel. There is no technical reason for using a separate 6.3V filament transformer like this, and a single mains transformer could be used. It is, however, essential to have two 6.3V filament

windings, because one of the 6.3V windings has to supply the EL37, and it should be strapped to the cathode of this valve: this means that it will be between 200V and 300V positive with respect to earth, and so it is not suitable for feeding the EF42 and the front panel output. When looking for a suitable transformer it was found that it was cheaper to buy a standard domestic mains transformer with one 6.3V winding and buy a second filament transformer to provide the other 6.3V supply.


Two on/off switches are used. One is a single-pole single-throw mains switch for switching the whole unit on and off. This is connected in the primary circuit of the transformer T1 and T2. The other is similar to the first, and is used to switch off the H.T. supply, while keeping the valve filaments on.

The filter uses a 5H smoothing choke, a 32μF electrolytic input capacitor, and an 8μF smoothing capacitor—all quite conventional.

Constructional Details

The construction and layout of the unit can be seen from Fig. 6. The layout is not at all critical,

the only important point being that the grid lead to V3 should be kept short, so as to minimise any hum pick-up. The chassis is of a box form about 12in. \times 10in. \times 2½in., with a front panel 12in. \times 7in. The layout of the power supply section will depend to some extent upon the transformer and choke used, and in the unit constructed by the author both the transformer and the choke are of the chassis mounting type, and are on top of the chassis. The smoothing choke did not have any fixing holes, and so is held in place by a strip of metal strapped around it, and fastened to the

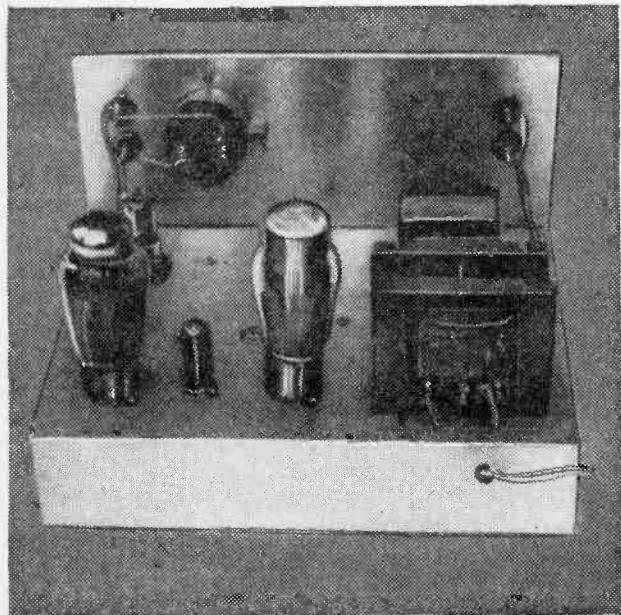

Another view of the power supply.

chassis. The small filament transformer is fixed underneath the chassis, being bolted to the side panel near to the back. The electrolytic capacitors fit under the chassis—their actual fixing depending upon the type of component used.

The two on/off switches are fixed through the front panel and the front of the chassis.

A six-way tag board is used to hold many of the components in the stabiliser circuit, and this is mounted to one end of the chassis to one side of the line of valves. Five components are mounted upon it, the sixth tag serving as an anchor point for the resistors R4 and R5. The voltage control potentiometer, R9, is mounted at the end of the chassis. The pre-set potentiometer, R8, is mounted underneath the chassis with the shaft upwards. The meter is fixed to the front panel—its actual method of fixing will depend upon the meter chosen. H.T. and 6.3V output terminals are fitted on either side of the meter on the front panel.

Wiring

As has been mentioned, the wiring is, with one exception, not critical. The one exception is that the grid lead to V3 should be kept short. If the

layout shown in Fig. 6 is followed, then this will be achieved. The only point about the remainder of the wiring is that it should be kept reasonably neat.

Setting Up

Having constructed the unit the only setting up required is the adjustment of the pre-set potentiometer R8. This should be adjusted until the potentiometer R9 permits the output voltage to be varied from 200V–300V.

The working range of the instrument is nominally 200V–300V, 5mA–50mA for a mains variation of $\pm 6\%$. Somewhat higher output can, however, be obtained at lower output currents. From Fig. 2 (last month), operation is possible anywhere below the line of the -2V grid bias limit; thus it is possible to have an output of 400V, provided the current is 10mA or less, and an output voltage of 350V can be obtained at currents of less than 24mA. It will be necessary to use both R8 and R9 to obtain these higher voltages.

It is also possible to operate below the 200V lower limit at all current levels. Below 200V, however, the gain of V2 falls off rapidly, and the stabilisation provided by the unit becomes very poor. Down to about 175V it is, however, still better than the results obtained from a simple H.T. power supply, and it may well be useful for some purposes. The -2V grid bias limit is drawn for the mains 6% low condition, and when it is known that the mains are normal or high this limit can be moved up, and higher voltages and currents taken from the unit.

Thus the basic trouble-free operating range of the unit is 200V–300V, 5mA–50mA; but provided one is prepared to study and understand the load diagram of Fig. 2, and to keep the diagram handy, the operating range can be usefully extended.

An Unusual Cause of Hum

An unusual cause of hum was encountered during the fitting of a 2V booster transformer to the heater of a CRT fitted in an Ekco T164.

The 25% booster transformer was fitted on the roof of the cabinet and the heater leads taken down to the tube base. A prominent buzz was heard from the rear of the receiver that had not existed before. The scanning coils were examined as was the laminations of the newly fitted transformer and during these tests the buzz faded and returned erratically. In the glare of the bench light the outline of the flex leads from the boost transformer seemed blurred. They were strongly vibrating and causing a mechanical buzz against the focus assembly. When pulled away from the region of the focus magnet, they ceased to buzz. The heavy current flowing in the flex (over 1A) produced a magnetic field that reacted with the powerful focus-magnet field sufficient to vibrate the wires at the mains frequency. Dressing back the flex from the magnet stopped the buzz.

TRACING TV FAULTS

By G. J. King

(Continued from page 618 of the September issue)

LAST month, the need for logical step-by-step location of faulty parts in TV receivers was stressed and a general description of TV circuitry given. This month a specific type of fault will be examined.

Signal Paths

Referring again to Fig. 2, it will be seen that the directly related stages of the signal paths follow a definite pattern. This applies particularly to those stages concerned with I.F. signals, for in order to ensure optimum stability, the designer has to arrange the layout of the stages so that the stray inductances and capacitances of the interconnections are as small as possible. This means, of course, that adjacent stages have to be placed as close as possible together.

This was illustrated in Fig. 1, from which it may be seen that the signal from the tuner (stage 3) goes direct to the common I.F. stage (stage 4), and that stage 4 goes direct to stages 5A and 5B, and that stage 5B goes direct to stage 6B and so on.

This necessary pattern assists considerably in stage identification. In most cases, the various stages, as shown in block form in Fig. 1, can be picked out without too much trouble simply by examining the top of the chassis, with the back cover removed from the cabinet. It may be necessary to establish certain valves in terms of function and type, but this is not difficult with the help of a valve data booklet. In some cases, however, it may be necessary to remove the bottom cover from the cabinet, or slip the chassis from the cabinet in order to examine the stage continuity from underneath, but this should be avoided if possible (unless the inspection cover at the base of the cabinet may be removed easily) for the disturbance in removing an awkward chassis may introduce other faults before the original fault is found, when it is undertaken by an inexperienced operator. Nevertheless, later on in the process, it may be necessary to remove the chassis.

In most cases, it will be unnecessary fully to identify all the stages. For example, if now we go back to the fault lack of sound detailed earlier, and assume that there is no residual hum from the loudspeaker and no crackle when the volume control is turned, all we need find out first of all is the location of the loudspeaker. This, of course, is simple enough, as also is tracing the wires from the loudspeaker to the sound output transformer. At this stage the fault may be found—it may well be a wire disconnected from the speaker circuit.

Tracing in Greater Detail

On the other hand, the speaker leads may be intact. The next stage, then, would be to locate the sound output valve. Again, this should not be difficult, as the loudspeaker is connected to the output transformer and the output transformer is connected to the output valve (see Fig. 2). Moreover, we should now have some idea of the type of valve used as output.

Having located the valve, the receiver should be switched on and the heater of the valve observed. If this is alight then, at least, we know that the valve is receiving heater current and that the heater of the valve is good (two more observations as to what is *not* wrong). Now give the set time to warm up properly (five to ten minutes) and test the temperature of the valve with the hand. If the valve is taking a fairly reasonable anode current, as it should do, the temperature of the envelope will be such that the hand (or finger) cannot be held in contact for more than a couple of seconds. Take care to avoid electric shock when delving inside a television set with the power switched on. There is always a risk of shock, and this a hazard that the experimenter has to accept, but if due precautions are taken, such as ensuring in the case of A.C./D.C. type receiver that the chassis is connected to mains neutral (use a neon tester). Also take care that earthed objects, such as other electrical appliances and the like, are outside the range of contact when dealing with the inside of a "live" set, and that the hand is steered clear of E.H.T. and H.T. points.

If the valve is hot, it is passing H.T. current. If it is warm, then it is possibly being warmed up by its heater alone. If it is excessively hot, and glowing red hot internally, then there is trouble in the associated circuit. This would possibly be the case with the symptom under discussion; a red hot screen grid and no residual hum from the speaker would indicate without doubt that the output valve is running without anode voltage. The screen grid would then pass very much more current than it should and would thus become red hot.

In nine cases out of ten, lack of anode voltage here is caused by an open-circuited sound output transformer primary winding—the winding which is connected between the anode of the valve and H.T. positive. There are other possibilities, but they are somewhat remote, such as a short-circuit in a tone-correction capacitor connected between anode and chassis. Normally, however, such a capacitor is connected in series with a resistor across the primary winding of the transformer, so a short, although cutting out sound (or most of it) would not starve the anode of H.T. voltage.

Lack of H.T. Voltage

If the valve is only warm to the touch, the trouble would be caused either by a low-emission valve or by lack of current in the valve. In the latter instance, either the screen grid feed resistor or (if fitted) the main resistor supplying H.T. voltage to the output valve would be suspect.

In Fig. 3 is shown the sound output stage of the receiver under discussion, and the valves tie up with those marked in Fig. 2. It will be seen that the anode of the output valve (the pentode section of V9) connects to one terminal of the output transformer T1 and the other terminal is connected to the H.T. positive line via resistor R78. Failure of this resistor would cut off H.T. voltage, and the valve would be just warm, as described. C63A could have developed a short-circuit which would overload R78 and possibly cause it to burn out. This would be seen by inspection. R79 is the screen grid H.T. feed resistor, and would fail likewise with the same symptom should C63B develop a short. Another cause of the trouble could be open-circuiting of the bias resistor, R81. This would possibly "blow" C64, which would then have considerably higher voltage across it than its working rating provides.

To check these latter possibilities it would have been necessary to graduate from pure observation to practical servicing. However, the fault may have been discovered long before this time from observation alone. For example, the speaker wires may have become disconnected; the output trans-


former primary may have been open-circuited as indicated by the symptom of a glowing screen grid; R78 or R79 may be obviously burnt, indicating a short in C63A or C63B. At some stage in the exercise, V9 itself may have been tested in a dealer's shop on a valve tester. This would have given one more important positive or negative fact which would govern the subsequent action.

Output Stage Normal

We must now assume that the initial tests of operating the volume control and listening closely in the speaker indicated that the output stage was in order. We will suppose, therefore, that residual hum could be heard from the speaker, but that there was no apparent crackling when the volume control was operated.

This latter factor should not be rated too highly, since the volume control may be in good order and not produce crackles when turned. Nevertheless, we must be sure that the output stage and sound amplifier are working before continuing with the diagnosis, bearing in mind still that the fault must be somewhere in stages V8 and V9 (Fig. 3) as we proved in the very first place.

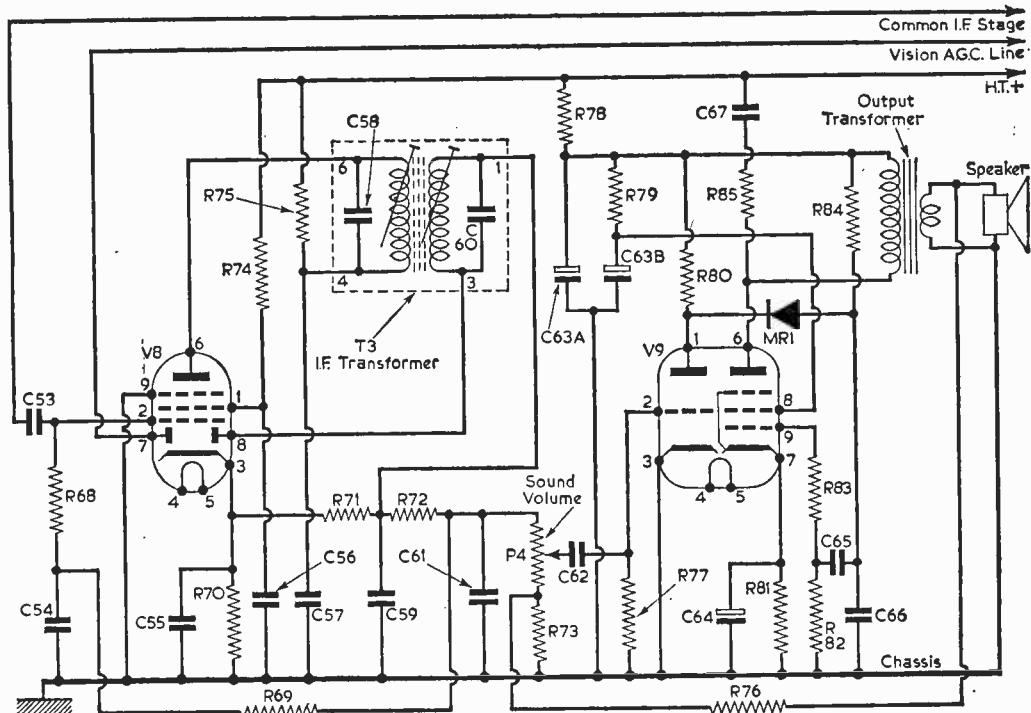It may now be necessary to remove the inspection cover from the bottom of the cabinet or, at least, gain access to the volume control itself, which may be possible without removing anything more than the back cover.



Hum Test

The volume control should be turned to maximum and, with the set switched on, the blade of a screwdriver should be brought into contact with the centre tag on the side of the control (but be sure that contact is not made with any of the tags on the mains on/off switch at the back of the control, as an electric shock or a mains short-circuit may result). If the screwdriver is being held by the insulated handle a finger should then be brought into contact with the blade. If the sound amplifier and output stages (V9 in total) are working, then a very loud hum will be heard from the loudspeaker.

If this does not happen, the screwdriver should be brought into contact with the control grid of the pentode section (pin 9—Fig. 3). If the output stage is working, which it should be in view of the build up to this stage, a lesser hum will occur from the loudspeaker.

Anode Load Resistor

If all is according to the plan; that is if hum is present at the control grid of the pentode but not at the centre tag of the volume control, the sound amplifier (triode section of V9) stage is at fault. Apart from the valve itself, the most likely and possibly only cause is open-circuit of R80, the triode anode load resistor.

Now we must assume that hum occurs at the volume control, but the symptoms still remain. The trouble must now be somewhere in the sound detector or sound I.F. amplifier stage (V8 of Fig. 3). It is unusual for much to happen to the sound detector as it does not carry H.T. power and possesses only a few components. However, if the circuit features a semiconductor diode, this is best tested by substitution before going any more deeply into the problem.

The sound I.F. valve should, as before, be observed for heater glow and tested for tempera-

ture with the fingers. This valve will not get as hot as the output valve, but should run at a fairly reasonable temperature, which after 20 seconds or so should become uncomfortable to the touch.

A valve which is only slightly warm will indicate emission failure or lack of H.T. current. The former may be proved by a valve test or substitution test, while the latter really requires a test-meter of some kind.

The H.T. voltage on the anode, screen grid and cathode should be measured. The actual voltage is not highly important at this stage, since the symptom is one of complete failure and there is bound to be a complete failure of some component or other, which would almost certainly have caused H.T. failure in the I.F. amplifier, assuming that it had been necessary to follow the exercise right through to the stage now being described.

The most likely cause would be a short-circuit in the screen decoupling capacitor, C56, resulting in R74 overloading and possibly burning out. Again, this would be seen from close examination of the associated components around the valve-holder of V8.

The complete process of logical stage-by-stage testing for the symptom of no sound (vision normal) has now been described. The exercise has been one to reduce the number of operations to a minimum by observing the behaviour of the set when the controls are operated, and then concentrating on those sections of the circuit in which the fault is most likely to be present, after first eliminating those sections which are obviously working correctly. In most cases the fault will be discovered long before the game is played right out, and in some cases the faulty part may be found by pure observation and without having to put a meter to the circuit or even take the chassis from the cabinet.

(To be continued)

Uncommon CRT faults

(Continued from page 16)

This is accomplished, of course, by injecting more current through the heater via the resistor. For instance, if an extra 50mA is required to bring the voltage back to normal, then the resistor should have a value equal to the power voltage divided by the extra current required. If the mains voltage is, say, 250, the resistor should be $250/0.05$, which is $5,000\Omega$.

The power rating of the resistor is important, since it is called upon to drop almost 250V at 0.05A, which works out to 12.5W. In practice a 15W wire-wound, component would be employed. This should be mounted in a well ventilated position so that its heat will not affect any of the other parts.

Altered Tube Characteristics

With certain reconditioned tubes and with normal tubes as they age, the characteristics sometimes differ from these of new tubes. This may show up in one of two ways: it may be found impossible to black out the screen completely by

turning down the brightness and contrast controls; or it may be found impossible to secure sufficient brightness to secure the correct contrast ratio by turning up the brightness control—resulting in a picture which is too black and white.

The former symptom would mean that the tube requires a larger negative bias on its grid for beam current cut-off than is normal. In practice a cure can usually be effected by increasing the value of the resistor connected between the brightness control and the H.T. line (R1 in Fig. 3). This makes the grid less positive at minimum brightness setting (e.g., more negative with respect to cathode).

The latter symptom would mean that the tube requires a smaller negative bias on its grid for beam current cut-off than is normal. This is best handled by introducing a resistor at the earthy end of the brightness control, as shown by R2 in Fig. 3. Sometimes resistor R2 may already be fitted. In this event, its value should be raised by about 5k to 10k to give the required range of brightness control adjustment.

FURTHER HUGE PURCHASES DIRECT FROM SOURCE

13 CHANNEL TVs

TABLE MODELS, FAMOUS MAKERS. Complete with all valves and tubes. Unequalled in value. They are unrested and not guaranteed to be in working order.

AMAZINGLY POPULAR-IDEAL SECOND SET**12" - £2.19.** (p. & p.)**14" - £4.19.** (p. & p.)**12" 5 CHANNEL TV's 39/-** (p. & p.)**14" 5 CHANNEL TV's 59/-** (p. & p.)**COMPLETE RECORD PLAYERS**

B.S.R. UAS, 4 Speed Autochanger ... 26 15 0

B.S.R. UAS, 4 Speed Autochanger Stereo

Head 26 19 0

B.S.R. UA14, 4 Speed Autochanger ... 27 19 0

B.S.R. UA20, Autochanger ... 26 19 0

Garrard 210/209 ... 24 12 6

EMI 4 Speed Single Player ... 24 12 6

P. & P. on above 4/-.

4-SPD. RECORD PLAYERS

Latest B.S.R. TU9 Turntable, together with light-weight Star Galaxy dual sapphire crystal turnover pick-up head. Truly amazing value at **£3.10.0**. Carr. 5/-

RENEW YOUR PICK-UP

with the following CARTRIDGES. ACOS G.P. 63.3, 22/6; SONOTONE 17/-; STEIG and REUTER 15/-; POWER POINT 17/- All the above complete with "STAR-GALAXY" Tone Arm, 3/- extra.

SILICONE DIODES. 125 v. 300 m.A. 2 in series make superior replacement for EM4, RMB, etc., 8/- each.

We are always pleased to answer your enquiries, S.A.E.

TUBES**DIRECT FROM OUR FACTORY**

Due to the increasing demand for our wide range of CRTs and our efficient handling methods we offer unbeatible value.

REGUNNED TUBES have new Gun Getters, Aquadac Coatings, Bases, etc.**TOP QUALITY GUARANTEED**

Carriage and Insurance 12/6
CRM192, MW22-7, MW22-14, MW22-14C,
MW22-17, MW22-18

15KPA, 16K, CRM121, CRM121A,
CRM121B, CRM123, CRM123A, MW31-14C,
MW31/18, MW31/18, MW31/74

141K, 7201A, C14FM, CRM141, CRM142,
CRM142, MW38-24, MW38-44

171K, CL7FM, CRM171, CRM172, MW43-64,
MW45-89

7401A, AW43-80, C14BFM, C17BFM, CRM151,
CRM152A, CRM152B, CRM153, CRM173,

MW42-80, MW44-1, 17ASPF
AW53-80, CRM182, MW53-80, MW53-80

AW53-80, CRM182, MW53-80, MW53-80

6 MONTHS **12 MONTHS** **18 MONTHS**
SECONDS **REGUNNED** **BRAND NEW**
£1-10 **£3** **£4**
£1-15 **£3-10**

£2 **£4** **£5**
£2-15 **£4-15** **£6**
£3-15 **£5-15**

CRM173 **MW38/44** **MW38/64**
£5

£6 **CRM173** **MW43/64**
£6

£7 **CRM173** **MW43/64**
£7

£8 **CRM173** **MW43/64**
£8

PLEASE! NOTE: Many other types not listed available. S.A.E. enquiries.

HI-FI F.M. TUNER KIT

Guaranteed Non-drift. Frequency coverage 88/100 Mc/s. Two I.F. Stages and Discriminator. Using good quality mains transformer, and valve rectifier. Size of complete tuner 8 x 6 x 5in. Price 99/-, Plus 5/- p. & p.

MAINS AMPLIFIERS

3 valve (10F3, 10P14, UIU9), 3 watt, 8 in. Loudspeaker in two tone case with controls. Ideal for record players, P.A. work, etc., 19/-, P. & P. 5/6.

RESISTORS 6/6

100 CONDENSERS 10/-
Miniature Ceramic and Silver Mica Condensers. 3 pF to 10,000 pF. LIST VALUE OVER £5.

CO-AX standard and low loss, 25yds, 12/6.
50yds., 22/8. 100yds., 42/6.
Co-ax. Plugs 1/8". Wall outlet boxes 3/6.

EY51 SHORT 4/6 U25 SHORT 8/-
ENDS 4/6 END 8/-

LOUDSPEAKERS

TOP MAKES—MANUFACTURER FRESH. 2 in. (Special) 18/-; 5in. 18/-; 8in. 19/-; 10in. 22/6;
12in. Closed Field 27/6; 6x 4 16/-;
8x 3 18/-; 8x 6 19/6; 10x 8 23/6; 8x 13 35/-;
10in. Bronze Wharfedale 89/-, P. & P. 1/6.

P.M. SPEAKERS

3 ohms, top makes performance guaranteed;
8in. 8/- 6in. 11/- 10in. 13/-
6in. 8/- 7x4 11/- 10x 6 13/-

UNIVERSAL VOLT OHM—MULTIMETER

Reads A.C. and D.C. Volts to 1000. 5 Ranges to 1000 Ohms per Volt. D.C. Current, 3 Ranges to 500 Milliamperes. Resistance reading to 200k in 2 Ranges. Complete with Probe. 59/-, P. & P. 1/6.

PORTABLE**TAPE-RECORDER CASES**

104 x 144 x 54, 14/-, 16 x 12 x 7, 20/-, 11 x 9 x 5, 10/6. Covered Attractive Bazine. P. & P. 3/-

VALVES BY RETURN OF POST**THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY**

10% DISCOUNT SPECIAL OFFER
TO PURCHASERS
of any SIX VALVES marked in black type (16%
in dozen). Post: 1 valv. 6d, 2-11, 7/-.

**NEW LOW PRICES
GUARANTEED 3 MONTHS**

FREE TRANSIT INSURANCE. All valves are new
or of fully guaranteed ex-Government or ex-equipment
origin. Satisfaction or Money back Guarantee
on goods if returned unused within 14 days.

OZ4 5/- GAL5 2/6 6J36 4/- 6X5GT 5/6 1297GT 5/- 158K 10/8 6/ECC85 7/9
LA9GT 5/- 6AM6 3/- 6J37 5/6 6T8G 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1CG5T 9/6 6AQ5 6/- 6J37 5/6 6T8G 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1D5 8/6 6AT9 6/- 6J37 5/6 6T8G 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1D6 9/6 6AB6 7/6 6J37 5/6 6T8G 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1H5GT 5/- 6AB6 7/6 6J37 5/6 6T8G 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1L5 5/- 6AB6 7/6 6J37 5/6 6T8G 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1LD3 5/6 6BA6 7/6 6J37 5/6 6T8G 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1LN5 4/6 6RE6 5/6 6K7GT 5/6 7K7 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1LN5GT 9/6 HUG9G 12/6 6L1 12/6 7Q7 5/6 20D1 5/- 6P6 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1R5 6/- 6BD6 6/- 6L6 9/6 7Q7 5/6 20D1 5/- 6P6 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1S4 6/- 6J6 6/- 6L6 9/6 7Q7 5/6 20D1 5/- 6P6 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1S5 4/6 6R7R 9/3 6L18 7/6 7Q7 5/6 20D1 5/- 6P6 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
1T4 3/6 6BW6 7/6 6L19 12/6 7Z4 7/6 20P1 5/- 6P6 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
2A3 7/6 6BW7 5/6 6L19 12/6 7Z4 7/6 20P1 5/- 6P6 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
2D121 4/6 6BX6 4/6 6L19 12/6 7Z4 7/6 20P1 5/- 6P6 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
3A4 4/6 6C5 4/6 6L20 8/6 10C14 5/6 256A 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
3186 5/- 6C5 6/6 6L20 8/6 10C14 5/6 256A 5/6 1298GT 5/- 158K 10/8 6/ECC85 8/6
3844 7/6 6C6 4/6 6P1 14/- 6L14 7/6 2518GT 5/- 158K 10/8 6/ECC85 8/6
3455GT 8/6 6C6 8/6 6P25 8/6 10LDS 7/6 2518GT 5/- 158K 10/8 6/ECC85 8/6
384 6/- 6CD6 21/- 6L12 12/6 2518GT 5/- 158K 10/8 6/ECC85 8/6
3V4 6/6 6C116 8/8 6Q7G 8/8 10P13 9/- 2525 5/- 158K 10/8 6/ECC85 8/6
5845 6/6 6D1 6/6 6Q7G 8/8 10P14 9/- 2525 5/- 158K 10/8 6/ECC85 8/6
JT4 8/9 6D2 8/6 6R7 7/6 10P18 7/6 30C1 7/6 158K 10/8 6/ECC85 8/6
3U4G 4/6 6D3 12/6 6BA7 5/6 10P18 7/6 30C1 7/6 158K 10/8 6/ECC85 8/6
5V4G 8/6 6D6 4/6 6S6 10/6 12AH7 6/6 158K 10/8 6/ECC85 8/6
5Y3G 7/6 6F6G 4/6 6S6 10/6 12AH8 6/6 158K 10/8 6/ECC85 8/6
3Y3GT 6/- 6F6G 7/6 6SK7 5/6 12AT6 7/6 158K 10/8 6/ECC85 8/6
3Y4G 11/- 6F6G 7/6 6SK7 5/6 12AT7 5/6 158K 10/8 6/ECC85 8/6
5244 6/- 6F6G 6/6 6SK7 5/6 12AT7 5/6 158K 10/8 6/ECC85 8/6
5245 6/6 6F12 6/6 6SK7 5/6 12AT7 5/6 158K 10/8 6/ECC85 8/6
5246 6/6 6F13 6/6 6SK7 5/6 12AT7 5/6 158K 10/8 6/ECC85 8/6
5247 11/- 6F13 6/6 6SK7 5/6 12AT7 5/6 158K 10/8 6/ECC85 8/6
A47 10/- 6F14 9/6 6SS7 4/6 13BE 8/6 3524GT 5/6 158K 10/8 6/ECC85 8/6
549G 9/6 6F15 9/6 6UAGT 10/6 12BHT 10/6 3524GT 5/6 158K 10/8 6/ECC85 8/6
6A8GT 12/6 6F16 8/6 6UAGT 10/6 12BHT 10/6 3524GT 5/6 158K 10/8 6/ECC85 8/6
5A8S 7/- 6F23 8/6 6V6G 5/6 12C21 10/6 3524GT 5/6 158K 10/8 6/ECC85 8/6
6ACT 4/3 6H6 2/- 6V6G 5/6 12C21 10/6 3524GT 5/6 158K 10/8 6/ECC85 8/6
6AG5 3/6 6J5 4/3 6X2 9/6 12C21 10/6 3524GT 5/6 158K 10/8 6/ECC85 8/6
6AG7 7/9 6J5 4/3 6X2 9/6 12C21 10/6 3524GT 5/6 158K 10/8 6/ECC85 8/6
6AK5 6/6 6J5 4/3 6X2 9/6 12C21 10/6 3524GT 5/6 158K 10/8 6/ECC85 8/6

Post: 2 lbs. 1/6, 4 lbs. 2/6, 7 lbs. 2/9, 15 lbs. 3/6, etc.

No C.O.D.

ALL ITEMS 5% & POST FREE IN DOZENS.

(Callers always welcome). LIST OF 1000 SNIPS £d.

P.O. BOX 21 (W)

350-352 FRATTON ROAD, PORTSMOUTH.

TECHNICAL TRADING CO.


A Precision Wobbulator

By N. Mears

(Continued from page 615 of the September issue)

THIS VERSATILE
WIDE-RANGE
INSTRUMENT
WAS DEVELOPED
AROUND
A MODERN
SEMICONDUCTOR
JUNCTION DIODE

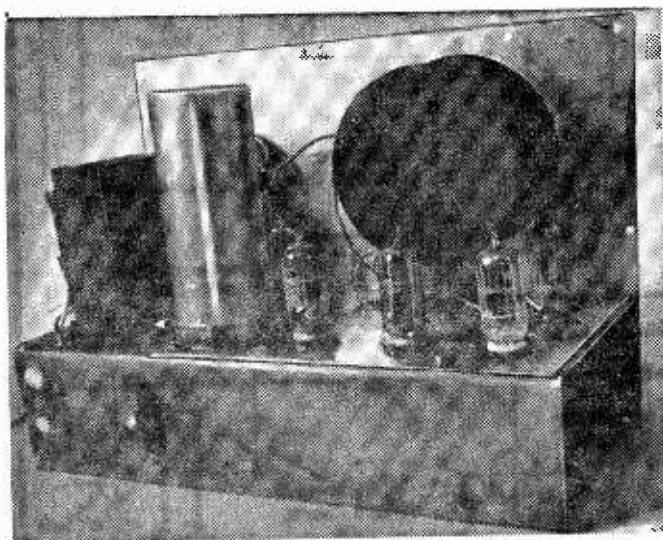JHE power supplies for the unit were not included with the main circuit (Fig. 4, last month) and are given in Fig. 7 on the next page. They are conventional in the supply of H.T., and



A rear view of the wobbulator without the cabinet. Note the oscillator screen (see Fig. 5).

6.3V A.C. at about 3A. The H.T. value of 140V may seem somewhat low, but the reason for this is that if the supply is stabilised by a neon lamp there is plenty in hand. It is essential to remove all hum from the H.T. supply—the aim should be to have not more than 0.1V ripple—and in the construction of the unit care must be taken to keep heater supplies well away from high-impedance grid points. For this reason, grid impedances are kept as low as practicable throughout. Here and there values of 2.2M have to be employed however, and these are the points at which to avoid 50c/s pick-up. Smoothing by a $200 + 200\mu\text{F}$ condenser is employed in the prototype, with a resistance of 4.7k in a 250V A.C. supply to the rectifier. A metal rectifier produces least heat in use and is recommended.

The Schmitt trigger circuits are reasonably

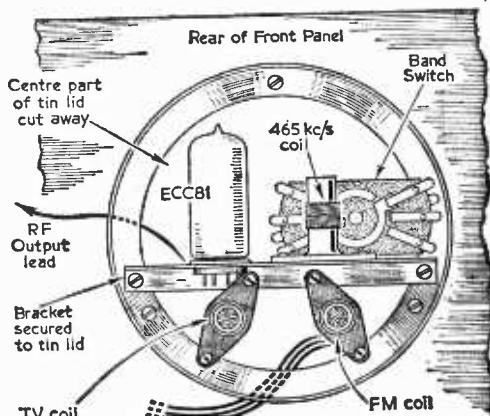


Fig. 5.—The layout inside the oscillator screening can.

stable with regard to frequency, provided stabilised H.T. is used. Multivibrators are inherently sensitive to H.T. variation, however, and if the supply is not stabilised it will be necessary to bring out the 200c/s circuit speed control to the front of the panel. There is the advantage in this in any case that the

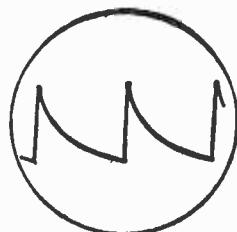
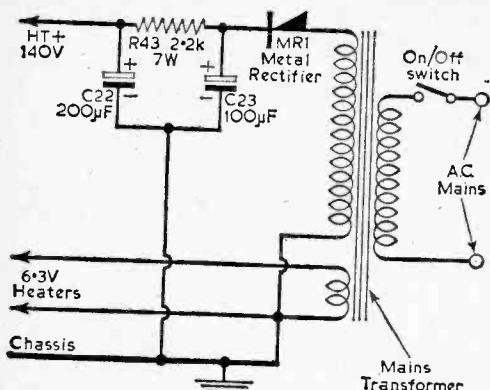


Fig. 6.—Sawtooth sweep wave.


number of markers may be varied at will from about 5 to as many as 20, if desired.

**Screening**

The oscillator section is very carefully screened. Unless the output from any kind of signal generator is to be transferred to the receiver in a rough-and-ready fashion, radiation or induction field must only be allowed to escape from the case at one point, namely the coaxial output point. Otherwise an unknown, and usually large, amount of field escapes and may find its way into the receiver at almost any point. This is no way to conduct experiments! A reader's recent letter remarking that he could receive sound ITV on the broadcast band of his set indicated that the ITV signal was leaking in very easily, only requiring H.F. parasitics in either

Fig. 7 (left).—A suitable power supply circuit.

Fig. 8 (below).—The chassis drilling details.

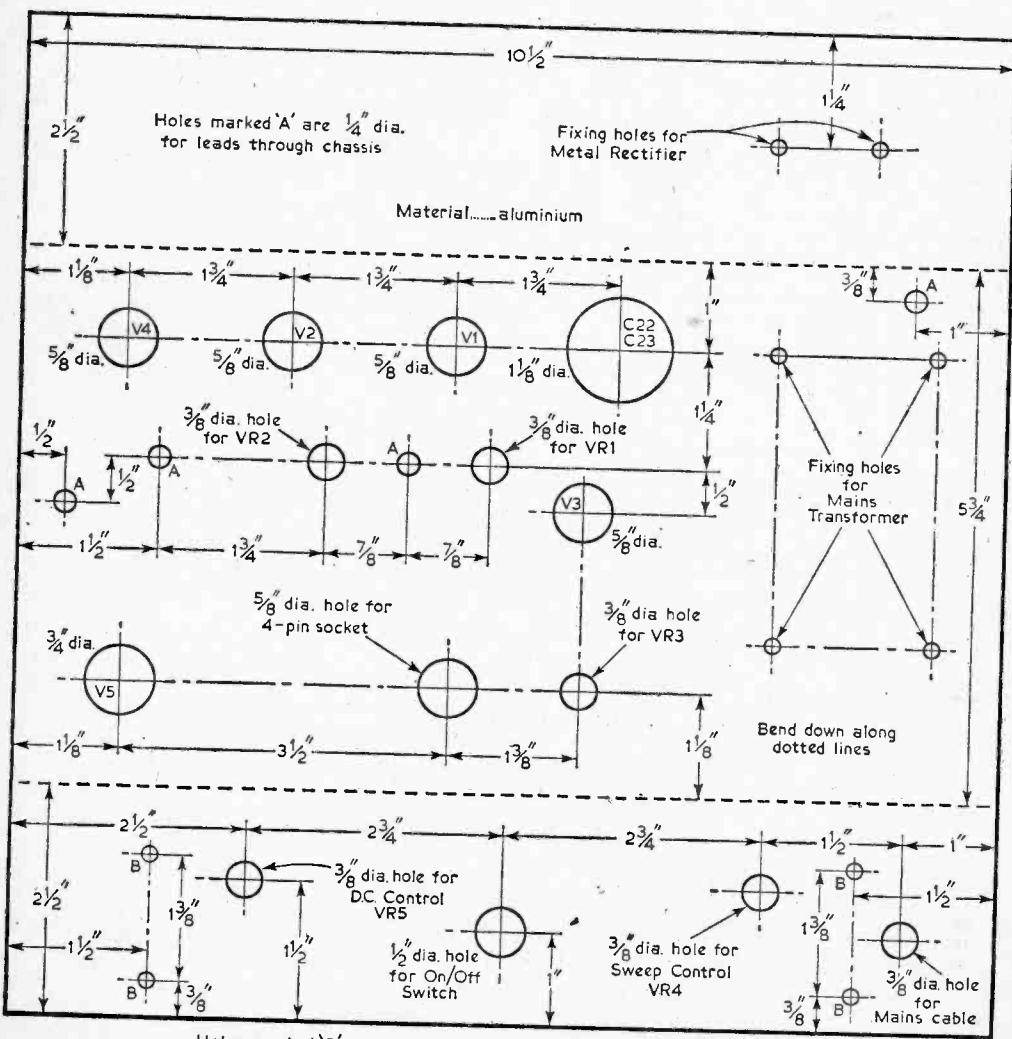

COIL WINDING DATA	
10.7 Mc/s	50 turns, tapped at 18t from the earthy end, 32s.w.g. enamelled wire; close-wound.
34-38 Mc/s	18 turns of 24s.w.g. enamelled wire; spaced by the diameter of 32s.w.g. wire (wires wound together, cemented, and when dry the 32s.w.g. winding is stripped out). It is tapped at 7 turns from the earthy end.
465 kc/s	900 turns of 42s.w.g. enamelled wire, scramble wound and tapped 200 turns from the earthy end. If this coil is too much to wind, use 400 turns of 38s.w.g. enamelled wire tapped 150 turns from the earthy end and tune to 1 Mc/s or near, so avoiding the I.F. range and injecting signal into the aerial only. This gives equally good results.

All the above coils are on $\frac{1}{2}$ in. diameter formers, fitted with iron dust cores on the 465 kc/s and 10.7 Mc/s ranges and with an iron dust core for 34-38 Mc/s or brass slug for 40-65 Mc/s range, if preferred. Harmonics of this range can be picked up in Band III, and so the overall response curve of a receiver obtained. Naturally, recalibration of the marker pulses will be needed if measurements are to be made.


R.F. oscillator or audio stages (probably the latter) to render its presence all too obvious.

Correspondingly, thorough decoupling of the oscillator within its screen is needed. Both H.T. and L.T. leads are decoupled, together with the leads carrying D.C. and sweep voltages to the SV1 diode.

In the prototype, the oscillator screening can consist of an empty cold-cream "tin" of aluminium $3\frac{1}{2}$ in. in diameter and $2\frac{1}{2}$ in. deep. A small chassis is constructed to fit into this, and on the chassis is built the complete oscillator. The lid of the tin is fixed to the front panel of the instrument, the centre portion of the tin having been cut out with a sharp penknife, and the chassis is mounted at right angles to it in such a position that, when everything is in place, the tin can be screwed into the lid. Leads are brought out between the lid and the panel—the aluminium is sufficiently ductile to permit this—and when the tin is screwed into place, the whole is firmly held and effectively screened. Slots are cut in the tin for ventilation; ideally they would be covered with wire gauze, but this has proved unnecessary since the instrument is built into a complete metal container a double screen is afforded which gives very good reduction of external field. In the prototype, the mains leads are also decoupled by means of 100-turn chokes and 2000pF capacitors; the only leakage of R.F. field is from the centre spigot of the coaxial connector and the $\frac{1}{4}$ in. trimming holes cut in the front panel.

(To be continued)

Fig. 9—The front panel drilling.

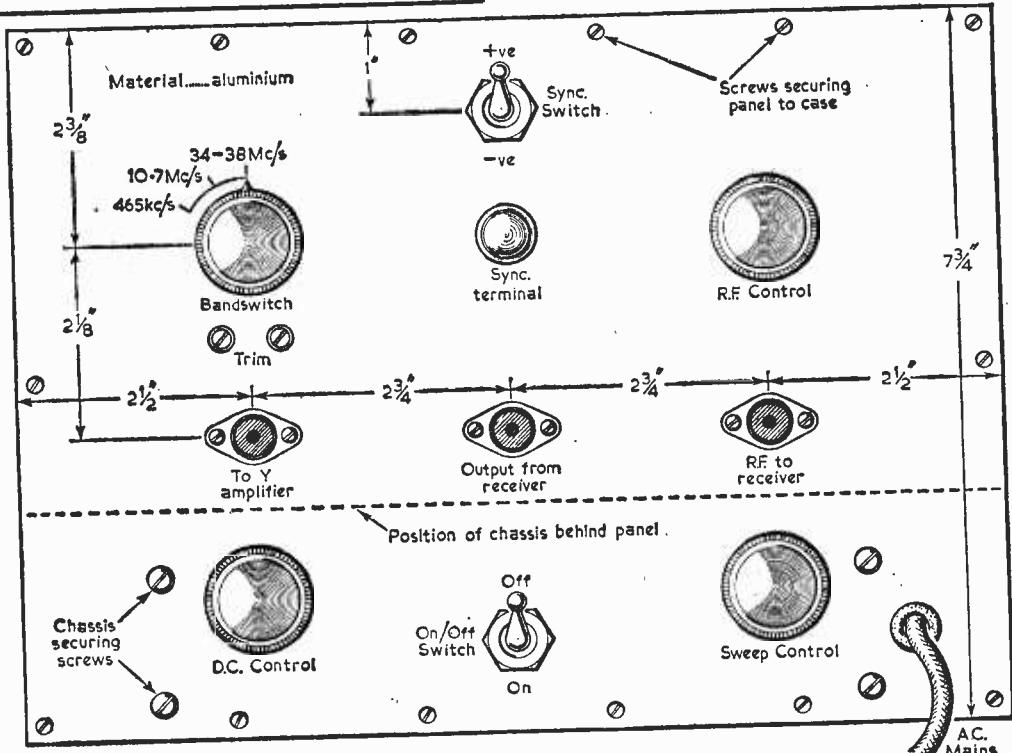

Practical Television

MULTIMETER

IN designing a multi-range meter for home construction, a number of requirements, some conflicting, have to be kept in mind. Firstly, the manufacturer not only has access to the scale of the meter, but has the technical facilities for graduating all of the several scales he will use. If the home constructor tries this he usually produces a rather unsightly job—and can seldom work to better than 5% accuracy in handmarking the scales.

Then, the home constructor is seldom able to obtain the special switches that make such a reliable job of the commercial meter. Shunts, too, present a problem, as difficult to solve as the production of a current transformer—without which the scales on A.C. measurement are necessarily non-uniform.

In the design described, the aim has been to offer an instrument which affords the best compromise for the home experimenter. Expense has been kept in mind, as has the fact that readily obtainable components have to be used.

The Meter Instrument

The instrument used as the basis of the test assembly is a Taylor, model 60, "Vista", which reads from 0 to $50\mu\text{A}$ in $0.5\mu\text{A}$ steps. With this instrument, reading to 1% accuracy is simple. Its internal resistance is about $1,300\Omega$. The actual value of resistance is quoted on the meter itself. Its internal damping is very high. This latter is actually a slight disadvantage. It can readily be shown that the most rapid reading is obtainable on an instrument which is not dead-beat but which has about 10% overshoot. This instrument reads quickly enough on voltage ranges, but current and resistance take an appreciable time to reach a steady reading. This is, however, offset by the high accuracy obtainable and—important for a portable

instrument—the needle cannot be made to swing about wildly if handled inadvertently. Thus damage is prevented and accuracy maintained.

Nomenclature

It should be noted that in this article, references are made to "A.C. current" and "D.C. current"; "A.C. voltage" and "D.C. voltage". Although these terms may appear repetitious—Alternating Current current, for example—it is felt that they are in general use and readily understood.


The Switches

Two 3-wafer rotary switches of good construction and low contact resistance are specified. For most certain results, these ought to interlock so that only one at a time can be brought into use. However, this has been rendered less essential in the present design by arranging the switching so that even if a totally incorrect combination of settings is switched, the meter remains undamaged. This does not mean, of course, that the meter cannot be damaged by careless use.

The meter instrument is so arranged in the circuit that at least one lead is disconnected whenever a switch is rotated; when shunts are in use the probability of damage to the movement is high if the meter remains in circuit while switching takes place. Of course, the careful experimenter will always disconnect a meter when changing ranges—or nearly always—but the possibility of an accident cannot be completely excluded.

To make D.C. measurements, the switch S2 is moved so that the pointer knob indicates "D.C.", while for A.C. measurements the other switch is moved to the "A.C." position. For resistance measurements the following procedure is adopted:

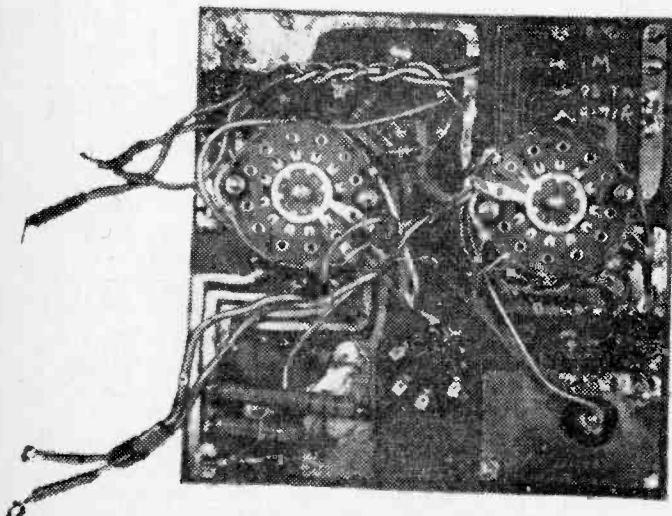- (1) set the zero-adjusting knob to the minimum position (fully anti-clockwise),
- (2) set the appropriate switch to the resistance range required,
- (3) set the other switch to "Resistance";
- (4) short-circuit the instrument leads,
- (5) adjust the meter to full-scale reading by means of the zero-adjusting knob,



View of the 'printed' side of the multimeter wiring.

METER

By D. R. Bowman

- (6) connect the leads to the component of which the resistance is required.

It should be noted that for simplicity a single adjustable shunt does duty for all three resistance ranges. It would be more fool-proof to have a separate adjustable shunt for each range, because if step (1) above were omitted and the range were changed, the meter might be much overloaded when zero is set.


Making the "Printed Circuit"

A "resist" material should be made up by dissolving 3oz of shellac in about 4oz of methylated spirit. This will take some while to dissolve, and is conveniently left overnight to complete the process. If some sealing-wax is added at the same time, or a little mahogany spirit dye, the resist solution will be found more visible when applied.

In use, this "resist" solution is used to cover the parts of the copper surface which are not to be removed during the etching process.

A water-colour brush is used to apply the solution which should be reasonably "thick" or else it may run where not desired. A steady hand is needed, and some practice is essential; this may well be carried out on a sheet of glass or paxolin. All parts which are to be conducting must be covered. These parts are shown *unshaded* in the drawings on the blueprint. The only parts not covered are those which are to be etched away.

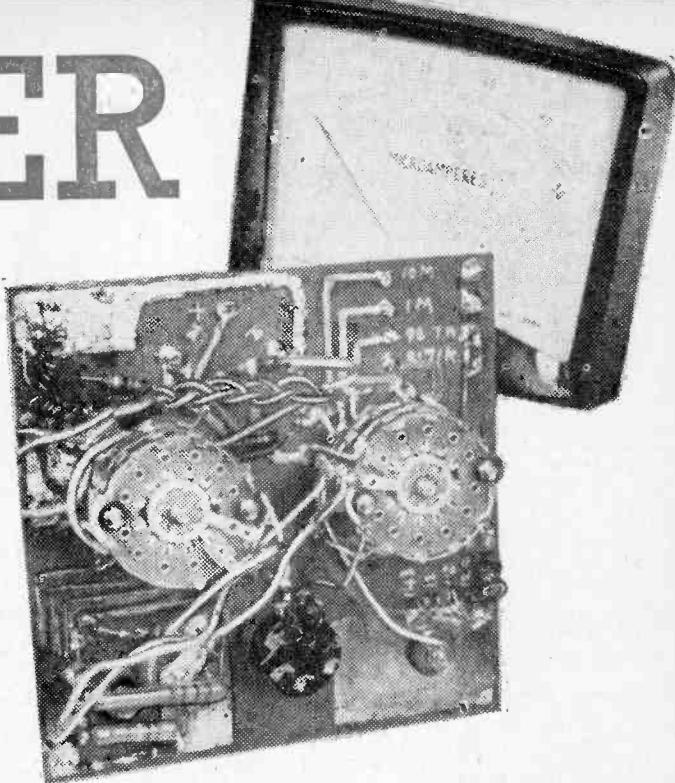Mistakes can be corrected by a plug of cotton



wool damped (not saturated) with methylated spirit; the plug should be turned frequently so that all traces of the resist are removed from the area concerned. Thorough cleaning is essential and is not easy, so mistakes are best avoided. When it is decided that all is in order, the resist coating is gone over again to thicken it. Finally, the prepared board is left overnight to dry.

A solution of ferric chloride, FeCl_3 , is made up by dissolving 4oz ferric chloride in 6oz water, adding 1oz concentrated hydrochloric acid—HCl. (Commercial "spirit of salts" is suitable.) This will form a very deep orange clear solution which is corrosive and must be kept in a well-corked, labelled bottle well out of the way of food and out of the reach of children. For use, the solution is poured into a flat container such as a photographic dish, and the laminated board immersed in it.

Etching will take a little while to accomplish; about an hour should be allowed but it may take longer, depending on the temperature. When the copper is completely removed, where required, the board should be removed from the solution, washed for a few minutes in running water, and dried with a soft cloth.

All necessary holes should now be pierced. For most holes, a $\frac{1}{8}$ -in. drill will be adequate, but where thick wires have to be anchored, a larger drill will be required. Of course, larger holes will be needed for the switches and the wires to the terminals, and where several wires will be anchored at one point, a hole of large diameter will be needed. It is not strictly necessary to drill at all points where connections have to be made; if a connection is carried through the board a hole will of course be needed.

The Ranges.

Twenty-one ranges are available as follows:

(a) Voltage	(b) Current
D.C. 0-5V	D.C. 0-50 μA
0-5V	0-500 μA
0-50V	0-5mA
0-500V	0-50mA
A.C. 0-1V	0-500mA
0-10V	0-2A
0-100V	0-10mA
0-500V	0-100mA
	0-1A
	0-1.5A
(c) Resistance	using internal batteries.
0-15k	
0-1M	
0-10M	

Construction

Although the use of the printed circuit is not absolutely essential, it is recommended as being very convenient and more reproducible than normal wiring. If not used, the meter shunts must be mounted on tag strips, and adequate insulation provided, especially at points where voltages may be high. Assuming that the printed circuit is to be used, one or two practical points need to be observed during construction.

The first is that the width of conducting strip—left after etching—must be adequate. A width of $\frac{1}{8}$ in. should be the aim, and this applies, of course, only to the main connecting conductors. The copper areas connected to the shunts (B, P and N, together with U, V, W and X, H, J, K, L and M, all shown on the blueprint) should be as specified, or as near as possible. These areas are made as large as possible for two reasons: firstly, so as to radiate heat effectively, and secondly, so as to offer as low resistance as possible. To improve the second, and so to minimise both heat developed and voltage drop, certain areas should be covered with solder. The areas concerned are H, J, K, U, V, W, B-B1-B2, and the area N-N1-N2-N3-N4. This is best carried out

by cleaning the surfaces concerned with kitchen scouring powder, *lightly*, so as not to damage the surface too much, and then laying on the surface here and there small pieces of Multicore solder—about $\frac{1}{4}$ in. long—snipped from a strand of the solder used. A hot soldering iron is then passed rapidly over the area, melting the small pieces and spreading the solder as evenly as possible. If an instrument-type soldering iron is used, some auxiliary heating—for example a gas-ring—may be needed. If this operation is carried out with moderate skill, the effect achieved is similar to dip-soldering. Care must be exercised, of course, so that excessive heating does not take place, otherwise the copper sheet may lift from the insulated board.

The Shunts

For current measurement, the shunts are made as compact as possible, and are of material best suited to the range concerned. Carbon resistors are employed for the low-current ranges, but for higher currents, Eureka resistance wire is specified. Eureka has the advantage of ease in soldering, but at the same time it has a high thermoelectric effect with copper. Thus it is essential to wait until

LIST OF COMPONENTS

- One 6in. square of copper-clad laminate (Bakelite grade DH74)
- Two 3-pole, 12-way switches; non-shorting type (Specialist Switches Ltd)
- One 5k wire-wound variable resistance
- Two insulated terminals—one red, one black (Bell and Lee)
- One 0-50 μ A meter (Taylor Electrical Instruments Ltd., "Vista" model 60)
- Four OA70 diodes (Mullard)
- Resistors (all carbon and of 1W rating except the adjusting resistors which are $\frac{1}{2}$ W, and the others as stated)
 - 1—for the D.C. voltage ranges
 - one 10M 1%
 - one 1M 1%
 - one 100k 1%
 - adjusting resistors as required (10%)
 - 2—for resistance measurement
 - one 150k 10%
 - one 15k 10%
 - one 1.5k 10%
 - 3—for D.C. current ranges
 - one $150\Omega \frac{1}{2}W$ (selected, or adjusted, to be 143Ω)
 - two $27\Omega \frac{1}{2}W$ (selected to be 26Ω each; wired in parallel)
 - one 10Ω and an adjusting series resistor to give 13Ω total
 - 4—for A.C. voltage ranges
 - one 10M 1%
 - one 1-65M (1.5M 1% with series adjusting resistor of 150k 10%)
 - one 150k 1%
 - one 11k (10k 1% with series adjusting resistor of 1k 10%)

5—for A.C. current ranges

one $33\Omega 1\%$ (or resistors in series to give the exact value)

Eureka resistance wire:

one yard of 24s.w.g.
one yard of 30s.w.g.

Shunts required:

R5	0.033Ω	Four 2-65in. lengths of 24s.w.g. Eureka in parallel
R6	0.13Ω	2-65in. of 24s.w.g. Eureka
R7	1.3Ω	8-4in. on 30s.w.g. Eureka
R8	13Ω	10 Ω carbon with 1ft 7-4in. 30s.w.g. Eureka in series
R9	143Ω	carbon
R14	0.1Ω	2-05in. 24s.w.g. Eureka
R15	0.2Ω	4-1in. 24s.w.g. Eureka
R16	3.0Ω	1ft 7-4in. 30s.w.g. Eureka
R17	33Ω	carbon

Note:—24s.w.g. Eureka has a resistivity of $0.588\Omega/\text{ft}$.
30s.w.g. Eureka has a resistivity of $1.859\Omega/\text{ft}$.

From the above, resistance wire lengths can be calculated for any series adjusting resistor needed—for example, R8 can be made up of a 12Ω carbon resistor with a series adjusting resistor of 6-5in. of 30s.w.g. Eureka.

All the above lengths of resistance wire are the lengths of effective wire between the wrapped and soldered ends. The actual wire cut should be $\frac{1}{2}$ in. longer before preparation, and, if the shunts are to be adjusted *in situ*, 1in. longer than the above.

complete cooling has taken place, after soldering, before any adjustments are made to shunts; otherwise misleading deflections of the meter will vitiate the results. Manganin is on the whole a better material, but it has to be hard-soldered.

After the shunts have been made and secured to the printed circuit board, they should be coated liberally with shellac varnish to protect them from atmospheric oxidation.

The shunts are prepared as follows. The exact length should be exceeded by $\frac{1}{4}$ in. at each end, and the ends cleaned up by very light and careful sandpapering. Then some tinned copper wire is wrapped round the cleaned end so as to leave the precise length of resistance wire between. The gauge of wrapping wire should be appropriate to that of the resistance wire—the same or a size or two smaller will do well. When this has been done the copper wrapping, and the resistance wire on which it has been wound are soldered together. Care must be taken that solder does not intrude on the resistance wire between the two ends. Fig. 1 shows the procedure. When carried out carefully, this procedure can give correct resistance to better than 2% accuracy by measurement of length alone, using standard gauges of resistance wire. When soldering these shunts into position care is needed to ensure that the conditions are not altered.

Wire Gauge

In order to cater for reasonably accurate measurement of length, the actual length of wire used must not be too short. This means that a reasonably small gauge of wire is needed. For the highest direct current range, four lengths of wire in parallel are employed; thus the shunt is not too small physically and its current-carrying capacity is improved.


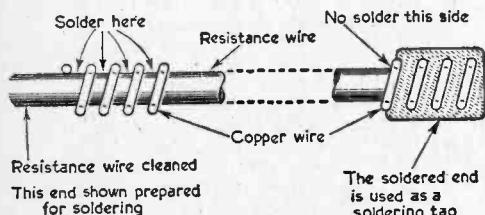


Fig. 1.—Preparation of the shunts: tinned copper wire is wrapped round the cleaned ends of the wires so as to leave the precise length of resistance wire effectively in circuit. (The text describing this operation is above.)

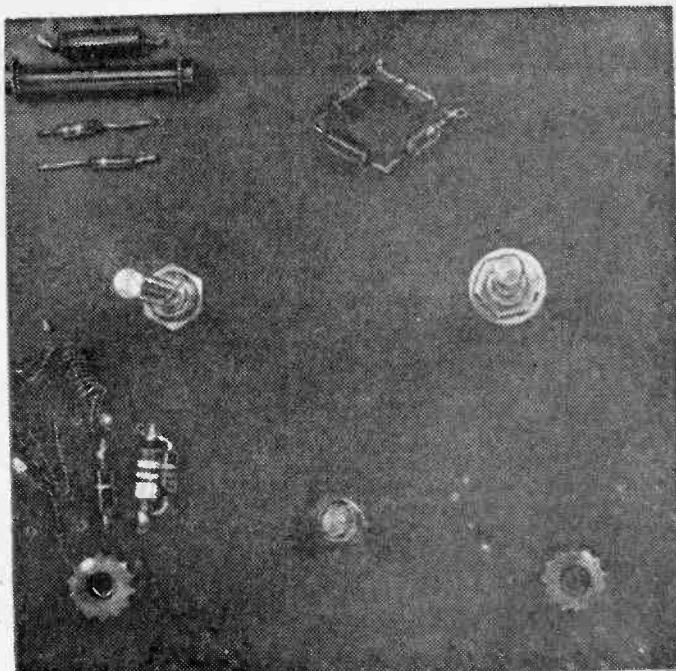

The rear of the printed panel—the bridge rectifier can clearly be seen together with several resistors.

For lengths of resistance wire exceeding four or five inches, it is useful if non-inductive winding is arranged. It is not essential in this meter, but if it is intended to adjust shunts *in situ* for purposes of calibration the non-inductive winding has advantages. All that is necessary is to fold the length of bare wire in half, first coating all but the centre inch with shellac varnish, and wind the shunt on the shank of a $\frac{1}{8}$ in. drill as a temporary former. The shunt adjustment can then be carried out on the unvarnished centre inch of wire, which now conveniently protrudes at the end of the shunt remote from the circuit board.

Adjustment

Adjustment of the shunt is then carried out as follows. First lightly clean the adjustment loop with sandpaper, having cut the shunt wire about $\frac{1}{4}$ in. longer than the specified length. Then, passing a known current through the instrument, slowly but very firmly twist the wires together until the correct reading is nearly but not quite achieved. Next solder the twisted portion, observing the meter reading. If not quite accurate, twist a very little more and again solder. Repeat as necessary. If this is done carefully a precise calibration can be obtained. The reader is reminded of the need to avoid thermoelectric effects.

The shunts specified for this instrument relate to the particular meter used in development, and if a meter with an internal resistance differing from $1,290\Omega$ is employed, slight variations will be needed. As an alternative, the meter resistance may be made up to, say, $1,500\Omega$ by a suitable length of Eureka

wire, and shunts calculated accordingly. Unfortunately, the switch contacts also have resistance which is part of the shunt; practical values of switch resistance have been taken into account in designing the circuitry, and good accuracy should be obtained without shunt adjustment on the lower current ranges, but on the higher ranges adjustment is strongly advised.

Series Resistors (D.C. Ranges)

The tolerance of the resistors for the series multipliers should be 1%. This is actually practicable only for the resistors of higher value — 10M down to 100k; with these, the resistance of the meter movement can be neglected compared with the series resistance. However, for the lower values of series resistor it is necessary to choose such a value that the total resistance, including that of the meter movement, is of the required amount. It is actually preferable to correct the 100k resistor in this way.

The prototype meter movement had an internal resistance of 1,290Ω. Thus, the 100k total series resistance, for reading 0-5V D.C., had to be reduced to 98.7k approximately. In the prototype, this value was selected from stock, but an equally good way would be to shunt the 100k 1% resistor with 7.6M, made up of two 10% resistors in series perhaps. The fact that the adjusting resistor is so much larger in value than 100k means that its "accuracy" can be a good deal worse than 1% without introducing appreciable error. Similarly the resistor R4 (the 0—0.5V D.C. multiplier) must be 8.71k; in the prototype, a resistor of the correct value was selected from the 8.2k stock. A 10k 1% resistor could just as well be shunted by a 680k 10% resistor.

Calculation

If a meter differing from 1,290Ω in resistance is supplied, the formula for calculating the adjusting resistor (RA) is

$$RA = \frac{RS \times [RS - RM]}{RM}$$

where RS is the total series resistance required and RM is the resistance of the meter movement. Thus if RS = 100k and RM = 1,290Ω,


$$RA = \frac{100,000 \times [100,000 - 1,290]}{1,290}$$

$$= 7.6M.$$

Thus, if a 100k 1% resistor were used for the multiplier on the 0—5V D.C. range, with a meter resistance of 1,290Ω, a 7.6M 10% could be connected in parallel to obtain the correct series resistance (as was quoted above).

A.C. Ranges

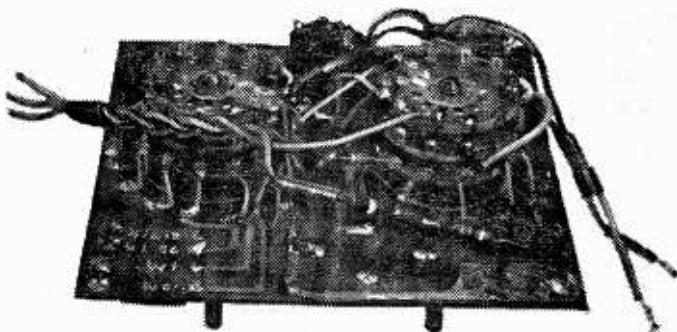A large increase of diode resistance when the impressed voltage is small is characteristic of all semi-conductor diodes—including the copper oxide rectifier. Consequently the scale readings on A.C. do not correspond with those on D.C., and the scale is non-linear. This disadvantage can be overcome to a large extent by reducing the meter sensitivity



Another view of the multimeter.

from, say, 20,000Ω/V to about 1,000Ω/V, so requiring a much larger current from the rectifying unit. Also, by the use of transformers, a more constant voltage can be offered to the rectifiers at the expense of reduced frequency range. Other devices can be used to improve scale linearity as well as constancy of scale "law" for different voltage and current ranges.

R.F. Tests

This instrument, however, is designed to offer as little difficulty as possible to the amateur, and it is also arranged so that comparisons at R.F. can be made—a valuable feature not met with in some quite expensive instruments. Consequently the simple device of a "universal" shunt on alternating current ranges has been employed. This does not improve the linearity of the scale but preserves the scale "law" for the different current ranges.

Alternating voltages, except the lowest, require the same scale law. The lowest range requires a modified scale, because the series resistance is not very large compared with the meter resistance plus rectifier resistance.

The printed scales to be given next month will be found accurate on A.C. ranges to about 5%, provided full scale reading is adjusted to be correct. Voltage readings, using the proper value of series multiplier, will be equally accurate without such adjustment. With current ranges, however, accuracy depends also on the resistance of switch contacts so that for the higher current ranges (50mA and over) this needs to be taken into account. Consequently, for the higher current ranges (on both A.C. and D.C.) scales are only correct if the full-scale reading is adjusted to be correct.

Calibration

Provided 1% tolerance resistors are employed, or accurate values selected from stock, calibration on the D.C. voltage ranges is unnecessary. Calibration of the D.C. current ranges presents only the minor problem of shunt adjustment, already described. Assuming a standard instrument can be borrowed, the technique is merely to pass the same current through both instruments; adjust the current—which is best provided by an accumulator—by means of a rheostat of suitable value, and adjust the shunt to obtain the correct full-scale reading.

(Continued on page 51)

**Examine it
FREE
on 7 DAYS'
APPROVAL**

RADIO, TELEVISION & ELECTRICAL REPAIRS

AMAZING 'KNOW HOW' BOOK *Saves You Pounds*


Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install lighting points, or repair any domestic appliance, from a bell or an iron to a vacuum cleaner or washing machine. Explains basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults, carry out maintenance and repairs by the most modern methods. Special section on frequency modulated receivers. See this great volume NOW on 7 days' FREE TRIAL. Yours (if kept) for 21/- (Standard Edition) or 23/- (De Luxe, leathercloth). Or on Easy Terms: 5/- down, and 3 monthly payments (total credit prices: Stnd. 22/-; De Luxe 24/-).

ESSENTIAL TO EVERY SERVICE ENGINEER, ENTHUSIAST AND HANDYMAN !

Getting the best from RADIO AND TV SETS

Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set.

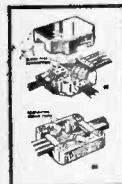All you need to know about DOMESTIC WIRING



Learn from these helpful pages how to carry out all kinds of installations and extensions—with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.

BASIC RADIO CIRCUITS

All you want to know about circuits, so that you can find your way around modern sets without hesitation. How components form various types of set; gives circuits for 1-valve receiver, 3-valve receiver, battery TRF receiver 4-valve superhet, Universal sets, etc.


See how to maintain

Vacuum Cleaners
and Floor Polishers,
Refrigerators, Cookers
and Boiling Plates,
Washing Machines, etc.

Do your own

BATTERY CHARGING

Here are clear, complete instructions.

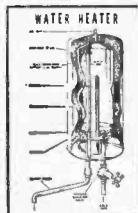

FIRES & SPACE HEATERS

Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!

TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from how to carry out Preliminary Tests to how to align R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the causes of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loudspeakers and how to deal with any faults that may develop.



DISCRETE SEPARATE OF THE HAND CLAMP



**480
PAGES
OVER
400
ILLUSTRATIONS**

ALL THIS—AND MORE IN ONE GREAT VOLUME!

Comprehensive Contents Include

Current, Voltage and Resistance. Coils, Capacitors and Valves. Basic Radio-receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers. Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-Amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging, Testing and Repairs, etc.

DO THIS NOW!

Fill in form and post in 2d. stamped, unsealed envelope to Dept. H.F.35, Odhams Press Ltd., Basted, Sevenoaks, Kent. Book comes to you on FREE APPROVAL; if satisfied you send remittance, otherwise return book in 8 days. Approval offer applies in U.K. only, closes October 31. Eire customers please remit full cash with order.

POST FORM TODAY!

To: Dept. H.F.35, Odhams Press Ltd., Basted, Sevenoaks, Kent.

Without obligation to purchase, please send me "Radio, Television and Electrical Repairs" in Edition indicated. Within 8 days I will either return book in good condition, postage paid, OR remit full cash price. Alternatively, I will send correct down payment as detailed in advertisement. Cross out Edition NOT wanted: STANDARD/DE LUXE. Delete words NOT applicable. I wish to pay CASH/BY TERMS. I am (a) homeowner (b) tenant in house or flat (c) temporary resident (d) single (e) married (f) over 21 (g) under 21. Signature _____

(If under 21, signature of parent or guardian)

BLOCK LETTERS BELOW

NAME _____

Full Postal _____

ADDRESS _____

H.F.35/Oct. 1961

PC97 Beam Triode

(from "Mullard Outlook," August 1961 issue)

A NEW VALVE FOR TV TUNERS

THE PC97 is a new frame-grid triode intended for use as an R.F. amplifier in television tuners. The use of a single triode in place of the usual double-triode cascode stage has the advantages of reduced cost and simpler circuitry. It is therefore likely to be encountered in future receivers.

The noise factor of a PC97 R.F. stage is of the same order as a PCC89 cascode stage. The gain however will be somewhat less than for a triode used in a cascode arrangement, but in television tuners high gain is not always an advantage, and it may be more satisfactory to increase the I.F. sensitivity of the receiver by using the frame-grid pentodes EF183 and EF184.

A frame-grid construction in the PC97 enables a mutual conductance of 13mA/V to be obtained at an anode current of 11mA . The PC97 is designed for an anode potential of 135V , which enables the high slope to be achieved but only at the expense of cross-modulation. However, by operating the valve from a 200V line with a suitable series resistor, the cross-modulation curve is improved and the valve will handle signals of up to 100mV quite satisfactorily.

Beam Triode

In the U.S.A., where the use of the cascode stage is not as popular as in the U.K., triodes and tetrodes are commonly used in the R.F. stage of VHF tuners. The triode is inherently less noisy than the tetrode, but has the disadvantage of a high value of anode-to-grid capacitance. The advent of a beam triode, however, has offset this disadvantage to a large degree, and has thus made a single triode stage an attractive alternative to the cascode arrangement of a double triode.

In a conventional valve the grid support rods are the main contributing factors to the anode-to-grid capacitance. The method employed to reduce this anode-to-grid capacitance in the PC97 beam triode is illustrated in Fig. 1. The anode is formed by two plates specially shaped so that only the "active" areas are close to the grid. A shield is placed between each support rod and the anode and these, together with the action of the anode, divide the electron stream into two main beams. The plates forming the shield are brought out to a separate base pin which is normally earthed. Two cathode pins and a special arrangement of the cathode leads also give improved input damping.

By the above means an anode-to-grid capacitance of the order of 0.5pF , has been achieved which may be compared with 1.5pF for a typical R.F. triode. This low anode-to-grid capacitance simplifies the problem of neutralising.

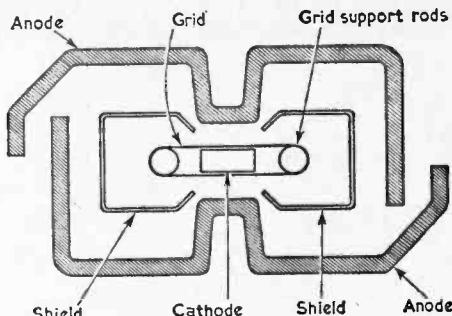


Fig. 1.—Cross-section of the PC97.

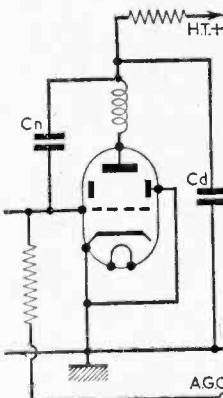


Fig. 2.—
Theoretical
neutralising
circuit.

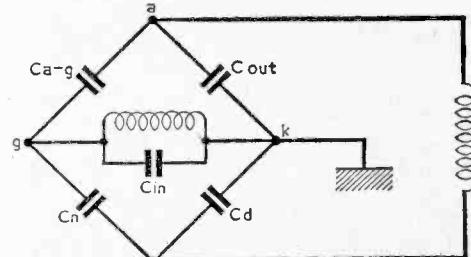


Fig. 3.—The bridge neutralising circuit.

Neutralisation in VHF Tuners

In a VHF tuner the anode-to-grid capacitance provides a feedback path from the output to the input.

The phase relationship of the voltage feedback is such that it causes the input signal to be reduced, thus affecting the selectivity of the tuner. It also produces phase distortion of the signal. This feedback can be neutralised by introducing another voltage equal to the instantaneous value of the anode-to-grid voltage, but 180° out of phase with it.

The neutralising voltage may be developed across a capacitance C_n , which is usually connected between the anode and grid to form one arm of a bridge network. The anode-to-grid capacitance Ca-g makes up the adjacent arm. The

remaining two arms of the bridge include the output capacitance C_{out} of the valve, and a capacitance C_d connected between the H.T. end of the anode load and the cathode of the valve (Fig. 2). The neutralising bridge network for this circuit is shown in Fig. 3.

When the bridge is at balance there is no current flowing in the centre arm. For the bridge to stay in a balanced condition the alternating potential at the point "g" must always be equal to the alternating potential at the point "k". Therefore, under this condition the voltage across the neutralising capacitor will always be equal to the anode-to-grid voltage.

Hence if the capacitance of the neutralising capacitor is chosen so that the bridge is balanced, then the network will be correctly neutralised. The only voltage developed across the centre arm (that is between the grid and the negative H.T. line) will be the input signal. There will be no phase distortion caused through anode-to-grid feedback and no reduction of the input signal.

Neutralising the PC97

There are numerous types of neutralising bridge network and one especially suited to the PC97 is shown in Fig. 4. This neutralising circuit utilises the capacitance between the beam plates and the grid, and has the advantage that one side of the neutralising capacitor is earthed. The input capacitance of the valve should not be included in the ratio arms of the neutralising bridge. This capacitance varies with the anode current, and therefore if AGC is applied the stage will not be correctly neutralised. The inductance of C_d must be

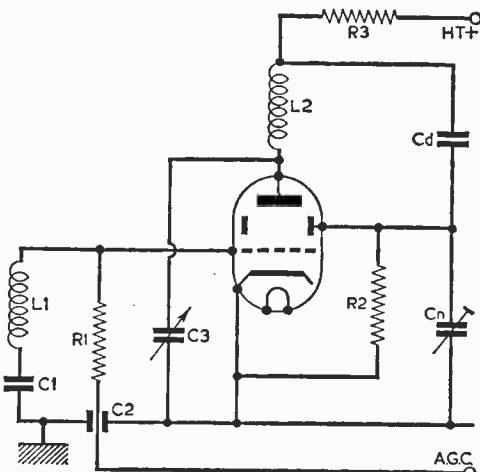


Fig. 4.—The form of a practical circuit for the PC97.

extremely low as complete neutralising can only be achieved if the capacitor is purely capacitive.

One important feature of the circuit in Fig. 4 is that the value of neutralising capacitance will be small. This is a direct consequence of the low anode-to-grid capacitance of the PC97, the special construction of which makes the valve very suitable for VHF applications.

Servicing Television Receivers

(Continued from page 11)

Correct width is obtained when the sleeve is withdrawn far enough from the scanning coils to permit about $\frac{1}{2}$ in. overlap at each side of the picture. The line linearity should be correct at this point. If the sleeve is pushed in too far it will cause not only lack of width but also overheating of the scanning coils. The sleeve is about correct when $\frac{1}{2}$ in. is protruding. If the sleeve has not been altered, check the line timebase valves V12, V13 and V14 and R69.

Loss of Line Hold

This is nearly always due to loss of emission in V12 (ECC82) but on occasions it may be necessary to check associated circuitry (perhaps V13 and R69).

Fuse Blowing Immediately upon Switching On

Check C25, and for signs of flash-over in between the metal rectifier plates. If the fuses blow as the set warms up check the PY81 and if this becomes red-hot prior to the fuse failing, check C65. Check the PY81 for internal shorts.

Frame Distortion

If the top or bottom of the picture is compressed, check the setting of R53 (adjusted through printed

panel, Fig 1—vert. Lin). If this does not help, check V11 (PCL82) and R52 (820k). If the picture is also dark, check C67 for leakage.

Frame Hold

Check V12, R48 and R51 if the hold control is over one way and the picture continues to roll. If the sync is poor and the frame can be made to roll in either direction, but will not lock securely, check R63.

Oscillator Tuning

Maximum sound on whichever channel is selected should occur at approximately the mid position of the fine tuner. Should this position change it may be necessary to retune the relevant oscillator coil core. The position of the cores is shown in Fig. 8 and these are accessible when the station selector and fine tuner knobs are removed. Care must be exercised when tuning and the use of a larger tool than required can result in damage particularly to the Band I coil which easily becomes loose, thus leading to persistent oscillator drift. If the coil or core is loose, the chassis should be removed and the coil and core secured by adhesive or wax.

now!


YOU can MASTER ELECTRONICS!

**BRITAIN'S MOST COMPREHENSIVE
PRACTICAL COURSE
IN RADIO • ELECTRONICS
TELEVISION!**


**THESE SPECIAL TRAINING
KITS — YOURS TO KEEP**



Multi-Range
TEST METER

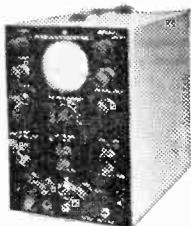

CATHODE RAY
OSCILLOSCOPE

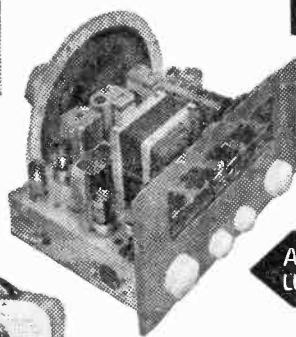

AM and VHF/FM
LUXURY RECEIVER



SIGNAL GENERATOR




Complete set of
Picture Way books and
Experimental Manuals

**LEARN BY BUILDING
NOW for your
CAREER • HOBBY
OWN BUSINESS**

YOU RECEIVE

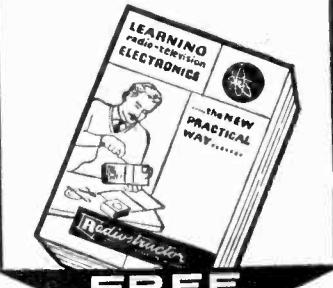- Complete kits of equipment as illustrated.
- Complete set of experimental manuals.
- Complete set of "picture-way" theory books.
- Modern test-yourself examination sheets.
- Study programme.
- Unlimited consultation with Tutors.



**FREE
BROCHURE
POST
NOW**

RADIOSTRUCTOR

TO RADIOSTRUCTOR (DEPT. M102)
READING, BERKS.

Name _____ BLOCK _____

Address _____ CAPS _____

PLEASE

(We do not employ representatives) 10/61

ALPHA RADIO SUPPLY CO.

MULLARD TRANSISTORS

OC19	48/-	OC72	8/-	OC78D	8/-
OC35	25/6	OC72p	16/-	OC81	8/-
OC44	11/-	OC73	16/-	OC84	11/-
OC45	10/-	OC75	8/-	OC170	13/6
OC70	6/6	OC77	10/-	OC171	14/6
OC71	6/6	OC78	8/-	OC202	36/-

A SPECIAL OFFER OF SIX MULLARD TRANSISTORS

I OC42, 2 OC45, 1 OC81D, 2 OC81.
Only 37/- set.

EDISON TRANSISTORS

XAI04 12/-, XAI03 10/-, XAI02 6/6 ea.

LOUDSPEAKER UNITS

All Brand New

2½in. square Rola C25	26/10
2½in. square EMI	18/6
4in. square Elac Tweeter	12/6
5in. round Plessey with O.P.T.	16/6
6½in. round Celestion	17/6
8in. round Richard Allen	18/6
10in. round Elac	25/-
12in. round Plessey	29/6
6in. x 4in. Plessey	19/6
7in. x 4in. Plessey	19/6
8in. x 5in. Celestion and Richard Allen	19/11
10in. x 6in. Celestion and Plessey	22/6

ALPHA RADIO TERMS.—Cash with or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 1/8; 20/- add 1/9; 40/- add 2/6; 25 add 3/8. Minimum C.O.D. Fee and Postage 3/- For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

ALPHA FOR VALVES AND SPARES FROM STOCK

VALVES BY RETURN POST

AZ1	10/-	EF91	5/9	PCL82	11/6
DF96	8/-	EF92	6/-	PCL84	13/6
DAF96	8/-	EL41	9/-	PL36	13/6
DK96	8/-	EL84	9/-	PL81	11/-
DL96	8/-	EL91	4/6	PL82	8/6
EABC80	9/-	EM80	9/-	PL84	12/7
EAF42	9/-	EM81	10/6	PLX25	12/6
EBC41	8/9	EY51	9/6	PY32	15/6
EBF80	9/-	EY86	10/-	PY80	8/6
EBF89	9/-	EZ40	7/6	PY81	8/6
ECC81	8/-	EZ80	7/-	PY82	7/-
ECC82	7/6	EZ81	7/-	U25	13/6
ECC83	9/-	FC13	5/-	UAF42	9/6
ECC84	10/-	GZ32	11/6	UBC81	11/4
ECC85	9/6	HL42DD		UCB81	11/11
ECF80	12/-			UH42	9/6
ECF82	10/6	OZ4	4/6	UCL82	11/6
ECH42	9/6	PCC83	13/6	UCL83	16/-
ECH81	9/-	PCC84	8/6	UF85	9/-
ECL80	9/6	PCC85	11/6	UL41	9/-
ECL82	10/6	PCF80	8/9	UY41	6/6
EF50	5/-	PCF82	11/6	3D6	5/-
EF86	12/6				

Hi-Fi Transistor FM Tuner for the Home Constructor, complete kit £18/18/- Fully illustrated booklet with diagrams, full shopping list etc. 3/6.

LOUDSPEAKER CABINETS

Type suitable for an 8in. unit. 21/-
Type suitable for a 10in. unit. 25/6
Type suitable for a 7 x 4in. unit. 17/6

CATALOGUE

OUR 1962 CATALOGUE IS NOW AVAILABLE. PLEASE SEND 1/- IN STAMPS FOR YOUR COPY. TRADE CATALOGUE ALSO AVAILABLE, FOR WHICH PLEASE ATTACH YOUR BUSINESS LETTER HEADING.

CRYSTAL CALIBRATOR No. 10

Crystal controlled. Directly calibrated. Functions: Crystal controlled oscillator providing fixed frequency signals of 500 kcs and all harmonics of 500 kcs up to 30 mcs variable oscillator from 250 kcs—500 kcs, enabling all intermediate frequency between 250 kcs to 500 kcs to be produced and modulated. Complete in carrying case/bag with all valves, leads and instruction book. £4/10/- each.

103 LEEDS TERRACE,
WINTOUN STREET, LEEDS 7.

VACUUM
ELECTRONIC
LIMITED

KEEPS YOU IN THE PICTURE

WITH THE
FINEST REBUILT CATHODE RAY TUBES

12 MONTHS
GUARANTEE

12"-14" £4·15·0

15"-17" £5·5·0

21" £7·15·0

CASH WITH ORDER OR
PRO FORMA, ADD 12·6 FOR
CARRIAGE AND INSURANCE.

15/-

ALLOWED
ON RECEIPT
OF OLD
TUBE

DELIVERY FREE IN LONDON AREA

WRITE PHONE OR CALL
VACUUM ELECTRONIC LTD.

35. SACKVILLE STREET
LONDON, W.1
REGENT 6404

AERIALS

BAND I BAND II BAND III

Combined Arrays I and III
1+3 Element Loft Mounting .. 38/3
1+5 Element Loft Mounting .. 46/9
1+3 Element Wall Mounting .. 45/3
1+5 Element Wall Mounting .. 61/9
1+3 Element Chimney M'ting .. 57/10
1+5 Element Chimney M'ting .. 66/9

Band I

Single Dipole Wall Mounting .. 24/7
Single Dipole Chimney M'ting .. 40/2
X Aerial Chimney Mounting .. 62/3
H Aerial Chimney Mounting .. 67/7

Band III

3 Element Yagi Wall Mounting .. 33/-
6 Element Yagi Wall Mounting .. 43/-
9 Element Yagi Wall Mounting .. 56/-
Chimney Lashing Mounting add 10/-
Double 6 Array, only with clamp 83/-

Band II

Single Dipole Wall Mounting .. 20/5
Single Dipole Chimney M'ting .. 29/9
H Array Chimney Mounting .. 52/4

REPAIR KITS

Band III Folded Dipole With Insulator, Complete .. 9/3
Band I Insulator With Two 4 inch Dipoles For 1 or
4 inch Booms, Complete .. 19/5
6 inch Lashing Kit, 12/11, 7½ inch Lashing Kit .. 14/8
6 inch Wall Bracket With U Bolts .. 14/8
1-4, 1-1 inch Clamps, 3/10, 1-2 inch Clamps Universal .. 5/4
Bracket Repair Kit, J Bolts; U Bolts; 20ft Lashing
Wire; Thimbles; Corner Plates .. 6/-
Insulator, All Types .. (Enquire)
Co-Ax Semi Air Spaced, 7d. yd. .. Plugs 1/2
Send 6d. for Lists. Please state Channel when ordering.
Cash with Order. Post and Packing 3/- extra.

SATISFACTION OR MONEY BACK GUARANTEE

WALKER & SQUIRES

PINNOX STREET, TUNSTALL, STOKE-ON-TRENT

Phone: Stoke-on-Trent 88767

Underneath the Dipole

A MONTHLY
COMMENTARY

By Ikonos

WHEN I heard that Granada was going to put on "The Dumb Waiter", another play by that much-praised playwright, Harold Pinter, I made a special note not to miss it. Granada TV plays for "Television Playhouse" are always presented in the most polished and professional manner and invariably strike a new note. Here was a play that was commended by some of the theatre critics when produced on the live stage last year; a play with a reputation for building up tension, having you sitting breathless on the edge of your seat as the drama proceeded between two professional gunmen awaiting their next assignment.

Alas! If the Pinter stage play had tension and the kind of macabre atmosphere one expects of an Alfred Hitchcock thriller, these qualities were missing in its television form. The gunmen in the basement argue about irrelevances and talk inconsequently as they wait, interrupted from time to time by a noisy dumb-waiter lift which arrives with written messages or by the whistle from an adjacent speaking tube, through which verbal instructions (unheard by viewers) are given. That was all. For the ordinary viewer who is possibly a bit of a "square" so far as *avant garde* plays are concerned, it meant very little. By the time the sudden climax arrived at the end, few of them, including me, cared anyway. It seemed a pity that the good acting of Roddy McMillan and Kenneth J. Warren as the gunmen, and the fine production values of sets by Stanley Mills and direction by Paul Almond, should be expended upon such a peculiar and puzzling script.

Video Tape

Like nearly all TV plays these days on both BC and ITV, "The Dumb Waiter" was recorded on magnetic video tape. There must


be over a hundred of these machines installed in television studios and centres in various parts of Britain alone. This must represent a capital investment of over £2,000,000 upon which no import duty is payable, because magnetic television tape recorders have not been made in Britain since the BBC's original and ingenious (but not very practical) Vera tape recorder was abandoned. The video tape machines now in use here are mainly manufactured by Ampex, though recently a number of tape machines by R.C.A. have been imported from America and are proving highly satisfactory.

Outwardly, the main difference between the R.C.A. and Ampex equipment is that the current models of the former are rack mounted, while the latter make favours the console. Both systems work to the same standards, however, allowing tape recorded on either make to be played off on the other. A Japanese television

tape recorder which has proved highly successful, is non-compatible with either of the American machines, since the scanning is on an entirely different concept and in certain respects is said to be an improvement. However, newer models of the rival American makes are coming along in different shapes and with numerous refinements which will make the existing equipments look a bit old-fashioned! I hate to think of the high annual depreciation percentage the television accountants have to deduct from the capital asset value of these tape recorders!

Long-Life Magnetic Heads

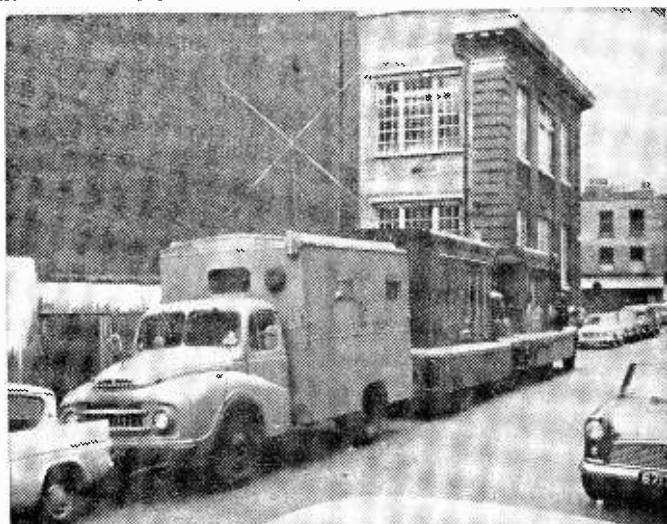One of the biggest headaches of the video tape operation is the short life of the magnetic head assembly, which wears rapidly and requires renewal after about 200 hours use (or less). Ampex have brought out a new type ferrite head equipment which, it is claimed, will last ten times as



So much electricity was used by television and radio receivers and other electrical appliances at the New Horticultural Hall, Westminster, where the "New TV Show" was held, that extra power was supplied from these mobile generators parked outside.

long. R.C.A. have designed a new, much simplified type machine which uses transistors in many of its circuits and has a very easy tape threading facility. Both makes have electronic interlocking systems to permit rapid switching from live studio or O.B.'s to tape playback, without flashing or rolling of the picture. And so the systems progress, following the usual pattern of refinement after refinement until an entirely new method of television recording is evolved. That is already on the horizon in the U.S.A.—thermo-plastic recording—which puts a visible picture on a special tape, thus enabling cutting and editing to be carried out as with cinema films.

Television Debates

Sound radio had its great days of talks and debates, especially when there was no alternative Light or Third Programme. In these days, the most popular use of sound radio seems to be for pumping out a continuous flood of music, which transistorised receivers deliver to picnic parties, the beach, the railway compartment and (literally) to the man-in-the-street. It is not easy to plant yourself in a deck chair very far away from rival portable transistor sets or gramophones, each adding its quota of pop and plug to drown the soothing noises of the waves and seagulls. The best sound radio debates seem to have moved into television in a big way. I suppose the BBC TV's "Tonight" started it all, though this in itself was really a television development of the almost ancient "In Town Tonight".

John Freeman's famous interviews had their own startling flavour and the American Ed Murrow's interviews had an eye-and-ear-arresting quality. Now the ITV companies are occasionally getting off the band wagon and indulging in startling debates. "Under Fire" probably led the way, and now "Head On" carries on the controversial note, by taking a celebrity and having a panel discuss his merits and demerits in his presence. It is, in fact, another method of presenting "This is Your Life" but tempering the praise with a good deal of criticism. The first victim in this series was Randolph Churchill, whose reactions to both praise and criticism were revealed in close-up. "Head On" must

have required a great deal of research. The film interpolations of early incidents in Mr. Churchill's life were excellent.

"Appointment with—"

Another highly successful interview series has been "Appointment with—" in which Malcolm Muggeridge ranges over a wide variety of current topics with a well-known personality or public figure. Sir Charles Snow and J. B. Priestley have appeared in this series, in which points of view are often exchanged with uncompromising frankness. One has the impression at times that the producers of this programme, Peter Plummer and Patricia Lagone, were putting the viewer in the position of an eavesdropper listening to a private conversation between Mr. Muggeridge and his interviewee. I don't always agree with Mr. Muggeridge's point of view, but his easy, smiling manner and his relaxed questioning undoubtedly draws out his "victims" in a manner which is disarming. This again is first-class television debate material which make good entertainment.

Black Spots

The television public is becoming more critical of the quality of pictures in fringe areas and in the black spots where only the

highest of multi-element aerials will bring in a picture at all. In some places, pictures are ruined by freak interference between transmitters geographically hundreds of miles distant from one another, which are using the same frequency. Channel Nine, London, for instance, has interfered with local station Channel Nine reception in a few places many miles from London. The BBC have made great strides with small unmanned local transmitters called "translators," a typical example of which is at Folkestone, where signals are received on Channel Two and are rebroadcast on Channel Four on very low power. Similar installations at Sheffield, Ipswich, Barrow, Scarborough, Swindon and Caernarvon, amongst others, will greatly benefit local viewers. The ITA have now embarked on a similar scheme and I expect that quite a number of ITV black spots will, before long, be receiving a really good signal. It seems fairly easy to reach about 85 per cent of the population of the country with a good, strong signal. But there are pockets of population in small towns and villages in the remoter areas which have tolerated pictures full of snowstorms of interference for a long time. It is this last 15 per cent of the population which presents both BBC and ITA engineers with problems that are difficult to solve.

PRACTICAL WIRELESS Chief Contents of the October Issue (including FREE "Tutor" blueprint)

Now on Sale 2/-

- REMOTE CONTROL UNIT
- TROUBLE IN THE LOCAL OSCILLATOR
- ABOUT LOUDSPEAKERS
- AN EARTHED GRID R.F. AMPLIFIER
- A COMPACT POWER SUPPLY
- CALCULATING π-NETWORKS
- HOW TO KEEP RADIO EQUIPMENT COOL
THE P.W. 'TUTOR'
- A RECORDING LEVEL METER
- WOBBULATOR FOR F.M. I.F. ALIGNMENT
- S.W. SECTION
- CLUB NEWS
- ETC., ETC., ETC.

LASKY'S RADIO

GREAT TV OFFER

Don't neglect this final offer of well-known television products, all brand new, at clearance prices. Full data and instructions supplied. Call or post your order without delay.

MAKER'S SURPLUS COMPONENT BARGAINS

WIDE ANGLE	38 m.m.
Line E.H.T. Trans.	Ferrox-cube core, 9-16 KV.....
Scanning Coils, Low imp. line and frame	19/6
Ferrox-cube cored Scanning Coils and Line Output Trans. 10-15 KV EY51	winding Line Trans. with width and linearity controls, circuit dia., pair.....
Frame Output Transformer.....	50/-
Frame or line block osc. Transformer	6/6
Focus Magnets Ferrox-core. P.M. Focus Magnets, iron-cored	12/6
Duorax Focalisers	15/-
300 m/a Smoothing Chokes.	10/6

STANDARD 35 m.m.

Line Output Transformers 6.9 kV E.H.T. and 6.3 v. winding. Ferrox-cube.....	17/6
Scanning Coils, Low imp. line and frame	7/6
Frame or line blocking oscillator Transformer	4/6
Frame Output Transformer.....	7/6
Focus Magnets: Without Vernier	9/6
With Vernier	12/6
200 m/a Smoothing Chokes.	7/6

110° SLIMLINE 17" TV CHASSIS

Complete with 14 valves and 12-channel turret covering all Bands I and III. Valves: 2 PY82, 2 PL82, 2 PCF80, PCL84, 3 BW6, PCL89. Uses 17in. C.R. tube type CI7AT. Overall dim.: 19 x 12 x 6in.

LASKY'S PRICE 19 Gns. Carr. & Ins. 7/6 less C.R. Tube

Complete with C.R. tube. £24.19.6. Carr. & Ins. 19/6.

Above Chassis less valves, C.R. tube and Line Output Transformer. 99/6. Carr. 7/6.

C.R. TUBE type CI7AT, separately. £8.19.6. Carr. & Ins. 19/6.

Line Output Transformer with EY51. 29/6. Post 2/6.

Sound & Vision Chassis. Printed circuit, all components wired, complete with valves: 3 SW7, PCL84, 2 PCF80. Overall size 4 x 16 x 5in. (including valves). 55.19.6. Carr. 7/6. Less valves. Carr. 51.6.

"FIREBALL" TURRET TUNER

Covers all 12 channels, Bands I and III. L.F. 33-38 Mc/s. Size 4 x 3in. Complete with valves PCC99, PCL80.

LASKY'S PRICE 47/6 Post 2/6. Less valves 25/-.

207 EDGWARE ROAD, LONDON, W.2. | 33 TOTTENHAM COURT ROAD, W.I.

PADDINGTON 3271/2.

LASKY'S PRICE £18.19.6

less C.R. Tube

Carr. & Ins. 7/6.

Complete with new Brimar C17SM 17in. tube. £23.19.6. Carr. & Ins. 19/6.

Above Chassis less valves, C.R. tube and Line Output Transformer. 79/6. Post 7/6.

NEW C.R. TUBES

All sizes in stock at lowest prices. 17in. from 79/6. Send for list.

FERRANTI 17in. type TR17/10. 6.3 v. 0.3 amp. heater. 26.16.6. Carr. & Ins. 12/6.

REGUNNED C.R. TUBES

GUARANTEED for 12 MONTHS

Type Carr. & Ins.

12in. round	25 10 0	12/6
14in. rect.	25 10 0	12/6
15in. & 16 round	25 19 6	12/6
17in. rect.	25 19 6	12/6
21in. rect.	27 19 6	21/-

CLARKSON'S TUBE CHANGE

6A DENISON ROAD, LEEDS 2

Tel. Leeds 24576.

We are now able to offer SUPER SCREEN TV TUBES with 12 months' guarantee at the keenest exchange price ever.

Example:

Tubes all types	Cash allowance on return of old tube	Actual Cost of Tube
12"-14"	£5	£4. 5. 0
15"-17"	£6	£4. 15. 0
21"	£8	£6. 10. 0

Carriage and Insurance 10/- extra

These tubes are COMPLETELY REBUILT by experts, with the most up-to-date electronic equipment, and are fitted with the famous American Golden Grid Electron Gun. Many thousands of these tubes are in service today. Our factory is open to inspection to readers of "Practical TV". Technical advice and queries are answered free of obligation. All tubes are dispatched with adhesive paper and return labels. Cash allowance is sent on receipt of old tube.

RST

MAIL ORDER DEPARTMENT
211 Streatham Road, Mitcham, Surrey
ALL VALVES LISTED ARE NEW STOCK
& Terms C.W.O. or C.O.D. Postage 3d. per valve.
MITCHAM 6201

AZ 15/8	EF82 5/-	PCF82 8/6	UX85 6/6	8KBG 7/6
B65 5/6	EL42 10/-	PCL82 8/6	VPA8 17/6	6K8GT
DAF91 7/6	EF84 7/-	W81M 5/9	SL1 15/6	
DAF96 7/6	EL90 8/6	W142 9/-	SL1 15/6	
	EM80 10/-	W719 7/6	SLBG 7/6	
DF91 4/-	EM81 10/-	WT27 7/6	SL18 12/6	
DH719 7/6	EY81 10/6	X78 21/-	SL18 12/6	
DK91 9/6	EY84 10/6	X79 21/-	6N7G/GT	
EABC80	EY88 10/6	Z70 7/6		
	EY91 9/6	Z71 12/6		
	EY93 9/6	Z77 4/9		
EAF42 10/-	EZ35 7/6	Z152 8/6		
E801 5/-	EX40 7/6	PL81 14/9	ZT19 7/9	8SN7GT
EBC41 8/6	EZ41 7/6	PL82 8/-	1R5 9/-	5/6
EBBF80 9/6	EZ80 7/6	PL83 10/6	5U4G 4/6	8V8G 5/-
EBBF89 7/6	EZ81 7/6	PY80 8/-	5V4G 9/6	8X5GT 5/-
EC91 9/6	FC21 8/6	PY81 7/6	6X3GT 8/6	757 10/6
ECC33 5/-	FC4 17/6	PY82 8/-	5Z4G 10/-	7X4 7/6
ECC31 8/6	FC13 17/6	PY83 8/6	6A8GT 10/-	8D3 4/-
ECC83 9/6	FC13C 21/-	R10 21/-		10LD11
ECC84 9/6	GZ32 11/6	R19 19/6	6AL5 6/-	15/-
ECC85 8/6	H30 5/6	TDD 17/6	6AM6 4/-	12AHG 10/-
ECF89 12/6	H63 9/6	TP22 17/6	6AN5 7/6	12ATG 9/6
EKF82 12/6	HL92 8/6	U142 8/-	6AQ5 8/3	12AUT 9/6
ECH42 10/-	HL13D 9/6	U147 7/-	6BA6 7/6	12AX7 9/6
ECH81 9/6	U153 9/6	UABC80 7/-	6BJ8 7/6	12BA6 9/6
ECL80 9/-	KT33C 7/-	UR87 15/-	6BR7 15/-	12BH7 15/-
	KT86 17/6	UAC41 9/6	6BW6 7/-	12JVG/GT
	LZ319 12/6	UBF30 9/6	6BW7 5/-	9/6
	MKT4(3)	UCH42 8/6	6BX6 6/-	12K7GT
	(or 7) 17/6	UCH81 8/6	6F12 10/6	12K8GT
	ML4 15/-	UCL83 8/6	6F13 17/6	12Q7 8/6
	MSP417/6	UF41 8/6	6FSG 4/6	12Q7/GT
	MU14 9/-	UF42 8/6	6FT1 10/6	8/6
	MX40 17/6	UF43 8/6	6J7GT 9/6	35Z4GT
	N142 9/6	UF52 8/6	6K7 4/6	
	N153 11/6	UF53 8/6	6K7G 3/-	7/6
	PCC84 9/6	UL84 7/6	6K7GT 10/6	50L9GT
	EF89 10/-	UY41 7/6		9/-
	EF91 4/-	9/6		

SEND FOR LISTS.

Quotations given for any types not listed. Obsolete and old types a speciality.

D. & B. TELEVISION

131 & 131a KINGSTON ROAD
SOUTH WIMBLEDON, S.W.19

FOR THE FINEST, FASTEST SERVICE IN THE COUNTRY.
We are Open from 10 a.m. Until Midnight. For any information
or problems you have Call or Phone, we are always pleased to help.

SEND FOR OUR COMPREHENSIVE
L.O.P.T. SCAN COIL L.B.O., F.B.O., F.O.P.T. LIST
Prices of nearly all makes and models, 2/6, post free.
Invaluable as a service aid. The finest list ever compiled.

TRANSISTORS

Genuine Mullard Transistors in sets of Six: 1. OC44; 2. OC45's;
1. OC81D; 2. OC81's in matched pair. Including OA81. Diode.
for ONLY 22.6/-

Genuine G.E.C. Transistors in Sets of Six: 1. GET874; 2. GET873;
1. GET114; 2. GET114's in matched pair; plus 1. GEX34
for ONLY 18.6/-

SINGLE TRANSISTORS PRICE LIST

Mullard: OC44, 10/-; OC45, 9/-; OC70, 6/-; OC71, 6/-; OC72, 7/-;
OC78, 7/-; OC79, 7/-; OC81, 7/-; OC81D, 6/-;

G.E.C.: GET874, 9/-; GET873, 8/-; *GET114, 5/-.

* Available in matched pairs at 1/- extra.

Mullard Diodes: OA70, 2/9; OA79, 2/9; OA81, 2/9; OA91, 3/8.
G.E.C.: GEX34, 3/8.

All above are genuine manufacturers new 1st grade.

SURPLUS TRANSISTORS

Red Spot, A.F. OC71 and 72. Equivalent 4/3 each
White Spot, R.F. OC44 and 45. Equivalent 5/- each
Diodes, general purpose 1/- each
Various other types in stock. Please ask for prices of types not listed.

TURRET TUNERS, Various Makes: 10, 16, 38 Mc/s. 40/-

EXAMPLE OF TRANSFORMER LIST

	L.O.T.	SCAN COILS
FERGUSON:	(New)	(Used)
100TH, 105T	69/9	35/-
99/4/6/8	69/9	60/-
P.Y.E.	69/9	35/-
V4, VT4, VT7	69/9	60/-
VT7, CTM4	52/6	35/-
MURPHY:	69/9	55/-
V214, V240, V250	69/6	35/-
ECKO:	69/6	35/-
221, 283..	47/3	30/-
231, 284, 285..	54/4	35/-
		40/6
		27/8

REGUNED CATHODE RAY TUBES

all with 12-month Guarantee

ALL MAKES: 12in., 23.15-0; 14in., 24.50-0; 17in., 24.15-0.
ADD: 10s. for 90° tubes; 15/- for 100° tubes; 5/- for Electrostatic types.

SECONDS, with 12-month Guarantee— ALL MAKES: 12in.,
22.15-0; 14in., 23.05 (when available); 17in., 23.15-0.
SECONDS, No Guarantee— ALL MAKES: 12in., £1.50; 14in.,
21.15-0 (when available); 17in., 22.15-0.

NOT APPLICABLE TO NO GUARANTEE SECONDS:
10/- allowance on old tube if in good condition.

THE FABULOUS R.T.D. TRANSISTOR SIX

LATEST ON THE KIT MARKET

Spec.: Six transistor plus diode, printed circuit, superhet,
ferrite rod aerial. Automatic gain control to stop overloading.
Output 450mW in push pull. All components brand new and
guaranteed. Neat, small, two-tone grey cabinet. Two radios in
one, portable and car radio. Incorporates car aerial input socket.
Everything to build this superb Transistor Radio. Only 28.9.6.

AZ31	8/6	EF92	5/-	PL81	8/6	UCH42	7/-	6F13	7/-
B36	5/6	EL33	8/6	PL82	6/9	UF41	8/6	6F14	8/6
D77	3/-	EL38	14/6	PL83	7/-	UF42	3/9	6F15	9/6
DH77	4/6	EL38	7/-	PY31	7/-	UL41	7/3	6L1	12/6
DK91	5/9	EV51SE	8/-	PY32	10/-	UL46	7/3	6V8	5/-
DK92	8/-			PY30	6/8	UL44	11/6	10F1	4/6
DK96	7/6	EV51	7/9	PY31	6/8	UY41	8/6	10C1	10/-
DL82	5/9	EV86	7/6	PY32	8/6	UY42	10/-	10C2	13/-
DL94	8/9	EZ40	6/-	PZ30	10/-	UY49	8/6	10P13	9/-
DL98	7/6	KT330	8/-	UY49	8/6	SP41	2/3	10P14	9/-
EB91	3/-	KT36	8/6	U24	10/-	SP61	2/3	12ATV	5/6
EBC35	5/-	KT68	15/-	U25	12/-	W77	5/-	12AU7	5/6
EBC80	9/6	PCC84	7/-	U26	12/-	Z77	3/-	20D1	8/6
ECG22	5/3	PCC89	8/6	U31	9/6	SU4	5/-	20F2	12/-
ECG28	5/9	PCF80	7/-	U50	8/6	5V4	9/-	20L1	12/6
ECF80	8/-	PCL82	U52	7/-					
ECI33	9/-		10/9	U191	9/-	5Z4	10/-	20P3	12/-
ECI81	6/-	PCL83	18/1	U281	9/-	6AL5	3/-	20P4	16/6
ECL80	6/9		11/3	U282	20/-	6AM6	3/-	27SU	14/-
EF39	5/-	PCL84	9/6	U301	20/-				
EF50	3/9	PL33	8/6	U801	22/6	6CD6	27/8	30C1	7/-
EF80	4/6	PL36	10/9	UAF42	8/6	6D2	9/-	30L1	7/-
EF91	3/-	PL38	14/6	UBC41	7/9	6F1	5/-	30PA	10/9
						6F12	3/-	185BT	14/-

These are only examples of our valves: if you do not see what you require send stamped addressed envelope for special quotation.

We pride ourselves that we can obtain and supply ANY TV SPARES
OUR GIGANTIC STOCKS INCLUDE: Line Output, Frame Output,
Sound Output, Line and Frame Blocking, Osc. Trans. and Scan Coils for
any make or model Television. Please ask us for ANY components you
require we are almost certain to have them.

TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra.
Postage on Valves, 6d. each. C.R.T.s 12/6 inc. insurance.
SATISFACTION ASSURED. RETURN POST SERVICE.

Phone:
Cherrywood 3955

For Safety's Sake
use
AVO Prodclips

Pat. No. 748811

...with Trigger-Action Spring-Loaded Clips

PRESS TRIGGER TO OPEN
RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multimeter
and Avo Electronic Test Meter Leads.

Post Free
15/-
per pair.

AVO LTD. • AVOCET HOUSE,
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
Victoria 3404 (12 lines)
A Member of the Metal Industries Group of Companies

REBUILT TV TUBES
FULLY GUARANTEED 12 MONTHS
COMPLETE NEW GUN FITTED IN EVERY TUBE

12in.	£4.00
14-15in.	£4.10.0
17in.	£5.00
21in.	£7.00

Immediate Delivery, Carriage and Insurance 10/- extra
ALLOWANCE ON OLD TUBE

NU-GUN TELETUBES LTD.
3 The Mews, Duckett Road, Harringay,
London, N.4
Telephone: MOUntview 2903

The book for the serious model-maker...

RADIO- CONTROLLED MODELS
by F. J. Camm

The remote control by radio of models—whether aeroplanes, boats, locomotives, tanks or steam rollers as well as stationary models—is an important post-war development with a keen, widespread following of hundreds of thousands of enthusiasts. This practical book is the result of the author's numerous experiments and long research on the subject and includes information already published in the national press, "Practical Mechanics" plus additional material. Contents include steering control gear; receivers; transmitters; control box; turn reeds; model actuators; tuning transmitting aerials; details for model battleship and aircraft, etc. Fully illustrated with circuit details, diagrams, etc.

12s. 6d. FROM ALL BOOKSELLERS
or in case of difficulty, 12s. 6d. by post from C. ARTHUR
PEARSON LTD., Tower House, Southampton Street,
London, W.C.2.

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

SPECIAL NOTE: Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

A SERVICING HINT

SIR.—In the hope that the following will be of interest to other readers, I should like to give details of a servicing fault which I had. The symptoms were those of a failing tube. The customer said the tube had gradually become darker, and, when I tried it, the picture was there, but very faint. Turning up the brilliance gave a very slight improvement, but without producing a negative picture which I expected with a faulty tube. I tested all the usual points, H.T., EHT etc., without finding anything wrong. It was when I went to remove the tube base for testing that the fault became revealed. The flex lead carrying the signal to the tube had frayed all but one strand, and that was on the point of breaking. Apparently the extremely high resistance of that single fractured strand was just sufficient to carry some intelligence to the screen, and the breaking of the wires one by one had given the gradual reduction in signal strength. When cleaned, retinned and soldered back the results returned to normal and I have heard nothing in the way of a complaint since. The moral seems to be, take nothing for granted, but test systematically.—G. BORDEN (Paisley).

CHANGING TV DATA

SIR.—I feel that it is time for somebody, either the P.M.G. or some Parliamentary body to come down to earth and make one final decision regarding television. At the Radio Show I was confronted with all sorts of statements from various stands, and it would appear from what I was told that the industry is indeed in a sorry plight. How many lines, colour or black and white, and actual frequency, are all in the air, and the poor viewer doesn't know whether he will have to scrap his existing aerials and buy new ones, or whether, if he keeps his present equipment, he will soon be lagging behind his neighbours. Why can't someone make a firm decision for the benefit of both the general public and the Trade?—F. F. GREGORY (Hammersmith).

TRANSISTORISED TV

SIR.—Now that some manufacturers have successfully made a commercial receiver utilising the

ubiquitous transistor I would feel it time for one of your technical writers to provide those of us who find our main enjoyment in experimenting with some data to enable us to go ahead. I have designed a successful receiver section, for both vision and sound. I believe the manufacturers I mentioned above make use of both an American circuit and American transistors, but have been unable to confirm this. I trust, therefore, that we shall shortly see some really practical data on this aspect of TV.—R. PALMERSTON (Leeds).


CANNIBALISM

SIR.—I read in a daily paper some time ago that a store in London advertised sets for cannibalising, and I thought that the following data might be of interest. I had a Pye set which had given up the ghost, and had been relegated to the loft owing to being unable to dispose of it anywhere. I bought a set advertised for the cannibalising process, and to my surprise it was the same Pye model which I had put away. I got them both out and on making the usual tests I found that the components which had gone wrong were a mains transformer on one and a line output transformer on the other. I changed the line output transformer on the faulty set and it worked satisfactorily. I then looked at the remaining faulty set, which now had a faulty line and mains transformer, and on visiting the junk shops managed to pick up both of these items for a mere song, and as a result I have two working sets, both of which I have been able to give to O.A.P.'s, as I bought a new set when the first went wrong. I am sure that if one understands the technical aspect thoroughly, there are many odd pieces from sets which can be utilised to get a set to function after a break-down, without having to rely upon the special type of original component.—F. RATHBONE (W.6).

CHANNEL CHANGING

SIR.—I sympathise with Mr. Olivant (P.T. August) and his trouble. It is one I experienced in an acute form. This is due to being able to receive the BBC on four channels and ITV on three, any pair of which may be best on any given evening, depending on co-channel interference, Continental stations butting in, or just plain weakness. I solved the problem by using two turret tuners, one Band I and the other Band III. A simple change-over switch or relay (I use one on a remote control unit) gives two channels with a minimum of fiddling with fine tuners and the like, yet does not restrict choice.—R. G. YOUNG (Peacehaven).

ITA Station in South-East England

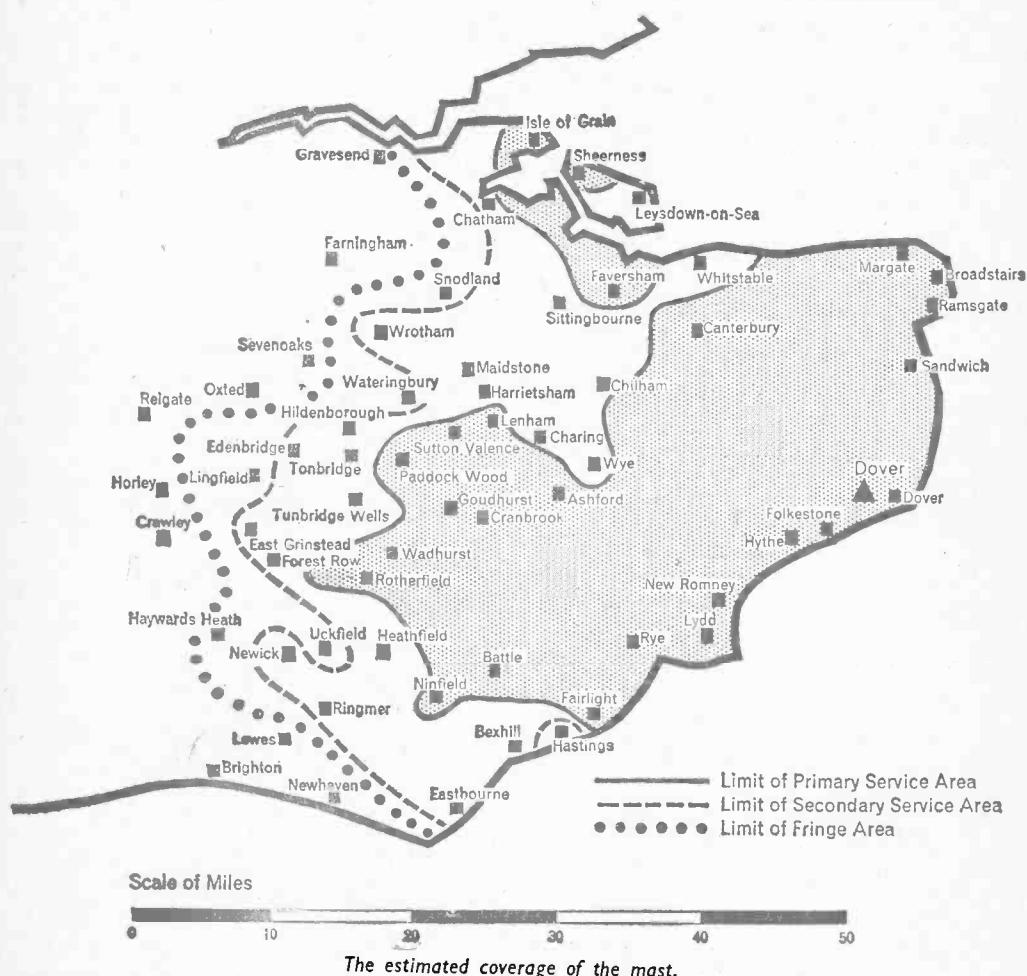

THIS map, issued by the Independent Television Authority, shows the coverage of the Dover station.

The transmitter, which went on the air on 31st January, 1960, has a highly directional aerial system that radiates a maximum power of 100kW a little South of West, 25kW to the North and East but only 1kW to the South. This special radiation pattern was designed to avoid creating any interference with television services on the Continent.

Within the primary service area (see map) most viewers, unless they are situated in particularly un-

favourable positions, should receive a consistently satisfactory service.

In the secondary service area, a substantial proportion of viewers should receive a satisfactory service, but in a few unfavourably situated places reception may be poor.

In fringe areas acceptable reception should be secured in many locations although this service may be subject to some interference from time to time.

The mean aerial height is 1,175ft above sea level.

The signal is vertically polarised on Channel 10, and the vision frequency is 199.7135Mc/s., the sound frequency being 196.1985Mc/s.

- ★ **TV TUBES 15/- each.** 15in. CRM 153 and 12in. CRM 121B. Ex. rental, service stock. Ideal for spares. Carr. and Ins., 5/-.
- ★ **TV TUBES 35/- each.** 36/24, 14KP4. Due to large purchase of renters replacement tubes. Carr. and Ins., 5/-.
- ★ **17in. TV CHASSIS £10.10.0.** Tube, valves, speaker, knobs, ITA/BBC, 12 months' guarantee on tube and 3 months' chassis. Carr. and Ins., 25/-.
- ★ **TRANSISTORS 47/6 per set.** Or, Mullard 1—OC81D, 3/9 ea. 1—OC44, 9/9 ea. 2—OC81, 6/9 ea. 2—OC45, 8/9 ea. 1—Diode, 1/9. G.E.C. 1—114, 6/9 ea. 1—873, 8/9 ea. 2—874, 9/9 ea. EDISWAN. XC121 and XB113, 8/9 ea. Post free.



EXTENSION SPEAKERS 19/9. Polished cabinet. With Bin. P.M. Speaker flex and switch. Ideal for kitchen, bedroom, workshop. Carr. and Ins., 3/9.

SPEAKERS 8/9. 5 inch—6 inch—8 inch—7 x 4 inch. Ex. manufacturers salvage. P. & P. 2/9.



BRAND NEW VALVES

8/9 each. EL91, EL42, EZ90, EZ40, EF86, ECC81, EF81, EF91, 6V6, ECC33, HI41.

11/9 each. ECC84, EL34, EL38, EL37.

SALVAGE GUARANTEED

9d. EACH. C2C, CV66, DI, DI52, EA50, EB91, EF50, HL41DD, HL42DD, LD210, SP41, SP61, VR35, VR51, VR106, VR107, VR109, VR137, VR201, 4D1, 6D1, 6D2, 6H6, 9D2, 12Y4, 15D2, 78, 2050.

119 EACH. D77, DH77, EB41, EF91, NI42, PEN45, PEN46, W148, Z77, ILC6, 6F1, 6F12, 6F13, 6F14, 6F15, 6K7, 6P25.

2/9 EACH. B36, EBF80, ECC31, ECC34, ECC81, ECC82, ECC91, ECH42, EF80, EF92, EL32, EL36, EY51, KT36, KT38, KTW61, L63, N18, N37, PL33, TH41, TH233, UAF42, UB41, UCH42, UF41, UF42, UY41, U22, U31, U35, U151, U281, 6C10.

5/9 EACH. EBC33, EBF80, ECF80, ECL80, EL33, EL38, EL41, EL45, GZ32, KT33C, KT63, LN152, LN309, LZ319, NI52, NI309, NI339, PCC84, PCF80, PCF82, PL38, PL81, PL82, PL83, PY80, PY81, PY82, PZ30, UBF80, U142, U152, U251, U801, W76.

ALL VALVES POST 6d. PER VALVE EXTRA



COMPONENTS LTD.

219 ILFORD LANE, ILFORD, ESSEX
Stamp for FREE Catalogue

Become a Television expert this easy way

The Bennett College offers you a complete course

You have to be really in the know to keep up with television these days. And the value of this special new course prepared by The Bennett College is that you are taught *all* the latest methods and techniques. You have the advantage of studying this profitable and fascinating medium in the quiet of your own home. And personal tuition by The Bennett College makes all the difference.

The Bennett College offers you a course that's non-mathematical and particularly easy to follow. It contains clear diagrams which cover everything you want to know from beginning to end (and

even includes the basic principles of sound radio if you wish).

The complete home-study course covers *everything*: Production of the signal, scanning and reproduction of picture from signals. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret incremental, etc. Television test gear. Television faults.

For more details, please fill in the coupon below. Your studies cost very little and the book you need is included in the cost.

To THE BENNETT COLLEGE
(Dept. J55NTV,) Sheffield
Please send me details of the new
TELEVISION SERVICING
COURSE

NAME.....

ADDRESS.....

AGE.....

"WAVE GUIDE AERIALS"

Manufacturers of TV Radio and Ham Transmitting Antennas wish to offer examples from their range of products. For the amateur Enthusiast and the Do-It-Yourself type.

A SUPER HIGH GAIN ARRAY FOR THOSE DIFFICULT RECEPTION SPOTS

	£ s. d.	£ s. d.	
3 Element BBC Folded Dipole, Channel 1, with a Double Five Channel 9 ITA, complete with all clamps	7 10 0	5 Element ITA Loft Aerial	1 6 0
or Double Eight Element ITA	8 10 0	8 Element ITA Aerial outdoor ...	2 9 4
Mast Equipment per your specification extra		Double 5 ITA Super Fringe outdoor Aerial	4 0 0
S/D 5 Combined BBC, ITA Loft Aerial ...	1 10 0	Double 8 ITA Super Fringe outdoor Aerial	5 0 0
S/D 5 Combined BBC, ITA Outdoor Aerial, wall mounting, complete ...	2 13 6	32ft. Garden Masts, complete for erection, two sets guy pickets, etc., with fitting instructions	12 10 0
H & 7 combined BBC, ITA with chimney lashing equipment	4 13 0	Coax Cable semi low loss, 7d. per yard; super low loss 1/2d. per yard.	
BBC Loft Aerial	12 9	Cross over boxes for combining separate BBC and ITA Aerials 9/6d.	
V.H.F. Loft Aerial	11 3	Please send 6d. stamp for full list of aerials and accessories. Terms C.W.O. orders over £4 post and packing free.	
5 Element ITA Aerial for attaching to existing mast	1 10 0		

PLEASE STATE CHANNELS REQUIRED WHEN ORDERING

WAVE GUIDE AERIALS


MIDLAND BANK CHAMBERS, FORE STREET, HERTFORD

*Two new books for the serious
Hi-Fi enthusiast and engineer ...*

INTRODUCTION TO HI-FI by Clement Brown

This book is a clear introduction to what we can and cannot do in the world of hi-fi, what is and is not important, which items of equipment can be bought cheaply, and for which this would be false economy. CONTENTS: Introducing High Fidelity - Records and Pick-ups - Amplifiers and Radio Tuners - Loudspeakers - Listening Room Acoustics - Stereophonic Sound - Tape and High Fidelity - Choosing Your Equipment - Installing Your Equipment - Hi-Fi in the Future - Further Reading - Useful Data. This book also includes a list of Recommended Records and Tapes plus a Glossary of terms used in hi-fi.

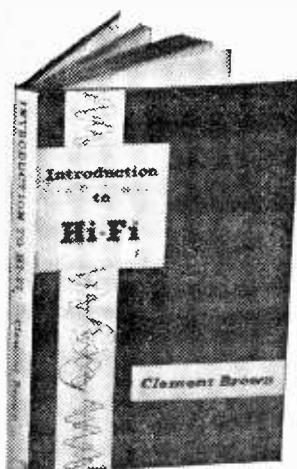
208 pages • 85 illustrations • 21s. net (22s. by post)



Books which will add to the knowledge and enjoyment of all who use Hi-Fi

FROM ALL BOOKSELLERS

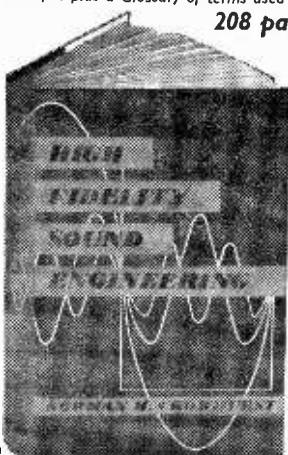... or, in case of difficulty at the post offices shown from the publishers
GEORGE NEWNES LTD.,
Tower House, Southampton Street,
London, W.C.2.



HIGH FIDELITY SOUND ENGINEERING

by Norman H. Crowhurst

This new book—by an international authority on high fidelity—provides the reader with basic concepts and design procedures of proved and lasting practical value. The material comes from a hitherto unpublished library of design data and information.

CONTENTS: Basic Requirements of Systems - Electrical Transfer in Simple Passive Circuits - Simple Active Circuits Transformers and L-C Filters - Power Amplification - Feed-back Transducers - Transducer Matching - Oscillators and Sound Generators - Test Equipment - System Design - Control of Acoustics - Design Data - Selected References.

336 pages • 262 illustrations • 50s. net
(51s. 6d. by post)



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDER-TAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 51 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

EKCO T221

There is no raster and no sound; the only valves lit are those in the sound strip, and the 20P4, U301, and 20L1, these latter three being excessively bright. Sparking occurs inside the U301. The following valves are in order: three 20D1's, 20S2 and 20PS. I have no service sheet.—W. Wells (Sunderland).

The symptoms indicate a heater-cathode leak in the "20" series heater chain. In your case these are the 20L1 line and frame oscillator and the 20F2 sync separator.

PYE VT4

The picture enlarged and went out of focus, and the screen went blank. After a few seconds, the picture returned. This happened two or three times at about quarter-hour intervals, but, eventually, the picture failed to return. The sound is unaffected.—A. Long (Holmrook).

A faulty EY51 EHT rectifier is the probable cause of the symptoms. In view of the intermittent nature of the fault, we suggest that you try resoldering the EY51 heater wires before you replace the valve.

FERGUSON 204T

The sound is rather harsh and a little distorted. I have replaced the PCL83 with no improvement.—G. Brigg (Ipswich).

Replace the 30pF capacitor connected to pin 6 of the PCL83. If the trouble persists, replace the 0.01μF capacitor connected to pin 1 of the same valve.

McMICHAEL MPI8

The frame is extended at the top and the bottom of the picture is folded over. I have changed the ECC82 with little or no results. — C. G. Scoll (Rotherhithe).

You should replace the PL84 frame output valve. If there is no improvement, check the 0.01μF linearity capacitors associated with its valve base.

SOBELL T171

The picture takes a long time to appear, and is then about 2in. short all round. It gradually enlarges until the screen is filled apart from a small space at the bottom of the picture. I have replaced the PY32, but with no effect. — C. F. A. Snook (Taunton).

If the PY32 is not at fault, we would advise you to check the appearance of the valve heaters during the warming up period. If these are very dim for the first few minutes, you should check the thermistor (VA1015) wired adjacent to the PY32 valveholder. Check also the rear centre PCL83, the right side PY81 and PL81 valves is necessary. If the bottom compression persists, check the 100μF capacitor (25VW) next to the PCL83 (on top of the chassis connected through to pin 7 of the valveholder).

DECCA DM14

From time to time, the picture becomes displaced in bands according to the picture detail, at the same time, sound on vision occurs. This fault can be produced or rectified by a sharp tap on the cabinet. —G. Powell (Marden).

The fault is probably caused by a blob of solder lodged between two tags promoting a short which is cleared by sharp vibration. We cannot be sure of this and you should trace the fault methodically, by first checking the effect of tapping each valve, ensuring that all are fitted, then turning the receiver on its side, take off the bottom cover and probe the valveholders, tag-strips, etc., to ascertain the exact point of the short.

ALBA T356

The line hold control will not quite lock the picture, leaving broken lines at the top and bottom of the screen and sometimes a wedge-shaped piece across the middle. The frame hold is good and so is signal strength.—P. J. Sanders (Taunton).

In most cases which we have investigated involving symptoms such as you describe, the trouble has been traced to the aerial which is receiving reflected signals. Resiting the aerial has restored normal line sync in most instances. If you find that the aerial is not at fault, and there is no sign of ghost images, check D1, disconnect D2, check C80 and C27.

K.B. MV100

Generally, this set gives a clear picture, but at times the picture breaks up and will not lock.—W. L. Dallow (Durham).

If the effect is most noticeable on camera changes or more on some scenes than others, check the aerial. If the break-up is complete, necessitating resetting of the line hold, check by replacing the rear right side 12AU7 (ECC82) valve and check the 220k resistor wired from the hold control to chassis.

FERRANTI T1002

The channel selector switch is "noisy" and a second fault is that the picture has been slipping down to about half size and gradually righting itself. Recently, it has been slipping more rapidly, and takes longer to right itself. — J. J. Davies (Wrexham).

First turn the receiver on its side; remove the bottom cover, free one end of the tuner unit lid,

and lift out of the slots at the other. This exposes the turret contacts. Thoroughly clean all the silver plated studs, rotating the channel selector switch to expose each pair of biscuits in turn. No further action is really necessary, but a light film of "Vaseline" or MS4 silicone grease can prevent further tarnishing.

For the second fault, replace the 30PL1 valve (PCL83) in the centre of the chassis.

PETO SCOTT 1712

It takes 2 minutes for the sound and 5 minutes for the picture to appear. When the picture first appears, it is weak and ragged. — B. Evans (Brighton).

You should replace the PZ30 H.T. rectifier valve. This should restore the normal warming up period. The irregular edges which slowly fill out are the result of loss of emission in the tube. Advancing the brilliance fully will help straighten the edges more quickly.

MARCONIPHONE VT157

This set works perfectly for about five minutes. The vision then disappears leaving a weak picture and loss of line hold accompanied by an increase in volume of the sound which is rough with a hum. — C. H. Griffiths (Garnant).

An extremely common fault in these receivers is for one of the vision coils on the top right side (as viewed from the rear) to become open-circuited at one end. These coils should therefore be checked. Normally, this does not affect the sound in any way and on this account, we would be more inclined to check the $8\mu F$ capacitor to the left of the mains dropper on the left side power board.

G.E.C. BT1252

A barretter 305 is fitted to this set which burns out every five months of normal use, together with either the line output valve PL81 or the sync separator PCF80 (L2319) whichever seems the weakest. — E. Whitehouse (Birmingham 24).

Check that the voltage tapping, especially the heater one, is in correct position. Suspect V329 for intermittent heater-cathode shorts or in fact any of the first seven valves in heater chain after the barretter.

SOBELL T171

There is a raster but no picture or sound on this set. The line whistle is very prominent and sounds a little rough. The raster is not at full brilliance even when the control is advanced. I have replaced the tuner valves with no result; also I have tried another PL81 but this made no difference. The raster is not steady but looks as if being viewed through water which has been disturbed. — J. Bowman (Wallsend).

Check EF80 common sound and vision I.F. amplifier and the valve base voltage to pins 7 and 8. If these are in order check the $0.005\mu F$ decoupling capacitor (pin 8 to chassis). Next check the H.T. supply to the tuner unit (blue lead) and follow the supply to pin 1 of the PCF80 (and contact nearest fine tuner) via the $6.8k$ and $3.3k$ resistors, both of which should be checked.

MARCONIPHONE VT53 DA-TRF

This television receiver is for the London area and is in good working order. Is it possible to alter this set for Wenvoe? — R. Barnes (Aberdare).

It is possible to alter the coils to receive Channel 5 but this involves a great deal of modification, coil rewinding etc. A more satisfactory solution would be to fit a turret tuner of the P38H (Cyldon) or 35S (Brayhead) type and feed the output of this to the V2 (Z77) stage, altering the coils to produce a 34-38Mc/s I.F. i.e., tune sound coils from 41.5Mc/s to 38Mc/s and the vision coils to 35Mc/s approx. The receiver would then behave as a superhet. Even this is no easy modification if a signal generator circuit is not available.

ALBA MODEL?

I have recently come into possession of this 12/14in. receiver which I believe is three years old. When the set has been switched on for about 20 minutes to half an hour, there appears along the bottom of the picture a black bar about 1in. wide. This shortens the picture. Use of the vertical hold does only a little to reduce this before the picture starts to roll. There are ten valves in the set and I would like your advice on remedying the defect. Apart from this fault the picture is good. — P. Norman (Aubourn).

You should change the frame output valve, probably an ECL80 or PL82. As you give us no idea of the model number of the receiver or any description of it we cannot be of greater assistance.

BAIRD 2117

When I turn the brightness or contrast up the faces of the people on the screen glisten on the light parts of their features then the picture becomes negative. The picture is not very bright but I can draw a good long spark from the EHT rectifier. There is also another fault. When the time-bases are running free, the whole screen is scanned but when I turn up the contrast the picture is about three inches short at the top with stretching at the top of the screen and cramping at the bottom. When the titles come up on the screen the bottom halves are out of sight, below the screen. The frame linearity controls will fill the screen but they only make the stretching and cramping worse. The voltages on the frame amplifier seem to be correct and the feedback components seem to be in order. I have the circuit for this set. — F. Fawton (Oldham).

The first fault described is most certainly due to a failing tube. The second fault is due to a low ECL80 V12 and the picture should be properly centred when this valve has been replaced.

BUSH TV22


I have just replaced a PL38 in this set but neither this nor adjustment to horizontal hold cured lines across the screen. Thinking this valve might not be seating on its socket I pushed on it and the EY51 burnt out. There is quite a bit of buzzing etc. on the sound. — K. Wagstaff (Seven-oaks).

We are not sure of what is meant by the EY51 burning out. If the heater of this valve has failed

(Continued on page 51)


LAWSON

DIRECT REPLACEMENT Reprocessed TUBES

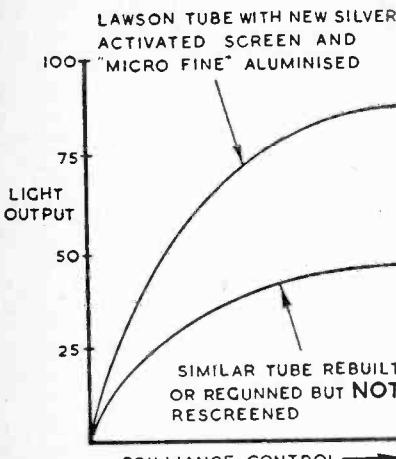

12 MONTHS FULL REPLACE-
MENT GUARANTEE

ENGINEERS WITH EXPERIENCE

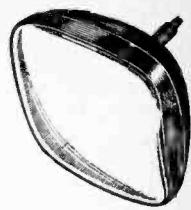

Know that as a tube gets old, not only does it become Low Emission but the light efficiency of the Phosphor Screen also deteriorates (up to 10% per year). This deterioration of the Screen obviously continues if the tube is only rebuilt or regunned.

Don't risk a "DEAD SCREEN", enjoy the brilliant crisp high definition of a LAWSON TUBE. Tubes which are absolutely BRAND NEW throughout (excepting the glass), and which incorporate the very latest CRT developments. New silver activated screens, "micro fine" aluminising, high efficiency gettering, plus Brand New electron guns by Britain's premier manufacturers, Mullard, Mazda, Emuscope, Cossor, Brimar, Emitron, English Electric, etc.

ALL MAKES AND TYPES FROM STOCK

LAWSON. The ONLY replacement tubes, for which all types are guaranteed, correct and direct plug-in replacements.

C.O.D. or C.W.O.

10/-

12" - £4.10.0
14" - £5.5.0
15-17" - £5.15.0

CARR. and INS. 7/6

Gladly refunded
if you wish to return
your old tube
(excepting 12")

EXPRESS PASSENGER SERVICE—

Orders received by 3 p.m. are dispatched same day.
Special direct services to Scotland and Ireland

TRADE AND QUANTITY DISCOUNTS

LAWSON TUBES LTD.

156. PICKERSLEIGH RD. MALVERN. Worcs.

TEL. 3798

NEW 7th EDITION

RADIO VALVE DATA

Characteristics of 4,800 valves & transistors, rectifiers & cathode ray tubes.
Compiled by staff of "WVW"

6/-

Postage 10d.

TELEVISION SERVICING HANDBOOK, by G. J. King. 30/- Postage 1/3.

THE RADIO AMATEUR'S HANDBOOK, 1961 ed. by A.R.R.L. 32/6. Postage 2/-.

PIN POINT TV TROUBLES IN 10 MINUTES. 31/6. Postage 1/-.

TELEVISION ENGINEERS' POCKET BOOK, by J. P. Hawker. 12/6. Postage 6d.

TELEVISION SERVICING Vol. 4. by G. N. Pritchett. 7/6. Postage 6d.

SERVICE VALVE EQUIVALENTS and R.S.G.B. Pub: 2/- Postage 4d.

A BEGINNER'S GUIDE TO TELEVISION, by F. J. Camm. 7/6. Postage 6d.

TAPE RECORDER MANUAL, by W. S. Sharps. 21/-. Postage 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET
LONDON, W.2

Phone: PADdington 4185
Open 6 days 9-6 p.m.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS	1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ..	Set 4 for 19/6
	DAF96, DF96, DK96, DL96	4 for 27/6
	6K7G, 6K8G, 6Q7G, 6V8G, 6X5G, or 5Y3G ..	5 for 24/6

1A7GT	11/6	6LD20	8/-	35A5	14/-	ECC82	6/3	EZ81	7/-	U24	17/6
1D5	8/-	6P1	13/6	35L6GT	9/-	ECC81	7/-	FW450	8/3	U25	19/6
1H8GT	10/-	6P25	9/-	35ZAGT	6/9	ECC81	8/9	GZ39	8/8	U26	10/-
1NSGT	10/-	6Q7G	8/-	35ZSGT	8/6	ECC85	8/3	GZ32	9/6	U50	8/-
1R _o	8/-	6Q7GT	9/6	50L8GT	8/9	EFC80	8/6	ATC3C	7/-	U52	4/6
1S4	8/-	6SL2GT	6/3	AC/TH1	16/9	EFC82	8/6	KT41	11/6	U78	4/9
1S5	5/3	6SN1GT	4/9	AZ31	9/6	EHC21	13/6	KT44	5/9	UABC80	8/9
1T4	3/6	6U4GT	11/-	B95	9/6	EHC42	8/9	KT61	10/-	UAF42	9/6
1S9	5/9	6V8G	5/6	D33	12/3	EHC42	11/6	KT63	6/8	UB41	8/6
3A5	9/-	6W5GT	4/9	DAC32	10/-	EHC81	8/-	MU14	6/6	UBC41	7/9
3S4	6/-	6X2GT	4/9	DAF91	5/3	ECL90	7/6	MX40	8/8	UBF80	8/9
3S4	6/-	6X5GT	5/-	DAF96	7/6	ECL82	9/6	N18	7/-	UBF89	8/6
5V4	5/-	7B6	9/-	DCC90	9/-	EF39	7/6	PC95	10/-	UC95	12/6
5U4G	4/6	7B7	7/6	DF33	10/-	EF40	12/6	PCC84	7/6	UC94	13/3
5V4G	8/-	7C5	7/6	DF91	3/6	EF41	3/6	PC93	11/6	UC85	7/6
5Y3GT	6/-	7C6	7/6	DF96	7/6	EF42	11/6	PCF80	7/9	UCF80	14/6
5Z4G	7/9	7H7	7/6	DH76	4/9	EF80	5/6	PCF82	8/-	UCH21	13/6
6AL5	3/9	7S7	9/-	DH77	6/9	EF85	5/6	PCF88	14/-	UH42	8/-
6AM6	3/6	7Y4	7/-	DK32	11/6	EPA99	9/9	PCL28	9/-	UCH81	8/-
6AQ5	6/-	10C2	17/8	DK91	8/-	EF89	7/-	PCL83	11/6	UCL82	10/9
6AT6	6/9	10P13	14/6	DK96	7/6	EF91	3/6	PCL84	7/6	UCL83	13/3
6BA6	6/-	12A7GT	5/-	DK96	7/6	EF92	4/3	PCL85	13/6	UF41	8/9
6BH6	5/9	12A7T	5/-	DL33	9/-	EF183	14/-	PEN4A	11/-	UF42	5/6
6BJ8	5/9	12AU7	6/3	DL35	9/6	EL33	10/-	PEN36C	8/-	UF85	8/6
6BW6	8/-	12AX7	7/-	DL92	6/-	EL41	8/6	PL36	11/6	UF89	7/-
6CD6G	27/3	12K7GT	5/3	DL94	7/-	EL42	9/-	PL81	9/8	U41	9/-
6F1	12/6	12Q1GT	4/9	DAEBC80	7/-	EL84	7/-	PL82	7/1	U44	7/6
6F6G	6/6	12Z5	7/6	EAF42	8/6	EM34	6/8	PL83	7/8	UR4C	10/6
6F13	11/-	14S7	19/6	EB91	3/9	EM80	8/6	PL84	10/-	UU6	13/6
6F14	16/6	20F2	17/6	EBC93	5/-	EM81	10/-	PX32	11/-	UY21	13/6
6K7G	2/6	20L1	17/6	EB94	8/-	EY31	7/6	PX30	7/6	UY41	6/6
6K7GT	5/-	23AS8GT	8/-	EBF89	8/9	EY84	10/-	PX32	6/6	VP4B	9/6
6K8G	6/3	23AS8T	7/9	EBF89	8/9	EY86	7/9	PX33	7/9	VP41	5/-
6K8GT	9/3	23ZAGT	7/6	EBL21	13/6	EZ40	6/9	PZ30	17/-	W76	5/3
6L18	10/3	23ZB8GT	9/6	ECC40	15/-	EZ41	7/-	T41	9/6	W77	4/6
6L19	12/-	30L15	11/-	ECC81	5/-	EZ80	6/3	U22	7/3	Z77	3/6

Post one valve extra.

Any Parcel insured
Against Damage in
Transit 6d. extra.
Any C.O.D. Parcel 3/-
extra.

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL,
LONDON, N.16

STA 4587

ALL TUBES
Guaranteed 12 Months
Carriage Free
Speedy Passenger Train despatch.

NEW

12"	MW31-74 etc.	£5.50
17"	CRM 171, 172	£7.00



COMPLETELY REPROCESSED TO MAKERS' SPECIFICATIONS!

REBUILT, RESCREENED, REALUMINISED TUBES OF THE HIGHEST QUALITY

14"	£5.50
15"-17"	£5.10.0
21"	£8.00


THAT "DIFFICULT" TUBE? LET US QUOTE

ASTOUNDING BARGAIN! The "Clarion" Transistor Battery Tape Recorder. Push-button controls, 3½ i.p.s. Portable. Durable plastic case. List price 25 gns. Complete with Mike and Tape. Our Price ONLY

16
Carr.
7/6.

TRADE ENQUIRIES INVITED

WESTWAY RADIO

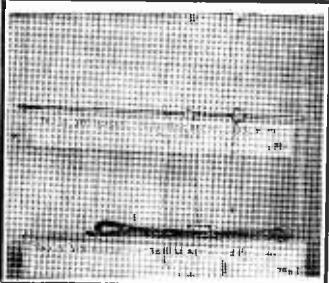

Ben Nevis Aerial Kit

For any Band 3 Station. Horizontal or vertical. Full assembly instructions with illustrations. All parts supplied to instal either in Loft, or on Mast up to 2in. or on Window, Chimney, or Wall. Kit includes 45 feet Co-axial cable with Plug fitted. Price, post paid, 59/6.

ANDREW SLOSS

Ben Nevis Works, Stranraer.

'CAPRI' ALL TRANSISTOR RADIO



All Transistor Radio with carrying case. Miniature loud-speaker design. Covers all medium waves. Very reliable. Works for months off 3d battery. Can be assembled in an hour or two using our simple ABC pictorial open out step-by-step plan. Complete set of parts including miniature speaker—everything!—only 27/6 plus 2/- P/P (C.O.D. extra). Parts can be bought separately. Demonstrations Daily—Money back guarantee. Send now.

CONCORD ELECTRONICS
(Dept. PT5), 210 Church Rd., Hove, Sussex

A comprehensive "basic" course in TV . . .

A BEGINNER'S GUIDE TO TELEVISION

by E. J. CAMM. Covers:—Persistence of Vision and Scanning. Cathode-ray Tube. The Television Receiving and Transmitting Systems. The Aerial. Tracing the sides through the Receiver. Video Section. The Television Camera. The tuning Signal Test Card C, and tracing faults. Colour. The N.T.S.C. System—Tricolour Tubes explained. Telecine—Video Tape Recording. Stereoscopic Television. Technical Terms. With 61 illustrations.
ONLY 75/- 6D. FROM ALL BOOKSELLERS

* In case of difficulty send 8s. 6d. to **GEORGE NEWNES LTD.**, Tower House, Southampton St., London, W.C.2.

LINE OUTPUT TRANSFORMERS

Direct Replacements for 500 sets.

T164, T167, T172, 2014, 1712	53/-
Bush. TV 11A, B, 12A, B; TVF 12A,	TUG12A, B; TRG 12A, B	60/-
TV12AM; TV22, 24; TV24, TUG24	45/-
Cossor. 930, 931, 933, 934, 948, etc.	58/-
Ekco. TS146; TS113-114; T161	T221, 231; TSC311, etc.	45/-
Ferguson. 841, 2, 3; 941 to 945	55/-
990T-998T; 103-145T; 203-246T.	66/6
Ferranti. T143, 14T4, 17K3, T123-4	45/-
T140S, T141, T142S, T150S, T152	T120S, T121S, T122S, T132S	65/-
G.E.C. and H.M.V. mostly 55/ to 100	80/-
Invicta. T101-104; T108-110	T114-126; T133-142	52/-
Murphy. V114C, V116C, V118C	60/-
V120C, V180, V178, V200, V202C	V240, 250	57/6
Philips. 114 UF/UM, 111S, 113, 1437 U,	62/6; V214, 216	69/-
144S, U, 1728, U, 1746 U, 1747 U	65/-
383A, 463A, 563A, 663A	60/-
Pye. LV30, 16T, CS12, VT17, VT17	60/-
CTM 14, 14T, CS17, VT17	52/6
Ultravox. 814, 815, 817, 915, 917, VV80,	85/-
VV730, VV734, VV736, VV720, VV710	14/53, 15/60, 17/60, 17/53, 17/60, 17/63-4,	85/-
(complete assembly with U25)	17/70-1-2, 21/50, 21/60, 21/70-1-2 ..	60/-
All Ultra Frame O.P.T. ..	Add post 2/6.	28/6

100 mixed resistors, 4W-2W-7W/8 post 1s.

ANOTHER BARGAIN. Complete set of 6 NEWMARKET High Gain Transistors and 1 Diode. Individually selected for max. gain and stability. Equiv. OC44, OC45(2), OCT1, OCT4 (matched pair) ONLY 22. Valves, Multimeters, Record Players, Tape Recorder Decks, see previous issues.

S.A.E. with enquiries please.

5 Westward Way
Preston Road, Harrow, Middx.
Tel. WOR 2683

FIRST-CLASS TELEVISION and RADIO COURSES

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E. A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148 HOLBORN LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne.

(Continued from page 48)

it should of course be replaced. Pushing in the PL38 would hardly have caused this. You should retune the station tuner knob to the right of the aerial terminals or if the input is excessive use an aerial attenuator.

PHILIPS 1768U

Although the sound is perfect, there is no raster. I have changed the EHT rectifier and all the line output valves. The ion trap has been checked and found to be in order. The line whistle is audible and there is spark when the EHT lead is advanced to the chassis. I shorted the grid to the cathode of the CRT, but with no result. I have a circuit of this model.—W. Burtonshaw (Croydon).

When the EHT clip is advanced to the chassis the resulting spark should be vigorous and quite long. A weak or subdued spark should direct attention to the EY86 valve inside the transformer housing, ensuring that the heater is glowing visibly. If you are satisfied that the EHT is satisfactory, check the heater voltage across pins 1 and 12 of the CRT base (6.3V) and the voltages applied to pins 2, 10 and 11. Since you have already partially checked the 2 and 11 potentials by shorting the tags together, attention should be directed to pin 10. If this potential is low check the boost line decoupling capacitor; 18,000pF on early models, 27,000pF on later models.

BUSH TV 53

Three months ago I fitted a regunned tube to this set and, until a few days ago, the picture was quite good. Now however, the picture is rather dim and the brightness control has little effect. Advanced or retarded from about the mid position, this control causes the raster to become black. The picture is at one moment reasonably bright and the next

is almost black. The width of the picture also seems to vary with the brightness content. When the brightness control is advanced, the picture is brought well into focus. The sound is quite all right. I have a service sheet. — K. F. Gorman (Cudworth).

First ensure that the ion trap magnet on the rear neck of the tube is correctly adjusted for maximum brightness. If there is little or no improvement, you should change the EY51 (EY86 in later models) on top of the line output transformer. Check the ECC82 and P181 if the width is inadequate.

K.B. LVT50

After having checked the aerial, cleaned the biscuit contacts and springs, fitted new PCC84 and PCF82 valves in the tuner unit and cleaned all the valve pins on this set, the following faults still prevail. On ITV the resolution of the picture is good, as is the contrast, but the whole of the picture is covered with a "crawling" effect. There is also a deal of background noise. On BBC only, a dim ragged picture is obtained and the "crawling" effect is noticeable. The sound is in order. I have a circuit diagram of this set.—C. Bradford (Buxton).

The trouble most certainly appears to be due to a faulty aerial system. Another receiver should be tried with the aerial to test it. If the aerial is not at fault note the effect of disconnecting the AGC (remove the 6AL5) and connecting a 4.5V battery—positive to the chassis, negative to the anode pin of the AGC diode anode (the junction of 0.1 μ F, 1.5M, 150k, and 220k components). If there is an improvement although the contrast is inoperative, check the AGC system thoroughly; 6AL5, 0.5 μ F, 0.25 μ F, etc. If there is little difference check the 10k triode anode load resistor of the PCF82 (pin 1), and the 100k resistors of the PCC84 (pin 2). Check the 6AM6 decoupling capacitor—0.001 μ F.

Practical Television MULTIMETER (Continued from page 32)

Alternative Method

If, however, a standard instrument is not available, good results can be obtained, if care is exercised, by the following method:

1. Using a 90V dry battery, or a stable source of H.T. voltage of about 100V, insert in series with this and the meter a resistor of about 2M. By putting a little more resistance in circuit, or reducing the series resistor a little, adjust the meter to give precisely full-scale reading on the 0—50 μ A range. A hand lens should be used to ensure an accurate reading.

2. Switch to the 0—0.5mA range. The reading should now be exactly 5. If not, adjust the shunt a little, as necessary, until an exact reading is obtained. The hand lens will be needed again.

Accuracy

The above procedure can be repeated for the next range (0—5mA) without much loss of accuracy. However, proceeding in this way the errors are cumulative, and unless a check against a standard can be obtained too much reliance should not be placed on the higher current readings.

In calibrating A.C. current ranges in this way it is possible to use the 6.3V heater supply from a mains transformer for the higher current ranges. For the lower current ranges, the shunts are larger in value and switching from one range to another causes enough variation in total resistances to alter the current appreciably. Hence, when the 10mA and 100mA ranges are being calibrated, the full 230V mains supply should be used, together with a series resistor of suitable value to limit the current. Since on the A.C. ranges a "universal" type shunt is used, it is necessary to do all shunt-adjusting progressively, beginning with R14 and proceeding in turn to R15, R16 and R17.

(To be continued)

QUERIES COUPON

This coupon is available until OCTOBER 20th, 1961, and must accompany all Queries sent in accordance with the notice on page 47.

PRACTICAL TELEVISION, OCTOBER, 1961.

SETS & COMPONENTS

BRAND NEW 17" Television Cabinets by famous maker Continental design. Complete with screen, mask, back knobs and tube mountings. Ideal for converting your old 14" to 17" set. £4.12.6. tubes supplied £4.10.0; carr. 7/6. 12 months' guarantee. GLICKSONS, 32 Cradock St., Swansea.

REBUILT TELEVISION TUBES—12in. £5.; 14in. £5.10/-; 17in. £6.10/-. Twelve months' guarantee. 10/- Carr. **TRANSISTORS, WHITE SPOT** 5/-; **RED SPOT** 5/-; **YELLOW** 5/6; **RED/YELLOW** 7/6; **CRYSTAL DIODES** 1/-; **1/2**; **4/8**; **ELECTROLYTICS**, all values; **CONDENSERS**, silver and paper; **RESISTORS**, all types; **RECLAIMED VALVES**, most types, 5/- each; **AIRSPACED CO-AXIAL CABLE** from 6d. per yard. **BRAVY HEAD TURRET TUNERS** £6.19/6; **REPLACEMENT VOLUME CONTROLS, TRANSFORMERS, TELEVISION and MAINS; SMALL PARTS REPLACEMENTS** and numerous **SECOND HAND COMPONENTS**. Stamped addressed envelope please with all enquiries.

DEVIZES TELEVISION SERVICE
28-30 The Nursery, Bath Road,
Devizes, Wilts. Tel.: Devizes 1100.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.**, Dept. PT22/9, 138 Lewisham Way, S.E.14. Tideway 6666.

ELECTRICAL FACTORS

OFFER THE FOLLOWING UNREPEATABLE BARGAINS

Brand New Television 12in. Tubes, Type M.W. 31-74. £2.19.6 (Carr. & Ins. 12/6)

Salvaged TV Chassis, 30/-, 5/- Carr. Ultra 814, 815, 817, H.M.V. 1824, 1825, 1829, 1840, Philips 1746U, 1748U/45, 1726U/15, 1446U, 1115UF/45, 1115U/15. K.B. KF50, F.V. 30L, H.F. 40L, J.F. 40, Ferguson 993, 998, McMichael T.M.54, Ambassador T.V.IIT.M. G.E.C. 6542 Sobell, T.S.14, T174. Master-Radio, T.D.T.7, T917. Many Others. Salvaged guaranteed 2/9 each. 30/- dozen. 10FI, EF80, EF91, EB91.

Short List New Valves

EF183	7/6	6F19	8/6	30P4	12/6-
EF184	7/6	6F23	10/-	30P5	6/-
U26	9/6	10LD12	8/6	30P6	10/6
U193	8/6	10F18	9/6	30PL13	12/6
PCC89	11/6	30CI	8/-	30FL1	9/6
6D2	5/-	30LI	8/-	30LI5	10/6

Fantastic clearance of Stereo Amplifiers, including two Mullard ECL82 and EZ80, pilot lights, knobs, one speaker circuit diagram, etc. £2.19.6 (carriage 3/6).

TELEVISION COMPONENTS AT BARGAIN PRICES

Please write for your individual requirements.

S.A.E. for Free Lists

4 HENDERSON ROAD
EASTNEY : PORTSMOUTH

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to "Advertisement Manager," "Practical Television" Tower House, Southampton St., London, W.C.2.

SETS & COMPONENTS (continued)

SURPLUS, AND NEW VALVES guaranteed. S.A.E. for list. Also reclaimed Valves, tested perfect, 5/- maximum plus 6d. postage each. Genuine Valve bargains. Valves bought. Lewis, 46, Woodford Avenue, Ilford, Essex.

TV SPARES

LINE OUTPUT TRANSFORMERS

A few examples from our extensive range.

TELEPHONE ORDERS SENT SAME DAY C.O.D.

Alba T301, 304, 394, 484, 494, 42/6.
Alba T321, 324, 424, 524, 39/6.
Baird 164/5/7, 172/5, 1812/15, 62/6.
Baird P2014/7, P214/7, 58/6.
Banner B112/4/7, 124, 412, 436, 65/-.
Beethoven B77, 80, 94.9, 106.9, 65/-.
Bush TV53, 69/6; TV24C, 89/6; TUG34, 5 gns.
Cossor 930-9, 58/6; (new), 30/- (used).
Deca D14/17, 58/6; DM14/17, 55/-.
Ekco T221, 231, 311, 284, 330, 55/-.
Ekco T161, T1C12, TC166, TU169, 30/- (used).
Ferguson 992/6/8 66/9; (new) 30/- (used).
Ferguson 992/6/8 66/9; (new) 30/- (used).
Ferranti 14T3/4/5, 47/6; 14T2/1T225, 62/6.
Ferranti T1002/5, 55/-; T129-138, 47/6.
G.E.C. BT, 1251/2, 1746/8, 2250, 50/-.
H.M.V. 1824/9, 1840-8, 2805-5902, 69/6.
K.B. NF 70/7M, MV/OF 100, PV20, 75/-.
Masteradio T917, TE77, T409/12, etc, 58/6.
McMichael TM/C/CR 51-2, 55/-; C/R 53 75/-.
Murphy V 240/250/280, 49/6; V200, 49/6.
Pye/Parm/Invicta V4/7, VT4/7, LV30, FV1 908-958, T118-120, 55/- CS17, etc. 75/-.
New Scan Coils on all above 65/-.
Peto-Scott TV122/4/6, 67/6; TV141, 72/6.
Philco 1457-67, 171-74, 1753-77, 87/6.
Philips 1114U, 1115, 1437, 1446, 89/6.
Pyle CV76, 77, 84, 87, etc. 65/-; TV94, 89/6.
Portadynes TA 17, T237, T417, used 39/6.
R.G.D. C55, 1455/6, 1755/6/7, etc. 89/6.
Ultra VT-17, etc, with U25 5 gns.
Vidor CN4206-12, 59/6; CN4217-31, 65/-.
We stock or can obtain most L.O.T.S. Scan Coils, Frame O.P.s, and spares.

PLEASE SEND S.A.E. FOR IMMEDIATE QUOTE.

Callers welcome. Open all day Saturday. Terms C.W.O. or C.O.D. Add 2/6 P. & P.

NEW TV BARGAINS

We have a limited number of 1962, Slim line Television Receivers by Famous Makers at special prices. For example 17 inch. List 57 gns. Our Price 44 gns, plus 25/- Carr. & Ins., 110 Tube, Printed Circuit. Contemporary Styling. All Channels. Full guarantee. All in sealed boxes. Immediate despatch on your order.

TELEVISION CONSUMER SERVICES LTD.
112 CAMBERWELL RD., S.E.5.
RODney 7917

SETS & COMPONENTS (continued)

B.V.A. NEW and rebuilt TV tubes. S.A.E.: REDWATT TUBE DISTRIBUTORS, 41 Denmark St., Wakefield, Yorks.

H.P. on Regunned C.R.T.s

At No Extra Charge
12 Months' guarantee
12" & 14" .. £3.10.0
17" .. £4.10.0
21" .. £5.10.0

Phone or Call only:
Rod 7778

P. J. F. Andrews
61-63 ROSEMARY RD.
LONDON, S.E.15

TV VALVES, all 3/6 inc. p. & p.-
INGRAM, 18 Plunket Rd, Doncaster.

TUBES! BRAND NEW 12in., 14in., £3.£4. 1 year guarantee. Also most rebuilds. Finest value!-3 Park Ave. New Barnet. BAR 1934.

In Scotland RENVUE for Better Value

COMPLETELY REPROCESSED TUBE (NEW GUN, RESCREENED ALUMINISED)

12.6v. and 6.5v. 0.3 amp. 17 and 15in. Types £6.10.0
12.6v. and 6.5v., 0.3 amp., 14in. Types £6. 0.0
12v., 15in. Types £7. 0.0
2v., 12 and 15in. Types £6. 0.0
Electrostatic 90 degree and 110 degree tubes 10/- extra. Carr. paid.

10/- ALLOWED ON OLD TUBE
Terms arranged.

FERGUSON

14in. BBC and STV Consoles ... £12.10.0
14in. BBC and STV Receivers ... £10.10.0
17in. BBC and STV Receivers ... £19.0.0

COMPLETELY OVERHAULED AND FITTED WITH COMPLETELY REBUILT TUBE

with One Year's Guarantee
£5 Deposit. Terms on Balance

Renfrew Electronics Ltd.
Anderson Drive
Renfrew : Scotland
Tel.: Renfrew 2642

LINE OUTPUT TRANSFORMERS

SCAN COILS SPECIALISTS

Makes	Models	Prices
AUE:	Spares available.	
ALBA:	T301, T304, T309, T484, T494, etc. .. .	39/-

AMBASSADOR: Spares supplied.

ARGOSY: Most models available.

ARMSTRONG: Spares supplied.

BAIRD, BANNER, BEETHOVEN: Spares supplied.

BUSH: TV11A, 11B, 12A, 12B,
TVG12A, TV22, TV33, TVG34

TVG34A, T36, TV36, TVG36

TV36C, TVG36C, TV43 .. .

TV53, TV66, T67, TV67, Rew'd

TVG58, TV92, TV93, TV96, only

TV67, etc. .. .

930, 931, 932, 933, 934, 935, 937,

938, 939 & F, 940, 941, 945, 946, 948 .. .

CHAMPION, COLUMBIA: Spares supplied.

DECCA: D17 & C .. .

DM1, DM2, DM3, DM4/C .. .

DM5, DM14, DM17, 444, 555 .. .

TR1433, TR1733 .. .

DEFIANT: Spares supplied.

DYNATRON: Spares supplied.

EKO: T933, TC5102, TS103, TS114,
TC124, TC131, TS185 .. .

T119 .. .

TC140, TC141, T141, TV142 .. .

TC141, TC142, T164, T165, etc. .. .

TC209, TV209, T231, T221,
T231A, T243, T263, T284, T294 .. .

T293, etc. .. .

ENGLISH ELECTRIC/ETRONIC: Spares supplied.

FERGUSON: 103T, 105T, 113T, 135T .. .

145T .. .

941T-953T inclusive .. .

991T-997T inclusive .. .

203T-246T inclusive .. .

306T, 308T .. .

1473, 1473P, 1474 .. .

17K & F, 1773 & F .. .

17K4 & F, 178K4 & F .. .

17T4 & F .. .

1475, 178K5, 17K5 .. .

BT1251, BT1252, BT1748 .. .

BT1748, BT4743 .. .

BT4643, BT5147, BT5246-48 .. .

BT5348-BT5643 inclusive .. .

and 89/6

H.M.V.: 1824 & A to 1831 inclusive .. .

1840-1842-1848 .. .

INVICTA: T118, T119, T120 .. .

K.B.: All other models .. .

LFT50, LFT50, LFT60 .. .

MV50 .. .

All models available, etc. .. .

MARCONI: All models available.

MASTERADIO: All models available.

McMOHAN: All models available.

MURPHY: V200, V202 .. .

V240, V250 .. .

PAM, PETO, SOUT' PHILCO: All models available.

PHILIPS: 1765U, 2168U .. .

All models available.

PILOT: All models available.

PORTADYNE: All models available.

PYE: CTM, PY4, PY4C0L .. .

V4, VT4, VT7, VT7 .. .

LV30, PV1, PV10 .. .

CM17, CTM17F, CW17 .. .

CW17C, CW17CF, CW17F, etc. .. .

All models available. .. .

RAYMOND: All models available.

REGEONTONE: All models available.

R.G.D.: 6017T, 7017, C64, etc. .. .

SOBELL: TS17, TS18 .. .

All models available. .. .

STELLA: ST3721U, ST3671U, ST8917U .. .

STRAD, TELEVOICE, TRUVOICE: Available.

ULTRA: 86 series, 815 series, with

U25 etc., complete .. .

VALRADIO: Spares available.

VIDOR: CN4217-CN4231 inclusive .. .

WESTMINSTER: Spares available.

WHITE-IBOTSON: Spares available.

Scancoll, Osc. and Output Txs. for all above makes available.

Post and Packing 2/6. C.O.D. 3/- extra.

All Enquiries S.A.E.

WYNDSOR TELEVISION

Dept. P.T.
ST. ALBANS RD., BARNET, HERTS.
BAR 1769

SETS & COMPONENTS (continued)

C. EDWARDS

1070 Harrow Rd., London N.W.10.
Ladbrooke 1734.

500 S/H TV Sets must be cleared
as taken part exchange. Condition
unknown.

ALL SETS COMPLETE

12in. BBC 25/- 13 Channel 50/-

14in. , 50/- .. . 75/-

17in. , 85/- .. . 125/-

Plus 15/- carriage.

Guaranteed Valves

10C2 10/-, 20D1 6/-, 6K25 8/-,
PL38 10/-, PL81 8/-, PY81 8/-,
PY80 7/6, PZ30 10/-.

TUBES-AERIALS-VALVES

Regunned tubes, guaranteed one year,
full range of aerials and fittings, I.T.V.
boosters, valves, Brayhead tuners, T.V. sets,
transistor radios, all electrical applican-
ces, television aerials, cables and house wiring
cables, fluorescent fittings.

All quotations without obligation. Special
terms to the trade and Home Engineers.

S.A.E. for Catalogue.

G. A. STRANGE
BROADFIELD, NORTH WRAXHILL,
Nr. Chippenham, Wilts. Tel. Marshfield 236

Television Tube Shop

now stock

Tubes for every make of set OVER 600 TUBES IN STOCK

12 inch Mullard type .. . £4. 5.0
12 inch Mazda type .. . £4.15.0
14 inch Mullard type .. . £5. 5.0
14 inch Mazda type .. . £5.10.0
15 inch Mazda type .. . £5.15.0
16 inch G.E.C. & Mullard type £6.12.6
17 inch Mazda & Mullard type £6.10.0
17 inch G.E.C. & Brimar type £6.15.0
21 inch Mullard type .. . £8. 0.0
Add 10/- for insured carriage to your
door within 48 hours, or 5/- via B.R.S.
Terms £2 down (plus carriage).

All tubes tested before despatch and
guaranteed for 12 months. Guarantee
cards enclosed with each tube.

Special Purchase of 110°, 17 inch tubes—

Slight mark, Guaranteed for 12 months.
Mazda CME 1703 } replace AW43-88,
GEC 7405A } £6.00

Shop Soiled Tubes.
(Slight scratches or marks) Guaranteed
12 months. Ideal for second set. 12in.
3/18, 3/31 37/6, MW31-74 50/-, 14in.
MW 36-44 52/6, CRM141 55/-, 17in.
CRM171, MW 43-64 60/-.
Others available from time to time.
Please enquire.

Service Engineers
Our Rebate Scheme shows real savings
—send for details.

Television Tube Shop

48 Battersea Bridge Road, S.W.11
BAT 6859
Just South of the Bridge. Open
Saturdays.

SALVAGED VALVES TESTED ON A MULLARD HIGH SPEED VALVE TESTER TO 100% STANDARD

POTENTIOMETERS

Carbon Pots, 25k .. . 1/- ea.

V/C and SP/SW, 500k .. . 3/- ea.

RESISTORS

Card of 1W Resistors, 72 Per

values covering complete card

10% range .. . 94/-

Full range of Separate Resistors

available.

CONDENSERS

100μf + 200μf 275v. D.C. 9/-

100μf 350 v. D.C. .. . 7/6

D14 2/8 .. . 2/3

D141 2/8 .. . 3/-

DF91 2/8 .. . 2/-

DH77 2/8 .. . 10d.

DK96 2/8 .. . 10d.

DW4/3502/6 .. .

EM41 1/3 .. . 15/-

EM41 1/3 .. . 15/-

EP80 1/3 .. . 15/-

EP91 1/3 .. . 15/-

F120 1/3 .. . 15/-

H141 DD50 .. . 10d.

KT330 1/3 .. . 10d.

KT42 2/6 .. . 8d.

KT61 2/6 .. . 8d.

KT741 2/6 .. . 8d.

L63 2/8 .. . 8d.

M14 2/8 .. . 8d.

M15-P4 2/8 .. . 8d.

M30 2/6 .. . 8d.

P41 2/8 .. . 8d.

P61 2/8 .. . 8d.

PC1584 4/- .. . 8d.

PC1584 4/- .. . 8d.

PL82 4/- .. . 8d.

PN-15 1/3 .. . 8d.

PEN44 2/8 .. . 8d.

PENDD 4/- .. . 8d.

PL20 2/8 .. . 25/-

PL33 2/8 .. . 25/-

PL41 4/- .. . 25/-

PL42 2/8 .. . 25/-

PL49 1/3 .. . 25/-

PL50 1/3 .. . 25/-

TDD13C 2/6 .. . 25/-

TN220 2/6 .. . 25/-

TP2620 2/6 .. . 25/-

U16 2/6 .. . 25/-

U31 2/6 .. . 25/-

U251 2/6 .. . 25/-

U74 2/6 .. . 25/-

U77 2/6 .. . 25/-

W77 1/3 .. . 25/-

W77 2/8 .. . 25/-

X41 2/8 .. . 25/-

Z63 2/6 .. . 25/-

Z66 2/6 .. . 25/-

Z77 1/3 .. . 25/-

Z90 1/3 .. . 25/-

Z71.9 2/8 .. . 25/-

Z71.9 2/8 .. . 25/-

Z10.7 2/8 .. . 25/-

SETS & COMPONENTS
(continued)**SPARES—VALVES—TUBES****NEW, EX-EQUIPMENT or SURPLUS**

6K25	4/6	EB91	2/-	PL33	4/6
12AT7	3/-	ECL80	4/6	PL38	10/-
10P1	4/6	EF80	2/-	PL81	4/6
10P1	4/6	EF51	2/-	PL82	4/6
10P14	4/6	EL33	4/6	PL31	4/6
20D1	3/-	EF88	4/6	PY50	4/6
20P1	4/6	EV51	4/6	PL81	4/6
275U	10/-	KT36	4/6	PZ30	4/6
185BT	12/6	PCP84	4/6	U24	7/6
B3C	4/6	PCP80	4/6	U801	12/6

Pre-war 4, 5, 7 pin types, 5/- postage 6d. each.

NEW TRANSISTORS. Red Spot, 2/6;

OC45, OCT4, 76, OC44, 3/6, OC35, 2/-

SPEAKERS. 6in., 5in., 10in. 12in. Post 2/-

Send S.A.E. with enquiries for full list.

"ST. JOHN'S RADIO", 3 Jews Row,

London S.W.18. Phone: VAN 8822

FOR SALE

VALVE CARTONS at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a Godwin Street, Bradford 1.

T.V. engineers are now using "LUBITEC". The amazing new multi-purpose contact restorer.

SIX STAR FEATURES

- ★ Cleans.
- ★ Lubricates.
- ★ Restores contact.
- ★ Protects corrosion and tarnish.
- ★ Conceals scratches on polished woodwork.
- ★ Cleans aluminium.

For instant clean contact in band switches, push button units, turret tuners, valve pins, valve sockets, volume controls.

HARMLESS TO THE CIRCUITRY**INDISPENSABLE TO ALL TV MEN**

Tested, approved, and used extensively by thousands of engineers and leading rental companies. From:

Main Distributors

WIRRAL TELEVISION
Heswall, Wirral, Cheshire.

Engineers bench size—6/6d. pint container with application brush, postage 1/6 extra.

100 BAYS of brand new adjustable steel shelving, 72in. high by 34in. wide by 12in. deep, stove enamelled dark green. Sent unassembled. Six shelf bay—£3/15/0. Sample delivered free. Quantities discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

TURRET TUNERS

BRAYHEAD £3.19.6

Brand New, any area, complete with fitting instructions. State set and 2 channels, 10 M/only. EXTRA COILS 10/6 per channel.

METAL RECTIFIERS

RECTIFIERS—CONTACT COOLED.

14RA1282 (FC101) type 250 v. 200 mA. 13/6.

14RA1283 (FC53) type 250 v. 300 mA. 17/6.

350 mA. 19/8.

RECTIFIERS—FIN TYPES

Equips. inc RM4 250 v., 250 mA. 14/-, RM5

250 v., 300 mA. 17/6; 14A99 400 mA. 18/6;

14A86 10/6; 14A97 20/-; 14A100 22/6 14A124

22/6; LWT 20/8.

CABY MULTIMETERS

A10 - 18 ranges, £4.17.6; B20 20 ranges, £8.10.0. S.A.E. for full details.

Cash with order. Post free. C.O.D. 2/6.

DURHAM SUPPLIES

175 Durham Road, Bradford 8, Yorkshire.

1,000 TELEVISIONS, all makes, from £3 working, 10/- not. Callers only. 9 till 6 including Sat. 39 Whitehorse Lane, Stepney, London.

FOR SALE
(continued)**TV'S FOR SALE****PRICES REDUCED**

BBC/ITA in good working order: C.R.T. Good Rebuilt
14in. Ultra V1815: KB LVT 30 .. £13 217
14in. Ekco T221 or T283 .. £18 221
10in. Ferguson 992 .. £9 213
17in. Plessey RGD .. £17 221
Send for Lists. Carr. Paid.

CADMANS

Bryan Street, Hanley
Phone: Stoke-on-Trent 2357.

GARRARD 210 £9.8/6; B.S.R. UA14 £7.15/0; T.U. 9 £4.2/6; B.S.R. Tape Deck £7.10/0. Set of 7 Transistors. standard quality 32/6. Full list from H. F. JAMES, 21 Claremont Road, Twickenham, Mdx.

Television Tubes Rebuilt. Please note we have appointed M/S R. S. Strudwick, 17 Hollingdean Road, Brighton 7, as Sole Agent for our Genuine Rebuilt Television Tubes for the South Coast. For details of prices, etc., please refer to our advertisement in the inside front cover.

MARSHALL'S
for TELEVISION LTD.

131 St. Ann's Road, Tottenham, London, N.15.
Stamford Hill 3267 & 5555

ALUMINIUM LADDERS/STEPS. Gigantic offer, 400 models. SANCO LTD., 17 (P.T.) Boundary Rd., Hove.

Star TV Tubes
70/-

all sizes up to and including 17in. includes old glass or plus 7/6 without C.W.O. Carriage 7/6.

WHY PAY MORE
new guns, 12 months' guarantee.

also 20/- each

12in., 14in., Part Exchange Televisions. Callers only.

ARTHUR SLARK
43-45 Thicketford Road, Tonge Moor,
Bolton.
Phone: 26684.

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, 5.000 models. Lists 1/- S.A.E. enquiries: TELLRAY, 11 Maudland Bk., Preston.

FAULTFINDER FILES (TV) showing common faults that each receiver is prone to and other useful servicing information, 2/- each. List 9d, plus postage. S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

SERVICE SHEETS — We have the largest stock of Radio & TV Service Sheets in the country for sale at 4/- each. Why tolerate delay in obtaining your supplies when we will dispatch by return? Service sheet list 1/- Also Manufacturers' Manuals for sale and hire. 1961 List now available, 1/-. S.A.E. please. Mail orders only to: S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

SERVICE SHEETS. Radio and TV 4/- each. List 1/-. All orders despatched on day received. Also manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

SERVICE SHEETS
(continued)

SERVICE SHEETS: also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20 Extension, Shepherd's Bush Market, London W.12 (Phone: SHE 3032).

SERVICE SHEETS (1930-1961) from 1/- with Free Fault-finding Guide. Catalogue 6.000 models 1/-, 125 Radio/TV Sheets covering 370 popular models 20/-, S.A.E. enquiries: HAMILTON RADIO, Western Road, St. Leonards, Sussex.

MISCELLANEOUS

DANCE BAND — Vacant dates.—GEORGE DARWIN, A.L.C.M., 19 George Street, St. Helens, Lancs. Phone: St. Helens 4246.

EDUCATIONAL

"HOW AND WHY" of Radio and Electronics made easy by a new, non-maths practical way. Postal Instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from Dept. 12, P.T. RADIOSTRUCTOR, Reading.

**Radio
Television
& Electronics**

Learn at home with the world's largest home study organisation. Brit. I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for FREE prospectus stating subject to

I.C.S.

Dept. 516
Intertext House, Parkgate Road, London, S.W.11.

FREE FROM THE I.P.R.E. Syllabus of famous radio and TV courses. Membership Condition booklets 1/-. Sample copy the Practical Radio Engineer 2/- post free. Secretary, 22 Fairfield Road, London N.8.

ELECTRONICS

Key to YOUR Future?

An exciting career—A new Hobby—Your own spare- or full-time BUSINESS?

New experimental course includes big kits for building test gear and a complete AM/VHF receiver.

FREE

brochure from

RADIOSTRUCTOR
DEPT. E78, READING, BERKS.



WANTED

WANTED: Service Sheets. No quantity too large, highest prices paid. **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

NEW VALVES WANTED — EY31, ECL80, PCC84, PCP80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. **DURHAM SUPPLIES**, 175 Durham Rd, Bradford 8, Yorkshire.

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., Beverley House, Manville Terrace, Bradford 7.

BOOK REQUIRED, Television Optics by L. M. Myers, published in 1936 by Pitman's. Good price paid for a copy in any condition.—R. W. FRANKLIN, 3 Hercules Street, London N.7. Tel.: ARCHway 7639.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES IN MINUTES from that great book "The Principles of TV Receiver Servicing." 10/6 all book houses and radio wholesalers. If not in stock from: Secretary, I.P.R.E., 20 Fairfield Road, London, N.8

RES/CAP. BRIDGE

38/-
p. & p. 2/6

Checks all types of resistors, condensers
6 RANGES

Built in 1 hour. Direct reading

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. QV)

Raleigh News, Raleigh Street, Nottingham

WANTED!

A BETTER, BRIGHTER
CLEARER
PICTURE
PATENTED



It can be done if you
plug this on your TV
Tube
Important! State
Make, Model No.
Name and Ad-
dress in Block
Letters Please.

STANDARD MODEL .. 22/6
DE LUXE MODEL .. 30/-

Postage 2/6 either model?

SINCLAIR ELECTRONICS Dept. P.T.2
18 Newport Court Charling X Rd. WC2
Terms: C.W.O., C.O.D.

BBC - ITV - F.M. AERIALS

B.B.C. (BAND 1), Tele-
scopic loft, 19'6", External,
S/D, 26/3.

L.I.V. (BAND 3), 3 Ele-
ment, loft array, 24'/5'
Element, 32'/6", Wall
mounting, 3 Element, 33/9.
5 Element, 41/3.

COMBINED B.B.C. +
L.I.V., Loft 1+3 Element,
41/3, 1+5 Element, 48/9.
Wall mounting, 1+3 Ele-
ment, 58/3, 1+5 Element,
63/9. Chimney and mast
mounting units also available.

F.M. (BAND 2), Loft "H", 28/-. 3 Ele-
ment, 52/6, S/D loft, 12/6. External
S/D, 28/3. State channel when ordering.

C.W.O. or C.O.D. P.P. 2/6. Coaxial cable.
8d. yd. Coaxial plugs, 1/3. Send 8d.
stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.T.)
38 Godstone Road, Kenley, Surrey

"TELFAC"**Regunned
TV Tubes**

Supplied from stock and despatched
per British Railways SAME DAY.
COMPLETE NEW GUNS fitted in every
tube and fully guaranteed for TWELVE
MONTHS.

	Mullard	Mazda
12 in. ...	£4. 0.0	£4.10.0
14 in. MW ...	£4.10.0	£5. 0.0
14 in. AW ...	£5. 0.0	£5.10.0
15 in. 2 Volt ...		£5.10.0
15 in. 12 Volt ...		£5. 0.0
16 in. ...	£5.10.0	
17 in. MW ...	£5. 0.0	£5.10.0
17 in. AW ...	£5.10.0	£6.10.0
21 in. MW ...	£6.10.0	
21 in. AW ...	£7. 0.0	£7. 0.0

MW = Magnetic Focus
AW = Electrostatic Focus

Plus 10/- for Carr. & Ins.

Other types not listed available. Please
contact:—

J. P. WRIGHT

Television Factors

103 Carr House Road, Doncaster
Sole Distribution Agent
'Phone: DON 2636

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6,-	DAF96, DF96, DK96, DL96, SET of 4 26/6,-
1R5 7/- DL92 5/11 PCF80 6/9	PCFB2 7/6
1R5 6/- DL94 6/9 PCFB2 6/9	PCL82 8/3
1S5 4/6 DL95 6/9 PCFB2 6/9	PCL83 11/6
1T4 3/3 EB91 3/- PCLB83 11/6	PCLB84 7/6
3S4 5/1 EB91 7/6 PCLB84 7/6	PCLB85 7/6
3V4 6/9 EB90 7/6 PL28 10/9	PL29 10/9
5U1G 4/3 EB91 12/6 PL81 8/8	PL82 8/8
5Y2G 5/8 EB90 14/6 PL83 6/8	PL84 6/8
5Z4G 7/3 EB91 4/9 PL83 6/8	PL84 6/8
6AM8 2/9 EB92 5/9 PL84 9/8	PL85 9/8
6KTG 1/9 EB93 6/3 PY32 11/-	PY33 11/-
6KBG 4/9 EB94 8/- PY80 7/-	PY81 6/-
6Q7G 5/6 EB95 7/9 PY82 6/-	PY83 7/3
6VBG 4/9 EB96 8/3 PY83 6/-	PY84 7/3
6V9GT 6/6 EB92 8/3 PY83 6/-	PY84 7/3
6XG5T 4/9 EB91 12/6 U25 12/6	U26 12/6
12K7GT 4/9 EB92 7/6 UAF90 8/8	UAF91 8/8
12K7GT 11/6 EB90 6/9 UAF91 8/8	UAF92 8/8
12Q7GT 6/6 EB90 12/6 UAC41 7/1	UAC42 7/1
3516GT 8/6 EB91 7/6 UF80 8/8	UF81 8/8
3524GT 8/6 EB91 4/9 UCC85 7/1	UCC86 7/1
A231 8/9 EB95 5/- UCH21 12/6	UCH22 12/6
CL33 11/9 EB96 8/9 UCH42 7/6	UCH43 7/6
DAC32 9/6 EB93 6/9 UCH81 8/-	UCH82 8/-
DAF91 4/6 EB91 2/9 PL82 10/9	PL83 10/9
DAF96 6/9 EL41 7/- UCL83 13/-	UCL84 13/-
DF33 9/6 EL84 6/3 UF41 7/9	UF42 7/9
DF91 3/3 EB91 7/3 UF85 8/-	UF86 8/-
DF96 8/9 EB90 7/3 UF89 6/6	UF90 6/6
DK37 6/4 EB91 6/7 UU11 7/1	UU12 7/1
DK32 11/6 EB91 6/9 UU34 7/1	UU35 7/1
DK91 6/- EB90 5/9 UU21 13/-	UU22 13/-
DK92 7/3 EB91 6/8 UU41 5/6	UU42 5/6
DK96 6/9 MU14 8/- UU95 6/3	UU96 6/3
DL33 8/6 PCF84 8/9 VP48 8/6	VP49 8/6
DL35 9/6 PCF89 10/- ZTT 2/9	ZTT 2/9


Postage 6d. per valve extra. Any Parcel
Insured Against Damage in Transit 6d. extra
Any C.O.D. Parcel 3/- extra.
Office address, no callers.

GERALD BERNARD

(Note new address—formerly of Leeds)
83 OSBALDESTON ROAD,
STOKE NEWINGTON, LONDON, N.16.

**COYNE'S NEW
PIN-POINT TV
TROUBLES**

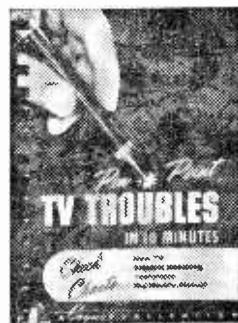TAKES HEADACHES OUT OF
ALL SERVICING PROBLEMS



Your most useful on-the-job "tool"! Quickly
and easily pin-point the exact trouble in any
TV set. Over 70 symptoms; 200 trouble
spots. Over 340 cross-indexed pages; 50 time-
saving Check-Charts; 290 diagrams and photos;
explanation of circuits and designs.

**SIMPLE CHECK-CHART SYSTEM SAVES
TIME!**

This amazingly practical handbook shows you
how to find the trouble in an TV circuit
FAST! Simple cross-index tells you in what
section you'll find cause of trouble. Handy
Check-Charts then help you accurately locate
the EXACT trouble spot. Cut waste time,
eliminate hours of aggravation, get right to the
heart of the trouble in minutes.

**USE THIS BOOK RIGHT ON THE JOB—NO
NEED TO MEMORIZE!**

This Pin-Point Book was designed especially
for on-the-job trouble-shooting. You simply turn
to the indexed section, locate the circuit de-
scription and Check-Chart, and in minutes you
have the trouble spot located and ready for
repair. No complicated theory or mathematics.
Down-to-earth practical circuit
description, service methods and trouble-
shooting techniques. Published by the famous
Coyne Electrical School and approved by
leading authorities in the field.

J. E. C. Grover of Streatham says:
"Immediately I glanced through this book I
was convinced that your claim concerning the
simplicity of the work was justified for it is,
without a doubt, the finest book of its kind
that I have ever come across. It is not only
unique in its presentation but it is also sup-
erbly produced."

G. Axam of London S.E.6, says:
"I have spent nearly £50 on technical books
over the past 5 years all of which I feel has now
been wasted as your book is the best I have
yet had the pleasure of examining. It is practical,
to the point, with just the right amount of
technical information needed, covering almost
every aspect of TV servicing."

SEND NO MONEY!
Just mail coupon for free trial. After 7 days
send only low price or return book and pay
nothing!"

FREE TRIAL OFFER!
Mail Coupon NOW!

Mail Order Division, SIM-TECH TECHNICAL
BOOKS, Dept. P.2, Gater's Mill, West End,
Southampton, Hants.

RUSH, TV Troubles 31/6d. plus 1/8d.
postage for 7 day FREE TRIAL as per
offer.

**Tick here if enclosing full price, we pay
postage: Same 7-day money back guarantee**

Name

Address

City County

COYNE'S NEW JOB TRAINING BOOKS

**Put Money-Making Time
Saving Know-how at your
fingertips!**

Shows you the way to easier TV—Radio repair—time saving, practical working knowledge that helps you to repair sets faster! How to install, service and align ALL radio and TV sets, even colour-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated maths or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home.

TRY ANY THREE BOOKS ON NO RISK FREE TRIAL

Look over the list of books and select the first three books you would like to examine. Circle the book numbers on the coupon. Additional books you would like to see may be entered on a separate piece of paper, and these will be sent to you after completion of the first transaction.

SPECIAL OFFER COYNE ELEMENTARY PRACTICAL RADIO-TELEVISION SET OF THREE VOLUMES, total 1,038 pages, sturdy Vinyl washable covers. £3.12/6d. the set!

These three volumes present the principles of construction, operation and testing of radio and television equipment in a SIMPLE, EASY TO FOLLOW manner.

By using NEW & DIFFERENT methods of explanation these books clearly explain the direct relation between the various parts of sets. This information is especially helpful in repair work where many times a burned out valve, resistor or transformer is actually caused by some other defective part of a circuit. Until the cause of the trouble is removed the parts would continue to burn out. For this reason each part of the radio or television unit is explained, thus, making the material especially helpful to the experienced radio man, as well as the amateur.

The very important way in which these books differ from many other radio and television books is that the publishers did not try to assume the "student of technical knowledge" of the reader. Every subject is explained COMPLETELY—while at the same time keeping it brief and to the point.

You will find hundreds of photos, charts, diagrams, etc., in these books. These have been provided to make it easier to understand the explanations. To get this special offer, send no money now, then 12/6d. after free examination, and 20/- per month.



No. 9
Pin-Point

Transistor troubles in 12 minutes

In this extremely practical handbook, the famous Coyne Check-Chart Trouble-Shooting Method is applied to Transistorized Equipment and includes such subjects as Pre-amplifiers and Hearing Aids; Audio Amplifiers; Portable Sets; and Special Types of equipment. Hundreds of photos, illustrations, diagrams and Check-Charts; Valuable reference sections. 328 pages. Spiral Binding. Price 47/6. (Please send coupon with order).

No. 4. LATEST INSTRUMENT FOR SERVICING RADIO AND TELEVISION. Coyne.

This up-to-the-minute book tells all about modern radio, TV and electrical testing equipment and how to use it. Money-making short cuts on trouble-shooting, servicing, construction, and other jobs. Over 350 pages, 220 photos and diagrams. Covers Multimeters, Resistors, Ohmmeters, Oscilloscopes and many others. All data has been pretested in the Coyne radio shops. Vinyl cloth covers. 26/-.

No. 5. PRACTICAL TELEVISION SERVICING AND TROUBLE SHOOTING MANUAL. Coyne.

A book of fast time saving methods for servicing TV receivers. Includes dozens of new testing ideas all of which have been proven on the job. This book shows how radio knowledge can be applied to help solve television problems. Contents include TV Servicing methods, TV Servicing Instruments, Tuners, Video I.F., Amplifiers, alignment, etc., with 200 crystal clear photos and diagrams. 437 pages. Washable vinyl cloth covers. Price 34/-.

No. 6. COYNE TELEVISION SERVICING CYCLOPEDIA. Harold P. Manly. Coyne.


Quick and concise answers to TV problems in alphabetical order, cross indexed, fully illustrated, covers hundreds of questions involving radio, TV, electronics operation and repair. 450 illustrations; photos, diagrams, charts, test patterns, etc. 860 pages. Vinyl cloth covers. Price 47/6.

No. 18. TELEVISION EXPLAINED. Miller and Spalding. (LILFFE)

In simple terms and non-mathematical language gives step-by-step survey of modern television receivers and aerial systems, including AGC and Flywheel Synchronising. 184 pages. 12/6.



FREE TRIAL OFFER!

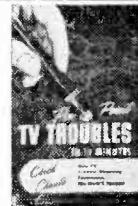

No. 8

COYNE'S NEW PIN-POINT TV TROUBLES

TAKES HEADACHES OUT OF ALL SERVICING
PROBLEMS

Your most useful on-the-job "too". Quickly and easily pin-points the exact trouble in any TV set. Covers 70 symptoms, 700 trouble spots. Over 340 cross-indexed pages; 50 time-saving Check-Charts; 290 diagrams and photos; explanation of circuits and designs.

SIMPLE CHECK-CHART SYSTEM SAVES TIME!

This amazingly practical handbook shows you how to find the trouble in any TV circuit FAST! Simple cross-index tells you in what section you'll find cause of trouble. Handy Check-Charts then help you accurately locate the EXACT trouble spot. Cut waste time, eliminate hours of aggravation, get right to the heart of the trouble in minutes. Price 31/6.

No. 22. PIN POINT COLOUR TV TROUBLES IN 15 MINUTES. Edited by Robert G. Middleton.

This book deals with 150 types of faulty pictures and sound with over 1000 troubles which may be the cause. Some of the subjects covered are: Antenna, Tuned Video and Luminance Amplifiers, Matrices, Picture Tube (Black & White, and Colour), One-Gun Tube, Set up of Colour Television, Colour Killers and Automatic Colour Control, Low Voltage, Power Supply, TV Sound, etc. Picture Pattern Section—362 Check Charts. Diagrams and Photos. 548 pages. Price 47/6.

No. 7. TRANSISTOR CIRCUIT HANDBOOK. Louis E. Garner, Jr. Coyne.

A practical Transistor Circuit Reference Handbook by the eminently qualified Louis E. Garner, Jr., one of the greatest writers on transistor applications. Covers Transistor Circuity, Basic Transistor Circuit Applications and General Reference material. Dozens of how-to-do-it illustrations with more than 200 circuit diagrams. Over 400 pages. Vinyl cloth covers. 39/8. (When ordering this book please be sure to clip the coupon).

No. 10. TELEVISION RECEIVER SERVICING. Vol. 1. by E. A. W. Spreadbury. 1961 Edition. (LILFFE)

Timetable Circuits, including the Cathode Ray Tube. How to check the Waveform at the Input and Output of each Section—Faults—Blank Screen—Obtaining a Raster, Applying a Signal, Synchronisation, Interlace Quality, etc. 362 pages. 25/-.

NOTE

* Any Liffe or Coyne book is available on time payment plan!* Send name and title required.

Just mail coupon for free trial. After 7 days send only low price or return books and pay nothing. If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum three books). To buy one book send one-half in 7 days, and one-half in 30 days.

LIMITED OFFER! ACT NOW!

To SIM-TECH BOOK COMPANY (U.K.)

Mail Order Division, DEPT. PTV14, Gaters Mill, West-End, Southampton, Hants.

- Please send me the special Elementary Radio TV Set as per special offer.
 Rush the books circled below for 7-day FREE TRIAL as per offer.

- Tick here if enclosed full price. Same 7-day money back guarantee.

Name

Address

City..... County..... Postage 1/6, orders under £3. 2/- orders over £3.

TELEVISION TUBES RE-BUILT BY "RE-VIEW"

PRICE:

12in.	£4.10.0
14in.	£4.15.0
15in.	£5. 0.0
17in.	£5. 0.0
21in.	£7. 0.0

SAVE £££sCorrect voltage heaters
All types**TWELVE MONTHS' GUARANTEE**

Free carriage and insurance

Cash with order or C.O.D.

Be one of our satisfied customers. Call and see our TUBES REBUILT and TESTED

RE-VIEW (London) LTD., 385 London Road, West Croydon, Surrey

Terms to the Trade

Tel.: THORNTON HEATH 1826

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee
“NO PASS — NO FEE”**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25. a week, send for your copy of "ENGINEERING OPPORTUNITIES" FREE.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng...
Electrical Eng...
Civil Engineering...
Radio Engineering...
Automobile Eng...
Aeronautical Eng...
Production Eng...
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
A.I.O.B.
B.Sc.
A.M.Brit.I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.
SCHOOL OF ELECTRONICS****POST COUPON NOW!**

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
(Write if you prefer not to cut page)

NAME.....**ADDRESS**.....

I

II

III

IV

V

VI

VII

VIII

IX

X

SUGGEST OR EXAM
THAT INTERESTS ME

(£2/20).

**BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/20), 29 Wright's Lane, London, W.8**

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

CRT BOOSTER TRANSFORMERS

TYPE A. OPTIONAL 25% and 50% BOOST.
2 V. OR 4 V. OR 3 V. OR 10.8 V. OR
13.3 V. MAINS INPUT. 12/6

TYPE A2. HIGH QUALITY, LOW CAPACITY,
10/15 pF. OPTIONAL BOOST 25%, 50%,
75%. MAINS INPUT. 16/6

TYPE B. MAINS INPUT, MULTI OUTPUT 2,
4, 6.3, 7.3, 10 and 13 VOLTS. BOOST 25%
AND 50%. LOW CAPACITY. 21/-

FULL instructions supplied.

TRIMMERS. Ceramic. 30, 50, 70 pF. 8d.: 100 pF,
150 pF. 1/3; 250 pF. 1/6; 500 pF. 1/9.
RESISTORS. Preferred values. 10 ohms to 1 meg.,
1 w.; 4d.; 1 w.; 4d.; 1 w.; 8d.; 2 w.; 1/2.
HIGH STABILITY. 1 w. 1 pF. 2/- Preferred values.
100 ohms to 1 meg. Ditto. 3Ω, 100Ω to 5 meg. 1Ω, 9Ω.
3 watt } WIRE-WOUND RESISTORS { 1/3
10 watt } 25 ohms—10,000 ohms { 1/6
15 watt } 25 ohms—10,000 ohms { 2/-
12.5K to 50K 10 w. 3/-

AMERICAN "BRAND FIVE"
PLASTIC RECORDING TAPE

Double Play	7in. reel, 2,400ft.	80/-	Spare
Long Play	5in. reel, 1,200ft.	37/6	Plastic
	5in. reel, 1,800ft.	35/-	Reels
	5in. reel, 1,200ft	23/6	3 in. 1/6
Standard	5in. reel, 900ft	18/6	4 in. 2/-
			5 in. 2/-
"Instant"	Bulk Tape Eraser and Head De- sulper, 200/250 v. A.C. 27/6.	51 in. 2/-	
	5in. reel, 600ft	16/-	7 in. 2/-

"Instant" Bulk Tape Eraser and Head De-
sulper, 200/250 v. A.C. 27/6. Leaflet, S.A.E.

O.P. TRANSFORMERS. Heavy Duty 50 mA, 4/6,
Multi-tap, push-pull, 7/8. Ditto, 10w, 15w, Miniature,
384, etc. 4/6. **L.F. CHOKES** 15/10 H, 60/65
mA, 5/-; 10 H, 80 mA, 10/6; 10 H, 150 mA, 14/-

MAINS TRANSFORMERS 200/250 v. A.C.
STANDARD 100 mA, 5Ω, 3.5 a. tapped
4 v. 4 a. Rectifier 100 mA, 3 a. 5 v.
2 a. or 4 v. 2 a. ditto, 350/0-350 22/6
MINIATURE 200 v. 100 mA, 6.3 v. 1 a. 10/6
MIDGET 220 v. 45 mA, 6.3 v. 1 a. 15/6
SMALL, 220-0-220, 50 mA, 6.3 v. 2 a. 17/6
STD. 250-0-250, 65 mA, 6.3 v. 3 a. 17/6
HEATER TRANS. 6.3 v. 1 1/2 amp. 7/6
Ditto, tapped sec. 2, 4, 6.3 v. 1 1/2 amp. 8/6
Ditto, sec. 6.3 v. 3 amp. 10/6
GENERAL PURPOSE LOW VOLTAGE, 2a,
3.4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/6
AUTO TRANSFORMERS, 150 w. 22/6
0, 120, 200, 230, 250 v., 500 w. 22/6

ALADDIN FORMERS and core, 1in., 8d.; 1in., 10d.
0.3in. **FORMERS** 59/78 and Core, ITA/2, 1in. sq. x
2in. and 1in. sq. x 13in., 2/- ea. with cores.

SOLON Soldering Iron, 200 or 240 v. 25 w. 24/-

MARSH DROPPERS, 3in. x 1in. Adl. Sliders,
0.3 amp. 1,000 ohms, 4/6. 0.2 amp., 1,000 ohms, 4/6.

LINE CORE, 0.25, 0.5, 0.8 ohms per ft., 0.2 amp., 100
ohms per ft., 2 way, 1/2 ft., 3-way, 1/4 ft. per ft.

LOUDSPEAKER P.M. 3 OHM, 21/6, 19/6, 16/6, 13/6,
8in. Pleasey, 19/6, 8in. 21/6, 19/6, 16/6, 13/6, 10/6,
Rola, 18/6, 10 x 8in., 27/6. 10in. 30/
4in. Hi-Fi Tweeter, 25/-, 12 in. ROLA, 30/
STATORIAN HF1012, 10in. 3 to 15 ohms, 10w, 95/-
12in. Baker 15 watt 3 ohms or 15 ohms, 10w, 95/-
CRYSTAL DIODE G.E.C. 2/-, GEX34, 4/-

HIGH RESISTANCE PHONOS. 4,000 ohms, 15/- pr.

MIKE TRANSF. 50 : 1, 3/9 ea.: 100 l. Potted, 10/8.

SWITCH B CLEANER. Fluid squirt sput. 4/3 tin.

TWIN GANG TUNING CONDENSERS 365 pF

miniature 1in. x 1in. x 1in., 10-15, 500pF Standard

with trimmers, 9/-; midget, 7/8 with trimmers, 9/-

SINGLE, 30 pF, 75 pF, 100 pF, 160 pF, 5/6.

Gold dielectric 100, 300, 500 pF 3/6.

New and Boxed VALVES 90-day Guarantee.

1R6	7/8	2K8G	7/8	EABCN0	9/6	HABC0	9/6
185	7/8	6L6G	10/-	EB19	9/6	EB19	12/6
1T4	6/-	6N7M	10/-	EB20	9/6	HV2A	8/6
2X2	3/6	6Q7G	9/6	EBC33	10/-	HV2A	8/6
384	7/8	6SA7	10/-	EBC41	8/6	MU14	9/6
3V4	7/8	6SA7	10/-	P01	9/6	10/-	9/6
5U4	7/8	6SA7N	8/6	ECC84	9/6	PC84	9/6
5Y3	7/8	6VG6	9/6	ECC84	9/6	PC84	9/6
5Z4	9/6	6X4	10/-	ECL82	10/-	PC84	9/6
6AM6	5/-	6X5	6/6	EP39	5/6	PL82	11/6
6AB8	5/-	12AT27	8/-	EF41	9/6	PY80	10/6
6BE6	7/8	12AU7	8/-	EF50	5/6	PY81	9/6
6BH6	9/6	12AX7	8/-	EF80	8/-	PY82	7/6
6BW6	9/6	12BE5	8/-	EF86	12/8	SP61	3/6
6D6	6/-	12K7	6/6	EF91	5/-	1BC41	9/6
6FG6	7/8	12Q7	6/6	EF92	5/6	EHC42	9/6
6H6	9/6	12M5	10/-	EL32	5/6	UFC41	9/6
6J5	5/6	3826	9/6	EL32	5/6	UFC41	9/6
6J6	5/6	3824	7/8	EL44	8/6	UFC41	9/6
6J7G	5/6	808	10/-	EL44	8/6	UFC41	9/6
6KG6T	8/6	807	5/6	EZ40	7/8	U22	8/6
6KG7	8/6	954	1/8	EZ80	7/8	VR105	9/6
6KG7K	5/6	EA50	1/6	E1148	1/6	VR150	9/6

"REGENT" 4 VALVE

"96"

RANGE
VALVES
KIT PRICE
£6. 6. 6.
Carr. 4/-

**PRINTED CIRCUIT
BATTERY PORTABLE KIT**

Medium and long wave. Powerful
7 x 4in. high Flux Speaker. T.C.C.
Printed Circuit and condensers. Components
of finest quality clearly identified
with assembly instructions. Osmor
Ferrite Aerial Coils. Rexine covered
attache case cabinet. Size 12in. x 8in. x
4in. Batteries used B126 (L5512) and
AD35 (L5040), 10/- extra. Instructions
9d. (free with kit). Mains UNIT ready
made for above, 39/6. Sold separately.

**TV REPLACEMENT
LINE OUTPUT
TRANSFORMERS**

FROM 45/- ea. Most makes avail-
able. S.A.E. with all enquiries.

LINE BLOCKING TRANSFORMERS, from 10/-.
from 10/-.
from 13/6.

FRAME OUTPUT TRANSFORMERS, from 27/6.

NEW MULLARD TRANSISTORS
Audio 0.021 ... 8R 10/6
0.021 ... 8/6 OC45 9/6
Sub Miniature Electrolytes, 15 volt.
1, 2, 4, 5, 8, 25, 50, 100 ohms, 2/6 each.
Weyrad Printed Circuit Components Stock.
Book 2/-, 7 x 4 in. Speaker 35 Ω 25/-.

HIGH GAIN TV PRE-AMP KITS

BAND I BBC

Tunable channels 1 to 5. Gain 18dB.
ECC44 valve. Kit price 29/6 or 49/6 with power
pack. Details D1 (PCC44 valves if preferred.)

BAND III ITA—Same prices.

Tunable channels 8 to 13. Gain 24dB.

ECC44 valve. (PCC44 valves if preferred.)

CRYSTAL MIKE INSERT by Acoes
engineered. Size only 1in. by 1in. 8/-

ALUMINIUM CHASSIS, 18 s.w.g.
With 4 sides riveted corner and fixing
holes, 2 1/2in. sides, 4/6 x 9 in., 5/6 x
11 x 7in., 6/6; 13 x 9in., 5/6; 14 x 11in., 10/6;
15 x 14in., 12/6; 18 x 16 x 3in., 16/6.

ALUMINIUM PANELS, 18 s.w.g., 12in. x 12in.,
4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/3.

JASON F.M. TUNER COIL SET, 29/-.
H.F. coil, aerial coil. Oscillator coil. Two L.F. trans.
10.7 Mcs. Ratio Detector and heater choke.
Circuit book using four GAN46, 2/6.

COMPLETE JASON F.M. KIT, FMT1, with
set of 4 valves, etc., £6.50.

BBC TRANSISTOR RADIO. Med. and Long
Wave. Two transistors and diode. Complete
kit, 32/6, phones 7/8 extra. Deaf Aid Earpiece
with Special Lead, 10/8. Details 6d.

45 Kc/s. SIGNAL GENERATOR. Total cost
100. Uses H.F.O. Unit ZA 3003 ready made.

POCKET SIZE 21 x 4 in.

Slight modifications required, full instructions
supplied. Battery 7/6 extra 69 v. + 1 1/2 v.

I.F. TRANSFORMERS 776 pair.
465 Kc/s. Slug Tuning. Miniature Can. 1 1/4 x
1in. High Q and good bandwidth. Data sheet
supplied.

RECORD PLAYER BARGAINS

BSR
The British Scientific Research Society
Monarch
World's First Liquid Amplifier
4 Speed Auto-changers, B.S.R., U.A.14 27.10.0
Collaro Auto-changer 27.10.6
Garrard Model 210, GCS Head 27.10.0
4 speed Single Players, EMI 27.10.0
Garrard TA Mk.II, GCS Head 27.10.0
Garrard Model 4SP GCS 27.10.7
Garrard Stereo Heads, 2 extra.
Suitable player cabinets (except 4 H.F.) 49/6
Amplifier player cabinets (except 4 H.F.) 63/-
2-valve amplifier and 6in. speaker 79/6
3-valve amplifier and 6in. speaker 95/-
Wired and tested ready for use with above.
All sapphire stylus available from 6/-.

Volume Controls 80 ohm COAX
Long spindles. Guaranteed 1 year. Midget
5K ohms to 2 Meg. No 8w. D.P.W. 3/-
4/6 Linear or Log Spindle

COAX PLUGS 1/-
LEAD SOCKET 2/-
OUTLET BOXES 4/6
BALANCED TWIN FEEDER 1/- 6d. 80 ohm
DITTO SCREENED per fd. 1/- 80 ohm only.
WIRE-WOUND POTS, 3 WATT. Present
TV Type. All value 25 ohms to 50 k. 3/- ea.
30 K., 50 K., 100 K. (Carbon 30 K. to 2 meg. 3/-).
WIRE-WOUND 4 WATT. Pots Long Spindle
Values. 50 ohms to 50 K. 6/6; 100 K. 7/6;
CONDENSERS. New Stock. 0.001 mfd. 7 kV.
T.C.C. 5/6; Ditto, 20 kV. 9/6; 7 kV. 9/6;
Tubular 5/6; 0.001 mfd. 0.1 mfd. 9/6; 0.1, 1/1.
0.25, 1/6; 0.5/6; 1/8; 1/10; 1/20; 1/50; 1/100; 1/200 v.
0.1/1,000 v. 1/9; 0.1 mfd. 2,000 ohms, 3/6.
CERAMIC CONDS. 500 v. 0.3 pF to 0.01 mfd. 9/6.
SILVER MICA CONDENSERS, 10% pF to 500 pF.
1/- 1/10,000 pF to 3,000 pF. 1/3. Close tolerance
(± 1 pF). 1.5 pF to 47 pF. 1/6. Ditto 1% 50 pF to
815 pF. 1/9; 1,000 pF to 3,000 pF. 2/-.

NEW ELECTROLYTICS. FAMOUS MAKES

TUBULAR TUBULAR ... CAN TYPES
1/350v. 2/- 50/350v. 5/6 16/450v.
2/450v. 2/3 100/25v. 2/- 52/350v. 4/-
4/450v. 2/3 250/25v. 5/6 100/270v. 5/6
8/450v. 2/3 500/12v. 3/- 2,500/3v. 5/6
8/500v. 2/9 8/450v. 3/6 5,000/6v. 5/6
16/450v. 3/- 8/16/450v. 3/6 32/34/350v. 5/6
16/500v. 4/- 8/16/500v. 5/6 32/32+32/350v. 7/-
32/450v. 3/9 16/16/450v. 4/3 50/50/350v. 5/6
32/25v. 1/9 16/16/500v. 6/- 64/120/350v. 11/6
50/50v. 2/- 12/32/32/350v. 4/6 10/275/12/6
RECTIFIERS SELENIUM 300 v. 85 mA, 7/6.
CONTACT COOLED 250 v. 200 mA, 21/- 300 mA, 8/6.
8/8, 200 mA, 21/- 300 mA, 8/6.
COILS Wairite "Type 1" type, 3/- each. Osmor Midget
"Q" type ad. dust cover, 4/- All ranges.
TELETRON, 4/- Med. T.R.A., with reaction, 3/6.
FERRITE ROD AERIALS M.W. 9/6; M. & L. 12/6.
FERRITE COILS A.H.F. 7/- pair. H.F. CHOKES, 2/6.
FERRITE ROD, 8in. x 3in. dia. 2/6.
FULL WAVE BRIDGE SELENIUM RECTIFIER,
2, 6 or 12 v. 11 amp., 8/8; 2, 8, 11/8; 4, 6, 17/8.
CHARGER TRANSFORMERS. Tapped input 200/
250 v. for charging at 2, 6 or 12 v., 14 amps, 15/0,
2/6, 17/6; 4 amps. 22/6. Circuit include.
VALVE AND TV TUBE equivalent books, 9/6.
TOGGLE SWITCHES, S.P. 2/-, D.P. 3/6. D.P.D.T. 4/-
WAVECHANGE SWITCHES
8 p. 4-way 2 wafer long spindle ... 6/6
8 p. 4-way, 3 p. 2-way short spindle ... 2/6
2 p. 6-way, 4 p. 3-way 1-way long spindle ... 3/6
3 p. 4-way, 3 p. 3-way long spindle ... 3/6
VALVEHOLDERS, Pax Int. 4d. EF50, EA50,
6d. B12A, CRT, 1/3, Eng. and Am. 5/6 and
5 in. 1/2. **MOULDED MAZDA** 1 in. Oct. 6d.
7TG, BZA, B8G, B9A, 9d. B1G, with can, 1/6.
B9A with can, 1/9. **CERAMIC EF50**, RTG, B9A.
Int. Oct. 11/6. **SCANS** BTG, B9A, 1/-, 1/2.
SPAKER FRET GOLD CLOTH, 17in., 25in., 5/6-
25in. x 36in., 10/-, Tyrex, 53in. wide, 10/-, 26in.
wide, 5/6. Green or red. Samples 8.A.E.

OUR ONLY ADDRESS
337 WHITEHORSE RD.,
WEST CROYDON

RADIO COMPONENT SPECIALISTS
Post and Packing 1/-, over £2 free. (Export post Extra.) C.O.D. 116. (Wed. 1 p.m.) THO 1665. Buses 133 or 68