

TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS


20p

FEBRUARY
1972

COLOUR



CAMERAS

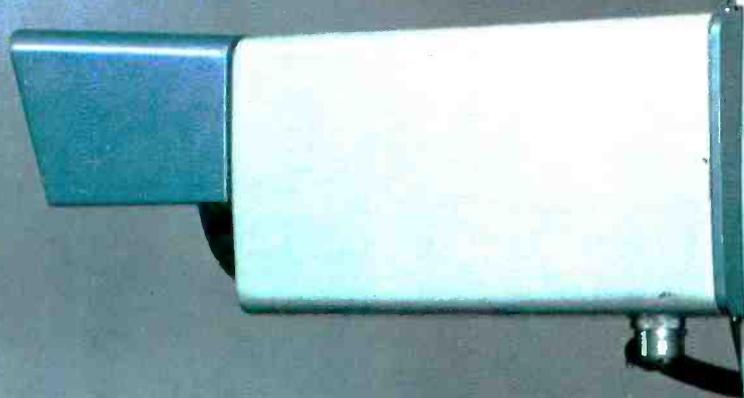

Also:

THE DO-BE OSCILLATOR
SIMPLE OUTDOOR UHF AERIAL
THE SANYO 10-T120U PORTABLE

STEPHENS

ELECTRONICS,
24 PARTON ROAD,
AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded.

GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE

1 YEAR'S GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS

AZ31	50p	ECF80/2	471p	EL803	85p	PC685	421p	PY83	50p	UL41	571p	6AR5	321p	6EJ7	35p	6SK7	321p	12BE6	321p	30FL1	771p
AZ50	80p	ECF86	55p	EL821	55p	PC688	70p	PY88	41p	UL84	51p	6AR6	321p	6EJ7	35p	6SK7	321p	12BE6	321p	30FL13	90p
CB11	80p	ECF35	671p	ELL80	70p	PC689	61p	PY300	£1.00	UM80/4	45p	6AR5	35p	6F1	70p	6SN7GT	30p	12BY7	50p	30FL14	85p
CB13	85p	ECF42	66p	EM34	80p	PC689	61p	PY500	80p	UY41	40p	6AN7G	80p	6F8	40p	6SN7	40p	12K5	50p	35A3	50p
CY31	35p	ECF81	51p	EM71	621p	PC689	61p	QQT'02-622-10	34p	UY85	34p	6AT9	45p	6F6G	25p	6NR7	371p	12K7GT	35p	35A5	55p
DAF91	41p	ECF83	40p	EM80	40p	PC682	521p	QQ'03-10	U25	U26	75p	6AU6	30p	6F12	221p	6T4GT	62p	12MC7	35p	35C3	85p
DAF96	41p	ECF84	471p	EM81	421p	PCF84	471p	QV03-12	65p	U191	721p	6BA6	471p	6F13	35p	6T8	35p	12NS7	35p	35D5	35p
DF91	45p	ECL80	40p	EM84	371p	PCF86	51p	R19	65p	U193	41p	6BE6	60p	6F14	60p	6V6GT	321p	12SH7	25p	35L64T	471p
DF96	45p	ECL82	49p	EM87	55p	PCF200-1	81p	R20	75p	U301	85p	6BH6	421p	6F15	55p	6X4	25p	12SJ7	25p	35W4	25p
DK91	571p	ECL83	571p	EN91	321p	PCF801	61p	SC2150A	75p	W29	55p	6BJ6	421p	6F18	40p	6X5GT	271p	12SK7	40p	35Z3	55p
DK96	571p	ECL86	49p	EY31	321p	PCF802	61p	T22	60p	Z759	£1.221	6BK7A	50p	6P22	321p	6X8	55p	12SL7GT	40p	35Z4G	25p
DL82	371p	ECL800	49p	EY80	45p	PCF805	621p	T22	62.50	OA2	321p	6BL8	35p	6P23	771p	6Y6G	60p	12SN7GT	40p	35Z5GT	371p
DL94	371p	EY81	81p	EY81	81p	PCF806	61p	T22	62.50	OA3	45p	6B55	421p	6P24	671p	7Y4	60p	12SN7	40p	50A5	85p
DL96	46p	EF39	521p	EY83	55p	PCF808	671p	U1820	671p	O18	45p	6B6	40p	6P25	75p	9BW6	421p	12SR7	321p	50B5	35p
DM70	321p	EF80	40p	EY86	40p	PCF820	70p	U20	671p	O82	321p	6B6	40p	6P26	35p	10C2	50p	1487	80p	50C5	35p
DF867	40p	EF83	50p	EY87	421p	PCL82	51p	U25	75p	O83	50p	6BQ5	25p	6P27	35p	10D1	40p	20D1	45p	50L6GT	40p
EY802	421p	EF85	41p	EY88	421p	PCL83	61p	U26	75p	O83	35p	6BR7	75p	6P28	70p	10D1	40p	20D1	45p	50L6GT	40p
E55L	£2.75	EF86	66p	EZ35	271p	PCL84	51p	U31	45p	O1C	45p	6BR8	85p	6P29	321p	10D2	40p	20L1	£1.00	83A1	90p
ES8CC	40p	EF89	49p	EZ80	45p	PCL85	521p	U31	£1.50	3Q4	40p	6BW6	821p	6P30	35p	10F1	90p	20P1	50p	83A2	371p
E130L	£4.50	EP91	421p	EZ41	271p	PCF806	61p	U50	40p	3V4	40p	6BX6	60p	6P31	35p	10F4	90p	20P3	60p	90AT	£2.40
E180F	50p	EP92	50p	EZ80	271p	PD500	£1.521	U52	30p	3V4	40p	6BZ6	321p	6P32	671p	10L1	40p	20P5	£1.00	90CU	£1.25
EAF80	521p	EP93	471p	EZ81	271p	PFL200	74p	U76	25p	5R4GY	55p	6BZ6	321p	6P33	671p	10L1	40p	20P5	£1.00	90CU	£1.25
EAF42	50p	EP94	771p	EZ90	25p	PL36	64p	U78	25p	5U4G	30p	6C4	30p	6K6GT	50p	10DL11	55p	20P5	45p	807	471p
EAF30	55p	EP95	621p	GL80C	£5.00	PL38	90p	U191	75p	5U4C/B	371p	6C5GT	35p	6K7	321p	10P13	55p	25L6GT	371p	81A1	£1.50
EB41	471p	EP183	50p	GY301	671p	PLA1	81p	U201	35p	5V4G	40p	6C6GT	£1.40	6K8G	30p	10P14	£1.00	25Z4G	30p	612A	£3.25
EB8C1	35p	EP184	35p	HL82	35p	PLA2	621p	U281	40p	5Y3GT	30p	6C4A	271p	6K23	50p	12A85	50p	25Z64T	50p	813	£3.75
EB90	471p	E280F	£2.10	GZ31	30p	PL82	36p	U282	40p	6Z7	521p	6C6	271p	6K25	75p	12AC6	371p	30A3	40p	866A	70p
EBF80	40p	EF800	£1.00	GZ32	471p	PL83	51p	U301	571p	824GT	40p	6C8C	271p	646GT	45p	12AC6	371p	30C15	75p	5642	60p
EBF83	40p	EF804	£1.00	GZ33	40p	PL84	41p	U403	50p	630L2	75p	6C106A	£1.15	671	321p	12A16	371p	30C15	75p	5642	60p
EBF89	40p	EP811	75p	GZ34	55p	PL900	821p	U404	371p	6AB4	321p	6C67	45p	6L18	30p	12A15	40p	30C17	80p	6080	£1.371
EB91	26p	EL34	521p	HK30	321p	PL504	85p	U601	£1.00	6AF4A	471p	6C16	55p	6L1D20	321p	12A25	40p	30C18	75p	6146	£1.50
EC53	50p	EL36	471p	HL82	35p	PL505	£1.45	U601	40p	6ABC90	521p	6AG7	371p	6C6V4	50p	6N7GT	35p	30F12	921p	6146B	£2.371
EC86	60p	EL41	55p	HL94	40p	PL508	£1.00	U601	40p	6BF89	61p	6C16	621p	6P1	60p	12A76	25p	30F11	75p	6267	321p
EC88	60p	EL42	571p	KT66	£1.371	PL509	£1.54	U601	40p	6C17	49p	6C35	40p	6P23	£1.05	12A76	75p	30F11	75p	6267	321p
EC90	30p	EL81	50p	KT88	£1.66	PL502	86p	U601	40p	6AK5	46p	6C37	50p	6P28	62p	12A76	75p	30FL3	50p	6386	£1.25
EC92	321p	EL83	41p	N78	£1.05	PL505	86p	U601	40p	6AK6	571p	6D3	40p	6Q7	371p	12A77	45p	30FL4	771p	6939	£2.10
EC93	471p	EL85	421p	PABC80	40p	PY33	621p	UCH81	54p	6AL3	421p	6DC6	671p	6R7G	35p	12AX7	30p	30L1	45p	7199	75p
EC94	40p	EL86	421p	PC86/8	51p	PY80	321p	UCL92	61p	6AL5	16p	6DK6	421p	6R2	40p	12AY7	671p	30L15	85p	7360	£1.80
EC98	40p	EL90	321p	PC86/8	51p	PY80	321p	UCL92	61p	6AL5	16p	6DQ6B	75p	6R4	371p	12BA4	50p	30F12	921p	7586	£1.25
EC98/5	421p	EL91	25p	PC86/8	51p	PY800	41p	UF41/2	55p	6AM6	221p	6D84	40p	6S7	321p	12BA5	321p	30P18	35p	9002	321p
EC98/8	55p	EL95	35p	PC97	41p	PY801	41p	UF80/5	371p	6AQ5	321p	6E8A	55p	6S7	321p	12BA6	321p	30P18	35p	9002	321p
E88CC	621p	EL360	£1.15	PC84	46p	PY802	35p	UF89	41p	6AQ6	50p	6E17	321p	6J7	371p	12BA7	321p	30P19	75p	9003	50p

CATHODE RAY TUBES

New and Budget tubes made by the leading manufacturers. Guaranteed for 2 years. In the event of failure under guarantee, replacement is made without the usual time wasting forms.

Type	New	Budget	Type	New	Budget
	£	£		£	£
MW36-20	£4.50	£2.50	A50-120W/R	CME2013	£10.85
MW36-21	£4.50	£2.50	AW53-80	CME2101	£8.93
MW43-69Z	CRM171		AW53-88	CME2101	£8.25
	CRM172	£6.60	AW59-50		
MW43-80Z	CRM173	£6.60	A59-91	CME2303	£9.58
AW43-80Z	CME1702	£6.60	A59-15W	CME2301	£7.20
	CME1703	£6.60		CME2302	
	CME1706	£6.60	A59-11W	CME2305	£9.58
	C17A	£6.60	A59-13W	CME2306	£13.65
	C17AF	£6.60	A59-16W	CME2306	£10.97
	CME1705	£6.60	A59-23W	CME2305	£12.80
AW43-88	CME1705	£6.60	A50-23W/R	CME2413	£13.50
AW47-90			A61-120W/R	CME2413	£13.50
AW47-91	A47 14W	£5.95	A65-11W	CME2413	£16.50
A47 14W	CME1901	£5.95			
	CME1902	£5.95	COLOUR TUBES		
	CME1903	£5.95	A49-191X	19 inch	£52.50
	C19AH	£5.95	A56-120X	22 inch	£57.50
147 13W	CME1906	£10.27	A63-11X	25 inch	£62.50
A47-11W	CME1905	£8.88	PORTABLE SET TUBES		
A47-26W	CME1905	£8.88	TSD217	P11-50	£11.50
A47-26W/R	CME1913R	£9.33	TSD282	P11-50	£11.50
			A28-14W		Not supplied
					£7.75
					£8.00

A discount of 10% is also given for the purchase of 3 or more tubes at any one time. All types of tubes in stock. Carriage and insurance 75p anywhere in Britain.

TRANSISTORISED UHF TUNER UNITS

NEW AND GUARANTEED FOR 3 MONTHS

Complete with Aerial Socket and wires for Radio and Allied TV sets but can be used for most makes.

Continuous Tuning, £4.50; Push Button, £5.00.

SERVICE AIDS

Switch Cleaner, 55p; Switch Cleaner with Lubricant, 55p; Freezer 621p. P. & P. 77p per item.

PLUGS

Jack Plugs and Sockets
Standard Plugs 19p
Standard Sockets 121p

	Co-Axial Plugs	Belling Lee (or similar type)	61p
	Add 2p per doz. p. & p.		
LINE OUTPUT TRANSFORMERS			
G.E.C. BT454	£4.75	G.E.C. 2028	£4.75
G.E.C. BT456	£4.75	G.E.C. 2041	£4.75
G.E.C. 2010	£4.75	G.E.C. 2000 Series	
G.E.C. 2013	£4.75	Philips 19TG	£4.75
G.E.C. 2014	£4.75	Pye Mod. 36	£4.75
G.E.C. 2018	£4.75	Pye Mod. 40	£4.75
G.E.C. 2043	£4.75	Thorn 800-850	£4.75
G.E.C. 2048	£4.75		

STYLISH—BRITISH MANUFACTURED

All types in stock.
Single Tip "S" 13p Double Tip "S" 33p
Single Tip "D" 37p Double Tip "D" 47p
"S" = Sapphire "D" = Diamond

CARTRIDGES

	Inc. P.T.	each	B.S.R.	Inc. P.T.	each	RONETTE	Inc. P.T.	each
ACOS		£0.63	X3M	S/S	105	S/S	90p	
GP79		£1.05	X3H	S/S	106	S/S	99p	
GP91-18c -1		£1.05	X5M	S/S	106	S/S	70p	
GP91-28c		£1.05	X5H	S/S	106	S/S	70p	
GP91-38c		£1.05	SX5M	S/S	105	D/S	£1.11	
Suitable to replace			SX5H	S/S	106	D/S	£1.11	
TC8		£1.32	SX5M	D/S	106	D/S		

TV'S 19" NOW £11.95

TWO YEARS GUARANTEE ALL MODELS

405/625: 19" £29.95; 23" £39.95

FREE CATALOGUE

DAILY DEMONSTRATIONS FOR PERSONAL SHOPPERS



COMPONENTS

MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 15p.

Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p.

VHF/FM Tuners: 95p. 88-108 megs. takes ECC85 valve (extra). Post 15p.

Precision Tape Motors: £1.95. 200 250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free.

Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p.

Transistors 15p each. Post free. AC126, AC128, AF114, AF17, OC45, OC71, OC81, OC81D.

Valve ELL80 50p. Only stock in the country.

Pats.: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg. 100 KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg.

HI-FI VALUE


1. GARRARD SP25 MK III £11.50 P. & P. 50p.

2. TEAK PLINTH & TINTED COVER £4.95. P. & P. 35p.

3. SONOTONE 9TAHC CART-RIDGE £2.50. P. & P. 5p.

BARGAIN PACKAGE—1, 2, 3 £17.95. P. & P. 85p.

TV TUBES REBUILT GUARANTEED 2 YEARS

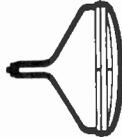

14" £3.95; 17" & 19" £5.95;

21" & 23" £6.45

Exchange Bowls carr. 55p.

TEAK HI-FI STEREO CABINETS £14.95

Brand new 44" wide x 16" deep x 18" high with legs. A superb piece of furniture. Carriage £1. WHILE STOCKS LAST.

DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12
Phone 01-478 6001-2-3 Stamp for Free List

"NO




I'D RATHER HAVE A MINITEST"

The SEI MINITEST has made a remarkable impact in the pocket-sized multi-range meter market, by making itself a firm favourite with discerning people in the industry. Let's look into the reasons why.

First, the appearance. Diminutive, neat, wipe-clean cycloc case with shock and magnetic field proof steel liner. Controls are simple and easy to use.

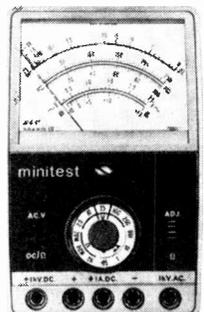Second, the range. The Minitest measures a.c. and d.c. voltages d.c. current and resistance over 20 ranges to a sensitivity of 20,000 and 2,000 ohms per volt d.c. and a.c. respectively. Third, high voltage probes. These extend the range to 25 or 30kV d.c. Little wonder the Minitest is preferred!



SALFORD ELECTRICAL INSTRUMENTS LTD
Peel Works, Barton Lane, Eccles, Manchester M30 0HL
Telephone 061-789 5081 Telex 667711
A Member Company of GEC Electrical Components Ltd.



VALVES

SAME DAY SERVICE
NEW! TESTED! GUARANTEED!

SETS 1R5, 1R5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for £1.02. DAF96, DF96, DK96, DL96, 4 for £1.48.

1R5	-88	30C17	-78	EABC80	-88	EM81	-41	PCL84	-84	UBC41	-58
1R5	-82	30C18	-61	EAF42	-60	EM84	-82	PCL85	-88	UBF80	-84
1T4	-16	30F6	-64	EB41	-40	EM87	-84	PCL86	-88	UBF89	-88
3B4	-88	30FL1	-61	EB91	-10	EY61	-83	PCL88	-65	UCB84	-82
3V4	-87	30FL12	-88	EBC33	-40	EY86	-89	PCL800	-75	UCB85	-85
5U4G	-81	30FL14	-68	EB41	-54	EZ40	-48	PENA4	-77	UCF80	-88
5V4G	-84	30L1	-89	EBC90	-82	EZ41	-48	PEN36C	-70	UCH42	-88
5Y3GT	-88	30L15	-67	EBF80	-82	EZ80	-82	PFL200	-52	UCH81	-82
5Z4G	-84	30L17	-67	EBF89	-89	EZ81	-83	PL36	-49	UCL82	-82
6/30L2	-64	30P4	-57	ECC81	-17	QZ30	-84	PL81	-44	UCL83	-55
6AL5	-11	30P12	-72	ECC82	-80	QZ32	-40	PL81A	-47	UF41	-66
6AM6	-18	30P19	-57	ECC83	-58	QZ34	-48	PL82	-31	UF89	-80
6AQ6	-82	30PL1	-60	ECC85	-84	KT41	-77	PL83	-83	UL41	-67
6AT6	-80	30PL13	-75	ECC804	-64	KT61	-55	PL84	-80	UL44	£1.00
6AUB	-80	30PL14	-65	ECC80	-87	KT66	-78	PL500	-83	UL84	-80
6AUB6	-80	30PL15	-90	ECC82	-86	LN319	-83	PL504	-83	UM84	-82
6BP6	-81	35L6GT	-45	ECH35	-80	LN329	-72	PM84	-88	UY41	-82
6BJ6	-41	35W4	-85	ECH42	-88	LN339	-83	PX25	-85	UY85	-85
6BW7	-82	35Z4GT	-85	ECH81	-89	N78	-87	PY22	-85	VP4B	-77
6F14	-40	807	-45	ECH83	-40	P61	-40	PY33	-55	X78	£2.75
6F23	-68	6063	-62	ECH84	-86	PABC80	-84	PY81	-85	X79	£2.75
6F25	-53	AC/VP2	-77	ECL80	-80	PC86	-47	PY82	-82	Z77	-82
6K7G	-12	B349	-65	ECL82	-81	PC88	-47	PY83	-82	Transistors	
6K9G	-17	B729	-82	ECL86	-88	PC96	-42	PY88	-83	AC107	-17
6Q7G	-85	6CH85	-67	EP88	-88	PC199	-89	PY600	-84	AC127	-18
6SN7GT	-80	CY31	-80	EF41	-80	PC900	-81	PY801	-81	AD140	-87
6V6G	-88	DAF91	-82	EF80	-82	PC884	-89	R19	-80	AF115	-20
6V6GT	-88	DAF96	-86	EF85	-88	PC885	-85	R20	-86	AF116	-20
6X4	-83	DF33	-88	EF86	-80	PC888	-40	U25	-84	AF117	-20
6X5GT	-88	DF91	-16	EF89	-88	PC889	-45	U26	-86	AF118	-48
10P13	-68	DF96	-86	EF91	-18	PC890	-48	U47	-84	AF125	-17
12AT7	-17	DH92	-80	EF98	-86	PC895	-66	U49	-68	AF127	-17
12AU6	-80	DK32	-83	EF183	-88	PC890	-88	U50	-88	OC26	-85
12AU7	-80	DK91	-88	EF184	-81	PC892	-81	U52	-81	OC44	-12
12AX7	-82	DK92	-88	EH90	-85	PC896	-45	U78	-84	OC45	-12
19BG6G	-87	DK96	-88	EL33	-55	PC890	-58	U191	-59	OC71	-12
20P2	-67	DL35	-40	EL34	-45	PCF801	-88	U193	-42	OC72	-12
20P3	-77	DL92	-88	EL41	-54	PCF802	-48	U251	-84	OC75	-12
20P4	-82	DL94	-87	EL84	-82	PCF805	-81	U301	-88	OC81	-12
28L8GT	-19	DL86	-88	EL90	-88	PCF806	-66	U329	-66	OC81D	-12
28U4GT	-57	DY86	-84	EL95	-83	PCF808	-88	U801	-80	OC82	-12
80C1	-88	DY87	-84	PL500	-82	PCL82	-82	UABC80	-82	OC82D	-12
80C15	-88	DY802	-88	EM80	-41	PCL83	-67	UAF42	-81	OC170	-88

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Post/Packing on 1 valve 6p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

for men of vision rebuilt T.V. tubes

	Current types		
17"	£4.75	21"	£5.50
19"	£5.00	23"	£6.00
	Panorama & Rimguard types		
19"	£7.00	23"	£9.00
	Twin panel		
19"	£7.50	23"	£9.50

Cash or P.O. with order no C.O.D. Carriage free in England, Scotland, Wales. Add 75p for carriage Northern Ireland. For all enquiries please send S.A.E. Each tube fitted with new electron gun assembly. Fully guaranteed for two years against any fault except breakage.


Special terms for Hospitals, Orphanages, Old People's homes.

Manufactured in our own factory backed by over 20 years' experience in the field of electronics. Callers always welcome (by appointment) at

k.s.t. ltd.

Providence Mills, Viaduct Street,
Stanningly, Nr. Leeds, Yorks.

REBUILT TUBES!

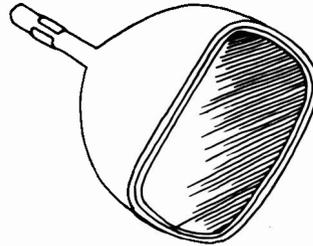

**YOU'RE
SAFE
WHEN YOU
BUY FROM
RE-VIEW!**

HERE IS WHAT YOU PAY:

12in.	£4.75	21in.	£7.25
14in.	£5.00	23in.	£8.50
15in.	£5.25	Twin Panel & Rimguard	
17in.	£5.25	19in.	£8.00
19in.	£5.87	23in.	£10.50

Cash or cheque with order, or cash on delivery

COLOUR TUBES AVAILABLE

Discount for Trade

- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for two years against all but breakage.
- ★ Each tube is delivered free anywhere in the U.K. and insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

RE-VIEW ELECTRONIC TUBES

237 London Road, West Croydon, Surrey
Tel. 01-689/7735

AUTO-TRANSFORMERS

0-240. 110v. 50 Cycles. For use with non-motorised appliances.

0-240. 100v. For use with 60-Cycle motorised appliances.

RANGE 1.

Fully Shrouded. Complete with two-pin terminal outlet. Fitted with 6 ft. 240v. mains lead. (Where starred, fitted two 2-pin terminal outlets.)

VALUES

80w.....	£2
150w.....	£2.50
300w.....	£3.40
500w.....	£5
800w.....	£6.50
1,000w.....	£7.50*
1,500w.....	£9*

Plus postage & packing	25p
Plus postage & packing	25p
Plus postage & packing	25p
Plus postage & packing	35p
Plus postage & packing	35p
Plus postage & packing	50p
Plus postage & packing	50p

Also available
alternative style.
Fully shrouded.
Terminal block
connections.
0-100-110-220-240v.

RANGE 2

Complete with carrying case. Mains indicator light. Two 3-pin American sockets. Fitted with 6 ft. 240v. mains lead, 13 amp. plus attached.

VALUES

1,000w.....	£10.00
1,500w.....	£12.50
1,750w.....	£14
2,250w.....	£16.50
3,000w.....	£26.00
5,000w.....	£30

Plus postage & packing	60p
Plus postage & packing	60p
Plus postage & packing	75p
Plus postage & packing	£1
Plus postage & packing	£1.25
Plus postage & packing	£2

OPEN TYPE ONLY. TERMINAL BLOCKS OR FLYING LEADS. OPTIONAL.

THESE TRANSFORMERS ALWAYS IN STOCK

OLYMPIC TRANSFORMERS LTD.

Transformer Manufacturers,
224, Hornsey Road, LONDON, N.7.

TELEPHONE: 01-607-2914.

HOURS OF BUSINESS:

Weekdays—8 a.m.-6 p.m.

Saturday—10 a.m.-2 p.m.

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone 01-722-9090

0A2	0-30	6AR6	1-00	6F25	0-54	7H7	0-28	20L1	0-98	8A3A	0-40	DF91	0-14	EFB83	0-38	EF183	0-28	HL21D1	0-50	PCF806	0-57	PZ30	0-48	UY9	0-40
0B2	0-30	6AT6	0-18	6F28	0-60	7R7	0-65	20P1	0-50	90A0	3-38	DF96	0-34	EFB89	0-27	EF184	0-29	HL21D2	0-50	PCF808	0-68	QV03/10	0-22	UY12	0-22
0Z4	0-25	6AU6	0-20	6F32	0-15	7V7	0-25	20P3	0-79	90AV	3-38	DH63	0-27	FBL21	0-60	FPF60	0-50	HN309	1-40	PCF2000	0-62	Q878/20	1-20	UY1N	0-50
1A3	0-25	6AV6	0-28	6GH8A	0-60	7Z4	0-50	20P4	0-80	90C1	1-70	DH76	0-28	EC54	0-60	EH90	0-38	HVR2	0-53	PCF82	0-32	UY41	0-38		
1A5	0-25	6AW8A	0-54	6GK3	0-50	9BWB	0-50	20P5	1-00	90C2	1-68	DH77	0-18	EC96	0-60	EL32	0-18	HVRA20	0-53	PCF83	0-58	UY85	0-25		
1A7GT	0-35	6AX4	0-38	6H47	0-70	91Y	0-78	25A6G	0-20	90C3	0-58	DH78	0-20	EC98	0-58	EL34	0-44	IW3	0-38	PCF84	0-34	UY10	0-45		
1B3GT	0-35	6B8G	0-13	6H6AT	0-15	10C2	0-49	25B6G	0-20	100B2	0-58	DH107	0-90	EC99	0-58	EL35	1-00	IW4350	0-38	PCF805	0-50	UY12/14	0-38		
1D5	0-38	6BA6	0-20	6J5G	0-19	10D1E7	0-50	25Y3	0-38	301	1-00	DK82	0-33	EC00	0-58	EL37	0-74	IW4500	0-38	PCF86	0-38	UY16	0-30		
1D6	0-48	6BC8	0-50	6J3GT	0-20	10F9	0-45	25Y3G	0-43	302	0-83	DK40	0-55	EC01	0-58	EL38	0-74	KT9	0-40	PCF88	0-38	UY17	0-35		
1FD1	0-38	6BE6	0-21	6J6	0-18	10F18	0-35	25Z4G	0-28	303	0-75	DK91	0-26	EC02	0-58	EL39	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1G6	0-30	6BH6	0-43	6J7G	0-24	10L1D11	0-53	25Z5	0-40	305	0-83	DK92	0-35	EC03	0-58	EL40	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1H5GT	0-33	6BJ6	0-39	6J7GT	0-38	10P13	0-54	25Z6GT	0-43	306	0-65	DK96	0-35	EC04	0-58	EL41	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1L4	0-33	6BK7A	0-56	6J78A	0-50	10P14	1-00	30A3	0-43	307	0-65	DK97	0-35	EC05	0-58	EL42	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1L5	0-30	6BQ5	0-22	6K7G	0-10	12A6	0-63	30A1	0-28	1821	0-53	DL92	0-25	EC06	0-58	EL43	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1N5	0-40	6BQ7A	0-38	6K7GT	0-23	12A6C	0-40	30C15	0-60	5702	0-80	DL94	0-32	EC07	0-58	EL44	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1N5GT	0-37	6BR7	0-79	6K8AG	0-16	12A6E	0-40	30C17	0-77	5763	0-50	DL96	0-35	EC08	0-58	EL45	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1R5	0-26	6BR8	0-63	6L1	0-98	12A6E	0-48	30C18	0-60	6060	0-30	DM70	0-30	EC09	0-58	EL46	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1R4	0-22	6BS7	1-25	6L9GT	0-39	12A7E	0-23	30P1	0-65	7193	0-53	DM71	0-38	EC10	0-58	EL47	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1R5	0-20	6BW6	0-72	6L7	0-38	12A7T	0-16	30P1E1	0-60	7473	0-70	DM74/500	0-38	EC11	0-58	EL48	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1U4	0-29	6BW7	0-54	6L7A	0-44	12A7U	0-19	30P1E2	0-60	7473	0-70	DM74/500	0-38	EC12	0-58	EL49	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
1U5	0-48	6BZ6	0-31	6L9	1-38	12A7U	0-19	30P1E2	0-60	A2134	0-98	DY87	0-24	EC13	0-58	EL50	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
2D21	0-35	6C4	0-28	6L920	0-48	12A7E	0-28	30P1L4	0-68	A3042	0-75	DY82	0-35	EC14	0-58	EL51	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
2GK5	0-50	6C6	0-19	6N7GT	0-40	12A7T	0-22	30L1	0-29	AC044	1-16	DY87	0-24	EC15	0-58	EL52	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
3A4	0-25	6C9	0-73	6P28	0-59	12A7T	0-68	30L15	0-58	AC2/PEN	0-88	EB3F	1-20	EC16	0-58	EL53	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
3B7	0-25	6C17	0-63	6Q7	0-43	12B6A	0-30	30L17	0-67	0-98	EB8CC	0-60	0-98	EB8CC	0-60	EL54	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
3D6	0-19	6CBA6	0-26	6Q7G	0-27	12B6B	0-30	30P4MR	0-85	AC6PEN	0-38	E92CC	0-40	EC17	0-58	EL55	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
3Q4	0-38	6CD6G	1-06	6R7	0-48	12B7H	0-27	30P1E2	0-60	AC2	0-98	E180F	0-80	EC18	0-58	EL56	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
3Q5GT	0-35	6C08A	0-50	6R7G	0-35	12E1	0-85	30P16	0-48	DD	0-98	E182CC1	0-90	EC19	0-58	EL57	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
3S4	0-25	6CH6	0-38	6S7A7GT	0-35	12F5GT	0-30	30P19	0-98	AC PEN (7)	0-98	E1148	0-58	EC20	0-58	EL58	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
3V4	0-25	6CL6	0-43	6S7A7	0-35	12J7GT	0-33	30P4	0-58	0-98	EA30	0-18	EF42	0-33	EC21	0-58	EL59	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75	
4CB8	0-50	6CL8A	0-50	6S7GT	0-33	12K5	0-50	30P1L1	0-59	AC/TH1	0-98	EA76	0-85	EC22	0-58	EL60	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
5C6G	0-50	6CM7	0-50	6S7GT	0-33	12K5	0-50	30P1L1	0-59	AC/TP	0-98	EA8C80	0-30	EC23	0-58	EL61	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
5R4GY	0-53	6C05	0-30	6S7H	0-53	12Q7GT	0-28	30P1L4	0-65	AL60	0-78	EA9C91	0-38	EC24	0-58	EL62	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
5V4G	0-54	6C07A	0-63	6S7H	0-53	12S7A7GT	0-48	30P1L5	0-67	ARP3	0-85	EAF42	0-48	EC25	0-58	EL63	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
5Y3GT	0-26	6C12	0-35	6S7H	0-53	12S7A7GT	0-48	ATP4	0-12	ATP4	0-12	EB34	0-28	EC26	0-58	EL64	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
5Z2	0-45	6I6	0-15	6S7H	0-53	12S7A7GT	0-48	AZ1	0-40	AZ1	0-40	EB91	0-10	EC27	0-58	EL65	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
5Z4G	0-48	6DE7	0-50	6S7GT	0-38	12S7H	0-15	AZ31	0-40	AZ31	0-40	EB91	0-10	EC28	0-58	EL66	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6P30L2	0-55	6DT6A	0-60	6U4GT	0-60	12S7H	0-23	B36	0-53	B36	0-53	EB91	0-10	EC29	0-58	EL67	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6G8G	0-33	6E5	0-35	6U7G	0-53	12S7K	0-24	B36	0-53	B36	0-53	EB91	0-10	EC30	0-58	EL68	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AC7	0-15	6EW6	0-55	6V8G	0-17	12S7GT	0-50	CL35	0-80	CL35	0-80	EB91	0-10	EC31	0-58	EL69	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AG5	0-25	6F1	0-59	6V8GT	0-30	13D3	0-45	CV3	0-58	CV3	0-58	EB91	0-10	EC32	0-58	EL70	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AJ5	0-43	6F6	0-39	6X7	0-29	14T7	0-48	CY1C	0-53	CY1C	0-53	EB91	0-10	EC33	0-58	EL71	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AK5	0-25	6F6G	0-25	6X5GT	0-25	14S7	0-75	CY31	0-31	CY31	0-31	EB91	0-10	EC34	0-58	EL72	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AK6	0-30	6F13	0-33	6Y6G	0-55	19A3G	0-24	D63	0-25	D63	0-25	EB91	0-10	EC35	0-58	EL73	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AM6	0-17	6F14	0-42	6Y7G	0-63	19G6	0-50	DAC2	0-33	DAC2	0-33	EB91	0-10	EC36	0-58	EL74	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AM8A	0-50	6F15	0-65	7B6	0-58	19H1	2-00	DAF91	0-20	DAF91	0-20	EB91	0-10	EC37	0-58	EL75	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AN8	0-49	6F18	0-45	7B7	0-32	20I1	0-49	DAF96	0-33	DAF96	0-33	EB91	0-10	EC38	0-58	EL76	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AQ5	0-22	6F23	0-68	7C6	0-30	20I4	1-05	DB3	0-33	DB3	0-33	EB91	0-10	EC39	0-58	EL77	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		
6AR5	0-30	6F24	0-68	7F8	0-88	20P2	0-65	DB3	0-33	DB3	0-33	EB91	0-10	EC40	0-58	EL78	0-74	KT9	0-40	PCF88	0-65	UY18/20	0-75		

NEW VALVES!

Guaranteed and Tested
24-HOUR SERVICE

1R5	-25	DCC90	-80	EF86	-28	PCL85	-37
1R5	-15	DF91	-14	EF89	-24	PCL86	-37
1T4	-14	DF96	-35	EF91	-12	PL200	-51
384	-24	DK91	-25	EF92	-30	PL36	-47
3V4	-37	DK92	-35	EF183	-26	PL81	-43
5Y3GT	-25	DK96	-36	EF184	-22	PL82	-43
6P30L2	-53	DL92	-24	EL33	-54	PL83	-31
6AQ5	-21	DL94	-37	EL34	-22	PL84	-29
6BW7	-50	DL96	-36	EY31	-30	PL500	-81
6F1	-57	DY86	-23	EY86	-28	PL504	-81
6P23	-67	DY87	-23	EZ80	-20	PY81	-23
6P25	-51	DY802	-30	EZ81	-21	PY82	-24
6S7A7GT	-28	EAB8C80	-30	KT91	-54	PY800	-32
25L6GT	-18	EBF89	-9	KT66	-7	PY801	-32
30C15	-56	EBR33	-38	N78	-85	R19	-29
30C17	-75	EBF89	-27	PCN6	-45	U25	-63
30C18	-58	ECC81	-15	PCN8	-45	U26	-55
30F5							

WILLOW VALE



BY RETURN WHOLESALE SUPPLIERS OF:

COMPONENTS

Dubilier capacitors. Erie wire-wound resistors. $\frac{1}{2}$, 1 and 2 watt carbon film hi-stabs. Sprague bias and smoothing electrolytics. Egen presets. AB metal volume controls. Smoothing electrolytics. Printed circuit aerial panels. Valve bases. Belling and Egen co-axial plugs, Din Plugs and sockets. Thermistors (ITT).

TRANSISTORS AND SEMI-CONDUCTORS

Full range of current colour transistors. AC, AF, BC, BF, BD, OC, etc., types always in stock. Rectifiers and VDRS. Full trade discount. Reputable makes. Mul-lard, Siemens, Valvo, etc.

VALVES

Entire range of entertainment types in stock at 41 per cent or 48 per cent discount. See catalogue for details. *Twelve months' guarantee.*

C.R.T.'s

Full range of monochrome and colour tubes. Rebuilt and new. 2-year and 4-year guarantees. All sizes from 17 in. to 25 in. stocked. Panorama, Rimguard, Mono and Twin-Panel.

LINE OUTPUT TRANSFORMERS

All makes supplied. Exchange units or new replacement trans-formers. (*Subject to availability.*) Bush, Philips, Pye, Ekco, Sobell/ G.E.C., Ferguson, Philco, Ferranti, Peto-Scott, etc., etc.

SERVICE AIDS

Electrolube, Servisol, Multicore Solders, tools, multi-meters in stock.

WE ARE THE ONLY SPECIALIST WHOLESALE TO THE SERVICE ENGINEER

TWO DEPOTS:

Excellent Trade Discounts. Purchase our catalogue, 20p in stamps please. Refunded on first order. Strictly trade only.

OUR REPRESENTATIVES COVER THE COUNTRY AND WILL BE PLEASED TO CALL

4 & 5 THE BROADWAY, HANWELL, LONDON, W.7

Telephones: 01-567 5400 01-567 2971 01-579 3582

42 WEST END, STREET, SOMERSET 045-84 2597

TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

VOL 22 No 4
ISSUE 256

FEBRUARY 1972

ANOTHER CORNER?

IN this industry the heart sometimes seems to rule the head. For years many people willed that colour television should be started. Events have proved that it was perhaps wise to wait, but of one thing we can be sure—that the phrase "colour TV is just around the corner", optimistically coined a good few years before the actual fruition of the dream, at one time seemed to be about to pass into folk legend. It was at any rate one of the most elusive corners we ever encountered.

Just now we seem to have another corner on our hands—and around this one is lurking the domestic video recorder. This particular piece of equipment has perhaps rather unkindly been called the greatest non-product in the history of home entertainment, and there is some justification for this epithet (no, we did not say epitaph!).

Since those rather crude whirring devices with a frequency response put optimistically at around 1MHz which were unsuccessfully launched (it seems) back in prehistoric times developments have certainly accelerated and there are some splendid end-products to prove this. If we set aside the controversies about the non-compatibility of the various competing systems—regular readers will know our views on all this anyway—what are we left with?

Basically a good deal of verbiage, revolving around the great "revolution" about to break out on the domestic front. Lovely vistas have been built up of Mr. Man-in-the-Street sitting at home re-running celebrated films, sports events and recordings of his favourite TV programmes. "The biggest thing since television" it has been enthused. Yet what have we in the way of viable products? A number of competing (and of course non-compatible) audio-visual equipments suitable for educational and commercial use, but on the home front nothing much that looks like proving an economic (or even feasible) proposition for the average viewer.

Philips have promised a home videocassette recorder by the end of this year, but the hardware will cost over £300 (at 1971 prices) and the software in the region of £15 for a 60-minute cassette. A company spokesman has envisaged a sale of 2.5 million models by 1980. To us at this point in time this seems to be expecting rather too much.

W. N. STEVENS, *Editor*

THIS MONTH

Teletopics	150
TV Test Report—The Eagle KHP30 EHT Test Probe <i>by E. M. Bristol</i>	152
A Look at Imported Sets—the Sanyo Mains/Battery Portable Model 10-T120U <i>by H. K. Hills</i>	154
Colour Cameras <i>by J. I. Sim</i>	157
Angus UHF Service Area Map	161
Servicing Television Receivers—the GEC BT302 Series—cont. <i>by L. Lawry-Johns</i>	162
Long-Distance Television <i>by Roger Bunney</i>	164
ICs for Television—Part 5—Motorola TV ICs 2 <i>by K. T. Wilson</i>	166
For the Service Engineer	167
The Do-Be Oscillator <i>by N. Banton</i>	168
Simple Outdoor UHF Aerial <i>by K. E. G. Pitt, B.Sc.</i>	171
A Closer Look at PAL—Part 3 <i>by E. J. Hoare</i>	172
Increasing the X Sensitivity of the Heathkit OS1 Oscilloscope <i>by K. J. Young</i>	178
Service Notebook <i>by G. R. Wilding</i>	179
Colour Receiver Circuits—Chrominance Signal Demodulation <i>by Gordon J. King</i>	182
Your Problems Solved	185
Test Case 110	187

**THE NEXT ISSUE DATED MARCH
WILL BE PUBLISHED FEBRUARY 21**

TELETOPICS



BEAB TO TEST TV SETS

The British Electrotechnical Approvals Board for Household Equipment (previously the British Electrical Approvals Board) is to start a testing and approvals programme for TV sets, starting with monochrome sets with screen sizes not less than 17in. The scheme will eventually cover all domestic sound and vision equipment. Monochrome TV sets will be tested to the requirements of the revised edition of BS415 and the first sets to gain approval and the right to carry the BEAB mark will be announced next August.

ITA BACKS COMPUTERS

In its latest annual report the ITA says that the application of general-purpose computers to the operation and control of large television transmitter networks is being intensively studied by its engineering staff: the aim is to apply computers to automatic monitoring and the general improvement of information flow within the organisation, though the ITA stresses that it intends to continue visual monitoring—in part because there are aspects of picture quality that are not yet defined closely enough to make them amenable to automatic measuring techniques. Considerable progress is reported in the recovery of weak signals from distant transmitting stations which need to be monitored from a regional centre. Such signals are normally heavily impaired by random noise and co-channel interference. Computer processing of these signals would enable unattended stations to be monitored without the need for additional plant at the remote station. The experimental system assembled in the Authority's laboratories is we understand being field tested to check operator reaction as well as the technical operation of the system.

THE TRADE SCENE

With colour licenses up to 946,361 at the end of September, a jump of 200,000 in three months, the colour set boom looks well established. RBM who two years ago estimated sales of colour sets during 1972 at 600,000 are now predicting sales of twice this figure. They say that if deliveries continue at the present monthly rate total monochrome plus colour set sales will reach 5 million this year. Hitachi have surveyed the market for portable sets in the UK and suggest sales of 250-300,000 this year, twice last year's figure. The survey found that last year one third of the sales of portables were for replacement purposes and two thirds were for use as second sets. To command a sizeable share of the market they say that a set must have a screen size of 12in. or more. Some recent

figures from the Department of Trade and Industry throw an interesting sidelight on the boom: apparently retailers are at last beginning to increase their share of the market, with a slight drop in the percentage of total business done by the rental specialists. With this trade boom and announcements by setmakers of component shortages we wonder why BREMA felt it necessary to send a deputation recently to see the Minister of Aerospace—who is responsible for the electronics industry—in an attempt to have quotas on colour set imports from Japan introduced.

Those Pye dealers who were asked recently to vote for or against the maintenance of recommended prices voted overwhelmingly for their retention. 77% of the dealers replied, with 76% of replies in favour of recommended prices and 24% against. Pye say they will therefore be continuing their policy of suggesting recommended prices but will review the position from time to time in the light of changing retail conditions.

BREMA announce that at present 18% of setmakers' output consists of dual-standard sets and that this is expected to fall to 10% by the end of the year. ITT and GEC have already given up producing dual-standard sets but GEC say they could re-enter the market if the position warrants it.

TRANSMITTER NEWS

BBC-1 on u.h.f. is now being transmitted from the **Malvern** (channel 56, aerial group D with vertical polarisation) and **Fenton** (channel 31, aerial group A with vertical polarisation) relay stations. In addition the BBC-Wales service from **Kilvey Hill** (Swansea) is now in operation on channel 33 (aerial group A with vertical polarisation).

IS THAT DECOUPLER REALLY LEAKY?

Rank-Bush-Murphy report that dealers are returning to them as faulty some of the small 0.1 μ F capacitors used in their single-standard colour chassis as decouplers associated with the intercarrier sound i.c. but that most of them have been found to be OK when tested at their Chiswick laboratory. The capacitors are semiconductor low-voltage ceramic disc types and the basic difference between them and conventional ceramic disc types is the barrier-layer dielectric which gives very small size (capacitances as much as 100 times greater than those obtained with normal disc ceramic capacitors can, for a given size, be achieved). The main electrical difference is that they exhibit a much lower leakage resistance. They are intended therefore primarily as a.f. bypass and coupling capacitors in low-impedance transistor circuits where size is of importance. The leakage resistance

falls markedly with increase in applied voltage and is quoted therefore for the capacitor's rated voltage. It is assumed that dealers have returned these capacitors because of the comparatively low resistance readings obtained when measurements have been made using an Avo or similar ohmmeter.

NEW VIDICON FROM MULLARD

A new inexpensive miniature vidicon television camera tube announced by Mullard has a resolution of 550 TV lines—more than adequate for a high-quality picture. This resolution has been achieved by fitting the tube—type 20PE13—with a separate mesh. Electromagnetic focusing and scanning are used. The 20PE13 requires a heater supply of 6.3V at 95mA. When subject to an illumination of 10 lux from a lamp with a colour temperature of 2854K it has a signal current of 150nA. Its dark current is 20nA.

The new vidicon is designed for use in small inexpensive cameras for closed-circuit television systems. Its small size—17.70mm. in diameter and 108mm. long—makes it particularly suitable for use in cameras that have to be hidden, as in the security systems of banks etc. The 20PE13 can be supplied complete with yoke assembly and socket for £26.25 or the individual components can be ordered separately.

DO-IT-YOURSELF AERIAL

Antiference have introduced a TV aerial kit for the do-it-yourself enthusiast. The kit consists of a 10-element array in two sections, mounting arm and bracket, coaxial output box, 6ft. flylead, cable guards, clips, wall plugs and screws. The kit costs £4 and comes complete with assembly instructions. There are group A, B and C/D versions. Antiference Ltd., Aylesbury, Bucks.

THE VIDEO RECORDING FRONT


An agreement between Sony and 3M has been announced. 3M are to manufacture Sony's ½in. U-Matic videocassette equipment and Sony are to produce 3M's new high-energy magnetic tape which uses a cobalt-energised iron oxide formula giving improved signal-to-noise performance.

Decca announce that they hope to market their Teldec Videodisc players in 1973-4 at about £70 (monochrome) and £150 (colour) before tax.

The introduction of Ampex's Instavideo cartridge videotape recorders/players has been delayed—prototypes were expected to have been on show in London last October. An official announcement says the system "is being held in the US for further development". In common with other systems it is understood that difficulty is being experienced in meeting new rulings from the US FCC.

ITA's CONCRETE TOWER

The ITA is justly proud of its new aerial-support tower at Emley Moor in Yorkshire, being the first self-supporting concrete tower ever to be built for television broadcasting in the UK. Some statistics: the concrete section is 900ft. high and has a base diameter of 80ft., tapering to 20ft. at the top; above this are triangular lattice steel sections carrying the transmitting aerials, covered by glass-reinforced-

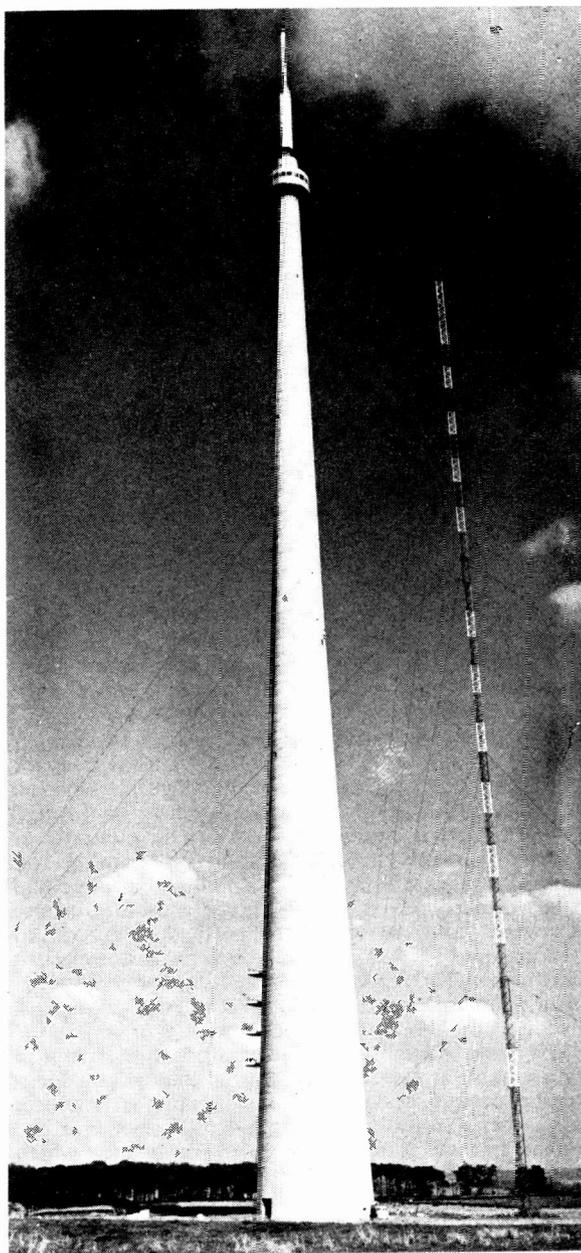

plastics—bringing the total height to 1,080ft.; the total weight of the tower and its foundations exceeds 15,000 tons. The tower was built to replace the tubular steel mast which collapsed on March 19th, 1969. Work on the new tower began in the summer of 1969. A unique feature of the construction was the lifting—in a week-long operation—of the entire steel section with the u.h.f. aerials in position (a weight of about 60 tons) up through the centre of the tower.

The new aerials and increased transmission power have resulted in a significant improvement in the pictures received by viewers. The change from the temporary low mast brought almost another 1¼ million viewers within reach of Yorkshire Television's 625-line colour and black-and-white programmes. This improvement in coverage also applies to the BBC-1 and BBC-2 u.h.f. services from Emley Moor which also use aerials on the new tower.

TV TEST REPORT

E. M. BRISTOL

THE EAGLE KHP30 EHT PROBE

AN accurate and easy-to-use means of reading e.h.t. has always been a necessary item of workshop equipment and now that colour receivers are finding their way into the workshop in increasing numbers it is more essential than ever as a colour set's e.h.t. must be adjusted exactly and many fault conditions must be investigated by first of all checking the e.h.t.

The majority of devices hitherto available fall into three main categories. First there are the test probes designed to work in conjunction with a normal meter. These are quite reasonably priced and accurate but are designed for a particular meter sensitivity. Convenience of use is not a strong point as leads must be changed and the meter switched. Also they are fairly bulky. And the meter is tied up when it may be needed for making simultaneous measurements—say of the boost voltage.

A self-contained instrument is more convenient but accurate e.h.t. meters are not cheap, some being around the £20 mark. Although this is not a great sum for a professional workshop it is enough to make the enthusiast think twice.

As a result there has also been a crop of cheaper devices consisting in the main of calibrated spark gaps. Discharge has either been through air between two electrodes and visible to the operator or through a neon lamp via limiting resistors. The accuracy of these instruments depends among other things on atmospheric conditions so that small errors have had to be accepted. Even so they served a useful purpose as general e.h.t. testers in the early days of valved monochrome TV sets. With modern transistor circuits however any sudden violent surge as a result of inducing a deliberate spark discharge can have disastrous effects on the line output transistor.

The Eagle KHP30 is a self-contained e.h.t. meter at a reasonable price. It is no bigger than many high-voltage probes designed to work with an external meter, being only 14in. long and 2in. wide at the thickest part. It is housed in a grey plastic case which is claimed to be strong and impact resistant.

Contact with the e.h.t. source is made by means of an exposed 1½in. long metal spike. This is followed by a tapered barrel some 5½in. long and ¾in. thick at the widest point. Then comes the spark trap and the body which houses the meter and serves as a handle. The meter is set at a slight angle from the horizontal, enabling it to be read easily from the rear. It is clearly calibrated 0-30kV d.c. in 1kV divisions with a red mark at the 25kV point. The needle is edge-type and coloured red. A zeroing screw is flush-mounted just below the meter scale.

The handle part tapers back and is of half-round section, the outer surface being slightly crinkle-finished.

to give a non-slip grip. The earth return is by means of a plastic lead permanently wired into the end of the instrument. This is some 3ft. long and terminated by an insulated crocodile-clip.

Our first concern was the accuracy of the instrument which is claimed to be within 3%. As no other e.h.t. meter of sufficient accuracy to provide a standard of comparison was to hand a new colour receiver was used to check the meter. First of all the set was carefully set up and its boost voltage adjusted to the maker's figure. Under these conditions the e.h.t. should be exactly 25kV. A measurement was taken with the probe and indeed it read spot on the 25kV mark. A check was then made at the low end of the scale by measuring the boost voltage of another receiver which was adjusted to 800V. This should give a reading on the probe of just below the first 1kV division. It was rather lower than expected although over the halfway point. It is perhaps asking a lot for an accurate reading as low as this—all meters are at their least accurate at the low end of the scale. Even so it wasn't very far out.

Experience with monochrome receivers with a wide range of e.h.t.s over the several months the instrument was on test in the workshop indicated that the readings were consistently spot on over the important part of the scale, from 10 to 25kV.

The Probe in Use

The current taken from the source is low. The meter has a sensitivity of $20\text{k}\Omega/\text{V}$ and so takes $50\mu\text{A}$ for a full-scale reading, the load being $600\text{M}\Omega$. There should therefore be no observable voltage drop as a result of the connection of the probe. As a result the probe is very docile in use: approaching and touching the e.h.t. point does not cause a fierce spark or crack. In fact because of this there is a danger of misleading readings: if the probe is inserted under an e.h.t. cap but does not touch the metal connector there will be an e.h.t. discharge to the probe and a reading several kV lower than the full e.h.t. value will be obtained. Because there is no sound or fuss from this small discharge—not even splashes on the picture if one is being received—the operator may be unaware that the probe is not in actual contact with the connector. The rule when probing under the plastic e.h.t. cap should therefore be to push the probe well in until you *feel* that contact has been made. Do not rely just on the fact that a reading has come up on the meter.

How then does the instrument handle in use? In most cases very easily. The probe can be guided home and the meter read all in one action without, as is the case with a probe and separate meter, having to divert attention. The spike slides easily under the e.h.t. flap once the edge has been lifted and is just the right length to make contact with the connector in the centre. The barrel is long enough in most cases to get between the panels and receiver hardware and the c.r.t. flare. Some sets are rather awkward to get at but this would be so with any test instrument.

Altogether then I can enthusiastically recommend this probe as a well designed and worthwhile addition to any TV repair workshop, outside engineer's kit or home experimenter's outfit. It is packed in a solid polystyrene container with contoured well for the instrument and this can be used to house the probe when not in use. The retail price is £10.40 which is subject to the normal trade discounts.



The Eagle KHP30 high-voltage test probe.

NEW LINE OUTPUT TRANSFORMERS

ALBA 655, 656, 717, 721 **£3-75**, 890, 895, 1090, 1135, 1195, 1235, 1395, 1435 **£5-00**.

ARGOSY 17K10, 17K11, 17K12, 17K14, 19K17, 17K43 **£4-00**.

BAIRD All models price **£5-90**. From model 600 quote part no. normally found on TX base plate.

BUSH TV53 to TUG69 **£2-00**, TV91 to TV139 **£4-75**. (From Model TV123 an alternative Square Tag Panel was fitted on Main Bobbin, please state if required.) TV141 to TV176 please state part number **£4-50**, TV75 to TV86 **£4-75** (except TV80).

COSSOR 904 to 957 Rewind **£4-50**, CT1700U to CT2378A **£5-00**.

DECCA DM1, DM3C (90°), DM4C (70°), DR1, DR2, DR121 **£4-50**, DR95, DR100, DR101, DR202, DR303, DR404, DR505, DR606 **£4-50**.

DEFIANT 7P20 to 7609. Prices on request.

DYNATRON TV30, TV35, TV36, TV37, TV38, TV39, TV40, TV41, etc. **£4-00**.

EKCO T231, T284, TC267, T283, T293, T311, T326, T327, T330, TMB272, T344, T344F, T345, TP347, T348, T348F, TC347, TC349, TC356, T368, T370, TC369, T371, T372, TP373, TC374, T377A, T393, T394, 433, 434, 435, 436, 437 all at **£4-00**, 503, 504, 505, 506, **£4-75**.

FERGUSON 306T, 308T, 406T, 408T, 416, 436, 438, 506, 508, 516, 518, 536, 546, 604, 606, 608, 616, 619, 636, 646, 648, 725, 726, 727, 3600, 3601, 3602, 3604, 3611, 3612, 3614, 3617, 3618, 3619, 3620, 3621, 3622, 3623, 3624, 3625, 3626, 3627, 3629, **£4-00**. Jelly Pots, please state colour - red, black or white.

FERRANTI T1001, T1002, T1002/1, T1004, T1005, T1023, T1024, T1027, T1027F, TP1026, T1071, T1072, T1121, TC1122, TC1124, T1125, TC1126 **£4-00**, 1154, 1155 **£4-75**.

G.E.C. BT302, BT342 **£3-50**, BT454DST-456DST, 2012, 2013, 2014, 2012, 2000DS, 2001DS, 2002DS **£4-50**.

H.M.V. 1865, 1869, 1870, 1872, 1874, 1876, 1890, 1892, 1894, 1896. All models to 2645 **£4-00**.

KB OV30, NF70, NV40, PV40, QV10, QV30, RV10, RV20, RV30, PVP20 **£4-50**, Featherlight **£4-50**, Chassis No. VC1-VC2-VC3-VC4 **£4-50**.

MASTERADIO 4013 DST, D500 DST, D507 DST **£4-50**.

MARCONI VT153, VT155, VT156, VT157, VT159, VT161, VT163, VT165, VT170, 4611, 4800, 4801, 4803, 4615 **£4-00**.

MURPHY V310 to 929 **£4-75**.

PAM 600S to 5106 **£4-00**.

PETO SCOTT. Prices on request.

PHILCO 1019, 1020, 2021 **£4-13**, 1029, 1030, 1035, 1036, 1040, 1050, 1060 **£4-13**.

PHILIPS 11TG190 to 24T301 **£5-00**.

PILOT PT450, 452, 455, 650, PT651, P60A, P61 **£4-00**.

PYE V200, V400, 200LB, 210, 220, 300F, 300S, 310, 210S, 410, 510, 530, 600, 620, 630, 700 A or D, 710 A or D, 830 A or D or LBA **£4-00**, 11U Series, 11U-P/NO, AL21003, 21F to 61. Part Nos must be given when ordering Pye LOPTS.

REGENTONE 197-198, 298, TV402, TV401, TV501, TV502 **£4-50**, 10-4-10-6, 10-21, 17-18, 10-12, 191-192 **£4-00**.

R.G.D. 626, 627, 628, 726, RV202, RV302 **£4-50**, 519-619-620-621C, 723 **£4-00**.

SOBELL 1000DS, 1002DS, 1005DS, 1010DST, 1012, 1013, 1014, 1018, 1019, 1020, 1021, 1032, 1033, 1038, 1039 **£4-40**.

STELLA T1011U to 2149A **£5-00**.

TOSHIBA 11TBB, all 11" models **£5-00**.

ULTRA 1770, 2170, 1772, 1782, 2172, 1771, 2171, 1775, 2175, 1774, 2174, 1773, 2137, 1980c, 1984c, 100c, 200c, 2380, 2384, 1984, 1985, 1986, 1980, 1980a, 1780, 2180, 2181, 2183, 2182, 1871, 1783, 6600, 6625, 6626, 6628, 6632, 6642 etc. **£4-00**.

Post and Packing 26p. C.O.D. 30p extra.

LINE OUTPUT TRANSFORMER INSERTS ONLY

BUSH TV75, TV85, TV92-TV93, TV-94-TV95-TV96-TV97, TV98, TV100, TV101, TV103, TV104, TV105, TV106, TV108, TV109, TV110, TV113, TV115, TV115R, TV115c, **£2-75**. Complete with heater windings.

DECCA DR95, DR101, DR202, DR303, DR404, DR505, DR606 **£2-75**.

RETURN OF POST SERVICE ON ALL STOCK ITEMS

CALLERS WELCOME. But to avoid disappointment please phone to check that the items you require are in stock.

All new components inserts are guaranteed for three months from the date of invoice subject to the breakdown being due to faulty manufacture or materials. **S.A.E. all enquiries.**

**Dept. "R" E. J. PAPWORTH AND SON LTD.
80 MERTON HIGH STREET, S.W.19 01-540 3513**

01-540 3955

a look at
Imported
SETS....

SANYO
10-T120U
mains/battery
portable

H.K.HILLS

CONTINUING our series in which we take a close look at the circuitry used in imported sets the spotlight this month is turned on the Sanyo 10in. mains/battery portable Model 10-T120U. The same basic chassis is also used in the Alba Model T10 Starlight. The set can be operated from 240V a.c. mains—via a double-wound transformer—or a 12V battery, a four-transistor voltage regulator circuit providing a 10-7V stabilised l.t. line on both systems. Other features include a two-stage noise-cancelled sync separator circuit, a gated a.g.c. circuit with delayed line to the tuner and a line output stage in the emitter-follower mode which also provides a 9.5kV e.h.t. supply, a 100V supply for the video output stage and a separate h.t. supply for the tube first anode and focus circuits and the brightness control.

Line Output Stage

We will take a look at the line output stage first since it is involved with so many other sections of the receiver and is representative of the arrangements found in many other small-screen portables. In some ways transistor line timebase circuits are comparable with valve circuits though in other respects they differ widely. As is usually the case a three-transistor circuit is employed, with a blocking oscillator line generator (Q117, 2SC536), driver stage (Q118) which is really a pulse amplifier and output transistor (Q119). The circuitry around the latter two stages is shown in Fig. 1 and it will be seen that both transistors are pnp types with their collectors returned to chassis. The high-amplitude output from the line oscillator alternately drives Q118 from cut-off to saturation so that the output from the driver is the rectangular waveform required for operating the output transistor Q119 as a switch, "on" during the latter part of the forward sweep and "off" during flyback and the first part of the forward sweep. As the output transformer and scan coils present a highly inductive load to the output transistor, switching in a d.c. voltage in this way produces a rising current that closely approximates the required sawtooth rise during the forward scan (with a purely resistive load the current waveform is of course a replica of the applied voltage waveform).

With valve circuits the current from the line output pentode provides beam deflection from about screen centre to the right-hand edge of the screen, current via the boost diode providing the forward scan at the left-hand side of the screen. The transition is of course gradual, with considerable overlap towards the centre, but the total current rate-of-change remains

substantially the same throughout the forward scan. In solid-state line output stages a broadly similar action occurs but with the difference that while valves can conduct in one direction only a switched on transistor can conduct in both directions so that when used for line output they can also function—within certain limits—as the reclaim or efficiency rectifier. In practice however a damping diode is always used with transistor line output stages since this greatly reduces the power dissipation of the transistor and linearises the scan.

Deflection Current

Starting with the spot in the centre of a line—when the scan coil current is instantaneously zero—current then flows with a linear rate-of-change through Q119, building a strong magnetic field around the scan coils (L109). The peak current reached at the screen edge is terminated by the arrival of the next pulse to reverse bias Q119, the sudden cessation of current in Q119 inducing a high reverse voltage which charges C613, C621 and C622—the total value of these capacitors determining the flyback duration. The start of the next sweep is produced by the reverse current which flows mainly through the damper diode D10, maintaining a current in the deflection coils which *decreases* with linear rate-of-change until the spot is at the centre of the line when the current direction is reversed as the


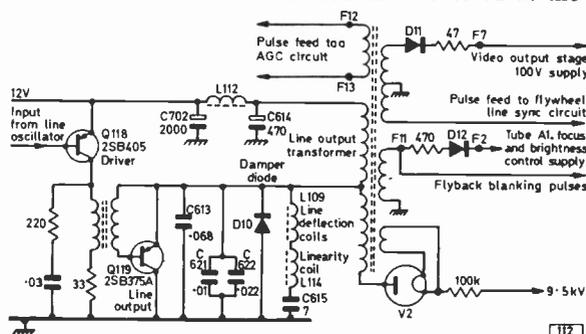


Fig. 1: The line output stage, which also provides two h.t. and three pulse feeds. There is no fixed forward bias to the line output transistor Q119: it is simply driven to saturation by the high-amplitude negative-going pulses transformer coupled from the driver Q118 to its base. The damper diode D10 fulfils a similar function to the efficiency diode used in a valve stage but without providing a boost h.t. supply.

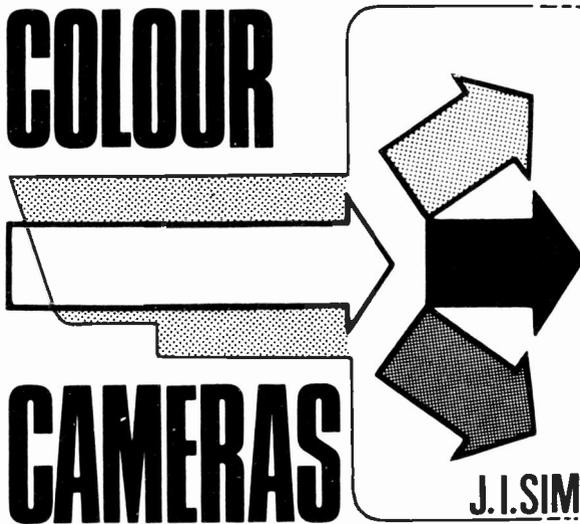

THE heart of any camera is the camera tube. This is especially true of a colour camera in which at least three tubes must be used to obtain the necessary Red (R), Green (G) and Blue (B) information from the scene.

The first generation of colour cameras used 3in. image orthicon camera tubes or a combination of image orthicons and vidicons. Both arrangements have great disadvantages: any camera using more than one image orthicon must be very large and cumbersome—not the thing for moving delicately and artistically around the studio floor. Vidicons could be used but these are not considered suitable for rapidly moving subjects because of “lag” (i.e. retention of an image on the target after the image has moved). The vidicon also has an uneven dark current: that is with no light falling on the tube the current which flows in the tube is not linear over a line or field period. This could be tolerable if each vidicon tube had the same characteristic—but unfortunately they don’t.

Both these vidicon defects are tolerable in monochrome television and the tube has an established place in small studios such as those used for regional news. In colour however the lag shows up as a coloured smear on the picture and uneven dark currents between tubes lead to tinted backgrounds.

Because of these defects Philips undertook development of a camera tube especially for colour television. The result, introduced early in the 1960s, was the Plumbicon tube. This uses a lead-based target—as the name suggests—but is otherwise very similar to the vidicon in construction. It works on similar principles as it is also a photoconductive type of tube. The tube’s characteristics are somewhat different however in that the Plumbicon has very much less lag than the vidicon and has a dark current which is very even and which is reproducible between tubes. Physically the standard sized Plumbicon is a little longer and a little larger than the 1in. diameter vidicon.

By using the Plumbicon either a three- or four-tube colour camera can be built that is little larger than the 4½in. image orthicon cameras which have been used for many years for monochrome productions.

Three- and Four-Tube Cameras

In the three-tube colour camera each tube produces the signal equivalent to one of the primary colours—

red, green and blue. These are the only essentials required because the luminance (Y) signal can be matrixed from these three primaries. There is however some advantage in using a fourth tube in the camera to produce the luminance signal directly.

There are a number of arguments in favour of both systems. To analyse these completely would cover the pages of this issue of TELEVISION, so we will simply put down the more important aspects:

Sensitivity: Under the low and variable light conditions often found in outside broadcast work the three-tube arrangement has the advantage—the available light being shared between fewer tubes. In studio work the differences are insignificant.

Monochrome reproduction: It would be expected that the four-tube camera has the advantage here because the luminance signal is obtained directly. In fact because corrections have to be made to this signal to achieve a compromise between the different values of gamma for a monochrome and a colour c.r.t. the resultant is no better than with the three-tube camera.

Registration (i.e. the convergence of the camera tubes and their scans): The three-tube camera is undoubtedly easier to register and this can usually be done more accurately. In a four-tube camera however the high-frequency information comes from the luminance channel (each of the three chrominance channels being bandwidth restricted to 1MHz). Most of the misregistration errors are therefore less noticeable.

Dimensions and running costs: A three-tube camera contains less items but as the size and weight of a camera are determined more by the lens system and the viewfinder the differences between three- and four-tube cameras are insignificant. On costs whereas there is less equipment to go wrong in the three-tube camera the condition of a four-tube camera can be allowed to deteriorate more before replacements are necessary to give the required performance.

As can be seen the arguments for and against both types of camera are hardly conclusive and the first purchases of camera channels by the broadcasting authorities showed little favouritism for one type or the other. As a compromise between three- and four-tube operation, particularly between sensitivity and convergence (registration) requirements, the major manufacturers have now turned to three-tube formats using red, blue and luminance or white. The sensitivity is then basically that of a three-tube camera but the registration is as tolerant as the four-tube arrangement.

As we must keep this article uncomplicated only the RGB three-tube camera will be looked at. The same principles are used in the four-tube camera and other versions of the three-tube format although there are some specialised differences.

Colour Camera Block Diagram

Figure 1 shows a simplified block diagram of an RGB three-tube colour camera. It is in two basic physical blocks—the camera itself on the studio floor, mounted on a tripod or pedestal, and the camera control unit fitted in the engineering area of the studio. Coupling the two blocks is the camera cable.

The video paths are fairly straightforward and are repeated for each channel—red, green and blue. The very small signal from the individual Plumbicon target (about 0.3µA peak signal current) passes to the head amplifier which determines to a great extent the overall signal-to-noise ratio of the camera channel. This

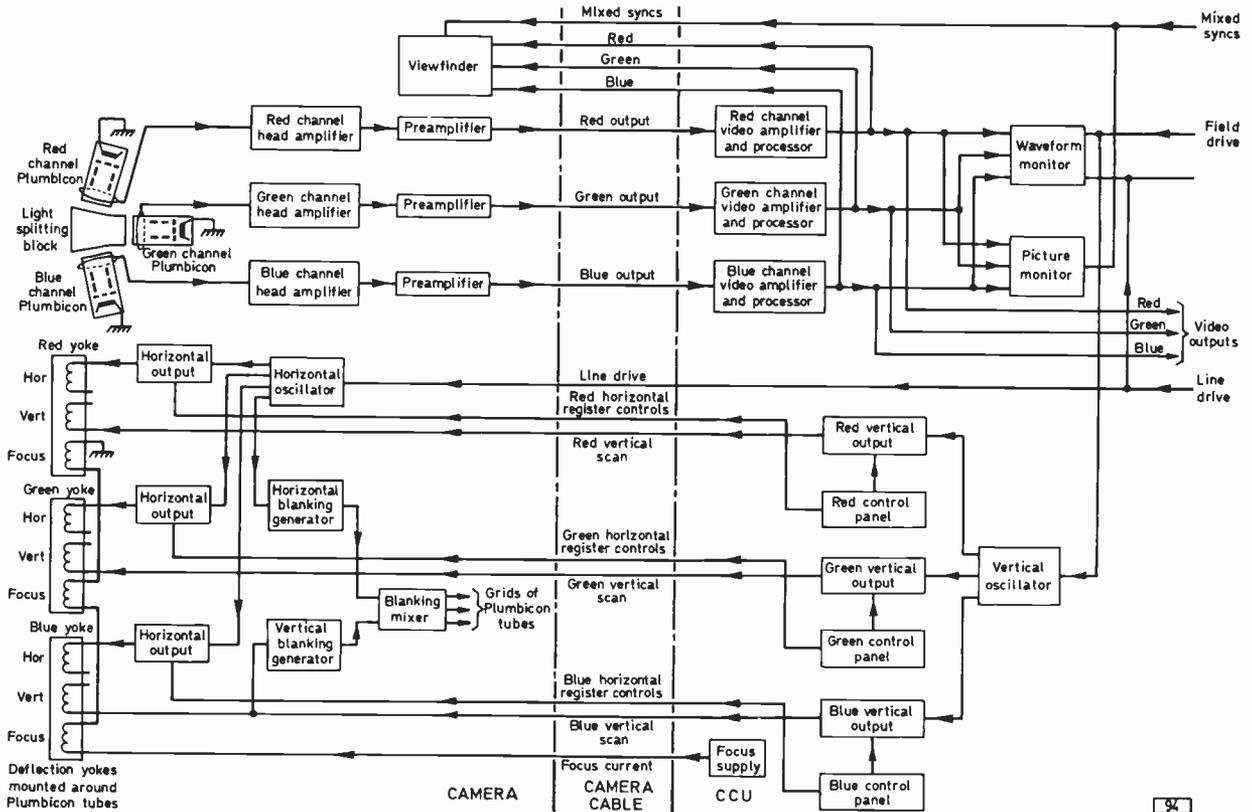


Fig. 1: Block diagram of a three-tube colour camera, with camera control unit.

amplifier output then passes to another amplifier—the preamplifier—to bring each video signal up to a sufficiently high level to be passed through the camera cable without interference. When the video signals reach the camera control unit (c.c.u.) they are further amplified and processed—in fact clamped, clipped, gamma corrected and blanked. The final stages form a distribution amplifier with the outputs being used to feed the picture and waveform monitors, the channel outputs and back up the cable to the viewfinder.

The scanning and scan control circuits of the camera channel are more complex. Basically the vertical scan generation is in the camera control unit and the horizontal scan generation is in the camera. Each deflection yoke on each Plumbicon tube is fed with both vertical and horizontal scan waveforms. Each feed is derived from a separate output stage which is controlled to make possible variation in shift, amplitude and linearity. These functions are controlled from the c.c.u.

Camera in Detail

Figure 2 shows the camera part of a Peto Scott PC60 camera channel. An electrically-controlled servo zoom lens is fitted at the front of the camera (left on picture). The controls for the zoom are brought on to the control arm at the rear. These include four preset zoom angles and an operating handle for general zoom work. Two basic zoom speeds are provided and these are supplemented by the pressure that the operator puts on the control handle.

The camera cable outlets can be seen on the side of the camera body and these can also be seen in Fig. 3.

This photograph of the camera with the left-hand side opened up also shows the bulk of the electronic layout. The three tubes are on the left-hand side with the green Plumbicon “firing” horizontally, the red Plumbicon “firing” downwards and the blue Plumbicon “firing” upwards. The small black box they all lie against is the optical splitting unit. Above the green Plumbicon is a screened box containing the three preamplifiers and to the right are the individual horizontal output assemblies.

Figure 4 shows the green Plumbicon assembly more clearly. The drilled cover has under it the head amplifier. The input to the head amplifier is taken direct from the tube’s target—the very short lead on the left—and the output is taken by the thin coaxial lead up to the preamplifier. The tube itself is inserted from the rear into the whole assembly—most of which is

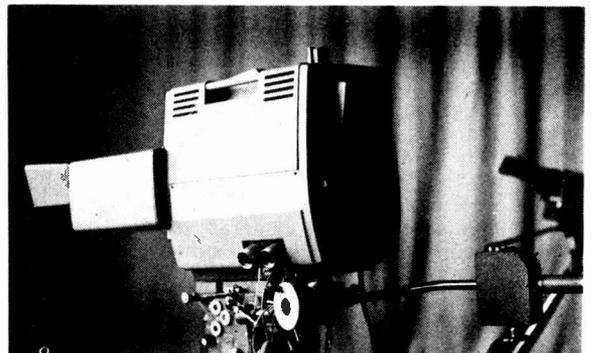


Fig. 2: The Peto Scott PC60 colour camera.

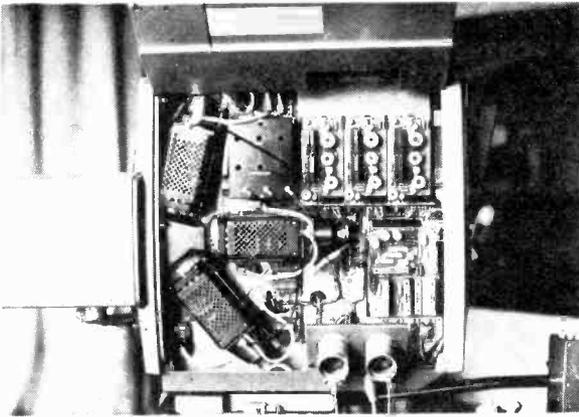


Fig. 3: Peto Scott PC60 colour camera with side opened

the scanning yoke.

At the other end of the camera cable lies the c.c.u. Fig. 5 shows a general view of the unit. From the top are housed a monochrome picture monitor, a waveform monitor, the operational controls and then the alignment controls. A monochrome picture monitor is necessary for alignment of a colour camera channel because of the accuracy of registration required. Such accuracy can only be gained with good resolution of the picture display and this is not obtainable with a colour monitor. The waveform monitor has automatic triggering on line and field. The display itself is in fact three displays—one period of red, one period of green and one period of blue information—laid in a row. The monitor also has its own internal calibration.

A closer view of the operational controls is shown in Fig. 6. The meter indicates the lens angle at any instant unless one of the three "target" buttons below it is pressed. If so that particular target voltage is indicated. The other controls (left to right) are remote servo control of lens iris, video gain control, black level control of all three channels and separate black level control for the red channel. Below these four controls are four push-buttons. The first three are for red, green and blue and switch the inputs to the picture monitor so that any of the channel signals can be displayed separately or in pairs or together. The fourth button inserts an external test signal into the monitor system.

The alignment controls forward of these operational controls are for the individual camera tubes

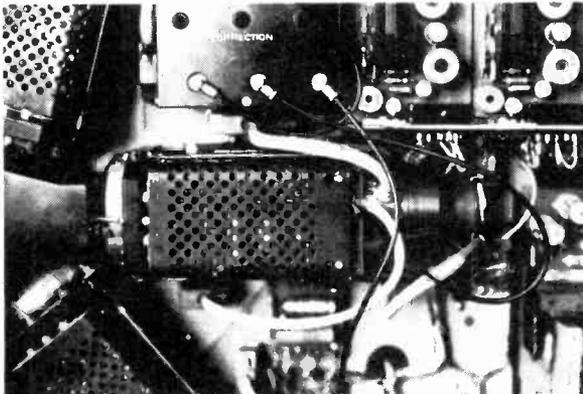


Fig. 4: Close-up view of the green tube assembly in the Peto Scott PC60 colour camera.

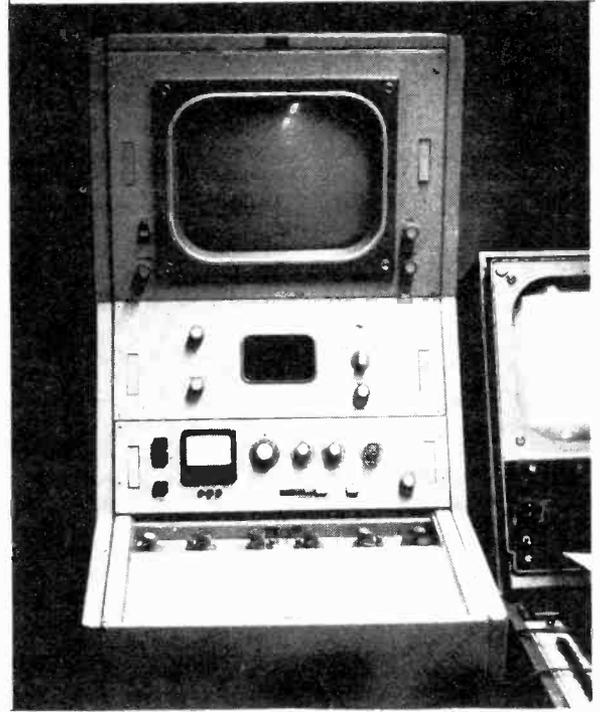


Fig. 5: The PC60 camera control unit.

and are the conventional ones of focus, beam, etc., and also the registration ones for shift, amplitude and linearity of the scans. These are not touched after the engineering line-up of the camera.

From our point of view the actual operating procedures are relatively unimportant and the individual circuits used for video processing are either very conventional or highly specialised. Two sections of the camera are however of particular interest.

Light Splitting System

The colour splitting system is probably the simplest and yet the most complex part of any colour camera. To get precise colour fidelity the light passed to each of the three colour tubes must be divided at exactly the same frequencies as the phosphors used in the shadowmask tube at the display end of the system. This science of chromaticity separation is a highly

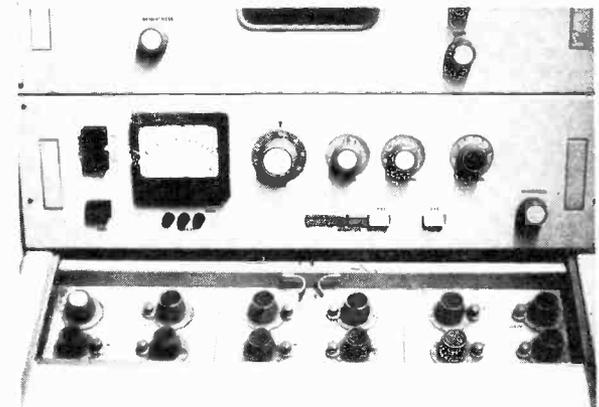


Fig. 6: PC60 operating controls.

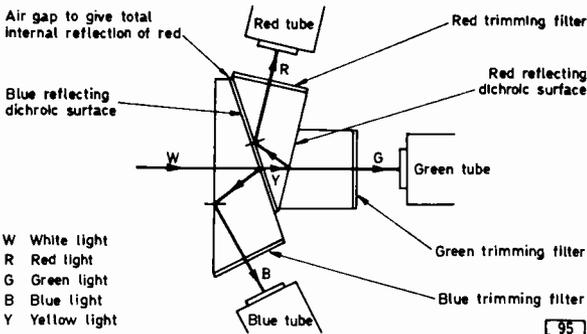


Fig. 7: Colour-splitting prism in the PC60.

specialised one and is yet still somewhat empirical. The system used in the Peto Scott camera is shown in Fig. 7.

The dichroic surfaces reflect only one particular bandwidth of light, allowing through all other bandwidths. An electrical analogy would be the bandstop filter. The colour trimming filters are really bandpass filters—shaping and cutting off the spectrum precisely.

The shorter the path each individual colour of light has to take the better. This reduces light transmission losses and the chances of different time delays at different light frequencies. Additionally each optical path must be the same length.

Head Amplifiers

It can be shown that the signal-to-noise ratio from a Plumbicon tube is large in comparison to many video sources (rather better than 50dB under the correct operating conditions). The output impedance of the tube however is very large and must be correctly matched by the head amplifier if this signal-to-noise ratio is to be preserved. At the same time the head amplifier must provide a reasonable amount of gain, must be stable, must have a bandwidth at least that of the video signal and most important must introduce very little noise.

We have seen in television receivers that good gain with low noise is obtainable from the cascode amplifier configuration. It might be useful to briefly explain this circuit again. Fig. 8(a) shows the simple, single-stage, grounded-cathode amplifier. It has the advantage of high input impedance but the disadvantage that the interelectrode capacitance from anode to grid (C_{ag}) becomes a feedback path and at high gain the stage is liable to go into oscillation. This problem can be overcome by the grounded-grid amplifier—Fig. 8(b)—where any feedback signal through C_{ag} is earthed by C . The gain is the same as with the grounded-cathode stage because the input signal is still applied between grid and cathode. A very big disadvantage however is that the anode current and cathode current are the same. The higher the stage gain the larger I_a becomes and the lower the input impedance. It can easily fall below 10Ω . This is obviously impossible to match to the high output impedance of the Plumbicon.

The cascode amplifier—Fig. 8(c)—combines the grounded-grid and grounded-cathode stages and combines their advantages. V_1 is the grounded-cathode stage and has high input impedance but little gain (to make it stable). Its low output impedance feeds the low input impedance of V_2 (the grounded-grid stage).

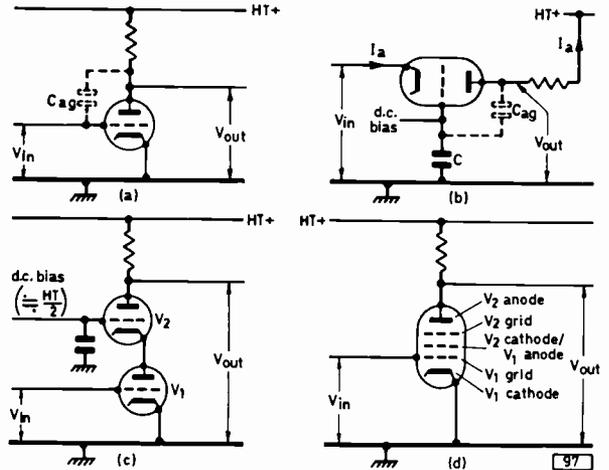


Fig. 8: Derivation of the cascode amplifier circuit.

The gain of this stage can then be made high because it is always matched perfectly at its input. It can be shown that the noise of this type of amplifier circuit is predominantly that of the first active device—in this case V_1 , a triode—but the gain is that of an equivalent pentode. Fig. 8(d) shows somewhat simply how this comes about.

To apply the cascode amplifier to a Plumbicon tube output sounds devastatingly simple. However the valve (even a triode) is basically a noisy device and it would be better to avoid it in this critical position. If a valve had to be used the choice of type would be very important (i.e. limited to nuvistors or a valve such as the E180F strapped as a triode). What would be better would be to use a semiconductor arrangement, bipolar transistors coming immediately to mind. But these have a low input impedance and although this can be increased it is only possible to do so to a limited extent and only at the cost of gain.

The answer to the problem is to use a field-effect transistor. These have the low noise figure of a semiconductor but the high input impedance of a valve. The f.e.t. need be used only in the lower part of the cascode arrangement as the upper device is only required to provide a low impedance input with high gain. Fig. 9 shows a typical f.e.t. head amplifier for a colour camera. Two f.e.t.s are paralleled so that they match the output capacitance of the Plumbicon tube (12pF). At the same time this arrangement

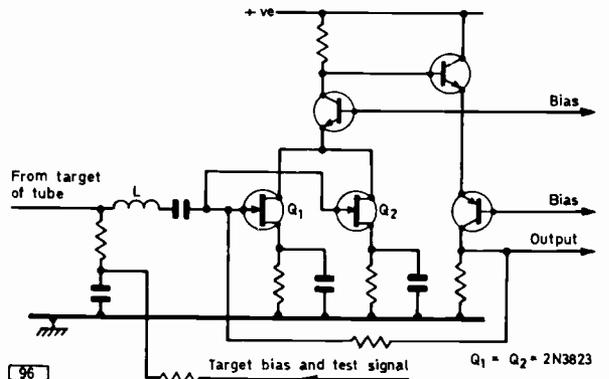


Fig. 9: Hybrid cascode head amplifier for a colour camera channel using f.e.t.s for the input.

doubles the gm for the signal but the noise, being a random quantity, adds in an r.m.s. manner: this gives an immediate improvement in signal-to-noise ratio of about 3dB. The second part of the cascode circuit consists of a bipolar transistor and the output is impedance matched and isolated by another transistor circuit.


L is known as a Percival peaking coil and by a resonance process gives an improvement in the signal-to-noise ratio at the higher frequencies. This coil has

been used for some years in various camera channels. Feedback is applied and the load resistor for the camera tube is in fact the feedback resistor. This greatly reduces the problems of equalisation that would arise by simply paralleling the camera tube load resistor across the input terminals of the amplifier.


We shall be publishing further articles by J. I. Sim on colour broadcasting techniques from time to time.

ANGUS UHF SERVICE AREA

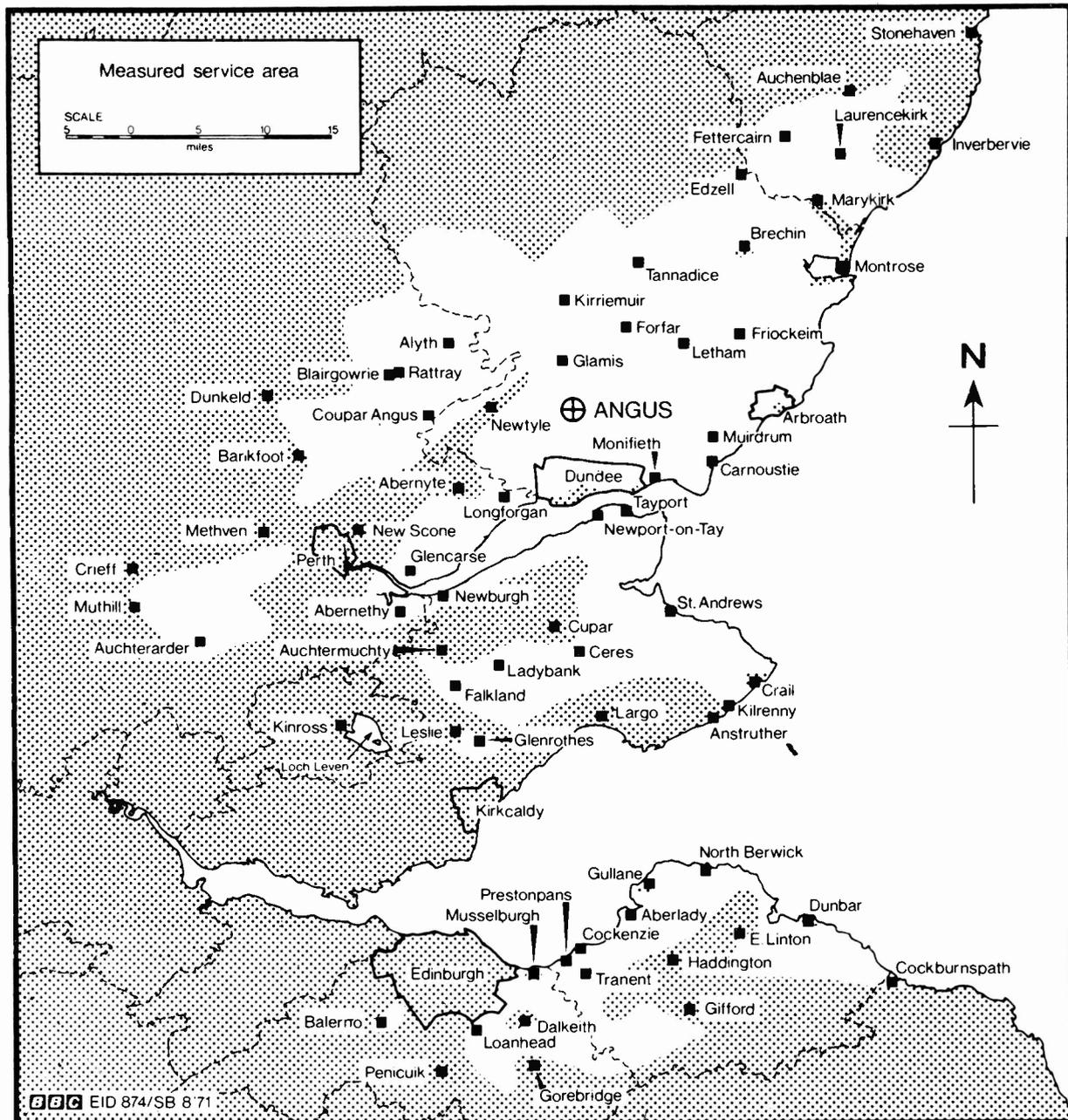Channels : Fourth 53, BBC-1 57, BBC-2 63, ITV 60
Receiving aerial group C, horizontal polarisation



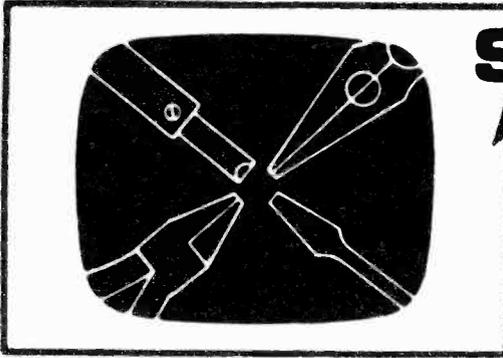The approximate service area is indicated by the unshaded parts of the map. Maximum vision e.r.p. is 100 kW. Map courtesy BBC Engineering Information Service.



SERVICING television receivers

L. LAWRY-JOHN'S

THE GEC BT302 SERIES—cont.

Incorrect Tube Supplies

If the e.h.t. is OK absence of a raster will indicate incorrect tube base supply. In this case check the heater voltage across pins 1 and 8, remembering that some tubes (7405A etc.) have a 12.6V heater, then check the voltage supply to pins 2, 3 and 7. Pins 2 and 6 are the grid pins and the voltage here should vary with the brilliance control setting from zero to approximately 170V. Pin 3 is the first anode: the voltage here should be over 400V depending on the meter used. If the voltage is not much more than 200V suspect C149 and disconnect it for test. Pin 7 is the cathode which should record very roughly 150V according to the video swing and the condition of the video stage and resistors.

The Display

Having got something on the tube face by getting the line timebase working just what is displayed will be determined by the performance of the vision signal stages and the condition of the tube itself. If the original tube is still fitted it can hardly be expected to provide a bright, crisp picture: a certain amount of softness must therefore be tolerated.

Bright Raster, No Picture

This is a fault which will almost certainly be encountered on some of these sets: the raster will be over bright with no picture signal. V6 will probably be bright red with shame (as you would be if you had a high oscillatory voltage on your grid). The cause is lack of decoupling in the vision i.f. stage. A replacement 0.001µF (C60) capacitor from pin 8 of V5 to chassis will usually put things back to normal and V6 will then stop blushing. It is possible however that V6 will not recover from its ordeal and may have to be replaced. Also check MR1 (GEX35, OA70 or similar) which may have suffered some damage. Always check the two 12kΩ video load resistors.

Normal Raster, No Picture

If this is accompanied by a no sound condition the cause will normally be in the tuner but remember that the i.f. stage V4 is common to both vision and sound and check this. The tuner valves are B319 (PCC84, 30L1, etc.) and LZ329 (PCF80, 30C1 etc.). Either could be at fault to cause a no signals (or weak signals) condition. Apart from the usual poor stud contact—which responds to cleaning—however the tuner does

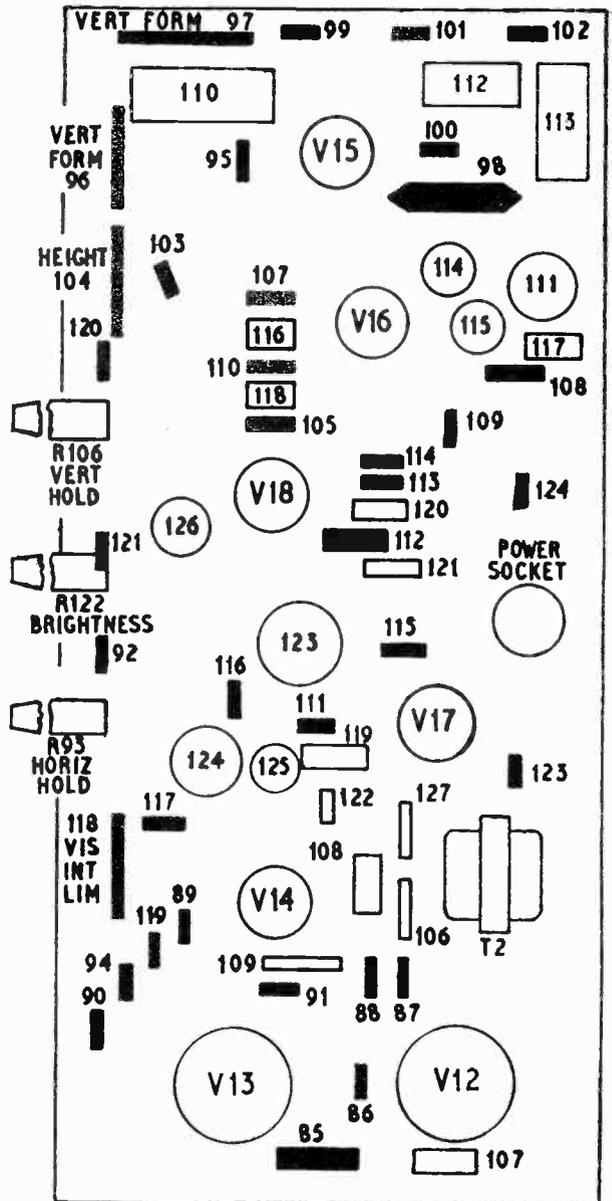


Fig. 4: Layout of the timebase printed panel. Capacitors shown in outline, resistors shown in solid black.

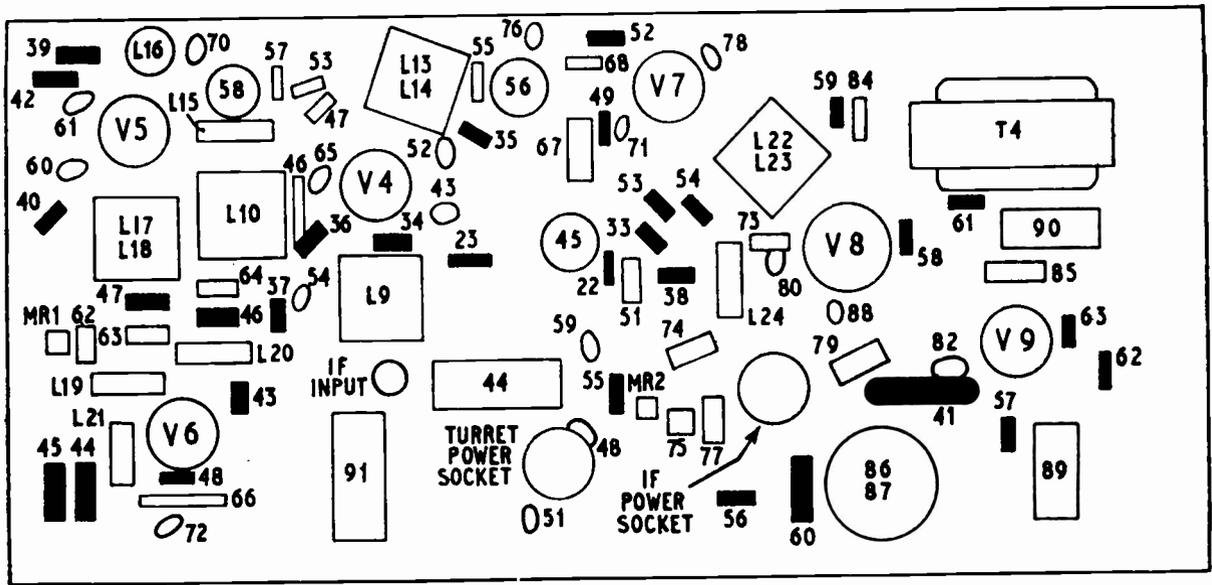


Fig. 5: Layout of the receiver section printed panel.

not give much trouble. Remember that the valve positions are the reverse of normal, V1 being at the front.

Picture Normal, No Sound

Whilst this could be due to a large number of factors it seems to have been our lot to find that usually the DH77 (6AT6, EBC90) has stopped functioning. If one of these is not to hand an EF91 (Z77) can be fitted for test purposes. This will produce some sort of weak sound at least to prove that the DH77 was in fact at fault.

Check V7, V9, MR2, R59 and the h.t. feed resistors R41 and R60 if necessary. And, er, by the way—make sure the speaker leads have been plugged in . . .

Sound Interference

A loud rustling noise varying in intensity often denotes a breakdown of the insulation between the pins of one of the two power plugs on the left side panel. Moving the plugs will often indicate which is at fault and therefore which is to be replaced (or the h.t. connection removed and made in some other way).

Sound-on-Vision

This is a very common complaint on these receivers. Normally it is due to the beehive type trimmers C58 (or C56) having been disturbed. C58 is the sound rejector trimmer and it is necessary for this and C56 to be finely set at 38.15MHz. A signal generator is not necessary if a constant tuning note can be received whilst the trimmers are set for minimum vision disturbance.

It is sometimes the case however that the trimmers cannot clear the sound-on-vision. This indicates that some form of undesired coupling is taking place. First ensure by turning the volume to minimum that this is not caused by vibration (a microphonic vision circuit valve will respond to sound waves in the cabinet or to vibration). Then check decouplers such as C45 (0.1 μ F a.g.c.) and C59 (h.t.). Valves V4 and V5 could

be faulty. It is also possible that one of the fixed capacitors across the trimmers has become faulty, but this is less likely.

Picture Shape and Size

Having a picture on the screen is one thing, having the right sort of picture is another. It is very common for the height of the picture to contract. Whilst this can be due to a number of factors it is the height control itself which in these receivers is most often at fault, developing one or more dud spots on its track. The only remedy is replacement: cleaning and attempting to repair the contact is rarely successful and is not worthwhile. To a lesser extent the same remarks apply to the linearity controls.

If these are not defective check the condition of the N379 valve (PL84 or 30P18), its bias electrolytic C111 and resistor R98.

The B729 (6-30L2) is occasionally at fault, mainly when the trouble is inability to lock or failure to open up the scan at all (because the valve is oscillating at the wrong frequency or not at all). The value of R105 is critical as far as the hold is concerned. Capacitors C110, C112 and C113 must be checked for leakage in the event of non-linearity.

Variation of Line Hold

The most persistent offender is V14, again a Z329. It is essential that a stable valve is used in this position and the first replacement tried may not be suitable. If the valve is not at fault check R90 and the values of R92, R93, R94 and R125 (if used).

Picture Shading

If the left side of the picture is brighter than the right check C149 which decouples the supply to pin 3 of the tube base: it could be open-circuit. If the top is lighter (or darker) than the bottom check the D77 (EB91) valve which could have heater-cathode leakage. V6 can produce the same effect but doesn't seem to so often.

LONG-DISTANCE TELEVISION

ROGER BUNNEY

NOVEMBER was a rather quiet month though conditions were about average for the time of year. The main highlight during the month consisted of improved Tropospherics over the period 2nd-3rd November, with various ORTF (France) transmitters on both v.h.f. and u.h.f. and—unusually here—the BRT (Belgium) E8 and E10 transmitters. Reports from other enthusiasts indicate that the improved conditions were widespread with various West German and other v.h.f./u.h.f. transmissions at similar distances. Unfortunately the Leonids Meteor Shower during the middle of the month did not give the expected increase in Meteor Scatter/Shower signals, only a slight improvement being noted. Possibly I was unlucky and missed the critical moment: did anyone else see anything? My log for the period is as follows:

- 2/11/71 CT (Czechoslovakia) R1 (MS); BRT E2,8,10 plus various ORTF (France) v.h.f./u.h.f. tropes.
- 3/11/71 NOS (Holland) E4 (tropes); ORF (Austria) E2a.E5; CT R1; via MS.
- 4/11/71 WG (West Germany) E9 (tropes).
- 5/11/71 TVP (Poland) R1 (Sp.E).
- 6/11/71 BRT E2.
- 8/11/71 NOS E4; WG E4 (MS).
- 9/11/71 CT R1.
- 10/11/71 NOS E4 (tropes).
- 11/11/71 DFF (East Germany) E4 (MS).
- 12/11/71 Switzerland E2 (MS); BRT E2.
- 13/11/71 NRK (Norway) E3 (Sp.E).
- 16/11/71 CT R1; NOS E4. An increase in MS was noted during the evening from the Leonids MS.
- 17/11/71 CT R1; WG E2 (MS).
- 18/11/71 BRT E2.
- 19/11/71 Switzerland E3 (MS).
- 20/11/71 ORF E2a; RAI (Italy) IB; both MS.
- 22/11/71 WG E4; DFF E4.
- 23/11/71 CT R1.
- 25/11/71 CT R1, NOS E4.

The opening of the new Belgian transmitter at Schoten on ch.E62 was just in time for the improvement in Tropospherics. This is located near Antwerp and we understand it is now operating with 200kW e.r.p. and that an electronic test card is in use. Our contact states that he has not seen this one in use before and we are awaiting further news and possibly a photograph. Whilst on the subject of test cards, the same contact advises that

the West German Deutsche Bundespost transmitters which carry the ZDF (2nd programme) are now using a test card with the identification "ZDF" within the centre of the electronically generated test card. Also, apparently, the HR (Hessischer Rundfunk) network in Germany is carrying a 15 minute news programme in English each Wednesday at 0645 (GMT).

We have had a report from our Dutch friend Peter van der Kramer saying that the Swiss test card has been noted carrying an identification "G". At present we do not know the reason for this new identification but are investigating. For the record the usual identifications on the Swiss card are as follows: Q experimental transmission; B Bellerive—studio for the German service; U Uetliberg—the main transmitter covering Zurich; D La Dole—the main transmitter covering the French speaking area of Switzerland; Z Studio Zurich. The identification is carried at the upper right-hand side of the test card. We understand that there is a possibility of a change in the normal Swiss test card but the card in its usual form is still being used at the time of writing.

News Items


Belgium: At present this country transmits using System C—that is positive-going vision modulation with a.m. sound. There appears to be a long-term plan for a change from this system to System B (negative-going vision and f.m. sound) as this is used extensively in Western Europe. The Band III transmitters at Wavre on chs.E8 and E10 will apparently be the first to change and this will allow for colour transmission. It would follow that the other Belgian transmitters on v.h.f. will eventually change to System B.

Holland: Our Dutch friends tell us that the Philips organisation is once again operating its own TV transmitter. The transmissions are on ch.E60 using an omnidirectional aerial, the transmitter power being 2kW. The Philips plant is at Eindhoven, south of the town of Waalre.

Monte-Carlo: We have recently reported on the activities of Tele Monte-Carlo with tentative television transmissions into the Northern Italy area. A second conflicting report has now come in—originating initially from a resident in Monaco—advising that only a low power (2kW e.r.p.) ch.E35 transmitter is being used at the Mt. Agel




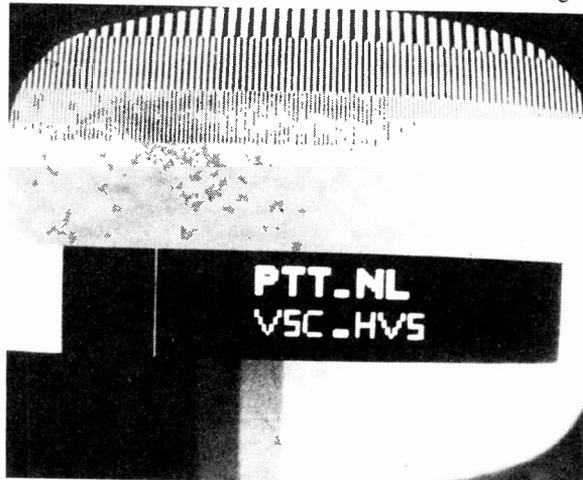
Main national news caption, Dziennik Telewizyjny, Warsaw, Poland. Courtesy OIRT Prague.



EBU test pattern in use with NOS Holland.

DATA PANEL 7—2nd series

ICELAND, EIRE

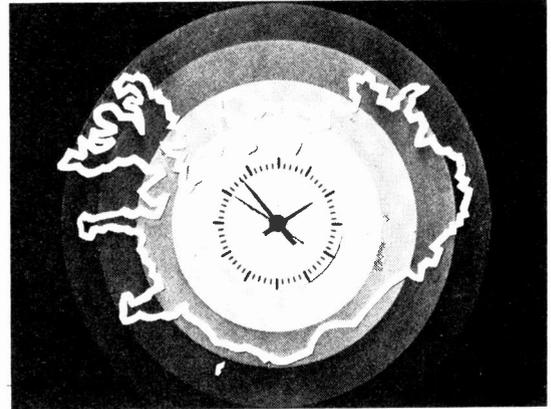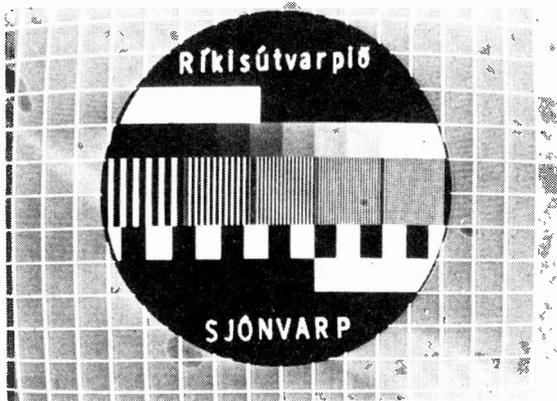


Above: Iceland Ríkisútvarpið Sjonvarp Test Card and Clock.

The above are official photographs issued by the broadcasting authorities. However, Iceland has been noted to use this card with or without the grid and rarely with the identification as shown here.

Right: Test Card used by Eire—Radio Telefís Eireann.

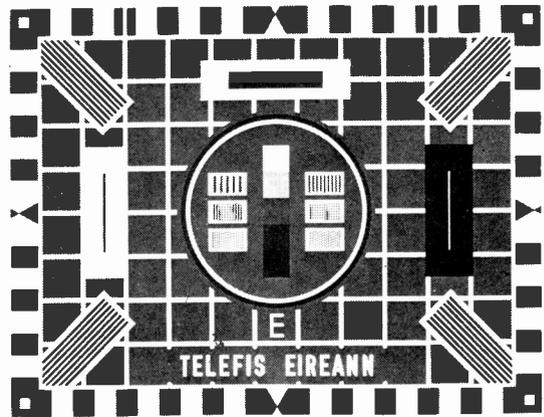Our thanks to the broadcasting authorities of both countries for their kind assistance in supplying information.



v.h.f. transmitting site. This is all very curious, especially in view of the very detailed first report. To try to get clarification we have written to our Italian contact at Bergamo to find out the true situation there.

ORTF-3

We have important news about the proposed new French network which will be known as ORTF-3. This network will commence operations towards the end of 1972 and will initially cover the Northern and Eastern parts of France. The network will expand rapidly to give near national coverage by the end of 1976. We understand that the first transmitters will be located at Paris, Lille and Strasbourg using 50kW units, the Lille transmitter having an e.r.p. of 1000kW. The Lille transmitter—actually Lille-Bouvigny—will operate on either ch.E24 or E27. I would make a guess and suggest that ch.E24 will be used by Lille as in the early days of Lille on ch.E27 interference problems were caused with NOS Lopik—also on ch.E27—resulting in Lille changing channel to ch.E21. The programme material will be “of a national rather than a regional theme”, and production facilities are to be encouraged outside Paris, the first main centres being at Lille and Marseilles. Programme transmission will be in colour—SECAM.

From Our Correspondents . . .

A new name in our correspondence column is Geoffrey Chapman of Blandford, Dorset who has obviously been very active during the summer months. He has written detailing the Sp.E openings logged at his home. Of particular interest is his reception of the West German

transmitter at Goettelborner Hoehe on ch.E2: this is a most difficult transmitter to receive, being vertically polarised, at a very short distance for Sp.E propagation and some 40 or so miles more distant than Luxembourg. The improved Tropospheric conditions during October were also noted at Blandford; one signal that gave a consistent strength through until nightfall was RTE-Dublin on the 7th October. Actually we are featuring this month the RTE test card in the Data Panel series.

Letters arrive from Eire from time to time and there seem to be a number of enthusiasts in that area. J. Bradley has received a number of signals during the summer and from his sketches we confirm reception of Switzerland and Poland. Mr. Bradley lives in the Dublin area and apart from a low-power ch.B3 transmitter the whole of Band I seems to be clear, certainly an unusual feature for most of us!

I. C. White of Farnborough, Hants, has written telling us of conditions there during October and of the stations received on his GEC portable and Baird colour receiver. The Dutch u.h.f. stations were particularly good in colour at high signal levels, and West Germany also. Mr. White was surprised to note that the Belgian u.h.f. network uses negative-going vision: in fact Belgium uses the same as West Germany and Holland for u.h.f. transmissions with positive-going vision for the v.h.f. transmissions only. The new EBU test pattern of NOS was also noted, carrying the long identification, and we are pleased to feature this photograph also with the column this month—thanks to our old friend P. D. van der Kramer.

From time to time letters arrive from overseas readers with the sender's address on the envelope only: as the envelope is often discarded and the letter then passed to

—continued on page 181



PART 5

K. T. WILSON

MOTOROLA TV ICs—2

DEMODULATION is one operation in a TV receiver that is particularly suited to integration. We saw in Part 1 the basic differential amplifier circuit—widely used in i.c.s—operating as an f.m. detector in an intercarrier sound i.c.: the circuit functioned as a quadrature detector for the f.m. input signal. The same basic circuit can however be used in other ways to provide demodulation, depending on the inputs applied to it. This month we are going to take a look at two Motorola detector i.c.s, the MC1330P which acts as a synchronous detector for the vision and sound signals and the MC1327P which acts as a chroma signal demodulator, RGB matrix and PAL switch. In both these i.c.s differential amplifier circuits are used as double balanced demodulators.

Video Synchronous Demodulator

The Motorola MC1330P low-level video detector is used in the new Decca 12in. mains/battery portable Model MS1210 and in the BRC 8000 single-standard colour chassis. Fig. 1 shows the i.c. in block diagram form together with the external circuitry as used in the BRC 8000 chassis. The input from the final i.f. stage is fed to an integrated emitter-follower at pin 7. This emitter-follower provides two drives, one to a limiter amplifier section and the other to the synchronous detector section. As is by now well known a synchronous detector requires two inputs, the signal to be demodulated and a reference signal to provide the switching action. In this case the 39.5MHz i.f. carrier is used as the reference signal. The limiter section removes the modulation and feeds the carrier to the external tuned circuit L108/C126. The 39.5MHz sinewave is then clipped and applied to the synchronous detector section. The detected output is fed to a video preamplifier section which provides across its external load resistors R126 and R232 the 6MHz intercarrier sound feed at pin 5 and the video signal at pin 4. L109/C129 remove the 6MHz signal from the feed to the luminance and chrominance sections of the receiver.

The use of this i.c. makes possible a number of basic changes in TV receiver design. First, detection is carried out at a much lower level (about 50mV) than is possible using a single diode detector. In addition

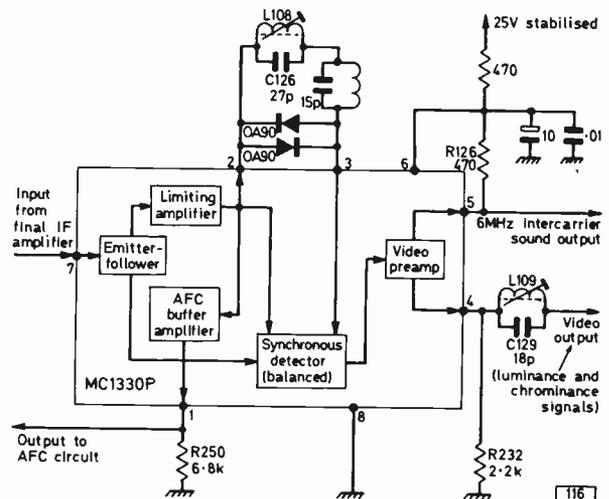


Fig. 1: Block diagram of the MC1330P low-level video synchronous demodulator i.c. together with the external circuitry as used in the BRC 8000 chassis. The carrier applied to the external 39.5MHz tuned circuit L108/C126 is used as the reference signal which gates the internal balanced synchronous detector. The latter provides full-wave rectification of the signal, giving an output consisting of half sinewave pulses of amplitude proportional to the modulation.

to providing more linear detection this means that less i.f. gain is required—making up the gain at v.f. is a simple matter. The advantages of this include less need for sound trapping, less critical tuning and more stable i.f. performance.

AFC Output

The i.c. also provides an output (a 350mV clipped carrier) across the external load resistor R250 to drive an a.f.c. circuit. In the BRC 8000 chassis the a.f.c. circuit consists of a limiter/amplifier stage, discriminator and d.c. amplifier.

Internal Circuit

The internal circuit of the MC1330P is shown in Fig. 2. The input emitter-follower is Q4. This drives the differential amplifier pair Q5/Q13 which forms part of the synchronous detector circuit and Q16 which with Q17 forms part of the limiter/amplifier section. The external 39.5MHz tuned circuit is connected between the collectors of Q16 and Q17 between which the clipper diodes D1 and D2 are also connected. As a result anti-phase squarewaves appear at the bases of Q8 and Q9 which act as emitter-followers driving Q7 and Q11, and Q10 and Q6, respectively. The double balanced synchronous detector consists of Q6, Q7 and Q5 on one side and Q10, Q11 and Q13 on the other side. The output is developed across the base-emitter junction of Q20 which is connected in the collector circuit of Q7 and acts as an emitter-follower to drive the video amplifier section Q23, Q24 and Q25. As we have seen external loads are connected to Q25—at its emitter and collector—providing the main output at pin 4 and an auxiliary output if required at pin 5. The carrier signal for the a.f.c. system is taken from the collector load of Q17 and passed via the buffer amplifier Q21, Q22 to pin 1. A d.c. supply of

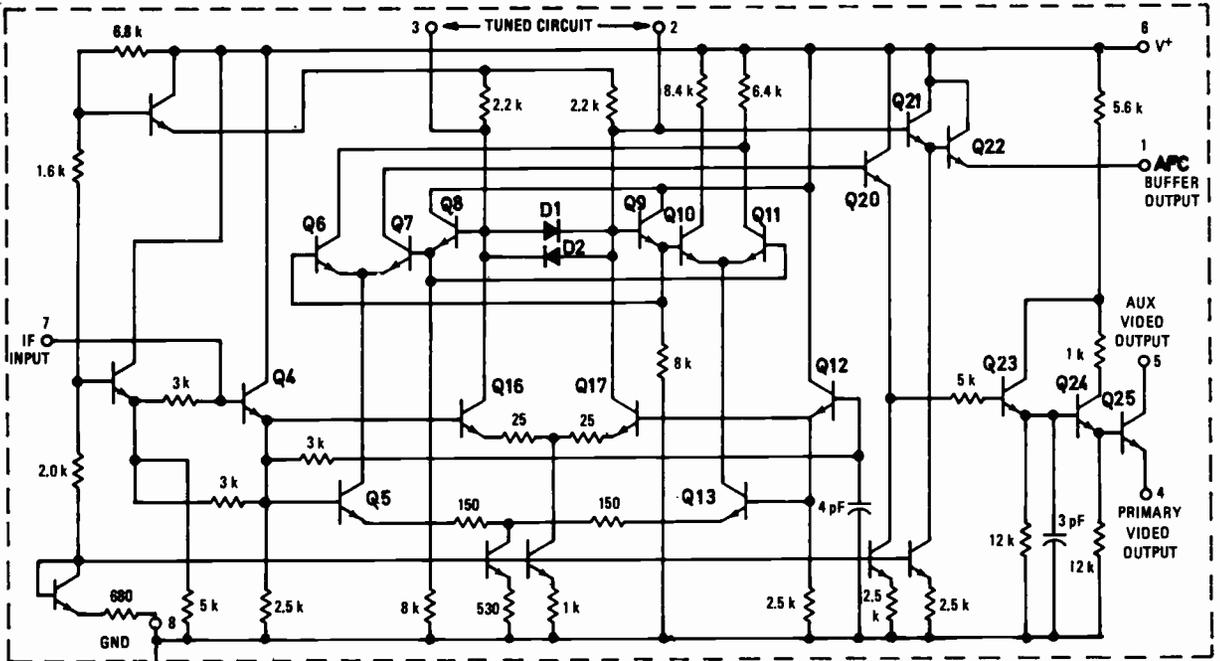


Fig. 2: Internal circuitry of the MC1330P video demodulator i.c.

about 20V stabilised is fed in at pin 6 while pin 8 provides the common earthing point.

Chrominance Demodulator

For chrominance signal demodulation, RGB matrixing and PAL V switching a Motorola type MC1327P i.c. is used in the BRC 8000 colour chassis. Fig. 3 shows a block diagram of the i.c. and the surrounding circuitry. The V and U signals, separated in the PAL matrix circuit part of which is shown, are fed in at pins 9 and 8 respectively to separate double-balanced chroma synchronous detector circuits which are of the same basic pattern as used in the MC1330P. The U and V reference carriers are fed in at pins 13 and 12 respectively, C178 and R191 giving a 90° shift

to the U reference carrier to obtain the correct quadrature conditions. The PAL V switch is built in and is driven by a waveform derived from the ident signal. This is fed in at pin 11. The luminance signal is fed in at pin 3 and line and field blanking pulses at pin 6: blanked RGB outputs are then obtained from emitter-followers behind pins 2, 1 and 4 respectively. A 5V peak-to-peak output signal is obtained with an input of 0.3V p-p and the i.c. incorporates a regulated power supply.

Acknowledgements are due to Motorola Semiconductors Ltd., Decca Radio and Television and the British Radio Corporation for their help with this and the previous part in the series.

TO BE CONTINUED

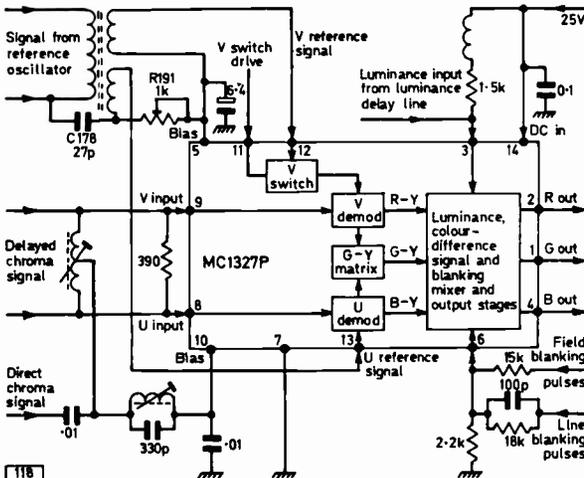


Fig. 3: Block diagram of the MC1327P chrominance signal synchronous demodulator, PAL V switch and matrixing i.c. which provides blanked RGB outputs. External circuitry as used in the BRC 8000 chassis.

FOR THE SERVICE ENGINEER

Meteronic (114-116 Shipbourne Road, Tonbridge, Kent) have introduced a fully portable lightweight oscilloscope, Model 113, featuring d.c.-8MHz bandwidth, 100mV/cm.-50V/cm. vertical sensitivity, 100nsec/cm.-150msec/cm. sweep speed range and a single control to cover all signal locking requirements. Power supply 7-9V d.c., size 8x6x4in., weight 3lb, price £93. Optional accessories are the MSB111 rechargeable Ni-Cd battery pack at £18, and the MSB112 mains/battery charger pack at £19.

To assist aerial riggers in siting and orientating u.h.f. aerials Labgear have introduced a new lightweight (5lb.) battery-powered u.h.f. signal-strength meter, Model CM6016/SM. The meter reads from 30µV to 3mV in four switched ranges to an accuracy of ±6dB and detects the peak amplitude of the signal to which it is tuned. Withdrawal of the aerial feeder plug automatically switches the instrument off and a circuit is incorporated to differentiate visually between the sound and vision carriers. The recommended trade price is £40.

THE N. BANTON DO-BE OSCILLATOR

THE changeover to the 625-line u.h.f. standard brought many problems to the amateur TV constructor but his infinite patience and not a little ingenuity resulted in a spate of converted receivers many of which were never intended to operate in this way. We well remember the time of an even greater conversion epic, when the Ministry of Supply unloaded its surplus v.h.f. gear in the late forties and for many of us opened the door to a new hobby and a wider technology. It was in those days that the family egghead, so called because of his preoccupation with junky old wireless sets, came into his own in producing for all to see a moving—albeit green—picture on the end of his thirty bob VCR97.

Timebase Conversions

The point to be made here however is that some of the types of problems encountered then are now causing trouble with u.h.f. conversions—namely finding reliable timebases and in particular line generators. Much depends of course on the type of set being converted, but even sets designed by the manufacturers for conversion can suffer from jittery locking when this is undertaken. The Thorn 850 convertible chassis for example can be critical in this way even with the flywheel sync circuit used in the conversion kit. Blocking oscillators are a firm favourite and can generally be easily modified for u.h.f. operation, but here again the triode types can be jumpy: pentodes are better but are much less frequently encountered. Many early models are suitable for trying out as conversions but are not equipped with facilities to enable flywheel sync control to be used, e.g. they may not have a winding on the line output transformer from which a suitable reference pulse for a flywheel circuit can be obtained. This is not to say that flywheel sync cannot be added in some way but if this is attempted will the locking

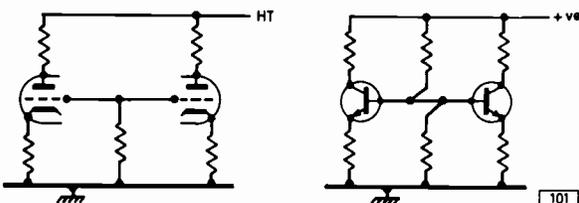


Fig. 1: Basic do-be (double beam) configurations, left valve circuit and right transistor circuit.

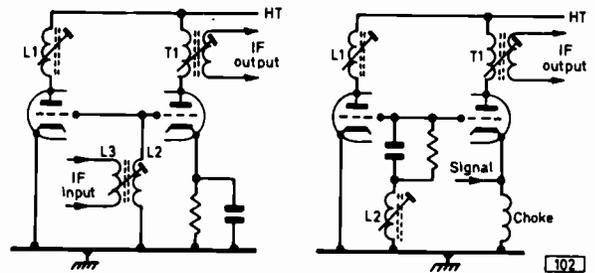


Fig. 2 (left): The do-be circuit used as an i.f. amplifier. The circuit is slightly regenerative but does not appear to sharpen the tuning or narrow the bandwidth.

Fig. 3 (right): The do-be circuit as a tuner, with the left-hand triode as local oscillator (L1 and L2 coupled to give the required feedback) and the right-hand triode acting as mixer to give an output at i.f.

be good enough without further modifications to the timebases? Let us not forget that amateur interest apart the other reason for doing the conversion is to save money.

Basic Do-Be Circuit

Can we then find a timebase generator that is sensitive enough to lock on to a mediocre strength sync pulse? After all if the display is good enough to watch the sync pulses should be reasonably strong. The answer I have found is the do-be, i.e. double-beam, oscillator. The basic circuit is shown in Fig. 1 and consists of two amplifying devices strapped together gridwise or basewise as the case may be. This simple circuit can be useful in a number of ways with the same basic configuration but different components. For example in Fig. 2 it is an i.f. amplifier: no gimmick, it is working at present in a u.h.f. set. The circuit is slightly regenerative but does not appear to sharpen the tuning or narrow the bandwidth. In Fig. 3 the circuit is a tuner. It could be a quadrature detector and so on but the version we are interested in is shown in Fig. 4 because here it is a timebase oscillator: uncomplicated, simple and with excellent stability.

Do-Be Timebase Generator

In this circuit V1a operates as a blocking oscillator with the l.f. transformer L1, L2 and the timing circuit C1, R2, R3 and R4. V1b acts with R1 and C2 as a linear sawtooth generator. On switch-on both valves conduct. The anode coil L1 produces a voltage across the grid coil L2 and this drives both grids and consequently the two valves hard on. V1b anode voltage falls rapidly, discharging C2 to give the flyback portion of the waveform. V1a anode voltage is of course also falling. As the valves approach saturation grid current flows producing a negative charge on C1 which cuts the valves off. C1 then commences to discharge via R2-R4 while C2 charges via R1 to give the forward scan portion of the waveform. When C1 has discharged sufficiently for the grids to reach the cut-on point the action is repeated.

V1a anode is not cluttered with components to interfere with its easy action and L1 is very sensitive to even a modest negative-going sync pulse. The circuit has given excellent results without flywheel sync but this can of course be added by following the usual practice with blocking oscillator circuits. The

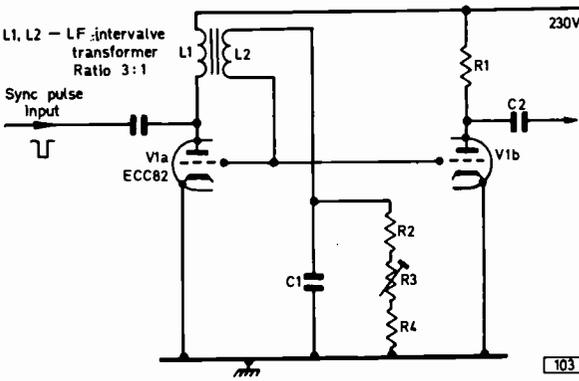


Fig. 4: The do-be circuit as a timebase generator, with V1a connected as a blocking oscillator and V1b acting as a discharge valve. When V1b conducts C2 discharges to chassis, giving the flyback portion of the timebase waveform. R3 provides hold control.

variable resistor in the grid leak network—giving hold control—can be altered in value to suit individual choice providing the fixed resistors are altered in proportion: some constructors no doubt prefer finer control. A noisy variable resistor will obviously give trouble in this position. Blanking pulses can be taken from V1b anode.

Practical Circuits

Figures 5 and 6 show respectively the line and field timebases—using do-be oscillators—in my conversion of the GEC Model BT2747. The timebase output stages and the power supply arrangements are in fact the only original circuits left on the chassis!

The do-be timebase generator is well worth a trial by anyone suffering with jittery locking and where the set initially uses a separate oscillator valve it should not be too difficult to instal this circuit. Where a blocking oscillator transformer is present on the set being converted this can be used for the do-be circuit: otherwise a 3:1 ratio l.f. transformer is suitable. Separate decoupling of the h.t. supply to the do-be oscillator has not been found to be necessary though I always use separate choke/capacitor smoothing to the timebase panel and i.f. amplifiers.

Thorn 850 Conversion

In a recent conversion of the Thorn 850 convertible chassis I found it worthwhile converting the field generator to a do-be circuit. This chassis is well worth spending a little time on: it's the one where you hang the u.h.f. conversion panel on the top rail rear. When all three programmes became available locally on u.h.f. I decided to chuck out the v.h.f. panel and do a complete u.h.f. modification: it would at least mean that I could close the back of the set again! It is not a difficult modification and the end product is a good u.h.f. set. I found the timebases to be a bit touchy but after experimenting with one or two sync separator circuits I got the line hold to settle down. The field hold continued to be jumpy even though all components likely to affect matters were replaced. So I decided to change to a do-be oscillator.

The modification consists mainly of substituting a transformer for the multivibrator components originally used—the existing valves are used in the conversion as are R145-R147 and Z3 in V13a anode

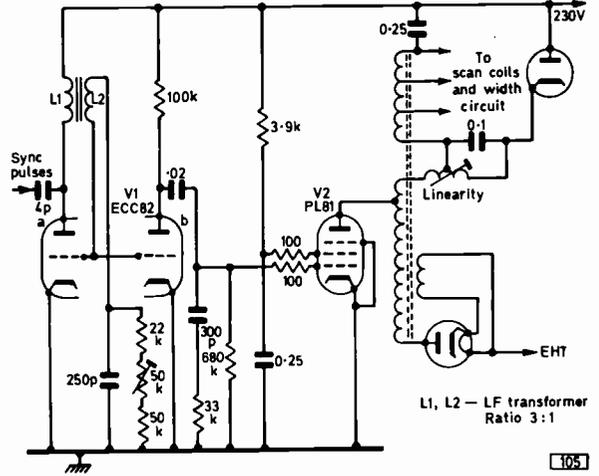


Fig. 5: GEC Model BT2747 line timebase conversion with do-be generator stage.

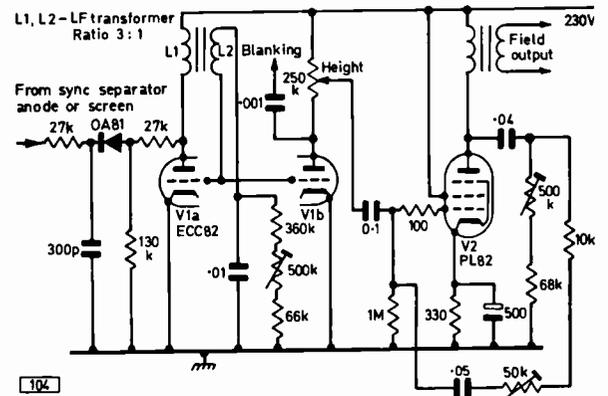


Fig. 6: GEC Model BT2747 field timebase conversion with do-be generator stage.

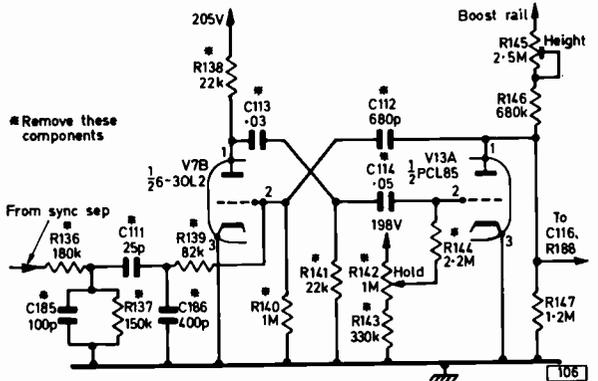


Fig. 7: Original field generator (multivibrator) stage used in the Thorn 850 convertible chassis, showing the components to be removed for the suggested conversion.

circuit. The field output stage V13b is not altered. Fig. 7 shows the components that have to be removed and Fig. 8 the completed modification. To make room for the 3:1 ratio blocking oscillator transformer I removed the smoothing capacitor block from the left-hand side of the chassis (looking from the rear). Room for the capacitors was found on the top rail using a spring-type clamp. The do-be oscillator grid leak resistors can be altered to suit the user—a 500kΩ

NEXT MONTH IN

TELEVISION

RENOVATING THE RENTALS

A large number of ex-rental sets are now appearing on the second-hand market and with judicious renovation can be made to give useful service for some time—particularly for the booming market in second sets. Many of these sets exhibit common stock faults and in this new series we shall be passing on tips and advice to help get—and keep—these sets going.

LINE TIMEBASES OF THE FUTURE

One of the developments that is likely to be with us before long is the slimline colour set, i.e. one fitted with a 110° shadowmask tube. The main technical difficulty concerns the line scanning and next month we shall be examining an interesting development—a thyristor line output stage—that has been evolved for this application.

COLOUR RECEIVER INSIGHT

A great deal of uncommon circuitry is to be found in colour chassis—the sort of thing you've not come across before and can spend hours puzzling over. So we've decided to take the lid off, so to speak, and explain in detail just what those apparent circuit mazes do. Starting with the ITT-KB CVC5 chassis.

SERVICING TELEVISION RECEIVERS

The next chassis to be covered in this popular feature is the Bush TV103/TV105 series.

PLUS ALL THE REGULAR FEATURES

Advance News: Starting in the **April** issue, the **TELEVISION Colour Receiver for the Constructor.**

ORDER YOUR COPY ON THE FORM BELOW

TO.....
(Name of Newsagent)

Please reserve/deliver the MARCH issue of TELEVISION (20p), on sale FEBRUARY 21, and continue every month until further notice.

NAME.....

ADDRESS.....


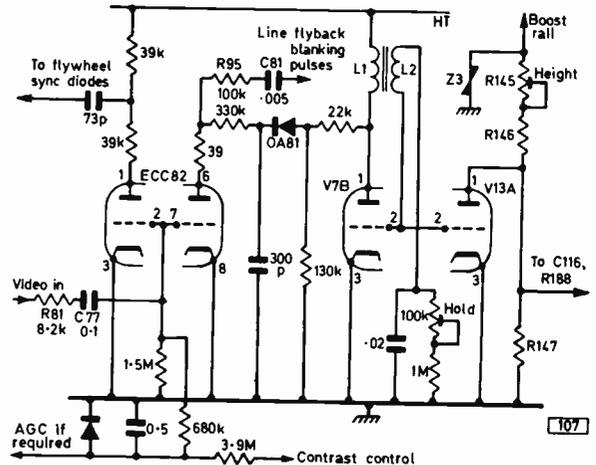


Fig. 8: Thorn 850 field timebase modification using a do-be generator stage.

Fig. 9: The field sync separator circuit shown in Fig. 8 locks the generator well with the set correctly tuned but is of a rather experimental nature. A more conventional arrangement that has been used successfully to lock do-be field generator circuits is shown here.

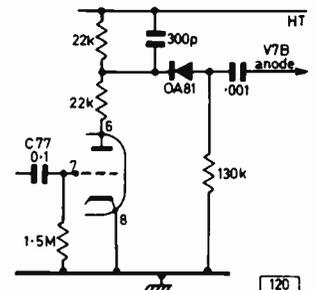

variable plus 680kΩ fixed resistor for example may be used—providing you obtain centre locking as near as possible. These oscillators are easy to set up and play around with—at least at these frequencies. The output is far more than adequate and the linearity excellent. If the original presets in the Thorn 850 chassis are still in circuit a replacement will be required for the field hold control (R142) since the original 1MΩ variable resistor is too big for use with this circuit. The modification is an easy one and although some constructors may think that the sync separator arrangement is a bit odd my excuse—if one is needed—is that it works! Those wishing to use an alternative however could try the field sync separator circuit shown in Fig. 9 which I have used with other do-be oscillator conversions. I mounted the ECC82 sync separator by the way in place of the 200μF electrolytic (C380) on the Thorn conversion panel. The set is working at present without a.g.c. and gives very good results: I intend however to build in an a.g.c. circuit suited to u.h.f. use in due course. Those wishing to retain the mean-level circuit in such a conversion can do so in the manner shown in Fig. 8. Changing the line oscillator to a do-be circuit doesn't seem worthwhile: the existing circuit is a blocking oscillator anyway and works well with the flywheel circuit on the conversion panel. The line hold control is sharp but does not slip.

This then is the do-be timebase oscillator. Perhaps it is not used commercially because it requires two triodes and a transformer whilst most commercial circuits use either two valves (multivibrator) or one valve and a transformer (blocking oscillator on its own). But do try it, in the place of those commercial Christmas trees!

SIMPLE OUTDOOR UHF AERIAL

K.E.G. Pitt B.Sc.

THE aerial described in this article does not fall readily into any of the commonly used types but instead is a mixture of several. It started life as a corner reflector but as this type of aerial is rather too bulky for outside use the reflector size was reduced to half wavelength square (from one wavelength by two). A single dipole is mounted about $\frac{1}{2}\lambda$ in front of the reflector. As shown in the photograph the aluminium reflector sheet may be bent to a roughly parabolic shape—a marginal increase in gain is found if this is done. The aerial does not have high gain but nevertheless gives quite good results in fairly strong signal areas. Its main advantage is that it is very short and may be mounted quite unobtrusively just inside or outside a window. The group C version shown measures only 4½in. from the front of the insulator to the back of the reflector. It will thus fit easily behind the curtains where it will pick up almost as much signal as when it is mounted outside.

The cross bar and dipole halves are cut from $\frac{3}{8}$ in. aluminium tubing while the reflector and its mounting bracket are sheet aluminium—the prototype used 18 s.w.g. sheet but the gauge used can be chosen with regard to availability and the strength needed to combat the weather if mounted outside. The aerial mounting bracket to the wall is similar in design to those used for the aerials described in the August 1971 issue. The block holding the dipole is made of wood:


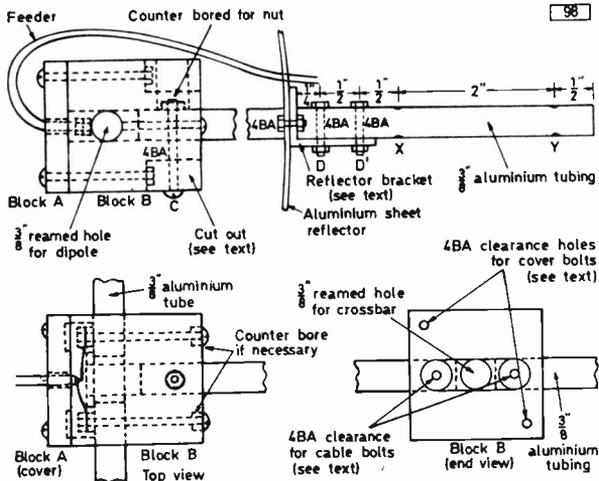


Fig. 1 Constructional details.

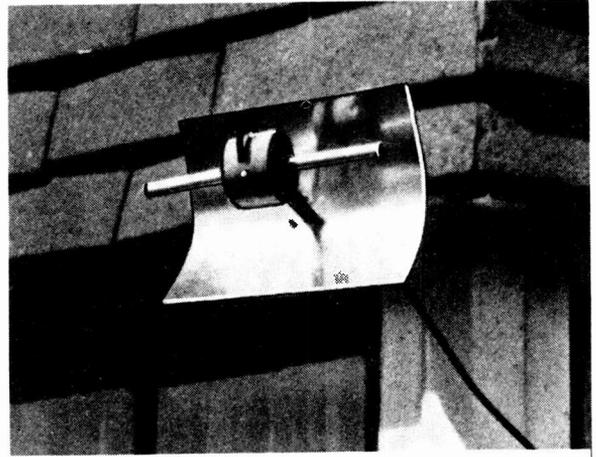

details are shown in Fig. 1. The aerial dimensions are listed in Table 1.

Table 1: Aerial Dimensions

Group	Spacing (in.)	Dipole length (in.)	Reflector sides (in.)
A	5.1"	2 × 5.3"	11.5" × 11.5"
B	4.1"	2 × 4.3"	9.0" × 9.0"
C/D	3 $\frac{3}{8}$ "	2 × 3.5"	7.5" × 7.5"


The reflector consists of a sheet of aluminium one half wavelength square and the cross bar passes through a tight fitting hole at its centre. The cross bar is clamped to the reflector by means of a bracket of similar material. In the prototype the bracket is 1½ by 2in. and is bent into two halves at right angles, each 1½ by 1in. A tight clearance hole for the cross bar is made in the bracket so that it is tangential to the bend. The cross bar is then inserted through the holes in the reflector and bracket as shown in Fig. 1 and two 4BA clearance holes made, one either side of the cross bar. Two holes—D and D'—are drilled as shown for 4BA bolts to secure the cross bar to the bracket. Holes X and Y are 2BA for attachment of the aerial assembly to a 12 s.w.g. aluminium mounting bracket which should be Rawlplugged to the wall or window sill.

Dipole Assembly

One of the difficulties in making weather-proof outside aerials is to construct a block which both supports the active elements and also protects them from corrosion. For this model two wood blocks are used and these should preferably be of one of the hard woods. As shown in Fig. 1 block A acts as a front cover for the actual mounting block (B). It is 1½in. square by ½in. deep. At its centre a tight clearance hole is drilled for the cable. Block B is a 1½in. cube. A pair of 4BA clearance holes are drilled at diagonally opposite corners through both blocks as shown in Fig. 1 to hold the cover on. After completion of the aerial two blind holes are drilled in block A to cater for the proud ends of the cable fixing bolts and their nuts. This will enable the two blocks to fit closely—the basis of the weather seal.

Block B has a $\frac{3}{8}$ in. reamed hole at its centre as
—continued on page 181

A CLOSER LOOK AT

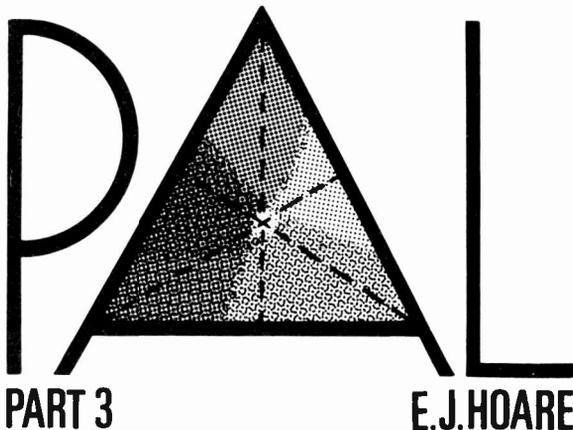

PAL DECODING ERRORS

No colour television receiver is immune to errors of hue and saturation caused by distortion of the signal or by imperfections in the design or alignment of the decoder and i.f. channel. Now although PAL is a very robust system there are bound to be imperfections in the chrominance content of the picture and it is instructive to see how these can occur. We are going to interpret the title of this article a bit loosely and include any cause of chrominance distortion affecting the signal whether it arises in the decoder circuits or elsewhere: this will enable us to discuss some of the interesting side issues which tend to get overlooked.

A good starting point in our discussion of chrominance distortion is the subject of Hanover bars or blinds. The presence or absence of blinds on a picture has more significance than is often appreciated, and an understanding of the processes involved is almost by definition an understanding of decoding itself.

Hanover Bars or Venetian Blinds

Anyone who begins to study the mysteries of PAL colour television techniques is almost immediately introduced to this phenomenon. It has an intriguing sounding name and is easy to identify on the screen of a receiver. It consists of pairs of horizontal lines on coloured areas of the picture and the degree of visibility depends upon the amount of colour present. Even a student can spot the effect quite easily and he retires happy in the knowledge that he has learnt something useful! Unfortunately the real significance and value of blinds and the mechanism by which they occur is seldom explained to him.

The fact of the matter is that blinds are a wonderful built-in test of decoder design and alignment, and are characteristic only of the PAL system. In NTSC the decoder alignment is very critical and difficult to assess: in PAL the alignment is not very critical and is easy to assess. If you inspect a well saturated colour picture on a PAL receiver and see no blinds at all you know immediately and without any further testing that most aspects of the decoder alignment are correct or at

least sufficiently so for practical purposes—by this we mean that the subcarrier (PAL) delay line matrixing and the synchronous demodulation processes are O.K. Conversely if blinds are present to an appreciable extent you can be certain that the alignment is not very good and needs checking. Furthermore if the blinds are clearly visible you can sometimes deduce what the errors actually are. There must be very few pieces of electronic equipment where this built-in checking facility is inherent in the system!

What are Blinds?

Blinds are caused by differences in luminance, hue or saturation between consecutive lines of a field. Due to the use of interlaced scanning this appears as differences between consecutive *pairs* of lines on a picture and gives rise to a rather coarse structure. Furthermore because of the four-field sequence of V axis switching with respect to the line scanning the eye strobos the blinds and they appear to be moving steadily up the screen of the c.r.t.

Differences in chrominance information between consecutive lines can be caused by misalignment of the decoder or by differential phase distortion either in the decoder itself or more commonly in the incoming signal. The effects are often aggravated by the breakdown of the constant luminance principle—but we will discuss this separately because it tends to get a bit complicated. Another cause of blinds is poor design of the decoder whereby crosstalk occurs between the two colour-difference signals. If R-Y gets into the B-Y channel or vice versa blinds will occur unless the demodulation phases are highly accurate.

Decoding an Undistorted PAL Signal

If we take a magenta hue the chrominance subcarrier and burst phases on alternate lines are as shown in Fig. 1. Fig. 2 is basically the same diagram but this time we have described the magenta hue in terms of the U and V colour-difference components which when modulated together give the chrominance subcarrier shown in Fig. 1 (and dotted in Fig. 2). You will notice that in all PAL phase diagrams a mirror image of V about the U axis is obtained on alternate lines.

In decoders incorporating a delay line there are two separate processes that have to be carried out in order to obtain the detected + or -U and V signals. With suitable adjustments of gain (de-weighting) in each channel these then become $B-Y=2.03U$ and $R-Y=1.14V$. The two processes are delay line matrixing and synchronous demodulation.

The purpose of the delay line is to store up information so that the chrominance subcarrier from one line of the picture can be mixed with the subcarrier from the line before to give completely separate U and V carriers. This not only makes the process of synchronous demodulation more accurate and less critical but also enables electronic averaging to cancel out certain errors.

Figure 3 shows the U and V components of our magenta hue on four successive lines. Now if we take the U and V subcarriers from lines 2 and 3 and add them we get $2 \times U$ as shown in Fig. 4(a) because the V carriers cancel. Similarly if we subtract one carrier from the other the U carriers cancel and we get $2 \times V$

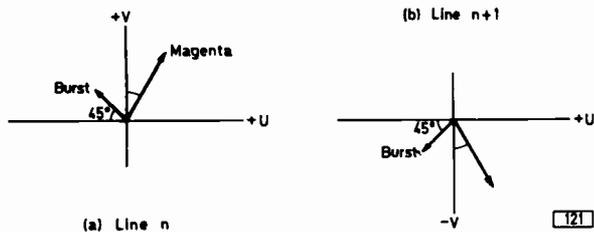


Fig. 1: The phase of the chrominance subcarrier on alternate lines corresponding to a magenta hue.

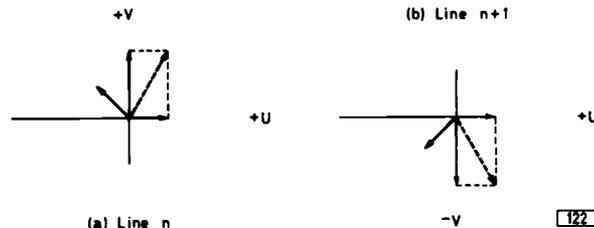


Fig. 2: The phase and amplitude of the V and U signal components that form the resultant chrominance subcarrier shown in Fig. 1 (and also in broken line above).

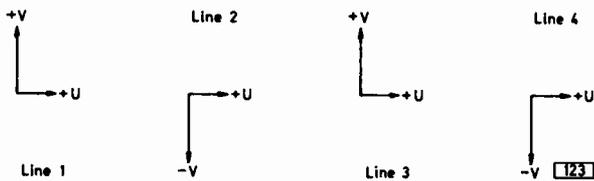


Fig. 3: The U and V components for four consecutive lines of a magenta hue (burst omitted).

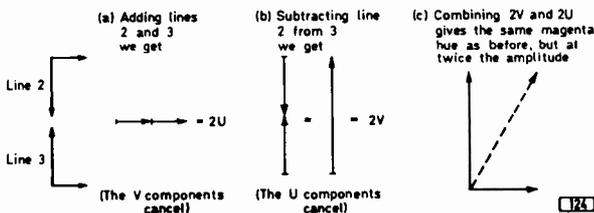


Fig. 4: The delay line matrixing process. Under correct conditions the U and V components of the signal are separated without distortion.

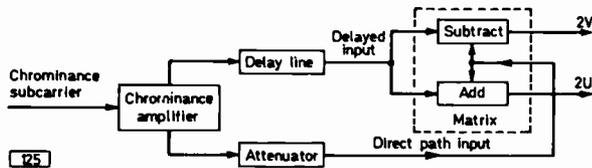


Fig. 5: Block diagram of the PAL delay line and its add and subtract matrix network.

—see Fig. 4(b). If we take lines 3 and 4 instead of 2 and 3 we get precisely the same answer and since consecutive outputs are identical there can be no blinds. We are assuming for the purpose of our example that the same chrominance information is being transmitted on all four lines. In practice this is substantially true and the principle breaks down only over the small picture areas where one hue changes to another and the transition is abrupt.

The delay line matrixing operation takes place in a circuit shown in block diagram form in Fig. 5. The U and V carriers obtained from the add and subtract

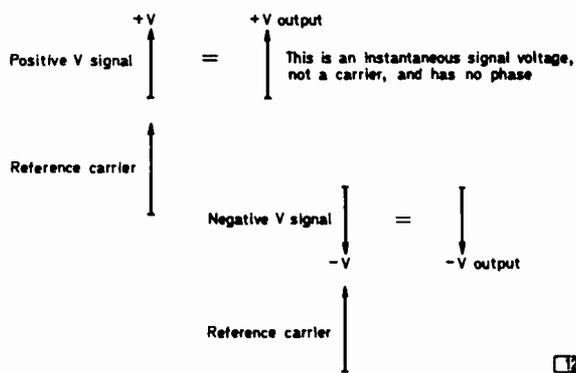


Fig. 6: Synchronous detection measures not only the amplitude of the U and V subcarriers but also their polarity, i.e. whether positive or negative at the instant when the demodulator is switched on by the reference carrier.

networks are then demodulated by two separate synchronous detectors. The U detector is also fed with a locally generated reference carrier in the same phase as the +U axis while the V detector is fed with a reference carrier switched 180° from line to line in the same phase as the V axis (alternatively the V signal itself may be switched 180° from line to line before being fed to the V detector).

Correct and Incorrect Demodulation

Thus if all is well with both reception and decoding a reference carrier exactly in step with the wanted U or V carrier is used at the demodulators as a switch so that the demodulators measure (a) the instantaneous amplitude of the U or V carrier and (b) its polarity (positive or negative). See Fig. 6.

It is important to note that if all is well no U signal appears in the V channel and vice versa. Clearly the detected V output should not contain any U signal. If the delay line matrixing is correctly carried out but the reference carrier applied to the V detector is in the wrong phase the detected V signal will be too small but at least will contain no U component.

A different situation arises if the matrixing is inaccurate: the U and V channel signals are then not completely separated and the U and V detectors can give outputs comprising a mixture of both.

Reference Carrier Phase Errors

We have just seen that if decoding is correctly carried out there is no difference in the information from line to line—assuming the input signal remains the same—so no blinds will be present on the picture. Now let us see what happens when the phase of the reference carriers applied to the demodulators is incorrect. We will assume an error in the quadrature conditions: i.e. one axis correctly demodulated and the other not.

Incorrect Quadrature Conditions

Let us take the same magenta hue as before and assume that the delay line matrixing is perfect. Thus the V channel contains only a pure V subcarrier and the U channel only a pure U subcarrier. Fig. 7(a) shows our V subcarrier in its correct phase and a reference carrier from the local reference oscillator with a very definite phase error (β) of about 20°. These two

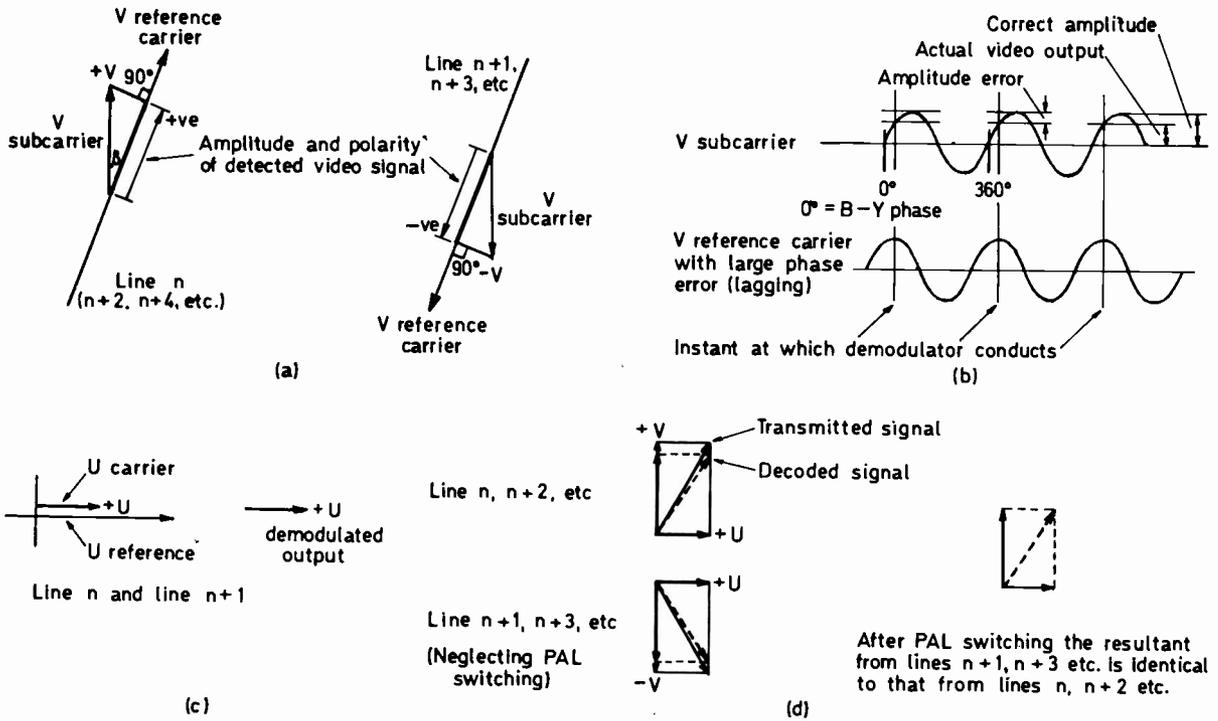


Fig. 7: (a) Vector diagram showing incorrect demodulation due to a shift in the V reference carrier phase. The amplitude of the demodulated signal = $V \cos \beta$. The amplitude error = $1 - V \cos \beta$ (β = the phase error of the reference carrier). (b) The same process as in (a) but drawn with sinewave carriers instead of vectors: how much more tedious to draw! (c) Accurate demodulation of the U signal because the phase of the U reference carrier is correct. (d) The resultant obtained from an incorrect V output and a correct U output from the demodulators is a hue error together with reduced saturation. The errors are identical on every line and thus no blinds are present on the display.

carriers are applied to the V synchronous demodulator and the outputs on every line will be pure V—since the V channel contains nothing else—but at a reduced amplitude. The amplitude will be the same on every line.

A different phase diagram showing exactly the same process is drawn in Fig. 7(b) only here we have abandoned vectors and used sinewave carriers instead. You will see that at the instant when the reference carrier is at its positive peak and the demodulator diodes open to measure the amplitude and polarity of the V signal carrier this is at less than its peak value. Thus the demodulator output is incorrect, i.e. too small. Now suppose that the U demodulator reference phase is correct: Fig. 7(c) shows that the correct U output is obtained.

What then is the overall result? If we add together the slightly small V signal and the correct U signal the resultant is rotated away from its original position and its length is reduced as shown in Fig. 7(d). This means that the transmitted hue and saturation have been changed in the decoding process. The magenta hue has become slightly too blue and the saturation has been reduced. Furthermore due to the incomplete application of the constant luminance principle—inherent in all present-day colour broadcast systems—any hue error is accompanied by a change in luminance because the chrominance signal carries some luminance information. Thus the saturation suffers a further error.

The effect of the hue and saturation errors on the picture is fairly small for the sort of demodulator phase

errors that occur in practical circumstances. A saturation error can easily be corrected by adjusting the saturation (colour) control. The hue error cannot of course be corrected at all in a delay line PAL receiver. Usually it will pass unnoticed except on subtle hues such as skin tones and these are commonly affected much more by errors of grey-scale tracking than by errors of demodulation.

So far we have discussed the case of a quadrature error, assuming that the static phase of the reference oscillator a.p.c. loop is correct and thus (in our example) that the U reference carrier is correctly phased on the U axis. The V reference carrier was rotated off the V axis so that the two reference carriers were not 90° apart: i.e. not in quadrature. Now let us consider the situation when the two reference carriers are in quadrature but the reference oscillator a.p.c. loop has a phase error which causes both reference carriers to be rotated equally away from their respective axes.

Reference Oscillator Phase Error

It is common practice to feed the output of the reference oscillator direct to one demodulator and via a 90° phase-shift network to the other demodulator. The V reference carrier (or V chrominance subcarrier) is switched 180° on alternate lines. The two reference carriers may be in perfect quadrature relationship (a phase difference of 90°) but if there is a phase error in the output of the reference oscillator this error will be applied equally to both demodulators.

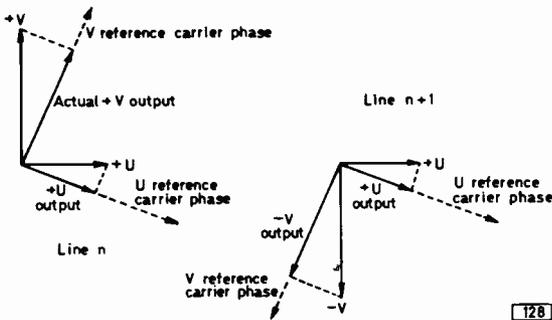


Fig. 8: With equal phase errors on both the U and V axes the U and V signals are reduced by the same proportion on all lines.

Figure 8 shows the same V and U components as before and the effects of a demodulation phase error of the same amount on each axis. It will be seen that both the V and U outputs are reduced in proportion. When these outputs are combined we get a resultant at the same angle as before, and therefore the same hue, but of reduced length. So we have the correct hue but at a reduced saturation. Note that the outputs on alternate lines are completely symmetrical and of equal amplitude and so there are no blinds present on the picture.

Causes of Blinds

Our quest for the causes of blinds has so far not been very productive but we have at least established the effects of demodulation phase errors on an accurate PAL chrominance signal. It is clear that the asymmetrical effects of a quadrature phase error are more important than those resulting from, say, a static phase error in the a.p.c. loop. You can always adjust the saturation control, but you can never adjust the hue—at least not with PAL.

If you think about it you will see that an accurate PAL chrominance signal applied to the demodulator can never result in the asymmetrical differences in output from line to line that are the cause of blinds. For blinds to occur there has to be a spurious switched component somewhere that gets demodulated differently on alternate lines. If for example there is a switched (i.e. 180° phase alternated) V component in the U channel then the U demodulated output will vary from line to line in the kind of way that we are looking for. The errors need only be quite small because the eye is very sensitive to changes in brightness or saturation, although less so to changes of hue.

More generally any kind of crosstalk that causes an unwanted V signal to appear in the U channel or U to appear in the V channel means that the delay line separation process has been partly nullified and some of the advantages of delay line PAL have been lost. Crosstalk between the U and V channels can occur

in a number of ways but the most obvious one is the case where the delay line matrixing has been inaccurately adjusted.

Matrix Adjustments

There are two operations that have to be carried out in setting up the delay line matrixing. In the first place the amplitudes of the delayed and undelayed signals must be precisely equal. This is usually achieved by means of a potentiometer in the undelayed signal path. A typical delay line causes an attenuation of about 15dB in the delayed signal and this must be matched by an equal degree of attenuation in the undelayed path (or appropriate gain must be introduced in the delayed signal path). We then get the amplitude relationships illustrated earlier in Fig. 4.

The other adjustment concerns the phase of the delayed and undelayed chrominance signals. Clearly the delay time must be equal to one line scanning period if electronic averaging is to be carried out between a picture element on one line and the similar element on the line immediately preceding it. Now although we need very accurate timing in the delay line in order to get nearly perfect registration of these two picture elements the vital factor is not the registration but the phase of the delayed and undelayed carriers. The phase difference between them must be kept to within about $\pm 3^\circ$ if complete separation of the U and V components of the chrominance subcarrier is to be achieved. This is equivalent to a delay time accuracy of about $\pm 2\text{nS}$ ($1\text{nS} = 1/1,000\mu\text{S} = 10^{-9}$ seconds). You can check this on the basis that there are 283.5 cycles of the subcarrier in one line period of $64\mu\text{S}$.

Effect of Amplitude Differences between the Direct and Delayed Signals

If we take the matrix circuit shown diagrammatically in Fig. 5 and make the amplitudes of the delayed and undelayed paths unequal what is the result? Fig. 9(a) shows the U and V components of the chrominance subcarrier for three consecutive lines of the picture. These are the inputs to the delay line matrix. Now if we make the direct signal which bypasses the delay line too large we get the signal components of Fig 9(b) in the matrix (mixing circuit) on lines 2 and 3. These U and V components are added at (c) to give the U output and subtracted at (d) to give V. Note again that the direct path signal is too large. Also we are subtracting the delayed signal from the direct one.

The results at (c) and (d) are not at all good. The U signal has incorrect amplitude—it is too large—and worse still it contains a switched V component. The V signal is also too large and it contains an unswitched but unwanted U component.

If we combine these U and V components in order

Summary of Decoding Errors

Perfect signal and matrixing

- Static phase error causes desaturation
- Quadrature phase error causes change of hue

Perfect signal, faulty matrixing

- Matrix amplitude error with correct demodulation causes saturation errors
- Matrix amplitude error plus incorrect demodulation causes hue and saturation errors which produce blinds
- Matrix phase error with correct demodulation causes hue errors and blinds
- Matrix phase error plus incorrect demodulation causes hue and saturation errors and blinds

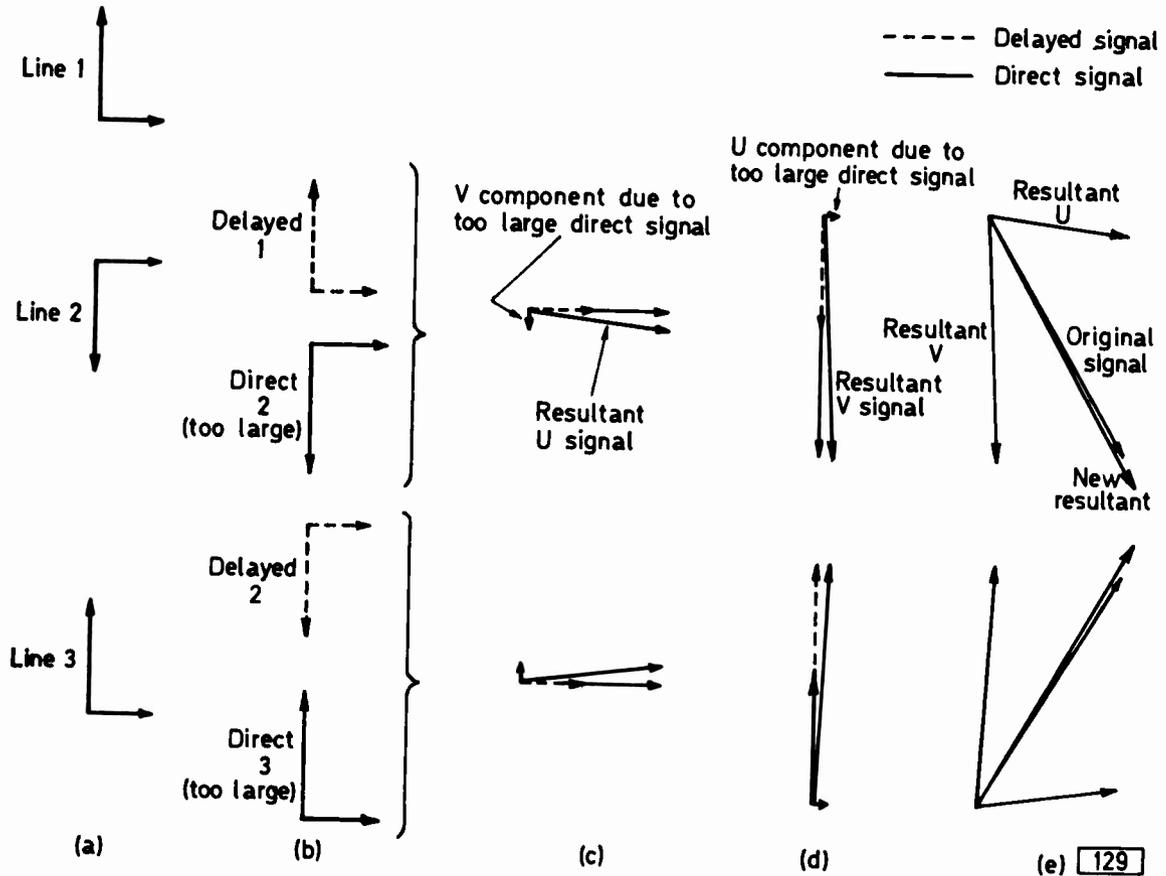


Fig. 9: The errors caused when the direct path signal to the matrix is too large (the direct and delayed signals should be equal). (a) Transmitted signal. (b) Delayed and direct signals applied to the matrix. (c) Adding to give the U output from the matrix. (d) Subtracting to give the V output from the matrix. (e) When the separated U and V signals are recombined the resultant obtained is not identical to the original signal.

to see what has happened to the original signal we get the resultant chrominance subcarrier shown in (e). This by itself however does not show clearly the evil effects which will accrue when it is demodulated even with minor errors of reference carrier phasing. Before going into this aspect of the matter let us see what happens when the delay line timing is wrong.

Incorrect Delay Time

It is difficult to manufacture a delay line to the very tight timing tolerances that are required and in any case differences of circuit impedance matching will cause slight variations of delay time. It is therefore normal practice to connect an adjustable coil across the input end of the line to introduce a reactive element which will produce a phase change of a few degrees in the subcarrier. This is used to cancel out as accurately as possible any small timing error in the line. Misadjustment of this phase correction causes a phase difference between the direct and delayed chrominance signals in the matrix and hence incomplete separation of U and V components.

We can see how this happens in Fig. 10. Diagram (a) shows the chrominance signal for three lines of the picture, as before. In (b) the U and V components are drawn for lines 2 and 3 at the input of the matrix circuit. The delayed signal in each case has a phase error of β . The result of adding these direct and

delayed path signals and hence the output to the U channel is shown at (c) while (d) shows the results of subtracting the two signals to obtain the V channel signal.

You will see immediately that things have gone wrong again, only more so. The signal being fed into the U channel changes in amplitude from line to line, has an unswitched V component and the vector is rotated away from its axis. Anything more conducive to causing blinds and decoding errors in general would be hard to devise, but it is matched by the signal fed to the V channel. This also varies in amplitude from line to line, has a constant U component and is rotated off its axis.

If the signal in either the U or V channel has a different amplitude from line to line it is clear that even with perfect demodulation the output will vary and blinds are the inevitable result. If demodulation phase errors are present as well it is only to be expected that the phase errors in the U or V signal and the spurious signal components will add to the general confusion and produce further spurious components in the output.

Effect of Matrix Errors when Demodulation is Correct

If we take the effects of amplitude errors in the matrix, which were illustrated in the vector diagrams

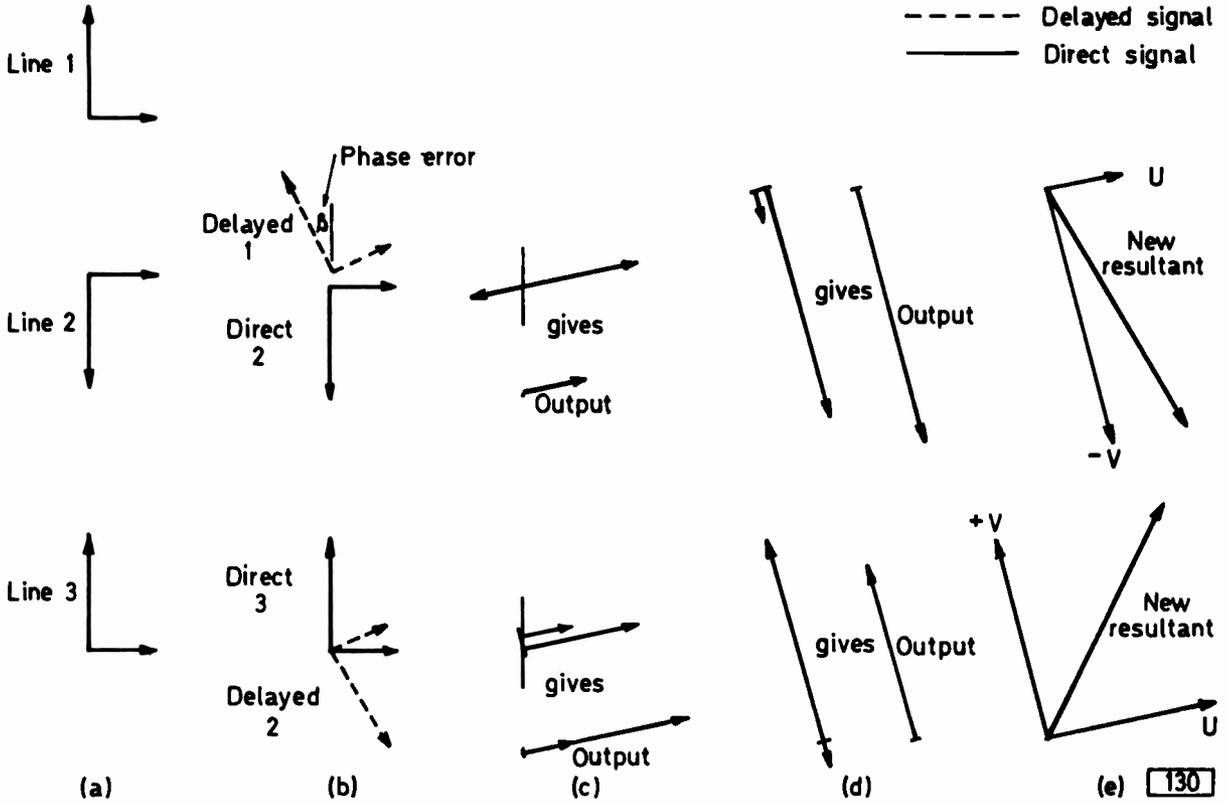


Fig. 10: The errors caused by a phase error in the path of the delayed signal to the matrix. (a) Transmitted signal. (b) Delayed and direct signals fed to the matrix. (c) Adding to give the matrix U output. (d) Subtracting to give the matrix V signal output. (e) The U and V signals vary in amplitude from line to line.

Note that the resultants shown in Figs. 9 (e) and 10 (e) will not be obtained with correct demodulation—only in the special case of demodulation along the axes of each individual U and V component.

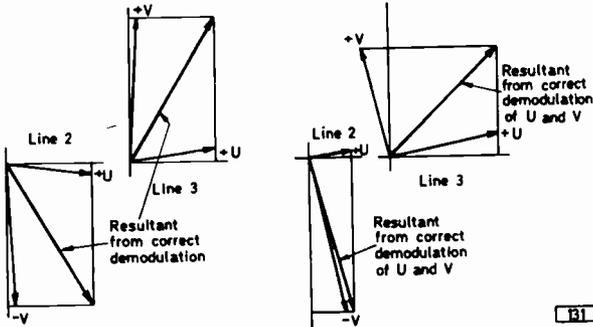


Fig. 11 (left): Correct demodulation of the U and V components shown in Fig. 9 (e) produces a resultant of incorrect amplitude but correct hue. There is no difference from line to line and thus no blinds.

Fig. 12 (right): The gross hue error on alternate lines caused by incorrect phase adjustment of the delay line. This causes hue blinds even with perfect demodulation.

in Fig. 9(c) and (d), and demodulate the U and V outputs correctly we get the state of affairs shown in Fig. 11. In each case the demodulated outputs are too large—because the U and V signals coming from the matrix are too large—but they are in the same proportion and so no hue error is caused. No blinds are present because there is no difference from line to line.

The effect of matrix phase errors is shown in Fig. 12. As we commented earlier the outputs from both the

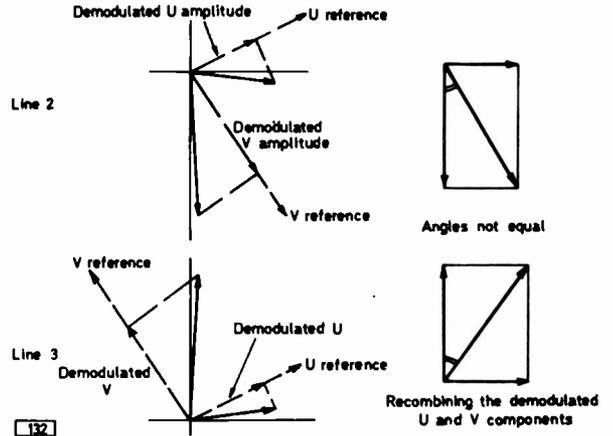


Fig. 13: Incorrect matrix amplitude adjustment and incorrect reference signal phases at the demodulators produce hue errors from line to line and thus blinds.

U and V channels differ from line to line even with perfect demodulation and so blinds are inevitable. But take careful note: the resultant of the U and V components shows a marked hue error from line to line. Thus the amplitude errors of the individual U and V components appear on the picture as "hue blinds" rather than "saturation blinds". You will probably have to look at the line structure of the picture quite closely to see the difference, but the

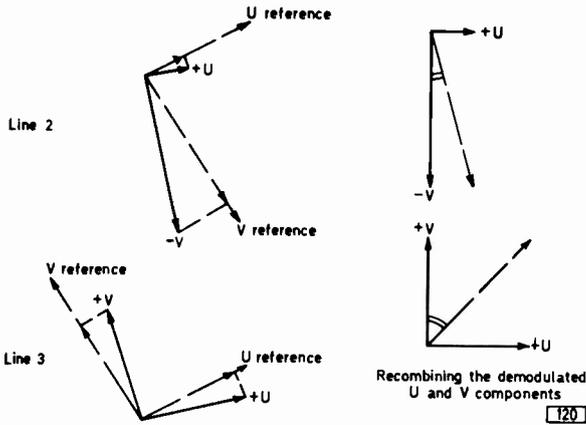


Fig. 14: The combination of a matrix phase error and demodulation phase errors causes gross hue errors and differences in saturation from line to line. The resulting blinds would be totally unacceptable.

diagnosis may come in useful when assessing decoding errors.

Matrix Errors + Faulty Demodulation

We do not wish to test your patience to breaking point with yet more vector diagrams, but it seems a pity not to complete our survey now that we have come so far together. You can always turn to the summary chart (p. 175) but here briefly are the results.

The effect of combined quadrature and static phase errors on the outputs of a matrix with inputs of unequal amplitudes is illustrated in Fig. 13. Unless the phase errors are equal to both demodulators there will be amplitude and hue errors in the resultant of the outputs. So we get blinds on the picture caused by both saturation and hue errors.

The equivalent case arising from a phase error in the matrix is shown in Fig. 14. The results are similar to those of Fig. 13 but the errors are enhanced by the

amplitude errors from line to line which are present in the output from the matrix.

Conclusions this Month

Perhaps now it is timely to apologise for inflicting so many diagrams upon you. Unfortunately it is not practicable to describe PAL decoding problems in any other way and since this is a much neglected subject it seemed well worthwhile doing the job properly. Even so there are still a number of issues that we have not yet covered.

Just to summarise matters, here are the main conclusions from our survey:

- (1) A static phase error in the a.p.c. loop swings both the U and V reference phases equally and causes equal desaturation to both demodulated outputs. It is not particularly harmful.
- (2) A quadrature error causes a change of hue.
- (3) An amplitude error in the matrix causes a saturation error with correct demodulation but hue and saturation blinds with even small swings of the phases of the reference carriers.
- (4) A phase error in the matrix causes hue blinds with correct demodulation and both hue and saturation blinds with incorrect demodulation.

A more general conclusion is that the matrix must always be adjusted with the greatest care. If you have not yet the right equipment or experience it is probably better to leave well alone.

A further point is that any crosstalk between the U and V channels will cause blinds unless demodulation is very accurate and sometimes even if it is. Crosstalk is a design problem and can be caused by: coupling in the earth paths of the U and V channels; chrominance subcarrier in the luminance channel getting into the decoder; phase changes of the U or V signal, or reference carriers, due to base input capacitance of transistor stages; and in a number of other ways.

Now go and look at your nearest colour receiver and see if you can spot any blinds!

INCREASING THE X SENSITIVITY OF THE HEATHKIT OS1 'SCOPE

by K. J. Young

WHEN it is desired to display lissajous figures or to plot curves using the Heathkit OS1 oscilloscope the coarse speed switch (see Fig. 1) is placed in position 1—rendering the X oscillator V4 inoperative—and the appropriate sinusoidal signals are fed to the X- and Y-amplifier inputs. As can be seen the X-amplifier input is taken to V4 anode and an input of about 6V r.m.s. with maximum X-gain setting is necessary. This problem can be overcome by modifying the circuit so that V4 acts as an X amplifier: the modification is shown in Fig. 1 and apart from the external a.f. transformer which is necessary for isolation and to preserve the correct phase relationship of the signals costs about 25p.

Position 1 on the left-hand capacitor switchbank shown in Fig. 1 must be permanently earthed. A socket in which the contact closes when the plug is withdrawn, for example a 3.5mm. phone socket, is connected between position 1 of the right-hand capacitor switchbank and chassis. The X signals are fed via the external transformer to a plug suitable for this socket. With the coarse speed switch in position 1

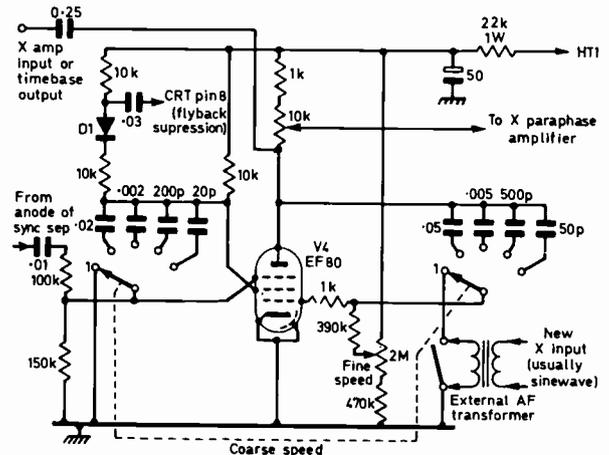


Fig. 1: Circuit details of the modification.

therefore V4 acts as an amplifier instead of being unused. This gives adequate sensitivity for all normal measurements and displays, e.g. curve tracing or bridge displays. The hole for the socket should be carefully drilled above the fine speed control, clear of other components.



SERVICE NOTEBOOK

G. R. WILDING

VHF Tuner Troubles

There was no v.h.f. sound or vision on an Ekco Model TC437, only a brilliant, completely noise-free raster. U.H.F. was not obtainable locally, but on switching to 625 background hiss came from the speaker and grain appeared on the raster, clearly indicating either a v.h.f. tuner fault or defective power switching from one tuner to the other. There was normal h.t. present on the v.h.f. tuner's power input tag but we noticed that there was a cold, slightly discoloured resistor on top of the push-button unit. This had h.t. at one end but not the other. Reference to the service manual showed this resistor to be R13, $12k\Omega$, used to supply h.t. to the PCF801 triode on v.h.f. A resistance test showed that there was no short from the valve end to chassis and on replacing R13 we obtained normal reception, clearing up in minutes what at first sight seemed to be a lengthy job.

Common Faults

This emphasises the point made by the service department of a leading British manufacturer, that up to 90% of the faults found in v.h.f. tuners returned to them for service were of a basically simple nature that could very quickly be put right. Most complaints with v.h.f. tuners are due to defective contacts, strained valveholders or resistor burn-ups and in most instances careful visual inspection will reveal the trouble. Burnt out resistors are usually caused by interelectrode shorts in valves, to transposed r.f. amplifiers and mixers or to a breakdown in decoupling or lead-through capacitors.

Low Gain

Low gain is rather more difficult to pin down and though—apart of course from the valves—usually the result of an open-circuit or dry-jointed decoupler the practice of temporarily soldering a replacement across them seldom gives conclusive results. Quite often you may find that soldering a replacement appears to improve the gain but when you remove the suspect and wire the new one in its place in similar short-lead fashion the increase in gain has disappeared: in such cases the replacement's long leads were probably introducing slight positive feedback and/or mistuning the stage. The best and usually the quickest way in the end—after probing has failed to reveal a dry-

joint—is to adopt the manufacturer's method and replace all suspect decouplers en bloc.

If printed circuit coaxial input sockets are used however check for a crack between the socket and the soldering points to which the aerial isolating capacitors are connected—this was a common fault with Pye/Ekco sets of a few years ago. Also check these capacitors by temporarily shorting them out with a screwdriver blade.

Although not part of the tuner make sure that the preset sensitivity or "delay" control circuitry is operative and applying a.g.c. to the r.f. amplifier only on high signal inputs. With valved tuners it is always safe to momentarily short-circuit the a.g.c. supply tag on the tuner to the earthed frame. On low inputs this action should produce negligible or zero gain increase but at high inputs it should produce a marked increase.

Also make sure that the right type valves are fitted—sometimes you may find a high-gain 30L15 in place of the earlier PCC84, used either mistakenly or in a misguided effort to increase the front-end sensitivity—and ensure that the coaxial output lead from the tuner to the i.f. strip is well connected at both ends.

If you find that touching the outer metal braid of the coaxial downlead or the shell of the coaxial plug increases contrast—these points are not directly earthed to the signal—there is either a soldering disconnection or the braid isolating capacitor is open-circuit. When contrast drastically falls following a local thunderstorm first take a look at these capacitors: on several occasions I have found one or other split open due to heavy instantaneous aerial voltages.

Cramped Raster Base

A raster that becomes cramped at the base a short while after switch-on is almost always caused by a defective field output pentode and/or reduced value cathode resistor. If the cramping remains fairly constant the odds are that the high-value electrolytic shunting the cathode resistor has lost most of its capacitance. On occasion however other faults can cause this base contraction and two quite different examples came our way recently.

The first was in an old convertible Pye model and after replacing the PCL85 and checking that the two series-connected cathode resistors totalled the correct 446Ω or very close to it we found that cathode voltage rose from its correct value of 18.5V at switch-on to almost 24V after about a quarter of an hour. The only likely cause for the underlying increase in cathode current was a leak to the pentode grid from the triode anode via the $0.01\mu\text{F}$ coupling capacitor and on replacing this component the cathode voltage stayed correct and the raster cramping ceased. Although these grid feed capacitors often come under suspicion in practice they seldom fail and we can recall only two or three other instances where they have been at fault.

The other example was a set fitted with the Thorn 950 chassis. This time the raster size and linearity were normal at switch-on but after about 20 minutes use the base contracted and there was also a slight reduction from the top. After checking the usual probabilities and as the resistors in the circuit had no discolouration (usually a reliable sign that they have not changed value) we disconnected the height-stabilising v.d.r. in the anode circuit of the PCL85

SERVICE ACTION: DISTORTED SOUND

(1) V.H.F./U.H.F. implying an a.f. fault.

Grating tone, probably worse at low volume levels: This is caused by the speaker coil rubbing against the magnet. Check speaker centring by light pressure on cone when distortion will increase or decrease as coil placement in gap is varied. The only real cure is replacement. With any speaker it should be possible to freely move the cone in and out without any suggestion of rubbing.

Nasal tone: This suggests an overbiased valve, particularly if it gets progressively worse as set temperature increases. Replace triode-pentode a.f. valve—usually a PCL82, PCL83 or PCL86—which will almost certainly be excessively hot due to grid current. Also check cathode-bias resistor for value reduction (common) or short-circuit bypass electrolytic (rarer).

A reduced-value pentode-cathode resistor will by underbiasing the valve cause excessive anode/screen current to further reduce the resistor's value in a cumulative manner and result in premature valve failure. Carbon type resistors tend to reduce in value on sustained overload currents.

If contacting the pentode control grid with a meter on its high-voltage range markedly reduces distortion check the feed capacitor from triode anode for leak. Surest method is to remove valve, short valveholder heater sockets and test for possible slight positive voltage at control grid socket. Occasionally leakage may only be apparent when set is warm. Replace capacitor if there is the slightest suspicion of its insulation not being perfect.

Also check that grid resistor is not high-resistance. *Excessively nasal, constant distortion:* This is caused by an open-circuit cathode resistor, resulting in the shunting electrolytic breaking down and providing a comparatively high-resistance connection to chassis and thus grossly overbiasing the valve.

Thin reedy tone: Short-circuit turns on primary of sound output transformer (rare).

Strident, high pitched tone: Open-circuit tone control or negative feedback component.

Shrill reproduction, tending towards instability: Open-circuit decoupler or r.f. bypass capacitor. Unearthed output transformer core or secondary winding. Unearthed screened leads.

High hum level: Poor heater-cathode insulation in a valve. Open-circuit or reduced-value h.t. electrolytic smoothing capacitor. Replacement h.t. feed resistor not of sufficient value.

Hum level varies with field hold setting: Pickup from field timebase circuit to (usually) triode grid circuit. Impaired h.t. rail smoothing. Unearthed screened leads of volume control casing. Misplaced triode grid wiring or use of excessively large grid capacitor. An earthed metal-cased type will invariably cure this trouble.

(2) V.H.F. only.

Changed value resistors reverse-biasing the noise limiter diode.


(3) U.H.F. only.

Defective diodes, maladjusted a.m. balance control or drift in 6MHz i.f. transformer. These transformers can safely be readjusted on signal since input is constantly on frequency.

Incorrect working voltages with EH90 type of discriminator.

Note on EH90 circuits

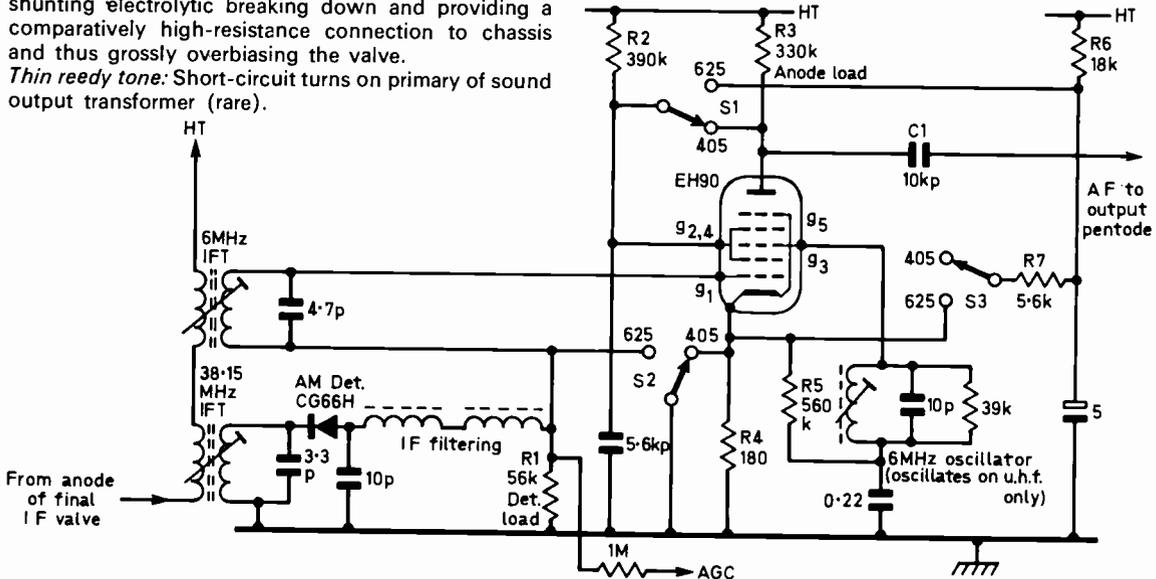These valves operate as heptode discriminators on u.h.f., the anode current being determined by the "locked-in" phase difference between the applied signal and the locally-generated 6MHz oscillation. See typical circuit below.



Typical EH90 circuit (Pye-Ekco). On v.h.f. the EH90 acts as a triode a.f. amplifier to the input signal across R1. On u.h.f. the EH90 acts as a high-output f.m. discriminator, S2 shorting the a.m. input and introducing cathode bias while S1 changes the valve to heptode operation and S3 powers the 6MHz oscillator via R5. Due to space-charge coupling within the valve the 6MHz tuned circuit begins to oscillate and this constant-phase signal plus the f.m. input control the anode current, i.e. the signal developed across R3 is determined by the phase difference between the a.f. signal impressed on the 6MHz carrier and the local 6MHz signal.

triode. The height immediately became excessive, as was to be expected, but on reducing it with the height control to just fill the screen we found that there was no subsequent variation. The field hold was not up to standard but as we didn't have the exact replacement to hand we fitted a $2M\Omega$ resistor in place of the v.d.r. This seemed to restore normal locking and was left till the replacement arrived.

Very Dark Picture

A very dark picture on a receiver fitted with the STC-ITT VC51 chassis proved to be due to a brightness circuit fault: fully advancing the brilliance control on no-signal failed to produce the customary blank raster.

Unless you are sure that the video pentode is a.c. coupled to the tube the first move must be to replace this valve, for if it is d.c. coupled a significant reduction in its anode current due to excessive bias, reduced screen voltage or any other reason will increase its anode voltage and thereby that of the c.r.t. cathode to overbias the c.r.t. As the PCL84 video pentode is a.c. coupled in this chassis however, we immediately checked the c.r.t. voltages, for with this fault the cathode voltage must be too high or grid voltage too low. The former was 140V, a normal figure, but even with the brilliance control fully advanced the grid voltage indicated on our meter remained under 75V whereas it should reach about 130V. As the d.c. supply to the c.r.t. grid is via a $68k\Omega$ resistor in series with another of $18k\Omega$ from the slider of the brilliance control however, individual meter readings could vary considerably.

On next checking the voltage at the h.t. tag on the brilliance control we found little more than 75V though as this $500k\Omega$ potentiometer is returned to chassis via a $47k\Omega$ resistor and one pole of the on/off switch and is fed from the 230V h.t. rail via a $330k\Omega$ resistor simple proportion indicated that there should be something in the region of 130/140V present depending on component tolerances. As anticipated, the $330k\Omega$ resistor turned out to be markedly high-resistance and after replacing it full brilliance could be obtained with the control well back from maximum.

SIMPLE OUTDOOR UHF AERIAL

—continued from page 171

shown in Fig. 1 to take the cross bar. In order to secure the cross bar rigidly hole C is drilled with the bar in place and then counter bored in the wood on one side only to enable the nut to bear directly on the aluminium. Cut out sections $\frac{1}{2}$ by $\frac{1}{4}$ in. are shown dotted at the back of the block: these were made to enable the two cover screws to be $1\frac{1}{2}$ in. types—if longer screws are used these cut outs will not be needed.

The dipole elements are slid into $\frac{1}{4}$ in. holes—also reamed—as shown. This hole will run into the cross-bar hole but this is unimportant provided neither of the dipole halves touches the boom. When the dipole halves are in place holes are drilled for the cable bolts. These holes are drilled from the front, through the tubing. The back of the block can be counter bored for the screw head, to give just enough thread to take two nuts, two washers and the cable. The front is also counter bored so that the inner nut locks the tube firmly in place in its hole. Surplus wood between the bolts is cleared to enable the bared cable to lie flush when the cover block A is attached.

The prototype model shown in the accompanying photograph used a round-section dipole block.

Finish

All nuts and bolts should be rust proofed and blocks A and B should each be given a coat of varnish or emulsion paint before assembly. After mounting the reflector on the cross bar the dipole block B is attached to it. The cable is threaded through block A and attached to its bolts. A liberal coat of Bostik White Seal is applied over the inner face of the two blocks and the cover then screwed on.

Remove the surplus White Seal. White Seal should also be put around the cable entry and over all exposed nuts and bolts to reduce further the risk of corrosion. ■

LONG-DISTANCE TELEVISION

—continued from page 165

me I am sometimes unable to reply. Such readers should ensure, therefore, that their address is on the letter itself! Two recent letters have been from a reader in the Lebanon requesting advice and from Leslie Hetesi of Hungary who apparently has been very active, with reception from most countries in Europe including BBC-1 and Jordan ch.E3 via Sp.E.

Sunspot Predictions

Predictions, courtesy of the Swiss Solar Observatory: November 50, December 48, January 47, February 45, March 43, April 42.

DX-TV Pamphlet

The DX-TV pamphlet proved extremely popular, so much so that we quickly disposed of two printings. In view of the growing interest in this hobby I decided to rewrite the information in a somewhat larger and more detailed form with information on World-Wide television transmissions. This project is coming along well and I expect to be able to announce its completion shortly. In the meantime I must apologise to all those who wrote in for the original pamphlet and were disappointed.



It gives better reception than mistletoe!

COLOUR RECEIVER CIRCUITS

CHROMINANCE SIGNAL DEMODULATION

GORDON J. KING

THE previous instalment took us up to the output of the PAL decoder and matrix circuit (adder/subtractor system). We discovered that as a result of the electronic averaging of the direct and delayed lines of chroma signal, and the fact that the V chroma signal is alternated in phase line by line, phase insensitive U chroma signal is obtained from the adder part of the matrix and V chroma signal from the subtractor part. The next requirement therefore is to demodulate these separate chroma signals in order to produce the original R-Y and B-Y colour-difference signals.

We must bear in mind of course that although effectively of video frequency, i.e. within the video spectrum, the signals emanating from the PAL matrix are sidebands of the original colour-difference signals based on the subcarrier frequency of 4.43MHz. The original modulation was of amplitude so it follows that a simple amplitude detector would yield the original R-Y and B-Y information. Things however are not quite as easy as this because before demodulation can be accomplished the missing subcarrier must be reinserted. The 4.43MHz signal provided by the receiver for this purpose is commonly called the *reference signal* and the source the *reference generator*. Fig. 1 shows in block schematic form the general arrangement.

Each PAL matrix output requires its own detector. Thus we find one detector accepting the V chroma signal and delivering the demodulated R-Y signal and the other accepting the U chroma signal and delivering the demodulated B-Y signal. It will also be recalled that PAL weighting factors were applied to the R-Y and B-Y signals at the V and U modulators at the transmitter. This means that the detectors or associated circuits must introduce deweighting so that the true values of the R-Y and B-Y signals are ultimately obtained. The detectors are variously referred to as the V and U detectors, the chroma detectors, the R-Y and B-Y detectors or the red and blue detectors. I prefer calling them simply the V and U detec-

tors after the names of the chroma signals applied to them.

One part of each detector receives the appropriate chroma signal and another part the reference signal. For accurate demodulation it is absolutely essential for the reference signal to match accurately the frequency and phase of the bursts transmitted on the back porches of the line sync pulses are derived from the transmitter's subcarrier generator. They are used at the receiver either to produce the reference signal or to synchronise the frequency and phase of the reference signal produced by the reference generator.

Because the V and U chroma signal subcarriers at the transmitter are in phase quadrature—as required for quadrature modulation—the equivalent reference signals applied to the V and U detectors in the receiver must also be in phase quadrature: that is a phase difference must exist between them of 90 degrees. As at the transmitter, a single source usually provides both reference signals and the quadrature shift is provided by a phase-shift network in one of the reference signal feeds to the detectors.

Demodulation of the U chroma signal is reasonably straightforward because the signal is "phase-constant" line by line. Because the phase of the V chroma signal changes line by line however the V detector must in some way be switched in synchronism with these alternations so that the R-Y output is also "phase-constant". This can be achieved by alternating the phase of either the reference signal or the chroma signal applied to the V detector line by line. Both schemes are found in practice.

The actual switching of the selected signal is not all that difficult but mild complications arise since the alternations must be synchronised with those at the transmitter. Clearly if the V detector is switched to operate in the +V phase when the actual signal phase is -V then the colour display is going to be seriously in error. The required synchronising information is provided by the swings of the bursts which it will be recalled are phased at 135 degrees (relative to the +U axis) when the V phase is positive and at 225 degrees when the V phase is negative. Thus the bursts swing ± 45 degrees (90 degrees overall) relative to the -U chroma axis. The method of swinging equally either side of the -U chroma axis means that the *average* phase is in fact along the -U axis which is another requirement.

At the receiver the swinging bursts are effectively "detected" and give rise to a quasi-squarewave output of half-line frequency. After processing this signal is used to synchronise the V detector switching. The frequency is approximately 7.8kHz and the term *ripple* or *ident* signal is commonly used to describe it. In many receivers it is—as earlier instalments have shown—the ident signal which operates the colour killer and also sometimes the chroma trap in the

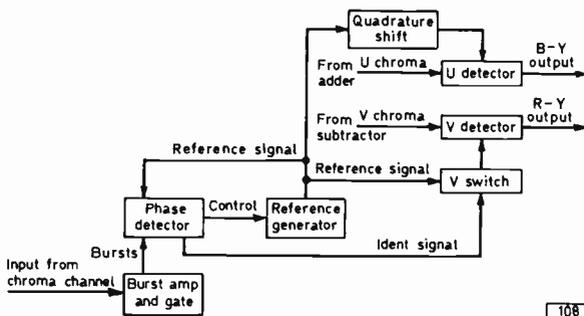


Fig. 1: Block diagram of the chrominance detectors and the reference signal arrangements required for synchronous demodulation.

luminance channel.

The block diagram (Fig. 1) summaries all this and the only sections not mentioned so far in this article are the burst amplifier/gate and the phase detector. The first picks up signal from the chroma channel via a 4.43MHz tuned circuit, the gate being arranged to open only during the periods of the bursts (the back porches of the line sync pulses). Thus the gate is switched by suitably processed line flyback or sync pulses. The gate blocks the chroma signal proper and the bursts that it passes are amplified and fed to the phase detector which also receives sample reference signal. It is the job of the phase detector to compare the reference signal with the bursts and when the parameters of frequency and phase fail to coincide to produce a control potential to correct the reference signal so that it matches the bursts in these respects.

The bursts from the amplifier/gate are also commonly rectified and used as a potential to automatically increase or decrease the gain of the chroma channel should the amplitude of the chroma signal decrease or increase for any reason. This of course is the automatic chroma control (a.c.c.) function which is desirable for maintaining the saturation level constant under various conditions of operation.

The various sections of Fig. 1 comprise a whole system and although from now on we shall be investigating each section separately in terms of the types of circuits used we should nevertheless keep the overall system in mind. Last month we concluded with the PAL decoder/matrix circuit so it is appropriate this month to go on to the V and U detector circuits.

The vast majority of colour receivers of recent design use four semiconductor diodes in each detector circuit (called a diode bridge circuit) but it is possible to employ two diodes or in fact a thermionic valve or transistor while in the latest sets integrated circuits are being increasingly used. For the time being however let us get to grips with the diode bridge circuit.

The basic diode bridge circuit shown in Fig. 2 is found in most PAL-D receivers. Two are used, one for the V chroma signal and the other for the U chroma signal. To make the V detector suitable for the alternating $\pm V$ chroma signal the phase of the reference signal fed in via T1 is generally alternated line by line by means of switching diodes (not shown) in the reference signal coupling circuit. For the moment though we will assume that the input is the U chroma signal or if you like the V chroma signal minus its phase alternations.

It is simplest to think of chroma detectors of this kind as being switched on by the reference signal during part of one half-cycle of each complete reference signal cycle. The reference signal is applied across points A and B on the diode bridge and since

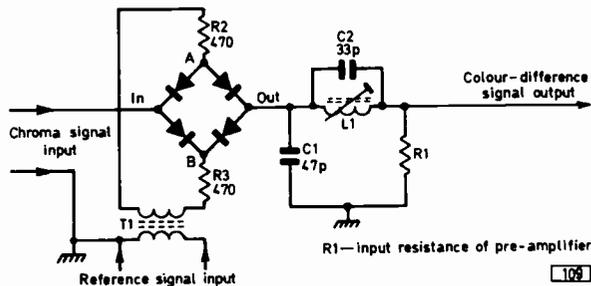


Fig. 2: The diode bridge synchronous detector circuit shown here is widely used in colour receivers.

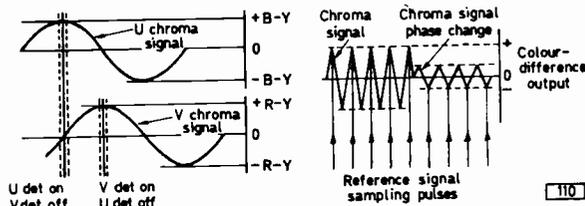


Fig. 3 (left): The signal sampling periods of the two chroma signal synchronous demodulators. The amplitude and polarity of the colour-difference signal output from the detectors is determined by the amplitude and phase of the chroma signal at the instant of sampling.

Fig. 4 (right): How the colour-difference signal output changes with the amplitude and phase of the chroma signal.

it is a sinewave it follows that on the half-cycle which makes point A positive with respect to point B all four diodes switch on thereby providing signal continuity between the points on the bridge marked in and out. At the same time of course the chroma signal is present at point in so the effective chroma signal voltage appears at point out where it passes through filter L1/C2 to the appropriate colour-difference pre-amplifier. On the subsequent half-cycle of reference signal point A swings negative with respect to B and the four diodes switch off thus disconnecting the path from in to out.

As this action continues the charge which develops on C1 results in the diodes switching on only during the peaks of the appropriate half-cycle of reference signal. This is because the time-constant of C1, R1 (the latter component being the detector load) is adjusted to suit the frequency of the reference signal. The time-constant of C1 and R1 is in fact in the order of 0.23 μ s. In some circuits R1 consists of the input resistance of the appropriate colour-difference pre-amplifier. L1 and C2 form a filter which removes the unwanted chroma components, leaving only the colour-difference signal for application to the pre-amplifier. Resistors R2 and R3 in series with the reference signal source serve as "hold offs" to avoid reference generator damping and high peak currents in the diodes due to the reference signal.

Chroma Detector Action

The action of a chroma detector can be described in various ways but the two main points to keep in mind are (1) that the amplitude of the chroma signal determines the magnitude of the colour-difference signal and (2) that the instantaneous phase of the chroma signal determines the polarity of the colour-difference signal. This is of course merely the reciprocal of the modulation operation.

The detector is designed so that the chroma signal is sampled for a short period of time during each reference signal cycle. Indeed the reference signal can as we have seen be regarded as a switching signal for the detector. The switching of the two chroma detectors in phase quadrature (remember that there is a 90° phase difference between the reference signals fed to the two detectors) is illustrated diagrammatically in Fig. 3. It will be seen that when the U detector is switched on by the reference signal to sample the amplitude and phase of the U chroma signal the V chroma signal should be passing through zero. Conversely when the V detector is switched on by its reference signal the U chroma signal should be at zero.

There can never be a really instantaneous sample because the diodes are bound to remain conductive for a finite part of the positive half-cycle of the reference signal. The sampling period ("dwell angle") differs between circuits but is not usually a significant portion of the switching half-cycle.

In Fig. 3 the U and V chroma signals are shown being sampled when their phases are positive-going. Thus the outputs will be $+B-Y$ and $+R-Y$ respectively. Owing to the nature of the colouring information the U chroma signal phase at the instant of sampling could be negative, in which case the appropriate detector output would be $-B-Y$ of magnitude governed by the amplitude of the modulation. The same of course applies to the V chroma signal.

Figure 4 attempts to illustrate the action when a chroma signal alters from one phase and amplitude to another. The amplitude change is obvious. To emphasise the phase change the chroma sinewaves are shown as expanded triangular waves. It will be seen that when the positive peaks of the larger amplitude sinewaves to the left are sampled a colour-difference output of positive polarity is obtained while after the signal phase change the lower amplitude negative peaks to the right appear at the sampling times and give a colour-difference output of negative polarity and smaller magnitude. For accurate operation it is essential for the reference signal to remain constant in frequency and phase.

That is all there is to it really! Some texts illustrate the effect differently and different writers have their own pet ways of explaining the action. Many people have difficulty in understanding why the chroma signal consists of 4.43MHz sinewaves since the sub-carrier is suppressed at the transmitter. The sinewaves of course represent the components of the sidebands and it is the modulation information which results in the amplitude and phase changes. The former controls the saturation and the latter the hue.

From all this it can be seen that the exact timing of the reference signal is of the utmost importance: timing in this context means phasing, and in a PAL-D receiver incorrect phasing can affect both the saturation and hue of a display. It can also result in crosstalk between the V and U signals at the detector outputs and encourage Hanover bar interference.

Before leaving the general theory of detector operation it should be understood that the amplitude and phase of a chroma signal can change more often and over more intermediate values than implied in Fig. 4. In this diagram the phase and amplitude of the chroma signal are shown remaining constant for a number of sampling reference signal cycles then changing to another stable value. This is what would happen for example during a transmission of the colour bars: in fact the change in amplitude and phase in Fig. 4 is representative of what happens from one colour bar to the next with the U chroma signal.

Complete Decoding System

To conclude this month Fig. 5 shows the complete system including the PAL delay line and matrix which were fully examined last month. Excluding this therefore we have the V detector D1 and the U detector D2, both diode bridge arrangements, which receive the appropriate signals from the PAL matrix. Each detector also receives a reference signal from the crystal-controlled reference generator.

The reference signal to the U detector passes first

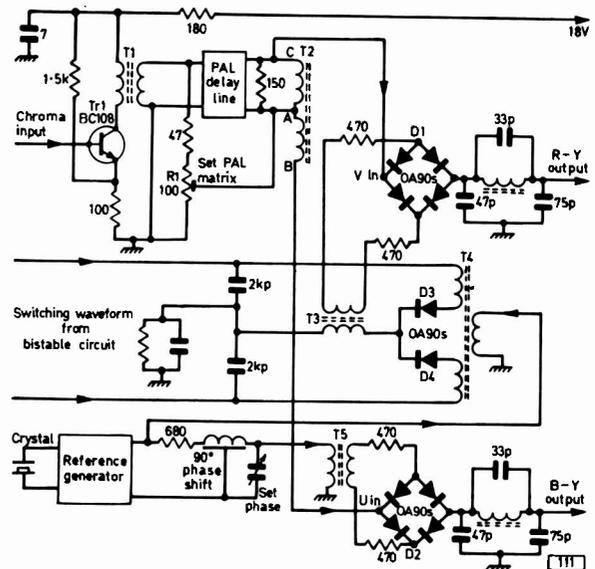


Fig. 5: The complete decoding system: PAL delay line, adder and subtractor (T2), synchronous detectors (D1 and D2), reference signal generator, PAL V switch (T4 with D3 and D4) and 90° phase shift network.


through the 90-degree phase shifter (to provide the correct timing for quadrature demodulation) and thence to the coupling transformer T5.

PAL V Switch

The reference signal to the V detector passes through a more complicated circuit which includes the switch for alternating the phase of the reference signal line by line to counter the PAL $\pm V$ chroma signal alternations. The reference signal goes first to T4 and thence via T3 to the detector D1. There are two secondary windings on T4 and to get from either one of these to T3 primary the signal has to pass through diode D3 or D4.

These diodes constitute the V switch and are themselves switched on and off alternately line by line by the squarewave outputs from a bistable circuit (not shown) which will be investigated in a subsequent instalment. The two secondary windings on T4 provide outputs in opposite phase, thus providing the actual phase inversion of the reference signal. In action D3 is on when D4 is off and vice versa. Thus when D3 is on the reference signal passes to T3 primary from the top secondary of T4 and when D3 switches off and D4 switches on the reference signal arrives at T3 primary in opposite phase from the bottom secondary of T4 via D4. Clearly then the phase of the reference signal applied to the V detector D1 swings over 180 degrees each time the diode switch D3/D4 is operated; and since the switch operates line by line, line by line phase alternations occur.

This is where we must leave off this month. The general plan of the scheme should now be clear and in this respect it would be a good idea to keep Fig. 1 handy or better still in mind! We should by now be fairly clear how the chroma detectors work—how they sample the amplitude and phase of the chroma modulation and yield colour-difference signal outputs of varying magnitude and polarity. With these very important factors resolved we can progress next month towards the various other circuits.

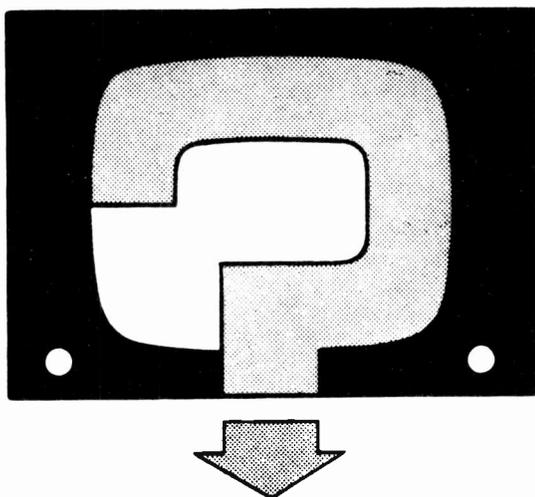

YOUR PROBLEMS SOLVED

★ Requests for advice in dealing with servicing problems must be accompanied by a 10p postal order (made out to IPC Magazines Ltd.), the query coupon from page 187 and a stamped, addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets or answer queries over the telephone.

FERGUSON 3800

This 20in. receiver is fitted with the BRC 1500 chassis. The height control is right at one end of its track. The PCL805 field timebase valve has been replaced and the voltages in the stage checked but they all seem to be OK. There is still a 1½in. band at the bottom of the picture.—F. George (Bradford).

If the picture is compressed at the bottom check the field output stage bias decoupler C79. The value of this is 160µF but a 250µF 25V one will do. If the overall height is lacking check R123 (330kΩ) and C89 (1µF) which decouple the boost feed to the oscillator section and R93 (330kΩ) in series with the height control.

EKCO T422

There is no raster and the PL36 glows cherry red. The picture went suddenly without any previous deterioration. The PL36 and PY800 have been tested and found to be OK.—P. Redmond (Norfolk).

It seems that the line oscillator valve V14, PCL84, is faulty. Check this and the coupling capacitors C90 47pF (150pF in some chassis) and C87 0.01µF.

GEC BT302

When the valves have warmed up there is a vertical band of light about 1in. wide accompanied by a very faint picture which fills the left-hand side of the screen. After a few moments the line whistle alters and the narrow strip expands to fill the whole screen area, growing very dim and then disappearing. If the PY81 top cap is removed the original fault condition reappears. All the line timebase valves have been replaced. The PL81 screen voltage appears to be rather high and the boost voltage low.—B. Gray (Basildon).

The defective component is the boost reservoir capacitor. This is C152, 0.1µF, on the left side just above the line output section. Use a replacement rated at 1kV.

PYE 169 CHASSIS

When a dark scene is being received there is vertical, alternately dark and light shading in the form of 2in. wide bars. The same effect is present on all programmes and aerial adjustment has made no improve-

ment. The bars go right across the screen but the one nearest the left is slightly stronger than the others.—R. Knight (Harrogate).

The problem seems to be trouble with the flyback suppression circuit and we suggest you check C82 1kpF, C35 22kpF and R92 120kΩ.

KB KV005

After about 20 minutes the sound becomes very distorted and stays this way until the set is switched off and allowed to cool.—T. Blake (London W3).

Replace the PCL86 audio output valve and check that its bias resistor R123 120Ω (pin 7) is the correct value. If necessary check the value of the 10MΩ resistor R115 which loads the noise limiter diode.

FERGUSON 3660

After switching on, the sound on one of these models (BRC 1400 chassis) periodically reduces, sometimes to nothing. The operation of a switch on another electrical appliance, e.g. fire, fridge or a light, will sometimes produce this fault and at other times bring the sound back to normal for a while. The fault is less troublesome when the set has been in operation for an hour or two and only affects v.h.f.—R. Didcomb (Leicester).

This is not an easy type of fault to pinpoint. However it is almost certainly due to a faulty capacitor and is likely to be one across one of the 405 sound i.f. coils. The suspects are C56 75pF, C65 22pF and C71 22pF.

PYE 11U

When first switched on the picture is normal. After five minutes or so however the picture becomes over contrasted and negative with loss of sync. The set is operating on u.h.f. If the preset contrast control is turned down the fault is cured for a minute or two but then recurs. This process can be repeated until you end up with a picture with little or no contrast in order to get a stable picture.—P. Dewhurst (Denbigh).

Replace the video/sync/a.g.c. valve PCL84 (V9) and then check the resistors in the video circuit—R26 5.6kΩ the screen feed, R30 150Ω the cathode bias and R27 330Ω the grid stopper.

UHF. COLOUR AND TELEVISION SPARES

COLOUR DLI DELAY UNIT £3-85 p.p. 25p. **LUMINANCE DELAY UNIT** £1-35 p.p. 15p. **PLESSEY SCAN COILS** £5-75 p.p. 35p. **CONVERGENCE COILS** £3-80 p.p. 25p. **BLUE LATERAL** £1-25 p.p. 9p. or Complete Set £10 p.p. 50p. **MULLARD TYPE, SCAN COILS** £3-50 p.p. 35p. **CONVERGENCE COILS** £1-75 p.p. 25p. **LUMINANCE/CHROMINANCE PANEL** £1 p.p. 25p. **INTEGRATED TRANSISTORISED DECODER UNIT** including Circuits £1-25 p.p. 10p. **LINE OUTPUT TRANSFORMER** including EHT and FOCUS ASSEMBLY £3-50 p.p. 35p. (Shop customers only, assortment Colour Panels of various makes.) ALSO COLOUR TV CAMERA UNITS.

COLOUR TV MONITOR PANELS Designed to highest BBC standards. PAL filter & delay £8-00. Chrominance £6-00. Luminance £4-50. Encoded Video Input £2-50 incl. circuit. p.p. 30p. **UHF 625 conversion kits and tuners** available at reduced prices. Lists available.

UHF tuners transistd. incl. S/M drive, indicator £3-95, or push-button £5-25. **UHF/VHF transistd basic tuner**, latest type, incl. circuit £3-95. **Cyldon valve type**, £1-75 p.p. 25p.

MURPHY 600/700 series UHF conversion kits in cabinet plinth assembly can be used as separate UHF receiver £7-50 p.p. 50p. **625 IF amplifier** incl. 5 valves and circuit £3 p.p. 35p.

SOBELL/GEC Dual 405/625 IF amp and o/p chassis incl. circuit £1-50 p.p. 30p. **PHILIPS 625 P/C IF panel** incl. circuit £1 p.p. 25p. **EKCO/FERRANTI UHF tuner kit**, incl. valves, slow motion drive, knobs, leads, aerial panel £5-50 p.p. 30p.

TV SIGNAL BOOSTER UNITS Latest **PYE/LABGEAR** all station UHF/VHF transistd. "Set back" mains operated £5-90 **UHF Masthead** £4-25. **Power Unit** £3-25 pp., 25p.

FIREBALL TUNERS Perg., HMV, Marconi, New £1-90 p.p. 25p. **PUSH BUTTON** Plessy, Ekco, Ferranti £1 p.p. 25p.

TURRET TUNERS. KB "Featherlight" VC11, Philips 170 series, GEC2010 £2-50, AB Dual Standard, Suitable Ferguson, Baird, KB etc. 75p. **Cyldon C 75p**, **Pye 110/510 Pam**, **Invicta**, **Miniature**, **incremental** £2-50. **Peto Scott 960**, **Cossor 1964**, **Decca 95/606** £2-00 pp 25p.

LINE OUTPUT TRANSFORMERS. Popular types available, brand new replacements, fully guar. A selection which can be supplied p.p. 25p. C.O.D. 25p.

MURPHY 470 to 530 (oilfilled) .. £3-75
MURPHY 849 to 939 .. £4-50
PHILIPS 1768/2168 .. £4-50

PHILIPS 17TG100 Range .. £3-90
STELLA 1011/1029 .. £3-90
PHILIPS IGTG111/12 .. £4-00
PHILIPS 19TG121 to 156 .. £4-50

PHILIPS 19TG170, 210 series .. £4-50
BUSH TV53 to 69 £1-75 105 to 135 £4-50
EKCO 221 to 331 (U25 or U26) £3-75

FERRANTI 1001/19 (U25 or U26) £3-75
EKCO 342 to 394, FERRANTI 1021 to 1065 .. £3-90

EKCO, FERRANTI 418, 1093 etc. .. £3-90
DECCA DM17, 3, 4 (70); DR95, 101/606 .. £3-95

FERG 305 to 436, 606 to 727 .. £3-90
FERG, HMV, MARCONI, ULTRA, PHILCO 3600, 2600, 4600, 6600, 1100, Jellypot .. £3-75

KB RV20, SV20, VC1 to VC11 .. £4-00
MARCONI VT157 to 172 .. £3-90
GEC 302 to 346, £2-50, 448 to 452 .. £3-25

GEC 454/6, 2000 series .. £4-50
HMV 1865/9, 1870/6, 1910/1924 .. £3-90

PYE CTM/CW series (printed circuit) 17/21, 17/8, 110 to 510, 700, 830, 1, 2, 3, 11U to 48 .. £3-90

PAM, INVICTA equiv. LOPTS to above PYE .. £3-90
PETO SCOTT 1419 to 1725 £1-75, 733 to 738, 235 .. £2-50

SOBELL/McMICHAEL TPS 173, 180, T23, 24, 178, 278, SC24, 270, MP17, 18, M72, M74, M247 .. £2-50

TPS 781, 279, SC34, 370, MP27, M75, 76, 93, T25, 280, TP8710 .. £3-25
195, 282 to 288, 762, 763 .. £3-25

SOBELL 196/7, 1000 series .. £4-50
PHILCO 1010 to 1021 .. £2-25
ULTRA 1770 to 2834 .. £3-90

PRACTICAL TV 625 RECEIVER
Integrated push button transistorised tuner .. £4-50 p.p. 25p
Transistorised IF panel .. £4-75 p.p. 25p

850 line output transformer .. £3-75 p.p. 25p
850 field output transformer .. £1-62 p.p. 15p
850 scan coils .. £3-90 p.p. 25p

(p.p. on complete set of 5 items 50p)

THORN 850 Time Base Panel, Dual Standard £1 p.p. 30p

THORN 850 Mains Droppers 25p, pp 10p (state approx. values)

VALVE BASES B9D for PL500 series and colour 12½p p.p. 5p

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6

(Near W. Hampstead tube stn; 28, 59, 159 Bus Routes) 01-794 8751

MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11

GEC 2048

On viewing the screen from the front the left-hand side of the picture is lighter than the right-hand side. The components associated with the tube grid circuit—C241, C233, C234, R245, R248, R244 and R249 have all been replaced without success. By altering component values the condition can be made worse but not better, i.e. the left-hand side of the picture can be made lighter still.—A. Chater (Chippenham).

The trouble is most likely to be due to faulty tube first anode or grid circuitry and as you have checked the latter we suggest you check the decoupling of the first anode supply—R243 680kΩ, C231 22kF and R311 22kΩ. If this does not solve the problem check the earthing of the tube coating. Then try removing the video signal, leaving a blank raster, to see whether the fault persists. If it is not now present check the smoothing of the l.t. supply to the transistor stages (derived from the line output transformer) as if the decoupling here is faulty the signal will be modulated at line frequency.

PYE 59

The sound is OK but the picture is dark when the brightness is set half way and also narrow with a 2in. margin at both sides. When the brightness control is turned up the picture widens to fill the screen but then disappears leaving a blank, dark screen. On turning the brightness down again the picture comes back as before. The height is OK. The line timebase valves and output transformer have been replaced without improving matters.—T. Hope (Daventry).

We suspect low h.t. and also suggest you check the main reservoir capacitor C66. Alternatively the drive to the line output valve may be incorrect. Also check the boost reservoir capacitor which is C118 (0.047μF).

BUSH TV103

On increasing the brightness or contrast control settings the picture goes negative. All valves have been checked and found to be up to standard. The picture tube voltages have been checked and the first and focus electrode readings seem a little low.—A. Creveny (Hull).

You will probably find that the focus control has changed value: change it or put a 1MΩ resistor in series with it. This will brighten the picture to some extent but the tube is no doubt wearing and in need of replacement.

LONG-DISTANCE ITV

We have installed here at Portslade, Sussex, a channel 9 aerial in order to try to receive London ITV, using a GEC model 2019. We get a fair picture but the fine tuner has to be adjusted so much in order to receive the sound that the picture is nearly lost. Is there any way of tuning in the sound better without losing picture quality? The local-distance link is set at distant.—L. Jarvis (Portslade).

Assuming that the aerial is an efficient one capable of long-distance reception we can only recommend a mast-head amplifier to boost the signals before they are applied to the set. Other than this the i.f.s could be peaked to narrow the bandwidth (increasing the overall gain) but this may impair the definition achieved with local transmissions.

HMV 2703

This colour set is fitted with the BRC 3000 chassis. The fault is no colour. Also after two-three hours the line hold control has to be adjusted to one end of its range, a black band then appearing on the left-hand side.—J. Trafford (Newport).

It is possible that both these faults are caused by the same component. However, first check the chrominance fault. Check that the fine tuning is correct. If it is connect an 82k Ω resistor from the junction of C323, C324 across the ident amplifier 7.8kHz coil to chassis. This will switch on the PAL switching transistor VT307 and over-ride the colour killer action. If you obtain a good colour picture by doing this the fault lies in the colour killer circuit: check the associated components especially the diodes W305 and W322. If on the other hand you obtain Venetian blinds it is most likely that the fault is in the 7.8kHz ident circuit or the PAL switch W309-W310. The switching diodes can easily be checked but the ident circuit is not so easy: if this is working however an audible whistle will be heard from the loudspeaker if a 470k Ω resistor is connected from the junction of C323, C324 to the slider of the volume control. If this cannot be heard check the ident circuit. If on over-riding the colour killer there is no colour at all check the reference oscillator VT304 and the chrominance stages VT110, VT309 and VT310. Turning now to the line oscillator fault, check the electrolytics C506 and C511 in the line oscillator stage. Check also the flywheel sync diodes W501 and W502. Also the resistors R502, R524 and R505 in the line hold control circuit as

these may be high-resistance. Finally C520, 7500pF, in the circuit which supplies the burst gating pulses can cause no colour which will return if the line hold is unlocked.

GEC 2018

Sound and vision disappeared on 625 lines. The tuner unit was removed for examination but no obvious fault was found. On refitting the tuner unit all three u.h.f. channels came back to life. After about four hours however the ITV signal went off. BBC-1 was tuned in and lasted a few more hours before that too went off. The same thing happened with BBC-2.—G. Dossett (Oxford).

The trouble you describe is quite common on this series of models and is caused by the mixer-oscillator transistor failing to oscillate. The transistor—Tr2, AF186—can be replaced or alternatively the problem can be overcome by raising the 12V supply to 13V by shunting the upper resistor R32 (10k Ω wire-wound) of the potential divider which supplies the u.h.f. tuner with a resistor of some 47k Ω —check with a voltmeter.

QUERIES COUPON

This coupon is available until February 21, 1972, and must accompany all Queries sent in accordance with the notice on page 185. Don't forget the 10p postal order!

TELEVISION FEBRUARY 1972

TEST CASE**110**

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

? A Philips Model G24T300 came in with the complaint of height varying spasmodically. The outside engineer had already performed the usual on-site tests, including changing the PCL85 and EF80 valves used in the field timebase, checking the field timebase panel interconnections and examining the obvious timebase components, but to no avail.

The back was removed in the workshop and the receiver operated normally when switched on and failed to show the symptom even after an hour's operation. It was then set up on the test bench with the back held in position at one fixing point, the display being checked from time to time by the apprentice. After thirty minutes or so the symptom appeared, starting with field judder and developing fairly quickly to intermittent height variation, ending up

with the height reducing to about 2in.

The apprentice was asked to observe the picture while the bench engineer quickly removed the back and performed an exploratory test armed with only a screwdriver. To the amazement of the apprentice the symptom disappeared and although there was slight vertical overscan the picture was perfect. What component was most likely to be responsible for the symptom and what could have been the exploratory test made by the engineer to prove the possibility? See next month's TELEVISION for the solution and for another item in the Test Case series.

SOLUTION TO TEST CASE 109

Page 138 (last month)

After testing almost every component in the line timebase, including the line output transformer, the technician in desperation decided to extract the scanning coils for detailed examination. This was where the trouble was discovered.

The line linearity control in this model consists of a copper foil loop cemented to the inside of a paper sleeve operating inside the scanning coils round the tube neck. Linearity is adjusted by moving the sleeve. If the sleeve and hence the loop is incorrectly adjusted the line scan as well as the linearity is affected due to the loop acting something like a shorting turn. The loop in the set in question had departed from the sleeve and had become stuck to the tube neck in the "shorting turn" position!

TELEVISION CLASSIFIED ADVERTISEMENTS

The pre-paid rate for classified advertisements is 5p a word (minimum 12 words), box number 10p extra. Semi-display setting £3 per single column inch. All cheques, postal orders, etc., to be made payable to TELEVISION and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, TELEVISION IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD, for insertion in the next available issue.

EDUCATIONAL



COLOUR TELEVISION TRAINING

11 WEEKS' COURSE for men with Mono experience. Shorter appreciation courses by arrangement. Hours 10 a.m. to 1 p.m. Monday to Friday. Next course commences Jan. 17th. Prospectus from: London Electronics College, Dept. C/2, 20 Penywern Road, London, SW5 9SU. Tel. 01-373 8721.

ENGINEERS—get a technical certificate, Exam. and Certificate Postal Courses in all branches of Engineering, Electronics, Radio and TV, Computers, Draughts, Building, etc. Write for helpful **FREE BOOK**, B.I.E.T. (Dept. H.6), Aldermaston Court, Reading, RG7 4PF.

BECOME "Technically Qualified" in your spare time, guaranteed certificate and exam Home Study courses in Radio, TV, servicing and maintenance, R.T.E.B., City & Guilds, etc., highly informative **FREE Guide**.—Chambers College (Dept. R105), Aldermaston Court, Reading, RG7 4PF.

RADIO AND TV Exams and Courses by Britain's finest home study School. Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Certificate, etc. Free brochure from British National Radio School, Russel Street, Reading.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 560, INTERTEXT HOUSE, STEWARTS ROAD, LONDON SW8 4UJ.
Accredited by the CACC

MISCELLANEOUS

RECORD TV sound using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p plus 10p P&P. Crowborough Electronics (T), Eridge Road, Crowborough, Sussex.

TELEPHONE Answering Machines New/Reconditioned. £55/£160. S.T.A.M. Co., 182a New North Road, N.I. 01-286 6119.

WANTED

CASH PAID for New Valves. Payment by return. **WILLOW VALE ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

SERVICE SHEETS purchased, **HAMILTON RADIO**, 54 London Road, Bexhill.

WANTED — Practical Television, all volumes 1960-1970. Best prices paid. C.O.D. G. Bradley, Coolcalm, Desertmartin, Co. Derry, N. Ireland.

WANTED: Radio and Television Servicing, 1955-1968. Also MW6/2 projection optics bearing CP100 on lens. **HUM-FRESS**, 43 DALGETY GARDENS, DALGETY BAY, FIFE. Phone D.B. 2339.

NEWNES "Radio and TV Servicing", 1959-65, 1968-71. State price/condition. Mohan, 59 Bosworth Road, St. Helens.

TOP PRICES PAID
for new valves, popular
TV & Radio Types

KENSINGTON SUPPLIES
(A), 367 Kensington Street
Bradford 8, Yorks

WANTED! New valves especially TV types. Cash waiting. Bearman, 6 Potters Road, New Barnet, Herts. Tel. 449/1934.

SERVICE SHEETS

SERVICE SHEETS

(1925-1971) for Radios, Televisions, Transistors, Radiograms, Car Radios, Tape Recorders, Record Players, etc.
By return post with

FREE FAULT FINDING GUIDE

PRICES FROM 5p

Over 8,000 models available.
Catalogue 13p.

Please send stamped addressed envelope with all orders and enquiries.

Hamilton Radio

54 London Road, Bexhill, Sussex
Telephone Bexhill 7097

LARGE SUPPLIER of SERVICE SHEETS

(TV, RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each.

PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES AND ORDERS.

Otherwise cannot be attended to.

(Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA 71 BEAUFORT PARK, LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

MAIL ORDER ONLY

★ Service Sheets and Manuals ★

COVERING RADIOS, TELEVISIONS, TAPE RECORDERS, RECORD PLAYERS, ETC. FROM 1933 UP-TO-DATE FROM 40p. EACH - 1971 SERVICE SHEET INDEX LIST 20p. - S.A.E. WITH ENQUIRIES PLEASE

NEW BOOKS & PUBLICATIONS	Price + Post
COLOUR TELEVISION SERVICING by Gordon J.King. 332 pages	£4.40 30p
COLOUR TELEVISION PICTURE FAULTS by K.J. Bohlman. Illustrated in Colour	£2.50 20p
THE MAZDA BOOK OF PAL RECEIVER SERVICING by D.J. Seal. FSERT.MRTS. 288 pages	£3.50 30p
T.V. FAULT FINDING BOOK by Data Publications Ltd. 405/625 Edition. 124 pages	£0.50 8p
UNDERSTANDING TELEVISION by J.R. Davies. 512 pages	£2.10 25p
HOW TO RECEIVE FOREIGN TV PROGRAMMES ON YOUR SET by W.J. West	£0.33 7p
PAL COLOUR TV by Mullard Ltd. How Colour Works. 100 pages	£0.65 10p
1971-72 MULLARD DATA BOOK. Data on Valves and Semiconductors	£0.30 7p
TRANSISTOR EQUIVALENTS AND SUBSTITUTES HANDBOOK by B.B. Babani	£0.40 7p
TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard Ltd. 205 pages	£1.50 15p
RADIO VALVE AND TRANSISTOR DATA by A.M. Ball. 9th Edition. 340 pages	£0.75 15p
GUIDE TO BROADCASTING STATIONS. 16th Edition. 219 pages	£0.50 8p

Send S.A.E. for 'FREE' List of Practical and Technical Books on Radio & Television now available to . . .

BELL'S TELEVISION SERVICES
Albert Place, Harrogate, Yorkshire. Telephone 0423-86844

SERVICE SHEETS (continued)

TRADER SERVICE SHEETS

40p each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED
29 CHURCH ROAD,
TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1971 List now available at 10p plus postage

If list is required indicate with X

From

Address

enclose remittance of
(and a stamped addressed envelope)
s.a.e. with enquiries please
MAIL ORDER ONLY (May T)

SERVICE SHEETS. Radio, TV, etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS with Free Fault Finding Chart 35p, plus stamped addressed envelope. LESMAR, 15 Conholt Road, Andover, Hants.

SETS & COMPONENTS

SOUTHERN VALVE COMPANY

44 Earls Court Road, London, W.8

SPECIALISTS IN QUALITY VALVES FROM TOP MANUFACTURERS; WE DO NOT CLAIM THE LOWEST PRICE, BUT GENUINE VALUE!

All new and boxed, some BVA. Send s.a.e. for list. Mainly British.

DY87	37p	PC86 & 8	50p	PCL805	45p	U193	35p	30L17	75p
DY802	45p	PC97	40p	PCL86	37p	U251	62p	30P12	70p
EB91	15p	PCF80	32p	PL36	52p	6/30L2	60p	30PL1	60p
ECC81	37p	PCF86	52p	PL81	46p	6BW7	60p	30P4MR	95p
ECC82	30p	PCF801	50p	PL84	55p	6CD6G	90p	30P19	70p
ECL80	40p	PCF802	50p	PL500/4	65p	6F23	75p	30PL13	75p
EF80	27p	PCF805	50p	PY81	35p	6F28	48p	30PL14	75p
EF183	37p	PCF808	60p	PY800	35p	20L1	85p	etc., etc.	
EF184	37p	PCL82	37p	PY801	35p	20P4	90p		
EH90	45p	PCL83(s)	50p	U25	65p	30C15	70p		
EY51	50p	PCL84	37p	U26	60p	30FL1 & 2	75p		
EY86/7	37p	PCL85	45p	U191	65p	30L15	75p		

POST FREE OVER £2, BELOW 2½p EACH.
MAIL ORDER ONLY.

PHILIP H. BEARMAN

A leading name in valves and Tubes!

(Mullard, Thorn, Telefunken, etc.)

NEW MOSTLY BVA VALVES! Huge range by post service well known to the trade. Brief list of television types herewith, full list S.A.E. All types ex stock!

DY86/7	40p	PCF86	60p	PY82	47p	20L1	90p
EB91	22p	PCF801/2	59p	PY800/1	47p	20P4	90p
ECC82	42p	PCF805	83p	R19	80p	30C15	86p
ECL80	47p	PCF808	80p	U25	91p	30C17	91p
EF80	39p	PCL82	48p	U26	91p	30F5	91p
EF85	41p	PCL83(S)	60p	U37	75p	30FL1 & 2	62p
EF183/4	54p	PCL84	57p	U191	86p	30L15	91p
EH90	51p	PCL805/85	54p	U193	47p	30L17	86p
EY51	60p	PCL86	63p	U251	91p	30P12	90p
EY86/7	40p	PL36/8	83p	U301	85p	30PL1	86p
PC86 & 8	72p	PL81	75p	U801	99p	30P4MR	£1-00
PC97	42p	PL83	81p	6/30L2	86p	30P19	83p
PC900	52p	PL84	62p	6AT6	52p	30PL13	95p
PCC84	47p	PL500	86p	6BW7	78p	30PL14/5	95p
PCC89	58p	PL504	86p	6CD6G	90p	etc., etc.	
PCF80	50p	PY81	47p	6F23	90p	Trade prices	

POST FREE OVER £3-00, 2½p PER VALVE BELOW £3-00

LATEST NEW BY100/127 type silicon rectifier 15p, 33Ω res 5p!

Large bulb Imported PCF80 30p! Note. Ask for separate component and transistor lists. Mullard/Mazda data books 20p.

6 POTTERS ROAD, NEW BARNET, HERTS.

(Adjacent to Post Office)

Tel, 01-449/1934 & 449/1935
(Robophone)

Special quantity terms, lists,
s.a.e. GIRO 34.361.4006

(Suppliers to H.M. Govt. etc.)

TESTED TOP 20 TV VALVES FROM 10p. PL504, 17½p. New PL508's, 45p. Individually boxed, p & p 4p per valve, 12 or over 2½p, over £3 free. Resistors and capacitors by leading manufacturers at competitive prices. Stockists of "THE WONDER LEAD" colour C.R.T. tester. Send for leaflet. Trade enquiries welcomed. S.A.E. for new free list. L. & D. Components Ltd., 71Westbury Avenue, Wood Green, N.22 6SA. 01-888 2701.

EX-RENTAL TV's (UNTESTED)

Complete with 13 channel tuners. Good cabinets. Carriage £1-50 extra.

17" Semi Slim (90° Tube)	..	£2-50
17" 21" Slim (110° Tube)	..	£4-50
19" Slimline	..	£5-50
23" Slimline	..	£8-50
19" BBC2 Sets	..	£14-50

TUBES EX-EQUIPMENT TESTED

SINGLE PANEL

17" any type	..	£2
19"/21" any type	..	£3
23" any type	..	£4

TWIN PANEL (BONDED)

19" bonded	..	£5
23" bonded	..	£6

PANORAMA TUBES (METAL RIM)

19" Panorama	..	£5
23" Panorama	..	£6

All tubes add £1 carriage

PERFECT SPEAKERS EX TV

Pm 3 ohm (minimum order two) 5 in. round, 8 in. by 2 in. rectangular—12½p each. Add 7½p per speaker p. & p. Special offer:—100 speakers delivered for £15.

VALVES EX EQUIPMENT

EB91	5p	30L15	12½p	PL36	22½p
EBF89	12½p	30P4	12½p	PL81	17½p
ECC82	12½p	PC97	17½p	PY81	15p
ECL80	7½p	PCF86	17½p	PY800	15p
EF80	12½p	PC84	7½p	PY82	7½p
EF85	12½p	PCF80	7½p	PY33	22½p
EF183	42½p	PCF89	12½p	U191	17½p
EF184	12½p	PCL85	22½p	6F23	17½p
EY86	17½p	PCL82	17½p	30PL1	22½p
30PL13	30p	PCL86	17½p	30F12	20p
630LZ	12½p	PCL83	12½p	30F3	10p

Add 2½p per valve p. & p., orders over £1 p. & p. free

UHF TUNERS

For Ferguson 850 900 chassis. Adaptable for most U.H.F. Chassis £2-50, p. & p. 50p.

TRADE DISPOSALS (Dept. PT/TS)

Thornbury Roundabout, Leeds Ed., Bradford.
Telephone: 0274-865670

TELEVISION TUBE SHOP

BRAND NEW TUBES AT
REDUCED PRICES

A28-14W (A28-13W)	£12.75
A31-18W	£12.50
A47-11W	£9.95
A47-13W	£12.50
A47-14W	£8.25
A47-26W	£10.75
A50-120WR	£12.50
A59-11W	£12.95
A59-13W	£13.50*
A59-15W	£9.95
A59-16W	£13.50*
A59-23W	£14.75
A61-120WR	£16.00
AW-21-11	£7.00*
AW36-21, 36-80	£5.75
AW43-80	£6.95
AW43-88, 43-89	£6.75
AW47-90, 47-91	£7.50
AW53-80	£7.50*
AW53-88, 53-89	£8.25
AW59-90, 59-91	£9.00
C17LM, 17PM, 17SM	£6.50
CME1201	£12.50
CME1402	£5.75
CME1601	£10.50
CME1602	£12.00
CME1702, 1703	£6.75
CME1705	£7.75
CME1713/A44-120	£14.50
CME1901, 1903	£7.50
CME1906	£12.50
CME1908	£7.75
CME2013	£12.50
CME2101, 2104	£8.25
CME2301, 2302, 2303	£9.00
CME2305	£14.75
CME2306	£13.50*
CME2308	£9.95
CME2413R	£16.50
CRM93, 124	£5.50*
CRM141, CRM142	£5.50
CRM171, CRM172	£6.50
CRM211, CRM212	£7.50*
MW36-24, 36-44	£5.50
MW43-69	£6.75
MW43-80	£6.75
MW53-20, 53-80	£7.50
TSD217, TSD282	£14.00†
13BP4 (Crystal 13)	£14.00†
190AB4	£9.25
230DB4	£11.25

†Rebuilt tubes also,
at £7.00 plus bulb

*These types are FULLY rebuilt.

ALL TUBES ARE TESTED AND GUARANTEED FOR A MINIMUM OF 12 MONTHS

ADD 75p FOR CARRIAGE AND INSURANCE

COLOUR TUBES

19 in. and 22 in. having slight marks or scratches at £35 each

TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD,
LONDON, S.W.11. 228 6859

WE GIVE GREEN SHIELD
STAMPS

AERIAL BOOSTERS

We make four types of Aerial Boosters. L45 625 U.H.F., L12 V.H.F. TV, L11 V.H.F. Radio, L10 M/W & S/W. Price L45, L12 and L11 £2.95, L10 £1.45.

VALVE BARGAINS

Any 5—45p, 10—70p:
6X52, 6CL80, 6F80, 6F85, 6F183, 6F184, 6BF89, 6B91, 6Y86, 6PC84, 6CC89, 6C97, 6CF80, 6CF86, 6CL82, 6CL83, 6CL84, 6CL85, 6PL36, 6PY33, 6PY82, 6PY800, 6PY801, 60L15, 60C15, 6-30L2.

POST AND PACKING: Under £1, 5p. Over £1, 10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

VELGO ELECTRONICS

62A Bridge Street, Ramsbottom, Bury, Lancs.

TRANSISTOR BARGAINS

We offer the following brand new marked transistors for sale. Any 5—40p, 10—75p—BC113, BC171, BC117, BC135, BC153, BF115-15p, BF184-15p, BF200-20p.

PRINTED CIRCUIT BOARD

2-8 ins. by 4 ins. boards complete with etching compound and instructions—40p.

MAINS DROPPERS

Three section 33-33-33 Ohms. 9p.

FOR SALE

VALVES EX. TV from 5p, 3p postage, speakers from 37p, postage 10p. Valve cartons, Globe Electrics, 151a Brighton Road, Surbiton, Surrey. 01-399 7333.

HEATHKIT Transistor Tester as new, £14. Tech RF Signal Generator as new, £13. J. C. Thompson, 16 South Grove, Tottenham, London N15 5QD.

COPIES "Television" Sept. 1965, Dec. 1971. Obsolete valves. S.A.E. please. Jackson, 37 Gibraltar Avenue, Halifax, Yorks.

AERIALS

AERIALS

UHF: Set Tops £2.10, Outside: 9 ele £1.25, 10 ele £1.90, 11 ele £2.50, 12 ele £2.55, 18 ele £3.25, 20 ele £3.50. Multi-beam 46 and Supremes £5.50.

All aerials supplied with clamps.

ANTIGHOST: Troubleshooters/Log-beams £5.

FM/VHF: H £2.25, 3 ele £3.25, 4 ele £3.75. Stereo 6 ele £6.

Motorized Units: Semi Auto £20, Auto £25.

All Aerials by leading makers.

ELECTRONICS, ACCESSORIES: Incl. Masts, Lashings, Plugs, Amps., Headphones, Meters, Stereo Cartridge Players, Cassettes, Tapes, etc., etc.

COAXIAL: Standard 100 Mtrs. £4.50. Low Loss £7, or per Mtr.

State channels for all TV Aerials/Amps. FM state wide band or channelized.

TERMS: CWO, COD, P & P 32p. Send 2½p stamps for lists. Callers Welcome.

OVERSEAS customers welcome. Note New Zealand/Australia by sea, 7 weeks min. By Air quotations given.

JEFFRIES SERVICES

31 Hambrook St., Portsmouth. Tel. 28354

BAINES for HIGH FREQUENCY AERIALS

POSTAGE PAID ON AERIALS INLAND

UHF Multibeams:
Colour or Monochrome reception. MBM 10 £1.90, MBM 18 £2.95, MBM 30 £3.60, MBM 38 £5.10, MBM 46 £5.50. Supplied complete with clamp.

405 Aerials:
BBC Dipole £1.75, BBC H £2.50, BBC X £2.40, BBC/LTA Dipole and 5 £2.70, BBC/LTA H and 5 £4.10, IFA 5 element £2.00.

FM Aerials:
Dipole £1.40, 2 element £2.00.

Pre-Amps:
Masthead £6.00, Colourbooster £3.88. Postage paid on these.

Accessories:
A SAE will bring a full list.
Co-Ax VHF 3p and UHF 5p per yard.
Please state channels or Transmitters on all aerial orders.

B. BAINES 11 Dale Cres, Tupton, Chesterfield.

WITWORTH Transformers

Line out-pot transformers
Manufacturers of the largest range in the country. All makes supplied. Free catalogue.

Modern

BAIRD, BUSH, GEC, PHILIPS.
Replacement types ex-stock.

For "By-return" service, contact your nearest Depot:

London: 01-948 3702
Tidman Mail Order Ltd., Dept. PT, 236 Sandycroft Road, Richmond, Surrey.

Birmingham: 021-643 2148

Hamond Components, 89 Meriden Street, Birmingham 5.

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-pot Transformers also stocked.

CALLERS WELCOME

CHROMASONIC ELECTRONICS

LOW NOISE HI-STABS

½ watt 5%, all E24 values 3 for 2p plus p. & p. 6p for up to 50 resistors + 1p for each additional 50.

POWER SECTIONS

7 to 20Ω	22 to 36Ω	at -7A
40 to 100Ω	120 to 270Ω	at -3A
—	726Ω	at -15A
300 to 560Ω	—	at -12A
1KΩ	—	at -1A
—	2KΩ	at -07A
20p. ea.	25p. ea. p. & p. 6p per section.	

REPLACEMENT DROPPERS

37 + 31 + 97 + 26 + 168Ω	50p	} p. & p. 7p. ea.
14 + 26 + 97 + 173Ω	50p	
30 + 125 + 2+85KΩ	50p	

AA119/20	10p	BC148	12p	BU103	£2.75
AC127/8	17p	BC157/59	20p	TAA661B	£1.80
AC176	23p	BC158/68	15p	TAA700	£2.00
BC147/9	15p	BE115/73	25p	PA237	£1.55

CARBON TRACK POTS, Single gang Log or Lin 12p

1972 CATALOGUE 10p post free

P. & P. on all orders other than resistors 6p
56 FORTIS GREEN ROAD, LONDON N10 3HN

120 NEW ASSORTED Capacitors, Electrolytic, Mica, etc., and Resistors, ¼/20W, 85p. Post Free. Whitsam Electrical, 33 Drayton Green Road, London, W.13.

LADDERS

LADDERS, 24½ft., £8.90, order C.O.D. Phone 02-993 5222. Home Sales, Baldwin Road, Stourport, Worcs. Callers welcome.

PHILIP H. BEARMAN,

A LEADING NAME IN
VALVES AND TUBES

LARGE STOCKS BY LEADING BRITISH AND FOREIGN MANUFACTURERS
TUBES GUARANTEED 2 YEARS, COLOUR 4 YEARS! ALL EX STOCK

Every tube tested before it leaves our premises.

FOR EXAMPLE:

			Cge.
CME1702, AW43-80, CRM173, MW43-80, MW43-69*, CRM172, AW43-88, AW43-89, CME1705, CME1703, C17AF	17"	£5-87p	55p
CME1903, CME1902, CME1901, AW47-90, AW47-91, A47-14W, C19AH, C19AF	19"	£6-87p	60p
CME2101, AW53-88, AW53-89, CRM211, CRM212, MW53-20, MW53-80, CME2104	21"	£7-87p	65p
CME2303, CME2301, AW59-90, AW59-91	23"	£9-50p	65p

* Rebuilds only

ALSO

TSD282	11"	£12-50
A28-14W	11"	£10-50
MW31-74	12"	£3-00
TSD290	12"	£9-80
MW36, 24, etc.	14"	£4-75
CME1601	16"	£7-50
CME1602	16"	£10-15
CME1906	} 19"	£10-12
A47-13W		
A47-11W	19"	£9-50
A50-120W	20"	£10-50
CME2306	} 23"	£15-00
A59-13W		
A59-11W	23"	£11-10
CME2413	24"	£13-00
CME2501	25"	£17-00

Plus carriage, but if sea journey, 50p extra

COLOUR TUBES

4 YEAR GUARANTEE

19" A49.11X, A49.120X	£49-00	plus £1 carriage
22" A55.141X, A56.120X	£53-00	plus £1 carriage
25" A63.11X, A63.200X	£57-00	plus £1 carriage

All prices net trade

We endeavour to maintain prices but all are subject to alteration without notice

6 POTTERS ROAD, NEW BARNET, HERTS. TEL: 01-449/1934 (Robophone) and 449/1935

Direct from the Manufacturers

U.H.F. AERIALS

EASY ASSEMBLY KITS

10 Element **SAVE** **£1-25** **40%** on normal retail price

14 Element **£1-50** 18 Element **£1-75**

Ready assembled add 20p allow 32½p. carriage and packing. Please state which channels or group.

TRADE SUPPLIED, SEND FOR LIST

APEX AERIALS (T.V.)
ALBAN WORKS, MARY ST.
JOHNSTONE, RENFREWSHIRE



GENUINE FULL SIZE
18 element TV aerial
as used by leading rental companies

FOR ONLY **£1.99** + 34p p.&p.


A fantastic buy, save money and do-it-yourself. Receives BBC1, BBC2 and ITV on UHF 625 channels, colour and black/white. 18 element aerial with grid reflector for better reception. A proper aerial, usually supplied only by riggers. Buy now and cut out the middle man. An ideal aerial for the person who likes to do it himself. Complete with fixing clamp and instructions. Money back guarantee. Use inside or out.



IMPERIAL TRADING
(Dept PT10)
45 Arkwright Street, Nottingham

U.H.F. TV AERIALS

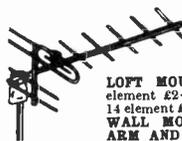Suitable for Colour and Monochrome Reception



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS. 7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75. **WALL MOUNTING c/w WALL ARM AND BRACKET.** 7 element £3-25. 11 element £3-75. 14 element £4-25. 18 element £4-75. **CHIMNEY MOUNTING ARRAYS c/w MAST AND LASHING KIT.** 7 element £4. 11 element £4-50. 14 element £4-75. 18 element £5-25. **MAST MOUNTING arrays only** 7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75. Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 9p yd. **KING TELE-BOOSTERS** from £3-75. **LABGEAR** all band V.H.F.-U.H.F.-F.M. radio mains operated preamps £7-50. State clearly channel number required on all orders. P.p. on all aerials 50p. Acca. 15p. C.W.O. Min. C.O.D. charge 25p.

BBC-ITV-FM AERIALS

BBC (band 1) Wall S/D £2. **LOFT** inverted 'T' £1-25. **EXTERNAL** 'H' array only £3. **ITV** (band 3) 5 element loft array £2-30. 7 element £3. **COMBINED BBC-ITV** loft 1+5 £2-75. 1+7 £3-50. **WALL AND CHIMNEY UNITS ALSO AVAILABLE.** Pre-amps from £3-75. **COMBINED U.H.F.-V.H.F. aerials** 1+3+9 £4. 1+5+14 £4-50. 1+7+14 £5. **FM RADIO** loft S/D £1. 3 element £3-25. 4 element £3-30. Standard coaxial plugs 5p. Coaxial cable 5p yd. Outlet box 30p. P.p. all aerials 50p. Acca. 30p. C.W.O. Min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS

40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

COLOUR TUBES STANDARD TUBES

METAL BAND TUBES

TWIN PANEL TUBES

Rebuilt with new Electron Guns at under 50% normal list price

SUFFOLK TUBES LIMITED

261 CHURCH ROAD,
MITCHAM, SURREY
01-640 3133

Britain's largest INDEPENDENT
TV Tube rebuilder

We also require large quantities of all types of old tubes for cash


The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107 15p	AFI15 17p	BCI40 35p	BCY31 22p	BF272 80p	EC403 15p	ORP60 40p	2N918 30p	2N2714 25p	2N3704 15p
AC113 20p	AFI16 17p	BCI41 35p	BCY32 25p	BF273 30p	GET880 27p	ORP61 40p	2N929 22p	2N2904 25p	2N3705 12p
AC115 23p	AFI17 17p	BCI42 45p	BCY33 15p	BF274 30p	MAT100 15p	5T140 12p	2N930 25p	2N2904A 30p	2N3706 12p
AC125 17p	AFI34 30p	BCI43 45p	BCY34 20p	BF308 35p	MAT101 17p	5T141 17p	2N1131 20p	2N2905 25p	2N3707 13p
AC126 17p	AFI24 21p	BCI45 45p	BCY70 17p	BF310 37p	MAT120 15p	5T142 17p	2N1132 22p	2N2905A 30p	2N3708 8p
AC127 17p	AFI25 20p	BCI47 17p	BCY71 30p	BF316 35p	MAT121 17p	UT46 27p	2N1302 17p	2N2906 25p	2N3710 10p
AC128 17p	AFI26 20p	BCI48 12p	BCY72 15p	BFW10 55p	MPF102 43p	V405A 25p	2N1303 17p	2N2906A 27p	2N3710 10p
AC141K 17p	AFI27 20p	BCI49 17p	BCZ11 20p	BFX29 27p	MPF105 43p	V410A 45p	2N1304 20p	2N2907 25p	2N3711 10p
AC157 17p	AFI86 45p	BCI50 17p	BD121 85p	BFX84 20p	OC19 30p	2G301 19p	2N1305 20p	2N2907A 30p	2N3819 40p
AC158 17p	AFI39 33p	BCI51 20p	BD123 85p	BFX85 27p	OC20 30p	2G302 19p	2N1306 22p	2N2923 13p	2N3820 41
AC154 15p	AFI79 50p	BCI52 17p	BD124 75p	BFX86 22p	OC22 30p	2G303 19p	2N1307 22p	2N2924 15p	2N3903 25p
AC155 17p	AFI80 50p	BCI53 27p	BD131 80p	BFX87 25p	OC23 33p	2G304 20p	2N1308 27p	2N2925 13p	2N3904 27p
AC156 17p	AFI91 50p	BCI54 30p	BD132 80p	BFX88 22p	OC24 45p	2G306 35p	2N1309 27p	2N2926 15p	2N3905 25p
AC157 17p	AFI86 45p	BCI57 20p	BDY20 41	BFY50 20p	OC25 25p	2G308 35p	2N1613 17p	(G)	2N3906 27p
AC165 17p	AFI39 33p	BCI58 17p	BF115 25p	BFY51 20p	OC26 25p	2G309 35p	2N1711 20p	2N2926	2N4058 10p
AC166 17p	AFI21 17p	BCI59 20p	BF117 45p	BFY52 20p	OC28 20p	2G319 17p	2N1889 35p	(Y)	2N4059 10p
AC167 20p	AFI22 45p	BCI67 13p	BF118 60p	BFY53 17p	OC29 40p	2G339A 15p	2N1890 45p	2N2926	2N4060 10p
AC168 20p	AL102 85p	BCI68 13p	BF119 70p	BSX19 15p	OC35 33p	2G344 15p	2N1893 37p	(O)	2N4061 12p
AC169 14p	AL103 85p	BCI69 13p	BF152 35p	BSX20 15p	OC36 40p	2G345 15p	2N2160 60p	2N3010 80p	2N4062 12p
AC176 23p	ASV26 25p	BCI70 13p	BF153 35p	BSY25 15p	OC41 20p	2G371 13p	2N2147 75p	2N3011 20p	2N5172 12p
AC177 20p	ASV27 30p	BCI71 13p	BF154 35p	BSY26 15p	OC42 22p	2G371B 10p	2N2148 60p	2N3053 20p	2N5459 43p
AC187 30p	ASV28 25p	BCI72 13p	BF157 45p	BSY27 15p	OC44 15p	2G374 17p	2N2192 30p	2N3054 50p	2S034 75p
AC188 30p	ASV29 25p	BCI73 13p	BF158 25p	BSY28 15p	OC45 12p	2G377 17p	2N2193 30p	2N3055 63p	2S031 50p
AC197 25p	ASV30 25p	BCI74 13p	BF159 30p	BSY29 15p	OC70 15p	2G378 15p	2N2194 27p	2N3391 17p	2S032A 45p
AC198 18p	ASV31 25p	BCI75 25p	BF160 30p	BSY38 15p	OC71 9p	2G382 15p	2N2217 20p	2N3391A 20p	2S032 45p
AC199 23p	ASV32 25p	BCI77 17p	BF162 30p	BSY39 15p	OC72 12p	2G401 30p	2N2218 25p	2N3392 17p	2S033 60p
AC200 20p	ASV34 25p	BCI78 17p	BF163 35p	BSY40 30p	OC74 12p	2G414 40p	2N2219 30p	2N3393 17p	2S034 75p
AC201 20p	ASV35 25p	BCI79 17p	BF164 35p	BSY41 35p	OC75 15p	2G417 25p	2N2220 22p	2N3394 15p	2S035 41
AC202 19p	ASV36 25p	BCI80 20p	BF165 35p	BSY95 12p	OC76 15p	2N388 30p	2N2221 22p	2N3395 20p	2S036 41
AC203 18p	ASV37 15p	BCI81 25p	BF167 22p	BSY95A 12p	OC77 25p	2N388A 50p	2N2222 27p	2N3402 22p	2S037 41
AC204 18p	ASV38 15p	BCI82 10p	BF172 22p	BU105 43 90	OC78 22p	2N487 22p	2N2223 22p	2N3403 22p	2S038 60p
AC205 18p	ASV39 15p	BCI83 10p	BF173 35p	C111E 60p	OC81D 15p	2N404A 40p	2N2224 22p	2N3404 30p	2S039 60p
AC206 18p	ASV40 15p	BCI84 10p	BF174 35p	C400 30p	OC82 15p	2N524 15p	2N2369A 15p	2N3405 45p	2S040 45p
AC207 18p	ASV41 15p	BCI85 10p	BF175 35p	C407 25p	OC82D 15p	2N527 60p	2N2411 50p	2N3414 20p	2S041 60p
AC208 18p	ASV42 15p	BCI86 10p	BF176 35p	C424 17p	OC83 20p	2N696 12p	2N2412 50p	2N3415 20p	2S042 60p
AC209 18p	ASV43 15p	BCI87 10p	BF177 35p	C425 40p	OC84 22p	2N697 15p	2N2413 50p	2N3417 37p	2S043 60p
AC210 18p	ASV44 15p	BCI88 10p	BF178 35p	C426 30p	OC139 15p	2N698 45p	2N2414 50p	2N3418 37p	2S044 60p
AC211 18p	ASV45 15p	BCI89 10p	BF179 35p	C427 30p	OC140 17p	2N699 55p	2N2415 50p	2N3419 37p	2S045 60p
AC212 18p	ASV46 15p	BCI90 10p	BF180 30p	C428 20p	OC170 15p	2N706 15p	2N2416 50p	2N3420 37p	2S046 60p
AC213 18p	ASV47 15p	BCI91 10p	BF181 30p	C429 20p	OC171 15p	2N706A 8p	2N2417 50p	2N3421 37p	2S047 60p
AC214 18p	ASV48 15p	BCI92 10p	BF182 30p	C430 20p	OC202 27p	2N708 12p	2N2418 50p	2N3422 37p	2S048 60p
AC215 18p	ASV49 15p	BCI93 10p	BF183 30p	C431 20p	OC203 25p	1N709 45p	2N2419 50p	2N3423 37p	2S049 60p
AC216 18p	ASV50 15p	BCI94 10p	BF184 25p	C432 20p	OC204 25p	2N718 24p	2N2420 50p	2N3424 37p	2S050 60p
AC217 18p	ASV51 15p	BCI95 10p	BF185 30p	C433 20p	OC205 25p	2N718A 30p	2N2421 50p	2N3425 37p	2S051 60p
AC218 18p	ASV52 15p	BCI96 10p	BF186 30p	C434 20p	OC206 25p	2N726 15p	2N2422 50p	2N3426 37p	2S052 60p
AC219 18p	ASV53 15p	BCI97 10p	BF187 30p	C435 20p	OC207 27p	2N727 15p	2N2423 50p	2N3427 37p	2S053 60p
AC220 18p	ASV54 15p	BCI98 10p	BF188 30p	C436 20p	OC208 27p	2N727 15p	2N2424 50p	2N3428 37p	2S054 60p
AC221 18p	ASV55 15p	BCI99 10p	BF189 23p	C437 20p	OC209 27p	2N727 15p	2N2425 50p	2N3429 37p	2S055 60p
AC222 18p	ASV56 15p	BCI100 10p	BF190 23p	C438 20p	OC210 27p	2N727 15p	2N2426 50p	2N3430 37p	2S056 60p
AC223 18p	ASV57 15p	BCI101 10p	BF191 23p	C439 20p	OC211 27p	2N727 15p	2N2427 50p	2N3431 37p	2S057 60p
AC224 18p	ASV58 15p	BCI102 10p	BF192 23p	C440 20p	OC212 27p	2N727 15p	2N2428 50p	2N3432 37p	2S058 60p
AC225 18p	ASV59 15p	BCI103 10p	BF193 23p	C441 20p	OC213 27p	2N727 15p	2N2429 50p	2N3433 37p	2S059 60p
AC226 18p	ASV60 15p	BCI104 10p	BF194 23p	C442 20p	OC214 27p	2N727 15p	2N2430 50p	2N3434 37p	2S060 60p
AC227 18p	ASV61 15p	BCI105 10p	BF195 23p	C443 20p	OC215 27p	2N727 15p	2N2431 50p	2N3435 37p	2S061 60p
AC228 18p	ASV62 15p	BCI106 10p	BF196 23p	C444 20p	OC216 27p	2N727 15p	2N2432 50p	2N3436 37p	2S062 60p
AC229 18p	ASV63 15p	BCI107 10p	BF197 23p	C445 20p	OC217 27p	2N727 15p	2N2433 50p	2N3437 37p	2S063 60p
AC230 18p	ASV64 15p	BCI108 10p	BF198 23p	C446 20p	OC218 27p	2N727 15p	2N2434 50p	2N3438 37p	2S064 60p
AC231 18p	ASV65 15p	BCI109 10p	BF199 23p	C447 20p	OC219 27p	2N727 15p	2N2435 50p	2N3439 37p	2S065 60p
AC232 18p	ASV66 15p	BCI110 10p	BF200 23p	C448 20p	OC220 27p	2N727 15p	2N2436 50p	2N3440 37p	2S066 60p
AC233 18p	ASV67 15p	BCI111 10p	BF201 23p	C449 20p	OC221 27p	2N727 15p	2N2437 50p	2N3441 37p	2S067 60p
AC234 18p	ASV68 15p	BCI112 10p	BF202 23p	C450 20p	OC222 27p	2N727 15p	2N2438 50p	2N3442 37p	2S068 60p
AC235 18p	ASV69 15p	BCI113 10p	BF203 23p	C451 20p	OC223 27p	2N727 15p	2N2439 50p	2N3443 37p	2S069 60p
AC236 18p	ASV70 15p	BCI114 10p	BF204 23p	C452 20p	OC224 27p	2N727 15p	2N2440 50p	2N3444 37p	2S070 60p
AC237 18p	ASV71 15p	BCI115 10p	BF205 23p	C453 20p	OC225 27p	2N727 15p	2N2441 50p	2N3445 37p	2S071 60p
AC238 18p	ASV72 15p	BCI116 10p	BF206 23p	C454 20p	OC226 27p	2N727 15p	2N2442 50p	2N3446 37p	2S072 60p
AC239 18p	ASV73 15p	BCI117 10p	BF207 23p	C455 20p	OC227 27p	2N727 15p	2N2443 50p	2N3447 37p	2S073 60p
AC240 18p	ASV74 15p	BCI118 10p	BF208 23p	C456 20p	OC228 27p	2N727 15p	2N2444 50p	2N3448 37p	2S074 60p
AC241 18p	ASV75 15p	BCI119 10p	BF209 23p	C457 20p	OC229 27p	2N727 15p	2N2445 50p	2N3449 37p	2S075 60p
AC242 18p	ASV76 15p	BCI120 10p	BF210 23p	C458 20p	OC230 27p	2N727 15p	2N2446 50p	2N3450 37p	2S076 60p
AC243 18p	ASV77 15p	BCI121 10p	BF211 23p	C459 20p	OC231 27p	2N727 15p	2N2447 50p	2N3451 37p	2S077 60p
AC244 18p	ASV78 15p	BCI122 10p	BF212 23p	C460 20p	OC232 27p	2N727 15p	2N2448 50p	2N3452 37p	2S078 60p
AC245 18p	ASV79 15p	BCI123 10p	BF213 23p	C461 20p	OC233 27p	2N727 15p	2N2449 50p	2N3453 37p	2S079 60p
AC246 18p	ASV80 15p	BCI124 10p	BF214 23p	C462 20p	OC234 27p	2N727 15p	2N2450 50p	2N3454 37p	2S080 60p
AC247 18p	ASV81 15p	BCI125 10p	BF215 23p	C463 20p	OC235 27p	2N727 15p	2N2451 50p	2N3455 37p	2S081 60p
AC248 18p	ASV82 15p	BCI126 10p	BF216 23p	C464 20p	OC236 27p	2N727 15p	2N2452 50p	2N3456 37p	2S082 60p
AC249 18p	ASV83 15p	BCI127 10p	BF217 23p	C465 20p	OC237 27p	2N727 15p	2N2453 50p	2N3457 37p	2S083 60p
AC250 18p	ASV84 15p	BCI128 10p	BF218 23p	C466 20p	OC238 27p	2N727 15p	2N2454 50p	2N3458 37p	2S084 60p
AC251 18p	ASV85 15p	BCI129 10p	BF219 23p	C467 20p	OC239 27p	2N727 15p	2N2455 50p	2N3459 37p	2S085 60p
AC252 18p	ASV86 15p	BCI130 10p	BF220 23p	C468 20p	OC240 27p	2N727 15p	2N2456 50p	2N3460 37p	2S086 60p
AC253 18p	ASV87 15p	BCI131 10p	BF221 23p	C469 20p	OC241 27p	2N727 15p	2N2457 50p	2N3461 37p	2S087 60p
AC254 18p	ASV88 15p								

THE NEW UM4 "COLOURBOOSTER"

UHF/625 LINE

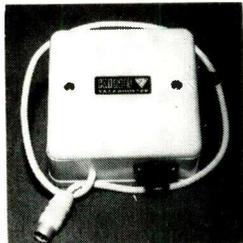

**CAN PRODUCE
REMARKABLE
IMPROVEMENTS IN
COLOUR AND
PICTURE QUALITY
IN FRINGE OR
DIFFICULT AREAS
WITH SIGNIFICANT
REDUCTION IN
NOISE (SNOW).**

HIGH GAIN—VERY LOW NOISE
FITTED FLY LEAD—INSTALLED IN SECONDS
HIGHEST QUALITY COMPONENTS
IVORY PLASTIC CASE 3¼ x 3¼ x 1½ CORK BASE
CHANNELS: Group A, Red code 21-33
Group B, Yellow code 39-51
Group C-D, Green code 52-68

EQUALLY SUITABLE FOR BLACK AND WHITE

Also the M4 DUAL BAND VHF UNIT
BOOSTS ALL BAND III and ANY SPECIFIED
BAND I CHANNEL SIMULTANEOUSLY
NOMINAL GAIN 17-18 DB BOTH BANDS

PRICES BOTH TYPES:

£3.75 Battery model or £5.87 Self-contained mains version
Postage and Packing 13p

TRANSISTOR DEVICES LIMITED
6 ORCHARD GARDENS, TEIGNMOUTH, DEVON
Telephone: Teignmouth 4757

NEW B.V.A VALVES

Full List. Return Post Service. Cash with order.
Stamped addressed envelope. Post Free over £3.00
order.

D.Y.86/7	40p	P.C.F.801/2	61p	P.Y.800/1	45p	30C17	79p
E.B.91	25p	P.C.F.805	65p	R.19	65p	30F5	82p
E.C.C.82	42p	P.C.F.808	67p	U.25	75p	30FL1	64p
E.C.C.80	40p	P.C.L.82	51p	U.26	75p	30FL2	64p
E.F.80	40p	P.C.L.83	61p	U.37	75p	30FL5	76p
E.F.85	41p	P.C.L.84	51p	U.191	72p	30L17	72p
E.F.183/4	56p	P.C.L.805	57p	U.193	41p	30PL2	77p
E.H.90	51p	P.C.L.86	51p	U.251	87p	30PL1	64p
E.Y.51	37p	P.L.36	75p	6/30L2	77p	30P4M.R.	100p
P.C.86	51p	P.L.81	57p	6AT6	49p	30P19	75p
P.C.97	41p	P.L.83	51p	6BW7	69p	30PL13	92p
P.C.900	51p	P.L.84	60p	6CD6	140p	30PL14	92p
P.C.C.84	46p	P.L.500	85p	6F23	77p	30PL15	92p
P.C.C.89	61p	P.L.504	85p	20L1	97p		
P.C.F.80	51p	P.Y.81	45p	20P4	100p		
P.C.F.86	61p	P.Y.82	35p	30C15	69p		

Transistors

A.C.107	15p	B.C.108	13p	81	13p
126	13p	107	13p	O.C.81D	13p
127	17p	B.F.194	15p	O.C.83	20p
128	13p	O.C.41	13p	O.C.170	23p
176	25p		44	O.C.171	23p
A.C.Y.17	15p		45	O.C.200	25p
A.F.239	37p		71	O.C.201	25p
A.F.186	50p		72	2N3819FET	45p
A.F.139	37p		73		

Power Transistors

O.C.26	25p	35	25p	2N3055	63p
28	30p	A.D.149	30p	R2008B	100p

Diodes

B.Y.127	20p	B.Y.133	20p
---------	-----	---------	-----

R. J. BENNISON

WHOLESALE SUPPLIES
1 WHARFEDALE PLACE, HARROGATE

T.V.
TUBES

"VIDEOCHROME"

T.V.
TUBES

FOR BRILLIANCE & DEFINITION



17" £5.00
19" £5.50
21" £7.00
23" £7.50

19" PANORAMA £6.25
23" PANORAMA £8.25

CASH OR CHEQUE WITH ORDER

TRADE SUPPLIED

ALL TUBES PRECISION REBUILT AT OUR OWN
FACTORY BY SKILLED CRAFTSMEN ● EACH TUBE
BENCH AND SET TESTED TO A VERY HIGH
STANDARD BEFORE DESPATCH

2 YEARS GUARANTEE ● FREE
DELIVERY ANYWHERE IN THE U.K.

VIDEOCHROME TUBES LTD.

25 BELLEVUE AVENUE

RAMSGATE, KENT.

Tel. THANET 52914

REBUILT TELEVISION TUBES

STANDARD TYPES:

17" £5.00 21" £6.50
19" £5.50 23" £7.50

'PANORAMA' & 'RINGUARD' TYPES:

19" £7.00 23" £9.00

TWIN PANEL or BONDED FACE TYPES:

19" £7.50 23" £10.00

COLOUR TUBES:

19" £25.00 22" £28.00
25" £30.00 26" £32.00

(exchange bulbs required)

Carriage & Insurance: 75p extra for standard tubes; £1.50 extra
ringuard and twin panel types. £3 extra colour.

- ★ Complete new gun fitted to every tube.
- ★ Two years' guarantee, monochrome. 1 year colour.
- ★ Trade enquiries invited.
- ★ 14 years' experience in tube rebuilding.

N.G.T. ELECTRONICS LTD.,
(NU-GUN TELETUBES)

22 Anerley Station Road,
London, S.E.20

Telephone: 01-778 9178

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast—makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. Elec.
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. Civ.
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier."—Case History G/321.

"In addition to having my salary doubled, my future is assured."—Case History H/493.

"Completing your Course meant going from a job I detested to a job I love."—Case History B/461.

FIND OUT FOR YOURSELF

These letters—and there are many more on file at Aldermaston Court—speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B1 Aldermaston Court, Reading RG7 4PF.

Accredited by the Council for the Accreditation of Correspondence Colleges.



(Write if you prefer not to cut this page.)

POST THIS COUPON TODAY

To: B.I.E.T., Dept. B1, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age

BLOCK CAPITALS PLEASE

Address

Occupation

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE