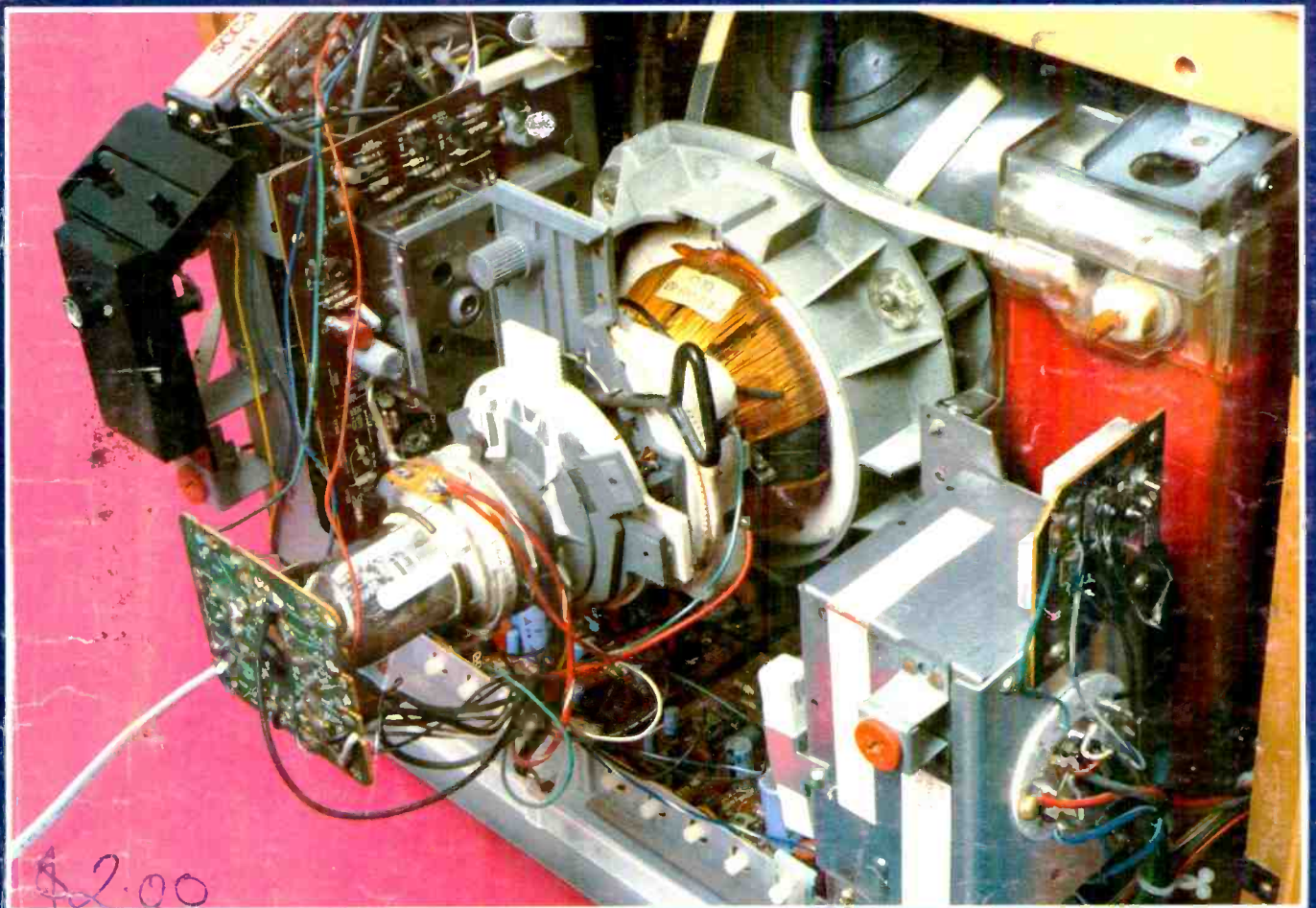


JANUARY 1987

Australia \$2, New Zealand \$2.75 (inc. GST), Malaysia \$5.75 **£1.20**

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS



**Servicing the Sony KV1800UB
TV Behind the Curtain
CRT Heater Voltage Checker
Brushless DC Motors • DX-TV
Designing Active Deflectors
TV Fault Finding • VCR Clinic**

MANOR SUPPLIES

MKV PAL COLOUR
TEST GENERATOR FOR TV & VCR.

TEST
DEMONSTRATIONS
AT 172
WEST END LANE




- ★ 40 different patterns and variations.
 - ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
 - ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
 - ★ Chequerboard.
 - ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
 - ★ Additional video output for CCTV & VCR.
 - ★ Facilities for sound output.
 - ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
 - ★ Mains operated with stabilised power supply.
 - ★ All kits fully guaranteed with back-up service.
 - ★ Also available with VHF Modulator.
- Price of Kit **£70.00**
Case (10"×6"×2 1/4") app. **£8.60**
Optional Sound Module (6MHz or 5.5MHz) **£3.90**
Built & Tested in Case including Sound Module **£108.00**

SPECIAL TEST
REPORT
'TELEVISION'
DEC. 1982

Post/Packing £2.50
Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

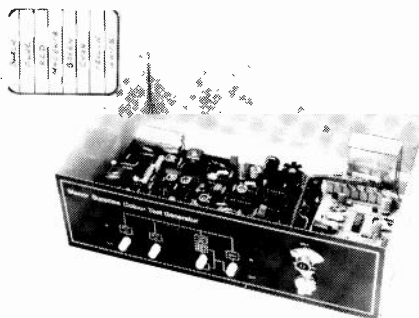

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT
**£30.00. CASE £8.60. BATT HOLDERS £4.20. MAINS
SUPPLY KIT £4.20 (Combined P&P £2.20).**

MK 4 (BATTERY) BUILT & TESTED **£58.00 + £2.20 P & P.**
MK 4 (MAINS) BUILT & TESTED **£68.00 + £2.20 P & P.**
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75.**
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD
VAT
15%

THORN TX9 MK2/3, TX10, teletext
Mullard Decoder panel + Interface **£35.00** p.p. £1.80
THORN TX10, PHILIPS G11 PRESTEL, TELETEX
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£38.00**
p.p. £2.50

EXTERNAL TELETEX ADAPTOR
(RADOFIN) with cable remote control. Fully tested. **£150.00** p.p.
£3.00. Plugs into aerial socket of any T.V.

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF
TECHNICAL EXPERTS

LOPTs, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.
SPECIAL OFFER Mullard/Philips quality UHF modulator (audio & video
input) ex new equipment **£5.00** p.p. £1.00.
PHILIPS G11 6 position touch tune channel selector units **£16.00** p.p. £1.80
(can replace earlier mechanical selector unit).
PHILIPS G11 PANELS (tested).
Power, frame, IF decoder **£18.00** each p.p. £2.00. Scan Panel **£28.00** p.p. £2.80.
PHILIPS G11 PANELS ex rental (untested).
Power, frame, IF, decoder **£10.00** each p.p. £2.00.
PHILIPS HANDSETS Ex rental, Teletext, Untested. KT3, K30, CTX, KT4,
K35 etc. **£3.50** p.p. £1.00.
FERGUSON Video Manual 3V24 **£8.50** p.p. £1.50
COLOUR MANUALS p.p. 50p.
FERGUSON 9800 **£2.00.**
PHILIPS G11 **£3.80**, KT3 **£3.80**, CTX-E **£1.50**, CTX-S **£1.50**.
GRUNDIG incorp. GSC200, 1644GB, 1645GB, 4245GB, 4445GB, 6245GB,
6445GB + CUC95 **£2.00.**
THORN REMOTE CONTROL HANDSETS
TX9 ULTRASONIC (3-button) **£15.00**; TX9, TX10 Infra red **£18.00**; TX9,
TX10 Infra red Teletext **£20.00**, p.p. £1.20.
THORN ex rental handsets untested 9600, TX9, TX10 **£5.00** p.p. £1.00.
TX9 Ultrasonic remote handset transducer **£2.00**, switches 3 for **£1.50** p.p. 50p.
TX9/TX10 Teletext interface panel (1524) **£5.00** p.p. 80p.
THORN TX9 Ultrasonic Remote/Control/Receiver panels. **£8.50** p.p. £1.50.
THORN TX10 Series Facia Control Panel with 8 position Channel Selector
£6.50 p.p. £1.50.
TX9, TX10 Facia control panel incl. infra-red remote control receiver **£8.50**
p.p. £1.80.
TX9, TX10 Remote & tuning control panel (1515) **£10.50** p.p. £1.80.
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V.,
Sound & Vision. **£28.50** p.p. £1.20.
THORN TX9, TX10 Saw Filter IF Panel. **£5.00** p.p. 80p.
PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. £1.00.
PAL ENCODER KIT (RGB to Video) **£18.50** p.p. £1.30.
TELETEX DECODERS New & Tested Mullard VM 6101 **£30.00**, Texas
XM11 **£28.00**, K73 Tested **£30.00**, Untested **£5.00** p.p. £1.60
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync, and UHF
Modulator, Battery Operated, also gives Peak White & Black Levels, can be
used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.90** p.p. £1.40.) ADDI-
TIONAL GREY SCALE Kit **£2.90** p.p. 45p.
UHF SIGNAL STRENGTH METER KIT **£22.00** Alum. Case **£2.90**. De
Luxe Case **£8.60** Built & Tested **£48.00** p.p. £2.30.
CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with
Case, Panel Meter Indicator — can be adapted for latest CRTs **£29.50** p.p. £2.80.
BUSH A823 Convergence, Time Base Panels **£5.00** each, p.p. £1.80.
GEC 2110 PANELS Sound **£2.50** (tested) p.p. 80p.
GEC 20AX Line Time Base **£18.00** p.p. £2.00.
THORN TX9 Panels ex factory for small spares. Includes I.C.s &
Semiconductors e.c. **£3.00** p.p. £1.80.
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains
Transformers. **£10.00** p.p. £3.00.
THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. £3.00.
THORN 8000, 8500, 8800 IF Decoder Panels Tested **£10.00** p.p. £2.30.
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. £1.80.
THORN 9000 IF/Decoder Panels Salvaged. For spares **£2.50** p.p. £1.80.
THORN 9000 Frame Time Base **£8.50** p.p. £1.80.
PHILIPS G8/G9 IF/Decoder Panels for small spares incl ICs **£2.50** p.p. £1.60.
PHILIPS G8 Line Driver Panel incl. Equalizing Coil. **£1.00** p.p. 60p.
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. £1.00.
U321 VARICAP **£7.80** p.p. 80p. Makers Controls PYE CT200 4PSN **£8.50**,
BUSH 4PSN **£4.80**, DECCA 4PSN **£5.80**, 6PSN **£6.80** p.p. 80p. etc.
BUSH "TOUCH TUNE" T20/22 Series Fascia Unit **£7.50** p.p. £1.50.
VARICAP UHF-VHF ELC 2000S **£9.80** p.p. £1.00.
UHF/625 TUNERS, many different types in stock. DECCA Bradford 5
position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. £1.80.
TV SOUND IF Panels **£6.80** p.p. £1.00.
LOPTs New and guar. P/P **£1.50**, Bobbins 80p.
FERG., HMV, MARCONI, ULTRA
1590, 1591, 1612, 1613, 1712, **£4.80**
FERGUSON 3787 (Normend) **£9.80**
THORN 1600, 1615, 690, 1691 **£9.15**
THORN 3000/3500 SCAN, E111 **£6.90**
THORN 8000, 8500, 8800 **£12.80**
THORN 9000 to 9600 **£12.90**
THORN TX9 **£12.50**
THORN TX10 **£16.50**
SPECIAL OFFER
DECCA 1700, 2001, 2020, 2401, 2420 **£3.80**
GEC 2114/Junior FineLine **£2.80**
PHILIPS 320 **£2.80**
RBM A823 **£4.80**
GEC 2028, 2040, 2100 **£4.80**
PYE 691-7 chassis type only **£5.00**
PYE 713, 715, PHILIPS 570, 571 **£6.80**
PHILIPS K9 **£6.80**
R.B.M. T20, T22 **£9.80**
R.B.M. T20, T22 Bobbin **£5.60**
DECCA Bradford (state Mod No) **£8.80**
DECCA 80, 100 **£8.80**
FIDELITY ZX2000, 3000 **£16.00**
GEC 2110 series **£10.60**
ITT CVC 5 to 9, CVC20 **£9.80**
ITT CVC25, CVC30 series **£8.80**
ITT CVC45 **£9.80**
PYE 725 (9P) 731 to 741 **£9.20**
PHILIPS G8 **£8.80**
PHILIPS G9 **£9.80**
PHILIPS G11 **£18.50**
PHILIPS KT3 **£9.80**
PHILIPS K30, K35 **£18.50**
PHILIPS CTX-E **£21.00**
PHILIPS CTX-S **£21.00**

OTHERS AVAILABLE. PRICES ON REQUEST.

TRIPLERS Full range available, Mono & Colour.

SPECIAL OFFER TRIPLERS

THORN 3000/3500 **£2.50**, PYE 725/731 (4 lead) **£1.50** p.p. £1.20.

THORN 1500 5 Stück **£1.50**, 1500 3 Stück **£1.50** p.p. 80p.

6-3V CRT Boost Transformers for Colour & Mono **£5.90** p.p. £1.40.

THORN TX10 focus control **£8.80** p.p. 80p.

CALLERS WELCOME AT SHOP PREMISES

THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED

LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

Goods available if in stock immediately over shop counter (Mail order

between 3 days and 1 week from receipt of order). ADD VAT 15%

Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door


W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford, N. Woolwich)

W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)

Access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT

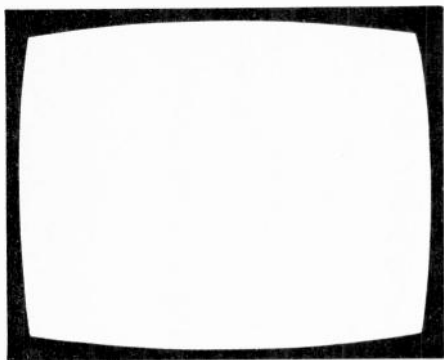PLEASE ADD VAT 15% TO ALL PRICES INCL P+P



TELEVISION

January
1987

Vol. 37, No. 3
Issue 435

On sale December 17th

COPYRIGHT

© IPC Magazines Limited, 1987. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £14 in the UK, £17 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Send orders for binders (£4.50) and indexes (vols. 30-35 only, 75p each) to the Editorial Office, Television, IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS. Prices include VAT and postage. Add 60p for overseas orders.

BACK NUMBERS

Some back issues published during the last six months are available from the Editorial Office at £1.40 inclusive of postage and packing. Address as above.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 157 Leader**
- 158 Servicing the Sony KV1800UB** *David Botto*
One of the older Sony colour sets, but typical of Sony practice at the time, with some unusual features to confuse the unwary.
- 162 Letters**
- 165 TV Behind the Curtain** *Keith Cummins*
A short report on TV conditions in the USSR, based on a recent visit.
- 166 The Operation of Electric Motors, Part 5** *Mike Phelan*
This concluding instalment deals with the brushless d.c. motor which has become very popular for VCR use. Basic drive circuitry and some fault conditions are included.
- 168 Band C Satellite TV Reception** *John Standen*
How North East Satellite Systems managed to resolve low-power 4GHz satellite signals using a modestly sized dish.
- 169 Micro Clinic**
Reports on microcomputer servicing problems from Roger Burchett and Nick Beer.
- 170 Teletopics**
News, comment and developments. Peter Marlow writes on a recent 3D-TV demonstration.
- 172 Tiny Tim's Testing Time** *Les Lawry-Johns*
At last the tide has turned and Tiny Tim is flooded out with faulty sets. Maybe he'll be able to pay some of those bills...
- 174 Low-cost Teletext Decoder, Part 2** *Peter Marlow, B.Sc.(Hons.), C.Eng.*
Constructional details and setting up.
- 177 Next Month in Television**
- 178 TV Fault Finding**
Reports from Richard Roscoe, D. Burke, Michael Dranfield and André N. Smith.
- 180 Long-distance Television** *Roger Bunney*
Reports on DX conditions and reception and news from abroad.
- 182 Practical Active Deflector Systems** *Roger Bunney*
Practical design considerations for active deflector systems.
- 186 Test Report: The Hameg HM204 Oscilloscope** *Eugene Trundle*
A suitable scope for modern high-tech servicing.
- 188 CRT Heater Voltage Checker** *J. LeJeune*
A simple but effective checker to help sort out tube problems.
- 190 VCR Clinic**
Reports from Philip Blundell, Eng. Tech., Les Harris, Christopher Holland, Martin Pomeroy, Roger Burchett, Jim Rainey and Alfred Damp.
- 192 Teletext Developments** *Peter Marlow, B.Sc.(Hons.), C.Eng.*
- 193 Service Bureau**
- 194 Test Case 289**

OUR NEXT ISSUE DATED FEBRUARY WILL
BE PUBLISHED ON JANUARY 21

P. V. TUBES

104 ABBEY STREET, ACCRINGTON, LANCS
 Tel: 0254 36521/32611/390936 BB5 1EE.
 Telex: 635562 Griffin G (For P.V.)

TRADE
 COUNTER
 OPEN
 MON-SAT
 9am-5pm
 (not Wed pm)



HOW TO ORDER
 ADD 87p per order P+P (U.K.).
 Heavier parcels e.g. cable, service
 aids, degaussing coils please allow
 £1.50 P+P (U.K.). Export orders
 charged at cost. First Class Mail is
 used whenever possible. Add 15%
 VAT to total except where it states
 zero rate. Bulkier items will be sent
 by carrier £5.00 + VAT up to 20K
 (except tubes).

THERE IS VAT ON P+P.

BOOKS AND MANUALS ARE ZERO V.A.T.
 Goods are despatched on the day we receive your order. If
 for any reason we are out of stock we will try to inform you
 as quickly as possible. We try our best to give a speedy,
 fair and efficient service. V.A.T. invoice on request. Give
 us a ring - we'll give you service. Please ask if what you
 need is not listed - we will try to help. Prices are subject to
 change without notice. In some cases we may have to
 supply an equivalent.

SEMICONDUCTORS

AC107	35	BC549	10
AC126	34	BC550	10
AC127	34	BC557	9
AC128	34	BC558	9
AC128K	40	BC635	19
AC141	62	BC637	39
AC141K	39	BC639	30
AC176	35	BC640	32
AC176K	35	BCY72	13
AC186	41	BD115	45
AC187	38	BD116A	90
AC187K	46	BD124P	84
AC188	35	BD131	50
AC188K	46	BD132	49
AD143=OC28	82	BD133	60
AD145	85	BD135	38
AD161	54	BD136	38
AD162	54	BD137	35
AD161/62 MP	1.15	BD138	38
AF106	49	BD139	45
AF114	89	BD140	34
AF118	1.20	BD144	1.70
AF121	75	BD150	60
AF124	48	BD159	65
AF125	53	BD160	1.60
AF126	53	BD166	52
AF127	53	BD179	70
AF139	63	BD182	1.20
AF178	1.54	BD183	1.18
AF239	60	BD201	85
AF279	1.56	BD202	91
AL102	4.90	BD203	80
AL106	7.50	BD204	99
AU110	3.01	BD222	46
AU113	5.20	BD223	56
BC107	20	BD225	47
BC108	20	BD232	82
BC109	20	BD233	66
BC114	12	BD234	63
BC115	17	BD235	60
BC116A	35	BD236	65
BC117	30	BD237	57
BC118	24	BD238	65
BC119	36	BD243	85
BC139	32	BD244	85
BC140	32	BD410	79
BC141	30	BD434	74
BC142	30	BD437	86
BC143	31	BD438	94
BC147	13	BD507	69
BC148	9	BD508	80
BC149	12	BD509	86
BC157	16	BD510	86
BC158	16	BD278A	81
BC159	15	BD517	60
BC160	52	BD519	1.08
BC161	32	BD520	75
BC170B	15	BD535	82
BC171	15	BD536	91
BC172	15	BD696A	1.49
BC173	16	BD697	1.63
BC174	10	BD698=702	1.50
BC177	27	BD701	1.63
BC178	26	BD707	1.50
BC182L	15	BDX32	2.10
BC163L	15	BF115	38
BC184L	15	BF117	36
BC186	35	BF125	26
BC187	25	BF127	47
BC204	10	BF154	15
BC208	13	BF158	18
BC209	10	BF160	27
BC212	15	BF167	24
BC212L	15	BF173	37
BC213	15	BF177	52
BC214	15	BF178	46
BC237	14	BF179	42
BC238	14	BF180	39
BC251A	18	BF181	39
BC252	12	BF182	36
BC261	33	BF183	29
BC262	30	BF184	42
BC300	50	BF185	36
BC301	51	BF194/394	16
BC303	33	BF195	16
BC307	20	BF196	16
BC308	25	BF197	16
BC323	99	BF198	18
BC327	22	BF199	21
BC328	18	BF200	35
BC337	18	BF224	40
BC338	18	BF225	20
BC461	42	BF241	38
BC527	35	BF256	60
BC547	13	BF257	34
BC548	13	BF258	34
BCX32 = BC637	39	BF259	34

SEMICONDUCTORS

BF262	84	OT121	1.91
BF263	81	R2008B	1.90
BF271	24	R2010B	1.92
BF273	24	R2265	1.50
BF274	24	R2322	84
BF336	40	R2323	67
BF337	41	R2461	1.60
BF338	41	R2540	3.20
BF355	56	RC4558	2.20
BF362	68	RCA16334	90
BF363	72	RCA16029	1.18
BF371	30	RCA16039	1.18
BF422	34	RCA16092	1.18
BF423	46	RCA16040	96
BF435 = BF491	35	RCA16041	84
BF457	35	RCA16334	90
BF458	43	=0N447	
BF459	58	RCA16335	90
BF460 = BF462	96	=0N448	
BF469	63	RCA16957	2.88
BF470	66	TIC45	90
BF597	16	TIC46	60
BF575	54	TIC47	72
BF578	54	TIL32	65
BF739	27	TIL78	48
BF758	54	TIP29C	43
BF793	30	TIP30A	47
BF840	30	TIP30C	43
BF841	30	TIP31C	55
BF842	42	TIP32C	42
BF843	42	TIP33B	75
BF844	42	TIP34B	1.06
BF845	30	TIP41C	47
BF846	30	TIP42C	50
BF847	46	TIP47	93
BF848	30	TIP120	65
BF849	30	TIP161	2.15
BF850	32	TIP295S	90
BF851	32	TIP305S	63
BF852	32	TIP310	32
BF853	32	TIP315	32
BF854	32	TIP316	32
BF855	32	TIP317	32
BF1000	32	TIP462	32

INTEGRATED CIRCUITS

AN214Q	3.91	SN76115N	2.27
AN240	3.84	SN76131N	2.00
AN318	6.37	SN76226DN	2.72
AN262	4.10	SN76227N	1.18
AN301	5.15	SN76533N	1.70
AN715Q	3.97	SN76533N	2.49
AN6341N	8.97	SN76544N	2.35
AN6344	8.50	SN76660N	80
BA521	2.80	SN76666N	1.82
BA536	3.00	SN76530A	1.47
STK015	1.36	STK015	1.36
STK032 =		STK032	
STK078	13.25	STK078	13.25
STK433	5.65	STK433	5.65
STK435	9.06	STK435	9.06
STK436	6.50	STK436	6.50
STK437	7.85	STK437	7.85
STK439	8.40	STK439	8.40
STK459	9.50		

SONY SPARES

SEMICONDUCTORS

We regret the Sony price increase and apologise for any inconvenience

CV12E		3.07
GH3F		1.82
IS1555		43
U05G	KV1810UB	1.27
V11N	KV1810UB	1.27
10E2		43
SG-264A		5.12
SG629	KV1810UB	8.05
SG-6533	SG613	13.20
BX342	SLC7UB	5.12
CX104A	KV1810UB	6.57
CX136A		9.23
CX143A	SLC5/7UB	6.57
CX186	SLC5UB	9.23
M51231P	KV2200UB	3.07
STK2129		17.27
TCP4621AF6	SLC6UB	13.87
TDA2578A		5.12
UPC 1394C		3.07
UPD 546C107	SLC7UB	22.28
UPD 547C049	SLC7UB	11.18
TL494NC	SLC7UB	6.57
2SA 771		3.04
2SA 835		1.82
2SA 1027R		1.27
2SA 1175	SLC7UB	40
2SB 733		1.18
2SB 740C		1.24
2SB 856		1.84
2SC 403C		32
2SC 867A		3.07
2SC 1034		6.57
2SC 1061=		
2SC1986		3.07
2SC 1114		6.57
2SC 1124		1.27
2SC 1316		8.05
2SC 1362-7		43
2SC 1364		43
2SC 1413A		9.23
2SC 1475		43
2SC 1962		1.84
2SC 2009		32
2SC 2278		1.24
2SC 2335 Kit		11.18
2SC 2369		4.14
2SC 2551		1.27
2SC 2785		43
2SC 3153		5.12
2SD 257		3.04
2SD 725		11.18
2SD 773		32
2SD 774		1.24
2SD 1164		1.27
2SD 1497-02		5.12
2SD 1497-06		5.12

SONY SPARES SUNDRIES

UHF Tuner BT-871 KV1810UB	48.36
Booster Antenna SLC7UB	40.79
RF Modulator SLC6UB	68.30

SONY REMOTE CONTROLS

SLC5UB RM751 (Wired)	29.04
SLC6UB RM-72 (Wired)	22.62
SLC7UB RMT200 (IR)	42.60

SONY SPARES VIDEO/AUDIO HEADS

Ace Assembly SLC7UB	31.33
Ace Assembly SLC6UB	
SYA-676-104-6A rep	49.39
Video Head DR3-21R SLC9UB	49.39
Video Head DSR-35A SLC20/30/40UB	49.39
Video Head DSR-36R SLC5C6/7UB	49.39
Video Head DSR-43A SL8000UB	49.39
Head Record-Playback PP12B-3602C/GEN	17.27
Head Record-Playback 181-3602D TC/HMK	5.35

PHILIPS - KT3

116 40025 Dual Pistor	1.80
124 70347 Main Electrolytic	6.50
101 20519 Focus Control	3.68
140 10161 LOPT	10.06
Tripler	12.50
276 80198 Select Unit 933	16.67
276 10673 On/Off Switch	3.84
212 20648 Lum. Chroma mk.1	31.09
212 37538 Lum. Chroma mk.2	19.80
212 20616 RG3 Panel	12.87
212 20647 Sound Panel	12.50
212 21114 Power Panel	21.48
212 20617 Line Frame Sync 21164	26.49
212 20649 Mains Input Rect. Panel	17.96
212 27445 I.F. Module(V321)	16.60
212 27522 I.F. Module(V321)	16.60
212 20646 I.F. Module(2003)	18.63
212 20796 Sound Panel	10.20

SONY SPARES MECH. REP.

Main Drum Assy SLC7UB	192.52
Rewind Idler Assy SLC7C5UB	5.95
Rewind Idler Assy SLC6UB	4.14
Forward Assy SLC9UB	8.94
Gear Kit SLC9UB	6.57
Guide Pin Kit SLC9UB	6.57
Pinch Roller TC-GEN	1.27
Pinch Roller TC204SD	1.84
Pinch Roller HMK44/44B	1.24
Pinch Roller TCK55	1.24
Cass Holder Assy TCK44	1.84
Lever Fwd. Assy WM2	1.24
F.Wheel Assy WM2	4.13
Limitter Assy SLC7UB	3.07
Idler Assy SLC7UB/C5/3000	1.27
Brake Assy SLC7UB	1.82
Pulley Load Assy SLC6UB	1.27
Thrust Bear. Assy SLC6UB	4.13
Screw Cass. Lid WM2	32
Coil Spring WM2	32
Battery Lid WM2	1.27
Lid Timer SLC7UB	1.27
Threading Gear SLC7UB	1.27
C5 C7 Capstan Motor	44.20
C7 Drive Motor	42.89
Pinch Roller SLC7UB	0.96

SONY SPARES BELTS

Belt WMR2	1.27
Rubber Belt TC-GEN	1.27
Take Up TC-GEN	1.27
Drive TC-GEN	1.27
Midway Pull TC-GEN	1.27
Capstan TC92	1.27
Capstan TC135/136SD	1.27
Flat New TC186SD	1.27
Capstan TC-GEN	1.27
Capstan HST300	1.27
Take Up HMK3000UK	1.27
Capstan HMK3000UK etc	1.27
Fast Fwd-Rwmd VO2850P	3.07
Forward VO2850P	1.82
Motor VP2850P	3.07
Capstan VP2000	5.01
Forward SLC7UB/SLC5UB	43
Capstan SL8000UB	1.27
Capstan SL8000UB	3.07
Extension SL8000UB	1.82
Drum SLC7UB	1.27
Fast Fwd Idler SLC7UB	43
Threading SLC7UB/CS	1.27
Capstan SLC7UB	1.27
Eject SLC7UB	43
Counter SLC7UB	43
Fast Forward SL77ME	1.27
Forward SL8000UB	1.27
Belt SLC6UB	1.27
Fast Forward SLC6UB	1.27
Counter SLC6UB	1.27
Threading SLC6UB	1.27
Relay SLC6UB	1.27
Capstan SLC6UB	1.82
Belt PS-5520 etc	3.18

SONY SPARES SWITCHES

Sw. (Sice wave) Filter KV2022UB	1.27
PB Switch Channel 1820/2 & 1340	18.86
PB Power KV-GEN	3.87
PB Switch SL8000UB	1.27
PB Power KV14/2060UB	4.14
Sw. Power KV2022UB	5.12
Sw. Slide Record SL8000UB	1.27
Sw. Slide Rec/psback SL8000UB	1.82
Sw. On/Off KV1612UB	5.12
Sw. Power KV-GEN	5.12
Button Stop/Eject WM4	1.27
Control Knob SLC7UB	1.27

SONY SPARES MANUALS (Zero VAT)

Instruction Manuals SLC9UB	4.14
SLC6UB Mk 2	2.47
SLC7UB	4.14
SLC5UB	6.84
SL6UB	1.72
KV2212UB/E2 KV2705UB	1.72
Service Manuals HMK3000	8.25
KV1400UB	8.25
SLC7UB	9.23
SLC5UB	9.23
SLC6UB	9.23
SL9UB	9.23
SLC6UB Mk 2	9.23

PHILIPS - CTX

CTX EHT Leads	7.36
---------------	------

PHILIPS K30

101 20561 Focus Unit	3.68
EHT Lead	8.30
140 10283 EPT	17.94
276 17083 On/Off Sw.	2.60
276 10781	
310 27455 Prog. Select	13.10
1002 late 1002 early	
All Gun Switches	70
212 27525 TMS 1000 (1234)	17.03
212 27593 Euro Decoder	46.00
K30/35 Sound	12.50

PHILIPS - K35

K30/35 Sound	12.50
K35 Tuner Drawer	12.50
K35 Remote Txt.	10.00
Slim	26.51

THORN SPARES

SEMI-CONDUCTORS

GL4850	TX10	74
TC45	TX9	1.18
T9222W	TX9	43
T9053/4	TX9	1.10
AN6360	3V29	6.81
HA11741	3V32	23.22
M293	TX9	7.10
M50790SP	3V36	6.98
M54544L	3V32	3.80
MC13002	TX9/TX10	4.98
MC1493	3V36	2.74
MM1219	3V36	11.43
TD1236	TX10	3.44
TD3652	TX10	6.00
TD44500	TX90	5.84
SL490	TX9/TX10/TX100	3.20
DTC144WF	3V36	3.8
R2540	900C	30
TX9M	TX9	3.43
T9051T	TX9	3.8
T6089V	TX9	1.46
T6071	TX100	3.84
T9063V	TX9	1.14
I9064V	TX90	20.78
UPD553C 164	3V29	17.13
UPD7519G 031 036	3V36	11.06
UPD7538C 020	3V38	8.74
10 Volt Tot	3V29	

THORN MANUALS (Zero VAT)

169D/1691	5.60
Service Manual 1790	1.14
Service Manual 9620	10.05
Service Manual 9800	7.54
Service Manual TX9	29.04
Service Manual TX10	40.90
Service Manual TX90	11.30
Service Manual TX100	11.20
Service Manual 3V00	17.50
Service Manual 3V16	26.24
Supplement to 3V00	1.28
Service Manual 3V23	36.82
Service Manual 3V24	28.42
Service Manual 3V29	29.08
Service Manual 3V29	3.28
Service Manual 3V30	17.50
Service Manual 3V30	14.81
Service Manual 3V30	2.85
Service Manual 3V31	25.84
Service Manual 3V35	1.63
Service Manual 3V35/3V36	27.28
Supplement to 3V35 3V38	1.24
Supplement to 3V35/3V39	90
Service Manual 3V42	23.94
Service Manual 3V43	36.72

THORN BELTS/LAMPS

Counter Belt 1	3292/3V00/3V16/3V22	60
Counter Belt 2	3292/3V00/3V16/3V22	1.00
Reel Drive Belt	3292/3V00/3V16/3V22	2.79
Capstan Belt	3292/3V00/3V16/3V22	3.28
Unloading Belt	3292/3V00/3V16/3V22	60
Drum Motor Belt	3292/3V00/3V16/3V22	2.79
Cassette Drive Belt	3V23	60
Capstan Belt	3V23/3V30	60
Loading Belt	3V23/3V30	60
Loading Belt	3V35/3V36/3V38	60
Tape Spool Drive	3V35/3V36/3V38	60
Take Up Clutch	3V29/3V30/3V35/3V36/3V38	60
Capstan Belt	3V35/3V36/3V38	1.21

THORN LAMPS

Tuning Indic Lamp	TX9	62
Cassette Lamp	3292/3V00	3.66
Cassette Lamp	3V15	1.53
Lamp Holder	3V15	60
Cassette Lamp	3V23	1.95
Lamp Holder	3V29/3V30/3V31/3V32	60
Loading Belt	3V29/3V30	1.41
Cassette Lamp	3V31/3V32	1.60

THORN VIDEO HEADS

Upper Drum Assy	3292/3V00	35.94
Upper Drum Assy	3V23	35.94
Upper Drum Assy	3V16/3V23/24/31/35/36/38/39	35.94
Upper Drum Assy	3V29/30	35.94



THORN SUNDRIES

Thom 1591 Speakers sm or lg	6.20
Thom 1500 Controls	59
Thom Focus Control	2.85
GEC	8.40
Thom 9000 Focus Unit	10.20
Thom 8500 Focus Unit	4.75
Thom TX10 Focus Unit	10.20
390K Frame Control	59
470K Line Control	59

V.C.R. MOTORS

Capstan Motor	3292/3V00/3V01/3V16	51.45
Drum Motor	3292/3V00/3V01/3V16/3V22	43.49
SMP Reel Motor	3V23	32.79
Cassette Housing	3V23	10.32
Motor Assembly	3V23	52.81
Capstan Motor	3V23/3V24/3V29/3V30	8.56
Loading Motor	3V29/3V30	27.32
Capstan Motor	3V29/3V30	32.79
Lower Drum Motor	3V29/3V30	78.72
Assembly	3V35/3V36/3V38	6.92
Cassette Motor	3V35/3V36/3V38	5.95
Mode Control Motor	3V35/3V36/3V38	27.93
Capstan Motor	3V35/3V36/3V38	

THORN REMOTE SETS

T723 Non Text	TX10	3767/3788	38.60
T725 Non Text/ Stereo	TX9	20A2/2282/3781/37081/37101/3714/37351/37361/37371	19.40
T731 Text/ Stereo	TX9	20A4/2284/37063/37093/37463/37371	20.01
T736 Text	100	20A3/2203/3795/3796/37003/37103/37353/37363/37373/37953/37963	31.60

THORN SWITCHES

On/Off Switch	TX9	2.98
On/Off Switch	TX10	2.74
Focus Unit	TX10	10.20
8 Way Tuner Unit (Not Drawer)	37141 TX90	12.88
8 Way Tuner Unit (Not Drawer)	37360 TX9	13.50
8 Way Tuner Unit (Not Drawer)	37340/37370 TX9	20.44
Volume Control	38030 1790	1.74
6 Way PB Assy	3722/4722/6722/8000 Thom 9000	20.70

THORN TRANSFORMERS & INDUCTORS

LOPT	9000	25.53
FHT Transformer	TX10	33.80
LOPT	TX10	15.00
LOPT	TX9	23.85
LOPT	38030	6.18
RFI Choke	TX9	3.45
DC Input Choke	TX9	15.36
Mains Transformer	TX90	15.83
Linear Line Coil	TX9	1.77
RFI Input Choke	TX9	60

THORN MECH. REP. VCR

Take Up Rubber Tyre	3V92/3V00	60
Rewind Tyre	3V92/3V00	60
Timing Gear Assembly	3V00	3.97
Audio Control Head		
Sub Assembly	3V92/3V00/3V01/3V16/3V22	42.38
Fast Forward Idler	3292/3V00/3V16	1.63
Fast Forward Tyre	3V00/3V16	60
Pinch Roller	3V92/3V00/3V01/3V16/3V22/3V23	7.30
Stop Solenoid	3V16	10.42
Pause Solenoid	3V16	16.60
Take Up Idler Assmb	3V00 up to Serial No. 19006	7.54
	3V15 up to Serial No. 16509	
	3V22 up to Serial No. 27700	
Take Up Idler Assmb	3V00 19007 onwds	5.28
	3V1	

P.V. TUBES 0254 36521 32611 390936	FIDELITY - Semiconductors ML923 2.21 SL490 1.77 TDA2270 1.65 TDA3330 2.21 TDA8180 3.32 BC638 33 BU5080 1.77 TDA3810 3.86	PLUGS AND SOCKETS Din Plugs 5 pin 180°/240°/360° 20 6 pin 28 7 pin 35 8 pin 56 Chassis Sockets DIN 5 pin din 180°/240°/360° 6 pin din 28 7 pin din 36 8 pin din 36 64 55 Phono plugs 12 2.5mm Jack plugs 11 3.5mm Jack plugs 15 3.5mm Jack Plugs Stereo 36 6.3mm Jack Plugs Stereo 36 Standard mono jack plugs 20 2 pin speaker plugs 10 I.D.C. plugs 36 way conn. 5.90 BNC plugs 1.15 Car aerial plugs 18 FM plugs 25 Coax plugs metal 18 Line connectors 18 Double ended female socket 1.20 In line socket metal 25 Crocodile Clips 25 Phono line socket 20 Phono chassis socket 17 2.5mm jack line socket 17 2.5mm jack chassis socket 14 3.5mm jack line socket 24 3.5mm jack chassis socket 28 3.5mm stereo line jack socket 18 3.5mm stereo jack chassis socket 25 6.3mm stereo jack socket 6.90 IDC 36 way socket 1.30 PL259 with reducer 16	ANTEX C15W Iron 240V 6.20 C240 Element 2.75 Bits 102, 106, 820, 821 1.18 CS17W Iron 240V 6.40 CS240 Element 2.75 Bits 1100, 1101, 1106 1.10 XS25W Iron 240V 6.50 XS240 Element 2.75 Bits 50, 51 1.10 Temp. Controlled 30W Iron CSTC 16.95 40W Iron XSTC 16.95 Unit TCSU1 60.95 Antex Stand 2.10 MLXS Auto Rep. Kit 8.40 Sundry Irons Cordless Gas Iron 15.99 Tips for Gas Iron 5.00 25 Watt Philips 5.50	VIDEO PINCH ROLLERS PANASONIC NV7000 4.35 SANYO VTC9300/VBS7000 4.35 SONY C7J7/SL17 4.35 JVC TCE3V00/01/06/16/23/24 HR220/3320/3330/3600/1100/7700 AKAI VS9700 4.35 HITACHI VT5000 4.35 SHARP VC6300/6500 4.35	
	HITACHI/GEC - Semiconductors LA7801 2.20 STR454 4.73 SN76709 8.00 TDA1870 6.46 TDA4503 5.68 2SD1453 2.20	FIDELITY - Switches On/Off AVS 94 On/Off Remote Cont. 2.43 On/Off CTV 140 94	FIDELITY - Transformers Flyback FCC2015BE up to 22" 12.00 FCC2215AE 22" 12.00 Mod. Kit included	WELLER Heat gun 15.95 Heat gun tips 83 3/16" Iron tips 25W 83	VIDEO BELT KITS VEKIT 1 AKAI JVC VS9300/VS9500/VS9800 HR3300/HR3320/HR3330/HR3360 TCE 8903/3V00/3V16/3V22 3.50 VEKIT 2 PANASONIC NV7000B/NV7200B 3.00 VEKIT 3 SONY SLCS7 3.75 VEKIT 4 SONY SL8000/6500/8600 4.50 VEKIT 5 SONY SL3000UB 4.99 VEKIT 6 PANASONIC NV3000B 3.80 VEKIT 7 SANYO 9900P 4.25 VEKIT 8 PANASONIC NV2000B 3.75 VEKIT 9 PANASONIC NV8600B/8610/V011 4.25 VEKIT 10 TOSHIBA V8600 3.80 VEKIT 11 SHARP VC7300 3.50 VEKIT 12 SHARP VC6300/6600 3.50 VEKIT 13 SANYO VTC5000 1.95 VEKIT 14 SANYO VTC5300 2.50 VEKIT 15 JVC HR7650 2.50 VEKIT 17 SHARP 8300 1.78 VEKIT 18 SHARP 9300 1.47 VEKIT 19 HITACHI VT8000 2.15 VEKIT 20 HITACHI VT11/33 2.15 VEKIT 21 HITACHI 9500 1.12
HITACHI/GEC - VCR GEC V4000H/Hitachi 8000 Belt Counter (122) 47 Belt Loading 43 Belt Take Up 30 Idler FF/Rewind 1.87 Lamp Tape Sensor 1.87 Play Idler Assy V6414221 3.74 Pressure Pinch Roller 5.16 Pulley FF/Rewind V6383531 5.2 Relay 2.54 Upper Cylinder (Head) 35.62	FIDELITY - Remote Controls 4 Button CTV20R/22R/140R 9.95 8 Button F14R 11.05 12 Button IS500 11.05 14 Button AVS 9.95 32 Button Teletext 12.16 Tuner Flap CTV 14S 83 Loudspeaker CM14/CTV140R 1.99	FIDELITY - Service Manuals (Zero VAT) Audio IS500 1.70 IS700 1.70 IS750 1.70 CM14 1.70 TV CTM1400 1.70 F14R 1.70 TV140 1.70 CTV20R 1.70 AVS1600 1.70 AVS2000 1.70 CTV20 1.70 Teletext 1.70 VCR 2 Parts VCR 2.90	SERVISOL Freeze-It 1.20 SUPER SERVISOL 1.04 Foam Cleanser 1.02 Plastics Seal 1.14 Silicone Grease 1.30 Tubes Silicone Grease 1.66 Aero Klene 94 Aero Duster 1.20 Excel Polish 96 Video Head Cleanser 90 Super 40 1.66 Fire Extinguisher 640G 3.08 Heat Sink Compound 25G 1.10 Solder Mop standard reel 77 Hydrosil Silicone Rubber 2.98	VIDEO HEADS Thom New Life Heads (exchange) 21.45 3HSS 30.00 4HSS 31.00 PS38 Sony/Beta 35.00 Philips V2000 64.00 Philips 1700 64.00 Sanyo 9300/9455/9500 53.00 Sanyo 5000/5300/5400 53.00 Toshiba 9600 Upper Ass. 37.00 Toshiba 9600 (Rep. type only) 12.50 Sharp 2300 58.00 Sharp 6300 58.00 Sharp 7300/7700/7750 58.00 Sharp 8300 58.00 Sharp 3300/9700 56.00 Sharp 3HSS (S.P.) 42.00 Hitachi HVI 35.62 Hitachi VT33E/GEC 4004 35.62 Hitachi VT11/GEC 4100 35.62	
HITACHI/GEC - VCR GEC V4000I1/V4002/Hitachi 9300/9500E Belt (259) 47 Belt (289) 47 Belt Take Up (213) 30 Capstan Motor 31.00 Idler FF/Rewind 1.80 Lamp Tape Sensor 91 Play Idler Assy VS861482 3.72 Pulley FF/Rewind V6345173 36 Video Head 35.62 Remote Cont. Handset 9.33	FIDELITY - Service Manuals (Zero VAT) Audio IS500 1.70 IS700 1.70 IS750 1.70 CM14 1.70 TV CTM1400 1.70 F14R 1.70 TV140 1.70 CTV20R 1.70 AVS1600 1.70 AVS2000 1.70 CTV20 1.70 Teletext 1.70 VCR 2 Parts VCR 2.90	NATIONAL PANASONIC SPECIFIC VIDEO VXP0234 Play Idler 1.10 VXP0401 Idler Unit 1.08 VXP0344 Idler Unit 1.22 VXP0331 Idler Unit 1.28 VXP0141 Idler Unit 1.08 VXP0521 Idler Arm Unit 4.08 VXP0325 Loading Gear 1.63 VXP0520 Load Gear Unit 1.36 VDG0016 Action Gear 46 VDG0017 Interm. Gear 43 Direct Rep. Video Bulb 1.00	LEADS 2mm Fly r/m 70 2mm Fly m/f 70 4m Fly r/m 70 10m Fly 1.90 Fig. 8 Mains 62 Computer/TV 97 5 pin din/5 pin din 98 5 pin din/7 pin din 98 TA81 car bat. Thom 1691 4.47 TA51 car bat. Thom 1615 3.66 Car battery Philips 3.95 Scart Leads 2m (open end) 3.50	VIDEO TAPES SKC E60 2.50 E120 2.88 E180 2.80 E240 3.78 L500 2.90 L750 3.40 E30 3.66 E60 4.00 E120 3.24 E180 3.86 L750 5.22 VCC360 6.33 VCC480 7.23 Philips LVC 1700 120 17.50	
HITACHI/GEC - VCR GEC V4004/Hit. VT33E Belt (302) 30 FF/Rewind Arm V6886971 2.90	FIDELITY - Service Manuals (Zero VAT) Audio IS500 1.70 IS700 1.70 IS750 1.70 CM14 1.70 TV CTM1400 1.70 F14R 1.70 TV140 1.70 CTV20R 1.70 AVS1600 1.70 AVS2000 1.70 CTV20 1.70 Teletext 1.70 VCR 2 Parts VCR 2.90	MAINS DROPPERS Decca 20 2.48 Decca 27R/47R 1.40 Decca 56R/68R 1.40 R&M 823 56R/68R 94 PYE 725/31 3R/56R/27R 1.84 PYE 725 56R/27R 1.04 Philips 5050 30R/125R 1.75 Philips 5051 118/14B 1.93 Philips G8 47R 72 Philips G8 2R7/68R 1.38 Thom 1400 1.52 Thom 1500 1.47 Thom 1600 1.77 Thom 3500 1.20 Thom 8000A 1.24 Thom 8500 1.36 Decca 2R5 96 Decca Modulohm 3R9 60	SECURITY EQUIPMENT CONTROL PANELS 1011 Hiclare 29.50 Hiclare Zone Exp. 32.50 BELLS/BOXES "C" Type Dummy 3.25 "C" Type Polyprop. 4.56 "C" Type Translux. 7.80 6" MO Bell 5.52 CABLE 4 Core 5.43 6 Core 7.84 8 Core 10.37 INFRA-RED PASSIVE 6J Mini 26.15 Invader 24.00 SECURITY LIGHTS Floodlights 17.74 Infrascan 62.94 S.A.B. MODULES Castle SAB 13.48 P.A. BUTTONS Stainless 2.88 CONTACTS 5 Term Flush M 59 5 Term Surface M 59 4 Wire Flush M 62 4 Wire Surface M 62 RECHARGE. BATTERIES 12V 1.9A 7.06 EXTERNAL SOUNDERS 712 Ext. Siren 116dB 5.75 1010 Ext. Siren 116dB 5.96 Dinablast 127dB 18.14 PIEZO SOUNDERS SB1 (140dB) 3.37 SB2 (111dB) 5.17 PZ28 (105dB) 4.61 BUZZERS HB722 60 TAMPER SWITCHES 2 1/2 Tamper 50 TRUNKING Fused Spur 2.58 XENON FLASHER 128 PCL 6.75 121 PCL 6.98 JUNCTION BOXES 6 Way 21 8 Way 39 CABLE CLIPS 3.5m 100 96 4.5m 100 1.08 CASSETTE DRIVE BELTS 35mm 35 46mm 37 57mm 37 66mm 39 71mm 43 90mm 43 101mm 59	VIDEO SUNDRIES VHS Drum Motor 25.50 VHS Capstan Motor 25.50 Sanyo 5000 Reel Motor 12.95 Sharp Reel Motor 15.60 Take up Idler Ass./Clutch Ass. VHS (general purpose) 5.95 Thom/JVC etc. Sharp 381/383/386/9100 9300/9500 2.48 Sanyo Hitachi F.F. Idler VT11E/VT33E 6.95 Video Lamps 2.90 Nat. Pan. Bulb VHS 1.00 General Purpose VHS 1.41 3/23 with plug VHS 1.95 Video Care Care Kit Deluxe 5.00 Care Kit 3.58 Universal Copy Kit 5.50 Head Cleaner 90 Beta Eccentricity Gauge 55.00	
HITACHI/GEC - VCR GEC V4100/Hitachi VT11E Belt 312 30 Belt 313 30 Belt 317 47 Belt 318 40 Capstan Motor 22.18 Upper Cylinder (Head) 33.35	FIDELITY - Service Manuals (Zero VAT) Audio IS500 1.70 IS700 1.70 IS750 1.70 CM14 1.70 TV CTM1400 1.70 F14R 1.70 TV140 1.70 CTV20R 1.70 AVS1600 1.70 AVS2000 1.70 CTV20 1.70 Teletext 1.70 VCR 2 Parts VCR 2.90	MOTORS ELECTRONIC/ROTATION CLOCKWISE 6V MD6515 4.95 9V MD9516 4.95 12V MD12517 4.95	EVER READY BATTERIES HP2/R20 82 LR20 Gold 39 R20S Silver 27 R20B Blue 27 RX20 Rechargeable 2.61 HP11/R14 74 LR14 Gold 33 R14S Silver 33 R14B Blue 24 RX14 Rechargeable 2.31 HP7/R6 41 LR6(BC4) Gold 43 LR6(BC2) Gold 41 R6S Silver 21 R6B Blue 15 RX6 Rechargeable 1.31 PP3/6F22 1.53 6LF22 Gold 74 PP3S Silver 54 PP3B Blue 54 RX22 Rechargeable 4.89 HP16/R03 41 LR03 Gold 18 Blue 18 No. 8 Battery 30 5 Hour. Batt. Charger 7.50 Univ. Chg. 9.18	VIDEO HEADS Thom New Life Heads (exchange) 21.45 3HSS 30.00 4HSS 31.00 PS38 Sony/Beta 35.00 Philips V2000 64.00 Philips 1700 64.00 Sanyo 9300/9455/9500 53.00 Sanyo 5000/5300/5400 53.00 Toshiba 9600 Upper Ass. 37.00 Toshiba 9600 (Rep. type only) 12.50 Sharp 2300 58.00 Sharp 6300 58.00 Sharp 7300/7700/7750 58.00 Sharp 8300 58.00 Sharp 3300/9700 56.00 Sharp 3HSS (S.P.) 42.00 Hitachi HVI 35.62 Hitachi VT33E/GEC 4004 35.62 Hitachi VT11/GEC 4100 35.62	
HITACHI - Sundries Vertical Output Module GECC2286, Hit. CPT2226 C2067 C2069 3.98	FIDELITY - Service Manuals (Zero VAT) Audio IS500 1.70 IS700 1.70 IS750 1.70 CM14 1.70 TV CTM1400 1.70 F14R 1.70 TV140 1.70 CTV20R 1.70 AVS1600 1.70 AVS2000 1.70 CTV20 1.70 Teletext 1.70 VCR 2 Parts VCR 2.90	AUDIO HEADS Mono record/playback 4.32 Stereo playback 4.79 Stereo record/playback 4.99 Stereo record/playback (Dolby) 6.90 Mono/stereo erase 2.25	NEW → "C" Type Dummy 3.25 "C" Type Polyprop. 4.56 "C" Type Translux. 7.80 6" MO Bell 5.52 NEW → 4 Core 5.43 6 Core 7.84 8 Core 10.37 NEW → 6J Mini 26.15 Invader 24.00 NEW → Floodlights 17.74 Infrascan 62.94 NEW → Castle SAB 13.48 Stainless 2.88 NEW → 5 Term Flush M 59 5 Term Surface M 59 4 Wire Flush M 62 4 Wire Surface M 62 NEW → 12V 1.9A 7.06 712 Ext. Siren 116dB 5.75 1010 Ext. Siren 116dB 5.96 Dinablast 127dB 18.14 SB1 (140dB) 3.37 SB2 (111dB) 5.17 PZ28 (105dB) 4.61 HB722 60 2 1/2 Tamper 50 Fused Spur 2.58 XENON FLASHER 128 PCL 6.75 121 PCL 6.98 6 Way 21 8 Way 39 3.5m 100 96 4.5m 100 1.08 35mm 35 46mm 37 57mm 37 66mm 39 71mm 43 90mm 43 101mm 59	THORN NEW LIFE EXCHANGE VHS VIDEO HEADS Send us your old VHS head. We'll send an exchange one by return. £21.45 + VAT.	
REPAIR KITS INC. FOIL/BUTTON MATRIX/INSTRUCTIONS No. 8 Battery 8.95 Philips KT3/30 1. without Text 8.95 2. with Text 8.95	REPAIR KITS INC. FOIL/BUTTON MATRIX/INSTRUCTIONS No. 8 Battery 8.95 Philips KT3/30 1. without Text 8.95 2. with Text 8.95	REPAIR KITS INC. FOIL/BUTTON MATRIX/INSTRUCTIONS No. 8 Battery 8.95 Philips KT3/30 1. without Text 8.95 2. with Text 8.95	REPAIR KITS INC. FOIL/BUTTON MATRIX/INSTRUCTIONS No. 8 Battery 8.95 Philips KT3/30 1. without Text 8.95 2. with Text 8.95	REPAIR KITS INC. FOIL/BUTTON MATRIX/INSTRUCTIONS No. 8 Battery 8.95 Philips KT3/30 1. without Text 8.95 2. with Text 8.95	REPAIR KITS INC. FOIL/BUTTON MATRIX/INSTRUCTIONS No. 8 Battery 8.95 Philips KT3/30 1. without Text 8.95 2. with Text 8.95

VARICAP TUNERS	LINE OUTPUT TRANS.	RECTIFIER TRAYS	VALVES CONT'D	EQUIPMENT	AERIAL EQUIPMENT		
ELC1043-05 8.40 ELC104305 Mullard 12.50 ELC1043-06 8.40 ELC2003 15.50 Philips G8/G9 10.50 Philips G11 (U321) 9.90 U322 7.20 U341 9.50 U342 8.50	Philips 320 8.70 Philips 210/300 Mono 10.00 Philips G8 8.75 Philips G9 9.50 Philips KT3 10.06 Philips K30 17.94 Philips TX2 13.39 Philips TX3 14.41 Philips G11 15.58 Pye 713/715 10.00 Pye 725 90° 10.50 Pye 169 10.00 Pye 741 8.20 Bang & Olufsen (2000,3000) 14.69 Decca 80 8.58 Decca 100 8.58 Decca 1700 9.00 Decca 1730 8.58 Decca 2230 8.58 GEC 2110 16.75 GEC 2040 9.50 ITT CVC 1/9 10.85 ITT CVC 25/30/32 8.65 ITT CVC 20 8.60 ITT CVC 45 8.60 R.B.M. T20 13.95 R.B.M. A774 Mono 11.74 R.B.M. BUSHRANGER T16A 10.00 R.B.M. BUSHRANGER T18A 10.00 Thom 3000 EHT 9.95 Thom 3000 SCAN 7.95 Thom 8500 17.50 Thom 3000/3500 Mains 10.00 Thom 1615 12.50 Thom 1691 9.68 Thom TX9 23.85 Thom 9600 21.79	Thorn 1500 3 Stick 5.20 Thorn 1500 5 Stick 5.99 Thorn 3500 7.98 Thorn 8000 6.95 Thorn 8500/8800 7.15 Thorn 9000 7.10 Decca 1730/1830 6.48 Decca 30 5.76 Decca 80 7.12 Decca 100 7.50 Decca/Tatung 120/130 6.50 GEC 2100 7.40 GEC 2200 (20AX) 6.50 GEC 2040/2028 6.60 GEC 2110 (pre or post Jan '77) 7.00 Philips G8 Short Focus Lead 7.12 Philips G8 Long Focus 550 7.12 Philips G9 6.37 Pye/Philips KT3 12.50 Pye 691/3 7.58 Pye 713 4 Lead 8.79 Pye 713 5 Lead 8.79 Pye 731/25 8.75 R.B.M. A823 plug in 7.12 Rank T20/22 7.12 ITT CVC5/9 7.50 ITT CVC20/25/30 (Mullard) 7.12 ITT CVC45 8.65 Universal 6.00 TV 11 Stick 9.00 TV 13 1.26 TV 14 1.29 TV 18 1.10 TV 20 1.43	30FL2 1.70 DY802 98 DY86/7 66 ECC81 1.08 ECC82 98 ECC83 1.07 ECC84 80 ECC85 98 ECC88 1.35 ECF80 1.30 ECF82 88 ECH81 1.60 ECH84 1.66 ECL8C 84 ECL8E 1.30 ECL86 1.99 EF80 95 EF86 2.20 EF183 99 EF184 1.09 EL90 1.75 EL34 3.50 EL84 1.05 EY86/7 68 EY500A 2.25 EZ80/81 56 GY501 1.45 GZ34 3.50 KT66 8.50 KT77 8.50 KT88 (alt type) 12.00 PC92 4.50 PC97 1.65 PCC85 85 PCC805 1.40 PCF80 1.00 PCF200 1.35 PCF800 1.38 PCF801 1.13 PCF802 1.12 PCF805 1.80 PCF808 1.63 PCF200 1.45 PCL82 1.20 PCL84 1.20 PCL805 1.08 PCL86 92 PFL200 1.86 PL36 1.87 PLB1 94 PL95 2.25 6L6GT 2.30 12HG7 3.20 12BH7A 2.75 PL504 1.65 PL508 2.90 PL509/19 5.30 PY86 81 PY500A 2.30 PY800/1 69 UCL81 2.25 UCL83 1.82 UY85 1.35 PL802T 4.00 40K06 5.30 21LU8 3.50 17DW4A 4.00 3AT2B 5.00 12BY7A 3.75	Testlead Set (AVO Type) 2.20 6" pressed bkt. 19.00 Signal injector 4.00 Electric Circuit Tester 1.50 Probes (x10) or (x1) 16.90 Philips Switchable Probes 13.25 Automatic Wire Strippers 6.95 I.C. Inserters 1.18 Micro Pliers 4.20 Micro Cutters 5.00 Trim Tools Metal Ended 3.30 Side Cutters sm. 1.20 Long Nose Pliers 1.20 Sm. Neon Screwdriver 40 Lg. Neon Screwdriver 65 Quick Set Adhesive (Superglue) 75 Dynascan Tube Reju./testers 399.00 467 model inc. bases 299.00 470 model inc. bases 299.00 available without bases for 50.00 less	Chimney Kits 55 6" pressed bkt. 56 6" bkt. with kit 1.75 9" welded bracket 1.35 9" bkt. with kit 2.90 Double bkt. 2.39 Double bkt. with kit 4.75 13.5" Cradle bkt. 2.25 13.5" Cradle with kit 4.25 Std repair pack 1.10 Double repair pack(2) 2.39 Wall Brackets 1.30 6" welded 1.30 12" T&K 3.30 9" welded 1.87 Gutter Brackets 1.00 Clamps 1.68 1" x 1" 25 2" x 2" 19 Universal No. 1 1.02 1" u bolts 20 J bolts 20 1.25" u Bolts 28 2" u bolts 20 UHF TV Aerial 1.62 10 element 2.63 UHF TV Aerial 5.68 3 element 6.50 4 element 9.00 Masts 1.00 3ft crank 7/s shape 1.00 6ft 1" 1.60 10ft 1.5" 5.25 12ft 1.5" 6.00 16ft 2" 9.00 High Gain Aerials 17.10 Antiference X68 17.10 Antiference X614 17.10 Set Top Aerials 2.30 Mercury Olympic 11 2.30 Antiference Super Set Top 5.56 Antiference Carratenna 6.80 Antiference Caravan Kit 11.00 Loop Aerial 1.00 Corner Plates 7 Lashing Wire 7.95 Lead Wall Nails (100) 45 Rawbolts 60 Cable Clips (100) 75 Coax Plugs 12 Line Connectors 18 Attenuators 1.80 Tape 76 Wood Screws 7.92 Mast couplers 8 27Hzc filter 2.10 Outlet Boxes 80 Surface Single 1.10 Surface Twin 95 Y Splitter 85 Flush Single 95 Flush Twin 1.20 TV/FM Flush 1.35 Antiference 2.37 SB11 Splitter 3.94 CS200 Comb/Split 4.66 COB11 Outlet 9.77 CS1000 Comb/Split 11.65 PV1240 power 9.09 UP1300 MHA 14.46 XS2 xtraset 22.50 XS4 6wayDA 43.13 XS4-6 68 Diplexers 2.83 Match Trans 68 Back Boxes 45 Metal Single 80 Metal Double 61 Plastic Single 1.09 Plastic Double 1.09 Budget Range 5.50 Outdoor Splitter 5.50 Mast Head amp. 5.00 Power Unit 5.00		
PUSH BUTTON ASS. Hitachi 4 way 12.36 Philips G8 (early) 17.82 Philips G8 (late) 18.97 Philips G11 Tip Switch unit 26.50 Philips KT3 16.67 Philips KT30 13.22 Pye 6 way (207/715) 18.40 Pye 697 repair kit 10.35 Pye 725-735 (also Red Mk.1) 12.80 Pye 725-735 tuning head with PCB 12.50 Decca 4 way 9.17 Decca 6 way 17.50 Decca 4/6 way conversion kit 15.62 Decca 7 way piano key rep. kit 10.92 GEC 6 way slim 10.29 GEC/ITT/PYE 7 way 16.67 GEC Conversion kit 16.50 Rank AB23 12.36 Rank T20A 11.21 ITT CVC 8/9 (mod) 13.80 ITT 6 way with VCR 8.90 Thom 8500 6.50 GEC 7 B/P c neons 10.50	SWITCHES/ACCESSORIES On/off gen. purpose 4A 80 G8 on/off metal or plastic 1.98 G11 on/off 1.58 G11 on/off remote 1.58 Rotary on/off gen. purpose 66 ITT CVC5 on/off 1.24 ITT mains switch w/ty solenoid 4.50 Rank T20 on/off switch 1.95 Rank mains switch with solenoid 4.50 Thom TX9/10 2.98 Thom 9/10 2.1x 98 GEC 2040 on/off 20 Rank tuner buttons 3 sizes 98 Thom 3500 A1 beam switch 35 GEC 2110 tuner neons 86 GEC 2110 A1 cont. R/B/G 58	FUSES Quick Blow 1.25" 73 100ma 60 250ma-500ma-750ma-1A 60 1.5A-2A-2.5A-3A-5A 90 Quick Blow 20mm 90 100ma, 250ma, 315ma, 500ma, 630ma, 800ma 60 1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A 90 Mains Fuses 1.00 2A, 3A, 5A, 10A, 13A Antisurge 1.25" 1.70 250ma, 500ma, 630ma, 750ma, 850ma 1.70 1A, 1.25A, 1.5A, 2A 2.70 2.5A, 3A, 5A Antisurge 20mm 4.80 80ma 2.50 100ma 2.20 160ma, 200ma 1.30 315ma, 500ma, 630ma, 800ma 1.30 1A, 1.25A, 1.6A, 2A 1.30 400ma, 2.5A, 3.15A, 4A, 5A 1.90	SEND FOR A FULL CATALOGUE includes: ARROW STYLI (special dealer packs) UNISEF AUDIO PRODUCTS (illustrated leaflet available)	THORN NEW LIFE TUBES AVAILABLE AT TRADE COUNTER TURBO RECHARGEABLE Screwdriver Kit 22.71 Drill Kit 25.99 Sold. Iron Kit 16.99 Rep. Tips 2.20 Rep. Bulbs 28	LABGEAR CM7261 Power Unit 12V 11.80 CM7262 Power Unit 12V 12.86 CM7065 VHF/UHF W/B 15.05 CM7066 UHF/WB 14.04 CM7067 UHF MHA A/B/C/D 11.25 CM7068 UHF High Gain A/B/C/D 16.74 CM7253 Behind Set (Mains) 13.65 CM7243 Second Set Amp. 12.72 CM7093 Three Set Amp. 16.03 CM7063 Dist. Amp. VHF/UHF 23.27 CM7108 8+1 Dist. Amp. 43.26 CM9700 27mhz CB Suppressor 4.45 CM6011 Outdoor Splitter 7.83 CM9003 Flush Sing. Outlet 1.95 CM9010 Flush Twin Outlet 2.04 CM9034 UHF Filters A/B/C/D 8.87 CM9033 6way Pass Splitter 9.72 CM7042 TV Games Combiner 3.09 CM9009 Flush TV/FM Outlet 3.20 CM9006 VHF/UHF Diplexer 3.78 CM7122 Televenta Up. VHF to UHF 36.20 CM7122 Televenta Down UHF to VHF 41.81 CM7094 Dist. Amp. UHF/VHF 30.86 CM7271 MHA 15db 8.66 CM7274 4 Way Dist. Amp. 21.45 CM7082 UHF/VHF Dist. Amp. 66.89 CM7080/10 UHF MHA 15.71	EXPORT CS200 Comb/Split 2.94 COB11 Outlet 4.66 CS1000 Comb/Split 11.65 PV1240 power 9.09 UP1300 MHA 14.46 XS2 xtraset 22.50 XS4 6wayDA 43.13 XS4-6 68 Diplexers 2.83 Match Trans 68 Back Boxes 45 Metal Single 80 Metal Double 61 Plastic Single 1.09 Plastic Double 1.09 Budget Range 5.50 Outdoor Splitter 5.50 Mast Head amp. 5.00 Power Unit 5.00	ORDERS WELCOME MULTIMETERS Amprobe Digital Meter AM7 45.00 Amprobe Digital Meter AM9 55.00 Amprobe Volt/Ameter/Ohmmeter RF3 68.00 Philips Meter 2000 R. per V. 20.71
CAPACITORS Main Replacement Electrolytic Pye 169 (200/200/100/32) 3.74 Pye 691/7 (200/300/350V) 2.97 Pye 731 (600/300V) 2.85 Philips G8 (600/300V) 2.53 Philips G9 (600/300V) 2.44 Philips G11 (470/250V) 3.19 Philips G11 (75/1500V) 1.02 Philips 320 (400/400/200V) 3.40 Decca 30 (400/400/350V) 3.74 Decca 80 (400/350V) 4.37 RBM A823 (2500/2500/30V) 1.83 RBM A823 (600/300V) 3.12 RR1 T20A (220/400V) 2.20 ITT CVC 5/9 (200/200/75/25) 3.28 ITT CVC 20 (220/400V) 2.20 GEC 2110 (600/250V) 2.14 GEC 200/200/150/150 2.42 Thom 1500V (150/150/100/300V) 2.42 Thom 1500V (12/300V) 35 Thom 1591/1691 4700/25V 1.32 Thom 3500 (400/40V) 33 Thom 3500 (175/100/100/400/350V) 3.06 Thom 3500 (1000/63V) 95 Thom 3500 (1000/70V) 95 Thom 8000/8500 (2500/2500/63V) 3.72 Thom 8000/8500 (700/250V) 2.55 Thom 8000/8500 (400/350V) 2.82 Thom 9000 (400/400V) 3.61	CMOS 4006B Series 4026 1.99 4068 22 4510 76 4539 77 4007 39 4069 22 4512 72 4541 96 4001 21 4028 64 4070 22 4513 1.88 4543 1.12 4002 21 4029 90 4071 40 4514 1.88 4551 96 4008 72 4032 1.04 4072 22 4515 1.88 4553 2.40 4011 31 4035 88 4073 22 4516 76 4554 1.20 4012 21 4038 99 4075 22 4518 76 4556 48 4013 30 4040 72 4076 80 4519 64 4560 1.76 4014 74 4042 58 4077 22 4520 75 4561 74 4015 76 4043 71 4078 22 4521 1.68 4562 1.20 4016 42 4044 71 4081 22 4522 88 4560 3.60 4017 66 4046 96 4093 49 4523 88 4581 1.84 4018 72 4047 70 4094 1.56 4527 1.20 4528 88 4582 88 4019 70 4049 32 4099 1.20 4528 88 4582 88 4020 76 4050 32 4160 72 4529 1.04 4583 1.00 4021 70 4051 72 4161 72 4530 62 4584 4.00 4022 70 4052 72 4162 72 4531 72 4585 88 4023 21 4053 72 4163 72 4532 1.00 4597 1.84 4024 50 4060 96 4502 72 4536 2.64 4598 2.40 4025 21 4066 43 4505 1.88 4538 1.04 4599 2.00	CALLERS ALWAYS WELCOME	TRADE COUNTER OPEN MON-SAT 9am-5pm	HOW TO ORDER ADD 87p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degaussing coils please allow £1.50 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate. Builder items will be sent by carrier £5.00 + VAT up to 20K (except tubes).	BOOKS AND MANUALS ARE ZERO V.A.T. Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. invoice on request. Give your name and address on all orders - we will give you service, please ask if what you are not listed - we will try to help. Prices are subject to change without notice. In some cases we may have an equivalent.		


P. V. TUBES
104 ABBEY STREET, ACCRINGTON, LANCs
Tel: 0254 36521/32611/390936 BB5 1EE. (not Wed pm)
Telex: 635562 Griffin G (For P.V.) THERE IS VAT ON P+P!

HOW TO INCREASE YOUR PROFITS, IMPROVE YOUR SERVICE, WITH COST EFFECTIVE TEST EQUIPMENT.

HAMEG OSCILLOSCOPES

HAMEG are Europe's top selling **DUAL TRACE OSCILLOSCOPES**. Select from four superb models. All incorporate a useful **COMPONENT TESTER**. Size - all models - 285mm x 145mm x 380mm. Clear display 8 x 10cms. Mains supply 110/125/220/240V AC 50/60Hz. **2 YEAR WARRANTY**

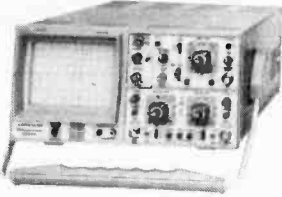HM203-6 20MHz Standard FREE Securicor Delivery



- SPECIFICATION**
- Bandwidth DC-20MHz
 - Sens. Ch1, Ch2, 2mV/cm
 - Delay Line
 - Time Base 0.25s/cm - 20ns/cm
 - Trigger DC-40MHz AC, DC, HF, LF, (TV Frame)
 - Active TV Sinc. Sep.
 - Invert both channels
 - Variable hold-off 10.1
 - Calibrator
 - Plus many more features

Price **£298.00 + £44.70 V.A.T.**
Including two probes


FREE Securicor Delivery HM204-2 20MHz Multi-function



- SPECIFICATION**
- Bandwidth DC-20MHz
 - Sens. Ch1, Ch2, 1mV/cm
 - Delay Line
 - Time Base 1.25s/cm - 10ns/cm
 - Delayed Sweep 100ns - 0.1s
 - Trigger DC-50MHz AC, DC, HF, LF, (TV Frame)
 - Variable hold-off 10.1
 - Overscan LED indicators
 - Calibrator
 - Plus many more features

Price **£402.00 + £60.30 V.A.T.**

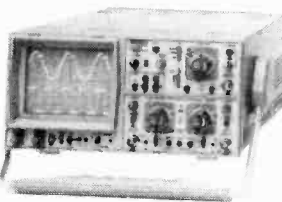HM205 20MHz Digital Storage FREE Securicor Delivery



- SPECIFICATION**
- Digital Storage
 - Analogue Real Time (Same as 203-6)
 - Bandwidth DC-20MHz
 - Sens. Ch1, Ch2, 2mV/cm
 - Trigger DC-40MHz AC, DC, HF, LF, (TV Frame)
 - Active TV Sinc. Sep.
 - 100KHz Sample Rate
 - 2 x 1K Storage
 - Storage Range: 1ms-5s/cm
 - Variable hold-off 10.1
 - Calibrator
 - Plus many more features

Price **£498.00 + £74.70 V.A.T.**
Including two probes


FREE Securicor Delivery HM605 60MHz Multi-function



- SPECIFICATION**
- Bandwidth DC-60MHz
 - Sens. Ch1, Ch2, 1mV/cm
 - Delay Line
 - Delayed Sweep 100ns - 0.1s
 - Trigger DC-80MHz AC, DC, HF, LF, (TV Frame)
 - Variable hold-off 10.1
 - Switchable Calibrator
 - Overscan LED indicators
 - Plus many more features

Price **£567.00 + £85.05 V.A.T.**

B.K.'s CRT TESTER-REJUVENATOR

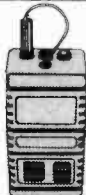

Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

Price **£32.00 + £4.80 V.A.T.**

B.K.'s REVOLUTIONARY DYNAMIC 'LOPT' TESTER

Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC

Price **£25.99 + £3.90 V.A.T.**



THANDAR SC110A PORTABLE OSCILLOSCOPE



- Only 2 1/4" thick
- Fits in a brief case
- Sens. 10mV
- Bandwidth 10MHz
- Full trig. fac. inc. TV frame etc.
- Battery or mains adaptor
- Size 255mm x 148mm x 50mm

Price **£165.00 + £24.75 V.A.T.**

ACCESSORIES
Carry Case £6.25 + £0.93 V.A.T.
Probe £7.50 + £1.30 V.A.T.
Mains Adaptor £7.30 + £1.09 V.A.T.

DIGITAL CAPACITANCE METER



- High Accuracy
- 0.1pf - 2,000µf
- LCD display
- 8 Ranges
- Accuracy ± 0.5%
- Full scale ± 1 digit

Price **£55.00 + £8.25 V.A.T.**


INSULATION TESTER 500V



- Electronic battery operated
- Measuring Voltage 500V DC
- Measuring Range 0-100Mohm
- Centre scale 2Mohm

Price **£65.00 + £9.75 V.A.T.**

LEADER LCT910-A CRT TESTER REJUVENATOR

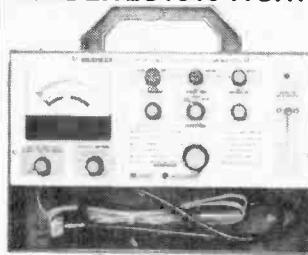

- Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W CRT's.
- Tests for shorts and leakage between electrodes.
 - Tests cathode emission characteristics.
 - Separately checks condition of guns.
 - Removal of shorts and leakage between electrodes.
 - Checks heater warm-up characteristics.
 - Rejuvenation of low emission cathodes with automatic timing.
 - Super rejuvenation with manual control.
 - Complete with tube base adaptors.
 - Size H230mm W330mm D120mm.

Price **£317.00 + £47.55 V.A.T.**

SADELTA FIELD STRENGTH METER TC-402

THE SADELTA FIELD STRENGTH METER TC-402 has been designed to measure the signal levels delivered by the antenna to a TV or FM receiver, in order to test the performance of the antenna and evaluate the best conditions during installation etc. To facilitate measurements, the tuning frequency readout is shown on a digital display.

FEATURES

- Covering FM and all TV bands (UHF/VHF) including CATV freq.
- Digital tuning display (3 digits) for direct frequency readout.
- Accurate 10 turn tuning potentiometer.
- Built-in loudspeaker enables monitoring of sound in AM/FM.
- Meter measurement in voltage and dB from 20µV (26dB/µV).
- Continuity tester 0-500 ohms.
- Fully portable (battery).
- Sturdy carry case.

Price **£249.00 + £37.35 V.A.T.**



SADELTA COLOUR PATTERN GENERATORS

THE SADELTA RANGE OF HAND HELD COLOUR PATTERN GENERATORS is intended for use in production, installation and service of both colour and monochrome TV sets, video and computer monitors. In order to control and adjust the various parameters built-in switchable patterns are provided. The technician has ready access to Laboratory, workshop and field use as the Generator has been designed using the latest micro-technology to achieve truly pocket size instruments. Internal re-chargeable Ni-Cd's. Supplied with 9V power supply charger. Size 131mm x 81mm x 23mm.

T.V. PATTERN GENERATOR PAL MC11B UK

- Band IV (21-34)
- O/Put 10mV into 75ohms
- Band III (5-12)
- Sound output
- PAL I.

Price **£124.95 + £18.74 V.A.T.**

PAL VIDEO COMPOSITE GENERATOR

- PAL B, G.I.
- Audio O/Put 10mV
- O/Put 1V p.p. @ 75ohms

Price **£124.95 + £18.74 V.A.T.**

SECAM VIDEO COMPOSITE GENERATOR


- SECAM B, G, D, K, L.
- Audio O/Put 10mV
- O/Put 1V p.p. @ 75ohms

Price **£124.95 + £18.74 V.A.T.**

R.G.B. PATTERN GENERATOR

- O/Put sigs. Pos. RGB
- O/Put TTL 5V P-P
- Neg. Composite
- Blank Pulse etc. CCIR

Price **£111.95 + £16.79 V.A.T.**

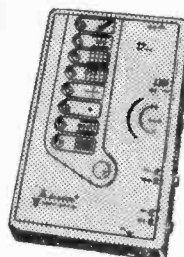

DIGITAL THERMOMETER



- Pocket Size
- -50°C to +750°C
- 1°C Resolution
- 0.5" LCD
- Supplied with thermocouple

Price **£59.50 + £8.92 V.A.T.**

200MHz DIG. FREQ. METER



- Pocket Size
- 8 Dig. LED Display
- Freq. Range 20Hz to 200MHz
- Resolution 0.1Hz
- Sensitivity 10mV

Price **£75.50 + £11.32 V.A.T.**

LEADER HIGH VOLTAGE METERED EHT PROBE

LEADER High Voltage Metered EHT PROBE. Measures up to 40KV DC with safety. Built in meter. Accuracy ± 3%

Price **£45.00 + £6.75 V.A.T.**



DIGITAL CAPACITANCE METER



- High Accuracy
- 0.1pf - 2,000µf
- LCD display
- 8 Ranges
- Accuracy ± 0.5%
- Full scale ± 1 digit

Price **£55.00 + £8.25 V.A.T.**

INSULATION TESTER 500V



- Electronic battery operated
- Measuring Voltage 500V DC
- Measuring Range 0-100Mohm
- Centre scale 2Mohm

Price **£65.00 + £9.75 V.A.T.**



Price **£23.00 + £3.45 V.A.T.** each

The **THANDAR TP1 LOGIC PROBE** and **TP2 LOGIC PULSER** are effective and economical tools for checking both TTL and CMOS circuits. TP1 can show 14 different circuit conditions and can detect pulses down to typically 10ns. TP2 can inject a signal directly into a circuit without damaging sensitive components. Together they can stimulate and monitor responses of components 'in circuit', greatly aiding fault finding.



U.K. POST PAID, export enquiries welcome. Visa/Access or cheque with order, payable B.K. Electronics. Official Orders welcome from Govt. Depts., Colleges, P.L.C.'s etc. Large S.A.E. for technical leaflets of complete range. Delivery normally within seven days.



B. K. ELECTRONICS DEPT. T

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572

HUSSAIN CENTRAL TV LTD

GREAT NEWS

FOR THE SOUTH OF ENGLAND

NEW BRANCH NOW OPEN IN LONDON

RING 01-961 5005

FOR THE BEST DEAL IN TOWN

EXAMPLE

BRAND NEW 14" PORTABLES FROM £100

BRAND NEW MITSUBISHI FST

BRAND NEW 20" GEC

BRAND NEW 16" PANASONIC REMOTE CONTROL

MANY MORE LATE MODEL TVs IN STOCK

BRAND NEW FRONT LOADING REMOTE CONTROL VIDEOS

All TVs have excellent cabinets

VHS: WORKING. Bring your own tape and try them yourself

UNTESTED ELECTRONIC VHS ALSO AVAILABLE

BETAMAX VIDEO'S

ELECTRONIC BETA Full working order. Hundreds in stock.

PLENTY OF UNTESTED BETA

Toshiba 9600, 5470, Sanyo 5000, 5300, 5010, Sony C5, C6, C7.

PLUS MANY MORE MODELS IN STOCK

Prices are subject to 15% VAT and based on quantity

*Deliveries arranged on quantity or call at our branches
for fast and friendly service from the professionals*

SOUTHAMPTON
0703-777254

BIRMINGHAM
021-622 1023
021-622 1517

PRESTON
0772-312101

CHEPSTOW
0291 271000

LINEOUT TRANSFORMERS

Table listing various lineout transformers with part numbers and descriptions.

VALVES

Table listing various valves with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

MIXED DIELECTRIC CAPACITORS

Table listing various mixed dielectric capacitors with part numbers and descriptions.

OTHER RESISTORS

Table listing various other resistors with part numbers and descriptions.

SAFETY CERAMIC STANDARD RANGES

Table listing various safety ceramic standard ranges with part numbers and descriptions.

MAIN DRIPPERS

Table listing various main droppers with part numbers and descriptions.

UNIVERSAL CONVERGENCE POTS

Table listing various universal convergence pots with part numbers and descriptions.

SLIDE CONTROLS

Table listing various slide controls with part numbers and descriptions.

TUNER UNITS

Table listing various tuner units with part numbers and descriptions.

PRESETS

Table listing various presets with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

REMOVAL SPARES

Table listing various removal spares with part numbers and descriptions.

PLEASE ADD £1.25 POST & HANDLING THEN 15% VAT TO TOTAL.

BLACK SALE TV SPARES THE COACH HOUSE, MUXTON LANE, TELFORD, SALOP


FULL LIST OF OVER 3000 ITEMS SENT WITH ORDER OR SEND 9" x 4" SAE. PLEASE USE STOCK NUMBER WHEN ORDERING, OR USE SET MAKER'S PART NUMBER. ACCESS AND VISA ACCEPTED. OFFICIAL ORDERS FROM GOVERNMENT OR SCHOOLS WELCOMED. ALL GOODS ARE STOCK ITEMS.

152 TELEVISION JANUARY 1987

AMSTRAD & Sinclair

Genuine Spares Available from Stock

★ Phone NOW! For free comprehensive Sales Brochures.

 **(0772) 555034**

★ Same Day Despatch, Securicor or First Class Post. ★ Open 8 till 5.30 for your convenience.

★ Answerphone Service out of office hours (0772) 555038. ★ You can confidently call on us for a First Class Spares Service.



Nationwide Spares Distribution
194-200 North Road, Preston, Lancashire,
PR1 1YP England. Telex 677122.

SWITCH ON TO PROFIT!

3,000 TV's and Video's in stock—

Teletext from £50

Thorn 9-6 from £25 working

Working Mechanical Videos from £70.

Non-working Mechanical Videos from £30.

Electronic Videos from £70.

GRADED WHITE GOODS
GAS and ELECTRIC

Built In and Free Standing
COOKERS, MICROWAVES
REFRIGERATION, LAUNDRY
and FIRES

LEADING BRANDS All with manufacturers
GUARANTEE

SUPERB RANGE OF WORKING VIDEOS

ELECTRIC

Incorporating MONITEC NEW 16,000 sq. ft WAREHOUSE

UNIT 22, GREEN ST INDUSTRIAL ESTATE
 GREEN ST, KIDDERMINSTER DY10 1HN
 Telephone (0562) 755526 or 741666

City

MAKE YOUR INTERESTS PAY!!

Train at home for one of these Career Opportunities

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics <input type="checkbox"/>	Radio, Audio & TV Servicing <input type="checkbox"/>
Basic Electronic Engineering (City & Guilds) <input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Car Mechanics <input type="checkbox"/>
Elec. Contracting/Installation <input type="checkbox"/>	Computer Programming <input type="checkbox"/>
GCE over 40 'O' & 'A' level subjects <input type="checkbox"/>	

Name: _____

Address: _____

P. Code _____

ICS

International Correspondence Schools,
 Dept. EGS17, 312/314 High St., Sutton, Surrey
 SM1 1PR. Tel: 01-643 9568 or 041-221 2926
 (both 24 hours).

FIRST IN TUBE REBUILDING TECHNOLOGY

30AX; 540 SERIES!

**REDUCED SERVICING COST,
FIT A DIRECT REPLACEMENT**

**AVAILABLE ONLY FROM CHROMAVAC.
PRE CONVERGED AS ORIGINAL.
EXTERNAL MULTIPOLE UNIT NOT REQUIRED.**

QUALITY REBUILDS

**SPECIAL
OFFERS
ON
INLINE**



Get on the hot-line today!

LOOK! AT NO EXTRA COST **061 681 2959**
30AX PRE CONVERGED

**most types of Inline Re-builds or
new ex-stock** PRICES SUBJECT TO
GLASS EXCHANGE

Delta Rebuilds

Up to 19"	£28
Up to 22"	£30
Up to 26"	£34
110° up to 22"	£34
110° up to 26"	£38
Low focus	+£2
A47 342 New	£28
17FHP New	£30
470EHB New	£30
Delta only. Less 5% 5+	

Inline Rebuilds

Up to 22" .. From	£40
Up to 26" .. From	£45
A56 - 540x	£56
A66 - 540x	£58
Bonded Coil	+£5

ALL SIZES OF NEW AND
REBUILT MONO TUBES
AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

Please enquire types not listed

370 HFB-A37-590	£45	AXT 56-001	£62
370 HUB	£45	660 AB	£65
AXT 37-001	£45	A67-701	£65
420 CSB	£45	670 CZB	£65
420 EDB-A42-590	£45	A66-540 with coil	£85
420 EZB	£45	420FSB	£55
420 ERB	£45		
470 KUB	£50		
510 UFB/A51-590	£55		
510 VSB	£60		
AXT 51-001	£60		
560 DYB-560 DTB	£62		
560 EGB	£62		
560 CGB	£62		
560 DMB	£62		

MIN. CARRIAGE £5
10+ CARRIAGE PAID
TERMS
Cash with order
ALL PRICES
EXCLUSIVE OF VAT

QUANTITY
DISCOUNT
AVAILABLE
Ask for details


★ WE PURCHASE SURPLUS STOCKS
OF INLINE TUBES: ALSO A56/
66 - 510/540 ETC. OLD GLASS.
DELIVERY: By return on all stock items.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMAVAC

CHROMAVAC LTD., PUMP STREET,
HOLLINWOOD, OLDHAM OL9 7LR

Ask for Mr Butterworth ON: 061-681 2959

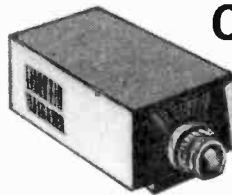

CCTV CAMERAS FROM ONLY £69.50 EACH! PLUS CARRIAGE & VAT

Crofton Electronics are pleased to announce that they are now able to supply C.C.T.V. cameras complete with standard lens, starting at the amazing price of £69.50 + VAT & carriage. Two models are available. Model 'A' incorporates a 3/4" vidicon tube, and model 'B' has a 1" tube. Both models employ vidicon racking thus allowing focusing from a few inches to infinity. Both models also have a standard 'C' mount and thus will accept a wide range of different lenses. Model 'B' can be driven from external sync pulses and produce a composite/non composite output. Though not new each camera has been completely refurbished to a high standard in our own workshops and comes ready to work with any suitable monitor, digitiser, VCR etc. (may also be used with a domestic TV set by the addition of a simple modulator - kit available.) From an input of 240v ac, the cameras produce an output of 1 volt peak-peak and are equipped with standard tripod mounting bushes. With applications as diverse as education, amateur dramatics and shop/industrial/domestic/farming security systems, demand is sure to be high and orders will be dealt with in strict rotation.

Model 'A' all inclusive price £85.10 subject to availability.

Model 'B' all inclusive price £97.75 subject to availability.

DON'T DELAY - PLACE YOUR ORDER TODAY!

Also available on special offer - Brand New Time Date Generators at the amazing price of £132 inclusive. Normal price £477. These generators are mains driven and accept normal composite video in. They produce video out with time/date/day/month/year added to the signal, and with the option of normal or inverse video of the added data. The position on the screen of the added data is adjustable. Switchable character size is also provided for, on an internal DIL switch. A REAL MUST FOR SECURITY APPLICATIONS WHEN RECORDING. There are only a limited number of these, so hurry to avoid disappointment. Orders will be dealt with on a strictly first come first served basis.

We also have for disposal a whole host of used items such as cooling fans, power supplies etc - so please ask for list. Our complete range of products include plugs, sockets and cables, TV aerial accessories, monitors, computer products, security telephones and door entry/alarm equipment, and surveillance and counter surveillance equipment. If you would like all our cats please send a 40p SAE.

MOST MAJOR CREDIT CARDS ACCEPTED

CROFTON ELECTRONICS

☎ 05448 557

'KINGSHILL', NEXTEND, LYONSHALL, HEREFORDSHIRE HR5 3HZ

TELEPART

Telegen-1

PRICE £18.35 (Inc. VAT)

- * EXCEPTIONALLY LIGHT AND DURABLE
- * POCKET SIZE FOR OUTSIDE SERVICE
- * PP3 BATTERY POWER SOURCE
- * FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV
- * CROSSHATCH GRID * DOT MATRIX
- * WHITE RASTER
- * HORIZONTALS * VERTICLES
- * 3.5mm JACK SOCKET FOR OPTIONAL P.S.U.



A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

PRICE £34.45 (Inc. VAT)

- * EXCEPTIONALLY LIGHT & DURABLE
- * COMPACT 10 x 12 x 4.5 cms
- * RED RASTER * GREEN RASTER
- * BLUE RASTER
- * COLOUR BARS
- * 3.5 mm JACK SOCKET FOR P.S.U.
- * PROVIDES UHF SIGNAL APPROX. CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.
PRICE £4.55 (Inc. VAT)

ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)
All goods should be delivered within 4 working days.

**32 TEMPLE STREET, WOLVERHAMPTON
WV2 4AN. TEL: (0902) 29022
(U.K. ONLY)**



£1 BAKERS DOZEN PACKS

Price per pack is £1.00.* Order 12 you may choose another free. Items marked (sh) are not new but guaranteed ok.

1. 5-13 amp ring main junction boxes
2. 5-13 amp ring main spur boxes
4. 5-surface mounting light switches
5. 3-electrical switches intermediate type, will also replace 1 or 2 way switches, white flush mounting
7. 4-in flex line switches with neon
9. 2-mains transformers with 6V 1A secondaries
10. 2-mains transformers with 12V 1/2A secondaries
11. 1-extension speaker cabinet for 6 1/2" speaker
13. 12-glass reed switches
17. 2-ultrasonic transmitters and 2 receivers with circuit
19. 2-light dependent resistors
25. 4-wafer switches - 6p 2 way, 4p 3 way, 2p 6 way, 2p 5 way, 1p 12 way small one hold fixing and good length 1/4 spindle your choice
28. 1-6 digit counter mains voltage
30. 2-Nicad battery chargers
31. 1-key switch with key
33. 2-aerosol cans of ICI Dry Lubricant
34. 48-2 metre lengths colour-coded connecting wire
39. 1-long and medium wave tuner kit
41. 8-rocker switch 10 amp mains SPST
45. 1-24 hour time switch mains operated
49. 10-neon valves - make good night lights
50. 2-12V DC or 24V AC, 3 CO relays
51. 1-12V 2 CO miniature relay very sensitive
52. 1-12V 4 CO miniature relay
54. 10-rows of 32 gold plated IC sockets (total 320 sockets)
55. 1-locking mechanism with 2 keys
56. 1-miniature unselector with circuit for electric jigsaw puzzle
60. 5-ferite rods 4" x 5/16" diameter aerials
61. 1-Mullard thyristor trigger module
66. 1-magnetic brake - stops rotation instantly
67. 1-low pressure 3 level switch can be mouth operated
69. 2-25 watt pots 8 ohm
70. 2-25 watt pots 1000 ohm
71. 4-wire wound pots - 18, 33, 50 and 100 ohm your choice
77. 1-time reminder adjustable 1-60 mins clockwork
85. 1-mains shaped pole motor 3/4" stack - 1/4 shaft
89. 1-mains motor with gear box 1 rev per 24 hours
91. 2-mains motors with gear box 16 rpm
96. 1-thermostat for fridge
98. 1-motorised stud switch (s.h.)
101. 1-2 1/2 hours delay switch
102. mains PSU 9V
103. 1-mains power supply unit - 6V DC
104. 1-mains power supply unit - 4 1/2V DC
107. 1-5" speaker size radio cabinet with handle
111. 2-musical boxes (less keys)
112. 1-heating pad 200 watts mains
114. 1-1W amplifier Mullard 1172
115. 1-wall mounting thermostat 24V
118. 1-leak effect extension 5" speaker cabinet
120. 2-p.c. boards with 2 amp full wave and 17 other recs
121. 4-push push switches for table lamps etc.
122. 10-mtrs twin screened flex white p.v.c. outer
124. 25-clear plastic lenses 1 3/4" diameter
127. 4-pilot bulb lamp metal clip on type
128. 10-very fine drills for pcbs etc.
129. 4-extra thin screw drivers for instruments
132. 2-plastic boxes with windows, ideal for interrupted beam switch
134. 10-model aircraft motor - require no on/off switch, just spin to start
142. 10-4BA spanners 1 end open, other end closed
145. 2-4 reed relay kits 3V coil normally open or c/o if magnets added
146. 20-pilot bulbs 6.5V 3A Philips
154. 1-12V drip proof relay - ideal for car jobs
155. 3-varicap push button tuners with knobs
169. 4-short wave air spaced trimmers 2-30f
172. 10-12V 6W bulbs Philips m.e.s.
178. 3-oblong amber indicators with filiputs 12V
180. 6-round amber indicators with neons 240V
181. 100-p.v.c. grommets 3/8 hole size
182. 1-short wave tuning condenser 50 pf with 1/4" spindle
184. 1-three gang tuning condenser each section 500 pf with trimmers and good length 1/4" spindle
188. 1-plastic box sloping metal front, 16 x 95mm average depth 45mm
193. 6-5 amp 3 pin flush sockets brown
195. 5-B.C. lampholders brown bakelite threaded entry
196. 1-in flex simmerstat for electric blanket soldering iron etc.
197. 2-thermostats, spindle setting - adjustable range for ovens etc.
199. 1-mains operated solenoid with plunger 1" travel
200. 1-10 digit switch pad for telephones etc.
201. 8-computer keyboard switches with knobs, pcb or vero mounting
211. 1-electric clock mains driven, always right time - not cased
216. 1-stereo pre-amp Mullard EP9001
232. 2-12V solenoids, small with plunger
236. 1-mains transformer 9V 1 amp secondary C core construction
241. 1-car door speaker (very flat) 6 1/2" 15 ohm made for Radiomobile
241. 2-speakers 6" x 4" 4 ohm 5 watt made for Radiomobile
243. 2-speakers 6" x 4" 16 ohm 5 watt made for Radiomobile
244. 1-mains motor with gear-box very small, toothed output 1 rpm
245. 4-standard size pots, 1/2 meg with dp switch
249. 1-13A switched socket on double plate with fused spur for water heater etc.
266. 2-mains transformers 9V 1/2A secondary split primary so ok also for 115V
267. 1-mains transformers 15V 1A secondary p.c.b. mounting
291. 1-ten turns 3 watt pot 1/4 spindle 100 ohm
296. 3-car cigar lighter socket plugs
298. 2-15 amp round pin plugs brown bakelite
300. 1-mains solenoid with plunger compact type
301. 10-ceramic magnets Mullard 1" x 3/8 x 5/16
303. 1-12 pole 3 way ceramic wave charge switch
304. 1-stereo amp 2W per channel
305. 1-tubular dynamic microphone with desk rest
308. 1-T.V. turret tube (black & white T.V.)
310. 2-oven thermostats
313. 5-sub miniature micro switches
316. 1-round pin kettle plug with moulded on lead

MULLARD UNILEX AMPLIFIERS

We are probably the only firm in the country with these now in stock. Although only four watts per channel, these give superb reproduction. We now offer the 4 Mullard modules - i.e. Mains power unit (EP9002) Pre amp module (EP9001) and two amplifier modules (EP9000) all for £6.00 plus £2 postage. For prices of modules bought separately see TWO POUNDERS.

CAR STARTER/CHARGER KIT

Flat Battery! Don't worry you will start your car in a few minutes with this unit - 250 watt transformer 20 amp rectifiers, all parts with data £15 case £4 p&p £2.




Ex-Electricity Board. Guaranteed 12 months.

VENNER TIME SWITCH

Mains operated with 20 amp switch. One on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95 without case, metal case - £2.95 adaptor kit to convert this into a normal 24hr time switch but with the added advantage of up to 12 on/off per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

SOUND TO LIGHT UNIT

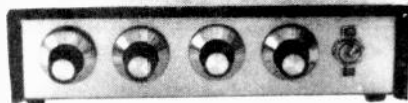

Complete kit of parts of a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form.

12 volt MOTOR BY SMITHS

Made for use in cars, etc. These are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle - 1/10 hp £3.45 1/8 hp £5.75. 1/6 hp £7.50

25A ELECTRICAL PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. A beautiful unit at £2.50

THIS MONTH'S SNIP

400 Watt Mains Isolation Transformer 230 volts in 230 volts out. Supplementary 10 volt winding for voltage adjustments. Toroidal construction makes it most compact. Regular price £40. Our price only £10.00 + £2 post.

MAKING SUBNEDS?

CHOKO AND STARTER for 6" 100uVa tube £2, post £1 for 1 or 50p each in quantity. TUBE HOLDERS Canopy type spring loaded, 4 pairs for £1, 100 pairs £20, 1,000 pairs £150, post paid.

TANGENTIAL HEATERS

We again have very good stocks of these quiet running instant heat units. They require only a simple case, or could easily be fitted into the bottom of a kitchen unit or book case etc. At present we have stocks of 1.2kw, 2kw, 2.5kw, and 3kw. Prices are £5 each for the first 3, and £6.95 for the 3k. Add post £1.50 per heater if not collecting. CONTROL SWITCH snabbing full heat, half heat or cold blow, with connection diagram. 50p for 2kw, 75p for 3kw.

FANS & BLOWERS

Woods extractors 5" £5 + £1.25 post. 6" £6 + £1.50 post 4" x 4" Muffin equipment cooling fan 115V £2.00 4" x 4" Muffin equipment cooling fan 230/240V £5 5" Plannair extractor £3.50 9" Extractor or blower 115V supplied with 230 to 115V adaptor £9.50 + £2 post. All above are ex computers but guaranteed 12 months. 10" x 3" Tangential Blower. New. Very quiet - supplied with 230 to 115V adaptor on use two in series to give long blow £2.00 + £1.50 post or £4.00 + £2.00 post for two.

IONISER KIT


Freshen your home, office, shop, work room etc. with a negative ION generator. Makes you feel better and work harder - a complete mains operated kit, case included. £11.95 plus £2 D0 post.

TELEPHONE BITS

Master sockets (has surge arrester - ringing condenser etc) and takes B.T. plug £3.95 Extension socket £2.95 Dual adaptors (2 from one socket) £3.95 Cord terminating with B.T. plug 3 metres £2.95 Kit for converting old entry terminal box to new B.T. master socket, complete with 4 core cable, cable clips and 2 BT extension sockets £11.50

MINI MONO AMP

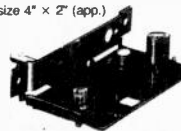on p.c.b. size 4" x 2" (app.) Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new. perfect condition, offered at the very low price of £1.50 each, or 13 for £12.00



J & N BULL ELECTRICAL (T)

250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 50T MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £20 add £1 service charge. Monthly account orders accepted from schools and public companies. Access & B/C card orders accepted. Brighton 0273 734648. Bulk orders: write for quote.

OVER 400 GIFTS YOU CAN CHOOSE FROM

There is a total of over 400 packs in our Baker's dozen range and you become entitled to a large free gift with each dozen pounds you spend on these packs. A classified list of these packs and our latest "News Letter" will be enclosed with your goods, and you will automatically receive our next news letter.

£2 POUNDERS*

- 2P2 - Wall mounting thermostal, high precision with mercury switch and thermometer
- 2P3 - Variable and reversible 8-12V psu for model control
- 2P4 - 24 volt psu with separate channels for stereo made for Mullard UNILEX
- 2P6 - 100W mains to 115V auto-transformer with voltage tappings
- 2P8 - Mains motor with gear box and variable speed selector. Series wound so suitable for further speed control
- 2P9 - Time and set switch. Boxed, glass fronted and with knobs. Controls up to 15 amps. ideal for program electric heaters
- 2P10 - 12 volt 5 amp mains transformer - low volt winding on separate bobbin and easy to remove to convert to lower voltages for higher currents
- 2P12 - Disc or Tape precision motor - has balanced rotor and is reversible 230V mains operator 1500 rpm
- 2P14 - Mug Stop kit - when thrown emits piercing swawk
- 2P15 - Interrupted Beam kit for burglar alarms, counters, etc.
- 2P17 - 2 rev pr minute mains driven motor with gear box, ideal to operate mirror ball
- 2P18 - Liquidgas shut off valve mains solenoid operated
- 2P19 - Disco switch-motor drives 6 or more 10 amp change over micro switches supplied ready for mains operation
- 2P20 - 20 metres extension lead, 2 core - ideal most Black and Decker garden tools etc.
- 2P21 - 10 watt amplifier, Mullard module reference 1173
- 2P22 - Motor driven switch 20 secs on or off after 250V
- 2P24 - Clockwork operated 12 hour switch 15A 250V with clutch
- 2P26 - Counter resettable mains operated 3 digit
- 2P27 - Goodmans Speaker 6 inch round 8 ohm 12 watt
- 2P28 - Drill Pump - always useful couples to any make portable drill
- 2P31 - 4 metres 98 way interconnecting wire easy to strip
- 2P32 - Hot Wire amp meter - 4 1/2 round surface mounting 0-10A - old but working and definitely a bit of history
- 2P34 - Solenoid Air Valve mains operated
- 2P38 - 200 F.P.M. Geared Mains Motor 1" stack quite powerful, definitely large enough to drive a rotating aerial or a tumbler for polishing stones etc.
- 2P43 - Small type blower or extractor fan, motor inset so very compact. 230V
- 2P46 - Our famous drill control kit complete and with prepared case
- 2P47 - Telephone ringing unit reduces mains to 50 volts and changes frequency from 50 hz to 25 hz to give right ringing tone
- 2P49 - Fire Alarm break glass switch in heavy cast case
- 2P51 - Stereo Headphone amplifier, with pre-amp
- 2P55 - Mains motor, extra powerful has 1 1/2" stack and good length of spindle
- 2P62 - 1 pair Goodmans 15 ohm speakers for Unilox
- 2P64 - 1 five bladed fan 6 1/2" with mains motor
- 2P66 - 1 2kw tangential heater 115v easily convertible for 230V
- 2P67 - 1 12v-0-12v 2 amp mains transformer
- 2P68 - 1 15v-0-15v 2 amp mains transformer
- 2P69 - 1 250v-0-250v 60 mA & 6.3v 5A mains transformer + E.I. post
- 2P70 - 1 E.M.I. tape motor 2 speed and reversible
- 2P72 - 1 115v Muffin fan 4" x 4" approx. ex computer
- 2P75 - 1 2 hour timer, plugs into 13A socket
- 2P82 - 9v-0-9v 2 amp mains transformer
- 2P84 - Modern board with press keys for telephone redialler
- 2P85 - 20v-0-20v 1/2A Mains transformer
- 2P88 - Sangamo 24 hr time switch 20 amp S.H.
- 2P89 - 120 min. time switch with knob
- 2P90 - 90 min. time switch with edgewise engraved controller
- 2P95 - 13A socket on satin chrome plate with superior G.E.C.
- 2P97 - mains transformer 24V 2A upright mounting
- 2P98 - 20m 4 core telephone cable, white outer
- 2P99 - 500 hardened pin type staples for telephone cable
- 2P101 - mains transformer 15v 4A upright mounting
- 2P105 - capillary type thermostat adjustable for air temperatures with 10A switch
- 2P107 - membrane keyboard, telephone type superior plug in type
- 2P108 - mains motor with gear box giving 110rpm
- 2P109 - 5" wide black adhesive pvc tape 33m, add £1 post if not collecting
- 2P111 - ITT line output unit
- 2P112 - 6 volt 200MA Voltage regulated PSU for 13 amp socket
- 2P113 - 9 volt 200MA Voltage regulated PSU for 13 amp socket
- 2P114 - 12 volt 200MA Voltage regulated PSU for 13 amp socket
- 2P116 - FM front end with tuning capacitor and F.M. circuitry
- 2P118 - 30rpm mains motor with gearbox
- 2P119 - Under carpet switch mat for burglar alarm etc.

LIGHT CHASER KIT

Motor driven switch bank with connection diagram, used in connection with 4 sets of X-mas lights makes a very eye catching display for home, shop or disco, only £5 ref 5P56

£5 POUNDERS*

- SP1 - 12 volt submersible pump complete with a tap which when pushed back switches off, an ideal caravan unit.
- SP2 - Sound to light kit complete in case suitable for up to 750 watts.
- SP3 - Silent sentinel ultra sonic transmitter and receive kit, complete
- SP5 - 250 watt isolating transformer to make your service bench safe, has voltage add, taps, also as it has a 115v tapping it can be used to safely operate American or other 115v equipment which is often only insulated to 115V. Please add £3 postage if you can't collect as this is a heavy item.
- SP6 - 12V alarm bell with heavy 6" gong, suitable for outside if protected from direct rainfall. Ex. GPO but in perfect order and guaranteed.
- SP15 - Unselector 5 pole 25 watt 50 volt coil
- SP18 - motor driven water pump as fitted to many washing machines
- SP20 - 2 kils. matchbox size, surveillance transmitter and FM receiver
- SP23 - miniature (appr. 2 1/2" wide) tangential blow heater. 1.2kw
- SP24 - 1/4hp motor, ex computer, 230v, mains operation 1450rpm. If not collect add £3 post
- SP25 - special effects lighting switch. Up to 6 channels of lamps can be on or off for varying time periods
- SP27 - cartridge player 12v, has high quality stereo amplifier
- SP28 - gear pump, mains motor driven with inlet and outlet pipe connectors
- SP32 - large mains operated push or pull solenoid. Heavy so add £1.50 post
- SP34 - 24v 5A toroidal mains transformer
- SP35 - modern board from telephone auto dialler, complete with keypad and all IC's
- SP37 - 24 hour time switch, 2 on/off and clockwork reserve, ex. Elec Board loading up to 50A. Add £1 post
- SP41 - 5" extractor fan, very quiet runner sh, gntd 12 mths.
- SP45 - pack of 6 cooker clock switches
- SP48 - telephone extension bell in black case, ex-GPO
- SP50 - box of 20 infra red quartz glass enclosed 360w heating elements
- SP51 - 200w auto transformer 230v to 115v toroidal
- SP52 - mains transformer 26v 10A upright mounting, add £2 post
- SP54 - mains motor with gear box, final speed 5rpm
- SP58 - Amstrad stereo tuner FM and LM and S. AM
- SP60 - DC Muffin type fan 18w to 27v, only 3w
- SP61 - drill pump mounted on frame, couples to mains motor
- SP62 - 2 1/2kw tangential blow heater, add £1 50 post if not collecting
- FP69 - Fluorescent light box for viewing PCB's or can be used for shop window sign



1986 CATALOGUE available - range of components greatly increased - over 136 pages fully illustrated. Price £1.00 per copy (free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelope. Order your copy now - will be sent within 7 days.

JANUARY SPECIAL



£2.99 CIGAR LIGHTER PLUG

Useful plug with lead & multi-plug plug; 2.5 & 3.5 Jack & 2.1 D.C. Max. Current 2A. Fuse built into plug.

FULL RANGE OF SPARES FOR

AMSTRAD FERGUSON

SANYO SHARP SONY

Send large S.A.E. for complete lists which will be available as from 1/1/1987. Please bear with us over delay.

TOOLS

TWEEZERS

- Blunt 0.85
- Pointed 0.95
- Spring Loaded 1.90
- Inspection Mirror 3.75

DRILLS

- Reliant 12v 7.25
- Titan 12v 11.20
- Saturn-Mains 12.25

Full range of high speed twist drills for metal and drill bits.

INTEGRATED CIRCUITS (£) EACH


709C	0.35	TDA2140	2.90
741	0.25	TDA2160	2.50
AN214Q	3.80	TDA2522	2.75
AN240P	3.42	TDA2530	2.20
BT1621B	1.98	TDA2532	2.20
CA301AT	6.80	TDA2560	3.20
CA358	0.66	UPC5756Z	1.45
CA810QM	1.20	UPC1350C	4.05
CA3020	2.10	UPC1156H	4.05
CA3065	1.00	UPC1218H	1.80
CA3088E	0.85	UPC1356C2	3.00
CA3140E	0.35	UPC2002H	2.78
HA1366WR	1.59		
LA4422	3.20		
LC7131	4.90		
LM324N	0.45		
LM3908-N	1.15		
LM3908N4-P	1.80		
LM1011N	3.00		
LM1458N	1.75		
LM3900N	0.85		
M51513L	1.90		
M51515L	2.98		
MC1307P	1.60		
MC1327P	1.60		
MC1330P	1.50		
ML232B	2.10		
ML237B	2.30		
NE555	0.25		
SN754025	6.00		
SN76226DN	1.10		
SN76227N	1.10		
SN76533N	1.70		
STK015	13.20		
STK032	6.00		
STK078	13.00		
STK435	8.99		
TA7146P	4.80		
TA7203P	2.50		
TA7204P	2.50		
TA7205AP	1.80		
TA7222P	2.32		
TAA550	0.50		
TAA611A12	4.50		
TAA621AX1	4.50		
TAD100	2.90		
TD120A	1.20		
AS/SB/TAU	0.80		
TD120B	1.30		
SAVSAUQ	1.30		
TBA520	1.50		
TBA530	1.20		
TBA540	1.64		
TDA560C	1.50		
TBA8105	1.20		
TBA950/2A	3.05		
TCA2705A	4.02		
TD1000A	2.32		
TD1003A	2.50		
TD1006A	2.45		
TD1035S	4.50		
TD1170S	1.99		
TD1352A	1.80		
TD2002	1.80		
TD2020	4.06		
TD2030	1.80		

TRANSISTORS - DIODES

Type	Price (£)	Type	Price (£)
AC127	0.28	BC118	0.16
AC128	0.30	BC119	0.28
AC129K	0.34	BC125	0.28
AC141	0.58	BC140	0.27
AC141K	0.38	BC141	0.24
AC142	0.56	BC142	0.24
AC142K	0.38	BC143	0.26
AC151	0.45	BC147	0.18
AC152	0.45	BC147B	0.14
AC153	0.57	BC148	0.10
AC153K	0.46	BC148B	0.12
AC176	0.30	BC149	0.10
AC176K	0.38	BC149C	0.14
AC187	0.28	BC177	0.10
AC187K	0.38	BC158	0.26
AC188	0.28	BC159	0.12
AC188K	0.38	B/C	0.14
ACY22	1.50	BC160	0.30
AD142	0.88	BC161	0.30
AD143	1.10	BC168B	0.20
AD149	0.72	BC169C	0.12
AD161/162	1.20	BC170A/B/C	0.16
AD162	0.52	BC171A/B	0.10
AF114	1.20	BC172/B/C	0.12
AF115	2.10	BC177A/B/C	0.24
AF121	0.56	BC102A/B	0.12
AF124	0.42	LA LD LC	0.10
AF125	0.58	BC183A/B/C	0.10
AF126	0.58	BC183L	0.10
AF127	0.38	LA LB LC	0.10
AF139	0.40	BC184	0.10
AF178	2.28	A B CL LC LB	0.10
AF239	0.50	BC207	0.15
AF279S	1.40	BC212A/B/C	0.10
AL100	5.40	BC212L	0.09
AL102	4.40	LB LC	0.10
AS700	5.20	BC213A/B/C	0.10
ASZ17	2.00	BC213L	0.10
AU110	2.80	LA LB LC	0.10
AU122	4.40	BC237	0.11
BD100	1.03	BC238	0.12
BA110	0.68	BC251A/B	0.14
BA115	0.45	BA115	0.10
BA121	0.40	A B	0.28
BA129	0.38	BC301	0.30
BA148	0.16	BC302	0.30
BA155	0.45	BC303	0.30
BA157	0.28	BC307A	0.18
BB105B	0.50	BC317A	0.30
BB105G	0.48	BC323	0.90
BB110C	0.42	BC327	0.16
BC107	0.10	BC328	0.16
A or B	0.12	BC337	0.12
BC108	0.10	BC338	0.12
A B or C	0.13	BC350A	0.12
BC109	0.10	BC351	0.16
A B or C	0.14	BC400	0.36
BC115	0.12	BC441	0.40
BC116	0.12	BC461	0.58
BC117	0.22	BC478	0.24

Type Price (£)

BC516	0.48	BF178	0.26	BU126	1.40	ORP12	0.95
BC547	0.12	BF180	0.27	BU133	1.90	R2008B	1.20
A or B	0.10	BF181	0.27	BU204	1.30	R2010B	1.20
BC548	0.12	BF182	0.32	BU205	1.30	R2540	1.20
A B or C	0.10	BF183	0.32	BU206	1.50	TIP30A	0.35
BC549	0.10	BF184	0.30	BU208A	1.40	TIP31C	0.35
A or B	0.10	BF185	0.28	BU236S	1.75	TIP32	0.35
BC550	0.10	BF194A	0.15	BU407	1.10	TIP33A	0.35
A or B	0.10	BF195	0.12	BUX80	3.70	TIP34A	0.70
BC551	0.10	BF224J	0.20	BUY20	2.75	TIP41C	0.42
BC558A	0.10	BF240	0.30	BUY69A	2.60	TIP42	0.42
BC570	0.16	BF241	0.30	BUY69B	1.98	TIP47	0.44
BC6210	2.60	BF244A	0.30	BY100	0.80	TIP211	0.63
BD124P	0.70	BF258	0.26	BY122	0.60	TIP2955	0.70
BD129	0.60	BF259	0.30	BY126	0.60	TIP3055	0.58
BD130Y	0.68	BF262	0.34	BY127	0.60	TIP316B	0.50
BD131	0.36	BF263	0.38	BY133	0.60	TIP320	0.27
BD132	0.36	BF270	0.30	BY135	0.35	Y628	0.14
BD135	0.26	BF271	0.28	BY164	0.45	IN4001	0.04
BD136	0.26	BF272	0.22	BY179	0.56	IN4003	0.05
BD138	0.28	BF274	0.34	BY182	0.80	IN4004	0.05
BD139	0.30	BF275	0.45	BY184	0.38	IN4006/7	0.07
BD140	0.28	BF276	0.32	BY187	0.65	IN4148	0.04
BD142	1.26	BF338	0.28	BY189	0.64	IN5402	0.13
BD145	0.72	BF355	0.37	BY199	0.72	IN5405	0.16
BD150A	1.58	BF450	0.36	BY210	0.21	IN5406	0.17
BD168	0.24	BF457	0.38	BY217	0.16	IN5408	0.19
BD201	0.52	BF458	0.36	BY217A	0.24	2N2122A	0.34
BD202	0.40	BF459	0.36	BY218	0.28	2N2904A	0.48
BD203	0.50	BF460	0.86	BY220	0.22	2N2926G	0.14
BD222	0.40	BF471	0.68	BY228	0.46	2N3053	0.30
BD225	0.40	BF473	0.86	BY238	0.65	2N3054	0.60
BD226	0.40	BF474	0.86	BY240	0.65	2N3055	0.65
BD227	0.40	BF475	0.86	BY242	0.40	2N3056	0.65
BD232	0.45	BF476	0.86	BY243	0.40	2N3057	0.65
BD234	0.30	BF477	0.86	BY244	0.40	2N3058	0.65
BD235	0.38	BF478	0.86	BY245	0.40	2N3059	0.65
BD236	0.38	BF479	0.86	BY246	0.40	2N3060	0.65
BD237	0.38	BF480	0.86	BY247	0.40	2N3061	0.65
BD238	0.38	BF481	0.86	BY248	0.40	2N3062	0.65
BD239	0.38	BF482	0.86	BY249	0.40	2N3063	0.65
BD240	0.38	BF483	0.86	BY250	0.40	2N3064	0.65
BD241	0.38	BF484	0.86	BY251	0.40	2N3065	0.65
BD242	0.38	BF485	0.86	BY252	0.40	2N3066	0.65
BD243	0.38	BF486	0.86	BY253	0.40	2N3067	0.65
BD244	0.38	BF487	0.86	BY254	0.40	2N3068	0.65
BD245	0.38	BF488	0.86	BY255	0.40	2N3069	0.65
BD246	0.38	BF489	0.86	BY256	0.40	2N3070	0.65
BD247	0.38	BF490	0.86	BY257	0.40	2N3071	0.65
BD248	0.38	BF491	0.86	BY258	0.40	2N3072	0.65
BD249	0.38	BF492	0.86	BY259	0.40	2N3073	0.65
BD250	0.38	BF493	0.86	BY260	0.40	2N3074	0.65
BD251	0.38	BF494	0.86	BY261	0.40	2N3075	0.65
BD252	0.38	BF495	0.86	BY262	0.40	2N3076	0.65
BD253	0.38	BF496	0.86	BY263	0.40	2N3077	0.65
BD254	0.38	BF497	0.86	BY264	0.40	2N3078	0.65
BD255	0.38	BF498	0.86	BY265	0.40	2N3079	0.65
BD256	0.38	BF499	0.86	BY266	0.40	2N3080	0.65
BD257	0.38	BF500	0.86	BY267	0.40	2N3081	0.65
BD258	0.38	BF501	0.86	BY268	0.40	2N3082	0.65
BD259	0.38	BF502	0.86	BY269	0.40	2N3083	0.65
BD260	0.38	BF503	0.86	BY270	0.40	2N3084	0.65
BD261	0.38	BF504	0.86	BY271	0.40	2N3085	0.65
BD262	0.38	BF505	0.86	BY272	0.40	2N3086	0.65
BD263	0.38	BF506	0.86	BY273	0.40	2N3087	0.65
BD264	0.38	BF507	0.86	BY274	0.40	2N3088	0.65
BD265	0.38	BF508	0.86	BY275	0.40	2N3089	0.65
BD266	0.38	BF509	0.86	BY276	0.40	2N3090	0.65
BD267	0.38	BF510	0.86	BY277	0.40	2N3091	0.65
BD268	0.38	BF511	0.86	BY278	0.40	2N3092	0.65
BD269	0.38	BF512	0.86	BY279	0.40	2N3093	0.65
BD270	0.38	BF513	0.86	BY280	0.40	2N3094	0.65
BD271	0.38	BF514	0.86	BY281	0.40	2N3095	0.65
BD272	0.38	BF515	0.86	BY282	0.40	2N3096	0.65
BD273	0.38	BF516	0.86	BY283	0.40	2N3097	0.65
BD274	0.38	BF517	0.86	BY284	0.40	2N3098	0.65
BD275	0.38	BF518	0.86	BY285	0.40	2N3099	0.65
BD276	0.38	BF519	0.86	BY286	0.40	2N3100	0.65
BD277	0.38	BF520	0.86	BY287	0.40	2N3101	0.65
BD278	0.38	BF521	0.86	BY288	0.40	2N3102	0.65
BD							

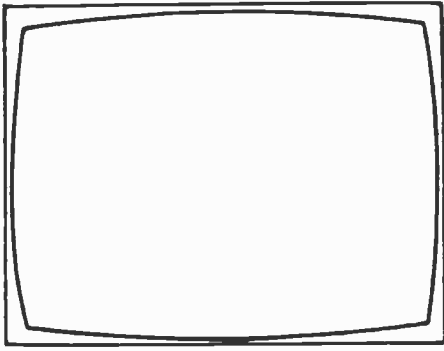

TELEVISION

Financing and Controlling TV

EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 145.

ADVERTISEMENT MANAGER

David W.B. Tilleard
01-261 6671

SECRETARY

Janet Reeve
01-261 6671

CLASSIFIED ADVERTISEMENTS

Pat Bunce
01-261 5942

ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey
01-261 6035

PRICE INCREASE

The price of *Television* will be £1.30 from the next issue dated February. We regret the need to make this price adjustment to cover the increased costs we and our distributors have to meet. We aim to offer good value: larger issues have been published regularly in recent months and the present issue is the largest ever.

COVER PHOTO

This month's cover photo shows a Sony KV1800 with the rear cover removed. See servicing article on page 158.

CAN YOU HELP?

Does anyone know of a source of information/circuit diagrams/spares for the Viptronic 22in. CTV (no model number or country of origin indicated in the set) and a 12in. "Continental" portable, Model GA-X-31, made in Korea? Our enquirer states that these sets have been distributed in Ireland.

CORRECTION

Fig. 4, page 113 last month (low-cost teletext decoder interface panel circuit diagram) had two R8s: the resistor in series with the LED should have been shown as R18. In addition REGs's earth connection was omitted.

The Home Secretary Douglas Hurd has called for public discussion on the subject of financing the broadcasting services. So far as TV is concerned the first question must be whether any change is needed or is desirable. The government seems to think so. It set up the Peacock Committee with a view to getting proposals for change and, despite having received from the Committee a rather curious report, seems to be determined that the matter should not be allowed to rest. Addressing the Royal Television Society recently Mr. Hurd commented on "the increasingly curious system under which the public pays for TV through the licence fee" and said, on the subject of "cycles in broadcasting history", that "I believe we have now once again reached the point in this cycle when the pressures are building up for a change".

One is inclined simply to say bosh! Except that the matter is rather serious, with profound implications for the control of broadcasting. Cycles in broadcasting history? This is of course a pure flight of fancy. Broadcasting is still too young to have experienced anything that can meaningfully be described as a "cycle". There have been significant changes from time to time, but to talk of cycles is to show very little grasp of the development of broadcasting so far. Mr. Hurd is nearer the truth when he talks of pressures for change building up, but even here one has to discount a large imaginary element. It seems probable that the government is being carried away by the pressures it has itself generated through its committees, reports and so on. As to the licence fee system, being increasingly curious one has to ask why? I can see nothing remotely curious about it. Inconvenient in some respects perhaps, but not curious – unless that's how you want to get people to see it. In fact of course the licence system goes back the earliest days of broadcasting, when it was necessary to provide funds for a new service and, by great good fortune, a means of doing so while guaranteeing the service's independence was adopted. The licence fee system has proved to be a remarkably effective way of providing finance for broadcasting and seems as appropriate today as at any time.

But the government seems to hanker after what it likes to think of as radical solutions to problems, whether these are real or largely imaginary. The danger here is that of politicians – and others – who feel it appropriate to be associated with change whether or not this is required. But as Keith Cummins comments on another page, after successively sampling the offerings of US and Russian TV, "we've a lot to be thankful for". In fact we've a first class broadcasting system that deserves support and encouragement rather than being messed about with. It's true that we suffer from excessive repeats, which is a symptom of inadequate funding, but let's not fool ourselves that there's a simple way of unlocking vast new funds for broadcasting.

One problem seems to be that the government thinks the changes that technological development have made feasible imply some need to alter the ways in which the broadcasting services are operated. We've had a bellyful of nonsense about cable in recent years, a subject that the government clearly didn't understand – and wasn't helped to do so by its advisers. Satellite TV has more recently added to the confusion. It will be interesting to see who gains the franchise for this and what they make of it. But the whole way in which the subject of satellite TV has been handled to date is questionable. Exactly why are the three proposed channels to be handed over to a single operator? If the aim is that the new services should provide maximum viewer choice surely at least two franchisees should have been given the opportunity to show us what they could provide? After all several well backed groups have been competing for the franchise. What it seems to come down to, especially after the débâcle of earlier attempts to get DBS started, is a feeling that the whole thing is a bit of a gamble and that the best way of getting a service with minimum public involvement is to hand it over to a single operator.

It's perhaps surprising that five consortia have considered it worthwhile putting so much effort into getting a franchise which, as Raymond Snoddy writes in the *Financial Times*, could be "a licence to lose money on an unprecedented scale". Running the service is going to mean spending several hundred million pounds with no guarantee of a commercial return. Many figures have been suggested. For example, Patrick Whitten, managing director of CIT Research and a realist when it comes to broadcasting opportunities, has suggested that for DBS to be viable in the longer term it will need to attract ten per cent of viewers within five years, going into two million homes, rising to 15-20 per cent over ten years. But he considers that the number of homes going for DBS will be a fraction of this requirement and that accumulated losses could top £1bn within ten years. All pure guesswork of course.

What could induce anyone to invest in such an enterprise? The danger is that the whole thing could end up in a great big shambles – and that this could coincide with the supposed need for change in broadcasting. We could in fact find the whole of broadcasting thrown into the melting-pot. If this scenario is valid, it seems important to ensure that our present broadcasting services do not suffer, though they are bound to do so to some extent. In the past, new services have been tacked on to the existing framework with such associated changes and safeguards as have been considered appropriate. The evolutionary approach has served us well. The danger of the radical approach is that we could all too easily end up with far worse services than we already have.

Servicing the Sony KV1800UB

David Botto

Though this was one of the first Sony colour sets to be released in the UK large numbers were sold and many are still in use, giving good results. A 90° Trinitron tube is used and there's an unusual "non-PAL" colour decoder. There are a number of circuit features to confuse those not familiar with Sony practice of the time. For example the pincushion correction circuit modulates the supply to the line output transformer and there's a separate flyback transformer which is driven by the "converter" transistor Q802. The latter has a regulator arrangement in its emitter circuit. A conventional series regulator circuit produces a stabilised 110V h.t. line.

Access

Access for service is easy. Start by pulling off the brightness and field hold knobs at the top of the cabinet back. Next remove four screws from the back and two on the underside. Lay the set on its face on your rubber bench mat and lift the entire cabinet away.

Panel Arrangement

The circuit boards are identified by letters in the usual Sony fashion and are connected together by wiring that goes to various numbered circuit points. We'll use these board identification letters in this article and identify some of the circuit points. The board mounted upright on the left-hand side when you look into the receiver from the rear is board C. This contains the decoder circuitry, the luminance channel and the RGB output stages, also the sync separator. Next to this is board S, which contains the signal circuitry – the i.f. strip, the a.g.c. and a.f.c. circuits and the intercarrier sound channel. Boards D and P are mounted horizontally at the bottom of the chassis. Board D contains the field timebase and the line timebase up to and including the line driver stage (which drives the converter transistor, the two parallel-connected line output transistors Q801A/B being driven by a winding on the flyback transformer). Board P contains the mains bridge rectifier, the series regulator control circuit, the pincushion correction circuit, the line output transformer and various rectifier diodes fed from the flyback transformer. At the right-hand side, mounted upright, is the small horizontal regulator board HR – this circuit is connected in series with the converter transistor.

Major Circuits

As with most TV sets the majority of faults occur in the power supply and/or the line timebase, so for fast fault-location it's important to understand the arrangements used. Fig. 1 shows the mains input and rectifier circuits and the series regulator that produces the 110V h.t. line. The block diagram in Fig. 2 indicates how the converter, line output and associated circuits are arranged while Fig. 3 provides a simplified circuit diagram of the system outlined in Fig. 2. At first sight it looks a bit complicated, but the whole thing breaks down into a number of relatively simple circuits.

The mains input (see Fig. 1) is fed via fuse F901 (2AT)

and the double-pole on/off switch (incorporated with the volume control) to the mains autotransformer T903. This feeds the heater transformer T902 and the mains bridge rectifier D601-4 which produces 130V across C902A. The 2A circuit breaker CB901 is connected in one side of the feed to the mains bridge rectifier – it seems to do a good job of protecting the circuitry. The unregulated 130V supply is fed to the collector of the series regulator transistor Q902 which is mounted at the top right of the receiver (viewed from the rear). Its control circuit (Q601, Q602 etc.) is conventional and is mounted on board P which receives the regulated 110V output from Q902 at point 17. VR601 is used to set up the 110V line. If the series resistor R631 (2.7k Ω , 0.25W) has to be replaced use an 0.5W type at least. Notice that Q602 receives its collector supply via R902/3 (both 0.5W types) which can and do fail or change value.

The 110V line should be set up before any other adjustments are made. Do this with a digital multimeter connected between point 17 on panel P and chassis: disconnect the aerial and adjust VR601 carefully for exactly 110V. Check the reading again after the set has been running for half an hour.

The three presets VR602/3/4 (all 250k Ω) on board P provide low-level white balance adjustment. You set them up by turning the first anode preset VR605 (also on board P) to give a barely visible picture, preferably using a crosshatch input signal.

There are two presets in the pincushion correction circuit on panel P. VR608 (5k Ω) sets the width while VR606 (10k Ω) provides pincushion adjustment. The waveform shown in Fig. 4(a) should be present at the emitter of Q604 when a set is correctly adjusted – the d.c. voltage present at this point should be about 100V.

Dealing with a Dead Set

What to do when a set won't start up? Since the panels are all wired together it's not easy to isolate them for fault finding. Fortunately however if the set is dead or tries to start up but can't quite make it tracing the faulty section is not too difficult.

Start by examining fuse F901 (with the mains disconnected of course). If it's open-circuit with no signs of blackening it may well have failed of old age – especially if it's the original one. Replace it – after checking that the cutout (CB901) is pushed in – and try the receiver on the mains. If the set works run it for at least three hours before returning it to the customer.

If F901 is in order but the receiver just won't start up examine C531 on board D. This capacitor forms part of the line oscillator start-up circuit (see Fig. 5). It can dry up, falling in value and leaking. It may well fall apart in your hands when you touch it. If it's the original one change it anyway – this will save you an almost certain callback later. In the event of a fault in the line timebase Sony suggest connecting a 3.9k Ω , 5W resistor between the cathode of D510 and the 110V end of R555 in order to get the line oscillator going. We prefer to use a separate d.c. supply, variable between 11-18V. You'll then be able to check the line oscillator circuit with the mains supply

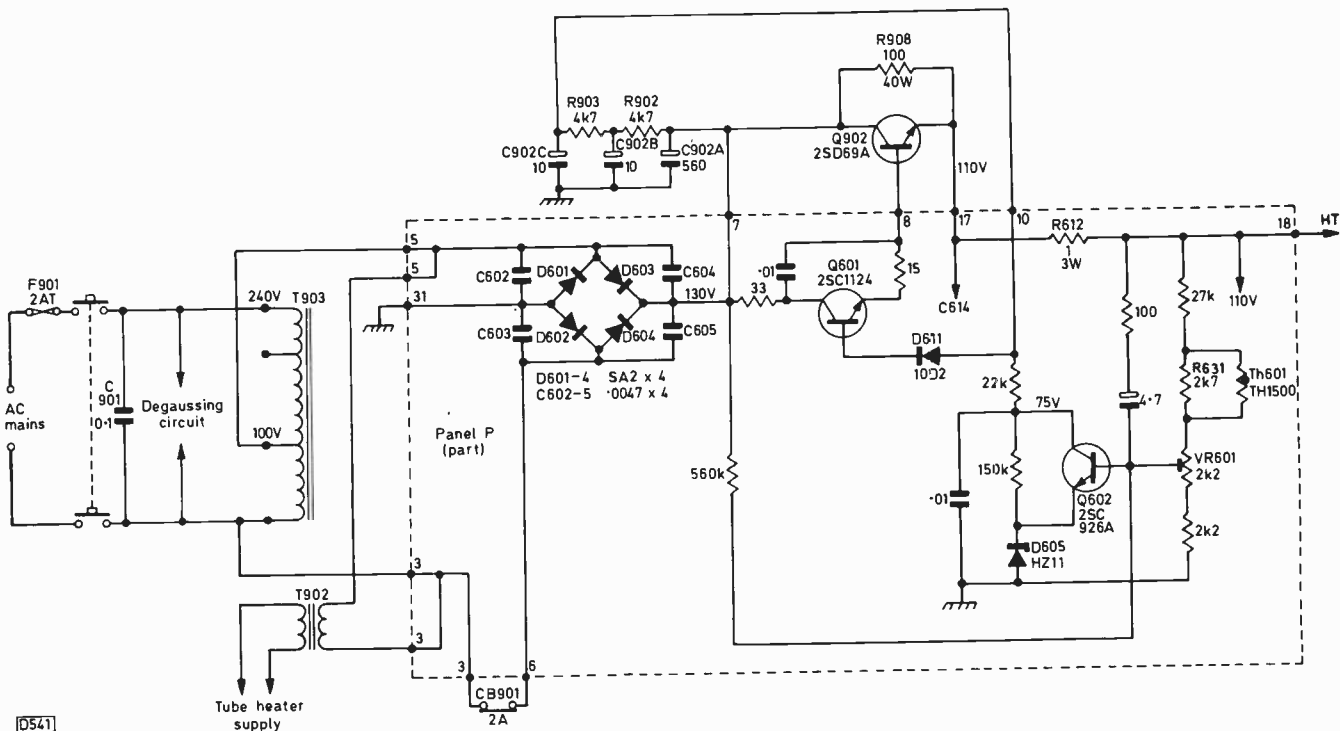


Fig. 1: The mains input, rectifier and series regulator circuits. D601-4 are type SA2 or U05E.

disconnected.

A variac or tapped mains input transformer is essential when working on this model: a component tester (see *Television*, June 1984) saves hours of time since all components on the board you're testing can be speedily checked. When a variac/tapped transformer is used the set must be switched on and the mains input increased gradually. Even if the set is in perfect order it won't start when the mains input is slowly increased from zero because the line oscillator start pulse provided by C531 will not be present. You'll need the external 18V supply.

Now a brief warning. Always keep the mains switch in the "on" position whilst the set is connected to your variac. Don't switch it on and off. If you do there'll be a sudden surge of a.c. input that may well blow out transistors all over the receiver. Please don't ask me how we found this out . . .

If fuse F901 is o.k. and capacitor C531 is in order, make sure that the receiver is disconnected from the a.c. mains supply then check the line output transistors Q801A/B, the series regulator transistor Q902, the converter transistor Q802 and the two transistors Q851/2 on the HR panel. If any are faulty replace them - but don't connect the mains supply to the receiver yet. If all appears to be in order, connect the positive side of your external d.c. supply, adjusted to 11V, to the cathode of diode D510, negative to chassis, to power the line oscillator. Connect your oscilloscope (10:1 isolation probe) to the collector of transistor Q510 in the line oscillator circuit (it's a multivibrator, using Q509 and Q510, both types 2SC1364). A waveform similar to that shown in Fig. 4(b) should be seen. Since the line oscillator is running free you may observe some variations in this waveform. The important thing is that it is present.

If the waveform is present, disconnect the d.c. supply and instead connect it between the junction of R536/R534 and chassis. Increase the supply to 18V. The waveform should continue to be present.

If the line oscillator doesn't produce an output waveform check the two transistors Q509 and Q510.

While you're about it, check the flywheel line sync phase splitter transistor Q507 (another 2SC1364) and the line driver transistor Q511 (2SC867). If any of the transistors on board D show signs of corrosion on their leads replace them even if they test all right. Diode D510 (10D2), the flywheel line sync discriminator diodes D505/6 (type 1T22A) and diodes D508/9 (type 1T40) in the line driver stage should also be tested. The KV1800UB has now seen a few years service, so remember that the small tubular electrolytics tend to dry out. Check, in the following order, C525 (4.7µF, 25V), C539 and C522 (both 1µF, 50V), then C521 (47µF, 25V). C531 we've already mentioned. If the line oscillator works with an 11V supply but not with an 18V supply at the junction of R534/6 and both C521 and D510 are in order check C615 (470µF, 35V) on board P. Check C614 and C619 at the same time. Although they are not connected to the line oscillator circuit this will save time in the long run.

If you don't have a variable d.c. supply handy, use a single PP9 battery in place of the 11V d.c. supply and two PP9s to provide 18V.

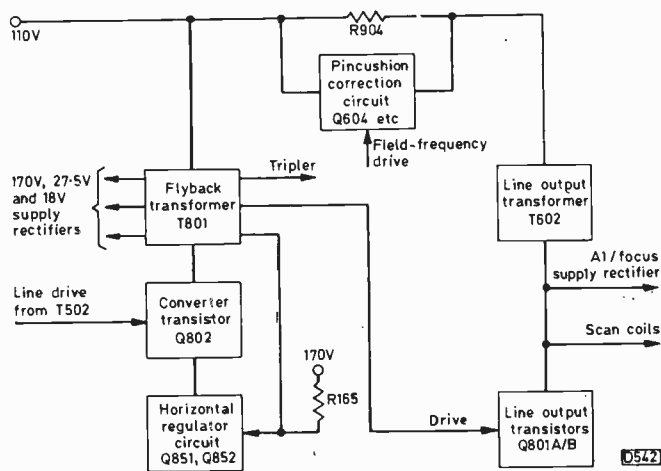


Fig. 2: Block diagram showing the converter and line output stage arrangements.

Make sure that the track of the line hold control VR505 is intact. It's a good idea to apply a little Castrol DWF to the slider.

Power the line oscillator from the external 18V supply, connect your scope to the collector of the line oscillator transistor Q510 and switch the receiver on. Connect your digital voltmeter across the output from the mains bridge rectifier, i.e. between the junction of D603/4 and chassis, then slowly turn up the variac or tapped transformer until you obtain a reading of about 50-60V d.c. Reduce the mains input to zero and transfer the voltmeter to point 17 on board P, i.e. Q902's emitter. If you have two meters available they can be simultaneously connected to these points. Advance the input cautiously until the reading obtained at point 17 is 110V d.c.

Transfer the scope probe to the collector of line driver transistor Q511 then to the collector of converter transistor Q802. The waveforms should be as shown in Fig. 4 (c) and (d).

If a voltage appears at the junction of D603/4 but the 110V line is missing the fastest way to deal with the fault is to check Q601/2 and the associated diodes on board P with your component tester. Replace any that show signs of corrosion even if they test "good". Next examine all the small tubular electrolytics on the board for signs of drying out, starting with C616 (33 μ F, 160V). Also check the board for dry soldered joints.

We've not had a faulty flyback or line output transformer to date in one of these sets, but bear in mind that they are getting older. (We recently had our first ever line output transformer failure in a Sony KV2000UB.)

Once the receiver is functioning, turn the variac input voltage completely to zero before disconnecting the mains supply. Remove the external 18V d.c. supply and, provided you're sure that C531 and R555 are in order, connect the receiver directly to the mains supply. Switch on and you should obtain picture and sound.

Despite its age the tripler, housed in block DC801 which also contains the 1M Ω static horizontal convergence control VR801, seldom fails. If you suspect it, disconnect its input from the flyback transformer and see if the receiver starts up without it, i.e. the d.c. supplies and waveforms are correct. Don't be in a hurry to remove the tube's final anode cap as this contains an extra connector for the static horizontal convergence voltage - refitting it is not easy. If these two connectors short together the picture will be strange indeed!

The Field Timebase

The field timebase circuitry on board D seldom causes problems. The line-up is as follows: Q501 (2SA677) field blocking oscillator; Q502 (2SC1364) field amplifier; Q503 (2SA677) field driver; Q504 (2SA677) phase inverter; Q505 and Q506 (both 2SD291) field output transistors. Reduced field scan is usually caused by the field scan coupling capacitor C511 (470 μ F, 25V) going open-circuit or leaky. If reservoir capacitor C619 on board P dries out and C515 (470 μ F, 35V) on board D does the same (the two are in parallel) all sorts of weird fluctuations in the field scan may occur. If the field output transistor(s) Q505 and/or Q506 fail, check Q503/4/2 and the bias diodes D503/4 (type 1T40) before you replace them.

To make sure that the field oscillator is working check the waveforms at the collector of Q501 and the base of Q502 - see Fig. 4 (e) and (f) respectively. The coupling capacitor between these two stages, C508 (100 μ F, 16V),

can lose capacitance, cutting off or reducing the drive to Q502. As with every board in the KV1800UB, inspect all the small electrolytics for signs of corrosion.

Signals Circuits

The tuner seldom fails. If it does the wisest course is replacement. If you've a dusty or weak picture, before condemning the tuner remove the lead from point 10 on board S (the tuner a.g.c. connection) and bias the tuner from an external source. If this results in a good picture suspect transistors Q209 (2SA677) and Q210 (2SC633A) on board S. If these are o.k. check C239 (33 μ F, 16V).

Board S seems to be relatively trouble free, though occasional faults do occur. 18V is supplied to this board at point 15 and is fed via choke L214 (680 μ H) to the various circuits on the board. If this choke goes open-circuit or suffers from dry-joints nothing will work. There are two i.c.s on the board, the intercarrier sound chip IC201 (AN241) and the a.f.c. chip IC202 (CX089D). Perhaps we've been fortunate, but so far we've found these i.c.s to be entirely reliable. The sound output transistor, Q901 (2SC867) is mounted off the board, near the loudspeaker. If you get weak or distorted sound, check Q901 then, in the following order, C252/3 (both 1 μ F, 50V) and C251 (100 μ F, 16V). These electrolytics tend to lose capacitance, giving rise to weak, distorted or no sound. Note that Q901 receives its collector voltage via point 21 and R603 (68 Ω , 0.125W) on board P. If R603 fails you'll wonder where the sound went . . .


To check the video output from board S, connect your oscilloscope (10:1 probe) to point 7 on board C. You should see the complete video signal - use a colour bar input. The video output from board S is fed to board C via the slider of VR903 (1k Ω) on the front panel. Sony call this the picture control.

The i.f. output from the tuner goes first to the UIF board. This is tucked away below the tuner and causes few problems. You can however get a noisy or speckled picture if the transistors on this board (Q751/2, both type 2SC1128) get corroded or if the supply smoothing capacitor C752 (33 μ F, 25V) loses capacitance.

The Decoder Panel

Board C contains the luminance and chroma circuitry and, with the front-panel mounted hue control, tends to remind the TV engineer of NTSC receivers. The "non-PAL" circuitry does however produce a surprisingly good colour picture - provided the hue control is correctly set to compensate for phase errors in the received signal. There are forty three transistors on the board and no i.c.s. We should perhaps mention that the circuitry was devised to avoid infringing the PAL patents. The circuitry decodes the PAL signal, but does so in a non-PAL manner that doesn't take advantage of the PAL phase error cancellation feature. There are nonetheless a chroma delay line and a bistable to carry out signal switching.

Although the chroma circuitry looks complex it's not difficult to locate the faulty section using an oscilloscope (10:1 probe) and a colour bar input to the receiver. Start at circuit point 1, where the composite video signal is fed to C301 (39pF). Then transfer the scope probe to the junction of C341 (39pF) and the secondary winding on T305 (CAT-2) where you should see the familiar cotton-reel waveform. Next move the probe to the secondary of T306 (BAT-1) to check the burst waveform, then check

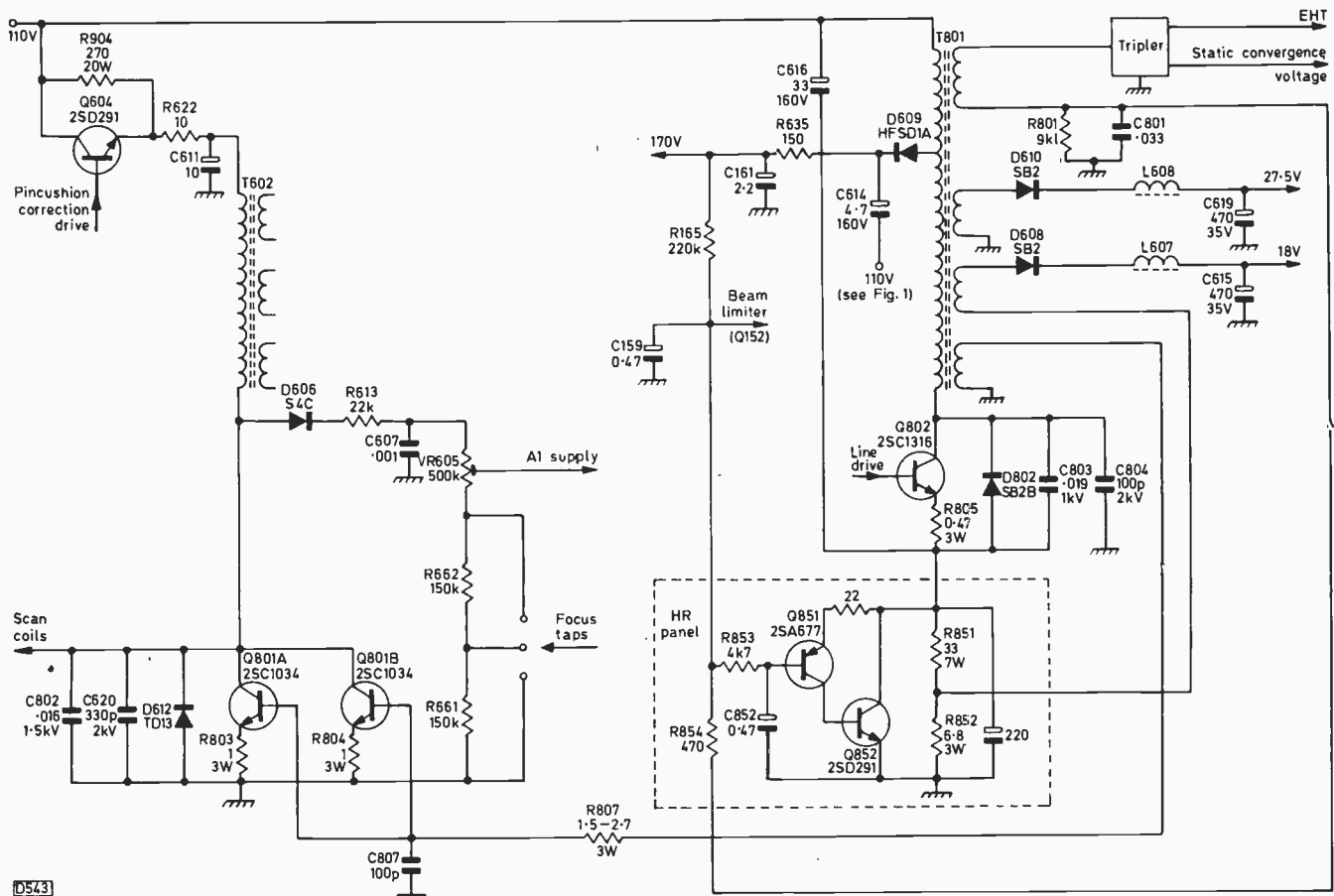

D543

Fig. 3: Simplified circuit showing the converter, line output and associated stages. D608 and D610 are type SB2 or V09C. Component reference numbers indicate location, i.e. R165 is on board C, Q604 on board P, etc.


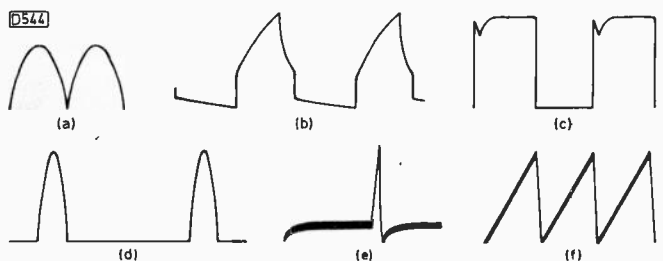


Fig. 4: Key waveforms for testing. Peak-peak voltages: (a) 10V; (b) 4V; (c) 230V; (d) 450V; (e) 6V; (f) 1V.

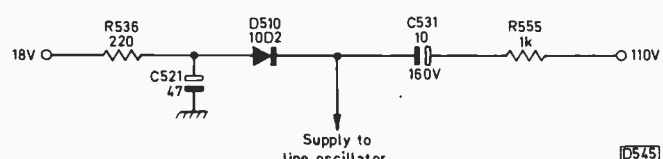

D545

Fig. 5: The line oscillator start-up circuit.

for a 4.43MHz signal at the junction of C362 (27pF) and the secondary of T307 (COT-1). This checks out the B - Y burst/reference oscillator channel. There's a separate burst/reference oscillator channel concerned with the R - Y signal. In this case check for the burst signal at the secondary of T308 (BAT-2) and for a 4.43MHz signal at the secondary of T309 (COT-2). The R, G and B outputs should be present at points 18, 16 and 15 respectively on the board. Make sure that there's a nice squarewave at the collector of Q162 (2SC633A) in the bistable circuit.

The 18V input to the panel enters at point 4 and is fed via L156 (680μH) to the various circuits. If this choke corrodes or is dry-jointed you'll lose the 18V supply. This sounds simple - but it's easy to get caught. Fluctuating or

intermittent colour is often caused by the clock pulse amplifier transistor Q324 (2SC633A) leaking. The sync separator transistor Q154 (2SA677) is mounted on this board: when it plays up it can cause colour and sync problems.

Before making a lot of voltage and scope checks on panel C it pays, as with the other panels, to examine the transistor leads for corrosion and the small capacitors for drying out. Replace any that fail this test. You'll then usually find that the circuitry works correctly! Unless someone has fiddled with the preset adjustments they are best left alone - they don't seem to drift.

Tidying Up

When all repairs have been completed spray any panels you've soldered with a thin coat of circuit varnish and make sure that all the connecting leads between the panels are in their correct positions. Run the set for a few hours before returning it to the customer.

Modifications

The main modifications of concern to the service engineer are as follows:

- (1) R623 changed to 220Ω, 3W metal oxide.
- (2) R910/R920 changed to 2.2MΩ (0.5W) with a 470pF (250V a.c. rating) added in parallel.
- (3) C803 changed from 0.02μF to 0.019μF (1kV).
- (4) After serial number 25,301 a modified flyback transformer (T801) was fitted. Part no. for the earlier type is 8-983-662-15 and for the later type 1-439-132-11. These

transformers are not interchangeable.

(5) Also after serial no. 25,301 R445 was changed to 390Ω and R807 (originally between 0.68-1.8Ω) was changed to 1.5-2.7Ω. Examine the original before replacing. R807 can fail if the line output transistors go short-circuit. The precise value depends on the gain rating of the transistors fitted. This is indicated at the right beneath the transistor type number. If the rating is 3, use a 1.5Ω resistor; if the rating is 4 use a 1.8Ω resistor; if the rating is 5 use a 2.7Ω resistor.

(6) The voltage rating of C233 on board S was changed from 16V to 10V – but always fit a 25V working type when a replacement is necessary.

(7) A “squelch” circuit board was fitted in the audio circuit after serial number 33,301. If the board seems to have little effect measure the voltage between the base of Q052 (2SC633A) and chassis. The reading should be 0V with no signal rising to approximately 4.5V d.c. or more with a good signal. If it doesn't, replace capacitor C054 (3.3μF, 25V).

Letters

TELETEXT DECODER

Peter Marlow's article was of considerable interest to me since I have already constructed a teletext decoder on similar lines, albeit using a 6502 microcomputer control board and providing RGB outputs for use with a colour monitor. The decoder will also provide a printer dump of the displayed page on any Epson lookalike printer.

Like Peter Marlow I used the /AHS sync signal from the VM6101 decoder but found that the field sync was intermittently lost about thirty seconds after switch on when an incoming video signal was present. Removing the signal cured the problem – but of course removed the ability to receive teletext! I found that a better solution was to use the off-air sync from the decoder board – this is automatically switched to /AHS in the absence of a video input signal, thereby allowing after-hours display.

I also implemented a “next page” and “previous page” increment/decrement facility but found that the decoder randomly forgot one of the digits in a transmitted page number. This doesn't appear to be a timing or a decoder board fault. Any comments?

R.G. Nevell,
Warrington.

GRUNDIG GSC100 CHASSIS

The article on the Grundig GSC100 chassis (September 1984 issue) covered most faults experienced with these sets. A chroma fault I had recently was traced to C863 (0.1μF) which decouples pin 8 of the TDA2521 chip in the colour module. The voltage at this pin read approximately 6V instead of 9V because C863 was leaky (350Ω). Failure of this capacitor also caused flashing grey lines when there was no colour. C861 (0.1μF) which decouples pin 9 of the chip could presumably cause similar problems.

D. Parsons,
London W12.

VCR UPDATING

After my two Philips N1500s, converted to half-speed operation, had notched up over fifty thousand hours' use each I decided that the time had come to upgrade to newer, VHS machines – the rising price of N1700 heads was a major factor in this decision.

After making enquiries I decided on Panasonic, whose machines have a reputation for reliability, and bought two NV7200Bs from a dealer in Truro (he offered me a “quantity” discount!). To get best results I modified the receivers to work as PAL input monitors and found that the overall quality obtained using the combination of ancient Rank A823 chassis with modified line timebases

and the NV7200Bs was very good.

One of the machines developed a fault after a few weeks but we could find no reference to the fault in back copies of *Television*. The machine left a loop of tape after threading out, so that it was necessary to press rewind briefly before playing or ejecting. This went on for some time until I noticed that rewind got sluggish when the machine had been in use for some time, and eventually it wouldn't play for more than about half an hour before cutting out. Fearing the worst I monitored the tape motor voltage by connecting an AVO via flying leads soldered to the motor plug, but nothing seemed to be amiss. The fault was eventually cured by removing the two turntables and applying a very small amount of Three-in-One oil to the shafts, taking care not to splash the belts or rubber wheels.

For the benefit of others using NV7000 series machines here's a list of faults etc. noted in back issues:

July 1981, page 465.	Loading failure.
October 1981, page 632.	Cassette lamp failure.
January 1982, page 153.	Unthreading: Hall sensor fault.
March 1982, page 241.	Unthreads after threading.
October 1982, page 647.	Aerial amplifiers.
May 1984, pages 386/8.	Tuning drift and timer faults.
August 1985, page 566.	Capstan fault: oiling.
September 1985, page 635.	Jammed supply spool.
March 1986, page 308.	Programme switch replacement.
June 1986, page 511.	Sound fault.
July 1987, page 590.	Servicing article.
<i>John de Rivaz, B.Sc. (Eng.), A.M.I.E.E., Truro, Cornwall.</i>	

S. AFRICAN SATELLITE TV RECEPTION

I understand that signals can be received here in South Africa from the Russian Ekran satellite at 99°E with 714MHz transmissions. Could any S. African reader interested get in touch with a view to exchanging information on the technology involved?

Dez Boldizar, 14 Goudsnip Road, Atlasville,
Boksburg 1459, Transvaal, S. Africa.

FOR DISPOSAL

We have a Saba Ultra CSL Model 6745 fitted with the H Telecomcommander chassis for disposal. It's clean and was owned by a non-smoker but has a low tube and unknown faults. We just can't bring ourselves to throw this beautiful abomination on the skip! It's free of charge to anyone who likes to collect it.

R.S. Daynes, Radio and TV Service,
Deepdale House, Dibdale Road, Dudley,
W. Midlands (telephone 0384 56 355).



Newlife

VIDEO HEADS

**A new exchange service for
upper drum assemblies incorporating
the latest in video technology**

CONTACT YOUR NEAREST DISTRIBUTOR FOR MORE INFORMATION

**NEWCASTLE GENERAL
SUPPLY CO. LIMITED**
4-10 Leazes Park Road,
Newcastle upon Tyne NE1 4QJ.
Telephone: 902 323177

VACUONICS LIMITED
Peartree Lane,
Peartree Lane Industrial Estate,
Dudley, West Midlands DY2 0QY.
Telephone: 0384 74182

**PECO ELECTRONICS
Head Office**
248 Grand Drive,
Raynes Park, London SW20 9NE.
Telephone: 01-543 0548

PECO ELECTRONICS
New England House,
New England Street,
Brighton, Sussex BN1 4GH.
Telephone: 0273 688395/6

D.D. DISTRIBUTORS
27 Florence Road,
Parkstone, Poole,
Dorset BH14 9JF.
Telephone: 0202 722622

H.B. LITHERLAND
237 Caunce Street,
Blackpool,
Lancs FY3 8HG.
Telephone: 0253 302841

WEST RADIO LIMITED
24 St. Thomas Street,
Bristol BS1 6JL.
Telephone: 0272 292525

WEST RADIO LIMITED
165 Goldcroft,
Yeovil, Somerset.
Telephone: 0935 76022

WEST RADIO LIMITED
Ferndale Road,
St. Thomas,
Exeter, Devon.
Telephone: 0392 79909

**WILLOW VALE
ELECTRONICS LIMITED**
11 Arkwright Road,
Reading, Berkshire RG2 0LU.
Telephone: 0734 876444

**WILLOW VALE
ELECTRONICS LIMITED**
Unit 4, Enterprise Park,
Reliant Street, Oldham Road,
Manchester M10.
Telephone: 061 682 1415

**PERKVALE
ENTERPRISES LIMITED**
Unit 2,
Robin Hood Industrial Estate,
Clondalkin, Dublin 12.
Telephone: 0001 519631

P.V. TUBES
104 Abbey Street,
Accrington, Lancs BB5 1EE.
Telephone: 0254 36521/32611

D.B. COMPONENTS
St. Matthias Mission,
Armada Street, North Hill,
Plymouth, Devon PL4 8LZ.
Telephone: 0752 24369

H.R.S. LIMITED
Electron House,
Great Barr Street,
Birmingham,
Midlands B9 4BB.
Telephone: 021 771 2525

P.J. HILL
Rear of 25 High Street,
Tewkesbury,
Glouc GL20 5AT.
Telephone: 0684 294317

COOPER ELECTRONICS
82 Terenure Road East,
Dublin 6, Ireland.
Telephone: 0001 900470/900824

CHARLES HYDE AND SON LIMITED
Prospect House, Barmby Road,
Pocklington, Yorks YO4 2DP.
Telephone: 07592 3068

Factory B Pallion Industrial Estate St Lukes Road Sunderland SR4 6SR Sales Desk 0783 44429

UPDATING COURSES

HIGH PERCENTAGE OF PRACTICAL WORK INTENDED FOR QUALIFIED SERVICE ENGINEERS.

VCR SERVICING

(3 WEEKS FULL TIME)

NEXT COURSES START ON JAN. 26th & MAR. 16th 1987 – TUITION FEE £575

MICROCOMPUTER SERVICING

(ONE WEEK FULL TIME)

NEXT COURSES START ON DEC. 29th, FEB. 16th & APR. 6th. – TUITION FEE £250

(MSC grants available on JTS/ATS training schemes, subject to approval. If you are unemployed, or are currently employed and require retraining, or updating, you or your employer may be eligible for financial assistance under one of the above schemes.)

Further details from:

LONDON ELECTRONICS COLLEGE (VC Dept.)

20 Penywern Road, Earls Court, London SW5 9SU

Tel: 01-373 8721

TELEVIDEO SERVICES

145 STATION ROAD, BEESTON, NOTTINGHAM NG9 2AZ

TEL: 0602 226070

VIDEO ENGINEERS SERVICE KITS

A large percentage of video recorder problems are due to simple mechanical faults such as broken belts, worn idlers, sensor lamps gone etc. Nothing is more annoying than having to put a machine to one side and wait for a minor part. Now the answer at last with the TELEVIDEO SERVICES

Video Service Kits

Our kits contain all the spares necessary to effect repairs to the most popular video recorders in use today. Then having completed the job and satisfied the customer simply recorder the parts used to keep the kit up to date. Supplied in sturdy interlocking storage units. Ideal for bench or field use.

Price of components if bought separately **£92.00 + VAT**

KIT PRICE INC. STORAGE UNIT ...

£69.95 + VAT

VHS & BETA IDLER KIT

CONTAINS:

SHARP REEL IDLER (fits Sharp, Amstrad, Saisho, Triumph etc.)
HITACHI REEL IDLER (fits VT11E, VT14E, VT17E, VT19E & GEC 4100 etc.)
PANASONIC REEL IDLER NV2000
PANASONIC REEL IDLER NV7000, NV7200
PANASONIC REEL IDLER NV333, NV366
PANASONIC REEL IDLER NV370, NV230, NV730 etc.
HITACHI REEL IDLER VT8000, 8300, 8500
HITACHI REEL IDLER VT9300, 9500
SONY REWIND IDLER KIT C5, C7
SONY REWIND IDLER KIT C6
SANYO REEL DRIVE PULLEY VTC5000 etc.
FERGUSON CLUTCH (LARGE) 3V00, 3V16, 3V22 also fits all JVC equivalents
FERGUSON REEL IDLER 3V29, 3V30
FISHER REEL IDLER FVHP615 etc.
PANASONIC PLAY IDLER NV2000
PANASONIC PLAY CLUTCH NV7000, NV7200



ALSO AVAILABLE!

LAMP KIT BELT KIT PINCH ROLLER KIT

PLEASE SEND S.A.E. FOR FULL DETAILS OF ALL KITS

ORDER FORM

Please send me Idler kit(s) @ £69.95 + £1 postage + VAT.
Please send me Genuine belt kit(s) @ £89.95 + £1 postage + VAT.
Please send me Replacement belt kit(s) @ £55.00 + £1 postage + VAT.
Please send me Lamp kit(s) @ £39.95 + £1 postage + VAT.
Please send me Pinch Roller kit(s) @ £62.50 + £1 postage + VAT.

DEDUCT A FURTHER £10.00 DISCOUNT IF ORDERING ALL FOUR KITS.


Satellite TV

Stockists of 4, 11 & 12GHz Equipment. Distributors for:



DH Satellite TV

DX ANTENNA

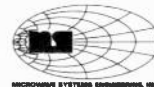

Specialists in supplying to Dealers

Harrison Electronics

CENTURY WAY, MARCH, CAMBS., PE15 8QW. ENGLAND
TELEPHONE: (0354) 51289 TELEX: 995801 GLOTX-G REF: H25

TUNERS + TUNERS

- ★ If you repair sets regularly – phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART
(U.K. ONLY)

32 Temple Street,
Wolverhampton WV2 4LJ.
Phone: (0902) 29022.

TV Behind the Curtain

Keith Cummins

Last summer I took my holiday in Eastern Europe, passing through East Germany, Poland and the USSR before emerging via Finland and crossing the Baltic to Scandinavia. I was particularly interested in observing the TV scene in the USSR – we see only edited snippets on our news. There were three things to consider: the quality of the transmissions (using the SECAM colour system), the TV sets and the programmes available.

Communication in the USSR is rather difficult for the Western visitor. Not only is the language a problem but unless you know the Cyrillic alphabet it's almost impossible to read anything. A similar problem occurs in Greece of course. As a result it was much more difficult for me to get at the facts than it had been on my earlier visit (see *Television* January 1986) to Canada and the USA, where all you have to do is ask. In the USSR I had to depend almost entirely on observation, and although I had technical questions there was no one I could easily ask and most of them had to remain unanswered.

Having outlined the constraints I'll try to give you a picture of TV behind the curtain. First, a visit behind the Iron Curtain is not as rigidly controlled an affair as it once was. We were able to walk about freely and look at things: we weren't allowed to take photos of touchy subjects like border posts, military installations and airports, but we were otherwise not too restricted in our movements.

Receivers

The Russian TV sets I saw, in hotels and elsewhere, were generally very substantial – constructed like the proverbial brick-built outhouse. All were of hybrid design, with plenty of valves and pictures of varying quality. Some were very good, others dreadful, but this is true the world over and is not peculiar to the USSR. Most of the sets could receive two channels. All TV broadcasting in the USSR is at v.h.f. I read that the Moscow transmitter has a service area of 200km radius and is "of sufficient power that no relay stations are needed". The area is quite flat and v.h.f. will go a long way, but even so the power must be formidable. I was told that three channels are available in Moscow.

Transmission Standards

Transmission standards appeared to be consistently good. As the USSR covers such a vast area microwave links are used for TV and other communications. I saw some that had the dishes mounted horizontally near the ground, firing upwards towards a reflector plate mounted on a tower. The plate reflected the signal horizontally in the right direction.

Receiving Aerials

A weird and wonderful variety of TV aerials were to be seen. Many had a definite DIY look about them, particularly out in the country. It was unusual to see them mounted on a house – most were mounted alongside on a pole with stays, the pole often consisting of a long sapling stripped of its branches. Band I and Band III aerials were

in evidence near centres of population: in the country Band I only was usual. I saw many "Double Diamond" aerials (see Fig. 1) west of Leningrad. These were definitely home built, probably from a bought-in kit. Judging by the varieties seen the constructor had to supply his own timber. This is a particularly unusual type of aerial – I've seen nothing like it elsewhere in my travels. Fig. 2 shows some other aerials seen.

Economic Conditions

Progress seems to be slow in the USSR: there isn't the commercial competition we see in the West, with different

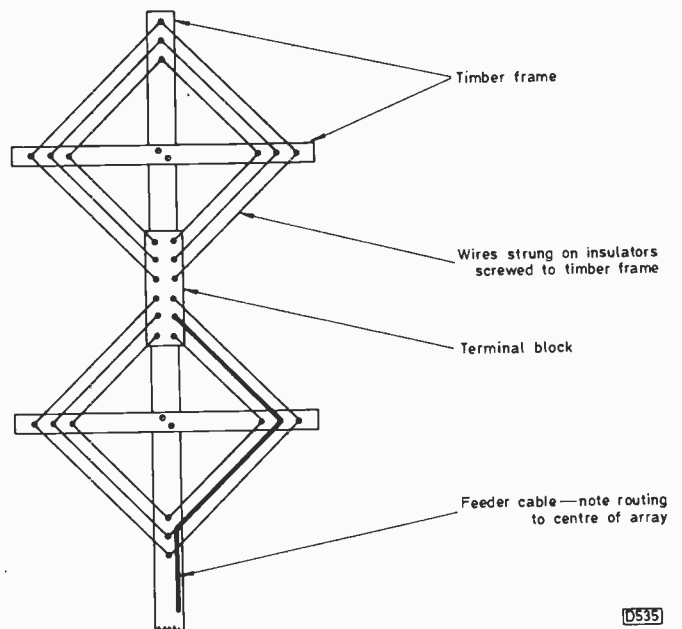


Fig. 1: Double-diamond type aerial.

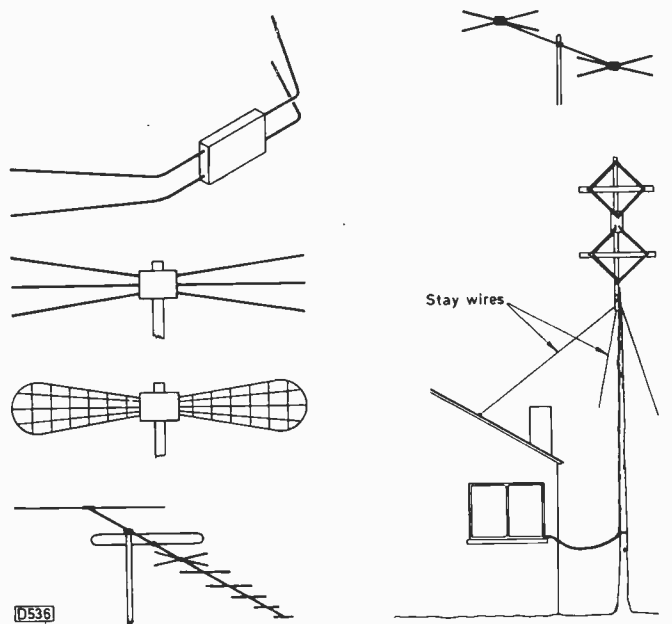


Fig. 2: Some other types of aerial seen and an example of a double-diamond aerial mounted on a stripped tree.

companies leap-frogging each other in an attempt to be first with the latest technology. The Russian philosophy seems to be that if something works all right stick with it and don't try to get too fancy (you can certainly see that this is true of their cars, the popular ones being mostly based on obsolete Fiat designs). In addition, economic priorities are assigned by government control, and when you see people queueing in some places for milk and bread it's obvious that there's not much cash available for luxuries. A black-and-white set costs approximately £200 and a colour set around £500. Wages are low (typically £200 a month) but since accommodation is cheap (some £20 a month inclusive) the economic conditions are not as harsh as they might at first appear. Nevertheless the purchase of a colour set represents a much bigger chunk of a Russian's income than it does for us and a typical shop had just two sets in stock.

The Programmes

I wasn't very impressed by the programmes, though

having no understanding of the language didn't help. Their shots seemed to last too long, particularly with "talking heads" and stage productions. Production techniques are nothing like as slick as ours (no Quantel) and in some ways it's like going back twenty or thirty years. Presumably the viewers don't miss what they've never seen. If Mr. Gorbachev is saying something important on the news you get the whole lot, without editing. One night he was on for half an hour solid during an hour-long news programme. Somehow there doesn't seem to be much fun in Russian TV. The complete reverse is of course the ghastly American games show, all flashing lights, screaming contestants, "big bucks" and "whammies"!

Postscript

I still believe that in the UK we have the best TV in the world, in all respects. There will always be criticisms of course, and nothing's perfect, but believe me when, after successive visits to the USA and the USSR, I say that we've a lot to be thankful for.

The Operation of Electric Motors

Part 5: Brushless DC Motors

Mike Phelan

In this final part of the present series we'll take a look at what is now becoming the most popular type of motor for video applications. This is the brushless motor which uses semiconductor devices instead of the conventional commutator and brushes to carry out pole switching.

In the commutator motors described in Parts 3 and 4 the commutator and brushes provide a means of supplying current to the rotating armature windings in turn as the motor rotates. There are several disadvantages to this arrangement. A few of these are as follows. Switching is abrupt, the self-inductance of the windings causing interference – a "ringing" component is superimposed on the armature current. In addition a large number of poles are required to give sufficient smoothness of rotation. In most cases this is not enough: the motor must run at a fairly high speed under load, with considerable gearing down to the driven component – drum or capstan – and even more inertia added in the form of a flywheel in order to allow smooth servo speed control.

Development of the Brushless DC Motor

If we make the current flowing through the windings as nearly sinusoidal as possible, with two or more poles receiving currents with phase displacements equal to 360° divided by the number of poles, then we have a fairly good polyphase a.c. motor. With a stationary set of windings and rotating magnets the resemblance to a synchronous motor can be clearly seen.

To provide sinusoidal a.c. with two or more phases it's necessary to have some sort of frequency source. Now in a VCR we are already closely controlling the speed and phase of the drum and capstan motors, so it's no use having a fixed frequency source – it has to be varied to control the speed. The motor itself can therefore be employed to provide the switching, by using some sort of pick-ups spaced equidistantly around the motor. There are several ways of doing this – magnetic, mechanical or optical to name a few. As the rotor is a magnet (see Fig.

1) this is the obvious choice. The sensing devices could be coils, but Hall effect sensors are normally used in practice. These are four-terminal semiconductor devices whose resistance varies when subjected to a magnetic field: d.c. is supplied to two of the terminals, the current flowing via the remaining two terminals being amplified by an i.c. or transistors to carry out pole switching.

This type of motor can be looked upon as a polyphase synchronous motor (it must be synchronous as the supply frequency is locked to the speed of rotation!) which behaves as a normal d.c. motor, i.e. the speed can be controlled by varying the supply voltage.

The performance is vastly superior to the commutator type in all respects. Low-speed running is smooth as the mechanical inertia is high, due mainly to the heavy magnet. In addition the current through the Hall-effect sensors can be made to approach a sinusoid by suitable design of the magnet. This also eliminates the interference problem. Mechanical design of the tape transport system is much simpler, belts, pulleys and flywheels being eliminated. There may be belt drive for ancillary functions such as reel drive and loading, but we're concerned here with drum and capstan drive. Finally the only parts that wear are the bearings, so the motor lasts longer.

Drive Electronics

The electronics required consist simply of a means to amplify the Hall current. Early systems used discrete components but more modern machines tend to use chips designed for the purpose. A stable d.c. supply is essential. Fig. 2 shows a simplified circuit. Most motors have either two or three sets of poles, with two coils per pole.

Construction

Fig. 3 shows the construction of a typical motor – the head drum motor used in the JVC HR7700, which has a discrete component drive circuit. The rotor magnet

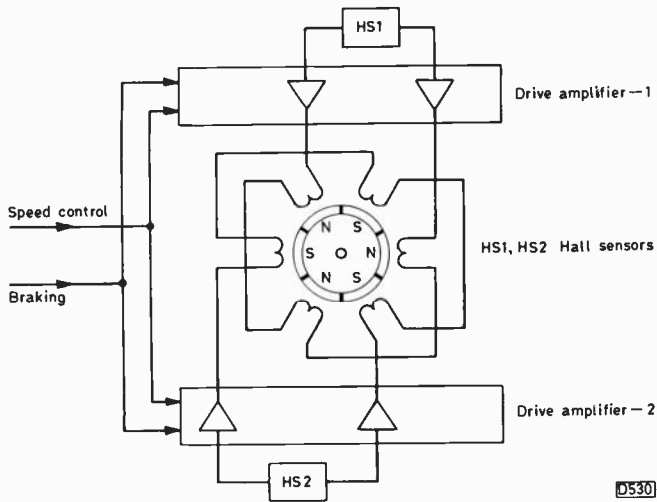


Fig. 1: General arrangement of a brushless d.c. motor and its drive amplifier system.

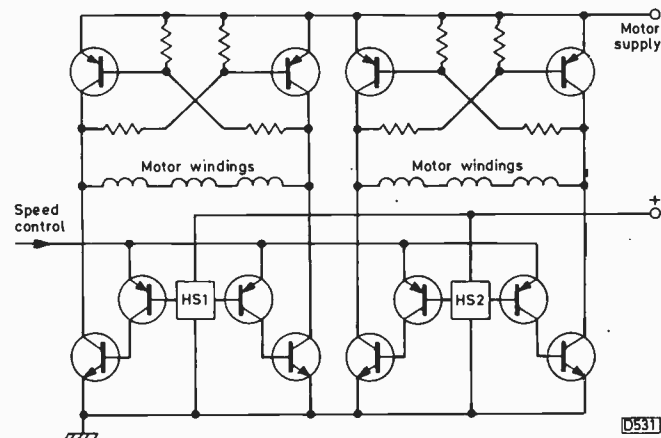


Fig. 2: Basic motor drive amplifier circuit, simplified.

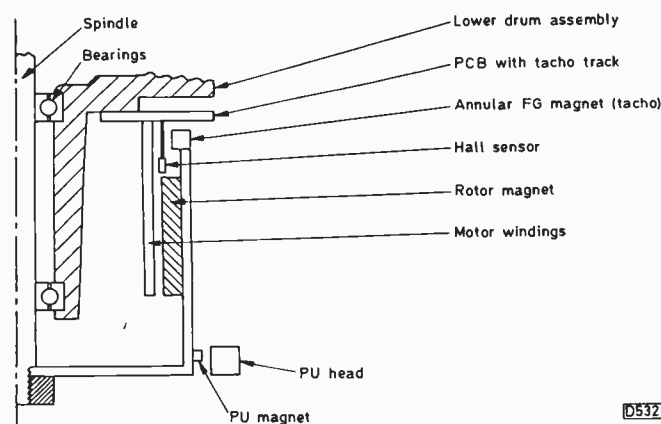


Fig. 3: Motor construction - cylindrical type.

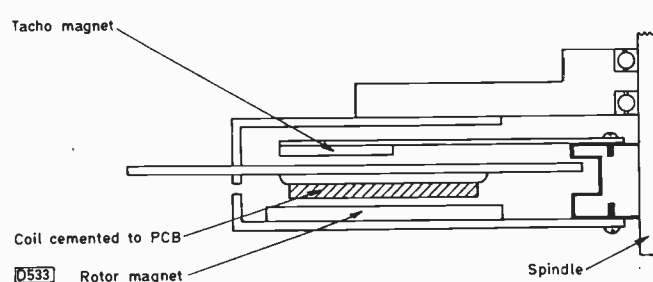


Fig. 4: Motor construction - disc type.

operates the Hall sensors, and there's a multipolar magnetic ring to provide a frequency input for the servo's speed control loop - this corrects for wide speed variations before phase correction is applied. The small external magnet on the rotor triggers the drum flip-flop: this signal is used in many parts of the machine.

Fig. 4 shows an alternative form of construction. This is used in Hitachi machines and results in a very flat motor. The rotor magnet is in disc form, some four inches in diameter and no more than an eighth of an inch thick. The windings are mounted with adhesive on a PCB which also carries the Hall sensors and the drive i.c. The plastic-ferrite ring that provides the capstan servo tacho signal, in conjunction with a printed sinewave track, is cemented to part of the rotor.

Faults

This tends to be a trouble spot: the cement occasionally gives way, the magnet becoming detached. The result is a rumbling noise, and if this is unheeded the magnet wears through the tacho track. The capstan then runs very fast. A rather curious effect can occur when this happens: touching the live side of the tacho circuit with a finger or screwdriver reduces the speed of the capstan motor to almost the correct value. This is obviously because we are injecting mains hum into the tacho line. Whilst maybe not the correct waveform, it's better than nothing! The unwary might think they've stumbled upon a dry-joint or something similar.

This fault can sometimes be cleared by removing the flywheel and PCB carefully, then cementing the magnet back on. If the capstan speed is out the PCB is of course open-circuit and it's too late to effect a repair except by bridging the track - this is rarely possible. Careful reassembly is necessary as the clearances in this type of motor are very small.

Other brushless motors suffer from different faults. The JVC type is occasionally noisy because particles have flaked off the magnet, possibly due to rough handling. In some motors the bearings are "preloaded" and the manufacturers do not recommend any dismantling. Preloading means that where we have two bearings on a spindle pressure is applied during assembly so that the bearings are forced together. When the motor is warm the spindle expands, giving the bearings the correct clearance. If one of these motors is assembled without preloading it may be noisy in use. The ball races in this type of motor are usually sealed and cannot be lubricated. Any solvent will get past the seals however, washing out the lubricant and rendering the bearing useless.

Short-circuit turns in one winding are not too unusual. The symptoms can range from fuse blowing to a sideways displacement of part of the picture (if the offender is the drum motor). This looks like a hum-bar but doesn't move. The symptom can also occur if one pole of the motor is not being supplied with current for any reason. Shorted turns will result in overheating of the driver device(s) and their eventual failure.

In Conclusion

This concludes our discussion of the electric motor. We hope that it has given readers an insight into the operation of this important component and that it will in some cases enable repairs which may not have been attempted previously to be carried out.

Band C Satellite TV Reception

John Standen (North East Satellite Systems)

We've been involved with satellite TV since the days when the only signals that were available were those in Band C (3.4-4.2GHz). This band remains a source of considerable interest to us. In the early days it was all that we could offer, and in terms of a sensible dish size it had to be the Russian Gorizont transmissions. Although our company operates in the commercial sphere we still find that a real enthusiast from time to time appears. He may be a radio amateur who has 11GHz equipment but finds that reception in this band is just too easy and wants something a bit more difficult. C band reception provides the answer. This article is intended for those who want something that approaches DX-TV, with the struggle for reception and the prize of receiving unexpected transmissions from the far corners of the world.

Just four years ago you'd have had to be rather well-heeled to consider reception of the very low-power transponders used in Band C. In those days Megaset advertised a 1m dish at £1,000: it would just about give you a picture from the Gorizont satellite, which is almost a power generator in the sky. It all came down to dish size and efficiency. A 30ft dish could give you some noisy but interesting results. Prices can now be reduced however, and with the latest technology it's possible to resolve pictures from low-power transponders that would have been considered impossible as signal sources four years ago. A few months back I decided to try out such a system. This enabled me to compare the results and costs of modern equipment with those of 1982.

The heart of any system is of course the dish. A poor large dish equals a very good small dish. We opted for a spun parabolic reflector. Being a single unit the efficiency is inevitably higher than that of a segment dish – and much higher than that of a mesh dish. To get a decent buying price we made a quantity purchase from the USA, but we were not happy with the US mount. So we produced our own, which we've tested and found to be stable in winds of over 50 m.p.h. The only problem is that the structure weighs about half a ton, so it's not cheap to transport.



With good dish gain the next requirement was to transfer the signal to the LNA via a scalar horn. Too many 4GHz horns today are of the polarotor type. This is fine if you want to receive linear, left or right circular polarity signals with some loss, but the C-band signals are so weak that such laziness will result in unacceptable

signal loss. The feedhorn required is of the basic throughfeed type, with a PTFE block to give reception of left and right polarity signals – for a linear signal, remove the block (there are no linearly polarised Band C signals available in Europe at present). Without the PTFE block, you'll lose 3dB of your left/right polarity signal.

As we were using a spun aluminium dish as opposed to mesh dish it was considered to be easier and more accurate to set up the dish using Ku-band (11GHz) signals. A Ku band LNB was fitted at the focal point and the polar mount was set to track from the Intelstat satellite at 27.5°W to the Intelstat satellite at 60°E. Horns and feeds were then exchanged and the polar arc was scanned at 4GHz, using a standard Ku-band receiver. The result was nothing, apart from the old favourite Gorizont which we could have picked up using a fire element reflector. So the system was working but producing nothing from the weak transponders.

Remember that these transmissions are intended for an Intelstat A station with a 33m dish. So what could we do with our little 2.7m terminal? Answer: reduce the bandwidth. All good quality Ku-band receivers that cover more than the required input bandwidth of the C-band transmissions incorporate a 70MHz outside loop. Into the loop we placed a 70MHz bandpass filter which was variable from 10-32MHz. With the filter in circuit the stations started to appear. Quite good reception was obtained from most 4GHz transponders, but in search of the best we changed the 85° LNA for a 55° LNA. And that's where the system rests today.

The dish tracks from 60°E to 60°W and although I have equipment to look at all the Ku-band transponders I spend far more time plucking very weak C-band signals from space. We receive Libya, Nigeria, Argentina, Saudi Arabia, France, Spain, AFRTS, Brightstar, CBS, ABC, CNN, international news feeds and Soviet transmissions from the 14°W and 57°W satellites. There's always something interesting at any time of the day or night. Nothing really superb, except for France and Gorizont. There's lots of noise but the signals are quite watchable and there's plenty of work left for the enthusiast to do by way of improving the reception using some of the many threshold extension techniques. Band C is an experimenter's paradise, where the unexpected becomes normal. It's the closest thing to DX-TV but with a greater surety of success.

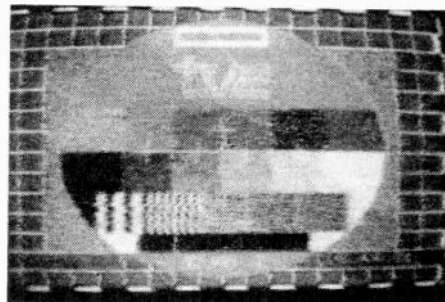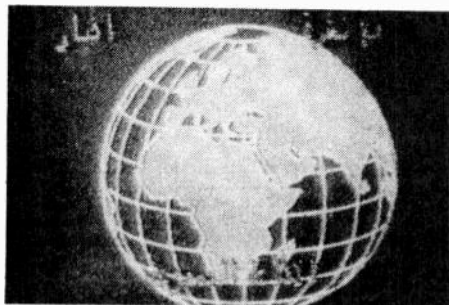

Examples of Band C satellite TV reception at Cropton, North Yorkshire using the equipment described in the article above. Left, Saudi Arabia; centre, Libya; right, Spain (TVE).

4GHz equipment is not readily available in the UK today. To cater for enthusiasts wishing to experiment we are stocking a range of systems (the range is greater than that we stocked in the old 4GHz only days) based on the 2.6 or 2.7m dish. The selling price is £1,335 plus VAT (terms available), the major problem being delivery as the dish/mount assembly weighs over half a ton. Being massive a large lorry is required to move it. There are fifteen systems and the ordering delay is up to two weeks. Refinements to the feed system give reception of the 11GHz and DBS bands.

Various transmissions are available in the 12.2-12.75GHz band. The Telecom-1 satellite provides many different French feeds, including lately Monte Carlo, also PAL feeds from France to the UK. There are also the French TV5 and TV6 network signals, some of which are

scrambled (using the discreet system). Most of the signals are clear however.

Tests on the French system here in Yorkshire have provided huge signals on a 1.25m dish. Further tests are to be carried out using a 90cm dish: from previous results we feel that this dish size will be acceptable. For those interested a small number of LNBS have been imported and are available at £198 plus VAT.

All the systems mentioned in this article are currently in operation at our Yorkshire base. Anyone who wants to see the full range of satellite TV from 3.4-12.75GHz in a polar arc is welcome to phone for an appointment – we can be open any evening and all weekend and enthusiasts are always welcome. For further details apply to North East Satellite Systems, Cropton, Pickering, North Yorkshire YO18 8HL (telephone 075 15 598).

Micro Clinic

Sinclair Spectrum

Although this machine seemed to be working normally, when an Opus disc drive was purchased the computer ignored it. The cause was traced to pin 27 of the CPU chip being stuck low. Replacing the chip provided a cure – pin 27 is the /M1 line and was telling the disc drive that something else was being loaded.

As the edge connectors appeared to have had plenty of use I was left wondering what had happened to cause the fault. As luck would have it another of these machines came along – with a blown ULA chip because the customer had pushed the computer into the disc drive and then switched on without bolting the two together. Now the slot in the Spectrum's edge connector can become slightly enlarged, and the Opus's key is rather thin. It's possible for the connectors to short together if the two are left free. After changing the ULA I checked for any other damage – and found that the CPU's pin 27 was stuck low. Problem solved! **R.B.**

Dragon 32

We've been doing a few repairs on these machines recently. The most common fault is failure of IC15 (74LS783), causing rubbish to be printed on the screen. These chips are unfortunately rather expensive. **R.B.**

Sinclair Spectrum

The following tales show how careful you have to be when working on micros. The computer had a faulty ROM and after removing it and fitting a holder for the replacement I found I had a dead keyboard. After checking the ULA chip I started to look for solder splashes, using an eyeglass. Not being able to find one, out came the trusty scope. After much running around the circuit it finally dawned on me that the /INT line was not going low enough for the CPU to scan the keyboard. There was a minute solder splash under the CPU's holder: it was removed by sliding a piece of paper under the holder. The /INT line was going down to about 2V. A lot of wasted time and slapped wrists!

The next machine had been "got at" in some way by a small boy, but we didn't know the exact details. Transistor

Reports on microcomputer servicing problems from Roger Burchett and Nick Beer

Tr4, the ROM and the CPU were all faulty, but the machine still wouldn't initialise when these had been replaced. Again out with the scope: data line 5 was found to be shorted to chassis. This once more meant an eyeglass search for something conductive. The cause was found under the ULA's holder: it looked like silver paper. Presumably this had got in during the said small boy's investigation, i.e. he took it apart while eating something wrapped in silver paper! Perhaps something easy now? **R.B.**

Sinclair Interface 1/Microdrive

The ULA in the interface can suffer if the interface moves about or is suddenly disconnected. The usual result is a "microdrive not present" message when a microdrive cartridge is loaded, and sometimes the Spectrum won't initialise due to a grounded data line. Just occasionally a ULA chip will overheat spectacularly, causing a crater in the case just above it. As the ULAs are expensive it pays to bolt the two machines together.

It's surprising how many odd faults will go away if the main board edge connectors and the microdrive/interface connectors are given a good clean. I cannot stress this point enough. In the long run it pays to examine each machine carefully after repair. **R.B.**

Sinclair Spectrum

Several of these machines have been brought in with a permanent black raster and white border. The cause is a faulty ULA chip. **N.B.**

Sinclair Spectrum Plus

A common problem with these machines is no colour due to a faulty encoder chip. We find that it usually happens when the "SN" equivalent of the LM1889 is fitted. **N.B.**

Acorn Electron

The customer had opened up this machine and diagnosed a faulty regulator as the 5V and -5V lines were missing (they're marked on the PCB you see). What he didn't do,

and what I always do to give myself enough room to work, was to disconnect the keyboard. The voltage lines then returned. There's an 0.47 μ F tantalum capacitor on the keyboard panel – it was leaking heavily. R.B.

Sinclair QL

The customer brought in her Microvitec monitor, saying that it wouldn't work with her Sinclair QL. She didn't think to bring the computer in! We connected a BBC

computer to the monitor, using the nearest lead to hand, but what we didn't know was that this computer had an intermittent fault somewhere in the RGB output section (it's normally used with a u.h.f. input only TV set). Alarm and panic (this is where I was brought in). The monitor was o.k., so the QL was sent for. After much head-banging we were able to duplicate the fault – the reset button was sticking in! This all involved a lot of running around, because the customer had humped along a 14in. monitor but not the little computer . . . R.B.

Teletopics

BOOM TIME

The first six months of 1986 was certainly a boom period for the UK radio and TV trade, as the latest figures from the British Radio and Electronic Equipment Manufacturers Association show. BREMA comments that the consumer electronics industry benefited from a boom in High Street spending, with deliveries of major products registering strong growth and a marked upturn in the second quarter. Total colour TV receiver deliveries during the period amounted to 1,633,000 compared to 1,388,000 during the first six months of 1985. Of the 1986 total, 982,000 sets were UK produced and 651,000 were imported – the comparative figures for 1985 were 933,000 and 455,000 respectively. It will be noticed that along with increased UK production there has been a marked increase in imports. This is put down to increased own-brand activity by the major High Street multiples, with rising imports from all the major Far Eastern exporting countries – South Korea has now become a significant supplier. A major feature in the large-screen receiver market was a six-fold increase in deliveries of sets fitted with FS tubes: by the end of the period the majority of large-screen sets were fitted with this type of tube. VCR deliveries rose to 812,000 from 555,000 in 1985. Imports of VCRs from Japan fell by 44 per cent during the period, to 239,000. BREMA has expressed concern that overall economic trends could mean that the surge in spending will not continue into the next year.

TV BROADCASTING

A decision by the IBA on the award of the UK DBS franchise is imminent as we go to press. The period of the franchise is to be extended from twelve to fifteen years in recognition of the substantial investment required and the risks involved. The government has also decided to increase the current ITV franchise period by three years instead of two – till January 1st, 1993. Ministers of the EEC have agreed to adopt the MAC transmission standard for European DBS broadcasting.

BBC's DATACAST SERVICE

The BBC's Datacast service is now in operation. This works in a similar manner to teletext, the data being transmitted during the field blanking period, but instead of whole pages the data is transmitted in the form of addressed digital data packages which can be picked up by a receiver whose decoder has been suitably programmed. This latter feature enables the service to be individually charged to users who have separate codes. Information providers send data to the transmitters over leased lines.

The service is on trial by the London Stock Exchange to transmit price information, by the banking communications service Euromoney Publications of London, and by the *Financial Times*.

PICTURE-IN-PICTURE VCRs

Hitachi is now selling in Japan and the USA a VCR that features a picture-in-picture facility. This is made possible by incorporating a digital memory using nine dynamic RAMs. Users can, by remote control, superimpose a smaller picture in any corner of the main picture. The picture can be off-air or via the VCR's video input socket and the two pictures can be interchanged. Either picture can be frozen. There are also special effects. For example the user can change the picture to a mosaic-like effect – this is done by reducing the 64 tones to as few as only eight. A strobe effect operates at field rates of up to 16 images a second. In the USA the machine is also being sold by RCA and Sears.

TV DEVELOPMENTS

An interesting new TV chip from SGS, type TDA8100, incorporates the complete field timebase, with direct yolk drive from pin 17, plus the sync separator and line generator circuitry.

A couple of new Toshiba TV sets released in Japan incorporate a field store to enable the line scan rate to be doubled. While this doesn't increase the resolution it does make the line structure of the picture less visible. The sets have 21 and 28in. tubes.

DIXONS LOGIK BRAND

As mentioned in this column last October Dixons have placed a substantial order for TV sets with Thorn. The sets are now being sold in Dixons' outlets under the Logik brand name.

JVC's GCR9 CAMCORDER

The JVC GRC9 camcorder, claimed to be the world's lightest and cheapest, is to be released in Europe this spring. It's a record-only version of the GRC7.

PHILIPS SERVICE VIEWDATA LINK

Philips Service has introduced a system called MOVIES (Multi-Option Viewdata Interactive Enquiry System) which enables dealers to pass orders, enquiries and messages to the Philips Service computer via the Viewdata network. A charge of £300 a year is made for this facility, but to encourage its use various benefits have been introduced including a reduced handling charge on orders under £50. In addition to placing orders, an update on orders placed can be obtained and part numbers, prices and availability can be checked. Technical and general information is also available, including service hints, de-

tails of recent modifications and technical assistance. Philips Service has also introduced floppy disc training packages.

GOLD MEDAL WINNER

Peter Richards of Crickieth TV, North Wales has won an international engineering competition. He led a strong UK contingent to the sixth Sony International Service Contest which was held in Tokyo on October 27th. Altogether 68 contestants from 24 countries competed for gold medals in six categories – four for Sony engineers and two for dealers. Peter entered the audio competition and completed his set task in 41 minutes, 13 minutes less than his nearest rival. Our congratulations to Peter, who from time to time contributes articles to *Television*.

IVAC 87 MOVES TO BRIGHTON

IVAC '87, the International Video and Communications Exhibition, will be held at the Metropole Hotel, Brighton, from 18-21 October 1987. While previous exhibitions tended to be dominated by equipment suppliers the 1987 event will be considerably expanded to include not only hardware suppliers but also duplicator manufacturers, production companies and dealers offering specialist products and services. There will be a complementary programme of technical seminars and workshops, aimed particularly at programme makers and production engineers.

PUBLICATIONS

The latest edition of Roger Bunney's DX-TV book has now been published at £5.95 by Bernard Babani (publishing) Ltd., The Grampians, Shepherds Bush Road, London W6 7NF. The book (order no. BP176) has been retitled "A TV-DXers Handbook" and is in a new, large format. It provides a comprehensive review of propagation modes and reception techniques (with numerous practical circuits), data on international transmission standards and channel allocations, and notes on related subjects such as off-screen photography. A copy of the 1987 Babani catalogue of electronics, radio and computer books can be obtained free of charge from the address above.

Those interested in vintage equipment may care to note that Chas E. Miller, who contributes regularly to these pages, is publishing a magazine entitled *The RadioGram* which is aimed at "all valve radio enthusiasts". The technical content includes complete circuits of individual sets and descriptions of unusual circuitry (and there's certainly been some of that over the years!). The magazine is published bimonthly and is available on subscription (£6 for six issues in the UK/Eire, £8.10 to Europe and to other countries by arrangement) from The RadioGram, "Larkhill", Newport Road, Woodseaves, Stafford ST20 0NP.

Electrovalue, the components by mail specialists, are now issuing an updated and currently priced catalogue three times a year. To obtain a copy send your request to Electrovalue Ltd., Freepost, 28 St. Jude's Road, Egham, Surrey TW20 8BR – you don't even have to stick a stamp on. Alternatively phone Egham (0784) 33603.

3D-TV

Peter Marlow writes: A new system of 3D-TV was demonstrated at a well attended meeting at the Institution

of Electrical Engineers on November 4th. The speaker was Dr. Reinhart Börner of the Heinrich-Hertz Institut, West Berlin, who had carried out the original research. Previous 3D-TV systems have required the use of special viewing glasses. With one system red/green filters are needed while another system uses time-sequential liquid-crystal filters. No special glasses are required with the new system however. The images are projected on to a specially designed screen from which they can be viewed directly in 3D: the method is not holography but simply that used for the 3D postcards that have been available for some years.

The basis of the new system is the "parallel lenticular" screen. This consists of many small Perspex strips of semicircular profile, placed side by side and running from the top to the bottom of the screen, with a highly reflective aluminium foil backing – the strips are not individual but are formed in a large Perspex sheet. The screen is laterally curved. A great deal of effort has gone into its design, mainly concerned with the radius, overlap and depth of the strips. The demonstration screen had been custom made in Hong Kong to a tolerance of 0.01mm.

Initial work with the system was done using 35mm slides. Six shots were taken sequentially to produce one complete 3D picture, with a camera mounted on an optical bench and each picture displaced slightly from the previous one. The six slides were then projected on to the lenticular screen, the projectors being placed in the same relative positions as the camera (exact placing is not critical). The result, called a panoramagram, provides the viewer with a 3D picture consisting of five continuously following stereo images as the viewing angle changes. Hidden objects appear as in a hologram. The use of six photographs virtually eliminates blind areas where viewers cannot see the 3D effect in certain places in front of the screen.

An improvised demonstration was given using two slide projectors and a one square metre screen. The effect was good, although the viewing position was critical due to the use of only two projectors instead of six.

A 3D television system based on the principle has been built at the Heinrich-Hertz Institut, using a five by two metre screen and six monochrome cameras/projectors. The cameras are mounted in a semicircular arc with a fixed focal point. A method is being developed to allow dynamic synchronised focusing. Development of a colour system is also in progress, but this will involve colour convergence problems.

Transmission of 3D-TV images would of course require HD-TV bandwidths, but a certain amount of pre-processing could reduce the bandwidth. Synchronised video recording should be possible, though expensive, making its application in aircraft trainers attractive now. Another use for the system is in 3D molecular analysis.

The lecture certainly demonstrated the technical feasibility of the system, despite certain practical problems. The cost of TV projectors would probably limit the use of the system, particularly in the domestic context. Development of a picture tube with a lenticular screen would seem to be the best way forward, though it would need to be large to give the 3D effect properly. I look forward to having one to set up in the workshop!

Meanwhile, back with polarised viewing glasses, 3D VHD discs have been launched in Japan by JVC. The system is to be marketed by other firms in the VHD group, including Matsushita, Sharp and Toshiba.

Tiny Tim's Testing Time

Les Lawry-Johns

Things had been slack for some months and Tim was beginning to get used to it, even to like it. Except for the bills that kept coming in.

Then, last Friday, the avalanche started. The first one came in at nine o'clock.

"I'm just off down town. Be back in half an hour. Don't want to spend more than ten quid. Ta Ta."

Before Tim could say "...off" the chap had gone, leaving neither his name nor any other information. So Tim wrote PIG on the sheet and started to lift the set on to the bench. Another car then pulled up outside and a bloke staggered in carrying a 26in. Bush set of the Z718 variety. He panted out his name and address and Tim felt sorry for him. "Call back at lunchtime" he said, after being told that the screen kept going blue before the tuner selectors failed. As the chap went out someone else came in. A music centre this time. None of the lights lit, one side was dead and the stylus was broken. Tim's eyes noted the Shure cartridge.

"Call back on Monday."

"But we want it for our party tonight."

"I'll try but can't promise."

Tim put the jobs in line and was about to start on the first when a woman came in with a white portable of the Thorn 1690 variety.

"I can't stop and talk about it. I want it for Sunday and the only time I can call to collect it is on Sunday morning at about ten o'clock. Do whatever needs doing. Bye for now."

She trotted off before Tim could say a word. His Sunday had gone for a Burton as usual. Oh well, mustn't moan.

Minutes later a large ITT FT110 was brought in. "Picture's very dull and it won't respond to the contrast."

Tim's mind said "beam limiter", but he didn't actually say anything. He didn't like the FT110, mainly because he'd not done a lot of them. And he couldn't remember how the beam limiter worked. But he knew the owner quite well. "Phone me tomorrow and I'll tell you all about it."

Left alone Tim started on Mr. Pig's set. It was a Pye CT200. He hardly had time to note the smashed tube base when another lady came in.

"Would you lift my record player out of the car for me?"

Tim went out to the blue Volvo estate and noted what appeared to be a radiogram standing in the back. It was one of the large, old HMV ones. A record player indeed, with a Garrard unit, twin speakers, etc.

Tim lifted it out while the woman chattered. "It was going all right except it wouldn't play the records right through, then it went dead. I said to my husband I don't want you mucking about with it, I'll take it to that little man down the road. They say he can do things all right and doesn't charge much. Not like some of these people do nowadays and you don't know what they get up to, do you? I think it's all wrong that people should take your things and interfere with them like they do, then charge you through the nose."

Tim put a tenner on the bill right away but he didn't say

much. "Pop in tomorrow" he suggested.

"Oh dear, I'll have to do without my Mozart tonight" she moaned. Tim took her name etc. and off she went, talking away to herself nine to the dozen.

The Pye's Problems

Back to the Pye. After a bit of a struggle Tim repaired the tube base socket and refitted it. When the juice was applied the heaters lit. There was a blurred raster and Tim realised he'd left the focus lead off. With that refitted the raster could be resolved but there was no picture or sound however much he fiddled with the tuner selectors. So he went down to the rear left side where the tuner joins the i.f. gain and filter unit. He removed the latter and resoldered all the contacts, noting that the one from the tuner had a track crack. Ah ha! This done the sound boomed out and a grossly misconverged picture appeared. This was attended to and he was left with a nice teletext message wishing him a pleasant day. Hardly had he finished when the owner appeared.

"Ah Mr. Pig, your set's ready after all."

"Name's not Pig, it's Sty."

"Nearly right sir."

"Actually I was only joking about calling back for it in half an hour. I've been told it's beyond repair. Thought you might give me a chit to that effect."

Tim got a bit angry. He switched the set on and showed the Sty man.

"Good lord, as quick as that. You must be a genius."

"I am but I don't let it show" said Tim modestly. He wrote the bill out and handed it to the Styman.

"Heavens. That much for such a short time?"

"Cheap for a genius, sir."

So off he went and Tim was left wondering. The set had been knocked over or off, and seeing the broken tube base someone had assumed that the tube was cracked. Oh well.

The Big Bush

Tim next turned to the big Bush. He soon found that it was a nightmare. First he took the tuner out and renewed the plastic nuts - one of the four had cracked open and was jamming the channels, as the blue ones do.

With the tuner refitted he could get a picture and was better able to see the effect of the blue flashing. He went over the blue drive from the TCA800 chip to the driver and output transistors and found that the voltages at all points varied with respect to the red and green channels. The most marked variation was at the collector of the blue output transistor.

Removing all three c.r.t. drives should have left a blank screen. It flashed blue. Tim's diagnosis was immediate and wrong. A heater-cathode short-circuit in the blue gun he thought. So he carefully removed the heaters' chassis connection and wired a resistor between the blue cathode and the heater. No change. It then dawned on him that the short-circuit was between the grid and cathode. His muddled mind recalled the adaptor he'd invented years ago to deal with a grid-cathode short in a tetrode tube by

shorting the grid to the cathode and transferring the drive to the first anode. "All right with a monochrome set but you can't do that with a colour tube with its three guns, you fool" he scolded himself. The things that go through your head when you're faced with a problem. Tiny Tim's trouble is his tiny mind. Not like you lot out there.

But he had to make up his little mind. He'd render the blue gun inoperative. He disconnected the supply to the blue gun's first anode. This left a slight blue haze in the centre. It wouldn't worry anyone but of course the picture was only a pleasant red and green, with no blue apart from the faint glow. The owner didn't complain and said he's seen enough blue to last him a lifetime...

Ribald Club Strikes Again

Next on to the bench was the FT110. Tim surveyed the displayed picture and again thought to himself "beam limiter" - and remembered that he'd been proposed as president of the Ribald Club (removal of beam limiters). He studied the tripler and its earth return circuit, then checked all the components here. Each one checked out perfectly so he moved over to the left-hand side and studied the transistors concerned with beam limiting - three of them, T212, T213 and T214. He checked these and the associated components - quite a few of them - and again each one checked out all right. He then removed the front panel to ensure that all the connections were good and that the controls were working. He refitted the panel and injected signals here and there from the final i.f. stage to the luminance delay line. The signals were lost somewhere between the distribution amplifier stage T211/T206 - the stage that provides separate feeds

to the a.g.c., luminance and chroma circuits - and the luminance delay line. The beam limiter transistors act on the distribution amplifier stage and Tim found that the voltages in the beam limiter circuit were wrong. He got more and more confused and after an hour or so he did something very naughty, he shorted out the first transistor in the beam limiter circuit, T213, by linking its collector and emitter. The picture was immediately restored to normal. He removed the short and made further investigations but still couldn't find anything wrong. He finally lost his temper, shorted T213 again and left it shorted. Ribald indeed.

Tim's Audio Department

He now turned his attention to the record player and heaved this on to the bench. On moving the pickup arm over towards the centre he found that it stuck before it got there. This was an old one indeed (the fault, not the deck). He took the turntable off and freed the small swing arms on the toothed wheel, removed them and cleaned the centres with easing oil. They now swung happily and the turntable was reassembled. He turned the unit on its end and removed the bottom cover. A fuse had gone though it didn't look like it. First bit of luck today thought Tim. It now played records and changed properly, so it was returned to the corner.

The Fidelity music centre was the one with the Shure cartridge, a fact that worried Tim a bit. He had the stylus in stock but they're costly. In fact when he'd got the whole thing working and the lamps fitted etc. the stylus cost more than the rest of the repair (shouts of traitor!), but they wanted it for that night and they happily popped down to the bank to draw out the money (why they didn't want to write out a cheque Tim couldn't say, but they paid cash and departed happily).

The Portables

Tim finally turned to the Thorn 1690 - and some other portables that had been brought in during the day. The 1690 gave him a stiff time. There were shorted turns in the line output transformer's e.h.t. overwinding. Tim selected an overwinding from the shelf - he'd sent for some a week before. He fitted the winding with care and confidently switched on. The result was a faint, small raster with poor sound. A check on the stabilised supply line showed that it was at 8V instead of the expected 11V. So Tim checked the regulator circuit thoroughly and noticed that it was running warm. He went through everything in this area and was getting more and more angry. At last he removed the new overwinding and prepared to give up the job. Then a thought struck him. He switched on again and the sound boomed out while the tube's heater glowed brighter. He couldn't believe it. Another overwinding was quickly fitted and a perfect picture appeared.

Tim said (shouted) some naughty words and the dogs hid away in shame. The cat licked her paws, having heard it all before. Tinker Bell appeared and announced that the vacuum cleaner had failed. Tim shouted at her as well but repaired it anyway. The Electrolux had shed a connection at the suppressor (remove four screws and take the top off to gain access). The connection was soldered back on and peace was restored. Tim then returned to the other portables and waded through half of them, the other half being deemed not worthwhile after an initial inspection.

The rest of the jobs had to wait another day. Tim hoped the whisky wouldn't be too cold.

TV LINE OUTPUT TRANSFORMERS	
PRICES INCLUDE VAT & CARRIAGE	
Delivery by return of post.	
BAIRD: 8290, 8752, 8773	12.00
RANK BUSH MURPHY	
A774 with stick rectifier	9.78
A816, T16, T18, Z712, Z715	10.35
T20, T22, T26, Z179, A823	11.50
Z718 Basic unit	13.50
DECCA: 1210, 1211, 1511	11.50
1700, 2001, 2020, 2401, 2404	9.20
CS1730, 1733, 1830, 1835	9.20
30, 70, 80, 90, 100, 120, 130	9.20
FERGUSON, THORN: 1590, 1591	9.20
1690, 1691, built in rect.	9.78
1600, 1615, 1700, 1790	P.O.A.
3000, 3500, 8000, 8500, 8800	P.O.A.
9000, 9200, 9300 series	12.00
9500, 9600, 9650 series	10.99
9800, TX9, TX10, TX90, TX100	P.O.A.
MOVIESTAR 3781, 3787	12.00
TX10 focus unit	10.87
FIDELITY: FTV12 mono	10.35
ZX2000 ZX3000	16.43
G.E.C. 2047 to 3135 mono	9.20
1201H, 1501H, 2114, 3133, 3135	9.20
DUAL & SINGLE hybrid col.	10.00
SINGLE STD solid state	12.00
SINGLE STD split diode	P.O.A.
INDESIT: 24EGB, 12LGB, 12SGB	10.35
WINDINGS	
TYNE: main winding	6.80
RBM: T20, T22, T26, Z179	6.33
WALTHAM: W125 eht winding	2.37
WALTHAM: W190, W191 eht coil	6.00
KORTING: hybrid winding	6.90
THORN: 8000, 8500, 8800 eht	6.70
ITT: VC200 to VC402	9.20
CVC1, CVC2 (FORGESTONE)	11.50
CVC5, CVC7, CVC8, CVC9, CVC20	10.35
CVC25, CVC30, CVC32, CVC45	9.20
CVC800, 1100, 1150, CVC40	P.O.A.
CVC1200, 1204, 1210, 1215, 2600	P.O.A.
PYE: 169, 173, 569, 368	9.20
CT200, CT200/1, CT213	10.35
725-731, 735, 737, 741	9.78
PHILIPS: 170, 210, 300	9.20
320 series	9.78
TX, T8, TX2, TX3 mono	P.O.A.
G8 and G9 Series	£9.20
KT2, KT3, series	9.20
CTX G11, K30, split diode	P.O.A.
BINATONE: 9909, 9860, 9488	P.O.A.
DORIC Mk3, Mk1	11.50
SONY KV 1400, 1612, 2000	P.O.A.
GRUNDIG: most models in stock	
NORDMENDE: 8290, Z206, Z306	P.O.A.
SANYO: 5101, 5103, 7118	P.O.A.
SHARP: C1851H, C2051H	P.O.A.
TOSHIBA: C800, C800B	P.O.A.
TANDBURG: 190, CTV2, CTV3	P.O.A.
TELEFUNKEN: most models in stock	
HITACHI: 1471, CPB260, 2501	P.O.A.
AMSTRAD: CTV2200	P.O.A.
Tidman Mail Order Ltd.,	
236 Sandycombe Road,	
Richmond, Surrey TW9 2EQ.	
Approx. 1 mile from Kew Bridge.	
Phone: 01-948 3702	
Mon-Fri 9 am to 12.30 pm &	
1.30-4.30 pm	
Sat 10 am to 12 noon.	

Low-cost Teletext Decoder

Part 2

Peter Marlow, B.Sc. (Hons.), C.Eng.

Part 1 last month dealt with the theoretical aspects of the project. This month we'll provide constructional details. Fig. 5 shows the interface board component layout, Fig. 6 the track pattern and Fig. 7 the hole drilling details. Board construction is straightforward: note that the microcontroller chip IC1 is socketed and that the regulators are mounted off the board, Veropins being inserted in their fixing holes. If you decide to use Veroboard construction keep the wiring around Tr1, Tr2 and IC3 as short as possible. Fig. 8 provides component pinning details while Fig. 9 shows the connection points on the VM6101 decoder panel.

Lastly connect pin 5 of the SAA5020 chip to pin 4 of PL5, via a link on the underside of the board, to provide the /AHS feed to the interface board. PL1 and PL3 are Pressac series 300 connectors which are not easy to obtain in small quantities: it's better to remove the sockets from the board and wire direct (it's unlikely that the board will need to be removed, unless Murphy's Law prevails). Connector 5 is a line of pins and is thus ideal for making direct solder connections. These changes should all be done carefully as the VM6101 board comes ready calibrated. Don't touch the components around the SAA5030 chip or the factory prealignment will be disturbed.

Work on the Decoder Panel

Some preparation work must be done on the VM6101 board before it can be used. Details are shown in Fig. 9. Reverse the polarity of the $1\mu\text{F}$ video input capacitor. Link pins 4 and 5 of PL3. Short out the two 470Ω resistors in series with the DLIM and /DATA lines. Connect pin 2 of the SAA5050 chip to the 5V supply at pin 1 of PL5 via a $4.7\text{k}\Omega$ resistor wired on the underside of the board.

Case Drilling

Drilling details for the case are shown in Fig. 10. Proceed as follows:

- (1) Stick adhesive boss mounting pillars (not the ones supplied with the box) on the inside top of the box (the top has long sides) on squares 1A, 1K, 5A and 5K.
- (2) Drill through pillars 1K and 5K and the top of the box with a 3.2mm drill and countersink holes for 6BA bolts.

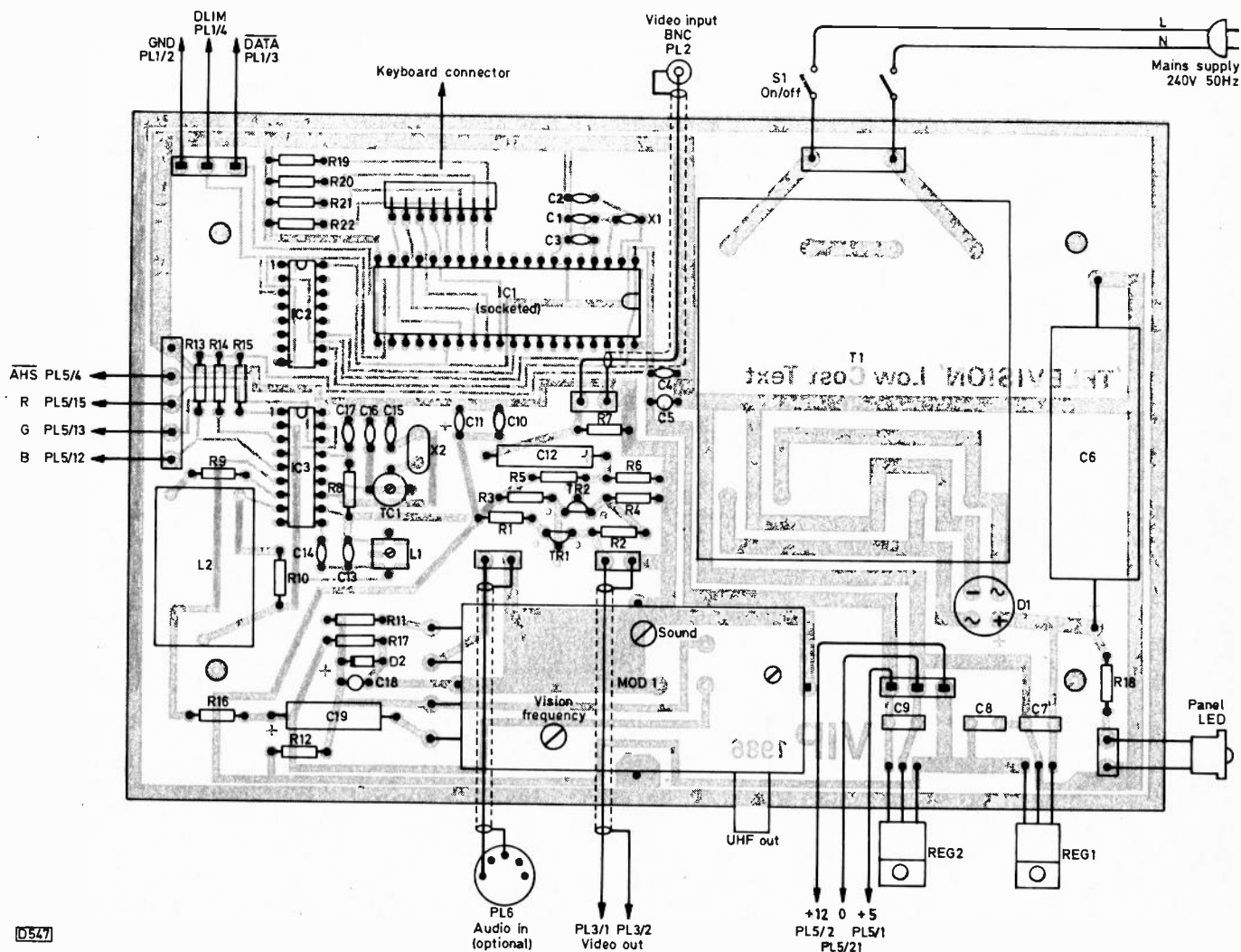


Fig. 5: Interface board - component layout and connections.

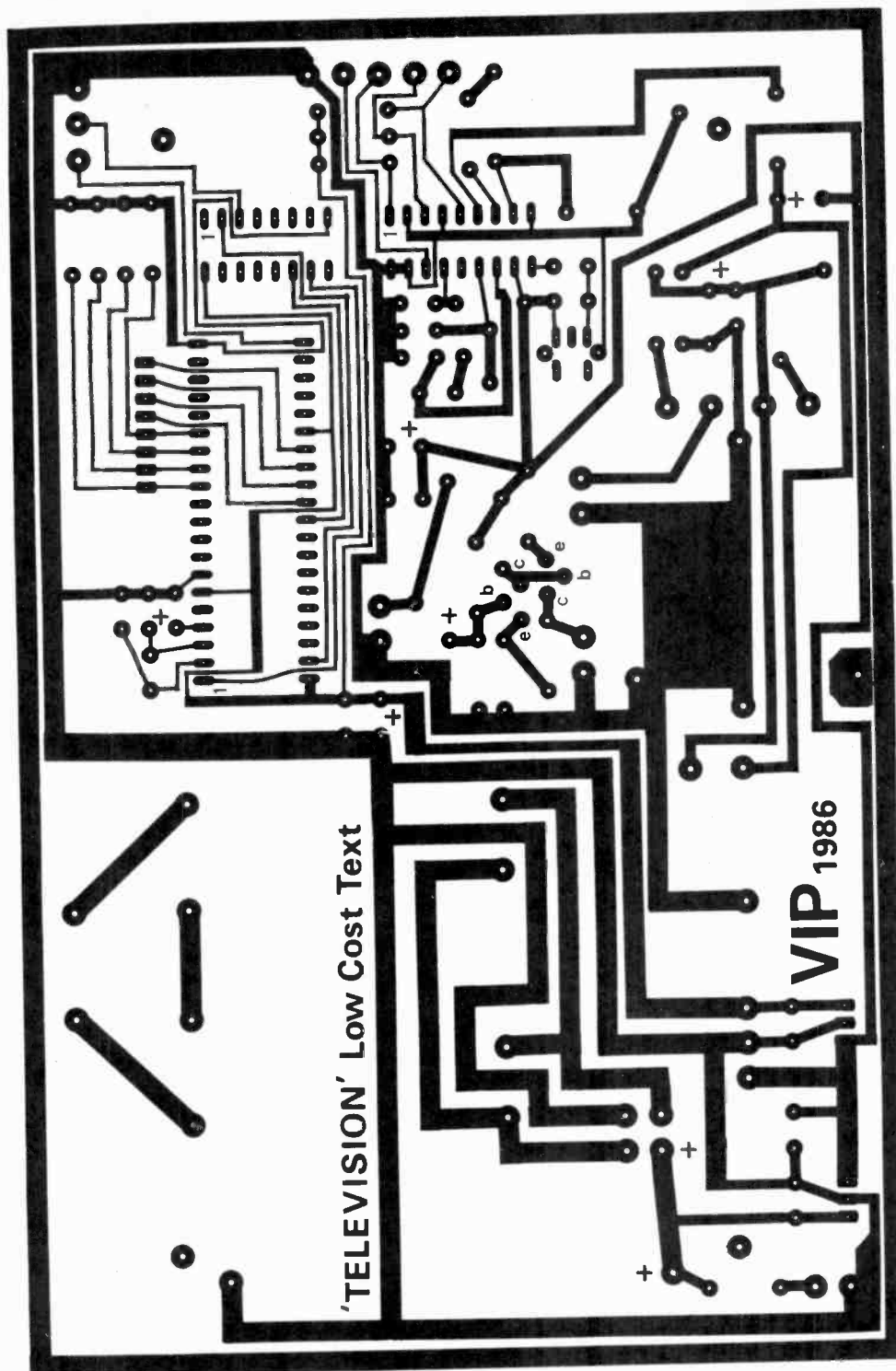


Fig. 6: Track pattern for the interface board. Scale 1:1.

(3) Make a 3mm slot for the keyboard lead at the front of the top of the box (dimensions as shown – the front of the box has a slight lip on its edge). Use either a drill and file or a soldering iron (avoid fumes).

(4) Screw the interface board to the boss mounting pillars with the 6BA screws at one end and self-tapping screws at the other.

(5) Stick the keyboard to the top of the box. Bring the connector through the slot to mate with the interface board.

(6) Drill the front (plastic) panel to take the switch and LED. As the layout is not critical details are not shown. Drill the back (aluminium) panel as shown: the only critical hole is for the u.h.f. output.

(7) Put boss pillars on the teletext board, using self-

tapping screws. Stick the teletext board on the inside bottom of the box. The pillars do not take up grid positions – the board position is not critical.

Wiring

Wire up the box following the details given in Fig. 5. Use screened cable for the video and audio signals, stranded cable for the other signals and power lines.

Setting up

To set up the teletext adaptor system proceed as follows.

(1) Check the wiring, particularly the connections to the

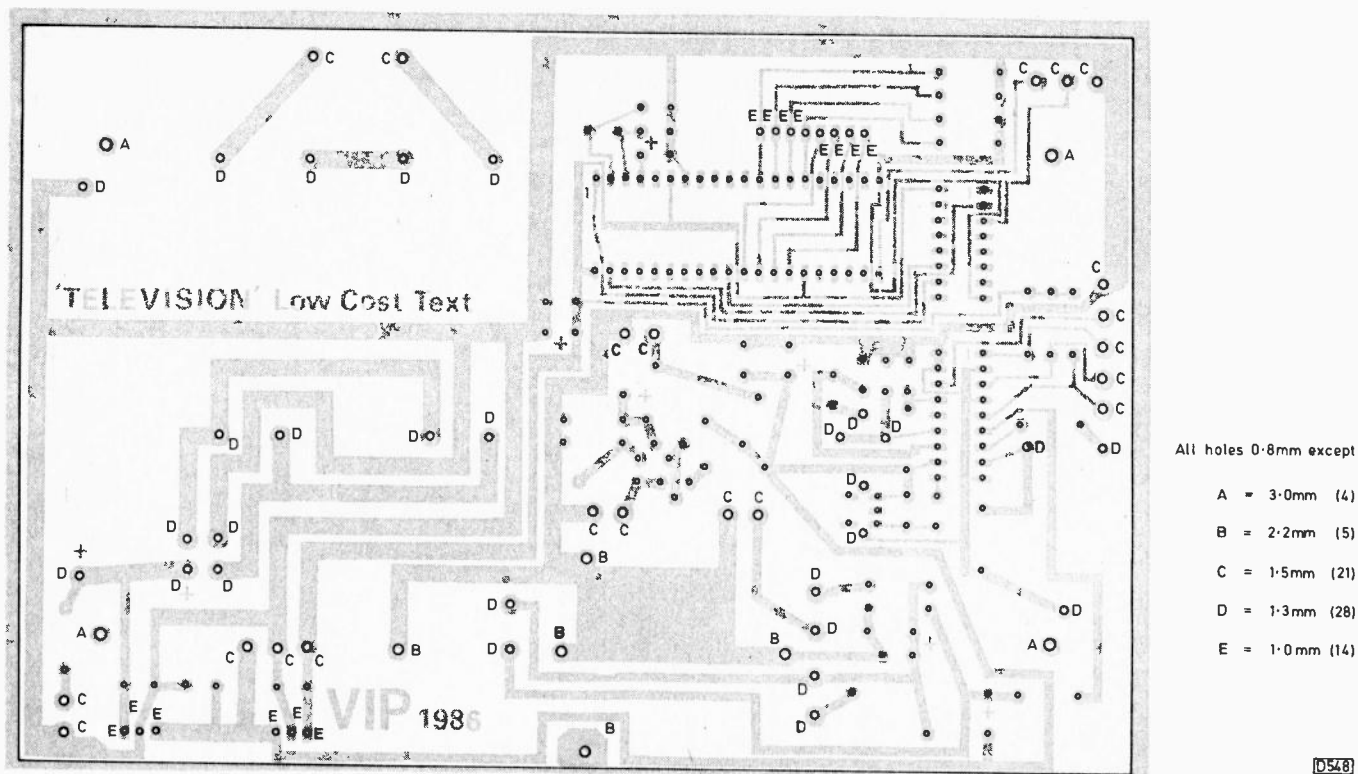


Fig. 7: Interface board hole drilling details.

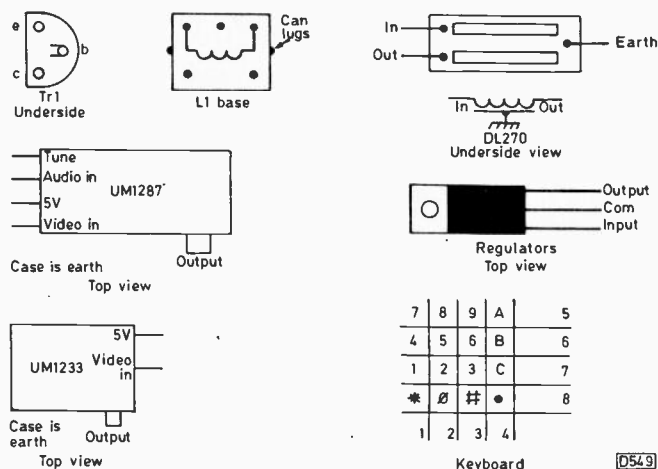


Fig. 8: Component pinning details. If the keyboard connector is viewed from the front of the keyboard pin 1 is on the left.

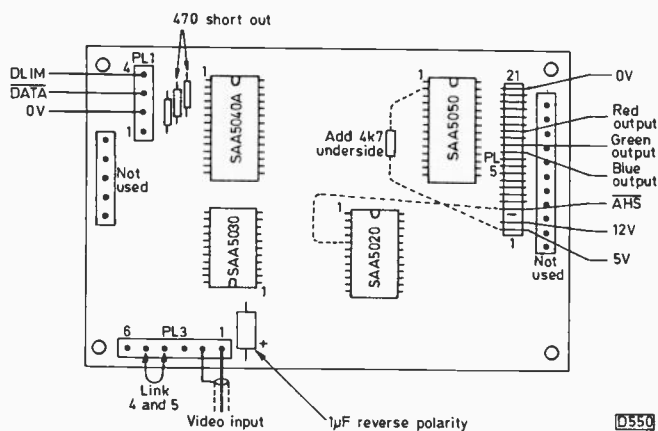


Fig. 9: Connections to the VM6101 teletext decoder panel and details of the modifications required.

voltage regulator.

(2) Apply mains to the unit and check the 12V and 5V lines. Switch off.

(3) Connect the VCR's auxiliary video output signal to the decoder unit. Set the VCR to give a BBC-1 output. Switch it on.

(4) Connect the unit's u.h.f. output to the TV set's aerial input socket, tuned to the VCR's output channel (ch. 36) – the UM1287 (or UM1233) modulator is already tuned to this channel. Switch on the TV set and the teletext

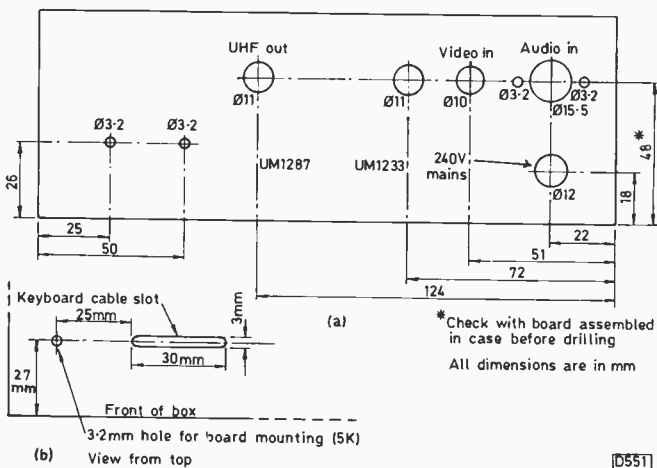


Fig. 10: (a) Back panel drilling details. (b) Drilling details for the case top.

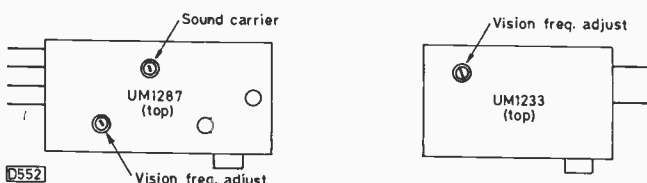


Fig. 11: Modulator tuning – core locations.

decoder unit. Wait for a picture to appear – Ceefax page 100.

(5) Adjust TC1 on the interface board to get a colour picture. If suitable measuring equipment is available, set TC1 for 8.867238MHz at pin 12 of IC3.

(6) Adjust the core of the chroma filter coil L1 for minimum interference and no smearing of letters. If a scope is available tune L1 for the maximum colour burst output amplitude at pin 6 of the TEA2000 chip (IC3). This should correspond with minimum patterning on the teletext display. If colour stability is poor, change C17 (see comments last month).

(7) Adjust the modulator's u.h.f. output by tuning the core (see Fig. 11) to a spare channel (avoid the VCR's output channel). Connect the splitter/combiner (see Fig. 3) in series with the VCR's output. The VCR's output should appear on one channel, the teletext signal on another, without interference.

(8) Inject a sound input. Adjust the modulator's sound core (UM1287 only) for the best signal.

Final Checks

Switch the VCR to different channels and observe the teletext picture. Try different page numbers and commands. As with all teletext systems the quality of the results obtained depends on the quality of the TV signal, especially on freedom from ghosting. Pages are frequently refreshed, so characters and letters missed the first time round should be corrected.

Warning

A word of warning. We have not, for obvious reasons, been able to try out the teletext adaptor unit with each and every combination of TV set and VCR – thousands of models have been sold. The TV set should present no problems, though we have found that line-frequency pickup can cause interference to the operation of the microcontroller with the adaptor on the line output transformer side of the set – moving the unit to the tuner side provides a cure. The i.f. strip in a VCR is not designed with teletext use in mind but we would not expect problems with modern machines using SAW filters. We've tried the unit with a number of VCRs and the only machine that failed to give good results was an old Sanyo model.

Other Possibilities

This decoder design is of course only one of many possibilities, low cost being the main aim. The decoder used in the Philips KT3/K30 chassis or the Mullard VM6103 (both Eurodecoders) could be used in place of the VM6101. In this case a small change is needed in the 8748's program. Superimposition and remote control could be explored and added as piggy-back circuit boards. Additional software could be written into the 8748 to provide extra decoder functions (the 8748 EPROM can be reprogrammed). A follow-up article will provide details on how to use the KT3/K30 panel which is now readily available from suppliers.

Acknowledgement

Finally I would like to acknowledge the help given by Mark Dawson in developing the prototype.

next month in

TELEVISION

● VERSATILE CRT TESTER-BOOSTER

This tube tester-reactivator was originally designed as a battery-powered unit for portable use. It could as well be built as a workshop instrument powered by the bench power supply or as a mains-powered unit, with the advantage that only a low-voltage mains transformer is required. The test/boost voltages are generated by switch-mode circuits: the heater supply is continuously variable from 0-12V and the boost voltage is in the region of 450V.

● THE PROBLEM OF TAPE DAMAGE

Christopher Holland on the causes of tape damage with VHS machines and a particularly awkward intermittent problem that arose with a JVC HR7700/Ferguson 3V23 VCR.

● MORE FUN WITH THE SONY KV1810

These sets are notorious for the expense that can be involved when the two gate-controlled switches used in the chopper and line output circuits fail. Conversion to transistor operation has been described before in these pages: this latest approach has the advantage that the chopper driver transformer doesn't have to be replaced while a low-cost, home-made line driver transformer is used. The two test-bed sets have worked impeccably for many months.

● COMPUTERS AND SERVICING

Following Vivian Capel's recent account of what a word processor can do for you Chas E. Miller describes the ways in which a computer can help with servicing – by storing information on data held, major components used in particular chassis, customer records and so on. The data recording program used by Chas is dBase II.

● SERVICING THE SANYO VTC5000 SERIES

John Coombes provides servicing notes on fault conditions experienced with the Sanyo VTC5000, VTC5300, VTC5400, VTC5600 and VTC5150 series of Betamax VCRs.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the February issue of TELEVISION (£1.30), on sale January 21st, and continue every month until further notice.

NAME

ADDRESS

.....
.....

TV Fault Finding

Reports from Richard Roscoe, D. Burke, Michael Dranfield and André N. Smith

Dead Mitsubishi

Mitsubishis with model numbers ending in 23B (e.g. CT1423B, CT1623B, CT2223B etc.) are now coming up to their second birthday and we are starting to get instances of them ceasing to work. The standby light is on but the set is otherwise dead. Up to now this has always been due to dry-joints on the line driver transformer T571.

More annoyingly, later sets with model numbers ending in 27BM (CP1427BM etc.) have in a few cases given trouble only a few weeks after installation, the set going completely dead. These are remote control sets with a separate power supply to drive the standby circuits on the ETS board, a secondary board mounted on the left-hand side of the cabinet. This power supply is protected by safety resistor R7A0 (1.2Ω, 0.5W) which goes open-circuit for apparently no good reason. It's a safety component, part no. 103P39801. **R.R.**

Hitachi CTP1455 Colour Portable

Last year we sold a batch of thirty Hitachi colour portables, Model CTP1455, to a local holiday camp. Our problems began almost immediately. The mains fuse FS901 began to blow in set after set. The mains rectifier D901, type RM11C, was found to be short-circuit and usually the regulator chip (STR4211) and the R2M crowbar zener ZD953 were also damaged. We at first assumed that the problem was due to mains surges: down here the mains supply tends to be like the local scrumpy – potent but pretty rough! As the number of failures increased however we contacted Hitachi who told us that the cause actually lay with D901. They recommend replacing it with two similar diodes in series (part no. 2335981), which is what we've now done to all thirty of them. **R.R.**

Toshiba Tips

Here are a couple of common faults we've had on the newer Toshiba chassis. There have been several cases of tuning drift on the 140E4B and 140R4B colour portables due to RA05 (33kΩ). These sets employ the now usual pulse width tuning arrangement and RA05 is the integrating transistor's collector load. Other, larger screen models with "4 series" numbers use similar circuitry, but in the remote control and text versions R4B and T4B the tuning is on a separate plug-in control board.

On the earlier "3 series" sets the type 202 tuner has been responsible for several cases of video streaking and picture jumping. Once seen it's unmistakable. In this respect the 202 tuner is definitely inferior to the later 204.

We had a similar looking fault on a brand new 222R5B but this time the cause was C833 (470μF) in the 13.5V supply. One of its solder joints had broken away from the copper track. **R.R.**

Rank T22 Chassis

A 22in. Murphy set fitted with the Rank T22 chassis had field collapse with, peculiarly, the bright horizontal line bouncing up and down an inch or so on either side of the

centre of the screen. Voltage checks in the field timebase showed that all was well except in the field charging circuit, which consists of the charging capacitor 4C10, the height control 4RV4 and its feed resistors (one connected to the 12V supply, the other to the 200V supply), and the discharge transistor 4VT10 (a pnp type with its collector connected to chassis). 4VT10's emitter was at only half a volt or so instead of several volts, though its base voltage was correct at about 4V. The 200V and 12V supplies were present and correct and the feed resistors were of the correct value. 4VT10 checked out o.k. and 4C10 was not leaky. So where was the voltage disappearing to? There seemed to be no other way it could go. We then noticed that the height control has a screen which is connected to chassis. This is not shown in the circuit diagram and we had overlooked it on our first inspection of the board. Sure enough by disconnecting the screen from chassis normal voltages and field scanning were restored. **R.R.**

Hitachi NP83CQ Mk II Chassis

The problem with an Hitachi Model CPT2248 – a remote control set fitted with teletext – was very weak field sync with severe line pulling at the top of the picture. Because of the effect of the obviously degraded sync pulses on the sound muting circuit the audio level was being intermittently reduced. We knew that the fault had been getting gradually worse over a period of two or three weeks so we felt it safe to ignore the HA11423 line and field generator chip IC701 which also contains the sync separator. The bias for this part of the chip is at pin 9 and consists of R748 (82kΩ), C747 (4.7μF) and R747 (100Ω). The voltage at the pin was correct at about 6V but when we checked the bias components "cold" we discovered that R748 had risen in value to about 500kΩ. Incidentally C747 was 2.2μF instead of the 4.7μF shown in the circuit diagram but it seemed to work satisfactorily.

The following day I discovered that the same resistor had failed in another CPT2248. This time the symptoms were no sound (muted) and inability of the autotuning circuit to lock on to the received signal correctly. The sync seemed to be unaffected! **R.R.**

Philips KT3 Chassis

This set wasn't doing very much and disconnecting plug M5 exonerated the power supply. The BU205 line output transistor was next checked and found to be o.k., showing no sign of leakage. The tripler was then disconnected, found to be faulty and replaced. Sound and e.h.t. were now present but there was no luminance. Replacing the TDA3560 colour decoder chip restored the picture and after checking the h.t. (which was correct) we were about to put the back on when the set cut out again. This time the BU205 needed replacement. Changing it didn't call for much by way of muscle power since it had never been properly tightened on the heatsink. This was probably a good idea at the time of the original assembly, considering the condition of the heatsink surface – definitely not of textbook smoothness, being a mass of abrasions that extended under the insulator. Smoothing the metalwork

and replacing the transistor and insulator (which didn't look at all well) restored normal operation.

Before the back could be replaced one other item required attention – the long tag from the heatsink was dry-jointed where it connects to the mother board. **D.B.**

Philips CTX-S Chassis

An impatient child had plugged this set in and switched it on just after a particularly nasty thunderstorm had rumbled by and out of earshot. The effects of lightning, especially on rural power lines, can travel a considerable distance: the result was a dead set in a short while. Unusually the surge limiter resistor was intact. But the mains fuse, rectifier, chopper transistor, excess current sensing resistors and transistors had to be replaced. This chain of failures has been reported in *Television* before. It seems that all the above mentioned items are vulnerable in thundery weather. **D.B.**

Grundig GSC100 Chassis

Tripping was the complaint with this set. Replacing the flyback thyristor provided a cure. **M.D.**

Philips KT3 Chassis

A thunderstorm can cause the mains fuse, surge limiter resistor and mains bridge rectifier(s) to fail without further damage to the set. If there's no h.t. after replacing these items check D454 and D455 (both type BAS11) which are situated near the line output transformer. They sometimes both go short-circuit along with the other items. **D.B.**

G11 Chassis – Pye Version

This one looked easy. The mains fuses had blown and the usual two rectifiers on the power supply panel had gone short-circuit. There was also a loose connection in the mains plug. Replacing the faulty items produced sound and an h.t. supply that varied. It appeared that something was amiss in the active smoothing circuit, but while checking in this area the original fault recurred. A spare power supply panel was fitted, after making sure that the h.t. fuse was of the correct value and type. This time there were no results as the line oscillator start-up resistor R2010 was dry-jointed. Resoldering this restored sound but no picture. This state of affairs didn't last long since a repeat performance was not long in coming. Two panels down, the h.t. fuse intact and a fault lurking somewhere . . .

The two power supply panels were repaired first. Both needed an identical set of components – mains bridge rectifier diodes D4091-4, beam limiter circuit components Tr4085/6 and D4090, and the trigger phase control transistor Tr4045. Not being too familiar with the Pye version of the chassis we first thought that some extra wires from the power panel were fitted and lying around somewhere to cause mischief, but this was not so. A check on the wiring from the power supply and line scan panels soon revealed the cause of all this bother. The loom that normally resides behind the metal support for the mains input panel was jammed between the metal and the panel. The wires appeared to be undamaged but there were a few small burn marks on the metalwork – VDR R1307 with its strong, untrimmed legs was probably the culprit.

Starting the set up with all items secured revealed the cause of the h.t. trouble originally encountered – the

presence of D6011, the second zener diode in the beam limiter circuit, fitted on the chroma panels in some earlier sets. This was leaky and after taking care of it the set worked normally. **D.B.**

Rank T22 Chassis

This set was dead with the 1.6A fuse (7FS1) in the power supply open-circuit. No shorts could be found so a new fuse was fitted and the set was switched on. When the raster appeared it was very dull with bowed edges and a bright centre foldover. The bowed edges suggested an EW modulator fault so attention was turned to the line scan panel. It took us some time to discover that 5C15 in the line scan/EW modulator circuit was faulty. It looked o.k. but a capacitance meter check revealed that its value had fallen from $1\mu\text{F}$ to only $0.3\mu\text{F}$. **M.D.**

ITT CVC8 Chassis

Some quickies on these sets:

(1) Touchy line sync but not total loss of line sync: change R393 and R394 (both $2.7\text{M}\Omega$) in the flywheel sync circuit.

(2) Weak sound: check for dry-joints on the audio coupling capacitor C75 (22nF).

(3) Intermittent loss of sound: check for dry-joints where the components in the audio output stage are earthed to chassis via the horizontal chassis support.

(4) A point to note is that faults in the line output stage can cause loss of line drive with the PL509 overheating. This is because at switch on the PCF802 line oscillator valve is powered from the h.t. line via R402 ($270\text{k}\Omega$): when the line output stage comes into operation however its supply is taken from the boost rail, via R403 ($180\text{k}\Omega$). Thus until the line output stage is operational the line oscillator stage is run at low power, the result being a great reduction in line drive. The symptoms look like loss of line drive. **M.D.**

ITT CVC30 Chassis

The problem with this set was crooked verticals: optimum adjustment of R905 (pincushion control) left the verticals bending inwards at the left and right side top quarter of the picture – adjustment for correct verticals at the top produced pincushion distortion. An additional symptom was slight change of picture width when the scene changed from a dark to a light one and vice versa. The latter symptom provided a clue. A picture breathing correction voltage from the e.h.t. circuit is applied to the EW modulator panel where it's smoothed by C901 ($22\mu\text{F}$) and applied to the base of the correction control transistor T901. C901 turned out to be open-circuit, replacement restoring a symmetrical picture without the width flutter on scene changes with a marked contrast difference.

On another of these sets the pincushion correction was wrong at switch on from cold, correcting itself within 30 seconds or so of warm up. R905 was found to be dry-jointed – the pins had not been properly cleaned during assembly.

Here are some other faults: Intermittent loss of colour was traced to poor contact between the pins of the TBA540 i.c. on the decoder panel and its holder. Intermittent loss of height with a bright white line across the top of the picture was traced to dry soldered joints between the mother board and chassis lugs. Trip operation followed by shut down was traced to EW modulator diode D24 (BY223) being short-circuit. **A.N.S.**

Long-distance Television

Roger Bunney

October was relatively quiet following the excellent tropospheric openings during late September and early in the month, though there was some sporadic E reception. Activity tends to fall during the winter months and for Band I reception we have to rely mainly on meteor shower activity. Sporadic E propagation often occurs during mid-December however and it's well worth keeping an eye out over the period December 10-30th. The relatively poor conditions are reflected in this month's rather bare log.

- 7/10/86 +PTT (Switzerland) ch. E2; RUV (Iceland) E4.
- 8/10/86 +PTT E2; RAI (Italy) IA, B; CST (Czechoslovakia) R1.
- 9/10/86 ARD (W. Germany) E2; RAI IA; JRT (Yugoslavia) E3, 4; TVE (Spain) E2, 3.
- 14/10/86 RAI IA; +PTT E2.
- 15/10/86 DFF (E. Germany) E4.
- 16/10/86 TSS (USSR) R1, 2; SR (Sweden) E3, 4; TVP (Poland) R2; CST R2.
- 17/10/86 TVP R2; SR E4; RUV E4.
- 19/10/86 RAI IA; +PTT E2; CST R1, 2.
- 21/10/86 TVE E2; TVE-2 E2; RAI IA; +PTT E2; CST R1, 2; ORF (Austria) E2a; TVP R1, 2.
- 28/10/86 TVE E2, 3.
- 30/10/86 RTP (Portugal) E3.

The above loggings cover SpE reception in the UK. Minor auroras were noted in Scotland on the 20th and 21st. Unfortunately I'm still without access to equipment due to building work - I hope to resume activities towards the end of November. My thanks to Simon Hamer (Powys), Iain Menzies (Aberdeen), Dave Shirley (Hastings), Tim Anderson (Bexhill) and Bill Cotterill (Tipton) for sending in reception reports.

Ryn Muntjewerff (Beemster, Holland) has sent in details of his reception during the excellent late September tropospheric openings. His W. German reception log resembles the EBU station list! During the period Ryn logged TVP-1 chs. R9, 12, 29, 30; TVP-2 chs. R25, 35, 38; CST chs. R9, 10, 22, 31, 33, 36, 38; many ORF, SR and

American Forces transmitters, TSS (USSR) ch. R9 and some thirteen British Forces relays/transmitters. A remarkable log!

Adding Directors to Collinear Arrays

The stacked bowtie (collinear) wideband u.h.f. array, e.g. the Wolsey Colour King or Triax BB Grid system, is very popular for DX-TV reception due to its relatively flat response over the full u.h.f. bandwidth, its compact size - and its reasonable cost. The one disadvantage in comparison with the long-Yagi with X director assemblies is the lower forward gain from mid-band upwards. A long-Yagi may peak at 16-17dBd whereas the maximum gain obtained from the Colour King type array is around 12.5dBd. An attempt has been made recently in Poland to improve the performance of the standard four-bay collinear aerial by adding a boom with six director elements in front of each full-wave bowtie dipole. The director chain is cut to the top end of the aerial's bandwidth, i.e. ch. 68 for the UK but often around ch. 62 in continental Europe, giving a claimed 3dBd gain increase at the higher frequency end of the bandwidth. This would give a typical gain of 11-15.5dBd across the bandwidth. For comparison, the Fuba XC391 long-Yagi has a gain of 10.5dBd at ch. 21 rising to 16.5dBd at ch. 66.



An experimental collinear u.h.f. array of this type could be fitted with a set of director elements based on those used in a domestic UK group C/D Yagi aerial, though careful thought would need to be given to the support arrangements to ensure mechanical stability.

News Items

UK: There have been suggestions that a combined transmission authority will be set up and come into operation during the mid-1990s to maintain and operate the u.h.f. TV transmitter system at present run by the BBC and the IBA at common sites.

W. Germany: Changes have been made to NDR-1 regional programming. Network origination variations occur at 1800-2000 Mondays to Fridays and 1730-2000 on Saturdays (local time). Details are as follows:

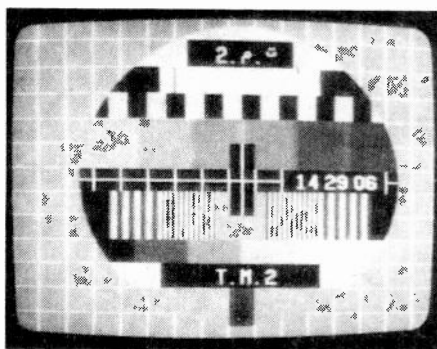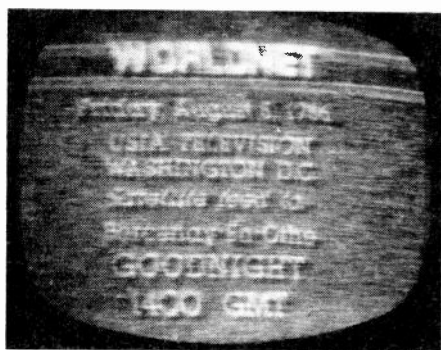- (1) NDR Hamburg transmits the "Hamburger Journal" on ch. E9. Test card indicates "NDR-1 Hamburg".
- (2) NDR Schleswig-Holstein transmits the "Schleswig-Holstein Magazin" from Flensburg ch. E4, Keil E5, Lubek E7, Heide E10 (vertical), Neumunster E28, Sylt E41, Lauenburg E46, Bungsberg E50 and Molin E53. The FUBK card identification is "NDR-1 Kiel".
- (3) NDR Niedersachsen transmits "Hallo Niedersachsen" from Visselhovde ch. E7 (vertical), Hanover E8, Harz E10, Lingen E41, Dannenberg E43, Stadthagen E47,



Left: Reception of the 11GHz Worldnet satellite downlink by Jaroslav Cerny in Czechoslovakia, using home-made equipment. Centre: RTM-2 Morocco ch. E27 received by Hugh Cocks in the Algarve, Portugal. The transmitter is thought to be near Tangier. Right: Portuguese Faro, ch. E28 pirate station received by Hugh Cocks.

Osnabruck E50, Cuxhaven E51, Aurich E53, Steinkimmen E55 and Hamburg E56. The former identification was "LF HS NDS" (see mystery ch. E10 signal mentioned last month). The current FUBK card identification is "NDR-1 Hanover".

Incidentally, other FUBK card identifications are "NDR 1 SH" (Schleswig-Holstein), "NDR 1 HH" (Hamburg-Hanzestadt), "NDR 1 ON" (East Niedersachsen) and "NDR 1 WN" (West Niedersachsen).

Various W. German local TV channels are being planned: a list will be included next month - indications are that high powers will be used in some areas.

Australia: Following the merger of SBS and ABC in January SBS will become "ABC One" and ABC "ABC Two". Proposals to restructure the commercial TV networks are causing controversy. The government suggested a single Queensland coverage instead of two, the NSW coverage to be reduced from three to two and the Albury region to be absorbed into the single Victoria coverage, the idea being to increase the viability of the regionals in the face of the large commercial networks by expanding their market bases. Following opposition to the plan it seems that the existing stations will be given a further monopoly for up to five years before any basic changes take place.

Transmitter Listings

Latest EBU listings of interest are as follows:

France: Carcassonne ch. L3 100kW e.r.p. vertical (this answers several queries about DX reception!), Limoges ch. L10 260kW e.r.p. horizontal. Both transmit TDF-4/ Canal Plus.

Jordan: The Suweilih ch. E3 and E6 transmitters are to remain on air.

Sweden: Hoerby SR-1 ch. E2 closed down on July 11th.

Gosta van der Linden has sent us the following list of projected French TV5/6 transmitters. The power figures given are e.r.p.

TV5 Network

Paris/Tour Eiffel	E30	12.5kW	Troyes	E29	60kW
Marseille	E32	90kW	Vannes	E58	100kW
Rouen	E59	10kW	Mont Landon	E47	50kW
Nantes	E21	50kW	Lens Bouvigny (near Lille)	E51	10kW
Toulon	E57	50kW	Beauvais (St. Just)	E49	100kW
Orleans	E52	20kW	Cherbourg	E35	20kW
Bourges	E21	100kW	Montpellier	E48	250kW
Niort	E38	500kW	Puy-de-Dome	E30	100kW
Rennes	E34	25kW	Saint Raphael	E36	80kW
Brest	E34	25kW	Metz/Luttange	E39	200kW
Reims	E53	25kW	Le Mans/Mayet	E32	150kW
Tours	E57	80kW	Mont Pilat	E59	250kW

TV6 Network

Paris/Tour Eiffel	E33	12.5kW	Toulon	E60	50kW
Marseille	E38	90kW	Lens Bouvigny	E54	10kW
Rouen	E62	10kW	Niort	E31 or L4	25kW
Nantes	E65	50kW			

Alex Gordon has sent us the following list of Saudi Arabian second network stations: Riyadh ch. E7; Shakra E25; Jeddah E12; Taif E8; Al Hada E59; Makkah E5; Jabal Shamse E45; Jabal Madafa E44; Al Baha E11; Damman E29; Hafr Al Batin E11; Al Houfouf E28; Abha E9 (vertically polarised); Al Qassim E6; Al Zulfi E7; Hail E7; Al Madinah E7; Jabal Silaa E11; Tabuk E8

UHF Signal Strength Meter Model SSMU1



The SSMU1 is a portable, battery-powered, signal strength meter for use in the setting up of aerials and distribution amplifier systems within the specified frequency range of coverage. The unit may be operated either with standard HP7 batteries or with rechargeable Ni-Cads, with the adaptor. Signal strength is measured in millivolts or decibels and indicated on a meter with 3 gain settings. The meter can be illuminated when required. To aid video and sound identification a low level sound source is built into the case. A carrying case is also supplied equipped with shoulder strap.

Specification

Frequency Range . . . Channels 21-69 (470-860MHz) . . . Varicap Tuned, measures 20µV to 40mV in three ranges, with an accuracy of ±4dB. Power source is 12 volts derived from 8 × HP7 batteries or 10 size AA rechargeable Ni-Cads.

PLANET SSMU1 UHF Signal Strength Meter £149.95
(Carriage & insurance on above item £3.00)

WOLSEY HG36 'Quick Silver' Multi-element High Gain (18dB) Aerial, available in Groups A, B and C/D £35.95

TRIAx 40055 'Professional' type UHF wideband amplifier, 25dB High Gain, minimum low noise figure 1.5dB; High signal handling 102dBµ £27.80

TRIAx 601/60 matching 24v Power supply for use with above amp £12.75

NEW-ANTIFERRENCE 'SILVER SENSOR' Wideband UHF Set-top Aerial, super sensitive with extra large elements for increased signal pickup £13.45

We are the specialist aerial company for all installations - domestic, fringe distribution and DX. Try our comprehensive Catalogue at 65p packed with all the latest equipment, please include SAE with any other enquiries.

All prices inclusive of VAT. Delivery 7-10 days.
ACCESS & VISA Mail and Telephone orders welcome.



AERIAL TECHNIQUES (T)
11, Kent Road, Parkstone,
Poole, Dorset, BH12 2EH. Tel: 0202 738232.



(vertical); Yanbou E8; Ar Ar E8; Sharourah E8.

From our Correspondents . . .

Jean-Louis Dubler reports from Seoul, Korea that the 1988 Olympic Games will be fully reported using the NABTS teletext system (a North American version based on the French Antiope system and currently used there by CBS and NBC). Samsung showed a NABTS adaptor with infra-red remote control, costing under US\$340, at the recent Seoul International Trade Fair. Interesting that Samsung have a design that uses the Korean alphabet. Dual-channel sound and teletext are to be provided on all Korean networks by 1988.

Jaroslav Cerny writes from Czechoslovakia that he has successfully received 11GHz satellite TV using a home designed and built receiver and a home constructed 1.8m dish. The receiver system uses the well-known Mitsubishi oscillator/mixer module (see *Television*, February 1985), with a 4.5V motor to provide remote tuning of the module's oscillator - it takes thirty seconds for complete rotation of the oscillator screw adjustment. All channels in the 11GHz band can be received, with noise present. Reasonable sound quality has also been achieved. A valved monochrome receiver is used as the display device.

Hugh Cocks writes from the Algarve, Portugal that he has now installed proper DXing aerials. Transequatorial skip/spread F propagation usually gives him Ghana ch. E2 from around 1600-1700 GMT, lifting to give ch. E3 video on good evenings. On some nights the signals appear at scanner level, i.e. very weak, while on other nights the signals cause overloading. Programmes start at 1800 and are preceded by a ten-minute test-card transmission - a large circle with four corner circles and the identification

"GBC" at the centre. The signals usually fade at 1900-1930. GBC local news starts at 1900.

Hugh comments that tropospheric reception from the Canary Islands is "odd". Pozo de las Nieves ch. E59/10 fluctuates between noise level and perfect colour over a one minute cycle. He can receive some eleven TV channels from the Canaries. Pirate radio and TV is active in the region. Faro ch. E28 transmits "pirated" RTP material and films taken from the Premiere downlink. A "potent" signal is received from another pirate, TV Algarve, to the west of Faro. RTM (Morocco) is well received, though the programmes are not what you might expect - the TV5 satellite downlink is transmitted on ch. E34 while ch. E37 also carries RAI-1. These transmitters are co-sited. The EBU list doesn't mention any Moroccan transmitters at present though several have been received. When the TV5 service is not available the transmitter radiates TVRO equipment noise!

John Roper (North Walsham, Norfolk) has written to us about early DX-TV. John built his first TV receiver, using a VCR97 surplus radar unit/timebase, an R1355 receiver and RF25 tuner, as soon as Alexandra Palace resumed transmissions in 1947. His aerial was an H type made from 1/2in. copper water pipe and electrical conduit fittings, with hosepipe for the insulation, all mounted atop a 39ft. wooden pole. Foggy nights were best for reception. Improved results were later obtained by using a 45MHz

Pye i.f. strip. More consistent reception was provided when Holme Moss opened, despite John's location being some 150 miles from either transmitter. Interesting that John has two working R1355s and has just constructed a timebase/display unit using the original VCR97 circuit. In 1947 John was 14: he comments that "you can imagine the excitement when the picture locked in and we sat in a shed watching the small green screen". Happy days indeed!

405-line Corner

John Stothart has for disposal to a good home, preferably someone with a 405-line TV collection, a working Sony CV2000 1/2in. video tape recorder complete with service manual - and some 405-line recorded tapes. If anyone is interested and can collect, drop us a line with s.a.e. and we'll forward the letter to John.

Help Needed

David Moller (King's Heath, Birmingham) asks to be put in touch with an enthusiast who would build a BATC project for him - a colour version of the video sync processor. Materials, information and financial reimbursement would be provided. For medical reasons David is unable to undertake constructional work. If anyone can help, please let us know.

Practical Active Deflector Systems

Roger Bunney

The November issue contained an interesting article discussing the basics and practicalities of an active deflector system to provide TV reception at an otherwise screened location. The following notes are based on experience gained during the design of a number of such systems and will, I hope, provide further guidance for anyone tackling this sort of exercise. With one exception, in all the systems I've been involved with the signals have been retransmitted on the same channels as received. Fig. 1 shows a typical system.

Aerial Systems

The use of a Yagi aerial at the deflector site was generally avoided, the Triax BB Grid/Wolsey Colour King type of array being used for both reception and transmission. The BB Grid has a particularly good reflector screen and consequently a good front-back ratio, which is essential for avoiding feedback (r.f. "howlround"). The Grid type aerial has a relatively flat response and will have a gain variation of typically 1dB across a given channel group. When used for transmission this type of aerial avoids the upper channel gain tilt typical with a Yagi array, so that a fairly level field strength on all channels should be available at the domestic receiving site. This avoids the need for channel equalisers with the insertion loss (and expense) they introduce. A typical Yagi aerial has a gain variation of at least 3dB across a channel group: it's suitable for use at the domestic receiving site where the higher h.f. gain assists in overcoming cable losses etc. that tend to rise with increased frequency.

The Grid type aerial is a wideband system covering the entire u.h.f. band. It might be thought that this could give

rise to problems with adjacent channel group signals but in practice no problems have been experienced. The perfectionist might however consider the use of a Labgear CM9034 u.h.f. group pass filter. This introduces an insertion loss of typically 1dB, with out-of-group signal attenuation of some 21dB. For optimum noise performance such a filter should be incorporated after the head amplifier at the receiving site - though the presence of interfering signals could make it preferable to include it in the feed to the head amplifier. If aircraft radar interference in the ch. 35-36 region is a problem a u.h.f. notch filter (RSPK4) can be inserted in line before any amplification.

With horizontally polarised signals the -3dB beamwidth of a single Grid aerial is typically 60°, which is far too broad. For reception at the deflector site two such arrays should be used, stacked side-by-side, giving a reduction in beamwidth to 30° at the -3dB points. This will also result in a much smoother polar response than with a Yagi array, due to the phase cancellation characteristics with signals coming from the sides. Stripline filters such as the Triax 721 (or 741 if a quad stack is used) offer minimal insertion loss while allowing efficient stacking for optimum gain.

Amplifiers

The head amplifier, assuming that the received signals are weak or noisy, should be a low-noise, low-gain, high signal handling capability device: the recently introduced Labgear CM721 with its 1-6dB noise figure (15dB gain) is ideal. A secondary amplifier such as the Triax wideband u.h.f. type with a.g.c. loop incorporated should be in-

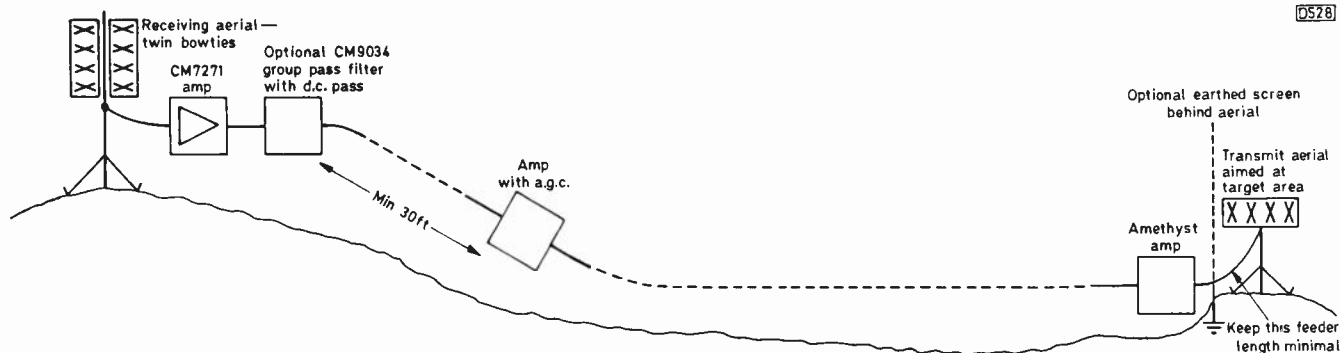


Fig. 1: Practical active deflector system. Note that the receiving aerial array is horizontally mounted, i.e. the bowties are horizontal, while the transmitter aerial array is vertically mounted.

cluded some 30ft. farther along the feeder. During high-pressure, anticyclonic weather conditions an otherwise fair to poor strength signal at the receiving site can rise to very high levels. Although, as noted, a head amplifier able to handle high signal levels should be used later stages can be pushed into severe non-linearity and saturation under such conditions. The a.g.c. loop amplifiers produced by Triax for masthead/outside use are designed to overcome this problem by reducing the gain when a signal reaches a predetermined level. This arrangement will maintain signal stability over a wide and varying signal range.

The amplifier cascade gain needs to be chosen with the feeder length between the receive and transmit sites in mind. If necessary a further low-gain repeater amplifier could be inserted.

The Wolsey Amethyst distribution amplifier used at the transmitting site provides d.c. powering at its input to supply 24V to remote amplifier(s). The 12V Labgear range can easily be modified for 24V operation. The Wolsey Countryman amplifier mentioned in the November article for use at the receiver site is undoubtedly a very high quality unit but does have a rather high noise figure: including a low-noise head amplifier prior to the Countryman will enable optimum signal/noise performance to be achieved.

Transmitting Site

The distance between the receive and transmit sites can be as little as 50m, though care must be taken to avoid feedback. If necessary, erect a close-mesh screen behind the transmit aerial – the screen should be well earthed.

We generally use a wideband Amethyst amplifier at the transmitting site, fitted close to the aerial system. A grouped version of the Amethyst is available: this provides a higher output – at a cost!

The Triax Grid type aerial was generally used at the transmitting site due to its flat response, minimum back radiation and forward beamwidth that can be tailored to suit the receiving area. Of great importance is to reverse the transmit polarisation with respect to the receiving polarisation. If a horizontally polarized signal is being received, the signal transmitted from the active deflector site should be vertically polarised. This will provide protection at the domestic receiving site where low-level signals received directly from the main station could otherwise give rise to line pairing, patterning or worse. In hilly areas there's always the possibility that signals direct from the main station will be resolved along with those from the deflector, so to avoid interference effects ensure that the polarity is reversed.

Apart from being of reversed polarity the transmitted

signal needs to be as strong as possible at the domestic receiving site. A typical transmit aerial system will consist of at least two stacked bowtie grids, perhaps four. A vertically mounted four-bay Grid/bowtie array will have a beamwidth of well below 30° – nearer 20°. Two such arrays stacked side by side, i.e. eight bowties in line, will severely limit the beamwidth, which could be a problem when the home receiving sites are dispersed. Use of an Ordnance Survey map with at least 2½in. to the mile is recommended to calculate the required beamwidth at the –3dB points for the transmissions. Stacking two vertical bowtie/grid arrays one above the other will maintain the signal beamwidth, limit the vertical beamwidth and increase the gain by nearly 3dB. Results should be acceptable over a distance of about a mile. Mount the transmitting aeriels a few feet above ground level and aim them at the valley/screened location to be served. It's wise to provide as high a transmitted signal level as possible to ensure that the domestic receiving aeriels provide a noise-free output for the sets.

General Considerations

An 18-element Yagi aerial should provide an adequate signal at the domestic receiving sites, the high-frequency tilt overcoming the greater losses with rising frequency. Recourse to a preamplifier with a less adequate aerial is not recommended as this can result in co-channel interference being visible.

When considering an active deflector, review all locations within the intended service area – and just outside (it's possible that someone with adequate reception just outside the intended service area of the active deflector will experience interference once the deflector is in operation).

Arranging for a power supply to a remote deflector site can be difficult. If a mains supply is available, few problems will arise. I've known a remote site to be d.c. fed from the nearest dwelling via GPO twin telephone wire (on the ground) – taking into account the quite considerable voltage drop on load. At another site – in fact a second deflector in a double-hop system – a battery trickle powered by a wind-driven generator and time clock arrangement was used.

All deflector systems should have DTI approval – though I suspect that more than a few systems are in use in hilly parts of the UK without the authorities being aware of their existence. From information that comes to hand from time to time it's clear that our colleagues in the southern parts of Ireland operate many deflector systems with great enthusiasm, high powers and transmission distances of several miles.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

15/80H	3.30	2SA940	1.81	2SC535	0.79	AF180	0.55	BA656	8.99	BC560C	0.14	BOX63A	1.96	BFY52	0.27	BYX71-350	1.40
15/85R	3.30	2SA940-2	2.14	2SC536	0.41	AF181	0.53	BA7100	10.85	BC635	0.36	BOY20	1.21	BFY79	0.49	BYX94	0.16
16039	0.79	2SA950	0.72	2SC537	0.53	AF186	0.53	BA841A	28.98	BC636	0.42	BOY81	1.18	BFY90	0.61	BY556	1.20
16181	1.04	2SA951	1.26	2SC605L	1.16	AF239	0.43	BA843	3.96	BC637	0.24	BF115	0.40	BLY49	2.20	BZ93C30	1.86
16182	1.04	2SA966-Y	1.16	2SC620	1.46	AF279	0.88	BA854	5.76	BC639	0.20	BF117	0.66	BR00	0.22	BZYR8 RANGE	0.10
16334	0.98	2SA999	1.36	2SC643A	1.54	AL113	1.36	BAV18	0.21	BC640	0.24	BF118	0.67	BR01	0.75	BZK61 RANGE	0.18
16335	0.94	2SB774	1.15	2SC668	0.67	AN115	3.98	BAV19	0.11	BC879	0.39	BF121	0.25	BR03	0.75	BZ79 RANGE	0.10
16446	0.98	2SB185	1.13	2SC681	4.40	AN155	1.89	BAV20	0.31	BC880	0.31	BF123	0.21	BR03	1.26	C106D	0.46
16600	1.38	2SB375	3.87	2SC682	1.88	AN206	2.58	BAV21	0.34	BCX34	0.40	BF127	0.13	BRC116	0.77	C106M	0.76
16802	1.27	2SB400	4.00	2SC684	1.65	AN208	3.55	BAW62	0.19	BCY70	0.30	BF137	0.29	BRC300	2.01	CA129	0.58
17052	5.61	2SB405	1.03	2SC693	0.63	AN210	2.28	BAX12	0.44	BCY71	0.21	BF153	0.58	BRC5296	0.77	C1304	2.55
17053	5.61	2SB407	3.24	2SC710	0.69	AN211	3.25	BAX13	0.11	BCY72	0.20	BF154	0.26	BRC6109	0.83	CA3089	0.83
17074	9.30	2SB449B	6.98	2SC711A	0.50	AN214Q	2.75	BAX16	0.11	BD115	0.46	BF157	0.33	BRC82	1.08	CA3090AQ	3.25
17089	5.35	2SB511	2.50	2SC717	1.28	AN231	14.65	BC107	0.13	BD116	0.70	BF158	0.18	BRC83	2.18	CA3094	2.20
17127	3.51	2SB54	1.39	2SC734	1.43	AN234	5.92	BC107A	0.11	BD124	1.31	BF159	0.18	BRC84	2.09	CA3131EM	3.12
17376	1.58	2SB546	3.75	2SC761-Y	0.95	AN236	3.78	BC107B	0.18	BD124P+KIT	0.69	BF160	0.31	BRX44	0.60	CBF16848N-071	1.56
17523	1.32	2SB56	2.80	2SC783	3.98	AN239	6.95	BC108	0.15	BD131	0.54	BF167	0.38	BRX49	0.53	CD4001	0.38
17524	1.32	2SB618A	2.22	2SC790Y	1.64	AN240P	1.52	BC108B	0.15	BD132	0.42	BF173	0.34	BRX93	0.69	CD4002	0.27
1N4001	0.06	2SB631	3.25	2SC828	0.28	AN241	1.71	BC109	0.12	BD133	0.53	BF177	0.35	BSS38	0.69	CD4008	1.35
1N4002	0.06	2SB643	0.61	2SC867A	3.05	AN245	4.49	BC109B	0.15	BD135	0.36	BF178	0.40	BSTB0140G	5.25	CD4011	0.29
1N4003	0.06	2SB669	3.67	2SC876	0.96	AN253	2.97	BC109C	0.12	BD136	0.26	BF179	0.36	BSTC0246	7.25	CD4012	0.24
1N4004	0.06	2SB681	3.96	2SC930	4.54	AN260	3.85	BC113	0.14	BD137	0.36	BF180	0.36	BSTC0233	7.25	CD4013	0.47
1N4005	0.08	2SB695	1.98	2SC935	0.13	AN262	1.98	BC119	0.36	BD138	0.46	BF181	0.32	BSTCC0143	3.07	CD4016	0.46
1N4006	0.08	2SB75	1.04	2SC936	8.66	AN272	7.92	BC126	0.23	BD139	0.34	BF182	0.34	BSTD1043	2.85	CD4017	0.82
1N4007	0.07	2SB774	0.72	2SC940	4.68	AN281	6.65	BC132	0.14	BD140	0.67	BF183	0.39	BSV57B	3.49	CD4020	1.23
1N4148	0.06	2SB819	0.89	2SD1128	2.90	AN295	5.52	BC135	0.14	BD144	1.70	BF184	0.43	BSW68	0.60	CD4021	0.39
1N4448	0.05	2SC1034	6.75	2SD1138	1.07	AN301	3.60	BC137	0.18	BD150	1.25	BF185	0.39	BSX19	1.29	CD4023	0.28
1N5401	0.14	2SC1050	5.06	2SD1273	1.25	AN302	3.99	BC138	0.34	BD157	0.67	BF194	0.14	BSX20	0.34	CD4025	0.64
1N5402	0.15	2SC1096	1.16	2SD1453	0.75	AN303	4.39	BC139	0.28	BD160	1.60	BF195	0.14	BSY52	0.50	CD4028	0.94
1N5403	0.16	2SC1104	3.98	2SD152K	2.64	AN305	9.47	BC140	0.45	BD163	0.71	BF196	0.17	BSY79	0.51	CD4040B	0.85
1N5404	0.15	2SC1106	4.54	2SD198	3.87	AN315	2.46	BC141	0.34	BD165	0.62	BF197	0.18	BT100A	1.61	CD4047	1.06
1N5408	0.25	2SC1114	6.75	2SD234	0.49	AN316	5.53	BC142	0.34	BD166	0.42	BF198	0.17	BT106	1.55	CD4049	0.46
1N914	0.04	2SC1116	4.95	2SD235	0.60	AN318	6.27	BC143	0.33	BD168	0.73	BF199	0.17	BT108	1.45	CD4052	0.75
1R3403	5.00	2SC1124	1.26	2SD24	2.29	AN320	5.47	BC147	0.08	BD175	0.60	BF200	0.37	BT119	1.76	CD4066	0.38
1S1555	0.20	2SC1129	0.34	2SD257	2.94	AN321	2.25	BC148A	0.11	BD179	0.49	BF218	0.36	BT120	2.17	CD4069	0.29
1S44	0.10	2SC1131	0.64	2SD292	2.59	AN322	5.85	BC148B	0.13	BD181	0.99	BF224	0.17	BT121	2.48	CD4070	0.66
1S5012A	0.81	2SC1158	3.33	2SD313	2.59	AN331	4.59	BC148C	0.11	BD182	0.99	BF227	0.65	BT123	1.98	CD4081	0.35
1S921	0.10	2SC1162	1.05	2SD325D	1.95	AN337	5.37	BC149	0.11	BD183	0.99	BF240	0.17	TBA970	3.06	CD4093	0.72
2N1303	0.38	2SC1172	2.22	2SD348	16.13	AN340P	1.17	BC149B	0.13	BD184	1.21	BF241	0.17	BT151-800R	1.15	CD4511	1.10
2N2219A	0.40	2SC1195	3.26	2SD350	5.20	AN355	5.98	BC153	0.14	BD187	0.53	BF245	0.50	BT160	2.42	CD4528	2.04
2N2222	0.38	2SC1212A	1.97	2SD350A	2.80	AN362	1.75	BC154	0.14	BD189	0.69	BF245A	0.52	BT18124	4.89	CD4556	1.47
2N2646	0.80	2SC1213	0.89	2SD353	7.50	AN370	3.95	BC159	0.36	BD190	0.69	BF245B	0.49	BU106	2.48	CD202A-M-8	1.55
2N2904	0.26	2SC1226	1.46	2SD389	2.41	AN5010	5.70	BC160	0.40	BD201	0.53	BF246A	2.52	BU108	1.50	CV12E	3.07
2N2905	0.43	2SC1293	0.90	2SD401	2.55	AN5111	2.92	BC161	0.28	BD202	0.60	BF255	0.20	BU109	2.65	CX095D	3.14
2N2906	0.38	2SC1306	1.98	2SD414	1.98	AN5120N	4.50	BC168	0.36	BD203	0.50	BF256	0.28	BU110	5.69	CI104	9.64
2N2926	0.15	2SC1316	4.10	2SD471	2.13	AN5132	4.39	BC169C	0.16	BD204	0.61	BF256LB	0.42	BU111Y	4.18	CX108	10.50
2N3053	0.27	2SC1317	0.87	2SD560	2.95	AN5250	3.98	BC170	0.16	BD207	1.79	BF256LC	0.42	BU125	2.46	CX109	7.96
2N3054	0.99	2SC1364	0.49	2SD588A	2.36	AN5435	3.08	BC171	0.11	BD208	0.34	BF257	0.34	BU126	1.55	CX130	8.76
2N3055	0.61	2SC1383	1.20	2SD600	3.25	AN5610	2.85	BC172	0.13	BD222	0.49	BF258	0.36	BU137	6.53	CX134	11.04
2N3442	1.56	2SC1391	2.45	2SD601R	0.65	AN5612	4.25	BC172B	0.17	BD225	0.49	BF259	0.34	BU205	1.08	CX136	11.49
2N3702	0.14	2SC1398	0.94	2SD613	1.03	AN5613	4.63	BC173	0.27	BD228	0.63	BF262	0.57	BU206	1.27	CX139	11.83
2N3703	0.14	2SC1413A	3.05	2SD621	12.85	AN5630	3.95	BC174B	0.27	BD229	1.05	BF263	0.57	BU207	1.65	CX157	4.10
2N3705	0.16	2SC1446	1.25	2SD636	0.55	AN5701N	1.66	BC177	0.20	BD232	1.00	BF271	0.34	BU208	1.82	CX158	4.10
2N3706	0.14	2SC1447	2.07	2SD639-R	0.85	AN6250	2.95	BC178	0.26	BD234	0.42	BF273	0.20	BU208/02	1.97	CX177	6.75
2N3707	0.16	2SC1475	0.37	2SD655	0.98	AN6300	7.00	BC179	0.26	BD237	0.47	BF274	0.20	BU208A	1.12	CX186	5.26
2N3711	0.11	2SC1505	1.00	2SD657	3.25	AN6310	8.74	BC182	0.09	BD238	0.39	BF324	0.35	BU208D	1.95	CX755	12.95
2N3717	2.04	2SC1514	1.41	2SD661A	0.80	AN6320N	4.28	BC182L	0.45	BD239	0.45	BF336	0.33	BU209	1.93	CD885A	6.85
2N3772	1.71	2SC1573Q	1.25	2SD731	2.45	AN6340	11.00	BC182LB	0.14	BD240	0.37	BF337	0.40	BU226	2.95	DEC1	2.20
2N3773	2.29	2SC1578	8.74	2SD773	0.33	AN6341	5.98	BC183L	0.11	BD241	0.39	BF338	0.44	BU326	2.00	DEC2	2.20
2N3819	0.42	2SC1583	1.17	2SD811	1.54	AN6342	1.61	BC183LB	0.26	BD242	0.39	BF355	0.49	BU326A	2.20	DS3486N	4.33
2N3823	1.17	2SC1617	3.89	2SD823	5.98	AN6363	16.00	BC184	0.13	BD243A	0.37	BF362	0.66	BU326S	2.20	DS3487N	4.33
2N3904	0.62	2SC675	1.41	2SD837	1.56	AN6371	9.24	BC184L	0.14	BD243C	0.79	BF363	0.60	BU406	1.49	E1222	0.40
2N3908	0.62	2SC1678	1.98	2SD841	3.65	AN6387	7.95	BC184LB	0.26	BD244	0.51	BF371	0.50	BU406D	1.79	E5004	0.28
2N4101	1.73	2SC1741	1.25	2SD856	2.25	AN6531	1.95	BC186	0.27	BD244C	0.79	BF391	0.25	BU407	0.62	E5386	0.25
2N4240	3.30	2SC1810	1.70	2SD857Q	1.84	AN6551	1.35	BC187	0.28	BD245C	0.99	BF417	0.84	BU407D	1.09	ES903	0.46
2N4444	1.73	2SC1815	0.66	2SD882	1.50	AN6552	0.68	BC204	0.16	BD246C	1.25	BF418	1.87	BU412	1.95	ES905	0.50
2N5293	0.50	2SC1826	0.65	2SD894	1.50	AN6610	2.40	BC207	0.14	BD253	1.05	BF422	0.29	BU426A	1.67	ESM3108P	4.15
2N5294	0.50	2SC1829	3.34	2SD898	5.45	AN6677	8.95	BC212	0.11	BD278A	0.80	BF423	0.52	BU500	1.95	FDN500	5.78
2N5296	0.49	2SC1875	5.85	2SK105H	2.15	AN7111	1.45	BC212B	0.26	BD317	2.60	BF450	0.35	BU508A	1.75	GC374	1.65
2N5297	0.50	2SC1881K	2.98	2SK152	2.95	AN7114E	5.94	BC213L	0.10	BD318	2.85	BF451	0.29	BU536	5.80	GD243	4.95
2N5298	0.61	2SC1893	3.02	2SK34	0.76	AN7115	2.55	BC213LB	0.15	BD3							

TEL 0902 712083 TELEX 338490

HA1374	4.80	LR3419	9.37	NE565N	1.33	SKE4F208	1.24	STK3042	11.05	TA7312P	2.45	TD62105P	2.50	TDA3560	5.25	TUA2000	8.98
HA1377	4.98	LR3471	9.37	NE645BN	3.35	SKE4F206	0.85	STK3044	5.75	TA7313AP	1.50	TD62104P	2.50	TDA3570	2.97	TV106	1.86
HA1389R	2.05	LU1141	7.27	NP1106	8.60	SKE4F210	1.24	STK1409	4.50	TA7314	1.50	TD62706P	4.90	TDA3576	7.09	TV6010B	1.97
HA1389	2.39	LU52012	5.95	DA202	0.11	SKE4G202	0.96	STK430	11.75	TA7323P	3.15	TDA1001B	2.31	TDA3590	5.79	U05G	2.14
HA1392	3.90	LU52011	14.95	DA47	0.14	SKE5F310	0.82	STK432	4.95	TA7325P	1.15	TDA1003A	2.25	TDA3591	6.45	ULN2204	11.45
HA1394	3.95	LUQ3112	12.37	DA91	0.09	SKS110	1.60	STK433	5.94	TA7328P	1.60	TDA1005A	2.11	TDA3650	7.50	UPA53C	4.94
HA1397	3.76	M193	12.75	DA95	0.12	SL1310	1.94	STK432	8.25	TA7339P	1.60	TDA1006A	2.22	TDA3652	5.44	UPC1003	5.95
HA1398	3.98	M21C	1.00	DC28	2.95	SL1430T	3.18	STK435	5.94	TA7340P	5.06	TDA1010F	4.25	TDA3651AQ	2.95	UPC1009C	6.32
HA1406	2.07	M23C	0.83	OC29	2.15	SL414	3.69	STK437	12.25	TA7607AP	13.90	TDA1011	2.98	TDA3651A	3.30	UPC1025H	1.24
HA1452	1.63	M293	9.15	OC36	1.28	SL432A	3.44	STK437	7.80	TA7611AP	4.80	TDA1011A	1.25	TDA3652	3.40	UPC1028H	2.00
HBF4003AF	2.48	M51102L	6.35	DC45	0.35	SL439	2.48	STK439	8.31	TA7622AP	5.94	TDA1028	2.45	TDA4050B	3.95	UPC1020H	0.77
HD14538	2.07	M5115P	5.24	DC75	0.44	SL471	4.70	STK441	11.28	TA7628P	8.98	TDA1034B	2.42	TDA4280	7.20	UPC1032H	2.82
HD38702-A2	7.45	M51203L	3.15	DC75	0.44	SL480	3.98	STK443	10.29	TA7629P	7.50	TDA1035S	2.95	TDA4290	4.47	UPC1042C	8.95
HD38750A53	8.95	M51231P	3.04	DN236	1.06	SL490	2.37	STK457	13.45	TA7630P	2.98	TDA1035T	2.55	TDA4400	2.27	UPC1156H	2.36
HD38750A-7	7.25	M5134-9341	4.13	DN782	1.98	SL901B	6.35	STK460	14.83	TA7640AP	1.55	TDA1037	1.95	TDA4420	4.02	UPC1158	5.84
HD4801A05	14.09	M51353P	5.25	DT121	1.45	SL918A	4.58	STK461	9.68	TA7672P	2.25	TDA1037D	2.08	TDA4422	8.32	UPC1161C	4.50
HEF4001BP	0.67	M51384P	4.50	PT6042	2.45	SN16861AND	6.35	STK463	11.53	TA7676P	2.81	TDA1044	2.62	TDA4427S	9.00	UPC1182H	1.85
HISH1010	8.59	M51394P	7.78	PT8504	4.98	SN16862AN	2.98	STK466	16.95	TA7676P	1.27	TDA1059B	1.38	TDA4440	2.87	UPC1181H	1.24
HISH1004	6.00	M5142P	5.49	R1039	2.19	SN16966N	10.25	STK466	6.32	TA7676P	6.45	TDA1059M	0.95	TDA4442	4.75	UPC1185H	2.95
HISH1002	9.50	M5144P	4.25	R2008B	1.33	SN29717N	7.19	STK501	5.74	TA7676P	1.74	TDA1060	2.60	TDA4500	6.30	UPC1188	6.95
HM6231	8.89	M51513L	2.55	R2009	1.98	SN29716N	3.66	STK502	9.48	TA7676P	4.85	TDA1082	3.25	TDA4600	2.84	UPC1213C	1.25
HM6232	4.85	M51515BL	3.23	R2010B	1.33	SN29715N	6.04	STK531A	12.67	TA7676P	9.48	TDA1151	1.22	TDA4610	4.80	UPC1212C	1.72
HM7103	4.05	M51517L	3.71	R2029	1.33	SN29723AN	1.85	STK7216	6.95	TA7676P	6.95	TDA1190	2.11	TDA4620	4.78	UPC1225H	3.25
HM9032	3.22	M5192	2.20	R2030	1.33	SN29723AN	7.30	STR1096	5.45	TA7676P	5.45	TAA700	3.96	TDA45500	4.78	UPC1230	5.24
HM9012	3.22	M5194AP	5.74	R2257	3.71	SN29770B	4.24	STR4090	11.98	TA7676P	11.98	TAA930	1.88	TDA45700	2.60	UPC1238	3.15
HM9015	3.24	M5231L	1.95	R2265	1.49	SN29770B	4.24	STR4090	11.98	TA7676P	7.85	TAA970	2.52	TDA4720S	2.25	UPC1263	3.45
HT4207	17.16	M53274P	1.33	R2305	1.18	SN29772BN	3.91	STR440	7.85	TA7676P	6.50	TAA110	0.73	TDA4770S	3.55	UPC1277H	5.85
HT4208	0.25	M54532P	2.15	R2322	0.59	SN29771BN	4.25	STR441	4.95	TA7676P	4.95	TA7676P	1.06	TDA4770S	1.33	UPC1278H	4.85
IN5401	18.11	M54544L	4.75	R2323	0.76	SN29791	1.57	STR453	5.66	TA7676P	8.16	TA7676P	1.06	TDA4770S	1.03	UPC1351C	1.81
IR2403	4.25	M58478P	6.75	R2354A	2.01	SN29798N	5.56	STR453	5.66	TA7676P	7.50	TAA120A	1.24	TDA4770S	1.33	UPC1350C	1.40
IR2405	4.25	M58485P	12.45	R2354B	2.01	SN29798N	0.44	STR454	5.66	TA7676P	7.50	TAA120AS	1.05	TDA4770S	1.03	UPC1353	7.85
IR3P06	2.95	MA06	1.07	R2443	0.88	SN7400N	0.34	STR6020	8.31	TA7676P	8.31	TAA120S	2.45	TDA4770S	2.45	UPC1355C	2.13
IR3P08	4.25	MA8001	0.82	R2461	1.50	SN7400N	0.65	T6029V	5.75	TA7676P	0.95	TAA120T	0.95	TDA4770S	3.16	UPC1362	2.98
IR94558	2.85	MA8003	1.16	R2540	2.31	SN7402N	0.36	T6035V	0.73	TA7676P	2.50	TAA120V	2.50	TDA4770P	4.25	UPC1365C	6.98
IS751	6.25	MB3705	1.98	R2540X	3.30	SN7404N	0.24	T6036	0.67	TA7676P	1.05	TAA120A	1.05	TDA4770P	7.45	UPC1366	7.25
IT2425	0.18	MB3712	1.85	R2615	0.67	SN7408N	0.27	T6037	2.11	TA7676P	2.03	TAA120A	2.03	TDA4770P	5.90	UPC1386	4.51
IZ0003GE	5.37	MB3713	1.69	RCA16029	2.01	SN7410N	0.27	T6044V	0.97	TA7676P	1.62	TAA120A	1.62	TDA4770P	7.45	UPC1387H	4.25
IZ00020GE	5.93	MB3730	3.25	RCA16600	1.38	SN74121	1.60	T6045	1.20	TA7676P	5.20	TAA120A	5.20	TDA4770P	2.90	UPC141C	3.75
K1749P	3.46	MC13002	3.55	RCA16802	1.08	SN7413N	0.37	T6049	1.45	TA7676P	2.80	TAA120A	2.80	TDA4770P	3.15	UPC1458	8.66
KA2101	2.92	MC1310P	2.25	RCA17074	6.60	SN74141N	2.65	T6052V	0.86	TA7676P	3.99	TAA120A	3.99	TDA4770P	4.88	UPC151C	2.95
KC581C	6.32	MC1327P	1.33	RCA17376	1.58	SN74151AN	1.51	T6058	3.08	TA7676P	1.10	TAA120A	1.10	TDA4770P	6.48	UPC2002	1.48
KC582C	3.97	MC1330P	1.69	RCA17524	0.83	SN74154N	1.27	T6059	3.05	TA7676P	2.90	TAA120A	2.90	TDA4770P	4.85	UPC200C	2.67
KC583C	5.54	MC1350P	1.61	RCA17523	0.83	SN74190	2.00	T9003V	1.25	TA7676P	2.39	TAA120A	2.39	TDA4770P	2.87	UPC324C	4.70
L200CV	1.69	MC1351P	3.96	RCA2060	2.00	SN7420N	0.34	T9005V	2.38	TA7676P	2.45	TAA120A	2.45	TDA4770P	1.95	UPC329C	4.90
LA1201	1.02	MC1352P	2.50	RGPO1-15	0.70	SN7430	0.49	T9011V	0.96	TA7676P	6.58	TAA120A	6.58	TDA4770P	5.08	UPC41C	4.18
LA1210	1.56	MC1357P	2.15	RG10	0.50	SN7440N	0.27	T9013V	7.49	TA7676P	2.60	TAA120A	2.60	TDA4770P	1.76	UPC558C	2.15
LA1230	2.87	MC1358P	1.55	RG30M	0.59	SN7472	1.54	T9014V	1.44	TA7676P	1.90	TAA120A	1.90	TDA4770P	2.11	UPC74A	5.11
LA1320	2.87	MC14001	2.40	RT402	0.58	SN7474N	0.44	T9016	1.20	TA7676P	1.84	TAA120A	1.84	TDA4770P	0.27	UPC74A	1.85
LA1352	1.75	MC14013	0.41	RT905A	2.38	SN7490AN	0.93	T9019W	1.98	TA7676P	1.45	TAA120A	1.45	TDA4770P	2.90	UPC544C	1.85
LA1357N	11.07	MC14433P	11.95	SI299	5.74	SN74LS26N	6.53	T9034V	1.45	TA7676P	2.33	TAA120A	2.33	TDA4770P	1.68	UPC566C	2.95
LA1363	7.25	MC14494P	2.15	SI75	31.48	SN76001N	1.65	T9035V	2.33	TA7676P	7.45	TAA120A	7.45	TDA4770P	1.75	UPC574	3.25
LA1364	3.02	MC14497	3.65	S2062D	2.07	SN76013ND	2.48	T9051	1.65	TA7676P	1.15	TAA120A	1.15	TDA4770P	1.75	UPC574C	2.40
LA1365J	3.44	MC14510BAL	1.10	S2802	5.54	SN76023N	5.15	T9054V	0.70	TA7676P	1.15	TAA120A	1.15	TDA4770P	2.99	UPC577H	2.58
LA1385	1.94	MC14511BCP	2.70	S2818	3.47	SN76023N	3.96	T9057V	0.70	TA7676P	1.40	TAA120A	1.40	TDA4770P	1.59	UPC577H	1.25
LA1387	7.60	MC14528BCP	1.10	S3702S	4.05	SN76033N	4.15	T9062V	0.49	TA7676P	1.60	TAA120A	1.60	TDA4770P	2.07	UPC580C	4.13
LA3155	1.25	MC1712	3.88	S409W	10.89	SN76115AN	1.61	TAG002	4.35	TA7676P	1.60	TAA120A	1.60	TDA4770P	2.07	UPC580C	1.34
LA3301	1.66	MC5192	19.50	S6080B	8.80	SN76131	1.92	TAG027	4.80	TA7676P	4.01	TAA120A	4.01	TDA4770P	0.75	UPC587C2	2.15
LA3350	1.43	MC7724CP	3.19	S6080B	5.17	SN76227N	1.33	TAG050	1.74	TA7676P	4.03	TAA120A	4.03	TDA4770P	1.85	UPC592H	2.85
LA3361	1.23	MC7818C	2.18	SA0063	5.17	SN76228N	1.90	TAG051	1.74	TA7676P	3.13	TAA120A	3.13	TDA4770P	0.41	UPC595	1.98
LA3365	3.98	MC81007-7	1.85	SA01006	1.75	SN76228N	3.27	TAG054	2.55	TA7676P	1.76	TAA120A	1.76	TDA4770P	4.95	UPC596	3.98
LA3390	4.25	MC8106-5/6	0.85	SA01020	4.76	SN76242	8.95	TAG060AP	4.60	TA7676P	2.60	TAA120A	2.60	TDA4770P	0.16	UPD1514C	8.95
LA4030P	4.20	ME0220/7	2.28	SA01025	4.40	SN76243	5.23	TAG061AP	1.27	TA7676P	1.85	TAA120A	1.85	TDA4770P	0.38	UPD2819C	4.98
LA4031P	3.20	ME0402	0.17	SA01024	2.81	SN76243	2.90	TAG069	3.13	TA7676P	3.27	TAA120A	3.27	TDA4770P	1.35	UPD4013B	4.00
LA4032P	2.35	ME0404/2	0.47	SA01075	6.25	SN76243	2.47	TAG070P	1.83	TA7676P	3.55	TAA120A	3.55	TDA4770P	3.46	UPD4066B	4.95
LA4100	1.25	ME0411	0.28	SA01121	7.44	SN76533N	2.95	TAG072P	2.57	TA7676P	2.90	TAA120A	2.90	TDA4770P	0.69	UPD553-164	19.25
LA4101	1.30	ME0602	0.26	SA01124	3.25	SN76533N	4.87	TAG073P	1.96	TA7676P	1.71	TAA120A	1.71	TDA4770P	3.71	UPD8049C-1	10.85
LA4102	2.81	ME06102	0.28	SA01130	4.99	SN76545N	3.47	TAG074P	5.86	TA7676P</							

Test Report: Hameg HM204-2 Scope

Eugene Trundle

In general test equipment has a long life. This is certainly true of oscilloscopes. Many scopes still in use date from the early seventies, when they were acquired to help with fault conditions experienced during the first colour receiver boom. Most of these scopes now have tired tubes and many of them lack the versatility required in today's high-tech world. Time perhaps to change to a more modern type?

The scope featured in this review was selected from the wide range produced by Hameg of East Germany, whose products seem to have come to the fore in the TV/video/audio servicing sphere. In a nutshell the HM204-2 is a mains-powered 20MHz 5mV (1mV at 5MHz) dual-trace instrument with a rectangular 8 × 10cm 2kV screen, a timebase ranging from 0.5sec to 100nsec/cm plus ×10 magnification, a variable sweep delay system plus variable hold-off time, a signal delay line to reveal the triggering edge, an X-Y display facility and a built-in component tester. It costs £365 plus VAT. An abridged specification is given in Table 1.

Evaluation

I gave my own bench oscilloscope a three-week holiday while I had this one. During this time the Hameg scope saw a great deal of TV and video work – also something of a CD player that was in for service at the time. In addition, some specific tests were set up to help evaluate the scope's performance. By the time it left I'd got to know it quite well!

The Y amplifiers worked well and were found to be able to handle a full-height display of a 20MHz sinewave signal. The slight shortcoming I noticed with a 1MHz squarewave was due to my probe rather than the scope. The signal delay line in the Y path made it possible to see the triggering pulse, typically the leading edge of a line sync pulse. I found the ×5 Y magnification facility useful with low-level signals: signals down to 500µV amplitude, e.g. a tape sound head output, could be examined with a straight-through probe – the reduced 5MHz bandwidth in this mode was no handicap. The "invert 1" and "add" facilities permit differential measurements in the Y1 and Y2 amplifiers, a useful feature though not one required every day – all common Y1/Y2 information is discarded in the display, which thus shows only the difference between the Y1 and Y2 signals. Using the "add" mode with both probes connected to the same point results in a maximum sensitivity of 500µV/cm.

The instrument's front panel bristles with green LEDs that indicate what's happening. A useful pair comprise the vertical overscan indicators: these are arrow-shaped and light up to show which way the trace disappeared off the screen – very useful in "lost-trace" situations.

A choice of test signals for calibration checking and setting h.f. compensating trimmers in probes is available at front panel sockets: 200mV and 2V doses of 1kHz and 1MHz squarewaves, the former for probe adjustment and the latter a stringent test of both probe and Y amplifier performance.

The X-Y facility provided is increasingly useful for servicing, notably for servo adjustment in CD players: at

the low kHz frequencies used here the internal phase shift due to unequal X and Y bandwidths is not relevant, though it must be borne in mind when attempting to set up Lissajous or similar displays at frequencies above 50kHz.

A good trigger performance is essential with the increasingly complex waveforms encountered when servicing modern domestic electronic equipment, particularly when only a small segment of a recurring signal has to be analysed. I found that the Hameg HM204-2 is well equipped in this respect, with provision for triggering from a.c. (normal), d.c. (very low-frequency and variable duty-cycle pulses), h.f. (high-pass filtered), l.f. (low-pass filtered, e.g. field triggering from a composite video/blanking/sync signal), or line (50Hz mains) signals. All these coupling modes worked well for me, particularly the last two for field-rate TV work and observing mains-rate ripple on power supply lines respectively. Once a trigger mode has been selected the signal can be routed to the trigger circuit from an external source or the Y1 or Y2 channels. Two useful features are present in the latter case: triggering can be from the unused Y channel in the single-trace mode, and alternate triggering from the two Y channels is possible, permitting the simultaneous display of two asynchronous waveforms.

Either the positive- or negative-going slope of the trigger signal can be selected and the level at which the timebase fires is set by means of a rotary control – pushing this knob switches to automatic (peak value) triggering, avoiding the need to fiddle with the level control when displaying simple repetitive waveforms. The "hold-off" facility can be used in difficult cases (the timebase triggering is muted for a preset period during the signal cycle). I found its main advantage to be the provision of a clear display of sections of complex pulse trains like NRZ (non-return to zero) serial data pulse trains.

Whereas the short, fixed Y-signal delay permits the timebase to be fired before the trigger edge is displayed, a very wide-ranging monostable sweep delay system is fitted: there's a seven-position switch and a multi-turn potentiometer. With these, the start of the sweep can be delayed after the trigger point by any period from 100nsec to one second. This system comes into its own for segment examination, for example the full screen width display of a single teletext line or a VITS pulse, the study of a single (stationary!) picture feature at some point along a TV line, or losing a preamble signal such as a framing code in a serial data pulse train. The status of the sweep delay circuit is indicated by an LED: similar indicators show when the timebase is being triggered, when the power is on and, in the single-shot mode, when the timebase is armed. Like many other features of this scope, the single-shot facility is increasingly useful in consumer goods servicing – in this case for the analysis of transient events, though you have to pay close attention to the screen.

I found that these comprehensive triggering arrangements worked excellently. It's essential to study the Hameg operator's manual if full advantage is to be taken of the facilities available. Even so, I've become used to the simpler and more reliable method of externally triggering the scope – this makes the timebase operation

independent of the amplitude, content and trace height of the displayed waveform. Virtually all the waveforms of interest in TV, video and related equipment are tied to field, line, colour subcarrier or clock rates and test points carrying these reference (trigger) signals are usually easy to find. I use a third probe (1:1) plugged into the BNC trigger input socket and get a rock-steady display – and a baseline on the screen when the signal probe falls on the floor . . .

The timebase section worked most adequately. There are 21 preset sweep speeds between 0.5sec/cm and 100nsec/cm, expandable (at the expense of brightness) to 10nsec/cm by using the $\times 10$ magnifier. Fine control is by means of a vernier potentiometer, which brings the minimum scan speed down to 1.25sec/cm. I found that the calibration accuracy was better than 2 per cent and looked in vain for any visible retrace.

An oscilloscope is only as good as its display system, and the price of an instrument closely mirrors the goodness of the tube fitted. In the medium price range into which this model fits, a 2kV tube is par for the course. This is perfectly adequate for most purposes, giving a bright and reasonably sharp waveform display. In the "strobe" modes however, such as the segment observation and sweep-delay situations previously mentioned, the duty cycle of the scanning spot is very low, and since the eye responds only to the average brightness of the image the perceived brightness is correspondingly low. When the brightness control is advanced to compensate, the focus performance suffers. As a result a display of one test data line (duty cycle 1:625) or a single vertical line of a test pattern (duty cycle typically 1:200) will be quite dim and possibly ill-defined. The only solution to this problem is to spend a great deal more money on an oscilloscope with a very high post-deflection accelerating potential (say 10-20kV), since this will have a greater brightness reserve to cater for such situations. That said, the display on this Hameg review model had shocking astigmatism in all the display modes. Adjustment of the internal astigmatism preset produced a great improvement, but the focus performance at high brightness levels and in the strobe

Table 1: Brief specification.

Operating modes: Channel 1, channel 2, channels 1 and 2 alternate or chopped at 500kHz. Sum/difference: channel 2 \pm channel 1. X-Y mode.

Y amplifiers: Bandwidth d.c.–20MHz (–3dB). Rise time 17.5nsec. Deflection coefficients 5mV/cm to 20V/cm in 12 steps. Accuracy \pm 3%. Times five magnification at d.c.–5MHz (–3dB). Delay line fitted.

Timebase: 100nsec/cm to 0.5sec/cm in 21 steps. Vernier 2.5:1. X magnification to 10. Hold-off maximum 10:1. Trigger auto/normal, \pm slope from sources ch. 1, ch. 2, alternate chs. 1/2, mains, external. Coupling a.c./d.c./h.f./l.f.

Sweep delay: 100nsec to 0.1sec/cm. Variable fine control 10:1 to 1sec.


X deflection: Bandwidth d.c. –2MHz (–3dB). Input via ch. 2.

Component tester: Maximum test voltage 8.5V r.m.s. (open-circuit load). Maximum test current 24mA r.m.s. (short-circuit load).

General: 8 \times 10 internal graticule with 3-step illumination. 2kV e.h.t. Z modulation TTL, two-state: + = bright. Calibrator inputs 1kHz and 1MHz switchable: rise time <5nsec at 0.2V and 2V \pm 1%.

Operating voltage 110/125/220/240V a.c., 40-400Hz. Power consumption 41W.

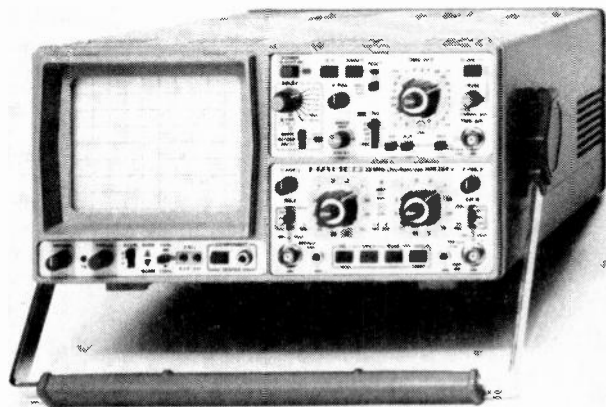Weight 7.7kg. Cabinet dimensions 285 (w) \times 145 (h) \times 380mm (d). Colour brown/grey. Lockable tilt handle/stand.



The Hameg HM204-2 oscilloscope.

modes remained unspectacular.

On the credit side, the internal graticule and its illumination system are very good indeed for both parallax-free observation and for photography. If I had the instrument I'd certainly buy the matching HZ65 viewing hood.

My enforced entry to carry out the astigmatism adjustment gave me an opportunity to assess both the internal construction of the scope and the recalibration/setting-up instructions (also layout and circuit diagrams) in the manual. Both were excellent. The instrument's circuit is conventional and reliable: it uses easy to obtain components like BC557 and BF458 transistors, 78 series regulators and 74 series logic chips. While I'm blowing the trumpet, I'd commend the clear and logical front panel layout, the tilt handle/stand and the dummy three-pin "socket" at the rear for stowing the mains lead. For field work however the front of the instrument is somewhat vulnerable without a hard protective cover – the HZ46 carrying case is an optional extra.

Component Tester

An unusual feature of this and other Hameg scopes is the component tester. This works by applying a sinewave voltage (50Hz) to the component under test and to the X deflection system. The current flowing in the test circuit deflects the scanning spot vertically, so that the pattern traced out shows the current/voltage characteristic of the component being checked – resistors produce diagonal lines, inductors and capacitors produce ellipses and semiconductor devices produce knees and angles. Some of the prettiest patterns I produced resulted from in-circuit tests of semiconductor devices in reactive (LC) circuits. The principle was described by David Botto in the June 1984 issue (page 426). It's certainly a quick and effective method of testing most components, particularly semiconductor devices. Built into the scope and ready for use at the press of a button this is certainly a very convenient feature, though it's limited in both range and accuracy with passive components like resistors and capacitors.

Verdict

Apart from my minor (and perhaps carping) criticisms of the c.r.t. and the unprotected front panel I have to report that I was very happy with this scope, which has many of the features of its more expensive 60MHz/15kV

brother the MH605. It was much in demand by my colleagues (notably Tony the Audio) while it resided in the workshop. It's versatile, easy to drive and has good performance. I'm sure that it represents good value for money at £365 plus VAT and it's well backed up, during and beyond the guarantee period, by the UK service and calibration department of Hameg at Luton, Beds. There are European depots in France, Germany and Spain.

The HM605

I subsequently had the opportunity to try out the 60MHz version, Model HM605. This is of similar construction and appearance but incorporates Y amplifiers with a bandwidth of 60MHz and a faster sweep speed to match. My first test was to hook it to the i.f. output of an ordinary u.h.f. tuner, whereupon a beautiful carrier envelope pattern of the 39.5MHz modulated carrier was

displayed, with gain to spare. The tube in this scope is operated at 15kV which gives a dazzlingly bright trace and an excellent display of short duty-cycle waveforms.

Judged overall the HM605 does not have as good an internal trigger performance as others, such as the "pulse-counting" scope I once reviewed or the wideband Philips type (which, incidentally, is much more expensive), but at about £567 plus VAT it offers the best price/performance ratio of any wideband scope I've come across.

Availability

Hameg scopes are available from most major trade component distributors and from several of our advertisers, e.g. BK Electronics, Stewart of Reading, etc. The review scopes were kindly lent to us by HRS Electronics Ltd., Great Barr Street, Birmingham B9 4BB (telephone 021 771 2525).

CRT Heater Voltage Checker

J. LeJeune

In virtually all present-day CTV receiver designs the c.r.t. heater voltage is provided by a winding on the chopper or line output transformer. Such a supply is preferable to the older mains transformer supply since the stabilisation is far higher. The shortening of tube life due to incorrect heater voltage becomes noticeable when the voltage varies from the rated figure by more than five per cent, which is less than the guaranteed mains supply limits. Since the c.r.t. is by far the most expensive single item in a receiver the changeover to a stabilised source of heater voltage has been a great advantage. A minority of service engineers maintain however that tube life was longer when the heaters were fed from a 50Hz source.

Theory

The sole purpose of the heater supply is to raise the temperature of the c.r.t.'s cathodes to the optimum level for electron emission. Higher or lower temperatures will result in deterioration of the cathode surface, to the detriment of the tube's life.

The heating effect of an alternating current is defined by its r.m.s. value, this being the value of direct current or

voltage that produces the same heating effect. Bench multimeters are calibrated to indicate the r.m.s. value of a sinewave, and produce misleading readings when fed with alternating voltages and currents that are non-sinusoidal, such as the pulse voltages derived from a line output transformer. Furthermore the frequency at which they are intended to operate is normally 50 or 60Hz: they give erroneous indications when used with frequencies that are significantly different from those for which they were calibrated.

There are various sophisticated methods of measuring true r.m.s. values, but they are expensive and often delicate – two features that make them unsuitable for normal workshop use. The simple, inexpensive and very robust checker to be described was developed after the writer's endurance had been tested to the limit watching service engineers attempt to divine the correct heater voltage using a rectifier-voltmeter combination and guesswork.

Checker Features

The checker uses no batteries and can be forgotten about when not in use. It's fast in action and fairly immune to misuse, though inadvertent connection to a voltage higher than 12V will fuse the lamp – when this item is replaced the unit's calibration must be reset. Lamp protection was considered but all attempts to achieve this resulted in loss of sensitivity and accuracy over a wide frequency range. The meter is isolated from the supply and is well protected by the parameters of the solar cell. The few components required are inexpensive and readily available – some may be found in odd corners of the workshop. In the original prototype a tape recorder level meter, a photocell from a damaged photographic exposure meter and a plastic box that once housed 35mm transparencies were used.

Circuit Description

The checker's circuit is shown in Fig. 1. It measures the heater voltage by using the supply's heating effect to light a small lamp whose output falls on the sensitive surface of

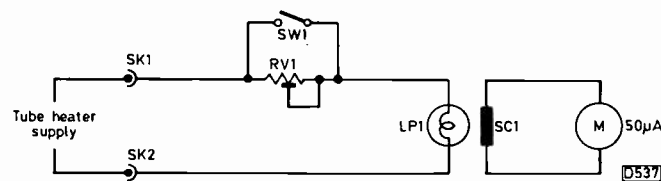


Fig. 1: Circuit diagram of the checker.

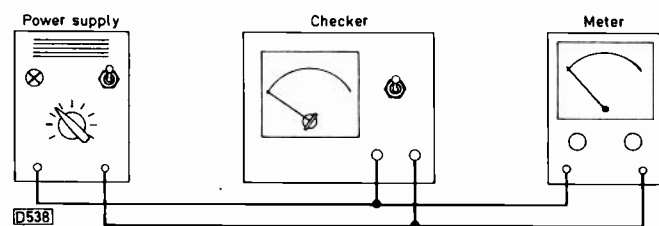


Fig. 2: Set-up for calibrating the checker.

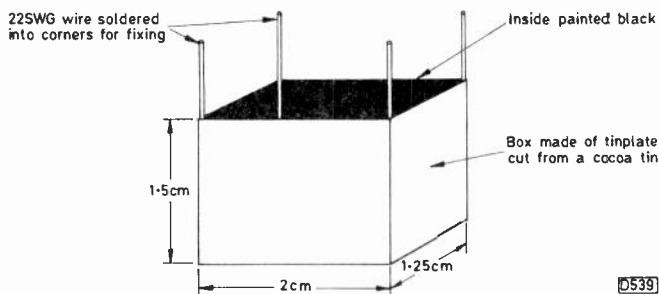


Fig. 3: Lightproof cover for the lamp and solar cell.

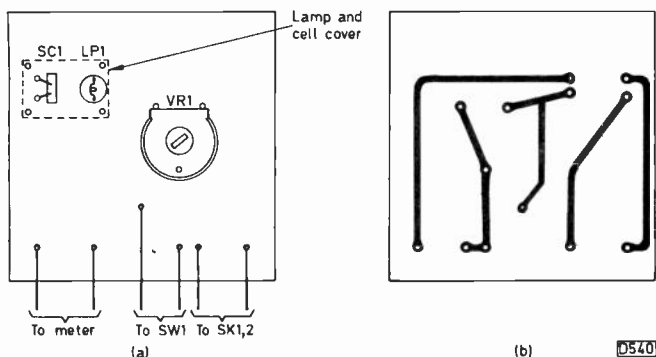


Fig. 4: PCB component layout (a) and track pattern (b).

a photovoltaic cell. This cell generates a direct current which is indicated by the meter. A resistor is switched into the circuit to allow 12V sources to be measured: this resistor drops the incoming 12V to 6V and eliminates any need for switching in the meter circuit – with the very low current involved such switching would be likely to cause trouble. The arrangement also means that the lamp's filament is rarely run at full voltage. Because of its 12V rating an attempt to test a 12V source with the checker's range switch set to 6V won't damage the lamp.

In use the checker bridges the c.r.t.'s heater supply at the tube base socket, the lamp consuming only 20mA. The effect of this on the voltage supplied to the tube's heaters via the usual ballast resistor is negligible; being of the order of 40mV with the usual 1.8-2Ω ballast resistor.

Calibration

Fig. 2 shows the best method of calibrating the checker. A variable voltage d.c. bench power supply is the easiest source of voltage to use, though a 12V battery and a 470Ω, 0.5W variable resistor can be used instead. To measure the d.c. voltage accurately an Avo 8 that's been recently recalibrated is the least that's necessary: a digital voltmeter would be ideal.

Initial setting up of the checker is simple. Uncase the checker and with the arrangement shown in Fig. 2 apply exactly 6.3V d.c. at its input sockets – the polarity doesn't matter. The lamp should light dimly and the meter will give an indication. Any incident light falling on the solar cell from room lighting, doors and windows will also produce a meter reading, so choose a dark corner to do the setting up. Adjust the distance between the lamp and the solar cell to obtain an approximately 'mid-scale' meter deflection. Check this with the light-tight box in position over the lamp and cell. A distance of approximately 1cm will serve as a starting point: the components can be bent closer to or farther away from each other as required.

I chose exactly mid-scale for the 6.3V indication and made other marks on the meter scale at 0.1V intervals,

from 5.8V to 6.8V – do this with the checker's cover in place over the lamp and cell. This completes the 6V calibration.

Set the checker's switch to the 12V position and increase the power supply output to 11.5V. RV1 sets the meter's indication for the 12V range. Adjust it until the meter pointer is at the 6.3V calibration mark. Vary the power supply output in 0.1V steps over the range 11-12V and make another set of calibration marks for this range. Don't disturb the positions of the lamp or solar cell otherwise the unit will have to be reset all over again.

Since the lamp bulb will gradually blacken over an extended period of regular use it's advisable to check the calibration from time to time. The frequency of these checks depends on the amount of use the checker gets: in a busy rental business workshop where fitting replacement c.r.t.s is a common occurrence there will be a greater need to check the calibration – it should be done after about a year of daily use. For the casual user checking the calibration is a matter of judgement.

Use

The checker should be used whenever a reprocessed c.r.t. has been fitted to a receiver. Make the last check the c.r.t. heater voltage – after all the other operating voltages have been correctly adjusted. With some imported c.r.t. gun assemblies the heater current differs slightly from that of the original gun, and because of the heater ballast resistor you will get variations outside the normal rating of the tube. Any doubt about the correct heater voltage should be taken up with the c.r.t. supplier. The checker will also show up faulty or out-of-tolerance ballast resistors.

The prototype checker has proved to be fast and reliable in use, with well over a year's service to its credit. Although its 20mA consumption means that it isn't universally applicable, some of the more exotic models reaching our shores being outside its capability, its usefulness in the diagnosis of tube-related complaints has been inestimable.

Components and Layout

There are few restrictions when it comes to the selection of components to use. Choice of solar cell is limited because few such devices are readily available. The Maplin MS4A (order no. BL23A) is one suitable type. The lamp is critical inasmuch as it should be a 12V, 30mA type. The one used in this instrument is an RS Components T1.25 (stock no. 586-380).

The checker's layout is largely a matter for the constructor's discretion, but the capacitance of the input to the lamp should be kept low as this could affect the checker's accuracy at high frequencies. While a PCB gives a neat finish to the unit it could be considered a luxury. Fig. 4 shows a layout – it may have to be altered to suit the components used.

Components

LP1	12V, 30mA lamp, type T1.25
M	50μA meter
RV1	470Ω, 0.5W skeleton preset
SC1	Silicon solar cell, e.g. Maplin MS4A
SK1, 2	Wander sockets
SW1	SPST switch

VCR Clinic

Reports from Alfred Damp, Martin Pomeroy, Christopher Holland, Les Harris, Jim Rainey, Roger Burchett and Philip Blundell, Eng. Tech.

Sharp VC3300

The fault with this portable machine was poor wind and rewind. The AUX brake wasn't releasing on wind/rewind though it did release on playback. The solenoid that operates the brake would pull in (as it should) then release again as the return coil was pulsed. Reference to the timing diagram in the manual showed that this shouldn't have been the case. After spending some time chasing round the brake drive circuit I had a look at the block diagram for inspiration. This revealed that a power failure signal is sent to the brake circuit from the power supply, and although the low-battery LED was out the signal line was floating at 3V. One half of operational amplifier IC901 was found to be open-circuit. Replacing the op-amp cured the fault but then the take-up spool didn't go round in playback! As this had been o.k. before I retraced my steps, one of which had been to swap over the reel drive and loading drive i.c.s. Although the circuit shows them as being of the same type one of them has an A suffix. Swapping them back restored normal operation (the A one should drive the reels). **P.B.**

JVC HR7200/Ferguson 3V29

The problem with this rather worn machine was intermittent loss of drum servo lock in search. The cause was a crack in the servo panel by connector 302. **P.B.**

Toshiba V31B

Severe overloading and no sound in the E-E mode, with the playback light permanently on, was due to Q663 being short-circuit. As a result the play-12V line was present all the time. **P.B.**

Philips/Finlux VR1010

An unusual problem with one of these machines was wow on sound and a rumbling noise coming from the capstan. The old screwdriver stethoscope trick proved that the noise was indeed coming from the bearing, but on these machines the races are riveted into the chassis. So I sent the machine back to Finlux who replaced the complete transport assembly. The noise was still there: red faces all round! If I'd tried replacing the tape servo board I may have traced the fault to a noisy TDA1432 DA converter chip. Sorry Gerry! **P.B.**

JVC HR7700/Ferguson 3V23

The fault on this machine served as a reminder that logical fault finding saves time and money through ordering the correct part first time: work on the assumption that all components are innocent until proved guilty. The complaint was no sound in the E-E mode, with the monitor producing an oscillation in the record mode. A hum test at pin 2 of IC1 (HA12005) produced no output while a similar test at output pin 6 produced results. We assumed that the i.c. was faulty, but were wrong. Further checks revealed that the voltage at pin 7 was low in both the record and playback modes. This pin is controlled by switching transistor X4 whose base was found to be

constantly high. This took us back to X44 on the mechacon board, then to IC3 (UPD4066C) on the junction board. Replacing this item finally cured the fault. **A.D.**

Hitachi VT88

This machine would accept and play cassettes properly but was loath to give them back when requested – when the cassette was ejected it was immediately taken back into the machine. We found that the cassette housing timing gears had slipped, as a result of which the cassette-in detector switch was operating too early, before the cassette had been fully ejected. Resetting the gears will provide only a temporary repair: the complete cassette housing assembly should be replaced. **A.D.**

Hitachi VT8500/8700

Failure to record was the complaint with a Hitachi VT8500: there was neither sound nor picture in the E-E mode. The supplies to the tuner and i.f. strip were correct but there was no output from the i.f. module. Fault finding here didn't look to be easy because of the close proximity of the tuner, with both modules soldered into a mother board. Just before I was about to remove the tuner/i.f. pack a picture flashed on the screen then off again: tapping the i.f. module would make the sound and picture come and go. When the i.f. module was unsoldered and its covers removed three obvious dry-joints were seen at earthing points, about a third of the way across the module from the left-hand side. Because of the difficulty experienced in removing the module we decided to do a blanket soldering job. When the module was replaced we had nice E-E vision and sound with no more problems.

A similar machine, a VT8700 in a Granada case, had a pluggable i.f. module. The complaint was the same and on opening the module the same three dry-joints were noted. Resoldering just these three joints restored normal service. **A.D.**

Sony SLC30

Crawling beat-frequency bars on the screen during playback (also in the E-E mode, though less evident) were eventually traced to a $\pm 1\text{MHz}$ oscillation on the UN12V line. This disappeared when plug CN001 was removed from the r.f. modulator – the oscillation was modulating the regulated 9V and 12V lines. After delving around in the modulator it was found that adding an 8.2Ω resistor in series with the UN12V line at plug CN001 (pin 3) solved the problem. It was easily fitted by cutting the print at the pin and mounting the resistor across the break. **M.P.**

Sanyo VTC5000

On playback there was a horizontal line three-quarters of the way down the screen – even with a prerecorded tape. Replacing the head disc didn't provide a cure so I tried swapping over the whole cylinder motor and upper cyl-

North East Satellite Systems

CROPTON, PICKERING, NORTH YORKSHIRE, YO18 8HL. Tel. (07515) 598.

Established 1982 — A PRE PIONEER COMPANY IN SATELLITE TV

Equipment suppliers to: BRITISH GOVERNMENT, UNIVERSITIES OF: OXFORD, HULL, LEEDS, BRADFORD, KENT, MANCHESTER; JODRELL BANK RADIO TELESCOPE, LONDON EDUCATION AUTHORITY, SOVIET EMBASSY, OIL INDUSTRY, HOTEL, TRADE & DOMESTIC SYSTEMS ETC, ETC.

OUR EXPERTISE AND LONG TERM INVOLVEMENT IS YOUR GUARANTEE THAT WE SHALL STILL BE OPERATIONAL IN 2010

EQUIPMENT

For the enthusiast: Limited numbers only. A 2.7m dish, with full horizon to horizon POLAR mount, 3.7-4.2 Ghz International band LNB, Scalar horn with depolarizer, IF active filter, International RX. Can also be used with extra LNB's at Ku band. Weight of system 1200 lbs. £1335 plus VAT

Special Systems:

French Telecom System:
1.25m dish, 12.2-12.75 LNB, RX. £799.00 + VAT

ECS or Intelsat system:
1.25m dish, 10.9-11.7 Ghz LNB, RX with fixed mount dish. £490.00 + VAT

Budget Price "Gorizont" system:
1.25m dish, 100° LNB, RX. £475.00 + VAT

LNB's etc.

4 Ghz, 100°, 950-1450 Mhz IF	£98.00
BDC 3.7-4.2, 950-1450 IF	£63.00
10.9-11.7 Ghz Standard IF	£148.00 (2.0dB NF)
12.2-12.75 Ghz Standard IF	£198.00 (2.0dB NF)
All above prices ex of VAT	

RECEIVERS

950-1750 IF INPUT	
DRAKE 324E	£255.00
Echosphere 1000E	£178.00
Echosphere 3000E Remote Control	£298.00
PAL to SECAM Transcoder	£150
All above prices ex of VAT	

Lower cost receivers will be in stock shortly.

Dishes from 1.25m-2.7m in stock. Reflectors only or full polar mount.

Motordrives, polarizers, OMT's, Splitters, Amplifiers, Scalar Horns etc. in stock.

Our associate company "Guideline Microwave Ltd." will produce to your specification, any active or passive device in the range 1-60 Ghz.

Mrs. K. M. Standen (Sales & Advertising)
Mr. D. J. Standen (Technical queries only)

TRAINING COURSE

In view of the number of Companies offering both equipment and courses in order to sell their own products, we intend to run a fully comprehensive course for Engineers, Installers & Enthusiasts.

The two day course will consist of:

4/11/12/ Ghz LNA/LNB Tests and repair.

Receiver technology, Varicap, remote, IR etc.

Parabolic dish techniques: this includes hands on experience of both offset and prime focus antennae from 1.0m-3.0m.

Experience in the use of test equipment, including: Spectrum Analyser, Storage Scope, Digital Counter, Sat. TV field strength meter, etc., etc.

SMATV systems both for UK and Europe with data on both VHF and UHF systems.

The course will give a clear understanding of the technology involved in satellite TV broadcasts in the current 4 operational bands.

We will train you to install both 4 & 11 Ghz systems, and identify the problems that you will meet during installation.

Other aspects of the course will cover terrestrial interference and its solution, encryption & de-encryption, legality & copyright.

The above is but a small part of the very intensive course.

COST: £100 + VAT
FOR THE TWO DAY COURSE

If required accommodation can be arranged.

inder from a VTC5300 (same unit!). This cleared the fault. Replacing the original upper cylinder assembly brought the fault back. On these machines the fixed head section of the transformer is mounted above the head disc in the upper cylinder: I suspect that the cause of the trouble could have been a short-circuit turn. L.H.

Toshiba V9600

This machine had very poor rewind – it would often stop. The problem was not due to the usual upper cylinder or rewind idler wear but to the two pillars that locate into the rear underside of the cassette. They were misaligned, causing the right-hand spool to drag. Unscrewing the pillar fixing screws and relocating the pillars correctly cured the problem. L.H.

Toshiba V8600

No output from the modulator due to Q661 being faulty – usually open-circuit base to emitter – has been mentioned before in these pages. I phoned Toshiba to see if any modifications were needed but it seems that the reason for this relatively common failing is not known. R.B.

Samsung VI510T

The problem with this machine was perfect playback of a prerecorded tape but only noise on the screen from one of its own recordings, though the sound was good. With such symptoms the first check should be on the voltages that control the video head switching transistors at the head preamplifiers. The fault is normally due to either the

record voltage being incorrect or a playback voltage being present during record. What caused the problem with this repair was an apparent mistake in the manual: this suggests that during record there should be 12V on the record line, most easily checked at pin 26 on the Y/C panel. In fact there should be 12V here during playback with zero volts during record. Once this error had been confirmed by checking with a good machine it was easy to trace the fault to IC8 on the syscon panel. It's one of those one-sided green i.c.s with the internal components bulging through the casing. C.H.

Ferguson 3V35/3V36

In both the playback and record modes the drum speed hunted at a regular rate. The cause of the fault was traced to R446 (270kΩ) which had gone high in value. It's in the drum speed control circuit, connected between pins 14 and 15 of IC404, i.e. providing feedback in the drum speed error signal amplifier stage. J.R.

JVC HRD120/Ferguson 3V35. Erase Problems

Over the years various VHS machines have suffered from problems at the full erase head. When you consider that each time a tape is played the supply loading arm pushes the erase head assembly out of its way after which the assembly springs back into position it's not surprising that with a number of machines you get dry-jointed erase heads or loose plugs at the erase head panel. The resultant symptoms vary from model to model. In all cases traces of colour from a previous recording will be left on the tape, since although the f.m. record current will remove all

traces of luminance information any strong areas of colour will remain. With the erase head out of circuit new audio is recorded normally though I have come across models where the previous audio remains as the erase head appears to be an active part of the h.f. circuit and, if not connected, the h.f. oscillator will not start up. In either case the accepted solution is to solder the leads directly to the pins of the erase head, removing the plug if one is used.

For some time I've been plagued by a couple of JVC HRD120s with very intermittent failure to record the audio signal, the previous track being left on the tape.

Soldering up the erase head made no difference – in fact on these machines if the erase head is left open-circuit the only apparent effect is smeary colour on the new recording. The problem is due to the h.f. oscillator circuit not starting up – if it doesn't start up for a particular recording it remains inactive throughout the recording. The solution that's finally come through is the following modification. Change transistor Q8 in the oscillator circuit from type 2SD638R to type 2SD638S and alter the value of C48 by soldering a 5.6nF capacitor across it. Should the same fault be encountered in the later JVC HRD140 it's worth checking the h.f. oscillator coil T1 for dry-joints. C.H.

Teletext Developments

Peter Marlow, B.Sc. (Hons.), C.Eng.

The future of teletext was the subject of a very interesting lecture at the Institution of Electrical Engineers on October 20th. The speaker was Gerald Crowther, who is adviser for new applications to the Mullard board. As manager of the Mullard Applications Laboratory for several years he had been involved with the development of the first Mullard teletext chip set.

Initial Development

The talk began with a history of the teletext system since its early beginnings at the BBC's Kingswood Warren laboratories in 1972. The system was rugged, reliable and straightforward and could be put into practice economically using the technology of the time. No complicated data processing was required as the data was sent in a fixed format that corresponded directly with the screen position. Texas Instruments pioneered the first decoder chip set (Tifax), closely followed by Mullard.

The original system had the limitation that "black holes" would appear in graphics diagrams. This was corrected by the use of non-printed characters (escape codes) within the text to define the background colours. This limited the amount of printed information that could appear on a line however.

There are now ten million sets with teletext facilities in use in the UK. Fifty per cent of the large-screen sets now sold have teletext and there's a drive on to get the setmakers to fit teletext to smaller-screen models. This is an attractive proposition as the proportion of the cost of a TV set accounted for by the extra chips has dropped from 40 per cent in 1981 to ten per cent in 1985. UK manufactured chips dominate the market, which now covers most of western and some of eastern Europe. Mullard have recently introduced a second-generation two-chip decoder set which gives a better display (12 x 10 characters instead of 9 x 5) and allows for text and data manipulation by an external microcomputer. Other manufacturers are developing similar chips which have a wider application than just teletext, e.g. viewdata.

The Future

Teletext is evolving in several ways which the new second-generation chips are putting into use: multipage memory (up to eight pages at present); hardcopy facility using a printer; full channel operation – where the TV transmission is all text with no pictures; multilingual capability to allow for accented characters (Welsh has

some of these) and non-latin based text; programming home terminals with telesoftware; downloaded character sets to provide enhanced graphics; and faster access time with the use of editor selected linked pages. With this last feature the decoder captures several other related pages at the same time as the one selected by the user. These pages are relevant to the subject requested, decided by the editor at the teletext studio. A menu of these pages will be displayed at the bottom of the text page, in coloured boxes: by pressing the appropriate coloured button on the remote control handset the relevant page is instantly displayed. This feature is at present being tested by the BBC and the IBA and sets should be available during the course of 1987.

It's felt that the data rate and the error detection and correction system are not in need of improvement. Users of telesoftware, which is the most demanding application in terms of accurate data, have reported that transmission by teletext is more reliable than via BT, though I suppose it depends on where you live.

Any teletext improvements have to be downwards compatible so that older decoders will receive something recognisable. The present system is called level 1: level 2 will have enhanced graphics and text, level 3 high-definition graphics, level 4 alpha-geometric graphics and level 5 full-colour still pictures.

The level 1 system uses 24 rows (or packets) of 40 characters. These are numbered 0 to 23. A five-bit binary address defines the packet, allowing up to 32 packets to be transmitted in higher level systems while retaining compatibility – 24 to be seen and the rest for colour and graphical information about the picture (formerly called "ghost rows"). These need not be limited to 40 characters. Two more packets (24/25) can be used to display status information on the screen. Packet 30 is the most interesting addition: it will contain broadcast service data which will include a network label, an accurate clock and a programme designator – the latter could be used to control a VCR.

The applications of teletext are not confined to the domestic viewer. Subscription (not closed) user groups can obtain information nationwide – Aircall Ltd. has a system in operation already. The most startling proposed teletext use is as a credit card verifier. Shops would have a teletext receiver linked to a card reader and certain teletext pages would contain the numbers of stolen or lapsed cards, allowing a cross check. In using technology to track down criminals history seems to be repeating itself – future Doctor Crippins beware!

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1-50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

FERGUSON TX90 CHASSIS

Performance is perfect except for the following field collapse trouble. Onset of the fault is usually signalled by faint light or black lines jittering across the bottom quarter of the screen. This is followed by collapse of the bottom half of the raster to a greater or lesser extent: the collapse is sudden and takes the form of severe cramping of the lower lines, with reasonable linearity still maintained in the section above. Once the bottom half of the raster has completely collapsed the top half begins to collapse: again the lowest lines collapse into a central line, pulling the remainder of the picture down. Eventually there's just a single central line across the screen. A smart blow on the case will restore the picture to a greater or lesser extent – persistence with this technique will usually recover the whole picture which may or may not collapse again. No amount of local panel tapping or pushing has succeeded in isolating a sensitive area and application of a multimeter produces an instant and prolonged cure.

We've known this problem to be caused by hairline cracks and dry-joints in the print around the connections to the field output transistors TR104 and TR105. We have also found that these two transistors, types TIP29E and TIP112H respectively, can be responsible. Change them both after making a thorough check of the print and connections in the area. It's important that the transistors are obtained from Ferguson. Substitutes will not work satisfactorily.

PANASONIC NV8610

The problem is with the load/unload function and occurred after replacing the mains transformer. Operation of the power switch starts the drum and capstan motors but not the loading motor. The voltages on the transport/servo panels seem to be o.k. and the loading motor works when an alternative voltage source is applied to it.

The three symptoms (capstan running, head rotating, no loading action) are typical of a machine that thinks it is already loaded. The cause is almost always a stuck or faulty loading and/or load-end switch. These switches are mounted on sub-board VJB00310 on the deck.

ITT CVC20 CHASSIS

Field collapse was cured by replacing the output transistors T9/10 and diode D8 which is in series with them. Next day the set came back with the complaint that there is a band across the picture. It's a dark band about a quarter of an inch wide with bright edges, about two thirds of the way down the screen. We've replaced the driver and pre-driver transistors T8 and T7 and the resistors in T7's base circuit. All resistors are of the correct value and new output

transistors have been tried. The output stage bias diode D7 has also been replaced. The linearity is good and there's plenty of height – apart from the band – but we can't get the output transistors to switch over correctly.

You've checked most of the likely culprits. We've often known D7 to be responsible for this fault and find that the correct type (BA316) is essential. Other items worth checking are C23 (1,500 μ F), C26 (22 μ F) and C27 (1,000 μ F) and in particular the three resistors (R62/3/5) associated with D7.

ITT VC300 CHASSIS

The problem with this monochrome portable is that the 11V supply line is low. Adjustment of the voltage control preset has no effect.

Start by disconnecting the tube's e.h.t. cap. If this restores the correct supply line voltage replace the e.h.t. rectifier stick. If not, measure the current flowing via supply fuse F2. If this is low (below 1A) the power supply is faulty – possibly the series regulator transistor T2 (R2441) is defective. If the current is high, check for leakage in the line output transistor (T14) and the diodes linked to the line output transformer (D15/16/18).

SANYO CTP5101

The problem with this set is field collapse – there's about an inch of scan. The voltages in the field oscillator stage are correct but some of the voltages in the following stages are out.

With this chassis field collapse is usually caused by defective electrolytics in the field timebase. We suggest you replace the scan coupling capacitor C436 (220 μ F), the bootstrap capacitor C433 (10 μ F) and the drive coupling capacitor C431 (10 μ F). If necessary check the values of R444 (18 Ω), R454 (68 Ω), R445 (1.2k Ω) and R446 (3.3k Ω) before suspecting the field output transistors Q905/6.

THORN TX9 CHASSIS

This set (Ferguson 37003) behaves as though it's receiving signals from the remote control unit when the latter is not being used. Mostly the set changes channels, and when it does the red LED sometimes stays lit. The fault may occur several times during an evening, then not for days. Response to operation of the remote control unit is correct at all times.

Disconnect plug 32 at the rear of the IR preamplifier. If the problem disappears the cause is noise or instability in the preamplifier, which is probably easier (and cheaper) to replace than to repair. If the fault remains, check the quality (voltage and ripple) of the 11.6V line, at pin 13 of IC101 (SAA5012). If the supply is present and correct, IC101 itself is suspect.

QUERY COUPON

■ Available until 21st January 1987. ■
■ One coupon, plus a £1-50 (inc. VAT) ■
■ cheque or postal order, must accom- ■
■ pany EACH PROBLEM sent in accor- ■
■ dance with the notice above. ■

TELEVISION JANUARY 1987

SONY KV2706UB

The picture on this set is marred by random white spots which appear approximately ten minutes after switching on – they can be seen clearly on a dark raster. I suspected corona discharge but have been unable to locate any. There's no interference on sound.

This problem can be caused by micro-arcing at the internal connections of electrolytic capacitors, usually those in the power supply. Check C653 then if necessary the other reservoir capacitors connected to T603's secondary windings. Check also the mains switch, the safety resistor R617 and for bad joints in the power supply and especially its plug/socket connections. If necessary check the earthing of the picture tube's external conductive coating and for corrosion/discharge at the anode cavity connector and focus connection pins 2 and 3.

TEST CASE

289

Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

It often means finis when a TV set reaches the age of seven or eight years and its tube is in trouble. The economics of replacing a picture tube and the recent tightening up of the manufacturers' seven-year spares rule (have you noticed?) conspire to put the viability of such a job in great doubt. A good tube rejuvenator will often provide the answer, but not always...

When the set is the subject of a maintenance agreement something has to be done! We had just such a case recently. The set was a 1979 vintage ITT Model CS712, fitted with the CVC30 chassis. On its first visit to the workshop – after a chequered history of field service calls – the complaint was of a "grotty picture", an apt description. All the signs of a tired tube were present, which is perhaps not surprising after seven years. We treated the tube with our wonder tube-jacker and after a soak test and set-up the receiver was returned to its owner. After no more than a couple of months the set was back on the bench. It looked better than it did when it first came in, but not as good as when it subsequently went out! Once more the impression was of a tired tube.

A suitable replacement tube was found amongst the rental pile of old, condemned TVs. An emission test proved that this was o.k., so it was fitted to the ailing ITT set. After being set up, the picture was reasonable rather than good, but a delivery order was nevertheless raised. It was a few days before delivery could be arranged: on the appointed morning the delivery man took one look at the set's picture and decided there and then that it wasn't good enough to take back. Even the workshop fraternity

had to agree – the picture was somewhat defocused, the grey scale had that sickly green look, and the whites were crushed into grey at high settings of the contrast and brightness controls.

Off with the back and hook up the wonder tube-jacker again. It showed that the emission was quite reasonable. Each gun was then tickled rather than jacked, but this produced very little improvement in the picture. Resident Sage was worried. Not only had the reliability of his tube-jacker been called into question, but the set had by now been the recipient of many man-hours of attention. And here we were back at square one. He settled himself behind the set with an oscilloscope, a test meter and a stern air. Alarm bells began to ring when a scope test revealed that the R, G and B signal waveforms at the collectors of the appropriate output transistors were crushed. A check on the h.t. line supplying these stages produced a reading of a little over 200V instead of the expected 225V. Hmm. When the RGB outputs at the TCA800 demodulator/matrixing chip were scoped some flattening of the white response was evident. This led to a check on the 12V line – at pin 9 of the chip. The reading was low at about 10.2V. Attention was next turned to the 12V regulator transistor T14. The input at its emitter was a mere 13V, not really enough for it to bite on... It was proposed to change the reservoir capacitor at this point (C71, 470 μ F) and Resident Sage sent NAT (newly arrived trainee) to the stores to get one. Before he got back however RS had put two and two – or rather thirteen and two hundred – together and had arrived at a correct diagnosis. What was it, and why wasn't the width down all this time? What a wind-up! Answer next month.

ANSWER TO TEST CASE 288 – page 117 last month –

By way of a Christmas treat for our readers we described a Sharp XC30 colour camera fault last month. The last few lines of the story were a give-away! The no-picture condition was accompanied by a remarkable video preamplifier docility: its gain is normally so great that oscillation and instability result from any contact – or even approach to – the target connection lead. The other vital clue was the missing target voltage. In fact the target lead was earthed inside the cast screening cover over the front end of the vidicon tube. Connection to the target ring is made by a spring contact which is anchored to a supporting plastic moulding by a tiny self-tapping screw. As so often happens with plastic mouldings this one had rotted and crumbled away, allowing the spring contact to touch the earthed screen. Switch cleaner cannot be blamed this time!

The service manual contains no obvious part number for this little plastic treasure, but we found that the tube is centred within it by two moulded-on spacer blocks that contact the target ring on each side. We carefully bent and shaped a tiny strip of brass to make a U-shaped shoe to slip over one of these, forming a tight wedge-fit between it and the tube's target ring. After fitting a slightly longer signal-connection wire we were back in business.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (Asia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £14, overseas (surface mail) £17 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

MICRO-X

SAVE TIME AND MONEY

EUROPE'S No 1 DISTRIBUTOR IN SATELLITE RECEIVER SYSTEMS

DISHES	
Alcoa 1.8 petallized (black mesh or solid) original p/mount	325
Alcoa 2.4 petallized (black mesh or solid) original p/mount	495
Alcoa 1.2 offset aluminium motorized horizon-to-horizon built-in p/rotor	275
Levick 1.6 m spun aluminium with polar mount, feed horn & ground stand	239
Levick 1.25 m spun aluminium with p/mount and ground stand	163
I.R.T.E. 1.5 m pressed aluminium with p/mount and feed horn	329
Laux Beta9 2.8 m aluminium petallized with p/mount	650
Skyscan 1.5 m offset GRP. with p/mount & stand	299
DISH POSITIONERS	
Houston Tracker II controller + 18" jack	199
Houston Tracker II controller only	139
Houston Tracker 18" jack only	68
Houston Tracker II remote upgrade	22
Houston Tracker III + 18" jack	259
Drake APS24E + 24" jack	189
Drake APS424E + 18" jack	229
Skyscan jack only	75
NEC 2025 Tracker + 18" superwinch	285
RECEIVERS	
Drake ESR 324E 24 presets. manual	166
Drake ESR 424E fully remote (black)	269
NEW NEC 2022 fully remote+graphics	320
Maspro SRE 80L manual	385
Maspro SRE 80R remote	299
Luxor Mk2 remote	349
Echostar SR1000	135
Echostar SR3000 fully remote	245
Skyscan receiver + built-in dish control	435
LNB's	
SPC electronics typ. 2.0db	114.95
(Buy 30 + for £99 each)	120.00
NEW NEC 2021 typ. 2.3 db	136.00
Echostar LNB typ. 2.0 db	199.00
Maspro 770X typ. 1.8 db	

POLARIZERS

New Chaparral 2293 11 GHZ	54.90
New Alcoa with feed & support	77.50
New I.R.T.E. (no moving parts)	79.00
New Maspro PS 75ET	149.00
Skyscan	45.00
I.R.T.E. orthmode + rings	129.00
Luxor V/H switch	69.00
Maspro V/H switch	69.00
Levick feed with Scaler	18.00

CABLE & CONNECTORS

Raydex RA519 low loss	139.00
250 m drum	
New 1-Run ribbon 4 cables in 1	149.00
100 m drum	
New Star-core actuator cable	49.00
100m drum	
Crimp-on gilbert N-connectors (RA519)	3.85
Crimp-on gilbert F-connectors (RA519)	
RG6 F-connectors	1.10
American N-crimp-on	0.29
Crimp tool N or F	1.95
F male to N female	22.00
F female to N male	2.75
Double N female or male	3.95
2 way splitter N type passive	4.50
4 way splitter N type passive	38.00
4 way active splitter active	46.00
Line amp 18 db equalized	56.00
Inogen inclinometer	34.40
	39.00

YOU CAN MAKE OVER 100 DIFFERENT SYSTEMS FROM THE ITEMS IN THIS PRICE LIST!

Buy the easy way: call Micro-X on London 968 6622 or Telex 915866 Microx G FAX: 01-960 1130

SOME SELECTED SYSTEMS

High Quality, Low Cost
Levick 1.25m dish with polar mount
SPC LNB
Drake ESR 324E receiver
£416

Drake Fully Remote
Drake ESR 424E receiver
SPC LNB
Alcoa 1.8 m dish (black mesh or solid)
Alcoa polarotor
Houston Tracker II
£899

NEC Fully Remote
New NEC 2022 receiver
New NEC LNB
Alcoa 1.8 m dish (black mesh or solid)
Alcoa polarotor
Houston Tracker II
£925

The "Skyscan" System
1.5 m offset dish
Receiver with built-in dish control
LNB & p/rotor & actuator
£869

The Fully Remote "Special"
New NEC 2022 receiver
New NEC LNB
New Alcoa 1.2 m aluminium offset
with built-in motorized
horizon-to-horizon
mount and built-in polarotor
Houston Tracker 1R controller
£799

EXPORT ENQUIRIES WELCOME

quality products from leading manufacturers who care about you and your customers, all products supplied by Micro-X are covered by full warranty and spares are readily available should you require them.

Micro-X, Europe's leading distributors of Satellite receiver systems bring you the best systems from the World's greatest manufacturers. When you buy from Micro-X you are buying high

**MICRO-X LIMITED, 765-767 HARROW ROAD
LONDON NW10 5NY. TELEPHONE: 01-968 6622
TELEX: 915866 MICROX G. FAX: 01-960 1130**

MICRO-X

LARGE DISCOUNTS ON QUANTITY ORDERS



ALAN PERROW
 National Trade Sales Manager
 618 Gt. Horton Road,
 Bradford
 BD7 3ER.
 Tel: 0274 501680

**For the best deals in ex-rental
 colour TV's and video**

JACK SWAN
 Depot Manager
 426a Helen St, Govan
 Glasgow G51 3HR.
 Tel: 041-445 6566



ALF PERROW
 Depot Manager
 618 Gt. Horton Road,
 Bradford BD7 3ER.
 Tel: 0274 502881



ERIC SIMPSON
 Depot Manager
 221 - 225 Walton Road
 Liverpool L4 4AJ.
 Tel: 051 207 1138

CHRIS HILLS
 Depot Manager
 247 - 249 High
 Road,
 Tottenham
 London N15 5BJ.
 Tel: 01-809 4866.



GEORGE PERRY
 Depot Manager
 478 - 486 Old Kent Rd.,
 London SE1 5AG.
 Tel: 01-232 0547/0567

**give your area head
 the nod.**

SIMON GOULDING
 National & Export Sales
 Manager
 478 - 486 Old Kent Road
 London SE1 5AG.
 Tel: 01-232 0567



SuperTel

You've tried the rest - now try the best

ALSTON-BARRY SATELLITE SERVICES

36 MILTON ROAD, CAMBRIDGE. TEL: (0223) 69215

Main importers and distributors for R.L. Drake, Ohio, USA.
American satellite technology at its best, now in stock.

SYSTEM	RECEIVER	POSITIONER	L.N.B.	DISH/POLOROTOR
£795 rec. retail single satellite	Manual ESR324E	_____	Drake	1.2 metre offset
£995 rec. retail multi- satellite	Manual ESR324E	APS 24	Drake	1.2 metre offset
£1195 rec. retail multi satellite	I/R remote 24 channel ESR424E	APS 24 (works remotely)	Drake	1.2 metre offset
£1275 rec. retail multi satellite	I/R remote 24 channel ESR424E	APS 424 (30 satellite programmable).	Drake	1.2 metre offset


All above prices include VAT but not installation. Multi-ribbon feed cable available by the metre.

Other dish sizes on request. Trade prices available to bona fide dealers and installers.

All items sold separately. Don't delay, call today for immediate delivery.

We also stock a large range of late model Pye/Philips televisions at trade prices.

Save £££s, call us first!

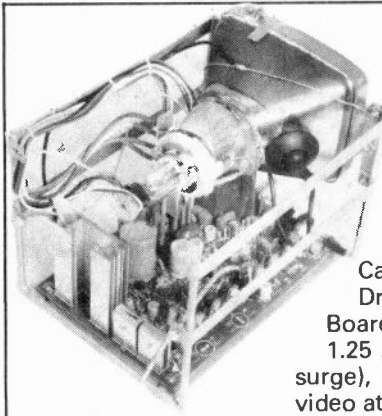

Professional Monitor Drive Board & Tube

This Crofton Monitor Kit comprises a 12" P31 Cathode Ray Tube and Drive Board. The Drive Board requires 12 volts at 1.25 Amp continuous (1.85A surge), separate line, field and video at TTL levels. By the addition of a few standard components this board can be driven from standard composite signals.

The Drive Board has a bandwidth of 24 MHz and is capable of displaying 25 lines of 80+ characters.

This is a professional board and tube as supplied to manufacturers of terminals, and out performs monitors costing many times this price.

A few boards and tubes are also available mounted on a metal frame.

A circuit diagram, together with full instructions, are provided with each board and tube.

You will be absolutely delighted with the performance.

Board and Tube **£34.50 inclusive of VAT**

Board and Tube on Metal Frame **£40.25 inclusive of VAT**

Carriage is £13.50 or come and collect direct from our Warehouse.

**Crofton Electronics,
"Kingshill", Nextend, Lyonshall, HR5 3SX.
Telephone: 05448 557**

PRO-VISION

TOP QUALITY SETS
IN SHOWROOM CONDITION FROM

EX-HOTEL CONTRACTS &
SMALL RENTAL COMPANIES

—
PYE DECCA GEC FERGUSON ITT ETC.

—
WE SET THE STANDARDS YOU KEEP THE PROFITS

021-471-5116

THE PROFESSIONALS

CUSTOMER CAN'T PAY?

DONT LOSE HIM FIT A TV METER

COINAGE AVAILABLE: 10p - 50p - £1
COMPLETELY VARIABLE TIMINGS



Alberice METERS LIMITED

MANUFACTURERS OF TV COIN OPERATED METERS

Contact: (0202) 674272
87-89 Sterte Avenue, Poole, Dorset BH15 2AW
Telex: 418253 PORTLX G.

WE WILL ONLY SUPPLY TOP
QUALITY, BRANDED COMPONENTS.
REPUTATION COUNTS WITH US

G.G.L. COMPONENTS

108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
PHONE (0228) 20358/39693

BUY WITH



TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)
AN2140	1.95	AN303	3.75	AN305	3.50	AN318	5.25
AN7114E	2.30	AN7115E	2.35	AN7116	2.10	AN7145M	2.95
AN7188	2.95	HAI1339A	2.95	HAI1366W	1.85	HAI1366WR	1.85
HAI1374	2.45	HAI1377	2.95	HAI1392	2.95	HAI1397	3.95
LA1201	1.25	LA1230	2.95	LA1365	2.45	LA4440	2.75
LA4445	2.45	LA4460	2.45	LA4461	2.45	MC13002	3.95
SA11250	3.85	SA11251	4.95	SA13027	3.95	SA15010	4.95
SA15012	4.95	SAF1032P	3.25	SAF1039P	2.75	SA5560S	2.45
SA5570S	2.45	SA5580S	2.65	SA5590S	2.65	SL470	2.95
SL471DP	2.95	SL480	2.85	SL490	2.50	SL1430	1.95
SL1432	1.75	SN78660N	.65	STK0039	6.45	STK0040	5.95
STK077	6.95	STK1278	8.50	STK433	5.95	STK4332	5.95

TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)
TDA2521/3	2.95	TDA2523	2.80	TDA2525	3.20	TDA2530	2.00
TDA2532	2.10	TDA2540	1.95	TDA2541	2.70	TDA2545	3.55
TDA2546	4.95	TDA2560	2.40	TDA2571A	4.95	TDA2576A	3.30
TDA2577	3.50	TDA2578A	2.95	TDA2581	2.00	TDA2582	1.95
TDA2591	2.30	TDA2593	2.30	TDA2594	2.95	TDA2600	6.35
TDA2611A	1.50	TDA2633A	3.55	TDA2654	4.30	TDA2655A	5.95
TDA3190	3.95	TDA3540	3.70	TDA3541	3.70	TDA3560	4.95
TDA3561A	4.95	TDA3562A	6.50	TDA3565A	4.75	TDA3651	2.70
TDA3651AQ	3.80	TDA3652	3.35	TDA4427	4.80	TDA4500	3.95
TDA4600/2	2.85	TDA4600/2D	3.30	BT116	1.30	BU126	1.50
BU205	1.40	BU208A	1.45	BU208/02	1.50	BU208D	1.95
BU326A	1.45	BU500	1.95	BU508A	1.75	BU508D	1.95
BU526	2.20	BU807	1.30	BU871A	2.50	UPC1230H	4.35
UPC1363C	3.95	UPC1365C	4.20	UPC1365C	4.20	UPC1365C	4.20

TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)
BUX84	.90	DECCA 100	7.20	DECCA 120/130	6.95	ITT CVC20/30	6.95
ITT CVC45	7.30	PHILIPS G8	7.90	PHILIPS G8	7.90	PHILIPS G8	7.90
PHILIPS G8	7.90	PHILIPS KT3	7.95	RBM T20/T22A	7.35	THORN 8000	4.00
THORN 8500/8800	7.20	THORN 9000	8.00	UNIVERSAL	5.95	DECCA 80	7.20
DECCA 100	7.35	ITT CVC20/30	6.95	ITT CVC25/30/32	8.40	ITT CVC45	7.95
PHILIPS G8	7.90	PHILIPS G11	14.95	PHILIPS KT3	9.25	PHILIPS K30	12.95
RBM T20/T22A	7.35	THORN 8000	4.00	THORN 8500/8800	7.20	THORN 9000	8.00
UNIVERSAL	5.95	DECCA 120/130	6.95	ITT CVC20/30	6.95	ITT CVC25/30/32	8.40
ITT CVC45	7.30	PHILIPS G8	7.90	PHILIPS G11	14.95	PHILIPS KT3	9.25
PHILIPS K30	12.95	RBM T20/T22A	7.35	THORN 8000	4.00	THORN 8500/8800	7.20
THORN 9000	8.00	UNIVERSAL	5.95	DECCA 80	7.20	DECCA 100	7.35
ITT CVC20/30	6.95	ITT CVC25/30/32	8.40	ITT CVC45	7.95	PHILIPS G8	7.90
PHILIPS G11	14.95	PHILIPS KT3	9.25	PHILIPS K30	12.95	RBM T20/T22A	7.35
THORN 8000	4.00	THORN 8500/8800	7.20	THORN 9000	8.00	UNIVERSAL	5.95

TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)
DECCA 80	7.20	DECCA 100	7.35	ITT CVC20/30	6.95	ITT CVC25/30/32	8.40
ITT CVC45	7.30	PHILIPS G8	7.90	PHILIPS G11	14.95	PHILIPS KT3	9.25
PHILIPS K30	12.95	RBM T20/T22A	7.35	THORN 8000	4.00	THORN 8500/8800	7.20
THORN 9000	8.00	UNIVERSAL	5.95	DECCA 80	7.20	DECCA 100	7.35
ITT CVC20/30	6.95	ITT CVC25/30/32	8.40	ITT CVC45	7.95	PHILIPS G8	7.90
PHILIPS G11	14.95	PHILIPS KT3	9.25	PHILIPS K30	12.95	RBM T20/T22A	7.35
THORN 8000	4.00	THORN 8500/8800	7.20	THORN 9000	8.00	UNIVERSAL	5.95


TYPE	PRICE (£)
HM6232	5.95
HM6251	4.70
HM9032	5.70
STR441	5.50
STR451	5.50
STR454	5.50
STR6020 (Kit)	6.35
ET548 Tuner	14.95
ET566A Tuner	9.95

TYPE	PRICE (£)
NV333 Idler	1.10
NV2000 Idler	1.30
NV3000 Idler	1.25
NV7000 Idler	1.20
NV2000 Load. Gear	1.60
NV7000 Load. Gear	1.60
NV333 Pinch Roller	4.95
NV7000 Pinch Roller	4.95

TYPE	PRICE (£)
Capstan Motor	32.95
Gear Idler	6.95
Load. Roller	1.95
Pinch Roller	5.85
Reel Motor	8.95
Reel Pulley	6.70

TYPE	PRICE (£)
Hitachi 9300	95
National NV2000	1.00
Sharp 8300	1.00
Sharp 9300	2.65
Thorn (Plug)	.95
Universal	.50

TYPE	PRICE (£)
Repair Kits Text	
Handset Buttons & Foils	£5.95
Video Head Universal Copying Kit	£5.75

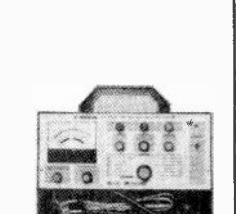

TYPE	PRICE (£)
V4000H/VT8000	
Audio Head	18.95
Capstan Motor	31.90
Idler F.F./Rew	1.85
Pilot Lamp	.65
Pinch Roller	4.95
Play Idler	3.95
Service Manual	6.30
Video Head	34.95
V4100H/V4002H	
3300E/9500E	
Capstan Motor	30.95
Idler F.F./Rew	1.80
Play Idler	4.30
Pinch Roller	5.50
Pulley F.F./Rew	.40
R.F. Converter	28.95
Service Manual (9300)	6.40
Service Manual (9500)	8.50
Video Head	34.95
V4100H/VT11E	
Audio Head	19.95
Capstan Motor	21.95
Clutch Assy	9.40
F.F./Rew Arm	2.90
Pinch Roller	5.50
Relay	2.95
Service Manual	6.50
Video Head	32.95
V4004H/TV33E	
Video Head	34.95

TYPE	PRICE (£)
VCR 6460/00/05	
Audio Head	25.95
Idler Arm	8.25
F. Load Motor	14.10
Loading Motor	12.95
Service Manual	7.50
Take-up Reel	5.30
Tuner	13.95
Video Head	59.95
VCR 6462/00	
Capstan Motor	38.95
Control Motor	9.95
Erase Head	11.75
Modulator	35.95
Winding Motor	43.35
Video Head	39.95
VCR 6520/00/05	
Audio Head	26.50
F/Load Motor	14.10
Idler Unit	8.25
Loading Motor	12.95
Service Manual	7.50
Take-up Reel	5.60
Video Head	59.95
VCR 6560/00/05	
Capstan Motor	44.70
Control Motor	8.50
Modulator	48.60
Video Head	32.95
VCR 6660	
Capstan Motor	36.95
Control Motor	9.95
Take-up Idler	8.95
Video Head	39.95

TYPE	PRICE (£)
C5/C7	
Ace Head Assy	35.50
Limiter Assy	3.15
Motor (BHF1100D)	39.95
Pinch Roller	1.30
Rewind Kit	5.25
Service Manual C5	9.40
Service Manual C7	9.40
Video Head	45.00
C6	
Ace Head Assy	42.20
Reel Motor	17.60
Reel Motor (C6MKII)	28.00
Rewind Kit	4.20
Service Manual (C6)	9.40
Service Manual (C6MKII)	9.40
Video Head	45.00
C9	
OC-DC Conv.	22.70
Gear Kit	6.70
Guide Pin Kit	4.95
Service Manual	9.40
Video Head	45.95
VIDEO BELT KITS	
Hitachi 9300/9500	1.80
Hitachi VT11E	2.95
Nat. Pan. 2000	2.55
Nat. Pan. NV7000	2.25
Sanyo 5000	1.00
Sanyo 5300	2.45
Sharp 7300	2.60
Sharp 8300	2.45
Sharp 9300	2.45
Sony C5/C7	2.80
Sony C9	2.45
Thorn 3V00/16/22	2.80
Thorn 3V29	1.80

TYPE	PRICE (£)
3V00/16/22	
Capstan Motor	49.95
Drum Motor	43.95
F.F. Idler	1.60
Pinch Roller	7.20
Rewind Idler	6.25
Take-up Idler (LG)	7.50
Take-up Idler (SM)	5.80
Video Head (3HSS)	32.95
3V29/30	
Capstan Motor	38.60
Loading Motor	8.95
Pinch Roller	6.95
Reel Motor	31.90
Take-up Clutch	2.35
Take-up Idler	1.40
Video Head (3HSS)	32.95
3V35/36	
Capstan Motor	28.50
Cass. Housing	34.95
Cass. Motor	6.70
Erase Head	9.60
Guide Roller	.30
Leaf Switch	1.45
Service Manual	26.00
Take-up Clutch	2.45
UHF Tuner	36.50
VIDEO MOTORS	
Capstan Motor to fit Thorn 3V00/16/22	24.95
Sony C9	2.45
Drum Motor to fit Thorn 3000/16/22	24.95

TYPE	PRICE (£)
THANDAR/LEADER TEST EQUIPMENT (top quality at realistic prices)	
THANDAR/LEADER TEST EQUIPMENT	
THANDAR SC110A (PORTABLE OSCILLOSCOPE)	
Mains/battery, compact and professional. Bandwidth 10MHz, Sensitivity 10MV, Screen 32x26mm, Trigger-int./ext.	£160.00 + VAT

LEADER LCT910A CRT TESTER/REJUVENATOR

This widely respected & essential piece of equipment is probably as versatile as anyone would require and has been a market leader since its introduction

£317 + VAT

OSCILLOSCOPE MODEL LB0522

Dual Trace, 2-Channel, 20MHz. Sensitivity 5MV/DIV

£415.00 + VAT

ORDERING

Please add 75p for p/p U.K. Add 15% VAT to this total. Service Manuals p/p 90p. Export Orders - Cost. Delivery by return on all stock items.

AN127Q	E.20	AN7146M	E.20	HA1199	E1.85	LA1111P	E0.95	M5106P	E2.75	STK5451	E5.75	TA7628P	E2.85	2SA101	E0.60
AN203	E.20	AN7154	E1.90	HA1396W	E1.80	LA1140	E2.20	M5134P	E2.25	STK5720	E6.45	TA7640AP	E1.75	2SA103	E0.60
AN210	E1.75	AN7156N	E2.50	HA1397	E1.80	LA1201	E0.85	M5155P	E1.85	STK5730	E6.20	TA7641BP	E1.85	2SA329	E0.40
AN211A	E0.80	AN7158N	E3.25	HA1339A	E1.85	LA1222	E1.00	M51102L	E3.95	STK7308	E5.95	TA7658P	E1.75	2SA350	E0.60
AN214Q	E1.80	AN7160	E3.75	HA1366W	E1.80	LA1230	E1.50	M51513L	E1.80	STK8250	E10.10	TA7668BP	E1.98	2SA495	E0.40
AN217B	E2.20	AN7161	E3.75	HA1366WR	E1.85	LA1231	E2.35	M51514AL	E1.95	STR440	E5.80	TA7688P	E2.95	2SA539	E0.40
AN228W	E2.90	AN7168	E2.75	HA1367	E3.25	LA1240	E1.95	M51515BL	E2.70	STR441	E5.80	TA7688P	E2.95	2SA592	E0.40
AN234	E5.95	AN7178	E2.95	HA1368	E1.90	LA1362	E1.50	M51516L	E2.80	STR2012	E7.20	UPC168C	E1.95	2SA643	E0.70
AN236	E2.20	HA1368R	E1.95	LA1367	E3.60	M51517L	E2.80	STR4211	E7.20	UPC200C	E2.20	2SA733	E0.35		
AN239Q	E4.20	AN7223	E3.95	LA1372	E3.50	M51518L	E2.20	STR6020	E7.20	UPC300C	E2.20	2SA768	E0.95		
AN240P	E1.50	AN7273	E3.95	HA1374	E2.50	LA2100	E2.95	M51521AL	E1.80	UPC410C	E2.30	2SA899	E0.75		
AN241P	E1.50	AN7310	E1.70	LA1377	E2.20	LA3160	E1.90	TA7051P	E1.80	UPC561C	E2.50	2SA952	E0.40		
AN247P	E2.50	AN7311	E1.70	HA1388	E3.50	LA3161	E1.90	TA7059P	E1.80	UPC566H	E0.75	2SA1015	E0.35		
AN259	E2.75	BA301	E0.80	HA1389R	E2.20	LA3201	E0.95	TA7066P	E1.75	UPC1025H	E2.30	2SA1102	E0.20		
AN260P	E2.20	BA311	E0.95	HA1392R	E2.20	LA3210	E0.75	TA7070P	E1.50	UPC574J	E0.65	2SA1103	E0.20		
AN263	E1.60	BA313	E0.80	HA1392	E2.50	LA3300	E1.65	TA7074P	E1.95	UPC575C	E1.00	2SA1104	E0.20		
AN271A	E2.50	BA318	E1.50	HA1394	E2.95	LA3301	E1.30	TA7104P	E2.50	UPC576H	E2.20	2SA1105	E0.25		
AN274	E2.75	BA401	E0.80	HA1397	E2.75	LA3350	E1.30	TA7108P	E1.75	UPC587C	E1.30	2SA1106	E0.25		
AN295	E3.60	BA402	E0.80	HA1396	E2.75	LA3361	E1.75	TA7120P	E2.00	UPC592H	E0.95	2SB54	E0.70		
AN301	E0.80	BA403	E1.95	HA1457W	E1.75	LA4030P	E2.80	TA7122AP	E1.90	UPC595C	E2.20	2SB341V	E0.75		
AN302	E3.30	BA511A	E1.80	HA1112W	E3.75	LA4031P	E1.95	TA7130P	E1.00	UPC1001H	E2.20	2SB405	E2.80		
AN303	E2.75	BA514	E1.90	HA11211	E2.30	LA4032P	E1.90	TA7136P	E1.00	UPC1009C	E2.20	2SB426	E2.95		
AN305	E3.50	BA521	E1.80	HA11215A	E4.35	LA4033P	E1.90	TA7137P	E1.00	UPC1018C	E1.95	2SB471	E3.50		
AN310U	E2.75	BA526	E3.50	HA11219	E2.70	LA4061P	E2.20	TA7139P	E1.00	UPC1025H	E2.30	2SB492	E1.75		
AN315	E2.30	BA527	E1.60	HA11223	E3.80	LA4062P	E2.20	TA7140P	E1.75	UPC1026C	E1.00	2SB5090	E1.95		
AN316	E3.75	BA532	E1.80	HA11225	E3.80	LA4102	E1.40	TA7142AP	E2.95	UPC1028H	E0.90	2SB536	E0.95		
AN318	E4.95	BA536	E2.40	HA11229	E1.95	LA4110	E1.40	TA7145P	E2.50	UPC1031H	E1.95	2SB546	E0.95		
AN319	E2.95	BA547	E2.50	HA11226	E4.50	LA4112	E1.75	TA7150P	E2.75	UPC1032H	E1.60	2SB561	E0.35		
AN340P	E1.80	BA612	E1.80	HA11227	E2.20	LA4120	E2.95	TA7152P	E2.30	UPC1035C	E1.95	2SB898	E0.40		
AN360	E1.30	BA631	E5.75	HA11244	E4.60	LA4126	E2.60	TA7157P	E1.65	UPC1037H	E1.25	2SB924	E0.35		
AN362L	E1.60	BA656	E4.50	HA1401	E2.80	LA4140	E0.80	TA7172P	E4.00	UPC1156H	E2.85	2SC372	E0.80		
AN364P	E1.70	BA843	E3.75	HA11423	E4.75	LA4160	E2.40	TA7193P	E4.50	UPC1158H	E0.95	2SC380	E0.35		
AN374P	E2.20	BA847	E4.50	HA11440A	E3.95	LA4170	E3.50	TA7202P	E4.00	UPC1165C	E1.30	2SC458	E0.30		
AN377	E1.00	BA853	E7.50	HA11701	E3.50	LA4182	E2.10	TA7203P	E1.75	UPC1168C	E1.30	2SC460	E0.35		
AN381	E1.80	BA1310F	E1.75	HA11703	E4.50	LA4192	E1.95	TA7204P	E1.90	UPC1170H	E1.60	2SC461	E0.35		
AN382	E1.80	BA1320	E1.75	HA11704	E5.00	LA4200	E1.50	TA7205AP	E1.75	UPC1171C	E1.50	2SC463Y	E0.35		
AN383	E2.25	BA1330	E1.25	HA11705	E6.95	LA4210	E1.60	TA7208P	E1.00	UPC1176C	E1.75	2SC536	E0.35		
AN385	E3.20	BA1330	E1.75	HA11706	E4.75	LA4220	E1.50	TA7210P	E2.60	UPC1177H	E1.60	2SC537	E0.35		
AN386	E2.75	BA1360	E1.80	HA11710	E3.75	LA4230	E2.25	TA7212AP	E2.30	UPC1181H	E1.10	2SC710	E0.35		
AN387	E3.50	BA5102A	E2.75	HA11711	E3.50	LA4250	E2.75	TA7215P	E2.30	UPC1182H	E1.10	2SC732	E0.35		
AN390	E1.80	BA5406	E3.20	HA11713	E6.50	LA4250	E1.60	TA7217AP	E1.60	UPC1183H	E2.20	2SC733	E0.35		
AN391	E1.80	BA6137	E2.75	HA11714	E3.95	LA4422	E1.40	TA7220P	E2.50	UPC1185H	E2.50	2SC734	E0.35		
AN392	E1.85	BA6209	E3.75	HA11715	E6.25	LA4430	E1.40	TA7222AP	E1.90	UPC1186H	E0.90	2SC840	E1.50		
AN393	E1.85	BA6304	E2.20	HA11716	E4.75	LA4440	E2.50	TA7223P	E2.30	UPC1187V	E1.35	2SC900	E0.35		
AN394	E1.95	BA6426	E0.50	HA11717	E5.75	LA4445	E2.75	TA7225P	E3.25	UPC1215V	E1.75	2SC9290	E0.35		
AN395	E1.95	BA6528	E2.90	HA11718	E4.75	LA4460	E1.80	TA7226P	E3.25	UPC1223C	E2.20	2SC9300	E0.35		
AN396	E1.95	BA6558	E2.75	HA11719	E4.46	LA4463	E1.80	TA7227P	E3.25	UPC1225H	E2.00	2SC1034	E4.75		
AN397	E1.95	BA6587	E5.95	HA11745	E9.00	LA4500	E2.60	TA7229P	E1.95	UPC1230H	E2.50	2SC1061	E1.75		
AN398	E1.95	BA6587	E5.95	HA11747	E9.00	LA4505	E2.80	TA7230P	E1.95	UPC1235C	E2.50	2SC1096	E0.35		
AN399	E1.95	BA6587	E5.95	HA11749	E9.00	LA4505	E2.80	TA7232P	E2.95	UPC1277H	E2.75	2SC1364	E0.75		
AN400	E1.95	BA6587	E5.95	HA11749T	E9.00	LA4507	E4.25	TA7240AP	E2.95	UPC1278H	E2.75	2SC1815Y	E4.95		
AN401	E1.95	BA6587	E5.95	HA11749	E4.75	LA4520	E2.50	TA7241AP	E2.95	UPC1300C	E1.20	2SC1875	E2.45		
AN402	E1.95	BA6587	E5.95	HA11750	E4.75	LA5112	E1.85	TA7241AP	E2.95	UPC1335C	E1.95	2SC1942	E3.25		
AN403	E1.95	BA6587	E5.95	HA11751NT	E9.50	LA5120	E1.20	TA7270P	E2.75	UPC1356C	E2.00	2SC1967	E1.75		
AN404	E1.95	BA6587	E5.95	HA11753NT	E9.50	LA7016	E1.20	TA7271P	E1.50	UPC1363C	E2.00	2SC1969	E1.75		
AN405	E1.95	BA6587	E5.95	HA11758NT	E9.50	LA7215	E2.75	TA7312P	E1.50	UPC1378H	E2.40	2SC2078	E0.95		
AN406	E1.95	BA6587	E5.95	HA11768	E4.50	LA7255	E2.75	TA7313AP	E1.50	UPC1382C	E1.10	2SC2166	E0.95		
AN407	E1.95	BA6587	E5.95	HA11768	E4.50	LA7255	E2.75	TA7314P	E1.50	UPC1384C	E2.85	2SC2335	E1.50		
AN408	E1.95	BA6587	E5.95	HA11788	E4.50	LA7255	E2.75	TA7315AP	E2.35	UPC1387C	E2.50	2SC2577	E1.95		
AN409	E1.95	BA6587	E5.95	HA11816NT	E9.50	LA7800	E1.95	TA7317P	E2.75	UPC1395H	E1.50	2SC2579	E1.95		
AN410	E1.95	BA6587	E5.95	HA11829NT	E9.50	LA7810	E2.95	TA7317P	E2.75	UPC1403CA	E3.75	2SC2580	E2.75		
AN411	E1.95	BA6587	E5.95	HA12001W	E9.50	LA7806	E2.75	TA7324P	E1.85	UPC1420CA	E6.50	2SC2580	E2.75		
AN412	E1.95	BA6587	E5.95	HA12002	E2.95	LA7808	E2.75	TA7325P	E1.00	UPC1458C	E0.95	2DA1515	E4.50		
AN413	E1.95	BA6587	E5.95	HA12017	E2.75	LA7827	E2.75	TA7328AP	E2.20	UPC1533HA	E2.75	2DA2002	E0.80		
AN414	E1.95	BA6587	E5.95	HA12035	E3.50	LA8105	E2.20	TA7331P	E2.20	UPC4557C	E1.50	2DA2003	E0.90		
AN415	E1.95	BA6587	E5.95	HA12038	E6.75	LA8106	E2.95	TA7347P	E2.95	UPC4558C	E0.90	2DA2005	E2.75		
AN416	E1.95	BA6587	E5.95	HA12068	E2.75	LA8107	E2.75	TA7348P	E2.95	UPC4559C	E0.90	2DA2005	E2.75		
AN417	E1.95	BA6587	E5.95	HA12143	E2.75	LA8108	E2.75	TA7608CP	E2.70	UPC04514BC	E3.20	2DA2006	E1.50		
AN418	E1.95	BA6587	E5.95	HA12130	E2.95	LA8109	E3.75	TA7609CP	E2.70	X00425C	E2.20	2DA2020	E1.40		
AN419	E1.95	BA6587	E5.95	HA13402	E4.95	LA8113	E3.75	TA7611AP	E2.70	X0077CE	E1.95	2DA2030	E1.40		
AN420	E1.95	BA6587	E5.95	HA13403	E7.50	LA8116	E2.75	TA7614AP	E2.75	X0092CE	E3.50	2DA362A	E3.50		
AN421	E1.95	BA6587	E5.95	HA13404	E4.50	LA8117	E2.75	TA7617AP	E2.75						

T. POWELL

16 PADDINGTON GREEN, LONDON W2 1LG

Tel: 01-723 9246 (Answerphone)

VIDEO BELT KITS		LATE EXTRA	
AKAI VS-2EG/5EG (5)	£2.00	AN5430	£2.95
AKAI VS 9700EG (5)	£2.25	AN7140	£2.20
FISHER VBS 7000 (6)	£2.20	UPC1365C	£3.60
FISHER VBS 9000 (3)	£1.50	UPC1394C	£1.95
HITACHI VT5000 (7)	£2.20	SA11059	£1.95
JVC HR3300/3600 (9)	£2.50	SA11250	£3.25
JVC HR3360/3660 (7)	£2.50	SA11271	£3.95
JVC HR7700 (3)	£1.70	SA1252C	£2.25
PANASONIC NV333 (5)	£1.90	SA5010	£1.50
PANASONIC NV2000 (5)	£1.90	SA5010	£1.50
PANASONIC NV7000 (5)	£1.75	SA5020	£1.50
PANASONIC NV8600 (7)	£2.25	SA5030	£1.50
SANYO VTC5500 (3)	£1.50	SA5030	£1.50
SANYO VTC9300 (4)	£2.75	SA5040A	£1.50
SHARP VC6300 (5)	£2.25	SA5040B	£10.50
SHARP VC7300/7700 (5)	£1.80	SA5050	£8.00
SHARP VC8300 (5)	£2.00	SA5050	£8.00
SHARP VC9300	£1.80	TDA1908	£1.50
SONY SLT7ME/77 (6)	£2.00	TDA2653A	£5.20
SONY SL800/8080 (6)	£2.50	TDA3550	£4.75
SONY SLC7/J7 (6)	£2.00	TDA3560	£4.50
SONY SL800/8080 (6)	£2.50	TDA3651	£2.95
TOSHIBA V5475 (6)	£2.20	TDA4431	£2.25
TOSHIBA V7540 (5)	£2.25	TDA4600	£2.95
TOSHIBA V8600 (6)	£1.80		

CASSETTE MOTORS	
6-9-12-13 2 Volts	£2.95

CASSETTE HEADS	
Mono	£1.50
Auto Reverse	£2.75
Mini-Stereo	£2.75

VIDEO HEADS	
JVC AHSS	£1.50
PANASONIC AHSS	£1.50
PANASONIC NV730	£1.50
SONY DSR36R	£1.50
HITACHI VT5000/6000/9000	£1.50
HITACHI VT1114/33	£1.50
HITACHI VT1171/19	£1.50
SANYO VTC5000	£1.50
JVC IDLER PL147/52	£1.50
HITACHI IDLER VT11-114-17	£1.50

TV CERAMIC SOUND FILTERS	
LEAD TYPE	
SFE 4.5MB	£0.35
SFE 5.5MB	£0.35
SFE 6.0MB	£0.35
SFE 6.5MB	£0.35
SFE 6.8MB	£0.40

MONTANA MAIL ORDER

SPECIAL OFFER
1 470/250 welded can
1 TDA2600 with socket
£9.50

TRANSISTORS		INTEGRATED CIRCUITS	
AC127	£9.34	BRF258	£0.40
AC128	£9.34	BRF259	£0.35
AC176	£9.34	BF336	£0.30
AC187	£9.30	BF337	£0.40
AC188	£9.30	BF338	£0.40
AD149	£1.00	BF355	£0.52
AD161	£0.54	BF362	£0.70
AD162	£0.54	BF422	£0.30
AF124	£0.48	BF423	£0.35
AF125	£0.48	BF458	£0.32
AF126	£0.48	BF459	£0.34
AF127	£0.50	BF462	£0.40
AF239	£0.60	BF597	£0.16
AU113	£0.20	BF939	£0.35
BC107	£0.19	BF979	£0.35
BC108	£0.19	BFY50	£0.35
BC109	£0.19	BFY51	£0.40
BC141	£0.40	BR100	£0.20
BC142	£0.40	BR101	£0.84
BC143	£0.40	BR103	£0.84
BC147A	£0.10	BR303	£1.00
BC147B	£0.12	BSS101	£0.80
BC148	£0.14	BT116	£1.00
BC149	£0.12	BT151-800	£1.00
BC157	£0.12	BU126	£1.00
BC158	£0.16	BU205	£1.00
BC159	£0.12	BU209	£1.40
BC171	£0.15	BU208A	£1.40
BC172C	£0.20	BU208D	£1.00
BC177B	£0.20	BU326A	£1.00
BC182B	£0.11	BU406	£1.00
BC182L	£0.12	BU407	£1.20
BC183	£0.10	BU407A	£1.20
BC183A	£0.10	BU500	£2.30
BC184	£0.12	BU508A	£2.00
BC185	£0.13	BU526A	£2.00
BC186	£0.13	BU806	£1.00
BC187	£0.14	BU907	£1.00
BC192	£0.12	BU984	£1.50
BC212L	£0.14	BYW56	£0.34
BC213	£0.14	BYW96	£0.80
BC214	£0.14	BY1276P	£0.18
BC214L	£0.14	BY133	£0.12
BC237	£0.14	BY164	£0.50
BC238	£0.14	BY179	£0.16
BC239	£0.14	BY206	£0.16
BC258	£0.14	BY210-800	£0.32
BC259	£0.14	BY223	£0.30
BC260	£0.14	BY227	£0.30
BC303	£0.48	BY229-800	£1.00
BC307	£0.13	BY298	£0.24
BC308	£0.14	BY299	£0.26
BC309	£0.10	BYX10	£0.20
BC309B	£0.12	BYX55-600	£0.30
BC327	£0.16	BUX84	£0.40
BC328	£0.14	ME6002	£0.80
BC337	£0.16	MJE340	£0.50
BC337L	£0.16	OA91	£0.16
BC338	£0.16	SKE4F	£0.20
BC413C	£0.18	SKE5F	£1.00
BC547	£0.12	STR441	£0.80
BC548	£0.12	STR451	£0.80
BC549	£0.10	STR6020	£0.20
BC557B	£0.12	TIC44	£0.60
BC558	£0.09	TIP30C	£0.50
BC559	£0.17	TIP31A	£0.54
BC560	£0.20	TIP32A	£0.40
BC727	£0.22	TIP32C	£0.48
BC771	£0.29	TIP33	£1.00
BCX30	£0.15	TIP41A	£0.45
BCX36	£0.15	TIP41C	£0.45
BD124P	£0.76	TIP42A	£0.45
BD131	£0.76	TIP42C	£0.45
BD132	£0.50	TIP47	£0.82
BD136	£0.34	TIP112	£0.72
BD137	£0.40	TIP117	£0.72
BD138	£0.32	TIP132	£1.10
BD139	£0.20	TIP137	£1.10
BD179	£0.72	TIP2955	£0.90
BD203	£0.62	TIP3055	£0.90
BD222	£0.66	VA1104	£0.90
BD225	£0.60	VA8650	£0.56
BD233	£0.60	7805	£0.82
BD234	£0.44	7812	£0.82
BD237	£0.48	IN971	£0.06
BD238	£0.48	IN4001	£0.06
BD239	£0.42	IN4002	£0.06
BD278A	£0.72	IN4003	£0.06
BD410	£1.00	IN4004	£0.06
BD437	£0.50	IN4005	£0.06
BD438	£0.50	IN4007	£0.06
BD441	£0.60	IN4148	£0.04
BD442	£0.60	IN4446	£0.04
BD589	£0.84	IN5410	£0.13
BD707	£0.84	IN5402	£0.17
BD708	£0.84	IN5404	£0.15
BD709	£0.84	IN5406	£0.17
BDX32	£1.00	IN5407	£0.18
BF180	£0.36	IN5408	£0.24
BF178	£0.10	IN3055	£2.00
BF194	£0.20	2N4444	£2.00
BF195	£0.12	2N5246	£0.80
BF196	£0.16	2N5496	£0.80
BF197	£0.22	2N3702	£0.10
BF198	£0.15	2N3703	£0.10
BF199	£0.17	2N3704	£0.10
BF200	£0.60	2N3706	£0.10
BF257	£0.36	2N3904	£0.10
BR-M-300	£0.00	STK436	£0.00
BA301	£1.20	STK439	£0.00
BA311	£1.20	STK441	£13.95
BA313	£1.60	STK443	£13.50
BA511A	£2.50	STK459	£10.00
BA521	£2.30	STK460	£12.95
BA536	£3.00	STK461	£12.95
BA843	£4.00	TAT060AP	£1.00
BA1330	£1.00	TAT072P	£4.00
HA1306W	£2.60	TAT152P	£4.00
HA1322	£3.00	TAT176	£2.46
HA1366W	£1.96	TAT193P	£0.95
HA1366WR	£2.00	TAT201P	£3.00
HA1367	£7.20	TAT203P	£2.60
HA1368	£1.00	TAT204P	£2.00
HA1368R	£2.40	TAT205AP	£1.94
HA1377	£0.00	TAT208P	£2.70
HA1389	£3.36	TAT210P	£4.50
HA1389R	£2.54	TAT211P	£3.00
HA1392	£3.04	TAT215P	£2.95
HA1397	£3.00	TAT222AP	£2.20
HA1398	£4.00	TAT227	£3.40
LA1352	£2.00	TAT229P	£3.40
LA3160	£2.30	TAT313AP	£1.66
LA3350	£1.40	TAT760	£3.00
LA3351	£1.84	TAT760B	£3.05
LA4031P	£3.00	TAT7611	£4.40
LA4032P	£2.00	TAA550	£0.40
LA4051P	£2.00	TAA621	£2.50
LA4100	£1.28	TBA120SB	£1.10
LA4102	£1.46	TBA120U	£1.10
LA4125	£2.02	TBA395	£1.40
LA4220	£1.00	TBA396	£1.34
LA4422	£2.00	TBA520	£1.60
LA4430	£1.50	TBA530Q	£1.00
LA4460	£3.00	TBA540	£1.50
LA4461	£3.00	TBA560	£1.30
LM1011	£2.24	TBA720A	£1.86
MS152L	£1.00	TBA750Q	£3.00
MS1515BL	£3.02	TBA800	£1.12
MS3274P	£1.40	TBA810S	£1.46
MC1352	£1.10	TBA920	£1.90
MB3705	£2.00	TBA950 2X	£2.40
MB3712	£1.00	TBA990	£1.55
MC2113	£1.00	TBA1441	£1.00
ML2318	£2.60	TCA2700	£2.20
ML237	£2.60	TCA800	£7.00
ME555	£0.40	TCA940	£2.00
SA1124	£3.00	TDA440	£3.00
SA1025	£4.00	TDA1002	£1.60
SA10510	£0.00	TDA1003	£3.70
SA1251	£4.00	TDA1006	£2.40
SASS60	£2.10	TDA1035T	£3.50
SASS70	£2.52	TDA1044	£3.20
SASS80	£3.00	TDA1074	£1.70
SASS90	£3.00	TDA1170	£2.94
SL901	£7.50	TDA1180P	£2.94
SL917	£7.50	TDA1190P	£2.94
STA401	£0.00	TDA1236	£4.30
STK0059	£0.00	TDA1327	£1.60
STK011	£4.00	TDA1412	£1.52
STK013	£1.00	TDA15120	£2.00
STK014	£1.00	TDA1770	£5.95
STK016	£1.00	TDA1908	£2.00
STK077	£0.00	TDA2003	£1.96
STK080	£1.00	TDA2004	£3.00
STK433	£0.00	TDA2006	£1.00
STK435	£0.50	TDA2010	£2.00
STK436	£0.00	STK439	£0.00
STK441	£13.95	STK443	£13.50
STK459	£10.00	STK460	£12.95
STK461	£12.95	TAT060AP	£1.00
TAT072P	£4.00	TAT152P	£4.00
TAT176	£2.46	TAT193P	£0.95
TAT201P	£3.00	TAT203P	£2.60
TAT204P	£2.00	TAT205AP	£1.94
TAT208P	£2.70	TAT210P	£4.50
TAT211P	£3.00	TAT215P	£2.95
TAT222AP	£2.20	TAT227	£3.40
TAT229P	£3.40	TAT313AP	£1.66
TAT760	£3.00	TAT760B	£3.05
TAT7611	£4.40	TAA550	£0.40
TAA621	£2.50	TAA9503	£3.70
TBA120SB	£1.10	UA741	£0.80
TBA120U	£1.10	UPC1020	£2.50
TBA395	£1.40	UPC1025H	£3.00
TBA396	£1.34	UPC566H	£1.40
TBA520	£1.60	UPC575C2	£1.70
TBA530Q	£1.00	UPC576	£3.00
TBA540	£1.50	UPC587C2	£1.68
TBA560	£1.30	UPC1020	£2.50
TBA720A	£1.86	UPC1025H	£3.00
TBA750Q	£3.00	UPC1026C	£1.25
TBA800	£1.12	UPC1028H	£1.25
TBA810S	£1.46	UPC1031	£2.00
TBA920	£1.90	UPC1032H	£0.70
TBA950 2X	£2.40	UPC1156H	£2.40
TBA990	£1.55	UPC1181	£1.60
TBA1441	£1.00	UPC1182H	£1.70
TCA2700	£2.20	UPC1185	£3.45
TCA800	£7.00	UPC1186	£4.00
TCA940	£2.00	UPC1365C	£5.50
TDA440	£3.00	UPC2002	£1.60
TDA1002	£1.60	Z80MPL	£2.50
TDA1003	£3.70		
TDA1006	£2.40		
TDA1035T	£3.50		
TDA1044	£3.20		
TDA1074	£1.70		
TDA1170	£2.94		
TDA1180P	£2.94		
TDA1190P	£2.94		
TDA1236	£4.30		
TDA1327	£1.60		
TDA1412	£1.52		
TDA15120	£2.00		
TDA1770	£5.95		
TDA1908	£2.00		
TDA2003	£1.96		
TDA2004	£3.00		
TDA2006	£1.00		
TDA2010	£2.00		
TDA2020	£2.00		
TDA2030	£3.00		
TDA2151	£3.00		
TDA2160	£4.00		
TDA2170	£4.10		
TDA2522	£2.00		
TDA2525	£4.50		
TDA2540	£1.80		
TDA2541	£3.20		
TDA2545	£4.80		
TDA2576A	£4.25		
TDA2581	£3.12		
TDA2593	£2.50		
TDA2600	£7.00		
TDA2611A	£2.10		
TDA2640	£3.15		
TDA2640A	£4.95		
TDA2690	£2.56		
TDA2785	£3.95		
TDA3190	£3.50		
TDA3950A	£3.00		
TDA4290	£3.90		
TDA4420	£3.00		
TDA4431	£2.64		
TDA4500	£3.25		
TDA4503	£4.30		
TDA4600-2	£3.00		
TDA4600-20	£3.00		
TDA49503	£3.70		
UA741	£0.80		
UPC1020	£2.50		
UPC566H	£1.40		
UPC575C2	£1.70		
UPC576	£3.00		
UPC587C2	£1.68		
UPC1020	£2.50		
UPC1025H	£3.00		
UPC1026C	£1.25		
UPC1028H	£1.25		
UPC1031	£2.00		
UPC1032H	£0.70		
UPC1156H	£2.40		
UPC1181	£1.60		
UPC1182H	£1.70		
UPC1185	£3.45		
UPC1186	£4.00		
UPC1365C	£5.50		
UPC2002	£1.60		
Z80MPL	£2.50		
I/C SOCKETS			
8 pin	£0.30		
14 pin	£0.30		
16 pin	£0.30		
16 pin On to			
Quill	£0.35		
18 pin	£0.30		
20 pin	£0.30		
22 pin	£0.30		
24 pin	£0.30		
28 pin	£0.40		
40 pin	£0.80		
MIXED DIELECTRICS			
.01mfd 1000V	£0.25		
.047mfd 1000V	£0.45		
.10mfd 1000V	£0.45		
.22mfd 1000V	£0.66		

CENTRAL

T.V. & VIDEO WHOLESALERS LTD.
BIGGEST SELECTION – KEENESE PRICES

SPECIAL OFFERS THIS CRISTMAS

VHS — WORKING

★ STAR BUY

FERGUSON
MECHANICAL
FROM

£65



ELECTRONIC
FROM

£110

★ STAR BUY – FERGUSON PORTABLE COLOUR TX90 – 14" from **£90**

PLUS LATE MODEL FRONT LOADER e.g. FERGUSON 3V45

3V24, 3V29/30 – HITACHI, PANASONIC, etc.

UNTESTED BETA from **£25**. PHILIPS 2020 from

£10

★ STAR BUY – FERGUSON 9K from only

£15

PLUS 4K from

£8

PHILIPS G11 from

£25

G8-550 from

£10

ALSO IN STOCK: FERGUSON TX10 TXT. & STEREO TXT

ALL SIZES — IN MINT CONDITION INC. HANDSET

LARGE SELECTION OF HITACHI/FERGUSON VIDEO HEADS

GRADE B T.V., AUDIO, HI-FI etc.

EXPORT
ENQUIRIES
WELCOME


All Prices based on quantity and are subject to 15% VAT

Phone 01-807 4090
01-884 1314

CENTRAL, Cedar House, Nobel Road, Eley Estate, Edmonton N18

TAYLOR

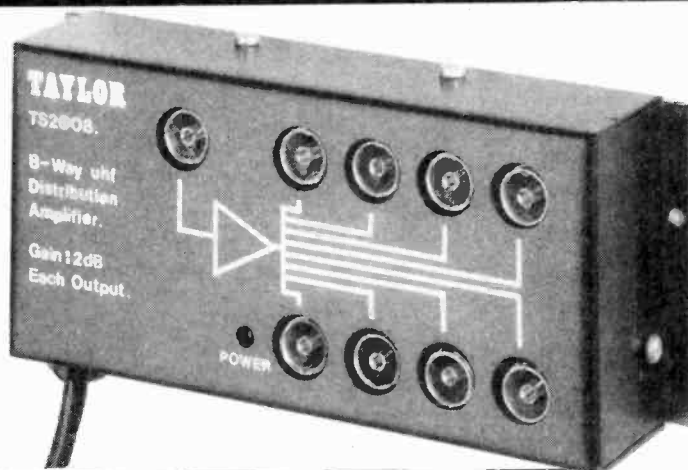T.S. 2008 8 WAY U.H.F. T.V.
DISTRIBUTION AMPLIFIER



SPECIFICATION

Frequency	-	470-860 MHz
Gain per Outlet	-	2dB minimum
Power Requirement	-	240V A.C. 4.8 Watts

RUGGED SCREENED CASE

PRICE

1- 3	£19.95 each
4-19	£15.62 each
20-99	£13.86 each
100 +	£13.48 each

Prices exc. V.A.T. & Carriage.

TAYLOR BROS (OLDHAM) LTD
BISLEY STREET WORKS, LEE STREET,
OLDHAM, ENGLAND.

TELEPHONE: 061 652 3221 TELEX: 669911

FAST VIDEO SPARES FAST

VIDEO HEADS

Panasonic	
NV2000, 2010, 7000, 7200, 8600, 8610, 333, 370 genuine	£39.50
NV366, 688, 777, 788 genuine	£56.95
Panasonic 4HSS Equivalent heads	£31.95
Ferguson	
3V22, 3V00, 3V16, 3V22, 3V23, 3V24, 3V29, 3V30, 3V35, 3V36, 3V38 genuine	£39.50
Ferguson 3HSS Equivalent heads	£31.95
Sharp	
VC9300, 9500, 9700, 381, 386, 387, 388, 482, 581 genuine	£49.90
Sharp VC7300, 7700, 8300 genuine	£58.20
Sharp VC9300 etc Equivalent	£39.90
Sony	
C5, C6, C7 genuine	£49.50
Sony SL8000, 8080 genuine	£54.50
Sony C9, C20, C30 genuine	£54.50
Sony C9, C20, C30 Equivalent	£36.50
Sony C5, C6, C7 Equivalent	£31.95
Sanyo	
VT9300, 5000, 5150, 5300, 5400 genuine	£49.90
Toshiba	
V9600, V31, V33 Equivalent	£42.50
Toshiba V9600, V31, V33 genuine	£49.90
Toshiba V8600 genuine	£56.95
Hitachi	
VT5000, 8000, 8300, 9300, 9500, 9700, VT11, VT14E genuine	£39.95

PINCH ROLLERS

Panasonic	
NV2000, 7000, 7200	£5.95
NV333, 366, 688, 370	£6.95
NV430, 730	£6.95
Sharp	
VC6300	£5.95
VC7300, 7700, 8300	£7.90
VC9300, 381, 386 etc	£4.90
Hitachi	
VT5000, 8000, 9000	£6.95
VT11E, 14E, 17E, 19E	£6.95
Sony	
C5, C6, C7	£5.95
SL-C20, C30, C40	£6.95
SL8000, 8080	£12.75
Ferguson/JVC	
3V00, 3V16, 3V22	£5.95
3V23, 3V24, 3V29/30	£7.95
3V35, 36, 38, 39	£8.90
Sanyo	
VT9300, 5000, 5300	£7.95
VT9300, 5150, 6500	£7.95

SENSOR LAMPS

All Panasonic	£1.80
All Ferg/JVC	£1.80
Sharp VC9300 etc	£2.15
Sharp VC7300 etc	£2.60
Amstrad 7000	£2.15
All Hitachi	£1.80

SENSOR L.E.D.'s

All Panasonic	£2.90
All Ferg/JVC	£2.90
All Hitachi	£5.75

**HUNDREDS OF SPARES FOR
PANASONIC, HITACHI, SANYO,
SONY, FERGUSON, ETC.
AVAILABLE**

**WE CARRY HUNDREDS OF VIDEO SPARES
INC. PLAY IDLERS, CLUTCHES, MOTORS,
SERVICE MANUALS, TENSION BANDS,
BELTS AUDIO/CONTROL HEADS,
ALIGNMENT TOOLS AND TAPES ETC.
SPECIAL ORDER FACILITIES
FOR NON-STOCK ITEMS**

ALL SPARES LISTED ARE GENUINE PARTS. WE ALSO STOCK THE FULL RANGE OF CHEAPER REPLACEMENT PARTS E.G. BELT KITS, PINCH ROLLERS, HEADS, ETC. P.O.A.

**CREDIT CARD
ORDERS BY
TELEPHONE
RECEIVED BY
4 PM. ARE
DESPATCHED
SAME DAY**

IDLERS

Panasonic	
NV2000, 7000, 7200	£3.45
NV333, 366, 688, 788	£3.45
NV777, 370, 430	£4.50
NV730	£6.50
Sharp	
VC9300, 9500, 9700	£3.90
381, 386, 387, 388	£3.90
482, 483, 486, 581 etc	£3.90
Amstrad	
7000	£3.90
Sony	
C5/C7 Idler kit	£6.95
C6 Idler kit	£6.95
C5/C7 Idler only	£1.65
Sanyo	
Reel drive pulley	£8.88
VT9300, 5150, 6500	£8.88
Hitachi	
VT8000, 8300, 8500	£4.72
VT9300, 9500, 9700	£4.75
VT11E, 14E, 17E, 19E	£6.50
Ferguson	
Clutch assy large	£6.95
3V29, 3V30, 3V16, 3V22	£6.95
Clutch assy small	£6.95
Idler assy 3V29, 30	£3.45
3V35, 3V36, 3V38, 3V39	£4.50
Fisher	
FVHP615	£6.90

MOST OTHERS AVAILABLE

BELT KITS (GENUINE)

Panasonic	
NV2000, 2010	£6.50
NV7000, 7200	£6.50
NV333, 366	£6.50
NV688, 788	£4.70
NV8600, 8610	£6.50
Sharp	
VC6300	£6.50
VC7300, 7700	£6.50
VC8300	£6.50
VC9300, 381 etc	£6.50
Sanyo	
VT9300	£6.50
VT9300	£1.99
VT9300, 5400	£6.50
Sony	
SLC5, C7	£6.50
SLC6	£7.50
SL8000, 8080	£6.50
Hitachi	
VT5000	£6.50
VT8000, 8500	£2.90
VT9300, 9300	£3.30
VT11E, 14E, 17E	£6.50
Ferguson/JVC	
3V00, 3V16, 3V22	£6.50
3V23	£4.50
3V29, 3V30	£6.50
3V35, 36, 38, 39	£3.90
Toshiba	
V8600	£6.50
V9600	£6.50
MOTORS	
Reel Motors	
Sharp 9300 etc	£15.30
Amstrad 7000	£15.30
Sanyo 5000 etc	£14.20
Panasonic NV333	£14.20
Drum Motors	
Ferg/JVC, 3V22 etc	£36.60
Sharp 9300 etc	£24.60
Hitachi VT5000	£22.75
VT8000, 8300, 8500	£37.70
VT9300, 9500	£37.70
VT11E, 14E, 17E	£27.30
Capstan Motors	
Sharp 9300, 9500	£24.60
VC8300	£39.90
VC7300, 7700, 7750	£24.60
Ferg/JVC, 3V22 etc	£36.60
3V29, 3V30	£29.60
3V35, 36, 38, 39	£36.90
Hitachi VT5000	£22.75
VT8000, 8300, 8500	£37.70
VT9300, 9500	£37.70
VT11E, 14E, 17E	£27.30

TELEVIDEO SERVICES

145 STATION RD, BEESTON, NOTTINGHAM NG9 2AZ, TEL: 0602-226070



Send 2 x 17p stamps for full catalogue.

Please add 50p post & packing and then add 15% VAT to total

OVERSEAS ORDERS WELCOME ON CREDIT CARDS, POSTAGE AT COST

INSTALL YOUR OWN SYSTEM AND SAVE

SECURITY

MODULES ACCESSORIES KITS

NEW

Control Unit CA 1382

with automatic circuit testing and simple on/off operation.

- Fully automatic siren re-set.
- Audible entry & exit warning.
- Alarm Sounded memory.
- 2 separate loop inputs + 24hr circuits.
- Built-in electronic siren.
- Easily installed, full instructions supplied.



This brand new control panel provides effective and reliable control of all types of security installations. Using advanced electronics, the unit automatically checks the loop circuits every time that it is switched on, thereby reducing the possibility of false alarms and incorrect operation. Using a simple on/off key switch, it is easily operated by all members of the family. Additionally, 24hr personal attack and anti-tamper protection is provided irrespective of whether or not the unit is switched on. Housed in a strong, attractive steel case, the unit is supplied with full operating instructions and 2 keys. Supplied fully built and tested ready for installation.

Also available in kit form with fully built electronics
£39.95 + VAT

ONLY **£44.95 + VAT**

RISCAMP LIMITED

Dept TV62,
51 Poppy Road,
Princes Risborough,
BUCKS. HP17 9DB
Tel: (084 44) 6326



Order by 'phone or mail or call at our showroom and see

UNITS ON DEMONSTRATION

Monday to Friday 9.00 - 5.00 p.m.
Saturday 9.00 - 1.00 p.m.
Please add 15% VAT and 75p P&P to all UK orders
Export no VAT - postage at cost

Lighting Controller DP 3570

only **£13.95 + VAT**



This versatile module provides timed switching of loads up to 3A for pre-set times between 10 secs and 5 mins. The timed period being triggered by the opening or closing of an external loop or switch. The built-in 12V 250mA power supply is available for operating external sensors. Priced only £13.95 + VAT Suitable plastic enclosure, £2.85 + VAT

500W Quartz Halogen Floodlight FL 500

only **£14.95 + VAT**



Whilst intended for security lighting applications, this unit is suitable for lighting patios, pathways and gardens etc. Supplied complete with 500W lamp, priced only £14.95 + VAT Protective grill, £1.95 + VAT

Infra-red System IR 1470



only **£25.61 + VAT**

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 80 x 50 x 35mm

HW 1250 - Enclosure & fixings for CA 1250

only **£9.50 + VAT**



This attractive case is designed to house the control unit CA 1250 together with the appropriate LED indicators and key switch (Extra). Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 x 180 x 700mm.

Control Unit CA 1250

Price **£19.95 + VAT**



This tried and tested control unit represents the finest value for money in control systems, providing the following features:

- Built-in electronic siren drives 2 loud speakers.
- Provides exit and entrance delays together with fixed alarm time
- Battery back up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

Individual Enclosure SC 5063

only **£2.95 + VAT**

Suitable metal enclosure for housing the ultrasonic module type US 5063. Supplied with the necessary mounting pillars and screws etc.

Digital Ultrasonic Detector US 5063

only **£13.95 + VAT**

- 3 levels of discrimination against false alarms
 - Crystal control for greater stability
 - Adjustable range up to 25ft
 - Built-in delays
 - 12V operation
- This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

Complete systems from only £39.95 + VAT

For full information of systems and accessories, send or call for details.

LOOK AHEAD!


WITH MONOLITH MAGNETIC TAPE HEADS

DOES YOUR VCR GIVE WASHED OUT NOISY PICTURES - ITS PROBABLY IN NEED OF A NEW HEAD - FAST FROM OUR EX-STOCK DELIVERIES. SAVE £££'s ON REPAIR CHARGES.

Our replacement video heads fit most models of VHS or Betamax VCR's. Following our replacement guide and with a practical ability, you can do the whole job in your own home with our head replacement kit.



VIDEO HEAD REPLACEMENT KIT

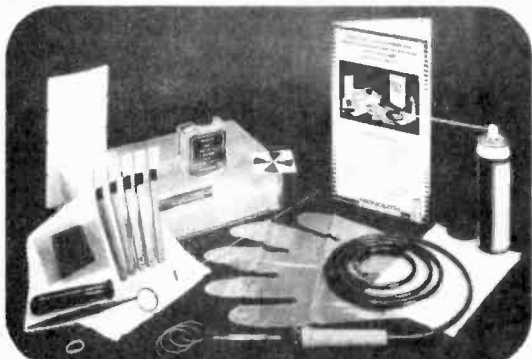

VMC-02 KIT ONLY £19.95 inc. VAT + £2.50 p&p
(Kit does not include video head)

TELEPHONE US NOW FOR INFORMATION OF THE REPLACEMENT HEAD FOR YOUR VIDEO RECORDER.

CATALOGUE: For our full Catalogue of Replacement Video and Audio Cassette/Reel to Reel Heads, Motors, Mechanisms, etc. Please forward 50p p&p.

THE MONOLITH ELECTRONICS CO. LTD.
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England.
Telephone: Crewkerne (0460) 74321 Telex: 46306 MONLTH G

TUBES

New and rebuilt for most makes of T.V.

including:

Hitachi, Panasonic, Philips, Thorn, Toshiba, Sharp, Sony and Mullard 20AX, 30AX etc.

Two year guarantee with a four year option.

Tube fitting service available.

Cash or credit allowed for certain types of In-line glass.

Nationwide delivery.

Price list available on request.

EXPRESS T.V. SUPPLIES

Rugeley, Staffs.

08894-77600

(9.00-6.00 Mon-Sat)

Bristol

0454-316285

(After 4pm)

A.J.C.

Exmouth

0395-

266210

— NEW VIDEO HEADS —

**£24.95 each plus V.A.T.
& carriage**

Our selected range of NEW VIDEO HEADS have been manufactured to the Highest specification and are fully Guaranteed for 1 Year.

Although these units are Totally New Assemblies and an exchange unit is not necessary, we offer an extra discount of £1.00 per returned drum for each New Electrovisia Head purchased.

For quantity discounts and Trade Terms please contact us.

**ELECTROVISIA
LIMITED**

P.O. Box 55
Stratford-upon-Avon
Warks. CV37 0UB
0789-298510

HITACHI VHS COLOUR CAMERAS

Mains Only Tested/
Working

VHS VIDEOS

FERGUSON

3V00, 3V22, 3V23, 3V16, 3V29,
3V30, 3V31, 3V32, 3V35

NATIONAL PANASONIC
NV8600, 8610, 2000, 7000,
370, 333, 2010

SHARP

620, 630, 640, 2300 H T/P

BETAMAX

SANYO VTC 9300, 5000, 5300

SONY C5, C6, C7, C9
and SL F1UB T/P

Also Bush, Toshiba, Hitachi and Blau Punkt

PLUS

17" 18" 20" 22" 26" Hybrid/
Solid State CTVs
Remote Control & Teletext

Discount for Quantities

Complete loads delivered from pick up point

**JOHN CARTER
(Electrical) LTD
FURNACE ROAD,
GALLOW'S INN,
ILKESTON**

Phone: 0602 303124

RECHARGEABLE BATTERIES SPECIAL OFFERS

**FERGUSON 12v RECHARGEABLE
BATTERIES TYPE VA214 — NEW!**




Suits JVC 2650 PORTABLE, JVC 2200, FERGUSON 3V24. Also suits JVC 6" MONITORS, MODEL No's TM22, TM41. ONLY £25 each including post and packing

ONLY £25

UNIVERSAL NICAD CHARGER

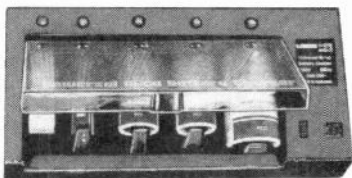A brand new universal charger (charges any combination of PP3, AA, C & D CELLS), complete with 4 rechargeable AA/HP7 cells (ex-equipment but tested and guaranteed) for only £6.95 plus 80p post and packing.



ONLY £6.95

NEW NICADS AA, PP3, C and D cells.

Send for Price List.

E. CROYDON DISCOUNT ELECTRONICS
40 LOWER ADDISCOMBE ROAD, CROYDON, SURREY
☎ 01-688 2950 SHOP HOURS Mon-Sat
10-5.30 (Closed Weds)

**BRITAIN'S
LARGEST SUPPLIERS
OF
EX-RENTAL TV
AND VIDEO
SPECIAL OFFER**



VHS VHS VHS

**HITACHI
5000**

**FERGUSON
3V22**

£60



*Makes inc. PHILIPS, GEC,
HITACHI, ITT, BUSH,
PANASONIC, SONY, DECCA,
FERGUSON, GRUNDIG etc.*

COLOUR TV from £5

**CALL & SEE OUR SELECTION
DELIVERY ARRANGED FOR
BULK PURCHASES
LOAD DIRECT FROM SOURCE
AT VERY KEEN PRICES**

FRANK FORD

(TV TRADE DISPOSALS)

SCHOOL LANE

GUIDE

BLACKBURN, LANCS

TEL: 0254 64489

**CelTel
wish you a
Merry
Christmas
and a
Profitable
New Year.**

During 1987 make CELTEL your profitable choice
for Ex-rental TV's & VCR's.

CELTEL

2 BREACH ROAD, WEST THURROCK, ESSEX. TEL: (0708) 861404

Phone: 0800-289239 (Toll Free)

BOLTEN LTD.

63, JEDDO ROAD, LONDON W12 9EE.

Tel: 01-749 0915 (2 lines)

Telex: 262421 BOLTEN G

VIDEO HEADS

Sony (Universal)	£33.95
Sony C9.....	£47.95
Ferguson/JVC (Universal)	£32.95
National Panasonic (Universal)	£32.95
National Panasonic (370/380/430/460)	£35.95
National Panasonic (777/330)	£46.95
National Panasonic (3 Pin Head)	£48.95
Hitachi	£35.95
Hitachi VT11/HIVI/VT33 (Originals).....	£38.95
Toshiba.....	£46.95
Sanyo Genuine.....	£46.95
Fisher VHS Genuine.....	£51.95
Akai (most Models)	£32.95
Sharp	£46.95
Belt Kits (Most Models)	£3.99
Remote Controls for T.V.	
Grundig/Philips	£16.95
Remote Controls Philips Teletext (4300)	£17.95
Pinch Wheels (various Models).....	£5.95
Idler Kits for Sony	£4.50

Other Accessories – Mod kits, Integrated Circuits, Idler Assy, Gear Idler Assy, Reel & Loading Belts, Capstan & Reel motors, Reel Drive Pully Units also available in most models. Please call for full list.

Please add 15% VAT plus £1.00 p&p per order.

Delivery within 7-14 days subject to availability.

**PLEASE NOTE OUR NEW ADDRESS
AND TELEPHONE NUMBER**



AA117	9p	BC337	6p	BF184	20p	BFY57	25p	TIP32A	24p	2N.1132	28p	BY296	20p	7818	35p	PCL805	55p	LA-4461	180p	TBA560	100p	74L522	17p
AA119	9p	BC338	6p	BF185	20p	BFY64	25p	TIP32C	24p	2N.1132	28p	BY298	20p	7824	35p	PFL200	85p	LA-5112	120p	TBA750	100p	74L524	38p
AA132	2p	BC339	6p	BF190	5p	BFY90	25p	TIP33	24p	2N.1673	24p	BY299	20p	7835	35p	PL36	80p	LM301	26p	TBA800	35p	74L526	17p
AC107	2p	BC340	6p	BF195	5p	BLY48	85p	TIP34	24p	2N.1711	24p	BY416	90p	7812	40p	PL82	45p	LM311	26p	TBA810S	60p	74L527	17p
AC126	17p	BC341	6p	BF196	5p	BLY49	85p	TIP41A	22p	2N.2102	50p	BYX10	15p	7915	40p	PL83	32p	LM324	35p	TBA820	75p	74L528	17p
AC127	15p	BC342	6p	BF197	7p	BR100	14p	TIP41C	25p	2N.2160	300p	BYX55/350	30p	7918	40p	PL84	50p	LM325	45p	TBA820	100p	74L530	17p
AC128	15p	BC343	6p	BF198	7p	BR101	14p	TIP42A	22p	2N.2218A	24p	BYX55/600	30p	7924	40p	PL95	140p	LM329	45p	TBA850	100p	74L532	17p
AC129	15p	BC344	6p	BF199	7p	BR102	14p	TIP42B	22p	2N.2218B	24p	BYX55/800	30p	7812	40p	PL500	110p	LM339	40p	TBA900	100p	74L534	17p
AC141K	17p	BC345	6p	BF200	18p	BSX20	15p	TIP47	40p	2N.2221	23p	BYX70/300	29p	7812	28p	PL504	95p	LM348	60p	TCA270	40p	74L537	17p
AC142K	30p	BC346	6p	BF201	18p	BSX26	18p	TIP48	40p	2N.2222	23p	BYX70/500	32p	7815	28p	PL508	170p	LM360	100p	TCA800	200p	74L537	17p
AC153K	23p	BC347	6p	BF202	18p	BSX29	19p	TIP50	60p	2N.2369	15p	BYX55/600	30p	7824	28p	PL519	450p	LM381	150p	TCA940	100p	74L538	17p
AC176	18p	BC348	6p	BF203	18p	BSX32	20p	TIP51	60p	2N.2396	18p	BYX55/800	30p	7812	40p	PL500	110p	LM382	130p	TDA1170	100p	74L540	39p
AC176K	6p	BC349	6p	BF204	18p	BT109	90p	TIP52	120p	2N.2646	40p	OAA47	6p	7915	40p	PL508	170p	LM387	100p	TDA1412	60p	74L542	39p
AC178	17p	BC350	6p	BF205	18p	BT116	80p	TIP53	120p	2N.2904	20p	OAA90	4p	7912	45p	PL500	110p	LM390	100p	TDA2002	80p	74L547	70p
AC187K	20p	BC351	6p	BF206	18p	BT119	100p	TIP54	140p	2N.2905	20p	OAA91	4p	7915	45p	PL500	110p	LM390	100p	TDA2003	150p	74L548	60p
AC188	17p	BC352	6p	BF207	18p	BT120	100p	TIP55	140p	2N.2906	20p	OAA90	4p	7915	45p	PL500	110p	LM390	100p	TDA2003	150p	74L551	17p
AC188K	23p	BC353	6p	BF208	18p	BU100A	110p	TIP107	65p	2N.2926	8p	IN.914	2p	LM3137K	220p	AN-240P	150p	M741 MET	58p	TDA2030	140p	74L554	17p
ACV18	48p	BC354	6p	BF209	18p	BU104	110p	TIP107	65p	2N.2926	8p	IN.914	2p	LM3137K	220p	AN-240P	150p	M741 MET	58p	TDA2522	90p	74L555	17p
ACV19	48p	BC355	6p	BF210	18p	BU105	110p	TIP110	47p	2N.3019	28p	IN.4001	4p	LM323C	420p	AN-7110	140p	LM748	35p	TDA2530	100p	74L573	28p
AD142	60p	BC356	6p	BF211	18p	BU108	110p	TIP111	50p	2N.3053	18p	IN.4002	4p	LM723	32p	AN-7114	140p	LM1458	35p	TDA2540	100p	74L574	28p
AD149	45p	BC357	6p	BF212	18p	BU110	110p	TIP112	40p	2N.3054	35p	IN.4003	4p	78HGKC	670p	AN-7115	160p	LM1990	30p	TDA2540	100p	74L575	32p
AD161	22p	BC358	6p	BF213	21p	BU111	140p	TIP115	45p	2N.3055	35p	IN.4004	4p	78HGKC	520p	AN-7120	140p	M-51513L	180p	TDA2560	100p	74L576	28p
AD162	22p	BC359	6p	BF214	21p	BU112	140p	TIP116	45p	2N.3055H	50p	IN.4005	4p	78HGKC	520p	AY3-1270	680p	M-51515B	270p	TDA2593	100p	74L578	34p
AF124	25p	BC360	6p	BF215	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51516	280p	TDA2590	100p	74L583	48p
AF125	25p	BC361	6p	BF216	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AF126	25p	BC362	6p	BF217	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AF127	25p	BC363	6p	BF218	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AF139	22p	BC364	6p	BF219	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AF238	22p	BC365	6p	BF220	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AL112	70p	BC366	6p	BF221	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AL113	80p	BC367	6p	BF222	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AS215	100p	BC368	6p	BF223	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AS217	100p	BC369	6p	BF224	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AU110	110p	BC370	6p	BF225	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AY102	180p	BC371	6p	BF226	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
AY106	180p	BC372	6p	BF227	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BA146	10p	BC373	6p	BF228	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BA148	10p	BC374	6p	BF229	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BA154	6p	BC375	6p	BF230	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BA157	12p	BC376	6p	BF231	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BB101	13p	BC377	6p	BF232	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BB103	13p	BC378	6p	BF233	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BB105	13p	BC379	6p	BF234	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BB205B	24p	BC380	6p	BF235	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC107	7p	BC381	6p	BF236	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC108	7p	BC382	6p	BF237	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC109	7p	BC383	6p	BF238	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC115	10p	BC384	6p	BF239	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC118	11p	BC385	6p	BF240	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC140	19p	BC386	6p	BF241	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC141	19p	BC387	6p	BF242	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC142	19p	BC388	6p	BF243	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC143	19p	BC389	6p	BF244	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC147	6p	BC390	6p	BF245	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p
BC148	6p	BC391	6p	BF246	21p	BU124	60p	TIP127	50p	2N.3440	58p	IN.4006	4p	78HGKC	215p	AY3-1350	300p	M-51517	280p	TDA2590	100p	74L583	48p

SPECIAL OFFER THIS MONTH

**PHILIPS YEARS AHEAD
THE CREDIT CARD CALCULATOR
SOLAR POWERED £4.75**

NEW PHILIPS SBC 1R31 Solar & Battery Powered Calculator **£8.00**

NEW PANELS

G8 100K Pots on Panel & Lead for 6 Push Button Unit	£2.00
K30 Mains Switch remote	£1.00
K35 Mains Switch remote	75p
K35 Aerial Socket and Plug in Lead to Tuner	£1.50
KT3-K30 Slider Pots 4.7ku 47ku	20p each
LARGE Focus Pots. Fis Pve, GEC, ITT, Decca	75p
G8 Power Supply Panel	£4.00
EX DECCA 80 Line O/P Panel	£5.00
EX DECCA 80-100 Decoder	£5.00
EX DECCA 80-100 Frame	£5.00
THORN 8000-8500-8800 Decoder	£6.00
GLASS BEADS Diodes 200v/1.2A	25 for £1.00
G11 IF Panel	£8.00
THORN 9000 Line Panel	£12.00
G11 Decoder Panel	£8.00
POWER SUPPLY 731	£6.00
G11 611 Condenser 470/250V ITT	£1.50
G9 Power Panel	£3.50
G8 Line Panel	£12.00
G8 6 Push Button	£9.00
KT4-KT3-KM Handset Replacement	£8.00
HF1250 METER 20,000 Fuse Diode Protector Logic Test Facility	£15.90
9000 SERIES Decoder 011 929 014 080 Thorn	£5.00
THORN TX remotor panel 51.C ML923.SI.490.MC1452HB-MC14493P-SL470 & Main Trans	£5.00
MAX G1C LOPT Panel with Split Diode	£4.00
LOPT Split Diode 2432871	£7.00
RANK T20 Focus Pot	75p
RANK 718 Focus Pot	£1.00
THORN 9000 LOPT Panel	£12.00
26" LOPT Split Diode 2432801	£8.00
16" LOPT Split Diode 2433481	£6.00
Ex Panel Split Diodes 2432871/2432981	£5.00
HITACHI Mains Switch	50p
HITACHI AE Socket	30p
1 CONDENSER Axial Leads 450 /A/C 1200 D/C	15p
MAINS TRANSFORMER 240v in/200v	£1.00
GREEN FLAT. NEC. LED'S	3p each 100 for £2
124-12V 2.8VA Print 1"x1"	75p
84-8V 1 Amp Print	75p
HITACHI 6 x 4 8Ω Speaker	50p
ET596 UHF V/CAP Tuner, small	£2.50
FIDELITY Panels with I.C.	£1.00
FIDELITY LOPT Split Diode AT2076/80	£3.00
FIDELITY FBS 1245AE LOPT Mono	£1.00
FIDELITY Split Diode FCC2015BE	£5.00
H-FI MICROPHONE N8501 Philip	£8.00
G8 TUNER V/CAP on Panel	£3.50
G8 SPEAKER	75p
9,000 SPEAKER	£1.00
5 AMP METERS, AC, DC	£2.00
THORN 9000 Sound O/P Panel	£9.00
ONE I.C. K35 Decoder	£7.00
THICK FILM, Hitachi RB-32 4A	£2.00
K30 IF/K35 IF	£3.00
THICK FILM, Hitachi Frame	£5.00
THORN Lopt 8500-8800	£4.00
TX9 THORN Tuner Panel with ICS Pots	£3.00
N.E.C. Light Emitting Diodes	40p
Split Diode 2433752	£6.00
BY223 Replacement	30p
THORN CHASSIS 1600-1700 Series Mono	£10.00
THORN 1600 Rec & Anode Cap	50p
KT3-K30 Slider Pots 4.7k	£1.00 for 10
ET-614 UHF V/CAP Tuner	£2.00
6 x 2 1/4 SPEAKER 5W Hitachi 80	50p
K35 20 Turn Pots	6p each
HITACHI & GEC 20k Pots	20 for £1.00
KT3 K30 Speaker	30p
K35 Sound O/P Panel Plug in	£3.00
K35 12 way Push Button Unit	£1.50
K35 L.O.P.T. Split Diode	£6.00
RANK T20 Front Panel	£6.00
G8 6 Button Unit, New Type	£9.00
6 off LED DISPLAYS, Mixed	£1.00
HAND SET TESTER, Infra Red	£8.00
PHILIPS SBC 471 2 Way Stereo Headphone with Volume Controls	£17.00
AERIAL SPLITTER with filter	£1.00
DYNAMIC STEREO HEADPHONE EM 6146	£10.00
PHILIPS UNI DIRECTIONAL Dynamic Microphone	£10.00
20 TURN POT'S with Band Switch	10p
PUSH BUTTON Mains Switch with Screw Holes Fixing	4 for £1
PYE 713 Line Trans	£4.50
PYE 731 Line Trans	£4.50
800p DIODES at 3 amps. Glass Beads	6p each, 20 for £1.00
G11 6 Touch Unit with Cable Forms (Drawer Unit)	£12.00
KT3 Line Output Transformer	£5.00

SENDZ COMPONENTS

63 BISHOPSTEIGNTON,
SHOEBURYNES, ESSEX SS3 8AF.
SAME DAY SERVICE

All items subject to availability. No Accounts: No Credit Cards. Postal Order/
Cheque with order. Add 15% VAT, then £1 Postage. Add Postage for Overseas.

Callers: To shop at

212 LONDON ROAD, SOUTHEND. Tel. 0702-332992

Open 9-1/2 30-6. GVMT + school orders accepted on official headings. Add 10% handling charge.

VIDEO HEADS

AKAI VS9001 VS9000 VS9700 VS9800	£34.90
FERGUSON 3V00, 3V16, 3V22, 3V23, 3V24, 3V29, 3V30, 3V31, 3V35, 3V36	£34.90
HITACHI VT4000, VT4200, VT5000, VT5500, VT6500, VT8000, VT8400, VT8300, VT8500, VT8700, VT9300, VT9500, VT9700, VT111	£36.90
JVC HR3300, HR3320, HR3330, HR3660, HR4100, HR7200, HR7600, HR7650, HR7700	£34.90
SHARP VC381, VC383, VC385, VC386, VC2300, VC3300, VC6000, VC6300, VC7300, VC7700, VC8300, VC9300, VC9500, VC9700	£48.95
SANYO VTC5000, VTC5350, VTC5400, VTC5500, VTC9100, VTC9300, VTC9350, VTC9500	£45.95
SONY SL8000, SL8080, SL8500, SL8600, SL85, SL86, SL87	£38.50
FISHER VBS7000, VBS7320, VBS7500, VBS7600, VBS9000, VBS9900	£45.95
NATIONAL PAN. NV331, NV2000, NV3000, NV7000, NV7200, NV7800, NV8050, NV8400, NV8600, NV8610, NV8620	£38.50

PINCH ROLLERS

Akai NEC Sony Toshiba etc	£4.95	National Panasonic	£4.95
Akai JVC Mitsubishi Nordmende, Saba, Telefunken, Thom, etc	£4.95	Sanyo Fisher Tensa, etc	£4.95
Akai VS9700	£4.95	Sharp	£4.95

MOTORS, CLUTCH ASSEMBLY, IDLERS, ETC.

JVC & FERGUSON CAPSTAN MOTOR, PH45879	£29.50	SHARP CAPSTAN MOTOR, VC8300	£32.89
JVC & FERGUSON DRUM MOTOR, PU46414M	£29.50	SANYO REEL DRIVE PULLY	£8.50
JVC & FERGUSON CLUTCH ASS. 01X0003588	£5.95	SANYO REEL MOTOR 5000	£19.90
JVC & FERGUSON CLUTCH ASS. 01X0018729	£6.50	SHARP REEL IDLER VC381, 9300, ETC	£3.90
SONY REWIND KIT, ES05C7	£4.85	HITACHI REEL IDLER, VT8300	£4.75
SHARP CAPSTAN MOTOR, VC7300, VC7700, VC7750	£19.45	HITACHI PLAY IDLER, VT9300	£6.50

VIDEO BELT KITS

AKAI VS21G, VS56E, VS9300, VS9500, VS9700, VS9800	£2.95
FERGUSON 3292, 3V00, 3V01, 3V16, 3V22, 3V23, 3V24, 3V29, 3V30, 3V31, 3V32, 3V35, 3V36	£2.95
FISHER VBS7000, VBS7500, VBS7600, VBS9000, VBS9900	£2.95
HITACHI VT3000, VT5000, VT8000, VT8500, VT83	£2.95
JVC HR3300, HR3330, HR3360, HR3660, HR4100, HR7200, HR7650, HR7700	£2.95
NATIONAL PANASONIC NV300, NV333, NV2000, NV3000, NV7000, NV7200, NV8600, NV8610	£2.95
SANYO VTC5000, VTC5300, VTC5400, VTC5500, VTC9300	£2.95
SHARP VC381, VC383, VC385, VC386, VC6000, VC6500, VC6600, VC7300, VC7700, VC7750, VC8300, VC9300, VC9500, VC9700	£2.95
SONY SL8000, SL8080, SL8500, SL8600, SL85, SL87, SL7ME, SL7MEER	£2.95
TOSHIBA V5475, V7540, V8600	£2.95

RECTIFIER TRAYS	PYE	SEND LARGE SAE FOR A PRICE LIST	SEMICONDUCTORS (Cont.)	ICs (Cont.)
THORN 1750	713/715/4LED	£6.50	B0640	FB8000
950 MKII	713/715/5-4LED	£8.50	B0131	T8A610
1406 35T	691/693	£7.25	B0132	T8A820
1500 SST	725/731	£8.50	B0133	T8A20M
3000	RANK	£8.50	B0134	TD1170
3500	823	£8.50	B0135	TD2002
8000	120/120A	£7.50	B0136	TD2003
8500	UNIVERSAL	£5.95	B0137	TD2004
9000	DECCA	£4.95	B0138	UPC1181
1750	1750	£4.95	B0139	UPC1182
1830	1830	£4.95	B0140	UPC1156
2030	2030	£7.50	B0141	UPC1185H
2230	2230	£7.50	B0142	UPC1230H
2630	2630	£7.50	B0143	HA1366V
30	30	£5.75	B0144	HA1377
80	80	£7.50	B0145	HA1388
100	100	£7.50	B0146	HA1397
ITT	ITT	£5.50	B0147	STK463
CV1-9	CV1-9	£8.20	B0148	STR451
CV20-25/30	CV20-25/30	£8.20	B0149	LA4100
CV45	CV45	£8.65	B0150	LA4031P
PHILIPS	PHILIPS	£6.95	B0151	LA4460
68520-530	68520-530	£8.50	B0152	LA4461
68550	68550	£7.50	B0153	M5157L
69	69	£7.50	B0154	TA7279P
KT3	KT3	£7.50	B0155	TA7299P

UNIVERSAL ELECTRONIC DISTRIBUTORS

40 SILVER ARCADE, LEICESTER LE1 5FB. TEL: 0533 29438

MINIMUM ORDER £5.00 PLEASE. AND WELCOME. PLEASE ADD £1.00 P&P AND 15% VAT TO THE TOTAL. ALLOW MORE POSTAGE ON HEAVY ITEMS. PLEASE ALLOW UP TO 7 DAYS FOR DELIVERY.

CRICKLEWOOD ELECTRONICS LTD

FREE!
catalogue

It's no secret...

that there is a real difference at Cricklewood Electronics
That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (No SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED

40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161

Telex: 91 4977



MANTEL

No 1 for Quality TVs & Videos 100s of V.H.S. Videos in stock

Large Quantities of Late Model Thorn TVs. All with first class cabinets.

TELE-TEXT/ULTRASONIC/INFRARED/REMOTES

All at UNBEATABLE PRICES for QUANTITY & QUALITY

Also Philips G11/Pye G11/Basic/Remote/TELE-TEXT

Some examples of QUALITY working TVs

THORN 8800 *****£25
 THORN 8800 (remote) *****£30
 THORN 9000 *****£30
 THORN 9000 (remote) *****£35
 THORN 9600 *****£40
 THORN 9600 (full feature remote) *****£45

THORN 9600 TELETEXT ***** from £75
 (VARIOUS MODELS)
 THORN 9900 *****£50
 THORN 9900 f/f remote *****£60
 PHILIPS G11 *****£55

(prices quoted are based on quantity)

NO DEALER TOO LARGE OR SMALL. SINGLES SOLD

Brand New Remote Control Hand Sets Available for the majority of British & European TV sets.

1000s of UNTESTED Colour TVs

I.E. DECCA 30s, GEC 2110, GRUNDIG, TANBERGS, G8s 520s-550s, Thorn 3500/8000/8500, TT, PYE, ETC.

(Many of these untested TVs just switch on)

ALL AT LOW LOW PRICES

VAN LOADS DELIVERED DIRECT FROM SOURCE RING FOR QUOTE

New TV Trolley Stands

£4.95 Also Video Stands

POA

Colour TV panels & tubes available

All prices subject to V.A.T.

CALLERS WELCOME

Export Orders Welcome for those Countries using the P.A.L. System

**419 BARLOW MOOR ROAD,
 CHORLTON, MANCHESTER M21 2ER.**

TEL: 061-861 8501

TVS TRADE SERVICES BROMSGROVE

Large selection of quality clean TV & Video always in stock, including:

THORN 3V22 from **£45.00**
 ELECTRONIC VCR from **£75.00**
 VHS Top Quality Workers with Leads & Instruction Books **£80.00**

FEW ONLY DIRECT TV. LOADS

Available before Christmas.

To reserve yours

PHONE A.S.A.P.

DON'T DELAY!

We also specialise in working sets, fully serviced and ready to deliver to your customer's home. Spares back up service available to customers. You've seen the junk, so why not now come and pay us a visit - we think you will be pleasantly surprised by our prices and the quality of our equipment. Delivery service available.

For further details phone:

**COLIN BROOMFIELD,
 UNIT 7, STATION STREET,
 BROMSGROVE, WORCS.
 (0527) 37037/71186**



CREWE WHOLESALE TV

77 Coleridge Way, Crewe

Tel: 0270 582924

15 mins from Junction 17, M6 motorway

WORKING TVs FULLY ENGINEERED AND TESTED. TRY THEM BEFORE YOU BUY. NO REGUNNED TUBES.

Decca 80s & 100s	£25
Bush T20 & T22 etc	£30
ITT CVC 20 & 30 & 32 upwards	£25
G11s	£35
GEC Starline	£25
GEC 2110, 2111	£20
Rediffusion Mk 3	£25
Rediffusion Mk 1 & 1A	£12
Thorn from 8,800 to T/X from	£20
Text Sets Available	POA

LARGE SELECTION OF OFF THE PILE SETS FROM **£5**. DECCA, GEC, ITT, BUSH, REDIFFUSION, ETC. ALL UNTOUCHED, CHECK FOR COMPLETION BEFORE YOU BUY. UNTOUCHED VIDEO ELECTRONIC FROM **£90**. WORKING TOUCH TUNE VIDEO FROM **£135**. ALL WORKING PRICES QUOTED ARE FOR LOTS OF 5. ALL OFF THE PILE ARE FOR LOTS OF 10.

IMPORTANT TRADE ANNOUNCEMENT

SATELLITE TVRO SYSTEMS

Demonstration Model

Supersat have introduced a TVRO demonstration model especially for retailers who wish to display and familiarise themselves and their staff with Satellite TV systems. The Satellite TVRO system is probably the only new development in the world of television which seems capable of capturing the imagination. The sort of interest being developed is, in our opinion, bound to lead to the acceptance of Satellite TV as the new mass entertainment medium. Most people are aware that there is something called "Satellite TV", but have not, as yet, been enthralled by perfect TV pictures which have travelled some 45,000 miles through space from a variety of different countries.

Price Revolution

It will come as a very pleasant surprise to most would be purchasers that at £695 (inc. VAT) our cheapest system is well within their reach. To copy a much used catch

phrase - "The price is right". All that is needed to stimulate the market is an increase in public awareness and it is for this reason that we make our Demonstration Model offer.

Demonstration Offer

We at Supersat know that success for both of us depend initially on our ability to persuade you to demonstrate Satellite TV. We also know that another key factor is your initial investment cost. The Demonstration Model cost will be £399. It is expected that the major portion of this initial investment cost will be recouped by way of the profit on your very first sale. Further stock investment need not be necessary because Supersat offer a next day delivery. The offer is limited to one system per retail outlet (a qualification we will strictly control). The equipment is from a well known national supplier.

If you are a genuine retailer with retail premises you should phone immediately for further details.



A TELEPART ASSOCIATE COMPANY

**32 TEMPLE STREET
WOLVERHAMPTON
WV2 4LU
Telephone: (0902) 29022**

**CUT OUT THE
VOUCHER
& SHAVE 50P!**

This is your chance to save 50p off the cost of admission to the UK's number 1 Woodworking Show - the 6th Annual Practical Woodworking Exhibition at Wembley.

If you're interested in woodworking, this is your show - the one occasion every year when craftsmen, suppliers, dealers and enthusiasts come together from all over Europe.

The 1987 Exhibition will be bigger and better than ever. We're putting the Craft Market in a hall of its own - which leaves all the more space for the display of timbers, veneers, fittings, finishes, tools and machinery in the main exhibition. There'll be lectures and demonstrations as always, and Christie's will be there again to value antique furniture from photographs and your old woodworking tools.

The Exhibition is open from Thursday January 15 - Sunday January 18, 1987, and opening times are 10am - 7pm (6pm on Sunday). Admission prices are £1.50 for adults and £2.00 for senior citizens and children under 16.

Bring the 50p off voucher below to the exhibition and you will be entitled to 50p off normal admission price.

**The 6th Annual
PRACTICAL WOOD
WORKING
EXHIBITION**

50p OFF

This voucher entitles the bearer to a reduction on the purchase of one adult or child full price ticket. This cannot be used with any other offer.

WEMBLEY CONFERENCE CENTRE
JANUARY 15-18 1987

AUTUMN SPECIALS

HITACHI VHS VIDEOS SUPERB CONDITION LARGE QUANTITIES

10 GEC SOLID STATE	£150
10 BUSH T20	£250
10 ITT CVC35	£300
10 REDIFFUSION MARK 1 REVAMP	£120
10 THORN 8000 17"	£150

ALL + VAT

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154
THE NO. 1 WHOLESALE IN THE SOUTH

<p>OSCILLOSCOPES</p> <p>TEKTRONIX 2215 60MHz. Dual Trace Delay Sweep. With Manual.....£475</p> <p>TELEQUIPMENT D75. Dual Trace 50MHz. Delay Sweep.....£350</p> <p>COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual.....£200</p> <p>TELEQUIPMENT D61A Dual Trace 10MHz With Manual.....£175</p> <p>ADVANCE OS250TV. Dual Trace 10MHz With Manual.....£160</p> <p>PHILIPS PM3230. Dual Beam 10MHz Solid State £100</p> <p>TELEQUIPMENT D43. Dual Trace 15MHz. With Manual.....£100</p> <p>TELEQUIPMENT S54A. Single Trace 10MHz. Solid State. With Manual.....£110</p> <p>ADVANCE/GOULD DVMS</p> <p>Auto ranging; max reading 20,000. AC/DC volts - resistance..... Only £50 (P&P £5)</p> <p>MULTIMETERS</p> <p>AVO 9 Mk4 (Identical to AVO 8 Mk4 but scaled differently) Complete with Batteries & Leads.....£55</p> <p>AVO 8 Mk2 Complete with Batteries & Leads.....£45</p> <p>Above items in GOOD WORKING ORDER - appearance not A1 hence the price.</p> <p>AVO TEST SET No 1 (Military version of AVO 8) Complete with batteries, leads & Carrying Case £65</p> <p>AVO Model 7x. Complete with batteries, leads & carrying case.....£40</p> <p>AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads.....£18</p> <p>AVO 72 - Similar to above but no AC current range. With batteries & leads.....£10</p> <p>AVO TRANSISTOR TESTER TT169</p> <p>Handed. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12</p> <p>ISOLATING TRANSFORMER</p> <p>240V In - 240V Out 500VA.....£15 each P&P £5</p> <p>240V In - 240V Out 100VA.....£6 each P&P £2</p> <p>DISK DRIVE PSU. 240V 1W; 5V 1.6A & 12V 1.5A out.</p> <p>Size: W125mm, H75mm, D180mm. Cased. Un-used. Only £10.00 each (P&P £2)</p> <p>Qwerty keyboard (as in Lynx Micro). Push to make. Cased.....£5 each (P&P £2)</p> <p>Various 5 1/4" Floppy Disk Drives and Stepping Motors Available.</p> <p>USED EQUIPMENT - WITH 30 DAYS GUARANTEE. MANUALS SUPPLIED IF POSSIBLE. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.</p>	<p>SPECIAL OFFERS</p> <p>B+K Precision CRT Restorer/Analyser Model 467. Supplied with 2 Bases and Manual. (P&P £7) ONLY £125 each</p> <p>Labgear Colour Bar Generator KG1 8 Test Patterns. (P&P £4). ONLY £40 each</p> <p>LABGEAR COLOURMATCH PATTERN GENERATOR</p> <p>Type CM6038-DB Crosshatch/Grey Scale/Blank Raster. Mains or Battery..... ONLY £12 each (P&P £2)</p> <p>CROSSHATCH GENERATOR TVT5M Crosshatch/Dots/White. RF & Video Outputs. Tuner Control £10 (P&P £4)</p> <p>DEGAUSSING COILS.....£20 (P&P £4)</p> <p>ADVANCE AM SIGNAL GENERATOR SG62B. 150 KHz-220MHz.....£45</p> <p>ADVANCE AM SIGNAL GENERATOR Type 62. 150KHz-220MHz.....£30</p> <p>METRIX WOBBLULATOR Type 210. 5-220MHz.....£20</p> <p>LABGEAR COLOUR BAR GENERATOR CM6037 (P&P £4).....£60</p> <p>RACAL 32MHz UNIVERSAL COUNTER TIMER Type 835 with Manual.....£50</p> <p>MARCONI TF2604 (Later version of TF 1041 VTM) 20Hz-1500MHz; AC/DC/Ohms AC 300mV-300V FSD.....£60</p> <p>MARCONI VALVE VOLTMETER TF2600 10Hz-10MHz; 1mV-300V FSD.....£40</p> <p>PHILIPS COLOURBAR GENERATOR type 5501 (P&P £5).....£100</p> <p>PHILIPS COLOURBAR GENERATOR type 5508. Video out. Many Functions.....£125</p> <p>NEW EQUIPMENT</p> <p>HAMEG OSCILLOSCOPE 605. Dual Trace 80MHz. Delay Sweep. Component Tester.....£567</p> <p>HAMEG OSCILLOSCOPE 203.6. Dual Trace 20MHz. Component Tester & 2 Probes.....£298</p> <p>All Other Models Available.</p> <p>BLACK STAR FREQUENCY COUNTERS P&P £4</p> <p>Meteor 100 - 100MHz.....£99</p> <p>Meteor 600 - 600MHz.....£126</p> <p>Meteor 1000 - 1GHz.....£175</p> <p>BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 £110</p> <p>BLACK STAR ORION. PAL TV/VIDEO COLOUR PATTERN GENERATOR.....£199</p> <p>HUNG CHANG DM1 7030. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC 0.1%. Complete with batteries & leads. P&P £4.....£39.50</p> <p>OSCILLOSCOPES PROBES. Switched x1. x10. P&P £2.....£11</p>
<p>STEWART OF READING</p> <p>110 WYKEHAM ROAD, READING, BERKS RG6 1PL</p> <p>Telephone: 0734 68041</p> <p>Callers welcome 9 am-5.30 pm Mon.-Fri. (until 8 pm Thurs.)</p>	

HOCKLEY DISCOUNT

TELEVISIONS

SPECIAL TRADE ANNOUNCEMENT

LARGEST STOCKS OF EX-RENTAL 'THORN'

COLOUR TVs & V.H.S. VIDEOS

8800 R/C	3V00
9000 R/C	3V16
9200 R/C	3V22
9600 R/C	3V23
9600 TTX	3V29
TX9/TX10	3V35

Cabinet 9600 with Brand New Hand Sets
 Thorn 9000's at £16 Special Offer Price and
 also Thorn 8800 Special Offer Price £13.

ALSO UNLIMITED SELECTION OF

BUSH T20/24 DECCA 80/100
 G.E.C. SOLID STATE & STARLINE
 HITACHI ITT CVC30 & CVC45
 PHILIPS G8, G11 & KT3 R/C
 REDIFFUSION MK 1 & MK3
 REDIFFUSION MK 4 & TELETEXT

TV & VIDEO STANDS IN STOCK

Lorry Loads Delivered from Source

DON'T HESITATE TO CONTACT US

FOR FRIENDLY SERVICE

TRY US - YOU'LL LIKE US!

MIDLAND BRANCH
 Hockley
 Discount Televisions,
 94 Soho Hill, Hockley,
 Birmingham B19 1AE.
 021-551 2233 - Ask for Jazz

NORTH-EAST BRANCH
 Northern TV Distributors,
 Unit 2, Perth Court,
 11th Avenue, Team Valley,
 Gateshead, Tyne & Wear.
 091-487 5389 - Ask for Joe

Universal Semiconductor Devices Ltd.

17 GRANVILLE COURT, GRANVILLE ROAD,
 HORNSEY, LONDON N4 4EP, ENGLAND.
 TEL 01-348 9420/9425 * TLX. 25157 usdco g



WE OFFER ONE OF THE LARGEST RANGES OF SEMICONDUCTORS AT HIGHLY ECONOMICAL PRICES. THE FOLLOWING SEMICONDUCTOR TYPES ARE AVAILABLE FROM STOCK. IF WE DON'T STOCK WHAT YOU NEED THEN WE CAN GET IT FAST FROM OUR FACILITIES IN WEST GERMANY AND USA UPON REQUEST.

TRANSISTORS - BIPOLARS - GERMANIUM AND SILICON
 SMALL SIGNAL
 POWER
 DARLINGTONS - ALL SHAPES AND SIZES
 VHF/UHF DEVICES - ALL SHAPES AND SIZES

FETS - POWER MOSFETS
 UNIUNCTIONS

DIODES - GERMANIUM AND SILICON
 RECTIFIERS AND BRIDGES
 OPTO-ELECTRONIC DEVICES
 LEDS OF ALL SHAPES AND SIZES

THYRISTORS AND TRIACS - ALL

SHAPES
 SIZES
 RATINGS

INTEGRATED CIRCUITS:
 CONSUMER - DIGITAL/ANALOGUE
 MICROPROCESSORS AND PERIPHERALS
 IC SOCKETS

MAIL ORDER CUSTOMERS: PLEASE SEND FOR OUR COMPREHENSIVE PRICE LIST, ENCLOSING £1.00 IN STAMPS, CHEQUE OR POSTAL ORDER.

CATALOGUE SENT FREE OF CHARGE, WHEN REQUESTED ON OFFICIAL LETTERHEAD (WITHOUT REFUND), TO OEM'S, SCHOOLS, COLLEGES, UNIVERSITIES, GOVERNMENT INSTITUTIONS, COMPUTER FIRMS, ELECTRONIC REPAIR FIRMS AND DISTRIBUTORS.

SPECIAL DISCOUNTS AND PAYMENT TERMS ARE AVAILABLE TO ABOVE INSTITUTIONS.

PLEASE ENQUIRE FOR QUANTITY DISCOUNTS.

WE WELCOME TELEPHONE AND TELEX ENQUIRIES!



THE WORLD OF . . . "TELEPANELS"

8-10 Rhoda Street, London E2 7EF. Tel: 01-729 0506.



WORKING
PANELS
GALORE!

P+P 1 PANEL £1.50. 2 PANELS OR MORE £3.00

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	8.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731			10.00		18.00	10.00	7.00	8.00		4.50
BUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
PHILIPS G11	14.50 WITH COMBINED SOUND MODULE		12.00		19.00	19.00	5.00	11.50		
DECCA 80	12.00	POA	14.00		12.00	10.00		14.00		POA

POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!

D.I.Y. TV TUBE POLISHING

with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25* tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £57 inc P&P and VAT. Available from Luton only.

Also supplied worldwide for £57 including P&P.

*Depends on depth and area to be polished.

TV TUBES FREE DELIVERY*

5% DISCOUNT ON TUBES COLLECTED FROM LUTON

Quality, High Temperature Reprocessing

TUBE SIZE INCLUDING & UP TO	IN LINE & PIL I.e.	MININECK (22.5mm colour)	SONY TRINITRON	
20"	AXT37-001 470ESB22 470ERB22 A51-161X A51-421X A51-426X A51-570X A51-580X A51-580X A51-610X A51-701X	560AKB22 560BYB22 560DYB22 560DZB22 560EGB22 560FG22 560GAB22 A56-510X A56-540X A67-701X	370HGB22 370KRB22 370KSB22 370KXB22 420FS22 420FTB22 470NUB22 470NWB22 470RDB22 470RHB22 510ADF22 510YWB22 510YXB22 510ZUB22	330AB22 400EFB22 470BE22 470DLB22 470FWB22 520KB22 520NB22 520SB22 570EB22 570HB22 680DB22 680EB22
22"	£44	£50	£58	
26"	£46	—	£64	
26"	£48	—	£85	

Tube types not listed, please enquire.

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee. All tubes exchange glass required. Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. From £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 or 2 tubes £6. 3 or more tubes **FREE DELIVERY***

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

Open Mon-Fri 9am-6pm. Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

Phone between 2-5pm.

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.

Tel. 0494 778197

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901

114-134 Midland Rd,
Luton, Beds.




★ Do you use cathode ray tubes?

★ Can't find a replacement or shocked by the cost?

★ It may well be that a rebuilt tube will solve your problem.

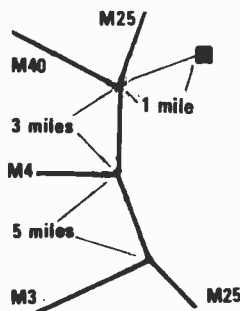Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



WE ARE LOCATED IN UXBRIDGE

At probably the most accessible part of S.E. England. The nearest junction of the M25 is only about 1 mile away and we are less than 10 minutes from the interchanges on the M25/M3, M25/M4, M25/M40.

Why not telephone Terry Smith on Uxbridge (0895) 55800, to discuss your requirements?

DISPLAY ELECTRONICS LTD.

UNIT 4, SWAN WHARF,
WATERLOO ROAD,
UXBRIDGE, MIDDLESEX.

SEMPLER SERVICE



AT LAST!!

AN EX-RENTAL WAREHOUSE OPEN IN

★ NORFOLK ★

DON'T GO WEST FOR YOUR EX-RENTALS

100's OF
TV's

ALSO

MECH AND ELECTRONIC
VIDEOS

59 HALL ROAD
CLENCH WARTON
KINGS LYNN

PHONE NOW!
(0553) 766766

CentreVision

TEL: 0222-44754

SLOPER ROAD, LECKWITH, CARDIFF CF1 8AB
OPPOSITE CITY FOOTBALL GROUND, 5 MINS FROM M4

FERGUSON VHS VIDEO £65

MANY ELECTRONIC VIDEOS IN STOCK

MANY TOP QUALITY REMOTE CONTROL WORKING TV's

PHONE FOR LATEST PRICES

PRICES SUBJECT TO VAT


OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30; SATURDAY 9.00 - 1.00

Kent Ledgerwood Wholesale Ltd.

**FOR RECENT MODEL
TELETEXT TV'S
AND ELECTRONIC
VCR'S**

**ALL
MAKES
AND
MODELS**

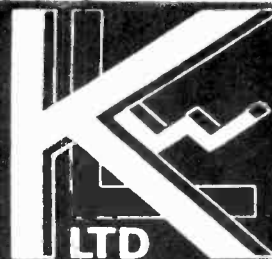

**THE
BIGGEST
AND
BEST
SELECTION
AT THE MOST
COMPETITIVE PRICES**

**SPECIAL
OFFER**

BETAMAX VCR'S
Most makes from £19
**SHARP 2300 H VHS, MAINS
PORTABLE VCR'S from £60**



OPEN 6 DAYS WEEKLY AND SUNDAY BY APPOINTMENT AT

**Working VCR's
or Teletext CTV's
Any Model
single or small
orders welcome**

**BRADFORD
TRITEL TV**
1043 Leeds
Road
Thornbury
Roundabout
BRADFORD

Tel: 0274 665670

**LEEDS
TRITEL
DISCOUNT
STORES**
Long Row
Horsforth
LEEDS

Tel: 0532 590252

**SCOTLAND
TRITEL TV**
Unit 4

Peacock Cross

Industrial Estate
Burnbank Road
HAMILTON

Tel: 0698 282141

**Now Open in
London at:-**

**UNIT E1,
WATERLOO
ROAD,
STAPLES
CORNER,
LONDON NW2**

Tel: 01 208 2063



IRISH T.V. DEALERS (PLEASE NOTICE)

LARGE SELECTION OF IN-LINE UHF/VHF DECCA, DORIC, FERGUSON, PHILIPS & BUSH, WORKING COLOUR SETS. CABINETS RESTORED TO A1 CONDITION. PRICES START FROM PILE @ £50 INC. VAT. B/W @ £25. ALSO IN STOCK RE-GUN TUBES & VIDEO HEADS.

(EXPORT SPECIALISTS)

T.V. TRADE SALES
E.D.I. HOUSE
KYLEMORE PK. WEST
DUBLIN 10. (Off Naas Road).
Tel: 01-264139/263517
BONA FIDE DEALERS ONLY SERVED

ALSO

T.V.T.S.
CLOVER PLACE
COLLEGE ST.
KILLARNEY.
Tel: 064-33655

APOLLO LANCASHIRE

NATIONWIDE MAIL ORDER 3-4 DAYS PHONE FOR QUOTE
LOCAL DELIVERY - 2 YR GUARANTEE - SONY TYPES - VDU & BW
56 & 66-540 GLASS BOUGHT (COLLECTED)

A47 342/343X - 470 BCB22/CTB22/BGB22/DHB22	£39
470-ESB22/EFB22/ERB22/FTB22	£53
A51-220X/192X	£39
A51-161X/162/163/168	£53
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£53
510-VLB22(E55) DTB22/001/RFB22/RCB22/SFB22	£53
A51-590 New	£55
A51-570X/580/001/210/241	£53
A56-120X/123/140/410	£39
560-DZB22(E56)/HBB22/AKB22/TB22/AWB22	£55
560-ETB22/DTB22/CSB22/DMB22/DNB22	£53
A56-611X/615X	£53
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X/510X - A66-500X/510X	£53
30AX - A56-540X - A66-540X	£56

PLEASE PHONE BEFORE CALLING
LOCAL DELIVERY FROM ACCRINGTON, LANCS.

Phone enquiries and letters to:

Apollo, The Potters Wheel,
Mullion Cove, Mullion, Nr. Helston, TR12 7ET.
0326 240781

N.G.T. COLOUR TUBES

First Independent Rebuilder with
B.S.I. CERTIFICATION

DELTA - IN-LINE - PIL - BONDED YOKE
including

AXT Series, DZB series 20AX - 30AX
A56 610/67 610 series, A51 570/580/590X
A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

N.G.T. ELECTRONICS LTD.,
120 SELHURST ROAD, LONDON SE25
Phone: 01-771 3535.

25 years experience in television tube rebuilding.

SETS & COMPONENTS

TV's - HITACHI, MITSUBISHI, Panasonic, Sony, Toshiba, JVC, Sharp. Fully refurbished. PEARSON TELEVISION, 0484-863489. Delivery arranged.

GENUINE GRUNDIG SPARES. Fast helpful service, sensible prices. TELEQUIPMENT, PHILIPS, OSCILLOSCOPES, TEST EQUIPMENT, MANUALS. Oehre Mill Technical. Stone 0785 814643.

CASH PAID Now for your surplus TV spares, Transistors, I.C.'s etc. Tel. MR. FORSHAW 0902 29022.

PHILIPS G11 AND BUSH T20 regular supplies. For prices phone 01-845 2036.

Trent Tubes

For Professionally Rebuilt Tubes

39A RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM
NC2 5FF TEL: (0602) 813329

TWO year guarantee extendable to FOUR years

ALL STD DELTAS ONE PRICE £33.00

A51-A56 - A66/500-510 20AX £44.00

560DZB, 510VLB, 560EGB, A51-161 - A51 570, 370LDB, 370NJB etc. etc. One price £48.00

A56-540 A66-540 30AX £49.00

Sony types from £55.00

1000's more types available. VDU, & MONITOR types a SPECIALITY (colour & mono).

1000's more types available. VDUs, MONOs, Industrials etc.

Suppliers to Broadcasting Authorities, Government depts & National Companies and Manufacturers

ALL PRICES EX WORKS + VAT & EXCHANGE

WE SPECIALISE IN JAPANESE TYPES

INSURED DELIVERY SERVICE AVAILABLE

QUANTITY DISCOUNTS

TECHNICAL ADVICE SERVICE AVAILABLE

Agents, wholesalers required high discount rates

WOODSDALE COMPONENTS

RANK BUSH MURPHY

TRANSFORMERS

Line Output

Z718 (T703A, T706A)

New (Complete) £15.00

T20, T22 (T705A)

£11.00

T26 (T705B)

£11.00

TDA2190 Plug-in Replacement module suitable for Bush T22/26 and any set using same device

£6.00

Switch Mode

T114A

£6.00

Genuine RBM Units.

Prompt Postal Service P&P Paid.
DISCOUNTS for QUANTITIES.

34 Field End Road, Eastcote,
Pinner, Middlesex. HA5-2QT.

Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

VIDEO SPARES

VHS video heads - 3HSS/4HSS (state model) £31.00

Video heads for Sony C5/C6/C7 £34.00

Sanyo reel motor £12.00

Sharp Idler wheel (state model) £2.90

Sharp reel motor (state model) £15.00

Please add 15% VAT and £1.00 p&p per order.
Send sae for full list.

A.Z. ELECTRICS

174 Kettering Road, Northampton NN1 4BE

Tel: (0604) 24380

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.78 per single column centimetre (minimum 2.5 cms). Classified advertisements 40p per word (minimum 12

PRICE BUSTERS IN BIRMINGHAM FOR

TESTED AND UNTESTED TV'S AND VIDEO'S

ALSO AVAILABLE DIRECT LORRY LOAD

RING - 021-772 2733

WILTSGROVE LIMITED

(Next Door to UNCLE'S DISCOUNT STORE)

128-130 Ladypool Road,
Sparkbrook, Birmingham B12 8JA.

CASH ONLY

"STOP PRESS"

NOW IN STOCK ELECTRONIC VIDEO'S AT UNBEATABLE PRICES

BOURNEMOUTH

BEST SOURCE IN THE SOUTH FOR CLEAN WORKING TV & VIDEOS

TVs Bush/Decca/GEC/ITT/Japs/Philips

Thorn REMOTE & TEXT

Videos 2000, Beta & VHS

PLEASE PHONE FOR LIST

Mon-Fri 9-1, 2-5

HILLIER'S, UNIT 2A,
11-15 FRANCIS AVENUE,
WALLISDOWN. TEL: 0202 581932

PHILIPS VIDEO SPARES

Model VR 2324. Brand new unused includes power supply tuner, timer clock, R.F. panels, cabinet, electronics only, no mechanism £35 inc VAT and postage.

EFJAY PRODUCTS
13 Placehouse Lane,
Old Coulsdon, Surrey
Phone: 01-684 1665

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS

£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd., Hayes End, Middlesex

T.V. SPARES, PANELS AND MANUALS
PHILIPS · GRUNDIG

TELEVIEW 01-994 5537

194, Acton Lane, London W.4.

SERVICE PAGES

words), box number 70p extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 204B (H.H.), IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

THE TRADING POST

CLEARANCE SALE OF EX-RENTAL COLOUR TELEVISION SETS AND VIDEO'S

Colour TV's working from £20.00 + VAT
Off the pile £12.00 + VAT (batches of 10)
T.V. Stands from £3.00

GOOD DISCOUNTS FOR DIRECT LOADS

Open 9am to 5pm Monday to Friday
10am to 4pm Saturday - Sunday by appointment

THE TRADING POST, UNIT 13, SAVILLE ROAD,
WESTWOOD, PETERBOROUGH
TEL. 0733 261500

WHY NOT
LET
TELEVISION
SELL YOUR
PRODUCT
RING NOW
ON
01-261 5942

FYLDE T.V. AND VIDEO DISTRIBUTORS

Unit 7, Arkwright Court.

Blackpool/Fylde Industrial Estate
Very End of M55 left at roundabout.

UNLIMITED SELECTION OF

THORN 8800	PHILIPS G11
8800 R/C	G11 R/C
9000	G11 TTX
9000 R/C	GEC S/S
9600 R/C	JVC 20"
9600 TTX	MONO's 20" + 24"

AND MANY MORE

TRADE WORKERS TO ORDER

PHONE BLACKPOOL

(0253) 64413

B.G. COMPONENTS T.V. & VIDEO SPARES

We supply spares for most makes including Sony and Fidelity all at competitive prices.

We also stock a comprehensive range of rebuilt C.R.T.'s including Hitachi and Sony.

Open Monday-Saturday.

Hill Street, Oldham OL4 2AG.
061-624 1753.



AUDIOCASTLE LTD.

Importers and Exporters of Electrical and Electronic Components

MAIL ORDER

Components * Components * Components
Transistors, Linear I.C.'s, Valves, Rectifiers, Diodes, Thyristors, and many more components.

Export and Trade Enquiries Welcome

TEL: 01-888 2930 or TELEX: 268381
28 days delivery

I.T.V.C.

BEST QUALITY EX-RENTAL AND
GRADED TVs & VIDEOS

OFFERING A FRIENDLY & FIRST CLASS
SERVICE TO THE TRADE

GET ON THE WAY TO SUCCESS

BUY AT COMPETITIVE PRICES
TO INCREASE YOUR PROFITS

VHS VIDEOS

(Mech. Electronic)
FERGUSON, HITACHI,
JVC, NAT. PAN., etc.

BETA

SANYO, SONY,
TOSHIBA, etc.

TELEVISION

PHILIPS 550, G11, KT3
BUSH T20, T22, T24, T26
THORN 8.8K, 9K, 9.6K, TX
HITACHI, NAT. PAN.,
I.T.T., PYE, etc.

VAN LOADS DELIVERED DIRECT FROM SOURCE

PHONE STEVE
0602 864627

UNIT 3, MEADOW TRADING ESTATE,
MEADOW LANE,
OPP. CATTLE MARKET,
NOTTINGHAM NG2 3HQ

WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for THORN, PHILIPS,
PYE, RANK, GEC, SHARP, SONY,
DECCA + ITT.

FIDELITY SPARES MAIN DISTRIBUTOR.

Did you know we also stock

FUSES	I.Cs
TUBES	TOOLS
AERIALS	VIDEO LEADS
AEROSOLS	AUDIO LEADS
RESISTORS	SEMICONDUCTORS
CAPACITORS	SERVICE MANUALS
VALVES	TEST EQUIPMENT
HANDSETS	TV/VIDEO TROLLEYS
AND MUCH MORE	

Counter open Monday-Friday 9am-4.45pm

TRADE ONLY

EMPRESS STREET WORKS,
EMPRESS STREET,
MANCHESTER M16 9EN.

Tel: 061-872 5438; 061-848 0060.

DEALERS ONLY

GENUINE REGULAR LARGE QUANTITIES

Philips G8 - 520 £15 26"
Philips G8 - 550 £25 20 & 22" 10
Philips G11 - Guarantees Only

WORKING

520 - 30 550 - 45
SPARES PANELS AVAILABLE

Tel. 514047 or call:
Cullum TV & Video

Unit 5, Worle Ind Estate, Queensway,
Worle, Weston Super Mare, Avon
(Junct 21 M5 200yds)

**BESCO LTD T/A
NORTH WEST ELECTRONICS
NEW STOCKS ARRIVING DAILY**

**NEW YEAR CLEARANCE
WORKING TVS AND VIDEOS
ON SHOW.**

**H.P. REPOS AND EX. RENTALS
COLOUR TV'S AND VIDEOS**

Refurbished TV's

BUSH T20/T26 £45
G11 £50
PYE KT3 £65

Others done to order.

**DISCOUNT
FOR
QUANTITY**

EX-EQUIPMENT PANELS
NO EXCHANGE REQUIRED

	IF	De-	Line	Power	Frame
		coder	scan		
T20/22 X	14	18	17	14	
T26 X	16	20	17	X	

ALL PRICES INCLUSIVE OF
POSTAGE BUT PLUS VAT
CHEQUE WITH ORDER PLEASE

**Annual Clearance
Rock Bottom Prices**

PYE G11 EXC		PYE KT3	£50
CAB.	£40	GEC 2213	£30
BUSH T20/26 CH	£35	THORN 3000	£7
HITACHI 191	£20	GRUNDIG G415/ 4206	
FERGUSON TX	£65		
		Best Stock in Country over 2000 in stock (90% of our TV's Switch on)	
GEC 2010	£20	Special Price Quoted	
PYE 222	£20	For Bulk Purchases From Source.	
PHILIPS 550	£15		
BUSH 718	£20		
BUSH 2 CHIP	£8		
GRUNDIG 5010	£10		

Video

SHARPS 7300,
8300, 9300
HITACHI,
VT11,
FERGUSON
3V29

SANYO,
SONY,
BETA


**LAUREL STREET, LEEDS ROAD,
BRADFORD, W. YORKSHIRE BD3 9TP.**

5 MINS FROM MOTORWAY

**100's PX
HOOVER JUNIOR
VACS**

All models in stock

**Tel (0274)
660995**

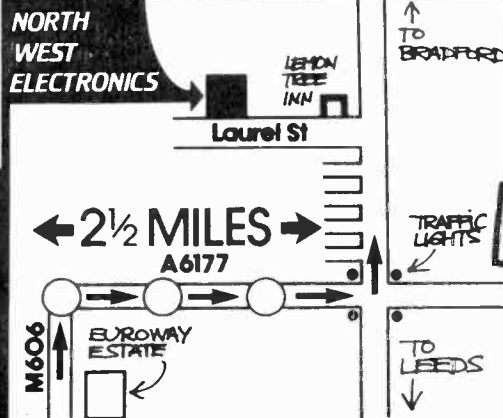

**P.X. WASHERS
COOKERS
ETC**

CASH ONLY

**OPEN 6 DAYS
SAT 9-5.30**

WE ARE CLOSED DEC 25th
& 26th, JAN 1st

AUDIO VISUAL SERVICES

special announcement

DO YOU REQUIRE FULLY REFURBISHED VHS VIDEO?

If so, read on . . .

READY FOR RESALE – VHS RECORDERS FULLY SERVICED
(ie new belts, clutches, heads)

ALL MACHINES SUPPLIED TO A VERY HIGH STANDARD COMPLETE WITH INSTRUCTIONS AND LEADS AND REMOTES. EVERYTHING YOU NEED INCLUDING OUR OWN FULL GUARANTEE (delivery to any UK destination)

MECHANICALS

ELECTRONICS

Makes include

Thorn · Hitachi · Sharp · Panasonic · Philips · Akai · Mitsubishi

Please note we do actually keep the above stock, we do not just advertise it.

FOR A NO FUSS SERVICE, CONTACT:

DAVE on HIGH WYCOMBE (0494) 26852

TUBES

NEW OR REGUNS

ONE YEAR GUARANTEE

14" 370 – KRB – LHB – HGB – HFB – HUB – BRB – EGB – EFB – MEB – GUB – AXT 37 – 001 – AXM 37 – 001 – 37 – 565 – 570 – 552 – 554 – 590 – A34 EAC 00X.

Broken Tube We Can Help.

16" 420 EDB – EFB – CZB, 42 – 001, 42 – 556.

20" 51 – 161, 51 – 500 – 554 – 570 – 575 – 580 – 590 – 51 – 001 AXT – 510 JKB – VB – UFB – RJB – UDB – HWB – 510 ABUB from £45.

22" 56 – 500, 56 – 540 – 610 – 611 – 615 – 700 – 712 – 560 EGB – DAB – DMB – BYB – EGB – TB – GAB – AXB – ETB – HB – DYB – ATB – BMB – HW 56 – 001 AXT.

26" 66 – 500 – 510 – 540 – 611 – 615 E55.

HITACHI 510 HWB – VLB – VSB – 560 DZB – HWB – 490 DKB22 FROM £34.

SONY £65 Cash & Carry only.

DELTA £29.00 Reguns.

£14.50 Slightly used. 6 month guarantee.
A56-120 A56-140 A51-110 A49-191 A47-342 or 343
A44-270-1 A66-120 A66-140 (410) A67-120

All prices are inclusive

U-VIEW

29, Warmsworth Road, Doncaster,
Yorkshire DN4 0RP. Tel: 0302 855017.

Callers ring first, open every day including Sunday
1/2 a mile from A1

N.F.P.C.

PERSONALISED PROTECTIVE COVERS
FOR TELEVISIONS & VIDEO RECORDERS
PROMOTE and PROTECT!

All covers made from sturdy quilted anorak-type material & personalised with your trading name.

PERSONALISED T.V. TRANSIT COVERS

(tea cosy style)

* No more scratched screens!

Price (including P&P)

Standard size £7.50 each Extra Large (for the 'monsters')

(Pack of 5 – £35) £8 each (Pack of 5 – £37.50)

(Pack of 10 – £65) (Pack of 10 – £70)

PERSONALISED VCR PROTECTIVE COVERS

* Give all-round protection against damage/scratching during transit

* Fasten with Velcro fasteners – no dangling mains flexes

* Fit all modern VCRs – excluding portables

* Allow discreet removal to and fro

Price (including P & P)

£6.50 each

Pack of 5 – £30

Pack of 10 – £55

SPECIAL DISCOUNT PACKAGE

2 x Standard TV Covers

2 x VCR Protective Covers

1 x Extra Large TV Cover

£30

WHY NOT JOIN OUR MANY SATISFIED CUSTOMERS?

DON'T DELAY – ORDER TODAY!

You'll wonder what you did without them!

Just print out your trading name and enclose with your order and cheque/P.O. to:

N.F.P.C., 3 Fenham Hall Drive, Newcastle upon Tyne NE4 9UT

Tel: 091-272 4646

Please allow 21 days for delivery

PUSH-BUTTON UNITS

New & Exchange Mainly Preh for
R.C.M./Doric/Murphy Mk. 3 & 4,
Ferguson, Decca, etc.

Send faulty units
with cheque for £12.50:

B.J. ELECTRONICS

DORIC HOUSE

ROUGHTON, WOODHALL SPA,

LINCOLN LN10 6YJ

PHONE (06582) 6621

TURN YOUR SURPLUS

ICS transistors etc. into cash, immediate settlement. We also welcome the opportunity to quote for complete factory clearance.

Contact:

COLES-HARDING & CO

103 South Brink, Wisbech, Cambs.

Tel. 0945 584188

* ESTABLISHED OVER 10 YEARS *

STARLITE ELECTRONICS

WILLOWS FARM,
A13 RAINHAM, ESSEX.

Rainham 23225 also
Hornchurch 50238.

EX RENTAL TVs
UNTESTED FROM £15.00
WORKING TVs £20.00
RE-GUNNING TUBES

2 year guarantee
Most types available
including Sony



EXPORT
ORDERS WELCOME

COLOUR TV's

FROM £12 EACH

PHILIPS G8, G11, GRUNDIG

ITT, BUSH, FERGUSON, GEC,

JAPS. PLUS MANY OTHER MAKES

01-965 1230 – 01-965 3997

SMITHS ELECTRONICS

43 PARK PARADE

HARLESDEN, LONDON NW10

EUROLEC U.K.

VCR CASSETTES

EXPORT ORDERS WELCOMED

BASF LVC 180 £8.00, BASF VCC 240 cassettes NEW £6.00,
LVC 150 £6.50, LVC 120 £5.00, PHILIPS LVC 90 £4.00, LVC 60
£3.00 (Some have outer wrappings removed but are all new).

Above prices include V.A.T. & P&P. NTSC-PAL-NTSC transfers, VHS,
BETA. +UMATIC £15 first hour, thereafter £10 per hour (Tapes included
in price). Optical transfer 8mm standard & super 8 transfer to VHS 50p per
minute, tape & postage extra. We specialise in the sale & purchase of
NTSC equipment. We also buy and sell Sony edit equipment & recorder/
players.

SPECIAL CHRISTMAS OFFER:

CROWN STEREO WALKMAN WITH HEADSET £12

Mail Order address:

35 Sandy Lane, South Wallington, Surrey.
Telephone 01-669 2611 Fax 01-773 1934

SURPLUS/REDUNDANT ELECTRONIC COMPONENTS WANTED

I/Cs - Tuners - Transistors - Valves - Diodes etc. any quantity considered - immediate payment.

ADM ELECTRONIC SUPPLIES
Tel: 0827 873311

COURSES

TV & Radio Aerial Rigging? Intensive "Foundation" Training Courses for the Technician Engineer

Start off on the right course... be fully informed! One week intensive instructional courses, run by an ex-broadcasting engineer. Residential, marvellous accommodation with excellent food. Theoretical and practical "Hands on" instruction. Training covers all aspects of television and radio reception. Become an aerial erector who can provide the best, because he's learnt the best way!

Courses held throughout the year, amidst the beautiful Highland scenery. Non-participating partners welcome at minimum extra cost. Transport from Inverness provided if necessary.

Further details by SAE to:
R.B. Mannion (Assoc. Member of Confederation of Aerial Industries),
Badcaul House, Badcaul,
Dundonnell, By Garve,
Ross-Shire IV23 2QY.
Tel: 085-483-213.

METERS

AVON METERS

We buy and sell and repair TV coinmeter. Reasonable prices, one year guarantee.

327 Church Road,
St George, Bristol.
0454 776413

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

SERVICE SHEETS

TECHNICAL INFO SERVICES (T) - 76 Church St., Larkhall, Lanarkshire ML9 1HE.

World's Sole Publishers of Comprehensive TV/Video Repair Manuals & Largest Known Stockists of Service Manuals and Service Sheets for all kinds of equipment both British and Foreign from 1935 to latest issues.

MAIN STOCKIST OF ALL HEINEMANN-NEWMES TECHNICAL BOOKS
DELIVERY BY RETURN FULL LIST ON REQUEST

Big Catalogues of thousands of Service Sheets & Manuals + Chassis Guide + £4 Vouchers - saves time and expense £3.

Any published single service sheet for £2.50 + Isae except ctv/mus-c/combis from £3.50 + Isae. A selection from our stocks of thousands of Service Manuals ready for despatch by return post. Any Sony: Hitachi ctv from £9.50. Thom 3000/3500 £9.50. Thom 8000/8004/8500/8600 £9.50. Philips G8 complete £9.50. Decca 30/31 £8.50. Ferguson/JVC 1st video £19.50 or 3V00 types basic manual £19.50. Any Finlandia: Tyne CTV £9.50 each. Rank A823 complete £9.50.

COMPREHENSIVE PRACTICAL TV REPAIR MANUAL £9.50 PRACTICAL RADIO SERVICING & REPAIR COURSE £9.50
THE 11 TUNBRIDGE TV REPAIR MANUALS ONLY £88 THE 5 McCOURT TV REPAIR MANUALS ONLY £55
ANY SET OF 5 INDIVIDUAL TV VIDEO REPAIR MANUALS FOR £12.50 OR ALL 3 SETS (15 MANUALS) FOR £36.

UNIQUE COLLECTIONS OF CIRCUITS, LAYOUTS, ETC. . . . FANTASTIC VALUE

British ctv from hybrids to modern (3 binders) £58 Videos, all types (3 binders) £58 . . . any 1 for £20
Mono TV (2) £38 Foreign ctv (2) £38 Domestic Eqpt (2) £38 Portable British ctv (1) £20 plus VAT.

COMPLETE REPAIR SYSTEMS . . . huge savings from published prices

British ctv 4 binders of Circuits plus 6 Repair Manuals plus ref books, etc. for only £125
Foreign ctv 2 binders of Circuits plus 4 Repair Manuals, etc. for only £65
Videos 3 binders plus 15 individual Repair Manuals cover all the commonest models for only £85
Complete Integrated T.V. Repair System only £250 or in 12 sections at £25 per section.
Contents: 8 binders of circuits/16 Repair Manuals/dozens of other manuals . . . Any new publications from us within 1 year of ordering 1st section will be added at no extra charge. No VAT on Systems

NEW - PRACTICAL TRANSISTOR - **NEW** - VIDEO REPAIR SYSTEM 3 £29 - **NEW**
From beginners/students elementary theory to more advanced. Huge section British/Foreign equivalents/alternatives/other data. £5.95 Post Free. Binder of Circuits alone £20 5 Repair Manuals £12.50
3V31/32 Sharp 2300 to 9700 Philips Laser Disc Pan 7000/7200/7800.

Repair data/Circuits/Service data almost any individual mono tv £12.50 basic ctv £12.50 video £10.50

LSAE BRINGS ANY REQUESTED QUOTATION - FULLER DETAILS - FREE MAGAZINE - PRICE LISTS ETC.
PHONE 0698 884585 Mon-Fri before 5pm or 0698 883334 any other time - FOR FAST QUOTES

SERVICE DATA-UK VCR & CTV

Circuit diagrams with layouts ONLY
OR complete service manuals

(SAE brings list)

DATA-GO, 112 Ameysford Road,
Ferndown, Dorset BH22 9QE

SERVICE SHEETS ON MONO TV's, radio etc at £2 each plus S.A.E. We also stock manuals on video recorders and colour TVs. Please send for quote: BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorks HG1 5JG.

SITUATIONS VACANT



ENGINEERS



Looking for a brighter future?
Join the fast moving and lucrative
computer servicing industry.

Vacancies are now available on our MICROPROCESSOR SYSTEMS TECHNICIANS COURSE

A 16 week full time course designed for TV Engineers wishing
to retrain in:

MICROPROCESSOR TECHNOLOGY

The course concentrates on realistic hands on practical work.

Start date:

JANUARY 12th 1987

Apply with full c.v. to:

MILTON KEYNES SKILLCENTRE

Chesney Wold, Bleak Hall, Milton Keynes

Or ring Bryan Hall on (0908) 670001

for further details.

NO TUITION FEES. A training allowance and lodging/travel allowance will be paid.

(M.S.C. - J.T.S. funded course)

'BOBS'

TELEVISION
WAREHOUSE

A NEW CONCEPT IN EX-RENTAL T.V. & VIDEO

WORKING TV & VIDEO

ENGINEERED TO THE HIGHEST
SPECIFICATION READY FOR
YOUR SHOWROOM

NON WORKING

GUARANTEED COMPLETE AND
UNCANNIBALISED GOOD
CABINETS AT LOW LOW PRICES
ELECTRONIC, REMOTE, FRONT
LOADER VIDEOS

**NAT PAN, JVC, HITACHI,
TOSHIBA, SANYO, SONY,
ETC, ETC.**

K30, KT3, G11, TEXT, REMOTE
AND BASICS


**ITT, GEC, BUSH, JAPS.,
DECCA, ETC.**

PHONE BOB BEAN ON:

0268 728966

AND DISCUSS YOUR REQUIREMENTS

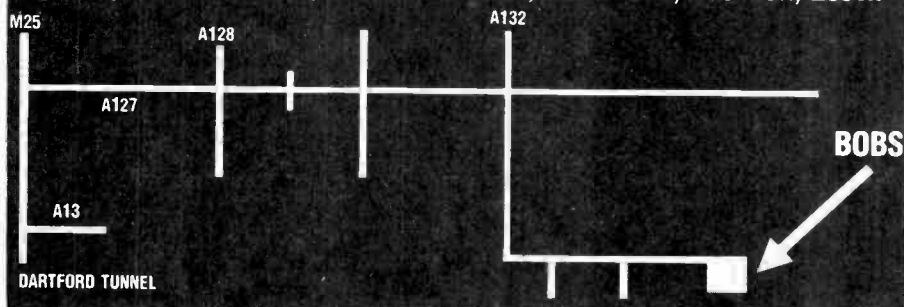BOBS T.V. WAREHOUSE, 1 Swinbourne Ct, Burnt Mills, Basildon, Essex



AERIALS

TV AERIAL BOOSTERS

B45H/G UHF AMPLIFIER 20db gain, next to the set fitting, battery PP3 or 8V to 14V working. **SPECIAL PRICE £7.70.**

B45N/G VIDEO as a transmitter (export), or feeding into a aerial system for up to 6 TV's. On channel 36 (variable) **Price £10.50.**

P&P £1 NO VAT. ACCESS/VISA CARDS WELCOME

ELECTRONIC MAILORDER,
62 Bridge Street, Ramsbottom,
Lancashire, BL0 9AG.
Tel: (070 682) 3036. (24 hr).

MULTI-OUTLET/MULTI-CHANNEL Installations. Large or small distribution systems. Equipment and/or consultancy by post or on site. Catalogue (full of trade know-how and trade equipment) £1 (refundable). **WRIGHTS AERIALS,** 43 Greaves Sike Lane, Micklebrng, Rotherham. (0709) 813419.

BUSINESS FOR SALE

I.O.W. RETAIL BROWN GOODS DOUBLE-FRONTED SHOP PRIME POSITION

With excellent sales hire and rental, video library premises include 2 bedroomed gas c/h flat - freehold £85,000 + S.A.V.

Reply to Box No. 229

WANTED

WANTED. WORKING AYR TELETXT ADAPTOR. Preferably with service manual. Tel 0969 22598.

SERVICE MANUALS 1974 or later. VCR. CTV, MTV. Camera, Audio, et. anything considered. cash paid (no photo copies). 0202 892279.

CASH PAID now for your surplus TV spares, transistors, I.C.'s etc. Tel. MR. FORSHAW, 0902 29022.

GOLD PLATED SCRAP WANTED. Scrap edge connectors, circuit boards, anything considered. Contact P & F TURNER & SONS. Tel. Oxford (0865) 510293.

WANTED Video's, portables, colour TV etc. Any quantity. Immediate collection. Cash paid. Tel. Stoke on Trent 416401.

WANTED. SONY RMT-211 Remote control for TT-F1 timer/tuner. Please phone Swindon 303357.

WANTED
Ex RENTAL COLOUR
TVs IN BULK
QUICK COLLECTION
Phone 0742 312832
(Sheffield)
IN STRICTEST CONFIDENCE

FOR SALE

JAPANESE TELEVISIONS FOR SALE

PRE USED 14"/22"

For details:

Phone: 0484 863489

TURN YOUR COMPUTER into a storage multimeter with my interface. Works with any 8 bit computer with hand-shake lines -Vic. C64. BBC. Program for Vic, C64 (State which) easily convertible. Circuit, program instructions £10. Program for Vic, C64 Xhatch, vert, hor, blank, colour bars. £3.50 send remittance to DELTRONICS. 10 Snell Hatch, West Green, Crawley. Sussex RH11 7JB (0923) 542823.

G8/550 EX-RENTAL GOOD TUBES. - Spare set panels with each TV £20. 5 sets £80. Buyer collects, cash only. RENTACET, 0525 403466 Bedfordshire.

2 SETS OF FULLY RECONDITIONED tube re-gunning plants for sale. Training provided. From only £3,995. Tel. 0582-410787.

TV/VCR SPARES & EQUIPMENT FOR SALE. Meteor 600 mhz frequency counter £80, Manor Supplies MK5 generator £60, Gould OS4020 digital storage scope £900. All plus VAT. For other details tel 01-841 1769. 6-7 pm.

PRECISION 3 METRE DISH ANTENNA with stand and custom built 4 wheel trailer. £1,850. Tel 061-437 2631.

LEADER LCT-910A CRT Tester/Rejuvenator condition as new £145. Box No 228.

VHS VIDEO'S 3V00/3V22

£40 each + VAT

Minimum quantity 10

Tel: (0602) 397555

ACTIVE DEFLECTORS

We produce a 4 channel power amplifier (10dB power gain) as an add-on to existing 1 volt amplifiers.

£150.00

DISTRIBUTORS WANTED
SKYEWAVE ENGINEERING LTD.
Watnish, Isle Of Skye
Tel. 0478 2843

DEVONICS

Quality Tube Rebuilders

2 YEAR WARRANTY

Inline Tubes	
Up to 20"	£43
22"	£45
26"	£46
Sony Tubes	+ £15
Bonded Coil	+ £5
30 AX (-540X)	+ £7

Delta tubes from £30
Mono Portables from £15
All plus carriage and VAT

2A BARTON HILL ROAD,
TORQUAY TQ2 8JH.
0803 33035



Sabaco

For a great deal!

TRY US YOU'LL LIKE US TOP QUALITY TV'S & VIDEO'S AT ROCK BOTTOM PRICES

VAN LOAD DIRECT FROM SOURCES ALL SETS & VIDEO'S OFF THE PILE (Mostly switch-ons)

Largest selection of 4000/8800/9000/9200/ 9600/Ferg TX9/TX10 Stereo Teletext Colour Portables

Mainly teletext and remote with handset.

Also Pye KT30/G11/T20/T26/Hitachi/ Philips 550/Grundig & many more.

BRAND NEW SETS AT LOW PRICES

VHS VIDEO'S

Good Working Order from 3V22, 3V23, 3V29 Portable Video's etc.

Also a selection of brand new video & £180 video tapes

OPENING HOURS:

MONDAY TO SATURDAY 9am to 5.30pm

CASH ONLY All goods subject to VAT & availability
PHONE NOW FOR UP TO DATE COMPUTERISED PRICES
AND DELIVERY DAYS, BE HERE WHEN LORRY ARRIVES
FOR FIRST CHOICE — PHONE US NOW ON:

(0602) 397555



Head Office:
Sabaco
Saba House,
46A Derby Road,
Sandiacre, Nottingham
(0602) 397555

Sabaco
75 Robertson Street,
Glasgow
(041) 221-2146

SWITCH ON TO PROFITS

WITH

G11 PYE AND PHILIPS 22"	£20	
ITT REMOTES	£35	OFF
G11 TEXT PYE/PHILIPS	£55	THE
KT3	£50	PILE
VIDEOS	£10	PRICES

ALSO ON STOCK

DECCA 80-100-88-0911 TEXT. PYE 713, 725, 222. ITT CVC 20-23-25-30-32. PANASONIC 2E1, 85GA, 2205 REMOTE. TELEFUNKEN 8256 REMOTE. SONY 1810, 2022. FERGUSON TX, 3740, 3757, 9000, 9200, 3722 REMOTE. GEC 2242, 2642, 2069 TEXT. TOSHIBA 2095 REMOTE. GRUNDIG 3020-3022 TEXT, 4400 REMOTE, 6610. MITSUBISHI CT200, 2606, REMOTE, 2206. HITACHI 192, 260 REMOTE, 180, 2051, 210. AND MANY OTHER TYPES.

MOST OF OUR SETS OFF THE PILE SWITCH ON

100s AND 100s OF FULLY WORKING SETS AVAILABLE, ALL SEEN WORKING. CALL & CHECK THEM OUT. STANDARD TYPES 17" TO 26", REMOTES, TEXT. CABINETS ARE EXCELLENT AND READY FOR IMMEDIATE SALE OR RENT.

VHS VIDEO ELECTRONIC AND ALL WORKING, GOOD CASES. STANDARD TO FULL I/R REMOTE CONTROL. BY PANASONIC 2000, 2010, 366, 7200. MITSUBISHI, SHARP, GEC 4001-4108. HITACHI VT9, 8300, 8700. JVC 2200 PORTABLE, 7200, 7300, 7700. AMSTRAD, DECCA DK7200 AND MANY OTHERS.

2000 SYSTEM – SWITCH ONs **£20**
2020-2021-2022. GRUNDIG 2x4 – 2x4 SUPER

CLEARANCE COLOURS CHEAP 10 SETS £80 AND SOMETIMES EVEN LESS. SLOT METERS AVAILABLE – ASK. ALL PRICES BASED ON QUANTITY. ALL PLUS VAT.

GENERAL FACTORS
UNION STREET
DONCASTER, SOUTH YORKS.
0302-349583

CASH NO CHEQUES
ONLY 2½ MILES FROM
(AIM) FOR M18-M1
10am to 5pm
MON TO FRIDAY

If an advertisement is wrong we're here to put it right.

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

The Advertising Standards Authority ✓

ASA Ltd. Dept 3
Brook House, Torrington Place,
London WC1E 7HN

MAIL ORDER ADVERTISING

British Code of Advertising Practice
Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

INDEX TO ADVERTISERS

ADM Electronics	218
Aerial Techniques	181
Alberice Meters Ltd.	197
Alcon Instruments Ltd.	200
Alston - Barry Satellite Services	197
Apollo	213
ASJAA International Ltd.	204
Audio Castle	215
Avon Meters	218
A-Z Electronics	214
Besco Ltd.	216
B.G. Components	215
B.J. Electronics	217
B.K. Electronics	150
Bob's Television Warehouse	219
Bollen Ltd.	206
Bull, J & N Electrical	155
Carter, John (Electrical) Ltd.	205
Cetel	206
Central TV & Video Wholesalers Ltd.	201
Centrevision	212
Chromavac Ltd.	154
Coles Harding & Co.	217
CPC	153
Crewe Wholesale TV	209
Cricklewood Electronics Ltd.	208
Crofton Electronics	154, 197
Cullum TV & Video	215
Devonics	220
Display Electronics Ltd.	212
East Cornwall Components	156
East Croydon Discount Electronics	205
Economic Devices	184, 185
Electric City	153
Electronic Mail Order	219
Electrovisa Ltd.	205
Eurolec (UK) Ltd.	217
Express T.V. Supplies	203
Flintdown Channel 4	221
Ford, Frank	206
Fylde T.V. & Video Distributors	215
Garton, D & G	219
General Factors	222
G.G.L. Components	198
Grandata Ltd.	207
Harrison Electronics	164
Hilliers	214
Hockley Discount Televisions	211
Holmes, D.J.	217
Hussain Central T.V. Ltd.	151
ICS	153
I.T.V.C.	215
Junction 11 T.V. Trade Disposals Ltd.	204
Kent Ledgerwood Wholesale Ltd.	213
London Electronics College	164
LRC (Spares) Ltd.	199
Mannion, R.B.	218
Manor Supplies	Cover II
Mantel	209
Micro-X Ltd.	195
Milton Keynes Skill Centre	207, 218
Monolith Electronics Co. Ltd., The	203
Montana Mail Order	200
N.G.T. Electronics Ltd.	213
North East Satellite Systems	191
Papworth Transformers	223
Powell, T.	199
Pro-Vision	197
P.V. Tubes	146, 147, 148, 149
Quick Save T.V. Spares	152
Repossessed T.V. Centres Ltd.	223
Riscomp Ltd.	203
Sabaco	219
Sample Service	212
Senz Components	208, 224, Cover III, Cover IV
Skywave Engineering	220
Smiths Electronics	217
Sparkworld Ltd.	207
Starlite Electronics	217
Stewart of Reading	211
Supersat	210
Supertel	196
Taylor Bros. (Oldham) Ltd.	202
Technical Information Service	218
Telepanels	212
Tele-part	154, 164, 223
Teletraders	210
Televideo Services	164, 202
Television	214
Thom EM	163
Tidman Mail Order Ltd.	173
Trading Post, The	215
Trent Tubes	214
TVS Trade Services	209
T.V. Trade Sales	213
Universal Electronic Distributors	208
Universal Semiconductor Devices Ltd.	211
U-View Tubes	217
Vincent, J., Technical Books	221
Wellview	212
Willow Vale Electronics Ltd.	221
Wiltsgrove Ltd.	214
Wing Electronics	214
Woodsdale Components	214

REPOSSESSED T.V. CENTRES LTD.

061-273-2854


YOUR CHOICE

MINT WORKING SETS. These arrive at our premises in A1 working order, cabinets are superb. **£45 to £70**

GUARANTEED UNTESTED SETS. These are just as they arrive, in good condition with plenty of plug in workers. We do not sort them as we have our separate source of working sets. **£10 to £35**

VHS Videos in stock.

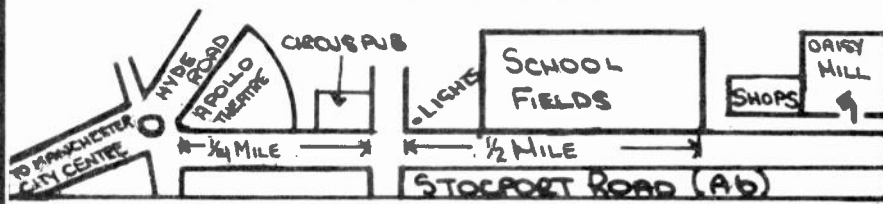*Well stored in large centrally heated premises. Ample viewing space and stored only four high!
Come and have a look round.*



**TRADE WAREHOUSE,
DAISY WORKS,
345 STOCKPORT ROAD,
LONGSIGHT,
MANCHESTER M13 0LF**

**ALSO AT
335-341 STOCKPORT ROAD
(NEXT DOOR)**

TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

DECCA		PHILIPS	
CS1730 1733 colour	9.00	G8 & G9 series colour	8.00
CS1830 1835 colour	9.00	PYE 368, 169, 569, 769 mono	8.00
'30' series Bradford colour	9.00	725-741	8.00
80 series colour	8.00	REDIFFUSION Doric Mk.3	10.00
100 series colour	8.00		
KB - ITT		PAPWORTH TRANSFORMERS	
VC200 VC205 VC207 mono	8.00	80 Merton High Street, London SW19 1BE 01-540 3955	
CVC5 CVC7 CVC8 CVC9 col.	9.00	Delivery by return of post.	
CVC20 series colour	8.00		
CVC30 CVC32 series colour	8.00		
CVC45	8.00		
FT100 FT110 state p/no.	10.00		
All lopts and windings are new and guaranteed			

Barclaycard and Access welcome

24 hour answering service

REWIND SERVICE

WINDINGS

RANK	BUSH	MURPHY
T20a T22, T26 Pri & Sec		6.00
Z718 primary state 18" or 22"		6.00
Z718 EHT overwind		8.00

SOVEREIGN FARA £15.00
14" colour overwind

ULTRA THORN	
1690-1691 EHT overwind	7.00
Waltham 190 EHT overwind	6.00
1590 EHT overwind	6.00

Open Mon.-Fri. 9 to 5.30 pm

**EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●**

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (WTON)

**32 TEMPLE STREET,
WOLVERHAMPTON (0902) 29022**

Philips small stereo headphones £4	CV 8617 10p	MJ 2253 60p	Philips car radio speaker door pair £7	Nickel Cadmium Battery Charger AA-C-D-PP9 £6	PC772A3 Compact Disc Headphones Headphone Type £13
Stereo Philips Rank UHF 4 push button tuner £4	Y 716 30p	MJE 3040 60p	2x Hi-Fi Philips car tune up tweeter EN8320 £10	12 Volt Aerial Changer over Relays 144 Mc/s 45 watts 50p	ITT Display Tube 98705 50p
GRC power supply PC743B £10	Y 730 10p	MJE 2209 10p	ITT CVC45 8 way resistor unit for V/cap £3	GE Hitachi V/Cap tuner, after 1979 Series £8	8 Seg Display FN0500 20p
Rank front panel Z950 £5	Y 827: 6A/1KV 20p	SP 8385 50p	4700/10v x 10 50p	6 Push Button Unit for GEC 2100 Series Replacement for Touch Button Unit £8	Model 3000 Pocket Personal D.M.M. Vols. range AC, DC 200Mv to 300V. Rev. 2000K/m £24
Power panel 8,500 Thorn £5	Y 860 50p	SAB 3205 £1.00	68/16 x 10 50p	20AX GEC Split Diode lead £1.00	Export PYE731 6 Push Button unit with (UIIF-VHF) hand switch £4
Fidelity mains switch & lead and filter panel £1	Y 969 50p	SAB 4209 £1.00	150/16 x 10 50p	Electronic Buzzer 60p	ITT Micro Phone M5 50p with switch
Fidelity mono lopt with diode FB51245AE £3	Y 997 30p	G11 condenser 300M + 700 320V £1.80	22/100v x 10 50p	NI.CD Charger MW398 6A.A. £8	Philips Solar Scientific SBC1739 Calculator £12
6 TAG print mains switch PREH 1983 ITT 75p	Min 12 volt Relays R 1038 40p	300M + 700 320V 200 + 100 + 100 + 50 300V 50p	100/350v 70p	NI.CD 5 Hours Battery Charger £8	15v-4.15v 1 Amp Transforms 10p
Rank 1003A tuner on panel £6	R 1039 40p	200 + 100 + 250M 300V 50p	400/350v 70p	Multi Core 60-40 Solder 500G 20 SWG £4.50	RGP30K 8p
Scan control panel Z544 £3	R 2009 80p	Chassis complete Computer Transformer 20v/2.25A; 20v/1.5A; 17.5A; 19.5A; 28v/0.5A £3	.47/500v 25p	15 Watt Stereo Amp Sanyo Module with Data 25pcs Precision Screwdriver & Tool Set £4.00	RGP30G 8p
Rank Z582 IF £3	R 2029 50p	Mains ViewData Torroids £3.75	1/600v 25p	25 Watt Solder Iron	RGP10B 5p
Rank convergence Z910 £3	R 2322/2323 pair 80p	240V/240/6V/4 amp/vb 500ma in / out ----- £3.50	.022/1kv 10p	Various Tools and Accessories	RGP15G 6p
Rank Z582 IF £3	R 2323 15p	Voltage Regulators +5V/UA78P05SC 30p	TV V/Aerial 3000 or 750 10p	1.C.D. clock display with alarm 75p	
Rank Z582 IF £3	R 2324 15p	-5V/LM79M05CP 25p	D/P push mains switch 20p each	Mains lead & two pin socket for radio cassette TV loop aerial 75p	
Rank Z582 IF £3	R 2325 60p	-8V/79M08c 30p	Radio Telescopic Aerial 1.00	Philips Neon Lamps for TV sets 5p	
Rank Z582 IF £3	R 2326 60p	+6V/78M06c 30p	Freeze Philips 1.20	Freeze Philips 1.20	
Rank Z582 IF £3	R 2327 60p	+10v/78LA10 20p	Foam Cleaner Philips 1.20	Contact Cleaner Philips 1.20	
Rank Z582 IF £3	R 2328 60p	LM 317T 35p	Cans of Anti Static, Degrease Cleaner and Anti Corona Lorlin Full Remote Relay Switch fit most TV sets, mains 4 tag, 2 tag 12 volt Mains timer, 13 amp — up to 2 hours: easy to use, plugs into socket Screen locking agent, large can Red E.H.T. LAED and Anode Cap 10 x G11 Cap 47u250 Weller solder iron 15 watt/25 watt Hitachi Silver Oxide Battery G13 UCC357 IEC SR44 1.5V 70ML Silicone Sealer (clear) 100 Coax Plugs De-solder pump + 2 nozzels Philips Plastic box for i.e.s. 6"x3"x1/2" Flat Red LED and Green 50mg 60/40 solder reel Solder 1 kilo reel Clearweld glue pack Dual v/u meter -20 - +10db K30 thermistor 232266298009 GEC Mains Power Supply R.E.G. De-solder Pump	Philips 1.20	Philips, Pye 1.00
Rank Z582 IF £3	R 2329 80p	LM 337 30p	BYX 10 6p	BYX 10 6p	
Rank Z582 IF £3	R 2330 80p	LM 342/18 30p	BYX 36/600 35p	BYX 36/600 35p	
Rank Z582 IF £3	R 2331 80p	LM 347/5.0 50p	BYX 49/600R 75p	BYX 49/600R 75p	
Rank Z582 IF £3	R 2332 80p	+12V/LM 340T12 50p	BYX 55/350 10p	BYX 55/350 10p	
Rank Z582 IF £3	R 2333 15p	+15V/78M15 15p	BYX 55/600 (Bead) 10p	BYX 55/600 (Bead) 10p	
Rank Z582 IF £3	R 2334 15p	+18V/MC78M18 20p	BYX 71/600 50p	BYX 71/600 50p	
Rank Z582 IF £3	R 2335 15p	+24V/78M24 30p	BYX 72/600 20p	BYX 72/600 20p	
Rank Z582 IF £3	R 2336 15p	MC 7724cp 40p	BYX 36/600 50p	BYX 36/600 50p	
Rank Z582 IF £3	R 2337 15p	MC 7824 40p	BYV 95B 10p	BYV 95B 10p	
Rank Z582 IF £3	R 2338 15p	TIS 90 10p	BYV 95C 12p	BYV 95C 12p	
Rank Z582 IF £3	R 2339 15p	TIS 91 20p	BYV 96D 10p	BYV 96D 10p	
Rank Z582 IF £3	R 2340 15p	TIS 92 20p	BYZ 106 10p	BYZ 106 10p	
Rank Z582 IF £3	R 2341 15p	TIS 93 20p	BPW 41 15p	BPW 41 15p	
Rank Z582 IF £3	R 2342 15p	U 19885 40p	BYW 56 2A/1000v G11 8p	BYW 56 2A/1000v G11 8p	
Rank Z582 IF £3	R 2343 15p	U 3832 15p	BZU 15/24 54p	BZU 15/24 54p	
Rank Z582 IF £3	R 2344 15p	U 3845 15p	BZY 93c75 50p	BZY 93c75 50p	
Rank Z582 IF £3	R 2345 15p	MR 508 10p	BZV 15/18 30p	BZV 15/18 30p	
Rank Z582 IF £3	R 2346 15p	MR 501 10p	BZV 15/30 30p	BZV 15/30 30p	
Rank Z582 IF £3	R 2347 15p	MR 502 10p	BZW 70c6v2 10p	BZW 70c6v2 10p	
Rank Z582 IF £3	R 2348 15p	BCW 71R 10p	BZX 79.3v 10p	BZX 79.3v 10p	
Rank Z582 IF £3	R 2349 15p	BYF 1202 10p	Bush thyristor RCA 76122 £1	Bush thyristor RCA 76122 £1	
Rank Z582 IF £3	R 2350 15p	BYF 1204 10p	Transformer 240v/20v-500Ma 75p	Transformer 240v/20v-500Ma 75p	
Rank Z582 IF £3	R 2351 15p	BYF 3126 40p	Chassis type Transformer 240v/12 Volts 500ma 75p	Chassis type Transformer 240v/12 Volts 500ma 75p	
Rank Z582 IF £3	R 2352 15p	BYF 3214 40p	CVC 20 tube base £2	CVC 20 tube base £2	
Rank Z582 IF £3	R 2353 15p	BYX 10 6p	Tube Base Rank & G11 £1.20	Tube Base Rank & G11 £1.20	
Rank Z582 IF £3	R 2354 15p	BYX 36/600 35p	6v-9v-13v tape motor 75p	6v-9v-13v tape motor 75p	
Rank Z582 IF £3	R 2355 15p	BYX 38/600 25p	Infra red led LD57CA 15p	Infra red led LD57CA 15p	
Rank Z582 IF £3	R 2356 15p	BYX 49/600R 75p	G 8 transductor £1.25	G 8 transductor £1.25	
Rank Z582 IF £3	R 2357 15p	BYX 55/350 10p	AT 4041/41 transductor £1	AT 4041/41 transductor £1	
Rank Z582 IF £3	R 2358 15p	BYX 55/600 (Bead) 10p	15K-20 turn pots 20p	15K-20 turn pots 20p	
Rank Z582 IF £3	R 2359 15p	BYX 71/600 50p	Thorn panel 6x100 pot + changeover switch (Irish) 50p	Thorn panel 6x100 pot + changeover switch (Irish) 50p	
Rank Z582 IF £3	R 2360 15p	BYX 72/600 20p	Battery converter TA 75 for colour TV. 12/24v Thorn 3787 50p	Battery converter TA 75 for colour TV. 12/24v Thorn 3787 50p	
Rank Z582 IF £3	R 2361 15p	BYX 36/600 50p	Thorn 3500 2A cut out £6	Thorn 3500 2A cut out £6	
Rank Z582 IF £3	R 2362 15p	BYV 95B 10p	Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit £6	Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit £6	
Rank Z582 IF £3	R 2363 15p	BYV 95C 12p			
Rank Z582 IF £3	R 2364 15p	BYV 96D 10p			
Rank Z582 IF £3	R 2365 15p	BYZ 106 10p			
Rank Z582 IF £3	R 2366 15p	BPW 41 15p			
Rank Z582 IF £3	R 2367 15p	BYW 56 2A/1000v G11 8p			
Rank Z582 IF £3	R 2368 15p	BZU 15/24 54p			
Rank Z582 IF £3	R 2369 15p	BZY 93c75 50p			
Rank Z582 IF £3	R 2370 15p	BZV 15/18 30p			
Rank Z582 IF £3	R 2371 15p	BZV 15/30 30p			
Rank Z582 IF £3	R 2372 15p	BZW 70c6v2 10p			
Rank Z582 IF £3	R 2373 15p	BZX 79.3v 10p			
Rank Z582 IF £3	R 2374 15p	Bush thyristor RCA 76122 £1			
Rank Z582 IF £3	R 2375 15p	Transformer 240v/20v-500Ma 75p			
Rank Z582 IF £3	R 2376 15p	Chassis type Transformer 240v/12 Volts 500ma 75p			
Rank Z582 IF £3	R 2377 15p	CVC 20 tube base £2			
Rank Z582 IF £3	R 2378 15p	Tube Base Rank & G11 £1.20			
Rank Z582 IF £3	R 2379 15p	6v-9v-13v tape motor 75p			
Rank Z582 IF £3	R 2380 15p	Infra red led LD57CA 15p			
Rank Z582 IF £3	R 2381 15p	G 8 transductor £1.25			
Rank Z582 IF £3	R 2382 15p	AT 4041/41 transductor £1			
Rank Z582 IF £3	R 2383 15p	15K-20 turn pots 20p			
Rank Z582 IF £3	R 2384 15p	Thorn panel 6x100 pot + changeover switch (Irish) 50p			
Rank Z582 IF £3	R 2385 15p	Battery converter TA 75 for colour TV. 12/24v Thorn 3787 50p			
Rank Z582 IF £3	R 2386 15p	Thorn 3500 2A cut out £6			
Rank Z582 IF £3	R 2387 15p	Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit £6			
Rank Z582 IF £3	R 2388 15p				
Rank Z582 IF £3	R 2389 15p				
Rank Z582 IF £3	R 2390 15p				
Rank Z582 IF £3	R 2474 15p				
Rank Z582 IF £3	R 2475 1				

