



PRACTICAL WIRELESS

FEBRUARY
1973

20p

3-RANGE CRYSTAL MARKER • 9 VOLT BATTERY ELIMINATOR

General Coverage RECEIVER

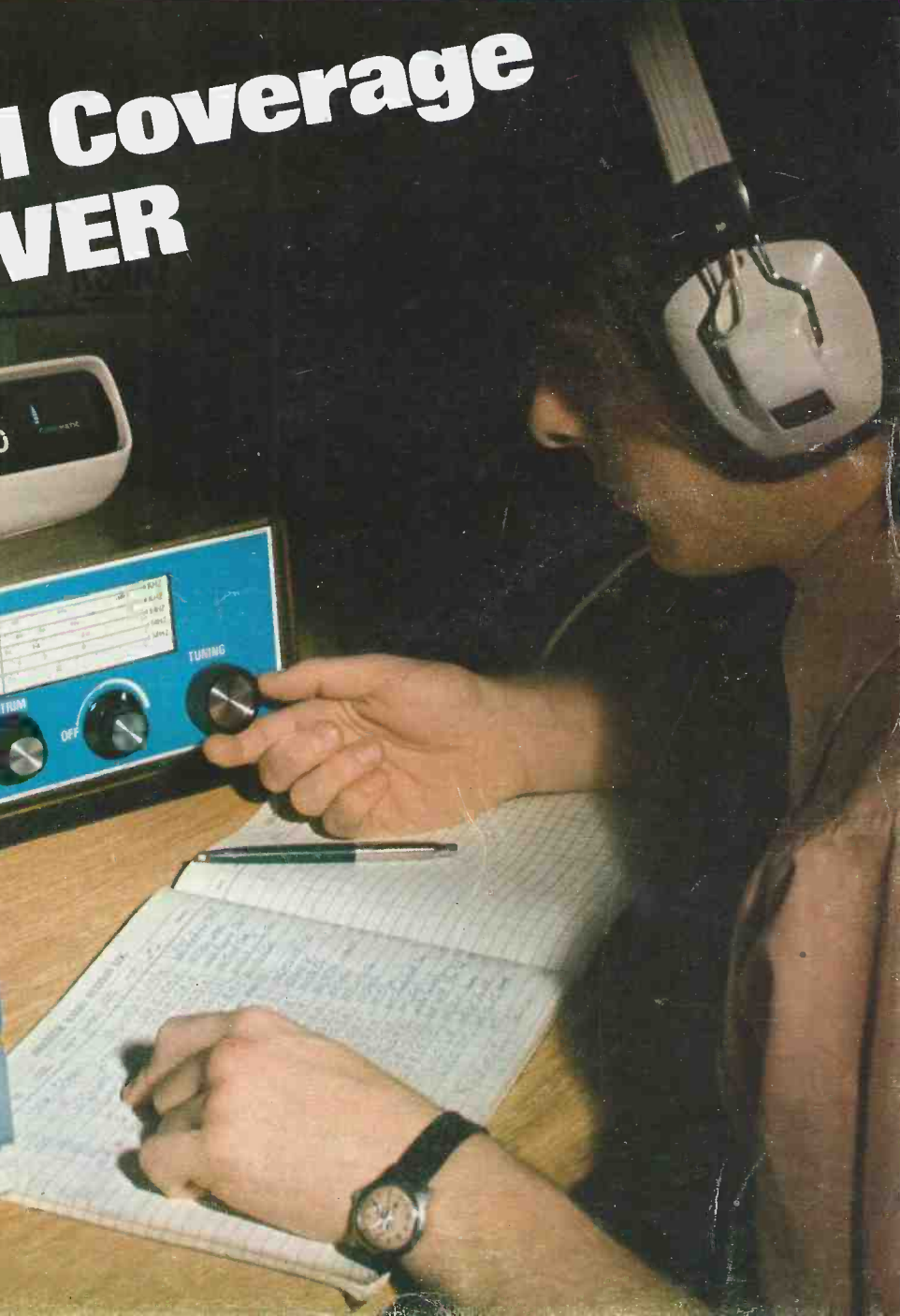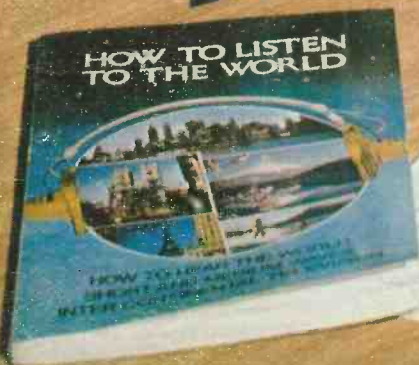

R.S.C. STEREO PACKAGE OFFERS



PACKAGE PRICE FOR ILLUSTRATED UNITS

ONLY **£39-95** Carr. £1-00

Or deposit £9-95 and 9 monthly payments £4-22 (Total £44-98). Individual Rec. Retail Prices:

LINEAR 505 AMP	
LINEAR 505 5 + 5 Watt Amplifier	£17-50
GARRARD 2025 Autochanger + KS40A Cartridge	£18-58
Teak Veneer Plinth with Transparent Plastic Cover	£ 6-10
Pair A55 LOUDSPEAKERS (Inc 8" x 8" 10,000 Gauss)	£11-50
TOTAL	£44-98

SEND S.A.E. FOR FREE COLOUR BROCHURE

SAVE £31-60 ON HIGH FIDELITY UNITS

PACKAGE PRICE FOR ILLUSTRATED UNITS

ONLY **£99-95** Carr. £1-75

Or deposit £15-00 and 12 monthly payments £8-00 (Total £111-00)

Individual Rec. Retail Prices:

GOLDRING GL72 Transcription Turntable + P.U.	£81-89
GOLDRING 6800 Magnetic Cartridge	£12-21
D-E-LUXE PLINTH with Roll-over Cover	£10-50
Pair R.S.C. MONARCH LOUDSPEAKERS	£38-70
R.S.C. SUPER 30 Mk III AMPLIFIER	£88-75
TOTAL	£181-55



FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams, Frequency Response 25 Hz-2 KHz. Impedance 8-15.

Tremendous Value at **£9-95** post free

RSC G66 Mk II 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating 1.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db.



Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and

COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS **£11-50** Carr. 40p. OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £14-99 or dep. £2-20 and 9 monthly payments £1-70 (Total £17-50).

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER



AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE

HF808T 8" 10W	£2-85	HF120D 12" 15W	£4-99
HF102D 10" 10W	£3-40	HF126 12" 15W	£5-75
HF120 12" 15W	£4-50	HF126D 12" 15W	£6-25



FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10-watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. PLEASE STATE IMPEDANCE WHEN ORDERING MODEL 807T 8" 15w with parastic Tweeter. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15.



HIGH FIDELITY LOUDSPEAKER UNITS


Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available. DORCHESTER (Illustrated) Size 16x11x9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts, Fitted High flux 13x8in. £9-45 Carr. 40p.

DUAL Cone speaker. Imp. 3 or 15 ohms. MONARCH Size 19x10x9in. appr. Rating 10 watts. Inc. 13x8in. speaker with highly flexible P.V.C. cone surround, long throw voice coil and 10,000 line magnet. High flux pressure tweeter. Handsome design cabinet. Range 30-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. See 'package offers' for illustration. Carr. 50p **£19-35**

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc. JES Size 16 x 11 x 9in. SE8 For optimum performance. Pressurised. Gives pleasing sound with any 8in. Hi-Fi spkr. Size 22 £6-47

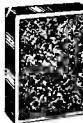8in. Hi-Fi speaker. SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter. SE10 For outstanding results with 10in. Hi-Fi spkr. Size 24 x 15 £6-74



R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v and 30v. to battery radio where A.C. mains 200/250v. 50c/s is available. COMPLETE KIT ASSEMBLED READY FOR USE **£3-25** WITH DIAGRAM **£3-75**

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2db. Harmonic Distortion 0-3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm spkrs. Max. sensitivity 5mv Output rating 1.H.F.M. Fully enclosed enamelled case, 9 1/2 x 9 1/2 x 3 1/2in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£10-95** Carr. 40p. **£7-75**



NOW IN STOCK! FANE 'CRESCENDO' GROUP/DISCO LOUDSPEAKERS

Send S.A.E. for leaflet on this range of extraordinarily efficient units including the very latest BASS CRESCENDO '12'. 100 WATTS FULL DISCOUNT to Genuine Trade Customers. CARR. FREE.

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED.

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2in. 250v., 60mA, 6-3v. 2a. 99p	TOP SHEROURED DROP-THRO' TYPE 250-0-250v. 70mA, 6-3v. 2a. 0-5-6-3v. 2a. £1-35	CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. 89p; 2 1/2a. £1-10; 3a. £1-25; 4a. £1-45; 6a. £1-65; 8a. £2-20	SELENIUM RECTIFIERS F.W. (Bridged) All 6/12v. D.C. output. Max. A.C. input 15v. 1a, 25p. 2a, 35p. 3a, 50p. 4a, 65p. 6a, 80p.
250-0-250v., 60mA 6-3v 2a. £1-05	250-0-250v. 100mA, 6-3v. 3.5a. £1-55	AUTO (Step UP/step DOWN) TRANSFORMERS 0-110/120v. 200-230-250v. 50-80 watts £1-10, 150 watts, £1-90 250 watts £2-75; 500 watts £2-75	SMOOTHING CHOKES 150mA, 7-10H, 250 Ω 70p; 100mA, 10H, 200 Ω 80p; 80mA, 10H, 350 Ω 50p; 60mA, 10H, 50 Ω 400 Ω 25p.
FULLY SHEROURED UPRIGHT MOUNTING 250-0-250v. 60mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-40	250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20	OUTPUT TRANSFORMERS Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 50p	
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20	300-0-300v. 100mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-65	Push-Pull 8 watts EL84 to 3 Ω or 15 Ω ... £1-37	
300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a. For Mullard 510 Amplifier £2-65	300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20	Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15 Ω ... £1-85	
350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20	300-0-300v. 130mA, 6-3v. 4a., c.t. 6-3v. 1a. Suitable for Mullard 510 Amplifier. £2-60	Push-Pull EL84 to 3 or 15 Ω 10-12 watts. £1-35	
350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-25	350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20	Push-Pull Ultra Linear for Mullard 510, etc. £2-20	
425-0-425v. 200mA, 6-3v. 4a., c.t., 6v. 3a. £4-95	350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-60	Push-Pull 15-18 watts, sectionally wound 6L6, KT86, etc., for 3 or 15 Ω ... £1-99	
425-0-425v. 200mA, 6-3v. 4a., 6-3v. 3a., 6v. 3a. £5-10	FILAMENT or TRANSFORMER POWER PACK Types 6-3v. 1.5a. 49p; 6-3v. 2a. 54p; 6-3v. 3a. 79p; 6-3v. 6a. £1-80; 12v. 1a. 65p; 12v. 3a. or 24v. 1-5a. £1-25; 0-9-18v 1 1/2a. £1-10; 0-12-25-42v 2 1/2a. £1-76.	Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT86 etc. to 3 or 15 Ω £3-80	
450-0-450v. 250mA, 6-3v. 4a., c.t., 6v. 3a. £5-50			

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET Only high grade components by leading manufacturers

- * Push Button Selector Switching
- * Jack Socket for Headphones
- * Neon Indicator
- * Satin Silver Finish Metal Fascia
- * Solid State Circuitry
- * Twenty Silicon Transistors
- * Four Diodes, Four Rectifiers

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ± 1 1/2 dB.



COMPLETE KIT (less cabinet). Carr. 65p. Cabinet if req. £5 extra. **£25**

FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £3-99 (Total £42-91). **£38-75**

R.S.C. STEREO FM TUNER. Visually matches Super 30 Mk. III at **£44-95**

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- * Moderate size only 25 x 14 x 10in. approx.
- * Response 30-20,000 c.p.s. Impedance 15 ohms
- * Performance comparable with units costing considerably more Carr. 65p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-47 (Total £26-83). **£23**



DEMONSTRATIONS AT ALL BRANCHES

RSC GROUP/DISCO UNITS



HEADPHONES MICROPHONE

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN
TYPE C412 30-40 WATTS Fitted two exceptionally efficient, low feedback bowl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £3 and 9 monthly payments £2-22 (Total £22-98) Carr. 50p. **£19-95**
TYPE C412S 50 WATTS Fitted four 12" 11,000 line 15 watt speakers: Overall size approx. 56 x 14 x 9in. Terms: Dep. £4 and 9 monthly payments £3-37 (Total £34-38) Carr. 75p. **£31**
TYPE C4100 100 WATTS inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 58 x 16 x 10" Acoustically fitted and pressurised. Terms: Dep. £11 and 12 monthly pmts. £5-18 (Total £78-16). **£65** Carr. £1


R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output. Hum level—70dB. Response ±3dB 20-20,000 cfs. All high grade components. Valves 6F86, 6F86, ECC83, EL34, EL34, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram. Pick-up etc. for mixing purposes. 200-250v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Twin-handled perforated cover £1.90. 12 MONTHS' GUARANTEE. Carr. 65p. **£19-75**
TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22-90). Send S.A.E. for leaflet.

LINEAR T40/60D 50W GROUP/DISCO AMPLIFIER


★ FULL MONITORING FACILITIES
 ★ Individual Bass and Treble controls
 ★ Twin jack output sockets for speakers
 ★ Input sockets for medium or high impedance Microphones or Guitar P.U.s and Crystal or Ceramic Gram. P.U.s
 ★ Frequency response 20-20,000 Hz.
 ★ Output overload protection plus double fusing
FRONT PANEL (Jack inputs)
 Gram, Microphone/Guitar P.U.; plus monitoring socket.
CONTROLS Vol. (1) (2) (3) and (4). Bass, Treble, Master Vol., Monitor Selection Switch Gram (1) or (2), Mains Switch

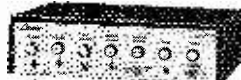

£49-50 Carr. free
 Simulated black rexine, plastic bonded metal case.
ALSO STOCKED LINEAR T80/100D £69-75
 Or Deposit £7-50 and 9 monthly payments £5-37 (Total £55-83)

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

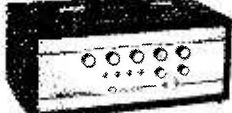Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker's 3 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £7-25 & 9 monthly payments £34-95 Carr. 70p. **£34-95**




RSC PHANTOM '50' Combined 50w Amplifier and 12in. Loudspeaker. For Bass instruments). Inc. 3 inputs and 2 vol. controls plus Treble Bass and Presense. Output Jack for additional 15ohm Speaker. Attractively finished in black with silver-finish fascia and trimmings. Compact size. Fitted carrying handle. Available early February. Carr. £1-50 Terms Deposit £3-95 and 9 monthly pmts. £6 (Total £28-95) **£55-95**

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.
 ★ Two extra heavy duty 12in. 50w Loudspeakers.
 ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls.
 Credit Terms: Deposit £15 & 9 monthly payments of £2-25. **£65** Carr. £2 Send S.A.E. for leaflet.



RSC GP30 HI-FI AMPLIFIER

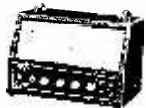

For Guitar, Vocal or Instrumental Group
 A 4 input. 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet
 For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 9 monthly payments of £2-45 (Total £26-45). **£23-50** Carr. 65p

with handles. Attractive black/gold P.V.C. fascia. Neon indicator.

PACKAGE OFFER

- Units listed below
 (a) 100w POWER AMPLIFIER
 (b) PAIR OF HI-FI HEAD- PHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to headphones)
 (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets
 Size approx. 18" x 18" x 8"
 (a)(b)(c)&(d) Carr. £1-25
£72-85

Terms on Amps. Speakers and Head- phone/Mike. Deposit £15 and 18 monthly payments of £4-00 (Total £87-00).

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 Mk.III turntables and Sonotone or Accos turntables with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Rexine covered Cabinet with lid. see illus. on left. Carr. £1-25
 Or Dep. £13-25 and 9 monthly pmts £6-88 (Total £75-17) or Dep. £15 and 18 monthly payments £3-68 (Total £80-18). **£67-10**

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.
'POP' 100 18" 100Watt 14,000 gauss 8/15Ω **£22-95** Dep. £6 and 9 monthly payments £2-20 (Total £25-80)
'POP' 60 15" 60 Watt 13,000 gauss 8/15Ω **£12-90** Dep. £3-50 and 9 monthly payments. £1-30 (Total £15).
'POP' 50 12" 50 Watt 13,000 gauss 15Ω **£10-90** Dep. £2 and 9 monthly payments £1-20 (Total £12-80) PAIR SUITABLE ALL PURPOSES
 FOR BASS GUITAR, ELECT. ORGAN, ETC.

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for use other than Bass Guitar or Electronic Organ). Carr. free **£6-75** or Dep. £1-25 and 9 monthly payments 75p (Total £8-00).

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

DESCRIPTION	PRICE	PACKAGE PRICE
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95	£45 carr. £1
PR. FANE POP 25/2 25W/L SPEAKERS	£13-50	
Terms: Deposit £6-50 and 9 monthly payments of £4-92 (Total £50-78)	£48-45	
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95	£52 carr. £1
PR. FANE POP 50 L/SPEAKERS	£21-80	
Terms: Deposit £10 and 9 monthly payments of £5-37 (Total £58-33)	£58-75	
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95	£56 carr. £1-25
PAIR L12/25 25W L/S in cabinets	£23-90	
Terms: Deposit £10 and 9 monthly payments of £5-88 (Total £62-92)	£58-85	
LINEAR T40/60D AMPLIFIER	£49-50	£69-95 carr. £1-50
PAIR L12/25 L/S in cabinets	£23-90	
Terms: Deposit £9-95 and 9 monthly payments of £7-67 (Total £78-88)	£78-40	
F.A.L. PHASE 100 AMPLIFIER	£61-95	£99-95 carr. £2
4 FANE POP 50 L/SPEAKERS	£43-60	
Terms: Deposit £15-95 and 9 monthly payments of £10-78 (Total £112-52)	£105-55	

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH
L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50. **£34-50**
 Or deposit £5-50 and 9 monthly pmts. of £3-70. Total £28-80
L12/20 12" 20-25 WATT 13,000 lines 15 ohms. Carr. 50p. **£11-95**
L13 13" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State impedance required. Carr. 40p. **£5-25**

★ CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

NOW FOUR NEW BRANCHES
NOTTINGHAM 19/19A MARKET STREET
SUNDERLAND 5 MARKET SQUARE
STOCKPORT 8 LITTLE UNDERBANK
COVENTRY 7 SHELTON SQUARE

New premises at **HULL & NEWCASTLE** See Addresses



MAIL ORDERS & EXPORT ENQUIRIES TO—
 AUDIO HOUSE, HENCONNER LANE, LEEDS, 13. Tel: Pudsey (09735) 77631.
 TERMS C.W.O. or C.O.D. No C.O.D. under £1. POSTAGE 25p EXTRA UNDER £2. 30p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED. S.A.E. PLEASE WITH ENQUIRIES.
 SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS

R.S.C. Branches operate a 5-day week OPEN ALL DAY SATURDAY

- BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349
BLACKPOOL (Agent) O & C Electronics 227 Church Street
BIRMINGHAM 30/31 Great Western Arcade, Tel. 021-236 1279 (Closed Wed.).
COVENTRY 17 Shelton Square
DERBY 26 Osaston Rd., The Spot (Closed Wed.). Tel. 41361
DARLINGTON 19 Northgate (Closed Wed.) Tel. 68043
EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158
HULL 7 Whitefriargate Tel. 20505
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28282
LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629
MANCHESTER 60A Oldham Street, (Closed Wed.). Tel. 236 2778
MIDDLESBROUGH 106 Newport Rd. (Closed Wed.).
NEWCASTLE UPON TYNE Tel. 47096
 28 Newgate Shopping Centre (Closed Wed.). Tel. 21469
NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 42068
SHEFFIELD 13 Exchange Street (Castle Market Bldg.) (Closed Thurs.). Tel. 02716
STOCKPORT 8 Little Underbank. Tel: 480-0777.
SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 70573

TOP QUALITY — LOW COST



AMATEUR RADIO EQUIPMENT



P.R.40

SOLID STATE
R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now superceded. It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain, up to an overall average of 30 dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee. . . . £8-90 Carriage 30p.



MULTIBAND-6

SOLID STATE
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery). £13-20 Carriage 35p. Stamp brings illustrated leaflets.



ON THE DESIGN STAFF—
G3SZM G3IRE


CODAR

TELECOMMUNICATIONS AND ELECTRONIC
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

BN15 - 8TZ

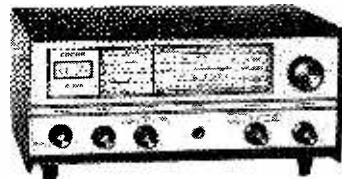

CR70A

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

Complete ready built £27-50, Carriage 70p.

SEND FOR YOURS TODAY!

NOTE: These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers and are FREE of Purchase Tax. Some portable receivers being advertised as Communication Receivers do not meet these requirements.

GUNTON ELECTRONIC IGNITION KIT £7-95

+ 35p P. & P.

READY BUILT UNIT
GUARANTEED 5 YEARS

£9-95 + 35p P & P

Patents pending. 12 volt only—state pos. or neg. earth. Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- ★ Continual Peak-Tuned Performance
- ★ Up to 20% reduced fuel consumption
- ★ Easier All-weather Starting
- ★ Increased Acceleration and Top Speed
- ★ Longer Spark Plug Life
- ★ Increased Battery Life
- ★ Elimination of Contact Breaker Burn
- ★ Purer Exhaust Gas Emission



Kit includes absolutely everything for assembly: Case, Cables, Coil Connectors, Silicon Grease, etc. 8 page illustrated instructions cover fitting of all Types of Tachometers. Call in for a Workshop Demonstration. S.A.E. all enquiries please or Phone 33652 (many letters from satisfied customers).

ALUMINIUM BOXES

Complete with baseplate and screws

At direct from manufacturer prices with return of post service

Type No.	L	W	D	Price	P & P
7*	5 1/2	2 1/2	1 1/2	25p	15p
8*	4	4	1 1/2	25p	15p
9*	4	2 1/2	1 1/2	25p	13p
10*	5 1/4	4	1 1/2	29p	18p
11	4	2 1/2	2	25p	13p
12	8	2	1	22p	13p
13	8	4	2	35p	18p
14	7	5	2 1/2	42p	19p
15	8	6	3	54p	26p
16	10	7	3	61p	26p

*THESE SIZES ACCEPT STANDARD VEROBOARD RANGE

DEPT. PW ELECTRONICS DESIGN ASSOCIATES
82 BATH STREET, WALSALL WS1 3DE

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for £1-12. DAF96, DF96, DK96, DL96, 4 for £1-55.

1R5	-28	30C15	-58	EABC80	-32	EL500	-62	PCF808	-68	U801	-75
1S5	-22	30C17	-78	RAF42	-50	EM80	-36	PCL82	-30	UABC80	-31
1T4	-16	30C18	-58	BB91	-10	EM81	-36	PCL83	-55	UAF42	-50
3B4	-26	30F5	-64	EB33	-40	EM84	-32	PCL84	-33	UBC41	-45
3V4	-47	30FL1	-49	EM87	-50	PCF85	-38	PCF86	-38	UBF89	-34
5U4G	-31	30FL2	-69	EB31	-30	EY61	-36	PCL86	-37	UBF89	-32
5V4G	-35	30FL14	-68	EB30	-22	EY36	-29	PCL88	-68	UCC84	-32
5Y3GT	-30	30L1	-29	EBF80	-32	EY87	-29	PCL800	-39	UCC85	-35
5Z4G	-35	30L15	-70	EBF83	-39	EZ40	-39	PCL805	-38	UCF80	-30
6/30L2	-54	30L17	-67	EBF89	-29	EZ41	-39	PENA4	-77	UCL44	-33
6AL5	-11	30F4	-65	EC81	-17	EZ50	-31	PEN36C	-70	UCL81	-30
6AM6	-13	30P12	-69	EC82	-20	EZ81	-32	PFL200	-51	UCL82	-32
6AQ5	-22	30P19	-65	EC83	-35	EZ90	-25	PL36	-48	UCL83	-35
6AT6	-20	30P11	-60	EC85	-34	GZ30	-34	PL81	-43	UF41	-32
6AT6	-20	30P13	-89	EC804	-54	GZ32	-40	PL81A	-47	UF89	-30
6BA6	-20	30P14	-80	ECF80	-30	KT41	-77	PL92	-31	UL41	-33
6BE6	-21	35L6GT	-45	ECF82	-26	KT61	-55	PL83	-33	UL84	-30
6B36	-41	35W4	-25	ECH35	-55	KT66	-78	PL84	-30	UM84	-22
6BW7	-50	35Z4GT	-25	ECH42	-59	LN319	-68	PL600	-68	UY41	-39
6F14	-35	50CD6G	-68	ECF81	-29	LN329	-72	PL504	-63	UY86	-25
6F23	-68	807	-49	ECF83	-38	LN339	-65	PM84	-30	VP4B	-77
6F25	-53	AC/VP2	-77	ECF84	-35	N78	-37	PX25	-95	W77	-43
6J7G	-24	B349	-70	ECL80	-30	P81	-40	PY32	-82	Z77	-29
6K7G	-12	B729	-54	ECL82	-29	PABC80	-31	PY33	-52	Transistors	-
6K8G	-36	OCH35	-67	ECL86	-35	PC86	-47	PY81	-25	AC107	-17
6Q7G	-35	CY31	-28	EF39	-38	PC88	-47	PY82	-25	AC127	-18
6DL7GT	-30	DAF91	-22	EF41	-57	PC86	-42	PY83	-26	AD140	-37
6SN7GT	-30	DAF96	-68	EF80	-23	PC87	-36	PY88	-33	AF115	-29
6V6G	-28	DF91	-16	EF83	-27	PC800	-29	PY900	-31	AF116	-30
6V6GT	-28	DF96	-36	EF86	-30	PC884	-29	PY801	-31	AF117	-30
6X4	-23	DH77	-20	EF89	-26	PC885	-23	R19	-30	AF125	-17
6X6GT	-28	DK32	-33	EF91	-13	PC888	-38	R20	-70	AF127	-17
10P13	-53	DK91	-28	EF92	-27	PC899	-43	U25	-73	OC26	-25
12AT7	-17	DK92	-60	EF98	-65	PCF889	-48	U26	-65	OC44	-12
12AU7	-20	DK96	-45	EF83	-27	PC805	-70	U47	-73	OC45	-12
12AX7	-22	DL35	-40	EF184	-29	PCF80	-28	U49	-70	OC71	-12
19BG6G	-75	DL92	-26	EH90	-34	PCF82	-33	U52	-31	OC72	-12
20F2	-67	DL94	-47	EL33	-55	PCF86	-46	U78	-28	OC75	-12
20P3	-75	DL96	-38	EL34	-48	PCF800	-58	U191	-68	OC81	-12
25L6GT	-19	DY86	-24	EL41	-54	PCF801	-28	U193	-31	OC82	-12
25U4GT	-57	DY87	-24	EL90	-26	PCF802	-39	U251	-61	OC82	-12
30C1	-26	DY802	-33	EL95	-33	PCF806	-56	U301	-38	OC82D	-12
								U329	-68	OC170	-33

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per. valve extra)


Any parcel insured against damage in transit 3p extra.

look!

electronics really mastered

**... practical
... visual
... exciting!**

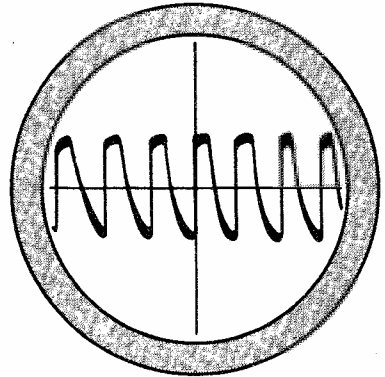no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

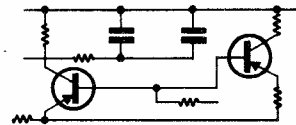2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL23

special free gift also to all our students

DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE SERIOUSLY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

GARRARD SP25 Mk. III SPECIAL OFFER
£17.45
 Garrard SP25 Mk. III Goldring G800
 Teak plinth and tinted cover. All leads supplied.
 Please add £1.25 for P. & P.

TURNTABLES

Please add 75p P. & P.
 Garrard SP25 Mk. III £9.90
 Garrard AP76 £17.45
 Garrard SL65B £12.90
 Garrard 401 £29.95
 Garrard Zero 100 (Auto) £37.95
 Garrard Zero 100 (Single) £36.45
 BSR MP60 £21.80
 Goldring GL72 £27.40
 Goldring GL72/P £26.75
 Goldring GL75 £23.90
 Goldring GL75/P £20.00
 Goldring 101/PC £26.50
 Wharfedale Linton & cart. Thorens TD125AB Mk. II New product £91.75
 Thorens TD150 Mk. II £26.90
 Thorens TD150A Mk. II £33.75

TUNERS

Please add 75p P. & P.
 Amstrad Multiplex 3000 £29.75
 Armstrong 523 £39.50
 Armstrong 524 £31.45
 Rogers Ravensbrook FET4 (Chassis) £30.70
 Rogers Ravensbrook FET4 (Cased) £34.90
 Rogers Ravensbourne FET4 (Chassis) £42.15
 Rogers Ravensbourne FET4 (Cased) £42.15
 Rogers Ravensbourne FET4 (Cased) £46.95
 Sinclair PRO60 (Module) £15.60
 Sinclair Cased Tuner £28.85
 Leak Delta FM (Cased) £53.65
 Leak Delta AM/FM (Cased) £62.95
 Alpha Highgate FT 150 £38.25

TUNER/AMPLIFIERS

Please add 75p P. & P.
 Alpha Highgate 150 £49.95
 Armstrong 525 (Teak cased) £69.45
 Armstrong 526 AM/FM (Teak cased) £77.25
 Leak Delta 75 £120.95
 Philips RH702 £82.50
 Teleton 2100 £31.00
 Goodmans One Ten £98.00
 Rogers R/brook (Teak) £81.50
 Rogers R/brook (Chassis) £74.75
 Alpha FR 3000 New Prod. £74.40
 Nivico 4VR 5414 (Quad) £175.00
 Goodmans Mod 80 (Teak) £66.75

All prices correct at time of writing. E. & O.E. and are subject to alterations.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. PW2, 174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m.

LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

AMPLIFIERS

Please add 75p P. & P.
 Amstrad 8000 Mk. II £15.50
 Amstrad IC2000 £28.95
 Amstrad Integra 4000 £22.75
 Armstrong 521 (teak cased) £44.50
 Alpha Highgate 212 £23.75
 Alpha Highgate FA300 £32.63
 Alpha Highgate FA400 £38.00
 Leak Delta 30 £45.85
 Leak Delta 70 £55.95
 Metrosound ST20E £24.15
 Metrosound ST60 £45.50
 Pioneer SA600 £57.00
 Pioneer SA900 £86.45
 Pioneer SA1000 £93.00
 Rogers R/brook (Chassis) £38.25
 Rogers R/brook (Cased) £41.95
 Rogers R/bourne (Chassis) £41.75
 Rogers R/bourne (Cased) £48.35
 Sinclair PRO60 2 x Z30/PZ5 £14.70
 Sinclair PRO60 2 x Z30/PZ6 £16.70
 Sinclair PRO60 2 x Z50/PZ8/Trans £20.90
 Sinclair ABU (Filter Unit) £42.20
 Sinclair 605 £17.90
 Sinclair 2000 £20.95
 Sinclair 3000 £28.10
 Wharfedale Linton £42.95
 Wharfedale SAQ307 £23.95
 Rocel RA 210 £30.25
 Rocel RA 610 £47.75

SPEAKERS

Please add £1.25 P. & P. per pair
 Amstrad 138 £13.90
 Wharfedale Denton 2 £27.85
 Wharfedale Linton 2 £26.75
 Wharfedale Melton 2 £46.95
 Wharfedale Dovedale 3 £59.75
 Celestion Ditton 120 £39.25
 Celestion Ditton 15 £52.00
 Celestion Ditton 25 £85.25
 Celestion County (new prod.) £35.50
 Goodmans Double Maxim £47.75
 Goodmans Mezzo 3 £46.75
 Goodmans Magister £76.95

£3.05



Plus 35p p. & p.
 Finished in teak veneer with tinted dust cover, fully assembled. For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR McDonald MP60 and others. For AP76; P75; SL72B; SL95B; £4.30 plus 55p P. & P. Also finished in walnut to match Japanese equipment—at no extra.

CARTRIDGES

Please add 10p for P. & P.
 Goldring G800 £3.15
 Goldring G800 £4.95
 Goldring G800E £8.00
 Goldring G800 Super E £14.15
 Shure M3D £3.70
 Shure M44E £4.90
 Shure M55E £5.60
 Shure M75E Type 2 £10.25
 Sonotone 9TAHC £1.40

TV's 19" NOW £11.95


TWO YEARS' GUARANTEE ALL MODELS

405/625: 19" £25.95
 FREE 23" £35.95

CATALOGUE CARR £1.95


COLOUR TV 19" £145
 OR 25" £185

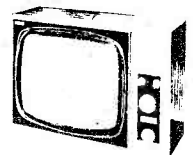LIMITED SUPPLY, REGRET PERSONAL CALLERS ONLY
 A SELECTION OF RECENT YEARS MODELS
 U.K. MANUFACTURE



TV TUBES REBUILT GUARANTEED 2 YEARS

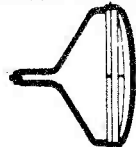17" and 19" £5.95; 21" and 23" £6.45
 Exchange Bowls carr. 55p



COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 22p.
 Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p.
 Record Player Cabinets: £3.75p
 Designed for the modern auto-changer. Size 17" x 15" x 7 1/2". p.p. 55p.
 Radio: £3.95 8 transistor LW/MV. Free case, battery. Post 15p.
 Precision Tape Motors: £1.95. 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free.
 Modern Gang Condensers: 30p.
 AM/FM or AM only 20p. Post 10p.
 Press Button VHF Tuner 75p.
 Brand new, takes PCF806, PC89. Post 25p.
 Valve ELL80 50p
SPECIAL OFFER
 Pots: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg/100 KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg.

DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12. Phone 01-478 6001-2-3

MINIATURE POWER DRILLS

Capable of Drilling Mild Steel

IDEAL FOR PRINTED CIRCUITS
 PRECISION DRILLING,
 CUTTING, GRINDING

12 volt D.C.;



PRICES FROM £3.00

EXPO DRILLS LTD.,
 DEPT. PW1, 62 NEAL STREET, LONDON, W.C.2

TRADE DISTRIBUTOR N. Rosa (Electrical) Ltd., London, W.C.1.

AUTOMATIC EMERGENCY SUPPLY

250v 50Hz—150 watt Inverter. Full kit of parts excluding meter. Circuit as appeared in December P.V. Complete kit—£16.95 + 80p P. & P.

OTHER INVERTERS AVAILABLE IN KIT FORM

150 Watt—£13.50 + 60p P. & P. 75 Watt—£7.80 + 60p P. & P.
 300 Watt—£17.90 + 85p P. & P. 40 Watt—£5.20 + 40p P. & P.
 25 Watt—£2.60 + 20p P. & P.

All above operate from 12v. battery and give 250v.—50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

SPECIAL OFFER

12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc. 12 inch—8 watt—£3.40 post paid. 21 inch—13 watt—£4.20 post paid. Large discounts available for quantities.

TEXAN AMPLIFIER

Fibre glass P.C. board—£2.00 + 10p P. & P.
 Transformer—£4.00 + 30p P. & P.
 Other components including Teak Cabinet—£24.00 + Postage.

ASTRO ELECTRONICS

6, BARNES ROAD, CHESTERFIELD, DERBYSHIRE

Build yourself a TRANSISTOR RADIO

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)

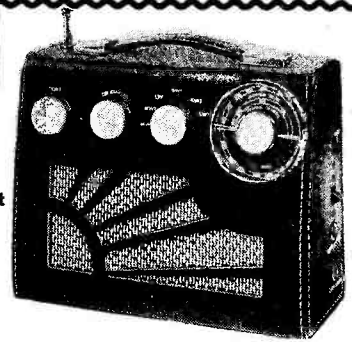


ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW Transistors. Car aerial and Tape record sockets. Selectivity switch, 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

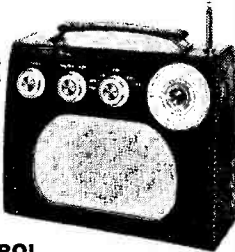
Total building cost **£6-98** P.P. & (Overseas P. & P. £1) Ins. 45p.



ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

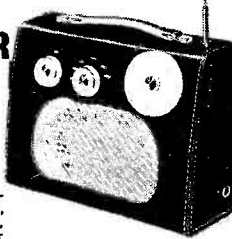
Total building costs **£5-98** P.P. & (Overseas P. & P. £1) Ins. 45p.



ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3, Trawler, band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—8 transistors and 2 diodes Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 25p (FREE with parts).

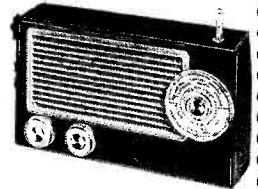Total building costs **£3-98** P.P. & (Overseas P. & P. £1) Ins. 30p



POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended MW band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-29** P.P. & (Overseas P. & P. 63p) Ins. 23p



TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-50** P.P. & (Overseas P. & P. 63p) Ins. 24p




TRANS EIGHT

8 TRANSISTORS AND 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for MW, and LW. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

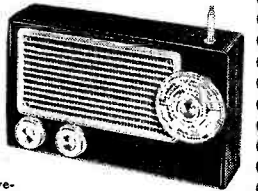Total building costs **£4-48** P.P. & (Overseas P. & P. £1) Ins. 32p



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/4" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

Parts price list and easy build plans 25p (FREE with parts).

All parts including **£5-50** P.P. & (Overseas P. & P. £1) Ins. 32p



(Overseas P. & P. £1)

FULL AFTER SALES SERVICE

* Callers side entrance "Lavells' Shop
* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 15A. Tel. 0234 52367

I enclose £..... please send items marked.

ROAMER TEN ROAMER SEVEN
ROAMER EIGHT TRANS EIGHT
TRANSONA FIVE ROAMER SIX
POCKET FIVE EDU-KIT

Parts price list and plans for.....

Name.....

Address.....

PW50

SEW PANEL METERS

CLEAR PLASTIC PANEL METERS


USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

- LOW COST
- QUICK DELIVERY
- OVER 200 RANGES IN STOCK
- OTHER RANGES TO ORDER

"SEW" BAKELITE PANEL METERS

Type SW.100 100 x 80 mm.

50μA	\$2.80
50-500μA	\$2.80
100μA	\$2.80
100-1000μA	\$2.70
500μA	\$2.50
1000μA	\$2.40
20V. D.C.	\$2.40
50V. D.C.	\$2.40
300V. D.C.	\$2.40
1 amp. D.C.	\$2.40



5 amp. D.C. \$2.40
VU Meter \$2.15

Type SD.830 82.5mm x 110mm Fronts

10mA	\$2.50
50mA	\$2.50
100mA	\$2.50
100-1000μA	\$2.50
500μA	\$2.50
1 amp. D.C.	\$2.50
5 amp. D.C.	\$2.50
10 amp. D.C.	\$2.50
50V. D.C.	\$2.50
100V. D.C.	\$2.50
200V. D.C.	\$2.50
300V. D.C.	\$2.50
1mA	\$2.50
5mA	\$2.50

Type SD.640 63.5mm x 85mm Fronts

50μA	\$2.60
50-500μA	\$2.55
100μA	\$2.55
100-1000μA	\$2.55
500μA	\$2.55
1000μA	\$2.55
1mA	\$2.35
5mA	\$2.35
10mA	\$2.35
50mA	\$2.35
100mA	\$2.35

Type SD.460 46mm x 59.5mm Fronts

50μA	\$2.40
50-500μA	\$2.35
100μA	\$2.35
100-1000μA	\$2.35
500μA	\$2.35
1000μA	\$2.35
1mA	\$2.15
5mA	\$2.15
10mA	\$2.15
50mA	\$2.15
100mA	\$2.15

***MOVING IRON—**
ALL OTHERS MOVING COIL
Please add postage

Type MR.85P. 4 1/2in. x 4 1/2in. fronts

50mA	\$2.80
100mA	\$2.80
500mA	\$2.80
1 amp.	\$2.80
5 amp.	\$2.80
15 amp.	\$2.80
30 amp.	\$2.80
20V. D.C.	\$2.80
50V. D.C.	\$2.80
150V. D.C.	\$2.80
300V. D.C.	\$2.80
15V. A.C.	\$2.80
300V. A.C.	\$2.80
15V. A.C.	\$2.80
300V. A.C.	\$2.80
8 Meter 1mA	\$2.80
VU Meter	\$2.85
1 amp. A.C.*	\$2.80
5 amp. A.C.*	\$2.80
10 amp. A.C.*	\$2.80
20 amp. A.C.*	\$2.80
30 amp. A.C.*	\$2.80

Type MR.52P. 2 1/2in. square fronts

50μA	\$2.40
50-500μA	\$2.35
100μA	\$2.35
100-1000μA	\$2.35
500μA	\$2.35
1000μA	\$2.35
1mA	\$2.20
5mA	\$2.20
10mA	\$2.20
50mA	\$2.20
100mA	\$2.20
500mA	\$2.20
1 amp.	\$2.20
5 amp.	\$2.20

Type MR.65P. 3 1/2in. x 3 1/2in. fronts

50μA	\$2.70
50-500μA	\$2.60
100μA	\$2.60
100-1000μA	\$2.60
500μA	\$2.60
1000μA	\$2.60
1mA	\$2.40
5mA	\$2.40
10mA	\$2.40
50mA	\$2.40
100mA	\$2.40
500mA	\$2.40
1 amp.	\$2.40
5 amp.	\$2.40
10 amp.	\$2.40
15 amp.	\$2.40
20 amp.	\$2.40
30 amp.	\$2.40
50 amp.	\$2.75
5V. D.C.	\$2.40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

Type MR.38P. 1 21/32in. square fronts

200mA	\$1.75
300mA	\$1.75
500mA	\$1.75
750mA	\$1.75
1 amp.	\$1.75
2 amp.	\$1.75
5 amp.	\$1.75
10 amp.	\$1.75
3V. D.C.	\$1.75
10V. D.C.	\$1.75
15V. D.C.	\$1.75
20V. D.C.	\$1.75
50V. D.C.	\$1.75
100V. D.C.	\$1.75
150V. D.C.	\$1.75
300V. D.C.	\$1.75
500V. D.C.	\$1.75
750V. D.C.	\$1.75
15V. A.C.	\$1.85
300V. A.C.	\$1.85
15V. A.C.	\$1.85
300V. A.C.	\$1.85
8 Meter 1mA	\$1.85
VU Meter	\$2.80

Type MR.45P. 2in. square fronts

50μA	\$2.50
50-500μA	\$2.30
100μA	\$2.30
100-1000μA	\$2.30
500μA	\$2.30
1000μA	\$2.30
1mA	\$2.15
5mA	\$2.15
10mA	\$2.15
50mA	\$2.15
100mA	\$2.15
500mA	\$2.15
1 amp.	\$2.15

"SEW" EDGWISE METERS

Type PE.70. 3 1/2in. x 1 1/2in. x 2 1/2in. deep

50μA	\$2.40
50-500μA	\$2.30
100μA	\$2.30
100-1000μA	\$2.30
500μA	\$2.30
1000μA	\$2.30
1mA	\$2.15
5mA	\$2.15
10mA	\$2.15
50mA	\$2.15
100mA	\$2.15
500mA	\$2.15
1 amp.	\$2.15

Type MR.65. 3 1/2in. square fronts

1 amp.	\$2.15
5 amp.	\$2.15
15 amp.	\$2.15
30 amp.	\$2.15
50 amp.	\$2.15
5V. D.C.	\$2.15
10V. D.C.	\$2.15
20V. D.C.	\$2.15
50V. D.C.	\$2.15
150V. D.C.	\$2.15
300V. D.C.	\$2.15
500V. D.C.	\$2.15
750V. D.C.	\$2.15
15V. A.C.	\$2.15
300V. A.C.	\$2.15
15V. A.C.	\$2.15
300V. A.C.	\$2.15
8 Meter 1mA	\$2.15
VU Meter	\$2.15

Type S-80 80 mm. square fronts

50μA	\$2.50
50-500μA	\$2.40
100μA	\$2.40
100-1000μA	\$2.30
500μA	\$2.30
1000μA	\$2.30
1mA	\$2.15
5mA	\$2.15
10mA	\$2.15
50mA	\$2.15
100mA	\$2.15
500mA	\$2.15
1 amp.	\$2.15

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. The 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	\$5.50
100μA	\$5.10
1mA	\$4.85
50-500μA	\$5.10
1-10mA	\$4.85
1A d.c.	\$4.85
5A d.c.	\$4.85
10V d.c.	\$4.85
20V. d.c.	\$4.85
50V. d.c.	\$4.85
300V. d.c.	\$4.85
Dual range 100mA/5A d.c.	\$5.10
5V/50V d.c.	\$5.10

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. In. dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 80p. P. & P. 71p.
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. \$1.15 P. & P. 71p.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. \$1.65 P. & P. 71p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

S-260 General Purpose Bench Mounting		S-260B Panel Mounting	
1 Amp	\$7.00	1 Amp	\$7.00
2-5 Amp	\$8.05	2-5 Amp	\$8.05
5 Amp	\$11.75	Please add postage	
8 Amp	\$15.90	ALL MODELS	
10 Amp	\$22.50	INPUT 230 V 50/60 CYCLES	
12 Amp	\$23.50	OUTPUT V. VARIABLE 0-260 VOLTS	
20 Amp	\$49.00	Special discounts for quantity	
25 Amp	\$58.00		
40 Amp	\$82.50		

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

80 W	\$2.10	P. & P. 18p
150 W	\$2.70	P. & P. 18p
300 W	\$3.60	P. & P. 23p
500 W	\$5.25	1. & P. 33p
1000 W	\$7.50	P. & P. 33p
1500 W	\$10.20	P. & P. 43p
2250 W	\$17.25	P. & P. 50p
5000 W	\$35.00	P. & P. 21

MCA.220 AUTOMATIC VOLTAGE STABILISER

Input 88 125 VAC or 176 250VAC. Output 120V AC. or 240 VAC. 200 VA rating. \$11.97, carr. 50p.

BH.001 HEAD SET AND BOOM MICROPHONE

Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. \$4.62. P. & P. 15p.

240° Wide Angle 1mA Meters

MW 1-6 60mm square \$2.97
MW 1-8 80mm square \$4.97
P. & P. extra

RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current

Input 220/240V AC. Size 185 x 85 x 105mm. \$2.97
P. & P. 25p.

PS. 200 REGULATED P.S.U.

Solid state. Variable output 5-20 volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240 V. A.C. Size 7 1/2" x 5 1/2" x 3 1/2". \$14.97. P. & P. 25p.

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V AC. Size 4" x 5 1/2" x 6 1/2". \$11.97. P. & P. 25p.

230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPM CW; 2 RPH CW; 20 RPM CW; 2 RPH ACW; 30 RPH CW; 50p each Post 12p.

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5v batteries. Complete with all instructions, etc. \$4.50. P. & P. 20 p.

LB3 TRANSISTOR TESTER

Tests ICO and B, PNP / NPN. Operates from 9v battery. Complete with all instructions, etc. \$3.95. P. & P. 20p.

HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station, \$2.97. 3 Station \$5.25, P. & P. 15p.
4 Station \$8.62, P. & P. 17p.

SEND SAE FOR LIST OF SEMI CONDUCTORS & VALVES


G. W. SMITH & CO. (RADIO) LTD.
Also see next three pages

MULTIMETERS for EVERY purpose!




TS60 POCKET MULTIMETER
High-precision at low-cost. Ranges: D.C. 15V, 150V, 1,000V (10,000 opv). A.C. 15V, 150V, 1,000V (1,000 opv). D.C. Current 150mA. Resistance 100k ohms. **£1.85. Post 15p.**

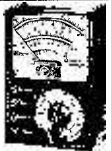MODEL 1092 TESTMETER
5,000 O.P.V.
0/3/15/30/300/1200 V. D.C. 0/6/30/300/600 V. A.C. 0/300/3000 MA
0/10K/1 meg Ω
Decibels -10 to +16db
£2.75 each +15p P. & P.



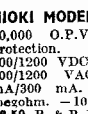
HIOKI MODEL 720X
20,000 O.P.V.
Overload protection
5/25/100/500/1000 VDC.
10/50/250/1000 VAC.
500 μ A/250V. 20K/2 meg ohm. -5 to +62db.
£4.97. P. & P. 15p.



HIOKI MODEL 730X
30,000 O.P.V. Overload protection. 6/30/60/300/600/1200 VDC. 120/120/600/1200 VAC. 60 μ A/300 mA/300 mA. 2K/200K/2 megohm. -10 to +63db.
£6.50. P. & P. 15p.



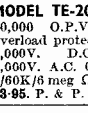
MODEL TE-12
20,000 O.P.V. 0/0.6/6/30/120/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/60 μ A/6/60/600mA. 0/6K/600K/6Meg/60 Meg. 0/50F/0.2mF. **£5.97. P. & P. 17 1/2p.**




MODEL TE-200
20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V. D.C. 0/10/50/250/1,000V. A.C. 0/50 μ A/250 mA. 0/60K/6 meg Ω . -20 to +62db.
£3.95. P. & P. 15p.



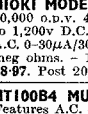
MODEL 500
30,000 O.P.V. with overload protection mirror scale
0/5/2.5/10/25/100/250/500/1,000V. D.C. 0/2.5/10/25/100/250/500/1,000V. A.C. 0/50 μ A/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg/60 Meg Ω .
£8.87. Post paid.



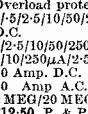HIOKI MODEL 750X
50,000 o.p.v. 43 ranges 0-0.3 to 1,200V D.C. 0-3 to 1,200V A.C. 0-30 μ A/300mA. 0-3K/3 meg ohms. -10 to +17dB.
£8.97. Post 20p.



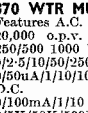HT100B4 MULTI-METER
Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection.
0/5/2.5/10/30/250/500/1000 V. D.C.
0/2.5/10/50/250/1000 V. A.C.
0/10/250 μ A/2.5/25/250 MA/10 Amp. D.C.
10 Amp A.C. 0/20K/200K/2 MEG/20 MEG. 20 +62db.
£12.50. P. & P. 25p.




370 WTR MULTI-METER
Features A.C. current ranges. 20,000 o.p.v. 0/5/2.5/10/50/250/500 1000 V. D.C. 0/2.5/10/50/250/500/1000V A.C. 0/50 μ A/1/10/100mA/1/10 Amp D.C.
0/100mA/1/10 Amp A.C.
0/5K/50K/500K/5 MEG/50 MEG. -20 +62db.
£15. P. & P. 25p.



RUSSIAN 22 RANGE MULTIMETER
Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V D.C. 2.5/10/50/250/500/1000V A.C. DC Current 100mA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3m Ω . Complete with batteries, test leads, instructions and sturdy steel carrying case.
OUR PRICE £5.97. P. & P. 25p

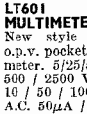
ROUND SCALE TYPE PENCIL TESTER MODEL T.S.68
Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V AC and DC to 2,000 o.p.v. Resistance 0-20K ohms. ONLY **£1.97 P. & P. 13p.**



LT601 MULTIMETER
New style 20,000 o.p.v. pocket multimeter. 5/25/50/250/500/2500 V. D.C. 10/50/100/500/1000V. A.C. 50 μ A/250mA. 6K/6 meg ohms. -20 to +22 dB.
£2.57. Post 20p.



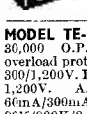MODEL TH-12
20,000 o.p.v. Overload protection. Slide switch selector 0/25/2.5/10/50/250/1000V. D.C. 0/10/50/250/1000V. A.C. 0/50 μ A/25/250mA. D.C. 0/3K/30K/300K/3 meg -20 to +50dB
£4.97. Post 15p.



MODEL TE-300
30,000 O.P.V. Mirror scale, overload protection 0/6/3/15/60/300/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30 μ A/6mA/6mA/300mA/600mA. 0/8K/8K/800K/8 meg. ohm -20 to +63 db. **£5.97. P. & P. 15p.**




MODEL PL436
20k Ω /Volt D.C. 8k Ω /Volt A.C. Mirror scale. 50K/Volt. D.C. 5K/Volt A.C. D.C.: Volts 125, 25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50 μ A, 2.5, 5, 10, 25, 50, 250, 500mA. 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω . Decibels: -20 to +81.5db
£6.97. P. & P. 12 1/2p.




TMK MODEL TW-50K
48 ranges, mirror scale, 50K/Volt. D.C. 5K/Volt A.C. D.C.: Volts 125, 25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50 μ A, 2.5, 5, 10, 25, 50, 250, 500mA. 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω . Decibels: -20 to +81.5db
£8.50. P. & P. 17 1/2p.



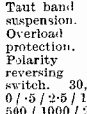
MODEL K228A
Tape band suspension. Overload protection. Polarity reversing
20,000 o.p.v.
0/1.5/2.5/15/50/250/500/1000/2500V. D.C. 0/15/50/150/500/1000V. A.C. 0/50 μ A/5/50/500mA/5A D.C. 0/3K/300K/3 meg. **£8.95. Post 20p.**



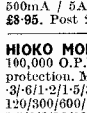HIOKO MODEL 700X
10,000 O.P.V. Overload protection. Mirror scale.
3/6/11/21/5/3/6/12/30/60/120/300/600/1200V DC
1.5/3/6/12/30/60/150/300/600/1200 V. A.C.
6/15/30A/3/6/30/60/150/300mA
16/2 AMP. DC. 2K/200K/2 Meg/20 Meg ohm -20 to +63db. **£13.60. P. & P. 20p.**



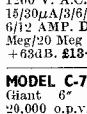MODEL C-7080 EN
Giant 6" mirror scale. 20,000 o.p.v. 0/2.5/10/50/250/500/1000V. D.C. 0/2.5/10/50/250/500/1000V. A.C. 0/50 μ A/1/10/100/500mA/10 amp. D.C. 0/2K/200K/20 meg -20 to +50 dB.
£13.95. Post 35p.



U4312 MULTIMETER
Extremely sturdy instrument for general electrical use. 607 o.p.v.
0/5/15/7.5/30/60/150/300/600/900 VDC and 75mV.
0/3/1.5/7.5/30/60/150/300/600/900 VAC.
0/300 μ A/1.5/6/15/60/150/600mA/1.5/6 AMP. D.C.
0/1.5/6/15/60/150/600mA/1.5/6 AMP. A.C.
Accuracy DC 1%. AC 1.5%.
Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9.50 plus P. & P. 25p.**

Selected TEST EQUIPMENT

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and IGO, NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. **£7.50. Post 20p.**



TE-16A TRANSISTORISED SIGNAL GENERATOR

5 ranges 400Hz-30mHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. **£7.97. Post 25p.**




Model S-100TR MULTIMETER TRANSISTOR TESTER

100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V DC 0/6/50/120/600 V AC 0/12/600 μ A/12/300mA/12 AMP DC. 0/10 K/1 MEG/100MEG. -20 to +50db. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. **£13.50. P/P 25p.**



TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

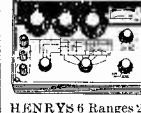A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω - 11.1 meg. 6 Ranges \pm 1% L1 μ H - 111 HEN RYS 6 Ranges 2% = C. 10pF \pm 110mF 6 Ranges \pm 2%. TURN S. 1:1/1000. Operates on 9V battery. At 1,000 cps. Operated from 9 volts. 100 μ A. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2 in. **£20. P. & P. 25p.**



MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta in / out. Checks Ico. Checks diodes in / out. Checks SCR, etc. Beta HI 10 - 500. LO 2 - 50. Ico 0 - 5000 μ A. 220/240 V A.C. operation **£17.50. Post 25p.**



MODEL TE 15 GRID DIP METER

Transistorised. Operates a Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440Kc/s-280Mc/s in 6 coils. 500 μ A Meter. 9V battery operation. Size 180 x 40mm. **£12.50. Post 20p.**



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Size 18 x 200.0mm. Square 18 x 50.0mm. Hz 0-1000. Output max. +10 dB. (10 K ohms) Operation in internal batteries. Attractive 2-tone case 7 1/2 x 5" x 2". Price **£17.50. Carr. 17p.**



TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. Attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions **£15. Carr. 37p.** Size 140 x 215 x 170 mm.



MODEL L-55 FET V.O.M.

Input impedance 10 meg ohms. 0/3/1/2/6/30/120/600V. D.C. 0/3/12/60/120/600V. A.C. 0/120 μ A/120mA D.C. 0/1K/100K/10 meg/100 meg ohms **£15.97. Post 15p.**



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz VRMS/500KHz. Preset triggered sweep 1-3,000usec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V. AC operation. **£39.00. Carr. paid.**



TO-3 PORTABLE OSCILLOSCOPE

3in. tube, V amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25F X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps 300 kHz. Synchronization. Interval external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2lb. 220/240V. A.C. Supplied brand new with handbook. **£40.00. Carr. 50p.**



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mcs/Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in. x 4in. C.R.T. Calibrated triggered sweep from 2 usec. to 100 millisees. per cm. Free running time base 50 cfs-1 mcs. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual **£37. Carr. Paid.**




MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-111db. 0.1db step. Impedance 600 ohms. Max. input power 30dbm. Size 180 x 90 x 55mm. **£12.50. Post 37p.**



TE-65 VALVE VOLTMETER

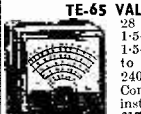28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 100 megohms. 200/240V. A.C. operation. Complete with probe and instructions. **£17.50. P. & P. 30p.** Additional probes available: R.F. **£2.12**; H.V. **£2.50.**



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER


Sensitivity 330 ohms/Volt AC and 1% AC. Accuracy 5% D.C. 1% AC. Scale length 165mm. 0/300/750 μ A/1.5/3/7.5/15/30/75/150/300/750 μ A/1.5/3/7.5/15/30/75/150/300/750V DC 0/3/7.5/15/30/75/150/300/750V AC. Automatic cut out. Supplied complete with test leads, manual and test certificates. **£49.00. Post 50p.**



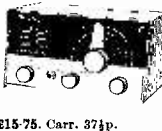G. W. SMITH & CO (RADIO) LTD.
Also see opposite page and next two pages

UNR-30 RECEIVER

4 Bands covering 550 Kc/s - 30 Mc/s. B.F.O. Built-in Speaker 220/240v A.C. Brand new with instructions. £15-75. Carr. 37½p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550 Kc/s-30 Mc/s. FET 8 Meter. Variable BFO for SSB, Built-in Speaker, Bandsread, Sensitivity Control. 220/240v A.C. or 12v. D.C. 12½" x 4½" x 7". Brand new with instructions. £25. Carr. 37½p.

SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 KHz and -55 to 30 MHz. Illuminated slide rule dial. Bandsread. Aerial tuning BFO, AVC, ANL, 'S' meter. AM/CW/SSB. Integrated speaker and phone socket. Operation 220/240v AC or 12v DC. Size 325 x 206 x 150 mm. Complete with instructions and circuit. £28-50. Carr. 50p.

LAFAYETTE HA-600 SOLID STATE RECEIVER



General coverage 150-400Kc/s. 550 Kc/s-30Mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter. S. Meter, Bandsread, RF Gain. 15" x 9½" x 8½". 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £50. Carr. 50p.




TRIO 9R59DS COMMUNICATION RECEIVER

4 band covering 550Kc/s to 30 Mc/s. continuous and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW, ANL, Variable BFO, S meter, Sep. bandspread dial. IF frequency 455 Kc/s, audio output 1.5w. Variable RF and AF gain controls 115/250v. A.C. Size: 7" x 13" x 10" with instruction manual. £49-50. Carr. Paid.



EMI LOUSPEAKERS
Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 37p.
Model 450. 13" x 8" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £8-82 each. P. & P. 25p.

HONEYWELL DIGITAL VOLTMETER VT.100

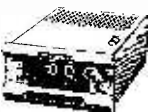

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt. current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1-999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100v. D.C. Input: Fully floating (3 poles). Input power: 110-230v. A.C. 50/60 cycles. Overall size: 5½in. x 2.13in. x 8 3/16in. AVAILABLE BRAND NEW AND FULLY GUARANTEED. £35-50. Carr. 50p.

SINCLAIR IC-12

OUR PRICE £1-80
P. & P. 10p

SINCLAIR EQUIPMENT

Project 60 Package offers.
2 x Z30 amplifier, stereo 60 pre-amp, PZ6 power supply. £15-95 Carr. 37½p. Or with PZ6 power supply £18-00 Carr. 37½p. 2 x Z30 amplifier, stereo 60 pre-amp, PZ8 power supply. £20-25 Carr. 37½p.
Transformer for PZ8. £2-97½ extra.
Add to any of the above £4-45 for active filter unit and £13-00 for pair of Q16 speakers. All other Sinclair products in stock.
2000 Amp £21-95 Carr. 37½p.; 3000 Amp £28-50 Carr. 37½p.; Neoteric Amp £43-95. Carr. 37½p. IC12 £1-80 p. & p. 10p.
NEW PROJECT 605 — £20-97. Carr. 37½p.

SPECIAL OFFER! GOODMANS AXIOM 301

Hi Fi 12" 20 watt twin cone full range speaker. 30-16,000 Hz. 16,500 gauss. 8 ohm impedance. Brand new and boxed. (List price £21-72) OUR PRICE £12-50 each. Carr. 50p.

EA.41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7½ x 3 x 4½in. £5-97. P. & P. 15p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 14½" x 9" x 7½". 8 ohms. 8 watt RMS. 16 watt peak. Complete with DIN lead. £12-95 pr. Carr. 50p.

HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5MU/100MU. Output 50MW. £5-97. P. & P. 15p.

SPECIAL PURCHASE! NEAT G30J STATIC BALANCE PICK-UP ARMS



Identical specification to NEAT G30 arm but with two-tone chrome and black finish. Complete with head shell, pick up rest and plug in phono leads.

BRAND NEW—FULLY GUARANTEED ONLY £8-95. P. & P. 25p.

ARF-300 AF/RF Signal Generator

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10v. P-P. RF 100KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. AC. Complete with instructions and leads. £29-95. Post 50p.

AKAI BARGAINS

SUPER MONEY SAVING OFFERS—BUY NOW WHILE STOCKS LAST! BRAND NEW AND FULLY GUARANTEED

1721 Tape Rec. £73-95
X5000 Tape Rec. £99-95
GX365 Tape Rec. £37-00
4000D Tape Deck £61-50
4000DS Tape Deck £73-95
X200D Tape Deck £99-95
X200E Tape Deck £184-95
GX280D Tape Deck £249-40
X1300SJ Tape/8 track Rec. £101-95
X2000SD Tape/Cas/8 Rec. £223-30
CR81 8 track Rec. £85-95
CR81D 8 track Rec. £118-90
CR81T 8 track/Receiver £145-00
CR80S 8 track system £79-00
CR85 Cassette Rec. £74-95
CR85D Cassette Deck

GXC40 Cassette Rec. £75-25
GXC40D Cassette Deck £75-95
GXC40T Cassette/Receiver £83-95
GXC45D Cassette Deck £95-95
GXC46D Cassette Deck £103-50
GXC60D Cassette Deck £111-25
GXC65D Cassette Deck £110-25
CS83D Cassette Deck £59-50
AA6200 Receiver £74-95
AA6300 Receiver £58-50
AA6900 Receiver £109-00
AA8500 Receiver £175-00
ADM11 Microphones (Pair) £7-50


Carriage 50p extra. (Recorders & Decks 75p)

DOLBY SYSTEM NOISE REDUCTION UNIT




Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 15kHz ± 1dB 19kHz ± 35dB. Size 15½" x 9" x 3½". AC 200/250V. OUR PRICE £32-50 Carr. 50p.

1021 STEREO LISTENING STATION

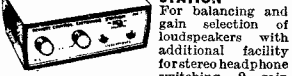

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2½". £2-25. P. & P. 15p.

MP7 MIXER PREAMPLIFIER

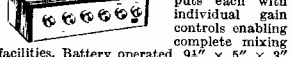


5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9½" x 5" x 3" Inputs Mic: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8-97. P. & P. 20p.

TE-1035 STEREO HEADPHONES



Low cost high performance stereo headphones. Foam rubber ear cups Adjustable head-band. 8 ohm impedance 25-15,000 Hz. With lead and stereo jack plug. ONLY £1-97½. P. & P. 12½p.

NEW GARRARD MODULES

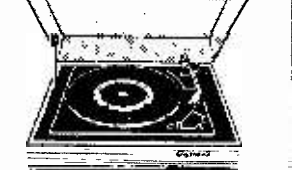

Popular range of Garrard decks with Shure cartridge fitted in deluxe plinth with hinged lid.
SP25 III Module/M75-6 £23-50
AP76 Module/M75-6 £33-80
AP96 Module/M75-6 £38-75
Zero 100S Module/M93E £52-60
Carr. 50p extra any item.

HOSIDEN DH-08S DE-LUXE STEREO HEADPHONES




Features unique mechanical 2 way units and fitted adjustable lever, controls on 8 ohm impedance 20-20,000cps. Complete with spring lead & stereo jack plug £7-97½. P. & P. 12½p.

GENUINE BARGAIN! KOSS SP.3XC STEREO HEADPHONES



Response 10-16,000Hz. Impedance 4-8 ohms. Brand new, boxed & fully guaranteed (List £9.50). OUR PRICE £6-50. P. & P. 25p.

HOSIDEN DH-02S STEREO HEADPHONES

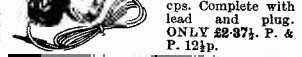


Wonderful value and excellent performance combined. Adjustable head-band. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug. ONLY £2-37½. P. & P. 12½p.

TAPE CASSETTES



Top quality Hi-Fi Low Noise in Library cases.
C50 3 for 75p. 10 for £2-25
C50 3 for £1-95 10 for £3-30
C120 8 for £1-35 10 for £4-20
Tape Head Cleaner 80p each. P. & P. 10p extra.

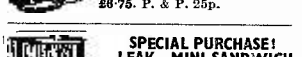SPECIAL OFFER! ROTEL RH700 STEREO HEADPHONES




20-20,000Hz. 8-16 ohm. (List £9-95). OUR PRICE £8-75. P. & P. 25p.

SPECIAL PURCHASE! LEAK MINI-SANDWICH SPEAKERS



Brand new and fully guaranteed. 8 watts, 8 ohm. Teak finish. (Rec. List £59-50 pr.) OUR PRICE £39-50 pair. Carr. 21-00.

TRANSISTORISED FM TUNER

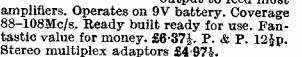

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2½in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6-37½. P. & P. 12½p. Stereo multiplex adaptors £4-97½.

TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £7-97. P. & P. 15p.

G. W. SMITH & CO (RADIO) LTD. Also see previous pages and opposite page

SOUND BARGAINS



GIANT POWER MULTI-WAVEBAND BROADCAST RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE £10.50
+40p P. & P.

No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating

Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas PLUS A SPECIAL

WEATHER-BAND. Frequency ranges: MW340-1600 KHZ, FM88-108MHZ, Airband 108-145 MHZ, VHF 145-175MHZ, 23 semi-conductors—12 transistors, 11 diodes and thermistors. Automatic frequency control. 31" telescopic aerial. Runs off mains AC 230/250 volts or off 4 U11 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10" x 6" x 3". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries FREE. HURRY! Limited quantity Fully guaranteed.

BATTERY CHECK INDICATOR

OUR PRICE £28.95
+50p P. & P.



Tune into the world with this amazing world radio. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable

with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial.

Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350Kcs. Medium 353-1605Kcs.

Marine 1.6-4.5Mcs. Short Wave 12-24Mus.

FM/VHF 88-108Mcs. Aircraft 108-136 Mcs.

PUBLIC SERVICE BANDS 135-174Mcs. Fully guaranteed.


8 WAVEBANDS AND WORLD MAP & TIME ZONE DIAL

N.B. - The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

SONIC SOUND AUDIO LTD.

(Dept. PW9), 272 EDGWARE ROAD, LONDON, W.2. Tel. 01-723 0094. Callers welcome Monday to Saturday 9 a.m.-6 p.m.

COLBERT WORK POSITIONERS - 300 SERIES

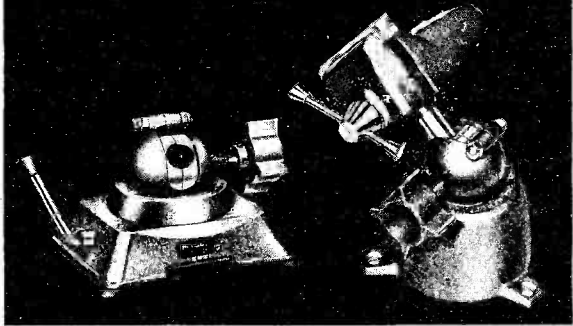

Colbert Pana-Vise WORK POSITIONERS are specially designed to quickly and easily achieve the most CONVENIENT, COMFORTABLE and TIME-SAVING work position. The required work position is firmly secured with a patented ONE KNOB CONTROL, a unique feature of COLBERT POSITIONERS.

Available with vacuum clamp or screw-on base. They can be ROTATED, TIPPED, TILTED, ANGLED, ELEVATED, LOWERED. A series of special holders is available for various types of work.

Full details available on request.

Distributors:

SPECIAL PRODUCTS DISTRIBUTORS LTD.

81 PICCADILLY, LONDON, W.1. Tel. 01-628 9556

Cables: SPECIPROD LONDON

(made in U.S.A.)

FERRANTI

ZN414 MICROCIRCUIT RADIO

AS SEEN ON TV! Only £1.20

WITH FREE DATA

Post & Packing 5p.

WE ARE SPECIALISTS IN FERRANTI SEMI-CONDUCTORS

BFSS9	13p	ZTX310	8p	ZTX504	39p	ZS170	9p
BFS60	18p	ZTX311	9p	ZTX510	15p	ZS171	11p
BFS61	18p	ZTX312	9p	ZTX530	19p	ZS172	14p
BFS96	13p	ZTX313	10p	ZTX531	20p	ZS174	15p
BFS97	21p	ZTX314	11p	ZTX550	15p	ZS176	21p
BFS98	18p	ZTX320	28p	ZTX551	15p	ZS178	34p
ZTX107	8p	ZTX330	13p	2N3055	65p	ZS270	10p
ZTX108	7p	ZTX331	14p			ZS271	14p
ZTX109	10p	ZTX382	11p	DIODES		ZS272	16p
ZTX212	12p	ZTX383	13p	ZS120	7p	ZS274	17p
ZTX213	12p	ZTX384	16p	ZS121	9p	ZS276	23p
ZTX214	13p	ZTX450	15p	ZS122	11p	ZS278	33p
ZTX300	10p	ZTX451	15p	ZS123	14p		
ZTX301	11p	ZTX500	10p	ZS124	16p	ZENERS	
ZTX302	15p	ZTX501	11p	ZS140	22p	KS030A to	
ZTX303	12p	ZTX502	15p	ZS141	39p	KS180A—	
ZTX304	19p	ZTX503	12p	ZS142	30p	all types 17p	

ALL DEVICES TOP GRADE, BRAND NEW, AND FULLY GUARANTEED

WE CAN SUPPLY ANY FERRANTI DEVICE. Send SAE for quotation.

POSTAGE AND PACKING 10p. FREE over £2.00. Send SAE for our full price list and data sheet.

BUY NOW AND BEAT V.A.T.! ALL PRICES MUST RISE ON APRIL 1st.

DAVIAN ELECTRONICS

PO BOX 38, OLDHAM, LANCs. OL2 6XJ

TEXAN 20+20 WATT. STEREO AMPLIFIER

Electro Spares can now supply all the components to build the "Texan" Amplifier, featured in *Practical Wireless* May/June 1972. All components are brand new with fibre glass p.c. board, all metalwork, knobs, finished silver trim front panel, etc. etc.

TOTAL COST OF COMPLETE COMPONENTS ONLY £27.85—POST FREE!

All components are available separately, to enable the constructor to obtain just what parts he requires at any one time. Please send S.A.E. for free list.

SPECIAL CONTEMPORARY STYLE SLIMLINE METAL CASE WITH WOODEN END CHEEKS IS NOW AVAILABLE FOR THIS AMPLIFIER—DETAILS INCLUDED WITH ALL LISTS, OR AVAILABLE ON RECEIPT OF S.A.E.

P. E. 'GEMINI' STEREO AMPLIFIER

30 Watts (R.M.S.) per Channel into 8 Ohms !!

Total Harmonic Distortion 0.02% !!

Frequency Response (-3 dB) 20Hz-100kHz !!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but it is well within the capabilities of the ambitious constructor.

We can now supply a reprint of the articles in booklet form, price 55p plus 4p postage, with free complete component price list.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.

All parts available separately.



ELECTRO SPARES

21 BROOKSIDE BAR, CHESTERFIELD, DERBYSHIRE. QUALITY • SERVICE • VALUE

Why take the risk?

of damage to expensive transistors and integrated circuits, when soldering?

Use Antex low-leakage soldering irons



220-240 Volts or
100-120 Volts

Model X25

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".

Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8".
2 other bits available 3/32" and 3/16".

Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be re-ved

PRICE: £1.75 (rec. retail)
Suitable for production work and as a general purpose iron

Model CCN 220 volts or 240 volts

The 15 watt miniature model CCN. also has negligible leakage.

Test voltage 4000v. A.C.

Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"

4 other bits available
1/8", 3/16" 1/4" and 1/16"

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8"

PRICE: £1.95 (rec. retail)

A SELECTION OF OTHER SOLDERING EQUIPMENT.



MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24
PRICE: £1.70 (rec. retail)

MODEL CN2


Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.
PRICE: £1.70 (rec. retail)



MODEL G

18 Watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.
PRICE: £1.83 (rec. retail)

MODEL SK.1 KIT

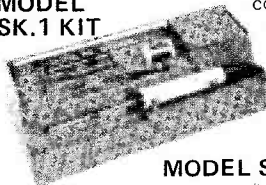

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £2.75
(Rec. retail)

MODEL SK.2 KIT

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder and booklet "How to Solder"



PRICE £2.40
(Rec. retail)

MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder."

PRICE £1.95
(Rec. Retail)



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from:—
ANTEX LTD. FREEPOST
(no stamp required) **Plymouth**
PL1 1BR Tel: 0752 67377

- Please send the ANTEX colour catalogue.
 Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME _____

ADDRESS _____

PW/2

EXCLUSIVE STEREO SYSTEM

LASKYS Super New Year Offer

Laskys bring the pleasure of real stereo to you for the New Year at a bargain price - with the exclusive RIGONDA "Electroacoustic" stereo system. This tremendous quality system comprises two RIGONDA combined amplifier/speaker units (each containing bass and treble speakers) housed in handsome teak veneer cabinets, with brushed aluminium grille panel. All controls including bass, treble, and volume together with input sockets etc., are neatly inset at side of cabinet. The system is completed by an attractive B.S.R. 4 speed Auto-record changer with cartridge and sapphire stylus, styrene plinth and tinted cover. The RIGONDA Stereo system will bring all the magic of stereo to your home with rich tone and ample six watts (max each unit) output power. Size - each RIGONDA: 23 x 10 1/2 x 9 1/2 in. Player size: 13 1/2 x 8 x 5 1/2 in. All units AC mains operated. RIGONDA units may also be used singly to provide enhanced sound and power from Transistor Radio sets, mono tape recs. and record players with suitable output. 9V DC output provided to power radio or cassette recorder. Complete with all leads etc. Fully guaranteed. DEFINITELY THE STEREO BARGAIN OF THE YEAR
ORIGINAL LIST VALUE OF THE SYSTEM AS OFFERED OVER £46.00!
COMPLETE STEREO SYSTEM - NO EXTRAS



LASKYS SUPER
NEW YEAR
OFFER PRICE

ONLY £29.75

C & P
£1.25.

RIGONDA units are available separately for use with existing equipment or any record player of your choice £11.50 each - C & P 50p or £22.00 per pair - C & P 85p.

See Laskys full page advertisement for addresses.

4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. £0.40.

MAINS INTERCOM

No batteries - no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £12.40 P. & P. £0.55

INTERCOM/BABY ALARM



OUR
PRICE
ONLY
£3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 14p. P. & P. £0.25.

Transistor TELEPHONE AMPLIFIER



£2.99

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p. extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.S)
169 KENSINGTON HIGH STREET, LONDON, W.3.

B.H. COMPONENT FACTORS LIMITED

MULLARD POLYESTER C280 250V. (μ F) 0-01, 0-015, 0-022, 0-033, 0-047, 8p, 0-068, 0-1, 0-15, 4p, 0-22, 5p, 0-33, 7p, 0-47, 8p, 0-68, 10p, 1-0, 13p, 1-5, 20p, 2-2, 25p.
MULLARD POLYESTER C296: 160V. (μ F) 0-01, 0-015, 0-022, 2p, 0-047, 0-068, 3p, 0-16, 0-22, 3p, 0-33, 5p, 0-47, 8p, 0-68, 1-0, 10p, 300V. (μ F) 0-001, 0-0015, 0-0022, 0-0033, 0-01, 2p, 0-015, 0-033, 3p.
MULLARD ELECTROLYTIC C426. 5p. each. (μ F/V) 0-64/64, 1-6/25, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/8-4, 125/16, 125/10.
MULLARD C437: 84/64, 160/25, 640/6-4, 8p, 160/40, 11p, 1600/6-4, 14p.
LARGE ELECTROLYTIC: 600/25, 10p, 500/60, 12p, 1000/12, 10p, 1000/25, 2000/12, 2500/12, 15p, 1000/60, 35p, 3000/25, 25p, 2500/25, 30p, 3000/50, 65p, 6000/50, 35p, 2500/50, 55p.
CERAMIC PLATE. 750V (pF) 5, 10, 25, 40, 70, 220, 22p. (μ F/V) 0-0047/30, 0-01/350, 21p, 0-047/30, 3p, 0-1/30, 4p, 0-1/100, 5p, 22pF 0-01/4F, 50V, 2p. (E12 series up to 1,000pF E6, above).
CARBON FILM RESISTORS. \pm W. 5% 10ohms-2.2M 1p, each, or 100 for 55p.
SPECIAL RESISTOR KITS (\pm W 5% Carbon Film) 10E12KIT. 10 each E12 value, 10ohms-1M A total of 610. £2-30 net 25E12KIT. 25 each E12 value, 10ohms-1M A total of 1525. £6-50 net

VEROBOARD 0-1 0-15 **CARBON POTS**
2 1/2" x 6" 25p 5K-2M Log and Lin
2 1/2" x 3 1/2" 25p 17p single 15p, single
3 1/2" x 5" 25p 30p with SW. 24p, dual
3 1/2" x 3 1/2" 25p 5p 42p.
Pins, Pkt. 25 8p **SCREENED WIRE**
2 Pin DIN Plug 12p, Skt. 10p Single 5p/yd., twin
3 Pin DIN Plug 13p, Skt. 10p, stereo 1p, quad 1p
5 Pin DIN Plug 18p 15p, Skt. 12p, 15p
Red Panel Neon 240v. 15p
RF Chokes (μ H) 0-22, 2-2, 12, 22 8p
PVC Wire 7/0076, 5 x 10 yds. 30p
PVC Wire 14/0076, 5 x 10 yds. 30p
Neon Bulb 50V, wire ended 5 for 200
Mtn. Push button, push to make 10p
Mains Transformer 32-0-32 at 150mA 15p
1N4001, 8p, 1N4002, 7p, 1N4003, 8p, 1N4004, 8p
1N914, 8p, 7400N, 15p, 7401-7410-7430, 15p
2N706, 10p, μ L914, 30p, BC108, 11p, BFY51, 20p
CWO, pp 10p. Discount £10-10%. The above items are only a few taken from our catalogue which is available free. Money back refund.
Dept. PW, 61 CHEDDINGTON RD., PITSTONE
LEIGHTON BUZZARD, BEDS., LU7 9AQ.
Tel.: Cheddington 668446 (STD Code 0296)

SINCLAIR EQUIPMENT


IC12 £2.00
Z50 £4.25
PZ5 £3.97
Z30 £3.50
Project 60
tuner £16.80
AFU £4.50




Stereo 60 £7.80
Project 60S £19.00

S-DECS AND T-DECS

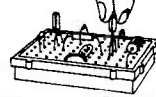S-DECS £1.40
T-DECS £2.80
 μ DEC A £3.00
16 dit IC
carriers £1.25



SINCLAIR EXECUTIVE CALCULATOR

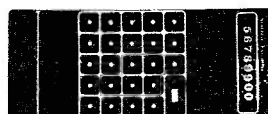

Weights only 2.4oz. Fits the pocket. Runs for 3 months average use on one set of tiny hearing aid batteries. Contains 7000 transistors. Brilliant 8 digit display. Adds, subtracts, multiplies and divides. Constant multiplier facility. Floating point or fixed point with 2, 4 or 6 decimal places. Subject to manufacturer's complete 5 year guarantee. Comprehensive after sales back up is supplied by Sinclair's famous service dept. If any Executive purchased from us fails to give satisfaction and is returned undamaged in 10 days we undertake to refund the whole purchase price.

SAVE £10.
OUR PRICE ONLY £69 (List Price £79).

SWANLEY ELECTRONICS 32 Goldsel Road, Swanley, Kent

Mail order only. Postage 10p per item.
Our Hi-Fi colour catalogue is 10p post free.
Official credit orders welcome.

1 R.P.M. MOTOR

Smiths. 240V 50 cycle mains working. Ideal motor to drive clock mechanisms. Price £1 each or 10 for £9.

3 PIN PLUG AND SOCKET

Our Ref. No. P801. Flat pins American style rated at 10A 250V. Socket panel mounting. Plug is white and intended for flex. Useful where non standard power outlet is required. Also suitable for speaker leads, etc. etc. Price 25p per pair.

THERMOSTAT WITH PROBE

Our Ref. No. TH01. Made by Ranco. Range 0-107°C 15A 250v switch. Joined to a 10" probe by approx. 40" of capillary tubing. 1 hole fixing. Normal control spindle 85p each.

PUSH SWITCH

Our Ref. No. 804. This is fitted to table lamps etc. Superior quality and reliable (Leviton). Conservatively rated 1A 250v. Has 2 flex leads attached measuring 40" and 12" each respectively. Price 10p each.

INDUCTION MOTOR

Made by G.E.C. Normal type with approx. 1" of 3/8 spindle. Standard fixing 1" stack. Brand new 65p each less usual quantity discounts. Good stocks available.

MINIATURE ROCKER SWITCH

Our Ref. RS01. 10amp 240v. Self-fixing into hole size approx. 1" x 3" by famous push down the letters maker Russenburgh. Price 10p each.



ROCKER SWITCH

Our Ref. R802. 15amp self-fixing into hole approx. 1" x 4". Made by the Carr Fastener Co. Very reliable. Price 8p each.

PHOTO TRANSISTOR

OCPT0—ideal for burglar alarms and similar applications. Price 65p each.

EXIT SIGNS



One of our customers has pointed out how easily our box signs can be converted to exit signs. These are illuminated having a 20w fluorescent lamp with associated control gear. The front is very thick, clear plastic. Directly onto this you can stick down the letters available at most sign makers. There is room inside the box for a battery and low volt lamp in the case of power failure. Size of sign is 2ft high x 14" wide x 5" deep. Solidly made from sheet steel and hammer finished in enamel. Price £3-50 plus 50p carriage per 200 miles.

6 PIN PLUG AND SOCKET

And metal case with flex grip for one end, this can be fitted either to a plug or socket and the other part fitting to the equipment. Price 40p per pair—10 pairs £3-60.

TAPE HEADS

We are gradually obtaining more information about the Traxox tape heads we have, we are told that these have been wound in a very ingenious way so that winding may be coupled either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and now offer these in pairs, 1 record and 1 erase head. Price of the 2 track 45p per pair, 4 track 75p per pair. Pair mounted on plate 45p extra.

REED SWITCH COILS

These are solenoids wound on moulded formers of the correct size and dimensions to take standard reed switches. They have printed circuit board mounting. Six types available:—
RC1 takes 1 reed—Operates 10-15v 600 ohm 30p
RC2 " 2 " " 10-15v 180 ohm 25p
RC3 " 1 " " 18-30v 1K ohm 35p
RC4 " 2 " " 15-30v 300 ohm 45p
RC5 " 1 " " 45-70v 650ohm 35p
RC6 " 2 " " 45-70v 350ohm 40p
Standard reed switches available 10p each or 10 for 90p, 100 for £3-50.

THROAT MICROPHONES

Dynamic type. Made for government contract—many uses: i.e. motorcyclists talking to pillion passengers, etc. Price 30p each. 10 for £2-70.

MUTUAL INDUCTANCE COIL

Laboratory type. M=0.001H. Inductance of coils 0.0022H and 0.0021H. Coil resistance 0.53 ohms and 0.51 ohms respectively. Maximum current through coils=3 amps. Completely encased with 4 screw down terminals. Overall size 6" diameter by 3" deep Price £4 each.


WIRE ENDED FUSES

Useful where you want a quick solder in fuse. Rated 2A 250v. These are about the size of a resistor. Price 5p each.

BAKELITE INSTRUMENT CASE



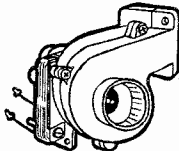Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price 45p each.



CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods, powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size of blower is approx. 4 1/2" x 4 1/2". When mounted by its flange air is blown into the equipment but to suck air out cooling the centre using a clamp, ideal for mounting electrical equipment, or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc. etc. A real bargain at £1-85.

MULLARD I.F. MODULE

This is a fully screened intermediate frequency module for amplification and detection of f.m. signals at 10.7MHz and a.m. signals at 470kHz. The first stage is used as an i.f. amplifier for f.m. and a self oscillating mixer for a.m. operation, in conjunction with an external oscillator coil. 85p each. 10 for £7-85. 100 for £62-50p. With connection dig.



TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal lined case or cabinet.

Only need control switch, £3-50. 2kW Model as above except 2 kilowatts, £2-50. Don't miss this. Control Switch, 45p. P. & P. 45p.

ELECTRIC TIME SWITCH

Made by Smiths these are A.C. mains operated. NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket, 2 completely adjustable time periods per 24 hours, 5 amp change-over contacts will switch circuit on or off during these periods £2-50 post and ins., 23p. Additional time contacts 50p pair



COMPUTER TAPE

2,400ft of the Best Magnetic Tape machine can buy—users claim good results with Video and sound. 1in wide £1-00 plus 33p post and insurance with cassette. 1/2in wide £1-00 plus 30p post and insurance with cassette. 1/4in wide 85p plus 25p post and insurance with cassette. Spare spools and cassettes—1in 75p, 1/2in 75p each plus 20p post and insurance.



THIS MONTH'S SNIP

MULLARD 4 WATT AMPLIFIER EP 9000

Suitable for mono or stereo systems. It's output approx. 4w. speech or music into a 12-15 ohm speaker. Power requirements 24 volts 10 watts. Harmonic distortion at typical listening level is less than 2%. Frequency response at typical listening level 50hz to 16khz. Totally enclosed in moulded case size 3 1/2" x 2 1/2" x 1 1/2" with screw terminal connections. A fantastic bargain at only £1-45 while stocks last. Don't miss this—it's one of our best bargains ever. FREE to all who purchase we give a copy of the Mullard Booklet "Do it yourself stereo" telling all you need to know about building your own stereo system.


HORSTMANN "TIME AND SET" SWITCH

(A 30 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special price £1-50, p. & ins. 23p.



HONEYWELL THERMOSTAT

Made by Honeywell for normal air temperatures 40°-50°F (5-25°C). This is a precision instrument with a differential which can be adjusted to better than 1/2°F. A mercury switch breaks on temp. rise—the switch is operated by a coiled bi-metal element and adjustable heater is incorporated for heat anticipation. Elegantly styled and encased in an ivory plastic case with clear plastic windows thermometer above and 1 1/2" x 1 1/2" mercury switch below—1 1/4" deep—can be mounted on conduit box or directly on wall. Price £1-25 each or ten for £11-25.

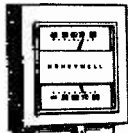


PAPST MOTORS

Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. £1-50 each. Postage one 23p, two 33p. 230v model £3.



RADIO STETHOSCOPE

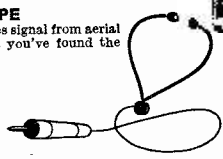Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2—twin stetho set instead of earpiece 75p extra post and ins. 20p.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work, £2-25 plus 23p P. & I



DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-50 plus 13p post and insurance. Made up model also available, £2-25 plus 13p post & p.

MIGHTY MIDGET

as featured in January issue £2 complete post paid or send for price list.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

CAR PANEL SWITCH

Our Ref. No. 802. Arco made. Has long flat ended toggle, black and chrome finish. Rated 2A at 250v and is double pole on/off. Listed at 45p. Our price £2p each.



CAR PANEL AUTO SWITCH

Ref. No. 803. Again a flat ended toggle. Made by Arrow. A 3 position double pole changeover switch, centre off for auto aeriels, reversing motors etc. 30p each.

3 PIN REVERSE PLUG & SOCKET

Our Ref. P802. For bringing live leads to equipment. All brown bakelite construction, rated 10A 250v. Price 35p per pair.

13 AMP JUNCTION BOXES

Made to take 7029 cables so ideal for ring mains. Price 8p each or 10 for 72p.

PORCELAIN FUSE AND CARRIER

20A 250v. MEM Ref. No. 15LBB/15LRHW. Make your own fuse board. Price 20p per pair.



AUTO TRANSFORMER

Primary 220-240V. Secondary 110-120V. Well built and varnish impregnated. 250 watt intermittent rating. 150w continuous rating. Size approx. 3 1/2" x 3" x 3". £1 plus 20p post and insurance.



SPIT MOTOR

200-250v Induction Motor, driving a carter gear box with 1 1/2" of output drive shaft running at 5 revs per minute. Intended for roasting chickens—windmill, coloured disc lighting effect, etc. etc. £1-85 plus 20p post and insurance.



PANEL NEON INDICATOR

Our Ref. No. P101. Oblong type self-fixing into oblong hole. Suitable for 200/250v. Price 15p each.



30KV EHT UNIT

This unit is self-contained and on wheels. It stands approx. 6ft high and 3ft square. On the front panel is a Variac, Voltmeter, a 60 second Timer as well as the normal overload trip on/off switch and cut outs etc. The transformer itself is oil filled and rated at 7 KVA 30KV. The Variac is in the primary so all voltages up to 35KV are available. We believe the normal use for such a unit would be as a breakdown and flash tester. 1 only—not new but in good order. Price £150, carriage extra at cost.

INSTANT START UNITS


For 2ft tubes, Phillip's or Smart & Brown in a tray complete with tube clips and tube ends. Price £1-50 each or 10 for £13-50.

FLOUORESCENT TUBES

Standard types—Bi pin ends, ideal pelmet lighting as well as for standard replacements—18" 15 watt, 24" 40 watt, 36" 40 watt, 39 1/2" 40 watt. All first grade tubes offered at one price—£3-50 per box then please add 50p per box per 200 miles.

DIGITAL DISPLAY

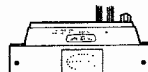Panel mounting unit measuring approx. 3 1/2" x 1 1/2" x 1 1/2" deep. Size of the display aperture is approx. 1 1/2" x 1". Light up to 0-9. Ex equipment but unused and in perfect order. Price £1 each.



DIGITAL SWITCHES

Small type S.T.C. number SW21/630CA. These are a snap in fit hole approx. 1 1/2" x 1". Knob engraved 0-9. Gold plated contacts 1 pole 10 way. Thumb wheel operation. These are designed so that they may be stacked in rows. Price 75p each.

6 DIGIT COUNTER

Operated by 240v A.C. mains through resistor or direct from 115v A.C. or from 80v D.C. Made by Veeder-Root of America. Metal encased for surface mounting. Size approx. 3 1/2" x 2 1/2". Price £1 each. 10 for £9.

COLOURED 13 AMP SOCKETS

Standard Flush mounting available in the following colours: Yellow, Green, Grey and Cream. These are a good quality socket with porcelain interior made by Ward and Goldstone. Useful on control panels. Price 20p each, 10 for £1-90.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

J. BULL (ELECTRICAL) LTD.

(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

R T V C THE

THE FABULOUSLY SUCCESSFUL VISCOUNT III AUDIO £52 complete

14 + 14 watts r.m.s. 40Hz to 40kHz $\pm 3\text{dB}$. Total distortion at 10 watts at 1kHz -0.1%

This is real value for money! We have designed 2 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For both systems we have chosen the famous Garrard SP25 Mk. III deck which comes with fitted magnetic cartridge, simulated teak plinth and tinted acrylic dust cover. The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

SPEAKERS

Duo Type II Size approx. 17in. \times 10 $\frac{1}{2}$ in. \times 6 $\frac{1}{2}$ in. Drive unit 13in. \times 8in. with parasitic tweeter. Max. power 10 watts, 8 ohms. Simulated Teak cabinet. £14 pair + £2 p&p.

Duo Type III Size approx. 23 $\frac{1}{2}$ in. \times 11 $\frac{1}{2}$ in. \times 9 $\frac{1}{2}$ in. Drive unit 13 $\frac{1}{2}$ in. \times 8 $\frac{1}{2}$ in. with H.F. speaker. Max power 20 watts at 8 ohms, Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

SPECIFICATION R101

14 watts per channel into 3 to 4 ohms. (suitable 3-15 ohms). Total distortion @ 10W @ 1kHz 0.1%. P.U.1. (for ceramic cartridges) 150mV into 3 Meg. P.U.2. (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within $\pm 1\text{dB}$ R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal-to-noise ratio:* (all controls at max) -P.U.I. and radio -65dB, P.U.2 -58dB. *Cross talk* better than -35dB on all inputs. *Overload characteristics* better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ \times 9in. \times 3 $\frac{1}{2}$ in.

BRITISH MADE—12 MONTHS WRITTEN GUARANTEE

Send S.A.E. for fully illustrated brochure

-ONLY FROM US

PRICES: SYSTEM 1


Viscount III R101 amplifier	£22-00+90p p&p
2 x Duo Type II speakers	£14-00+£2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23-00+£1-50 p&p
Total	£59-00

Available complete for only £52 + £3-50 p&p

PRICES: SYSTEM 2

Viscount R101 amplifier	£22-00+90p p&p
2 x Duo Type III speakers	£32-00+£3 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23-00+£1-50 p&p
Total	£77-00

Available complete for £69 + £4 p&p

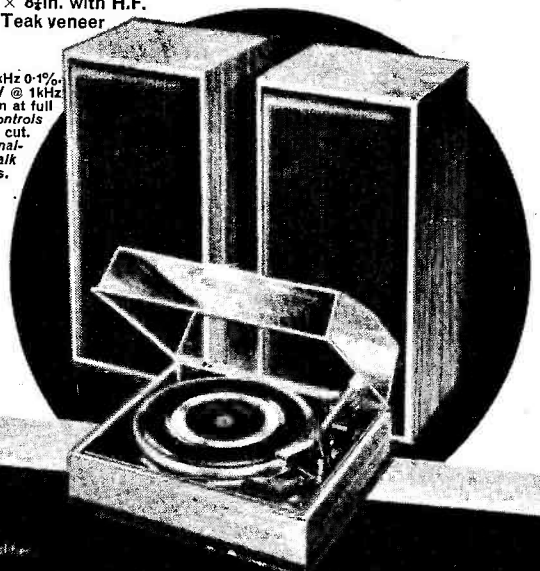

MUSIC MAKERS

UNISOUND FOR THE NEW SOUND


AT £25



The whole system is complete *including superb cabinets in simulated teak*—just simply screw together the components and you save pounds!
 Amplifier is based on the famous Mullard Unilex system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13" x 8" EMI Twin-cone speakers ready for mounting in their elegant cabinets, which simply need screwing and gluing together. All glue and screws supplied.
 Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound.
 £25 complete plus £2.50 p. & p.
 Diamond Stylus £1.25 extra.
 Power output: 4 watts per channel into 8 ohms.
 Inputs: 120 mV (for ceramic cartridges).
 Stereo headphones with adaptor £4.00

UNISOUND MODULES ONLY £6.95

If you prefer, you can buy the three modules—pre-amplifier, power supply/dual power amplifier, and control panel—by themselves for only £6.95. P. & P. 50p extra.
 No soldering, just simply screw together with screwdriver supplied. Their overall specification is the same as shown for the complete Unisound console, using the high efficient I.C. monolithic power chips to ensure very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum.

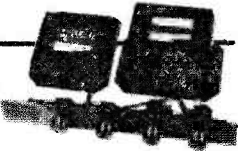

ANRTVC EXCLUSIVE DESIGN S.A.E. for leaflet

A 'NATURAL' ONLY FROM **ANRTVC**

THE PULLMAN PB CAR RADIO KIT

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components, this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. Four push-buttons for medium wave, one for long wave. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohm speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms. Power consumption is less than 1 amp.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale for easy reading at night. Approx. Chassis size is 7in. wide, 2in. high and 4½ in. deep (excluding front panel, etc.).

- ★ Circuit diagram and comprehensive instructions 50p, free with parts.
- ★ Fully retractable, lockable, Car aerial £1.25 post paid.

Price only £7.00 + 50p p&p. 8 ohm speaker with baffle and fixing strips £1.50 post free if bought with kit + 25p p&p.

If you can solder on printed circuit board you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.



S.A.E. for leaflet

RELIANT MK.IV

- ★ 5 Electronically Mixed Inputs. ★ 3 Individual Mixing Controls. ★ Separate bass and treble controls common to all 5 inputs. ★ Mixer employing F.E.T. (Field Effect Transistor). ★ Solid State Circuitry. ★ Attractive Styling. ★ Sides Finished in solid teak

INPUTS:—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram., Tuner, Monitor, Organ, etc.). All 250mV sensitivity. **CONTROLS:**—3 Volume controls. Bass control range: -13dB @ 60Hz. Treble control range ±12dB @ 15KHz. Separate ON/OFF Switch. Neon Indicator. **POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker. **SIGNAL/NOISE:**—Better than -60dB on inputs 3, 4 and 5 & -50dB on 1 & 2. **SUPPLY:**—220-250 AC Mains. **£10.50**
 SIZE:—12½" x 6" x 3½". (VISIT OUR SHOWROOMS) plus p. & p. 60p

JUST ANNOUNCED

The new 20 watt (into 8 ohms) version for just £3 extra. All other specifications as above.

£13.50



Radio and TV Components (Acton) Ltd.
 21C High Street, Acton, London W3 6NG
 323 Edgware Road, London, W2.

Mail orders to Acton. Terms C.W.O. All enquiries S.A.E. Goods not dispatched outside UK.



VISIT OUR SHOWROOMS

ESSENTIAL BOOKS FOR RADIO AMATEURS

New Book
TELEVISION INTERFERENCE MANUAL
by B. Priestley
G3JGO

The causes of interference to TV receivers are examined, and ways in which they can be overcome are suggested in this latest RSGB publication.
90p post paid

1973 AMATEUR RADIO CALL BOOK

The 1973 edition of this invaluable book records over 2,700 amendments and 1,500 new calls notified since the 1972 edition was printed.
70p post paid

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's UK origin ensures easy availability of components. Complete coverage of technical and constructional fields.
£4.10 post paid

AMATEUR RADIO TECHNIQUES

by Pat Hawker, G3VA
Aimed at extending the reader's awareness of new devices and techniques. Provides a source book for many useful circuits and diagrams. 256 pages; 600
£1.80 post paid

These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send s.a.e. for complete list

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



BARGAIN PARCELS 14lb at £1.45 plus 32p p.p.; 28lb at £2.75 plus 52p p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res, Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save ££s. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 09J 4 1/2 in. dia. Length 15in. Also 7BP7 and 5FP7. All unused as new. Price £1.40 post paid.

NEW HEAVY COAX CABLE dia. 3/8" 70 ohms approx. 50ft. lengths £1.40, p. & p. 30p. 100 ft. lengths £2.70, p. & p. 50p.

AERIALS. New Condition Whip Type, 4ft. 20p; 11ft. 75p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 62 1/2 p. & p. 25p.

CRYSTALS AS NEW. Hc 6u, 5.345; 5.030; 4.945; 4.875; 4.840; 4.795; 4.580; 4.660; 4.520; 4.510; 2.300; 2.295 Kc/s. 50p each plus 8p p.p.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2 1/2 in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2 P. & P. 25p. minimum order of six.

ANY HEIGHT AERIAL TUBULAR SECTIONS 3/4" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 20p p. & p. 5p each. Minimum order 6.

AS NEW AERIAL TUNER UNIT No. 6 RF, consisting of 1 1/2 inch 500 micro/ampmeter 3 gang tuner 75 PF geared BNC type socket size 5 1/2" x 4 1/2" x 5". Price £1.50, p. & p. 25p.

HEADPHONES DI. High impedance. Good condition 75p. p. & p. 15p. R209. Set of valves 62 1/2 p. p. 25p.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 75ft. 40p, 90ft 47 1/2 p. 100ft. 55p, p. & p. 20p.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1 each section. Carriage 35p each section. 1/2" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1 + 30p p.p.

SLIDING RESISTORS, 12 amp, 1 ohm. Approx. 9in. long. 1-4 amp., 14 ohms. Approx. 7in. long. As new Ex Eqp. 75p, p.p. 15p.

QUOTATIONS FOR QUANTITY.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY
WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

NEW VALVES ! GUARANTEED AND TESTED

24-HOUR SERVICE

1R5	-25	30FL14	-87	EF89	-27	EF183	-25	PCF80	-25	PY800	-80
186	-21	30L17	-86	ECC81	-15	EF184	-27	PCF86	-44	PY801	-80
1T4	-14	30PL1	-58	ECC82	-15	EH90	-33	PCF801	-27	R19	-87
384	-24	DAF91	-21	ECC83	-21	EL33	-54	PCF802	-38	U251	-60
3V4	-48	DAF96	-35	ECC85	-31	EL41	-52	PCF805	-56	U329	-66
6A0L2	-44	DP91	-14	ECH35	-58	EL64	-20	PCL82	-25	U801	-78
6AT6	-58	DF96	-35	ECH42	-56	EY86	-27	PCL83	-52	UABC80	-29
6AQ5	-21	DH77	-18	ECH81	-28	EZ80	-19	PCL84	-31	UBF89	-28
6BW7	-48	DK91	-25	ECL80	-27	EZ81	-21	PC85	-36	UC85	-82
6E1	-57	DK96	-43	ECL82	-27	KT61	-54	PCL86	-35	UCH42	-58
6F23	-84	DL82	-24	ECL86	-32	KT66	-75	PFL200	-49	UCH81	-28
6F25	-49	DL94	-46	EF39	-38	N78	-85	PL85	-45	UCL82	-80
12AU7	-18	DL96	-36	EF41	-56	PC86	-44	PL81	41	UP41	-49
25L6GT	-18	DY86	-21	EF80	-22	PC88	-44	PL82	-29	UF89	-28
30C15	-56	DY87	-21	EF85	-28	PC97	-35	PL83	-31	UL41	-52
30C17	-75	DY802	-28	EF86	-27	PC90	-28	PL84	-28	UL84	-27
30C18	-56	EABC80	-28	EF89	-24	PCC84	-27	PL80	-59	UY41	-27
30P5	-60	EBC33	-38	EF91	-12	PCC89	-41	PL84	-59	UY85	-22
30PFL1	-59	EBC41	-47	EF92	-26	PCC189	-46	PY81	-23	W77	-42
								PY82	-23	Z77	-18

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no callers.

GERALD BERNARD 83 Osbaldeston Road, Stoke Newington, London N.16

TECHNICAL TRADING Jason KITS

SEND FOR LISTS
ALL MAIL ORDER TO:—

15-17 QUEEN STREET ARUNDEL
Tel: 0903 882299

OR CALL AT OUR HI-FI CENTRES AT:

- ★ **PORTSMOUTH** 350-352 Fratton Road (Tel. 22034)
- ★ **SOUTHAMPTON** 77 East Street (Tel. 25851)
- ★ **BRIGHTON** (Tel. 23975) 6 Queen's Road

FANTASTICALLY POPULAR ★ TAPE ★

Standard Play		Long Play	
3in. 150ft.	12p	3in. 225ft.	18p
4in. 300ft.	22p	4in. 450ft.	27p
5in. 600ft.	45p	5in. 900ft.	52 1/2 p
5 1/2 in. 900ft.	52p	5 1/2 in. 1,200ft.	65p
7in. 1,200ft.	62 1/2 p	7in. 1,800ft.	92 1/2 p

Triple Play		Quadruple Play	
4in. 900ft.	65p	5in. 1,200ft.	£1.12 1/2
5in. 1,800ft.	£1.70	5 1/2 in. 2,400ft.	£1.70
7in. 3,600ft.	£2.40	7in. 3,600ft.	£2.40

Postage 3p. rec. Post Free less 5% on three reels.

ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £80 radios! * Send & test 7 days—we'll refund instantly if you are not astounded. Elegant black and chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer and sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth 24 hours a day, including all normal transmissions, VHF, AM, FM, MW, LW, USW, plus local and new stations not yet operational and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities and spares available for years and years to come, if ever necessary!). With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra) **BOX, POST, ETC. 50p.** ***BUT WAIT**, for only 55p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (It enables you to time, pinpoint and get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard 'longlife' batteries **PLUS** ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) **HURRY!** Send today or call at either store. It's a chance of a lifetime that nobody can afford to miss.

JUST ARRIVED! THIS YEAR'S NEW * **COMPUTERISED!** RUSSIAN MIRACLE!

BRAND NEW SPACE AGE model SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!

THE FABULOUS ASTRAD 17 PORTABLE RADIO & COMMUNICATIONS RECEIVER

THE ONLY ONE LIKE THIS!

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS & STATIONS FOUR IN FROM THE FOUR CORNERS OF THE EARTH!



28 TRANSISTORS AND DIODES! **WAVEBANDS:** STANDARD LONG and MEDIUM **Plus 5 SHORT WAVEBANDS** **Plus ULTRA SHORT WAVES (V.H.F. AM, FM, MW, LW, USW.)**

*COMPARE ITS PERFORMANCE with **£80 RADIOS!**

BATTERY MODEL £20.75 **BOX POST ETC. 50p** **MAINS/BATTERY ELIMINATOR £1.48 extra**

FIRST TIME EVER! *NOW AVAILABLE WITH **fabulous 'COMPUTERISED' WORLD TUNING GUIDE!** **NO MORE GUESSWORK!** **INSTANT DATA** at your fingertips—enables you to **TUNE IN A FLASH** to transmissions the world over!

SHOPERTUNITIES FOR BARGAINS!

BUY ONE FROM US! **SAVE £20.25 NOW!** **fabulous BRAND NEW SOLID STATE** This equipment got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE £44

OUR PRICE £23.75 **CARR. ETC. 35p**

Shopertunities 'thunder' ahead with an offer that's **FANTASTIC** (even by our standards!) We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player** combined and it also runs off standard batteries or mains. Simply plug in the 220/240v. AC (line cord). Record and play back anything, anywhere! Even tape direct from the radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44!** **WE OFFER AT ALMOST HALF PRICE!** Wonderful features: * Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** * "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic leveler! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case with carry handle. (**DESIGNS VARY SLIGHTLY**). Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. **AND** the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus B.B.C. National, VHF. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £££ more for a Car Radio or Car Cassette player **ALONE!** £23.75, **CARR., ETC. 35p.** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send today to Uxbridge Rd. and test 7 days—refund if not absolutely delighted. Or call at either store. **BONUS OFFER:** Batteries and Cassette Tape 25p extra if required.

FIRST TIME EVER! SAVE £14.48! **BRAND NEW AC/DC BATTERY/MAINS**

Cassette TAPE RECORDER & PLAYER **FIRST CLASS MAKERS**

With remote control microphone.

WE COULD CHARGE UP TO £26.97!

OUR PRICE £12.49 **POST ETC. 31p**

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £12.49!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) and **AUTOMATIC LEVEL CONTROL**. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60 or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid rewind! Fast forward! Beautiful tone from a whisper to a roar. Completely self contained—record anywhere, indoors or out! Runs on standard batteries **AND 220/240v. AC** mains. Separate jacks for remote control microphone, etc. Size 9 1/2in. x 5in. x 2 1/2in. approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. **ONLY £12.49**, post etc. 31p. *Refund if you don't agree we could charge up to **£26.97!** **BONUS OFFER** (strictly one per customer): Cassette tape, set of standard batteries **AND** microphone stand, all for 50p extra if req. Send today and test 7 days, refund if not delighted. Or call.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn store.)

SHOPERTUNITIES LTD.

Dept. WP/27, 164 UXBURIDGE ROAD (facing Shepherds Bush Green), LONDON, W12 8AQ (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opp. Chancery Lane), LONDON, W.C.1 (Thurs 7) BOTH STORES OPEN MON TO SAT 9 A.M. UNTIL 6 P.M.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunications Techns'. Certs.
 - Radio Amateurs' Examination
 - General Radiocommunications Certificate
 - C. & G. Radio Servicing Theory
 - General Certificate of Education, etc.
- Now available Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

Accredited by the CACC

Member of the ABCC

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam)

NAME
(BLOCK CAPITALS PLEASE)

ADDRESS

AGE.....OCCUPATION

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. XT28 Intertext House, Stewarts Road,
London, S.W.8 4UJ

ICS

POWERTRAN ELECTRONICS

APPOINTED DISTRIBUTORS

FOR THE

TEXAN



TEXAS INSTRUMENTS DESIGNED & APPROVED FULL KIT

£28.50

post (UK) 45p

INCLUDES TEAK CASE

20 Watts per channel, 6 Integrated Circuits, 10 Transistors. HARMONIC DISTORTION 0.05% at 15W 1KHz into 15 ohm, 0.09% at 20W 1KHz into 8 ohm. FREQUENCY RESPONSE 5Hz to 35KHz (-3dB), SIGNAL TO NOISE RATIO 60dB magnetic pick-up, 72dB radio.

Components available in separate packs Eg. Resistors and Capacitors £3.70, Switches and Controls £2.35, Fibre Glass PCB £2.50, Semiconductors £8.35.

For other parts and full specification please see our free list. More amplifier kits (Wireless World designs), slider potentiometers, low priced semiconductors, etc. in our free list.


FOR FREE ILLUSTRATED LIST PLEASE WRITE TO

DEPT. D
22 THE PANTILES BEXLEYHEATH KENT
MAIL ORDER ONLY

PRINTED CIRCUIT KIT

BUILD 50 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleaner/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs* (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 50 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

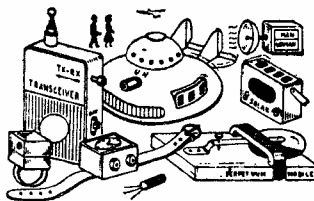

**EXPERIMENTERS
PRINTED CIRCUIT KIT**
60p

Postage & Pack. 10p. (U.K.)

Commonwealth:

SURFACE MAIL 20p

AIR MAIL 60p

Australia, New Zealand,
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photoelectric Radio. (8) "TRI-FLEXION" Triple Reflex with Self-adjusting regeneration (Patent Pending). (9) Solar Battery Loud-speaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Miniature Radio Receivers based on the "Triflexion" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62" x .86" x .25". (11) Wristwatch Radio 1.15" x .80" x .55". (12) Ring Radio 7/8" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P.P. Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal. Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Rain Alarm. (33) Ultrasonic Switch Alarm. (34) Stereo Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. . . plus 10 Photoelectric Circuits, Alarms, Modulators, Stabilisers. . .

YORK ELECTRICS, Mail Order Dept.
335 Battersea Park Road, London, S.W.11

Send a S.A.E. for full details, and a brief description of all Kits and Projects.

BI-PRE-PAK

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 25p

POST & PACKING 15p

TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V. 0.5 to 2mA.	50p
B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors, Mixed types and values.	50p
H9	2	OCPT1 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncodcd TO-5 can	50p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8-43V.	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types.	50p
H39	10	Integrated Circuits, 6 Gates BMC 962, 4 Flip Flops BMC 945	50p
H40	20	BFY50/2, 2N696, 2N1613 NPN Silicon uncodcd TO-5	50p

UNMARKED UNTESTED PACKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits, Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OVER **1,000,000** TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.
Audio NPN, similar to ZTX300, 2N3708/9 BC107/B/9, BC168/9 etc.

R.F. NPN and switching NPN Types also. Please state type of transistor required when ordering.

ALL AT 500 for £3, 1,000 for £5, 10,000 for £40

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN silicon similar ZTX 300 range
TYPE "H" PNP silicon similar ZTX 500 range

POWER TRANSISTOR PRICE BREAKTHROUGH!

Plastic cased Silicon Power Transistors of latest design. 40watts and 90watts. PNP & NPN types. All types available at the most shattering low prices of all time. All are fully tested, marked and guaranteed!

1-12 13-25 26-50

40W NPN 20p 18p 16p
40W PNP 21p 19p 17p
90W NPN 24p 22p 20p
90W PNP 25p 23p 21p

PAK - PAKS of Complementary pairs

MP40 40W + 40W 50p 48p 46p
MP90 90W + 90W 60p 58p 56p

A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

8 RELAYS FOR VARIOUS TYPES P & P 25p £1

INTEGRATED CIRCUITS

	1-12	13-25	26-50
Clocked Flip Flop	BMC931 20p	18p	16p
Ex. 2/4-input Buffer	BMC932 12p	11p	10p
2/4-input Expander	BMC933 12p	11p	10p
Hex. Inverter	BMC934 12p	11p	10p
Hex. Inverter	BMC935 12p	11p	10p
Hex. Inverter	BMC936 12p	11p	10p
Hex. Inverter	BMC937 12p	11p	10p
Decade Counter	BMC938 25p	23p	21p
Div. by 16 Counter	BMC939 25p	23p	21p
Hex. Inverter	BMC940 12p	11p	10p
Hex. Inverter	BMC941 12p	11p	10p
Type D Flip Flop	BMC942 20p	18p	16p
Ex. 2/4-input Power	BMC944 12p	11p	10p
Clocked Flip Flop	BMC945 20p	18p	16p
4/2 Input NAND Gate	BMC946 11p	10p	9p
Clocked Flip Flop	BMC948 20p	18p	16p
4/2 Input NAND Gate	BMC949 12p	11p	10p
Pulsed Trig. Binary	BMC950 20p	18p	16p
Monostable Multivib.	BMC951 25p	23p	21p
Dual J/K Flip Flop	BMC953 20p	18p	16p
Dual J/K Flip Flop	BMC955 20p	18p	16p
Dual J/K Flip Flop	BMC956 20p	18p	16p
Quad. 2-input Power	BMC958 12p	11p	10p
2/4-input Gate	BMC961 12p	11p	10p
3/3-input NAND Gate	BMC962 11p	10p	9p
3/3-input NAND Gate	BMC963 12p	11p	10p
Audio Amp. 3w. SL403D	£1.50	£1.40	£1.36
Linear Op. Amp 709C	25p	20p	15p
Decade Counter SN7490	65p	60p	55p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile
16 pin type at 16p each. } type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.1 Transistor Equivalents and Substitutes; 40p
This includes many thousands of British U.S.A., European and C.V. equivalents.

The Hiffe Radio Valve & Transistor Data Book 9th Edition; 75p
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Postage and Packing 21p.
Send for lists of these English publications

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX. S50 9DF
TELEPHONE: SOUTHEND (0702) 46344

COMET HI-FI discount warehouses



NEW LOW PRICES

STEREO AMPLIFIERS

	Rec. Retail Price	Comet Price
ALBA UA 700	37-93	25-25
ALPHA 212 by Highgate	37-75	24-75
AMSTRAD IC 2000	46-25	27-50
AMSTRAD Integra 4000	35-50	21-50
ARMSTRONG 521	59-00	43-75
DULCI 207M	32-00	19-25
FERROGRAPH F307 Mk. II (cased)	68-00	45-50
GODWIN RH 25 25	59-95	47-95
H.L. Audio Phoenix 707	29-00	14-95
JVC Nivico MCA 104Z	85-00	70-95
MCA VSE Quadraphonic	130-50	109-95
MCA V9E Quadraphonic	89-00	74-95
MCA V9E Quadraphonic	148-00	124-95
KELETRON KSA 700	29-00	17-95
KELETRON KSA 1500	39-00	23-50
LEAK Delta 30 (cased)	69-00	46-95
LEAK Delta 70 (cased)	85-90	57-95
METROSOUND ST20E	39-50	24-20
METROSOUND ST60	70-00	45-45
PHILIPS RH521	109-00	89-95
PHILIPS RH 630	30-50	21-50
PIONEER SA500A	47-10	32-95
SA600	95-48	57-95
SA800	126-55	75-95
SA900	133-83	83-95
SA1000	155-82	94-95
QD 800 Quadraphonic decoder	42-85	29-95
Q 800 Quadraphonic	138-60	122-95
QC 800 Quadraphonic pre-amp	129-98	84-95
QM 800 Quadraphonic pow. amp	160-84	104-95
Reverberation 202w	54-95	35-95
RANK ROTEL 210	34-90	23-50
RANK ROTEL 310	52-00	34-95
RANK ROTEL 610	70-50	51-95
RANK ROTEL RA 810	105-50	72-95
RANK ROTEL RA 1210	129-00	89-95
ROGERS Ravensbourne	64-50	49-25
Ravensbourne (cased)	69-50	53-95
Ravensbrook Mk. II	50-50	38-95
Ravensbrook (cased) Mk. II	55-50	41-95
SINCLAIR 2000	45-00	28-95
3000	45-00	28-95
PROJECT 605	29-95	18-90
SOLARVOX 20, 10 watts, RMS per channel	39-95	24-95
SOLARVOX 30, 15 watts RMS per channel	49-95	32-95
SOLARVOX AM108 2 x 8 watts, RMS plus MATRIX 4 channel	28-45	19-95
SOLARVOX AM318 2 x 18 watts, plus MATRIX 4 channel	41-38	26-95
TANDBERG TA300	69-90	54-95
TELETON SAQ 206B	33-00	20-50
307	33-00	20-50
GA 202 15 watt, RMS per channel	45-75	28-95
WHARFEDALE Linton amplifier	65-00	41-95

All take both ceramic and magnetic cartridges.

TUNERS

AMSTRAD Multiplex 3000 FM	39-95	28-95
*ARMSTRONG 523 AM/FM	52-68	40-95
*ARMSTRONG 524 FM	40-97	31-95
*ARMSTRONG Mk Decoder	9-50	6-95
*DULCI FMT 7 FM	24-43	17-50
DULCI FMT 7S Stereo	32-29	24-95
GODMANS Stereomax	75-74	35-95
JVC Nivico MCT VSE AM/FM	86-89	69-95
MCT V7E AM/FM	122-42	99-95
LEAK Delta FM	79-50	57-95
LEAK Delta AM/FM	89-50	69-95
METROSOUND FMS 20	54-92	38-75
PHILIPS RH 690	48-50	31-95
PHILIPS RH 621	109-00	89-95
PIONEER TX500A AM/FM	75-52	50-95
PIONEER TX600 AM/FM	104-57	73-95
RANK ROTEL 320	59-50	42-95
RANK ROTEL 620	93-50	67-95
ROGERS Ravensbourne Chassis	57-95	43-95
Ravensbourne in Teak Case	62-63	47-95
Ravensbrook Chassis	42-14	31-95
Ravensbrook (cased)	48-00	36-95
SINCLAIR 2000	45-00	29-95
3007	45-00	29-95
Project 60 Tuner (Stereo)	35-00	17-50

All above Tuners are complete with MPX Stereo Decoder except where starred

TUNER/AMPLIFIERS

AKAI CR80T FM/AM Tuner Amplifier with built in Eight Track Tape Recorder	149-84	89-95
AKAI A A8500	249-00	179-85
AKAI 6200	105-00	75-95
AKAI 6300	137-50	79-95
AKAI 6600	159-00	108-95
ARENA 2600	111-30	59-95
ARMSTRONG M8 Decoder	9-50	6-95
ARMSTRONG 525	90-14	69-95
ARMSTRONG 526	102-72	77-95
CARLTON M4000 AM/FM with 8 track player and speakers	69-95	39-95
GODMANS Module 80, 35w, RMS Module 80 Compact	93-00	69-95
Module 90	168-00	127-95
Module 110 FM/MW/LW/SW/100w, RMS	119-00	91-95
139-00	105-95	

TUNER/AMPLIFIERS—continued

	Rec. Retail Price	Comet Price
GODMANS Module 110, Compact	245-00	187-50
JVC Nivico VR 5500/5501 AM/FM	96-96	81-95
VR 5511 AM/FM and SEA	134-00	74-95
4VR 5414 Quadraphonic	175-00	146-95
212-00	179-95	
KYOTO 1000 AM/FM Tuner/Amplifier with built in Stereo Cassette Recorder. Complete with two speakers and two microphones	85-00	61-95
LEAK Delta 75	175-00	129-95
PHILIPS RH 790	215-00	179-95
PHILIPS RH 720	215-00	179-95
PIONEER SX525	140-53	98-95
SX626	192-49	134-35
SX727	231-74	162-95
SX828	297-20	208-95
QX 800 Quadraphonic	286-24	199-95
ROGERS Ravensbrook Chassis	98-57	73-95
ROGERS Ravensbrook (cased)	105-35	78-45
ROTEL RX 150	67-93	45-95
ROTEL RX 150A	69-90	50-95
ROTEL RX200A	89-50	65-95
ROTEL RX 400A	107-50	78-95
ROTEL RX 600A AM/FM	149-00	109-95
ROTEL RX 800A	189-50	139-95
ROTEL RX 154A Quadraphonic	129-50	94-95
SOLARVOX TAM 1105 2 x 5 watts RMS AM/FM Multiplex comp. with 2 speakers and featuring Matrix 4 channel	38-50	24-95
TANDBERG MPX	103-03	84-95
TANDBERG TR200 MPX	106-00	85-95
TANDBERG TR1000 FM MPX (teak)	156-00	129-60
TANDBERG TR 101 AM/FM MPX	169-00	139-95
WHARFEDALE LINTON WE40	115-00	95-95
TELETON CR55	125-26	68-50
TELETON R8009 AM/FM	42-16	21-95

All the above take magnetic cartridges except Teleton R8000 which takes ceramic only. All include MPX Stereo Decoder with the exception of Armstrong where M8 decoder is extra.

TURNABLES

CONNOISSEUR BD1 kit	13-34	10-95
CONNOISSEUR BD2 Chassis	32-71	25-95
CONNOISSEUR BD2 P/C/SAU2	41-29	33-95
GARRARD SP25 Mk. III	149-37	109-95
GARRARD 40B	13-63	10-95
GARRARD SL55B	20-93	13-75
GARRARD SL95B	49-21	32-25
GARRARD 401	39-04	25-95
GARRARD SL72B	32-60	21-95
GARRARD AP76	28-44	17-25
GARRARD Zero 100A	57-42	38-95
GARRARD Zero 100S	52-83	36-95
GARRARD WB4 Base Mk. 112 to fit Zero 100 and Zero 100S	6-55	4-95

The following Turntables are complete with base, plinth, plastic cover and cartridge. Fully wired and ready for use. All at special prices.

GARRARD SP25 Mk. 111 with Goldring G300	Special Price £18-50
McDONALD MP60 with Goldring G800	Special Price £17-50
McDONALD MP60 with SHURE M 44/7	Special Price £18-95
McDONALD MP60 with SHURE M 44/E	Special Price £19-95
McDONALD HT70 with Goldring G300	Special Price £25-50
GARRARD AP76 with Goldring G800	Special Price £26-50
GARRARD AP76 with Shure M55E	Special Price £30-50
GARRARD AP76 with Shure M75EJ	Special Price £32-50
GARRARD 2025 with Sonotone 9TAHC	Special Price £12-75
GOLDRING GL75	Special Price £39-50
THORENS 150 AB complete with TX11 cover, Shure M55E cartridge	£60-35 £49-95

Base and cover to fit GARRARD	Sp. Price	3-60
SP25, SL55, SL65B	29-64	20-50
GOLDRING G101P/C	31-39	20-95
GOLDRING GL72P Chassis	40-81	27-50
GOLDRING GL75P	41-86	28-95
GOLDRING GL75P	51-82	35-25
GOLDRING GL85P/Cover	87-19	56-95
Covers for 72P	4-71	3-25
Cover for 75P (de Luxe)	5-23	3-50
Cover for 85P	6-98	4-95
C99-plinth and cover for G99	15-35	11-95
GOLDRING G99	29-84	19-25
LEAK Delta	69-50	52-50
JVC Nivico SRP 473 Quadraphonic, including plinth and cover	69-50	58-95
McDONALD MP60	14-78	9-50
McDONALD 610	18-75	12-95
McDONALD H10	20-63	15-50
Base and cover for MP60 and 610	Sp. Price	3-95
PHILIPS GA212 Electronic	69-00	57-50
PIONEER PL12D with base and cover	49-18	34-50

TURNABLES—continued

PIONEER PL61 with base and cover	176-83	119-95
THORENS TX25 cover	8-85	6-50
THORENS TD125	76-73	62-63
THORENS TD125 Mk. II	82-63	66-50
THORENS TD125AB	115-69	79-95
THORENS TD 125AB Mk. II with TP 16 arm	124-54	99-95
THORENS TD 160/c including base and cover	69-80	56-95
THORENS TD150 Mk. II	36-30	28-95
THORENS TD150A Mk. II	46-33	35-95
THORENS TD150AB Mk. II	50-17	39-95
THORENS TX11 cover	4-49	3-60
WHARFEDALE Linton	37-50	26-95

PICK UP ARMS AND HEADS

AUDIO Technica AT 1005 Mk. 11	18-78	14-25
AUDIO Technica L2 lifts	2-61	1-95
CONNOISSEUR SAU2	14-61	11-95
GOLDRING Lenco 75	13-96	9-25
GOLDRING Lenco L69	10-46	6-50
GOLDRING PH6 Head Shell	2-97	1-99
SME 3009 with S2 Shell	32-34	23-95
SME 3009 HE with S2 Shell	33-71	24-95
SME 3012 with S2 Shell	34-44	25-50
SME 3012 HE with S2 Shell	35-81	26-50
SME S2 Headshell	2-59	1-95

SPEAKERS

AMSTRAD 138 (pair) Teak	26-00	13-95
AKAI SW 155	64-50	44-95
B and W Model 70	159-50	109-95
B and W DM2	69-99	47-50
B and W DM4	49-68	37-95
B and W DM5 (pair)	59-48	43-95
CELESTION COUNTY (pair)	47-94	35-95
Ditton 120 (pair)	56-40	38-50
Ditton 15	37-40	26-00
Ditton 25	65-00	42-50
Ditton 44	54-00	35-00
Ditton 66	99-00	70-95
FERROGRAPH S1 inc. stand	95-00	67-95
GODMANS Minister Pair	49-20	35-95
Havant (pair)	57-12	39-40
Magister	65-63	42-00
Double Maxim	67-40	48-50
Mezco	35-70	23-45
Miram K2	46-20	29-50
Woodwood	55-00	36-95
Dimension 8	72-44	44-95
DIN 20 NT Kit	12-19	8-50

KELETRON KN 400 2-speaker system (pair)	15-86	11-95
KN600 3-speaker system (pair)	26-45	16-95
KN800 3-speaker system (pair)	31-80	18-95
KN1100 4-speaker system (pair)	40-80	23-95
KN1600 3-speaker system	25-20	14-95
KN2100 3-speaker system	30-60	18-95
LEAK 150 (pair)	50-00	37-50
LEAK 250 (pair)	63-70	45-95
LINEAR 10 watt Teak (Pair)	49-50	34-50
MARSDEN HALL Annexe 100 Walnut (pair)	Sp. Price	13-50

METROSOUND HFS 103 (pair)	30-00	17-95
207	29-20	20-95
Duplex 15	32-00	21-95
Duplex 25	56-00	37-50
PIONEER CS53	46-72	29-95
SINCLAIR Q16	8-98	6-50
TANDBERG Tan 7	29-50	23-00
Tan 11 (pair)	40-00	31-95
TL 12 Teak (pair)	55-50	44-50
TL 25 Teak (pair)	71-50	56-95
TL 50 Teak	68-00	50-95
TELETON 8000 (pair)	21-08	11-95
THORPE GRENVILLE TG100 (pair)	28-95	16-95
TG200 (pair)	41-95	24-95
TG300 (pair)	55-95	29-95
WHARFEDALE Denton Mark II (pair)	42-00	28-95
Linton Mark II (pair)	52-00	37-50
Triton 111 (pair)	65-00	46-95
Melton Mark II	35-00	23-75
Devalde 3 Mark III	47-50	32-25
Rosedale	69-00	44-95
Unit 3 speaker kit	12-50	8-95
Unit 4 speaker kit	19-00	12-95
Unit 5 speaker kit	27-50	18-75

CHASSIS SPEAKERS

GODMANS Twin-axiom 8	9-12	6-95
Twin Axium 10	10-06	7-50
Axiom 401	17-68	11-95
Axiom 8P	5-49	4-15
Axiom 10P	5-97	4-50
Axiom 12P	13-00	9-15
Axiom 15P	21-00	14-60
Axiom 18P	35-70	24-45
Axiom 100 40 watts din.	12-00	8-35
ARU 172	4-50	3-20
Axent 100	6-90	4-80
Midax 650	13-59	9-50
Atomaster	3-30	2-60
Crossover network XO/950	7-77	5-45
WHARFEDALE 8 in. Bronze/RS/DD Super 8/RS/DD	4-75	3-30
Super 8/RS/DD	8-50	6-25
Super 10/RS/DD	14-00	9-95

OVER 1000 ITEMS ALWAYS IN STOCK
All items brand new and fully Guaranteed
and backed by after-sales service

— latest models in manufacturers' sealed cartons

COMET for
after-Sales Service
THROUGHOUT THE U.K.

Pictured. Service Dept. at Clough Rd., Hull,
 also at Birmingham, Bredington, Doncaster,
 Edinburgh, Gosle, Leeds, Leicester,
 Rotherham, Sheffield, Stockport, Wakefield
 and York.

	Rec. Price	Retail Price	Comet Price
CARTRIDGES			
AMSTRAD 900C	5.32	8.40	
AMSTRAD 900D	8.10	5.40	
AMSTRAD 900 EX	11.90	8.50	
AUDIO TECHNICA AT 66	6.47	3.45	
CONNOISSEUR Ceramic SCU1	6.09	4.95	
GOLDRING G850	6.10	3.75	
GOLDRING G800E	12.21	4.50	
GOLDRING G820	11.62	8.25	
GOLDRING G820E	17.44	12.25	
GOLDRING G820 Super E	23.25	16.25	
GOLDRING G800 Super E	24.41	15.25	
EMPIRE 1000ZE/X	62.42	39.95	
EMPIRE 999E/X	44.44	28.95	
EMPIRE 999SE/X	26.13	18.95	
EMPIRE 999SE/X	21.11	13.95	
EMPIRE 999E/X	16.36	10.95	
EMPIRE 909E/X	12.79	8.50	
EMPIRE 909E/X	9.94	6.95	
SHURE M3DM	6.10	3.75	
SHURE M31E	11.63	6.95	
SHURE M32	10.73	6.50	
SHURE M44-G	8.30	4.95	
SHURE M44-7	7.90	4.50	
SHURE M-44C	7.90	4.90	
SHURE M44E	8.60	4.50	
SHURE M55E	9.70	5.90	
SHURE M75	14.70	8.35	
SHURE M75-6 (S)	8.36	5.45	
SHURE M75-6	13.60	7.60	
SHURE M75EJ	15.40	8.75	
SHURE M75LD	19.10	10.15	
SHURE M91ED	20.80	12.95	
SHURE V15-11	38.45	24.95	
*SONOTONE 9TAHC Diam/5aph	3.75	1.45	
Starred cartridges above are ceramic. All others are magnetic.			
BLANK TAPES			
SCOTCH DYNARANGE CASSETTES			
C60	0.71	0.40	
C90	0.99	0.50	
C120	1.49	0.75	
SCOTCH HIGH ENERGY COBALT CASSETTES			
C60	1.10	0.65	
C90	1.45	0.85	
SCOTCH Low Noise 8-TRACK			
BLANK CARTRIDGES			
40 mins.	1.50	0.90	
50 mins.	1.60	1.10	
SCOTCH HI-FI DYNARANGE SPOOLED TAPES			
5" L.P. 900	1.88	1.10	
5 1/2" L.P. 1200	2.20	1.30	
7" L.P. 1800	2.95	1.80	
SCOTCH HI-FI DYNARANGE DOUBLE PLAY			
5" D.P. 1200	2.51	1.40	
5 1/2" D.P. 1800	3.15	1.95	
7" D.P. 2400	4.03	2.50	
Postage—Tape, cassettes and 8T cartridges 1-9 items 5p per order. Packs of ten post free.			
BASES AND COVERS			
CONNOISSEUR Plinth BD1	5.57	4.50	
CONNOISSEUR Cover	4.17	3.40	
CONNOISSEUR P.U. Mount Board	4.95	4.00	
GARRARD WB1 Base	3.78	2.95	
GARRARD WB4 Base	5.60	4.25	
GARRARD SP1 Cover	3.68	2.75	
GARRARD SP4 Cover	4.38	3.25	
Special Offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500. Sp. Price 3.60			
GARRARD WB4 base MK 11z to fit Zero 100 and Zero 100S	6.55	4.80	
GOLDRING Plinth 75	9.77	6.75	
GOLDRING Plinth 72	9.42	6.50	
GOLDRING Covers 72P	4.71	3.25	
Cover for 75P De Luxe	5.23	3.60	
THORENS TX 25 (for TD125AB)	8.85	6.50	
THORENS TX11 Cover	4.49	3.60	
SME Plinth System 2000 with motorboard	46.20	35.95	
MOTORBOARDS only	5.85	4.45	
SME P1 Spacer	0.98	0.75	
HEADPHONES			
AMSTRAD HP35A	7.50	3.90	
HP35A with volume control	10.70	7.90	
HP37A base and trable controls	13.95	9.90	
AKAI ASE9	7.25	4.25	
AKAI ASE22	11.90	7.25	
AKG K180	28.00	16.95	

	Rec. Price	Retail Price	Comet Price
HEADPHONES—continued			
AKG K60	15.00	8.95	
AKG 100	8.00	4.95	
AKG 120	10.00	4.50	
KOSS HV1	20.00	15.95	
KOSS ESP-9 Electrostatic	45.00	34.95	
KOSS K2 plus 2 Quadrafone	45.00	35.95	
KOSS PRO 5 L/C	30.00	23.95	
KOSS PRO-4AA	28.00	20.95	
KOSS KO-727B	16.50	12.45	
KOSS 747	20.00	14.95	
KOSS K-711	10.00	7.75	
KOSS K6	12.50	9.50	
KOSS K6/LC (with volume control)	14.00	10.50	
KOSS K6/LCQ Quadrafone	20.00	16.95	
PIONEER SE 50	21.90	13.25	
PIONEER SE 30A	12.60	8.75	
PIONEER SE 20A	7.98	4.95	
PIONEER SE 10	10.53	6.00	
PIONEER SEL 40	17.43	11.30	
ROTEL RH 630	6.50	4.50	
ROTEL RH 700	9.95	6.75	
SOUND MD806	6.40	2.70	
WHARFEDALE DD1	12.50	8.75	
WHARFEDALE ISODYNAMIC	19.95	14.95	
MANUFACTURERS' HI-FI STEREO SYSTEMS—COMPLETE			
ALBA UA 552	47.75	29.95	
BUSH A1005	69.89	53.25	
DANSETTE Consort Stereo	34.43	23.95	
DANSETTE 4005	71.45	51.95	
DANSETTE 4020	47.99	31.95	
DECCA SOUND 613	Sp. Price	46.50	
DECCA SOUND 1204	Sp. Price	72.95	
DECCA SOUND 1204	Sp. Price	70.95	
DECCA COMPACT 2	Sp. Price	78.95	
DECCA COMPACT 3	Sp. Price	98.95	
DECCA 403	Sp. Price	44.95	
EKCO ZU4	166.00	125.90	
FERGUSON 3450 B with Radio (new model)	79.50	61.95	
FERGUSON 3451 B with Radio (new model)	107.00	82.95	
FERGUSON 3454	41.50	32.95	
FIDELITY UA1 Music Master with Radio	100.00	69.95	
FIDELITY UA2 Music Master	43.50	30.95	
FIDELITY UA3 Music Master	63.00	45.95	
FIDELITY Stereo Nine	38.50	22.95	
G.E.C. 2810	79.00	59.95	
GROSVENOR MPX 8-400 AM/FM MPX Tuner/Amplifier, magnetic input with built-in 8-track cartridge player with speakers	67.50	39.95	
HMV 2451	122.00	95.95	
HMV 2452	66.00	49.95	
HMV 2453	66.00	49.95	
KB 1025 with 662 speakers	48.25	37.95	
KB 1250 with KS 653 Speakers	71.00	53.95	
KB 2010 with 550 speakers	101.50	77.95	
KB 2250 with 658 speakers	124.00	95.95	
MURPHY 902 Studio 1, AM/VHF Radio	84.50	64.95	
MURPHY 903	84.42	64.95	
PHILIPS 809	105.00	76.95	
PHILIPS GF 924	65.30	49.65	
PHILIPS 825	49.50	38.95	
PHILIPS 826	75.00	52.95	
PHILIPS 836	68.50	49.55	
PHILIPS 836	95.00	69.95	
PYE BLACK BOX unit Stereo 1022	60.93	65.95	
RIGONDA Party Time	28.50	20.95	
STEEPLETONE Stereo System	41.75	27.95	
ULTRA 6028	59.95	45.95	
ULTRA 6540 B (new model)	79.50	61.95	
ULTRA 6455	41.35	31.95	
ULTRA 6454	38.85	29.95	
TAPE RECORDERS			
AKAI 1721L	99.90	73.95	
AKAI 4000D 4-track stereo deck	83.65	64.50	
AKAI 4000 DS	99.50	73.95	
AKAI X201D	179.00	132.95	
AKAI X1810	229.00	169.95	
AKAI GX221D	229.00	169.95	
AKAI GX1900D	239.00	177.95	

	Rec. Price	Retail Price	Comet Price
TAPE RECORDERS—continued			
AKAI GX370D	350.00	259.95	
AKAI CR80D 8-track stereo deck	85.02	58.25	
AKAI CR80 8-track stereo recorder	100.39	74.00	
AKAI CR80T 8-track stereo recorder and tuner amplifier	149.94	89.95	
AKAI CR81	109.50	80.95	
AKAI CR81D	89.50	65.95	
AKAI X200D	157.93	99.95	
AKAI GX 220D	229.00	164.95	
FERGUSON 3253 4-track	70.45	51.95	
FERROGRAPH 702/704 Dolby	285.53	241.95	
FERROGRAPH 722/724 Dolby	297.28	251.95	
FERROGRAPH 722/724 Dolby	326.65	276.95	
FERROGRAPH 722H Dolby	338.40	286.95	
FERROGRAPH 702/704	235.00	172.95	
FERROGRAPH 722/724	276.13	198.95	
FIDELITY Brannan 4-track	34.75	19.95	
GROSVENOR MPX 8-400 AM/FM MPX Tuner/Amplifier, magnetic input with built-in 8-track cartridge player with speakers	67.50	39.95	
GRUNDIG TK 121 (twin-track)	56.25	39.95	
GRUNDIG TK 141 (4-track)	62.10	45.95	
GRUNDIG TK 146 (4-track auto)	66.95	49.95	
GRUNDIG TK 147 (4-track auto)	88.65	76.95	
GRUNDIG TK 148 (4-tr. auto 2 spd.)	74.10	57.95	
GRUNDIG TK 246 4-track Stereo Deck	131.85	101.95	
GRUNDIG TK 3200 Hi-Fi (Battery)	141.10	105.95	
PHILIPS 4303 Twin-track	98.50	66.95	
PHILIPS 4313 4-track stereo deck	200.00	145.95	
TANDBERG 2041 4-track stereo	130.50	108.50	
TANDBERG 1841 4-tr. stereo deck	66.00	49.95	
TANDBERG 3021X 2-track stereo	113.00	89.95	
TANDBERG 3041X 4-track stereo	113.00	89.95	
TANDBERG 4021X 2-track stereo	199.30	159.95	
TANDBERG 6041X 4-track stereo	199.30	159.95	
TAPE RECORDERS (CASSETTE)			
AKAI CS35D tape deck	79.95	59.50	
AKAI CS35 Stereo Inc. Speakers	112.50	82.95	
AKAI GXC 40D tape deck	112.50	82.95	
AKAI GXC 40	167.50	123.95	
AKAI GXC 40T recorder, tuner/amp.	129.50	95.95	
AKAI GXC 45D tape deck	129.50	95.95	
AKAI GXC 460 Dolby tape deck	139.50	103.50	
AKAI GXC 65D Dolby auto-reverse tape deck	154.50	110.25	
APCO Battery/Mains AM/FM Radio	35.00	22.95	
BROWNIE Radio/cassette recorder	45.00	19.95	
BUSH Discassette DC70	20.62	15.95	
BUSH TP 60	27.62	15.95	
BUSH TP 66 Battery/Mains	28.18	21.50	
BUSH TR 70 Battery/Mains	28.13	19.95	
BUSH RTP 100 Battery/Mains with AM/FM Radio	43.95	33.95	
BUSH Arena C440 Stereo Deck with chromium dioxide switch	61.73	49.95	
CARLTON LCR 500	Sp. Price	11.95	
DANSETTE DCT 105	20.62	14.95	
ERG 350 batt./mns. VHF/MW Radio	39.97	29.95	
FERGUSON 3240 with cassette	24.90	15.95	
FERGUSON 3253	42.40	31.95	
FERGUSON 3257	56.45	41.95	
FERGUSON 3257 5 spkrs. for above	16.00	12.00	
FERGUSON 3262 (battery/mains)	30.15	22.95	
GEC CR200 AM/FM Cassette Radio Battery/Mains with slide controls	Sp. Price	35.95	
GRUNDIG C210 Batt./mains	48.75	36.95	
HARVARD Elite Cassette/AM/FM Radio (battery/mains)	44.75	23.95	
JVC Nivico 9420 LS with AM/FM radio, battery/mains	61.45	45.95	
JVC Nivico 1710 Radio/Cassette, AM/FM	61.00	42.95	
PHILIPS 2202/2203	24.00	17.95	
PHILIPS 2204 battery/mains	29.10	24.95	
PHILIPS 2405 Stereo with 2 RH401 LS	72.00	54.95	
PHILIPS 3302	21.50	15.95	
PIONEER CT 4141 Dolby Deck	150.02	104.95	
PYE 9109	20.37	14.95	
PYE 9115 Stereo	69.90	49.95	
TELETON STC 106 Stereo Deck	46.45	30.95	
WHARFEDALE Dolby DC9 Mk. II	119.00	85.95	

FREE Technical Advisory Service. If in doubt ask us! Price list on request. Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) **OR, IF SECURICOR DELIVERY REQUIRED ADD £1.95 ONLY.** Make cheques, Money Orders payable to 'COMET'.

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

OPEN DAILY TO THE PUBLIC FROM:
 9am-6pm Monday
 9am-1pm Tuesday
 9am-8pm Wednesday
 9am-8pm Thursday
 9am-8pm Friday
 9am-5.30pm Saturday

- Dept. PW BIRMINGHAM: Heeley Road, Selly Oak, B29 6EY. Tel.: 021-472-6181 and at Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley B26 1BU. Tel.: 021-706-0684
- Dept. PW DINGWORTH: 1 Newhouse Road, E166 6GX. Tel.: 031-554-4454 (9 lines)
- Dept. PW HULL: Reservoir Road, Clough Road, HUG 7QD Tel.: 0482 46441 (6 lines)
- Dept. PW LEEDS: 78 Armlay Road, LS12 2EF. Tel.: 0532 40551
- Dept. PW SHEFFIELD: The Mill, 1 Loxley Road, Malin Bridge, S6 4TN. Tel.: 0742 3417216
- Dept. PW STOCKTON: Teesway, Portrack Lane, Teesside TS18 2RH Tel.: 66132/65215
- Dept. PW ROCHDALE: Corner of Well 1'th Lane and Queensway. Tel.: 50606
- Dept. PW LEICESTER: Syston Street. Tel.: 0533 2236
- Dept. PW WIGAN: Wigan, Princess Street, WNS 4EZ. Tel.: 0942 34741
- Dept. PW HACKBURY: Felnax Trading Estate, 190 London Road, Hackbury, Wallington Surrey. Tel.: 01-669-0271
- Dept. PW DAGENHAM: Rainham Road South, Dagenham RM10 8ST. Tel.: 01-595-5111

CASH SAVING PACKAGES

The Space Age WORLD RECORD award winning 7' 6" long All Band JOYSTICK VFA Antenna—JOYMATCH A.T.U.—TRIO RECEIVER or TRANSCIEVER—Matching HEADPHONES—A COMPLETE STATION IN ONE COMPACT PACKAGE—THE FLAT DWELLER'S DREAM!

1972 JOYSTICK VFA £11.40 (A); JOYMATCH ATU 111 * or 111A £11.40 (B); JOYMATCH ATU LO-Z500 £16.45 (C).

COMMUNICATIONS HEADPHONES £2.60 (D)

(All including postage, packing, accessories & insurance.)

PARTRIDGE PACKAGE No. 1

9R59DS receiver ... £49.50
* Items (A); (B); (D) above ... £11.00
Complete Gen. Coverage Station ... £60.50

PARTRIDGE PACKAGE No. 2

JR310 receiver ... £75.00
* Items (A); (B); (D) above ... £7.00
Complete Amateur RX Station ... £82.00

PARTRIDGE PACKAGE No. 3

JR599 receiver ... £185.00
* Items (A); (B); (D) above ... FREE
Complete Amateur RX Station ... £185.00

PARTRIDGE PACKAGE No. 4

TS/PS515 Transceiver 180W ... £210.00
* Items (A); (C); (D) above ... FREE
Complete TX-RX Station ... £210.00

BARCLAYCARD — ACCESS — PERSONAL LOANS!!

ALSO: SP5D SPKR. £4.50; 2M CAR TRANSCIEVER TR7100 £99.50; 2M PERSONAL TRANSCIEVER TR2200 £62.50; CW FILTER (TS515) £14.00; 10AZ FILTER (JR310) £14.76; 100KHz CAL CRYSTAL £3.18; OA2 MAINS STABILISER 67p; B1016L P.T.T. HAND MIC (515) £3.38.

PARTRIDGE BUDGET LINE—

ARTIFICIAL EARTH—SOLVES YOUR EARTH PROBLEMS £4.80; AERIAL BANDSWITCH—TUNED AERIAL £4.80; A.T.U. KIT—FULL COVERAGE TX/RECEIVER £4.80; ASSEMBLED £5.80.

(All including Postage, Packing, Accessories & Insurance.)

Send 3p stamp for full illustrated details of Partridge Products.

TRIO brochures (state which) 3p stamp extra.

CARRIAGE & INSURANCE EXTRA OVERSEAS.

**BOX 5
PARTRIDGE ELECTRONICS LTD.
BROADSTAIRS, KENT**

Phone: 0843 62535 or 62839 cheap periods.

COMPARE OUR PRICES

Speaker Bargains
E.M.I. 13 x 8 in 3, 8 & 15 OHMS
PLAIN ... £2.00
W/17 TWEETER ... £2.25
Type 350-20 watt with Tweeter ... £2.50
8 OHM p. & p. 37p ... £7.25
TWIN TWEETER ... £3.50
8 x 5 in 3, 8 & 15 OHMS ... £1.30
7 x 4 in 3 & 8 OHMS ... £1.05
FANE 8" 8 OHM DUAL CONE ... £2.30
CELESTION 8" 15 OHM ... £1.50
GOODMANS 10 x 9.3 OHM ... £1.60
BAKER GROUP 25 12" 25 WATT 8 or 15 OHM ... £5.75
2 1/2" 8 or 64 OHM p. & p. 10p. POSTAGE 25p per SPEAKER50

Kit-Form Cabinets Teak
(17" x 10" x 6") with a 13" x 8" or 8" CUT OUT ... £2.75
(12" x 12" x 6") with a 8" x 5" or 8" CUT OUT ... £2.25
(PLEASE SPECIFY CUT OUT)
Add 35p per Cabinet for p. & p.

Cartridges with standard fittings & shell
ACOS GP91/2SC or GP91/3SC STEREO COMPATIBLE ... £1.05
ACOS GP94 STEREO CER. ... £1.90
ACOS GP95 STEREO CRYST. ... £1.35
9THAC SONOTONE STEREO CERAMIC (DIAMOND) ... £2.00
ACOS GP67/2C MONO CRYST.65
ACOS GP101 COMP. CRYST. 19-TI SONOTONE STEREO CRYSTAL90
POSTAGE 5p per CARTRIDGE

Microphone Bargains
MIC45 "ACOS" metal case, crystal hand95
CM 20 Crystal Hand45
DX143 Dynamic, cassette-type stick ... £1.00

Microphone Bargains—continued
MIC60 "ACOS" stick crystal ... £1.00
CM70 PLANET stick metal, switch crystal ... £1.45
DM60 Dynamic uni-dir, ball metal ... £3.75
UD130 50K/600 OHM uni-dir, ball metal ... £4.50
TW209 LESSON DUAL IMP ball metal, uni-dir. ... £5.75
GUITAR MIKE45
LAPEL TYPE, crystal40
POSTAGE 17p each.

Amplifier Modules
One valve chassis Amplifier for record player 2 Watt output, volume control and tone control, on/off switch, £3.50 (P. & P. 25p).
3 Watt mono Audio Module (Transistorised) £2.50 (P. & P. 10p).
15 Watt Mono Audio Module (Transistorised) £3.95 (P. & P. 10p).
3 Watt Stereo Module (1 1/2" Watt/Channel) £3.75 (P. & P. 10p).
5 Watt Stereo Module (2 1/2" Watt/Channel) £5.50 (P. & P. 15p).

Stereo Headphones
De-Luxe finish 8-16 Ohm Matching imp. mono/stereo switch complete with lead and stereo jack plug only £2.75 (P. & P. 25p).

NO STEREO PHONO SOCKET!
Headphone Adaptor only £1.35 (P. & P. 10p)

Tapes — "MYLAR" base finest quality British made.
5" 600 ft 36p 5 1/2" 1800 ft 85p
5" 900 ft 45p 7" 1200 ft 55p
5" 1200 ft 80p 7" 1800 ft 80p
5 1/2" 900 ft 49p 7" 2400 ft 95p
5 1/2" 1200 ft 55p
POSTAGE 9p each.

THIS MONTHS SPECIAL OFFER
Converts your battery operated radio or cassette recorder to mains 'Binatone Battery Eliminator' 230V in 6 or 9 Volts out. Only £1.99 (P. & P. 10p).

SEND 25p FOR COMPLETE CATALOGUE

RIVERSDALE ELECTRONICS

Mail Order Department W2/73, P.O. Box 470, Manchester M60 4BU

ALL OUR MERCHANDISE IS FULLY GUARANTEED

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDEGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 4285

The T.V. Graveyard of the North, as seen on T.V. Close to the Motorway. Plenty of Free Parking Space. Call in and see us any day 9-6. Closed Sunday. Est. 1935.

NEW TOP QUALITY MAINS TRANSFORMERS. 250v-0-250v at 80mA. 6.3v at 4amp. Not to be missed at £1.50 Post Paid. Weight 10lbs.

ONLY 40 OF THESE SO HURRY. Grundy Transistor Tester. Tests PNP & NPN Types. Base Current 10-500uA, Leakage, Gain etc. Clean Condition but Untested. Less Battery and Meter. £1.30 Post Paid.

This is a Nice Unit. Portex X-Ray Unit Model 3. Mains Operated. 2, 3" Meters 0-250v and 0-20mr. 0-12Sec. Timer. Untested £2.50 Carriage Paid. Good Breakdown Unit.

STUDENTS' WIRELESS PROCEDURE TRAINING SET. Comprising: Mike, Single L.R. Phone and Connector. In small Wood Case. Good Condition, but Untested. A Gift at £1.25 Post Paid. Complete Untested T.V. Sets, with Back and all Valves, BBC1 and ITV 17" 90° Tube £2. 17" 110° Tube £3. 19" Slim £5. Carr. and Ins. £1.50.

Reclaimed T.V. Tubes. All with 12 Months' Guarantee. AW43/88 £1.50. AW43/80 £1.50. MW43/69 £1. Many other Types in Stock. Carriage and Ins. on any Tube £1.50.

Latest Air Ministry Release. Radio Receiver Type R4187. 2.8 to 18MHz. In Three Bands. With 17 Miniature Valves, 26 Volt Motor Power Supply. Motor and Manually Tuned. Very clean less Crystals and Untested £5. Carr. and Ins. 75p.

Ex Equipment Valves. All Tested on our Mullard Valve Tester before despatched. 3 Months' Guarantee on all Valves. Single Valves Post 3p, over Post Paid.

ARPI2	5p	PCF80	5p	PY82	8p
EB91	4p	PCC84	5p	PY33	17p
EF80	8p	PCL82	12p	U191	20p
EF85	12p	PCL83	12p	6BW7	10p
EBF89	12p	PCL84	12p	6U4	10p
ECC81	10p	PL81	17p	20P1	15p
ECC82	12p	PL82	8p	20P3	10p
ECL80	8p	PL83	8p	30F5	10p
EF50	60p per doz.	PL36	17p	30FL1	20p
EF91	4p	PY81	8p	6/30L2	20p
EY86	20p				

SAXON ENTERTAINMENTS.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES
FOR DOMESTIC & COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2.95 carr. free

25 WATTS RMS. 7 transistors 7 diodes

SA35 £4.45 carr. free

35 WATTS RMS. 7 transistors 7 diodes

SA100 £10.90 carr. free

100 WATTS RMS. 11 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000 Hz \pm 1dB
Distortion	0.2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	25-45 volts SA25/35 40-70 volts SA100
Size	4 1/2" x 4" x 1" (SA100) 4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

Stab PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
PU70	Unstabilized supply for one or two SA100	£7.75 carr. 40p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON
GLASS FIBRE P.C. BOARD
AND ARE SUPPLIED FULLY TESTED

OTHER SAXON PRODUCTS...

120 WATT HEAVY DUTY MODULE **£13.90** + 20p carr. or with supply **£18.95** + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

SPECIFICATION

Power output 120 watts into 8 ohms
Freq. response 20-20,000 HZ \pm 2dB
Input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)
Low distortion parallel push-pull output stage.



NEW £27.90
160 watt version & supply

SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



SPOT BANKS INCLUDING 3 SPOTS
STATE COLOURS: RED, BLUE, GREEN.
£8.90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue stelvite hooded cover. Fully guaranteed.

£19.75 carr. 30p

MONO VERSION **£6.50** carr. 20p (As illustrated left S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



£15.80 carr. 30p

SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. **THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic input.)

COMPLETE AMPLIFIERS

The CSE 100. **£34.90** carr. free

This versatile unit is now available in a black vyndie case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.'s., etc.



The SAXON 100 **£48.50** carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms **£5.95** carr. 30p. 15" 50W.8/15 ohm **£14.50** carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm **£11.50** carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use.

D11DHL rrp **£11.00** our price **£9.45** post free
D190C High Z rrp **£21.50** our price **£17.45** post free
D1000C 24 ct gold plate rrp **£37.00** our price **£32.00** post free

SEND SAE FOR
OUR A.K.G. PRICE
LIST. DISCOUNTS
ON ALL MICS.

CALLERS & MAIL ORDER:

351 Whitehorse Rd.,
West Croydon, Surrey.
CRO 2HS 91-689 3885

CALLERS ONLY:

OUR NEW
DISTRIBUTORS

CIRCLE SOUND,
325-330 The Banks, Rochester.
Medway 404199

BUSINESS HOURS:

9.30 a.m.
to 5.30 p.m.


TERMS OF BUSINESS:

C.W.O. or C.O.D. (35p extra)
All cash in regd. envelopes please!
Telephone orders to our CROYDON BRANCH.
TRADE & EXPORT enquiries invited.



I.L.P. (Electronics) Ltd

THE HY41

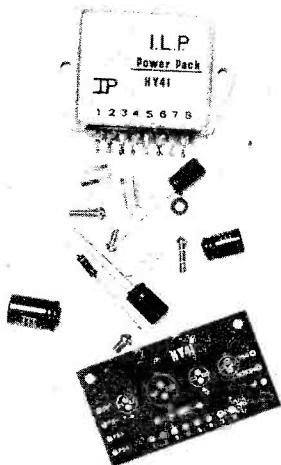

The HY41 supersedes the popular HY40 introduced by ILP last year. This highly improved module achieves true High Fidelity with a dramatic reduction in distortion (typically 0.05% at 1KHz into 8 ohms!) and is electronically and mechanically compatible with the HY40.

With this important improvement the HY41 retains all of the quality characteristics found in the earlier version and P.C. board, Resistor, Capacitors, Hardware Mountings and comprehensive manual are included in the basic kit. No further components are required to construct a complete power amplifier of extremely high performance sufficiently versatile to provide power not merely for Hi-Fi but also for public address systems and industry.

The free manual gives a full circuit diagram of the HY41 and its various applications including a complete stereo amplifier.

Like its predecessor the HY41 is based on conventional and proven circuit techniques developed over recent years.

OUTPUT POWER: British Rating 40 WATTS PEAK, 20 watts R.M.S. continuous.

LOAD IMPEDANCE: 4-16 ohms.

INPUT IMPEDANCE: 30K ohms at 1KHz.

VOLTAGE GAIN: 30db at 1KHz

TOTAL HARMONIC DISTORTION: less than 0.15% (typical 0.05%) at 1KHz.

FREQUENCY RESPONSE: 5Hz-50KHz \pm 1db.

SUPPLY VOLTAGE: \pm 22.5volts D.C.

SUPPLY CURRENT: 0.8 amps maximum.

PRICE: inc. comprehensive manual, P.C. board, five extra components and P. & P.:-

MONO: £4.90

STEREO: £9.80

UNIQUE HYBRID PRE-AMPLIFIER

The HY5 has rapidly established a position in the WORLD as the sole hybrid pre-amplifier to contain all feedback and equalization networks within an integrated pre-amplifier circuit.

Supplied with the HY5 are two stabilizing capacitors and by the addition of volume, treble and bass potentiometers it is ready for use.

Internally the HY5 provides equalization for almost every conceivable input, the desired function is achieved by use of a multi-way switch or by direct interconnection.

Two distinctive features of the HY5 are its inbuilt stabilization circuit, allowing it to be run off any unregulated power supply from 16-25 Volts and a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo pre-amplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY41 and PSU45 forms a completely integrated system.

INPUTS

Magnetic Pick-up (within \pm 1db RIAA curve) 2mV, 47K Ω

Tape Replay (external components to suit head), 4mV, 47K Ω

Microphone (flat) 10mV, 47K Ω

Ceramic Pick-up (equalized and compensatable) 20-2000mV, variable.

Tuner (flat) 250mV, 100K Ω

Auxiliary 1 250mV, 47K Ω

Auxiliary 2 2-20mV, 100K Ω

OUTPUTS

Main Pre-amp output 500mV.

Direct tape output 120mV.

ACTIVE TONE CONTROLS (Bexendall)

Treble + 12db.

Bass + 12db.

INTERNAL STABILIZATION


Enables the HY5 to share an unregulated supply with the Power Amplifier.

SUPPLY VOLTAGE

16-25 volts

PRICE: MONO: £3.60

STEREO: £7.20

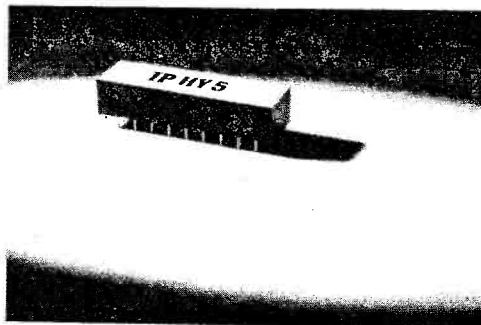

SUPPLY CURRENT

6mA approx.

OVERLOAD CAPABILITY

better than 26db on most sensitive input infinite on tuner and auxl.

OUTPUT NOISE VOLTAGE: 0.5mV.

POWER SUPPLY PSU45

The versatile P.S.U.45 is designed to supply your HY41's +HY5's in stereo or mono format.


Specification

Input: 200-240 Volts.

Output: \pm 22.5 Volts at 2 amps.

Overall Dimensions: L. 7"; D. 3.8"; H. 3.1"

PRICE: £4.50 inc. P. & P.

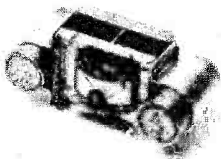

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

PRACTICAL WIRELESS

VOL 48 NO 10

Issue 792

FEBRUARY 1973

Letter from your new Editor

AT the time of going to press we have seen the last of the Apollo series of manned space flights to the moon. Fifteen years ago when the USSR launched *Sputnik 1*, followed by the U.S. launching of *Explorer 1*, little did many people imagine what space research could do to provide further knowledge and skills for everyday living. One could comment in depth on this, but rather than indulging yet again in retrospect, let us look to the future.

NASA space programmes are to be directed towards space laboratories in which man can examine the influences of near sterile conditions on terrestrial activities. Already it is expected that crystal growth in a space laboratory will be tried, so perhaps we who have a particular interest in semiconductor technology will again reap the benefits of such an exercise.

* * *

On a more domestic note, following the celebrations of 50 years broadcasting, further progress is being made to improve communications: The IBA have now used their colour programmes digital converter in service; stereo is established on Radio 2 (v.h.f.), although there is apparently some unexplained mono material intruding; the planning of commercial radio is well underway; the third Goonhilly dish has increased the international telephone capacity to handling almost half of Britain's 60 million calls by satellite; the first UK i.c. radio chip receiver design for home constructors has been published; the BBC has announced the CEEFAX news service for television.

We shall be taking a closer look at the world of communications inside and outside the home; giving you up-to-date information on components and equipment; extending our popular ranges of simple-to-build projects; encouraging readers to participate with us in do-it-yourself communications.

* * *

Many of you will have followed the writings of your new editor elsewhere. To PW newcomers we welcome you to the club; we hope to provide plenty to stimulate your interest in future issues. In the meantime, we are always interested to hear your views on matters appropriate to the magazine. We are also convinced that a great deal of talent exists among the readership in designing projects, as is evident from our correspondence. If you feel that you would like to show others what you do, drop us a line; better still, how about writing it up into an article.

M. A. COLWELL—Editor

**THE MARCH ISSUE WILL BE
PUBLISHED ON FEBRUARY 2nd**

NEWS AND COMMENT

Leader	889
News . . . News . . . News . . .	890
Letters	902
Practically Wireless by Henry	908
CQ! CQ! CQ!	919
On the Short Waves	
by Malcolm Connah and David Gibson, G3JDG	925
MW Column by Charles Molloy	934
Electronotes by S. Ginsberg	934

CONSTRUCTIONAL

VHF Signal Generator	
by R. H. Longden	896
Experimenters Corner,	
Novel 'Scope Calibrator,	
by J. A. Nekrews	898
10 + 10 Watt Stereo Amplifier,	
Part 2, by W. Cameron	905
3-Range Crystal Marker	
by R. F. Graham	909
General Coverage Receiver	
by F. G. Rayer, G3OGR	912
9V Battery Eliminator by M. Wallis	920
Take 20, No. 45, Signal Injector/Tracer,	
by Julian Anderson	922

OTHER FEATURES

Guide for Constructors by V. Capel	892
IC of the Month, SGS TBA231 Audio Preamplifier, by L. A. J. Ireland	901
Going Back by Colin Riches and Arthur Dow	929
Using Zener Diodes by J. N. Watt	932
Transistor Circuitry for Beginners, Part 14, by H. W. Hellyer and Michael Hollier	937

©IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.


by
Colin Riches

KW catalogue

A new catalogue has just been released by KW Electronics Ltd., Specifications and pictures of KW transmitters, receivers and associated equipment are shown and a price-list is included.

Free copies of this catalogue may be obtained by writing to KW Electronics Limited, Dartford, Kent.

Ignition system

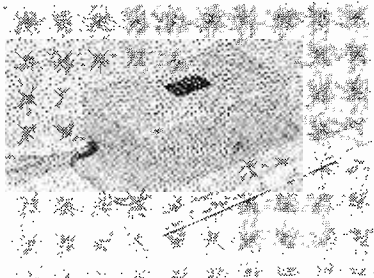

Future Techmatics announce a new low-cost capacitive discharge ignition system, named "Highwayman" and designed for both the fleet owner and the private motorist. The unit priced at £9.90 plus 35p postage is claimed to give fuel economy, improved performance and excellent starting under adverse conditions.


Fitting is simple with only three wires to connect. Using the conventional coil and contact breakers, "Highwayman" produces well over 30,000 volts to the spark plugs with a rise time of 2.6 microseconds. Maximum operating rate is 600 pps. Battery drain is 1.5 amps. The contact breaker resistance limit is 25 ohms and current and voltage at contact breakers is 0.15 amps at 12V.

Further information on the range of electronic ignition systems and other devices, may be obtained from Future Techmatics Limited, Waldeck House, Waldeck Road, Maidenhead, Berks.

Solder feed

The Mark 3 Anextra includes several improvements to simplify its main function of eliminating the need for "three hands" when soldering. The reel of solder, 18 to 22 gauge is contained in the pistol grip which is easily attached to most types of soldering iron.

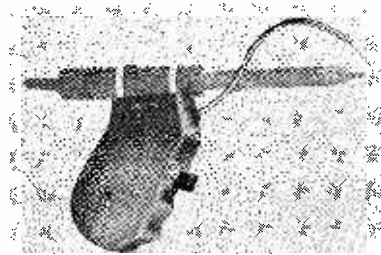The maximum 4oz. reel of solder is easily changed. The amount of solder fed by each pressing of the trigger is quickly adjusted to suit the joints being made. The operator thus holds



both the iron and solder in one hand, being free to hold the work with the other hand.

Supplied with a 1oz. reel of 60/40 22 s.w.g. solder, with simple instructions, the Anextra is £3.75 post free U.K., direct from the makers. If you send an s.a.e. you can obtain a leaflet on the unit. Anextra Ltd., Chiltern Works, Rear of 77/78 Chiltern View Road, Uxbridge, Middx.

Working /MDS

Who ever heard of a radio Amateur going mobile on a dog-sled?


I didn't believe it at first but here's the full story:

Having supplied quantities of radio equipment to the South African Antarctic Expedition, Racal Electronics is naturally in fairly close touch with events and told us of the claim by one of the Expedition's members to have effected the world's first radio contact (QSO) by an amateur from a dog-sled mobile installation. The QSO was achieved on 7MHz between the sled in Antarctica and a station in South Africa. Racal has supplied the Expedition with a number of TR.28 h.f. transceivers which it uses for mobile applications.

The Expedition's base station (call sign ZS1ANT) which is equipped with Racal transmitter and receiver, is in the charge of Frank Schneider, a radio ham who operates most evenings between 1600 and 1900 GMT on s.s.b. at about 14.30MHz (call sign ZS6GE). As Antarctica is classed as a separate continent for many amateur radio certificate awards, a contact with Frank is considered a rare achievement and so his QSL cards confirming radio contact are in great demand among the world's radio amateurs.

If any U.K. hams manage to contact ZS1ANT, the address for QSL cards is 5 Prinshof Street, Pretoria, South Africa, or via the SAARL QSL Bureau.

New Mechanics

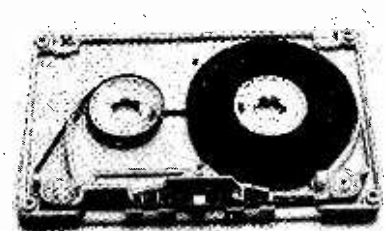

The range of "LH" (low, noise high output) ferric oxide compact cassettes from BASF is available with the patented Special Mechanics (SM) developed by BASF technicians in West Germany.

The Mechanics comprise two plastic tusks and a roller system which together guide the tape on and off the spools. They ensure constant free running of the tape and eliminate jerking caused by static.

The improvement in tape running is most noticeable with C120 cassettes which, because of their extreme tape length of over 56 feet and thinness, are prone to running difficulties.

Recommended retail prices, including purchase tax, of the LH SM cassettes are 81p (C60), £1.11 (C90) and £1.51 (C120). BASF United Kingdom Limited, P.O. Box 473 Knightsbridge House, 197 Knightsbridge House, London, S.W.7 1SA.

Ronson Blowtorch



Ronson Products Ltd., the people that make the lighters and shavers recently let me have a look at their blowtorch.

It's hardly the sort of unit you would use on a transistor p.c. board or anything requiring delicate soldering but for heavy soldering jobs, it's ideal.

With its micro-adjustment to give a precision choice of flame size and heat intensity, the Blowtorch when used with its copper soldering tip can undertake relatively fine soldering jobs on metal, wire splices, pipes and tubing, etc. It's ideal, too, for bending or fashioning glass, metal tubing and rod and for all types of hand forging, shrink fitting, enamelling or light brazing.

The range of Ronson Blowtorches is made up of three models. All are supplied complete with the large capacity Hi-Heat butane refill. The standard pack costs just £2.45 or with copper soldering tip at £2.79. The complete Blowtorch kit—at £3.99—comes with three handy attachments (soldering tip, flame spreader and diffuser head) all neatly contained in a packaway case, as can be seen in the photograph. *Ronson Products Ltd., Leatherhead, Surrey.*

"Texan" Reprints

Reprints of the "Texan" 20+20W Stereo Amplifier are available.

They may be obtained by sending 35p (30p+5p postage/packing) to "TEXAN" REPRINT, c/o Chief Cashier, Practical Wireless, Tower House, Southampton Street, London WC2E 9QX.

Electrovalue cat.

Electrovalue have sent me their catalogue No. 6—already in its third printing. Including i.c. circuit and connection diagrams as well as semiconductor outlines and technical gen, the catalogue contains many other interesting items plus a purchase refund voucher for the 25p it costs to buy.

Copies can be obtained from *Electrovalue Limited, 28 St. Judes Road, Englefield Green, Egham, Surrey.*

Bib test cassette

Bib recently let me hear their Hi-Fi Stereo Test Cassette which is entitled, "How to get the best stereo and mono reproduction and recording".

The tape, devised by Richard Arbib, managing Director of Bib Sales is recorded by Decca using the Dolby system.

The Max Harris Jazz Trio play some specially composed pieces, illustrating tests including balance control, channel identification speaker phasing, reducing tape hiss and adjusting record volume controls.

Members of the Trio, playing six instruments are used to check cassette recorder reproduction over a wide frequency range.

Side 1 of the cassette deals with reproduction and side 2 with recording. Other advice and tests include wow and flutter, movement between channels and how to clean tape heads.

To illustrate various points, excerpts from Bach's Toccata and Fugue in D minor and Khachaturian's Spartacus are given together with excerpts from Vivaldi's "The Four Seasons" and some Gilbert and Sullivan operas to illustrate high quality sound.


This cassette represents a very useful addition to those who like me suffer from "cassette-itus" and a none too perfect stereo system.

The Bib reference for the cassette is "53" and the price £2.25. The tape plays for 50 minutes, which represents an extra 25% of playing composed with a standard Musicassette. *Bib Division, Multi-core Solders Ltd., Hemel Hempstead, Herts.*

Litesold's latest

Light Soldering Developments inform us that they have marketed two new devices. Both are for use with their ETC/1 temperature-controlled and Conquerer irons. The De-Soldering Unit (priced at £.75) slips onto the iron and converts it to a self-contained de-soldering tool.

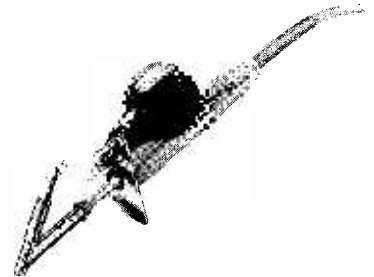The i.c. De-Soldering Head, at £2.25, slips on in place of the soldering bit to give simultaneous de-soldering of all leads of 14 and 16 way dual-in-line i.c.'s. *Light Soldering Developments Ltd., 28 Sydenham Road, Croydon, CR9 2LL.*



De-soldering unit

Digital Clock

The 24 hour digital clock shown on the cover this month is mains driven and incorporates an alarm buzzer. It can be obtained from Sternway Electrical Ltd., 111 Fleet Street, London EC4, for £7.95 plus 25p post and packing.

The "CQ" Column

Just a little reminder about the CQ Column. As readers write in, I put all their letters in strict order so that it is a case of "first come, first served." Requests for entries in this column now number many dozens a week and as we cannot always include a "CQ Column" in every issue of *P.W.* there is often some delay before the items appear.

Should there be any immediate urgency for a mention to appear, our Advertising Department will be pleased to accept "small ads" for a small charge.

Guide for Constructors

V. CAPEL

EACH issue of both *Practical Wireless* and *Television* carries articles of a constructional nature. With any hobby or interest, the greatest pleasure and reward comes from participation, having a go oneself rather than just reading about or examining the work of others. Thus these constructional features fill a very necessary need and are widely appreciated.

However, modern radio and television techniques are of a complex nature, and it is understandable, that in spite of the clear description, circuit and layout diagrams, readers sometimes get into difficulties, resulting in a written plea for help to the Editor, who in many cases refers it back to the writer of the original article. Many of these difficulties and queries though, would not arise if certain basic principles and precautions were observed. This article is designed to assist constructors prevent problems before they arise.

COMPONENTS

First we will consider the components. It is always best to obtain **all** the components at the start, if at all possible. If any are left out, to be obtained later, it means that the tags or print where they would be connected are left unordered and therefore adjoining components are left high and dry. If the omitted component is used as an anchoring point such as a transformer or can electrolytic, then it will not be possible to fit the associated components at all. Where a number of parts are deferred in a complex circuit it is very likely that one or more may be overlooked altogether, and considerable trouble caused in trying to get the circuit to work before the omission is discovered.

Having gathered the components together it is wise to check them for faults. Unfortunately, there is always a percentage of new parts that are defective, as each one cannot be individually checked by the maker. Small though the percentage may be, it means that somebody is going to get one, and that could be you!

Transformer windings should be checked for continuity, and then with the ohmmeter switched to its highest range, check for leaks between windings, and between windings and core.

Capacitors are the most likely source of faults especially the miniature electrolytics used in transistor circuits. These should be checked for leaks; some leakage may be found using the high resistance range of the meter, but it should not be very much. If in doubt compare with other electrolytics. Any giving a substantially lower reading than the others should not be used. Of course, a lower reading will be obtained with the meter polarity connected the wrong way round; usually, the polarity on the ohms ranges is **opposite** to that for the voltage and current ranges.

While leaky capacitors are more common than open-circuit ones, the latter condition can be tested for by observing the meter needle kick when the capacitor is connected across it. The larger the value of the capacity the greater the kick, so with low values a response may not be observed. It will not be necessary to check the values on a bridge; if it is not leaky or o/c, the value will probably be right.

Assuming the colour code markings are clear it is very rare for a resistor to be of incorrect value or o/c so these can be taken for granted, especially if there is a large number and checking them all would be rather tedious. However, circuits where close tolerances are necessary such as measuring and test equipment, may demand the individual checking of appropriate resistor values. Also very high values are worth checking as these are generally less reliable than the lower ones. Resistors with dubious markings should be checked.

TOLERANCES

Sometimes queries are received about tolerances and capacitor voltage ratings showing that these limitations are not always understood.

The tolerance means the amount by which the value may deviate from that stated. Thus a 100Ω 10% resistor may be anything from 90 to 110Ω in value. Resistors may be obtained in 1%; 2%; 5%; 10% and 20% tolerances, the 5% ones being indicated by a gold ring and the 10% ones by a silver one. In most practical circuits values of resistance are worked out and then taken to the nearest preferred value, so in most cases the values are not very critical. Unless otherwise stated, the 20% tolerance will be satisfactory, but of course if closer tolerance resistors happen to be available they can be used. The closer the tolerance, the higher the cost, so it is a waste of money using close tolerance components where they are not needed.

If close tolerance is specified in the components list, then the circuit is more critical and the stated tolerance should be used. If for some reason a close tolerance component of the value required cannot be obtained, but there are some of that value with larger tolerance to hand, check these with a meter. It may be that they could fall within the required tolerance. A 20% resistor does not mean that it is **bound** to be 20% outside the stated value, only that it **may** be. The error is guaranteed to be less than 20%. Thus it is often possible to select by measurement a 20% resistor that is spot-on in value, or nearly so.

Critical circuits often contain a preset control which must be set to give a specified voltage or

current. Thus the resistors associated with that part of the circuit need not be of close tolerance. In fact, different values that are near to those specified can be used at a push, because the preset will compensate.

The same thing applies to capacitors. Many electrolytics are rated at -20% $+100\%$ which means that they may be up to 20% less or 100% more than the stated value. It is usually better to have a little more capacity than less, especially where decoupling circuits are concerned. Some capacitors are available that are -20% $+50\%$ if a closer tolerance is required. It can be seen from this that the average electrolytic is likely to be rather higher than its stated capacity. It is also obvious that values are not too critical, so if the required value is not available, the next highest can generally be used. Thus $50\mu\text{F}$ can be used in place of $25\mu\text{F}$, and $16\mu\text{F}$ in place of $8\mu\text{F}$.

Paper and polyester capacitors are usually 20% or 25% tolerance, although for special purposes where accuracy is important 5% tolerance or better can be obtained. As with resistors, if a bridge is available, it is often possible to select from a number one that is quite close to the required value.

Ceramic capacitors are usually made with wide tolerance ratings; -25% $+50\%$ is common where value is not too important but a little more rather than a little less is preferred. Such can be used for r.f. decoupling purposes, 1000pF. to 3000pF. being common values. Ceramics can be obtained in the lower values at 10% tolerance or better and these or mica capacitors should be used for tuned circuits and similar r.f. applications.

It may be felt that these tolerances are rather wide, but remember that they are the maximum permissible deviations for the category. Most components will be found to be well within the tolerance rating.

VOLTAGE RATINGS

The voltage rating of capacitors seems to be something with which some readers have difficulty. For d.c. circuits it means simply that the applied voltage must not exceed that for which the capacitor is rated. The minimum rating then, must be the applied voltage plus a safety margin. Thus with a 200 volt h.t. line all h.t. capacitors should be 250 volt working minimum. Lower voltage working capacitors can be used elsewhere such as for cathode bias bypass. For the earlier stages this may be a few volts but output stages run at up to 20 volts bias normally, so 25 volt working capacitors should be suitable. With some stages the bias is higher, and 50 volt capacitors must be used, but these are also often used with lower bias voltages to give a higher safety margin.

The miniature capacitors used with transistor equipment come in various low-voltage ratings. Again, the rating can be selected by considering the supply voltage and circuit position. If the battery voltage is 9 volts, then a rating of say 12 volts or higher would do for any circuit position. Lower voltage ratings can be used for emitter capacitors, usually 6 volt being ample here. Coupling capacitors in both valve and transistor equipment can be rated at about half the supply voltage but it must be remembered that a fault condition may put the

whole of the supply voltage across the capacitor, so it is best to use one rated for the full supply voltage.

With one make of record-player, the designers slipped up on this point. It was valved, but with a silicon rectifier. A 150 volt coupling capacitor was used which was amply rated for normal running. When the player was first switched on the supply voltage was instantly available, before the valves had warmed up. This meant that around 250 volts appeared across the capacitor during this period. Needless to say a number of these players found their way into the workshop with short circuited coupling capacitors!

Note from what has been said before, that the capacitor voltage rating **must not be exceeded**. This means that one with a higher rating than is necessary can be used if the desired rating is not available. The higher the voltage, the more bulky the capacitor and with some exceptions, more costly. Generally though, size is the main consideration. If the equipment is small and the space limited use the lowest voltage rating consistent with requirements, but if space is not at a premium, higher ratings can be used if desired.

For a.c. or pulse circuits, the capacitor must be considerably uprated. The peak value of an a.c. sine wave is 1.4 times that of the r.m.s. voltage. The peak-to-peak voltage then will be 2.8 times, so a capacitor should be rated at three times its d.c. working voltage. Thus for 250 volts a.c., a 750 volt working capacitor would be the minimum. Usually, 1000 volt capacitors are used to give a good safety margin.

CONSTRUCTION

Having selected and obtained our components, there are a number of points to watch for when fitting them. First, check the colour coding of resistors and that you are reading them the right way round. For example, a 270k Ω (red-violet-yellow) can be mistaken for a 4.7k Ω (yellow-violet-red) if the coding is read from the wrong end of the resistor. Also, a 1.2k Ω (brown-red-red) resistor can be mistaken for a 220 Ω (red-red-brown) one. With the preferred values now in use, these are the only "back-to-front" mistakes that can be made, so be careful when handling resistors. With many resistors, especially in the smaller wattages, mistakes can easily be made. Make sure too, that the colours are what you think they are. Some markings in orange are quite deep in tone and can be mistaken for red, particularly when viewed in artificial light.

Another mistake that can easily be made is to wire in polarised components incorrectly. We all know that electrolytic capacitors should only be connected one way round, but when fitting a large number of parts to a printed board it is easy for the odd one to go in the wrong way round. Double checking is the only answer. Similarly, diodes have to be watched. If anything, it is easier to make a mistake here as the markings and shape of the very small ones are not easy to identify. The ring and rounded end with Mullard diodes indicates the cathode, but often the ring is indistinct, and the other end appears rounded as well.

It is best to work to a system in construction. Do all the mechanical operations first, drilling, cutting

circuit boards and fitting components such as transformers, controls and sockets. It is easy to have a mishap and damage some of the smaller components if any of this work is left to later. Wiring of the circuit can now begin. This should be done stage by stage, and when a stage is completed, go back and check component values, electrolytic and diode polarity, and trace through the connections (it is easy to solder a lead to the adjacent tag or printed strip to the one intended). Having satisfied oneself that the stage is wired correctly, then pass on to the next. If the construction has to be left (constructors have been known to go to bed at times!), try to complete a stage. This is a danger-time when errors and omissions can easily be made.

When re-starting it is prudent to check the previous stage again. All this checking may seem tedious and time-consuming, but even experienced engineers can and do make mistakes when constructing things and it is better to check and double-check rather than spend hours trying to correct baffling faults found when the equipment is first switched on.

Modern transistors are less heat-conscious than their predecessors, but they still can be damaged by too much heat. It is a good idea to leave the transistors in any particular stage as the last component to be fitted, then they cannot be affected by heat when soldering in adjacent components. When actually soldering the transistors, leave the iron on the connection only long enough to make a good joint. If for any reason it is not satisfactory and needs re-doing, leave it to cool for a few seconds before tackling it again. It is good practice to use a heat-sink whenever possible.

SOLDERING

When making a large number of joints it is possible that even the expert will make one or two "dry" joints. The only remedy is to be painstaking with each one and not to rush it. Wire-ended components are supposed to be ready tinned, but often solder will not take readily, and if they are soldered into print or to a tag, the solder will flow around the wire but take on the print and appear to make a good joint, but it will be bad inside.

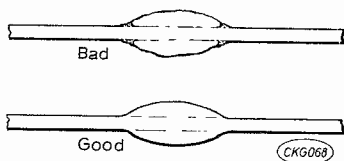


Fig. 1: Many dry joints exhibit an inward curve where the solder meets the wire (top). A smooth contour from wire to solder is usually the sign of a good joint (bottom).

Always tin the wire initially and see that the solder has taken all around before attempting to make a joint. This may mean that the wire must be scraped first. It is sometimes possible to tell a bad joint by the way the solder meets the wire. Reference to Figure 1(a) shows the solder curving inward where it meets the wire. This is due to surface tension in the solder when it was molten and shows that it has not taken on the wire because the solder had a separate surface. Often there will be traces of

resin from the solder core at the junction. In Figure 1(b) the solder has bonded itself to the wire and has no separate surface, hence there is a smooth flow from the wire to the bulk of the solder. This is not an infallible way of judging joints as the solder may have taken just at the point where the wire leaves the joint but not inside; or it may have taken inside, as in the first example, but not at the edge; but at least it does give a clue. A further check can be made by gently pulling or twisting the wire to see if there is any movement between it and the joint.

Excess solder must be guarded against, especially on printed circuits where there is a danger of it shorting over to adjacent print. A golden rule which should be observed at all times is never to interrupt the making of a joint. If the wire is pushed through the print or wrapped around a tag, and then one is called away without soldering the joint, more likely than not one will proceed with the next joint on returning. Time and again joints have been left unsoldered because of interruptions. If the house is burning down, let it, but make sure you finish your joint!

More could be said on the important art of soldering but it is hoped to make this the subject of a complete future article.

CIRCUIT BOARDS

There are several printed circuit methods available to the constructor. Veroboard is a popular one because it is versatile and ready to use. When cutting across a section of print to isolate it, remove a complete segment. Just cutting across with a blade may permit the solder to later bridge the cut, or the cut may not be complete to start with. Fig. 2 shows the right and wrong way.

Better still, use the proper spot-face cutter sold for this purpose. The physical mounting of the printed board may pose problems as it is desirable to have access to both sides for servicing. One successful method is to solder a tag board to a strip of unused print at the edge. The tags can then be mounted

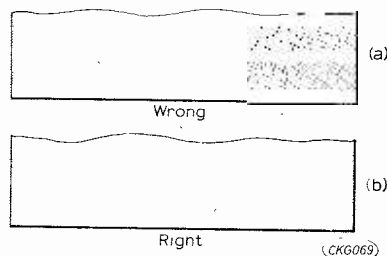


Fig. 2 (a) A narrow cut in a copper rail can be easily bridged with solder or dirt so a wide cut (b) is much preferred.

with nuts and bolts where required. This gives a vertical mounting with access to both sides the tags being bent to give the printed board any desired angle. Fig. 3 illustrates this arrangement.

Wiring should be done with solid rather than stranded wire, because it stays put and can be formed to give a much neater appearance. Bare copper wire can be used with sleeving, or as the usual plastic-covered wire. Whichever is chosen, it

is good to use different colours for different parts of the circuit. Quite a range of colours can be obtained. Red can be used for positive supply circuits, black for earth or negative; green for grid or base circuits; grey for a.g.c.; orange, unsmoothed h.t. and so on. This enables future testing to be so much easier, but stick to the coding once it has been decided upon.

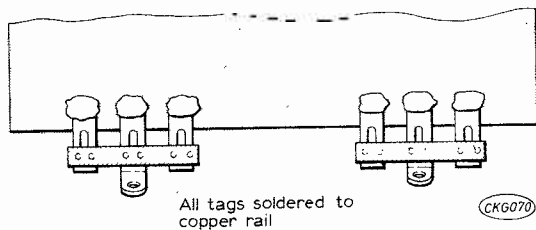


Fig. 3: Method of mounting Veroboard in a vertical position allowing access to both sides of the board.

It is a good practice to earth all appropriate components to one point in each stage. Furthermore, these points can then be linked and earthed to the chassis or frame at one point. This prevents h.f. chassis currents, in the case of radio equipment, leading to common impedance coupling and instability. With audio equipment it reduces the possibility of hum from the same cause. It is true that in many cases it may prove unnecessary, but like providing adequate decoupling, it is good preventive practice and difficult to carry out once the circuit has been wired.

TESTING

Having completed the building of the project, the time eventually comes for the first switch-on. It is not unknown for this action to be accompanied by a blinding flash, smoke or other disquieting phenomena! A simple precaution is to take a resistance reading across the power supply circuits before switching on. The initially low resistance reading should quickly rise as electrolytics charge up from the meter battery. (Remember, the positive side of the test meter is negative battery polarity). Any permanent low resistance must be investigated. Then, wire the meter, switched to a high current range, in series with the supply and switch on. An abnormally high current should prompt an immediate switch-off and examination.

It may be that in spite of all these precautions, the equipment constructed fails to work satisfactorily. Normal fault-finding techniques must now be applied to find the cause of the trouble. Voltage measurements find the majority of faults, so go to work with the meter, and with the aid of the published circuit diagram check to find if there are volts where they should be. Check too, as to whether the voltages are approximately correct. This will depend on the equipment and its function. As a very general rule with transistor stages, the collector voltage should be about half that of the supply, emitter voltage should be about 1 volt and the base should be about 0.1 volt higher than the emitter for germanium and about 0.6 volts higher for silicon transistors. With oscillators, emitter followers

and similar stages, voltages will be different from the above.

Directly coupled stages can be confusing and a fault in one can affect the voltages in another. Note though, that the base/emitter voltage difference is present as this forward bias is essential for the transistor to conduct, in normal circuits. Some low-current circuits, as used in the input stages of audio amplifiers, may use a high value resistor of $3M\Omega$ or so from base to collector, to supply bias, and the meter current will cause a much lower reading. This must be allowed for, or if available a valve-voltmeter should be used. Incidentally, when the equipment is working satisfactorily, it is a good idea to take all the voltages and note them down on the circuit, for future reference.

If there are still no results and the voltages seem right, then check through the signal circuits using some form of signal injection. However, by following some of the tips outlined here, construction will not be such a hit-or-miss affair, but one reasonably certain of immediate success.

MODIFICATIONS

Now we come to the question of modifications. Some readers may wish to add extra facilities or to tailor the equipment to their own particular needs. This sometimes leads to letters to the Editor or author requesting modification design details. Now while we try to help as far as possible, producing designs to order is something that cannot be undertaken. Not only is a good deal of time involved, but any theoretical design must be built and development work carried out before it can be passed as workable. Obviously this is not possible.

Minor modifications should be within the capabilities of most readers if they have read carefully the various theoretical and practical articles that regularly appear in radio magazines. More ambitious modifications could provide a subject for private research and experiment; really, with this hobby, there is more satisfaction and pleasure to be derived by experimenting and trying out one's ideas than there is by following a tried and tested circuit. A recommendation though, is to get the unit working as first planned, and then introduce the modifications. If they prove unworkable, one can then revert to the original. ■

Back Numbers Important Announcement

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of **Practical Wireless and Television**.

To ensure obtaining regular copies of these magazines readers are strongly urged to place a regular order with their local newsagent, or to take out an annual postal subscription.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

VHF Signal Generator

R.H. LONGDEN

WHEN it is necessary to adjust a VHF receiver or converter such as may be used for the 144MHz amateur band, a signal generator covering the required frequency is extremely useful. As an example, even a straightforward unit such as the 144MHz converter in the July 1972 issue of *Practical Wireless* has four circuits which must be tuned to about 144MHz. With such equipment, if all of the circuits are initially considerably off tune, it may not be easy to peak them for maximum noise or reception of signals which are not very strong. On the other hand, when a suitable signal is available, it is easy to trim all the circuits for maximum efficiency.

The generator described here is intended particularly for the frequencies from 105MHz to 170MHz, thus including the 2-Metre Band, but it can be used at frequencies outside these limits, and particularly for checking the coverage and alignment of converters and the simpler types of VHF receivers. It is a small, self-contained solid state unit, providing a modulated r.f. output.

GENERATOR CIRCUIT

In Fig. 1, Tr1 is the audio tone generator or modulator. The transformer T1 is connected in the correct phase to obtain audio oscillation and this modulates the r.f. oscillator, which is supplied through the winding 3-4 of T1.

Tr2 is the r.f. oscillator. L1 is tuned to the required r.f. frequency by VC1, which has a dial for logging frequencies. An adequate signal is generally obtained by having the generator near the equipment being adjusted, but output can be taken to an external lead by the loop L2, if desired.

With a crystal controlled converter such as that mentioned, reception must be at the correct frequency, because VHF signals can only come out at a particular lower frequency. In this particular converter, 144MHz is tuned at 4MHz on the receiver.


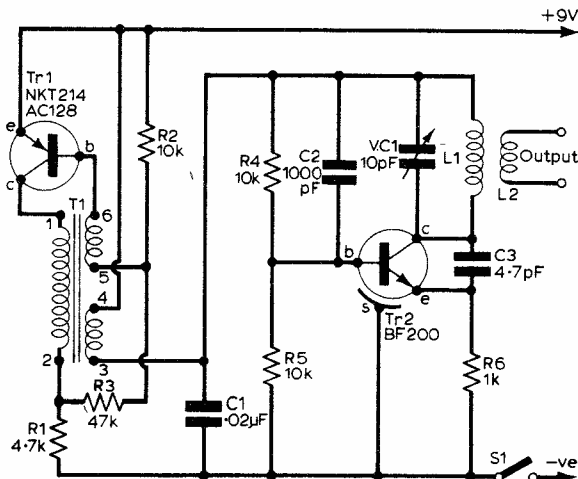


Fig. 1: The complete circuit of the VHF signal generator.

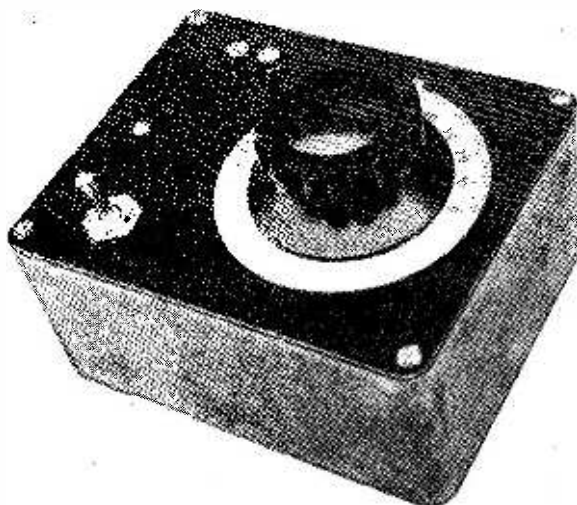

145MHz at 5MHz, and 146MHz at 6MHz on the receiver scale. So for adjusting such equipment, there is no real need for VC1 to be calibrated. Instead, VC1 is merely tuned until the VHF signal comes through the converter, which can then be adjusted. In other cases, it is helpful to calibrate VC1, in the way described. This will allow the frequency range of fully tunable equipment to be checked.

CONSTRUCTION

VC1, Tr2 and the associated items are assembled on a tag board about 1½ x 2 in. as in Fig. 2. As an alternative to the tag or group board, plain Vero-board with 10 pins inserted could be used, or eyelet board, or ¼ in. thick paxolin drilled to take the leads. Veropins will have to be snipped off nearly

★ components list

Resistors

R1	4.7kΩ	R4	10kΩ
R2	10kΩ	R5	10kΩ
R3	47kΩ	R6	1kΩ

All resistors 10% ¼W

Capacitors

C1	0.02µF disc ceramic
C2	1000pF disc or tubular ceramic
C3	4.7pF silver mica

Transistors

Tr1	NKT214 or AC128
Tr2	BF200 or similar VHF planar epitaxial transistor

Miscellaneous

VC1 Jackson C804 10pF
 T1 T/T3, 3.6:1 + 1 (R.S. Components)
 On-off switch
 Two small sockets
 Tag and insulated board
 Case about 4½ x 3½ x 2in. deep
 0-100 knob dial, KN1, Home Radio (Mitcham)

flush, as if this is not done the spindle of VC1 may not project enough to take the numbered dial.

The board is drilled for VC1. A washer is later put between this board and the panel, on the bush of VC1 and the bush nut then holds the whole assembly to the panel.

All connections in this section should be short, though the wires from Tr2 need not be cut down to less than $\frac{1}{2}$ in. Solder these rapidly after other wiring is taken to the tags, and use a heat shunt such as a pair of flat-nosed pliers on the leads while soldering.

L1 is chosen from the details given, for the coverage which is required. L2 is a single turn, some $\frac{3}{8}$ in. to $\frac{1}{2}$ in. from L1, and is the same for all coils.

This section can be tested by connecting the S1 lead to negative on a 9V battery and the lead which runs from C1 to 3 on T1 to a meter, which is clipped on the battery positive terminal. If the circuit is oscillating, current falls slightly when VC1 is shorted by placing a metal tool from moving to fixed plates. Actual current was 4mA, falling to about 3.8mA but this figure is not very important, and will depend on the particular transistor used. However, it is important that this change in current is found. If it is not, the circuit is not oscillating and no r.f. is produced.


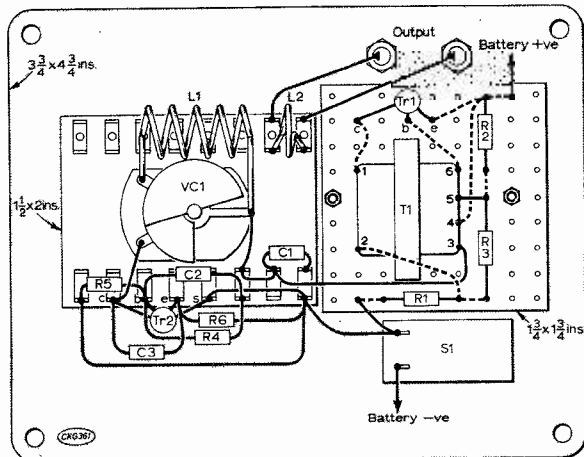


Fig. 2: The component layout.

With particular transistors in the Tr2 position, an upper frequency limit will be found, where oscillation grows weak and ceases. No particular difficulty arises in obtaining oscillation up to 180MHz or so. In fact, a number of transistors will work, and if the one fitted oscillates up to the highest frequency wanted, this is satisfactory. There is no point in using a transistor which could operate at a much higher frequency than required, as these cost considerably more than the popular types suitable for up to 180MHz. On the other hand, some cheap transistors which are supposed to be suitable for this frequency will cease to oscillate or become very inefficient. Should some particular VHF transistor be to hand, and not work with the values given, then the values at R4 (or R5), C3, and R6 may be changed to find if oscillation can be obtained.

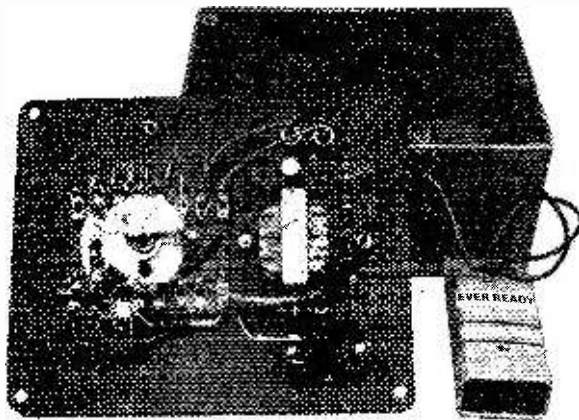T1, Tr1 and the three resistors are mounted on a piece of eyelet or other insulated board about $1\frac{3}{4}$ x $1\frac{3}{4}$ in. as in Fig. 2. Leave flying leads for the battery positive, S1 (battery negative) and from tag 3 of T1 to go to C1.



An internal view of the prototype.

This part of the circuit may be tested by connecting phones to 3-4 and applying 9V. With the components listed, a clear audio tone should be obtained.

Two countersunk 8BA bolts fix the board as shown. Spacers, nuts or washers are put between the panel and board.

The front panel should be made of paxolin. If it is metal, the bush of VC1 should be isolated from it with insulated washers. VC1 is fitted with a 0-100 degree dial, or with a control knob allowing markings to be made on a paper scale fixed to the panel.

The case was a die-cast box $4\frac{3}{4}$ x $3\frac{3}{4}$ x 2in. deep, but a small plastic lunch-box or other case will do equally well. L1 is placed so that it is well clear of metal when the panel is fitted to the box.

L1, FREQUENCY AND CALIBRATION

Exact coverage will naturally depend on individual layout and the length of leads, but should be reasonably close to the figures given. The frequency is lowered by using more turns on L1, by winding L1 to a larger diameter, or by compressing L1 so that its turns are closer together. Fewer turns, smaller diameter, or stretching raises the frequency. In all cases L1 is of 20s.w.g. tinned copper wire, self-supporting. Details of L1 are:


- 105-125MHz: 5 turns, $\frac{1}{2}$ in. outside dia. and $\frac{5}{8}$ in. long. Ends $\frac{3}{8}$ in. and $\frac{5}{8}$ in. long.
- 125-148MHz: 5 turns, $\frac{3}{8}$ in. outside dia. and 1in. long. Ends $\frac{1}{8}$ in. and $\frac{1}{2}$ in. long.
- 148-170MHz: 4 turns, $\frac{3}{8}$ in. outside dia. and $\frac{1}{4}$ in. long. Ends each $\frac{1}{2}$ in. long.

Where a crystal controlled converter is available, or a VHF receiver, these will furnish calibration marks through the ranges they cover. This may prove handy when building other, fully tunable VHF equipment.

The VHF enthusiast can calibrate the oscillator by using a Lecher line and measuring the length of this to find the wavelength in metres. This is practical at these frequencies as the line will only be up to three metres or so long, and resonance produces a dip in battery current.

For some lower frequencies it may be possible to pick up the signal when the generator is tuned so that a harmonic is heard in the receiver. Second harmonic reception will arise when the generator is tuned to one-half the receiver frequency.

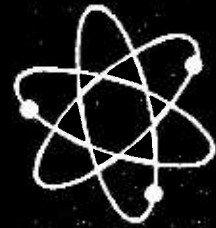When some calibration points have been obtained, these can be entered on a scale or list, or on a graph which will give intermediate frequency readings. ■



NOVEL 'SCOPE CALIBRATOR

J. A. NEKREWS


THE instrument to be described will work well with virtually any oscilloscope and facilitates the voltage calibration of both the X and Y axes in one simple operation. It is easy to build and use and the total outlay, including a suitable case, should not exceed £2.

CIRCUIT

The circuit is basically a conventional phase-shift network with the addition of resistors R2 and R3, and zener diodes D1 and D2. The values of C1 and R1 were found by experiment to give an almost perfect circle output from the phase-shift network. Addition of the zener diodes clips the alternative half cycles and produces the rather novel square display as shown in the photograph. Resistors R2 and R3 simply limit the zener current to an acceptable level and eliminate any chance of loading the phase-shift network. Provision of the ganged potentiometers allows the amplitude of the display to be varied from zero volts to the maximum zener voltage which in the prototype was set to be 5V.

Although a matched pair of zener diodes is to be preferred, odd diodes can be matched by inclusion of series resistance at points marked A and B on the circuit diagram. Indeed the constructor could use virtually any zener diodes that happen to be at hand as long as the nominal zener voltage is equal to, or in excess of, the maximum required for display. It will be found that the polarity of the zener diodes is of no consequence in this circuit, it will operate whichever way the diodes are connected. The prototype used Mullard OAZ201 5.1V types adjusted as above to provide exactly 5V. The rating of the diodes should be at least 250mW.

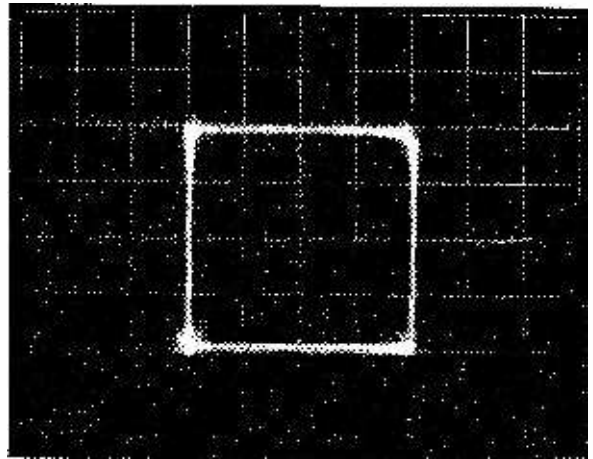The constructor is not hindered in any way in the construction of this instrument as the layout is by no means critical and there is considerable flexibility in the selection of components. Any transformer supplying 12-20V will suffice as the current required is negligible. A type MT98 9.0-9V available from



Henry's Radio is ideal as it is small enough for Vero-board or printed circuit board mounting. The ganged potentiometer should be a good quality type with a resistance between 500kΩ and 1MΩ. If the reader wishes, separate potentiometers, individually calibrated for each axis, could be used. Resistors R2 and R3 should not be reduced in value or the zener diodes may be damaged. The outputs can be taken via any type of terminals convenient to the constructor. No further constructional notes are considered necessary as the reader is free to use whatever form of construction that he (or she!)* finds most convenient. Of course there is no reason why the unit could not be incorporated as an integral part of an oscilloscope provided sufficient space is available.

CALIBRATION

Having constructed the instrument with an established 5V maximum output, the first step in calibration is to set the potentiometers for maximum amplitude and mark this point as 5V. Then adjust the oscilloscope gain controls until the display is ten divisions of the oscilloscope graticule on each side. This gives a display of 0.5V per division. Then, without touching the scope gain controls, gradually reduce the calibrator output by one division at a time marking the dial at 0.5V steps. You then have a reasonably accurate instrument capable of voltage calibration of both axes of your oscilloscope in a single operation.

There is ample scope for the constructor to tailor the unit to suit his own needs and for this reason constructional details have been cut to a minimum.

* Concession to Women's Lib.—Ed.

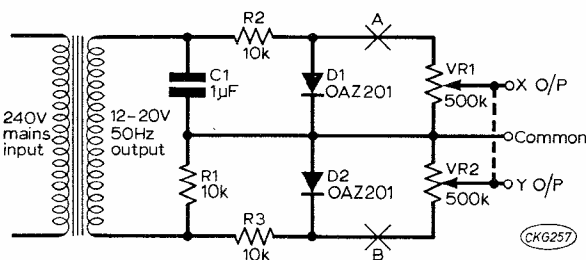


Fig. 1: The circuit of the 'scope calibrator.

The Catalogue you **MUST** have!

HOME RADIO COMPONENTS



250 pages 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ "

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p. plus 20p **POST AND PACKING**

POST THIS COUPON
with cheque or P.O. for 75p.

Name _____

Address _____



HOME RADIO (Components) LTD.
Dept. PW, 234-240 London Road, Mitcham CR4 3HD




The price of 75p applies only to customers in the U.K. and to B.F.P.O. addresses

Candles are for Eskimos.

The 1973 answer to power cuts.
The Jermyn inverter.

When plugged into any 13 amp socket these units charge 12/24v car batteries (up to 10 amps). In the event of a power failure they automatically start inverting, providing a 240v 50Hz emergency supply at 150/300 watts. Enough for a couple of standard lamps and the TV or the central heating pump and the hi-fi. All this and full protection against overload and wrong battery lead connection.

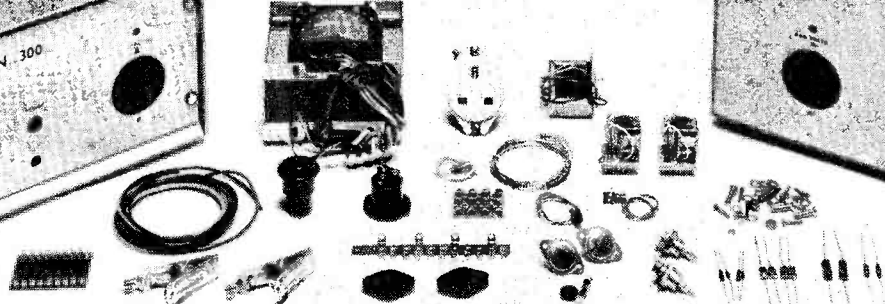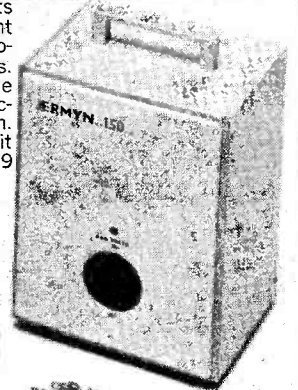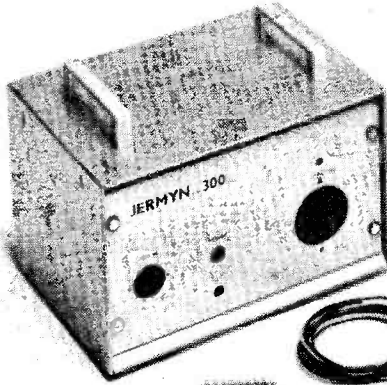A complete kit of parts costs £25 for the 150 watt unit or £34 for the 300 watt version (made up and tested) £29 and £39 respectively.




To Jermyn Industries
Vestry Estate
Sevenoaks
Kent

Please rush me Kit(s),
 made up invertors.
I enclose cheque/postal order for £

Name
Address

Block Capitals Please

VEROBOARD

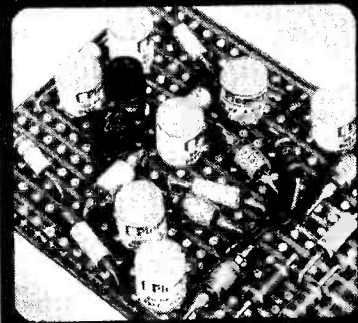

VEROBOARDS GIVE A PROFESSIONAL
FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper
clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER

TRADE DISTRIBUTOR: N. Rose Electrical Ltd London WC1



VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford,
SO5 3ZB Tel: Chandler's Ford 7312



LOUDSPEAKER BARGAINS

Fane Pop 100 Watt 18" 8/15 ohm	£19.50
Fane Pop 60 Watt 15" 8/15 ohm	£11.15
Fane Pop 50 Watt 12" 8/15 ohm	£9.25
Fane Pop 25/2 12" 25 watts 8/15 ohm	£5.40
Fane Pop 15 12" 10 watts 8/15 ohm	£4.00
Baker Group 25 12" 3, 8 or 15 ohm	£6.60
Baker Group 35 12" 3, 8 or 15 ohm	£8.00
Celestion PS8 for Unilex	£2.35
EMI 13 x 8, 3, 8 or 15 ohms	£2.25
EMI 13 x 8, 3, 8 or 15 ohms	£2.25
EMI 13 x 8 twin tweeter 3, 8 or 15 ohms	£2.60
EMI 13 x 8 type 350 15 watt 8 ohm	£8.00
Richard Allen 8" 3, 8 or 15 ohm	£2.35
Richard Allen 12" dual cone 3 or 15 ohm	£2.50
Fane 8" dual cone 808T 8 or 15 ohm	£2.85
Fane 8" d/cone roll surround 807T 8 or 15 ohm	£3.50
Elac 59RM109 9" x 5" 15 ohm	£2.70
Elac 59RM114 9" x 5" 8 ohm	£2.70
Elac 6 1/2" d/cone 8 ohm	£2.25
Elac 6 1/2" d/cone, roll surround 8 ohm	£3.50
Elac 4" tweeter 8 ohm	£1.50
Crossover for above (p. & p. free)	£1.50
Goodmans 8 P, 8 or 15 ohm	£4.75
Goodmans 10 P, 8 or 15 ohm	£5.25
Goodmans 12 P, 8 or 15 ohm	£5.25
Goodmans 15 P, 8 or 15 ohm	£17.00
Goodmans 18 P, 8 or 15 ohms	£27.50
2", 2 1/4" or 3" 80 ohm	.65
Phillips 5" 8 ohm	£1.95
7" x 4" or 8" x 5" 3 or 8 ohm	£1.50
10" x 6", 3, 8 or 15 ohm	£2.00

FREE with orders over £6—"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect.
Prompt despatch p. & p. 25p per speaker.

WILMSLOW AUDIO, Dept. PW

10 Swan St., Wilmslow,
Cheshire, SK9 1HF

GEIGER COUNTERS

(FOR MAINS OR PORTABLE BATTERY USE)



Latest Home Office release and probably the last of this well known Contamination Meter No. 1, this very useful instrument is used for the measurement of Radio-Activity. Indicated on an internal Meter scaled 0.1 to 10 milli Rontgens/Hour, a socket is also provided for additional sound Monitoring on headphones. This instrument is housed in a Strong light Alloy

Case, placed in a carrying Haversack with shoulder strap. Containing Cable and Hand held Probe, Instruction Card, plus the latest plug in Vibrator Power Unit, which uses current small Transistor Radio Batteries (4 Mallory Long Life RM12 or 4 EverReady H.P.7 or equivalent makes). For Mobile use anywhere. (Cost Gov. approx. 270 each). Supplied Brand New in Carton only 25.50 carr. 50p. An additional plug in Power Unit for Laboratory use, operating from 100-120 volts or 200-250 volts A.C. Mains is available. Supplied Brand New in Carton at only 22.50 post 25p. A few Geiger Counters as above but not boxed in cardboard cartons, available at only 24.50.




Meter Dose Rate Portable

Trainer No. 1
This was used to train in the use of Geiger Counters. A very compact self-contained Geiger Counter, being very sensitive.

Radiation indicated on internal Meter scaled 0 to 3 Rontgens/Hour x 10-4. Unit contained in Waterproof Alloy Case, which is hand held. Uses Internal Batteries (4 EverReady B105 and 1 U2 or equivalent makes) Not Supplied. These had little or practically no use, supplied as New in Cartons. Few only 23.50 carr. 50p.

JOHNS RADIO

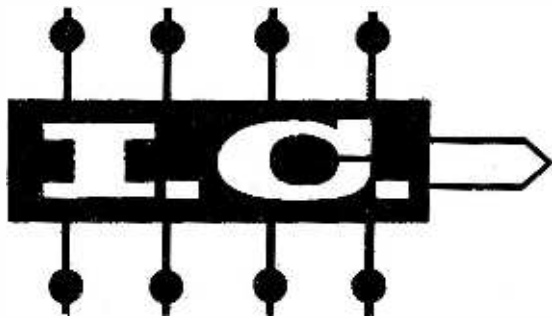Dept. D, 424 Bradford Road,
Batley, Yorks. Phone Batley 7732



OF THE MONTH

L.A.J. IRELAND

Number 35

SGS TBA231 Audio Preamplicr

THE SGS TBA231 i.c. reviewed this month follows along the fairly well established lines of high performance quality audio preamplifiers set by the RCA3052 which has already been reviewed in this column (May 1970). Low noise and high gain coupled with low power consumption are features being demanded more and more both by industry and the discerning audio enthusiast and the tight specifications associated with the TBA231 (noise figure less than 70dB, flat frequency response gain of 29dB) should make this i.c. meet the requirements of any amateur seeking a good quality audio preamp.

In Fig.1, a complete circuit diagram of one of amplifiers in the TBA231 is given. It is not intended to analyse the circuit in detail but a number of the more unusual features in the design will be pointed out. First a string of diodes D1 to D6 accurately control the constant current transistors Tr3 and Tr6 which also act as active bypass elements. In addition provision is made for limiting the output current in the event of a short circuit at pin 1. In this instance, the voltage increase developed across R6 automatically biases off Tr7 and Tr8 thereby preventing damage to the chip from an excessive current flow.

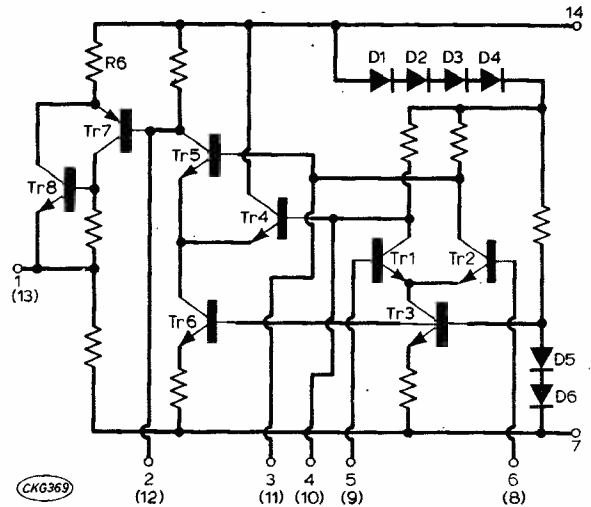


Fig. 1: Circuit of the TBA231. Numbers in brackets are pin connections of second identical amplifier.

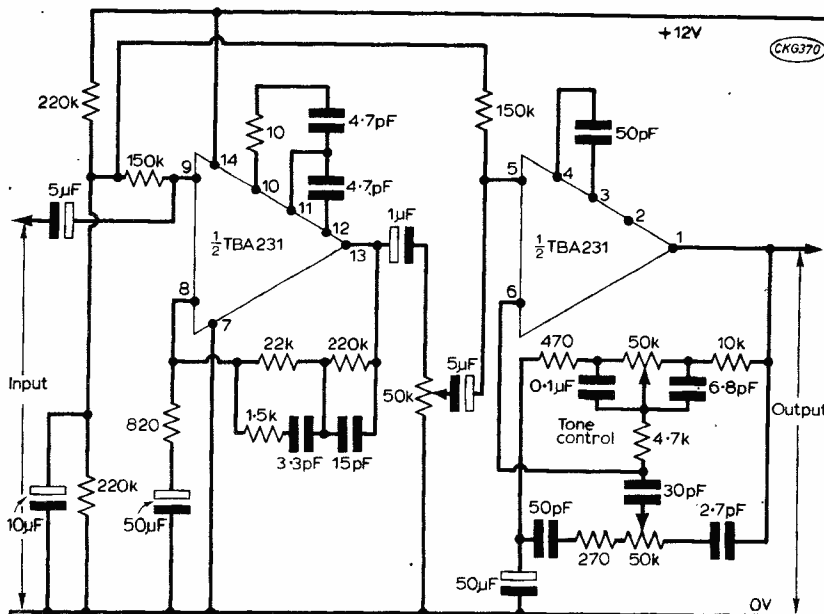


Fig. 2: Amplifier incorporating RIAA equalisation and active tone control circuits.

Also, even though the two amplifiers are fabricated and electrically connected on the same monolithic chip, channel separation of 140dB results from careful design and layout. So any inter-channel inter-action will more than likely be caused by poor external bias decoupling or power supply fluctuations.

A typical application of the TBA231 as a hi-fi preamplifier utilising the first section for RIAA equalisation and the second amplifier section as an active tone control unit is illustrated in Fig.2. Typical performance specifications of this design are associated usually only with the more expensive hi-fi amplifier units.

The TBA231 is available from any SGS distributor such as Quarndon Electronics Ltd., Slack Lane, Derby.

EIS again . . .

Further development work carried out on the Electronic Ignition System has indicated that the output voltage of the original circuit was a little high and resulted in an increased possibility of crossfire and distributor cap flashover in damp conditions. As a result the output voltage has been reduced and it is now recommended that for optimum operation the value of the capacitor be increased from $0.47\mu\text{F}$ to $1.0\mu\text{F}$.

Because of the arduous operating conditions imposed on this capacitor it is recommended that a triple foil type with at least 440V a.c. or 1000V d.c. rating be used. A suitable capacitor has been developed specifically for C-D ignitions and these are available from Magtor Ltd., 68 Dale Street, Manchester, at a cost of 35p including post and package.—**Stephen Soar**, (Manchester).

. . . and again

Just a brief note on the PW Electronic Ignition System. I found that the unit caused interference on my car radio so I bought a filter kit from Magtor Ltd., as advertised in PW. I fitted the three components inside a cylindrical aluminium can taken from an old vibrator unit and wired it into the E.I. box. In some cases it might be possible to fit the components into the E.I. box itself.

The filter kit is actually intended to decouple E.I. circuits when a tachometer is also fitted but it certainly proved effective against interference to my radio.—**P. Beaman**, (Bridgnorth, Shropshire).

(The decoupling kit can be obtained from Magtor Ltd., 68 Dale Street, Manchester, M1 2HS, price £1 including p and p.)—Editor.

Padding out

I write with reference to the many designs of receiver appearing in PW using Denco Miniature plug-in coils.

On reading through the manufacturer's literature on these coils it came to my notice that no padder was required for range five (red) coils. To satisfy my

curiosity, I drew a graph of mid range frequency against padder value for each of the five coils. This came out as a straight line, and gave the range five padder to be $6,000\text{pF}$. This value was then tried in my receiver, which uses these coils, and it gave a marked improvement at the l.f. end of the band. On mentioning this to a friend who has built a receiver along similar lines to mine, he also tried it and got results similar to mine.

I would like to know what other readers, and maybe even Denco Ltd., think on the subject.—**P. Richards**, (Manchester).

A bit tight

I am sure many readers, at some time or another, have been frustrated to find that they have been unable to remove the bits from their 25 Watt Henley Solon soldering irons when they are due for replacement.

Having purchased a new iron some time ago, I slightly reduced the diameter of the bit with emery cloth and fitted a sleeve made from aluminium foil to come between bit and the body of the iron. Thus the binding between bit and iron is eliminated.

The foil I used was obtained from a cup containing a mince pie and if other readers follow my example, they can eat the by-product with their coffee whilst doing a soldering job!—**R. H. Roling**, GW6WM (Glamorgan).

What do you get?

Please will you tell me what a man who pays £10 plus for a tone arm actually gets for his money?

I have recently constructed a pair of tone arms using standard 'Meccano' parts throughout. Both are heavy, but due to the screw-adjusted counter weight, tracking weights of much less than that of a Meccano nut are easy to arrange. They are about 13in long from pivot to head. Tracking error should not be too great if it is set correctly, which I suppose would involve setting the stylus to point along the groove while the arm is about one-half of the way across the track of the record. I have

been unable to test it as yet due to the lack of a cartridge and stylus, which I am not allowed to remove from our Record Player for testing purposes (or any other), therefore, I used a dummy weight to simulate this.

The cost of the arm with the screw adjusted counterweight would be less than £1 if all the parts were bought new.—**S. Sellick**, (Devon).

Aerial problem

May I enquire through the columns of PW for help.

I have a portable receiver which is for use on the 108-136 MHz and 145-175MHz bands. The set is equipped with the usual telescopic aerial, and this is ideal for reception from airborne aircraft or when within sight of an airport control tower.

I would like to build an aerial which I can place on the housetop (40ft above ground) which I am sure would give me better reception from the local airport, which is 5 miles from my home.

I have written to 3 major aerial manufacturers for either details or purchase of a suitable aerial but they do not seem to be interested in the problem.—**J. Stirzaker**, (4 Maitland Avenue, Anchorsholme, Blackpool, Lancs). (The lack of interest may be explained by the fact that the Ministry of P&T has repeatedly pointed out that a Licence [not generally available to the public] is required for the reception of transmissions by Fire Brigade, Aircraft, Ship-ping, etc.)—Editor.

Help!

At the moment I am having difficulty in obtaining a diagram and wiring instructions for a Ferdio wireless PR41 "Town and Country" with trawler band.

I have the service sheet for PR41 but this is the older one and has 8 coils, but the one I want has 9 coils, which must have been the last model made. It has a tone control on the side and tape DIN socket on the back of the case. Can anyone help please?—**Richard Cowley**, Kerrouglass, Kirk Michael, Isle of Man.

Disco

SOUND & LIGHTING EQUIPMENT

from 4 SPECIALISED DISCO STUDIOS

HIGH POWER SPEAKER SYSTEMS

Strong leather cloth finish 1" board, fully lagged. Fitted high efficiency 8 or 16 ohm speakers.

- PRINCE. 50 watt rms. 12". Size 24" x 16" x 12"
- CONSORT. 100 watt rms. 2-12" speakers. Size 38" x 18" x 12"
- MAJESTIC. 100 watt rms. 15" Crescendo. Size 38" x 24" x 15"
- SOVEREIGN. 100 watt rms. 18" Bass, 12" Full range. Size 50" x 26" x 14"

FULL RANGE OF MICROPHONES, STANDS, ETC. ALWAYS IN STOCK

SOUND CONTROLLED AND SOUND TO LIGHT UNITS

Mid, Treble and Bass Channels, up to 1kw of lamps per channel plus override switching.

DJ30L. Sound to Light. Takes output from most amplifiers. Adjustable levels.

DJ40L. Sound controlled version. Built in microphone, no connections required.

ASSEMBLED DISCO THEQUES

DISCO-PLINTH. Consists of 2 turntables fitted with high quality ceramic cartridges. The unit has a built in cross-fade rotary control for transferring the sound from left to right decks. The unit has no amplification built in and must be used with amplifiers such as the D.J. 105S or D.J. 70S. Size 32" x 14 1/2" x 7" (incl. HA).

DISCO-IMP. The latest addition to the Disco-sound Range of discotheques. Even smaller and more compact than the Disco-Mini, it contains all the necessary features for the smooth running of a mobile unit. Size 29" x 18 1/2" x 7"

DISCO-MINI. Complete portable Disco with built-in full function preamplifier/mixer. For use with any power amplifier such as "Disc-master". Size 30" x 20" x 8"


DISCO-STANDARD. Has all the facilities of the Disco-Mini with the addition of a built-in 100 watt power amplifier making it a completely self contained disco unit. A V.U. meter gives visual indication of output levels. Size 32" x 27" x 10"

DISCO-SUPER. A slightly larger version of the Disco-Standard. Fitted individual controls for both mic. and deck inputs plus a cross-fade for deck to deck transfer. A built in P.F.L. cueing system, mic. override, also a V.U. meter gives visual indication of output levels.

DJ. 30L (3000V) 3-channel psychedelic light unit is a standard fitting. Deck cut out switches are also featured for ease of cueing. Size 38" x 27" x 10"

DISCO-SUPREME. All facilities of the Disco-Super plus a third turntable which can be used for Jingles or other effects without using the main deck system. Flexi lights are also fitted. Size 50" x 27" x 10"

PA-DISCO AMPLIFIERS

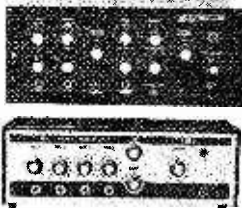

DISCO-AMP. 100 watt rms. output for 8-16 ohms, 4 channel inputs, 2-mic, 2 decks. Separate volume control plus masters. Response 30Hz -30KHz, distortion less than 1%. Treble/Bass/PFL/Mic over-ride etc. Panel size 16 1/2" x 7"

DJ.70S MIXER/AMPLIFIER. 70 watt rms. output for 8-16 ohms. 2-mic, 2-aux/decks. Master volume/Bass/Treble. Size 15 1/2" x 5" x 6"

DJ.105S. 30 watt rms. version. Size 11 1/2" x 5" x 6".
DISCMASTER SLAVE AMPLIFIER. 100 watt rms. for 8-16 ohms.

NEW D.J. 500 SERIES P.A. AMPLIFIERS 50 WATT, 70 WATT & 100 WATT MODELS

This new range incorporates many features that make them ideal for the professional user, clubs, discotheques, factories etc. Fibre glass P.C. Boards are used throughout with low noise silicon transistors, high stability resistors, generously rated components and hand wired assembly to ensure reliability and quality.

★ Exclusive "Fail Safe" Electronic Protection circuit.

★ Fault Condition warning lamp.

★ Built in bass boost below 30 Hz.

★ 4 channel mixer with slider controls.

All three amplifiers have a built in emitter follower output socket for connecting a slave amplifier to enable the power output to be increased up to 1000 watts or more if required. A matching range of slave power amplifiers and a separate matching 100v line transformer is available

SPECIFICATION

Frequency Response	50-20,000 Hz ± 3db (10dB Bass Boost at 10 Hz)
Signal/Noise Ratio	better than -50db.
Harmonic Distortion	less than 1%
Speaker Impedance	8-16 ohms.
Inputs: Mic 1 & 2	5mV at 50K ohms (50 or 600 ohm to order)
Aux 3 & 4	100mV at 1 meg ohm.
Size (all models)	15 1/2" x 5" x 6"
Power Output:	
(at 8 ohms)	Model D.J.500 — 50 watts R.M.S.
	Model D.J.700 — 70 watts R.M.S.
	Model D.J.1000 — 100 watts R.M.S.

DISCO MINI

Hardly larger than a suitcase yet contains all the necessary features for a high quality mobile unit. The pre-amp has separate tone controls for both mic. and decks, and each input has its own individual volume controls and inputs.

plus the addition of a cross fade for deck to deck sound transfer. A built in P.F.L. system for cueing, together with mic-over-ride facility are standard on all units. Response 20-20,000 Hz. Mic. input 5mV, 50K. Output 1 volt.

McDonald M.P.60 Turntables are used with high quality ceramic cartridges, and each deck has its own individual cut out switch fitted. This unit is suitable for Discos or Clubs having a power amplifier, or for use with the "Discmaster" 100 watt power amplifier as above. Size 32" x 20" x 8"



EFFECTS PROJECTORS



A small selection from our vast stock.

DISCO COLT. 150 watt. LIQUIMATIC MINI, 50 watt Q1 with 6" wheel. DISCOWHEEL, 50 watt Q1 with quick change Cassette.

GNOME 150, 150 watt Q1 with Cassette. LIQUIMATIC, 150 watt Q1 with 6" wheel. FLUTO TUTOR-2, 250 watt Q1 with Cassette and 6" wheel.

TUTOR-2, with Liquisplode Tank. **KALEIDOSCOPE LENS** (for Tutor-2) 6" Liquid Wheel and Crystal Wheel Liquid Cassette and Moire (24 different types to choose from). Portable Hi-Power Strobes.


YOU WILL BE SURPRISED BY THE LOW PRICES & PERFORMANCE

SDL POWER SPEAKERS

High efficiency 12" speakers. Ferrite magnets. Heavy duty voice coils and cones for Disco and Group use.

- 12" 50 watt rms. 8 ohm Full range.
- 12" 250 watt rms. 15 ohm Mid-Treble.
- 15" 50 watt rms. 15 ohm Full range.
- 18" 100 watt rms. 15 ohm Bass.
- 18" 100 watt rms. 15 ohm Bass.

DISCO SPOT BANK

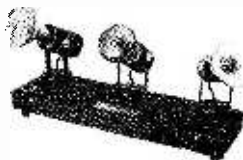

Designed to take three E/S Type spot or colour bulbs up to 150 watts each. The unit is of all metal construction and has one 3-pin mains input socket plus one 3-pin mains output socket for connecting more than one bank together if required. The unit can be left free-standing or wall mounted if needed. Black crackle finish gives the unit a very professional appearance.

Size 18" x 6" x 7" (excluding bulbs)

In stock: Ultra Video Spot Lamps and Fluorescent Lamps, Standard and Colour Spot Lamps and Fittings. Rotating Colour Displays. Flexlights, Fibre Optics, Dimmers, Flashers Effects Foils, etc. Your enquiries invited.

MIXER UNITS

DJ.101. Battery powered, 6-channel, variable levels, 3 x 50K mic., 1 x 100mV. aux., 2 x 100mV p.u. Output 250mV.

DJ.102. Mains operated, 4-channel, variable levels. 2 x 50K mic., 2 x 100mV p.u. PFL control, master volume, mic. over-ride, output variable 0-500mV.

DISCO 40. Pre amp part of Disco amp (see above). All facilities. Output will drive up to ten 100 watt amplifiers.

Discoscene

536, Sutton Road,
Southend, Essex.
(0702) 611577

Discosound

122, Balls Pond Road,
London, N.1.
(01) 254 5779

Discosound

(Birmingham) Ltd.
494, Bristol Road,
Selly Oak, B'ham 29.
(021) 472 1141

Henry's Disco

309, Edgware Road,
London, W.2.
(01) 723 6963

CHECK WITH YOUR NEAREST STUDIO FOR LATEST PRICES AND DETAILS (TRADE AND RETAIL SUPPLIED)

BRAND NEW


SEMICONDUCTORS & COMPONENTS

GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

2G301	0-15	2N2924	0-12	2N5174	0-20	AF116	0-25	BC307	0-10	BF271	0-21
2G302	0-15	2N2925	0-12	2N5175	0-20	AF117	0-20	BC307A	0-10	BF272	0-21
2G303	0-20	2N2926	0-12	2N5176	0-20	AF121	0-20	BC307VI	0-10	BF273	0-21
2G306	0-20	Green	0-10	2N5177	0-20	AF124	0-24	BC308A	0-10	BF274	0-21
2G344A	0-25	Orange	0-10	2N5190	0-20	AF125	0-20	BC308B	0-10	BF275	0-21
2G345A	0-25	Orange	0-10	2N5191	0-20	AF126	0-19	BC309	0-10	BF469	0-57
2G346R	0-25	2N3053	0-21	2N5192	0-24	AF127	0-20	BC309A	0-10	BF521	2-10
2G371	0-15	2N3054	0-47	2N5193	1-01	AF129	0-25	BC309B	0-10	BF521A	2-10
2G374	0-15	2N3054	0-46	2N5194	1-01	AF172	0-25	BC313	0-20	BF528	0-22
2G381	0-20	2N3055	0-50	2N5195	1-46	AF178	0-25	BC327	0-24	BF591	0-27
2G417	0-20	2N3290	0-20	2N5245	0-48	AF179	0-55	BC328	0-22	BF598	0-25
2N109	0-48	2N3391	0-20	2N4467	0-20	AF180	0-50	BC337	0-19	BFW10	0-21
2N174	1-40	2N3391A	0-22	2N4468	0-33	AF186	0-40	BCY30	0-85	BFX10	0-25
2N176	0-75	2N3392	0-12	2N5459	0-33	AP200	0-35	BCY31	0-40	BFX13	0-25
2N174	0-75	2N3393	0-12	3N128	0-28	AP239	0-41	BCY32	0-60	BFX29	0-25
2N335	0-75	2N3394	0-12	3N138	0-37	AP240	0-72	BCY32	0-76	BFX30	0-25
2N511	1-00	2N3402	0-17	3N199	1-36	AP279	0-54	BCY33	0-34	BFX37	0-25
2N376	1-00	2N3403	0-19	3N140	0-44	AP280	0-54	BCY34	0-35	BFX44	0-28
2N384	0-20	2N3404	0-24	3N141	0-60	APY42	0-74	BCY38	0-40	BFX63	2-28
2N388A	0-20	2N3405	0-27	3N142	0-54	APY11	0-55	BCY39	1-05	BFX68	0-24
2N404	0-20	2N3414	0-10	3N143	0-64	AL202	0-75	BCY40	0-50	BFX84	0-20
2N404	0-20	2N3415	0-10	3N152	0-79	AL103	0-70	BCY42	0-15	BFX85	0-24
2N456	0-75	2N3416	0-15	3N153	0-74	ALY26	0-30	BCY43	0-15	BFX86	0-24
2N456A	0-75	2N3417	0-21	3N154	0-74	ALY27	0-38	BCY43	0-28	BFX87	0-24
2N457A	0-80	2N3470	1-25	3N157	1-00	ALY28	0-38	BCY49	0-22	BFX88	0-24
2N491	0-25	2N3471	1-25	3N187	1-00	ALY29	0-30	BCY66	0-68	BFX89	0-20
2N584	0-40	2N3572	0-27	3N200	1-07	ALY60	0-20	BCY67	0-94	BFY10	0-35
2N591	0-84	2N3702	0-10	3N201	1-05	ALY65	0-25	BCY70	0-17	BFY11	0-35
2N696	0-15	2N3703	0-10	40050	0-78	ASZ21	0-55	BCY71	0-22	BFY17	0-20
2N697	0-15	2N3704	0-10	40051	0-81	AU103	1-25	BCY72	0-13	BFY19	0-20
2N698	0-25	2N3705	0-10	40052	0-81	BC109	0-13	BCY88	2-40	BFY20	0-50
2N699	0-25	2N3706	0-10	40059	0-81	BC109A	0-14	BCY88	2-40	BFY20	0-50
2N700	0-13	2N3707	0-10	40310	0-50	BC110	0-13	BCY89	0-80	BFY29	0-40
2N700A	0-13	2N3708	0-70	40311	0-50	BC113	0-12	BCZ10	0-35	BFY37	0-20
2N708	0-38	2N3709	0-90	40313	0-62	BC114	0-13	BCZ11	0-50	BFY41	0-43
2N709	0-38	2N3710	0-90	40318	0-92	BC115	0-15	BD115	0-75	BFY43	0-22
2N711	0-30	2N3711	0-90	40322	0-92	BC116	0-15	BD116	0-75	BFY49	0-16
2N718	0-20	2N3712	0-96	40360	0-46	BC117	0-21	BD123	0-82	VFY52	0-16
2N718A	0-20	2N3713	0-96	40361	0-46	BC118	0-11	BD124	0-67	VFY53	0-16
2N720	0-60	2N3714	1-15	40362	0-44	BC119	0-27	BD130	0-57	BFY66	0-24
2N721	0-65	2N3715	1-23	40363	0-44	BC121	0-23	BD131	0-40	BFY64	0-24
2N914	0-15	2N3716	1-30	40389	0-46	BC122	0-29	BD132	0-50	BFY75	0-20
2N916	0-17	2N3717	2-35	40394	0-56	BC123	0-29	BD135	0-45	BFY75	0-22
2N918	0-20	2N3774	3-38	40395	0-50	BC125	0-20	BD136	0-49	BFY77	0-24
2N919	0-20	2N3775	4-85	40406	0-44	BC132	0-80	BD137	0-55	BFY78	0-26
2N929	0-20	2N3776	4-84	40407	0-88	BC134	0-11	BD138	0-83	BFY90	0-30
2N940	0-14	2N3777	4-84	40408	0-55	BC135	0-11	BD139	0-71	BRY39	0-30
2N1090	0-23	2N3778	2-25	40410	0-53	BC136	0-16	BD140	0-83	RX319	0-13
2N1091	0-24	2N3779	3-15	40410	0-53	BC137	0-15	BD141	0-83	RX319	0-13
2N1131	0-20	2N3780	4-40	40411	2-00	BC138	0-24	BDY11	1-50	BSX21	0-30
2N1132	0-20	2N3781	8-67	40414	3-55	BC140	0-84	BDY17	1-50	BSX26	0-34
2N1184	1-27	2N3782	3-27	40438	1-44	BC141	0-39	BDY18	1-75	BSX27	0-34
2N1303	0-16	2N3789	1-76	40477A	0-69	BC142	0-24	BDY19	1-97	BSX28	0-26
2N1304	0-20	2N3790	1-80	40485A	0-69	BC143	0-21	BDY20	0-82	BSX29	0-27
2N1305	0-20	2N3791	2-06	40600	0-69	BC144	0-24	BDY28	0-65	BSX30	0-58
2N1306	0-20	2N3792	2-06	40601	0-67	BC145	0-21	BDY29	0-65	BSX30	0-58
2N1307	0-22	2N3794	0-10	40602	0-46	BC147	0-11	BDY61	0-85	BSX60	0-54
2N1308	0-25	2N3819	0-27	40603	0-58	BC148	0-10	BDY62	0-75	BSX60	0-54
2N1309	0-25	2N3823	0-50	40604	0-66	BC149	0-13	BF115	0-23	BSX76	0-15
2N1483	0-20	2N3824	0-75	40636	1-10	BC153	0-18	BF117	0-43	BSX77	0-20
2N1507	0-24	2N3826	0-23	AC107	0-85	BC154	0-13	BF119	0-58	ASX78	0-25
2N1613	0-20	2N3854	0-16	AC113	0-16	BC158	0-18	BF121	0-45	BFY121	0-28
2N1631	0-35	2N3854A	0-16	AC115	0-16	BC159	0-14	BF125	0-25	BSY25	0-15
2N1637	0-35	2N3855	0-16	AC117	0-20	BC160	0-37	BF127	0-27	BSY26	0-20
2N1638	0-27	2N3855A	0-16	AC117	0-20	BC167B	0-11	BF152	0-20	BSY27	0-15
2N1671	1-00	2N3856	0-16	AC121	0-13	BC168B	0-13	BF153	0-29	BSY28	0-15
2N1701	1-10	2N3856A	0-16	AC127	0-20	BC168C	0-11	BF154	0-18	BSY38	0-15
2N1702	2-15	2N3858	0-16	AC129	0-20	BC169C	0-13	BF159	0-27	BSY39	0-25
2N1711	1-17	2N3858A	0-16	AC141K	0-25	BC170	0-11	BF160	0-23	BSY32	0-25
2N1883	0-35	2N3859	0-16	AC142K	0-25	BC171	0-13	BF161	0-23	BSY43	0-25
2N2102	0-30	2N3859A	0-16	AC151V	0-17	BC172	0-11	BF163	0-20	BSY64	0-20
2N2147	0-70	2N3860	0-16	AC152V	0-17	BC172	0-11	BF163	0-20	BSY64	0-20
2N2148	0-60	2N3866	0-70	AC153K	0-22	BC182L	0-10	BF167	0-18	BSY65	0-15
2N2192	0-40	2N3877	0-25	AC153K	0-25	BC183	0-09	BF173	0-19	BSY78	0-40
2N2193A	0-40	2N3877A	0-25	AC154	0-20	BC183L	0-09	BF177	0-25	BSY79	0-40
2N2193B	0-40	2N3877B	0-25	AC154	0-20	BC184	0-11	BF178	0-25	BSY79A	0-40
2N2194	0-27	2N3900	0-20	AC176K	0-20	BC184L	0-11	BF179	0-30	BSY95A	0-25
2N2194A	0-27	2N3900A	0-20	AC187K	0-20	BC185	0-05	BF180	0-25	BF180	0-25
2N2196	0-37	2N3901	0-22	AC187K	0-20	BC187	0-25	BF181	0-32	BU105	2-25
2N2196A	0-37	2N3901A	0-22	AC187K	0-20	BC187	0-25	BF181	0-32	BU105	2-25
2N2196B	0-37	2N3901B	0-22	AC187K	0-20	BC205	0-10	BF183	0-40	D40N3	0-62
2N2198A	0-18	2N3903	0-30	AC1Y18	0-15	BC204	0-10	BF184	0-17	GET111	0-42
2N2198B	0-18	2N3904	0-17	AC1Y19	0-20	BC206	0-10	BF185	0-17	GET113	0-20
2N2210	0-37	2N3905	0-21	AC1Y21	0-19	BC207	0-10	BF186	0-17	GET114	0-20
2N2220	0-20	2N4036	0-63	AC1Y22	0-13	BC209	0-18	BF198	0-15	GET115	0-50
2N2221	0-20	2N4037	0-42	AC1Y28	0-18	BC209	0-18	BF198	0-15	GET115	0-50
2N2221A	0-88	2N4038	0-12	AC1Y30	0-42	BC211	0-30	BF196	0-15	GET119	0-85
2N2222	0-31	2N4059	0-90	AC1Y39	0-55	BC212K	0-10	BF197	0-15	GET120	0-85
2N2222A	0-41	2N4060	0-11	AC1Y40	0-17	BC212L	0-12	BF198	0-15	GET126	0-20
2N2269	0-11	2N4061	0-11	AC1Y44	0-31	BC214L	0-14	BF199	0-18	GET535	0-20
2N2269A	0-11	2N4062	0-11	AC1Y44	0-31	BC226	0-16	BF200	0-35	GET535	0-20
2N2269B	0-17	2N4302	0-25	AD136V	0-96	BC227	0-09	BF224J	0-09	GET535	0-20
2N2264	0-41	2N4303	0-22	AD140	0-50	BC238	0-09	BF252J	0-19	GET573	0-12
2N2264A	1-20	2N4313	0-80	AD140	0-50	BC239	0-09	BF257	0-22	GET580	0-30
2N2271	0-12	2N4314	0-80	AD142	0-50	BC251	0-09	BF258	0-22	GET583	0-12
2N2272	0-12	2N4315	0-95	AD144	0-45	BC252	0-18	BF244	0-16	GET587	0-20
2N2273	0-17	2N4316	0-11	AD149V	0-68	BC253	0-28	BF245	0-33	GET590	0-22
2N2274	0-17	2N4317	0-17	AD149V	1-28	BC254	0-09	BF246	0-33	GET590	0-22
2N2904	0-18	2N4318	0-50	AD150	0-63	BC258	0-09	BF247	0-49	GET590	0-22
2N2904A	0-25	2N4319	0-53	AD161	0-37	BC259	0-13	BF254	0-14	RETURN	0-25
2N2905	0-28										

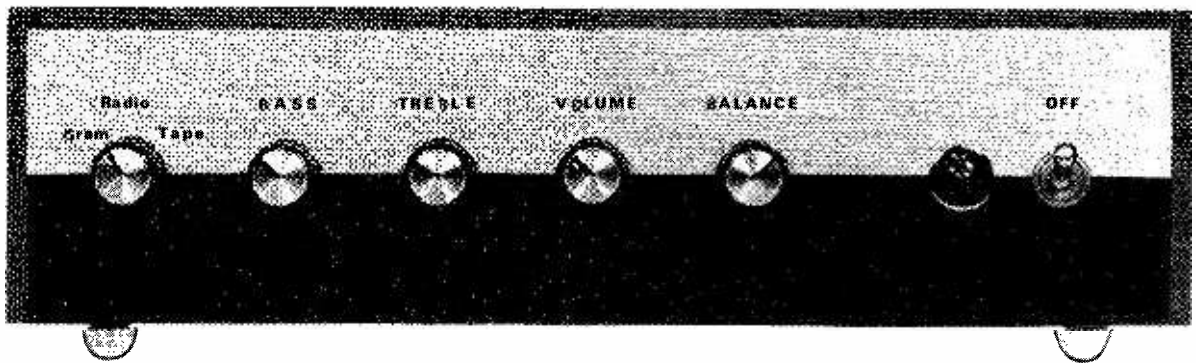

10+10 WATT stereo amplifier

W. CAMERON

PART TWO

PREAMPLIFIER

Construction is on the same lines as the driver amplifier, on a group board with common earth bus-bar, and is shown for one channel, Fig. 6a and circuit diagram Fig. 6b. Decoupling components R10, R24 and C2 and C12 are common to both channels. Screened leads are used from the input sockets to the selector switch, and from the switch to the input tags and also from the volume control to the driver amp inputs. The switch wiring is shown in Fig. 7a. Note that the equalising components are mounted directly on the switch (Sections c and d).

It is at the input sockets where the only earth connections to chassis are made (apart from mains earth) this is important as hum and distortion can easily occur if earth loops are formed by connecting more than one point to the chassis.

The modular construction of the preamp with its earth bus-bar ensures that its own earth returns are all common to itself. (This applies also to the driver module.)

It will be seen that the chassis earth at the input is carried via the screened leads to the preamp, and then to the earthy side of the volume control, thence to the driver amp, through to the common point on the power supply, where the return from the power amps via the speakers are also returned. This is made clear in the layout drawing Fig. 8. The preamplifier has a number of connections to the controls, and it will be found easiest to solder connecting wires in place on the module before fitting to

chassis. Leads of different colours would be a further aid. The leads should then be trimmed to length and taken to their control terminations in pairs. Driver and power amplifier can be treated in a similar manner.

Note that with all the transistors, the collector and case are common, so care must be taken to ensure that the case does not come in contact with other component or earth connections.

Output sockets for "Record" can be fitted if required. These are fed from each channel via a 100kΩ resistor from the negative side of C7, and will provide a signal of 100mV at high impedance, or 1mV per 1kΩ for impedances less than 100kΩ. Connections are shown in Fig. 6b.

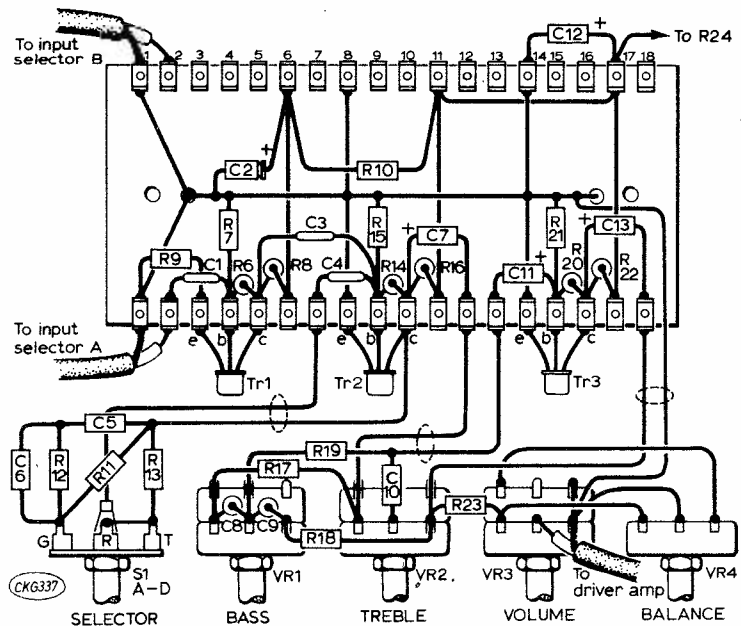


Fig. 6a: The wiring of the preamplifier section, only the components for the R.H. channel are shown; those for the other are mounted on the other side of the board and on the rear section of the pots.

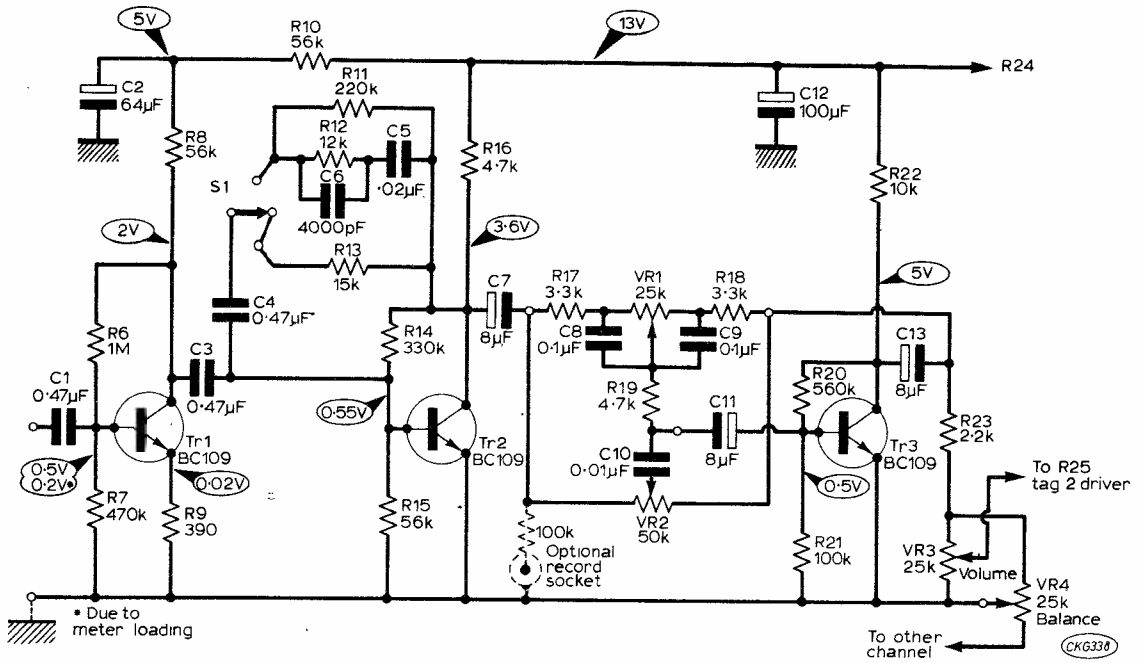


Fig. 6b: The circuit of one channel of the preamplifier. The decoupling components in the positive line are common to both channels.

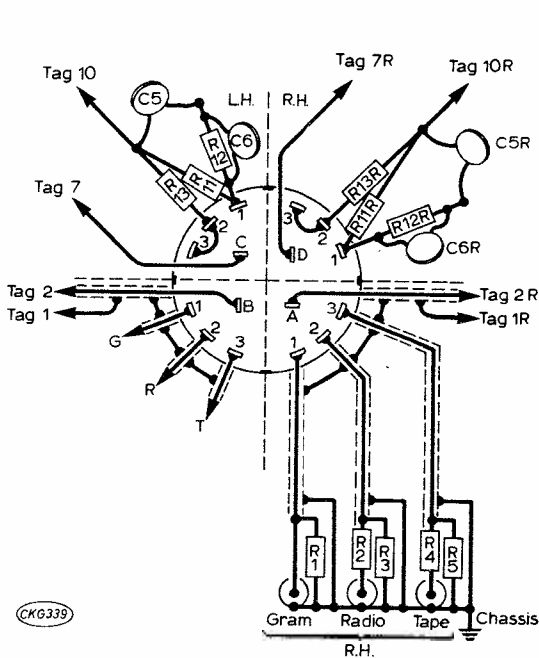


Fig. 7a: The wiring of the selector switch S1.

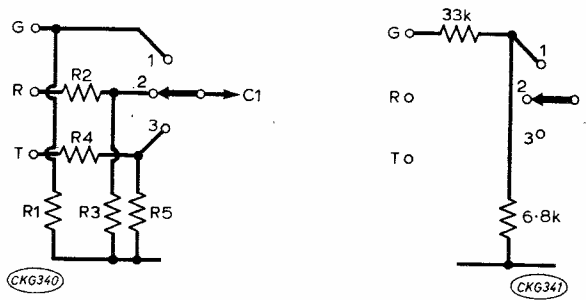


Fig. 7b (left): The circuit of the input selector section.
Fig. 7c (right): Modification for a ceramic pickup.

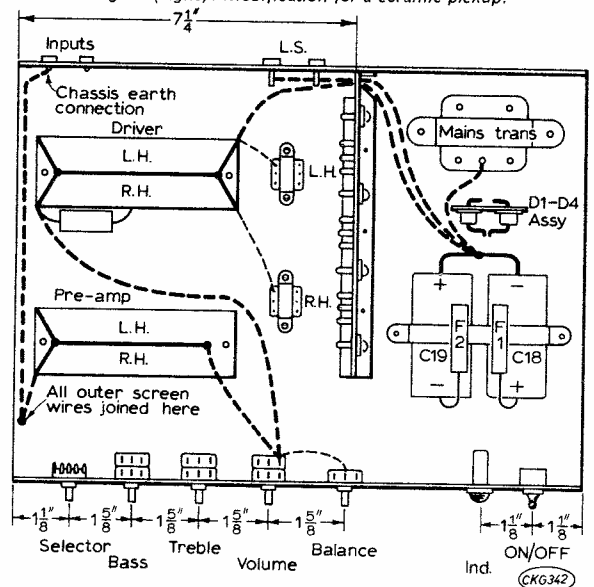


Fig. 8: The general layout showing the connection of the earth line to avoid earth loops.

If the gram input is intended for a ceramic cartridge, this input must be attenuated with a divider of $33k\Omega$ and $6.8k\Omega$, in the same manner as the radio and tape inputs. This will provide a sensitivity of $100mV$ and loading to give the pickup similar characteristics to a magnetic type, to suit the equalisation.

If the radio or tape recorder to be used is mono only, the appropriate input sockets should be linked together so that the single input plug is connected to both channels.

POWER SUPPLY

The layout and circuit diagram are shown in Fig. 9 and need little comment. The rectifiers are "top-hat" types mounted on a piece of lin. x 1½in. paxolin. A 2A bridge rectifier can be used here if desired; the symbols shown correspond to the bridge connections.

Capacitors C18 and 19 are held in place with an aluminium strip, to which the fuseholders are also secured.

The mains earth can be made to any convenient chassis point. A useful addition would be a 2-pin mains outlet on the rear panel to feed the gram motor or other ancillary equipment. This would be taken from the 240V connections on the mains transformer, to operate via the amplifier on-off switch. Note that the earth connections to any ancillary equipment comes automatically from the amplifier, and should not be connected to a separate mains earth, which would invariably result in excessive hum.

TESTING

Switching on any equipment for the first time always gives one a little concern, wondering if a mistake has been made somewhere, and if something is going to blow up, knowing that fuses do not always blow quickly enough to prevent damage.

Anyone feeling this concern can alleviate it in this case, simply by removing the fuses, and soldering 0.5W resistors of 4.7Ω to 10Ω in their place. Switch on; the resistors will only become warm, particularly the one in the positive line, if everything is well, but will immediately burn if a serious fault exists. One can then switch off before any damage is done, locate the fault and try again, replacing the fuses when satisfied that all is well.

A check can now be made on the voltage readings, starting at the fuses and working forward. The voltages shown are approximate, small variations can occur due to component and transistor tolerances. During this check the volume control should be at minimum, and resistors of 15Ω (or thereabouts) connected in place of each speaker. The resistors need only be ½W or 1W as the amplifier is not delivering any power (or shouldn't be).

Switch the meter to a.c. (25V) and check that no voltage appears across the speaker sockets at any position of the volume control, tone controls, and selector switch. An a.c. reading of 10-15V would indicate r.f. instability, and the resistor across the speaker sockets would overheat. This would only occur if the layout or wiring differed from that shown

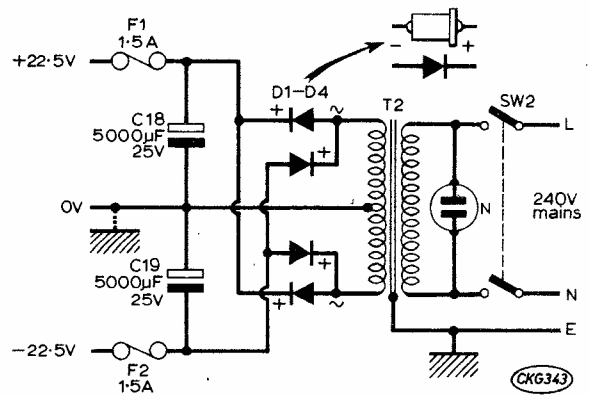


Fig. 9a: The circuit of the power supply.


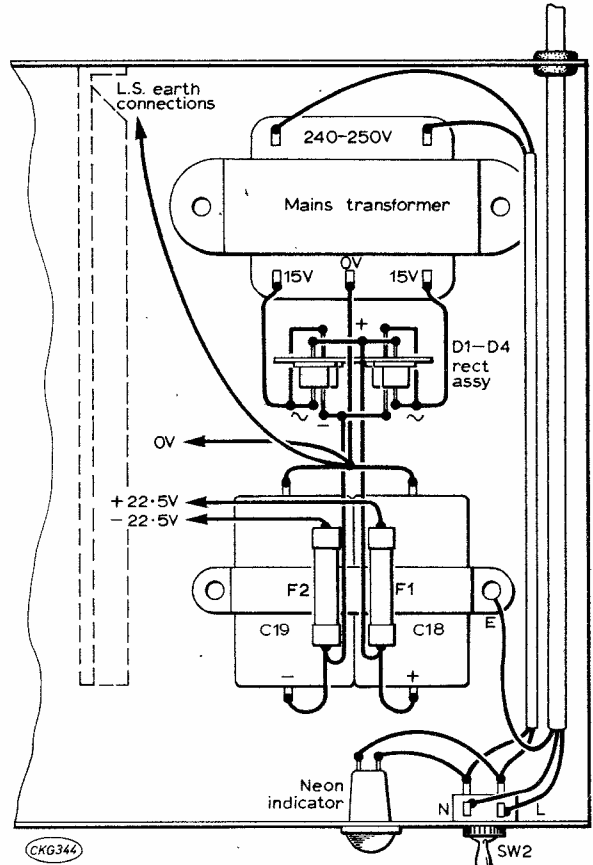


Fig. 9b: The layout of the power supply.

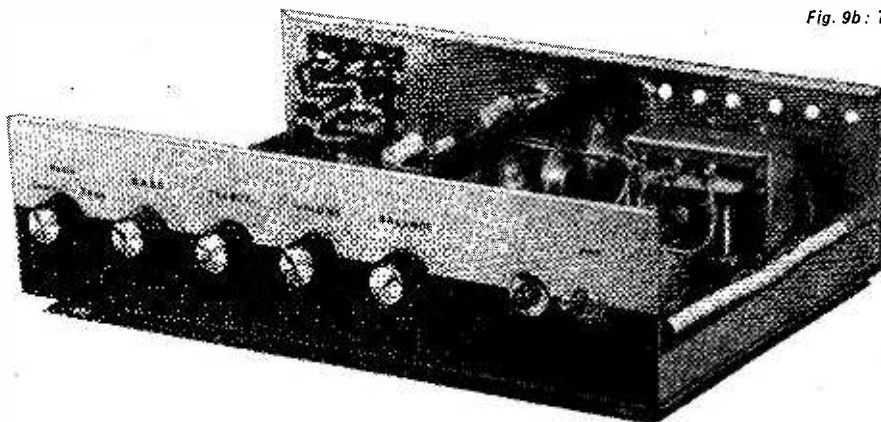

to create stray coupling and hence r.f. feedback. The cure would be to connect a by-pass capacitor of 100-250pF from collector of Tr2 to Tr3 to chassis.

The amplifier is now ready to go, and speakers and inputs can be safely connected. Choosing loudspeakers and a record player deck can present a problem to some people. The short answer is to pay as much as one can afford. ■

practically wireless commentary by HENRY

No. 96

Protection
Racket

THE nearest approach Henry ever made to the Grim Reaper—in the course of duty—was when some well-meaning idiot omitted to remove the short-circuit from the safety switch of the supply unit of a high-powered transmitter

True, it was impossible to work on the Army's '10-set' once any of the rack-mounted units had been slid from its rails. A link of wire across the safety-switch contacts became routine test procedure. But lying there, while the petrol-driven generator pumped futile fumes across Breedon Moor, and the Naafi wagon was miles away was no recommendation, for a trust in protective devices.

Hence, perhaps, my present suspicion that regulation, control and 'protection', when not forced upon an electronics manufacturer by



"Oh, but it shouldn't!" cry the makers.

law, is usually a kind of gimmick, spawned from convenience, nurtured in wrath, weaned by ingenuity and matured in advertisement.

In particular, the curious convolutions of audio circuit producers (not designers, for Henry is painfully aware that these gentlemen languish in a limbo, surveying the prostitution of their ideas by the pimps of commercialism) result in tinselly circuits with curious protection gadgets, tweaked to safeguard the precious output devices against the ham-

fisted handling of the common herd. It causes a budding circuit maker to wonder where expediency leaves off and practicality takes over.

Often quite passable output stages are ruined by utter instability when the supply voltage wanders a touch or two. 'Oh, but it shouldn't', cry the makers. 'The British mains supply system is the best in the world.'

O.K. Henry goes along with that. But, even so, when, on Sunday morning, all the pinafores aspirants to Womens Lib are chickening in; or on Saturday evenings, when the great British public (sorry, public) is tuning in to David Coleman and that travesty of human behaviour we laughingly call 'Sport'; then, and during those episodes of televisual dramuck that bring a paler shade of Whitehouse to the cheek, the mains supply voltage drops to a level where a Tandberg tape recorder refuses to rewind, a Quad amplifier forgets its steep transfer curve has certain advantages and ninety-nine from a hundred average radios rampage into avid crossover distortion.

For some reason connected with out insular arrogance, British designers expunge the idea of true regulation, protection and control. At the very least, we find a series regulator in the American (well then, Japanese) importations.

Henry is always amused by those models with cut-outs, which pop off dramatically when the impedances of loudspeakers (usually Scandinavian in origin) hit them below the belt. There are others, more genteel, which choke themselves into silence with a strangulated burp, waiting for you to light a cigarette, apologise to the dollybird you were hoping to impress, and switch on again—hoping the fault has now disappeared.

Protection circuits, *per se*, bring trouble. For every attempt by a well-meaning designer to cherish

his brain-child, there will be one or two electronic catastrophes.

For protection in *excelcis* we turn to the Whichdogs of the Consumer Council (past, present or future—what's in a name?) and some Naderish fumings from across the Atlantic. If you spent an evening, or, God Help You, a cocktail half-hour, in the presence of George Darling, M.P., who steered the Trades Description Act through Parliament, you



... the dolly bird you were hoping to impress.

would come away believing that every maker of electronic equipment conspires to do you down.


I don't think that is quite true. Seems more like the maker of electronic equipment fearing the user will do *him* down. Why else would Sony label their cassette cutout feeler a 'miserase protecting lever'?

There's a famous amplifier with a delicious FET protection circuit, with a diode from gate to source. The driver stage is wonderfully protected, yes? But when things go wrong, the mid-rail flies up to 55 volts and that driver is only rated at 40V. It goes up in smoke, taking its 47-ohms emitter resistor with it, and often the 2N3055 output transistor as well.

It's about time we constructors were protected from the misborn circuitry and afterthought mods of manufacturers. What about it lads? Join UPESCO—the Union for the Protection and Encouragement of Suffering Constructors.

3-Range Crystal Marker

R. F. GRAHAM

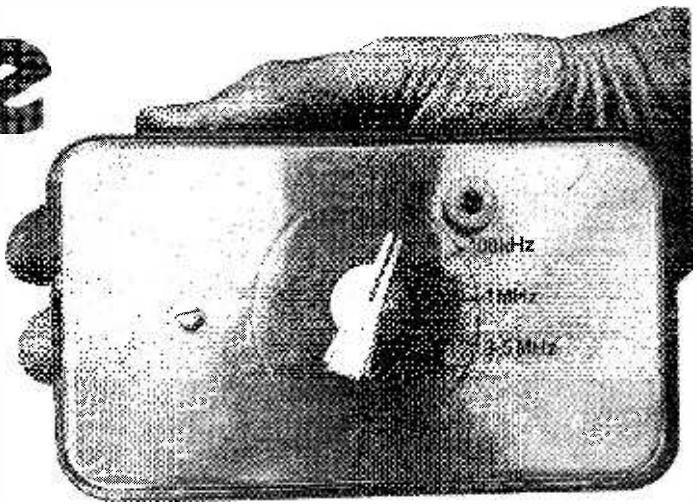

A CRYSTAL marker is used to calibrate receivers, signal generators, transmitter v.f.o.'s and similar equipment or to check their calibration. The marker described here is self-contained and requires few components. Details of typical uses are given later.

CIRCUIT

Fig.1 is the circuit, the single BFY51 transistor operating as a crystal controlled oscillator having three fundamental frequencies selected by a 3-pole 4-way switch. S1a and S1b select one of the three crystals, 100kHz, 1MHz or 3.5MHz. The remaining switch position is "Off."

When the 100kHz crystal is in use C2 is across L1, and the core is adjusted to approximately this frequency. For the higher frequency crystals C2 is not connected, the windings of L1 acting as an r.f. choke. Output is taken from a coupling winding and isolating capacitor C3.

With the unit operating at 100kHz this frequency and its harmonics or multiples will be heard on a receiver. Harmonics such as 500, 600, 700kHz up to

1500kHz allow easy calibration of a receiver or tunable signal generator in the medium wave band.


Higher harmonics of this frequency are used for general short wave calibration, or the calibration of a transmitter v.f.o. For example, 1.8, 1.9 and 2.0MHz harmonics for Top Band and 3.5, 3.6, 3.7 and 3.8MHz for the 80m band.

When tuning, especially on higher frequencies, a quick indication of 1MHz points is useful and harmonics of the 1MHz crystal will be found at multiples of this frequency—2, 3, 4, 5MHz and so on.

For amateur band reception, in particular, a band-edge crystal is extremely useful. That fitted here is 3.5MHz, its harmonics appearing at 7.0, 14.0, 21.0 and 28.0MHz as well as the fundamental at 3.5MHz and harmonics 10.5, 17.5 and 24.5MHz which are, of course, remote from amateur bands.

CONSTRUCTION

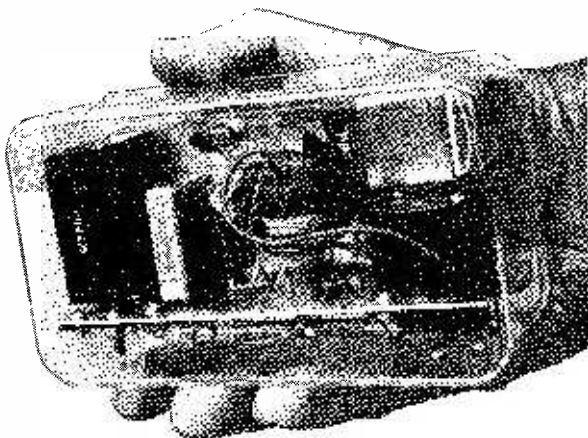A piece of sheet aluminium 5 x 4in. is bent as in Fig.2. The whole unit is assembled on this and will afterwards fit in a plastic box approximately 5½ x 3 x 2¾in.



Rear view of the finished unit mounted in a plastic box.

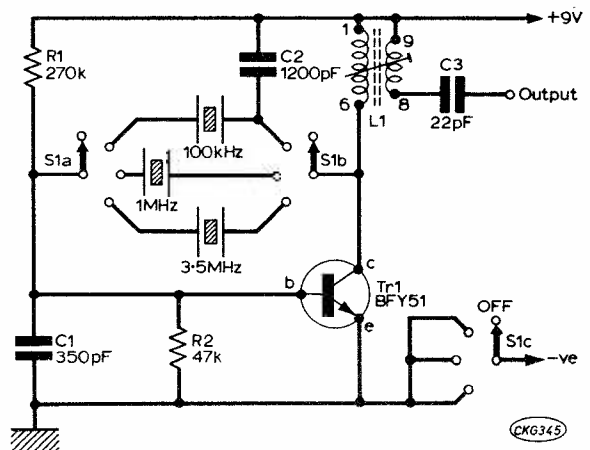


Fig. 1: Circuit diagram of the crystal marker.

Crystal holders to suit the particular crystals used are bolted as in Fig.2. The box lid is also drilled for the switch, output socket and a small bolt to hold a battery clamp. Heavy pressure during drilling may crack the plastic, so a little care is required.

The transistor and most other small components are supported by soldering their leads directly on to the switch tags. Run leads X-X down through a hole to one crystal holder, leads Y-Y to the second holder and connect Z-Z similarly to the remaining holder. A card marked with the switch positions is placed between the case top and metal panel and held together by the switch nut and output socket. A hole is drilled to fix a piece of metal shaped to secure the 9V battery to the left of the switch.

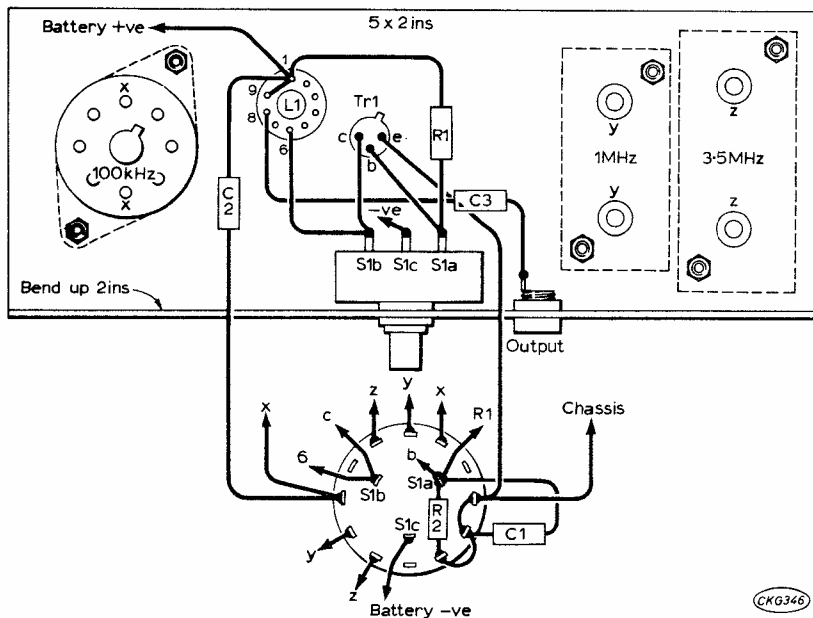


Fig. 2: Layout of components on chassis with details of switch connections.

★ components list

Resistors

R1 270k Ω R2 47k Ω $\frac{1}{2}$ W 10%

Capacitors

C1 350pF C2 1200pF C3 22pF

Crystals

100kHz, 1MHz and 3.5MHz surplus types with holders to suit.

Miscellaneous


Tr1, BFY51. L1, "Yellow" Range 1 (Denco valve type). S1, 3-pole, 4 way wafer switch. Aluminium 5 x 4 in. Plastic box $5\frac{1}{2}$ x 3 x $2\frac{3}{8}$ in. approx. Knob. Insulated socket. Battery 9V with terminal clips.

ADJUSTMENT

Rotation of the core of L1 allows the second harmonic of 100kHz crystal to be moved slightly in frequency to secure zero beat with the BBC on 200kHz or MSF on 2.5 or 5MHz. When the marker signal and received transmission are about the same strength, the frequency error of the harmonic will be heard as a low pitched growl, falling to a repetitive swishing sound, or flutter, or seen as a rise and fall of the receiver tuning meter, as the error is reduced. In any case at frequencies of 1MHz and higher the error will be only a few parts in a million and accuracy is higher than necessary for any ordinary purpose.

IN USE

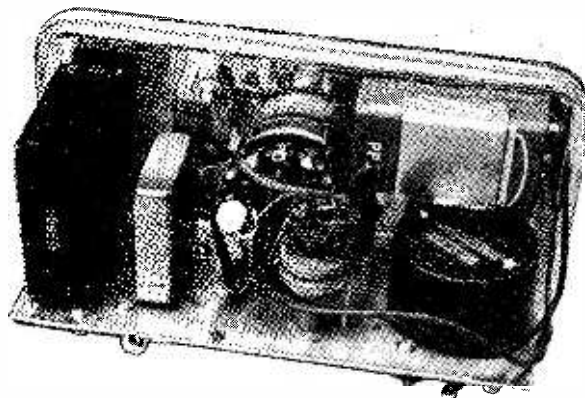The output can be coupled to a receiver by a short lead plugged into the socket and placed near the receiver, or near a short wire in the receiver aerial socket or plugged into the receiver, depending on the



Another view of the crystal marker. The transistor is wired directly on to the switch tags.

strength required. Harmonics grow progressively weaker and the limit to which they can be detected depends on receiver sensitivity. The marker signal is unmodulated, so the receiver b.f.o. should be on and set to zero.

To calibrate a tunable generator or v.f.o., couple its output to the receiver and tune the v.f.o. or generator to zero beat with the appropriate crystal harmonic. The receiver is tuned to the wanted frequency, but receiver tuning has no effect on calibration in this case. The b.f.o. is not in use in this instance.

VFO calibration at 50kHz points can be achieved by tuning the receiver to the second harmonic of the v.f.o., and 100kHz points provided by the crystal will then fall at 50kHz points on the v.f.o. scale. The 10kHz points can be estimated from the v.f.o. scale.

Harmonics can be used to adjust r.f., mixer or i.f. stages for best results, using a meter to read cathode or emitter current of an a.g.c. controlled stage. ■

IN NEXT MONTH'S

PRACTICAL WIRELESS

THE 'digitronic'


SOLID-STATE DIGITAL CLOCK




*"Hickory, Dickory, Dock,
Just look at our Digital Clock!
With four figures or six,
Using just thirty bits,
No winding, no ticking, no tock!"*

FREE inside

6" x 5" TRANSFER SHEET

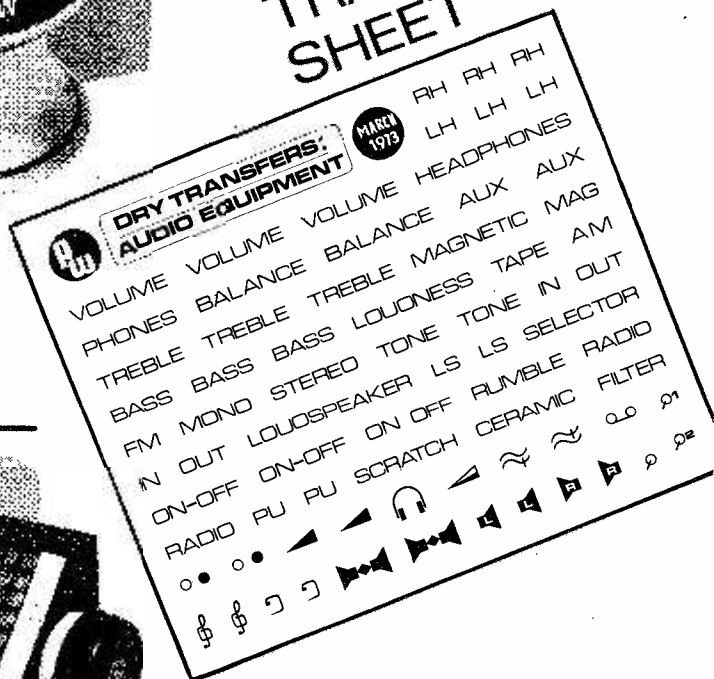

electronic MAZE

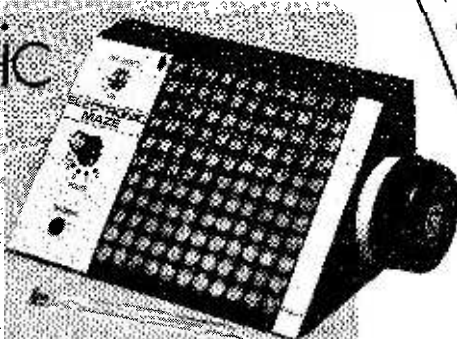

Here's a project which will give all ages hours of fun—an Electronic Maze. Using the probe, thread your way across the matrix, avoiding the dead ends and false trails; a delay circuit adds the touch of skill that makes the game such fun. A variety of routes can be selected simply by switching. The cost? About £2 all in but it will keep everyone amused for hours.

The finishing touch . . . that's what our panel transfers will give to your audio projects. They have been specifically designed for P.W. readers. Using them is simple—the process is entirely dry; just cut out the relevant section, peel off the backing and rub down.

MANY OTHER CONSTRUCTIONAL ARTICLES PLUS ALL THE REGULAR FEATURES. PRICE 20p.

ALL IN THE MARCH ISSUE ON SALE 2nd FEBRUARY

THIS receiver features modular construction, easy accessibility of units, and complete coverage from 150kHz to 30MHz. It will thus provide reception on long, medium and all the short wave bands from about 200 to 10 metres.

To facilitate construction, wiring and testing the receiver is built as three units—a mixer-oscillator assembly using a dual-gate field effect transistor mixer with separate f.e.t. oscillator; a high gain 2-transistor intermediate frequency amplifier; and a 4-transistor audio amplifier and output section. These units are then assembled into a case which carries the panel and a chassis with coils, etc.

MIXER-OSCILLATOR

The circuit for this unit is shown in Fig. 1. Tr1, a 3N141, is the mixer, with the signal fed to G1 and oscillator input to G2. Output from this stage is from the drain to the 1st i.f.t. of the i.f. unit.

Tr2, an MPF102, is the oscillator with injection to G2 of the mixer via C4. The feedback windings 8-9 of the oscillator coil L2 provide feedback from the drain to the gate of Tr2, to enable this stage to oscillate.




Coils are fitted in pairs, "Blue" in the L1 position and "Red" for L2. Coverage is approximately as follows:

Range 1	150-500kHz	2000-750 metres
Range 2	515-1545kHz	580-194 metres
Range 3	1.67-5.3MHz	180-57 metres
Range 4	5-15MHz	60-20 metres
Range 5	10.5-31.5MHz	28.9.5 metres

Range 1 is for long waves, but in this circuit the i.f. is 470kHz so coverage has had to be curtailed from that listed above or instability arises at the h.f. end of this band. This is easily done by marking the scale for Range 1 to suit. An alternative is to solder

GENERAL CO RECEIVER


F. G. RAYER G30GR

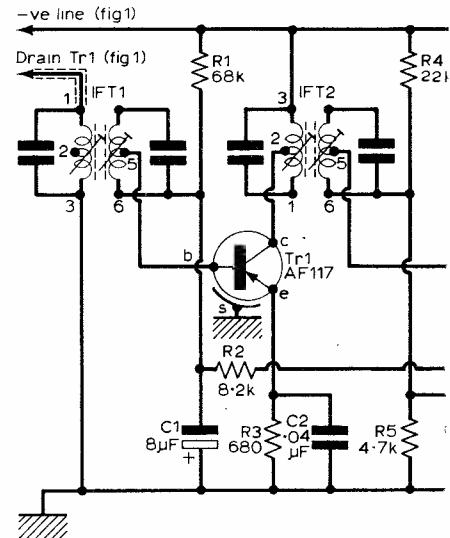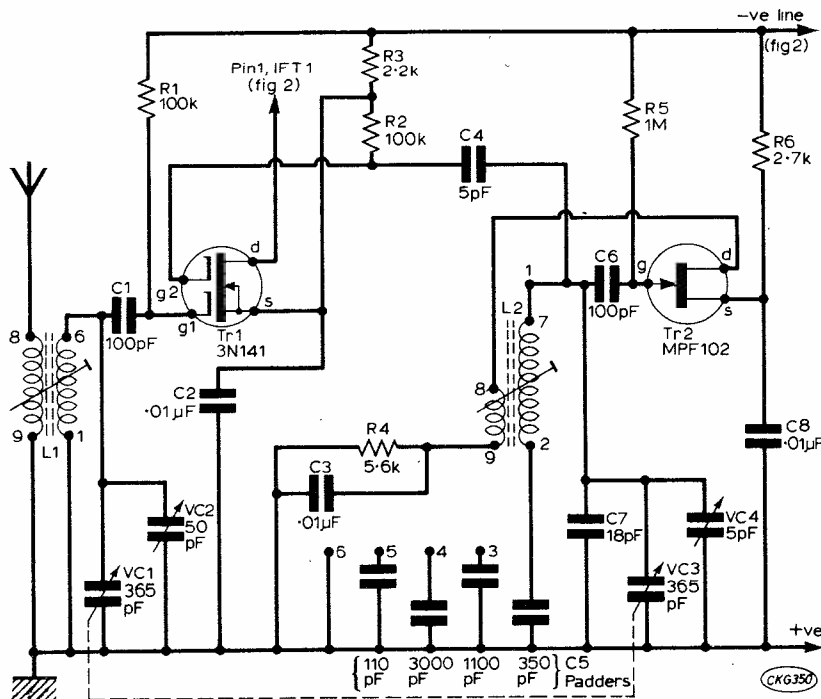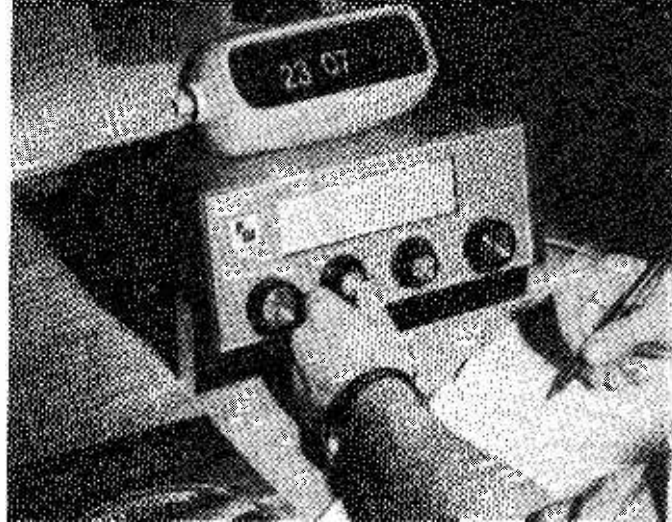

◀ Fig. 1: Circuit of the mixer-oscillator board.

GENERAL COVERAGE RECEIVER

F. G. RAYER G30GR

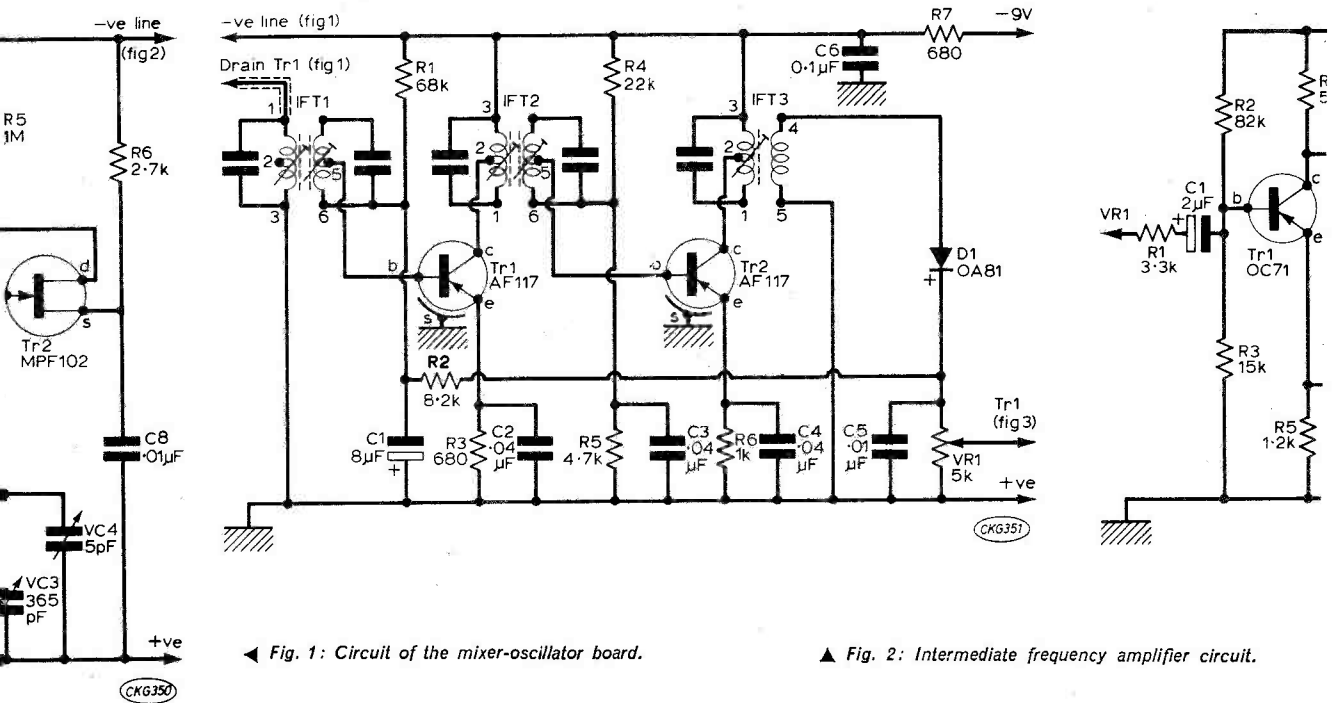

OVERAGE



a 50pF capacitor directly across the tuned section of Range 1 coils. Such capacitors must not be fitted at the holder because of their effect on other ranges.

Range 2 is for medium waves, while the remaining ranges are for the higher frequencies. Actual coverage can be modified somewhat by adjusting the cores.

Plug-in coils as used at L1 for aerial tuning and at L2 for the oscillator have several advantages. Construction and wiring are simplified when compared with the permanent fitting of all coils and a multi-way bandswitch. With plug-in coils, it is also a simple matter to obtain only those coils for the bands required. Coils for other bands can always be obtained later and no changes have to be made to the receiver to allow them to be used.


A panel aerial trimmer VC2 is fitted which has the advantage that the aerial circuit can be peaked up for best results with any aerial, on any frequency. Tuning on the higher frequencies becomes critical, so the bandspreading capacitor VC4 is provided for fine tuning. No additional bandspreading capacitor is necessary for the aerial coils.

Ranges 1, 2, 3 and 4 have their own oscillator coil padders, 110pF for Range 1, 350pF for Range 2, 1100pF for Range 3, and 3000pF for Range 4. No padder is used for Range 5. These padders go respectively to tags 5, 2, 3, 4 and 6, as in Fig. 1. The coils are so made that the correct padder is automatically in circuit when a coil is inserted.


IF AMPLIFIER

Fig. 2 shows the intermediate frequency amplifier which has two double-tuned i.f.t.'s and one single tuned i.f.t. This results in good selectivity and gain.

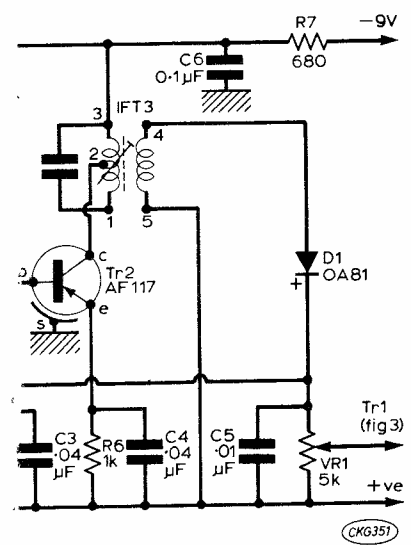Diode D1 is the demodulator which also provides automatic gain control bias through R2 for Tr1. Audio signals are taken from the volume control VR1 to the a.f. amplifier.



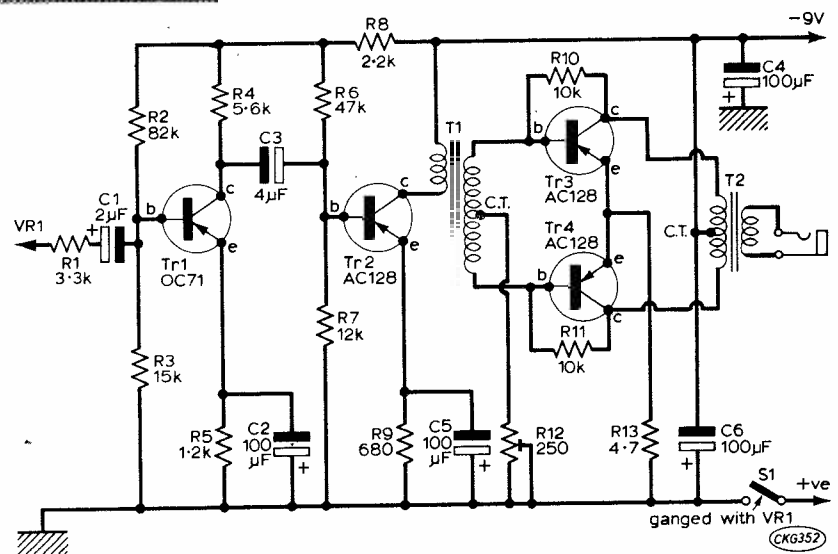▲ Fig. 2: Intermediate frequency amplifier circuit.



▲ Fig. 3: Circuit of the audio amplifier and output stages.

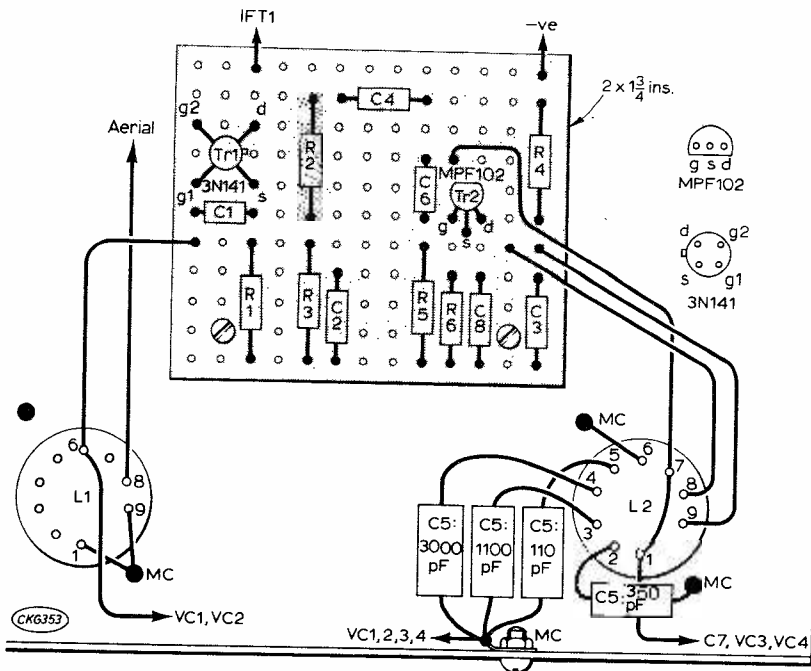


Fig. 4: Layout of the mixer-oscillator board and wiring of padding capacitors.

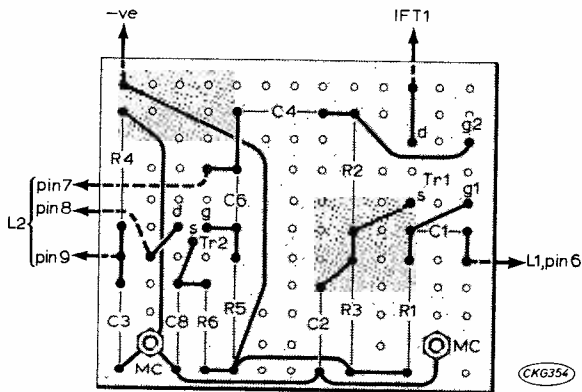


Fig. 5: Underside wiring of board shown in Fig. 4.

AF AMPLIFIER

The circuit for this section is shown in Fig. 3. Tr1 is the 1st a.f. amplifier, followed by the driver Tr2. The driver transformer T1 couples to the push-pull output pair Tr3 and Tr4 and T2 is the output transformer for a 2 or 3-ohm speaker. The pre-set R12 is adjusted for proper operating conditions in the output stage.

This type of circuit gives plenty of amplification and output. Its great advantage lies in the fact that the d.c. operating conditions of each stage are isolated from other stages, so it is not necessary to use matched sets of transistors. Some simplification would be possible by omitting Tr1 and taking C1 to the base of Tr2, though the extra stage of amplification is useful with weak signals.

MIXER-OSC BOARD


This section is wired on a piece of plain Veroboard 2 x 1 3/4 in. Do not remove the shorting ring from Tr1 until the transistor is fitted in the way explained.

Two 1/2 in. 6BA bolts with tags are secured in the positions in Figs. 4 and 5. Extra nuts on these space the board from the metal chassis to clear wiring. These bolts also provide a chassis return when the board is fixed to the chassis.

Resistors and capacitors are positioned as in Fig. 4. The board is turned over and wired as in Fig. 5. Place sleeving on leads where necessary. Veropins can be inserted for external connections, or flying leads can be left for this purpose and cut down to length later. Leads run from C1 to pin 6 of L1, from Tr1 drain to pin 1 of i.f.t.1, from C6 to pins 1 and 7 of L2, from Tr2 drain to pin 8 on L2 and from C3 and R4 to pin 9 on L2. These pins or leads are identified by locating them as in Fig. 4. A pin or black lead is also required for the negative connection, which runs to a pin provided on the i.f. board.

Tr1. This should be supplied with a shorting collar, spring or ring, which is left in position until Tr1 is fitted. With an insulated gate transistor, static charges from the fingers, or a metal or plastic tool, can damage the unprotected transistor. Spread the wires with a matchstick or piece of wood so that they can be inserted in the holes shown in Figs. 4 and 5. Solder drain and source leads. Solder the G1 lead by keeping the iron in contact with the R1 side of the joint, and the G2 lead by keeping the iron against the R2 side of the joint.

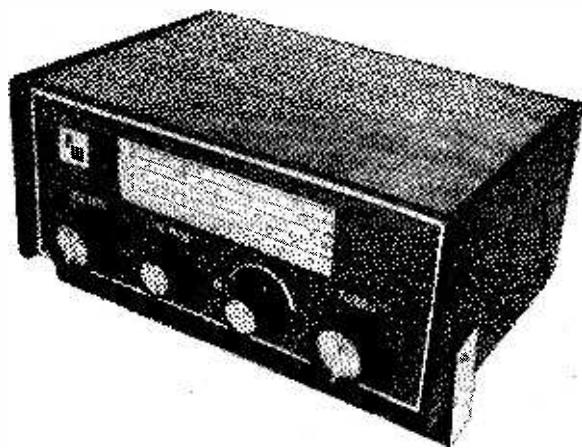Once the transistor is fitted, it is protected by R1, R2 and R3, and the shorting spring can be pulled off. If it is necessary to unsolder this transistor, bind thin wire round the leads in advance. Do not touch the



General view of completed receiver with metal strap fitted to lift front edge.

unprotected G1 or G2 wires with the soldering iron, fingers or metal plastic tools.

Tr2. This transistor can be soldered in the usual way. A 3-lead holder was fitted for it primarily as a simple means of testing various transistors in the oscillator position.

When this section is finished, it is fixed with extra nuts as in Fig. 4, and the leads for L1 and L2 are cut and soldered. The 1/2 in. bolts should leave enough clearance between the chassis and joints, but a piece of card or other insulating material about 2 x 1 3/4 in. in size can be put under the board.

Fig. 4 also shows how the padders are wired. Do not forget the lead 6 to chassis for Range 5. Leads from pin 8, L1 and the chassis run to sockets at the back of the case for aerial and earth.

IF AMPLIFIER BOARD


This is 3 7/8 x 1 3/4 in. and the components are placed as in Fig. 6. Holes are drilled for the pins and screening can tags of the i.f.t.'s with a central hole so that the lower cores can be reached with an adjusting tool. A very small round file is useful here if some of the holes are not in quite the correct positions.

Two bolts MC with tags are fitted in the same way as with the mixer-oscillator board, to mount the i.f. amplifier and provide the positive chassis return.

When fitting the transistors bring them down to within about 3/8 in. of the board so that leads are reasonably short. Wires can be identified and short circuits prevented by putting 3/8 in. pieces of sleeving on them—green for emitter, blue for base and red for collector. Connections underneath are shown in Fig. 7. It may be found helpful to put red sleeving on positive circuits, black on negative circuits and some other colour on other wires.

Pins are inserted for the external connections—negative supply from R1 to the mixer-oscillator; mixer to i.f.t.1, pin 1; from R7 to negative on the a.f. amplifier and battery; and from D1 positive to VR1.

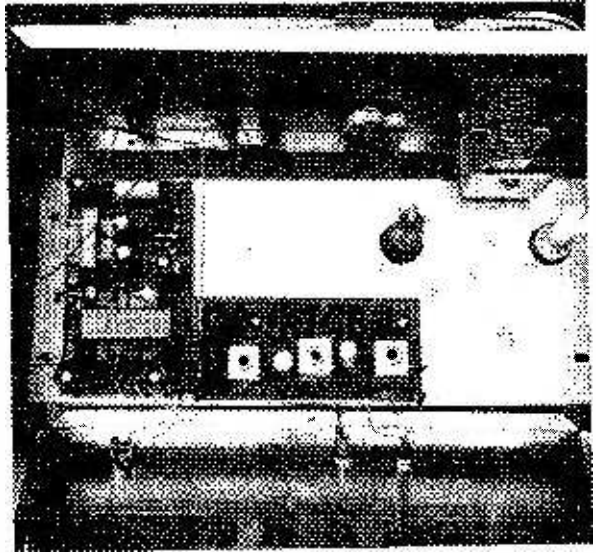The i.f. amplifier is fixed 3 1/4 in. from the end of the chassis, level with the back of the chassis, with i.f.t.1 towards the mixer-oscillator section. Fig. 4 is the underside of the chassis, but i.f. and a.f. sections are on top of the chassis.



View of receiver with sides and back removed to show placement of the i.f. and audio boards.


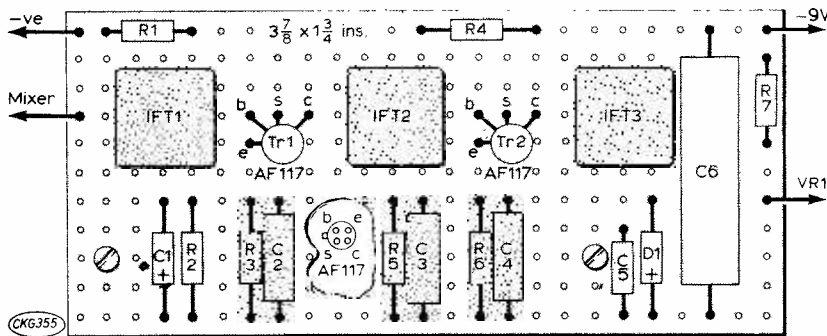


Fig. 6: Layout of components on the i.f. amplifier board and lead-out connections for the AF117 transistors.

Fig. 7: Wiring details under the i.f. amplifier board. Points marked MC are the bolts fixing the board to the chassis.

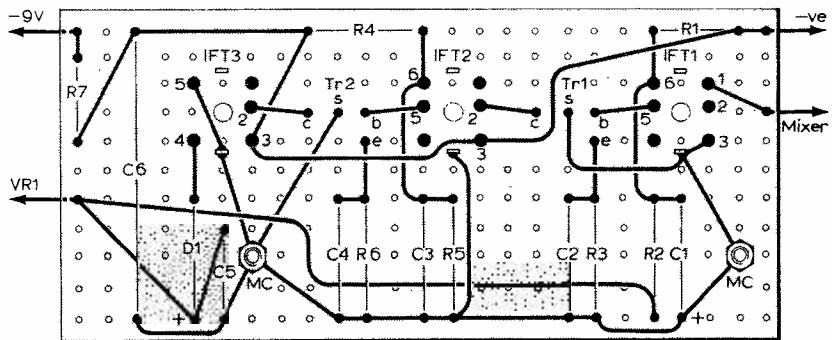

CKG356

AF AMPLIFIER BOARD

Components are placed as in Fig. 8, using a board $3\frac{3}{4} \times 2\frac{1}{4}$ in. in size. Bolts with tags are again used for chassis return and mounting with pins fitted for the junction of R1 with C1, for battery negative and for leads which will run from the secondary of the output transformer T2 to the loudspeaker.

Wiring should be straightforward as shown in Fig. 9. Coloured sleeving can be used to identify transistor and other leads, as already mentioned.

When this board is complete, it can be mounted in the space to the right of the chassis. Joints must be clear of the metal, or protection provided against shorts by placing card under the board, as described earlier.

CHECKING THE AF

The a.f. section may be checked by connecting a loudspeaker and providing a signal to R1 from a radio tuner, audio oscillator, pick-up or other source. VR1 should be in circuit to avoid overloading.

Initially set R12 so that little resistance is in circuit. With a 9V battery connected and the amplifier working, increase the value of R12 by moving the slider until the current is some 8mA to 10mA or so with no signal. Current peaks will be very much higher than this, increasing as the volume is increased.

Alternatively, R12 can be set to a position which results in clear reproduction with plenty of volume, though battery drain is increased if R12 is too high in value.

IF ALIGNMENT

The i.f. amplifier can be checked and aligned by itself or in conjunction with the a.f. section. VR1 must be connected and R1 of the a.f. section is connected to VR1; or phones may be connected to VR1, with an isolating capacitor in one lead to avoid upsetting the a.g.c. circuit.

As the i.f.t.'s are supplied pre-aligned, only a little adjustment of the cores should be necessary. If a signal is being obtained from the mixer-oscillator section, tune in a medium wave BBC or other stable transmission. Keep signal strength low by using a short piece of wire as an aerial, or by looping an insulated wire round the lead from pin 8 of L1. A proper tool is then used to rotate each core in turn, for best results. VR1 should be at maximum. A strong signal is avoided because it will operate the a.g.c. circuit and so make the correct core settings less precise. In any case, little or no adjustment of the cores may be needed, as explained.

If a signal generator is used, proceed in the same way, but couple the generator to the primary of i.f.t.1 by placing an insulated lead near pins 2 or 3. In this case, the mixer-oscillator section need not be in use.

★ components list

MIXER/OSCILLATOR

Resistors

R1 100k Ω R3 2.2k Ω R5 1M Ω
R2 100k Ω R4 5.6k Ω R6 2.7k Ω

Capacitors

C1 100pF SM C5 *
C2 0.01 μ F C6 100pF SM
C3 0.01 μ F C7 18pF SM
C4 5pF SM C8 0.01 μ F

* Padders:—110pF, 350pF, 1100pF and 3000pF

All silver mica

VC1/3 2 x 365pF gang (Jackson Type 02)
VC2 50pF variable (Jackson Type C804)
VC4 5pF variable (Jackson Type C804)

Semiconductors

Tr1 3N141 Tr2 MPF102

Inductors

L1 Denco "Blue" valve type for ranges required
L2 Denco "Red" valve type for ranges required

Miscellaneous

Valveholders B9A (2). Veroboard, plain, 0.15in. matrix 2 x $1\frac{1}{2}$ in.

IF AMPLIFIER

Resistors

R1 68k Ω R4 22k Ω R7 680 Ω
R2 8.2k Ω R5 4.7k Ω VR1 5k Ω pot.
R3 680 Ω R6 1k Ω with switch S1

Capacitors

C1 8 μ F 4V C4 0.01 μ F
C2 0.04 μ F C5 0.01 μ F
C3 0.04 μ F C6 0.1 μ F

Semiconductors

Tr1 AF117 Tr2 AF117 D1 OA81

Miscellaneous

IFT1/2 (Denco IFT18/465). IFT3 (Denco IFT14/465)
Veroboard, plain, 0.15in. matrix $3\frac{3}{8} \times 1\frac{1}{2}$ in.

AF AMPLIFIER

Resistors

R1 3.3k Ω R6 47k Ω R11 10k Ω
R2 82k Ω R7 12k Ω R12 250 Ω pre-set
R3 15k Ω R8 2.2k Ω R13 4.7 Ω
R4 5.6k Ω R9 680 Ω
R5 1.2k Ω R10 10k Ω

Capacitors

C1 2 μ F 6V C4 100 μ F 10V
C2 100 μ F 6V C5 100 μ F 6V
C3 4 μ F 6V C6 100 μ F 10V

Semiconductors

Tr1 OC71 Tr2-3-4 AC128

Miscellaneous

T1, driver transformer 3.5 : 1 + 1. T2, output transformer 3 + 3 : 1. Veroboard, plain, 0.15in. matrix $3\frac{3}{8} \times 2\frac{1}{2}$ in.

All Resistors $\frac{1}{4}$ W 10%

Cabinet, etc.

Universal chassis sides, flanged 10 x 4in. (3), DL44 2 $\frac{1}{2}$ in. drum, DL34 Type G cord drive, DL31 tension spring, DL36A pulley wheels (2) drive cord. (All Home Radio). Perspex 10 x 4in. 3-ply wood, 10 x $7\frac{1}{2}$ in., 10 x 7in., $7\frac{1}{2} \times 4\frac{1}{2}$ in. (2), knobs, etc.


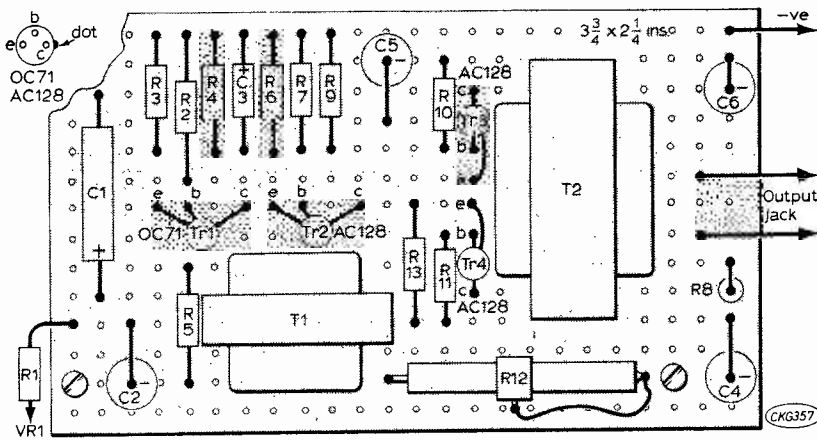


Fig. 8: Components on the audio stages board are placed as shown. Observe correct polarity of the several electrolytic capacitors.

Fig. 9: Wiring underneath the audio amplifier board. Again points MC are "earth" returns, via the fixing bolts, to the chassis.

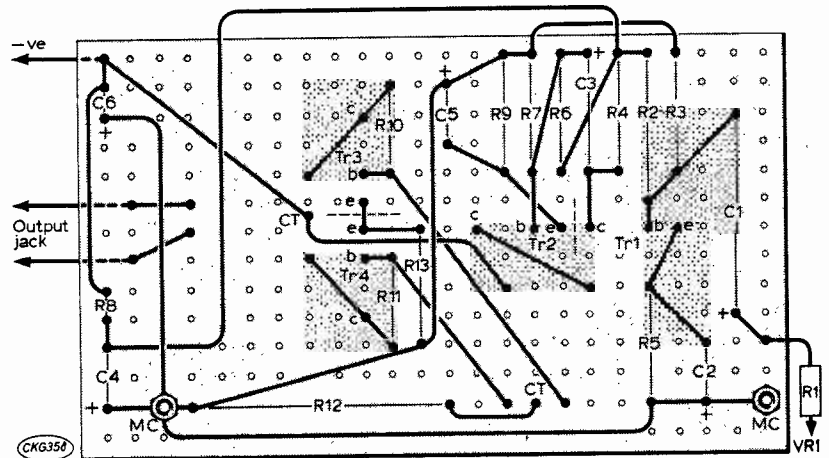

MIXER-OSC ADJUSTMENT

The mixer-oscillator is most easily tested and aligned when the receiver is otherwise completed. The coil adjusting screws are screwed in by the makers so that the coils can be placed in the cans in which they are supplied so initially all the cores have to be unscrewed several turns from this position.

Deal with each pair of coils separately. The cores can be locked with 6BA nuts when they are correctly adjusted.

Band coverage at the low frequency end of the band is adjusted by moving the core of L2. The core of L1 is adjusted so that near the low frequency end of the band signals peak up with VC2 nearly half closed. In these circumstances, it should be found that VC2 can be peaked for best results throughout the whole band. If it becomes necessary to close VC2 more and more, as the receiver is tuned from the h.f. end of the band towards the l.f. end, this shows that the core of L1 needs screwing in slightly. On the other hand, if when tuning in this way VC2 has to be opened more and more for best results, the core of L1 is too far in.

With the tuning capacitor VC1/3 fully closed, the frequency reached is lowered by screwing in the core of L2 and raised by unscrewing this core. This allows ranges to be adjusted so that there is some overlap between bands. A corresponding adjustment has to be made to the core of L1.

It should be found that alignment is not difficult, either by tuning in transmissions, or by using a signal generator. Maximum results will in any case be obtained if VC2 can be peaked for best volume throughout the whole of any range and is then seen not to be either fully open or fully closed.

R4 on Tr2 is the lowest value which does not result in strong spurious oscillations marring reception. The best value depends somewhat on Tr2 and is likely to be between about 1.2kΩ and 8.2kΩ.

CASE ASSEMBLY

Three 10 x 4in. flanged universal chassis members are used, one as the case front, one as the back and the third as a chassis to carry the three circuit boards and coil holders.

The sides are 3-ply, sanded and varnished, each 7 1/2 x 4 1/2in. The top is similar 3-ply, 10 x 7 1/2in. while the bottom is 10 x 7in.

A piece of 1/8in. perspex, 10 x 4in. backed by card, except for a window over the tuning scales, is also required for the front.

Fig. 10 shows how the case is assembled. Mark through the holes punched in the flanges of the 10 x 4in. members so that the wooden sides can be drilled. The back is flush. The 10 x 4in. member forming the chassis is set forward about 7/8in. and is 1 3/8in. above the lower edge of the back so that there is clearance for the mixer-oscillator board below, as well as for VC1/3 above.

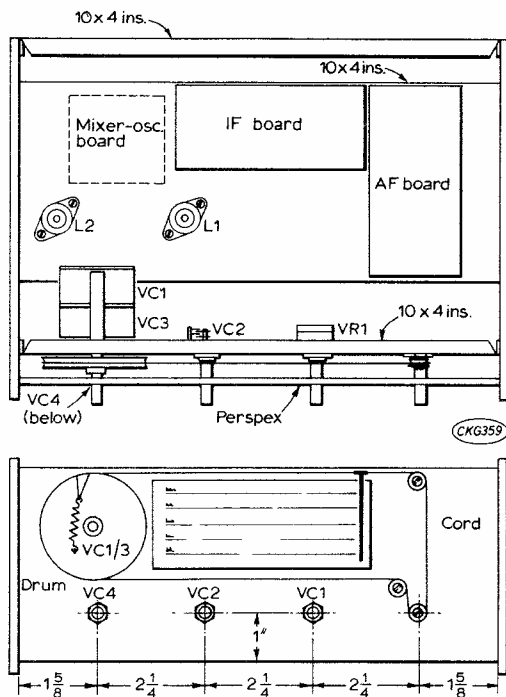


Fig. 10: Positioning of the major components on the chassis and front panel with details of the dial drive mechanism.

The front is set in lin. from the front edges of the side pieces as in Fig. 10. Drill the front for VC4, VC2, VR1 and the cord drive bush. Mark the same hole positions on the perspex, and drill clearance holes for the operating spindles. Also drill four holes to match with those punched in the front near the flanges.

When assembly is otherwise complete, the perspex is put in place and held with four lin. 6BA bolts, each with three nuts, so that it covers the drum and cord drive. A piece of card, with a cut-out through which the scales can be seen, fits behind the perspex.


Drill the front for VC1/3, fixing this with countersunk head 4BA bolts with extra nuts or spacers behind. The two wheels for the cord run on bolts as in Fig. 10. The cord has one complete turn round the driving spindle and is held taut by the spring in the drum.

The card for the scales is brought forward by means of a piece of wood about $\frac{1}{4}$ in. thick fixed to the 10 x 4in. member. A small piece of tinplate is cut and folded so that it can be clipped to the cord with pliers and a vertical wire pointer is soldered to this, the pointer and drum being as shown in Fig. 10 with the ganged capacitor fully closed.

The receiver can be wired and tested with the back, top and bottom completely removed, so that all units can be reached easily. The bottom is attached with three or four self-tapping screws. The top requires to be hinged, or provided with strips to hold it in place, so that it can be lifted off the case to change coils.

CALIBRATION

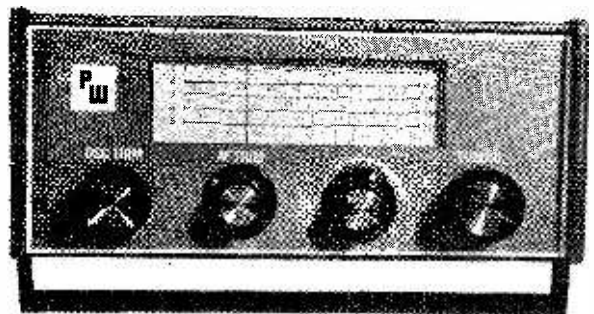
Markings are made before fitting the perspex. If the scales are to be calibrated in frequency first check coverage and ganging and fix the coil cores with 6BA nuts. Calibration is then most easily done



The markings of the four controls and dial calibration can be seen in this view of the receiver.

with a signal generator. This is set to various frequencies, the signal is tuned in on the receiver, and the appropriate scale is marked. Take care to avoid harmonics and second-channel responses, in the usual way.

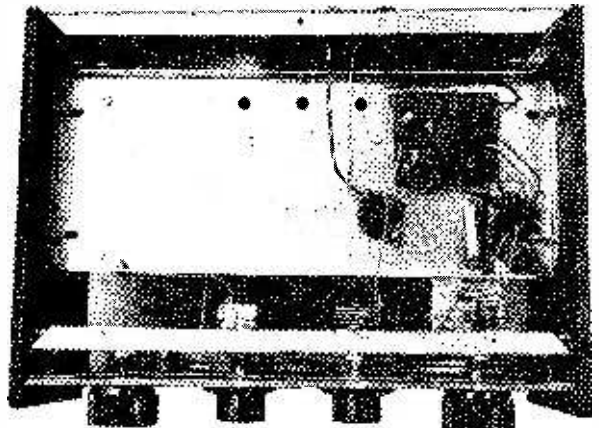An alternative is to tune in various bands, such as 19 or 31 metres, and mark these. Another possibility is to fit a 0-100 or similar horizontal scale, against which stations tuned in, or known frequencies can be logged. A rule calibrated in mm. will act as an easily obtainable ready-made scale.



Only the mixer-oscillator board and associated coil holders are mounted underneath the chassis.

AERIAL AND EARTH

Remember that conditions on the various frequencies vary enormously according to the time of day and other factors. Quite a large number of transmissions should be received with some 5ft. to 20ft or so of wire as an indoor or outdoor aerial. For weak signals in the 1.5-5MHz region, a longer aerial will make a great difference by improving signal strength. For good results on these frequencies, some 50ft. to 150ft. or so of wire as high as possible and clear of earthed objects, can be worth while.

Though many signals are sufficiently strong with no earth the use of an earth connection will give a worthwhile improvement in volume on some frequencies and often allow the reception of weak signals which cannot otherwise be received. An earth lead can be an insulated wire taken to an earth spike or other metal object buried in the ground. Where this is impossible, a counterpoise earth consisting of an insulated wire running near the ground or in an opposite direction to the aerial can be helpful. ■



ISSUES WANTED

- ..P.E. Aug. 1965, Sept. 1966, Nov., Dec., 1968, Jan., Feb., April, June, Aug., Sept., Oct., Nov. 1969. P.W. Jan., Feb., Mar. 1967.—A. G. Hodgett, 3, Ely Way, Felgate, Jarrow, Co. Durham.
- ..P. E. Mar. 1972.—G. Barracough, Rustic Gables, Waterhill Lane, Sowerby Bridge, HX8 2UA.
- ..Jan., Feb., Aug., 1970.—Dec. 71; July 1972; of P.W. Nov. 1969;—Sept. 70; July 1972, P. E. July 72.—E. E.—G. D. Lloyd, 28 Underhill, Bolham Road, Rivoton, Devon. EX16 6SF.
- ..buy, loan, exchange P.W. April, May, June, 1969.—W. L. Brunson, 28 Meadfoot Road, Wallasey, Wirral, Cheshire.
- ..wanted—March & April 1970 to P.W. containing articles on 'General Coverage RX' buy or loan.—C. MacAddhabhui, Machaire Gathian, Derrybeg, Co. Donegal, Ireland.
- ..November 1971 edn. 'Everyday Electronics' Cover price and postage paid.—T. C. Rickard, 10, Berridge Road, Sheerness, Kent.
- ..P. W. Nov. 1969, Dec. 1969, Jan. 1970.—R. P. Moore, 'Caton', Furnham Crescent, Chard, Somerset.
- ..Radio Constructor Aug. 1968, Jan. 1969, March 1969, April 1969, May 1969, June 1969, Aug. 1969.—R. J. McBride, 37, Border Street, Greenock, PA15 2EF, Renfrewshire.
- ..P. E. Sept. 1970 (Guitar pickup Construction).—A. D. Black, 16 Rosebury Avenue, Worthing, Sussex.
- ..Any W.W. or P.W. before 1930.—P. Kemmis, 92 Wildwood Road, London, N.W.11 6UD.
- ..Buy or borrow the May 1972 issue of "Television".—F. D. M. Wilson, 83, Marshal's Drive, St. Albans, Herts.
- ..P. E. August, containing the articles by A. Douglas on building an Electronic Organ, about March onwards I think.—E. Robinson, 171 Allendale Avenue, Aspley, Watlingham.
- ..Mar. and April issues (1972) P.W.—D. Mooney, 85 Audhineurk Road, Glenanne, Co. Armagh, N. Ireland.
- ..P.W. August—November 1967, willing to pay full price, or borrow to photocopy.—D. F. Boughey, 4 Milton Road, Birkenhead, L42 0JU.
- ..Wanted Practical Wireless for Jan., Feb., March 1972. I am ready to pay for them. M. Ilyas, 214 Golders Green Road, London, N.W.11 9AT.
- ..June 1971 P.W. to borrow or buy.—W. Kyle, 23, Lammermuir Drive, Potterhill, Paisley.
- ..March 1971, May 1971, October 1971.—E. McCaughey, 132 Foley Street, Dublin 1, Ire.
- ..May 1972 edition of P.W.—A. K. Bisset, 2 Brynteg Avenue, Bridgend, Glamorgan.
- ..Wanted issues of P.W. dated September and October 1971, willing to pay full price.—C. North 29 Kent Road, Harrogate, Yorks. HG1 2LJ.
- ..Practical Wireless: May 1971 to Sept. 1971 inclusive. Practical Electronics: Jan. 1971 to April 1971 inclusive and July 1971.—A. M. Cash, S. Codrington Road, Bristol, B27 8ET.
- ..pre 1972 P.W., P.E.; P.T.V.: Radio Construction.—N. Vaswaney, 28 Angus House, New Park Road, London, SW2 4LB.
- ..P.W. Feb. 1972 containing Part 1 quality Hi Fi System by C. R. Bradley.—P. Parker, 31 Fairview Handsacre, Nr. Rugeley, Staffs.
- ..Practical Wireless Vol. 46. (May 1970—April 1971). Also May and June 1971. Practical Electronics Vols. 5, 6, and 7 (Jan. 1969 to Dec. 1971). Also March 1972. Radio Constructor November and December 1968, August 1969 and May 1970.—M. Ridge, 25 Broomfield Crescent, Leeds LS6 3DD.
- ..January 1971 issue of Practical Wireless as I would like to build the stereo tape recorder described in that issue.—J. F. Heath, P.O. Box 355, Florida, Transvaal, South Africa.
- ..Practical Wireless for January 1968.—D. How, 25 Hillcote Avenue, Norbury, London, S.W.19 3BH.
- ..Practical Wireless Feb. and March 1972 (containing the transistorised oscilloscope) and the April 1972 issue. Also for the following: Handbook or any information on the Cossor Oscillograph Model 1049 Mk III.—B. S. Bainbridge, 7 Montclair Drive, Liverpool, 18.
- ..1971 December issue of Practical Wireless.—K. Avery, 22 Palington Grove, Canley 2, Doncaster, Yorks. DN4 6LP.
- ..August 1968 P.W. or plans for Portable Keyless Organ, also P.E. August to November 1968 containing Sound Light and Colour series.—W. Kelly, Cairns Cottage, Memsie, Fraserburgh, Aberdeenshire.
- ..Wanted P.W. Sept. and Dec. 1971.—C. Jones, 45 Currock Park Avenue, Carlisle, CA2 4DJ.
- ..P.W. May to August 1970 inclusive.—M. Hollamby, 310 Ifield, Crawley, Sussex. RH11 0EW.
- ..April 1971 P.W. also June, July editions P.W.—O. Wilson, 57 Bellevue Road, Berea, Durban, South Africa.
- ..wanted P.W. September 1971—March 1972.—R. A. Leigh 416 Birmingham Road, Bromsgrove, Worcestershire.

INFORMATION WANTED:

- ..supplier of E3016 i.c.—B.P. Hellbone, 44 Goring Valley Road, Lower Willingdon, Eastbourne, Sussex.
- ..any details, date of manufacture, circuit etc., of my Marconiphone Model No. 347, Serial No. C/1 12214, approx. 20 years old, WWII photocopy and return or buy.—R. J. Stone, 53 Burch Road, West Bridgford, Nottingham, NG2 8EQ.
- ..any info. dealing with modifications to the No. 19 set (March 1966).—W. Bryant, 50 New Road, Stokenchurch, H. Wycombe, Bucks.
- ..any info. on where I could purchase parts of P.E. Mercury 6 (one I.F.T.).—J. Baw, Esq., 2 Beatie Avenue, Hanstenton, Hereford.
- ..info. wanted on the A.T.V. No. 6, and also on the BC906 field strength meter.—A. Salisbury, 28 Dyke St., Brumby, St. Helens, Lancs.
- ..any info. on circuit etc. for Halicrater S40A receiver.—J. E. Ford, 68c East Hill, Dartford, Kent.
- ..circuit and details of Admiralty B28 receiver (Marconi CR100?).—A. G. Jones, 6 Cowey View, Llanelli, Carmar, SA15 3SN.
- ..info. on building Fluorescent 12V lights for Caravan 12" and longer.—E. Dale, 2 Fordham Square, Sunderland, SR4 0BB.
- ..circuit for a simple portable 2m Tx with banspread and BFO if poss.—S. Fletcher, G-14003, 35 Elm Grove, Norton, Bromsgrove, Worcs.
- ..info. regarding receiver type R4187, ST.C. ie. mods., for mains, manual, etc. loan or buy. J. Warrillow, 52 Lochdochart Road, Glasgow, G34 0BH.
- ..to loan or buy, instruction handbook for Hartley 13A oscilloscope and/or Cossor 1039M oscilloscope.—J. Banner, c/o Johnsons (Radio), St. Martins Gate, Worcester.
- ..circuit for T.C.S. receiver to loan or buy. Also any mods. welcome.—E. Pinder, 266 Clipsley Lane, Haydock, Nr. St. Helens, Lancs.
- ..any info. (Manual, C.D. Pin connections, etc.) on Ex Air Ministry Rx type 4187. Will buy or borrow manual.—G. Clear, 17 Christianfields Avenue, Gravesend, Kent.
- ..details of and discs for "Emidicta" Disc dictaphone, also manufacturers instruc-

- ..circuit diagram for stellophone twin track tape recorder type ST 451.—D. R. Lees, 62, Gwynfryn Avenue, Rhyl, Flintshire, LL18 2BE.
- ..Borrow, hire or purchase—operating manual for Mullard High Speed Valve Tester.—E. B. Dickson, 402, London Road, Carlisle.
- ..circuit of a voltage controlled oscillator and a ring modulator for sound machines L. Svenson, N. Bellevuevaag 5, S-370 20 Lyckeby, Sweden.
- ..gen and circuits for following RX's: Phillips, type 462 A-15, Invicta Model 510, Marconiphone, Model 296, Also any I.C. Data Sheets.—J. Rowley, 1, Wolverton Road, St. Andrews, Bristol, BS7 9BB.
- ..any gen and/or instruction manual on Air Ministry Receiver R89/ARN-5A.—F. Mitchell 68A, Shaftesbury Road, Wilton, Nr. Salisbury, Wilt.
- ..any info circuit diagrams etc. on a G.E.C. single unit V.H.F. transmitter receiver F.M. serial number 130 BRT205.—R. Brown, 13, Albertville Drive, Belfast, BT14 7BX, N. Ireland.
- ..Service manual for Lorax RX App 9-R65. Hire or buy.—F. J. Murphy, Big Street, Termonteeckin, Drogheda, Ireland.
- ..buy or borrow, manual for G.E.C. BRT. 400E receiver, Cash or?—F. J. Martin, 59, McFarlane St., Hamilton E, New Zealand.
- ..Loan of handbook and circuit for Eddystone 680X.—H. Vance, 13 Abbey Road, Enfield, Middlesex.
- ..any info on my old set, MW, LW, S1, S2, valve line up UU6, TH41, PEN45, HL4100, and YA11? Sockets for PU.A.E.L.S. Transformer type 2ER N5 B2012, 1 think.—B.P. Tolley, 36 Northumberland Avenue, Cleveleys, FY5 2LH.
- ..instruction manual and/or any gen regarding Ex-R.A.F. Communications receiver type R1155(a)—G.P.C. Low, 117, Andover Road, Newbury Berks.
- ..Details of a Music Synthesizer.—S. Sudarsono, Garstang Flats, Room 3-13, Mt. Preston, Leeds, LS2 9JT.
- ..Gen on Treco Scope (Serial S748) made by the "Range" Electronics Co., London —S. Franklin, 200 City Road, London, EC1V 2PH.
- ..any gen on English equivalents of Tap transistors in a Tech. Tradiper model TE15 grid dip meter. The numbers are: Toshiba 2(SB)54.—H. Britton, 14 Kennel-Green, Kings Heath, Northampton.
- ..a circuit for the construction of a simple musical rhythm unit.—G. Smith, 13 Dean Park Road, Plymstock, Plymouth, PL9 7NY.
- ..the address of "Viking Electronics" Ltd., of London. I have one of their "Viking Bass 40" amp, which has gone wrong and needs a circuit diagram.—D. Durrant, Puzzle Trees, Punnett's Town, Heathfield, Sussex.
- ..a circuit to build a reverberation unit to use with a Motorola car radio pos earth.—A. Hughes, 34 Culliford Way, Littlemoor, Weymouth, Dorset.
- ..wanted urgently, loan of manual or circuit for Erskine Model 13 Oscilloscope. Details to L. E. Howes, Assistant Editor, Practical Wireless, Fleetway House, Faringdon Street, London, EC4A 4AD

TELEVISION

FEBRUARY ISSUE

ASSESSING RECEIVER PERFORMANCE

How good is your set and how do you go about assessing the quality of the picture? This month we start a new series on subjective performance testing, i.e. without the need to use any test equipment.

CRT REJUVENATOR

This simple item costs very little to build but saves pounds by prolonging the life of old tubes—cathode reactivation can often in fact be a case of new tubes from old!

SHORT BACK-FIRE AERIAL

Here's a new one for aerial constructor enthusiasts to try out! Reg Roper reports on the excellent results he obtained recently using this type of aerial.

SERVICING TV RECEIVERS

In response to many requests, this month L. Lawry-Johns deals with the Philips T-Vette/Stella Companion mains-battery transistor portables.

PLUS ALL THE REGULAR FEATURES

ON SALE JANUARY 15th

Power For Ever!

9V BATTERY ELIMINATOR

M. WALLIS

HAVE you ever worked out how much it costs you using batteries rather than the mains supply for operating your equipment? Obviously it depends on the type of battery you use, what current you are drawing and how often the equipment is used but a quick calculation shows that the current costs about 2,000 times as much as operating through a power supply. Certainly a power supply costs rather more than a battery but this is rapidly recovered by savings in battery costs.

The unit described here is a replacement for the popular PP9 type of battery that is fitted in a number of the larger types of transistor portable radios. This battery is also very popular with amateur constructors. Although designed to replace the PP9 type, the circuit of course holds good for any 9V battery with a maximum current supply of about 80mA but the size of the unit described here may be too large to act as a direct replacement.

The cost of our battery eliminator is about £1, appreciably less than the commercial units available. In addition our unit is exactly the same size as the battery that it replaces—it is built inside the old battery casing—and so it will neither be too large, or too small, when in place.

THE CIRCUIT

The theoretical circuit is shown in Fig. 1 and is absolutely standard. The transformer (the type number and suppliers are mentioned in the components list) has a 7.0-7V secondary and this is connected to the rectifier diodes D1 and D2 giving full-wave rectification; this is then smoothed by the capacitor C1. The reason for the resistor R1 is to act as a bleeder, when the unit is on it will then be drawing at least 20mA and ensures that the peak voltage that may be present is never applied to the unit. With no load at all connected to the power supply, the voltage reaches well over 10V and this is

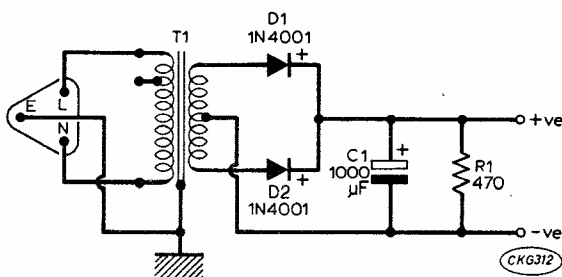


Fig. 1: The circuit of the battery eliminator.



not desirable as damage may result. As shown, with no load other than R1, the prototype measured 9.2V and with 80mA being drawn about 8.5V.

CONSTRUCTION

As can be seen from the photographs, the unit is built inside an old battery case. This has to be taken apart as follows:—

First, using a screwdriver, prise up the bent-over metal ridge that holds the top of the battery in place and work all around this, levering it up. Straighten this metal with pliers or the top will not come out easily and reassembly will be difficult. When this is done the entire contents of the battery will fall out.


The top panel with the snap-on contacts should be cut free of the connecting wires or bands of metal and put to one side. Just enough of the original metal on the underside should be left for making the connections later.

The circuit is built on a piece of drilled s.r.b.p. board with dimensions exactly $2\frac{1}{8} \times 2\frac{1}{2}$ in. Holes will have to be drilled in this to take the transformer mounting lugs which are then fitted through and bent over. The remaining components are "threaded" through convenient holes and soldered together as shown in Fig. 2. C1 is shown here very much smaller than it actually is to make this drawing clear; in fact C1 will be so large that it probably overlaps the diodes and R1. Both sides of the transformer have three wires coming out, the secondary is that with two brown and one blue wire, the primary has brown, blue and a green. The mains wire should be connected to the primary side to the brown and blue, unless you live in an area where the mains supply is 230V or below in which case the mains should be wired to the brown and green.

The earth wire should be stripped back and a

★ components list

R1	470Ω $\frac{1}{4}$ W, 10 per cent
C1	1000µF, 15V minimum
D1, D2	1N4001 silicon diodes
T1	Mains transformer with 7.0-7V secondary, type MT98 (Henry's Radio)
Hardboard, see text; Mains lead; Old PP9 battery; Drilled s.r.b.p. board.	

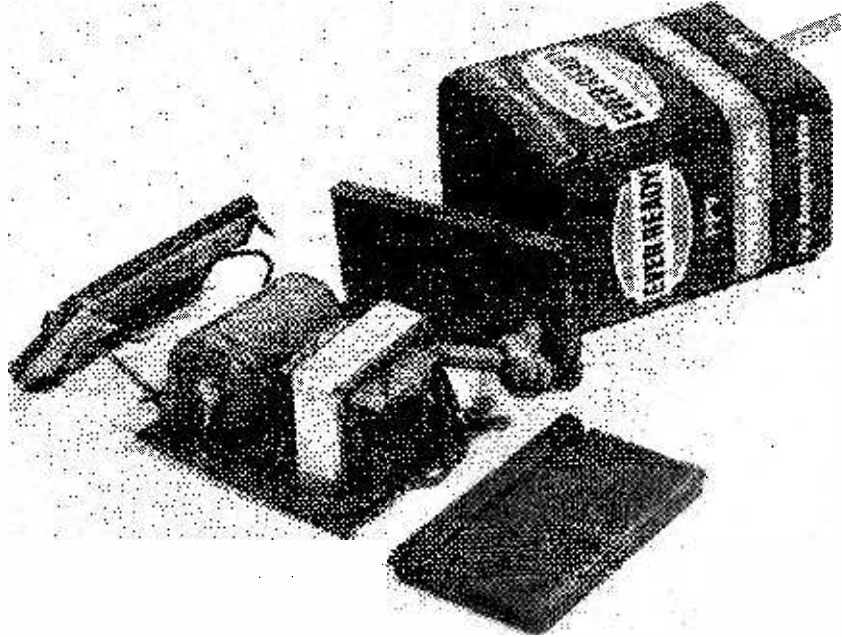

The prototype just before final assembly.

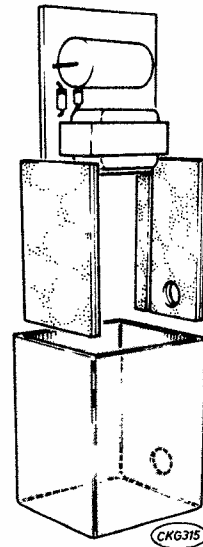


Fig. 4: How the unit fits together.

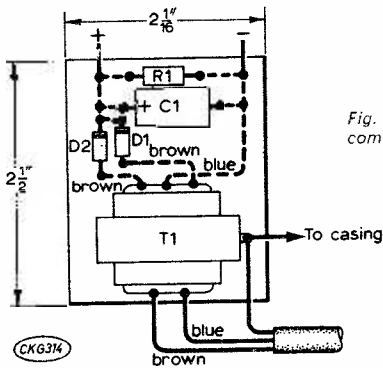


Fig. 2. The wiring of the components on the drilled s.r.b.p. board.

second short length of wire twisted with this and then both soldered to the case of the transformer. The reason for this is safety; this second wire will later be soldered to the battery case and if by any chance this solder joint breaks from the transformer, the battery case will still remain earthed.

Neither side of the 9V is shown earthed since it

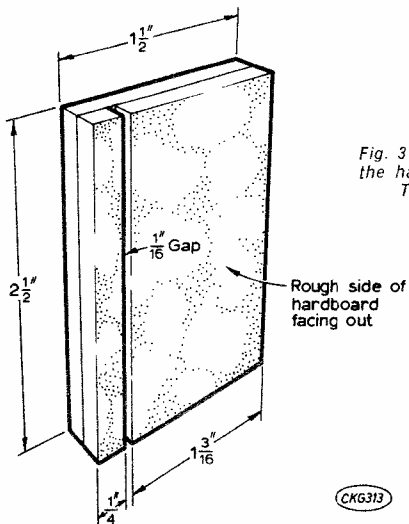


Fig. 3: The dimensions of the hardboard side fillets. Two are required.

will depend on the design of the equipment which side requires earthing. If the equipment is negative chassis, the earth should run to the negative side and conversely for positive earth equipment.

The circuit board is held inside the battery case by means of two side fillets made up from hardboard, the dimensions for one of these is shown in Fig. 3; the other is of course identical. Three pieces are needed for each and these are then glued together.

When the side fillets are ready they should be fitted inside the case with the circuit board to ensure that everything is a tight fit and that they don't rattle about. If all is well, the bits should be taken out and one of the side pieces replaced to make the hole for the mains wire, both the piece of hardboard and case should be drilled together to ensure that the holes line up exactly.

It is important that the mains lead is fitted through one of the short sides with the hardboard fillets as this will prevent it chaffing on the sharp metal case; a grommet will be of little help as the metal sides will cut right through it in a very short while.

A knot should be made in the mains lead as close as possible to the transformer, as can be seen from the photograph, this will prevent it being pulled away from the unit with possibly disastrous results.

The unit is then reassembled as shown in Fig. 4. This should leave three wires coming out of the top: positive, negative and the earth wire from the transformer casing. The last should be soldered to the metal casing anywhere inside. The supply leads are then fitted to the snap contacts, remembering that for a battery the female contact is the negative and the male the positive. The original top can then be replaced and this should rest on the side fillets.

Before completing the assembly, the unit should be tested to ensure that it works; taking it apart again can be quite a job. If all is well the top metal, which is standing proud, should be bent down to hold the top in place.

The dimensions for the fillets are only applicable to the modern Ever Ready PP9 batteries. Other types of batteries have different inside dimensions and this will affect the length of the fillets; in this case the dimensions will have to be worked out. ■

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

ONE of the disadvantages of being interested in radio and electronics is that you act as a magnet for faulty transistor radios and the like. Certainly you can say "No!" to requests to "have a look at it," but if you take this attitude you will not be very popular. Your author usually agrees, on the condition that mechanical troubles are not handled (broken cabinets, dial mechanisms etc) and that if replacement components are required it is up to the owner to get the bits. If you stick by these principles, repairs can be done very quickly but *only* if you have the right equipment. The most useful item is a multimeter—it is hopeless trying to work without one—but running a close second is a signal injector/tracer and this forms the subject of our project this month.

Inject

The circuit of the signal injector/tracer is shown in Fig. 1; SW1 alters the function and is in the "inject" mode. The circuit is a multivibrator producing a square-wave output at C1 to which a probe can be attached. The square-wave is in the audio range but it is so full of harmonics (a square wave is a fundamental frequency plus all its harmonics) that these go up to several megahertz. If you place a transistor radio on the medium wave band even near this circuit, the output will be heard all over the band. If we inject this signal at the volume control we will be able to establish if the amplifier part of the set is O.K.; if it doesn't work then we can concentrate our efforts in this direction.

If this is O.K. we can work back along the i.f. section and we shall eventually discover where the fault lies.

★ components list

R1	1M Ω , $\frac{1}{4}$ W, 5 per cent	1p
R2	2.7k Ω " "	1p
R3	1M Ω " "	1p
R4	2.7k Ω " "	1p
C1	3300pF disc ceramic	3p
C2	3300pF disc ceramic	3p
C3	3300pF disc ceramic	3p
C4	100 μ F, 10V minimum	5p
Tr1	BC109	10p
Tr2	BC109	10p
D1	1N914	7p
SW1	One-pole, 2-way slide switch	8p
SW2	On-off switch, toggle type	5p
	Crystal earpiece and jack socket	35p
		93p

Prices are those recently advertised and may have changed. No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

No. 45 SIGNAL INJECTOR/TRACER

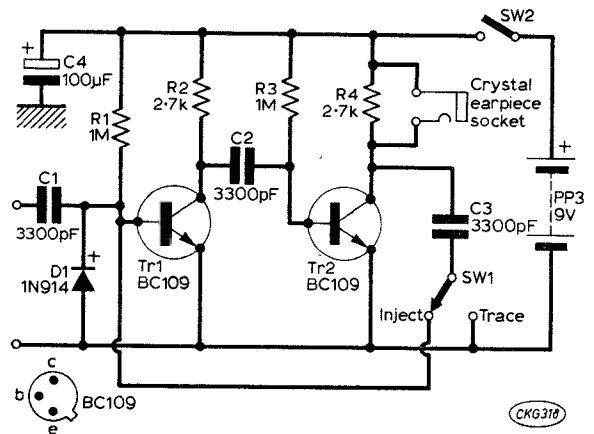


Fig. 1: The circuit.

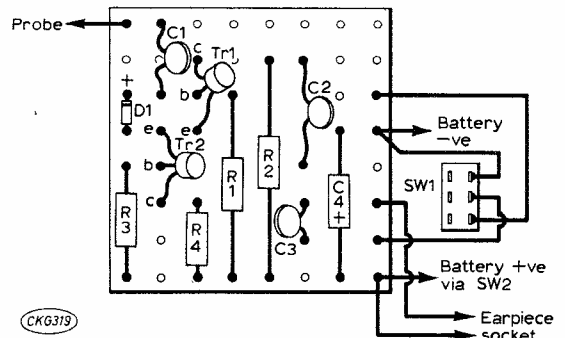


Fig. 2: Suggested layout on Veroboard.

Trace

When SW1 is switched to "trace", the circuit is no longer a multivibrator but becomes a highly sensitive amplifier. If the probe is fixed to an r.f. point the signal will be rectified by the diode D1 and amplified by both stages and fed to the crystal earpiece. It is smoothed by C3 which now, instead of coupling back to the base of Tr1, goes to the negative line.

The current drain of the unit is quite small and a PP3 battery is quite sufficient.

Two wires, fitted with crocodile clips, should be connected to the negative line and to C1 as these will be needed to couple the injector/tracer to the circuit under test. If using the injector at r.f. frequencies, the output is so high that the wire from C1 has only to be held near the aerial, it is not necessary to make a direct connection.

Construction

The components can be mounted in any convenient form but a suggested component layout is shown in Fig. 2; this is built on a small piece of Veroboard with 0.15in matrix, 8 x 8 holes; no breaks are necessary in the conductor strip. SW1 can be a small slide switch wired as shown; SW2 can take any convenient form.

at these prices you can afford instruments for your test bench

**under
£15**



Portable VVM
£13.80

The Heath range of low-cost testers and instruments in kit form fulfills the many and varied requirements of the practical hobbyist, the engineer and others engaged in a wide range of electronic activities.


**under
£5**




Transistor/diode checker
£3.90



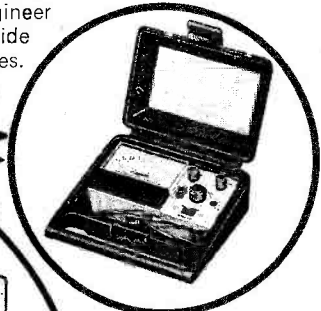R and C substitution boxes
£4.80 and £3.90




Portable transistor tester
£13.80

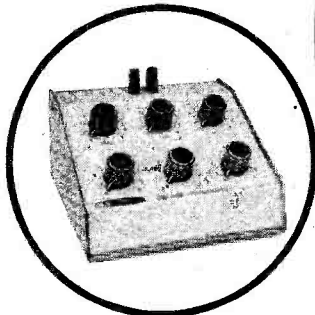


Decade resistance box
£14.80



R.F. probe
£3.50

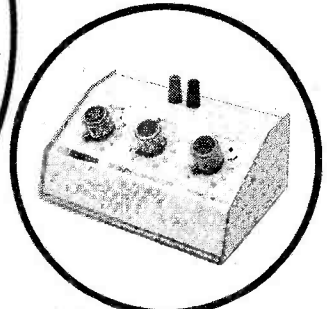


Decade capacitance box
£9.80

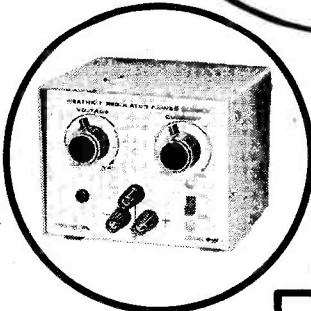

Power supply
£9.80

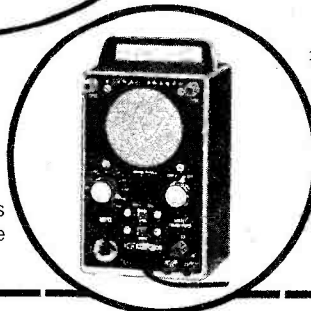
No deposit terms up to
£30
Budget plans also available



Signals tracer
£13.80

Kit prices quoted

free catalogue

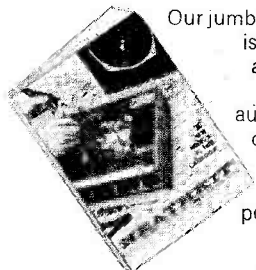

Our jumbo sized Heathkit catalogue is full of good things. Stereo amplifiers, tuner amplifiers, tuners, loudspeakers and audio accessories, electronic calculator, metal detectors, shortwave receivers, intercoms... even a powerful battery charger kit.

Please send me a FREE Heathkit catalogue

Name _____


Address _____

Heath (Gloucester) Limited, Department PW/2/73
Gloucester GL2 6EE. Telephone 0452 29451

HEATH
Schlumberger

(Mail order prices and specifications subject to change without notice)

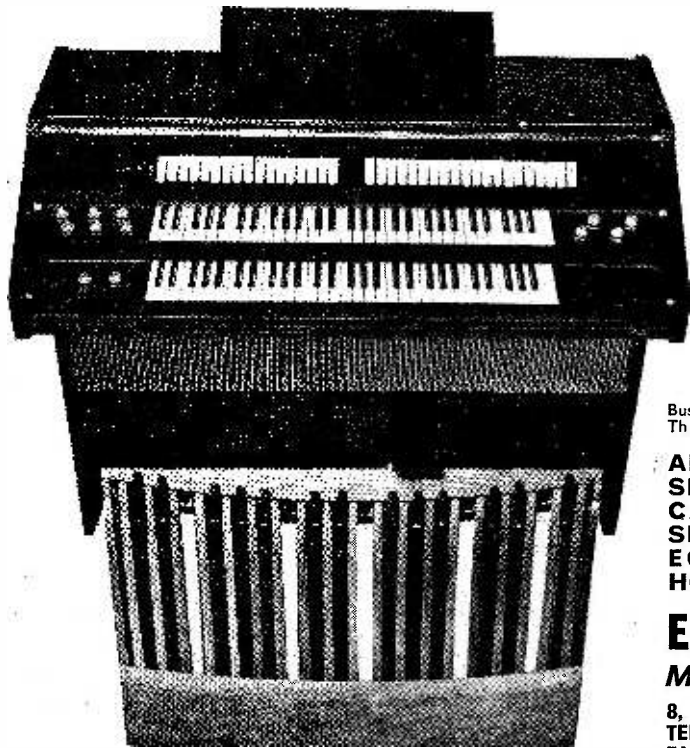Heath (Gloucester) Limited, Gloucester GL2 6EE.



ORGAN KITS

Build your own Electronic Organ, if you want the best value for your money. Yes you really save over 50% and get the best and up-to-date designs. There are four models to choose from.

- ★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, at £145.29.
- ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato built in amplifier and 50 watt 12" Goodmans speaker at £199.75.
- ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Percussion, Wah Wah, etc. at £406.00.
- ★ Console—2 x 5 octave keyboards and 32 note pedal boards, 32 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Percussion, 3 Couplers, etc., at £553.60.

Business hours: 10 a.m. to 7 p.m. Monday to Saturday, Thursday closed.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT AND ELECTRICAL HOUSEHOLD APPLIANCES.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE ROAD, LONDON, S.W.18
TEL: 01-870 4949
EAST LONDON BRANCH OPENING SOON.

BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON S.W.17 01-672 3984
(Nr. Tooting Broadway Underground Station)
(Closed all Wednesdays)

CARTRIDGES—Stereo Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output, £1.40. S106 High Output £1.40. Acos GP93/1 Sapphire, £1.90. GP94 1 Sapphire, £2. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7p on each.

CARTRIDGES—Mono GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95p. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7p.

HI-FI STEREO HEADPHONES

Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms. Frequency range 30-15,000 Hz 6ft. cord and standard stereo plug
Only £2.57½. P. & P. 27½p.



STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones.
Only £1.50. P. & P. 13p.

VYNAIR

Widths from 50 to 54in., 75p yd. off roll. P. & P. 10p, ½ yard 40p. P. & P. 10p. Send 5p stamps for samples.

£3.15

BOOST THE SOUND

of TAPE RECORDERS, RECORD PLAYERS
P. & P. 61p **CAXTON** EXTENSION SPEAKERS

Makes all the difference to volume and quality. Contains 3 speakers in series—ex-TV Output 8 watts. Impedance 9 ohms. Available in black leathercloth. Size 2½" x 5½" x 5½". Keyhole slot for wall mounting. Twin connecting cable 12yds., 35p min.



FAST—RELIABLE SERVICE

FOR

ELECTRONIC COMPONENTS

SEND NOW FOR A **CATALOGUE**

5th Edition

AND DISCOUNT VOUCHERS

25p POST FREE (UK)

W.E.C. LTD. HIGH STREET, RIPLEY, SURREY

Established 1954

P.W. STEREO Hi-Fi AMPLIFIER

By W. Cameron

(was built entirely from parts supplied by us)

Unit Kits of parts (Stereo)	
Pre-amp kit (inc. all controls)	£5.85
Driver amp. kit	£2.36
Power amp. kit (inc. special driver transformers)	£6.62
Power supply kit	£5.54
COMPLETE PARTS KIT (all of above)	£19.60

Also available as extras:

Metalwork; chassis and heatsink, bent but undrilled	£1.50
Special front panel trim, black and grey	30p
Set of sockets for phono inputs and L/Spkrs.	60p
Set of knobs (5) black and chrome	50p

Post. Individual kits 20p. Complete kit 35p.

**C & D ELECTRONICS, 1 NEVILLE ROAD,
ST. LUKES CROSS, SUNDERLAND SR4 6QT.**

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

CHRISTMAS is over and here we are in another New Year. I know that many of my readers will have asked for presents of money so that they can save towards the new receiver that they want and many will write to me asking advice on the best set to buy.

Unless a second-hand purchase is anticipated the reasonably serious listener will have to pay around £50 for a good receiver. There are of course many sets on the market for much less and several which cost a lot more.

In this middle price range there are two receivers which stand out as being very good value for money and for this reason they are very popular with DXer's. The first is the Lafayette HA600 which is a general coverage receiver (550kHz to 30MHz) this set has the advantage of being all solid-state which means that it can be run from either the mains or from 12 volts d.c. The second is the Trio 9R59DS which is again general coverage but can only be operated from 240 volt mains.

Before anyone asks, my personal preference is for the Lafayette. There are two reasons for this, the first is that I have always owned Lafayettes and had no trouble with them at all. The second is that when I worked in an Electronics Laboratory, designing circuits, I only used transistors and integrated circuits, never valves. Consequently I feel more at home with a solid state receiver and if anything goes wrong I will be more able to repair it myself.

A great number of readers will, of course, not be lucky enough to afford one of these sets but they can increase their enjoyment of the hobby in many ways.

The 1973 edition of the World Radio TV Handbook has just been published and although it costs about £3 many experienced DXers will tell you that it is an invaluable text that they would never be without. The book lists all the Broadcasting Stations in the world with full details on each, including frequencies used, hours of transmission and the languages used. The book also contains a section on general information and a complete listing, by frequency, of all the stations.

A good New Year Resolution would be to erect a new and better aerial, about which much has been published in the past few months. There is, however, a snag which was pointed out to me by Mr. A. W. Lewington of Bath. I also noticed the difficulty when I moved house recently and wanted to erect a new aerial. The problem is that nobody seems to sell good aerial wire any more. A few years ago Woolworths used to sell aerial wire which consisted of stranded copper wire with thick plastic insulation. This had the two important properties of being strong and flexible to withstand the ravages of our British weather. It is, however, no longer available.

If any reader knows of a good source of aerial wire

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

I would be pleased to hear from him so that I can pass the information on to all our readers.

Yet another way of getting more enjoyment from the hobby is by joining a reputable DX Club. These clubs publish magazines for their members and these are used to exchange news and views about all aspects of the hobby. The membership fee is usually about £1.50 and the magazines alone make this outlay very well spent. The club that I would recommend is the World DX Club and the Secretary is Clive Jenkins, 11 Wesley Grove, Portsmouth, PO3 5ER.

In a recent article I published a specimen Reception Report. Mr. A. J. Wills of Elgin wrote to me to point out that the space devoted to programme details was not long enough. This was due to an error on my part when typing out the article. The most important part of the report is the section on programme details. All the other details on the report can be obtained from such sources as the World Radio TV Handbook.

The programme details are the only way in which the station can be sure that it was in fact their transmissions that were heard. The more complete the details are the greater is the likelihood of the station confirming the report with a QSL card.

All this chat has left me with very little space for your reports so I will start straight away with one from James Pruden of Sturminster Newton in Devon. James has a Skywood CX-203 receiver with a 15 metre end-fed aerial, this combination enabling him to hear:

- 6010 RTB, Belgium in French at 1510.
- 9545 Radio Ghana in English at 2120.
- 9610 Radio Kiev, USSR, in English at 1930.
- 11650 Radio Bangladesh in English at 1715.
- 15015 Voice of Vietnam in English at 2015.
- 15165 Radio Denmark, ID in English at 1330.
- 15170 ELWA, Liberia in Arabic at 2230.
- 15345 Radio Norway in English at 1615.
- 21570 Radio Japan, news in English at 0800.

Craig Tyson of Wembley in Western Australia used his Lafayette HA600 receiver and inverted 'L' aerial to hear the following stations:

- 6090 Phnom Penh in English at 1230.
- 7215 AFN, Taiwan in English at 1300.
- 7470 R Liberation, N. Vietnam, English at 1030.
- 9510 Lakeland Radio, Malawi, English at 1945.
- 9520 VLT9, New Guinea in English at 0730.
- 9580 Voice of the Philippines, English at 1300.
- 15170 Radio Tahiti in French at 0700.
- 15185 Voice of Nigeria in English at 0700.

Reports should arrive by the 15th of the month and be addressed to me at 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

SHORT WAVES

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz ● Times in GMT

HAPPY New Year. Now, how about a resolution to devote at least 30 per cent of your listening time to bands which you normally ignore? If you are an h.f. type, you could do no better than start off with top band transatlantics. These are tests carried out at certain times and on certain dates. The first ones in 1973 are as follows. January 14 and February 11 from 0500 to 0730 hours.

For something a little more difficult, how about the transpacific tests? These are to be held on January 13 and February 10 from 1330 to 1600 hours. The U.S. and Canadian stations will be transmitting between 1800 and 1807kHz. The D.X. stations will use 1825 to 1830kHz or 1800 to 1805kHz. It should be noted that stations in other countries are often restricted in choice of frequencies. For example, Japanese Amateurs may only use 1907 to 1912.5kHz while stations in New Zealand are restricted to 1875kHz. Doubtless we will get some Lid calling an endless CQ on these frequencies. How wonderful it would be for me to be proved wrong on this. How about it, Lids?

John Spacey (Devon) tells of A51PN putting in an appearance on 14MHz. He also mentions that Swan Island is active (listen for W6MTE/HR6) as is VU25FBZ on Andaman Island, both on 14MHz.

Two useful New Year presents you can treat yourself to. One is the latest countries list from the RSGB. Second is a good world atlas. For example, do you know where Swan Island or Andaman Island (mentioned above) are?

Which bands to listen on and at what time is really a matter of personal choice. However, the following remarks are based on readers' reports and personal observations by your scribe's ears.

The h.f. bands (14, 21 and 28MHz) become somewhat erratic during the winter months. By contrast, the three lower frequency bands (1.8, 3.5 and 7MHz) all improve compared to their summertime performance. Fifteen and twenty metres start to close down quite early now. Often, by 2000 hours there are no signals at all and this state of affairs remains until around 0600 hours.

On ten metres it is often a matter of luck. This band now opens at about 0800 hours and closes again at around 1700 hours. However, 28MHz is really a sort of lucky dip. If there is a high sunspot activity the band will suddenly burst into life.

Most of the winter D.X. activity migrates to 7MHz and this is particularly evident when the h.f. bands (14MHz and upwards) close down for the night. In theory, the sunspot activity should continue to decline in the coming months. This activity follows an 11-year cycle and we are currently on the way down towards a trough.

R. Kell (Northumberland) sends in a five-band log which includes earfuls of activity on 3.5 and 7MHz. Guilty parties aiding and abetting include a "modified" R109 with an a.t.u. and 150ft. end fed antenna. Goodies on 3.5MHz include; CN8HD,

XV5AC, ZM4PG, 9H5D. Plundering forty metres brought the following r.f. jewels; CO3GS, CN8HD, HR1RF, KZ5PW, OA4SO, PY2ELX, PY2FKZ, TF1TP, VR2DE, XE111J, YV4AGP.

John Hulse signing himself "Yours faithfully" and residing in Cheshire, tells of a sparkling new FR50B receiver. Duper squeaks on 28MHz from; CR6CN, CR7IC, CX2CF, ET3JH, KZ5PW, LU5DEK, LU5DTV, OY9LV, PY1AGC, ST2SA, VK6CF, VP7ND, VP9BO, XW8CN, YV4EBH, ZP5AQ, ZS6OS, 3B8CV, 3B8CZ. Down on 21MHz, the following menu was provided; CP1FU, CT2BG, EL4B, EP2TC, ET3DS, FP8DH, HI3XSJ, HK3CCO, HK3CLX, OD5FU, PZ1CU, VP1BH, VU25DK, XV5AC, YA1OS, YV5AK, ZD3X, ZE7JC. All stations using s.s.b. and the receiving aerial is described as a 66ft. dipole at 10m height.

Stefan Kaye (Oxon) made a brave attempt to break the habit. But the soulful look in the silent eyes of his AR88D got to him. Result of this joyous reunion was; CE3PY, CT2AC, LU3DTV, LU9DTQ, VQ9MC, ZS1WS—all on s.s.b. on ten metres. Down on eighty, a listen was rewarded by: FW8IA, HB0AIC, K3UQU/W1, ON0NJ, TZ2AC, VE1ADV, VE1IE, VE3PT.

R. Iball (Notts.) uses a diamond aerial! Well, it's shaped like a diamond, is 7ft. long and hidden in the loft. The receiver is a JR500SE (not hidden in the loft) and the 14MHz c.w. signals were received by courtesy of: HS4AGN, UA0DV, VE7ZR, VE3ZT, ZL1ARV, ZL1MQ, ZL3GQ, ZM1AFW, ZM3ABC. Donald Duck mode of signals on the same band from: FP8DH, PZ1DR, VE6PP, VP8RA, VK1BF, VK6PG, VK6VW, VP9GA, VP9GE, VS9MB, ZL1AH, ZM4KM.

Trevor Thomsen (Bulawayo, Rhodesia) sends letters with pretty stamps and includes logs heard on his Hallicrafters S53A and 40ft. end fed. The list for s.s.b. on 21MHz reads: EL2CB, GR3NM, K3TGM, K4MQG, WA3GJZ, WB8JEY, W1AWE, W4SKO, W5RO, W8COG, 6W8AL, 6W8EM. Bernard Hughes (Worcester), JR310, 66ft. long wire, 28MHz s.s.b.

Logs, in alphabetical order please, to arrive by the 15th of the month to 12 Cross Way, Harpenden, Herts.



AMATEUR BANDS RECEIVER DECEMBER 1972
Part 1. Fig. 2C, potentiometer (500 ohms) associated with S-meter should be marked VR2. Fig. 2D, power supply diodes should be marked D1 and D2. The OA2 voltage stabiliser should be marked V1. Amend Components List:—Fig. 2D, V1 OA2, V2 ECL86.

I.C. LINEAR CAPACITANCE METER JANUARY 1973
D3 should be a C5V6 5.6V (not 3.3V). This applies to both the circuit and the components list.

SUPERSOUND 13 HI-FI MONO AMPLIFIER




A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 18 watts

r.m.s. into 8 ohm. Frequency response 12Hz-30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V.

PRICE £10.50. P. & P. 25p.

DE LUXE STEREO AMPLIFIER

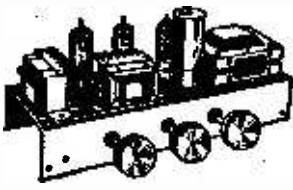

A.C. mains 200-240 V. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Valve line up:- 2 x ECL86 Triode Pentodes, 1 x E250 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Simple control with knobs, chassis size 11" w x 4 1/4". Overall height including valves 5". Ready built & tested to a high standard. PRICE £8.92 P. & P. 45p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7.5v, and 9v, and 12v, at 1 amp continuous (1amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radio, Tape Recorders, Amplifiers etc. Ready PRICE £4.50 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T.O.S. complete with nuts and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.

COILED SPRING BACK TELEPHONE CABLE. Closed approx. 10" extends to 36". 4 core or 6 core. 25p each P. & P. 5p. 5 or more post free. LIMITED NUMBER!

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. Half wave at 1 amp, or 10-10-10, 20-20-30, 30-30-40v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £1.85 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri 200/240v. Sec. 9-0-9 at 500mA. 85p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.45. P. & P. 30p.

SPECIAL OFFER MAINS TRANSFORMER 200/240V. A.C. Input 35v at 1 1/2 amp A.C. output overall size 2 1/2" x 2 1/2" x 3" approx. Suitable drop through or vertical mounting 90p. P. & P. 30p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100µA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 88p. P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 3p.

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £8-97 Carr. 50p. With stereo cartridge £7-97 Carr. 50p.

SPECIAL BARGAIN OFFER!

PRECISION ENGINEERED PLINTHS Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL56B, AT60 etc. or P.S.R. C109, C129, A21 etc. Black lacquer finish. Size 12 1/2" x 14 1/2" x 3 1/2" high approx. 7 1/2" high, including rigid smoked acrylic cover). NOW ONLY £4.50, P. & P. 35p.

LATEST ACOS GP91/1SC mono compatible cartridge with £10 stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

SONOTONE STARC COMPATIBLE STEREO CARTRIDGE 7/10 stylus Diamond Stereo LP and Sapphire 78. B.S.R. or ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for LP/LP/78. £1-63 P. & P. 10p. **LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. ONLY £1-50 P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 5in. deep x 6in. high. Ready built and tested. PRICE £8-95 P. & P. 40p. **ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £5-25 P. & P. 50p.

DELUXE QUALITY PORTABLE R/P CABINET MK II. Uncut motor board size 14 1/2 x 12in. clearance 2in. below, 3 1/2in. above. Will take above amplifier and any B.S.R. or GARBARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 5in. PRICE £4-75, P. & P. 50p.

SPECIAL OFFER! HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £8.40 Carr. 65p
Cabinet Available Separately £4-50 Carr 60p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter 260 Carr. 65p

LOUSPEAKER BARGAINS

5in. 3 ohm £1-05, P. & P. 15p. 7 x 4in. 3 ohm £1-15, P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-60, P. & P. 20p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1-62, P. & P. 20p. E.M.I. 13 1/2 x 5in. with high flux ceramic magnet 3, 8 or 15 ohm £2-20, P. & P. 30p. E.M.I. 13 x 5in. 3, 8 or 15 ohm with two twin built tweeters and crossover network £4-20, P. & P. 30p. E.M.I. 13 x 5in. twin cone (parasitic tweeter) 8 ohm £2-25, P. & P. 30p.

BRAND NEW 15in. 15w. H/D Speakers, 3 or 15 ohms. Current production in British maker. Now with HiLux ceramic ferrobar magnet assembly £6-75. Spring models: 25w. £6-75, 35w. £8-50. P. & P. 38p.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £2-75, P. & P. 25p.

12in. "RA" TWIN CONE LOUSPEAKER. 10 watts peak handling, 3, 8 or 15 ohm £2-20, P. & P. 30p. 35 ohm SPEAKERS 3in. only 68p P. & P. 13p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER. Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 15W r.m.s. (15 peak). Impedance 8 ohm only. Frequency response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5-95 each. P. & P. 25p.

VYNAIR & REKINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1-75 yd., our price 75p yd. length. P. & P. 15p per yd. (min 1 yd.) S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £2-95, P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1-05, P. & P. 8p

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knob, wire solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response ±3db 12-30,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth: ±2db 12-15,000 Hz. Bass boost approx. to ±12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 55v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 13p plus large S.A.E.

AMPLIFIER KIT £10-50 P. & P. 15p
(Magnetic input components 30p extra)
POWER PACK KIT £3-00 P. & P. 30p
CABINET £5-00 P. & P. 50p

(Post Free if all units purchased at same time) Full after sales service. Also available ready built and tested £21-00. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi Fi Discophile use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, E250 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4-95. P. & P. 35p.

HSI "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4-10. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 8.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. £2.95 P. & P. 35p BARGAIN PRICE

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouted section wound output transformer to match 2-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP86 and E250 rectifier. Simple instruction booklet, 13p (Free with parts). All parts sold separately. ONLY £7-97 P. & P. 35p. Also available ready built and tested £10-97 P. & P. 60p.

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbeldon Tube Station.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

VALVES

VALVES		25		30		40		50		60		70		80		90		100				
6BA6	25	6J6	20	7C5	11-13	12SR7	40	37	40	DAF91	30	EBL31	11-50	EL34	50	N78	11-60	PL500	80	U403	60	
6BE6	30	6J7M	45	7C6	75	14H7	50	42	50	DAF95	45	EC90	35	EL41	60	N108	11-50	PL604	80	U404	60	
6BH6	50	6J7GT	45	7D5	60	19AQ5	50	50B5	50	DCC90	11-35	ECC81	35	EL42	65	OC2	35	PL508	90	U401	11-18	
6BJ6	50	6J7GT	45	7E5	50	20D1	50	50C5	50	DF33	55	ECC82	30	EL84	25	OC3	35	PL509	11-10	U403C90	40	
6BQ7A	45	6K8GT	60	7R7	75	20P2	70	50CD6G	11-20	DP70	45	ECC83	30	EL95	35	OC4	40	PL802	95	U4AF2	55	
6BR7	50	6K7M	35	7S7	35	20L1	11-10	50L6GT	55	DP91	30	ECC84	30	ELL80	11-00	OC5	40	PL803	95	U4AF4	55	
6BR8	50	6K7M	35	7Y4	65	20F4	11-10	75	50	DF92	20	ECC85	40	EM80	45	OC6	40	PL804	95	U4AF6	55	
6BS7	11-30	6K7GT	35	9WB6	60	20P5	11-20	75	45	DF96	45	ECC86	40	EM81	45	OC7	40	PL805	95	U4AF8	55	
6BW6	65	6K8M	60	10C2	60	25A6	35	80	50	DH3-91	27-00	ECC87	40	EM82	45	OC8	40	PL806	95	U4AF10	55	
6BW7	30	6K8G	40	10F1	75	25L6GT	50	85A2	40	DH77	35	ECH35	11-00	EY51	40	OC9	40	PL807	95	U4AF12	55	
6C4	30	6C4	33	6K8GT	50	10F3	90	25V5	65	150B2	60	DK32	45	ECH42	75	OC10	40	PL808	95	U4AF14	55	
6C5G	35	6K25	75	10F9	60	25Z4	30	150C4	60	DK91	40	ECH81	30	EZ35	40	OC11	40	PL809	95	U4AF16	55	
6L6G	25	6L6G	50	10P18	50	25Z5GT	55	801	60	DK92	55	ECH83	45	EZ41	50	OC12	40	PL810	95	U4AF18	55	
6C6DG	11-25	6L18	45	10LD11	85	25Z6	65	7475	50	DK96	45	ECH84	45	EZ42	50	OC13	40	PL811	95	U4AF20	55	
6C6H	60	6Q7G	40	10P13	60	30C1	30	81USA3	25-75	D166	11-25	ECL82	30	EZ43	50	OC14	40	PL812	95	U4AF22	55	
6C6W4	35	6Q7GT	43	11E3	24-00	30C15	80	866A	75	D192	35	ECL83	70	EZ44	50	OC15	40	PL813	95	U4AF24	55	
6D6	48	6D6	35	6BA7M	40	12AT6	70	90	96A	60	DL93	40	ECL86	40	GY501	30	OC16	40	PL814	95	U4AF26	55
6E5	11-00	6E87M	75	12AT7	35	30C18	80	1625	55	DL94	48	ECL800	60	GZ60	30	OC17	40	PL815	95	U4AF28	55	
6E87M	35	6E87M	40	12AU6	35	30F5	85	4022AR	25-50	DL95	50	G232	11-05	GZ32	48	OC18	40	PL816	95	U4AF30	55	
6E87M	45	6E87M	40	12AU7	30	30FL1	75	5783	70	DL96	45	EF9	75	GZ34	48	OC19	40	PL817	95	U4AF32	55	
6E87M	35	6E87M	35	12AX7	30	30FL12	11-20	7193	30	DM70	45	EF37A	11-20	HN309	11-50	OC20	40	PL818	95	U4AF34	55	
6E87M	40	6E87M	40	12BA6	40	30FL14	40	30L15	85	AT4	45	EF82	11-25	KT81	21-05	OC21	40	PL819	95	U4AF36	55	
6E87M	40	6E87M	40	12BE6	40	30L15	85	AT5	45	AT5	45	EF83	11-25	KT81	21-05	OC22	40	PL820	95	U4AF38	55	
6E87M	40	6E87M	40	12C8GT	35	30L17	80	ATP4	45	EF84	35	EF85	11-25	KT81	21-05	OC23	40	PL821	95	U4AF40	55	
6E87M	40	6E87M	40	12E1	23-00	30P4	40	ATP5	60	EA50	20	EF86	11-25	KT81	21-05	OC24	40	PL822	95	U4AF42	55	
6E87M	40	6E87M	40	12F5GT	30	30P12	30	ATP7	60	EAB30	35	EF87	11-25	KT81	21-05	OC25	40	PL823	95	U4AF44	55	
6E87M	40	6E87M	40	12G7GT	30	30P19	35	AT8	45	EAF42	20	EF88	11-25	KT81	21-05	OC26	40	PL824	95	U4AF46	55	
6E87M	40	6E87M	40	12H7GT	40	30P11	75	AU5	75	EA50	20	EF89	11-25	KT81	21-05	OC27	40	PL825	95	U4AF48	55	
6E87M	40	6E87M	40	12BA6	40	30P13	93	AZ1	55	EBC31	50	EF89	11-25	KT81	21-05	OC28	40	PL826	95	U4AF50	55	
6E87M	40	6E87M	40	12BE6	40	30P14	90	AZ31	55	EBC41	55	EF91	11-25	KT81	21-05	OC29	40	PL827	95	U4AF52	55	
6E87M	40	6E87M	40	12G7GT	40	30P15	90	CB131	11-00	EBC90	35	EF92	11-25	KT81	21-05	OC30	40	PL828	95	U4AF54	55	
6E87M	40	6E87M	40	12A7GT	50	35A5	75	CB131	11-00	EF80	35	EF98	11-25	KT81	21-05	OC31	40	PL829	95	U4AF56	55	
6E87M	40	6E87M	40	12S7GT	35	35I6	60	OC35	75	EF80	40	EF98	11-25	KT81	21-05	OC32	40	PL830	95	U4AF58	55	
6E87M	40	6E87M	40	12H7	35	35Y4	35	CL33	11-30	EF83	40	EF98	11-25	KT81	21-05	OC33	40	PL831	95	U4AF60	55	
6E87M	40	6E87M	40	12S7	35	35Z3	70	CBF89	30	EF89	30	EF98	11-25	KT81	21-05	OC34	40	PL832	95	U4AF62	55	
6E87M	40	6E87M	40	12Z4GT	40	35Z4GT	40	CY31	40	EBL1	11-00	EF92	11-25	KT81	21-05	OC35	40	PL833	95	U4AF64	55	
6E87M	40	6E87M	40	12S7	50	35Z5	50	DAC32	50	EBL2	60	EL33	11-75	MX40	63	OC36	40	PL834	95	U4AF66	55	

Transistors

AC128	20	BY100	15	NKT713	25	OC44	12
AC320	20	BZ398	15	OA70	10	OC45	17
AD149	15	CA739	47	OA71	10	OC67	60
AD149	15	DD003	15	OA81	08	OC68	60
AD161	37	GE102	30	OA85	12	OC69	65
AF115	45	GJ782	25	OA91	07	OC71	12
AF115	45	GJ7M	37	OA211	30	OC72	20
AF117	25	K8100A	30	OA2201	50	OC81	20
AF117	25	K8100B	30	OA2207	47	OC81D	20
BC107	10	MJ2295	87	OA2210	35	OC82	25
BC108	10	OA2222	45	OC82D	20	OC90	20
BC109	10	MJ3055	87	OA2224	45	OC84	25
BC169C	30	NK7212	27	OA2241	25	OC170	25
BF98	28	NK7214	15	OA2242	22	OC171	30
BF99	22	NK7223	38	OA2246	25	OC200	40
BF751	20	NK7251	24	OC55	50	OCF71	97

Integrated Circuits

7430	20	7474	40	74100	22-50	74157	11-90
7432	42	7475	55	74107	50	74170	24-10
7433	70	7476	45	74110	80	74174	22-00
7437	65	7480	30	74111	11-45	74175	11-35
7438	65	7482	37	74113	11-00	74176	11-60
7440	12	7441	23	74119	11-90	74190	11-95
7401	20	7412	22	7440	11-00	74121	60
7402	20	7413	30	7442	75	74122	11-35
7403	20	7416	30	7445	75	74123	22-70
7404	25	7417	30	7447	75	74129	22-00
7405	20	7420	20	7449	28	74131	22-50
7406	20	7422	48	7451	20	74132	21-85
7407	30	7423	48	7452	20	74133	21-85
7408	20	7425	48	7460	20	74134	21-85
7409	45	7427	42	7472	30	74135	21-85
7410	20	7428	50	7473	40	74136	21-85

RST VALVE MAIL ORDER CO. 16a WELLFIELD ROAD, LONDON SW16 2BS

Special Express Mail Order Service TELEX 946708 Send large S.A.E. for list. Phone 677 2424 (4 lines)

Express postage 1p per transistor, over 10 post free. Integrated Circuits & Valves 5p, plus 1p for each additional item, over £5-00 post free

IMPORTANT
IF YOU WANT A RADIO THAT PICKS UP VIRTUALLY EVERYTHING THAT'S BROADCAST - AND WE MEAN EVERYTHING - THIS IS IT!

BATTERY OR MAINS WORLDMASTER

A COMPLETE VHF RADIO COMMUNICATIONS RECEIVER



Forget about Everything else you've seen, this is it! - the most amazing portable VHF Radio and communications receiver

we've yet offered. **BRAND NEW** - manufactured and guaranteed by one of the most reputable companies in advanced radio and electronic communications equipment. You won't match this for value and variety of performance anywhere - we sell similar sets at three times this price! **AND YOU RISK NOTHING** because you can return with in 10 days if not 100% satisfied. We can't list everything that this remarkable receiver picks up. **BUT** we can say that the 8 wavebands cover just about everything that's broadcast - by anyone - from anywhere in the world. You name it - it gets it! Exciting specialised transmissions as well as BBC, Local Radio, Luxembourg, Continental and Pop Stations. **PLUS** broadcasts from all corners of the world on the earth shrinking **SHORT WAVEBANDS**. Attractively finished in leatherette and stainless steel to enhance any lounge or study. **USE ANYWHERE** - costs virtually nothing to run using standard batteries or plugs into mains. **Tone, volume and tuning controls** enables adjustment to individual listening perfection. 2 aerials, advanced keyboard type push button waveband selector. **Dial light** (essential for use in darkness). **Special world-wide dial and world map** computes correct time in any country of the world. Personal hi-f earphone for private listening. 14 transistors, 9 diodes, 1 thermistor. **FREQUENCIES:** Long: 150-350 kcs.; Medium: 585-1605 kcs.; 3 **SHORT BANDS:** 1.6-4.5 mcs; 4-12mcs; 12-24mcs.; 3 **VHF BANDS:** 68-108mcs.; 108-185mcs.; 135-174mcs 227.50 + 50p p. & p. or 27-50 dep. + 50p p. & p. and 6 months at 24 (£31-50).

Send 5p stamp for Comprehensive Brochure of Unusual Frequency Radios.




Multicore

for fast, easy reliable soldering


Each Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning away oxide surfaces. No pre-flux is required.

IDEAL FOR HOME CONSTRUCTORS




Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges.

EASY-TO-USE DISPENSERS



Size 5 (Savbit) 18swg, 18p (illustrated)
Size 19A (60/40 alloy) 18swg, 18p
Size 15 (60/40 alloy) 22swg, 22p

BIB WIRE STRIPPER AND CUTTER



Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings. 4 & 6BA spanner ends, ground cutting edges Price 32p. Also available, de luxe Model 8. Price 58p.

NEW!


From Electrical and Hardware Shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**

SCIENTIFIC & TECHNICAL (PW2)


TOWERFIELD TRADING ESTATE, SOUTHEND, ESSEX (Mail Orders)

Principal Showrooms: 507-511 LONDON ROAD, WESTCLIFF, ESSEX.

GOING BACK...

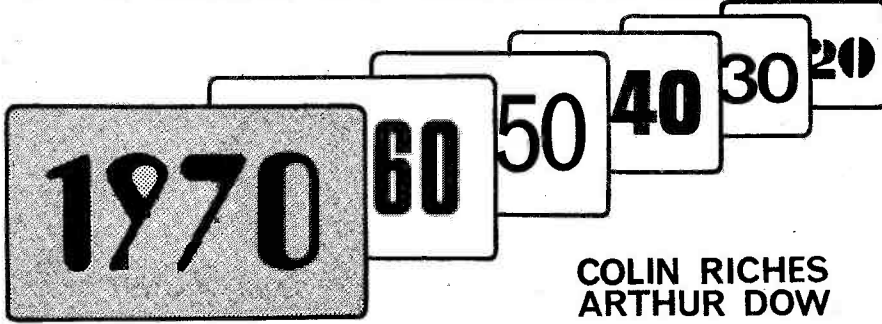

COLIN RICHES
ARTHUR DOW

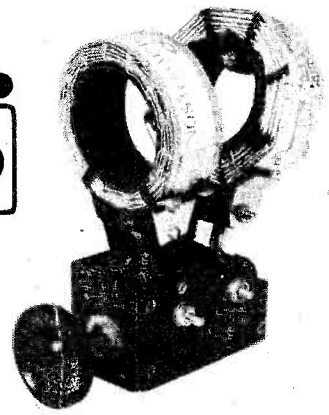

MULLARD Limited, as their 50th Anniversary tribute to the BBC, staged a two month exhibition at Mullard House in London. It was opened on November 2 by Lord Hill, chairman of the BBC.

The Post Office gave its full support and co-operation to the exhibition which was complementary to the one organised by the BBC and held at the Langham Hotel, near Broadcasting House.

The Mullard exhibition was designed with a four-fold aim in mind—to show how technical innovation has contributed to the growth of broadcasting, to stress the pioneering effort that went into it, to enable the public to gain more of an insight into the technical aspects of broadcasting and to illustrate how development and research are continuing for the future.

The first part of the exhibition was entirely devoted to the development of broadcasting. It included a replica of the original Savoy Studio 1 of the early 1920s and a pictorial story showing how the microphone was evolved.

Two famous microphones exhibited were those used by Dame Nelly Melba and Sir Winston Churchill.

Visitors were also able to speak into one of the early "meat-safe" microphones and hear their voices



Her Majesty the Queen compares vintage and modern tape recorders.

reproduced on a tape machine. Also on display, was an early cylinder gramophone and one could, at the touch of a button, hear the kind of reproduction that could be obtained from such a machine.

An early pianola was shown and it was difficult to realise that in the earlier days of broadcasting, the announcers actually had to pedal units like these as continuity between programmes!

On the same stand there was a recording machine of the type used by BBC War Correspondents and in one of the photographs shown in this article Her Majesty the Queen can be seen comparing this with a modern cassette tape recorder.

The section of the exhibition devoted to the story of television began with the actual first Emitron TV camera. Photos showed the various outstanding developments of television and the display was climaxed by a reconstruction of a live TV studio.

There was an audio/visual link with the BBC exhibition at the Langham, and Mullard House visitors were able to see themselves on colour TV, and to read the news on closed circuit TV. From our picture it looked as though the BBC had taken on a new cameraman to demonstrate the colour camera—his face looked very familiar though!

Mullard themselves had a display showing the part their components had played over the five decades of sound and TV broadcasting.


They also had a "Colour TV Look-in", a six minute



The lip microphone: designed by the BBC Research Department to cut out background noise. It was first introduced in 1937.



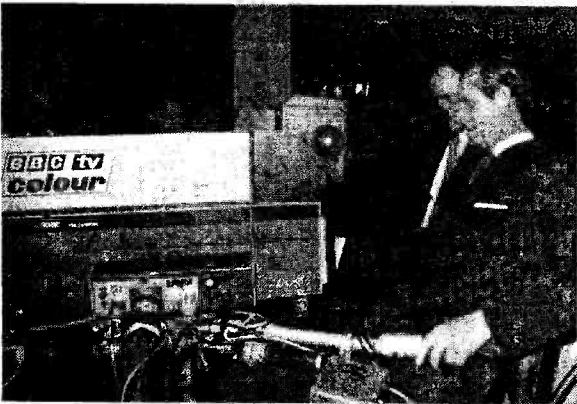The Queen shows interest in a horn loudspeaker and the "meat safe" microphone.



Prince Philip "has a go" at being a BBC cameraman.



The "Twenties" room setting at the Langham Hotel exhibition.



This picture shows the central display feature at the Langham exhibition. It reflects the development of the BBC over the years.

presentation telling the story of the Company's contribution to colour TV development.

Exhibits were also devoted to colour TV techniques and demonstrations in which the public could take part. Visitors could experiment with a BBC Radio-phonics unit and see a demonstration of 3D television together with exhibits showing what the future may hold for transmission techniques.

The BBC held their own exhibition at the Langham Hotel, formerly one of London's most luxurious hotels and now offices and studios of the BBC.

Facing visitors, in the main area of the exhibition, was a multifaceted panoramic screen consisting of 20 separate screens. Forty-two slide projectors, with a total of 3,500 slides projected onto this screen. Scenes shown were chosen from a quarter of a million original BBC pictures and gave an extremely good visual impression of broadcasting in the past, present and future. These projectors, incidentally, were controlled by a simple computer which maintain the correct picture sequences.

Underneath this screen, which stood about 9ft. above ground level, there were mock-ups of room settings of different periods of broadcasting history.

Of particular interest to "Going Back" fans was a typical room of the '20s. The man is (see photograph) depicted hearing the first BBC broadcast on his home-made receiver on November 14, 1922.

In front of the stand was a row of buttons and excerpts from 1920s' type programmes could be heard by pressing any button. Famous voices heard included Flotsam and Jetsam, Tommy Handley and Jack Hylton.


Other room settings were shown depicting the broadcasting years rolling on. A large planographical map of the British Isles provided the basis of another exhibit and showed the growth of programme coverage from 1922 onwards, achieved by many miniature "transmitter" masts that lit up. Behind this stood a 20ft. high display reflecting the growth of the BBC's services at home and abroad.

Pictures kindly supplied by Mullard Ltd. and the BBC



"Where can I get exclusive units at lowest prices?..."

ROC ELECTRONICS!

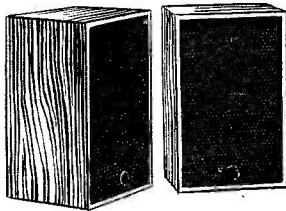

R 088 MATCHED STEREO LOUD SPEAKERS. Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut. **ROC PRICE £9.50 pair.** Normal Price £10.75

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls - magnetic phono (high/low) tuner, aux, mono, master. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz ± 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono - 50db; tuner/aux - 65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.



As reviewed in "POPULAR HI-FI" February 1972

ROC PRICE £35.20
Normal Price £55.50



OLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as its good looking design! But of course it's also the RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz; AM: 525-1605 kHz. FM Sensitivities: FM, 3µV; AM, 250µV. Stereo separation 30db at 1kHz, image rejection 60db. Size: 11 1/2" wide, 4" high, 7 1/2" deep.

ROC PRICE £31.20
Normal Price £50.00



REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide x 3" high x 5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/ tuner and power on/off side switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz ± 3db. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.


ROC PRICE £12.45
Normal Price £21.00



TEC HR-007 HEADPHONE RADIO

When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW. **Normal Price £7.50 ROC PRICE £5.80**

ROC PRICE £5.80

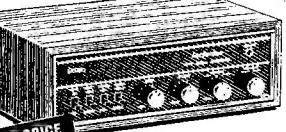

OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3db. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3.0mV RIAA, crystal phono 100mV; tape 160mV; tuner 160mV. Size: 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well - sounds even better!

ROC PRICE £24.10
Normal Price £39.90



A-3000 36-WATT SOLID STATE STEREO AMPLIFIER

The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms; Frequency response 20-35,000 Hz (± 2db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux, Tape Play. Size: 345mm x 300mm x 130mm.

ROC PRICE £28.00
Normal Price £35.70

CONSTRUCTORS KITS

TWO TRANSISTOR RADIO KIT
Complete with solar cell
£2.50

10 PROJECT INTEGRATED CIRCUIT KIT
Build a radio, more key etc.
£3.50

SOLAR ELECTRONIC KIT
20 ways of harnessing the sun's energy
£4.50

TWO OCTAVE ELECTRONIC ORGAN KIT
Make your own music. Complete with speaker.
£4.50



R 446 3-WAY MATCHED SPEAKERS

These will do justice to your amplifier - and to your pocket. At only £20.00 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a 6 1/2" base unit plus tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 8" wide, 8 1/2" deep.

ROC PRICE £20.00
Normal Price £27.00 per pair.



OLSON AM-400 4 WATT STEREO AMPLIFIER


Here's a marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3db. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.

ROC PRICE £10.50
Normal Price £15.70

25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-5b

This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units. An 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.

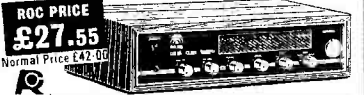ROC PRICE £27.25
Normal Price £39.95 each.



PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16

This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to 'Stereo'! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz. AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3db. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.

ROC PRICE £27.55
Normal Price £42.00

ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317

This exclusive ROC Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 8 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz ± 3db; output 3.5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise ratio better than 45db.

ROC PRICE £5.50
Normal Price £7.75



OLSON AM-372 16-WATT STEREO AMPLIFIER

Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3db. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

ROC PRICE £15.10
Normal Price £25.20

ROC ELECTRONICS LTD

M. JORY Esq, 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211

CALLERS WELCOME 9-6 MON. TO SAT.

ALSO AT 87 TOTTENHAM COURT RD. LONDON W1
TEL: 01-580 3739 OPEN 9-6 MON.-FRI. SAT. 9-1

Return-of-post mail order service from Edgware Rd. Orders over £10 post free (UK only). Add 25p for p. & p. for orders under £10. HP terms available for callers.



USING ZENER DIODES

J. N. WATT

THIS short article aims to bring to readers' attention some lesser known facts of zener diode operation—facts which are so useful when it comes to making the most of a voltage stabiliser or regulator.

Temperature

Almost all zener diodes, like other semiconductor diodes, have a temperature coefficient of voltage; that is, their exact voltage varies as their temperature varies. However, a study of manufacturers' literature shows that this temperature coefficient is by no means the same for all zener diodes and in fact varies with voltage as shown in Fig.1.

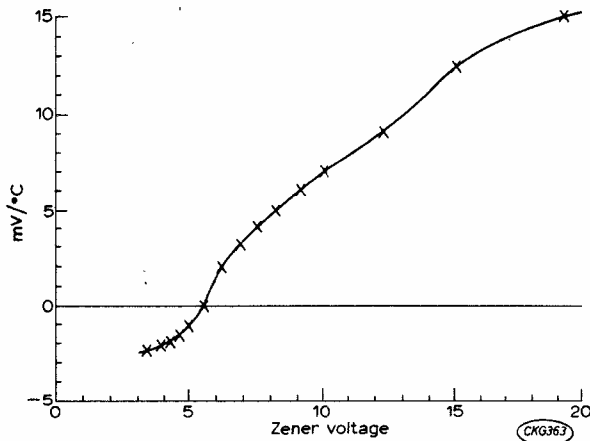


Fig. 1: Graph showing temperature coefficient for different zener voltages.

It can be seen that, at one particular zener voltage, namely 5.6V, this temperature coefficient is actually zero and that the coefficient becomes positive at higher voltages and negative at lower voltages. The values used to plot the graph were extracted from Mullard data but, in point of fact, all makes of zener diodes show this effect, which is presumably connected with the level of doping employed to obtain the various voltage ratings. Of what particular use is this information to the home experimenter?

Environment

Consider the environment in a motor-car. This could very easily range from 25°F to 85°F (-5°C to 30°C) and yet amateurs happily use a zener of any voltage thought appropriate, when, with a little further consideration, a higher performance could easily be obtained. For example, to stabilise a car battery supply at 10V for instrumentation, control or

communication purposes, the use of 6.2V and 3.9V zeners in series will give an almost zero temperature coefficient, so contributing to the accuracy of any measurements and to the frequency stability of receiver local oscillators etc.

A further point of interest is that a forward biased silicon diode has a temperature coefficient of about -2.2mV/°C, so that such a diode used in series with a zener diode of 6.2V, see Fig.2, once again would give a zero temperature coefficient, this time with an output voltage of about 6.9V. Note that the forward biased diode can be the base-emitter junction of a silicon transistor if, for any reason, this is more convenient.

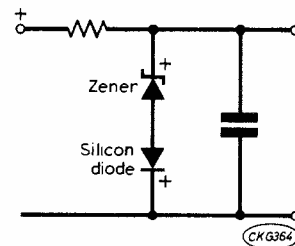


Fig. 2: Circuit illustrating the use of a forward biased diode and a zener diode in series.

So far, we have considered the effect of temperature on the actual voltage of a zener diode, using car applications as an example, but it should be remembered that almost any situation will experience temperature variations and the effect of these on any voltage regulators should not be overlooked. Steps to reduce any such voltage changes can then be taken, as described.

Stability

A further cause of disappointment in the voltage stability of zener diodes arises from the finite value of dynamic slope resistance of the zener. For example, in Fig.3a for a load of up to 20mA and a zener current of 5mA, resistance R is:—

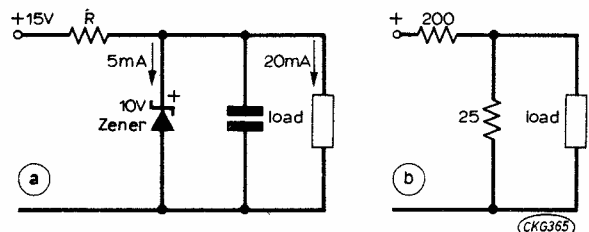


Fig. 3a: A typical zener diode application with Fig. 3b showing the effective dynamic equivalent circuit.

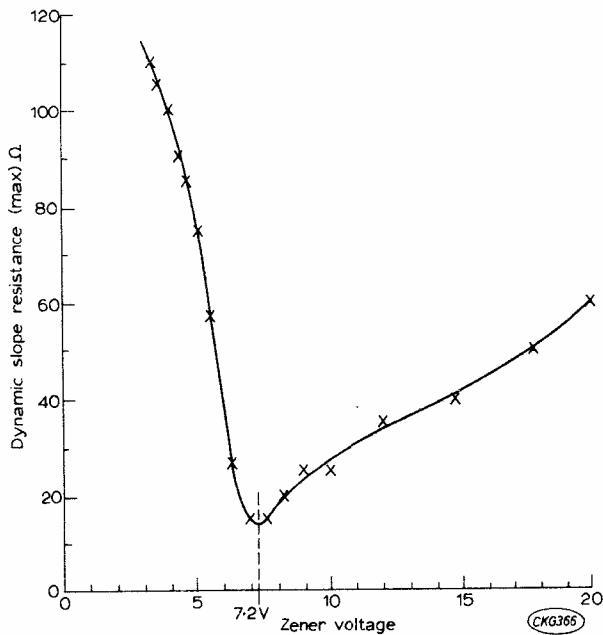


Fig. 4: Dynamic slope resistance of a range of zener diodes.

$$R = \frac{(15-10)10^3}{20+5} = 200\Omega$$

Now, a 10V 400mW zener can have, again according to Mullard data as plotted in Fig.4, a dynamic slope resistance of 25Ω. Thus, the effective dynamic equivalent circuit is as shown in Fig.3b. This leads to the result that, for a change in supply voltage V_i of 1V, the change in output voltage, V_o , will be:—

$$V_o = 1 \times \frac{25}{200+25} = 0.11V$$

which is surprisingly high. A quick measurement confirmed such a value.

Output stability

A dramatic improvement in output voltage stability, as the input voltage varies, can be brought about by the use of a constant current circuit, provided that the load current to be supplied is almost constant. This is usually so where the zener diode is used to supply a reference voltage in a voltage regulator, and in supplies to receiver local oscillators, for example.

At very low zener voltages and, to some extent at the higher voltages also, quite large values of dynamic slope resistance are noted e.g. 85Ω at 4.7V and 60Ω at 20V so the constant current circuit of Fig.5 will greatly assist in providing voltage stability.

In this example, there is a load current of 10mA with 8mA zener current. Now, with a constant potential difference between transistor base and input voltage, due to the use of forward biased silicon diodes, and thus a constant difference between emitter and input voltage, a constant current *must* flow through the zener diode and load in parallel. Therefore, as the input voltage varies, the current through the zener hardly varies and we have largely eliminated the effect of its dynamic slope resistance.

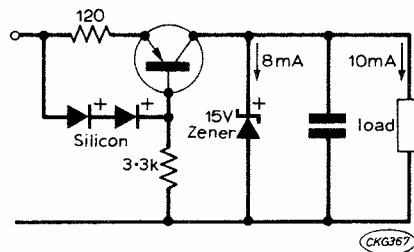


Fig. 5: In this circuit a constant current feed is provided for the zener diode.

Results

A series of measurement was made of the output voltage of the circuit of Fig.5, and of a simple resistance of 620Ω plus zener diode combination, as the input voltage was varied. The results are plotted in Fig. 6, where the remarkable improvement given by the constant current circuit is clearly seen.

A reduction of output voltage variation by a factor of about 30 over the range of 18V to 26V input voltage is surely well worth the additional complexity.

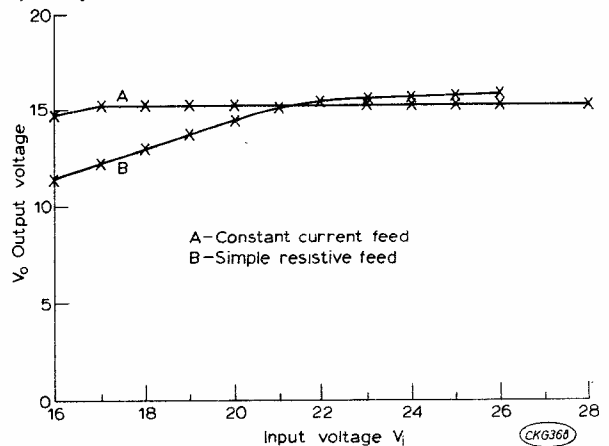


Fig. 6: Performance of zener stabilisers with constant current feed (A) and simple resistive feed (B).

It would doubtless have been possible to have extended the flatter part of curve B down to, say, 18V input voltage, but this would have required a very much smaller value of series resistor than the 620Ω actually employed in obtaining the curve of Fig.6. This would have probably called for the use of a zener diode of greater power rating, and yet it still would not have led to as good a performance as the constant current circuit.

If the zener diode so driven is employed to supply a reference voltage in a series stabilised power supply hum rejection is also greatly improved, for the constant current transistor has a very high output resistance, and this, together with the (relatively) low impedance of the zener diode, gives attenuation of ripple. This offers the chance to use smaller smoothing capacitors. A saving of space and money is the result, as well as improved performance.

One final point. In all the circuits given here a capacitor is shown across the zener diode. This is done since zener diodes are quite effective noise generators! The capacitor also helps to lessen any hum present if a poorly smoothed mains source of power is used with the simpler zener diode circuits.

CHARLES MOLLOY


THE Medium Wave Column

PETER WRIGHT of Formby, Lancashire has tried his PCR2 receiver and 50ft outdoor aerial on the medium waves at 0030hrs and he logged WINS 1010kHz located in New York City. Ian Geddes who lives in Dumbarton, Scotland reports CJON 930kHz in St John's Newfoundland; CHER 950kHz in Sydney Nova Scotia; CKBW 1000kHz Bridgewater N.S.; CFRB 1010kHz Toronto; WOR 710kHz New York City; WOWO 1190Hz in Fort Wayne, Indiana; WABC 770kHz New York City; WKBW 1520kHz in Buffalo N.Y.; WCKY 1530kHz Cincinnati, Ohio; WWVA 1170kHz Wheeling, West Virginia; WNEW 1130kHz New York City. Ian writes "CJON is the most consistent signal from midnight until 0200hrs". Others to listen for from midnight onwards are CBM 940kHz in Montreal; CBA 1070kHz Moncton, New Brunswick; WHN 1050kHz in New York City. A weak French-speaking station can often be heard on 1375kHz after the close down of Lille, France 1376kHz at 2300hrs. This is Radio St Pierre in the French Territory of St Pierre et Miquelon which lies a few miles to the south of Newfoundland. Radio St Pierre verifies readily and is the sole broadcaster on the islands which form a 'medium waves only' DX country.

Kevin Peel (Hornchurch Essex) has an 8 transistor Astrad receiver and a 100ft outdoor aerial and he heard the following broadcasts in English on the medium waves. Radio Portugal 755kHz at 2245hrs; Radio Tirana, Albania on 1394kHz at 2030hrs and Vatican Radio 1529kHz at 2045hrs. J. Cesarczyk (South Croydon) used his Grundig Elite Boy receiver with internal ferrite aerial to hear Radio Jerusalem 737kHz at 2230hrs (with interference from Warsaw and Madrid); Radio Bucharest, Romania 755kHz at 2050hrs; the Voice of America Kavalla, Greece 791kHz (in English at 2300hrs); VOA Rhodes 1259kHz (in English at 0300hrs); BBC World Service, Berlin on 809kHz (in English at 2315hrs after the close down of BBC R4).

During the evening quite a few distant stations can be found in the gaps between European channels. Baghdad, Iraq on 760kHz can be heard between West Germany on 755kHz and Sottos, Switzerland 764kHz and is usually on the air all evening with programmes in Arabic. Riyadh, Saudi Arabia is on 588kHz between Madrid 584kHz and Frankfurt 593kHz; Ovazim, Iran 841kHz is often strong when it signs-off at 2030hrs, listen between Nancy, France on 836kHz and Rome on 845kHz; Ahwaz, Iran can be found on 1394kHz in between Radio Centro Madrid 1385kHz and Albania on 1394kHz; the BBC relay on Masirah Island in the Persian Gulf (heard in English at 2040hrs) is on 1410kHz between the French network on 1403kHz and the Spanish channel on 1412kHz.

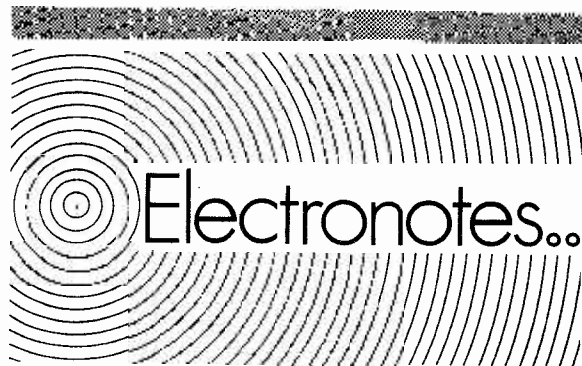Please send logs and information about the medium waves to the author at 132 Segars Lane, Southport, PR8 3JG.



Electronotes..

S. GINSBERG

THE calculator market is flooded with many different types, each claiming some unique feature(s). Of particular interest to the buyers —us— is the price. News has now arrived from a semiconductor manufacturer that i.c. chips are currently in production which are so cheap that an electronic calculator could easily be manufactured and sold at a market price of less than £20.

There are four versions of the chip which are four-function (add, subtract, multiply and divide), eight-digit units with a seven segment output circuit. The entire electronics are housed on a chip area of only 166 x 162 millimetres.

In the United States these chips are already in production and coming off the line at the rate of some 75,000 every four weeks. The Company also reports that orders for the chips in the U.K. have already exceeded £100,000.

Heat sinks are comparatively uninteresting items of electronic hardware. Usually, they consist of a piece of metal often with fins protruding. Their purpose in life is to conduct heat and to dissipate it.

A new introduction is a hollow heat sink which spreads the heat evenly. The difference in temperature between the heat-producing element (say, a power transistor) and the furthest point on the heat sink is only around 1°C.

The heat sinks are fabricated rather like a hot water radiator. The hollow section is evacuated to a virtual vacuum. Water is then fed in. Because the air pressure is so low, the water boils. It then starts to lose heat and also gives off steam which condenses and turns back into water again. Eventually, equilibrium is established and the heat sink cools to room temperature.

The spread of heat on these sinks is extremely fast and the fins may be connected to the heat source by a pipe which has also been evacuated and filled with water. The fins may thus be located remotely from the heat source and the difference of 1°C holds over any part of the heat sinking system.

The cry still goes on about pollution, and electronics has come up with some useful ideas for monitoring. One research laboratory is busily engaged on producing an infra red diode which will emit radiation in the 3 to 6µm band. Carbon monoxide, carbon dioxide and hydrocarbons all absorb radiation strongly in this band and thus the amount of absorption of the radiation gives a measure of the pollution of these chemicals. Infra red diodes already exist, but they radiate at around 0.9µm and hence the need to design a new diode with radiation in the required region.

ATTRACTIVE DISCOUNTS ON MANY ITEMS

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS

Brand new—no seconds or surplus. Highest quality and reliability. Insulating sets FREE with power types.

MANY HUNDREDS OF DIFFERENT TYPES IN STOCK ALL IN OUR NEWEST CATALOGUE

No.	Type	Multi-purpose (General)
2N697	Sil. NPN	
2N1804	Ger. NPN	
2N1805	PNP	
2N2646	Sil. UJT	
2N5226	NPN	
2N8056	NPN	
2N8702	PNP	
2N8704	NPN	
AC126	Ger.	
AC128	Ger.	
AC178	Ger.	
AD149	Ger.	
*AD181	Ger.	
*AD182	Ger.	
BC107	Ger.	
BC108	Ger.	
BC109	Ger.	
BC177	Ger.	
BC178	Ger.	
BC179	Ger.	
BC181	Ger.	
BC182	Ger.	
BC183	Ger.	
BC184	Ger.	
BC185	Ger.	
BC186	Ger.	
BC187	Ger.	
BC188	Ger.	
BC189	Ger.	
BC190	Ger.	
BC191	Ger.	
BC192	Ger.	
BC193	Ger.	
BC194	Ger.	
BC195	Ger.	
BC196	Ger.	
BC197	Ger.	
BC198	Ger.	
BC199	Ger.	
BC200	Ger.	

MINITRON DIGITAL INDICATOR

TYPE 8015F Seven segment indicator compatible with standard logic modules and power supplies. 0-9 on illuminated film.

We are official distributors for SOLDERSTAT SOLDER IRONS

As appointed distributors for well-known Elemen-Wolf "Solderstat" irons we offer this light weight model HMS in 16 or 24 watt, ratings 220/240V a.c. £1.87 nett

INFINITELY VARIABLE TEMPERATURE CONTROLLED SOLDER IRON

Designed essentially for micro-miniature and printed board assemblies. Temperature is adjusted as control on base and remains constant or on load. Although for working to standards, the iron is of rugged constructionally reliable. £9.20 with base, nett

BP desolder 50p

RESISTORS

Code	Power
C	1/8W
C	1/4W
C	1/2W
C	1W
MO	
WW	

Values: E12 denotes their decade 91 and 10 power of resist

BATTERIES


As described in special catalogue RMS/15 carr. Speaker Pack Pack

CARBON Small h. 470 Ω, 470K, mounting.

ZENER DIODES 2.7V to 38V, 1.5W, 4.7V to Clip to increase

MINIATURE TUBES 2A/250V, DP/DT, etc.

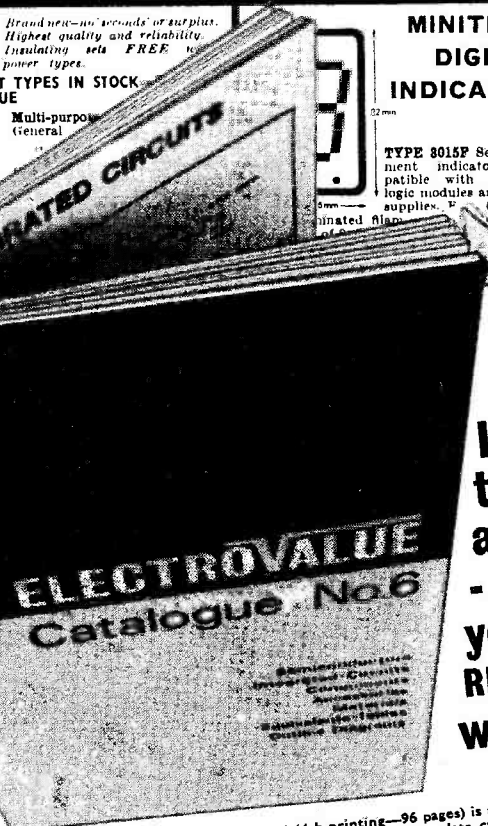MAINLINE AMPLIFIERS 70 watt power amp, mono supply kit, £6.00 nett. Match amp kit, power supply kit as building your own cabinet, £38



It's more than just a catalogue - and we give you a 25p REFUND VOUCHER with it

The Electrovalue Catalogue No. 6 (4th printing—96 pages) is as much a manual of valuable technical information as it is a comprehensive, up-to-date catalogue of semi-conductors, components, accessories, materials, tools etc. All items are brand new and to makers' specifications. Prices are competitive, there are attractive additional discounts offered and now we include a refund voucher for 25p available for spending on orders for £5 or more. Send 25p for latest Electrovalue Catalogue now, post free. Size 8 1/2" x 5 1/2"

- Hundreds of today's most wanted transistors with data and outlines
- Diodes, thyristors and triacs fully detailed
- Associated heat sinks & parts
- I.C.s plus schematics, theoretical and connection diagrams
- Slide and rotary potentiometers, knobs, plates, etc.
- Resistors & capacitors in very wide ranges
- Siemens pot cores
- Connectors, switches, relays
- Transformers, solder irons etc.
- S-Dec, T-Dec, mounting boards
- Materials, Hardware etc.

Any prices appearing in this advertisement are for guidance only. Current prices are as shown in catalogue.

Code	Price
734731	45p
(7475)	45p
(7478)	45p
(7480)	65p
(7482)	87p
(7484)	1.32
(7486)	38p
(7488)	80p
(7490)	28p
(7492)	28p
(7494)	28p
(8322)	28p
(8324)	2

**Why pay more - look at our
Fantastic Bargain Offer!**

PENTHOUSE

A COMPLETE AUDIO SYSTEM


An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder. 4 wavebands Long/Medium/Short/VHF. 8 watts per channel (music power) output. The latest BSR C129 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.
OUR PRICE £63.00



Credit terms £6-30 deposit plus £2-00 p. & p. followed by 12 payments of £5-32. Total Credit Terms £70-14 SEND £8-30 TODAY.


TRANSEUROPEAN

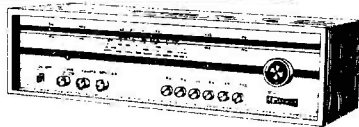A TRANSISTORISED HI-FI STEREO RADIOGRAM SYSTEM AT LESS THAN HALF NORMAL PRICE



The system includes elegantly styled solid state Teak finish cabinet tuner/amplifier. Push-button selection, 4 waveband VHF/FM, short, medium & long wavebands. The latest 4-speed B.S.R. Mono/Stereo record changer with two 10in. x 6in. matching elliptical speakers. Supplied ready for housing.
EASILY FITTED — NO TECHNICAL KNOWLEDGE NECESSARY. OUR PRICE £39.95. Credit Terms of first payment of £3-95. 10 payments of £4-10. Total credit price £44-95, p. & p. £2. SEND £5-95 TODAY


THE AVON AUDIO SYSTEM

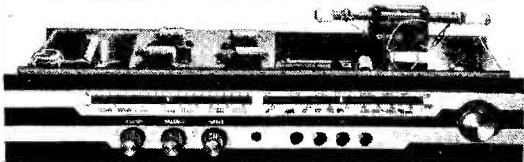

The unboxed system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

BSR 4 SPEED STEREO/MONO RECORD CHANGER plays all types or 7in., 10in., and 12in. Mono of Stereo records. Manual or automatic play.

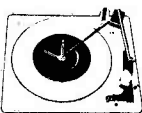TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.



EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45-74. **OUR PRICE £37-00.** Credit Terms £3-70 deposit plus £2 Post & Packing followed by 12 payments of £3-15 (Total Credit Terms £41-50) Don't miss this bargain.
SEND £5-70 TODAY

ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

Please send me free details of your range

Name

Address

PW 2/73

LEWIS radio

100, Chase Side London N.14
Tel: 01-886 3733/9666

Post coupon
NOW for...
FREE
leaflets

YOU MUST HEAR

**miniWISE audiLECT
YOUR
PERSONAL TUTOR**

**THE
No. 1
HIT**

Get **PLEASURE** from your **CAREER**
or **HOBBY** through
ORGANISED TUITION

YOUR PERSONAL TUTOR will give you rapid
UNDERSTANDING—the key to **SUCCESS**
in your own **HOME** and at your own **SPEED**.

Your **FUTURE** in **RADIO, T.V. or
ELECTRONICS** could **EASILY** be much
BRIGHTER.

FOR DETAILS OF THIS UNIQUE METHOD
just send us your name and address

**MINIWISE PRODUCTS
FREEPOST (W), BLETCHLEY, BUCKS.**
(no one will call)

INCLUDE ONLY £1.20 TO OWN A TRIAL LESSON*
on a C90 cassette or L.P. Tape (state which)

* Your money **INSTANTLY REFUNDABLE** if not 100% convinced
that this can be the turning point in your hobby or career.

THE NATURAL WAY TO LEARN

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive, 88—108Mcs, with circuit diagram. **£2 10p.**

B.F.W. 10 Fet. New (unmarked) 5 for **£1 00p.**

SPECIAL OFFERS of Unmarked Tested Power Transistors.

2N3055 Silicon NPN 30p each 4 for **£1.**

2N3054 Silicon 20p each 3 for **50p.**

Plastic 40 Watt NPN 25 Volt 20p each 3 for **50p.**

P-C BOARDS (not computer panels).

1 off 6 transistors single wave band

1 off 4 transistor audio

1 off 3 transistor **£1 50 the three.**

Encapsulated bridge rectifier (itt usd 3 3mdh) 100 PIV 2 amps.
50p each.

Transistor F.M. Stereo Multiplex Decoder. Size: 5 1/2 x 2 1/2 x 1 1/2.
As used in well known British stereo units with circuit. **£3 75.**

GARRARD SP25 MK. II less Cartridge. **£10-50.**

10 VOLUME CONTROLS consisting of 2 off each.

100K log. ganged L/S—20K log. ganged L/S

470K log. D.P. Switch—10K lin. L/S—50K lin. L.S. **£1 25.**

4 PHONO SOCKETS ON PANEL. 10 panels for **£1 25.**

12 PLASTIC KNOBS. Chrome and Gold, 3 types—4 off each
—spring clip **£1 25.**


10 COMPUTER PANELS packed with components including
one panel with 2 Power Transistors. **£1 00.**

All items post paid in

GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

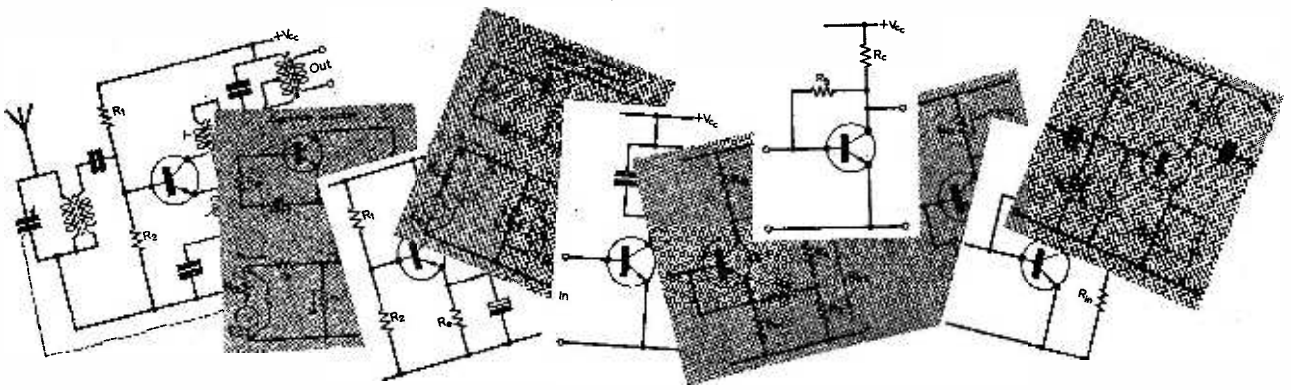

TRANSISTOR CIRCUITRY for beginners

PART 14

H.W. HELLYER & MICHAEL HOLLIER

Feedback etc.

Queries have arisen about our use of the term 'feedback' and its relation to equalisation. This month, while, at the time of writing, colleague Mike Hollier basks in holiday sunshine, seems as good a time as any to indulge myself in a little explanation of the terms we are using and why.

First, feedback. This is simply, as explained last month, a method of picking off part of the output from an amplifier and 'feeding it back' to the amplifier's input section. The feedback can be a simple resistor from collector to base of a single stage amplifier Fig. 67 (a), can be in series with the source signal (b) or in shunt with it (c).

Note that I have deliberately reverted to p.n.p. transistors in these examples. One reason is to remind you of the opening of this series of articles, where the precise examples were quoted; the other is to be able more easily to explain the action of the feedback. Here, I must insert the warning that people, like me, who were brought up on valves began to find difficulties with the revision of feedback concepts as applied to transistors, principally because the operation of transistor circuitry depends on the relationship of the 'circuit blocks' to each other. One has to consider the input and output 'loads' very much more than one did when dealing with valved circuits. So I use the germanium transistor circuits to lead into my subject—don't worry, it will get more complicated later on. . . .

The three examples of Fig. 67, are all of negative feedback. That is, the re-applied signal tends to reduce the gain of the amplifier. Its purpose, of course, is not *just* to reduce the gain but also to stabilise the circuit, help reduce noise and internally generated distortion. The feedback can be applied over several stages, not just the simple sub-circuit shown. And here it is shown as resistive feedback, i.e., effectively d.c. But we shall later be concerned with a.c. feedback, with capacitors in the loop, so that the amount of gain reduction varies as the frequency the circuit is handling also changes. Which will bring us to equalisation: which I would define as the application of frequency-dependent feedback.

Taking Fig. 67 in detail, (a) combines both a.c. and d.c. negative feedback if we insert a series capacitor (shown dotted) with the collector-base resistor R_F and retain the d.c. conditions by the negative feedback across the emitter resistor R_E . Apart from the emitter resistor effectively increasing the

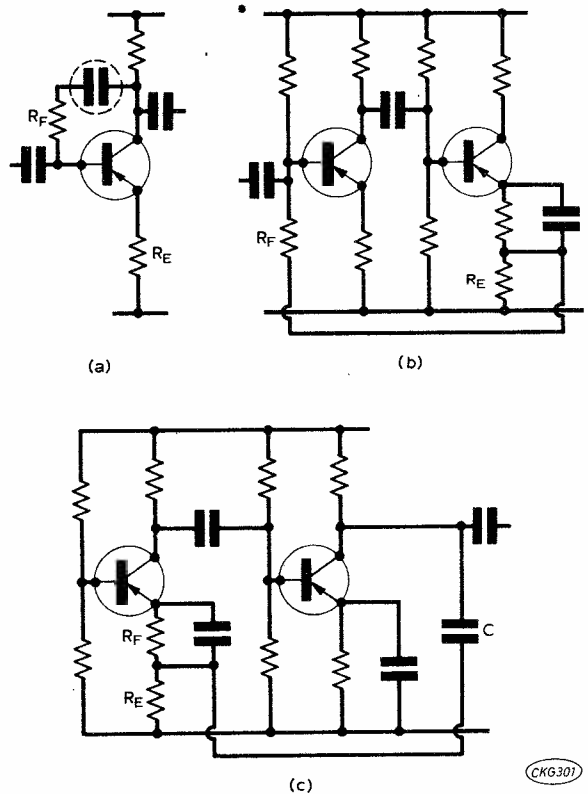


Fig. 67 (a): Simple collector/base negative feedback with d.c. blocking capacitor ringed. Change in value here affects a.c. feedback. (b) series feedback. (c) shunt feedback, from collector of second stage to emitter of first.

CKG301

input resistance to the transistor, which is an advantage, it reduces the gain by being added to the denominator of the formula for voltage gain.

In the sub-circuit (b), the voltage developed across R_E is fed back in series with the lower part of the base bias potentiometer, the latter becoming R_F , and in (c), which is voltage feedback rather than current feedback, as before, R_E does its job in the first emitter while R_F picks off a portion of the amplified signal, the amount dependent on C, and modifies the reduction of gain which R_E is already effecting.

All this has been discussed before, and the relative figures and formulæ given in detail. It does not do us any good going over the same ground, but keep the above three examples in mind as basic 'styles' of feedback when we come to consider the action of equalising circuits. In talking of the virtual resistance circuits during Parts 11, 12 and 13 the point of relative gain with and without feedback, and the change in effective resistance should have been made clear.

Corrective feedback

Why do we want equalisation? If the source itself was 'linear', there would be no need of more or less gain at special frequencies. But there are reasons of plain mechanics and basic magnetics that demand the 'tailoring' of response curves of the input circuits of an amplifier.

Consider the case of a magnetic pick-up cartridge. Because of its construction—virtually a coil in which a moving metal piece causes a changing voltage by altering a magnetic field—and is therefore an inductance, not a pure resistance. The formula for the reactance (an a.c. term for resistance, no more) of a coil is $X_L = 2\pi fL$, where X is the reactance, f the frequency the coil is handling and L its inductance. We will neglect the small resistance of its windings in the case of the pick-up cartridge.

From this, we can see that the higher the frequency, the greater the reactance. So it would seem that our corrective feedback to handle an input from a cartridge need only reduce the gain in proportion to the frequency of the signal—which, in fact, it does.

But the problem is worse than this. To get the

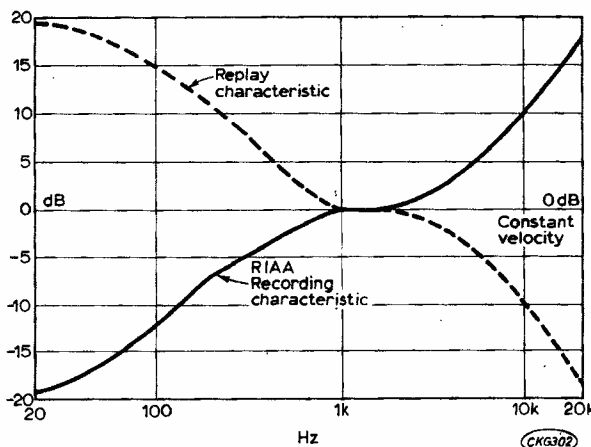


Fig. 68: RIAA recording characteristic as practically employed. Mirror image replay characteristic dotted. Note the short 'plateau' around 1kHz.

dynamic range on to the disc and to maintain as good a signal-to-noise ratio as possible, the bass is attenuated and the treble enhanced. By international agreement, the way in which this is done conforms pretty closely to a standard. This is the RIAA characteristic, Fig. 68.

Modern discs are supposed to be recorded to this characteristic, although any enthusiast will tell you that there are some suspicious variations, difficult to prove except by comparison.

Unfortunately, a magnetic cartridge produces an output (voltage) proportional to its stylus movement. That is to say, it should. So if the characteristic is level, the output should be constant. Over a small portion of that given curve in Fig. 68 the characteristic is level, so testing only at this one frequency cannot give a true picture of the performance of either cartridge or pre-amplifier.

If we now consider how a disc is made, we shall see that the RIAA bass attenuation means that at frequencies below about 1kHz the velocity of the stylus will be reduced, although the amplitude remains constant, just as it very nearly remains constant at the higher frequencies, where the velocity now rises. In fact, the 'average' slope of the given curve is around 4dB per octave, instead of the more generally regarded 6dB per octave, which would be the ideal slope over the two nearly straight portions of the curve. (See also Fig. 71.)

To put matters in perspective, 6dB per octave means that the output voltage doubles for each octave upwards. So a bass note, say A4, the lowest of the white keys, whose frequency is 27.5Hz, giving, say, 1 millivolt at a certain loudness, would be compared with the top A on the piano 'third white note from the top, Joe', at a frequency of 3250Hz, would give 64mV if the original sound had been at the same level.

In fact, this circumstance would not so often apply, and our correction curve can be a replica of the original, mirrored, as shown dotted in Fig. 68 and the dynamic range could be left to take care of itself if the input sensitivity of the pre-amplifier and its overload characteristic are both in order. Too often, one or other is not.

As intimated in Part 11, one reason for the Cambridge style of virtual earth pre-amplifier was to achieve a very much better than usual overload performance. The average output of a magnetic cartridge is between 5 and 8mV (from a voltage output of between 1 and 1.5mV per centimetre per second of recorded velocity). But therein lies the rub.

Bass end overload

We have already seen that it is advisable in the interests of best signal handling to keep our variable controls (volume, tone and balance) after the input circuits. So our magnetic pickup circuit has to be able to handle signals from a couple of millivolts or less to 60mV or more. In practice, because there is bass boost applied during replay to make up for that attenuation during recording, the problem arises at the bass end, and we find that most pre-amplifiers will handle modern records if they have within a 3-30mV input sensitivity ratings. A 30dB overload rating is sometimes specified. If you consider that maximum velocity at 1kHz could be around 25cm/sec and that a cartridge with an output as



LEAK TRUSPEED

2-speed 45 and 33 rpm belt drive turntable complete with plinth, cover and SHURE cartridge. LIST PRICE £69.50

LASKY'S PRICE **£47.50** C & P £1.50

Also available chassis with plinth and cover only, less arm and cartridge **£29.00** C. & P. £1

Garrard Record Players



SP25 Mk. III Deck Only

4 speed Automatic Single Player

Lasky's price **£10.85**

Garrard SL95B Deck	£32.50
Garrard SL95B on base with 9TA cart.	£44.00
Garrard AP76 deck only	£18.85
Garrard 40B deck only	£9.50
Garrard 7025TC deck only	
complete with KS40A stereo ceramic cartridge	£8.50
Garrard ZERO 100 Automatic	£39.95
	C & P £1.50
Garrard ZERO 100S Single Player	£37.50
	C & P £1.50

Garrard Plinths & Covers

WB4 Mk. II Plinth	£5.45
SPC4 Mk. II cover	£4.25
Price together	£9.70
WB1 Plinth	£3.70
SPC1 cover	£3.60
Price together	£7.30

Garrard Module Series

Modules are complete wired units with cartridge, plinth and cover.

SP25 Mk. III Module

SP25 Mk. III with SHURE M75/6 cart. **£23.95**

AP76 Module

AP76 with SHURE M75/6 cartridge **£33.95**

AP96 Module

Single play version of SL95B with SHURE M75/6 cartridge **£38.75**

Zero 100S Module

ZERO 100S with SHURE M93/E cartridge **£52.75**

CARRIAGE

DECK ONLY 50p. PLINTH & COVER ONLY 25p. DECK WITH PLINTH AND COVER 75p.

BSR McDONALD MP60

High precision low-mass counter-balanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.




LASKY'S PRICE **£10.40** C & P 50p

BSR McDONALD UNITS & PACKAGES
 A. Chassis only. B. Complete with Lasky's plinth cover and AD76K cartridge. C. As B but with Shure M55E cartridge. D. McDonald TPD1 package. E. As D plus Goldring G800 cartridge.

MODEL	A	B	C	D	E
MP.60	10.40	18.95	21.00	16.95	19.60
HT.70	14.75	22.95	25.50	21.50	23.95
610	13.75	22.75	24.50	20.70	—

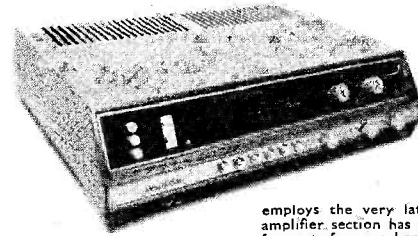210 Complete with plinth, cover & BSR cartridge MP.60 TPD2 Styrene base 17.50 21.00
 810 transcription model £33.50
 810 with BSR plinth and cover £45.00



THE NEW IMPROVED WHARFEDAILE 100.1 STEREO RECEIVER 'SCOOP'

The fully transistorised Wharfedale 100.1 is one of the most powerful stereo receivers made in Britain and has all the refinements that Wharfedale are famous for. The Wharfedale 100.1 super section employs the very latest circuitry including F.E.T.s and I.C.s. The amplifier section has a wide range of inputs together with outputs for up to four speakers. Controls include volume, bass, treble, balance, together with switches for stereo/mono, muting, low pass filter and band selection. Oiled teak case, smoked glass tuning scale black with brushed satin trim. Size: 17.6in x 4.3in x 12.5in.

TUNER SECTION: Sensitivity (AM) 250µV. Signal/noise: (AM) 20dB; (FM) 30dB. Frequency Range: 510-1,650KHz. 150-275KHz. (AM): 87.5-108MHz. (FM). Distortion: less than 0.5%.
 AMPLIFIER: Power Output 35W + 35W into 8 ohms. Frequency Range: 12.5Hz-50,000 Hz. Inputs: (Mag) 3.5mV, (Ceramic) 20mV. (Tape + Aux.) 100mV. Distortion 0.7%. Power Supply 110-127 220-240V. 50/60Hz.

Wharfedale Package

2 WHARFEDAILE Melton II Speakers

GARRARD AP76 Turntable LASKY'S Plinth and cover SHURE M55E cartridge

List Price £249.09
LASKY'S £169.00
 PRICE C. & P. £2.50

DEPOSIT £34.12 Monthly payments of £12.60 TOTAL CREDIT PLAN PRICE £185.20

LIST PRICE £135.00
LASKY'S PRICE £87.50

C. & P. £1.50

INTERNATIONAL MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. RT.20 Message Tape 225ft	19p
3in. RT.21 Triple play, 600ft. Mylar	50p
5in. RT.23 Double play, 1,200ft.	75p
5in. RT.18 Long play, 900ft. Acetate	50p
5in. RT.17 Standard play 600ft.	43p
5in. RT.15 Double play, 1,800ft. Mylar	£1.13
5in. RT.16 Long play 1,200ft. Acetate	75p
5in. RT.24 Standard play 900ft. P.V.C.	68p
5in. RT.14 Long play 1,200ft. Mylar	75p
5in. RT.25 Triple play, 2,400ft.	£1.31
7in. RT.22 Standard play, 1,200ft. Acetate	63p
7in. RT.10 Standard play, 1,200ft. Mylar	63p
7in. RT.12 Long play, 1,800ft. Mylar	95p
7in. RT.13 Double play, 2,400ft. Mylar	£1.25
7in. RT.11 Long play, 1,800ft. Acetate	£2.50
7in. RT.19 Triple play, 3,600ft. Mylar	£2.50
3in. RT.22 Quad play, 1,100ft.	£1.02

P & P 5p extra per reel, 4 reels and over Post Free. Special quotes for quantities.

LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Single	5	10	15
C60	26p	£1.29	£2.53	£3.71
C90	38p	£1.85	£3.62	£5.33
C120	47p	£2.29	£4.48	£6.59

Each cassette individually boxed in Philips, type plastic library. C & P: each 7p, 5—25p, 10—40p, 20—68p.

TM-5 TEST METER

5000 ohms volt

Another pocket multimeter from Lasky's. The "slimline" impact resistant case-size 4 1/2in x 2 1/2in x 1 1/2in fitted with extra large 2 1/2in square meter. Readability is superior on all low ranges, making this an excellent instrument for servicing transistorised equipment. Zero ohms adjustment. Buff finish with crystal clear meter cover. ● DC/V: 3—15—150—300—1,200 at 5K ohms/V. ● AC/V: 6—30—300—500 at 2.5K ohms/V. ● DC Current: 0—300µA, 0—300mA. ● Resistance: 0—10K ohms. 0—1Mohms. ● Decibels: —10dB to 16dB ● complete with test leads, battery and instructions.



LASKY'S **£2.55** C. & P. 35p PRICE

LASKY'S STEREO HEADPHONES Model LSH-30

A new open back headphone with acoustically treated rear vents for increased bass response. Individual controls are provided on each phone for volume and tone. Finished in impact resistant plastic with matching padded headband and ear pads. Complete with coiled lead and stereo jack plug. Freq. range: 30-20,000Hz. Imp.; 8 ohms.

LASKY'S **£6.50** C&P PRICE 25p

LSH-20

A new high quality stereo headphone with individual volume controls for each phone plus a stereo/mono switch. Fully adjustable with softly padded headband and ear pads for comfort. Complete with coiled lead and stereo jack plug. Freq. range: 40-19,000Hz. Imp.: 8 ohms.

LASKY'S **£3.50** C&P PRICE 25p

AUDIO-TRONICS 1973 JUST PUBLISHED

The 1973 edition of Lasky's famous "Audio-Tronics Pictorial" is now available. Bigger, brighter and better than ever. Lasky's brand new catalogue now contains 48 pages packed with all the latest Hi-Fi and electronics equipment—everything for the layman and enthusiast alike. All the goods shown in the "Audio-Tronics Catalogue" are available from any of our branches or by Mail Order to any address in the U.K. or overseas. Free on request. Just send your name, address and 15p for post and inclusion on our regular mailing list.

FREE SEND TODAY—and bring the benefit of shopping at Lasky's to you in the comfort of your home.



Lasky's Radio Limited

Branches

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605
 Open all day, 9 a.m.—6 p.m. Monday to Saturday

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271
 Open all day, 9 a.m.—6 p.m. Monday to Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 0845
 Open all day, 9 a.m.—6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812
 Open all day Thursday, early closing 1 p.m. Saturday

MAIL ORDERS TO: 3-15 CAVELL ST. LONDON E1 2BN 01-790 4821

**Fully guaranteed
individually packed
VALVES**

B19H £1.75	ECH84 45p	N78 £1.75
CY31 35p	ECH200 82p	OAB2 35p
DAF96 43p	ECL80 42p	OB2 35p
DF96 45p	ECL82 35p	PABCO80 37p
DK96 43p	ECL83 7p	PC87 45p
DL92 32p	EAL186 40p	PC800 47p
DL94 45p	EF96 45p	PC834 40p
DL96 45p	FF37A £1.25	PC859 50p
DM70 30p	FP40 50p	PC889 55p
DY86 33p	FP41 65p	PC890 77p
DY87 32p	FP80 25p	PC890 30p
DY802 45p	FP83 55p	PC892 33p
E88CC/01 £1.00	EF85 35p	PC894 60p
	EF86 30p	PC896 60p
	EF89 28p	PCF200 78p
E180CC 42p	EF91 30p	PCF201 78p
E181CC 90p	EF92 35p	PCF801 45p
E182CC £1.20	EF95 35p	PCF802 50p
	EF98 35p	PCF803 50p
EAB50 20p	EF183 30p	PCF805 30p
EACB80 30p	EF184 35p	PCF806 70p
EAF42 52p	EL200 75p	PCF808 85p
EB91 18p	EL34 50p	PCH200 70p
EB93 50p	EL41 58p	PCL181 47p
EB94 50p	EL42 58p	PCL82 35p
EB95 31p	EL84 24p	PCL83 60p
EB96 40p	EL85 42p	PCL84 42p
EB97 40p	EL86 40p	PCL85 42p
EB98 30p	EL90 35p	PCL86 43p
EC81 30p	EL95 55p	PF1200 81p
EC82 28p	EL96 55p	PL36 36p
EC83 30p	EM31 25p	PL81 48p
EC84 30p	EM30 40p	PL82 40p
EC85 40p	EM34 35p	PL83 42p
EC86 45p	EM37 70p	PL84 35p
EC88 37p	EY51 40p	PL600 78p
EC8189 52p	EY86 40p	PL604 75p
EC890 35p	EY81 40p	PK4 £2.50
EC892 35p	EY88 40p	PY33 60p
EC893 75p	EZ41 50p	PY80 35p
EC894 62p	EZ80 25p	PY81 27p
EC895 62p	EZ81 27p	PY82 35p
EC896 35p	EZ84 58p	PY83 35p
EC897 61p	EZ87 70p	PY88 37p
EC898 23p	EZ88 22.05p	PY890 40p
EC899 40p	KT88 £2.40	PY801 50p

**SPECIAL OFFER p & p
09) TUBE £2.50 50p**

OA5 20p	OC71 12p	IN828A £1.80	3N154 85p	BC108 10p	GET115 45p
OA10 25p	OC72 20p	IN4785 50p	3N159 £1.45	BC113 10p	GET116 50p
OA70 10p	OC73 80p	IN4785 35p	FR5 45p	BC118 20p	GET116 50p
OA71 10p	OC75 25p	IZM710 37p	IZFR60 75p	BCY72 15p	NKT222 20p
OA73 7p	OC76 25p	IZT5 87p	40F64 12.5p	BF115 25p	NKT304 50p
OA74 7p	OC81 20p	IZT10 50p	40F73 25p	BF173 25p	RA8910A 40p
OA79 (GD15 10p)	OC82 20p	2G385 51p	40G68 11.5p	BFY51 25p	6J3GT 25p
	OC83 20p	2G403 51p	40G68 11.5p	BFY52 25p	6J3GT 25p
	OC84 20p	2N912 37p	40G69 11.5p	BS 45p	6K7 25p
	OC85 20p	2N912 37p	40G69 11.5p	BS 45p	6K7 25p
	OC86 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC87 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC88 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC89 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC90 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC91 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC92 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC93 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC94 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC95 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC96 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC97 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC98 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC99 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p
	OC100 20p	2N1806 25p	40G69 11.5p	BS 45p	6K7 25p

TRANSISTORS, ZENER DIODES etc.

6J3GT 25p	19413 24.25p	6065 65p
6J8 20p	19416 21.50p	6080 21.50p
6J7G 25p	19414 21.50p	6112 21.50p
6J7M 40p	20P4 41.00p	8020 22.25p
6K6GT 56p	251.6GT 40p	9001 22.00p
6K7 20p	30C15 70p	9002 25p
6K7G 20p	30C17 80p	9003 50p
6K8GT 40p	30C18 70p	9004 13p
6K9 40p	30C19 80p	9006 16p
6SA7 40p	30R11 75p	
6SA7GT 22p	30R12 75p	
6S8GT 35p	30R13 50p	
6S9GT 35p	30R14 50p	
6S9GT 35p	30R15 50p	
6S9GT 35p	30R16 50p	
6S9GT 35p	30R17 50p	
6S9GT 35p	30R18 50p	
6S9GT 35p	30R19 50p	
6S9GT 35p	30R20 50p	
6S9GT 35p	30R21 50p	
6S9GT 35p	30R22 42p	
6S9GT 35p	30R23 42p	
6S9GT 35p	30R24 42p	
6S9GT 35p	30R100 42p	

Colmor ALL valves guaranteed

6J3GT 25p	19413 24.25p	6065 65p
6J8 20p	19416 21.50p	6080 21.50p
6J7G 25p	19414 21.50p	6112 21.50p
6J7M 40p	20P4 41.00p	8020 22.25p
6K6GT 56p	251.6GT 40p	9001 22.00p
6K7 20p	30C15 70p	9002 25p
6K7G 20p	30C17 80p	9003 50p
6K8GT 40p	30C18 70p	9004 13p
6K9 40p	30C19 80p	9006 16p
6SA7 40p	30R11 75p	
6SA7GT 22p	30R12 75p	
6S8GT 35p	30R13 50p	
6S9GT 35p	30R14 50p	
6S9GT 35p	30R15 50p	
6S9GT 35p	30R16 50p	
6S9GT 35p	30R17 50p	
6S9GT 35p	30R18 50p	
6S9GT 35p	30R19 50p	
6S9GT 35p	30R20 50p	
6S9GT 35p	30R21 50p	
6S9GT 35p	30R22 42p	
6S9GT 35p	30R23 42p	
6S9GT 35p	30R24 42p	
6S9GT 35p	30R25 42p	
6S9GT 35p	30R26 42p	
6S9GT 35p	30R27 42p	
6S9GT 35p	30R28 42p	
6S9GT 35p	30R29 42p	
6S9GT 35p	30R30 42p	
6S9GT 35p	30R31 42p	
6S9GT 35p	30R32 42p	
6S9GT 35p	30R33 42p	
6S9GT 35p	30R34 42p	
6S9GT 35p	30R35 42p	
6S9GT 35p	30R36 42p	
6S9GT 35p	30R37 42p	
6S9GT 35p	30R38 42p	
6S9GT 35p	30R39 42p	
6S9GT 35p	30R40 42p	
6S9GT 35p	30R41 42p	
6S9GT 35p	30R42 42p	
6S9GT 35p	30R43 42p	
6S9GT 35p	30R44 42p	
6S9GT 35p	30R45 42p	
6S9GT 35p	30R46 42p	
6S9GT 35p	30R47 42p	
6S9GT 35p	30R48 42p	
6S9GT 35p	30R49 42p	
6S9GT 35p	30R50 42p	
6S9GT 35p	30R51 42p	
6S9GT 35p	30R52 42p	
6S9GT 35p	30R53 42p	
6S9GT 35p	30R54 42p	
6S9GT 35p	30R55 42p	
6S9GT 35p	30R56 42p	
6S9GT 35p	30R57 42p	
6S9GT 35p	30R58 42p	
6S9GT 35p	30R59 42p	
6S9GT 35p	30R60 42p	
6S9GT 35p	30R61 42p	
6S9GT 35p	30R62 42p	
6S9GT 35p	30R63 42p	
6S9GT 35p	30R64 42p	
6S9GT 35p	30R65 42p	
6S9GT 35p	30R66 42p	
6S9GT 35p	30R67 42p	
6S9GT 35p	30R68 42p	
6S9GT 35p	30R69 42p	
6S9GT 35p	30R70 42p	
6S9GT 35p	30R71 42p	
6S9GT 35p	30R72 42p	
6S9GT 35p	30R73 42p	
6S9GT 35p	30R74 42p	
6S9GT 35p	30R75 42p	
6S9GT 35p	30R76 42p	
6S9GT 35p	30R77 42p	
6S9GT 35p	30R78 42p	
6S9GT 35p	30R79 42p	
6S9GT 35p	30R80 42p	
6S9GT 35p	30R81 42p	
6S9GT 35p	30R82 42p	
6S9GT 35p	30R83 42p	
6S9GT 35p	30R84 42p	
6S9GT 35p	30R85 42p	
6S9GT 35p	30R86 42p	

1.5mV/cm/S would give 38mV from such a recorded groove, you can see that distortion on signal peaks would be inevitable, as this would require an overload rating of some 38dB.

So the overload safety margin diminishes toward the lower end of the frequency spectrum, and this is where mains hum, disc rumble, turntable rumble and other problems can rear their ugly heads. Hence the need, when we design our 'front-end' amplifiers to ensure that we get good gain figures before applying our feedback—and, what is more, a stable amplifier without (or with minimum) feedback, for it is precisely at this dangerously low end of the spectrum that the feedback will be least.

This is not the place to go on about cartridges, but I hope I have helped clear up a few of those queries about the need for good basic pre-amplifier design as well as the application of very precise feedback. And perhaps dropped a few hints about choice of pickup: if you have an amplifier with a sensitive magnetic pickup pre-amplifier and shove a high output cartridge into it, you can expect a bit of bass overload. As this occurs before any control you can apply, there is no real cure except correct matching.

In practice

One could quote extensively from commercial circuits to prove a point, but to combine our previous talk about virtual earth circuits and to use a design which has been proven by constructors, let me cite the modular pre-amplifier by John L. Linsley Hood, which appeared first in *Wireless World* in July 1969, and which, although parts have been modified since, happens to suit our purpose. Mr. Hood has kindly consented to allow us to quote him.

Fig. 69 shows his basic concept of a stage used to obtain the RIAA replay characteristic. Looking at it carefully, we see that it is again a virtual earth design, with point X the null point, provided the gain of the amplifier is high enough. The input impedance of the circuit will be approximately equal to that of the input network R1/C1. The load resistance of a magnetic cartridge is around 47kΩ at 1kHz, and provided C2 is large enough and R2 equal

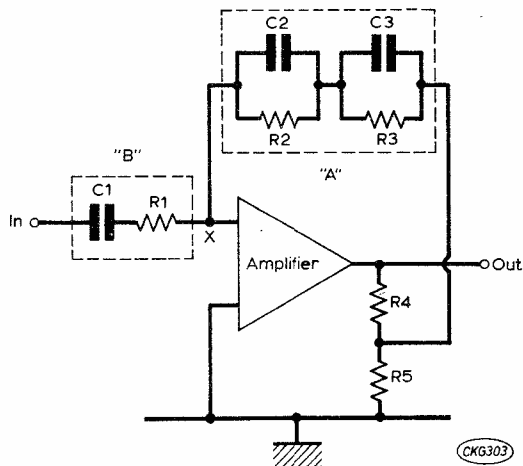


Fig. 69: Frequency selective feedback to achieve the RIAA replay characteristic, applied around a virtual earth amplifier.

to R1, C3 relatively small in relation to R2 (at 1kHz), stage gain can be given approximately by $R4 + R5/R5$.

The designer aimed at a gain of 10, this being deemed sufficient to deal with outputs between 4 and 10mV. The frequency response is determined by the two networks 'A' and 'B', shown in dotted 'boxes' in Fig. 69. In this idealised state, the circuit is not entirely practical, of course. Fig. 70 shows the actual circuit, drawn so that these frequency corrective components are at the front.

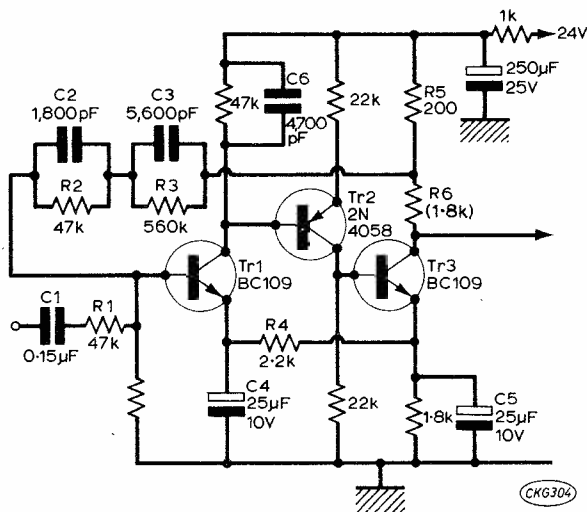


Fig. 70: The redrawn circuit of Fig. 69, part of the J. L. Linsley Hood modular pre-amplifier.

But we must also consider the effect of C4 and C5, which, in conjunction with C1 and R4, give a steep-cut rumble filter (18dB/octave) with an attenuation of more than 40dB at 8Hz and a turnover point of 25Hz. The results can be seen in the RIAA replay curve, measured from the pre-amp, in Fig. 71.

Two things remain to be mentioned. C6 is put across the collector load of the first transistor to sharpen up the transient response: the dotted curve

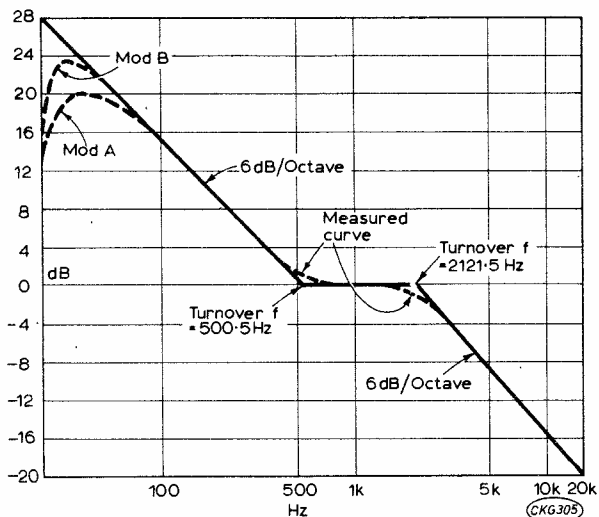


Fig. 71: Theoretical RIAA replay response curve with measured deviations. Bass roll-off is deliberately obtained by component changes.

at the bass end of this curve is in two parts. The lower is for the circuit shown; the higher, for a modified circuit. The last because the author (Mr. J. L. Linsley Hood), suspects that sufficient recording bass lift is not always given to accord with RIAA standards, and he consequently changed some values of his feedback components to get a flatter response down to 25Hz with a steeper roll-off as a protection against rumble.

These changes were as follows: R5—470Ω, R6—1.5kΩ, C1—0.47μF, C3—6,800pF and C6—6,800pF.

These modifications reduce the gain, and he has thus added a sub-circuit that we can now include in our armoury—the floating emitter, collector-follower. We show his addition in Fig. 72.

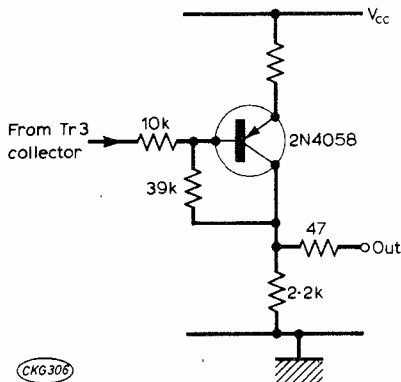


Fig. 72: A floating emitter collector-follower stage added to compensate for loss of gain.

Coping with the outputs of both magnetic and ceramic pick-up cartridges may seem a bit ambitious and, as done commercially, is not always very effective. But one can do it by switching those networks, 'A' and 'B' of our Fig. 69.

A ceramic cartridge normally likes to 'see' an impedance of a megohm or more at the amplifier input and as it is a capacitive device will suffer from low-frequency loss if this input is reduced. Hence the poor performance of many cheap record players, which have to suffer the design restrictions of transistor amplifiers with high input impedance, while retaining the best possible gain and noise performance. By using the virtual earth configuration, one gets over this problem neatly and the three suggested sub-circuit alterations by Mr. Hood are shown in Fig. 73. Here we have (a) a network that will retain the curve sensibly level down to about 30Hz, with the bass roll-off now made better by halving the values of C4 and C5 as well. And (b), a change to network 'B', while 'A' is as in the first modification. This is a suggestion by the author to obtain a 6dB/octave rise, followed by a level response, making a 'platform' over the portion of the replay curve of Fig. 68 that is fairly level from around 1kHz to around 2kHz.

To get even more treble response, without nasty peaks, i.e., to give this same 'platform' effect to a 12dB level after about 4kHz, (c) is suggested. The reason for these changes is to equalise for the 12dB drop in voltage anticipated when an RIAA recording (having velocity characteristics) is replayed with a displacement-sensitive device, such as a piezo-electric cartridge. As you can see, the modification entails shunting part of the input resistor with a small capacitor.

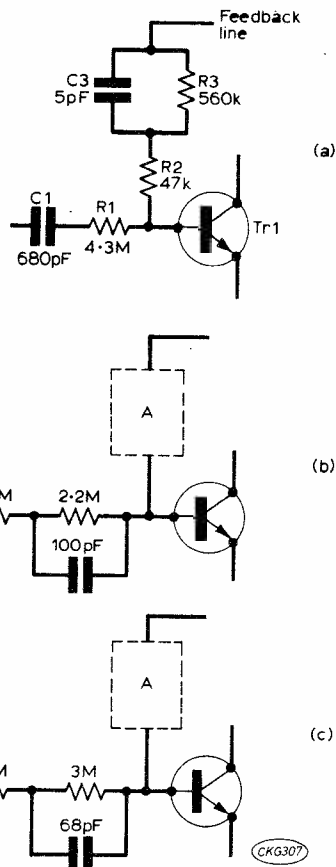


Fig. 73: Circuit changes to permit a ceramic cartridge to be fed into the same amplifier with (a) level response above 35Hz (b) a 6dB lift from 1 to 2kHz and (c) a 12dB lift at 6dB/octave, followed in each case a level response.

This, finally, brings me to the point that Mike asked me to make after last month's contribution had made its way irrevocably to the printers, viz., a capacitor shunted across the feedback resistor will give treble reduction while if it is across the input series resistor it gives treble lift, as in this previous example.

Just thought you'd like to know . . . !

TO BE CONTINUED

Back Numbers

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of **Practical Wireless** or **Television**.

To ensure obtaining regular copies of these magazines readers are strongly urged to place a regular order with their local newsagent, or to take out an annual postal subscription.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

BSR LATEST SUPERSLIM STEREO AND MONO
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in. Above motor board 31in. below motor board 21in. with STEREO and MONO XTAL £8.75, Post 25p.
MONO-COMPATIBLE £7.75 Post 25p.
Plays all records

BSR JUNIOR
Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono cartridge £4.50 Post 25p.

E.M.I. WOOFER AND E.75 TWEETER KIT
Available separately Post 25p.
Wooler #4-25 Tweeter #1-90
Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 440z, 70 Gauss, 15,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.
Impedance Standard 8 ohms
Maximum Power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps

SUITEABLE ENCLOSURE 20 x 13 x 9 in. £9 POST 25p
MODERN DESIGN TEAK WOOD FINISH

SPECIAL OFFER
SMITHS CLOCKWORK 15 AMP TIME SWITCH
Single pole two-way.
Makers list price £4.50.
Brand new and fully guaranteed. Surface mounting with fixing screws.
Will replace existing wall switch to give light for return home, garage, automatic anti burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available for 1 or 2 hours.
OUTR PRICE £1.50. P & P 15p or £3 pair Post Free. (Please state type when ordering).

WEYRAD P50—TRANSISTOR COILS
RAW Ferrite Aerial... Spare Cores... 3p
Osc. P50/LAC... Driver Trans. LFDT4... 58p
I.F. P50/200... Printed Circuit, PCA1... 58p
I.F. P50/300... D.P. Tuning Gang... 65p
P51/L or P51/2... Weyrad Booklet... 10p
P50/3V... OPTI... 58p
Mullard Ferrite Rod 8 x 1/2 in. 20p, 6 x 1/2 in. 20p.

VOLUME CONTROLS
Long spindles. Midsize Size 5 K. ohms to 2 Mega Ohm or 20 Mega Ohm.
L.I.F. L/S 15p. D.P. 25p.
STEREO L/S 55p. D.P. 75p.
Edge 5K. S.P. Transistor 25p.

800hm Coax 4p. vd. BRITISH AERIAL TYPE PERAXIAL-AIR SPAED 40 vd. £1.40; 60 vd. £2. FRINGE LOSS 10p vd. Ideal 625 and colour.

8in & 10in ELAC HI-FI SPEAKERS
Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm coil. 8in. 10 watt. 10in. 12 watt music power. £3.75

E.M.I. 13 1/2 x 8in. SPEAKER SALE!
With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 25p
With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p £2.25

TEAK CABINET £5 Post 25p. 16 x 10 x 8in.

BRITISH MADE STEREO MULTIPLEX DECODER
Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2 1/2 x 6 1/2 in. Pre-aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100V i.n.t. Full instructions for any FM Tuner. Some technical experience essential. £6.50

BLANK ALUMINIUM CHASSIS 18 s.w.g. 2in. sides, 6 x 4in. 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 80p; 14 x 11in. 95p; 15 x 14in. 99p; 11 x 9in. 50p; 16 x 10in. £1
ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 9p; 8 x 8in. 15p; 14 x 8in. 18p; 10 x 7in. 19p; 12 x 5in. 20p; 12 x 8in. 23p; 16 x 8in. 28p; 14 x 9in. 34p; 12 x 12in. 40p; 16 x 10in. 50p.

HI-FI STOCKISTS RETURN OF POST DESPATCH
RADIO COMPONENT SPECIALISTS
Illustrated Colour Brochure, Radio Books & Component Lists 10p. (Export: Remit cash and extra postage.)

WHARFEDALE SUPER 10" HI-FI SPEAKER
15 watt 4 to 8 ohms. Response 20 cps to 12 Kcs. Bass resonance 45 cps. Massive Ceramic Magnet. Deep fabric cone surround. Cast alloy frame. Weight 5 lbs. Value £10.50
OUR PRICE £5.50

THE FAMOUS WHARFEDALE SOUND!

R.C.S. STABILISED POWER PACK KITS
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240v. AC. Output voltages available 6 or 9 or 12 or 15 or 18 or 20v. DC at 100mA or less.
PLEASE STATE VOLTAGE REQUIRED. £2 POST FREE
Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2 in.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE
Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2 in. Response 25 c.p.s. to 25 Kcs. 28db gain. For use with valve or transistor equipment. 90p Post 10p
Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS	CAN TYPES
2/350V . 14p	250/25V . . . 35p
4/350V . 14p	500/25V . . . 20p
8/450V . 14p	1000/25V . . . 35p
15/450V . 14p	1000/50V . . . 47p
32/450V . 20p	8+8/450V . 18p
25/25V . 10p	8+16/450V . 20p
50/50V . 10p	16+16/450V . 25p
100/25V . 10p	32+32/350V . 25p
	100+50+50/350V . 48p

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 12V. 15p
1000mF. 12V. 15p
1000mF. 6V. 25p
2500mF. 50V. 62p
6000mF. 6V. 25p

CERAMIC 1P-F to 0.01 mF. 4p. Silver Mica 2 to 5000P.F. 4p. PAPER 350V-0.1 4p. 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%; 2.2-5000P.F. 5p; 500-2.200 P.F. 10p; 2.2-5000 P.F. 20p; 6.8000P-F 0.01, mid 30p; each. TWIN GANG. 50-0.0206P.F. + 176P.F. 65p; Slow motion drive 365 + 365 with 25 + 25p. 50p; 500P.F. standard, 45p; Single gang 500P.F. 75p; small 3-gang 500P.F. £1.60. SHORT WAVE, SINGLE. 10pF 30p; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS 250V AC/DC Amber 20p. RESISTORS. 1/4 w. 1, 1/2, 1p. 2 w. 5p. 10 ohms to 10 meg. HIGH STABILITY. 1/4 w. 2, 10 ohms to 1 meg. 10p. Ditto 5%. Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K. 10p each; 2 1/2 watt, 1 ohm to 8.2 ohms 10p TAPE OSCILLATOR COIL. Valve Type 35p.

GARRARD DECCA DISCO DECK
£18.50 Post 25p
Single Play Stereo Mono
Deram transcription head and arm. Four speeds. 10 in. turntable. Anti-rumble filter. Bias compensation. Laboratory motor.
METAL PLINTH & PLASTIC COVER £4.50
Cut out for most Garrard or B.S.R. Most will play with cover in position. 12 1/2 x 14 1/2 x 7 1/2 in. Covered in black leatherette. Post 35p

ALSO AVAILABLE IN SOLID NATURAL MOHOGANY WAX POLISHED FINISH-AT SAME PRICE

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp.	£1.50
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£2.50
350-0-350 80 mA. 6.3 v. 5 a. 6.3 v. 1 a. or 5 v. 2 a.	£3.00
300-0-300 v. 120 mA. 6.3 v. 4 a. CT.; 6.3 v. 2 a.	£3.25
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 x 2 in.	75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 x 2 in.	90p
HEATER TRANS. 8.3v. 3 a.	60p

GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2.25
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60, £2.55
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60, £3.05
3 amp. 5, 8 and 18v £1.00; Ditto 5 amp. £1.20
3 amp. 3, 5, 8, 10, 13 and 5-0-5v. £1.30; Ditto 5 amp. £1.50
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 10w. £2.25; 50w. £6.25; 75w. £10; 100w. £14.
CHARGER TRANSFORMERS; Input 200/250V. for 6 or 12v. 1 amp. £1.50; 2 amp. £1.80; 4 amp. £2.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS; 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p
BATTERY CHARGERS 1 1/2 A; 2A; 3A; 3A; 4A £4.
LUCAS 2DS500 Full wave Bridge 70V 5 amp 95p.

FACTORY ACT! MAINS ISOLATING TRANSFORMER
Primary 0-110-240v. Secondary 0-240v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make. Value £13.
OUR SPECIAL PRICE £10 Carriage 50p.
Can be used as 800 watt Auto Transformer 240-110V.

MINIMUM POST AND PACKING 15p CUSTOMERS FREE CAR PARK CALLERS WELCOME
337 WHITEHORSE ROAD, CROYDON
Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)
Buses 50, 68, 159 Rail Selhurst. Tel. 01-684-1665

ALL MODELS "BAKER SPEAKERS" IN STOCK
Hi Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free

BAKER 12in. MAJOR £9
30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch £8	12 inch £9	15 inch £20
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS.
For 12in. or 10in. dia. speaker 20 x 12 x 9in. £9. Post 25p
For 18 x 8in. or 8in. speaker 18 x 10 x 9in. 25. Post 25p
For 10 x 6in. or 6in. speaker 18 x 8 x 6in. £4. Post 25p
LOUDSPEAKER CABINET WADING ISIN. wide, 15p ft.

GOODMANS 6 1/2 in. HI-FI WOOFER £4
8 ohm, 10 watt. Large ceramic magnet. Special Cambria cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns, Hi-Fi Enclosures Systems, etc.
Sin. STANDARD CONE 12W. £4.50

ELAC CONE TWEETER
The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 x 2in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1.90 Post 10p

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kcs, 10W 8 ohm or 15 ohm £1.95 De Luxe Horn Tweeters 2-18 Kcs, 15W, 15 ohm £2. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p. **LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in. £1.25; 6in. £1.50; 8 x 6in. £1.60; 8 x 2 1/2in. £1.50 8in. £1.75; 10 x 6in. £1.90.**
SPECIAL OFFER! 80 ohm 2 1/2in.; 2 1/2in.; 35 ohm, 2in.; 3in 25 ohm, 2 1/2in. dia.; 3in dia.; 6 x 4in.; 7 x 4in.; 8 x 5in. TYPE 3 ohm 2 1/2in.; 2 1/2in.; 3in. 5in. dia. (6 x 4in. 3 ohm £1 each)
RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4 watt; 10in. 5 watt; 12in. 6 watt 3 or 8 or 15 ohm models £2.20 each. Post 15p.
VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50.1 25p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER
4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.95
BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE 25.95
BARGAIN FM TUNER 88-108 Mc/Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £14.85
BARGAIN FM TUNER as above less cabinet £9.85
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £4.50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p
OUTLET BOXES. SURFACE OR FLUSH 25p
BALANCED TWIN RIBBON FEEDER 300 ohms 5p yard;
JACK SOCKET 5id. open-circuit; 14p. closed circuit 23p.
Chrome Lead Socket 45p. Phone Plugs 6p. Phone Socket 5p
JACK PLUGS 5id. Chrome 15p; 8 5mm Chrome 12p. DIN SOCKETS chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 6p; CANS 5p.

E.M.I. TAPE MOTORS Post 15p.
120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. £1.25
Size 3 1/2 x 2 1/2 x 2 1/2 in. (Illustrated).
E.M.I. GRAM MOTORS
120v. or 240v. A.C. 2,400 r.p.m. 2-pole 70mA. Spindle 3/8 x 1/2 in. 75p.
Size 2 1/2 x 2 1/2 x 2 1/2 in. Post 15p.

943


LINEAR

AMPLIFIERS FOR GUITAR PICK-UPS GRAM PICK-UPS RADIO or TAPE

OVERLOAD PROTECTION INCORPORATED. SOLID STATE CIRCUITRY

Suitable for application of Loudspeaker impedances between 8 and 30 ohms. Combinations not to measure less than 6 ohms across both speaker output jacks simultaneously.

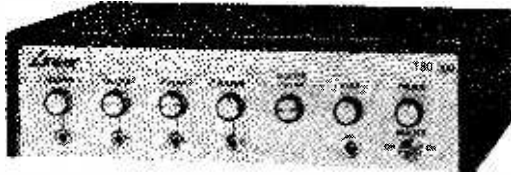The Amplifier cover is made of rigid plastic, bonded metal on the top and two sides. Finished in Black to suitably contrast with anodised metal control panel. Size approx. 14" x 4 1/2" x 9 1/2".



GENERAL PURPOSE AMPLIFIER

Model T80/100 70 - 100 Watts Output Power

Four individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.

Compact size, robust construction. Ideal for clubs, hotels, restaurants, schools etc. Inputs for almost any type of microphone


Rec. Retail Price **£69-75**

GENERAL PURPOSE GROUP/DISCO AMPLIFIER Model T80/100D

70 - 100 Watts Output Power

Three individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.

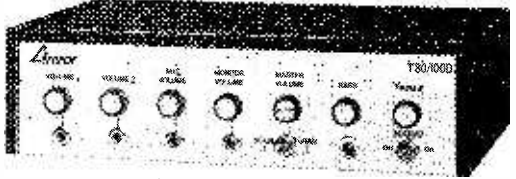Compact size. Robust construction. Ideal for discotheques, clubs, hotels, schools, etc. Inputs for most types of microphones. Facilities for head-phone monitoring with changeover switch from input (1) to input (2).




Rec. Retail Price **£69-75**

Wholesale and Retail enquiries to the Manufacturers Send S.A.E. for leaflet/s All Linear Amplifiers Guaranteed for 12 Months

LINEAR PRODUCTS LTD., Electron Works, Armley, Leeds. LS12 3SA Tel. 630126

SAVE TIME AND MONEY

LIST PRICE **£6-25** | OUR PRICE **£4-84**

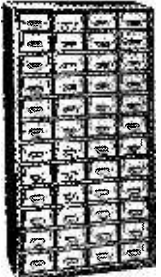

As supplied by us to **SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY.** Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21 1/2" x 11 1/2" x 6 1/2". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available. Callers welcome Mon.-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. NEW as illustrated **OUR PRICE ONLY £4-84** plus 35p carriage on orders less than £10. Money back guarantee. **SEND FOR FREE COLOUR BROCHURE.**

TRADE AIDS

(DEPT. PW7), 111 CHILTERN DRIVE, BERRYLANDS, SURBITON, SURREY

01-399 4383

100 yds. Berrylands Railway Station.

EX COMPUTER PRINTED CIRCUIT PANELS

2 x 4 in. packed with semi-conductors and top quality resistors, capacitors, diodes etc. Our price 10 boards 50p (8p). With a guaranteed min. of 35 transistors—data included.

SPECIAL BARGAIN PACK

25 boards for £1 (25p).
ELECTROLYTICS
10,000µ 75v, 33,000µ 40v, 4 1/2 x 2 1/2 in. dia., 2,500µ 25v, 20,000µ 30v, 8,000 55v, 4 1/2 x 3 in. dia. 50p (12p), 15,000µ 15v, 4 1/2 x 2 in. dia. 20p (10p), 2,000µ 25v wire ended, 3 x 1 in. dia. 15p (5p) or 12 for £1 (15p).

250 MIXED CAPACITORS 60p (8p)
250 MIXED RESISTORS 60p (8p)
20A STUD RECTIFIERS, 100 p.i.v. 4 for £1 (7p)

3A STUD RECTIFIERS, 100 p.i.v. 4 for 50p (5p)

ASSORTED RELAYS 8 for £1 (25p)
SUB MIN. CO-AX. PLUGS & SKTS. 4 pairs 50p (5p)

MINIATURE GLASS NEONS 12 for 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)
MICRO SWITCHES, MIXED 8 for 50p (8p)

PAPST EXTRACTOR/BLOWER FANS 100 cfm 4 1/2 x 4 1/2 x 2 £3-50 (28p)

QUARTZ HALOGEN BULBS 12v 55w 50p (5p)

Postage and package for each item shown in brackets.

KEYTRONICS


(Mail Order only)

44 EARLS COURT ROAD LONDON W8.

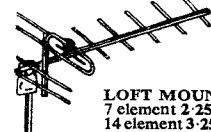01-478 8499

U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS
7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75.
WALL MOUNTING c/w WALL ARM & BRACKET
7 element 3-25. 11 element 3-75. 14 element 4-25. 18 element 4-75. **CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT.** 7 element 4-00. 11 element 4-50. 14 element 4-75. 18 element 5-25. **MAST MOUNTING** arrays only. 7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75. Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 9np yd. **KING TELEBOOSTERS** from 3-75. **LABGEAR** all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np C.W.O. Min. C.O.D. charge 25np.

BBC—ITV—FM AERIALS
BBC (band 1) Wall S/D 2-00. LOFT inverted 'T' 1-25. EXTERNAL 'H' array only 3-00. ITV (band 3) 5 element loft array 2-50. 7 element 3-00. **COMBINED BBC—ITV, loft 1+5 2-75. 1+7 3-50. WALL & CHIMNEY UNITS ALSO AVAILABLE.** Pre-amps from 3-75. **COMBINED U.H.F.—V.H.F. aerials** 1+5+9 4-00. 1+5+14 4-50. 1+7+14 5-00. **F.M. RADIO** loft S/D 1-00 3 element 3-25. 4 element 3-50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

CALLERS WELCOMED OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS

40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY
Telephone 01-648 4884

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-20	AD162	0-33	BC148	0-10	BD137	0-45	BF188	0-40	OC19	0-35	2G371	0-16	2N2219	0-20	2N3054	0-46	2N4059	0-10
AC113	0-20	AD181 & AD182	0-50	BC149	0-12	BD138	0-50	BF189	0-12	OC20	0-35	2G371B	0-12	2N2220	0-20	2N3055	0-50	2N4060	0-12
AC115	0-23	AD182 (MP)	0-50	BC150	0-16	BD139	0-55	BF190	0-12	OC21	0-35	2G373	0-17	2N2221	0-20	2N3056	0-14	2N4061	0-12
AC117K	0-20		0-50	BC151	0-20	BD140	0-60	BF191	0-14	OC22	0-38	2G373	0-17	2N2222	0-20	2N3057	0-16	2N4062	0-12
AC122	0-12	ADT140	0-50	BC152	0-17	BD155	0-60	BF197	0-14	OC24	0-56	2G377	0-30	2N2268	0-17	2N3092	0-14	2N4291	0-17
AC125	0-17	AF114	0-24	BC153	0-28	BD175	0-60	BF200	0-45	OC25	0-38	2G378	0-16	2N2369	0-14	2N3393	0-14	2N4285	0-17
AC126	0-17	AF115	0-24	BC154	0-30	BD176	0-60	BF222	0-95	OC26	0-25	2G381	0-16	2N2369A	0-14	2N3394	0-14	2N4286	0-17
AC127	0-17	AF116	0-24	BC157	0-18	BD177	0-65	BF257	0-45	OC28	0-50	2G382	0-16	2N2411	0-24	2N3395	0-17	2N4287	0-17
AC128	0-17	AF117	0-24	BC158	0-12	BD178	0-65	BF259	0-45	OC29	0-50	2G401	0-30	2N2412	0-24	2N3402	0-21	2N4288	0-17
AC132	0-14	AF118	0-25	BC159	0-12	BD179	0-70	BF262	0-55	OC36	0-50	2G414	0-30	2N2446	0-47	2N3403	0-21	2N4289	0-17
AC134	0-14	AF124	0-30	BC160	0-45	BD180	0-70	BF262	0-55	OC36	0-50	2G414	0-30	2N2446	0-47	2N3403	0-21	2N4289	0-17
AC137	0-14	AF125	0-25	BC161	0-50	BD185	0-65	BF263	0-55	OC41	0-20	2N388	0-35	2N2712	0-22	2N3404	0-28	2N4290	0-17
AC141	0-14	AF126	0-28	BC167	0-12	BD186	0-65	BF270	0-85	OC42	0-14	2N388A	0-55	2N2714	0-21	2N3414	0-15	2N4292	0-17
AC141K	0-17	AF127	0-28	BC168	0-12	BD187	0-70	BF271	0-85	OC44	0-15	2N404	0-20	2N2714	0-21	2N3414	0-15	2N4292	0-17
AC142	0-14	AF129	0-30	BC169	0-12	BD188	0-75	BF272	0-80	OC45	0-12	2N404A	0-28	2N2905	0-21	2N3416	0-28	2N5172	0-18
AC142K	0-17	AF178	0-50	BC170	0-12	BD189	0-75	BF273	0-35	OC70	0-10	2N524	0-42	2N2905A	0-21	2N3407	0-28	2N5458	0-32
AC151	0-15	AF179	0-50	BC171	0-14	BD190	0-75	BF274	0-35	OC71	0-10	2N527	0-49	2N2906	0-15	2N3408	0-09	2N5459	0-40
AC154	0-20	AF180	0-50	BC172	0-14	BD195	0-85	BFW10	0-60	OC72	0-14	2N598	0-43	2N2906A	0-18	2N3525	0-10	2S301	0-50
AC155	0-20	AF181	0-45	BC173	0-14	BD196	0-85	BFX29	0-27	OC74	0-12	2N599	0-45	2N2906A	0-18	2N3709	0-09	2S302A	0-42
AC156	0-20	AF186	0-45	BC174	0-14	BD197	0-80	BFX84	0-22	OC75	0-15	2N696	0-12	2N2907	0-20	2N3703	0-10	2S302A	0-42
AC157	0-24	AF189	0-37	BC175	0-22	BD198	0-80	BFK25	0-30	OC76	0-15	2N697	0-13	2N2907A	0-22	2N3704	0-11	2S302	0-42
AC158	0-20	AL102	0-65	BC176	0-19	BD199	0-85	BFK86	0-22	OC77	0-25	2N698	0-24	2N2926	0-14	2N3705	0-10	2S303	0-55
AC166	0-20	AL103	0-65	BC178	0-19	BD200	0-85	BFK87	0-24	OC81	0-15	2N699	0-25	2N2926	0-14	2N3706	0-09	2S304	0-70
AC167	0-20	AS126	0-25	BC179	0-19	BD205	0-80	BFK88	0-22	OC81D	0-15	2N708	0-09	2N2926 (G)	0-12	2N3707	0-11	2S305	0-84
AC168	0-24	AS127	0-30	BC180	0-24	BD206	0-80	BFY50	0-20	OC82	0-15	2N708A	0-09	2N2926 (G)	0-12	2N3707	0-11	2S305	0-84
AC169	0-14	AS128	0-25	BC181	0-24	BD207	0-95	BFY51	0-20	OC82D	0-15	2N708	0-12	2N2926 (Y)	0-12	2N3709	0-09	2S307	0-84
AC176	0-20	AS129	0-25	BC182	0-10	BD208	0-95	BFY52	0-20	OC83	0-20	2N711	0-30	2N2926 (Y)	0-11	2N3710	0-09	2S321	0-58
AC177	0-24	AS130	0-25	BC192L	0-10	BDY20	1-00	BFY53	0-17	OC84	0-20	2N717	0-35	2N2926 (O)	0-11	2N3711	0-09	2S322	0-42
AC178	0-28	AS151	0-25	BC193	0-10	BDY21	0-24	BFZ25	0-65	OC139	0-20	2N718	0-24	2N2926 (R)	0-10	2N3819	0-28	2S322A	0-42
AC179	0-28	AS152	0-25	BC193L	0-10	BF117	0-45	BRX19	0-15	OC140	0-20	2N718A	0-50	2N2926 (R)	0-10	2N3920	0-50	2S323	0-58
AC180	0-17	AS154	0-25	BC184	0-12	BF118	0-70	BSX20	0-15	OC169	0-25	2N726	0-28	2N2926 (B)	0-10	2N3923	0-28	2S325	0-70
AC180K	0-20	AS155	0-25	BC184L	0-12	BF119	0-70	BSY25	0-15	OC170	0-25	2N727	0-28	2N2926 (B)	0-10	2N3923	0-28	2S325	0-70
AC181	0-17	AS156	0-25	BC186	0-28	BF121	0-45	BSY26	0-15	OC171	0-25	2N743	0-20	2N2926 (B)	0-10	2N3904	0-28	2S327	0-70
AC181K	0-20	AS157	0-25	BC187	0-28	BF123	0-60	BSY27	0-15	OC200	0-25	2N744	0-20	2N3010	0-70	2N3905	0-28	2S701	0-42
AC187	0-20	AS158	0-25	BC192	0-10	BF125	0-50	BSY28	0-15	OC202	0-28	2N918	0-30	2N3051	0-14	2N3906	0-27	40361	0-40
AC187K	0-20	AS159	0-25	BC208	0-11	BF127	0-50	BSY29	0-15	OC202	0-28	2N918	0-30	2N3055	0-17	2N4058	0-12	40362	0-45
AC188	0-22	BC107	0-09	BC209	0-12	BF152	0-55	BSY38	0-18	OC203	0-25	2N929	0-21						
AC188K	0-22	BC108	0-09	BC212L	0-11	BF153	0-45	BSY39	0-18	OC204	0-25	2N930	0-21						
AC189	0-25	BC109	0-10	BC213L	0-11	BF154	0-45	BSY40	0-28	OC205	0-35	2N1131	0-20						
AC191	0-20	BC112	0-10	BC214L	0-14	BF155	0-70	BSY41	0-28	OC309	0-40	2N1132	0-22						
AC1919	0-20	AS159	0-25	BC225	0-25	BF156	0-45	BSY42	0-28	P36A	0-20	2N1302	0-14	AA119	0-08	BY133	0-21	OA10	0-35
AC1920	0-20	BC115	0-15	BC226	0-35	BF157	0-55	BSY43	0-28	BFY95A	0-12	PF09	0-43	AA120	0-08	BY164	0-50	OA47	0-07
AC1921	0-20	BC116	0-15	BC230	0-24	BF158	0-55	BSY44	0-28	OC207	0-43	2N1305	0-17	AA129	0-08	BYX38/30	0-50	OA70	0-07
AC1922	0-16	BC117	0-15	BCY31	0-26	BF159	0-60	BSY45	0-28	OC208	0-43	2N1306	0-21	AA130	0-08	BYX38/30	0-50	OA70	0-07
AC1927	0-18	BC118	0-10	BCY32	0-30	BF160	0-40	C400	0-50	ORP60	0-40	2N1307	0-21	AA131	0-08	BYZ10	0-35	OA81	0-07
AC1928	0-19	BC119	0-30	BCY33	0-22	BF162	0-40	C407	0-25	ORP61	0-40	2N1307	0-21	AA132	0-10	BYZ11	0-30	OA85	0-09
AC1929	0-35	BC120	0-30	BCY34	0-25	BF163	0-40	C424	0-20	RP140	0-12	2N1308	0-23	AA133	0-10	BYZ12	0-30	OA90	0-08
AC1930	0-20	BC121	0-12	BCY35	0-25	BF164	0-40	C425	0-50	RP141	0-17	2N1309	0-23	AA134	0-22	BYZ13	0-25	OA91	0-08
AC1931	0-28	BC122	0-18	BCY71	0-18	BF165	0-40	C426	0-35	TIS43	0-30	2N1813	0-20	AA135	0-14	BYZ16	0-40	LA45	0-07
AC1934	0-21	BC132	0-12	BCY72	0-14	BF167	0-22	C428	0-20	UT46	0-27	2N1711	0-20	AA136	0-12	BYZ17	0-35	OA200	0-06
AC1935	0-21	BC134	0-18	BCZ10	0-20	BF173	0-22	C441	0-30	2G301	0-09	2N1859	0-32	AA137	0-15	BYZ18	0-35	OA202	0-07
AC1936	0-28	BC135	0-12	BCZ11	0-25	BF176	0-25	C442	0-30	2G302	0-19	2N1890	0-45	AA138	0-14	BYZ19	0-35	OA202	0-07
AC1940	0-17	BC136	0-15	BCZ12	0-25	BF177	0-35	C444	0-35	2G303	0-19	2N1893	0-37	AA139	0-13	BYZ19	0-35	OA202	0-07
AC1941	0-18	BC137	0-15	BCZ13	0-30	BF178	0-30	C450	0-12	2G304	0-24	2N2147	0-72	AA140	0-15	CG62	0-28	SD19	0-05
AC1944	0-35	BC139	0-40	BD123	0-65	BF179	0-30	MAT100	0-10	2G306	0-40	2N2148	0-20	AA141	0-12	(Eg) OA91	0-28	IN34	0-07
AD130	0-38	BC140	0-30	BD124	0-60	BF180	0-30	MAT101	0-20	2G308	0-35	2N2160	0-60	AA142	0-17	CG63	0-05	IN34A	0-07
AD140	0-48	BC141	0-30	BD131	0-50	BF181	0-30	MAT120	0-19	2G309	0-35	2N2192	0-35	AA143	0-12	CG65	0-11	IN914	0-06
AD142	0-48	BC142	0-30	BD132	0-60	BF182	0-40	MAT121	0-20	2G339	0-20	2N2193	0-35	AA144	0-14	(Eg) OA70	0-28	IN916	0-06
AD143	0-38	BC143	0-30	BD133	0-65	BF183	0-40	MPP102	0-42	2C139A	0-16	2N2194	0-35	AA145	0-15	OA79	0-06	IN414B	0-06
AD148	0-35	BC145	0-45	BD135	0-40	BF184	0-35	MPP104	0-37	2G344	0-18	2N2217	0-22	AA146	0-15	OA8	0-35	IN821	0-10
AD161	0-33	BC147	0-10	BD136	0-40	BF185	0-25	MPP105	0-37	2G345	0-16	2N2218	0-22	AA147	0-16	OA6SL	0-21	IN851	0-08

DIODES AND RECTIFIERS

AA119	0-08	BY133	0-21	OA10	0-35
AA120	0-08	BY164	0-50	OA47	0-07
AA129	0-08	BYX38/30	0-50	OA70	0-07
AA130	0-08	BYX38/30	0-50	OA70	0-07
AA131	0-10	BYZ10	0-35	OA81	0-07
AA132	0-10	BYZ11	0-30	OA85	0-09
AA133	0-10	BYZ12	0-30	OA90	0-08
AA134	0-22	BYZ13	0-25	OA91	0-08
AA135	0-14	BYZ16	0-40	LA45	0-07
AA136	0-12	BYZ17	0-35	OA200	0-06
AA137	0-15				

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV 1A	3A	5A	5A	7A	10A	15A	30A
T05	T066	T066	T066	T048	T048	T048	T048
50	0-28	0-25	0-35	0-37	0-50	0-58	1-15
100	0-25	0-32	0-47	0-47	0-50	0-63	1-40
200	0-35	0-37	0-49	0-49	0-57	0-61	1-60
400	0-43	0-47	0-56	0-56	0-67	0-75	0-93
600	0-53	0-57	0-68	0-68	0-77	0-87	1-25
800	0-63	0-70	0-80	0-80	0-90	1-20	1-50

SIL. RECTS. TESTED

PIV 300mA	750mA	1A	1.5A	3A	10A	30A
50	0-04	0-05	0-05	0-07	0-14	0-21
100	0-04	0-06	0-03	0-13	0-16	0-23
200	0-05	0-09	0-06	0-14	0-20	0-24
400	0-06	0-18	0-07	0-20	0-27	0-37
600	0-07	0-18	0-10	0-20	0-34	0-46
800	0-10	0-17	0-11	0-25	0-37	0-55
1000	0-11	0-25	0-14	0-20	0-46	0-63
1200	—	0-33	—	0-38	0-57	0-75

TRIACS

VBOM 2A	6A	10A
TO-1	TO-66	TO-98
\$p	\$p	\$p
100	30	50
200	50	60
400	70	75

DIACS

FOR USE WITH TRIACS
BR100 (D32) 37p each

FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G398A 2N1902
T10	8 2G417 AP117

All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 25p each.

180 VOB MIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND 120, 1-24 17p each, TO-5 N.P.N.

Sil. trans. suitable for P.E. Organ Metal TO-18 Eqvt. ZTX300 5p each.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENT—OC29-28-29-30-35-35. NKT 401-403-404-405-406-430-451-452-453. TI3027-3028, 2N2504, 2N456A-457A-458A, 2N511 A & B. 2G290-292, ETC. VCEO 80V VCEO 50V IC 10A FT. 30 WATTS Hfe 30-170. PRICE 1-24 49p each 25-99 100p each 50p 25p

SILICON High Voltage 250V NPN TO-3 case. G.F. Switching & Amplifier Applications. Brand new Coded R 2400 VCEO 250V/VCEO 100/IC 6A/30 WATTS. HFE type 20/IT 5MHZ. OUR PRICE EACH: 1-24 50p 25-99 100p each 50p

AD161/162 PNP M/P COMP GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 13p ea. 11W (Top-Hat) 13p ea. 10W (SO-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 90p each

NEW LINE

Plastic Encapsulated 2 Amp. BRIDGE RECTS. 50 v RMS 32p each 100 v RMS 37p each 400 v RMS 49p each Size 15 mm x 6 mm.

UNIJUNCTION

UT46. Eqvt. 2N2646. Eqvt. TI848. BEN3000 27p each, 25-99 25p 100 UP 20p.

CADMIUM CELLS

ORP12 48p ORP60, ORP61 40p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N706/8. BSY-2728/85A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	3p
50	For	9.00
100	For	1-00
500	For	1-75
1000	For	7-50
1000	For	13.00

SIL. G.P. DIODES 5p

300mW 30. 0-50 40PIV(Min.) 100. 1-50 Sub-Min. 500. 5-00 Full Tested 1,000. 9-00 Ideal for Organ Builders.

NEW EDITION 1971

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 80p each.

2N3055 115 WATT SIL POWER NPN 50p EACH

SILICON 50 WATTS MATCHED NPN/PNP BIP 19N NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCEO 100V/VCEO 50/IC 10A. HFE type 100/IT 3mHZ. OUR PRICE PER PAIR: 1-24 prs. 60p 25-99 prs. 55p 100 prs. 50p

KEY OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-50
U 2	60 Mixed Germanium Transistors AF/RP	0-50
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-50
U 4	40 Germanium Transistors like OC81, AC128	0-50
U 5	60 300mA Sub-Min. Silicon Diodes	0-50
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0-50
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000-50	0-50
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-50
U 9	20 Mixed Voltage, 1 Watt Zener Diodes	0-50
U10	20 BA50 charge storage Diodes DO-7 Glass	0-50
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-50
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-50
U13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0-50
U14	150 Mixed Silicon and Germanium Diodes	0-50
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-50
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-50
U17	30 Germanium PNP AF Transistors TO-5 like ACV 17-22	0-50
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-50
U19	25 Silicon NPN Transistors like BC108	0-50
U20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-50
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-50
U23	30 MADT's like MHz Series PNP Transistors	0-50
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-50
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0-50
U26	80 Fast Switching Silicon Diodes like 1N914 Micro-Min.	0-50
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0-50
U29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR1/25-600	1-00
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0-50
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-50
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-50
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-50
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 9S302/4	0-50
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-50
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-50
U37	30 Silicon Alloy Transistors 80-2 PNF OC200, 2S222	0-50
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-50
U39	30 RF. Germ. PNP Transistors 2N1309/3 TO-5	0-50
U40	10 Dual Transistors 6 lead TO-5 2N2060	0-50
U41	25 RF Germanium Transistors TO-5, OC45, NKT72	0-50
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0-50
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-50
U44	20 Sil. Trans. Plastic TO-6 BC115/NPN	0-50
U45	7 3A SCR. TO66 up to 600PIV	1-00

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to RP X-25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

F.E.T.'S 2N3819 35p 2N5458 50p 2N3820 50p 2N6459 40p 2N3821 35p BFW10 40p 2N3823 30p MPF105 40p

NEW EDITION 1971

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 80p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

SILICON 50 WATTS MATCHED NPN/PNP BIP 19N NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCEO 100V/VCEO 50/IC 10A. HFE type 100/IT 3mHZ. OUR PRICE PER PAIR: 1-24 prs. 60p 25-99 prs. 55p 100 prs. 50p

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0-50
Q2	18 White spot R.F. transistors PNP	0-50
Q3	4 OC 77 type transistors	0-50
Q4	6 Matched transistors OC44/45/81/81D	0-50
Q5	4 OC 75 transistors	0-50
Q6	5 OC 72 transistors	0-50
Q7	4 AC 128 transistors PNP high gain	0-50
Q8	4 AC 126 transistors PNP	0-50
Q9	7 OC 81 type transistors	0-50
Q10	7 OC 71 type transistors	0-50
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-50
Q12	3 AF 116 type transistors	0-50
Q13	3 AF 117 type transistors	0-50
Q14	3 OC 171 H.F. type transistors	0-50
Q15	7 2N2925 Sil. Epoxy transistors mixed colours	0-50
Q16	2 GBT880 low noise Germanium transistors	0-50
Q17	5 NPN 2 x ST.141 & 3 x ST.140	0-50
Q18	4 MADT'S 2 x MAT 100 & 1 x MAT 120	0-50
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-50
Q20	4 OC 44 Germanium transistors A.F.	0-50
Q21	4 AC 127 NPN Germanium transistors	0-50
Q22	20 NKT transistors A.F. R.F. coded	0-50
Q23	10 OA 202 Silicon diodes sub-min.	0-50
Q24	8 OA 81 diodes	0-50
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0-50
Q26	8 OA95 Germanium diodes sub-min IN69	0-50
Q27	2 10A PIV Silicon rectifiers IS42R	0-50
Q28	2 Silicon power rectifiers B Y Z 13	0-50
Q29	4 Silicon transistors 2N 2N696, 1 x 2N697, 1 x 2N698	0-50
Q30	7 Silicon switch transistors 2N706 NPN	0-50
Q31	6 Silicon switch transistors 2N708 NPN	0-50
Q32	3 PNP Silicon transistors 2N 2N1131, 1 x 2N1132	0-50
Q33	3 Silicon NPN transistors 2N1711	0-50
Q34	7 Silicon NPN transistors 2N2369, 800mHz (code P397)	0-50
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0-50
Q36	7 2N3645 TO-18 plastic 300 MHz NPN	0-50
Q37	3 2N3053 NPN Silicon transistors	0-50
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0-50

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and 'e' Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2 cm x 4cm. Complete with case and instructions. Price each: 23-35

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Out" which include Functional and Part-Functional Units. These are classed as "cut-off" products as they rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0-50	UIC46	= 5 x 7446	0-50	UIC86	= 5 x 7486	0-50
UIC01	= 12 x 7401	0-50	UIC47	= 5 x 7447	0-50	UIC87	= 5 x 7487	0-50
UIC02	= 12 x 7402	0-50	UIC48	= 5 x 7448	0-50	UIC88	= 5 x 7488	0-50
UIC03	= 12 x 7403	0-50	UIC49	= 5 x 7449	0-50	UIC89	= 5 x 7489	0-50
UIC04	= 12 x 7404	0-50	UIC50	= 12 x 7450	0-50	UIC90	= 5 x 7490	0-50
UIC05	= 12 x 7405	0-50	UIC51	= 12 x 7451	0-50	UIC91	= 5 x 7491	0-50
UIC06	= 8 x 7406	0-50	UIC52	= 12 x 7452	0-50	UIC92	= 5 x 7492	0-50
UIC07	= 8 x 7407	0-50	UIC53	= 12 x 7453	0-50	UIC93	= 5 x 7493	0-50
UIC08	= 12 x 7410	0-50	UIC54	= 12 x 7454	0-50	UIC94	= 5 x 7494	0-50
UIC09	= 12 x 7411	0-50	UIC55	= 12 x 7455	0-50	UIC95	= 5 x 7495	0-50
UIC10	= 12 x 7412	0-50	UIC56	= 12 x 7456	0-50	UIC96	= 5 x 7496	0-50
UIC11	= 8 x 7413	0-50	UIC57	= 8 x 7472	0-50	UIC100	= 5 x 74100	0-50
UIC12	= 12 x 7450	0-50	UIC58	= 8 x 7473	0-50	UIC121	= 5 x 74121	0-50
UIC13	= 12 x 7450	0-50	UIC59	= 8 x 7474	0-50	UIC141	= 8 x 74141	0-50
UIC14	= 12 x 7440	0-50	UIC60	= 8 x 7475	0-50	UIC141	= 8 x 74151	0-50
UIC15	= 12 x 7440	0-50	UIC61	= 8 x 7476	0-50	UIC154	= 6 x 74154	0-50
UIC16	= 5 x 7441	0-50	UIC62	= 8 x 7476	0-50	UIC193	= 6 x 74193	0-50
UIC17	= 5 x 7442	0-50	UIC63	= 5 x 7480	0-50	UIC199	= 6 x 74199	0-50
UIC18	= 5 x 7443	0-50	UIC64	= 5 x 7481	0-50	UICIXI	= 25 Assorted	74's 1-50
UIC19	= 5 x 7444	0-50	UIC65	= 5 x 7482	0-50			

-the lowest prices!

74 Series T.T.L. I.C.'s



BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

1		25		100+		1		25		100+	
SN7400	0-15	0-14	0-12	SN7450	0-15	0-14	0-12	SN74129	£2.00	£2.70	£2.80
SN7401	0-15	0-14	0-12	SN7451	0-15	0-14	0-12	SN74141	0-67	0-64	0-58
SN7402	0-15	0-14	0-12	SN7453	0-15	0-14	0-12	SN74145	£1.50	£1.40	£1.30
SN7403	0-15	0-14	0-12	SN7454	0-15	0-14	0-12	SN74160	£3.00	£2.70	£2.50
SN7404	0-15	0-14	0-12	SN7460	0-15	0-14	0-12	SN74151	£1.00	0-95	0-90
SN7405	0-15	0-14	0-12	SN7470	0-29	0-28	0-24	SN74153	£1.20	£1.10	0-95
SN7406	0-35	0-31	0-28	SN7472	0-37	0-35	0-24	SN74154	£1.80	£1.70	£1.60
SN7407	0-35	0-31	0-28	SN7473	0-37	0-35	0-32	SN74155	£1.40	£1.30	£1.20
SN7408	0-18	0-17	0-16	SN7474	0-37	0-35	0-32	SN74156	£1.40	£1.30	£1.20
SN7409	0-18	0-17	0-16	SN7475	0-45	0-43	0-42	SN74167	£1.90	£1.80	£1.70
SN7410	0-15	0-14	0-12	SN7476	0-40	0-39	0-38	SN74160	£1.80	£1.70	£1.60
SN7411	0-25	0-24	0-23	SN7480	0-67	0-64	0-53	SN74161	£1.80	£1.70	£1.60
SN7412	0-35	0-31	0-28	SN7481	£1.20	£1.15	£1.10	SN74162	£4.00	£3.75	£3.50
SN7413	0-29	0-26	0-24	SN7482	0-37	0-35	0-24	SN74163	£4.00	£3.75	£3.50
SN7416	0-43	0-40	0-38	SN7483	£1.10	£1.05	0-95	SN74164	£2.20	£2.15	£2.10
SN7417	0-43	0-40	0-38	SN7484	£1.00	0-95	0-90	SN74165	£2.25	£2.20	£2.15
SN7420	0-15	0-14	0-12	SN7486	£3.60	£3.50	£3.40	SN74166	£3.25	£3.25	£3.20
SN7422	0-50	0-48	0-45	SN7486	0-32	0-31	0-30	SN74174	£2.30	£2.20	£2.10
SN7423	0-50	0-48	0-45	SN7489	£5.50	£5.25	£5.00	SN74175	£1.60	£1.50	£1.40
SN7425	0-50	0-48	0-45	SN7490	0-37	0-34	0-58	SN74176	£2.50	£2.40	£2.30
SN7427	0-45	0-42	0-40	SN7492	£1.00	0-95	0-90	SN74177	£2.50	£2.40	£2.30
SN7428	0-70	0-65	0-60	SN7492	0-67	0-64	0-58	SN74180	£2.00	£1.90	£1.80
SN7430	0-15	0-14	0-12	SN7493	0-67	0-64	0-58	SN74181	£5.50	£5.00	£4.75
SN7432	0-45	0-42	0-40	SN7494	0-77	0-74	0-68	SN74182	£2.00	£1.90	£1.80
SN7433	0-80	0-75	0-70	SN7495	0-77	0-74	0-68	SN74184	£3.50	£3.25	£3.00
SN7437	0-64	0-62	0-60	SN7496	0-37	0-34	0-78	SN74190	£1.95	£1.90	£1.85
SN7438	0-64	0-62	0-60	SN74100	£1.68	£1.60	£1.55	SN74191	£1.90	£1.85	£1.80
SN7440	0-15	0-14	0-12	SN74104	0-97	0-94	0-88	SN74192	£1.95	£1.90	£1.85
SN7441	0-67	0-64	0-58	SN74105	0-97	0-94	0-88	SN74193	£2.00	£1.90	£1.80
SN7442	0-67	0-64	0-58	SN74107	0-40	0-38	0-36	SN74194	£2.70	£2.60	£2.50
SN7443	£1.80	£1.25	£1.20	SN74110	0-55	0-53	0-50	SN74195	£2.00	£1.90	£1.80
SN7444	£1.30	£1.25	£1.20	SN74111	£1.25	£1.15	£1.10	SN74196	£1.90	£1.70	£1.60
SN7445	£1.30	£1.25	£1.20	SN74112	£1.00	0-95	0-90	SN74197	£1.90	£1.70	£1.60
SN7448	0-97	0-94	0-88	SN74119	£1.35	£1.25	£1.10	SN74198	£2.50	£2.40	£2.30
SN7447	£1.00	0-97	0-95	SN74121	0-40	0-37	0-34	SN74198	£2.50	£2.40	£2.30
SN7448	£1.00	0-97	0-95	SN74122	£1.40	£1.30	£1.10	SN74199	£2.50	£2.40	£2.30

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	Price	1-24	25-99	100 up
BP990	12p	12p	11p	10p
BP992	12p	12p	12p	11p
BP993	12p	12p	12p	11p
BP995	12p	12p	12p	11p
BP996	12p	12p	12p	11p
BP944	12p	12p	12p	11p
BP945	25p	24p	22p	20p
BP946	25p	24p	22p	20p
BP948	12p	11p	10p	9p
BP951	65p	60p	55p	50p
BP962	12p	11p	10p	9p
BP9933	40p	38p	35p	32p
BP9094	40p	38p	35p	32p
BP9097	40p	38p	35p	32p
BP9099	40p	38p	35p	32p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

LINEAR I.C.'s—FULL SPEC.

Type No.	Price	1-24	25-99	100 up
BP 201C—SL201C	63p	53p	45p	40p
BP701C—SL701C	63p	50p	45p	40p
BP 702C—SL702C	63p	50p	45p	40p
BP 709—72709	53p	45p	40p	35p
BP709—72709	36p	34p	30p	28p
BP 709P—LA709C	36p	34p	30p	28p
BP 710—72710	44p	42p	40p	38p
BP 711—LA711	45p	43p	40p	38p
BP 741—72741	75p	60p	50p	45p
LA709C—LA709C	29p	26p	24p	22p
TAA 263—	70p	60p	55p	50p
TAA 293—	80p	75p	70p	65p
TAA 350—	170p	153p	150p	140p

S.G.S. EA1000 2-63

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each	1-24	25-99	100 up
Epoxy TO-5 case				
uL800 Buffer	35p	33p	27p	
uL914 Dual 21/p gate	35p	33p	27p	
uL923 J-K flip-flop	50p	47p	45p	

Date and Circuits Booklet for IC's Price 7p.

DUAL IN LINE SOCKETS.

14 & 16 Lead Sockets for use with

DUAL-IN-LINE I.C.'s. TWO RANGES PROFESSIONAL & NEW LOW COST. PROF. TYPE No. 1-24 25-99 100up. TSO 14 pin type. 30p 27p 25p TSO 16 " " 35p 32p 30p

LOW COST No.

BPS 14	15p	13p	11p
BPS 16	16p	14p	12p

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than 1% at 1KHz.


★ Signal to noise ratio 80dB.

ONLY **£3.25p** each

★ Supply voltage 10-35 Volts.

★ Overall size 63mm x 105mm x 13mm.

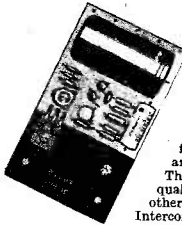Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT—TESTED—GUARANTEED.



STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer M780, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Discos Systems, Public Address, Intercom Units, etc. Handbook available, 10p PRICE £2.95

TRANSFORMER BMT80 £1-95 p. & p. 25p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz - 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs : 1. Tape Head	1-25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1-5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters : Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than - 65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

ONLY £11-95
SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23-00 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail.

Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

CHASSIS and CASES by



H. L. SMITH & CO LTD
 287/9 Edgware Road
 London W2 1BE
 Telephone: 01-723 5891

BLANK CHASSIS


FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	34p	17p	10x8x2½"	66p	30p
7x4x1½"	33p	18p	12x7x2½"	66p	33p
7x5x2"	40p	19p	12x9x2½"	76p	38p
8x4x2"	38p	19p	13x8x2½"	76p	38p
8½x5½x2"	44p	21p	14x7x2½"	80p	36p
9x7x2"	50p	26p	14x10x2½"	85p	47p
10x4x2½"	50p	21p	15x10x2½"	92p	50p
12x4x2½"	55p	22p	17x10x3"	£1 10	55p
12x5x3"	66p	26p			

CASES

ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8x6x2"	£1 00	W	12x7x7"	£2 50
N	6x6x3"	£1 05	W	15x9x8"	£3 15
N	4x4x2"	80p	Y	8x6x6"	£2 25
U	4x4x4"	95p	Y	12x7x7"	£2 80
U	5½x4½x4½"	£1 15	Y	13x7x9"	£3 15
U	8x6x6"	£1 45	Y	15x9x7"	£3 35
U	9½x7½x3½"	£1 55	Z	17x10x9"	£4 15
U	15x9x9"	£3 00	Z	19x10x8½"	£4 35
W	8x6x6"	£1 90			

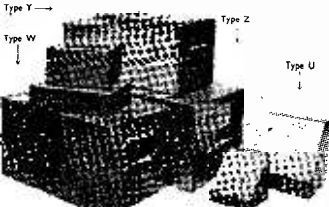

Type N has removable bottom. Type U removable bottom or back. Type W removable front. Type Y all screwed construction. Type Z removable back and front. Plus p & p.

TO FIT OUR CASES

7x5½x1½"	38p	21p	12x6x2½"	60p	33p
7x5½x2"	43p	21p	14x8x2½"	74p	44p
11x6x1½"	48p	30p	15½x9x2½"	94p	52p
11x6x2"	55p	30p	17½x9x2½"	£1 05	59p

PANELS: Any size up to 3ft. at 36p sq. ft. 16 s.w.g. (18 s.w.g. £12p) Plus postage and packing

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
 THE VALVE SPECIALISTS Telephone 6743

0A2	30	5BR7	79	6QT7M	43	12S07	50	85A3	40	EB34	20	EL37	74	PC88	44	PY80	33	AC156	20	BCY33	20	OA81	09
0B2	30	6BR8	63	9RT7G	35	14H7	48	90C1	59	EB91	10	EL41	53	PC95	53	PY81	24	UC50	40	BCY34	23	OA85	09
0Z4	25	6BR7	125	6RT7M	55	14S7	75	90C6	170	EB44	48	EL81	50	PC97	38	PY82	23	U403	33	BCY35	23	OA90	13
1A8	23	6BRW6	725	6SA7CT	35	19A95	24	150B2	58	EB81	29	EL83	35	PC90	29	PY83	26	U404	38	BCY39	25	OA91	09
1A7CT	32	6BRW7	50	6SA7CT	35	19A95	24	150B2	58	EB81	29	EL83	35	PC90	29	PY83	26	U404	38	BCZ11	38	OA95	09
1B3GT	33	6BRZ1	31	6SO7T	33	20D4	105	5702	80	EBF80	30	EL84	21	PC84	27	PY84	31	U405	38	BCY42	15	OA99	09
1B5GT	33	6C8BA	26	6SM7CT	33	20F2	65	5763	50	EBF83	38	EL85	40	PC85	24	PY85	35	U4020	38	BCY43	20	OC29	38
1L4	13	6C4	78	6SH7	35	20L1	98	7475	70	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY44	20	OC32	38
155GT	37	6C9	78	6SH7	35	20P1	50	AC/PEN	98	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY45	20	OC34	38
1J5	26	6CDDG	106	6SK7CT	33	20P2	76	AC/PEN	98	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY46	20	OC35	38
1K4	22	6CQTA	50	6SQ7CT	33	20P4	69	AC/PEN	98	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY47	20	OC36	38
1L4	22	6CH6	38	6U7CT	30	20P5	145	AC/PEN	98	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY48	20	OC37	38
1L6	48	6CL6	45	6VG6	27	25A6G	29	AC/TH1	50	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY49	20	OC38	38
2021	35	6CM7	50	6V6GT	27	25L6G	20	AC/TP	98	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY50	20	OC39	38
20K3	50	6CU3	30	6X4	20	25Y54	43	AL60	78	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY51	20	OC40	38
3A4	25	6CW4	63	6X5GT	28	25Z4G	28	ATP4	12	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY52	20	OC41	38
3D6	18	6DE7	50	7B6	58	25Z5	40	AZ1	40	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY53	20	OC42	38
3Q4	38	6DF8A	50	7B7	32	25Z6G	48	AZ31	46	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY54	20	OC43	38
3Q6GT	35	6DFW6	35	7H7	28	30A5	44	AZ41	53	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY55	20	OC44	38
3K4	23	6E5	55	7R7	65	30C15	55	CL33	50	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY56	20	OC45	38
4CB6	50	6F1	59	7Y4	60	30C17	74	CV63	58	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY57	20	OC46	38
5C3H	50	6F6	63	7Z4	50	30C18	58	CY1C	53	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY58	20	OC47	38
5T4	30	6F13	33	9BW6	50	30F5	61	CY31	39	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY59	20	OC48	38
5T4G	30	6F14	40	9D7	78	30FL1	58	DAF91	20	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY60	20	OC49	38
5T4G	30	6F15	45	10C2	49	30FL2	58	DAF96	33	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY61	20	OC50	38
5Y3CT	35	6P23	65	10D7	50	30FL12	67	DP91	14	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY62	20	OC51	38
5Z4T	38	6P24	68	10F1	75	30FL13	47	DP96	34	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY63	20	OC52	38
5Z4GT	38	6P25	51	10F9	45	30FL14	66	DP96	28	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY64	20	OC53	38
5Z6L2	53	6P28	60	10F18	35	30L15	55	DK40	55	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY65	20	OC54	38
5A8G	33	6P29	15	10L11	53	30L17	65	DK92	33	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY66	20	OC55	38
5A8G	33	6P18	45	10C2	49	30L12	58	DAF96	33	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY67	20	OC56	38
5Y3CT	35	6P23	65	10D7	50	30FL12	67	DP91	14	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY68	20	OC57	38
5Z4T	38	6P24	68	10F1	75	30FL13	47	DP96	34	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY69	20	OC58	38
5Z4GT	38	6P25	51	10F9	45	30FL14	66	DP96	28	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY70	20	OC59	38
5Z6L2	53	6P28	60	10F18	35	30L15	55	DK40	55	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY71	20	OC60	38
5A8G	33	6P29	15	10L11	53	30L17	65	DK92	33	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY72	20	OC61	38
5A8G	33	6P18	45	10C2	49	30L12	58	DAF96	33	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY73	20	OC62	38
5Y3CT	35	6P23	65	10D7	50	30FL12	67	DP91	14	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY74	20	OC63	38
5Z4T	38	6P24	68	10F1	75	30FL13	47	DP96	34	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY75	20	OC64	38
5Z4GT	38	6P25	51	10F9	45	30FL14	66	DP96	28	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY76	20	OC65	38
5Z6L2	53	6P28	60	10F18	35	30L15	55	DK40	55	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY77	20	OC66	38
5A8G	33	6P29	15	10L11	53	30L17	65	DK92	33	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY78	20	OC67	38
5A8G	33	6P18	45	10C2	49	30L12	58	DAF96	33	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY79	20	OC68	38
5Y3CT	35	6P23	65	10D7	50	30FL12	67	DP91	14	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY80	20	OC69	38
5Z4T	38	6P24	68	10F1	75	30FL13	47	DP96	34	EBL21	60	EL91	23	PC89	31	PY86	31	U410	38	BCY81	20	OC70	38
5Z4GT	38	6P25	51	10F9	45	30FL14	66	DP96	28	EBL21	60												

**MANUFACTURERS OF
ELECTRONIC AND AMPLIFICATION
EQUIPMENT**

TUAC

**TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD**
163 MITCHAM ROAD, LONDON SW17
01-672 3137-9080

SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT, PRESENT AN OUTSTANDING RANGE OF KITS FOR THE ELECTRONICS AND AUDIO ENTHUSIAST ALIKE

PRE-AMPLIFIERS Carr. 20p.

VA06 — Vol., Treble & Bass Controls.
£3.09 Treble +22dB -15dB @ 12KHz.
Bass ±18dB @ 40Hz. Ref. 1KHz.
Sensitivity 8mV for 30mV O/P.

VA08 — Vol., Treble, Middle & Bass.
£3.96 Treble +28dB @ 18KHz.
Middle +20 -15dB @ 4KHz.
Bass +20 -10dB @ 40Hz.
Sensitivity 4mV for 30mV O/P.

SVA01 — Vol., Treble, Middle, Bass & Balance.
£6.80 As VA08 but for Stereo.

MVA01 — Two separate Input Channels. Vol. &
£2.90 Tone Control on each input.
Tone Control +25dB @ 12KHz to
+20dB @ 40Hz. Sensitivity 2mV.

MEVA01 — Magnetic Cartridge Equalisation. Connects
to input of VA06 or VA08.
£2.10 Voltage gain 15 times. With vol. control.

SIPAM — Master Volume and Presence Control.
£1.90 High treble boost of +15dB @ 15KHz.
Unity voltage gain when feeding Tuac
Power Modules.

EFVA01 — Increases the output of any of the
£1.90 above to 1 Volt R.M.S. Low impedance
emitter follower output.

POWER AMPLIFIER MODULES



All TUAC Power Modules are constructed on glass fibre P.C. board and each circuit incorporates a robust driver transformer stage (except TP25W) with thermal overload protection on the output stage.

ALL OUTPUT POWER RATINGS ARE R.M.S. CONTINUOUS SINE WAVE ±0.5dB USING SPECIFIED SUPPLY.

TP 100W (illus.) 170W r.m.s. sq. wave into 8Ω.
£14.28 PS 100 Supply £9.66. Carr. 50p
Carr. 45p PS 100/100 Supply £16.00. Carr. 65p

TP 50W 90W r.m.s. sq. wave into 8Ω.
£9.31 PS 50 Supply £6.12. Carr. 50p
Carr. 40p PS 50/50 Supply £9.68. Carr. 65p

TP 25W 40W r.m.s. sq. wave into 4Ω.
£7.25 PS 25 Supply £3.95. Carr. 40p
Carr. 40p PS 25/25 Supply £7.35. Carr. 55p

BRIEF TECHNICAL SPECIFICATION
Full Power Response: 10Hz—20KHz ±2dB.
Input Sensitivity: 30mV r.m.s. into 3KΩ.
Hum & Noise: Better than -70dB.
External Heatsink required.

LIGHT MODULATORS



These exceptional units are constructed on glass fibre P.C. board. Triacs are used giving full wave control. Operating sensitivity only 1 Watt! Full interference suppression.

S1LMB — 3 separate 1000 Watt channels. Master
£15.50 sensitivity. Individual Bass, Middle &
Carr. 35p Treble Controls. Isolated input transformer.
(illus.) does not affect amplifier operation.

S2LMB — Single channel with increased capacity
£3.25 of 1800 Watts. Master sensitivity control.
Carr. 25p Isolating input transformer does
not affect amplifier operation.

TUAC AMPLIFICATION



100 WATT General
Purpose Amplifier
complete... £35.00

50 WATT Version
£37.50

100 WATT Slave
£45.00

Suitable for Guitar, Disco, P.A., Organ, etc.
Carr. 75p.

ALL TUAC KITS SUPPLIED WITH FULL EASY TO FOLLOW WIRING INSTRUCTIONS INCLUDING CIRCUIT DIAGRAM AND COMPLETE COMPONENT COMPLEMENT

TUAC

S.A.E. WITH ALL ENQUIRIES. PLEASE CALL, WRITE OR PHONE FOR FULL DETAILS OF ABOVE AND OTHER PRODUCTS NOT LISTED

ALL TUAC EQUIPMENT CARRIES A 12 MONTH GUARANTEE

TRADE AND EXPORT ENQUIRIES WELCOME

**NEW
LOW
PRICES**

RADNOR SUPPLIES

23 ARBURY RD.
NUNEATON
TEL.
5174

PLUGS AND SOCKETS

Speaker Plugs 6p	Sockets 6p
5 Pin Din 180° 10p	Sockets 8p
5 Pin 240° 10p	Sockets 8p
Standard Jack 10p	Sockets 10p

SEMICONDUCTORS

AC128 15p	BC107 10p	2N3702 12p
AC176 15p	BC108 10p	OA91 7p
AD161 30p	BC109 10p	BY100 15p
AD162 30p	BC113 10p	IN914 6p
AF115 20p	BC148 10p	IN4001 6p
AF116 20p	BF195 15p	IN4007 12p
AF117 20p	2N2926g 10p	ORP12 50p
	2N3055 50p	

RESISTORS

½w. 1% & ½w. E12 Series 1p, 10+, 9p, 100+, 7p.

POTENTIOMETERS

5kΩ to 2MΩ Carbon Track, Log or Lin, Single 12p, D.P.S.W. 24p.

SKELETON PRESETS

Lin. 100Ω to 5MΩ Horizontal or Vertical. Sub. Min. 5p.

SLIDER PRESETS

3k, 10k, 100k, 250k, 500k, 1m, 2.2m 9p.

CABLES

Mains Lead	White	Twin	6p yd.
	White	3 Core	8p yd.
Screened	Single	Grey	5p yd.
	Twin	Grey	7p yd.
	Stereo	Ivory	8p yd.

CAPACITORS

Electrolytic R.S. P.C. Type.
0.47/63, 1/63, 2.2/63, 4.7/40,
10/63, 22/40, 100/10, 7p each.
47/40, 10p. 100/63, 220/40,
470/16, 13p. 1000/16, 16p.

TRIMMERS	40pF	9p
	140pF	10p
	250pF	13p
	500pF	16p

SLIDERSWITCHES, D.P.D.T.

Sub. Min., Length 23mm. 11p
Miniature, Length 34mm. 11p

WAVECHANGE SWITCHES

1p	4w	3p	3w
1p	12w	3p	4w
2p	2w	4p	2w
2p	4w	4p	3w
2p	6w		

TERMS OF BUSINESS: —

Cash with Order only. Make P.O.s/Cheques payable Radnor Supplies.

Please include 10p P.P.

S.A.E. all enquiries.

This List cancels all previous issues. Send 10p for complete list containing many more components.



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

**BRITISH NATIONAL RADIO &
ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

WB23
BLOCK CAPS please

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	33p
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	36p
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	36p
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	36p
Rod Aerial	RA2W		72p
Driver Transformer	LFDT4/1		58p
Output Transformer	OPT1		58p
Printed Circuit	PCA1		58p

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	39p
T41/2E	2nd I.F. Transformer	39p
T41/3T	3rd I.F. Transformer	57p
T41/3T	B.F.O. Coil	57p

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt £3.20. Kit Form £2.70
300 Watt—£2.70. Kit Form £2.20

All plus 10p post and packing.
Please send C.W.O. to:--

DEXTER & COMPANY
2 ULVER HOUSE, 19 KING STREET,
CHESTER CH1 2AH Tel: 0244-25883

As supplied to H.M. Government Departments.

TRANSFORMERS

DOUGLAS GUARANTEED

12 or 24 volts		Price P. & P.
Output V. & Amps.	Ref. No.	
12V x 2 250 mA x 2	MT111 CS**	20-91 9p
12V x 2 500 mA x 2	MT213 CT**	20-97 10p
12V x 2 1A x 2	MT 71 AT**	21-88 24p
12V x 2 2A x 2	MT 18 AT	22-06 30p
12V x 2 3A x 2	MT 70 AT	22-69 32p
12V x 2 4A x 2	MT 108 AT	22-92 34p
12V x 2 5A x 2	MT 72 AT	23-33 42p
30 volts. All tapped at 0-12-15-20-24-30V		
Out-put	Ref. No.	Price P.P. Out-Ref. No. Price P.P
Amps.	£	Amps. £
500 mA MT 112 CT*	1-12 16p	3A MT 20 AT 2-64 32p
1A MT 79 AT*	1-55 29p	4A MT 21 AT 3-10 40p
2A MT 3 AT	2-22 30p	5A MT 51 AT 4-31 42p
50 volts. All tapped at 0-19-25-33-40-50V.		
500 mA MT 102 AT*	1-45 24p	3A MT 105 AT 3-91 41p
1A MT 103 AT	2-00 32p	4A MT 106 AT 5-06 41p
2A MT 104 AT	3-10 32p	6A MT 107 AT 7-47 50p
60 Volts. All tapped at 0-24-30-40-48-60V.		
500 mA MT 124 AT*	1-46 30p	2A MT 127 AT 3-16 41p
1A MT 126 AT	2-24 32p	3A MT 128 AT 4-69 41p

AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 113 CT	20-89 14p
75 VA	"	MT 64 AT	21-72 30p
150 VA	0-115-200-220-240	MT 4 AT	22-15 32p
300 VA	"	MT 65 AT	23-00 32p
400 V. Output at 50 HZ. Ref. IT3 AT			
C.D. Ignition system by R. M. Marston			22-90 29p
Eq.			

EQUIPMENT RANGE


Sec. Output (r.m.s.)	Ref. No.	Price P. & P.
3-0-3 V.	200 mA MT 238 CS**	20-89 8p
9-0-9 V.	100 mA MT 13 CS**	20-81 8p
12-0-12	50 mA MT 239 CS**	20-91 8p
20-0-20	30 mA MT 241 CS**	20-91 8p
0-20 x 2	300 mA x 2 MT 214 CT**	21-21 16p
0-9-9 x 2	500 mA x 2 MT 207 CT**	21-46 19p
0-15-20 x 2	500 mA x 2 MT 205 AT**	22-12 29p
0-15-27 x 2	500 mA x 2 MT 203 AT*	22-45 29p
0-15-27 x 2	1A x 2 MT 204 AT*	23-42 30p
10-12-0-12-20	700 mA (d.c.) MT 221 AT*	21-11 20p

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. spills; *with interwinding screen; † untapped 240V Primary; ‡ Primary tapped at 210-240V. other Primaries tapped at 200-220-240V.
Over 200 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD.
(Dept. MO10FW), Thames St., LOUTH, Lincs. LN11 7AD

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

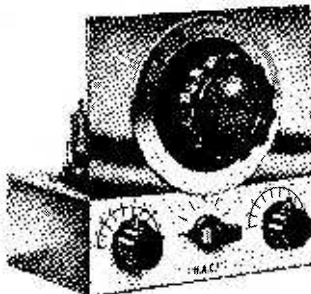

Famous for over 35 years for Short-Wave Reception of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER

Complete kit—price £3.80 (post & packing 20p). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

HENRY'S - Your complete Semi-Conductor Store!

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIRCHILD




Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
SN7400	0-20	0-18	0-16	SN7450	0-20	0-18	0-16	SN74145	1-50	1-40	1-30
SN7401	0-20	0-18	0-16	SN7451	0-20	0-18	0-16	SN74150	3-25	2-25	2-15
SN7402	0-20	0-18	0-16	SN7453	0-20	0-18	0-16	SN74151	1-10	0-95	0-90
SN7403	0-20	0-18	0-16	SN7454	0-20	0-18	0-16	SN74153	1-35	1-27	1-20
SN7404	0-20	0-18	0-16	SN7460	0-20	0-18	0-16	SN74154	2-00	1-75	1-55
SN7405	0-20	0-18	0-16	SN7470	0-30	0-27	0-25	SN74155	1-65	1-47	1-35
SN7406	0-30	0-27	0-25	SN7472	0-30	0-27	0-25	SN74156	1-55	1-47	1-35
SN7407	0-30	0-27	0-25	SN7473	0-40	0-37	0-35	SN74157	1-80	1-70	1-50
SN7408	0-20	0-18	0-16	SN7474	0-40	0-37	0-35	SN74160	2-80	2-40	2-25
SN7409	0-45	0-42	0-35	SN7475	0-55	0-52	0-50	SN74161	2-80	2-40	2-25
SN7410	0-20	0-18	0-16	SN7476	0-45	0-42	0-39	SN74162	3-40	3-25	3-20
SN7411	0-23	0-22	0-20	SN7480	0-80	0-76	0-67	SN74163	3-40	3-25	3-20
SN7412	0-42	0-40	0-35	SN7481	1-25	1-15	1-10	SN74164	2-75	2-30	2-10
SN7413	0-42	0-40	0-35	SN7482	0-75	0-70	0-65	SN74165	1-60	1-35	1-20
SN7414	0-30	0-27	0-25	SN7483	1-00	0-90	0-85	SN74166	4-00	3-50	3-00
SN7415	0-30	0-27	0-25	SN7484	0-90	0-85	0-80	SN74167	2-25	5-60	5-10
SN7416	0-30	0-27	0-25	SN7485	0-45	0-41	0-38	SN74170	4-10	3-55	3-05
SN7417	0-30	0-27	0-25	SN7486	0-75	0-70	0-65	SN74174	2-00	1-75	1-30
SN7418	0-20	0-18	0-16	SN7487	0-75	0-70	0-65	SN74175	1-35	1-27	1-15
SN7419	0-48	0-44	0-40	SN7488	0-75	0-70	0-65	SN74176	1-60	1-35	1-20
SN7420	0-48	0-44	0-40	SN7489	0-75	0-70	0-65	SN74177	1-60	1-35	1-20
SN7421	0-48	0-44	0-40	SN7490	0-80	0-75	0-70	SN74180	1-55	1-30	1-20
SN7422	0-48	0-44	0-40	SN7491	1-00	0-97	0-95	SN74181	7-00	6-00	5-50
SN7423	0-48	0-44	0-40	SN7492	1-00	0-97	0-95	SN74182	2-00	1-80	1-60
SN7424	0-48	0-44	0-40	SN7493	0-75	0-70	0-65	SN74184	2-40	2-00	1-80
SN7425	0-48	0-44	0-40	SN7494	0-80	0-75	0-70	SN74185	2-40	2-00	1-80
SN7426	0-48	0-44	0-40	SN7495	0-80	0-75	0-70	SN74186	1-85	1-55	1-75
SN7427	0-48	0-44	0-40	SN7496	1-00	0-97	0-95	SN74187	1-50	1-40	1-30
SN7428	0-50	0-45	0-42	SN7497	0-85	0-80	0-80	SN74188	2-00	1-80	1-60
SN7429	0-50	0-45	0-42	SN7498	0-85	0-80	0-80	SN74189	2-00	1-80	1-60
SN7430	0-20	0-18	0-16	SN7499	0-85	0-80	0-80	SN74190	2-00	1-80	1-60
SN7431	0-20	0-18	0-16	SN7500	2-50	2-30	2-20	SN74191	1-85	1-55	1-75
SN7432	0-42	0-39	0-35	SN7501	1-45	1-35	1-20	SN74192	1-85	1-55	1-75
SN7433	0-70	0-61	0-44	SN7502	1-35	1-25	1-20	SN74193	2-00	1-90	1-80
SN7434	0-65	0-60	0-50	SN7503	0-50	0-45	0-40	SN74194	2-00	1-90	1-80
SN7435	0-65	0-60	0-50	SN7504	0-50	0-45	0-40	SN74195	1-85	1-70	1-60
SN7436	0-65	0-60	0-50	SN7505	0-50	0-45	0-40	SN74196	1-50	1-40	1-30
SN7437	0-65	0-60	0-50	SN7506	0-50	0-45	0-40	SN74197	1-50	1-40	1-30
SN7438	0-65	0-60	0-50	SN7507	0-50	0-45	0-40	SN74198	4-60	3-70	3-35
SN7439	0-65	0-60	0-50	SN7508	0-50	0-45	0-40	SN74199	4-60	3-70	3-35
SN7440	0-75	0-72	0-70	SN7509	0-50	0-45	0-40				
SN7441	0-75	0-72	0-70	SN7510	0-50	0-45	0-40				
SN7442	0-75	0-72	0-70								
SN7443	1-00	0-95	0-90								
SN7444	2-00	1-75	1-60								
SN7445	2-00	1-75	1-60								
SN7446	2-00	1-75	1-60								
SN7447	1-75	1-60	1-45								
SN7448	1-75	1-60	1-45								

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
TEXAS HANDBOOK NO. 2, I.C. 700 PAGES DATA 60p. POST 20p.
HIGH POWER SN 74 LOO Now in stock—send for list No. 36
LOW POWER SM 74 LOO

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA930	10p	BC147	12p	BU105	2.25	OC44	15p	T1843	35p	2N3055	55p
AA942	15p	BC1890	12p	BY100	15p	OC45	15p	V405A	25p	2N3440	75p
AAZ13	10p	BC182	10p	BY126	15p	OC57	50p	ZTX108	12p	2N3449	1.25
AC107	35p	BC214	15p	BY127	15p	OC71	15p	ZTX300	12p	2N3525	75p
AC126	25p	BCY32	75p	BY213	35p	OC72	25p	ZTX301	12p	2N3614	55p
AC127	25p	BCY34	35p	CI06D	65p	OC77	45p	ZTX302	12p	2N3615	75p
AC128	25p	BOY39	1.00	GET111	55p	OC81	25p	ZTX341	20p	2N3702	10p
AC176	35p	BCY42	35p	GET115	55p	OC82	25p	ZTX500	15p	2N3764	15p
AC187	25p	BCY43	25p	GET250	45p	OC140	55p	ZTX503	17p	2N3705	10p
AC188	25p	BCY55	2.50	LM309K	1.00	OC170	25p	2G301	30p	2N3714	1.80
ACY17	30p	BCY70	15p	(T03)	1.87	OC171	30p	2N404	20p	2N3771	1.75
ACY20	20p	BOY71	20p	MAT121	25p	OC200	45p	2N627	35p	2N3773	2.00
ACY21	20p	BCY72	15p	MJE340	50p	OC202	75p	2N696	15p	2N3790	2.25
ACY39	55p	BCY87	2.90	MJE370	70p	OC202	30p	2N697	15p	2N3819	35p
AD140	50p	BCZ11	50p	MJE520	75p	OC203	50p	2N708	10p	2N3820	50p
AD149	50p	BD124	80p	MJE2855	1.00	OC271	30p	2N930	20p	2N3866	85p
AD161	35p	BD131	75p	ORP12	50p	OC272	30p	2N987	45p	2N3903	15p
AD162	35p	BD132	80p	MJE3055	1.10	ORP60	40p	2N1131	25p	2N3906	12p
AF117	20p	BF115	25p	P346	20p	RA8510AF	45p	2N1132	25p	2N4001	12p
AF118	20p	BF107	25p	MPP105	30p	TAA263	75p	2N1133	25p	2N4002	12p
AF124	25p	BF173	25p	NKT214	20p	TIP209	35p	2N1134	25p	2N4062	12p
AF139	30p	BF179	30p	NKT216	40p	TIP28A	50p	2N1135	25p	2N4062	12p
AF186	40p	BF180	30p	NKT217	40p	TIP31A	60p	2N1136	25p	2N4126	15p
AF239	40p	BF194	15p	NKT403	70p	TIP32A	70p	2N1137	25p	2N4871	35p
ASV27	30p	BF195	15p	NKT404	50p	TIP33A	80p	2N1138	25p	2N4877	55p
ASV28	25p	BF861	25p	OA5	50p	TIP34A	1.00	2N1139	25p	2N4901	1.00
BA102	30p	BF108	25p	OA10	35p	TIP35A	1.50	2N1140	25p	2N4902	1.00
BA115	7p	BFX13	25p	OA81	10p	TIP36A	2.50	2N1141	25p	2N4903	1.00
BA145	15p	BFX34	75p	OA91	7p	TIP38A	3.00	2N1142	25p	2N4904	1.00
BAX13	5p	BFX37	30p	OA200	7p	TIP41A	3.00	2N1143	25p	2N4905	1.00
BAX16	7p	BFX98	20p	OA202	10p	TIP42A	3.50	2N1144	25p	2N4906	1.00
BC107	10p	BFY50	20p	OC18	75p			2N1145	25p	2N4907	1.00
BC198	10p	BFY51	20p	OC20	45p			2N1146	25p	2N4908	1.00
BC109	10p	BFY52	20p	OC23	85p			2N1147	25p	2N4909	1.00
BC109C	12p	BFY64	50p	OC25	40p			2N1148	25p	2N4910	1.00
BC113	15p	BFY90	59p	OC28	85p			2N1149	25p	2N4911	1.00
BC117	20p	BLX36	8.00	OC35	50p			2N1150	25p	2N4912	1.00
BC143	35p	BSX20	15p	OC36	65p			2N1151	25p	2N4913	1.00
		BSY27	15p	OC42	40p			2N1152	25p	2N4914	1.00

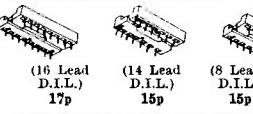INTEGRATED CIRCUIT SOCKETS LOW PROFILE PLATED PINS



QUANTITY DISCOUNTS


10% 12+ : 15% 25+ : ANY ONE TYPE
20% 100+ : 25% 250+ :
From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value £1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	59p	2N2926	10p
1000 MC/S		All Colours	
25 + 20p		25 + 9p	
100 + 17p		100 + 8p	
500 + 15p		500 + 6p	
		1000 + 5p	
AF117 Mullard	25p	2N3819 Texas	35p
25 + 17p		25 + 30p	
100 + 15p		100 + 25p	
500 + 12p		500 + 20p	

Sinclair Project 60

Stereo 60

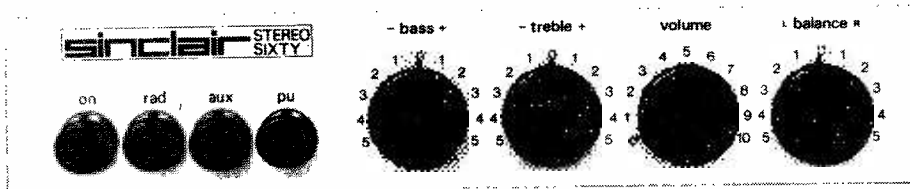

Built and tested post free
£9.98

pre-amplifier/control unit

The versatility of Project 60 high-fidelity modules is well demonstrated in this excellent unit. It provides the facilities essential to good stereo and will enhance the quality of any system it is used with, whether Project 60 or any other top line power amplifiers. Compact, yet robustly constructed, the unit is easily panel mounted and will operate satisfactorily from 18 to 35 volts supply. Silicon epitaxial transistors are used throughout to achieve a very high signal to noise ratio with excellent separation between channels. Distortion at maximum output is barely 0.02% with magnetic p.u. input. Accurate equalisation is provided for all inputs, which are selected by push buttons. For maximum effectiveness, the Sinclair A.F.U. is recommended for use with the Stereo 60 pre-amp/control unit. A comprehensive manual supplied with Project 60 modules makes installing and connecting easy and ensures best possible results from your system.

SPECIFICATIONS

Input sensitivities: Radio – up to 3mV. Mag. p.u. 3mV correct to R.I.A.A. curve $\pm 1\text{dB}$, 20 to 25,000 Hz. Ceramic p.u. – up to 3mV; Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE ± 12 to -12dB at 10KHz; BASS $+12$ to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Super IC.12 integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC, make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak), 6–8 Ω . **Frequency Response:** 5Hz to 100KHz $\pm 1\text{dB}$. **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Project 605



The easy way to buy and build Project 60

Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

Everything you need to assemble a superb 30 watt high fidelity stereo amplifier without having to solder.

sinclair

Sinclair Radionics Ltd, London Road, St. Ives, Huntingdonshire PE17 4HJ. Tel: St. Ives 64311

the world's most advanced high fidelity modules

Z.30 & Z.50 power amplifiers

Built, tested and guaranteed with circuits and instructions manual. **Z.30 £4.48** **Z.50 £5.48**

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to provide unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and are intended for use principally with other units in the Project 60 range. Their performance and design are such, however, that Z.50s and Z.30 may be used in a far wider range of applications.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).—Power Outputs: **Z.30** 16 watts R.M.S. into 8 ohms using 35 volts : 20 watts R.M.S. into 3 ohms using 30 volts. **Z.50** 40 watts R.M.S. into 3 ohms using 40 volts : 30 watts R.M.S. into 8 ohms using 50 volts. **Frequency response:** 30 to 300,000Hz ± 1dB. **Distortion:** 0.02% into 8 ohms. **Signal to noise ratio:** better than 70dB unweighted. **Input sensitivity:** 250mV into 100 Kohms (for 15w into 8Ω). For speakers from 3 to 15 ohms impedance. **Size:** 14 x 40 x 57mm.



Project 60 Stereo F.M. Tuner

Built and tested. Post free. **£25**

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.


SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7µV for lock-in over full deviation. **Squelch level:** Typically 20µV. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10Hz – 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2µV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.



A.F.U. High & Low Pass Filter Unit

Built, tested and guaranteed. **£5.98**

For use between Stereo 60 unit and two Z.30s or Z.50s. The unit is very easily mounted and is unique in that the cut-off frequencies are continuously variable. As attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. There are two filter sections – rumble (high pass) and scratch (low pass). H.F. cut-off (–3dB) variable from 28KHz to 5KHz. L.F. cut-off (–3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) 0.02% at rated output. Operating voltage from 15 to 35V. Current 3mA. **Size:** 66 x 40 x 90mm.

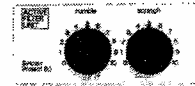

Power Supply Units

Designed specifically for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 or PZ.8 where a stabilised supply is essential.

PZ.5 30 volts un stabilised £4.98
PZ.6 35 volts stabilised £7.98
PZ.8 45 volts stabilised £7.98
(less mains transformer)
PZ.8 mains transformer £5.98



Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (**£25**) & A.F.U. (**£5.98**) may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

SINCLAIR RADIONICS, ST IVES, HUNTINGDONSHIRE PE17 4HJ

Please send

I enclose cash/cheque/money order.

Name

Address

PW 2/73

sinclair

Practical Wireless Classified Advertisements

Aerials

GENUINE FULL SIZE
18 element TV aerial
as used by leading
TV companies

£1.99
+ 35p cart



ITV BBC1 & 2 BLACK/WHITE & COLOUR
Guaranteed Perfect Pictures. Save £2s. We supply this genuine U.H.F. aerial for only £1.99, can be fitted out side or inside. Quality made, technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions, advice.
Money Back Refund Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters.

Send direct to Dept PW10, 219 Mansfield Rd., Nottingham.

IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists.

Direct from the Manufacturers
U.H.F. AERIALS

EASY ASSEMBLY KITS
10 Element **SAVE 40%**
£1.25 on normal retail price



14 Element 18 Element
£1.50 **£1.75**
Plus 25p cartage & 30p Plastic assembly and 30p silver 12p cartage and packing. Please state which channel or channels.

APEX AERIALS (P.W.)
ALBION WORKS, WABY ST., JOHNSTONE, HENFREESHIRE

BAINES for High Frequency Aerials
Postage paid on all items.
MULTIBEAMS by J BEAM
MBM 10 £2.20. MBM 18 £2.90.
MBM 30 £3.90. MBM 46 £6.00.
2 MBM 46 £15. MBM 70 £11.
Log Periodic £5 UHF Diplexers 65p
FM Stereo FM45 £5.55 FM6S £7.80.
MASTHEAD PRE-AMPS.
Single Stage £6.00. Twin £8.00.
Wideband £6.95.
SAE will bring full details.
11 Dale Cres., Tupton,
Chesterfield S42 6DR.

For Sale

MORSE MADE EASY!!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).
Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.
Beginner's Section only £3.30. Complete Course £4.60 (Overseas £1.00 extra) details only, 4p stamp. 01-650 2895
G3HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials.
S.A.E. K. R. WHISTON, Dept. PW,
NEW MILLS, Stockport.

Ladders

LADDERS, 20ft, £7.80; 24½ft £9.80.
Carr. 80p. Leaflet. (Dept. WLS) Home Sales Ladder Centre, Baldwin Road, Stourport, Worcs. Tel. 029-93 5222.

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Service Sheets

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"
Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model, number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

Situations Vacant

MEN!
£50 p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators Training Centre
M94, Oxford House
9-15, Oxford Street, W.1.
Telephone: 01-734 2874
127, The Piazza, Dept. M94,
Piccadilly Plaza, Manchester 1.
Telephone: 061-236 2935

SOUND EQUIPMENT. Interesting and varied job installing and servicing Public Address equipment. A working knowledge of audio is needed, (or radio might do). Clean driving Licence essential, 5 day week. Write or phone —Mr. N. Reder, N. Reder Ltd., Jubilee Works, Esther Road, London E.11. Phone 01-539 0136.

Wanted

TOP PRICES PAID for NEW VALVES popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

* SERVICE SHEETS • MANUALS • BOOKS *

SERVICE SHEETS OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK | **SERVICE SHEET** ON RADIOS, TV'S, R.PLAYERS AND T.RECORDERS, ETC... | **SERVICE SHEET** 30p + Postage | **PLEASE ENCLOSE S.A.E. WITH ENQUIRIES...** | **Catalogue 20p.**

NEW BOOKS & PUBLICATIONS	PRICE + P.&P.
1. COLOUR TELEVISION-SERVICING by G.J. King. 332 pages.	14.40 30p
2. COLOUR TELEVISION PICTURE FAULTS by K.J. Bohman. Illustrated in Colour	£2.50 15p
3. MAZDA BOOK OF PAL RECEIVER SERVICING by D.J. Seal. FS.E.R.T.M.S. 298 pages	£3.80 30p
6. T.V. TECHNICIAN'S BENCH MANUAL by G.R. Widing. 187 pages. 127 illustrations	£2.25 15p
9. BEGINNERS GUIDE TO TELEVISION 5th Edition by G.J. King. 212 pages. Illustrated	£1.60 15p
30. RADIO TECHNICIANS BENCH MANUAL by H.W. Hellyer. 215 pages. 131 illustrations	£3.00 15p
36. TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard Ltd. 230 pages. New Edition	£1.80 15p
38. SERVICING WITH THE OSCILLOSCOPE by G.J. King. 176 pages.	£1.80 15p
44. TAPE RECORDERS by H.W. Hellyer. Guide to Purchase & Operating. 239 pages.	£2.25 15p
57. THE HI-FI AND TAPE RECORDER HANDBOOK by G.J. King. 304 pages	£2.00 20p
62. GUIDE TO PRINTED CIRCUITS by G.J. King. 140 pages. 95 illustrations	£2.50 15p
76. RADIO, TV & AUDIO TEST INSTRUMENTS. 2nd Edition by Gordon J. King	£3.80 30p
85. MANUAL OF SOUND RECORDING. 2nd Edition by J. Aldred. 269 pages.	£3.50 15p
87. PICKUPS & LOUDSPEAKERS by John Earl. 203 pages. 126 illustrations	£3.00 15p
88. PUBLIC ADDRESS HANDBOOK. A Manual of Sound Reinforcement by V. Capel	£3.00 15p
123. AUDIO TECHNICIANS BENCH MANUAL by John Earl. 182 pages. 114 illustrations.	£3.00 15p
124. TUNERS & AMPLIFIERS by John Earl. 187 pages. 127 illustrations	£2.10 15p
125. WORLD RADIO-TV HANDBOOK 1972. Immense amount of tabulated matter	£2.80 25p
126. VIDEO-RECORDING, RECORD & REPLAY SYSTEMS by G. White. 216 pages	£3.25 20p

Send S.A.E. for Free LISTS of Practical and Technical Books on Radio & Television now available to

BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorks. Tel. 0423-86844

TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commencing January 1st. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. A/2, 20 Penwyern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**



RADIO, TV, RTEB Certs., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book—FREE. BIET (Dept BPW 23), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

CIE, AMSE, City & Guilds, etc. Thousands of exam successes. Postal courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept BPW 34), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Receivers and Components

NEW GUARANTEED DEVICES ORDER WITH CONFIDENCE

MICROCIRCUITS: 709 28p; 728 57p; 741 28p; 748 37p; PA230 70p; SL402A £1.00; SL702C 40p; SN76013N £1.24; FET Op Amp £4.28. **TRANSISTORS:** 2N656 14p; 2N697 14p; 2N1613 16p; 2N1711 16p; 2N2219 19p; 2N2904 17p; 2N2926 REDE 6p; OR: 7p; YEL: 8p; GRN: 9p. 2N3053 15p; 2N3064 35p; 2N3055 85p; 2N3702 10p; 2N3703 10p; 2N3704 10p; 2N3706 9p; 2N3710 9p; 2N3711 9p; AC127 10p; AC128 10p; AC176 15p; ACY21 17p; AF124 22p; BC107 7p; BC108 7p; BC109 7p; BC177 13p; BC178 12p; BC179 16p; BCY70 10p; BCY71 22p; BD142 35p; BF115 20p; BF194 13p; BFX29 24p; BFX84 20p; BFX86 15p; BFX87 24p; BFX88 18p; BFX90 15p; BFX91 15p; BFX92 15p; BXS20 12p; BLY47A 40p; OC44 12p; OC45 12p; OC71 12p; OC72 12p; OC81 18p; OC83 24p; RECTIFIERS 1 AMP: 60V 31p; 100V 4p; 200V 5p; 400V 9p. IC Sockets 12p; SOLDER-CONS 0.5p per PIN; LED Panel Lamp 45p; Carbon 1W 5% RESISTORS 22ohm to 2.2Mohm 1p each or 5p per 10 of one value. ZENER DIODES BZY88 Series 400mW 5% 2.7V to 33V 8p. DALO PC RESIST PEN 80p. ME Series TRANSISTORS also available.

JEF ELECTRONICS (P.W.2)

York House, 12 York Drive, Grappenhall, Warrington WA4 2EJ. Mail Order Only. C.W.O. P & P 9p per order. O/seas 65p. Discounts start at 10% for 10+. List free. **NEW FULL SPEC. GOODS. MONEY BACK ASSURANCE**

HEADPHONES. Matching 9R59DS, EC10 and all low impedance receivers. Luxury lightweight adjustable, foam padded. Japanese: £2.60. Partridge Electronics Ltd., Broadstairs, Kent.

FERRIC CHLORIDE, 1lb 25p. Magnetic counters 10p. 50 resistors 16p. 20 capacitors 20p. Constructor's sample parcel and lists 30p. QSL Display Units (120 Cards), 25p. Postage extra. Derwent Radio, Scarborough.

5-N-CHANNEL FETs 3819E—£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.

Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LIMITED

45 Station Road, Gerrards Cross, Bucks. Mail Order only

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 incl. postage. C.W.O. to Caledonian Components, Fosterton Firs, Strathore Road, Thornton, Fife.

PRECISION POLYCARBONATE CAPACITORS

FRESH STOCK — FULLY TESTED
Close tolerance. High stability. All 63V d.c.

0.47µF:	±5%	30p:	±2%	40p:	±1%	50p
1.0µF:	±5%	40p:	±2%	50p:	±1%	60p
2.2µF:	±5%	50p:	±2%	60p:	±1%	75p
4.7µF:	±5%	70p:	±2%	90p:	±1%	£1.15
6.8µF:	±5%	85p:	±2%	£1.15:	±1%	£1.60
10µF:	±5%	£1.10:	±2%	£1.40:	±1%	£1.80
15µF:	±5%	£1.60:	±2%	£2.10:	±1%	£2.70

TANTALUM BEAD CAPACITORS— Values available 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF, 25V, 15µF, 20V, 22µF, 15V, 33V, 10V, 47µF, 6V, 100µF, 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (72 capacitors) £5.

NEW—TRANSISTORS. BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices.

POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1. IN916—9p each, 6 for 50p, 14 for £1. IS44—5p each, 11 for 50p, 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5 mA. All new and marked. Price 10p each, 6 for 50p, 14 for £1.00. Special offer 6 off each voltage (66 zeners) £4.50.

RESISTORS. Carbon film 1W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

400V A.C. CAPACITORS. 0.1µF, size 1 1/2in x 1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47 and 0.5µF, size 1 1/2in x 1/2in, 35p; 1.0µF, size 2in x 1/2in, 45p; 2.0µF, size 2in x 1in, 75p each.

SILICON PLASTIC RECTIFIERS 1.5 Amp Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5. **V. ATTWOOD, DEPT. D4, P.O. Box 8, ALRESFORD, HANTS.**

INTEGRATED CIRCUIT FREQUENCY MARKERS

Designed for amateurs, SWL's and professional use. Providing fundamental frequencies and harmonics up to over 450 Mhz.

MK I OUTPUTS at 1 Mhz, 500, 100, 50 & 10 KHz. Kit £5.55, Built and tested £6.25

MK II OUTPUTS at 1 Mhz, 500, 100, 50, 25, 12.5 & 6.25 KHz. Kit £6.30, Built and tested £7.00
Dozens of units already in use throughout the world. Send crossed cheque or P.O. to

CHILTERN AMATEUR RADIO CLUB

G3CAR,

12 ROUNDLANDS, LACEY GREEN,

AYLESBURY, BUCKS.

or S.A.E. for further details.

TAPE-HEAD reconditioning service. Guaranteed satisfaction. Send worn head with £2 to: Sara Electronics, Fawkham Avenue, Longfield, Kent.

Trampus electronics

All Brand New. Money Back if dissatisfied. Fast Service. **5V DIGITAL INDICATOR** 0.9DP, with socket and red filter £1.35, 7447 £1.49. **IG GAS DETECTOR.** Smoke, Butane, Vapour, etc. £1.99, data 9p. **ULTRASONIC TRANSDUCER.** Transmit or receive, £2. **LIGHT EMIT DIODES.** Visible red panel clip/data, 59p. **INFRARED (invisible beam),** £1.19. **DIGITAL CLOCK** integrated circuit, 2 pin DIL 12/24 hr. 4/6 digit. £11.50, data 15p. P.C.B. £1.29. **COMPLETE KIT** with Plastic Case £19.99. **CALCULATOR: RATTIDMAN 800** £39.50. Data Free. **FW TEXAN KIT** less chassis £21.49. PAKS: 10/semi-conductor 88 Caps £2.49. Res £1. Transformer £2.67. TIP 41/42 pair £2. 741/748 86p ea. **INTEGRATED CIRCUITS** with data. 741 Op amp DIL 30p, 709 T05 21p, DIL 29p, 710 36p, 748 39p. **PHOTO DETECTOR/amp** 44p. **VOLTAGE REGULATORS:** 14 amp 5 or 12 V. type 21.67, 723 59p, 855 TIMER/stat oscillator 89p. **AUDIO AMP** 3-W Hi-Fi etc. £1.24. Stereo. Dual Pre-amp £1.49. MPX Decoder for any FM RX £2.69. 74N: Data Booklet 12p, gates 7400 etc. 15p, 7490 59p, 7470/72 29p, 7475 39p, 7492 73p, 7413 29p. **DIL SOCKETS** low profile 14 or 16 pin, for 74N. 13p. **SEMICONDUCTORS** 2N8955, 39p. BC107, 8p. BC108, 7p. BC109, 8p. AC126/67/8. AC127/8. AC187/8. AF117, 18p. AD161/2, 35p. BC187/8/9, 17p. BC177/8/9, 15p. BC182/3/4, 11p. BC212/3/4, 18p. BCY70, 16p. BFY50/51/52, 17p. T1S43 UJT, 20p; 2N706A, 12p; FET 2N3819, 28p; 2N2926 O. Y., 9p; 2N3053, 17p; 2N3702/3/4/5/6/7, 11p; 2N3708/9/10/11, 9p. **1A RECTS:** 60V 4p, 400V 5p, 50V Bridge 29p. IN914/8 5p, OA81/91 7p, OA200/202 10p. **ZENERS:** BZY88 400mW 11p, 5.1V/10W 29p. MINI SCR 4A/400V 65p, TRIAC 6A/400V 87p. **CAPACITORS:** 25/30V Electrolytic. 10/50/100µF, 5p; 200/500µF, 8p; 1,000µF, 15p. DTC: 225F thro' to 0.047µF, 5p; 0.01 to 0.1µF. **RESISTORS** 1W 5%, 1p. PRESETS 0.25W, 5p. VERO 16p/25p, etc., DIN pins, 13p; sockets, 9p. **A.M. MEDIUM WAVE RADIO KIT** £2.89. **ELECTRONIC: CAR IGNITION KIT**, £6.67. FREE CATALOGUE, SAE, Data 5ht, 6p ea. CWO. P & P 7p, Overseas 85p. Discount 10+10%. P.O. BOX 29, BRACKNELL, BERKS.



SLEEVINGS, Varnished Glass, Terylene, Cotton, PVC. Fast delivery any quantity. Carlingwood Ltd., Bridge Green, Prestbury, Cheshire. Telephone: Prestbury 48342.

COMPONENTS—Integrated Circuits, Digital Displays, Diodes, Resistors, Capacitors, Switches. List 5p. Cavern Electronics, 29 Clarendon Road, Leicester LE3 6FB.

RADIOSPARES COMPONENTS at lowest prices. Send us list of items required and we will price it by return post. Grayshaw Instruments, 126 Sandgate High Street, Folkestone, Kent.

MINI MAINS TRANSFORMER MT7, 30 x 30 x 37mm, 7.0-7V rms, 120mA, for 9V rectified d.c. Top quality component with really comprehensive data. 70p, UK post 5p. Mail order only. **AMATRONIX LTD.,** 396 Selsdon Road, South Croydon, Surrey CR2. 0DE.

ELEVEN BAND RADIO. SW1-4 (4.30 MHz). Marine. LW, MW, FM. PB (76-86). Aircraft (108-136). PB (148-174). Battery/Main. BFO. AGC. Squelch Control. Output: 1-3W. 1.5in x 1.0in x 5 1/2in, £66. Eight Band Model, with BFO, £42. Four Band, MW, FM. Aircraft. PB. £15. SAE. Full Lists. Langtons Radio, High Street, ROCHESTER, Staffordshire, Tel. 388.

THE

TEXAN

NOW ON DEMONSTRATION



Designer approved Kit only £28.50
Instructions only 35p

- Pack 1. RESISTORS 80p
- Pack 2. SMALL CAPS £1.50
- Pack 3. LARGE CAPS £1.40
- Pack 4. SUNDRIES £1.90
- Pack 5. SWITCHES 90p
- Pack 6. CONTROLS £1.45
- Pack 7. SEMI COND. £8.25
- Pack 8. TRANSFORMER £4.95
- Pack 9. P.C. BOARD £2.00
- Pack 10. CHASSIS, etc. £2.75

Post extra—parts available separately
Send for list and technical spec.

Kits also available for

- ★ Radio Control Systems
- ★ Digital Clock Systems
- ★ Integrated Circuit Amplifiers (to 50W)
- ★ Hi-Fi Pre-amps
- ★ Stabilized Power Supply Units

TELETRADIO HI FI, 325 Fore Street,
Edmonton, London N.9 01-807 3719

CLOSED ALL DAY THURSDAY

BRAND NEW COMPONENTS BY RETURN. Electrolytics 16V or 25V—1, 2, 2, 4, 7, 10 mfd— $\frac{1}{2}$ p, 22, 47—4p, 100—5p, 50V— $\frac{1}{2}$ p extra. Subminiature bead-type tantalums—1/35V, .22/35V, .47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V— $\frac{1}{2}$ p, .002, .005, .01, .02—2p, .04, .05— $\frac{1}{2}$ p, .068, .1—3p. Polystyrene 63V—10pf—10,000pf, E.12 series—2p. Mullard miniature Carbon Film Resistors E12 series 1/3W 1 Ω —10M Ω 8 for 5p. Insured postage 8p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

COMPUTER PANELS 3p, Reed Switches, Micro Switches 8p, 50 assorted new components 25p, 25 assorted (Modern) Capacitors 25p, P.P. 5p. Grimsby Electronics, 64 Tennyson Road, Cleethorpes, Lincs. EXPERIMENTERS Catalogue 5p. (Mail Order Only).

TV LINE OUTPUT TRANSFORMERS Tidman Mail Order Ltd., 236 Sandycroft Rd., Richmond, Surrey. TW9 2EQ. 01-948 3702.

VALVE BARGAINS any 5—Give Free ECC82 EF183-EF184. PCF80. PCL82 PY800. PL36. When buy TVS. 19in. U.H.F./V.H.F. TV £6.50 carriage £1.50. Slotmeters. Perfect working £1.50. Post Free. MIR Radio & TV, 193 Ramsey St., Rochdale, Lancs. Tel. 40599.

TAPE AMPLIFIERS £3

Use 2 x ECC83, EL84, EZ80. Low impedance high sensitivity i.p. 3 ohm 2W O/P. Solenoid operated single motor non-standard deck. 7in. x 4in. speaker. All in polished oak cabinet, £2 (£1) with cct.

RESISTORS: 300 5%, 60p (15p); 200 5%, Hi-Stabs, 60p (12p); 100 1%, an 2%, 60p (8p); 100 metal oxide, 60p (8p). One of each, £2 (25p). 3W 5%, R's: 270, 470, 6K8, 15k, 27k, 33k, 82k, 100 for 50p (25p). Meters: 2 $\frac{1}{2}$ in. 500V d.c., 40p (10p); 2 $\frac{1}{2}$ in. 10V a.c., 40p (10p); 2 $\frac{1}{2}$ in. 1,500V electrostatic, 60p (10p); 2 $\frac{1}{2}$ in. 12 $\frac{1}{2}$ 0-12 $\frac{1}{2}$ A, £1 (10p); 3 $\frac{1}{2}$ in. 1mA, 75p (15p); 2 $\frac{1}{2}$ in. 100V rect. (5mA FSD), 60p (10p); 5 $\frac{1}{2}$ in. 0-15-50-150-300-500V mirror scale, £2 (40p). Ferric chloride, 1lb, 40p (15p); 10lb, £3.50 (50p); μ A709C, 25p; μ A741C, 25p; 2N3055, 35p; BC107-8-9, 8p or 14 for £1; 80 + 80 + 20 μ F/350V, 10p, 10 for 75p (25p); 8 μ F/2,500V, £2 (40p); Reed switch unit, contains 31 250V 1 $\frac{1}{2}$ A reeds mounted round a drum with magnet inside, also R's plugs, etc., £1 (25p); 2 for £1.65 (35p); reeds, 4p μ A723C, 40p; 2N1613, 12p.

TEST GEAR: TFI44G sig. gen., recalibrated as new, £20 (£2); decade res. box 0-9999 ohms, £7.50 (50p); BSR audio oscillator, 0-16kHz metered O/P, £9 (£1).

GREENWELL ELECTRONICS (PW9), 24 GOODHART WAY, W. WICKHAM, KENT. Tel. 01-777 2001. S.A.E. list. Post in brackets, small parts, 3p. Callers welcome. Please ring first (up to 10.30 p.m.).

Books and Publications

RadioBOOKS

- Handbk of Transistor Equiv and Substitutes 47p
- Handbook of Tested Transistor Circuits 47p
- Rad & Electr Colour Codes and Data Chart 20p
- Hi Fi, PA & Disco Amplifier Design H'bk 82p
- Boys Bk of Crystal Sets and Simple Circuits 23p
- How to make FM & TV Aerials, Bands 1, 2, 3, 23p
- Radio Servicing for Amateurs 25p
- High Fidelity Loudspeaker Enclosures 47p
- Practical Tape Recording Handbook 36p
- Practical Stereo Handbook 36p
- Practical Radio Inside Out 47p
- Transistor Circuits Manual No. 1 20p
- Transistor Circuits Manual No. 2 20p
- Coil Design and Construction Manual 36p
- Radio TV and Electronics Data Book 30p
- Transis Circuits for Radio Controlled Models 47p
- Pract Transistor Audio Amplifiers, Book 1 25p
- Transistor Test Equip and Servicing Manual 30p
- Handbook of Simple Transistor Circuits 42p
- Modern Transistor Circuits for Beginners 47p
- Sound and Loudspeaker Manual 57p
- Resistor Colour Code Disc Calculator 15p
- Manual Transistor Audio Amplifiers 47p
- Practical Car Radio Handbook 36p
- Radio TV and Industrial Tube & Valve Equiv 47p
- Practical Transistor Novelty Circuits 47p

(All prices include Postage & Packing)

FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
4 Tredwell Close, Bromley, BR2 9RH

DENCO CLACTON LIMITED

355-7-9 Old Road

Clacton-on-Sea, Essex

Catalogue 20p post paid

S.A.E. all enquiries

"HOW TO LISTEN TO THE WORLD 1973" £1.90. "World Radio TV Handbook" published December, £2.80. Post (first class) 10p each. David McGarva, Box 114H, Edinburgh EH1 1HP. Giro 17 412 0001.

Miscellaneous

Darned Electronic Wizardry

by Dewtron

Famous Kits, e.g. waa-waa complete kit £2.95; Fuzz kit £1.75, auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

"AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS"

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW
(S.A.E. for details)

TO: 'BOFFIN PROJECTS'

DEPT. KW2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

RECORD T.V. SOUND

using our loudspeaker isolating transformer. Provides safe connection for recorders, Hi-Fi equipment or extension speakers.

£1 post free. Instructions included.

Crowborough Electronics (PW)
Eridge Road, Crowborough, Sussex.

Bargain of the year. Small new, rexine covered box containing high quality 7 x 4 speaker, 1 watt transistor amplifier, volume control, 100V line input transformer, etc. £3 each, p.p. 25p. We are sole distributors for the popular new BEC teak end instrument cases. Please send large s.a.e. for pictures and prices. Electronic Supplies, 408 Sharrowvale Road, Sheffield.

FASCIA PANELS to individual specification in etched aluminium. Hardware supplies for constructors. Printed circuit boards one-off's. Send 5p for list. Ramar Constructor Services, 29 Shelborne Road, Stratford-on-Avon, Warwickshire.

BUILD IT in a DEWBOX quality cabinet. 2in x 2 $\frac{1}{2}$ in x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

THE PICTURE BOOK METHOD OF LEARNING

BASIC ELECTRICITY 5pts £4.50. **BASIC ELECTRONICS** 6pts £5.40. **BASIC TELEVISION** 3pts £3.60

(Postage and Packing included)

The Pictorial Approach Manuals assure the quickest and soundest method of gaining mastery over these subjects. The clear and concise illustrations make study a real pleasure. Your money refunded if not completely satisfied in your 100% Guarantee. Free Illustrated Prospectus on request.

Send now to **SELRAY BOOK CO., 60 HAYES HILL, BROMLEY BR2 7HP**

12 VOLT FLUORESCENT LIGHTS

(as illustrated)



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:
12 ins. 8 watt £3.60 post paid
21 ins. 13 watt £4.60 post paid

Callers welcome.

For lists or enquiries, large s.a.e.

**SALOP ELECTRONICS, 23 WYLE COP.
SHREWSBURY, SHROPSHIRE.**

BYWOOD STOP PRESS

RADIO CHIP (Tomorrows World)

2nd Nov. 1972

AM 10 trans TRF circuit in T018 package, plus six components equals one radio, price £1.25 incl P & P.

DIL size switches:

1p3w, 2p4w, 4p2w, 4 @ 1p2w.

75p 80p 85p 90p + 12p p & p.

NEW LED PRICES:

TIL 302 Large 7 seg display £3.50

TIL312 1/2 inch 7 seg display £2.00

TIL209 LED point, four for £1.00

P & P on LEDS 12p.

No more Room—Catalogue 15p—Now!

**BYWOOD
ELECTRONICS**

181 EBBERNS RD, HEMEL HEMPSTEAD, HERTS.
0442 62757

150W INVERTOR P.W. DEC. 1972
Transformers, transistors, etc. M. Hamner finished steel case and drilled front plate.
COMPLETE KIT—£12.95 + 75p postage
TRANSFORMERS only—£5.50 + 50p postage
300 watts 24 volt input also available.
COMPLETE KIT—£14.95 + 75p postage.
TRANSFORMERS only—£6.50 + 50p postage
All Kits complete with circuit and instructions. No surplus components. BOTH MODELS AVAILABLE READY BUILT.
ELTON ELECTRONICS,
Hulme St. Bury, Lancashire.
Tel: 061-761 1202.

SPECIAL OFFER. Build it in an IMHOV Cabinet. 19 1/4 in x 8 in x 4 1/2 in. Green Stove enamel finish with Aluminium Trim and Front Panel. £3.50 each £6.00 pair. Terms: C.W.O. postage free. Apply: GSVRX 7, Holling Head, Tong Park, BILDON.

THIS MONTHS BARGAIN* for

BARGAIN HUNTERS
100 square ins (min) packs of best quality mixed veroboard only £1.15 post/packing free C.W.O. to:-

LAWRENCE ELECTRONICS
5 Rialto Buildings,
Salford 7.

Telephone: 061-773-3953.

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACV22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (H)

17 Buckridge, Portpool Lane, London, E.C.1

RADIO BARGAINS



Grundig Mariner TR865	£35.00
Grundig Elite Boy 500 bat/mains	£27.00
Grundig Melody Boy 500 bat/mains	£27.00
Grundig Melody Boy 1000	£41.00
Grundig Yacht Boy 210	£34.50
Grundig Satellit 1000	£125.00
Aiwa AR158 6w.b. (Inc. air)	£31.00
Koyo KTR 1664 8w.b.	£47.50
Koyo KTR1661 8w.b.	£40.25
Koyo KTR1770 11w.b.	£69.50
ITT/KB Golf Preset	£22.50
ITT/KB Touring Int. Marine	£45.00
Toshiba IC70	£16.50
Grundig RF430	£26.50

FREE With each set "Guide to Broadcasting Stations" (160 pages)

**WILMSLOW
AUDIO, Dept. PW,
10 Swan St., Wilmslow,
Cheshire, SK9 1HF**

AERIAL BOOSTERS

We make four types of Aerial Boosters. L45 62 5 UHF. L12 VHF 405. L11 VHF Radio L10 M/VW & S/W. Price L45, L12 & L11 £2.95. L10 £2.45.

VALVE BARGAINS

Any 5—45p. 10—70p:

ECC82, ECL80, EF80, EF85, EF183, EF184, EBF89, EB91, EY86, PCC84, PCC89, PC97, PCF80, PCF86, PCL92, PCL83, PCL84, PCL85, PL36, PY33, PY62, PY600, PY901, 30L15, 30C15, 6-30L2.

19" UHF/VHF TV £7.50

THORN 850 SERIES

Untested but with complete set of spare valves. Price £7.50. Carriage £1.50.

100 MIXED RESISTORS 60p

From 1/2 watt to 2 watt and from 10-ohms to 10m-ohms our choice.

100 MIXED CAPACITORS £1

From 220PF to 200MFD and from 12v/w to 500v/w—our choice.

POST & PACKING under £1.5p. Over £1.10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

VELCO ELECTRONICS

62B Bridge Street, Ramsbottom,
Bury, Lancs.

Please mention

PRACTICAL WIRELESS

when replying to
Advertisements

TV's! COLOUR TV's!

SURPLUS & REPOSSESSED STOCKS!
PERFECT WORKING ORDER
REPOLISHED CABINETS
MAKES INCLUDE BUSH, FERGUSON 2000,
PHILIPS 500, DECCA, BAIRD
19" COLOUR FROM £189.00
25" COLOUR FROM £135.00

Cash and collect. (Sorry no cheques), or telephone Mr. Wilson for delivery quotation.

UHF TV's from £4

19"/23" SLIMLINES
REPOLISHED CABINETS

UHF TUNERS FOR

FERGUSON 850/900 CHASSIS

ADAPTABLE MOST MODELS

£2.50 each—inc. post—CWO

Send SAE for lists of TVs, Tubes, Valves,

Slotmeters, etc.

Deliveries arranged anywhere.

Working sets to order.

Opening hours: Weekdays until 8 p.m.

Saturday 5.30; Sunday 10 a.m. to 1 p.m.

(15 mins. M1, M62)

TRADE DISPOSALS

1043 LEEDS ROAD, BRADFORD, 3
Telephones:
Midlands & North—BRADFORD 665670
Scotland—HAMILTON 29511
South West—REDRUTH 6579

Strike a new note with AUDIO

Britain's exciting new-style magazine in music and hi-fi
AUDIO is about every important aspect of the modern sound scene—from the make-up of sound, to the latest means of reproducing it . . . the equipment, its installation and its operation.
AUDIO examines new trends, looks at the latest discs and tapes, shows you how to get the most for your money—in clarity, definition and craftsmanship.

AUDIO

Monthly 20p

for your greater enjoyment of
leisure and listening

NEW

ALL SILICON!



PRACTICAL WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 3/4" x 3 3/8" x 2". Complete assembly and wiring manual 25p, refundable on purchase of kit.

Suitable for 12v or 6v systems with Pos. or Neg. earth.
 Price: Standard Kit£7.25 U.K. Post Free
 De-Luxe Kit£8.75 U.K. Post Free
 Quantity Discounts: 1-5 Nett
 6-9 Less 10%
 10-49 Less 15%
 50-99 Less 20%
 100-999 Less 25%
 1000 up Less 30%

Trade and Overseas
 Enquiries Invited

Mail Order Only

STATE POS. OR NEG. EARTH AND 6V OR 12V WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
 WALSALL, STAFFS. WS1 1UZ
 Tel. Walsall 34365

P. C. BOARDS



Reverberation Unit PCB.

FOR P.W. PROJECTS

- All PCB's Fibreglass, Drilled, Roller-Tinned
 Circuit and Layout Diagrams free with each PCB
- REVERBERATION UNIT (Nov/Dec 1972)**
 PCB (2in x 11 1/2in). Specially designed to also hold Slider Pots with spacing compatible with published front panel £1.20
 SET of R's, C's, S/C's, Slider Pots, Transformer, and 16in Spring-line Unit £12.90, (with 9in unit £9.70)
- 8 WATT AMPLIFIER (Nov 1972)**
 PCB (Mono—2 1/2in x 3in) 60p
 R's, C's, Semiconductors: Stereo Set £7.70, Mono Set £3.90
- PRE-AMPLIFIER (Nov 1972)—for use with 8 Watt Amplifier**
 PCB (Stereo—3 1/2in x 7 1/2in) Specially designed to also hold all Pots, either rotary or slider, plus Selector Switch £1.50
 R's, C's, Rotary Pots, Selector Switch, Semiconductors:
 Stereo Set £5.20, Mono Set £2.50
 Slider Pots & Knobs instead of Rotary Pots:
 Stereo—Extra £1.52, Mono—Extra £1.26
- LOUDHAILER & SIREN (Dec 1972)—PRE-AMP & SIREN GENERATOR**
 PCB (2 1/2in x 2 1/2in) 75p.
 Set of R's, C's, Pot (with switch) S.C's £1.45
- VIBRASONIC GUITAR PRE-AMP (Sept 1970)**
 PCB (4in x 13in) for Mic Pre-Amp, 2-Guitar Pre-amp, Tremulant & Tone Controls, Wah-Wah, Master Volume. Specially designed to also hold all pots, either Rotary or Slider. £2.85
 Set of S/c's, R's, C's, Rotary Pots, LDR, Lamp, Coupling T/former £7.75
 Slider Pots & Knobs instead of Rotary Pots—EXTRA £3.78
 Other Designs Available. S.A.E. for List (F/scap) and enquiries.
 POSTAGE: U.K. 10p any order. OVERSEAS at cost.

PHONOSONICS

DEPT. PW2, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
 MAIL ORDER ONLY

INDEX TO ADVERTISERS

Antex Ltd.	875	Felstead Electronics	940	Radio Book Service	956
Apex Aerials	954	Gladstone Radio	958	Radio Component Specialists	943
Astro Electronics	868	Global Audio Discount Warehouse	868	Radio Exchange Ltd.	869
Actwood, V.	955	Greenweld Electronics	956	Radio & T.V. Components (Acton) Ltd.	878, 879
B. H. Component Factors	876	HAC Shortwave Products	950	Radio Society of Great Britain	880
Baines, R.	954	Hadley, C.	958	Radnor Supplies	949
Bell's Television	954	Harverson Surplus Co. Ltd.	927	Readers Radio	866
Bentley Acoustic Corporation Ltd.	948	Heath (Gloucester) Ltd.	923	Redhawk Sales	955
Bernard, Gerald	880	Henry's Radio Ltd.	951, cov. iv	Riversdale Electronics Ltd.	886
B.I.E.T.	948, cov. iii	Home Radio (Components) Ltd.	899	ROC Electronics Ltd.	931
Bi-Pak Semiconductors	945, 946, 947	I.C.S.	882	RSC Hi-Fi Centres Ltd.	cov. ii, 865
Bi-Pre-Pak Ltd.	883	I.L.P. (Electronics) Ltd.	888	R.S.T. Valve Mail Order Co.	928
Boffin Projects	956	Imperial Trading	954	Salop Electronics	957
British National Radio & Electronic School	867, 949	Jef Electronics	955	Saxon Entertainments	887
Broadway Electronics	924	Jermyn Industries	900	Scientific & Technical	928
Bull, J. (Electrical) Ltd.	877	Johns Radio	900	Selray Book Co. Ltd.	956
Bywood Electronics	957	K.V.A. Electronics	944	Sinclair Radionics Ltd.	952, 953
C. & D. Electronics	924	Kensington Supplies	954	Shopertunities Ltd.	881
C. Caranna	954	Keytronics	944	Smith, G. W. & Co. Ltd.	870, 871, 872, 873
Chiltern Amateur Radio Club	955	King, J. M.	957	Smith, H. L. & Co. Ltd.	948
Codar Radio Co.	866	Lasky's Radio Ltd.	876, 939	Sonic Sound Audio Ltd.	874
Colomar Electronics Ltd.	940	Lawrence Electronics	957	Special Products Distributors Ltd.	874
Comet High Fidelity Discount Warehouses	884, 885	Lewis Radio	936	Surplronics	936
Crowborough Electronics	956	Linear Products Ltd.	944	Swanley Electronics	876
D.E.W. Ltd.	956	London Computer Operators Training Centre	954	Technical Trading... ..	880
Dabar Electronic Products	959	London Electronic College	955	Teleradio Co. Ltd.	956
Davian Electronics	874	Marshall, A. Son	904	Thacker, A. H. & Sons Ltd.	880
Denco (Clacton)	956	Miniwise Products	936	Tidman Mail Order	956
Dexter & Co.	950	Morse	954	Trade Aids... ..	944
Discosound	903	Multicore Solders Ltd.	928	Trade Disposals	957
Douglas Electronic Industries Ltd.	950	Padgetts Radio Store	886	Tramspan Electronix	955
Duke & Co. (London) Ltd.	868	Partridge Electronics Ltd.	886	Tuac Ltd.	949
Elton Electronics	957	Phonsonics... ..	959	Velco Electronics	957
Electronic Design Associates	866	Powertran Electronics	882	Vero Electronics	900
Electronic Supplies	956	Prolog Services Ltd.	958	W.E.C. Ltd.	924
Electrospares	874	Radio Exchange Ltd.	869	West London Direct Supplies	876
Electrovalve	935	Radio & T.V. Components (Acton) Ltd.	878, 879	Weyrad (Electronics) Ltd.	950
Elekon Enterprises	948	Radio Society of Great Britain	880	Wilmslow Audio	900, 940, 957
Elvins Electronic Musical Instruments	924	Radnor Supplies	949	York Electrics	882
Expo (Drills) Ltd.	860	Readers Radio	866	Z. & I. Aero Services	960

TRANNIES

(formerly C. HADLEY) HARLOW 37739

All our stocks are brand new with money back refund

24, WOODHILL, HARLOW, ESSEX

Add 5p P. & P. Price list S.A.E. No callers please.

TRANSISTORS	BD116	79p	OC44	13p	TIP33A	85p	2N3711	10p
AC107 15p	BD102	50p	OC71	13p	TIP34A	£1.80	40251	48p
AC126 11p	AL103	40p	OC72	12p	2N697	13p	40536	55p
AC127 11p	AU103	85p	OC79	12p	2N1171	24p		
AC128 11p	AU111	95p	OC81	12p	2N1804	25p		
AC176 25p	BC107	3p	OC81D	12p	2N1905	25p		
AC141K 20p	BC108	3p	OC83	20p	2N2646	47p		
AC142K 20p	BC109	3p	OC83	20p	2N2926	10p		
AD14 40p	BC154	20p	OC200	25p	2N3053	20p		
AD150 44p	BC168	10p	OC201	25p	2N3056	40p		
AD162 M/P55p	BC189	11p	OC25	25p	2N3702	12p		
AF114 15p	BC182L	3p	OC28	30p	2N3703	12p		
AF115 15p	BC183L	3p	OC29	36p	2N3704	12p		
AF116 15p	BC212L	3p	OC35	25p	2N3705	12p		
AF117 15p	BC214L	3p	OC36	36p	2N3706	10p		
			TIP29A	45p	2N3707	10p		
			TIP30A	55p	2N3708	9p		
			MP8513	45p	TIP31A	55p		
			OC41	13p	TIP32A	60p		
					2N3710	10p		

CAPACITORS

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0-01µF, 0-015µF, 0-022µF, 3p. 0-033µF, 0-047µF, 0-068µF, 3p. 0-1µF, 5p. 0-15µF, 5p. 0-22µF, 5p. 0-33µF, 5p. 0-47µF, 5p. 0-68µF, 11p. 1-0µF, 13p. 1-5µF, 20p. 2-2µF, 24p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 2p. 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3p. 0-047µF, 0-068µF, 0-1µF, 4p. 0-15µF, 6p. 0-22µF, 7p. 0-33µF, 11p. 0-47µF, 13p.
150V: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 0-068µF, 3p. 0-1µF, 5p. 0-15µF, 4p. 0-22µF, 5p. 0-33µF, 6p. 0-47µF, 7p. 0-68µF, 11p. 1-0µF, 13p.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES 6p each
(µF/V) 10/2.5, 20/2.5, 50/2.5, 100/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6-4/6-4, 25/6-4, 50/6-4, 100/6-4, 200/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2-5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1-6/25, 6-4/25, 12-5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64, 20/64, 32/64.

MULLARD C437 SERIES
100/40, 160/25, 250/16, 400/10, 640/8, 800/4, 1000/2-5, 9p. 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1000/6-4, 1600/2-5, 12p. 160/64, 250/40, 400/2-5, 640/16, 2000/4, 1000/10, 1600/6-4, 2500/2-5, 15p. 250/64, 400/40, 640/25, 3200/4, 1000/16, 1600/10, 2500/6-4, 4000/2-5, 18p.

Miniature Fixed Ceramic Plate 3p each.
Preferred values from 1-5p to 10,000 p.

MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0-9 and decimals (Data Sheet on request)

ONLY £1-50

16 DIL Socket 30p
Driven by 7447 95p

SUPER LOW PRICED LINEAR I.C.'S

801A To99	40p
301A DIL	45p
709C To99	28p
709C DIL	30p
723C To99	87p
723C DIL	90p
741C To99	10p
741C DIL	84p
741C 9p DIL	84p
747C DIL	40p
748C To99	38p

VOLUME CONTROLS
Potentiometers
Carbon track 500 Ω to 2-2M Ω
Log or Linear
Single 12p. Dual gang (stereo) 40p.
Single type with D.P. switch 12p extra.

RESISTORS
1 watt 5% carbon 1p each
1 watt 10% carbon 1p each
range 2-7 Ω to 10 M Ω type TR5
triple rated 1-1/2, tin oxide x25
range 10 Ω to 1 M Ω. 8p each

SLIDE SWITCH
SPST 10p each. D.P.D.T. 12p each.

MINIATURE NEON LAMPS
240v or 110v 1-4 5p. 5 plus 41p each.

CARBON SKELETON PRE-SETS
Small high quality, type P.R., linear only
100 Ω, 220 Ω, 470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 4M7, 10M Ω. Vertical or horizontal mounting, 6p each.

TIL 209 LIGHT EMITTING DIODE. Made by TEXAS INST. (Red). 35p.

VEROBOARD

21 x 3pin	0-15 Matrix	0-1 Matrix
21 x 5in	17p	23p
31 x 3pin	25p	25p
31 x 5in	35p	35p
Vero Pins (Bag of 36)	20p	20p
Vero Cutter	45p	
Pin Insertion Tools (-1 and -15 matrix) at 55p.		

SLIDE POTENTIOMETERS
55mm, TRACK
SINGLE GANGED, LOG or LIN
1k to 1M. 40p each.
TWIN GANGED, LOG or LIN
1k to 500K. 60p each.


SUPER PACKS

Pack of 10 BC169 (unmarked) but tested	50p	Pack of 25 IN4148	50p
2N2646 (unmarked) 30p each		Pack of 10 BC108 BC107 (Plastic can)	50p 50p
AC127 & AC128 1-9 10 plus 100 plus	13p 11p 8p	AD161, AD162 M/P	54p 48p
Pack of 10 2N2924G unbranded but tested	50p	BC107-BC108 BC109	8p 7p
Unmarked but fully tested 2N3055	30p 25p	Pack of 10 Plastic BC109	50p
1-9 10 plus			

A NEW CONCEPT IN SOUND REPRODUCTION

SONAR SOUND TRANSDUCER

(IMPORTED FROM N.AMERICA)

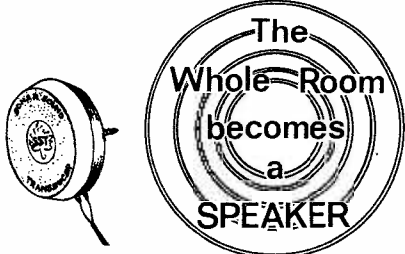

Special Offer
£16.45

SOUND IN THE ROOM OF EXCEPTIONAL QUALITY
1 YEAR WARRANTY

Use on walls, floors, ceilings, cupboards, cabinets, doors, partitions, caravans, cars, boats, indoors and outdoors, in corrosive atmosphere - underwater, swimming, diving.

Impedance: 8 Ohms
Freq. Response: 100-17000 Hz
Max. Rating: 15 W r.m.s.
30 W IHFM
Min 2 W for background level music

Weight: 2lb
Size: 4" dia. x 1 1/2".
No expensive cabinet needed.
No cutting out required.
Concealed mounting.
Full instructions provided.

Mail Order Only
Cheques/P.O./M.O. with order/letter.
Payable to: PROLOG SERVICES LTD.
Postage & Packing 30p extra
Allow 14 days for delivery.
Money refunded if Transducer returned undamaged within 14 days of despatch.

Sole European Distributors
PROLOG SERVICES LTD.
PROLOG HOUSE,
FLAWBOROUGH,
NOTTM. NG13 9PA
Tel: Watton 50681

MAINS TRANSFORMERS. 240-250v. input Deduct 10% from total bill for more than one transformer.

- A. 100v. at 100ma. 35p (20p)
- B. Charger 12v. at 1A, 80p (20p)
- C. 200v. at 50ma. & 6-3v. at 1A, 35p (20p)
- D. 250v. at 50ma., 22v. at 1A, 6-3v. at 2A, 75p (25p)
- E. 250v. at 50 ma., & 6-3v at 1A, 50p (20p)
- F. 19v. & 30p (15p). G. 19v. 2A, 75p (20p)
- H. 90v. at 100ma., & 220v. at 50ma. 35p (20p)

Copper laminate board 11" x 5" x 1/4". Five for £1 (post 15p). 5" 3-ohm speaker 60p (post 15p); DULCI 207 stereo amp. £19 (50p post); SGB-audio amp. modules EA 1000 with handbook, 3 W. into 15-ohm each amp. Two for 24-25 (post 20p).



STEREO AMPLIFIER 2 x 3W. Printed circuit. Valves E280 & 2 ECL82. Liquidated stock of well-known manufacturer. Front panel 12" x 2". Chassis 9" x 3". Controls on-off, balance, ganged vols., ganged tones; for 200-250v. a.c. Output transformers for 3-ohm speakers. With knobs. Also available for 110v. a.c. Only £8 (p. & p. 50p) 110v. type £5 plus post.



MW/LW TRANSISTOR RADIO

Complete set of parts for this MW/LW Transistor Radio. Coverage 192-555m + 1070-1870m. 9 volt 6 transistor superhet using 3 AF17 in RF and IF stages powered by a two stage AF amplifier using 3 x AC128. Output approx. 500mW. Also works off car-aerial. Ply case, rexine covered. Requires PP7 battery, price 27p extra. 3 1/2" high-quality speaker. Price £6 plus 40p. P. & P.

POWER SUPPLIES (A) 3, 4 1/2, 7 1/2 & 9v. 400ma. £3-50. (B) 3, 4 1/2, 6, 7 1/2, 9 & 12v. 500ma. £4-25. (C) Car Adaptor, Neg. earth only 12v. input (11v. to 16v.), output 6, 7 1/2, 9v. 450ma. £5-60. Add post 20p one item, 30p for two.

METAL FILM RESISTORS 1 watt 27-ohm to 2-7m. (E12 5% range) 1p each Minimum order 50p. Post paid.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants (Closed Wednesday)

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 12 $\frac{1}{2}$ np in £ for postage and handling
MINIMUM CHARGE 15np. No C.O.D. orders accepted
Please note that the valves offered below are not necessarily of U.K. origin

0A2	0.40	6AR6	0.85	6F5	0.75	6Y6G	0.80
0A3	0.48	6AR11	1.25	6F6G	0.45	7Y4	0.75
0B2	0.40	6AS5	0.50	6F11	0.50	9BW6	0.70
0B3	0.70	6AS7G	0.85	6F13	0.50	10D1	0.85
0C3	0.40	6AV6	0.75	6F14	0.70	10D1	0.85
0D2	0.40	6AL6	0.20	6F15	0.65	10D3	0.65
1B3GT	0.45	6AV6	0.40	6F18	0.50	10F1	0.75
1L4	0.25	6AW8A	0.85	6F23	0.90	10F9	0.85
1R4	0.50	6BA6	0.28	6F24	0.80	10P18	0.80
1R5	0.45	6B66	0.32	6F25	1.00	10L1	0.80
1R4	0.30	6B76	0.55	6F26	0.85	10L11	0.70
1R5	0.30	6B16	0.55	6F28	0.70	10P13	0.75
1P4	0.30	6B16	0.55	6GK6	0.60	12AB5	0.70
1U4	0.40	6BK7A	0.75	6J4	0.60	12AC8	0.60
1U5	0.75	6BN5	0.43	6J5GT	0.40	12AD6	0.60
1V2	0.55	6BN6	0.60	6J6	0.80	12AP8	0.60
1X2B	0.65	6BQ5	0.25	6J7	0.45	12AL7	0.55
2P21	0.40	6BQ7	0.75	6K47T	0.60	12AQ9	0.50
3A4	0.45	6B87	1.35	6K67	0.75	12AT6	0.40
3A5	0.75	6BW6	0.30	6K7	0.43	12AT7	0.40
3BP1	3.50	6BW7	0.90	6K8G	0.45	12AT6	0.45
384	0.40	6BX6	0.25	6K25	0.75	12A17	0.33
3V4	0.65	6BZ6	0.45	6L6GT	0.55	12AV6	0.45
6H4GT	0.75	6C4	0.85	6L7	0.45	12AW7	0.70
6U4G	0.40	6C6T	0.75	6L18	0.50	12AX7	0.32
5V4G	0.45	6CDB	0.40	6LD20	0.50	12AY7	0.75
5Y3GT	0.40	6CD6A	0.40	6N7GT	0.55	12B4A	0.65
5Z3	0.75	1.80		6P25	1.50	12BA6	0.45
5Z4G	0.45	6CG7	0.80	6P28	0.65	12BA7	0.50
6/30L3	0.90	6CH6	0.80	6Q7	0.50	12B36	0.50
6AB4	0.45	6C16	0.60	6Q7	0.45	12A17	0.70
6AF4	0.80	6C16	0.60	6S7	0.45	12BQ9	0.50
6AG5	0.25	6CV4	0.70	6S7G	0.45	12B77	0.65
6AG7	0.45	6CY5	0.50	6SK7	0.50	12K5	0.60
6AH6	0.60	6C77	0.75	6SL7GT	0.45	12K7G	0.50
6AJ8	0.30	6D2	0.55	6SN7GT	0.45	12Q7G	0.65
6AK5	0.40	6D6C	0.80	6S8Q	0.50	12R7	0.50
6AK6	0.60	6D6C	0.75	6S8Q	0.50	20D1	0.80
6AL3	0.43	6D6GB	0.75	6S8Q	0.50	30L13	1.10
6AL5	0.22	6D84	1.25	6T4GT	0.70	30P1	0.50
6AM5	0.40	6EA8	0.65	6U5G	0.75	20P4	1.10
6AM6	0.37	6E47	0.30	6U8A	0.48	20P5	1.20
6AQ5	0.42	6E7H	0.35	6V6GT	0.45	25C6	0.80
6AQ6	0.70	6E7G	0.30	6X4	0.40	25L6GT	0.50
6AR5	0.55	6F1	0.75	6X5GT	0.45	25Z6	0.50
				6X8	0.85	25ZGT	0.75

First Quality Fully Guaranteed



ELECTRONIC VALVES

30A5	0.60	50CD6G	1.20	DL96	0.55	ECC88	0.40
30A1E3	0.40	50ZH5	0.65	DM70	0.80	ECC95	0.50
30C1	0.30	60L6GT	0.80	EM160	0.85	ECC97	0.65
30C15	1.00	85A2	0.55	EY51	0.55	ECC189	0.65
30C17	1.10	90A2	2.40	DY86	0.35	ECC807	1.00
30C18	0.90	90AV	2.50	DY87	0.38	ECC80	0.35
30F5	1.00	90C1	0.75	E88CC	0.70	ECP87	0.50
30FL1	0.90	90CV	2.40	E180F	1.00	ECP89	0.45
30FL2	1.10	807	0.50	E180F	0.90	ECH42	0.75
30FL14	0.90	E18	4.00	EABC500.38		ECH81	0.30
30L1	0.40	866A	0.85	EAF43	0.60	ECH83	0.45
30L15	0.95	5642	0.70	EBC23	0.60	ECH84	0.45
30L17	0.95	6080	1.75	EBC41	0.85	ECL80	0.50
30L18	1.00	6146	1.60	EBC81	0.33	ECL81	0.50
30P19	0.95	6146B	2.50	EBC82	0.48	ECL82	0.55
30PL1	0.95	6360	1.25	EBE83	0.40	ECL83	0.70
30PL13	1.10	6939	2.25	EBF89	0.32	ECL84	0.55
30PL14	1.25	7199	0.85	EBL31	1.50	ECL85	0.55
30A3	0.60	7360	2.20	EC53	0.50	ECL85	0.40
35A5	0.75	7586	1.50	EC86	0.60	ECL800	
35B5	0.65	7895	1.50	EC88	0.50	EY81	0.40
35C5	0.80	A2293	2.20	EC90	0.85	EF37A	2.20
35D5	0.75	AZ1	0.60	EC92	0.50	EF40	0.50
35L6GT	0.75	AZ31	0.55	EC93	0.60	EF41	0.65
36W4	0.40	CBL1	0.90	ECC25	1.00	EF49	0.70
36Z3	0.75	CBL31	1.00	ECC40	0.70	EF80	0.30
36Z4G	0.40	CY31	0.50	ECC81	0.40	EF85	0.35
36ZGT	0.70	DAF96	0.50	ECC23	0.33	EF86	0.30
50A5	0.50	DF96	0.50	ECC33	0.33	EF89	0.28
50B5	0.70	DK92	0.70	ECC84	0.30	EF91	0.37
50C5	0.60	DK96	0.60	ECC85	0.40	GT1C	3.00

EF92	0.35	GY501	0.70	PF86	0.70	U282	0.55
EF95	0.40	GZ30	0.45	PF818	1.00	U301	0.55
EF97	0.65	GZ31	0.40	FL300	0.65	U403	0.70
EF98	0.75	GZ32	0.50	FL303	0.60	U404	0.70
EF183	0.30	GZ33	0.75	PL36	0.55	U801	0.60
EF184	0.35	GZ34	0.60	PL31	0.50	UABC80	
EF804	1.25	HABC800.55	PL82	0.45			0.40
HK90	0.32	HK90	0.50	PL83	0.45	UAF41	0.70
EL33	1.50	KT66	2.35	PL84	0.40	UAF43	0.60
EL34	0.50	KT88	2.25	PL302	0.95	UB41	0.65
EL36	0.50	N78	1.80	PL304	0.75	UBC41	0.55
EL37	1.70	PAB380.40	PL609	0.90	UBC81	0.45	
EL41	0.75	PC86	0.60	PL509	1.10	UBF80	0.40
EL81	0.55	PC88	0.60	PL801	1.00	UBF89	0.40
EL83	0.60	PC92	0.05	PL802	0.95	UBL1	0.70
EL84	0.25	PC87	0.50	PL84	0.60	UBL21	0.70
EL85	0.45	PC900	0.45	PY91	0.35	UC92	0.45
EL86	0.40	PC84	0.40	PY33	0.83	UC85	0.45
EL90	0.42	PC85	0.40	PY80	0.40	UC80	0.70
EL95	0.35	PC88	0.55	PY81	0.30	UC81	0.60
EL821	0.60	PC89	0.55	PY82	0.35	UCH42	0.70
EL832	1.40	PC189	0.80	PY83	0.38	UCH81	0.40
EL180	0.75	PC805	0.65	PY88	0.40	UC84	0.60
EM34	1.00	PC806	0.85	PY800	0.47	UC182	0.35
EM71	0.80	PC890	0.30	PY801	0.50	UC183	0.65
EM80	0.45	PCF82	0.35	PZ30	0.38	UF9	0.65
EM81	0.60	PCF84	0.60	QQV02-6		UF11	0.60
EM83	0.50	PCF86	0.60			UF41	0.65
EM84	0.35	PCF87	1.10	QQV03-10		UF42	0.65
EM85	1.00	PCF80	1.50			UF43	0.65
EM87	0.70	PCF803	0.50	QQV03-20A		UF80	0.35
EN91	0.40	PCF805	0.90			UF85	0.40
EY51	0.40	PCF806	0.75	TT21	3.40	UF89	0.40
EY80	0.75	PCF808	0.90	TT22	3.50	VL41	0.65
EY81	0.40	PCF2000.70	U1820	0.75		UL84	0.43
EY85	0.55	PCL81	0.50	U25	0.85	UM84	0.38
EY86	0.40	PCL82	0.35	U26	0.85	UYN1	0.50
EY87	0.43	PCL83	0.65	U31	0.70	UY11	1.00
EY88	0.43	PCL84	0.45	U37	0.50	UY41	0.48
EZ40	0.50	PCL86	0.45	U52	0.40	UY82	0.50
EZ41	0.75	PCL88	1.25	U76	0.40	UY85	0.40
EZ80	0.28	PCL800	1.10	U78	0.40	WY29	0.75
EZ81	0.29	PCL801	0.95	U191	0.75	Y63	0.75
		PD500	1.30	U201	0.50	Z803U	1.35
				U281	0.55		

TRANSISTORS

2N696	0.15	AC128	0.15	BD121	0.65
2N697	0.15	AC132	0.35	BD123	0.80
2N698	0.30	AC153	0.20	BD124	0.30
2N706	0.70	AC154	0.15	BD131	0.75
2N706	0.10	AC157	0.17	BD132	0.80
2N708	0.13	AC169	0.10	BF115	0.20
2N763	0.25	AC169	0.10	BF167	0.19
2N763	0.25	AC167	0.17	BF173	0.20
2N922	0.20	AC187	0.25	BF179	0.30
2N950	0.20	AC188	0.25	BF180	0.30
2N997	0.30	AC177	0.25	BF181	0.30
2N1131	0.25	ACY18	0.20	BF184	0.20
2N1132	0.25	ACY19	0.25	BF185	0.20
2N1184	1.25	AC190	0.20	BF194	0.14
2N1308	0.17	ACY21	0.20	BF195	0.14
2N1308	0.17	ACY22	0.10	BF196	0.12
2N1304	0.20	AD140	0.60	BF197	0.12
2N1305	0.20	AD149	0.45	BF200	0.35
2N1306	0.25	AD161	0.35	BFW57	0.25
2N1307	0.25	AD162	0.35	BFW88	0.20
2N1308	0.25	AD163	1.25	BFW89	0.20
2N1309	0.25	AD212	1.25	BFV91	0.20
2N1613	0.17	AF114	0.17	BFX88	0.20
2N1711	0.20	AF115	0.17	BFY17	0.40
2N1756	0.20	AF116	0.17	BFY19	0.25
2N2147	0.75	AF117	0.17	BFY50	0.20
2N2160	0.80	AF118	0.30	BFY51	0.20
2N2217	0.20	AF125	0.20	BFY52	0.20
2N2218	0.20	AF127	0.20	BSY26	0.17
2N2219	0.20	AF180	0.35	BSY27	0.15
2N2369A	0.15	AF181	0.35	BSY28	0.17
2N2477	0.65	AF186	0.40	BSY65	0.20
2N2548	0.40	AF239	0.38	BSY95A	0.12
2N2905	0.25	AFZ11	0.45	OC16	0.50
2N2923	0.12	AFZ12	1.00	OC22	0.50
2N2924	0.13	ASV26	0.25	OC23	0.60
2N2926	0.10	ASV27	0.30	OC24	0.60
2N3053	0.20	ASV28	0.25	OC25	0.35
2N3054	0.50	ASY29	0.30	OC26	0.25
2N3055	0.40	ASY54	0.25	OC28	0.50
2N3133	0.25	ASZ15	0.70	OC29	0.50
2N3134	0.25	ASZ16	0.70	OC35	0.50
2N3391	0.17	ASZ17	0.75	OC36	0.45
2N3392	0.17	ASZ18	0.75	OC42	0.20
2N3393	0.15	ASZ19	0.25	OC44	0.15
2N3394					

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes


That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn. Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.
 "My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

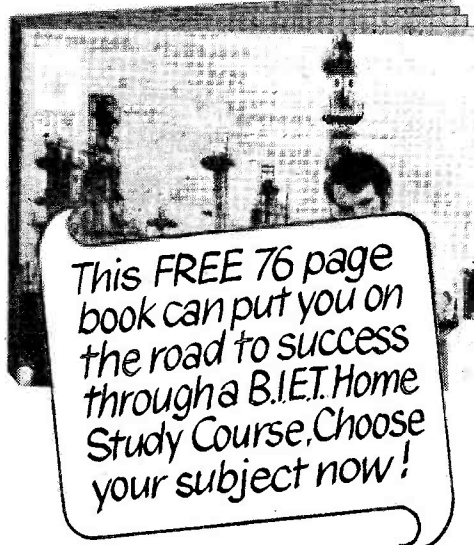These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T., Dept. BPW1 Aldermaston Court, Reading RG7 4PF




This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

- | | | |
|--|--|---|
| <p>MECHANICAL
 A.M.S.E. (Mech.)
 Boiler Inspection & Operation
 C & G Eng. Crafts
 C & G Fabrication
 Diesel Eng.
 Eng. Inspection
 Eng. Metallurgy
 Inst. Eng. & Tech.
 Inst. Motor Ind.
 Maintenance Eng.
 Mechanical Eng.
 Sheet Metal Work
 Welding</p> | <p>Man. Prod.—cont.
 Salesmanship
 Storekeeping
 Work Study
 Works Management
 DRAUGHTSMANSHIP
 A.M.I.E.D.
 Design of Elec. Machines
 Die & Press Tool Design
 Electrical Draughtsmanship
 Gen. Draughtsmanship
 Jig & Tool Design
 Technical Drawing</p> | <p>Constructional-cont.
 Building Drawing
 Building Foreman
 Carpentry & Join.
 Civil & Municipal Engineering
 Constructional Engineering
 Construction Surveyors
 Insulators
 Clerk of Works
 Council Eng.
 Geology
 Health Eng.
 Heat & Vent.
 Hydraulics
 Inst. of Builders
 Inst. Clerk of Works
 Inst. Works & Highway Supers.
 Painting & Dec.
 Public Hygiene
 Road Engineering
 Structural Eng.
 Surveying</p> |
| <p>ELECTRICAL & ELECTRONIC
 A.M.S.E. (Elec.)
 C & G Elec. Eng.
 C & G Elec. Inst.
 C & G Elec. Tech.
 Computer Elect.
 Elec. Maths
 Elec. Science
 Electronic Eng.
 Electrical Eng.
 Install. & Wiring
 Meters & Measuring Instruments</p> | <p>MANAGEMENT & PRODUCTION
 Automatic Control
 Computer Prog.
 Electronic Data Processing
 Estimating
 Foremanship
 Inst. Cost & Works
 Accountants
 Inst. Marketing
 Management
 Metrication
 Motor Trade Man.
 Network Planning
 Numerical Control
 Operational Research
 Personnel Man.
 Planning Eng.
 Production Eng.
 Quality Control</p> | <p>RADIO & TELE-COMMUNICATIONS
 Colour TV
 C & G Radio/TV/ Electronics
 C & G Telecomm. Tech.
 Prac. Radio & Elec. (with kit)
 Radio Amateurs Exam.
 Radio Servicing & Repairs
 Radio & TV Eng.
 Transistor Course
 TV Main. & Serv.</p> |
| | <p>AUTO & AERO
 Aero Eng.
 A.M.I.M.L.
 A.R.E. Cert.
 Auto Engineering
 Auto Repair
 C & G Auto. Eng.
 Garage Management
 MAA/IMI Diploma
 Motor Vehicle Mechanics</p> | <p>GENERAL
 Agricultural Eng.
 Council of Eng. Inst.
 Farm Science
 General Education
 Gen. Plastics
 Pract. Maths
 Pract. Slide Rule
 Pure & Applied Maths
 Refrigeration
 Rubber Technology
 Sales Engineers
 Tech. Report Writing
 Timber Trade University Ent.</p> |

G.C.E.
 58 'O' & 'A' LEVELS SUBJECTS
 Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

	To B.I.E.T., Dept. BPW1 Aldermaston Court, Reading RG7 4PF	CU BPW1
NAME _____		
Block Capitals Please		
ADDRESS _____		
SUBJECT OF INTEREST _____		
AGE _____		
Accredited by the Council for the Accreditation of Correspondence Colleges.		
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY		

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kington Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2-8-0.
 PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

U.K.'s LARGEST ELECTRONICS CENTRES!

HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.

NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381
354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736
309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963
303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1BW



ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.


BUILD THE TEXAN

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

★ **FREE TEAK CABINET** with complete kits!

FEATURES. New slim design with 6 - IC's, IC sockets, 10 silicon transistors 4 resistors, 25p. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work. HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

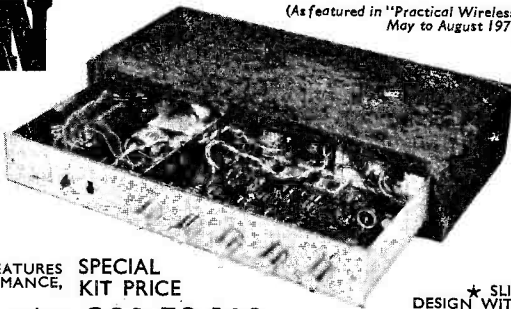FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request). Constructional details Ref. No. 21 30p



(As featured in "Practical Wireless" May to August 1972)


SPECIAL KIT PRICE
£28-50 P & P
45p

★ SLIM DESIGN WITH SILVER TRIM
Overall chassis size 14 1/2" x 6" x 2" high

COMPLETE WITH FREE TEAK CABINET

Designer approved kits distributed by Henry's!

LOW COST HI-FI SPEAKERS

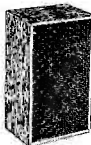

E.M.I. Size 13 1/4" x 8 1/2" Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms. £2-20. Post 22p.
TYPE 150 TC Twin cone version £2-75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3-85. Post 25p.
TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7-70. Post 28p.



POLISHED CABINETS 150, 150TC 450 £4-60. Post 30p. ASSEMBLED IN POLISHED CABINETS (8 ohms) SERIES 6 (Assembled 150 TC) per pair £16-50. Post 70p SERIES 8 (Assembled 450) per pair £18-95. Post 70p

ML-3 MW/LW TUNER TO BUILD



Uses Mullard Module. Slow motion tuning. Built in battery. Over aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4-85. Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bands for extra selectivity. Also slow motion geared tuning, 600 mV push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7-98, p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed. PRICE 55p Post Paid (40p FOR CALLERS)

PLUS! FIV 10p VOUCHERS

Send to this address—HENRY'S RADIO LTD. (Dept. FAW) ALBEMARLE WAY, LONDON, E.C.1. — for catalogue by post only. All other mail and callers to "303" see above.




TEST EQUIPMENT

Just a selection!
SE250B Pocket Pencil Signal Injector £1-90
SE500 Pocket Pencil Signal Tracer £1-50
THL33D Robust 2K/Volt £4-55 with case £4-95
TE15 Grid Dip Meter 440 KHz-280 mHz £13-45
500 30 K/V Multimeter £9-25
With leather case £10-50
200H 20K/V Multimeter £4-20. With case £4-95
AF105 50K/V Multimeter £8-50. With case £9-50
U4341 AC/DC Multimeter with transistor tester with steel case £10-50
TE20D RF Generator 120KHz-500MHz £15-95. Carr. 35p
TE22D Audio Generator 20Hz-200KHz £17-50. Carr. 35p
CI-5 3" Pulse Scope 10Hz-10mHz £39-00. Carr. 50p
TE65 Valve Voltmeter 28 ranges £17-50. Carr. 40p
ALL NOMBREX MODELS IN STOCK



PA-DISCO-Lighting

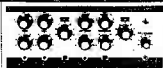
UK's Largest Writing phone or call in. Details and demonstrations on request.



DJ30L 3 Channel sound to light unit, 3kW. £29-75
DJ40L 3 channel Mic (built-in) to light, 3kW. £38-75
DJ70S 70 watt Disco amp/mixer. £49-95
DISCOAMP 100 watt amp/mixer, £66-50
DJ105S 30 watt amp/mixer, £32-75
Anti-Feedback Unit, Mic. £11-50
DJ500 50 watt PA Amplifier £44-00
GROUP 300 150 watt rms "Group" Valve Amplifier £86-00
FIBRE OPTICS LIGHTING. — MICS. EFFECTS. PROJECTORS. SPOTS. DIMMERS — STANDS. MIXERS. SPEAKERS. Everything for PA — Disco — Lighting. FREE Stock List Ref. No. 18
● PORTABLE DISCOS — DETAILS ON REQUEST
● CREDIT TERMS FOR CALLERS

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6-97, p.p. 20p. Decoder Kit £5-97. Tuning meter unit £1-75. Mains unit (optional) Model PS900 £2-47. Post 20p. Mains unit for Tuner and Decoder PS6/12 £3-25. Post 20p

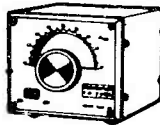

SINCLAIR PROJECT 60 MODULES — SAVE POUNDS!

Z30 £3-57; Z50 £4-37
STEREO 60 PZ5 £3-97
£7-97; PZ8 £4-77
PZ6 £6-37;



PACKAGE DEALS

Transformer for PZ8 £2-95
2xZ30, Stereo 60, PZ5 £15-95
2xZ30, Stereo 60, PZ6 £18-00
2xZ30, Stereo 60, PZ8 £20-25
Transformer for PZ8 £2-95
PROJECT 605 KIT £19-95

RECORD DECKS
CHASSIS (POST 50p)
SP25/3 £10-25 HT70 £14-50
MP60 £3-95 MP610 £12-95
AP76 £17-95 GL75 £28-30
PLINTH/COVERS (State Model)
SP25/MP60/610 £3-30 post 40p
AP76 £4-50 post 40p
CART/PLINTH/COVER (Post 70p)
(HL) MP60/G800H/PC £18-50
MP610/SC5MD/TPD2/PC £19-95
AP76/M7565M/PC £32-50
AP96/M7565M/PC £39-95
(HL) AP76/G800/PC £28-95
(HL) SP25/G800H/PC £18-95
HT70/G800/TPD1/PC £24-50
(HL) 2025/9TAHCD/PC £13-95
MP60/SC5MD/PC £17-25
(HL) GL75/G800E/PC £41-95
(HL) GL75/G800/PC £38-95

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal for remote switching and signalling. Complete with data and circuits. £5-90 per pair. Post 10p

MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO
'17' High Impedance £2-00
'18' Med. Impedance £2-00
'36' Med.-Low Imp. £3-50
Erase Heads for above 75p
'63' 2 track mono—£1-75
Hi Imp.
'43' Erase Head for above 75p

POWER INTEGRATED CIRCUITS

Plessey SL403D—3 watt with 8-page data, layouts and circuits £1-50. P.C. Board 60p. Heat Sink 14p. Sinclair IC12—6 watt with data and circuits £1-80. TH9013P—20 watt Power Amp Module £4-57. TH9014P-IC Preamp £1-50. Data/Circuits for above No. 42 10p

7 SEG & NIXIE TUBES

(Post 15p per l to 6)
XN3, XN13, GNE 0-9 side view with data 85p.
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
3015F 7 seg £2 each. £7 per 4 with data.
12 and 24 hour clock circuits Ref. No. 31 15p.

Miniature Amplifier

5 transistor. 300mW o/p. Fitted volume and sensitivity control, 9 volt operated. £1-75 each P/P 15p.

Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. SK 10K, 25K, 100K, 250K, 500K.
1 meg, Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged. 60p each.

Hi-Fi & Tape Equipment

Acknowledged as U.K.'s Largest Stockists with Lowest Prices Plus 12 months Guarantee. Write or call for FREE 16 page lists (Ref. N. 17)

Transistors - IC's - SCR's - Rectifiers - Triacs, etc. LATEST BROCHURE Ref. No. 36 on request, or see our earlier page.

MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S
All the parts you need plus Data and Circuits — Get a Catalogue — it's all in there!
Prices subject to change without notice E. & O.E.

309/354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H